

PRACTICAL

ELECTRONICS

AUGUST 1975


30p

BIG SOUND

for
the
small
screen...

T.V. SOUND SEPARATOR

FOR USE WITH HI-FI SYSTEMS

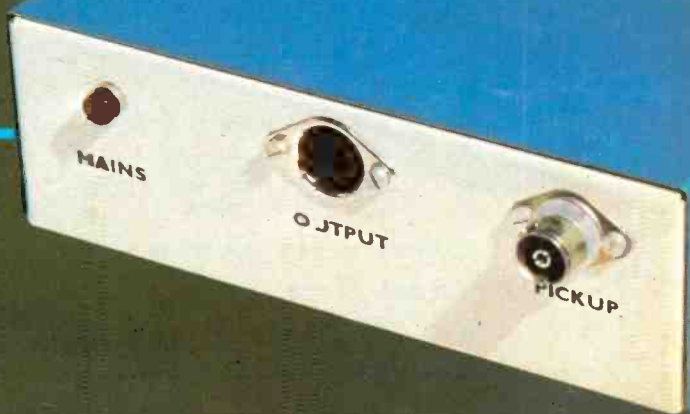

NEW EDU-KIT MAJOR

**COMPLETELY SOLDERLESS ELECTRONIC CONSTRUCTION KIT
BUILD THESE PROJECTS WITHOUT SOLDERING IRON OR SOLDER**

- 4 Transistor Earpiece Radio
- Signal Tracer
- Signal Injector
- Transistor Tester NPN -PNP
- 4 Transistor Push Pull Amplifier
- 5 Transistor Push Pull Amplifier
- 7 Transistor Loudspeaker Radio MW/LW
- 6 Transistor Short Wave Radio
- Electronic Metronome
- Electronic Noise Generator
- Batteryless Crystal Radio
- One Transistor Radio
- 2 Transistor Regenerative Radio
- 3 Transistor Regenerative Radio
- Audible Continuity Tester
- Sensitive Pre-Amplifier

Components include:

- 24 Resistors
- 21 Capacitors
- 10 Transistors
- 3 1/2" Loudspeaker
- Earpiece
- Mica Baseboard
- 3 12-way Connectors
- 2 Volume Controls
- 2 Slider Switches
- 1 Tuning Condenser
- 3 Knobs
- Ready Wound MW/LW/SW Coils
- Ferrite Rod
- 61 yards of wire
- 1 yard of sleeving, etc.
- Parts price list and plans 65p (free with parts)

TOTAL BUILDING COSTS

£7-23 P.P. & Ins. 58p
(Overseas Seamail P. & P. £3-40)
(+25% VAT £1-80)

ROAMER TEN

Mk. II

WITH VHF INCLUDING AIRCRAFT



Now with free earpiece and switched socket.

10 TRANSISTORS. 9 TUNABLE WAVE BANDS. MW1, MW2, LW, SW1, SW2, SW3. TRAWLER BAND. VHF AND LOCAL STATIONS. ALSO AIRCRAFT BAND


Latest 4" 2 watt Ferrite Magnet Loudspeaker. Built-in ferrite rod aerial for MW/LW. Chrome plated 6 section telescopic aerial, can be angled and rotated for peak short wave and VHF listening. Push-pull output using 600mW transistors. Car Aerial and tape record sockets. 10 transistors plus 3 diodes. Ganged tuning condenser with VHF section. Separate coil for Aircraft Band. Volume/on/off, wave change and tone controls. Attractive case in black with silver blocking. Size 9in x 7in x 4in. Easy to follow instructions and diagrams. Parts price list and plans 50p (FREE with parts).

TOTAL BUILDING COSTS **£9-50** P.P. & Ins. 65p
(Overseas Seamail P. & P. £3-50)
(+25% VAT £2-37)

POCKET FIVE

NOW WITH 3" LOUSPEAKER

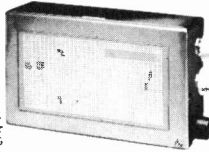3 Tunable wavebands. MW/LW and Trawler Band. 7 stages, 5 transistors and 2 diodes. supersensitive ferrite rod aerial, attractive Black and Gold Case. Size 5 1/2in x 4 1/2in x 3 1/2in approx. Plans and parts price list free with parts.



Total Building Costs **£2-95**
(+25% VAT 75p)
P.P. & Ins. 38p
(Overseas Seamail P. & P. £2-30)

ROAMER EIGHT

Mk. I

NOW WITH VARIABLE TONE CONTROL



7 TUNABLE WAVEBANDS:

MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Built-in ferrite rod aerial for MW and LW. Chrome plated telescopic aerial can be angled and rotated for peak short-wave listening. Push-pull output using 600mW transistors. Car aerial and tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Latest 4" 2 watt Ferrite Magnet loudspeaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9in x 7in x 4in approx. Easy to follow instructions and diagrams. Parts price list and plans free with parts.

TOTAL BUILDING COSTS **£6-98** P.P. & Ins. 65p
(Overseas Seamail P. & P. £3-50)
(+25% VAT £1-75)

NEW JIFFY TESTER

Easy to build and operate, fits in the pocket. A quick checker for continuity of resistors, chokes, diodes, transistors, circuit wiring (not mains) and loudspeakers. Also for checking short circuits of capacitors, tuning capacitors and many other uses not listed here. See instruction sheet free with kit.

Complete with earpiece, jack plug and socket, resistors, capacitors, components, etc. Parts Price List and Easy Build Plans free with Parts.

Total Building Costs

£2-25 (+25% VAT 56p)
P.P. & Ins. 22p (Overseas Seamail P. & P. £1-70)

NEW EVERYDAY SERIES EV6




Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/4 x 2 1/2ins. approx. 6 Transistors and 3 diodes. Powered by 9 volt Battery. Ferrite rod aerial, 3" loudspeaker, etc. MW/LW coverage. Push Pull Output. Parts price list and plans free with parts.

TOTAL BUILDING COSTS **£3-98** P.P. & Ins. 50p
(Overseas Seamail P. & P. £2-30)
(+25% VAT £1-00)

TRANS EIGHT

8 TRANSISTORS AND 3 DIODES

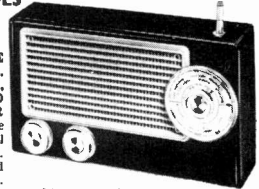

6 TUNABLE WAVEBANDS. MW, LW, SW1, SW2, SW3 AND TRAWLER BAND. Sensitive ferrite rod aerial for MW and LW. Telescopic aerial for short waves.

3in speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9in x 5 1/4in x 2 1/2in approx. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans free with parts.


TOTAL BUILDING COSTS **£4-78** P.P. & Ins. 50p
(Overseas Seamail P. & P. £2-50)
(+25% VAT £1-20)

"Edu-Kit"

Build Radios, Amplifiers, etc., from easy stage diagrams. Five units including master unit to construct.

Components include: Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine tone 3" moving coil Speaker: Terminal Strip: Ferrite Rod Aerial: Battery Clips: 4 Tag Boards: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1in Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans free with parts.

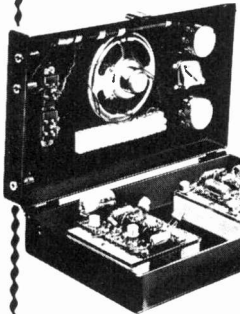TOTAL BUILDING COSTS **£5-50** P.P. & Ins. 50p
(Overseas Seamail P. & P. £3-40)
(+25% VAT £1-37)



★ Callers side entrance "Lavelis" shop
★ Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

RADIO EXCHANGE LTD

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD MK40 1SA
Tel. 0234 52387 Reg. No. 788372

I enclose £..... for.....

- | | | | |
|--------------|--------------------------|---------------|--------------------------|
| ROAMER TEN | <input type="checkbox"/> | EV6 | <input type="checkbox"/> |
| ROAMER EIGHT | <input type="checkbox"/> | TRANS EIGHT | <input type="checkbox"/> |
| JIFFY TESTER | <input type="checkbox"/> | MAJOR EDU-KIT | <input type="checkbox"/> |
| POCKET FIVE | <input type="checkbox"/> | EDU-KIT | <input type="checkbox"/> |

Name

Address

PRACTICAL ELECTRONICS

VOLUME 11 No. 8 AUGUST 1975

CONSTRUCTIONAL PROJECTS

- TV SOUND SEPARATOR** *by D. S. Gibbs & I. M. Shaw* 630
Improve the quality of your television sound
- DIGITAL CLOCK** *by A. J. Sutton* 636
A 12 or 24 hour unit with a large easy-to-read display
- P.E. JOANNA—4** *by A. J. Boothman* 650
Circuits and construction of the voice filters
- 8-CHANNEL LOGIC TRACE MULTIPLIER** *by A. C. Ainslie* 664
Eight channels of logic information displayed on an oscilloscope

GENERAL FEATURES

- SEMICONDUCTOR UPDATE** *by D. W. Coles* 644
A review of interesting devices
- TRANSDUCERS—5** *by P. R. Allcock* 647
Considering piezoelectricity and its applications
- THE TRANSISTOR AS A ZENER** *by I. D. Evans* 660
Making use of the Zener effect in transistors
- INGENUITY UNLIMITED** 670
Heads or Tails—Display for Digital Alarm Clock—Fuzz Effect—Coin Toss—Versatile Flasher/Pulser

NEWS AND COMMENT

- EDITORIAL**—Victims of V.A.T. 629
- NEWS BRIEFS** 674
Tifax—Oh Buoy—Tigerfish—Disappearing handmark
- SPACEWATCH** *by Frank W. Hyde* 635
Mercury Fly-Past
- STRICTLY INSTRUMENTAL** *by K. Lenton-Smith* 643
Electronics and music
- LONDON ELECTRONIC COMPONENT SHOW** 658
Some of the highlights of the 1975 show
- BOOK REVIEWS** 634
Selected new books we have received
- INDUSTRY NOTEBOOK** *by Nexus* 677
What's happening inside industry
- PATENTS REVIEW** 678
Thought provoking ideas on file at the British Patent Office

Our September issue will be published mid-August, 1975

© IPC Magazines Limited 1975. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Publisher's Subscription Rate including postage for one year, Inland £4.80, Overseas £5.00. USA and Canada \$13.50. International Giro facilities Account No. 5122007. State reason for payment, "message to payee".



CHINAGLIA



THE **MINOR** PROFESSIONAL QUALITY TEST EQUIPMENT

WITH

33 RANGES
20k Ω /V d.c.
4k Ω /V a.c.


- ROBUST CLASS 1.5 PRECISION MOVEMENT
- ACCURACY 2.5% D.C. AND 3.5% A.C.
- 12 MONTH GUARANTEE
- SELF-POWERED AND POCKET-SIZED
- OPTIONAL 30KV D.C. PROBE

PRICE £19.00 inc. VAT (P. & P. 80p)
PROBE £8.80

For details of this and the many other exciting instruments in the Chinaglia range, including multimeters, component measuring, automotive and electronic instruments please write or telephone:

CHINAGLIA
(U.K.) LTD. 19 Mulberry Walk, London
SW3 6DZ Tel: 01-352 1897

TRADE ENQUIRIES WELCOMED

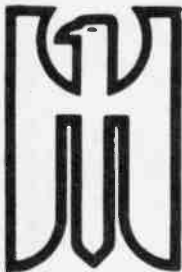

Phoenix Electronics (Solent) Ltd.

139-141 Havant Road
Drayton, Portsmouth, Hants
PO6 2AA

You already know us—get to know us better! Our catalogue is now only 20p—returnable on your first order.

Our prices on a wide range of semiconductors, i.c.'s and passive components include VAT, and, despite rising postal costs, carriage is only 20p, too!


THIS MONTH'S BARGAIN OFFER!

Rectifier kit. 4 each 1N4148, AA144, 1N4004, 1N4006, 1N5402, 1N5406, SCR 0.6A/200V, Bridge 1A/400V, Triac 2.5A/100V, + 4 voltages of 400mW Zeners — Catalogue value £10.60. Bargain pack PEP/4A—£6.50

Please send your catalogue — now!

Name _____

Address _____

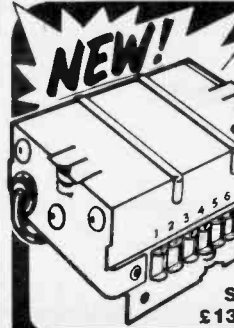


THE HOT ONE

DX FRONT END
VTO3 88-108 MHz

- * 2 DUAL GATE MOSFETS
- * SILVER CLAD CHASSIS
- * A.G.C. and A.F.C.

A 4 stage Front End. Will pull out stations which on conventional receivers would be lost in the noise.
Gain 30dB + at 100 MHz.
Noise 6.5dB Typ.

Send
£13.50

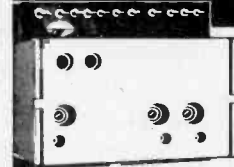

V.H.F. FRONT END/CONVERTER

- * ADVANCED DESIGN
 - * DUAL-GATE MOSFET FIRST STAGE
- Covers: AIRCRAFT · WEATHER · SATELLITES · AMATEURS

VARICAP TUNED:
Input 118-150 MHz
I.F. Output 10.7 MHz

Send £10.90

I.F.10. HIGH PERFORMANCE DE-LUXE I.F. STRIP

NOW with 70dB gain

Send £8.60

- * SHARP SKIRT SELECTIVITY
- * CONTROLLABLE SQUELCH
- * CENTRE ZERO TUNING METER + SIGNAL STRENGTH METER OUTPUT

ALL PRICES QUOTED INCLUDE VAT AND P. & P.

Send 8p + S.A.E. for Data Sheets. Sole U.K. Agents

REEDHAMPTON LTD.

182-184 Addington Road, Selsdon, Surrey CR2 8LB

ORDER DIRECT FROM THE U.S. AND SAVE

SHIPMENT MADE WITHIN 3 DAYS FROM RECEIPT OF ORDER VIA AIR MAIL - POSTAGE PAID

10% Off on orders over £10
15% Off on orders over £50
20% Off on orders over £100

TTL



7400	£0.11 p	7448	£0.80 p	74150	£0.75 p
7401	11	7450	12	74151	60
7402	11	7451	13	74153	71
7403	11	7453	13	74154	1.05
7404	13	7454	14	74155	95
7405	13	7460	11	74156	71
7406	22	7464	21	74157	71
7407	22	7465	21	74161	95
7408	14	7472	22	74163	1.05
7409	14	7473	26	74164	1.25
7410	11	7474	26	74165	1.25
7411	16	7475	41	74166	1.15
7413	35	7476	26	74173	95
7415	22	7483	70	74175	95
7416	22	7485	80	74176	95
7417	22	7486	24	74177	85
7420	11	7489	1.50	74180	80
7422	22	7490	45	74181	2.50
7423	22	7491	71	74182	80
7425	22	7492	44	74184	1.55
7426	23	7493	44	74185	1.45
7427	22	7494	49	74190	95
7430	12	7496	49	74191	95
7432	22	7496	55	74192	90
7437	25	74100	1.25	74193	85
7438	21	74105	60	74194	95
7440	11	74107	27	74195	60
7441	60	74121	32	74196	1.00
7422	55	74122	50	74197	75
7443	55	74123	55	74198	1.70
7444	60	74125	50	74199	1.70
7445	75	74126	50	74200	3.90
7446	85	74141	68		
7447	80	74145	75		

LOW POWER

74L00	£0.16 p	74L51	£0.16 p	74L90	£0.93 p
74L02	16	74L55	18	74L91	80
74L03	16	74L71	18	74L93	89
74L04	18	74L72	27	74L95	89
74L06	18	74L73	38	74L98	1.53
74L10	16	74L74	38	74L164	1.53
74L20	16	74L78	44	74L165	1.53
74L30	16	74L85	85		
74L42	89	74L86	38		

HIGH SPEED

74H00	£0.16 p	74H21	£0.16 p	74H55	£0.20 p
74H01	16	74H22	18	74H60	21
74H04	16	74H30	18	74H61	21
74H08	16	74H40	16	74H62	20
74H10	16	74H50	16	74H74	32
74H11	16	74H52	18		
74H20	16	74H53	20		

8000 SERIES

8091	£0.33 p	8214	£0.93 p	8811	£0.38 p
8092	33	8220	93	8812	60
8095	76	8230	1.42	8822	1.42
8121	49	8520	71	8830	1.42
8123	88	8551	91	8831	1.42
8130	1.20	8552	1.37	8835	1.7
8200	1.42	8554	1.37	8880	73
8210	1.92	8810	44		

9000 SERIES

9002	£0.21 p	9309	£0.49 p	9601	£0.54 p
9301	63	9312	49	9602	49

Data sheets supplied only on request. Add 25p ea. for data supplied on items less than 50p ea.

CMOS

74C00	£0.21 p	74C74	£0.63 p	74C162	£1.78 p
74C02	30	74C76	93	74C163	1.78
74C04	41	74C107	82	74C164	1.92
74C08	41	74C151	1.59	74C173	1.59
74C10	36	74C154	1.92	74C195	1.65
74C20	36	74C157	1.20	80C95	82
74C42	1.18	74C160	1.78	80C97	82
74C73	85	74C161	1.78		

8008 CENTRAL PROCESSING UNITS

8 bit single chip for micro computer systems. With specifications. £22
2102-2 1024 bit N channel static RAM for use with 8008 CPU. £2-75p

CLOSEOUT ON CALCULATOR CHIPS

These early model calculator chips have been superseded and are now offered at this lowest price ever. Complete with data.

CT5001 12 digit display and calculate, 4 function, chain operation, fixed dec. 40 pin package. **96p**
 CT5002 Same as 5001 except battery operation. **£1-23p**
 CT5005 12 digit display and calculate, 4 function plus memory. 28 pin package. **£1-70p**

WITH PURCHASE OF ANY OF THE ABOVE -

MAN 3M led display. RH common cathode. 12 character. **12 for 80p**

MEMORIES w/data

1101	256 bit RAM MOS	£0.96 p
1103	1024 bit RAM MOS	2.72
5203	2048 bit erasable PROM	13.68
5260	1024 bit RAM Low Power	2.16
7489	64 bit RAM TTL	1.50
8223	Programmable ROM	2.72

CALCULATOR & CLOCK CHIPS w/data

5001	12 DIG 4 funct fix dec	£1.46 p
5002	Same as 5001 exc btry pwr	1.95
5005	12 DIG 4 funct w/mem	2.42
MM5725	8 DIG 4 funct chain & dec	1.10
MM5736	18 pin 6 DIG 4 funct	2.42
MM5738	8 DIG 5 funct K & Mem	2.42
MM5739	9 DIG 4 funct (btry sur)	2.92
MM5311	28 pin BCD 6 dig mux	2.42
MM5312	24 pin 1 pps BCD 4 dig mux	1.94
MM5313	28 pin 1 pps BCD 6 dig mux	2.42
MM5314	24 pin 8 dig mux	2.42
MM5316	40 pin alarm 4 dig	2.42

LED & OPTO ISOLATOR

MV10B	Red TO 18	£0.14 p
MV50	Axial leads	8
MV5020	Jumbo Vis. Red (Red Dome)	18
	Jumbo Vis. Red (Clear Dome)	18
ME4	Infra red diff. dome	18
MAN-1	Red 7 seg. 270"	1.38
MAN-2	Red alpha num. 32"	2.72
MAN-4	Red 7 seg. 190"	1.18
MAN-5	Green 7 seg. 270"	1.62
MAN-6	6" high solid seg.	3.81
MAN-7	Red 7 seg. 270"	74
MAN-8	Yellow 7 seg. 270"	2.17
MAN-64	4" high solid seg.	2.45
MAN-66	6" high spaced seg.	2.55
DL 707	Red 7 seg. 3"	1.18
MCT2	Opto-iso transistor	38

DTL

930	10 p	937	10 p	949	10 p
932	10	944	10	962	10
936	10	946	10	963	10

4000 SERIES RCA EQUIVALENT

CD4001	£0.31 p	CD4013	£0.66 p	CD4023	£0.31 p
CD4009	47	CD4016	69	CD4025	31
CD4010	47	CD4017	162	CD4027	74
CD4011	31	CD4019	74	CD4030	52
CD4012	31	CD4022	1.50	CD4035	1.56

DIGITAL CIRCUITS (DIP PKG)

7448	BCD - 7 seg	
7474	Decoder/Driver (30V)	66p
7478	Dual D flip-flop	19p
74107	Dual J-K flip-flop	22p
74123	Retrig monostable multivib w/clr	39p

LINEAR CIRCUITS (DIP PKG)

380	2 watt audio amplifier	59p
3900	Quad amplifier	20p

9 DIGIT LED DISPLAY

On multiplexed substrate, comm. cathode compatible with all 8 digit calculator chips. 7 segment right hand decimal, red with clear magnifying lens. .12" character, 1 to 4 MA, 1.8V typ 2 1/2" x 3/4" x 1/8" high. **£1-95p**

LINEAR CIRCUITS



300	Pos V Reg (super 723)	TO-5	£0.43 p
301	Hi Perf Op Amp	mDIP TO-5	18
302	Volt follower	TO-5	43
304	Neg V Reg	TO-5	49
305	Pos V Reg	TO-5	52
307	Op AMP (super 741)	mDIP TO-5	38
308	Micro Pwr Op Amp	mDIP TO-5	60
309K	5V IA regulator	TO-3	74
310	V Follower Op Amp	TO-5 mDIP	65
311	Hi perf V Comp	mDIP TO-5	58
319	Hi Speed Dual Comp	DIP	71
320	Neg Reg 5.2, 12, 15	TO-3	74
322	Precision Timer	DIP	60
324	Quad Op Amp	DIP	1.07
329	Quad Comparator	DIP	92
340T	Pos Volt Reg (6V-12V-15V-18V-24V)	TO-220	1.07
370	AGC/Squelch AMPL	TO-5 or DIP	65
372	AF-IF Strip detector	DIP	44
373	AM/FM/SSB Strip	DIP	1.78
376	Pos. V Reg	mDIP	33
377	2w Stereo amp	DIP	1.47
380	2w Audio Amp	DIP	81
380.8	.6w Audio amp	mDIP	69
381	Lo Noise Dual preamp	DIP	98
382	Lo Noise Dual preamp	DIP	98
550	Pre V Reg	DIP	54
555	Timer	mDIP	44
560	Phase Locked Loop	DIP	1.94
562	Phase Locked Loop	DIP	1.94
565	Phase Locked Loop	DIP	1.20
566	Function Gen	mDIP	1.20
567	Tone Decoder	mDIP	1.20
709	Operational AMPL	DIP	27
710	Hi Speed Volt Comp	DIP	21
711	Dual Difference Compar	DIP	44
723	V Reg	DIP	38
738	Dual Hi Perf Op Amp	DIP	65
741	Comp Op AMP	mDIP TO-5	27
747	Dual 741 Op Amp	DIP or TO-5	44
748	Freq Adj 741	mDIP	27
1304	FM Muxpx Stereo Demod	DIP	65
1307	FM Muxpx Stereo Demod	DIP	45
1458	Dual Comp Op Amp	mDIP	48
LH2111	Dual LM 211 V Comp	DIP	1.07
3065	TV-FM Sound System	DIP	38
3075	FM Det LMT-R & Audio preamp	DIP	44
3900	Quad Amplifier	DIP	33
7524	Core Mem Sense AMPL	DIP	1.04
7534	Core Mem Sense Amp	DIP	1.42
8864	9 DIG Led Cath Drvr	DIP	1.37
75451	Dual Peripheral Driver	mDIP	21
75452	Dual Peripheral Driver	mDIP	21
75453	(351) Dual Periph. Driver	mDIP	21
75491	Quad Seq Driver for LED	DIP	50
75492	Hex Digit Driver	DIP	55


Data sheets supplied only on request. Add 25p ea. for data supplied on items less than 50p ea.

The prices as listed are in British pounds and pence. Send bank cheque or personal cheque with order. If international postal money order is used, send receipt with order. Minimum order £2-50p.

INTERNATIONAL ELECTRONICS UNLIMITED
 P.O. BOX 1708 MONTEREY, CA. 93940 USA
 PHONE (408) 659-3171

The above prices do not include any taxes leviable by a purchaser's country of residence

Sinclair hi-fi

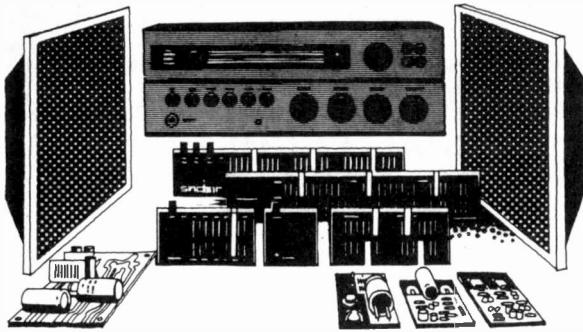

The watts...

The Sinclair range of hi-fi products. Three different ways of achieving hi-fi excellence - whatever area of hi-fi you're interested in.


And the Sinclair range fact-file gives you the full run-down on all of them.

On Project 80 - the build-as-you-please hi-fi module system.

On IC20 - the revolutionary integrated circuit amplifier kit.

And System 4000 - the luxury hi-fi amplifier and matching tuner.

and the wherefores.

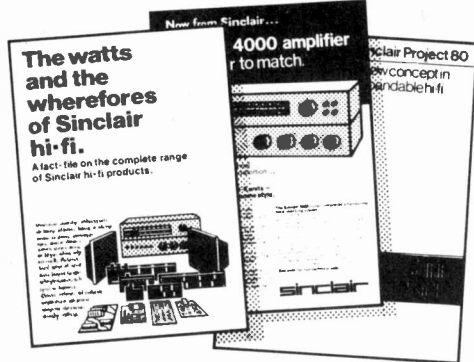

The Sinclair range fact-file shows you the whole story. Technical specifications... complete descriptions... big, clear pictures... and test reports by impartial hi-fi journals.

A real bundle of goodies.

Send for Sinclair's range fact-file - now!

See if the answer's here - the information on the component you've been looking for.

Simply cut the coupon and send it to the no-stamp-needed FREEPOST address below.

We'll send you the Sinclair fact-file - giving you all you need to know about Sinclair hi-fi. And information about a few extras you're sure to find rather interesting.

Sinclair Radionics Ltd,
London Road, St Ives,
Huntingdon, Cambs., PE17 4JH
St Ives (0480) 64646

Please send me the Sinclair range fact-file immediately

Name _____


Address _____

HF/PE/8/75

Please print

To: Sinclair Radionics Ltd,
FREEPOST, St Ives,
Huntingdon, Cambs., PE17 4BR

sinclair

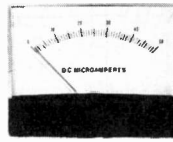

4 1/4 in x 3 1/2 in METER. 30µA, 50µA or 100µA, £3-85. 13p P. & P.

**TAPE
RECORDER
LEVEL
METER**

500µA, 70p. 10p P. & P.



**CARDIODE
DYNAMIC
MICROPHONE**

Model UD-130. Frequency response 50-15,000c/s. Impedance Dual 50K and 600 ohms, £7-40. 13p P. & P.

42 x 42mm meters 100µA, 500µA, 1mA, 500mA, £2-76. 11p P. & P.

60 x 45mm meters 50µA, 100µA, 500µA and 1mA VU meter, £2-92. 11p P. & P.

Edgewise meters 90mm x 34mm 1mA, £3-40. 13p P. & P.

**MULTI-
METER**

Model ITI-2
20,000 ohm/
volt, £6-90.
16 1/2 p P. & P.



**3 WATT STEREO (1 1/2 + 1 1/2)
PER CHANNEL
AMPLIFIER**

£4-30. 12 1/2 p P. & P.

All above prices include 8% V.A.T. LARGE S.A.E. for List No. 11. Special prices for quantity quoted on request.

M. DZIUBAS

158 Bradshawgate • Bolton • Lancs. BL2 1BA

RELAY UNIT

Smart steel case 12 x 7 x 4 1/4 in with 22 PO Type relays, most with at least 3 sets c/o contacts; 4 reed relays + coils, 2 pots, resistors, capacitors, 12BH7 valve, various diodes, tag board, etc., etc. Only £3-50.

PC ETCHING KIT MK. II

Anyhous 11b Ferric Chloride, 100 sq. in. copper clad board, DALO etch resist pen, abrasive cleaner etching dish and instructions. Now also includes 2 miniature drill bits. £3-50.

71b BARGAIN PARCELS

Hundreds of new components - pots, resistors, capacitors, switches + PC boards with transistors and diodes, also loads of odds and ends. Contents always changing. Only £3.

COMPUTER PANELS

Large quantity always available. 31b asstd. £1-80; 71b £2-85; 561b £15. Pack with about 500 components inc. at least 50 transistors £1.

FERRIC CHLORIDE

Anhydrous technical quality in 11b double sealed packs. 11b 80p; 31b £1-80; 101b £4-85; 1001b £25.

TRANSFORMERS

All mains primaries. 6-0-6V at 100mA 80p; 9-0-9V 100mA £1-82; 12-0-12V 100mA £1-06; 24-0-24V 500mA £2-20; 1A multitrapped to give 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 or 30V. also 12-0-12 or 15-0-15 £3. 2A version £4-40. 6-5-0-6-5V 500mA £1-45; 17V 1A £2. 9V 10A £3; sub-miniature 12-0-12V at 50mA 80p.

PE GAS IGNITOR KIT

All parts to build this project featured in July PE still available. Complete kit of parts + instructions only £3

All prices quoted include U.K. post and VAT at 8% or 25% as appropriate. Surplus components and equipment wanted for cash. S.A.E. for list or enquiries.

GREENWELD (PE8)

51 Shirley Park Road, Southampton, SO1 4FX. Tel. (0703) 772501. Also callers at 21 Deptford Broadway, SE8. Tel. 01-892 2009, and 38 Lower Addiscombe Road, Croydon. Tel. 01-688 2950.

BARGAIN PACKS

12 BC107	£1-20	25 1N4001	£1-20
14 BC108	£1-20	22 1N4002	£1-20
12 BC109	£1-20	20 1N4003	£1-20
15 BC148	£1-20	18 1N4004	£1-20
12 BC149	£1-20	16 1N4005	£1-20
12 BC157	£1-20	14 1N4006	£1-20
12 BC158	£1-20	12 1N4007	£1-20
12 BC159	£1-20	40 1N4148	£1-20
2 2N2646	£1-20	3 2N3055	£1-20
10 BC328	£1-20	12 BC548	£1-20
12 BF194	£1-20	12 BF195	£1-20
7 BF173	£1-20	5 BF181	£1-20

All full spec. marked components.

8 PIN DIL 71's

10 x 20p; 25 x 23p; 100 x 21p; 250 x 20p.

555 TIMERS

3 x 60p; 10 x 50p; 25 x 40p; 100 x 43p.

RESISTORS AND CAPACITORS

400 asstd. carbon resistors £1-40, 250 Hi-stab 1, 2, 5%, 1/4, 1W £1-35, 100 Wirewounds, 2W to 15W £2, 200 ceramic, mica, etc. caps £1-10, 100 C280 polyesters, 0-01-0-47 £1-30, 200 min. electrolytics, but mainly normal. Out of spec. £1-35. 15 airspaced and compression trimmers up to 1250pF £1-10. JUMBO PACK - 1 each of the above. £9-80 value for only £7-50! 11

VEROBOARD

100 sq. in. about 8 pieces asstd. sizes and pitches £1-15.

MISCELLANEOUS

SPCO microswitch, 5a 12p; 15 asstd. pots 75p; plug in relay, 2,500 1/4c/o 25p; 4 x 80V 10A rectis. on heat sink. Ideal batt. charger £1-20; SN76680N £1. Good range close tolerance resistors - S.A.E. list. 96kHz crystal £1. Push button bank - 8 interlocking buttons, each 4 pole change, only 4 x 2 x 1/2 in £1.

TRANSISTOR PACKS

Large quantity of mainly unmarked out of spec. transistors just arrived. Sample tests show 75% OK. Sold in mixed packs with PNP, NPN, RF, AF, plastic, metal can, small signal and power devices. At least 200 for £1-50; 500 for £3-90; 1,000 for £8. Out of spec. 2N3055's 8 for £1-10, 25 untested BFY51 type transistors £1-10, 25 untested BC108 £1; 100 £3.

BI-PRE-PAK

Bargains in Semi-Conductors, components, modules & equipment.

BARGAINS FROM OUR FREE CATALOGUE

6th edition. 20 large pages filled with real bargains in transistors, I.C.s, components, equipment, etc. Send large S.A.E. with 7p stamp for your FREE copy by return. Meanwhile, for prompt delivery order from our ad. this month NOW.

X-HATCH GENERATOR MK.2



Rotary selector switch provides choice of four patterns—essential for colour TV alignment. Featuring plug-in IC's and a more sensitive sync-pick-up circuit. The reinforced fibre-glass case is virtually unbreakable—ideal for the engineer's toolbox—only measures 3in x 5½in x 3in. Operates from three U-2-type batteries (extra).

Ready built unit only **£9.93**

P. & P., add 30p

Complete kit **£7.93**

PLASTIC POWER TRANSISTORS

40 WATT SILICON				90 WATT SILICON			
Type No.	Gain	VCE	Polarity	Type No.	Gain	VCE	Polarity
40N1	15	15	NPN	90N1	15	15	NPN
40N2	40	40	NPN	90N2	40	40	NPN
40P1	15	15	PNP	90P1	15	15	PNP
40P2	40	40	PNP	90P2	40	40	PNP

TRANSISTOR PACKS—ALL AT 50p EACH TESTED AND GUARANTEED

B79	4	IN4007 Sil. Rec. diodes 1.000 PIV 1 amp. plastic	H39	6	Integrated circuits 4 gates BMC 962. 2 flip flops BMC 945
B81	10	Reed Switches, 1in long ½in dia. Highspeed P.O. type	H41	2	BD131/BD132 Complementary Plastic Transistors
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked	H65	4	40361 Type NPN Sil. transistors TO-5 can comp. to H66
H38	30	Short lead Transistors, NPN Silicon Planar types Ex-equipment	H66	4	40362 Type PNP Sil. transistors TO-5 can comp. to H65

UNMARKED AND UNTESTED

B1	50	Germanium Transistors PNP, AF and RF	H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can
B66	150	Germanium Diodes Min. glass type	H67	10	3819N Channel FET's plastic case type
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	OVER A MILLION TRANSISTORS IN STOCK—All most-needed types MARKED — TESTED — GUARANTEED—SEE CATALOGUE		
B86	100	Sil. Diodes min. 1N814 glass equivalent to 1N4148			

TO CLEAR

Hundreds of various portable transistor radio chassis FM and AM. Ideal for experimenters. Components electronically sound; chassis not all perfect. No instructions, or tuning drives. A cheap way to make a radio set. **£1 Each**

MAINS TRANSFORMERS

P. & P., add 35p per unit
Type A—18V/1A (suit SS. 103) £1.50.
Type B—25V/2A (suit SS. 110) £2.00.
Type C—30V/2A (suit SS. 140) £3.25.

Bridge Rectifiers: Type A 27p; Types B & C 38p.

CAPACITOR DISCHARGE IGNITION KIT

Easy to assemble and fit to your car. **£7.50** With instructions. (P. & P. add 30p)

TERMS OF BUSINESS

V.A.T. Prices shown do NOT include V.A.T. Please add 25% to total value of your order including postage for V.A.T. except for items marked ● or (8%) for which the V.A.T. rate is 8%. No V.A.T. on overseas orders.

Overseas—add £1, any difference being charged or refunded.
PAYMENT Cash with order. Cheque or money order. Minimum value—£1. You can also pay by ACCESS.

IMPORTANT—Every effort is made to ensure accuracy of prices and description at time of preparing this advertisement and going to press. Prices are subject to alteration without notice.

BI-PRE-PAK LTD

Co Reg No R20919

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 0DF.

TELEPHONE: SOUTHEND (0702) 46344.


WRITE ORDER SEPARATELY AND ATTACH COUPON IF NECESSARY



CHALLENGING VALUES!

Stirling Sound

STIRLING SOUND AUDIO MODULES come to you as basic units assembled on P.C.B.s enabling you to add required components in layouts of your own choice. Modules are tested and boxed before despatch and include well printed instructions.

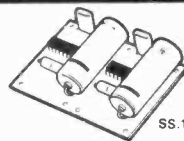

SS.103-3

AMPLIFIER MODULES

Pre-amplifiers; tone control

SS.100 Active tone control unit to provide bass, treble, balance and volume controls


£1.60

SS.101 Pre-amp for ceramic cartridge, tape and radio

£1.60

SS.102 Pre-amp for low output magnetic cartridge tape and radio. With R.I.A.A. correction $\pm 1dB$ at 1kHz

£2.25

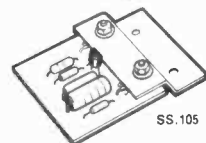

SS.105

POWER AMPLIFIERS

SS.103 Compact I.C. amp. with 3 watts R.M.S. output. Operating voltage 10-20. Size 3½in x 2in.

£1.75

SS.103-3 Stereo version of above using one I.C. on each channel

£3.25

SS.105 A compact and useful all-purpose amplifier which will run excellently on a 12V supply. With 5 watt output, two make a good stereo amp. Size 3½in x 2in. New Mk. 2 version.


£2.25

SS.110 Similar in size to SS.105 but with a 10 watt output. Ideal for many domestic and small-size P.A. applications. Operates from 26-32V.


£2.70

SS.140 Excellently designed 40 watt R.M.S. (into 4 ohms) hi-fi amplifier. S/N ratio better than 75dB T.H.D. better than 0.2%. Power requirements—45V d.c. With 0.15in centre edge connections. Two can be bridged to give 80 watts R.M.S. into 8 ohms.

£3.60

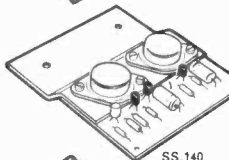

SS.140

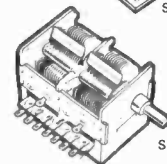

SS.201

BUILD A STEREO F.M. TUNER!

SS.201 Front end with ganged tuning and geared slow-motion drive in rugged housing. Excellent sensitivity. Tunes 88-108MHz. With A.F.C. facility. Operates from 6-16V


£6.25

SS.202 I.F. stage (with I.C.). Pre-tuned. A.F.C. connection. Operates from 4.5-14V

£5.25

SS.203 Stereo Decoder. Designed essentially for use with SS.201 and SS.202, this module can also be used on most mono F.M. tuners. A L.E.D. may be attached. Operating voltage 9-16V d.c.

£5.62

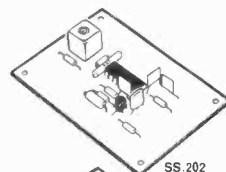

SS.202

SPECIAL MONEY SAVING OFFER!


Save £5—buy all 3 units (SS.201, SS.202 and SS.203) together for

£12.12

POWER SUPPLY STABILISER

SS.300 Add this to an unbalanced supply (say typically 45V output) to obtain a steady powerful working output adjustable from 12 to 60V. Essential for your audio and special systems. Money saving, very reliable and ideal for the workbench.

£3.25

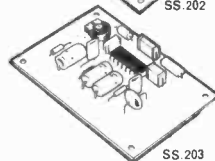

SS.203

STIRLING SOUND DISCO MINOR

Twin turntable console with cross-fade mic (with over-ride) and headphone monitor jacks, etc. plus unique 'AMPOWER 40' speaker with built in 40 watt R.M.S. power amp. You can add up to ten to give 400 watts! Portable console and one AMPOWER £100 plus £3.50 carr. U.K., plus VAT.

Have you had your FREE CATALOGUE?

To BI-PRE-PAK, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX


Please send

for which I enclose


NAME

ADDRESS

PE8

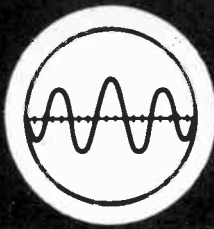


TUAC

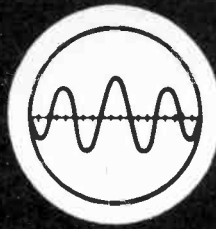

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.
163 MITCHAM RD · LONDON SW17 9PG 01 672 3137 9080

TUAC POWER MODULES offering more power and quality than ever before

● 125 watts RMS continuous sine wave output

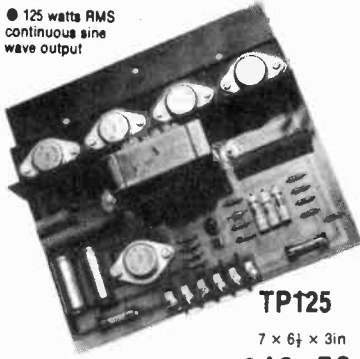


TP125

7 × 6½ × 3in


£19·50

● 4 R.C.A. 150 watt 15 amp output transistors

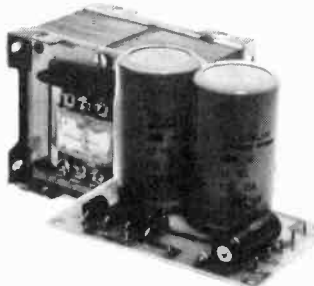Power supplies vacuum impregnated Transformers with supply board incorporating pre-amp supply:



PS 125 ± 50 volts for one TP125 £12·25
PS 100 ± 45 volts for one TL100 £11·25
PS 60 ± 40 volts for one TL60 £10·00
PS 30 ± 50 volts for one TL30 £5·90
PSU 2 for supplying disco mixer £4·75

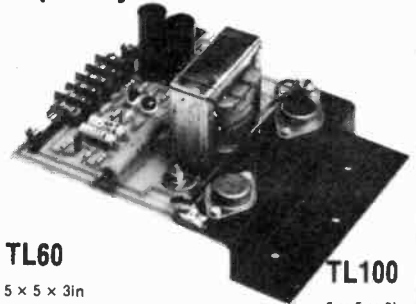

TL60

5 × 5 × 3in

● 60 watts RMS continuous sine wave output
● 2 R.C.A. 110 watt 15 amp transistors

£12·50

TL100

5 × 5 × 3in

● 100 watts R.M.S. continuous sine wave output
● 2 R.C.A. 150 watt 15 amp transistors

£15·00

● Rugged layer wound driver transformer
● Short—Open—and Thermal overload protection
● Only 6 connections

Specification on all power modules: All output power ratings ± 0·5dB; Output Impedance 8–15 ohms; THD at full power 2% typically 1%; Input sensitivity 60mV into 10kΩ; Frequency response 20Hz–20kHz ± 2dB; Hum and noise better than –70dB.

TUAC DISCOTHEQUE MIXER WITH AUTO FADE



Designed for the discerning D.J. of professional standard. Offering a vast variety of functions. Controls: Mic Vol; Tone, over-ride depth; auto/Manual Sw; Tape Vol; L & R Deck Faders; Deck Volume; Treble and Bass; H. Phon Vol Selector; Master Vol On/Off Sw. Max output 1V RMS.

Specification: Deck Inputs—50mV into 1MΩ; Deck Tone Controls—treble +20 –10dB at 12kHz, Bass +22 –15dB at 40Hz; Mic Input—200 ohms upwards, 2mV into 10kΩ; Mic Tone Control—Total Variation Treble 15dB, Total Variation Bass 10dB; Tape Input—30mV into 47kΩ; Power Requirements—30–45 volts at 100mA.

£31·50
PANEL SIZE
18 × 4½in
DEPTH 3in

HOW TO ORDER BY POST


Make cheques/P.O.s payable to TUAC LTD (PE2/3)
or quote Access/Barclay Card No.
and post to TUAC LTD (PE8-3)
163 Mitcham Road, London, SW17 9PG
We accept phone orders against
Access/Barclay Card Holders
Phone: 01-672 3137/9080

STOCKISTS—CALLERS ONLY


Arthur Salls Ltd., 28 Gardner Street. Tel. Brighton 65806
Bristol Disco Centre, 86 Stokes Croft. Tel. Bristol 41666
Socodi, 9 The Friars. Tel. Canterbury 60948
Cookles, 132 West Street. Tel. Crewe 4739
Calbarrie Audio, 88 Wellington Street. Tel. Luton 411733
Al Music Centre, 88 Oxford Street. Tel. Manchester 236 0340
Damon Electronics, 99 Carrington Street. Tel. Nottingham 53880
Electra Centre, 58 Lancaster Road. Tel. Preston 58488
Mitchell Electronics, 64 Winchester Street. Tel. Salisbury 23689
Wec Lighting, 10 Commercial Road. Tel. Southampton 28102

ALL PRICES INCLUDE V.A.T. (8%) AND POSTAGE AND PACKING

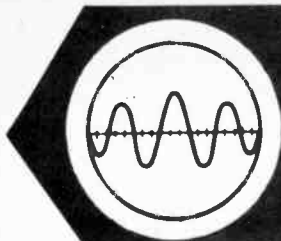ACCESS & BARCLAY CARDS ACCEPTED: JUST SEND OR PHONE US YOUR NUMBER · H.P. ARRANGED THROUGH PAYBONDS




TUAC

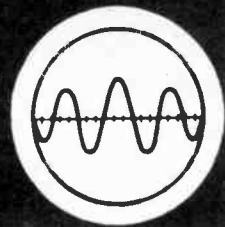

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.
163 MITCHAM RD. LONDON SW17 9PG 01-672 3137 9080

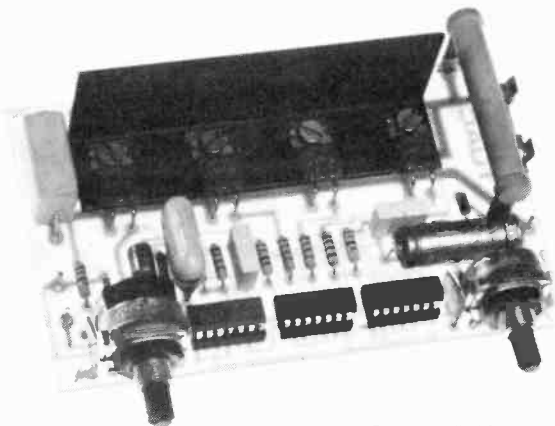NEW !!! 4 CHANNEL SOUND TO LIGHT SEQUENCER—4LSMI



- RCA 8A Triacs
- 1000W per channel
- Fully suppressed and fused
- Switched master control for sound operation from $\frac{1}{4}$ W to 125W
- Speed control for fixed rate sequence from 8 per minute to 50 per second
- Full logic integrated circuitry optical isolation for amplifier protection
- Full wave control
- 13 easy connections

Patent applied for

£18.25

3 CHANNEL LIGHT MODULATOR


- R.C.A. 8A Triacs
- 1000W per channel
- Each channel fully suppressed and fused
- Master control to operate from 1W to 100W
- Full wave control
- 12 easy connections.

1500 Watts


Single Channel Version

£7.25

£15.50

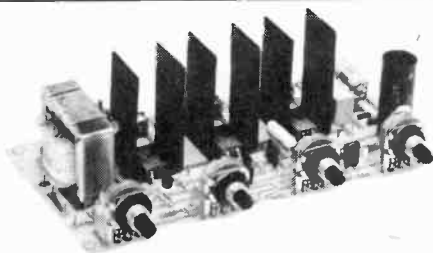

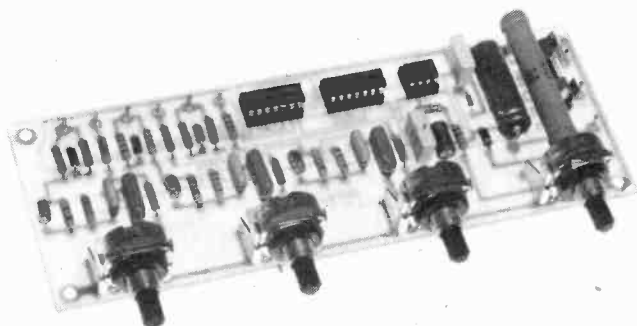
ADD SEQUENCE AND DIMMING EFFECTS TO YOUR TUAC 3 CHANNEL LIGHT MODULATOR



SEQUENCE DIMMER MODULE—3SDMI

Speed Control 3 per min. to 10 per sec.
Full logic integrated circuitry
Dimmer control to each channel
9 easy connections

£9.50

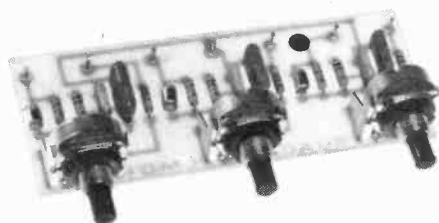

DIMMER MODULE—LMDI


Dimmer control for each channel
7 easy connections

£4.25

MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT
SPECIALISTS IN QUALITY TRANSISTOR EQUIPMENT OPEN 6 DAYS A WEEK 9.30am - 6.00pm

IMPROVE PETROL CONSUMPTION

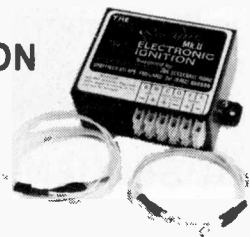Fit the
Brilliant New
P.E. Scorpio Mk. II
"Dual Polarity"
Capacitive Discharge
Electronic Ignition system



- ★ Genuine improvement in overall petrol consumption (Independent report claims at least 8%-10%)
- ★ Much easier cold weather starting, less strain on your battery
- ★ Less use of choke—increases engine life
- ★ Smoother running at lower revs—makes your four cylinder car feel like a six cylinder

Together with the following "Scorpio Mk. II" plus features not previously available with other makes:

- ★ Only one model used for both positive (+) and negative (-) earth vehicles—if you change your car, you can certainly transfer your "Scorpio"
- ★ Retains your original contact breaker points, which last their mechanical life—no points burn
- ★ Will drive electronic tachometers.


Send a stamped addressed envelope for our free interesting brochure, "Electronic Ignition—How it Works", containing circuit and itemised price list.

Price for complete kit of parts, with easy to follow, comprehensive instructions, connecting wire, etc. ONLY £10.85, including VAT and postage and packing.

Ready made unit, fully tested, for immediate installation with easy to follow instructions, all leads, etc., ONLY £13.85, including VAT and postage and packing.

THOUSANDS ALREADY IN USE—FULLY GUARANTEED.

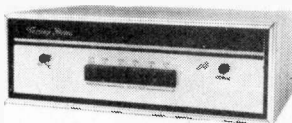P.E. "VARICAP" STEREO PUSH BUTTON F.M. TUNER



The P.E. "Varicap" Stereo Tuner uses the latest Mullard modules for R.F. and I.F. circuits—highly sensitive and pre-aligned for ease of construction.

This superb kit has everything to enable you to construct this highly sensitive F.M. Stereo Tuner, with instant push button station selection, self contained regulated power supply, stereo decoder, etc., etc. Easy to construct, highest quality reproduction.

Price only £34.50, including VAT and postage and packing. Please send stamped addressed envelope for our free brochure on the Varicap, which gives performance figures, detailed description, etc., etc.

P.E. "GEMINI" STEREO AMPLIFIER

Output genuine 30W R.M.S. per channel!

Distortion 0.01% (maximum)!
Frequency response—3dB, 20Hz to 100kHz into 8 ohms!
Fully comprehensive inputs, disc, tape, MIC, etc.!

Yes, we are still supplying all components for this superb Stereo Amplifier, since we have not yet found a better one!

Fully comprehensive constructional booklet available, containing full specification, performance graphs, step-by-step assembly instructions, photographs, fault finding guide, etc. etc. Price 55p plus 9p postage and packing.

For itemised price list only please forward stamped addressed envelope.

ELECTRO SPARES, 288 ECCLESALL ROAD, SHEFFIELD S11 8PE

Please allow 14 days minimum for delivery, for postal delays, cheque clearance, etc.

ASTOUNDING OFFER

We are offering you the choice of two superb scientific pocket slim calculators (size 13.5cm x 6.75cm x 1.75cm) at a fantastic price.

DECIMO 2001

In addition to common functions it registers all functions appertaining to natural logs,

common logs, trigonometry in algebraic logic. A special feature is a memory exchange.

DECIMO 2001E


In addition to all the above features it has a 10 digit mantissa with 2 figure exponent, 2 figure display hyperbolics and functions on separate keys.

Functions

- 8 figure Mantissa
- Common Logs
- Natural Logs
- Trig. functions
- Memory
- Memory + -
- Memory Exchange
- Sign Change
- Reciprocals
- Square Roots
- Radians/Degrees
- Register Exchange
- π
- Algebraic Logic
- Floating point
- Positive feel
- 25hr battery time

£29.95

+ P. & P. + 8% VAT
including carry case

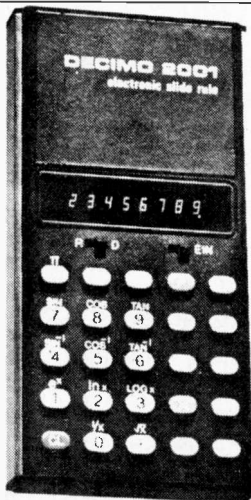

Functions

- 10 figure Mantissa
- 2 figure Exponents
- 2 sign display
- Common Logs
- Natural Logs
- Trig. functions
- Memory
- Memory + -
- Memory Exchange
- Sign change
- Reciprocals
- Square roots
- Radians/Degrees
- Grads.
- Hyperbolics
- Register Exchange
- π
- Algebraic Logic
- Floating point
- Positive feel
- 25hr Battery time

£37.46

+ P. & P. + 8% VAT
including carry case



BARCLAY ELECTRONICS are specialists in all types of Calculators. Don't hesitate to write for one that will suit your purpose.

To Dept. 10P, BARCLAY ELECTRONICS
Stanley House, 1115 Finchley Road, London, N.W.11

Please send me (number) Mains adp. Add £3 to total
Decimo (type) Total £..... p.

Name
Address

2001E—£37.46 + 60p P. & P. + £3.05
VAT
Total £41.10 each
2001—£29.95 + 60p P. & P. + £2.44
VAT
Total £32.99 each

Marshall's

Everything you need is in our
New 1975 Catalogue
available now price 25p
(100 pages of prices and data)

A. Marshall (London) Ltd. Dept. PE
42 Cricklewood Broadway London NW2 3DH Telephone 01-452 0161 2 Telex 21492
& 85 West Regent Street Glasgow G2 2QD Telephone 041-332 4133

Call in and see us 9-5.30 Mon-Fri
9-5.00 Sat
Trade and export enquiries welcome

Top 500 Semiconductors From the Largest Range in the U.K.

2N456	0-80	0-80	2N5192	1-24	AF106	0-40	BC184	0-13	BF153	0-25	
2N456A	0-85	2N3053	0-25	2N5195	1-46	AF109R	0-40	BC184L	0-13	BF154	0-20
2N457A	1-20	2N3054	0-60	2N5245	0-47	AF114	0-35	BC186	0-25	BF159	0-27
2N490	4-14	2N3055	0-75	2N5294	0-48	AF115	0-35	BC187	0-27	BF160	4-23
2N491	4-38	2N3390	0-45	2N5295	0-48	AF116	0-35	BC207	0-12	BF163	0-32
2N492	5-00	2N3391	0-28	2N5296	0-48	AF117	0-35	BC208	0-11	BF166	0-40
2N493	5-30	2N3391A	0-29	2N5298	0-50	AF118	0-35	BC212K	0-18	BF167	0-25
2N695	0-22	2N3392	0-15	2N5457	0-49	AF124	0-30	BC212L	0-18	BF173	0-27
2N697	0-16	2N3393	0-15	2N5458	0-46	AF125	0-30	BC214L	0-18	BF177	0-20
2N698	0-82	2N3394	0-15	2N5459	0-49	AF126	0-28	BC237	0-16	BF178	0-35
2N699	0-59	2N3402	0-18	2N5492	0-58	AF127	0-28	BC238	0-15	BF179	0-43
2N706	0-14	2N3403	0-19	2N5494	0-58	AF139	0-65	BC239	0-15	BF180	0-35
2N706A	0-16	2N3440	0-59	2N5496	0-61	AF166	0-46	BC251	0-25	BF181	0-38
2N708	0-17	2N3441	0-97	2N5777	0-45	AF200	0-65	BC253	0-25	BF192	0-35
2N709	0-42	2N3442	1-40	2N6027	0-45	AF239	0-65	BC257	0-16	BF183	0-55
2N711	0-50	2N3414	0-20	3N128	0-73	AF240	0-90	BC258	0-18	BF184	0-30
2N718	0-23	2N3415	0-21	3N139	1-42	AF279	0-70	BC259	0-17	BF185	0-30
2N718A	0-28	2N3416	0-36	3N140	1-00	AF280	0-79	BC261	0-25	BF194	0-12
2N720	0-57	2N3417	0-24	3N141	0-81	AL102	1-00	BC262	0-25	BF195	0-12
2N814	0-39	2N3638	0-15	3N200	2-48	AL103	1-00	BC263	0-25	BF196	0-13
2N815	0-28	2N3638A	0-15	40361	0-40	BC107	0-14	BC309C	0-20	BF197	0-15
2N818	0-32	2N3639	0-27	40362	0-45	BC108	0-14	BC301	0-34	BF198	0-18
2N929	0-37	2N3641	0-17	40363	0-88	BC109	0-14	BC302	0-29	BF200	0-40
2N930	0-22	2N3702	0-12	40389	0-46	BC113	0-15	BC303	0-54	BF225J	0-23
2N1302	0-19	2N3703	0-13	40394	0-56	BC115	0-17	BC307	0-17	BF244	0-21
2N1303	0-19	2N3704	0-15	40395	0-65	BC116	0-17	BC308A	0-15	BF245	0-45
2N1304	0-28	2N3705	0-15	40396	0-81	BC116A	0-18	BC309C	0-20	BF246	0-58
2N1305	0-24	2N3706	0-15	40407	0-35	BC117	0-21	BC237	3-27	BF247	0-65
2N1306	0-31	2N3707	0-18	40408	0-50	BC118	0-14	BC238	3-28	BF254	0-19
2N1307	0-30	2N3708	0-14	40409	0-52	BC119	0-29	BC337	0-20	BF255	0-19
2N1308	0-47	2N3709	0-15	40410	0-52	BC121	0-35	BC338	0-20	BF257	0-47
2N1309	0-47	2N3710	0-15	40411	2-00	BC125	0-16	BCY30	0-80	BF258	0-53
2N1671	1-54	2N3711	0-15	40594	0-74	BC126	0-23	BCY31	0-85	BF259	0-55
2N1671A	0-87	2N3712	1-20	40595	0-84	BC127	0-18	BCY32	0-85	ME0412	0-18
2N1671B	1-85	2N3713	1-20	40601	0-67	BC134	0-13	BCY33	0-85	BF0412	0-11
2N1711	0-45	2N3714	1-38	40602	0-61	BC135	0-13	BCY34	0-79	BF521A	2-30
2N1907	5-50	2N3715	1-50	40603	0-58	BC136	0-17	BCY38	1-00	MF528	0-92
2N2102	0-78	2N3716	1-80	40604	0-56	BC137	0-17	BCY39	1-50	BF561	0-27
2N2147	0-84	2N3717	2-20	40636	1-10	BC138	0-24	BCY40	4-47	BF598	0-25
2N2148	0-84	2N3772	1-60	40659	0-60	BC140	0-68	BCY42	0-28	BF225	0-30
2N2160	0-30	2N3773	2-65	40673	0-73	BC142	0-68	BCY58	0-30	BFX30	0-27
2N218A	0-22	2N3789	2-06	AC126	0-20	BC142	0-23	BCY59	0-32	BFX84	0-24
2N2219	0-24	2N3790	2-40	AC127	0-20	BC143	0-25	BCY70	0-17	BFX85	0-30
2N2219A	0-26	2N3791	2-35	AC128	0-20	BC145	0-21	BCY71	0-22	BFX87	0-28
2N2220	0-25	2N3792	2-60	AC151V	0-27	BC147	0-14	BCY72	0-15	BFX88	0-25
2N2221	0-18	2N3794	0-24	AC152V	0-49	BC148	0-14	BD115	0-75	BFX89	0-50
2N2221A	0-21	2N3819	0-37	AC153	0-35	BC149	0-15	BD116	0-75	BFY50	0-23
2N2222	0-20	2N3820	0-64	AC153K	0-40	BC153	0-18	BD121	1-00	BFY51	0-23
2N2222A	0-25	2N3823	0-78	AC154	0-25	BC154	0-18	BD123	0-82	BFY52	0-21
2N2368	0-25	2N3904	0-27	AC176	0-30	BC157	0-16	BD124	0-67	BFY53	0-18
2N2369	0-20	2N3906	0-27	AC178K	0-40	BC158	0-18	BD131	0-40	BFY90	0-75
2N2369	0-55	2N4036	0-67	AC187K	0-35	BC160	0-60	BD132	0-50	BRV39	0-23
2N246	0-98	2N4037	0-42	AC188K	0-40	BC167B	0-15	BD135	0-43	BSX20	0-21
2N2647	0-59	2N4058	0-18	AC188	0-24	BC168B	0-15	BD136	0-48	BSX21	0-29
2N2904	0-22	2N4059	0-15	AC191V	0-27	BC168C	0-15	BD137	0-65	BU104	2-00
2N2904A	0-24	2N4060	0-15	AC1920	0-22	BC169B	0-15	BD138	0-53	BU105	2-25
2N2905	0-25	2N4061	0-15	AC1921	0-28	BC169C	0-15	BD139	0-71	CI06D	0-85
2N2905A	0-28	2N4062	0-15	AC192V	0-20	BC170A	0-15	BD140	0-87	CA3018A	1-80
2N2906	0-19	2N4126	0-21	AC1930	0-58	BC171	0-18	BD158	0-80	CA3020A	1-80
2N2906A	0-21	2N4289	0-34	AD142	0-57	BC172	0-17	BD530	0-80	CA3028A	0-79
2N2907	0-22	2N4919	0-95	AD143	0-68	BC177	0-28	BDY20	1-05	CA3035	1-36
2N2907A	0-24	2N4920	1-10	AD149V	1-20	BC178	0-27	BF115	0-35	CA3046	0-70
2N2924	0-20	2N4921	1-83	AD150	1-15	BC179	0-30	BF117	0-55	CA3048	2-11
2N2925	0-20	2N4922	1-00	AD161	0-50	BC182	0-12	BF121	0-35	CA3052	1-82
2N2926	0-19	2N4923	1-00	AD162	0-58	BC183L	0-12	BF123	0-35	CA3088E	1-98
Green	0-12	2N5190	0-92	AD161	PR	BC183	0-12	BF125	0-35	CA3090Q	4-23
Yellow	0-12	2N5191	0-96	AD162	J	BC183L	0-12	BF152	0-20	LM301A	0-48

LM308	2-50	OC35	0-40
LM309K	1-86	OC42	0-50
LM309K	1-86	OC45	0-32
LM380	1-10	OC71	0-20
LM381	2-20	OC72	0-25
LM702C	0-75	OC81	0-25
LM709	0-38	OC83	0-24
TO99	0-48	ORF12	1-55
BD1L	0-38	RS3	1-80
14D1L	0-40	SL414A	1-80
LM710	0-47	SL610C	1-70
LM723C	0-90	SL611C	1-70
LM741	0-43	SL612C	1-70
TO99	0-40	SL620C	2-60
BD1L	0-40	SL614C	4-50
14D1L	0-38	SL623	4-50
LM747	1-00	SL640C	3-10
LM748	0-30	SL641C	3-10
BD1L	0-30	SN76030N	2-92
14D1L	0-60	SN76031N	1-95
LM3900	0-70	SN76032N	1-95
LM7805	2-00	SN76033N	2-92
LM7812	2-50	ST2	0-20
LM7815	2-50	TAA263	1-10
LM7824	2-50	TAA300	1-80
MC1303	1-50	TAA350	2-10
MC1310	2-92	TAA500	2-10
MC1330P	0-90	TAA611C	2-18
MC1351P	0-80	TAA621	2-03
MC1352P	0-80	TAA661B	1-32
MC1466	3-50	TBA647B	2-25
MC1469	2-75	TBA651	1-68
ME0402	2-20	TBA800	1-50
ME0404	0-13	TBA810	1-50
ME0412	0-18	TBA820	1-15
ME4102	0-11	TBA920	4-00
ME4104	0-11	TIL209	0-30
MAJ480	0-95	TIP29A	0-48
MU481	1-20	TIP29C	0-48
MU490	1-05	TIP30A	0-58
MU481	1-45	TIP30C	0-85
MU265	1-00	TIP31A	0-62
MJE340	4-00	TIP31C	1-00
MJE2955	1-00	TIP32A	0-74
MJE3055	0-75	TIP32C	1-25
MJE370	0-65	TIP33A	1-01
MJE371	0-75	TIP33C	1-45
MJE521	0-70	TIP34A	1-51
MP8111	0-32	TIP35A	2-90
MP8112	0-40	TIP36A	3-70
MP8113	0-47	TIP41A	0-79
MPF102	3-39	TIP41C	1-40
MPSA05	0-25	TIP42A	0-90
MPSA06	0-31	TIP42C	1-80
MPSA12	0-35	TIP49C	0-70
MPSA56	0-26	TIP53	1-70
MPSA56	0-21	TIP2955	0-98
MPSU05	0-85	TIP3035	0-50
MPSU05	0-85	TIP3035	0-50
MPSU55	0-63	ZTX300	0-13
MPSU56	0-80	ZTX301	0-13
NE555V	0-70	ZTX302	0-20
NE556	1-30	ZTX500	0-15
NE580	4-48	ZTX501	0-13
NE561	4-80	ZTX503	1-15
NE565A	4-48	ZTX530	0-23
OC23	3-15		
OC28	0-76		

PW TELEENNIS KIT

As featured on BBC Nationwide and in the Daily Mail 2 Oct. 74. Ideal game for whole family. No need to modify your TV set. Just plug in to aerial socket.
Parts list as follows: A Resistor Pack £1 P & P. 20p. B Potentiometer Pack £1.25 P & P. 20p. C Capacitor Pack £3.10 P & P. 20p. D Semiconductor Pack £14.50 P & P. 20p. E IC Sockets £4 P & P. 20p. F Transistor £1.25 P & P. 25p. G PCB a £7.50 P & P. 20p. H Switches £4.50 P & P. 20p. I UHF Modulator Kit £7.50 P & P. 20p. Special Prices—complete kit excluding case £42 P & P. 50p. Sections A-F incl. £23.50 P & P. 30p. Assembly instructions with complete kit or 75p on request.

P.C. Marker Pen Dalo 33PC 0-87p.
Zeners 400MW, 11p; 1W, 17p.
IC Sockets 8 DIL 18p; 14 DIL 17p; 16 DIL 20p.
Resistors 1W 2p; 1/2W 3p; 2W 5p; 5W 10p; 10W 17p.

Scorpio Car Ignition Kit—£11.50 + VAT.
1 IMF440V £1.10.
BSTBO248 £1.20. Transformer £3.

OPTO and LEDs
Red, green and yellow.
0.16 diameter 3ip; 0.20 diameter 3ip.
DL707 £2.35 or 4 for £8.
Mintron £1.55.

Cmos Circuits (CD Range)

4000	0-36	4016	0-68	4030
------	------	------	------	------

SPARKRITE MK2

CAPACITIVE DISCHARGE ELECTRONIC IGNITION KIT

Sparkrite Mk. 2 is a high performance, high quality, capacitive discharge, electronic ignition system. Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire because contact breaker bounce is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and therefore eliminates the possibility of blowing the transistors or the SCR. (Many capacitive discharge ignitions are not completely foolproof in this respect.)

Sparkrite can therefore give you: up to 20% better fuel consumption, instant all weather starting, cleaner plugs—they last up to 5 times longer without attention, faster acceleration, higher top speeds, longer coil and battery life, efficient fuel burning and less air pollution, smoother running, continual peak performance.

NOTE—FUEL CONSUMPTION:

The fitting of a Sparkrite Mk. 2 should reduce fuel consumption although the amount of the reduction will vary. A fair estimate of the savings which could be expected, based on reports by our customers and upon our own experience, are as follows:
 any 4-cylinder vehicle, 10% improvement
 any 6-cylinder vehicle, 15% improvement
 any 8-cylinder vehicle, 20% improvement
 It is worth remembering that while fuel saving is important there are many other advantages to be gained from fitting a Sparkrite ignition system.

Voted best of 8 ignition systems tested by a leading Motoring Magazine


THE KIT COMPRISES EVERYTHING NEEDED: Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heatsink, top quality 5-year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions. **WE SAY IT IS THE BEST SYSTEM AT ANY PRICE.**

OPTIONAL EXTRAS

Electronic R.P.M. limitation. This can be included in the unit to prevent over revving, an advantage to most companies, hire firms, high performance drivers, etc.

Electronic/conventional ignition switch.

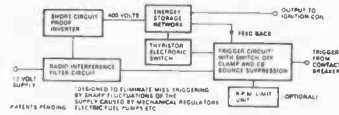Gives instant changeover from Sparkrite ignition to conventional ignition for performance comparisons, static timing, etc., and will also switch the ignition off completely as a security device. Includes: switch, connectors, mounting bracket and instructions. Cables excluded.



PRICES: D.I.Y. assembly kit £10-92*. Ready built unit £13-86* (both to fit all vehicles with coil/distributor ignition up to 8-cylinders).

Switch for instant changeover from Sparkrite ignition to conventional ignition £2-79*. R.P.M. limiting control £2-42* (fitted in case on ready built unit, dashboard mounting on kit).

*Including VAT, post and packing. We can supply units for any petrol-engined vehicle (boat, motorcycle, etc.) with coil/contact breaker ignition. Details on request. **CALL IN AND SEE US FOR A DEMONSTRATION.**

ELECTRONICS DESIGN ASSOCIATES of WALSALL

ALUMINIUM BOXES FLUORESCENT LIGHT KIT

These project boxes are manufactured from 18-gauge aluminium and come complete with lids and screws.

The prices shown include VAT (at 8%) but 18p should be added to the total order value for postage and packing.

Order No.	Length (in)	Width (in)	Height (in)	Price (inc. VAT)
7	5½	2½	1½	47p
8	4	4	1½	48p
9	4	2½	1½	45p
10	5½	4	1½	49p
11	4	2½	2	46p
12	3	2	1	38p
13	6	5	2	59p
14	7	5	2	75p
15	8	6	3	93p
16	10	7	3	£1-14

Boxes can be made to any size but the minimum order for special sizes is 500. General trade enquiries welcome.

You can build this reverse polarity protected 12V, 8W, fluorescent light. Everything needed is supplied: white enamelled drilled metalwork, ready drilled heatsink, printed circuit board, high quality components and transformer, and caps, cable, the fluorescent tube, nuts, bolts, washers, and simple assembly and operating instructions.

When complete the light has many uses: workshop and workbench illumination, garage lighting, emergency lighting, lighting for camping, caravanning, and boating, as an inspection lamp and many more.

If you can't spare ½ hour to put the light together then we will supply it ready built (FOR A FEW EXTRA PENCE).

PRICES

Assembly kit £3-46 (inc. VAT, post and packing).
 Ready built £4-10 (inc. VAT, post and packing).
 Diffuser 59p extra (inc. VAT, post and packing).

ORDER NOW

To: ELECTRONICS DESIGN ASSOCIATES DEPT. P.E. 8
 82 Bath Street, Walsall WS1 3DE Phone 33652.

From: Name _____
 Address _____

Please Supply

Quantity	
_____	SPARKRITE Mk. 2 DIY assembly kit at £10-92
_____	SPARKRITE Mk. 2 ready built negative earth at £13-86
_____	SPARKRITE Mk. 2 ready built positive earth at £13-86
_____	Ignition changeover switches at £2-79
_____	R.P.M. Limit systems in the above units at £2-42
_____	Fluorescent light assembly kits at £3-16
_____	Fluorescent light built units at £3-79
_____	Diffusers for the above at 59p
_____	of number _____ alum boxes at _____
_____	of number _____ alum boxes at _____
_____	of number _____ alum boxes at _____

I enclose cheque/P.O. for £ _____ Cheque No. _____
 (Send S.A.E. if brochure only required)

INVERTORS

240V—50Mz from your 12V car battery	150W—£18-30 + 80p p & p.
25W—£3-90 + 30p p & p.	30W (12V)—£28-80 + £1-05 p & p.
40W—£6-80 + 55p p & p.	300W (24V)—£22-70 + £1-05 p & p.
75W—£9-95 + 75p p & p.	

All above invertors are in kit form but may be purchased built up and ready for use. Price list sent on receipt of stamped addressed envelope.

P.W. AUTOMATIC EMERGENCY SUPPLY

250V—50Hz—150W inverter with built in battery charger. In event of power failure switches over automatically from battery charging to inverter operation. Cct. as appeared in Dec. 73 P.W. Complete kit of parts (excluding meter) £22-50 + £1-10 p & p.

COMPLETE FLUORESCENT LIGHT INVERTOR KIT

8W—12V—Fluorescent light, suitable for tents, caravans, houses, boats and secondary lighting for factories, hotels etc. 12in—8W £2-90 + 25p p & p. 21in—13W £3-30 + 30p p & p.

TRANSFORMERS AND COILS

Both high volume and small order capacity available for Mains, R.F., and I.F. Transformers. Before you buy elsewhere let us quote you and see what you save. V.A.T. at 8% included.

TRADE AND EXPORT ENQUIRIES WELCOMED

ASTRO ELECTRONICS, 10A SPRINGBANK ROAD, CHESTERFIELD, DERBS.

SPECIAL OFFER

Ferranti ZN414 Radio I.C. £1-06

NEW PRECISION TIMER I.C.

Ferranti ZN1034E £2-90

Ferranti Applications Booklet for ZN414, 25p includes circuits for earpiece radios, loudspeaker radios, crystal controlled receiver and frequency standard receiver.

RADNAGE RADIO & ELECTRONICS

2 Bottom Road, Radnage, High Wycombe, Bucks.

Prices inclusive plus 15p Post and Packing

Mail order only

ENGINEERS

FREE

YOURSELF FOR A

BETTER JOB WITH MORE PAY!



Do you want promotion, a better job, higher pay? "New opportunities" shows you how to get them through a low-cost, Home Study Course. There are no books to buy and you can pay as you learn.

This easy to follow GUIDE TO SUCCESS should be read by every ambitious engineer. Send for this helpful 76-page free book NOW! No obligation, nobody will call on you. It could be the best thing you ever did.

CHOOSE A BRAND NEW FUTURE HERE

CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

- | | | |
|---|--|---|
| <input type="checkbox"/> ELECTRICAL ENGINEERING
City & Guilds Wiring and Installations
<input type="checkbox"/> C. G. Electrical Tech-Primary
<input type="checkbox"/> Gen. Electrical Eng. | <input type="checkbox"/> RADIO & TV
Gen. Radio and TV Eng.
<input type="checkbox"/> Radio Servicing, Maintenance and Repairs
<input type="checkbox"/> Practical Radio & Electronics (with self-build kit)
<input type="checkbox"/> Radio Amateurs' Exam | <input type="checkbox"/> DRAUGHTSMANSHIP
Institute of Engineering Draughtsmen & Designers
<input type="checkbox"/> General Draughtsmanship
<input type="checkbox"/> Architectural Draughtsmanship
<input type="checkbox"/> Technical Drawing |
| <input type="checkbox"/> AERONAUTICAL ENGINEERING
Air Registration Board Certificates
<input type="checkbox"/> Gen. Aero Engineering | <input type="checkbox"/> ELECTRONIC ENGINEERING
Gen. Electronic Eng.
<input type="checkbox"/> Practical Electronics (with kit) | <input type="checkbox"/> CONSTRUCTION & BUILDING
Institute of Building
<input type="checkbox"/> Construction Surveyor's Inst.
<input type="checkbox"/> Clerk of Works Diploma
<input type="checkbox"/> C. & G. Building Quantities
<input type="checkbox"/> General Building
<input type="checkbox"/> General Civil Eng.
<input type="checkbox"/> Heating, Ventilating & Air Conditioning
<input type="checkbox"/> Carpentry & Joinery |
| <input type="checkbox"/> AUTO ENGINEERING
City & Guilds Auto Engineering
<input type="checkbox"/> Practice Inst. Motor Industry
<input type="checkbox"/> M. A. A./I. M. I. Management Diploma
<input type="checkbox"/> Gen. Auto Engineering
<input type="checkbox"/> Auto Diesel Maintenance
<input type="checkbox"/> Motor Mechanics
<input type="checkbox"/> Service Station and Garage Management | <input type="checkbox"/> AGRICULTURAL ENGINEERING | <input type="checkbox"/> MECHANICAL ENGINEERING
Society of Engineers
<input type="checkbox"/> Inst. Engineers and Technicians
<input type="checkbox"/> General Mechanical Eng.
<input type="checkbox"/> Welding
<input type="checkbox"/> Maintenance Eng.
<input type="checkbox"/> General Diesel Eng. |
| <input type="checkbox"/> TELECOM-MUNICATIONS
City & Guilds Telecommunications | <input type="checkbox"/> REFRIGERATOR SERVICING | <input type="checkbox"/> Painting & Decorating
<input type="checkbox"/> Plumbing
<input type="checkbox"/> C. E. I. (Part I)
<input type="checkbox"/> Inst. Cost & Management
<input type="checkbox"/> Accountants
<input type="checkbox"/> Works Management etc. etc. |

POST NOW

G.C.E.

—58 'O' & 'A' Level Subjects
—over 10,000 Group Passes!

Aldermaston College

Dept. TPE08, Reading RG7 4PF

also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London EC2Y 5ET. Tel. 01-628 2721.

NAME (Block Capitals)

ADDRESS


Postcode

Other subjects of interest Age

Accredited by C.A.C.C. Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Sinclair System 4000

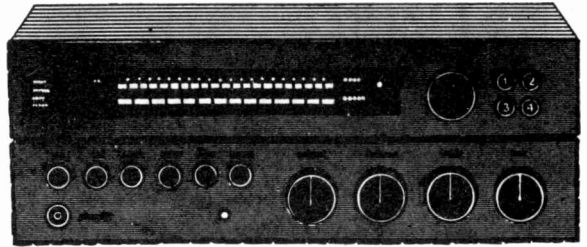

The watts...

Black, beautiful, and incredibly good value. Sinclair's two self-contained hi-fi units - in one handsome, elegant style.

A 17 watts per channel amplifier and a matching FM tuner.

The amplifier offers 17 W RMS per channel output... 0.05% total harmonic distortion... and a price tag

of around £50.

The System 4000 tuner completes a handsome, hard-working system.

Engineered and designed to accompany the System 4000 stereo amplifier, the FM tuner matches it in specification and design - and at around £40 completes a system of outstanding value.

and the wherefores.



Get the full technical specifications...

See what impartial hi-fi journals thought of its performance...

And read up on the rest of the Sinclair range...

It's all in the Sinclair hi-fi range fact-file.

Send for Sinclair's fact-file now!

See if the answer's here - the information on the component you've been looking for.

Simply cut the coupon and

send it to the no-stamp-needed FREEPOST address below.

We'll send you the Sinclair fact-file - giving you all you need to know about System 4000, and the rest of the Sinclair hi-fi range.

Plus information about a few extras you're sure to find rather interesting.

You've plenty to gain... so cut the coupon now!

Sinclair Radionics Ltd,
London Road, St Ives,
Huntingdon, Cambs., PE17 4HU
St Ives (0480) 64646

Please send me the Sinclair range fact-file immediately

Name

Address

40/PE/8/75

To: Sinclair Radionics Ltd,
FREEPOST, St Ives,
Huntingdon, Cambs., PE17 4BR

Please print

sinclair

RTVC*

NEW!

VISCOUNT IV STEREO SYSTEM

System 1a. £65.00

The new 20+20 watt Stereo Amplifier incorporating the latest silicon transistor solid state circuitry, the RT-VC VISCOUNT IV gives you a powerful 20 watts RMS per channel into 8 ohms. Superb teak-finished cabinet, with anodised fascia to harmonise with any decor. Polished trim and knobs.

The VISCOUNT IV has a comprehensive range of controls - volume, bass, treble, balance, mono/stereo, mode selector, and scratch filter.

Front panel socket for stereo headphones. And a host of sockets at the rear - for left and right speakers, tape recorder, auxiliary, tuner, disc and microphone.

SPECIFICATION: 20 watts RMS per channel 40 watts peak. Suitable 8-15 ohms speakers. Total distortion @ 10 watts better than 0.2%. Six switched inputs: 1. Magnetic P.U. - 3 millivolts @ 47 K ohms (R.I.A.A.); 2. Crystal/ceramic P.U. - 50 millivolts @ 50 K ohms (R.I.A.A.); 3, 4, 6. Tape Tuner/Aux. - 140 millivolts @ 50 K ohms (flat frequency response); 5. Microphone - 3 millivolts @ 50 K ohms (flat frequency response).

CONTROLS: Push button ON/OFF, stereo/mono, scratch filter, 6 position rotary selector. Individual rotary controls for treble, bass, balance and volume. Headphone socket, tape out socket. Aux. mains output. Frequency response: 25 Hz to 25 KHz @ full rated output. Signal to noise ratio: better than -50 dB on all inputs. Tone control range: Bass ± 15 dB @ 50 Hz; Treble ± 12 dB @ 10 KHz. Power requirements: 200-250V A.C. mains @ 60 watts. Approx. size: 15½" x 3" x 10".

MP60 type deck with magnetic cartridge, de luxe plinth and cover.

Two Duo Type III matched speakers - enclosure size approx. 19½" x 10½" x 7½" in simulated teak. Drive unit 13" x 8" with 3" tweeter, 15 watts handling, 30 watts peak.

Complete System with these speakers £69.00 +£6.50 p & p.

System 2. £81.00

Viscount IV amplifier (As System 1a)
MP60 type deck (As System 1a)

Two Duo Type III matched speakers

- Enclosure size approx. 27" x 13" x 11½". Finished in teak simulate.

Drive units 13" x 8" bass driver, and two 3" (approx.) tweeters, 20 watts RMS, 8 ohms frequency range - 20 Hz to 18,000 Hz.

Complete System with these speakers £85.00 +£7.60 p & p.

PRICES: SYSTEM 1a
Viscount IV R103 amplifier £25.00+£1.90 p & p.
2 Duo Type III speakers £30.00+£6.50 p & p.
MP60 type deck with Mag. cartridge de luxe plinth and cover £20.00+£3.30 p & p.
Total if purchased separately: £75.00
Available complete for only: **£65.00** +£6.50 p & p.

PRICES: SYSTEM 2
Viscount IV R103 amplifier £25.00+£1.90 p & p.
2 Duo Type III speakers £46.00+£7.50 p & p.
MP60 type deck with Mag. cartridge de luxe plinth and cover £20.00+£3.30 p & p.
Total if purchased separately: £91.00
Available complete for only **£81.00** +£7.60 p & p.



20x20 SYSTEM

Scotland P & P Surcharge System 1a £1.75 System 2 £3.50

EMI SPEAKERS AT FANTASTIC REDUCTIONS

LE-4 SPEAKERS

Superb performance and beautifully finished in selected teak veneers. A professional standard four-way speaker system giving 25 watts RMS power handling. Bass unit is 14" x 9" with 8" x 5" unit for mid-range and twin 3" high frequency units to give monitor type quality and performance.

Specification - Size 33" x 14" x 16" approx. Impedance 8 ohms. Power handling 25W RMS. (Peak 50 watts.) Frequency range 35 Hz-20 KHz.

Our Price £34.00
(normally £66.00)+£5.80 p & p.

EASY TO BUILD SPEAKER KITS

These superb simulated teak-finished speaker kits have been specially designed by RT-VC for the cost-conscious hi-fi enthusiast who wants top quality speakers but doesn't want to spend the earth. Built to EMI's exacting specification, these new RT-VC speaker kits (350 type kit) incorporate 13" x 8" woofer, 3½" tweeter and matching crossover.

Easily put together with just a few basic tools. **Specification (each speaker):** Impedance 8 ohms. Power handling 15 watts RMS (30 watts peak). Response 20-20,000 Hz. Size 20" x 11" x 9½" approx. Comparable built units (EMI LE3) sold elsewhere for over £45 pair.

£22.00 pair complete

+£5.20 p & p. Complete with crossover Components and circuit diagram



EMI 350 KIT

System consists of a 13" x 8" approx. woofer with a 3" tweeter, crossover components and circuit diagram. Frequency response: 20 Hz to 20 KHz. Power handling 15 watts RMS into 8 ohms. (Peak 30 watts.)

£6.50 +£1.20 p & p.


Complete with crossover Components and circuit diagram



DECCA STEREO AMPLIFIER CHASSIS

Specification: 4+4 watts into 8 ohms. Input Sensitivity 4mV into 47K (for magnetic cartridges). AC Mains only 240V. Controls - volume, bass, treble, on/off, mono/stereo switch. Chassis size 11" x 5½" x 3½" approx.

£6.90 +£1.20 p & p.

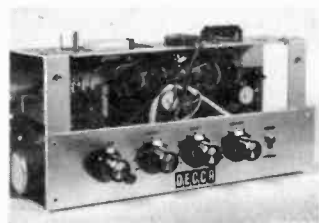

PUSH BUTTON CAR RADIO KIT— THE TOURIST TT*



NO SOLDERING REQUIRED

NOW BUILD YOUR OWN PUSH BUTTON CAR RADIO

Easy to assemble construction kit comprising fully completed and tested printed circuit board on which no soldering is required. All connections are simple push fit type making for easy assembly. Fine tuning push button mechanism is fully built and tested to mate with printed circuit board. **TECHNICAL SPECIFICATION:** (1) Output 4 watts RMS output. For 12 volt operation on negative or positive earth. (2) Integrated circuit output stage, pre-built three stage IF Module.

Controls volume manual tuning and five push buttons for station selection, illuminated tuning scale covering full, medium and long wave bands.

Size chassis 7" wide 2" high and 4 3/4" deep approx. **£9.50** + £1.05 p & p. Speaker including baffle and fixing strip **£2.00** + 45p p & p. Car Aerial Recommended — fully retractable **£1.60** + 40p p & p.

The Tourist I Kit For the experienced constructor. If you can solder on a printed circuit board you can build this model. Same technical specification as Tourist TT. **Price £8.20** + £1.05 p & p.

*STEREO 21 QUALITY SOUND FOR LESS THAN £24.00



Stereo 21, easy to assemble audio system kit. No soldering required.

The unit is finished in white P.V.C. and the acrylic top presents an unusually interesting variation on the modern deck plinth. Includes — BSR 3 speed deck, automatic, manual facilities together with stereo cartridge.

Two speakers with cabinets. Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.

Specifications — For the technically minded: Input sensitivity 600mV. Aux. input sensitivity 120mV. Power output 2.7 watts per channel. Output impedance 8–15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs — radio, tape, etc. and outputs for taping discs. Overall Dimensions. Speakers approx. 15 1/2" x 8" x 4". Complete deck and cover in closed position approx. 15 1/2" x 12" x 6".

Complete only £23.20 + £3.00 p & p.

Extras if required. Optional Diamond Styli **£1.60**. Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance **£5.80**.

*DISCO AMPLIFIER



Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties. Output 20 watts RMS into 8 ohms (suitable for 15 ohms).

Inputs *4 electrically mixed inputs. *3 individual mixing controls. *Separate bass and treble controls common to all 4 inputs. *Mixer employing F.E.T. (Field Effect Transistors). *Solid State circuitry. *Attractive styling.

INPUT SENSITIVITIES — Input — 1). Crystal mic. guitar or moving coil mic. 2 and 10mV. (Selector switch for desired sensitivity.) — Inputs — 2). 3). 4). Medium output equipment — ceramic cartridge, tuner, tape recorder, organs, etc. — all 250mV sensitivity. AC Mains, 240V operation. Size approx: 12 1/2" x 6" x 3 1/2".


£20.00 + £1.35 p & p.

*8 TRACK HOME CARTRIDGE PLAYER



Elegant self selector push button player for use with your stereo system. Compatible with Viscount IV system, Unisound module and the Stereo 21. Technical specification Mains input, 240V. Output sensitivity 125mV. Comparable unit sold elsewhere at **£24.00** approx. Yours for only

£16.20 + £1.70 p & p.

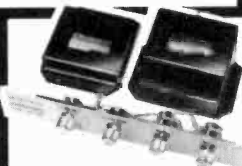


BUILD YOUR OWN *STEREO AMPLIFIER

For the man who wants to design his own stereo — here's your chance to start, with Unisound — pre-amp, power amplifier and control panel. No soldering — just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only.

Also available with 2 speakers (7" x 4") **£10** + £1.75 p & p. **£8.95** + £1.05 p & p.

PORTABLE DISCO CONSOLE*

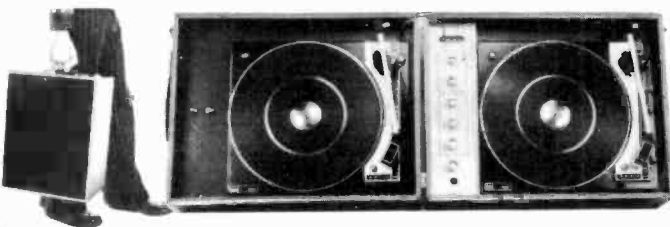

INCORPORATES: Pre-Amp with full mixing facilities, including switched input for mic with volume control, switched input for auxiliary with volume control, bass and treble controls, volume control and blend control for turntables. Two B.S.R. MP60 type single play professional series decks, fitted with crystal cartridges.

TECHNICAL SPECIFICATION:
Pre-amp — Output — 200mV.
Auxiliary inputs — 200mV and 750mV into 1 meg. Mic input — 6mV into 100K. 240 volt operation.
Turntables capacity — 7", 10" or 12" records. Rumble, wow and flutter. Rumble Better than —35dB. Wow Better than 0.2%. Flutter Better than 0.06% (Gaumont kale meter).
Finish — Satin black mainplate with black turntable mat inlaid with brushed aluminium trim. Tonearm and controls in black and brushed aluminium.

Console size — Unit Closed — 17 1/2" x 13 1/2" x 8 1/2" (app.) Unit Open — 35 1/2" x 13 1/2" x 4 1/2" (app.) This disco console is ideally matched for the Reliant IV and Disco 50 or any other quality amplifier. The unit is finished in black PVC with contrasting simulated teak edging, diamond spun control knobs with matching control panel.

Yours for only £57.00 + £6.50 p & p.



DO NOT SEND CARD

Just write your order giving your credit card number

Mail orders to Acton. Terms C.W.O. All enquiries stamped addressed envelope. Goods not despatched outside U.K.

Leaflets available for all items listed thus* Send stamped addressed envelope. All items subject to availability. Prices correct at 1st June 1975 and subject to change without notice.

All prices include V.A.T. at 25% rate.

R T V C

21D HIGH STREET, ACTON, LONDON W3 6NG
323 EDGWARE ROAD, LONDON W2

Personal Shoppers EDGWARE RD: 9 a.m.—5.30p.m. Half day Thurs
ACTON: 9.30a.m.—5p.m. Closed all day Wed.

The Shop Window for the Very Best...

CPC



**COMBINED
PRECISION
COMPONENTS
(PRESTON) LTD**

Department PE
194-200 North Rd.
Preston PR1 1YP
Tel: 55034
Telex: 677122

TOSHIBA VALVES

Type	Price (p)	Type	Price Each (p)
DY87	30.0	AD149	40
DY802	30.0	AD161	38
ECC82	28.0	AD162	38
EF80	29.5	AF114	24
EF183	34.5	AF115	21
EF184	34.5	AF116	22
EH90	35.5	AF117	19
PC900	24.5	AF118	50
PC909	40.0	AF139	35
PCC189	45.0	AF178	45
PCF80	31.5	AF180	45
PCF86	39.0	AF181	45
PCF801	42.0	AF239	40
PCF802	40.0	AF240	60
PCL82	39.0	BC107	11
PCL84	39.0	BC108	10
PCL85	44.5	BC109	14
PCL86	41.0	BC109C	14
PFL200	59.5	BC113	13
PL38	55.5	BC116A	19
PL84	25.0	BC117	14
PL504	64.5	BC125B	15
PL506	67.0	BC132	25
PL519	£1.60	BC135	15
PY88	35.5	BC137	19
PY800	33.0	BC138	26
PY500A	85.0	BC142	23
		BC143	25

SEMI CONDUCTORS

Type	Price Each (p)	Type	Price Each (p)
AC127	17	BC148	10
AC128	13	BC153	15
AC141K	25	BC154	15
AC142K	25	BC157	14
AC151	20	BC158	10
AC154	18	BC159	11
AC155	18	BC173	18
AC156	20	BC178B	20
AC176	22	BC182L	12
AC187	19	BC183L	12
AC187K	24	BC187	25
AC188	17	BC214L	15
AC188K	26	BC232	28
AD142	45	BC337	19

DIDES

Type	Price Each (p)	Type	Price Each (p)
BD124	75	BF179	40
BD131	45	BF180	31
BD132	39	BF181	32
BD160	£1.39	BF184	25
BD235	43	BF185	25
BD237	52	BF194	9
BDX32	£2.40	BF195	8
BF115	20	BF196	10
BF160	15	BF197	12
BF167	20	BF200	25
BF173	20	BF218	30
BF178	35	BF224	23
BF179	40	BF258	34
BF180	31	BF338	28
BF181	32	BF337	35
BF184	25	BF355	54
BF185	25	BFX86	28
BF194	9	BFY50	19
BF195	8	BFY52	20
BF196	10	BSY52	35
BF197	12	BT106	£1.20
BF200	25	BU105/02	£1.95
BF218	30	BU108	£2.10
BF224	23	BU208	£2.95
BF258	34	E1222	30
BF338	28	MJE340	45
BF337	35	OC71	15
BF355	54	OC72	16
BFX86	28	R2008B	£2.00
BFY50	19	R2010B	£2.00
BFY52	20	RCA16334	80
BSY52	35	RCA16335	80
BT106	£1.20		
BU105/02	£1.95		
BU108	£2.10		
BU208	£2.95		

INTEGRATED CIRCUITS

Type	Price Each	Type	Price Each
BA115	7	TAA550	49p
BA145	14	TAA700	£2.95
BA148	19	TBA120AS	£1.00
BA154/201	11	TBA120SQ	£1.00
BY126	11	TBA480Q	£1.40
BY127	12	TBA520Q	£2.35
BY159	27	TBA530Q	£1.75
BY206	21	TBA540Q	£1.75
BY238	25	TBA560Q	£2.40
OA90	6	TBA800	£1.50
OA202	7.5	TBA920Q	£2.90
IN60/OA91	5	TBA990Q	£2.90

Type	Price Each	Type	Price Each
NEW TOSHIBA TUBES		TCA2700	£2.90
15" A49/191X	£48.95	ETR6016	£2.00
20" 510DJ22	£50.75	TB8630D	£1.50
22" A56/120X	£54.25		

EHT MULTIPLIERS MONOCHROME (BARC)		EHT MULTIPLIERS - COLOUR	
Type	Price Each	Type	Price Each
2HD 950MK1, 950	£1.70	11TAQ IIT CVCI, 2 & 3	£4.50
2TD 950MK2, 1400	£1.85	11TAC GEC/Sobell	£4.50
2DAK 1500 (17" & 19")	£1.85	11TAZ GEC 2110	£4.85
2TAK 1500 (23" & 24")	£2.00	11TAM Philips G8	£4.50
		11TBD Philips 550	£4.50
		31CW Pve 691/693	£3.50
		1TH Decca 30 Series	£4.50
		11TAQ Decca 'Bradford'	£4.50
		3TCU Thorn 3000/3500	£5.00
		11HAA Thorn 8000	£1.90
		11HAB Thorn 8500	£4.25

PRICES SUBJECT TO 25% V.A.T.
All goods subject to settlement
discount of 5% 7 days and 2%
monthly.
No postage charges or minimum
order values.
Write or phone for full details now.

...In Prices, Quality and Service.

B. BAMBER ELECTRONICS

5 STATION ROAD, LITTLEPORT, CAMBS., CB6 1QE

Telephone: ELY (0353) 860185 (2 lines) Tuesday-Saturday

TV plugs, metal type, 6 for 50p.
TV sockets, metal type, 5 for 50p.
TV line connectors (back-to-back socket), 5 for 50p.
T03 transistor insulator sets, 10 for 50p.
Mixed electrolytics, large bag, £1.
PC board withdrawal handles, mixed coils, 8 for 50p.
Solder, 20SWG, 80/40 alloy, approx. 9yds, 25p.
OAB1 diodes, 15 for 25p.
OC200 transistors, 6 for 50p.
Parapex coil formers, 1 1/2in x 1/2in dia., 5 for 25p.
Turret tags, 1/2in dia., 25p pack.
Rotary switches, min. 4 pole 2-way, 2 for 50p.
Telephone type earpiece single, 50p.
Reeds (for reed relays) insert-pole make, 5 for 30p.
Mullard tubular ceramic trimmers, 1-18uF, 6 for 50p (as featured in Rad. Comm. Jan. p. 25).
I.C.s, some coded, 14DIL type, untested, mixed, 20 for 25p.
IF cans 1/2in square, suitable for rewind, 6 for 30p.
Small neons, 6 for 25p.
24V min. reed relays, encapsulated single-pole make, 2 for 50p.
24V 2-9W lamps, MES type, 6 for 20p.
Chassis tags, 25p-pack.
Cable clips, for nailing cable, 15p pack.
Miniature slider switches, 2 pole, 2-way, 5 for 50p.
BSY95A transistors, 6 for 50p.
6-3V 0-3A capless lamps, 10 for 25p.
PNP audio type T05 transistors, 12 for 25p.
Black plastic knobs, 1/2in dia., 1/2in spindle, 4 for 50p.
Ring magnets, 7mm outside dia., 20 for 50p.
Large box of P.C. Boards, containing transistors, I.C.s, trim pots, resistors, capacitors, etc. (not unknown computer rubbish), £3 per box.
1 1/2in polythene chassis mounting fuseholders, 6 for 30p.
LES Lamps, 24V 1-2W, 10 for 40p.

MAINS TRANSFORMERS

All 240V input voltages quoted approx. RMS. (Please quote type no. only when ordering).
TYPE 10/2, 10-0-10V at 2A, £1-50 each.
TYPE 18/2, 18V at 2A, £1-85 each.
TYPE 18/6, 16V at 6A + 45V at 100mA, £4.
TYPE 28/4, 28V at 4A + 125V at 500mA, £4.
TYPE 63/1, 6-3V at 1A, 85p each or 2 for £1-50.
TYPE 129, 400V at 20mA + 200V at 10mA + 6-3V at 500mA, £1-25.
TYPE 72703, 400V at 10mA + 200V at 5mA + 6-3V at 400mA, £1-25.
TYPE T0462, 250-0-250V at 80mA + 6-3V at 2A, £1-75.
RADIOSPARES, 500W AUTO TRANSFORMERS, 100-110-130-220-240-250V tapped input and output, step-up or step-down facility, on-onw equip, £8.
CURLY LEADS, 4 core telephone type, 2 for 20p.
TRANSISTOR HEATSINKS, to take 2 x T018 transistors, screw in clamps, block size 1 x 1/2 x 1/2in, with holes for mounting, 3 for 50p.
VARIABLE STABILISED PSU, solid-state 240V a.c. input, output 0-24V d.c. at 500mA, + 32V d.c. at approx. 50mA. Voltage controlled by external 5kΩ pot. Size 7 1/2 x 4 x 2 1/2in (less 5kΩ pot), £5 each.
THREE-TURN WIRE-WOUND POTS, 5kΩ, for above, 75p each.
LARGE DIE CAST BOXES (brand new ITT) 10 1/2 x 8 1/2 x 2 1/2", £2 each.
25-way ISEP PLUGS AND SOCKETS, 40p set (1 plug + 1 socket).
DIN SPEAKER SOCKETS (2-pin) 4 for 30p.
HIGH QUALITY SPEAKERS, 8 1/2 x 6 1/2in elliptical, only 2in deep, inverse magnet, 4 ohms, rated up to 10W, £1-80 each, or 2 for £2-78 (qty. discount available).
Rotary switches 9-way 4-pole (separate wafers, plastic) 1/2in spindle, 40p each.
Heatrinks (Approx. 3in x 4in x 2in high), 12 pins (drilled for 1 x T03 transistor) brand new, 45p each.

TERMS OF BUSINESS: CASH WITH ORDER (minimum order: £1) POST FREE (UK ONLY). PLEASE ADD 25% VAT.

Export enquiries welcome. Callers welcome. Tues. to Sat. Please enclose S.A.E. with ALL enquiries.



become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

free! Brochure, without obligation to:
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL
Dept. EB85, P.O. Box 156, JERSEY

NAME: _____
ADDRESS: _____

BLOCK CAPS please

SAXON

Money saving high performance audio equipment
DIRECT FROM OUR OWN FACTORIES

GUARANTEED TESTED HIGH PERFORMANCE MODULES—now better value than ever

- SA35** £6.60 Carriage free
35W RMS 25-50V
7 transistors, 7 diodes
- SA50** £8.50 Carriage free
50W RMS 25-65V
7 transistors, 7 diodes
- SA100** £12.50 Carriage free
100W RMS 45-70V
10 transistors, 7 diodes
- 120 watt module complete with built-in supply—extra heavy duty £24.75** Carr. 60p
- ★ 25Hz-25kHz
 - ★ 0.2% distortion
 - ★ Noise—80dB
 - ★ 500mV into 20K
 - ★ 4-16 ohms
 - ★ Simple wiring
 - ★ Short and open circuit proof
 - ★ Continuously rated
 - ★ Top-grade components

POWER SUPPLIES

UNSTABILISED		READY WIRED AND FUSED	
PU45	Suits 2 SA35 or 1 SA50 (4 ohm)	£6.50	Carriage 50p
PU70	Suits 2 SA50 or 2 SA100 (8 ohm)	£9.50	Carriage 60p
STABILISED			
PS45	Suits 2 SA35 or 2 SA50 (4 ohm)	£5.50	Carriage free
MT45	Transformer for above	£3.90	Carriage 50p
PS70	Suits 2 SA100	£6.50	Carriage free
MT70	Transformer for above	£5.50	Carriage 60p

THE SA100 MODULE

N.B. PS70 is not suitable for the SA50

Mk II STEREO DISCO MIXER £29.50

Carr. 50p

This well tried Pre-Amp mixes two decks, handles any ceramic cartridge, and features mic over-ride plus separate full range bass and treble controls on both mic and deck inputs. Ample headphone power is available for P.F.L. May be used for mono and is mains operated. Fitted with sturdy screening case. Controls: Mic vol, bass, treble. Left/Right fade, deck volume, bass, treble, h/phone select, vol, Mains. Size 17½in x 3in x 4in deep.



DISCO MODULE £12.50

Carr. 50p

Thousands sold of this extremely popular mono Pre-Amp. A mic input may be fitted using the VA30 (see below). Low consumption from a 9V battery. Features the same high standards of reproduction as the Stereo version. Controls: H/phone select, vol, Left deck vol, Right deck vol, bass, treble, master vol. Size 12½in x 3in x 2in deep.



3-CHANNEL SOUND-LITE £24.75

Carr. 50p

Only SAXON can supply such incredible value for money. This unit features 3kW power handling, full-wave control, bass, middle, treble AND master controls. Twin loudspeaker jacks for "through" connections. Uses coloured reflector lamps and panel mount next to either of the above. Size 12in x 3in x 2½in deep. Professional standards at a price you can afford!



SINGLE CHANNEL VERSION £7.90 Carr. free
High sensitivity, compact, handles 1kW. Full wave operation


Add 8% VAT to all orders

MULTI-PURPOSE MIXERS


M4HL £25.00 Carr. 60p
M6HL £35.00 Carr. 60p

Featuring multiples of our VA30 module, the M4HL and M6HL fulfil the requirements of all clubs, groups, etc. where a high quality mixer is required. Each channel has one high and one low impedance input, plus volume, treble and bass controls. Input impedances may, if required, be easily changed. The M4HL has four channels, and one output, and the M6HL six channels (12 inputs), and a master control and two outputs. Either unit may be used free-standing or panel mounted. These mixers will feed all types of amplifier. Recommended for their versatility and high performance, and excellent value for money.

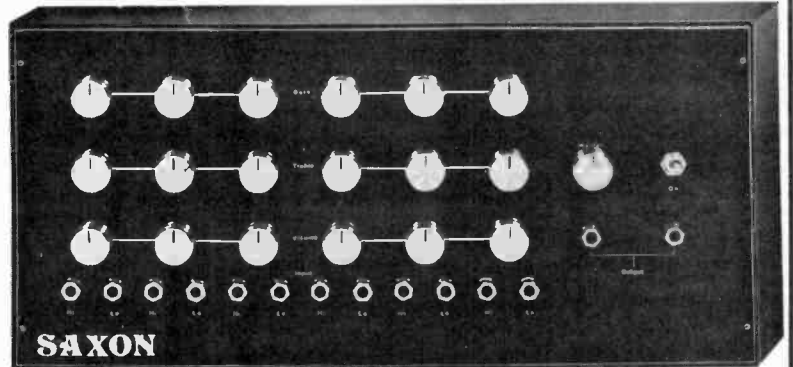VA30 CHANNEL MODULE £3.90 Carr. free
This is the basic channel module in the above mixers and may also be used for extra inputs on either the mono or stereo mixers. Fitted with volume, bass and treble controls, requires just a jack and supply (9-100V)



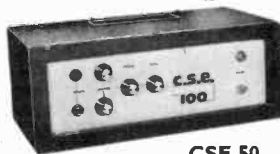SAXON CSE 100 COMPLETE AMPLIFIER £39.90 Carr. 60p
100W of speech and music—Two separately controlled inputs. Wide range bass and treble controls. Sturdy and attractive vyndie case. Twin outputs. Ideal for groups, discos, etc. Fully tested and guaranteed. 50W version identical in appearance.



CSE 50 £33.00 Carr. 60p

NEW!!

SAXON MULTIMIX 100 £57 Carr. £1.00

100W RMS SLIDER controls PLUS master slider. Wide range bass and treble controls—fantastic value. Ideal for complete Disco's, Groups, Clubs, etc.


SAXON MULTIMIX 50 EXACTLY AS ABOVE £45 BUT 50W RMS

CALLERS AND MAIL ORDER:
SAXON ENTERTAINMENTS LIMITED
329-333 WHITEHORSE ROAD • CROYDON CR0 2HS

(Please quote magazine when ordering)

SHOP HOURS: 9 a.m. - 5 p.m. — LUNCH 12.30 - 1.30 p.m. MAIL ORDER DESK: 10 a.m. - 3 p.m.
24-HOUR ANSWER SERVICE TEL. 01-684 6385. TECHNICAL ENQUIRIES 01-684 0098

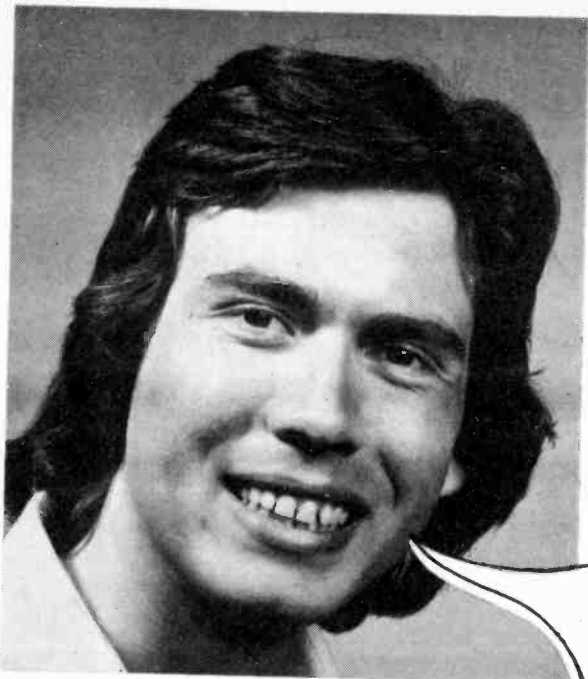SEND 15p FOR OUR NEW 26-PAGE MANUAL—full circuits and details.
TERMS OF BUSINESS: C.W.O., C.O.D. or ACCESS (just send in card number). Send £1 for C.O.D.
Please include S.A.E. with all enquiries.
VAT at 8% must be added to all orders including carriage charges.



*It's the
LONG LIFE!
Catalogue!*

You have heard of "Long Life" batteries, milk and beer, so why not a "Long Life" catalogue? The thought struck me the other night when I visited a friend to chat about a joint project we were building. We needed a few bits and pieces, so he went to a drawer and pulled out a catalogue. Yes, it was the famous Home Radio Components catalogue all right, but at first I didn't recognise it. "Gracious! How old is it?" I exclaimed. "Oh," he said, "about 5 or 6 years." Fascinated, I said, "Can you still use it? Surely, it's years out of date?" "No, not really," he said, "you see, many basic things like plugs, sockets, resistors, capacitors, switches, don't change much. Only the prices change, and Home Radio were wise enough to take all prices out of their catalogue many years ago and put them on a separate list. What's more, they were far sighted enough not to change their catalogue numbers, so all I have to do is to write or phone them occasionally and 'hey presto' along comes an up to date price list. Not a penny extra to pay!" "You really believe in getting your money's worth out of a catalogue," I said. "Sure thing," he replied, "but I might have bought four or five catalogues and still not ordered any more goods. These catalogues must cost Home Radio a bomb to produce, so I imagine they are quite pleased if one of their catalogues produces business for say two years or more. However I must admit it's about time I got myself a new one."

This conversation set me thinking. Home Radio Components really do produce a catalogue that will last and last, and a service to back it up. So if you are keen to save the pennies, send for a copy today. You may still be using it in 1977. On the other hand, if you really like to keep up with the latest developments, Home Radio will be happy to sell you a new one. Each year they spend at least 5 or 6 months revising it in order to bring the latest trends to your notice. Either way you cannot lose. Especially when you bear in mind, that although the initial cost is 65p plus 33p postage and packing, they enclose 14 vouchers each worth 5p if used as directed. Add to that the fact you could easily make it last two or three years . . . well, to borrow a phrase, "You never had it so good". Don't wait, send off the coupon today with your cheque or P.O. for 98 pence.

65p plus 33p POST AND PACKING

POST THIS COUPON
with cheque or PO for 98p.

The price of 98p applies only to customers in the U.K. and to BFPO addresses.

Please write your Name and Address in block capitals

NAME

ADDRESS

HOME RADIO (Components) LTD., Dept. PE
234-240 London Road, Mitcham, Surrey CR4 3HD

Regd. No.
912966, London



HOME RADIO (Components) LTD., Dept. PE, 234-240 London Road, Mitcham, CR4 3HD Phone 01-648 8422

VICTIMS OF V.A.T.

An unworkable law is a bad law. On this count—certainly in the light of experience of those involved in retail distribution—the higher V.A.T. rate as applied to many electronic components must be recognised as a bad law. It must be reconsidered by the Government without delay.

On another count, this law is grossly unfair. Its effects are not equally or fairly distributed. One obvious result is the victimisation of the private constructor.

By the recent ruling of H.M. Customs and Excise, the majority of small to medium power general purpose components are subject to the higher rate of V.A.T. So far as set and equipment manufacturers are concerned, any components of this category which they use carry the higher V.A.T. rate if the end product is for home entertainment or is a domestic appliance. But the lower, standard rate applies to all industrial, professional, scientific and commercial type equipments and to all the individual components from which they are built, regardless of the latter's standing as individual items.

Now consider the position of the private constructor. He faces a 25 per cent V.A.T. charge on the majority of the components he will buy, regardless of the nature of the project in which they are destined to be embodied. This is because the private individual, unlike the set or equipment manufacturer, is not registered for V.A.T. purposes and cannot recover, subsequently, any excess V.A.T. paid on his components.

The unfairness is apparent when one considers the large number of home-built projects that do not come under the headings of home entertainment or domestic appliances. For example: digital clocks, pocket calculators, power controllers, metal locators, gas detectors, car ignition systems, windscreen wiper controllers, electronic games, and test and measuring instruments. As manufactured units, all these items would be subject to the lower rate of V.A.T.

One concession has been won from H.M. Customs and Excise in connection with complete kits of parts for projects of the kind just mentioned (as reported in this issue). But the constructor who buys anything less than a complete kit must be charged the higher rate of V.A.T., where applicable. This is tantamount to adding insult to injury, so far as the many thousands of dedicated, bona fide amateur enthusiasts are concerned; for their ranks include designers, experimenters, as well as genuine constructors—as opposed to kit assemblers. And they all buy the vast majority of their components on a piecemeal basis. They are the victims of V.A.T.

Despite this latest imposition, the constructor is at the end of the day still in pocket when one considers the outlay for a comparable commercial product. This is mainly because his own labour carries no V.A.T. charge (as yet!). But this is no justification for unfair treatment. Furthermore, any debilitating effect this higher V.A.T. may have on home constructors could have more far reaching and serious repercussions in the longer term. Our entire electronics industry could be the poorer in future were private constructor activities to be curbed.

We earnestly hope that the Government will heed the representations made by the electronics industry and that the two-tier system of V.A.T. ratings now applicable to electronic components will be abolished. Individual constructors and component suppliers should in their own (and common) interest make their feelings known to their M.P.

F. E. B.

Editor
F. E. BENNETT

Editorial
R. D. RAILTON *Assistant Editor*
D. BARRINGTON *Production Editor*
G. GODBOLD *Technical Editor*
R. W. LAWRENCE, B.Sc.

Art Dept.
J. D. POUNTNEY *Art Editor*
D. J. GOODING
R. J. GOODMAN
K. A. WOODRUFF

Advertisement Manager
D. W. B. TILLEARD
Phone: 01-634 4202


P. J. MEW
Phone: 01-634 4210

C. R. BROWN, *Classified*
Phone: 01-634 4301

Editorial & Advertising Offices:
Fleetway House, Farringdon St.
London EC4A 4AD
Phone: Editorial 01-634 4452
Advertisements 01-634 4202

T.V. SOUND SEPARATOR

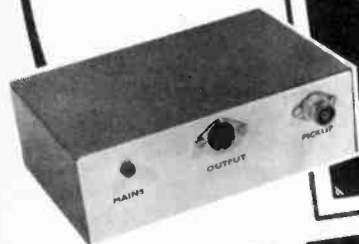By D. S. GIBBS & I. M. SHAW* C. Eng., M.I.E.E.



THE standard of sound quality transmitted with 625-line television programmes is equal to that of the v.h.f. f.m. broadcasts and yet it is a sad fact that most TV receivers give a standard of sound reproduction little better than a transistor radio. To most of the public, cabinet styling and picture size are of paramount importance and little thought is given to the sound reproduction of the set. Consequently there is very little market for sets with good sound reproduction and those that exist are very expensive.

METHODS AVAILABLE

The ideal solution for the hi-fi enthusiast would be to feed the TV sound channel through his existing equipment. There are three possible ways this can be done:

- By a direct audio feed from the set via an audio isolating transformer.
- By building a complete TV sound tuner.
- By building a device to pick up the stray 6MHz radiation from the i.f. strip of the TV set.

*Ferranti Ltd.

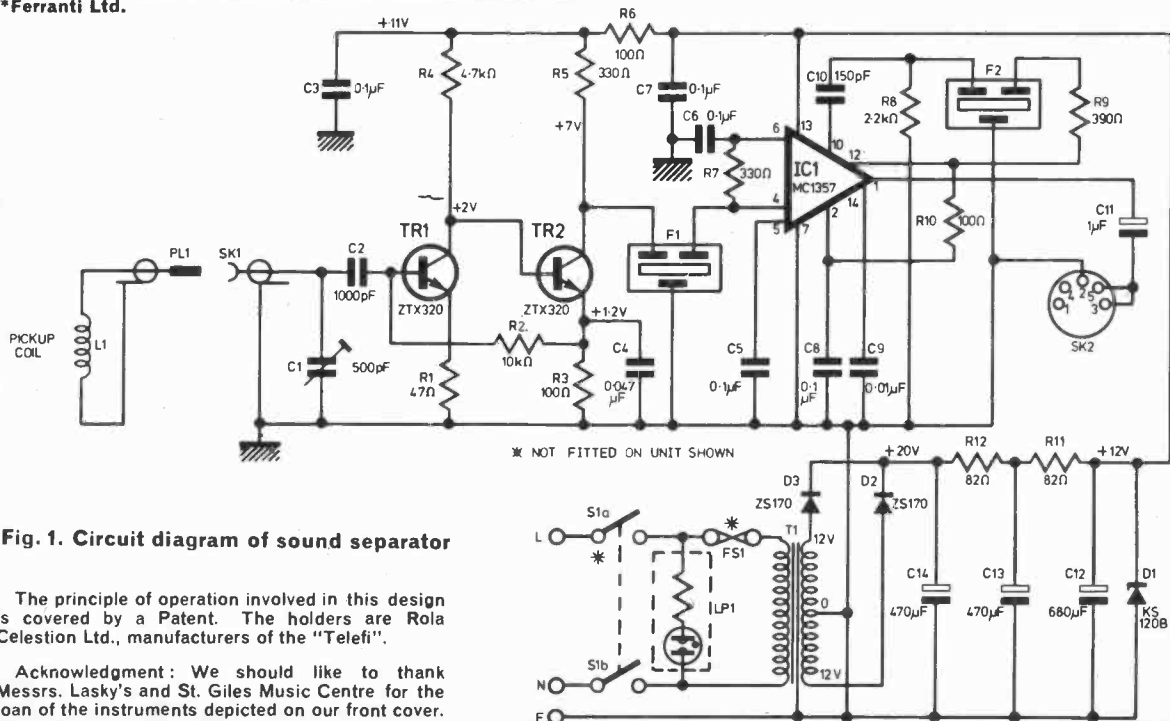


Fig. 1. Circuit diagram of sound separator

The principle of operation involved in this design is covered by a Patent. The holders are Rola Celestion Ltd., manufacturers of the "Telefi".

Acknowledgment: We should like to thank Messrs. Lasky's and St. Giles Music Centre for the loan of the instruments depicted on our front cover.

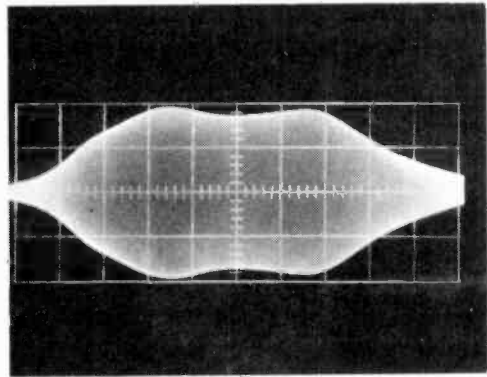
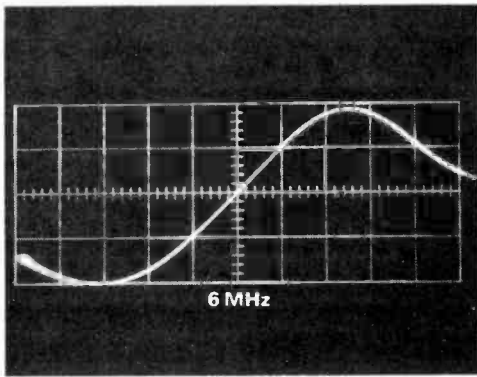


Fig. 2 (left). Response of discriminator. Horizontal scale is approximately 50kHz per division and the output has good linearity over this. (Right) Response of input stage and filter indicating a bandwidth of about 300kHz

Method (a) is probably the simplest—but as it requires modifications to the TV set it cannot be used with rented sets. Also the audio transformer must be capable of withstanding full mains voltage between its windings as there is a possibility of the chassis of the set being “live”.

Method (b) is the most complex and expensive as it requires a completely separate tuner and i.f. strip. As these are already present in the TV set it seems a little wasteful to duplicate them—which leads us to method (c). This makes use of the existing tuner and i.f. strip in the TV set by picking up the stray 6MHz radiation from the sound i.f., amplifying and filtering it and then detecting it. This method requires few components, is easy to construct and align, and requires no direct connection to the TV set. Consequently this method was chosen for the unit described here.

CIRCUIT DESCRIPTION

The circuit diagram of the unit is shown in Fig. 1. The pickup coil L1 is tuned to 6MHz and is positioned on the outside of the TV set to pick up the maximum level of 6MHz radiation.

The output signal from the coil is then amplified by TR1 and TR2. These give a voltage gain of about 100 and provide a suitable output impedance to match the ceramic filter F1. This filter has a bandwidth of about 300kHz and provides the main selectivity of the unit. The output of the filter is applied to the MC1357 limiter and discriminator. This gives a high degree of limiting—thus removing noise and a.m. components—and the output of the limiter drives a quadrature detector.

An unusual feature of this circuit is the use of a ceramic filter element in the quadrature detector. The Murata CDA 6.0 MC filter is specially designed for this purpose and the associated component values have been chosen to give the best compromise between linearity and output. The use of a ceramic filter element in the discriminator means that there is virtually no alignment to do other than peak up the pickup coil—and this is very non critical in any case.

The de-emphasis time constant of 75 μ s is defined by the 0.01 μ F capacitor connected to pin 14 of the i.c.

COMPONENTS . . .

Resistors

R1	47 Ω	R7	330 Ω
R2	10k Ω	R8	2.2k Ω
R3	100 Ω	R9	390 Ω
R4	4.7k Ω	R10	100 Ω
R5	330 Ω	R11	82 Ω
R6	100 Ω	R12	82 Ω

0.33 watt 5% carbon film

Capacitors

C1	500pF compression trimmer
C2	1,000pF disc ceramic
C3	0.1 μ F 30V disc ceramic
C4	0.047 μ F 12V disc ceramic
C5	0.1 μ F 30V disc ceramic
C6	0.1 μ F 30V disc ceramic
C7	0.1 μ F 30V disc ceramic
C8	0.1 μ F 30V disc ceramic
C9	0.01 μ F HI-K tubular ceramic
C10	150pF polystyrene
C11	1 μ F 35V tantalum
C12	680 μ F 16V electrolytic
C13	470 μ F 25V electrolytic
C14	470 μ F 25V electrolytic

Filters

F1	Murata SFE 6.0 MA ceramic filter
F2	Murata CDA 6.0 MC ceramic filter

Semiconductors

TR1	ZTX320 Ferranti	D1	KS120B Ferranti
TR2	ZTX320 Ferranti	D2	ZS170 Ferranti
IC1	MC1357PQ Motorola	D3	ZS170 Ferranti

Coil

L1 Wound as described, see text

Miscellaneous

Case—West Hyde Developments, Samos size S3.
P.c.b. (Davian Electronics.)

T1—R.S. Components 12V 6VA miniature mains transformer (Doram).

NE1—R.S. Components miniature neon lamp.

DIN 5 way socket, Belling Lee coax socket, screws, spacers, grommet, connecting wire, TV 75 Ω coax cable.

The printed circuit board, a kit of semiconductors, and the two ceramic filters can be obtained from Davian Electronics, PO Box 38, Oldham, Lancs., OL2 6XJ.



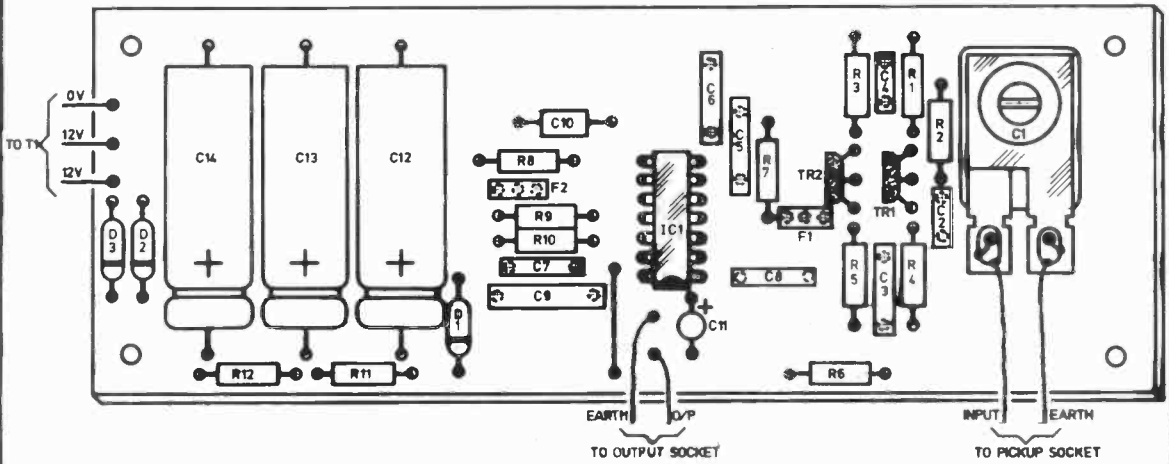


Fig. 3. P.c.b. and component mounting details

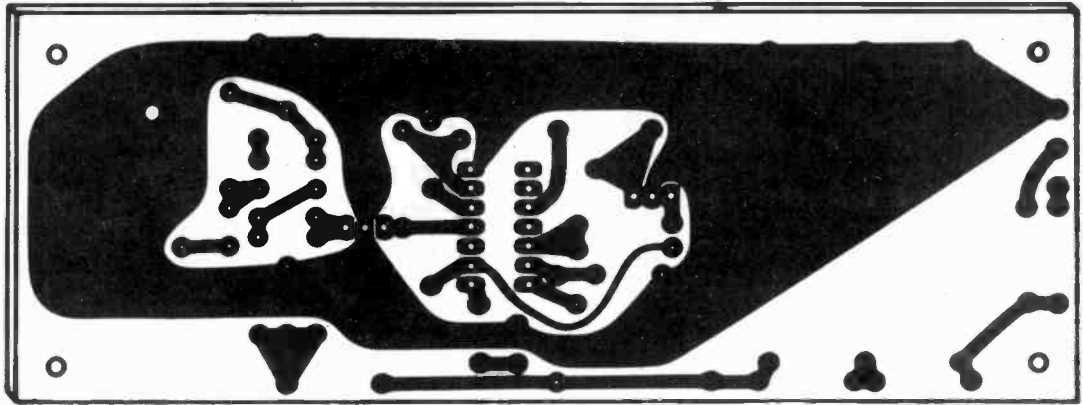

Fig. 4. Details of the pick-up coil L1

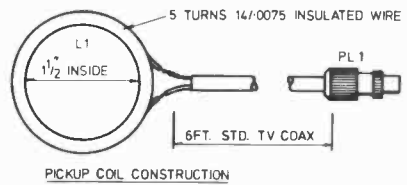

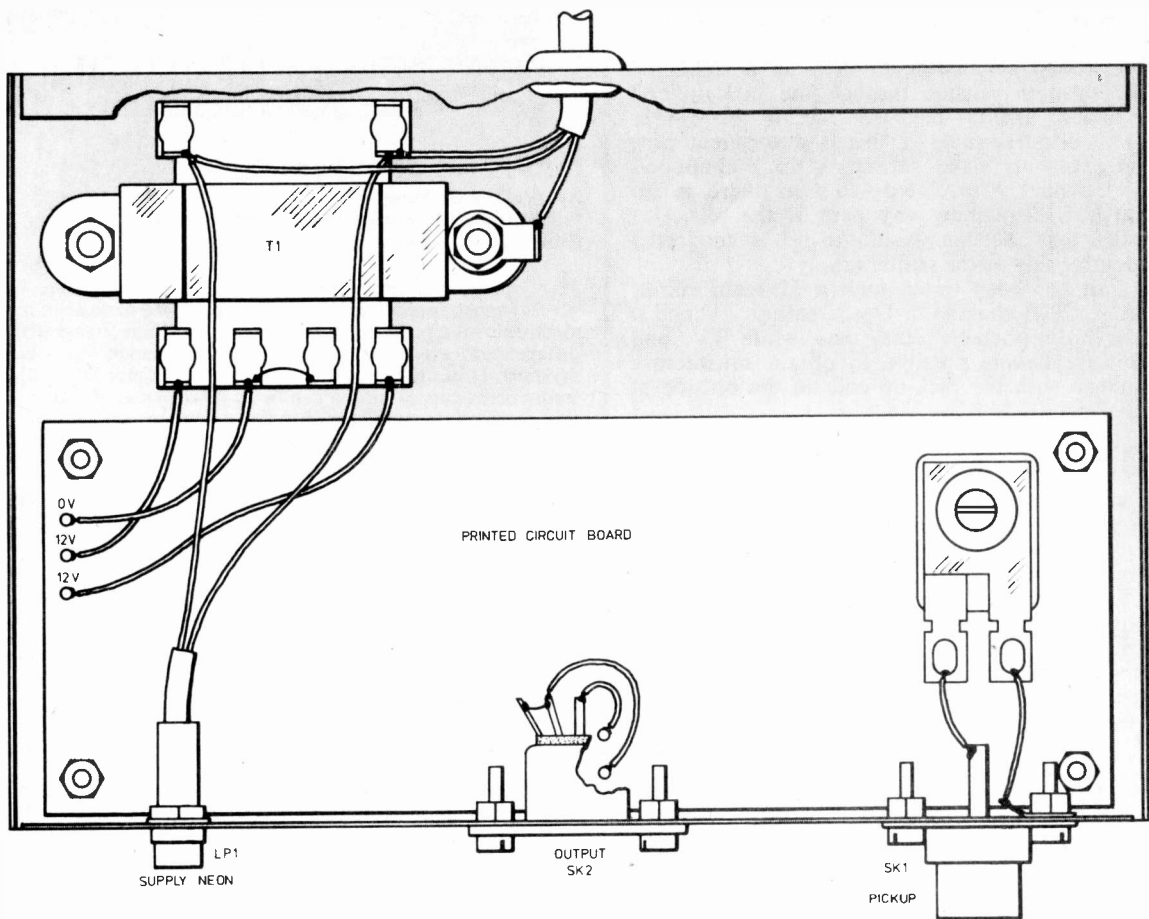


Fig. 5. Assembly details of sound separator

CONSTRUCTION

Most of the components are mounted on the printed circuit board shown in Fig. 3. If you decide to make your own board the copper pattern shown should be followed carefully or stability problems may arise. Do not use Veroboard.

The assembled printed circuit board is a complete module and can be incorporated into your hi-fi system if desired. Alternatively it can be built up as a separate unit as shown in the illustrations.

The prototype unit was built into a West Hyde Developments' Samos case size S3. An assembly diagram for this is given in Fig. 5.

On the latest R.S. Components' 6VA miniature mains transformers the screen tag is at the bottom and it will be necessary to connect a wire to this tag before the transformer is mounted in the box, as this tag is inaccessible afterwards. The assembled printed circuit board is mounted on four $\frac{3}{8}$ in (9.525mm) spacers, and after this has been fixed in place the coax. socket, DIN socket and the neon lamp can be inserted and the unit wired up.

No mains switch or fuse have been included as many amplifiers have a switched mains output to power auxiliary equipment, but these can easily be added by the constructor if desired.

PICK-UP COIL

The pick-up coil L1 consists of five turns of ordinary connecting wire (14/0076 insulated wire was used in the prototype) wound around a 1.5in (38.1mm) diameter former. The coil thus formed is soldered to the end of a length of standard Band I/III TV coaxial cable, and the whole assembly is then bound with p.v.c. insulating tape so that the coil and its connections are completely covered. The coax. cable forms part of the tuning capacitance of the coil but the length is not critical and anything up to about 10ft (3.048m) should be satisfactory. A 6ft (1.8288m) length was used with the prototype unit (Fig. 4).

ALIGNMENT

Before switching on check the circuit carefully for errors and make sure that all the semiconductors are connected the right way round.

Connect the output of the unit to an amplifier and switch on. You will probably hear a selection of foreign stations at first but when the pickup coil is placed near to the TV set the TV sound channel should be heard. Move the pick-up coil around over the outside of the TV set until the position giving minimum background noise is found. Then adjust

C1 for best sensitivity and seal it with a blob of adhesive. Once the optimum position for the pick-up coil has been found it can be fixed in position with adhesive tape.

It is found impossible to pick up a signal of sufficient strength outside the set, the pick-up coil can be placed inside—near to one of the 6MHz sound i.f. coils. However if this is done great care must be taken to make sure that the pickup coil is very thoroughly insulated—so that there is no possibility of it touching any part of the set. Also make sure that the chassis of the set is connected to the neutral side of the mains supply.


This unit has been tested with a Marconi colour TV (T.C.E. 3000 chassis), a Decca colour TV and a Ferguson 3816 portable black and white TV, and in each case it was possible to obtain satisfactory performance with the pick-up coil on the outside of the set.

USING THE TUNER

It is subjectively rather strange to hear the sound coming from a different direction to the picture—so it will usually be necessary to move one of the loudspeakers so that it is close to the TV set. This should not cause any problems with black and white sets, but colour sets are very sensitive to external magnetic fields and if a loudspeaker is placed too close some interesting effects on the picture may be obtained! In practice it will usually be sufficient to place the loudspeaker a few feet to one side or behind a colour TV.

If a buzz is noticed on the output of the tuner this could be either intercarrier buzz from the TV set or an earth loop. It should be possible to remove the former by a slight adjustment to the tuning or contrast controls of the TV set. An earth loop will be present if both the unit and the amplifier are separately earthed and the cure is to disconnect one of the earths. It is probably best to disconnect the earth to the tuner unit so that it is then earthed via the amplifier.

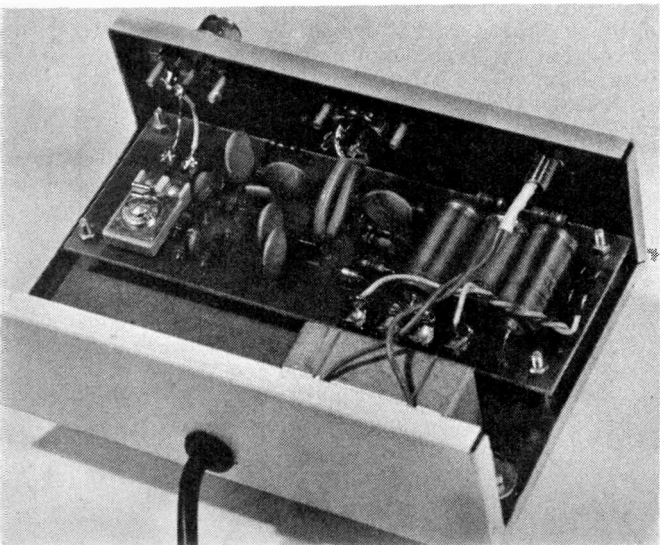This unit will not operate with 405-line receivers as these do not have a 6MHz sound i.f.. Also overseas readers should note that in many countries a sound i.f. of 4.5 or 5.5MHz is used. It should be possible to modify the unit to operate at these frequencies by using the appropriate ceramic filters but the necessary experimental work must be left to the constructor. ★



BOOK REVIEWS

IC OP. AMP. COOKBOOK

By Walter G. Jung
Published by Prentice/Hall International
Clothbound. Price £6.60

OF operational amplifiers appearing in this magazine the 741 must surely be the most familiar. We have seen it in electronic music circuits, ramp generators, filters, integrators, differentiators etc. To many this "gain packet" is still a mystery. It has the qualities of a super-transistor but at high frequencies cannot hold a candle to its forebear. Of course, this criticism does not apply to the whole op. amp. family.

Obviously then, although the 741 can provide a fantastic range of audio and d.c. application it still has its limitations.

It follows, that to make the best use of these now standard design tools, one must understand the language of manufacturers' literature for selection and know the basic rules for design.

The book is arranged in three parts: Part I introduces op. amp. basics and the evolution of general purpose and specialised groups. Operating procedures and precautions in use completes this section. Part II covers practical circuit applications: signal generators, regulators, signal processors and audio designs. Some of the more unusual op. amps. are examined at length.

Part III consists of two appendixes of manufacturers' data.

Following the tradition of all good cookbooks this does not stint on the recipes as there are over 250 practical circuit applications.

In all, an instructive reference to anyone interested in op. amp. design techniques.

G.G.

PUBLISHER'S ANNOUNCEMENT

The contents of PRACTICAL ELECTRONICS is fully protected by international copyright and reproduction of it in any form is prohibited without our consent.

With effect from this announcement any application for permission to reproduce, or use our material in any way or part of, must be made to the Editor. Under no circumstances will permission be given to reproduce material in a similar or competitive publication, without payment. No application need be made in the case of a private constructor, constructing one item for his/her own enjoyment and interest.

THREE TIMES A WINNER

Perhaps no space adventure will ever vie with the manned *Apollo 13*, with its explosive panel incident. Then at least there was first hand assistance with the co-operation of crew and ground based control. However, *Mariner 10* has now completed the third fly-past of Mercury and for the second time there were problems close to the time of passing. In September 1974 the teams responsible for the measurement of plasma high energy particles and the magnetic field, gave up their priorities in order that the imaging teams should have maximum value from the second encounter with Mercury.

Naturally the news that *Mariner* might still be out of control at the due pass time, led to considerable apprehension. Once again there was a mixture of unexpected happenings and a brilliant rescue.

At Mission control the spacecraft had been carefully nursed to keep it operational. The nitrogen, for control jets so vital to the final trajectory guidance, had been conserved by using other means of direction. This took the form of using the pressure of light on the solar panels and the high gain antenna.

The spacecraft had been allowed to operate in an uncontrolled mode its position being checked by the background of stars whose images were registered by telemetry. The roll period was some 60 hours.

TROUBLE

The Canopus tracker allowed the calculation of the position from which the locked mode to the star Canopus could be set. It had been decided that the spacecraft should pass over the dark northern hemisphere at 75 degrees at a height of 125 miles. A few days before this encounter it was required that the roll should be stopped and the star tracker orient the position of *Mariner*.

It was at this point that trouble appeared. During the short period needed to recognise the star Canopus a bright particle passed through the field of view, the tracker mistook this for the star and the spacecraft was commanded to roll in the wrong direction. Instead of the high gain antenna being directed to Earth the vehicle rolled to a null point with the low gain antenna towards Earth and communication was lost.

For some months the stellar magnitude channel had been inoperative, making recognition difficult. The craft could not be controlled from the smaller antennas on the ground. It seemed that the fly-past would be perfect but in silence.



An attempt was made to command from the Goldstone large antenna. This was not successful. The next possibility was Canberra, but with the German spaceprobe *Helios* approaching a critical phase in its mission, this antenna was fully committed.

However, at great risk to this critical point in their programme, the West German control gave up one of the antennas for a short time. This allowed the Madrid station to command the *Mariner* to its correct position. This was accomplished on the day before the encounter was due.

MERCURY FLY-PAST

The pass was highly successful but with some problems in imaging. All the data required by the non-imaging teams was acquired. The data proved that the magnetic field of the planet was intrinsic and not due to the solar wind and its interaction. The magnetic field experiment was confirmed and the results of the first pass extended. The predictions made using the data from the first pass, were very close to those obtained on the third encounter.

The results from the magnetic field, the relativistic particle experiments and the electron component of the solar wind indicate without doubt that Mercury is one of the few magnetised planets in the Solar System.

The question of origin of the magnetism is still not established. Whether it is due to magnetised crust or to a dynamo mechanism of a fluid core is not known for certain. The people operating the *Mariner* experiments lean towards the dynamo hypothesis. One result

that emerges from the experiments is that planets do not have to be rapidly rotating to produce a magnetic field. Mercury's rotation period is 58.5 days.

The low energy solar wind electrons were observed and these suggest that the magnetosphere is like a scaled down version of the Earth's own magnetosphere. The same tadpole like effect appears.

There were intensive bursts of electrons and protons. This indicates, from the rapid but short duration of the bursts, that the controlling magnetic fields must be subject to cancellation. The spiral radius of particles along the field lines of Mercury's orbit is almost the same as the planet's radius.

This fly-by has also provided evidence that there is a continual solar emission of hydrogen and helium nuclei from active centres. These may be due to hot calcium plages where sunspots appear.

ANOTHER X-RAY NOVA

Following the success of the *Ariel 5* discovery of the Cen-Xmas X-ray binary and the nova at the centre of the galaxy, noted in last month's *Spacewatch*, the teams have now made a further addition. This is the new X-ray nova near the Crab Nebula.

The discovery was made when the standard calibration task was being performed. The basis of comparison for the X-ray measurements is the X-ray source in the Crab itself. The field of vision of the X-ray detector is some 17 degree and therefore covers a considerable area of sky.

On April 21 it was noticed that there was an X-ray source near the Crab which was not there in the previous survey. As it is some four degrees from the Crab it cannot be an appendage to it. When first observed the new source was about 7 per cent of the brightness of the Crab source. On the next observation ten days after the discovery the new source had become twice as bright as the Crab source, which itself is the second brightest X-ray source. As the pointing accuracy is extremely high, one minute of arc, there can be no doubt that it is new.

The teams have a right to be excited for this could be another binary system. After the previous discovery it is natural that these should be sought, for the period is important to the physics of these sources. Also there is the possibility that it could be an artefact for there is the chance that the periodicity could be 104 seconds.

A preliminary survey by both optical and radio astronomy has not yet revealed a visual or radio counterpart of the source.

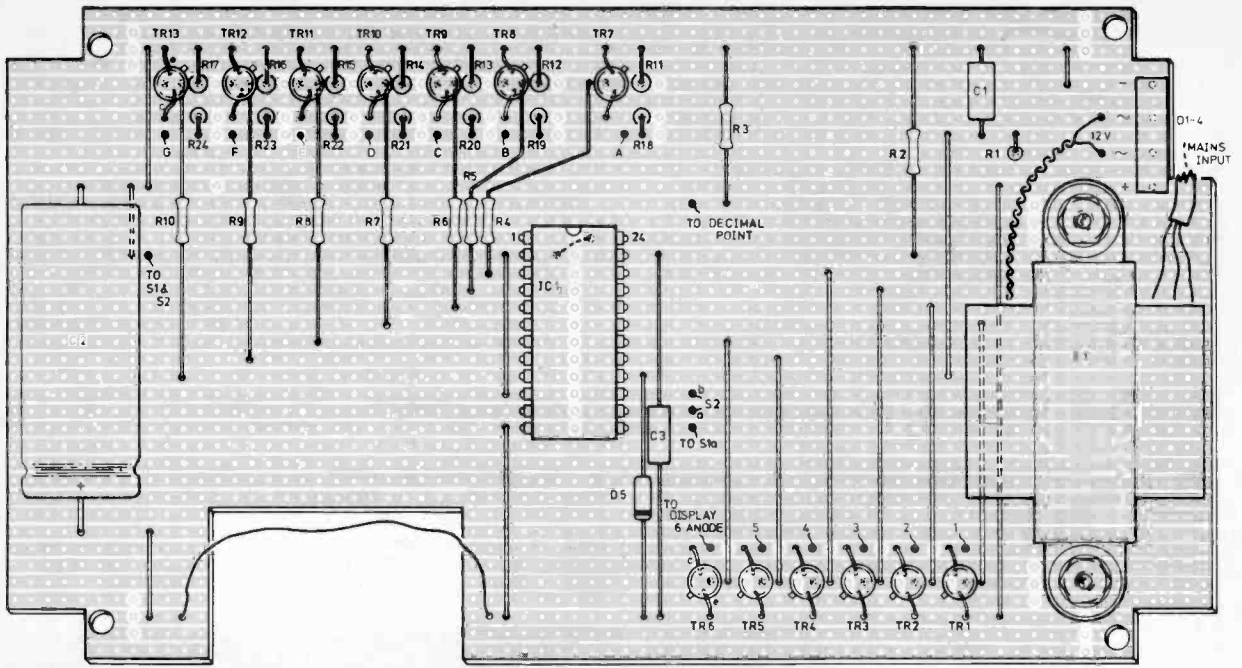


Fig. 2 The main component board mounted in the case. Note the cut-out for access to the Hold and Slow/Fast switches. The display board is mounted on the case lid

CONSTRUCTION

Construction should start with the main clock board. If the recommended board is purchased it will economically furnish both the clock board and the board for the display.

Commence by making all the breaks shown on the board layout. If the clock is to be built into the suggested case then the cut-outs at the corners and the cut-out for the time setting switches should be made at this stage. The cut-outs at the corners of the clock board enable the board to fit snugly into the suggested case. The board will be fitted to the case with the screws supplied.

After the breaks in the copper rails have been made, fit the 22 s.w.g. copper links exactly as shown in the layout, taking care to see that each link is perfectly straight. If the links are kept straight and tidy there is no need to sleeve them and the fitting of the links should present no difficulty.

The holes for fixing the board into the case, and the two holes for fixing the transformer should be drilled with a number 27 drill or a little larger for good clearance.

The author used nylon 4BA screws and nuts for fixing the transformer as there is then no danger of shorting adjacent copper rails. If ordinary nuts and screws are used the copper rails should be insulated with mica washers or similar. Coloured wires are brought out from the board as this method enables the wires to be easily identified when connecting the display board to the clock board. The following colours were used in the prototypes:

Brown — Hours × 10
 Red — Hours × 1
 Orange — Mins × 10
 Yellow — Mins × 1
 Green — Secs × 10
 Blue — Secs × 1

Brown — Cathodes A
 Red — Cathodes B
 Orange — Cathodes C
 Yellow — Cathodes D
 Green — Cathodes E
 Blue — Cathodes F
 Mauve — Cathodes G

COMPONENTS . . .

Resistors

R1-R2 100k Ω (2 off)
 R3 560 Ω
 R4-R10 2.2k Ω (7 off)
 R11-R17 10k Ω (7 off)
 R18-R24 270 Ω (7 off)
 All $\frac{1}{4}$ W, 10% carbon.

Capacitors

C1 0.01 μ F plastic or paper
 C2 2,200 μ F >25V
 C3 0.022 μ F


Semiconductors

*TR1-TR6 BC478
 TR7-TR13 BC108
 IC1 MM5314N
 D1-D4 Rec 63 (Bridge rectifier)
 D5 1N914 (1N4148)
 * L.E.D. Displays 1-4 DL747
 5-6 DL707

Miscellaneous

Case, Vero Electronics (order code 65-25224) (Approx. dimensions 180mm × 55mm × 100mm). S1 switch, S.P.D.T. or S.P.S.T. S2 switch, S.P.D.T. bias to centre OFF. Veroboard 0.1in matrix 11 $\frac{1}{2}$ in × 3 $\frac{3}{4}$ in. T1 transformer, Min. Trans 12V (6VA). (RS Components, Doram).

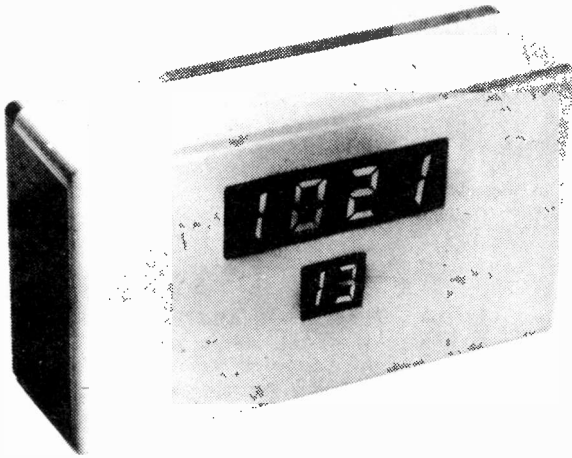* Note. For 4-digit version delete transistors TR5 and TR6 and the two l.e.d. displays type DL707.



It should be obvious that the group of six transistors are for the digit enable outputs, while the group of seven transistors are the seven-segment outputs. Fig. 2 shows the layout of the clock board viewed from the plain (component) side.

Viewed from the component side of the board, a wire is taken from each hole to the right of each collector connection. These wires should be, from left to right, Brown, Red, Orange, Yellow, Green and Blue. They are the digit enable connections, and will connect to the anode on each I.e.d. package.

The emitters of the seven driver transistors for the seven segments, type BC108, are taken to earth. From the lefthand side of resistors R19 to R24, a coloured wire is taken. The order, right to left is: Brown, Red, Orange, Yellow, Green, Blue,

Mauve. These are the cathode connections for the I.e.d.s, Brown being Cathode A, Red being Cathode B, etc. (Fig. 3).

POSSIBLE VERSIONS

Before going further it must be decided which version of the clock is required. The clock board in Fig. 1 is for a six digit, twelve-hour clock operating from 50Hz. If a 24-hour clock is required the link between pins 2 and 10 adjacent to the i.c. should be omitted. Also, if a four-digit clock is desired the link between pin 24 of the i.c. and the negative rail should be omitted. If the clock is to be used on a supply having a frequency of 60Hz, pin 11 of the i.c. should be connected to the negative rail. Thus it is simple to programme the clock to suit one's requirements.

One last tip before we leave the clock board on one side. Do not apply the soldering iron to the pins of the clock i.c. for longer than necessary or damage will result. A socket for the package was not used in the prototype for reasons of economy, but a 24-pin dual in line socket can be used.

I.E.D. DISPLAYS

Before commencing the construction of the display board, it might be as well to make ourselves familiar with the I.e.d. displays. Two types are used for the six digit version of the clock. Four are type DL747 having a character height of 0.6in and pins numbered 1 to 18. The DL747 packages are for the hours and minutes display. The other two displays, for the seconds readout, are type DL707. These have a character height of 0.3in. They are smaller than the other displays for reasons of economy and current saving. Although not as large as the DL747, the DL707 is of equal brightness. It will soon be obvious, when looking at the


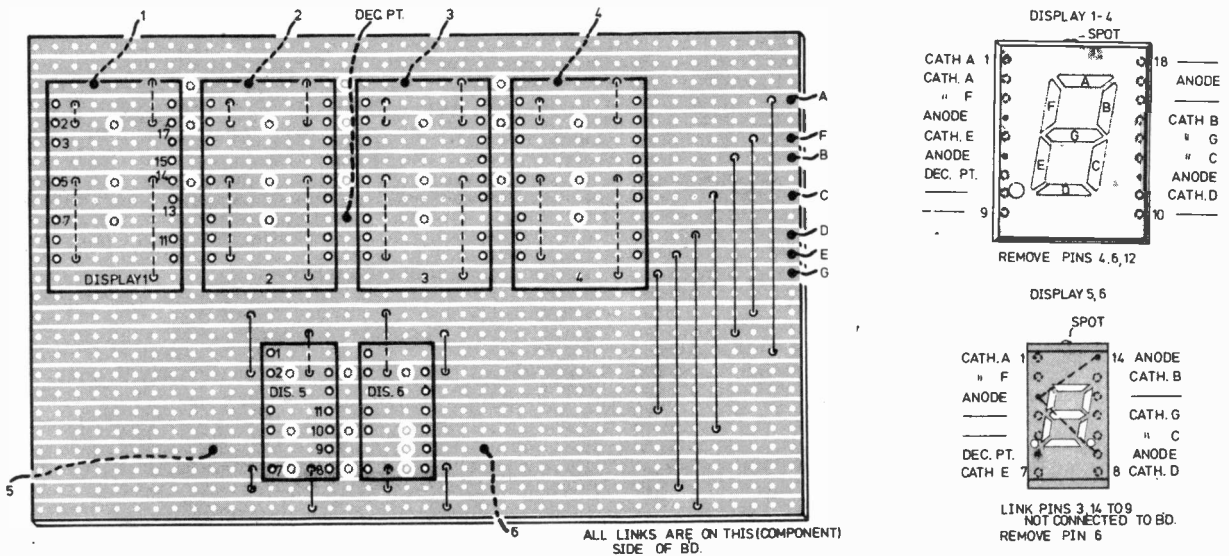


Fig. 3. Display board and I.e.d. display details

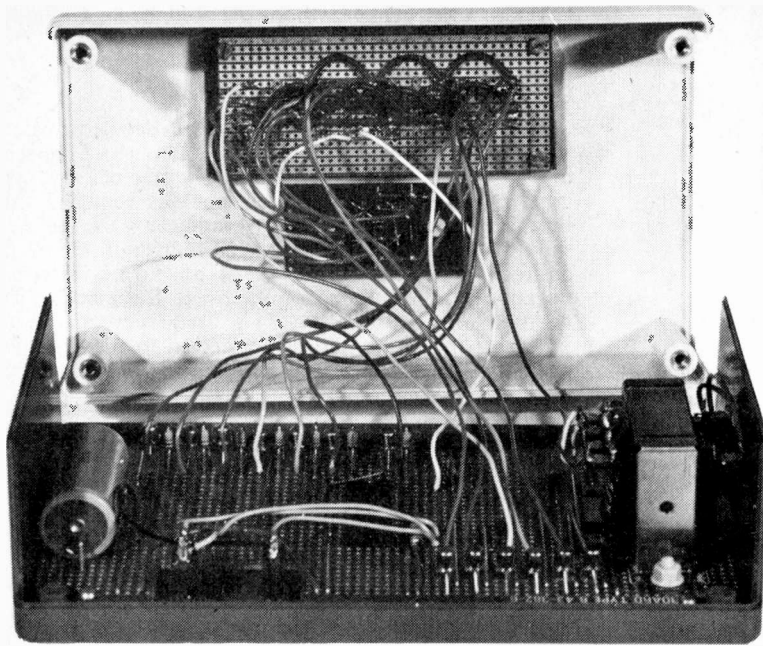

displays it will be necessary to very carefully take a little off the rear edge of the sides of these displays in order for them to fit close together on the board without any gaps between them.

The smaller display packages can be soldered slightly proud of the display board to bring their faces up to the same height as the four larger displays. The stand-off strips should be just high enough to make the display surfaces flush with the front face of the case. They should be drilled and tapped to suit 6BA screws.

It will be obvious from the positioning of the cutout in the clock board where the time setting switches are placed. No details for drilling the holes for the time setting switches are given. The space allowed gives ample scope in the placing of the switches, the toggles of which stand out from the rear of the case.

two display devices, that neither is carrying its full complement of pins. The smaller DL707 has pins 4, 5 and 12 missing, while the larger DL747 has pins 1, 8, 9, 10, 16 and 18 missing.

DISPLAY BOARD ASSEMBLY

The type of construction employed for the display board eliminates the interconnecting of similar pins which would otherwise have to be done. This method of construction saves a lot of wires and generally helps keep the whole of the display board tidy. It also means less confusion, as there are less actual connections to be made. However, it does mean that we have to modify the display packages a little. This must be done with meticulous care so as not to spoil a display i.e.

Taking the smaller DL707 first, pins 14, 3 and 9 must be linked with sleeved light gauge tinned copper wire. 10 amp fuse wire will do the job. It will be seen that the pins referred to are the anode connections which, on this package, are not common and must therefore be joined together. The three pins should be joined with the wire which must be soldered as close to the rear of the package as possible. Now remove, with small side cutters, pins 3, 6 and 14 so that they cannot protrude through the board. There are no pins to be linked on the larger DL747, but carefully remove pins 4, 6 and 12.

The display packages can now be laid aside while the construction of the display board takes place. Veroboard is again used and the layout as viewed from the plain side can be seen in Fig. 3.

Four 6BA holes should then be drilled out as shown to enable the board to be fixed to standoff strips which are glued in position inside the case. Now the display packages can be fitted to the plain side of the board. In the case of the larger DL747

VENTILATION

In a confined space without ventilation the transformer can run uncomfortably warm, but the temperature rise can be kept minimal by the drilling of as many holes as possible below and to the rear of the transformer. The holes should be not less than $\frac{1}{16}$ in diameter.

SETTING THE CLOCK

Time setting is easy and reasonably fast. When the clock is connected to the mains, hold the "Fast/Slow" switch in the fast position. The clock will change its readout one hour every second.

Let us assume the time is actually seven minutes past eight. With the clock running in the FAST position it is best to release the switch soon after it has changed to the seventh hour. Now hold the switch in the slow position and it will alter one minute each second. The time as shown by the clock can now be conveniently brought to the right time (8.07), when the switch should be released. It will now count normally.

If one is fastidious enough to want the seconds to count down correctly, bring the clock to a time just in advance of the actual time—say eight o'clock. As soon as the clock changes over to eight, operate the hold switch. If this is done promptly the clock will now display 8.00 and 00 secs. Now telephone for the correct time, waiting for the time signal for 8.00, then operate or release the hold switch and the clock will run with the correct seconds count being displayed. It all actually takes less time to set up than it takes to read the notes on the procedure.


The clock can be mounted in any case, always ensuring adequate ventilation, but the case used by the author makes the clock presentable and modern in appearance, fitting in well with any decor. ★

New **BIGGER! BETTER!** DORAM

CATALOGUE 2nd Edition

SPECIFICALLY DESIGNED FOR THE AMATEUR
RADIO, ELECTRONICS AND HI-FI ENTHUSIAST.

- * MUCH, MUCH BIGGER RANGE OF QUALITY ELECTRONIC COMPONENTS AND AUDIO ACCESSORIES FROM TRUSTED BIG NAME MANUFACTURERS
- * THOUSANDS UPON THOUSANDS OF COMPONENTS - ILLUSTRATED, INDIVIDUALLY CODED AND PRICED. MANY NEW COMPONENTS ADDED FROM CUSTOMER REQUESTS
- * 16 EXTRA PAGE DATA SECTION
- * **UNIQUE** FREE UP-DATE PRODUCT INFORMATION SERVICE DURING LIFE SPAN OF CATALOGUE
- * ALL COMPONENT REQUIREMENTS SENT BY RETURN POST
- * **POST AND PACKING FREE** (only applies for Great Britain, N. Ireland plus B.F.P.O. Nos. - overseas orders F.O.B.)
- * **NO-QUIBBLE REPLACEMENT PART SERVICE**

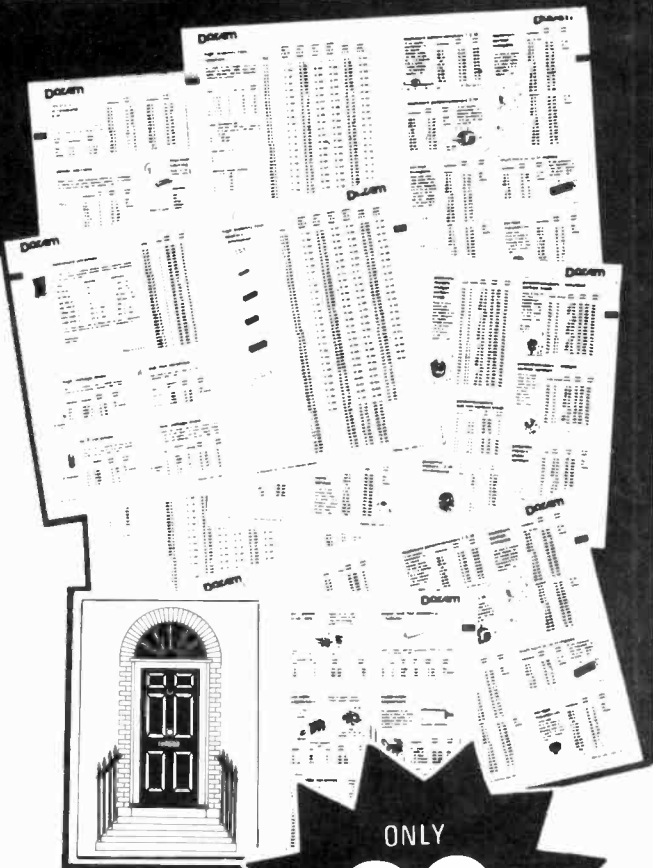

ONLY
60p
Inc. Post and Packing

All this and more - so don't delay

*send for
your new
catalogue
TODAY!*

The doorway to amateur electronics

DORAM

DORAM ELECTRONICS LIMITED
P. O. Box TR8
Leeds LS12 2UF

I enclose 60p. Please send me by return my new Doram Catalogue. (Overseas orders except for N. Ireland, please add 30p for post and packing surface only).

PLEASE PRINT BLOCK CAPITALS PE8

NAME _____

ADDRESS _____

Post Code _____

RST VALVE MAIL ORDER CO.

16a WELDFIELD ROAD, LONDON SW16 2BS
SPECIAL EXPRESS MAIL ORDER SERVICE

Sp	Sp	Sp	Sp	Sp	Sp
1N21	0-17	AFZ11	1-15	BY213	0-25
1N23	0-35	AFZ12	2-00	BY210	0-45
1N85	0-88	ASV26	0-35	BY211	0-40
1N253	0-50	ASV27	0-25	BY212	0-40
1N266	0-60	ASV28	0-25	BY213	0-42
1N645	0-16	ASV29	0-30	BY215	1-25
1N725A	0-20	ASV36	0-25	BY216	0-80
1N914	0-06	ASV50	0-20	BZY88	0-10
1N4007	0-12	ASV51	0-40	C111	0-55
18113	0-25	ASV53	0-20	CR81/05	0-35
18202	0-28	ASV62	0-25	CR81/40	0-50
2G371	0-06	ASV66	0-33	CS10B	1-80
2G381	0-22	ASZ21	1-00	DD000	0-15
2G414	0-30	ASZ23	0-75	DD003	0-15
2G417	0-25	AU104	1-00	DD006	0-25
2N404	0-22	AUY10	1-00	DD007	0-40
2N697	0-18	BC108	0-18	DD008	0-28
2N698	0-80	BC109	0-14	GD3	0-35
2N706	0-12	BC113	0-15	GD5	0-33
2N706A	0-12	BC115	0-20	GD8	0-25
2N708	0-16	BC116	0-20	GD12	0-10
2N709	0-40	BC116A	0-25	GET102	0-50
2N1091	0-55	BC118	0-20	GET103	0-40
2N1131	0-25	BC121	0-20	GET104	0-25
2N1132	0-24	BC122	0-20	GET114	0-30
2N1802	0-18	BC125	0-65	GET115	0-90
2N1803	0-18	BC126	0-65	GET116	0-85
2N1904	0-25	BC128	0-65	GET120	0-50
2N1805	0-22	BC140	0-55	GET127	0-30
2N1806	0-22	BC147	0-10	GET875	0-40
2N1807	0-22	BC148	0-10	GET876	0-40
2N1308	0-28	BC149	0-14	GET881	0-25
2N2147	0-78	BC158	0-12	GET882	0-35
2N2148	0-80	BC160	0-63	GET885	0-40
2N2180	0-78	BC160	0-63	GET885	0-40
2N2218	0-22	BC169	0-14	GEX44	0-08
2N2219	0-25	BC171	0-15	GEX45/1	0-45
2N2220	0-25	BCY32	0-25	GEX46/1	0-45
2N2369A	0-16	BCY33	0-25	GEX47	0-45
2N2444	1-99	BCY34	0-45	GJ4M	0-50
2N2613	0-75	BCY35	0-55	GJ5M	0-25
2N2646	0-50	BCY38	1-60	GJ7M	0-50
2N2904	0-20	BCY39	1-50	HG1005	0-50
2N2904A	0-25	BCY40	0-80	H8100A	0-20
2N2806	0-20	BCY70	0-18	MA1100	0-20
2N2807	0-22	BCY71	0-22	MA1101	0-25
2N2924	0-13	BCZ10	0-60	MAT120	0-20
2N2925	0-18	BCZ11	0-65	MAT121	0-25
2N2926	0-12	BCZ12	1-00	MJ2340	0-47
2N3054	0-45	BD123	1-00	MJE520	0-65
2N3055	0-45	BD124	1-45	MJE2955	1-27
2N3702	0-11	BDY11	1-05	MJE3055	0-70
2N3705	0-15	BF115	0-20	MPP102	0-40
2N3706	0-11	BF167	0-25	MPP103	0-38
2N3707	0-13	BF173	0-28	MPP104	0-35
2N3709	0-10	BF181	0-35	MPP105	0-38
2N3710	0-11	BF184	0-22	NKT128	0-45
2N3711	0-11	BF184	0-22	NKT129	0-80
2N3819	0-85	BF194	0-10	NKT211	0-25
2N4289	0-30	BF195	0-13	NKT213	0-25
2N5027	0-63	BF196	0-15	NKT214	0-24
2N5068	0-38	BF197	0-15	NKT216	0-40
28301	0-89	BF197	0-15	NKT217	0-45
28304	1-15	BF198	0-25	NKT218	0-45
28601	0-75	BFX12	0-25	NKT219	0-25
28703	1-00	BFX13	0-25	NKT222	0-30
AA129	0-20	BFX29	0-28	NKT224	0-25
AAZ12	0-78	BFX30	0-28	NKT251	0-24
AAZ13	0-12	BFX35	0-25	NKT271	0-20
AC107	0-51	BFX35	0-25	NKT272	0-20
AC126	0-25	BFX36	0-25	NKT273	0-20
AC127	0-25	BFX37	0-25	NKT274	0-20
AC128	0-15	BFX38	0-25	NKT275	0-25
AC187	0-21	BFX87	0-25	NKT277	0-20
AC188	0-20	BFX88	0-24	NKT278	0-25
ACY17	0-40	BFY10	0-50	NKT301	0-25
ACY18	0-27	BFY11	0-50	NKT304	0-75
ACY19	0-27	BFY12	0-50	NKT403	0-70
ACY20	0-22	BFY18	0-45	NKT404	0-60
ACY21	0-22	BFY19	0-55	NKT878	0-20
ACY22	0-18	BFY24	0-45	NKT713	0-20
ACY27	0-25	BFY44	1-00	NKT773	0-25
ACY28	0-25	BFY50	0-21	NKT777	0-25
ACY39	0-78	BFY51	0-20	OAS	0-72
ACY40	0-22	BFY52	0-20	OAS	0-18
ACY41	0-22	BFY53	0-17	OAS	0-18
ACY44	0-55	BFY64	0-25	OAS	0-18
AD140	0-50	BFY90	0-81	OA71	0-10
AD149	0-50	BHX27	0-50	OA73	0-15
AD161	0-44	BHX60	0-93	OA74	0-15
AD162	0-44	BHX76	0-18	OA79	0-10
AF106	0-30	BSY26	0-17	OA81	0-18
AF114	0-25	BSY27	0-40	OA85	0-15
AF115	0-25	BSY51	0-50	OA85	0-15
AF116	0-25	BSY95A	0-12	OA90	0-07
AF117	0-24	BSY95B	0-12	OA91	0-07
AF118	0-57	BT102/500R		OA95	0-07
AF119	0-20	BTY42	0-75	OA200	0-06
AF124	0-80	BTY79/100R		OA302	0-06
AF125	0-30	BTY79/400R		OA210	0-20
AF127	0-30	BTY79/400R		OA211	0-25
AF139	0-41	BTY79/400R		OA2200	0-50
AF178	0-55	BY100	0-27	OA2201	0-45
AF179	0-55	BY126	0-14	OA2202	0-45
AF180	0-55	BY127	0-12	OA2203	0-45
AF181	0-50	BY182	0-85	OA2204	0-45
AF186	0-48				

Open daily to callers: Mon.-Fri. 9 a.m.-5 p.m.
Valves, Tubes and Transistors - Closed Sat. 1 p.m.-3 p.m.
Terms C.W.O. only - Tel. 01-677 2424-7
Post and Packing 10p per order.
V.A.T. Transistors 25%. Integrated Circuits 3%.

12in LONG PERSISTENCE CRT. Full spec. Price £6-50 to include V.A.T. and Carriage.

MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED SOLID STATE SWITCH. 2Hz to 8MHz. Hook up to a 9 volt battery and connect to your scope and have two traces for ONLY £8-25. P & P 25p. (Not cased, not calibrated.)

WIDE RANGE WOBBLULATOR. 5MHz to 150MHz up to 15MHz sweep width. Only 3 controls. preset RF level, sweep width and frequency. Ideal for 10 T or TV IF alignment, filters, receivers Can be used with any general purpose scope. Full instructions supplied Connect 6 3V a.c. and use within minutes of receiving. All this for ONLY £6-75. P & P 35p. (Not cased, not calibrated.)

20Hz to 200kHz WB. SINE and SQUARE GENERATOR. Four ranges independent amplitude controls, thermistor stabilised. Ready to use. 9V supply required. £8-85 each. P & P 35p. (Not cased, not calibrated.)

GRATICULES 12cm x 14cm high quality plastic 15p each. P & P 8p.

Large quantity of good quality components—NO PASSING TRADE—so we offer 3lb of ELECTRONIC GOODIES for £1-70. Post paid.

ROTARY SWITCH PACK—6 brand new switches (1 ceramic, 1 off 4 pole, 2 way, etc.). 50p. P. & P 37p.

P.C.B. PACKS. S & D. Quantity 2 sq. ft.—no tiny pieces. 50p. P. & P 37p.

CAPACITOR PACK—50 brand new components. only 50p. P. & P 37p.

TRIMMER PACK. 2 twin 50/200pF ceramic; 2 twin 10/60pF ceramic; 2 min strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW. 25p the lot. P. & P. 15p.

PHOTOCELL equ. OCP71, 13p each. MULLARD OCP70, 10p each.

DELIVERED TO YOUR DOOR. 1cwt of Electronic Scrap chassis, boards, etc. No rubbish. FOR ONLY £4.

MODERN TELEPHONES. Type 706: two-tone grey or black. £3-75 each. Type 7006: two-tone grey or green. £3-75 each. Style similar to Type 746: grey, green or black. £3 each. P. & P. all types 45p each.

Ideal EXTENSION TELEPHONES with standard GPO type dial, bell and lead coding. £1-75 each. P. & P. 45p.

HANDSETS. Complete with 2 inserts and lead. 75p each. P. & P. 37p.

DIALS. ONLY 75p each. P. & P. 25p.

HIGH VALUE—PRINTED BOARD PACK. Hundreds of components, transistors, etc.—No 2 boards the same. No short leaded transistor computer boards. £1-75, post paid.

BEEHIVE TRIMMER 3/30 pF. Brand new. Qty 1-9 13p each. P. & P. 15p. 10-99 10p each. P. & P. 25p; 100-999 7p each. P. & P. free.


HE CRYSTAL DRIVE UNIT. 19in rack mount. Standard 240V input with superb crystal oven by Labgear (no crystals) £5 each. Carr. £2.

1,000pF FEED THRU CAPACITORS. Only sold in packs of 10, 30p. P. & P. 15p.

ALWAYS SOME CHEAP SCOPES AVAILABLE—order or build your own. Send for our tube list with a S.A.E.

PLEASE ADD V.A.T. AT 8%
OPEN 9 a.m. to 6.30 p.m. ANY DAY

CHILTEAD LTD
7/9 ARTHUR ROAD, READING, BERKS.
(near Tech. College) Tel.: Reading 562605/65916

Use Access here 

DIGITAL CLOCK KITS

SENSATIONAL OFFER

£2 OFF

FAST BUILDING, EASY TO FOLLOW INSTRUCTIONS. A VERY COMPLETE KIT

CLOCK DATA
SIZE 6½ x 3 x 2½ in
MAINS
OPERATION
50/60Hz
12/24 HOUR

USUAL PRICE TO P.E. READERS
NEW ALL WOOD CASE 70p EXTRA
NO KNOWLEDGE OF ELECTRONICS REQUIRED
LATEST 1975 DESIGN—ONLY £14
(including P. & P., VAT, Circuit)

COMPARE OUR PRICES IF PURCHASED AS SINGLE ITEMS (INCLUDING VAT AND P. & P.)

1 MOS Clock Chip 12-24 hr option	1-95
4 0-63" LED Displays (latest HI BRI Type)	4-60
1 Segment Driver Chip	0-50
1 Pack Resistors, Caps., Transistors, Switch, etc.	1-60
1 Double Sided Glass Fibre P.C. Board	0-95
1 Circuit/Assembly Manual	0-50
1 Futuristically-styled Case (state colour)—Yellow, Orange, Red, Black, White, Mauve, Green, Blue	4-40

Plug in sockets—low profile
14 pin DIL
16 pin DIL

Pulse Electronics Ltd
Dept. PE2, 202 Shefford Road, Clifton, Beds.
Tel. Hitchin (0462) 814477

Strictly Instrumental

by K. Lenton-Smith

THE swingeing increase in VAT earlier this year provides an incentive to build an electronic musical instrument rather than buy the commercial variety. Most constructors spend a great deal of thought on circuitry—rightly so—and will want to get a quart out of a pint pot more than ever before. It could be that exact imitation of the acoustic counterpart is the ideal, if so, there are problems to contend with.

JOANNA

Alan Boothman's second-generation piano is an excellent little instrument and was particularly well received when demonstrated to meetings of The Electronic Organ Constructors' Society at the time the articles in this magazine commenced; a number of readers will have been at these meetings and heard for themselves. Members of the E.O.C.S. are a critical bunch (in the strictly musical sense!), so "Joanna's" reception was praise indeed. Whatever one's musical tastes, this instrument can cope both expressively and accurately.

When the physical characteristics of an acoustic piano are considered, the electric piano's realism is moderately surprising. The grand piano's "loud pedal" lifts all the dampers so that on playing any note, harmonics of those strings also sound by sympathetic resonance. Hammers strike the strings at approximately the same distance from the bridge irrespective of the length of the string, so the harmonic content varies across the spectrum of the keyboard. In the electronic counterpart, filtering can take care of the last point to some extent but sympathetic resonance is almost impossible to reproduce by electronic means.

CHORUS

The majority of keys in the acoustic piano's compass employs three strings and, though each

of the strings may be in perfect tune with each other and with the equally-tempered scale, they will not necessarily vibrate in phase; the chorus effect so produced adds to the richness of sound. Yet nearly all electric pianos, including "Joanna", are divider instruments which lack chorus effect due to the single octave tone source and strict phase relationship between octaves.

The electric piano is accepted as realistic because careful design results in attack/decay characteristics which closely match those of the hammer and string. With organs, the listener automatically expects to hear a "mighty Wurlitzer" emerge from what is only too often a fairly small speaker because he identifies organs with Blackpool, a church or concert hall!

ECONOMY

This "grand sound" is asking a great deal from the divider generators of the average home organ. As with electric pianos, dividers score on grounds of both cost and weight. Manufacturers mainly use i.c. dividers (such as SAJ110) because of their reliability and simplicity where wiring is concerned.

Separately tuned master-oscillators (Hartley, Colpitts or multi-vibrators) normally precede each divider string, but the relatively high tuning accuracy of the single-master-oscillator i.c. has made for further economies in recent years.

IMPROVEMENTS

By careful mixing and filtering, the noticeably hollow tone of square waves can be overcome. Staircasing may be achieved by adding small amounts of super-octaves to the fundamental tones.

A reverberation unit will produce signals in jumbled phase and gives some semblance of chorus when mixed with the main signal, using separate speaker systems. A

chorale (slowly rotating) speaker produces phase differences with the main unit, though some listeners find the effect somewhat monotonous. Even so, these devices improve a simple divider organ considerably.

Some years ago, the Baldwin Piano Co. used a completely different approach to this problem in their Chorotone Projector. In this case, the main audio signal was amplified and passed through a phase splitting network to produce three signals with 120 degree differences. Each of these were fed to four three-stage phase-shift oscillators operating at 1, 2, 4 and 8Hz with bandpass filters in their outputs.

Incoming signals at about 400Hz were frequency-modulated at 1Hz, 800Hz modulated at 2Hz and so on, up to 8Hz modulation for the highest frequencies. Each of the four broad frequency bands, slowly modulated at appropriate rates, were mixed with the main signal to produce a "cathedral effect" from lowly divider generators!

THE ULTIMATE

No amount of electronic trickery can disguise the fact that a single set of dividers is inadequate—to the critical ear. A good example of a multiple-generator instrument is the "Magic Organ", featured by Harry Stoneham on EMI's stereo LP OU 2068.

Designed by Jaap Keizerwaard, a Dutchman, this organ has no less than 24 sets of generators. Four of these are allotted to the first manual, eleven to the second manual (six for individual voices and five for its excellent string tones), five to the third manual and four to the pedals.

The designer apparently is willing to build another "Magic Organ" for a mere £35,000 (not forgetting the Chancellor's share), delivery time being five years!

PLAY ON

Finally, Mr P. D. Scargill (his letter in the June issue) may be assured that this column does not "scoff at the younger generation". There are plenty of examples of skilfully performed pop music but, like all Art forms, a consistently high standard cannot exist. Electronic gimmickry substituted for sheer musical ability is not uncommon, and it is this aspect that gives the impression I mentioned to musicians of any age group.

SEMICONDUCTOR UPDATE . . .

By R. W. COLES

TRI-STATE LAMP

The **MV5491** is a new device from Monsanto which looks as though it may prove to be a big success. Like all good ideas, this new device is essentially very simple, consisting as it does of a standard "match-head" light emitting diode package, containing not *one* i.e.d. but *two*, one red and the other green, sharing a common lense. These two i.e.d. chips are not intended to be "ON" at the same time, and this is ensured by the connection of the two diodes in "inverse parallel" inside the package, making the MV5491 a two-terminal assembly.

The operation of this novel device is elegantly simple—bias it one way and it glows RED, bias it the other way and it glows GREEN; if you don't bias it at all, of course, no light is emitted, making the MV5491 a three-state indicator. This TRI-STATE capability adds a whole new dimension to applications such as tuning indicators, logic probes, voltage polarity sensors and a host of others.

Incorporation into practical circuits is easy. To build a simple polarity indicator, all that would be required in addition to the MV5491 is a single current limiting resistor connected in series in standard i.e.d. fashion. This simple arrangement does not allow for the difference in brightness between the GaAsP (RED) i.e.d., and the GaP (GREEN) i.e.d., but to add compensation for this difference requires only one extra resistor and a silicon diode.

HOME GROWN

"Support your local i.c. manufacturer" could well be the sales maxim of Ferranti Ltd. since their CDI (Collector Diffusion Isolation) process is about the only original British developed process around, and it certainly *is* refreshingly different. Remember the ZN414, the radio in a TO18 can used in the P.E. Triffid receiver? Well, that was one of the early examples of what this home-grown technology could produce.

CDI has come of age since then, with a wide range of interesting circuits, both linear and digital, many of them "custom" specials for equipment manufacturers.

Naturally, some examples of "general purpose" CDI goodies, such as the ZN414, continue to find their way through to wider sales horizons, and one such interesting new device just announced by

Ferranti, is the **ZN1040E**, universal count and display circuit.

Primarily a digital design, the ZN1040E is an all-singing, all-dancing, counter circuit which will not only count up or down over four decades at 5MHz, but will also store a previous zero and feed it out for display in a ready decoded seven-segment format as well as b.c.d. Display electronics include automatic leading zero blanking, a display multiplexer and an on-chip display clock.

This versatile device will drive many kinds of display directly, including seven-segment i.e.d.s, resulting in a very low component count in typical applications such as frequency counters, timers, and dual-slope voltmeters. The ZN1040E comes in a 28-pin plastic package, runs from a single five-volt supply, and costs about £7.50 100 up.

NEGATIVE THINKING

Anyone who has sampled the delights of using the new "fixed-voltage" regulator i.c.s such as the Motorola 7800C series, will welcome a new range of devices from the same company. The 7800C series (and equivalents from other manufacturers) are a blessing wherever a fixed positive regulated supply is required, and are available in a range of voltages including all the favourites such as 5, 6, 12, and 15. Their great advantage over more traditional variable voltage types, is that very few discrete components are required to ensure correct operation, making circuitry quite simple.

Until now, however, producing a negative regulator circuit was rather unsatisfactory since it meant using one of the positive regulator i.c.s in the earthy side of the negative voltage supply. The new **7900C series** from Motorola overcomes this problem because it introduces a range of "dedicated" negative regulators which complement the 7800C series.

The 7900C devices are available in the same voltage increments as their positive counterparts, making it a simple matter to construct a complementary supply, such as the plus and minus 15 volts often required by operational amplifiers like the 741.

POWER TO THE PEOPLE

In general, monolithic audio amplifiers are not popular with hi-fi, or even mid-fi designers who prefer to have the greater control over circuit operation afforded by a discrete design. An interesting carrot is now

being dangled to tempt these reluctant designers into the monolithic fold, in the shape of the **TDA1410** and **TDA1420** devices from SGS/ATES

These two i.c.s are set fair to succeed where others have failed, because they integrate only the parts of a power amplifier which stand to benefit most from the close thermal tracking and parameter matching obtainable with a monolithic approach, i.e. the final output stage. This novel new answer to audio designers' criticisms of previous monolithic amplifiers leaves the designer to concentrate on the low level stages which may be better implemented with discrettes.

These devices are a compromise between "Power-Darlington" and a fully integrated amplifier.


FASTER STILL, AND FASTER

Finally, the **CA3100**, an interesting new RCA operational amplifier is now becoming available in Britain at a realistic price. This device takes OP-AMP technology a step further by using a combination of bi-polar and *p-mos* devices on the same chip to give a bandwidth extending to 38MHz and a 70V/microsecond slew rate, alongside the now expected low drift d.c. performance.

If you are tempted to say, "so what?" contrast that 70V/microsecond slew rate with the typical figure of 0.5V/microsecond for the ubiquitous 741, and you will see what kind of advance the CA3100 represents.

This fast amplifier comes in a TO5 can, with optional lead forming to make it pin compatible with the eight-pin plastic "Mini-DIP". As an added bonus, pin assignments are identical with its famous predecessors such as the 748 and the 741, making it possible to use it as a plug-in replacement to increase the bandwidth and risetime of existing amplifiers. Compensation (when needed) is by means of a single capacitor, and voltage offsets can be nulled in standard 741 fashion with a 10kΩ pot.

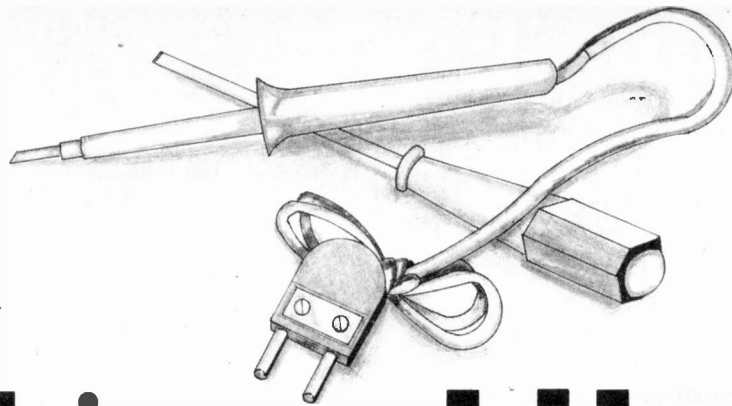The CA3100 brings speed and bandwidth to the people, because, while it was possible to obtain devices with these desirable characteristics before the CA3100 showed up, it was an expensive business and a substantial premium had to be paid. The price of the CA3100?, about £3, 1 off.



This could lead to something big.

A soldering iron and a screw driver. If you know how to use them, or at least know one end from the other, you know enough to enrol in our unique home electronics course.

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You build, see and learn as, step by step, we take you through all the fundamentals of electronics and show you


how easily the subject can be mastered and add a new dimension not only to your hobby but also to your earning capacity.

This course is accepted by and used in a large number of schools and colleges and forms an invaluable grounding for professional training in the subject. All the training is planned to be carried out in the comfort of your own home and work in your own time. You send them in when you are ready and not before. These culminate in a final test and a certificate of success.

1

Build an oscilloscope.


As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a professional test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.

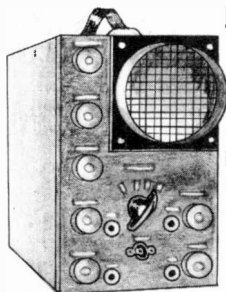

2

Read, draw and understand circuit diagrams.

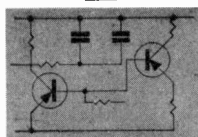
In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.




3

Carry out over 40 experiments on basic circuits.

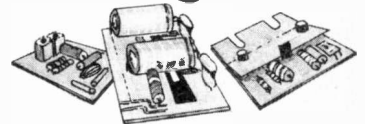We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.



PLUS

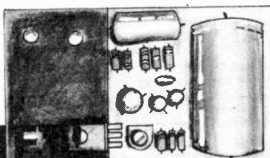

FREE GIFT

ALL STUDENTS ENROLLING IN OUR COURSES RECEIVE A FREE CIRCUIT BOARD ORIGINATING FROM A COMPUTER AND CONTAINING MANY DIFFERENT COMPONENTS THAT CAN BE USED IN EXPERIMENTS AND PROVIDE AN EXCELLENT EXAMPLE OF CURRENT ELECTRONIC PRACTICE

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

WAA

Brochure without obligation to:
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept EL85
P.O. Box 156, Jersey, Channel Islands.

NAME

ADDRESS

(Block caps please)



GIRO NO. 331 7056. Access accepted.
C.W.O. only. P. & P. 15p on orders below £5
Discount: £10-10% (except net items)
Export Order enquiries welcome (VAT free)

Official Orders accepted from
Educational & Government Departments
ALL PRICES INCLUDE VAT AT 8%

DUE TO RECENT V.A.T. CHANGES PLEASE ADD 15% TO TOTAL ORDER VALUE EXCEPT TEST METERS.

SPECIAL RESISTOR KITS (Prices include post & packing)

10E12 1/2W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.85 net
25E12 1/2W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £9.00 net
Due to current world shortages, resistor kits may contain some wattage and value substitutions.

MULLARD POLYESTER CAPACITORS C280 SERIES
250V P.C. Mountings: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 33p, 0.068µF, 0.1µF, 41p, 0.15µF, 5p, 0.22µF, 6p, 0.33µF, 8p, 0.47µF, 10p, 0.68µF, 13p, 1µF, 16p, 1.5µF, 24p, 2.2µF, 27p.

MULLARD POLYESTER CAPACITORS C296 SERIES
400V, 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 0.0047µF, 3p, 0.0068µF, 0.01µF, 0.015µF, 0.022µF, 0.033µF, 31p, 0.047µF, 0.068µF, 0.1µF, 41p, 0.15µF, 7p, 0.22µF, 9p, 0.33µF, 13p, 0.47µF, 15p.

MINIATURE CERAMIC PLATE CAPACITORS
50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 150, 220, 220, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8, (µF) 0.01, 0.015, 0.022, 0.033, 0.047, 21p. each. 0.1, 30V, 5p.

POLYSTYRENE CAPACITORS 160V 5% (pF) 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 6800, 10,000, 41p.

RESISTORS

CF—High Stab Carbon Film, 5% MF—High Stab Metal Film, 5%.

W. Type Range	1-99	100-499	500-999	1000+	Size mm
CF 12-1M	1	0.80	0.65	0.60	2.4x7.5
CF 22-2M2	1	0.80	0.65	0.60	3.9x10.5
CF 22-1M	1	0.80	0.65	0.60	5.5x16
MF 10-2M2	2	1.7	1.4	1.2	3x7
MF 10-2M2	2	1.6	1.3	1.1	4.2x10.8
1 MF 10-10M	3	1.98	1.81	1.65	6.6x13
2 MF 10-10M	4.5	3.52	3.08	2.75	8x17.5

For value mixing prices, please refer to our catalogue. (Price in pence each).
VALUES AVAILABLE—E12 Series only. (Net prices above 100.)

PRESET SKELETON POTENTIOMETERS

MINIATURE 0.25W Vertical or horizontal 7p each 1K, 2K, 4K7, 10K, etc. up to 1M Ω
SUB-MIN 0.05W Vertical, 100 Ω to 220K Ω 7p each.



B. H. COMPONENT FACTORS LTD.

(P.E.) LEIGHTON ELECTRONICS CENTRE,
59 NORTH STREET, LEIGHTON BUZZARD,
LU7 7EG. Tel.: Leighton Buzzard 2316 (Std. Code 05253). CATALOGUE No. 4, 20p.

Miniature Mullard Electrolytics

1.0µF 63V	7p	68µF 16V	7p
1.5µF 63V	7p	68µF 63V	14p
2.2µF 63V	7p	100µF 10V	7p
3.3µF 63V	7p	100µF 25V	7p
4.0µF 63V	7p	100µF 63V	17p
4.7µF 63V	7p	150µF 16V	7p
6.8µF 63V	7p	150µF 63V	17p
8.0µF 63V	7p	220µF 6.4V	7p
10µF 16V	7p	220µF 10V	7p
10µF 25V	7p	220µF 16V	8p
10µF 63V	7p	220µF 63V	21p
15µF 63V	7p	330µF 16V	8p
15µF 63V	7p	330µF 63V	25p
16µF 63V	7p	470µF 6.4V	14p
22µF 25V	7p	470µF 40V	26p
22µF 63V	7p	680µF 16V	8p
32µF 10V	7p	680µF 40V	25p
33µF 16V	7p	1000µF 16V	17p
33µF 40V	7p	1000µF 25V	28p
32µF 63V	7p	1500µF 6.4V	25p
47µF 10V	7p	1500µF 16V	28p
47µF 25V	7p	2200µF 10V	17p
47µF 63V	8p	3300µF 6.4V	28p

VEROBOARD

0.1	0.15
2 1/2 x 5"	36p 36p
2 1/2 x 3 1/2"	33p 25p
3 1/2 x 5"	42p 46p
3 1/2 x 3 1/2"	36p 36p
10p	9p
2 1/2 x 5" (Plain)	— 19p
2 1/2 x 3 1/2" (Plain)	— 16p
5 x 3 1/2" (Plain)	— 29p
Insertion tool	73p 73p
Track Cutter	56p 56p
Pins, Pkt. 25	22p 22p

TRANSISTORS

AC127	21p	BC212L	13p
AC128	22p	BC213L	13p
BC107	12p	BC214L	18p
BC108	12p	OC44	19p
BC109	13p	OC71	13p
BC148	13p	OC81	17p
BC149	13p	OC170	29p
BC182L	13p	T1543	34p
BC183L	13p	2N2926	13p
BC184L	14p	2N3702	14p

POTENTIOMETERS

Carbon Track 5K Ω to 2M Ω, log or lin (and 1K lin). Single, 17 1/2p Dual Gang 48p. Log single with switch 28p. Slider Pots. 10K, 100K, 500K, semi log 30mm, 34p, 45mm, 47p, 60mm, 55p.

DIODES

IN4001	61p	Din 2 Pin	12p
IN4002	71p	3 Pin	13p
IN4003	9p	5 Pin 180°	16p
IN4400	9p	Srd. Jack	20p
IN4005	12p	2.5mm jack	13p
IN4006	14p	Phono	7p
IN914	7p		
IN916	7p	Din 2 Pin	10p
BA100	10p	3 Pin	10p
OAS	42p	5 Pin 180°	12p
OA47	9p	Srd. Jack	18p
OA81	11p	2.5mm jack	13p
OA200	8p	Phono	7p

PLUGS

IN4001	61p	Din 2 Pin	12p
IN4002	71p	3 Pin	13p
IN4003	9p	5 Pin 180°	16p
IN4400	9p	Srd. Jack	20p
IN4005	12p	2.5mm jack	13p
IN4006	14p	Phono	7p
IN914	7p		
IN916	7p	Din 2 Pin	10p
BA100	10p	3 Pin	10p
OAS	42p	5 Pin 180°	12p
OA47	9p	Srd. Jack	18p
OA81	11p	2.5mm jack	13p
OA200	8p	Phono	7p

ELECTROLYTIC CAPACITORS, Tubular & Large Cans

(µF/V): 1/25, 2/25, 4/25, 4/7.10, 5/25, 8/25, 10/10, 10/50, 16/25, 22/63, 25/25, 25/50, 32/25, 50/25, 100/10, 100/25, 7p, 50/50, 8p, 100/50, 200/25, 10p, 250/50, 18p, 500/10, 8p, 500/25, 17p, 500/50, 25p, 1000/10, 17p, 1000/25, 25p, 1000/50, 40p, 2000/10, 20p, 1000/100, £1-10, 2000/25, 35p, 2000/100, £1-20, 2500/25, 38p, 2500/50, 68p, 5000/25, 68p, 5000/50, £1-20.

HI-VOLT: 4/350, 20p, 8/350, 23p, 100/100, 27p, 16/350, 35p, 16/450, 38p, 32/350, 50p, 50/250, 40p, 100/250, 40p.

METALLISED PAPER CAPACITORS

250V: 0.05µF, 0.1µF, 6p, 0.25, 6p, 0.5µF, 71p, 1µF, 9p, 500V: 0.025, 0.05, 6p, 0.1, 6p, 0.25, 71p, 0.5, 9p, 1000V: 0.01, 11p, 0.022, 13p, 0.047, 0.1, 19p, 0.22, 28p, 0.47, 36p.

PLEASE NOTE OUR NEW ADDRESS.

Our New Electronics Centre is now open in Leighton Buzzard and all callers are welcome. As well as our normal stock of over 2,000 products we have a large range of surplus bargains and calculators, etc. Open 6 days. 9-12.30. 1.30-5 p.m.



MULTIMETER U4323

22 Ranges plus AF/IF Oscillator 20,000 Ω/Volt.
Vdc—0.5—1000V in 7 ranges
Vac—2.5—1000V in 6 ranges
Idc—0.05—500mA in 5 ranges
Resistance—5 Ω—1M Ω in 4 ranges.
Accuracy—5% of F.S.D.
OSCILLATOR—1 KHz and 46.5KHz (A, M, X) at approx. 1 Volt.
Size—160 x 97 x 40mm.
Supplied complete with carrying case, test leads and battery.
PRICE £8.64 net P. & P. 50p.



U4323

MULTIMETER U4341

27 Ranges plus Transistor Tester, 16,700 Ω/Volt. Overload protected.
Vdc—0.3—900V in 8 ranges.
Vac—1.5—750V in 6 ranges.
Idc—0.06—600mA in 5 ranges.
Iac—0.3—300mA in 4 ranges.
Resistance—2K Ω—2M Ω in 4 ranges.
Accuracy—dc—2 1/2% of F.S.D.
ac—2% in 2 ranges.
Size—115 x 215 x 90mm.
Complete with steel carrying case, test leads, and battery.
PRICE £11.88 net P. & P. 50p.



U4341

MULTIMETER U4324

34 Ranges. High sensitivity. 20,000 Ω/Volt. Overload protected.
Vdc—0.6—1200V in 9 ranges.
Vac—3—900V in 8 ranges.
Idc—0.06—3A in 6 ranges.
Iac—0.3—3A in 5 ranges.
Resistance—25 Ω—5M Ω in 5 ranges.
Accuracy—dc and R—2 1/2% of F.S.D.
ac and db—4% of F.S.D.
Size—167 x 98 x 63mm.
Supplied complete with storage case, test leads, spare diode, and battery.
PRICE £10.64 net P. & P. 50p.



U4324

MULTIMETER U4313

33 ranges. Knife edge with mirror scale. 20,000 Ω/Volt. High accuracy. mVdc—75mV.
Vdc—1.5—600V in 9 ranges.
Vac—1.5—600V in 9 ranges.
Idc—60—120 microamps in 2 ranges.
Iac—0.6—1500mA in 6 ranges.
Resistance—1K Ω—1M Ω in 4 ranges.
db scale—10 to +12db.
Accuracy—dc—1 1/2%, ac—2%
Size—115 x 215 x 90mm.
Complete with steel carrying case, test leads, and battery.
PRICE £14.90 net P. & P. 50p.



U4313

66 Pages
3,000 Items
600 Pictures
YOUR COMPLETE ELECTRONIC STORES, MAIL ORDER AND SHOP
20p

PAYS FOR ITSELF WITH DISCOUNT VOUCHERS WORTH 20p

- * DISCOUNTS
- * ALL NEW STOCK
- * SATISFACTION GUARANTEE
- * DEPENDABLE SERVICE

HAVE YOU GOT YOUR

CATALOGUE No. 4 NEW CONVENIENT SIZE, AND FULLY ILLUSTRATED

CONTAINS MANY HARD TO GET ITEMS

SCOTT ELECTRONICS

ESTCOURT HOUSE, ESTCOURT ROAD
GREAT YARMOUTH, NORFOLK
Tel. Great Yarmouth 57383

- 5W Chassis Stereo Amplifier (2-5W/CH). Power requirements: 12V d.c. Output: 2-5W/CH into 8 ohms. Two inputs: tape head (3mV) and 100mV mic./P.U. with suitable external components. Controls: volume, balance and tone (slider controls): £4 plus 25% VAT
- 12V d.c. Solenoids (short duration), 2in x 1in x 1in approx.: 55p inc. VAT
- 12V Miniature Lamps fitted with flying leads. Pack of 10: 60p inc. VAT
- 8 Track Car Stereo Players, 12V negative earth. £14 plus 25% VAT
- Decade Resistance Box 0-111kΩ in 0.1 ohm steps. £38 plus 8% VAT
- High Power Strobes. 1 to 20 flash/sec. Ideal for disco/group use. £42 plus 8% VAT

All prices include postage and packing.
All goods supplied are new and guaranteed
C.O.D. available on all goods below £30

FABULOUS—FANTASTIC

P.E. ORION

FULL KIT OF PARTS, £38.
Transformer and Screen Printed Board, £11.
Complete Semiconductor Kit, £9.50.
H.M. Book and Case, £4.
As above but drilled, punched with Silk Screened Front Panel, £5.80.

ASTRO IGNITION SYSTEM

Complete Kit of Parts for this well proven Transistorised Ignition System, £9.50 Ready-built with only 2 connections to alter. £12.50
Thousands of these units are in use today and have been proven to give the following advantages: fuel economy, faster acceleration, excellent cold start, smoother running, no contact-breaker burning and many more.
Money back guarantee if you are not satisfied. Please state whether positive or negative earth.
Postage included in above prices but add V.A.T. at 8%.

ASTRO ELECTRONICS
Spring Bank Road, West Park, Chesterfield, Derbyshire

TRANSDUCERS

PART 5 or Piezoelectric Devices

By P.R. ALLCOCK*

PIEZOELECTRICITY is the name given to the phenomenon whereby electric charge dipoles are generated in certain crystals when they are subjected to mechanical stress. The effect was discovered in 1880 by Jacques and Pierre Curie and is reversible in that these materials suffer dimensional changes when under the influence of an electric field.

Natural crystals such as quartz, tourmaline and Rochell salt are traditional piezoelectric materials and have been used as transducers, for converting electrical energy into mechanical energy and vice versa, for many years. More recently ceramic piezoelectric materials have been produced and these have the advantage that they can be given almost any shape or size with direction of electric polarization freely chosen during manufacture. Physically, ceramic piezoelectric materials are hard and brittle with general mechanical properties resembling those of insulator-type ceramics and they are manufactured by much the same process.

By changing the chemical composition of the materials it is possible to emphasise one or more specific properties so that the requirements of a particular application can be met. Several grades of piezo ceramic are now available and some of the possible applications are listed in Table 5.1. Some grades are produced under the code name PXE and the charge dipoles in these materials are produced during manufacture by the application of a high electric field during a high temperature phase of the process.

The dipoles are aligned by this technique in one specific direction known as the poling direction. If the material is subjected to an external electrical field which acts in the same direction as the poling direction, the material will expand, or contract, depending on the sense of applied field. If an alternating field is applied the ceramic will vibrate and the amplitude of vibration will be greatest at the resonant frequency.

To ensure adequate coupling between the material and its environment (air, gas or liquid) a compliant structure is needed. A plate or diaphragm is one such structure that operates by "flexing" and can be realised as a bimorph plate or composite transducer.

THE BIMORPH

The bimorph plate principle is illustrated in Fig. 5.1. The bimorph is made up as a sandwich of two thin plates of PXE piezoelectric ceramic, cemented back-to-back so that their respective poling directions are in opposition. Electrical connections are made to the top and bottom silvered faces and the application

Table 5.1: Some Applications of Piezo-electric Materials

1. High voltage (impulse) generation	Gas ignition, cigarette lighters.
2. High power ultrasonics	Sonar, ultrasonic cleaning, soldering and drilling, fish location.
3. Sound and ultrasound in air	Microphones, intruder alarms, tweeters, earphones.
4. Sensors and Pick-ups	Accelerometers, record players, vibration pick-ups.
5. Filters	Remote control, I.F. circuits in radio and TV.
6. Delay lines	Computers and colour TV, acoustic wave devices.
7. Keyboards	Telephones, calculators.

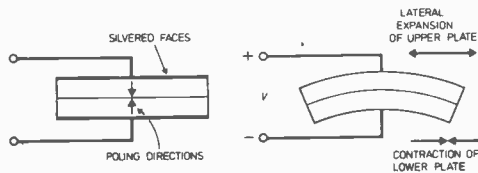


Fig. 5.1. The PXE bimorph plate principle

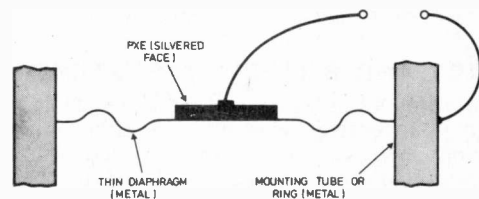


Fig. 5.2 Composite PXE metal transducer. Connection to the lower face is via frame, diaphragm and bonding

of a voltage between these faces causes the bimorph to flex. The bending action arises due to the contraction of the upper plate (along the poling axis) producing a lateral expansion of this plate whereas the opposite effect, a lateral contraction, appear in the lower plate. Because the plates are cemented together this differential expansion causes the bimorph to flex as shown.

To minimise damping of the plate, careful mounting of the bimorph is necessary and techniques sometimes used include knife edges and taut suspension wires. To maximise the acoustic output from a plate it may be necessary to screen part of the bimorph so that portions of the plate moving in antiphase cannot cause cancellation of sound.

Flexure transducers may also be produced by bonding a single disc of piezoelectric ceramic material to a metal plate or diaphragm as shown in Fig. 5.2. Flexing of the plate is similar to that of the bimorph except that the differential expansion is now the relative lateral expansion between the ceramic and the metal sheet. The bond to the metal plate must allow an electrical connection to the lower face of the PXE materials and this can be achieved due to the surface "roughness", providing the adhesive layer is thin and bonding is done under pressure. Alternatively a conducting adhesive can be used.

The frequency at which a composite transducer will resonate can be controlled by changing the dimensions of the metal plate or diaphragm. The resonant frequency is inverseley proportional to the square of the plate diameter and proportional to the plate thickness.

EQUIVALENT CIRCUIT

The electrical equivalent of a piezoelectric air transducer is shown in Fig. 5.3 and will be seen to be the familiar series-parallel arrangement that is commonly used to model the behaviour of a quartz crystal. The impedance of the transducer will be relatively low when the series arm resonates, but at a slightly higher frequency a maximum impedance condition arises due to the parallel resonance between the short capacitance and the effective inductance of the series arm above its own resonant point.

A typical impedance variation is shown in the curve in Fig. 5.3. Transducers of this type can be operated at any frequency in the region of resonance and since manufacturing tolerances, temperature and circuit loading cause variation of operating frequency, the associated circuits must be designed to accommodate variations of, say, 5 per cent. For this reason, a narrow band amplifier may be desirable and circuits that allow the transducer to "dictate" the operating frequency are sometimes used.

DIRECT AND REFLECTING SYSTEMS

Ultrasonic transducers can be arranged as transmitter and receiver elements, in either direct or reflecting systems. In the direct system the transmitter and receiver are separated and the beam of ultrasound is interrupted in some way by, say, objects (to be counted) on a conveyor belt. This system is illustrated in Fig. 5.4 and gives reliable operation since most objects strongly attenuate the ultrasound when they block the beam.

In the reflected sound system the transmitter and receiver can be positioned side by side but difficulties sometimes arise due to reflections from other

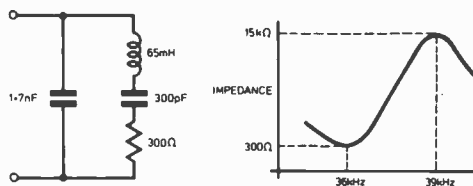


Fig. 5.3. Typical impedance variation and equivalent circuit. The values are typical for Mullard MB4015 transducer

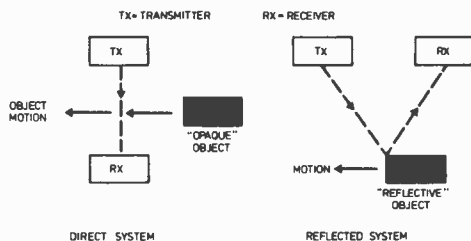


Fig. 5.4. Ultrasonic detection using the direct and reflecting systems

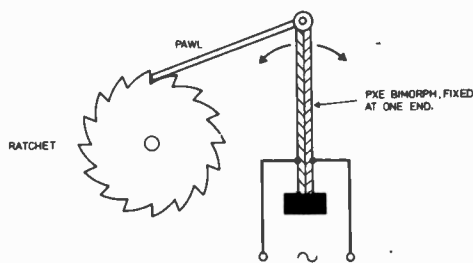


Fig. 5.5. An electric clock motor using the PXE bimorph principle

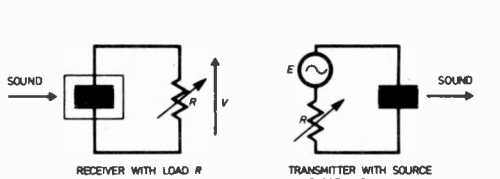
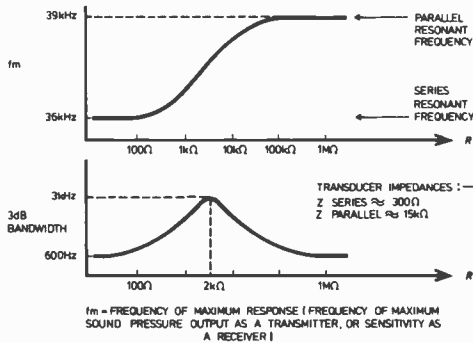


Fig. 5.6. Variation of characteristics with loading resistance

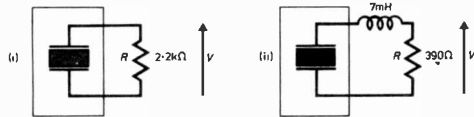
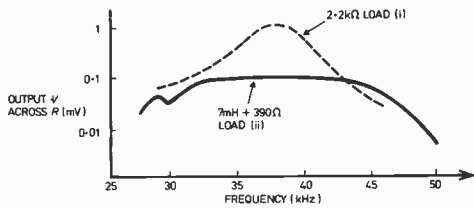


Fig. 5.7. Response with inductive loading added

than the wanted objects. Further, some objects do not give a strong sound reflection and acoustic screening is sometimes necessary between transmitter and receiver to improve the reflected signal/background "noise" ratio.

PIEZOELECTRIC MOTOR

An interesting example of one application of a PXE bimorph is as an electric clock motor. In this system the bimorph is made to flex and the movement is converted to rotary motion by a ratchet and pawl arrangement as shown in Fig 5.5. In a practical realisation using this principle a virtually silent clock mechanism was constructed using a 500-tooth ratchet wheel and fine wire loop as a pawl. The power consumption was about 1mW.

LOADING RESISTANCE

It has already been mentioned that the characteristics of an air transducer are very dependent on the electrical loading. When used as a receiver transducer the input resistance of the amplifier loads the element, whereas for transmitter applications the output resistance of the generator circuit represents the loading resistance. The frequency of maximum response and the 3dB bandwidth both vary with the loading resistance and typical variations are shown in Fig. 5.6.

When the loading is less than the impedance at the series resonant frequency, or greater than the impedance at the parallel resonant frequency, the bandwidth tends to a maximum value of about 600Hz. At an intermediate loading value the bandwidth reaches a maximum of about 3kHz. Notice that the maximum response frequency rises from the value of the series resonant frequency to the value of the parallel resonant frequency as the load resistance is raised.

Over the range of values for R from 100Ω to $50k\Omega$ the efficiency of the typical air transducer remains fairly constant. When used as a receiver (microphone) the frequency response can be made uniform over a band of 10 to 15kHz by employing inductance in series or parallel with load resistance R . This effect is illustrated in Fig. 5.7.

ATTENUATION

Since air attenuates the ultrasound emitted by a piezoelectric transducer and this loss increases as the frequency is raised, most simple low cost air transducers operate well below 100kHz. Specialised devices, operating at frequencies of several megahertz, are however used in applications involving liquids such as water and oil as the medium.

Applications are many and varied, ranging from high power Sonar and echo sounding to specialised devices for blood flow measurements and other medical investigations. The interested reader is referred to the literature for further information on these areas.

ELECTRET MICROPHONE

Capacitance variation has already been mentioned in this series as a well-known example of this principle is the capacitor (or electrostatic) microphone. One disadvantage of these microphones is the need for a polarising source to energise the capacitor circuit so that current fluctuations will occur when the capacitance is varied. Since the wanted output signal from such a microphone is small the hum and noise introduced by the power supply must be kept very low if reasonable signal-noise ratios are to be achieved.

A fairly recent development in this area is the so-called electret microphone due to Sesslen and West of the Bell Telephone Laboratories, in which the need for a power supply is removed. The diaphragm is made from a foil electret which is simply a special dielectric film which has been permanently polarised during manufacture. The film thus provides its own voltage source and can be used to make very small microphone capsules which are to be found in some makes of cassette recorders as well as being used as the basis for wide frequency response individual units.

As with the normal capacitor microphone, the output is very small and a high-impedance input pre-amplifier is often incorporated in the same housing as the microphone capsule to increase the available signal level to about 1mV in normal use. It should, perhaps be mentioned that the electrostatic principle has also been applied, very successfully, to the production of wide frequency response loudspeakers and high frequency tweeter units where advantage is taken of the low mass of the moving parts of the transducer.

Next Month: Opto-electronic devices

DISPLAYS CLOCK CHIPS

DL707	£1-70	3015F	£1-25	5LT01	£5-80	CT7001	£7-30*
DL704	£1-70	3017F	£2-00	MM5311	£5-18	CT7002	£7-30
DL701	£1-70	RDS1	£8-00	MM5314	£4-44*	CT7003	£7-30
DL747	£2-45	RDM2	£24-80	MM5316	£9-25	CT6002	£15-00
DL750	£2-45	DG12	£1-20	MK50250	£5-60*	TMS3952	£10-50
DL746	£2-45			HEEC2	£8-50		

*Available in a MHI kit

Other chips and displays usually available, ring for details or S.A.E. for catalogue and prices.

VAT on clocks, clock chips and displays still 8%.

We advise the use of sockets for all I.C.s. 24/28/40-pin £1.

BYWOOD ELECTRONICS

181 Ebbw Road, Hemel Hempstead, Herts., HP3 9RD

Terms: C.W.O., Access, Barclaycard (quote card No.).

All prices on this advert exclude VAT. Tel. 0442 62757

THERE are two basic sets of Voice Filters, one set covers the Piano tone, whilst the other set produces the Harpsichord effect. The Honky-Tonk sound is produced by mixing the two voices together. The full set of filters is shown in schematic form in Fig. 4.1. The bottom two octave outputs from the Envelope Board are connected to the low (L) input, the middle two octaves to the (M) input, and the top octave to the (H) input. The voice circuits make wide use of passive low and high pass filters, but the main response is obtained from the use of adjustable band pass amplifiers based on the integrated circuit operational amplifier type 741.

FREQUENCY RESPONSE

The overall frequency response of the Piano and Harpsichord filters are shown in Fig. 4.2. Referring to the Piano filter response curves it can be seen that the three filters are set up centred on different frequencies of approximately 420Hz, 550Hz, and 700Hz. This makes the bottom three octaves rich in at least the second harmonic, with a lower harmonic content for the top two octaves. The range of fundamental frequencies applied to each filter is indicated above the graph.

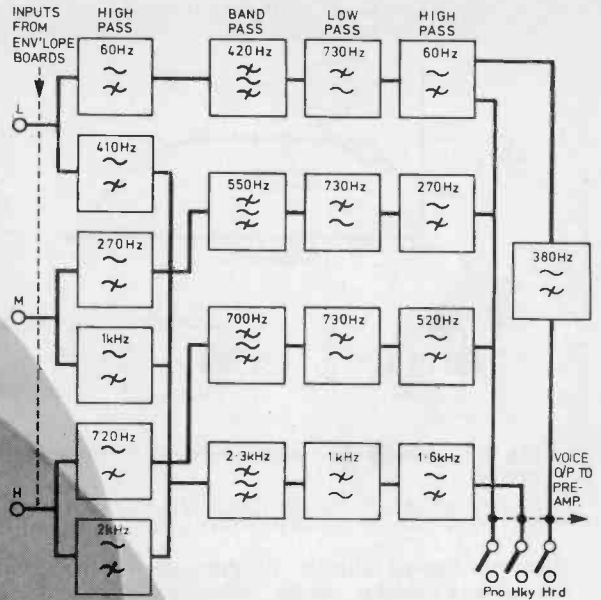


Fig. 4.1. Voicing filters for the Joanna

PE JOANNA PART 4

By A.J. BOOTHMAN B.Sc.

The Harpsichord filters have a very sharp bass cut response, with some variation between (L), (M) and (H) inputs. Consequently the second and higher harmonics are strongly emphasised, with the fundamental being well attenuated. A high frequency roll off is necessary in order to reduce the effect of beehive breakthrough. From both Fig. 4.1 and Fig. 4.2 it can be seen that a high degree of low frequency cut is used on the mid and high range Piano inputs. This controls the attack "thump" in these registers to a realistic degree, and further high pass filtering on the low range input reduces the bass response when the Honky-Tonk voice is selected.

OUTPUT WAVEFORMS

Sample waveforms are shown in Fig. 4.3, for each of the C notes on the Piano voice setting, and middle C on Honky-Tonk and Harpsichord voice settings. On the Piano voice waveforms the variation in harmonic content across the compass is clearly demonstrated, with predictable modifications to the waveform for the other two voices.

VOICE FILTER CIRCUITS

The Voice Filter circuitry is shown in Fig. 4.4. The low, medium, and high inputs are controlled by I.C. 8, 9 and 10 respectively whilst the main Harpsichord filter is built around IC7. The Q of these twin-T band-pass amplifiers can be adjusted by the associated preset potentiometers, and the voice selection is achieved by opening the correct voice switch which is normally shorting its signal to ground.



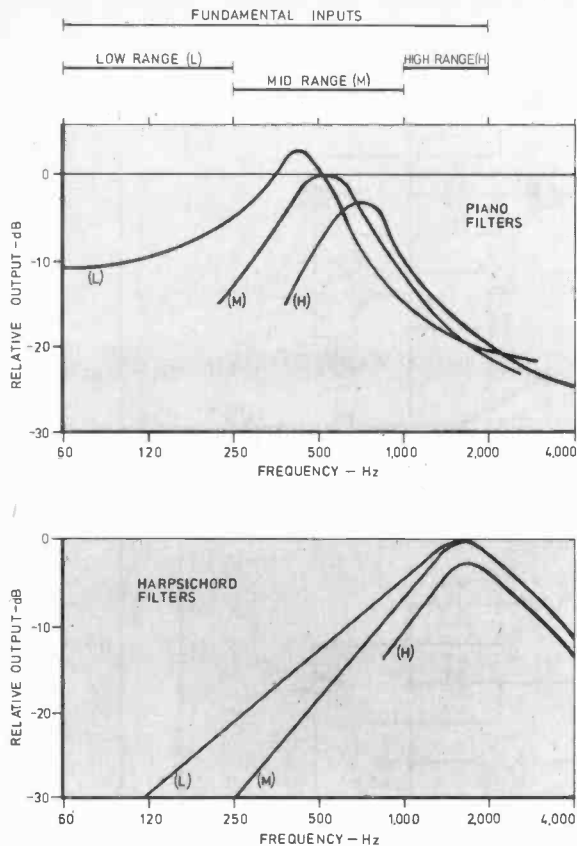


Fig. 4.2. Frequency responses for the Piano and Harpsichord filters

PREAMPLIFIER

The Voice Filter outputs are mixed into a 741 preamplifier, which has a voltage controlled amplifier type MFC6040 in a feedback loop. This i.c. can handle up to 500mV r.m.s. at pin 3 and therefore requires a voltage sharing resistor network on its input as shown in Fig. 4.5. Since the amplifier is an inverter its output is fed into the non inverting input of the 741 to give negative feedback. The overall gain of the preamplifier is controlled by a d.c. input line to pin 2 of the MFC6040 the voltage of which is set by preset potentiometer VR9, and is further adjusted by the Soft Pedal switch and Tremolo Generator.

HEADPHONE AMPLIFIER

The circuit for the headphone amplifier is also shown in Fig. 4.5, and uses a low power (250mW) Class B integrated circuit type MFC4000B. This amplifier will drive approximately 40mW into standard stereo headphones, which when connected in parallel have an impedance of approximately 4 ohms. The MFC4000B is powered by a 10 volt rail taken from the power supply unit on the input to the 5 volt regulator.

TREMOLO GENERATOR

A phase shift oscillator can be operated at two alternative frequencies to generate slow and fast tremolo effects, TR22 amplifies the sinewave output from the oscillator and modulates the d.c. control voltage to the MFC6040.

SUPPLY LINES AND SUSTAIN PEDAL CIRCUITS

In order to simplify Figs. 4.4 and 4.5, the power supply lines and components have been omitted and are shown in Figs. 4.6 and 4.7. The Sustain Pedal

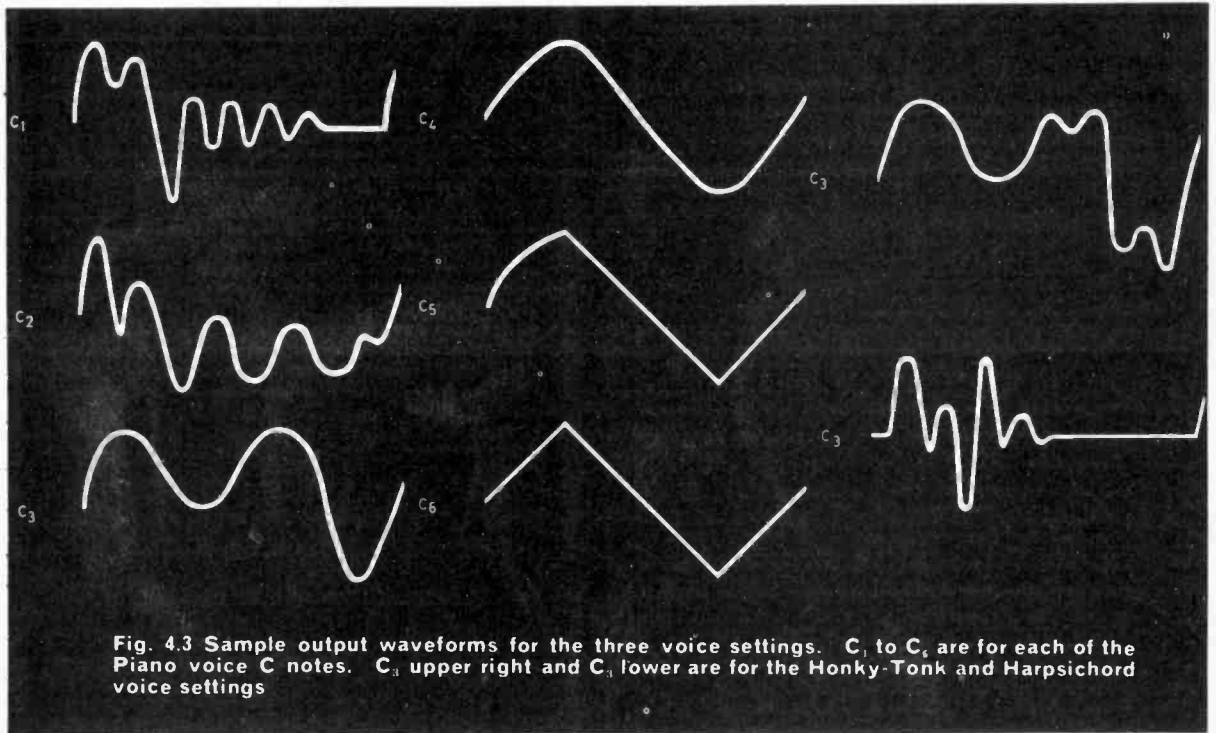


Fig. 4.3 Sample output waveforms for the three voice settings. C₁ to C₃ are for each of the Piano voice C notes. C₄ upper right and C₄ lower are for the Honky-Tonk and Harpsichord voice settings

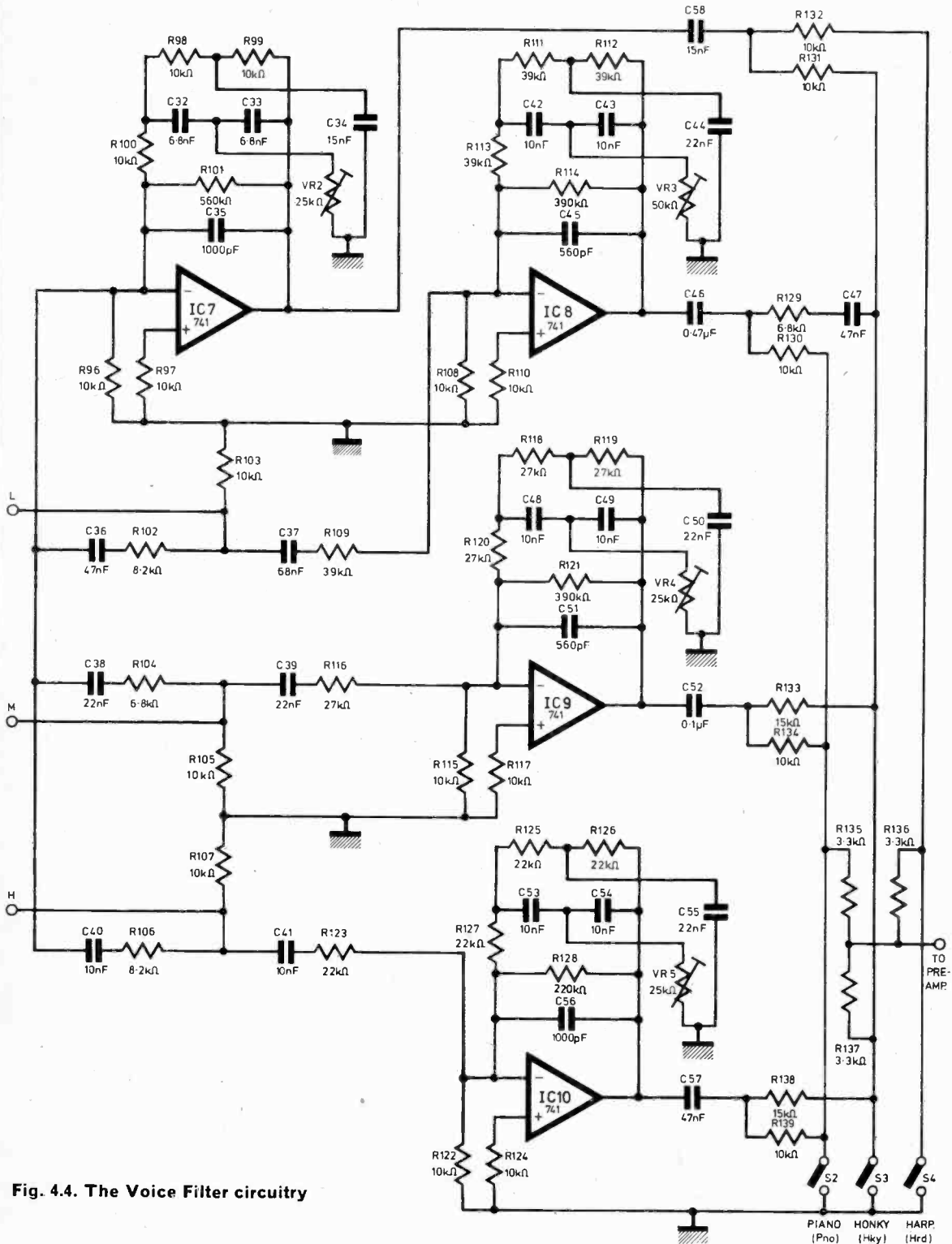


Fig. 4.4. The Voice Filter circuitry

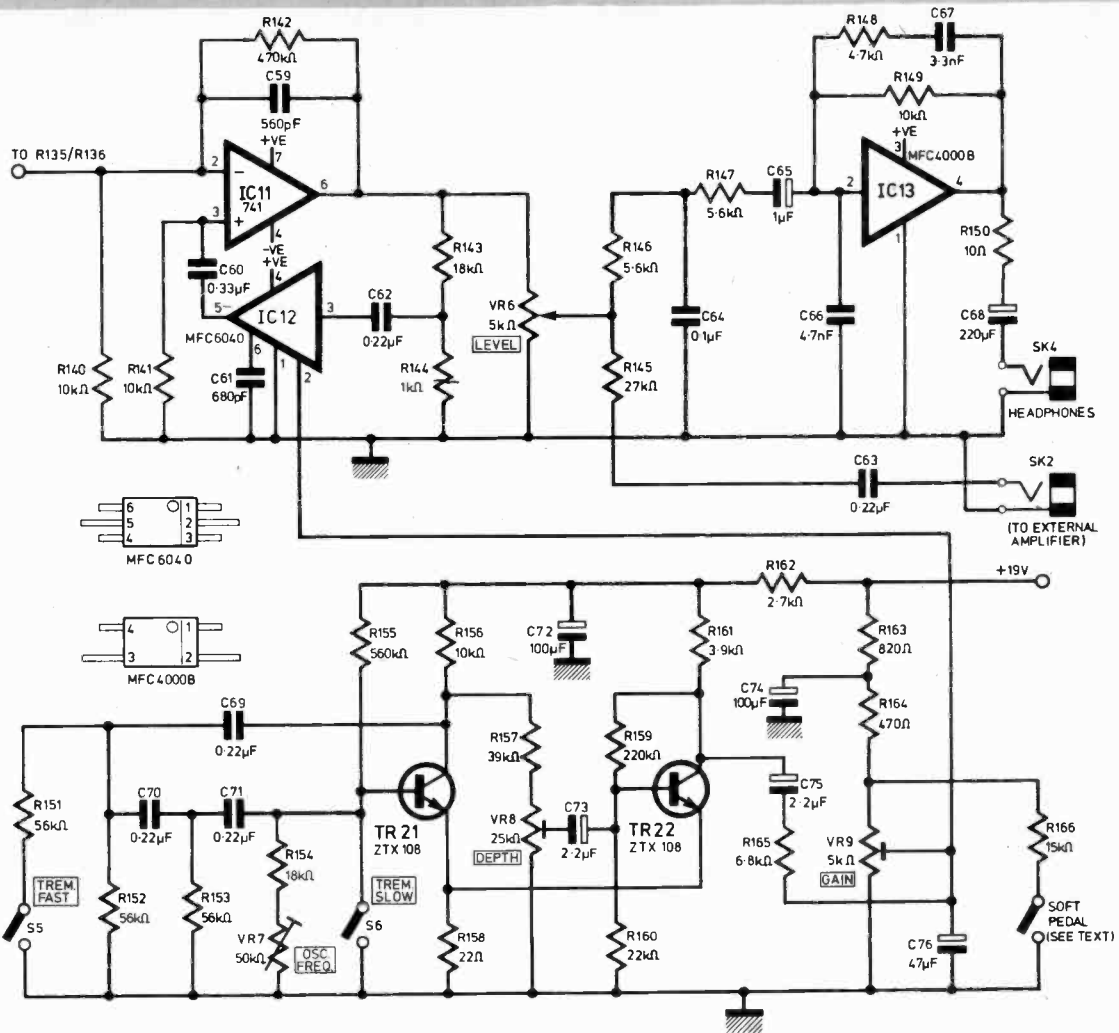


Fig. 4.5. Circuits for the Preamplifier, Headphone Amplifier, Tremolo Generator and Soft Pedal action

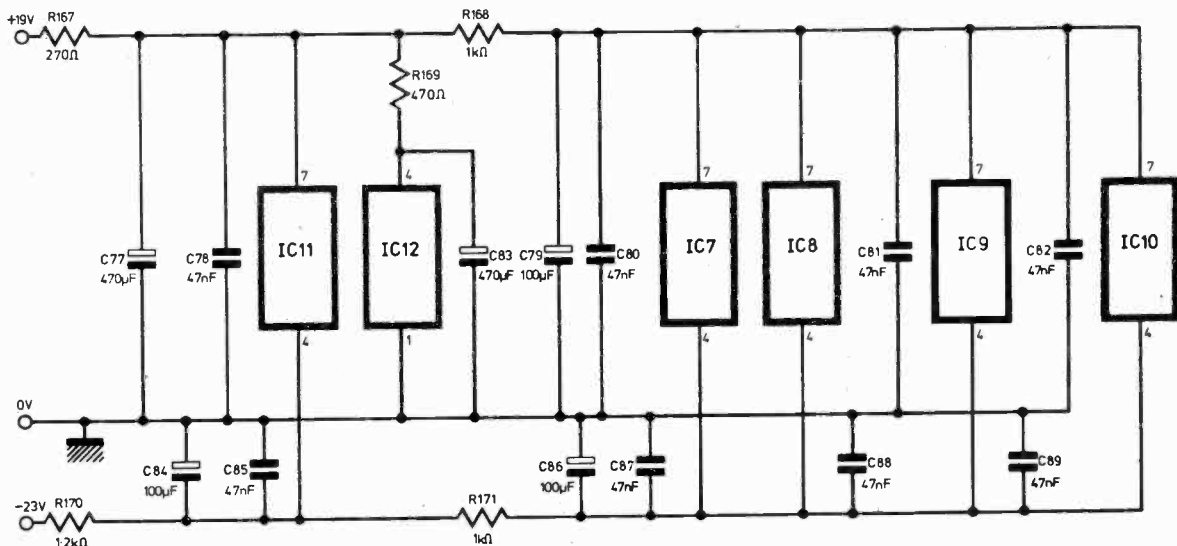


Fig. 4.6. Power supply line components for the Voice circuits and Preamplifiers

COMPONENTS . . .

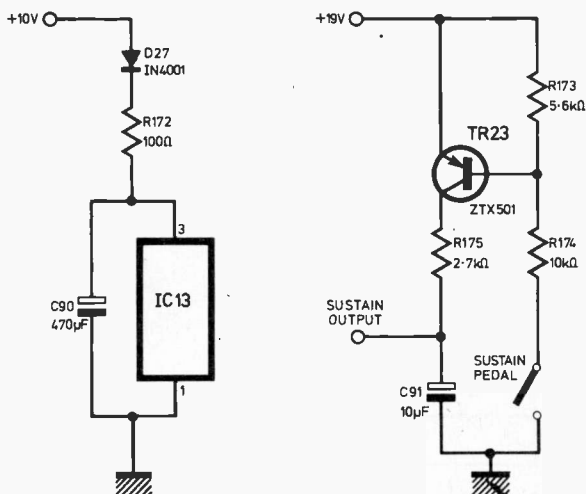


Fig. 4.7. Power supply components for Headphone Amplifier and the Sustain Pedal circuit

circuit is also shown which uses a *pnp* transistor, normally in the off condition. When the pedal is depressed, the transistor is switched on, and the output rises from ground potential to approximately 9 volts (see Fig. 4.7).

VOICE/PREAMPLIFIER BOARD

The Voice Filters, Preamplifier, Headphone Amplifier, Tremolo circuitry, Soft and Sustain Pedal circuitry are all mounted on a single printed circuit board, the etching and drilling details for which are given in Fig. 4.8, with component mounting details.

The component density on this board is very high, and some extra care will be necessary in construction to ensure that the components used can be accommodated on the board. Terminal pins and presets should first be assembled on the board, followed by resistors, small capacitors, transistors, and integrated circuits. The larger capacitors should be assembled last, and will in some cases be positioned at a distance from the board surface to clear small components which will lie underneath them. Care should be taken to ensure that the transistors and integrated circuits are inserted in the correct orientation, corresponding with the assembly details given in Fig. 4.8, and that the electrolytics are inserted with the correct polarity.

VOICE CIRCUIT ADJUSTMENT

The overall gain of the Preamplifier is first set by adjustment of VR9 to a level which does not distort the output when two heavy chords are played together at maximum weight, with the output level control VR6 set at maximum. The tone/colour of the Piano sound is set by VR3, VR4 and VR5, for the lower two octaves, middle two octaves and top octaves respectively. These should be individually adjusted, with S3 and S4 closed, to suit the ear of the constructor. VR2 controls the Harpsichord and should be adjusted with S2 and S3 closed, to the point of minimum background breakthrough.

VOICE/PREAMPLIFIER BOARD

Resistors

R96-100	10kΩ	R128	220kΩ	R157	39kΩ
R101	560kΩ	R129	6.8kΩ	R158	22Ω
R102	8.2kΩ	R130-132	10kΩ	R159	220kΩ
R103	10kΩ	R133	15kΩ	R160	22kΩ
R104	6.8kΩ	R134	10kΩ	R161	3.9kΩ
R105	10kΩ	R135-137	3.3kΩ	R162	2.7kΩ
R106	8.2kΩ	R138	15kΩ	R163	820Ω
R107-108	10kΩ	R139	10kΩ	R164	470Ω
R109	39kΩ	R140-141	10kΩ	R165	6.8kΩ
R110	10kΩ	R142	470kΩ	R166	15kΩ
R111-113	39kΩ	R143	18kΩ	R167	270Ω
R114	390kΩ	R144	1kΩ	R168	1kΩ
R115	10kΩ	R145	27kΩ	R169	470Ω
R116	27kΩ	R146-147	5.6kΩ	R170	1.2kΩ
R117	10kΩ	R148	4.7kΩ	R171	1kΩ
R118-120	27kΩ	R149	10kΩ	R172	100Ω
R121	390kΩ	R150	10Ω	R173	5.6kΩ
R122	10kΩ	R151-153	56kΩ	R174	10kΩ
R123	22kΩ	R154	18kΩ	R175	2.7kΩ
R124	10kΩ	R155	560kΩ		
R125-127	22kΩ	R156	10kΩ		

All $\frac{1}{2}$ watt, 5% tolerance.

Capacitors

C32-33	6.8nF	C62-63	0.22μF
C34	15nF	C64	0.1μF
C35	1,000pF	C65	1μF 16V elect.
C36	47nF	C66	4.7nF
C37	68nF	C67	3.3nF
C38-39	22nF	C68	220μF 10V
C40-43	10nF	C69-71	0.22μF
C44	22nF	C72	100μF 16V elect.
C45	560pF	C73	2.2μF 16V elect.
C46	0.47μF	C74	100μF 16V elect.
C47	47nF	C75	2.2μF 16V elect.
C48-49	10nF	C76	47μF 16V elect.
C50	22nF	C77	470μF 16V elect.
C51	560pF	C78	47nF
C52	0.1μF	C79	100μF 16V elect.
C53-54	10nF	C80-82	47nF
C55	22nF	C83	470μF 16V elect.
C56	1,000pF	C84	100μF 16V elect.
C57	47nF	C85	47nF
C58	15nF	C86	100μF 16V elect.
C59	560pF	C87-89	47nF
C60	0.33μF	C90	470μF 10V elect.
C61	680pF	C91	10μF 16V elect.

Diode

D27 1N4001

Transistors

TR21-22 ZTX108 TR23 ZTX501

Integrated Circuits

IC7-11 741 IC12 MFC6040 IC13 MFC4000B

Potentiometers

VR2	25kΩ horiz preset
VR3	50kΩ preset
VR4	5-25kΩ preset
VR6	5kΩ 1in pot. with switch
VR7	50kΩ horiz preset
VR8	22kΩ horiz preset
VR9	5kΩ horiz preset

Miscellaneous

S2-6 Single pole on-off switch
Terminal pins (27 off)

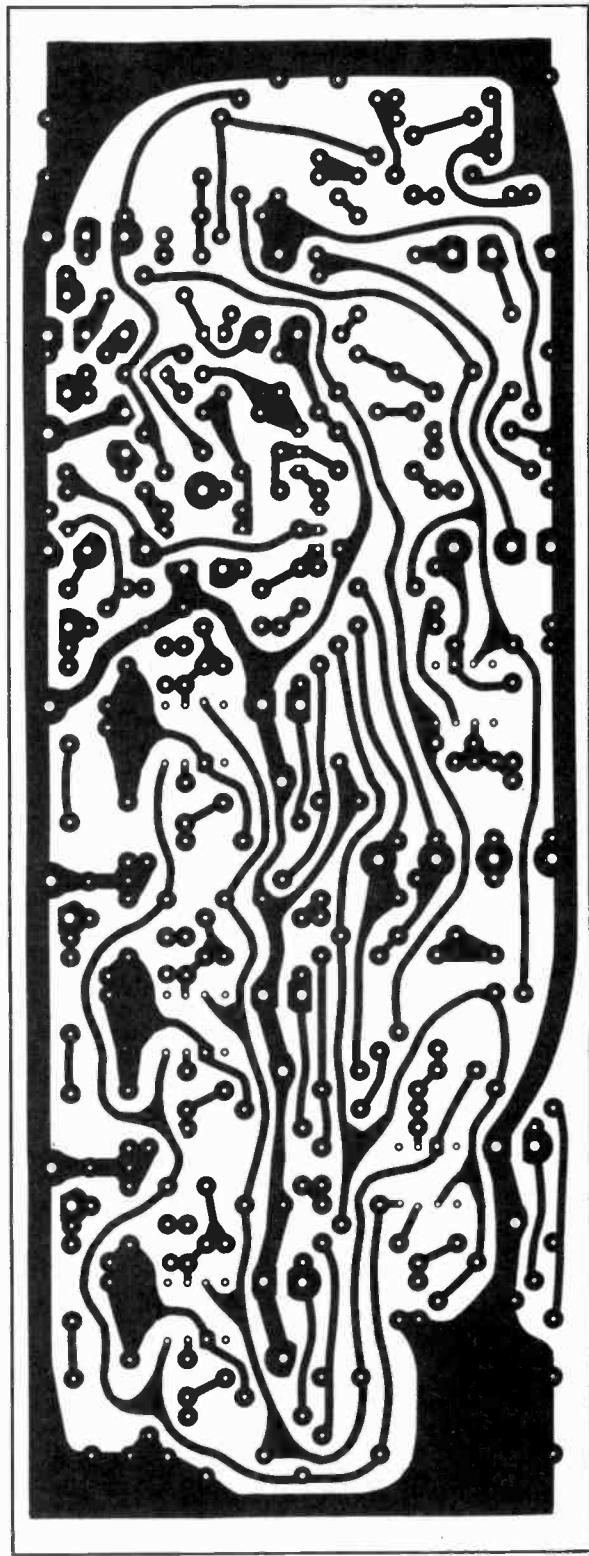
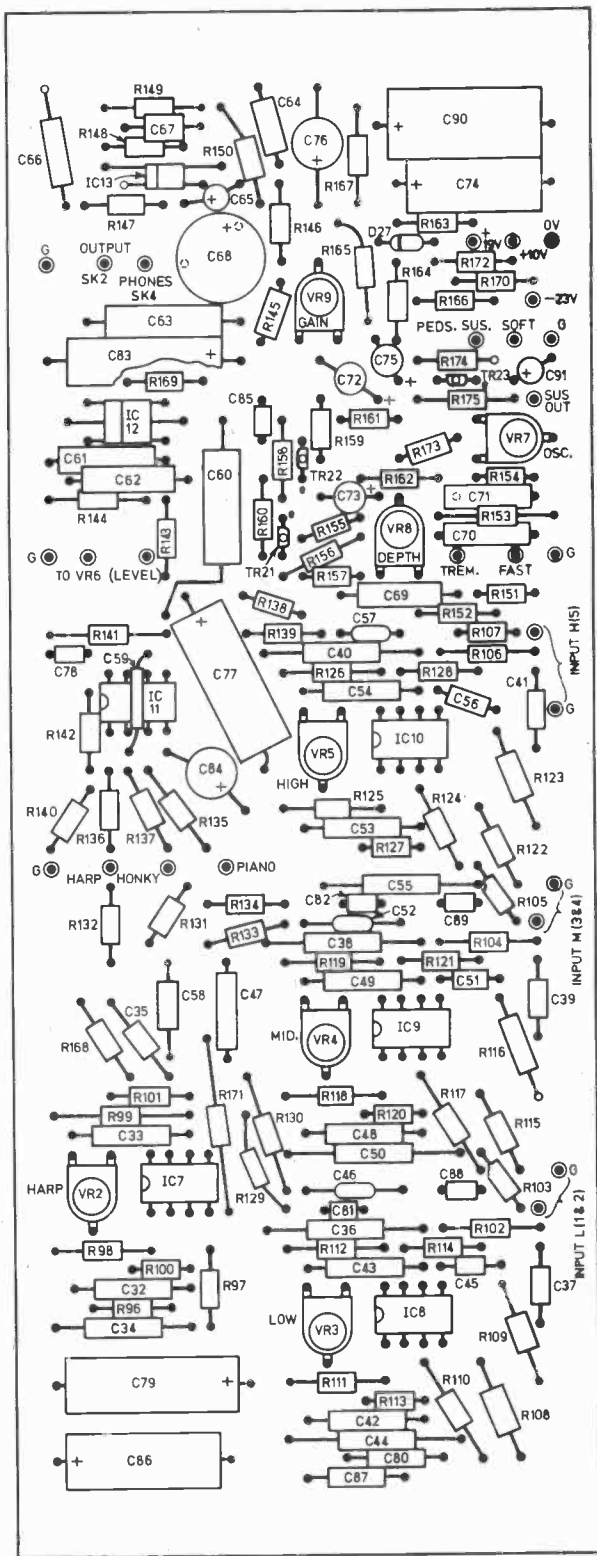


Fig. 4.8. Component mounting and p.c.b. etching details

TREMOLO ADJUSTMENT

With S6 open the Tremolo Generator may or may not oscillate immediately which can be determined by setting VR8 approximately at the centre of its travel. If oscillation does not occur, VR7 should be adjusted until oscillation commences. VR8 should then be adjusted until a good level of tremolo is obtained with minimum breakthrough sound in the speaker when a note is not being played. S6 should be switched on and off to ensure that the generator starts reliably every time, and VR7 slightly re-adjusted until a consistent start is obtained. With S5 closed the fast tremolo should work. If the background tremolo breakthrough increases on this setting, VR8 should be adjusted.

OVERALL TONE VARIATION

Some variation in overall tone may occur depending on the power amplifier and speaker combination used with the Piano. Further top cut may be obtained if required by increasing the value of C59.

PEDAL SWITCHES

The switches associated with the pedals have a very simple single pole on/off action, the mechanical arrangement of which will be described on the last part of the series. Pedal action occurs in both cases when the relevant switch is closed to ground, and can be simulated for test purposes by shorting straps on the board from the relevant pin to ground.

In the case of the Soft Pedal, the degree of attenuation is controlled by R166. The individual characteristics of each MFC6040 can effect the attenuated level, and it may in some cases be necessary to change the value of R166 to suit. A lower value should be used for increased attenuation.

It should be noted that patents are pending for the envelope generation system.

Next month: Case assembly, amplifier and tuning details.



V.A.T. AND COMPONENTS

FOR the benefit of our readers and advertisers we publish, in full, a press announcement by Customs and Excise and the Electronic Components Board. This explains how the new V.A.T. regulations are being interpreted in respect to circuit components (see opposite page).

The following additional information helps clarify the V.A.T. situation as it affects home constructors. The details were obtained in the course of direct consultations with the headquarters of H.M. Customs & Excise.

Readers having particular problems are advised to contact their local H.M. Customs & Excise V.A.T. Office.

HOME CONSTRUCTOR KITS

A concession has been made in respect of *Complete Kits* for making goods or equipment of a kind that are subject to the lower (standard) rate of V.A.T. (for examples see below). Where less than one third (by value) of the components included in the kit are rated, individually, at 25 per cent, the whole kit is chargeable at 8 per cent.

GENERAL PURPOSE MATERIALS

All Veroboard, blank s.r.b.p., and other general purpose building materials are chargeable at 8 per cent. Printed Circuit Boards, being designed for specific uses, are chargeable according to the rate appropriate to the finished equipment.

COMPLETE EQUIPMENTS

Subject to the Higher Rate of V.A.T.

Includes: Radio, television and audio equipment, electronic musical instruments, and most electrically operated domestic (and gardening) appliances, photographic aids, d.c./a.c. inverters, and power supplies.

Subject to the Standard Rate of V.A.T.

Includes: Digital clocks, pocket calculators, automobile devices (not for in-car entertainment), most kinds of electronic test equipment, e.g. electronic test meters, signal generators and c.r.o.'s, Geiger counters, gas detectors, metal locators, light dimmers, thermometer controllers, electronic games.

MAIL BAG

The on-going increase in postal and telephone charges does not seem to have made any difference to our post bag or our telephone bell. Enquiries continue to flood in.

We find that there are two points we are constantly mentioning. In the first place we just cannot afford to reply to any *readers letters*, particularly those not associated with projects we have published, unless they are accompanied by a *stamped addressed envelope*. Were we to undertake to do so our post bill would become astronomical.

We cannot deal with *technical enquiries by telephone*. Readers should write in, giving details of symptoms and perhaps some test point readings, when requesting technical help so that we can at least give the relevant author some idea of the problems involved.

Finally, whilst we normally supply details as to source of components in each project we do assume that the constructor refers to advertisements and has an awareness of general sources. Thus, where goods are generally available we do not specify a source. You could save the cost of a letter by reading the advertisement pages first.

V.A.T.

JOINT PRESS ANNOUNCEMENT BY CUSTOMS AND EXCISE AND THE ELECTRONIC COMPONENTS BOARD

The Electronic Components Board have made representations to the Government that the Finance Bill should be amended to exclude the application of the 25 per cent rate of VAT to electronic components. These representations are being considered, but meanwhile the Electronic Components Board and the Department of Customs and Excise have been in consultation in order to establish means of interpreting the law as it stands at present in such a way to give rise to a reasonable minimum of difficulty.

The Electronic Components Board and Customs and Excise have agreed upon the following recommendations to traders:

1. *Product categories to be charged at 25 per cent VAT*
 - a. TV cathode ray tubes.
 - b. TV tuners including tuners featuring touch button controls and/or remote control units.
 - c. TV delay lines.
 - d. TV, radio and audio loudspeakers (except loudspeakers suitable only for public address purposes).
 - e. TV and radio wound assemblies (deflection coils, colour correction coils, line output transformers, switched mode inductors, wound aerial rods, r.f. and i.f. wound assemblies).
 - f. All receiving valves for domestic use.
 - g. All voltage multipliers for domestic use (triplers, etc)
 - h. Modules for domestic appliances.
 - i. Consumer modules for TV, radio and audio equipment.
 - j. Linear integrated circuits suitable for use in TV, radio and audio equipment.
 - k. Discrete Semiconductors:
 - i Transistors, triacs and thyristors, plastic encapsulated and less than 3 amps rating.
 - ii Power transistors for TV deflection applications.
 - iii All plastic diodes of less than 1 amp rating, excepting 2f.
 - iv All plastic encapsulated Zener diodes of power rating less than 3 watts.
 - v Rectifiers of a kind suitable for use in low voltage battery charger equipment having a current rating of less than 5 amps.
 - l. Capacitors (excluding those types indicated in 2m).
 - m. Resistors (excluding those types indicated in 2n).
 - n. Switches having a rating of less than 5 amps and user controls (variable resistors, etc) of less than 2 watts max. dissipation of a kind suitable for use in TV, radio and audio equipment.
2. *Product categories to be charged at 8 per cent VAT*
 - a. Professional assemblies.
 - b. Storage systems.
 - c. Matrix stacks.
 - d. Industrial assemblies (Norbit logic elements, etc).
 - e. Automobile assemblies (excluding those products used for in-car entertainment equipment—radio, stereo, etc).
 - f. Microwave products (tube, solid state or passive networks).
 - g. Professional deflection assemblies.
 - h. All professional tubes.
 - i. Infra red devices.
 - j. Integrated circuits (excluding items indicated in 1f).
 - k. Ferrites and wound ferrites (excluding items indicated in 1e).
 - l. All discrete semiconductors (excluding those items indicated in 1k).
 - m. Capacitors:
 - i Paper capacitors of greater than 0.5 microfarad and/or metal cased.
 - ii Sintered Tantalum capacitors of greater than 300 microfarad and/or metal cased.
 - iii Film capacitors meeting IEC specification 68.2 or equivalent (21 day humidity rating) and/or metal cased.
 - iv Electrolytic capacitors meeting IEC specification 103 Type I—85 C or equivalent specification or operating in excess of 200 V.a.c.
 - v Mica capacitors.
 - vi Vacuum and pressure gas capacitors.
 - n. Resistors:
 - i Metal film with a stability better than 1 per cent over 1,000 hours.
 - ii Wirewound resistors (except main ballast resistors of a kind suitable for use in TV, radio or audio equipment).
 - o. Edge Connectors and connectors for more than 8 ways.
 - p. Electro mechanical components—excluding switches having a rating of less than 5 amps and user controls (variable resistors, etc) of less than 2 watts max. dissipation of a kind suitable for use in TV, radio and audio equipment.
 - q. Magnets.
 - r. Printed circuits for the assemblies described in items 2a, 2d and 2e.

It is recognised that there may be some individual products to which the application of these definitions is not entirely straightforward. If a firm finds one of its products is described above as chargeable at 25 per cent but, in its view, the product is not suitable for use as a part of goods within the Higher Rate Schedule, it may report the facts to the Electronic Components Board which will, if necessary, take the matter up with Customs and Excise, when an individual ruling will be given. The recommendations above will, in any case, be kept under review in the light of experience.

See also notes on page 656.



London Electronic Component Show

DESPITE the current economic climate, a much reduced volume of exhibitors and a general atmosphere of depression in the industry, the 1975 London Electronic Component Show was still well attended by both the trade and non-professional visitors. Indeed, for the first time in years it was almost possible to get round, in a very sketchy manner, in a day, rather than being faced with the very necessary two or three day effort the larger past events have demanded.

Clearly, the days of the Honeywell Girl and bikini-clad beauties draped over oscilloscopes or resistors are, almost, things of the past—a good or a bad thing dependent on your viewpoint. But the absence has not in any way detracted from the interest level of the show because, with a scope extending from simple resistors and capacitors right through to manufacturing plant and instrumentation, there was lots for all to see. The more so with the growing application of i.c.s to all walks of life.

TRAINS AND

In this context all the main names appeared to be on show and one of the more eye-catching exhibits was, of all things, a model railway on the GEC Semiconductors' stand. To be honest, the railway was only being used to illustrate the operation of a sorting system under the control of a microprocessor. In fact the demonstration was very effective, consisting of shunting a large number of small carriages, each

with a letter of the alphabet on its roof, until they made up a sentence which could be read.

Data input to the system to instruct what was to be "printed" was through a keyboard-input visual display unit and the actual sorting from a jumble of letters to a sensible set of words took only a matter of minutes. Indeed, the speed of the system was very obviously limited by the operational speed of the trains rather than the microprocessor.

From the comments of bystanders it is very obvious that this area of semiconductory is now well to the forefront of the development wave. It has obvious application areas in things like business machines, complex desk calculators, teaching machines and all sorts of data handling areas from industry to commerce.

The train system was demonstrated by GEC Semiconductors and used the Intel 8080 microprocessor chip. This is a new device which is fast proving itself out in the British market.


The same manufacturers now sell a simpler device, the 4040, which is capable of many applications such as badge reading, automotive control, multi-function calculator applications and so on, for a mere £13.97 one-off.

Clearly this type of product is finding its way into the low cost experimental areas.


SETS AND

Semiconductors are not the only area where more is being supplied in one package. On the television front it is not unusual to see tubes supplied ready equipped with yokes and other associated parts as a pre-assembled unit. Thus Thorn Colour Tubes now supply setmakers with their P.I. (Precision In-line) colour tubes as an assembly including scanning coils and beam bender units. In this way all the dynamic and static convergence and purity adjustments are precision set prior to the units leaving the factory.

Such sophistication allows the new tubes to be plugged into a



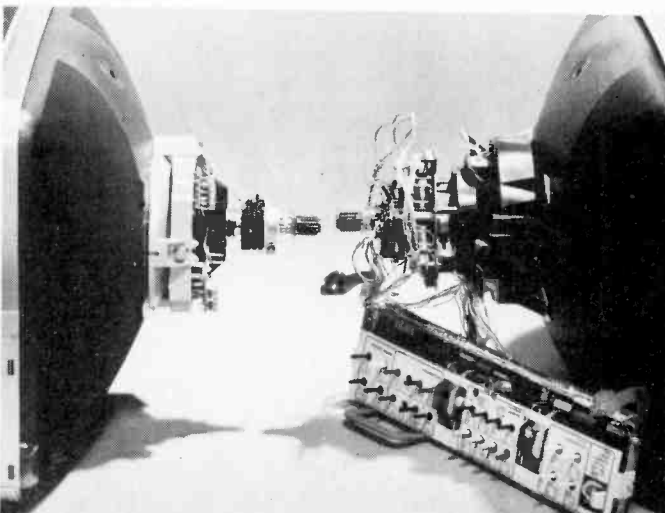The Weller
DS100 solder-
ing and desol-
dering station



Thorn precision
in-line 110
colour tube
compared with
a conventional
110 tube

colour set with much the same ease as a black-and-white tube.

TOOLS AND

Staying for a moment with the mechanical side of electronics, for the more wealthy amongst us Weller have produced a smart soldering and desoldering station specifically designed with the printed circuit man in mind. Incorporated are a soldering iron and a selection of bits, holder, low voltage transformer, desoldering tool in the shape of a further iron and suction equipment with a foot switch for "hands-free" actuation, and a nice "see-through" solder collector.

It is surprising just how many people were showing a very active interest in the British Central Electrical E-Z-Hook products, those tiny and not-so-tiny test terminals with projecting/sliding hooks which lend themselves to latching on to wires on a p.c.b. or in similar inaccessible places.

Their latest brainchild is the Micro-Hook, a version designed

to cope with multi-legged i.c.s so as to get signals in to or out from chips without removal or shorting.

MEASUREMENT

Instruments always attract a lot of interest at any electronic exhibition and this year probably one of the more interesting products was a tiny oscilloscope from the now renowned firm of Scopex.

Called the IS 10, the new instrument only measures $135 \times 196 \times 60\text{mm}$ and has the surprising bandwidth of d.c. to 10MHz at 500mV/div. This drops to 1MHz at 10mV/div.

Horizontal sweep speeds are from 1 μs to 1s/div and the trigger can be positive or negative and will free run when without a signal.

As a battery portable instrument priced at £198, this is quite something for the engineers briefcase, to go with his Sinclair Cambridge 300 and pocket tape recorder. For the rest of us the

normal Scopex 10MHz beast will presumably suffice quite well!

Still on the instruments front there were some interesting developments from J. J. Lloyd with a series of low-cost chart recorders which started at £110 for a single-channel version known as the CR500. This is a real down-to-earth instrument without any frills designed to meet most educational and quite a few industrial applications. It is a 1 per cent instrument with five ranges from 10mV or 10 μA up to 100V f.s.d., 2 per cent linearity and 0.5 per cent repeatability. Not at all bad for the price.

A three-channel version, the CR503, is also available.

Just to round off the instruments, there were quite a few overseas sourced items including complex automatic test gear. Some, indeed, seems to go beyond the needs of British customers since one manufacturer was showing telephone dial test equipment capable of coping with touch-dial machines.


Slowly it is dawning on many people that whilst touch dialling will be available here some time in the future it will not utilise the full speed of the system as each telephone will have to be fitted with a memory which will accept the mechanically inputted information and release it slowly enough for the telephone system equipment to cope with it.

MINIATURISATION

So much for high speed test gear!


Whatever direction one moves in, miniaturisation seems to appear on all sides. Resistors and capacitors get constantly smaller or are uprated, which amounts to the same thing, and hybridisation or other methods of construction allow yet further reduction in size. Typical items appeared on the Welwyn stand where hybridisation was displayed together with some rather interesting layer-built applications of the principle.

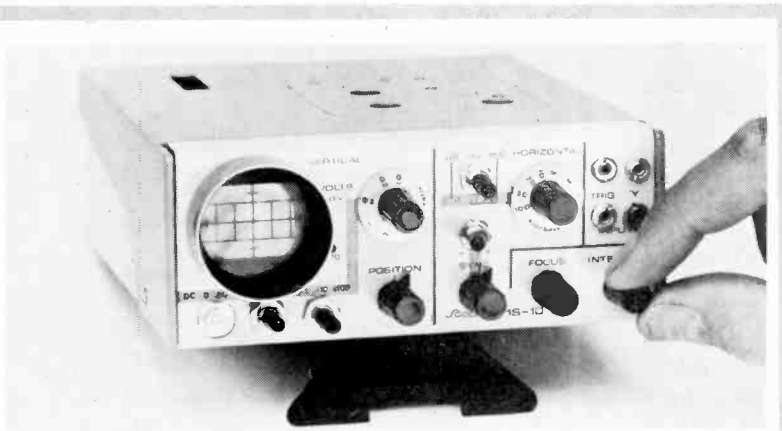On the same stand were some applications of planar resistors, truly precision devices mounted on TO18 or slightly larger headers. With a wide value range available capable of achieving down to ± 0.005 per cent this product is ideally suited to precision resistor networks.




The miniature Scopex 1S 10 10MHz oscilloscope

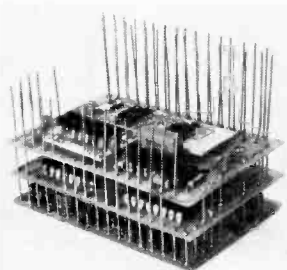A planar resistor mounted on a TO18 header



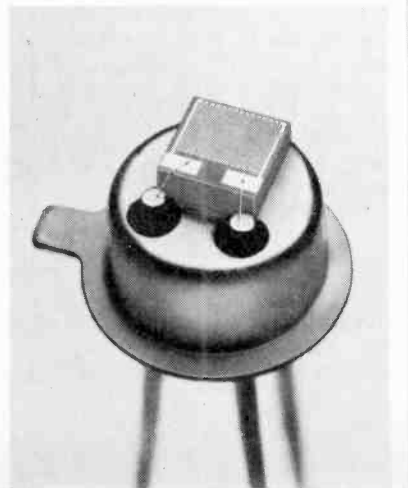The high component density obtainable with hybrid circuits



TO CONTROL the voltage applied to a circuit it is necessary to have a reference voltage which, typically, is obtained by the use of a Zener diode.

However, it is a well-known—if little used, fact that when a transistor is in operation the voltage between the base and emitter, V_{be} , is affected little by large changes in base current, I_b , assuming a value close to 0.2V for germanium transistors, and close to 0.6V for silicon transistors. Similarly, I_b is almost zero unless V_{be} exceeds a minimum value equal to roughly 0.1V and 0.5V for germanium and silicon transistors respectively.

This article explores a number of possible applications for this "built-in" reference voltage. It must be noted here that because of the relatively large fractional changes that occur in V_{be} with germanium transistors, the initial increase in base current with increasing base-emitter voltage is rather slower than for comparable silicon transistors and thus, for most of the uses discussed, silicon transistors operate more effectively than germanium transistors.

circuit of Fig. 1. Relevant information is presented in the form of Tables 1 and 2.

In Table 1, information is given describing the behaviour of two BC109s and two OC81s, the theoretical values being calculated assuming switch-on voltages of 0.55V and 0.09V for the BC109 and OC81 transistors respectively.

The Zener voltages recorded here were obtained by extrapolating the roughly linear, low resistance part of the I/V characteristics to obtain an intersection with the V -axis.

This can be done quite easily with silicon transistors, but is much harder with germanium transistors for the reason noted earlier, the values recorded for the OC81s thus suffering from considerable uncertainty.

Table 2 compares the behaviour of a number of silicon and germanium transistors (two of each type were used). The Zener voltages recorded are "apparent" because they were obtained simply by recording the voltage across the circuit of Fig. 1

THE TRANSISTOR AS A ZENER

By I. D. EVANS

ZENER DIODE CIRCUITS

Fig. 1 shows a simple circuit which can perform the function of a Zener diode, switching from a low to a high conductance state over a fairly narrow voltage range in the region of a voltage determined by the relative values of R_1 and R_2 . When V is low, V_{be} is determined solely by the R_1/R_2 potential divider since there will be no base current and hence all the current through R_1 must flow through R_2 . This will apply until V_{be} reaches the critical value referred to above, the corresponding value of V in

volts being approximately $\frac{R_1 + R_2}{10 \times R_2}$ and $\frac{R_1 + R_2}{2 \times R_2}$ for

germanium and silicon transistors respectively. As V increases above this value, I_b , and with it I_c start to increase in such a way that V_{be} remains nearly constant. The dynamic resistance of the circuit can be shown to be approximately equal to R_1 divided by β , the common emitter current gain of TR1.

Thus the circuit behaves like a Zener diode with a Zener voltage and dynamic resistance as given above. One important difference, however, is that the Zener voltage can readily be adjusted over a wide range by using a combination of variable and fixed resistors in place of R_1 and R_2 . Variation of R_2 alone is advised since this will have no effect on the dynamic resistance of the circuit when in the "on" state and little effect on the resistance of the device in the "off" state resulting from the finite values of R_1 and R_2 .

ACTUAL VALUES

It may be helpful, or at least of interest, to include comparisons between theory and the actual behaviour of selected transistors when used in the

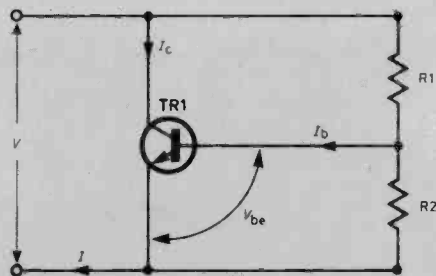


Fig. 1. Basic "Zener Transistor" circuit

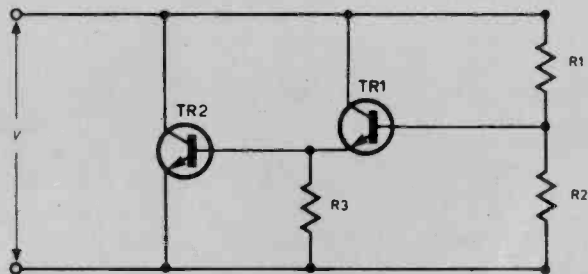


Fig. 2. A high version of the circuit of Fig. 1

when a current of approximately 0.25mA was flowing through the transistor.

This measurement can be made by connecting a 68kΩ resistor in series with the circuit of Fig. 1, applying 20V across the combination and measuring the collector-emitter voltage with a voltmeter having a resistance of 100kΩ or more (thus a 10kΩ/V, 10V f.s.d. instrument is quite satisfactory for the purpose).

The Zener voltages predicted here, assuming switch-on voltages of 0.55V and 0.09V for all the silicon and germanium transistors respectively, are 4.3V and 2.9V for the circuits using silicon and germanium transistors respectively.

A useful modification of this basic circuit is shown in Fig. 2. Here, two transistors are coupled in such a way that the combined gain is approximately equal to the product of the common emitter current gains of the two transistors. As a result of the very high effective β one can achieve a very low value for the dynamic resistance in the on state and/or a very low value for leakage current flowing through R1 and R2 in the off state.

R3, a suitable value for which will be in the range from 10kΩ to 1MΩ, helps reduce the effects of leakage current through TR1 which would be amplified by TR2. R3 is thus most important when germanium transistors are being used since these often have relatively high leakage currents; however it also helps circuit performance with silicon transistors.

Table 1. Practical (a) and theoretical (b) Zener voltages (R2 fixed at 10kΩ for the BC109's, or 2.2kΩ for the OC81's)

R1	BC109		OC81	
	a (volts)	b (volts)	a (volts)	b (volts)
10kΩ	1.1, 1.1	1.1	0.45, 0.5	0.5
47kΩ	3.2, 3.3	3.15	1.9, 2.1	2.0
68kΩ	4.3, 4.4	4.3	2.7, 3.0	2.9
100kΩ	6.2, 6.2	6.05	4.4, 4.8	5.0
150kΩ	8.9, 9.1	8.8	6.0, 6.5	6.2
220kΩ	11.8, 12.0	12.65	8.7, 9.5	9.1

Table 2. Apparent Zener voltages (see text) of a range of transistors in the circuit of Fig. 1 with R1 fixed at 68kΩ, and R2 fixed at 2.2kΩ or 10kΩ for germanium or silicon transistors

Type	- Description	Apparent Zener voltage
2N2926	nnp, silicon	4.4, 4.4
2N4059	npn, silicon	4.4, 4.5
2N4062	npn, silicon	4.3, 4.4
BC109	npn, silicon	4.4, 4.5
BC168	npn, silicon	4.5, 4.6
BC258	npn, silicon	4.3, 4.4
OC44	npn, germanium	2.7, 2.9
OC71	npn, germanium	3.2, 3.3
OC81	npn, germanium	2.8, 3.0

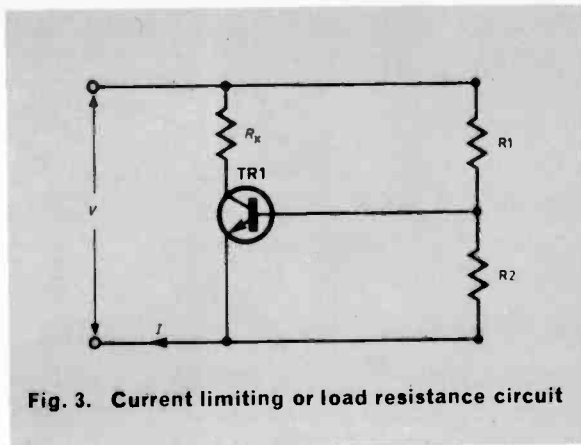


Fig. 3. Current limiting or load resistance circuit

Because of the two base-emitter junctions the Zener voltage is given approximately by $\frac{R1+R2}{5 \times R2}$ V and $\frac{R1+R2}{R2}$ for germanium and silicon transistors respectively, the value of R3 having little effect on this.

CIRCUIT VARIATIONS

Fig. 3 shows another variation of the basic circuit, the resultant circuit diagram being identical to that for the potential-divider biased common emitter amplifier stage. R_x here can serve two roles, either it can be a current-limiting device or it can be a load resistor or circuit.

In the first case the behaviour of the circuit, in terms of both the Zener voltage and the dynamic resistance, will be very little affected if R_x is less than $\frac{R1}{\beta}$. If R_x is greater than $\frac{R1}{\beta}$, then, as I increases,

R_x will take an increasing fraction of the voltage applied to the circuit and will limit the potentially damaging rapid initial increase in I and will thus serve to protect the device without increasing the initial dynamic resistance, as would be the case when a resistor is connected in series with a Zener diode.

Instead of being a current-limiting resistor, R_x may represent a component or circuit to which one wants to supply voltage in a controlled way.

If R_x is large compared to $\frac{R1}{\beta}$, then, almost as soon as the transistor starts to conduct, the whole of V is dropped across R_x , little power being dissipated at TR1, and thus this circuit could, for instance, be used instead of a thyristor in controlling the power supplied to a circuit, when V might be the output of a transformer-rectifier bridge network.

IMPORTANT DIFFERENCES

Two important differences between the functioning of this circuit and a thyristor are that this circuit switches at a point determined by the value of V rather than by a phase shift network, thus making its operation essentially frequency independent, and, that the current through this circuit does not have

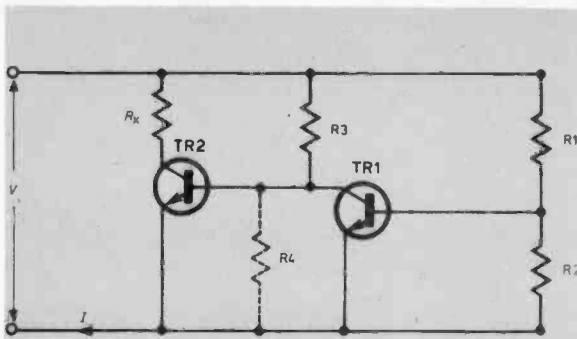


Fig. 4. Negative resistance circuit

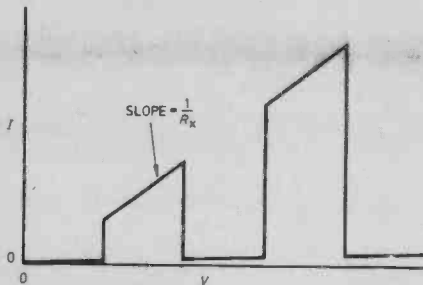


Fig. 5. Connecting a number of the elements of Fig. 4 in series can give a voltage/current relationship of this form

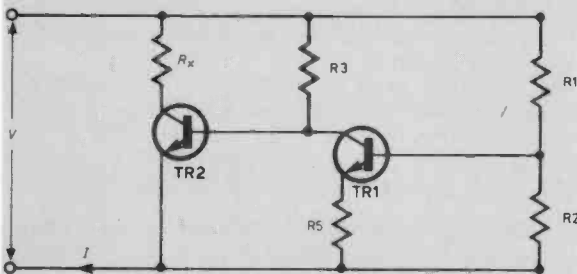


Fig. 6. An improved negative resistance circuit

to be reduced to zero for the device to revert to the off state, reduction of V below the critical value being sufficient.

NEGATIVE RESISTANCE CIRCUITS

It is a simple matter to use the circuit of Fig. 1 to achieve effectively the reverse of the function which the circuit performs. Thus, the circuit of Fig. 4 conducts current well up to a certain voltage—which

is approximately equal to $\frac{R_1+R_2}{10 \times R_2}$ and $\frac{R_1+R_2}{2 \times R_2}$ for

germanium and silicon transistors respectively, at which the current through R_x decreases over a fairly narrow voltage range to almost zero and stays very low while V increases further.

I , the total current entering the circuit, behaves in a similar way though it never decreases to quite such a low value and also, as one increases V , starts to increase again slowly after the rapid decrease.

If one also includes a resistor R_4 , as shown dotted in Fig. 4, then the circuit possesses both a switch-on voltage, determined by R_3 and R_4 , as well as a switch-off voltage, determined by R_1 and R_2 . Indeed (although the author can at present think of no practical reason for doing so) one can connect a number of these stages together, six being so far the maximum number attempted by the author, in such a way that, as the voltage applied is progressively increased, current through R_x is alternately switched on and off, yielding current/voltage characteristics of the type shown in Fig. 5.

If one considers the functioning of the circuit shown in Fig. 4, it is clear that, in the voltage range over which I is reduced from a high to a low value, the circuit possesses negative resistance characteristics, I decreasing while V is increasing. To be useful in practice, however, as a negative resistance device, a much wider range for the "negative resistance" is highly desirable.

ALTERNATIVES

To achieve this, several alternatives have been investigated. Firstly, by virtue of the fact noted at the end of the introductory section, germanium transistors perform the switching-off over a much wider range of values of V than a comparable silicon transistor.

Secondly, one can extend the negative resistance range by using a larger value for R_1 and/or a TR1 with a lower β ; in doing so, however, one must ensure that the effective resistance of TR1 can attain a low enough value to switch off TR2.

Thirdly, one can incorporate an extra resistor R_5 as shown in Fig. 6, of such a value (of the order of $10k\Omega$) that, whilst allowing the switch-on of TR1 to switch off TR2, V_{be} for TR1 increases relatively slowly with V because of the voltage across R_5 accompanying the collector current flowing through TR1. In this last case, it is of interest to note that the circuit will again revert to a low conductance state when V is increased to a sufficiently high value, determined, assuming the effective resistance of TR1 is then very much less than R_5 , by the relative values of R_5 and R_3 .



everyday electronics

INEXPENSIVE, EASY TO BUILD PROJECTS

- ★ INTRUDER ALARM
- ★ F.E.T. VOLTMETER
- ★ WHITE NOISE GENERATOR

PLUS

ALL OUR REGULAR FEATURES
ALL IN THE AUGUST ISSUE—
ORDER YOUR COPY NOW!

NEXT MONTH...

**FREE ENTRY
COMPETITION**

OVER £500 IN PRIZES TO BE WON!!

One of Britain's largest electronics companies joins forces with Practical Electronics to launch this novel thought-stimulating competition.

This is an opportunity for all our readers to show how resourceful they are in suggesting further practical applications for a specified circuit.

Full details and entry coupon will appear in the September issue. Remember *your* idea could win you a Big Cash Prize. And there are many valuable consolation prizes, also, to be won!



TIME LAPSE PHOTOGRAPHY

SEE NATURE AT WORK— Capture, on film, the growth of plants and many other slow moving phenomena.

A time lapse controller designed to provide a reliable method of operating a camera at preset intervals.

- # Interval time continuously variable from 10 sec. to 48 min.
- # Automatic switching of photoflood light (up to 1kW).

DIGITAL I.C. TESTER Allows rapid-checking of RTL, DTL and TTL chips.

PRACTICAL

ELECTRONICS

SEPTEMBER ISSUE ON SALE MID-AUGUST, 1975—PRICE 30p

PLACE A FIRM ORDER WITH YOUR NEWSAGENT TO AVOID DISAPPOINTMENT

8 CHANNEL LOGIC TRACE MULTIPLIER

By A.C. Ainslie

DURING the design of logic systems of any complexity a timing or sequence diagram is usually drawn to show the order in which operations or sequences start and finish in relation to one another. Should any difficulties arise in the development or testing stage, as they invariably do, it is very useful to display part or all of the timing diagram on an oscilloscope in order that the trouble may be traced.

Most scopes nowadays are double beam, with a few models having provision for a 4-channel plug-in. The design to be described enables up to eight logic channels to be displayed on a single beam oscilloscope. Dual trace scopes, therefore, will be able to display a single analogue signal (perhaps the output of a transducer feeding the logic) as well as a maximum of eight channels of logic.

The eight channels are obtained by a system of multiplexing and are in the correct timing relationship as viewed on the scope. The unit is capable of displaying two, four or eight channels and each channel gives a loading to the circuit under test of one TTL load.

In some systems a timing pulse may be very short (as little as 10ns or 20ns) in relation to the operating cycle which may be several seconds for an industrial control application. Clearly the short timing pulse would not show as it is so narrow. The unit therefore incorporates a "stretch" circuit so that the position of the timing pulse can be made visible in relation to the rest of the display. Provision has to be made to trigger the stretch circuit from both positive and negative going pulses.

SPECIFICATION . . .

Input Signals

One standard TTL load (i.e. logic 1 is between 2.4V to 5V, logic 0 is between 0V and 0.8V). A signal at logic 1 must supply a current of 40 μ A, and at logic 0 must be able to sink 1.6mA, whilst preserving the aforesaid voltages). There is also capacitive loading due to the connecting cable which should be as short as possible in high speed systems.

Frequency Response

Bit rates from d.c. to 5MHz.

Pulse Stretch

Will detect a pulse of 15ns and stretch to a length of between 2 μ s and 50ms in 3 ranges (Channel 8 only).

Mode

Chop or Alternate 2, 4 or 8 traces.

Chop Rate

Approximately 250kHz.

Trigger Section


The switch selects one of the 8 inputs for transfer to the Trig O/P socket.

Scope Timebase Gate Input

Handles a signal of from 2V to 50V pk, positive during scan.

Bright Up Output

15V pulse positive to cut-off trace. Output impedance <1k Ω .

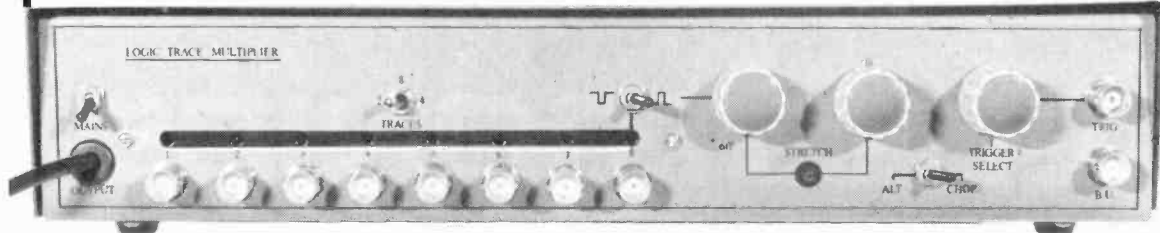

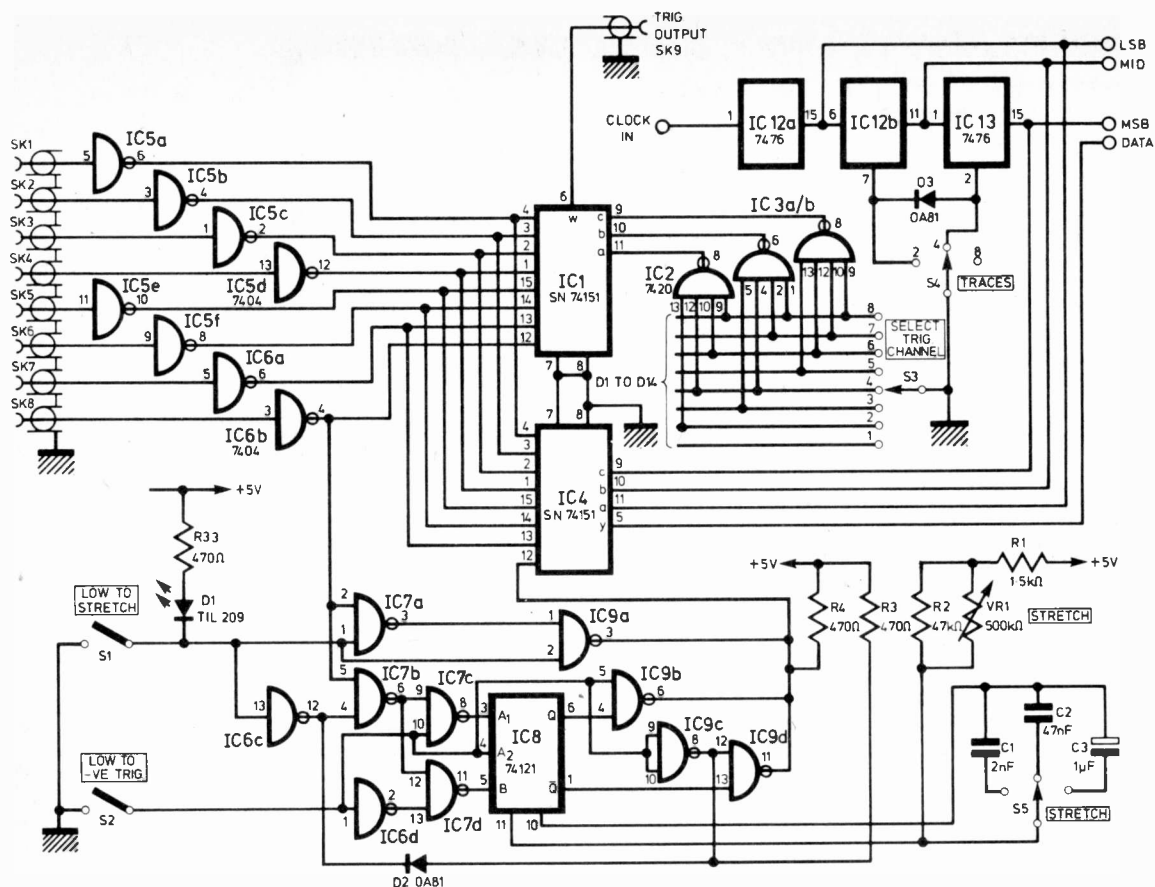


Fig. 1. Main circuitry of the trace multiplier showing the input multiplexing and trace stretching sections

In order for the display to be satisfactory at high sweep speeds and not show the multiplex action, the unit is capable of operating in the alternate or ALT mode, which means that, as in a conventional scope trace multiplier, each sweep is made of one input and the source change occurs during flyback. In the chopped or CHOP mode the unit sequentially samples each input as fast as is reasonably possible so that during a single sweep a complete multi-trace picture is built up.

In order that any switching transients may be blocked out a Bright Up output is available to drive the oscilloscope tube Z axis.

CIRCUIT DESCRIPTION

Fig. 1 shows the main circuitry for the input multiplexing and the stretch function.

IC5a to IC5f and IC6a and IC6b are input buffers to isolate the rest of the electronics from the unit under test.

IC1 and IC4 are identical 74151 data selectors/multiplexers. These pass to the output the signal input which is addressed on pins 9, 10 and 11 in binary.

IC1 selects the signal to be made available for triggering the scope timebase. It is convenient to use an 8-way switch for the selection at the front panel and so the switch position has to be coded to binary by IC2 and IC3, a total of three, 4-input NAND gates in two 7420 packages. The W output of the 74151 is inverting with respect to the input

but as each input is preceded by an inverter the output is in the same sense as the input selected by S3.

The W output of IC1 is made available at SK9 on the front panel to trigger the scope timebase, as internal triggering is obviously not feasible in this application.

PULSE STRETCHER

The output of IC6b is fed to IC7a and IC7b. When S1 is open IC7a and IC9a are enabled and the output from IC6b is fed directly to pin 12 of IC4, the multiplex chip.

When S1 is closed, however, IC7a and IC9a are no longer enabled and the signal passes through IC7b. According to whether S2 is open or closed the signal is passed to pins 3 or 5 of IC8, a 74121 monostable. Pin 3 is the "A" input and triggers the monostable when it goes negative; pin 5 is the "B" input which triggers when it goes positive.

To use the B input either pin 3 or pin 4 (the A₁ input) has to be low, and to use the A₁ input pin 4 must be high. This is achieved by coupling pin 4 to switch S2.

By changing S2 the monostable can be made to trigger from positive or negative pulse edges. To ensure that the output of the pulse stretch section is in the correct sense with respect to the pulse edge which triggered the monostable, S2 also switches gates IC9b and IC9d to pass either the Q or Q̄ output of the monostable respectively.

D1 is included to ensure that when S1 is open IC9d is not enabled. In the quiescent state the Q output of the monostable is also low so that only IC9a is enabled as is required.

To summarise, closing S1 passes the signal through the pulse stretch electronics. The l.e.d. D1 shows when the pulse stretch is in use.

With S2 open the signal is passed to the A₁ input of the monostable and the Q output is selected. With S2 closed the signal triggers the B input and the Q output is selected.


The signal at the output node of IC9a, IC9b and IC9d passes to pin 12 (input selected by address '111) of IC4.

In order to strobe through all the inputs the addresses to IC4 increase sequentially from 000 through 001, etc. up to 111 and then recycle. This is achieved very simply by the two timing counters, IC12b and IC13, both 7476 devices. IC12a serves to produce a true square wave drive for IC12b. The input to IC12b is also the Least Significant Bit (LSB) of the multiplex address and so must be symmetrical, otherwise alternate inputs will be strobed for a longer time—giving unequal trace brightness.

By setting the "Preset" of IC13 to ground the output will go high and so inputs 5, 6, 7 and 8 only will be strobed. Grounding the preset of IC12b (and also of IC13 through diode D3) sends both the Most Significant Bit (MSB) and the MID address bits high, so that only channels 7 and 8 are displayed. Channel 8, with the pulse stretch facility, is displayed in all of the 8-channel, 4-channel and 2-channel display modes.

CLOCK

Fig. 2 shows the clock which drives IC12a input. IC10 is an NE555 timer running at its maximum PRF of about 250kHz. C4 is required to keep supply spikes to a minimum.

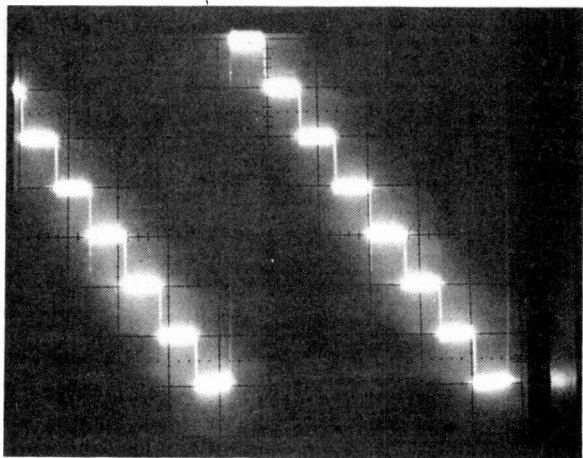

The output of the D/A displayed as a staircase without the bright-up connection being made

In the "CHOP" mode S6 is open and so IC11c is enabled, passing the 250kHz clock pulses through to IC11d and so to IC12a.

With S6 closed IC11b is enabled. The input to IC11b is from the emitter follower TR1. The positive gate signal (high during scan, low during flyback) from the CRO is applied to the base via R9 and C7. The input is at a fairly high impedance and so is compatible with most scopes—the only snag is that with a very high input (say, over 100V) the emitter of TR1 could pass spikes in excess of the 5V maximum that would normally occur with TR1 saturated. To remedy this and so avoid damaging IC11 a 4-7V Zener could be connected across R8. However with most transistor scopes this precaution would not be needed.

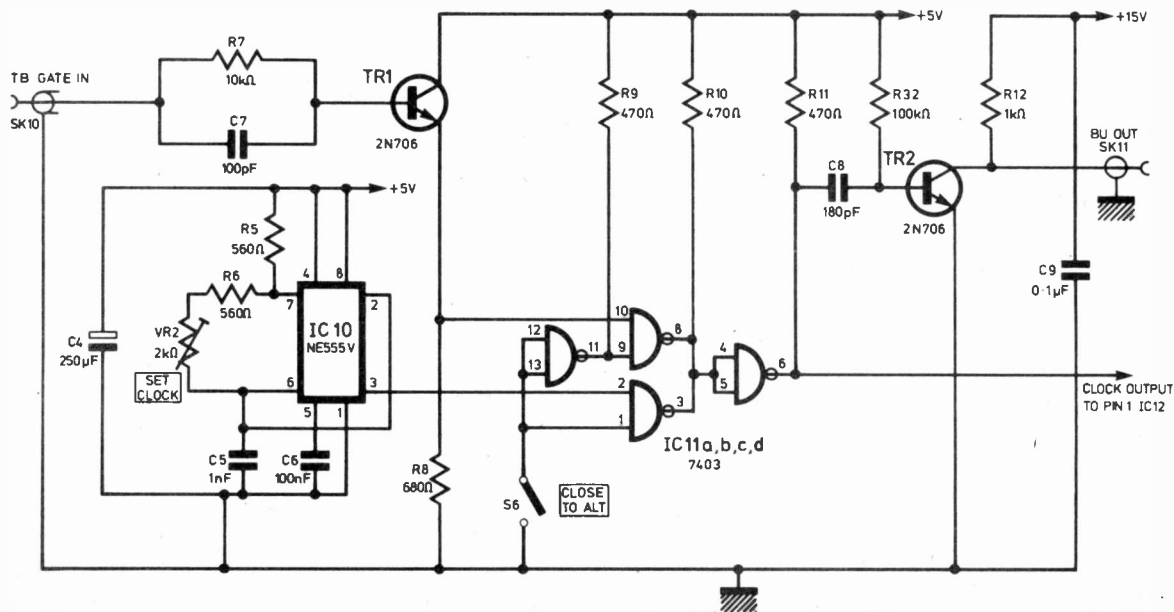


Fig. 2. The clock circuitry with input and output circuitry

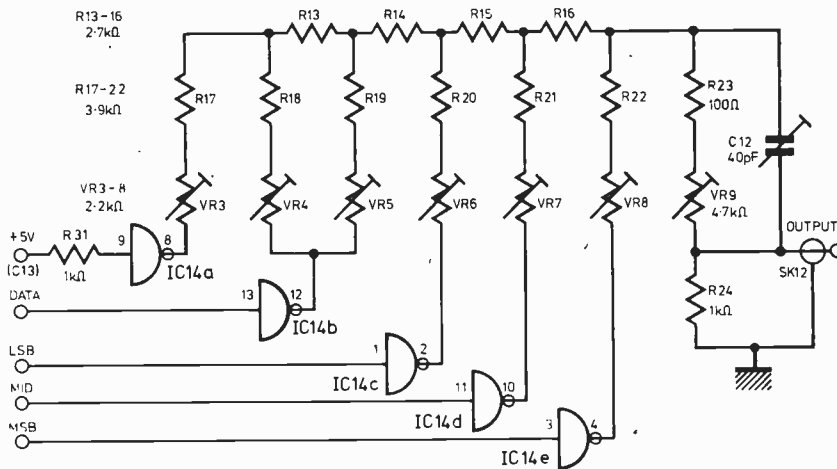


Fig. 3. The D-to-A converter circuitry which uses algebraic addition to achieve the staircase waveform

IC12a output changes in this mode once per sweep (at the end of the sweep) and so the scope sequentially displays one scan of input 1 and then one scan of input 2, etc. This mode can only be used on fairly fast speeds otherwise flicker may prove troublesome.

DIGITAL/ANALOGUE CONVERTER

So far we have only considered how the inputs are scanned and not how the eight traces are separated vertically.

Fig. 3 shows how by weighting the three address lines in proportion to their significance, and performing an algebraic addition we obtain a staircase. This is precisely what is needed for our application to give eight distinctly separated traces.

There are several ways of adding signals, the most common being in an operational amplifier. However, speed limitations exist which reduce the scope of the instrument even with expensive op-amps. The alternative method used in analogue-to-digital (A/D) and D/A converters is the "ladder network" as shown in Fig. 4. Here a 2-bit ladder is shown which gives four output levels according to the binary input. Consideration of Thevenin's theorem will confirm that in all cases the impedance "looking back" into the ladder is always R and that the outputs are as shown for the various binary codes applied.

This idea is easily extended to a 3-bit ladder to give an 8-step staircase. By adding two LSB's driven by the output from IC4 we can display eight traces one unit apart with the data having a height of 0.75 units. This leaves 0.25 units of space between adjacent traces. The whole display fits very nicely onto an 8cm × 10cm CRT.

DIGITAL/ANALOGUE CONVERSION

Fig. 3 shows the full circuit of the D/A converter. The ladder elements are easily distinguished. The ladder is driven directly from the outputs of the inverters in IC14. The gates have non-ideal switching characteristics with a high output of about 4V at 75Ω and a low output of 0.2V at 12Ω. In order that this variation of switch "resistance" does not upset

the ladder, the ladder impedance is almost 3kΩ, high compared to the 60Ω variation in switch "resistance".

The inverters are used to drive the ladder to provide isolation and to convert the binary code from a count up to a count down, so that trace 1 is displayed at the top of the display (highest D/A output) and trace 8 is displayed at the bottom (lowest D/A output).

The 0V end of the ladder is fed from the output of an inverter, whose input is held high, to avoid linearity difficulties that could arise if this point was taken direct to ground. This means that the actual analogue output is slightly offset from ground, but this is easily compensated by the oscilloscope shift controls.


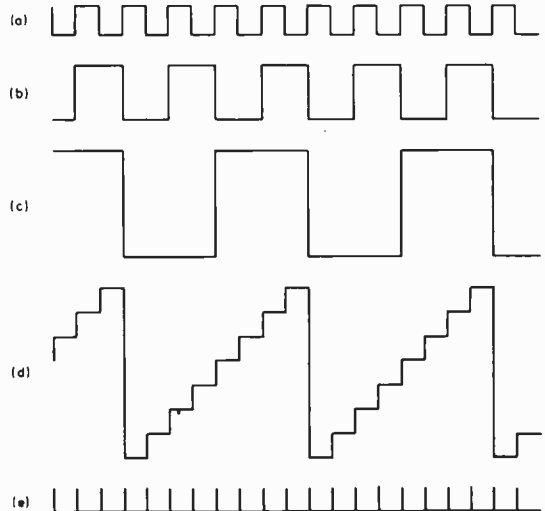


Fig. 4. Waveforms used in the D/A converter. (a) is the LSB, (b) the MID, (c) the MSB, (d) the output staircase which is an analogue output produced by adding the three binary weighted clock rates. (e) is the bright-up output

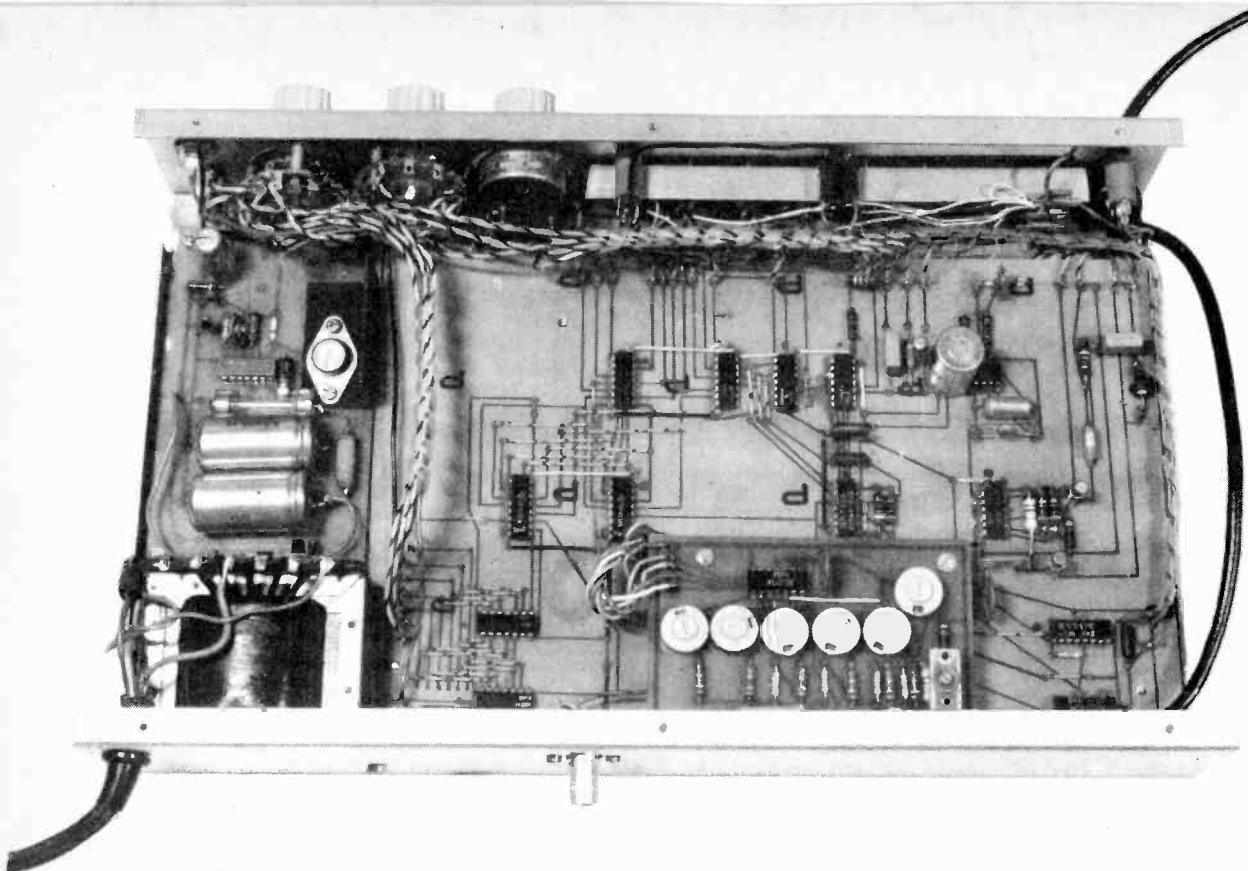

COMPONENTS . . .

Resistors

R1	1.5k Ω	R18	3.9k Ω
R2	47k Ω	R19	3.9k Ω
R3	470 Ω	R20	3.9k Ω
R4	470 Ω	R21	3.9k Ω
R5	560 Ω	R22	3.9k Ω
R6	560 Ω	R23	100 Ω
R7	10k Ω	R24	1k Ω
R8	680 Ω	R25	1 Ω
R9	470 Ω	R26	4.7 Ω 2W
R10	470 Ω	R27	100 Ω
R11	470 Ω	R28	4.7k Ω
R12	1k Ω	R29	2.2k Ω
R13	2.7k Ω	R30	1.0 Ω
R14	2.7k Ω	R31	1k Ω
R15	2.7k Ω	R32	100k Ω
R16	2.7k Ω	R33	470 Ω
R17	3.9k Ω		

All $\frac{1}{2}$ W, 5% unless stated

Potentiometers

VR1	500k Ω log. ganged to S1
VR2	2k Ω skeleton preset
VR3-VR8	2.2k Ω preset, 6 off
VR9, VR10	4.7k Ω skeleton preset, 2 off

Capacitors

C1	2nF	C11	0.1 μ F
C2	47nF	C12	40pF trimmer
C3	1 μ F	C13	0.1 μ F
C4	250 μ F elect. 6V	C14	100 μ F
C5	1nF	C15	1,000 μ F elect. 25V
C6	0.1 μ F	C16	1,000 μ F elect. 25V
C7	100pF	C17	100pF
C8	180pF	C18	10 μ F
C9	0.1 μ F	C19	220 μ F elect. 16V
C10	0.1 μ F	C20	10 μ F
		C21	100 μ F, 6V

All 5V working or greater unless stated

Semiconductors

IC1	74151	TR1	2N706
IC2	7420	TR2	2N706
IC3	7420	TR3	2N3054
IC4	74151		
IC5	7404	D1	TIL 209 or any general purpose i.e.d.
IC6	7404	D2	OA81
IC7	7403	D3	OA81
IC8	74121	D4	1N4001
IC9	7403	D5	1N4001
IC10	NE555V	D6	5.1V 400mW Zener
IC11	7403		
IC12	7476		
IC13	7476		
IC14	7404		
IC15	μ A723C		

Switches

S1	Single pole ganged with VR1		
S2	SPST	S5	1-pole 3-way
S3	1-pole 8-way	S6	SPST
S4	1-pole 3-way	S7	DPST mains on-off

Miscellaneous

T1 Mains transformer. 12V-0-12 @ 0.5A sec.
 D7 to D14 These are required if it is desired to indicate the trigger channel selected. Any general purpose i.e.d.s will suffice
 SK1 to SK12 BNC 50 chassis mounting sockets. SK12 may be replaced with 1m of cable terminated in a b.n.c. plug to reduce ground line noise pick-up (see text)
 FS1 250mA
 FS2 500mA fuse (1 $\frac{1}{2}$ in)
 Printed circuit board, TR3 heatsink, cabinet, wire and cable connecting leads, knobs, mains neon indicator, etc.

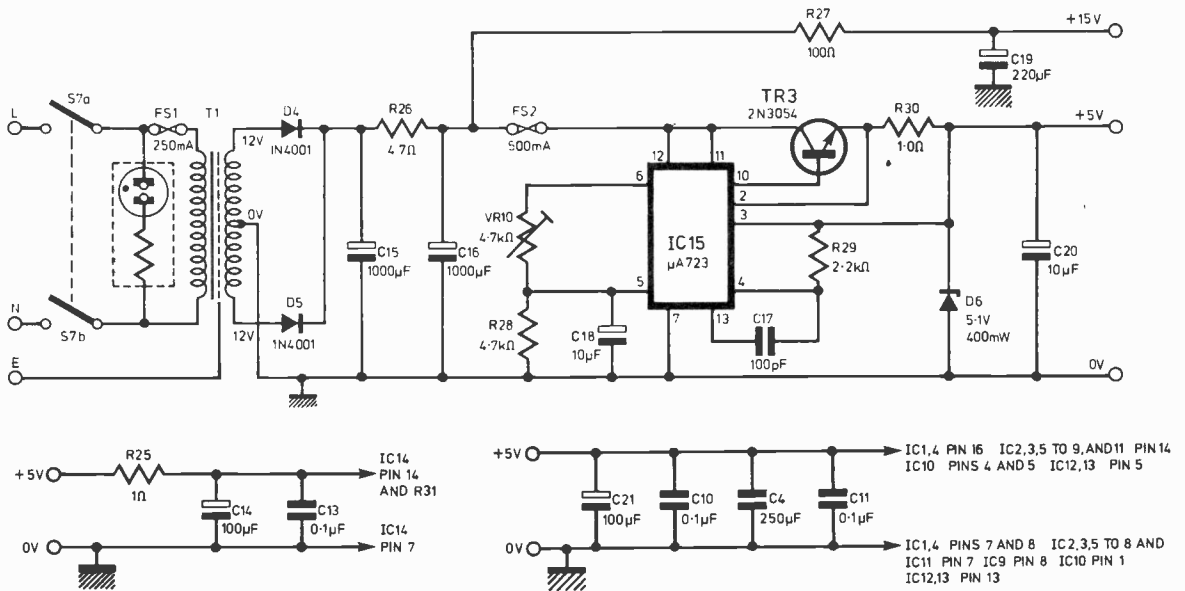


Fig. 5. Complete power supply circuit together with added smoothing for IC 14 and power bus to i.c.s.

The ladder output is at a fairly high impedance and is susceptible to waveform distortion by capacitance loading. To minimise this effect the output cable is fed from the potential divider VR9/R23. C12 provides high frequency compensation to trim up the leading and falling edges of the display.

Various switching transients on the supply lines can appear as a signal on the output of the D/A converter. To eliminate this disturbing effect the supply rail is well decoupled. The output lead braid must be grounded only at the point next to the D/A converter output to avoid picking up spikes on the ground line.

BRIGHT UP

At high speeds the transition times of the D/A converter can be quite significant and lead to an overall blurring of the display. The D/A steps occur on the falling edge of each clock pulse. TR2 is normally near saturation (V_{ce} about 1V) but the falling edge of the clock, applied through C8 (Fig. 2), cuts off the transistor momentarily. Thus the collector of TR2 has a series of +15V spikes, each coincident with a D/A step as shown in Fig. 4.

Applying these pulses to the cathode of the display CRT cuts off the trace for the duration of the transition and the short ringing period following. If a very high gain transistor is used in TR2 position it may saturate and so will not switch very fast. This can be remedied by increasing R23 a little, a quiescent collector voltage of about 1V or 2V should be aimed for. Should R23 need increasing, C8 may be reduced to keep the width of the spike at TR2 to about 10% of the clock period.

POWER SUPPLY


The power requirements for the instrument are a modest 5V at 500mA and 15V at 15mA.

Mains transformer T1 (Fig. 5) output is full wave rectified and smoothed. R26 and C19 provide additional decoupling for the nominal 15V supply.

The regulated 5V output is provided by IC15, a μ A 723, which feeds the emitter follower TR3. A portion of the 7V reference on pin 6 of the IC is fed to pin 5, the non inverting input, where it is compared with the output from TR3, which is fed to pin 4 via a 2.2k Ω resistor for thermal stability. C17 provides high frequency compensation to prevent oscillation or ringing with transient load changes.

Overcurrent protection is achieved by monitoring the voltage drop across R30, a 1.0 Ω . When the potential across pins 2 and 3 exceeds 0.6V the regulator shuts down. This corresponds to a current of $0.6 \div 1.0 = 600$ mA. Should the output exceed 5V, say, because of failure of TR3, then FS2 will blow as D6 will pass a heavy current.

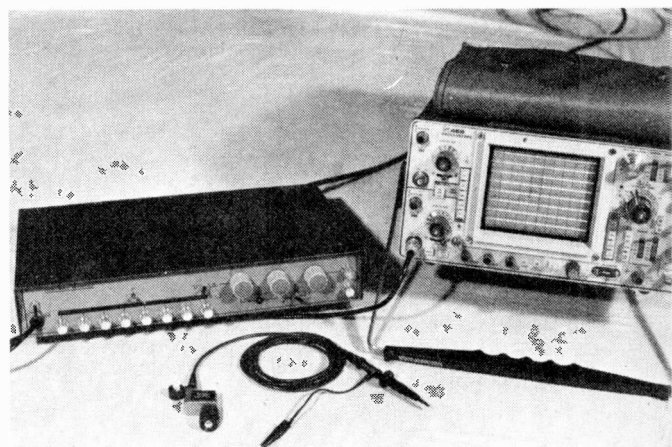Next Month: Full constructional details and setting-up.



INGENUITY UNLIMITED



A selection of readers' suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. Any idea published will be awarded payment according to its merits. Why not submit YOUR IDEA?

A VERSATILE FLASHER/PULSER

A SIMPLE circuit suitable for a lamp flasher, alarm pulser, or time pulse generator, is shown in Fig. 1. Transistors TR1, TR2 and timing network C and R, form a multivibrator circuit in which both transistors are turned on whilst capacitor C charges and turned off when C discharges. Resistors R1 and R2 provide just sufficient bias for TR1, to make the circuit self-starting when C is fully discharged. The circuit behaves as a free running astable multivibrator, and the on and off time periods may be made almost identical by choosing a suitable value for R1. This circuit differs from the more conventional astable multivibrator circuit by having only one CR timing network,

the single potentiometer allowing adjustment of both periods simultaneously over a wide range. Frequencies between 10kHz and 0.002Hz may be generated using values of C between 1,000pF and 1,000 μ F.

Reliable operation of this circuit can be obtained with supply voltages from five to fifteen volts.

Transistor TR3 is a medium power driver stage, controlling a lamp, i.e.d., buzzer, bleeper, etc. However, a collector load resistor may be connected to TR3 to produce a low output impedance pulse generator. If mains voltage lamps or equipment are to be controlled using this circuit, then TR3 may be connected to operate a relay or trigger a triac.

R. A. Smith,
Kempston,
Bedford.

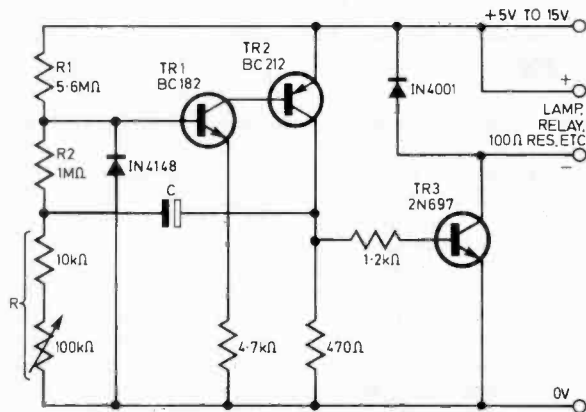


Fig. 1

COIN TOSSER

THE circuit illustrated was built as an electronic "coin toss" binary decision maker. With S1 depressed IC1 functions as an astable multivibrator with an equal mark-space ratio, and the i.e.d. flickers rapidly, the actual rate depending on the value of C2 and VR1.

When S1 is released the circuit stops with the output either on or off depending on its state at the actual instant of release, the connection of the output to the input + through S1 assisting to maintain the stable state.

D1 and D2 are necessary to prevent a small residual glow in the i.e.d. in its "off" state, caused by the inability of the 741's output to swing closer than within a volt of either supply rail. The forward voltage drop of the diodes overcomes this problem.

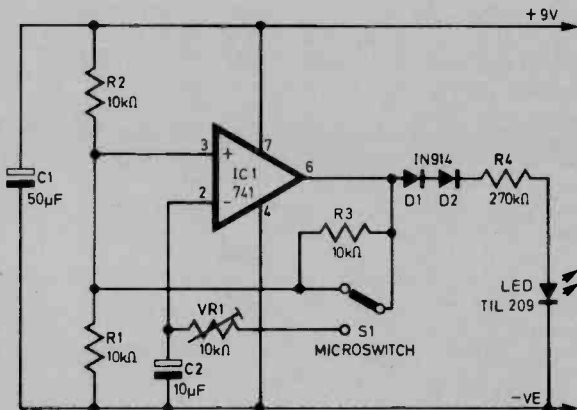


Fig. 1

The circuit may be used as a random decision maker, or ESP enthusiasts can try to influence a series of results.

A. J. Flind,
Taunton,
Somerset.

We don't miss anything out, so you won't miss out.

Our 1214 Series stereo equipment comes to you in kit form. And, as you would expect, coming from Heathkit, they are absolutely complete kits. With nothing left out.

So you'll have all you need to build our superb AR-1214 stereo receiver. Or, if you'd prefer, a separate amplifier and tuner (the A A-1214 and AJ-1214).

The easy to understand instruction manual you'll get makes assembly beautifully straightforward.

And very enjoyable.



And the high performance of the 1214 Series means you won't miss out on listening pleasure in any way either.

From the stereo receiver, or separate amplifier, you'll get 15 watts r.m.s. a channel, with reproduction so good it makes many ready-made systems really sit up and listen.

For full details of the 1214 Series, the rest of our audio range, including speakers, and our many other kits, just post the coupon now for your free Heathkit catalogue.

Or call in at the London Heathkit Centre, 233 Tottenham Court Road.

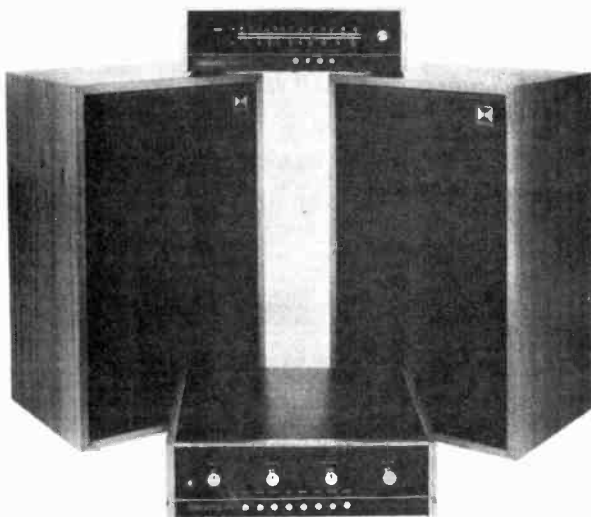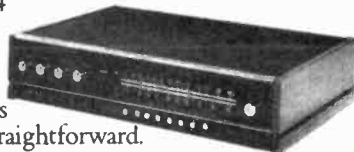Heath (Gloucester) Ltd., Dept. PE-85, Bristol Road, Gloucester GL2 6EE. Tel: (0452) 29451.



To: Heath (Gloucester) Limited, Dept. PE-85, Gloucester, GL2 6EE.
Please send me my free Heathkit catalogue.



Name _____
Address _____

Postcode _____

HEATH
Schlumberger

Remember easy terms are available with the Heathkit Monthly Budget Plan.

Soldering and de-soldering the professional way.

Until now, the soldering equipment shown here was only available to professionals. For the first time this top-quality equipment is being offered to you – now you too can get professional results!

Oryx 50 soldering iron.

A temperature controlled mains soldering iron. Adjustable between 200°-400°C while iron is operating, using same tip. Light, compact, and easy to handle. Rapid heating, and high performance. Yours for only

£6.95 (inc. VAT and p.p.)


Oryx SR3A desoldering tool.

Instantly removes unwanted solder from printed circuit boards, etc. Accurate, reliable, speedy, and safe. Yours for only

£6.30 (inc. VAT and p.p.)

Special price for both.

£12.50 (inc. VAT and p.p.)

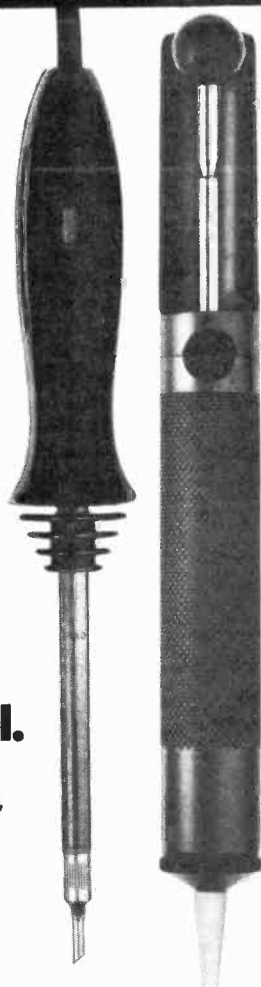

To: Greenwood Electronics, Portman Road, Reading RG3 1NE.
Please send me Oryx SR3A desoldering tool
Oryx 50 soldering iron Both (tick which applies).

I enclose cheque/P.O. to value _____

Name _____


Address _____

Greenwood Electronics

ALL OUR PRICES INCLUDE V.A.T.

BSR HI-FI AUTOCHANGER STEREO AND MONO

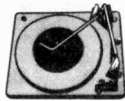Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. A.C. 200/250V Size 13 1/2 x 11 1/2. Above motor board 3 1/2in. Below motor board 2 1/2in.



with STEREO and MONO CARTRIDGE £9.25 Post 75p

PORTABLE PLAYER CABINET

Modern design. Resins covered. Vynair front grille. Chrome fittings. Size 17 x 15 x 8in approx. £5.25 Post 75p Motor board cut for BSR or Garrard deck.

COMPLETE STEREO HI-FI SYSTEM

Two full size loudspeakers 13 1/2 x 10 x 3 1/2in. Player unit clips to loudspeakers making it extremely compact. Overall size only 13 1/2 x 10 x 8 1/2in. 3 watts per channel, plays all records 33 r.p.m., 45 r.p.m. Separate volume and tone controls 240V a.c. mains.



Bargain Price £29

Attractive Teak finish £1 carriage

SPECIAL OFFER! SMITH'S CLOCKWORK 15 AMP TIME SWITCH

0-60 MINUTES £2.50 Post 35p. Single pole two-way. Surface mounting with fixing screws. Will replace existing wall switch to give light for anti-burglar home, garage, automatic return-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Brand new and fully guaranteed.



TEAKWOOD LOUDSPEAKER GRILLES will easily fit to Motor board. Size 18 1/2 x 10 1/2in—75p. 10 1/2 x 7 1/2in—45p

WEYRAD P50 — TRANSISTOR COILS

RA2W Ferrite Aerial 85p Driver Trans. LFDT4...65p Printed Circuit, PCA1...65p J.B. Tuning Gang...£1.20 Weyrad Booklet...10p P50/YAC...60p Mullard Ferrite Rod 8 x 1/2in., 20p. 8 x 1/2in., 20p. 3 x 1/2in. 10p

VOLUME CONTROLS

5kΩ to 2MΩ. LOG or LIN. L/S 20p. D.P. 35p. STEREO L/S 55p. D.P. 75p. Edge 3k. S.P. Transistor 25p

80 Ohm Coax 5p yd.

BRITISH AERIALITE AERIAL-AIR SPACED 40 yd. £2.80 yd. £3 FRINGE LOW LOSS Ideal 625 and colour 10p yd

8in. or 10 x 6in. ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50-18,000 c/s. Bass resonance 55 c/s, 8 ohm impedance. 10 watts, music power. £4.35 Post 35p.



E.M.I. 13 1/2 x 8in. SPEAKER SALE!

With tweeter and crossover. 10 watt. State 3, 4 or 15 ohm. £5.25 Post 35p As Illustrated.




With fibred tweeter cone and ceramic magnet. 10 watt. Bass res. 45-60 c/s. Flux 10,000 gauss. State 3 or 8 or 15 ohm. Post 35p

Bookshelf Cabinet

Teak finish 16 x 10 x 7 1/2in. 13 1/2 x 8in. Bass Woofer. 20 watts, £6.30 £7.60 Post 75p

THE "INSTANT" BULK TAP ERASER AND HEAD DEMAGNETISER

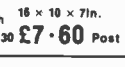Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/250V. Leaflet S.A.E. £4.35 Post 30p



BLANK ALUMINIUM CHASSIS. 18 a.w.g. 2 1/2in. sides 6 x 4in 45p; 8 x 6in 50p; 10 x 7in 65p; 12 x 8in 85p; 14 x 9in 90p; 16 x 6in 90p; 12 x 3in 50p; 16 x 10in £1.

ALUMINIUM PANELS 18 a.w.g. 6 x 4in 12p; 8 x 8in 18p; 14 x 3in 20p; 10 x 7in 24p; 12 x 5in 25p; 12 x 8in 34p; 16 x 3in 34p; 14 x 9in 40p; 12 x 12in 47p; 16 x 10in 60p.

ELAC 9 x 5in HI-FI SPEAKER TYPE 59RM

This famous unit now available, 10 watt, 8 ohm. £3.45 Post 35p

QUALITY LOUDSPEAKER ENCLOSURE

Teak veneered 3/4in thick wood cabinet. Size 18 1/2 x 18 1/2 x 8 1/2in. Weight 23lbs. This cabinet features a wide mesh Silver Grill covering a separate compartment for mounting Tweeters or Mid-Range Horn. The fully sealed bass compartment is cut out for 6 1/2 inch Woofer. £8.50 Carr. 85p. Rosewood Veneer £9.50 Carr. 85p. Baffle could be cut to take larger speaker.



RCS POWER PACK KIT

12 VOLT, 750mA. Complete with printed circuit board and assembly instructions. £3.35 Post 30p 12 VOLT 300mA KIT, £3.15. 9 VOLT 1 AMP KIT, £3.35.

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER—BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12V or H.T. line 200-300V d.c. operation. Size: 1 1/2 x 1 1/2 x 1 1/2in. Response 25 c/s to 25 kc/s. 26 dB gain. For use with valve or transistor oscillator. Post Full Instructions supplied. Details S.A.E. £1.45 30p

ELECTRO MAGNETIC PENDULUM MECHANISM

1.5V a.c. operation over 300 hours continuous. SP2 battery, fully adjustable swing and speed. Ideal displays, teaching electro magnetism or for metronome, strobe, etc. 95p Post 25p

BRITISH FM/VHF TUNING HEART

88 to 108 M/Cs British made. 2 Transistors ready aligned requires 10-7 M/C I.F. Complete with tuning gang. Connections supplied but some technical experience essential.

Our price £3.95 Post 25p

10-7 M/Cs I.F. strip £4.85 DECODER £4.95

MAINS TRANSFORMERS

	ALL POST 50p each
250-0-250V 70mA, 6-3V, 2A	£2.90
250-0-250 80mA, 6-3V 3-5A, 6-3V 1A or 5V 2A	£4.00
350-0-350 60mA, 6-3V 3-5A, 6-3V 1A or 5V 2A	£5.00
300-0-300V 120mA, 6-3V 4A C.T., 18-3V 2A	£7.00
MINIATURE 200V 20mA, 6-3V 1A	£1.10
MIDGET 220V 45mA, 6-3V 2A	£1.25
HEATER TRANS. 6-3V 1 amp 85p, 3 amp	£1.40
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2 amp, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V £4.00	
1 amp, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 £4.00	
2 amp, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 £7.00	
3 amp, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 £8.70	
5 amp, 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 £11.25	
8-0V 500mA 90p, 9V 1 amp, 85p, 12V 300mA 75p, 12V 500mA 85p, 12V 750mA 95p, 10V, 30V, 40V, 2 amp £2.75, 20V, 3 amp, £2.45, 40V, 3 amp, £2.25, 22-0-22V, 4 amp, £3.45, 16V, 1 amp, 85p, 18V, 2 amp, £2.90, 0, 5, 8, 10, 16V, 1 amp £1.85, 20V, 1 amp £1.75, 20V, 1 1/2 amp, £2.20.	
AUTO TRANSFORMERS, 115V to 200V or 230V to 115V 150W £4.80; 500W £8.70; 750W £17.50; 1000W £21.	
BATTERY CHARGERS. Ready built with leads and clips 4 amp £4; 5 amp £4.50	
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12V outputs, 1 1/2 amp 40p; 2 amp 55p; 4 amp 85p.	

MAINS ISOLATING TRANSFORMER

Primary 0-110-240V. Secondary 0-240V 3A 720W insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. OUR Carr. Famous make. (Value £19). PRICE £13.50 95p Can be used as 800W auto transformers 240-110V. IDEAL FOR COLOUR T.V. OR GARDEN TOOLS.

NEW ELECTROLYTIC CONDENSERS

2/350V	20p	250/25V	20p	50 x 50/300V	50p
4/350V	20p	500/25V	25p	600/350V	85p
6/350V	20p	100 x 100/275V85p	32 x 32/250V	20p	20p
16/350V	35p	150 x 200/275V85p	32 x 32/450V	50p	60p
32/500V	60p	8 x 8/450V	35p	150 x 50/325V	85p
25/25V	15p	8 x 16/450V	35p	100 x 50/350V	85p
50/50V	15p	16 x 16/450V	60p	32 x 32 x 32/350V	85p
100/25V	15p	32 x 32/350V	80p	4700/83V	95p

LOW VOLTAGE ELECTROLYTICS

1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200µF 15V 10p. 500µF 12V 15p; 25V 20p; 50V 30p. 1000µF 12V 17p; 25V 35p; 50V 47p; 100V 70p. 2000µF 6V 25p; 25V 42p; 50V 57p. 2500µF 50V 82p; 3000µF 25V 47p; 35V 65p. 5000µF 6V 25p; 12V 42p; 25V 75p; 50V 85p; 50V 95p.

TRIMMERS 10pF, 30pF, 50pF, 5p, 100pF, 150pF, 15p. CERAMIC, 1pF to 0.01µF, 4p. Silver Mica 2 to 5000pF, 4p. PAPER 350V-0.1µF, 0.5-1µF; 1mF 150V 15p; 2mF 150V 15p. 500V-0.001 to 0.05µF; 0.1-1µF; 0.25-1µF; 0.4-7µF.

MICRO SWITCH LEVER ACTION 20p. SUB-MIN MICRO SWITCH 25p. Single pole change over. TWIN GANG, "0-0" 200pF + 176pF £1.20; 500pF standard 75p. 385pF + 385pF with 25pF + 25pF. Slow motion drive 50p.


SHORT WAVE SINGLE. 100pF, 30p, 25pF, 55p, 50pF, 55p. NEON PANEL INDICATORS 250V AC/DC. Amber 30p. RESISTORS 1/4W, 1W, 1W, 20% 2p; 2W, 10p; 10Ω to 10M.

HIGH STABILITY, 1/2W 2% 10 ohms to 6 meg., 10p. DITO 5%. Preferred values 10 ohms to 10 meg., 5p. WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K 12p each.

TAPE OSCILLATOR COIL Valve type 35p.

NEW MODEL "BAKER LOUSPEAKER", 12IN 50 WATT. GROUP 50/12, 8 OR 15 OHM HIGH POWER. £14.50 FULL RANGE PROFESSIONAL QUALITY. Post 60p

BAKER MAJOR 12" £11.50

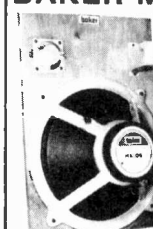

30-14,500 c/s, 12in. double cone, woofer and tweeter cone together with a 6AKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s. Rated 20W. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and wiring. Instructions. £14.50 Post 60p each Please state 3 or 8 or 15 ohms.

BAKER "BIG-SOUND" SPEAKERS Post 40p each

'Group 25'	'Group 35'	'Group 50/15'
12in. £8.80	12in. £10.50	15in. £19.50
25W	35W	50W
3 or 8 or 15 ohm	3 or 8 or 15 ohm	8 or 15 ohm

TEAK VENEERED HI-FI SPEAKER AND CABINETS For 12in or 10in dia. speaker 20 x 13 x 12in, £12.50 Post 75p For 13 x 8in or 8in speaker 16 x 10 x 7in, £7.60 Post 60p For 8 1/2in speaker 16 x 8 x 8in, £5.80 Post 40p LOUSPEAKER CABINET WADDING 18in wide, 20p ft.

GOODMANS 6 1/2in. HI-FI SPEAKER

4 ohm or 8 ohm, 10W. Large ceramic magnet. Special Cambric cone surround, Twin cone. Frequency response, 30-15,000 c/s. Ideal P.A. Columns. Hi-Fi Enclosure Systems, etc. £4.60



ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 c/s to 18,000 c/s. Size 3 1/2 x 2 1/2in deep. Rating 10W, 3 ohm. Crossover £1.80 £2.20, 1 post 20p

SPEAKER COVERING MATERIALS. Samples Large S.A.E.

Horn Tweeters 2-16kc/s, 10W 8 ohm or 15 ohm £3. De Luxe Horn Tweeter 2-16kc/s, 15W, 15 ohm £4.50 CROSSOVERS, TWO-WAY 3,000 c/s 3 or 8 or 15 ohm £1.60. LOUSPEAKERS P.M. 3 OHMS. 7 x 4in, £1.50; 6 1/2in, £1.60; 8 x 5in, £1.80; 8in, £2.20. SPECIAL OFFER: 60 x 2 1/2in, 2 1/2in, 35 ohm, 2 1/2in, 3 1/2in, 25 ohm, 2 1/2in, dia., 3 1/2in, dia., 8 ohm, 2 1/2in, 3 1/2in, 15 ohm, 3 1/2in, dia., 6 1/2in, 7 1/2in, 8 1/2in, 3 ohm, 2 1/2in, 3 1/2in, 5in, dia. £1.25 each RICHARD ALLAN TWIN CONE LOUSPEAKERS, 8in. diameter 4W £2.50, 10in. diameter SW £2.95; 12in. diameter EW £3.50, 3/8" 1/8" ohms, please state. VALVE OUTPUT TRANS. 40p; MIKE TRANS. 50:1 40p. Mike trans. mu metal 100:1 £1.25. Loudspeaker Volume Control 15 ohms 10W with one inch long threaded bush for wood panel mounting, 1/2in spindle. 65p each, Post 15p.

MAJOR 100 WATT ALL PURPOSE AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 8 1/2 ohm, a.c. Mains. Separate treble and bass controls. Guaranteed. Details SAE. NEW MODEL MAJOR—50 watt, 4 input, 2 vol. £49.95



BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER.

Add musical highlights and sound effects to recording. Will mix Microphones, records, tape and tuner with separate controls into single output. 8V. TWO STEREO CHANNELS VERSION £6.85

BARGAIN 3 WATT AMPLIFIER. 4 Transistor

Push-Pull Ready Built, with volume, Treble and bass controls. 16 volt d.c. Mains Power Pack £3.45

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 10p.


OUTLET BOXES, SURFACE 40p. FLUO 85p. TWIN 85p. BALANCED TWIN RIBBON FEEDER 30 ohms, 7p. JACK SOCKET 8td. open-circuit 18p, closed circuit 23p; Chrome Lead-Socket 45p. Phone Plug 6p. Phone Socket 8p. JACK PLUGS 8td. Chrome 30p; 3-5mm Chrome 15p. DIN SOCKETS Chassis 3-pin 10p, 5-pin 10p. DIN SOCKETS lead 3-pin 25p; 6-pin 25p. DIN PLUGS 3-pin 10p; 5-pin 25p. VALVE HOLDERS, 10p; CERAMICS 10p; CAN 8 10p.

SOUND TO LIGHT KIT.

Kit of parts to build a 3 channel sound to light unit, 1,000 watts per channel. £11.50. Post 35p.

EMI TAPE MOTOR £2

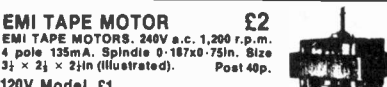4 pole TAPE MOTORS. 240V a.c. 1,200 r.p.m. 4 emi 135mA. Spindle 0.187x.75in. Size 3 1/2 x 2 1/2 x 2 1/2in (illustrated). Post 40p. 120V Model, £1.



RADIO COMPONENT SPECIALISTS

Radio Books and Components Late 10p. (Minimum posting charge 30p.) 337 WHITEHORSE ROAD, CROYDON Open 9-6. Wed. 9-1, Sat. 9-5 (Closed for lunch 1.15-2.30) Buses 50, 68, 159. Rail Seilhurst. Tel. 01-684 1665

HEADS OR TAILS

FIG. 1 shows a "heads or tails" circuit which is very low in cost and easy to build.

Gates a and b are connected as an astable multivibrator. Gates c and d are connected as a bistable. The astable output is applied through switch S1 to gate c. If a logic 1 is applied to pin 5, since pin 4 is connected to the positive supply line the output at pin 6 will be a 0 causing D2 to light.

S1 must be a push to make, release to break switch.

D. Manoharan,
Kuala Lumpur

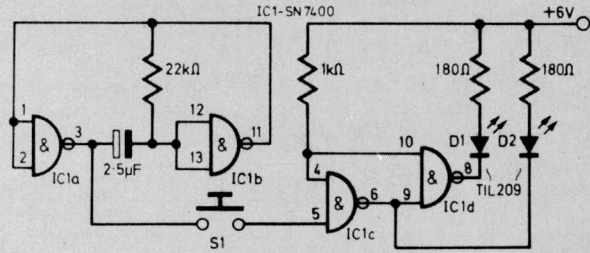


Fig. 1

DISPLAY FOR DIGITAL ALARM CLOCK

THE constructional feature on the Digital Alarm Clock in PE, April/May 1974 was most welcome. However, as not all constructors would want the complexity (quite apart from the high cost) of a liquid crystal display I wish to offer the following suggestions for using the clock chip with the more usual 7-segment i.e.d. display.

It is usual to buffer each of the display outputs with transistors in order to drive the appropriate segment of the i.e.d. indicator.

While the scheme works fine, it lands the constructor with two dozen or so transistors and a host of discrete components! To avoid this, use was made of the SN75492 i.c. in place of transistors. This i.c. is used to interface MOS circuits to i.e.d. displays in calculators, and each contains six Darlington drivers. Four SN75492 i.c.s will provide the 24 buffers required and the wiring is shown in Fig. 1.

Although common-anode i.e.d. indicators are drawn, it is possible to use common-cathode displays in similar fashion. In this case, however, the SN75491 i.c. which contains four Darlington drivers with free

emitter connections, has to be used in place of the SN75492. Six SN75491 i.c.s will therefore be required and the circuit is indicated in Fig. 2.

When using the SN75491 or SN75492 as drivers it is necessary to limit the supply voltage to 10V as this is their maximum rating.

Finally it is just as possible to use other types of 7-segment displays, e.g. Minitron indicators, provided the current required does not exceed the capabilities of the driving i.c.s used (250mA for SN75492 and 50mA for SN75491).

C. S. Soh,
Singapore. 9

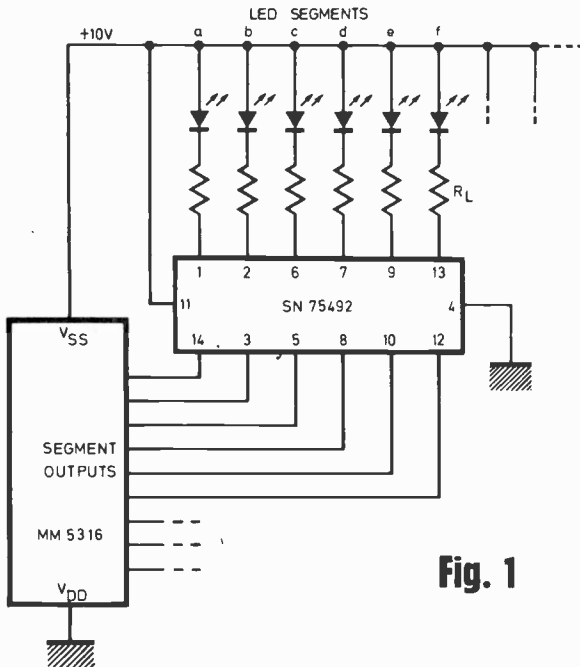


Fig. 1

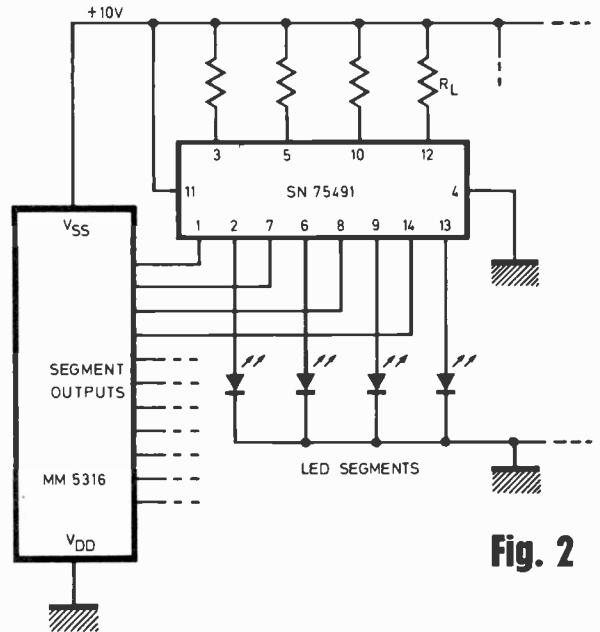


Fig. 2

FUZZ EFFECT

THE circuit shown in Fig. 1 produces the well known "Fuzz" effect associated with electric guitars, with a minimum of components and, thus, a very low cost compared with commercial equivalents.

Fuzz is obtained by amplifying the input (20–50mV) so as to produce a swing of over 0.6V on the output. Anything above this voltage causes one of the two silicon diodes to conduct and hold the output at a maximum/minimum of $\pm 0.6V$ – $0.6V$. The gain of the amplifier, which determines the degree of clipping or fuzz, is varied by selecting a different amount of negative feedback via the potentiometer. By this means the fuzz can be varied from zero to maximum.

With some guitars the input might be too high and cause some fuzz on the zero setting. Should this occur R1 should be increased until no distortion is present.

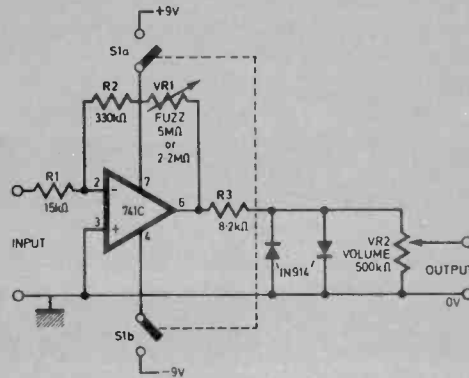


Fig. 1

The original was placed under a guitar scratch plate, powered by two rechargeable batteries (4.8V) together with an active tone control. This method has been found to be very

reliable and a lot more convenient than a normal foot operated unit.

S. Carter,
Bucks.

NEWS BRIEFS

Oh Buoy!

AN ingenious sonobuoy system which, when dropped into the sea by an aircraft, gives information of any submarines in the surrounding area was recently demonstrated by Plessey.

On contact with the water the buoy separates into upper and lower sections interconnected by a compliant cable. The lower section sinks to a predetermined depth at which it rotates in stepped stages through 360°. At each stage it transmits and receives sonar signals and relays the information thus obtained back to the aircraft via the floating buoy section above.

Another device known as a "dunking sonar" when lowered into the sea by a hovering helicopter gives the operator range, bearing and radial velocity target information on a c.r.t. display.

Tifax

THE world of Ceefax and Oracle (how to put printed information on your television screen) took a step in the right direction recently with the announcement by Texas Instruments that they have developed a dual Ceefax/Oracle decoder called Tifax.

Such a device will be able to take the BBC Ceefax and the IBA Oracle transmissions and decode them for visual presentation.

As a result, Decca have become involved in making up decoders using discrete LSI/SSI parts in low-power Schottky and including a bipolar Tifax compatible ROM.

Of course, it will be some time before anyone sees the results of this work. Production quantities to set

manufacturers from Texas are not expected to be available before next year and initially, at any rate, cost will be high, about £100 per set excluding a suitable control unit.

No doubt, as with all these things, the costs will drop dramatically but no-one seems to be too interested in making guesses at this time as to the possible cost of a system including a hand-held control unit.

Tigerfish

MARCONI Space and Defence Systems have received an order from the M.O.D. for the supply of Tigerfish submarine-launched torpedoes to the Royal Navy.

The Tigerfish, weighing about one and a half tons and twenty-one feet long, carries an on-board computer system and forms part of a sophisticated submarine weapon complex.

The connection to the submarine's control computer is made via a guidance wire which is reeled out from both the submarine and the torpedo. The wire therefore remains stationary in the water irrespective of the movements of the submarine or torpedo.

The target is detected by sonar beams produced by an array of acoustic transducers in the nose of the torpedo. The torpedo automatically homes in on the target under computer control whilst information in the torpedo computer memory is being continually updated.

Disappearing Landmark

WITH the dismantling of E.M.I.'s 200ft steel aerial tower, which has dominated the Hayes skyline since 1936, another historic landmark in the story of TV broadcasting has disappeared.

It was from their Research Laboratories that test pictures were first broadcast in 1935 (establishing the 405-line standard which was to remain in force until 1961) giving Britain a lead of several years over the rest of the world in TV broadcasting.

SONY HALF PRICE

These top quality SQ Decoder/Amplifiers are offered at half price while stocks last. Brand new in manufacturers' cartons with one year guarantee.



SQA 100
SQ DECODER/AMPLIFIER
SQA 100. A versatile and space saving SQ decoder/amplifier which can convert your existing stereo system (providing your amplifier has a tape/source monitor switch) to exciting 4-channel realism—just add model SQA 100 and a pair of rear speakers. Other features include tone controls, balance controls, and power amplifier giving 8W RMS output per channel, master volume control for simultaneous adjustment of 4 channels and decoder output controls for independent use of decoder. Many of your favourite artists are now recording albums in SQ—ask at your local record shop.

REC. RETAIL £52.00 incl. VAT
OUR SPECIAL HALF PRICE OFFER
ONLY £26.00 incl. VAT
Please add £1.50 P. & P. and Insurance

SQA 200
SQ DECODER/AMPLIFIER

SQA 200. Providing an output of 8W RMS per channel for the rear speakers, SQA 200 is a decoder/amplifier designed specifically to work with those complete audio units systems provided with a tape-source monitor switch. Now that so many of your favourite artists are recording SQ albums, the addition of SQA 200 plus a pair of rear speakers will add a new dimension to your stereo system.

OUR SPECIAL HALF PRICE OFFER
£38.80 incl. VAT
REC. RETAIL PRICE £77.68 incl. VAT
Please add £1.50 P. & P. and insurance



DECLON FOAM SPEAKER FRONTS
as used by leading manufacturers

18½ x 10 x ½ black or brown £2.00 each
22 x 12 x ½ brown £2.50 each
29 x 11 x ½ brown £3.00 each
26 x 15½ x ½ brown £3.00 each

Prices include VAT and Post and Packing.
Can be easily cut to suit any loudspeaker enclosure.
Pattern as illustrated.



THE FABULOUS SANSUI 210 TUNER AMPLIFIER



210
Sansui 210 34W AM/FM Stereo Multiplex Tuner Amplifier. Equipped with an FET front end for exceptionally sensitive FM reception, linear scale FM dial for precise tuning and automatic FM stereo/mo-no switching, this model also provides a full system of accessory circuits, wide 30 to 25,000Hz power bandwidth and holds distortion to less than 1%.

REC. RETAIL PRICE
£111.85 incl. VAT
OUR PRICE
£74.95 incl. VAT
+ £1.50 P. & P. and insurance

CHEQUES, P.O.s AND
MONEY ORDERS TO

medway mail order co.

P.O. BOX 4G
GILLINGHAM
KENT, ME7 5LB

Sound to Light Master Unit




600 watts per channel

Connects to your loudspeaker or loud-speaker socket. The unit can be connected to your existing spotlight fittings or to our type A or B fittings.

Special Introductory Price

Including channel output plugs and mains input socket.

Only **£29.95**
incl VAT plus p&p £1.00

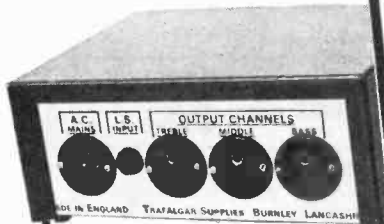

Type B 3 BANK UNIT



B.C. fitting (less lamp)

£6.50 incl VAT plus p&p 40p each

Type A

(less lamp)
£1.60 incl VAT plus p&p 25p each.



B.C. fitting

100 WATT Red, pink, yellow, green, blue, clear.
SPOT LAMPS Only £1.00 each
Minimum 3 lamps £3.00 plus p&p 25p.
B.C. fitting

TRAFALGAR SUPPLIES
Dept. H.T., STANDISH STREET,
BURNLEY, LANCs.



WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 253, 8 or 15 ohm £8-84
 Baker Group 35 3, 8 or 15 ohm £10-25
 Baker Group 50 12 8 or 15 ohm £14-00
 Baker Deluxe 12in d.cone £13-75
 Baker Major 12in d.cone £11-87
 Baker Regent £10-00
 Baker Superb £10-00
 Baker Auditorium 12 £18-12
 Castle Super 8 RS DD £10-31
 Celestion MF1000, 8 or 15 ohm £10-95
 Celestion PS8 for Unilex £3-75
 Celestion G12M 8 or 15 ohm £12-00
 Celestion G12H 8 or 15 ohm £15-00
 Celestion G15C 8 or 15 ohm £24-00
 Celestion G18C 8 or 15 ohm £33-00
 Decca London Ribbon Horn £30-00
 Decca London and crossover £37-50
 Decca DK30 and crossover £24-08
 EMI 13in x 8in 150 d.c. 8 ohm £2-84
 EMI 13in x 8in type 350 8 or 15 ohm £5-56
 EMI 13in x 8in 20W base £7-88
 EMI 6in 93850 4 or 8 ohm £2-90
 EMI 5in 14A 7030 mid range 8 ohm £3-50
 EMI 2 1/2in tweeter 97492AT £0-77
 Eagle DT33 30W tweeter £6-31
 Eagle HT15 horn tweeter £4-40
 Eagle CT5 cone tweeter £2-08
 Eagle CT10 tweeter 8 or 16 ohm £3-00
 Eagle MHT10 horn tweeter £4-44
 Eagle crossover CN23, CN28, CN216 £1-75
 Eagle FR4 £6-12
 Eagle FR65 £9-82
 Eagle FR8 £12-31
 Elac 9 x 5 59RM109 15 ohm, 59RM114 8 ohm £3-44
 Elac 6 1/2in 6RM171 d.c. roll surr. £4-08
 Elac 6 1/2in 6RM220 d.c. cone £3-12
 Elac 4in tweeter TW4 £1-75
 Elac 10in d.c. cone 10RM239 8 ohm £3-12
 Elac 8in 8CS175 3 ohm £2-87
 Fane Pop 15W 12in £5-25
 Fane Pop 25T 30W 12in £7-50
 Fane Pop 50W 12in £12-00
 Fane Pop 55 80W 12in £12-85
 Fane Pop 80W 15in £13-75
 Fane Pop 100W 18in £25-95
 Fane Crescendo 12A 100W 12in £34-50
 Fane Crescendo 12B bass £26-50
 Fane Crescendo 15in 100W £47-50
 Fane Crescendo 18in 150W £82-85
 Fane 801T 8in d/c roll surr. £8-12
 Fane 807T 8in d/c roll surr. £4-82
 Fane 808T 8in d/c £3-44
 Fane 701 twin ribbon horn £40-50
 Fane 910 horn £14-95
 Fane 920 horn £33-95

Goodmans 8P 8in 8 or 15 ohm £5-50
 Goodmans 10P 8 or 15 ohm £5-80
 Goodmans 12P 8 or 15 ohm £13-95
 Goodmans 12P-D 8 or 15 ohm £16-95
 Goodmans 12P-G 8 or 15 ohm £15-95
 Goodmans Audiomax 12AX 100W £36-50
 Goodmans Audiomax 15AX £40-25
 Goodmans 15P 8 or 15 ohm £21-00
 Goodmans 18P 8 or 15 ohm £28-00
 Goodmans Hifax 750 £16-00
 Goodmans Axent 100 tweeter £8-44
 Goodmans Audiom 100 12in £13-90
 Goodmans Axlom 402 12in £20-00
 Goodmans Twinaxiom 8 £10-14
 Goodmans Twinaxiom 10 £10-75
 Jordan Watts Module £17-08
 Kef T21 £8-06
 Kef T15 £8-84
 Kef B110 £8-37
 Kef B200 £9-50
 Kef B139 £16-50
 Kef DN8 £2-31
 Kef DN12 £5-75
 Kef DN13 £3-87
 Peerless Dome Tweeter KO10DT £8-08
 STC 4001G Super Tweeter £8-56
 Radford BD25 £18-44
 Radford FN11a £13-56
 Radford FN12a and 12b £12-44
 Radford MD9 £11-50
 Radford TD3 £8-08
 Richard Allen CG8T d.c./surr. £7-37
 2 1/2in 64 ohm, 70mm 80 ohm, 70mm 8 ohm £0-77
 2 1/2in 75 ohm £0-50
 7in x 4in 3 or 8 ohm £1-63
 8in x 5in 3 or 8 ohm £1-75
 10in x 6in 3, 8 or 15 ohm £2-69

SPEAKER KITS

Baker Major Module each £13-44
 Goodmans Mezzo twinkit pair £47-19
 Heime XLK25 pair £25-44
 Heime XLK30 pair £17-18
 Heime XLK50 pair £46-25
 Kefkit 1 pair £48-44
 Kefkit 3 each £42-50
 Richard Allan Twinkit each £10-37
 Richard Allan Triple 8 each £15-84
 Richard Allan Triple 12 each £23-12
 Richard Allan Super Triple each £27-50
 Wharfedale Linton 2 kit pair £23-12
 Wharfedale Glendale 3 kit pair £40-62
 Wharfedale Dovedale 3 kit pair £83-12
 Baker, Linear and Eagle PA disco amplifiers in stock.
 Send stamp for list.

FREE with Speaker Orders over £7

Hi-Fi Loudspeaker Enclosures book.

All units guaranteed new and perfect. Prompt despatch. Carriage and packing: speakers 38p each, 12in and up 50p each, speaker kits 75p each (£1-50 pair), tweeters and crossovers 25p.

Send stamp for free booklet: "Choosing a Speaker".

Including VAT 25% on HI-FI, 8% on PRO and PA

WILMSLOW AUDIO (Dept. PE)

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire SK9 1HF.

Discount Radio, PA, Hi-Fi: 10 Swan Street, Wilmslow.

Discount TV, Hi-Fi: Swift of Wilmslow, 5 Swan Street, Wilmslow.



Cassettes

The best buy!

	C80	90p	£3-00	£6	£10
Agfa Low Noise Cassettes AT LESS THAN HALF PRICE!	C90	94p	£2-75	£5-30	£8-30
	C120	78p	£2-75	£7-28	£7-28
AGFA HIGH DYNAMIC SUPER	C80 - 8	84p	£2-75	£8-28	£8-28
	C90 - 8	79p	£3-00	£8-75	£8-75
	C120	89p	£4-88	£9-08	£9-08
AGFA STEREO-CHROM CHROMIUM DIOXIDE	C80	1	£4-00	£8	£10
	C90	£1-10	£4-50	£8-50	£10-00

SAME DAY DESPATCH. P. & P. 15p per order

WILMSLOW AUDIO

(DEPT. PE)

10 SWAN STREET, WILMSLOW, CHESHIRE, SK9 1HF

Cut-price prerecorded cassettes—send stamp for list

Towers' International Transistor Selector

by

T. D. TOWERS
 MBE, MA, BSc, CEng, MIERE

Towers' International Transistor Selector

T.D. Towers, MBE, MA, BSc, CEng, MIERE

Over 11000 transistor types, 14000 diodes and hundreds of transistors with their pin and electrical characteristics, 17000 types and pin diagrams, 1000000



No professional or enthusiast engineer should be without this time saving, comprehensive reference work. Compiled by an expert to cater for the requirements of industry it is equally essential to the hobbyist, teacher, component buyer and service man.

The 142 large pages are crammed with concise information on over 10,000 British, U.S., European and Japanese devices, sensibly tabulated for easy reference.

Contents include electrical specifications, base types and connections, source of manufacture, maker's addresses and much other vital information.

All for
£3.40
 including postage


To: Technical Book Services (PE1)
 25 Court Close, Bray, Maidenhead, Berks.
 SL6 2DL
 Please supply (.....) copies of Towers' International Transistor Selector

I enclose cheque/postal order for £.....

Name

Address

BLOCK CAPITALS

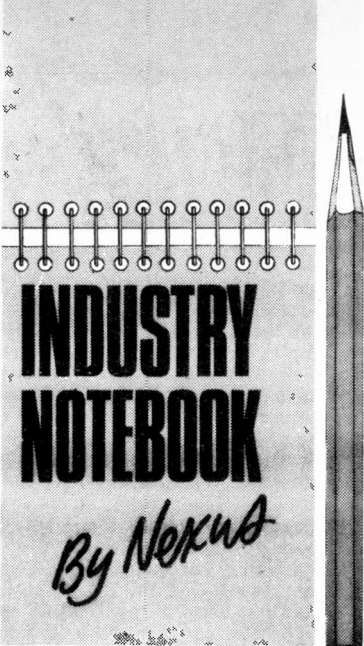

INDUSTRY NOTEBOOK

By Nexus

NEW-LOOK CEI?

Professional engineers still enjoy their old status among themselves but not, it seems, with the government or the public. They haven't the industrial muscle power of the trades unions or the leverage on wage claims resulting from real strength in an inflationary situation. To make things worse there are numerous well-intended but often ill-informed ginger groups getting plenty of publicity by blaming a lot of the ills of society on technology and, by inference, on the engineers who generate technology.

So one way and another the poor old engineer is in the dog-house. He often doesn't get the pay he deserves and isn't any longer a popular member of society.

For years the engineers have been fragmented, belonging not to trades unions but to learned societies which under their charters cannot practice in a union-like way. The whole spread of engineering sciences is served by fifteen learned societies of which two have very substantial numbers of electronic engineers in membership, the Institution of Electrical Engineers (IEE) and the Institution of Radio and Electronic Engineers (IERE). The third is The Royal Aeronautical Society to which many electronic engineers engaged in the aerospace industry belong.

Over twenty years ago there was a move towards closer cohesion and an Engineering Institution Joint Council was set up and from this emerged the Council of Engineering Institutions (CEI) in September, 1965. The CEI did good work on raising standards of qualification to membership and in other areas but failed to have much success with putting over what is vaguely termed "image".

The present state of play is that there are proposals that the initials CEI remain the same but the name is changed to the Chartered Engineering Institution and that the major change in constitution will be that individual engineers will be members as well as the fifteen existing institutions. In other words that the new CEI, if it comes into being, can speak directly on behalf of 200,000 chartered engineers at first-hand, instead of at second-hand as at present. But engineers will still, of course, also retain membership of their present institutions.

What are called "professional services" will be a new function for CEI. These include an appointments bureau, advice on education and training, health and insurance schemes, professional advice and similar activities to do with the professional well-being of members.

I give the new movement towards greater professional cohesion my full support. The pattern has already been established in the United States where some of the Institutions jointly run a Washington office to act as an advice centre for the Government on engineering matters and to keep a watching brief on all Congressional bills which have an effect on the professional engineering community.

TRADE BALANCE

The Electronic Engineering Association, representing some fifty British major companies in the electronics capital goods sector gives estimated deliveries for 1974 as worth £924 million compared with £740 million in 1973, which would be a substantial success story but for inflation. As it is, taking into account all the problems experienced in world trade in 1974, it is still a creditable achievement at some 25 per cent increase over the previous year and more than double the 1972 figure.

The balance of trade is precarious, however, with exports at £431 million only just above imports at £423 million. The culprits as usual are computers where Britain imported more than £76 million worth than were exported. But all the other sectors such as broadcast equipment, communications, radar, etc. together had a trade surplus of nearly £85 million over the imports.

One sees the pattern changing since the Middle East became the richest area in the world. Deliveries, especially to the OPEC countries, are shooting up. The Common Market countries, too, are taking much more British-built equipment and in 1974 accounted for 45.5 per cent of all capital goods exports while Commonwealth countries, once our biggest market, now takes less than 10 per cent.

Employment, at 128,000 people was higher and so were wages, over 20 per cent up by the end of 1974, and material input prices were up by 32 per cent. So profitability is suffering and so is investment. But the outlook remains surprisingly cheerful. Member companies of the EEA have substantial order books and even the defence cuts may not prove too harmful because smaller forces need more powerful communications and weapon systems so a greater proportion of money spent on defence will flow to the electronics industry.

ILECS

The International London Electronic Components Show at Olympia couldn't have opened its doors at a more politically stormy time. Pre-referendum squabbles were at their height and the business world was very apprehensive on the effect in both the short and long terms of Mr Benn's Industry Bill, although there were some signs of relief that the Prime Minister, by personal participation, would exert a moderating influence.

The 400 or so exhibitors and thousands of visitors couldn't be said to be exactly in carnival mood but everyone was surprisingly cheerful. A sort of re-run of the experience I had in New York a month earlier at the IEEE Intercon show. I remember in another time of difficulty being at the Paris Salon, still Europe's biggest components bonanza, when people just talked themselves into depression.

And another occasion when I was in Beirut and asked a local businessman how on earth he carried on trading with constant wars, skirmishes, and political upheaval in the countries with which he was trading. His answer was that it was always like that and you learned to live with it. So maybe we Europeans are acquiring the same philosophy.

On the other hand, when you look at the big order books in electronics and aerospace there is a lot to be thankful for. These two great industries, so closely related, continue to do well. In the first quarter of this year the aerospace lads exported £180 million of equipment, more than the figure for a whole year a decade ago. And when you see companies like Mullard, Plessey, Pye and dozens of others with not one or two, but whole new ranges of products coming to the market things can't be all that bad.

Purchasing power has shifted to new areas in the past two years but, as one exporter told me recently, provided you maintain your share of the market on a world scale, this is not important. The big slump only comes when all the money goes to one area and then the new-rich refuse to spend it.

PATENTS REVIEW...

TOUCH SWITCH

In BP 1 383 132, Magic Dot Inc., of Minnesota, U.S.A., claims an improvement over existing touch-actuated switches. The switch relies on the capacitance of an operator providing a reference between electronic circuitry isolated from earth and earth itself. It is suggested that some existing switches are liable to trigger prematurely or fail to trigger reliably.

The basic circuit is shown in Fig. 1. A metal touch switch plate is connected to the input of a d.c. to power frequency amplifier. The output of the amplifier is connected to the input of a second d.c. to power amplifier.

The power supply includes transformer T1, of which the primary receives mains frequency power and is connected to true earth. The transformer secondary is connected to the chassis earth but is isolated from the primary and thus from true earth. It is also connected to amplifier supply inputs.

The a.c. mains on the transformer primary causes the entire switching circuit to oscillate with respect to true earth at mains frequency. The capacitance of a finger on the touch plate provides a reference between chassis earth and true earth. This appears to the earth-isolated switching circuit as an alternating frequency power input of an amplitude equal to the amplitude at which the switch circuit is oscillating with respect to earth. Thus, the switch circuit is modulated by its own oscillation with respect to earth.

The inventors suggest that it is normally considered detrimental to such circuitry to have the input transformer and chassis oscillating with respect to earth. But they take

advantage of this customary disadvantage. The oscillation current appearing at the input of the amplifier may be in the order of only 20 nano-amperes. But the amplifier, with a gain of at least 10, is used to charge capacitor C1 connected to chassis between the two amplifiers. When C1 is charged it approximates a current source for the high gain amplifier. As a result, the application or removal of an operator's finger at the touch plate causes the resistance between output terminal of the high gain amplifier and chassis to approximate an electrical short circuit in a first state and an electrical open circuit in a second state. An added advantage of the circuit is that it requires no standby power.

DIGITAL RECORDING

BP 1 383 323

The Japanese company, Nippon Columbia, already has several conventional analogue records on the market which were recorded using digital (PCM) techniques. The BBC uses digital transmission to convey f.m. radio signals between national transmitters, and it has been an open secret for some time now that work is in progress at the BBC on the digital recording of television signals.

In BP 1 383 323, the BBC describes its successful techniques. Although these are intended primarily to solve problems encountered with TV recording, the invention concept has wider applications.

To record a full band width colour television signal requires information transfer rates in the region of 10^8 bits/second for the recording and replay systems. Holographic methods of attaining this have been proposed, but these are difficult to apply on a real time basis.

A continuous-wave laser is used to produce a coherent light beam which passes through an intensity modulator and is directed by a plane mirror to a circular scanner. The scanner includes a concave mirror on the end of a quartz fibre which is caused to nutate at line frequency (15kHz) by a tubular piezo-electric transducer at the other end of the fibre. As a result, the focused laser beam scans in a circular manner and the spot is arranged to pass over the ends of a circular array of glass fibre light guides.

The other ends of these fibres are arranged flat so that there is conversion from circular to linear scan. The light emerging from the ends of the fibres passes through an optical polariser and mask with ten apertures. Nine apertures are used to transmit the digital information and the tenth, centre, aperture passes a reference beam.

An electro-optic crystal (e.g. a Pockels cell) is located in front of each aperture. The lens images the fibre ends of the scan converter onto a length of 35mm movie film as it passes the lens. During scanning the digital information is applied word by word to the crystal and a micro-hologram of the "open" apertures of the mask is formed on the film.

It is interesting to note that the developed negative need not be printed up as a positive.

The recovery equipment consists of a laser, mirror, scanner and scan converter all similar to the record equipment. Due to diffraction at each micro-hologram, sets of discrete images are produced and one of the first-order set of images will have a similar geometrical disposition to that of the original binary mask used in recording.

The recovery mask excludes all but the wanted set of images, and the light emerging from the apertures of the mask is directed onto a set of photo detectors. The outputs of the detectors are used to generate a parallel stream of logic bit streams.

It is claimed that conventional, high contrast photographic film can be used in this way to record TV signals. Particularly interesting is the suggestion that if photo-conductive thermo-plastic recording tape with sufficient sensitivity becomes available in the future, this can be used instead of photographic film, and of course without development delay.

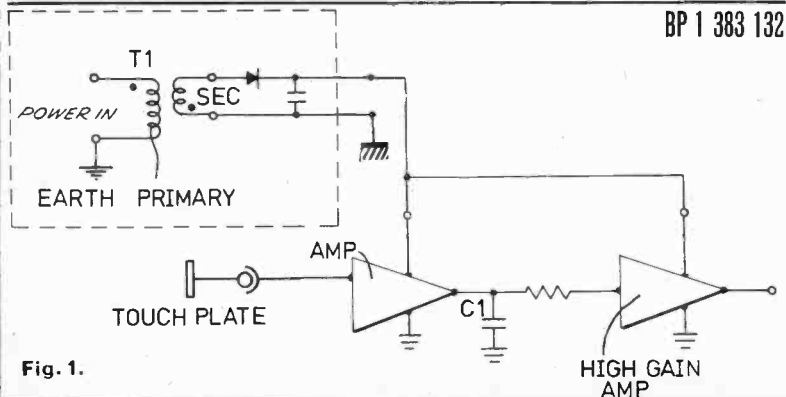


Fig. 1.

BP 1 383 132

CHROMASONIC electronics

Dept. 2, 56, Fortis Green Road,
Muswell Hill, London, N10 3HN.
telephone: 01-883 3705

C - MOS

74 TTL

LINEAR I.C.'s

C - MOS			74 TTL			LINEAR I.C.'s								
1-24	25-99	100up	1-24	25-99	100+									
CD4000AE	23p	19p	15p	7400	14p	12p	10p	555 (8 pin dip) V	55p	BHA0002	£3.01	MC1358 (CA3065) E1.16	SN76544N	£1.81
CD4001AE	23p	19p	15p	7401	14p	12p	10p	555 (TO-99) T	81p			MC1375	E1.48	SN76550-2 (TAA550) 89p
CD4002AE	23p	19p	15p	7402	14p	12p	10p	556 (14 pin dip)	£1.29	CA2111	£1.19	MC1455 (555T)	62p	SN76552-2
CD4003AE	£1.59	£1.33	£1.06	7403	15p	12p	10p	703 (RF/IF Amp)	59p	CA3045	£1.69	MC1456C	£1.88	SN76600N (TBA120) 75p
CD4007AE	23p	19p	15p	7404	14p	13p	11p	709 (8 pin dip)	38p	CA3053	58p	MC1458CP1	£1.54	SN76666N (CA3065) £1.12
CD4008AE	£1.75	£1.46	£1.17	7408	16p	13p	11p	709 (TO-99)	38p	CA3045	£1.60	MC1469G	£2.18	TAA263
CD4009AE	Use	CD4049		7409	14p	13p	11p	709 (14 pin dip)	38p	CA3075	£1.64	MC1495L	£4.24	TAA300
CD4010AE	Use	CD4050		7410	14p	13p	11p	710 (8 pin dip)	39p	CA3078	£1.26	MC1496G	96p	TAA310A
CD4011AE	23p	19p	15p	7413	27p	24p	20p	710 (TO-99)	45p	CA3080	59p			TAA320
CD4012AE	23p	19p	15p	7417	27p	23p	20p	711 (14 pin dip)	44p	CA3081	£1.86	MC3302P	£1.50	TAA350
CD4013AE	69p	58p	46p	7420	14p	13p	11p	711 (TO-99)	51p	CA3082	£1.86	MC3401P	74p	TAA370
CD4014AE	£1.75	£1.46	£1.17	7427	27p	23p	18p	709 (A.M. Radio)	£1.76	CA3089E (TDA1200E2.43)	£1.86	MFC4000B	87p	TAA570
CD4015AE	£1.75	£1.46	£1.17	7430	16p	13p	11p	723 (TO-99)	£1.09	CA3097E	£1.67	MFC4066A	79p	TAA700
CD4016AE	69p	58p	46p	7432	27p	23p	18p	723 (14 pin dip)	74p	CA3123E	£1.76	MFC6030A	79p	
CD4017AE	£1.75	£1.46	£1.17	7437	27p	23p	18p	741 (8 pin dip)	36p	CA3401E (LM3900)	68p	MFC6040	96p	TBA1205
CD4018AE	£2.51	£2.09	£1.67	7441	75p	62p	50p	741 (TO-99)	43p	CA3600E	£1.44	MFC6070	£1.66	TBA231
CD4019AE	80p	66p	53p	7442	65p	55p	43p	741 (14 pin dip)	36p	CT7001	£5.34			TBA281 (723)
CD4020AE	£1.97	£1.64	£1.31	7445	55p	45p	37p	747 (8 pin dip)	42p			MM5314	£4.80	TBA300C
CD4021AE	£1.75	£1.46	£1.17	7447	95p	83p	67p	747 (14 pin dip)	£1.04	LM005T1 (TO-3)	£1.46	MM5316	£9.99	TBA520Q
CD4022AE	£1.83	£1.53	£1.22	7447A	95p	83p	67p	748 (TO-99)	51p	LM031T1 (TO-3)	£1.46			TBA530Q
CD4023AE	23p	19p	15p	7448	85p	71p	57p	748 (14 pin dip)	49p	LM037T1 (TO-3)	£1.46	MVR5V (TO-3)	£1.45	TBA540Q
CD4024AE	£1.26	£1.05	84p	7470	30p	25p	20p	753 (F.M. 1st. I.F.) £1.08		LM129 (SOT-32)	85p	MVR12V (TO-3)	£1.45	TBA550Q
CD4025AE	23p	19p	15p	7472	25p	21p	17p			LM130 (SOT-32)	85p	MVR13V (TO-3)	£1.45	TBA560CQ
CD4026AE	£2.79	£2.33	£1.86	7473	30p	25p	20p	75491	88p					TBA625A
CD4027AE	99p	82p	65p	7474	34p	26p	21p	75492	£1.10	LM301 T (TO-99)	65p	NE540L	£1.25	TBA625B
CD4028AE	£1.53	£1.28	£1.02	7475	45p	37p	31p	Regulators 100mA		LM301 S (6 pin dip)	59p	NE555V	73p	TBA625C
CD4029AE	£1.12	£1.76	£1.41	7476	32p	26p	21p	7810SWC (TO-92)	60p	LM301A T (TO-99)	67p	NE556	£1.29	TBA651
CD4030AE	71p	59p	47p	7482	75p	62p	50p	7812WC (TO-92)	60p	LM301A S (8 pin dip)	59p	NE560B	£5.06	TBA720Q
CD4035AE	£1.75	£1.46	£1.17	7485	£1.30	£1.09	87p	7815WC (TO-92)	60p	LM307 T (TO-99)	59p	NE561B	£5.06	TBA750Q
CD4040AE	£2.01	£1.68	£1.34	7486	32p	26p	21p	Regulators 500mA		LM307 S (8 pin dip)	57p	NE562B	£5.06	TBA800
CD4042AE	£1.49	£1.24	99p	7489	£3.56	£2.80	£2.10	7815SAWC (TBA625A) 90p		LM308 T (TO-99)	£7.92	NE563	£2.96	TBA8105
CD4047AE	69p	58p	46p	7490	49p	40p	32p	7815SAWC (TBA625C) 90p		LM308 S (8 pin dip)	96p	NE565N	£1.87	TBA820
CD4050AE	69p	58p	46p	7491	65p	55p	45p	7815SAWC (TBA625C) 90p		LM308 S (8 pin dip)	96p	NE567	£2.83	TBA920Q
CD4051AE	£2.78	£2.32	£1.85	7492	57p	46p	36p	Regulators 100mA		LM309K	£2.34	SL414A	£2.09	TBA990Q
CD4052AE	£2.78	£2.32	£1.85	7493	49p	40p	32p	7815SAWC (TBA625C) 90p		LM309	£2.25	SL415A	£2.75	TCA270Q
CD4056AE	£2.12	£1.76	£1.41	7495	67p	55p	45p	7815SAWC (TBA625C) 90p		LM370N	£2.85	SL437D	£7.50	TCA760
CD4060AE	£2.51	£2.09	£1.67	74100	£1.08	89p	72p	7815SAWC (TBA625C) 90p		LM371	£2.88	SL440	£2.84	TCA800Q
CD4066AE	£1.13	94p	75p	74107	35p	28p	22p	7815SAWC (TBA625C) 90p		LM372N	£1.99	SL610C	£2.03	TCA8305
CD4068AE	28p	24p	19p	74121	34p	28p	23p	7815SAWC (TBA625C) 90p		LM377N	£2.71	SL611C	£2.03	TCA940
CD4069AE	28p	24p	19p	74122	47p	39p	31p	Regulators 1A		LM380	£1.25	SL612C	£2.03	TDA1054
CD4070AE	28p	24p	19p	74141	79p	63p	53p	7805KC (TO-3)	£2.09	LM381	£1.85	SL613C	£4.31	TDA1054
CD4071AE	28p	24p	19p	74145	68p	58p	48p	7812KC (TO-3)	£2.09	LM382	£1.66	SL620C	£3.06	TDA1200
CD4077AE	71p	59p	47p	74154	£1.75	£1.48	86p	7813KC (TO-3)	£2.09	LM383	68p	SL621C	£3.06	TDA1405
CD4081AE	28p	24p	19p	74174	£1.00	83p	67p	7818KC (TO-3)	£2.09	LM387	£1.66	SL622C	£7.62	TDA1412
CD4082AE	28p	24p	19p	74180	£1.06	88p	71p	7818KC (TO-3)	£2.09	LM3900	69p	SL623C	£5.57	TDA2100
CD4086AE	£1.28	£1.06	85p	74192	£1.35	£1.14	90p	7824KC (TO-3)	£2.09	LM1820	£1.03p	SL624C	£2.84	TDA2020
CD4089AE	£1.56	£1.30	£1.04	74193	£1.35	£1.14	90p	Regulators 1A		LM2111	£1.12p	SL640C	£3.75	UN2111A
CD4099AE	£2.95	£2.46	£1.96	74196	£1.64	£1.34	99p	7805UC (TO-220)	£1.72	LM3103L	£1.84	SL641C	£3.75	ZN402E
								7812UC (TO-220)	£1.72	LM3106P	80p	SL645C	£3.75	ZN414
								7815UC (TO-220)	£1.72	LM3131D	£2.29	SL650C	£9.85	
								7818UC (TO-220)	£1.72	LM3132	£2.49			
								7924KC (TO-3)	£2.09	LM3134	£4.13			
								ICL8038	£3.52	LM3135	£4.62			
								AY-1-0212	£6.93	LM3137	£1.12p			
								AY-1-5051	£1.44	LM3139P	83p			
								AY-5-1224	£3.95		£1.52			
								AY-5-3500	£6.59		64p			
								AY-5-3507	£6.59		89p			
								AY-5-4007	£7.94		£1.52			
											£1.52			

SIEMENS LCD's

LINE-O-LIGHT

LIQUID CRYSTAL DISPLAY complete with socket and removable reflective backing. Ref AN4132R 13mm character height. Can be directly driven by National Semiconductor Alarm Clock chip MM5316. £13.99



NEW LED Linear Cursors each device contains 10 light emitting diodes in a 20pin dual-in-line package. Ideal for solid state analogue meters or dials. Type 101 RED. £2.26



PHOTO-DARLINGTON

SPECIAL PURCHASE

SEVEN SEGMENT DISPLAYS

2N5777
V_{ceo}: V_{ceo} 25v; V_{ebo} 8v
V_{ceo}: V_{ceo} 25v; V_{ebo} 8v
f_{ie} 2500; I_c 250 mA **35p.**

enables
LIT707 90p ● LIT747 £1.99 ●
0.3" 0.6"

litronix
Xenon
Monsanto

I.C. SOCKETS
Dual-in-line TOS
Pins 8 14 16 24 28 36 40 8 10
● Price 13p 15p 15p 26p 30p 35p 44p 31p 35p

NEW
Litronix Double Digit Displays
0.5" Common Anode + 2 R/H
D.P.'s
DL721 gives +1.9
DL727 gives 0.0 to 9.9
Suitable for Clocks; Instruments;
T.V. Channel Indicator.
Our Price £4.75 each.

	COMMON ANODE R/H Dec. Pt.	COMMON ANODE L/H Dec. Pt.	COMMON ANODE - 1	COMMON CATHODE Dec. Pt.	Our Price
RED	DL707R	DL707	DL701	DL704	£1.82
GREEN	MAN51	MAN52	MAN53	MAN54	£1.82
RED	MAN71	MAN72	MAN73	MAN74	£1.82
YELLOW	MAN81	MAN82	MAN83	MAN84	£1.82
ORANGE	MAN3610	MAN3620	MAN3630	MAN3640	£1.82
GREEN	XAN51	XAN52	-	XAN54	£1.49
RED	XAN71	XAN72	-	XAN74	£1.49
YELLOW	XAN81	XAN82	-	XAN84	£1.49
GREEN	MAN4510	MAN4520	MAN4530	MAN4540	£2.32
RED	MAN4710	MAN4720	MAN4730	MAN4740	£2.32
YELLOW	MAN4810	MAN4820	MAN4830	MAN4840	£2.32
ORANGE	MAN4610	MAN4620	MAN4630	MAN4640	£2.32

L.E.D.'s
Free snap-on plastic retainer

	0.125" dia. lens (TIL209)	0.16" dia. lens	0.2" dia. lens (MLED 650)
	1- 10+ 100+	1- 10+ 100+	1- 10+ 100+
Red	15p 15p 13p	27p 24p 22p	18p 16p 14p
Green	27p 24p 22p	33p 30p 27p	30p 27p 25p
Orange	27p 24p 22p	33p 30p 27p	30p 27p 25p
Yellow	34p 31p 29p	35p 32p 29p	35p 33p 30p

NOTICE
Postage & Packing Charges


With the recent increase in postal charges and a continuing increase in packaging cost we have been forced to review our policy.

Henceforward:

- Orders valued at £5 or more will be post free.
- All U.K. "small package" orders will go first class mail.
- Minimum postage & packing charge will increase to 20p.

	C.A. L/H Dec. Pt.	C.A. L/H - 1	C.C. L/H Dec. Pt.	C.C. L/H - 1	C.C.
RED	DL747				

Sinclair Project 80

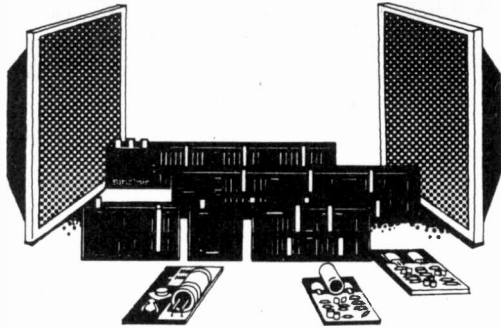

The watts...

14 different hi-fi modules.


Between them they cater for every variety of hi-fi set-up, from a tuner amp to a full CBS SQ quadraphonic system.

The value for money's amazing. A genuine 25 W per channel quadraphonic amplifier for under £80...

a 12 W per channel stereo amp for around £30...

And the satisfaction's even greater! If you can handle a soldering iron, you can handle Project 80. And if you can't... use Project 805 - the same modules but with solderless clip connections.

and the wherefores.

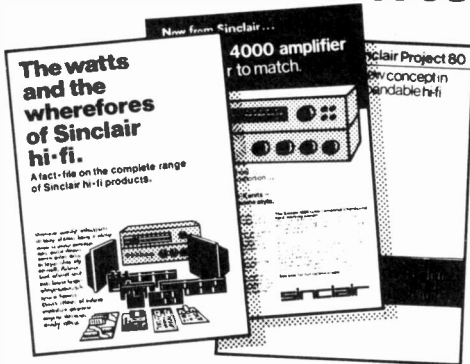

Take a look at some of the hi-fi systems you can build...

Get the full technical specifications...

See what impartial hi-fi journals thought of its performance...

And read up on the rest of the Sinclair hi-fi range...

It's all in the Sinclair hi-fi range fact-file.

Send for Sinclair's fact-file - now!

See if the answer's here - the information on the component you've been looking for.

Simply cut the coupon and send it to the no-stamp-needed FREEPOST address below.

We'll send you the Sinclair fact-file - giving you all you need to know about Project 80, and the rest of the Sinclair hi-fi range.

Plus information about a few extras you're sure to find rather interesting.

You've plenty to gain... so cut the coupon - now!

Sinclair Radionics Ltd,
London Road, St Ives,
Huntingdon, Cambs., PE17 4HJ
St Ives (0480) 64646

Please send me the Sinclair range fact-file immediately

Name

Address

P8/PE/8/75

To: Sinclair Radionics Ltd,
FREEPOST, St Ives,
Huntingdon, Cambs., PE17 4BR

Please print

sinclair

ELECTROVALUE

The best of all!

CATALOGUE 7 ISSUE 3

With 25p refund voucher

Up-dated Price and Product Information

112 pages plus cover. As comprehensive and up-to-the-minute as possible. Thousands of items from vast ranges of semi-conductors including I.C.s to components, tools, accessories, technical information and diagrams are included as well as a refund voucher worth 25p for spending on orders list value £5 or more **SEND NOW FOR YOUR COPY BY RETURN POST** It's an investment in practical money-saving and reliability! **30p** paid

PRICES—Electrovalue policy is to review prices every three months rather than try to keep up with day by day changes as they occur. We have, in fact, held our prices for two such periods (Jan. 1st-July 1st) and our next price review is due October 1st.

DISCOUNTS apply on all items except the few where prices are shown NETT. 5% on orders from £5 to £14.99; 10% on orders list value £15 or more.

FREE POST AND PACKING in U.K. for pre-paid mail orders over £2 (except Baxandall cabinets). If under there is an additional handling charge of 10p.

QUALITY GUARANTEE. All goods are sold on the understanding that they conform to maker's specification. No rejects, seconds or sub-standard merchandise.

ELECTROVALUE LTD

All communications to Section 2/5, 28, ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB. Telephone Egham 3603, Telex 264475. Shop hours: 9-5.30 daily, 9-1 pm Sats.

NORTHERN BRANCH: 690, Burnage Lane, Burnage, Manchester M19 1NA. Telephone (061) 432 4945. Shop hours: Daily 9-5.30pm; 9-1pm Sats.

ENGINEERS

FREE

YOURSELF FOR A

BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This helpful guide to success should be read by every ambitious engineer.

Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.



This 76 page
FREE book
shows how!

POST NOW

CUT OUT THIS COUPON

CHOOSE A BRAND NEW FUTURE HERE!

Tick or state subject of interest. Post to the address below.

<input type="checkbox"/> Practical Radio and Electronics (Technetron)	<input type="checkbox"/> Radio Amateurs	<input type="checkbox"/> Practical TV	<input type="checkbox"/> Colour Television	<input type="checkbox"/> Computer Electronics	<input type="checkbox"/> C. & G. LI Radio TV Servicing cert.	<input type="checkbox"/> Post Master General 1st & 2nd class certs.	<input type="checkbox"/> C. & G. Electrical Engineering Practise	<input type="checkbox"/> C. & G. LI Installations and Wiring	<input type="checkbox"/> General Electrical Engineering	<input type="checkbox"/> Society of Engineers (Electrical Engineering)	<input type="checkbox"/> Electrical Installations and Wiring	<input type="checkbox"/> C. & G. Electrical Technicians (Primary)	<input type="checkbox"/> C. & G. Telecommunications
---	---	---------------------------------------	--	---	--	---	--	--	---	--	--	---	---

To **ALDERMASTON COLLEGE** Dept. EPE06
Reading RG7 4PF
Also at our London Advisory Office, 4 Fore St. Avenue, Moorgate, London EC2Y 5EJ. Tel: 01-429 2721.

NAME (Block Capitals Please)

ADDRESS

Other subjects POSTCODE Age

Accredited by C.A.C.C. Member of A.B.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

PHONOSONICS

SUPPLIERS OF QUALITY PRINTED
CIRCUIT BOARDS, KITS AND
COMPONENTS TO A WORLD-WIDE MARKET

SOUND-TO-LIGHT (P.E. Apr./Aug. 71)

The ever-popular AURORA—4 or 8 channels each responding to a different sound frequency and controlling its own light. Can be used with most audio systems and lamp intensities. A MUST for any Disco, and a fascinating visual display for the home.

4 channel component set (excl. thyristors) £11-49
8 channel component set (excl. thyristors) £20-32
Power supply component set £4-78
PCB for 4 frequency channels £2-50
PCB for power supply and 8 lamp drivers £1-25
1 Amp 400V thyristors (1 per chan. requ.) each 75p
Panel meter (1mA) (optional) £3-50

VOICE OPERATED FADER (P.E. Dec. 73)

For automatically reducing music volume during "talk-over"—particularly useful for Disco work or for home-movie shows.

Component set incl. PCB £2-85

TAPE-NOISE LIMITER

Very effective circuit for reducing the hiss found in most tape recordings.

Component set (incl. PCB) £2-30
Regulated power supply (incl. PCB) £3-71

P.E. SYNTHESISER

The well-acclaimed and highly versatile large-scale mains-operated Sound Synthesiser complete with keyboard circuits, and having a wider range of functions than the P.E. Minisonic, though the two may be used in conjunction with each other to great advantage. Published in P.E. Feb. 1973 to Feb. 1974.

Full details of component sets, printed circuit boards and discount facilities are in our list. Send S.A.E.

HI-FI TAPE-LINK (P.E. Mar./Apr. 73)

Designed for use with reasonable quality tape-decks, this high performance pre-amp includes record, playback and metering circuits.

Stereo component set (excl. panel meter) £22-05
Mono component set (excl. panel meter) £13-31
Power supply component set £3-72
Stereo main PCB £2-50
Stereo sub-assembly PCB 86p

P.E. GEMINI 30W STEREO AMPLIFIER

An exceptionally high quality Stereo Amplifier system, specifications for which are shown in detail in our list, together with semiconductor requirements. While stocks last.

Main Amplifier:
Set of resistors, capacitors and presets £5-96
Stereo printed circuit board £1-28
Pre-Amplifier
Set of resistors, capacitors, potentiometers and switches—
Standard tolerance set £10-57
Superior tolerance set £18-04
Stereo PCB (as published) £2-20
Regulated Power Supply:
Set of resistors, capacitors and preset £4-58
Printed circuit board 72p

SIGNAL GENERATOR

SEND S.A.E. FOR DETAILS

VOLTAGE CONTROLLED FILTER (P.E. Oct. 74)

An independently designed VCF that can be used with the P.E. Synthesiser.

Component set £3-41
Printed circuit board £1-10

RHYTHM GENERATOR

Programmable for 84,000 rhythm patterns from 8 effects circuits (high and low bongos, bass and snare drums, long and short brushes, blocks and cymbal), and with variable time signatures. Really fascinating and useful! (Published in P.E. Mar./Apr. 1974).

NOW AVAILABLE WITH ALTERNATIVE INDEPENDENTLY DESIGNED PRE-AMPS AND MIXER GIVING EVEN GREATER VERSATILITY.

Full details of component sets, PCB's and discounts are in our list—send S.A.E.

SOUND BENDER (P.E. May 74)

A multi-purpose sound controller, the functions of which include envelope shaper, tremolo, voice operated fader, automatic fader and frequency-doubler.

Component set for above functions (excl. sw's) £5-86
Printed circuit board £1-44

Optional extra—additional Audio Modulator, the use of which, in conjunction with the above component set, can produce "jungle-drum" rhythms.

Component set (incl. PCB) £2-10

PHASING UNIT (P.E. Sept. 73)

A simple but effective manually controlled unit for introducing the "phasing" sound into live or recorded music.

Component set (incl. PCB) £2-20

PHASING CONTROL UNIT (P.E. Oct. 74)

For use with the above Phasing Unit to automatically control the rate of phasing.

Component set (incl. PCB) £3-50

P.E. JOANNA

The new Electronic Piano published in P.E., series commencing May 1975. Send S.A.E. for our details and discounts.

WIND AND RAIN UNIT

A manually controlled unit for producing the above-named sounds.

Component set incl. PCB £2-40

OTHER PCBs (all "as published") While stocks last

Bench Power Supply (P.E. Sept. 74) 80p
Digital Power Supply (P.E. Aug. 72) 50p
Electronic Piano
Pre-amp PCB (P.E. Oct. 72) 95p
Pitch PCB (P.E. Nov./Dec. 72) £1-50
Power Supply PCB (P.E. Oct. 72) 65p
Gemini Stereo Tuner (P.E. June 72) £1-50
Power Slaves (P.E. Aug. 74):
Power Supply PCB 55p
Rondo:
CBS SQ Decoder PCB (P.E. Sept. 73) 60p
Pre-amp PCB (P.E. Oct. 73) 60p
Tone, Balance and Vol-control PCB (Oct. 73) £1-50
Triffid i.c. Radio (P.E. Feb. 73) 60p

BIOLOGICAL AMPLIFIER (P.E. Jan./Feb. 73)

Multi-function circuits that, with the use of other external equipment, can serve as lie detector, alphaphone, cardiophone, etc.

Pre-Amplifier Module
Component set and PCB £3-48
Basic Output Circuits
Combined component set with PCBs, for alphaphone, cardiophone, frequency meter and visual feed-back lamp driver circuits £4-96
Audio Amplifier Module
Type PC7 £5-50

PHOTOPRINT PROCESS CONTROL

(P.E. Jan./Feb. 72)

For colour and B & W, an indispensable dark-room unit for finding exposure, controlling enlarger timing, and stabilising mains voltage.

Component set (excl. meter) £8-85
Printed circuit board £1-60
Panel meter (1mA) £3-50

ENLARGER EXPOSURE METER AND THERMOMETER (P.E. Sept. 73)

Dual-purpose dark-room unit with good accuracy.

Component set with PCB but excl. meter £4-00
Panel meter (100µA) £3-50

P.E. MINISONIC

A portable, battery or mains operated, miniature sound synthesiser, with keyboard circuits. Although having slightly fewer facilities than the large P.E. Synthesiser, the functions offered by this design give it great scope and versatility.

Full details of component sets, printed circuit boards and discount facilities are in our list. Send S.A.E.

REVERBERATION UNIT (P.W. Nov./Dec. 72)

A high quality unit having microphone and line input pre-amps, and providing full control over reverberation level.

Component set (excl. spring unit) £6-82
Printed circuit board £1-40
9 inch spring unit £4-95
Panel meter (50µA) (optional) £3-50

ULTRASONIC TRANSMITTER-RECEIVER

(P.E. May 1972)

A highly sensitive, tight-beam, long-range, "invisible beam" detection circuit with numerous applications.

Component set with PCBs but excluding transducers £4-40

SEMICONDUCTOR TESTER (P.E. Oct. 73)

Essential test equipment for the enterprising home constructor.

Set of resistors, capacitors, semiconductors, potentiometers, makaswitches and PCB £8-56
Panel meter (500µA) £3-50

PCB LAYOUT-AND CIRCUIT DIAGRAMS SUPPLIED WITH ALL PCBs DESIGNED BY PHONOSONICS

COLOUR CODE IDENTIFICATION SUPPLIED WITH MOST KITS AND AS PART OF LIST

ALL PCBs ARE FIBRE-GLASS, DRILLED AND TINNED

Semiconductors	BFY50	22p	2N3703	12p	Integrated Circuits	Zeners	Electrolytic Capacitors (µF/V)	Polyester (µF)	Tantalum (µF/V)		
AC128	29p	BFY51	22p	2N3704	12p	3-3V 400mW	0-47/63V	0.01	3p	0.1/35	12p
AC178	29p	BFY52	22p	2N3819	35p	3-3V 400mW	1-0/63V	0.015	3p	0.22/35	12p
BC107	13p	BSY95A	22p	2N3823E	39p	4-7V 1W	1-5/63V	0.022	3p	0.47/35	12p
BC108	13p	MJE2955	118p	2N4080	12p	5-8V 1.3W	2-2/63V	0.033	3p	1.0/35	12p
BC109	13p	MJE3055	75p	2N4817	39p	8-2V 400mW	10/25	0.047	3p	1.5/35	18p
BC147	12p	NK70033	112p	2N5245	51p	9-1V 400mW	10/25	0.068	3p	2.2/35	12p
BC149	12p	OC28	69p	2N5277	45p	6-8-40	10/25	0.1	5p	10/16	18p
BC149	12p	OC71	14p			11V 1W	10/25	0.15	5p	15/3	18p
BC149	12p	OC84	25p			12V 400mW	10/25	0.22	5p	22/16	18p
BC157	13p	ON42	69p	1N814	4p	12V 1.3W	10/25	0.33	3p	15/3	18p
BC158	13p	ZTX107	12p	1N4001	6p	18V 400mW	15/40	0.47	9p	22/16	18p
BC159	13p	ZTX503	15p	1N4002	6p	20V 400mW	22/25	0.88	11p	47/18V	25p
BC182L	12p	ZTX531	23p	1N4004	6p	18V 1W	22/25	1.0	14p	47/18V	25p
BC204	12p	2N708	13p	1N4005	6p	20V 400mW	22/25	2.2	24p	100/3	18p
BC204	12p	2N814	22p	1N4007	6p	20V 1.3W	33/6				
BC298C	14p	2N1304	22p	OA91	7p	27V 400mW	33/6				
BC298C	14p	2N2219	37p	OA200	7p		33/50				
BC213	15p	2N2825	37p	OA202	8p		47/10				
BC478	22p	2N2807	22p	15J50	11p		47/25				
BCY71	22p	2N3054	69p	15J50	11p		47/40				
BF178	49p	2N3702	12p	ZIL (ZLU)	75p						

LIST
Send S.A.E. with all U.K. requirements for free list giving full details of PCBs, kits, and other components. Overseas enquiries for list: Europe—send 20p. Other countries—send 30p.

POST AND HANDLING
U.K. add 22p.
Optional: Fee for compensation against loss or damage in post (U.K., Eire & C.I. only): 35p.

Overseas—will be charged extra, minimum charge 70p. Details of kit weights, and postage rates will be sent with list.
Eire and Channel Isles classify as overseas for posting purposes.

VAT
Add 25% (or current rate if different) to full total of goods, post and handling. Overseas—VAT does not currently apply.

PHONOSONICS, DEPT. PE38, 25 KENTISH ROAD, BELVEDERE, KENT DA17 5BW
MAIL ORDER AND C.W.O. ONLY
DON'T FORGET VAT!

Don't miss your copy of HENRY'S NEW 1975 CATALOGUE



only 50p Plus 15p P&P

- ★ OVER 5,000 ITEMS - largest UK range of electronic components for home constructors.
- ★ 200 PAGES - every aspect of electronics and components for amateurs and hobbyists - kits, projects, test gear.
- ★ DOZENS of new lines and new ranges.
- ★ MANY price reductions throughout the new Catalogue.
- ★ A Discount Voucher with every copy, worth 50p.

ALL PRICES INCLUSIVE OF VAT

Write now for your copy, enclosing 65p remittance.

NOW OPEN SUPERMARKET, BROWSE ROUND THE NEW SUPERMARKET AT 404 EDGWARE ROAD



Prices correct at time of preparation Subject to change without notice £ 6 0 6

ELECTRONIC FOOTBALL AND TENNIS WITH THE FABULOUS

VIDEO SPORT ON YOUR OWN TV

Play three exciting electronic ball games. FOOTBALL, TENNIS, HOLE IN THE WALL on your own TV! Just plug Video Sport into the aerial socket of your TV and away you go. Completely safe for you, your children and your TV. Mains operated.



OUR INCREDIBLE PRICE £35 incl. VAT Demonstrations now in all CENTRES!

AM/FM MODULES LP1179 LP1171

Combined AM/FM tuner modules, together with a small number of R+C, a Ferrite Aerial, make up a sensitive FM/MW/LW tuner. 6 Volts supply, supplied with data and circuit sheets.

LP1171 combined IF strip £4.50.
LP1179. FM front end and AM gang £4.60.
£5.62 the pair.
Suitable Ferrite aerial 87p.



UHF TV TUNERS

825 line receiver UHF transistorised tuners U.K. operation. Brand new. (Post/packing 25p. each). TYPE A variable tuning slow motion drive £3.50. TYPE B 4-button push button (adjustable) £4.60. TYPE C variable tuning £2.90. TYPE D 6-button UHF/VHF tuner £3.75.

BUILD THE TEXAN + FM TUNER TEXAN 20 - 20W STEREO AMP

Features glass fibre PC board. Gardens low field transformer. 6-I.C.s. 10-transistors plus diodes, etc. Designed by Texas Instruments engineers for Henry's and P.W. 1972. Overall size 151 x 21 x 51/2in. Mains operated. Free test sleeve with every kit.

£38.75 (carriage 50p) (also built and tested £46.87).



HENELEC STEREO FM TUNER

Features capacity diode tuning, lead and tuning meter indicators, mains operated. High performance and sensitivity. Overall size in test sleeve 8 x 2 1/2 x 5 1/2in. Complete kit with test sleeve.

£26.25 (carriage 50p) (also built and tested £31.20)

JOIN THE LARGE BAND OF CONSTRUCTORS!

SPECIAL OFFER GARRARD CT4 STEREO CASSETTE TRANSPORT MECHANISM

Features: *Stereo heads *Built in motor stabiliser. *Auto stop + eject. *Pause control. *12V d.c. operation. Robust, precision engineered mechanism based on the "STARR" patented design. Ideal for use in car stereo cassette players, Hi-Fi stereo cassette recorders, industrial and many other applications. Suitable for the "PW" Ascot Stereo Cassette Deck.



£13.50 incl. VAT P. & P. 35p

FREE Send now for our free list No. 36 for our complete range of over 10,000 semiconductor devices at new low prices.



Hi Fi and Electronics Centres Open 9am - 6pm

TRAMPUS

Electronics Ltd. WINDSOR, BERKS. 58/60 GROVE RD. SEND C.N.O. ADD VAT TO ALL PRICES IN U.K. P&P 15p. EXPORTS 80p.

MONEY BACK IF NOT SATISFIED. LARGE STOCKS. LOW PRICES. ALL BRAND NEW TOP GRADE FULL SPEC DEVICES. CALLERS WELCOME. CATALOGUE/LIST FREE SEND S&A. BARCLAYCARD & ACCESS * POST.

Digital Displays

SLA7 RED LED 0.3" 709 DIL4 29p
TIL 209 WITH CLIP RED 15p ea
GREEN&YELLOW £1.40
JUMBO LED 0.6" 747 709 T099 23p
DISPLAY £2.25 ea
3015F 0-9DP £1 ea.
ZENON FLASH TUBE £4. Data 15p.

LEDS red 13P

LEDS 209 STYLE ONLY 13p ea
TIL 209 WITH CLIP RED 15p ea
TIL 211 & CLIP GREEN 29p ea
LARGE 0.2" & CLIP RED 17p ea
LARGE 0.2" CLIP GREEN 30p ea
209 STYLE OR .2"ORANGE 39p ea
INFRA RED LED £1.2N5777 33p.

PHOTO IC 81P

TEC12 PHOTO AMP/SCMITT/RELAY DRIVER or LED TTL INTERFACE 81p



FLUORESCENT LIGHTS 12V MADE IN UK 8 WATT 13" £3. 13W 22" £3.50

DIGITAL CLOCK

IC AY51224 4 DIGIT CLOCK £3.75
MM5311/4 6 DIGIT CLOCK £7

CASSETTE mechanics £13.75

NEW 8tk CARTRIDGE MECHANISM £8
STEREO CASSETTE MECHANISM £13.75
Suitable for 'PW ASCOT' recorder with heads etc. SEND 15p for DATA

INTEGRATED CIRCUITS

709 DIL4 29p	LM377 2x2Wc2.87
555 TIMER 54p	LM380 2W AF 89p
703 RF/IF 28p	LM381 2xPre £2
709 T099 23p	LM3900 4xOPA69p
709 DIL 14 28p	MC1303 £1.20
710 DIL 14 34p	MC1306 49p
723 Reg. 54p	MC1310ALEDc2.65
741 DIL 8 27p	MC1312 SQ £2.10
710 DIL 14 29p	MC1330 69p
741 T099 29p	MC1339 2xPre £1
747 2x741 70p	MC1350 55p
748 DIL 8 33p	NE536 fetOPA £2
7805 5V £1.40	NE540 Driver £1
7812 & 15 £1.40	NE550 2vRef 79p
76013 6W AF £1	NE555 Timer 55p
8038 SIG GEN £3	NE556 2x" £1.20
CA3028 £1	NE560 PLL £3.15
CA3045 55p	NE561 PLL £3.15
CA3048 £2	NE562 PLL £3.19
CA3052 £1.50	NE565 PLL £2.69
CA3054 £1	SN72709 709 28p
LM300 2-20V £2	SN72741 741 26p
LM301 OPA 45p	SN72748 748 33p
LM304 0-40V £3	SN76660 1F £1
LM307 OPA 49p	SN76611 1F £1.25
LM308 H4Bo 95p	TAD110 & 1F £2
LM309K 5V £1.48	TBA810 7WAF 99p
LM372 IF £1.80	ZN414 RX £1.08

SPECIAL OFFERS

2N3055 FULL HIGH SPEC 115W 37p
741C 8PIN DIL 27p. MFC4000B 33p
NE555 TIMER 55p. ZN414 RX £1.09
BC109 9p. 2N3819e 16p. BFY51 15p

7400 TTL

7400 GATES 13p	7473/74/76 29p
7404 INVERT 17p	7475 45p
7401/2/10etc14p	7490 52p
7413 SCMITT 31p	7491/2/3/4 59p
7440 BUFFER 14p	74100 74175 £1
7444 DRIVER 89p	74121 35p
7447 DRIVER 89p	74123 35p
7470 & 7472 29p	74141 (&7441) 73p

TRANSISTORS & DIODES

Price each	MATCHING
AC127 & 128 16p	1NS, RUSH SET10p
AC187 & 188 19p	TIP 41 70p
AD149 43p	TIP 42 85p
AD161 & 162 33p	TIP 2955 90p
BC107 & 108 9p	TIP 3055 55p
BC109 10p	TIS43 see 2N2646
BC147/8/9 10p	ZTX109&301 13p
BC157/8/9 12p	1N4001 4 7p
BC167/8/9 12p	1N4004 & 4p
BC177/8/9 18p	1N4148 & 914 4p
BC182/3/4A&L10p	2N697 14p
BC212/3/4A&L11p	2N706&8 11p
BCY70/1/2 17p	2N2646 UJT 32p
BD131 & 132 39p	2N2904 & 5 20p
BRF51 23p	2N2926royg 9p
BRF50/51 23p	2N3053 17p
BRF88 250V 29p	2N3055 115W 37p
BFY50/1/2 15p	2N3563 & 64 16p
BSX19/20/21 16p	2N3614 49p
MJE2955 90p	2N3702 & 3 9p
MJE3055 65p	2N3704 & 5 10p
MPU131 PUT 49p	2N3706 & 7 9p
OAG1 OAG1 6p	2N3708 & 9 8p
OAG1 & OAG1 6p	2N3710 & 11 10p
TIP 29 & 30 52p	2N3819E FET 16p
TIP 31 & 32 69p	2N3823E FET 17p
	2N3904/5/6 15p

NEW TRAMPUS FULL SPEC PAKS

PAK A 10 RED LEDS our choice £1	PAK B 4 741 OP AMP £1
PAK C 4 2N3055 £1 D 12 BC109 £1	PAK E 10 BC182 £1 F 11 2N3704 £1
PAK G 8 BFY51 £1 H 9 2N3819e £1	PAK J 9 2N3053 £1 K 40 1N914 £1
BZY88 400mW 1A/50V SCR 36p	ZENER DIODES 9p TAG1/400 55p
BRIDGE RECT 1A 50V 20p C106 & 7 SCR D1 4A/400V 53p	BR100 DIAC 25p SC146D TRIAC 10A 400V 75p

VERO NEW LOW PRICES!

VERO PINSx36 28p.
COPPER CLAD VEROBORD 0.1"
24"x5" 25p 21x3" 26p. 31x3" 31p.
31"x5" 31p 31x 17" £1.50
DIL IC'S BOARDS 6x4" £1.50
24 way edge connector 60p.
36 way 90P. PLAIN 31"x17" £1.
FACE CUTTER 45p. FEC ETCH PAK 50p

DALopen69p

PRINTED CIRCUIT BOARD KIT £1.69
DECON NO MESS ETCH PAK NEW 69p
DECON DESOLDER BRAID REEL 59p

HEATSINKS

5F/T05 & 18F/T018 5p ea. TV4 15p.
TV3/T03 16p. EXTRUDED 4" 411 29p.
TGS308 GAS DETECTOR £1.80 ea.
LOGIC PROBE TTL TESTER PEN £5

CAPACITORS

CERAMIC 22pf to 0.1uf 50v 5p.
ELECTROLYTIC: 10/50/100 uf in 10v 5p. 25v 6p. 50v 8p. 2u/10v 5p.
1000 uf/25v 18p. 200/500 25v 9p.

POTENTIOMETERS (POTS) AB or EGIN

LN or LOG ROTARY 13p. SWITCH 14p
DUAL 45p. SLIDERS 29p. STEREO 57p
KNOBS 7p. PRESETS 6P/RESISTORS 11p
SWITCHES: SPST 18p. DPDT 25p.

DIN PLUGS ALL 12P. SOCKETS 10P.

ALI CASES AB5/AB7 50p. AB13 65p.
TRANSFORMERS 1A 6v6 or 12v12v
Only £1.34. 100mA type CT 75p.


OIL sockets

TEXAS GOLD
LOW PROFILE ea
8, 14, & 16 PIN 13p
SOLDERCON STRIPS
100 PINS 50p. 1K £3.




I.L.P. (Electronics) Ltd

SHEER SIMPLICITY!

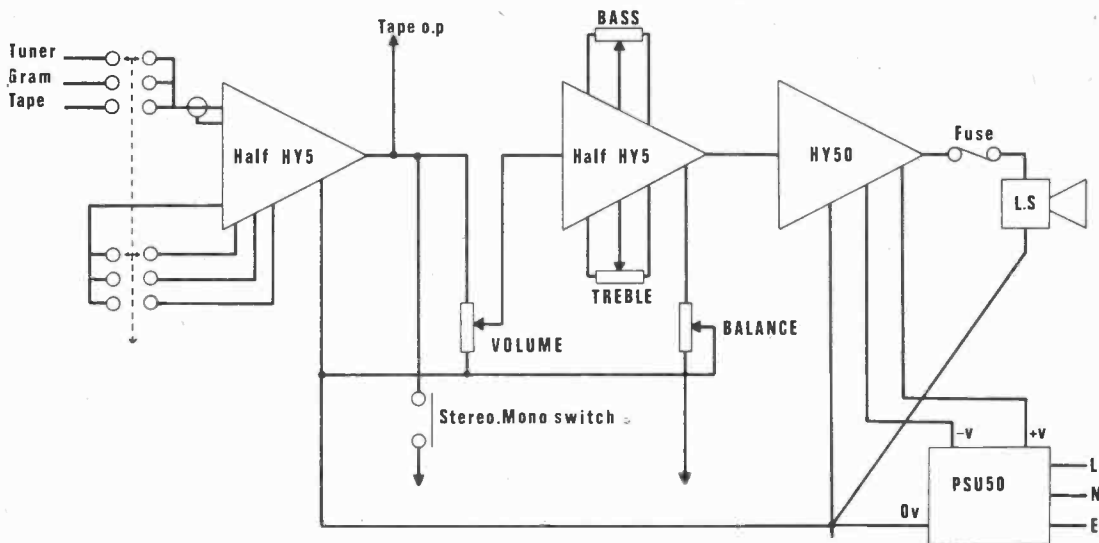

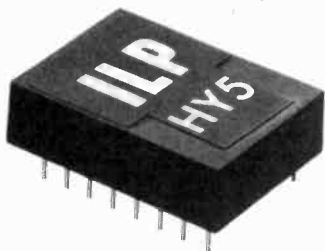MONO ELECTRICAL CIRCUIT DIAGRAM WITH INTERCONNECTIONS FOR STEREO SHOWN



The HY5 is a complete mono hybrid preamplifier, ideally suited for both mono and stereo applications. Internally the device consists of two high quality amplifiers—the first contains frequency equalisation and gain correction, while the second caters for tone control and balance.

TECHNICAL SPECIFICATION

Inputs: Magnetic Pick-up 3mV RIAA; Ceramic Pick-up 30mV; Microphone 10mV; Tuner 100mV; Auxiliary 3–100mV; Input Impedance 47k Ω at 1kHz. Outputs: Tape 100mV; Main output 0db (0.775V RMS). Active Tone Controls: Treble \pm 12db at 10kHz; Bass \pm 12db at 100Hz. Distortion: 0.5% at 1kHz; Signal/Noise Ratio: 68db. Overload Capability: 40db on most sensitive input. Supply Voltage: \pm 16–25V.

PRICE £4.75

+ £1.19 VAT
P. & P. free




The HY50 is a complete solid state hybrid Hi-Fi amplifier incorporating its own high conductivity heatsink hermetically sealed in black epoxy resin. Only five connections are provided: input, output, power lines and earth.

TECHNICAL SPECIFICATION

Output Power: 25W RMS into 8 Ω . Load Impedance: 4–16 Ω . Input Sensitivity: 0db (0–775V RMS). Input Impedance: 47k Ω . Distortion: Less than 0.1% at 25W typically 0–05%. Signal/Noise Ratio: Better than 75db. Frequency Response: 10Hz–50kHz \pm 3db. Supply Voltage: \pm 25V. Size: 105 x 50 x 25mm.

PRICE £6.20

+ £1.55 VAT
P. & P. free

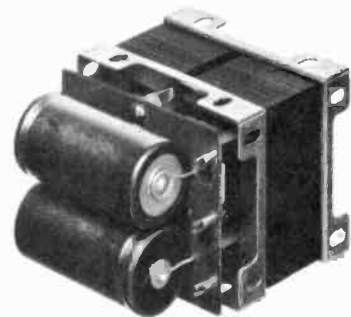

The PSU50 incorporates a specially designed transformer and can be used for either mono or stereo systems.

TECHNICAL SPECIFICATIONS

Output voltage: \pm 25V. Input voltage: 210–240V. Size: L.70, D.50, H.60mm.

PRICE £6.25

+ £1.56 VAT
P. & P. free

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd.
Crossland House,
Nackington, Canterbury,
Kent CT4 7AD.
Tel. (0227) 63218

Please Supply

Total Purchase Price

Enclose Cheque Postal Orders Money Order

Please debit my Access account Barclaycard account

Account number

Name and Address

Signature

BIG Discounts



SPEAKER BARGAINS		£	8in x 5in, Dual cone 8 ohm, 10W	2-85
P. & P. 65p per speaker.				
EMI 13in x 8in 3 or 8 ohm				
Plain	2-20		ELAC 6in 8 ohm Dual cone	2-85
With Co-Axial Tweeter			ELAC 8in 8 ohm Dual cone	3-70
8 ohm only	2-60		ELAC 10in 8 ohm Dual cone	3-75
With Tweeter and Crossover			ADASTRA 10in, 8 or 16 ohm, 10W	3-75
15 ohm	4-25		BAKER GROUP 25 12in, 8 or 16 ohm, 25W	11-80
Type 350, 8 ohm, 20W	8-25		The following, P. & P. 15p per speaker	
6in, 8 ohm, 10W	2-65		6in, 8 ohm, C/Mag.	0-85
8in, 8 ohm, 10W	4-50		2in, 8 ohm or 64 ohm	0-80
8in x 5in, C/Mag. 5W, 3, 8 or 15 ohm	1-70		7in x 4in, 3 or 8 ohm	1-30

TWEETER AND CROSSOVER		£	Dome Tweeter 8 ohm, 30W <th>5-75</th>	5-75
Cone Tweeter 8 or 15 ohm, 10W				
	2-85		Crossovers CN23 (3 ohm), CN28 (8 ohm), CN216 (16 ohm)	1-40
Cone Tweeter 8 ohm, 3W	1-55			P. & P. 0-18
Horn Tweeter 8 ohm, 20W	6-50			

KIT FORM CABINETS, TEAK VENEER		£	13in x 8in cutout <th>6-00</th>	6-00
12in x 12in x 6in with 8in, 8in x 6in or 6in and 3in cutout				
	4-00		17in x 10in x 9in with 7in or	6-00

MICROPHONES		£	TW209 uni-dir <th>5-80</th>	5-80
CM170 Planet stick metal, switch crystal				
	1-55		CONDENSER MIKE 600 ohm, uni-dir	9-80
DM160 Dynamic omni-dir, ball metal	4-90		Case, Stick Mike with R. Control on/off switch (2-5 and 3-6mm J/Ply)	1-85
UD130 50K/600 ohm, uni-dir, ball metal	6-75		Case, Stick Mike with R. Control (Phillips type)	2-00
UD147	9-50			P. & P. 0-30

SOLDERING IRONS		£	spare Bib, etc.) <th>3-40</th>	3-40
ANTEX CN240 15W				
	2-10		X25 25W (low leakage)	2-10
SK1 Kit (15 watt iron, 2				P. & P. 0-15

CARTRIDGES AND STYLII		£	SONOTONE 9TAHC or 9TAHC/G diam. <th>9-00</th>	9-00
ACOS GP91/29C or 38C Stereo comp.				
	1-10		3509 Stereo ceramic diam.	2-00
GP93/1 or 95/1 Stereo crystal	1-50		GOLDRING G850	3-25
GP94/1 or 96/1 Stereo ceramic	1-85		G800	4-10
GP101 Crystal comp.	0-80		G800E	7-10
GP104 Stereo ceramic	1-95			P. & P. 0-15
BSR X5M or 5XH Crystal comp.	1-95		D. Diamond Stylil for above	1-25
BS6M or 8X6H Crystal comp.	2-00		G800/G850	1-95
SC5M Stereo ceramic	2-75		G800E	8-85
				P. & P. 0-08

BATTERY ELIMINATORS		£	12V D.C. input, 6, 7-5, 9V output, 1 amp <th>4-25</th>	4-25
240V input 6, 7-5 or 9 300mA				
	2-95			P. & P. 0-15

TAPES		Stnd.	LP	DP	PLASTIC LIBRARY CASES
5in	50p	65p	1-00p	5in Reels 18p. 5in. 22p. 7in. 25p.	
3in	85p	80p	1-40p		
7in	80p	1-10p	1-80p	P. & P. 1-39p each, 4 or more lot 3p	

LOW NOISE CASSETTES		£	Cassette Head Cleaner <th>0-85</th>	0-85
C60	1-5	6-10	11-20	P. & P. 1-5 each
C90	35p	33p	30p	6-10 lot
C120	85p	43p	40p	11-20 post free
	75p	52p	50p	

BIB ACCESSORIES		£	CALCULATORS (VAT INCLUDED)
SINCLAIR Cambridge £18-95			
SINOLAIR Cambridge £19-95			
with memory Scientific £19-95			
WHARFEDALE SPEAKER BARGAINS		P & P	
Linton 2 Kit (pr.) 20-95 1-50			
Glendale 3 Kit (pr.) 35-95 2-00			
Dovedale 3 Kit (pr.) 58-80 2-00			
Denton 3 Speaker (pr.) 32-00 2-50			
Linton 3 Speaker (pr.) 47-80 2-50			
Dovedale 3 Speaker (each) 44-25 2-50			
Glendale 3 Speaker (pr.) 68-88 3-50			
Kingsdale 3 Speaker (each) 64-95 4-00			

VAT AT THE CURRENT RATE MUST BE ADDED TO ALL ORDERS
Send 25p for COMPLETE CATALOGUE, refundable upon first order.
ALL OUR MERCHANDISE IS FULLY GUARANTEED
Subject to manufacturers' increase and availability

Riversdale Electronics
Mail Order Department PE 8
P.O. Box 470, Manchester M60 4BU

TRANSFORMERS

MAINS ISOLATING

Pri. 120/240V Sec. 120/240V Centre tapped and Screened			
Ref. No.	VA (Watts)	£	P & P
07	20	2-80	38
149	60	4-37	45
150	100	4-89	45
151	200	8-13	53
152	250	9-83	73
153	350	11-88	73
154	500	13-65	91
155	750	20-51	BRS
156	1000	29-15	BRS
157	1500	33-23	BRS
158	2000	37-07	BRS

12 AND OR 24 VOLT

PRIMARY 240-250 VOLTS				
Ref. No.	12V	24V	£	P & P
111	0-5	0-25	1-35	23
213	1-0	0-5	1-74	30
71	2	1	2-29	38
18	4	2	2-86	38
70	6	3	4-12	45
108	8	4	4-56	45
72	10	5	5-14	53
116	12	6	5-52	53
17	16	8	7-28	60
115	20	10	10-29	73
187	30	15	13-59	83
226	60	30	16-83	BRS

30 VOLT RANGE

Secondary Taps 0-12-15-20-24-30			
Ref. No.	Amps.	£	P & P
112	0-5	1-81	30
79	1-0	2-40	38
3	2-0	3-49	38
20	3-0	4-53	45
21	4-0	5-13	53
51	5-0	6-41	53
117	6-0	7-16	60
88	8-0	9-87	67
89	10-0	9-90	73

50 VOLT RANGE

Secondary Taps 0-19-25-33-40-50			
Ref. No.	Amps.	£	P & P
102	0-5	2-58	30
103	1-0	3-38	38
104	2-0	4-68	45
105	3-0	5-81	53
106	4-0	7-60	67
107	6-0	12-10	67
118	8-0	12-98	85
119	10-0	16-99	BRS

60 VOLT RANGE

Secondary Taps 0-24-30-40-48-60			
Ref. No.	Amps.	£	P & P
124	0-5	2-33	38
126	1-0	3-41	38
127	2-0	5-08	45
125	3-0	7-32	60
123	4-0	8-75	67
40	5-0	9-75	73
120	6-0	11-30	85
121	8-0	15-00	BRS
122	10-0	17-52	BRS
189	12-0	19-98	BRS

AUTO TRANSFORMERS

Ref. No.	VA (Watts)	Auto Taps	£	P & P
113	20	0-115-210-240	1-67	30
64	75	0-115-210-240	2-90	38
4	150	0-115-200-220-240	4-12	45
66	300	"	5-82	53
67	500	"	8-82	67
84	1000	"	13-68	91
93	1500	"	18-11	BRS
95	2000	"	24-20	BRS
73	3000	"	35-09	BRS

CASED AUTO TRANSFORMERS

240V mains lead input and U.S.A. 2-pin outlets. 20VA £3.23 P & P 38p 113W
500VA £10.45 P & P 80p 67W
1000VA £17.51 BRS 84W

HIGH VOLTAGE MAINS ISOLATING

Prim. 200/220 or 400/440 Sec. 100/120 or 200/240			
VA	Ref.	£	P & P
60	243	4-37	63
350	247	10-41	95
1000	250	27-06	BRS
2000	252	41-07	BRS

MINIATURE TRANSFORMERS

with Screens				
Ref. mA	Volts	£	P & P	D
238	200	3-0-3	1-54	10
212	1A, 1A	0-6, 0-6	1-84	30
13	100	9-0-9	1-41	13
235	330, 330	0-9, 0-9	1-56	19
207	500, 500	0-8-9, 0-8-9	1-92	30
208	1A, 1A	0-8-9, 0-8-9	3-30	38
236	200, 200	0-15, 0-15	1-43	19
214	300, 300	0-20, 0-20	1-93	30
221	700 (D.C.)	20-12-0, 12-20	2-17	38
206	1A, 1A	0-15-20, 0-15-20	3-46	38
203	500, 500	0-15-27, 0-15-27	3-00	38
204	1A, 1A	0-15-27, 0-15-27	3-85	38

BRIDGE RECTIFIERS

50V 2A	30p
100V 2A	35p
200V 1A	40p
400V 4A	60p
600V 2A	45p
10APM 7A6 500V	£2.35

POWER UNITS

A125 6-9V at 200mA in moulded case forming a 2-pin 5A plug £2.45. P & P 25p
CC12-05 Output Switched
3-4-5-6-7-5-9-12V at 500ma. £4.08. P & P 30p

METERS

AVO 8 MK5	£50-80
AVO 72	£19-75
U4313*	£11-80
U4315*	£13-85

*(USSR) inc. steel case P & P 95p

Mains Keynectors

£3-25	P & P 25p
-------	-----------

Mains Timer

Delay 1-30 minutes (Adjustable)	£5-95
	P & P 25p

CARBON FILM RESISTORS

1/2W 10 ohm-1 Mohm
90p per 100 inc. P & P

CAPACITORS

MINIATURE CERAMIC
50V 22pf-0.047mfd 30p per DOZ.
PAPER (METAL CASED)
1000V 0.01-0.025-0.05-0.1mfd
85p per DOZ. P & P 15p

PLEASE ADD VAT

INCLUDING P. & P.
ELECTROSIL and SEMI-CONDUCTOR STOCKIST. Send stamp for catalogue

Barrie Electronics Ltd.
3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/8
NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST.

TRANSISTORS	VOLTAGE REGULATORS
BC204 11p	UA7815 220p
BC209C 11p	723 180p
BC182 10p	
BC184 11p	ARRAYS
BC212 14p	CA3046 85p
BC214 16p	CA3096AE 120p
BC213 15p	
BC213L 15p	OP. AMPS
ZTX300 15p	709/8 Dip 39p
ZTX500 17p	710/TOS 39p
2N2484 51p	741 28p
2N2904 30p	748 48p
2N2905 27p	FETMOPA 450p
2N2219 22p	
2N3054 100p	SPECIAL PURPOSE LINEARS
2N3055 50p	SG3402N 174p
	SG3402T 174p
FETS	SG1495D 290p
2N3819 46p	MFC6040 100p
2N5459 60p	
DIODES	T.T.L.
1N5401 21p	7402N 38p
1N914 5p	7410PC 24p
BA148 25p	7420N 24p
1S150 12p	7430PC 23p
1G7 10p	7473N 48p
	7475N 75p
NOISE DIODES	7476N 49p
Z1J 75p	7489N 860p
Z1M 120p	7493PC 85p
	REC46 255p
RECTIFIERS	REC70 40p
REC41A 120p	EA100/10 100p
REC46 255p	MDA942A/1 210p
REC70 40p	
EA100/10 100p	
MDA942A/1 210p	

P.E. POWER SLAVES
Special components available while stocks last.

High Voltage
MPSL01 39p; MPSL51 41p; MPSU07 89p; MPSU57 85p; SDT9203 150p.

Constantan Wire
0.03 ohms/cm as specified for the **POWER SLAVES**. 20cm lengths 10p.

VERO CARD FRAME CASE SYSTEM
As first advertised in P.E. May '75 Issue. Build your modular project into this superbly styled economically priced case system. Send for illustrated leaflet and price list.

VAT AT CURRENT RATE SHOULD BE ADDED TO FINAL TOTAL OF ORDER

LISTS
New lists are available for the:

P.E. SOUND SYNTHESIZER;
P.E. MINISONIC

Please include 7p stamp or 9 x 4in S.A.E. with all requests for lists or information.

POTS GALORE
24mm Carbon without switch. All values log. or lin. 5kΩ to 1MΩ 25p each
Wirewound 1W semi-precision. All values 10Ω to 25kΩ 82p each
Min. horiz. carbon presets, 100Ω to 2.2MΩ 10p each
Cermet presets, horiz. mtg., 100Ω to 1MΩ 45p each
Helical 10 turn W/W, 1kΩ, 5kΩ, 10kΩ £3.40 each

PE MINISONIC

MINISONIC P.C.B.'S

EA008a (Main Board), £3.35. Post free.

EA008b (Power supply and Temp. Stabilisation) £1.86. Post free.

MINISONIC COMPONENT KITS—PRICES ARE DOWN

V.C.O. (2 required) £3.07
V.C.F. (1 required) £4.24
ES/V.C.A. (2 required) £4.98
Voltage Ref. £0.54
Ring. Mod. (1 required) £3.62
Noise Gen. (1 required) £1.64
Kbd. Control (1 required) £3.70
HF Osc. and Det. £1.80
Power Amps £2.41

CASSETTES NEW !!!

"SYMBIOSIS"

a companion tape to Malcolm Pointons latest article on using the Minisonic. "INTRODUCING THE MINISONIC".

Each tape £1.06, U.K. post free. One of each for £1.86.

All above prices are for single kits of each type and include P. & P. Full details are included in lists.

Miscellaneous Items

5 way 180° DIN sockets 27p
5 way 180° DIN plugs 34p
Battery connectors 9p/pair
Hook up wire, 36 colours, ½ metre of each 70p
Min. DPDT toggle switch £1.20

SAVE BY PURCHASING A COMPLETE SET OF KITS AS DETAILED TOGETHER WITH SWITCH, BATTERY CONNECTORS, HOOK-UP WIRE AND P.C.B.

Price £38. U.K. post free.


RESISTORS
Triple rated high stability carbon film, 7p for 5
Stocked in E24 values from 4R7 to 3M9
0.5W metal oxide, 16p for 5
E12 values from 10R-1M

VERO CARD FRAME CASE SYSTEM
As first advertised in P.E. May '75 Issue. Build your modular project into this superbly styled economically priced case system. Send for illustrated leaflet and price list.

VAT AT CURRENT RATE SHOULD BE ADDED TO FINAL TOTAL OF ORDER

EATON AUDIO
P.O. BOX 3, ST. NEOTS
HUNTINGDON, CAMBS. PE19 3JB

TERMS: MAIL ORDER ONLY. C.W.O.
Cheques or P.O.'s payable to Eaton Audio. Orders over £5 free of P. & P. Otherwise please add 10p in the £1.



4-STATION INTERCOM



£16.15

Solve your communication problems with this system with this system (1 master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft and other accessories. P. & P. 65p.

MAINS INTERCOM NEW MODEL
No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £28.91 per pair. P. & P. 65p.

NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



ONLY £11.95 + VAT 96p

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/off switch, volume. Direct tape recording model at £12.95 + VAT £1.04. P. & P. 65p. 10-day price refund guarantee.

WEST LONDON DIRECT SUPPLIES (PE8)
169 KENSINGTON HIGH STREET, LONDON, W.8

INTERLOCKING PLASTIC STORAGE DRAWERS



DISCOUNT PRICES

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

BUY AT DISCOUNT PRICES!

SINGLE UNITS (1D) (5ins x 2½ins x 2½ins). **DOUBLE DOZEN.**

DOUBLE UNITS (2D) (5ins x 4½ins x 2½ins). **£3.50 DOZEN.**

TREBLE (3D) £3.50 for 8.

DOUBLE TREBLE 2 drawers, in one outer case (6D), £4.90 for 8.

EXTRA LARGE SIZE (6D1) £4.50 for 8.

PLUS QUANTITY DISCOUNTS!
Orders over £20, less 5%.
Orders over £60, less 7½%.

PACKING/POSTAGE/CARRIAGE: Add 50p to all orders under £10. Orders £10 and over, please add 10% carriage.

QUOTATIONS FOR LARGER QUANTITIES
Please add 8% V.A.T. to total remittance

FLANLIE (Dept. PE8), 124 Cricklewood Broadway, London, N.W.2
Tel. 01-450 4844

SOLID STATE HOBBY CIRCUITS
1975 ed.

by R.C.A. Price £1.25

UNIQUE IC OP-AMP APPLICATIONS by W. G. Jung Price £2.70

BEGINNER'S GUIDETO TRANSISTORS by J. A. Reddihough Price £2.00

INTRODUCING ELECTRONIC SYSTEMS by I. R. Sinclair Price £1.65

BEGINNER'S GUIDE TO ELECTRONIC WIRING by F. Guillou Price £2.00

INTRODUCING AMATEUR ELECTRONICS by I. R. Sinclair Price £1.40

ELECTRONIC SECURITY SYSTEMS by L. G. Sands Price £3.85

ELECTRONICS AND RADIO AN INTRODUCTION by M. Nelkon Price £3.00

DIGITAL LOGIC BASIC THEORY AND PRACTICE by J. H. Smith Price £1.85

BEGINNER'S GUIDETO ELECTRONICS by T. L. Squires Price £2.10


FIRST STEPS IN TELEVISION by B. Sexton Price £4.75

GETTING THE MOST OUT OF YOUR ELECTRONIC CALCULATOR by W. L. Hunter Price £2.05

★ PRICES INCLUDE POSTAGE ★

THE MODERN BOOK CO.
BRITAIN'S LARGEST STOCKIST of British and American Technical Books
19-21 PRAED STREET LONDON W2 1NP
Phone 01-723 4185
Closed Saturday 1 p.m.

Sinclair IC20

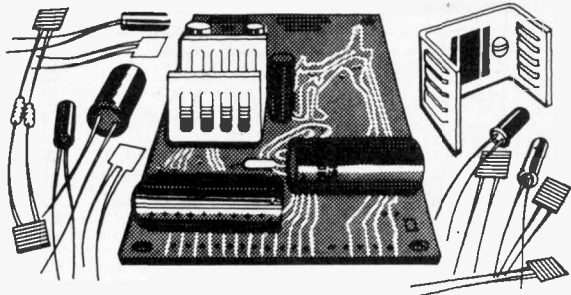

The watts...

The Sinclair IC20 is a revolutionary new 20 watts stereo amplifier kit.

It incorporates state-of-the-art integrated circuits – two monolithic silicon chips each containing the equivalent of over 20 transistors! These deliver 10 W per channel into 4Ω speakers.

And the IC20 has integral short-circuit protection and thermal cut-out – it's virtually indestructible. Use it for converting your mono record player to stereo... for upgrading your existing stereo... or for improving your car radio/tape player.

Its cost? Only £7.95 + VAT!

and the wherefores.



Get the full technical specifications...

See what impartial hi-fi journals thought of its performance...

And read up on the rest of the Sinclair hi-fi range...

It's all in the Sinclair hi-fi range fact-file.

Send for Sinclair's fact-file now!

See if the answer's here – the information on the component you've been looking for.

Simply cut the coupon and

send it to the no-stamp-needed FREEPOST address below.

We'll send you the Sinclair fact-file – giving you all you need to know about IC20, and the rest of the Sinclair hi-fi range.

Plus information about a few extras you're sure to find rather interesting.

You've plenty to gain... so cut the coupon – now!

Sinclair Radionics Ltd,
London Road, St Ives,
Huntingdon, Cambs., PE17 4HJ
St Ives (0480) 64646

Please send me the Sinclair range fact-file immediately

Name _____

Address _____

IC/PE/8/75

To: Sinclair Radionics Ltd,
FREEPOST, St Ives,
Huntingdon, Cambs., PE17 4BR

Please print

sinclair



"I MADE IT MYSELF!"

Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.

Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn—and pave the way to a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio... a Burglar Alarm. You learn Radio and Electronics by doing actual projects you enjoy—making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

No soldering—yet you learn faster than you ever dreamed possible.

Yes! Faster than you can imagine, you pick up the technical know how you need. Specially prepared step-by-step lessons show you how to: read circuits—assemble components—build things—experiment. You enjoy every minute of it!

You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course. **AT NO EXTRA CHARGE!** And this is a course anyone can afford. (You can even pay for it by easy instalments.)

So fast, so easy, this personalised course will teach you even if you don't know a thing today!

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics.

You become a man who makes things, not just another of the millions, who don't understand. And you could pave the way to a great new career, to add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own transistor radio. And after the course you can go on to acquire highpowered technical qualifications, because our famous courses go right up to City & Guilds levels.

Send now for FREE 76 page book—see how easy it is—read what others say!

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

POST TODAY FOR FREE BOOK

To: ALDERMASTON COLLEGE, DEPT. CPE04 | CPE04
READING RG7 4PF


Also at our London Advisory Office, 4 Fore Street Avenue,
Moorgate, London EC2Y 5EJ. Tel: 01-628 2721

Yes, I'd like to know more about your course. Please send me free details—plus your big, 76-page book that tells about all your courses.

NAME _____

ADDRESS _____

POSTCODE _____



BIET

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Practical Electronics Classified Advertisements

RATES: 11p per word (minimum 12 words). Box No. 30p extra. Semi-Display £8.50 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London EC4A 4AD. Tel. 01-634 4451.

RECEIVERS AND COMPONENTS

VALVES. Radio, TV, transmitting, industrial 1930 to 1975. Many obsolete, 2,000 types in stock. List 20p. We wish to purchase new and boxed valves also transistors. COX RADIO (SUSSEX) LTD., The Parade, East Wittering, Sussex. Tel. West Wittering 2023.

DRY REED INSERTS



Overall length 1.85" (Body length 1.1"). Diameter 0.14". Max. ratings 250V D.C. and 500 mA. Gold clad normally open contacts. 75p per dozen; £4.12 per 100; £20.25 per 1,000; £275 per 10,000. VAT and post paid.

G.W.M. RADIO LTD.
68/68 Portland Road, Worthing, Sussex BN11 3BQ

SPECIAL OFFERS. All including VAT at 8% or 25% as applicable. 10 x BC107 11p, 10 x BC108 11p, 12 x BC148 11p, 4 x 741 8 pin DIL 11p, 8 x SN7400 11p, 8 x mixed LEDs 11p, 100 x mixed resistors 11p, 50 x mixed capacitors 11p. Postage free. S.A.E. for lists. Mail order only to: G. NEWMAN, 12 Francis Avenue, St. Albans, AL3 6BX.

TTL AT LOW PRICES!

(Fast delivery. All prices include VAT)

Type	1/24	25/99	Type	1/24	25/99
7400	0-14	0-13	7473	0-33	0-31
7401	0-14	0-13	7474	0-33	0-31
7402	0-14	0-13	7475	0-45	0-44
7403	0-14	0-13	7476	0-34	0-31
7404	0-16	0-15	7480	0-47	0-42
7405	0-16	0-15	7483	0-89	0-80
7408	0-16	0-15	7486	0-30	0-26
7410	0-14	0-13	7489	2-99	2-80
7412	0-16	0-15	7490	0-46	0-44
7413	0-32	0-31	7491	0-74	0-69
7417	0-30	0-29	7492	0-48	0-45
7420	0-14	0-13	7493	0-46	0-44
7427	0-27	0-25	7495	0-61	0-58
7430	0-14	0-13	7496	0-77	0-69
7432	0-27	0-25	74107	0-34	0-31
7437	0-29	0-26	74121	0-34	0-31
7440	0-14	0-13	74123	0-65	0-61
7442	0-69	0-63	74141	0-71	0-69
7445	0-89	0-82	74145	0-86	0-78
7447	0-81	0-79	74151	0-91	0-88
7450	0-14	0-13	74153	0-76	0-72
7451	0-14	0-13	74154	1-60	1-58
7453	0-14	0-13	74157	0-87	0-79
7454	0-14	0-13	74174	0-99	0-90
7460	0-14	0-13	74175	0-99	0-90
7472	0-28	0-25	74181	2-09	1-95

TTL MAY BE MIXED TO TAKE ADVANTAGE OF THE QUANTITY PRICES.

IN4001	5p	ZTX109	13p	ZTX312	14p
IN4002	6p	ZTX300	16p	ZTX313	17p
IN4003	6p	ZTX301	18p	ZTX500	17p
IN4004	7p	ZTX302	24p	ZTX501	18p
IN4148	4p	ZTX303	19p	ZTX502	24p
ZTX107	12p	ZTX310	12p	ZTX503	19p
ZTX108	9p	ZTX311	14p		

Send S.A.E. for latest lists. 10p P. & P. on orders under £2, otherwise POST FREE. ALL GOODS SENT 1st CLASS POST. ALL PRICES INCLUDE VAT (TTL at 8%; NON TTL at 25%).

J. C. JONES

Dept. PE8, 46 BURSTELLARS, ST. IVES, HUNTINGDON, PE17 4XX (Mail Order only)

3 ASS. M.C. METERS £1.30 (40p). **BANK OF 20 NEONS** 74p (11p). **5-FIGURE RESETTABLE COUNTER** 18/22p, works on 12, £2.50 (30p). **BOX WITH 20 x LA2 POT CORES** + 20 1% CAPS £1.50 (50p). **COPPER CLAD FIBRE GLASS PANELS** 12 1/2 x 7in 80p; 18 x 4in 75p c.p. **COPPER CLAD P.A.X. PANELS** 5 1/2 x 5 1/2in. 6 for 65p; 8 x 9 1/2in. 7 for £1; 16 x 9 1/2in. 60p; 12 x 12in. 60p. All P.P. 34 SERIES I.C.s ON PANEL(S) 10 for 80p (10p). List of Valupacs, Computer panels, etc. 12p. Return on purchase. **71B ASSORTED COMPONENTS** £2.20 c.p.

J.W.B. RADIO

2 Barnfield Crescent, Sale, Cheshire M33 1NL Postage in brackets Mail order only

PRECISION POLYCARBONATE CAPACITORS

ALL HIGH STABILITY—EXTREMELY LOW LEAKAGE

440V AC (±10%)	63V Range	±1%	±2%	±5%
0.1µF (1" x 1/2")	50p	0.47µF	56p	46p 36p
0.22µF (1 1/2" x 1/2")	59p	1.0µF	66p	56p 46p
0.25µF (1 1/2" x 1/2")	59p	2.2µF	80p	65p 55p
0.47µF (1 1/2" x 1/2")	71p	4.7µF	11.30	11.05 85p
0.5µF (1 1/2" x 1/2")	75p	6.8µF	11.64	11.29 11.09
0.68µF (2" x 1/2")	80p	10.0µF	12.00	11.60 11.40
1.0µF (2" x 1/2")	91p	15.0µF	22.75	22.15 21.90
2.0µF (2" x 1/2")	11.25			

TANTALUM BEAD CAPACITORS—Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 15V/25V or 35V; 10.0µF at 16V/20V or 25V; 22.0µF at 6V/10V or 16V; 33.0µF at 6V or 10V; 47.0µF at 3V or 6V; 100.0µF at 3V. ALL at 10p each. 10 for 95p, 50 for 24.

TRANSISTORS:	BC183/183L	11p	BFY50	20p
	BC107/8/9	9p	BC184/184L	12p
	BC114	12p	BFY51	20p
	BC147/8/9	10p	BC12/21/2L	14p
	BC153/7/8	12p	BC64/7/8/8A	12p
	BC182/182L	11p	BF194	12p
			OC71	12p
			2N3055	50p

POPULAR DIODES—IN914 6p, 8 for 45p, 18 for 90p; IN918 6p, 8 for 45p, 14 for 90p, 18 for 90p, 24 for £1; IN4148 6p, 6 for 27p, 12 for 45p, 10 for 40p; IN4002 6p; IN4003 8p; IN4004 7p; IN4005 7p; IN4006 8p; IN4007 8p.

LOW PRICE ZENER DIODES—400mV. Tol. ±5% at 5mA. Values available: 3V, 3.3V, 3.6V, 4.7V, 5.1V, 5.6V, 6.2V, 6.8V, 7.5V, 8.2V, 9.1V, 10V, 11V, 12V, 15V, 18V, 18V, 16V, 15V, 12V, 20V, 24V, 27V, 30V, 33V. ALL at 7p each, 6 for 30p, 14 for 84p. SPECIAL OFFER: 100 Zeners for £5.50.

RESISTORS—High stability, low noise carbon film 5% 1/4W at 40°C, 1/4W at 70°C. E12 series only—from 2.2Ω to 2.2MΩ. ALL at 1p each, 8p for 10 of any one value, 70p for 100 of any one value. SPECIAL PACK: 10 of each value 2.2Ω to 2.2MΩ (70 resistors) 45.

SILICON PLASTIC RECTIFIERS—1.5 amp, brand new wire ended DO27: 100 P.I.V. 7p (4 for 26p); 400 P.I.V. 8p (4 for 30p).

BRIDGE RECTIFIERS—2 1/2 amp: 200V 40p; 350V 45p; 600V 65p.

SUBMINIATURE VERTICAL PRESETS—0.1W only: ALL at 8p each: 50Ω, 100Ω, 220Ω, 470Ω, 680Ω, 1kΩ, 2.2kΩ, 4.7kΩ, 6.8kΩ, 10kΩ, 15kΩ, 22kΩ, 47kΩ, 100kΩ, 250Ω, 680kΩ, 1MΩ, 2.5M, 5M.

PLEASE ADD 1p POST AND PACKING ON ALL ORDERS BELOW 45. ALL EXPORT ORDERS ADD COST OF SEA/AIRMAIL.

PLEASE ADD 25% V.A.T. TO ORDERS Send S.A.E. for lists of additional ex-stock items. Wholesale price lists available to bona fide companies

MARCO TRADING

Dept. E.S., The Old School, Edgaston, Nr. Wem, Shropshire
Tel.: Whixall 464/465 (STD 0948 72)
(Props.: Minicost Trading Ltd.)

R.T. SERVICES

(MAIL ORDER ONLY)

77 Hayfield Rd., Salford 6, Lancs.

Tapped Auto Transformer, 240V-110V, 80 watts, £2 P.P. New.

Tapped Auto Transformer, 240V-115V, 200 watts, £4.50 P.P. New.

100 Watt Valve Output Transformer. KT88s, etc. 8 or 15Ω or 100 volt line output, £13.60 P.P.

FM Tuner with R.F. Stage and A.G.C., 3 transistors, neg. earth, 2 1/2" x 2" x 1 1/2" in with circuit, £1.54 P.P.

Crouzet Gear Motors, 30 r.p.m. New, £1.75 P.P.

UHF TV Tuners. Transistorised, £2.10 P.P. Panels with I.C.'s on 8 1/2p per I.C. min. order 10 I.C.'s.

Transformers. 7.5V+7.5V 1/2A, £1.12 inc. P.P. 12-0-12V, 100mA, £1.25 inc. P.P. 9-0-9V, 100mA, £1.25 inc. P.P. 29V 50mA, 95p inc. P.P. 6-0-6V, 100mA, £1.25 inc. P.P.

Transformer. 24 volt, approx. 1 amp + 6.3V CT approx. 500mA, £1.60 inc. P.P.

Transformer. 20 volt, 1 amp, £1.40 P.P.

Transformer. 45 volt, 2 amp, £3.38 P.P. P.C. Board. 5/5, 5 1/2 x 5 1/2 in, 10 for £1.10 P.P. Transistorised Timer. Variable delay. 110 or 250V A.C. input. With instructions. Brand new, £2.25 inc. P.P. Size 3" x 2" x 2".

Power Unit Components Transformer. 18 volt 1 amp F/W bridge rectifier, 2 1250 mfd capacitors, all new £1.60 per kit. P.P. Electrolytic Capacitors, 4,000 MF, 50VW, 4 1/2" x 1 1/2" 90p. inc. P.P. Mixed Pack of C280 series Mullard capacitors. 100 for £1.30 inc. P.P.

CLEARING DISTRIBUTOR STOCKS, transistors, diodes, components, etc. Sample pack 65p incl. postage or send stamp for list. REDHAWK SALES LTD., 10 Maple Lodge Close, Rickmansworth, Herts. Mail order only.

BULK OFFERS

All goods full spec. and marked	BF181	£20.00			
IN4001	£2.50	BC118A	£8.00	BF194	£8.00
IN4002	£2.80	BC147	£8.00	BF195	£8.00
IN4003	£3.20	BC149	£8.00	BSY95A	£8.00
IN4004	£3.60	BC157	£8.00	2G302	£4.00
IN4005	£4.30	BC158	£8.00	2N2646	£4.00
IN4006	£4.70	BC159	£8.00	2N3055	£28.00
IN4007	£5.00	BC181	£10.00	NE555V	£38.00
IN4148	£2.20	BC267	£8.00	709C	£18.00
BC107	£7.00	BC328	£10.00	741C	£19.00
BC109	£7.00	BC548	£8.00	All prices per	
		BF173	£14.00	min. quantity 100	

Ferric Chloride £30 per 100 lb bags (8% VAT). Miniature mains transformers, 100mA sec: 6-0-6V £5/10; 9-0-9V £5/50/10; 12-0-12V £8/10; subminiature 6-0-6V 100mA £8/10; 12-0-12V 50mA £8/10, £30/100. Assorted small value capacitors—ceramic, mica, poly. etc. £28/10,000. Assorted C280 polyester £28/10,000. 10µF 25V PC £2/100; 47µF 40V axial lead £4/100. Minimum Order £5; Carr. Free. Add VAT at the appropriate rate (25%). S.A.E. enquiries.

JUNIPER ELECTRONICS (PE4)

P.O. Box 61, Southampton SO9 7EE

BRAND NEW COMPONENTS BY RETURN, Electrolytics 16V, 25V, 50V, 0.47, 1.0, 2.2, 4.7, 10mfd, 5p; 22, 47, 51p (50V, 6p); 100, 7p (50V, 8p); 220, 8p (50V, 10p); 500, 11p (50V, 18p); 1000/25V, 18p. Subminiature bead-type tantalums. 0.1/35V, 0.22/35V, 0.47/35V, 1.0/35V, 2.2/35V, 4.7/35V, 10/20V, 22/16V, 47/6V, 100/3V, 11p. Mylar Film 100V, 0.001, 0.002, 0.005, 0.01, 0.02, 3p; 0.04, 0.05, 3 1/2p. Mullard tubular polyester 400V E6 series, 0.001-0.022, 3 1/2p; 0.033-0.1, 4 1/2p. Mullard polyester 160V tubular or 250V miniature for vertical mounting E6 series, 0.01-0.047, 3 1/2p; 0.068, 0.1, 4 1/2p; 0.15, 0.22, 6p; 0.33, 7p; 0.47, 9p; 0.68, 11p; 1.0, 14p; 1.5/250V, 18p; 2.2/250V, 22p.

Mullard miniature C333 ceramics 63V E12 series 2% 1.8pF-47pF, 3p; 56pF-330pF, 3 1/2p. Plate ceramics 50V E6 series 470pF-47,000pF, 2p. Polystyrene 63V, E12 series 10pF-1,000pF, 3p; 1,200pF-10,000pF, 4p. Miniature highstab carbon film resistors 1/4W E12 series 5% (10% over 1MΩ) 1Ω-10MΩ, 1-2p; IN4002, 6p; IN4006, 8p; IN4148, 4p. Postage 10p. Prices VAT inclusive. THE O.R. SUPPLY CO., 127 Chesterfield Road, Sheffield, S8 0RN.

CMOS SPECIALISTS

(Sales, consultancy)
Trade-export-enquiries welcome

CD4000AE	Dual 3 1/2 NOR + INVERTOR	35p
CD4001AE	Quad 2 1/2 NOR	35p
CD4002AE	Quad 4 1/2 NOR	35p
CD4011AE	Dual 2 1/2 NAND	35p
CD4012AE	Dual 4 1/2 NAND	35p
CD4013AE	Dual D-type flip-flop + S&R	66p
CD4018AE	Quad bilateral switch	72p
CD4017AE	Decade counter divider	17p
CD4021AE	6 stage static shift register	172p
CD4023AE	Triple 3 1/2 NAND	35p
CD4025AE	Triple 3 1/2 NOR	35p
CD4027AE	Dual J-K master slave flip-flop	99p
CD4048AE	Micropower phase locked loop	248p
CD4047AE	Mono/stable multivibrator	159p
CD4049AE	Hex inverter/buffer	81p
CD4050AE	Hex buffer (non-inverting)	81p
CD4071BE	Quad 2 1/2 OR	45p
CD4072BE	Quad 4 1/2 OR	45p
CD4073BE	Triple 3 1/2 AND	45p
CD4075BE	Triple 3 1/2 OR	45p
CD4081BE	Quad 2 1/2 AND	45p
CD4082BE	Quad 4 1/2 AND	45p
CD4511BE	BCD to 7 segment latch decoder driver	287p
5082-7740	7 segment LED display	199p

Data sheets 5p. Add 8% VAT + 20p P. & P. All devices guaranteed to manufacturers specifications

CMOS SPECIALISTS

29 Manchester Street, London W1 (Mail order only)

BETA DEVICES

MANUFACTURERS BRANDED PRODUCTS

TRANSISTORS	IC's	DIODES & RECT.
AC187/188	709C TO99 0-80	1N914 0-04
FR.	709C D.I.L. 0-80	1N4148 0-04
BC107/1	741C TO99 0-36	0A202 0-09
BC108	741C D.I.L. 0-38	1N4001/2 0-05
BC109C	723C D.I.L. 0-80	1N4003/4/5 0-06
BC147/8	747C D.I.L. 0-85	1N4006/7 0-08
BCV70/1/720-13	748C D.I.L. 0-36	BRIDGES
BFX86/87/88	555-8-Pin 0-50	W01 1A 0-20
	556-14-Pin 1.00	W02 1A 0-20
BFY60	0-18	800V 0-30
BFY61/52	0-12	ZENERS
OC28	0-45	2N3055 0-38
OC35	0-35	D.I.L. SOCKETS
2N2646	0-30	8-Pin 0-12
2N3053	0-14	14-Pin 0-12
TIP29A	0-49	16-Pin 0-14
TIP31A	0-61	
TIP41A	0-74	
TIP42A	0-90	

C.W.O. PLUS P.P. 15p TO BETA DEVICES
4 High Bridge Street, Waltham Abbey, Essex

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact **COLES-HARDING & CO.**, P.O. Box 5, Frome, Somerset. Immediate cash settlement.

AXIAL PRODUCTS LTD.

DEPT. 28
23 AVERY AVENUE
HIGH WYCOMBE
BUCKS.

AXIALS
4 ELEMENT FM STEREO
£2.80 + 25% VAT + 50 P. & P.
18 ELEMENT TV
£2.00 + 25% VAT + 50 P. & P.
10 ELEMENT TV
£1.75 + 25% VAT + 50 P. & P.

New design, superior quality, including mounting bracket and full instructions.

AC127/8	12p	Zener Diodes	9p	TTL IC's	14p
BC107	9p	1W	15p	7400	14p
BC108	9p	1N914	4p	7403	14p
BC109	10p	1N4001	5p	7404	18p
BC113	10p	1N4002	5p	7405	18p
BC147	9p	1N4003	5p	7410	18p
BC148	9p	1N4004	5p	7412	18p
BC149	10p	1N4007	7p	7413	32p
BCV70	18p	1N4148	7p	7417	32p
BF194	10p	8 Pin DII	7p	7442	90p
BF195	10p	555	55p	7447	90p
BFY50	15p	741	28p	7474	33p
BFY51	15p	14 Pin DII	15p	7490	45p
2N2906	20p	741	28p	7491	35p
2N2928	9p	8 Pin DII	15p	7492	105p
		8kt			

Components add 25% VAT (except TTL 8%) + 10p P. & P. over £2 free P. & P.
C.W.O. MAIL ORDER ONLY

UNUSED. Guaranteed integrated circuits. 7446 60p, 7442 40p, 7413 20p. Send S.A.E. for list. PHILLIPS, 1 Lower Marshfield, Minehead, Somerset.

LED S

RED	0-125	0-2	INFRA RED
GRE	15p	19p	550uW
YEL	27p	33p	Axial lead 49p
			1.5mW
			TO48 £1-10

OPTO-ISOLATORS

UL74 1.5kV, 150kHz	£1	TO51A	25p	27p	46p
4350 2-5kV, 5MHz	£2-35	TO68 3A	27p	35p	50p

SCR's 50V 100V 400V
TO51A 25p 27p 46p
TO68 3A 27p 35p 50p

TRIAC TO5 2A 400V 50p

VOLTAGE REGS.

2N2926(G)	12p	7805 Plastic	5V
2N3053	15p	5A	£1-50
2N3055	41p	L129 Plastic	5V
2N3702/3/4	12p	600mA	£1-40

BRIDGE RECTS.

2A 50V	30p
2A 100V	30p
2A 200V	41p
2A 400V	46p

ZENERS BZY88 2.7-33V 9p

NE555V 60p
NE556 £1-10
LM380 £1-00
ZN414 £1-10
7400 16p

D.I.L. SOCKETS

8-pin	12p
14-pin	13p
16-pin	14p

OP. AMPS

709 all	25p
741 8-pin	28p
748 D.I.L.	38p

ICs + bushes
T03 TO6 5p
Dalo Pen 70p

PRICES INCLUSIVE + 15p P. & P. (1st class)
ISLAND DEVICES, P.O. Box 11, Margate, Kent

SERVICE SHEETS

SERVICE SHEETS, radio, TV, etc. 10,000 models. Catalogue 24p plus S.A.E. with orders-enquiries. TELRAY, 154 Brook Street, Preston, PR1 7HP.

PROFESSIONAL SERVICES

PATENTS AND TRADE MARKS. KINGS PATENT AGENCY LIMITED (Est. 1886). B. T. King, Director, M.I.Mech.E., Registered Patent Agent, 146a Queen Victoria Street, London, EC4V 5AT. Booklet on request. Tel. 01-248 6161. Telex 883805.

MISCELLANEOUS

FERRIC CHLORIDE. Anhydrous, 95% pure. Double sealed 1lb packs, 75p; 3 for £1-50; 10 for £4-25 inclusive. Trade enquiries welcome. Reductions for quantities. R. VANSITTART, 192 Villiers Road, Willesden, NW2 5PU (01-459 3359).

PRINTED CIRCUIT COPPER CLAD.

Single sided. Quality material. Flame retardant to N.E.M.A. Spec. Paper Base (FR2) $\frac{1}{8} \times 7 \times 5$, 3 for £1. Epoxy Glass (FR4) $\frac{1}{8} \times 7 \times 5$, 2 for £1. Also panels cut to your requirements, quotation by return. Prices include P. & P. Cash with Order.

P. G. OLIVER & CO.
4 Hearsall Lane, Coventry, CV5 6HH.

HARDWARE. Comprehensive range of screws, nuts, washers, etc. in small quantities, and many useful constructors' items. Sheet aluminium to individual requirements, punched, drilled, etc. Fascia panels, dials, nameplates in etched aluminium. Printed circuit boards for this magazine, and other individual requirements, one-offs and small runs. Machine engraving in metals and plastics, contour milling. Send 2 44p stamps for catalogue. RAMAR CONSTRUCTOR SERVICES, Masons Road, Stratford on Avon, Warwick. CV37 9NF.

MAKE MONEY from your hobby by writing articles for magazines and newspapers. Hundreds of outlets. Full details FREE from:

THE WRITING SCHOOL
Dept. PE1, 11 Ludgate Broadway
London EC4V 6DH

GLASS FIBRE P.C.B.s for all projects. Drilled and tinned. Send master and 30p per board plus 5p per square inch. ELECTRO CIRCUITS, 4 Highcliffe Way, Wickford, Essex.

SINTEL

Add 10p P. & P. for orders under £2. Data, and circula where appropriate, supplied with orders or available separately (send 9in x 4in S.A.E.)
ADD 8% VAT—Not 25%

DISPLAYS	CLOCK ICs—PCBs—KIT
DL704(Econ) 0 3in CC £8-25	M55588M Alarm £3-50
DL787 0 3in CA £1-75	PCBs, 8in for above £3-45
DL747 0 3in CA £2-45	PCB for 8 x DL704 £1-35
M5533 3 x 0 12in CC £1-85	8 dig Alarm Kit RH £16-50
M5523M 0 12in CC £8-45	(with case and 15mm LS)
FND500 0 25in CC £1-15	AYS1224 4 digit £4-25

SOLDERCON Pins 100 for 50p. 400-£2. 1,000-£4. 3,000-£10-50

CMOS from RCA and MOTOROLA

CD4001AE	£8-21	CD4023AE	£8-21	CD40719E	£8-30
CD4001AE	£8-21	CD4042AE	£1-37	CD40739E	£8-30
CD4012AE	£8-21	CD4048AE	£8-62	CD4085BE	£1-17
CD4013AE	£8-43	CD4050AE	£8-62	CD4086BE	£1-17
CD4018AE	£8-62	CD4063BE	£2-22	MC14501CP	£8-32
CD4019AE	£8-73	CD4068AE	£1-86	MC14510CP	£1-77
CD4022AE	£1-86	CD4069BE	£8-29	MC14518CP	£1-87

Other displays: IC, RCA CMOS. Resistors etc available send S.A.E. or phone (9.30 to 10 p.m.) for further information.
SINTEL, 53B ASTON STREET, OXFORD Tel (0865) 43203

ENAMELLED COPPER WIRE

S.W.G.	1lb Reel	1lb Reel
10-14	£2-05	£1-15
15-19	£2-15	£1-20
20-24	£2-20	£1-25
25-29	£2-25	£1-30
30-34	£2-35	£1-38
35-40	£2-50	£1-45

All the above prices are inclusive in U.K.
COPPER SUPPLIES
102 Parrswood Rd., Withington, Manchester 20
Telephone 061-445 8753

IC SOCKET PINS for low cost mounting of 2 to 40 pin DILs. 50p (+ 4p VAT) for strip of 100, £1-50 (+ 12p VAT), for 3 x 100, £4 (+ 32p VAT) for 1,000. Instructions supplied—send S.A.E. for sample. 10p P. & P. for orders under £2. SINTEL, 53b Aston Street, Oxford. Tel. 0865 43203.

"PE JOANNA"

BULK COMPONENTS LIST

(page 388 May '75 issue)

EVERYTHING LISTED FOR JUST £44.61 inc. VAT + OUR USUAL DISCOUNT VOUCHERS or WITHOUT DISCOUNT VOUCHERS

£41-61 inc. BY RETURN OF POST
... of course!

These are all top quality brand new components Capacitors and Resistors by Mullard, Diodes by I.T.T etc. For keyboard etc. see our catalogue 40p.
* CT2 Transformer in stock £2.72 inc. VAT *

Maplin Electronic Supplies
P.O. Box 3, Rayleigh, Essex

PCB MANUFACTURERS OFFER: SPECIAL this month, "P.W." Easybuilt organ PCBs in Epoxy/fibreglass, roller-timed and drilled I.P.C. approved, £5-50 (20p) the set. Also full spec., ready to assemble PCBs for "P.W." Tricolour, £1-25 (12p); Tele-tennis (6 PCBs), £3-50 (15p); Telephone exchange, £70 (12p); Derby, 70p (8p). "P.E." ORION with printed layout on PCB, £1-10 (12p); Power slaves (3 PCBs), £1-35 (13p); C.C.T.V. (2 PCBs), £1-40 (15p); Smoke detectors 70p (12p); Digital leaf, Scorpio 2, ferret locator, all 65p (9p). C.W.O. P. & P. in brackets. MANY OTHERS available. S.A.E. for lists. PRODUCTION SPACE FOR PCB production, electroplating, silk-screen printing, tinning plus all ART/GRAPHIC photographic aid design facilities. Estimates by return or phone. W.K.F. ELECTRONICS, Welbeck Street, Whitwell, Worksop, Notts., S80 4TW. Tel. Whitwell 695 (Derbys.). Callers only to 2/3 Station Road.

A.D. ELECTRONICS supply EVERYTHING YOU NEED TO FIT A BURGLAR ALARM

Battery alarm	£14-50
6in Bell, heavy duty	£7-75
H.P.I. battery	£2-45
Flush contact	75p
Surface contact	75p
Large mat	£1-85
Small mat (stair)	£1-25
Key switch	£2-59

A.D. ELECTRONICS
Warbeck Moor
Aintree, Liverpool L9 0HU
051-525 3440

MISCELLANEOUS
CONTINUED PAGE 690

Opportunities in Electronics

Train to be an Electronics Technician

If you are 16-18 years old and would like a career in Electronics, our special 3 year training scheme provides the opportunity you are looking for.

We are offering you the opportunity to become an Electronics Technician in a fast expanding industry with an ever increasing demand for those with the ability to

understand the practical workings of complex electronic equipment. Our scheme includes well paid employment whilst training and day release to attend college to study for the City and Guilds Electronics Technician Certificate.

In addition to a practical interest in electronics you will require 'O' levels or CSE grades in

Maths, Physics and English. Telephone or write to R. F. Honnor, Personnel Manager, G & E BRADLEY LTD., Electral House, Neasden Lane, N.W.10. Tel. 01-450 7811.

BRADLEY
electronics
A LUCAS COMPANY

LADDERS

LADDERS, timber and aluminium. Tel. Telford 588644 for brochure.

FOR SALE

\$100 WORTH 5 CHANNEL R/C EQUIPMENT. Part Built. Aeroplane, engine and accessories. Offers. 051-653 7796.

FOR SALE. Practical Electronics Volume 1 Number 1 to Volume 7 Number 12—Six volumes bound in Easibinders. Offers to FRY, Grove House, Elm Grove, Maidenhead.

PRACTICAL ELECTRONICS from Nov. 1964 (1st issue) to June 1975, £20 the lot. Tel. Leeds 454374.

LABORATORY CLEARANCE. Marconi-Ekco universal impedance bridge, type TF373/B, £10. Advance double-beam oscilloscope, type OS25B, as new £45. Solartron storage type oscilloscope, type QD910, with service manual, requires servicing, £55. Marconi U.S.W. signal generator, type TF390G, £10. Advance signal generator, type D1, £10. Racal SA520 frequency meter, £25. Or £150 the lot. Buyer collects. Phone 01-478 0023 or write 354 Ilford Lane, Ilford, Essex.

WANTED

WANTED. Company to manufacture and market new range of electronic musical instruments (pat. app. for). Tel. Leeds 530306.

TOP PRICES PAID
NEW VALVES AND TRANSISTORS
Popular T.V. and Radio types
KENSINGTON SUPPLIES (B)
367 Kensington Street
Bradford 8, Yorks.

ELECTRONIC CRAFTSMEN

Is your present job routine and uninteresting?

We are a research establishment and our craftsmen are engaged on a wide variety of work in the fields of prototype and small batch wiring and assembly, test and inspection, maintenance fault finding and repair. Why not join us and enjoy working in first class conditions in the country.

Earnings are good and our rates of pay are currently under review. We can offer good housing at low rental (for applicants who live outside the radius of our Assisted Travel Area) together with 3 weeks' paid holiday with holiday bonus, free pension and excellent sick benefit scheme.

Applicants who should have served a recognised apprenticeship or have had equivalent training together with experience in one of the fields detailed should phone Tadley 4111 (STD 073-56 4111), Ext. 5230, or write to:

Industrial Recruitment Officer
(PA/85/PE) Procurement Executive
Ministry of Defence
AWRE Aldermaston
Reading, Berks. RG7 4PR

MRC NEUROLOGICAL PROSTHESES UNIT

Junior Technician

required to work in experimental medical implant laboratory. Hobby experience in electronics and/or mechanics an advantage. School leaver with 4 O levels suitable. Opportunity for day release training. Salary scale £1,176-£1,977.

Applications to:

**THE DIRECTOR
MRC NEUROLOGICAL
PROSTHESES UNIT
DeCrespigny Park, Denmark Hill
London, SE5 8AF
Tel. 01-703 5411**

MEN! £90 p.w. can be yours

Tens of thousands of new computer personnel needed over the next few years alone. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks!

It can pay around £35 p.w. as a starter and can reach over £90 p.w. After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or 'phone TODAY, without obligation.

**London Computer Operators
Training Centre Y38, Oxford Hse.
9-15 Oxford St., W.1. Tel. 01-734 2874**

EDUCATIONAL

TECHNICAL TRAINING.

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers; also self-build radio kits. Full details from: ICS SCHOOL OF ELECTRONICS, Dept. 316, Intertext House, London, SW8 4UJ. Tel. 01-622 9911 (all hours).

CITY & GUILDS EXAMS.

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms. Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from: ICS SCHOOL OF ELECTRONICS, Dept. 315, Intertext House, London, SW8 4UJ. Tel. 01-622 9911 (all hours).

COLOUR TV SERVICING.

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from: ICS SCHOOL OF ELECTRONICS, Dept. 317, Intertext House, London, SW8 4UJ. Tel. 01-622 9911 (all hours).

MISCELLANEOUS CONT'D

DIGITAL CLOCK CHIP, AY-5-1224, with data and circuit diagram, **£3-66** plus VAT. "Jumbo" LED digits (16 mm high), Economy type. DL-747, only **£2-04** each plus VAT, post free. GREENBANK ELECTRONICS, 94 New Chester Road, Wirral, Merseyside, L62 5AG.

12 VOLT 21in 13 watt FLUORESCENT LIGHTING (by THORN/AEI) with diffuser and on/off switch. Ideal, caravan, boat, emergency lighting, etc. Guaranteed



£5-50 inc. VAT and post. List price £7-62 inc. VAT.
SALOP ELECTRONICS Tel. 53298
23 Wyle Cop, Shrewsbury, Shropshire

CLEARING LABORATORY, scopes, recorders, testmeters, bridges, audio, R.F. generators, turntables, tapeheads, stabilised P.S.U.s, sweep generators, test equipment, etc. Lower Beeding 236.

I.C. EXPERIMENTER'S KITS

Learn about modern electronics with our new step-by-step kits. Use and understand digital logic techniques. Kits contain specially selected I.C.'s, Holders, Veroboard, L.E.D.'s, instructions and data. Kit One (Gates) and Kit Two (Flip-Flops) now available, **£2-90** each. P. & P. 10p. Bargain Offer—EXPERIMENTER'S PAK **£2-90** Gates, Inverters, Flip Flops, Counters P. & P. 10p S.A.E. for further details to: **AUTOMATED HOMES**, 69 High St., RYTON, Coventry CV8 3FZ. (Mail Order Only)

LOW COST I.C. MOUNTING. 100 I.C. pin sockets **50p**. Quantity rates. S.A.E. details and sample. 7 and 8 hole plastic supports **5p/pair**. (P. & P. 8p/order). LED (MLED500) **20p** each post free. Quantity rates. P.K.G. ELECTRONICS, Oak Lodge, Tansley, Derbyshire, DE4 5FE.

BUILD YOUR OWN

YOU ARE INVITED TO SEND S.A.E. FOR LISTS ON OUR VERY EXTENSIVE RANGE OF HIGH QUALITY AMPLIFIERS, PRE-AMPS, F.M. TUNERS, INSTRUMENTS, RADIO CONTROL, IGNITION UNITS AND MANY OTHER KITS.

TELERADIO ELECTRONICS
325 Fore St., Edmonton, London N9

SUPERB INSTRUMENT CASE by Bazelli, manufactured from heavy duty PVC faced steel. Hundreds of Radio, Electronic, Hi-Fi enthusiasts and Industrial users are choosing the cases they require from our range. Make your VAT go further with our competitive prices which begin at a low 75p. Examples: Width, Depth, Height, 7" x 7" x 5" **£2-65**; 8" x 10" x 6" **£3-60**; 12" x 8" x 7" **£4**; 12" x 12" x 7" **£4-40**. Over 200 Models to choose from. Prompt despatch. Free literature (stamp would be appreciated). **BAZELLI**, Dept. No. 23, St. Wilfrid's, Foundry Lane, Halton, Lancaster LA2 6LT.

HOME SCIENTISTS

Get the key to a FANTASTIC WORLD of previously UNHEARD-OF PROJECTS. The NEW Boffin catalogue lists LOTS of HIGHLY UNUSUAL, LOW-COST BAR-GAINS, READY-BUILT MODULES.

Here are just a few examples, there are stocks more!

Dazzling MINI-STROBE (pocket size) **£3-50**
PEOPLE DETECTOR **£4-20**
Big-Ear SOUND-CATCHER **£4-20**
Mini DREAM LABORATORY **£4-20**

Don't take our word for it though! GET A COPY AND SEE! SEND ONLY 20p and WE'LL RUSH YOU A COPY (YOU'LL GET THE 'GOODIES' JUST AS QUICKLY TOO!)

BOFFIN PROJECTS
4 Cunliffe Road, Stoneleigh
Ewell, Surrey

(Mail Order U.K. only)

FANTASTIC NEW MICROTEST 80

MEASURES ONLY

90 x 70 x 18mm
ELECTRONIC ZERO Ω



Amazing Value at **£11-95**
8 fields of measurement
and 40 ranges

PRINTED CIRCUIT BOARD IS REMOVABLE WITHOUT SOLDERING

Volts d.c. 8 ranges: 100mV, 2V, 10V, 50V, 200V, 1,000V (20k Ω /V). 2% precision on d.c. and a.c.
Volts a.c. 5 ranges: 1-5V, 10V, 50V, 250V, 1,000V (4k Ω /V)
Amp. d.c. 8 ranges: 500 μ A, 500 μ A, 5mA, 50mA, 500mA, 5A
Amp. a.c. 5 ranges: 250 μ A, 2.5mA, 25mA, 250mA, 2.5A
Ohms 4 ranges: Low Ω , Ω x 1, Ω x 10, Ω x 100 (from 1/10 di Ω until 5M Ω)
V Output 5 ranges: 1-5V, 10V, 50V, 250V, 1,000V
Decibels 5 ranges: -6dB, +22dB, +36dB, +50dB, +82dB
Capacity 4 ranges: 25 μ F, 250 μ F, 2,500 μ F, 25,000 μ F



SUPERTESTER 680R ICE

20,000 Ohm per Volt sensitivity
Fully screened against external magnetic fields
Scale width and small case dimensions (28 x 95 x 35mm)
Accuracy and stability (1% in D.C., 2% in A.C.) of indicated reading
Simplicity and ease of use and readability
Full ranges of accessories

1,000 times overload
Printed circuit board is removable without desoldering
More ranges than any other meter. Ask for free catalogue
Accessories Extra
Accessories (extra) available to convert Microtest 80 and SuperTester 680R into following: LIGHTMETER, GAUSS METER, ELECTRONIC VOLT METER, AMPER-CLAMP, TRANSISTOR TESTER, TEMPERATURE PROBE, PHASE SEQUENCE INDICATOR, Ω x 100k Ω Multiplier, SIGNAL INJECTOR—Send for details.

£18-50

MORE RANGES FOR LESS MONEY!

AC/DC Multimeter type U4324

A-DC 0-06-3A-6 Ranges
A-AC 0-3-3A-5 Ranges
V-DC 0-6-1200 V-9 Ranges
V-AC 3-300 V-8 Ranges
Frequency in the range of 45 to 20KHz. Resistance: 500 ohm to 5 Mohm—5 ranges. Decibel: -10 to +12dB. Accuracy: $\pm 2.5\%$. DC $\pm 4\%$ AC. Dimensions: 167 x 98 x 63mm



Only **£9-25**

ALPHANUMERIC NIXIE TUBES B7971

The Alphanumeric NIXIE tube has the ability to display all the letters of the alphabet, numerals 0 thru 9 and special characters in a single tube. From the standpoint of both readability and electrical characteristics, the Alphanumeric NIXIE tube provides many unique benefits including * 170V-21mA * All d.c. operation * Uniform, continuous line characters of equal height * Memory with simple solid state drive circuits * Readability in high ambient light * 200 footlamberts brightness * Long life with no loss of brightness * Character height 2 1/2in.
Bases for above 68p each



Price only **99p** each plus 16p P./P.

JUST ARRIVED! !

NUMERIC INDICATOR TUBES

Ultra-long life, high quality, 0-9 and 2 independent decimal points. Supply volts. 200V d.c. Current 14mA. Pulse duration 100 μ s. Character height 0.51, overall size 1-4.
Brand new, guaranteed. Surplus to manufacturer's requirements. Type B5853at

1-25 **£1-00**; 25+ **90p**; 100+ **80p**;
1,000+ price on application.

Add 6% VAT to all items + 35p P. & P.
ELECTRONIC BROKERS LTD.
49-53 Pancras Road, London NW1 2QB
Tel. 01-837 7781

fibre optic suppliers

MARE'S TAILS. Build a decorative display with this professionally finished unit, 22in diameter with 7,000+ fibres. Looks immaculate. £10.
FIBROFLEX SIZE 1. Flexible 440 strand glass light conduit, bundle dia. 1.14mm. 40p per metre (£3 per 10m).
FIBROFLEX SIZE 4. 2.28mm bundle dia. £1.90 per metre (£12 per 10m).

CROFON 1818. 84-strand plastic light conduit, bundle dia. 1.8mm, O.D. 3.3mm. £1.50 per metre (£9 per 10m).
PLASTIC OPTICAL MONOFIBRE. For multiple illumination from one source, displays. Internal illumination, effects, optical coupling, etc.

OPTIKIT 103. Contains 2m Crofon 1810 plus 5m each FP20, FP40, FP60 plus polishing compound. A handy pack for the experimenter and laboratory. £4.90.

LENSES AND REFLECTORS. We stock a range of 6 lenses and 5 reflectors for use in proximity detectors, intruder detectors, batch counters, tachometers, short range optical communications.
OPTIKIT LB. 1 each of 6 lenses. £3.
OPTIKIT RR5. 1 each of 5 reflectors. £2.50.

CIRCULAR POLARISERS. Cut that glare. Reduce specular reflection by up to 20%—enhance contrast on CRTs, LED displays, nixies, instruments, etc. Available in red/amber/green/neutral. 50mm square 70p; 75mm £1.40; 150mm £4.50.
LIGHT SOURCES AND DETECTORS: MV54 Miniature (2mm) Red LED. 20p (10+ 17p); MLED500 TO92 Red LED. 20p (10+ 17p); MLED92 Infra-Red Emitter. 30p (10+ 25p); XC206-R 3mm Red LED. 20p; 2N5777 High Sensitivity Photodiode/Silicon Detector, gain x 2,500. 50p (10+ 42p); WRD150 Silicon Phototransistor—high speed, 4us good sensitivity. 70p (10+ 87p).

****NEW MLS203.** Latest Motorola Light Activated SCR. High sensitivity 10mW/cm²; high current 400mA (5A peak); 60V. Switch small motors or relay direct from optical control, up to 24W power. £1.20 (10+ £1.10).
SE05B-40TR/ULTRASONIC TRANSDUCER PAIR. Suitable for "Ultrasonic Doppler Shift Intruder Detector". Practical Electronics, March 1975. Tx/Rx pair £3.50.
SE05B-25TR/ULTRASONIC TRANSDUCER PAIR.

**** NEW **** The SE05B-40TR has proved to be an extremely popular item in our range and we are therefore introducing the 25kHz version. Although bandwidth is less at ±500kHz, sensitivity is better by 10dB. Suitable for burglar alarm systems, proximity switches, counters, level meters, anti-collision devices. 25kHz Tx/Rx pair £3.70.
 Please add 8% VAT to prices above (plus 22p on orders less than £3). Send 9in x 6in S.A.E. for short form lit.

FIBRE OPTIC SUPPLIERS
 (Dept. PE), 2 Loudon Road Mews
 London NW8 0DN
 (Please note change of address)

35 WATT/CHANNEL

Stereo Amplifier Chassis

Just needs 50 volt, 2-3 amp power supply. 1 glass fibre P.C.B. board including DIN sockets, etc.

35 WATT RMS @ 4Ω ch.
 25 WATT RMS @ 8Ω ch.

Disc 2mv. Aux. 1, Aux. 2, tape 200mv, £38 inc. P. & P. 50p.

P. F. STEVENS ELECTRO-ACOUSTICS
 8A CLARENCE ROAD
 SOUTH BENFLEET, ESSEX

BUILD THE TREASURE TRACER MK III Metal Locator



- Variable tuning
- Britain's best selling metal locator kit
- Fitted with Faraday shield
- Speaker and earphone operation
- Knocks down to only 17in
- Prebuilt search coil assembly
- Five transistor circuit
- Thoroughly professional finish
- You only need soldering iron, screwdriver, pliers and snips
- As seen on BBC-1 and BBC-2 TV

Send stamped, addressed envelope for leaflet!

Complete kit	£10.90	Built and tested	£15.25
	Post 60p + 92p VAT (8%)		Post 60p + £1.27 VAT (8%)

MINIKITS ELECTRONICS, 6g CLEVELAND ROAD, LONDON E18 2AN (Mail Order Only)

OSMABET LTD

We make transformers amongst other things

AUTO TRANSFORMERS 110-200 220 240V
 30W. £2.10; 50W. £2.70; 75W. £3.45; 100W. £4.50; 500W. £12.75W. £16.50; 1000W. £20.35, etc

LOW VOLTAGE TRANSFORMERS
 Prim 200.240V a.c. 5V 1A. 80p; 6 3V 1 5A £1.45; 3A £1.80; 6A, £3.80; 12V 1 5A, £1.80; 3A, £3.90; 6A CT. £4.50; 18V 1 5A CT. £3.30; 24V 1 5A CT. £3.30; 3A CT. £4.50; 5A, £8.75; 8A, £8.70; 12A, £12.40; 40V 3A CT. £8; 50V 6A CT. £15.75; 25V 2A - 25V 2A, £8.40; 12V 4A, £8.40.

LT TRANSFORMERS TAPPED SEC. Prim 200/240V
 0-10-12-14-16-18V 2A, £3.30; 4A, £4.50.
 0-12-15-20-24-30V 2A, £4.20; 4A, £8.
 0-5-20-30-40-60V 1A, £4.20; 2A, £8.
 0-40-50-60-80-90-100-110V 1A, £8.40.

MIDGET RECTIFIER TRANSFORMERS
 For FW rect. 200.240V a.c. 6-0-6V 1 5A or 9-0-9V 1A £1.85 each. 12-0-12V 1A or 20-0-20V 0.75A or 9-0-9V 0.3A or 12-0-12V 0.25A or 20-0-20V 0.15A or 8V 0.5A + 6V 0.5A or 9V 0.35A + 9V 0.35A or 12V 0.25A + 12V 0.25A or 20V 0.15A + 20V 1 5A. All at £1.90 each

MAINS TRANSFORMERS
 Prim 200/240V a.c. TX6 sec. 425-0-425V 500 MA, 6 3V CT 6A, 6 3V CT 6A, 0-5-6 3V 3A £18.75; TX1 425-0-425V 250 MA, 6 3V CT 4A, 6 3V CT 4A, 0-5-6 3V 3A, £11.25; MT3 Prim 0-110-240V, sec. 250V 100 MA, 6 3V 2A, E/S, £3.75.

O/P TRANSFORMERS FOR POWER AMPLIFIERS
 P.P. sec., tapped 3-8-15 ohms, A-A 6 kΩ 30W £8.75; A-A 3kΩ 50W £10.15; 100W (EL34 KT88, etc.) £17.25.

G.E.C. MANUAL OF POWER AMPLIFIERS
 Covering valve amplifiers of 30W to 400W 35p.

HI FI SPEAKERS
 5in 8Ω, £1.15; 7 x 4in 15Ω, £1.80; 6 x 5in 3, 8, 15 or 25Ω, £1.75 each; 8in 4Ω, £1.50; EMI 13 x 8in 8Ω, £4.50; £1.25; 8in twin coils 8Ω, £2; 8 x 5in 3, 8, 15 or 25Ω, £1.75.

LOUDSPEAKERS
 2 1/2in 8 or 75Ω, 2 1/2in 8 or 25Ω, 3in 3, 8 or 35Ω, 3 1/2in 8Ω, 15Ω or 80Ω, 95p each, 5in 3, 8 or 25Ω, 5 x 3in 3 or 8Ω, £1.15; 7 x 4in 3, 15 or 25Ω, 10 x 6in 3Ω, £1.50.


SPEAKER AUTO MATCHING TRANSFORMER
 12V 3 to 8 or 15Ω up or down. £1.50.

TAPE RECORDER MOTORS
 New, blowers, fans, etc., 110V a.c. 60p, £1 pair

"INSTANT" BULK TAPE/CASSETTE ERASER
 Instant erasure, any diameter tape spools, cassettes, demagnetises tape heads. 200/240V a.c., £3.75.

SYNCHRONOUS GEARED MOTORS, 200/240V a.c.
 Brand new, Smiths, Built-in gearbox, 2r.p.h., 75p each
 Carriage and VAT extra on all orders
S.A.E. ENQUIRIES, LISTS, MAIL ORDER ONLY
 45 Kenilworth Road, Edgware, Middx. HA8 8YG
 Tel. 01-958 9314

SYNTHESISER Modules by Dewtron®

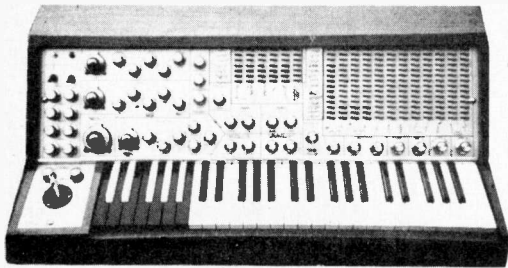

The synthesiser illustrated was built using Dewtron modules, as sold to constructors for some years now. With over 10 years' experience in mail-order, we have supplied many famous people and groups. Over 30 types of synthesis modules, some of extremely precision design, e.g. VCO-2 log-law oscillator; 3-wave o/ps; sample/hold/envelope module; pitch-to-voltage module allowing a whole equipment to "play itself" in unison/harmony with any solo input or voice. Modules for sequencer construction, too. Famous "Modumatrix" patching system makes other patching a thing of the past! Send just 20p for full catalogue to:

D.E.W. LTD.

254 Ringwood Road, Ferndown
 Dorset BH22 9AR

N.S.E. Professional Standard KITS

The first two of a range of kits to appeal to both the novice and the experienced assembler. Branded devices and high quality components used throughout.

3 CHANNEL SOUND TO LIGHT UNIT

1,000 Watts per channel Fibreglass P.C. Board

High sensitivity up-to-date design giving scintillating performance. Kit includes all components inc. mains—Transformer, Transistors and Triacs. Step-by-step instructions are provided. All you need is soldering iron, etc. No technical knowledge required. In the unlikely event of you being unable to get the unit operational it may be returned to us for correction.

PROFESSIONAL QUALITY AT THE UNBEATABLE PRICE OF £11.50. Carr. 50p.

5 WATT GUITAR PRACTICE AMPLIFIER WITH TREMOLO

Fibreglass P.C. Board

High quality unit with bass and treble controls plus speed and depth controls—Kit includes mains Transformers, etc. as above. Get it going service. Another N.S.E. first at only £9.70. Carr. 50p.

NOTE—PRICES INCLUDE VAT!

Send cheque/P.O. or Access number (cash in registered envelope only) to:

N.S.E. KITS

333 WHITEHORSE ROAD, CROYDON, SURREY
 Shop open Mon /Sat. 9.30 a.m.-5 p.m. Tel: 01-689 3685
 Please quote magazine when ordering

7400 13p 7401 14p 7402 14p 7403 16p 7404 18p 7405 16p 7406 36p 7407 36p 7408 18p 7409 18p 7410 13p 7412 21p 7413 32p 7414 60p 7416 33p 7420 14p 7422 25p 7423 32p 7427 37p 7430 14p 7432 25p 7437 25p 7440 14p 7441 85p 7442 60p 7447 75p 7448 70p 7450 15p	7451 18p 7453 16p 7454 18p 7460 15p 7470 27p 7472 25p 7473 30p 7474 30p 7475 45p 7476 30p 7480 50p 7481 95p 7482 70p 7483 30p 7485 120p 7486 30p 7489 270p 7490 40p 7491 75p 7492 45p 7493 40p 7494 48p 7495 85p 7496 78p 74107 30p 74121 30p 74122 48p	74123 88p 74141 85p 74142 250p 74151 72p 74153 82p 74154 150p 74155 78p 74160 99p 74161 99p 74162 99p 74163 99p 74164 120p 74166 130p 74174 120p 74175 85p 74180 100p 74181 340p 74182 85p 74185 145p 74190 150p 74191 150p 74192 120p 74193 120p 74194 110p 74195 78p 74198 188p 74199 185p	Popular Op Amps 709 OPA with ext comp 30p 710 Diff comparator 45p 741 OPA with int comp (8 pin DIL) 25p 747 Dual 741 70p 748 OPA with ext comp 34p	LINEAR I.C.s CA3046 Transistor Array 50p CA3048 4 Independent Amplifiers 230p ICL8038 VCO Fun. Gen 14-pin DIL 275p LM301A Op. Amp. with ext comp 36p LM380 Audio Amplifier 95p LM381 Stereo Pre Amp 150p LM3900 Quad Op. Amp 70p MC1310 Coilsless FM Stereo Dec. 200p MC1312 1100p MC1314 SQ Quadraphonic Dec. MC1315	MFC4000 iW Audio Amp 54p MFC6040 Electronic Attenuator 90p NES36 FET Op. Amp 250p NES55 Timer 8-pin DIL 45p NES56 Dual 555 14-pin DIL 100p NES60 PLL 16-pin DIL 325p NES61 PLL with AM Demod. 16-pin 355p NES62 PLL with VCO 18-pin 325p NES63 PLL FM/IF Demod 18-pin DIL 300p NES65 PLL 14-pin DIL 325p NES68 Function Generator 8-pin DIL 200p NES67 PLL Tone Decoder 8-pin DIL 250p TBA570 AM/FM Radio receiver 18p TBA800 5 Watt Audio Amp 90p TBA810 7 Watt Audio Amp 100p TBA820 2 Watt Audio Amp 60p ZN414 TRF Radio Receiver 110p	CLOCK I.C.s AY-5-1224 16 pin DIL 500p MM 5314N 24 pin DIL 430p 24 pin DIL Socket 100p Data sheets 20p each plus S.A.E. VAT 8% on above I.C.s.	Low Profile DIL Sockets by Texas 8 pin 13p, 14 pin 14p, 15 pin 15p Mica + 2 bushes for TO3 & TO66 5p
VOLTAGE REGULATORS (PLASTIC)				SCR-THYRISTORS		TRIACS	
723 14-pin DIL 45p Data sheets on vcl. reqs. 18p each				1 Amp +Ve 5V 7805 140p 12V 7812 140p 15V 7815 140p 18V 7818 140p 24V 7824 140p		-Ve 7905 250p 7912 250p 7915 250p 7918 250p 7924 250p	
				1A 40p 3A 43p 7A — 12A 140p 18A — BT106 148p		50V 100V 400V 600V 42p 50p 70p 48p 75p 100p 80p 84p 160p 175p 230p 170p 200p 270p C106D 45p. MCR101 25p.	
				Diodes		ZENERS	
				OA202 7p BY100 15p BY126 12p BY127 10p OA47 7p OA70 7p OA79 7p OA81 7p OA85 9p OA90 6p OA95 7p OA200 6p		IN914 4p IN4001 5p IN4004 6p IN4007 7p IN4148 3p OTHER BA145 15p BA148 13p LED TIL209 16p	
				BRIDGE RECTIFIERS		C-MOS I.C.s	
				50V 100V 400V 600V 0.25A — 20p 1A 22p 24p 27p 29p 2A 30p 35p 45p 48p 4A — 55p 6A 58p 63p		CD4000AE 19p CD4001AE 19p CD4002AE 19p CD4009AE 67p CD4011AE 21p CD4013AE 55p CD4016AE 50p CD4017AE 120p CD4018AE 175p CD4022AE 189p CD4023AE 18p CD4024AE 120p CD4027AE 91p CD4028AE 140p CD4029AE 175p CD4046AE 202p CD4047AE 154p CD4049AE 64p CD4054AE 190p CD4055AE 190p CD4060AE 229p CD4071AE 28p CD4081AE 26p CD4510E 160p CD4511AE 236p CD4528AE 120p	
				MOSFETS		OPTO-ELECTRONICS	
				40603 58p 40673 58p 3N128 75p 3N140 85p 3N141 75p		ORP12 50p ORP60 60p ORP61 60p LED TIL209 with clip 16p. Green/Yellow with clip 35p. SEVEN SEGMENT DISPLAYS 3015F 0.35in DIL 120p DL704 0.33in DIL 130p DL707 0.33in DIL 135p DL747 0.63in DIL 225p MAN-3M 0.127in PCB 100p MAN-4 0.19in DIL 180p	

Minimum order £2. P. & P. 20p. MAIL ORDER ONLY. Government, colleges, etc., orders welcome. **TECHNOMATIC LTD** 54 Sandhurst Road, London NW9. Tel. 01-204 4333

INDEX TO ADVERTISERS					
A.D. Electronics	688	Fibre Optics	691	Phoenix Electronics Ltd	614
Astro Electronics	622, 646	Fairline Supplies	685	Phononics	681
Automated Homes	690	Greenwell Electronics	616	Pulse Electronics Ltd.	642
A.W.R.E. (Ministry of Defence)	689	Greenwood	671	Radio Component Specialists	672
Axial Products	688	G.W.M. Radio	687	Radio Exchange	cover ii
Bamber, B. Electronics	626	Heath (Gloucester) Ltd.	671	Radnage	622
Barclay Electronics	620	Henry's	682	Reedhampton	614
Barrie Electronics	684	Home Radio (Components) Ltd.	628	Riversdale	684
Beta Devices	688	I.C.S. School of Electronics	690	R & TV Components Ltd.	624-625
B. H. Component Factors	646	I.L.P. Electronics Ltd.	683	R.S.T. Valve Mail Order Co.	642
Bi-Pre-Pak	617	International Electronics Unlimited	615	R.T. Services	687
Boffin Products	690	Island Devices	688	Salop Enterprises	690
Bradley, G. & E.	689	Jones, J. C.	687	Saxon Entertainments Ltd.	627, 691
British Institute of Engineering Technology	623, 680, 686	Juniper Electronics	687	Scott Electronics	646
British National Radio & Electronics School	626, 645	J.W.B. Radio	687	Service Trading	cover iii
Bywood	649	Kensington Supplies	689	Sinclair (Hi-Fi)	616
Chiltmead Ltd.	642	London Computer Operators Training Centre	690	Sinclair (System 4000)	623
Chinaglia (UK) Ltd.	614	Maplin Electronic Supplies	688, cover iv	Sinclair (Project 80)	680
Chromasonic Electronics	679	Marco Trading	687	Sinclair (IC20)	686
Cmos Specialists	687	Marshall, A. (London) Ltd.	621	Sintel	688
Combined Precision Components	626	Medical Research Council	690	Stevens, P. F.	691
Cooper Supplies	688	Medway Mail Order	675	Technical Book	676
D.E.W. Ltd.	691	Minikits Electronics	691	Technomatic	692
Doram Electronics Ltd.	641	Modern Book Co.	685	Teleradio Electronics	690
Dziubas, M.	616	Oliver, P. G. & Co	688	Trafalgar Supplies	675
Eaton Audio	685	Osmabel	691	Trampus Electronics Ltd.	682
Electronic Brokers	690			T.U.A.C. Ltd.	618-619
Electronic Design Associates	622			West London Direct Supplies	685
Electropares	620			Wimslow	676
Electrovalue Ltd	680			Writing School, The	688

RELAYS SIEMENS, PLESSEY, Etc. MINIATURE RELAYS

Col. (1)	1	2	3	4
Coil ohms				
Col. (2)	52	4-8	2 c/o	70p*
Working	58	5-9	6 c/o	80p*
d.c. volts	230	9-18	6M	60p*
Col. 3	430	15-24	2 c/o	70p*
Contacts	700	12-24	2 c/o	60p*
Col. (4)	700	16-24	4M 2B	60p*
Price	700	16-24	4 c/o	80p*
HD =	1,250	18-36	2 c/o	60p*
Heavy duty	2,500	31-43	2 c/o HD	60p*
	9,000	40-70	5 c/o	60p*
	15k	85-110	6M	60p*

*Incl. Base. All prices incl. P. & P.

OPEN TYPE RELAYS

6 VOLT D.C. 1 make contacts 35p. Post 15p.
 9 VOLT D.C. RELAY
 3 c/o 5 amp contacts. 70 ohm coil. 75p. Post 15p.

12 VOLT D.C. RELAY

3 c/o 5 amp contacts. 120 ohm coil. 75p. Post 15p.

24 VOLT D.C. 3 c/o 75p. Post 15p.

ENCLOSED TYPE RELAYS

24 VOLT D.C. 3 c/o 75p. Post 15p. Base 15p extra.

24 VOLT A.C. Mfg. by IIT. 3 h.d. c/o contacts. 55p. Post 15p. Base 15p.

55 VOLT A.C. RELAY

3 h.d. c/o contacts. Price 55p. Post 15p. Base 15p.

100 VOLT A.C. 3 c/o sealed type. 75p. Post 15p. Base 15p.

240 VOLT RELAY

3 h.d. c/o contacts. Price 75p. Post 15p. Occal plug in base 15p extra.

230/240 VOLT A.C. RELAY. Mfg. by Arrow 2 h.d. 15 amp c/o contacts. Amp connectors. Price £1. Post 15p.

220/240 VOLT A.C. RELAY

3 c/o 5 amp contacts. Sealed. Mfg. ISKRA. £1.25. Post 15p. Base 15p extra.

CLARE-ELLIOTT TYPE RP741 G8

Miniature relay. 675 ohm coil. 24 Volt D.C. 2 c/o. 70p post paid.

110V. 2 c/o. 20 amp contacts. £1.25. Post 15p. Many others from stock—phone for details.

VERY SPECIAL OFFER

Honeywell Type N100

10A changeover micro switch. 10A for £2.50. Post 25p.



PUSH BUTTON

MICRO SWITCH. 5 amp. c/o contacts. NEMCO for £2. Post 15p. (Min. order 20). Ditto press to break. 20 for £1.50. Post 15p.



SUB-MINIATURE REED

RELAY 3.9V d.c. 250 ohm Coil Single make, size 1 1/2 in. Outstanding Value only £1 for six, £1.50 for ten. Post 15p. (Min. order six.)



LATCHING RELAY

Twin latching relay. "flip-flop" 2 c/o each relay. Mains contacts. 115V A.C. or 50V D.C. operation. 240V A.C. with 2.5K resistor. 85p. Post 15p.



TRIAC

Raytheon Tag symmetrical Triac. Type TAG. 250/500V. 10 amp. 500 p.w. Glass passivated plastic triac. Swiss precision product for long term reliability £1.00. Post 10p. (Inclusive of Data and application sheet.) Suitable Diac 18p.

230 250 VOLT A.C. SOLENOID

Approximately 1 1/2 lb pull. Size of feet 1 1/2 in. Price £1.00. Post 15p.

HEAVY DUTY TYPE. Approx. 14 lb. pull. £2.50. Post 30p.

24 VOLT DC SOLENOIDS

UNIT containing 1 heavy duty solenoid approx. 25 lb pull 1 inch travel. Two x approx. 1 lb pull 1/2 inch travel. 6 amp. 240V. 40z. pull 1/2 inch travel. One 24 volt d.c. 1 heavy duty single make relay. Price £2.50. Post 75p. ABSOLUTE BARGAIN.

COIN MECHANISM (Ex London Transport)

Unit containing, selector mechanism for 1p, 2p and 5p coins. Micro switches, relays, solenoid operated hopper. 24 volt D.C. Precision built to high standard. Incredible VALUE at only £2.50. Post 70p. VAT 25%.

CENTRIFUGAL BLOWER

Mfg. Airflow Developments Ltd. Precision continuously rated. Smooth running. 230/240V a.c. motor 80 c.f.m. As illustration but with round aperture. £6.50. Post 50p.



All Mail Orders—Callers—Ample Parking
 Dept. PE8, 57 BRIDGMAN ROAD
 CHISWICK, LONDON W4 5BB
 Phone 01-995 1560
 Showroom open Mon.-Fri.

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT
 VARIABLE 0-260V All Types

SHROUDED TYPE
 200 watt (1 amp) £10.00
 0.5 KVA (2 1/2 amp) (MAX) £11.50
 1 KVA (5 amp) (MAX) £15.00
 2 KVA (10 amp) (MAX) £27.50
 3 KVA (15 amp) (MAX) £30.00
 4 KVA (20 amp) (MAX) £60.00
 37.5 amp (MAX) £102.50



CARRIAGE AND PACKING EXTRA
 OPEN TYPE 1 amp (panel mount) £10.00

L.T. TRANSFORMERS

0, 6, 12 Volt at 10 amp. £5-60. Post 70p.
 0, 10, 17, 18 Volt at 10 amp. £7-90. Post 70p.
 0, 4, 6, 12, 32 Volt at 12 amp. £9-90. Post 70p.
 0, 6, 12 Volt at 20 amp. £10-20. Post 70p.
 0, 12, 24 Volt at 10 amp. £9-20. Post 70p.
 0, 6, 12, 17, 18, 20 Volt at 20 amp. £10-20. Post 70p.
 Other types to order at short notice—Phone your enquiries.

'STC' 6" RED ALARM BELL

24/48 volt DC. Brand New. Price £4. Post 50p. VAT 25%.



'GENTS' 6" ALARM BELL

200/250V A.C./D.C. Brand New. Price £5. Post 75p. VAT 25%.

REVERSIBLE MOTOR

A.E.I. 1/2 h.p. reversible motor 100, 120 volt A.C. 50/60 cycle 1400/1680 r.p.m. Flange fixing. Dia. 4 1/2 length 6 1/2. shade 1 3/8. Brand New. Price £2.50. Post 50p. Suitable 110/240V. 150 watt Auto Transformer £3.50. Post 50p. (Post for both items together 75p.)



230/240 VOLT A.C. MINIATURE MOTOR.

20 R.P.M. Price £1. Post 15p.

BODINE TYPE N.C.I. GEARED MOTOR

(Type J) 71 r.p.m. torque 10 lb. in. Reversible 1/70th h.p. cycle 0.38 amp. (Type 2) 28 r.p.m. torque 20 lb. in. Reversible 1/80th h.p. 50 cycle 0.28 amp. The above two precision made U.S.A. motors are offered in 'as new' condition. Input voltage of motor 115V A.C. Supplied complete with transformer for 230/240V A.C. input. Price, either type £6.25. Post 65p or less transformer £3.75. Post 50p.



'FRACMO' 240 VOLT A.C. 50 cycle SINGLE PHASE GEARED MOTOR

33 r.p.m. 30 lb. ins. Reversible. Fitted with mounting feet. Brand New. £14. Post £1.00. (Total price incl. VAT £16.20).



9-12 VOLT D.C. GOVERNED REVERSIBLE MOTOR

Machine cut gear train, giving final speed of 2 r.p.m. with cam driving 3 sub-miniature micro-switches (removable). Spindle 12mm long 6mm dia. Built to PO spec., in heavy metal hinged case. £3.75. Post 40p.



'CARTER' 230 VOLT A.C. GEARED MOTOR

230/240V A.C., smooth, powerful, continuously rated. Two types: 32 r.p.m. or 110 r.p.m. Either type £4.50. Post 50p.



POWER RHEOSTATS !!

Superior Quality Precision Made

NEW POWER RHEOSTATS

New ceramic construction, vitreous enamel embedded winding, heavy duty brush assembly, continuously rated.

25 WATT 10/25/50/100/150/250/500/1k/1.5k/2.5k ohm. £1.70. Post 15p.

50 WATT 1/5/10/25/50/100/250/500/1k ohm £2.10. Post 20p.

100 WATT 1/5/10/25/50/100/250/500/1k/1.5k/2.5k/3.5k/5k ohm £3.30. Post 25p.

Black Silver, Skirted knob calibrated in Nos. 1-9 1/2 in. dia. brass bush. Ideal for above 22p each.



VAT

VAT at 8% MUST BE ADDED TO ALL ORDERS FOR THE TOTAL VALUE OF GOODS INCLUDING POSTAGE UNLESS OTHERWISE STATED.

SERVICE TRADING CO.

STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation. RANGE OF FOUR STROBE KITS FROM STOCK. PRICES FROM £6.30 to £22. S.A.E. for details.

BIG BLACK LIGHT

400 Watt. Mercury vapour ultra violet lamp. Powerful source of u.v. P.F. ballast essential. Price of matched ballast and bulb £21. Post £1. Spare bulb £8. Post 40p.

BLACK LIGHT FLUORESCENT U.V. TUBES

4ft 40 watt, £5.50 (callers only).
 2ft 20 watt, £4.25. Post 40p. (For use in standard bi-pin. MINI. 12in 8 watt, £1.60. Post 25p. 9in 6 watt, £1.30. Post 25p. Complete ballast unit and holders for 9in and 12in tube, £1.70. Post 25p. (9in and 12in measures approx.)



METERS NEW

90mm diameter

Type 65C5. 2A D.C. M/C; 5A D.C. M/C 10A D.C. M/C; 20A D.C. M/C; 50A D.C. M/C
 Type 62T2. 1A A.C. M/I; 20A A.C. M/I; 300V A.C. M/I; ALL ABOVE £2.50. Post 20p.
 Type 65LS. 300V A.C. R/M/C; £2.75. Post 20p.

64mm X 56mm RECTANGULAR

Type 85C1. 5A D.C. M/C; 20A D.C. M/C. Type 85L1. 5A A.C. R/M/C; 10A A.C. R/M/C; 300V A.C. R/M/C; All at £3. Post 20p.

ROTARY VACUUM AIR PUMP AND COMPRESSOR


Carbon vane, oilless, 100/115V a.c., 1/2 h.p. motor, 50/60 cycle, 2875/3450 r.p.m., 20 in vacuum, comp. 1.25 c.f.m., 10 p.s.i. (approx. figures). New unused surplus stock. Supplied with electrical connection data. FRACTION OF MAKEUP PRICE £12. Post 50p. Suitable 110/240V. 150 watt auto transformer £3.50. Post 50p. (Both items together Post 75p.)



PROGRAMME TIMERS

230/240V a.c. 15 r.p.m. Motors. Each cam operates a c/o micro switch. Ideal for lighting effects, animated displays, etc. Ex equipment tested.

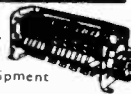2 cam model. 15 r.p.m. £2.00 post 35p.
 4 cam model. 15 r.p.m. £2.50 post 35p.
 8 cam model. 20 r.p.m. £4.75 post 40p.
 8 cam model, each cam fully adjustable. 6 r.p.m. M.f.g. by Magnetic Devices. £7.50. Post 35p.



A.C. MAINS TIMER UNIT

Based on an electric clock, with 25 amp. single pole switch, which can be preset for any period up to 12 hrs. ahead of time, or for any length of time, from 10 mins. to 6 hrs. then switch off. An additional 60 min. audible timer is also incorporated. Ideal for Tape Recorders, Lights, Electric Blankets, etc. Attractive satin copper finish. Size 135mm x 130mm x 60mm. Price £2. Post 40p. (Total incl. VAT and Post £2.59).



TIME SWITCH

'Horstmann' Type V Mk. II Time switch. 200/250V a.c. Two on two off every 24 hours, at any manually preset time. 30 amp contacts. 36 hour spring reserve in case of power failure. Day omitting device. Fitted in heavy high impact case, with glass observation window. Built to highest Electricity Board Spec. individually tested. Price £7.75. Post 50p. (Total incl. VAT £8.91)



600 WATT DIMMER SWITCH

Easily fitted. Fully guaranteed by makers. Will control up to 600W of lighting except fluorescent at mains voltage. Complete with simple instructions. £2.75. Post 25p.

NICKEL CADMIUM BATTERY

1.5V. 15A. Size 154mm high, 76mm wide, 29mm deep. Price £1.50. Post 50p.

INSULATION TESTERS NEW!

Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L 8in. W 4in. H 6in. weight 6lb. 500V, 500 megohms. £30. Post 80p.



Personal callers only. Open Sat.

9 LITTLE NEWPORT STREET
 LONDON WC2H 7JJ
 Phone 01-437 0576

130 fourth Ave

More than just a catalogue


Projects for you to build.

4-digit clock, 6-digit clock, 10W high quality power amp., High quality stereo pre-amp., Stereo Tuner, F.M. Stereo decoder, etc., etc. . . .


CIRCUITS . . . Frequency Doublers, Oscillators, Timers, Voltmeters, Power Supplies, Amplifiers, Capacitance Multiplier, etc., etc. . . .

Full details and pictures of our wide range of components, e.g. capacitors, cases, knobs, veroboards, edge connectors, plugs and sockets, lamps and lampholders, audio leads, adaptor plugs, rotary and slide potentiometers, presets, relays, resistors (even 1% types!), switches, interlocking pushbutton switches, pot cores, transformers, cable and wire, panel meters, nuts and bolts, tools, organ components, keyboards, L.E.D.'s, 7-segment displays, heatsinks, transistors, diodes, integrated circuits, etc., etc. . . .

REALLY GOOD VALUE FOR MONEY AT JUST 40p.

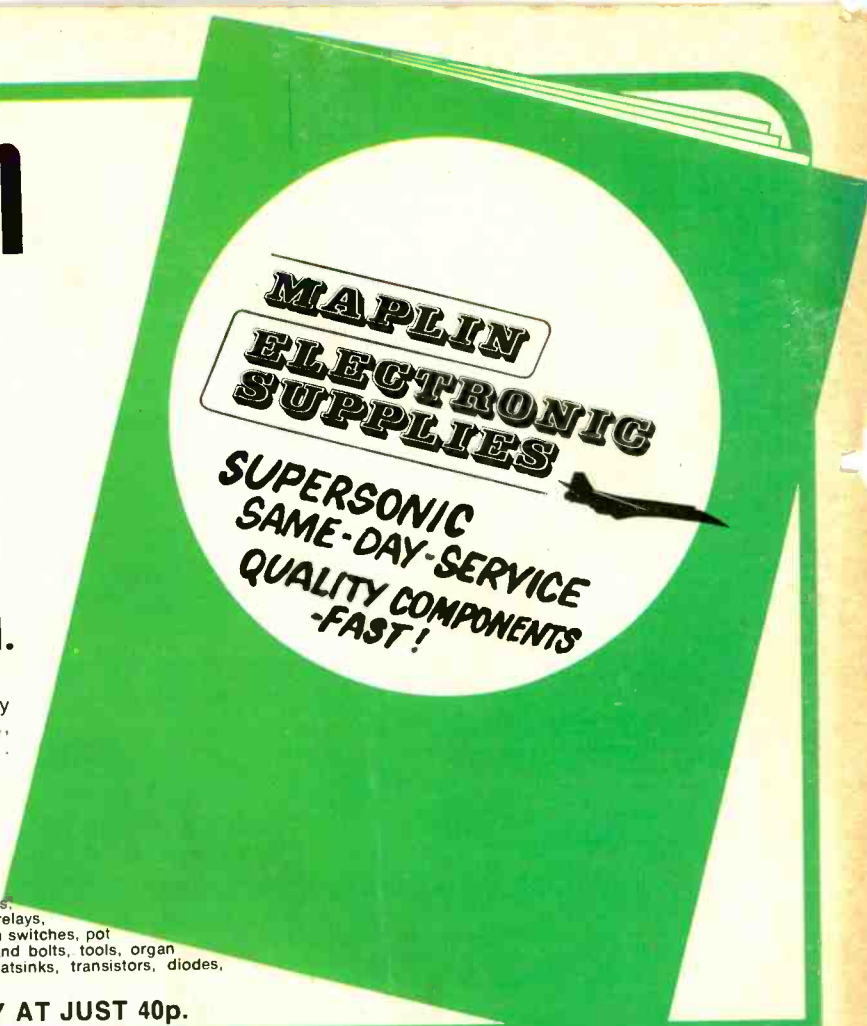

ELECTRONIC ORGAN

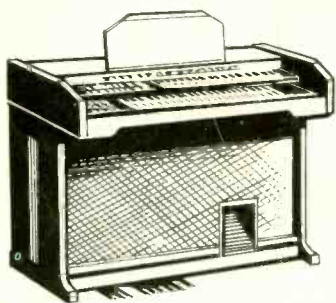

Build yourself an exciting Electronic Organ. Our leaflet MES51, price 15p, deals with the basic theory of electronic organs and describes the construction of a simple 49-note instrument with a single keyboard and a limited number of stops.

Leaflet MES52, price 15p, describes the extension of the organ to two keyboards each with five voices and the extension by an octave of the organ's range.

Solid-state switching and new footages along with a pedal board and a further extension of the organ's range are shown in leaflet MES53, also priced at 15p.


No more doubts about prices

Now our prices are **GUARANTEED** (changes in VAT excluded) for two month periods—and we'll tell you about price changes in advance for just **30p** a year (refunded on purchases). If you already have our catalogue send us an S.A.E. and we'll send you our latest list of **GUARANTEED** prices. Send us **30p** and we'll put you on our mailing list—you'll receive immediately our latest price list then every two months from the starting date shown on that list you'll receive details of our prices for the next **GUARANTEED** period *before* the prices are implemented!—plus details of any new lines, special offers, interesting projects—and clip-off coupons to spend on components to repay your **30p** when used as directed.

NOTE: The price list is based on the Order Codes shown in our catalogue so an investment in our super catalogue is an essential first step.

Call in at our shop, 284 London Road, Westcliff-on-Sea, Essex. Please address all mail to P.O. Box 3, Rayleigh, Essex, SS6 8LR.

SYNTHESISER

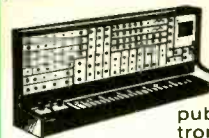

A reprint of the complete article giving full construction details

published by "Electronics Today International" between January-September '74 of the International Voltage Controlled Synthesiser, developed as a "state of the art", will be available shortly, price **£1.50**. S.A.E. please for detailed price list.

GRAPHIC EQUALISER



A really superior high quality stereo graphic

equaliser as described in the January edition of "Electronics Today International". We stock all the parts (except woodwork) including the metalwork drilled and printed. **15p** brings you a reprint of the article or a S.A.E. please for our detailed price list.

MAPLIN ELECTRONIC SUPPLIES

P.O. Box 3 Rayleigh Essex SS6 8LR.
Telephone: Southend-on-Sea (0702) 44101