


PRACTICAL

ELECTRONICS

APRIL 1980

55p

30W I.C. STEREO AMPLIFIER

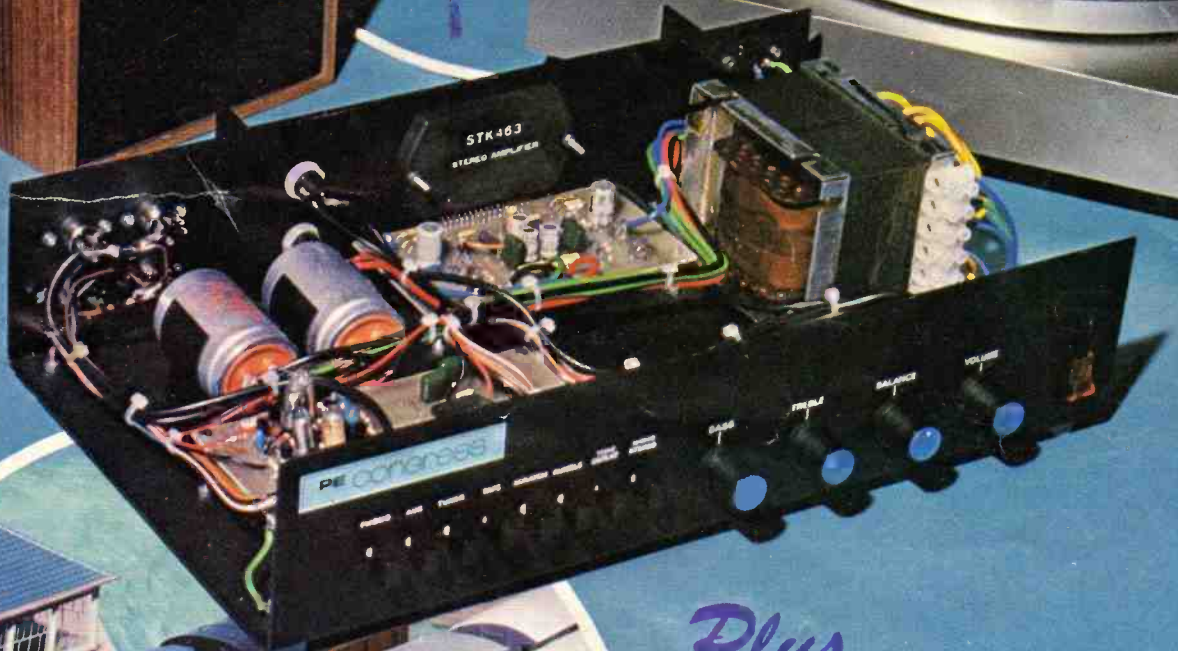

2 WIRE TRAIN CONTROLLER

Plus
**VIDEOTONE GB3
SPEAKER OFFER**

Also...
**SPECIAL
SUPPLEMENT
VIDEO for
EVERYONE!**

COMPUKIT UK101

EUROPE'S FASTEST SELLING ONE BOARD COMPUTER



Simple Soldering due to clear and concise instructions compiled by **Dr. A.A. Berk, BSc PhD**

- ★ 6502 based system — best value for money on the market.
- ★ Powerful 8K Basic — Fastest around
- ★ Full Qwerty Keyboard
- ★ 4K RAM Expandable to 8K on board.
- ★ Power supply and RF Modulator on board.
- ★ No Extras needed — Plug-in and go.
- ★ Kansas City Tape Interface on board.
- ★ Free Sampler Tape including powerful Dissassembler and Monitor with each Kit.
- ★ If you want to learn about Micros, but didn't know which machine to buy then **this is the machine for you.**

Build, Understand and Program your own Computer for only a small outlay

KIT ONLY **£199** + VAT NO EXTRAS NEEDED

AVAILABLE READY ASSEMBLED & TESTED READY TO GO FOR **£249** + VAT

Specially designed case for CompuKit in orange/black With room for accessories **£29.50** + VAT


6502 Assembler/Editor for CompuKit **£14.90** + VAT

The **CompuKit UK101** comes in kit form with all the parts necessary to be up and working, supplied. No extras are needed. After plugging in just press the reset keys and the whole world of computing is at your fingertips. Should you wish to work in the machine code of the 6502 then just press the M key and the machine will be ready to execute your commands and programs. By pressing the C key the world of Basic is open to you.

This machine is ideal to the computing student or Maths student, ideal to teach your children arithmetic, and is also great fun to use.

Because of the enormous volume of users of this kit we are able to offer a **new reduced price of £199** + VAT

8MHz Super Quality Modulators	£4.90
6MHz Standard Modulators	£2.90
C12 Computer Grade Cassettes 10 for	£4.00
Super Multi-rail P S U. +5 -5 +12v	£29.50
Nascom I with Nas-sys Kit	Special Price £125.00
Assembled } Limited quantities	£140.00
ETI Breakout Game — Chip and PCB	£9.90
S100 Expansion Motherboard for Nascom I	£39.00
Anadex Printer Paper — 2000 sheets	£25.00
Floppy Disks 5 1/4" Hard & Soft Sectored	£3.50
Floppy Disk Library Case 5 1/4"	£3.50
Lexicon Language Translator	£125.00
Modules for Lexicon	£29.00
Eprom Boards	£63.00
8K Static Ram Boards — S100	£110.00
Grandstand Video Game	£59.00
Cartridges for Grandstand	£11.99
George Risk Ascii Keyboard	£39.00
Cartridges for Atan — Full Range in Stock	£13.90
Interface PET IEEE — Centronics Parallel Not decoded	£49.00
Decoded	£77.00
Interface to Centronics parallel for TRS80	£75.00
Verocases for Nascom 1 & 2 etc.	£22.50
Keyboard Cases	£9.90
Electric Pencil for TRS80	£29.00

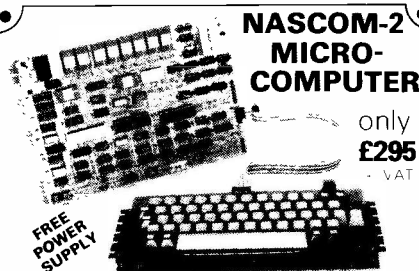

NASCOM-2 MICRO-COMPUTER

only **£295** + VAT

FREE POWER SUPPLY

Microprocessors Z80A 8 bit CPU This will run at 4MHz but is selectable between 1.2 4 MHz This CPU has now been generally accepted as the most powerful, 8 bit processor on the market

INTERFACE

Keyboard New expanded 57 key Licon solid state keyboard especially built for Nascom Uses standard Nascom, monitor controlled, decoding

T.V. The lv peak to peak video signal can drive a monitor directly and is also fed to the on-board modulator to drive the domestic T V

I.O. On-board UART (Int 6402) which provides serial handling for the on board cassette interface or the RS232 20mA teletype interface

The cassette interface is Kansas City standard at either 300 or 1200 baud This is a link option on the NASCOM-2 The RS232 and 20mA loop connector will interface directly into any standard teletype.

The input and output sides of the UART are independently switchable between any of the options i.e. it is possible to house input on the cassette and output on the printer

PIO There is also a totally uncommitted Parallel I/O (MK3881) giving 16, programmable, I/O lines. These are addressable as 2 x 8 bit ports with complete handshake controls

Documentation Full construction article is provided for those who buy a kit and an extensive software manual is provided for the monitor and Basic

Basic The Nascom 2 contains a full 8K Microsoft Basic in one ROM chip with additional features like DEEK, DOKE, SET, RESET for simple programming With free 16K RAM board

only **£295** + VAT

Expand your TRS80 by 32K **32K** Memory on board Centronics parallel port Disk controller card Real time clock Requires Level II Basic interface for 2 Cassette decks complete with power supply

TRS80 EXPANSION INTERFACE



only **£399** + VAT



TRS80 LEVEL 2 16K

Fully converted to UK 1 V Standard Comes complete with easy to follow manuals UK Power Supply Cassette Leads Sample tapes Special box to enable you to plug into your own TV Recommended for first time buyers Just plug in and go Full Range of Software Available

NEW REDUCED PRICES

8K **£449**

16K **£549**

32K **£649**


RRP £795 for 32K



The PEDIGREE PETS

Very popular for home & business use 8K Microsoft Basic in ROM 8K Pet 32K & 16K with new improved keyboard All with green screen

Extra cassette deck **£55** Full range of software available

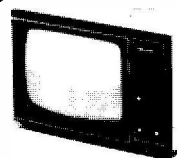

video 100

12" BLACK & WHITE LOW COST VIDEO MONITOR

RRP £79

only **£69** + VAT

- Ideal for home, personal and business computer systems
- 12" diagonal video monitor
- Composite video input
- Composite video input
- Compatible with many computer systems
- Solid-state circuitry for a stable & sharp picture
- Video bandwidth - 12MHz + 3DB
- Input impedance - 75 Ohms
- Resolution - 650 lines Minimum In Central 80% of CRT; 550 Lines Minimum beyond central 80%.

COMP SHOP
"Europe's Largest Discount Personal Computer Store"

Please add VAT to all prices — Delivery at cost, will be advised at time of purchase. Please make cheques and postal orders payable to COMPSHOP LTD., or phone your order quoting BARCLAYCARD, ACCESS, DINERS CLUB or AMERICAN EXPRESS number.

CREDIT FACILITIES ARRANGED — send S.A.E. for application form.

14 Station Road, New Barnet, Hertfordshire, EN5 1QW Telex: 298755 TELCOM G

Telephone: 01-441 2922 (Sales) 01-449 6596

OPEN - 10 am - 7 pm — Monday to Saturday

Close to New Barnet BR Station — Moorgate Line.

COMP COMPUTER COMPONENTS
(Part of the Compsshop Ltd. Group)



PRACTICAL ELECTRONICS

VOLUME 16 No. 4 APRIL 1980

CONSTRUCTIONAL PROJECTS

CHIP CHECKER by <i>L. V. Cooper</i>	25
Versatile i.c. tester	
PRESCALER by <i>Michael Tooley B.A. and David Whitfield B.A., M.Sc.</i>	34
V.H.F. accessory for the DFM	
PE CONGRESS Part 1 by <i>Graham Jackson</i>	38
Hi-fi stereo amplifier	
PE TRAVELLER	70
Part 2—Installation and Suppression	
2 WIRE TRAIN CONTROLLER Part 1 by <i>J. Milne</i>	72
Allows independent control over four channels	

GENERAL FEATURES

EDUKIT REVIEWED by <i>Mike Abbott</i>	22
A really low cost learning tool	
SEMICONDUCTOR UPDATE by <i>R. W. Coles</i>	24
ZMOS F.E.T. AG1000 IU101	
POWER SUPPLIES FOR M.P.U.s Part 1 by <i>A. Clements</i>	54
Design basics for adequate supplies	
MICROBUS by <i>D.J.D.</i>	60
Programming problems—low cost SC/MP system—Hex keyboard/display	
INGENUITY UNLIMITED	64
Model Railway Controller—Metal Detector—Low Noise Mic Pre-amp	

NEWS AND COMMENT

EDITORIAL	17
MARKET PLACE	18
INDUSTRY NOTEBOOK by <i>Nexus</i>	33
MICRO-PROMPT	63
SPACEWATCH by <i>Frank W. Hyde</i>	66
SPEAKER OFFER	68
COUNTDOWN	71
PATENTS REVIEW	79
READOUT	80
BOOK REVIEWS	80
POINTS ARISING	80

SPECIAL SUPPLEMENT

VIDEO FOR EVERYONE by <i>G. K. Gardner</i>	44
State of the art and the future	

OUR MAY ISSUE WILL BE ON SALE FRIDAY, 11 APRIL 1980
(for details of contents see page 37)

© IPC Magazines Limited 1980. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

ELECTROVALUE

CATALOGUE

10

HAD YOURS YET?

Our computer has already selected thousands of our customers to whom our new catalogue has automatically been sent. If you would like a copy too, simply send us your name and address. It's

FREE

(You don't even have to pay return)

IT'S A GOOD DEAL BETTER FROM ELECTROVALUE

- **We give discounts**
on C.W.O. orders, except for a few items market Net or N in our price lists.
5% on orders, list value £10 or more
10% on orders list value £25 or more.
Not applicable on Access or Barclaycard purchase orders.
- **We stabilise prices.**
by keeping to our printed price lists which appear but three or four times a year.
- **We guarantee**
all products brand new, clean and maker's spec. No seconds, no surplus.
- **We pay postage in U.K.**
on C.W.O. orders list value £5 or over. If under, add 30p handling charge.
- **Appointed distributors for**
SIEMENS, VERO, ISKRA, NASCOM and many others.

OUR NEW CATALOGUE No 10

Full 128 pages. Thousands of items. Improved classification for easier selection. Valuable working information. Illustrations. Separate quick-ref price list.

ELECTROVALUE LTD

HEAD OFFICE (Mail Orders)

28(B) St. Judes Road, Englefield Green, Egham, Surrey
TW20 0HB. Phone: 33603 (London prefix '87. STD 0784) Telex 264475.

NORTHERN BRANCH (Personal Shoppers Only)


680 Burnage Lane, Burnage, Manchester M19 1NA
Phone: (061) 432 4945.

WICCA



Electronic Systems Ltd

P.E. ULTRASONIC CLEANER

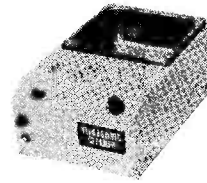

All the designer approved parts, including fibre glass case, to complete this exciting project as featured in the January 1980 issue.

£68.00

SANYO

STK 463

Hybrid stereo power amp I.C. delivers 30W R.M.S. into 8 ohms from each channel, all contained in one package approximate size as outline to this item. From one of the worlds leading manufacturers this new I.C. features only 0.5mV output noise and THD of .07% and IMD of .1% at 1W. Price includes P.C.B., data sheet and additional support components to complete. Just add pre-amp and power supply (not supplied) to build a high quality stereo amp.

£15.80



PS463

Toroidal transformer, bridge rec and smoothing caps and instructions to make a suitable power supply for the STK 463 **£13.80** p.p. £2.00

CPLM1

A versatile self contained sound to light unit comprising red, green and blue lamps in moulded cases that snap together to form columns on modulator. Extra snap together lamp cases to extend column or to construct extra lamp columns are available with lamps. Sockets on rear of unit enable up to 1000 watts of lamps to be connected to each channel. No need to connect to amplifier as modulator has a built in microphone, just connect to mains and its ready to go.

£29.50

p.p. £2.50

extra lamp holders with lamps £4.50 p.p. £1.00 each.



Send large S.A.E. for further details of all our products.

Terms C.W.O. Add £1.00 p.p. unless stated. Prices do not include VAT, add 15% to total order and carriage price. Send order to

WICCA ELECTRONIC SYSTEMS LTD

Orchard Works, Wallington, Surrey
Phone: 01-669 6047

MAIL ORDER

CALLERS BY APPOINTMENT ONLY

NEW

CONSTRUCTORS PACK 7

ALL THE PARTS TO BUILD THE PE TRAVELLER CAR RADIO

- * EASY TO BUILD * 5 PUSH BUTTON TUNING * MODERN STYLING DESIGN * ALL NEW UNUSED COMPONENTS
- * 6 WATT OUTPUT * READY ETCHED & PUNCHED P.C.B.
- * INCORPORATES SUPPRESSION CIRCUITS



The pack contains all the electronic components to build the radio, you supply only the wire and solder as featured in the Practical Electronics March issue. The P.E. Traveller features pre-set tuning with five push button options, black illuminated tuning scale, with matching rotary control knobs, one, combining on/off volume and tone-control, the other for manual tuning, each set on wood simulated fascia. The P.E. Traveller has a 6 watts output, negative ground and incorporates an integrated circuit output stage, a Mullard IF module LP1181 ceramic filter type, pre-aligned and assembled and a Bird pre-aligned push button tuning unit. The P.E. Traveller fits easily in or under dashboards. Complete with instructions.

£10.50 p&p **£1.50**

CONSTRUCTORS PACK 7A
Suitable stainless steel fully retractable locking aerial and speaker (approx 6" x 4") is available as a kit complete.

£1.95 Per Pack, p & p £1.00.
Pack 7A may only be purchased at the same time as Pack 7.


A FEATURED PROJECT IN PRACTICAL ELECTRONICS



323 EDGWARE ROAD, LONDON W2. For Personal Shoppers Only.
21B HIGH STREET, ACTON W3 6NG. Mail Order Only. No Callers.

Mon-Sat 9.30am-5.30pm
Closed Thursday

NEW 12 + 12 AMPLIFIER KIT

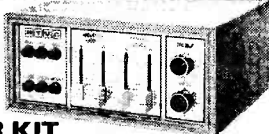


An opportunity to build your own 12 watts per channel stereo amplifier with up-to-the-minute features. To complete you just supply screws, connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs—tape, speakers and headphones. By the press of a button it transforms into a 24 watt mono disco amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus 2 power amplifier assembly kits. Also featured 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia panel with matching knobs. Easy to assemble teak simulate cabinet and ready made metal work. For further information instructions are available price 50p. Free with kit. Size 9 1/4" x 8 3/4" x 4"

NOTE: for use with 4 to 8 ohms speakers p&p £2.55 **£13.95**

50 WATT MONO DISCO AMP £30.60 p&p £2.70



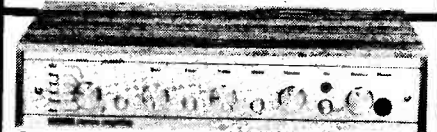Size approx. 13 3/4" x 5 1/4" x 6 3/4"
50 watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.



20 x 20 WATT STEREO AMPLIFIER
Viscount IV unit in teak simulate cabinet Silver finish rotary controls and pushbuttons with matching fascia. red mains indicator and stereo jack socket. Functions switch for mc magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features fuse holder, DIN speaker and input sockets. 20 x 20 watts RMS. 40 x 40 watts peak for use with 8 to 15 ohm speakers. **£31.90**
Size 14 3/4" x 3" x 10" approx. NEW feature—units now includes a built in four channel stereo sound facility. **£3.00 p&p**

Mullard AUDIO MODULES IN BARGAIN PACKS

ACCESSORIES ARE ONLY AVAILABLE TO THOSE CUSTOMERS WHEN BUYING OUR BARGAIN PACKS

CURRENT CATALOGUE PRICE AT OVER

£25 PER PACK

SEE OUR PRICES



1 PACK 1 2 x LP1173 10w RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input. OUR PRICE **£5.00** p+p £1.00

2 PACK 2 2 x LP1173 10w RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs. illus. OUR PRICE **£7.65** p+p £1.00

ACCESSORIES Suitable mains power supply parts, consisting of mains transformer, bridge rectifier, smoothing capacitor and set of rotary stereo controls for treble, bass. **£3.00** plus £1.50 p&p

Two Way Speaker Kit Comprising of two 8" x 5" approx. 4 ohm bass and two 3 1/2" 15 ohm mid-range tweeter with two cross-over capacitors. AVAILABLE ALSO TO PURCHASERS OF THE 10 + 10 AMPLIFIER KIT Per stereo pair plus **£1.55 p&p £4.05**



323 EDGWARE ROAD, LONDON W2
21B HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only. No callers
ALL PRICES INCLUDE VAT AT 15%
All items subject to availability. Price correct at 1.2.80 and subject to change without notice.
All enquires Stamped Addressed Envelope.
NOTE: Persons under 16 years not served without parent's authorisation.

30x30 WATT AMPLIFIER IN KIT FORM

For the experienced constructor complete in every detail, same facilities as Viscount IV, but with 30x30 output 60x60 watts peak. For use with 4 to 15 ohms speakers **£31.50** p&p **£3.00**



EMI SPEAKER BARGAIN

Stereo pair 350 kit. System consists of 13" x 8" approx woofer with rolled surround. 3 1/2" Goodman tweeter crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS. 20 watts max. 8 ohm impedance. **£18.25** p&p **£3.65** Per stereo pair **£3.65 p&p**



BSR P200 £25.50

Belt drive chassis turntable unit semi-automatic, cueing device. p&p **£2.60**
Shure M75 6 Magnetic Cartridge to suit. **£7.95**



BSR Manual single play record deck with auto return and cueing lever. fitted with stereo ceramic cartridge 2 speeds with 45 r.p.m spindle adaptor ideally suited for home or disco use. **£12.25** p&p **OUR PRICE £2.75**

PHILLIPS RECORD PLAYER DECK GC037

HiFi record player deck, belt drive complete with GP401 magnetic cartridge—LIMITED STOCK. **£27.50** complete. UNBEATABLE OFFER AT BUYER COLLECT ONLY.




BARGAIN OFFER
Ariston pick-up arm manufactured in Japan. Complete with headshell. Listed price over **£30.00**. **OUR PRICE £11.95** p&p **£2.50**

OUR PRICE £11.95 p&p **£2.50**

Personal Shoppers EDGWARE ROAD LONDON W2 Tel: 01-723 8432. 9.30am-5.30pm. Closed all day Thursday. ACTON: Mail Order only. No callers. GOODS DESPATCHED TO MAINLAND AND N. IRELAND ONLY

TUNE IN!

Build the World Famous
CHROMA-CHIME

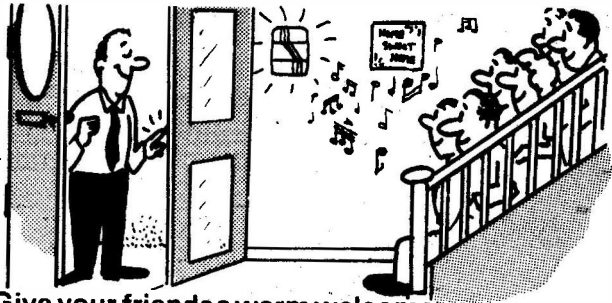

Give your friends a warm welcome

This kit has been carefully prepared so that practically anyone capable of neat soldering will have complete success in building it. The kit manual contains step by step constructional details together with a fault finding guide, circuit description, installation details and operational instructions all well illustrated with numerous figures and diagrams.

- Handsome purpose built ABS cabinet
- Easy to build and install
- Uses Texas Instruments TMS1000 microcomputer
- Absolutely all parts supplied including I.C. socket
- Ready drilled and legended PCB included
- Comprehensive kit manual with full circuit details
- No previous microcomputer experience necessary
- All programming permanently retained is on chip ROM
- Can be built in about 3 hours!
- Runs off 2 PP3 type batteries.
- Fully Guaranteed

* Save pounds on normal retail price by building yourself.

**ONLY
£9.95**
+ 75p p&p
UK ONLY

TMS 1000N

-MP0027A Micro-computer chip available separately if required. Full 24 tune spec device fully guaranteed.

This unique chip can be used not only for electronic door chimes but for other projects requiring musical output: **New low price only**

Car Horns
Musical Boxes
Amusement Machines
Alarms
Public Address etc

£4.95 inc. ip & p.
Free applications manual and data supplied with device!
(Or 30p separately.)

ALL CHROMATRONICS PRODUCTS SUPPLIED WITH MONEY BACK GUARANTEE
PLEASE ALLOW 7-21 DAYS FOR DELIVERY

Please send me:

TO: CHROMATRONICS, RIVER WAY, HARLOW, ESSEX.

NAME _____

ADDRESS _____

I enclose cheque/PO value £ _____

or debit my ACCESS/BARCLAYCARD account no. _____

Signature _____


CHROMATRONICS

LIGHTING & AMPLIFIER MODULES FROM L & B

01-6894138

YOU'VE ALL HEARD OF OUR SUPERB MODULES, AND IF YOU HAVEN'T, IT'S TIME YOU DID, SO READ ON! SHOWN HERE ARE A RANGE OF THE MOST RELIABLE SYSTEMS ON THE MARKET.

LB31000SLC
£29.90

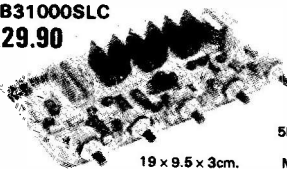


19 x 9.5 x 3cm.

LB31000SL SOUND TO LIGHT. A SUPERB PERFORMING SYSTEM AT AN INCREDIBLY LOW PRICE.
3 channels. 1000w each. Fully fused. Very high input impedance. Operates from 1/4 to 300w sound input. Third order filters. Zero voltage fired. Master/Vol/Base/Mid/Treble controls.

LB31000SLC SOUND TO LIGHT/CHASER. THE MOST ADVANCED SOUND TO LIGHT MODULE AVAILABLE, WITH AUTOMATIC SWITCHING TO CHASE UPON ABSENCE OF A MUSIC INPUT.

3 Channels, 1000w each. Fully fused Very high input Impedance. Electronic filters. 5HZ to 70KHz bandwidth. Operates from 1/4 to 300w sound input. Triac zero voltage triggering. Master Vol/Base/Mid/Treble/Chase speed controls.

LB31000SL
£21.40

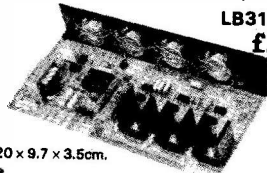

20 x 9.7 x 3.5cm.


£26.50
LB81000LC

19 x 9.5 x 3cm.

LB41000LS LOGIC RANDOM SEQUENCER, WITH TWO SPEED CONTROLS OFFERING A WIDE RANGE OF EFFECTS.

4 channels, 1000w each. CMOS circuitry. Zero voltage fired.

LB31000LD

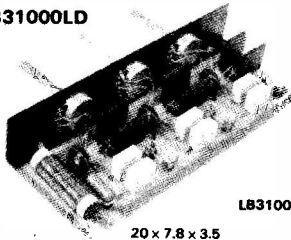

20 x 7.8 x 3.5


POWER AMPS, 250, 150, 100 & 25W RMS. RUGGED TOUGH DEALING POWER AMP MODULES.

Full spec available in our catalogue.

LB250	LB150	LB100	LB25
10Hz TO 25KHz S/N 110dB THD 0.1% 0.5v SENS	10Hz TO 25KHz S/N 110dB THD 0.1% 0.5v SENS	10Hz TO 25KHz S/N 110dB THD 0.1% 0.5v SENS	20Hz TO 50KHz S/N 90dB THD 0.07% 0.5v SENS
£39.50	£26.50	£18.20	£11.20

LB81000LC CHASER. A FULLY DIGITAL 8 CHANNEL CHASER, ALLOWING VARIATION OF CHASE SPEED AND CHASE RETURN DELAY.

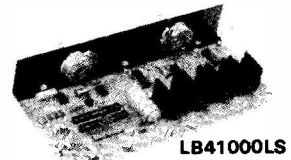1000w per channel. CMOS circuitry. Zero voltage fired. Can be footswitch triggered. Additional modules can be cascaded to form 16, 24, 32 chan etc.




LB41000LS
£17.50

20 x 9.2 x 3.5cm.

LB31000LD AND 11000LD DIMMERS. FULL POWER 3 & SINGLE CHANNEL LIGHTING DIMMERS FOR USE IN CLUBS/PUBS/THEATRES/SCHOOLS, ETC.

1000w per channel. Fully fused phase controlled. Full input and individual Triac filters.

LB31000LD £14.70 LB11000LD £6.70

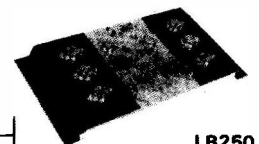

LB250
27 x 15 x 3.6cm.

POWER SUPPLIES

Four types of powerful supply units for our power amps. Consisting of a varnish-impregnated mains transformer and rectifier board (fuse protected).

LB250PS £24.50
LB150PS £18.00
LB100PS £14.70
LB25PS £11.20

PREAMPS

LBPA3. Complete stereo disco preamp system. Comprising of L&R deck mixers, mic mixer, deck and mic tone stages, mic auto fade over decks, PFL, output drivers and its own regulators.

LBPA2. General purpose 4 chan. mixer/tone stage.

LBPA1. Stereo Hi-Fi System




LBPA1 £19.50
LBPA2 £17.20

LBPA3-M (magnetic deck inputs) £30.70

LBPA3-C (ceramic deck inputs) £30.70

LBPA3-M
20.4 x 9.5cm.

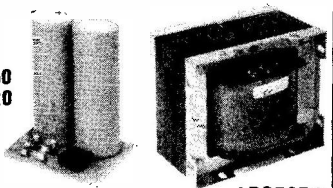

LB250PS

YOU REQUIRE A BOARD THAT'S MIGHTY COMPETITIVE, RELIABLE, MANUFACTURED FROM THE HIGHEST QUALITY COMPONENTS, OF HIGH PERFORMANCE, TESTED AND INSPECTED, SUPPLIED WITH CONNECTION AND CCT, DGM AND GUARANTEED. IN TWO LETTERS YOU REQUIRE L & B.

All prices shown are inclusive of VAT (15%)
P/packing FREE in the UK except power supplies (£1.00)
Trade and Overseas Inquiries welcome.
For your FREE catalogue send a 10p stamp to:

L & B 45 WORTLEY ROAD
WEST CROYDON
SURREY CR9 3EB
ELECTRONIC TEL. 01-6894138



The pocket sized solar cell from Ferranti.

It's the Ferranti ESC3, a rugged and reliable building block for the construction of small solar power arrays.

Designed for educational use and experiments, it's rugged, with strong casing, clear fresnel lens and solid metal terminal pins. Output 0.5V/0.8A.

We also offer the ESC3/6, which has six individual cells connected in series—output 3.0 volts/0.11 amps. Schools and universities will find these cells ideal for silicon solar cell characterisation tests, and for measuring spectral response, V/I characteristics and temperature dependence of output.


They can also be interconnected for driving

electronic circuitry or d.c. motors, or for recharging batteries, and used in industry for basic experimental work and one-offs.

Price: ESC3 module: up to 20 off **£12.14** each
21 to 50 off **£10.20** each

ESC3/6 Prices on application.

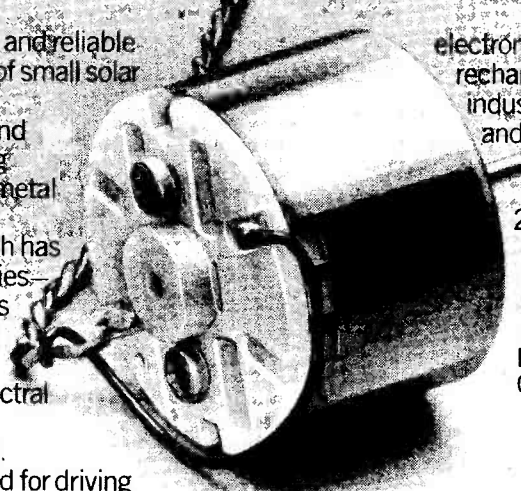From Hird Brown Electronics Limited, Lever St., Bolton. Tel: (0204) 386361 or Ferranti Electronics Limited, Fields New Road, Chadderton, Oldham OL9 8NP. Tel: 061-624 0515



FERRANTI
Semiconductors

The NEW Marshall's 79/80 catalogue is just full of components

and that's not all . . .

... our new catalogue is bigger and better than ever. Within its 60 pages are details and prices of the complete range of components and accessories available from Marshall's.

These include Audio Amps, Connectors, Boxes, Cases, Bridge Rectifiers, Cables, Capacitors, Crystals, Diacs, Diodes, Displays, Heatsinks, I.C.s, Knobs, LEDs, Multimeters, Plugs, Sockets, Pots, Publications, Relays, Resistors, Soldering Equipment, Thyristors, Transistors, Transformers, Voltage Regulators, etc., etc.

Plus details of the NEW Marshall's 'budget' Credit Card. We are the first UK component retailer to offer our customers our own credit card facility.

Plus — Twin postage paid order forms to facilitate speedy ordering.

Plus — Many new products and data.


Plus 100s of prices cut on our popular lines including I.C.s, Transistors, Resistors and many more.

If you need components you need the new Marshall's Catalogue.

Available by post 65p post paid from **Marshall's, Kingsgate House, Kingsgate Place, London NW6 4TA**. Also available from any branch to callers 50p.



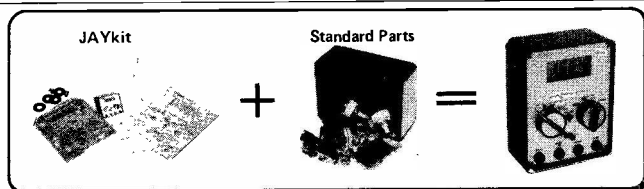Retail Sales: London: 40 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/2. Also 325 Edgware Road, W2. Tel: 01-723 4242. Glasgow: 85 West Regent Street, G2 2QD. Tel: 041-332 4133. And Bristol: 108A Stokes Croft, Bristol. Tel: 0272 426801/2.



DM-2



DIGITAL MULTIMETER

- ★ DC Volts 1mV to 1000V
- ★ AC Volts 1V to 500V
- ★ DC Current 0.1mA to 0.2A
- ★ Resistance 1Ω to 20MΩ
- ★ 3½ digit LCD
- ★ Auto Low Battery indication
- ★ Auto Polarity & Zero
- ★ 1% accuracy (DC volts)
- ★ Designed around Intersil 7106 IC
- ★ Total cost around £30 (incl. case)

FG-1a



FUNCTION GENERATOR

- ★ 30mV to 10V pk-pk
- ★ 1Hz to 100kHz
- ★ DC coupled
- ★ Sine, Square & Triangle
- ★ Separate TTL output
- ★ Designed around Intersil 8038 IC
- ★ Total cost around £25 (incl. case)

Provided in a JAYkit is a Printed Circuit Board, a punched and lettered Front Panel overlay, a Circuit Diagram and Instruction Sheet and a comprehensive and up to date Component List showing suppliers and current prices. Difficult to obtain pieces of hardware are supplied with the kit.

Jayen Developments, 21 Gladeside, Bar Hill, Cambridge CB3 8DY

To: JAYEN Developments
21 Gladeside, Bar Hill,
Cambridge CB3 8DY
Tel: (0954) 80285

Name _____
Address _____

Please send:

- DM-2 @ £5.45
 - FG-1a @ £4.95
- (Incl. VAT and P&P)

Money to be refunded if the kit is returned within 10 days.

JAYkits

AURA SOUNDS AND WERSI

Are pleased to announce a new kit in the Wersi Do-it-Yourself Organ range. Fantastic value at only **£220.00 COMPLETE**. Fill in the coupon now for advance details and send to:—

AURA SOUNDS 14-15 Royal Oak Centre, Brighton Road, Purley, Surrey. Tel: 01-668 9733 and at 17 Upper Charter Arcade, Barnsley, W. Yorks. Tel: Barnsley (0226) 5248

Name.....
Address.....
(PE4)

The Proto-Board®

Now circuit designing is as easy as pushing a lead into a hole ...
 No soldering
 No de-soldering
 No heat-spoilt components
 No manual labour
 No wasted time




For quick signal tracing and circuit modification
 For quick circuit analysis and diagramming
 With or without built-in regulated power supplies
 Use with virtually all parts — most plug in directly, in seconds.
 Ideal for design, prototype and hobby

NO	MODEL NO	NO OF SOLDERLESS TIE POINTS	IC CAPACITY (14-pin DIPs)	UNIT PRICE	PRICE INC P&P 15% VAT	OTHER FEATURES
1	PB 6	630	6	9.20	11.73	Kit
2	PB 100	760	10	11.80	14.72	Kit
3	PB 101	940	10	17.20	21.21	
4	PB 102	1240	12	22.95	27.83	
5	PB 103	2250	24	34.45	41.34	
6	PB 104	3060	32	45.95	54.56	
7	PB 203	2250	24	55.15	65.14	5V @ 1A
8	PB 203A	2250	24	74.70	87.63	5V ± 15V
9	PB 203AK	2250	24	59.00	69.57	& Kit

Tomorrows tools for todays problems

CONTINENTAL SPECIALTIES CORPORATION

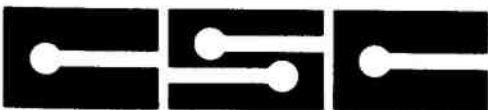

C.S.C. (UK) Limited,
 Dept. 5U Unit 1, Shire Hill Industrial Estate,
 Saffron Walden, Essex. CB11 3AQ.
 Telephone: Saffron Walden (0799) 21682
 Telex: 817477.

C.S.C. (UK) Ltd., Dept 5U Shire Hill Industrial Estate, Unit 1, Saffron Walden Essex. CB11 3AQ

1 Qty Req	2 Qty Req	3 Qty Req	4	5 Qty Req	6 Qty Req	7 Qty Req	8 Qty Req	9 Qty Req
-----------	-----------	-----------	---	-----------	-----------	-----------	-----------	-----------


Name _____ Address _____

I enclose Cheque/P.O. for £ _____ or debit my Barclaycard, Access,
 American Express card no. _____ exp. date _____


FOR IMMEDIATE ACTION — The C.S.C. 24 hour 5 day a week service
 Telephone (0799) 21682 and give us your Barclaycard, Access,
 American Express number and your order will be in the post immediately

For FREE catalogue tick box

The professional scopes you've always needed.

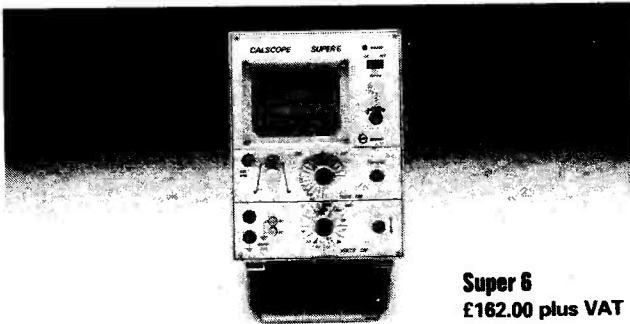

Super 6
£162.00 plus VAT

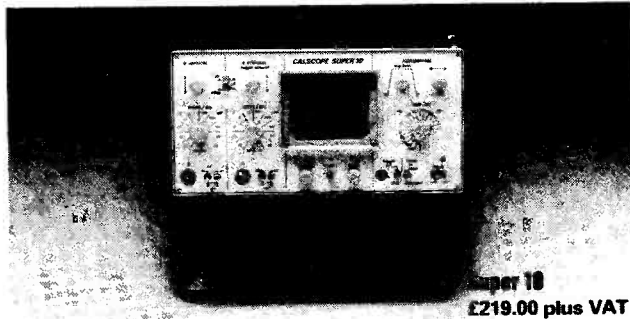

Super 10
£219.00 plus VAT

When it comes to oscilloscopes, you'll have to go a long way to equal the reliability and performance of Calscope.

Calscope set new standards in their products, as you'll discover when you compare specification and price against the competition.

The Calscope Super 10, dual trace 10 MHz has probably the highest standard anywhere for a low cost general purpose oscilloscope. A 3% accuracy is obtained by the use of stabilised power supplies which cope with mains fluctuations.

The price £219 plus VAT.

The Super.6 is a portable 6MHz single beam model with easy to use controls and has a time base range of 1µs to 100ms/cm with 10mV sensitivity. Price £162 plus VAT.

Prices correct at time of going to press

CALSCOPE DISTRIBUTED BY

Watford Electronics
33-35 Cardiff Road,
Watford, Herts.
Tel: 0923 40588

Audio Electronics,
301 Edgware Road, London W.2.
Tel: 01-724 3564
Access and Barclay card facilities
(Personal Shoppers)

Maplin Electronics Supplies Ltd.
P.O. Box 3
Rayleigh, Essex.
Tel: 0702 715 155
Mail Order

CALSCOPE

microtan 65

6502 based microcomputer. Superb 1K monitor TANBUG. Expands into a system. VDU alphanumeric display on un-modified domestic TV. Optional chunky graphics. Excellent documentation.

1K RAM for user programme stack & display memory. Optional lower case pack making 128 displayable characters.

MICROTAN 65 outperforms all other small microcomputers in terms of value for money and performance.

It is much easier to use as a result of the video display, intelligent keyboard socket, and very powerful monitor. The system grows to become a very useful, complete micro-computer in sensibly priced and very well designed modules.

Quite simply the best microcomputer system.


IDEAL

as a self teaching tool for beginners,
as a low cost 6502 development system,
as a basis for a powerful microcomputer in its expanded form.

CALL OR PHONE FOR FULL DETAILS or send COUPON plus 12p STAMP to

FOREHILL WORKS, FOREHILL, ELY, CAMBS. TEL: COMPUTER SYSTEMS (0353) 3633

TANGERINE

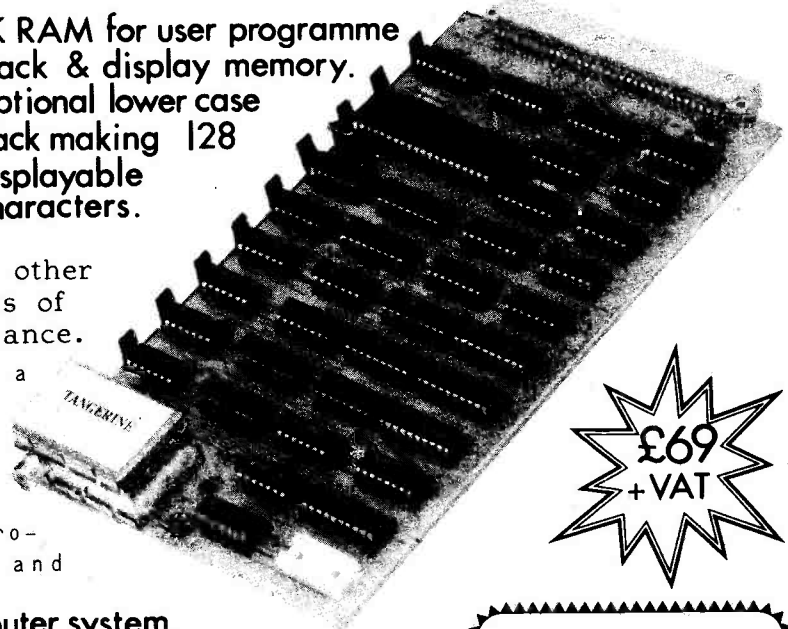


£69
+ VAT

NAME
ADDRESS
.....
.....

TANGERINE

C/MOS PRICE INCREASE: PLEASE ADD 25% TO LAST MONTH'S PRICES AS ADVERTISED

FULL SPEC KIT TELETEXT DECODER

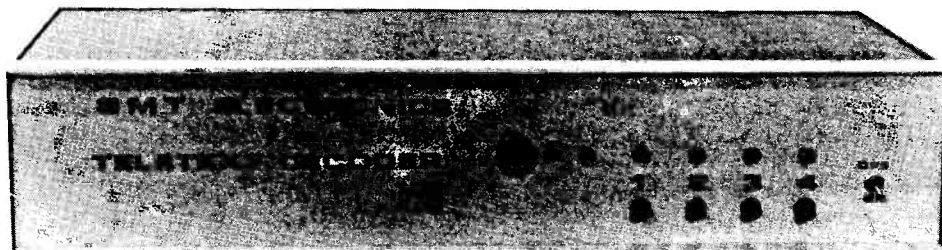

- STATE OF THE ART L.S.I. CIRCUITS
- DOUBLE HEIGHT CHARACTER SELECTABLE FOR LEGIBILITY
- CHARACTER ROUNDING - EFFECTIVELY DOUBLES DEFINITION
- ULTRASONIC REMOTE CONTROL
- HIGH QUALITY THROUGH PLATED P.C.B.
- ALL I.C. MOUNTED ON SOCKETS
- PREALIGNED UHF/IF MODULES
- NEEDS NO INTERNAL CONNECTION TO THE TELEVISION SET
- SIZE 430mm x 90mm x 220mm
- SUPPLY 240v 50Hz 35w
- *NEW *TOUCH CONTROL KEYPAD* NEW*

INCLUDES TUNER, P.S.U., DECODER, REMOTE KEYBOARD, P.A.L. ENCODER, U.H.F. MODULATOR CASE WITH SCREENED AND PUNCHED FRONT PANEL.

— **£189.90 inc VAT.** P & P £3.00.


FULL TELETEXT MANUAL IF BOUGHT SEPARATELY — **£2.50** P & P £0.50.

P.C.B.'S AND L.S.I. I.C.'S NOT SOLD SEPARATE FROM KITS.

P & P INCLUDES CARRIAGE, PACKING AND INSURANCE

C/MOS PRICE INCREASE: PLEASE ADD 25% TO LAST MONTH'S PRICES AS ADVERTISED


F.E.T. POWER AMPLIFIER

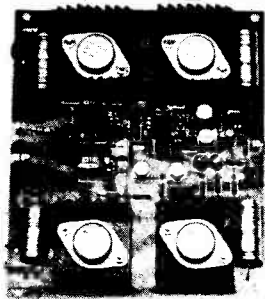

Bring your HI-FI up to date. Available now is a 100 watt audio amplifier using POWER MOSFETS. The POWER MOSFET has several advantages over bipolar transistors. It has good frequency response, no carrier storage delay, thermal stability, no secondary breakdown, and high input impedance. The MOSFET Amplifier has been designed to deliver a continuous power output of 100 watts with full heatsinking into 8 ohms from 5 Hz to 100 kHz with no more than 0.01% total harmonic distortion, which is about a tenfold improvement on ordinary bipolar techniques. The high output impedance and thermal stability of the MOSFET reduces the size of the total circuit by about 30%. The kit does not include a case.

POWER MOSFET AMPLIFIER MODULE **£27.50**


DOPPLER RADAR ALARM

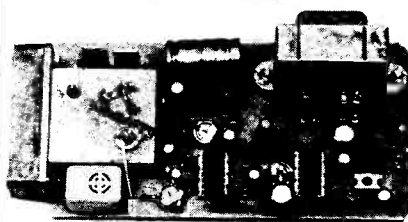

Do your goodies need protecting? No need to run miles of wire, and hack window and door frames to pieces. Just build a Doppler Radar Alarm kit. It can be mains or battery operated (external battery required), and is triggered by any movement in its detection area. It incorporates an arming delay - to enable you to leave its detection field safely, and a trigger delay (0 to 45 seconds), so you can catch the thief red handed without a prior warning having been given. The unit provides a 12 volt output, normally high (low on alarm), to supply an external remote relay, which is not supplied. The unit has an integral buzzer to give an indication when the unit is being armed, and when triggering is complete. The unit comes complete with a suitable case.

DOPPLER RADAR ALARM **£39.50**

1 AMP P.S.U.

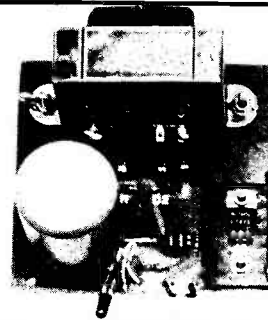


Need a one amp power supply at five volts or twelve volts? Fed up with lash ups? Here is a basic 'no frills' 1 amp P.S.U. kit, based on the well known ua7800 series three terminal regulators. When assembled, all components, including the transformer, are mounted on the printed circuit board. Use the module as a bench power supply, or as part of a piece of equipment.

1 AMP PSU - 5 VOLTS **£6.00**

1 AMP PSU - 12 VOLTS **£7.50**

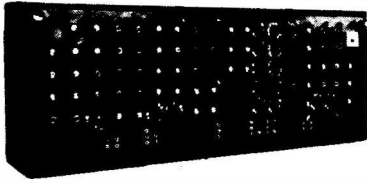D.I.Y. KITS FOR SYNTHESISERS, SOUND EFFECTS



BASIC COMPONENTS SETS include all necessary resistors, capacitors, semiconductors, potentiometers and transformers. Hardware such as cases, sockets, knobs, keyboards, etc. are not included but most of these may be bought separately. Fuller details of kits PCBs and parts are shown in our lists.

LAYOUT DIAGRAMS are supplied free with all PCBs unless "as published".

PHONOSONICS

MAIL ORDER SUPPLIERS OF QUALITY PRINTED CIRCUIT BOARDS, KITS AND COMPONENTS TO A WORLD-WIDE MARKET

P.E. 128-NOTE SEQUENCER

Enables a voltage controlled synthesiser to automatically play pre-programmed tunes of up to 32 pitches and 128 notes long. Programs are keyboard initiated and note length and rhythmic pattern are externally variable.

Set of basic component kits, PCBs and layout charts
KIT 76-7 **£34.58**
Set of text photocopies **£1.36**

P.E. 16-NOTE SEQUENCER

Sequences of up to 16 notes may be programmed by the use of external panel controls and fed into most voltage controlled synthesisers.

Set of basic component kits, PCBs and layout charts
KIT 86-5 **£27.99**
Set text photocopies **£1.84**

P.E. STRING ENSEMBLE

A multivoiced polyphonic string instrument synthesiser.

Set of basic component kits, PCBs & layout charts
KIT 77-8 **£92.89**

P.E. JOANNA PLUS ORGAN VOICING

A modified version of the P.E. 5-octave piano that retains all the original facilities and includes organ voicing circuitry.

Set of basic component kits, PCBs & layout charts
KIT 71-7 **£119.87**
"Sound Design" booklet **£1.00**

ELEKTOR ELECTRONIC PIANO

A touch-sensitive multiple-voicing piano using the latest integrated circuit techniques for the keying and envelope shaping, and virtually eliminating "bee-hive" noise hitherto inherent in previous electronic pianos.

5-octave set of basic components and PCBs (as published)
KIT 80-9 **£136.41**
Additional 3-octave extension and basic parts and PCBs (as published)
KIT 80-10 **£54.62**
Set of text photocopies **£1.81**

P.E. MINISONIC MK2 SYNTHESIZER

A portable mains operated miniature sound synthesiser with keyboard circuits. Although having slightly fewer facilities than the large Formant and P.E. synthesisers the functions offered by this design give it great scope and versatility.

Set of basic component kits (excl. KBD R's & tuning pots—see list for options available) and PCBs (incl. layout charts)
KIT 38-26 **£76.92**
"Sound Design" booklet **£1.00**

P.E. SYNTHESIZER

The well acclaimed and highly versatile large scale mains operated synthesiser. Other circuits in our lists may be used with it to good advantage.

Main Unit basic component kits, PCBs & layout charts
KIT 23-31 **£101.43**
Keyboard Unit basic component kits, PCBs & layout charts
KIT 23-32 **£60.47**
Main Unit set of text photocopies **£5.91**
Keyboard Unit set of text photocopies **£2.30**

ELEKTOR FORMANT SYNTHESIZER

A very sophisticated synthesiser for the advanced constructor who puts performance before price.

Set of basic component kits, PCBs (as published)
KIT 66-14 **£247.60**
Set of text photocopies **£7.83**

P.E. GUITAR EFFECTS UNIT

Modulates the attack, decay and filter characteristics of a signal from most audio sources, producing 8 different switchable effects that can be further modified by manual controls.

Basic parts with foot switches, PCB & layout chart
KIT 78-3 **£10.02**
Text photocopy **28p**

ELEKTOR DIGITAL REVERB UNIT

A very advanced unit using sophisticated i.c. techniques instead of mechanical spring lines. The basic delay range of 24 to 90ms can be extended up to 450ms using the extension unit. Further delays can be obtained using more extensions.

Main unit basic component kit and PCB (as published)
KIT 78-3 **£53.68**
Extension unit basic component kit and PCB (as published)
KIT 78-4 **£48.85**
Text photocopy **86p**

ELEKTOR ANALOGUE REVERB

Using i.c.s instead of spring-lines the main unit has a maximum delay of up to 100ms, and the additional set extends this up to 200ms. May be used in either mono or stereo mode.

Main unit basic component set
KIT 83-1 **£29.49**
Additional Delay basic components
KIT 83-2 **£20.07**
PCB (as publ.) to hold both kits
PCB9973 **£4.31**
Text photocopy **67p**

P.E. GUITAR MULTIPROCESSOR

An extremely versatile sound processing unit capable of producing, for example, flanging, vibrato, reverb, fuzz and tremolo as well as other fascinating sounds. May be used with most electronic instruments.

Set of basic component kits, PCBs & layout charts
KIT 85-5 **£54.37**
Set of text photocopies **£2.52**

P.E. PHASER

An automatically controlled 6-stage phasing unit with integral oscillator.

Basic components, PCB & chart
KIT 88-1 **£10.14**
2-Notch extension, PCB & chart
KIT 88-2 **£6.36**
Text photocopy **68p**

ELEKTOR PHASING & VIBRATO

Includes manual and automatic control over the rate of phasing & vibrato, and has been slightly modified to also include a 2-input mixer stage.

Set of basic components, PCB & layout chart
KIT 70-2 **£21.67**
Text photocopy **67p**

P.E. PHASING UNIT

A simple but effective manually controlled phasing unit.
Basic components, PCB & chart
KIT 25-1 **£3.52**
Text photocopy **28p**

PHASING CONTROL UNIT

For use with Phasing Kit 25 to automatically control rate of phasing.
Basic components, PCB & chart
KIT 36-1 **£5.21**
Text photocopy **10p**

P.E. SWITCHED TONE TREBLE BOOST

Provides switched selection of 4 preset tonal responses.
Basic components, PCB & chart
KIT 89-1 **£3.82**
Text photocopy **78p**

P.E. TREBLE BOOST UNIT

A simple treble boost unit with manual control depth.
Basic components, PCB & chart
KIT 53-1 **£2.76**

ELEKTOR RESONANCE FILTER

Allows a synthesiser to produce a more realistic simulation of natural musical instruments.

Set of basic components & PCB (as published)
KIT 82-2 **£19.90**
Text photocopy **57p**

P.E. GUITAR OVERDRIVE

Sophisticated versatile fuzz unit incl. variable controls affecting the fuzz quality whilst retaining attack and decay, and also providing filtering. Usable with most electronic instruments.

Basic components, PCB & chart
KIT 56-3 **£9.35**
Text photocopy **68p**

P.E. SMOOTH FUZZ

Basic components, PCB & chart
KIT 91-1 **£5.01**
Text photocopy **55p**

TREMOLO UNIT

A slightly modified version of the simple P.E. unit.

Basic components, PCB & chart
KIT 54-1 **£3.23**

GUITAR FREQUENCY DOUBLER

A slightly modified and extended version of the P.E. unit.

Basic components, PCB & chart
KIT 74-1 **£4.97**
Text photocopy **39p**

P.E. GUITAR SUSTAIN

Maintains the natural attack whilst extending note duration.

Basic components, PCB & chart
KIT 75-1 **£5.64**
Text photocopy **38p**

P.E. WAH-WAH UNIT

Can be controlled manually or by integral automatic control.

Basic components, PCB & chart
KIT 51-1 **£3.99**

P.E. AUTO-WAH UNIT

Automatically gives Wah or Swell sounds with each note played.

Basic components, PCB & chart
KIT 58-1 **£8.43**
Text photocopy **58p**

ELEKTOR WAVEFORM CONVERTER

Converts a saw-tooth waveform into sinewave, mark-space saw-tooth, regular triangle, or square-wave with variable mark-space.

Basic components, PCB & chart,
but excl. sw's
KIT 67-1 **£9.24**

P.E. V.C.F.

A voltage controlled filter extracted from P.E. Minisonic project.

Basic components, PCB & chart
KIT 65-1 **£7.88**

P.E. RING MODULATOR

Extracted from P.E. Minisonic project.

Basic components, PCB & chart
KIT 59-1 **£6.05**

ELEKTOR RING MODULATOR

Compatible with the Formant & most other synthesisers.

Set of basic components & PCB (as published)
KIT 87-2 **£6.40**
Text photocopy **38p**

10% DISCOUNT VOUCHER (PE 83)

TERMS: Units in current adverts & lists over £50 goods value (excl. P&P & VAT). Correctly coded, C.V.O., U.K. orders only. This voucher must accompany order. Valid until end of month on cover of P.E. Does not apply to credit card orders.

ADD: POST & HANDLING

U.K. orders: Keyboards add £2.30 each. Other goods: Under £5 add 25p, under £20 add 50p, over £20 add 75p. Recommended insurance against postal mishaps: add 50p for cover up to £50, £1 for £100 cover, etc., pro-rata. Insurance must be added for credit card orders. N.B. Eire, C.I., B.F.P.O. and other countries are subject to higher export postage rates.

ADD 15% VAT

(or current rate if changed). Must be added to full total of kits, discount post & handling on all U.K. orders. Does not apply to Exports, or photocopies.

EXPORT ORDERS ARE WELCOME but to avoid delay we advise you to see our list for postage rates. All payments must be cash-with-order, in Sterling by international Money Order or through an English Bank. To obtain list - Europe send 25p, other countries send 50p.

Note that we do not offer a C.O.D. service and that our terms are payment in advance.

PHONOSONICS · DEPT PE83 · 22 HIGH STREET · SIDCUP · KENT DA14 6EH

TERMS: C.V.O., MAIL ORDER OR COLLECTION BY APPOINTMENT (TEL 01-302 6184)

AND OTHER PROJECTS

PHOTOGRAPHS in this advertisement show two of our units containing some of the P.E. projects built from our kits and PCBs. The cases were built by ourselves and are not for sale, though a small selection of other cases is available.

LIST—Send stamped addressed envelope with all U.K. requests for free list giving fuller details of PCBs, kits and other components.

OVERSEAS enquiries for list Europe—send 20p; other countries—send 50p.



KIMBER-ALLEN KEYBOARDS AND CONTACTS

KIMBER-ALLEN KEYBOARDS as required for many published projects. The manufacturers claim that these are the finest moulded plastic keyboards available. All octaves are C to C, the keys are plastic, spring-loaded, fitted with actuators, and mounted on a robust aluminium frame.

3 Octave (37 notes) **£25.50** 4 Octave (49 notes) **£32.25** 5 Octave (61 notes) **£39.75**

CONTACT ASSEMBLIES (gold-clad wire) — 1 required for each KBD note:

Type GJ — SPCO **25.10** ea. Type GA — 1 pr of contacts, normally open **24p** ea. Type GB — 2 pr N/O **28.10** ea. Type GC — 3 pr N/O **37.10** ea. Type GE — 4 pr N/O **46.10** ea. Type GH — 5 pr N/O **58.10** ea. Type 4PS — 3 pr N/O plus SPCO **67p** ea.

P.E. NOISE GENERATOR

Extracted from the P.E. Minisonic.

Basic components, PCB & chart
KIT 60-1 **£4.00**

WIND & RAIN EFFECTS UNIT

A slightly modified version of the original P.E. unit.

Basic components, PCB & chart
KIT 2B-1 **£4.68**
Text photocopy **28p**

P.E. ENVELOPE SHAPER WITHOUT VCA

Provides full manual control over attack, decay, sustain and release functions, and is for use with an existing VCA.

Basic components, PCB & chart
KIT 44-1 **£5.24**
Text photocopy **49p**

P.E. ENVELOPE SHAPER WITH VCA

Has an integral Voltage Controlled Amplifier, and has full manual control over the A.D.S.R. functions.

Basic components, PCB & chart
KIT 50-1 **£7.34**
Text photocopy **58p**

P.E. TRANSIENT GENERATOR

An ADSR envelope shaper without VCA, and additionally providing Repeat-triggering enabling a synthesiser to be programmed for mandolin or banjo effects.

Basic components, PCB & chart
KIT 63-2 **£7.13**
Text photocopy **58p**

P.E. EXTERNAL-INPUT SYNTHESIZER-INTERFACE

Allows external inputs such as guitars, microphone etc., to be processed by synthesiser circuits.

Basic components, PCB & chart
KIT B1-1 **£3.23**

P.E. TUNING FORK

Produces B4 switch-selected frequency-accurate tones with an LED monitor clearly displaying beat-note adjustments.

Set of basic components, incl. power supply, PCBs & charts
KIT 46-3 **£23.32**
Text photocopy **97p**

P.E. TUNING INDICATOR

A simple 4-octave frequency comparator for use with synthesizers and other instruments where the full versatility of KIT 46 is not required.

Basic components, PCB & chart, but excl. sw.
KIT 69-1 **£8.19**
Text photocopy **58p**

P.E. DYNAMIC RANGE LIMITER

Preset to automatically control sound output levels.

Basic components, PCB & chart
KIT 62-1 **£5.03**

P.E. CONSTANT DISPLAY FREQUENCY COUNTER

A 5-digit counter for 1Hz to 55kHz with 1Hz sampling rate. Readout does not count visibly or flicker due to blanking.

Basic components, PCB & chart
KIT 79-2 **£32.28**
Text photocopy **78p**

P.E. 6-CHANNEL MIXER

A high specification stereo mixer with variable input impedances.

Basic components, (excl. sw.'s) and set of PCBs and charts.
KIT 90-8 **£51.35**
Extra 2-channel set with PCB
KIT 90-9 **£9.69**
Set of Text photocopies **£1.50**

STEREO HEADPHONE AMPLIFIER

Extracted from P.E. 6-channel mixer.

Basic components, PCB & chart
KIT 92-1 **£5.04**

DIGITAL EXPOSURE UNIT

Controls up to 750 watts in $\frac{1}{2}$ second steps up to 10 minutes, with built-in audio alarm.

Basic components, PCBs & charts
KIT 93-3 **£22.40**
Text photocopy **£1.20**

P.E. DISCOSTROBE

A 4-channel light show controller giving a choice of sequential, random, or full strobe mode of operation, and with additional audio input.

Basic components, PCB & chart
KIT 57-2 **£23.79**
Text photocopy **78p**

RHYTHM GENERATORS

Several available, including programmable 16 beat 64000 pattern, 128 beat almost infinite pattern, and pre-programmed 15 pattern using either M252 or M253 rhythm chips. A selection of effects instrument circuits is also available.

P.E. VOICE OPERATED FADER

For automatically reducing music volume during talkover — particularly useful for disco work.

Basic components, PCB & chart
KIT 30-1 **£4.37**

TAPE NOISE LIMITER

Very effective circuit for reducing the hiss found in most tape recordings.

Basic components, PCB & chart
KIT 6-3 **£4.13**



PRICES ARE CORRECT AT TIME OF PRESS.
E. & O. E. DELIVERY SUBJECT TO AVAILABILITY.

PHONOSONICS

All these advantages...


- Instant all-weather starting
- Smoother running
- Continual peak performance
- Longer battery & plug life
- Improved fuel consumption
- Improved acceleration/top speed
- Extended energy storage

..in kit form

SPARKRITE X5 is a high performance, top quality, inductive discharge electronic ignition system designed for the electronic DIY world. It has been tried, tested and proven to be utterly reliable. Assembly only takes 1-2 hours and just a little even less due to the patented clip-on, easy fitting

The superb technical design of the Sparkrite circuit eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which has damaged electrically by a pulse suppression circuit which prevents the contact from the points from opening at top R.P.M. Contact breaker points eliminated by reducing their speed by 95% of the normal

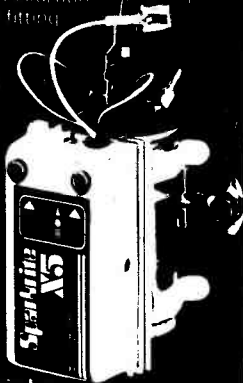There is also a unique extended dwell circuit which allows the coil a longer period of time to store its energy before discharging to the plugs. The circuit includes built-in static timing light system, fuse, fuse light, and security alarm over switch. Will work on all engines.



Fits all 12v negative-earth vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISE SEVE RYTHING NEEDED Die pressed case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips and accessories. All kit components are guaranteed for a period of 2 years from date of purchase. Fully illustrated assembly and installation instructions are included.



Roger Clark the world famous rally driver says "Sparkrite electronic ignition systems are the best you can buy."

Sparkrite

HIGH PERFORMANCE
ELECTRONIC IGNITION

Electronics Design Associates, Dept. PE1179, 82 Bath St., Walsall, WS1 3DE

Electronics Design Associates, Dept. PE480
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 614791

Name _____
Address _____

Phone your order with Access or Barclaycard

Inc. V.A.T. and P.P.

QUANTITY REQ'D.

I enclose cheque/PO's for

X5KIT £16.95

£

Cheque No.

ACCESS OR BARCLAY CARD No.

Send SAE if brochure only required.

MARPLIN

ELECTRONIC SUPPLIES




PRINTED CIRCUIT DRILLS

Miniature 12V DC drills designed for drilling pcb's. Small drill. Order as **BW03D** Price **£5.75**
Large drill. Order as **BW02C** Price **£10.63**



ANTI-STATIC MAT & GUN

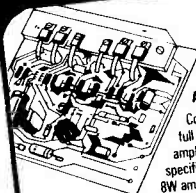Turntable mat removes static from discs while they are playing. Order as **LX10L** Price **£2.95**
Gun removes static charge from discs. After use dust no longer clings and may be easily brushed off. Order as **LX04E** Price **£4.99**



AMP KITS

Complete kits of parts with full instructions to make hi-fi amplifiers with excellent specifications.

8W amp kit. Order as **LW36P** Price **£3.83**
50W amp kit. Order as **LW35D** Price **£13.73**
150W amp kit. Order as **LW32K** Price **£14.89**



HEADPHONES

High quality stereo headphone with large padded headband and slider volume controls. Order as **WF14Q** Price **£7.99**




CONDUCTIVE PAINT

Repair pcb's, car demisters, etc., with this silver paint. Phial contains 3gm. Order as **FY72P** Price **£2.59**



McKENZIE POWER SPEAKERS

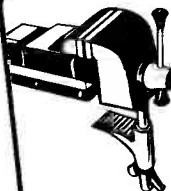High quality, high power speakers. 12in. 50W 8Ω. Order as **XQ79L** Price **£18.79**
12in. 50W 16Ω. Order as **XQ80B** Price **£18.79**
12in. 80W 8Ω. Order as **XQ81C** Price **£26.92**
12in. 80W 16Ω. Order as **XQ82D** Price **£26.92**
15in. 150W 8Ω. Order as **XQ83E** Price **£57.80**
15in. 150W 16Ω. Order as **XQ84F** Price **£57.80**



MINIATURE VICE

Small modellers vice in tough plastic with metal faced jaws. Clamps to bench. Jaws width 41mm, maximum opening 30mm. Order as **FY53H** Price **£2.78**



20,000 OHMIVOLT MULTIMETER

A 20,000 ohms per volt multimeter at an incredibly low price. DC volts 5, 25, 125, 500, 2,500; AC volts 10, 50, 250, 1,000; DC amps 0 to 0.05mA, 0 to 250mA; Resistance 0 to 50k, 0 to 5M ohms; Decibels -20 to +22dB. Complete with test leads, battery and instruction leaflet. Order as **YB83E** Price **£13.70**



ELECTRET MICROPHONES

Super quality genuine electret microphones operating on 1.5V battery (HP7-type) supplied. Cassette type with miniature jack plugs. Order as **YB33L** Price **£3.84**
Omnidirectional low-cost with standard jack plug. Order as **YB34M** Price **£3.75**
Unidirectional 600Ω with standard jack plug. Order as **YB36Q** Price **£3.75**
Unidirectional 600Ω/150kΩ dual with standard jack plug (pictured). Order as **WF34M** Price **£16.77**



WIRING TOOLS

Miniature box-jointed wiring pliers with insulated handles and return spring. Order as **BR69A** Price **£4.52**
Miniature box-jointed side cutters with insulated handles, return spring and precision cutting edges. Order as **BR70M** Price **£4.45**
End action wire strippers, fully adjustable, insulated handles. Order as **BR76H** Price **£5.85**



CLOCK MODULE

Module requires only transformer and two push switches to operate 4-digit, 0.7in red LED display. Alarm and radio outputs. Battery back-up when mains fail. Sleep and snooze timer. Seconds display. Just add speaker for alarm tone. Full details on page 267 of our catalogue. Order as **XL14Q** Price **£8.41**



MEGAPHONE

High quality megaphone with differential microphone. Requires eight HP11 batteries (not supplied). Shoulder strap for portable operation. Order as **XQ72P** Price **£49.50**



DEMAGNETISER

Tape head demagnetiser with curved probe ideal for cassette tape heads. Cures hiss due to permanently magnetised heads. Amazing low price. Order as **F062S** Price **£4.15**



CAR AERIAL BOOSTER

High gain car aerial booster for long, medium, short and VHF bands. Negative earth cars only. Very easy to fit - just plugs in plus one wire to +12V. We have measured gains of 20dB at 90MHz! Order as **XX37S** Price **£5.95**



TEACH YOURSELF ELECTRONICS

There is no better way of learning basic electronics than by practical experience and this set of books is undoubtedly the very best basic course for doing just that. Set of five Basic Electronics books. Order as **XX10L** Price **£8.30**



MULTIMETER & TRANSISTOR TESTER

Superb high sensitivity multimeter and transistor tester in one. Sensitivity 100,000 ohms per volt DC. Ranges DC volts 0.5, 2.5, 10, 50, 250, 1,000; AC volts 5, 10, 50, 250, 1,000; DC current 0.01, 0.025, 0.5, 5, 50, 500mA, 10A; AC current 10A; Resistance 5k, 50k, 5M, 50M ohms; Decibels -10dB to +62dB. Complete with test leads, three leads for transistor tester batteries and instruction leaflet. Order as **YB87U** Price **£39.30**



TURNTABLES


Autochanger complete with stereo ceramic cartridge and circuit to make a complete low cost record player ideal for the young pop fan.

Order as **XD00A** Price **£18.48**
Single-play rim drive turntable with stereo ceramic cartridge. Order as **XB23A** Price **£24.79**
Single-play belt drive turntable 'S' shaped tone arm. Order as **XB25C** Price **£30.63**



TRANSISTOR TESTER

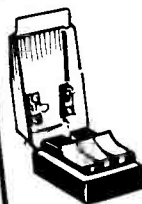Accurate transistor tester measures dynamic gain, identifies unknown transistors, also ideal for matching transistors into pairs. Order as **LW05F** Price **£12.28**



QUICKTEST

A safe and quick way to connect to the mains. Just snap the wires under the sprung keys and close the lid. Completely safe both open and closed. Order as **YB21X** Price **£8.54**

All prices include VAT and postage and packing, but if total under £4 please add 30p handling charge. Prices guaranteed until May 8th 1980. Export customers deduct 13% and export postage will be charged extra at cost. Please use order code. All items in stock at time of going to press.

FOR FULL CATALOGUE DETAILS SEE BACK COVER.

MARPLIN

ELECTRONIC SUPPLIES LIMITED

All mail to PO Box 3, Rayleigh, Essex SS6 8LR. Telephone: Southend (0702) 554155.
Shop: 284 London Road, Westcliff-on-Sea, Essex (closed on Monday). Telephone: Southend (0702) 554000.

THE TROUBLE with looking at the future in electronics is that advances take place so quickly that by the time the prophesies are made the ideas are often already at prototype stage or even in production. Our video supplement takes a look at the present state of the art and also mentions some new techniques. These techniques will undoubtedly lead to a new range of smaller, cheaper domestic recorders though, at the present time, it is difficult to see how LVR will ever achieve the quality of reproduction now available from helical scan recorders. Perhaps by the time these words are published the new machines will be in production.

The video market has now taken off in this country and the indications are that sales will quickly grow over the next few years. What we don't yet know is the influence the videodisc will have.

MONEY

How about electronic money? We warn you that SGS ATES have already made the first steps in that direction with the introduction of an electronic credit card. Designed for an Italian

telephone company—PO where are you?—the card is intended for use with pay phones but the implications are obvious.

In the future you may never need loose change, in fact we can foresee a time when the minting and printing of money will no longer be necessary. Instead of drawing out money from your bank you simply get a new card. You then use your card for purchases—possibly over the phone—or stick it in the till or ticket barrier on the bus, at the station, cinema, sports centre, etc.

Each time you use the card the relevant credits are used up. When all the credits are used the card reader withholds the goods or services. Where are the benefits? No money to be stolen or carted to the bank—no loose change to carry or acquire when necessary. For the vendor it also means payment in advance, reduced machine maintenance and no money left in machines to tempt thieves. It will be possible to develop tills to accept the cards, to put card readers in taxis, TV's, petrol pumps, amusements etc.

Once again this is a product that is now available; the type numbers are M274D1 for the d.i.l. ceramic evalua-

tion package and XCARD for the card. The chip is essentially an EPROM of 17 x 8 bits with a claimed 100 year data retention.

Security is taken care of by writing in an 8 bit word during manufacture and then blowing an on-chip fuse. If any attempt is made to erase the card to regain its original credit value the security key is also erased rendering the card useless. A plastic tab, which has to be removed to use the card, prevents resale after initial use.

APRIL!

Although this is the April issue and certain devices described elsewhere in these pages are not all they seem at first glance, we assure you that the above information has nothing to do with the date and is based on an actual product.

What other advances are there? How about a hi-fi amp of excellent quality for about £70—see the *PE Congress*; an MPU kit for less than £30—read the *EDUKIT* review, or even a *2 Wire Train Controller*—we believe we are the first to publish a design for the hobbyist in the U.K.

Mike Kenward

EDITOR

Mike Kenward

Gordon Godbold ASSISTANT EDITOR

Mike Abbott TECHNICAL EDITOR

David Shortland PROJECTS EDITOR

Jasper Scott PRODUCTION EDITOR

Jack Pountney ART EDITOR

Keith Woodruff ASSISTANT ART EDITOR

John Pickering SEN. TECH. ILLUSTRATOR

Isabelle Greenaway TECH. ILLUSTRATOR

Colette McKenzie SECRETARY

ADVERTISEMENT MANAGER D. W. B. Tilleard } 01-261 6676

SECRETARY Christine Pocknell }

AD. SALES EXEC. Alfred Tonge 01-261 6819

CLASSIFIED MANAGER Colin Brown 01-261 5762

Editorial Offices:

Practical Electronics,
Westover House,
West Quay Road, Poole,
Dorset BH15 1JG
Phone: Editorial Poole 71191

We regret that lengthy technical enquiries cannot be answered over the telephone (see below).

Advertising Offices:

Practical Electronics Advertisements,
King's Reach Tower,
King's Reach, Stamford Street, SE1 9LS
Telex: 915748 MAGDIV-G

Make Up/Copy Dept.: 01-261 6601

Technical Queries

We are unable to offer any advice on the use or purchase of commercial equipment or the incorporation or modification of designs published in Practical Electronics.

All letters requiring a reply should be accompanied by a stamped, self addressed envelope and each letter should relate to **one published project only.**

Components are usually available from advertisers; where we anticipate supply difficulties a source will be suggested.

Back Numbers

Copies of most of our recent issues are available from: Post Sales Department (Practical Electronics), IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at 75p each including Inland/Overseas p&p.

Binders

Binders for PE are available from the same address as back numbers at £4.10 each to UK or overseas addresses, including

postage and packing, and VAT where appropriate. Orders should state the year and volume required.

Subscriptions

Copies of PE are available by post, inland or overseas, for £10.60 per 12 issues, from: Practical Electronics, Subscription Department, Oakfield House, Perrymount Road, Haywards Heath, West Sussex RH16 3DH. Cheques and postal orders should be made payable to IPC Magazines Limited.

Market Place

Items mentioned are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned. All quoted prices are those at the time of going to press.


by
David Shortland

and
Jasper Scott

TEMP PROBE

The new T-10 temperature probe from Racal-Dana Instruments has been designed to turn a digital multimeter into an accurate digital thermometer.

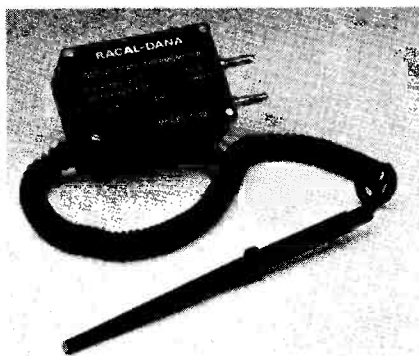The unit uses a constant current bridge circuit with a solid state sensor to give an output of 1mV per degrees Centigrade. The basic accuracy of the T-10 is to within 2 degrees from 0°C to 100°C and to within 3°C from -50°C to 150°C.




The sensor, which is housed in a high temperature plastic probe, is embedded into a low mass brass tip for improved response during measurement. The probe is attached to the main unit via a coiled lead and the compact, self-powered mains unit plugs directly into a multimeter.

The T-10 is priced at £79.00 excluding VAT and p&p.

For further information contact **Racal-Dana Instruments Ltd., Duke Street, Windsor, Berkshire SL4 1SB (07535 69811)**.

RECORD VALET

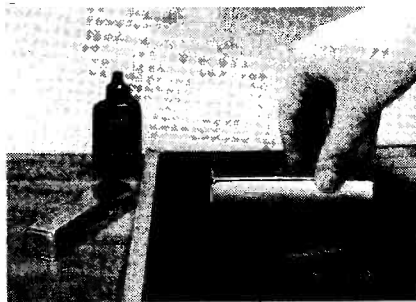The improved Record Valet from BIB is ideal for removing dust and static from gramophone records. The handle is a reservoir for anti-static liquid which is fed to a velvet cleaning pad. Adjacent to the pad is a brush which removes the dust from the record and deposits it on the cleaning pad.



The Valet which should ideally be used before each record is played, to ensure both the record and the stylus are protected is priced at £5.47 including VAT. A 15ml bottle of anti-static cleaning fluid is also included with each Valet.

BIB Hi-Fi Accessories Ltd., Kelsey House, Wood Lane End, Hemel Hempstead, Herts. HP2 4RQ.

HOME RADIO

Home Radio have informed us that they have now moved to new premises at 269A Haydons Road, Wimbledon, London SW19 8TY.

The mail order address is still PO Box 92, 215 London Road, Mitcham, Surrey (01-543 5659).

DMM

The Simwood MC523 battery powered DMM provides a full range of measurement functions, and uses CMOS LSI circuitry for accuracy, long-term operational stability and low power consumption.

Five measurement functions are available with 30 current, voltage and resistance ranges. These consist of five a.c. and five d.c. voltage ranges from 200 mV to 600 V, with basic d.c. accuracies from 0.25 per cent; five a.c. and five d.c. current ranges from 200 µA to 1A,



with accuracies from 0.8 per cent; and ten resistance ranges from 200 ohms to 20 megohms, with accuracies of 0.25 per cent on all but the 20 megohm range. The ohms ranges offer high- and low-power measurement capabilities, for checking both circuit resistance and active components.

The liquid crystal display automatically indicates the measurement parameter—a.c. or d.c. volts; a.c. or d.c. current; ohms; kilohms or megohms—as well as polarity.

Other features of the MC523 which is priced at £75 include a high input resistance, autozero and auto-overrange, and overload indication. Battery life of 200 hours is claimed under normal conditions of usage. The instrument measures 95 x 155 x 45mm and weighs 300g.

Simwood Limited, Garretts Hall, Shalford Green, Essex (0371 820006).

WORDPROCESSOR PACKAGE

The latest WordPro II wordprocessor package from Commodore has been specifically designed for use with the 16K and 32K "big keyboard" versions of their PET Computer. WordPro II is unusual for as well as floppy disk-based software, the package also includes the necessary ROM hardware to accommodate the program functions.


The WordPro II package, which can be installed in the PET with a minimum of fuss, in conjunction with Commodore's 2040 dual drive floppy disk unit, gives the user a capability to process up to 303 pages of text.

Combine this with a printer and you have an extremely powerful computer-word processor system for under £2,600. For applications requiring a high quality print-out, the system configuration can include a daisy

wheel printer instead of the matrix printer, but as such, will still cost less than £4,000.

In operation, WordPro II follows conventional wordprocessor practise. Firstly the text is entered into the PET, using the keyboard and the VDU displays a working text area of 24 lines. As the text is processed, it can be moved either up or down the screen thereby bringing fresh text onto the VDU. A "status line" at the top of the screen ensures that the operator is always fully aware of the cursor position as line editing is carried out.

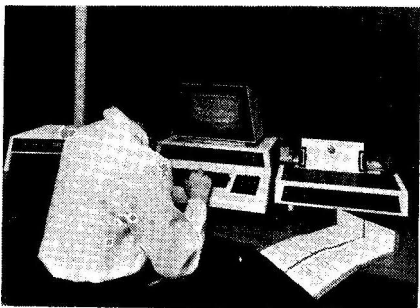Other text handling features include: an option to carry out right hand justification, variable left and right hand margins and a variable page length facility.




Once the text editing is complete, then it can be converted into hard copy via the printer, controlled by a formatting routine. It is therefore possible to produce both multiple copies of a fixed content letter from one command and multiple copies of a variable content letter from one command with insertions, such as name, address etc., taken from a secondary file.

The Commodore WordPro II Wordprocessor package which costs £75 comes complete with ROM, diskette, documentation and demonstration files in a stiff-backed multi-ring binder.

Commodore Business Machines, 360 Euston Road, London NW1 (01-388 5702).

ANTI-STATIC SLEEVE

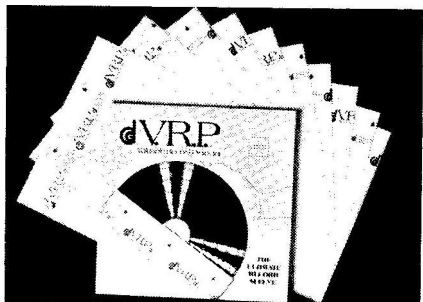A new protective record sleeve which is claimed to offer distinct advantages over ordinary sleeves is being introduced by Zerostat Components Ltd.



The sleeve is made from polypropylene which is extremely smooth for scratch free record removal and replacement. This stable material which is electrostatically compatible to the record vinyl greatly reduces the attraction of static charges.


The Zerostat Discwasher 'VRP' is on sale through hi-fi retailers at approximately £1.95 for a pack of ten or may be ordered direct from **Zerostat Components Ltd., Edison Road, Industrial Estate, St. Ives, Huntingdon, Cambridgeshire PE17 4LF.**

NASCOM PRINTER

A compact, low price printer which accepts both punched and unpunched plain paper is available from Nascom Microcomputers Ltd.

Called the IMP, the printer is of the impact matrix type producing characters in a 7x7 dot matrix at a speed of 80 characters per second. It accepts either pinfeed paper under tractor feed, to a maximum width of 9½ in, or unpunched paper under pressure feed. The latter allows the use of A4, foolscap or quarto letterheads.

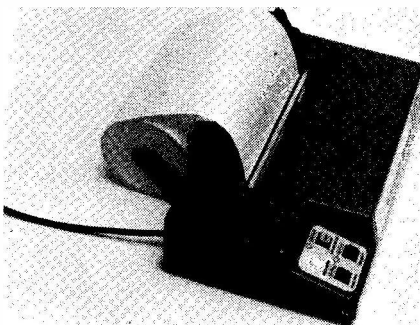The IMP offers bidirectional printing and a 96 ASCII character set with the hash mark replaced with a £ sign. The ribbon used is a cartridge-loaded, endless loop type with a five-million character life.



Input data may be in either seven or eight bit formats with either one or two stop bits. Parity may be odd, even or ignored. Should a data transmission error be detected, an ASCII 7F character will be printed and the operator informed by indicator. "Linefeed" signals may be automatically generated when the printer is in use with computer systems providing only "carriage return" signals. In conjunction with Nascom monitors NAS-SYS 1 and NASBUG T4 this facility may be used to generate double spaced output.


Input is designed for RS232 levels and may be at any standard baud rate between 110 and

KEYBOARD

A solid state ASCII keyboard measuring just 8.2mm thick has been introduced by Interface Components Ltd.

Known as the TASA Micro-Proximity Keyboard the touch-activated keyboard is claimed to be virtually indestructible.

The keyboard is a thin rectangular board with a totally flat surface. The micro-proximity touch sensors are protected by a shield of tough polycarbonate which can be kept clean by wiping with a damp sponge. Because it can be easily cleaned and disinfected, it is ideal for sterile environments. It also can be used in hostile environments where dust, temperature extremes, moisture, chemicals or radio frequency interference are a problem.

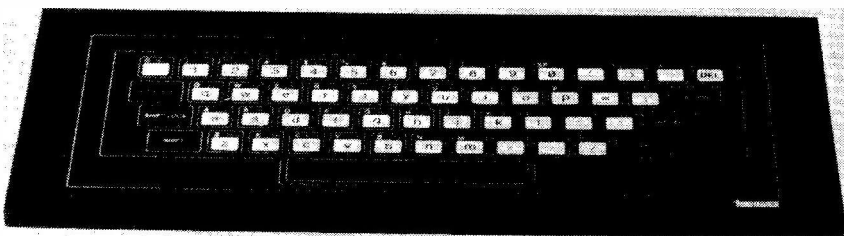

9600. A TTL output is available at 16 times the selected baud rate for operating an external 6402 type UART. A "busy" signal will be output when only 10 characters need to be input to fill the 945 character buffer. The signal will be maintained until more buffer space is available.

Priced at £325 plus VAT, the Nascom IMP is available from Nascom Microcomputers and selected Nascom distributors.

Nascom Microcomputers Ltd, 92 Broad Street, Chesham, Bucks. (02405 75155.)

VERO CATALOGUE

Designed to a new format, the latest 52 page hobbyist catalogue from Vero Electronics contains a wide selection of products that are particularly interesting to the home constructor.

Several new products are illustrated including Verobloc; a new prototyping method of building and testing circuits; a S100 bus system; a rack mountable development kit for evaluation or microprocessor-based systems to the S100 format and low profile d.i.p. sockets.

The catalogue is available for 40p from **Vero Electronics Limited, Industrial Estate, Chandlers Ford, Eastleigh, Hants. SO5 3ZR.**

CO-AX CONNECTORS

From Greenpar Engineering comes a new range of u.h.f. co-axial connectors designed specifically with the hobbyist in mind.

The range consists of three basic designs—free plug, panel socket and straight adaptor. Various versions of the plug are available to suit different types of co-axial cable. All connectors have nickel plated brass bodies and silver plated centre contacts. Phenolic insulators in the plugs and sockets ensure high temperature stability.

The connectors come in packs of ten, and are available direct from: **Greenpar Engineering Ltd., PO Box 15, Station Works, Harlow, Essex.**

Measuring 158mm deep by 382mm wide by 18.2mm thick the keyboard has a full 128 position 8 bit ASCII output plus continuous strobe, parity select. Other features include:

Built-in electronic shift lock; two-key rollover to prevent accidental two-key operation (excluding "control" and "shift") electronic hysteresis for firm "feel"; signal activation time of 1 millisecond; Output via 12-way edge connector; CMOS compatible with pull-up resistor; parallel output: active pull-down, direct TTL compatible (one load) open collector type.

The TASA Keyboard costs £49.50 excluding VAT and is available from **Interface Components Ltd., Oakfield Corner, Sycamore Road, Amersham, Bucks. (02403 5076.)**

MORE BIG VALUE FROM YOUR TANDY STORE

1000 OHMS/VOLTS AC/DC 8 RANGES

Handy multimeter for home and work-shop. Easy-to-read two colour 5cm meter, pin jacks for all 8 ranges. Reads AC and DC volts: 0-15-150-1000 DC current; 0-150 mA. Resistance: 0-100,000 ohms. Accuracy: $\pm 3\%$ full scale on DC ranges, $\pm 4\%$ on AC ranges. Complete battery. 22-027. REG. PRICE


£6.95



6-DIGIT FREQUENCY COUNTER

Counts frequencies from 100 Hz to over 45 MHz with 100 mS gate time. Accuracy is 3 ppm at 25°C or less then ± 30 Mhz on 10 MHz! Overload-protected 1-meg input. Sensitivity, 30 mV up to 30 MHz. Reg. 9V battery. 22-351. REG. PRICE


£79.95

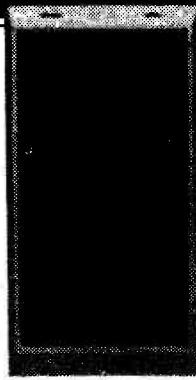

MULTITESTER

Dual FET input for accuracy and minimum loading. 11.5cm mirrored scale. DC volts, 0-1-3-10-30-100-300-1000. DC current 0-100 a. 0-3-30-300 milliamp. Resistance 0-30-300-3k-301C-1 megaohm. 0-100-1k-101C-100K-3 megaohms. Reg. 9V battery. 22-209.


REG. PRICE
£29.95

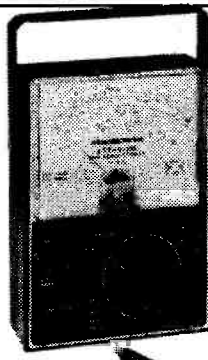

TRANSISTORIZED SIGNAL TRACER

Spot circuit troubles and check RF, IF and audio signals from aerial to speaker on all audio equipment. With 9V battery, instructions. 22-010.

REG. PRICE
£9.95

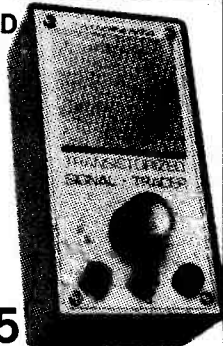

DIGITAL IC LOGIC PROBE

Unique circuitry makes it a combined level detector, pulse detector and pulse stretcher. Hi-LED indicates logic "1". Lo-LED is logic "0". Pulse LED displays pulse transitions to 300 nanoseconds, blinks at 3 Hz for high frequency signals (up to 1.5 MHz). Input impedance: 300K ohms. With 36" power cables. 22-300.


REG. PRICE
£19.95



SIGNAL INJECTOR

For RF, IF, AF circuits. Maximum accuracy. Easy pushbutton operation. Needs two "AA" batteries. 22-4033.

REG. PRICE
£2.79

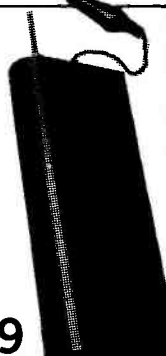

AC/DC CIRCUIT TESTER


Accuracy in 1-300 volts ranges. Safe in live/dead circuits. Needs two "AA" batteries. 22-4034.

REG. PRICE
£1.99

REALISTIC DX 300

General coverage receiver. Quartz-synthesised tuning, digital frequency readout. 3-step RF Attenuator. 6-range preselector with LED indicators. SSB and CW demodulation. Speaker. Code oscillator. Batteries (not included) or 12V DC. 20-204.


REG. PRICE
£229.95

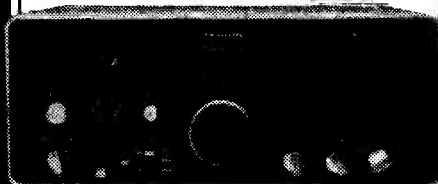

DYNAMIC TRANSISTOR CHECKER

Shows current gain and electrode open and short circuit. Tests low, medium or high power PNP or NPN types. Go/no-Go test from 5-50mA on power types. 22-024.


REG. PRICE
£9.95

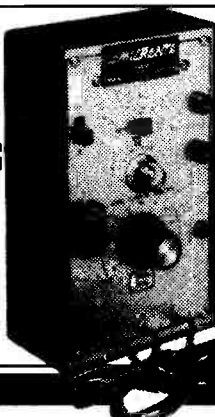

VARIABLE POWER SUPPLY

Power project boards. IC's, other low-voltage DC equipment. Load regulation: less than 450mV at 1 amp at 24V DC. Ripple: less than 25mV. Maximum output current: 1.25 amps. Switchable colour-coded meter reads 0-25V. DC and 0-1.25 amps. Three-way binding posts take wires, banana plugs or dual banana plugs with 0.75" centres. For 220/240V AC. 22-9123

REG. PRICE
£35.95

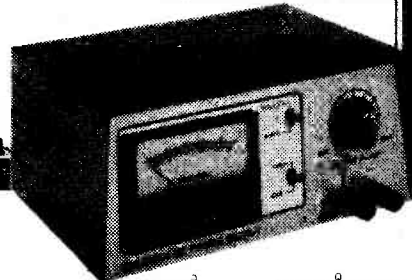

You save because we design, manufacture, sell and service. Tandy have over 7,000 stores and dealerships worldwide. Over 2,500 products are made

specifically for or by Tandy at 16 factories around the world. The quality of our products has been achieved by over 60 years of continuous technological advancement.


KNOWN AS RADIO SHACK IN THE U.S.A. MAKERS OF THE WORLD'S BIGGEST SELLING MICROCOMPUTER TRS80

TANDY

The largest electronics retailer in the world.

Offers subject to availability. Instant credit available in most cases.

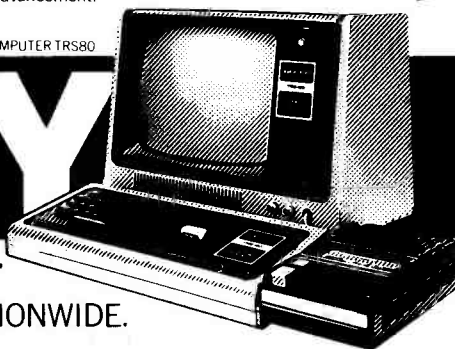OVER 170 STORES AND DEALERSHIPS NATIONWIDE.



TANDY DEALER

Most items also available at Tandy Dealers. Look for this sign in your area

Access, Barclaycard and Trustcard welcome. Prices may vary at individual stores.

VIDEOTONE

Videotone who have joined with us this month in our special speaker offer (see pages 68, 69) have decided to open a direct selling showroom in South London and cease selling through retail outlets. Videotone believe they are the first major hi-fi company to enter the direct selling market which has proved so successful for other consumer products.

The aggressive change in marketing policy which has resulted in price reductions of up to 50 per cent also allows speakers to be brought on a 21 day home trial basis; money back guarantee on all products; an extra 10 per cent discount on any own brands which are out of stock when an order is placed and also any hi-fi club who registers with Videotone will be given an extra 10 per cent discount.

Typical prices include Minimax II's at £44.00 including VAT and Coral MC81 moving coil cartridges at £48.87 including VAT.

A brochure and order form is available from Videotone Ltd., 98 Crofton Park Road, London SE4 (01-690 8511).


SECOND-HAND INSTRUMENTS

With rapid advances in electronic technology making the latest "state of the art" instrumentation almost obsolete within 24 months, it might be reasonable to assume that there was a booming market for the sale of unwanted and under-utilised equipment within the electronics industry.

But this is not the case, according to second-hand instrument dealers Carston Electronics are a subsidiary of Livingston Hire. Carston's business is to buy unwanted instruments and equipment from various sectors of the electronics industry, restore and recalibrate it to the manufacturer's original specification and then resell it. The result is that most of their equipment is between 1 to 8 years old in perfect working order, but only costs between 50-70 per cent of its original price.

MINI MOUNTABLES, MEMORY MINDERS

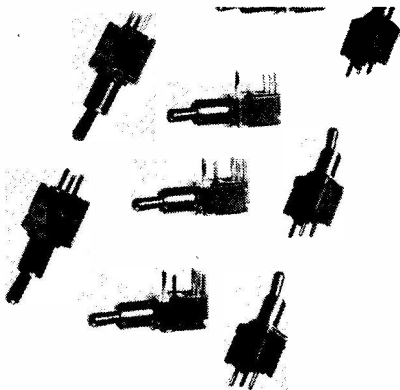A new range of p.c.b. mountable miniature switches has been launched by Hunter Electronic Components. Both single and double




pole switches are available, and they are particularly suited to p.c.b. mounting as the terminals are spaced to fit into the standard 0.1 grid pattern. Contacts and terminals are gold

Several educational establishments have already taken advantage of the Carston service and have purchased items such as signal generators, power supplies and pulse generators. The value of the service is that it is now possible to buy high performance/high quality instrumentation at economical prices.

Further details and catalogues are available from: **Carston Electronics Limited, Shirley House, 27 Camden Road, London NW1 9NR (01-267 3262).**

SCOPE FOR PORTABILITY

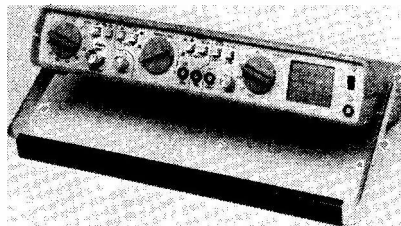In addition to their range of handsome digital multimeters, Sinclair have now come up with a truly portable oscilloscope. While most standard oscilloscopes are supposed to be portable, Sinclair's SC110 will actually fit into the average briefcase or handbag, as it measures only 254 x 147 x 40mm and weighs a mere 1½ lbs. To compliment its por-



ability, the SC110 has the added advantage of exceptionally low power consumption, enabling it to run for long periods on low cost disposable batteries. With a 10MHz bandwidth and 10mV sensitivity, Sinclair claim that its performance matches that of many standard bench models.

At £139, the SC110 must be well within reach of most serious hobbyists. Further information from: **Sinclair Electronics Ltd., London Road, St. Ives, Huntingdon, Cambs., PE17 4HJ.**

plated, giving a contact resistance of less than 20 Mohm @ 100mV 1mA d.c. The price for a single pole double throw switch is about 50p.

Also available from Hunter is a new low-voltage, 5-volts, MOS Memory Protector series. These TransZorb transient voltage suppressors, designated the GMP-5 Series, have a maximum surge rating of 215 amps for 50 microseconds and 70 amps for 1 millisecond. They feature a very low 6.9 volt maximum clamping level at 10 amps for an impulse waveform of 10 x 1000 microseconds. The series is characterized by its extremely fast response time (theoretically 1 x 10⁻¹² seconds), and low series resistance (RON).

They are effective in providing protection for VMOS, HMOS, NMOS, and CMOS circuits from pulses generated by electromechanical switching, electromagnetic coupling, capacitive or inductive load switching, voltage reversals, and electrostatic discharge (ESD). TransZorbs effectively shunt unwanted transients while maintaining the circuit voltage level for continuous system operation.

For further information, contact: **Hunter Electronic Components Ltd., 55 High Street, Burnham, Bucks. Telephone (06286) 65421.**

CALCULATOR NOTES


What's the square root of "Yes we have no bananas"? Beethovens Fifth? Not quite—in fact I can guarantee it's a tune that you've never heard before. With the Casio ML-81 your calculations will certainly take on a new dimension, for as well as having three ready-programmed pieces of music for the timer and two alarms, the calculator can be used to play



melodies within an eleven note range. Unfortunately, the lack of semi-tones severely limits the variety of tunes available, though in other areas the ML-81 is more versatile. In addition to the calculator and clock functions, the ML-81 incorporates a stopwatch and a calendar programmed until the year 2099.

Two silver oxide batteries give approximately 14 months continuous operation and to save battery life the duration of a note is limited to between one and two minutes.

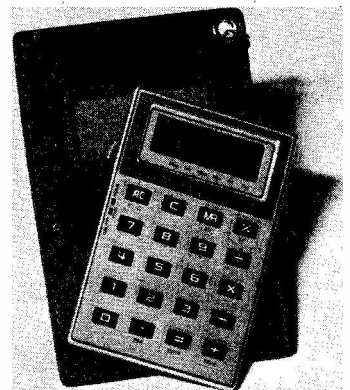Also emanating from the Casio stable is their MQ-6 Micro Card Watch, which measures a mere 67mm x 43mm, and is only 5mm thick. Obviously intended as a modern equivalent to the pocket-watch, it comes complete with a leather pouch and chain. This



model also incorporates calendar, stopwatch and basic calculator functions, though surprisingly, it lacks an alarm. The MQ-6 is priced at £19.95 (Tempus discount price) and for another £3 or so you can buy the ML-81, and have the pleasure of being woken every morning by 'Frühlingslied'.

Both the ML-81 and the MQ-6 are available from **Tempus, (Dept. PE), Beaumont Centre, 164-167 East Road, Cambridge CB1 1DB.**

EDUKIT

Reviewed

MIKE ABBOTT


AT £30 the Edukit is a genuine “throw away” training tool, although the “waste bin” will *really* be the spares box, or dedication to some micro based project. At any rate no fortune is lost should you fail to get on with the *microprocessor*, and you are not plagued with the usual pre-purchase questions such as upwards expandability. The idea was conceived, and the machine designed by Dr. A. A. Berk. There is no keyboard monitor, cassette interface or I/O port, and two seven segment displays indicate memory contents only—you have to know the address you should be at! Yet it is precisely because of these points that the Edukit is excellently tailored to its vocation.

THE HARDWARE

The glass fibre p.c.b. is double sided; not plated-through, and measures 130 × 210mm. There are no edge connector fingers, and only one i.c. socket is supplied, which is for the RCA COSMAC 1802 μ P. This is a good choice of m.p.u., for it incorporates 40 × 16-bit registers, 32 of which are general purpose. With this much memory *on the house* and capable of simultaneous hi/lo order byte storage at any one address, the 1802 is eminently suitable for that intelligent burglar alarm, or musical doorbell project. Just the kind of thing, in fact, you might wish to do with your Edukit when you have “graduated”.

A Memory Protect toggle switch is edge mounted on the p.c.b. with a tinned copper wire loop strapped over it to give stability. Two l.e.d.s indicate the processor’s mode of operation, and a third l.e.d. can be linked to indicate the status of the m.p.u.’s Q flag. See Fig. 1 for the block diagram.

Fig. 1. Block diagram. An external power supply of 5 or 6V at up to 0.5A is required

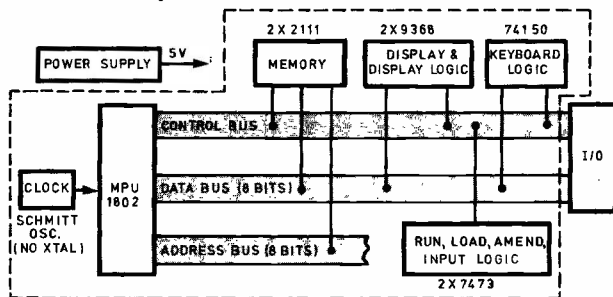

KEYPAD

There are twenty keys, sixteen of which are hexadecimal (0–9, A–F), and four control keys which are used in conjunction with the two mode status l.e.d.s. These control keys are: “L” for load, “R” for run, “Am” for amend, and “In” for increment.

In order to minimise expense, the Edukit uses the cheapest of keypad switches; a very firm push being necessary with some keys. This was rather a nuisance in the case of the *In* key because it is the number of pushes by which you determine the memory location you are looking at.

However, these switches can be “popped” apart, cleaned, and reassembled if necessary. To be fair, our keypad underwent an excessive amount of “fiddling”, which resulted in the switches being less reliable than evidenced by their past record. In addition, a switch debounce modification is now being incorporated in all machines being sold.

Legends for the keys are cut into strips from a printed card, and spot glued across each row of switches. See photographs.


OPERATION

Entering a program is simply a matter of turning off the Memory Protect switch, entering each op-code (or data) via the keyboard, and then pressing *In* to move on to the next location. Before entering or running a program it is necessary to reset the program pointer to the first memory location (00) again by means of the *R* key. Under memory protect, the *In* key can be used to inspect memory contents without altering it in any way. The contents of any individual memory location can be altered using the *Am* key. Using Edukit is simple. Because you find yourself eyeball to eyeball with the microprocessor itself, without a monitor throwing up a smoke screen, you soon learn, that cleared of these clouds of firmware “the chip” is essentially a simple programmable i.c.

A link connects the third l.e.d. to the Q flag, but if this link is replaced by an earphone or small speaker, sound effects can be produced quite easily, whilst still allowing the l.e.d. to work.

THE MANUAL

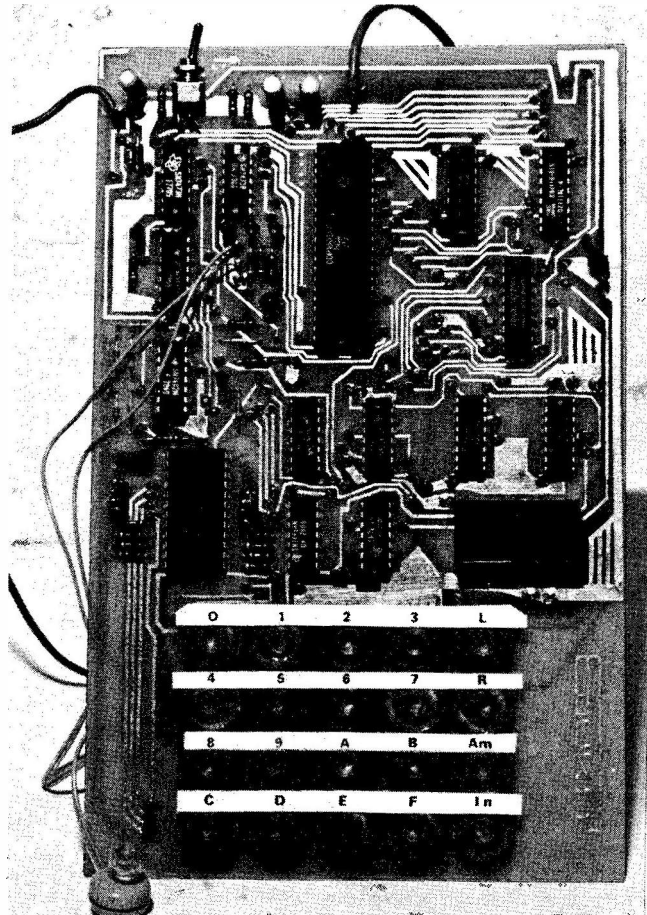With a teaching aid such as this, the manual is all important, and it is always difficult for the knowledgeable author to predict what will confound the beginner, particularly in a jargonistic discipline. However, in the Edukit Manual every attempt has been made to accompany all references with an explanation.



The constructional notes in Chapter One overlook nothing. Even the l.e.d.s are described as "red translucent objects". Chapter Two swoops in on the various numbering systems; binary, hexadecimal and decimal etc., and Chapter Three starts you off with a simple program, showing how you can see and hear the machine operate.

To help in understanding how the machine functions, so called "Dry Run" tables describe the step by step operation. One group of instructions missed out, is the Long Branch instruction which involves high address locations. This omission is deliberate because only the low order address byte is used by Edukit on account of its limited memory (two 2111s plus the 1802 registers). The whole package is only meant to be an introduction and plenty of supplementary reading material is recommended.

Chapter Five moves on to matters of a hardware and control nature, describing a "switches and l.e.d.s" experimentation circuit. Some example applications include a temperature gauge and a security system; which is good because dedicated applications such as these seem to be comparatively neglected on the amateur micro scene.


The appendices include a short teach-in on soldering, and the COSMAC op-code table.

CONCLUSION

The two winning features of the Edukit must be: (a) its simplicity without pretence to being the first building block of an enormous system, and (b) its remarkable price tag, which means you can risk being wrong.

Some expansion/add-on plans are in the pipeline which will allow the Edukit to be put to good use in its retirement. The exact nature of the expansion plans were not crystallised at the time of writing, but it was expected that a small RAM or ROM memory board would be available which would plug into the 1802's socket, re-housing the 1802 on itself.

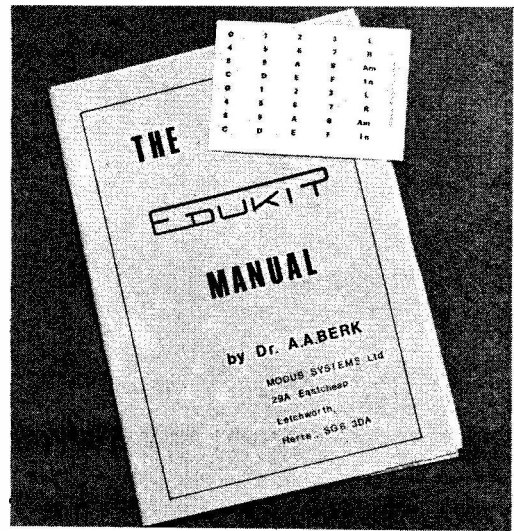An Edukit Users' Club is also anticipated, so anyone who would like to participate in, or belong to it, should contact Modus Systems.



Edukit Manual, and keypad legend card. Although there is no I/O chip as such, the manual explains fully how to interface to the outside world. The 1802's four External Flag lines can be used to scan the status of up to 16 sensor switches, or simply accept BCD data. The method of transferring bytes to and from external devices using direct bus access is also covered. To clarify the capability of the machine, and to set the heading straight, it was really Mike Abbott who reviewed the Edukit, although in a few generations time . . . who knows?

Some prices are: Basic Edukit £29.95 plus VAT and 80 pence for post and packing. The 1802 manual can be purchased for £3.99 plus 50 pence p&p, and a set of sockets for the remaining i.c.s at £2.60 plus VAT. Edukit is available from Modus Systems Ltd., 29a Eastcheap, Letchworth, Herts. SG6 3DA. There will be a special Edukit offer in PE next month for those that can wait!



Avoid a break in the middle

Make sure you get every issue when you're following projects in PRACTICAL ELECTRONICS. Use this order form for a year's supply to be posted to you.
ANNUAL SUBSCRIPTION RATES (including postage and packing) inland and overseas £10.60.

PRACTICAL ELECTRONICS SUBSCRIPTION ORDER FORM

Please send me Practical Electronics each month for one year. I enclose a Sterling cheque/international money order for (amount).

PLEASE USE BLOCK LETTERS

NAME Mr/Ms/Miss _____

ADDRESS _____

POSTCODE _____

Make your crossed cheque/MO payable to: IPC Magazines Ltd., and post to: Practical Electronics, Room 2613, King's Reach Tower, Stamford Street, London SE1 9LS.
 Practical Electronics is published in England by IPC Magazines Ltd. Regd. No. 53826. Regd. Office: King's Reach Tower, Stamford Street, London, SE1 9LS. A subsidiary of Reed International Ltd.

Semiconductor UPDATE...

FEATURING ZMOS F.E.T. AG 1000 IU 101

R. W. Coles

ZMOS F.E.T. (X520, X530)

All the rage in U.K. discos later this year will be the new range of ZMOS f.e.t.s from the Welsh firm of Llyis Electronics. At last the unflagging research efforts of this energetic young company have come to fruition, and there will be no stopping them now. Working with only limited capital and outdated equipment, the back-room boys at Llyis have taken on the might of giants like Texas Instruments and Motorola, beating them at their own game with radical and innovative technology of the very highest standard. Llyis make their own silicon because they have found imported material to contain too many impurities, and with the confidence encouraged by a bulging order book, they have now found it possible to take up their option on a section of Prestatyn beach, thus ensuring a ready supply of raw material for years to come.

The new ZMOS power transistor family is typical of Llyis products. Designed primarily for high current, high power applications in disco power amplifiers, the new ZMOS family manages to combine the best of bipolar, MOSFET and valve technology in one easy to use "HEX-NUT" package. The ZMOS X520 for example, is very sensitive to static charges and requires a high current drive source, and yet it has the highest "on" resistance in the industry and runs from a 200V h.t. supply. All the ZMOS range feature industry-standard 6.3V a.c. heaters and unique "disco safety" circuits which render the amplifier harmless during transient musical passages which might otherwise lead to auditory damage. The 4kW per channel (typical, using 4 x X520S) or 8kW per channel (typical using 4 x X530S) is higher than anything unleashed in discos before, and has forced Llyis to develop companion loudspeakers with leather cones. Every device carries a government health warning, but under extreme conditions the "disco safety" circuit will cause the output devices to self-destruct before the 160db pain threshold is exceeded.

The novel ZMOS "HEX-NUT" package features ports for standard microbore central heating pipes, and for evaluation purposes a domestic radiator and central heating pump system topped up with ice water before a session will be about ready to brew coffee two mind blowing hours later. For serious applications a thirty gallon header tank will be needed, and a full quadrophonic system can provide central

heating for an average street if used for just four hours per day.

· Nice one boys!

MINI-DIP GRAVITY CIRCUIT (AG 1000)

In these days of energy crisis and threats to our oil supplies, it is refreshing to find that the energy problem is not being ignored by the semiconductor manufacturers. The German firm of TRASKERT GmbH has been experimenting with new forms of energy conversion using gallium arsenide photon emitters for several years now, and if the data sheets and samples we have just received are anything to go by, they are on the edge of a breakthrough in this fascinating area. Their AG 1000 anti-gravity circuit is integrated on to a small semiconductor chip, and yet when coupled to a low cost gravity anomalizer it can generate the power of 10^9 space shuttle engines. Details of the chips operation are still secret at this stage, but we wired ours up on a small piece of Veroboard using the application notes in the data sheet and tried it out. Despite the "birds-nest" layout, we achieved warp factor 8 on our first run, but re-entry was a problem and the legs of our bench were badly charred. Hobbyists are cautioned not to run the chip above 2 volts unless proper ablative heat shields are worn. (Note: Wicket keeper's pads are *not* sufficient.)

On our second try we fitted the circuit board in place of the engine in an old Ford Popular and wore skin diving air tanks. Since their AG 1000 takes only 2 ma at 9 volts we were able to do an orbit of Jupiter on a single PP3 battery before returning via the sling-shot effect. A fully charged car battery should get you to *Alpha Centauri* and back if you take enough sandwiches.


The AG 1000 is packaged in an 8 pin mini-dip, but at warp factor 1 this actually turns into a flatpack, so make sure your soldering is up to standard. The device is currently priced at 18p in hundreds, but this is certain to fall as demand increases.

ROBOT MICRO (IU 101)

At last the millions invested by the British taxpayer in Inmos seems to be paying off. The first circuit to be unveiled by Doctor A. N. Droid at a recent press conference is a new microprocessor designed for applications in robotics. The design of this chip was carried out entirely in the U.K.

although pilot production will initially take place in the U.S.A. until the Inmos manufacturing facility over here is fully operational. The new device, coded IU 101, is unlike other microprocessors in that it can be programmed in a "learn" mode. Pins on the 64 pin package are allocated for serial audio inputs and outputs, and two 8 bit DMA channels are available for the connection of a pair of colour TV cameras. Motor outputs are driven by means of a multiplexed control bus which can handle up to 256 separate muscle servos. Internally the IU 101 CPU has a 64 bit wide pipe-lined architecture with no less than 18 subsidiary 8 bit processors for I/O handling and memory management. On-chip firmware in ROM provides a high level English language interpreter (French available late 1980) and various utility routines to handle basic motor functions and sensor interpretation. A fast NMOS cache memory (64K x 64 bit words) and a 20 Megaword long term backing store using bubble memory technology are also included on the chip. Although the chip is large by today's standards Dr. Droid stated that yields were high, and earlier testing problems were now being overcome. One of the most exciting innovations on the chip were the 2 nanosecond A to D converters which had been fabricated using Schottky technology, said Dr. Droid.

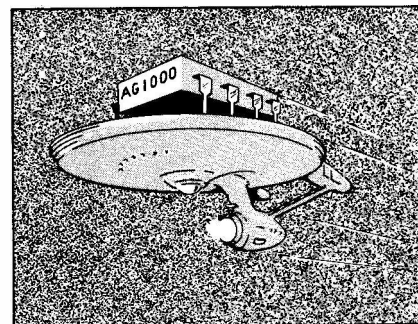Applications for the IU 101 are expected to include basic household robots and the manufacture of Fiat cars. All the pilot production is being used in-house at Inmos at the moment, ostensibly for brain transplants. Dr. Droid stated that a politician version (with limited memory and stripped down CPU) would be available in early 1981.



Warp testing the AG 1000

CHIP CHECKER

L.V. COOPER

THIS device differs from most i.c. testers in as much that the logic states of all the i.c. pins can be seen at a glance. Not only are the high and low states displayed, but this checker differentiates between high, low, inadmissible, and open circuit states.

Although the tester does not check *all* the different aspects of a logic i.c. it does allow go/no-go devices to be identified quickly and can, with practice, go a long way to identifying an unknown i.c.

The circuit design allows the use of cheap calculator type multiplexed displays.

OPERATION


The operation of the device is basically simple and consists of a set of three comparators which are very rapidly switched around the pins of the i.c. under test, whilst at the same time enabling the appropriate display digit.

CD4016 quad analogue switches i.c.'s 1 to 4 are employed to switch the comparators onto each pin.

The switching sequence is controlled by a four to sixteen line decoder (IC5) which operates the switch controls and also enables the digit drivers (IC's 7, 8 & 9).

The decoder is fed by a binary counter IC6 which is in turn clocked by a 500Hz oscillator made up from two of the gates in IC12.

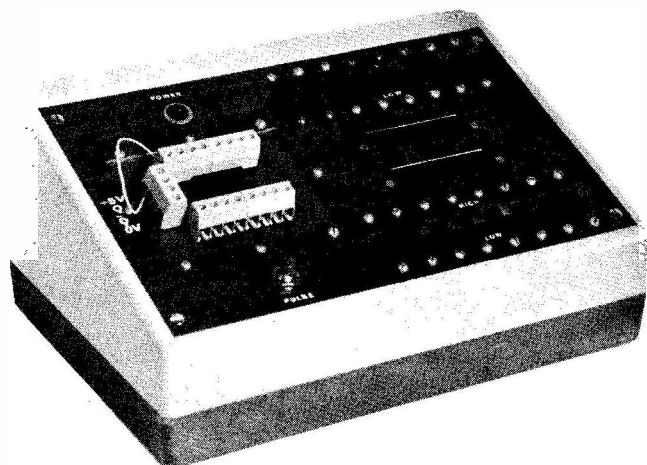Interdigit blanking is necessary and is achieved by feeding clock pulses from the oscillator, after inversion by TR2, to the blanking input of the binary to seven segment decoder IC13. This ensures that all displays are off during the first half of the clock pulse.



COMPARATORS

IC10 (LM324) is a quad op-amp and three of the four amplifiers in the package are used as comparators to detect the logic state of the pin being sampled.

Logic "1" is detected by IC10c, the output of which goes high if a voltage greater than +2.4 volts is present at its input.


Logic "0" The outputs of all three comparators are arranged to be low when a voltage between 0 and +0.4 volts is present on the inputs.

Inadmissible levels (+0.4 volts to +2.4 volts) are detected by IC10a. The output is high when a voltage greater than +0.4 volts is present on its input.

Open circuit Any pin that is open circuit either by design or a fault condition is detected by IC10b.

A negative voltage is fed onto each test pin by means of 1M Ω resistors 1-16, and clamped by germanium diodes D1-16 to approximately -0.2 volts. When an i.c. is plugged into the test socket this small negative voltage, when connected to a live pin, will be clamped to zero or overridden by the positive voltage present on that pin, provided of course that the supply is connected to the i.c. under test by means of the terminals provided.

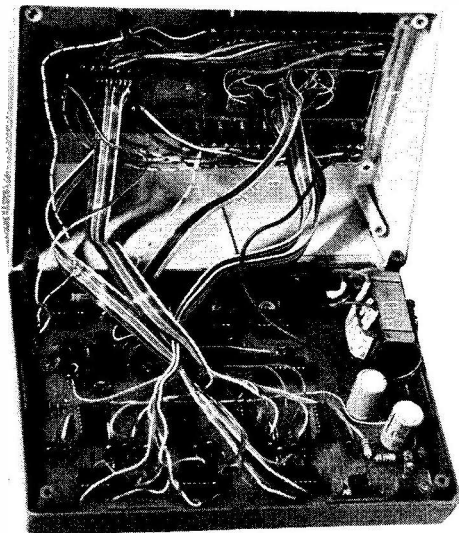IC10b detects the presence or absence of this negative voltage, and if present its output goes high, the output from the gating circuitry presents a binary code greater than nine to the decoder IC13 and it automatically blanks the display. Any other condition causes IC10b to produce a low output, leaving the display format to be decided by the other two comparators.



COMPONENTS . . .

Resistors

R1-R16, R32	1M $\frac{1}{8}$ W (17 off)
R17-R19, R21, R22, R33	100k $\frac{1}{8}$ W (6 off)
R20, R23, R34, R54	10k $\frac{1}{8}$ W (4 off)
R56, R24	22k $\frac{1}{8}$ W (2 off)
R57	6M8 $\frac{1}{8}$ W (1 off)
R25-R31	150 $\frac{1}{8}$ W (7 off)
R51, R52, R55	1k $\frac{1}{4}$ W (3 off)
R35-R50	2k7 $\frac{1}{4}$ W (16 off)
R53	330 $\frac{1}{4}$ W (1 off)

Potentiometers

VR1, VR2, VR3	47k min. preset
VR4	100k min. preset

Capacitors

C1	10n Disc Cer.
C2	1 μ Tant.
C3, C9	47,0 μ elect. 15VDC (2 off)
C4, C5, C7, C10	100n 30V Disc Cer. (4 off)
C6, C8, C11	100 μ 16V Tant (3 off)
C12	22 μ 16V elect. (1 off)

Transistors

TR1, TR2	BC107 (or similar) (2 off)
----------	----------------------------

Diodes

D1-D16, D29	OA90/91 (gen. purp. germanium) (17 off)
D17-D23	IN914 (or similar) (7 off)
D24-D25	IN4001 (or similar) (2 off)
D26-D27	6.8V Zener 400mW (2 off)
D28	0.2 in. i.e.d. (green) & holder

Integrated Circuits

IC1-IC4	4016 or 4066 (4 off)
IC5	4514
IC6	4516
IC7-IC9	75492 (3 off)
IC10	LM324
IC11, IC12	4011 (2 off)
IC13	4511
IC14	74121 optional
IC15	7805

Switches

S1-S16	3-way centre-off slide switch (16 off) (Progressive Radio)
S17	Single or double pole 250V ac 1A toggle (1 off)
S18	Push-to-make switch (optional)

Miscellaneous

14-pin d.i.l. i.c. sockets	(11 off)
16-pin d.i.l. i.c. sockets	(3 off)
24-pin d.i.l. i.c. sockets	(1 off)
T1. mains transformer	6.3V 1A
Displays. Bowmar	8 or 9 digit, or NSA 1298 (2 off) (Henry's Radio) These are common cathode
1 $\frac{1}{2}$ Metres	8-way ribbon cable
Printed circuit board	
2-core mains cable	
Vero case	2523E
Terminal blocks	Electrovalue type 7204 4-way (5 off)

DISPLAY FORMAT

The outputs from the comparators are gated by IC's 11 and 12, TR1 and D21, D22 and D23, to produce the following display characters:—

- Logic "1"—displays "1"
- Logic "0"—displays "0"
- Inadmissible—displays "8" flashing at 2Hz.
- Open circuit—displays blank

The fourth op-amp in the LM324 package is used as an astable oscillator running at 2Hz. By feeding this into the gating arrangements it causes the "8" to flash at 2Hz.

PULSE GENERATOR

A 74121 monostable (IC14) is provided on board to provide a clock pulse for checking counters. The Q and \bar{Q} outputs are brought out to a terminal block near the test socket. The monostable is triggered by means of a push button switch, S18 mounted on the front panel. This part of the circuit may be omitted if not required.

POWER SUPPLY

The power supply consists of a 6.3 volt mains transformer feeding two rectifiers D24 and D25 which together with the reservoir capacitors C7 and C9 provide positive and negative rails of approximately 9 volts each. A split supply is provided

from the op-amp package of ± 6.8 V, Zener stabilised by D26 and D27.

The output voltage of the op-amps is 1.5 volts less than the supply at maximum and a further 0.6 volts is dropped by the isolation diodes, D17, 18, 19, 22 and 23, which are in series with the op-amp outputs. The total voltage loss is therefore approximately 2 volts. In order to ensure that the 5 volt logic circuitry interprets a high output from the op-amps as logic "1" the supply rail for the amplifier package needs to be 2 volts above the 5 volt supply, hence the 6.8 volts.

The 5 volt logic supply and the supply for the i.c. under test is provided by a 7805 i.c. regulator from the raw 9 volt supply, IC15.

The use of a 7805 in this situation provides a double benefit because apart from providing good regulation, should one inadvertently switch a test pin down to chassis whilst it is connected as a supply pin, the 7805 shuts down and restores power when the short is removed, suffering no ill effects and with no damage to the offending switch.

A power indicator i.e.d. is fitted (D28), mainly to help avoid an i.c. being inserted with power on, which could result in damage to the i.c. The indicator also reduces the risk of leaving the tester switched on when not in use, which could all too easily happen if all switches were set to the centre position and the test socket unoccupied, leaving a totally blank display.

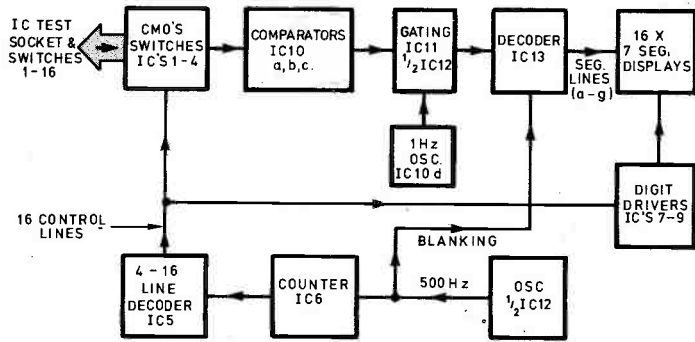


Fig. 1. Block diagram of Chip Checker

E6295

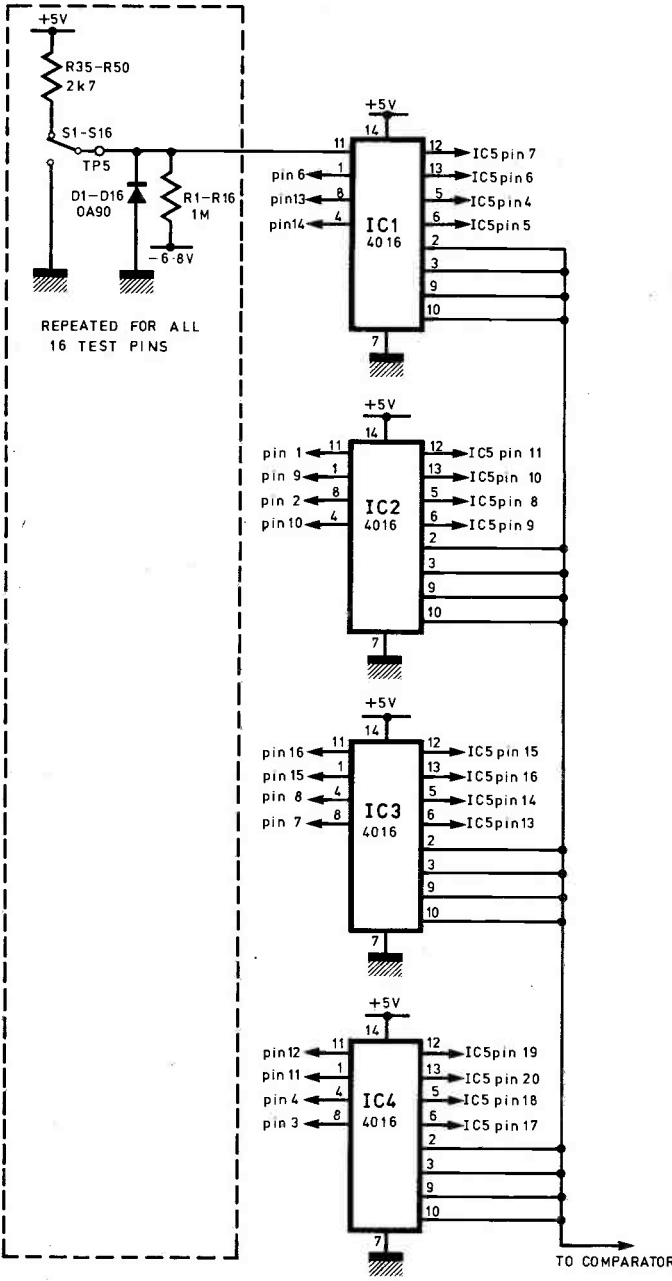


Fig. 3. CMOS switching stage

E6296

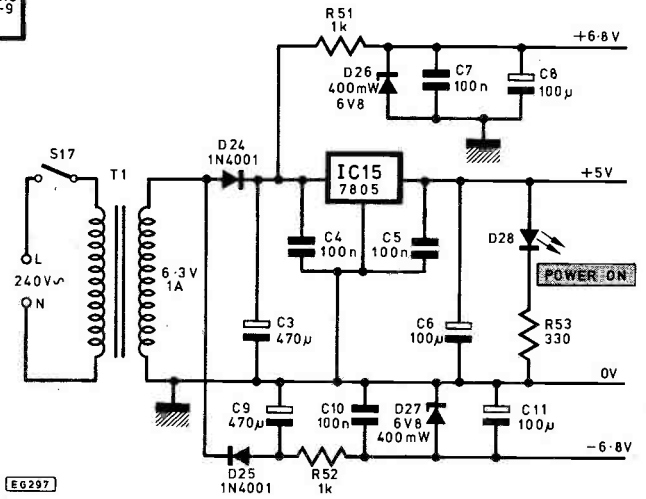


Fig. 2. Power supply

E6297

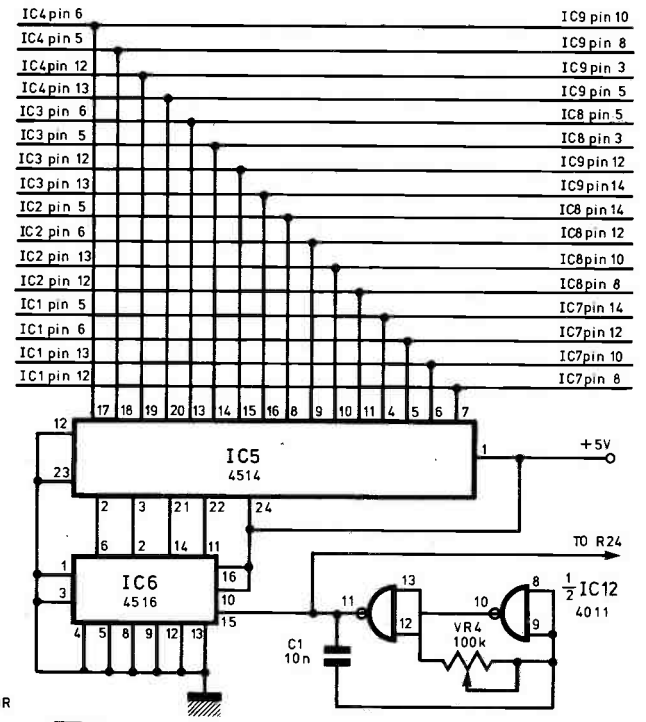


Fig. 4. Clock, and switch sequence control

E6298

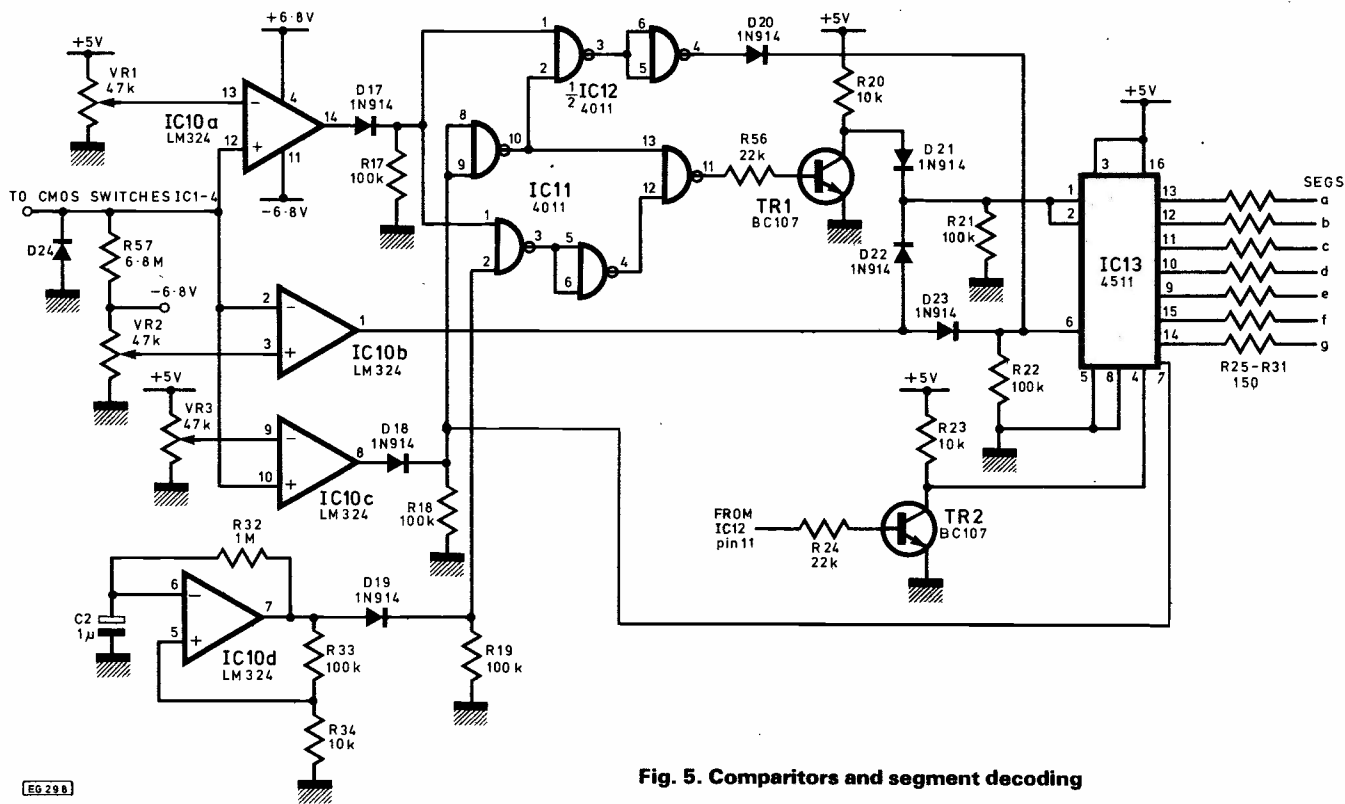


Fig. 5. Comparitors and segment decoding

EG 298

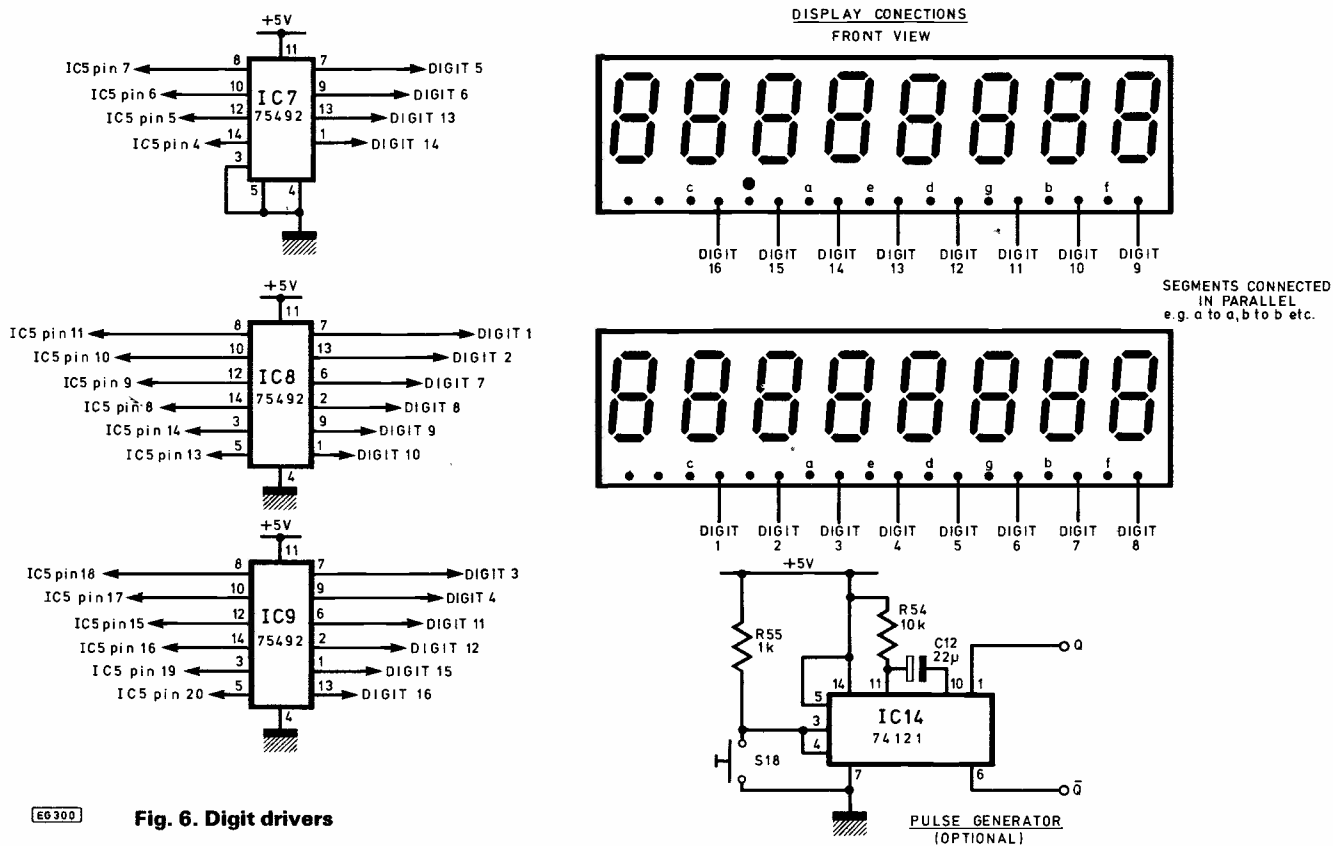


Fig. 6. Digit drivers

EG 300

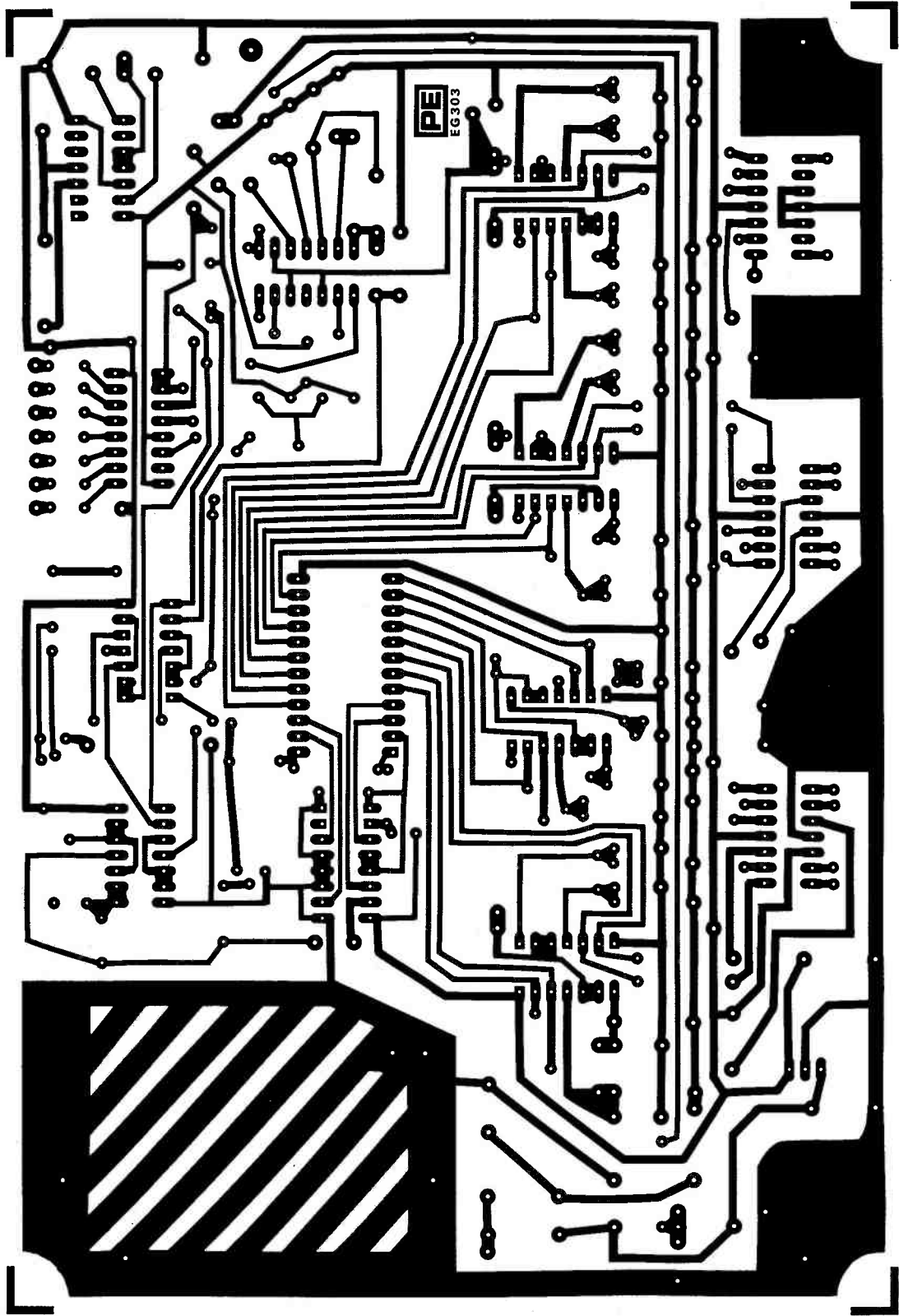


Fig. 7. Printed circuit layout (actual size)

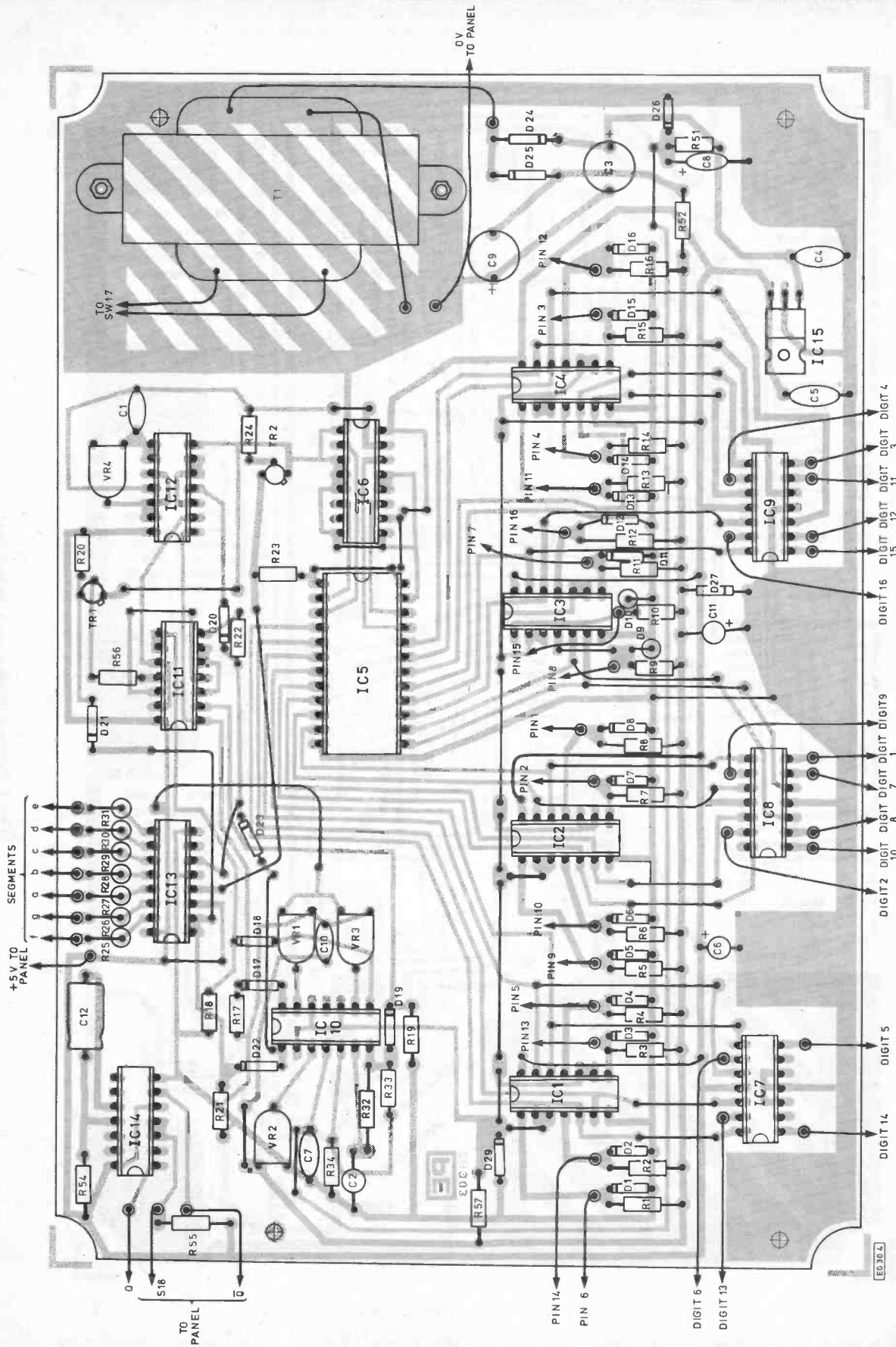


Fig. 8. Component layout

The +5 volts rail and the ground rail are brought out to terminals on the front panel to power the i.c. under test, and for external use if required.

The +5 volts is connected to the i.c. under test by means of a wire link connected to the +5V terminal and the appropriate supply pin on the test socket. The ground connection is made by switching the appropriate switch low.

TEST SOCKET

The test socket, apart from being wired to screw terminals, is also wired to a set of sixteen switches, S1-16, which allow any one pin to be set high, low or floating. In high position +5 volt is applied to the pins by 2k7 pull up resistors (R35-50), which allow open collector devices to be tested, and prevent smoke being produced by the device under test if two inputs are short circuit.

CONSTRUCTION

The layout is in no way critical and should present no problems to anyone wishing to use a different form of construction.

If the printed circuit layout is used it may help to fit all the jumper wires first, using sleeving if required. This avoids missing and jumpers due to the position being obscured by other components.

Before fitting any i.c.s, check that the negative voltage on the cathodes of the clamp diodes D1-16 and D24 is -0.2 volts or less. Any voltage greater than -0.2 volts will cause the 4016 i.c.s to fail. The various supply rails should also be checked at this point.

When fitting the i.c.s, make sure the power is off, and check orientation very carefully.

Ribbon cable is strongly recommended for connections between the front panel and the main board; it makes for a much easier time during assembly and fault finding if necessary.

SETTING UP

- (1) Set all front panel switches to the centre position.
- (2) Set all four presets to mid position. Displays should now be active.
- (3) Adjust VR2 until displays are just off.
- (4) Switch off and connect a 1K or 5K potentiometer across the +5 volt supply with the wiper to any test pin terminal. Connect a meter between wiper and zero volts. Switch on.
- (5) Adjust the pot. for a reading of +2.4 volts on the meter and adjust VR3 until display just reads "1".
- (6) Reset the pot. for a reading of +0.4 volts on the meter and adjust VR1 until display just reads "0".
- (7) Rotate the pot. from one end to the other and check that the display reads "0" at one end, "flashing 8" around the centre and "1" at the other end. If this does not happen you have a fault.
- (8) Disconnect pot. and meter and set all front panel switches to the low position one at a time, and check that the digit applicable to that switch reads "0".
- (9) With all switches set low adjust VR4 for minimum flicker on the displays.
- (10) Set all front panel switches high and check the appropriate display reads "1".

Returning all switches to centre should leave display totally blank.

USING THE CHIP CHECKER

When a TTL or DTL i.c. is plugged in and the power supply connected, if all switches are placed in the floating position, the open circuit pins if there are any, will be blank. The out-

put pins will display one or zero and of course so will the supply pins. The input pins will normally adopt an inadmissible level of approximately +1.4 volts. The input pins will be obvious due to the flashing 8 displays. The switches may be used to program the inputs whilst the outputs can be observed on the displays and correct or faulty operation ascertained.

Counters may be clocked using the push button and monostable arrangement and the outputs all monitored at once.

If an *unknown* i.c. is plugged in, the power supply pins may sometimes be found by leaving all switches in the floating position and applying +5V only to each pin in turn and noting the number of ones present on the display. The supply pins produce the largest number of ones, thus the two pins that produce the same number as well as the larger number, may normally be assumed to be the supply pins. The polarity can then be determined with an ohmmeter.

If the supplies are then connected, the inputs will be visible by the presence of the inadmissible logic levels. The inputs can now be systematically programmed high or low, the outputs monitored and a truth table made up.


The ability of Chip Checker to detect an open circuit pin is useful when testing tri-state devices, a disabled tri-state output should behave as an open circuit and produce a blank display digit.

It should be noted that input pins can interact with one another if left floating and so all pins that need to be high should be switched high and not left floating. A short circuit between two inputs or adjacent pins will be obvious, when one is taken low by a switch the other will indicate low also even though it is switched high.

Chip Checker was primarily designed to test TTL i.c.s. EG 74L, 74S, 74LS, and of course standard 74 series. It will however handle DTL and CMOS i.c.s although the input pins of CMOS will produce blank displays due to the very high input impedance of these devices, and of course the logic levels are incorrect for CMOS. DTL i.c.s behave similar to 74 series.

Since the tester was first built it has been used for checking untested "fall out" devices and the monitor ROM's of an MK14, also buffers and gates from home computer systems after those inevitable accidents that occur during system expansion and modification.

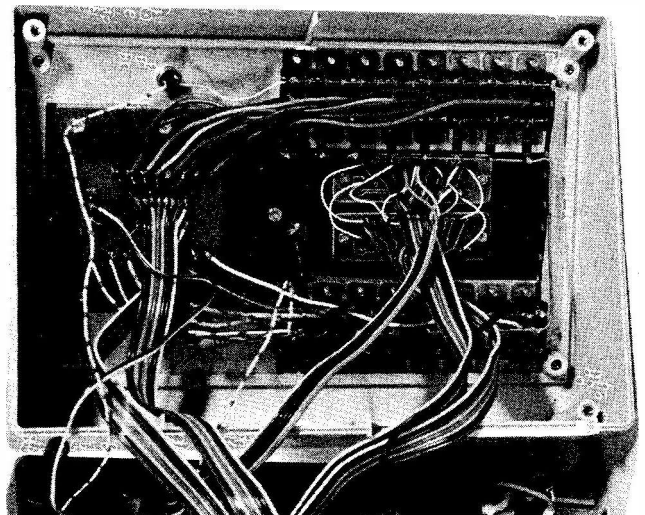The device has proved both reliable, and with a little practice, easy to use. ★




TRANSAM

COMPONENTS AND SYSTEMS FROM TRANSAM COMPUTERS

•CP/M
•BASIC
•PASCAL

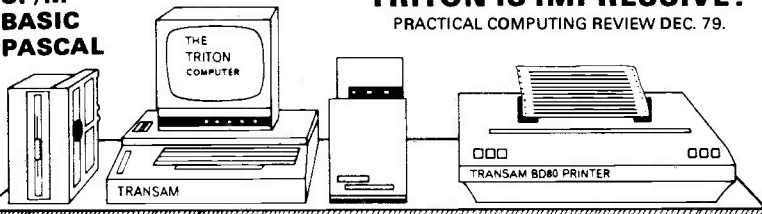TRITON IS IMPRESSIVE!
PRACTICAL COMPUTING REVIEW DEC. 79.



TRITON COMPUTER SYSTEM.

Designed for ease of construction and flexibility. Kits come complete and all components and software are available separately. UK designed and supported. Fully documented hardware and software and a totally flexible approach to system building. Powerful and easy to use system monitors - a range of languages available. Firmware is Eprom based and upgrading from one level to the next is easy.

- L5.2 with 1.5k monitor 2.5k basic **£294.00**
- L7.2 with 2k mon 8k extended basic **£409.00**
- L8.2 4k ed/mon 20k res pascal **£611.00**
- L9.2 CP/M disc based system **P.O.A.**
- 8k ram card kit (21141) **£97.00**
- 8k eprom cards (EXCL 8-2708) **£31.00**
- Motherboard expansion 8 slot **£50.00**
- Trap-res asm/edit etc (8-2708) **£80.00**
- Transam BD80 bi-dir printer **£595.00**
- TVM 10 video monitor 9" **£79.00**
- Eprom prog (2708) kit **£29.50**

SEND FOR OUR CATALOGUE FOR FULL
DETAILS OF TRITON FEATURES !

CP/M AVAILABLE NOW FOR TRITON

Disc operating system complete with text editor, assembler, debugger, system utilities and complete file management. Makes Triton fully CP/M compatible and able to run CP/M based software. Triton will support up to four 5 1/2 or 8" drives single or double density full CP/M software user group facilities available. SAE for details.
CP/M Disk + manuals (6) £75.00

DISK DRIVES & POWER SUPPLIES

SHUGART	SA400 5 1/2" drive	£205.00
	SA800 8" drive	£380.00
	Power one quality power supplies	
	CP249 1 x 5 1/2 PSU	£33.00
	CP232 2 x 5 1/2 PSU	£60.00
	CP205 1 x 8" PSU	£56.00
	CP206 2 x 8" PSU	£76.00

TCL PASCAL - CP/M COMPATIBLE

A standard Pascal compiler available on a resident (20k) Eprom based configuration* or available to run under CP/M on 8" disc plus documentation. CP/M version **£90.00**. *P.O.A. TCL Pascal Manual and specification **£6.50**.

DIL PLUG SOCKETS & SWITCHES

W/WRAP SKTS	OIL SKTS	OIL PLUGS	OIL SWITCHES
80IL 0.20	80IL 0.14	140IL 0.60	40IL 1.20
140IL 0.35	140IL 0.15	160IL 0.85	70IL 1.75
160IL 0.42	160IL 0.17	SCOTCHFLEX	80IL 1.80
180IL 0.60	180IL 0.24	140IL 1.30	16wZIF* 4.95
240IL 0.82	200IL 0.27	160IL 1.50	24wZIF* 6.20
280IL 0.74	240IL 0.30	240IL 2.80	
400IL 0.95	280IL 0.30		
	480IL 0.50		


ZERO INSERTION FORCE

FULL RANGE OF MICRO SUPPORT CHIPS - IN STOCK

SUPPORT				RAMS			
SN74LS00N 22	SN74LS54N 21	SN74LS138N 95	SN74LS195AN 85	SN74LS325N 2.55	220 2101	232	
SN74LS01N 22	SN74LS55N 21	SN74LS139N 95	SN74LS196N 1.20	SN74LS328N 2.55	8216	2.60	2102L4 1.20
SN74LS02N 26	SN74LS56N 1.50	SN74LS145N 1.20	SN74LS197N 1.20	SN74LS327N 2.55	8224	2.80	2111 2.32
SN74LS03N 26	SN74LS73N 35	SN74LS148N 1.75	SN74LS221N 1.25	SN74LS352N 1.35	3852 (F8)	10.00	2112 2.48
SN74LS04N 28	SN74LS74N 40	SN74LS151N 85	SN74LS240N 2.20	SN74LS353N 1.50	8228	4.20	6810 4.00
SN74LS05N 28	SN74LS75N 46	SN74LS153N 60	SN74LS241N 1.90	SN74LS355N 85	8228	1.75	8154 11.50
SN74LS08N 28	SN74LS76N 35	SN74LS154N 1.00	SN74LS242N 1.90	SN74LS366N 85	8228A	1.90	2114L-450 5.50
SN74LS09N 22	SN74LS78N 35	SN74LS155N 1.25	SN74LS243N 1.95	SN74LS367N 85	8228	8.75	2114L-250 7.80
SN74LS10N 18	SN74LS83AN 1.15	SN74LS156N 1.25	SN74LS244N 2.10	SN74LS368N 85	8228	5.00	74C920 11.00
SN74LS11N 26	SN74LS85N 1.10	SN74LS157N 60	SN74LS245N 3.60	SN74LS373N 1.75	8251	5.00	74C929 11.00
SN74LS12N 26	SN74LS86N 40	SN74LS158N 99	SN74LS247N 1.25	SN74LS374N 1.70	8253	11.00	74C929 11.00
SN74LS13N 25	SN74LS90N 65	SN74LS160N 1.15	SN74LS248N 1.95	SN74LS375N 72	8255	5.00	74C929 11.00
SN74LS14N 88	SN74LS91N 99	SN74LS161N 1.15	SN74LS249N 1.30	SN74LS377N 1.75	8257	11.00	4027 5.00
SN74LS15N 25	SN74LS93N 90	SN74LS162N 1.15	SN74LS251N 1.45	SN74LS378N 1.32	8259	12.50	4044 7.00
SN74LS20N 20	SN74LS938N 65	SN74LS163N 90	SN74LS253N 1.25	SN74LS379N 1.40	8155	12.50	4045 7.00
SN74LS21N 26	SN74LS95AN 1.20	SN74LS164N 1.50	SN74LS257N 1.40	SN74LS381N 3.65	6402	5.00	4080 7.00
SN74LS22N 26	SN74LS96N 1.75	SN74LS165N 1.70	SN74LS258N 95	SN74LS386N 67	6821P	4.50	2107 7.80
SN74LS26N 29	SN74LS107N 39	SN74LS166N 1.75	SN74LS259N 1.45	SN74LS390N 1.90	6850P	4.50	4116/58 for 8180
SN74LS27N 35	SN74LS109N 39	SN74LS168N 1.95	SN74LS260N 39	SN74LS393N 1.90	6852P	5.50	4116 20.00
SN74LS28N 35	SN74LS112N 38	SN74LS169N 1.95	SN74LS261N 3.50	SN74LS395N 1.80	AT-5-2376	11.50	Z80P10 8.00
SN74LS30N 25	SN74LS113N 44	SN74LS170N 2.50	SN74LS266N 39	SN74LS396N 1.70	MC14411	12.00	Z80CTC 8.00
SN74LS32N 27	SN74LS114N 44	SN74LS173N 2.20	SN74LS273N 1.85	SN74LS398N 2.75	M57109	12.43	Z80AP10 9.50
SN74LS33N 38	SN74LS122N 79	SN74LS174N 1.15	SN74LS279N 79	SN74LS399N 1.80	M57160	10.00	Z80ACTC 9.50
SN74LS37N 28	SN74LS123N 90	SN74LS175N 1.85	SN74LS280N 1.75	SN74LS424N 4.50	M57161	10.00	EPROMS
SN74LS38N 29	SN74LS124N 1.50	SN74LS181N 2.75	SN74LS283N 1.80	SN74LS445N 1.25	TMS6001	5.00	1702 5.00
SN74LS40N 25	SN74LS125N 65	SN74LS181N 1.75	SN74LS290N 1.80	SN74LS447N 1.25	81158	1.80	5204 2.50
SN74LS42N 79	SN74LS126N 65	SN74LS191N 1.75	SN74LS293N 1.80	SN74LS490N 1.95	81LS96	1.80	2708 8.00
SN74LS47N 95	SN74LS132N 75	SN74LS192N 1.45	SN74LS295AN 2.20	SN74LS688N 95	81LS97	1.80	2516 25.00
SN74LS48N 95	SN74LS133N 39	SN74LS193N 1.75	SN74LS298N 2.20	SN74LS689N 95	81LS98	1.80	2532 50.00
SN74LS49N 1.00	SN74LS136N 40	SN74LS194AN 1.89	SN74LS324N 1.80	SN74LS870N 2.70			

DPS.1 MAINFRAME - PASCAL SYSTEM

\$100 to IEEE spec

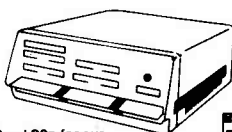

Send 30p for our ITHACA catalogue.

WE STOCK THE FULL RANGE OF S100 CARDS AND ACCESSORIES

ITHACA

PASCAL/Z build your own Pascal Micro Development system. IEE-S100 bus system using DPS.1 main-frame. Supports K2, ASSEMBLE/Z and PASCAL/Z on 8" disc. Complete system **£2910.00**

S100 BOARDS

8k Static RAM board (450ns)	£99.00
8k Static RAM board (250ns)	£117.00
280 cpu board (2MHz)	£105.00
280 cpu board (4MHz)	£123.00
2708/2716 EPROM board	£57.00
Video display board (bare board)	£15.00
Video display board (64-16, 128U/L Ascii)	£108.75
Disc controller board	£131.25
K2 disc operating system	£45.00
ASSEMBLE/Z Macro Assm	£37.50
PASCAL/Z compiler	£205.00
PASCAL/Z CP/M	£235.00
16k Static RAM	£275.00

MULTIWAY CONNECTORS

INSULATION PIERCING	35/70	4.80
20 way plug	2.30 36/72	4.74
26 way plug	2.70 40/80	5.00
34 way plug	3.30 43/86	5.50
50 way plug	4.80 50/100	8.00
20 way skt	3.40 GOLD .156 PITCH	
26 way skt	4.00 6/12	1.25
34 way skt	4.80 10/20	1.50
30 way skt	6.00 12/24	2.00
EDGE CONN PCB	15/30	2.20
60DIL .1" PITCH	18/36	2.30
22/44	22/44	2.65
25/50	3.60 28/56	3.30
28/56	3.90 36/72	3.80
30/60	4.15 43/86	4.60

64 way DIN male 2.50
64 way DIN female 4.50

VISIT OUR SHOWROOM

WE ALSO STOCK:- a comprehensive range of books and magazines, VERO products including S100 and Eurocard and Wire Wrap equipment, Weller soldering equipment, Ribbon Cables, tools, tapes, diskettes, connectors and OK Tool range. Systems continuously on display in our showroom.

CRYSTALS	4MHz	2.10	FB (3850)	9.50
100k	4.43M	1.00	8080A	6.33
200k	5MHz	2.70	6809	24.00
1MHz	6MHz	2.70	Z80	8.00
1008k	7MHz	2.70	Z80A	15.00
1843k	7.160M	2.50	8085A	12.55
2MHz	8MHz	2.70	6502	8.00
2457k	10MHz	2.70	SCMP11	10.00
3276k	10.7M	2.70	6802	13.95

ALL PRICES

Exclude VAT & P/P
VAT 15% P. & P. 40p on small orders.
For larger items please Tel.
Telephone credit card orders accepted subject to £5 min.
RAPID MAIL ORDER SERVICE



CATALOGUE


NEW A4 SIZED ONLY 40p & A.E.



VISIT OUR SHOWROOM SOON
9.30-5.30 Mon-Fri
1.30-2.30 closed lunch
9.30-5.00 Sat
Thursday half day 1.30

TRANSAM COMPONENTS LTD, 12 CEMONT STREET, LONDON NW1

Tel: 01-402 8137 Telex: 444898

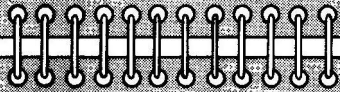

INDUSTRY NOTEBOOK

By Nexus



'Finniston'

The Committee of Inquiry into the Engineering Profession started its work under the chairmanship of Sir Montague Finniston, F.R.S., in July 1977. Its 65,000 word Report, 'Engineering Our Future', was published in January this year by Sir Keith Joseph, Secretary of State for Industry, and the next step, a White Paper, is expected by about Easter. This, in turn, will be debated publicly over a further period of months.

'Finniston', as the Report will doubtless be called, is of immediate value only in calling the attention of the general public to the importance of engineering. Professional engineers, their learned societies and institutions, and their employers already know this.

All the old topics of the past 20 years are served up once again, spiced with some new catch-phrases such as 'the engineering dimension' and 'awareness brokers'. It was clearly difficult to find anything really new to say about the lowly status of engineers in society, salary levels, education, trade union and employer attitudes, codes of practice, registration of engineers, encouraging lady entrants to the profession and 'regeneration of UK manufacturing competitiveness through market-oriented engineering excellence in British products.'

The main interest of 'Finniston' is not in the diagnosis but in the cure which, in the view of the Committee, is the establishment of more bureaucracy and spending more taxpayer's money, some £60 million, with a new Engineering Authority costing about £10 million a year to run. The Authority will promote and strengthen the influence of engineering within the British economy, working in co-operation with the National Economic Development Council and acting as the qualification and registration body for all engineers.

Registration, except for consultant engineers, will be voluntary. Except that if you want a job with the Government or in the public sector of industry or in any company which supplies them, registration will be virtually mandatory because these organisations are to set the lead by recruiting only registered engineers. If found unfit to practice you will be struck off the register.

A new three-tier structure to take care of status is proposed. The elite would become Registered Engineering Diplomates, the great bulk of present degree engineers will become Registered Engineers and the army of technician grades Associate Engineers. Paid study leave should be a statutory right and, as at present, there will be 'ladders and bridges' for engineers to move upwards.

Effect

What effect 'Finniston' will have on civil, mechanical, aeronautical, mining or chemical engineers, or for naval architects and other categories of engineers I am not qualified to judge. But so far as electronic engineers are concerned it is difficult to imagine that it will make the slightest difference.

In fact the broad proposals already exist. Engineers are already registered and existing institutions should only need strengthening, not dismantling. On the question of status, the present title of Chartered Engineer surely sounds more professional than the proposed Registered Engineer. This however is a small point but nothing is achieved by tinkering around with job titles and setting up new committees even though dignified by the title of Authority. In the end it is only job satisfaction and salary which have real influence in attracting people to any occupation, in determining performance and even status in society. Electronic engineers are generally enthusiasts who can't imagine doing anything else. In this they are fortunate as, indeed, in working in an expanding industry with consequent high morale.

It is all a question of attitudes of people towards work and achievement, and Sir Monty Finniston has admitted that he does not expect attitudes to change in less than a generation. My own belief is that the new drive towards a universal core curriculum in schools with compulsory mathematics, English and far greater emphasis on science subjects will do far more to encourage young people into engineering and in raising the status of engineers than any number of talking shops spending weary months compiling reports, however learned they may be.

Rewards

In the light of 'Finniston' a quick check of current job offers showed a remarkable spread of financial reward in electronics. Starting salary for a lecturer can still be as low as £3,480 and a degree standard information office: preparing abstracts starts at

£3,700. In the mid-range a development engineer can command £5,335, a test engineer £6,830, a MPU applications engineer £7,000 plus car. At the higher level a group leader on instrumentation, £12,000.

Overseas posts are looking less attractive than they once were for salary, but £8,630 tax free in Brunei looks reasonable. In West Germany £8,000-10,000 is offered for tidying up the grammar in English literature on data sheets and technical manuals for an instrument company, suggesting that the UK is not the best place to work in Europe if salary is the prime consideration.

The beauty of employment in electronics is the enormous spread of job interests. You can practice in almost any field. If you have a secondary interest in aircraft, you can get into avionics; if you are keen on human welfare, take up medical electronics; or if keen on chemistry, get into analytical instruments. The variety is almost unlimited, and with the present demand for electronic skills at all grades, nobody need stay in a job with an uncongenial environment.

Decca

As forecast last month in this column, Rascal has now emerged into the open with a bid for Decca. I have frequently billed Rascal as 'unstoppable' and this seems to be the case through good times and bad. Rascal-Tacticom has landed a turnkey project worth £40 million for an undisclosed overseas customer. The contract, spread over three years, includes equipment and systems from all the Rascal radio companies in the UK. Another order, worth £4 million, came from the British Ministry of Defence. This is for automatic antenna tuning units for Clansman military radios. The ATUs were designed as a private venture, illustrating Rascal's consistent get-up-and-go philosophy.

Inmos

The 'British Disease' was once again exemplified by screams of protest on the proposed siting of the first Inmos manufacturing plant at Bristol, near the company's technology centre. The screams are entirely political from the development areas of the country which all see the siting of the four plants in other than strictly business terms. Inmos has a difficult enough task to succeed without being instructed to site plants in what the management views as unsuitable or otherwise inconvenient locations. One sympathises with those depressed regions which are naturally disappointed, but trying to block the building of the first factory is no solution if the national need for a large micro-circuit facility is really necessary.

Meanwhile the new GEC-Fairchild plant at Neston, Cheshire, is on schedule with the exterior completed and inside work proceeding at a fast pace. It is difficult not to draw comparisons and conclude that private enterprise gets better and quicker results than enterprises in the public sector.

FREQUENCY METER PRESCALER



Michael Tooley B.A. David Whitfield B.A. M.Sc.

CONSTRUCTORS who have built the Digital Frequency Meter featured in last month's issue may find the maximum operating frequency of the basic counter rather limited for many applications. The performance of the portable DFM may, however, be extended well up into the v.h.f. region by the addition of the self-contained prescaler described here.

The prescaler is a small self-contained unit which may be used with almost any digital frequency counter. It provides a fixed frequency division of $\div 100$ for signals in the range from 1 MHz to typically over 200 MHz, with corresponding outputs in the range 10 kHz to 2 MHz. The unit may be built for a total outlay of under £10, and the simple alignment procedure requires only a d.c. voltmeter.

CIRCUIT DESCRIPTION

The circuit for the prescaler is shown in Fig. 1. It essentially consists of two distinct sections: the input r.f. pre-amplifier, and the $\div 100$ frequency divider. The amplifier is used to provide a useful gain (>10 dB) over the operating range, thus extending the low frequency sine-wave performance down to 1 MHz (the prescaler i.c. requires a minimum signal slew rate of 50 V/ μ s for reliable operation).

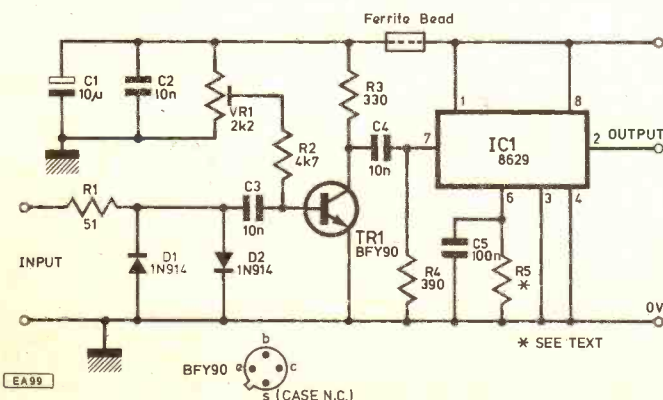


Fig. 1. Circuit diagram of the Prescaler


The maximum operating frequency is limited by the prescaler i.c.; the input stage still provides around 6 dB gain at 500 MHz.

The input r.f. pre-amplifier makes use of the high cut-off frequency ($f_c \approx 2$ GHz) and high gain characteristics of the BFY90 to provide a gain of more than 10dB over the operating range. The transistor, TR1, operates in common emitter mode with the base bias adjusted by VR1. A relatively low value of collector load is used to ensure a reasonably flat gain/frequency characteristic.

The 8629 used in the second stage is a fixed ratio ECL $\div 100$ counter with a minimum guaranteed toggle frequency of 150 MHz (typically to over 200 MHz). The device is used here in single-ended mode and is capacitively coupled to the preceding stage. The output from the divider stages is converted to TTL signal levels.

CONSTRUCTION

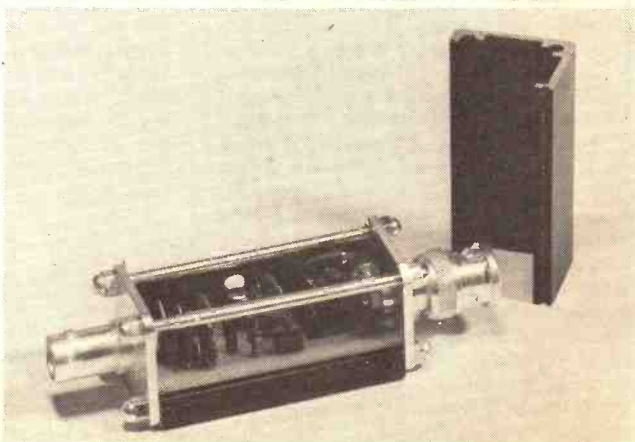It is important that all components used in the circuit are suitable for the frequencies involved. Leads should be kept short to minimise stray inductance, and signal connections



should be made by means of screened cables. Printed circuit construction is recommended and a suitable track design is shown in Fig. 2. The corresponding component layout is shown in Fig. 3. An ideal encapsulation for the p.c.b. is an in-line module case. These modules feature male and female connectors at opposite ends of the fully screened circuit enclosure, allowing direct connection to the normal counter input socket without the need for an additional co-ax cable. The signal cable may then be connected to the female socket on the front of the module. A small connector (e.g.

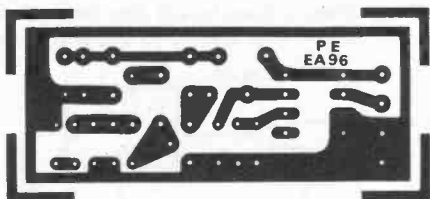


Fig. 2. P.c.b. design

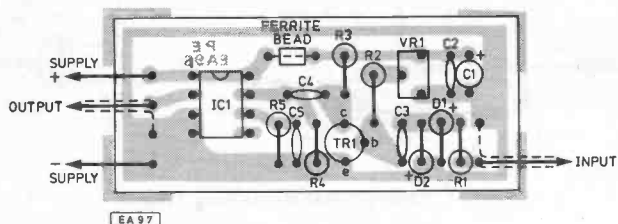


Fig. 3. Component layout

3.5 mm jack socket) should also be provided to supply power to the module; the prescaler requires approximately 6V d.c. at approximately 50mA. The supply should not be allowed to exceed 7.5V, and it should be noted that performance is seriously degraded below approximately 5.2V. A suitable power supply is a pack of four HP7-type dry cells.

COMPONENTS . . .

Resistors

R1	51
R2	4k7
R3	330
R4	390
R5	See text

All resistors $\frac{1}{4}$ W 5% carbon

Potentiometers

VR1	2k2 sub. min vertical preset
-----	------------------------------

Capacitors

C1	10 μ tant.
C2, C3, C4	10n ceramic (3 off)
C5	100n ceramic

Semiconductors

TR1	BFY 90
D1, D2	1N914 (2 off)
IC1	8629

Miscellaneous

Ferrite anti-parasitic bead
p.c.b.
In line circuit module (RS 456-201)

Constructor's Note

Components and p.c.b. are available from **Howard Associates, 59 Outlands Avenue, Weybridge, Surrey KT1 9SU, s.a.e. for details.**

Alignment of the prescaler is simply a matter of setting the d.c. potential at the collector of TR1 to half of the supply voltage by varying the setting of VR1. The value of R5 is a compromise between open-circuit stability and overall circuit sensitivity. Under no-signal conditions the prescaler i.c. will tend to oscillate (at typically 160 MHz). This may or may not be desirable, depending on the application. To avoid this oscillation, which does not otherwise affect the circuit, a resistor may be connected between pin 6 of IC1 and ground. This will cause some loss of sensitivity. Typically a value of 2k2 will prevent oscillation, though larger values (up to 10 k)

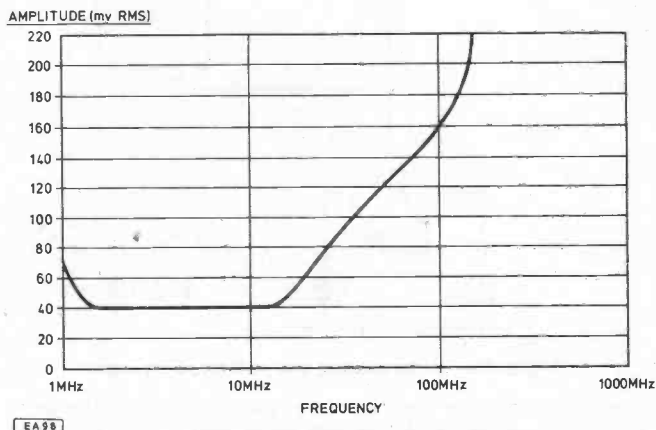


Fig. 4. Prescaler response curve

may be required. Thus, R5 is an optional component. The response of the prescaler circuit to sine-wave signals is shown in Fig. 4; the value of R5 was 2k2.

ADDITIONAL FACILITIES

A number of modifications can be carried out to the DFM which extend the basic facilities provided to the user. Unlike the v.h.f. prescaler, these enhancements require slight modifications to the wiring layout of the basic instrument. For this reason it is suggested that these additions are made after the basic circuit has been built and tested.

VARIABLE SAMPLING INTERVAL

The basic counter features a fixed interval between samples for each range. The sampling interval may be increased by wiring additional resistance, conveniently in the form of a potentiometer, in series with the existing R6. Thus, doubling the value of series resistance (i.e. R6 + potentiometer) will increase the sampling interval by approximately 50 per cent. A potentiometer of 100k or 220k will provide a useful range of control. Fig. 5 shows the modified circuit details. In

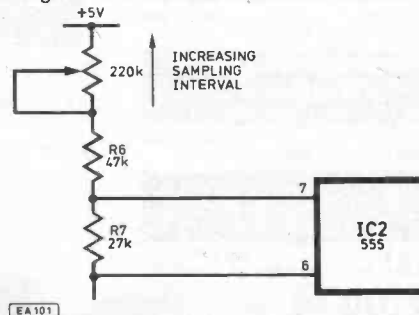


Fig. 5. Modified sampling circuit

practical terms it is only necessary to open circuit R6 and connect one end of the potentiometer to the free end. The other end of the pot is then connected to +5 V at any convenient point.

STORED DISPLAY

In many situations a signal is only available for measurement for a limited period of time. It is then often desirable to save the measured value for later use (e.g. measure the frequency of an oscillator one day and compare it against the value on the next day). This facility is easily provided by inhibiting the action of the re-sampling logic in the control logic section. The simplest way to disable the re-sampling logic is to open circuit the timing capacitor (C4/C5). The arrangement is shown in Fig. 6. The switch shown may be

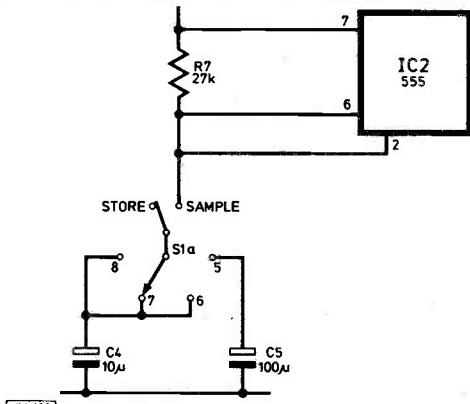


Fig. 6. Circuit to disable the re-sampling logic

combined with the potentiometer used in the variable sampling interval control to provide an overall display sampling control.

MEASUREMENT OF WAVEFORM PERIOD

The signal gating circuitry can be modified to measure waveform period rather than frequency by interchanging the Clock and Signal connections (see DFM Fig. 4). This will then provide a readout of the waveform period with a resolution

equal to the periodic time of the selected clock, e.g. using a 1 kHz clock (periodic time = 1 ms) will provide a readout in milli-seconds (ignoring the decimal point). The resolution corresponding to each of the four ranges on the basic counter is shown in the table below:

- Range 1 reads in units of seconds
- Range 2 reads in units of 100's of ms
- Range 3 reads in units of 10's of ms
- Range 4 reads in units of ms

In all cases the decimal point should be ignored.

The circuit details for the changeover switching are shown in Fig. 7. The printed circuit board has been designed with two wire links (LNK1 and LNK2) to allow this modification

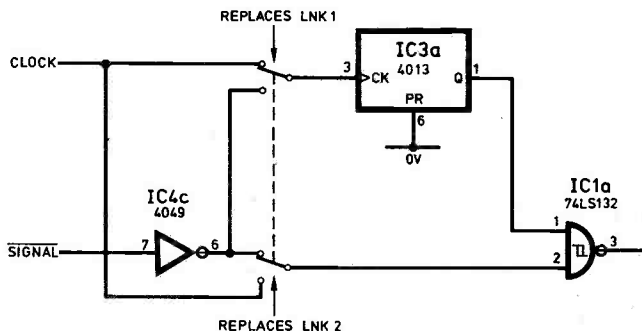


Fig. 7. Changeover switching details

to be implemented with the minimum of disruption to the existing wiring. All that is required is a two-pole changeover toggle switch, though greater elaboration may be employed with S1 being replaced with a multi-wafer type switch and additional l.e.d.s used to indicate the display units. ★

Enter the 80's with SAXON

STEREO DISCO SYSTEMS WITH LIGHT SHOW & DISPLAY

STANDARD CENTAUR 100W

£309 inc. carr. & VAT Deposit £62
12 mth £24.80 or 24 mth £14.51

SUPER CENTAUR 200W

£366 inc. carr. & VAT Deposit £74.00
12 mth £29.32 or 24 mth £17.16

GXL 200W with PDF BINS (illus)

£499 inc. carr. & VAT Deposit £99
12 mth £40.17 or 24 mth £23.50

CUSTOM CENTAUR 400/600W with four PDF 100A Bins

£833 inc. carr. & VAT Deposit £167
12 mth £66.87 or 24 mth £39.13

MINI DISCO 100W MONO

£229 inc. carr. & VAT Dep. £46
12 mth £18.38 or 24 mth £10.58



- Headphone monitor/cue light
- Full mixing/crosstape
- Tape & mic inputs
- Top Quality
- 4 channel soundlight

All systems complete
with loudspeakers, leads,
& 2 years warranty

20%
DEPOSIT
CREDIT
TERMS

100 WATT

£207 inc. carr. & VAT Dep. £42
or 12 mth £6.87
or 24 mth £3.69

- Four mixing inputs & master
- Bass & treble controls
- Sturdy construction
- Twin Pielco cabinets

200 Watt £309 inc. carr. & VAT Dep. £62
• Twin 200W cabinets
• Six inputs—three channels
12 mths £24.80
24 mth £14.51



JUST PLUG IN AND GO!!

AP100
AMPLIFIER £65
AP200 AMPLIFIER £109

P.A SYSTEMS C/W LOUSPEAKERS



£30 FREE!

Vouchers with our new catalogue over 200 items of disco systems, lighting and accessories. Send £1.50 now.

EXAMPLES:

Fuzz lights	£26.50
Projectors from	£43.50
Strobes	£35-£220
Rope lights 25'	£42.50
Disco stands	£23.50
Echo chambers	£75
100W speakers	£27.50
10 way chaser	£275
100W twin horn bin	£110
800W spot bank	£39.50

Mixers, mics, amplifiers, goosenecks, light units, bubble machines, mirror balls, helicopters, bins, consoles, and much more.

AND IF WE HAVEN'T GOT IT - WE'LL GET IT!

SAXON
ENTERTAINMENTS
333 WHITEHORSE ROAD
CROYDON
SURREY CR0 2HS
Tues-Sat 9am-5pm


ALL MAIL & CREDIT ENQUIRIES TO
CROYDON TO ORDER
Send cheque/crossed POS or Telephone (01) 684 6385
Access/Barclaycard. Telephone orders accepted
For Credit Sales & Enquiries Ring
SUE ABEGB ON (01) 684 8007

MANCHESTER
DISCO CENTRE
237 Deansgate
Manchester
(061) 832 8772
Tues-Sat 10am-5pm

Full range of Pluto, D.J.
Lightomation products in
stock
Send £1.50 now for your
catalogue - worth £30!!!

next month


FREE Stickies

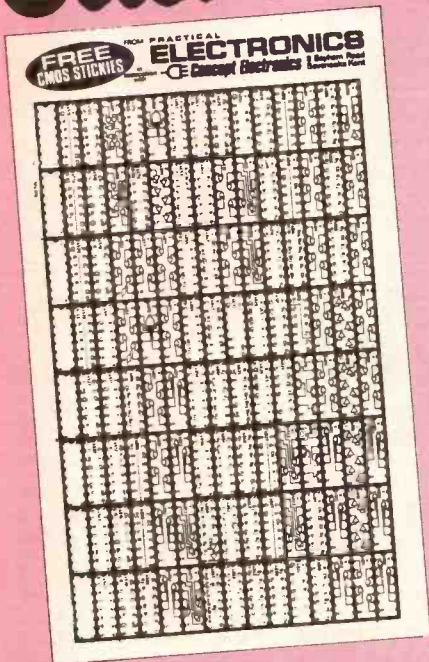

SPLIT-PHASE TREMULO

A simple but effective substitute for a rotary cabinet. With this a function generator output is phase split and modulated by the input. Output amplitudes are variable through two channels.

DYNAMIC SEMICONDUCTOR TESTER

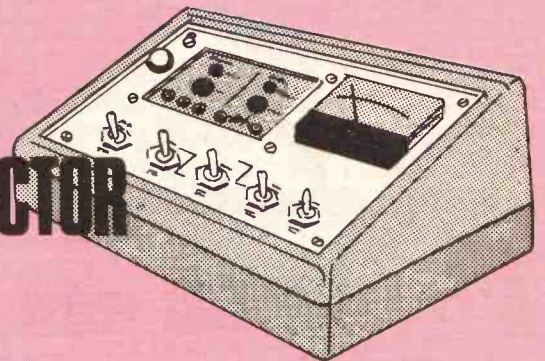

This unit is capable of testing the vast majority of semiconductor devices available, under actual working conditions. Diodes, bipolar transistors, junction and insulated gate f.e.t.s. can be checked and many unmarked devices tested and identified.

Worth
at least **60p**


SPECIAL OFFER... EDUKIT

PRACTICAL

ELECTRONICS

OUR MAY ISSUE WILL BE ON SALE FRIDAY, 11 APRIL 1980

PE congress 30W I.C. STEREO AMPLIFIER

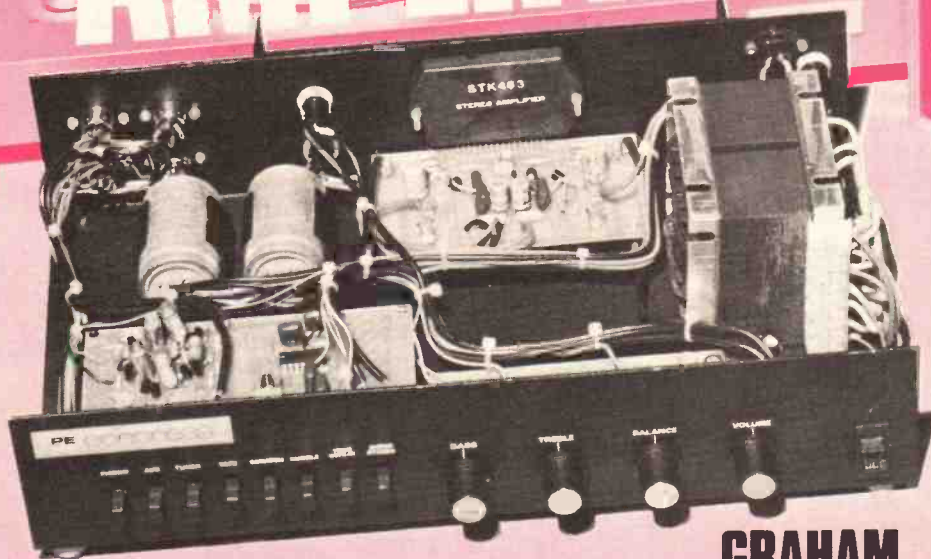

GRAHAM JACKSON

ON DECIDING to design a budget amplifier certain considerations immediately spring to mind. What is meant by "budget", apart from inexpensive for example. It seems that a budget amplifier suffers by virtue of its necessarily basic circuitry. Filters, are often not included, the phono stage is based around an integrated circuit, or a simple two transistor stage, which is either noisy or has poor overload or distortion characteristics, and the main amplifier is generally of modest standard with an output power in the range of 10-15 watts, both channels driven.

Over the months leading to the design featured here, many circuits were tried, and the result is a coming together of the various circuits that gave the best results, hence the name "Congress". It is felt that although the price puts it in the budget range, the performance that can be expected puts it on par with amplifiers costing a good deal more. The decisions behind each design stage are therefore detailed in the following article.

BLOCK DIAGRAM

Looking at the block diagram of Fig. 6, it can be seen that

a separate phono input stage is provided. This is so that there is no switching in the input and equalisation paths which would be necessary if this stage was made to amplify all of the inputs. This goes to the select switches where auxiliary and tuner inputs are provided. Any input not used is switched to ground to help prevent unwanted breakthrough.

A tape monitor function is also provided. The selected input then goes to a buffer amplifier, with a gain of two, which can also be switched as a scratch filter. A rumble filter is incorporated in the disc input stage where it may be independently selected. The tone control section providing bass cut and lift and treble cut and lift, can be switched out of circuit if not required by the tone defeat function. This has the advantage that any noise generated by this stage is removed, and that both channels are then known to have a "flat" response. The main amplifier follows the volume and balance controls and the stereo-mono switch. The tape input has its own buffer amplifier so allowing monitoring via the tape decks own internal amplifier whilst recording the input signal.

SPECIFICATION...

We have noticed that in some published amplifier projects parts of the specification have been omitted and in some cases quoted figures are not theoretically obtainable. In order to obtain a totally unbiased specification for the PE Congress, which could be compared with reviews in the hi-fi press, we asked Gordon J. King to carry out a full laboratory test on the amplifier. Mr. King has written many books on hi-

fi and is employed by a number of hi-fi publications as an equipment reviewer, his book *Audio Equipment Tests* will aid readers requiring more information on the data.

The following figures, notes and diagrams are the results of Gordon King's tests on the final amplifier design which will be described in this short series of articles. The data is published in full without any alteration. **We believe this is a unique step in the presentation of an amplifier design and one which will allow readers to feel confident in the specification given.**

Editors Note The 2dB rise in the R1AA equalisation curve (Fig. 5) at approximately 40Hz has been corrected and the scratch filter response is now 12dB per octave. The photographs are of the prototype which was modified before these tests were carried out.

O/p to clipping continuous sinewave			
per ch. both driven 8 ohms:	30W (14.8dB)	32.4W (15.1dB)	32W (15dB)
ditto 4 ohms:	33W (12.2dB)	37.2W (12.7dB)	37W (12.7dB)
per ch. one driven 8 ohms:	38.3W (15.8dB)	40.5W (16dB)	38.3W (15.8dB)
ditto 4 ohms:	45.5W (13.6dB)	49W (13.9dB)	49W (14.1dB)
O/p 16kHz per ch. one driven 5 ohms:	45W (14.5dB)		
ditto Z_L :	— (15dB)		
Z_L /5 ohms headroom:	±0.5dB		
O/p 1kHz 1HF bursts per ch. both driven			
8 ohms:	42.3W (16.3dB)		
4 ohms:	50W (14dB)		
Burst/steady state headroom			
8 ohms:	+1.2dB		
4 ohms:	+1.3dB		
Recovery from 10dB symmetrical 1HF burst overload:	virtually instantaneous		
Distortion factor 500mV i/p	8 ohms	4 ohms	
auxiliary both ch. driven			
20Hz* 10dB/OdB o/p:	0.083%/0.086%	0.1%/0.1%	
1kHz 10dB/OdB o/p:	0.024%/0.024%	0.046%/0.044%	
20kHz 10dB/OdB o/p:	0.04%/0.041%	0.09%/0.068%	
Distortion factor and residual 500mV i/p auxiliary both ch.			
driven 16kHz			
5 ohms:	0.044% (Fig. 1) at -10dB o/p		
Z_L :	0.048% (Fig. 2) at -10dB o/p		
Intermodulation distortion 19kHz + 20kHz 10dB o/p per ch.	0.03% 1kHz product		
both driven	0.063% 1kHz product (Fig. 3)		
8 ohms:			
4 ohms:	Fig. 4		
Squarewave 16kHz Z_L 0dB o/p:	3.2µs		
Rise time 0dB o/p 4 ohms:	≈ 5.5Hz-109kHz (-3dB points)		
Freq. response auxiliary i/p 0dB o/p 4 ohms:	>5 (ref. 14.8dB 1kHz o/p 8 ohms)		
Slew factor ref. 13dB o/p 4 ohms:	66		
Damping factor 8 ohms 40Hz and 0dB o/p:			
Input sensitivity 1kHz, 0dB 4 ohms**	22mV		
high level i/ps:	0.4mV		
PU:	44mV		
Tape			
PU overload threshold			
20Hz:	15.5mV		
1kHz:	185mV		
20kHz:	1,800mV		

SPECIFICATION...

Signal/noise ratios ref. 0dB 4 ohms o/p*** high level i/ps ref. 500mV: PU ref. 5mV i/p:	85.7dB (86dB tone defeat on) 74dB (74.6dB tone defeat on)
Stereo separation 0dB 4 ohms o/p**** auxiliary 1kHz/10kHz: tuner ditto: tape ditto: PU ditto:	72dB/49dB ref. 500mV i/p 72dB/49dB ref. 500mV i/p 51dB/36dB ref. 500mV i/p 70dB ref. 5mV i/p/48dB ref. 50mV i/p
Crosstalk 1kHz from 500mV i/p tuner 0dB 4 ohms o/p to auxiliary: to tape: to PU:	84dB (noise floor of test) i/p open 84dB (noise floor of test) i/p open 77dB i/p open
Residual hum and noise 4 ohms o/p DIN audio band: weighted:	0.66mV 0.115mV
Offset d.c. at o/p across 4 ohms left ch.: right ch.:	6.6mV 0.5mV
Deviation from RIAA PU i/p:	Fig. 5 upper curve
Tone control responses relative to "flat" and defeat:	Fig. 5 middle curves
Low and high filter responses:	Fig. 5 upper left/middle right
Tape recording o/p:	120mV for 100mV i/p at aux.

* Includes mains ripple

** Measured in tone defeat mode

*** Signal/noise ratios and noise measured with CCIR/ARM weighting

**** Non-speaking channel input shorted for these measurements

Notes: Tests made after amplifier was conditioned for one hour at one-third rated output. The dB outputs refer to 2.828V across the stated load (n.b.: 2.828V into 8 ohms equals 1W). Z_L refers to a reactive load simulating a difficult loudspeaker of 5 ohms modulus and 60 degrees phase angle at approximately 16kHz.

Laboratory facilities by Gordon J. King (Enterprises) Limited, Brixham, Devon.

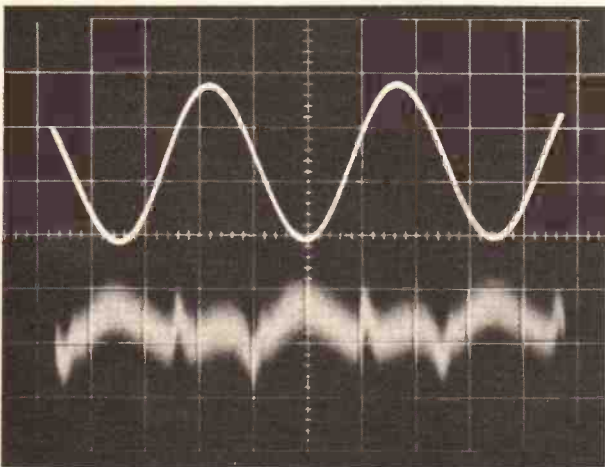


Fig. 1. Distortion factor residual at 16kHz -10dB output across 5 ohms resistive, corresponding to 0.044 per cent. Input auxiliary

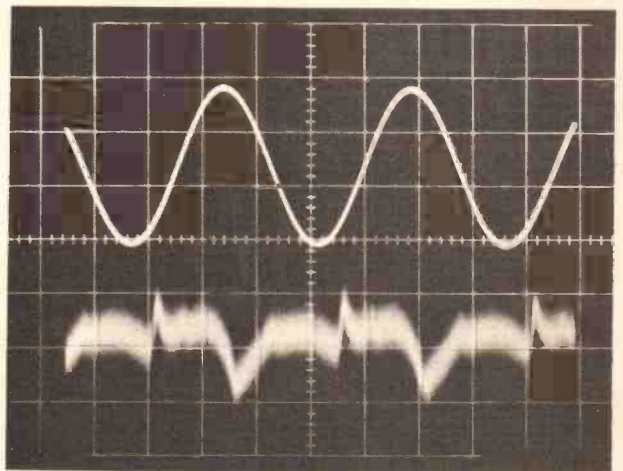


Fig. 2. Distortion factor residual at 16kHz -10dB output across Z_L (see notes at bottom of the lab chart for definition), corresponding to 0.048 per cent. Input auxiliary

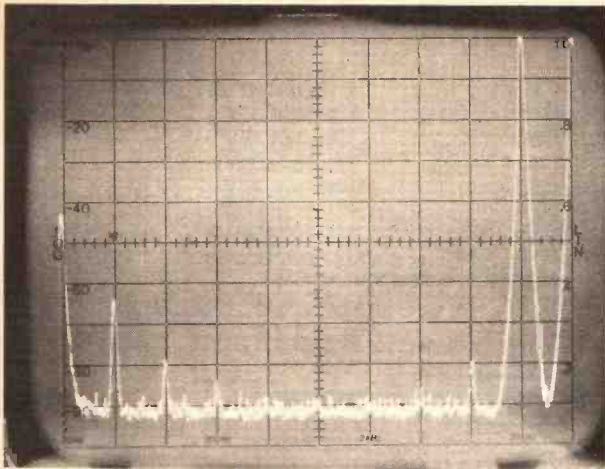


Fig. 3. Two-tone 19+20kHz equal amplitude intermodulation distortion with the 1kHz product as the parameter, corresponding to 0.063 per cent at 10dB output across 4 ohms resistive. Input auxiliary

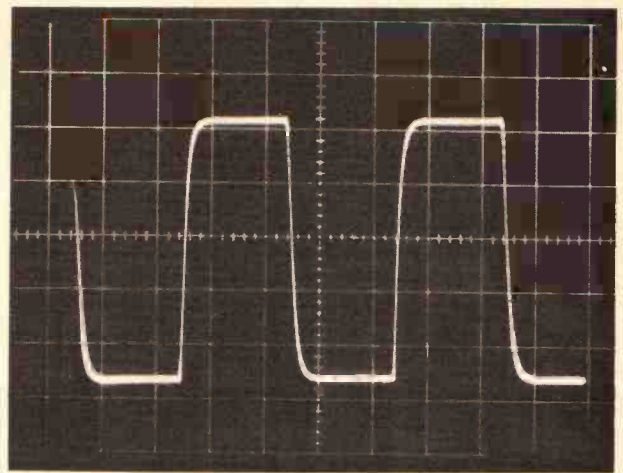


Fig. 4. Squarewave at 16kHz across Z_L at 0dB output, input auxiliary

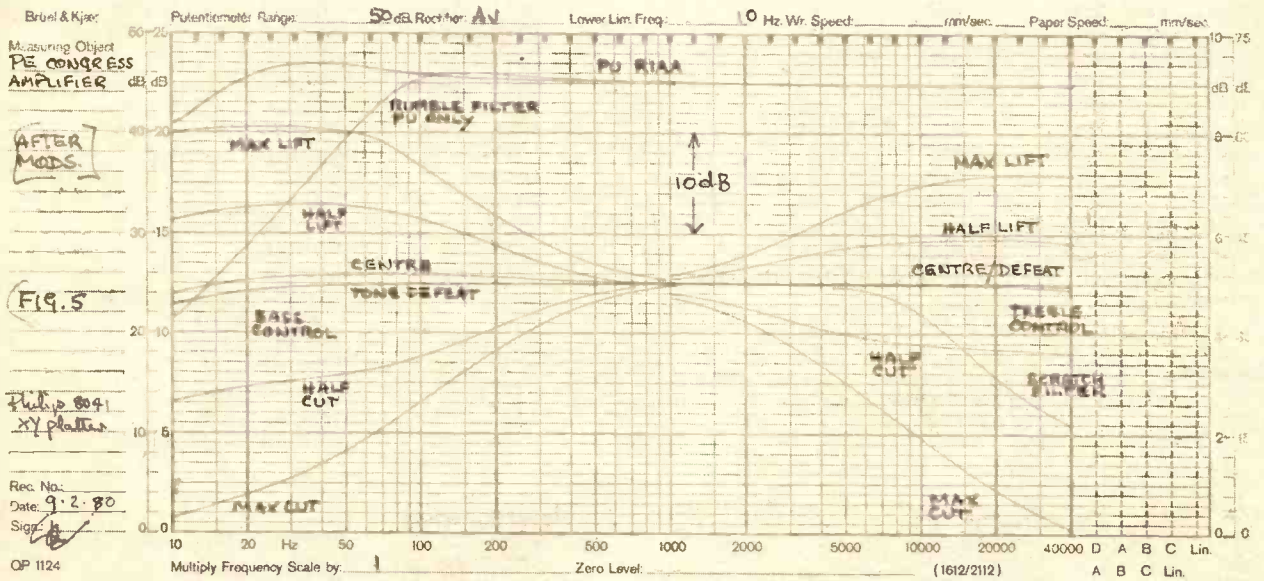


Fig. 5. Pen-chart graph of 50dB range (1dB per minor vertical division) and 10Hz-40kHz sweep showing deviation from RIAA at pickup upper, tone control responses relative to "flat" and defeat middle, and low (rumble) and high (scratch) filter responses. Input auxiliary



COMPONENTS . . .

Resistors

R1 —101	10k	R35—135	120
R2 —102	47k	R36—136	120
R3 —103	47k	R37—137	10k
R4 —104	220	R38—138	15k
R5 —105	10k	R39—139	33k
R6 —106	10k	R40—140	10k
R7 —107	180k	R41—141	3k3
R8 —108	82k	R42—142	180k
R9 —109	56	R43—143	47k
R10—110	56	R44	10k
R11—111	1k	R45—145	10k
R12—112	10k	R46—146	47k
R13—113	10k	R47—147	120
R14—114	100k	R48—148	120
R15—115	100k	R49—149	1k
R16	470	R50—150	33k
R17—117	100k	R51—151	330
R18—118	27k	R52—152	0Ω33 2W5 w.w.
R19—119	27k	R53—153	33k
R20	10k	R54—154	100
R21—121	180k	R55	10k
R22—122	10k	R56—156	4Ω7 1W
R23—123	10k	R57	10
R24—124	120	R58	10
R25—125	120	R59	33
R26—126	180k	R60	120
R27	10k	R61	10k
R28	470	R62	10k
R29—129	10k	R63	120
R30—130	100k	R64	33
R31	10k	R65	100 1W w.w.
R32	10k	R66—166	10k
R33—133	100k	R67—167	1k
R34—134	180k	R68—168	10k

$\frac{1}{3}$ W carbon film unless stated

C32	4,700μ elect 40V
C33	10μ elect 35V
C34	10μ elect 35V
C35	10μ elect 35V
C36	10μ elect 35V
C37	470μ elect 50V
C38	470μ elect 50V
C39—139	22p polystyrene

Mylar unless otherwise stated

Semiconductors

TR1 —101	BC184C
TR2 —102	BC184C
TR3 —103	BC212C
TR4 —104	2N5400
TR5 —105	2N5550
TR6 —106	BC182B
TR7 —107	2N5400
TR8 —108	2N5550
TR9 —109	BC182B
TR10—110	2N5400
TR11—111	2N5550
TR12—112	BC184C
TR13—113	BC184C
TR14—114	2N5400
TR15—115	2N5400
TR16—116	2N5550
TR17—117	2N5550
TR18	BD535
TR19	BD536
TR20	BC212B
TR21	BC182B
TR22—122	BC182B

IC1 STK463 (Sanyo stereo power amplifier i.c.)

D1—D13 1N4148 (13 off)

D14—D17 1N5402 (4 off)

D18, 19 BZY88 C30V

D20—D23 1N4148 (4 off)

D24—D27 WO2 1A bridge rectifier

Potentiometers

VR1—101	100k dual ganged lin.
VR2—102	100k dual ganged lin.
VR3—103	10k dual ganged lin.
VR4—104	22k dual ganged log.

Miscellaneous

SK1 to 4, SK101 to 104 phono sockets (4 pairs)
 SK5—105 panel mounted 4mm banana sockets (4 off)
 S1 to S8, S101 to S108 preassembled switch bank with buttons
 S9 single pole mains switch with built in neon
 T1 125VA mains transformer 28-0-28V plus 35-0-35V (off load voltages)
 FS1 500mA antisurge fuse and panel mounting holder
 FS2, FS3—102, 103 3A quick blow fuses and p.c. mounting holders (4 off)
 Printed circuit boards, materials for chassis and case, fixings, wire, knobs, mains lead, grommet etc.

All components, including p.c.b.s are available from **Wicca Electronics Systems Ltd., Orchard Works, Church Lane, Wallington, Surrey.**
Components for second channel shown with designations plus 100.

Capacitors

C1 —101	5p6 polystyrene
C2 —102	22μ elect 25V
C3 —103	22n
C4 —104	1n5
C5 —105	8n2
C6 —106	47μ elect 16V
C7	10μ elect 35V
C8 —108	1μ elect 35V
C9	10μ elect 35V
C10—110	1n
C11—111	470p polystyrene
C12—112	10μ elect 35V
C13	10μ elect 35V
C14	10μ elect 35V
C15	10μ elect 35V
C16—116	1μ elect 35V
C17	10μ elect 35V
C18—118	10μ elect 35V
C19—119	47n
C20—120	680p polystyrene
C21	10μ elect 35V
C22—122	10μ elect 35V
C23—123	390p ceramic
C24—124	100μ elect 16V
C25—125	100n
C26	10μ elect 35V
C27	10μ elect 35V
C28	10μ elect 35V
C29	4,700μ elect 40V
C30	4,700μ elect 40V
C31	4,700μ elect 40V

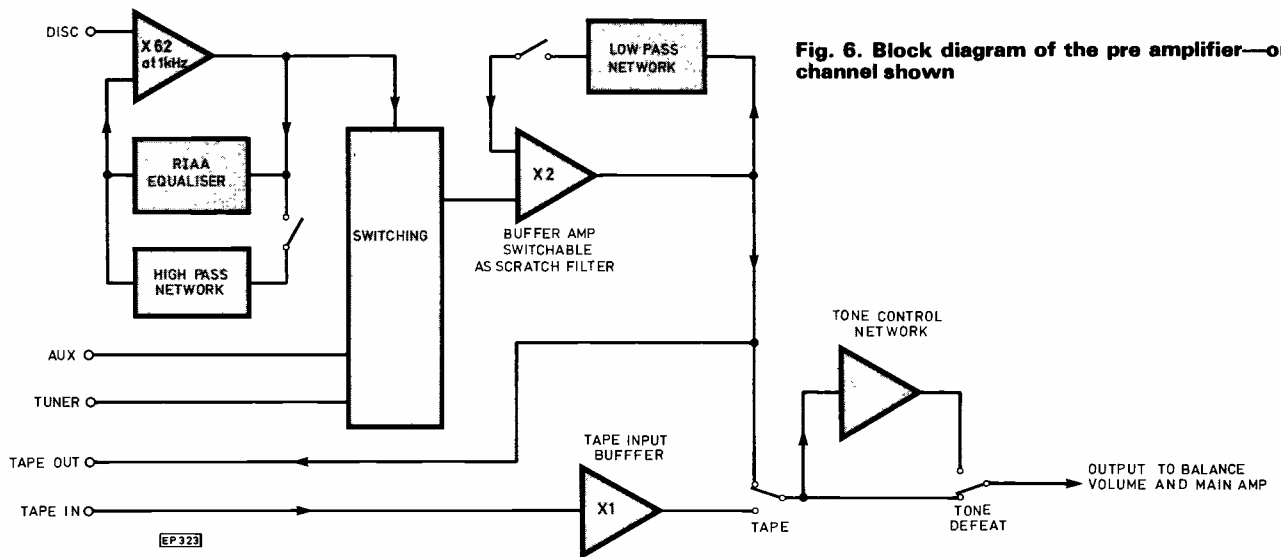


Fig. 6. Block diagram of the pre amplifier—one channel shown

PHONO INPUT STAGE

It was decided to use the operational amplifier configuration so that the entire amplifier runs on the split rail principle giving very good supply ripple rejection at the speaker and saving the expense of a regulated supply for the main amp. Various i.c.s were tried at the input stage but all were found to be far too noisy. It is surprising how much detail in the sound from disc can be masked by noise, and it is important to get the noise generated by the input stage down to as low a value as economically possible.

A discrete version of the op. amp has therefore been adopted. Referring to Fig. 7 which shows a simplified circuit of the one employed, TR1 and TR2 form the differential input. These two transistors (BC184Cs in the amplifier) have been designed to run on collector currents of 40 μ A which is about optimum for noise generation in these devices. Transistors TR3 and TR4 form a high gain stage so as not to load TR1's collector too severely. The collector load for these transistors is a constant current source set at about 10mA. A network giving equalisation for RIAA with an accuracy of ± 1 dB is then returned to the base of TR2.

The tone control circuitry is the standard Baxandell type and is built round two discrete differential amplifiers of the same type as the disc input stage. The amplifier has been designed so that this stage can be switched out if not required.

MAIN AMPLIFIER

The main amplifier posed a problem. It was decided that 35 watts one channel driven or 30 watts per channel both driven into 8 ohms was a minimum requirement with

40 watts being ideal to allow the handling of transients. Low distortion coupled with good bandwidth was also required and preferably the elimination of the normal a.c. load line protection which can cause problems when driving inductive or capacitive loads such as speakers with their associated crossover networks. Various circuits were tried with price in mind, but the output transistors either did not have suitable characteristics or were too expensive to keep the amplifier to a sensible overall price.

Attention was drawn to the new Sanyo device type STK463 which is a dual output stage. This fulfilled all of the requirements except that crossover distortion was apparent when tested. However, it was noticed that this distortion was symmetrical showing that the output stage was well designed. Also it was noticed that clipping at 20kHz into 8 Ω gave some tendency to instability and was not symmetrical. On close inspection of the recommended circuit it was noted that a bootstrap load was externally provided for the class A drive stage, formed from two resistors and a capacitor.

From the value of the resistors the nominal current had been set at 5mA. As an experiment this was replaced by a 5mA constant current source with impressive results. The crossover distortion was reduced to a very low level, even at 20kHz, and the clipping became stable and symmetrical showing good recovery time. Having obtained these results this module has been adopted without reservation for its excellent performance.


In this design power outputs of 30 watts r.m.s. sine wave were given per channel, both channels driven or 38 watts r.m.s. sine into one channel (8 ohms). The module has been designed to fuse under short circuit conditions as it can withstand 2 seconds into a short circuit, long enough for a fuse to blow. This has the advantage cited previously of eliminating a.c. load line protection, but it is of course essential that fuses are replaced with the correct types. A complete circuit diagram will be shown next month.

It is interesting that this amplifier was used to replace one costing several hundred pounds, driving Yamaha NS1000 monitor loudspeakers and employing a Shure MkIV magnetic cartridge on a Thorens deck for the disc input, and that the opinion of people hearing the comparison, albeit not under controlled conditions, was that they could not tell the difference!

We would like to thank Quality Hi Fi, North Road, Poole, for supplying the AKAI deck shown in the front cover and heading photographs

NEXT MONTH: circuit and construction

Fig. 7. Simplified circuit of the op amp—phono input stage

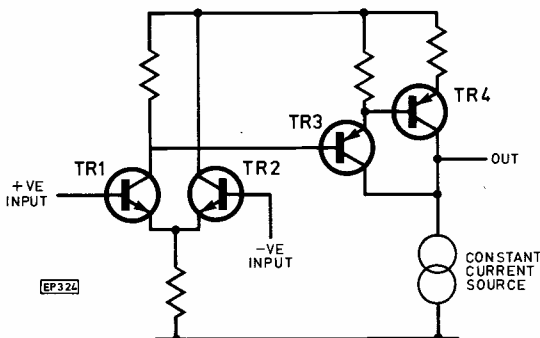

SPECIAL SUPPLEMENT

VIDEO

FOR EVERYONE!

G.K. GARDNER

ONE OF the major problems encountered with video recording techniques is that the developments have been extremely rapid, with the result that there is a profusion of conflicting information made available to the general public.

This article is intended to clarify the situation a little. One word of warning . . . Although video techniques have reached an important point in their development, it goes without saying that new ideas and developments are just around the corner.

That is not to say—don't go out and buy—the existing systems will be with us for many years. However, it must be recognised that progress in the advancement of the technology in electronics is so rapid that new ideas are inevitable. During the next decade video equipment of all kinds is all set to undergo an unprecedented boom, the like of which has never been seen before. It is an established fact that domestic video recording techniques are still very much in their infancy. Despite this fact it is conservatively estimated that about 100,000 VCRs were sold during last year, and sales for this year are predicted to be some 50 per cent higher.

APPLICATIONS

The basic application of the VCR is its ability to record TV programmes off air, and replay them through a conventional domestic TV receiver at the owner's leisure. The current technology enables the user to record a programme either when it is being viewed, or record an alternative channel at the same time. Additionally, with the aid of a preset timer, it is possible to record programmes without the presence of the viewer, so that they can be watched at a convenient time. This concept of "time shift" is an important feature of modern domestic video.

The addition of a suitable TV camera (either black and white or colour) offers the facility for the viewer to make his own

programme. At present the cost of a colour camera is disproportionately high, and this is probably the limiting factor in growth of this market.

The comparatively recent availability of portable systems (Portapack) running of rechargeable batteries means that it is now feasible to record "live events" such as the school sports, football matches, or even the local airshow. The advantages of this system over conventional cine is that the pictures and sound are instantly replayable through the domestic TV. The major drawback is the comparatively bulky nature of the camera and recorder compared to cine equipment, but it is only a matter of time before this problem is rectified.

HISTORY

In order to understand the development of domestic video techniques, it is necessary to take a brief look at developments in this field since 1948.

In the early days, it was demonstrated that the magnetic tape medium was capable of recording and playing back video information, albeit of a quality below broadcast standards. Between 1958 and 1968, many companies developed video recording systems, which because of their lower complexity and smaller size became acceptable to both industry and education alike. The major breakthrough in recording techniques was that of the open reel helical scan system, and as a direct result of this system it was possible to further simplify and drastically reduce the price to an acceptable level.

One of the most significant advances made was the development by the BBC of an experimental recorder in 1952. This system was called VERA, but not surprisingly disappeared soon after its debut on "Panorama" in 1958. Toshiba in 1953 lay claim to the development of the helical scan system now com-

mon to all domestic recorders. This system was at that time not without problems, which were caused by inferior tape quality and frictional drag of the rotating head drum. In 1956 Ampex in the U.S.A. developed the Quadruplex system, and such was the enthusiasm shown for this in the U.S.A., some 80 units were sold within months of its debut. Consequently the VR-1000 as this was called, became the recognised broadcast standard in the U.S.A.

In 1961 Sony took the wraps off a completely transistorised recorder designated the SR-201. Unlike the VR-1000, it used the helical scan principle of Toshiba. 1962 heralded the arrival of the Telecan system from the Nottingham Valve Co. Unlike its competitors it used $\frac{1}{4}$ inch tape and a fixed head system. The fact that this recorder sold for £61 (the VR-1000 by comparison was \$50,000) may have something to do with the technical difficulties which killed off this machine by 1964. Not a serious competitor!

Philips then introduced the EL 3400 which broke the £1,000 price tag barrier. By achieving this low price new markets were opened up, mainly in the industrial sector. It is interesting to note that at this time Ampex were close to introducing a fixed head recorder (VR 303) but withdrew this in favour of a helical scanner (HVR) selling at only £450.

This American breakthrough was short lived, however, when Sony introduced a helical scanning recorder selling for only £200 (TVC 2000). Sony did not stop there, they also produced the world's first domestic VTR (a four head version of the CV 2000). Their rival Akai introduced the VX 1100, but this machine was never sold, and a helical scanning model was offered in its place.

In 1967 Sony offered the DVK 2400 portable recorder, which sold for a mere £700, and weighed in at a modest 9lb. By comparison, a year later Ampex offered a portable recorder based on Quadruplex, which sold for £23,000 and weighed 50lb. Hardly a domestic machine.

Sony produced a $\frac{3}{4}$ inch cassette format which was aimed predominantly at the domestic market in 1969. This system was

called Umatic, and was to become so successful it was adopted as the world standard for industrial and educational use. Its relatively high price limited its domestic acceptance though. Philips introduced the 1500 series cassette based VCRs in 1972, and to all intents and purposes the 1500 was the first true domestic recorder.

The main reasons for this so called "domesticity" were the fact that it contained its own UHF tuner, timer, and modulator meaning it could be easily used with a domestic TV. The inclusion of a timer/time switch gave birth to the concept of "time shift recording". Unfortunately the ruggedness and reliability aspects of this recorder were to lose it the battle with the Umatic system for worldwide acceptance as a non-domestic recorder but despite this Philips claim to have sold over 200,000 of these machines.


Meanwhile in Japan, Sony had introduced the Betamax I system, and one year later in 1976 JVC introduced their own VHS system. With the threat of competition from these systems in Europe, Philips hurriedly launched the 1700 series. The first machines arrived in the U.K. in the autumn of 1977. Philips designated this system VCR-LP and offered the user a two hours recording time. The following year, both Betamax and VHS systems were introduced by Sony and JVC respectively in Europe. Grundig followed with the Super Video Recorder (SVR) which is a variant of VCR-LP. The ensuing battle has resulted in the fact that VHS has captured a large share of the market with VCR-LP running second, with Betamax a surprising third. SVR has found relatively little support so far.

It will be interesting to observe the effect on the market of the Philips Video 2000 system, which is potentially capable of regaining the lead for Philips. However, it may well be that the battle is already lost to VHS, and that 2000 series will become the white elephants of the 80s. Time alone will tell.

DOMESTIC CASSETTE RECORDER

The essential feature of all domestic machines is the helical scan system, which together with the use of $\frac{1}{2}$ inch wide tape

Internal view of the new Grundig 2X4 (Video 2000 system)

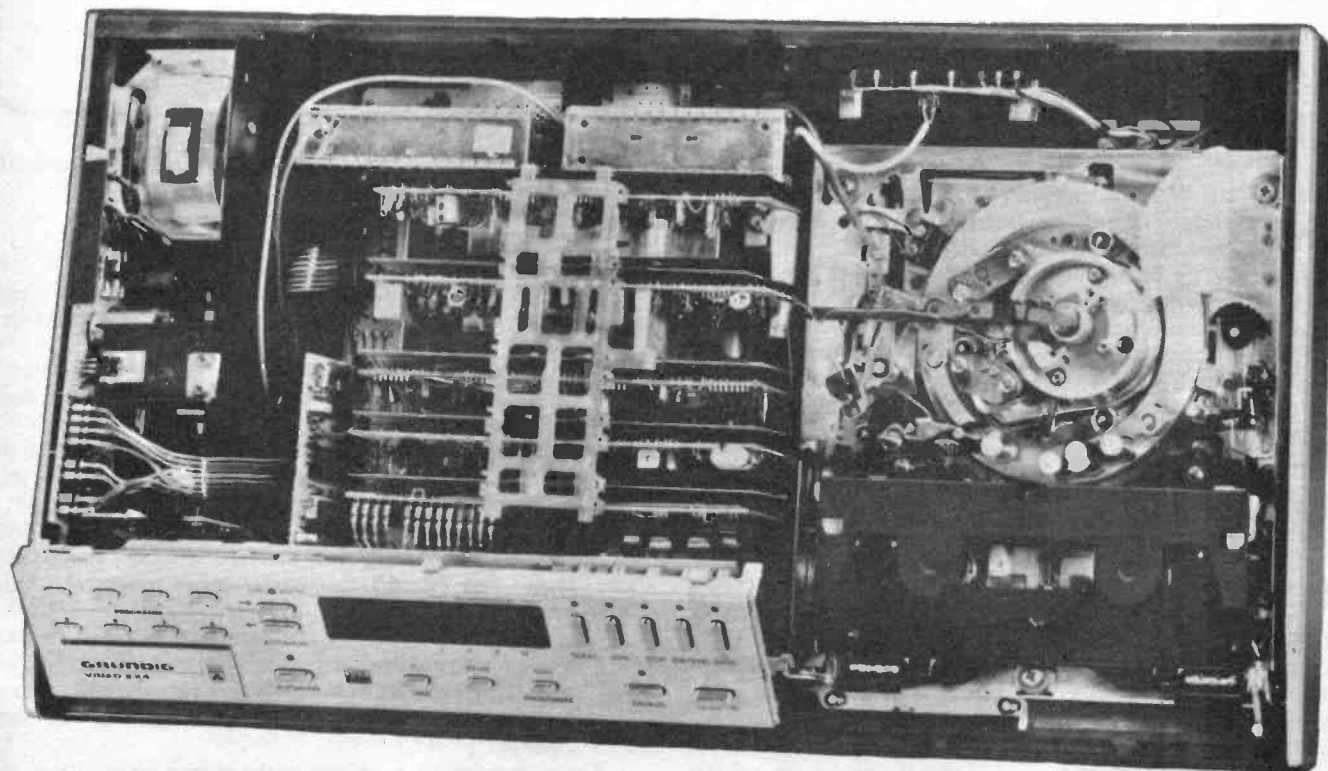

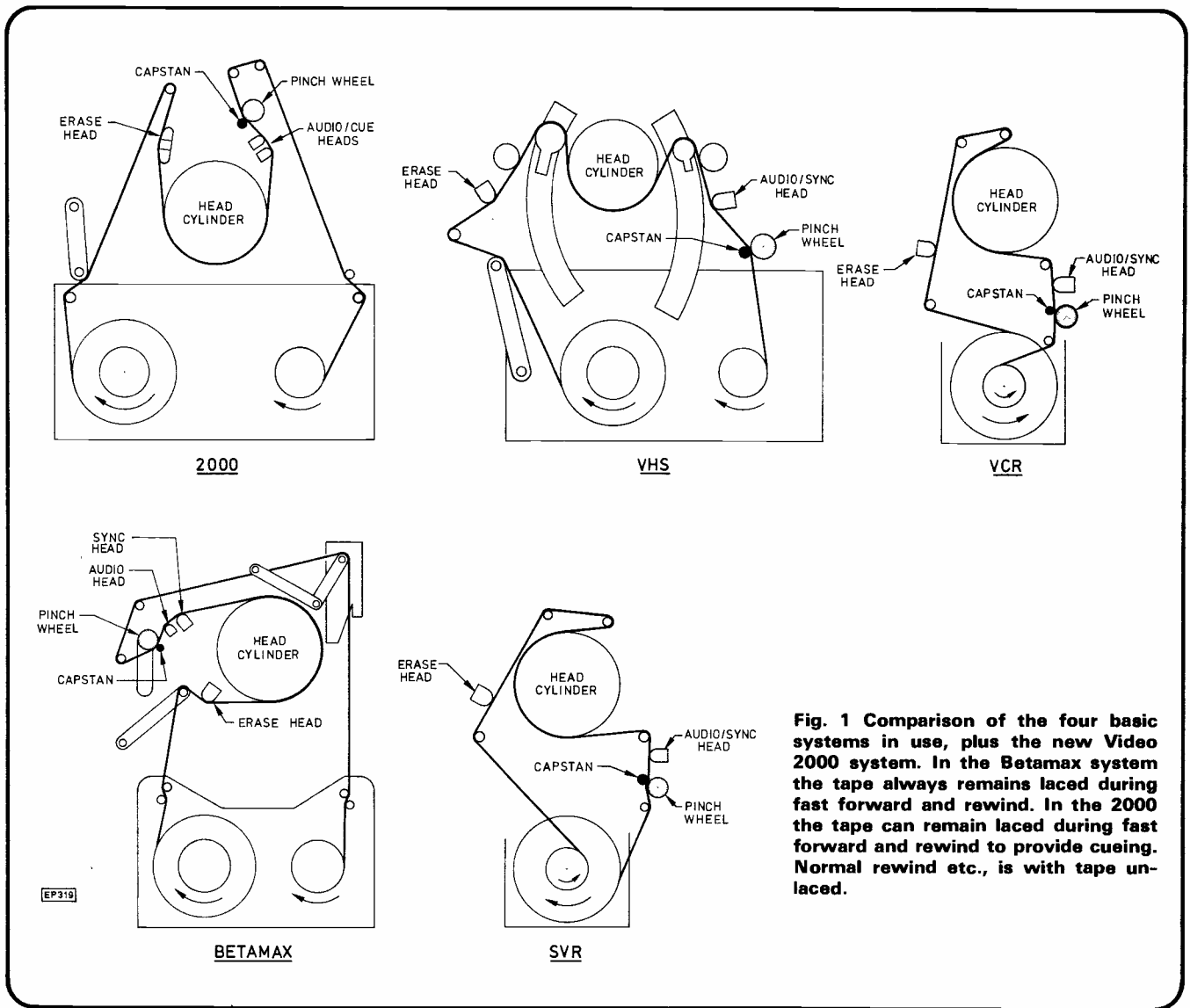


Fig. 1 Comparison of the four basic systems in use, plus the new Video 2000 system. In the Betamax system the tape always remains laced during fast forward and rewind. In the 2000 the tape can remain laced during fast forward and rewind to provide cueing. Normal rewind etc., is with tape unlaced.

allows the high packing density necessary for the storing of video signals. With the exception of SVR, VCR and VCR-LP, the tape is stored in a cassette (rather like an enlarged version of the well-known Philips audio cassette), see Fig. 1.

Ironically, the Philips VCR uses a stacked spool arrangement which is mechanically inferior to both the VHS and Betamax cassettes. Philips reluctant admission of this is clearly evident in that the tape format adopted for the new 2000 series is very similar to the VHS, but is unfortunately incompatible. One of the major advantages of using a cassette based system for domestic applications is that mechanical handling of the tape is greatly simplified, as the tedious (and delicate) process of threading the tape around the drum without damaging the heads is eliminated.

SYSTEMS AVAILABLE

Apart from the new Video 2000, there are four basic systems currently in use for domestic machines. The Philips 1500 VCR format is effectively obsolete, mainly because of its limited playing time. However, there are still a large number of these machines in every day use, and some specialist companies are offering to update these to VCR-LP.

For the sake of simplicity, and so that the reader can quickly

compare the systems, Table 1 shows technical details and differences between them.

WHY VHS?

There are several reasons why the VHS format has a high popularity, particularly in Europe. Some of these reasons are listed below:

- 1) Cheaper tape feed costs (typically £3.50/hr.).
- 2) Aesthetic appearance of hardware (it has a professional appearance).
- 3) VHS is supported by far more brand names than its rivals, which gives the customer more confidence in this system (see Table 2).
- 4) Fast winding is achieved with the tape retracted into the cassette, rather than with the tape wrapped around the drum. This has the real advantage of minimising head wear.
- 5) Video input and output facilities mean easy interface with a Video camera, and enables two machines to be connected together, so that dubbing of recordings from one machine to the other can be achieved with optimum quality.

The picture quality is related to the writing speed, which by

TABLE 1. TAPE FORMATS

Format	Video Writing Speed (M/sec)	Linear Tape Speed (cm/sec)	Drum Rotational Speed (r.p.m.)	Drum Diameter (mm)	Maximum Recording Time (min)	Lace Up Time (secs)
VHS slant azimuth 2 head helical scan	4.83	2.34	1500	105	180	3
Betamax slant azimuth 2 head helical scan	6.60	1.873	1500	62.5	195	3 (laced up in FF and REW modes)
SVR slant azimuth 2 head helical scan	8.21	3.95	1500	105	240	
VCR slant azimuth 2 head helical scan	8.10	14.29	1500	105	60 nominal 75	3 thread 3 lockup
VCR-LP slant azimuth 2 head helical scan	8.10	6.56	1500	105	120 nominal 150 (1702-180)	3 thread 3 lockup
Video 2000 slant azimuth 2 head helical scan	5.08	2.44	1500	65	240 + 240 (reversible cassette)	5.5

reference to Table 1 would appear to indicate that SVR and VCR-LP in theory at least are capable of slightly better quality than the others. In actual practice, provided a well adjusted TV receiver is used, then it is hard to distinguish between the different systems. It goes without saying that the picture quality of all the machines can be improved if a small (12 inch to 18 inch) screen TV is used, rather than the more usual domestic giant. The differences in the systems are most probably more markedly shown with projection TV systems.

Table 2 shows the principle features, and highlights the differences between the different VCRs currently available on the UK market. No doubt the list will grow. Most extensive details can be found in the various manufacturers' handbooks, and the inclusion of this data in this table has been deliberately omitted for the sake of clarity.

PORTABLE RECORDERS

With the introduction of the video cassette for domestic VCRs it was only a matter of time before this system was adapted for use in a totally portable system. Existing semi-

professional and professional portable systems employ the Umatic format, which for reasons already stated, exclude its acceptance in the domestic market on the ground. It came as no surprise when JVC introduced the 4100 portable colour video system in June/July 1979.

This system incorporates the GC4100 twin tube camera, HR4100 VHS recorder, TU41 tuner/timer, and AAP41 power

Matsushita's prototype solid state colour camera built around a 210,000 element chip. Claimed to virtually eliminate blooming the camera gives resolution of 280 (hor) by 480 lines and will operate at 500 lux. Mass production techniques are now being investigated for this small, lightweight camera

The Toshiba Betamax recorder model V-5470B with freeze frame, frame advance and double speed facilities, plus visual cue and review in fast wind modes

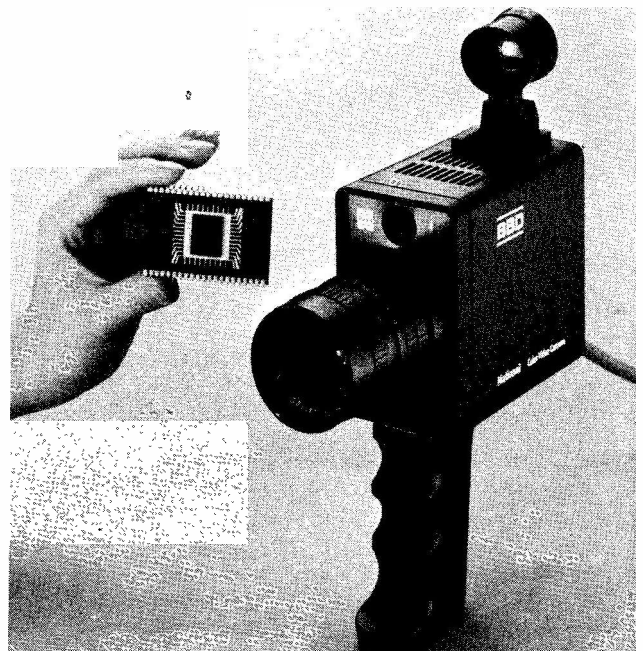


TABLE 2. DOMESTIC VIDEO RECORDERS


Make/Model	Format	Timer	Resolution	Audio Dub	Input/Output	Special Features	Other Remarks
JVC HR330EK Ferguson 3292 Akai Vs 9300 Mitsubishi HS 200 B Baird 8900 Nordmende	VHS	24hrs on only. Timer 1 sec	240 lines S/N 40dB max	Yes	RF: coax Video: uhf	Electronics — Mitsubishi	
JVC HR 3330 Ferguson 3VOO Akai VS 9500	VHS	8 day	250 lines S/N 40dB	Yes	as above	Search button	
JVC 3660EK	VHS	8 day on/off	as above	Yes	as above		Remote control, including variable speed playback. RF output test signal
Hitachi VT 3000	VHS	3 day on only	Probably similar to HR330EK	Yes	as above		
National Panasonic NV8600B NV8610B	VHS	24 hrs. on/off 7 days on/off	240 lines about 42db s/n	Yes	as above	RF test signal, moisture sensor	NV 8610 has still frame, single frame advance
Sony SL8000	Betamax	3 days on only	270 lines S/N 42db	No	RF in/out standard coax	Still frame	Max. recording time 195 mins.
Toshiba V-5250	Betamax	3 days on only	270 lines S/N 42db	No		Remote pause	
V-5470B	Betamax	7 days allows 3 separate recordings	240 lines S/N 42db			Still frame, single frame advance, double speed, visual cue	
Sanyo VTC 9300	Betamax	3 days on only	270 lines S/N 42db	No	Video BNC		Timer 0-62 min. every day at same time
Grundig SVR 4004	SVR	on/off 10 days ahead	240 lines min. (300)	No	RF only Standard coax	Still frame transport logic. Remote control and self seek timer	max. recording time 240 mins.
Grundig SVR 4004 AV	SVR	as above	as above	Yes	RF and Video	as above	
Grundig 2X4	2000	10 days 4 separate recordings	approx 3MHz	Yes during recording	AV (DIN)	Full function remote control	Reversible tape 2X4 hrs can remain laced on ff/rew for cueing
ITT Philips Philips 1700	SVR VCR VCR-LP	3 days on/off	3.5 MHz max s/n 40 db	No	RF only standard coax		as for SVR 4004 Max. recording time 60 mins. (90m) Max. recording time 150 mins.
Philips 1702	VCR-LP	10 days on/off	as above	no	as above	3 hrs. tape duration. 4 digit tape counter	Max. recording time 180 mins.
Philips 2020	2000	Microprocessor controlled, allows 5 separate recordings up to 16 days forward	S/N 50db	Yes, with add on unit	RF and Video in add-on unit	Infra red hand held remote control. 26 input channels. 4 digit LED tape counter	Max. recording time 2 x 4 hrs., on reversible cassette

supply. For simple portable recording all that is required is the camera and recorder. To convert the recorder to a machine having off air recording facilities, including pre-set recording, the other units are required.

One of the major problems with any portable piece of equipment is making the system small and light enough. The GC4100 camera weighs 3.7kg, and the recorder a mere 9.3kg, including rechargeable battery pack. Not too bad when you think about it.

One additional problem encountered with this type of equipment is its ability to operate in a variety of positions without malfunctioning. JVC have evercome these problems in the 4100 using a quartz locked capstan servo, and a quick response head drum servo to maintain the stability of the mechanics at all times. Ruggedness is an essential quality for portable machines.

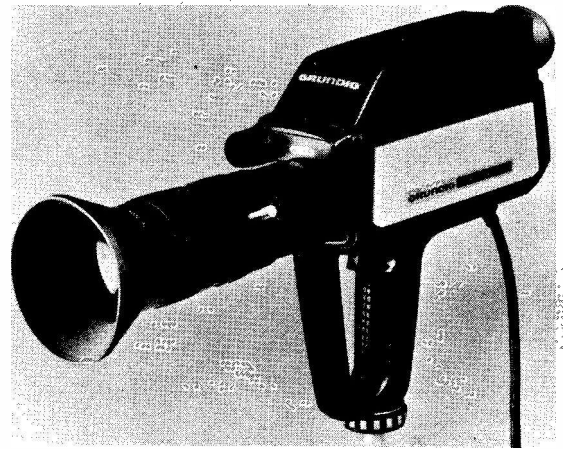There are now several other VHS portables on the market,



The Grundig FAC 1800 single tube colour camera incorporates an electronic viewfinder

Panasonic WV 3300E camera in action. This model has an electronic viewfinder and is priced at £839.50



the majority of which show similarity to the 4100. Table 3 shows current models available in the U.K.

PORTABLE VIDEO CAMERAS

There are a number of colour video cameras, suitable for use with both portable and mains operated domestic VCR's. Where it is intended to use the camera with a portable recorder, then it is important to have the facility of having an electronic viewfinder, thus enabling the operator to actually see what is being recorded.

Another important aspect is the facility that a zoom lens can offer. Ideally a zoom lens with a 6:1 zoom ratio and having a wide angle (12.5mm) is a must for creative work. It is also useful to have a macrofocussing facility, so that close up work can be accomplished. Ideally the provision for connecting a remote microphone enables a high signal to noise ratio for the sound to be maintained.

TABLE 3. PORTABLE VIDEO TAPE RECORDERS (COLOUR)

Make/Model No.	Tape System	Tape Speed (cm/sec)	Writing Speed (M/sec)	Power	Resolution	Recording Time	Weight (Kg)
JVC CR440E	Umatic	9.53	8.54	13.5W	140 lines	20 min.	11.2
Hitachi SV340	Umatic				240 lines		14.0
Sony V03800P	Umatic						
RCA HR1020	$\frac{3}{4}$ inch type A	not known		12V at 14W	not known	over 2 hrs.	12.2
JVC HR4100	VHS	2.339	4.83	12V at 10W	240 lines at 40dB S/N	60 min. record. 180 min. playback	9.3
Ferguson 3V01							
Akai VT530							
National Panasonic NV8400	VHS	as above		12V, 3AH	not known, but similar to above	as above	8.9
Grundig VCR601	VCR	14.29	8.10	12V	3MHz, 42dB S/N	60 min.	10.0
Philips LDL1100							
Sony SL3000	Betamax		as for standard Betamax system			not known	not known

TABLE 4. COLOUR VIDEO CAMERAS (DOMESTIC & SEMI-PROFESSIONAL)

Make/Model No.	Vidicon	Resolution	Lens	Power	Sensitivity	Weight (Kg)	Remarks
JVC G71-P	single 25mm	230 lines (hor) 300 lines (vert)	6 × Zoom (17-102mm)	12V, 12W	down to 100 lux	3.6	Macro lens facility
JVC G31-P	as above	as above	25mm f1.8	as above	as above	2.7	Optical viewer
JVC GC3300 JVC GC4100	2 × 17mm vidicon	400 lines S/N 45dB	12.5-75 mm f1.8	12V, 13W	down to 250 lux down to 100 lux	3.4 3.7	used in HR4100
JVC G X33U JVC G X66U	not known		3 × Zoom 6 × Zoom	not known		1.5 1.5	
Hitachi-Denshi GP-7 GP-5	single 25mm vidicon	250 lines (hor) 40 dB S/N	details not known	12V 11W	100 lux at f2	2.2	
Hitachi Denshi FP 3030H FP 3060H	single 25mm vidicon	270 lines (hor) S/N 43dB		12V 12W		3.0	
FP 1020	single 25mm saticon three × 17mm saticons	270 lines (hor) S/N 46dB 500 lines S/N 46dB		12V 15W 12V 22W		7.0	
Ikegami HL 77	three × 17mm PbO	500 lines (hor) S/N 48dB				7.4	
CTC 2400	three × 17mm saticon, newvicon, PbO, chalnicon, vidicon	550 lines (hor) S/N 46dB					
National Panasonic WV 3300E WV 3310E	25mm cosvicon		17-102mm 25mm f1.8		down to 100 lux	2.5 1.7	
Sony DXC-1610P	single 25mm MF trinicon				optimum 1000 lux min 200 lux (f/2.1)	6.6	
Grundig FAC 1800	single 25mm	250 lines (hor)	6 × Zoom 17-102mm	220-240V a.c.	100 lux at f/2	2.5	


Table 4 lists a number of domestic and semi-professional colour video cameras that are available. Of particular interest is the Hitach-Denshi GP5, which unlike the JVC GC4100 contains only one vidicon tube. The use of this single tri-electrode tube enables a high quality, small and low cost camera to be made available to the public.

It is claimed that this single vidicon is capable of producing pictures which are just as good as those produced by two and three tube cameras. One important point about the tube used in this model is that it is capable of functioning at very low light levels. The manufacturers also claim that this camera is capable of operating correctly between temperatures of -10 degrees C and +40 degrees C.

The camera is extremely easy to use. The built-in automatic sensitivity control (ASC) circuits means that the camera at all times operates under optimum conditions. The only controls that require adjustment are the "Colour Temperature" and "Brightness". Because of the very low power consumption, the camera can operate off batteries for a maximum of one hour. Alternatively it can be operated from the mains using a suitable adaptor. The optional electronic viewfinder can easily be attached to the camera. Apart from the desirability of having this facility, it is also possible to observe the recording already made using this device. Further details of this camera are included in Table 4.



Sanyo VTC 9300 Betamax machine

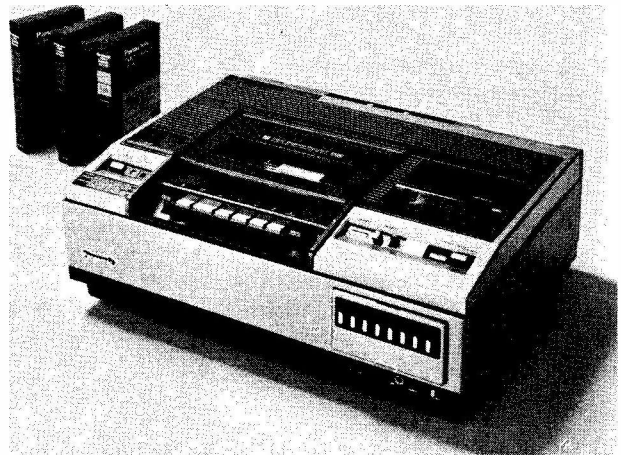

Panasonic NV-8610 with freeze frame facility

Mitsubishi VHS recorder



FUTURE DEVELOPMENTS

The Philips 2000 video system has already been mentioned in this report, but with its introduction, a new generation of microprocessor controlled recorders must be just around the corner. If past events are anything to go by, it is almost a forgone conclusion that the Japanese rivals of Philips have their extensive research and development facilities working flat out to produce yet another type of machine. One can only hazard a guess and suppose that as the current generation of machines has almost certainly reached the technological limit, then the next will have to utilise digital rather than analogue recording techniques.

As far as camera improvements are concerned, we can look toward the introduction of solid state technology in place of the conventional vidicon. Although, like digital recording techniques, the introduction of CCD's in cameras could almost be prohibitive from a cost point of view, mass production will ultimately result in systems that will be physically smaller, more reliable, and cost less.

One development that certainly lends itself to miniaturisation is a system of recording originally developed by BASF for domestic machines called LVR (linear video recording). This has recently been used by Blaupunkt to produce a new miniature machine called Mini-Maz 1. This uses a tiny tape transport mechanism which is capable of being held in one hand. The distinct possibility of incorporating such a device *inside* a video camera would mean a camera system comparable in size to a standard Super 8 Cine camera. The sheer ease, convenience and low cost of such a system suggest a very interesting future for the Mini Maz, assuming this reaches large scale production.

Toshiba have also developed an LVR system, first shown in prototype form at the Chicago Consumer Electronics Show last June. Toshiba plan to launch their system in September, it will have a two hour recording capability and employ an endless loop cassette. The "target price" will be £250 and a three to four hour cassette is also being developed.

DISC

So far this article has concentrated solely on the recording and playback of video information, and no article that was seeking to state the future of video would be complete without at least a mention of the Videodisc. Although a playback only type system, it is bound to make a profound impact when it arrives. Introduction of at least one or possibly as many as three systems are due to be launched in the UK in June or July of this year. The main advantage of VLP (as Philips call it) is that it will be possible to offer full length feature films at a fraction of their cassette cost. A further advantage is that high quality slow motion and still facility is offered by this system.

One thing is certain about the future — whatever format wins the battle, and whatever disc system is accepted, the growth of this sector of the electronic market will be such that it is confidently predicted that there will be over one million VCRs in British homes in four years time. ★

The new front loading Grundig 2X4, Video 2000 recorder



Metac

ELECTRONICS & TIME CENTRES

QUARTZ LCD 11 Function Slim Chronograph

12:30^{pm} 45

Hours mins secs

8 14TH

Month date day

0:00 00

Min sec 1/10 1/100



6 digit, 11 functions, Hours, mins., secs., day, date, day of week, 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet.

Price only
£9.95

Also available:
SOLAR CHRONOGRAPH
M9 Price £11.95

SAME DAY DESPATCH.

M3 Price includes POST & PACKING

QUARTZ LCD ALARM with Snooze Alarm

12:30^{pm} 45

Hours mins secs

8 14TH

Month date day

7:30^A

Alarm



6 functions plus Alarm. Conference signal, 5 minute snooze alarm, Conference signal sounds 4 secs. before main alarm to give advance warning and an option to cancel. Snooze sounds 5 mins. after main alarm and is always preceded by the conference signal.

Price only
£9.95

SAME DAY DESPATCH.

M4 Price includes POST & PACKING

QUARTZ LCD ALARM CHRONOGRAPH with 12/24 display

12:30^{pm} 45

Hours mins secs

8 14TH

Month date day

0:00 0

Min sec 1/10th

7:30^A

Alarm



Hours, mins, secs, day of week. Month, date, day of week, alarm, hour, mins., a.m./p.m. 24 or 12 hour display mode. Alarm test. Chronograph, lap time, stop watch 1/10 secs.

Price only
£13.95

Also available:
SOLAR ALARM CHRONO
M7 Price £17.95

M16 Price includes POST & PACKING

QUARTZ LCD Ladies Day Watch

Hours, mins., secs., day, date, back light, auto calendar.

12:30

Hours mins

8 14

Month date

:45

Secs



Fully adjustable bracelet. Only 25 x 20mm and 6mm thick. Silver or Gold.

Price only
£7.95

M15 SAME DAY DESPATCH. P.&P. included

QUARTZ LCD Ladies Cocktail Watch

Beautifully designed with a very thin bracelet.

12:30

Hours mins

8 14

Month date

:45

Secs



Hours., mins., secs., day, date, backlight and auto calendar. Bracelet fully adjustable to suit slim wrists. State Gold or Silver finish. Only 25 x 20 x 6mm.

Price only
£14.95

M18 SAME DAY DESPATCH. P.&P. included

HANIMEX Electronic LED Alarm Clock

Features and Specification:

Hour, minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indication. Repeatable 9-minute snooze. Display bright/dim modes control. Size: 5.15" x 3.93" x 2.36" (131mm x 11mm x 60mm). Weight: 1.43 lbs (0.65 kg).



M13

Price only
£10.20 Thousands sold!

QUARTZ LCD 5 Function

Hours, mins., secs., month, date, auto calendar, back light, quality metal bracelet. 6mm thick.

12:30


Hours mins

8 14

Month date

:45

Secs

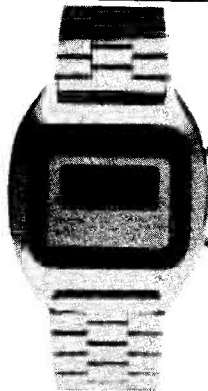

Price only

M1 SAME DAY DESPATCH. **£6.95** P.&P. included

METAC GUARANTEE

All METAC products carry 12 months guarantee and we also refund your money if not satisfied with our goods or service in the first 10 days.

METAC's well equipped service centre minimises service delays. Please note, we do not delay your order to clear cheques.

Telephone your order using Barclaycard/Access

Number on on



03272 - 76545

OR

01-723 4753

24 hour answering service
OR COMPLETE THE
COUPON

WHOLESALE MAIL ORDER

Send for our trade price list and order details. Sell our products to your friends and earn yourself

£££'s

**NEW 24 HOUR
DESPATCH SERVICE**

METAC have opened a new even faster Mail Order and Service Centre at DAVENTRY. Orders received before 3.30 p.m. will be despatched same day.

**VISIT OUR ELECTRONIC TIME CENTRES
AND SEE ONE OF THE MOST IMPRESSIVE QUARTZ WATCH
RANGES IN BRITAIN**

LONDON
327 EDGWARE ROAD,
LONDON W.2
Telephone: 01-723 4753

DAVENTRY
67 HIGH STREET,
DAVENTRY, NORTHANTS.
Tel: 03272 76545/77659

NORTHAMPTON
ST. GILES SQUARE,
NORTHAMPTON
(Opens 1st February, 1980)

**QUARTZ MELODY
Alarm Chronograph**
INCREDIBLE WATCH 34 Functions



5 independent working modes, day of week in English, French or German. (Just select the one you like). Hours, mins., secs., day, date, countdown alarm, dual time zone, 1/100th sec., stopwatch. Lap/split time, 1st and 2nd place times. Melody test function.

Price only
£19.95

Price includes
POST &
PACKING

M30 SAME DAY DESPATCH.

**CASIO CHRONO
95QS - 32B**

Stainless steel case, water resistant to 66 feet. Hours, mins., secs., am/pm, year, month, date, day. Auto calendar. Pre-programmed until the year 2029. 12/24 hour. Stopwatch function. Range 7 hours, 1/100 sec. (Mode) Net time/lap-time/1st - 2nd place times. Dual time function. Accuracy 15 secs. per month. Battery life approx. 4 years.



Price only
£23.95

M22 SAME DAY DESPATCH.

**CASIO F-200
Sports Chrono**

Attractive Mans watch in black resin with mineral glass. Hours, mins., secs., am/pm. Month, date, alpha-numeric day. Auto-calendar set 28th Feb. Stopwatch working range 1 hour, units 1/100 sec. Mode, Net Time/lap/time/1st - 2nd place times. Accuracy approx. 15 secs. per month. Battery 12 months.



Price only
£15.95

M24 SAME DAY DESPATCH.

**CASIO ALARM
CHRONO**

81CS - 368
Hours, mins., secs., day, and also day, month and year perpetual automatic calendar. 100th sec. chronograph to 7 hours. Net time/lap/time/1st and 2nd place times. User optional 12/24 hr. display. 24 Alarm. User optional, hourly chime. Backlight, mineral glass, stainless steel. Water resistant to 100 ft. Battery life approx. 4 years.



Price only
£35.95

M25 SAME DAY DESPATCH.

**CASIO F-8C
3 year battery life**

Hours, mins., secs., am/pm, date, day. Auto calendar set 28th February. Accuracy 15 secs. per month. Battery life approx. 3 years.



Price only
£10.95

M36 SAME DAY DESPATCH.

**SEIKO
CHRONOGRAPH**

Hours, mins., secs., and day of the week. Month date and day of the week. Stopwatch display - Hours, mins., secs., up to 12 hours (mins., secs., 1/100 secs. up to 20 minutes). Lap timing. Continuous time measurement of two competitors. Stainless steel, mineral glass.




Price only
£39.95

SAME DAY DESPATCH.
M33 including POST & PACKING

**SEIKO ALARM
CHRONOGRAPH**

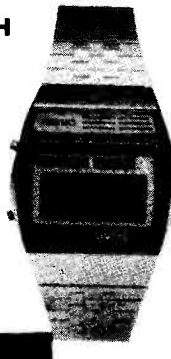With WEEKLY Alarm, Hours, mins., secs., month, date, day, am/pm. Weekly alarm - can be set for every day at designated time, e.g. 6.30 am on Monday, Wednesday and Friday. Alarm set time displayed above time of day. Full stopwatch functions, laptime, split etc.



Price only
£79.95

SAME DAY DESPATCH.
M10 including POST & PACKING

**SEIKO DIGI-ANA
CHRONOGRAPH**

TIME AND CALENDAR FUNCTION
Analog part display Hour, mins., secs. Digital part display; Hour, mins., secs., date, day and colon. Calendar-month, date, day, stopwatch - Hour, mins., secs., 1/100 secs. LAP/STOP and stop marks. Counter-function. Time and calendar setting function.



Price only
£79.95

SAME DAY DESPATCH.
M62 including POST & PACKING

POST COUPON TO: METAC (24 hour despatch centre), FREEPOST, 47a High Street, Daventry, Northants.

PLEASE COMPLETE BOTH COUPONS

Please send me

I enclose P.O./Cheque value

Barclaycard/Access No.

Name

Address

FROM:

**METAC ELECTRONICS & TIME CENTRE, (PE),
67 HIGH STREET, DAVENTRY, NORTHANTS.**

Name

Address

POST, PACKING AND VAT INCLUDED IN PRICE.

Power Supplies for M.P.U.s

Alan Clements B.Sc. Ph.D. Part 1

AN article devoted to power supplies for microprocessors may, at first sight, appear odd. After all, a power supply is often dismissed as nothing more than a black box with its input terminals connected to the public 240V, 50Hz, electricity supply. However, this black box has the physical characteristics of volume, mass, power dissipation, regulation, reliability, and cost. In this article a brief description of the operation and characteristics of power supplies is given. The aim is to make the designer of a microprocessor system aware of the power supply, and in particular of the penalties which must be paid if it is inadequate.

All microprocessors require a source of current at a constant voltage to provide them with the power without which they cannot function. The vast majority of microprocessors, their MOS peripherals and bipolar support chips have a single 5 volt supply. Some devices, notably EPROMs and dynamic RAMs, require additional sources of current at 12V, -12V or -5V. Fortunately, the trend is to design new i.c.s needing only a single 5V supply.

It is often thought that the provision of a power supply for a microprocessor system is a trivial matter. This is not so. In the last few years the power consumed by active devices has fallen dramatically, from the watts dissipated by valves, to the milliwatts dissipated by discrete transistors, and now to the microwatts dissipated by active devices on silicon chips. However, as the power consumed per active devices has fallen, the total number of active devices per system has risen from tens to millions. Today, sophisticated multiple microprocessor systems can be found with power supply busses carrying 120 amps.

The primary function of a power supply is the production of an adequate current at a constant voltage. A secondary function of a power supply is the

protection of the circuit being supplied with power from mains borne transients, or from the failure of some part of the power supply itself. The total power required by a microprocessor system is often largely dependent on the size of the memory used in the system. A small system with only 1024 bytes of RAM has a power consumption mainly determined by the microprocessor and its associated control circuitry. A large system with 64K bytes of static RAM tends to have a power consumption which is almost entirely dominated by the RAM. The actual power consumed by the memory of a microprocessor system is very much a function of the particular RAM chips which make up the memory.

In general, the power consumption per bit falls as the number of bits per chip increases. The power consumption of memory chips is also a function of the access time of the chip, the faster the chip the greater the power consumption (and the price). The relationship between power, access time and size of four memory components is given below, although it should be remembered that advances in technology are constantly improving these parameters.

Memory Components	Access Time	Total Power Ave/Max	Ave Power/1K bits
TMS44-45 (4096 bits)	450nS	275/495mW	69mW
TMS15-15 (4096 bits)	150nS	440/649mW	110mW
2102 AL-2 (1024 bits)	450nS	174/275mW	174mW
2102 AL-4 (1024 bits)	250nS	225/325mW	225mW

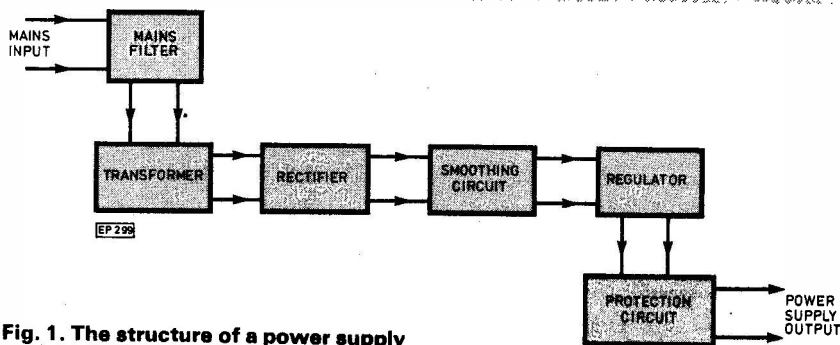


Fig. 1. The structure of a power supply

TYPICAL CIRCUIT

A power supply consisting of several circuits connected together in tandem, is illustrated in Fig. 1. The mains filter is used to keep mains borne high frequency noise and transients out of the system. The transformer performs two functions: it converts the 250V mains into a much lower voltage with very little loss of energy, and it provides a means of physically isolating the system from the mains. The rectifier and smoothing capacitor transform the alternating current from the transformer into a direct current at an approximately constant voltage. The regulator converts the approximately constant voltage into the precisely constant voltage required by the microprocessor system. The protection circuit plays a passive role, and isolates the microprocessor system in the event of a dangerous rise in the output voltage from the regulator. The protection circuit is often included in the regulator.

OPERATION

The operation of a power supply is now described and criteria for the selection of the components which make up the power supply are given.

TRANSFORMER, RECTIFIER AND SMOOTHING CIRCUIT

Three arrangements of transformer and rectifier are commonly used to provide a basic unsmoothed d.c. power supply. These are the half wave rectifier circuit, the full wave rectifier circuit with a centre-tapped transformer, and the full wave rectifier circuit with a bridge rectifier. The circuit diagrams of these three arrangements are given in Fig. 2 together with graphs of their respective outputs as functions of time. In practise the half wave rectifier circuit is almost never used (at least in microprocessor applications) because the rectifier conducts for only half a cycle, a very inefficient arrangement.

Furthermore, the half wave rectifier circuit puts a very heavy demand on the smoothing circuit, which must provide an output current to the load during the half cycle when the rectifier is not conducting.


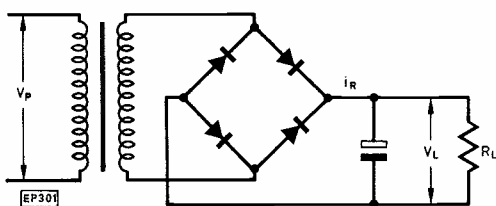


Fig. 3. The effect of a smoothing capacitor

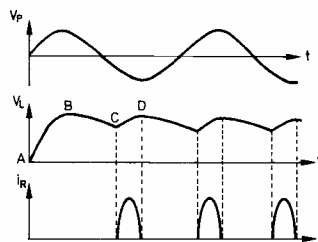

The two full wave rectifier arrangements of Fig. 2 make use of both half cycles of the mains input so that the output of the rectifier consists of a series of pulses at a repetition rate twice that of the mains frequency.

Both the centre-tapped transformer circuit and bridge rectifier circuit are widely used in power supplies. An additional advantage of these circuits over the half wave rectifier circuit is that no net d.c. component of the output current flows through the transformer, magnetising the core and increasing the power loss. The bridge rectifier configuration is most widely used for two reasons:

1. Transformers are costly components and the bridge rectifier requires only one winding with two terminals which is cheaper to manufacture.
2. The bridge circuit requires a transformer with a lower volt-ampere rating than the corresponding centre-tapped transformer circuit, and therefore makes more efficient use of the transformer.

The chief disadvantage of the bridge rectifier configuration is the need for four rectifiers. It is not only the additional cost of a bridge rectifier that causes problems, but the power dissipated by it. Unlike hi-fi

amplifiers or radio transmitters, with power supplies in the region of 60V in the former case and possibly 1000V in the latter case, a microprocessor system has a power supply of 5V. Clearly, if the voltage drop across a rectifier is approximately 1V, the power dissipated by the bridge rectifier is an appreciable fraction of the power consumed by the microprocessor system.

The pulses of current at the output of a full wave rectifier circuit must be smoothed or averaged to produce an approximately constant voltage. The process of smoothing may be thought of as that of integration or lowpass filtering.

SIMPLEST FILTER

A wide variety of smoothing or filtering circuits exist, but the simplest, and most common circuit uses a capacitor connected across the output of the rectifier circuit. Fig. 3 illustrates the effect of a

smoothing capacitor (sometimes called a reservoir capacitor), and gives a graph of the voltage across the capacitor as a function of time.

Assuming that the power is first applied at a zero-crossing, the smoothing capacitor charges up during the first half

cycle. After the peak of the cycle, point B, the voltage across the capacitor is greater than that across the transformer secondary, resulting in the rectifier becoming reverse biased and therefore non-conducting. Between points B and C the capacitor discharges exponentially into the load. At point C the transformer secondary voltage, which is now rising in the next half cycle, reaches the falling voltage across the capacitor, and the rectifier once more becomes forward biased. Current now flows through the rectifier to charge the capacitor to the next peak at D, and the process repeats itself every half cycle.

CHOOSING THE CAPACITOR

In Fig. 3 it can be seen that the rectifiers conduct for only a part of each half cycle, and that the rectifier current consists of a series of pulses. The amplitude of these pulses plays an important role in the selection of the rectifier and smoothing capacitor. Clearly, the effect of increasing the value of the smoothing capacitor is to reduce the ripple voltage superimposed on the average d.c. output of the power supply—a good thing. However, as the capacitance increases the period of conduction of the rectifiers is reduced resulting in an increase in the amplitude of the current pulses through the rectifiers—a bad thing. The amplitude of these pulses must not exceed the maximum surge rating of the rectifiers. To avoid excessive rectifier currents it is usual to limit the amount of smoothing to a peak to peak ripple voltage of 10 to 30 per cent of the mean voltage across the capacitor.

The simplest way of obtaining a value

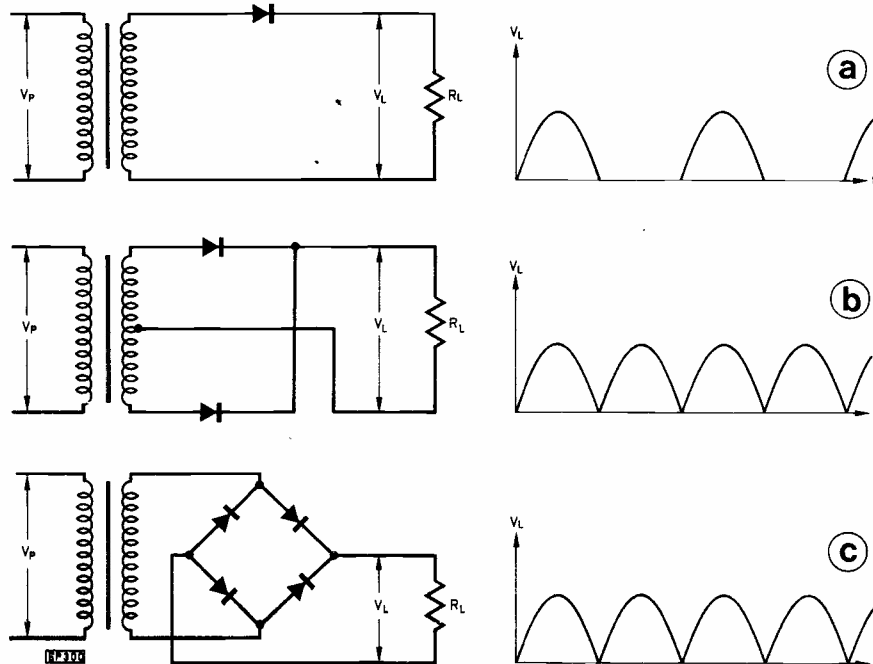


Fig. 2. Three rectifier circuits and their outputs

for the smoothing capacitor is to apply the formula $Q = CV$ to Fig. 4, a linearised version of Fig. 3.

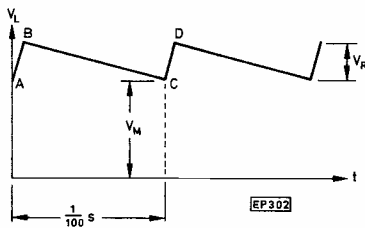


Fig. 4. A linearised representation of the voltage V_L across the load of a bridge rectifier circuit with a smoothing capacitor

$$Q = CV$$

so that $i = C \frac{dv}{dt}$

or $C = i \frac{dv}{dt}$

The value of $\frac{dv}{dt}$ is given by the slope of

BC in Fig. 4. For example, for a 50Hz power supply with a peak to peak ripple (V_R) of 5V and a mean output ($V_M + \frac{V_R}{2}$) of 20, the slope of BC is

5 volts in one hundredth of a second. If the mean load current is 5 amps, then C is given by

$$C = i \frac{dv}{dt} = 5 \frac{1}{1/100} = \frac{5}{500} = \frac{1}{100} \text{ F} = 10,000 \mu\text{F}$$

One of the most popular procedures for the design of a power supply with a reservoir capacitor connected directly to the output of the rectifier (i.e. capacitor-input filter), is based on the use of tables or graphs. Of particular interest is the relationship between the peak alternating voltage at the output of the transformer secondary and the output voltage across the smoothing capacitor, as a function of ωCR_L . Fig. 5 shows such a set of curves for a full wave rectifier circuit, from which it can be seen that the output voltage is not greatly increased when ωCR_L is greater than about 10. Other graphs presented by Schade include the relationship between the peak rectifier current and the value of the smoothing capacitor. For a full wave rectifier circuit with $\omega CR_L = 10$, the peak rectifier current is approximately seven times the average rectifier current.

SELECTING THE TRANSFORMER

In many manufacturers' catalogues four parameters are used to characterise transformers: the primary r.m.s. voltage, the secondary r.m.s. voltage, the volt-ampere (VA) rating, and the regulation. The maximum voltage across the smoothing capacitor under no load conditions is given by:

$$V_C = V_S \times 1.41$$

where V_S is the r.m.s. secondary voltage of the transformer. From Fig. 5 it can be seen that this value of V_C can, in practise, be approached only when ωCR_L is greater than 100 and the effective series resistance is less than $\frac{1}{2}$ per cent of the load resistance.

The largest mean direct current which can be drawn by the load in a bridge rectifier circuit is given by:

$$I_L = I_{a.c.} \times 0.62 = \frac{VA}{V_S} \times 0.62$$

where VA is the volt-ampere rating of the secondary.

SELECTING THE RECTIFIER

The most popular form of rectifier is the relatively inexpensive silicon junction diode. Bridge rectifiers, containing four silicon diodes mounted in epoxy plastic, can readily be obtained and are widely found in full wave rectifier circuits. Rectifiers are usually characterised by four parameters: the peak inverse voltage, the average forward current, the maximum forward current, and the voltage drop across the rectifier when it is conducting.

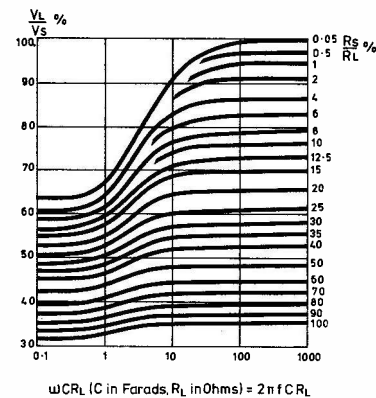



Fig. 5. The relationship between V_p and V_L in a bridge rectifier circuit with a capacitor-input filter

The maximum peak inverse voltage of a rectifier is the largest voltage that can safely be applied across the rectifier when it is reverse biased. In a half wave rectifier circuit the maximum voltage across the rectifier occurs at the peak of the half cycle when it is non-conducting. The total voltage across the rectifier is the transformer secondary voltage plus the voltage across the capacitor, i.e. $2 \times V_C = 2 \times 1.41 \times V_S$, or nearly three times the r.m.s. rating of the transformer secondary. In a bridge rectifier circuit two diodes are connected in series so it might be thought that the p.i.v. rating of each diode need be only half that of the equivalent half wave rectifier circuit, i.e. $1.41 \times V_S$. Unfortunately, when the diodes are reverse biased, their series resistance is indeterminate and there is no guarantee that the

voltage will be distributed equally across the diodes. Hence both diodes in series in a bridge rectifier should have p.i.v.'s three times the value of V_S , or p.i.v.'s $1\frac{1}{2}$ times V_S only if voltage equalising resistors are connected in parallel with them.

The maximum current which flows through the rectifiers is governed by the value of the smoothing capacitor. In a bridge rectifier circuit the maximum rectifier current is approximately seven times the average forward current at $\omega CR_L = 10$, and twenty times the average forward current at $\omega CR_L = 100$ ($\frac{R_S}{R_L} = 0.02\%$).

When a rectifier is forward biased there is a voltage drop between its anode and cathode, consisting of the voltage drop across the rectifying junction plus a voltage drop due to the ohmic resistance of the rectifier. A typical voltage drop across a bridge rectifier, at 10A, is 1.88V. The forward voltage drop across silicon diodes is of little importance in high voltage power supplies, but in low voltage power supplies, producing the high currents required by large memories, the forward voltage drop is an appreciable fraction of the voltage across the

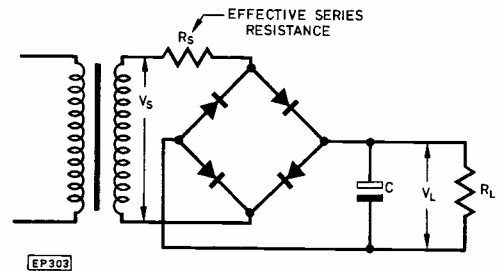

smoothing capacitor. Conventional silicon junction diodes lower the rectification efficiency of the circuit and waste a large amount of power. Possible alternatives to silicon junction diodes are Schottky diodes with their lower forward voltage drop, or synchronous rectifiers using transistors which have a collector-emitter saturation voltage of approximately 0.3V.

SELECTING THE CAPACITOR

The choice of an electrolytic capacitor in a filter circuit is determined by three parameters: the capacitance, the maximum applied voltage, and the maximum ripple current. The capacitance may be calculated as described earlier in this article, and the voltage rating of the capacitor must be greater than the peak

secondary voltage plus an amount large enough to allow for increases in the primary voltage due to line overloads. Capacitors also have a maximum surge voltage rating which is the maximum instantaneous voltage which may be applied across the capacitor. Unfortunately the surge voltage of an electrolytic capacitor is often not appreciably greater than the maximum working voltage.

The ripple rating of the smoothing capacitor is very important, but is sometimes neglected by inexperienced designers. As we have seen, the voltage across the smoothing capacitor is composed of a constant voltage plus a ripple component. The ripple voltage causes a current, the ripple current, to flow through the capacitor. If we assume that the ripple voltage is approximately sinusoidal, the ripple current is given by:

$$I_{\text{ripple}} = \frac{V_r}{2\sqrt{2}} \times \frac{1}{X_C} = \frac{V_r}{2\sqrt{2}} \times \frac{2\pi f C}{1} \\ = 222 V_r C$$

In the above example, $V_r = 5$ and $C = 0.01F$, so that $I_{\text{ripple}} = 11.1A$. Failure to choose a capacitor with an adequate ripple current rating leads to high internal temperatures and a reduced capacitor life. Note that the maximum ripple current rating of a capacitor is temperature dependent.

THE REGULATOR

The smoothed voltage across the reservoir capacitor is far from the constant voltage required by most digital integrated circuits, i.e. $5V \pm 5\%$. In order to create a true constant voltage source an electronic regulator must be used. Electronic regulators can have very complex circuits, and several books have been written on the subject of their design. Fortunately, the designer of a small to medium size microprocessor system has been freed of the relatively complex task of designing his own regulator by the availability of monolithic regulators. Monolithic regulators are high performance integrated circuits which provide a constant voltage output from an unregulated input. Their advantage is twofold: they are very cheap; and they are easy to use, having only three terminals. Table 1 gives the parameters of four monolithic regulators, each of which has a 5V output, and Fig. 6 shows how a regulator is used. Note that most monolithic regulators have internal protection circuitry which saves the regulator from the effects of short circuiting their output. Some regulators (e.g. 78H05) also include protection against thermal overload—the device is shut down when the junction temperature rises above a predetermined limit.

Monolithic regulators suffer from two

Characteristic	7805	L005	LM309K	LM323K	78H05K
Output current	1A	600mA	1.2A	3A	5A
Input voltage range	7-25V	7.5-20V	7-35V	7.5-20V	8-25V
Load regulation	0.2%	0.3%	1%	0.3%	10mV
Ripple rejection	70dB	62dB	70dB	58dB	60dB
Output resistance	30mΩ	15mΩ	50mΩ	—	2mΩ
Line regulation	0.2%	0.1%	0.1%	0.1%	10mV
Output noise voltage	0.04mV	0.07mV	0.04mV	0.04mV	0.04mV
Short Circuit current	750mA	190mA	—	—	7A
Case	Plastic	T03	T03	T03	T03

important disadvantages. They are sometimes prone to instability and may oscillate in the megahertz region, superimposing a high frequency waveform with an amplitude of several volts on the 5V output. Such oscillations are normally prevented by connecting two capacitors between the regulator input and ground, and between the regulator output and ground, as shown in Fig. 6. These capacitors should be located as close as possible to the pins of the regulator. It may seem strange that a $0.22\mu F$ capacitor is used to bypass a smoothing capacitor of $10,000\mu F$, but the reactance of an electrolytic capacitor rises rapidly above 10kHz. The effect of this is to prevent the capacitor from bypassing high frequency noise.

A second limitation of the monolithic

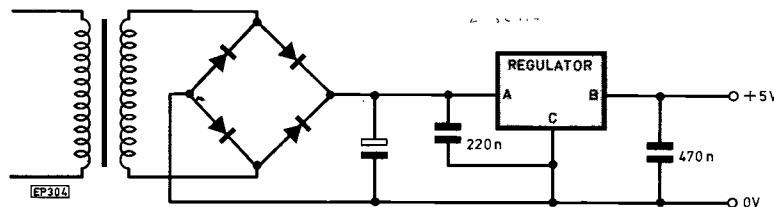


Fig. 6. A stabilised power supply using a monolithic voltage regulator

regulator is its inability to pass really large currents (above 10 amps). This forces the designer to seek one of two alternatives, to design a regulator circuit with discrete high power transistors, or to distribute the unregulated power supply to each module in the microprocessor system and use on-board regulators to provide a local stabilised 5V supply. It is difficult to choose between these alternatives because both have their advantages and disadvantages. The SS50 bus and the S100 bus both have a power supply rail carrying an unregulated (approximately 8V) power supply plus on-board regulation on all memory, CPU, and peripheral cards.

The principal advantages of a multi-regulator power supply are:

1. Simple, inexpensive, one-amp regulators may be used instead of a complex and, possibly expensive, high current regulator.
2. A very low impedance power supply bus need not be used to distribute the stabilised power between individual cards—this can greatly

simplify the design of the system and save money.

3. The regulators provide additional isolation between the various modules.
4. The failure of a single monolithic regulator will not damage more than one module.

The principal disadvantages of a multi-regulator power supply are:

1. The power dissipation of the regulators is put on the modules where it is least wanted. On some large memory boards using the older 1K chips, up to four one-amp regulators are required considerably increasing the waste heat generated by the board. When a single regulator is employed it is normally located in an enclosure,

away from the more delicate modules.

2. Although the use of several regulators reduces the total damage done if a regulator fails—the chance of a failure is increased because there are more regulators to fail.
3. Regulators with their associated bypass capacitors and heat sinks take up valuable space on the cards where they are located. Furthermore, they often limit the minimum spacing between adjacent cards.

POWER SUPPLY PROTECTION

An ideal power supply and the a.c. mains to which it is connected should have the following characteristics:

1. The mains supply is a perfectly sinusoidal voltage of constant amplitude and frequency.
2. The mains has always been connected to the power supply, and always will be connected to it. That is, the

power is never turned on or off, thus avoiding switching transients.

- The components which make up the power supply are perfect: they never age (i.e. change their properties) or fail.

Unfortunately the above situation does not exist. Because the mains supply has a non-zero impedance (typically $0.4 + 0.25j$ ohms at 50Hz), the waveform at the power supply transformer primary contains components due to the effects of other loads connected to the mains. Common sources of mains-borne interference are:

- Switched inductive loads—motors, solenoids, relays etc.
- Lightning strikes to, or near, the power distribution networks.
- Alternating-current switching circuits—e.g. SCR phase control circuits.
- Energising or de-energising transformer primaries.

It is not uncommon for transients of the order of 1000V to be superimposed on the mains supply, although most transients have an amplitude of less than 200V and a duration of tens of microseconds. Transients usually have the form of an exponentially damped sine wave with a very rapid rise time. Why are the designers of power supplies so concerned about transients? A transient can, occasionally, have enough energy to destroy components inside the power supply or within the microprocessor system itself. More commonly, a transient may be large enough to affect a logic level on the system bus, causing a logical one to be interpreted as a logical zero by some device (or vice versa). This can cause a program to crash—especially if an address is corrupted and a random jump executed.

TECHNIQUES USED

A common technique of removing some of the effects of mains borne interference involves the insertion of filter networks between the mains and the power supply. A typical commercially available filter has an attenuation of 35dB between 150kHz and 30MHz, and its circuit diagram is given in Fig. 7

Another type of transient suppressor is the zinc oxide voltage dependent resistor (VDR) which has a highly non-linear voltage-current characteristic. The V/I curve of a typical zinc oxide VDR is given in Fig. 8. A power supply is protected from mains borne transients by connecting the VDR across the mains terminals at the input to the power supply. When a transient appears across it, its resistance falls, causing a current to flow through. In this way a large fraction of the energy of the transient is dissipated within the body. A ten fold increase in the

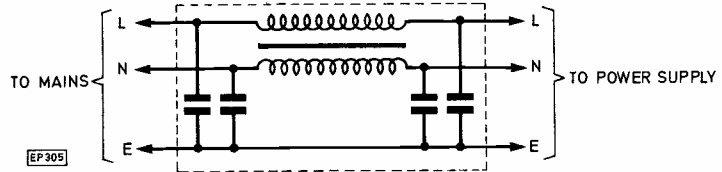


Fig. 7. The circuit diagram of a mains filter

current through it corresponds to an approximately 8% increase in the voltage across it.

LOAD PROTECTION

In addition to protecting the power supply from mains borne transients it is usual to provide protection against excessive load current and load voltages. To protect the power supply from excessive load currents, a current sensor must detect an overload condition and then take action to stop any further increase in output current. This is done in one of two ways, by holding the output current constant, or by fold-back current limiting, which reduces the current to a very low value until the cause of the overload is removed. As many microprocessor systems use monolithic regulators, the power supply designer must choose the regulator with the type of current limiting best suited to his application.

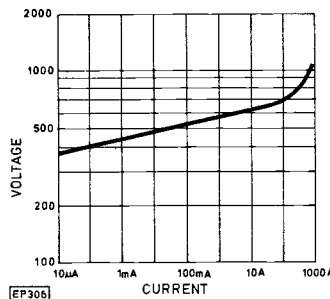


Fig. 8. Typical V/I characteristics of a zinc oxide VDR for use with a mains supply

It is advisable to add over-voltage protection to the output of a power supply. A widely used method of over voltage protection is the crowbar circuit. The crowbar circuit is so named because of its 'brute force and ignorance' technique of putting an almost dead-short across the power supply terminals in the event of an overload. The effect of the short circuit switches off the drive to the regulator either by means of a resettable electronic switch or by a simple fuse.

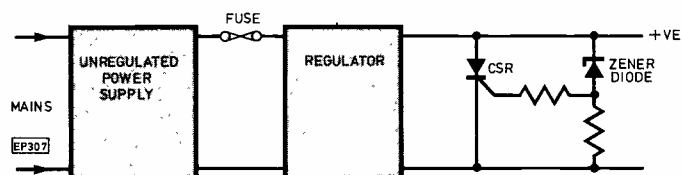


Fig. 9. A simple crowbar overvoltage protection circuit

The circuit diagram of a crowbar circuit is given in Fig. 9. The silicon controlled rectifier (SCR) placed across the output terminals of the power supply, is normally in the non-conducting state. When a positive going pulse appears at its gate the SCR conducts and remains conducting until it is reset by turning off the power supply. The gate voltage required to turn on the SCR is provided by sampling the power supply output with a zener diode which is non-conducting until the reverse bias voltage across its anode-cathode terminals reaches its zener point. The crowbar circuit does not always give complete protection of the circuit because the SCR takes about a microsecond to turn on, and there is a further delay of several microseconds in the zener diode trigger circuit. During this delay it is still possible for a large over-voltage transient to cause some damage to MOS and TTL devices.

TRANZORBS


The zinc oxide voltage dependent resistor is usually used to suppress high voltage transients at the mains input. General Semiconductor Industries produce a device called the Tranzorb, which is able to suppress transients on low voltage lines. A tranzorb is a silicon *pn* avalanche device designed to suppress transients above a predetermined level, at which the *pn* junction breaks down (reversibly) and conducts—in other words a tranzorb is a special type of Zener diode. Tranzorbs have relatively low breakdown voltages and are designed to protect the outputs of power supplies, or even the MOS and bipolar TTL circuits themselves. Normally they are simply connected across the output of a power supply.

Next Month: A power supply for a small microprocessor system is described with design calculations.

STEVENSON

Electronic Components

SPRING SPECIALS

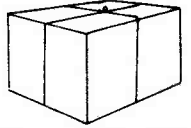

- Set of 4 AA (HP7) Rechargeable Cells . . . 500p 450p
- PP3 Rechargeable cell . . . 450p 410p
- Pack of 10 miniature slide switches . . . 150p 120p
- Pack of 10 push to make switches . . . 150p 120p
- Pack of 10 push to break switches . . . 200p 150p
- Murata Ultrasonic Transducers, per pair . . . 350p 300p
- Resistor Development packs.
 - 10 off, each value from 4.7 ohm to 1M $\frac{1}{2}w$ 570p 500p
 - $\frac{1}{2}w$ 750p 650p
- Polyester Development packs.
 - 5 off, each value from 0.01 to 3u2 . . . 620p 520p
- Preset Potentiometer pack
 - 5 off, each value 100 ohm to 1M, 65 presets 395p 305p
- Ceramic Development pack
 - 10 off, each value 22pF to 0.1uF, 310 caps. 595p 525p
- LED pack, 10 off,
 - each type 0.2 Red, green, yellow . . . 350p 300p
- Pack of 10 CA3080 Transconductance amps. 700p 620p
- Pack of 10 LM301AN Op. amp. . . . 260p 230p
- Pack of 10 LM380N 2W Audio Amp . . . 750p 620p
- LM380 + LM381 and data . . . 235p 180p
- Pack of 3 LM3909 LED flasher . . . 185p 150p
- Pack of 10 TL081 Jfet Op. amp. . . . 450p 320p
- MM57160 Stac. Timer + data . . . 600p 550p
- SN76477 Sound generator + data . . . 240p 200p
- Pack of 2 ZN414 AM chips . . . 160p 130p
- SS-2 Breadboard . . . 1085p 990p
- Expo Reliant Drill . . . 665p 570p
- Expo Titan Drill . . . 1030p 920p
- Drill stand for above . . . 1200p 1100p
- Pack of 8 2708 Eprom . . . 4720p 4500p
- Pack of 8 2114 Ram LP 300ns . . . 3125p 3000p
- Pack of 8 4116 . . . 4660p 4300p

CMOS

4001	20p	4025	20p	4070	20p
4002	20p	4027	45p	4071	20p
4007	20p	4028	85p	4072	20p
4009	40p	4029	85p	4081	20p
4011	20p	4040	110p	4093	50p
4012	20p	4041	85p	4510	80p
4013	35p	4042	80p	4511	90p
4015	80p	4043	95p	4518	80p
4016	30p	4046	110p	4520	80p
4017	65p	4049	45p	4527	90p
4018	90p	4050	45p	4528	90p

LINEAR

THIS IS ONLY A SELECTION!

LM308	60p	NE531	98p
LM324	45p	NE555	23p
LM339	45p	NE566	60p
LM348	90p	NE567	100p
LM377	170p	RC4136	100p
LM378	230p	SN76477	230p
LM380	75p	TBA800	70p
LM381	150p	TBA810S	100p
LM382	120p	TBA1022	620p
LM3900	50p	TL081	45p
LM1458	35p	TL084	125p
LM3909	65p	ZN414	80p
LM3911	100p	ZN425E	390p
MM57160	590p	ZN1034E	200p

MICRO

MEMORIES	21L02	85p	2516	2185p
CPU'S	2112	175p	2716	2185p
6800	550p	2114	390p	AYS-1013
8080A	390p	4116	570p	
Z80	950p	2708	590p	

TRANSISTORS

AC127	17p	BC548	10p	ZTX107	14p
AC128	16p	BCY71	14p	ZTX108	14p
AC176	18p	BD131	35p	ZTX300	16p
AD161	38p	BD132	35p	ZTX500	16p
AD162	38p	BD139	35p	2N3053	18p
BC107	8p	BD140	35p	2N3055	50p
BC108	8p	BFY50	15p	2N3442	135p
BC108C	10p	BFY51	15p	2N3702	8p
BC109	8p	BFY52	15p	2N3704	8p
BC109C	10p	MJ2955	98p	2N3706	9p
BC147	7p	MPSA06	20p	2N3819	15p
BC148	7p	MPSA56	20p	2N3905	8p
BC177	14p	TIP29C	60p	2N3906	8p
BC178	14p	TIP30C	70p	2N5459	32p
BC182	10p	TIP31C	65p	2N5777	30p
BC182L	10p				
BC184	10p	1N914	3p	1N4006	6p
BC184L	10p	1N4148	2p	1N5401	13p
BC212	10p	1N4002	4p	BZY88ser.	8p
BC212L	10p	ITT product			
BC214L	10p	1N4148	-	£1.40/100.	

TTL

7400	10p	7474	22p	74145	55p
7402	10p	7475	25p	74148	90p
7404	12p	7476	20p	74150	55p
7408	12p	7486	20p	74157	40p
7410	10p	7490	25p	74164	55p
7413	22p	7493	25p	74174	55p
7414	39p	7496	45p	74177	50p
7420	12p	74121	25p	74190	50p
7430	12p	74123	38p	74191	50p
7432	18p	74125	35p	74192	50p
7442	38p	74126	35p	74193	50p
7447	45p	74132	45p	74196	50p
7448	50p	74141	55p	74197	50p

FULL DETAILS IN CATALOGUE!

CAPACITORS

POLYSTYRENE

High quality foil type. 63V working, 5% tol.

22pf to 1000pf	.6p each
1500pf to 0.01uF	.8p each

TANTALUM BEAD

0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1 & 2.2uF @ 35V 8p

4.7, 6.8, 10uF @ 25V 13p

22 @ 16V, 47 @ 6V, 100 @ 3V 16p

OPTO

LED's	0.125in.	0.2in	each	100+
Red	TIL209	TIL220	9p	7.5p
Green	TIL211	TIL221	13p	12p
Yellow	TIL213	TIL223	13p	12p
Clips	3p	3p		

DISPLAYS

DL704	0.3 in CC	130p	120p
DL707	0.3 in CA	130p	120p
FND500	0.5 in CC	100p	80p

MYLAR FILM

0.001, 0.01, 0.022, 0.033, 0.047 3p

0.068, 0.1 4p

POLYESTER

Mullard C280 series

0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1. 5p

0.15, 0.22 7p

0.33, 0.47 10p

0.68 14p

1.0uF 17p

CERAMIC

Plate type 50V. Available in E12 series from 22pF to 1000pF and E6 series from 1500pF to 0.047uF 2p

SKTS

Low profile by Texas

8pin	8p	18pin	14p	24pin	18p
14pin	10p	20pin	16p	28pin	22p
16pin	11p	22pin	17p	40pin	32p

3 lead T018 or T05 socket. 10p each

Soldercon pins: 100-50p 1000-370p

MINIATURE TRIMMERS

Miniature film type, in 1.4pF - 5pF, 2pF - 22pF, 2pF - 22pF, 2pF - 10pF, 5.5pF - 65pF. 18p each

RADIAL LEAD ELECTROLYTIC

63V	0.47	1.0	2.2	4.7	10	5p
						7p
						13p
						20p
						5p
						8p
						10p
						15p
						23p

PCBS

VEROBOARD

Size in.	0.1in.	0.15in.	Vero	Cutter	80p.
2.5 x 1	14p				
2.5 x 3.75	45p	45p			
2.5 x 5	54p	54p			
3.75 x 5	64p	64p			
3.75 x 17	205p	185p			

Single sided pins per 100 40p 40p

Top quality fibre glass copper board. Single sided. Size 203 x 95mm. 60p each.

'Dalo' pins 75p each.

Five mixed sheets of Alfac. 145p per pack.

CONNECTORS

JACK PLUGS AND SOCKETS

2.5mm	unscreened	9p	13p	7p
3.5mm	9p	14p	8p	
Standard	16p	30p	15p	
Stereo	23p	36p	18p	

DIN PLUGS AND SOCKETS

2pin	7p	7p	7p
3pin	11p	9p	14p
5pin 180°	11p	10p	14p
5pin 240°	13p	10p	16p

1mm PLUGS AND SOCKETS

Suitable for low voltage circuits. Red & black. Plugs: 6p each Sockets: 7p each.

4mm PLUGS AND SOCKETS

Available in blue, black, green, brown, red, white and yellow. Plugs: 11p each Sockets: 12p each

PHONO PLUGS AND SOCKETS

Insulated plug in red or black 9p

Screened plug 13p

Single socket 7p Double socket 10p

RESISTORS

Carbon film resistors. High stability, low noise 5%

E12 series. 4.7 ohms to 10M. Any mix:

0.25W	each	100+	1000+
1p	0.9p	0.8p	
0.5W	1.5p	1.2p	1p

Special development packs consisting of 10 of each value from 4.7 ohms to 1 Meg-ohm (650 res) 0.5W £7.50. 0.25W £5.70.

METAL FILM RESISTORS

Very high stability. Low noise rated at $\frac{1}{2}w$ 1%. Available from 51 ohms to 330k in E24 series. Any mix.

0.25W	each	100+	1000+
4p	3.5	3.2	

POTENTIOMETERS

Preset vertical or horizontal 100ohms - 1M 6p

Rotary 5K-2M2 Log or Lin single 28p

Rotary 5K-2M2 Log or Lin double 80p

Slide 60mm travel 5K-500K Log or Lin, single 60p

Suitable knobs for above with coloured caps in red, blue, green, grey, yellow and black. Rotary controls 14p each. Slide type 12p each.

SWITCHES

- #### TOGGLE
- Subminiature toggle. Rated at 2A. SPST 52p. SPDT 62p. DPDT 69p.
- Standard type. Rated at 1.5A. SPST 34p. DPDT 48p.
-
- #### SLIDE
- | | | |
|-----------|------|-----------|
| Miniature | DPDT | 15p each. |
| Standard | DPDT | 15p each. |
-
- #### ROTARY
- Available in 4 pole 3 way, 3 pole 4 way, 2 pole 6 way, 1 pole 12 way 43p each
- Key operated switch 380p each
- Miniature push to make 15p each
- Miniature push to break 20p each
- Rockers rated at 10A. SPST 32p each SPDT 42p each.

We now offer one of the widest ranges of components at the most competitive prices in the U.K. See catalogue for full details. We welcome callers at our shop in College Rd, Bromley, from Mon-Sat, 9am-6pm (8pm on Weds and Fridays). Special offers always available. We also provide an express telephone order service. Orders received before 5pm are shipped same day. Contact our sales office now with your requirements. TEL: 01-464 2951/5770.

Quantity discounts on any mix TTL, CMOS, 74LS and Linear circuits: 100+ 10%, 1000+ 15%. Prices VAT inclusive. Please add 50p for P & P. no charge for orders over £15. Official orders welcome. All prices valid to April 1980.



BARCLAYCARD & ACCESS WELCOME

Mail orders to: STEVENSON (Dept PE)

76 College Road, Bromley, Kent BR1 1DE.

MICRO-BUS

Compiled by DJD.

Appearing every two months, Micro-Bus will present ideas, applications, and programs for the most popular microprocessors; ones that you are unlikely to find in the manufacturers' data books. The most original ideas will probably come from readers working on their own microcomputer systems, and payment will be made for any contribution featured here. This is also the place to air your views, in general, on this new technology, so let's be hearing from you!

THE main topic in this month's Micro-Bus is a design for an extremely simple SC/MP-based microprocessor system which, while using a minimum of components, makes it possible to run and debug programs. Also included are designs for a hex keyboard and a two-digit hex display which can be added to the system.

NINE PROBLEMS

But first, here are nine light-hearted problems each to do with some aspect of programming micros, and gathered from a variety of sources. Solutions to all the problems will be presented in the next Micro-Bus.

One. National Semiconductor has just developed a micro with four registers, labelled A, B, C and D, and an instruction set consisting of the following five instructions (where X and Y stand for any of the four registers, and L represents a label):

LD X, Y Load X with the value in Y
DEC X Subtract 1 from the value in X
JZ L Jump to L if result of previous
DEC was zero
JNZ L Jump to L if result of previous
DEC was non-zero
DIS X Display value of X

Write a program for this rudimentary microprocessor, using as few instructions as possible, to display the highest prime factor of a number in the A register. For example, for 91 it should give the result 13, and for 19 the result 1.

When you have reached a solution you are advised to translate it into BASIC, or the machine code of a more reasonable micro, and run it to check that it really does work.

Two. The following problem has no possible practical application, but it should nevertheless cause some head-scratching among SC/MP programmers:

On SC/MP the obvious way to load zero into the accumulator is by executing 'LDI O' (C4 00). Without making any assumptions about the contents of any of the registers, can you find four other ways of clearing the accumulator in just two bytes?

Three. It is very easy, in BASIC, to print the larger of two numbers by using an 'IF' statement and a 'GOTO', but how can it be done in

a single statement, and without using 'IF'? In other words we want the equivalent of:

```
PRINT MAX (A, B)
```

without, of course, using the functions MAX or MIN.

Four. For a certain application using a 6800 system the programmer needed to reverse the order of bits in a byte in less than 10 cycles. One attempt is shown in Fig. 1; this routine shifts bits from A to B via the carry bit, and in the process sets B to the reverse of A as required. Unfortunately the routine takes 99 cycles to execute, and at this point the programmer gave up!

```
0000 CE 0008 REVERS LDX EB
0003 44 LOOP LSR A
0004 59 ROL B
0005 09 DEX
0006 26 FB BNE LOOP
```

Fig. 1. Program for the 6800 to reverse the order of bits in the accumulator; see problem 4.

In fact the problem can be solved, although the approach is somewhat unconventional, and the solution can be extended to more general applications.

Five. There are three things that you might want to do to the carry bit of a micro, namely set it, clear it, or complement it. The Z80 provides instructions to set it (SCF) and complement it (CCF), and clearing it is no problem: you must do SCF, CCF. On the other hand the SC/MP, 6502, and 6800 micros provide the clear carry and set carry instructions, and leave you to work out how to complement the carry. Without affecting the contents of the other registers, what is the shortest way to complement the carry bit on these three micros?

Six. A very pleasing feature of the high-level language Pascal is the 'CASE' statement, illustrated by the example in Fig. 2 (a) which prints one of three values, A, B or C.

```
'CASE' N 'OF'
1: WRITE (A);
2: WRITE (B);
3: WRITE (C)
'END'
10 IF N = 1 THEN PRINT A
20 IF N = 2 THEN PRINT B
30 IF N = 3 THEN PRINT C
```

Fig. 2. Two programs which print one of three values depending on the value of N, written in (a) Pascal, or (b) BASIC.

depending on whether N is equal to 1, 2 or 3 respectively. To do the same in BASIC one might use three 'IF' statements, as shown in Fig. 2 (b). Can the same effect be achieved with a single BASIC statement, and if so, how?

Seven. The effect of the SC/MP instructions 'LDI O, CAI O' is to set the accumulator to X'FF if the carry bit is clear, and to X'00 if the carry bit is set. How, without making any assumptions about the contents of any of the registers, can the same be achieved in half the number of bytes?

Eight. The 6800 micro provides two types of instructions to shift the accumulator right; a logical shift right (LSR A) which shifts a zero into the top bit of the accumulator, and an arithmetic shift right (ASR A) which preserves the sign bit, for working with signed twos-complement binary numbers. Unfortunately the 6502 micro only provides us with an LSR A instruction; what is the shortest way of implementing an ASR A using the existing 6502 instructions?

Nine. Finally, a problem for all 6800 owners who wish they had a 6809. One of the great improvements of the 6809 over its predecessor is that its instruction set makes it easy to write relocatable programs. If you did not realise that it is difficult to write relocatable programs on the 6800, try finding a set of instructions with the same effect as:

```
HERE LDX £HERE
```

but which will work correctly wherever they are loaded into memory.

LOW-COST SC/MP SYSTEM

The following SC/MP system can be built with a small number of readily available components, and it works without the need for a monitor ROM or EPROM of any kind. It was designed by Andrew Aitken who submitted the following details about its operation.

"The full circuit, shown in Fig. 3, includes a single-cycle facility comprising a flip-flop and a few gates. The system has 256 bytes of RAM, at addresses 0000 to 00FF, and the states of the address and data lines are shown on 18 l.e.d.s. The whole circuit needs a 5 volt supply of about 1/2 amp, and two or three 0.1µF capacitors should be added across the power rails at various points for decoupling.

PROGRAMMING

"Programs and data are entered into the memory as follows: With S1 set to 'PROGRAM' and S4 set to 'SINGLE CYCLE' press 'RESET'. The MPU will then be halted while it is fetching the first word from memory, and NRDS will be low thus enabling the data buffer. Whatever is now set on the data switches will be present on the data bus, and will be read by the MPU. Set the data switches to C4 (the op-code for the Load Immediate instruction) and switch the 'CYCLE' switch S2 up and then down. The instruction is then executed, and the MPU will again set NRDS low, waiting for the data which forms the second byte of the instruction. This is likewise entered at the data switches, and the

programs in any sequence, and to change the contents of any location at will. When the program has been entered set S1 to 'RUN', leave S4 on 'SINGLE CYCLE', 'RESET', and cycle through the program by toggling S2. If everything seems fine 'RESET', set S4 to 'CONTINUOUS', toggle S2 once, and the program will run. A particularly pleasing aspect of the system is the ability to stop a program in mid run, by setting S4 back to 'SINGLE CYCLE', change an instruction, and then allow the program to continue so as to see the effect of the change immediately.

"S1 is a double-pole switch to ensure that when the system is in 'RUN' mode the data switches are disconnected from the data bus. Alternatively the data buffer EN line could be

corresponding to that key is presented to the inputs of the CMOS inverters by a diode matrix. The outputs of these inverters are connected to the inputs of both of the 4-bit latches. The CMOS inverters were used as buffers because the key switches could only tolerate small currents. If more robust switches are available it would be possible to connect the outputs of the diode matrix directly to the latch inputs; in this case the 12k resistors should be changed to 1k and the data should be taken from the Q outputs of the latches.

"A key-press is detected by a diode gate which charges up a 4.7μF capacitor. This causes the output of the second Schmitt trigger to go high, which clocks the flip-flop

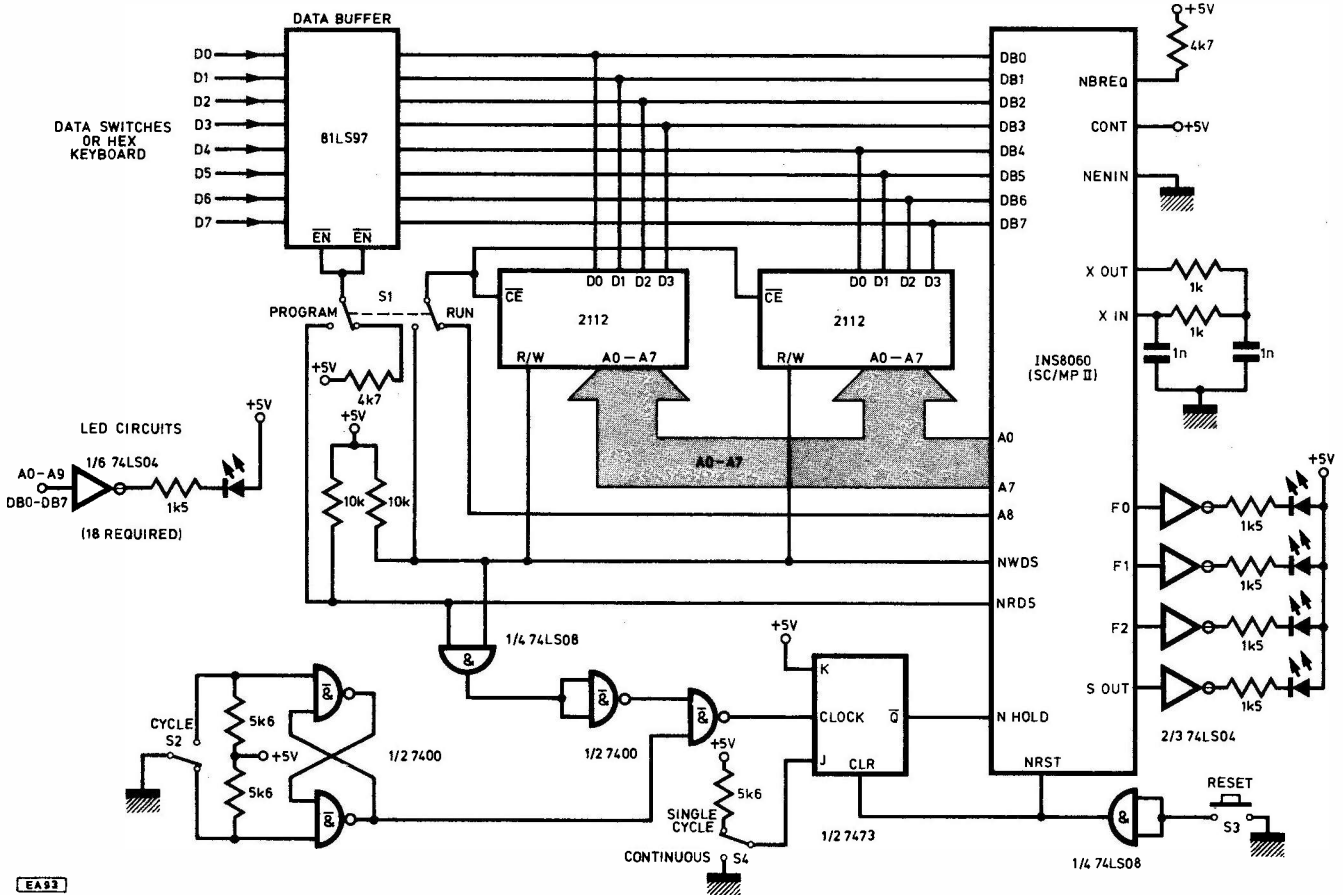


Fig. 3. Complete circuit of the simple SC/MP microprocessor system.

MPU will load this data into the accumulator.

"Now enter C9 (Store relative to pointer register P1) followed by the required memory address. Pointer P1 was set to zero on reset, so on the next cycle the MPU will store the contents of the accumulator, the required data, at this address. When the MPU writes to memory NWDS goes low which will enable the RAM.

For example, to enter 8F at location 0002 the full sequence is:

RESET, C4, CYCLE, 8F, CYCLE, C9, CYCLE, 02, CYCLE.

"The sequence is repeated to enter data at a different address and although the sequence looks quite long, in practice programs can be loaded into RAM fairly easily. The beauty of the system is that it is possible to enter

connected to an inverted address line so that the data switches could be read from a program.

HEX KEYBOARD

"Although data for the SC/MP system can be entered by means of eight toggle switches at the input of the data buffer, a far more convenient method is to use the hex keyboard circuit shown in Fig. 4. The keyboard is based on a circuit in the *September 1978 PE* and would be useful in any application requiring hex data entry.

CIRCUIT OPERATION

"The keyboard circuit buffers two hex key-presses to give an 8-bit value at the output. When a key is pressed the binary code

and triggers the monostable. The flip-flop steers the pulse from the monostable to enable the appropriate latch, and this latches the key's value.

"When the key is released the 4.7μF capacitor will discharge through the 1k resistor, and the output of the second Schmitt trigger will return low. The capacitor thus serves to debounce the keys both when they are pressed and when they are released. The next key-press will load data into the other latch, and the pulse from the monostable will be available on the strobe line to signal that a full 8-bit word is ready at the outputs of the latches. When loading a program this strobe line is not required, but it can be tied to SC/MP's Sense-B input so that programs can detect when data has been entered.

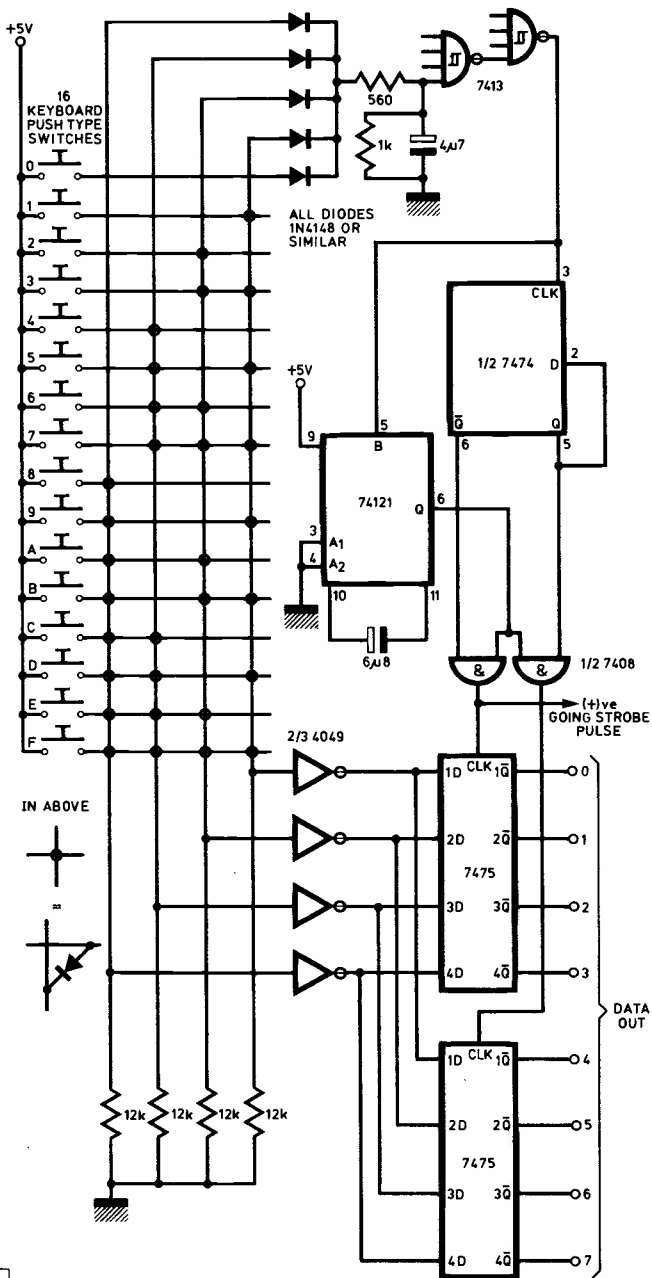


Fig. 4. Hex keyboard circuit which can be added to the SC/MP system to make data entry easier.

TWO-DIGIT HEX DISPLAY

"A two-digit hex display of the output from the keyboard is another useful addition to the system. The circuit of Fig. 5 achieves this with few parts, and without the need for an expensive decoder chip. The l.e.d. display is a small common-cathode multiplexed type.

"The four NAND gates form an oscillator that drives the cathodes of the displays in turn. One output of the oscillator is also taken to the select input of a 74157 quad two-input data selector which routes the appropriate 4-bit nibble from the data bus to the decoding circuitry. The 74154 decoder pulls one of its 16 outputs low depending on the code at its inputs. Each output is connected to certain segments of the displays by diodes; when the output is pulled low these segments are turned off

to produce the required hex character on the display. Turning segments off is simpler than turning segments on, and results in a considerable saving in the number of diodes required. The 2k7 pull-up resistors may be reduced to 1k5 if the display is not considered bright enough.

"The oscillator thus switches the segment codes for each nibble to each display digit in turn, at high speed, giving a two-digit hex display of the data bus."

I/O PORT TESTER

The Acorn 6502-based computer provides two 8-bit I/O ports, and when these are being interfaced to external circuitry it often becomes difficult to keep track of the logic levels on the 16 lines. In such cases the routine

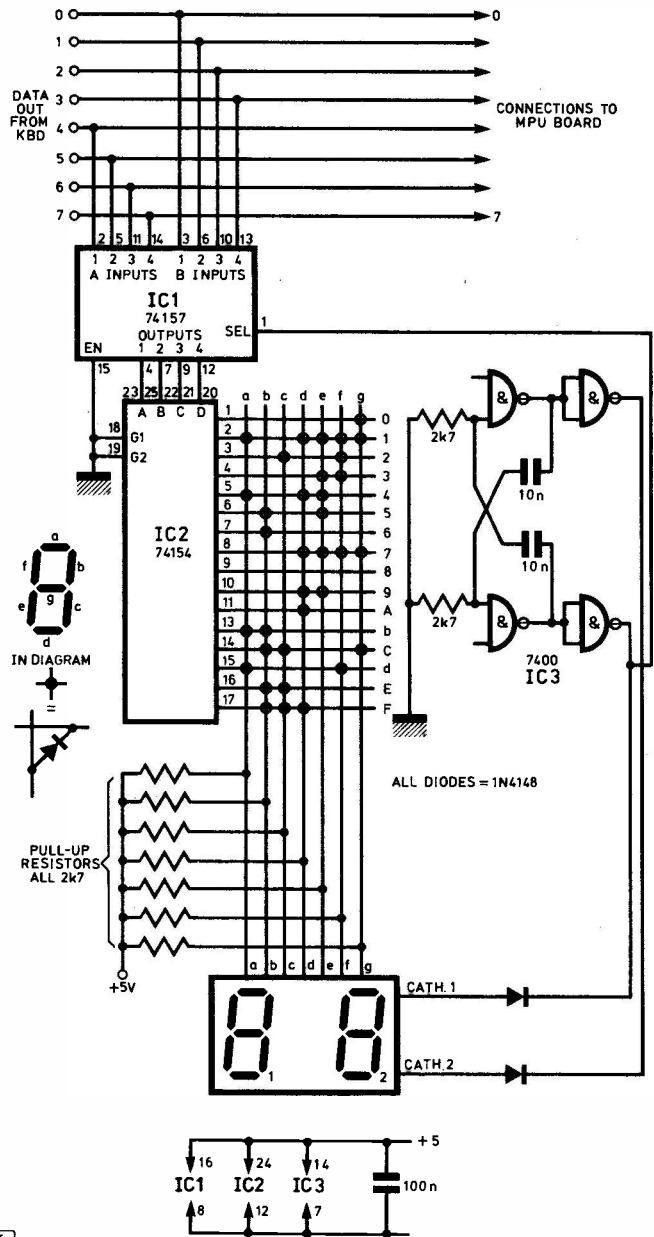


Fig. 5. Circuit which will display the output from the keyboard as two hexadecimal digits.

of Fig. 6 should prove useful; it gives a continuous display of the states of the ports, in binary, as two rows of 8 dashes on the l.e.d. displays. The top row corresponds to the 8 bits of port A and the bottom row corresponds to the 8 bits of port B. The leftmost dash in each row is bit 7, and the rightmost dash is bit 0. A particular dash is illuminated if the appropriate input line is high, and blank if the line is low.

The routine can also be incorporated into programs which control the I/O ports, thus providing a continuous visual indication of what they are doing. In this case modify the last instruction of the routine to an RTS instruction, and insert a call to the routine in the most frequently executed section of your program.


```

; DISPLAY STATE OF I/O LINES
;
DISP  = $0010      DISPLAY BUFFER
REPEAT = $000E
ABIT  = $0900      TEST A-SIDE BIT
BBIT  = $0908      TEST B-SIDE BIT
DISPLY = $FE0C     DISPLAY ROUTINE
;
0000      . = $0200
0200 A9 1F TEST LDA E$1F SINGLE SWEEP OF
0202 85 0E STA REPEAT DISPLAY.
0204 A2 07 LDX E7
0206 BD 08 09 LOOP LDA BBIT,X BIT 7 = STATE
0209 0A ASL A INTO CARRY
020A 7D 00 09 ADC ABIT,X
020D 95 10 STA DISP,X PUT IN BUFFER
020F CA DEX
0210 D0 F4 BNE LOOP
0212 20 0C FE JSR DISPLAY SWEEP DISPLAY
0215 10 E9 BPL TEST I.E. ALWAYS

.END

```

Fig. 6. Program for a 6502 displays the states of an Acorn's I/O lines.


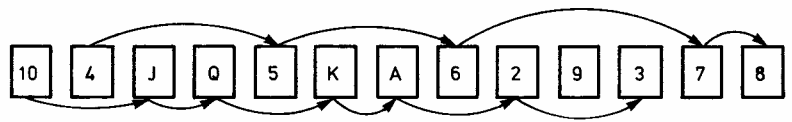


Fig. 7. Diagram to solve the card-trick problem.

CARD TRICK SOLUTION

In the last Micro-Bus you were asked to deduce which card in a series of thirteen cards had been removed, and replaced at a different position. The problem could be solved by entering the sequence of cards into one of the card-trick programs. Alternatively consider the sequence separated into two ascending series as indicated by the lines in Fig. 7. The nine is then clearly anomalous, and so this was the chosen card.

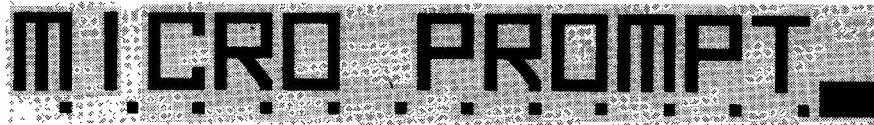

The hardware and software exchange point for PE computer projects

Yes, we know! This is supposed to be a bimonthly column; it appeared last month, yet here it is again! Well, the Prompt file is full of goodies, some of which we know are anxiously awaited, so we slipped this one in whilst no one was looking.

SAVE IT

Having stated in our first Prompt that the 101 has no cassette file handling firmware, we are now knee-deep in letters explaining various ways of saving raw data on tape. Below is a program which should provide the seed for some rewarding experimentation in cassette file keeping. It is an optimised combination of all the ideas sent in, some crude, some not so crude, plus our own refinements, and allows a named data file to be recorded. The data can be numbers or strings of text, since the technique utilises the SAVE and LOAD commands under program control. This program will take five words from you and record them as "FILE A"

save on tape

```

5 FOR A = 1 TO 5:INPUT
"WORD ": W$(A) : NEXT
10 PRINT "TURN TAPE TO
RECORD, & WAIT" : FOR A = 1
TO 8000 : NEXT
20 PRINT : PRINT "HIT ANY KEY"
25 POKE 11, 0 : POKE 12, 253 : X =
USR (X)
30 SAVE : PRINT "FILE A"
40 FOR A = 1 TO 5 : PRINT W$(A) :
NEXT
50 POKE 517, 0
60 END

```

Run the SAVE program, rewind the data tape, and then run the LOAD Program (RUN 120). All data will thus be cleared from memory, and recovery of the words will rely entirely on the tape file.

load from tape

```

120 PRINT "TURN TAPE TO
REPLAY, AND HIT ANY" :
PRINT "KEY IMMEDIATELY"
125 POKE 11, 0 : POKE 12, 253 : X =
USR (X)
130 LOAD
140 INPUT T$
150 IF RIGHT$(T$, 6) = "FILE A"
THEN 170
160 GOTO 140
170 FOR A = 1 TO 5 : INPUT W$(A) :
NEXT
180 POKE 515, 0 : PRINT : PRINT :
PRINT
190 PRINT RIGHT$(T$, 6) : PRINT :
FOR A = 1 TO 5 : PRINT W$(A) :
NEXT

```

Advantage is taken of the fact that any PRINT statement after a SAVE command will write to the cassette interface, and any INPUT statement after a LOAD command will take data from the cassette.

To revert to normal operation in each case, it is necessary to POKE the relevant SAVE/LOAD flag off again with a zero (lines 50 and 180).

A delay is included (dead FOR-NEXT loop) to wait for the tape leader to clear and the recorder to settle down etc.,

Lines 150 and 190 use RIGHT\$ to look at only these six characters: "FILE A", which may find themselves tacked on the end of some noise characters—all of which will think they are T\$.

101 LOCATIONS

Here are some useful UK 101 scratchpad memory locations which have been discovered by P. Goodwin of Southampton.

hex	dec	
0200	512	Cursor position along line
0206	518	VDU operating speed
0213	531	Character returned by keyboard input routine
0130	304	NMI Vector
01C0	448	IRQ Vector
		} these are in the middle of the stack
0203	515	LOAD Flag
		POKE 515, 0 turns Load off
0205	517	SAVE flag
		POKE 517, 0 turns Save off
0218	536	Input Vector
021A	538	Output Vector
000F	15	Terminal Width
0300		Program End pointer (POKE this at your peril)

HEAT POLLUTION

We received a letter from Mr. J. Briggs of Malton, N. Yorks, describing a problem with his 101 concerning video stability. The machine worked fine with the family television, but when used with a portable (PYE Model 191) the picture broke up as if incorrectly tuned, after about 10 minutes. Heat from the 5V regulator seemed to be affecting the modulator capsule, and anyone experiencing the same difficulty should note that the problem was cured by mounting the regulator and heatsink separately from the p.c.b.

The 3300µF reservoir capacitor has on some 101 boards suffered from excessive heat too. We have been told this can produce video and keyboard problems.

Next month's Prompt will include a table of handy and unexpected characters available direct from the 101 keyboard, and a review of some software which enables line editing and programmable cursor movement in all directions. We shall also publish that promised CHAMP program.




A selection of readers' original circuit ideas. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought.

Why not submit *your* idea? Any idea published will be awarded payment according to its merits.

Articles submitted for publication should conform to the usual practices of this journal, e.g. with regard to abbreviations and circuit symbols. Diagrams should be on separate sheets, not inserted in the text.

Each idea submitted must be accompanied by a declaration to the effect that it is the original work of the undersigned, and that it has not been accepted for publication elsewhere.

MODEL RAILWAY CONTROLLER

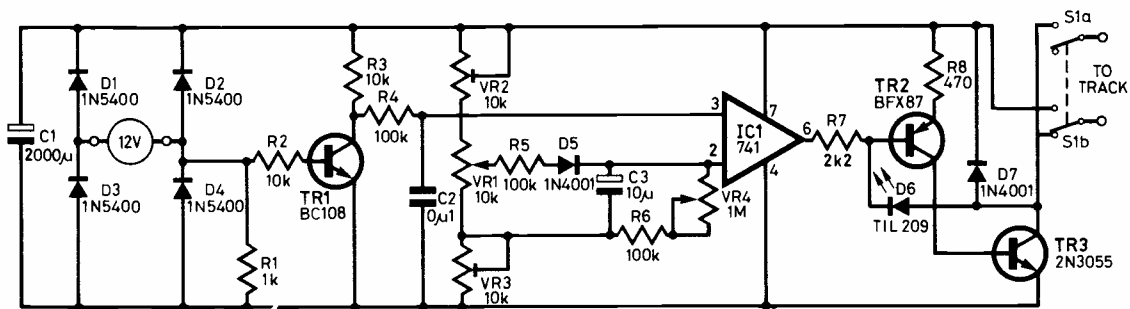

THE circuit shown is a pulsed power speed controller which includes simulated inertia and brake effects. It can also be used as a conventional pulsed power controller or as one in which both inertial acceleration and braking effects are controlled by the same potentiometer. I personally find this latter mode very satisfactory.

The controller will supply 1A at 12V and since the full output voltage is supplied to the motor during even the shortest pulses, the best possible control is achieved at slow speeds.

The half wave rectified output from the bridge rectifier is squared up by TR1 and integrated by R4 and C2 to produce an approximate saw-tooth waveform at the non-inverting input of the op-amp IC1.

The potentiometer VR1 and its associated presets VR2 and VR3 provides a reference voltage which can be varied over the range of the saw-tooth waveform. When this reference voltage at the inverting input is higher than the saw-tooth, the output of the op-amp goes low, switching on TR2 and TR3.

If all the components R5, R6, VR4, D5, C3 are omitted, the controller will be a conventional one with a very linear output.

If only R5 and C3 are included, the output will rise and fall exponentially giving exceptionally smooth starting and stopping and calling for some skill from the operator when shunting! The value of R5 may be adjusted for individual preference.


With all the above mentioned components, VR1 acts as the regulator and VR4

the brake. D6 acts as a current limiter and visual warning in the event of a short circuit.

To set up the preset potentiometers, connect a small loudspeaker in series with a 1 kilohm resistor across the output terminals. Turn VR1 to maximum and adjust VR2 until the 50 cycle note from the loudspeaker just disappears. Turn VR1 to minimum and likewise adjust VR3. Repeat this procedure once or twice until the note just disappears at both maximum and minimum ends. The controller is now ready for use.

J. O. Linton.
Harrogate.

METAL DETECTOR

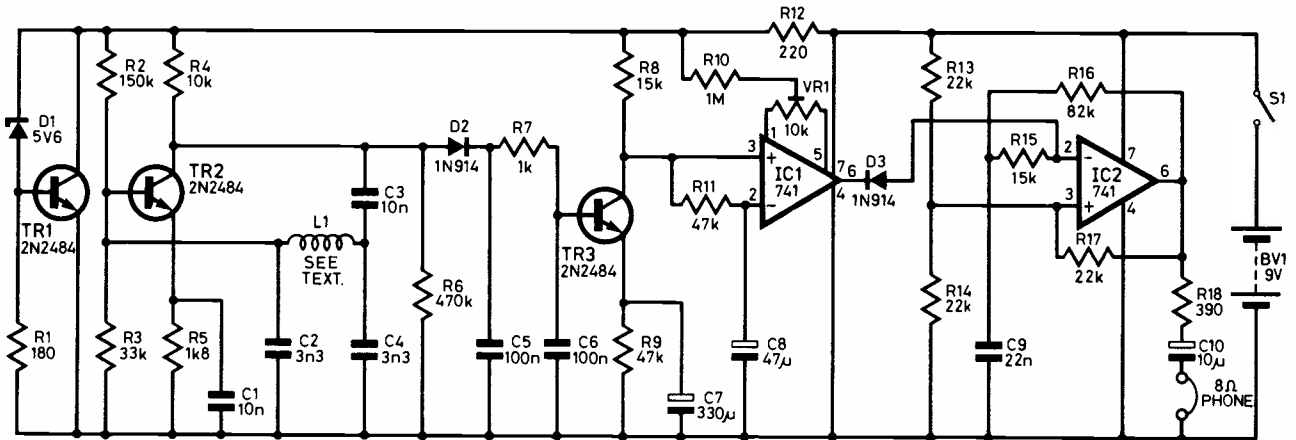

THE operating principle of this unusual metal detector relies on the fact that the high frequency field generated by the search coil, L1, produces eddy currents in any nearby metallic object. The energy used to produce these eddy currents is taken from the oscillator, formed around TR2. This is a Colpitts oscillator running at 140kHz; just inside the legal limit for metal detectors. This drain of energy, which finally produces heat in the metal, results in a reduction in the amplitude of the oscillations.

The signal at the collector of TR2 is rectified by D2; the peak value being stored in C5. Any change in the d.c. voltage will be amplified by TR3. A positive-going voltage at the collector of TR3, resulting from metal detection, will cause the output of the comparator, IC1, to switch positive, since the inverting input is for a time held

more negative than the non-inverting input by C8. The audio oscillator, IC2, which was previously inhibited by D3, now oscillates at 400Hz, driving the earpiece.

Stability of the circuit is ensured by the shunt regulator around TR1. The comparator, IC1, uses a rather unusual method of offset control, VR1, to enable a fairly large adjustment range. This is to null out any noise, interference and instability which could arise in this very sensitive circuit.

Since the circuit detects changes in voltage rather than absolute values, it needs no re-adjustment once VR1 has been initially set. Furthermore, the operator has no variable controls to manipulate, making the unit very simple to operate. This is also true of the detection signal, which is of the tone/no tone type. An operator would need no skill in

detecting a 10p piece at a depth of 6 inches, or larger objects up to 3 feet deep.

When the unit is switched on, it needs 60 seconds to stabilise. Once a metallic object is brought into the field, the detection signal remains for about 2 seconds, after which the circuit re-adjusts to the new value of oscillator amplitude.

L1 is a rectangular coil 3in by 6in wound with 55 turns of 5A flexible wire. A PP3 battery would give about 20 hours of continuous operation.

P. R. Williams,
Stevenage,
Herts.

LOW NOISE MIC PRE-AMP

THE circuit shown was designed to fulfil the need for a very high quality microphone amplifier such as is essential for serious tape recording and in studios.


The signal to noise ratio is 78dB for an output of 1V r.m.s. and a source impedance of between 600 ohms and 50 kilohms. This very high signal to noise ratio is achieved by operating TR1 at a collector current of just 25µA, and a V_{ce} of 2V.


The frequency response is 25Hz-24kHz (-3dB), the upper limit being due to C3, which ensures high frequency stability. The amplifier is very stable due to the use of multiple feedback paths. R5 completes a d.c. feedback path, and also provides the correct bias for TR1. R4 and C2 complete an a.c. feedback path, providing negative feedback to the emitter of TR1 to control the overall gain. Negative feedback also reduces distortion and lowers the output impedance to just 800 ohms. The input impedance is 200 kilohms.

The purpose of R7 is to decrease the voltage/gain of TR2 such that TR1 has to work at a high gain, aiding the signal to noise ratio. The overall voltage gain is 35dB, but this can be altered by changing

the value of R4. Inputs of up to 100mV can be accepted without undue distortion.

F. R. Williams,
Stevenage,
Herts.

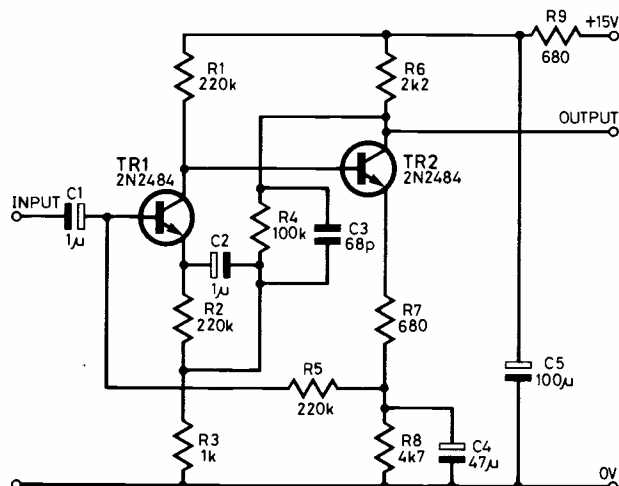

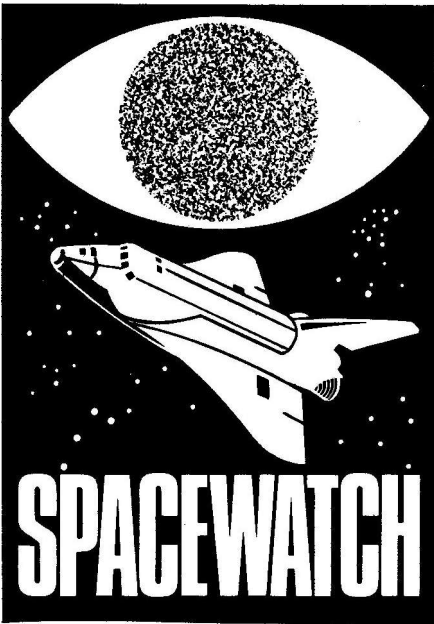

FRANK W. HYDE

INTERNATIONAL ULTRAVIOLET EXPLORER (IUE)

In January last the IUE satellite completed two years of outstanding operation as an orbiting astronomical observatory. The satellite was originally designed for a useful life of three years. Now it is reasonably certain to exceed that period. It is fortunate that this is so, for the demand for time is beyond the capability as originally supposed. Already there is request for more than double the present time available.

The mission is a joint venture by the Science Research Council, the eleven member countries of the European Space Agency and the National Aeronautics and Space Administration of America. All three participants have agreed to continue the operation of the satellite so long as justified by the scientific return of data.

The Science Research Council provided the ultraviolet sensitive television cameras and image processing software. The European Space Agency provided the solar arrays and the ground station which is situated near Madrid. The National Aeronautics Space Administration supplied and launched the spacecraft and also operates the ground station in America at Maryland. More than 500 scientists from 20 different countries are in the process of studying 12,000 ultraviolet spectra of planets, stars, the interstellar medium and the galaxies. The strongest characteristics of light emission of the common atoms and ions lie in the region of the ultraviolet wavelengths of 115 nanometres to 320 nanometres. A vast amount of information can be obtained about the composition and physical state of astronomical objects.

IUE has pioneered a new method of operating a space telescope. When astronomers visit a ground station they are able to operate and direct the telescope as if it were at a ground based observatory. The satellite telescope is small compared with the

equivalent ground based instrument for this work, but because the satellite telescope is outside atmosphere the efficiency is much greater. There are no cloud problems, no background light haze and much less turbulence to consider. Long exposures, which are essential to this work, can be carried out with great precision. An example of this was found when exposures of 14 hours were made and used to study the spectra of distant quasars of the order of magnitude 17. New information has thus been made available about these somewhat enigmatic objects.

Some of the discoveries are worth noting specifically. For example the stellar winds, which are caused by the radiation of matter from stars, have been found to exist around some of the very hot stars, something not previously known in connection with particular objects. New results show that the shockwave from an old supernova interacts with the interstellar material. Gas forming a high temperature halo around the galaxy with which the Solar System is associated (popularly called nowadays the Milky Way Galaxy) has been assessed and it is surmised that other galaxies may exhibit the same phenomenon. Observations have also been made of other galaxies, distant and active and other bodies such as quasars which emit vast amounts of energy. Studies were made of X-ray binary stars which are thought to be a normal star orbiting an object which could be a white dwarf, a neutron star or even a black hole.

The flexibility of the operating facilities of IUE has made it possible to allow for the unexpected, such as a new comet or the advent of a supernova, when the discovery could be followed by continuous observation.

These activities have already been widely discussed at some of the Conferences round the world. Perhaps the most succinct remark at a meeting of the International Astronomical Union Conference in Montreal, sums up the situation—"It is the first time that a whole day of the General Assembly has been devoted to the results of an 18 inch telescope only 18 months after its inception."

LASER COMMUNICATION SYSTEM (LASERCOM)

A Lasercom package carried on a space platform test satellite contains a transmitter as well as a low data rate receiver. The transmitter has been added to allow real-time telemetry data as the satellite passes over the White Sands missile range and gathering information on the performance of laser transmissions down through the atmosphere. The main aim of the tests is to evaluate the expected potential of space applications for high speed data transmission, increased transmission security and the ability to resist jamming.

The transmitter will be operated at a data rate of 800 bits/sec. This will enable the research team at the ground station to ensure that the transmissions are accurately pointed at the satellite. The satellite is to be placed in a 400 naut/mile orbit so that the ground station will have about 10 minutes of contact with the lasercom equipment aboard the spacecraft at each orbital pass.

The experimental module contains a multi-access receiver which is capable of acquir-

ing several messages simultaneously. This receiver has a field of view of 4 degrees. In order to assess the spread of the laser beam over long distances and the effects of atmospheric variations, the transmissions will be at varying rates. That is, there will be data rates of 100 bits/sec. to 20 kilobits/sec. Ground testing of the high rates has already been undertaken since 1978. The test set-up was made with the receiver and transmitter at one point and a 24 in. diameter reflector set up about a kilometre away. Already flight testing at 30,000 ft. has shown significant results at 100 bits/sec.

NEW THEORY FOR THE SOLAR SYSTEM

It was to be expected that someone would want to set up another model for the Solar System. This time, needless to say, the computer is being used to provide evidence. It is certain that the Velikovsky myths will be put forward as having prior claims to the authorship of the new suggestions.


The details so far available are based on the fact that the computer has offered a conclusion that large planets were stable at an earlier date in the evolution of the Solar System. It is natural that there would be an immediate assumption from some quarters that Jupiter is the planet in question. The reason? Because Jupiter is the largest planet in the Solar System. The reason could be that Velikovsky claimed that around 1500 BC a comet erupted from Jupiter and formed the planet Venus. Aside from the timing, the lack of understanding of basic facts by Velikovsky has set many fantasies and claims among the gullible. It is often the bizarre that attracts a very large number of people to these ideas and they cannot be persuaded that most of the statements have no basic credibility.

Some years ago the writer and a few more astronomers speculated that in one hypothesis it could be said that the original body, or bodies, assuming a binary system, could by some process which caused imbalance result in the separation of a large portion of the original matter which by the momentum changes left the remnants (very small mass) which became the planets, leaving the larger mass to become the centre of mass with the remnant balancing the system. Space does not permit more than this brief note.

Coming back to the new report it is quite conceivable that there was a transition period where large bodies formed and became stable. The size is not easily suggested for such bodies, nor is the suggestion from the team at the Ames Spaceflight Centre and California University that stability necessarily means a rocky core in the centre of such bodies. While it is true that there is no absolutely concrete data about the present physical conditions deep inside planets, yet a model which postulates a solid interior of rock would raise more problems than can be answered at the moment. Indeed the tremendous increase in our knowledge of the planets that has resulted from the latest pictures and other data from Jupiter and Saturn will change many preconceived ideas. These, however, will not and do not support a composition of double evolution. Nor is it the case that such details of ageing which are generally accepted at the present time give any support to such an idea.

Maintain the lead with Acorn 6809

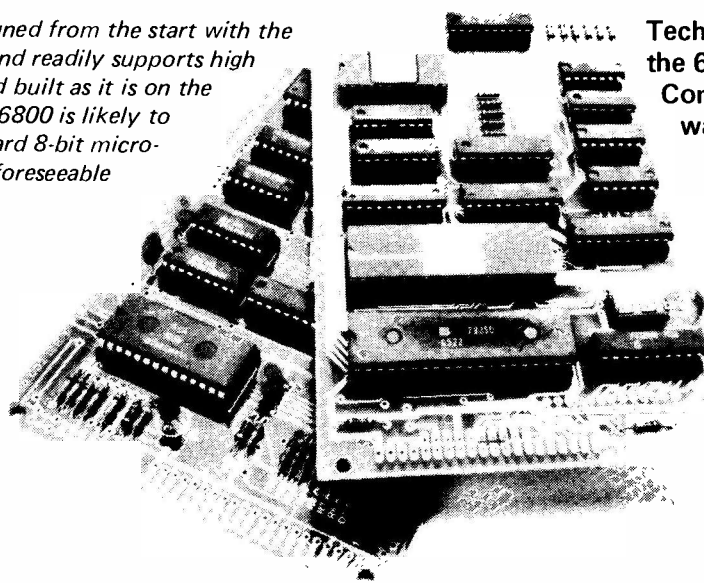... the 6809 designed from the start with the programmer in mind readily supports high level languages and built as it is on the experience of the 6800 is likely to become the standard 8-bit micro-processor for the foreseeable future. . . .



Technology leader in microprocessors the 6809 is now available from Acorn Computer with full supporting hardware on a eurocard paired with the Acorn VDU interface at a special introductory price.



Acorn is offering their two most powerful modules as the basis for a 6809 development system requiring the addition of keyboard, power supply and monitor. For existing owners of Acorn Systems, the 6809 CPU card is a direct plug-in replacement for the 6502 CPU and can be used with all the supporting cards presently consisting of 8K memory, tape interface, VDU interface, Floppy disc drive, Analogue to digital/digital to analogue and Universal interface.

For newcomers to Acorn the two card system can readily be linked to terminals printers, etc., the operating system firmware is designed for modularity and has disc bootstrap.




- 1K RAM
- Direct printer drive
- ASCII keyboard input
- Fully buffered address and data bus
- 2K operating system with
 - Printer routine
 - VDU routine
 - Cassette load and save
 - Disc bootstrap
 - Trace
 - All usual debug facilities

VDU

- Seven colours
- Teletext compatible
- Upper and lower ASCII and graphics
- Memory mapped
- Transparent access
- Programmable screen format
- RGB & Sync output
- Light pen facility
- Single 5v rail

- Fastest execution time of any 8-bit processor
- More addressing modes than any other processor
- Position independent code
- Re-entrant programming
- High level language efficiency
- Indirect, indexed and auto increment/decrement
- Four 16-bit registers
- Super powerful instruction set including multiply
- 6800 software compatibility

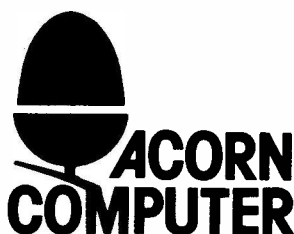All Acorn modules are covered by a money-back guarantee and a fast repair/advice service, kits are supplied with full assembly instructions and operating details including where necessary sample programs.



Acorn Computer,
4a Market Hill, Cambridge CB2 3NJ

PE 4

Please send me the following

qty 6809/VDU kit Special offer @ £160 + £24 VAT **£184**

6809 CPU kit @ £95 + £14.25 VAT **£109.25**

VDU Interface kit @ £88 + £13.20 VAT **£101.20**

Details on all Acorn cards

I enclose Cheque/PO to value

Name _____

Address _____

Acorn Computer 4a Market Hill Cambridge CB2 3NJ VAT No. 215 4002 20

Bind it

It's so easy and tidy with the Easibind binder to file your copies away. Each binder is designed to hold approximately 12 issues and is attractively bound and blocked with the PRACTICAL ELECTRONICS logo: Gold Letraset supplied for self blocking of volume numbers and years.

Price £4.10 including postage, packing and VAT. Why not place your order now and send the completed coupon below with remittance to: IPC Magazines Ltd., Post Sales Dept., Lavington House, 25 Lavington Street, London SE1 0PF.

it's easy with **EASIBIND**

Order form PRACTICAL ELECTRONICS

I enclose P.O./cheque value
for.....binders

Years required
(BLOCK LETTERS PLEASE)

Name

Address

Date

PRACTICAL
ELECTRONICS

VOL. 15
1979

A new book for the home electronics constructor

Microprocessors for Hobbyists

Ray Coles

- * An introduction to microprocessors based on two popular series in *Practical Electronics*
- * Covers the architecture of microprocessor chips and systems, programming memory and input-output components
- * Describes home computers together with a comparison of different models and the appropriate software
- * Includes a comprehensive glossary of terms to explain the 'buzz-words' of the micro-processor scene

1980 96 pages £2.95 US \$6.75

Newnes Technical Books
Borough Green, Sevenoaks, Kent TN15 8PH

Butterworths has companies in Australia, Canada, New Zealand, South Africa and the USA, where local prices apply.

SPECIAL OFFER!

VIDEOTONE

GB3

SPEAKERS

£41 PER PAIR

INCLUDING V.A.T and CARRIAGE

We believe this is an exceptional loudspeaker and that we are offering it at an exceptional price—we urge you to compare it with any advertised price or any other "offer"! The phrase "Value for money" is used in the Practical Hi-Fi and Audio review quoted below—that phrase was based on a normal retail price of approximately £80 (yes eighty)—need we say more?

The GB3 is a two-way bookshelf loudspeaker of very compact dimensions which is based on the extremely successful Minimax. However, all the design and development work for the GB3 has been completed by Videotone engineers in the U.K.

As in the Minimax, the bass unit utilised is a high performance, 5 inch unit which incorporates a lightweight, rigid paper cone with rubber roll surround and a one inch double wound voice coil. These combined with the high density magnet give the unit a very long throw with good linearity and this results in a powerful, clean bass and very good power handling.


The tweeter used is a brand new one inch dome developed specially for the GB3. This unit has a smooth frequency response which extends beyond 20kHz and the use of it in the GB3 gives the speaker a good polar response, enabling the listener to listen off axis from the speaker without undue loss of extreme high frequency sound.

The crossover that combines the woofer and tweeter together is also of a new design, incorporating mylar capacitors and top quality air cored inductors to ensure a well integrated and smooth response throughout the crossover region. The drive units and crossover are contained in a very high quality cabinet. This is constructed from reinforced plywood (which is better than chipboard for the absorption of unwanted rear-radiated sound) and filled with a measured quantity of acoustic wadding to further absorb cabinet resonances. The cabinet is covered, both back and sides, in a high quality wood veneer of either polished teak or walnut.

The use of more sophisticated and expensive components and drive units in the GB3 have resulted in a sound quality that is superior to the highly regarded Minimax in almost every way.

Typical Specification:

Type:	Two way, sealed box (infinite baffle) enclosure
Impedance:	8 Ohms nominal
Recommended amplifiers:	Those delivering between 15 and 40 watts (r.m.s. into 8 Ohms)
Frequency response:	50-20,000 Hz (80-20,000 Hz ± 4dB)
Efficiency:	3 watts (r.m.s. into 8 Ohms) gives 88dB S.P.L. at 1 metre
Crossover:	12dB per octave network, utilising high quality components, and crossing over at 3.4kHz
Size:	260mm (10½in) high, 150mm (5¾in) wide, 220mm (8½in) deep

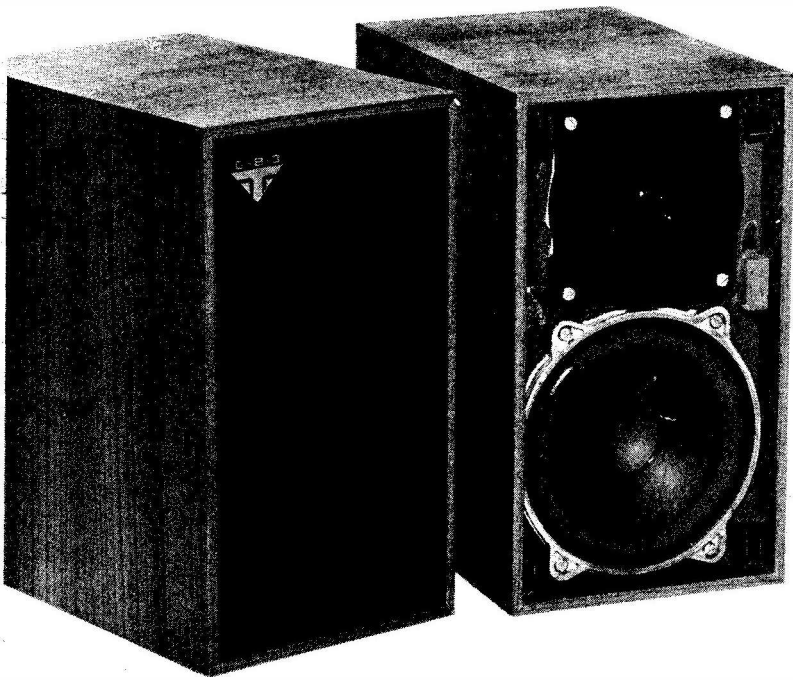

To: Videotone Ltd., 98 Crofton Park Road, London S.E.4. Tel. 01-690 8511

Please send me

<input type="checkbox"/>	Teak finish
<input type="checkbox"/>	Walnut finish

GB3 loudspeakers at £41 per pair

I enclose P.O./Cheque No. Value.....

Name

Address

.....

Please allow 28 days for delivery
OFFER CLOSES FRIDAY MAY 2nd 1980

Name

Address

.....

.....

From: Videotone Ltd. 98 Crofton Park Road, London S.E.4. Tel. 01-690 8511

Please complete both parts of the coupon in BLOCK CAPITALS

Extracts from review by Bill Anderton in the October Issue of Practical HiFi and Audio.

When under test, the GB3s were compared with a monitor loudspeaker system costing four times as much and this should be borne in mind when evaluating comments.

Initial impression: excellent.

Mid range and high frequencies very good and clear. No over emphasis of record surface noise. Excellent overall—no immediately obvious distortion.

Percussion: stereo image solid and well defined. Top end good—cymbals clean, accurate sound, not tinny. Realistically high listening levels obtainable despite relative inefficiency. Mid-range very good. Electric guitar has bite and depth to its sound quality.

Orchestral with solo violin: solo violin reproduced accurately—no unnecessary harshness. Upper mid-range excellent. Overall an excellent high-quality performance, very impressive.

Orchestral with piano: top end well controlled and impressions, realistic reproduction. Rock and jazz: brass excellent accurate sound, reproducing reedy, raspy timbre accurately. Very impressive and will reproduce high sound levels without introducing any noticeable distortion.

Organ: considering the size of these loudspeakers, bass performance is excellent. Mid-range and high frequencies accurate.

Choral: excellent stereo separation between sound images, male voice speech. Tonal

quality can sound thin but overall performance excellent.

White noise: very smooth—no obvious level difference between drive units and no obvious suck-outs or peaks. Low frequencies missing but otherwise accurate.

Drums: cymbals clear and accurate.

Electric bass and bass drum: remarkable performance for such a low priced speaker.

Guitar 12 string: excellent reproduction of transients.

Piano: same comments as for 12-string guitar.

Bass acoustic: very good. Transient response accurate.

Cello: excellent. No loudspeaker resonances evoked by this instrument.

Violin: very good.


Bass flute: very accurate reproduction. Breath tones clear without over-emphasis.

Alto flute: same comment as for bass flute.


Oboe: characteristic timbre accurately reproduced. Performs well in this, frequency range.

English horn: excellent, accurate reproduction of the tonal quality of this instrument.

"Comparison with Minimax 2: smoother upper mid-range and high frequency reproduction. Slightly less efficient but general tonal clarity has been improved—not quite so lively as the Minimax but overall the sound quality has been improved by quite a major degree." "Distortion measurement results were excellent." "Value for money is certainly the phrase I would use to describe the diminutive GB3s. They are styled simply and attractively and have a performance quality that surpasses all expectations from a loudspeaker of this nature. Full marks to Videotone and the GB3."

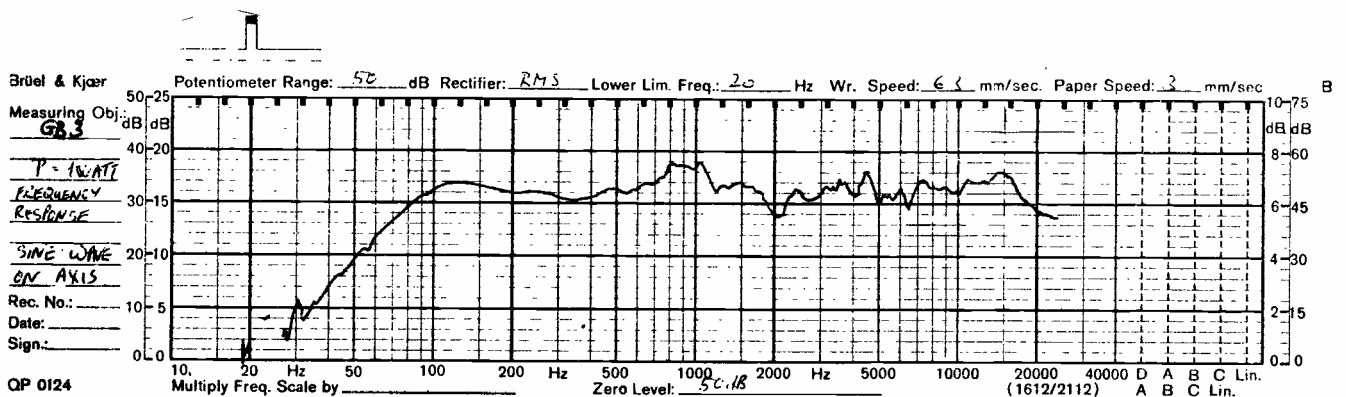

CAR RADIO

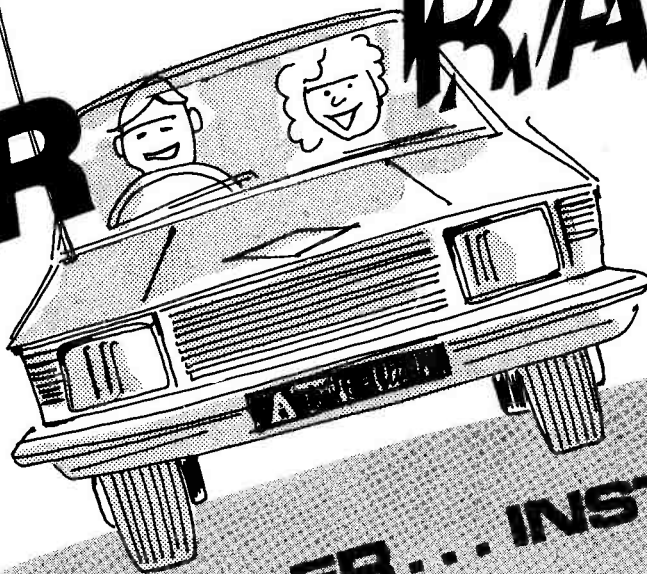

PE TRAVELLER... INSTALLATION

AFTER the Traveller has been assembled and aligned a piece of cardboard should be fitted over the track of the p.c.b. to improve the insulation. If a multimeter is available check that a short does not exist between the two feed through capacitors and the chassis. The current consumption of the set is very low without a signal and should not exceed 1 amp. at full volume.

Under no circumstances should the cores of the tuner or the r.f.-i.f. module be adjusted as the unit is pre-aligned and tuned for optimum results.

SETTING THE PUSH BUTTONS

The push buttons can be set by tuning the receiver to the medium wave and pulling out the first button, next to the volume control, which should move approximately 6mm from its static position. The station required should then be selected using the manual tuning knob and when the set is accurately tuned in the push button should be pressed firmly home.

AERIAL

A suitable aerial for the Traveller should have a total capacity (aerial and lead) of 70-80pF. If a high capacity aerial is used there will be problems in adjusting the aerial trimmer. Ensure that there is a good earth between the aerial and the car body.

With all the connections made to the set but before the escutcheon is fitted the aerial trimmer should be adjusted. It is best to use a weak station at the h.f. end of the medium waveband. There should be a point where the volume peaks with a clear drop either side. The two square trims can then be fitted to the escutcheon along with the printed tuning scale.

INSTALLATION

If a dashboard cut-out for a radio is provided then the volume, tuning control knob and the escutcheon should be removed. The two remaining distance nuts can then be adjusted to the correct gap between the set and the escutcheon.

With all the connections made to the set it should be fitted into the dashboard from behind and the knobs and escutcheon refitted. After the set has been fitted check that there is sufficient clearance for the push buttons to operate correctly.


If there is no aperture the set can be mounted either on the parcel shelf or under the dashboard. The set should not be fitted near the heater outlet as frequency shift due to extreme temperature may occur.

Two 2BA tapped fixing holes are provided either side of the casing and these can be used to mount the set (max. length of screws 12mm). Two 'L' shaped brackets should be formed (Fig. 1) and fitted to the car and then the radio screwed into position.

INTERFERENCE SUPPRESSION

After the set has been installed it should be checked for any interference. To ensure that the interference is not from any outside source the following checks should be carried out away from any building, power lines, etc.

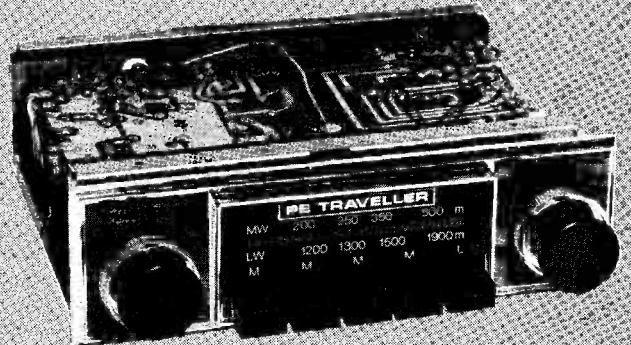Tune the radio to the medium wave away from any station



and with the volume turned up only a background hiss should be audible. If there are any crackles re-check the aerial and earthing points for loose or dirty connections. If an electric clock is fitted this can be suppressed with a $1\mu\text{F}$ capacitor between its 12V supply and earth. With the ignition turned on the electric fuel pump (if fitted) may cause a whine or tick in which case another $1\mu\text{F}$ capacitor should be across its supply to earth.

With the engine running there might be a trace of interference. If however there is a whine which increases with engine revs this will be the generator. A $1\mu\text{F}$ capacitor should be connected across the live output terminal to earth. *Do not* connect it to the field terminal. Alternators should be suppressed using $2\mu\text{F}$ capacitors connected across the output lead and the nearest earth.

If the interference is a crackle which varies with engine revs then the ignition coil should be suppressed with a $1\mu\text{F}$ capacitor connected across the switch terminal (SW,+) and earth. *Please note* that if your car has electronic ignition then you must check with the manufacturer's instructions otherwise the system may be damaged.

In most cases the procedure outlined above should give

Countdown

- Computermarket** Mar. 11-13. Manchester. **U1**
Computermarket Mar 18-20. Glasgow. **U1**
Keyboards And Switches (mini) Mar. 18-20. National Microprocessor and Electronics Centre, London. **L1**
Computermarket Mar. 25-27. London. **U1**
Electro-Optics/Laser International March 25-27. Metropole Convention Centre, Brighton. **T1**
Viewdata Mar. 26-28. Wembley Conference Centre, London. **O**
Computer-Aided Design (conference & exhibition) Mar. 31-April 2. Metropole, Brighton. Details: CAD 80/0483-31261
Small ATE April 1-3. National Microprocessor and Electronics Centre, London. **L1**
Applying Microprocessors April 8-10. National Microprocessors and Electronics Centre, London.
Seminex April 14-18. Dept. Physics, Imperial College, London. **H1**
Communications 80 April 14-18. National Exhibition Centre. **I**
Calibration April 15-17. National Microprocessor and Electronics Centre, London. **L1**
Peripherals 80 April 16-17. London. **L**
Welsh Amateur Mobile Rally April 20. Memorial Hall. **C**
Electronic Test & Measuring Information April 22-24. Wythenshaw Forum, Manchester. **T**
International Conference On The Electronic Office April 22-25. London Penta Hotel. Organised principally by the Institute of Electronics & Radio Engineers. 99 Gower St., London WC1E 6AZ
North Midlands Mobile Rally April 27. Drayton Manor Park, Tamworth, Staffs. Details: Norman Gutteridge, 68 Max Rd., Quinton, Birmingham
All-Electronics Show April 29-May 1. Grosvenor House, London. **E**
The Mersey Micro Show April 30-May 2. Adelphi Hotel, Liverpool. **O**
Compec Europe May 6-8. Centre International Rogier, Brussels. **L**
International Word Processing (Exhibition and Conference) May 20-23, Wembley Conference Centre. **O**
East Suffolk Wireless Revival May 25. Grounds of Ipswich Area Civil Service Sports Association, Straight Rd., Bucklesham. There should be a good variety of happenings to interest both radio addicts and non-addicts, including, it is hoped, a demonstration of a PO television detector van. **V1**
Satellite Communications (Conference) June 18-19. London Press Centre. **O**
Great British Electronics Bazaar June 20-22. Alexandra Palace. **E**

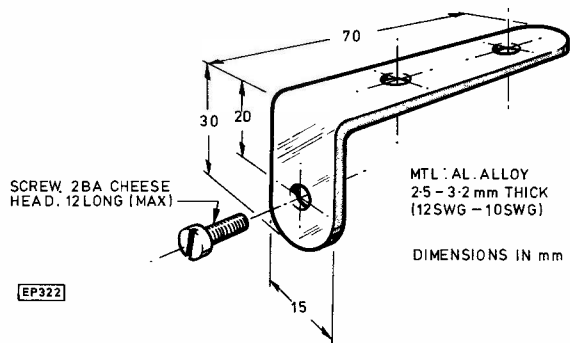


Fig. 1. Mounting bracket details (2 off)

interference-free suppression. Should the interference continue, however, then check that the bonnet top is firmly closed and that it makes a good electrical connection to the body of the car. Also check the outer screen of the aerial lead is well earthed at the base of the aerial and the aerial plug makes a good contact in the socket. ★

- Intel Fair** June 24. Wembley Conference Centre, London. **U**
Tempcon July 1-3. Wembley Conference Centre. Exhibition devoted to temperature control & measurement. **T**
Transducer July 1-3. Wembley Conference Centre. **T**
Microsoft (symposium) July 7-10 University of Sussex. **S1**
The 1980 Microcomputer Show July 10-12. Royal Lancaster Hotel, London. **O**
BAEC Amateur Electronics Exhibition July 12-19. The Esplanade Shelter, Penarth, near Cardiff, S. Glam. **B**
Computer Graphics (exhibition & conference) Aug. 12-14. Metropole, Birmingham. **O**
Harrogate International Festival of Sound Aug. 16-19 (18 & 19 trade). The Exhibition Centre + hotels. **X**
Avionics (symposium) Sept. University of Surrey. **S1**
BEX (Business Equipment Exhibition) Oct. 1-2. The Guildhall, Plymouth. **K**
BEX Oct. 15-16. Assembly Rooms, Edinburgh. **K**
BEX Nov. 5-6. Sophia Gardens, Cardiff. **K**
Semiconductor International 80 November 25-27. Metropole Convention Centre. **T1**.

- B** British Amateur Electronics Club, 26 Forrest Road, Penarth, S. Glamorgan.
C Barry College of F.E. Radio Society, College of Further Education, Colcot Rd., Barry, S. Glam. CF6 8YJ
E Evan Steadman, 34-36 High St., Saffron Walden, Essex. ☎ 0799 22612
I Industrial Trade Fairs. ☎ 021-705 6707
K Douglas Temple Studios, 1046 Old Christchurch Rd., Bournemouth, Dorset BH1 1LR. ☎ 020 20533
L Iliffe Promotions. ☎ 01-261 8437/8
O Online Conferences. ☎ 0895 39262
T Trident International Exhibition. ☎ 0822 4671
U Brian Crank Associates, 58 London Rd., Southborough, Kent. ☎ 0892-31812 38414
X Exhibition & Conference Services, Claremont Ho., Victoria Ave., Harrogate, Yorks. ☎ 0423-62677
H1 Seminex Ltd. ☎ 0892 39664/5
L1 P. Smith, London World Trade Centre, Europe House, London E1 9AA. ☎ 01-488 2400
S1 Society of Electronic & Radio Technicians, 57-61 Newington Causeway, London SE1 6BL. ☎ 01-403 2351
T1 Kiver Communications U.K., Millbank House, 171/185 Ewell Road, Surbiton, Surrey KT6 6AX.
U1 Couchmead Ltd. ☎ 01-437 4187
V1 Jack Tootill, G41FF, 76 Fircroft Rd., Ipswich, Suffolk IP1 6PX. Send s.a.e. (9 x 5 ins.) for details.

2 WIRE TRAIN CONTROLLER

PART 1
J. MILNE

THIS article describes the principles, and construction, of a control system for model locomotives, which allows independent operation anywhere on an interconnected rail layout.

The construction of a four channel controller is described, but it should be possible to expand the system to at least ten channels, including point and signal control.

PRINCIPLES OF OPERATION

The rails are supplied with 20V a.c. from a transformer. Regulation of the current flow through each of the motors, is carried out in a unit attached to the motors. How this occurs can be explained more easily, if the following simple examples are considered first.

A d.c. motor will run with an a.c. supply, of suitable voltage, if it is half wave rectified, with a diode, as in Fig. 1(a).

If the motor speed is required to be variable, the diode can be replaced with a thyristor, as in Fig. 1(b). By adjusting the triggering point of the thyristor, in the supply cycle, the motor speed can be altered from zero, to maximum.

To allow the motor to run in either direction, a second thyristor can be fitted in parallel with the first, but inverted, as in Fig. 1(c).

Only one of the thyristors is triggered at any time, and the speed control is similar to the previous example.

The two thyristors can be replaced by a single triac, as in Fig. 1(d), which simplifies the triggering arrangement, but controls the motor current in exactly the same way.

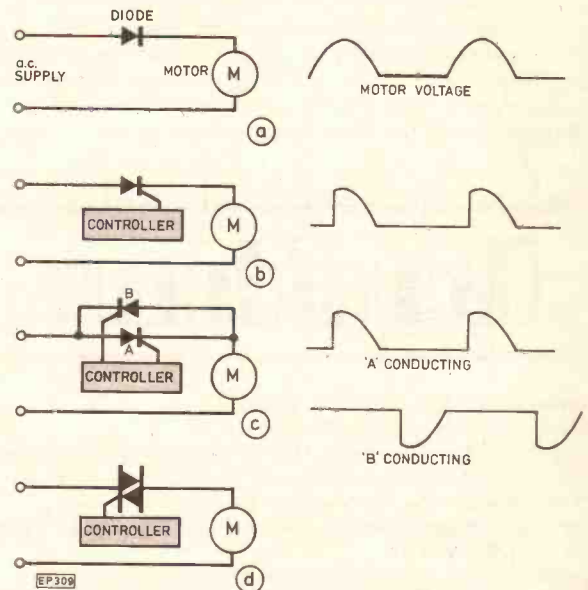


Fig. 1 Variants on motor speed control from an a.c. input (a) half wave rectified (b) phase controlled (c) phase control with back-to-back thyristors (d) triac equivalent

The characteristics of a triac, are very similar to that of the thyristor. Once triggered, it will continue to conduct, regardless of its gate current, until the load current falls below the minimum holding current, when it will switch off. When the



device is in an a.c. circuit, this will occur at the end of each half cycle, at or near zero voltage. The main difference between the triac and the thyristor is that it will conduct in either direction, and that it can also be triggered by a gate current in either direction.

A triac is fitted in each of the units attached to the locomotive motors, and is the main working component in the system. The rest of the circuits are there only to ensure that the triacs are turned on at the right time.

Fig. 2 shows a block diagram for the system. For each of the channels, a logic circuit working at supply frequency, gives an output varied by the position of a potentiometer, which is then used to operate a switch in the output of an oscillator. The outputs of all channels are then combined by a summing amplifier, before being passed to the output stage, and so to the rails. In the receiver unit, at each locomotive, a tuned amplifier sorts out its own control signal from the others, and the supply frequency. On detecting the control frequency, a trigger amplifier causes a pulse of current to flow in the triac gate circuit, so turning it on.

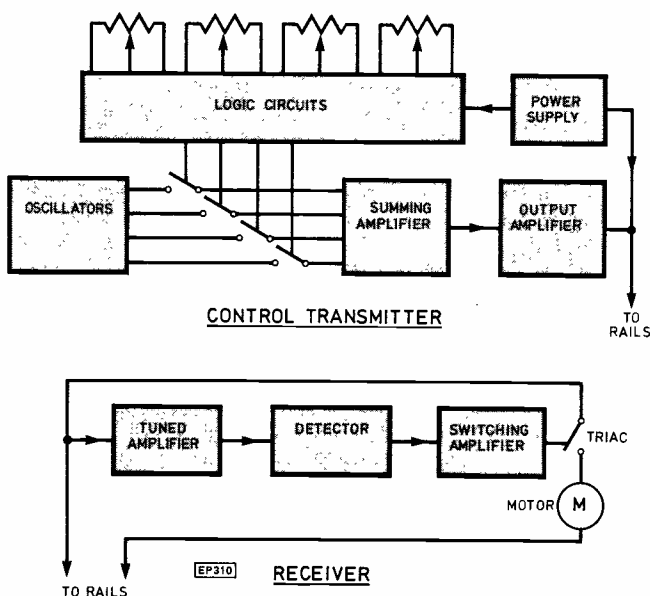


Fig. 2 Block diagram of system

DESIGN CONSIDERATIONS

The choice of control frequencies, was a matter of some compromise. It is convenient, and simple, to use chokes to contain the control signals within the rail system. The chokes must have a low impedance at supply frequency, or they will restrict the motor load current. For an impedance of less than one ohm an inductance of 1mH to 2mH appeared suitable.

It also appeared desirable to keep the control frequencies as low as practical, and well clear of the radio frequency range. This then has the advantage that the wide range of audio frequency components can be used.

A 2mH choke has an impedance of over 100Ω at 10kHz, and by using a low output impedance amplifier to supply the control signals, at least ten circuits with their chokes, can load the amplifier without causing a significant drop in signal level. 10kHz appears to be the lowest usable frequency, and was used in my initial experiments.

The control oscillators should give a reasonably pure sine wave output, to prevent interference with channels at higher frequencies, through the generation of harmonics, and be free of significant temperature drift, to prevent interference with adjacent channels.

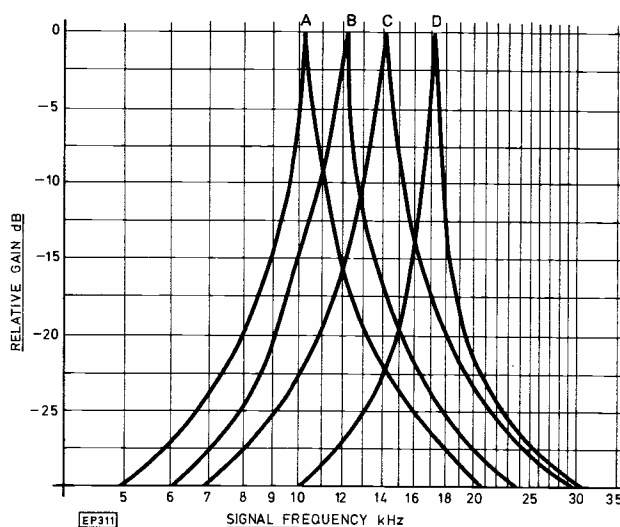


Fig. 3 Response curves for tuned amplifiers

The tuned amplifier stage in the locomotive receivers should also be drift free, as well as having a reasonable Q value, and be physically small. The Q value also has to be considered when deciding the spacing of the frequencies. Fig. 3 shows the response curves for the prototype RC tuned amplifiers, which confirmed that a spacing of less than about 20%, was impracticable for this type of amplifier.

Small d.c. motors generate wide band electrical noise, and in quantities out of proportion with their size. Precautions have to be taken to prevent, not only the effects this can cause on the reliable operation of the locomotives, but also to prevent the possibility of causing annoyance to others through radio frequency interference.

These are some of the factors taken into consideration during the development of this controller, and will be referred to in the description of the individual parts of the circuits, together with the other significant features.

PERFORMANCE

In use, the system is very similar to the pulsed d.c. systems, and has the same advantages and disadvantages. Starting with the good points, the low speed control is very good, and a reliable creep speed down to about one inch per minute is possible. Even at low speed settings, the motor torque is high, and the wheels tend to slip on heavy loads, rather than stall the motor. Because the full supply voltage is on the rails, all the time, the locomotives are more tolerant of oil and dirt on the track.

There are two disadvantages, caused by the discontinuous flow of current through the motors. The first is that because of the high a.c. component, the motor eddy current loss is increased, causing the motor to run hotter. I have not had any difficulty through this cause, but some manufacturers issue a warning not to run their locomotives for prolonged periods on half wave current, and the same must apply here. The second is that the torque produced by the motor is also discontinuous, and with wear on the reduction gearing, can cause an unrealistic rattle. This is not so offensive if the model is of a diesel, but one of the "high mileage" steam locomotives used for testing the system required quite a bit of attention to make it acceptable.

The other point that must be made at this stage is that most commercial model controllers are "inherently safe", and can withstand a short circuit for indefinite periods, and limit the short circuit current to a safe value. In this design, of necessity, the rail supply transformer is connected almost

directly on to the rails, so the potential fault current is high. A fast and reliable circuit breaker must be fitted in the transformer secondary circuit, and the primary circuit fused.

CONTROL TRANSMITTER

This unit houses all the electronics to produce the control signals, the rail supply transformer, and the power supplies. The electronic components are accommodated on two circuit boards: the logic board and the oscillator amplifier board.

The signals produced, and the effect on the motor voltage, is illustrated for one channel, in Fig. 4. The logic circuit produces a negative pulse, of variable width, starting at some point during one half cycle of the supply voltage, but always ending at the end of that half cycle. The logic circuit output is used to operate an f.e.t. switch in the oscillator output, allowing the signal to pass on to the rails. The signal is then detected by the locomotive receiver, and the triac switched on. The control signal is transmitted throughout the triac conducting period, even though only a few milliseconds at the start of the period should be necessary to trigger the triac. However, poor rail contact, etc, could cause a short signal to be missed, so on the principle of "better late than never", the longer signal pulse is used.

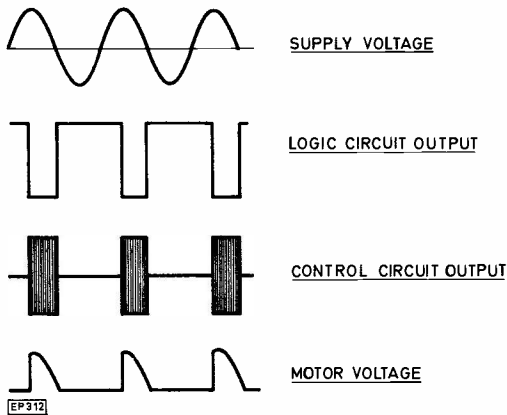


Fig. 4 Signal processing from logic circuit to motor

LOGIC CIRCUITS

As referred to previously, the function of these circuits is to produce an output suitable to switch on and off the control signals. The required output from one channel is shown in Fig. 5 with various locomotive speed settings.

The circuit diagram for this part of the circuit, is shown in Fig. 6. This has been drawn, showing only one channel for simplicity, but is marked with the component numbers for all the channels.

A 20V a.c. input is connected through R18 and C14 to D1, to give a near square wave representation of the supply voltage. C14 gives a few degrees of phase advance to compensate for delays later in the circuit. TR1 amplifies the leading and trailing edges of the square wave, and gives a TTL compatible output. From here the circuit divides, first into two, then into four parallel paths, so again for simplicity, only the channel with the lowest component reference numbers is used in the following explanation.

IC1 NOR gate (c), and IC3 gate (c) are both connected as inverters. IC5 and IC9 are monostables, used to provide the variable length pulses. With the connections used, pin 6 voltage is normally low, but will go high when pin 5 is switched from the low to high states. Pin 6 will then remain high for a period $t = Ct Rt \log_2 2$ seconds where: Ct is the value of the timing capacitor, connected between pins 10 and 11 and Rt is the sum of the internal and the external resistors connected between pin 9 and the positive supply.

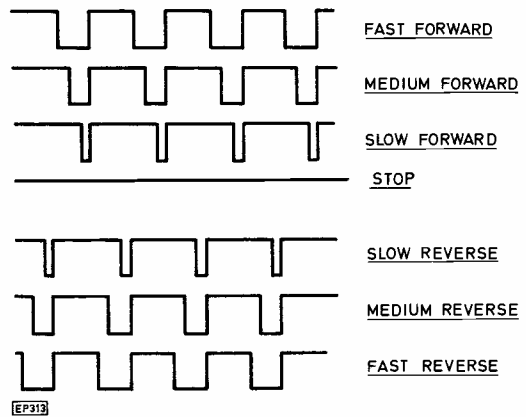


Fig. 5 Logic Board control output signals

IC1 (c) output connects to IC9 input, and IC3 (c) to IC5. Referring to Fig. 7, it will be seen that the timing period of IC9 starts at the beginning of the supply positive half cycle, and IC5 for the negative half cycle. IC5 and IC9 share the same variable timing resistor VR1, so when this is set at mid travel, and with a suitable value of timing capacitor, the timed period can be equal to a half cycle period, that is 10ms. This is shown in Fig. 7 (d) and (e). IC9 output, and IC3 output, shown in Fig. 7 (c), connect to the inputs of gate IC1 (b), and similarly, the outputs of IC5 and IC1 (c), Fig. 7 (b), to IC1 (a). By inspection, it can be seen that the output of both gates, IC1 (a) and (b), will be low at all times and that the output of IC1 (d) will remain high.

If VR1 is moved from the mid position, so that the timing period of IC9 increases, Fig. 7 (f), and IC5 decreases, Fig. 7 (g), IC1 (b) output will be low continuously, but IC1 (a) output, Fig. 7 (h), will be high from the end of the timing period, to the end of that half cycle. One input of IC1 (d) is low continuously, so the output will be the inverse of the other output. It should also be noted that if VR1 is moved further in the same direction, IC5 timing period will be reduced again, and the start of IC1 (a) output pulse will move to a new position earlier in the half cycle.

If VR1 is now moved in the opposite direction, so that IC9 is near to the minimum, Fig. 7 (i), and IC5 near to maximum, Fig. 7 (j), by analogy with the previous example, the output of IC1 (b) will be high from the end of the timing period to the end of the positive half cycle, Fig. 7 (k), and will again be inverted by IC1 (d).

Effectively, the timing period derived from IC9 controls the locomotive speed in one direction, and that from IC5 in the opposite direction. Fixed value resistors are fitted in series, and in parallel with VR1. The series resistors prevent the timing period becoming too short, when maximum speed is selected, as this can result in erratic triggering of the triac, caused by low instantaneous supply voltage and high motor back e.m.f. The parallel, or shunt resistors, R9 and R13, compensate for the variations in the actual values of VR1, and the timing capacitors, C18 and C22.

CONSTRUCTION

The circuit layout is not critical, and all the usual precautions when using TTL devices should be taken. A suitable circuit board, and the component layout is shown in Figs. 8 and 9. Extra decoupling capacitors have been used in the supply to the devices, because of high electrical noise in the circuits near to the board.

It is desirable that the components that effect the timing periods are subject to some selection. Readily available capacitors have a tolerance of 10%, and potentiometers

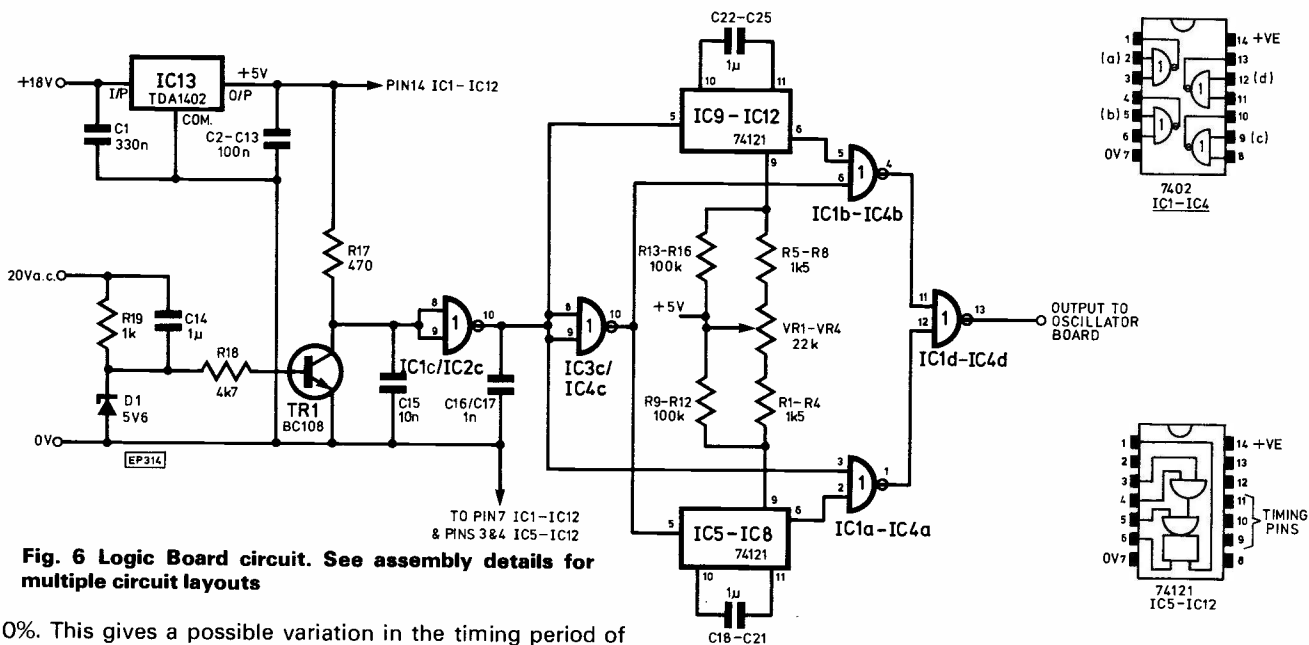


Fig. 6 Logic Board circuit. See assembly details for multiple circuit layouts

20%. This gives a possible variation in the timing period of $\pm 30\%$ from the calculated time. This variation is acceptable for the minimum time period, but when the maximum exceeds the supply periodic time the logic of the circuit breaks down and an erratic output is produced. To prevent this occurring, the maximum timing period should be between 17 and 18ms, to allow for changes in potentiometer slider contact resistance. If the facilities are available, measure the values of the timing capacitors, C18 to C22, and the track resistance of the potentiometers VR1 to VR4. Each potentiometer should be grouped with a pair of similar valued capacitors, such that a high value potentiometer is assigned to a low value pair of capacitors, and vice versa. Multiply the value of the capacitors, in μF , to the value of the potentiometer track resistance in kilohms, and if the resultant exceeds 23, shunting resistors will be required, and fitted in the positions marked for R9 to R16. For resultants less than 23, the resistors are not required, and their positions left unused. The required values of shunting resistors can be calculated from:

$$R_s = \frac{18(R_v + 1.5) - 1.4C_t(R_v + 1.5)}{0.7C_t(R_v + 3.5) - 18} \text{ kilohms}$$

Where C_t is the measured value of the timing capacitor in μF and R_v is the measured track resistance of the potentiometer in kilohms. When it is impracticable to measure the capacitors, they could be assumed to be of reasonable value, and just the potentiometer track resistance measured. For values over $23\text{k}\Omega$, the previous equation can be simplified, and the appropriate value of shunting resistor found from:

$$R_s = \frac{23.7(R_v + 1.5)}{R_v - 22.2} \text{ kilohms}$$

If it is impracticable to do any of this, a $100\text{k}\Omega$ resistor could be fitted which will compensate for all but the extreme values.

I used one of my own heat sinks for the 5V regulator, and Fig. 11 shows how it can be made; however, a commercial component could be fitted. Referring to the board layout, shown in Fig. 9, fix into position the thirteen links in the positive rail, drawn as a double line on the component side diagram. 22 s.w.g. p.v.c. covered single core copper, or similar wire, should be used for this. Then fix the twenty two signal links, using 26 s.w.g. single core p.v.c. covered, or similar. The use of d.i.l. sockets is recommended, and these should be fitted next, followed by the resistors and the

capacitors. Fit the 5V regulator (IC13) and its heat sink into position, using a small quantity of silicon grease on the contact surface. Finally, fix into place TR1 and D1.

TESTING

Before fitting the i.c.s into their sockets, connect a variable voltage power supply to the positive and negative

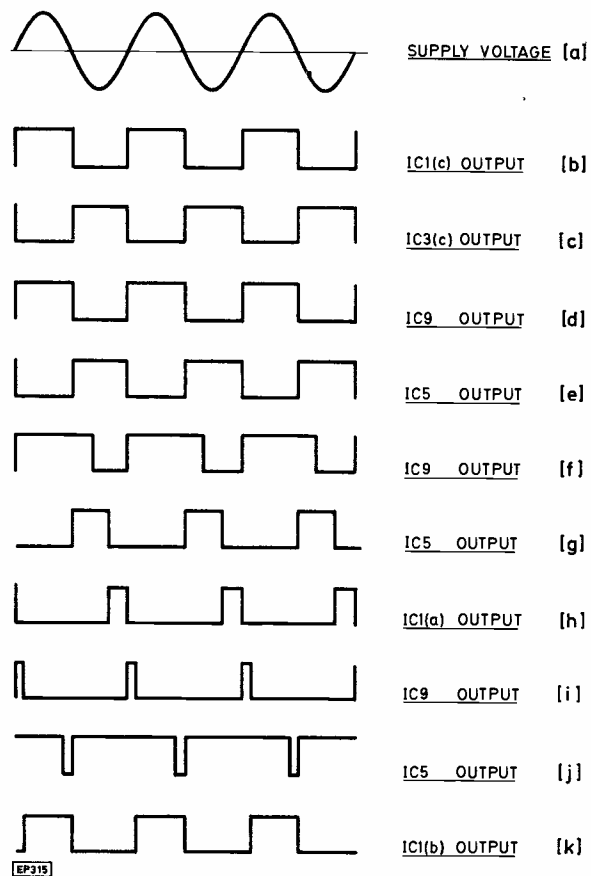


Fig. 7 Oscillograms for i.c. outputs

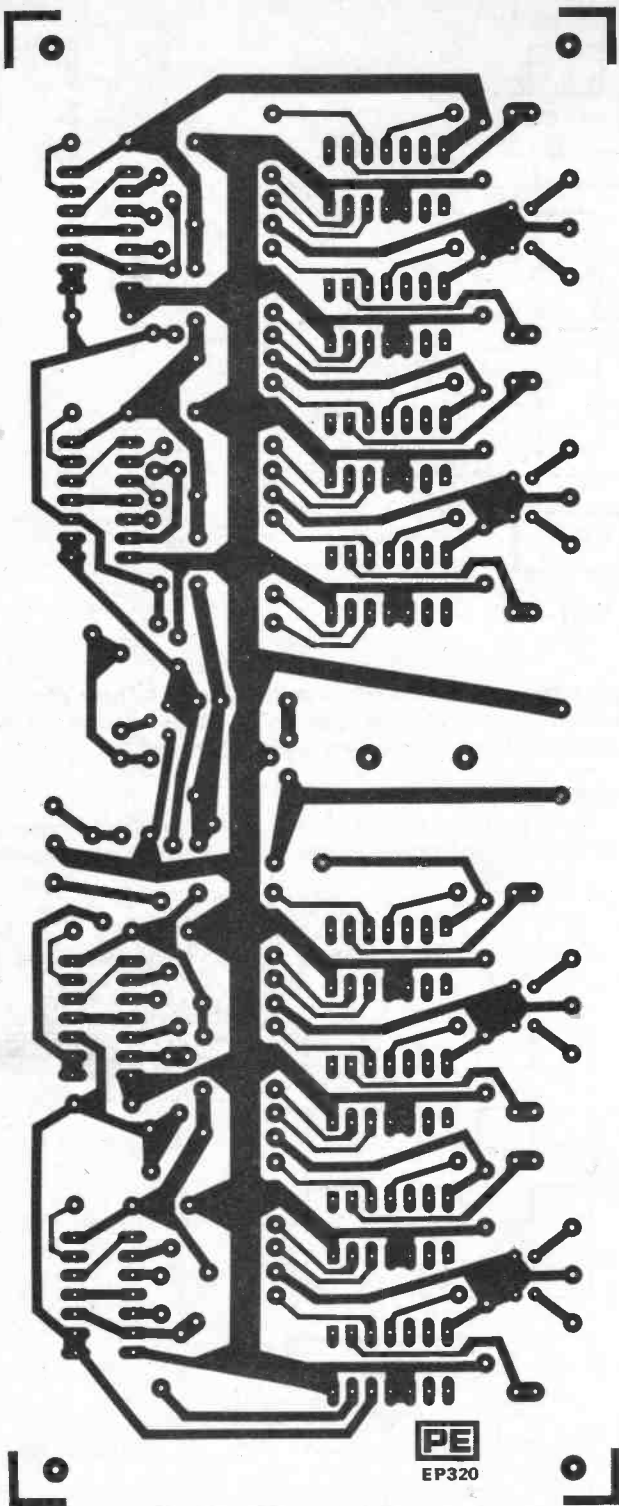


Fig. 8 Logic Board p.c.b.

supply points on the board. Slowly increase the voltage from zero, checking the output of the 5V regulator to ensure it stabilises between 4.8V and 5.2V when the supply voltage exceeds 8V. If this is satisfactory, reduce the voltage to zero, fit the i.c.s into their sockets, and repeat. The current supply to the board should be approximately 180mA.

To carry out any further checks an oscilloscope is necessary. Temporarily connect the speed control potentiometers VR1 to VR4 to their selected channels, the d.c. test supply, and a 20V a.c. supply. Connect the

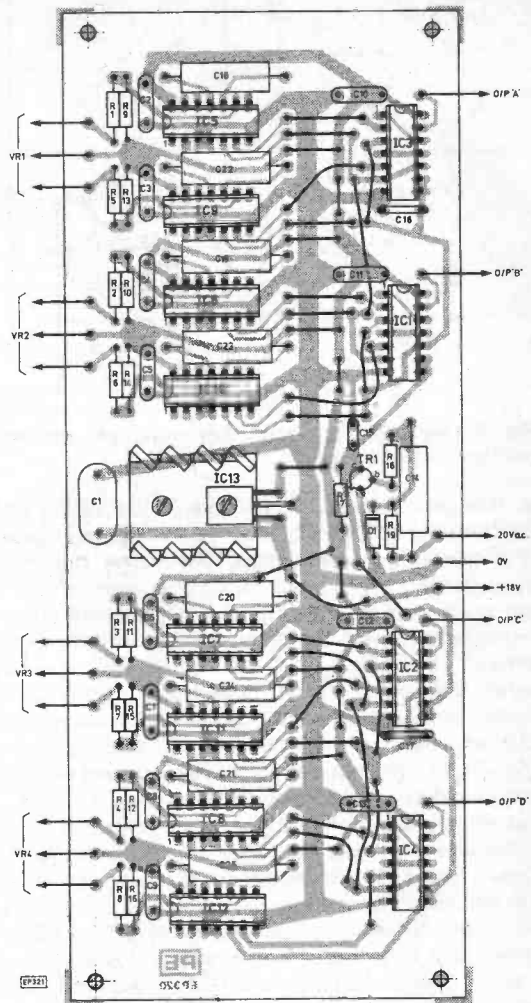


Fig. 9 Component layout

oscilloscope to each of the board output terminals, in turn, and observe the change in output as the potentiometers are rotated. This should be similar to that shown in Fig. 5, with negative pulses occurring only in one half cycle period, at any time. If the output becomes erratic when the potentiometer approaches the end of travel, the maximum time period of the monostables should be checked, and probably a lower value shunt resistor fitted. With the potentiometer at mid position, there should either be no output, or very short pulses, at the end of both positive and negative half cycles. If these are shorter than about 0.5ms, because of the time delay in the locomotive receivers, they can be ignored. Longer pulses should be corrected by increasing the timing periods.

OSCILLATOR AND AMPLIFIER CIRCUIT

This part of the circuit contains the control oscillators, the f.e.t. switches, and the amplifiers. The circuit diagram is shown in Fig. 10, and for simplicity has been drawn showing one channel, but is marked with the component numbers for

COMPONENTS

LOGIC BOARD

Resistors

R1 to R8	1.5k Ω
R9 to R16	100k Ω see text
R17	470
R18	4k7
R19	1k

$\frac{1}{4}$ W carbon film 5%

Potentiometers

VR1 to VR4	22k
------------	-----

Capacitors

C1	330n polyester or mylar
C2 to C13	100n ceramic disc 20v
C14	1.0 μ polyester
C15	10n mylar
C16	1.0n mylar or ceramic
C17	1.0n mylar or ceramic
C18 to C25	1.0 μ polyester

Semiconductors

IC1 to IC4	7402
IC5 to IC12	74121
IC13	5V regulator, TO126 case, TDA 1405, or similar
TR1	BC 108, or similar
D1	5V6 400mW Zener diode

RECEIVER BOARDS

Resistors

R1	47k			
R2	1k			
R3	10k			
R4	10k			
R5	10k			
R6	1M			
	A	B	C	D
R7	47k	39k	33k	27k
R9	22k	18k	15k	1
R10	100k			
R11	3k9			
R12	10k			
R13	12k			
R14	1k			
R15	10k			
R16	2k2			
R17	47			
R18	1k			

All $\frac{1}{4}$ W 5% carbon film

Capacitors

C1	2n2	mylar
C2	10 μ	35V tantalum
C3	10p	polystyrene
C4	330p	polystyrene 5%
C5	330p	polystyrene 5%
C6	680p	polystyrene 5%
C7	1n	mylar
C8	10n	mylar
C9	1 μ	35V tantalum
C10	10	35V tantalum
C11	10n	mylar
C12	10n	mylar
C13	1 μ	35V tantalum

AMPLIFIER/OSCILLATOR BOARD

Resistors

R20	12k
R21	10k
R22	8k2
R23	6k8
R24	12k
R25	10k
R26	8k2
R27	6k8
R28 to R31	270
R32 to R35	1M
R36 to R47	47k
R48 to R51	100k
R52, R53	10k
R54 to R57	2k2
R58, R59	1k
R60	4k7
R61 to R63	10k
R64	2.7

$\frac{1}{4}$ W carbon film 5%

Potentiometers

VR5 to VR12	4k7
VR13 to VR16	470
VR17	10k

miniature preset, vertical mounting

Capacitors

C26 to C33	1n polystyrene
C34 to C41	10n mylar or polyester
C42 to C45	1n mylar or ceramic
C46 to C49	10n mylar or polyester
C50, C51	100n mylar or ceramic disc
C52	470 μ 10V electrolytic
C53	10n mylar of polyester
C54	1n mylar or ceramic
C55	680n mylar or polyester
C56	100n mylar or polyester
C57	1 μ polyester 250V
C58	330n mylar or polyester
C59	100n mylar or ceramic disc

Semiconductors

IC14 to IC18	741
IC19	LM380
IC20	12V Regulator, TDA1412, TO126 case
TR2 to TR5	2N3819
TR6 to TR9	BC108A or similar
TR10 to TR13	2N3819
D1 to D4	1N914 general purpose silicon diode

POWER SUPPLY

Transformers

T1	20V. 55VA minimum
T2	12V to 14V. 500mA minimum
T3	18V to 24V. 30mA minimum

Choke

L1 1mH to 2mH $\frac{3}{8}$ in. or $\frac{1}{2}$ in. dia. 2 in. length ferrite rod. 24 s.w.g. enamelled copper wire

Resistor

R65	To suit indicator lamp
-----	------------------------

Capacitors

C60	1500 μ 25V electrolytic
C61	47n 300V a.c. rating

Miscellaneous

REC 1 1A 100V S1 Double pole, single throw. 240V a.c. 1A Panel mounting fuse holders, and fuses. FS1-1A FS2-100mA FS3-50mA Indicator lamp unit miniature circuit breaker 2A (R.S. 338-333), knobs 4 off, cabinet feet, cabinet.

Semiconductors

D1 to D8	General purpose silicon diode, 1N914, 1N4148, etc.
D9	12V 400mW Zener diode, BZY88, etc.
IC1	748 8 pin d.i.l.
IC2	741 8 pin d.i.l.
IC3	Darlington optoisolator RS 307-963, 897
CSR1	TAG302/400

Choke

L1	14mm pot core Mullard, FX2236. 34s.w.g. enamelled copper wire
----	---------------------------------------------------------------

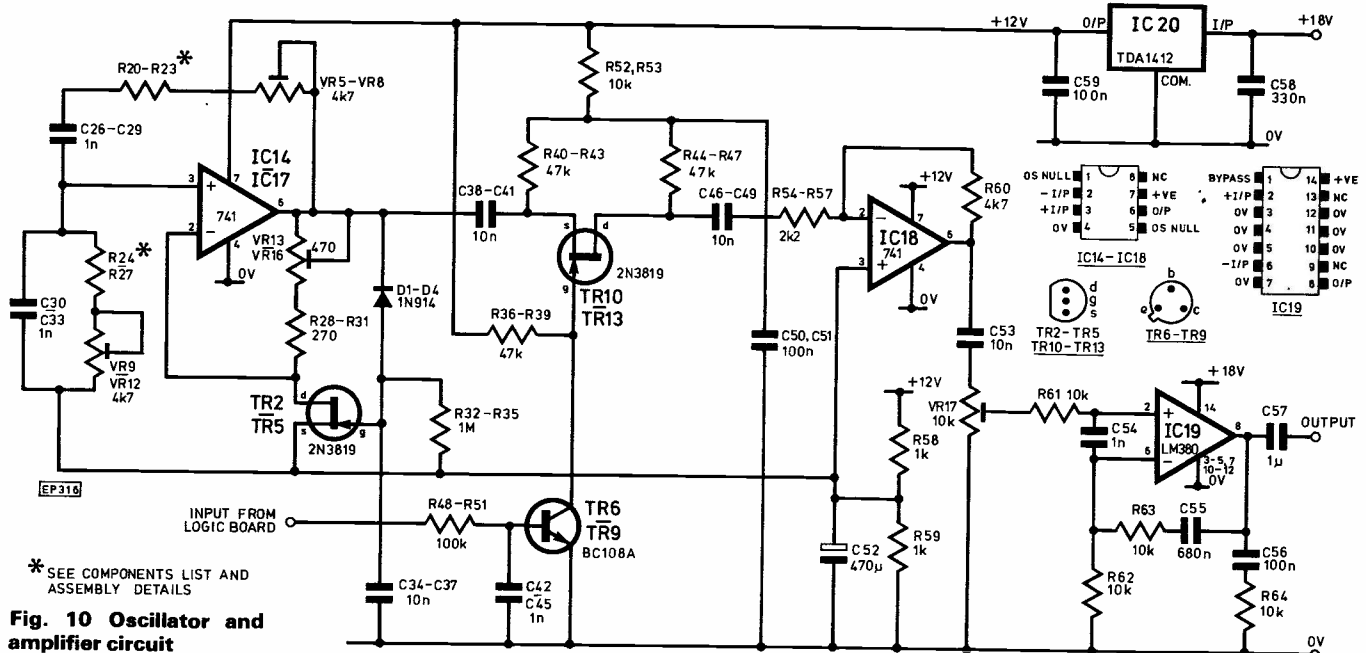


Fig. 10 Oscillator and amplifier circuit

all channels. In the following explanation, only the channel with the lowest component reference numbers is referred to.

IC14 is connected as an oscillator, and TR6 with TR10 form a switch in its output, controlled by the logic circuit. The outputs from the four oscillators are combined at the input of IC18, which adds or mixes them. IC19 is the output stage amplifier, which delivers the combined signal on to the rails.

The requirements for the oscillator used in this circuit are that it should give a sinusoidal output and have a low temperature drift. Several types were tested, but the Wien bridge gave the best results, and is used, but it is less simple than some of the alternatives. The basic circuit for the oscillator is shown in Fig. 11, and the frequency of oscillation is given by:

$$f_o = \frac{1}{2\pi RC} \text{ Hz}$$

Where R and C are the values of the resistor and capacitor in the two arms of the bridge.

The disadvantages of this circuit are that the impedance of the two arms of the bridge should be kept in balance, that is adjusted together, and that for a stable output the amplifier gain has to be exactly three.

The first appears to cause little difficulty, as long as the two potentiometers used for frequency adjustment are seen to be in similar positions.

For the second point, referring again to Fig. 12, the voltage gain for the amplifier in this configuration, will be given by:

$$A_v = \frac{R_1 + R_2}{R_2}$$

When $A_v = 3$, $R_1 = 2R_2$.

Unfortunately, the use of fixed value resistors is not accurate enough, so some form of automatic gain control must be used. R2 is replaced by an f.e.t. and its gate voltage is derived, through a diode, from the peak negative swing of the oscillator output. If the oscillator output increases, the f.e.t. gate voltage is driven more negative, increasing its effective drain to source resistance, so reducing the amplifier gain. R1 has been replaced by a fixed and a variable resistor, to allow for variations in f.e.t. characteristics.

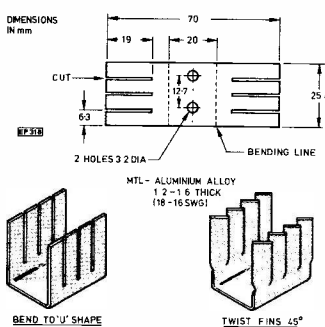


Fig. 11 Heat sink constructional details for the 5V regulator.

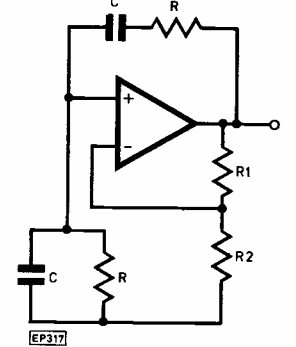


Fig. 12 (Right) Basic oscillator circuit

Referring to Fig. 10, the oscillator output is connected by C38 to the switching stage. The input from the logic circuit connects to the base of TR6, and its collector is connected to the gate of TR10. When the logic input is high, TR6 is driven on, so that the gate of TR10 is negative of its drain and source voltage. TR10 will then present a high impedance in the signal path, between C38, and C46. When the logic input is low, TR6 is turned off, TR10 gate increases to the same voltage as that of its source and drain, so its impedance falls, typically to about 250.

The control signals from the four channels are combined in the summing amplifier, IC18, which has a voltage gain of about 1.5.

The combined signal is then passed to the output stage, by way of C53 and VR17. The output amplifier, IC19, is a standard audio amplifier, to give a low impedance signal drive on to the rails. It has an internally connected negative feedback circuit and a voltage gain of 50. This gain is too high in this application, and R61 R62 R63 C54 and C55 form an additional feedback loop, to reduce the gain to less than 2. R64 and C56 reduce the possibility of r.f. instability.

IC20 is a 12V regulator and supplies the oscillators and the summing amplifier. The output amplifier is supplied directly from the unregulated supply.

Next Month: More construction and setting up procedure




PATENTS REVIEW...

Copies of Patents can be obtained from :
 the Patent Office Sales, St. Mary Cray, Orpington, Kent Price 95p each

MOUNTING CAR SPEAKERS

Although the idea claimed by two Swedish inventors Per Persson and Leo Koppelomaki, in recent British old law patent No 1 555 409, is hardly a world shattering invention, it could stimulate a useful train of thought for electronic hobbyists. As the inventors so rightly comment, it is always awkward to fit a stereo pair of loudspeakers in a motor car. If mounted on the rear window shelf they will play too loud for the back seat passengers and if mounted in the side doors they will beam their sound too low for ideal listening. The ideal position, argue the Swedes is the roof.

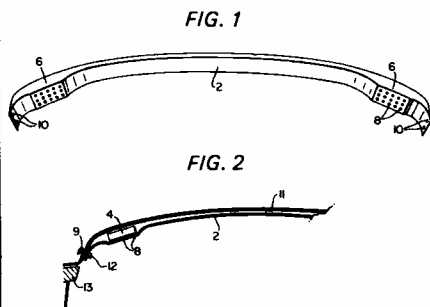

But how to effect easy fitting? The proposed answer is a cross beam moulded to follow the contours of the car roof, or of sufficiently flexible material to follow it. In the drawings the cross beam 2 has a box chamber 6 at each end in which a loudspeaker 4 is mounted to beam sound out through grille 8. The cross beam can be either open at the top and of U cross section, or closed at the top to provide a sealed acoustic cavity. In either case acoustic damping material is ideally loaded into the beam interior.

To fit the beam it is held loosely against the car roof and moved backwards and forwards until an ideal position is found for stereo imaging and sound balance between front and rear passengers. The beam is then secured to the roof by drilling holes at 10, and bolting at 9, 12.

AID FOR THE DUMB

Atari Inc. of California has patented (BP 1 550 996), issued under the old laws) a hand-held communications aid for the dumb. This can be used either for direct face-to-face "conversation" or over the telephone.

Figure 1 shows how the device resembles a calculator with an i.e.d. to l.c.d. display at one end of an alpha-numeric keypad, so that the device is handled like a torch. Words typed into the keypad move across the display to spell out a message for the benefit of anyone looking at it. An alert tone at the start of the message draws attention to the display.

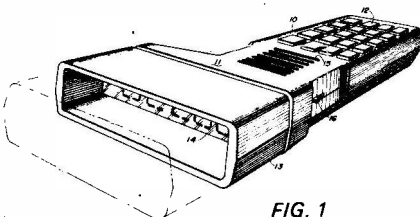


Figure 2 shows the basic circuit layout. Alpha-numeric keypad (with 20 dual function keys) is timed by oscillator 23. The column and row information is encoded at 24, processed at 27 and stored in accumulating register 28. This register drives ROM 29 and display 14. Blanking logic 32 extinguishes the display after a few seconds unless shunted by switch 34.

In many respects therefore the circuit resembles that used in some modern calculators. However the idea of interfacing with a telephone line appears more novel.

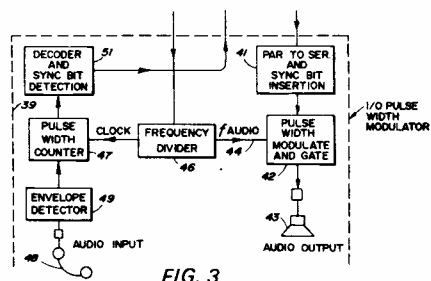
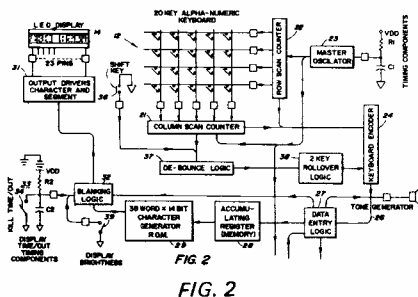


Figure 3 shows an interface for converting the digitally encoded keypad output into a pulse-width modulated format for transmission over normal telephone lines. A parallel-to-serial converter and synchronisation bit inserter 41 drives a pulse width modulation and gating unit 42 with an audio output 43 which couples acoustically with a telephone handset. Simultaneously, frequency divider 46 (driven by oscillator 23) provides an audio frequency and clocks a pulse width counter 47 which receives the audio output 48 from the telephone. Detector 49 senses the envelope width which is decoded at 51 to drive display 14 through logic 27.

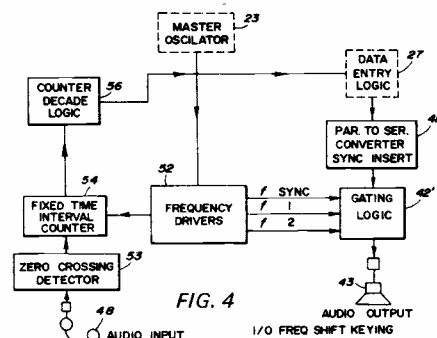


Figure 4 shows an alternative interface, based on frequency shift keying. With either interface circuit an alpha numeric message keyed into the local unit reads out on the remote display and a message keyed into the remote pad reads out on the local display, thereby enabling pairs of dumb people to communicate by telephone. The idea behind the invention could perhaps stimulate electronic hobbyists to experiment with the modification of existing equipment to interface with a telephone line by acoustic coupling of the type permitted by the British Post Office.

Readout...

A selection from our Postbag

Readers requiring a reply to any letter must include a stamped addressed envelope. Opinions expressed in Readout are not necessarily endorsed by the publishers of Practical Electronics.

Iron Controller

Sir—With regard to the article in your February edition of *Practical Electronics* relating to 'Soldering Iron Controller', we regret to inform you that we find this article somewhat detrimental to soldering equipment manufacturers generally and Adcola Products Limited in particular. The two illustrations on pages 30 and 32 bear an almost exact resemblance to a soldering station manufactured by Adcola Products Limited. This soldering station, known as the Unit 101, incorporates the features which the writer indicated controlled soldering equipment does not have, and in fact the Unit 101 has many other features that reduce the problems which modern soldering has created with regard to voltage and temperature sensitive components.

We should like to draw your attention to the fact that the method of controlling our Unit 101 is by proportional control using a zero-crossing i/c. We would also argue against the sensing device suggested, namely a diode. This diode is to be positioned against the tube of the tool where the heat does not exceed 150°C. The diode would therefore have the major part of its surface exposed to free air and only line contact with the soldering iron

tube. But more important is the heat limitation of 150°C; to obtain this, the diode will have to be positioned at a reasonable distance from the bit face. This will, in our opinion, cause a considerable time lag from drop in bit/tip temperature until the soldering iron tube reflects this temperature drop and so the control circuit can increase the power supply to the heating element. Adcola Products Limited uses a thermocouple positioned in the end of the tube, immediately behind the bit/tip face.

By use of an illustration which is so comparable to our Unit 101, your readers may feel that your researchers have based their findings of circuits on a Unit 101. Obviously this is not the case.

R. T. Lamb,
Managing Director,
Adcola Products Limited.

The resemblance between our illustrations and the Adcola 101 was completely unintentional and we would not like readers to gain a wrongful impression of any Adcola product as a result. We have a high regard for most soldering products available in this country and appreciate the extensive design and development work that is behind them. As you have pointed out, the comments in the article were not based on the Adcola 101 unit.—Ed.

Club Meetings

Sir—As you know, the British Amateur Electronics Club is the only national amateur electronics club in this country, and we have an obligation to offer all the help we can to our members, particularly beginners. We have a special Beginners' Section and also a very large library of technical books and magazines which are available to members free of charge (apart from postage), and many of your advertisers are allowing B.A.E.C. members special prices for their products.

However, there is one very important way in which we could help our members, and that is to provide meetings in various parts of the country, so that B.A.E.C. members can go to them and benefit by being able to meet and work with other electronics enthusiasts. We have held meetings at Penarth, S. Glam, since we started in 1966, but whilst several of our members have tried to start meetings in other parts of the country, the main snag has been obtaining a suitable room at a reasonable charge.

I am writing to ask if you would be kind enough to ask in your popular magazine, *Practical Electronics*, for your readers who belong to local Electronics Groups to let me know if they would be willing for B.A.E.C. members who live nearby to go to their meetings. Naturally, our members would be prepared to pay an affiliation fee, and I would be happy to send further information to any of your readers who may be kind enough to contact me regarding this matter.

If suitable arrangements can be made this would benefit both the local Groups and the B.A.E.C., and I would be grateful for any help you are able to give to help amateur electronics.

Cyril Bogod, B.A.E.C.,
26 Forrest Road,
Penarth, S. Glamorgan.



BOOK REVIEWS

PERSONAL COMPUTING

by Jim Huffman

Published by Reston Publishing Co. Inc.

Available from Prentice/Hall International
262 pages, 180 x 240 mm. Price £7.75

A thorough and concise survey of the 6800 microprocessor family, which is pleasantly presented and easy to read. The book takes you through a brief history of computing, which serves the purpose of defining the all important differences between mainframe and home computing. Assuming you have a fundamental knowledge of electronics, the book steers you to an understanding of the hardware involved, I/O, peripheral interfacing principles and memory. Even in the absence of a knowledge of electronics in depth, it should be possible to follow the logic in Chapter 7 *Putting It All Together With Programming*, although it is assumed you have the use of a machine at this stage.

To correct the situation if you have no computer, Chapter 6 gives details for the construction of a small system called the PC-68, which comprises the common hexadecimal keypad and four seven-segment display format.

The appendices include a list of American personal computer manufacturers, numbering systems, an ASCII conversion table, and 78 pages of specification sheets for the 6800 family, including the MCM6830L7 MIKBUG/MINIBUG ROM data sheet giving the MIKBUG REV.9 listing.

The most outstanding feature of this book is undoubtedly the chapter on building your own system with its "talk-through" of the design stages, and argument for the choice of the 6802 micro'. Good value for money by today's standards.

M.A.

POINTS ARISING

4 CHANNEL DIGITAL MEMORY (March 1980)


There should be a link between pin 1 (IC12) and pin 13 (IC15). It has been suggested that a 10nF capacitor be connected from pin 3 to ground and experimental values of from 10-100nF be connected from pin 11 to ground. These capacitor additions apply to IC16.

Your Commodore PET System

The Commodore PET is Britain's best selling microcomputer and the most popular choice in every field:-

- * In Education for teaching Computer Science and as a teaching aid for other subjects.
- * In Science and Engineering for solving problems and for monitoring laboratory equipment.
- * In Business the PET system can be put to a wide range of functions including Payroll, Accounting, Statistical Analysis, Stock Control and Word Processing.

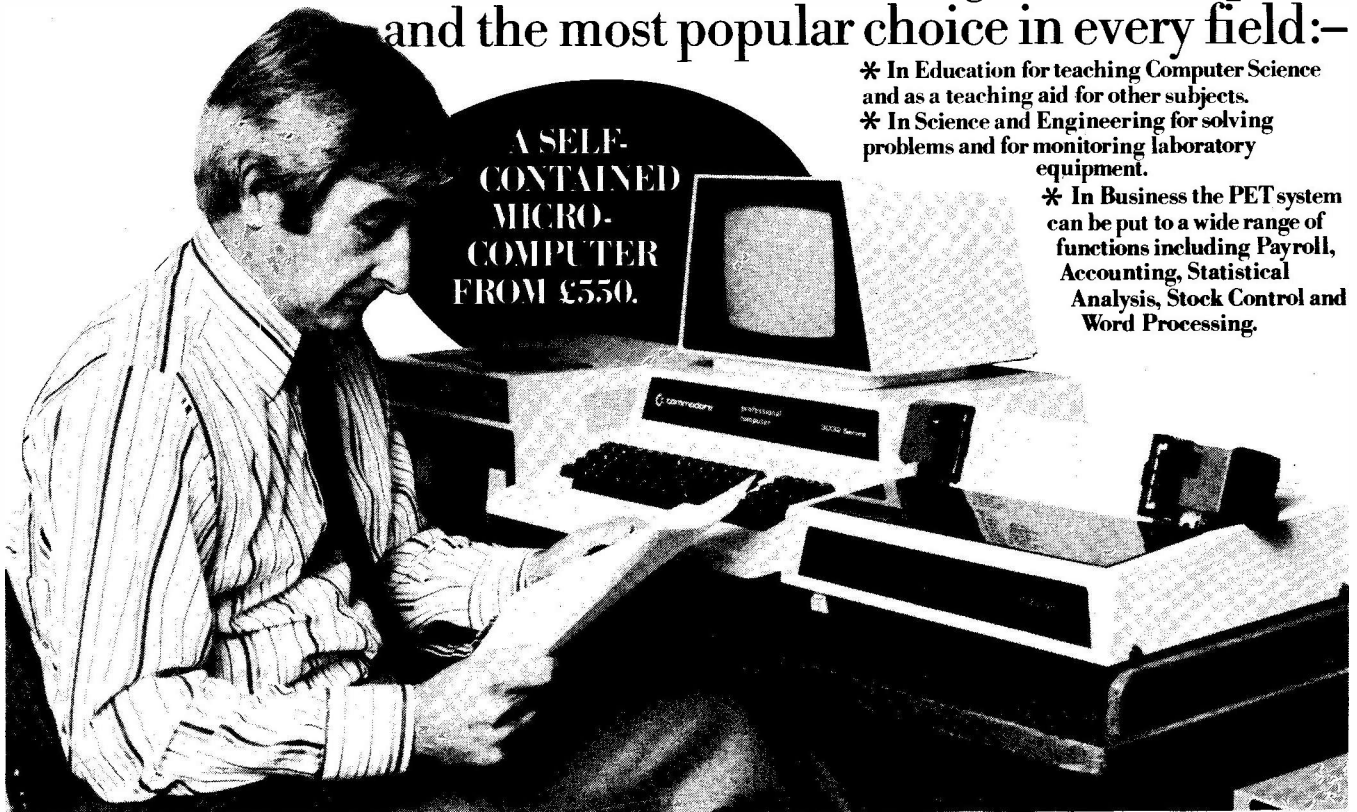A SELF-CONTAINED MICRO-COMPUTER FROM £550.



Not least of its attractions is the price of a PET - from £550 for a self contained unit, to under £2,500 for the complete system including Floppy Disk Unit and high-speed Printer. Ask your nearest Commodore dealer below for details about Commodore hardware, software and training courses.

Our Dealer* Network

LONDON

Capital Computer Systems, W1. 637 5551
ACE (by Top TV Ltd), SW1. 7301795
Micro Computer Centre, SW14. 876 6609
Logic Box Ltd, SW1. 222 1122
Sumlock Bondain Ltd, EC1. 250 0505
Da Vinci Computers Ltd, NW4. 202 9630
L & J Computers, NW9. 204 7525
Adda Computers, W1. 408 1611
CSS Business Equipment Ltd, E8. 254 9293
Advanced Management, EC2. 638 9319
Metyclean Ltd, SW1. 828 2511
Microcomputation, Southgate. 882 5104
T.L.C. World Trading Ltd, WC2. 839 3894

HOME COUNTIES

Orchard Electronics Ltd, OXON. 0491 35529
D. L. Chittenden Ltd, CHESHAM, 4441
J. R. Ward Computers Ltd, MILTON KEYNES, 562850
Dataview Ltd, COLCHESTER, 78811
South East Computers Ltd, HASTINGS, 426844
Symtec Systems Ltd, SOUTHAMPTON, 38868
Alphascan Ltd, BANBURY, 75606
Super-vision, SOUTHAMPTON, 774023
Millhouse Designs Ltd, ALTON, (042) 050374
Micro Facilities Ltd, MIDDX, 979 4546
DDM, BRENTWOOD, 230480
Stuart R. Dean Ltd, SOUTHEND, 62707
Alpha Business Systems, HERTFORD, 57423
HSV Microcomputers, BASINGSTOKE, 62444
HSV Microcomputers, SOUTHAMPTON, 22131
RUF Computers (UK), BURGESS HILL, 45211
Wego Computers Ltd, CATERHAM, 49235

T. & V. Johnson, CAMBERLEY, 62506
T. & V. Johnson, OXFORD, 721461
Petalect Electronic Services Ltd, WOKING, 23637/21776
Business Electronics, SOUTHAMPTON, 738248
Amplicon Micro Systems Ltd, BRIGHTON, 562163
Bromwall Data Services Ltd, HATFIELD, 60980/64840
MMS Computer Systems, BEDFORD, 40601
Isher-Woods, LUTON, 416202
Sumlock Bondain, NORWICH, 26259
CSE (Computers), READING, 61492
Oxford Computer Systems, WOODSTOCK, 811976

MIDLANDS & STH. HUMBERSIDE

Taylor Wilson Systems Ltd, KNOWLE, 6192
Betos (Systems) Ltd, NOTTINGHAM 48106
Holbrook Business Systems, DERBY, 368088
Lowe Electronics Limited, MATLOCK, 2817
Davidson-Richards Ltd, DERBY, 366803/4
Arden Data Processing, LEICESTER, 22255
Teldata Ltd, STOKES-ON-TRENT, 813631
C.S.M. Computer Systems, BIRMINGHAM, 360 6264

Business & Leisure Microcomputers, KENILWORTH, 512127
Caddis Computer Systems Ltd, HINCKLEY, 613544
Allen Computers, GRIMSBY, 40568
CPS (Data Systems) Ltd, BIRMINGHAM, 707 3866
Camden Electronics, BIRMINGHAM, 773 8240
Cliffstock (Computer Systems) Ltd, WOLVERHAMPTON, 24221

YORKSHIRE & NTH. HUMBERSIDE

Microprocessor Services, HULL, 0482 23146
Microware Computers, HULL, 562107
Computer Workshop, LEEDS, 788466
Hallam Computer Systems Ltd, SHEFFIELD, 663125
Ackroyd Typewriters Ltd, BRADFORD, 31835
Datron Micro Centre, SHEFFIELD, 585490
Yorkshire Electronics Service Ltd, MORLEY, 522181
Sheffield Computer Centre, SHEFFIELD, 53519

NORTH EAST

Dyson Instruments, DURHAM, 66937
Currie & Maughan, GATESHEAD, 774540
Wards Office Supplies, GATESHEAD, 605915

Tripont Associated Systems, SUNDERLAND, 73310
Newcastle Computer Services, NEWCASTLE UPON TYNE, (0632) 615325

SOUTH WALES & WEST COUNTRY

Computer and Design, BROADSTONE, 0202 697341
A. C. Systems, EXETER, 71718
Computer Supplies (Swansea), SWANSEA, 290047
Sigma Systems Ltd, CARDIFF, 21515
Devon Computers, PAIGNTON, 526303
Bristol Computer Centre, BRISTOL, 23430
J. A. D. Integrated Services, PLYMOUTH, 62616
Sumlock Tabdown Ltd, BRISTOL, 26685
Radan Computational Ltd, BATH, 318483
T. & V. Johnson Ltd, BRISTOL, 422061

NORTH WEST & NORTH WALES

B. & B. Computers Ltd, BOLTON, 26644
Megapalm Ltd, CARNFORTH, 3801
Tharstern Ltd, BURNLEY, 38481
Fylde Business Machines Ltd, PRESTON, 731901
Preston Computer Centre, PRESTON, 57684
RPL Microsystems, DOUGLAS, 4247/8

LIVERPOOL

Microdigital, LIVERPOOL, 227 2535
Rockliff Brothers Ltd, LIVERPOOL, 521 5830

MANCHESTER

Cytek (UK) Ltd, MANCHESTER, 832 7604
Executive Reprographic Ltd, MANCHESTER, 228 1637
Sumlock Manchester Ltd, DEANSGATE, (0618) 834 4233
Computer Workshop, MANCHESTER, 832 2269
Professional Computer Services Ltd, OLDHAM, 061-624 4065
D. Kipping Ltd, SALFORD, 834 6367
Catlands Computers Ltd, 0625 527166

SCOTLAND

Microcentre, EDINBURGH, 225 2022
Thistle Computers, KIRKWALL, 3140
McAllister Business Equipment, EDINBURGH, 336 2402

IRELAND

Softech Ltd, DUBLIN, 784739
Medical and Scientific, LISBURN, 77533

*This is a list of dealers participating in associated advertising and not a full list.


Commodore

We made small computers big business.

Commodore Information Centre, 360 Euston Road, NW1 3BL. 01-388 5702

Simply ahead . .

ILP'S NEW GENERATION OF HIGH

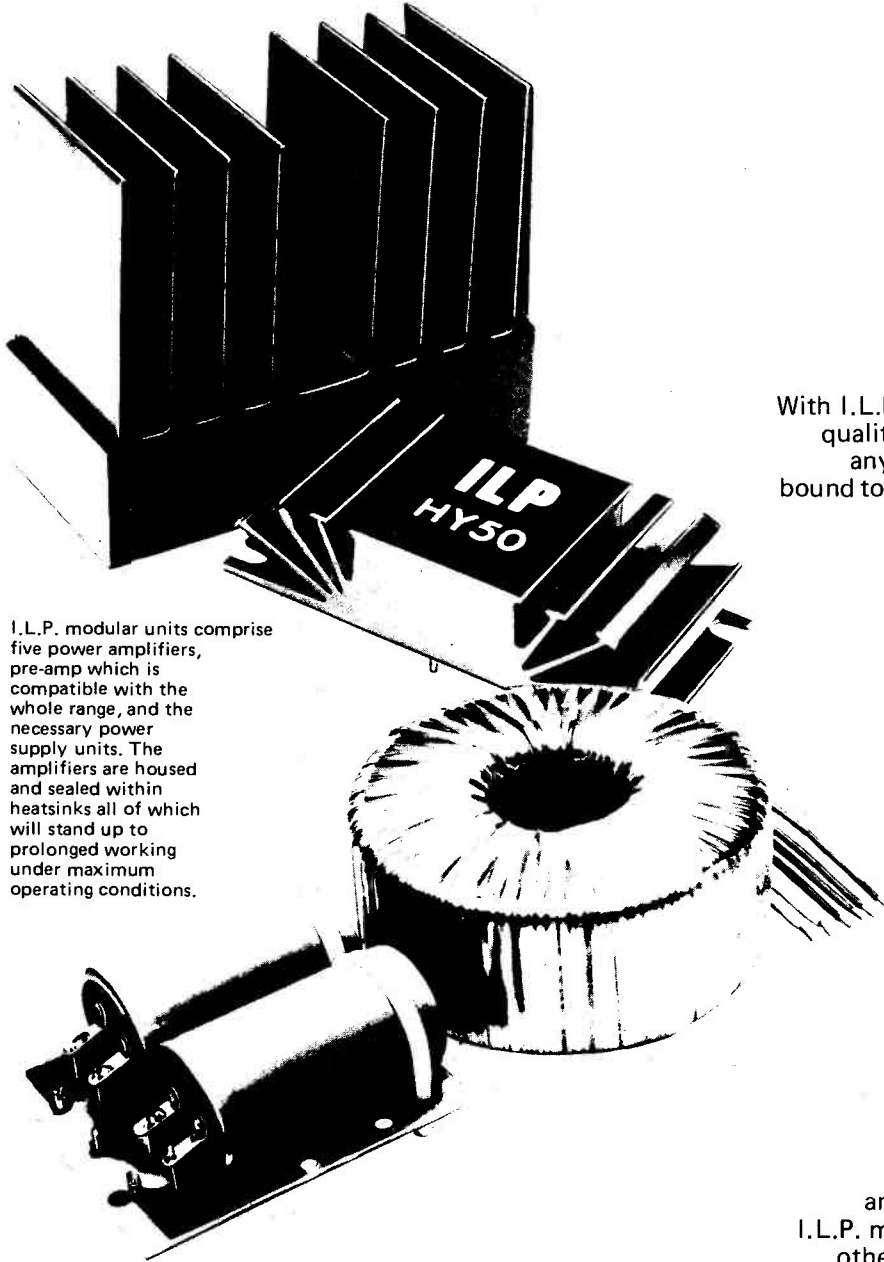

I.L.P. modular units comprise five power amplifiers, pre-amp which is compatible with the whole range, and the necessary power supply units. The amplifiers are housed and sealed within heatsinks all of which will stand up to prolonged working under maximum operating conditions.

With I.L.P. performance standards and quality already so well established, any advances in I.L.P. design are bound to be of outstanding importance – and this is exactly what we have achieved in our new generation of modular units. I.L.P. professional design principles remain – the completely adequate heatsinks, protected sealed circuitry, rugged construction and excellent performance. These have stood the test of time far longer than normally expected from ordinary commercial modules. So we have concentrated on improvements whereby our products will meet even more stringent demands such, for example, as those revealed by vastly improved pick-ups, tuners, loudspeakers, etc., all of which can prove merciless to an indifferent amplifier system. I.L.P. modules are for laboratory and other specialised applications too.



**PRODUCTS OF THE WORLD'S FOREMOST SPECIALISTS
IN ELECTRONIC MODULAR DESIGN**

ALSO AVAILABLE FROM SELECTED STOCKISTS

and staying there

PERFORMANCE MODULAR UNITS

HY5 PRE-AMPLIFIER

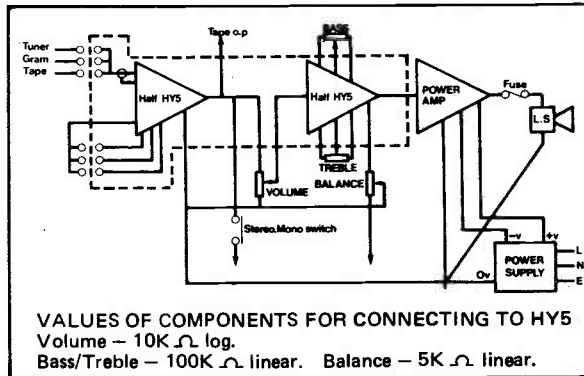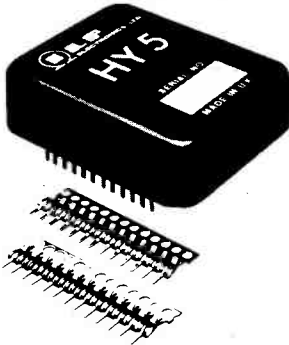


VALUES OF COMPONENTS FOR CONNECTING TO HY5
 Volume - 10K Ω log.
 Bass/Treble - 100K Ω linear. Balance - 5K Ω linear.

The HY5 pre-amp is compatible with all I.L.P. amplifiers and P.S.U.'s. It is contained within a single pack 50 x 40 x 15 mm, and provides multi-function equalisation for Magnetic/Ceramic/Tuner/Mic and Aux (Tape) inputs, all with high overload margins. Active tone control circuits; 500 mV out. Distortion at 1KHz - 0.01%. Special strips are provided for connecting external pots and switching systems as required. Two HY5's connect easily in stereo. With easy to follow instructions.

£4.64 + 74p VAT


THE POWER AMPLIFIERS

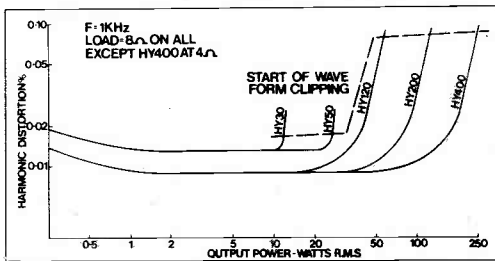

Model	Output Power R.M.S.	Distortion Typical at 1KHz	Minimum Signal/Noise Ratio	Power Supply Voltage	Size in mm	Weight in gms	Price + V.A.T.
HY30	15 W into 8 Ω	0.02%	80dB	-20 -0- +20	105x50x25	155	£6.34 + 95p
HY50	30 W into 8 Ω	0.02%	90dB	-25 -0- +25	105x50x25	155	£7.24 + £1.09
HY120	60 W into 8 Ω	0.01%	100dB	-35 -0- +35	114x50x85	575	£15.20 + £2.28
HY200	120 W into 8 Ω	0.01%	100dB	-45 -0- +45	114x50x85	575	£18.44 + £2.77
HY400	240 W into 4 Ω	0.01%	100dB	-45 -0- +45	114x100x85	1.15Kg	£27.68 + £4.15

Load impedance - all models 4 - 16 Ω
 Input sensitivity - all models 500 mV
 Input impedance - all models 100K Ω
 Frequency response - all models 10Hz - 45KHz - 3dB

THE POWER SUPPLY UNITS

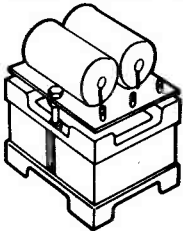

I.L.P. Power Supply Units are designed specifically for use with our power amplifiers and are in two basic forms - one with circuit panel mounted on conventionally styled transformer, the other with toroidal transformer, having half the weight and height of conventional laminated types.

PSU 30	$\pm 15V$ at 100ma to drive up to five HY5 pre-amps	£4.50 + £0.68 VAT
PSU 36	for 1 or 2 HY30's	£8.10 + £1.22 VAT
PSU 50	for 1 or 2 HY50's	£8.10 + £1.22 VAT
PSU 70	with toroidal transformer for 1 or 2 HY120's	£13.61 + £2.04 VAT
PSU 90	with toroidal transformer for 1 HY200	£13.61 + £2.04 VAT
PSU180	with toroidal transformer for 1 HY400 or 2 x HY200	£23.02 + £3.45 VAT

NO QUIBBLE
5 YEAR GUARANTEE

7-DAY DESPATCH ON ALL ORDERS

INTEGRAL HEATSINKS

BRITISH DESIGN AND MANUFACTURE

FREEPOST SERVICE - see below

★ ALL U.K. ORDERS DESPATCHED POST PAID

HOW TO ORDER, USING FREEPOST SYSTEM

Simply fill in order coupon with payment or credit card instructions. Post to address as below but do not stamp envelope - we pay postage on all letters sent to us by readers of this journal.



ELECTRONICS LTD.
 FREEPOST 2 Graham Bell House, Roper Close,
 Canterbury, Kent CT2 7EP.
 Telephone (0227) 54778 Telex 965780

Please supply
 Total purchase price £.....
 I enclose Cheque Postal Orders International Money Order
 Please debit my Account/Barclaycard Account No.
 NAME
 ADDRESS
 Signature

BAKER LOUDSPEAKERS
"SPECIAL PRICES"

Post £1.50 each

Model	Ohms	Size in	Power Watts	Type	Our Price
Major		12	30	Hi-Fi	£12
Deluxe Mk II	4, 8, 16	12	15	Hi-Fi	£14
Superb	8, 16	12	30	Hi-Fi	£22
Auditorium	8, 16	12	45	Hi-Fi	£20
Auditorium	8, 16	15	60	Hi-Fi	£30
Group 35	8, 16	12	40	PA	£12
Group 45	4, 8, 16	12	45	PA	£15
Group 50	4, 8, 16	12	60	PA	£20
Group 50	8, 16	15	75	PA	£30
Group 75	4, 8, 16	12	75	PA	£24
Group 100	8, 16	12	100	PA	£29
Group 100	8, 16	15	100	PA	£35
Disco 100	8, 16	12	100	Disco	£29
Disco 100	8, 16	15	100	Disco	£35

4 CHANNEL TRANSISTOR MIXERS
Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt battery operated with switch for four channel mono or two channel stereo working. **£8.00**

MINI MODULE BAFFLE KIT Post £1.
EMI 15 x 8 1/2 in. 3-way Loudspeaker System 5in. Bass, 5in. Middle, 3in. Tweeter; 3-way Cross-over & Ready Cut Baffle. Full assembly instructions supplied. Response 60 to 20 000 c.p.s. 12 watt RMS 8 ohms £10.95 per kit. Two kits £20. Suitable Bookshelf Cabinet £9.50 each. Post £1.60.



SINGLE RECORD PLAYER
Fitted with auto stop, stereo cartridge. Baseplate. Size 11 x 8 1/2 in. Turntable Size 7in. diameter a.c. mains 240V 3 speeds plays all size records. **£9.95**
Two for £18. Post £1 one or two.

NEW BSR SINGLE PLAYER £24.50
Model P182 3-speeds flared aluminium turntable. "S" shaped arm, cueing device, stereo ceramic cartridge.
S.S.R. De-Luxe Autochanger with stereo cartridge, plays all size records. Post £1.60 **£20.00**

BAKER 150 WATT ALL PURPOSE TRANSISTOR MIXER AMPLIFIER
Ideal for Groups, Disco, P.A. and Musical instruments. 4 inputs speech and music 4 way mixing. Output 4/8/16 ohm, a.c. Mains 240V. Separate treble and bass controls. 100 volt line model £14 extra **£85** Post £1.60



BAKER COMPACT 50 WATT AMPLIFIER
IDEAL FOR DISCOS, GROUPS, PUBLIC ADDRESS
Two inputs with volume controls. Master treble bass and volume controls. Suitable for all loudspeakers. **£65**. Post £1.60.

R.C.S. SOUND TO LIGHT DISPLAY MK II
Complete kit of parts with R.C.S. printed circuit. Three 1000W channels. Will operate from 200mV signal source. CABINET extra £4. **KIT = £18.00**

R.C.S. 10 WATT AMPLIFIER KIT
This kit is suitable for record players, tape play back, guitars, electronic instruments or small PA systems. Two versions are available. The mono kit uses 13 semiconductors. The stereo kit uses 22 semiconductors. Both kits have printed front panel and volume, bass and treble controls. Spec. 10W output into 8 ohms 7W into 15ohms. Response 20c.s to 30K.c.s. Size 9 1/2 x 3 x 2 in. A/C mains operated.
Mono kit **£12.50** Stereo kit **£20** Post 45p
Easy to build. Full instructions supplied

LOW VOLTAGE ELECTROLYTICS
1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p, 500mF 12V 15p; 25V 20p; 50V 30p; 1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p; 2000mF 40V 60p; 25V 42p; 2500mF 50V 62p; 3000 mF 25V 47p; 50V 65p; 2700mF 76V £1, 4700mF 63V £1.20; 25V 75p; 35V 85p; 5600mF 76V £1.75; 1200mF 76V 80p.

HIGH VOLTAGE ELECTROLYTICS
8/350V 22p 8-8/450V 50p 50-50/300V 50p
16/350V 30p 8-16/450V 50p 32-32/450V 75p
32/500V 75p 16-16/450V 50p 100-100/275V 65p
50/500V £1.20 32-32/350V 50p 150-200/275V 70p
MANY OTHERS IN STOCK

WOOD PLINTH CUT FOR B.S.R. £4.
Size: 16 x 14 1/2 x 3 1/2 in. Teak Veneered
METAL PLINTH CUT FOR B.S.R. £5.
OR GARRARD
Size: 16 x 14 x 3 in. £4. Silver or Black finish. Post £1.
TINTED PLASTIC COVERS ALL POST £1.60
Sizes: 14 1/2 x 12 1/2 x 3 in. £3.50, 16 x 14 x 3 1/2 in. £5.
15 1/2 x 13 1/2 x 4 in. £4. 17 1/2 x 9 1/2 x 3 1/2 in. £3.
14 1/2 x 14 1/2 x 2 1/2 in. Rosewood sides £4.
18 x 13 1/2 x 3 in. £6. 18 x 12 1/2 x 3 in. £6.
18 x 13 1/2 x 3 1/2 in. with stand up hinges £7.

R.C.S. LOW VOLTAGE STABILISED £2.95
POWER PACK KITS Post 45p
All parts and instructions with Zener diode printed circuit, rectifiers and double wound mains transformer input 240V a.c. Output voltages available 6 or 7, 5 or 9 12V d.c. up to 100mA or less. Size 3 x 2 1/2 x 1 1/2 in. Please state voltage required.

MAINS TRANSFORMERS ALL POST 75p each
250-0-250 70mA 6.3 2A £3.45
250-0-250 80mA 5.3V 3A 6.3V 1A £3.45
350-0-350 250mA 6.3V 5 amp, 6V 2A £12.50
300-0-300 120mA 2.6 3V 2A C T 6 3V 2A £8.50
220V 45mA 6.3V 2A £2.50
HEATER TRANS 6.3V 3A £2.1 amp £2.50
GENERAL PURPOSE LOW VOLTAGE Tapped outputs at
2A 3 4 5 6 8 9 10 12 15 18 24 and 30V £6.00
1A 6 8 10 12 16 18 20 24 30 36 40 48 60 £6.00
2A 6 8 10 12 16 18 20 24 30 36 40 48 60 £9.50
3A 6 8 10 12 16 18 20 24 30 36 40 48 60 £12.50
5A 6 8 10 12 16 18 20 24 30 36 40 48 60 £16.00
5 9 10 16V 1A £2.50 12V 100mA £1.30 12V 300mA £1.50.
12V 750mA £1.75 40V 2A tapped 10V or 30V £3.50.
10-0-10V 2A £3.40V 2A £3.50, 30V 5A 34V 2A C.T. £4.
2 x 18V 6A £11, 12-0-12V 2 amp £3.50, 25-0-25V 2 amp £4.50.
20-0-20V 1A £3.50, 30V 1A £3.30, 20V 1A £3.
9V 3 amp £3.50, 60V, 40V, 20V 1A £4, 150/15V 2 amp £3.75.
32-0-32V 61A £11, 9V 250mA £1.50, 30V 2 amp £3.50.
AUTO TRANSFORMERS 115V to 230V or 230V to 115V
150W £7; 250W £8; 400W £9; 500W £10.
CHARGER TRANSFORMERS input 200/250V for 6 or 12V
1 1/2 A £4.25, 3 amp £4, 4A £7.25.
FULL WAVE BRIDGE CHARGER RECTIFIERS. 6 or 12V outputs
1 1/2 A £6p; 4A £1.60. HALF WAVE 12V 1 1/2 A 35p.

BLANK ALUMINIUM CHASSIS, 18 s.w.g. 2 1/2 in. sides, 6 x 4 in. **95p**; 8 x 6 in. **£1.40**; 10 x 7 in. **£1.55**; 14 x 9 in. **£1.90**; 16 x 6 in. **£1.65**; 12 x 3 in. **£1.20**; 16 x 10 in. **£2.20**; 12 x 8 in. **£1.70**.
ALUMINIUM PANELS, 18 s.w.g. 6 x 4 in. 24p; 8 x 6 in. 36p; 10 x 7 in. 54p; 12 x 5 in. 50p; 12 x 8 in. 70p; 16 x 6 in. 70p; 14 x 9 in. 94p; 12 x 12 in. £1, 16 x 10 in. £1.16.
ALUMINIUM ANGLE BRACKET, 8 x 3 x 3 in. 25p.
ALUMINIUM BOXES, MANY OTHER SIZES IN STOCK
4 x 2 x 2 in. 86p; 3 x 2 x 1 in. 66p; 6 x 4 x 2 in. 95p; 8 x 6 x 3 in. £1.80; 9 x 4 x 4 in. £1.70; 10 x 7 x 3 in. £2.20; 12 x 8 x 3 £2.50.
THE "INSTANT" BULK TAP ERASER
Suitable for cassettes and all sizes of tape reels a.c. mains 240V **£7.50**
Leaflet SAE. Post 75p.
Head demagnetiser **£5.00**

RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, CROYDON, U.K.

Minimum post 30p. Access and Barclaycard Same day despatch Radio Books and Components Lists 20p Open 9-6 Sat. 9-5 (Closed Wednesday all day). Tel. 01-684 1665

Great new Crofton Treble

Self contained
MONITOR PCB

Complete with all leads and scan coil assembly. Tubes and transformers available separately from stock.
£35.50

Self contained
10" MONITOR

The unbeatable 10" Aztec, complete and ready to go.
£85.00

THE SOUGHT AFTER
★ **OHIO SUPERBOARD II** ★
(All prices ex VAT and P&P) Fully constructed at **£188.00**

CROFTON ELECTRONICS

Crofton Electronics Limited, 35 Grosvenor Road, Twickenham, Middlesex. Tel: 01 891 1923

LOW POWER SCHOTTKY TTL - EX STOCK

Device	Price	Device	Price	Device	Price
74LS00	13p	74LS85	80p	74LS174	65p
74LS01	13p	74LS86	36p	74LS175	65p
74LS02	12p	74LS90	40p	74LS190	100p
74LS03	13p	74LS93	70p	74LS191	100p
74LS04	14p	74LS95	85p	74LS192	100p
74LS05	25p	74LS107	40p	74LS193	100p
74LS08	30p	74LS109	50p	74LS196	100p
74LS09	20p	74LS112	50p	74LS221	100p
74LS10	16p	74LS113	50p	74LS244	220p
74LS11	23p	74LS114	50p	74LS245	280p
74LS12	25p	74LS123	80p	74LS247	100p
74LS13	30p	74LS125	30p	74LS248	100p
74LS14	40p	74LS126	30p	74LS249	90p
74LS20	17p	74LS132	50p	74LS251	90p
74LS21	21p	74LS136	45p	74LS273	185p
74LS26	30p	74LS138	75p	74LS279	50p
74LS27	15p	74LS139	80p	74LS283	100p
74LS28	30p	74LS151	75p	74LS290	90p
74LS30	15p	74LS153	65p	74LS293	100p
74LS32	17p	74LS155	90p	74LS298	93p
74LS37	20p	74LS156	90p	74LS352	110p
74LS38	30p	74LS157	70p	74LS353	110p
74LS40	17p	74LS158	70p	74LS366	50p
74LS47	15p	74LS160	100p	74LS367	80p
74LS49	52p	74LS161	100p	74LS368	55p
74LS74	33p	74LS162	100p	74LS374	160p
74LS75	32p	74LS163	130p	74LS386	36p
74LS76	38p	74LS164	100p	74LS670	150p

LOW PROFILE DIL SOCKETS BY TEXAS

8 Pin	8p	18 Pin	12p	24 Pin	16p
14 Pin	9p	20 Pin	13p	28 Pin	19p
16 Pin	10p	22 Pin	15p	40 Pin	30p

VERO PRODUCTS

Vero Wiring Pen (inc. 1 spool wire)	248p	VEROBOARD PCBs	
2 x Spare Sools	85p	2.5" x 5"	65p
Spot Face Cutter	98p	2.5" x 3.75"	85p
VeroBlock Breadboards	283p	2.5" x 17"	198p
		3.75" x 5"	65p
		3.75" x 17"	260p

CALCULATORS

Text 1500	375p	Brain Wave	770p
Text 1800	840p	Trader	900p
Scientific 2001	725p	LCD 300	940p

TERMS
Please add 35p for P&P plus 15% VAT to all orders. Export orders no VAT but postage at cost. Prompt delivery on all orders. Cheques, P.O.s, Money Orders to be made payable to:-

ROMANE ELECTRONICS
64 Newlyn Drive, Sale, Cheshire. M33 3LE
Tel. 061-962 2606

Now Casio give you
TIME TO SOLVE YOUR PROBLEMS

Be the first with
THE MIGHTY CHIP



"You can count on Casio"

IT HAD TO HAPPEN! Casio, world leaders in high quality calculators and watches, combine their talents to bring you the incredible

C-80 CALCULATOR WATCH (With finger touch keyboard)

- Hours, minutes, seconds, day, am/pm; And day, date, month, auto calendar pre-programmed to the year 2009.
- 8 digit calculator, 6+2 digits on double display.
- Professional 24 hour stopwatch function; measuring net, lap and 1st and 2nd place times to 1/100 second on double display.
- Dual time facility (24 hour clock). Nightlight.
- Mineral glass face. Water resistant. Black resin case and strap. Dimensions 44.9x35.8x10.2mm.
- 12 months battery life from two silver oxide uce 391.

Only £24.95 (RRP £29.95)

STAR BUYS FROM CASIO

81QS-35B Alarm Chronograph

Stainless steel. Mineral glass. Water resistant.

5 YEAR BATTERY.
Hours, minutes, seconds, day; And day, date, month and year. 12 or 24 hour display. 24 hour alarm, hourly chimes. Stopwatch from 1/100 second to 7 hours; net, lap and 1st and 2nd place times.

(£34.95) £29.95



Similar to illustration

F-80 Alarm Chronograph

Black resin case. Mineral glass.

Water resistant.
3 YEAR BATTERY
Hours, minutes, seconds, date, am/pm; or hours, minutes, alpha day, date, am/pm. 24 hour alarm, hourly chimes. Stopwatch from 1/10 second to 12 hours; net, lap and 1st and 2nd place. Nightlight.

ONLY £19.95



95QS-36B Chronograph

Stainless steel. Mineral glass. Water resistant.

5 YEAR BATTERY
Hours, minutes, seconds, am/pm and day (12 or 24 hour). Dual time (12 or 24 hour). Day, date, month and year calendar. Stopwatch from 1/100 second to 7 hours; net, lap and 1st and 2nd place times.

ONLY £19.95



111QS-34B Superbly finished chrome plated case.

Mineral glass. Water resistant.
Comprehensive display, hours, minutes, seconds, am/pm, day and date. Nightlight. Stainless steel bracelet.

ONLY £14.95

F-8C Black resin cased version £10.95



NEW CALCULATOR FOR 1980

MELODY 81

(£24.95) £22.95

Clock, calendar, two musical alarms, countdown timer. Stopwatch from 1/10 sec to 12 hours; net, lap, 1st & 2nd place. Calculator with full memory, %, square roots. 5/16x4 1/2". 1 year batteries.



MELODY 71

(£24.95) £22.95

As above but only one alarm. 3/16x3 1/2".



MQ-6 Micro Card The Big Digit Midget!

Pocket watch with full auto calendar. 1/10 sec stopwatch; net, lap, 1st & 2nd. 8 digit calculator with % and GT memory. Stylish fob chain, case. 3/16x1 1/2x2 1/4".

£19.95

MQ-12
As ML-71 but without music. Full month calendar display. 3/16x3 1/2x2 1/4".

£19.95



FX-81 Scientific

£12.95 (illustrated)

As FX-80 but without standard deviations and R-P, P-R conversions.

FX-80 (not illustrated)

37 scientific functions, 6+2 digit display. Pi, cube root, 6 levels (-), 4000 hours battery life from two AA size. 1 1/2x3x5 1/2".

£15.95



HR-10 Mini Printer. Only 1 1/2x3 1/2x6 1/2".

Most office functions plus full calendar printout from 1901 to 2099. 3 way powering.

ONLY £29.95

The "in" pendant for 1980
Winner of the

1980 GIFT AWARD (Fashion and personal accessories)

Features a genuine metal oxide silicon chip 24 pin dual in-line integrated circuit, set in a 9ct gold or a sterling silver clasp. Approx. 1 1/2x1/2x3/16". 11 gms. Supplied with leather thong.

Sterling Silver £30

9ct. Gold £69

SEIKO Latest models
Around 30% off!

SEIKO'S STAR BUY FOR 1980

TS2 Alarm Chronograph

Comprehensive display of hours, minutes, seconds, day, date and month. 24 hour alarm and hourly chimes. Stopwatch from 1/100 sec to 20 minutes then seconds to 20 hours. Upper display - lap times Lower display - total time. Audible button operation. S/steel encased. 8mm thick plus front buttons.

ONLY £47.50



TS1 Alarm Chronograph

WITH COUNTDOWN ALARM

Hours, minutes, seconds. Alpha day and date on upper display; And day, date, month. Alarm and hourly chimes. Countdown alarm (upper display). Stopwatch from 1/100 sec to 12 hours; net, lap and 1st and 2nd place times.

ONLY £57.50



TS7 Alarm Chronograph

100m WATER RESISTANT
Suitable for swimming, water skiing, etc. Time and calendar functions as TS2. Identical stopwatch functions but to 12 hours. Hourly chimes. WEEKLY programmable alarm. INTERVAL alarm timer up to 16 hours.

ONLY £74.95



TS4 Calculator Alarm

Hours, minutes, seconds, day; And day, date, month, am/pm. Alarm (2 tones), hourly chimes. 8 digit calculator with constants, delta %, Water resistant. 2 year battery with hatch. Approx 9mm thick +0.5mm for keys.

S/Steel £79.95

Gold plated £99.95



TS5 World Time/Alarm

TWO alarms, local and world time (dual tones). Hourly chimes. Normally displays hours, minutes, seconds, day, or optionally hours, minutes, day, date, month. World Time mode displays an atlas with each of the 19 time zones highlighted when selected. Date and summertime functions.

S/Steel £79.95

Gold plated £99.95

H127 Analogue/Digital (Same as P.E. offer)
Independent analogue watch. Digital watch with calendar, stopwatch and counter functions.

RRP £95

ONLY £69.95



Send 25p for our illustrated catalogue of Casio and Seiko products.
OUR RETAIL SHOP IS MOVING! PERSONAL CALLERS PLEASE TELEPHONE FIRST

Price includes VAT, P&P. Send your cheque, P.O. or phone your ACCESS or BARCLAYCARD number to:-

TEMPUS

Dept. PE, Beaumont Centre, 164-167 East Rd.,
Cambridge CB1 1DB. Tel. 0223 312866

TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics - now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

- Telecommunications Technicians
- Radio, T.V. Electronics Technicians
- Technical Communications
- Radio Servicing Theory
- Radio Amateurs
- Electrical Installation Work
- Also MPT Radio Communications Certificate

Diploma Courses

- Colour T.V. Servicing
- Electronic Engineering & Maintenance
- Computer Engineering and Programming
- Radio, T.V. and Audio, Engineering & Servicing
- Electrical engineering, Installations & Contracting

Other Career Courses

A wide range of other technical and professional courses are available including GCE.

FREE BOOK

Post this coupon or 'phone today for free ICS careers guide.

Name

Address

Age

ICS

To ICS, Dept T273, Intertext House,
London SW8 4UJ
or telephone 01-622 9911 (all hours)

SOUTH EAST ENGLAND'S ELECTRONICS CENTRE

Interested in Electronics? Then why not pay us a visit and see our vast range of Test Equipment, Oscilloscopes, PSUs, Computer Equipment, Government Surplus, VDUs, ICs, Transistors, Relays, Motors, Bulbs, Cable Transformers, PCBs, Resistors, Amplifiers, etc., etc.

★ ★ ★ THIS MONTHS SPECIALS ★ ★ ★

Miniature 5V 3 amp PSU, compact fully regulated, + crowbar protection.
£8.50 + P&P 70p

Wire wrap patch panels inc. 10 16 pin and 54 14 pin gold plated DIL WW sockets + 64 TTL and DTL I.C.'s dim. 6" x 7".
£8.95 + P&P 85p

Super value PCB pack. Contents include I.C.'s res. caps etc., etc. **Guaranteed** to include TTL and CMOS! 6 Boards, Our choice.
£2.50 + P&P 60p


49 key coded QWERTY keyboard, 8 bit output, delayed strobe, 5V rail, TTL output. Ex-equip. untested. Supplied with edge conn. & connection diagram.
£20.00 + P&P £1.60

NE555 10 for **£2.40**. 741 10 for **£1.80**. 1N4004 18 for **£1.00**. 0.125" RED LEDS 12 for **£1.00**. 2N3055H (RCA) 4 for **£2.25**. 1S44/1N4148 50 for **£1.00**. Stock list **50p**. Where P&P not shown please add 40p per order. Prices include VAT.

★ ELECTRONIC EQUIPMENT AND COMPONENTS PURCHASED FOR CASH
★ OPEN 9.30 TO 5.30 MONDAY TO SATURDAY ★ RETAIL AND TRADE
★ NO PARKING RESTRICTIONS ★ ACCESS & BARCLAYCARD

Display ELECTRONICS

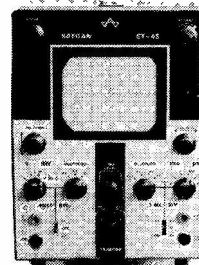64-66 MELFORD ROAD
THORNTON HEATH
SURREY. 01-689 7702



£135⁰⁰
SAFGAN ST-45
SINGLE TRACE OSCILLOSCOPE

● 10mv/div ● 5MHz ● BRITISH ● CHOICE OF FRONT PANEL ●

ST-45 SPECIFICATION VERTICAL SYSTEM

Sensitivity 10mv/div 5v/div in 9 cal. steps
Bandwidth (3dB)
DC Coupled DC 5MHz
AC Coupled 5Hz-5MHz
Risetime 70µsec
Input Impedance 1MΩ +22 PF approx. (for all ranges) 50Ω for 10mv/div 50mv/div
Input coupling AC CND DC
Input volts: 400V max.
Accuracy ±5%

HORIZONTAL SYSTEM

Time base speeds
50ms/div 1µsec/div in 15 cal. steps with X5 Multiplier to 250msec/div and X5 Expansion to 200msec/div
External - X sensitivity 1v/div
External - X Bandwidth 500KHz
Accuracy ±5%

ACCESSORIES

Passive Probe switched (X1. REF. x10)
100MHz bandwidth **£11.50 + VAT**
BNC to 4mm Socket Adaptor **£2.95 + VAT**

TRIGGER

Internal 0.5div (10Hz-2MHz), 1 div (2MHz-5MHz)
External 100mv (10Hz-2MHz), 200mv (2MHz-5MHz)
Bright Line Auto
Trace free runs in absence of signal
Trigger Level selects triggering point
Trigger (+)ve and (-)ve slope selection

FRONT PANEL

Black-Silver-White-ST-45-S The Silver Scope or
Black-Gold-White-ST-45-G The Gold Scope

GENERAL

Power consumption 10VA approx.
Mains selection 200V-220V-240V rms (40Hz-60Hz)
Weight 10lbs 4.5kg approx.
Case aluminium with black pvc finish and black handle, front panel white with black control knobs, black feet and tilt bar.

Safgan Electronics Ltd.,
56 Bishops Wood, St. Johns,
Woking, Surrey GU1 3QB

ORDERS TO: SAFGAN ELECTRONICS LTD.

56 Bishops Wood, St. Johns, Woking
Surrey GU21 3QB or Tel: Woking 66836.

Please send me.....ST-45-S.....ST-45-G.....Probe.....Adaptor

I enclose PO/Cheque.....(Goods + 15% VAT + £3.00 p&p)

Name.....


Address.....

*Ex VAT UK

CHROMASONIC electronics

56 FORTIS GREEN ROAD MUSWELL HILL LONDON N10 3HN
TELEPHONE 01-883 3705 01-883 2289

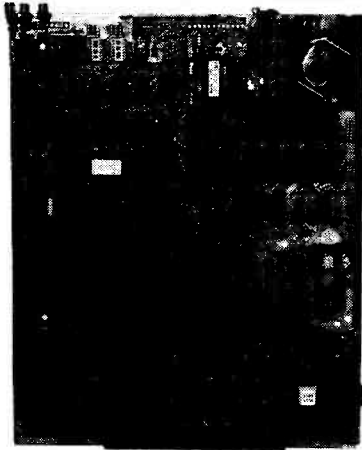your soundest connection in the world of components



Demonstration At Our Shop
(enter through stationers)

NOW AVAILABLE
Low cost computer in kit form

UK101

NO EXTRAS NEEDED
SIMPLY HIT
'RETURN' AND GO

As seen in
P.E.
August to November '79

Kit price
only **£199+VAT**

EXTRA 4K MEMORY
8 + 2114
ONLY
£35.00 + VAT

INCLUDED FREE
Sample tape with extended
machine code moditor and
disassembler

Price includes RF modulator and
power supply
**ABSOLUTELY NO EXTRAS
NEEDED**

Also available ready assembled,
tested and ready to go
only **£249 + VAT**

Build, understand, and program
your own computer for
only a small outlay

AVAILABLE SOON COLOUR ADD-ON CARD

Enable you to choose your foreground, the background colour anywhere on the screen. Flash any character on the screen at will. Full documentation and parts in kit form. Phone for details

STOP PRESS

The latest edition of our 'STOP PRESS' is now available, and contains an up-to-date price list showing all the items that we stock. Just send an S.A.E. or phone for your FREE copy. OUR catalogue is still available and if you're one of the few who haven't got a copy, order your FREE copy today.

PLUS SUPERBOARD II ONLY £188.00 + VAT

Dynamic RAMS	8228 4.13	CA3078S 1.00	ZN458A 1.35	74LS107 0.32	74LS251 0.96
2102A 1.10	8251 5.00	CA3080 0.67	ZN459CP 2.73	74LS109 0.32	74LS253 0.82
4027 5.01	8253 6.33	CA3080E 0.67	ZN1034E 1.90	74LS112 0.32	74LS257 0.82
4050 (200ns) 2.50	825t 5.08	CA3081 1.30	ZN1040E 6.85	74LS113 0.32	74LS258 0.82
4050 (350ns) 2.35	Baud Rate	CA3082 1.30	ZN1066E 5.85	74LS114 0.32	74LS259 1.38
4080 (300ns) 2.39	Generators	CA3086 0.48	ZNA116E 4.95	74LS122 0.69	74LS261 4.50
4116 6.74	MC14411 5.57	CA3089 1.75	ZNA134J 26.95	74LS123 0.72	74LS266 0.37
Static RAMS	MM5307 9.38	CA30900 3.95		74LS124 1.39	74LS273 1.70
2102A-2 1.16	UARTS	CA3097E 1.85		74LS125 0.36	74LS279 0.57
2111A-1 1m70	AY-5-1013 3.65	CA3123E 1.70		74LS126 0.36	74LS283 1.09
2112A-2 1.83	MM5303 5.04	CA3130E 0.85		74LS132 0.60	74LS289 4.50
21102 1.16	TMS6011NC 4.30	CA3140E 0.36		74LS133 0.39	74LS290 0.91
2114 5.17	2708	CA3160E 1.00		74LS136 0.36	74LS293 0.91
4035 (1000ns) 1.07	ONLY	CA3600E 2.69		74LS138 0.58	74LS295 1.30
4045 (250ns) 6.15	£6.26 + VAT	ICL7038A 2.57		74LS139 0.58	74LS298 1.16
5257 6.93		ICL8038BC 8.82		74LS145 0.87	74LS348 1.39
(TMS4044) 6.93		ICL8038CC 3.40		74LS151 0.81	74LS352 1.04
6810 3.03		ITT7120 1.90		74LS153 0.62	74LS353 0.92
ROMS		LF351N 0.40		74LS154 1.30	74LS362 4.21
2513 (U.C.) 6.25		LF358N 0.80		74LS155 0.72	74LS365 0.47
2513 (L.C.) 6.25		LM301AH 0.36		74LS156 0.72	74LS366 0.47
MM5230 4.62		LM301AN 0.25		74LS157 0.57	74LS367 0.47
CPU		LM307H 0.66		74LS158 0.57	74LS368 0.47
6800 6.01	Integrated Circuits	LM307N 0.43		74LS160 1.09	74LS373 0.78
8080 5.08	703 (8 pin) 0.95	LM308N 0.95		74LS161 0.18	74LS386 0.36
9900 26.05	709 (8 pin) 0.35	LM308 0.55		74LS162 1.16	74LS393 0.84
Z80 9.00	709 (14 pin) 0.38	LM318N 1.95		74LS163 0.69	74LS668 1.17
6502 9.50	709 (T099) 0.45	LM319H 2.25		74LS164 1.06	74LS670 1.71
E-PROMS	710 (8 pin) 0.36	LM322N 2.87		74LS165 0.72	
1702AO 5.16	710 (14 pin) 0.38	LM324N 0.50		74LS166 1.65	
2708 6.26	710 (T099) 0.45	LM339N 0.80		74LS168 1.71	
2716 24.00	711 (14 pin) 0.40	LM348N 0.90		74LS169 1.71	
T.V. Controller	711 (T099) 0.87	LM370N 2.90		74LS170 1.72	
SFF96364 14.50	739 (14 pin) 1.80	LM371H 2.05		74LS173 0.81	
Buffers	741 (8 pin) 0.18	LM373N 2.90		74LS174 0.97	
74365 0.52	741 (14 pin) 0.35	LM374N 2.90		74LS175 0.97	
74366 0.52	741 (T099) 0.42	LM377N 1.75		74LS177 0.88	
74367 0.52	747 (14 pin) 0.70	LM378N 2.05		74LS181 2.77	
74368 0.52	748 (8 pin) 0.33	LM379S 3.75		74LS188 0.44	
81LS95 0.86	748 (14 pin) 0.45	LM380N8 0.85		74LS189 2.08	
81LS96 0.70	748 (T099) 0.48	LM380N 0.75		74LS190 0.86	
81LS97 0.86	753 (8 pin) 1.50	LM381N 1.45		74LS191 0.86	
81LS98 0.70	AY-5-10212 5.80	LM381AN 2.50		74LS192 1.04	
8726 1.90	AY-5-5050 1.90	LM382N 1.20		74LS193 1.04	
8728 1.90	AY-1-5051 1.45	LM386N 0.78		74LS194 0.86	
8795 1.57	AY-16721/6 1.95	LM387N 0.95		74LS195 0.86	
8796 1.57	AY-3-8500 5.00	LM389N 0.85		74LS196 0.87	
8797 1.57	AY-5-1224 2.40	LM725CN 2.25		74LS197 0.87	
8798 1.57	AY-5-3507 4.15	LM1303N 1.00		74LS221 0.82	
8798 1.57	AY-5-4007 1.10	LM1808N 1.95		74LS240 2.06	
Interface	CA3036 1.10	LM1812N 5.40		74LS241 2.08	
8205 3.00	CA3045F 1.40	LM1820N 1.00		74LS242 2.08	
8212 2.00	CA3046 0.65	LM183N 1.08		74LS243 2.08	
8216 2.00	CA3065N 0.65	LM3065N 1.50		74LS245 2.09	
8224 2.77	CA3065J 0.72	LM3900N 0.50		74LS247 1.50	
	CA3075 2.00	LM3905N 1.00		74LS248 1.09	
				74LS249 1.09	

All prices are EXCLUSIVE of VAT. Postage and packing 30p (computers charged at cost). CALLERS WELCOME. Hours 9.00am-5.00pm (enter through stationers).
TRADE and EXPORT inquiries welcome. Phone your orders through our ORDER-RING line quoting your Access or Barclaycard number (Min. tel order £5).

8 + 4116
ONLY
£49.50
VAT

21L02
8 for
£8.50

16 for
£14.50

32 for
£26.50

64 for
£49.50
ALL VAT

Britain's first comp

A complete personal computer for a third of the price of a bare board.

Also available ready assembled for £99⁹⁵

The Sinclair ZX80.

Until now, building your own computer could easily cost around £300—and still leave you with only a bare board for your trouble.

The Sinclair ZX80 changes all that. For just £79.95 you get *everything* you need to build a personal computer at home...PCB, with IC sockets for all ICs; case; leads for direct connection to your own cassette recorder and television; everything!

And yet the ZX80 really is a complete, powerful, full-facility computer, matching or surpassing other personal computers on the market at several times the price. The ZX80 is programmed in BASIC, and you could use it to do quite literally anything from playing chess to running a power station.

The ZX80 is pleasantly straightforward to assemble, using a fine-tipped soldering iron. Once assembled, it immediately proves what a good job you've done. Connect it to your TV set...link it to an appropriate power source*...and you're ready to go.


Your ZX80 kit contains...

- Printed circuit board, with IC sockets for all ICs.
- Complete components set, including all ICs—all manufactured by selected world-leading suppliers.
- New rugged Sinclair keyboard, touch-sensitive, wipe-clean.
- Ready-moulded case.
- Leads and plugs for connection to any portable cassette recorder (to store programs) and domestic TV (to act as VDU).
- FREE course in BASIC programming and user manual.

Optional extras

- Mains adaptor of 600 mA at 9 V DC nominal unregulated (available separately—see coupon).
- Additional memory expansion board plugs in to take up to 3K bytes extra RAM chips. (Chips also available—see coupon.)

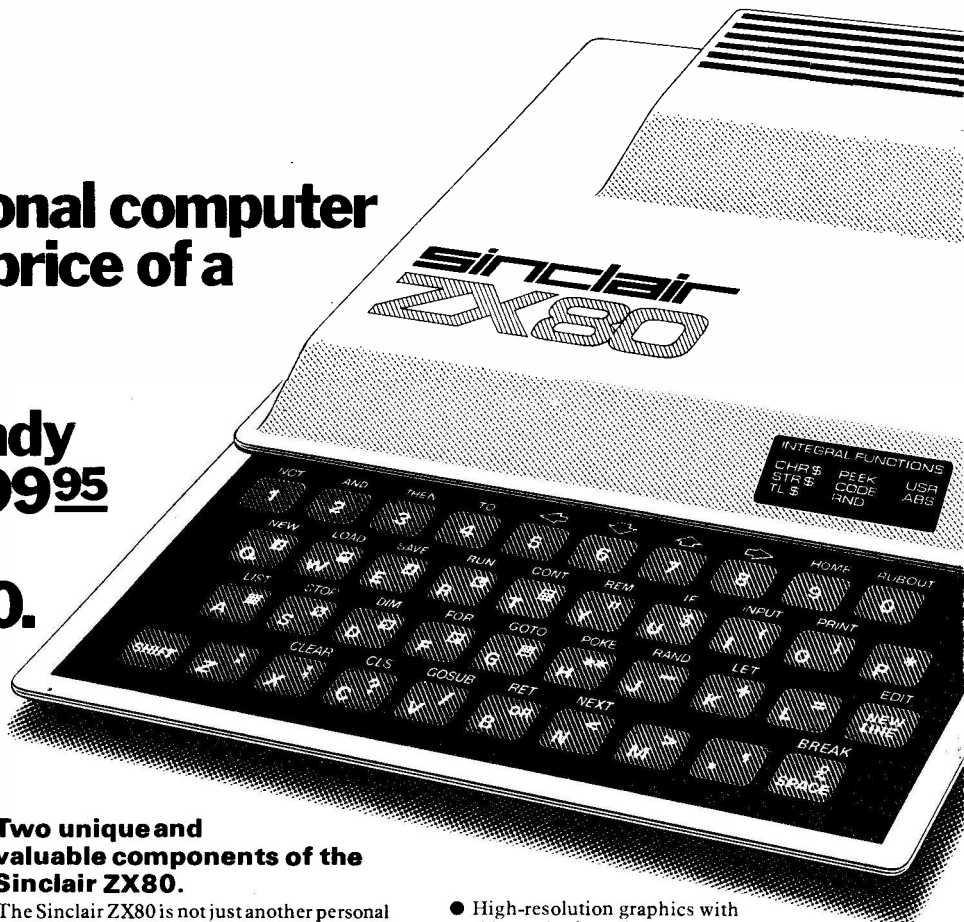*Use a 600 mA at 9 V DC nominal unregulated mains adaptor. Available from Sinclair if desired (see coupon).



Two unique and valuable components of the Sinclair ZX80.

The Sinclair ZX80 is not just another personal computer. Quite apart from its exceptionally low price, the ZX80 has two uniquely advanced components: the Sinclair BASIC interpreter; and the Sinclair teach-yourself BASIC manual.


The unique Sinclair BASIC interpreter... offers remarkable programming advantages:

- Unique 'one-touch' key word entry: the ZX80 eliminates a great deal of tiresome typing. Key words (RUN, PRINT, LIST, etc.) have their own single-key entry.
- Unique syntax check. Only lines with correct syntax are accepted into programs. A cursor identifies errors immediately. This prevents entry of long and complicated programs with faults only discovered when you try to run them.
- Excellent string-handling capability—takes up to 26 string variables of any length. All strings can undergo all relational tests (e.g. comparison). The ZX80 also has string input-to request a line of text when necessary. Strings do *not* need to be dimensioned.
- Up to 26 single dimension arrays.
- FOR/NEXT loops nested up to 26.
- Variable names of any length.
- BASIC language also handles full Boolean arithmetic, conditional expressions, etc.
- Exceptionally powerful edit facilities, allowing modification of existing program lines.
- Randomise function, useful for games and secret codes, as well as more serious applications.
- Timer under program control.
- PEEK and POKE enable entry of machine code instructions,USR causes jump to a user's machine language sub-routine.

- High-resolution graphics with 22 standard graphic symbols.
- All characters printable in reverse under program control.
- Lines of unlimited length.

... and the Sinclair teach-yourself BASIC manual.

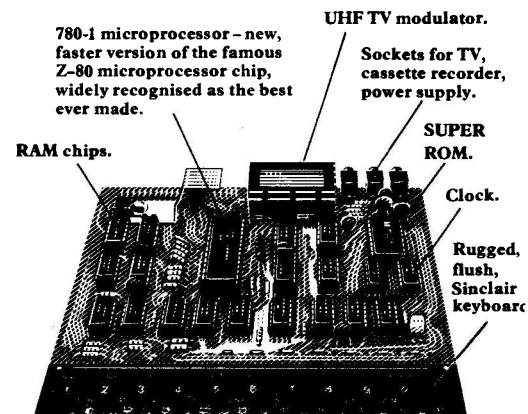If the features of the Sinclair interpreter listed alongside mean little to you—don't worry. They're all explained in the specially-written 96-page book *free* with every kit! The book makes learning easy, exciting and enjoyable, and represents a complete course in BASIC programming—from first principles to complex programs. (Available separately—purchase price refunded if you buy a ZX80 later.)



Complete computer kit.

£79⁹⁵

**Including VAT.
Including post and
packing.
Including all leads
and components**

**Fewer chips,
compact design,
volume production –
more power per pound!**

The ZX80 owes its remarkable low price to its remarkable design: the whole system is packed onto fewer, newer, more powerful and advanced LSI chips. A single SUPER ROM, for instance, contains the BASIC interpreter, the character set, operating system, and monitor. And the ZX80's 1K byte RAM is roughly equivalent to 4K bytes in a conventional computer, because the ZX80's brilliant design packs the RAM so much more tightly. (Key words, for instance, occupy just a single byte.)

To all that, add volume production – and you've got that rare thing: a price breakthrough that really is a breakthrough.

**The Sinclair ZX80. Kit: £79.95.
Assembled: £99.95. Complete!**

The ZX80 kit costs a mere £79.95. Can't wait to have a ZX80 up and running? No problem! It's also available, ready assembled, for only £99.95.

Whether you choose the kit or the ready-made, you can be sure of world-famous Sinclair technology – and years of satisfying use. (Science of Cambridge Ltd is one of the Sinclair companies owned and run by Clive Sinclair.)

To order, complete the coupon, and post to Science of Cambridge for delivery within 28 days. Return as received within 14 days for full money refund if not completely satisfied.

**sinclair
ZX80**

Science of Cambridge Ltd

6 Kings Parade, Cambridge, Cambs., CB2 1SN.
Tel: 0223 311488.

Order Form

To: Science of Cambridge Ltd, 6 Kings Parade, Cambridge, Cambs., CB2 1SN.
Remember: all prices shown include VAT, postage and packing. No hidden extras.

Please send me:

Quantity	Item	Item price £	Total £
	Sinclair ZX80 Personal Computer kit(s). Price includes ZX80 BASIC manual, excludes mains adaptor.	79.95	
	Ready-assembled Sinclair ZX80 Personal Computer(s). Price includes ZX80 BASIC manual, excludes mains adaptor.	99.95	
	Mains Adaptor(s) (600 mA at 9 V DC nominal unregulated).	8.95	
	Memory Expansion Board(s) (takes up to 3K bytes).	12.00	
	RAM Memory chips – standard 1K bytes capacity.	16.00	
	Sinclair ZX80 Manual(s) (manual free with every ZX80 kit or ready-made computer).	5.00	
		TOTAL	£

NB. Your Sinclair ZX80 may qualify as a business expense.

I enclose a cheque/postal order payable to Science of Cambridge Ltd for £

Please print

Name: Mr/Mrs/Miss _____

Address _____

PE/4/80

It's faster and more thorough than classroom learning; you pace yourself and answer questions on each new aspect as you go. This gives rare satisfaction - you know that you are really learning and without mindless drudgery. With a good self-instruction course you become your own best teacher.

Understand Digital Electronics

In the years ahead digital electronics will play an increasing part in your life. Calculators and digital watches mushroomed in the 1970's - soon we will have digital car instrumentation, cash cards, TV messages from friends and electronic mail. After completing these books you will have broadened your career prospects and increased your knowledge of the fast-changing world around you.

DIGITAL COMPUTER LOGIC AND ELECTRONICS £7.50

This course is designed as an introduction to digital electronics and is written at a pace that suits the raw beginner. No mathematical knowledge is assumed other than the use of simple arithmetic and decimals and no electronic knowledge is expected at all. The course moves painstakingly through all the basic concepts of digital electronics in a simple and concise fashion: questions and answers on every page make sure that the points are understood.

Everyone can learn from it - students, engineers, hobbyists, housewives, scientists. Its four A4 volumes consist of:

- Book 1** Binary, octal and decimal number systems; conversion between number systems; conversion of fractions; octal-decimal conversion tables.
- Book 2** AND, OR gates; inverters; NOR and NAND gates; truth tables; introduction to Boolean algebra.
- Book 3** Positive ECL; De Morgans Laws; designing logic circuits using NOR gates; dual-input gates.
- Book 4** Introduction to pulse driven circuits; R-S and J-K flip flops; binary counters; shift registers; half-adders.

DESIGN OF DIGITAL SYSTEMS £11.50

This course takes the reader to real proficiency. Written in a similar question and answer style to Digital Computer Logic and Electronics, this course moves at a much faster pace and goes into the subject in greater depth. Ideally suited for scientists or engineers wanting to know more about digital electronics, its six A4 volumes lead step by step through number systems and Boolean algebra to memories, counters and arithmetic circuits and finally to an understanding of calculator and computer design.


- Book 1** Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division.
- Book 2** OR and AND functions; logic gates; NOT, exclusive-OR, NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; karnaugh mapping; three state and wired logic.
- Book 3** Half adders and full adders; subtractors; serial and parallel adders, processors and arithmetic logic units (ALUs); multiplication and division systems.
- Book 4** Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters; random access memories (RAMs) and read only memories (ROMs).
- Book 5** Structure of calculators; keyboard encoding; decoding display data, register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control programme structure.
- Book 6** Central processing unit (CPU); memory organization; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing.

Flow Charts and Algorithms

are the essential logical procedures used in all computer programming and mastering them is the key to success here as well as being a priceless tool in all administrative areas - presenting safety regulations, government legislation, office procedures etc.


THE ALGORITHM WRITER'S GUIDE £3.75

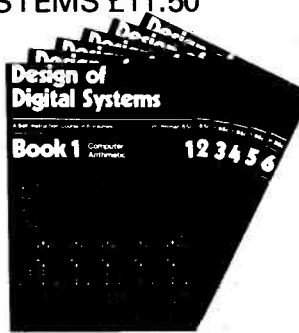explains how to define questions, put them in the best order and draw the flow chart, with numerous examples.



Microcomputers are coming - ride the wave! Learn to program.

Millions of jobs are threatened but millions more will be created. Learn BASIC - the language of the small computer and the most easy-to-learn computer language in widespread use. Teach yourself with a course which takes you from complete ignorance step-by-step to real proficiency with a unique style of graded hints. In 60 straightforward lessons you will learn the five essentials of programming: problem definition, flowcharting, coding the program, debugging, clear documentation. Harder problems are provided with a series of hints so you never sit glassy-eyed with your mind a blank. You soon learn to tackle really tough tasks such as programs for graphs, cost estimates, compound interest and computer games.

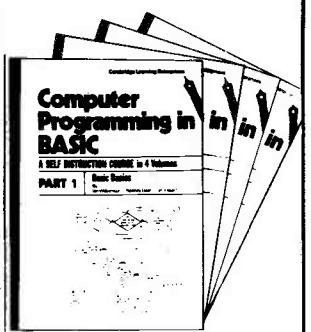

COMPUTER PROGRAMMING IN BASIC £7.50

- Book 1** Computers and what they do well; READ, DATA, PRINT, powers, brackets, variable names; LET; errors; coding simple programs.
- Book 2** High and low level languages; flowcharting; functions; REM and documentation; INPUT, IF...THEN, GO TO; limitations of computers, problem definition.
- Book 3** Compilers and interpreters; loops, FOR...NEXT, RESTORE; debugging; arrays; bubble sorting; TAB.
- Book 4** Advanced BASIC; subroutines; string variables; files; complex programming; examples; glossary.

THE BASIC HANDBOOK £11.50

This best-selling American title usefully supplements our BASIC course with an alphabetical guide to the many variations that occur in BASIC terminology. The dozens of BASIC 'dialects' in use today mean programmers often need to translate instructions so that they can be RUN on their system. The BASIC Handbook is clear, easy to use and should save hours of your time and computer time. A must for all users of BASIC throughout the world.

FORTRAN COLORING BOOK £5.40

"If you have to learn Fortran (and no one actually wants to assimilate it for the good of the soul) buy this book. Forget the others - this one is so good it will even help you understand the standard, dense, boring, unintelligible texts." *New Scientist*.

A.N.S. COBOL £4.40

The indispensable guide to the world's No. 1 business language. After 25 hours with this course, one beginner took a consulting job, documenting oil company programs and did invaluable work from the first day. Need we say more?

GUARANTEE - No risk to you

If you are not completely satisfied your money will be refunded on return of the books in good condition.

Cambridge Learning Enterprises, Unit 29, Rivermill Site, FREEPOST, St. Ives, Huntingdon, Cambs PE17 4BR England.

Please send me:-

-Digital Computer Logic & Electronics @ £7.00
-Design of Digital Systems @ £11.50
-Algorithm Writer's Guide @ £3.75
-Computer Programming in BASIC @ £7.50
-BASIC Handbook @ £11.50
-Fortran Coloring Book @ £5.40
-A.N.S. Cobol @ £4.40

All prices include worldwide surface mailing costs (airmail extra) **IF YOUR ORDER COMES TO OVER £18, DEDUCT £2**

Cheques/PO's payable to Cambridge Learning Enterprises or charge to Access/Barclaycard/Diners Club/etc account no

Telephone orders from credit card holders accepted on 0480-67446. Overseas customers (inc Eire) use credit card, or bank draft in sterling drawn on a London bank, or International Money Order (add £1 handling charge.)

Name

Address

Cambridge Learning Enterprises, Unit 29, Rivermill Site, FREEPOST, St. Ives, Huntingdon, Cambs PE17 4BR England.


Conquer the chip.

Be it career, hobby or interest, like it or not the Silicon Chip will revolutionise every human activity over the next ten years.

Knowledge of its operation and its use is vital. Knowledge you can attain, through us, in simple, easy to understand stages.

Learn the technology of the future today in your own home.

ELECTRONICS

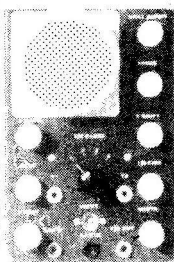

Build your own oscilloscope.

Learn to draw and understand circuits.

Carry out over 40 experiments.

DIGITAL TECHNIQUES

From watches to sophisticated instrumentation, Digital Electronics adds scope to hobby or career.



COMPUTER TECHNOLOGY


Learn to operate and programme your own home computer.



FREE BROCHURES



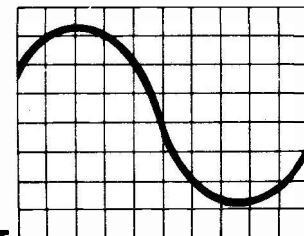No previous knowledge is necessary.
— Just clip the coupon for a brochure



TUTORCOURSE ELECTRONICS

Please rush me details of your
ELECTRONICS COURSE

Name _____

Address _____

Block Caps. Please
Post now, without obligation to:

**British National Radio
& Electronics School.**

P.O. Box 156, Jersey, Channel Isles

PER 4

The new Toolrange catalogue



still the only catalogue of its kind

The New Toolrange Catalogue is still the only comprehensive single source of electronic tools and production aids.

The product range has almost doubled since last year and now over 2,000 tools, toolkits and service aids are illustrated in full colour.

Products from over 100 top manufacturers are available from stock.

Over 60,000 catalogues are now in circulation. If you don't have one simply write, telephone or telex Toolrange for your free copy.



Upton Road, Reading, Berks. RG3 4JA
Telephone: Reading (0734) 22245 Telex: 847917

ZENER DIODES (400 mW) 2.7V to 33V 8p	SEND FOR TRADELIST	LINEAR CIRCUITS 4029 7493 4030 80p 4035 70p 710-14 33p 741-8 22p 747-14 44p 748-8 44p CA3018 70p CA3028A 85p CA3046 70p CA3054 70p CA3080 75p CA3130 90p CA3140 45p LF351N 85p LM348N 90p LM308N 80p LM318N 200p LM324N 74p LM339N 60p LM339N 85p LM377N 175p LM380N 90p LM381N 140p LM382N 130p LM310N 150p LM390N 85p LM390N 70p MCI495P 85p NE531 140p NE555 25p 7905 90p 7912/15 90p 7918/24 30p	ELECTROLYTIC CAP (25V) 1uF to 50uF 8p 50uF, 100uF 8p 150uF 9p 220uF 10p 470uF 13p 1000uF 22p	BRIDGE RECTIFIERS 1A/50V 22p 1A/400V 34p 2A/50V 40p 2A/400V 55p	POTENTIOMETERS (1/2W carbon) 4.7 Kohm to 2.2 Mohm Log and Linear 30p	VOLTAGE REGULATORS 7805 70p 7812/15 70p 7818/24 70p NE555 25p 7905 90p 7912/15 90p 7918/24 30p	CERAMIC CAP (50V) 22pF to 47nF 2p	POLY-ETHYLENE CAP (E12 50V) 10pF to 1nF 5p	POLYESTER CAP 1nF to 68nF 5p 100, 150nF 7p 220, 330nF 8p 470nF 8p 680nF 10p 1uF 14p 2.2uF 20p 3.3uF 22p 4.7uF 29p	OPTO/DISPLAY ORP12 60p MAN72 110p MAN74 110p 125° & 2° LEDs: Red 10p Green 14p Yellow 14p	DIODES OA47 8p DA91 8p IN4148 4p IN916 4p IN4002 4p IN4005 4p IN5400 13p IN5404 16p	DIL SOCKETS 8 pin 11p 14 pin 13p 16 pin 14p 18 pin 19p 22 pin 22p 24 pin 24p 28 pin 28p 40 pin 40p	CMDS 4000 16p 4001/2 16p 4006 7p 4007 16p 4008 84p 4009 40p 4010 42p 4011/2 16p 4013 40p 4014 85p 4015 75p 4016 44p 4017 57p 4018 80p 4019 45p 4020 90p 4021 85p 4022 82p 4023 18p 4024 55p 4025 15p 4027 70p 4028 45p	TRANSISTORS 20p AC126/7 23p 13p AC128 23p 50p AC176 23p 51p AC187/8 23p 75p AD161/2 40p 65p AF124 45p 42p AF139 40p 13p BC107 10p 13p BC108/9 10p 13p BC147/8 10p 28p BC149 10p 21p BC157/8 12p 14p BC159 12p 34p BC169C 13p 30p BC173 6p 32p BC177/8 18p 25p BC179 22p 36p BC182/3 12p 55p BC184 12p 40p BC209 13p	4029 7493 80p 7494 57p 107p 7495 44p 75p 7496 55p 70p 7497 44p 44p 74105 43p 84p 74107 26p 87p 74109 44p 55p 74110 40p 75p 74121 26p 44p 74122 40p 50p 74123 45p 18p 74125 37p 18p 74126 37p 18p 74132 40p 18p 74133 40p 18p 74141 60p 100p 74145 55p 100p 74150 78p 100p 74151 43p 100p 74153 48p 100p 74154 46p 100p 74155/6 32p 74157 43p 74160/1 64p 74162/3 64p 74164/5 78p 13p 74166 85p 18p 74173 77p 13p 74174 75p 13p 74175 60p 24p 74176 64p 13p 74177 60p 13p 74180 57p 18p 74181 90p 15p 74182 57p 27p 74190 75p 31p 74191 70p 25p 74192 65p 14p 74193 64p 17p 74195 57p 20p 74197 100p 25p 74199 120p	82p 7493 57p 7494 44p 7495 55p 7496 44p 7497 43p 74105 26p 74107 44p 74109 40p 74110 26p 74121 40p 74122 45p 74123 37p 74125 37p 74126 40p 74132 40p 74133 60p 74141 55p 74145 78p 74150 43p 74151 48p 74153 46p 74154 32p 74155/6 43p 74157 64p 74160/1 64p 74162/3 78p 74164/5 85p 74166 77p 74173 75p 74174 60p 74175 64p 74176 60p 74177 57p 74180 90p 74181 57p 74182 75p 74190 70p 74191 65p 74192 64p 74193 57p 74195 100p 74197 120p 74199	35p BC212/3 12p BC214 12p BC216 40p BC481 40p BC482 27p BC479 14p BC547/8 14p BC549 15p BC557/8 15p BC559 15p BCY70 15p BCY71/2 50p BD115 42p BD131 30p BF180 35p BN918 12p BF194/5 12p BF196/7 12p BF2448 40p BF259 32p BFR73 25p BFR79 25p BF829 25p BF834 25p BF878 22p BFY50 22p BFY51/2 60p BRV39 210p BU208 110p MJ2955 70p MJ340 110p MJ2955 85p MJ3055 40p MPF102/3 40p MPF104/5 50p MPF106 22p MPSA06 25p MPSA56 61p MPSJ06 92p OC35 48p TIP29B 48p TIP30B 40p TIP31/2 90p TIP33C 90p TIP35B 240p TIP36B 280p TIP41A 55p TIP3055 12p TX101 15p 2N6459 15p 2N6827	18p ZTX301 20p ZTX302 24p ZTX303 27p ZTX304 19p ZTX341 22p ZTX500 16p ZTX501 17p ZTX502 21p ZTX503 28p ZTX504 35p 2N696 35p 2N698 15p 2N706 20p 2N914 35p 2N918 20p 2N1131 35p 2N1302 40p 2N1303 25p 2N222A 20p 2N2368 17p 2N2484 55p 2N2646 20p 2N2904 23p 2N2905 20p 2N2906 20p 2N3202 140p 2N3266 20p 2N3053 50p 2N3054 50p 2N3055 140p 2N3442 20p 2N3702 11p 2N3711 150p 2N3772 250p 2N3773 22p 2N3815 20p 2N3820 60p 2N3823 90p 2N3866 48p 2N3903 10p 2N3904 10p 2N3905 10p 2N4037 45p 2N4058 14p 2N4059 14p 2N4060 40p 2N4547 40p 2N4548 15p 2N4549 15p 2N6827	ADD 35p FOR P & P
------------------------------------------------------	---------------------------	-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	-----------------------------------------------------------------------------------------------------------------------	------------------------------------------------------------------------------------	-----------------------------------------------------------------------------------------	----------------------------------------------------------------------------------------------------------------------------	------------------------------------------------	---------------------------------------------------------	-----------------------------------------------------------------------------------------------------------------------------------------------------	--------------------------------------------------------------------------------------------------------------------------	--------------------------------------------------------------------------------------------------------------------	-----------------------------------------------------------------------------------------------------------------------------------	----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	------------------------------

DELTA TECH
62 NAYLOR ROAD
LONDON N20 0HN
MAIL ORDER ONLY
SAE for complete list

DISPLAY LIGHTING KITS

Each unit has 4 channels (rated at 1KW at 240V per channel) which switch lamps to provide sequencing effects, controlled manually or by an optional opto-isolated audio input.

DL1000K
This kit features a bi-directional sequence, speed of sequence and frequency of direction change being variable by means of potentiometers. Incorporates master dimming control. £14.60

DL21000K
A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a preset pot. Outputs switched only at mains zero crossing points to reduce radio interference to minimum. £8.00

Optional Opto Input DLA1 60p

DIGITAL VOLTMEETER/THERMOMETER KIT

Based on the ICL 7106. This Kit contains a PCB, resistors, presets, capacitors, diodes, IC and 0.5" liquid crystal display. Components are also included to enable the basic DVM kit to be modified to a Digital Thermometer using a single diode as the sensor. Requires a 3mA 9V supply. (PP3 battery) £20.75

LEDs

0.1" Red	5p
0.1" Green	12p
0.1" Yellow	12p
0.2" Red	9p
0.2" Green	12p
0.2" Yellow	12p
0.2" clips	3p
Rectangular Red	18p
Rectangular Green	20p
Rectangular Yellow	21p

DISPLAYS

DL304 Red 0.3" c.c. pin compatible with DL704 70p
DL307 Red 0.3" c.c. pin compatible with DL707 70p
DL847 Red 0.8" pin comp. DL747 c.a. £1.80
DL850 Red 0.8" c.c. (pin comp. DL750) £1.80
DL727 Dual 0.5" c.c. Red £1.50

TRIACS

400V Plastic Case (Texas)

3A	49p	16A	90p
8A	58p	20A	165p
12A	80p	25A	190p
8A with trigger			80p
BA isolated tab			65p
Diac			18p

O.I.L. I.C. SOCKETS

(Low Profile Texas)

8 pin	8p	18 pin	17p
14 pin	12p	28 pin	24p
16 pin	14p	40 pin	36p

Soldercon Pins 50p/100

BARCLAYCARD All components brand new and to specification. Add V.A.T. at CURRENT RATE TO ABOVE PRICES PLUS 35p P.&P. Mail Order - Callers welcome by appointment.

VISA

T.K. ELECTRONICS (PE) 106 Studley Grange Road, London W7 2LX Tel 01 579 5794

STARCHASER 4000

THE NEW FOUR CHANNEL LIGHTING CONTROLLER




- 4 channels 750W each
 - over 1000 different sequence patterns and effects
 - 3 alternative sound triggers
 - A.G.C.
 - simulated strobing
 - zero reference triac firing
 - superb TUAC quality and reliability
- £119.00 inc. VAT.**

4 CHANNEL SOUND TO LIGHT SEQUENCE

CHASER = 4LSM1

£22.95

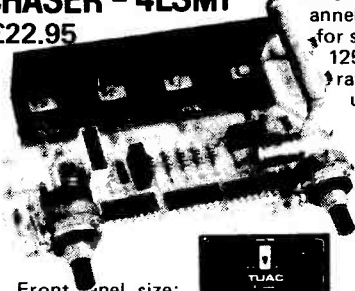

Front panel, size: 6½" x 4½". £7.75.

* RCA 8A Triacs * 1000W per channel * Switched master control for sound operation from ½W to 125W * Speed control for fixed rate sequence from 8 per minute to 50 per second * Full logic integrated circuitry with optical isolation for amplifier protection.

3 CHANNEL AUTO SOUND TO LIGHT

- AFL 6 £17.50


* RCA 8 Amp Triacs * 500W per channel * 2 channels flip flop, 1 channel sound to light * Fully automatic via built in mic * No connection to amplifier necessary.



STOP PRESS!

NOW AVAILABLE - THE FANTASTIC NEW TUAC STEREO AND MONO MIXERS. Send for details.

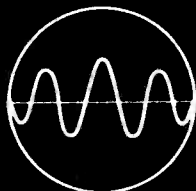SEND FOR OUR FREE 28 PAGE CATALOGUE, PLEASE ENCLOSE A STAMP.



TUAC

TUAC Ltd., 119/121 Charlmont Road, SW17.
Tel. 01-672 3137/9080
PRICE INCLUDES VAT. P+P FREE

TO ORDER BY POST. Make cheques/P.O.s payable to TUAC LTD. or quote Access/Barclaycard No. and post to TUAC LTD., 119/121 Charlmont Road, London SW17 9AB. We accept telephone orders from Access/Barclaycard Holders. Phone 01-672 9080.

TUAC MAIN DISTRIBUTORS (Callers Only)

- Birmingham, George Matthews, 85/87 Hurst Street, (Tel: 622 1941).
- London, Garland Bros., Deptford Broadway, (Tel: 01-692 4412).
- London, Session Music, 163 Mitcham Road, Tooting, (Tel: 01-672 3413) Mon-Sat 10am to 5.30pm. Closed Wed.
- Luton, Luton Disco Centre, 88 Wellington Street, (Tel: 411733).
- Manchester, A1 Music, 88 Oxford Street, (Tel: 236 0340).
- Middlesborough, Salcoglen, 43 Borough Road, (Tel: 242851).
- Watford, Component Centre, 7 Langley Road, (Tel: 45335)

NEW 1980 RADIO AMATEUR'S HANDBOOK

by A.R.R.L. Price: £8.00

WORLD RADIO T.V. HANDBOOK 1980 Price: £9.50

UNDERSTANDING MICROPROCESSORS by Texas Instruments Price: £4.25

MICROPROCESSOR COOKBOOK by M. F. Hordeski Price: £4.85

HOW TO USE INTEGRATED CIRCUIT LOGIC ELEMENTS by J. W. Streater Price: £4.45

DESIGN OF OP AMP CIRCUITS WITH EXPERIMENTS by H. M. Berlin Price: £5.65

THE ACTIVE FILTER HANDBOOK by F. P. Tedeschi Price: £5.50

Z80 ASSEMBLY LANGUAGE PROGRAMMING by L. A. Leventhal Price: £5.50

DESIGN OF PHASE LOCKED LOOP CIRCUITS WITH EXPERIMENTS by H. M. Berlin Price: £6.35

ADVENTURES WITH MICROELECTRONICS by T. Duncan Price: £2.30

★ ALL PRICES INCLUDE POSTAGE ★

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET LONDON W21NP

Phone 01-402 9176

Closed Saturday 1 p.m.

MAIL ORDER ADVERTISING

British Code of Advertising Practice

Advertisements in this publication are required to conform to the British Code of Advertising Practice. In respect of mail order advertisements where money is paid in advance, the code requires advertisers to fulfil orders within 28 days, unless a longer delivery period is stated. Where goods are returned undamaged within seven days, the purchaser's money must be refunded. Please retain proof of postage/despatch, as this may be needed.

Mail Order Protection Scheme

If you order goods from Mail Order advertisements in this magazine and pay by post in advance of delivery, PRACTICAL ELECTRONICS will consider you for compensation if the Advertiser should become insolvent or bankrupt, provided:

- (1) You have not received the goods or had your money returned; and
- (2) You write to the Publisher of PRACTICAL ELECTRONICS summarising the situation not earlier than 28 days from the day you sent your order and not later than two months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the Advertiser has been declared bankrupt or insolvent.

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine not, for example, payment made in response to catalogues etc. received as a result of answering such advertisements. Classified advertisements are excluded.

Codespeed Electronics

P.O. BOX 23, 34 SEAFIELD ROAD, COPNOR, PORTSMOUTH, HANTS., PO3 5BJ

8 DIGIT 0.1" LED DISPLAY multiplexed, common cathode. 99p each. DIGITAL ALARM CLOCK MODULE with 0.7" display. With data £5.99 each. 4 DIGIT CLOCK L.C.D. 0.5" digits, supplied with data, £4.99 each. MM5316 digital alarm clock chip with data £2.29 each. REJECT CALCULATORS. Untested, but good value for spares. £2.50 each. LED WRISTWATCH I.C. Mostek MK5030, with data 95p each. LED WRISTWATCH DISPLAY type DIS501, 0.1" digits. With data 95p each. SUPER SAVER Purchase an MK5030 and a DIS501 for only £1.50 the pair. NOTE the MK5030 and DIS501 are housed in a 'legless flatpack' style package and require some fairly fine soldering. 20 KEY KEYBOARDS calculator keyboards. 2 for 99p (not for use with NORTEC4204 calc. chip). 4 DIGIT 0.8" LED DISPLAY common cathode, with data £3.75 each. DIGITAL MULTI-METER CHIP MM5330 I.C. to build a 4½ digit multi-meter. With data £3.49 each. SUPER QUALITY JACK SOCKETS 1/4" (6.35mm) jack sockets, mono 23p each, stereo 25p each. SLIDE POT KNOBS please state colour required. 11p each. ROTARY VOLUME CONTROL KNOBS nice style. 18mm diam. Black with coloured cap. Please state colour required. 18p each. 10 LED DISPLAYS Untested material. 0.1" digits, common cathode. 95p. 6 DIGIT 0.1" LED DISPLAY multiplexed, common cathode. 99p. 555 TIMER I.C. with data and applications booklet. 23p. POLARIZING FILM max. 19" wide any length. Only 2p per sq. inch. Any size cut. SLIDER SWITCHES 2 pole, change over. 15p each. PUSH BUTTON SWITCHES spring loaded (momentary) with one n.o. contact 14p each. CALCULATOR CHIP Nortec 4204, 4 function and constant. With data 80p. 2102 MEMORIES Dynamic memories for your micro's. With data 95p each. WRISTWATCH L.C.D. supplied with polarizers and data sheet. 99p each.

NEW CATALOGUE (No. 7) NOW AVAILABLE. SEND MEDIUM S.A.E. FOR YOUR FREE COPY.

POST & PACKING PLEASE ADD 35p (OVERSEAS ORDERS ADD 90p)

ADD 15% TO THE TOTAL OF V.A.T. GOODS AND P & P.

Full SATISFACTION GUARANTEE on all items.

AITKEN BROS

35, High Bridge, Newcastle upon Tyne

Tel: 0632 26729



EXP300



PB6 Kit

EXP300

550 contacts with two 50-point BUS bars. Size 152x53mm. **£6-95.**

PROTO-BOARD 6 KIT

630 contacts, four 5 way binding posts, accepts up to 6 14 pin DIPs. **£10-98.**

CSC LOGIC PROBES

LP-2 ECONOMY PROBE

Min. pulse width 300 nanoseconds, 300 KΩ input impedance, tests circuits up to 1.5MHz. Detecting pulse trains or single-shot event in TTL, DTL, HTL, and CMOS circuits. **£20-95.**

LP-1 Memory Probe **£35-65**

LP-3 High Speed Memory Probe **£56-75**

CSC catalogue available. Please send S.A.E.

CALSCOPE SUPER 6 £186-30

A portable single beam 6MHz bandwidth oscilloscope with easy to use controls. High gain to 10 mm/cm and wide time base range from 1μs to 100 ms/cm. Full specification to request. Please send S.A.E. Professional scopes you can afford.

CALSCOPE SUPER 10 £251-85

A dual trace 10MHz instrument of the very highest performance and quality. It has an accuracy of 3% which is achieved by the use of built-in stabilised power supplies which keep the trace rock steady over a wide range of mains fluctuations. Full specification on request. Please send S.A.E.

TE20D TECH R.F. SIGNAL GENERATOR

Accurately covers 120 KCS to 500 MCS in 6 bands. Directly calibrated. Variable RF attenuator 240 VAC. Size 140x215x170mm.

Price **£52-50 (£50-55 to callers).**

TE22D TECH AUDIO GENERATOR

Sine & square wave audio generator. Sine wave range -20 cps to 20K cps in four bands.

Square wave range 20 cps to 15K cps in four bands 240V A.C. Size 140x215x170mm.


Price **£83-31 (£81-31 to callers).**

TMK 500 MULTIMETER 30,000 o.p.v. AC

volts 2.5, 10, 25, 100, 250, 500, 1000. DC volts 0.25, 1, 2.5, 10, 25, 100, 250, 1000. DC current 50μa, 5MA, 50MA, 12 amp. Resistance 0-6K, 60K, 6MEG, 60MEG. Decibels. -20 to +56 db. Buzzer continuity test size, 160 x 110 x 55MM. Batteries & leads included. **PRICE £25-95.**

CSC EXPERIMENTOR BREADBOARDS

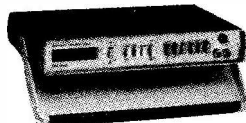No soldering modular breadboards, simply plug components in and out of letter/number identified nickel-silver contact holes. Start small and simply snap lock boards together to build breadboards of any size.



SINCLAIR DM350

£83-95

SINCLAIR DM450

£114-95

Size 255x148x40mm.
DM350 3½ digit display DM450 4½ digit display. Both provide six functions in 34 ranges. D.C. voltage 10μV to 1200V (100μV on DM350) A.C. voltage 100μV to 750V. D.C. current 1nA to 10A. A.C. current 1nA to 10A resistance 10mΩ to 20MΩ (100mΩ on DM350). Accessories for DM350 & 450 as for DM235 below. Full spec. on request. Please send S.A.E.

Sinclair PFM200 frequency meter

Size 157x76x32mm.
Range 20Hz to 200MHz. Accessories and illustration as for PDM35 below. **£57-95.**

SINCLAIR PDM35

DIGITAL POCKET MULTIMETER

DC volts (4 ranges) 1mV to 1000V AC volts 1V to 500V DC current (6 ranges) 1nA to 200MA. Resistance (5 ranges) 1Ω to 20 MEGΩ. **PRICE £39.95 AC Adaptor £4.25 de luxe padded carrying case £1-95 MN 1604 Battery £1-28.**
Size 157x76x32mm.

SINCLAIR DM235

BENCH-PORTABLE DIGITAL MULTIMETER.

DC volts (4 ranges) 1mV to 1000V AC volts (4 ranges) 1MV to 750V AC & DC current 1μa to 1000MA Resistance (5 ranges) 1Ω to 20 MEG Ω. **PRICE £60-98.** Carrying case **£8.95.** AC adaptor/charger. **£4-25.** Rechargeable Battery Pack. **£8-95.**
Size 255x148x40mm.



PANEL METERS

DIMS 60MM x 45MM. 50μ amp, 100μ amp 1MA, 5MA, 10MA, 50MA, 100MA, 500MA, 1 amp, 2 amp, 25V dc, 30V dc, 50V AC, 300V ac, "S", "VU" 50-0-50μa, 100-0-100μa, 500-0-500μa. **PRICE £5-95.**

DESOLDERING TOOL SUCTION PUMP.


£6-45

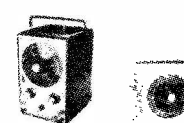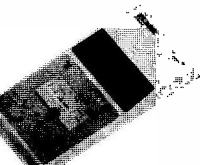Education Establishment Orders Accepted.
PHONE OR SEND YOUR ACCESS OR BARCLAYCARD NUMBER
ALL PRICES INCLUDE POSTAGE AND VAT.



SOME THINGS YOU CAN DO WITHOUT...

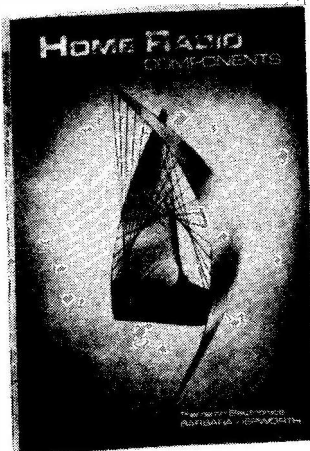but the **HOME RADIO CATALOGUE** is Top Priority for every constructor



- About 2,500 items clearly listed and indexed.
- Profusely illustrated throughout.
- 128 A-4 size pages, bound in full-colour cover.
- Bargain list of unrepeatable offers included free.
- Catalogue contains details of simple Credit Scheme.

HOME RADIO (Components) LTD.,
Dept. PE., P.O. Box 92, 215 London Road, Mitcham, Surrey.
Phone 01-648 8422

Please write your Name and Address in block capitals

NAME

ADDRESS

HOME RADIO (Components) LTD., Dept. PE
P.O. Box 92, 215 London Road, Mitcham, Surrey.

(Regn. No
London 912966




SANSEI LOGIC PROBES 3300A



TESTS TTL AND CMOS
POWER SUPPLY 5-18V DC
HI (RED) LO (GREEN) LED'S
INPUT FREQUENCY DC to 300KHz
INPUT IMPEDANCE 1 MEGOHM
SUPPLIED COMPLETE WITH 16p & 1p IC CLIP CONNECTOR, PROBE CAP & VINYL WALLET
GUARANTEED FOR 12 MONTHS
£15.85 INCL. P&P and V.A.T.

Send Cheque/P.O. to:
TABRIGHT LTD,
Bevan Road, Brockmoor, Brierley Hill,
West Midlands, DY5 3TP Tel: 0384 74433

STORAGE CABINETS

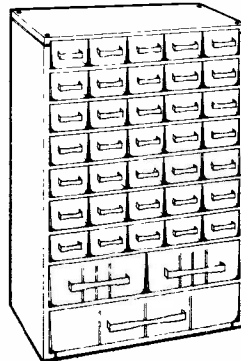

Type 1838

Metal Cabinets 12" wide x 5½" deep, finished blue with transparent plastic drawers.

Type	H (ins)	No. of Drawers	Price
1118	11	15 2 1	£10-75
1633	16	30 2 1	£13-75
1838	18	35 2 1	£15-75
2236	22	30 4 2	£17-85
2260	22	60 - -	£17-95

Access/Barclaycard welcome
Prices include VAT and Post. Cheque/P.O. to:
Millhill Supplies (Tools),
35 Preston Crowmarsh, Benson,
Oxon OX9 6SL.

POST THIS COUPON with cheque or P.O. for £1.30

Another projects book in the "110" series*

110 IC timer projects for the home constructor

Jules H. Gilder

- * Covers in detail the basic operation of the 555 timer IC that will enable you to design your own circuits using this device
- * Divided into three sections describing the basic modes of operation as a monostable device, astable device and logic element
- * Descriptions of applications include timer-based instruments, automotive applications, alarm and control circuits, and power supply and converter applications

1980

126 pages

£3.95

Newnes Technical Books

Borough Green, Sevenoaks, Kent TN15 8PH

*If you are not familiar with previous books in this series for the home constructor, write to the publishers for a free colour brochure of all their hobbyist books

OHIO SCIENTIFIC SUPERBOARD 2

50Hz model for UK tv sets. Full keyboard and cassette interface. Uses your tv as a vdu. 8K basic. 4K ram. Fully assembled £188 + 15% VAT, post free.

- * * * * * Special offer:- If bought with super-board these items are at the reduced price shown first. Also sold separately at the bracketed prices. Add 15% VAT.
- * Modulator and power supply kit £4.95
- * (£7.95). 4K extra ram £25.74
- * (£31.95). Cassette recorder £12.13
- * (£14.74). Case £19 (£21).

SINCLAIR PRODUCTS

PFM200 £51.95, case £3.40, adaptor £4.03, connector kit £11.27. Microvision TV £91.44, mains adaptor £6.88. PDM35 £34.23, mains adaptor £4.03, case £3.40. DM350 £76.70, DM450 £102.17, DM235 £55.55. Accessories for all 3 models - rechargeable batteries £7.99, mains adaptor/charger £4.03, case £8.40, Enterprise prog calculator £19.95. New SC110 10MHz oscilloscope £144.95.

COMPUTER GAMES

Chess champion £49.95. Chess challenger 7 £84. Checker challenger 2 £46. Star chess £62. Grandstand video entertainment computer £79.95. Videocarts £12.60. Philips G7000 Videopak home computer £149. Videopaks £12.95. Atari Videocomputer £147. Cartridges £1.85 (except chess £43.95 and backgammon £33.95).

TV GAMES

Tank battles kit £8.34. AY-3-8500 chip £3.00, kit £4.26. Stunt cycle AY-3-8760 chip £13.71, kit £4.95. 10 game peddle 2 AY-3-8600 chip £10.25, kit £7.03. Racing car chip AY-3-8603 £13.63. Modified shoot kit £5.28. Rifle kit £5.27. Colour generator kit £9.05.

MAINS TRANSFORMERS

6-0-6V 1½ £2.60. 9-0-9V 75ma 76p. 1a £2.22. 2a £3.94. 12-0-12V 100ma 92p. 1a £2.80. 15-0-15V 1a £3.15.

JC12 AND JC20 AMPLIFIERS

Integrated circuit audio amplifier chips with data and printed circuits. JC12 6 Watts £2.08. JC20 10 Watts £3.14.

CONTINENTAL SPECIALITIES PRODUCTS

EXP30 £6.61. EXP350 £3.62. EXP325 £1.84. EXP850 £4.14. EXP48 £2.64. LP2 £20.70.

PRINTED CIRCUIT MATERIALS

PC etching kits - economy £2.42, standard £4.46. 40 sq ins pcb 45p. 1 lb FeC1 £1.30. Etch resist pens - economy 50p, dalo 84p. Drill bits 1/32" or 1mm 30p. Etching dish 92p. Laminate cutter 90p.

HI-PAK AUDIO MODULES

AL30A £4.08. PA12 £8.38. PS12 £1.58. TS38 £2.70. S450 £25.06. AL60 £5.06. PA100 £17.33. SPM80 £4.74. BMT80 £6.06. Stereo 30 £21.57. AL80 £7.71.

S-DECS AND T-DECS

S-Dec £3.79. T-Dec £4.59. u-DecA £4.69. u-DecB £7.16.

BATTERY ELIMINATORS

3-way types with switched output and 4 way multi-jack:- 3/4/6V 100ma £2.39. 6/7/9V 300ma £3.14. 100ma radio types with press stud connectors 9V £3.57. 6V £3.57. 4.5V £3.57. 9-9V £4.79. 6+6V £4.79. 4+4.5V £4.79. Cassette recorder mains unit 7.5V 100ma with 5 pin din plug £3.57. Fully stabilized type 3/6/7.5/9V 400ma £5.89. Car converters 12V dc input, output 9V 300ma £1.19. output 7.5V 300ma £1.19. output 3/4+6/7.5/9/12V 800ma £2.66.

BATTERY ELIMINATOR KITS

100ma radio types with press-stud connectors 4.5V £1.49. 6V £1.49. 9V £1.49. 4+4.5V £1.92. 6+6V £1.92. 9+9V £1.92. Cassette type 7.5V 100ma with din plug £1.49. Heavy duty 13 way types 4+6/7/8.5/11/13/14/17/21/25/28/34/42V 1A £4.95. 2A £8.20. Car converter input 12V dc, output 6/7.5/9V 1A stabilized £1.35.

STABILIZED POWER KITS

The bracketed price is for kit without transformer, the bracketed price includes transformer. TTL computer supply 5V 2A £2.95 (£6.45). 5V 4A £3.95 (£10.32). 8-way types 3/4/6/7.5/9/12/15/18V 100ma £1.74 (£2.50). 1A £3.18 (£5.30). 2A £4.17 (£8.15). Variable voltage models 2-18V 100ma £2.12 (£2.98). 1-30V 1A £3.18 (£6.20). 1-30V 2A £4.98 (£11.24).

COMPONENTS

1N4148 0-5p. 1N4002 2-9p. 1N4004 3-4p. BC109B 5-5p. 723 14 di1 33p. NE555 8 di1 24p. bc183, bc213, bc547, bc549 4-9p. bc182, bc184, bc212, bc214, bc548 5-5p. tip31c, tip32c, 36p. tip41c 40p. bc131, bc132 2-7p. plastic equiv bc72 5p. fuses 20mm x 5mm cartridge -15, 25, 5, 1, 2, 3, 5 Amp quickblow 1p. anti-surge 3-6p. resistors 5% 1W E12 10R to 10M 1p. 0.8p for 50+ of one value, polyester capacitors 250V 015, 068, 1mf 1.5p, 01mf 3-5p. 022 033mf 3-5p. 047mf 3-5p. 15, 22, 33, 47mf 4-9p. polystyrene capacitors E12 63V 10 to 1000pf 3p. 1n2 to 10n 4p. ceramic capacitors 50V E6 22pf to 47n 2p. electrolytic capacitors 50V 5V 5, 1, 2mf 5p. 25V 5, 10mf 5p. 16V 22, 33mf 5p. 47, 68mf 3-5p. 100mf 6p. 330, 470mf 9p. 1000mf 10p. zeners 400mW E24 2V7 to 33V 7p. preset pots subminiature 0.1W horiz or vert 100 to 4M7 7p. potentiometers 1W 4K7 to 2M2 log or lin single 27p, dual 7p. 1 red LEDs 9-7p. ic sockets 8 di1 8-7p. 14 di1 10-1p. 16 di1 12p.

SWANLEY ELECTRONICS Dept. PE

32 Goldsrd Rd., Swanley, Kent BR8 8EZ.

Mail order only. Please add 30p postage. Prices include VAT unless stated. Lists 24p post free. Overseas customers deduct 13%. Official credit orders welcome.

TRAIN AT HOME

Be an ELECTRONIC ENGINEER

Do something PRACTICAL about your future. Firms all over Britain are crying out for qualified people. With the right training, you could take your pick of these jobs.

Now, the British Institute of Engineering Technology will train you in your spare time to be an Electrical Engineer.

You risk nothing! We promise to get you through your chosen course-or, refund your fee!

So, join the thousands who have built a new future through home study Engineering courses.

- Courses in
- C & G Elect. Technicians
- C & G Elect. Installations
- Telecomms. Technicians Exams
- Television Servicing
- Radio Maint. & Repairs (BIET)
- Pract. Radio & Electronics
- Plus over 60 other home study courses.

POST COUPON FOR FREE 44 PAGE GUIDE

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Aldermaston Court, Dept. TEE50 Reading RG7 4PF.

NAME (Block capitals please) _____
ADDRESS _____
POSTCODE _____
Other Subjects _____ AGE _____
Accredited by CACC Member of ABCC

PANELS, SCALES, CHASSIS AND FACIAS

Screenprinted to your special layout requirements, one-offs or quantity production.

Ashman and Clough Ltd.,
Designers and Printers,
7 Chapel Lane, Blisworth,
Northampton. (0604) 858274.

DIGITAL WATCH BATTERY REPLACEMENT KIT



These watches all require battery (power cell) replacement at regular intervals. This kit provides the means. We supply eyeglass, non-magnetic tweezers, watch screwdriver, case knife and screwback case opener. Full instructions and battery identification chart. We then supply replacement batteries—you fit them. Begin now. Send **£7.50** for complete kit and get into a fast growing business. Prompt despatch.

WATCH BATTERY REPLACEMENT CO.
(PE11)
11 Percy Avenue, Ashford, Middx. TW15 2PB.

ULTRASONIC TRANSDUCERS. £2.85 per pair + 25p P. & P. Dataplus Developments, 81 Cholmeley Road, Reading, Berks.

GUITAR/PA/MUSIC AMPLIFIERS

100 watt superb treble/bass, overdrive. 12 months guarantee. Unbeatable at **£48**; 60 watt **£38**; 40 watt **£34**; 200 watt **£90**; 100 watt twin channel sep. treble/bass per channel **£58**; 60 watt **£48**; 200 watt **£72**; 100 watt four channel sep. treble/bass per channel **£76**; 200 watt **£92**; slaves 100 watt **£32**; 200 watt **£60**; fuzz boxes, great sound **£10.00**; bass fuzz **£10.90**; overdriver fuzz with treble and bass boosters **£18.00**; 100 watt combo superb sound overdrive, sturdy construction, castors, unbeatable **£92**; twin channel **£100**; bass combo **£105**; speakers 15in. 100 watt **£35**; 12in. 100 watt **£23**; 60 watt **£18**; microphone Shure Unidyne B **£28**.

Send cheque or P.O. to:
WILLIAMSON AMPLIFICATION
62 Thorncliffe Avenue, Dukinfield, Cheshire.
Tel: 061-308 2064

PRINTED CIRCUITS. Make your own simply, cheaply and quickly! Golden Fotolak Light Sensitive Lacquer - now greatly improved and very much faster. Aerosol cans with full instructions **£2.25**. Developer **35p**. Ferric Chloride **55p**. Clear Acetate sheet for master **14p**. Copper-clad Fibreglass Board approx. 1mm thick **£1.70** sq. ft. Post/packing **60p**. **WHITE HOUSE ELECTRONICS**, P.O. Box 19, Castle Drive, Penzance, Cornwall.

GAMES FOR COMPUKIT

At last - 3 exciting programs to run on your UK101-COMPUKIT.
Attack - Four In A Row - Magic Drawing Board
Cassette containing all three programs
only **£6**.

R. A. LILLEY

41 Cunningham Ave., Guildford GU12PE

CLEARING LABORATORY. Scopes, recorders, testmeters, bridges, audio, R.F. generators, turntables, tapeheads, stabilised P.S.U.s, sweep generators, test equipment, etc. Lower Beeding 236.

NO LICENCE EXAMS NEEDED

To operate this miniature, solid-state **Transmitter-Receiver Kit**. Only **£10.95** plus 25p P. & P. 'Brain-Freeze' 'em with a **MINI-STROBE** Electronics Kit, pocket-sized 'lightning flashes', vari-speed, for discos and parties. A mere **£4.75** plus 25p P. & P. Experiment with a psychedelic **DREAM LAB**, or pick up faint speech/sounds with the **BIG EAR** sound-catcher: ready-made multi-function modules, **£5.45** each plus 25p P. & P.
LOTS MORE! Send 30p for lists. Prices include VAT.

BOFFIN PROJECTS

4 Cunliffe Road, Stoneleigh
Ewell, Surrey (P.E.)

NICKEL CADMIUM BATTERIES

Rechargeable and suitable for fast charge HP7 (AA) **£1.05** SUB C **£1.38**, HP11 (C) **£1.98**, HP2 (D) **£3.02**, PP3 **£3.79**, PP3 charger **£5.40**. All the above nickel cadmium batteries are brand new and are guaranteed full spec. devices. All cells are supplied complete with solder tags (except PP3). Brand new full spec. **RECHARGEABLE SEALED LEAD ACID** maintenance free batteries suitable for burglar alarms etc. 1-2 amp hr. 6V **£4.07**, 2-6 amp hr. 6V **£5.23**. Quantity prices available on request. Data and charging circuits free on request with orders over £10 otherwise 30p post and handling (specify battery type). Please add 10% P&P in orders under £10 - 5% over £10. VAT at the current rate should be added to total order. Cheques, Postal Orders. Mail order to:
SOLID STATE SECURITY DEPT (PE), 10 Bradshaw Lane, Parbold, Wigan, Lancs. Tel: 02575 4726.

PRACTICAL ELECTRONICS P.C.B.'s

Professional quality glassfibre, Fry's roller tinned and drilled.
Nov. 79 Diamatic EC10 **£2.26**
Digital dark room timer EG199 **£1.85**
Dec. 79 Ultrasonic burglar alarm EP200 EG126. Set of 2 pcb's **£2.06**
Cost a call EP216 **£1.38**
Feb 80 Dynamic noise limiter EG276 **£1.98**. Pso, EG274, 83p. Set of two **£2.60**.
Feb 80 Electrostat EG257 **£1.73**.
Mar 80 Audio isolator EG285 **89p**.
Frequency meter EG290 **£3.43**.
For full list and current pcb's please send SAE. Pcb's also produced to customers own masters. Trade enquiries welcome. Please write for quote. CVO Please.
Postage - Please add 30p postage and packing to complete order.

PROTO DESIGN

14 Downham Road, Ramsden Heath
Billericay, Essex CM11 1PU
Telephone 0268-710722

MK14 CORNER. Interface Board, includes flag driven mains relays, LED Indicators for all Serial I/O, A/D and single step chips, and prototype area; PCB and circuit **£3.95**. Replace calculator display with 3/4" FND 500's; PCB, filter, instructions **£1.95**. Ready Built replacement Keyboard **£11**. Useful notes on MK14 75p; programming sheets; PAD 95p. Rayner, 'Kismet' High St., Colnbrook, Bucks.

LEARN ELECTRONICS WITHOUT SOLDER

Built-in electronic circuits without solder on a Roden S-Dec. This has built-in contacts and holes into which you plug your components. Suitable for all ages. Can be used time after time. Ideal gift for students or experimenters. Full instructions and 2 circuit diagrams with each S-Dec.
Send cheque or P.O. to:
Roden Products, Dept PE
High March, Daventry,
Northants, NN11 4QE. **£3.85** plus 40p p.&p. each

SUPERB INSTRUMENT CASES BY BAZELLI, manufactured from P.V.C. Faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a Low **£1.05**. Chassis punching facilities at very competitive prices, 400 models to choose from. Suppliers only to Industry & The Trade. **BAZELLI** (Dept. No. 23), St. Wilfrids, Foundry Lane, Halton, Lancaster, LA1 6LT.

MAKE YOUR OWN PRINTED CIRCUITS

Etch Resist Transfers - Starter pack (5 sheets, lines, pads, I.C. pads) **£1.60**. Large range of single sheets in stock at 34p per sheet.
Master Positive Transparencies from P.C. layouts in magazines by simple photographic process. Full instructions supplied. 2 sheets (20 x 25cm) negative paper and 2 sheets (18 x 24cm) positive film **£1.30**.
S.A.E. lists and information. P&P 30p/order

P.K.G. ELECTRONICS
OAK LODGE, TANSLEY, DERBYSHIRE

USED I.L.P. MODULES, BI-Pak AL60 Case Details S.A.E. Noble, 50 Croft Hill Road, Slough, Berks.

RECHARGEABLE BATTERIES

TRADE ENQUIRIES WELCOME

FULL RANGE AVAILABLE. SAE FOR LISTS. **£1.25** for Booklet 'Nickel Cadmium Power' plus Catalogue. Write or call: Sandwell Plant Ltd., 2 Union Drive, BOLDMERE, SUTTON COLDFIELD, WEST MIDLANDS, 021-354 9784, or see them at T.L.C. 32 Craven Street, Charing Cross, London WC2.

QUALITY ELECTRONIC COMPONENTS AT LOW PRICES

Write or telephone for free pamphlet to:
HARRISON BROS.
Dept. P.E. Box 55, Westcliff-on-Sea,
Essex SS0 7LQ.
Telephone: Southend-on-Sea 32338

TIME?

ALWAYS CORRECT. MSF CLOCK never gains or loses, 8 digits show DATE, HOURS, MINUTES and SECONDS, auto GMT/BST and leap year, also second-in-a-month STOP CLOCK and parallel BCD output - for alarm etc. receives Rugby time signals, built-in antenna, **ABSOLUTE TIME, £48.80**.
60KHz Rugby Receiver, as in MSF Clock, 1000km range, audio and serial data outputs, **£13.70**.
SIG. GEN., 10Hz-200KHz, logic and variable sine and square wave outputs, harmonics for if, rf, **£10.80**.

Each fun-to-build kit includes all parts, printed circuit, case, postage etc, money back assurance so SEND off NOW.

CAMBRIDGE KITS

45 (FD) Old School Lane, Milton, Cambridge.

PRINTED CIRCUIT PROBLEMS? We can solve them. We specialise in P.C.B. artwork, design and manufacture at competitive rates. Small quantity or one-offs welcome. P.C.B.'s supplied built-up or bare, tested or untested. Electromechanical design on control work for motors, mechanical handling, traffic control, security systems, hybrid one-offs, etc., to completed control panel stage if required. Electronic circuit designs utilising digital and/or analogue disciplines with microprocessor applications. Efficient turn round - fixed price quotations. Just send circuit details. Contact Aardvark Electronics, Byron House, 140 Front Street, Arnold, Nottingham. Tel. Nottm. (0602) 269606.

RYDER ORGAN SYSTEM

The W.W. classical design for full-size keyboards, including couplers. Expanded range of units now includes chorus, vibrato, combination stop-control.
Data, p.c. boards, from:
HIYKON LTD. (P),
Woodside Craft, Ladybridge Lane,
Bolton BL1 5ED.

PARALLEL-TRACKING PICKUP ARM. Simple optoelectronic design as featured in 'Wireless World' Jan. 1980. Build your own from ready-machined parts. S.A.E. for full details to: J. Biles, 120 Castle Lane, Solihull, West Midlands.

NEAT! TIDY! HANDY! 1D 2D 3D 6D INTERLOCKING PLASTIC STORAGE DRAWERS

AS SUPPLIED: TO POST OFFICE & GOVT DEPTS

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units


interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

SINGLE UNITS (1D) (5in+2 1/2in+2 1/2in) £3.90 DOZEN
DOUBLE UNITS (2D) (5in+4 1/2in+2 1/2in) £8.50 DOZEN
TREBLE (3D) £5.90 for 8.
DOUBLE TREBLE 2 drawers, in one outer case (6D2), £8.90 for 8.
Extra large size (6D1) £7.90 for 8.

PLUS QUALITY DISCOUNTS
Orders over £60, less 5%. Packing/Postage/Carriage: Add £1.30 to all orders under £10. Orders £10 and over, please add 10% carriage.

QUOTATIONS FOR LARGER QUANTITIES
Please add 15% V.A.T. to total remittance.
All prices correct at time of going to press.

FLAIRLINE SUPPLIES (PE4) 124 Cricklewood Broadway, London N.W.2. Tel: 01-450 4844.



Readily available Hardware and Accessories for Home Constructors, Dev. Engineers, Modelmakers. Selected range of quality components, Drawing materials for p.c. boards, Reliable resist coated epoxy glass laminate, no unusual chemicals. Printed circuit boards, top quality to personal designs, prompt service. Photography for p.c.b. Solid tungsten carbide drills.

All immediately available.
Catalogue 15p stamps please to:

RAMAR CONSTRUCTOR SERVICES,
Masons Rd. Stratford on Avon
Warwks. CV37, 9NF 0789-4879

THE LEARN —CW!! way. Beginners tuition aid for Morse Code listening. Instructions and exercises on 4 cassette tapes. Computer generated audio tones, 6.5 to 16.5 w.p.m. £7.50 inc p&p. (UK). Extra single practice tapes 14.5 w.p.m. (C60) at £2.50 inc. p&p (UK). D. M. Rogers, 106/108 Shakespeare Street, Southport, Merseyside.

HIGH QUALITY PCB's

From your own artwork master negative or positive maximum 12" x 12"

Manufactured in glass fibre tinned and drilled
Express service for prototypes and small production runs
Small contract circuit boards assembled
Gold plating for reliability where edge connectors are used

ANODISED SELF ADHESIVE FASCIA PANELS WITH LEGENDS

Manufactured from your own artwork master
Various colours available brushed and satin finish
Express service and competitive prices

Send artwork or phone for prices
.125W 5% C.F. Resistors E12 Series 1p each
IN4148 Diodes 2p each
Ecoscope Instruments Ltd.,
51 Sandilands St., Glasgow G32.
041-778-2555.

SEEN MY CAT? 5000 Odds and ends. Mechanical. Electrical. Cat. free. Whiston Dept. PRE. New Mills, Stockport.

MEMORY MART

'UK 101' 'Superboard' 4K RAM **£35.00**
Memory Expansion **£4.50**
2114 1k x 4 each **£4.50**
2708 UV prom each **£6.50**

P & P 20p.
C.O.D. 60p extra.

MEMORY MART
19 Weatherby Gardens,
Hartley Wintney, Hants.

UK 101 SOFTWARE. Try our original programmes (on cassette) **GRAPHIC PAINT BRUSH** — **GRAPHIC PLOTTER** etc. Working programmes that will give you ideas of your own. S.A.E. M & B SERVICES, 182a High Street, Margate, Kent.

BURGLAR ALARM EQUIPMENT. Latest discount catalogue out now! Phone C.W.A.S. Alarm 0274 682674.

APPOINTMENTS

PADDINGTON COLLEGE

Paddington Green, London W2 1NB

TECHNICIAN STAFF

**in the
ENGINEERING TECHNOLOGY
DEPARTMENT:**

- (1) **CHIEF ELECTRONICS TECHNICIAN** grade 7 to be responsible to the Departmental Superintendent for the organisation and servicing of the radio/TV and electronics laboratories. Candidates must have HNC or HND or Advanced City and Guilds or equivalent, with at least ten years' experience (including training period). Salary scale £4941 to £5550, plus London Weighting £780.
- (2) **TECHNICIAN** grade 6 to be responsible for the satisfactory running of the **ELECTRONIC/MICRO-ELECTRONIC** laboratory. Some experience of micro-processors and use of computer terminals highly desirable. Candidates must have HNC or HND or Advanced City and Guilds or equivalent, with at least nine years' experience (including training period). Salary scale £4242 to £5067 plus £780 London Weighting.

Further details and application forms from the Secretary to the Department (ref: E/MDA).

SITUATIONS VACANT

Electronics Field-Technicians

Company Car

Linotype-Paul field technicians install, commission and service real time high technology systems for the printing/publishing industry. Our technicians can think logically, work alone and provide a timely, accurate service. Because they meet customers, often at high level, they also have to be diplomatic, tactful and friendly.

We want to build our team with men and women who are qualified to ONC level and have several years experience on electronics equipments which we will complement with progressive product training.

We provide a competitive salary and generous expenses and benefits. As there is considerable travel, sometimes involving overnight stays, a company car is provided which is available for private use. In time there may be the opportunity to work abroad for short periods.

We are continually expanding our markets and products and career prospects could not be better.

If you are interested contact: Personnel Department, Linotype-Paul Limited, Kingsbury Road, Kingsbury, London NW9. (01-205-0123)

Linotype-Paul

ASSISTANT FILM RECORDISTS AND TRAINEES

Would you like to specialise in sound with the BBC TV's Film Department?
There are vacancies in West London.

ASSISTANT FILM RECORDISTS work initially in sound transfer and dubbing areas operating sound recording and reproduction equipment for a wide range of programmes. There are prospects of progressing to mobile Film Recording work in due course. If you have professional experience in this field, the starting salary would be £4,185 p.a., perhaps higher if exceptionally qualified, rising to £5,605 p.a. An additional allowance is paid for shift work (not nights). Normal hearing essential.

EXCELLENT TRAINING is given if you have ambitions to do this type of work but lack

experience. You will need good 'O' level standard of education or equivalent, including Physics and Maths and a basic knowledge of electronics. You should be able to demonstrate a practical interest in sound and recording. Trainees will start at a salary of £3,800 p.a. at the end of August 1980, and should qualify for promotion to Assistant Film Recordists about a year later.

Salary review date April. Conditions of Service excellent. Contact us immediately for application form (quote ref. 2053/PE and enclose s.a.e.): **BBC Appointments, London W1A 1AA. Tel: 01-580 4468 Ext: 4619.**

BBC tv

COLOUR VDUS

FROM **£40** +VAT

Why dismantle your family's T.V. for a computer, CEEFAX or T.V. game? We can supply you with a HUGE range of working Ex-Rental C.T.V.'s suitable for adaption as V.D.U.'s.

Prices from **£40.00** +VAT.

Most makes (inc. Japanese) can be seen working in our warehouse. Working B/W T.V.'s also available from **£10.00** +VAT.

Deliveries arranged.
Write or phone for Details and Catalogue.

**W.M.T.V. Dept. P.E., Faraday Buildings, 92, High Street,
Kings Heath, Birmingham 14.**

Tel. 021-444 6464

PROGRESSIVE RADIO 31, CHEAPSIDE, LIVERPOOL L2 2DY
SEMICONDUCTORS. Texas R1038 T03 power trans. 50p. TBAB00 50p. 741 8 pin 22p. NE555 24p. TAG4443 SCR 45p. 723 14 PIN REGS. 35p. AD161/2 MATCHED PAIRS 70p. 2N5062 SCR 18p. 1N4005 10 for 35p. BD238-28p. BD438 28p. MPU131 P.U.T.'s 40V, 200mA, 375M/W 18p each. 2N3773 £1.75. Infra Red 0.2" LEDs 30p.
MINIATURE WINDING TRANSFORMERS. ALL 240VAC PRIMARY. 6-0-6 100mA, 9-0-9 75mA, 12-0-12 50mA all 75p each. 12V 200mA 75p. 6V 500mA £1.10p. 0-6V-0-6V 280mA £1.30p.
PULSE TRANSFORMERS. 1:1 (GPO type) 30p. 1:1 plus 1 min. P. C. mounting 60p.
MINIATURE SOLID STATE BUZZER. 33x17x15mm, output at 3 feet 70db, only 15mA drain, operating range 4-15VDC 75p each.
LOUD BUZZER. 6-12 volts 65p. GPO type adjustable buzzer 6-12 volts 27p.
POCKET MULTIMETER. MODEL N155 2,000 ohms per volt, 1,000 volts AC/DC, 100mA DC current, 2 resistance ranges to 1 meg. £5.50p.
SOLDER SUCKER. High suction/teflon nozzle, £4.65p
MURATA TRANSDUCERS. 40KHz. REC/SENDER £3.80 pair.
MOTORS. 3V model type 22p. 12V model 5 pole 38p. Replacement 12VDC 8 track motors 55p. Ex. equip. 5-7 volt cassette motors 70p. Low rev. mains motor 240VAC motor with gearbox 2 1/2 RPM 75p.
AMPHENOL COAX CONNECTORS. Plugs 47p, Sockets 42p, Elbows 50p, Reducers 13p, BNC plugs, crimp 38p.
HIGH IMPEDENCE HEADPHONES, mono 2,000 ohms imp. transducer type, adjustable band and padded ear-piece £2.75.
SPECIAL OFFER STEREO HEADPHONES. 8 ohms, adjustable, standard stereo plug only £2.95p.
INTERCOM UNITS (can be used as baby alarm) supplied with approx. 60' cable, call button, 2 way £5.25 pair, 3 way £7.25p. **WIRELESS INTERCOM,** 2 units both operate on 240VAC and mains connected, AM frequency 180KHz. £25.95p.
MINIATURE TIE PIN MICROPHONE. Omni, 1K imp., uses deaf aid battery (supplied) £4.95p. **LOW COST CONDENSER MIKE.** Stick type, Omni, 600 ohms, on/off switch, standard jack plug only £2.95p. **EM507 CONDENSER MICROPHONE.** Highly polished metal stick mike, uni directional, 600 ohms, 30-18KHz., on/off switch only £7.95p. **DYNAMIC STICK MIKE.** CARDIOD, dual imp., 600 ohms or 20K, 70-15K Hz., attractive black metal case only £7.75p.
PUBLIC ADDRESS HORN SPEAKERS. Suitable for outdoor use. 5" round 8 watts, 8 ohms, adjustable bracket £4.95p, 6" 15 watts 8 ohms adjustable bracket £8.25p.
CRIMPING TOOL, for standard terminals also 6 gauge stripper and wire cutter, insulated handles only £2.30.
Cash with order please, official orders welcome from schools etc. please add 30p post and packing. VAT inclusive. SAE for latest illustrated stock list. ALL ORDERS DESPATCHED BY RETURN POST

BUILD A SYNTHESISER!

**NO SPECIAL SKILLS
SPECIAL EQUIPMENT REQUIRED**



Using **Dewtron** (Reg'd)
PROFESSIONAL MODULES

Over 20 different electronic modules to select what YOU want to build a synthesiser; simple or complex. Start simple and add to it as you can afford. New attractive prices for the long-popular, well-tried range of Dewtron synthesiser and other effects modules.

Send 25p for Musical Miracles Catalogue NOW!

D.E.W. LTD.

254 RINGWOOD ROAD, FERNDOWN, DORSET BH22 9AR



New Bear Components



CALLERS AND MAIL ORDER: 40 Bartholomew Street, Newbury, Berks. Tel: 0635 30505

Microcomputing I.C.'s

MC6800	£ 7.15
MC6802	£ 8.50
MC6821	£ 4.63
MC6850	£ 6.74
MC6810AP	£ 3.61
MC6840	£ 12.72
MC8602P	£ 2.88
MC14536P	£ 3.69
MC3459	£ 2.43
Z80 CPU 2.5MHz	£ 8.99
Z80 P10 2.5MHz	£ 7.99
Z80 CTC 2.5MHz	£ 7.99
Z80A CPU 4MHz	£ 13.99
Z80A P10 4MHz	£ 10.00
Z80A CTC 4MHz	£ 10.00
SC/MP 11	£ 8.88
(INS 8060N)	
INS 8154N	£ 8.18
8080A	£ 6.00
6502	£ 9.90
6522	£ 7.90
6532	£ 12.56
6551	£ 10.79
6545	£ 16.66
Z8001	£142.50
AMD 9511: arithmetic package	£136.50

ACORN.....

SI00 at NEWBEAR

Z80 CPU BOARD	£26.25
8K STATIC RAM BOARD	£18.75
DISK INTERFACE BOARD	£26.25
V.D.U. BOARD	£18.75
2708/2716 EPROM BOARD	£18.75
PROTOTYPING BOARD	£18.75
RANGE OF MOTHERBOARDS	
SI00 CONNECTORS	£ 3.95

Memories

4116 (16K DYNAMIC)	£ 6.99
2102-1*	£ 0.85
2102L-1*	£ 0.99
2112	£ 2.25
2114	£ 6.99
2708	£ 6.99
MC68031.7 (MIKBUG)	£ 13.65
2716 (INTEL)	£ 21.50

6502 BASED MICRO KIT	£65.00
8K RAM KIT	£95.00
MAINS ADAPTOR	£ 5.00
V.D.U. KIT	£88.00

SPECTRONICS

UV Eprom-Erasing Lamp

PE14 Erases up to 6 chips. Takes approx. 19 mins.	£ 56.00
PE14T* Erases up to 6 chips. Takes approx. 19 mins.	£ 76.58
PE24T* Erases up to 9 chips. Takes approx. 15 mins.	£111.22
PR125* Erases up to 6 chips. Takes approx. 7 mins.	£237.84
PR320T* Erases up to 36 chips. Takes approx. 7 mins.	£384.09
PC1000* Erases up to 72 chips. Takes approx. 7 mins.	£842.83

UV Eprom-Erasing Cabinet

PC2000* Erases up to 144 chips. Takes approx. 7 mins.	£1227.69
---------------------------------------------------------------	----------

* Includes a 60 min. Timer.

TERMS: Credit Sales (minimum £10.00) Barclaycard and Access Welcome. Please add 15% VAT.

CALLERS ONLY: 220-222 Stockport Road, Cheadle Heath, Stockport Tel: 061 491 2290
SEND FOR OUR NOVEMBER CATALOGUE AND BOOK LIST.



Wilmslow Audio

THE firm for speakers!

SEND 30p STAMP FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS, ETC. AND DISCOUNT PRICE LIST

AUDAX ● AUDIOMASTER ● BAKER
BOWERS & WILKINS ● CASTLE ● CELESTION
CHARTWELL ● COLES ● DALESFORD
DECCA ● EMI ● EAGLE ● ELAC ● FANE
GAUSS ● GOODMAN'S ● I.M.F. ● ISOPHON
JR ● JORDON WATTS ● KEF ● LEAK ● LOWTHER
McKENZIE ● MONITOR AUDIO ● PEERLESS
RADFORD ● RAM ● RICHARD ALLAN ● SEAS
SHACKMAN ● STAG ● TANGENT ● TANNOY
VIDEOTONE ● WHARFEDALE ● YAMAHA

WILMSLOW AUDIO (Dept. P.E.)
SWAN WORKS, BANK SQUARE, WILMSLOW,
CHESHIRE SK9 1HF

Discount Hi-Fi, etc. at 5 Swan Street

Tel.: Wilmslow 529599 for Speakers

Tel.: Wilmslow 526213 for Hi-Fi

PLEASE MENTION

PRACTICAL ELECTRONICS
WHEN REPLYING TO ADVERTISEMENTS

LB ELECTRONICS

PROCESSOR ICs (ALL FULL SPEC.)

1702A £2.50, 2708 £7.25, 2716 single rail £28.50, LM323K 5 volts 3 amps £4.50, 7805 £1, 7812 £1.

DIL SKTS LOW PROFILE: 8 way 12p, 14 way 15p, 18 way 20p, 16 way 17p, 20 way 23p, 22 way 28p, 28 way 45p, 24 way 35p, DIL 16 WAY HEADER SPECIAL OFFER ONLY 45p.

74116 SPECIAL OFFER 75p, 74125 4 for £1, 74198 75p, 74194 50p, 74181 80p.

MM5240 character generator + data £3.50.

4 digit EX calculator display 4 for £1 + data.

P.E.T. edge connector (memory expansion) £1.40.

74LS. C.MOSS, sub miniature toggles, 74TTL, and computer equipment is stocked, i.e. V.D.U. printers etc. vast range of power supplies for callers.

L.B. ELECTRONICS, 11, HERCIES ROAD, HILLINGDON,

MIDDLESEX.

UXBRIDGE 55 399

(Just off A40)

OPEN: Monday, Thursday, Friday and Saturday 9.30-6.00.



STEP INTO A NEW WORLD WHEN YOU DISCOVER **MAPLIN**

For beginners or professionals, the Maplin catalogue will help you find just about everything you need for your project.

Over 5,000 of the most useful components — from resistors to microprocessors — clearly described and illustrated.

Send the coupon for your copy
and **STEP UP TO
MAPLIN SERVICE
NOW**



Post this coupon now for your copy of our 1979-80 catalogue price 70p.

Please send me a copy of your 280 page catalogue. I enclose 70p (plus 46p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.35 or ten International Reply Coupons. I enclose £1.16.

NAME _____

ADDRESS _____



MAPLIN

ELECTRONIC SUPPLIES LTD

All mail to:-

P.O. Box 3, Rayleigh, Essex SS6 8LR.

Telephone: Southend (0702) 554155.

Shop: 284 London Road, Westcliff-on-Sea, Essex. (Closed on Monday).

Telephone: Southend (0702) 554000.