

PRACTICAL

MARCH 1985 • £1.00

# ELECTRONICS

ROBOTICS • MICROS • ELECTRONICS • INTERFACING

**EXTRA  
8 PAGES!**

**LOW COST  
BBC SPEECH  
SYNTHESISER**

**HEART BEAT  
MONITOR**

**OSCILLOSCOPE  
SPECIAL OFFER!**

**New BBC FORUM**





# Industrial Soldering Equipment-for the discerning amateur


SEND FOR NEW CONCISE LEAFLETS


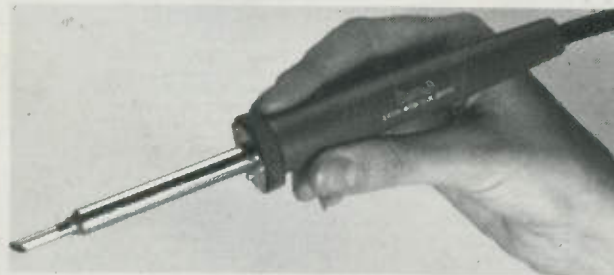
## 'K' SERIES SOLDERING TOOLS FOR ALL APPLICATIONS

- K1000 micro soldering
- K2000 general electronic soldering
- K3000 heavy duty soldering

● Small selection of  
**AD-IRON® LONG LIFE  
SOLDERING TIPS**  
suitable for all Adcola  
soldering irons.



*AD-IRON Soldering  
Tips*

B42LL B38LL B50LL B14LL B35LL B44LL B36LL B37LL B46LL B40LL



## 101 ELECTRONIC CONTROLLED SOLDERING STATION

for precision soldering  
with accuracy suitable  
for use on MOS, FET etc  
240V input - 24V on tool.  
Temperature range  
120-420°C  
*Many extra features*

## ADCOLA ACCESSORIES include: SIDE CUTTERS



## SNIPE NOSE PLIERS



## PLUS

- Desoldering Braid
- Desoldering Guns
- Tip cleaners
- Soldering aids
- Lamps, Lenses etc

# ADCOLA

(Regd Trade Mark)

## ELECTRONIC PRODUCTION EQUIPMENT

*For a no obligation demonstration, please contact:*

ADCOLA PRODUCTS LIMITED Gauden Road London SW4 6LH  
Telephone Sales (01) 622 0291 Telex 21851 Adcola G

## CONSTRUCTIONAL PROJECTS

<b>HEART BEAT MONITOR</b> by P. Leah .. .. .	10
Digital readout of your heart beat	
<b>AUTO SHUT-DOWN MULTIPLE REGULATOR</b> by Tom Gaskell BA(Hons) CEng MIEE .. .. .	18
Monitor system for a three rail power supply	
<b>LOW COST BBC SPEECH SYNTHESISER</b> by A. Foord .. .. .	31
Effective speech synthesis for the Beeb	
<b>MODULAR AUDIO POWER SYSTEM—Part 2</b> by M. Tooley BA and D. Whitfield MA MSc CEng MIEE ..	40
Dummy Load; Pre-amp; Mixer and Tone Controls	
<b>NEPTUNE AND MENTOR ROBOTS</b> by Richard Becker and Tim Orr .. .. .	48
Part Seven: Commissioning and testing of Mentor	

## GENERAL FEATURES

<b>SEMICONDUCTOR CIRCUITS</b> by Tom Gaskell BA(Hons) CEng MIEE .. .. .	17
Quad Supply and Line Monitor (UC 3903)	
<b>MARS ELECTRONICS</b> by Richard Barron .. .. .	22
Computer applications and control in industry	
<b>INGENUITY UNLIMITED</b> .. .. .	26, 50
Readers' circuit ideas	
<b>BBC MICRO FORUM</b> by D. Whitfield MA MSc CEng MIEE .. .. .	36
A scintillating cauldron of new ideas for BBC wizards	
<b>SPACEWATCH</b> by Dr. Patrick Moore OBE .. .. .	52
<b>SEQUENTIAL LOGIC TECHNIQUES</b> by M. Tooley BA and D. Whitfield MA MSc CEng MIEE ..	54
Part Six: De-multiplexing and time domain multiplexing	

## NEWS & COMMENT

<b>EDITORIAL</b> .. .. .	7	<b>BAZAAR</b> .. .. .	16	<b>INDUSTRY NOTEBOOK</b> ..	59
<b>NEWS &amp; MARKET PLACE</b> .. .. .	8	<b>SPECIAL OFFER</b> .. .. .	28	<b>P.C.B. SERVICE</b> .. .. .	60
		<b>LEADING EDGE</b> .. .. .	39		




The INMOS CAD design system lays out and simulates VLSI circuits.


A designer instructs the system where a transistor, or other structure is to be placed, and the screen displays an appropriate layout, obeying the design rules. It also stops the designer from for example, attempting to put two structures too close together.

Created for the design of INMOS' transputer the system is now available from Racal Redac as part of their CIEE electronics design and engineering package.

### SCOPE OFFER . . .

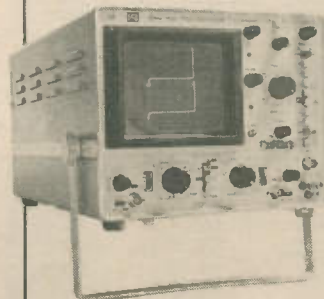

. . . See Page 28

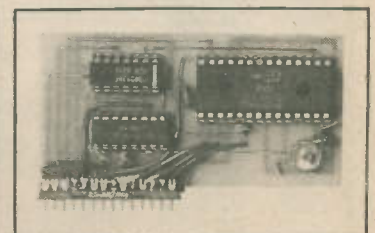

OUR APRIL ISSUE WILL BE ON SALE FRIDAY, MARCH 1st, 1985 (see page 35)

© IPC Magazines Limited 1985. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.







Mail order & shops:

441 PRINCES ROAD, DARTFORD, KENT DA1 1RB  
Telephone: (0322) 91454

ORDERING INFORMATION: P/P 50p on orders less than £20 in value otherwise post free. All components full spec & guaranteed. Discounts available on orders over £50 — phone for details. For unlisted components phone for price. Goods normally despatched by return post.

**NEW CATALOGUE NOW AVAILABLE  
CONTAINING THOUSANDS OF LINES  
MANY ILLUSTRATED**

This incredible volume contains everything required by the home constructor, amateur radio and CB user and computer enthusiast.

We think the semiconductor section contains more types than have ever been offered to the hobbyist.

Sections are headed as follows:

**Aerials, Amplifiers, Audio Accessories, Batteries, Boxes, Bulbs, Capacitors, Crystals, Car Components, Car Audio, CB & Ham Equipment, Computer Connectors, Fuseware, Hardware, Headphones, Knobs, Lamps, Leads, Loudspeakers, Microphones, Meters, OPTO, PCB, Resistors, Semiconductors, Special Effect Equipment, Switches, Power Supplies, Test Equipment, Tools, Transformers, Wound Components.**

In addition to listed items we continue to provide a procurement service for obsolete and difficult to obtain types.

*How many suppliers do you have at the moment that offer a service like this?*

Please fill in coupon below and send with £1.25. Print clearly as coupon is used as address label.

Catalogue contains £2.50 discount order form — You make a profit straight away.

NAME .....

ADDRESS .....

.....


.....

POSTCODE .....

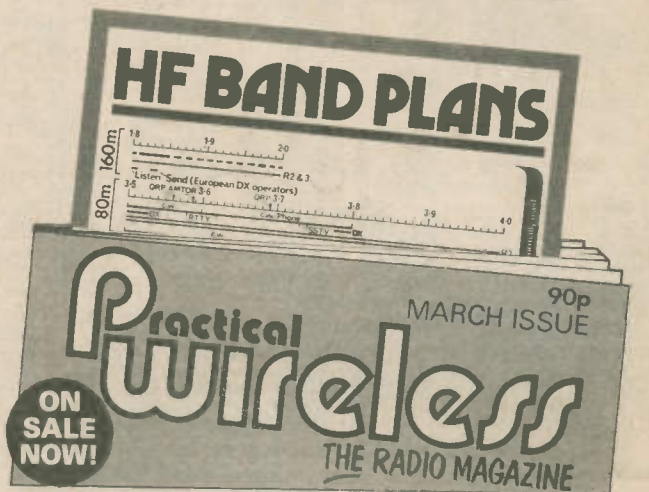**FREE DATA CARD!**


Shows where to find voice, morse, teleprinter and slow-scan television in the HF amateur bands.

**PLUS NEW SERIES  
AMATEUR TELEVISION**  
A practical approach to transmission and reception on the 23/24 cm. band.



**Master  
Electronics - Microprocessors  
- Now! The Practical Way!**

- Electronics — Microprocessors — Computer Technology is the career and hobby of the future. We can train you at home in a simple, practical and interesting way.
- Recognise and handle all current electronic components and 'chips'.
- Carry out full programme of experimental work on electronic computer circuits including modern digital technology.
- Build an oscilloscope and master circuit diagram.
- Testing and servicing radio — T.V. — hi-fi and all types of electronic/computer/industrial equipment.

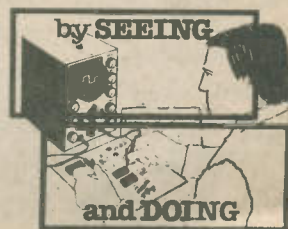

**New Job? New Career? New Hobby?**  
SEND THIS COUPON NOW.

**FREE! COLOUR BROCHURE**  
Please send your brochure without any obligation to

OR TELEPHONE US 062 687 2598  
OR TELEX 22758 (24 HR SERVICE)

NAME ..... I am interested in

ADDRESS .....

.....

.....

Other Subjects .....

**CACC**

**British National Radio & Electronics School P.O. Box 7, Teignmouth, Devon, TQ14 0HS**



## ELECTRONIC SIREN KIT

Produces an extremely loud piercing swept frequency tone from a 9-15V supply. Enable input for easy connection to alarm circuits. Includes 5in. Horn Speaker



£7.90

### Mini Siren

As above, but with a small speaker (instead of horn speaker) for internal use. Complete with box

£4.30

## SECURITY PRODUCTS

Protect your home and property and save by building your own burglar alarm system.



- Steir Mat 23 x 7 in (950 120) £1.70
- Floor Mat 29 x 16 in (950 125) £2.60
- Tamper-proof connecting block (950 110) £0.30
- Door/Window Contacts. Flush mounting, 4 wire, Magnet/switch Per Pair (950 140) £1.05
- Window Tape 0.5" wide 50cm (950 145) £2.50
- Window Tape Terminations Per pair (950 150) £0.36
- Key-operated Switch, 1.5A/250V SPST Heavy chrome metal (350 128) £4.50
- Passive Infra-Red Detector Detects intruder's body heat. Range 10 metres 12V DC, n/o & n/c contact. (950 135) £40.00
- Alarm Control Unit, 4 input circuits, 2-instant and 2-delayed. Adjustable entry, exit and alarm times. Built and tested. Full instructions supplied. Size: 180 x 130 x 30mm. Supply: 12V DC (950 160) £26.00
- Ultrasonic Burglar Alarm. Self-contained mains or battery powered unit complete with horn and AC adaptor. Inputs for pressure mats and other sensors together with exit/entry delays enable this unit to be used as a complete system. £45.00 + p&p £2.20
- 8W Horn Speaker, 5.5 ins. 8 ohm. Ideal for sirens, etc. 2.5m lead and 3.5mm jack plug. (403 148) £6.16

## IR GARAGE DOOR CONTROLLER KIT

For controlling motorised garage doors and switching garage and drive lights on/off up to a range of 40 ft.



Lots of applications like controlling lights and TVs,

etc. in the home. Ideal for aged or disabled persons, this coded kit comprises of a mains powered infra-red receiver with a normally open relay output plus two latched transistor outputs, battery powered transmitter and opto-isolated solid state mains switch.

- XX103 £25.00
- XX105 Extra transmitters £10.50

## PANTEC KITS


- PN2 FM Micro Transmitter £7.50
- PN3 Stabilised Power Supply £13.70
- PN5 2 x 10w Stereo Amplifier £14.50
- PN6 2 x 40w Stereo Amplifier £24.95
- PN7 Pushbutton Stereo Preamp £12.80
- PN8 Tone & Volume Control £13.60
- PN11 3w FM Transmitter £11.95
- PN13 Single Channel FM Transmitter £9.80
- PN14 Receiver for above £15.50

## TOP QUALITY . . . TOP SERVICE BOTTOM PRICES!

For FREE CATALOGUE send 9" x 6" SAE — contains full list of stock range all at very competitive prices. Cash with order (except account customers). Access or Barclaycard telephone orders welcome. Add 75p p&p + 15% VAT to all UK orders. Overseas customers add £2.75 p&p Europe, £6.50 elsewhere. Giro No. 529314002. Goods by return subject to availability. Shop open 9am—5pm (Mon-Fri). 10am—4pm (Sat). ALL PRICES EXCLUDE VAT



## INFRA-RED REMOTE CONTROL KITS

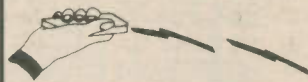

These kits are designed to enable infra-red remote control to be incorporated into virtually any application from switching car locks or alarms to controlling Hi-Fi or TV. The application will determine the interface circuitry between the receiver and the controlled device. General instructions and applications are supplied. The kits are coded and provide a high degree of security and noise immunity.

**MK 18 Transmitter Kit** — for use with MK11/MK12 receivers. Requires PP3 battery. Size: 8 x 2 x 13cms. Range approx 60ft. £6.80

**Keyboards for MK 18**  
 MK9 4-way for use with MK12 £1.90  
 MK10 16-way for use with MK12 £5.40  
 MK13 11-way for use with MK11 £4.35

**MK11 Receiver Kit** — mains powered. Provides 10 latched plus 3 analogue outputs ideal for controlling audio amplifiers, TV or lighting where control of light brightness is required. £13.50

**MK14 AC Power Controller Kit** — for (phase) controlling AC loads from MK11 analogue outputs, eg lamp dimming £5.20

**MK19 Stereo Amplifier Controller Kit** — for remote control of bass, treble and volume (or balance) by MK11. Includes a one of 10 decoder remote channel or input selection. May be connected between the pre-amp and power amp of almost any audio system. £10.70

**MK12 Receiver Kit** — mains powered with 16 latched or momentary outputs. Latched version is for applications requiring one output on at a time, eg TV channel selection. Momentary type gives an output only during transmission. Lines may be latched as required. Size: 9 x 4 x 2cms £13.50

**MK15 Dual Latched Solid State Relay** — for switching mains loads such as lamps, TVs, etc. from the outputs of the MK12 (momentary). 15 items may be switched independently using 8 MK15s. Triacs (not supplied) switch at mains zero to reduce interference. £4.50

## COMPONENT PACKS

- PACK 1 650 Resistors 47R 10M 10 per value £4.00
- PACK 2 40 x 16V Electrolytics 10 1000µF 5 per value £3.25
- PACK 3 60 x Polyester Capacitors 0.01 1µF 250V 5 values £5.55
- PACK 4 45 Presets 100R 1M £3.00
- PACK 5 30 x Low Profile IC Sockets 8, 14 & 16 pin £2.40
- PACK 6 25 Red LEDs (5mm) £1.75



## LCD DIGITAL MULTIMETERS

**LOW COST!** 10M ohm, 3½ digit 0.4 in display. Auto zero and polarity, low batt. indication, overload protection. Includes test leads, battery, spare fuse, manual, carrying case.  
 AC Volts: 0-200-500.  
 DC Volts: 0-2.20-200-1000.  
 DC Current: 0-20m-200mA.  
 Resistance: 0-2k-20k-200k-2M. Size: 138 x 86 x 36mm. (405 202) £25.95

**Professional** — 10M, 0.5 in, 3½ digit. Overrange and low battery indication. Overload protection. Includes leads, spare fuse, battery, manual and case. Transistor Checker. Size: 175 x 93 x 42mm.  
 AC Volts: 0-200-750.  
 DC Volts: 0-200m-2.20-200-1000.  
 DC Current: 0-20µ-2m-20m-200mA. 0-10A.  
 Ohms: 0-200-2k-20k-200k-2M. 0-20M. (405 204) £33.50

## BT STYLE PHONE CONNECTORS



**Line Jack Units**  
 Master Unit (first line unit) has bell capacitor and surge arrester

- Master (flush) (960 110) £3.00
- Master (surface) (960 112) £3.00
- Master (mini surface) (960 113) £3.50
- Secondary (flush) (960 114) £2.65
- Secondary (surface) (960 116) £2.65
- Secondary (mini surf) (960 117) £3.00
- Dual outlet adaptor (960 118) £4.20
- 4-way line cord with plug to spade terminals (960 120) £2.00
- 4-way line cord (960 130) £0.20 per m



**Auto Ranging, 3½ digit 10mm display.** Continuity buzzer, low battery, overload and range indication. 10A internal shunt for AC/DC current measurement. Carrying case supplied.  
 AC Volts: 0-2.20-200-500.  
 DC Volts: 0-0.2-2.20-200-1000.  
 AC Current: 0-200mA-0-10A.  
 DC Current: 0-200mA/0-10A.  
 Resistance: 0-200-2k-20k-200k-0-2M. Size: 160 x 85 x 29mm. (405 206) £44.85

**High Sensitivity, Temperature Probe.** For use with a multimeter to measure temperatures from -50°C to +250°C. Accuracy: 1.5°C@25°C, 2°C@100°C. Response time (in water), 5 seconds. Includes case, calibrated scale and instructions. (405 220) £8.50

## MICROPROCESSOR TIMER KIT

Designed to control 4 outputs independently switching on and off at preset times over a 7-day cycle. LED display of time and day, easily programmed via 20-way keyboard. Ideal for central heating control (including different switching times for weekends). Battery back-up circuit. Includes box, 18 time settings.



- CT6000K £39.00
- XX114. Relay Kit for CT6000 includes PCB, connectors and one relay. Will accept up to 4 relays 3A/240V c/o contacts £3.90
- 701 115 Additional Relays £1.65

## ELECTRONIC LOCK KIT

With hundreds of uses indoors, garages, car anti-theft devices, electronic equipment, etc. Only the correct easily changed four-digit code will open it! Requires a 5-15V DC supply. Output 750mA. Fits into standard electrical wall box.  
 Complete kit (except front panel) £11.50

**XX101 Electric Lock Mechanism** for use with existing door locks and the above kit. (Requires relay.) 12V AC/DC coil. (701 150) £14.95

## HOME LIGHTING KITS

These kits are designed to replace a standard wall switch to control up to 300w of lighting.



- TDR300K Remote Controlled Light Dimmer £14.95
- MK6 Transmitter for above £4.50
- TD300K Tough Dimmer £7.75
- TS300K Touch Switch £7.75
- TDE/K 2 way extension for above kits £2.50
- LD300K Rotary controlled Light Dimmer £3.95

## DISCO LIGHTING KITS

**DL1000K** — This value-for-money 4-way chaser features bi-directional sequence and dimming. 1kW per channel. £15.95

**DL21000K** — A lower cost uni-directional version of the above. Zero switching to reduce interference. £8.95

Optional opto input allowing audio 'beat' / light response (DLA/1) 70p

**DL3000K** — 3-channel sound to light kit features zero voltage switching, automatic level control and built-in microphone. 1kW per channel. £12.95

## DVM/ULTRA SENSITIVE THERMOMETER KIT

Based on the ICL 7126 and a 3½ digit liquid crystal display, this kit will form the basis of a digital multimeter (only a few additional resistors and switches are required — details supplied), or a sensitive digital thermometer (50°C to +150°C) reading 0.1°C. The kit has a sensitivity of 200mV for a full-scale leading automatic polarity and overload indication. Typical battery life of 2 years (PP3). £15.50

# ELECTRONICS

11-13 Boston Road  
 London W7 3SJ

ORDERS 01-567 8910  
 ENQUIRIES 01-579 9794

01-579 2842 TECHNICAL AFTER 3pm





## CHIPS FOR EVERYONE

IN JUST a few short months the chip suppliers have seen the market change from one where demand outstripped supply to one where they are laying off staff and shelving immediate development plans because there are now chips for everyone. While this is good for present users since it has resulted in the reduction of chip prices (although with the present pound to dollar ratio, these reductions are unlikely to show in the UK as most components are priced in dollars for sale around the world) the situation is worrying for the progressive future of high technology in general.

Over recent months up to 3,000 workers have been laid off by chip manufacturers in America and development planned for semiconductor plant in Scotland has been shelved. These cut backs are a direct result of the supply and demand situation; fortunately many of the manufacturers are indicating that their long term development plans are not being significantly changed. For instance NEC (a Japanese company) is planning to expand its Scottish factory and Hughes Microelectronics are also planning investment in Scottish plant.


The industry in general invests massive amounts of money in the development of new production methods, larger wafers, new base materials, bigger chips and improved plant. Without the continuing profitable massive sale of chips that investment

in future product cannot continue. The semiconductor industry is in the doldrums and the fifth generation is possibly staying out of reach because of it.
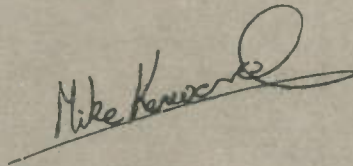
## FUTURE

We do of course still have Sir Clive who is promising wafer scale chips from his research centre; perhaps he will sell even more computers if chip prices fall this year. Interestingly Sir Clive may make more profit because of the supply/demand situation and it may be that he invests that profit in the future of the industry, rather than the chips makers. Of course he will need a manufacturer to build the chips since it is highly unlikely that Sinclair will buy or build the necessary factory. Provided *someone* in the business is prepared to invest development should continue. That ability to invest may also be tied up with the future sales of the C5 vehicle!

Wafer scale chips will probably play a very important role in our future which seems to be tied up with fifth generation and the massive industrial advantage it could bring. One company has already shelved wafer scale development because of the massive costs involved.



Editor Mike Kenward

Secretary Pauline Mitchell

Editorial Tel: Poole (0202) 671191

Advertisement Manager  
David Tilleard 01-261 6676

Secretary  
Christine Pocknell 01-261 6676

Classified Supervisor  
Barbara Blake 01-261 5897

Ad. Make-up/Copy  
Brian Lamb 01-261 6601

Queries and letters concerning advertisements to:  
Practical Electronics Advertisements,  
King's Reach Tower,  
Stamford Street, London SE1 9LS  
Telex: 915748 MAGDIV-G

## Letters and Queries

We are unable to offer any advice on the use or purchase of commercial equipment or the incorporation or modification of designs published in PE. All letters requiring a reply should be accompanied by a stamped addressed envelope, or addressed envelope and international reply coupons, and each letter should relate to **one published project only**.

Components are usually available from advertisers; where we anticipate difficulties a source will be suggested.


## Old Projects

We advise readers to check that all parts are still available before commencing any project in a back-dated issue, as we cannot guarantee the indefinite availability of components used.

## Technical and editorial queries and letters to:

Practical Electronics Editorial,  
Westover House,  
West Quay Road, Poole,  
Dorset BH15 1JG

## BACK NUMBERS and BINDERS...

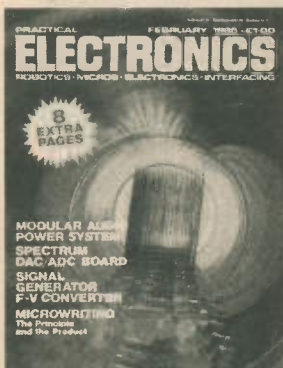

Copies of most of our recent issues are available from: Post Sales Department (Practical Electronics), IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at £1 each including Inland/Overseas p&p. Please state month and year of issue required.

Binders for PE are available from the same address as back numbers at £5.50 each to UK or overseas addresses, including postage, packing and VAT.



## SUBSCRIPTIONS

Copies of Practical Electronics are available by post, inland for £13, overseas for £14 per 12 issues, from: Practical Electronics, Subscription Department, IPC Magazines Ltd., Room 2816, King's Reach Tower, Stamford Street, London SE1 9LS. Cheques, postal orders and international money orders should be made payable to IPC Magazines Limited. Payment for subscriptions can also be made using a credit card.

Phone:  
Editorial Poole (0202) 671191

We regret that lengthy technical enquiries cannot be answered over the telephone.

Items mentioned are available through normal retail outlets, unless otherwise specified. Prices correct at time of going to press.

## Let Battle Commence

The arrival of cellular radio in the UK this year could be said to be the thin end of a wedge that will soon provide pioneering business people, commercial enterprises and the 'well off' with a carphone or portable handset. The thick end of that wedge will eventually put us all within reach of such communicative luxury—when prices fall or market saturation convinces us all that we cannot live without one!

Last year the Government granted 25 year licences to the two operating networks—British Telecom/Securicor with their Cellnet system and Racal with their Vodaphone system. The licences stipulate that each operator must have sufficient transmitter coverage to accommodate 90 per cent of the UK population by the end of the decade.

In marketing their respective wares the two organisations have appointed many well established retail outlets, who will sell, lease, install and connect the hardware. The AA for instance are one of Vodaphone's distributors who with their membership of 5.6 million motorists have a ready made clique of potential carphone customers. Another interesting appointment is that of Granada by Cellnet. They will deal through their massive chain of High Street shops which lengthened last year when they bought out Rediffusion. Prospective roving orators will be able to get hands-on experience at these outlets.

The cost of the various options will vary, those quoted here therefore should be treated as indicative; they pertain to the Cellnet price structure.

A Class 1 carphone will cost around



£1500 if bought outright, this includes installation and connection. To lease such a unit would cost around £60 per month, this includes a £25 per month subscription charge.

A portable unit will cost around £3000, to lease such a unit will be around £80 per month including the subscription charge.

Call charges will be 25 pence per minute during peak periods and 15 pence per minute at other times.

The principle of cellular radio lies in the constant re-use of radio frequencies by utilising small adjacent cells each containing its own transmitter. This principle represents a revolution in mobile communications. Cells vary in size from one to two kilometres across in urban areas to far larger cells in rural areas where demand is lower. As a user travels from one cell to the next his call is automatically transferred to the new cell's frequency without any interruption. The original cell, as a result, becomes free for the use of other subscribers. All of this allows the network to support a far greater number of simultaneous calls than any current system.

For further reading see 'Cellular Radio' *Practical Electronics*, Jan '85; and 'Leading Edge' in this issue.

## NEW SHOP FOR SKYBRIDGE

*Skybridge Ltd., have announced the opening of their new shop in Dartford, Kent.*


*Their product range includes the usual discreet components, which are stocked in depth, with the general product range being divided into categories. They include Audio and Electronics; Home radio; Computer; RC; Servicing; test equipment, etc. In many cases several options of the same product are available enabling cost conscious buyers to stick to a budget.*

*Customers at the shop can consult a technical library covering subjects from component data to constructional information; helpful advice is also on hand. A catalogue is presently being compiled so that a mail order service can be introduced. Skybridge Ltd. can be found at 441 Princes Road, Dartford, Kent (0322) 91454.*
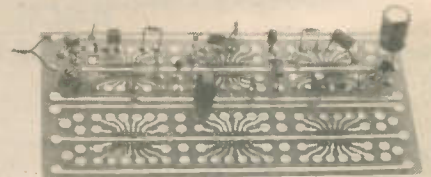
## DESIGN PCB

There are many avenues open to the constructor who wishes to develop prototype circuits quickly and economically, stripboard and plug-in blocks being a couple of obvious examples. A quite new option has now been developed by UK based E & H Electronics.

Protocard is a pcb measuring 210 x 100mm which houses six, 16 pin d.i.l. sockets whose pins are routed to large area solder pads. These extra large pads allow components to be tacked easily onto their surface for quick assembly of prototype circuits. There are also eight transistor pads on the board. Each i.c. is marked with a pin location, and supply tracks, signal tracks, etc., run the full length of the board.



Once the circuit has been proven the board can be stripped and used again. Admittedly, a rather self-indulgent aid for the true amateur, but nevertheless a very handy item.

Protocard costs £8.50 inc. VAT and p & p; it is supplied with 10 circuit planning cards and a small quantity of equipment, wire and solder. From E & H Electronics, 33 North Street, Keighley, West Yorkshire BD20 3SL (0535 44103).

# MARKET PLACE


## SPACE FLIGHT SIMULATOR

The Mitsubishi Electric Corporation, jointly with Korakuen Stadium Co., recently started marketing the "Flying Cabin", an amusement machine that moves in synchronisation with the image on a screen inside the cabin.

A six-axis hydraulic system used for a flight simulator is employed in the Flying Cabin for computer-controlled synchronisation of the moves of the 44-man cabin with the screen's crisp images and six-channel sound.


The Flying Cabin simulates space travel: the cabin sways, careens and dives in line with changing realistic scenes of ground surfaces and deep space, projected on a huge screen.

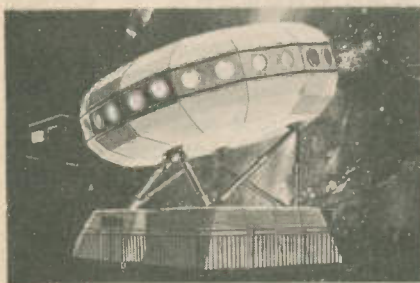The two companies hope to sell 20 systems in Japan and 40 abroad in the coming five years, chiefly to amusement parks and science museums etc. The Flying Cabin will cost over £1 million.


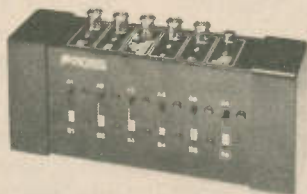
## TV Switch

For use in the fast growing number of homes where the family TV set is now the heart of an increasingly complex array of electronic entertainment equipment, Ross Electronics have introduced their RF-170 television control centre.



Measuring 205 x 90 x 65mm, the centre provides instant selection of TV, video recorder, home computer, video game, Cable TV or additional VTR dubbing and monitoring facilities. It has inputs (1 phono, 5 co-axial sockets) which may be freely interconnected through a bank of six low-loss slide switches.

Supplied with a switching chart, the RF-170 retails at circa £31.95. Further details from Ross Electronics, 49/53 Pancras Road, London NW1 2QB. (01-278 6371)

## Briefly...

The British Amateur Electronics Club (BAEC) is an amateur electronics club based in the UK, helping all who are interested in electronics. The key to the

club's success lies in their quarterly Newsletter which contains many pages of circuits, advice, letters, news and exchanges etc. The club was formed in 1966 and now has many members from beginners to experts.

Membership for UK and Eire members is £7.00, overseas £8.50 (£12.50 air-mail). Please enclose remittance in sterling with a s.a.e. to: C. Bogod Esq., "Dickens", 26 Forrest Road, Penarth, S. Glam. CF6 2DP.

In 1983 Britain's exports to the USA were around £8½ billion and it is expected the final 1984 figure will be around £11½ billion. Furthermore City brokers estimate, at present pound/dollar levels, an additional £4 billion worth of business could be won this year. This would mean that the UK visible exports to the USA could be said to have tripled in five years. High quality manufactured goods such as Jaguar cars and Wedgwood china have spearheaded this trend.

A progressive application of l.c.d. technology has been adopted by Nissan for their new car, the Laurel. Its rear view mirror has an automatic feature that protects the driver from headlamp reflections. The front of the mirror is covered by an l.c.d. which is normally transparent. A photosensor in the casing detects the excessive light and activates the l.c.d. which darkens; thus reducing the dazzle.

According to *Computing, the Newspaper*, Acorn Computers is withdrawing from the education market in the USA. Their hopes of capturing 10 per cent of the market were dashed following approval delays from the Federal Communications Commission. A further spanner in their works was the BBC micro's lack of success against Apple.

## Countdown ...

Please check dates before setting out, as we cannot guarantee the accuracy of the information presented below. Note: some exhibitions may be trade only. If you are organising any electrical/electronics, radio or scientific event, big or small, we shall be glad to include it here. Address details to Mike Abbott.

Component Fair March 10. Carleton Community Cntr., Pontefract (on A1 to Darrington). F2  
London Medical March 12-15. Earls Court. S2  
IFSSEC (fire/security) April 15-19. Earls Court, London. S  
Cast (Cable & Satellite) April 16-18. NEC, Birmingham F5  
Communications April 23-25. Olympia. I  
Photoworld April 23-May 6. Earls Court. I  
CAD April 26-28. Metropole, Brighton. K2  
Fibre Optics & Lasers April 30-May 2. Olympia. E  
Custom Electronics & Design Techniques April 30-May 2. E  
All Electronics Show/ECIF April 30-May 2. Olympia 2. E  
Circuit Technology March 26-28. E

Field Service & Repairs April 30-May 2. Olympia 2. E  
Automan (manufacturing) May. NEC. T1  
IBM Computer User May 14-16. NEC B/ham. O  
Business Telecom May 21-23. Barbican, London. O  
Scotex 4 June 4-6. Royal Highland Soc., ex. Hall, Ingleston, Edinburgh. A1  
Networks June 25-27. Wembley Conf. Cntr. O  
Cable July 9-11. Metropole, Brighton. O  
Personal Computer World Show Sept. 18-22. Olympia 2. M

A1 Institute Electronics ☎ 0706 43661  
E Evan Steadman ☎ 0799 26699  
F2 Pontefract Am. Rad. Soc. N. Whittingham ☎ 0977 792784  
F5 ☎ 01-487 4397  
I ITF ☎ 021-705 6707  
K2 Reed Exhibitions, Surrey Ho., 1 Throwley Way, Sutton, Surrey  
M Montbuild ☎ 01-486 1951  
O Online ☎ 01-868 4466  
S ☎ 01-387 5050  
S2 Fairs & Exhibitions Ltd., ☎ 01-831 8981  
T1 Cahners ☎ 0483 38085



# Heart Beat Monitor

P. Leah

THERE are a wide variety of methods to measure beats of the heart from feeling the pulse in one's wrist to monitoring the differences in electrical potential through the body using an electrocardiograph. Such methods have their advantages and disadvantages. The primary disadvantage of all these methods is that they involve direct contact to the body and consequently impose a safety hazard if any mains operated electrical equipment is associated with the heart beat measurement. In this particular design of a heart beat monitor, light from a 12V bulb is shone through the finger onto a photodiode.

As there are no electrical contacts to the body, this method of pulse detection is inherently very safe. Each time the heart beats, a surge of blood is sent through the body which increases the density of the small fleshy parts of the body, particularly the fingers. Consequently the light passing through a finger will vary at each heart beat, and this variation is detected by the photodiode. The output from the photodiode is amplified in a detector circuit to provide a CMOS compatible pulse each time the heart beats.

In this particular design, the photodiode and 12V bulb are mounted on opposite sides of a 1 inch diameter plastic tube which is secured in an instrument case. For measurements to be taken, the finger is inserted into the plastic tube until it covers the photodiode and is held steady.

As a digital readout is preferred to an analogue one, the time between successive pulses from the detector is accurately measured and digitally converted into beats per minute which are subsequently displayed on a 3 digit I.e.d. display. The display is latched for approximately 3 seconds before being updated by the next measurement.

## GENERAL PRINCIPLE

A conventional frequency measurement technique of merely counting the pulses from the detector over a known time period cannot be used when measuring the relatively slow time periods associated with heart beats. Even a fast heart rate such as 150 beats per minute would take at least 8 seconds to obtain an accurate reading. A low heart rate of around 60 beats per minute would take around 20 seconds to obtain an accurate reading. Consequently a novel, but simple measurement and conversion technique has had to be used which avoids the need for sophisticated devices such as microprocessors.

The block diagram of the unit is shown in Fig. 1. The output from the detector circuit to the main unit initially measures the time interval between three successive output pulses from the detector. Assuming that the detector is monitoring heart beats at 60 beats per minute, the time interval between three successive pulses is 2 seconds.

Counter A is enabled for this period and is subsequently clocked from an 83.3Hz clock train. Hence, 166 will be counted and stored in the Counter A. The output from this counter is used to preset counter B to 166. Exactly 10,000 pulses are then passed into the presettable counter B. The output pulses from this counter of  $10,000/166 = 60$  are then counted and stored in the display counter before being displayed on the I.e.d. display. The 83.3Hz clock pulse and 10,000 pulse train generator are derived from an accurate 100kHz oscillator.

## DETECTOR CIRCUIT DESCRIPTION

The detector circuit, shown in Fig. 2, comprises four operational amplifiers connected in series. A dual op amp (CA3240) IC1 was chosen for the initial amplification because of its relatively low noise and high impedance FET input. IC1a is connected as a simple amplifier which amplifies the variations in reverse leakage current through photodiode D3. The greater the intensity of light shining on the diode, the greater will be the reverse current through the diode. Resistor R17 provides additional bias current in order to ensure the output voltage of IC1a remains within the active region of the amplifier, even under extreme conditions of illumination. Resistor R13 is the feedback resistor for IC1a. Under direct illumination from the 12V bulb, the output of IC1a at pin 1 will be at almost 0V and will change to about 5.5V when placing a finger in front of D3. This output voltage is connected via resistors R19, R18 and C9 to the second operational amplifier IC14b.

This amplifier is connected as a second order, low pass filter with a cut off frequency of 15Hz, so that any mains frequency interference of 50Hz or 100Hz is attenuated. The output from this filter is coupled via C10 to another amplifier IC14a, which is connected as a straightforward, non-inverting, amplifier with a gain of approximately 50. The output from this amplifier is connected to IC1b via resistors R24 and R25. This amplifier is connected with positive feedback by connecting R26 between the amplifier output at pin 7 of IC1 and its positive input at pin 5. This feedback ensures the amplifier output voltage switches almost between the supply rails  $V_{DD}$  and 0V. Also, it ensures that the amplifier will switch between states at very small differences in input voltage, and will remain in the state to which it has switched, similar to a Schmitt trigger. As R24 and R25 are identical the current flowing through these resistors into pins 5 and 6 of IC1b will be identical. However, an additional current will flow into pin 5 from the output pin 7 via R20. Hence, if the amplifier output is at  $V_{DD}$ , pin 5 will be positive with respect to pin 6. A sudden change in light intensity impinging on the photodiode D3 will cause a rapid drop in

voltage at pin 1, the output of IC1a. This fall in voltage will also appear at pin 5 of IC1b but due to the capacitor C12, pin 6 will be slower to respond to the voltage change. Consequently pin 5 will go negative to pin 6 and the amplifier output will switch states to 0V. Due to the positive feedback described earlier, the output of IC1b will remain at 0V until a positive going voltage appears at the output of IC1a.

Before connection to the Main Unit, the output pulse from IC1b is connected via the CMOS monostable of IC13a and IC13b. The amplification circuit is very sensitive, and the monostable ensures double switching does not occur, as the output pulse from the monostable is approximately 80ms.

Resistors R15 and R16 provide a voltage divider chain which supplies  $V_{DD}/2$  for the bias voltage required for the operational amplifiers. C6 and C7 are supply decoupling capacitors.

## MAIN UNIT CIRCUIT DESCRIPTION

The conversion and display circuits on the Main Unit are shown in Fig. 4 with CMOS being used throughout. The out-

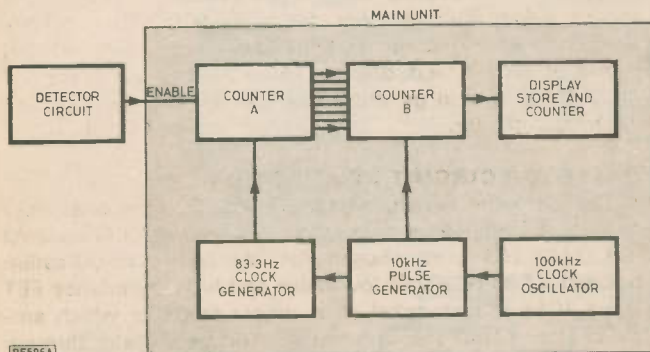


Fig. 1. Block diagram of the Monitor

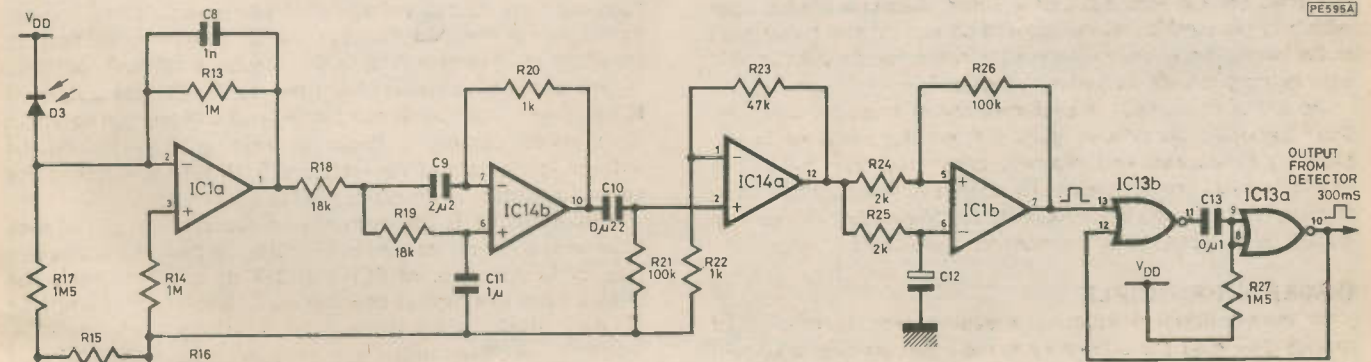


Fig. 2. Circuit diagram of the Detector circuit

IC1 = CA3240E  
IC13 = 14001  
IC14 =  $\mu$ 747

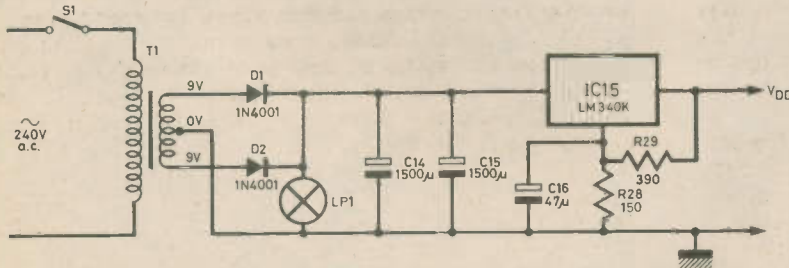


Fig. 3. Circuit diagram of the Power Supply Unit

put pulse from the detector is initially buffered by NOR gate IC2a, before clocking the binary counter IC6a. During the time interval between the 3rd and 5th pulse from the detector, pin 4 of IC6a will be in the high state.

The signal from pin 4 IC6a is used to enable counter IC7. After the fifth pulse from the detector, pin 5 of IC6a will be in the high state and inhibits further counting of IC6a.

IC7 is also a binary counter in which the two counters are cascaded together to form an 8-bit binary counter. IC7 counts and stores the number of pulses from an 83.3Hz pulse train that can be counted during the time the counter is enabled from IC6a. The 8-bit parallel output from IC7 is immediately preset into the presettable down counter IC8.

The 83.3Hz train is derived from a 100kHz oscillator comprising IC11a and IC11d. The oscillator can be varied by adjusting VR1 to compensate for component tolerances.

IC11c buffers the oscillator output before connection to IC3, a dual decade counter. These counters are connected in series to provide an output of 1kHz which is connected to IC4b. This counter divides the pulse train by six, using gates IC12c and IC12d. The 166.7Hz pulse train from IC4b pin 13 is connected to IC6b where it is divided by 2 to obtain the 83.3Hz clock, required at the clock input of IC7.

The 1kHz pulse train from IC3 is divided further by decade counter IC4a to produce 100Hz, and by decade counter IC5a to produce 10Hz at pin 6 of IC5. IC5 is only enabled after the 5th pulse from the detector has been received and counted by IC6, and IC7 has consequently counted and stored the 83.3Hz pulses as explained earlier. Initially all outputs from IC5 are at zero. When enabled, pin 5 will eventually change to high which clears the old preset number in IC8 and clears the display counter at IC9. Approximately 1 second later pin 11 of IC5 goes high which inhibits the 'clear' output of pin 5 via the NAND gate IC12b. The output from pin 11 of IC5 is a pulse train of 5Hz having an equal

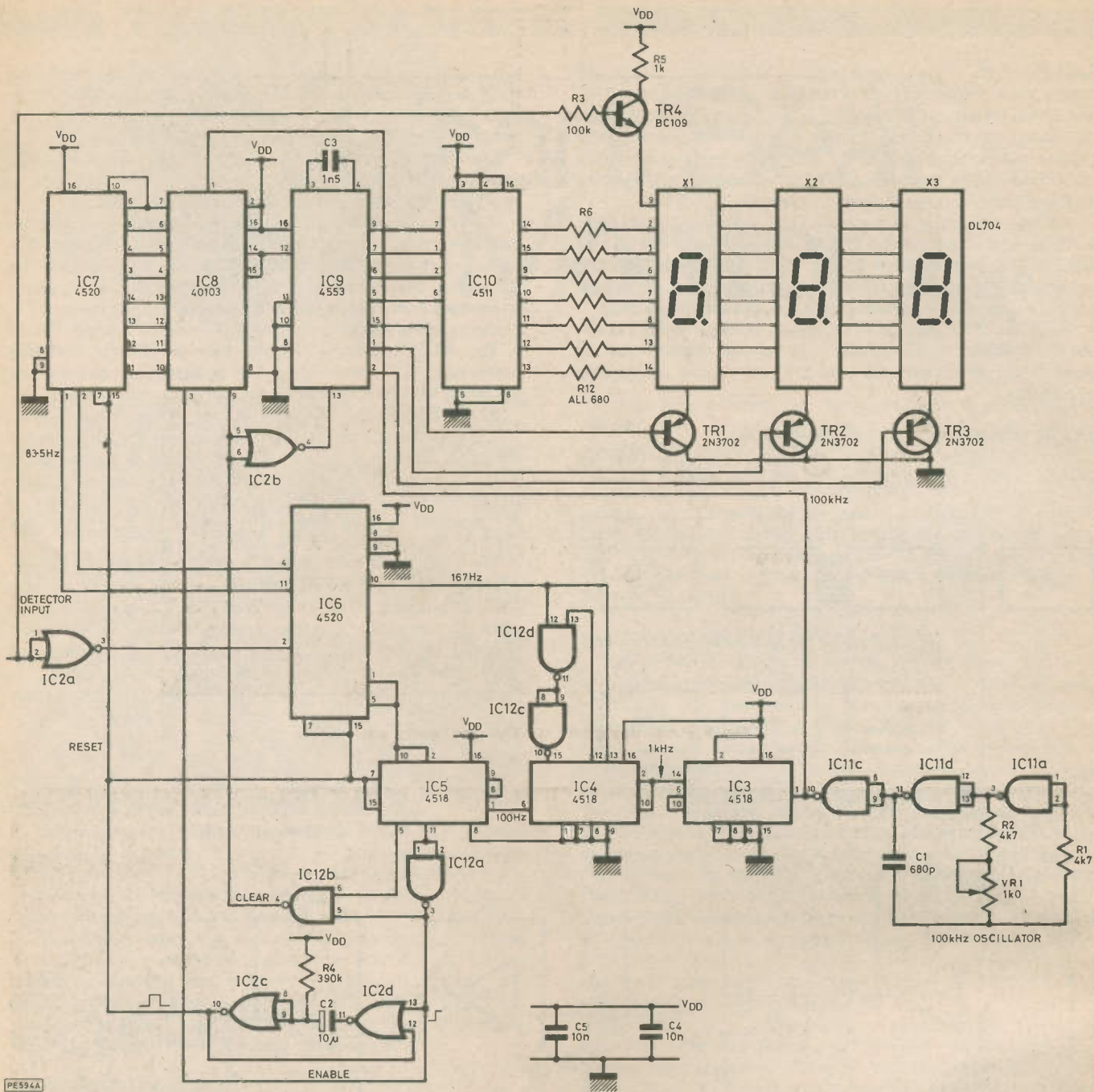


Fig. 4. Circuit diagram of the Main Unit

mark to space ratio. Hence, logic level 1 appears for exactly 100ms which is the exact time it would take 10,000 pulses to be counted from a 100kHz clock. This 100ms pulse enables IC8 while the 100kHz clock pulses from IC11c clock IC8. The resulting pulse train output from IC8 is clocked into IC9 to be counted and displayed. The falling edge of the 100ms enable pulse activates the reset monostable comprising IC2c and IC2d. The resulting reset pulse of approximately 3 seconds duration, resets counters IC5, IC6 and IC7, while inhibiting further counting during those 3 seconds. After the three second period has elapsed a further measurement may commence and the whole cycle will repeat.

IC9 is a three digit BCD counter which provides a mul-

tiplexed output, ideal for use with i.e.d. displays. The four BCD outputs are connected to IC10 a BCD-seven segment decoder driver which drives the i.e.d. displays X1, X2, X3 directly via current limiting resistors R6 to R12. The digit driver transistors TR1, TR2 and TR3 operate directly from the digit select outputs of IC9 to switch on the displays as appropriate.

The decimal point of all digits are commoned to provide an indication that a pulse is being received from the detector. If the decimal points are not illuminated it is an indication that no pulses are being received from the detector. Its usefulness will become evident when actually measuring heartbeats. Resistors R3 and R5 are the bias resistors for

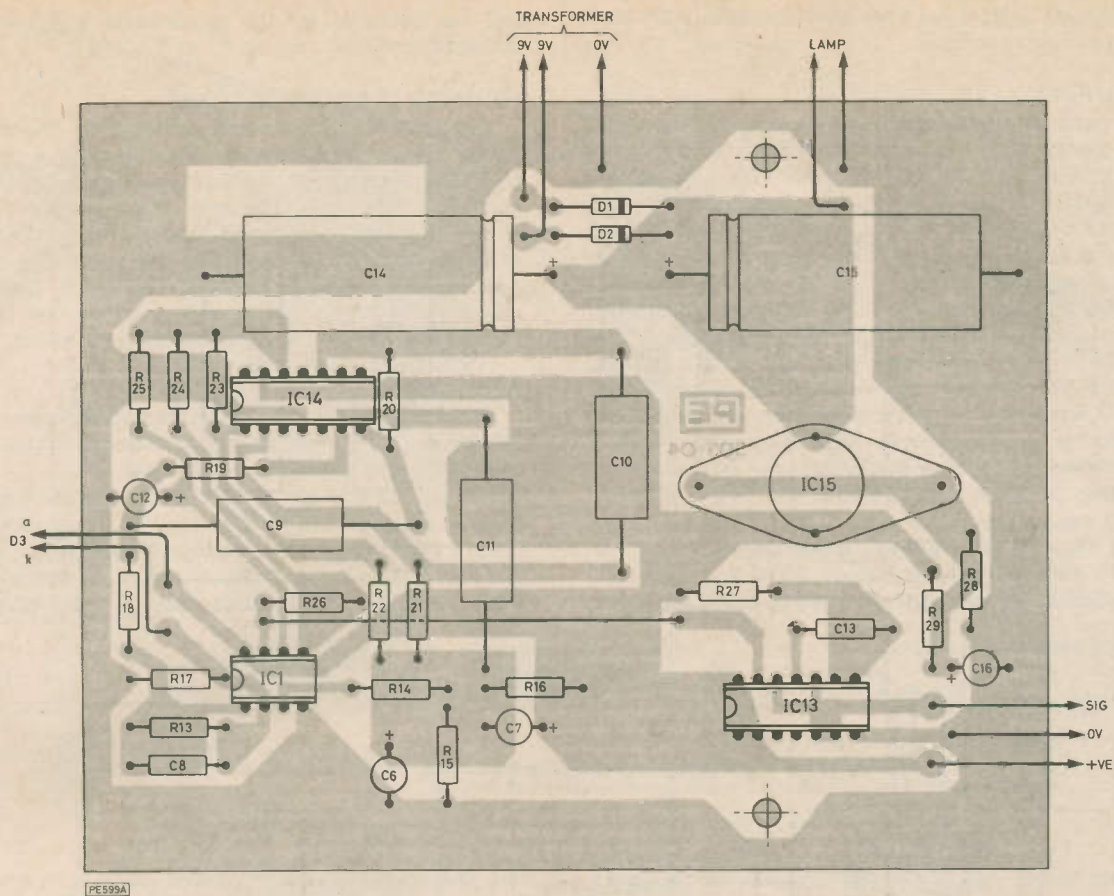


Fig. 5. P.c.b. design for the Detector and p.s.u.

## COMPONENTS . . .

### Resistors

R1,R2	4k7 (2 off)
R3,R21,R26	100k (3 off)
R4	390k
R5,R15,R16,	
R20,R22	1k (5 off)
R6-R12	680 (7 off)
R13,R14	1M (2 off)
R17,R27	1M5 (2 off)
R18,R19	18k (2 off)
R23	47k
R24,R25	2k (2 off)
R28	150
R29	390
All resistors $\frac{1}{2}$ W carbon	

### Capacitors

C1	680p polystyrene
C2	10 $\mu$ 16V tant
C3	1n5 ceramic
C4,C5	10n polyester (2 off)
C6,C7,C16	47 $\mu$ 16V tant (3 off)
C8	1n ceramic
C9	2 $\mu$ 2 polyester
C10	220n polyester
C11	1 $\mu$ polyester
C12	2 $\mu$ 2 16V tant
C13	100n polyester
C14,C15	1500 $\mu$ 25V elect (2 off)

### Semiconductors

D1,D2	1N4001 (2 off)
D3	IPL 33 photodiode
TR1,TR2,TR3	2N3702 (3 off)
TR4	BC109
IC1	CA3240E dual JFET op amp
IC2,IC13	4001 quad NOR gates (2 off)
IC3,IC4,IC5	4518 dual BCD counter (3 off)
IC6,IC7	4520 dual binary counter (2 off)
IC8	40103 256 presetable counter
IC9	4553 3 digit counter
IC10	4511 7 segment display driver
IC11,IC12	4011 quad NAND (2 off)
IC14	747 op amp
IC15	LM340K + 5V regulator
X1,X2,X3	I.e.d. 7 segment display (3 off)

### Miscellaneous

S1	s.p.d.t. miniature toggle switch
VR1	1k miniature hor. preset
T1	9-0-9V transformer 0.5A
Spartolight map light (Halfords)	
Single sided p.c.b. 100 x 120mm and 125 x 125mm	
0.1" stripboard 1" x 0.4"	
Instrument Case 220 x 174 x 100mm	
Red perspex filter 25 x 65mm	
Various 4BA and 6BA mounting nuts and bolts	
Interconnection wire 0.4mm and 0.6mm	
Co-ax cable (150mm length)	
Soldercon pins or d.i.l. holders	

TR4, the decimal point drive transistor. Capacitors C4 and C5 are decoupling capacitors.

### POWER SUPPLY

The unit requires a regulated power supply of 180mA at around 8V d.c. to drive the logic and detector circuits, and around 300mA at 12V d.c. for the lamp. The p.s.u. circuit diagram is shown in Fig. 3. Briefly this comprises an 18V centre tapped transformer which is full wave rectified by diodes D1 and D2 to provide a peak voltage of 12V. This is smoothed by reservoir capacitors C14 and C15 before connection to the 5V regulator chip IC15. Any variable or +5V regulator i.c. which provides at least 500mA will suffice. The resistors R28 and R29 effectively boost the output voltage to around 8V, yet maintain regulation. Good regulation of the supply is necessary to prevent noise on the supply rail being picked up by the detector, and to ensure that the 100kHz oscillator remains within tolerance. The power to the 12V lamp is taken directly from the two 15,000 $\mu$ F microfarad capacitors C14 and C15. Such a high capacitance value is essential to reduce the ripple on the supply to the lamp to less than 800mV. Excessive ripple will cause variations in light intensity emitted by the lamp which

will be detected by the photodiode and hence causes spurious readings.

### PRINTED CIRCUIT BOARDS

Two printed circuit boards are required. The detector and power supply circuits were laid out on one p.c.b. while the Main Unit, containing the counters and display circuits, was laid out on the other. The component layout of the detector circuit p.c.b. is shown in Fig. 5 while the component layout of the counter and display p.c.b. is shown in Fig. 6. Particular care should be taken in placing the CMOS devices on the counter and display p.c.b. as the orientation of the chips varies. This was necessary to aid the track layout.

### ASSEMBLY

The printed circuit board for the power supply and detector circuit is mounted directly on the base of the instrument case along with the mains transformer.

The positioning of the 1" diameter plastic tube, and the lamp to each other is critical however. It is essential that the lamp is held rigid in the instrument case as any movement, due to vibration etc., of the bulb will cause errors in the heart beat measurement. For this reason, a portable car map

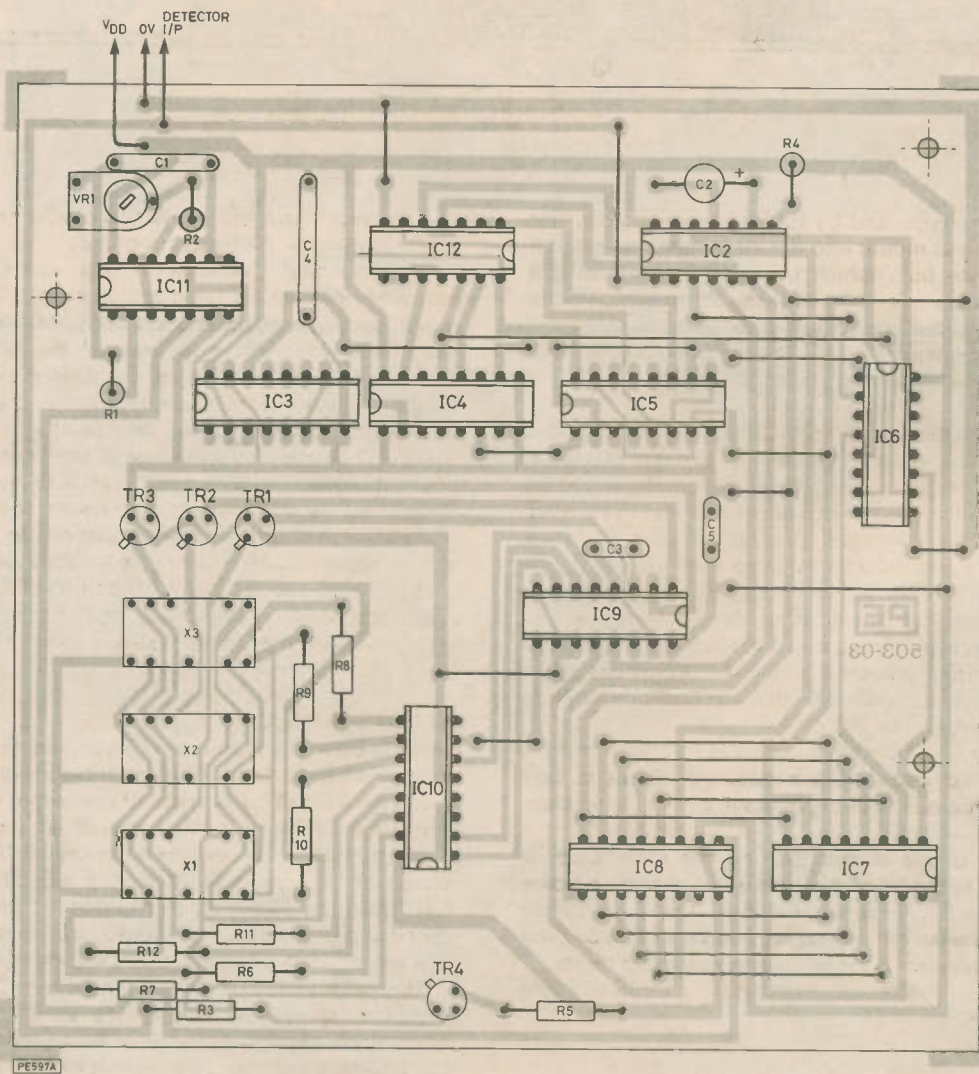


Fig. 6. P.c.b. design for the Main Unit



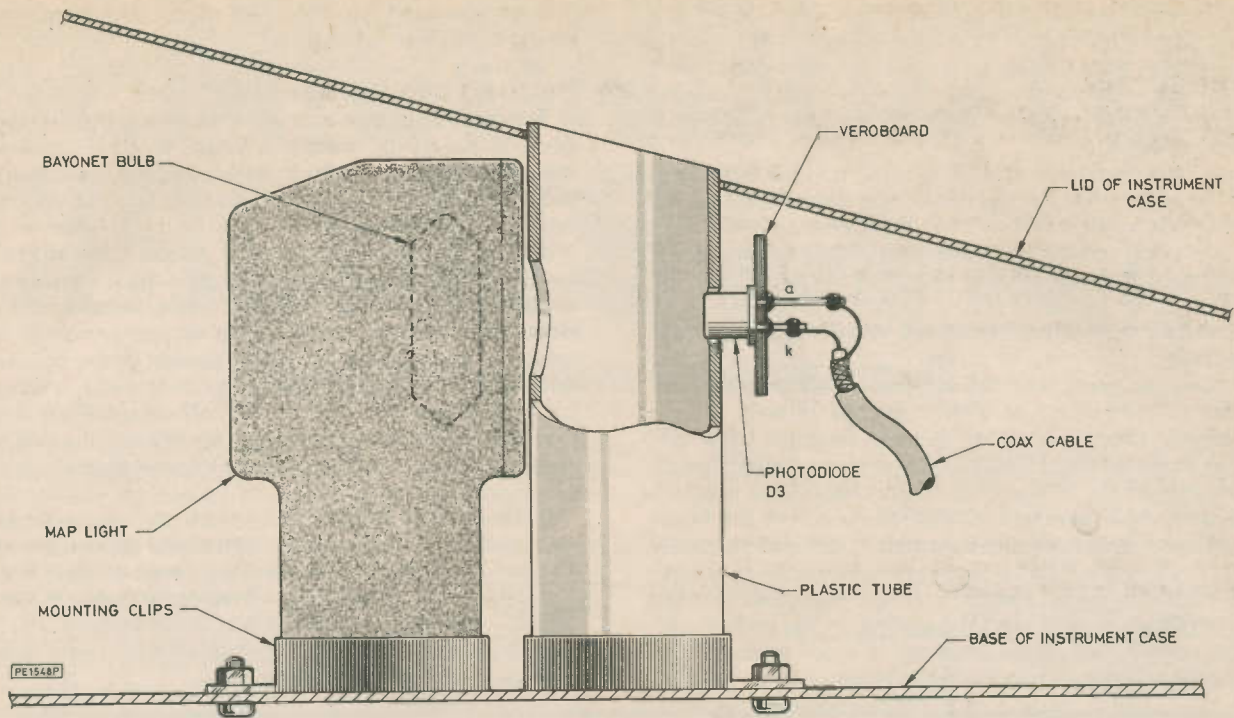


Fig. 7. Assembly diagram for the Monitor

reading lamp of the type sold by Halfords was chosen. Not only is it convenient to mount into the instrument case, but it has a bayonet style bulb which provides a superior light source. It is necessary to cut the bottom off the lamp holder in order to fit it into the instrument case, and to ensure the on-off switch is permanently 'on'. The lamp is secured by a 1" diameter vertical mounting capacitor clip, as shown in Fig. 7.

The plastic tube was cut so that it mounted directly onto the base of the case using a similar 1" diameter capacitor mounting clip as the lamp, and just protruded above the lid of the case. Hence the lid provides support against sideways movement of the plastic tube. The plastic tube must be mounted as close as possible to the lamp and immediately in front of it as shown in Fig. 7. Two holes should be drilled in the tube directly opposite each other. One hole of approximately 10mm diameter should be drilled in front of the lamp and the other of 4mm diameter should be drilled to mount the photodiode. It is essential that the photodiode is positioned exactly opposite the lamp.

The photodiode is mounted on a piece of Veroboard on which the screened cable to the detector circuit is terminated. The photodiode is then positioned in the 4mm hole in the plastic tube.

As the display circuit is mounted on the main p.c.b. it must be attached to the lid of the case using mounting holes drilled through the lid. A rectangular hole 13mm x 35mm must be cut into the lid for the display and should be backed by red perspex, araldited to the lid to emphasise the digits.

Further holes for the on-off switch and the mains cable must also be drilled.

#### TESTING AND SET UP

Testing and setting up the Monitor is greatly eased if an oscilloscope is available. Only the 100kHz oscillator needs to be accurately set up by adjusting VR1. This can simply

be achieved by monitoring IC11c pin 10 and adjusting VR1 until a reading of 100kHz is obtained.

An initial test should show that, when the unit is first switched on, only the lamp is illuminated. This indicates the power supply is operating correctly. Moving a solid object such as a screwdriver in front of the photodiode should cause the decimal points of the display to illuminate each time the screwdriver moves across the photodiode. This indicates the detector circuit is operating correctly. Rapidly moving the screwdriver in front of the photodiode five or six times should cause a number to appear on the l.e.d. display. This indicates the counter and display circuit is operating correctly. The display will not automatically reset to zero, but will be retained until replaced by a subsequent reading.

If this sequence of events is detected the Monitor will be operating correctly and heart rate readings may be taken, after reading the Practical Considerations section.

#### FAULT FINDING

If the unit fails to operate correctly check for the obvious things first such as the correct voltage on the power supply. Next check the voltage levels at the output of the operational amplifiers. Check that the output of IC1a pin 1 and the output at pin 10 IC14 is approximately 5.5V when no light shines on the photodiode, and is approximately 0V when light from the 12V bulb shines directly on the photodiode. When actually measuring heartbeats, no detectable change in waveform will be apparent, however, at these outputs.

The output of IC14 pin 12 should be a 3.5 d.c. level with any light intensity shining on the photodiode, on which a 200mV pk-pk waveform should be superimposed when measuring heartbeats. The output of IC1 pin 7 should show 0V to 6.5V transitions at each heart beat.

If the counter/display circuit is suspected as being faulty, again check the power supply voltage, and then the os-

LYNX 48K, INFO. R3Q FOR SCREEN/MEMORY DOOR...  
 DETAIL OF SCREEN/MEMORY DOOR...

cillator output, at IC11 pin 10. Check that there are waveforms of 100Hz and 167Hz at IC4 pin 6 and pin 13 respectively. If all is correct so far, the conversion or display circuit must be at fault. However, if the l.e.d.s are displaying something, even if it's all zeros it indicates the display circuit is operating correctly.

When fault finding on CMOS circuits, the low logic level should be at 0V while the high level logic state should be 8V. However, any voltage below 3.5V will appear as a low logic state while any voltage in excess of 4.5V will appear as the high voltage state to the input of a CMOS device.

**PRACTICAL CONSIDERATIONS WHEN USING THE MONITOR**

As explained previously, the detector circuit amplifies differences in light intensity which impinge directly on the photodiode. Consequently it is very sensitive. The differences in the levels of light being measured are very small, and any movement of the lamp, or the plastic tube in which the photodiode is mounted, or any movement of the finger itself will result in a false measurement. It is therefore essential that the finger is held perfectly stationary while measurements are being taken. Hence, it is recommended that the finger is placed directly onto the surface of the photodiode, without applying excessive pressure, in order to steady the finger while measurements are being taken.

The three decimal points on the l.e.d. display will illuminate each time a heart beat is detected. Hence it should be obvious when the instrument is correctly detecting heartbeats, and any double switching etc. will be indicated by several quick flashes of these decimal points. If this condition is prevalent, move the finger to a new position or alternatively, use a different finger. Note it may take a few seconds for the Monitor to 'settle down' before regular readings are obtained.

If the three decimal points appear continuously illuminated, the detector circuit is picking up noise, and the IC1b monostable is continually being activated. As the monostable has an output pulse of approximately 80ms, pulses at 80ms intervals will be passed to the counter circuit. As this equates to 750 pulses per minute, readings on the l.e.d. display of 714 or 769 will occur. Such noise is probably caused by airborne interference as detected by the photodiode if a mains operated tungsten filament is shone directly at the photodiode.

The heartbeat monitor is accurate to within 1 beat per minute over the range 40 to 200 beats per minute. Below 40 beats per minute, the readings become random. Above 200 beats per minute, the quantisation error involved in digitally converting a time period measurement into a frequency measurement, becomes significant. Hence, accuracy decreases with increasing frequency. ★

**FREE! READERS' ADVERTISEMENT SERVICE**

**PE BAZAAR**

**RULES** Maximum of 16 words plus address and/or phone no. Private advertisers only (trade or business ads. can be placed in our classified columns). Items related to electronics only. No computer software. PE cannot accept responsibility for the accuracy of ads. or for any transaction arising between readers as a result of a free ad. We reserve the right to refuse advertisements. Each ad. must be accompanied by a **cut-out valid** "date corner". Ads. will not appear (or be returned) if these rules are broken.

**LARGE** quantity new components for sale. Resistors, capacitors, semiconductors. Also lots of magazines, PE, EE, ETI. John Rinaldi, 36a Durham Road, London SW20. Tel: 01-879 3439 (days)  
**FOR** sale. Service manuals for Heathkit IM-230 voltmeter, GD-1U Griddip meter, HD-10 electronic keyer. £5 each. Mr. M. Small, 8 Cherry Tree Road, Chinnor, Oxon. OX9 4QY.  
**WASP** or other secondhand synth under £40 wanted. Mr. P. J. Andrews, 4 Watford Close, Cranley Road, Guildford, Surrey GU1 2EP. Tel: 0483 572705.  
**I AM** interested in electronic music. Wanted circuit diagrams, manuals of drum machines, synthesisers, effects. Pawel Buczkowski, Emilii Plater 36 M 29, 00-113 Warszawa, Poland.  
**TEKTRONIX** oscilloscope dual-trace 24 MHz. Good condition £130. Curve tracer for transistors

£85. Marconi LCR bridge £75. Mr. T. J. L. Haley. Tel: 01-868 4221.  
**SATELLITE** television 4GHz L.N.A. down converter. 2 metre/70cm transceivers. VDU terminal. Other equipment. SAE for full list. D. C. Chapman, 6 Pickhurst Green, Hayes, Bromley, Kent BR2 7QT.  
**CCIARCIAS** 280 build your own micro project. Anyone interested in forming a self help group contact: T. S. Houghton, Well Farm, Great Ouseburn, York YO5 9RQ. Tel: Green Hamerton 30620.  
**HELP** and advice needed on equipment required for recording 78 RPM acoustic records to acceptable quality. R. Newsome, 50 Carn Bosavern, St. Just, Penzance, Cornwall TR19 7QX. Tel: Penzance 787111.  
**UK101** 64K memory basic X basic 5 Cegmon via board disc drive vortex operated word wizard

disc £190. D. E. Melton, 35 Lyndhurst Road, London E4. Tel: 01-527 4492.  
**COMMODORE** 64 computer with cassette and software. Original cost over £450. Will accept £200. Marwen E. Eisabban, Corpus Christi College, Oxford OX1 4JF. Tel: 0865 52500 (evenings).  
**WANTED** transistor fundamentals volume I and II. Jack Anderson, 22 Landau House, Chatsworth Road, London NW2 4BW. Tel: 01-451 3093.  
**SOLARTRON** CX 1444 sweep-delay X-amp. CX 1443 X-amp sub-unit. Both unused in original packings with handbooks. Tel: 09358 23215.  
**WANTED** any broken C.B.s, linears, transceivers, etc. Cash paid. Write to: A. Jordan, 23 Tyton Lane East, Boston, Lincs.  
**WANTED** manual and circuit diagram for Hartley oscilloscope type CT436. Tel: 0303 42054.

Please publish the following small ad. FREE in the next available issue. I am not a dealer in electronics or associated equipment. I have read the rules. I enclose a **cut-out valid** date corner.

Signature ..... Date .....

**Please read the RULES** then write your advertisement here—one word to each box. Add your name, address and/or phone no.


**COUPON VALID FOR POSTING BEFORE 1 MARCH 1985**  
 (One month later for overseas readers.)

**SEND TO: PE BAZAAR, PRACTICAL ELECTRONICS, WESTOVER HOUSE, WEST QUAY ROAD, POOLE, DORSET BH15 1JG.**

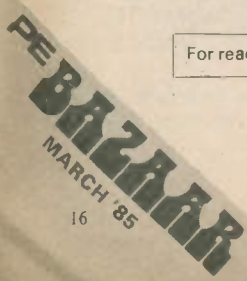**BLOCK CAPITALS PLEASE**

Name & Address:					

For readers who don't want to damage the issue send a photostat or a copy of the coupon (filled in of course) with a **cut-out valid** "date corner"



# SEMICONDUCTOR CIRCUITS

TOM GASKELL BA (Hons) CEng MIEE

## QUAD SUPPLY & LINE MONITOR (UC3903)


MODERN electronic equipment is particularly sensitive to deviations from its normal power supply voltages. An excessively high voltage can often cause permanent damage, whereas a low voltage results in malfunction of the circuitry. The problem is compounded in multiple supply systems, where a low voltage on one supply rail can cause damage if another rail is held at the nominally correct voltage. A good example of this is in split rail supplies, where the loss of just one rail can cause damage to some types of op-amp. In order to help the designer avoid these problems, Unitrode have introduced a new i.c., the UC3903, which is intended for use as a supply voltage monitor in multiple supply rail systems.

### BLOCK OPERATION

The block diagram of this i.c. is shown in Fig. 2. Essentially, it is a quad window detector capable of monitoring four voltages simultaneously. These four voltages are connected to the sense 1, 2, 3 and 4 inputs. The sense 4 input has an internal inverting op-amp provided which allows that input voltage to be either positive or negative, depending on the arrangement of external components used. Each sense input voltage is compared with two internally derived reference voltages, one which determines the over-voltage threshold, i.e. the maximum allowable limit of input voltages, and the other which determines the under-voltage threshold, which corresponds to the minimum allowable input voltage.

If one or more of the input voltages exceed the over-voltage reference, the O.V.Fault output transistor is turned on after a suitable delay period. Similarly, an under-voltage causes the

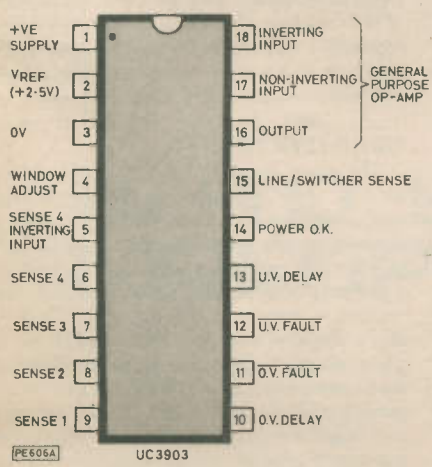U.V.Fault output transistor to turn on. If all the supplies are within the two voltage limits then the Power O.K., O.V.Fault, and U.V.Fault transistors are all turned off. However, if either an over-voltage fault or an



Characteristic	Notes	Minimum Value	Typically	Maximum Value	Units
Supply Voltage (normal operation)	Spec's measured at +15V supply unless otherwise stated	8		40	V
Quiescent Current	No faults		6	11	mA
	U.V., O.V., and line fault		10	18	mA
Temperature Range		0		+70	°C
Supply Under Voltage Threshold	Below this supply voltage threshold, fault outputs are disabled	5.5	7.0	8.0	V
Minimum Supply to Enable 'Power O.K.' Output			3.0	4.0	V
Reference Voltage	$V_{REF}$ at 25°C (and see Fig. 4)	2.465	2.5	2.535	V
Reference O/P Current	i.e. From pin 2, at 25°C			40	mA
Reference Load Regulation	O/P current (pin 2) = 0 to 10mA		1	15	mV
Reference Line Regulation	Supply = 8 to 40V		1	8	mV
Open Collector Output Voltage	Pins 11, 12 and 14			40	V
Open Collector Output Current (max)	Pins 11, 12 and 14, O/P = 2.0V	40	70		mA
Open Collector Saturation Voltage	Pins 11, 12 and 14, O/P current = 12mA		0.25	0.45	V
Sense Input Bias Current (max)	Pins 6, 7, 8, 9 and 15		±1	±6	µA
Sense Input Voltage	Pins 6, 7, 8 and 9	-0.3		+20	V
	Pin 15	-0.3		+40	V

Fig. 1. Pinout and specifications

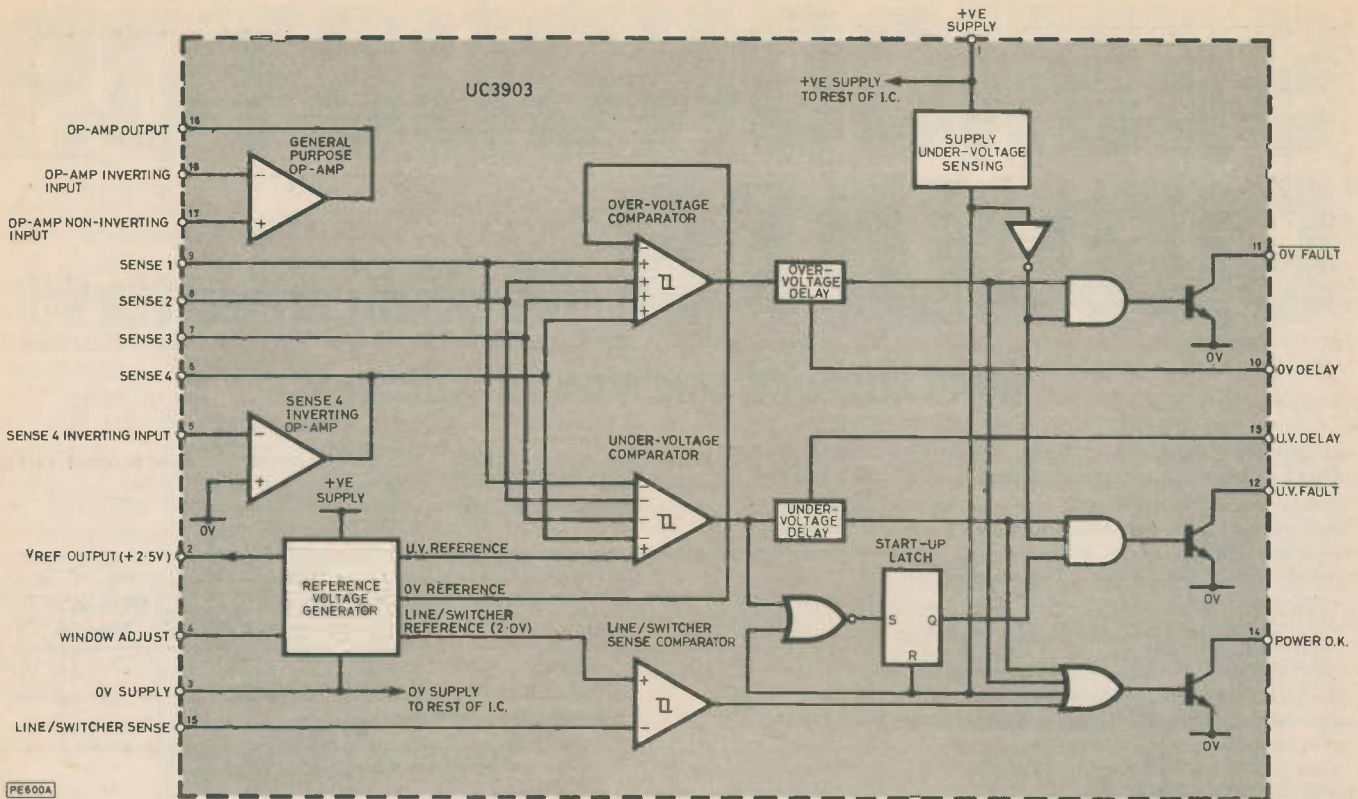


Fig. 2. Block diagram

under-voltage fault is detected, then the Power O.K. transistor is turned on, somewhat paradoxically showing that power is specifically *not* O.K.! To avoid false alarms, internal circuitry detects when the supply to the i.c. itself is at a low level (usually during turn on or turn off) and disables the outputs during this period. A separate line & switcher sense input is provided, which controls only the Power O.K. output to provide early warning of mains voltage or other power source failures. Finally, a 'general purpose' op-amp is provided to extend the flexibility of the i.c.; this is ideal for use when two negative supplies need to be monitored.

### INPUTS AND THRESHOLDS

The four sense inputs have a permissible range of  $-0.3$  to  $+20V$ , as can be seen in Fig. 1. In fact, the input circuitry includes a series  $2k$  resistor and a  $5.7V$  Zener diode to  $0V$ , so at voltages above  $5.7V$  the input impedance will be fairly low. This will rarely be a problem in practice because the i.c. is designed for a 'normal' input, i.e. a valid input voltage, of  $2.5V$ . The input impedance at around this voltage is very high indeed, so the various voltages to be monitored can be scaled with potential dividers (or amplified externally if required) to the nominal  $2.5V$  level.

The over and under-voltage thresholds are

set by voltage reference circuitry within the i.c., in conjunction with a 'window adjust' voltage applied to pin 4. The effect of this can be seen in Fig. 3. At low window adjust voltages the fault window (in this case the range of 'acceptable' input voltages) is narrow, so the i.c. is very critical of errors in the sense input voltages.

At high window adjust voltages the fault window is wide, so the i.c. is very tolerant of variations in sense inputs. Typically,  $1$  volt on pin 4 will allow the inputs to vary by  $\pm 10\%$  from nominal. Hysteresis prevents 'hunting' of the i.c. around the threshold points, and this is also shown in Fig. 3. Pin 4 is a fairly high impedance point so a simple pair of resistors can be used as a potential divider from the  $2.5V$  reference output, pin 2. Incidentally, the voltage reference is ideal for use in other parts of the circuitry, if required. It has reasonable regulation, and tracks well with temperature as shown in Fig. 4. Furthermore, it has a high output current capability—typically  $40mA$ .

### NEGATIVE INPUTS

The sense 4 input of the UC3903 can be used as either a positive or negative voltage monitoring point. By connecting pin 5 to a high voltage the inverting op-amp output will be reverse biased, allowing pin 6 to behave as a perfectly normal sense input. However, if a resistor is connected between pins 5 and 6, and a negative voltage is connected to pin 5 via a second resistor, the op-amp will invert the negative voltage (with whatever gain or attenuation is set by the ratio of the resistors) and allow the sense 4 facility to monitor this positive derivation of the original negative


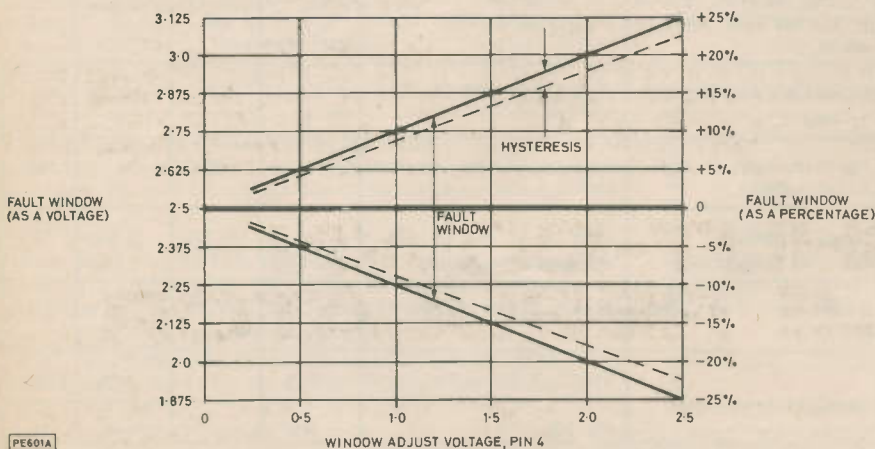


Fig. 3. The effect of the window adjust voltage on the fault window

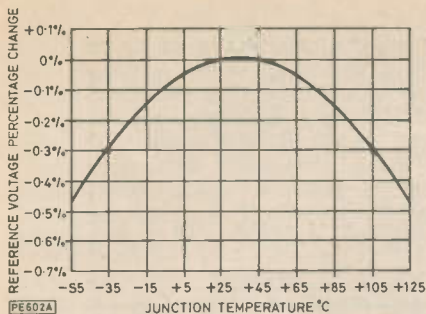

**Fig. 4. Variation on 2.5V reference with temperature**


voltage. The spare 'general purpose' op-amp is provided for any suitable application, one example of which is to invert a second negative voltage, and feed this into sense 1, 2 or 3 in a similar arrangement to that used for sense 4. The op-amp can source over 20mA of current, so it will come in useful for many other purposes in other parts of the circuitry.

### OUTPUTS

The three outputs from the comparators section of the i.c. are all open collector transistors. Hence, to get a voltage swing out of these outputs a pull-up resistor to a positive supply will be needed in each case. All the transistors can switch 40mA or more, so they are ideal for directly driving relays or indicators. Total dissipation for the whole i.c. should be kept below 1W (at 25 degrees centigrade). Naturally, if driving inductive loads, protection diodes should be added between the i.c.'s outputs and the load's positive supply rail.

The UC3903 is provided with sophisticated protection against erroneous outputs during power-up and power-down. Until the i.c.'s own supply has risen above a supply under-voltage threshold (between 5.5 and 8.0V) all the outputs are disabled, and the start-up latch is reset. The latch prevents any under-voltage fault being signalled until all the sense inputs have gone above their under-voltage thresholds for a first time since power was applied. When they have all gone above the threshold the first time, the latch is set, and normal operation of the U.V.Fault output can begin. This has all been designed to allow for slow-starting or supply sequencing, but should be borne in mind if immediate response to under-voltage conditions, when power is first applied, is required.

The line/switcher sense input is a general purpose facility that directly affects only the Power O.K. output. No time delay is included, and its threshold is nominally 2.0V rather

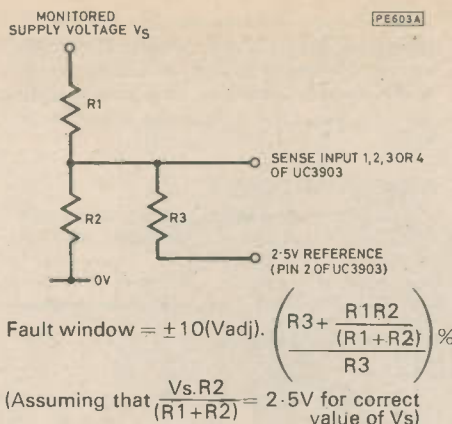


**Fig. 5. Widening an individual fault window**

than the 2.5V used elsewhere. The Power O.K. transistor is turned on (i.e. power is *NOT* O.K.) when the line/switcher sense input drops to below this threshold. Its intended use is to allow the monitoring of voltage levels earlier on in a power supply system, either from the secondary of the mains transformer or from a power transformer in a switching regulator. In both these cases the waveform would have to be rectified (by a series diode), smoothed (capacitor and resistor to 0V) and attenuated prior to monitoring. The smoothing capacitor should be made as small as possible to allow fast reaction to any loss of power. This arrangement could allow the UC3903 to shut down other circuitry and systems before serious damage might be caused.

### DELAYS

Both the under and over-voltage systems have a delay facility. This is activated by connecting capacitors from pin 10 and 13 to 0V. The effect is to delay the activation of the U.V.Fault or O.V.Fault outputs by a time of typically 30ms per microfarad. If the fault condition at the sense input is removed during the delay period then the delay is cancelled and no fault output is signalled. This arrangement allows for immunity against noise spikes on the supply causing spurious fault outputs. Leaving pin 10 or pin 13 open circuit provides the fastest possible response to fault conditions, but the least tolerance of noise on the supplies.

It is important to note that the delay circuitry was designed primarily to operate in the microseconds and small number of milliseconds range. Although fairly large capacitors can be used to give several seconds delay, they

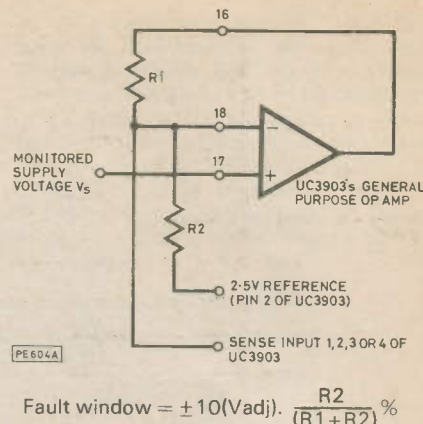

**Fig. 6. Narrowing an individual fault window**

can cause the start-up latch to operate incorrectly. Specifically, the use of large capacitors results in under-voltage sense inputs triggering the U.V.Fault output (after the appropriate delay) directly after power-up, without having to first be taken above the under-voltage threshold as would normally be the case. (This is due to the inability of circuitry within the i.c. to charge up very large capacitors quickly enough.)

### ADJUSTING WINDOWS!

Figs. 5 and 6 show techniques which can be used to alter an individual sense input's fault window. This can be necessary when just one particular input requires either tighter tolerance monitoring, as in the case of a precision reference, for example, or wider tolerance such as might be required for an unregulated supply.

The UC3903 is a very cleverly thought out device, which is ideal for use in monitoring supplies in larger electronic systems. Its uses don't end there of course, as it makes an excellent general purpose window detector for many types of transducer input, giving warning of variations in liquid level, temperature, light level, etc., as appropriate. Other devices in the family are the UC1903 and the UC2903, which are functionally identical to the 3903 but feature extended temperature ranges and slightly better specifications.

### AVAILABILITY

The UC3903 can be obtained from House of Power, Electron House, Cray Avenue, St Mary Cray, Orpington, Kent BR5 3QJ, or Thame Components, Thame Park Road, Thame, Oxfordshire.

# AUTO SHUT-DOWN MULTIPLE REGULATOR

**T**HIS circuit uses the UC3903 i.c. to monitor three supply voltages, as part of a three rail power supply system. The circuit diagram is shown in Fig. 7, and its Veroboard layout in Fig. 8. If any of the supplies are

taken further than  $\pm 10\%$  from their nominal value, *ALL* the supplies are shut down, and are kept shut down by blowing a pair of fuses! This offers a comprehensive, if cautious approach to ensuring that imbalance in multiple

supplies and over-voltages do not cause damage to the circuitry being powered by them.

IC2, IC3 and IC4 are the three voltage regulators in question, giving supplies of

$\pm 15V$  and  $+5V$  from unregulated  $\pm 20V$  inputs. These are provided with the usual protection diodes and stability-maintaining capacitors. R11 and R12 tap down the  $+15V$  supply to a nominal  $+2.5V$  to feed into IC1, and likewise R13 and R14 feed IC3's output to IC1. IC4 uses the sense 4 inverter, with R15 and R16 allowing, again,  $+2.5V$  to be present at pin 6 of IC1. Pin 8 is used to provide a push-button test facility, S1, which

15, is not used, so is kept biased to the positive supply rail by R17, and the general purpose op-amp likewise is unused, so it is connected as a voltage follower (pin 16 is connected to pin 18), with the non-inverting input tied to  $V_{REF}$ .

### SHUTTING DOWN

The automatic shutting down is not a subtle affair, but it is effective! CSR1 and CSR2 are

occur. (Naturally, if a 7805 is not used this voltage restriction does not apply.) The supply should have enough current capability to drive the required current out from the regulated supply outputs, plus a little in hand. Naturally, FS1 and FS2 should be matched to this maximum current capability. It may seem surprising that slow-blow types are recommended, but in practice the thyristors blow them effectively instantaneously, and their otherwise

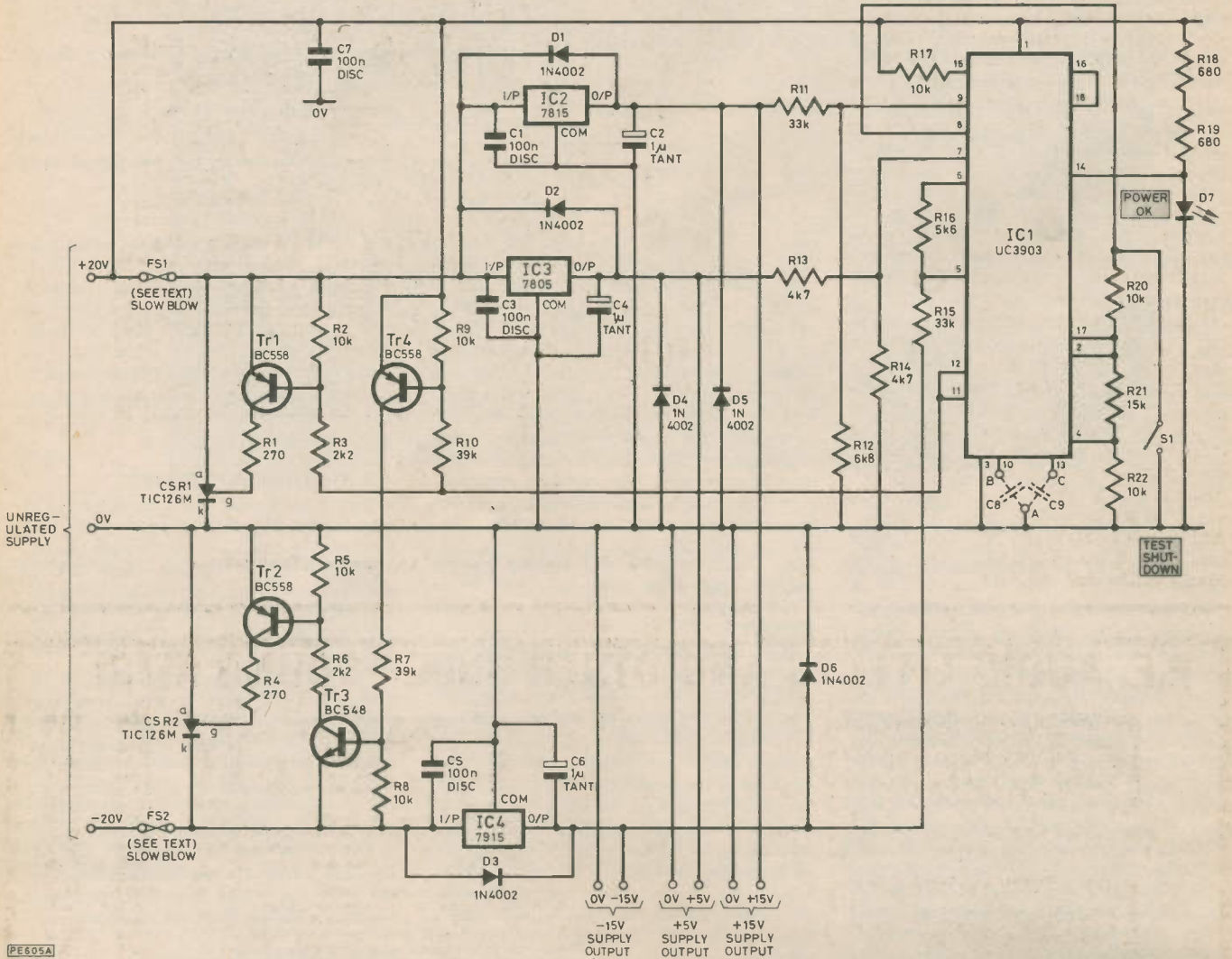


Fig. 7. Auto shut-down multiple regulator

tests the effect of an under-voltage at the sense 2 input. In normal use, sense 2 is sunk by IC1 to  $+2.5V$  by R20.

Resistors R18, R19 (two resistors keep the power requirement down) and D7 provide a 'Power O.K.' i.e.d. facility. When the Power O.K. output transistor of IC1 turns on, current from R18 and R19 is sunk by IC1 pin 14, and the i.e.d. turns off. R21 and R22 set the window adjust voltage at pin 4 to  $1.0V$ , which defines the fault window as  $\pm 10\%$ , as shown in Fig. 3. C8 and C9 are connected as shown between terminal pins A, B and C, since their values might need some experimenting with. The line/switcher input, pin

8 amp thyristors triggered by TR1 and TR2 respectively. TR2 in turn is turned on by TR3 and TR4, with associated resistors, which provide level shifting to the negative supply rail from the all-positive supply used by IC1. The U.V.Fault and O.V.Fault outputs are wired together so that the thyristor circuit is triggered by an over-voltage, an under-voltage, or even both simultaneously. When the thyristors are triggered they immediately blow both fuses and clamp the regulated supplies near to  $0V$  via D1, D2 and D3.

The unregulated supply should be nominally  $\pm 20V$ . The positive half should not exceed  $+24V$ , since damage to IC3 might

slow action prevents inadvertant blowing due to minor transient pulsing of the thyristors themselves when power to the circuit is turned off. The choice of thyristor is not critical, but 8 amp types were used in this case to be safe with surge current handling capability. The thyristors only conduct for a fraction of a second before the fuses blow, so there is no time for them to get hot and no need for heat-sinks. IC2, IC3 and IC4 have been placed close to the edge of the board to allow easy fitting of their heatsinks, via insulating kits due to the internal connection of their metal tabs to the centre pin. Any momentary switch, local or remote, can be used for S1.

## SELECTING THE DELAYS

Capacitors C8 and C9 should be selected to give the delays required. Typically, it is suggested that the response to over-voltages should be fast, as circuits are at considerable risk, whereas under-voltages are less serious. The prototype circuit used 1nF for C8 giving an over-voltage delay of approximately 30µs, and 100nF for C9, giving an under-voltage delay of 3ms. Be aware that too short a delay for under-voltages can result in false triggering due to the regulators not charging C2, C4 and C6 fast enough during turn-on, and too long a value can cause the effects described earlier. If a regulator output is under-voltage (for example, shorted to 0V) when power is first applied, the circuit will fail to shut down; the UC3903 requires that the sense input must first be taken above the under-voltage threshold. It can be impractical to use the Power O.K. output, since that goes into the 'not O.K.' condition during power-up. If this is a concern, however, it is a fairly straightforward process to add extra circuitry to combine all three outputs satisfactorily to provide shut-down under even these conditions.

The circuit can prove rather tedious to test, since the first thing that happens if there's a fault is that it blows the fuses, at which point there's nothing to test any more! Initial tests should be done with R1 and R4 omitted, which prevents CSR1 and CSR2 being triggered. When the fuses have been blown, the supply should be turned off and the unregulated supply allowed to discharge before new fuses are inserted, or they will blow immediately in all likelihood. PCB fuse clips are used in Fig. 8, but off-board fuseholders could equally well be used, of course.

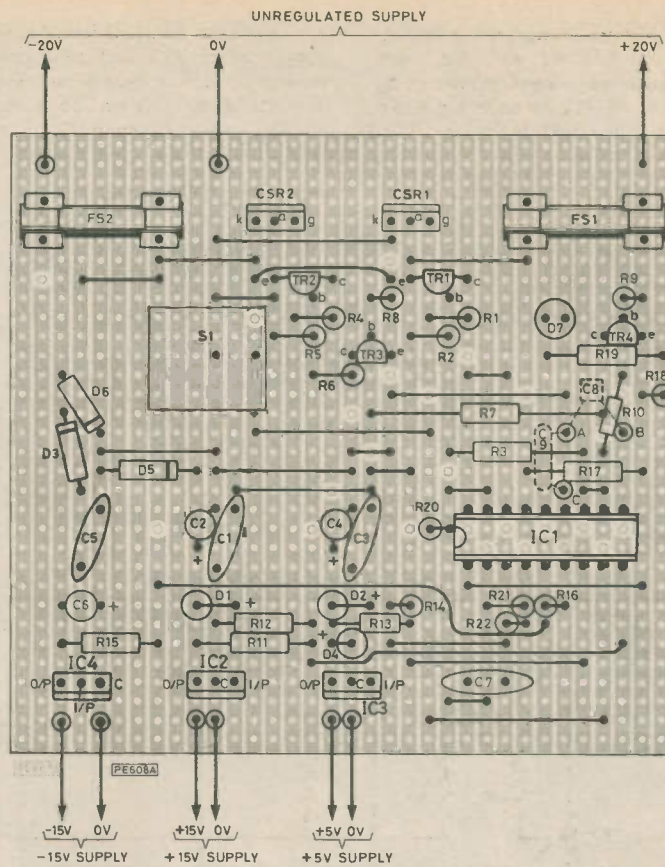


Fig. 8. Veroboard layout of the multiple regulator

## P.E. AUDIO EFFECTS AND OTHER SUPER SOUND KITS!



P.E. MONO-STEREO ECHO-REVERB (SEP84) 200ms echo, lengthy reverb, multi-tracking kit as published - BLK box: SET 218 £55.66



P.E. FILTER-SHIFT PHASER (OCT84). Enhanced Phasing with modulated filter shifting. Kit as published - BLK box: SET 226 £39.13



P.E. RING MODULATOR (NOV84). With multi-waveform VCO, Noise Gate & Auto-level Control. Kit as published - BLK box: SET 231 £39.99



P.E. MONO-STEREO CHORUS FLANGER (JAN85). Superb dual mode music enhancement. Kit as published - BLK box: SET 235 £55.66


BLK BOX - steel & aluminium, black plastic finish. STD BOX - plain aluminium, lipped lid. SET codes include PCBs, parts, instructions, boxes, wire, solder. More details & kits in catalogue - send S.A.E. (Overseas £1 or 5 IRC's).

	CODE	STD BOX	BLK BOX
BASS BOOST: Increases volume of lower octaves	SET 138B	£8.46	£11.46
BLOW BOX: Voice operated VCF & VCA for fascinating effects	SET 214	£24.33	£28.33
CHORUS (SIMPLE): Multiplied solo enhancement	SET 162	£31.40	£34.90
COMPRESSOR: Limits & levels maximum signal strength	SET 133	£10.86	£13.86
ENVELOPE SHAPER: Note triggered AOSR unit with VCA	SET 174	£17.15	£20.65
EQUALISER: Variable combinations of Low, Mid, Top & Notch	SET 217	£22.33	£25.83
EQUALISER: 10 Channels fully variable	SET 134	£37.83	£41.83
FAOER: Voice operated with 5 response controls	SET 167	£14.21	£17.21
FLANGER (SIMPLE): Fascinating phased resonance effects	SET 153	£22.74	£26.24
FREQUENCY CHANGER: Tunable note & waveform modifier	SET 172	£34.46	£37.96
FREQUENCY DOUBLER: Guitar octave raiser & tone changer	SET 98	£9.80	£12.80
FUNKY-WOBULO: Modulates a singing voice	SET 149	£12.40	£15.40
FUZZ: Smooth distortion, retains attack & decay	SET 91	£10.57	£13.57
GUITAR OVERDRIVE: Heavy fuzz with selectable qualities	SET 56	£19.73	£23.23
GUITAR SUSTAIN: Extends note decay time, with noise gate	SET 222	£22.81	£25.31
GUITAR TO SYNTH INTERFACE: With voltage & trig outputs	SET 173	£32.87	£36.37
HANO CLAPPER: Auto & manual variable clap effects	SET 197	£22.69	£25.69
HEADPHONE AMP: 2 watts into phones or speaker, variable	SET 156M	£12.03	£15.53
JABBERVOX: Voice disguiser with reverb & tremolo	SET 150	£23.84	£27.34
METRONOME: With audio output & visual beat & downbeat	SET 143	£13.81	£16.81
MIC PRE-AMP: Variable gain & switched tone response	SET 147	£7.13	£10.13
MIXERS: Several in catalogue			
MOCK STEREO: Splits mono signal into stereo simulation	SET 213	£19.87	£23.37
MULTIPROCESSOR: Flng, Rvb, Faze, Fuzz, Wah, Trem, Vib	SET 189	£57.14	£61.14
MUSIC MODULO: 8 variable tremolo & wah guitar effects	SET 196	£18.79	£21.79
MUSICAL CALL SIGN: Programmed call sign generator	SET 121	£12.91	£16.41
NOISE GATE: Reduces tape & system noise	SET 145	£9.97	£12.97
PHASER (SIMPLE): Auto & manual rate & depth controls	SET 164	£18.40	£21.90
REVERB: (SIMPLE) Mono/stereo, variable depth & delay	SET 203	£25.54	£29.54
RHYTHM GENERATOR: Computer driven, 9 drum effects	SET 185	£30.64	£34.64
RHYTHM GENERATOR: 15 pre-programmed rhythms, 9 effects	SET 170	£35.64	£39.14
ROBOVOX: Versatile robot type voice modifier	SET 165	£21.03	£24.53
SPEECH PROCESSOR: Clearer speech and level control	SET 110	£9.68	£12.68
STORMS EFFECTS: Auto & manual wind, rain & surf effects	SET 154	£15.86	£19.36
SWEEP GENERATOR: Auto sine wave 20Hz-15KHz, variable	SET 169	£16.41	£19.91
TOM-TOM SYNTH: Sound triggered, multivariable	SET 190	£15.05	£18.05
TONE CONTROL: Bass, mid, treble, gain & cut	SET 139	£13.17	£16.67
TREBLE BOOST: Increases volume of upper octaves	SET 138T	£8.13	£11.13
TREMOLO: Mono variable rate & depth modulation	SET 136	£9.71	£12.71
VOLTAGE CONTROLLED FILTER: 12dB, variable modes	SET 178	£17.02	£20.52
VOCOAVOX: Modular vocoder, 7 chns, extendable	SET 152	£64.31	£68.31
VOOALEK: Robot type voice modulator	SET 155	£12.44	£15.44
VOICE OP SWITCH: Variable sensitivity & delay	SET 123L	£13.41	£16.41
WAH-WAH: Auto, manual & note triggered	SET 140'	£17.26	£20.76

MAIL ORDER: Add 15% VAT & £1 P&P to all orders (overseas details in cat). Payment CWO, CHQ, PO, ACCESS, VISA. Details correct at press. E&OE. Despatch usually 10-14 days.

PHONONICS, DEPT PE53, 8 FINUCANE DRIVE, ORPINGTON, KENT, BR5 4ED.

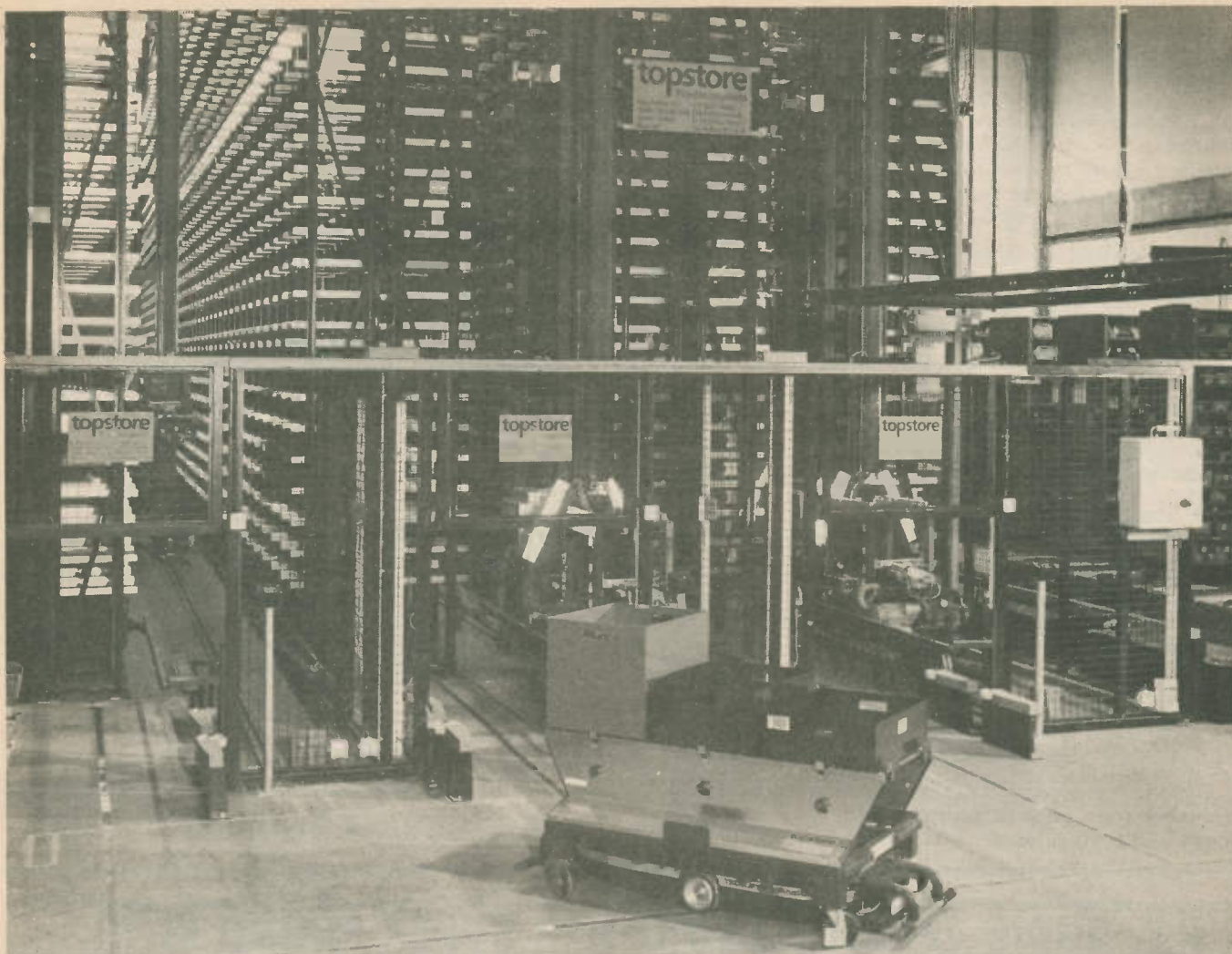Tel: Orpington 37821 (STD 0689, London 66), Mon-Fri 10-7.



# **MARS ELECTRONICS**

As most readers of *Practical Electronics* will know, we have, over the last few years, maintained extensive coverage of modern developments such as micro computers and robot technology. In keeping with this policy, we are now looking at the applications and effects of these technologies in practical use.

## **TECHNOLOGY IN INDUSTRY**

The scope and possibilities for the use of modern technology in all areas of commerce and industry are enormous. In a very short period of time, we have seen the introduction of computers, microprocessor control systems and robotics. Such acronyms as CAD/CAM, ATE and AGV have become everyday terms. Despite this, there are very few companies who have utilised this modern technology to any where near its full potential. Indeed it seems that the so called second industrial revolution is proving to be a fairly slow change.

The failure to respond by many firms, may well bring about their own downfall. However, one company which is committed to new technology is Mars Electronics which, for the last five years, had maintained a growth of 50 per cent per annum.

Mars Electronics are associated with Mars, the confectioners, and were originally set up to promote further outlets for their confectionery products. This was achieved by setting up their Money Systems Divisions in the seventies, which produced coin validation and acceptance mechanisms for vending machines. They now supply over 90 per cent of the European and 80 per cent of the world market in coin mechanisms.

Since then Mars have diversified their product range by setting up a Marine Systems Division which launched Vigil Radar in 1983. This product quickly established them as a market leader in small boat radar, a position which they look likely to maintain. In December 1984 they launched two new products, Vigil-2 and Vigil-RM which they claim will give them global supremacy for years to come.

At the moment they are working on Automatic Test Equipment (ATE), which they think will give many small electronics companies their first chance to buy advanced electronic test gear. Much of the ATE now available is far beyond the reach of these companies with prices often in the region of £100,000. Once again Mars confidently predict their superiority in the market place.



The key to the success of Mars lies in their unique manufacturing concept and clever marketing strategy. According to their Systems and Automation Manager, Nigel Kingsley "An ultimate aim of the company is to have total automation of stock handling and manufacturing processes." This together with their niche marketing strategy has made Mars one of the fastest growing companies in Europe.

*"An ultimate aim of the company is to have total automation of stock handling and manufacturing processes"*

## COMPUTER INTEGRATED MANUFACTURE (C.I.M.)

In one of their two British factories at Reading, Mars have created a futuristic working environment. In a fairly small building tailored to their own needs are housed over 200 terminals (keyboards and VDUs) all linked by their own local area network (LAN). With a total staff of only 600, working on three shifts per day, this gives an average of one terminal for each employee.

The factory itself is completely open plan, fully carpeted in all areas including the production line. No one has an office and the canteen caters for management and staff alike. Some rooms are cut off from others but for reasons of security rather than personnel importance.

The computer network is split into several sections each dealing with a particular task, such as design, manufacturing and commercial activity. Because all these functions are interrelated information is being constantly transmitted between sections, enabling a very flexible and cost effective system to operate. Using this system almost every process is computer aided or controlled. A block diagram of the C.I.M. model is shown in Fig. 1.

## COMPUTERS IN ACTION

The first stage in the production of a finished product is the design. This is only started after extensive market research into a particular area. The policy of Mars Electronics is to aim at a low to medium size market and then arrive at a product which they believe cannot be matched either in quality or price. This strategy allows them to lead a particular field and by constant improvement maintain this lead. (The reason for aiming at low to medium size markets is that it would be impossible at this stage to compete with mass production, and at the same time would drastically reduce flexibility.)

Much use is made of their CAD/CAM system (VAX 11/34), which is connected to the LAN and runs 'Aplicon BRAUD' software. The six work stations connected to the system provide a comprehensive CAD/CAM facility enabling advanced design capability. Plans are now ahead to take the system further by direct connection to the process machinery. This will allow design and manufacturing data to be transferred directly to the automated process machines making for a more efficient system.

Once a product has been designed, then the required materials are entered into the manufacturing computer system and a production line and test area is set up. At all times there is a facility to change at very short notice to another product, or modify designs to suit the manufacturing processes. In fact the Mars factory currently produce between 600 and 700 different products. This is achieved by their system of modular design whereby different production lines can easily be set up to meet changing demand.

The 'Manufacturing' computer (HP3000/48) has 3 Mbytes of on board memory with single 125 Mbyte and 404 Mbyte disc systems. Software such as: Manufacturing Management, Quality Assurance, Sales Specification and Administration are all carried out using around 40 terminals connected to the system.

# the way ahead *Richard Barron*

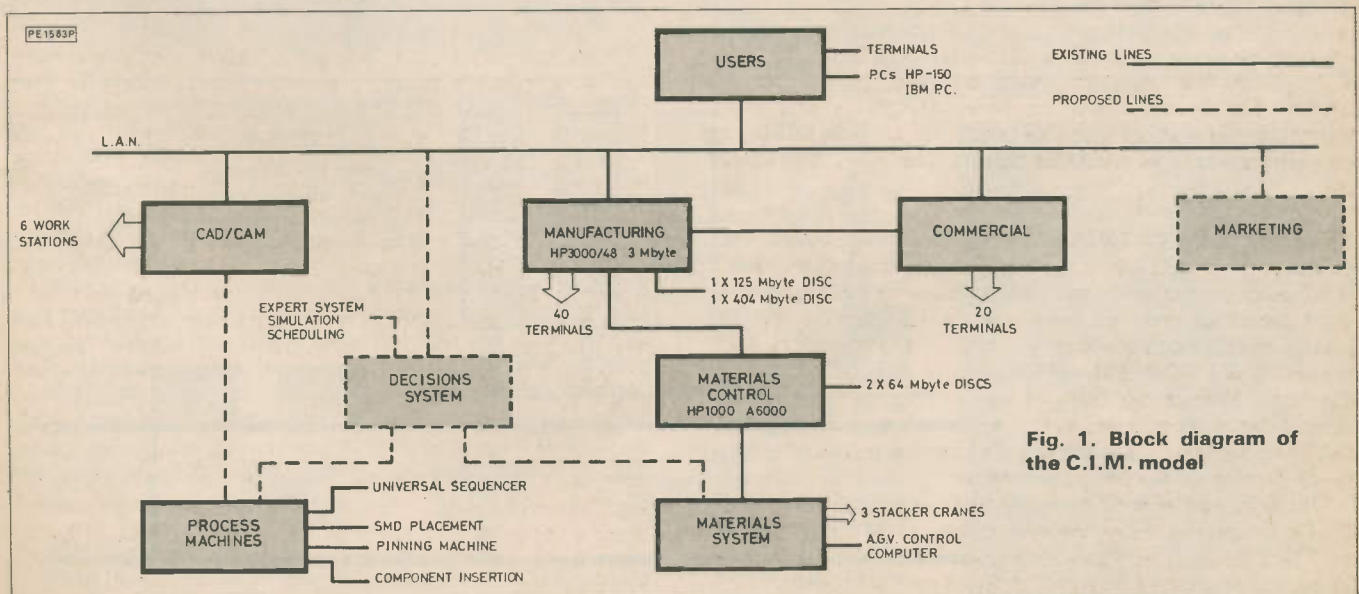


Fig. 1. Block diagram of the C.I.M. model

There are existing connections between this system, and the Commercial and Materials Control computer (HP 1000) via the DS/300 link. A further 20 terminals have access to the Commercial computer which performs: Sales order processing, Payroll, and various Ledger functions including Purchasing and Sales, to mention but a few. The Materials Control Computer has twin 64 Mbyte disks and provides all the necessary control data for the stock control system and the AGV's.

At this point automation really comes into its own. The computer's data store (memory) has all the necessary information to maintain stock levels and keep the production running smoothly. Much of the production is automatic and components can be distributed to any section of the assembly line or storage space as required. This is made possible by the use of Automatic Guided Vehicles (AGVs).

### AUTOMATIC STORAGE AND RETRIEVAL SYSTEM


When stock is delivered to the factory it is manually placed into trays and bar coded. At the same time the relevant details are fed into the computer. AGVs then transport the trays to the storage area where they are transferred to 'automatic fork lift cranes'. The cranes move the materials to the required storage space under the guidance of the Materials System computer. This means that once goods have entered the factory, the computer has a record of the level and whereabouts of all materials. A diagram of the stock control system is shown in Fig. 2.

Throughout the factory there is a network of buried foil tracks which can guide the AGVs. This allows the movement of goods to any required area under complete control of the operating system. For example, suppose a batch of resistors is needed at a particular production area, then it is a simple task for a manual operator to key in the required code. The system will respond by checking the storage location of the item required and instructing the stacker cranes to retrieve the correct tray, and pass it to an AGV. The AGV will take the items to the selected area where they are accepted by a manual operator who will read the bar code. This will cause the computer to update its stock files and respond accordingly, maybe by producing an order form for more components.

At any one time there may be a number of AGVs moving around the factory, transporting and retrieving materials from all areas. This system offers many advantages over the old fashioned manual method of stock handling, such as: increased efficiency, smaller storage and total reliability.
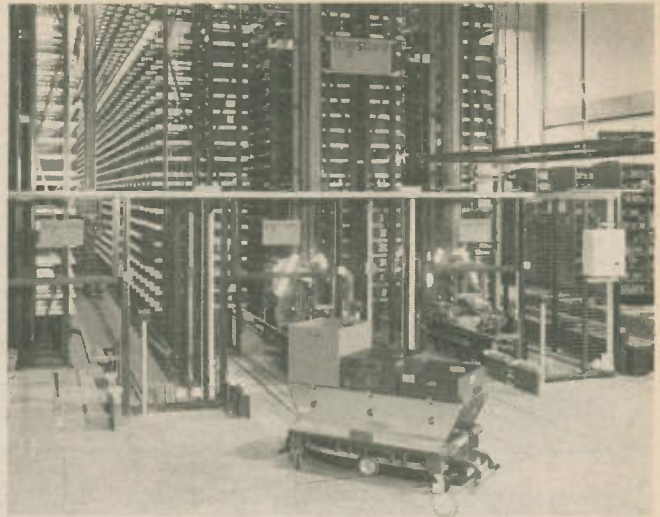
### PROCESS MACHINES

The process machines are not at the moment directly con-



Above: An AGV delivering materials to the store. Right: Complex machinery gives total control

ted to the LAN, but plans are under way for future development. Even so there are facilities for any machine to be serviced by the CAD/CAM and the AGVs, thus even at this stage there is little manual input. Mars have several process machines in operation including automatic sequencers, axial inserters, d.i.l. inserters, pin inserters and flow soldering equipment.

### AUTOMATIC SEQUENCER

When a production run is decided upon, then the required stock which is recorded in the computer can be retrieved as and when necessary. The stock is distributed between the various departments for use at the required time. All axial components such as resistors, capacitors, diodes and inductors can be automatically inserted into the p.c.b. This is quite a complex operation and must be done in a strict sequence. To ensure this sequence an automatic sequencer will load bandeleros of components to be fed into the insertion machine. It does this under the control of a computer program which instructs the machine to extract particular discrete components from a series of feeders and place them one at a time in the bandelero (similar to that of a machine gun). The bandelero is then transferred to the insertion machine which need not be programmed with the type of component but merely the insertion sequence.


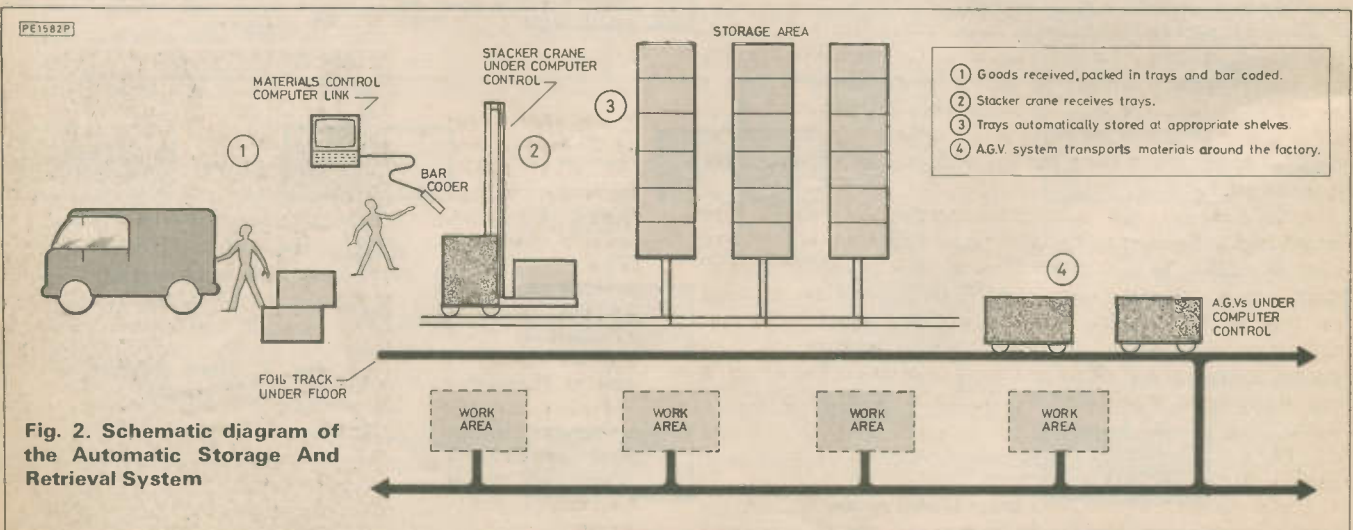


Fig. 2. Schematic diagram of the Automatic Storage And Retrieval System

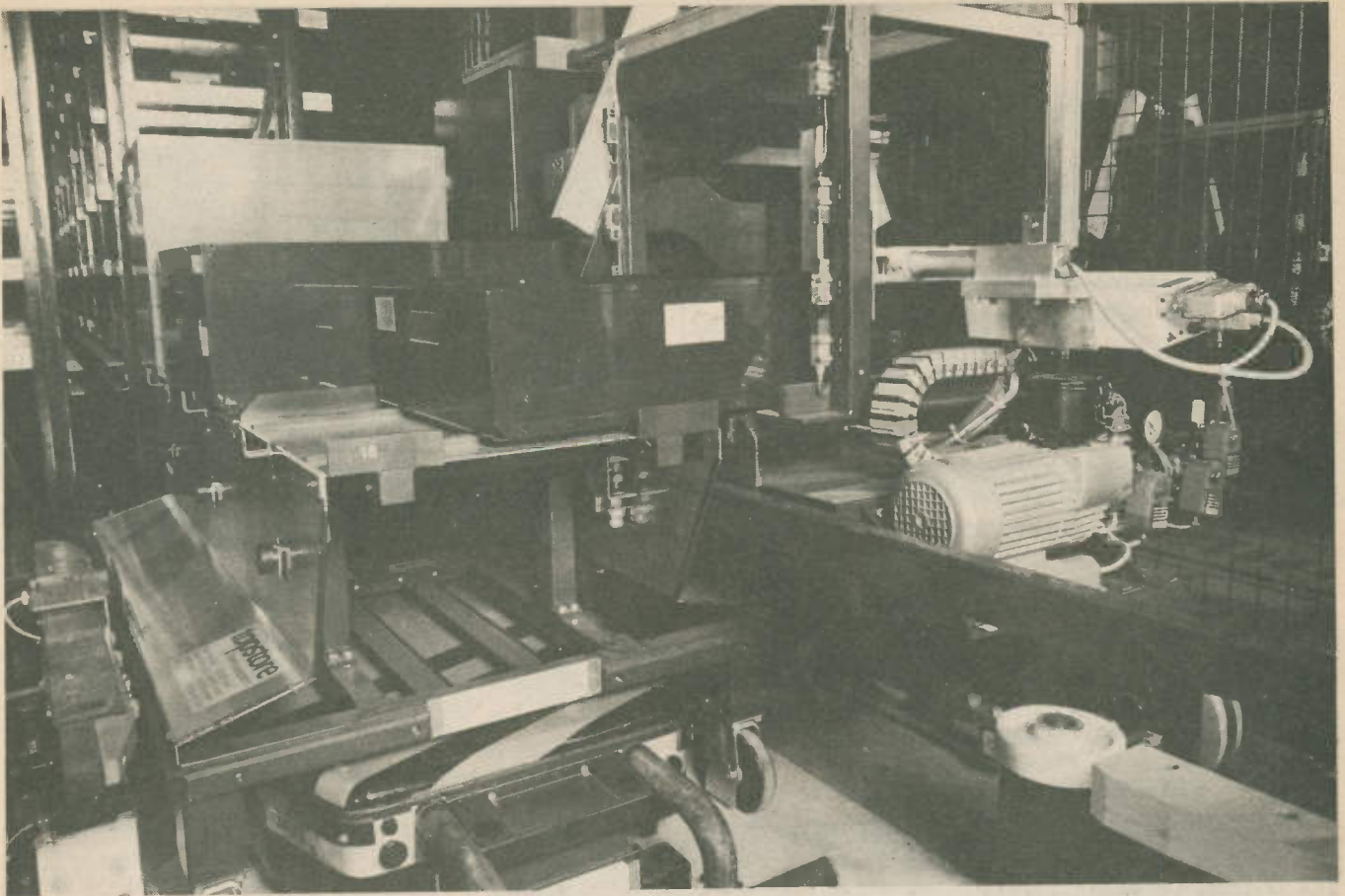

## INSERTION

Most of the components are automatically inserted, other than such items as relays and three terminal devices like transistors and regulators. The axial components are fed into the insertion machine already sequenced so it is a relatively straightforward task. The leads are formed to the required spacing and the p.c.b. is positioned under the insertion head. Each component is handled in much the same way. It is inserted into the pre-drilled p.c.b., the leads are cut and then bent over to provide mechanical strength. All parameters (lead length, bending etc.) are preprogrammable and may be altered at any time, so the whole operation may be done with the minimum of human supervision.

The d.i.l. package insertion is done in a similar way, except that the sequencing is an integral part of the operation. Feeders are loaded with a variety of devices, each feeder having a particular device. The p.c.b. is automatically positioned under the insertion head and the machine will select components in the required order, insert them, cut the leads, and bend them to the required pitch.

After these two operations are completed the p.c.b. is then transferred to the human operated production area via conveyor belts or AGVs. Here they are finished with any other components necessary before being transferred to the flow soldering machine. At any time throughout any of these operations a partially completed job may be taken back to the stores for temporary storage and at all times the computer would be aware of the progress and location of any particular component or part-work.

## FLOW SOLDERING

When the p.c.b.s have been assembled they are fed into the flow soldering machines which exposes them to several

processes. The boards are heated and fluxed before being fed into the solder bath. After this process the manually inserted component leads are cut and the whole board is immersed in cleaning fluid. When the boards come out they are fitted with the last few components which couldn't be immersed or exposed to heat. From here they are passed to the inspection and testing sections.

The testing departments make extensive use of ATE which on most occasions has been made or modified for their own particular needs. Test jigs are set up for each particular type of board and tests can then be made for component values and tolerances, and p.c.b. faults such as short or open circuits. Following this stage they are passed to mechanical assembly which at the moment is essentially manual.

**Photo illustrating an off-loading bay for the AGV. There are many of these situated around the factory at convenient positions. At the present off-loading is a manual operation but a five-year robotics plan is underway which will eventually make all stock handling automatic**



## PEOPLE

The working environment for manual production is a far cry from the sweatshops and soul-destroying tasks of the first industrial revolution, although there are still a number of boring manual jobs which have to be done. "It is the aim of the company to eventually replace any manual tedious operations with robots." They are presently equipping a factory adjacent to their existing premises which will have all the current facilities but will be enhanced by a five year robotics plan. Particular emphasis will be on "Pick and Place" robots.

*"It is the aim of the company to eventually replace any manual tedious operations with robots"*



The human input—a fairly relaxed working environment—carpets all round!

As was mentioned earlier the bulk of the mechanical assembly is done manually but to increase reliability and efficiency Mars have moved away from the traditional linear production line by introducing a Swiss idea of circular production. Here one person may be responsible for a complete assembly instead of being forced to a single task of, maybe inserting one type of component all day long.

This system works by having a rotating work station split into several sections. Each section will have a working area with the main assembly, and a parts tray. The idea is to fit one part to the assembly and then rotate to the next section and fit the same part to that assembly. When the initial section is reached another part may be fitted and the sequence repeated. At the end of the operation the result is a number of complete assemblies all being the responsibility of one person. This gives rise to a much greater sense of satisfaction than could otherwise be achieved under the old system.

## THE FUTURE

The consequence of modern technological developments and their use in industry has not yet been seen and it will be a few years before their full effects are appreciated. It is certain that


many laborious and repetitive tasks will be undertaken by automatic machinery and that the field of communication and commercial business will become computer controlled. However, with the predicted increase in consumer goods manufacture and the so called computer revolution there may well be a social problem requiring a complete change in social attitudes.

The promised employment opportunities in the new industries have not happened and it looks now as if they never will. A report from the National Economics Development Office showed that employment in the industry has dropped by 12 per cent since 1980. It is a catch-22 situation where governments and individual companies face a difficult decision. If new technology is adopted then new jobs are unlikely in great numbers, but without it firms will find it difficult to compete with efficient manufacturers. The way ahead? ★

# Ingenuity Unlimited

A selection of readers' original circuit ideas. Why not submit *your* idea? Any idea published will be awarded payment according to its merits. Each idea submitted must be accompanied by a declaration to the effect that it has been tried and tested, is the original work of the undersigned, and that it has not been offered or accepted for publication elsewhere. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought.

## SHOP COUNTER BELL

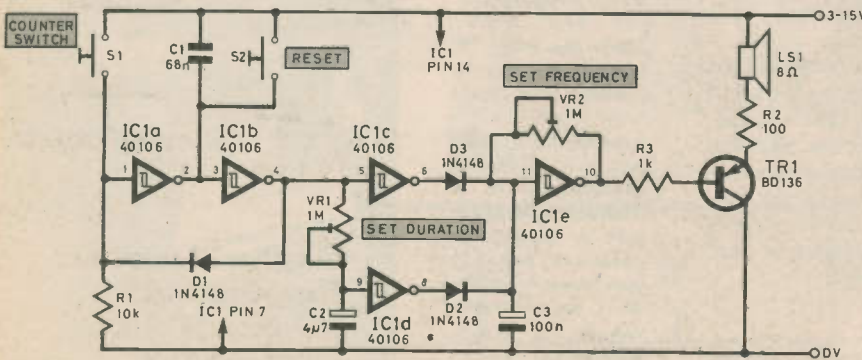

PE1636C

ANYONE who has worked in a shop or similar workplace, having a customer operated bell, will agree that an awful lot of people are persistent button pushers.

This circuit was designed to give a single pulse train at a set frequency for a set duration. Any subsequent button pushing will be of no avail, until the circuit is manually reset by the operator.

The circuit is of simple design, employing a CMOS i.c. 40106 as an astable and a monostable. The monostable sets the oscillator into operation when the counter switch S1 is pressed and the oscillator drives a speaker via TR1. Once activated, the oscillator will run its course and further operation will be inhibited until the reset is activated.

M. Miller,  
Topsham,  
Devon.

# Don't put it off any longer!

Protect your family and property with your know how and our security modules. Complete systems start from as little as

**£39.95**

## A COMPLETE SECURITY SYSTEM FOR ONLY £39.95 + V.A.T.

Control Unit  
Enclosure  
Key Switch & 2 keys  
L.E.D.'s  
5 1/2" Horn Speaker  
4 quality surface Magnetic Switches

CA 1250  
HW 1250  
KS 3901  
LED 1  
HS 588  
MS 1025



With only a few hours of your time it is possible to assemble and install an effective security system to protect your family and property, at the amazingly low cost of £39.95 + V.A.T. No compromises have been made and no corners have been cut. The outstanding value results from volume production and direct supply. Assembly is straight forward with the detailed instructions provided. When installed you can enjoy the peace of mind that results from a secure home. Should you wish to increase the level of security, the system may be extended at any time with additional magnetic switches, pressure pads or ultrasonic sensors. Don't wait until it's too late - order today.  
Order code CS 1370

CA 1250 - 2 zone alarm control unit with built in alarm & power supply £19.95 + V.A.T.  
HW 1250 Enclosure & Hardware Kit for above £9.50 + V.A.T.  
LED 1 - Set of 4 l.e.d.'s in chrome bezels + Push Switch to fit HW 1250 £2.15 + V.A.T.  
KS 3901 - 3 position Key Switch £3.43 + V.A.T.  
HS 588 - 5 1/2" Horn Speaker, output of 11-dbs with CA 1250 or SL 157 £6.25 + V.A.T.

Wide range of modules and accessories, etc. Send S.A.E. for details.

US 5063 - advanced Digital Ultrasonic Detector, high sensitivity, with false alarm suppression £13.95 + V.A.T.  
SC 5063 - Enclosure for US 5063 £2.95 + V.A.T.  
IR 1470 - Infra-red system to provide 50' invisible beam, includes both transmitter and receiver £25.61 + V.A.T.  
SL 157 - Siren Module 12V £2.95 + V.A.T.

## SELF-CONTAINED ULTRASONIC UNIT CK 5063

Requires no installation. Easily assembled using our professionally built and tested modules.



- Adjustable range up to 25 ft
- Built-in entrance and exit delay
- Built-in timed alarm
- Key operated switch - Off, Test and Operate
- Provision for an extension speaker
- Fully self-contained
- Uses US 5063, PSL 1865 Key Switch 3901, 3" Speaker 3515

only  
**£37.00**  
+ V.A.T.

Now you can assemble a really effective intruder alarm at this low price using tried and tested Riscomp modules. Supplied with full instructions, the kit contains everything necessary to provide an effective warning system for your house or flat. With a built-in LED indicator and test position the unit is easily set up requiring no installation. It may simply be placed on a cupboard or desk. Movement within its range will then cause the built-in siren to produce a penetrating 90dbs of sound, or even 110dbs with an additional speaker. All parts included and supplied with full instructions for ease of assembly.  
Size 200 x 180 x 70mm Order as CK 5063

Add 15% VAT to all prices  
Add 70p post and packing to all orders  
Units on demonstration  
Shop hours 9.00 to 5.30 p.m.  
Closed Wednesday  
Please allow 7 days for delivery


Saturday 9.00 to 1.00 p.m.  
S.A.E. with all enquiries  
Order by telephone or post  
using your credit card

**RISCOMP LIMITED**

Dept PE27,  
21 Duke Street,  
Princes Risborough,  
Bucks. HP17 0AT,  
Princes Risborough (084 44) 6326
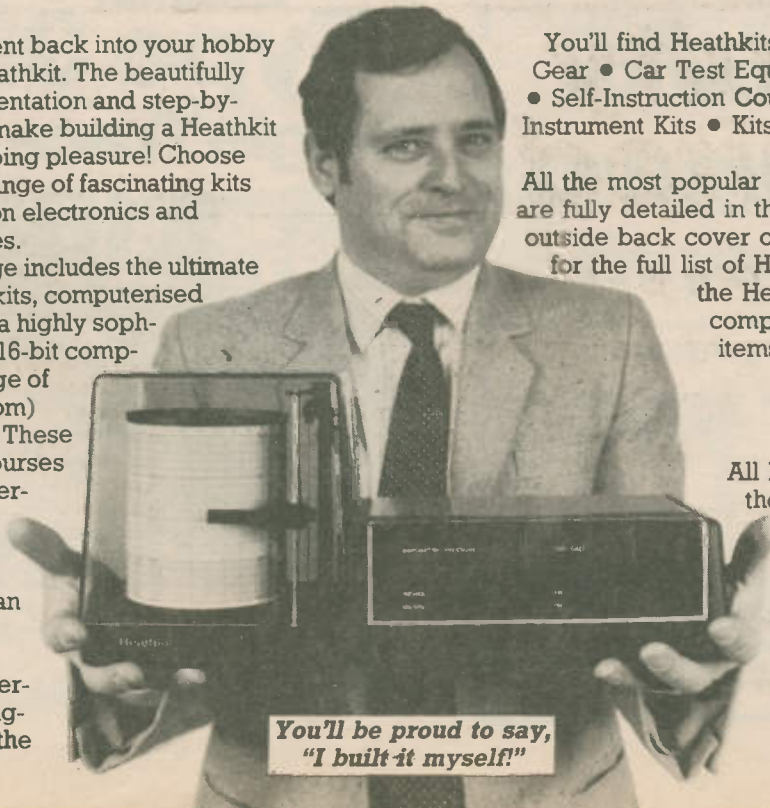
# Heathkit - IT'S A PLEASURE TO BUILD

Bring the enjoyment back into your hobby with a kit from Heathkit. The beautifully illustrated documentation and step-by-step instructions make building a Heathkit a relaxing, absorbing pleasure! Choose from their huge range of fascinating kits and self-instruction electronics and computing courses. The Heathkit range includes the ultimate in amateur radio kits, computerised weather stations, a highly sophisticated robot, a 16-bit computer kit and a range of home (or classroom) learning courses. These state-of-the-art courses have easy-to-understand texts and illustrations, divided into sections so that you can progress at your own pace, whilst the hands-on experiments ensure long-term retention of the material covered.



You'll find Heathkits available for Amateur Radio Gear • Car Test Equipment • Kits For The Home • Self-Instruction Courses • Computer Kits • Test Instrument Kits • Kits For Weather Measurements.

All the most popular kits and educational products are fully detailed in the 1984 Maplin catalogue (see outside back cover of this magazine for details) or for the full list of Heathkit products send 50p for the Heathkit International Catalogue complete with a UK price list of all items.


All Heathkit products available in the UK from:

**Maplin Electronic Supplies Ltd.**

P.O. Box 3, Rayleigh,  
Essex, SS6 8LR.  
Tel: (0702) 552911.

(For shop addresses see back cover.)

# SPECIAL OSCILLOSCOPE OFFER!

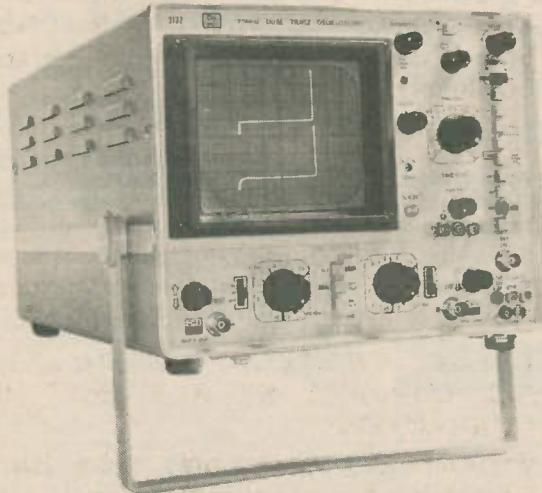

## Crotech Type 3132 Dual Trace 20MHz £299

- ★ 2mV/division to 10V/division (12 steps) calibrated sensitivity ( $\pm 3\%$ )
- ★ DC-20MHz bandwidth (-3dB). Rise time 17ns
- ★ X-Y operation
- ★ 130mm cathode ray tube
- ★ 40ns/division to 0.2s/division (18 steps) timebase ( $\pm 5\%$ )
- ★ 14 trigger functions
- ★ Triggering to 40MHz
- ★ Z modulation
- ★ 10 x 8 division display
- ★ Component comparator
- ★ DC source outputs
- ★ Measures 210H x 280W x 450D (mm), weight 8kg (approx.)

Post to: Crotech Instruments Ltd., 2 Stephenson Road, St. Ives, Huntingdon, Cambridgeshire, PE17 4WJ. Tel. (0480) 301818.

### PE/CROTECH OSCILLOSCOPE OFFER (UK READERS ONLY)

	Quantity	Total Value
Please supply	3132 @ £299	£
(Prices include VAT and delivery)	3030 @ £183	£
	3035 @ £199	£

Please complete both parts of the coupon in BLOCK CAPITALS

Access No. ....

Signature .....

I enclose cheque No. ....

Name .....

Address .....

Please allow 28 days for delivery


**OFFER CLOSES Friday, 19 APRIL, 1985**

Name .....


Address .....

Post to: Crotech Instruments Ltd., 2 Stephenson Road, St. Ives, Huntingdon, Cambridgeshire, PE17 4WJ.
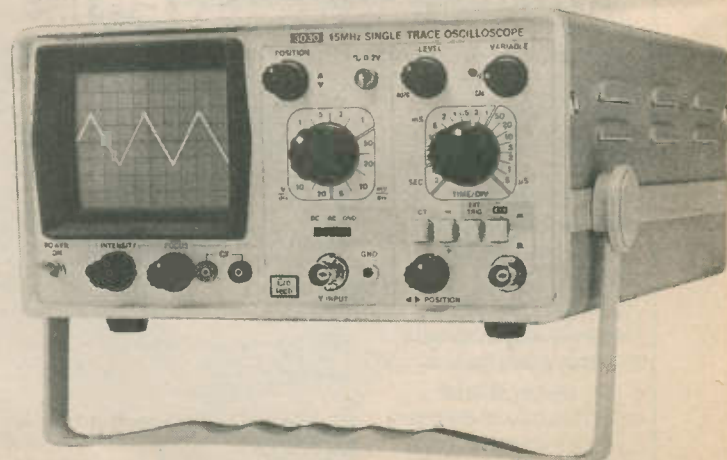
## Crotech Type 3030 Single Trace 15MHz £183


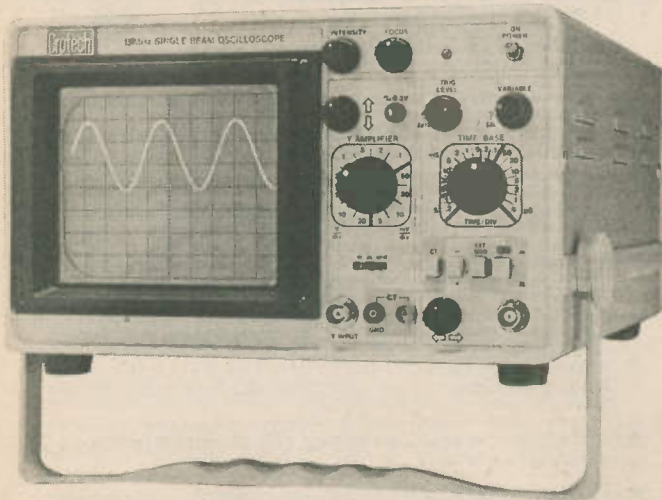
# Crotech Type 3035 Single Trace 15MHz £199



- ★ 5mV/division to 20V/division (12 steps) calibrated sensitivity ( $\pm 3\%$ )
- ★ DC-15MHz bandwidth (-3dB). Rise time 23ns.
- ★ X-Y operation
- ★ 130mm cathode ray tube
- ★ 200ns/division to 0.2s/division (18 steps) timebase ( $\pm 5\%$ )
- ★ 6 trigger functions
- ★ Triggering to 20MHz
- ★ 10 x 8 division display
- ★ Component tester
- ★ Measures 160H x 265W x 317D (mm), weight 6kg (approx.)

**PRICES INCLUDE  
VAT AND DELIVERY**

- ★ 5mV/division to 20V/division (12 steps) calibrated sensitivity ( $\pm 3\%$ )
- ★ DC-15MHz bandwidth (-3dB). Rise time 23ns.
- ★ X-Y operation
- ★ 95mm rectangular cathode ray tube
- ★ 200ns/division to 0.2s/division (18 steps) timebase ( $\pm 5\%$ )
- ★ 6 trigger functions
- ★ Triggering to 20MHz
- ★ 10 x 8 division display
- ★ Component tester
- ★ Measures 125H x 240W x 335D (mm), weight 4.6kg (approx.)

PRACTICAL ELECTRONICS is pleased to be able to offer these quality CROTECH oscilloscopes to readers at special discount prices which include VAT and delivery. The 'scopes can be purchased using Access to spread the load.

Any of these three items would be an invaluable addition to the test gear used by an amateur or professional engineer. Each unit is supplied with an input lead, instruction manual and a free copy of "Getting The Best From Your Scope". Additional probes and accessories are also available.

The 'scopes have the additional facility of a built-in component comparator or tester which allows in-circuit testing of both passive and active devices and, on the 3132 direct comparison of components. Each 'scope employs regulated internal supplies and features a 1KHz, 200mV P-P calibration output.

THESE CROTECH PRODUCTS ARE ALL COVERED BY A TWELVE MONTH GUARANTEE.


Unfortunately we can only make this offer to UK readers due to delivery problems overseas.

## EVERYDAY ELECTRONICS and computer PROJECTS

MARCH 1985 ISSUE ON SALE FRIDAY, FEBRUARY 15

### HEADLIGHT ACTIVATED SWITCH

## MONITORS... Buyer's Guide

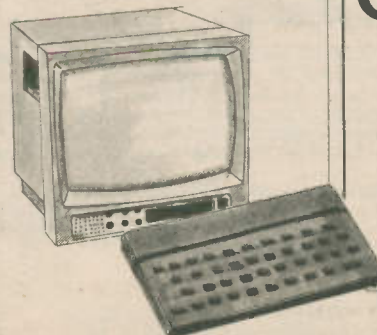

### On Spec...

This new regular feature will be of particular interest to Spectrum owners. Each month, a different aspect of the machine will be examined, including software, interfacing, and hardware add-ons.

# THE NEW MPF1-65



(6502 Microprocessor)

## ■ Professional Documentation ..... All the Instruction You Need.

In being a total learning tool, the MPF-1/65 supports the user with clear, operating documentation. Both the User's Manual and Monitor Program Source Listing Manual are written with the beginner and professional in mind.

The **User's Manual** includes a complete introduction to the features and capabilities of the system. Detailed descriptions of both hardware and software.

The **Source Code Listing Manual** provides complete listings of the monitor software. For the programmer and learner, this provides insight into all the capabilities and functions of the complete system.

## Technical Specification

■ **ADVANCED INTERACTIVE MONITOR:** The heart of the MPF-1/65 software resides in 16K bytes of permanent memory (ROM) located on board. The monitor is designed to provide a user friendly interface by presenting language that the microprocessor understands in an easily understood format. Self prompting single key commands also provide an easy yet powerful means of input. These features provide for the most effective means of understanding the real way in which a microprocessor operates.

The MPF-1/65 monitor includes a wide range of powerful features that offer user convenience, easy-to-learn commands and powerful programming capabilities. These include the screen editor, disassembler, text editor, two pass assembler, printer driver routines and special debugging commands.

**FLIGHT**  
Electronics Ltd.

Quayside Rd, Southampton,  
Hants SO2 4AD.  
Tel. (0703) 34003/27721. Telex 477793.

■ **DISASSEMBLER:** The built-in disassembler allows the user to list 6502 microprocessor instructions on both printer and video display. The disassembled data, in mnemonic symbols, translates the complex machine language of the microprocessor into symbolic form with 3 letter abbreviations. Understanding of low level operations provides learners with a comprehensive understanding of the 6502.

■ **SCREEN EDITOR:** The screen editor allows for rapid alteration of data displayed on the video output console. Commands previously entered onto the screen can be verified, monitored and changed accordingly. With word processor-like functions, the screen editor is an attractive feature for programmers and industry alike.

■ **MPF-1/65 MONITOR INDUSTRIAL COMMAND SUMMARY:** The commands of the system monitor allow for single key programming convenience. Such software includes the following features:

- Display/Alter of selected memory contents
- Move/Verify of a block of memory contents
- Display/Alter Registers
- Select display page/mode
- Mnemonic form listing of instructions
- Single key program execution
- Read/Write data to or from cassette tape
- Easy printer select for hard copy results

■ **TEXT EDITOR:** The text editor provides the power of changing, adding, or deleting instructions anywhere in the program without affecting any other portions of the program. The text editor's simple commands may be displayed on video output or in hard copy form. Source code in the machine's editing buffer can be efficiently translated into machine code for faster operation. The text editor also combines with other features to provide a powerful debugging tool.

■ **TWO PASS ASSEMBLER:** The two pass symbolic assembler provides 6502 programmers with the ability to write extremely efficient programs for applications requiring fast execution speed. OEMs and professionals can more efficiently develop complex programs. Students of the 6502 can use the functions of the two pass assembler to grasp the fundamentals of microprocessor programming.

■ **PRINTER DRIVER:** The printer driver resident in ROM provides software drive interface with Epson printers.

■ **DEBUGGING FEATURES:** The MPF-1/65 also packs features that provide software for programming simplicity and efficiency via strong debugging functions. These include:

- Setting, clearing and displaying breakpoints
- Single step program execution on printer or display
- Tracing of one instruction
- Displaying register contents

### MEMORY

- **USER MEMORY:** 64K dynamic RAM
- **PERMANENT MEMORY:** 16K of ROM stored in two 8K by 8-bit chips
- **DISPLAY MODES:** TEXT: Two pages of 40 × 24 text
- **GRAPHICS:** Bit mapped graphics in six colours controlled by machine code instructions.

### INPUTS AND OUTPUTS

- **AUDIO SPEAKER:** 2.25 inch 8 ohm speaker.
- **AUDIO CASSETTE INTERFACE:** 1000 bit per second data transfer from memory to cassette tape
- **PARALLEL PRINTER INTERFACE:** With Centronics printer interface and EPSON software driver.
- **COLOUR TV INTERFACE:** R/F-modulator with video and sound output provides for colour TV interface.
- **SYSTEM EXPANSION CONNECTOR:** 50 pin connector to provide interface with RS-232c or ROM cartridges.
- **KEYBOARD:** Standard QWERTY 49 key keyboard with 153 ASCII codes.
- **232-MPF-1/65 CARTRIDGE:** The optional RS-232c cartridge provides for an industry standard asynchronous serial communications capability.

Send for the latest catalogue Now!

See the latest systems and accessories; Single Board Computers with Z80, 6502 and the latest 8088-16 bit microprocessor.

Name \_\_\_\_\_

Address \_\_\_\_\_

Signature \_\_\_\_\_

Date \_\_\_\_\_

**Multitech**

See us at the Microprocessor Development  
Show - Wembley Conference Centre,  
12th - 14th February 1985.



# Low Cost BBC Speech Synthesiser

Anthony Foord

A number of designs have been published in the electronics press for speech synthesis units, either intended specifically for the BBC Computer or more widely compatible. They are generally connected to the parallel printer or user port. This ties up one port and takes up valuable desk space.

A much neater solution is provided by Acorn themselves. Their system consists basically of two integrated circuits for which provision has been made on the main p.c.b. The computer's internal speaker and amplifier are used and the operating system takes care of the interfacing requirements.

On consideration however, the Acorn unit does appear to have two drawbacks; firstly, it is preprogrammed, giving only a limited selection of words and, secondly, it retails at over £50.

The design presented here uses the popular General Instruments Speech Processor to give a virtually unlimited vocabulary. If constructed as described it may simply be plugged into one of the sockets inside the computer; no track cutting or other modifications are necessary. It is compatible with the operating system, and retains the other advantages offered by Acorn's system (but will not, of course, produce intelligible speech with software written for the Acorn Unit). As a bonus, two different volume levels can be selected under program control and the total cost should not be more than about £15.

## SYNTHESIS

There are several possible techniques for the production of artificial speech. One method is to record the required phrase in digital form and then play it back—hardly synthesis really. With adequate data rates this can sound extremely good (compact discs are an example). Acceptable quality can only be achieved at the cost of large amounts of memory, making this approach somewhat inflexible. At the other extreme, electronic analogues of the human vocal tract have been built. These consist of a number of filters, an oscillator and a noise source, all controlled from the computer.

At the present time the systems in widespread use fall into one of two classes. Either information describing complete words is stored (in a compacted form to reduce memory requirements); or, a collection of basic sounds, known as ALLOPHONES, are used, which may be strung together to form any desired word.

The latter approach is inherently more versatile, and it is this method which is used in the General Instruments SP-0256 i.c. The attendant disadvantage is that whereas human beings can subtly adjust the individual allophones, depending on the neighbouring sounds, to produce smoothly connected speech, electronics (as yet) cannot. Both methods are capable of adequate (though rather mechanical sounding) results.

The SP-0256 can produce 59 separate sounds (and five pauses of varying lengths) which enable English words to be built up. It should be noted that both the SP-0256 and the Texas Instruments TMS5220, used by Acorn, have digital, Pulse Width Modulated outputs. This takes the form of a series of pulses at a frequency of several kHz. Varying the width of the pulses alters the mean output voltage and this average level is recovered by low-pass filtering to give an audio signal.

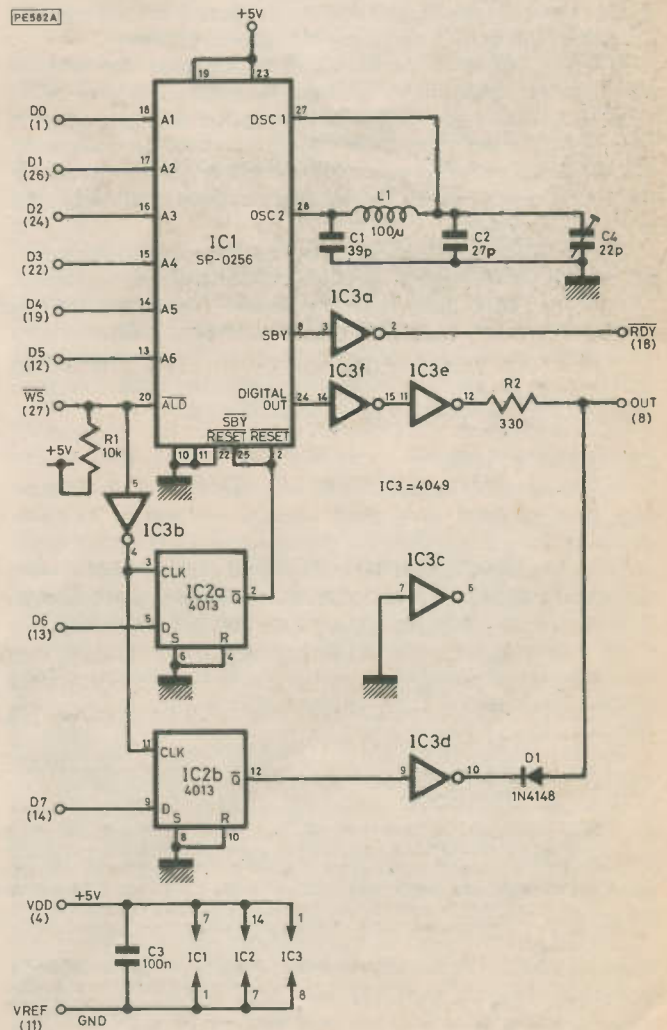


Fig. 1. Circuit diagram of the Special Synthesiser

## CIRCUIT DESCRIPTION

The heart of this circuit, like many others, is the SP-0256 i.c. This device is responsible for the actual speech synthesis. The remainder of the circuitry is required to allow it to replace a TMS5220, and to provide two switched volume levels. The circuit diagram is shown in Fig. 1.

All the necessary filtering and amplification is performed by components already present in the computer. The SP-0256 accepts a six bit binary input which corresponds to one of sixty four possible output sounds (including the five which are silent). This is taken from lines D0 to D5, and is stored in internal latches on receipt of an active-low  $\overline{WS}$  pulse. The remaining data lines, D6 and D7 are latched by the 4013 dual D-type flip-flop. Inverter IC3b is included as the 4013 expects an active-high clock signal. D6 is taken high by the computer as part of the procedure to reset the TMS5220, and so is used (in inverted form) to reset the SP-0256. This ensures that the unit remains silent on power-up and BREAK. D7 is used to select between volume levels. Both the output of the SP-0256 and that of the 4013 are buffered by inverters. If D7 is a logical '1', then the cathode of D1 is taken to +5V. It thus has no effect on circuit operation and full volume results. A logical '0' causes the cathode to be taken to ground and the diode clamps the voltage excursion at the output, reducing the volume obtained.

The SBY output of the SP-0256, which goes high when it has finished speaking or is reset, is inverted to give  $\overline{RDY}$ . This is an active-low signal informing the computer that it may send the next data byte. Using the active-low output of the SP-0256 would prevent the computer from successfully executing a reset operation as this too goes high, inhibiting the transfer of data.

L1, C1, C2 and C4 are frequency determining components for the SP-0256 internal oscillator. C4 enables some adjustment of the vocal pitch to be made, and it is worthwhile trying the effect of different settings. Increasing frequency also makes the computer talk slightly faster. Finally, note that a 4049 must be used. A 4069 has a reduced output capability, and may be too slow for this application.

## CONSTRUCTION


The method of construction adopted for the prototype (see photographs) is slightly unusual in that it involves soldering the p.c.b. directly to the d.i.l. header at right angles.

This is recommended as it results in a single, rigid, self-supporting assembly and cuts down on off-board wiring. However, it is perfectly possible to use the more conventional length of ribbon cable, and even to build the circuit on matrix board. If you make your own p.c.b. from the layout given, be sure to cut it to the size shown. There is very little clearance inside the BBC Computer.

The first step is to mount all the components on the p.c.b., not forgetting the eight wire links. IC1 is a relatively expensive MOS device and should certainly be socketed. It is probably worth using sockets for the other i.c.s. as this will save a great deal of trouble if any problems occur. Soldering calls for some care as several tracks run very close to each other.

The 28 pin headers used to be hard to find, although this seems no longer to be the case. An alternative is to chop up a 40 pin header. Anything else is definitely not a good idea—sticking bits of wire in may damage the BBC's socket. The next step then is to glue the p.c.b. to the header.

First tin the tracks where they are to be soldered to the header. The p.c.b. should be placed so that it is between the

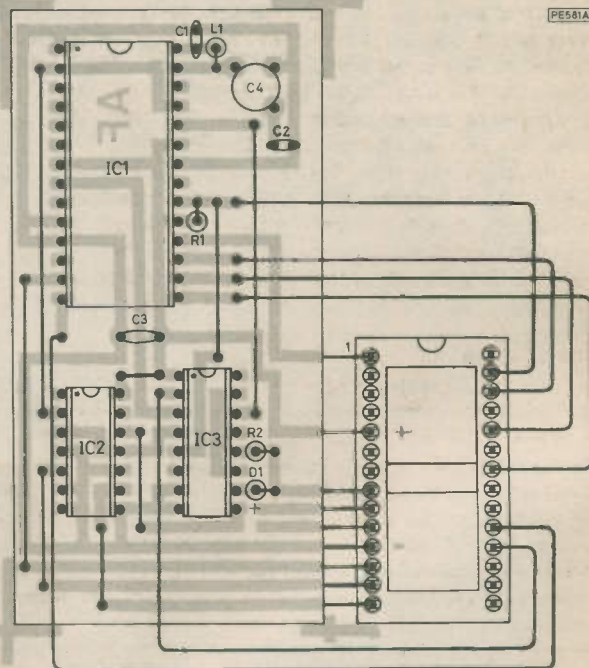

**Fig. 2. P.c.b. and component layout of the Speech Synthesiser**

two rows of pins and so that the tracks line up with the pins. A bracket is needed to hold it in this position. For the prototype a length of  $\frac{1}{4}$ " plastic channel which is generally available at modelling shops, was used, but a similarly sized strip of wood could be employed. With the p.c.b. located as shown in the photo and pressed against the header pins, glue the bracket to both it and the header, using a quick setting epoxy resin compound. This is the only tricky part. When this has set the six flying leads may be wired from the p.c.b. to the header, as shown in Fig. 2.

On the prototype it proved necessary to slightly file down one edge of the header to clear a capacitor in the computer.

## COMPONENTS ...

### Resistors

R1 10k  
R2 330  
All resistors  $\pm 5\%$   $\frac{1}{4}$ W carbon

### Capacitors

C1 39p metallised ceramic plate  
C2 27p metallised ceramic plate  
C3 100n disc ceramic  
C4 22p miniature trimmer

### Inductors

L1 100 $\mu$

### Semiconductors

D1 1N4148  
IC1 SP-0256  
IC2 4013  
IC3 4049

See our p.c.b. service on Page 60

### Miscellaneous

p.c.b. 503-05  
28 pin i.c. socket  
14 pin i.c. socket  
16 pin i.c. socket  
28 pin d.i.l. header  
 $\frac{1}{4}$ " plastic angle

## INSTALLATION

Fitting the unit is very straightforward. The top of the computer is secured by four screws. These are situated one either side at the back and underneath at the front.

All further directions assume the computer is viewed from the normal position, i.e. the keyboard is in front. Thus the power supply lies to the left. The speech processor socket (labelled IC 99) is the righthand of the two adjacent 28 pin sockets by the p.s.u. With the computer switched off, the speech synthesiser should be plugged in so that the p.c.b. is on the left side and extends towards the back. This can be seen in the photographs. Care should be taken to ensure that all the pins are correctly sited and pressed fully home.

The sound quality will be dramatically improved if the top is put back on the computer, although it would perhaps be tempting fate to replace the screws before testing the system!

## OPERATION

To send a byte to the speech synthesiser, use is made of the BBC Microcomputer's OSBYTE call (CALL &FFF4). This is entered with A% set to the parameter to be passed. An illustration of this is given by PROCspeak in the demonstration program. The program allows ten words to be defined and spoken. It was developed on a computer fitted with OS-1.2. To keep it as short as possible few REM statements have been included, but it should be quite self explanatory. PROCspeak expects data to be stored as character strings,

Allo- phone No.	+128	Example	Allo- phone No.	+128	Example
0	128	10mS	32	160	shOUt
1	129	30mS	33	161	Dot
2	130	50mS	34	162	Got
3	131	100mS	35	163	liVing
4	132	200mS	36	164	Gear
5	133	tOY	37	165	SHoe
6	134	tIE	38	166	meaSURE
7	135	pEt	39	167	tRap
8	136	Cone	40	168	Fat
9	137	Pet	41	169	taCK
10	138	roGer	42	170	Cat
11	139	tiN	43	171	Zap
12	140	tIn	44	172	kiNg
13	141	Tin	45	173	Lit
14	142	Rat	46	174	Wet
15	143	dUck	47	175	AIR
16	144	Mix	48	176	WHy
17	145	peT	49	177	Yet
18	146	THat	50	178	CHip
19	147	tEA	51	179	sIR
20	148	pAY	52	180	tURn
21	149	founD	53	181	gO
22	150	tUtor	54	182	oTHer
23	151	tAlk	55	183	Sit
24	152	tOp	56	184	Not
25	153	YEt	57	185	Hook
26	154	cAt	58	186	OR
27	155	Hit	59	187	pARt
28	156	haBit	60	188	EAR
29	157	THick	61	189	Go
30	158	hOOK	62	190	paddLE
31	159	mOOn	63	191	Bat

Table 1. Complete list of available allophones

Word	Allophones
B.B.C.	63 19 2 63 19 2 55 55 19
Computer	42 23 16 9 49 22 13 51
Exterminate	7 42 55 17 51 16 12 11 20 17
Peter	9 19 13 51
Piper	9 6 9 51
Picked	9 12 41 17
A	15
Peck	9 7 41
Of	23 40
Pickled	9 12 41 62 17
Pepper	9 7 9 51
E.T.	19 2 13 19
Phone	40 53 11
Home	57 53 16


Table 2. Some (appropriate) examples of word construction

other solutions are possible, such as integer arrays.

The numbers recognised by the speech synthesiser are listed in Table 1, together with their corresponding sounds. Values in the range 0 to 63 will cause the allophones to be spoken quietly, while those in the range 128 to 191 will result in the same allophones being spoken with greater volume. Numbers between 64 and 127 or 192 and 255 inclusive will turn the unit off, as will the BREAK key.

Table 2 contains some examples. Constructing words becomes very easy with a little practice. It is important to think of them as strings of sounds and to pay no attention to spelling. There are several very similar allophones, and the best result may only be obtained through trial and error. Not all the sounds are equally good, the 'TH's seem particularly bad, and here substitution of another allophone is often worthwhile. The short vowels such as 'E' (No. 7) and the 'S' and 'F' sounds can be used twice in succession to stress a syllable. It is also possible to place short pauses in words to good effect. A 50ms pause is about right between words in a phrase, and a longer pause between phrases. It is important to end with a pause or the last allophone will continue to sound. This is taken care of in PROCspeak.

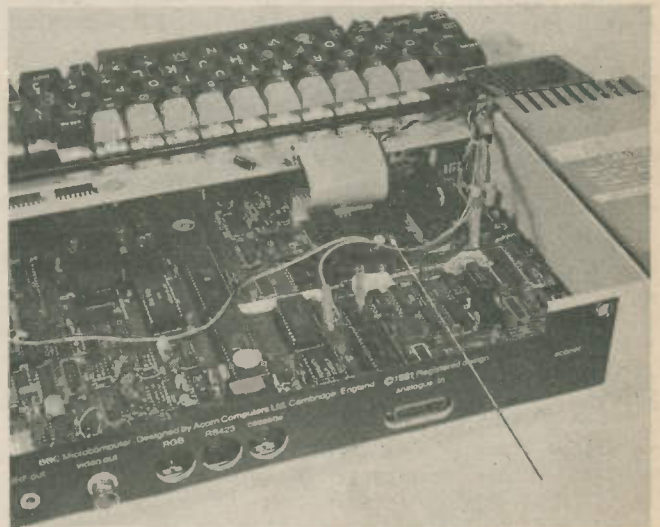There are algorithms which convert written text to allophones and one of these might be implemented. Obviously they cannot be perfect in a language which allows "cough" and "rough", and pronounces "lead" differently in




Photograph illustrating the position of the 28 pin socket (IC99) for the Speech Synthesiser

different contexts, but with judicious misspelling they are a big help, and often incorporate a dictionary of such exceptions. In addition to speech, some fascinating sound effects are possible, try a string of 'i's or 'p's or random allophones.

Like most speech synthesizers, it is much easier to understand if you are used to it and know what is being said.

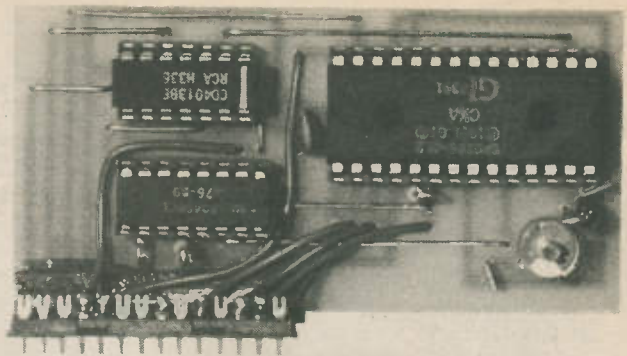Apart from its obvious applications for the blind and situations where you cannot watch a television screen, it is hard to suggest a compelling reason to build it, although there is great scope for experimentation with speaking alarm clocks etc. But, it is one of the cheapest computer peripherals available, and most people still find a speaking machine surprisingly impressive. ★



## DEMONSTRATION PROGRAM

```

10 MODE 7
20 DIM name$(9)
30 DIM allophone$(9)
40 PRINT TAB(6,2); "SPEECH DEMONSTRATION
PROGRAM"
50 PRINT TAB(6,3); "=====
=====
60 REM title$ IS ALLOPHONE STRING FOR TITLE
70 title$="7IS2C! GPXK7MgT%XKClg5=gZP"
80 PROCspeak(title$,1)
90 REM SET UP USER DEFINED KEYS
100 *FX225,128
110 *FX226,138
120 FOR index%=0 TO 9
130 allophone$(index%)=CHR$(0)
140 PROCmenu(index%)
150 NEXT
160 speakmode=FALSE
170 REPEAT
180 IF speakmode THEN PROCgetword ELSE PROCupdate
190 UNTIL FALSE
200 END
210 REM PROCupdate ALLOWS MENU TO BE ALTERED
220 DEF PROCupdate
230 PRINT TAB(2,23); "Type 'S' for Speech mode."
240 INPUT TAB(2,17); "WORD NUMBER (0-9)"; reply $
250 PROCwipe(17)
260 PROCwipe(23)
270 IF reply$="S" THEN speakmode=TRUE: ENDPROC
280 index%=VAL(reply$)
290 IF index%>9 THEN 240
300 PRINT TAB(2,19); name$(index%)
310 PRINT TAB(2,20);
320 FOR count%=1 TO LEN(allophone$(index%))
330 PRINT;ASC(MID$(allophone$(index%),count%,1));" ";
340 NEXT
350 PRINT TAB(2,23); "Press (RETURN) to continue
360 INPUT TAB(2,17); "WORD NAME ";reply$
370 IF reply$<> "" THEN name$(index%)=reply$
380 PROCwipe(17)
390 PROCwipe(23)
400 word$=""
410 REPEAT
420 PRINT TAB(2,23); "Press (RETURN) to continue."
430 INPUT TAB(2,17); "ALLOPHONE NUMBER
(0-63) "; reply $
440 PROCwipe(17)
450 IF reply$<> "" AND VAL(reply$)> -1
AND VAL(reply$)<64 THEN
word$=WORDS$+CHR$(VAL(reply$))
460 UNTIL reply$=""
470 IF word$<> "" THEN allophone$(index%)=word$
480 PROCmenu(index%)
490 PROCspeak(allophone$(index%),0)
500 FOR count%=19 TO 23
510 PROCwipe(count%)
520 NEXT
530 ENDPROC
540 REM PROCgetword GETS WORD FROM MENU
CORRESPONDING TO KEY PRESSED
550 DEF PROCgetword
560 PRINT TAB(2,23); "Type 'A' to Alter menu."
570 PRINT TAB(2,17); "{SHIFT) to raise volume.f0-f9 ?";
580 reply$=GET$
590 IF reply$="A" THEN speakmode=FALSE
:PROCwipe(17):PROCwipe(23):ENDPROC
600 index%=ASC(reply$)-128
610 If index%<0 OR index%>19 THEN 580
620 If index%>9 THEN loud=TRUE:index%=index%-10:
ELSE loud=FALSE
630 PROCspeak(allophone$(index%),loud)
640 ENDPROC
650 REM PROCmenu PRINTS ONE LINE OF MENU
SELECTED BY index%
660 DEF PROCmenu(index%)
670 PROCwipe(index%+6)
680 PRINT TAB(2,index%+6);index%
690 PRINT TAB(6,index%+6);name$(index%)
700 ENDPROC
710 REM PROCwipe ERASES ONE LINE SPECIFIED
BY Y%
720 DEF PROCwipe(Y%)
730 PRINT TAB(0,Y%);SPC(40);
740 ENDPROC
750 REM PROCspeak OUTPUTS STRING TO SPEECH
SYNTH
760 DEF PROCspeak(word$,loud)
770 IF loud THEN offset=128 ELSE offset=0
780 A%=159
790 FOR count%=1 TO LEN(word$)
800 Y%=(ASC(MID$(word$,count%,1)) AND &3F)+offset
810 CALL &FFF4
820 NEXT
830 Y%=offset
840 CALL &FFF4
850 ENDPROC


```

**8  
EXTRA  
PAGES**

all in your

**APRIL**

issue!

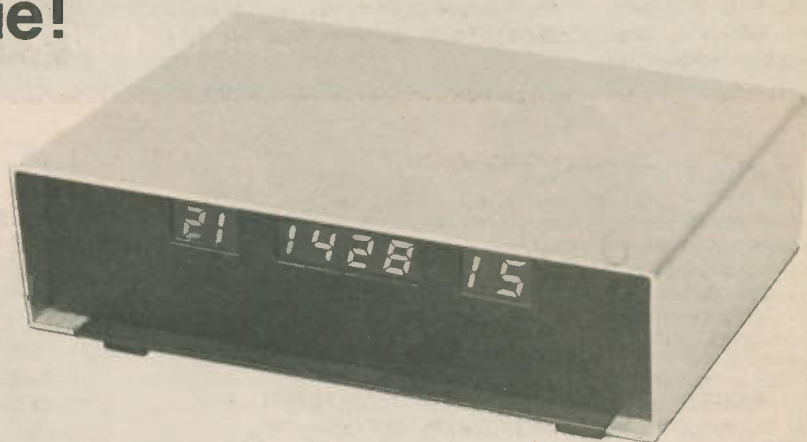

# RUGBY CLOCK

A standard time signal is transmitted from Rugby containing information about the time, date and year. This project will enable you to decode the time signal and produce a digital display of the date, hours, minutes and seconds. A further option will allow you to decode the actual day as well as the date.

## *Power Control Interface*

Another useful add-on for any computer with an 8-bit output port. The Power Controller Interface is capable of proportional a.c. power control with complete isolation at up to 10 amps. Designed to control heater elements, it may be used for many power applications.



A wide range of the currently available printers for computer systems are featured in this buyer's guide together with an explanation of specifications.

**PRACTICAL**

# **ELECTRONICS**

**ROBOTICS · MICROS · ELECTRONICS · INTERFACING**

**APRIL 1985 ISSUE ON SALE FRIDAY, MARCH 1**

# BBC Micro Forum...

David Whitfield MA MSc CEng MIEE

WELCOME to *BBC Forum*, P.E.'s new monthly page devoted to the BBC Micro. You may be wondering why we are intending to devote a whole page, every month, to this machine. After all this is an electronics magazine, and such columns have a habit of being full of software listings of interest only to an eccentric minority; no fit subject for a soldering iron user. Have no fear, the emphasis will be on *practical* applications of electronics to computers, and not computing for computing's sake. In this first column, therefore, we would like to take a little time to explain our approach to the subject. Incidentally, Sinclair owners may be interested to hear that our sister publication, *Everyday Electronics*, will be running a similar series aimed at the Spectrum.

Over 370,000 BBC Micros have been sold since the machines first became available in early 1982. It boasts a performance which still compares favourably with its most recent competitors, it's well equipped, widely used in schools, there's plenty of software available for it, and it can be used at the heart of all sorts of systems. Price is the BBC Micro's major drawback, but this does not prevent it from having a wide and enthusiastic following. I must confess to being a convert to the cause myself.

So much for the potted biography of the machine, but what about the reality of owning a computer? We are constantly told that computers will revolutionise our lives, but for many people 'home computer' is just another word for 'games machine'. At the next level, we see users moving on from proprietary software to writing their own, usually in BASIC. Equally, the trend is away from games to applications which actually set the machine to work, e.g. word processing. As our understanding of the machine increases, the more directly we are able to apply the power at our disposal, e.g. central heating control. To make this final step, however, we usually need to move away from BASIC, and look at the hardware of the computer itself. In this way we can add hardware to the computer to control our own peripherals such as lamps and valves, rather than the more traditional printers and cassettes already catered for. This is the objective of this column!

The projects and techniques that we will be looking at will not involve opening up the micro, and will only connect to the interfaces supplied as standard on the model B. However, even if you do not have a BBC Micro, many of the projects will be readily adaptable for many other machines, particularly those with a 6502 microprocessor such as the Commodore 64 and Apple IIe.

## INTERFACES

The BBC Micro is particularly well endowed with interfaces. Even if not actually fitted with a particular interface when delivered, the main circuit board, case and power supply are all designed to take all of the interfaces *without* the need for external add-on boxes or adaptor modules. In this way, any BBC Micro can be upgraded to the full specification if required. The interfaces which can be supported are as follows:

- Cassette Interface
- RS423 Port
- Analogue Input Port
- Light Pen Input
- RGB Monitor
- UHF Television
- Composite Video
- Parallel Printer Port
- Floppy Disc Interface
- User Input/Output Port
- 1MHz Bus Interface
- Processor Bus Interface
- Econet Interface
- Speech Synthesiser
- Paged ROMs

The model B is supplied with all of these fitted except the floppy disc interface, Econet and speech synthesiser. With the now discontinued Model A 16k RAM is fitted, and the interfaces are limited to UHF television, composite video and the cassette port. The BBC Micro can thus reasonably be described as having enough I/O facilities to be going on with! Indeed, the problem is a little more like being spoilt for choice. Over the next few months, therefore, we will be exploring these interfaces, their strengths and weaknesses.

Wherever possible, we will be including a brief discussion of the internal hardware which supports the interfaces.

## USER PORT

We start this month with a look at the user input/output port. Next month we will be describing this port and its uses in greater detail, but for the moment we will start by looking at its connections. The user port is the centre one of the five connectors located on the underside of the keyboard. As shown in Fig. 1, the port has eight input/output lines and two control lines. The 20-pin user port connector requires a mating insulation displacement cable mounting socket and ribbon cable for connection to the outside world. These are available, either separately or made up as leads, from a number of advertiser's in P.E. The RS part number of a suitable connector is 469-881, and of corresponding 20-way ribbon cable is 357-867. **NEXT MONTH:** Using the I/O Port. ★

## FINALLY

I would be delighted to hear from readers with suggestions, hints for inclusion or problems, but would like to stress that any reply will only be through this column. Correspondence should be addressed to 'BBC Forum Letters', at P.E.'s editorial address.

Anyone considering purchasing a BBC microcomputer can obtain pre-sale advice from a number of sources, including: *BBC Microcomputer System, PO Box 7, London W3 6XJ* (send a large SAE).


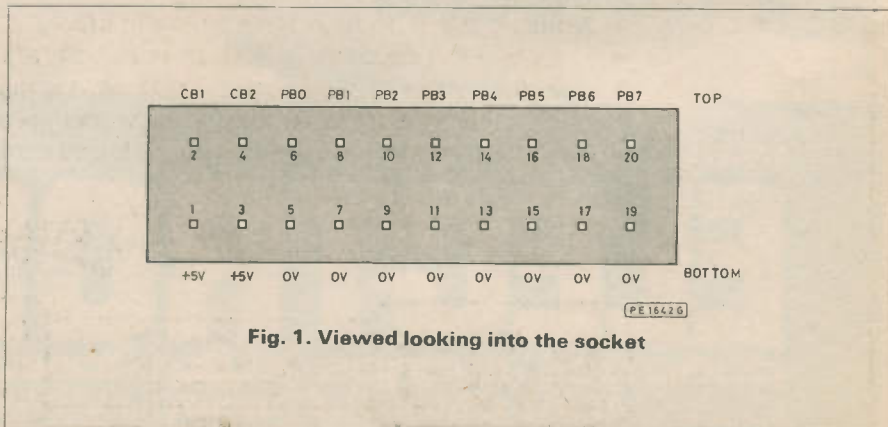


Fig. 1. Viewed looking into the socket
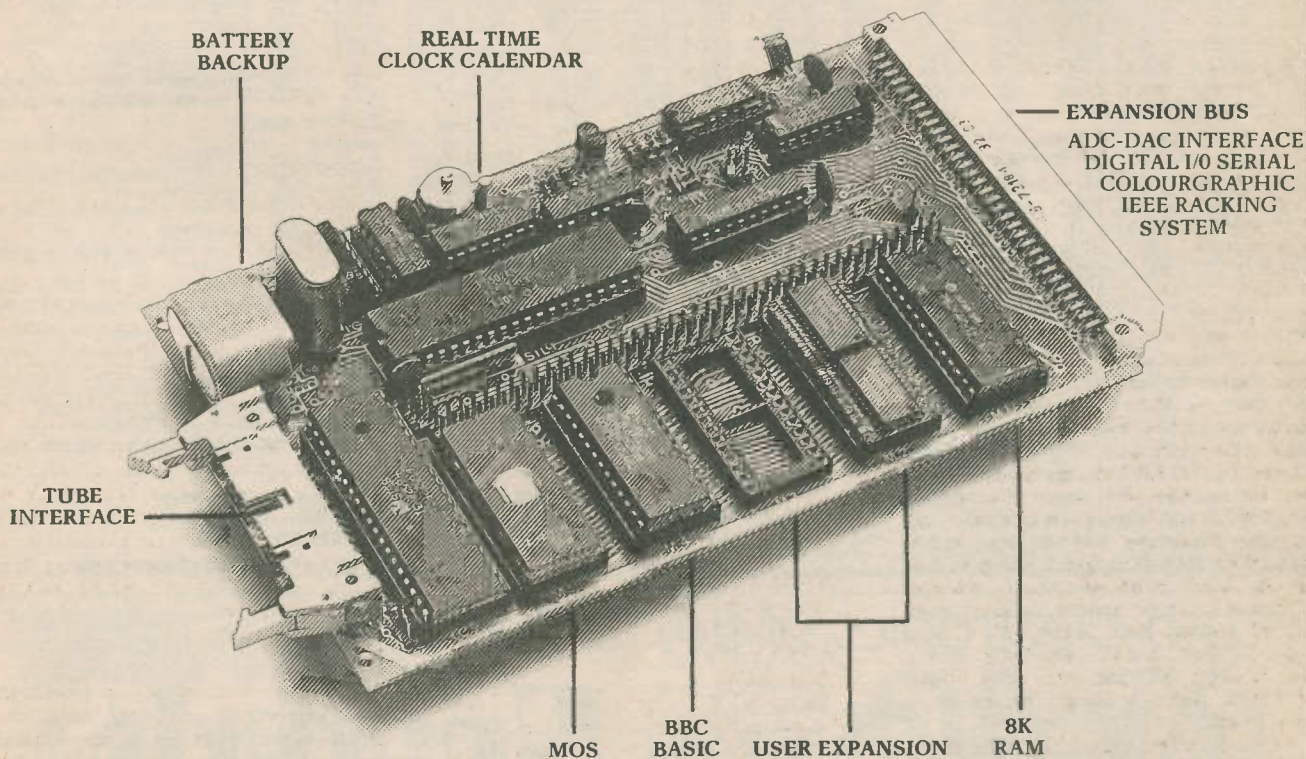
# PUT BBC BASIC IN CONTROL USE THE 6502 2ND PROCESSOR WITH BIG CONNECTIONS



- Single Eurocard – can stand alone and run BBC BASIC programs.
- Program your control applications in BBC BASIC . . . . .  
. . . . . FORTH, PASCAL or any other language ROM.
- Adds I/O expansion to your BBC via the 6502 bus connector.
- Tube Interface for fast development.
- Battery backed up Real Time calendar clock.
- Runs BASIC programs in ROM or from battery backed up RAM.
- Complete set of software utility modules available in ROM.
- A full range of Eurocards for use in target applications.
- Ideal for industry, education, research and commerce.

*Move over to CMS today*



44a Hobson Street  
Cambridge CB1 1NL  
(0223) 324141


Cambridge  
Microprocessor  
Systems Limited


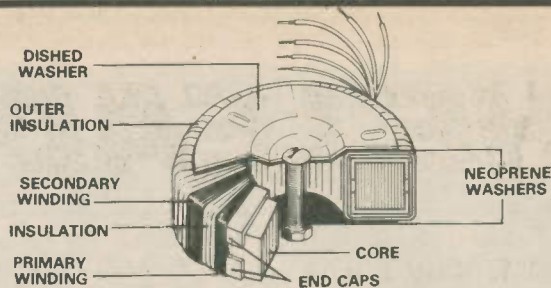
# TOROIDALS

The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroidals offer in size, weight, lower radiated field and, thank to I.L.P., PRICE.

Our large standard range is complemented by our SPECIAL DESIGN section which can offer a prototype service within 14 DAYS together with a short lead time on quantity orders which can be programmed to your requirements with no price penalty.



15 VA			50 VA			120 VA			225 VA			500 VA		
62 x 34mm			80 x 35mm			90 x 40mm			110 x 45mm			140 x 60mm		
Regulation 19%			Regulation 13%			Regulation 11%			Regulation 7%			Regulation 4%		
SERIES No.	SECONDARY Volts	RMS Current	2x010	6+6	4.16	4x010	6+6	10.00	6x012	12+12	9.38	8x016	25+25	10.00
0x010	6+6	1.25	2x011	9+9	2.77	4x011	9+9	6.66	6x013	15+15	7.50	8x017	30+30	8.33
0x011	9+9	0.83	2x012	12+12	2.08	4x012	12+12	5.00	6x014	18+18	6.25	8x018	35+35	7.14
0x012	12+12	0.63	2x013	15+15	1.66	4x013	15+15	4.00	6x015	22+22	5.11	8x026	40+40	6.25
0x013	15+15	0.50	2x014	18+18	1.38	4x014	18+18	3.33	6x016	25+25	4.50	8x025	45+45	5.55
0x014	18+18	0.42	2x015	22+22	1.33	4x015	22+22	2.72	6x017	30+30	3.75	8x033	50+50	5.00
0x015	22+22	0.34	2x016	25+25	1.00	4x016	25+25	2.40	6x018	35+35	3.21	8x042	55+55	4.54
0x016	25+25	0.30	2x017	30+30	0.83	4x017	30+30	2.00	6x026	40+40	2.81	8x028	110	4.54
0x017	30+30	0.25	2x028	110	0.45	4x018	35+35	1.71	6x025	45+45	2.50	8x029	220	2.27
			2x029	220	0.22	4x028	110	1.09	6x033	50+50	2.25	8x030	240	2.08
			2x030	240	0.20	4x029	220	0.54	6x028	110	2.04			
						4x030	240	0.50	6x029	220	1.02			
									6x030	240	0.93			

30 VA			80 VA			160 VA			300 VA			625 VA		
70 x 30mm			90 x 30mm			110 x 40mm			110 x 50mm			140 x 75mm		
Regulation 18%			Regulation 12%			Regulation 8%			Regulation 6%			Regulation 4%		
SERIES No.	SECONDARY Volts	RMS Current	3x010	6+6	6.64	5x011	9+9	8.89	7x013	15+15	10.00	9x017	30+30	10.41
1x010	6+6	2.50	3x011	9+9	4.44	5x012	12+12	6.66	7x014	18+18	8.33	9x018	35+35	8.92
1x011	9+9	1.66	3x012	12+12	3.33	5x013	15+15	5.33	7x015	22+22	6.82	9x026	40+40	7.81
1x012	12+12	1.25	3x013	15+15	2.66	5x014	18+18	4.44	7x016	25+25	6.00	9x025	45+45	6.94
1x013	15+15	1.00	3x014	18+18	2.22	5x015	22+22	3.63	7x017	30+30	5.00	9x033	50+50	6.25
1x014	18+18	0.83	3x015	22+22	1.81	5x016	25+25	3.20	7x018	35+35	4.28	9x028	110	5.68
1x015	22+22	0.68	3x016	25+25	1.60	5x017	30+30	2.66	7x026	40+40	3.75	9x029	220	2.84
1x016	25+25	0.60	3x017	30+30	1.33	5x018	35+35	2.28	7x025	45+45	3.33	9x030	240	2.60
1x017	30+30	0.50	3x028	110	0.72	5x026	40+40	2.00	7x033	50+50	3.00			
			3x029	220	0.36	5x028	110	1.45	7x028	110	2.72			
			3x030	240	0.33	5x029	220	0.72	7x029	220	1.36			
						5x030	240	0.66	7x030	240	1.25			

- Why a Toroid?**
- Smaller size & weight to meet modern 'slimline' requirements.
  - Low electrically induced noise demanded by compact equipment.
  - High efficiency enabling conservative rating whilst maintaining size advantages.
  - Lower operating temperature.
- Why ILP?**
- Ex-stock delivery for standard 240V range.
  - Fast prototype service available.
  - 3 weeks despatch for special orders.
  - 2 year no quibble guarantee.
  - No price penalty for call-off orders.

**Prices including P&P and VAT**

VA	Size	£	VA	Size	£
15	0	7.06	160	5	12.17
30	1	7.67	225	6	13.75
50	2	8.90	300	7	14.97
80	3	10.65	500	8	19.60
120	4	10.65	625	9	22.30

For 110V primary insert "0" in place of "X" in type number.  
 For 220V primary (Europe) insert "1" in place of "X" in type number.  
 For 240V primary (UK) insert "2" in place of "X" in type number.  
**IMPORTANT:** Regulation - All voltages quoted are FULL LOAD.  
 Please add regulation figure to secondary voltage to obtain off load voltage.

Mail Order - Please make your crossed cheques or postal orders payable to ILP Electronics Ltd.  
 Trade - We will open your credit account immediately upon receipt of your first order.

Post to: ILP Electronics Ltd., Dept. 2  
 Graham Bell House, Roper Close,  
 Canterbury, Kent. CT2 7EP  
 Tel: (0227) 454778 Telex: 965780



## Auto-Electronics of the future.

# AT-40 AT-80 KITS FOR SELF-ASSEMBLY Sparkrite


### ELECTRONIC CAR ALARM & SECURITY SYSTEM

- \* Guard doors, boot and bonnet from unauthorised entry.
  - \* AT-40 - Armed/disarmed using concealed switch.
  - \* AT-80 - Armed/disarmed by magnetic key fob.
  - \* Flashes headlights and sounds horn.
- ### AT-UL ULTRASONIC INTRUDER DETECTOR
- \* Supplementary to AT-40 and AT-80.
  - \* Detects attempted break-in.

Other kits in the SPARKRITE range include:  
 Electronic Ignitions SX1000 (£13.95), SX2000 (£20.95), TX1002 (£24.95) and TX2002 (£37.95).


AT-40 £11.95

AT-UL £17.95

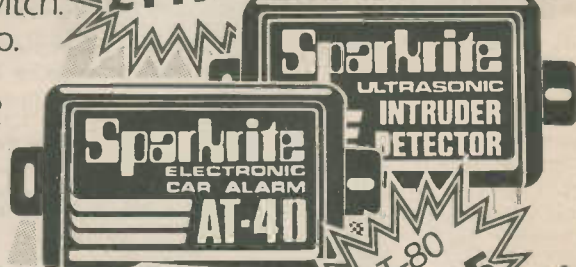

AT-80 £33.45

BRITISH ELECTRONICS

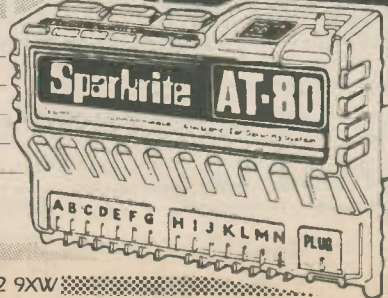

Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 I enclose Postal Order/Cheque/Access/Barclaycard No. \_\_\_\_\_  
 for £ \_\_\_\_\_, Kit Ref. \_\_\_\_\_  
 Prices include VAT, Postage and Packing.  
 Telephone: (0922) 614791. Allow 28 days for delivery.



# THE LEADING EDGE

## BARRY FOX

### COMMERCIAL BREAK

I make no apologies for coming back so soon to cellular radio. In no other area of electronics is so much of such importance happening so fast. By the time you read this, Britain should have its first cellular system. We shall by now be seeing how the Government policy of splitting the service between two rivals works in practice.

To recap very briefly, on the one hand there is TSCR, a joint venture between British Telecom and Securicor which will provide a service called Cellnet. The rival company is Racal which will provide the Vodafone service.

Technically both services are compatible, with transmission on the 900MHz UHF band, and 25kHz channel spacing. The British system TACS (Total Access Communication System) is derived from the American AMPS (Advanced Mobile Phone System) which operates at around 850MHz with 25kHz spacing.

Under the terms of the Government licence given to TSCR and Racal the two services have to be completely separate and running by March. The intention, of course, is to stimulate competition. In fact the situation is made even more competitive, because TSCR and Racal are only allowed to provide a service and sell air time. They cannot sell hardware to end users. This has to be done through retailers and it's where the real commercial battle is being fought.

The cellular service with the best retail backing is the one which will show a profit in the long run. In the short term it won't matter. There is a pent-up demand from people who desperately want a phone in their car or briefcase. They will buy from anyone. But once this pent-up demand has been satisfied, the service will have to be sold with a capital S.

### COMPUTER SWITCH

Racal played a quiet, clever game. While saying little to the press, the company struck a deal with Ericsson of Sweden to provide the computer switch. This is a daunting piece of equipment. It controls all the base stations in a city area, so that as a mobile moves from one cell to another the signal is "handed off" from one transmitter to another with a different frequency for each call.

If you talk to anyone in the armed forces, the odds are they will have heard of Racal. The company makes radio communications and location equipment for the services. So Racal knows about frequency hopping and chose Ericsson for the switch, because the Swedish company also has a big market in the defence sector. Moreover, Ericsson built the switches for the NMT, which is the Nor-

dic Mobile Telephone Service. This provides cellular radio for 120,000 subscribers across Finland, Sweden, Norway and Denmark, on the 450MHz band.

The Ericsson switch has two central processor units, run in synchronism, so that if one goes down the other drops in. The program is stored in a dual memory, of 1.5 megaword capacity. The words are 18 bits; 16 data plus 2 for error correction. The data store, for subscriber numbers and billing information, is of similar 1.5 megaword capacity. The power supply is 48V floating from the mains on batteries. All memories are doubled up for security.

One switch can support around 60,000 subscribers. The first Ericsson switch went to Racal for use in London and the next should by now be installed in Birmingham.

Choosing Ericsson for the switch helped Racal pull in its prize catch, retail support from Pye and Philips. In domino fashion the Pye-Philips liaison helped convince the AA to back Racal and so put the company automatically in touch with its 5.6 million members. These are all potential subscribers to cellular radio, although only a fraction will be able to afford it.

In a careful run-up to launch, Racal has been investing heavily in TV advertising which does nothing more than familiarize the public with the Racal name. Behind the scenes Racal has been talking to journalists in specialized areas, for instance broadcasting, telling them how valuable cellular radio will be to a news team on the run.

The deal with answering machine company Answercall, with Dixons as an outlet, puts Racal in touch with the high street. In fact, few people reckon that cellular radio will be a real consumer item. What is a consumer? "Someone who pays for what they buy out of their own pocket," says Len Davis of Philips, which is just about the best definition I've heard.

### ONE-STOP FITTING SERVICE

Most people who use cellular radio will be spending company money. Dixons will have to organise some sort of "one stop" fitting service, where customers can leave the car in the morning and pick it up at night, with dial tone buzzing. Buying and fitting piecemeal is a potential disaster.

Cleverly, Racal has insisted that all retailers use the service name Vodafone. This should cut through some of the confusion which is bound to arise when two competitive, different but compatible, rival cellular systems hit the market.

### CELLNET UPDATE

At ludicrously short notice TSCR held a press conference to bring us up to date on Cellnet activities. Invitations for a Wednes-

day meet were received through the post on Tuesday. With or without justification TSCR blamed the BT share flotation.

When you get behind some of the PR and management front at Cellnet, the engineering expertise is impressive. TSCR uses Motorola computer switching. Each unit handles around half the number of subscribers handled by the Ericsson switch used by Racal, around 30,000 instead of 60,000.

This will let Cellnet make its service dynamic, that is shrink and change the size of cells, reduce transmission power and change reception and hand-off thresholds to suit special requirements. For example, if every company director with a car or portable phone goes to Wimbledon tennis next summer, the Cellnet service can make more channels available for them by tightening the cells in that area. How will McEnroe react to the sound of phones ringing?

The dynamic approach may make it easier for Cellnet to provide a service for small hand portables rather than fixed car phones or bulky transportable units. These need higher signal strength and smaller cells.

At their last-minute demonstration, Cellnet showed frequency re-use. All demonstrations before that had relied on cells using different frequencies. But, of course, cellular theory relies on different cells in the same area re-using the same frequencies. Cellnet ran two 4 kilometre cells, around 15 kilometres apart, each using the same 10 channels, without mutual interference.

To test signal strength, Cellnet engineers have been driving around Britain for the last year with a Rover car equipped with a magnetometer. This plots its position accurately by reading the Earth's magnetic field. The car also has a signal strength measuring system which logs reception data every three centimetres which the car travels. This lets the engineers try out transmitter sites and see how they cover an area in practice.

### BE WARNED

In America some manufacturers are now selling off Japanese cellular equipment very cheap. It is likely that some of this will find its way into Britain, and will be offered for sale at under the going price of around £1,500 for a mobile transceiver.

Be warned. Unless you buy from an authorised dealer, the transceiver won't work with either the Cellnet or Vodafone system. US frequencies and channel spacings are different. The UK main computers just won't accept any calls unless the subscriber's number is stored into the Cellnet or Vodafone service memory with an OK code.

# MODULAR AUDIO POWER SYSTEM

**PART 2**  
**M. TOOLEY** BA  
**D. WHITFIELD**  
MA MSc CEng MIEE

The dummy load permits testing all of the power amplifier modules and configurations described without the need for adequately rated loudspeakers. A further obvious advantage is that testing can take place without damaging one's eardrums or alienating the neighbours! Unlike the loudspeaker systems which it replaces, the load is small, lightweight and inexpensive.

Although the load is somewhat conservatively rated at 100W continuous r.m.s. output power, it is capable of handling power levels in excess of 200W for short periods. Essentially the load consists of ten parallel connected flameproof ceramic resistors, each rated at 7W. The complete arrangement is immersed in an oil bath which aids cooling, hence raising the maximum total power dissipation.

The load is conveniently housed in a 1lb Golden Syrup tin, the seal between the outer case and lid being perfectly adequate to contain the oil without risk of spillage whilst the outer tin-plate casing provides further effective heatsinking. If desired the case can be painted matt black in order to assist with radiation of heat.

The load is also provided with a simple signal detector which, with the aid of a d.c. meter and the calibration graphs supplied, will enable constructors to ascertain the output power level achieved with a reasonable degree of accuracy.

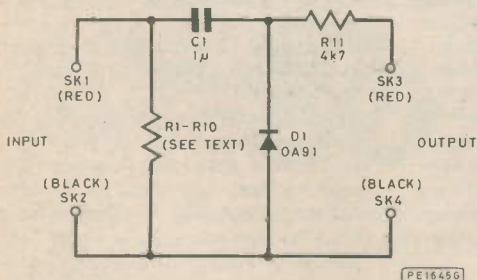


Fig. 2.1. Circuit diagram of the Dummy Load

The circuit of the dummy load is shown in Fig. 2.1 whilst the physical construction is shown in Fig. 2.2. The tin lid is prepared by marking out ten equidistant points on the flat section (near the outer rim). These points should be at intervals of 36 degrees and should be indented using a centre punch before drilling with a 1mm diameter drill. The four sockets should then be mounted and sealed (to prevent oil escaping from the container) using an epoxy resin based adhesive.

Next, the resistors should be mounted on the tin lid which provides a common termination for the resistors. The resistor leads should be fed through the 1mm holes and soldered on both sides of the lid before trimming. The other end of the resistors are then fed to a 'star' point which is linked to SK1 using a substantial conductor (e.g. 16/0.2mm stranded PVC covered wire). The remaining components are then assembled and soldered into place following the layout shown in Fig. 2.2.

Finally, the tin is filled with clean multi-grade oil to within 10mm from the top and then the lid assembly is lowered into the oil, checking that the resistor bodies are fully immersed. It is, of course, important to check that the lid is firmly in place before using the load.

Calibration graphs for 4 and 8 ohm dummy loads are shown in Figs. 2.3 and 2.4 respectively. Measurements are made with a d.c. milliammeter connected between SK3 and SK4 and with a 1kHz sinusoidal input. A suitable signal source based on a 741 operational amplifier will be described in Part Three.

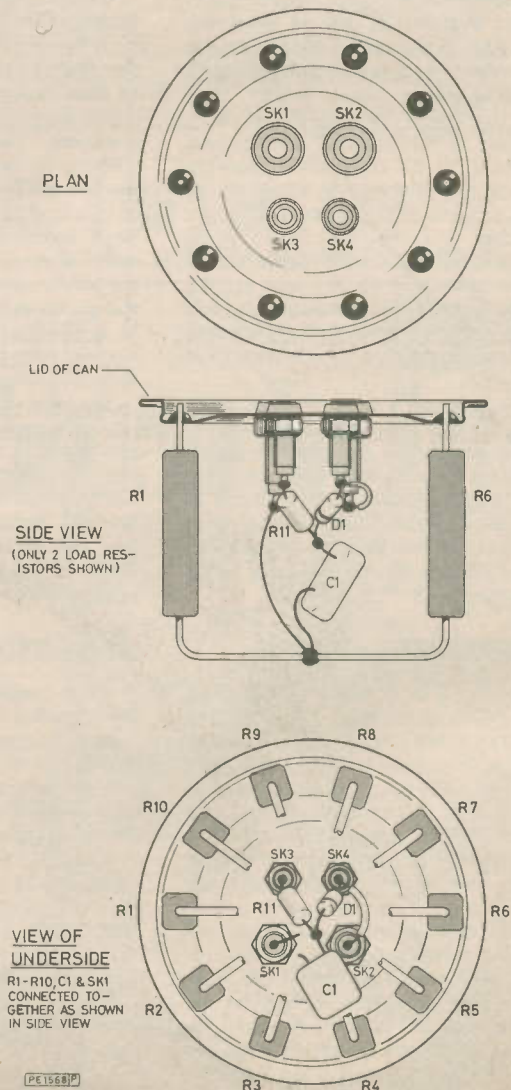


Fig. 2.2. Internal construction of the Dummy Load

## COMPONENTS . . .

### DUMMY LOAD

#### Resistors

R1-R10	39 or 82 ohm 7W ceramic (for the 4 and 8 ohm versions respectively) (10 off)
R11	4k7 0.25W

#### Capacitor

C1	1 $\mu$ 250V polyester
----	------------------------

#### Miscellaneous

D1	OA91
SK1	4mm socket (red)
SK2	4mm socket (black)
SK3	2mm socket (red)
SK4	2mm socket (black)
1lb Golden Syrup tin (see text)	
400ml (approx) multi-grade oil (see text)	

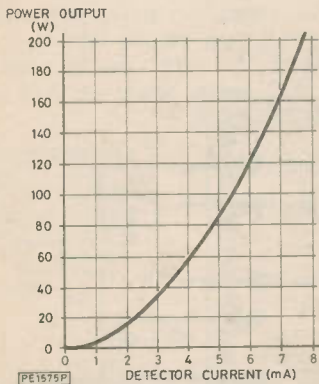


Fig. 2.3. Calibration graph for a 4 ohm load

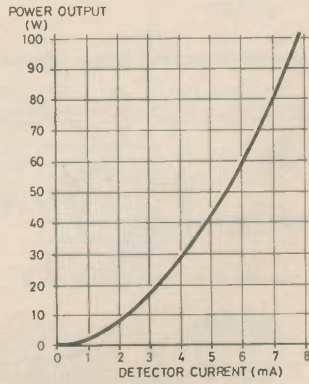


Fig. 2.4. Calibration graph for an 8 ohm load



## PRE-AMPLIFIER/LINE DRIVER

The power amplifier module described last month requires an input of approximately 1V r.m.s. for full output. Where a signal source is unable to provide such an output level, extra gain will be required. Furthermore, in many applications one or more power amplifier modules will have to be driven from a remote signal source. In such applications, low impedance distribution is advantageous as is the ability to provide a balanced output.

The pre-amplifier/line driver module provides a modest value of voltage gain which is adjustable from 1 to 5 approximately. The pre-amplifier/line driver has both low and medium impedance balanced and unbalanced outputs and operates from nominally +30V and -30V. These rails can be derived either from the power amplifier itself or from the power supply module described in Part Three.

## CIRCUIT DESCRIPTION

The circuit of the pre-amplifier/line driver module is shown in Fig. 2.5. A simple inverting operational amplifier is formed by IC1 and associated components. The gain of this stage is made adjustable by means of VR1. IC2 and its associated components form a unity gain phase inverter. Signal outputs at 1 and 2 are thus of equal amplitude but are in anti-phase. A Darlington transistor, TR1, is used as an emitter follower to provide a separate low-impedance unbalanced output. The supply voltage rails for IC1, IC2 and TR1, are regulated by means of shunt Zener stabilisers, D1 and D2.

## COMPONENTS . . .

### Resistors

R1, R2, R3	47k (3 off)
R4, R6	1k (2 off)
R5	470
R7, R8	100 (2 off)
R9, R10	100k (2 off)
R11	22
R12, R13	1k 0.5W (2 off)
VR1	220k min. horizontal skeleton pre-set
VR2	100 min. horizontal skeleton pre-set
Except where otherwise stated, all fixed resistors are 0.25W 5% carbon.	

### Capacitors

C1, C2	220n 250V polyester (2 off)
C3	100 $\mu$ 16V p.c. electrolytic
C4, C5	220 $\mu$ 16V p.c. electrolytic (2 off)

### Semiconductors

D1, D2	BZY88 C9V1 (2 off)
TR1	TIS151
IC1, IC2	TLO71 (2 off)

### Miscellaneous

P.c.b.	
8-pin d.i.l. sockets (2 off)	
Terminal pins (13 off)	
Small instrument case (see text)	
SK1, SK2	standard 0.25in. closed circuit jack sockets (2 off)
SK3, SK4	5-pin 270 deg. DIN sockets (2 off)

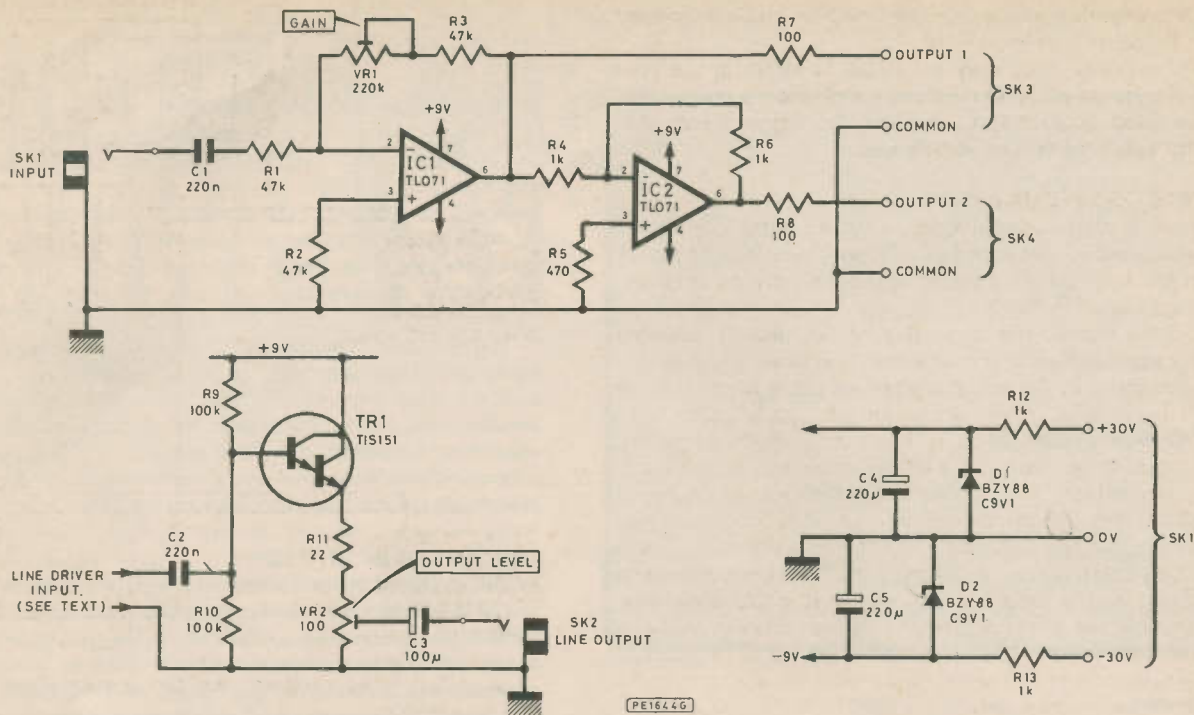


Fig. 2.5. Circuit diagram of the pre-amplifier/line driver module

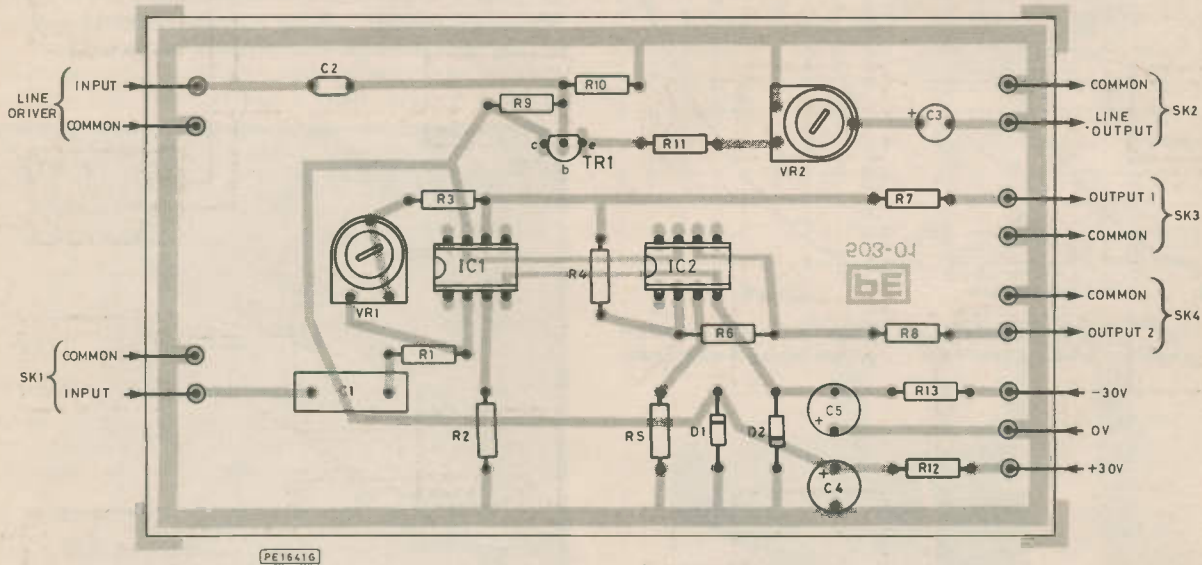


Fig. 2.6. P.c.b. design for the pre-amplifier/line driver

### CONSTRUCTION

With the exception of the input and output signal connectors, all components are mounted on a single sided p.c.b. measuring approximately 65mm x 115mm (i.e. identical in size to the power amplifier module). The component overlay for the p.c.b. is shown in Fig. 2.6. Components should be assembled on the p.c.b. in the following sequence; terminal pins, i.c. holders, resistors, capacitors, transistor, Zener diodes, and pre-set resistor. Care should be taken to ensure the correct orientation of all polarised components.

When the p.c.b. wiring is complete, the underside of the board should be carefully checked for solder bridges and dry joints whereas the component side should be examined paying particular attention to the correct placement of components.

In applications where the power amplifier module is to be used in the proximity of the signal source (as would be the case in a 'domestic' environment) the pre-amplifier/line driver module may be conveniently mounted within the same enclosure as that used for the power amplifier. In this case the supply rails can be simply derived from the power amplifier.

Alternatively, where the power amplifier module is located remotely, the pre-amplifier/line driver module may be mounted in almost any small instrument case. In this case a typical wiring layout is shown in Fig. 2.7. As before, the supply rails may be derived from the power amplifier module using a 3-core cable plus a separate screened signal lead. In some applications (i.e. where a very long cable run is necessary) such an arrangement may not be convenient and

hence the separate mains powered module (to be described in Part Three) should be utilised.

The line-driver input may be linked to either of the pre-amplifier outputs or, where remote distribution is concerned, may be used separately to monitor the signal input with medium/high impedance headphones.

### SYSTEM CONFIGURATION

Various system configurations are possible depending upon the number and location of power amplifier modules and on the total output power required. Six typical arrangements are shown in Fig. 2.8.

Fig. 2.8a shows the arrangement for driving a single power amplifier from a pre-amplifier/line driver module. Interconnection is by means of a screened cable which may be up to 10m in length. Where convenient, power for the pre-amplifier may be derived from the power amplifier module. In this case, three extra wires will be necessary in the interconnecting cable. These, however, need not be screened and, under no circumstances should they be contained within the same screened cable as the audio signal.

For long cable runs a 'local' pre-amplifier power source is preferable. In this case a single screened cable should be used to link the pre-amplifier/line driver module with its associated power amplifier. In Part Four we shall be describing a simple power unit which is suitable for use with up to four pre-amplifier modules.

Fig. 2.8b shows how further power amplifiers can be 'daisy-chained' from a single pre-amplifier/line driver module. As many as ten such units can be driven from a

OUTPUT TO POWER AMPLIFIER MODULE(S)

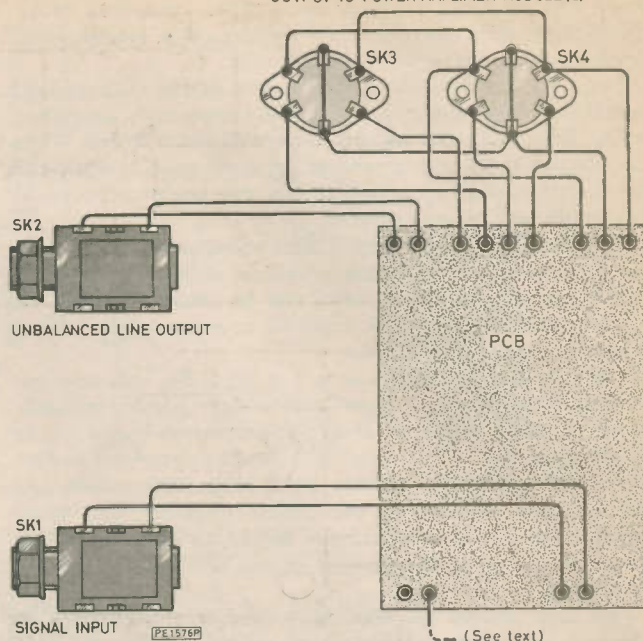


Fig. 2.7. Wiring diagram for the pre-amplifier/line driver module

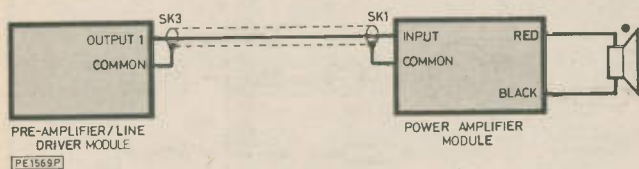


Fig. 2.8a.

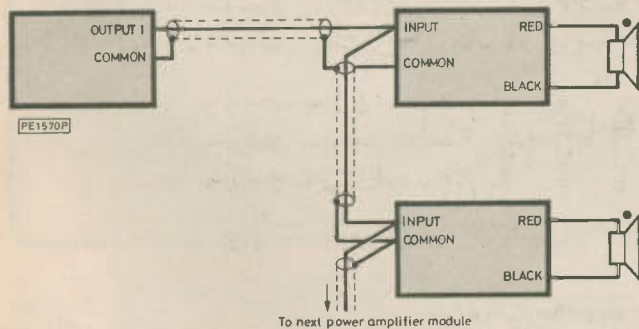


Fig. 2.8b.

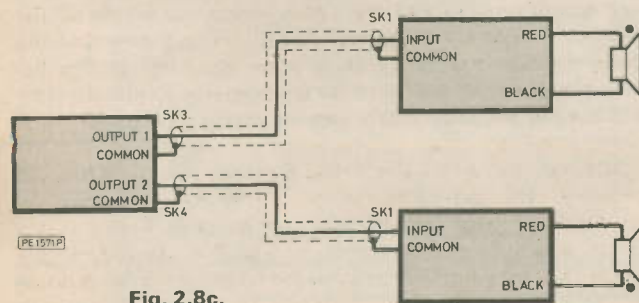


Fig. 2.8c.

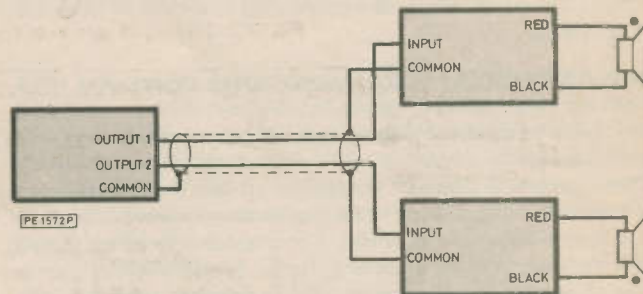


Fig. 2.8d.

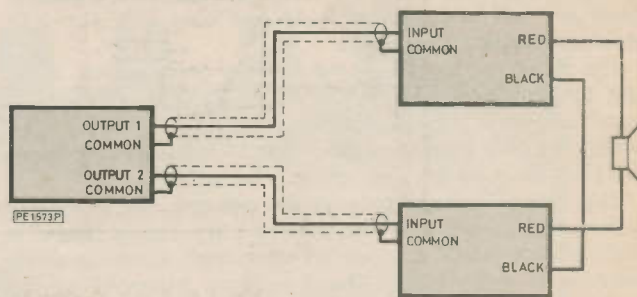


Fig. 2.8e.

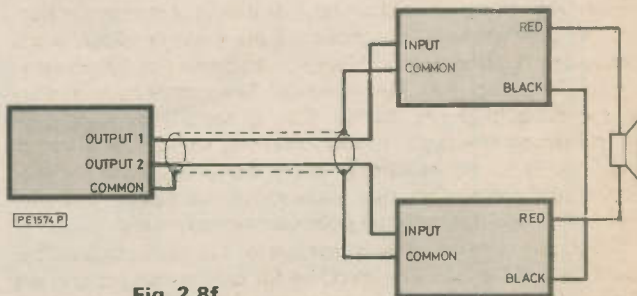


Fig. 2.8f.

Fig. 2.8. Typical system configurations

single pre-amplifier module. Each power amplifier must, however, have its own associated loudspeaker system since parallel output connection is inadvisable.

Since the pre-amplifier provides anti-phase outputs, it is possible to drive two power amplifiers separately, as shown in Fig. 2.8c. Here the important consideration is that, if the loudspeaker systems are serving the same area, or are in the same enclosure, it is essential that one set of speakers is connected with reverse polarity.

A useful alternative to Fig. 2.8c is shown in Fig 2.8d. Here the two power amplifiers are physically adjacent and thus a twin screened (balanced) cable can be employed. Like the previous arrangement, it is essential to ensure that one set of speakers is reverse phased.

A bridge output stage is shown in Fig. 2.8e. This arrangement is ideal where a single loudspeaker system (suitably rated) is to be operated at very high power levels (up to 200W from the power amplifier modules described in Part One). It is essential that both the loudspeaker system and the common outputs of the power amplifier are linked together using a very substantial conductor since, at 200W output into 4 ohm, the current in this link will be approximately 7A!

Fig. 2.8f shows an alternative bridge arrangement in which a twin screened (balanced) cable is employed. This balanced arrangement is instrumental in reducing the effects of hum and induced electrical noise and is much to be preferred in situations where cable runs in excess of 50m are unavoidable.

### PRE-AMPLIFIER, MIXER AND TONE CONTROL

Whilst the simple pre-amplifier/line driver described previously is ideal for driving one, or more, power amplifier modules from a single source, there will be many occasions where several signals of varying levels are to be combined before sending to one, or more, power amplifier modules.

A typical example is where a microphone is to be mixed with the output of an electric guitar or synthesiser. In such a case, a simple mixer arrangement is required coupled with some additional tone controls and a master gain control. The unit described was designed to satisfy just such a requirement and yet is simple to build and uses only low-cost, readily available components.

The simplified block schematic of the pre-amplifier, mixer and tone control is shown in Fig. 2.9. The pre-amplifier, mixer and tone control provides four input channels, each having its own individual gain control, has separate treble and bass controls and a master gain control.

The overall voltage gain of the pre-amplifier is well in excess of 200 and thus the maximum input sensitivity is of the order of 10mV to drive an associated power-amplifier module to full output. The frequency response of the prototype unit is shown in Fig. 2.10.

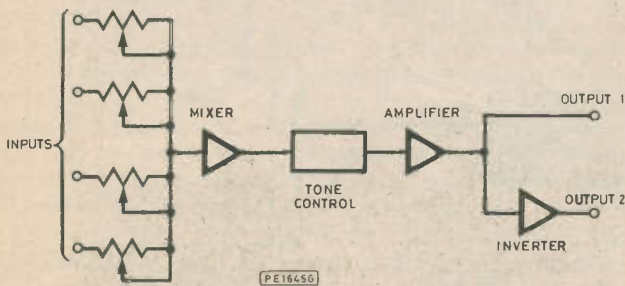


Fig. 2.9. Simplified block schematic of the pre-amplifier, mixer and tone control unit



## COMPONENTS . . .

### Resistors

R1-R4	(see text)
R5-R8	100k (4 off)
R9	22k
R10	1M
R11,R12	10k (2 off)
R13,R14	4k7 (2 off)
R15	100k
R16	1k 0.5W
R17	470
R18	1k 0.5W
R19,R20	100 (2 off)
VR1-VR4	50k log carbon pot (4 off)
VR5,VR6	100k lin carbon pot (2 off)
VR7	5k log carbon potentiometer

Unless otherwise stated, all fixed resistors are 0.25W 5% carbon.

### Capacitors

C1-C4	220n 160V polyester (4 off)
C5,C10,C11	10µ 16V p.c. elect. (3 off)
C6,C7	47n 250V polyester (2 off)
C8,C9	10n 250V polyester (2 off)
C12,C13	220µ 16V p.c. electrolytic
C14	470p ceramic

### Semiconductors

D1, D2	BZY88 C9V1 (2 off)
IC1	TL074

### Miscellaneous

- P.c.b.
- SK1 to SK4 standard 0.25 in. closed jack sockets (4 off)
- Low profile 14-pin d.i.l. socket
- Terminal pins (20 off)
- SK5 and SK6 5-pin 270 degree DIN (2 off)
- Case and matching knobs (7 off)

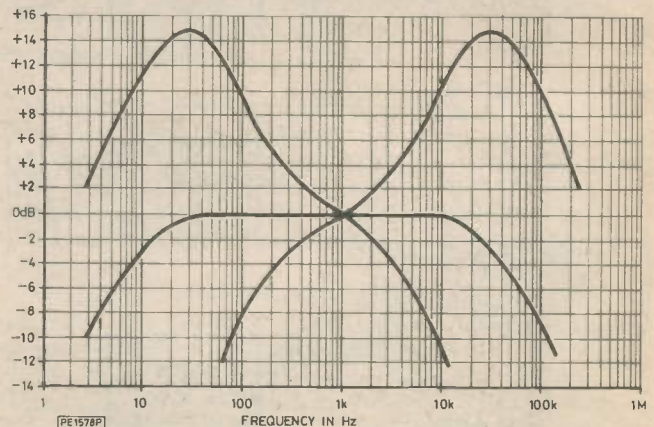


Fig. 2.10. Frequency response of the pre-amplifier, mixer and tone control unit

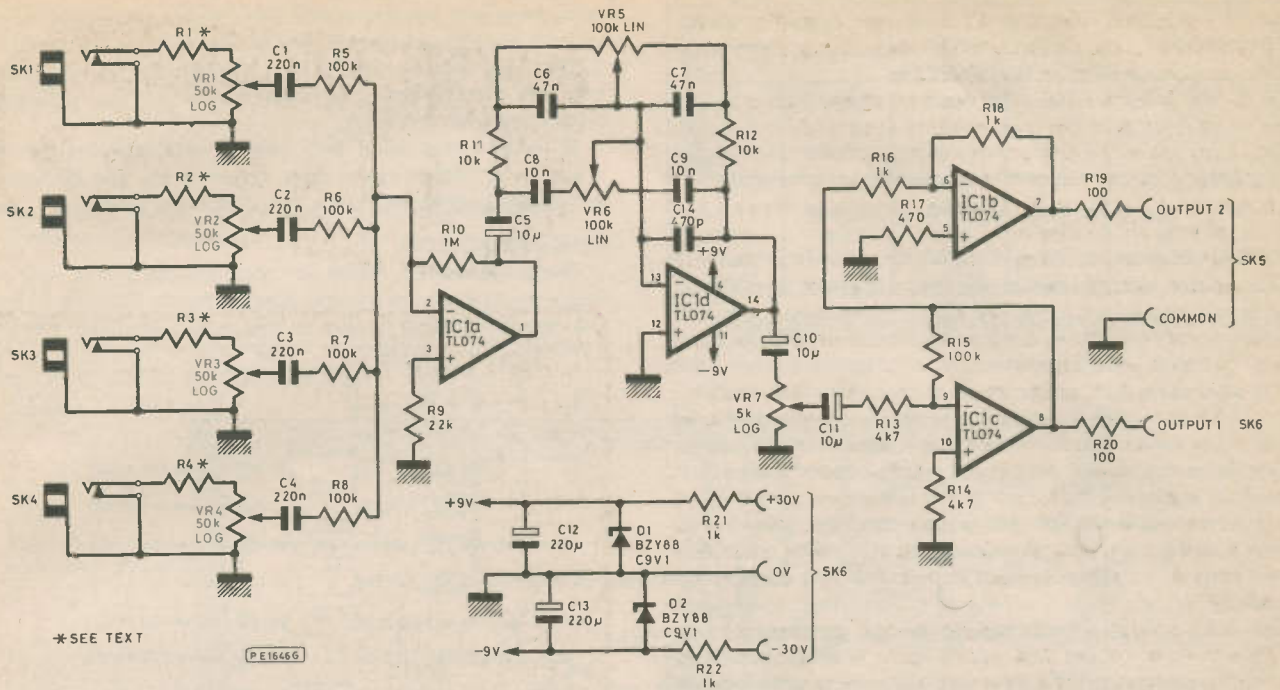


Fig. 2.11. Complete circuit diagram of the pre-amplifier, mixer and tone control unit


**CIRCUIT DESCRIPTION**

The complete circuit diagram of the pre-amplifier, mixer and tone control unit is shown in Fig. 2.11. A low-noise quad operational amplifier is used and this is operated from +9V and -9V supply rails stabilised by means of D1 and D2 respectively.

VR1 and VR4 act as the individual channel gain controls and R1 to R4 may be added in order to match a variety of in-

puts (see Table 1). IC1a forms a summing amplifier which provides a voltage gain of approximately 10 on each channel. IC1d is an active Baxandall arrangement which provides a maximum 'cut' and 'boost' of around 15dB at both LF and HF. C14 is added in order to ensure unconditional stability of the arrangement when maximum treble boost is selected.

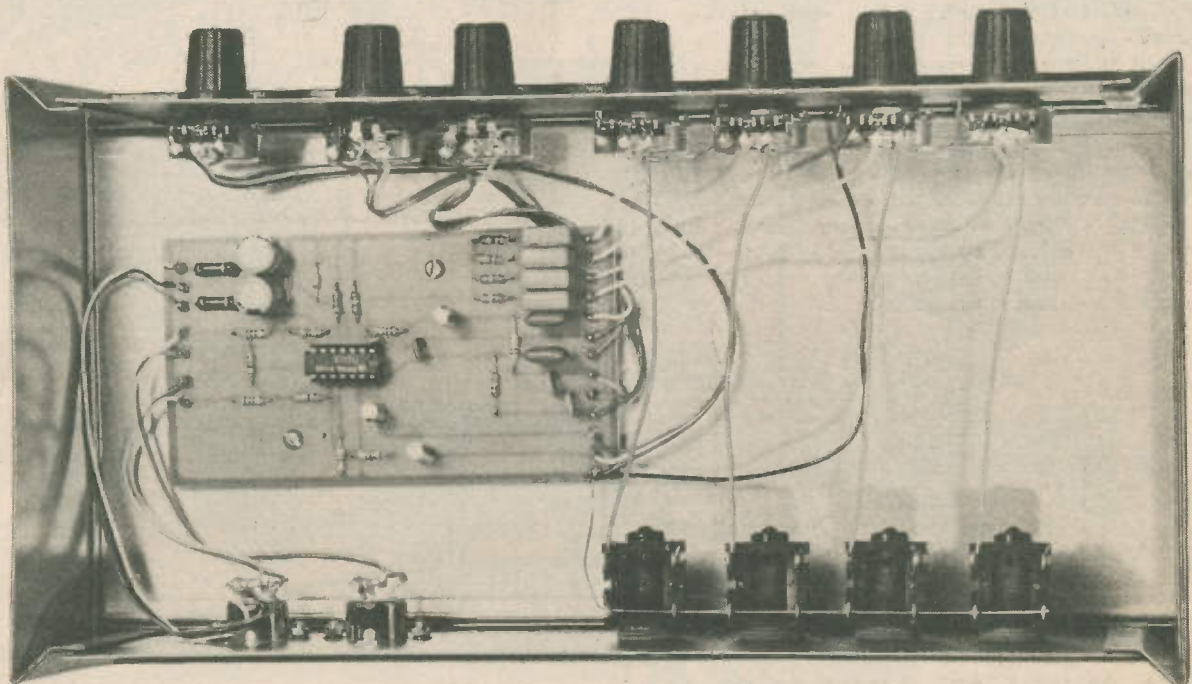IC1c operates as an inverting amplifier with a fixed



Internal view of the pre-amplifier

Signal source	Requires own pre-amp?	Nominal input impedance	Nominal sensitivity	Input resistance R1 to R4
Dynamic microphone (high output)	No	50kΩ	10mV	s/c
Dynamic microphone (low output)	No	600Ω	10mV	s/c
Electret microphone	No	50kΩ	10mV	s/c
Tape-deck	No	500kΩ	100mV	470kΩ
Ceramic pick-up	No	1MΩ	200mV	1MΩ
Magnetic pick-up	Yes	600Ω	10mV	s/c
Tuner	No	500kΩ	100mV	470kΩ

Table 1. Typical signal sources and input arrangements

voltage gain of approximately 20 (if desired, the gain may be increased to approximately 40 by raising the value of R15 to 220k). The output of IC1c is at a relatively low impedance and will directly drive as many as ten parallel connected power amplifier modules.

IC1b acts as a unity gain inverter and provides the low-impedance anti-phase output required for the differential and bridge output configurations described earlier.

### CONSTRUCTION

The pre-amplifier, mixer and tone control unit is built on a single sided p.c.b. measuring approximately 65mm x 115mm (i.e. again identical in size to the power amplifier module).

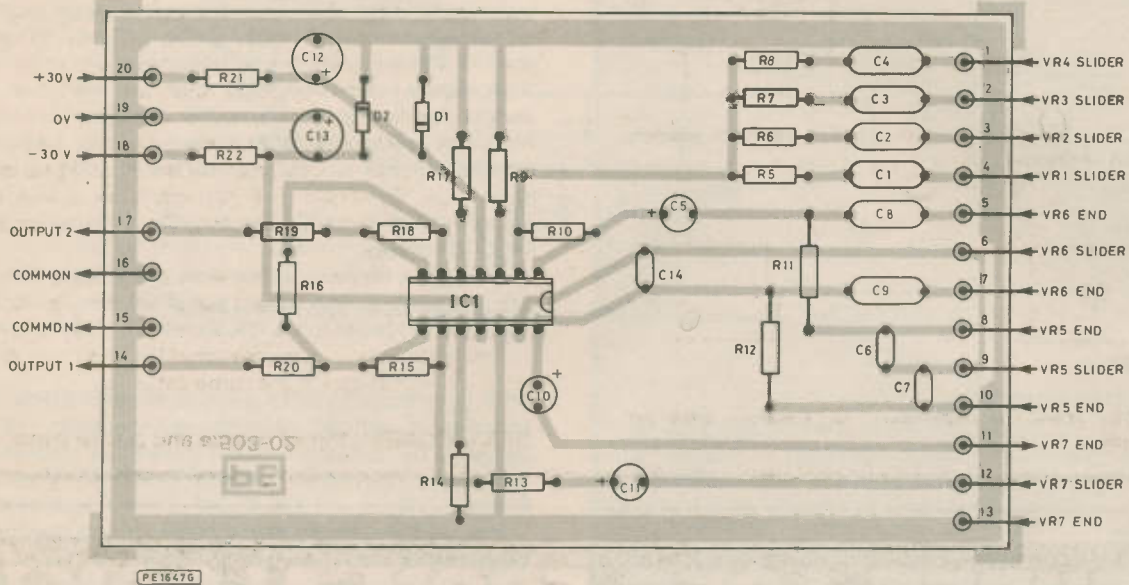


Fig. 2.12. Component layout of the pre-amplifier and tone control unit

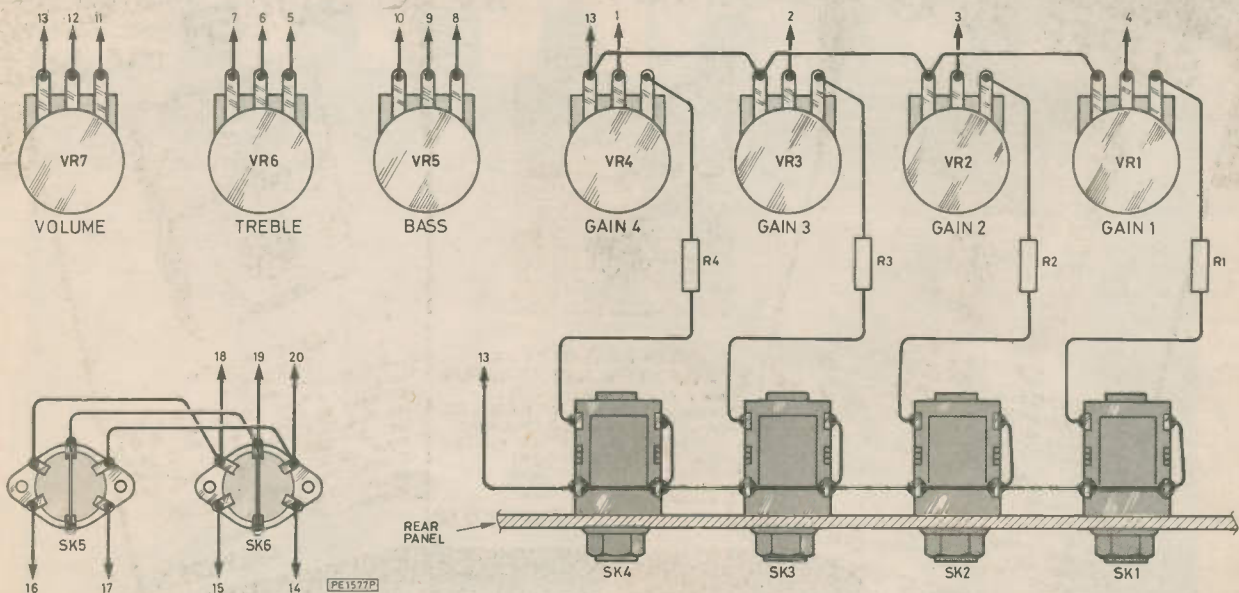


Fig. 2.13. Wiring diagram for the front and rear panel mounted controls and sockets



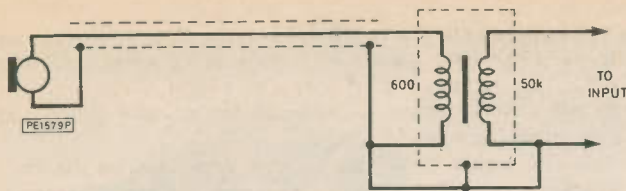


Fig. 2.14. Input arrangement for low-impedance unbalanced microphones


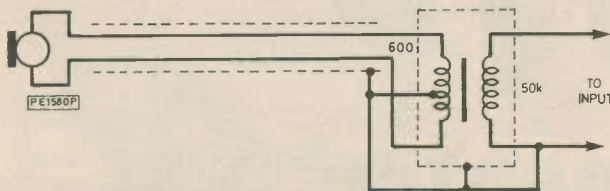


Fig. 2.15. Input arrangement for low-impedance balanced microphones

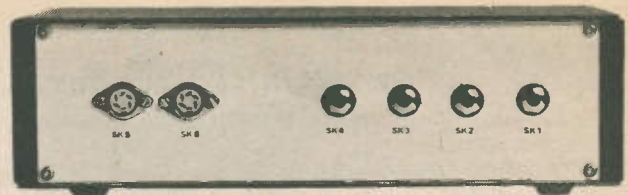

Fig. 2.16. Input arrangement for ceramic pick-up cartridges



Rear view of the pre-amplifier case

The component overlay for the p.c.b. is shown in Fig. 2.12. Components should be assembled on the p.c.b. in the following sequence; terminal pins, i.c. holder, resistors, capacitors, and Zener diodes. Care should be taken to ensure the correct orientation of all polarised components.

When the p.c.b. wiring is complete, the underside of the board should be checked for solder bridges and dry joints and the component side should be examined paying particular attention to the correct placement of components.

As before, and depending upon the individual constructor's preference, the pre-amplifier may be either mounted in the same enclosure as that used for the power-amplifier module or, alternatively, may be mounted in its own equipment case. This latter arrangement is, of course, preferable when one, or more, power amplifiers are to be used from remote locations.

A suitable internal wiring diagram is shown in Fig. 2.13 and the corresponding front panel labelling is shown in the photograph. Connectors, SK5 and SK6 will, of course, not be required where the pre-amplifier and power-amplifier modules are housed in the same cabinet.

NEXT MONTH: Signal source and power supply module.

# THREE ACES FROM ALCON!


## SUPER 20 A♣



**20KΩ/V a.c. & d.c.**  
**39 RANGES - INDESTRUCTIBLE**  
 automatically protected on all ranges but 10A  
 Accuracy: d.c. ranges and Ω 2% a.c. 3% (of f.s.d.)  
 39 ranges: d.c. V 100mV, 1.0V, 3.0V, 10V, 30V, 100V, 300V,  
 1000V;  
 d.c. I 50μA, 100μA, 300μA, 1.0mA, 3mA, 10mA, 30mA,  
 100mA, 1A, 10A,  
 a.c. V 10, 30V, 100V, 300V, 1000V; a.c. I 3mA, 10mA, 30mA,  
 100mA, 1.0A, 10A,  
 Ω 0-50kΩ, 0-50kΩ, 0-500kΩ, 5MΩ, 50MΩ.  
 dB from -10 to +61 in 5 ranges.  
 Dimensions: 105 x 130 x 40mm.

ONLY £33.50


## MINI 20 A♥

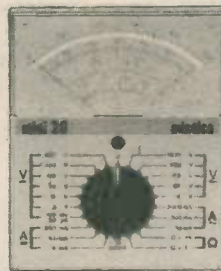

**20KΩ/V d.c. & 4KΩ/V a.c.**  
**28 RANGES WITH PROTECTIVE FUSE**  
 Accuracy: 2% d.c. and resistance, 3% a.c.  
 28 ranges: d.c. V 100mV, 3V, 10V, 30V, 100V, 300V,  
 600V, d.c. I 50μA, 600μA, 6mA, 60mA, 600mA,  
 a.c. V 15V, 50V, 150V, 500V, 1500V; a.c. I 30mA,  
 300mA, 3.0A. Ohms 0-2kΩ, 0-2MΩ.  
 dB from -10 to +62 in 6 ranges.  
 Dimensions: 105 x 130 x 40mm.

ONLY £21.60

## SUPER 50 A♠

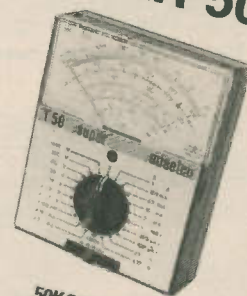

**50KΩ/V a.c. & d.c.**  
**39 RANGES**  
 Accuracy: d.c. ranges and Ω 2% a.c. 3% (of f.s.d.)  
 39 ranges: d.c. V 150mV, 1.0V, 3.0V, 10V, 30V, 100V,  
 300V, 1000V, d.c. I 20μA, 100μA, 300μA, 1.0mA,  
 3mA, 10mA, 30mA, 100mA, 1A, 3A, a.c. V 10, 30V,  
 100V, 300V, 1000V; a.c. I 3mA, 10mA, 30mA,  
 100mA, 1.0A, 3.0A,  
 Ω 0-50kΩ, 0-50kΩ, 0-500kΩ, 5MΩ, 50MΩ.  
 dB from -10 to +61 in 5 ranges.  
 Dimensions: 105 x 130 x 40mm.

ONLY £36.30

**3 HIGH QUALITY TEST INSTRUMENTS AT SUPERDEAL PRICES**

EACH INSTRUMENT COMES COMPLETE WITH A ROBUST CARRYING CASE, LEADS & INSTRUCTIONS.  
 PRICES Our prices include VAT and postage and goods are normally despatched by return.  
 Please write or telephone for details of these and the many other instruments in the Alcon range, including multimeters, components measuring, automotive and electronic instruments.

**ALCON** Instruments Ltd.

19 MULBERRY WALK · LONDON SW3 6DZ · TEL: 01-352 1897 · TELEX: 918867

# ROBOTS

## neptune and mentor

**C**ONSTRUCTION of the MENTOR robot starts at the base plate of the robot (Fig. 7.1) to which the power supply board and transformer are fitted. The main wiring loom passes through a slot under the board ready for connecting to the interface board which is later sited beneath the robot.

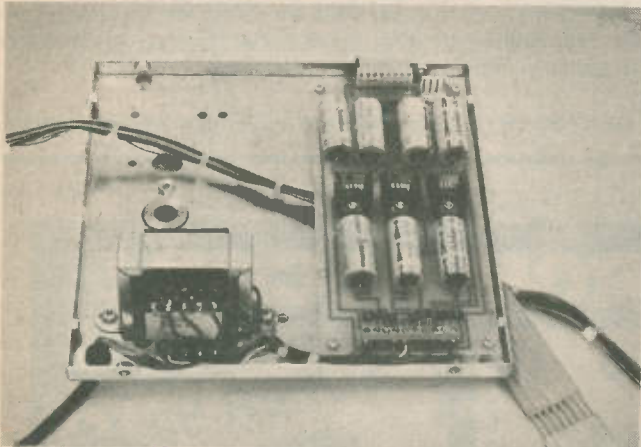


Fig. 7.1. Base plate assembly

### ASSEMBLY

The two side plates are next fitted to the base plate and the top plate and then screwed down (Fig. 7.2). In the top plate is a 60mm nylon bush through which the centre column is passed.

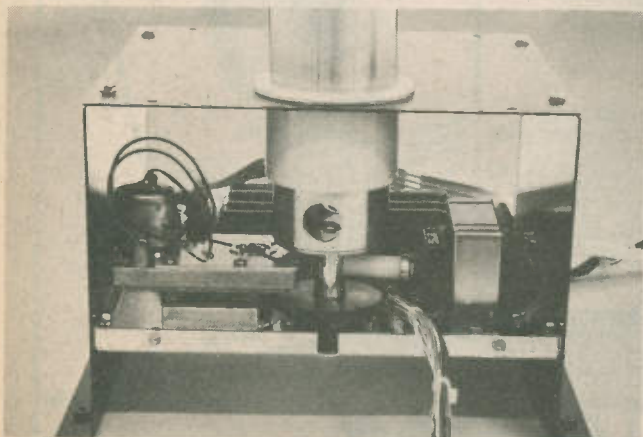


Fig. 7.2. Main chassis assembly

### PART SEVEN

At the base of the column is attached a gear which then engages with another gear fitted to axis 0 motor which is then secured to the base plate.

The arm assembly is secured to the column with a nut on axis 1 axle (Fig. 7.3) and the large counterbalance weights fitted. These result in the robot's position being stable when there is no power applied to the motors. They also increase the accuracy of the robot in that no error signal from the servo system is required simply to hold a position.

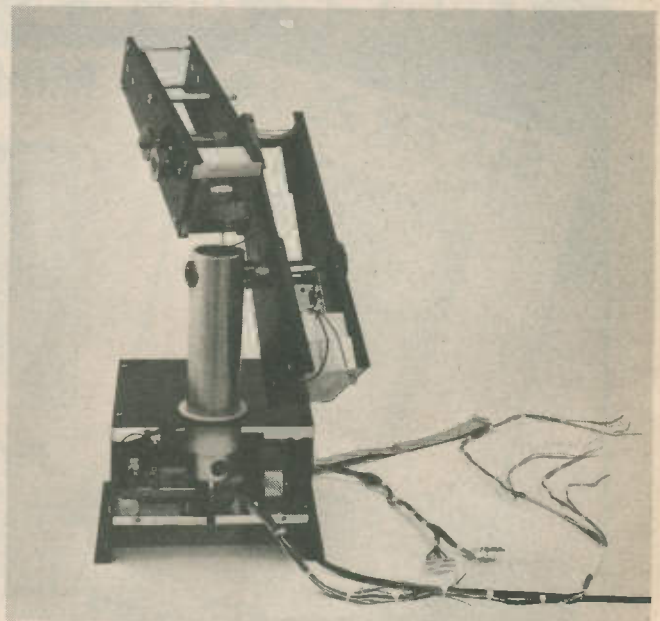


Fig. 7.3. Arm assembly

The wrist motors which together provide elevation and roll can now be screwed to axis 2 arm (Fig. 7.4) and the gears fitted. There are two pairs of spur gears to transfer torque from the motors to the wrist axles and three bevel gears to turn the torque through 90 degrees to the gripper assembly.

# ROBOTICS PROJECT

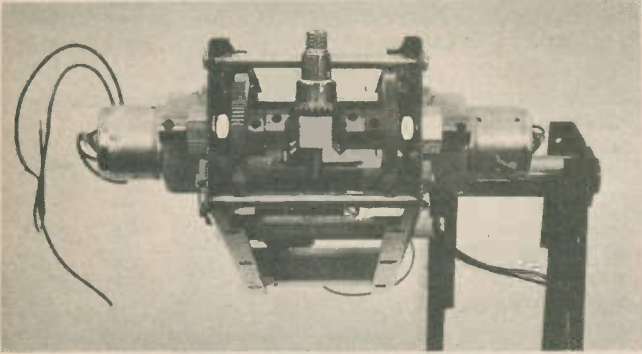


Fig. 7.4. Wrist motor assembly

The gripper components are now fitted (Fig. 7.5). A pair of torsion springs open the jaws after tension is released on the Bowden cable which closes them. The cable is driven by a motor attached to the cover of axis 1 arm (Fig. 7.6).

## POTENTIOMETERS

Next, the wiring harness and position sensing potentiometers are fitted. The potentiometers are adjusted such that the voltage on the wiper will be about 10% of the 10V supply voltage when the axis is at its minimum position. The harness passes up the column and through the axles branching out on the way to connect to the potentiometers and to the motors via terminal blocks.

The interface board is now screwed to its plate (Fig. 7.7) and after checking that the power supply is operating correctly the power supply lead and the harness are plugged into the board and the robot is then ready for connecting to a computer for calibration.

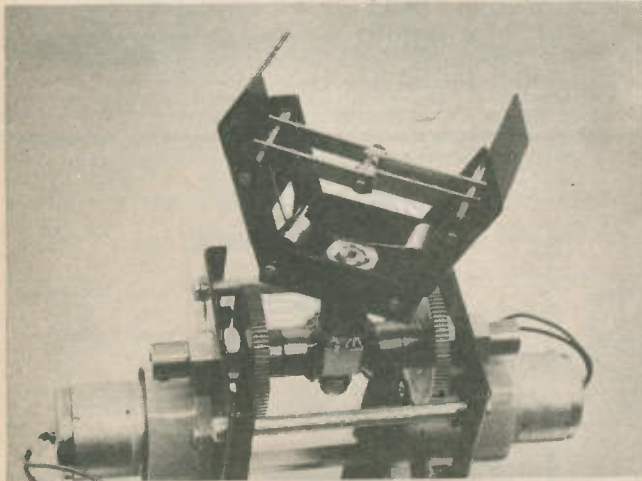


Fig. 7.5. Gripper assembly

## CALIBRATION

The robot is operated as if it were part of the memory of the computer and instructions consist of POKEs for sending data and PEEKs for receiving data. Axis 0 is at the lowest address in the block allocated to the robot. As the system is defined in 8 bits each axis has 256 possible positions to which it may move, i.e. there is a resolution of 1 part in 256 (0.04%) and the data sent to each axis may be any integer from 0 to 255. To send each axis to its centre position using the BBC computer the instructions are as follows:

## CALIBRATION PROGRAM

```
10 A=&FD00
20 FOR I=0 TO 5: ?(A+I)=128 NEXT I
Or for a ZX Spectrum:
10 LET a=32
20 FOR i=0 TO 5: POKE a+i,128: NEXT i
Or for a Commodore VIC20:
10 A=8192
20 FOR I=0 TO 5: POKE A+I,128: NEXT I
Or for a Commodore 64:
10 A=56832
20 FOR I=0 TO 5: POKE A+I, 128: NEXT I
```

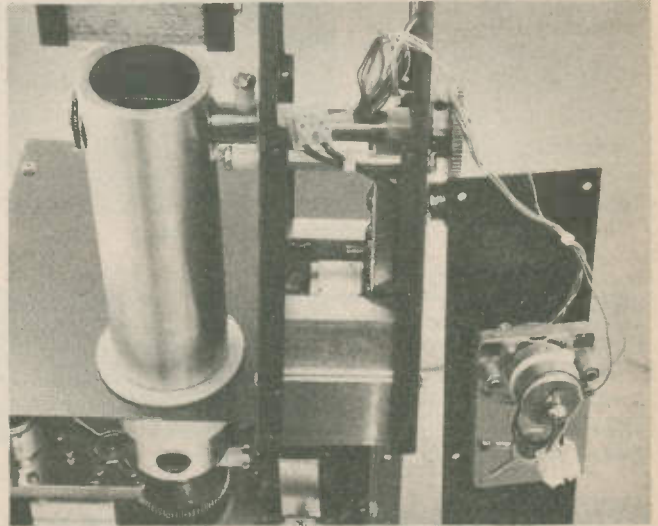


Fig. 7.6. Gripper motor assembly

The Commodore 64 plugs onto the same edge connector as the VIC20. The only significant difference between the interfaces is at the computer end where the board which plugs into the cartridge slot is laid out on a 0.1" pitch whilst the VIC20 is on 0.156" pitch. Virtually any 8- or 16-bit micro system or computer can be used provided there is access to the address, data and control bus.

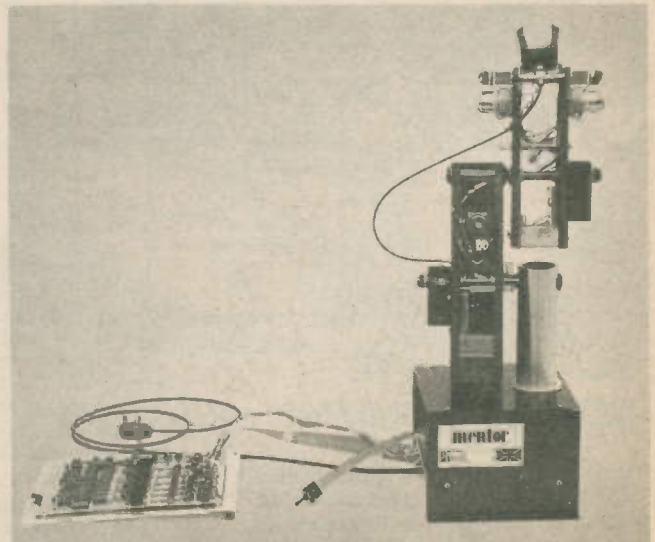


Fig. 7.7. Interface board

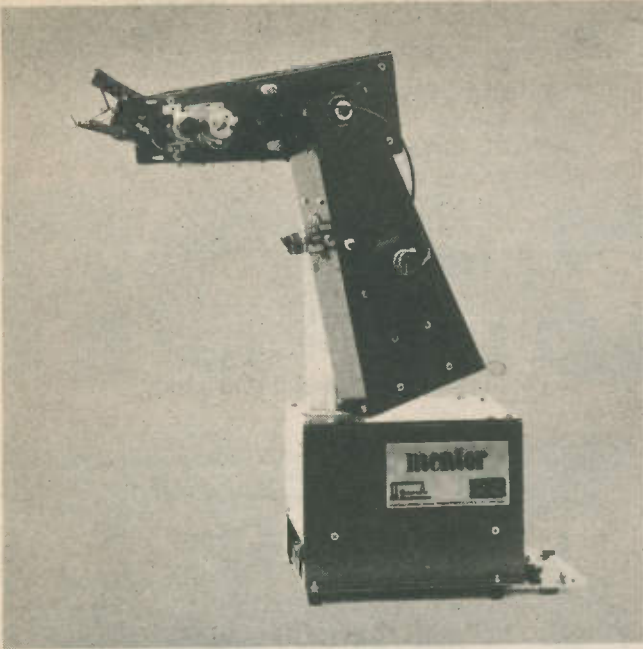


Fig. 7.8. The complete Mentor Robot

With mid-position data sent to each axis the wrist is set by slackening the gripper assembly, moving it and securing in the centre position. Fine adjustment is carried out with pre-sets P203,204.

Axes 0,1,2 are set by sending them in turn to position 0 and adjusting pre-sets VR200,201,202 so that the axis stops just before the end stop is reached. VR205 is used to make the gripper start to operate at some convenient datum such as 50.

#### POSITION DATA

There are ADCs on the interface board to enable the positions of the simulator and the robot axes to be read. To operate the robot it is not necessary to use the ADC but it is useful to know for certain when the required position has been reached. Otherwise a transit time would have to be calculated based upon

the size of the position change.

The arm ADC is read by first writing to it, with a POKE instruction, which axis is to be read. This is defined by the top 4 bits of the data byte so the data is the axis number multiplied by 16. The ADC is then written to at the next address to tell it to start conversion. After that the arm position is ready with a PEEK instruction. For the BBC computer the instructions to read axis 0 position are as follows:

```
30 ?(A+6)=0
40 ?(A+7)=0
50 DAO=?(A+17)
Similarly for axis 2:
60 ?(A+6)=32
70 ?(A+7)=0
80 DA2=?(A+17)
```

The simulator is read similarly except that the multiplexer address is defined by the bottom 4 bits of the data byte so the data is the axis number and the ADC is at an address one lower so to read axis 2 of the simulator via a BBC computer. The instructions are:

```
90 ?(A+6)=2
100 ?(A+7)=0
110 DS2=?(A+16)
```



By use of the following program the MENTOR will copy in real time the movement of the hand-held simulator showing clearly the ease of use of the MENTOR control system.

```
10 A=&FD00: FOR N=0 to 5
20 ?(A+6)=N: ?(A+7)=0
30 ?(A+N)=?(A+16)
40 NEXT N: GOTO 10
```

Furthermore by being on the bus of the computer it is very simple to add additional devices into the system. The BBC computer is particularly suited to this as the 1MHz bus is buffered and daisy-chaining of other robots, sensors etc. is easily implemented. ★
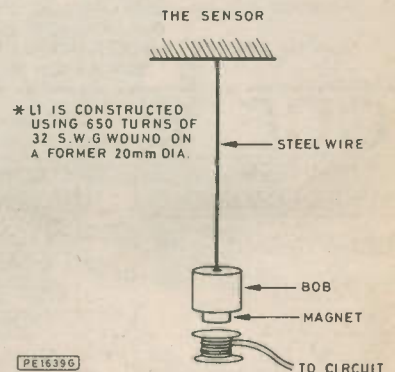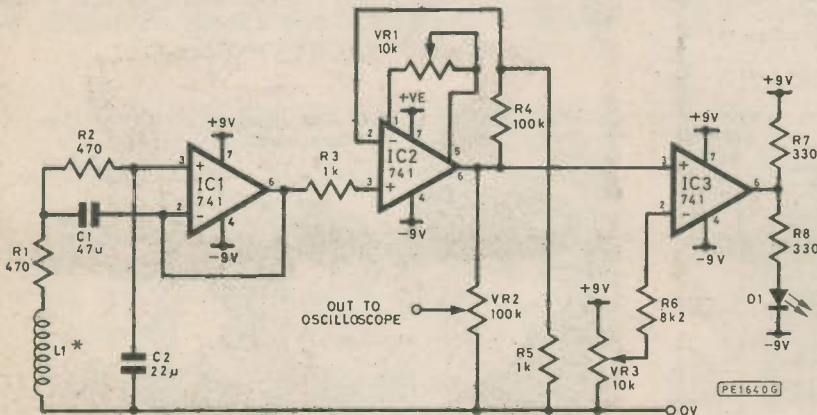
#### Constructors' Note

MENTOR and NEPTUNE are available as kits or ready-built from: **Cybernetic Applications, West Portway Industrial Estate, Andover, Hants.**



## ELECTRONIC SEISMOGRAPH

THIS circuit can detect the waves and oscillations of the movement of the earth. The sensitivity of the instrument depends upon the sensor and its construction. In this case it consists of a pendulum

made up of a magnet supported by a long steel wire. The longer the wire and the heavier the bob, the greater the sensitivity. To get the most reliable and accurate measurements the magnet should be in close proximity to the pick-up coil, L1.

When the magnet is disturbed by movement, a current is induced into the coil and a signal is passed to IC1. This acts as a standard low pass filter with a cut-off fre-

quency of around 10Hz. The filtered signal is amplified by IC2 and fed to an oscilloscope, where it can be monitored.

The signal is also fed to IC3 which is used to indicate an overload condition via D1, and VR2 is used to set the level of the oscilloscope signal.

K. Alizadeh,  
Tehran,  
Iran.



# MARCO TRADING



### TRANSISTORS

AC128	30p	BF338	0.38
AC176	28p	BFX28	0.28
AF239	68p	BFX84	0.24
BC107	0.10	BFX85	0.26
BC108	0.10	BFX87	0.26
BC109	0.10	BFY50	0.21
A.B.C.	0.12	BFY52	0.21
BC147	0.09	VFY90	0.90
BC182	0.09	BSX20	0.34
BC182L	0.09	BU208	1.55
BC184	0.09	BU407	1.65
BC184L	0.09	MJ2955	0.90
BC212	0.09	OC45	0.58
BC212L	0.09	OC71	0.50
BCY70	0.15	OC72	0.52
BD131/2	0.34	TIP31A	0.44
BD133	0.56	TIP32A	0.42
BD135	0.32	TIP33C	0.88
BD136	0.36	TIP34A	0.72
BF115	0.32	TIP2955	0.60
BF184	0.32	TIP3055	0.60
BF185	0.32	TIS43	0.88
BF194	0.08	TIS88	0.40
BF195	0.10	2N3055	0.45
BF196	0.10	2SC1096	0.68
BF197	0.10	2SC1173Y	0.82
BF200	0.20	2SC1306	0.92
BF224	0.20	2SC1307	0.40
BF244	0.26	2SC1957	0.76
BF244A	0.28	2SC2028	0.73
BF244B	0.30	2SC2029	2.10
BF259	0.32	2SC2078	1.05
BF262	0.30	2SC2166	1.20
BF263	0.30	3SK88	0.65
BF327	0.38	40673	0.80

### DIODES

IN916	0.04	AA119	0.12
IN4001	0.05	AA129	0.18
IN4004	0.06	AA130	0.16
IN4005	0.06	BA100	0.24
IN4007	0.07	BY126	0.12
IN4148	0.05	BY127	0.10
IN4149	0.06	BY133	0.16
IN5400	0.12	BY184	0.40
IN5401	0.15	OA47	0.10
IN5402	0.15	OA90	0.08
IN5404	0.16	OA91	0.09
IN5406	0.18	OA95	0.18
IN5408	0.20	OA200	0.06
IS44	0.06	OA202	0.15
IS921	0.08	IN914	0.04

### LINEAR I.C.'s

CA3011	1.80
CA3012	1.75
CA3014	2.38
CA3018	1.10
CA3020	2.10
CA3028A	1.30
CA3035	2.55
CA3080E	1.80
CA3085	1.20
CA3086	0.68
CA3090AO	5.00
CA3130E	1.40
CA3140E	0.60
HA1336W	3.15
LM324N	0.55
LM339	0.65
LM348	0.90
LM380	1.65
LM381N	1.45
LM382N	1.45
LM386	0.95
LM387	1.45
LM389N	1.20
LM3914N	2.55
LM3915N	2.60
ML232B	2.10
C-moss555	0.88
741	0.25
SAS560S	1.85
SAS570S	1.85
SL901B	5.20
SL917B	6.25
TA7205AP	1.50
TA7222P	2.12
TDA1004	2.90
TL072	98p
TL081	68p
TL084	1.28

### RESISTOR KITS

1/4W Pack 10 each value E12 10R-1M  
**Total: 610 resistors ONLY £4.48**  
 1/4W Pack 5 each value E12 10R-1M  
**Total: 305 resistors ONLY £2.75**  
 1/2W Pack 10 each value E12 2R2-2M2  
**Total: 730 resistors ONLY £5.25**  
 1/2W Pack 5 each value E12 2R2-2M2  
**Total: 300 resistors ONLY £3.50**

### 74LS

LS00	28p
LS01	28p
LS02	28p
LS03	28p
LS03	32p
LS08	28p
LS09	28p
LS10	28p
LS11	28p
LS12	25p
LS13	33p
LS14	58p
LS15	25p
LS20	28p
LS21	28p
LS22	28p
LS30	33p
LS32	28p
LS37	23p
LS74	38p
LS122	70p
LS138	45p
LS139	68p
LS151	75p
LS155	50p
LS157	45p
LS158	58p
LS160	60p
LS161	70p
LS162	72p
LS163	80p
LS166	1.95
LS170	1.75
LS244	1.00
LS245	2.00
LS257	73p
LS393	1.15

### TRANSFORMERS

British made transformers at very attractive prices  
 Primary Secondary Current 1+ 10+ 100+  
 240v: 6-0-6v 100mA 58p 52p 48p  
 240v: 6-0-6v 500mA 55p 60p 43p  
 P&P 45p per transformer £1.60 for ten.

### MIN. D CONNECTORS

9	15	25	37
way	way	way	way
Solder Lug	52p	65p	88p
Right Angle	89p	£1.34	£1.98
SOCKETS			
Solder Lug	78p	98p	£1.33
Right Angle	£1.18	£1.78	£2.70
COVERS	95p	95p	98p

### MULTI-METER SPECIAL

Requires AA cells (not supplied) and leads, etc.  
 Russian type U4324 20,000 O.P.V.  
 D.C. Voltage: 0.6, 1.2, 3, 12, 30, 60,  
 120, 600, 1200;  
 A.C. Voltage: 3.6, 15, 60, 150, 300, 600, 900;  
 D.C. Intensity M/A: 0.06, 0.6, 6, 60, 600, 3000;  
 A.C. Intensity M/A: 0.3, 3, 30, 300, 3000;  
 O.C. Resistance: 0.2, 5, 50, 500, 5000 kOhm;  
 g.e. level dB: -10 to +12.

**£12 FANTASTIC SPECIAL PRICE:**  
 including P/P and VAT

### SOLDERING AIDS

Antex 15Wiron	5.00
Antex 18Wiron	5.00
Antex 25Wiron	5.20
Antex Elements	2.00
Antex Bits	0.95
Antex stands	1.90
Desolder Tool	4.50
Spare nozzle	0.45
25W Kit-iron with 13A plug & stand	ONLY £6.20

### TELECOM EQUIP

BT Plug & 3M lead	£1.25
BT Master Socket	£2.85
BT Sec Skt	£1.95
BT 4-core cable	15p/M
£120/100M	

### ROTARY POTS

0.25W Carbon Log & LIN 1K-2M2	
32p ea.	£3/10.
Any 100	£28.00

### NI-CAD CHARGER

Universal charger to charge  
 PP3, AA, C, D. PRICE: £6.00

### VEROBOARD

2 1/2 x 3 1/4	85p
2 1/2 x 5	£1.00
2 1/2 x 17	£3.07
3 1/4 x 17	£1.05
3 1/4 x 15	£1.15
3 3/4 x 17	£4.10
4 3/4 x 17 3/4	£4.95
Pkt of 100 pins	50p
Spt facecutter	£1.48
Pin Insert, tool	£1.85
Vero Wiring Pen & Spool	£4.50
Dip Board	£3.85
Vero Strip	£1.25

### NI-CADS

PP3	4.45, 4/16.00
AA	0.95, 10/8.00
HP11	2.30, 4/8.50
C	2.35, 4/8.75

### VOLTAGE REGULATORS

78L05/12/15	30p
7805/12/15	55p
7905/12/15	65p
LM317K	£3.50

### MENTOR

Kit from £1250  
 NEPTUNE - for clean hydraulic power -  
 - tap water is the hydraulic fluid  
 Kit from £1725  
 MENTOR Kit from £345

ORDERING: All components are brand new and to full specification. Please add 45p postage/packing (unless otherwise specified) to all orders then add 15% VAT to the total. Either send cheque/cash/postal order or send/telephone your Access or Visa number. Official orders from schools, universities, colleges etc most welcome. (Do not forget to send for our 1985 catalogue — only 65p per copy.) All orders despatched by return of mail. NEW RETAIL 1000 sq ft shop now open Mon-Fri 9.00-5.00. Sat 9-12.00.



**1985 CATALOGUE**  
 Our latest 123 page catalogue over 4000 items fully illustrated. Send 65p now for your copy. FREE with orders over £5.00.

## FREE CAREER BOOKLET

**Train for success, for a better job, better pay**  
 Enjoy all the advantages of an ICS Diploma Course, training you ready for a new, higher paid, more exciting career. Learn in your own home, in your own time, at your own pace, through ICS home study, used by over 8 million already! Look at the wide range of opportunities awaiting you. Whatever your interest or skill, there's an ICS Diploma Course there for you to use. Send for your FREE CAREER BOOKLET today — at no cost or obligation at all.

**GCE** Over 40 'O' and 'A' Level subjects from which to choose. Your vital passport to career success.

COMPUTER PROGRAMMING	<input type="checkbox"/>	RADIO AMATEUR'S LICENCE	<input type="checkbox"/>
ELECTRONICS	<input type="checkbox"/>	INTERIOR DESIGN	<input type="checkbox"/>
COMMERCIAL ART	<input type="checkbox"/>	WRITING FOR PROFIT	<input type="checkbox"/>
TV, RADIO & AUDIO SERVICING	<input type="checkbox"/>	CAR MECHANICS	<input type="checkbox"/>
BOOK-KEEPING & ACCOUNTANCY	<input type="checkbox"/>		<input type="checkbox"/>

Please send FREE DETAILS for the course ticked above.

Name

Address

P.Code

**ICS** ICS Dept. EDS 35  
 8 Elliot Place  
 Clydeaway Centre  
 Glasgow G3 8EF

041 221 2926  
 or 01 622 9911 (all hours)

**CACC**

# ROBOTS

## For Education, Training and Industry

NEPTUNE I  
 NEPTUNE II  
 NEPTUNE - for clean hydraulic power - tap water is the hydraulic fluid  
 MENTOR Kit from £345

NEPTUNE I 6 axes; 8 bit control system; 2.5Kg capacity; 1120mm reach.  
 NEPTUNE II 7 axes; 12 bit control system; 2.5Kg capacity; 1120mm reach.  
 MENTOR DC servo desktop robot; 8 bit control system; 300gm capacity; 420mm reach.  
 Robots programmed from keyboard or hand-held simulator (model robot).

Robots may also be taught by 'lead by the nose' method.  
**Extensive software is supplied free with each robot.**  
 Leads available for connection to BBC, ZX Spectrum, Apple IIe, Commodore 64 and VIC 20.  
 Most other micros are also easily usable with these robots.

Please phone for brochure; 0264 50093.  
**West Portway Industrial Estate, Andover SP10 3PE.**  
 A private and independent company giving prompt, personal service.

**Cybernetic Applications**



### MARTIAN HEAD

Much has been heard recently about the 'head' on Mars, and I think I must deal with it—though as briefly as I can!

In the 1970s the *Viking* landers came down on Mars, one in the ochre desert of Chryse and the other in Utopia. Both sent back invaluable data. No definite traces of Martian life were found, but we learned a great deal about the nature of the surface and the atmosphere.

We were also able to study pictures of the areas round the grounded spacecraft. One rock bore an almost uncanny resemblance to a human face. Of course this was pure coincidence; but now, for some curious reason, there have been sensational reports that we really are seeing a piece of Martian artwork!

I have examined the evidence and the relevant pictures. There is absolutely no doubt that we are dealing with nothing more than a natural rock, with its attendant light and shade effects. Enough said.

There have been comments about the Solar Polar Mission, a joint ESA-NASA venture now officially renamed *Ulysses*. It is scheduled for launching in May 1986, from the Shuttle, and will travel out as far as Jupiter, passing round the giant planet and then coming back to pass over the Sun's poles in 1990. All kinds of investigations will be carried out, ranging from solar wind studies to measurements of the solar and interplanetary magnetic fields.

The number of asteroids with well-known orbits continue to increase. The total has now passed the three thousand mark. However, the four spaceprobes which have so far passed through the asteroid belt (two *Pioneers* and two *Voyagers*) have emerged unscathed, so it may be that there is less scattered material there than was once feared. No doubt time will tell.

### BETA PICTORIS

The southern constellation of Pictor, the Painter, is by no means conspicuous. It contains no star brighter than the third magnitude, and has no obvious shape. We remember it mainly because a fairly bright nova flared up in it in 1925. Pictor is not visible from Britain; it is too far south, and it is in fact close to Canopus, which is the brightest star in the sky apart from Sirius (and is much more luminous and remote).

The second star of Pictor is Beta Pictoris,

of magnitude 3.8; it has no individual name. It is white, with an A-type spectrum; its distance from us is 78 light-years, and it is approximately 60 times as luminous as the Sun. Up to now it has been dismissed as a very ordinary star indeed. But Beta Pictoris has suddenly leaped into the scientific headlines.

The story began in 1983, with observations carried out from the infra-red astronomical satellite *IRAS*. It is fair to say that *IRAS* was one of the greatest successes of the space age so far. It transmitted for the best part of a year, discovering thousands of new infra-red sources and also detecting comets, dust-tails to known comets and even a strange asteroid which ventures perilously close to the Sun.

When the equipment was being checked, infra-red excesses were found associated with several stars, including Vega and Fomalhaut. This was attributed to the presence of cool material which might well be planet-forming.

One star studied in this way was Beta Pictoris, and a few months ago two American astronomers, Drs. Bradford Smith and Richard Terile, decided to make an optical investigation. They went to the Las Campanas Observatory in Chile, where conditions are exceptionally good. Las Campanas comes under the same management as Mount Wilson in California, and like Mount Wilson it has a 100-inch reflecting telescope—the main difference is that the Mount Wilson 100-inch is old (it was completed in 1917) whereas the Las Campanas instrument is ultra-modern.

Smith and Terile used the telescope together with a CCD or Charge-Coupled Device, which is much more sensitive than any photographic plate. The results were startling. Beta Pictoris is surrounded by a disc of material which extends nearly 50,000 million miles from the star. The disc is seen nearly edge-on, and is probably no more than a few hundred million years old.

### LIFE FORMING

It is possible to make a shrewd estimate of the composition of the disc. Ices, silicates and carbonaceous substances are strong candidates. Now, these are the materials from which the planets in our own Solar System were formed well over 4,000 million years ago. Analysis of the density of the Beta Pictoris ring material indicates that planets may have been formed there too, and by extrapolation it seems that the interior particles in the disc have been swept away, possibly by orbiting planets.


What can we make of all this?

The main importance is that for the first time we have actually seen what may be an extra-solar planetary system; up to now we have had to rely either upon infra-red work, or upon the admittedly very uncertain measurements of nearby stars which 'wobble' slowly as they are perturbed by associated bodies which may be of planetary rather than stellar mass. There is absolutely no doubt that the Beta Pictoris shell does exist, and although we cannot be over-confident it seems that a planetary system is much the most likely explanation for it.

Beta Pictoris itself is a normal star; neither particularly luminous nor particularly dim, neither a cosmic heavyweight nor a stellar minnow. And if it is indeed the centre of a family of planets, the evidence in favour of numerous similar systems becomes almost overwhelmingly strong.

Investigations are proceeding, and there is every hope that more discs of the same kind will soon be found round other stars. Whether any of these hypothetical planets are inhabited is quite a different matter, but there seems no valid reason why not. Beta Pictoris has taught us a great deal, even though as yet we cannot claim to have done more than scratch the surface of the main problems.

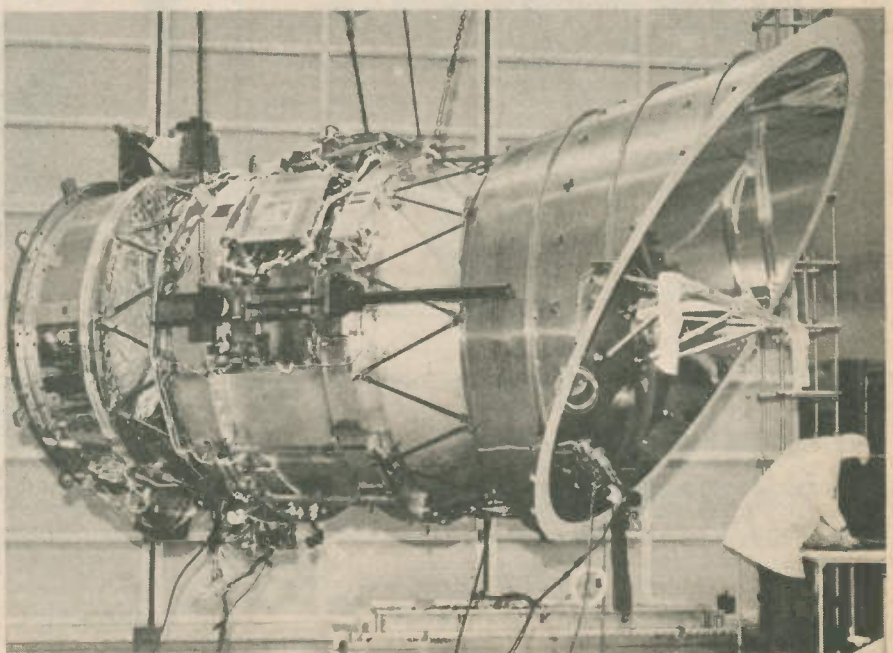**IRAS (International Infra-red Astronomical Satellite), shown here on test at the Fokker B.V. plant in the Netherlands. This was probably one of the greatest successes of the space age so far.**



## THE SKY THIS MONTH

Throughout this month the early-evening sky continues to be dominated by the planet Venus. It reaches its greatest brilliancy on 26 February, when its magnitude will be 4.3. Under such conditions it is easily found with the naked eye even when the sky is still bright, and is obvious with binoculars—though I must again repeat my oft-given warning never to sweep around with binoculars or a telescope unless the Sun is completely below the horizon.

As Venus draws in towards inferior conjunction, which will be reached on 3 April, its phase decreases. The amount of disc illuminated is 44 per cent at the beginning of February and only 25 per cent into March.

This being so, it may seem strange that Venus is at its brightest when less of the sunlit face is turned toward us. The answer is that as the phase decreases, the apparent diameter increases, because the planet is coming closer to us. At its very closest, of course, it is at inferior conjunction—more or less between the Earth and the Sun—and cannot be seen at all.

The only chances of seeing Venus when it is directly aligned with the Sun occur at the times of transit. However, the last transit took place as long ago as 1882, and the next will not be until 2004.

Of the other planets, Mercury is to all intents and purposes out of view; Jupiter and Saturn are morning objects, but badly placed; Mars is still visible in the evening, but its magnitude is now only 1.4, so that no telescope will show much on its surface. The apparent diameter of Mars is now less than 5 seconds of arc.

### HALLEY'S COMET

Halley's Comet is now under regular observation, and is becoming brighter as it moves inward, but it is still

beyond the reach of any but giant telescopes. However, there is one mildly encouraging sign. The comet is starting to become active earlier than expected, and it may eventually be brighter than was at first predicted, though it will certainly not be spectacular—as it has been at some past returns. The most we can really hope from Britain is that it will become a naked-eye object late this year.

Among the stars, Orion remains dominant. It is high in the south during February evenings, and is quite unmistakable, together with its brilliant retinue. Sirius also is at its best. It is a pure white star of spectral type A, but because it is so bright, and because it is never very high up as seen from Britain, it seems to flash various colours of the rainbow.

Sirius is, in fact, the supreme "twinkler", though when seen from countries south of the equator, where it can pass overhead, it looks much steadier. It is rather surprising to remember that Sirius is an ordinary Main Sequence star, a mere 26 times as powerful as the Sun—whereas Rigel in Orion, which looks well over a magnitude and a half fainter, is equal to 60,000 Suns combined.

There are opportunities this month for seeing Algol, in Perseus, at minimum light. Algol is an eclipsing binary. Its 'rest' magnitude is just below 2, approximately equal to the Pole Star, but during mid-eclipse the magnitude falls to below 3.

Fading takes 4 hours, and minimum lasts for only 20 minutes, after which a further 4 hours is needed for Algol to regain its lost light. Minima occur at 3.1 hours GMT on 18 February, 23.9h GMT on 20 February, and 20.7h GMT on 23 February. Of course, there are minima every  $2\frac{1}{2}$  days; I merely give these as being convenient to observe.

## MJI 102 — A NEW NUMBER IN BRITISH 'SCOPES . . .



Simple Operation — Fully Automatic Trigger —  
Single Beam — 100mV to 50V/Div. — Sensitivity —  
10mS to 1 $\mu$ S/Div. — Sweep — X - Y Facility —  
Lightweight and Compact

and at a very lightweight price

SEND FOR DETAILS NOW!

**£129<sup>95</sup>**

## MJ Instruments

HILLTOP HOUSE, THINGOE HILL,  
BURY St. EDMUNDS, SUFFOLK, IP32 6BE. Tel: (0284) 67104

## hobbyboard

### Printed Circuit Hardware & Component Catalogue

- ★ COPPER CLAD LAMINATES
- ★ PHOTO-RESIST LAMINATE & CHEMICALS
- ★ PRINTED CIRCUIT DRAUGHTING AIDS
- ★ VERO BOARD & PROTOTYPING SYSTEMS
- ★ CONNECTORS/CASES/GENERAL HARDWARE
- ★ SELECTION OF COMPONENTS
- ★ EDUCATIONAL COMPUTING
- ★ ELECTRONICS KITS

Send for your free catalogue to:



A FARNELL ELECTRONICS COMPANY

KELAN ENGINEERING LTD.  
Circuit Products & Components Division.  
27-29 Leadhall Lane, Harrogate.  
North Yorkshire. HG2 9NJ.  
Tel: (0423) 870938.

PE/3/85

NAME .....

ADDRESS .....

# Sequential Logic Techniques Part 6

M. TOOLEY BA and D. WHITFIELD MA MSc CEng MIEE

In Part Five of the series we looked at a family of devices which allow us to route several incoming data signals along the same path. We shall now look at the opposite problem; that of connecting a single incoming line to one of several output lines.

When explaining the action of the de-multiplexer we can, as before, use a simple switch analogy. A four-way de-multiplexer is, like its multiplexer counterpart, equivalent to nothing more than a single pole four-way switch. The important distinction is that, in the case of the data multiplexer data is being selected from one of four incoming signal lines whereas, in the case of the de-multiplexer, data is being routed to one of four outgoing lines. This vital difference is illustrated in Fig. 6.1. Furthermore, since digital multiplexers and de-multiplexers rely on logic gates (which are unidirectional devices) for their operation, the two functions are quite distinct.

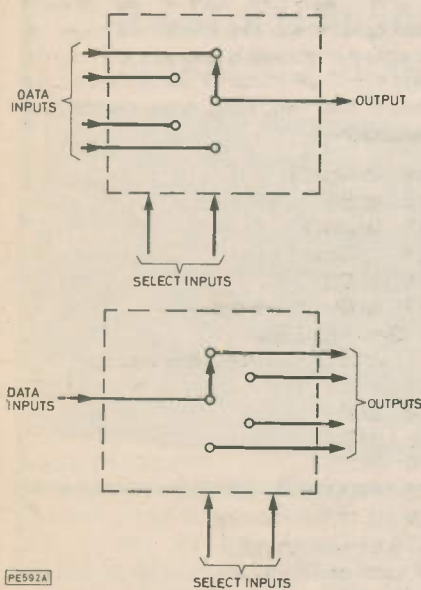


Fig. 6.1. Simplified switch equivalents of four-way data multiplexers and de-multiplexers; (a) four-way multiplexer, (b) four-way de-multiplexer

## THE 74LS139

The 74LS139 is a common example of a data de-multiplexer which contains two independent four-way de-multiplexers within a 16-pin d.i.l. package. Each four-way de-multiplexer has a single active-low enable input,  $\overline{EN}$ , two select inputs,  $S_0$  and  $S_1$ , and four outputs, 0 to 3. The pin connections for the 74LS139 are shown in Fig. 6.2. As for its data multiplexer

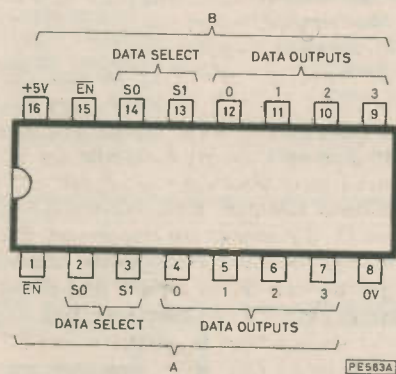


Fig. 6.2. Pin connections for the 74LS139

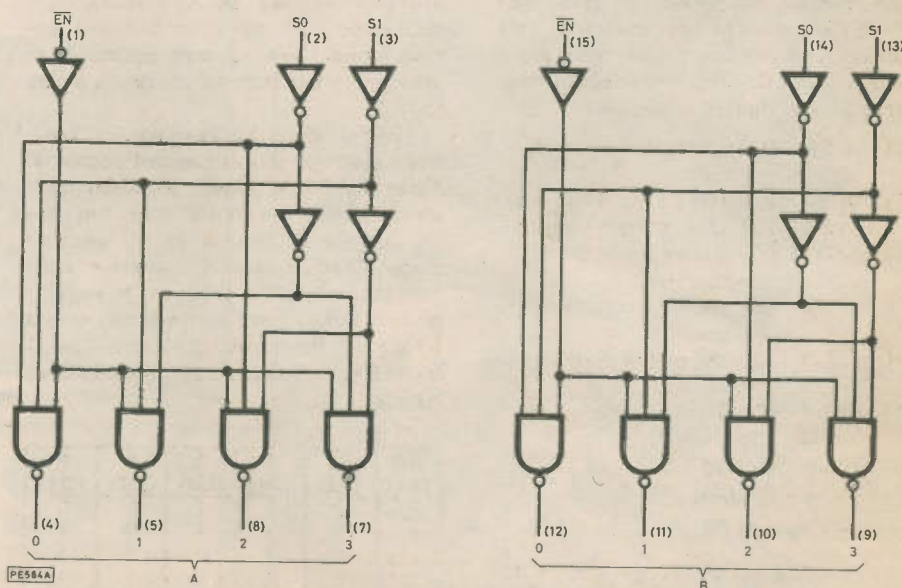


Fig. 6.3. Internal logic of the 74LS139

counterpart (the 74LS153) the two halves of the device (referred to as A and B) are conveniently brought out to pins on opposite sides of the package; the A-side using pins 1 to 7 whilst the B-side uses pins 9 to 15. The supply, which follows the normal convention of pin-8 (0V) and pin-14 (+5V) is common to both halves of the device.

The internal logic of the 74LS139 is shown in Fig. 6.3. This shows how the two select signals,  $S_0$  and  $S_1$ , are gated with the enable signals,  $\overline{EN}$ , in each of the four three-input NAND gates. It should be noted that, since NAND rather than AND gates are employed, the outputs go to logic 0 in the selected state and revert to logic 1 in the de-selected state. This is important since, in typical applications, the 74LS139 is used in conjunction with other devices which have active low select or enable inputs. If this is a little hard to follow don't despair as we shall be returning to this topic with a practical example a little later!

The complete truth table for the 74LS139 is shown in Table 6.1. This



# SEQUENTIAL LOGIC

INPUTS			OUTPUTS			
EN	S0	S1	3	2	1	0
1	x	x	1	1	1	1
0	0	0	1	1	1	0
0	1	0	1	1	0	1
0	0	1	1	0	1	1
0	1	1	0	1	1	1

x = don't care

**Table 6.1. Complete truth table for the 74LS139**

truth table is, of course, identical for each half of the device. When the  $\overline{EN}$  line is at logic 1 all four outputs go to logic 1 regardless of the state of the select inputs, S0 and S1. When both select inputs are at logic 0 and the  $\overline{EN}$  line is taken low, the 0 output line goes to logic 0 (the other three outputs remain at logic 1). With S0 at logic 1 and S1 at logic 0 the 1 output line goes to logic 0, and so on.


Developing the four-way switch analogy a little further, it should be noted that, the enable line effectively acts as a data signal input; the selected output reflecting the state of this line. To further explain this action, if we have selected output 0 (by placing a logic 0 on both S0 and S1), the 0 output line will follow the logical state of the EN input; i.e. when EN goes low the 0 output will go low and when  $\overline{EN}$  goes high the 0 output will go high.

We shall now turn our attention to a practical investigation of the 74LS139 using the circuit arrangement shown in Fig. 6.4. It should be noted that only one half of the device is used. The 74LS139 should be inserted into socket C of the Logic Tutor with pin-1 aligned with C1. The following connections should then be made:—

- C1 to S3 (S3 acts as the enable input)
- C2 to S1 (S1 acts as the S0 input)
- C3 to S2 (S2 acts as the S1 input)
- C4 to D1 (D1 shows the state of output 0)
- C5 to D2 (D2 shows the state of output 1)
- C6 to D3 (D3 shows the state of output 2)
- C7 to D4 (D4 shows the state of output 3)
- C8 to 0V (common)
- C16 to +5V (supply)

(A total of 9 links)

The enable input is produced by latching switch, S3, which should initially be adjusted to produce a logic 1 (disabling the de-multiplexer). The two

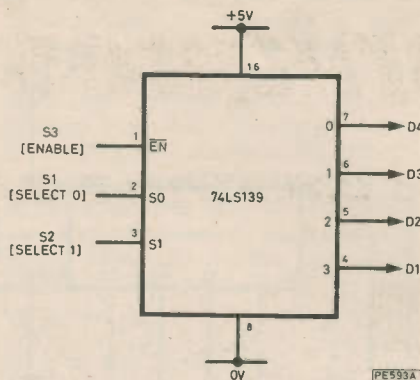

**Fig. 6.4. Circuit arrangement used in the practical investigation of the 74LS139**

momentary action switches, S1 and S2, will in the absence of a depression produce logic 0 on both of the select inputs, S0 and S1. In this state all four of the output indicating l.e.d.s, D1 to D4, should be illuminated.

S3 should now be adjusted to produce a logic 0 to enable the de-multiplexer. D1 should now become extinguished showing that, with the S0 and S1 inputs both at logic 0, output 0 has been selected. Now, leaving S3 at logic 0, S1 should be depressed. D2 will then become extinguished showing that, with S0 at logic 1 and S1 at logic 0, output 1 has been selected.

S1 should then be released and S2 depressed. D3 will now be extinguished confirming that, with the S1 input at logic 1 and the S0 input at logic 0, output 2 is selected. Finally, S1 and S2 should be simultaneously depressed. D4 will then become extinguished showing that output 3 is selected when both select inputs are at logic 1.


The results of this investigation have been summarised in the truth table of Table 6.2. This table has been constructed on the basis that the de-multiplexer is always in its enabled state. Readers should, however, confirm that whenever S3 is set to logic 1, all four outputs will immediately revert to logic 1 (illuminating all four l.e.d.s) regardless of the state of the two select inputs.

S0 (S1)	S1 (S2)	3 (D4)	2 (D3)	1 (D2)	0 (D1)
0	0	1	1	1	0
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	1	1	1

**Table 6.2. Truth table for the practical investigation of the 74LS139**

## FOUR-CHANNEL SEQUENCER USING THE 74LS139

In Part Four we showed how a sequencer could be constructed using a shift register. We shall now consider an alternative arrangement based on a

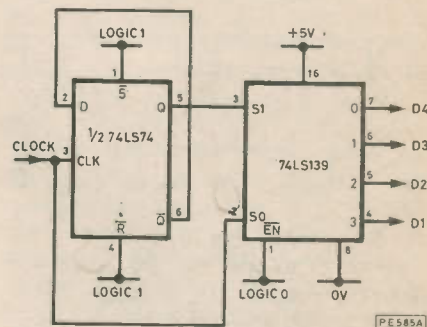

**Fig. 6.5. Four-channel sequencer using the 74LS139**


74LS139 de-multiplexer as shown in Fig. 6.5.

The two select inputs of the 74LS139 are fed from the outputs of a simple binary divider configured around a 74LS74 D-type bistable element. The select inputs are thus supplied with a binary count sequence and thus a low is transferred from one output of the de-multiplexer to the next on each falling clock edge.

The 74LS139 should be left in socket C whilst the 74LS74 should be inserted in socket B checking, as usual, that pin-1 aligns with B1 on the Logic Tutor. The following connections are required:—

- B1 to logic 1
  - B2 to B6
  - B3 to clock
  - B4 to logic 1
  - B5 to C3
  - B7 to 0V (common)
  - B16 to +5V (supply)
  - C1 to logic 0 (active-low enable)
  - C2 to B3
  - C4 to D1
  - C5 to D2
  - C6 to D3
  - C7 to D4
  - C8 to 0V (common)
  - C16 to +5V (supply)
- (A total of 15 links)

The sequence produced by the circuit should follow that shown in the timing diagram of Fig. 6.6. This shows that, at any time, three of the output indicating l.e.d.s are illuminated and one is extinguished. The effect is that a logic 0

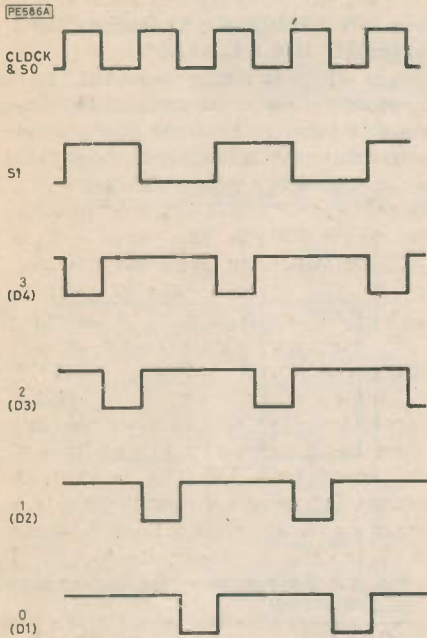

**Fig. 6.6. Timing diagram for the four-channel sequencer**


circulates from D4 → D3 → D2 → D1 and then restarts at D4.

### TIME DOMAIN MULTIPLEXING

Thus far we have only separately considered the actions of the multiplexer and de-multiplexer. The time has now come for us to put these two devices together in an arrangement which allows us to send several data signals over a common path and yet still separate them again at the far end.

Since we have restricted ourselves to the use of four-way multiplexers and de-multiplexers in this series we shall provide for four inputs at the 'sending end' and four outputs at the 'receiving end'. The multiplexer at the sending end provides us with a means of routing each data line to the common signal path for a pre-determined time whilst the de-multiplexer at the receiving end connects the common signal path to each output line for a similar pre-determined time.


It is, of course, important to ensure that the data appearing on each data input line is correctly routed to the corresponding data output line. It should, therefore, be apparent that some means of synchronising the data at the sending and receiving ends of the path is of paramount importance. To this end we shall need to generate a common set of select signals at each

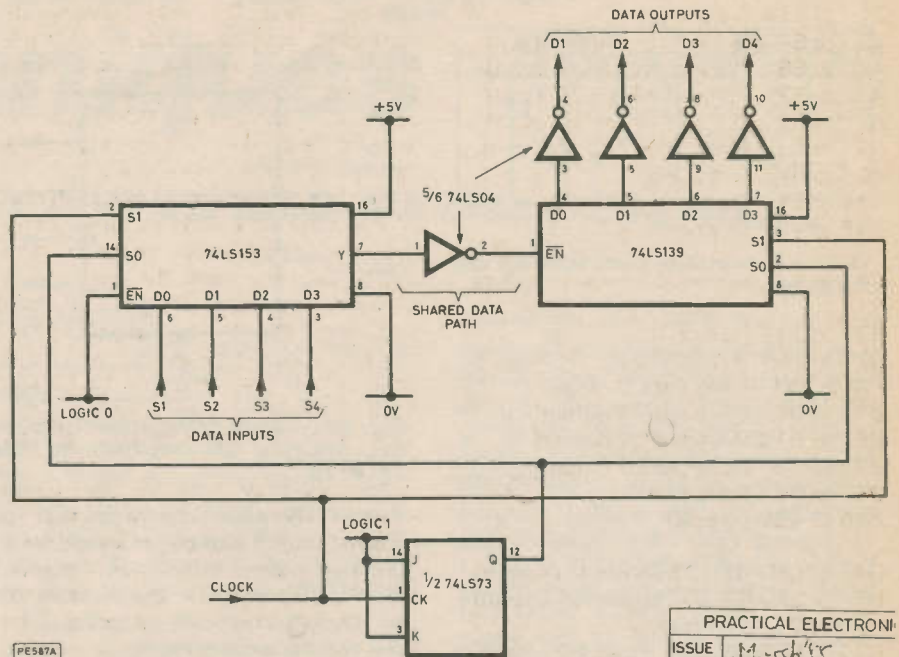

**Fig. 6.7. Time domain multiplexing using 74LS153 and 74LS139 devices**

end of the path.

Data communication systems of this type rely on the availability of a common clock signal at both the sending and receiving ends. At this point we should perhaps point out that, in most practical data communication systems, we would almost certainly prefer to

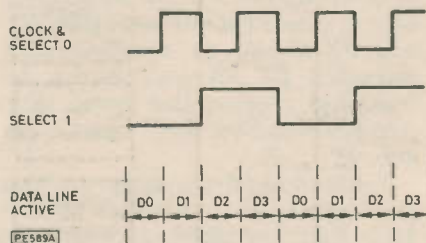

**Fig. 6.8. Timing diagram for the clock and select lines of the arrangement shown in Fig. 6.7**

have an asynchronous arrangement in which the data was 'self-clocking'.

The circuit arrangement employed in our practical investigation of time domain multiplexing is shown in Fig. 6.7. The common select signals are generated from the Logic Tutor's internal clock operating in conjunction with a single-stage binary divider based upon a 74LS73 J-K bistable. Fig. 6.8 shows the timing diagram of the clock and select input lines. Each data line is activated for half of the clock cycle

period and follows the sequence, D0, D1, D2, and finally D3. The sequence is then repeated with one complete cycle of all four data inputs occurring in a time equal to one cycle of the signal on the S1 line.

The four data inputs are applied to a 74LS153 multiplexer and, from there, follow a time shared common data path. Since the 74LS139 has an active-low enable input, a single inverting stage (using a 74LS04) is included in the common data path. Furthermore, due to the inverting action of the internal logic of the 74LS139 (remember that the selected output line goes low whilst the other three lines remain high) we shall need to invert each of its data outputs. This is achieved using a further four inverting gates of the 74LS04.

The integrated circuits should be inserted into the Logic Tutor in the following manner:—

- Socket A = 74LS153
- Socket B = 74LS139
- Socket D = 74LS04
- Socket E = 74LS73

In each case it is, as usual, important to check that pin-1 of the integrated circuit is correctly aligned with pin-1 of the Logic Tutor's connecting strip.

The following links are required:—

- A1 to 0V (active-low enable)

A2 to E14 (select 1)  
 A3 to S4 (S4 acts as the D3 input)  
 A4 to S3 (S3 acts as the D2 input)  
 A5 to S2 (S2 acts as the D1 input)  
 A6 to S1 (S1 acts as the D0 input)  
 A7 to D1 (time shared data output)  
 A8 to 0V (common)  
 A14 to E1 (select 0)  
 A16 to +5V (supply)

B1 to D2 (inverted time shared data input)  
 B2 to A14 (select 0)  
 B3 to E14 (select 1)  
 B4 to D3 (inverted D0 output)  
 B5 to D5 (inverted D1 output)  
 B6 to D11 (inverted D2 output)  
 B7 to D13 (inverted D3 output)  
 B8 to 0V (common)  
 B16 to +5V (supply)

D4 to LED D1 (D1 shows D0 output)  
 D6 to LED D2 (D2 shows D1 output)  
 D7 to 0V (common)  
 D10 to LED D3 (D3 shows D2 output)  
 D12 to LED D4 (D4 shows D3 output)  
 D16 to +5V (supply)

E1 to clock  
 E2 to logic 1  
 E3 to logic 1  
 E4 to +5V (supply)  
 E13 to 0V (common)  
 E16 to E3

(A total of 31 links)

All four of the input switches, S1 to S4, should initially be adjusted to produce logic 0 data inputs. In this state, all four of the output indicating l.e.d.s should be extinguished showing that all four data outputs are similarly at logic 0.

Now depress, and hold down, S1 to produce a logic 1 on the D0 input line. The l.e.d. indicator D1 will shortly become illuminated showing that the D0 output has gone to logic 1. Note,

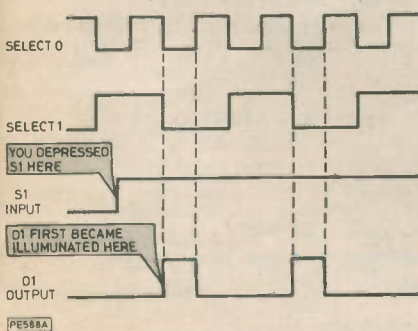


Fig. 6.9. Timing diagram for a signal on the D0 line in Fig. 6.7

however, that D1 only remains illuminated for the duration of each alternate low cycle of the clock (compare the indications produce by the clock i.e.d., D9 and the D0 output indicating i.e.d., D1). The corresponding timing diagram is shown in Fig. 6.9.

Readers should now check each one of the other data lines in turn, noting the correspondence between the switch depressed and the l.e.d. which becomes activated. Finally, all four switches should be adjusted to produce a logic 1 on all four data input lines. In this state the four l.e.d.s will flash in sequence, clearly showing the time shared characteristic of the arrangement.

Readers may now be wondering whether there is any way that a received logic 1 can be preserved for a period equivalent to the select 1 signal, thus maintaining the logical state of the output. This can, of course, be achieved by simply adding a suitable bistable latch to each data output such that data is latched each time the respective data line is enabled. Furthermore, if we were to use bistable latches in which the  $\bar{Q}$  output was

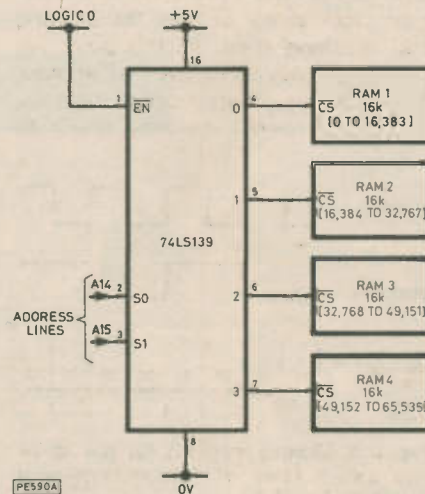


Fig. 6.10. Circuit arrangement used in the 64K memory address space decoder (Note: addresses are specified in decimal)

made available, we could dispense with the four output inverters. We will, however, leave this particular exercise for the more adventurous reader!

## ADDRESS DECODING

Finally, we shall consider a typical example of the use of a de-multiplexer

in the form of an address decoder for use in a microcomputer system. Let's assume that we have a 64K memory space which is occupied by four 16K random access memories (RAM). The data inputs and outputs of these memories are all connected to the system data bus (conventionally 8 bits wide). Each RAM is assumed to have fourteen address input lines (A0 to A13 inclusive) and one active-low chip select (CS) line. The address lines on each RAM are connected to the similarly numbered address line on the system address bus hence, unless we do something to prevent a conflict, we would find that all four RAM devices were being written to or read from at the same time. What is needed, of course, is a means of decoding the two most significant address lines, A14 and A15, in order to activate the four RAM chip select lines. A suitable decoding

ADDRESS LINES		CHIP SELECTED	ADDRESS RANGE (decimal)
A15	A14		
0	0	RAM 1	0 to 16,383
0	1	RAM 2	16,384 to 32,767
1	0	RAM 3	32,768 to 49,151
1	1	RAM 4	49,152 to 65,535

Table 6.3. Truth table for decoding the 64K address space

scheme is shown in Table 6.3. In effect, we have divided the total 64K address space into four blocks of 16K, each associated with a particular RAM. RAM1, for example, corresponds to the lowest 16K (decimal addresses 0 to 16,383 inclusive) whilst RAM4 corresponds to the highest 16K (decimal addresses 49,152 to 65,535 inclusive). RAM1 is selected whenever address lines A14 and A15 are both at logic 0 whilst RAM4 is selected when these two address lines are both at logic 1.

The problem of decoding the two most significant address lines is easily resolved using a 74LS139 in an arrangement similar to that shown in Fig. 6.10. The inverted logic of the 74LS139's outputs being just what is required for the active-low RAM chip select lines. (This, of course, is no mere coincidence!)


**NEXT MONTH:** We shall be concluding the Sequential Logic Techniques series with a look at binary full adders. We shall also include an Index to the complete series.

# FIND YOUR WAY THROUGH THE DIGITAL ELECTRONICS MAZE

First there was **SUPERKIT**

and now ...  
**NEW**

## SUPERKIT II

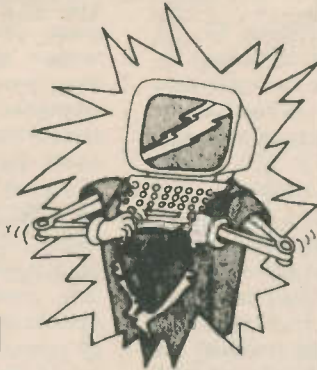

This practical self-instruction kit has been developed to extend the original beginners' **SUPERKIT**. **SUPERKIT II** includes an instruction manual and many more components, enabling you to design and use adders, subtractors, counters (ripple, up/down, synchronous, decade and Gray code), registers, pattern recognisers and 7-segment displays. You need the board and components from **SUPERKIT** to enable you to build the circuits in **SUPERKIT II**. Together the two kits provide an excellent introduction to digital electronics - what really goes on inside a computer.

**SUPERKIT (SUP) £22.00 SUPERKIT II (SUP II) £16.00**

**Special price £35.00 for both (SUP + II) (inc. VAT and p & p)**

The **SUPERKIT** series is backed by our theory courses, **DIGITAL COMPUTER LOGIC** (beginners' course), which covers the design of logical circuits, and **DIGITAL COMPUTER DESIGN** (more advanced), which covers the design of digital computers. **MICROPROCESSORS AND MICROELECTRONICS** teaches you what a microprocessor is and what it can do.

**DIGITAL COMPUTER LOGIC (DCL) £7.00**

**DIGITAL COMPUTER DESIGN (DCD) £9.50**

**MICROPROCESSORS AND MICROELECTRONICS (MIC) £6.50**

Please send for full information on these and our other courses.

**GUARANTEE** If you are not completely satisfied, return the item to us within 28 days for a full refund. All prices include worldwide surface postage (ask for prepayment invoice for airmail). Allow 28 days for delivery in UK. Overseas payment by International credit card or by bank draft drawn on a London bank.

**CAMBRIDGE LEARNING LTD, Unit 28, Rivermill Site, FREEPOST, St Ives, Cambs PE17 4BR, England.**

Tel: 0480-67446

VAT No 313026022 Transcash No 2789159 Reg No 1328762

Please send me (initial letters used):

..... SUP	@ £22.00	..... DCL	@ £7.00
..... SUP II	@ £16.00	..... DCD	@ £9.50
..... SUP + II	@ £35.00	..... MIC	@ £6.50

I enclose a cheque/PO payable to Cambridge Learning Ltd for £.....

Please charge my ..... credit card.

No ..... Expiry date .....

Telephone orders from credit card holders accepted on 0480 67446 (24 hrs)

Name .....

Address .....

Signature .....



**CAMBRIDGE LEARNING**

Unit 28, Rivermill Site, FREEPOST, St Ives, Cambs PE17 4BR, England.



# VIDEO NASTIES?

Pictures that wobble, won't lock or suffer from noise bars? - machines that won't latch, lace or light up? - our pages are full of guidance on VCR servicing problems. TV too - chopper, colour and linearity problems of every sort. Plus news and information on technical developments. March issue features...

**ELECTRONIC SPEECH FOR TVS AND VCRs**  
The theory of synthesised speech and a practical circuit that gives clear speech.



### ORIC AND SINCLAIR COMPUTERS



Oric 1 computer 48K **£85 (£82) £92**. Oric Atmos computer 48K **£171 (£158) £168**. Oric Colour Printer **£134 (£123) £140**. Sinclair flat screen TV **£113 (£105) £115**. Sinclair Spectrum Plus Computer **£182 (£176) £187**. Sinclair QL Computer **£406 (£385) £410**. Sinclair Spectrum 48K **£131 (£131) £143**. Microdrive **£51 (£50) £60**. RS232 interface 1 **£51 (£50) £60**. Special offer:- Microdrive + Interface 1 + 4 cartridges **£102 (£100) £120**. Blank microdrive floppy disc interface for Spectrum **£102 (£92) £112**. (See Cumana disc section for suitable disc drives). Fuller FDS keyboard for spectrum **£52 (£52) £52**. Fuller master unit **£56 (£56) £62**. Interface 2 **£20.45 (£20) £24**. 32K memory upgrade kit for 16K spectrum (issue 2 and 3 only) **£31 (£28) £30**. Spectrum Centronics printer interface **£51 (£47) £52**. ZX printer has been replaced by the Alphacom 32 **£71 (£69) £82**. 5 printer rolls (state whether Sinclair or Alphacom) **£13 (£16) £21**. ZX81 computer **£45 (£44) £54**. 16K ram packs for ZX81 **£28 (£25) £30**.

### COMMODORE COMPUTERS

Commodore C16 Starter Pack **£145 (£142) £162**. Commodore Plus/4 **£305 (£281) £301**. Commodore 64 **£222 (£215) £235**. Converter to allow most ordinary mono cassette recorders to be used with the Vic 20 and the Commodore 64: **£9.78 (£9) £11**. Bargain package:- cassette converter + compatible cassette recorder **£37 (£38) £44**. Commodore cassette recorder **£43 (£44) £50**. Printer interfaces for Vic 20 and the Commodore 64:- Centronics **£45 (£41) £46**. RS232 **£45 (£41) £46**. Disc drive **£233 (£209) £234**. 1520 printer/plotter **£165 (£149) £159**. MPS801 Printer **£235 (£220) £245**. Light pen **£29 (£29) £33**.

### SWANLEY ELECTRONICS

The Computer Export Specialists  
Dept PE, 32 Golsel Rd., Swanley, Kent BR8 8EZ, England.

Tel: Swanley (0322) 64851. Official orders welcome. UK prices are shown first and include post and VAT. The second price in brackets is for export customers in Europe and includes insured air mail postage. The third price is for export customers outside Europe (including Australia etc) and includes insured airmail postage.


### ACORN COMPUTERS

Electron **£173 (£179) £199**. BBC Model B **£404 (£357) £387**. Kenda double density disk interface system **£149 (£131) £141**. See below for suitable disc drives.

### CUMANA DISC DRIVES

To suit disc interfaces of Sinclair spectrum, BBC B and Videogenie. Single:- 40 track single sided **£176 (£158) £178**. 40 tr double sided **£218 (£195) £215**. 80tr ss **£207 (£186) £206**. 80tr ds **£234 (£209) £229**. Dual:- 40tr ss **£299 (£280) £320**. 40tr ds **£395 (£353) £393**. 80tr ss **£372 (£334) £374**. 80tr ds **£437 (£390) £430**.

### PRINTERS

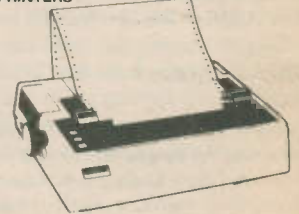


Oki Microline 80 **£138 (£135) £165**. Brother HRS **£162 (£146) £170**. Shinwa CTI CPA80 **£237 (£228) £258**. Cannon PW1080A **£382 (£344) £374**. Epson RX80 **£277 (£251) £282**. Epson RX80F/T **£314 (£286) £316**. Epson FX80 **£399 (£358) £388**. Combined matrix printers and electric typewriters:- Brother EP22 **£173 (£166) £186**. Brother EP44 **£258 (£235) £260**. MCP40 Oric colour printer/plotter **£134 (£123) £140**. Interfaces to run the above printers from Vic and the Commodore 64 **£45 (£41) £46**. We can supply interfaces to run the above printers from Sharp computers **£58 (£52) £55**.

### UK101, SUPERBOARD AND VIDEOGENIE

We still support these Computers. Write for our list.

### COMPUTER REPAIRS

We offer a world-wide repair service. Write for a quotation.



# INDUSTRY NOTEBOOK

By Nexus



## Public Ownership

The privatisation of British Telecom transformed Britain from a nation of shopkeepers to a nation of shareholders. Up to that point the company with the largest spread of shareholders was ICI with 350,000. Including overseas holdings BT enjoys the support of over 2 million shareholders. The initial figure was some 2.3 million, since whittled down by profit-taking. But this is no bad thing. First-time-ever investors, whether selling for a quick return or holding, have had a sniff of excitement which is bound to encourage them in future investment.

A Labour Party pledge to renationalise BT should they form a government fell on deaf ears. With a substantial share ownership among the electorate my guess is that the threat will be conveniently forgotten and that, in any case, the famous Clause 4 was all but dead before the BT sale. Old style public ownership is out, new style public participation is in.

## Self-Interest

The BT unions, following Labour policy, opposed privatisation and recommended members to ignore the share offer. In the event the free shares were taken up with gusto and the vast majority of the employees bought extra shares.

This wasn't the only example of self-interest triumphing over ideology. Strikes in the docks and in the automobile industry collapsed last year through lack of popular support. Steelmen resisted all attempts to entice them to limit output which supposedly would help the miners in their struggle. And the most extraordinary happening of all was union members taking their leaders to court.

The mining dispute, whatever the outcome, is bound to end in tears. A soap opera dragging on through months of farce as well as tragedy. The industrial result is that no government, no company, no householder will ever again rely entirely on coal as an energy source. Not the miners

but their leaders have alienated the markets that alone would secure their future.

No wonder that progressive union leaders are seeking better ways to improve their members' prospects and, incidentally, their own standing in society. These include expanding the market instead of destroying it, consulting the membership, perhaps even encouraging share ownership in the enterprises in which they are employed. Self-interest can be just as noble as martyrdom if it also leads to the common good.

## Change

It is of little use looking back to the great battles of 1926 (lost) or 1974 (won) as do the miners' leaders. The world is moving on and moving fast. Enterprise, the freer the better, is the fashion for the 1980s.

As I often mentioned in the past two years, China is the last of the truly great markets to be opened up. The Peoples' Republic has looked at South Korea, Singapore, Hong Kong and Taiwan, all booming economies not entirely unrelated to expertise in production of electronics goods. Why can't China be just like them?

No reason at all except that it is politically as well as practically difficult to dismantle 35 years of Chinese socialist planning overnight. So capitalism remains a dirty word while "responsibility" is newly acceptable. The first of the "responsibility systems" came in agriculture, boosting output and enriching many farmers and merchants. Now it's the turn of industry with incentives generating new levels of efficiency and more cash for workers to spend on luxuries.

Another Chinese euphemism is the "social channel" which, translated, means an individual having a financial holding in a company, in short becoming a shareholder and now permitted in some enterprises and likely to spread. In China, as in the Soviet Union, nobody is officially unemployed although plenty of people are, the blemish on society easily overcome by describing them as "waiting-for-jobs people".

Our most vigorous operator in the Chinese market is Cable & Wireless which has done wonders since privatisation. With a strong base in Hong Kong and the newly acquired Hong Kong Telephone Company there is no shortage of technical expertise and Chinese-speakers to assist the Peoples' Republic in modernising and expanding its communications systems, the prerequisite for industrial growth. In fact such is the technical standing and business trust of the company in Chinese eyes that a number of commentators suggest that C & W as a British flag carrier creates openings for newcomers.

It is interesting, too, to note that socialist France has reverted to capitalism and sound economics and that the newly elected Labour government of Mr Bob Hawke in Australia has swung decidedly right. Who could have imagined six months ago that Mrs Thatcher and President Mitterand, once mutually hostile, would be seen on TV in embraces of friendship? And yet so it is in a changing world.

Change indeed! Ever since semiconduc-

tor production started in bulk it has been the custom to send the part-finished product to the Far East for packaging because of lower wage costs. Today we see building work on a major packaging plant at Irvine, Scotland. The company is Indy, a U.S. specialist, who expect to employ 500 people when in full production.

With rising wage levels and transport costs in the Far East and improved methods of production the crossover point has now been reached when it is cheaper as well as faster to package in Europe. Packaging, in this context, includes die separation, wire bonding, sealing, testing, lead finishing and marking. Far East losses are Scotland's gain where other companies are also researching the economics and possible sites for a European packaging base.

## Oversold

Not that the free enterprise system is faultless. It did well in popularising the home computer and bringing it cheaply to the buyer. But it has done some harm in overselling the product and in a frantic rush to get to market quality has suffered.

In a survey of 100 retail outlets it is reported that the top seller had a return rate of 25 percent, others between 13 and 4 percent. Three-quarters were due to technical faults, the remainder because of customer dissatisfaction.

Product promotion has been first-class in respect of games. Utility is a different matter. Does any household of reasonable intelligence need a computer to handle simple accounts or compile an address book? An amusing exercise, perhaps, but hardly economic, time-saving or necessarily more accurate than old-fashioned pen and paper. As for word-processing you need to go well up-market for a really competent machine.

With so many companies making a fleeting appearance and then disappearing, the Japanese MSX approach has much to commend it with its standardised software and complete compatibility between makes. Critics are saying MSX will retard technical progress but at least customers are safe from loss of supply and know what they are paying for.

## Fifth Generation

We hear a lot about fifth generation computer research with Japan often quoted as potential world leader. Yet at the fifth generation computer conference in Tokyo last November the British were prominent and highly respected contributors. Not least, interest was enormous on the Inmos transputer and its Occam language together with aspects of the British Alvey programme in which industry and the government are equal partners.

It was a surprise to see how open the Japanese were on their government-funded Icot research programme and exchanges between computer scientists from all the leading countries, including Israel, showed that while competition is healthily fierce the outcome will benefit world industry.

# PRACTICAL ELECTRONICS PRINTED CIRCUIT BOARD SERVICE

Printed circuit boards for certain PE constructional projects are now available from the PE PCB Service, see list. They are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for overseas airmail. Remittances should be sent to: **PE PCB Service, Practical Electronics Editorial Offices, Westover House, West Quay Road, Poole, Dorset BH15 1JG.** Cheques should be crossed and made payable to IPC Magazines Ltd.

Please note that when ordering it is important to give project title, order code and the quantity. Please print name and address in Block Caps. Do not send any other correspondence with your order.

Readers are advised to check with prices appearing in the current issue before ordering.

**NOTE: Please allow 28 days for delivery. We can only supply boards listed here or in the November 1984 issue.**

PROJECT TITLE	Order Code	Cost
FEB '81		
Slave Light Dimmer	102-01	£1.88
MAR '81		
27/28MHz Converter	103-01	£1.79
Microphone Mixer	103-02	£1.83
Period Power Tester	103-03	£2.25
APRIL '81		
Speech Processor	104-01	£1.55
Mini Drill	104-02	£1.50
MAY '81		
Digisounder	105-01	£6.65
Thermometer	105-02	£1.49
JUNE '81		
pH Meter	106-01	£2.06
SEPT '81		
Horologicum	109-01	£3.16
"	109-02	£3.11
"	109-03	£2.97
Analogue Frequency Meter	109-04	£2.87
Ignition System	109-05	£2.47
"	109-06	£2.28
APRIL '82		
Med. Resolution Equaliser (UK 101)	204-01	£1.73
Enlarger Timer	204-02	£4.02
AUG '82		
Automatic Photographer	208-01	£1.94
Home Alarm	208-02	£3.21
JAN '83		
Audio Booster	301-01	£3.32
FEB '83		
Radio Booster	302-02	£1.80
MAR '83		
Into the Real World	303-01	£3.99
Accessory PSU	303-02	£1.35
4½ Digit Frequency Meter	303-03	£3.69
JUNE '83		
Program Conditioner	306-01	£2.30
SEPT '83		
Guitar Active Tone Control	309-01	£2.27
Ground Communication System	309-02	£2.13
	309-03	£2.31
DEC '83		
Expanding the Vic 20	312-01	£5.18
FEB '84		
Temp. Controller	402-04	£1.85
"	402-05	£2.61

PROJECT TITLE	Order Code	Cost
MAR '84		
Spectrum Autosave	403-01	£1.83
APRIL '84		
Microstepper	404-01	£10.74
MAY '84		
Sustain Unit	405-02	£2.82
Audio Signal Generator	405-03	£4.28
"	405-04	£2.51
JULY '84		
EPROM Duplicator	407-02	£3.74
Alarm System	407-03	£3.19
Oscilloscope Calibrator	407-04	£4.23
AUG '84		
Comm. 64 RS232C Interface	408-01	£3.02
Field Measurement	408-02	£3.19
"	408-03	£2.76
Simple Logic Analyser	408-05	£2.93
SEPT '84		
Parallel to Serial Converter	409-01	£2.92
Through the Mains Controller	409-02	£2.88
"	409-03	£2.71
OCT '84		
Logic Probe	410-01	£1.90
NOV '84		
Computer DFM Adaptor	411-01	£2.76
DEC '84		
Ni-Cad Charger	412-01	£2.40
JAN '85		
Outrider Car Computer (Set of 2 boards)	501-01/2	£9.10
FEB '85		
Modular Audio Power System		
Pt-1: Power Amp Board	502-01	£4.19
Spectrum DAC/ADC Board	502-02	£3.69
MARCH '85		
Modular Audio Power System		
Pt-2: Pre-Amp/Line Driver	503-01	£5.00
Main Board	503-02	£5.12
Heart Beat Monitor		
Detector	503-03	£8.90
Main Circuit Board	503-04	£6.62
Low Cost Speech Synthesiser	503-05	£3.42

**PE PRINTED CIRCUIT BOARDS SERVICE**  
Please send me the following p.c.b.s.

	Order Code	Quantity	Price
.....			
.....			
.....			
.....			
I enclose cheque/PO for £ .....			
Name .....			
Address .....			
.....			
.....			

## AFFORDABLE ACCURACY QUALITY MULTIMETERS FROM ARMON

### ANALOGUE

- HM-102BZ 10ADC Range, 20K $\Omega$ /VDC, Buzzer, Battery Test Scale 19 measuring ranges **£13.00**
- HM-102R Low end voltage & current ranges, Jack for Audio o/p Voltages..... **£11.00**
- 20 measuring ranges
- HM-101S Rugged, Pocket sized meter, for general purpose use..... **£7.50**
- 16 measuring ranges
- Battery, Test Leads and Manual included with each model.

### DIGITAL

- HC-6010 0.5% Accuracy, Standard Model **£33.50**
  - HC-5010T 0.25% Accuracy, TR Test Facility **£39.50**
- All models have full functions and ranges and feature:

- 3 1/2 digit 0.5" LED display
- Low battery indication
- Auto zero & Auto polarity
- ABS Plastic Casing & Tilt Stand
- DC AC 10amp Range
- Overload Protection on all ranges
- Battery, Spare Fuse, Test Leads and Manual

### FULL DETAILS ON APPLICATION FROM-



## ARMON ELECTRONICS LTD

DEPT L, HERON HOUSE, 109 WEMBLEY HILL ROAD, WEMBLEY, MIDDLESEX HA9 6AG  
TELEPHONE 01-902 4321 TELEX 923985  
PLEASE ADD 15% to your order for VAT, P&P Free of charge. Payment by cheque with order Offer applicable to mainland UK only


Trade enquiries invited

Please allow 28 days for delivery

HC 7030  
0.1% accuracy  
**£39.50**  
push button

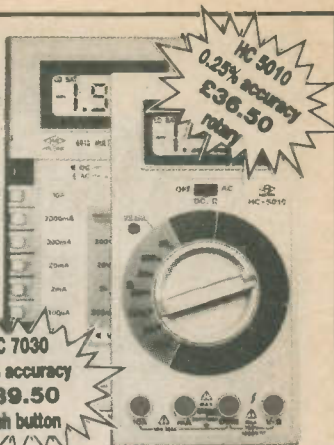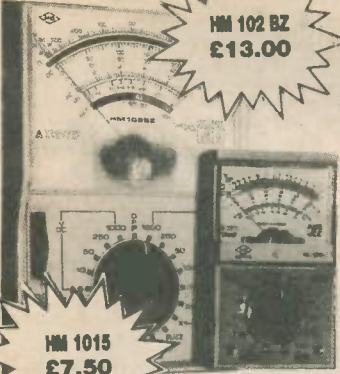

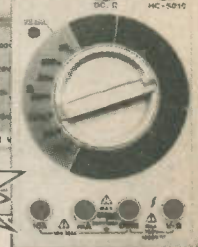HC 5010  
0.25% accuracy  
**£36.50**  
rotary



## CLEF ELECTRONIC MUSIC

### THE CLEF CMS

The FULLY programmable digital synthesizer that you can AFFORD  
THE NEW CLEF COMPUTER MUSIC SYSTEM is so user programmable that you need a BBC Micro to run it! 32 harmonically programmable oscillators, 32 programmable envelopes, 5 octave touch sensitive keyboard, up to 4 OSC/ENVS per note. Real time sequencing. Massive potential for future software. Complete system (without BBC Micro) £495 built. Phone or write for details. Modular systems also available.

### MASTER RHYTHM PROGRAMMABLE DRUMS

As Published in P.E

Twenty-Four Rhythm programmable Drum Machine with twelve instruments. Eight sections are extended to 24/32 measures for two bar programming. Sequence operation and instrument tone adjust.

COMPLETE KIT £79

STRING ENSEMBLE **£198.00**

ROTOR-CHORUS **£98.00**

MICROSYNTH P.C.B. & ELECT KITS **£86.90**

PERCUSSION SYNTH P.C.B. & ELECT KITS **£97.90**

## 88/72 NOTE PIANOS SPECIALISTS SINCE 1972

Using Patented electronic technique to give advanced simulation on Piano Key Inertia.

COMPONENT KITS including Keyboard

- 88 NOTE **£266**
- 72 NOTE **£234**

The above may also be purchased in four parts:

SQUARE FRONT KEYBOARDS

- 88 NOTE **£60**
- 49 NOTE **£29**
- 73 NOTE **£50**
- 30 NOTE **£19**

KEYSWITCH ITEMS ALSO AVAILABLE




## BAND-BOX PROGRAMMABLE BACKING TRIO

As Published in P.E.

THREE PIECE BACKING BAND Generates the sounds of three instrumentalists to back Soloists

DRUMS + BASS + KEYBOARDS Over 3,000 chord changes (60 scores) on 132 different chords - 16 chord sounds. Master Rhythm also required.

FULL KIT **£265** BUILT **£370**

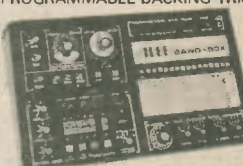

ALL PRICES INC. VAT, CARR & TELEPHONE ADVICE. S.A.E. for full Specs & MANF. PRICES. VISA-ACCESS-AMERICAN EXPRESS. Competitive quotes can be given for export, Allow 3-14 days for normal despatch.

CLEF PRODUCTS (ELECTRONICS) LIMITED (Dept P.E.) 44A BRAMHALL LANE SOUTH BRAMHALL STOCKPORT CHESHIRE SK7 1AH TEL 061-439 3297

AA117 0.950	BCV70 8.160	BU111 1.400	IBAS30 1.000	IN 3771 0.850	JAPANESE	PC285 0.428	LED	RED	3mm
AA119 0.950	BCV71 8.160	BU125 1.150	IBAS40 1.000	IN 3772 0.850	TRANSISTORS	PC290 0.583	LED	GREEN	3mm
AA132 0.950	BSV72 8.160	BU126 1.150	IBAS50 1.000	IN 3773 1.000	2SA73 8.300	PCF200 1.350	LED	RED	0.050
AC107 0.750	BD115 0.260	BU205 0.750	IBAR00 1.500	IN 4031 2.550	2SA104 3.320	PCF801 1.100	LED	3mm	YELLOW 0.100
AC126 0.170	BD124P 1.500	BU206 1.750	IBAR10 1.500	IN 4032 2.550	2SA106 2.220	PCF827 6.370	LED	3mm	GREEN 0.100
AC127 0.150	BD124 1.100	BU208 0.800	IBAR20 0.750	IN 4037 2.550	2SA203 0.300	PCF806 1.150	LED	5mm	RED 0.250
AC128 0.350	BD125 0.350	BU209 1.200	IBAR30 1.000	IN 4437 0.750	2SA473 3.370	PCF101 1.000	LED	5mm	GREEN 0.100
AC128K 0.236	BD131 0.250	BU210 1.200	IBAR40 1.500	IN 4448 0.750	2SB54 2.350	PCF159 4.500	LED	5mm	YELLOW 0.100
AC141K 0.300	BD132 0.250	BU211 1.200	IBAR50 1.000	IN 5081 0.200	2SB77 1.320	PCF185 0.550	LED	5mm	GREEN 0.100
AC142K 0.300	BD133 0.200	BU212 0.250	IBAR60 1.500	IN 5296 0.300	2SB837 1.200	PCF185 0.550	LED	5mm	YELLOW 0.100
AC158K 0.250	BD135 0.200	BU213 0.250	IBAR70 1.500	IN 5296 0.300	2SB91 1.000	PCF185 0.550	LED	5mm	GREEN 0.100
AC176 0.180	BD137 0.200	BU214 0.250	IBAR80 1.500	IN 5108 0.400	2SC460 0.210	PCF185 0.550	LED	5mm	YELLOW 0.100
AC176K 0.200	BD139 0.200	BU215 0.250	IBAR90 1.500	IN 5107 0.400	2SC465 0.600	PCF185 0.550	LED	5mm	GREEN 0.100
AC187 0.150	BD139 0.200	BU216 0.250	IBAR00 1.000	IN 5109 0.400	2SC733 8.400	PCF185 0.550	LED	5mm	GREEN 0.100
AC187K 0.200	BD140 0.200	BU217 0.250	IBAR10 1.500	IN 5128 0.550	2SC1191 1.100	PP1200 0.850	LED	5mm	YELLOW 0.100
AC188 0.170	BD141 0.050	BU218 0.250	IBAR20 1.500	IN 5143 0.550	2SC1221 1.500	PL135 0.800	LED	5mm	GREEN 0.100
AC188K 0.160	BD150 0.300	BU219 0.250	IBAR30 1.000	IN 5144 0.020	2SC1308 1.000	PL508 1.700	LED	5mm	YELLOW 0.100
AC196 0.440	BD151 0.300	BU220 0.250	IBAR40 1.500	IN 5201 0.800	2SC1307 1.500	PL701 1.700	LED	5mm	GREEN 0.100
AC197 0.440	BD156 0.350	BU221 0.250	IBAR50 1.500	IN 4000 0.040	2SC1210 2.500	PL708 1.400	LED	5mm	GREEN 0.100
AD142 0.600	BD156 0.350	BU222 0.250	IBAR60 1.500	IN 4003 0.040	2SC1219 1.500	PS204 1.800	LED	5mm	GREEN 0.100
AD149 0.450	BD171 0.300	BU223 0.250	IBAR70 1.500	IN 4004 0.040	2SC1219 1.500	PS204 1.800	LED	5mm	GREEN 0.100
AD151 0.220	BD177 0.300	BU224 0.250	IBAR80 1.500	IN 4005 0.040	2SC2079 1.200	ZENERS	BRIDGE RECTIFIERS	1A9V0 0.160	
AD162 0.220	BD179 0.320	BU225 0.250	IBAR90 1.500	IN 4006 0.040	2SC2232 0.900	400MV	1A100V 0.180	1A200V 0.180	
AD174 0.250	BD181 0.450	BU226 0.250	IBAR00 1.500	IN 4007 0.040	2SC2522 2.700	82V85 Range	1A400V 0.210	1A600V 0.210	
AF125 0.250	BD201 0.320	BU227 0.250	IBAR10 1.500	IN 4148 0.020	2SD234 0.370	BZV85 Range	1A800V 0.210	1A1000V 0.210	
AF127 0.250	BD203 0.420	BU228 0.250	IBAR20 1.500	IN 5400 0.060	2SC2223 0.800	2V to 3V0.360	1A200V 0.230	1A400V 0.230	
AF139 0.220	BD204 0.420	BU229 0.250	IBAR30 1.000	IN 5401 0.100	2SC2224 0.370	13W Zeners	2A100V 0.350	2A200V 0.350	
AF239 0.220	BD222 0.310	BU230 0.250	IBAR40 1.500	IN 5402 0.100	2SC1355 1.000	BZV61 Range	2A200V 0.360	2A400V 0.360	
AL113 0.800	BD222 0.310	BU231 0.250	IBAR50 1.500	IN 5403 0.100	WIP275 1.000	2V to 3V0.360	2A400V 0.360	2A600V 0.360	
AS215 1.000	BD223 0.310	BU232 0.250	IBAR60 1.500	IN 5404 0.100	IC5 SOCKETS	MEMORIES	2A800V 0.360	2A1000V 0.360	
AS217 1.000	BD224 0.240	BU233 0.250	IBAR70 1.500	IN 5405 0.100	8 pin 0.360	2114 2.000	3A200V 0.700	3A400V 0.700	
AU110 1.500	BD437 0.280	BU234 0.250	IBAR80 1.500	IN 5406 0.100	16 pin 0.280	2532 4.000	3A600V 1.000	3A800V 1.000	
AU102 1.800	BD635 0.380	BU235 0.250	IBAR90 1.500	IN 5407 0.100	25 pin 0.180	2764 7.000	4A200V 0.350	4A400V 0.350	
AV106 1.800	BD637 0.380	BU236 0.250	IBAR00 1.500	IN 5408 0.100	28 pin 0.180	4115 0.750	5A400V 0.100	25A/10V 1.600	
BA145 0.100	BD638 0.400	BU237 0.250	IBAR10 1.500	IN 5409 0.100	32 pin 0.180	6115 0.000	25A/10V 1.600	1.600	
BA146 0.100	BD639 0.400	BU238 0.250	IBAR20 1.500	IN 5410 0.100	40 pin 0.220	LM324 0.330	2A100V 0.200	ELECTROLYTIC	
BA154 0.080	BD645 0.800	BU239 0.250	IBAR30 1.000	IN 5411 0.100	48 pin 0.250	LM305 2.500	2A100V 0.200	4700UF 16V	
BA157 0.120	BF150 0.150	BU240 0.250	IBAR40 1.500	IN 5412 0.100	7805 0.350	LM7805 0.200	CAN	0.200	
BB101 0.130	BF181 0.180	BU241 0.250	IBAR50 1.500	IN 5413 0.100	7912 0.400	LM7912 0.200			
BB103 0.180	BF183 0.200	BU242 0.250	IBAR60 1.500	IN 5414 0.100	7915 0.400	LM7915 0.200			
BB105 0.180	BF184 0.250	BU243 0.250	IBAR70 1.500	IN 5415 0.100	7918 0.350	LM7918 0.200			
BB205 0.240	BF185 0.200	BU244 0.250	IBAR80 1.500	IN 5416 0.100	7824 0.350	LM7824 0.200			
BC107 0.070	BF194 0.050	BU245 0.250	IBAR90 1.500	IN 5417 0.100	7905 0.350	LM7905 0.200			
BC108 0.070	BF195 0.050	BU246 0.250	IBAR00 1.500	IN 5418 0.100	7912 0.400	LM7912 0.200			
BC109 0.070	BF196 0.060	BU247 0.250	IBAR10 1.500	IN 5419 0.100	7915 0.400	LM7915 0.200			
BC115 0.060	BF195 0.060	BU248 0.250	IBAR20 1.500	IN 5420 0.100	7924 0.400	LM7924 0.200			
BC116 0.110	BF200 0.160	BU249 0.250	IBAR30 1.000	IN 5421 0.100	78L05 0.280	LM78L05 0.200			
BC119 0.190	BF257 0.180	BU250 0.250	IBAR40 1.500	IN 5422 0.100	78L12 0.280	LM78L12 0.200			
BC120 0.190	BF258 0.180	BU251 0.250	IBAR50 1.500	IN 5423 0.100	78L15 0.280	LM78L15 0.200			
BC142 0.180	BF259 0.180	BU252 0.250	IBAR60 1.500	IN 5424 0.100	78L20 0.280	LM78L20 0.200			
BC143 0.180	BF259 0.180	BU253 0.250	IBAR70 1.500	IN 5425 0.100	78L25 0.330	LM78L25 0.200			
BC147 0.095	BF307 0.200	BU254 0.250	IBAR80 1.500	IN 5426 0.100	78L30 0.330	LM78L30 0.200			
BC148 0.095	BF308 0.200	BU255 0.250	IBAR90 1.500	IN 5427 0.100	78L35 0.330	LM78L35 0.200			
BC149 0.095	BF309 0.200	BU256 0.250	IBAR00 1.500	IN 5428 0.100	78L40 0.330	LM78L40 0.200			
BC157 0.055	BF422 0.110	BU257 0.250	IBAR10 1.500	IN 5429 0.100	78L45 0.330	LM78L45 0.200			
BC159 0.055	BF425 0.110	BU258 0.250	IBAR20 1.500	IN 5430 0.100	78L50 0.330	LM78L50 0.200			
BC162 0.060	BF450 0.150	BU259 0.250	IBAR30 1.000	IN 5431 0.100	78L55 0.330	LM78L55 0.200			
BC163 0.060	BF452 0.150	BU260 0.250	IBAR40 1.500	IN 5432 0.100	78L60 0.330	LM78L60 0.200			
BC173 0.060	BF475 0.200	BU261 0.250	IBAR50 1.500	IN 5433 0.100	78L65 0.330	LM78L65 0.200			
BC183 0.060	BF487 0.150	BU262 0.250	IBAR60 1.500	IN 5434 0.100	78L70 0.330	LM78L70 0.200			
BC184 0.060	BF487 0.150	BU263 0.250	IBAR70 1.500	IN 5435 0.100	78L75 0.330	LM78L75 0.200			
BC184 0.060	BF487 0.150	BU264 0.250	IBAR80 1.500	IN 5436 0.100	78L80 0.330	LM78L80 0.200			
BC184 0.060	BF487 0.150	BU265 0.250	IBAR90 1.500	IN 5437 0.100	78L85 0.330	LM78L85 0.200			
BC191 0.060	BF490 0.200	BU266 0.250	IBAR00 1.500	IN 5438 0.100	78L90 0.330	LM78L90 0.200			
BC192 0.060	BF490 0.200	BU267 0.250	IBAR10 1.500	IN 5439 0.100	78L95 0.330	LM78L95 0.200			
BC193 0.060	BF490 0.200	BU268 0.250	IBAR20 1.500	IN 5440 0.100	78L100 0.330	LM78L100 0.200			
BC194 0.060	BF490 0.200	BU269 0.250	IBAR30 1.000	IN 5441 0.100	78L105 0.330	LM78L105 0.200			
BC212 0.060	BF490 0.200	BU270 0.250	IBAR40 1.500	IN 5442 0.100	78L110 0.330	LM78L110 0.200			
BC212L 0.060	BF491 0.140	BU271 0.250	IBAR50 1.500	IN 5443 0.100	78L115 0.330	LM78L115 0.200			



# SMALL ADS

The prepaid rate for classified advertisements is 36 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £12.00 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Banks Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Practical Electronics, Room 2612, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

## NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser to check both prices and availability of goods before ordering from non-current issues of the magazine.

When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

### BRAND NEW COMPONENTS BY RETURN

**Electrolytic Capacitors 16V, 25V, 50V.**  
 0.47, 1.0, 2.2, 4.7 & 10 Mfds. — 5p.  
 22 & 47—6p. 100—7p. (50V—8p). 220—8p. (50V—10p).  
 470—11p. (40V—16p). 1000/15V—15p. 1000/25V—25p.  
 1000/40V—35p. 4700V/25V—70p.

**Subminiature bead Tantalum electrolytics.**  
 0.1, 0.22, 0.47, 1.0 @ 35V. 4.7 @ 63V — 14p.  
 2.2/35V, 4.7/25V—15p. 10/25V, 15/16V—20p.  
 22/16V, 33/10V, 47/6V, 68/3V & 100/3V—32p.  
 15/25V, 22/25V, 47/10V—35p. 47/16V—80p.

**Subminiature Ceramic Caps. E12 Series 100V.**  
 2% 10 pf. to 47 pf.—3p. 56 pf. to 330 pf.—4p.  
 10% 390 pf. to 4700 pf.—4p.

**Vertical Mounting Ceramic Plate Caps. 50V.**  
 E12 22 pf. to 1000 pf. E6 1500 pf. to 47000 pf.—2p.

**Polystyrene E12 Series 63V. Horizontal Mtg.**  
 10 pf. to 820 pf.—3p. 1000 pf. to 10,000 pf.—4p.

**Miniature Polyester 250V Vert. Mtg. E6 Series.**  
 01 to 068—4p. 1—5p. 15, 22—6p. 33, 47—10p.  
 68 — 12p. 1.0 — 15p. 1.5 — 22p. 2.2 — 24p.

**Mylar (Polyester) Film 100V. Vertical Mounting.**  
 001, 0022, 0047—3p. 01, 022—4p. 04, 05, 0.1—5p.

**High Stability Miniature Film Resistors 5%.**  
 1W E24 Series 0.51R — 10M0. — 1p.  
 1/4W E12 Series 1R0 to 10M0. — 1p.  
 1W E12 Series 10R to 10M0. — 5p.  
 1W metal film E12 Series 10R-1M0 5% — 2p. 1% E24 — 3p.  
 1N4148—2p. 1N4002—4p. 1N4005—6p. 1N4007—7p.  
 BC107/8/9—12p. BC147/8/9. BC157/8/9. BF195 & 7—10p.  
 8 Pin i.c.'s. 741 Op. amp.—18p. 555 Timer—24p.  
 DIL Holders 8 pin—9p. 14 pin—12p. 16 pin—14p.  
 LED's. 3 & 5mm. Red—10p. Green & Yellow—14p.  
 Grommets for 3mm.—1p. Grommets for 5mm—2p.  
 20mm. Q.B. Fuses 15, 25, 5, 1, 2, 3 & 5A—5p.  
 20mm. Ant. Surge 100mA to 50A—8p.  
 20mm. Fuseholders P.C. or Chassis Mtg.—8p.  
 Battery Snaps (pairs) PP3—6p. PP3—12p.  
 400mW Zener diodes E24 series 2V7 to 33V—8p.  
 Prices VAT inclusive Post 20p. (Free over £5.00).

**THE C.R. SUPPLY CO.**

127, Chesterfield Rd., Sheffield S8 0RN.

## HOME SECURITY CONT.

**WHO CAN PUT A PRICE ON PEACE OF MIND**

PROFESSIONAL EQUIPMENT AT LOW! LOW! PRICES.

**HOME SECURITY IS NOW AVAILABLE AT TRADE PRICES**

ADVANCED SECURITY PRODUCTS LTD

2 Ealing Road, Aintree, Liverpool L9 0HU, Merseyside.

Tel: 051-525 3440

FREE CATALOGUE PHONE OR S.A.E.

## RECEIVERS AND COMPONENTS

**RESISTORS 1,000 MIXED** 1/8w, 1/4w, 1/2w, 2%, 5%, 10%, C. Film £3.45 inc P&P. D. J. HOOKER, Romney Marsh Electronics, Pennywood, Clark Road, Greatstone, Romney Marsh, Kent TN28 8PB.

**TURN YOUR SURPLUS** capacitors, transistors, etc into cash. Contact COLES HARDING & CO., 103 South Brink, Wisbech, Cambs. Tel. 0945 584188. Immediate settlement.

**BELLS TELEVISION SERVICES** for service sheets of Radio, TV, etc £1.50 plus SAE. Colour TV Service Manuals on request. SAE with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

**BOURNEMOUTH/BOSCOMBE.** Electronic components specialists for 33 years. FORRESTERS (NATIONAL RADIO SUPPLIES), Late Holdenhurst Road. Now at 36, Ashley Road, Boscombe. Tel. 302204. Closed Weds.

## HOME SECURITY

# SECURITY Alarm Systems

FREE COMPREHENSIVE CATALOGUE!

- LOWEST DISCOUNT PRICES
- HIGHEST QUALITY EQUIPMENT
- FREE DIY DESIGN GUIDE
- FULLY ILLUSTRATED
- MICROCHIP CIRCUITRY
- QUICK DESPATCH SERVICE
- FULL INSTRUCTIONS

SEND SAE OR PHONE

C-TEC SECURITY, Dept PE.

Unit 1, Stephensway Ind. Estate, Goose Green, Wigan WN3 6PH. Telephone (0942) 42444

Trade Enquiries Welcome

## CENTURION ALARMS

Manufacturers of Professional Alarm Equipment for DIY & the TRADE. Send now for our New 16-page Brochure, Full of Information & the Lowest prices.



Tel: (0484) 21000 or 35527 24 hr.

**CENTURION Dept PE**  
 93 Wakefield Road, Huddersfield, HD5 9AB W. Yorks.

© CENTURION is a Registered Trademark of Centurion Alarms

## ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Electronics for ..... insertions. I enclose Cheque/P.O. for £..... (Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Electronics)


NAME .....

ADDRESS .....

## PRACTICAL ELECTRONICS

Classified Advertisement Dept., Room 2612, King's Reach Tower, Stamford Street, London SE1 9LS Telephone 01-261 5846

Rate: 36p per word, minimum 12 words. Box No. 60p extra.



## EDUCATIONAL/TUITION

### IMPROVE YOUR PROSPECTS

with skills that employers want - learn the easy way with modern home study courses from Ideal Schools.

#### MODERN ELECTRONICS

Train for success in the fastest ever growing industrial sector.

#### COMPUTER PROGRAMMING

The demand for Programmers is increasing constantly - don't miss out!

For free booklet write today to



## COURSES

# FULL-TIME TRAINING COURSES

### 2 YEAR

**B-TEC NATIONAL DIPLOMA (OND)  
ELECTRONICS &  
COMMUNICATIONS ENGINEERING**

### 15 MONTHS

**B-TEC NATIONAL CERTIFICATE (ONC)  
ELECTRONIC EQUIPMENT SERVICING**

### 15 MONTHS

**B-TEC NATIONAL CERTIFICATE (ONC)  
COMPUTING TECHNOLOGY**

### 9 MONTHS

**B-TEC HIGHER NATIONAL CERT (HNC)  
COMPUTING TECHNOLOGY  
& ROBOTICS**

THESE COURSES INCLUDE A HIGH PERCENTAGE OF COLLEGE BASED PRACTICAL WORK TO ENHANCE FUTURE EMPLOYMENT PROSPECTS

SHORT COURSES WITH PREVIOUS KNOWLEDGE

Prospectus from:

**LONDON ELECTRONICS  
COLLEGE**

Dept: AA, 20 Penywern Road,  
London SW5 9SU. Tel: 01-373 8721.

## SERVICES

### INVENTORS

Think of something new?  
Write it down! -

American industry offers potential royalties for your innovations and new products. We offer free confidential disclosure registration and initial consultation in London regarding your idea's potential value. Write without delay for your free information package.

American Inventors Corporation  
82, Broad Street, Dept PT  
Westfield, Massachusetts 01086  
United States of America.

A fee based marketing company.

## AERIALS

### AERIAL BOOSTERS

Next to the set fitting

B45H/G-UHF TV, gain about 20db, Tunable over the complete UHF TV band. PRICE £8.70.  
BII-VHF/FM RADIO, gain about 14db, when on the off position connects the aerial direct to the radio. £7.70.  
All Boosters we make work off a PP3/006p/6F22 type battery or 8v to 14v DC. P&P 30p PER ORDER.  
ELECTRONIC MAIL ORDER LTD., 62 Bridge St., Ramsbottom, Lancs BL0 5AG. Tel. (070682) 3036  
Access/Visa Cards Welcome SEA Leaflets

## FOR SALE

SPECIAL OFFERS. SE250C signal injector £2.20. 15 watt amplifier board £7.65. Antex C s/iron £5.95 P&P 40p. Thousands of components in stock. Phone or write for price list. SPECTRUM RADIO & ELECTRONICS LTD, 36 Slater Street, Liverpool L1 4BX. 051-709 4628.

## BOOKS AND PUBLICATIONS

FULL SIZE, top quality service sheets £2.50 + I.s.a.e. CTV/Music Centres £3.50 + I.s.a.e. Repair data almost any named TV-Video £10.50 inc. circuits. L.s.a.e. brings any quote free magazine/price lists. TISPE, 76 Churches, Larkhall, Lanarkshire. 0698 883334.

## MISCELLANEOUS

SPEED CONTROL KIT - Pulse width, D.C. Motors 4½-24V 15A max. £5.95 incl. p. (Enquiries S.A.E.) EVEREST ELECTRONICS, 11 Gordon Street, Sutton in Craven, Keighley, W. Yorkshire.

BURGLAR ALARM EQUIPMENT. Ring Bradford (0274) 308920 for our catalogue or call at our large showroom, opposite Odsal Stadium.

CLEARING LABORATORY, scopes, generators, P.S.U.'s, bridges, analysers, meters, recorders etc. Tel. 0403-76236.

ADAPTORS - Power supplies for calculators, TV games, computers etc. Send for details. RTE ELECTRONICS, Britania Mill, Rossendale, Lancs. BB4 8BA.

THE SCIENTIFIC WIRE COMPANY 811 Forest Road, London E17. Telephone 01-531 1568				
ENAMELLED COPPER WIRE				
SWG	1 lb	8 oz	4 oz	2 oz
8 to 34	3.63	2.09	1.10	-0.88
35 to 39	3.82	2.31	1.27	0.93
40 to 43	6.00	3.20	2.25	1.61
44 to 47	8.67	5.80	3.49	2.75
48	15.96	9.58	6.38	3.69
SILVER PLATED COPPER WIRE				
14 to 30	9.09	5.20	2.93	1.97
TINNED COPPER WIRE				
14 to 30	3.97	2.41	1.39	0.94
Fluxcore				
Solder	5.90	3.25	1.82	0.94

Prices include P&P VAT. Orders under £2 add 20p. SAE for list of copper and resistance wire. Dealer enquiries welcome.

SUPERB INSTRUMENT CASES by Bazelli, manufactured from PVC. Faced steel. Vast range, competitive prices start at a low £1.50. Punching facilities at very competitive prices. BAZELLI, (Dept. 23), St. Wilfreds, Foundry Lane, Halton, Lancaster LA2 6LT.

HEATHKIT. U.K. spares and service centre. CEDAR ELECTRONICS, Unit 12, Station Drive, Bredon, Tewkesbury, Glos. Tel. (0684) 73127.

## CABINET FITTINGS

Fretcloths. Coverings. Handles. Castors. Flight Case Locks & Parts. Jacks. XLRs. Bulgins. Reverb Trays. P & N mic Stands. ASS Glassfibre Horns. CELESTION POWER Speakers.

**ADAM HALL SUPPLIES LTD.**  
Send 30p cheque/  
P.O. for illustrated  
catalogue. Adam Hall (PE Supplies),  
Unit G, Carlton Court, Grainger Road,  
Southend-on-Sea.

# Leader of the Packs

## AC/DC COMPONENT PACKS

Pack No.	Qty	Description	Price
TF 11	12	RED 5mm LED	£1.00
TF 12	30	500mz ZENERS 5%	£1.00
TF 15	50	1 amp Rect. Diodes in 4000 series	£1.00
TF 16	6	1 amp Bridge Rect.	£1.00
TF 17	100	Transistor pads	£1.00
TF 18	20	A/S Fuses 20mm	£1.00
TF 19	10	3A Rect. Diodes	£1.00
TF 110	2	DRP 12	£1.00
TF 111	5	BR 100 DIAC	£1.00
TF 112	10	BC109B	£1.00
TF 113	10	LC's all different	£1.00
TF 114	50	BFR 86	£1.00
TF 115	12	8 pin DIL sockets	£1.00
TF 116	20	10mm Horiz. Pre set (10 values)	£1.00
TF 117	10	Slide Pots - 3K all the same	£1.00
TF 118	10	Mixed Pots	£1.00
TF 119	10	Feed throughs	£1.00
TF 120	25	Electrolytic Caps	£1.00
TF 121	50	Polyester Caps	£1.00
TF 122	100	Mixed Resistors - Incl. Wire Wound	£1.00
TF 123	100	Mixed Transistor Hardware	£1.00
TF 124	25	5mm LED clips and rings	£1.00
TF 125	10	BC 107	£1.00
TF 126	10	BC 108	£1.00
TF 127	6	Green 5mm LED	£1.00
TF 128	6	Yellow 5mm LED	£1.00
TF 129	150	Mixed nuts/bolts/washers/self tapper	£1.00
TF 130	25	Mixed Electrolytics Axial	£1.00
TF 131	25	Mixed Electrolytics Radial	£1.00
TF 132	50	Mixed Polyester Axial	£1.00
TF 133	50	Mixed Polyester Radial	£1.00
TF 134	15	BC 337	£1.00
TF 135	20	500MA A/S 20mm Fuse	£1.00
TF 136	50	Mixed Ceramic Discs	£1.00
TF 137	50	Mixed Ceramic Plates	£1.00
TF 21	200	47 pf 160V Polystone Cap	£2.00
TF 22	10	LM 3900 N	£2.00
TF 23	10	Mixed DTL	£2.00
TF 24	5	4700 mf 25V Tag Elect 2"x1"	£2.00
TF 25	10	1000 mf 63V Ax Elect	£2.00
TF 26	50	.022 mf 400V RAD PDLY	£2.00
TF 27	10	100 mf 250V Ax	£2.00
TF 28	10	2.2 mf 160V Polyester RAD	£2.00
TF 29	10	VDR's	£2.00
TF 210	10	Mixed TTL (74 series)	£2.00
TF 211	4	2N 3055 (HRC)	£2.00
TF 213	200	IN 4151 Diodes	£2.00
TF 214	200	IN 4148 Diodes	£2.00
TF 51	100	White/Red 5mm LED	£5.00
TF 52	50	BC 108C	£5.00
TF 54	½KG	Reel 22g ersin multicore	£5.00
TF 55	10	2N3055 (HRC)	£5.00
TF 56	5	DCP71	£5.00
TF 57	3	10,000 mf 40V Comp. grade elect	£5.00
TF 58	720	¼W Carbon film 1w-10Mw ten values	£5.00
TF 59	25	1,000 mf 25V Axial	£5.00
TF 510	25	1,000 mf 25V Radial	£5.00

ALL PRICES INCLUDE VAT - ALL GOODS BRAND NEW & NORMALLY DESPATCHED BY RETURN POST.  
TERMS: Cash with order. POST & PACKING: Please add 75p to total order.

## AC/DC ELECTRONICS COMPONENTS

DEPT P.E., 45 CHURCH STREET,  
ENFIELD, MIDDLESEX.

★ BAKER ★

GROUP P.A. DISCO AMPLIFIERS post £2

Table listing various Group P.A. Disco Amplifiers with specifications like wattage, inputs, and prices.

BAKER LOUSPEAKERS

Table listing Baker Loudspeakers with columns for Type, Model, Size, Watts, Ohms, Price, and Post £2 each.

DISCO CONSOLE Twin Decks, mixer pre amp £145. Carr £10. Distro Powered 120 watt £199; or Compact Disco £300. 120 watt £300; 150 watt £360; 300 watt £410. Carr £30.

DELUXE STEREO DISCO MIXER/EQUALISER as above plus L.E.D. V.U. displays 5 band graphic equaliser, left/right fader, switchable inputs for phone/line, mike/line. Headphone Monitor, Mike Talkover Switch £124 pp £2. As above but 3 Deck inputs, 4 Line/Aux inputs, 2 Mic. Inputs, 2 Headphone Monitors £145.

P.A. CABINETS (empty) Single 12 £32; Double 12 £38. carr £10. WITH SPEAKERS 75W £54; 90W £73; 150W £82; 200W £90. HORNBOXES 200 Watt £32, 300 Watt £38. Post £4.

WATERPROOF HORNS 8 ohms. 25 watt £22. 30 watt £25. 40 watt £33. 20W plus 100 volt line £38. Post £2. MOTOROLA PIEZO ELECTRONIC HORN TWEETER, 39mm. square £10. 100 watts. No crossover required, 4-8-16 ohm, 7.9x3.3in. £16

CROSSOVERS. TWO-WAY 3000 c/s 30 watt £3. 60 watt £5. 100 watt £5. 3 way 950 cps/3000 cps. 40 watt rating £4. 60 watt £5.50. 100 watt £10. LOUSPEAKER BARGAINS Please enquire, many others in stock. 4 ohm, 5m, 7x4in. £2.50. 6 1/2in, 8x5in. £3. 8in. £2.50. 6 1/2in. 25W £7.50. 8 ohm, 2 1/2in. 3in. £2. 5x3in. 6x4in. 7x4in. 5in. £2.50. 6 1/2in. 8x5in. £3. 8in. £4.50. 10in. £5. 12in. £8. 8in. 25W £5. 8in. 25W £5. 8in. 25W £5. 8in. 25W £5. 15 ohm, 2 1/2in. 3 1/2in. 5x3in. 6x4in. £2.50. 6 1/2in. 10W £5. 8in. £4. 10in. £7. 25 ohm, 3in. £2. 5x3in. 6x4in. 7x4in. £2.50. 120 ohm, 3 1/4in. dia. £1.

Table listing various speakers and models like GOODMANS, WHARFEDALE, CELESTION, AKAI, GOODMANS, HNH, GOODMANS, GOODMANS.

METAL GRILLES 8in. £3.00, 10in. £3.50, 12in. £4.50, 15in. £5.50, 18in. £7.50. Loudspeaker Covering Vynair etc. Samples. S.A.E.

DISCO SOUND / LIGHT CONTROLLER

Ready Built Deluxe 4 Channel 4,000 watt sound chaser + speed + programme controls £69. Mk. 2 16 programmes, £89. PP £2.

MAINS TRANSFORMERS

Table listing Mains Transformers with columns for Model, Price, and Post.

£8.50 post 50p MINI-MULTI TESTER

Pocket size instrument. o.p.v. DC volts 5, 25, 250, 500. AC volts 10, 50, 100, 250, 500. DC 0-250uA; 0-250mA. Resistance 10 to 600k. De-Luxe Range Doubler Meter, 50,000 o.p.v. x 5 v x 2in. Resistance 20 meg in 5 ranges. Current 50uA to 10A. Volts 0.25/1000V DC, 10v/1000V AC. £25.00 post £1

PANEL METERS 50uA, 100uA, 500uA, 1mA, 5mA, 100mA, 500mA, 1 amp, 2 amp, 5 amp, 25 volt, VU 2 1/4x2 1/4in. £5.50 post 50p

EQUIPMENT CASES. Black Vinyl Covered Top, All Base 4 x 2 1/2 x 2 1/4in. £2.50. 6 x 4 x 1 1/2in. £3.60. 8 x 5 x 2in. £4.00; 11 x 6 x 3in. £5.50; 11 3/4 x 6 x 5in. £9.00; 15 x 8 x 4in. £12.00.

ALU ANGLE BRACKET 6 x 3/4 x 3/4in. 30p. ALUMINIUM PANELS 18 s.w.g. 12 x 12in. £1.80; 14 x 9in. £1.75; 8 x 4in. 55p; 12 x 8in. £1.10; 10 x 7in. 56p; 8 x 6in. 90p; 14 x 3in. 72p; 12 x 5in. 90p; 16 x 10in. £2.10; 16 x 6in. £1.30. ALUMINIUM BOXES. MANY OTHER SIZES IN STOCK. 4 x 2 1/2 x 2in. £1.20; 3 x 2 x 1in. £1; 6 x 4 x 2in. £1.80; 8 x 6 x 3in. £3.60; 12 x 5 x 3in. £3.60; 6 x 4 x 3in. £2.20; 10 x 7 x 3in. £3.60.

Table listing High Voltage Electrolytics with columns for Model, Price, and Post.

SINGLE PLAY DECKS. Post £2.

Table listing Single Play Decks with columns for Make, Drive, Model, Cartridge, Price, and Post.

DECCA TEAK VENEERED PLINTH space for small amplifier Board cut for BSR or Garrard 18 3/4in. x 14 1/4in. x 4in. £5. Post £1

TINTED PLASTIC COVERS for Decks. £5 each. Post £1 17/8 x 13 1/2 x 3 1/4in. 18 1/4 x 12 1/2 x 3in. 21 1/2 x 14 1/4 x 2 1/2in. 17 x 12 7/8 x 3 1/2in. 14 7/8 x 13 x 3 1/4 14 1/2 x 13 3/8 x 2 3/4in. 22 9/8 x 13 7/8 x 3in. 16 9/8 x 13 x 4in. 21 x 13 9/8 x 4 1/8in.

RADIO COMPONENT SPECIALISTS

Dept 4, 337, WHITEHORSE ROAD, CROYDON

SURREY, U.K. Tel: 01-684 1665

ACCESS

Post 50p Minimum. Callers Welcome.

Same day despatch. Closed Wed. Lists 34p.

VISA



DON'T MISS OUT ON

CROFTON

CASH & CARRY BARGAINS

TELEPHONE 01-891 1923 NOW for details of

- Computer Monitors ● Combined Colour TV/Monitors ● ZX81 Keyboards ● Light Pens (BBC) ● TV Cameras ● Lenses ● Video Digitisers ● Eprom Erasers ● etc.

HIGH QUALITY PRODUCTS AT AMAZING PRICES

CROFTON ELECTRONICS

35 GROSVENOR ROAD, TWICKENHAM, MIDDLESEX TW1 4AD

INDEX TO ADVERTISERS

Table listing various advertisers and their page numbers, including AC/DC Electronics, Adcola Products, A.D. Electronics, etc.

NEW THIS MONTH

12V SOLENOID, 10mm travel. Overall length 46 x 13 x 15mm. Coil 75R. Only £1. ZS24 Super Modem panel 260x175mm with a host of top quality parts. 2x4way DIL switches, 2 BCD switches, 31 LS chips, TRI602B UART, 2211/2206 FSK Rx and Tx chips. £6.00. LEADS AT SILLY PRICES! PL516 DC adaptor lead for Walkman, 1.8m long 30p. PL528 2 pin DIN line skt to phono plug 0.2m long 20p. PL508 5 pin DIN to 3 pin DIN audio lead 1.2m long 40p. PL541 Intercom extn lead. 3.5mm line skt to 3.5mm plug. 6m long 40p. PL708 Video lead. PL259 plug to F type plug. 3m low loss coax 85p. FM TUNING MODULE. This neat unit 75x40x19mm as used in car radios etc. Standrad 10.7MHz IF output, 9-12V DC supply. Full connexion data supplied. £2.40. Stereo Cassette Head. Only £1.00.

SHOP SALE

23rd Feb to 9th Mar. Many bargains - worth a visit!! 1W AMPLIFIER ZS14 - Audio amp panel 95x65mm with TBA820 chip. Gives 1W output with 9V supply. Switch and vol. control. Just connect batt. and speaker. Full details supplied. Only £1.50, 10 for £12; 25 for £25. AM TUNER PANEL ZS16 - For use with mono amp above. Neat panel 60x45mm. Only £1.50; 10 for £12.00. 20 WAY RIBBON CABLE Twisted and flat computer grade for lower cost cable. Reformatted into flat sections every 21" for IDC connectors. Only £70p/21" or £25 per 100ft reel. PCB MOUNTING NI-CADS Much sought after 4.8V 150mA batts with PCB mntg tags on 25mm pitch. Batt size 25x16 Ø. Ideal for paralleling. 99p ea; 10+ 85p; 25+ 70p; 100+ 60p. NI-CAD CHARGER SPOOP!! Ever-Ready model CH4, this charger will take up to 4 AA, C or D cells plus 2 PP3 if required. Smart two tone gear case 212x97x50mm. Only £7.95.

1984/85 CATALOGUE

B4 page A4 size - Bigger, Brighter, Better - more components than ever before! With each copy there's discount vouchers, Bargain List, Wholesale Discount List, Bulk Buyers List, Order Form and Reply Paid Envelope. All for just £1.00! Winter Supplement out Now. - Send large SAE for your free copy.

"TREKKER"

Computer-controlled Robot built around the gearbox described below. Complete kit of parts inc PCB, program listings for BBC (other micros soon). £44.85. 20W ribbon cable (min 3m recommended - 5m better) £13.00m. SAE for illustrated leaflet.



The unit has 2 x 3V motors, linked by a magnetic clutch, thus enabling turning of the vehicle, and a gearbox contained within the black ABS housing, reducing the final drive speed to approx 50rpm. Data is supplied with the unit showing various options on driving the motors etc. £5.95. Suitable. Two new types of wheels can be supplied: the aluminium discs and smaller plastic wheels are now sold out. Type A has 7 spokes with a round black tyre and is 100mm dia. Type B is a solid heavy duty wheel 107mm dia with a flat rigid tyre 17mm wide. PRICES: Gearbox with data sheets: £5.95 ea Wheel type A: £0.70 ea Wheel type B: £0.90 ea

FIBRE OPTICS

Scope purchase of single and twin cable. For use with visible light or infra-red. Core 1mm dia, overall 2.25mm dia. Single 50p/m; 20m coil £5.30. Twin 50p/m; 20m coil £11.00. Official orders welcome - minimum invoice charge £10. No. min. on CWO. Our store has enormous stocks of components and is open from 9.5-3 Mon-Sat. Come & see us!! Minimum Access order £5.00

GREENWELD 443C Millbrook Road Southampton SO1 0HX Tel (0703) 772601/783740 ALL PRICES INCLUDE VAT. JUST ADD 60p P&P



# All new in the 1985 Catalogue



From a gentle purr to a mighty roar, the tightly controlled power of the beast is yours to command!

## PROFESSIONAL QUALITY HIGH POWER LOUDSPEAKERS

A new range of superb quality loudspeakers.

- ★ Virtually indestructible high temperature voice-coil reinforced with glass-fibre
- ★ 100% heat overload tolerance
- ★ Advanced technology magnet system
- ★ Rigid cast alloy chassis
- ★ Linen or Plastiflex elastomer surrounds
- ★ 5-year guarantee (in addition to statutory rights)




Available in 5, 8, 10, 12, 15 and 18 inch models with 8Ω and some 16Ω impedances and with input powers ranging from 50W to 300W e.g.

- 5in. 50W 95dB 8Ω: XG39N / 16Ω: XG40T £17.95§
- 8in. 100W 98dB 8Ω: XG43W £29.95§
- 10in. 100W 100dB 8Ω: XG46A £29.95§
- 12in. 100W 101dB 8Ω: XG49D £29.95§
- 12in. Twin Cone 100W 100dB 8Ω: XG50E / 16Ω: XG51F £31.95§

Note - the output power doubles for each 3dB increase (ref 1W @ 1m).

## PRECISION GOLD MULTIMETERS

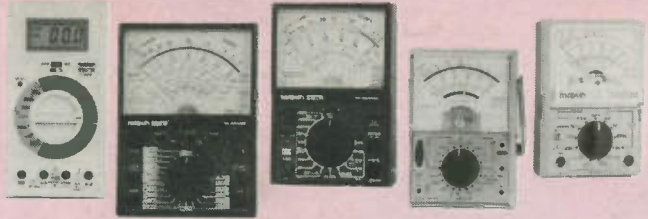

A new range of very high quality multimeters offering truly amazing quality at the price.

- Pocket Multimeter, 16 ranges, 2000Ω/V DC/AC £6.95§ (YJ06G)
- M-102BZ with Continuity buzzer, battery tester and 10A DC range, 23 ranges, 20,000Ω/V DC £14.95§ (YJ07H)
- M-2020S with Transistor, Diode & LED tester and 10A DC range, 27 ranges 20,000Ω/V DC £19.95§ (YJ08J)
- M-5050E Electronic Multimeter with very high impedance, FET input, 53 ranges including peak-to-peak AC, centre-zero and 12A AC/DC ranges £34.95§ (YJ09K)
- M-5010 Digital Multimeter with 31 ranges including 20Ω and 20μA DC/AC FSD ranges, continuity buzzer, diode test, and gold-plated PCB for long-term reliability and consistent high accuracy (0.25% + 1 digit DCV) £42.50§ (YJ10L)

N.B. All our prices include VAT and Carriage. A 50p handling charge must be added if your total order is less than £5 on mail order (except catalogue).

### MAPLIN ELECTRONIC SUPPLIES LTD.

Mail Order: P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend (0702) 552911 SHOPS

- BIRMINGHAM Lynton Square, Perry Barr, Tel: 021-356 7292.
  - LONDON 159-161 King Street, Hammersmith, W6. Tel: 01-748 0926.
  - MANCHESTER 8 Oxford Road, Tel: 061-236 0281.
  - SOUTHAMPTON 46-48 Bevois Valley Road, Tel: 0703 25831.
  - SOUTHWEND 282-284 London Rd, Westcliff-on-Sea, Essex. Tel: 0702-554000
- Shops closed all day Monday.

§ Indicates that a lower price is available in our shops.

Our huge range of top quality electronic components at very competitive prices are all detailed in our catalogue, and with well over 600 new lines in our 1985 edition and many design improvements, it's well worth getting a copy. Here are just a few examples from the catalogue. (The items below are NOT kits).


- ★ Most phono and jack plugs now with integral strain relief sleeve - gold-plated types also available from 14p (gold from 70p)
- ★ Stereo Disco Mixer with cross-fade, talk-over, cue monitoring, aux input, slide controls. Only £58.95 (AF99H)




- ★ 10-Channel Stereo Graphic Equalisers - 3 models - basic; with peak level meter; and with spectrum analyser - from £77.95



- ★ Digital Delay Line permits Slap-back, Doubling, Flanging, Chorus and Echo. 11 controls. Only £195.00 (AF98G)
- ★ Video Enhancer improves picture quality when recording from one VTR to another, and with TV's with monitor input. Only 28.95 (XG59P)
- ★ Detailed descriptions of the exciting new 74HC range of IC's which combine the advantages of CMOS and TTL. From 46p
- ★ Keyboards: sloping keys, two-tone grey, mounted in steel frame, very smart cases (extra) available. 61 keys, only £33.95 (YJ12N) 79 keys, only £37.95 (YJ13P)
- ★ 1% Resistors now 50ppm/°C, 0.4W, only 2p each!
- ★ Auto transformers 120/240V 50VA, £10.75§ (YJ56L). 100VA £14.95§ (YJ57M). 150VA £16.95§ (YJ58N). 250VA £21.95§ (YJ59P).
- ★ Digital Clinical Thermometer. Only £13.95 (FK51F)

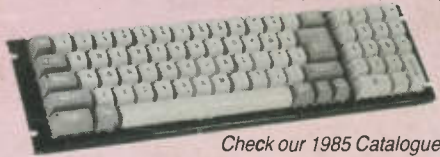

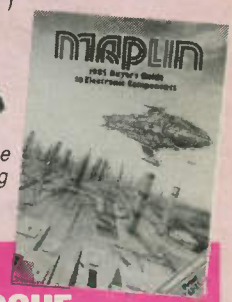Check our 1985 Catalogue for all our other fascinating new lines.



AMERICAN EXPRESS    map

AMEX    VISA

☎ Phone before 2pm for same day despatch.

## 1985 CATALOGUE

Pick up a copy now at any branch of W.H. Smith or in one of our shops. The price is still just £1.35, or £1.75 by post from our Rayleigh address (quote CA02C).

Post this coupon now for your copy of the 1985 catalogue. Price £1.35 + 40p post and packing. If you live outside the U.K. send £2.40 or 11 International Reply Coupons. I enclose £1.75.

Name .....

Address .....

.....

.....

PE 3/85

All offers subject to availability.

Prices firm until Feb 9th 1985.

Featured in  
Electronics &  
Music Maker

# TAKE COMPLETE CONTROL OF YOUR MUSIC with the

# MCS-1

## professional quality MIDI-controlled sampling unit

Once again, Powertran and E&MM combine to bring you versatility and top quality from a product out of the realms of fantasy and within the reach of the active musician.

The MCS-1 will take *any* sound, store it and play it back from a keyboard (either MIDI or Iv/octave). Pitch bend or vibrato can be added and infinite sustain is possible thanks to a sophisticated, looping system.

All the usual delay line features (Vibrato, Phasing, Flanging, ADT, Echo) are available with delays of up to 32 secs. A special interface enables sampled sounds to be stored digitally on a floppy disc via a BBC microcomputer.

The MCS-1 gives you many of the effects created by top professional units such as the Fairlight or Emulator. But the MCS-1 doesn't come with a 5-figure price tag. And, if you're prepared to invest your time, it's almost cheap!

### Specification

- Memory Size: Variable from 8 bytes to 64K bytes.
- Storage time at 32 KHz sampling rate: 2 seconds.
- Storage time at 8 KHz sampling rate: 8 seconds.
- Longest replay time (for special effects): 32 seconds.
- Converters, ADC & DAC: 8 bit companding. Dynamic range: 72 dB.
- Audio Bandwidth: Variable from 12 KHz to 300 Hz.
- Internal 4 pole tracking filters for anti-aliasing and recovery.
- Programmable wide range sinewave sweep generator.
- MIDI control range: 5 octaves.
- +1 V/octave control range: 2 octaves with optional transpose of a further 5 octaves.

### Digital Delay Line




Introduced in 1982, Powertran's DDL has brought digital quality effects to thousands of musicians. Still available in kit form at only £179.00 + VAT.

**KIT**  
**£499**  
**+ VAT**

**BUILT**  
**£699**  
**+ VAT**



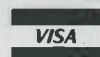Write or phone now to place an order.  
Powertran Cybernetics Limited,  
Portway Industrial Estate,  
Andover, Hants, SP10 3PE.  
Telephone: 0264 64455



**POWERTRAN** cybernetics Ltd