

JANUARY 1989

Australia \$3.25, New Zealand \$4.40 (inc. GST), Malaysia \$6.30,  
Ireland EIR2.13 (inc. VAT)


£1.40

# TELEVISION

SERVICING·PROJECTS·VIDEO·DEVELOPMENTS

*Extra this month*

*The Celtel Year Planner*

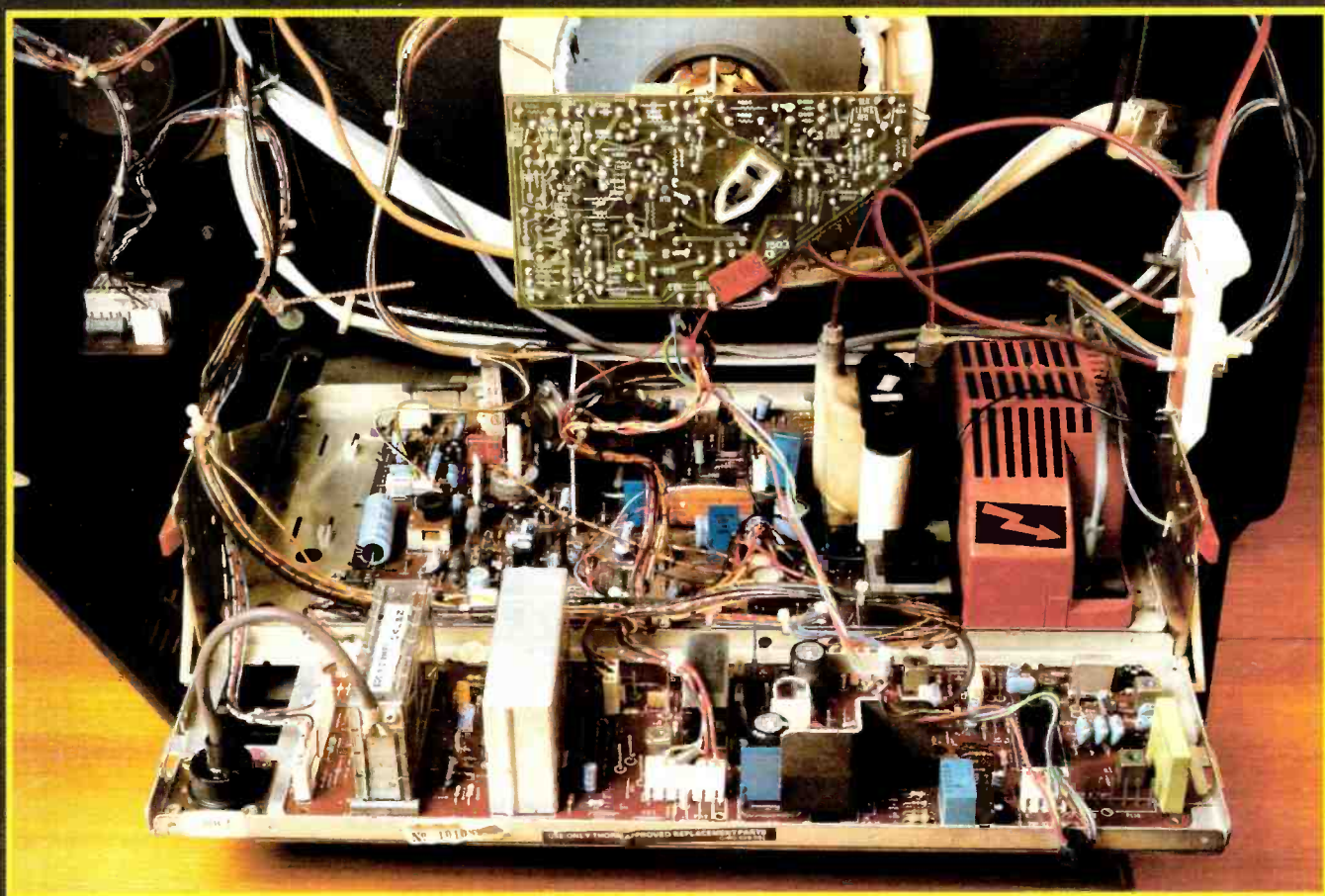

**Servicing the Ferguson TX10  
TTL Logic Probe/Analyser  
Practical Guide to Satellite TV  
How to Stop EHT Arcing  
VCR Clinic • IBC 88 Report  
TV Fault Finding • DX-TV**

# MANOR SUPPLIES

MKV PAL COLOUR TEST GENERATOR  
FOR DOMESTIC TV & VCR.

TEST  
DEMONSTRATIONS  
AT 172  
WEST END LANE




- ★ 40 different patterns and variations.
- ★ Fully interlaced sync pulses with correct picture blanking.
- ★ EBU colour bars, BBC colour bars, whole rasters & split bars (specially useful for VCR service), white, yellow, cyan, green, magenta, red, blue and black.
- ★ Chequerboard.
- ★ Mono outputs with border castellations, cross hatch, grey scale, vertical lines, horizontal lines and dots.
- ★ UHF modulator output plugs straight into receiver aerial socket.
- ★ Additional video output for CCTV & VCR.
- ★ Facilities for sound output.
- ★ Easy to build kit, standard parts. Only 2 adjustments. No special test equipment required.
- ★ Mains operated with stabilised power supply.
- ★ All kits fully guaranteed with back-up service.
- ★ Also available with VHF Modulator.

Price of Kit **£70.00**  
Case (10"×6"×2¼") app. **£8.60**  
Optional Sound Module (6MHz or 5.5MHz) **£3.90**  
Built & Tested in Case including Sound Module **£108.00**

SPECIAL TEST  
REPORT  
'TELEVISION'  
DEC. 1982

Post/Packing £3.00  
Add VAT 15% TO ALL PRICES

## PAL COLOUR BAR GENERATOR (Mk4)

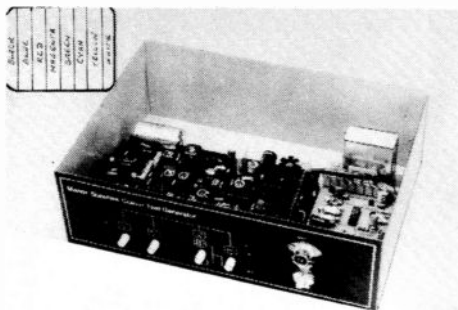

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars R-Y, B-Y etc.
- ★ Cross-hatch, grey scale, peak white and black level.
- ★ Push button controls, battery or mains operated.
- ★ Simple design, only five i.c.s on colour bar P.C.B.
- ★ Backup service available.

PRICE OF MK 4 COLOUR BAR GENERATOR KIT  
**£30.00. CASE £8.60. BATT HOLDERS £4.20. MAINS  
SUPPLY KIT £4.20 (Combined P&P £3.00).**

MK 4 (BATTERY) BUILT & TESTED £58.00 + £3.00 P & P.  
MK 4 (MAINS) BUILT & TESTED £68.00 + £3.00 P & P.  
VHF MODULATOR (CH 1 to 4) FOR OVERSEAS £5.75.  
EASILY ADAPTED FOR VIDEO OUTPUT & C.C.T.V.

ADD  
VAT  
15%

PAL DECODER KIT (Video to RGB) for Monitors £27.00 p.p. £1.00.  
PAL ENCODER KIT (RGB to Video) £18.50 p.p. £1.30.  
CROSS HATCH UNIT KIT, Aerial Input type, incl. T.V. sync. and UHF Modulator, Battery Operated, also gives Peak White & Black Levels, can be used for any set. £13.50 p.p. 80p. (Alum. Case £3.20 p.p. £1.40.)  
ADDITIONAL GREY SCALE Kit £2.90 p.p. 45p.  
UHF SIGNAL STRENGTH METER KIT £22.00 Alum. Case £3.20. De Luxe Case £8.60 (Built & Tested £48.00) p.p. £2.50.  
CRT TESTER & REACTIVATOR KIT For Colour & Mono complete with Case, Panel Meter Indicator - can be adapted for latest CRTs £29.50 p.p. £3.00.

# TV SERVICE SPARES

BACKED BY TWENTY YEARS EXPERIENCE & STAFF OF  
TECHNICAL EXPERTS

LOPTS, TRIPLERS, PANELS, TUNERS, SELECTORS ETC.

## PHILIPS SPARES

KT3, K30 PANELS, tested, exchange, sound, power, bridge rect, frame, RGB £7.50 each. Decoder (Non-text) £10.00 p.p. £1.50.  
G11 PANELS (tested), frame, IF, decoder £12.50 each. p.p. £2.00. Scan £20.00 p.p. £2.80. Power tested exchange £18.00 p.p. £2.80.  
G11 PANELS EX-RENTAL (untested) Scan, Frame, Decoder £5.00 p.p. £2.00.  
G11 IF PANEL (new) less Tuner £2.50 p.p. £1.30.  
G9 POWER SUPPLY UNIT £5.00 p.p. £2.30.  
G8/G9 IF/DECODER PANELS for small spares incl. IC's £2.50 p.p. £1.60.  
G8 6 Position Channel Selector (sloping buttons) £2.50 p.p. £1.00.  
HANDSETS (new replacements) p.p. £1.50.  
G11 ULTRASONIC non-text £19.50, infra-red text £19.50. Others available.  
KT3 non-text (RC4001) £22.50. KT3, K30 etc. Text £22.50.  
HANDSETS EX-RENTAL, TEXT UNTESTED. KT, TEXT/VIDEO TYPE £3.50 p.p. £1.00.  
MANUALS p.p. 80p. G11, K35, 2A £3.50. KT3 £4.50, CTX-E, CTX-S, CF1 £1.50 each.

## THORN/FERGUSON SPARES

8000, 8500, 8800, 9800 PANELS tested, exchange. Power £8.80, Frame £10.00 p.p. £2.30.  
8800, 9800 Touch Tune facia unit £3.50 p.p. £1.50.  
8000/8500 IF/Decoder panels salvaged £3.20 p.p. £1.80.  
9000 Series IF/Decoder £10.00 p.p. £2.30.  
9000 IF/Decoder panels salvaged, for spares £2.50 p.p. £1.80.  
TX9 Panels complete & tested £28.00 exchange (shop only)  
TX9 Panels ex-factory for small spares includes IC's & semiconductors, etc. £3.00 p.p. £2.00.  
TX9 panels salvaged ex-factory for spares incl. electronic & mains transformer. £8.50 p.p. £3.00.  
TX9/TX10 Facia, control panel incl. infra-red receiver £8.50 p.p. £2.00  
TX10 Focus control £8.50 p.p. £1.00.  
TX9/TX10 Saw filter IF panel £5.00 p.p. 80p.  
TX9/TX10 Remote & tuning control panel 1515 (incl. SAA5012) £7.50 p.p. £1.80.  
TX Remote & tuning control panel 1509 (incl. UAA1008A, battery) £5.00 p.p. £1.80.  
REMOTE CONTROL HANDSETS — TX9, TX10 infra-red (non-text) £18.00, TX9, TX10 infra-red text £19.50 p.p. £1.20. Large selection of others available: Grundig, Sony, etc.

ITT SPARES: CVC30 series convergence & purity panels £2.50 p.p. £1.50.  
CVC30 series panels surplus (untested) £2.50 each, CMP31, CMP31, CMA30, CMC52 p.p. 80p. CMD33 p.p. £1.80.  
CVC20/30 series chassis for small spares (shop only) £2.50.  
BUSH SPARES: T20/T22 panels, tested, exchange, power £18.00. Scan £25.00 p.p. £2.50. T20/T22 touch tune facia unit £7.50 p.p. £2.00.

GEC SPARES: 20AX MKII line tune base £18.00 p.p. £2.00. Power (PC778) tested exchange £18.00 p.p. £2.00.  
TELETEXT DECODER PANELS (tested) — Mullard VM6101 Type £25.00, Philips KT3, K30 £20.00 p.p. £2.30.  
MULLARD VM6230 teletext decoder (similar to VM6101) plus additional Prestel units.

VM6330 & line coupler £20.00 p.p. £3.00.  
GRUNDIG 8630 Series Varicap Tuners £5.00 p.p. £1.00.  
VARICAP TUNERS U321, U322/204, ELC1043 (equiv.), SC4, £7.80 p.p. £1.00.  
VHF Philips, NSF £6.80 p.p. £1.00.  
VARICAP UHF-VHF ELC 2000S £9.80 p.p. £1.00.  
UHF/625 TUNERS, many different types in stock. JAP Rotary £4.80 p.p. £1.80.  
LOPTS New and guar. P/P £1.50, Bobbins 80p.

FERG., HMY, MARCONI, ULTRA	R.B.M. T20, T22	£9.80
1590, 1591, 1612, 1613, 1712	R.B.M. T20, T22 Bobbin	£5.60
FERGUSON 3787 (Normende)	DECCA Bradford (state Mod No)	£8.80
THORN 1600, 1615, 1690, 1691, 1790	DECCA 100	£8.80
THORN 3000/3500 SCAN, EHT	FIDELITY ZX2000, 3000 (Not 22)	£15.50
THORN 8000	GEC 2110 series	£10.60
THORN 9000 to 9600	ITT CVC 5 to 9, CVC20	£9.80
THORN TX9	ITT CVC25, CVC30 series	£8.80
THORN TX10	ITT CVC45	£9.80
	PYE 725 (90°) 731 to 741	£9.20
	PHILIPS G8	£8.80
	PHILIPS G9	£7.80
	PHILIPS KT3	£9.80
	PHILIPS K30, K35	£27.00
	PHILIPS CTX-E	£22.50
	PHILIPS CTX-S	£22.50

OTHERS AVAILABLE, PRICES ON REQUEST.

TRIPLERS Full range available. Mono & Colour.  
SPECIAL OFFER TRIPLERS  
THORN 1500 5 Stick £1.50, 1500 3 Stick £1.50 p.p. 80p.  
6-3V CRT Boost Transformers for Colour & Mono £5.90 p.p. £1.40.  
455 CRYSTALS for Remote Control Handsets. 4 for £1.00 p.p. 50p.  
VHF to UHF Converters £26.50 p.p. £2.50.  
HELICAL POTS (standard 100K). 6 for £1.00 p.p. 50p.

CALLERS WELCOME AT SHOP PREMISES  
THOUSANDS OF ADDITIONAL ITEMS, ENQUIRIES INVITED  
LARGE SELECTION TESTED COLOUR PANELS POPULAR MODELS

Goods available if in stock immediately over shop counter (Mail order between 3 days and 1 week from receipt of order). ADD VAT 15%


Telephone 01-794 8751, 794 7346

# MANOR SUPPLIES

172 WEST END LANE, LONDON, NW6 1SD

100 yds. W. Hampstead Tube Stn. (Jubilee) Buses 28, 159, C11 pass door  
W. Hampstead Brit. Rail Stn. (Richmond, Dalston, Stratford, N. Woolwich)  
W. Hampstead Brit. Rail Stn. (Bedford, Luton, Kings X, Crawley, Gatwick, Brighton)  
Access from all over Greater London.

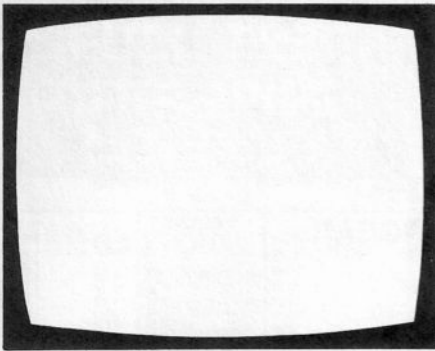PLEASE ADD VAT 15% TO ALL PRICES INCL P+P



# TELEVISION

January  
1989

Vol. 39, No. 3  
Issue 459

On sale December 21st

## COPYRIGHT

© IPC Magazines Limited, 1989. Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

## CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., King's Reach Tower, Stamford Street, London SE1 9LS.

## INDEXES

Indexes to Vols. 35, 36 and 37 are available at 80p each from the Editorial Office (address above).

## SUBSCRIPTIONS

An annual subscription costs £18 in the UK, £21 overseas (by surface mail). Send orders with payment to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex, RH16 3DH.

## BACK NUMBERS

Subject to availability, copies of issues published during the last 12 months are available at £1.80 each from Television, Vouchcheck Services, Unit A6, Poplar Business Park, Prestons Road, London E14 9LR. Please make cheques/postal orders payable to IPC Magazines Ltd.

## QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. Correspondents should enclose a stamped addressed envelope. Requests for advice on dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Service Bureau". Send to the address given above (see "correspondence").

## this month

- 173 **Leader**  
174 **Letters**  
179 **A TTL Logic Probe/Analyser** *Stuart Anderson, B.Ed. (Hons.)*  
Full constructional details of a probe that indicates not only the logic state at any point in a digital circuit but also whether a connection is open-circuit. With an introduction to the use of standard gates in combinational logic. Circuit state is indicated by a seven-segment display.
- 183 **Camera Workshop Accessories** *Nick Beer*  
The requirements of a camera/camcorder workshop differ somewhat from those of a VCR/TV workshop. In particular alignment cards and controllable lighting are required.
- 184 **How to Deal with EHT Arcing** *Nick Beer*  
A bodge job is all too often done when the problem with a TV set is e.h.t. arcing. This can lead only to a quick come-back. How to do the job properly.
- 185 **Still Confused** *Les Lawry-Johns*  
Confusion this time over e.h.t. triplers.
- 186 **Teletopics**  
News, comment and developments.
- 188 **IBC '88** *Geoff Lewis, B.A., M.Sc.*  
A report on the 1988 International Broadcasting Convention, where the main topic of interest was high-definition TV.
- 190 **Practical Guide to Satellite TV** *Roger Bunney*  
With Astra about to be launched, interest in the practicalities of satellite TV reception is at its highest ever. A report on equipment and installation based on over a year's experience of DXing with the 11GHz satellites.
- 192 **Servicing the Ferguson TX10 Chassis** *K. Rutherford*  
This popular and reliable chassis was for some years used in large-screen, 110° Ferguson models. A survey of the few faults that do occur from time to time.
- 195 **Next Month in Television**  
196 **At the Japan Electronics Show** *George Cole*  
A report on the latest consumer electronic products revealed at this leading exhibition.
- 198 **VCR Clinic**  
Reports from Eugene Trundle, Nick Beer, Philip Blundell, Eng. Tech., Chris Plaice, Ian Bowden, Alfred Damp and Joe Cieszynski.
- 202 **TV Fault Finding**  
Reports from Philip Blundell, Eng. Tech., Mick Dutton, B. Ross, Bob McClenning, John Coombes, J.S. Ruwala, J.L. Howard, Ray Vesey, David Botto, J. Olijnyk and Nick Beer.
- 204 **Test Report: Grundig Oscilloscopes** *Steve Beeching, T. Eng.*  
The Grundig M022 and M053 are well suited to the needs of modern consumer electronics servicing.
- 206 **Long Distance Television** *Roger Bunney*  
Reports on DX conditions and reception and news from abroad.
- 209 **Service Bureau**  
210 **Test Case 313**

OUR NEXT ISSUE DATED FEBRUARY WILL  
BE PUBLISHED ON JANUARY 18

# P.V. TUBES

104 ADDEY STREET, AORINGTON, LANCS  
 Tel: 0254 36521/32611/390936  
 Telex: 635562 Griffin G (For P.V.)  
 Partners S. & B. Cucknell  
 24hr. answering service

TIARED  
 COUNTEE  
 OPEN  
 MUM 5A1  
 9am-5pm  
 New Fax No.  
 0254 395361

Up to 12% DISCOUNT on all items  
 except where it states zero rate.  
 Bulkier items will be sent by carrier  
 £7.50 + VAT up to 25K (except tubes)  
 We do not despatch on Saturdays.

THERE IS VAT ON D.I.B.  
 ALL ITEMS ARE SUBJECT TO V.A.T. AT THE RATE OF 15% UNLESS OTHERWISE STATED.  
 Spec. for all goods unless stated. V.A.T. invoice on request. Give us a ring - we'll give you service. Please ask if what you need is not listed - we will try to help. Prices are subject to change without notice. In some cases we may have to supply an equivalent. We need expiry dates for credit card orders.

INTEGRATED CIRCUITS			
AN214Q	3.91	SL1430	1.58
AN240	3.84	SL1432	3.36
AN318	3.84	SL76544	2.05
AN262	4.10	SL490	1.89
AN301	5.15	SN76709	8.00
AT1750	3.97	SN76115N	2.27
AN6341N	8.97	SN76131N	2.00
AN6344	7.85	SN76226DN	2.72
AN6360	6.81	SN76533N	1.70
BA521	1.50	SN76544N	2.35
BA536	2.00	SN76660N	8.00
CA555	46	SN76666N	1.52
CA556	84	SN76530A	1.47
CA741	25	STR5412	8.45
CA748	45	STK015	7.36
CA1532	4.20	STK435	9.06
CA3065	1.80	STK436	6.50
DIC141WF	30	STK437	6.00
CV12E	3.07	STK439	8.40
GH3F	1.82	STK459	9.50
HA1137	3.20	STK441	11.57
HA1151	3.89	STK461	12.60
HA1175INT	10.82	STK465	12.30
HA1342	5.58	STK463	14.60
HA1306N	2.60	STK1219	17.27
HA1366WR	1.50	STK4352	6.00
HA1377	3.65	STR441	6.50
HA11219	4.21	STR454	4.73
HA11244	4.04	STR451	6.50
HA11741	23.22	STR6020	5.80
HA13008	13.58	SW153	3.90
IS1555	43	TA7050P	95
LA3350	95	TA7051P	1.60
LA4031P	3.21	TA7063P	2.20
LA4032P	1.30	TA7074P	3.46
LA4102	1.10	TA7108P	3.43
LA4112	3.25	TA7120P	2.43
LA4422	1.20	TA7129AP	3.74
LA7801	2.20	TA7130P	1.93
LC7130	5.93	TA7146P	4.67
LC7120	5.87	TA7193P	5.67
LC7137	5.80	TA7171P	8.90
LM1011	3.25	TA7172P	8.90
LM8361=		TA7173P	8.90
MM5387ANN	4.15	TA7176P	2.00
M293	7.10	TA7202P	4.27
M5079SP	6.98	TA7204P	1.35
M54544L	3.80	TA7205AP	3.72
MC13002	4.98	TA7208P	1.44
MC14493	8.97	TA7210P	6.60
MN1219	11.43	TA7222	1.20
MB3712	2.60	TA7223P	3.74
MC1307	1.99	TA7227P	5.98
MC1310P	1.84	TA7228P	5.98
MC1327	1.70	TA7310P	2.78
MC1330P	1.84	TA7310P	4.39
MC1351P	2.93	TA7611AP	2.70
MC1349	1.99	TAA570	3.98
MC1350	1.50	TAA310	2.83
MC1352	1.75	TAA320	5.00
MC1495L	3.00	TAA630	3.90
ML231	2.20	TBA120SA	1.49
ETTR6016		TBA120B	1.30
ML232	2.20	TBA120SB	1.37
ML237	2.50	TBA120T	1.47
ML238	6.00	TBA120U	1.49
ML922	3.29	TBA1440G	2.50
ML923	2.90	TBA395	50
MSM5807	7.87	TBA396	67
MS1513L	2.80	TBA440N	
MS1515L	3.28	(TBA1441)	2.75
SA11025	8.50	TBA440P	
SA11124	5.34	(TBA1440G)	2.50
SA11250	6.99	TBA480Q	1.82
SA5000Q	4.15	TBA510	3.00
SA5010Q	6.30	TBA520(Q)	1.10
SA5012	6.50	TBA530(Q)	1.00
SA5020	5.90	TBA540	1.10
SA5030	8.25	TBA560(Q)	1.10
SA5050	8.50	TBA570	1.79
SAF1032	6.30	TBA690	1.50
SAF1039	7.77	TBA700	2.12
SAS560S	2.07	TBA720	2.64
SAS570S	2.07	TBA750	2.98
SAS660	3.25	TBA800	1.90
SAS670	3.25	TBA810AS	5.00
SAS580	2.90	TBA820	1.25
SAS590	2.90	TBA820M	1.70
SG-264A	5.02	TBA890	3.94
SG629	8.15	TBA920(Q)	1.20
SG-6533	13.20	TBA950(2X)	1.08
SL971B	7.00	TBA970	4.09
SL917B	9.25	TBA990	1.10
SL1310	1.80	TCA760	2.30
SL1327Q	1.20	TCA270SQ	2.50
TCA800	5.95		
TCA830	3.44		
TCA900	2.20		
TCA910	2.20		
TCA940	90		
TCP4621AF6	13.87		
TD4440	2.20		
TDA1002	1.95		
TDA1003A	5.50		
TDA1006A	7.58		
TDA1005	3.60		
TDA1010	3.30		
TDA1011	4.00		
TDA1035	4.70		
TDA1037	2.95		
TDA1044	4.37		
TDA1060A	4.44		
TDA1083	1.68		
TDA1170S	3.00		
TDA1190	3.50		
TDA1190P	3.50		
TDA1180	2.91		
TDA1236	3.44		
TDA1270	3.95		
TDA1327	1.70		
TDA1352B	1.60		
TDA1412	95		
TDA1415	1.40		
TDA1470	4.67		
TDA1770	5.60		
TDA1908A	1.95		
TDA1950	2.39		
TDA2002	75		
TDA2003	1.10		
TDA2004	1.60		
TDA2006	1.45		
TDA2010	2.40		
TDA2140	5.95		
TDA2151	3.25		
TDA2020	4.66		
TDA2030	2.80		
TDA2270	1.65		
TDA1870	6.46		
TDA2523	3.40		
TDA2524	2.25		
TDA2525	4.00		
TDA2530	2.70		
TDA2532	9.10		
TDA2540	95		
TDA2541	3.84		
TDA2560	1.15		
TDA2576A	7.84		
TDA2577	4.73		
TDA2578A	5.12		
TDA2581	3.95		
TDA2582	2.60		
TDA2593	2.95		
TDA2600	6.90		
TDA2611A	2.35		
TDA2640	2.90		
TDA2653A	5.90		
TDA2680	3.40		
TDA2690	2.72		
TBA2900	1.60		
TDA3190	2.00		
TDA3330	2.21		
TDA3500	6.90		
TDA3540	2.35		
TDA3541	2.24		
TDA3560	6.00		
TDA3561A	6.66		
TDA3562	8.60		
TDA3571	3.75		
TDA3650	3.85		
TDA3651A	4.50		
TDA3652	6.00		
TDA3950	4.37		
TDA4420	5.55		
TDA4500	5.84		
TDA4503	5.68		
TDA4505	6.03		
TDA4600	2.95		
TDA4600-2D	2.95		
TDA8180	4.00		
TDA8190	4.94		
TDA9503	4.21		
TEA1009	1.86		
UPC554	2.63		
UPC566H	75		
UPC575C2	89		
UPC576H	1.90		
UPC585	3.06		
UPC587C2	2.34		
UPC1025H	2.15		
UPC1026H	90		
UPC1028H	90		
UPC1032H	58		
UPC1042C	1.56		
UPC1158H	2.45		
UPC1158H	3.50		
UPC1163H	2.48		

NEW PRODUCTS		
Sanyo 5000 PS3BSF Video Head		29.95
Amstrad 4600 PSF2 Video Head		25.80
Amstrad 9000 PSF1 Video Head		25.80
Amstrad 7000 3HSSR Video Head		25.00

BELT KITS		
VK32 Sanyo 1100/1300/1500		75
VK33 Ferguson 3V35/6		69
VK34 Ferguson 3V42/5/8		90
VK35 Fisher SVHP 710 716 722		1.20
VK37 Hitachi 9300		85

TAKE UP IDLERS		
Fisher 143-0-4904-00900		3.95
Fisher 143-0-4204-00300		4.50

SUPERWICK DESOLDER BRAD		
2mm x 1.6m		89
1.5mm x 1.6m		89
2mm x 30m		11.99
1.5mm x 30m		11.99

T.V. WALL BRACKETS		
P5245 Teletwist (12" 20")		24.16
P6045 Designer Twister		27.00
P6041 Little Twister		14.08
P5218 Swivel and Tilt Bracket		24.67

NEW POWER SENSOR SET TOP AERIAL WITH BUILT IN AMPLIFIER £24.90		
General Equipment		19.00
Degaussing Coil Stick		1.50
Electric Circuit Tester		10.90
Probes (x10) or (x1)		13.25
Philips Switchable Probes		6.95
Automatic Wire Strippers		1.18
I.C. Inserters		4.20
Micro Pliers		5.00
Micro Cutters		6.00
Trim Tools Metal Ended		1.20
Snip Cutters sm.		1.20
Long Nose Pliers		1.20
Sm. Neen Screwdriver		65
Quick Set Adhesive (Superglue)		75
Avo Meters Factory recd.		119.00
Avo Battery		2.09
Solder Sucker Antistat min.		4.50
Solder Sucker Antistat std.		5.40
Solder Sucker Antistat lge.		6.20
Solder 500g		See Special Offer
D.I.Y. Solder Small Pack		45
Solder Sucker Nozzles		81
Solda Mop Snd.		77
For sold. irons see Antex/Weller Under Specific Spares		
Choc Bloc 5A		20
Fuse Wire 5A, 15A, 30A		05
Fluorescent Starter (4-80W)		45
Battery Press Sluds min.		11
Battery Press Sluds std.		11
Vero Type Board		Lg. 2.59
Double Sided Adhesive Tape		5.75
Tinned Copper Wire		
18SWG 45 Amp		1.00
14SWG 100 Amp		1.00
17SWG 60 Amp		1.00
19SWG 45 Amp		1.00
20SWG		1.00
Insulated Copper Wire		9.11
Cable Ties ALT21 per 100 (large)		1.69
Power Adaptor (12v)		5.95
Reg. 89 Power Adap.		5.50
Reg. 850 Power Adap.		6.50
Philips Screwdriver		Sm. 1.95 Lg. 2.35

GENERAL EQUIPMENT		
Degaussing Coil Stick		19.00
Electric Circuit Tester		1.50
Probes (x10) or (x1)		10.90
Philips Switchable Probes		13.25
Automatic Wire Strippers		6.95
I.C. Inserters		1.18
Micro Pliers		4.20
Micro Cutters		5.00
Trim Tools Metal Ended		6.00
Snip Cutters sm.		1.20
Long Nose Pliers		1.20
Sm. Neen Screwdriver		65
Quick Set Adhesive (Superglue)		75
Avo Meters Factory recd.		119.00
Avo Battery		2.09
Solder Sucker Antistat min.		4.50
Solder Sucker Antistat std.		5.40
Solder Sucker Antistat lge.		6.20
Solder 500g		See Special Offer
D.I.Y. Solder Small Pack		45
Solder Sucker Nozzles		81
Solda Mop Snd.		77
For sold. irons see Antex/Weller Under Specific Spares		
Choc Bloc 5A		20
Fuse Wire 5A, 15A, 30A		05
Fluorescent Starter (4-80W)		45
Battery Press Sluds min.		11
Battery Press Sluds std.		11
Vero Type Board		Lg. 2.59
Double Sided Adhesive Tape		5.75
Tinned Copper Wire		
18SWG 45 Amp		1.00
14SWG 100 Amp		1.00
17SWG 60 Amp		1.00
19SWG 45 Amp		1.00
20SWG		1.00
Insulated Copper Wire		9.11
Cable Ties ALT21 per 100 (large)		1.69
Power Adaptor (12v)		5.95
Reg. 89 Power Adap.		5.50
Reg. 850 Power Adap.		6.50
Philips Screwdriver		Sm. 1.95 Lg. 2.35

COMMODORE ICs		
6510 CPU		7.07
6526 CIA Keyboard		5.11
Int.		5.74
6561 Col. Vid.		7.74
6569 Cont.		6.90
6581 Sound		20.77
Gen.		7.79
901225 Char.		7.79
ROM		3.37
901226 Basic		6.45
ROM		6.45
ROM		6.20
906114 PLA		4.51
4164 RAM		1.95
Timer 555		4.6
8501		4.18
8701 Clock Chip		5.46
8360		19.61

NEWS SPECTRUM + 3 CASSETTE LEADS £1.95		
UPC1167C2		2.70
UPC1168C		3.20
UPC1176C		2.53
UPC1177H		3.15
UPC		

### VIDEO BELT KITS

#### ★ PRICES DOWN ★

VKIT 1	AKAI JVC	9300/5500/9800	2.48
	HR3300/3300/3360		
	TCE	HR3300/18/22	
VKIT 2	PANASONIC	NV7000/7200	1.45
VKIT 3	SONY	SLS57	2.25
VKIT 4	SONY	SL8000/8500/8600/3.60	
VKIT 5	SONY	SL3000UB	2.10
VKIT 6	PANASONIC	NV3000UB	1.99
VKIT 7	SANYO	9300P	2.75
VKIT 8	PANASONIC	NV2000B	1.73
VKIT 9	PANASONIC	NV8000/8610/V0111.50	
VKIT 10	TOSHIBA	V8600	1.45
VKIT 11	SHARP	VT7300	1.50
VKIT 13	SANYO	VT33000	0.95
VKIT 14	SANYO	VT63000	1.85
VKIT 15	JVC	HR7650/3V31	2.00
VKIT 16	HITACHI	5000	1.90
VKIT 17	SHARP	8300	1.76
VKIT 18	SHARP	9300	1.50
VKIT 19	HITACHI	VT9000	1.05
VKIT 20	HITACHI	VT1333	1.30
VKIT 21	HITACHI	9500	1.12
VKIT 22	SONY	SLS6	1.90
VKIT 23	SANYO	5500	1.05
VKIT 24	PANASONIC	NV3000/333	1.55
VKIT 25	TOSHIBA	VT540	1.90
VKIT 26	JVC	HR7000	0.96
VKIT 27	THORN	3V29R/47200	1.75
VKIT 28	AMSTRAD	7000	1.45
VKIT 29	PANASONIC	NV777	1.80
VKIT 30	SONY	19	2.20
VKIT 31	TOSHIBA	9600	1.20

### ★ PRICES DOWN ★

### VIDEO PINCH ROLLERS

PANASONIC	NV7000	3.75
SANYO	VT3300/UBS/7000	3.75
SONY	C7/J7/SL17	3.75
JVC	TCE3000/01/06/18/23/24	3.75
JVC	HR2200/3320/3330/3660/1100/7700	3.75
AKAI	V59700	3.75
HITACHI	VT5000	3.75
SHARP	V6300/6500	3.75
SONY	TC6 GEN	3.75

### ★ PRICES DOWN ★

### VIDEO IDLER TYRES

SONY	O.Dia	1 Dia	Width	50p
SONY	23.7	17.4	4.9	50p
SONY	24.2	18	5.1	50p
HITACHI	31.8	25	4.9	50p
PANASONIC	31.8	25	3.9	50p
AKAI	26	20	3.9	50p
JVC	39.3	32.8	3.9	56p
JVC	31.2	23.9	4	56p
NATPAN	31.2	23	3.1	56p

### ANTEX

C15 Iron 240v	6.20
C240 Element	2.75
Bis 102, 106, 820, 821	1.10
CS 17W Iron 240v	6.40
CS240 Element	2.75
Bis 1100, 1101, 1106	1.10
X525W Iron 240v	2.75
X5240 Element	1.10
Bis 50, 51	1.10
Temperature Control 30W Iron CSTC	16.95
40W Iron XSTC	16.95
Unit TCSV1	68.95
Antex Stand	1.10
MLKX Auto Rep. Kit	1.10
Cordless Gas Iron	15.99
Tips for Gas Iron	5.00
Turbo Recl. Iron Kit	16.99
Philips 25 Watt Iron	4.50

### SERVISOL

Freeze II	1.34
Super Semisol	1.18
Foam Cleanser	1.18
Plastic Seal	1.26
Silicone Grease	1.46
Silicone Grease (Tubes)	1.82
Aero Klene	1.40
Excel Polish	0.96
Video Head Cleaner	1.08
Super 40	1.80
Fire Extinguisher	3.80
Heat Sink Compound	1.20
Soldia Map Slid	0.78
Hylofil Silicone Rubber	2.98
Aero Duster	1.40
Coddlene 110 Degreasing Solvent	1.78
Antistatic Spray	1.18

### TURBO RECHARGEABLES

Drill Kit	25.99
Sold. Iron Kit	16.99
Rep. Tps	2.20
Rep. Bubs	.60

### BELLS/BOXES

A75 SHORROCK ACDRN 75 PANEL	32.50
B1 EUROBEEL (No. S.A.B.)	21.00
B2 EUROBEEL (with S.A.B.)	26.95
BV 6V BATTERY FOR EUROBEEL	3.75

### SOUNDERS/SIRENS

S2 712 EXTERNAL SIREN (1150b)	5.75
S4 1010/2010 EXTERNAL SIREN (1150b)	5.95
S22 DYNABLAST (1270b)	18.14
S13 SOUND BOMB 1 (1040b)	3.37
S14 SOUND BOMB 2 (1110b)	5.17
S15 SOUND BOMB 3 MULTITONE	4.50
S16 PZ28 (1050b)	4.61
S17 MJKR (1100b)	5.28
S18 362 PIEZO (1100b)	7.80
S19 12V MUSICAL BUZZER	1.56
MB01 722 BUZZER	0.60
802 PNB27 BUZZER	0.70

## VIDEO SPARES

WE HAVE A LARGE STOCK LISTED UNDER SPECIFIC MANUFACTURERS IN CATALOGUE FOR THORN, SONY, HITACHI, FIDELITY, NATIONAL PANASONIC, PHILIPS.


### SPECIAL PRICES ON 5+ MIX VIDEO HEADS PLEASE ASK

REPLACEMENT VIDEO HEADS	JVC	NAT. PAN.	TOSHIBA
AKAI V51 3HSSV	18.00	NV100 3HSSU1N	25.99
V52 3HSSV	18.00	NV230 3HSSU2N	36.97
V53 3HSSV	18.00	NV250 3HSSU2N	36.97
V55 3HSSV	18.00	NV270 3HSSU2N	36.97
V510 3HSSV	18.00	NV280 3HSSU2N	36.97
V577 3HSSV	18.00	NV300 3HSSU	18.00
V588 3HSSV	18.00	NV320 3HSSU	18.00
VT100 3HSSV	18.00	NV330 3HSS3N	35.99
VT200 3HSSV	18.00	NV340 3HSSN	18.00
VT300 3HSSV	18.00	NV366 3HSS4NA	43.48
VT400 3HSSV	18.00	NV370 3HSSU1N	25.99
VS7200 3HSSV	18.00	NV380 3HSSN	18.00
VS9300 3HSSV	18.00	NV450 3HSSU2N	36.97
VS9700 3HSSV	18.00	NV470 3HSSU	36.97
VS9800 3HSSV	18.00	NV480 3HSSU2N	36.97
VS9900 3HSSV	18.00	NV660 3HSS3N	25.99
VS9900 3HSSV	18.00	NV730 3HSS4NB	41.95
VS9900 3HSSV	18.00	NV777 3HSS3N	35.99
VS9900 3HSSV	18.00	NV861 3HSSN	18.00
VS9900 3HSSV	18.00	NV2000 3HSSN	18.00
VS9900 3HSSV	18.00	NV3000 3HSSN	18.00
VS9900 3HSSV	18.00	NV7000 3HSSN	18.00
VS9900 3HSSV	18.00	NV7200 3HSSN	18.00
VS9900 3HSSV	18.00	NV7500 3HSSN	18.00
VS9900 3HSSV	18.00	NV7800 3HSSN	18.00
VS9900 3HSSV	18.00	NV8100 3HSSN	18.00
VS9900 3HSSV	18.00	NV830 3HSSV	18.00
VS9900 3HSSV	18.00	NV831 3HSSV	18.00
VS9900 3HSSV	18.00	NV832 3HSSV	18.00
VS9900 3HSSV	18.00	NV954 3HSSV	18.00
VS9900 3HSSV	18.00	NV955 3HSSV	18

### HAMEG OSCILLOSCOPES

HAMEG are Europe's top selling DUAL TRACE OSCILLOSCOPES. Select from four superb models. All, with the exception of the HM 1005, incorporates a useful COMPONENT TESTER. Size - all models - 285mm x 145mm x 380mm. Clear display 8 x 10cm. Mains supply: 110 125 220 240V AC 50/60Hz.  
All supplied with 2 PROBES, a COMPREHENSIVE MANUAL and a 2 YEAR WARRANTY.

#### HM203-6 20MHz STANDARD

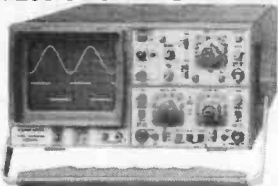


Price £314.00 + £47.10 V.A.T.

#### SPECIFICATION

- \* 2 Channels
- \* Bandwidth: DC-20MHz
- \* Sens: Ch1, Ch2, 2mV/cm
- \* Timebase: 0.2s-20ms/cm
- \* Triggngng: DC-40MHz
- \* Active TV-Sync-Separator
- \* Variable hold-off
- \* Trigger LED indicator
- \* Calibrator: 1KHz Square wave
- \* Component tester
- \* Plus many features

FREE Securicor Delivery

#### HM604 60MHz UNIVERSAL

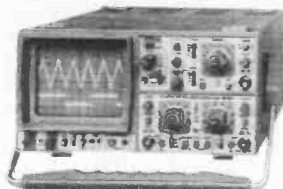


#### SPECIFICATION

- \* 2 Channels
- \* Bandwidth: DC-60MHz
- \* Sens: Ch1, Ch2, 1mV/cm
- \* Timebase: 2.5s-5ns/cm
- \* Triggngng: DC-80MHz
- \* Active TV-Sync-Separator
- \* After delay trigger
- \* Sweep delay \* Delay line
- \* Trigger LED indicator
- \* Calibrator: 1KHz & 1MHz Sq. Wave
- \* Component tester
- \* Plus many more superb features

Price £575.00 + £86.25 V.A.T.

FREE Securicor Delivery

#### HM1005 100MHz UNIVERSAL

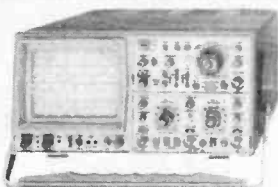

Price £726.00 + £108.90 V.A.T.

#### 3 CHANNELS-UP TO 6 TRACES

#### SPECIFICATION

- \* 3 Channels
- \* Bandwidth: DC-100MHz
- \* Sens: Ch1, Ch2, Ch3, 1mV/cm
- \* Timebase A: 2.5s-5ns/cm
- \* Timebase B: 0.2s-5ns/cm
- \* Triggngng: DC-130MHz
- \* After delay trigger \* Delay line
- \* Trigger LED indicator
- \* Overscan LED indicator
- \* Active TV-Sync-Separator
- \* Calibrator: 1KHz & 1MHz Sq. Wave
- \* Plus many more excellent features

FREE Securicor Delivery

#### HM205-2 20MHz DIGITAL STORAGE

#### SPECIFICATION

- \* Digital Storage
- \* Analogue real time (Same as 203-6)
- \* Bandwidth: DC-20MHz
- \* Sens: Ch1, Ch2, 2mV/cm
- \* Timebase Analogue: 0.2s-20ns/cm
- \* Timebase Digital: 5s-2µs/cm
- \* Triggngng DC-40MHz
- \* Active TV-Sync-Separator
- \* Max sampling rate: 2x25MHz
- \* Memory: 2x1024x8 Bit
- \* Dot Joiner
- \* Printer/plotter output
- \* Component tester
- \* Plus many more useful features

Price £527.00 + £79.05 V.A.T.

FREE Securicor Delivery

#### B.K.'s CRT TESTER-REJUVENATOR



Tests and rejuvenates blue, green & red guns separately. Fitted with delta and P.I.L. sockets. Compact size 120x65x60 mm. Supply 240V AC

Price £32.00 + £4.80 V.A.T.

#### B.K.'s REVOLUTIONARY DYNAMIC 'LOPT' TESTER

Revolutionary L.O.P.T. tester. Operates in dynamic mode which actually tests the L.O.P.T. under high voltage conditions without de-soldering or removal. Size 75x100x40 mm. Supply 240V AC



Price £25.99 + £3.90 V.A.T.

#### THANDAR SC110A PORTABLE OSCILLOSCOPE



Price £195.00 + £29.25 V.A.T.

\* Full trig. fac. inc. TV frame etc.

- \* Only 2 1/4" thick
- \* Fits in a brief case
- \* Sens: 10mV
- \* Bandwidth 10MHz
- \* Battery or mains adaptor
- \* Size 255mm x 148mm x 50mm

#### ACCESSORIES

- Carry Case £6.25 + £0.93 V.A.T.
- Probe £7.50 + £1.30 V.A.T.
- Mains Adaptor £7.30 + £1.09 V.A.T.

#### DIGITAL LCR METER

- \* LCD Display
- \* 18 Ranges
- \* Inductance 1µH - 2H
- \* Capacitance 1pF - 200µF
- \* Resistance 1ohm - 20Mohm
- \* High accuracy



Price £95.00 + £14.25 V.A.T.

#### INSULATION TESTER 500V



- \* Electronic battery operated
- \* Measuring Voltage 500V DC
- \* Measuring Range 0-100Mohm
- \* Centre scale 2Mohm

Price £65.00 + £9.75 V.A.T.

### B & K PRECISION CRT ANALYSER-RESTORER

The number one CRT Test Instrument. Over 5000 U.K. Television engineers wouldn't be without it.

\* All CRT's checked identically including all in-line and one gun types \* Tests all three guns of colour CRT's simultaneously under actual operating conditions (model 467) \* Exclusive multiplex technique (model 467) \* Measures true dynamic beam current that actually passes through G1 aperture to screen \* Measures all shorts and leaks - preserving more CRT's \* Tests focus electrodes lead continuity finding faults that other Testers miss \* Uses most powerful restoration method known with minimum danger to CRT \* Rejuvenated CRT's guaranteed as new for two years \* Obsolescence proof: Perpetual set up chart up-dated and new adaptors development \* Tests and rejuvenates VDU's and Oscilloscope tubes \* A range of over 40 CRT base adaptors available \* Increases profit \* Pays for itself in months.

#### PRICES

Model 467 Tri-dynamic three meter instrument Inc. 6 common adaptors	£395.00 + £59.25 V.A.T.
Without adaptors	£344.00 + £51.60 V.A.T.
Model 470 Single meter instrument Inc. 6 common adaptors	£294.00 + £44.10 V.A.T.
Without adaptors	£244.00 + £36.60 V.A.T.

Technical leaflets available. GET INTO PROFIT NOW!

### SADELTA FIELD STRENGTH METER TC-402

THE SADELTA FIELD STRENGTH METER TC-402 has been designed to measure the signal levels delivered by the antenna to a TV or FM receiver. In order to test the performance of the antenna and evaluate the best conditions during installation etc. To facilitate measurements, the tuning frequency readout is shown on a digital display.

#### FEATURES

- \* Covering FM and all TV bands (UHF/VHF) including CATV freq.
- \* Digital tuning display (3 digits) for direct frequency readout.
- \* Accurate 10 turn tuning potentiometer.
- \* Built-in loudspeaker enables monitoring of sound in AM/FM.
- \* Meter measurement in voltage and dB from 20µV (26dB/µV).
- \* Continuity tester 0-500 ohms.
- \* Fully portable (battery).
- \* Sturdy carry case.



Price £249.00 + £37.35 V.A.T.

### SADELTA COLOUR PATTERN GENERATORS

THE SADELTA RANGE OF HAND HELD COLOUR PATTERN GENERATORS is intended for use in production, installation and service of both colour and monochrome TV sets, video and computer monitors. In order to control and adjust the various parameters, eight switchable patterns are provided. The technician has ready access to Laboratory, workshop and field use as the Generator has been designed using the latest micro-technology to achieve truly pocket size instruments. Internal re-chargeable Ni-Cd's. Supplied with 9V power supply charger. Size 131mm x 81mm x 23mm.

#### T.V. PATTERN GENERATOR PAL MC11B UK

- \* Band IV (21-34)
- \* Band III (5-12)
- \* PAL 1
- \* O/Put 10mV into 75ohms
- \* Sound output

Price £124.95 + £18.74 V.A.T.

#### PAL VIDEO COMPOSITE GENERATOR

- \* PAL B.G.I
- \* O/Put 1V p.p. @ 75ohms
- \* Audio O/Put 10mV
- \* Switching 12V @ 4K7ohms

Price £124.95 + £18.74 V.A.T.

#### SECAM VIDEO COMPOSITE GENERATOR


- \* SECAM B.G.D.K.L.
- \* O/Put 1V p.p. @ 75ohms
- \* Audio O/Put 10mV
- \* Switching 12V @ 4K7ohms

Price £124.95 + £18.74 V.A.T.

#### R.G.B. PATTERN GENERATOR

- \* O/Put sigs. Pos. RGB
- \* Neg. Composite
- \* O/Put TTL 5V-P-P
- \* Blank Pulse etc. CCIR

Price £111.95 + £16.79 V.A.T.

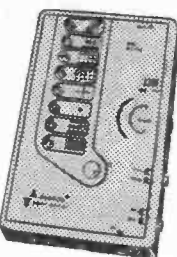

#### DIGITAL THERMOMETER



- \* Pocket Size
- \* -50°C to +75°C
- \* 1°C Resolution
- \* 0.5" LCD
- \* Supplied with thermocouple

Price £59.50 + £8.92 V.A.T.

#### 200MHz DIG. FREQ. METER



- \* Pocket Size
- \* 8 Dig. LED Display
- \* Freq. Range 20Hz to 200MHz
- \* Resolution 0.1Hz
- \* Sensitivity 10mV

Price £75.50 + £11.32 V.A.T.



#### DIGITAL CAPACITANCE METER

- \* High Accuracy
- \* 0-1pf-2,000µf
- \* LCD display
- \* 8 Ranges
- \* Accuracy ±0.5%
- \* Full scale ±1 digit

#### PRICE

£38.00 + £5.70 VAT  
Case Included



Price £23.00 + £3.45 V.A.T. each

The THANDAR TP1 LOGIC PROBE and TP2 LOGIC PULSER are effective and economical tools for checking both TTL and CMOS circuits. TP1 can show 14 different circuit conditions and can detect pulses down to typically 10ns. TP2 can inject a signal directly into a circuit without damaging sensitive components. Together they can stimulate and monitor responses of components 'in circuit', greatly aiding fault finding.




U.K. POST PAID, export enquires welcome. Visa/Access or cheque with order, payable B.K. Electronics. Official Orders welcome from Govt. Depts., Colleges, P.L.C.'s etc. Large S.A.E. for technical leaflets of complete range. Delivery normally within seven days.



## B. K. ELECTRONICS DEPT. T

UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX. SS2 6TR TEL: 0702-527572

# A Merry Clearance and Happy New Stock

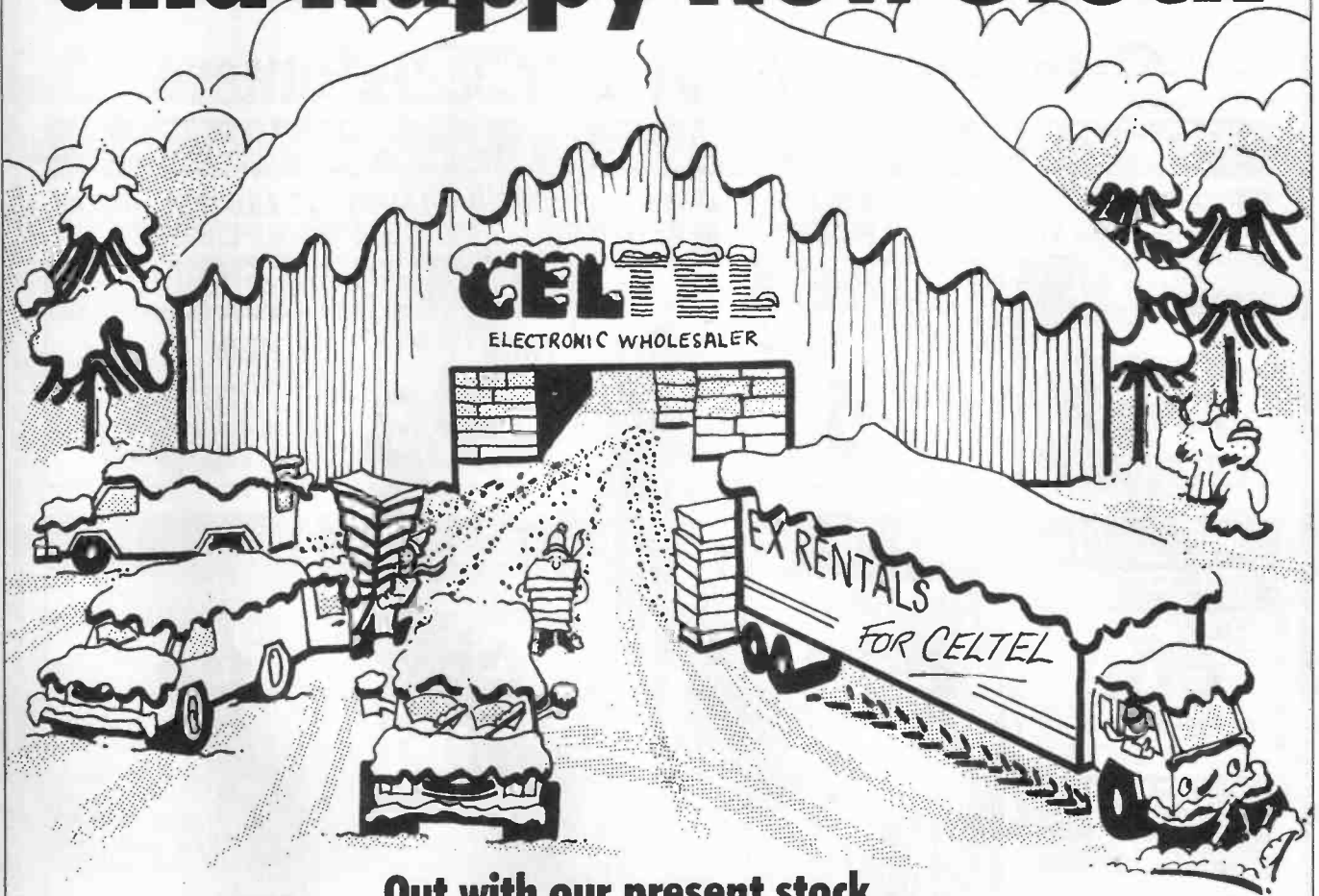

## Out with our present stock . . .

Cetel are clearing warehouse space by offering unbeatable discounts on all Ex-rental TV's, VCR's, Portables, Video Tape . . . you name it! Right up until Christmas.

### VIDEOS AND TV'S FROM NEW SOURCES

"ONE FOR ALL" REMOTE CONTROLLER  
TELEPHONE ANSWERING MACHINES  
FAX MACHINES (IN CAR FAX)

INFRA RED SECURITY DETECTOR  
WIRELESS BURGLAR ALARMS  
SOLAR LAMPS

### PLUS MUCH MORE AT UNBEATABLE PRICES

**STAINES**

Unit 18, Central Trading Estate,  
Staines, Middlesex TW18 4XE  
Tel 0784 64551.

# CELTEL

## CALL: 0800 289239

TOLL FREE LET CELTEL PICK UP THE COST OF YOUR CALL

ALL PRICES EXCLUSIVE OF VAT

**WEST THURROCK**

2 Breach Road, West Thurrock,  
Essex RM16 1NR

FAX 0256 474900



**A Happy Christmas and a Prosperous New Year to all our Customers**

**PRE-CHRISTMAS SALE AT SUPERVISION!**

TOP QUALITY SETS & VIDEOS TO SET YOU UP FOR THE WINTER TELEVIEWING AND VIDEO BOOM. BRIGHTEN YOUR WINTER PROFITS WITH BETTER SETS & VIDEOS FROM SUPERVISION

<b>FERGUSON</b> <b>£45</b> 26" TX10 TELETEXT	<b>THORN 9600 NON-WORKING</b> <b>£5</b>	★	<b>PHILIPS KT3/30</b> FROM <b>£30</b>	<b>GRUNDIG TVs</b> FROM <b>£35</b>
<b>FERGUSON STEREO TEXT</b> FROM <b>£90</b>	<b>TOSHIBA TVs</b> FROM <b>£35</b>	★	<b>ITT TVs</b> FROM <b>£35</b>	<b>PORTABLE TVs</b> FROM <b>£45</b>
<b>SHARP VHS VIDEOS</b> FROM <b>£65</b>	<b>FERGUSON VHS FULLY REMOTE VIDEOS</b> FROM <b>£75</b>	★	<b>NON-WORKING VIDEOS</b> FROM <b>£25</b>	<b>SANYO 5000 BETA VIDEO</b> ONLY <b>£25</b>

EXCELLENT TESTING FACILITIES

OPEN SIX DAYS A WEEK

EASY ACCESS FROM M1 & M62/M621

ALSO A LARGE SELECTION OF OTHER MAKES OF TV & VIDEO ON OFFER. DIRECT LOADS AVAILABLE AT VERY COMPETITIVE PRICES. YOU COLLECT OR DELIVERED TO YOUR DOOR

All Prices are subject to VAT and based on quantity (Handsets Extra)

**NEWS FLASH**

**ITT DIGIVISION (Full Square Tube)**

STEREO TEXT FROM £155

LOEWE OPTA STEREO TEXT FROM £95

**SUPERVISION**

UNIT 16, TOWER WORKS,  
2 GLOBE ROAD, LEEDS LS11 5QG.  
(off Water Lane, near Hilton Hotel (formerly Dragonara))

**RING OUR HOTLINES NOW!**

**NORTH**

**0532  
444795**

**SOUTH**

**01  
769 1029**





# LOW-COST VIDEO TIME/DATE MESSAGE GENERATOR WITH TIMER & STOPWATCH

The **TDMS1** is an all-new low cost versatile overlay unit for both Colour and Monochrome Video Sources, such as Video Cameras and VCR's etc. Accepting a standard 1V composite video input from a camera, off air or quality videotape, the TDMS1 will overlay a 4 line field including time, date, 8-character message (including European symbols – 128 character options) and 99-hour stopwatch. Using only 2 buttons, the user may move the display over the viewing area, set time/date and program the message. Once set, all information is retained for many months during power-down.

Based on a single chip micro design, the **TDMS1'S** functions are all under software control, and thus are extremely versatile, and many special OEM facilities could be provided by custom programing. **OEM's please note.**

Provision for two onboard relays has been included, the outputs of which may be independently switched to operate within a 24 hour period.

The **TDMS1** is available in either PCB or boxed form. The boxed unit includes mains transformer as well as input/output connectors and two push buttons. The PCB version only requires an AC supply of 15V at 6VA.

One off prices are as follows:

PCB only £121.75 + VAT and Carriage Total £145.76 Order reference **TDMS1**. Quantity prices available.

Boxed £134.25 + VAT and Carriage Total £160.13 Order reference **TDMS1/B**. Quantity prices available.

**Why not consult us for all your CCTV requirements? We think you will like our products, our prices, and our caring service.**

**We wont be beaten by anyone on price or service.** We have the most extensive range of CCTV products available. Send a 40p SAE for prices and data.

**IF IT'S CCTV – WE CAN SUPPLY IT**

Our Motto

## Crofton Creates Terrific Value

**ORDER YOUR REQUIREMENTS TODAY BY PHONING 05448 557 NOW – WE ACCEPT ALL MAJOR CREDIT CARDS**

CROFTON ELECTRONICS, KINGSHILL HOUSE, LYONSHALL, HEREFORDSHIRE HR5 3HZ TELEX 8951182

**WE ARE NOW ABLE TO OFFER THE BEST DEAL AVAILABLE ON THE COMPLETE RANGE OF NEC COMPUTER MONITORS AND PRINTERS.**


**ON SPECIAL OFFER IS THEIR 12" HIGH RESOLUTION (0.31) IBM PC COMPATIBLE MODEL 1203 AT THE INCREDIBLE PRICE £220 + VAT & CARRIAGE TOTAL £258.75 WHY NOT TREAT YOURSELF TO A REALLY SUPERB COLOUR DISPLAY FOR YOUR MICRO? AT THIS UNBEATABLE PRICE YOU WILL HAVE TO MOVE FAST. SO DON'T DELAY, PHONE US NOW GIVING YOUR CREDIT CARD NO., OR POST US A CHEQUE FIRST CLASS. SO AS NOT TO BE DISAPPOINTED, ALL ORDERS PHONED THROUGH BY 2.00 PM WILL BE DESPATCHED THE SAME DAY.**

# SOUTHSIDE TV

**UNIT 8, APPLE IND. EST.,  
WHITTLE AVE.,  
SEGENSWORTH WEST,  
FAREHAM OFF JUNCTION 9, M27  
LOCKSHEATH  
HANTS. TEL. (04895) 77251**

- ★ **TOP QUALITY** ex-rental TV's & Videos
- ★ Fresh stock deliveries **EVERY** week
- ★ All items complete with original handsets
- ★ Working stock always available in quantity
- ★ 24 hr ansaphone service

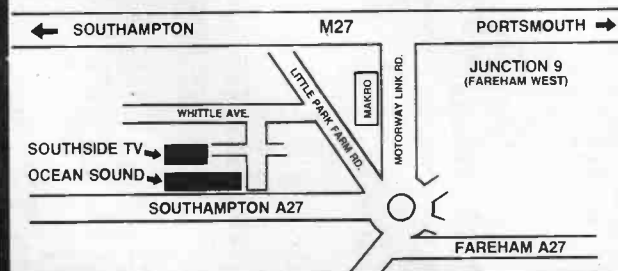Opening times: Mon-Fri 10am-5.30pm.  
Sat Mornings 10am-1pm.



## MAKE YOUR INTERESTS PAY!!

Train at home for one of these Career Opportunities

More than 8 million students throughout the world have found it worth their while! An ICS home-study course can help you get a better job, make more money and have more fun out of life! ICS has over 90 years experience in home-study courses and is the largest correspondence school in the world. You learn at your own pace, when and where you want under the guidance of expert 'personal' tutors. Find out how we can help YOU. Post or phone today for your **FREE INFORMATION PACK** on the course of your choice. (Tick one box only!)

Electronics <input type="checkbox"/>	Radio, Audio & TV Servicing <input type="checkbox"/>
Basic Electronic Engineering (City & Guilds) <input type="checkbox"/>	Radio Amateur Licence Exam (City & Guilds) <input type="checkbox"/>
Electrical Engineering <input type="checkbox"/>	Car Mechanics <input type="checkbox"/>
Elec. Contracting/Installation <input type="checkbox"/>	Computer Programming <input type="checkbox"/>
<b>GCE over 40 'O' &amp; 'A' level subjects</b> <input type="checkbox"/>	

Name: \_\_\_\_\_

Address: \_\_\_\_\_


P. Code \_\_\_\_\_

**ICS**

International Correspondence Schools,  
Dept. EGS19, 312/314 High St., Sutton, Surrey  
SM1 1PR. Tel: 01-643 9568 or 041-221 2926  
(both 24 hours).



# METEX PROFESSIONAL DMM'S

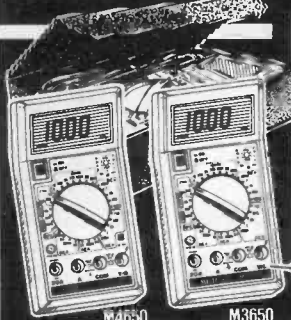

**EDUCATION AND QUANTITY PRICE & IN IN DIRECT**  
 0.1 and 1/10 12mm LCD Digital multi meters; 6 ranges AC and DC volts; AC Resistance (range to 20M ohms); DC to 20 Amps; Hfe Transistor test; Diode Test; Continuity; Auto polarity and zero. Plus extra features as below. Size 176 x 90 x 36 mm (3800 172 x 88 x 36). All with Test Leads: Fused; Hard carry case and instructions.

**ALL MODELS WITH FREE HARD CARRY CASE**

MODEL	DIGITS	RANGES	EXTRA FEATURES	BASIC	PRICE
3800	3½	32	Low AC/DC 0/20 micro amp ranges	0.5%	£35.00
3610	3½	30	LED continuity indicator	0.3%	£39.09
3630	3½	30	5-Range Capacitance Test	0.3%	£45.17
3650	3½	30	2-Range frequency counter 5-Capacitance	0.3%	£52.13
4630	4½	30	Data Hold 5-Range Capacitance	0.05%	£60.83
4650	4½	30	Data Hold, 2-Range Freq. 5-Capacitance	0.05%	£69.52

Add 15% VAT UK only - UK POST/INS etc. FREE (EXPORT EXTRA)

OPEN 6 DAYS A WEEK — CALLERS WELCOME

## AUDIO ELECTRONICS

TELEPHONE 01-724 3564  
 301 EDGWARE ROAD, LONDON W2 1BN  
 ORDER BY POST OR TELEPHONE

**INSTRUMENT CATALOGUE**  
 Ref TG  
 UK Send  
 SAE A4  
 £1.00

# TODD TRADING

## NEW WAREHOUSE OPEN! HIGH QUALITY TELEVISIONS & VCR's

Specialists in 'ready to retail' televisions and VCRs (packed with handbook and patch lead). Mostly Ferguson but all models stocked.  
 NEW 'B' GRADED EQUIPMENT AVAILABLE.

### ITEMS USUALLY IN STOCK

Ferguson Non Text, Text and Stereo Text & New F.S.T. B Grade.  
 Ferguson, JVC, Sharp, Hitachi, Sony, etc., etc. V.C.R.s working:  
 Ferguson 3V29/30 V.C.R.s ready for retail in fives £75 + VAT.  
 Ferguson Compact Disc Units, A Grade and B Grade, from £40 + VAT.  
 Sony C9 Beta in top condition, back to spec, plenty in stock.  
 Ferguson V.C.R.s for spares: 3V16/3V22/3V23/3V24/3V29/3V31/3V35/3V43/3V45/3V55.


### NATIONWIDE DELIVERY

EVEN ON SMALL ITEMS — MIN OF 5 UNITS

### PHONE FOR DETAILS
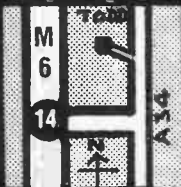
## TODD TRADING

UNIT 16  
 STONE BUSINESS PARK  
 STONE · STAFFS



SITUATED  
 APROX  
 3 MILES  
 FROM  
 JUNC. 14,  
 M6

0785 43447 Fax  
 0785 48202 0785 223137  
 OPEN 6 DAYS A WEEK, CALLERS BY APPOINTMENT PREFERRED

# FIRST IN TUBE REBUILDING TECHNOLOGY 30AX; 540 SERIES!

## REDUCED SERVICING COST, FIT A DIRECT REPLACEMENT

AVAILABLE ONLY FROM CHROMAVAC.  
 PRE CONVERGED AS ORIGINAL.  
 EXTERNAL MULTIPOLE UNIT NOT REQUIRED.

# QUALITY REBUILDS

**SPECIAL OFFERS!**  
 ON  
 INLINE



Get on the hot-line today!

### SAVE £££s

KEEP THAT OLDER SET  
 PURCHASE A NEW 56-410  
 OR 47-342/3 TUBE  
 FOR ONLY £5 + CARRIAGE  
 Also NEW 560 AKB22 £35  
 NEW 670 XB22 £37.50

061  
**681 2959**

most types of  
 Inline Re-builds  
 or new ex-stock  
 PRICES SUBJECT TO  
 GLASS EXCHANGE

### Delta Rebuilds

Up to 19" ..... £28  
 Up to 22" ..... £30  
 Up to 26" ..... £34  
 110° up to 22" ..... £34  
 110° up to 26" ..... £38  
 Low focus ..... +£2  
 A47 342 New ..... £28  
 17FHP New ..... £30  
 470EHB New ..... £30  
 Delta only. Less 5% 5+

### Inline Rebuilds

Up to 22" .. From £40  
 Up to 26" .. From £45  
 A56-540x ..... £56  
 A66-540x ..... £58  
 Bonded Coil ..... +£5

ALL SIZES OF NEW AND  
 REBUILT MONO TUBES  
 AT COMPETITIVE PRICES

### IN LINE TYPES (NOT REBUILDS) PHONE RE STOCK POS.

Please enquire types not listed

370 HFB-A37-590 ..... £50	AXT 56-001 ..... £67
370 HUB ..... £50	670 CZB ..... £80
AXT 37-001 ..... £50	A66-540 ..... £125
420 CSB ..... £50	420FSB ..... £60
420 EDB-A42-590 ..... £50	14" (A34); 16" (A38); 21" (A51); FST now available at special low prices
420 EZB ..... £50	
420 ERB ..... £50	
470 KUB ..... £50	
510 UFB ..... £67	
510 VSB ..... £67	
AXT51-001 ..... £67	
560 DYB-560 DTB ..... £67	
560 EGB ..... £67	
560 CGB ..... £67	
560 DMB ..... £67	

NOTE  
 Surcharge  
 without  
 exch. glass.

★ WE PURCHASE SURPLUS STOCKS  
 OF INLINE TUBES: ALSO A56/  
 66 - 510/540 ETC. OLD GLASS.  
 DELIVERY: By return on all stock items.

MIN. CARRIAGE £5  
 £10 if glass collected.  
 TERMS  
 Cash with order  
 ALL PRICES  
 EXCLUSIVE OF VAT

### THE COMPANY WHO PUT HIGH STANDARDS FIRST



CHROMAVAC LTD., PUMP STREET,  
 HOLLINWOOD, OLDHAM OL9 7LR

Ask for Mr Butterworth ON: 061-681 2959

# AVS

# THE A.V.S. GROUP

## AUDIO VISUAL SERVICES

### NEW YEAR SPECIALS FROM AVS GROUP



**TX10**  
NON TEXT\*    £25  
TEXT 22"    £65  
TEXT 26"    £60  
\* NON TEXT 8311 TYPE



**MANUFACTURERS B GRADE**  
VIDEOS FROM £110  
DUAL SPEED FROM £130  
MICROWAVE OVENS FROM £40  
AUDIO FROM £10



**ALL OTHER THORN EX-RENTAL PRODUCTS AT COMPETITIVE PRICES!**  
TV's FROM £10  
VIDEO'S FROM £35

## ALL THREE OF OUR BRANCHES ARE HAVING A JANUARY SALE!

**SPEND OVER £1000 (IN ONE GO) AND TAKE ADVANTAGE OF A 2½% DISCOUNT —  
SPEND OVER £2000 AND GET A 5% DISCOUNT**

**REMEMBER JANUARY ONLY FOR OUR GREATEST SALE EVER!  
"IF YOU WANT LOADS OF STOCK CONTACT DAVE HOLMES"**

**NEW I.R. HANDSETS UNBEATABLE FROM £10.00**

**SPECIALIST EXPORT DEPT AT RISBOROUGH**

**ALL PRICES SUBJECT TO V.A.T. HANDSETS EXTRA**

**BULK BUYERS WELCOME CONTACT DAVE HOLMES AT RISBOROUGH**

### SWINDON



**LAURIE PHILLIPS**

**0793 513484  
0793 513369**

AVS SWINDON  
UNIT 62 BSS HOUSE,  
CHENEY MANOR INDUSTRIAL  
ESTATE, SWINDON, WILTS.

### HEAD OFFICE PRINCES RISBOROUGH



**IAN NICOLL  
08444 3226  
08444 2995**

**AUDIO VISUAL SERVICES  
36 WYCOMBE ROAD  
PRINCES RISBOROUGH  
BUCKS.**

### HUMBERSIDE



**KEN HOW**

**0652 660242  
0652 660243**

AVS HUMBERSIDE  
UNIT 8 ST. MARY'S WORKS  
MARSH LANE, BARTON-ON-HUMBER  
SOUTH HUMBERSIDE.

## POPULAR BAKERS DOZEN PACKS

(Still available)


All packs are £1 each, if you order 12 then you are entitled to another free. Please state which one you want. Note the figure on the extreme left if the pack ref number and the next figures is the quantity of items in the pack, finally a short description.

- BD02 5 13A spurs provide a fused outlet to a ring main where device such as a clock must not be switched off
- BD07 4 in flex switches with neon on/off lights, saves leaving things switched on
- BD09 2 6v. 1A mains transformers upright mounting with fixed clamps
- BD11 1 6½" speaker cabinet ideal for extensions, takes your speaker. Ref BD137
- BD13 12 30 watt reed switches, it's surprising what you can make with these - burglar alarms, secret switches, relay etc. etc.
- BD22 2 25 watt loud speaker two unit cross-overs
- BD29 1 B.O.A.C. stereo unit is wonderful value
- BD30 2 nicad constant current chargers adapt to charge almost any nicad battery
- BD32 2 humidity switches, as the air becomes damper the membrane stretches and operates a microswitch 2 meter length of connecting wire all colour coded
- BD34 48 13A rocker switch three tag so on/off, or change over with centre off
- BD42 5 24hr time switch, ex-Electricity Board, automatically adjust for lengthening and shortening day. Original cost £40 each.
- BD49 10 neon valves, with series resistors, these make good night lights
- BD56 1 mini uniselector, one use is for an electric jigsaw puzzle, we give circuit diagram for this. One pulse into motor, moves switch through one pole
- BD59 2 flat solenoids - you could make your multi-tester read AC amps with this
- BD67 1 suck or blow operated pressure switch, or it can be operated by any low pressure variations such as water level in water tanks
- BD91 2 mains operated motors with gearbox. Final speed 16rpm. 2 watt rated
- BD103A 1 6 750MA power supply, nicely cased with input and output leads
- BD120 2 strip boards each contains a 400v 2A bridge rectifier and 14 other diodes and rectifiers as well as dozens of condensers etc
- BD122 10m twin screened flex with white pvc cover
- BD128 10 very fine drills for p.c.b. boards etc. Normal cost about 80p each
- BD132 2 plastic boxes approx. 3" cube with square hole through top so ideal for interrupted beam switch motors for model aeroplanes, spin to start so needs no switch
- BD134 10 microphones inserts - magnetic 490 ohm also act as speakers
- BD139 6 reed relay kits you get 16 reed switches and 4 coil sets with notes on making C/O relays and other gadgets
- BD148 4 safety cover for 13A msockets - prevent those inquisitive little fingers getting nasty shocks
- BD180 6 neon indicators in panel mounting holders with lens
- BD193 6 5 amp 3 pin flush mounting sockets makes a low cost disco panel
- BD196 1 in flex simmerstat - keeps your soldering iron etc always at the ready
- BD199 1 mains solenoid very powerful has 1" pull or could push if modified
- BD210 8 keyboard switches - made for computers but have many other applications
- BD210 4 transistor type 2N3055 probably the most useful power transistor
- BD211 1 electric clock mains operated put this in a box and you need never be late
- BD221 5 12v alarms make a noise about as loud as a car horn. Slightly solid but OK
- BD242 2 6" x 4" speakers 4 ohm made from Radiomobile so very good quality
- BD252 1 panostat, controls output of boiling ring from simmer up boil
- BD259 50 leads with push on ¼" tags - a must for hook ups - mains connections etc
- BD263 2 oblong push switches for bell or chimes, these can mains up to 5 amps so could be foot switch if fitted into pattress
- BD268 1 mini 1 watt amp for record player. Will also change speed of record player motor
- BD283 3 mild steel boxes approximately 3" x 3" x 1" deep - standard electrical
- BD293 50 mixed silicon diodes
- BD305 1 tubular dynamic mic with optional table rest
- BD667 2 4.7uf, non-polarised block capacitors, pcb mounting
- BD400 4 Books. Useful for beginners. Describes amplifiers, test equipment and kit sets
- BD653 2 Miniature driver transformers. Ref LT44. 20k to 1k, centre tapped
- BD553a 3 3.5 volt operated relays, each with two pairs C/O contacts

Most other packs still available and you can choose any as your free one.
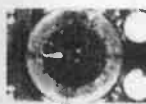
### POWERFUL IONISER

Generates approx. 10 times more IONS than the ETI and similar circuits. Will refresh your home, office, shop workroom etc. Makes you feel better and work harder - a complete mains operated kit, case included £11.50 + £3 P&P.



### 25A ELECTRICAL PROGRAMMER

Learn in your sleep. Have radio playing and kettle boiling as you wake - switch on lights to ward off intruders - have a warm house to come home to. You can do all these and more. By a famous maker with 25 amp ovv of switch. A beautiful unit at £2.50.



### ATARI 65XE COMPUTER

At 64K this is most powerful and suitable for home and business. Brand new, complete with PSU, TV lead, owner's manual and six games. Can be yours for only £45 plus £3 Insured delivery.

**DATA RECORDERS.** ACORN for Acorn Electron, etc., reference number ALF03, with TV lead, manual and PSU. Brand new. Price £10 plus £1.50 post. Order ref 10P44.

ATARI XC12 for all their home computers. With leads and handbook. Brand new. Price £10 plus £2 post. Order ref 10P53.

**JOYSTICK FOR ATARI OR COMMODORE** for all Atari and Commodore 64 and Vic20. New Price £5. Order ref 5P126.

**EXTRA SPECIAL OFFER.** The ATARI Compendium contains computer 65XE, data recorder XC12, joystick and six games for £57.50 plus £4 insured delivery.




### VENNER TIME SWITCH

Mains operated with 20 amp switch, one on and one off per 24 hrs, repeats daily automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only £2.95 without case, metal case - £2.95, adaptor kit to convert this into a normal 24 hr. time switch but with the added advantage of up to 12 on/off per 24hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is £2.30.

Ex-Electricity Board. Guaranteed 12 months.

### SOUND TO LIGHT UNIT

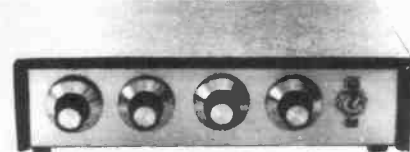

Complete kit of parts of a three channel sound to light unit controlling over 2000 wats of lighting. Use this at home if you wish but it is plenty rugged enough for disco work. The unit is housed in an attractive two tone metal case and has controls for each channel, and a master on/off. The audio input and outputs are by ¼" sockets and three panel mounting hose holders provide thyristor protection. A four pin plug and socket facilitate ease of connecting lamps. Special price is £14.95 in kit form.

**ORGAN MASTER** is a three octave musical keyboard. It is beautifully made, has gold plated contacts and is complete with ribbon cable and edge connector. Brand new, only £12 plus £3 postage. Order ref 12P5.

**MUSIC FROM YOUR SPECTRUM 128.** We offer the Organ Master three octave keyboard, complete with leads and the interface which plugs into your 128. You can then compose, play, record, store, etc., your own music. Price £19 plus £3 special packing and postage. Order ref 19P1.

**CAMERAS.** Three cameras, all by famous makers, Kodak, etc. One disc and two different instant cameras. All in first class condition, believed to be in perfect working order but sold as untested. You can have the three for £10 including VAT, which must be a bargain - if only for the lenses, flash gear, etc.

**ALBA TWIN CASSETTE RECORDER AND PLAYER WITH STEREO RADIO.** This is a mains/battery portable made to sell. We understand, at about £50 but the ones we have are line rejects. They are brand new still in the manufacturers' boxes but have a slight defect associated with the cassette section. The radio and amplifier section, both mono and stereo, is perfectly OK. If you are handy at mending things then this should be for you. Price £20 or two for £38 plus £3 insured post, either package. Order ref 20P7 or 2 x 20P7.

**1/8th HORSEPOWER 12 VOLT MOTOR.** Made by Smiths, the body of this is approximately 3in, the diameter 3in and the spindle 5/16th of an inch diameter. It has a centre flange for fixing or can be fixed from the end by means of 2 nuts. A very powerful little motor which revs at 3,000rpm. We have a large quantity of them so if you have any projects in mind then you could rely on supplies for at least two years. Price £6. Our ref 6P1, discount for quantities of 10 or more.

**PHILIPS LASER**  
This is helium-neon and has a power rating of 1.6mW. Completely safe so long as you do not look directly into the beam when eye damage could result. Brand new, full spec, £30 plus £2 insured delivery. Mains operated power supply for this tube gives 8kv striking and 1.25kv at 5mA running. Complete kit with case £13. No extra for post if ordered with tube.

**HIGH RESOLUTION MONITOR.** 9in black and white, uses Philips tube M24/306V. Made up in a lacquered frame and has open sides. Made for use with OPD computer but suitable for most others. Brand new, £16 plus £5 cost. Our reference 16P1.

**TANGENTIAL HEATERS.** We again have good stocks of this quiet running, instant heat units. They require only a simple case or could be fitted into the bottom of a kitchen unit, etc. 1.2kw, which is a very compact little unit and also a 2.5kw, which is approximately 10in long plus motor. Price for either model £5. Being rather fragile needs special packing so add £2 per heater for post and packing. Control switch for 2.5kw model giving full heat, half heat or cold boil. Price 50p.

**MINI MONO AMP** on p.c.b. size 4" x 2" (app)  
Fitted volume control and a hole for a tone control should you require it. The amplifier has three transistors and we estimate the output to be 3W rms.  
More technical data will be included with the amp. Brand new, perfect condition, offered at the very low price of £1.15 each, or 13 for £12.00.

**FDD BARGAINS**  
3½in made by Chinon of Japan. Single sided, 80 track, Shugart compatible interface. Interchangeable with most other 3½in and 5¼in drives. £28.50 plus £3 post, 3in Hitachi, reference 305SXA. Standard Shugart connection, works with most computers but particularly suitable and recommended for Amstrad 6128, etc. £30 plus £3 post.

Generous discounts for quantities

## J & N BULL ELECTRICAL

Dept. T.V., 250 PORTLAND ROAD, HOVE, BRIGHTON, SUSSEX BN3 5QT.

MAIL ORDER TERMS: Cash, P.O. or cheque with order. Orders under £20 add £1.50 service charge. Monthly account orders accept from schools and public companies. Access & B card orders are accepted - minimum £5. Brighton (0273) 734648 or 203500.

## BARGAINS STILL AVAILABLE

**SUB-MIN TOGGLE SWITCH.** Body size 8mm x 4mm x 7mm SBDT with chrome dolly fixing nuts. 4 for £1.00. Order ref BD649.

**VERY POWERFUL MAGNETS.** Although only less than 1in long and not much thicker than a pencil these are very difficult to pull apart. Could be used to operate embedded reed switches, etc. Price 50p each, 2 for £1.00. Our ref BD642.

**CLEAR LACQUER.** Quick drying for the protection of transfers, markings, maps, etc. Also protects wood and metal. Exceptionally clear. Large can for £1.00. Order ref BD660.

**PAPST AXIAL FAN. MANUFACTURERS REF NO TYP4580N.** This is mains operated 15watt rating and in a metal frame with metal blades so OK in high temperatures. Body size approximately 4¼in square x 1½in thick. £6.00 each, plus £1.00 postage. Our ref 6P6.

**TRANSMITTER SURVEILLANCE (BUG) -** tiny, easily hidden, but which will enable conversation to be picked up with FM radio. Can be housed in a matchbox. All electronic parts and circuit. Price £2. Ref 2P52.

**ASTEC PSU.** Mains operated switch mode so very compact (6½" x 4" x 2" approx.). Outputs: +5 Volts 3.5 amp. +12 Volts 1.5 amp. -5 Volt 1.5 amp. Brand new. Normal price £30+. Our price only £10. Ref. 10P34.

**APPLIANCE THERMOSTAT** - spindle adjust type suitable for convector heaters or similar. Price 2 for £1. Ref. BD582.

**3 CORE FLEX BARGAIN No. 1** - Core size 5mm so ideal for long extension leads carrying up to 5 amps or short leads up to 10 amps. 15mm for £2. Order Ref. 2P189.

**3 CORE FLEX BARGAIN No. 2** - Core size 1.25mm so suitable for long extension leads carrying up to 13 amps - or short leads up to 25A. 10m for £2. Order Ref. 2P190.

**CASE WITH 13A PRONGS** - to go into 13A socket, nice size and suitable for plenty of projects such as car battery trickle charger, speed controller, time switch, night light, noise suppressor, dimmers etc. Price - 2 for £1. Ref. BD565.

**ALPHA-NUMERIC KEYBOARD** - this keyboard has 73 keys with contactless capacitance switches giving long trouble free life and no contact bounce. The keys are arranged in two groups, the main area field is a QWERTY array and on the right is a 15 key number pad, board size is approx. 13" x 4" - brand new but offered at only a fraction of its cost namely £3, plus £1 post. Ref. 3P27.

**TELEPHONE EXTENSIONS** - it is now legal for you to undertake the wiring of telephone extensions. For this we can supply 4 core telephone cable, 100m coil £8.50. Extension BT sockets £2.95. Packet of 50 plastic headed staples £2. Dual adaptor for taking two appliances from one socket £3.95. Leads with BT plug for changing old phones 3 for £2.

**WIRE BARGAIN** - 500 metres 0.7mm solid copper tinned and p.v.c. covered. Only £3 + £1 post. Ref. 3P31 - that's well under 1p per metre, and this wire is ideal for push on connections.

**INTERRUPTED BEAM KIT** - this kit enables you to make a switch that will trigger when a steady beam of infra-red or ordinary light is broken. Main components - relay photo transistor, resistors and caps etc. Circuit diagram but no case. Price £2. Ref 2P15.

**CAPACITOR BARGAIN** - axial ended - 4700uf @ 25v Jap made. Normally 50p each, but you will get 4 for £1. Ref. 613.

**SPRING LOADED TEST PRODS** - heavy duty, made by the famous Bulgin company. Very good quality. Price four for £1. Ref. BD597.

**SOLAR POWERED NI-CAD CHARGER** 4 NI-CAD batteries AA (HP7) charged in eight hours or two in only 4 hours. It is complete, boxed ready to use unit. Price £6. Our Ref. 6P3.

**50v 20A TRANSFORMER 'C'** Core construction so quite easy to adapt for other outputs - tapped mains input, only £25, but very heavy so please add £5, if not collecting. Order Ref. 25P4.

**FREE POWER!** Can be yours if you use our solar cells - sturdily made modules with new system bubble magnifiers to concentrate the light and so eliminate the need for actual sunshine - they work just as well in bright light. Voltage input is .45 - you join in series to get desired voltage - and in parallel for more amps. Module A gives 100mA. Price £1. Our Ref. BD631. Module C gives 400mA. Price £2. Our ref 2P199. Module D gives 700mA. Price £3. Our Ref. 3P42.

**SWITCH AC LOADS WITH YOUR COMPUTER.** This is easy and reliable if you use our solid state relay. This has no moving parts, has high input resistance and acts as a noise barrier and provides 4kW isolation between logic terminals. The turn-on voltage is not critical, anything between 3 and 30V, internal resistance is about 1K ohm. AC loads up to 10A can be switched. Price is £2 each. Ref. 2P183.

**METAL PROJECT BOX.** Ideal size for battery charger, power supply etc. at 3,000rpm. Size 8" x 4¼" x 4" high, ends are lowered for ventilation other sides are flat and undrilled. Order Ref. 2P191. Price £2.

**BIG SMOOTHING CAPACITOR.** Sprague powertyc 39,000uF at 50V. £3. Our Ref. 3P41.

**4-CORE FLEX CABLE.** Cores separately insulated and grey PVC covered overall. Each copper core sized 7/0.2mm. Ideal for long telephone runs or similar applications even at mains voltage. 20 metres £2. Our Ref. 2P196 or 100 metres coil £8. Order Ref. 8P19.

**TWIN GANG TUNING CAPACITOR.** Each section is .0005uF with trimmers and good length ¼in spindle. Unused but old and may be slightly soiled. Sleeved prong type. £1 each. Our Ref. BD630.

**13A PLUGS.** Good British make complete with fuse, parcel of 5 for £2. Order Ref. 2P186.

**13A ADAPTERS** - Takes 2 13A plugs, packet of 3 for £2. Order Ref. 2P187.

**20v - 0 - 20v** - Mains transformers 2½ amp (100 watt) loading, tapped primary. 200-245 upright mountings £4. Order Ref. 4P24.

**POWERFUL 12V MOTOR** was intended for Sinclair Electric Car, rating approx. ½ HP. Price £15 plus £2 post.

**RE-CHARGEABLE NICADS 'D' SIZE** these are tagged for easy joining together but tags can easily be removed, virtually unused, tested and gntd. £2.00 each. Ref. 2P141, 6 for £10. Ref. 10P47.

**FLIP-OVER DIGITAL CLOCK** - Quite an eye-catcher, this is mains operated. The figures flip-over per minute and per hour and give a larger than usual visual display. Supplied complete with front and perspex panels to glue together to make its case. £2.00 each. Our Ref. 2P205.

**QUICK FIX MAINS CONNECTOR** - A must for your workshop. Saves putting on plugs as you just push the wires under the spring clips. Automatically off when lid is up. Price £7.50. Our reference 7P51.

**BT HANDETF** with curly lead terminating at BT plug. Colour cream. Price £5.00. Our reference 5P123.


**SINGLE SCREENED FLEX 7.02** copper conductors, pvc insulated then with copper screen, finally outer insulation. In fact quite normal screened flex. 10m for £1. Our ref BD668. Ditto, but solid conductor. 10m for £1. Our ref BD668A.

**WHITE CEILING SWITCH** 5 amp 2 way surface mounting with cord and tassel. Made by the famous Crabtree Company. Price £1 each. Our ref BD528.

**13A SWITCH SOCKETS** - Top quality made by Crabtree, fitted in metal box with cutouts so ideal for garage, workshop, cellar, etc. Price £2 each. Our ref 2P37.

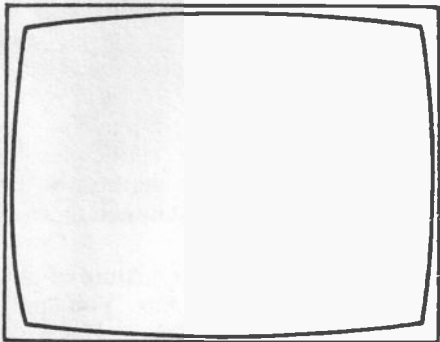**EHT TRANSFORMERS** - Normal primary, secondary 3.5v at 3mA continuous or 20mA intermittent. Ideal as a spark generator for boiler lighting, etc., or with a simple voltage doubler circuit would make a good ioniser. Price £7. Our ref 7P7. 8kv secondary 3mA. Price £10. Our ref 10P56.





# TELEVISION

## The Great Gamble

So now we know the government's intentions about the future of broadcasting in the UK, outlined in last month's white paper. They are much as had been predicted, but the more one thinks about the implications the more the whole thing takes on the appearance of being a colossal gamble. Not just by the government with the present arrangements and future possibilities, but also for those companies prepared to take part in the proposed new regime of unregulated broadcasting.

The changes could turn out to be profound in comparison to anything that's gone before. In the past the UK's TV services have evolved in a very orderly manner, with the additional networks as they have come on the scene complementing the services already in existence. The smoothest operation of all was Channel 4. Viewers required no new aerial, tuner or what have you: just push an extra button on the appointed day and there it was. Previous changes had not been quite so smooth. The advent of ITV in the mid-fifties called for a new aerial and maybe an adaptor, though suitable sets had been available for some time in preparation for the day. The ITV companies went through a worrying period initially as advertisers held off before the audience grew to appreciable figures, but the days of the "licence to print money" were not long in coming. The advent of BBC-2 coincided with the plan to move all transmissions to u.h.f. and add colour. Careful planning was the order of the day as the services expanded.

What we have in prospect this time is something quite different. Channel 5 will call for nothing more than a second aerial, but the satellite services will call for a new type of receiving set-up and the latest idea, terrestrial microwave TV, will require a further dish and tuner. The government would like to see all these services in operation by the mid-nineties at the latest - along with Astra's channels of course.

The past expansion of TV in the UK also took careful account of what was likely to be feasible economically - the BBC with its licence revenue, advertising to support ITV, and a carefully worked out method of arranging for Channel 4 to receive adequate revenue. While there is no doubt an unsatisfied demand for advertising slots, and the ITV companies have done quite nicely thank you out of their regional monopolies, it's unlikely that there is enough unsatisfied advertising demand to support all the extra services envisaged. So the public is going to be asked to contribute through subscription payments, while the extra competition will result in reduced rates to capture advertising revenue. No careful planning this time. Push 'em in the water and see who sinks or swims, one problem being that some of the present, acclaimed services could suffer in the process. The past history of UK TV broadcasting can provide no clues as to the eventual outcome if full use is made of the opportunities that will become available in the next two-four years: in addition to BBC-1/2/ITV/Ch. 4 up to 16 Astra channels, five DBS channels, Ch. 5, a suggested sixth and seventh u.h.f. service where it can be squeezed in, twelve or more terrestrial s.h.f. channels plus the cable services.

Freedom of the air is a fine concept; freedom of choice even more so. But it's possible to have excessive choice - you would find it hard to make sensible use of the options when some forty channels are on offer, quite apart from the fact that a plethora of channels does not of itself guarantee a wide choice of programme material.

The new generation of programme providers is not going to have an easy time. Viewers are renowned for their conservative habits. They will have to be persuaded not only to change channels but to contribute to the cost of many of them and to invest in extra receiving equipment. The new programme providers are going to have to show that they have something special on offer, hence all the current bidding for film rights, a hugely expensive business that starts long before any revenue begins to come in. Failures in the broadcasting field have in the past been unknown in the UK, though not elsewhere. Suddenly we have the problems of SuperChannel and its huge losses and Sky's more modest loss-making. Past experience in the USA has been of stations opening and closing while the main networks kept their hold on the majority of viewers.

At the end of the day the question will arise as to whether deregulation will have been worthwhile. At this point one simply cannot begin to try to make an informed guess. The main problem would seem to be that broadcasting revenue will be spread over too many operators and that some current, valued services may not be able to survive in a more stringent commercial atmosphere. The disturbing thing is that the changes are being introduced for ideological reasons rather than strict broadcasting ones. It could be that the only winners will be the Far Eastern manufacturers of hardware.

## APOLOGY - COMMODORE SPARES CATALOGUE

Unfortunately the HRS Commodore Computer Spares Catalogue was not available in time for inclusion in last month's issue. It is being distributed with the present issue instead. Our apologies to those inconvenienced by this omission.

## PRICE INCREASE

The price of *Television* is being increased to £1.50 from next month's issue dated February. We regret the need to make this increase, which is due to the effects of inflation on the cost of producing and distributing the magazine.

## EDITOR

John A. Reddihough

Please note that the telephone numbers below are for contact with the advertisement departments only. Editorial enquiries should be sent to the editor at the address given on page 161.

## ADVERTISEMENT MANAGER

David W.B. Tilleard  
01-261 6671

## SECRETARY

Janet Reeve  
01-261 6671

## CLASSIFIED ADVERTISEMENTS

Pat Bunce  
01-261 5942

## ADVERTISEMENT COPY AND MAKE-UP

Ron Scorey  
01-261 6035

## SUBSCRIPTION ENQUIRIES

0444 440 421

## CORRECTION

On page 838 of the September issue under the heading Some Quickies Ferguson 3878 should have read Ferguson 3787.

## COVER PHOTO

This month's cover photograph shows the Ferguson TX10 chassis - see article on pages 192-5. Note the later, replacement type focus unit on the right.

# Letters

## DEALING WITH SURFACE-MOUNTED CHIPS

With reference to Nick Beer's article on dealing with surface-mounted devices, I find that to lift each leg in turn rather than cutting the legs off with a knife is the best way. If you cut through the legs you not only destroy the chip but also stand a good chance of breaking the connection pads away from the very fine circuit tracks and causing other board damage. When a knife is run along the line of pins on the side of a chip several times it's all too easy to slip off the end and cut into the board or, as the last cut is made, the legs may twist in the direction of cutting and lift the print. Another problem is that if too deep a cut is made when the legs are cut the tracks that run from the legs and underneath the chip can be severed, something you might find out only after fitting a new chip and discovering that it doesn't work. The equipment I use consists of an anti-static work area, an earthed variable-temperature soldering iron, and a set of three soldering aid tools from RS with the spike tool filed down to a point. Also low melting-point solder, desoldering braid and good lighting.

To disconnect an i.c., first remove as much of the solder from the pins as possible, using desoldering braid with the iron temperature at maximum. Turn the iron temperature down, then insert the spike end between the upright edge of the chip and the vertical section of the first leg – see Fig. 1. Apply slight pressure to the leg, using the chip to lever against, then apply the iron to the outer end of the leg. The solder will melt and the leg will lift upwards away from the board. Move the iron to the outer underside of the inclined leg, heating and bending the leg up farther. This will melt any solder that's still holding the inner end to the pad in a way that avoids peeling the pad from the board. With the leg raised high enough the spike can be moved to the next leg and so on. After removing the chip, clean off any remaining lumps of solder with the iron and braid. I've had no board damage problems since adopting this method rather than cutting chips out. With a bit of practice an 84-pin chip can be removed in a few minutes.

When fitting a new chip I use 22-gauge low melting-point solder to avoid overheating problems. First align the chip, checking that all pins line up with the board print (also check that you have it the right way round!). Start by soldering two legs at opposite ends of the chip to stop it moving. Put the iron's tip vertically on to the outer section of the leg, then dab the solder on to the outer edge – it should flow evenly round the leg.

Soldering each pin individually is o.k. with chips that have wider spaced pins (24 pins etc.) but with larger types (e.g. 84 pins) this is very difficult. It's easier to solder

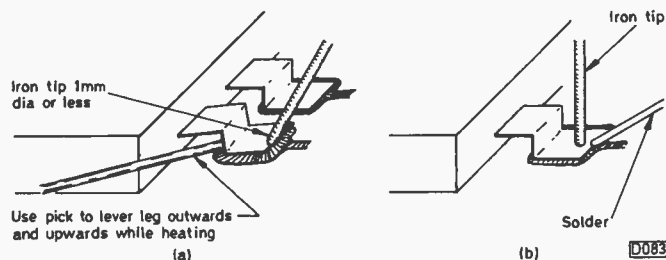


Fig. 1: (a) Unsoldering a surface-mounted chip. Leave each leg bent upwards to enable the pick to reach the next one. (b) Soldering a surface-mounted chip.

opposite corner pins as before – to hold the chip – then to solder all the pins of each side by starting at one end and moving both the iron and the solder along the line of pins. What usually happens is that two or three blobs of solder form, each across several pins, rather than a line connecting them all. This doesn't matter as long as all the pins are soldered. It's then just a matter of removing most of the solder with braid, leaving only the solder between the pins and the board.

I've tried using solder cream, which is a mixture of tiny blobs of solder held in suspension within flux. You apply this to the board before placing the chip on it. But what has tended to happen is that any excess solder flows behind the legs. This can cause shorts between them.

To reuse a chip it's just a matter of bending down all the pins so that they are level and making sure that none are twisted out of line.

This method of removal causes least damage to the board and saves the chip, which might not be faulty after all. I recently replaced an 84-pin surface-mounted chip in a CD player only to find that the fault was still present. It was caused by another component, but the replacement chip was also faulty, causing a different set of symptoms. The player worked perfectly when the original chip had been refitted.

I'd be interested to know if any readers use hot-air irons and whether these have any real advantages over the conventional type for this and other work.

Ian Bowden,  
Barnstaple, N. Devon.

## ESTIMATES AND VAT

In his otherwise excellent article on setting up a workshop David Botto has I think slipped up on one point regarding estimates. His idea of fixing an agreed sum below which a repair will be carried out is fine, but to slap VAT on top can be upsetting to the customer. It's just as easy to set the charge at an arbitrary whole number, e.g. £20, and work out the VAT backwards. This is done by dividing by 1.15 (where the VAT rate is 15 per cent) to get the base price, in this case £17.39 plus £2.61 VAT. Few if any customers having entertainment equipment repaired are likely to be VAT registered. I'm sure that if the engineer gives the customer the feeling that he cares about the cost, however high, the customer is more likely to respond favourably.

John de Rivaz, B.Sc. (Eng.), A.M.I.E.E.,  
Porthowan, Cornwall.

## SIGNALS FOR 405-LINE RECEIVERS

A few further points have occurred to me since writing my articles on keeping vintage TV equipment going.

First, to eliminate moiré patterning with optical standards conversion, simply reduce the height on the monitor until the scan lines just merge. Reduce the camera height by the same amount. Warning: this will put a new scan burn on the camera tube after a period of use, ruining it for normal critical applications.

Secondly, the photos of 405-line pictures in the November issue did not do justice to the original display, which was really excellent, with full resolution and good grey scale. The interpolation effects were reasonably clear however. The picture source was a Marconi BD617 monoscope at the Vintage Wireless Museum.

Thirdly, the Rediffusion tuners mentioned in the article are now also available from Stan Willetts of West



Bromwich (see advertisement on page 20 of the November issue). At the price asked it would be economical to buy two of them just to obtain the Rediffusion h.f. modulators, which are the basis of an excellent Channel 1 modulator. A follow-up article describing the modifications required to the Rediffusion units will appear in the February or March issue of *Television*.

It's possible that I will be able to design a digital 625-405 converter over the next year or so. The likely cost of parts, including a PCB, would be in the region of £200 to £300. An interpolator, if this is designed, would add a further £50 to £100, but would be an optional extra. I would like to assess the potential demand, so would anyone interested please write to me care of the magazine? A guaranteed batch size, especially if it exceeded 50, would help to keep the cost down as it would allow bulk purchase of components and PCBs.

Jeffrey D. Borin, B.Sc. (Eng.), A.M.I.E.E.  
Harlow, Middlesex.

### IMPROVED FIELD FLYBACK BLANKING

I read with interest the article (November issue) by John de Rivaz, B.Sc. (Eng.) on a blanking pulse generator circuit for use in the Rank A823 chassis, having myself had this problem of teletext interference. Others may be interested in the somewhat different approach I adopted to obtaining improved field blanking. I run four of these receivers and derive a great deal of enjoyment from maintaining them and carrying out the occasional modification, such as adding emitter-followers in the RGB output stages to improve the definition. Realignment has been carried out since in some sets, particularly those with varicap tuners, the ex-factory alignment wasn't very good, giving rather poor picture performance. But that's another story.

The field blanking modification I carried out is shown in Fig. 2 and involves alterations on only the c.r.t. base panel. The idea is to increase the amplitude of the field flyback blanking pulse from  $-40V$  to  $-140V$ . To achieve this 4R3 ( $220k\Omega$ ) is replaced with two  $110k\Omega$  resistors as shown and 4VT2 is changed to a high-voltage type such as a BF337. The collector of 4VT2 is disconnected from its previous point (the junction of 4D1/4VT1 emitter): instead the lead is bent round and connected via the

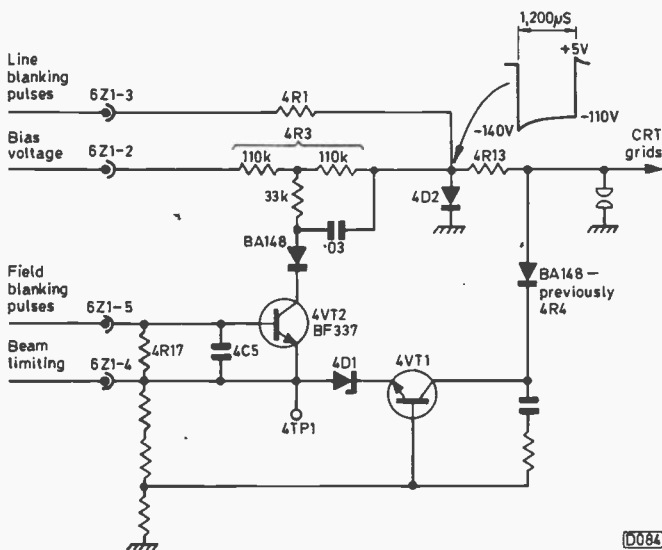


Fig. 2: Modification to the Rank A823 series chassis to obtain improved field flyback blanking. The amplitude of the blanking pulse is increased to  $-140V$ .

components shown to the c.r.t.'s grid circuit. After doing this 4R4 must be replaced with a diode. Everything else is left as before – the additional components can be fitted on the component side of the panel.

This modification has been working perfectly in all four sets for some time now, with no sign of the accursed lines. It has the advantage that no connection is made to the signal path and, like the circuit in the article, it doesn't affect the field flyback resonance conditions.

Incidentally, I would be happy to correspond with other like-minded enthusiasts of these old sets.

Colin Doman, 6 Churnet Close,  
Bedford, Beds MK41 7ST.

### FERGUSON 3V42/3/4 AND EQUIVALENTS

The problem of the take-up/supply poles not reaching the fully laced position in JVC HRD140/Ferguson 3V44 VCRs, mentioned in the December Service Bureau, is a common one on these machines – also the 3V42, 3V43 and the JVC, ITT and Toshiba equivalents. It's caused by the original grease applied to the plastic runners for the take-up/supply poles having become hardened and sticky. For a complete cure all grease should be removed from the plastic runners and fresh grease applied. To do this the video drum assembly has to be removed. This is easily done as it's held in by only three screws. Clean all grease from the locating notches for the poles, then apply fresh grease. Fresh grease should also be applied to the worm gear beside the control motor (part of the mode control assembly).

On the underside of the deck both gears should be removed and their centres cleaned – grease was applied to the shafts on which they are mounted. With these gears removed, the groove in the underside of the mode control assembly can be cleaned and regreased.

The manual contains all the relevant information for setting up the mode control timing. This should be strictly followed when reassembling the mechanism.

Alcohol can be used to remove the old grease. The replacement grease should be a molybdenum-based type.

Alfred Damp,  
Ryde, Isle of Wight.

### TELETEXT INTERFERENCE PROBLEMS

I've had the same trouble (teletext interference) described by John de Rivaz, B.Sc. (Eng.) in sets fitted with the Rank T20/T22 series chassis and the Philips G8 chassis. With the T20/T22 the problem can sometimes be overcome by adjusting the field output stage bias control, though to obtain a good picture it's often necessary to adjust the field linearity as well. With the G8 the problem has often been associated with other faults, i.e. one of the line output transistors has gone leaky and, to obtain a decent picture, the line output transformer may also need to be replaced.

Rothley Stevens,  
Coventry.

### USE MANUFACTURERS' SPARES

I feel I must comment on Dave Mackrill's letter (December) regarding the use of a BU208D as the chopper in the Amstrad Models CTV2200/2210. I would seriously question the use of this device, especially as it contains an efficiency diode connected between its collector and

emitter. My policy is to fit genuine manufacturer's approved parts wherever possible, bearing in mind that repairs must conform to BEAB requirements and that in the event of a fire etc. the engineer could be held responsible if incorrect parts had been fitted.

Whilst on this subject I would also recommend using genuine manufacturers' parts when servicing VCRs. I have a large stock of useless belts, idlers, etc. that are pattern parts which will not work, or in some cases belts that bear no physical relationship to the genuine items. In most cases there's very little difference between the price of pattern parts and genuine parts.

So take the trouble to track down genuine parts and stick to manufacturers' recommendations and instructions. This may put a few pounds on the final bill, but the repair will be that much more reliable and your business reputation can only improve.

*S. J. Cain, Valley Electronics,  
Holyhead, Gwynedd.*

### THE HITACHI VT17

In the October VCR Clinic Mick Dutton mentioned no clock display with the Hitachi VT17, due to absence of the 10V supply on the timer panel. Readers should note that there's an official Hitachi modification for this problem, as follows. Replace Q1795 with either a 2SD468 or a 2SD882 transistor, replace wire link K1788 with a 1S2076 diode (types 1S2473 of 1SS133 can also be used), and add an 0.022 $\mu$ F capacitor between pins 4 and 5 of RC1795 (10V generator).

*Jeff Crocker,  
Bargoed, Mid-Glamorgan.*

### MORE ON THE AMSTRAD CTV2200/2210

I would like to thank Dave Mackrill for his article on the Amstrad CTV2200/2210 (November issue). It was a great help in repairing one of these sets that no one else wanted to know about. The original problem was low, distorted sound. I didn't have a manual but found that R313 (100 $\Omega$ ) was open-circuit. The sound was o.k. after putting this right.

A week later the set came back dead. I couldn't believe it! The fuse, the chopper transistor, the 27 $\Omega$  resistor (R814, 20W) in the feed to the line output stage and the line output transistor had all failed. The capacitor that Dave mentioned had not so far given him trouble, C845 (4.7 $\mu$ F, 250V), was short-circuit. So beware of this one! It might in some cases cause tripping.

*J. E. Jones,  
Lampeter, Dyfed.*

### PANASONIC U2 CHASSIS AND D1 DECK

I think John Coombes (TV Fault Finding, December) must have had the Panasonic TC2205 rather than the TC2207 in mind – the TC2207 doesn't have remote control. D552 is however a trouble-maker in these sets (U2 chassis), usually going short-circuit rather than open-circuit. The associated diode D553 (BY299) then very often suffers. The EW modulator driver transistor Q753 (BD237) can fail, usually when the diodes have done so, resulting in EW pincushion distortion. D552 should always be replaced with a Panasonic type – I've seen BYX71-600 or BY223 diodes fitted in this position but, as in other Japanese sets, their long-term reliability is poor.

In the same issue Eugene Trundle mentions (VCR Clinic) trouble with the mode switches in the Panasonic D1 deck. A point worth making here is that it's worthwhile changing the securing bolt at the same time to prevent callbacks. Also VS0110 is not the only switch in use: the G7/10/12 use the VSS0135 while the NV830 uses another type again.

An extremely common fault with these decks is a knocking noise during reel movement. In some cases this can be caused by a dent in the VXP0521 idler (as in BSR turntable wheels!) but more commonly the cause is the VXP0600 reel clutch. We find that about 75 per cent of the machines that come in have this problem in varying degrees.

*Nick Beer,  
Bideford, N. Devon.*

### KEEPING 405-LINE TV ALIVE

Jeffrey Borin's articles (November and December) were much appreciated by the growing number of enthusiasts who are doing their best to keep 405-line TV alive.

The Rediffusion units mentioned make an ideal modulator. I've now built two of them: both worked first time, with absolutely no tuning or fiddling.

Most people seem to use VHS tapes for storing programme material. There's an urgent need to co-ordinate library material – I'd be pleased to hear from anyone who wishes to exchange some. Meanwhile I can supply tapes of test cards C and D as well as various tuning signals and apology messages.

It's important that 405-line enthusiasts should keep in touch with one another. The ideal means is through the British Amateur Television Club, mentioned by Jeffrey, which has been promoting home-generated 405-line TV since 1949 – yes, forty years!

*Andy Emmerson, G8PTH, 71 Falcutt Way,  
Northampton NN2 8PH.*

### SONY SLC5/6/7 – CAPSTAN LOCK PROBLEM

I noticed the mention of loss of capstan servo lock (VCR Clinic, December) as being a common problem with Sony SLC5/6/7 VCRs. By coincidence I happened to be working on an SLC6 at the time, the symptoms being that the capstan was running slow with the speed control unable to provide sufficient correction. After much checking and head scratching, including replacement of the capstan servo chip IC1, I discovered that the defect was due to C8, an 0.22 $\mu$ F electrolytic capacitor whose value had increased to 0.31 $\mu$ F. As C7 is the same type I checked this as well and found that it measured 0.32 $\mu$ F. After replacing these capacitors and resetting the capstan free-running speed, which was then too fast, the machine operated correctly. So maybe this could be the component ageing fault suggested.

*S. Herman,  
Stanmore, Middlesex.*

### FOR DISPOSAL

I have available free to individuals a quantity of T41 valves, brand new and boxed. They were used as timebase generators (thyatron) in many early TV sets. I also have quite a few 90CV valves, again free to individuals. In turn I'm looking to buy Labgear or Teldis upconverters.

*Douglas Biggar, 27 Auld Lea Road,  
Beith, Ayrshire KA15 2DA. (Telephone 050 55 2118).*

# BI-TECH

**NOW AT**

## LONDON & GLASGOW EX-RENTAL VIDEO & TV WHOLESALERS

**BI-TECH  
THE VERY BEST  
STOCK**


### LONDON DEPOT

CONTACT NEIL PATEL  
SALES DIRECTOR

TEL: 01-556 4199

Unit 3, Leyton Business Centre,  
Etloe Rd, Off Church Rd, Leyton, E10

**OPEN SUNDAY 10 - 1**

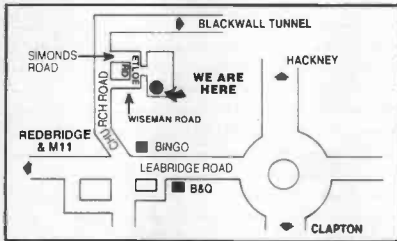

**BI-TECH  
THE VERY BEST  
PRICES**

### IT'S A FACT

YOU DO A  
GOOD DEAL  
BETTER  
AT

**BI-TECH**

BI-TECH HAS SUCCESSFULLY  
NEGOTIATED A NUMBER  
OF CONTRACTS AND NOW  
HAS A VASTLY INCREASED  
RANGE OF STOCK.

**BI-TECH  
THE VERY BEST  
SERVICE**

### GLASGOW DEPOT

CONTACT JACK SWAN  
SALES DIRECTOR

(Ex Super Tel Depot Manager)

TEL: 041-883 2610

Unit 9, Colquhoun Ave,  
Hillington Industrial Estate, Glasgow



## THE VERY BEST PEOPLE TO DEAL WITH

### VIDEO HEADS AT UNBEATABLE PRICES

#### FERGUSON/JVC/AKAI UNIVERSAL 3HSSV £16.00

FERGUSON 3V32 JVC HR7655	£40.99
FERGUSON 3V42/44/45/46/47/50	£22.50
FERGUSON 3V48 JVC HRD565	£40.99

#### SONY REPLACEMENT HEADS

SONY UNIVERSAL 1 PIN C5/C6/C7 AND 2 PIN/SL8080 ETC	£16.50
SONY SLF-1/C20/C30/F30/C40/SLT20ME/SLT30ME	£24.50
SONY SLC-8/C9/60/80/SLT50/SLF60/SL200	£36.00

#### PANASONIC UNIVERSAL 3HSSN £16.00

PANASONIC NV370/NV380/NV100-PHILIPS VR6460	£24.00
PANASONIC NV777/NV330 3 HEAD	£31.00
PANASONIC NV230/NV250/NV260/NV270/NV-G9/10/11	£34.50
PANASONIC NV430/NV460	£27.00
PANASONIC NV366 4 HEAD	£40.00
PANASONIC NV730 4 HEAD	£42.00
PANASONIC NV180 PORTABLE 4 HEAD	£44.00
HITACHI VT6500, VT7000, VT8000, VT8500, VT8700	£21.00
HITACHI VT11, VT14, VT33, VT34, VT330, VT340	£21.00
HITACHI VT4000, VT5000	£21.00
TOSHIBA V9600	£25.00
SHARP VC9300, VC9500, VC9600, VC9700, VC9800 ETC	£20.00
AMSTRAD VCR4500, 4600, 5200, 9000	£21.00
AMSTRAD VCR7000	£22.00
SAISHO VR605, 705, 805, 905, 100	£22.00
FISHER UNIVERSAL FVHD720, 520, 530 ETC	£22.00

#### VIDEO MOTORS

CAPSTAN MOTOR JVC/FERG PU55371V	£19.50
CAPSTAN MOTOR JVC/FERG 3V22 PU45979	£19.50
CAPSTAN MOTOR SONY C6 A-675-113-1A	£5.75
DRUM MOTOR JVC/FERG PU46414P	£19.75
REEL MOTOR JVC/FERG 3V29/30 PU51381V	£22.50
REEL MOTOR SHARP RMTV-1008-GEZZ	£15.00
REEL MOTOR SANYO VTC5000/5150	£7.50

ALL ABOVE HEADS ARE BRAND NEW AND OF JAPANESE ORIGIN  
WE ALSO STOCK BELT KITS, P/WHEELS, MOTORS, IDLERS, PULLEYS, LAMPS, ETC.  
RING NOW FOR OUR STOCK LIST. F.O.C.

ALL EX-STOCK ITEMS DESPATCHED SAME DAY. NO MINIMUM ORDER VALUE.

ADD £1.00 P&P PLUS V.A.T. TO ALL PRICES.

ORDERS BY ACCESS AND VISA ACCEPTED.



**ASK FOR OUR SPECIAL  
QTY VIDEO HEADS PRICE-LIST**



EXPORT & OVERSEAS ENQUIRIES WELCOME.

### OMEGA ELECTRONICS

252A HIGH STREET  
HARLESDEN, LONDON NW10 4TD  
Tel: 01-965 5748



QUALITY...

# SECURITY SUPPLIES

FOR  
DIY &  
TRADE

...AT LOWEST PRICES

#### CONTROL UNITS

- Automatic
- Modular
- Lighting
- Timer

#### SENSORS

- Passive Infra-Red
- Ultrasonic
- Infra-Red Beam

#### ACCESSORIES

- Contacts
- Pressure Pads

#### CARS & VANS

- Security Lighting
- Cable Etc. Etc.

#### HOMES & FACTORIES


## PRODUCT OF THE MONTH

### MINIATURE PASSIVE INFRA-RED SENSOR RP33

Detects intruders up to 12 metres away.

- Size only 80x60x40mm.
- Switchable detection indicator.
- Wide 85° coverage.

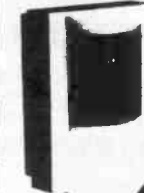■ Suitable for use with most security systems. ONLY £23.95 +VAT  
Quantity discounts start at 3 units.



TELEPHONE  
OR SEND FOR  
FREE  
LITERATURE  
TODAY

*The Security Specialist*

### RISCOMP LIMITED

Dept. TV1, 51 Poppy Road,  
Princes Risborough, Bucks.  
HP17 9DB

Callers by Appointment  
Office hours Mon - Fri  
9am - 5pm



(084 44) 6326



# SPECIAL OFFER THIS MONTH

UNIVERSAL TRIPLER, NEW TYPE.....	£4.00	4-6 Volts Relays	25p
VIDEO LEADS.....	80p	G11 6 touch unit with cable form & sockets	£13.00
AMSTRAD Line O.P. Transistors with Diode.....	£1.00	Send for list of video spare heads	£15.00 to £40.00
BU208A.....	75p or 20 for £10	<b>THORN PANELS</b>	
VIDEO LAMPS, Long Lead.....	24p	Thorn Panel with SAA5012 IC	£2.00
HITACHI & GEC FRAME, Thick Film.....	£6.00	515/753 509/12 515/357 564/03 508/161 515/353 515/173 515/357	£3.50
FIDELITY SPLIT DIODE..... FCC2215AE.....£20 FCC2015BE.....£10 FCC2215BE.....£10		TX9 - TX10 - TX100	
K30 FRONT PANEL TEL-TEX TYPE.....	£5.00	TEXT DECODER TX10 £8.00	
NEW G11 LINE OF PANEL.....	£9.00	NEW TYPE VHS 180	£2.50
NEW G11 FRAME PANEL WITH TDA 2600.....	£7.00	Philips Stereo headphones SBC3160's	£12.00
PHILIPS YEARS AHEAD			
THE CREDIT CARD CALCULATOR Solar Powered.....	£3.75	Philips Travelling alarm clock calculator	£7.50
NEW PHILIPS SBC 1833 Solar & Battery Powered Calculator.....	£8.00	Philips Travel Printer calculator SBC1888	£26.00
THORN PANEL TX9 REC & REMOTE PANELS with Mains Trans.....	£5.00	<b>AUTO RANGE</b>	
TX10 REC & REMOTE PANELS with Mains Trans.....	£5.00	DC and AC and Resistance Pocket 3000 Philips	£12.00
TX100 FRONT PANEL.....	£5.00		
TX10 TUBE BASE ON PANEL.....	£3.00		
TX9 IF.....	£2.00		
THORN PANEL No. 515-353, 548.02, 564.01, 509/102, 515/173, 508/161.....	£5.00		
THORN TX STEREO SOUND O.P. PANEL (I.C. TA7227P).....	£1.00		
THORN VIDEO AERIAL AMP 01 M4-597-001.....	£6.00		

G11 LOPTS	£3.00	LINE TRANSFORMER Philips TX 12" and 14" Portable	£12.00
PHILIPS DESK TYPE Dual Power Calculator SBC1704	£7.00	WANDER PHONES Key Pad and Hand Set, No Case.	£1.00
K40 FOCUS POT	£1.00	TV AERIAL AMPS 1 way £9; 2 way £11; 3 way £15; 4 way £40; 6 way £50; 4 way 6dB each £30	
4.7µF KT3 W/W	10 for £1.00	VIDEO HEAD 3HSS made in UK JVC	
FOCUS POT HDK TPA6006	£2.00	SCIENTIFIC CALCULATOR SBC1704 Philips. In case	£7.00
KT3 Triplers	£6.00	THORN 8500 LOPT	£2.00
RECEIVER K3 Tex Front Panels with I.C.s (SAA3027/PSAB3013/HO44832R)	£5.00	NEW GEC 2110 LOPT	£2.00
G8 100K Pots on Panel & Lead for 6 Push Button Unit	£1.00	DX-TUNER VHF-UHF SEND FOR DATA TUNER	50p 75p
K30 Mains Switch remote	£1.00	GEC 20AX POWER SUPPLY Mark 2	£10.00
K38 Mains Switch remote	£1.50	THORN 9000 4.7m 40UV	40p
K39 Aerial Socket and Plug in Lead to Tuner	£1.50	12 VOLT BATTERY PACK Nicad A.A.	£5.00
KT3-K30 Slider Pots 4.7k	20p each	G8 TUNER V/CAP on Panel	£3.50
LARGE Focus Pots, Fits Pye, GEC, ITT, Decca	75p	G8 SPEAKER	75p
G8 Power Supply Panel	£4.00	9,000 SPEAKER	£1.00
EX DECCA 80-100 Decoder	£5.00	THORN 9000 Sound Of Panel	£30p
EX DECCA 80-100 Frame	£5.00	ONE I.C. K35 Decoder	£7.00
THORN 8000-8500-8800 Decoder	£6.00	K30 IF/K35 IF	£2.00
GLASS BEADS Diodes 200v/1.2A	50 for £1.00	THORN Lopt 8500-8800	£4.00
G11 Tip Switch	£20.00	TX9 THORN Tuner Panel with ICS Pots & mains trans.	£3.00
G11 IF Panel	£8.00	THORN CHASSIS 1600-1700 Series Mono	£10.00
G11 Decoder Panel	£8.00	THORN 1600 Rec- & Anode Cap	50p
JVC HEADS 3H55	£20.00	KT3-K30 Slider Pots 4.7k	£1.00 for 10
G11 Condenser 470/250V ITT	£2.50	K35 20 Turn Pots	6p each
G9 Power Panel	£1.25	HITACHI & GEC 20K Pots and 100K and 69K Philips	20 for £1.00
G8 Transductor	£2.00	100K POT & 20K wcap type with band switch	
G8 Push Button Unit	£4.00	KT3 K30 Speaker	30p
G8 Con/Panel New Back Type		K30 Push Button Switch 6 Way	£1.00
KT4-KT3-K30 Handset Replacement	£12.00	K35 Sound O/P Panel Plug in and KT3 sound o/p	£3.00
HT520 METER 20,000 Fuse Diode Protector Logic Test Facility	£15.90	K35 12 way Push Button Unit	£1.50
HT420	£12.00	K35 L.O.P.T. Split Diode	£6.00
9000 SERIES Decoder 01 929 014 080 Thorn	£5.00	RANK T20 Front Panel	£6.00
LATEST VIDEO		G8 6 Button Unit, New Type	£2.00
For Latest Philips, GEC, Pye and Hitachi. Front panel with memory chip and push button and pots and LED's.	£6.00 NEW	6 off LED DISPLAYS, Mixed	£1.00
20AX GEC LOPT Panel with Split Diode	£4.00	HAND SET TESTER, Infra Red	£3.00
RANK T20 Focus Pot	75p	AERIAL SPLITTER with filter	£1.00
RANK T18 Focus Pot	£1.00	UNI DIRECTIONAL Dynamic Microphone	£2.00
16" LOPT Split Diode 2433481	£6.00	20 TURN POTS with Band Switch	10p
Ex Panel Split Diodes 2432871/2432981	£5	PUSH BUTTON Mains Switch with Screw Hoies Fixing	4 for £1
Split Diode 2433752	£6	PYE 731 Line Trans	£3.50
T703A LOPT Transformer Rank with Focus Pots and Diode	£2.00	PYE 731 New Power Supply	£4.00
HITACHI Mains Switch	50p	800v DIODES at 3 amps, Glass Beads	6p each, 20 for £1.00
HITACHI AE Socket	30p	KT3 Line Output Transformer	£5.00
-1 CONDENSER Axial Leads 450 A/C 1200 D/C	15p	9000 THORN Front Panel with POTs & Push Buttons	£4.00
MAINS TRANSFORMER 240v in/20v/8v	£1.00	THORN 8500 Time Base	£3.00
GREEN FLAT, NEC, LED's	3p each 100 for £2	7 SEG DISPLAYS 4 Bank Displays Z-6042T	25p
15V015V 1 Amp Print Type	£1	SPLIT DIODE FBS1245AR	£5.00
12+12V 2.8VA Print 1"x1"	75p	PHILIPS KT3 4R7 W.W. Resistor	15 for £1.00
8+8V 1 Amp Print	£2.50	GEC TEXT PANEL PC895A7	£10
EI596 UHF V/CAP Tuner, small	£1.00	SEND FOR LIST OF VIDEO SPARES	£13 to £46 HEADS
FIDELITY Panels with I.C.	£3.00		
FIDELITY LOPT Split Diode AT2076/80	£5.00		
AT 2076/80			
ITT CYC20 to 45 PANELS Send for list			
MULLARD TEL-TEX DECODER Type VM6103	£7.00		
WE HAVE OVER 1,000 6 DIODE TRIPLER AT £1 EACH			
THORN main TV chassis complete TX9-TX10-TX90-TX925-TX100	£15.00		
TX10 8 way button unit	£8.00		
TX900 with PRR-SR7	£6.00		
PHILIPS VHS Tape 180	£2.25		
CVC 40 Cabinets	£15.00		
NEW IN - ITT BOXES	Post £5.00		

2431851	2433952	<b>SPLIT-DIODE £6 EACH</b>
2432211	2432984	
2432301	K4 L.O.P.T.	
2432491	K40	
2432871	2434274	
2432981		
2432984		
2433212		
2433481		
2433581		
2433751		<b>L.O.P.T.</b>
2433452	TX100 THORN	

36212	<b>L.O.P.T. SPLIT DIODE PHILIPS £5 EACH</b>
33651	
36072	
36362	
36383	
36482	
36761	
36831	
36832	
36833	
36921/79	
36922/79	

<b>TRANSFORMERS</b>	
AT2036/00	£1.00
AT2048/11	£1.00
AT2055	£1.00
AT2076/35	£1.00
AT2076/38	£1.00
AT2076/51	£1.00
CVC 420	£1.00
CVC 880	£1.75

AT2076/55	SHARP
AT2076/71T	MISHIUCHI
AT2080/15	
RCO ST CT3325	
OT2041	
FB165KA Orion	
2076/51	
2432461	
<b>£10 EACH</b>	
REGULATED POWER SUPPLY, Size 6"x5"x2 1/2"	
0.3v - 0.4.5v - 0.6v Lamp. Pre-set	
3v-to-12 volts, 1 amp.	
£5.00 Post £2.00	

<b>ITT TUNER CAN</b> CMC 800/3 £20.00	<b>I.C. Holders</b>
Decca 100 Lopt Panel and Frame £5.00	DIL - DIL
<b>PIN DATA</b>	40 Pin x 4 £1.00
Min with co-ax socket UHF w/cap	42 Pin x 5 £1.00
tuner 40dB gain £1.50 or 10 for £10	28 Pin x 5 80p
Can be adapted for video	16 Pin x 10 70p
	24 Pin x 5 75p
	14 Pin x 10 70p
	18 Pin x 10 80p
<b>TTT PANEL</b>	DIL - QIL
CMC 301 CMC 113 CMC 302	16 Pin x 10 £1.00
CMC 115 CMC 303 CMC 964	18 Pin x 10 £1.00
£5.00	28 Pin x 4 £1.00
<b>CMC 800</b>	AB Mains Switch
Power Supply Switch Mode	u/v 30p
£5.00	
<b>SEL ITT</b>	
IFB254F2 Front Panel	
£15.00	
<b>DECCA - GEC - ITT</b>	Philips Electrodynamic
6 push button - £5.00	Stereo Headphones
100 BC-BF Transistor £1.00	N6315 £10

SEND FOR LIST BRITISH MADE V.H.S. VIDEO HEADS from £15 to £20. SEND FOR LIST OF VIDEO SPARES, VIDEO LEAD AND BELTS

## SENDZ COMPONENTS

**63 BISHOPSTEIGNTON, SHOEBOURNE, ESSEX SS3 8AF.**

**SAME DAY SERVICE**

All items subject to availability. No Accounts: No Credit Cards. Postal Order/Cheque with order.

Add 15% VAT, then £1 Postage. Add Postage for Overseas.

**Callers: To shop at**

**212 LONDON ROAD, SOUTHEM. Tel. 0702-332992. Fax. 0702 338805**

Open 9-1/2.30-6. GVMT + school orders accepted on official headings. Add 10% handling charge.

# A TTL Logic Probe/Analyser

Stuart Anderson, B.Ed. (Hons.)

When building or servicing logic circuits it's of considerable advantage to have a piece of equipment that will readily reveal the logic state at any given point in the circuit. It's also useful if the unit can not only indicate logic one or zero but will also indicate whether or not a point is floating, i.e. not connected to anything at all.

The operation of the unit to be described relies upon two main factors: (1) the tri-state nature of the exclusive-or logic gate (to be described later) and (2) the fact that the inputs to TTL gates rise to the logic one state when they are left unconnected.

## Basic Gates

Before considering the probe circuit in detail it's relevant to take a look at basic logic gates. A logic gate performs a certain action under specified conditions, its output being totally dependent on the input(s).

The simplest logic gate is the not gate (inverter). Its output is simply not its input, hence a logic one input produces a logic zero output and vice versa. Fig. 1 shows the circuit symbols used and a simple single transistor implementation.

The nor gate is really a two-input not gate. Its output is high when neither input is high, i.e. when neither A nor B (see Fig. 2) is high.

The or gate is simply the inverse of the nor gate, see Fig. 3. Its output is high when either input, A or B, is high. The output is also high when both inputs are high. As the two-transistor circuit shows, the or gate is a nor gate followed by an inverter.

The output from an and gate (Fig. 4) is high only when both inputs are high, i.e. A and B must both be high.

The nand gate is the inverse of the and gate: it gives a logic zero output when both inputs are at logic one. Fig. 5 shows the symbols.

We have not shown simple transistor circuits for the and and nand gates. This is because they can be made up from the or, nor and not gates previously described. This is useful because it means that gates can be connected together in order to carry out different functions. This is known as combinational logic.

## Combinational Logic

At this point two important rules concerning logic gates can be stated: (1) any logic gate can be constructed using only nand or nor gates; (2) a nand or nor gate with its inputs connected together becomes an inverter.

The simplest example of how nand gates can be used to implement a different gate is that of the and gate: as Fig. 6

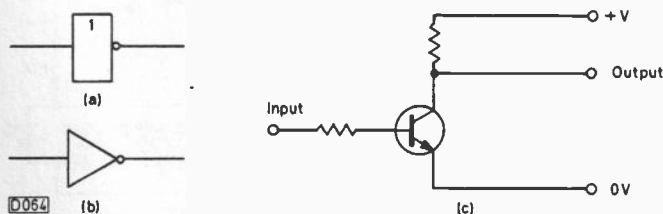


Fig. 1: The not gate. (a) Latest BS symbol. (b) Conventional symbol. (c) Single transistor implementation.

shows, the and function can be obtained simply by inverting the nand function.

A more complicated piece of combinational logic is shown in Fig. 7. Careful analysis of this circuit will show that it provides the nor function. You might ask why it might ever be necessary to use four nand gates in this way

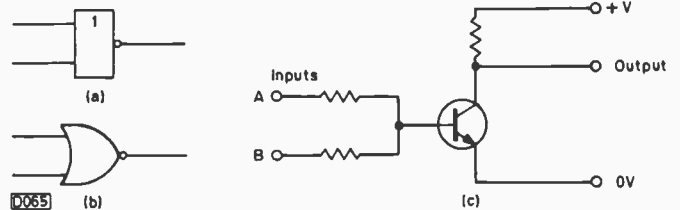


Fig. 2: The nor gate. (a) Latest BS symbol. (b) Conventional symbol. (c) Single transistor implementation.

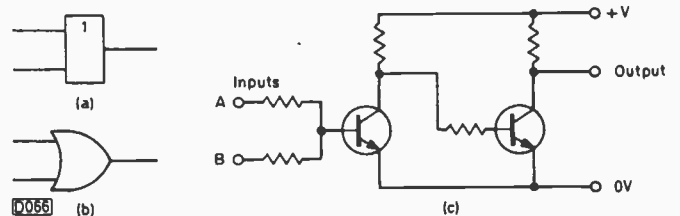


Fig. 3: The or gate. (a) Latest BS symbol. (b) Conventional symbol. (c) Two transistor implementation.

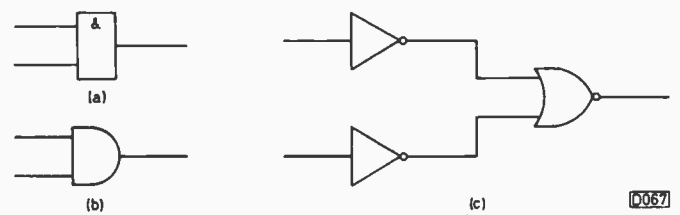


Fig. 4: The and gate. (a) Latest BS symbol. (b) Conventional symbol. (c) Implementation using two not gates followed by a nor gate.

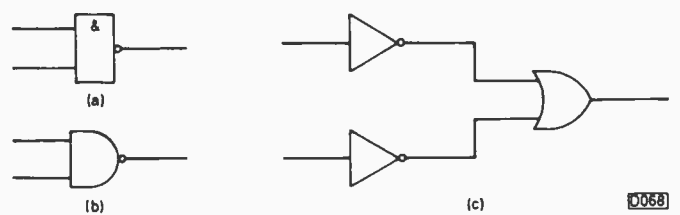


Fig. 5: The nand gate. (a) Latest BS symbol. (b) Conventional symbol. (c) Implementation using two not gates followed by an or gate.

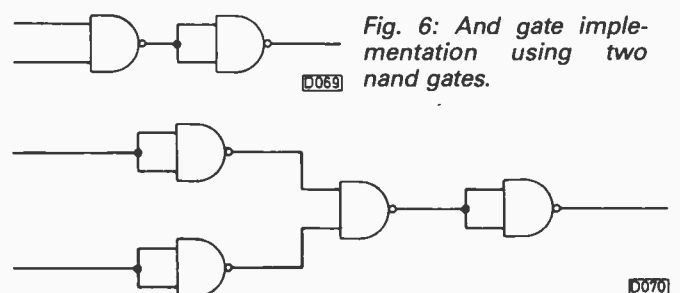


Fig. 6: And gate implementation using two nand gates.

Fig. 7: Nor gate implementation using four nand gates.

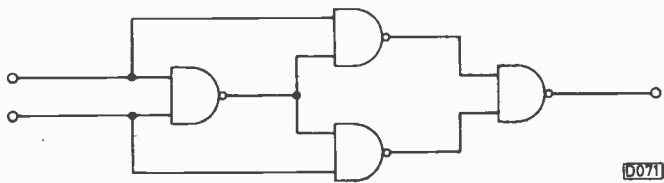


Fig. 8: Exclusive-or gate implementation using nand gates.

Not gate		Nor gate			Or gate		
In	Out	A	B	Out	A	B	Out
0	1	0	0	1	0	0	0
1	0	0	1	0	0	1	1
		1	0	0	1	0	1
		1	1	0	1	1	1

And gate			Nand gate			Exclusive-or gate		
A	B	Out	A	B	Out	A	B	Out
0	0	0	0	0	1	0	0	0
0	1	0	0	1	1	0	1	1
1	0	0	1	0	1	1	0	1
1	1	1	1	1	0	1	1	0

Fig. 9: Truth tables for logic gates.

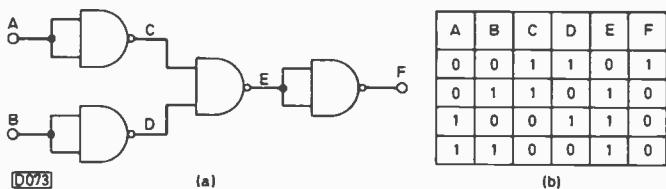


Fig. 10: Analysis of nor gate implementation using nand gates, (a) circuit, (b) truth table.

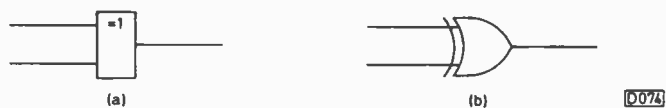


Fig. 11: Exclusive-or gate symbols, (a) latest BS, (b) the conventional symbol.

instead of using a single nor gate. There are two answers to this. First, in a more complicated logic circuit design several gates may be left over – gates are usually packaged in i.c. form in groups of four. Thus spare gates can be used to implement other gates required. Secondly reduction to nand gates can be used for minimisation, i.e. you might find that in a very complicated circuit two inverters follow each other and can thus be eliminated.

Fig. 8 shows another example of combinational logic. Four nand gates are once again used, but in a different configuration. In fact we have here a completely different gate, the exclusive-or gate. It provides a high output when either input is high but not when both inputs are high. The best way to see how it achieves this is to draw up a truth table. Truth tables show the output state for all possible input state(s). Thus the simplest truth table is that for the not gate (inverter) which has only two rows and two columns – see Fig. 9 where the truth tables for the gates described so far are shown.

Fig. 10 shows how the truth table for the nor gate conditions is obtained with the circuit shown in Fig. 7. The first two nand gates are connected as inverters, so that their outputs at C and D are the inverse of the inputs at A and B. The third gate performs the nand function whose conditions are listed in columns C, D and E. The fourth gate again provides inversion, its output being shown in column F. To see the actual function provided by this combination of gates, refer to columns A, B and F of the truth table: these represent the nor function.

With this kind of analysis it can be shown that the exclusive-or configuration shown in Fig. 8 provides the truth table shown in Fig. 9. Fig. 11 shows exclusive-or circuit symbols.

### Circuit Description

The exclusive-or gate is of particular interest to us since it forms the heart of our logic probe. The exclusive-or gate has a tri-state nature, though this must not be confused with a real tri-state device. These can be used as buffers whose outputs take up a logic one or zero state or a high-impedance output condition. They can be used for example in data lines in microprocessor systems. In the present context tri-state means that there are three variables associated with the input and output logic conditions. The significance of this is that since the output is logic one in accordance with the or function and zero in accordance with either the nand or the or functions we have, in combination with other gates, the three output possibilities required for our logic probe.

Fig. 12 shows the circuit diagram of the probe. We can now examine its mode of operation.

Although ready-made exclusive-or gates are available the function has been implemented using a 7400 quadruple nand gate (IC2). This readily available device costs no more than an exclusive-or gate and takes up no more space.

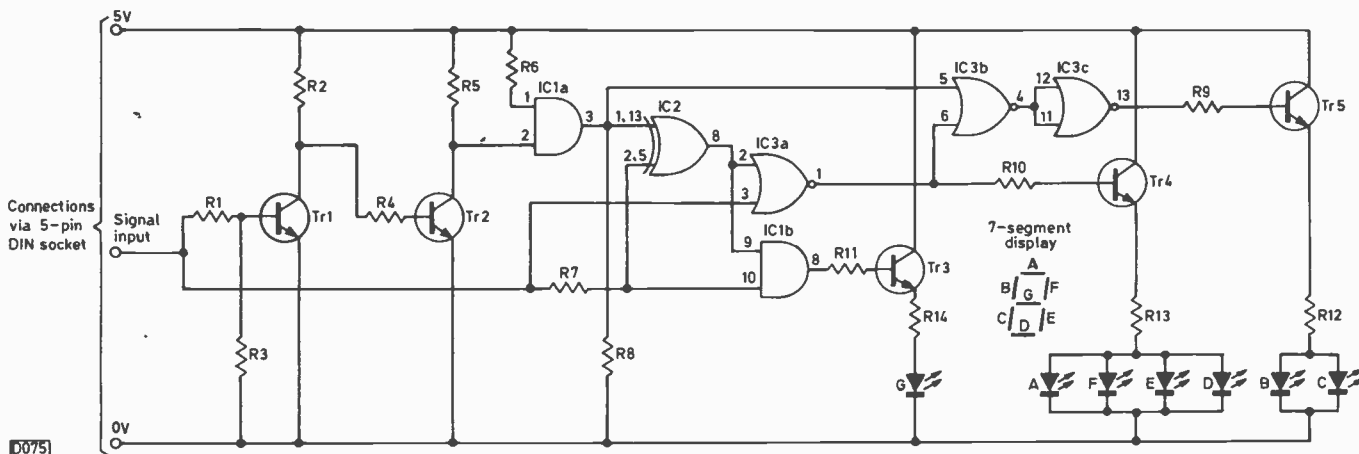


Fig. 12: Circuit diagram of the logic probe/analyser. Note that the nor gates IC3b and c are used to implement the or function, while IC2, a 7400 quad nand gate, implements the exclusive-or function.

The probe input is fed to the two-transistor buffer Tr1 and Tr2 and also to pin 3 of the nor gate IC3a. It is also connected via R7 to pins 2 and 5 of the exclusive-or gate IC2 (7400) and pin 10 of the and gate IC1b. Thus all these pins take up the value of the input.

Let's assume first that the input is a logic one. Pin 1 of and gate IC1a is always at logic one since it's connected via R6 to the 5V line. Pin 2 will become logic one via the transistor buffer, so pin 3 will also be at one. This output is connected to pins 1 and 13 of the exclusive-or gate IC2. Under these conditions both inputs to IC2 are at one and its output at pin 8 is zero. Thus one input of nor gate IC3a is at zero and the other at one, so its output at pin 1 is zero. One input of and gate IC1b is at zero (from pin 8 of IC2) while its other input is at one, so its output is at zero. Finally, pin 3 of and gate IC1a is connected to pin 5 of the or gate made up from nor gates IC3b/c whose output at pin 13 rises to one. Thus Tr5 conducts and the seven-segment display indicates one.

If the probe's input is logic zero, a similar analysis will show that IC1b gives zero output while the outputs from IC3a and IC3b/c are at one. This gives a zero indication.

If there's no input at all, pin 2 of and gate IC1a is at zero since the input to the transistor buffer is connected to the negative side of the supply via R3. Pins 2 and 5 of IC2 and pin 10 of IC1b will rise to logic one however. Following through the rest of the logic you can see that the only high output is at pin 8 of IC1b. Thus only the central portion of the seven-segment display lights up, indicating a floating input. Pin 3 of IC1a is connected to the negative side of the supply via R8 to prevent it rising to logic one in the absence of an input signal.

These logic sequences are summarised in Fig. 13, where Z indicates a floating input.

### Construction

The probe can be built on a Veroboard strip or a printed circuit board can be made. In my opinion the use of Veroboard is simplest, so we'll describe this first.

The prototype was built on a piece of Veroboard less than 10 × 6cm (36 × 24 holes). Fig. 14 shows the method of implementing the exclusive-or gate using a 7400 i.c.

### Components List

R1	2.2k	R6	1k	R11	22k
R2	1k	R7	2.2k	R12	33Ω*
R3	1k	R8	47k	R13	22Ω*
R4	15k	R9	4.7k	R14	68Ω*
R5	2.2k	R10	10k		

Tolerance and power ratings are not critical. All resistors could for example be 10%, 0.5W.

\*See text.

Tr1-5	BC108 or equivalent
IC1	7408 quad and gate
IC2	7400 quad nand gate
IC3	7402 quad nor gate

Maplin 0.3in FR38R or 0.5in FR41U seven-segment displays are suitable.

Maplin LH14Q plastic box was used for the prototype.

5-pin DIN plug and socket, crocodile clips plus Veroboard or PCBs. Prototype used 10 × 6cm and 4 × 3cm boards.

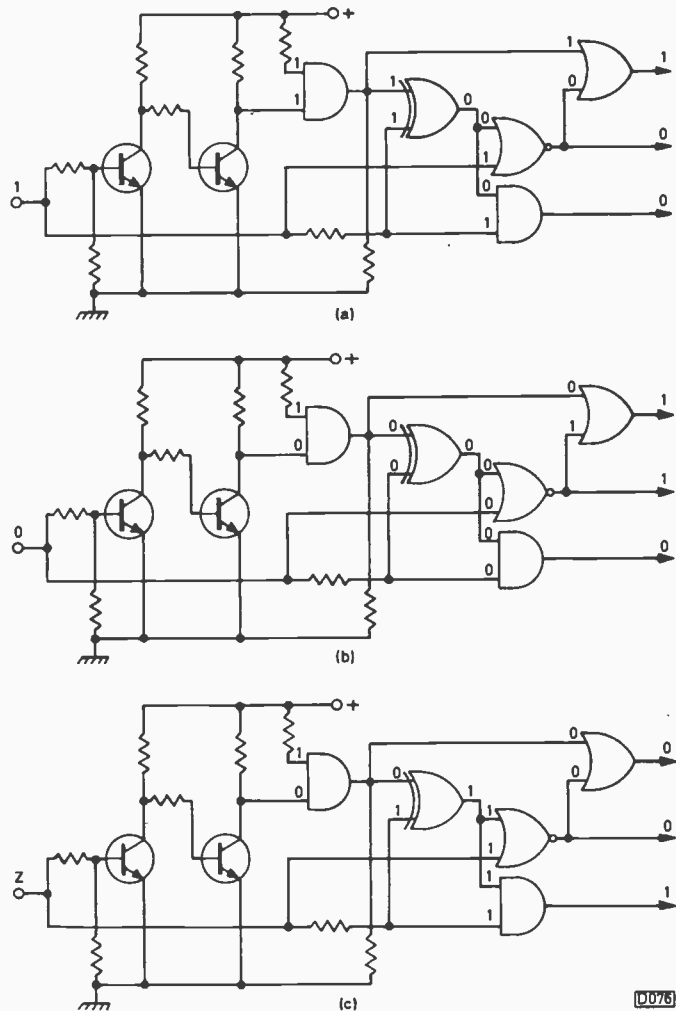


Fig. 13: Analysis of the logic probe conditions (a) with logic one input, (b) with logic zero input and (c) with a floating input.

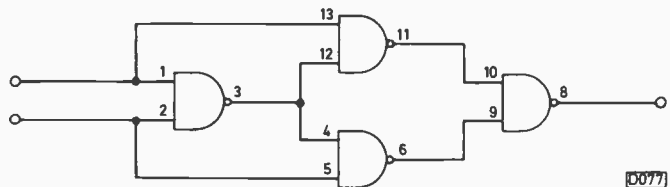


Fig. 14: Exclusive-or implementation using a 7400 chip containing four nand gates.

The inputs are pins 1/13 and 2/5 while the output is pin 8. The method of connecting the 7402 chip to implement the or function is clear from the circuit diagram.

Fig. 15 shows an outline layout as used in the prototype while Fig. 16 shows the completed circuit. The seven-segment display and its associated limiting resistors R12/3/4 are mounted on a separate piece of Veroboard with connections to the main board via wires. The size of the seven-segment display is a matter of choice, but the design assumes the use of common cathodes. With a small display size R12 is 18Ω, R13 10Ω and R14 33Ω. With larger displays, e.g. half inch, these values should be approximately doubled (see components list).

Fig. 17 shows a suitable PCB design if this is preferred while Fig. 18 shows a layout for the display.

Nine wire links or jumpers are required. It's probably best to fit these first since two are underneath i.c.s. Fitting the links is no problem if i.c. holders are used and this is generally to be recommended. It's even easier if i.c.

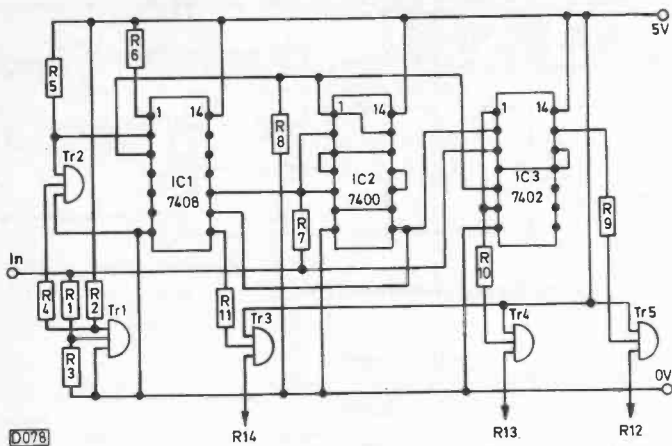


Fig. 15: Outline layout for construction using Veroboard.

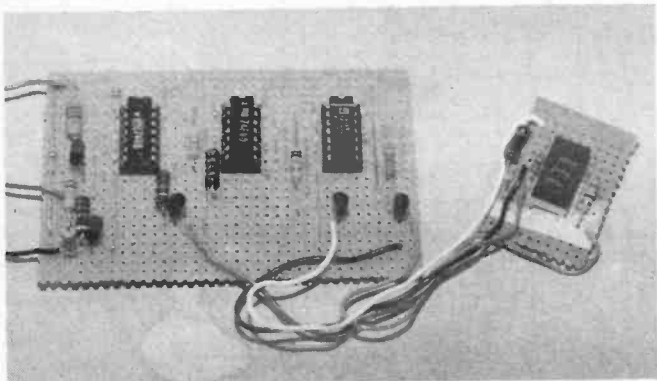


Fig. 16: The completed unit, built on Veroboard.

socket strip is used as there is no plastic base in between. These strips are very versatile and there is no waste.

After fitting the links and i.c. holders, fit the five transistors then the eleven resistors. The seven-segment display panel can then be made and the two linked together with colour-coded wires.

Once these operations have been completed the i.c.s can be slotted into place and the unit tested. This can be accomplished simply by connecting a 5V supply. With no input only the central segment of the display should light. One and zero should be displayed when the input is connected to 5V and 0V respectively.

If the checks prove satisfactory the unit can be housed. The prototype was incorporated in a box measuring 11 × 7.5 × 3cm. Holes for the display and a five-pin DIN socket were made in the lid, these items being bolted in

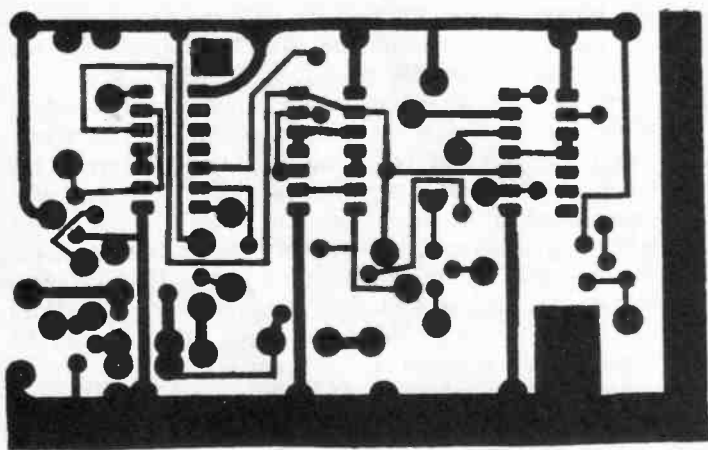


Fig. 17 (left): PCB layout for the logic unit. Scale 1:1.

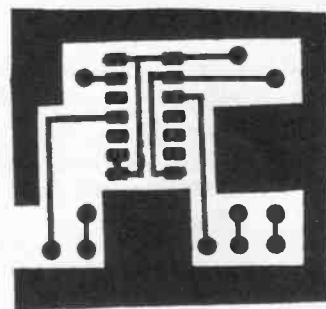


Fig. 18 (right): PCB layout for the display unit. Scale 1:1.

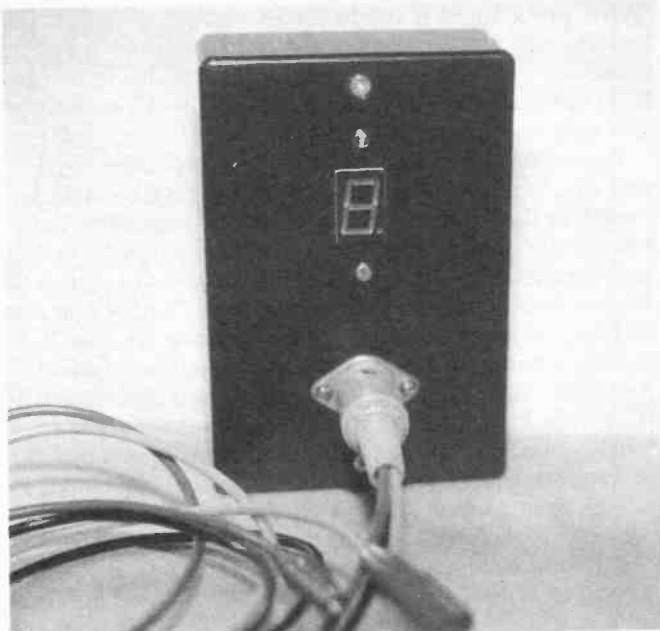


Fig. 19: The completed unit in its case.

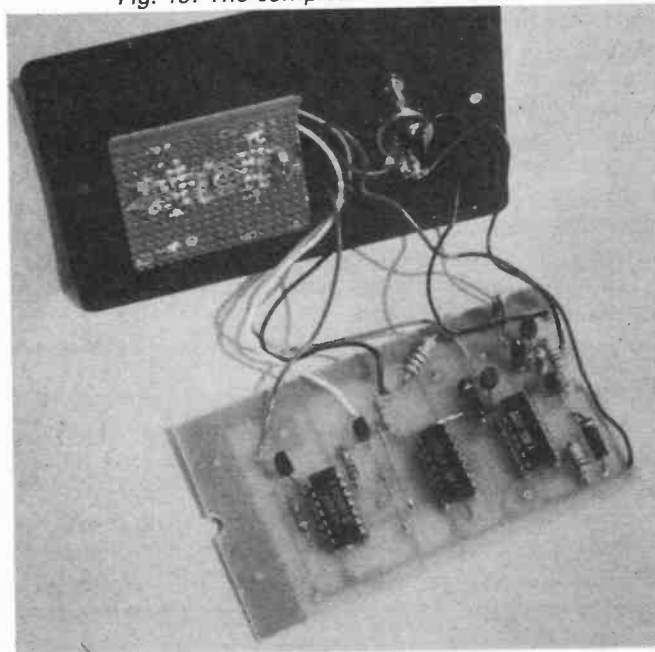


Fig. 20: Internal view of the completed unit.

place. The probe was made from an old meter probe, the other connections being made via standard crocodile clips. These details can of course be varied to suit individual requirements.



# Camera Workshop Accessories

Nick Beer

Servicing cameras and camcorders is a specialist business that should be tackled only by those equipped and competent to do so. The increasing number of cameras and camcorders now on the market means that few dealers will not come into contact with them.

A considerable investment is required to set up a complete camera/camcorder workshop. As a result, many people fall into the trap of attempting repair and alignment without any form of aid. If you have a technically competent staff (and a VCR engineer does not automatically qualify as a camera engineer) but your camera turnover does not justify spending several thousand pounds on a workshop, a usable servicing area can nevertheless be constructed without immediate need for that most expensive item of camera test gear the vectorscope. The camera workshop should however be in a separate room which is whited out, and rather more stringent rules of cleanliness than in the average TV workshop should be observed. Accurate lighting of a specific intensity and temperature is required — obviously alignment calls for a standard.

In addition to the usual workshop equipment — scope, meter, etc. — the accessories mentioned in this article are required. Operation along these lines should provide a workable alternative to a dedicated camera/camcorder servicing department. If you cannot justify this amount of effort your camera servicing should be subcontracted to someone with the necessary facilities.

## Alignment Charts

Most camera head alignment is based on the use of viewing charts. These are viewed under accurate lighting conditions. It's important that both the charts and lighting are accurate. Some service manuals, notably those produced by Panasonic, include some very basic charts to check linearity and focusing, but the most important charts are those required for alignment of the vision circuits.

The first of these is a colour-bar chart. This is self-explanatory, usually resembling the pattern produced by your current pattern generator. A quick check with various manufacturers indicates that the average price of such a chart is in excess of £100 — this may come as quite a shock for a single chart. We have some good news on this score however — see later.

Secondly comes a logarithmic grey-scale chart. This consists of a series of accurately painted grey bars from white to black and black to white. This is again used for white balance alignment. It tends to be even more expensive — typically around £150.

A resolution chart provides a way of determining focus accuracy and the horizontal resolution of the pickup device/camera head.

Another type of chart is used to align camera geometry. It comes in several forms but basically consists of a crosshatch pattern and a circle.

Obviously the total cost of a set of charts could be considerable. Now for the good news: PAG Ltd., Video Division, 565 Kingston Road, London SW20 8SA (telephone 01-543 3131) has available a set of charts consisting of colour bars, a logarithmic grey scale, resolution and

registration patterns in a sturdy folder at a trade price of £94 plus VAT. They are of superb quality, presented in a folder with a calibration slip and instruction leaflet. Representing a massive saving, they are thoroughly recommended. These charts have a laminated finish to enable them to be cleaned. The firm also has a series of matt finish charts of US origin available. These can be bought separately and are somewhat more expensive. A shiny surface is no problem with diffused lighting.

## Illumination

The charts are normally positioned about 2m (depending on chart size) from the front of the pickup device. They should be on a flat, level, perpendicular surface — as should the camera under test.

The level of illumination required varies with different manufacturers. Typical values are 1,400 and 2,200 lux (3,200°K). The illumination must be very even, with no other light sources (from a window for example) affecting the chart area. The most practical way to achieve this is to paint the whole area white — matt to avoid reflections.

There are several sources of the required light. We use a 1,000W tungsten halogen unit from RS. Aico International, the camera accessories firm, do a fan-cooled 1,000W Braun unit that's suitable and is not expensive. To vary the light level at the chart you can incorporate a dimmer or physically move the light. Either way you will need a light meter to set the level.

## Light Meter

Again, RS have a suitable unit. As you would expect, it's well built and comes with a carrying case and strap. The light sensor is separate from the meter itself, connected by a small lead. It sits in the top half of the case, being strapped in. According to the instruction leaflet you can use the sensor in this position, but since the strap runs through its centre some of the light is blocked, giving a slightly low reading. We found the best approach to be to lift the sensor out and sit the meter on a nearby bench, making use of the amply long lead. The meter is battery powered (one PP3 battery), is guaranteed for a year and is covered by the RS repair/exchange service (for the appropriate fee).

Those determined to do the job without the equipment and expertise required — there will always be a few — will probably be saying that they can use their stills camera light meter. This is not the same thing however. When we tried a couple against the RS one we found that there were inaccuracies.

The RS meter has four ranges, 50, 250, 500 and 2,500 lux f.s.d., also a battery test. Its order number is 610-815 and the trade price is £135 plus VAT. We found it to be ideal for use in our camera workshop and thoroughly recommend it. A  $\times 10$  neutral density filter is available at £53.50 trade plus VAT, order number 610-821.

This concludes my round-up of the accessories required for camera servicing. Finding supplies of, in particular, the charts can be difficult, so I hope this piece may save you some time and money. Thanks are due to Steve Beeching, T. Eng., for his assistance.

# How to deal with EHT arcing

Nick Heer

The problem of e.h.t. tracking, arcing or flashing can be what you will encounter from time to time in these columns. The thing that interests me is the way in which some "engineers" deal with it.

The trouble usually arises because of breakdown of an insulator, maybe the e.h.t. or focus lead, the tripler or line output transformer casing, or the e.h.t. cap itself. Particularly in the latter case damp, condensation and dirt are well known contributory factors: the e.h.t. tracks along this resistive path and the resulting heat causes damage to the cap, thus making the problem worse.

## Initial Steps

When confronted by an e.h.t. problem the first thing to do is to switch off and discharge the c.r.t., if it has remained charged (obviously the tube will be discharged if the leak is large enough). The correct way to do this is via a large resistance to the Aquadag earth strip – a convenient method is to use the e.h.t. probe you employ with your meter. Unfortunately many people still discharge to the metal chassis, then wonder why the set has a fault it didn't have previously – remember that most chips operate with a supply of between 5V and 12V!

Once you've established that the tube is discharged, examine all the suspect areas – obviously if you saw a flash from the tripler's case you needn't look much farther for

the fault, but whenever you have a flashover the cap, tripler and line output transformer cases, the e.h.t. leads, the focus potentiometer and spark gap and the area of the tube surrounding the e.h.t. rose should be checked. If there are any signs of perishing, tracking, cracking, cuts or other damage the item concerned should be replaced.

## EHT Caps and Leads

The most common thing to fail is the cap itself. Many people just pour on sealer or silicone grease until the arcing quietens down, only to find themselves facing the set again days later. Unless it's perfect, an e.h.t. cap should always be replaced. Many people seem to be unaware that separate caps are available from suppliers, e.g. the HRS EHTCAP1 at 59p + VAT, the Willow Vale 03425 at 74p + VAT and the SEME ANODECAP at 99p + VAT (one off prices). Thus from the price point of view it's not worth thinking twice before changing a cap.

Before you do so, the rose of the tube should be scrubbed: the best fluids for the job are methylated spirit, RS solvent cleaner or RS aerosol demoisturising lubricant (purple squirt as we call it). Use a rag to remove all dirt, rust and moisture from the area. When you've finished, remove all traces of the fluid. The cap should then be pressed home so that it's a tight fit – adjust the clips if it's slack – and the lead routed as it should be, clipped and

# TAYLOR

U.H.F. TELEVISION DISTRIBUTION AMPLIFIERS



T.S. 2008 8-Way U.H.F. Distribution Amplifier

Price

**£19.95** each + Carriage & VAT [Total £24.68]  
10+ £16.40 + Carriage & VAT  
20+ £15.09 + Carriage & VAT

**Specification:** Frequency: 470 - 860 MHz  
Minimum Gain per outlet: 2dB  
Mains: 240V A.C.

T.S. 2004 4-Way U.H.F. Distribution Amplifier

Price

**£14.95** each + Carriage & VAT [Total £18.93]  
10+ £12.60 + Carriage & VAT  
20+ £11.59 + Carriage & VAT

**Specification:** Frequency: 470 - 860 MHz  
Minimum Gain per outlet: 2dB  
Mains: 240V A.C.

VISA

**TAYLOR BROS. (OLDHAM) LIMITED**  
Bisley Street Works, Lee Street,  
Oldham, Lancs., England. OL8 1EE

Telephone: 061-652 3221  
Fax: 061-626 1736  
Telex: 669911 Taylor G



tied correctly.

Another thing that can be overlooked when a cap is replaced is the series resistor (if one is fitted). If at all possible, save the original one. It's usually fitted in the neck of the cap, so bear this in mind before removing the old one.

Finally on the subject of caps don't smother them with silicone grease, rubber or other gunges. This will only attract muck and start the problem up again. Look at a new set: it doesn't have gunge around the cap does it?!

Leads from diode-split line output transformers are another favourite for this kind of trouble – I think of Philips, ITT and B and O sets in particular. The leads usually plug or push into the transformer at one end, with the cap on the other end. Again, replace the lead if you are in the least bit suspicious. Don't do what I've seen done – the lead taped up or a section cut out. Remember that the leads are tuned lengths, and again usually have a series resistor. It's perfectly in order to fit a new cap to one of these leads so long as the rules outlined above are observed.

### **Triplers and LOPTs**

If the case of a tripler or line output transformer breaks down the action required is replacement without question, not as some people would have it a quick squirt of plastic

seal over the fracture. These items are critical to safety. The cost of replacement may be high, and this could mean writing a set off and loss of a repair job, but is this worse than being sued for damages when the customer's house burns down as a result of the economy repair? Don't say this won't happen – it has.

### **Plastic Sealing and Silicone Rubber**

I am absolutely against the use of plastic sealing material in e.h.t. areas: it just seals in the fault which will reappear soon. As an aside however I would recommend the use of plastic sealing as the perfect solution for noisy transformer coils, transducers and suchlike – forget wood glue and rawplugs or whatever else you might use. This is far and away the easiest and cleanest as well as the most effective way of silencing wound components, but always allow plenty of time for the sealing to set before switching the receiver on again.

Silicone rubber, which again shouldn't go within a mile of e.h.t. areas, is perfect for repairing VCR fronts where the buttons that are hinged by the elasticity of the plastic have snapped, usually necessitating replacement which is expensive.

If you're thinking what a load of rubbish this concern for correct action is, just remember Denis Mott's article on "The Legal Aspect" (July 1988).

## **Still Confused**

*Les Lawry-Johns*

I'm still confused but people keep asking me to do things they can't do. Like the Decca set that came in yesterday. The owner asked if he could stay as he lives a long way from here.

### **Trouble with Triplers**

As it was tripping I started by disconnecting the tripler. This stopped the tripping so I told him how much it was going to cost him. He agreed and I reached for the last new universal tripler. I didn't get it down but instead I looked at the one fitted. As it didn't have a diode lead I decided to fit a spare Philips G8 tripler which was next to the universal one. This was duly fitted and connected – as the e.h.t. lead was a bit short it had to be fitted with the chassis lowered. I then switched on. The sound boomed out and I waited for a picture to appear. And waited. I turned up the brightness. Still no picture.

I checked the e.h.t., which was present, so I moved to the tube base voltages. No first anode supply. Something stirred in my befuddled mind. I cut the mauve lead at the bottom of the right side panel, intending to try an alternative supply. Big sparks came from under the line output transformer, so I hurriedly reconnected the cut lead. There was no model number on the rear cover but I was pretty certain it was an 80 series chassis, so I looked up the circuit, aware that I'd done this only a short time ago. There's no separate rectifier diode for the first anode supply. I then recalled that last time I'd changed the tripler I'd fitted a universal type with the diode and earth leads connected.

So I reached up for the last universal type and hurriedly

fitted it. A picture appeared, too bright because I'd turned up the first anode controls. I turned them down and then turned down the colour to set up a good black-and-white display. Having done this I turned the colour up and the customer commented that it was the best picture he'd seen on the set. I apologised for the delay and he continued:

"You ought to be working in a government factory experimenting with things that won't go right . . ."

He paid up and departed and just at that moment Rick Kinslow drew up in his car. In his hand he had a tripler that looked like the one I'd just changed.

"Have you got a tripler for a Decca Les?"

"I've just used my last one."

He looked up on the shelf. "There's one" he said.

He took down one that I'd taken to be another type, but I could see the difference.

"Take it and try it" I said, ashamed of myself for not having seen it. All the trouble I'd brought upon myself for not looking properly. Oh well.

### **Processions**

I then had to cross the road to post a letter. Half way across I was amazed to see an army of ants marching down the road in perfect step, carrying banners.

"What's that on the banner?" I asked.

The ant carrying it looked up and angrily snapped "it's God of course".

"But it looks like an ant to me."

"Of course it does. What do you think God looks like?"

"Well", I faltered, "God made man in His own image".

"What do you mean His own image? You've given Him a gender!"

"Those males always do" a female ant shouted. "They think they're God and they could well destroy our planet within a few years. Why doesn't their God stop them?"

I ran over to the post box, a bit fed up with these processions that keep coming by. They'd gone by the time I got back.

# Teletopics

## THE WHITE PAPER

The government's white paper on the future of broadcasting in the UK was published a few days after our last issue went to press. The main proposals about TV broadcasting are as follows. ITV to be known as Channel 3, with ten-year licences going to the highest bidder after a process of vetting. The IBA and the Cable Authority would be replaced by an Independent Television Commission which would be responsible for all commercial TV including cable and satellite broadcasting. While being responsible for licensing and laying down programme requirements it would not be concerned with detailed programme scheduling. The BBC to lose one of its channels during the night-time hours and be subject to a licence revenue squeeze to encourage it to seek alternative ways of raising revenue. Its other channel to be retained for night-time broadcasting only if used for subscription services. Channel 5 to be established as a national service reaching some seventy per cent of the population by 1993, financed by subscription and advertising. Broadcasters would apply for time segments. Viewers would require a separate aerial with probably different polarisation. The main area where a Channel 5 service will not be possible, due to interference problems with Continental stations, is along the south coast. The two unallocated DBS channels to be made available at an early date. In fact the franchises are to be advertised by the IBA this January and services could start in 1990, within a year of the start of BSB's three DBS channels. BSB and Virgin are amongst the organisations that have already expressed an interest in bidding for the two channels. Following a study that has confirmed its feasibility, local MVDS (microwave video distribution systems) TV services are to be encouraged — local in the geographical rather than the programming sense. The feasibility study carried out for the Department of Trade and Industry by Touche Ross Management Consultants confirmed that an extra twelve national channels could be made available to viewers in this way within two years, so terrestrial microwave TV might be with us by 1991, probably in the 12GHz band. The 2.5GHz band is believed to be too crowded while the technology is not yet available to use the 30GHz band. The study emphasised that MVDS would be cost competitive with other methods of broadcasting.

The suggestions contained in the white paper remain for the time being as proposals, and a great deal of debate on them is expected during the early months of 1989. A government bill implementing the proposals is expected to be put before parliament in late 1989 or early 1990.

## ASTRA

Following the successful launch of the French TDF-1 TV satellite, Astra is due for launch on December 9th. W. H. Smith Television has signed a multi-million pound contract to lease two of Astra's transponders for its Lifestyle and Screensport channels. Transmissions will initially be to the PAL standard, changing to D-MAC with Eurocrypt scrambling in mid-1989. Financing will be by both advertising and subscription.

A number of manufacturers have announced plans to launch equipment for the reception of Astra transmis-

sions. Of particular interest is Toshiba's plan to market a PAL-only, upgradeable receiver in March: purchasers will be able to have their receivers upgraded for PAL/D-MAC operation by buying an add-on unit. A PAL/D-MAC receiver with the full range of broadcast hi-fi, text and digital enhancements will be released by Toshiba in October.

Rupert Murdoch's Sky Television is to add a fifth channel to its Astra TV services. Sky has set up a joint venture with the Walt Disney Company to make available as a subscription service costing viewers £12 a month Sky Movies and The Disney Channel. The latter will be operated by Disney and will provide 18 hours of programming daily. A smart-card system is to be used for this service. Subscribers will be sent a card — similar to a credit card but incorporating some electronics — to enable their decoders once a month or quarterly. Scrambling is to start on September 1st, before which the channels will be available free.

Robert Maxwell plans to lease two transponders on Astra for the MTV-Europe pop music service and a news and information channel.

Satellite Supplies Ltd. (234 High Street, London NW10 4TD — telephone 01-961 1346) will be supplying a complete TVRO package for reception of the Astra transmissions from February. The Sakura system features a twenty-channel memory and infra-red remote control at a trade price of £160. It's upgradeable for MAC via a five-pin DIN socket.

Tatung is holding a countrywide series of satellite workshops to prepare dealers for the new TV services. Further information is available via the Tatung dealer hotline 0952 290 111 ext. 251.

## SATELLITE TV

BSB is to pay over \$160m for the exclusive right to broadcast some 175 feature films owned by Columbia pictures. The company previously concluded other, smaller deals with Cannon, Warner, MGM-UA and a new company set up by David Putnam. BSB is to ask its investors for more money to cover the cost of securing these film rights. A second round of financing this summer is expected to raise £500-£600m instead of the originally planned £400m.

SuperChannel has been placed under court-appointed administration. The Italian company Beta Television (Videomusic TV) which took a majority interest in the channel last month has announced that SuperChannel's debts and liabilities for future commitments are greater than expected.

The Department of Trade and Industry has awarded licences to six companies to provide satellite information services, including TV, to closed-user groups, e.g. betting shops, securities houses etc. Licencees include BSB, Maxwell Satellite Communications and British Aerospace.

The IBA has announced that its two eight metre dishes which will provide the uplink for the DBS services are now in position at Chilworth, Southampton. Acceptance tests have started.

## SATELLITE TV BOOKS

Swift Television Publications, 17 Pittsfield, Cricklade, Swindon, Wilts SN6 6AN has just published at £8.95 the *Satellite Television Installation Guide* by John Breeds. This well produced and extensively illustrated book provides a thorough, practical guide to installing satellite TV equip-

ment. Examples common for the main European satellites are included along with dish setting up angles covering the whole of the UK. There's a very helpful glossary at the end. The book has been adopted by the Confederation of Aerial Industries for trainees on CAI courses accredited by the City and Guilds of London Institute.

*All You Need to Know about Satellite TV* by S. Guest-Lee at £2.99 is a well-produced book intended for the general public. It's available from Satellite TV Publications, 79a Bournemouth Road, Chandlers Ford, Southampton, Hants SO5 3AP.

## **BUSINESS NEWS**

According to the latest figures from BREMA, CTV deliveries during the third quarter of 1988 were 1.3m compared to 1.1m in the previous year. Imports took 47 per cent of the market compared to 40 per cent, led by a surge in small-screen CTV deliveries from the Far East. VCR deliveries increased by nine per cent in the third quarter and by 22.6 per cent during the first three quarters of the year.

The European Commission has extended the scope of its investigation into charges of CTV dumping from South Korea, started in February 1988, to include China and Hong Kong. The three countries increased their exports of small-screen CTVs to the EC from 35,000 in 1985 (three per cent of the market) to 620,000 in 1987 (21.5 per cent of the market).

The South Korean manufacturer Daewoo is to set up an £18m VCR plant in Antrim, Northern Ireland with a production capacity of 500,000 machines a year.

Rumbelows has taken over the Surrey-based Ketts chain of 36 radio and TV stores. Polly Peck is taking over the Italian CTV manufacturer Imperial Electronics which was at one time part of Telefunken. Imperial has a capacity of 200,000 sets a year and for thirty years has produced sets for the own-brand market. Poly Peck's main CTV production is in Turkey.

Sony (UK) Ltd.'s manufacturing plant at Bridgend, South Wales has won the 1988 Quality Award. The award, made by the British Quality Association, is the premier UK award for quality achievement in British manufacturing and service industries.

## **S-VHS NEWS**

Arrangements have been made to enable European Super-VHS equipment to be used with TV sets having a scart connector. There are three different methods. First, S-VHS equipment can be connected via the composite video signal input of a TV set's standard scart socket. Some sets however now have a second scart socket with pins 15 and 19 modified for Y/C signal input. This approach reduces cross-colour and dot interference. S-VHS VCRs and camcorders are switchable between composite video and Y/C outputs. It's also possible to split the S-VHS signal into its RGB components and feed these into an RGB compatible scart input: JVC is to release an S-VHS/RGB converter, Model KM-V7EG, for this purpose.

JVC is also releasing two high-resolution TV sets for use with the S-VHS format. Models AV-S250 and AV-S280 have 63 and 70cm screens respectively and feature wideband video processing circuitry which provides a horizontal resolution of 560 lines with the AV-S250 and 630 lines with the AV-S280. Both sets feature an S (Y/C) terminal, phono audio sockets and twin scart sockets, one

of which is modified for Y/C signal input. Other features include a timer, a 74-line buffer timer, a two-way, four-speaker system and surround sound circuitry.

Mitsubishi and Ferguson have introduced S-VHS VCRs. Ferguson's Model FV39S includes nicam 728 capability, VHS hi-fi stereo, long play and advanced indexing facilities. It's expected to sell at around £1,000 with a comprehensive package of accessories. Mitsubishi's HS-B70 has a similar specification and price, with automatic digital tracking, an LCD programmable remote control system and full on-screen operating and programming graphics.

Mitsubishi has also launched two large-screen TV sets equipped with nicam decoders and S connectors. The CT3703STX has an 89cm screen and dynamic beam focusing. The suggested price is £2,500 and the weight 92kg! The CT2553STX has a 59cm screen, an automatic switch-off timer and sells at a suggested £650. There are optional video cabinets for these two sets.

S-VHS tape for European use has been introduced by TDK: the XP (extra professional) tape has superfine particles and a coercivity of 900 Oersteds. A new calendaring process is used to improve the surface smoothness and a new binder and backcoating have been developed. TDK claims that a special additive improves head friction and durability. A permanent anti-static shell reduced dust contamination. The tape is available in two lengths, SE-120XP and SE-180XP at £10 and £11 respectively.

## **WIZARD DISTRIBUTORS**

The Manchester-based component wholesaler Wizard Distributors of Empress Street Works, Empress Street, Manchester M16 9EN (061 872 5438) has produced its 1989 catalogue. Copies are available free of charge to trade customers. The new 84-page edition includes a section devoted to Hinari spares and a comprehensive video head identification list.

## **CABLE TV**

The CATV franchises for Avon and Thames Estuary North and South, covering some 700,000 homes, have been awarded to United Cable, one of the largest US cable operators.

The Cable Authority is considering cancellation of the franchises awarded to some companies that have failed to start installing cable. Of the 27 franchises that have been awarded, covering some six million homes, well under half are in operation.

## **PANASONIC'S VIDEOPHONE**

Panasonic intends to launch a videophone, Model WGR2, in the UK this summer at around £200. The unit has a camera and 4.5in. screen and can transmit and receive a monochrome still picture via the telephone line in about ten seconds. Transmission with a picture costs about the same as a standard phone call.

## **VIDEO NEWS**

A digital VCR, Model VR6648, has been added to the Philips range. Digital features include picture-in-picture (PIP), multi-PIP, nine-picture tuner scan and strobe. The suggested price is £540.

We have been asked to correct the price of the Pentax 8mm camcorder Model PV-C840E mentioned in this

column in the October issue (page 902). The suggested price is £899.

## IN BRIEF

Finlux has developed an experimental 12in. flat monochrome TV display screen using electroluminescence as the light source. . . Philips has introduced a programmable universal remote control unit, Model RC775, at £70. It has an LCD screen and can memorise up to 370 com-

mands applicable to up to ten appliances. . . Maplin has available a high-gain amplifier intended mainly for use when two TV sets or radios or a combination of these is used with a common aerial downlead. Model YP42V has a bandwidth of 40-860MHz, a typical gain of 15dB and is available at £17.95. Operation is from the mains. Other Maplin amplifier products include a battery-powered unit and units to drive up to three or four sets. . . Oracle has started its own soap opera called Park Avenue. It's updated at 1700 each day and occupies ten pages.

# IBC '88

*Geoff Lewis, B.A., M.Sc.*

This was without doubt the largest and best-supported IBC to date, with large increases in the number of visitors to all aspects of the event. Even the typical IBC weather had an all time high: the tail end of hurricane Gilbert swept in soon after the opening, to provide some problems for the dish farm on the esplanade. It also ensured that visitors moved between the various venues in double quick time.

IBCs are intended to provide a forum for the exchange of the latest technological ideas and to make it possible to look at new practices and developments that affect the broadcast industry in general. This is done by the presentation of papers at the technical sessions and through the hardware displays in the exhibition. In one particular respect IBC '88 was again very thought provoking — the question of new TV standards was very much to the fore.

## General View

From the advance list of papers it seemed that 1988 was to be the year of high-definition TV (HDTV). This was true, up to a point. If you step back a couple of years, you might then have supposed that by now the question of standards would have been settled. Not so! One began to wonder which of the 57 varieties was going to surface next. While Europeans have been trying to resolve the MAC-D/D2 problem, yet further MAC possibilities have been presented. Similarly in Japan variants on the NHK Muse system have been spawned, while reports from the USA confirmed that a lot of development work is going into HD-NTSC.

Slightly more than half the technical papers related to HDTV or satellite TV feeds to cable systems, and it might be pertinent to ask where this leaves terrestrial broadcasting systems? At present in the UK we have four channels of pretty good quality, and a fifth is on its way. Viewers have VCRs to enable programmes to be time-shifted and give access to a wide range of prerecorded material. The system is well understood. Will HDTV and satellite systems really give us a much wider viewing experience? And will they be economically viable?

It may be recalled that following the HDTV '87 colloquium in Ottawa last October there were to be public demonstrations of HDTV in its various forms, enabling comparisons to be made with high-quality NTSC images. Some 7,000 people took part in the survey, and the results are just becoming available. Whilst nearly everyone preferred HDTV, support fell when cost considerations were taken into account. Provided the extra cost of a top-of-

the-range receiver was about \$300-\$400, there was considerable support for a change to HDTV. But when a more realistic figure of \$1,500 per receiver was suggested interest waned considerably. It seems that there is considerable consumer demand provided the improvement in video and audio quality is accompanied by good quality programming and that the extra cost is reasonable.

IBC '88 brought out the rapid expansion in the application of digital techniques throughout broadcasting in general. Many systems are now computer or micro-processor controlled. Many electronic graphics and digital effects systems are based on the familiar IBM or look-alike personal computers. Digital effects machines are certainly becoming an important tool for the programme maker.

## Satellite TV

The technical sessions provided information on developments for the Astra and BSB satellites, and some of the associated hardware was on display. The first Astra transmissions will use PAL, though MAC-D2 may well come into use as the number of channels increases. BSB is to use MAC-D from the start. It's a good job that dual-standard chip sets are likely to be available fairly soon to resolve at least one standards problem. BSB's diamond-shaped Squarial was to be seen, but few details of its performance were available. A gain of 12dBi was suggested. This compares reasonably well with the gain of 28dBi quoted for the BBC's steerable flat-plate aerial which has about ten times the surface area. If the Squarial has a beamwidth of 4-6° however, as is commonly expected, adjacent satellite interference could be a problem. Some brief details of the Eurocypher system to be used by BSB were made available. It uses the US G.I.-Videocypher system, which is fast becoming an industry standard, with an additional facility that allows the encrypting algorithm to be changed at will.

## HDTV Systems

The Japanese NHK/Muse system was well presented in several displays. A production facility was shown in the Sports Hall of Sussex University, complete with a video effects and graphics machine. Further displays of the Electronic Cinema and Videoconferencing were available and were well patronised. From some of the comments overheard from the American contingent it seems that many in North America are glad that the Europeans didn't accept Muse as a world standard at the CCIR Dubrovnik meeting in May 1986. The delay has given them time for thought and consideration of the possibilities of their own evolutionary approach to HDTV, i.e. systems that are compatible with current NTSC broadcasting. Possibly as a result of this delay Muse-E and Muse-T now have three further relatives. There are Muse-6 and Muse-9 which require one and one and a half 6MHz

channels respectively, and Narrow-Muse. But the standards conversion is at present costly, as the 1,125/525 lines and 60/59-94 fields/second standards have no convenient ratios.

As reported after HDTV '87 in Ottawa, the search for an NTSC-compatible HDTV system continues. Of the five or six well-known centres that are carrying out research into this, probably the front-runner is the David Sarnoff Research Laboratories (ex-RCA) which has come up with two proposals, level-1 using a single 6MHz channel with enhanced definition and level-2 using two channels that provide NTSC-compatible HDTV.

The MAC family is not without a new offshoot, MAC-T, which has been proposed for electronic news gathering links. The video components would be processed in the standard MAC fashion, with conventional sync pulses and a colour burst instead of the digital sync bits. This has been devised to provide studio-quality images from portable equipment, to allow MAC-type scrambling and controlled access to be used, plus sound in syncs.

The EUREKA-95 MAC-HD display in a separately constructed seafront pavillion showed what has been achieved by European cooperation in just two years. The display covered the studio, transmission and the MAC-HD concept including MAC-D and MAC-D2. Receivers ranged from domestic sets with inputs via a Scart/Peritel Euroconnector to wide-screen equipment using either front or rear projection. The quality of the displayed images was of a very high standard. The comparison with PAL pictures produced comments to the effect that Alan Sugar should view the stand then donate a million pounds to the charity of his choice.

Fig. 1 shows the general arrangement of this display. The signal originating equipment, all to the MAC-HD standard, consisted of a studio plus two outside broadcast (OB) vehicles. The first OB vehicle was equipped with a camera and a VTR while the second one was equipped with suitable VTRs, audio recorders, monitors and mixer desks, acting as a control centre whose output was fed to a MAC-HD encoder. This output was further encoded into both MAC-D and MAC-D2 signals which were sent over various transmission links including a simulated satellite TV path, 10km of 140Mb/sec optical fibre and a microwave distribution link. The received signals were then decoded and displayed on suitable receivers — as previously outlined. In addition LaserVision video disc players and VCRs provided outputs of prerecorded material to complete the domestic scene.

Compatible HDTV images are produced in the studio, with 1,250 lines per frame. This is reduced to 625 lines for the MAC transmission, to provide an input for a standard MAC receiver. The line reduction is done in such a way that an HD receiver can reconstruct the missing lines

using a digital assistance signal encoded into the MAC data structure.

## Microwave TV

A particularly interesting distribution system was shown in operation and described in a paper entitled "M<sup>3</sup>VDS — the cheapest, quickest and least obtrusive means of providing multichannel domestic TV?" M<sup>3</sup> means millimetre-wave, multichannel, multipoint, the frequency band being 29GHz. While it was shown that such a system could easily support MAC-HD signals or up to thirty standard TV channels, the title must have been chosen with tongue in cheek. The GaAs semiconductor technology required to provide suitable receiver LNBs is about two years away, while the cost of the head-end transmitters is unknown and would certainly be greater than for the previously proposed 2.5GHz systems. So much for the "cheapest and quickest" bits. The 15cm diameter dish and LNB assembly was certainly unobtrusive, and might provide a range of 2-9km. There's still a strong case to be argued with the Department of Trade and Industry to try to get it off the fence and provide a frequency allocation for such services in the 2.5GHz band. At least we would then have the cost and availability benefits of the research that has already been done.

## All-electronic Video Recorder

The most intriguing device to be described and displayed was without doubt a video recorder with no moving parts. This has been developed by Questech Ltd., using digital techniques with 512 dynamic random access memories (DRAMs) for storage. It's capable of recording 78 seconds of video with variable speed playback without loss of quality. Whilst this is very short by present standards the recorder is nevertheless useful for action replay of sporting events. A unique feature is that the device has several output ports that allow a single frame and the events that led up to it to be displayed simultaneously. By 1989/90 it's anticipated that 4Mbit DRAMs will be available, enabling the recording time to be extended to more than five minutes. This would make the recorder a valuable tool for the producer of commercials, etc.

## In Conclusion

From conversations with engineers on the stands of the UK broadcasting organisations I detected a degree of caution and concern regarding the future of British TV. Such is the impact of the government's ideas about deregulation of the industry. The effects that the proposals contained in the government's White Paper might have on research and development in the UK, which has always been in the forefront of advances in broadcasting, were being pondered. An interesting comment from one old-hand suggested that governments periodically dig at the roots of broadcasting just to see if they are still alive. This is acceptable — provided the roots aren't disturbed so much that the plant is killed off.

The next meeting of the CCIR, to discuss the question of a single world standard for HDTV, is scheduled for 1990. I wonder what the odds are that there will be a proposal to adopt three standards, Muse, MAC-HD and HD-NTSC, with a further proposal to meet again to decide on a single conversion standard in 1992 or subsequently?

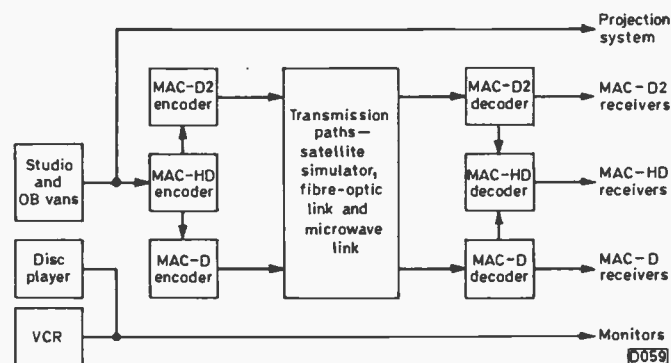


Fig. 1: The EUREKA-95 display at IBC '88.

# Practical Guide to Satellite TV

Roger Bunney

In the March/May 1988 issues I described a simple, low-cost satellite TVRO system. The aim was to achieve efficient reception at minimal cost, and in that end a dish with patio mount was used. When I bought that package of equipment I knew very little about satellite TV reception. Since then I've learnt a lot, in particular from hands-on experience of playing with and modifying the system. This has enabled me to assess the merits and shortcomings of basic equipment.

With the ever increasing interest in satellite TV reception a wide range of equipment has become available at reasonable prices. My first package, which included everything, cost just £302 plus VAT. This included a 90cm dish with patio mount for reception from a single satellite.

## Dishes

The dishes available on the domestic UK market fall into two categories, prime-focus and offset types. As the name suggests, the prime-focus type focuses the incoming signal at a point in front of the dish. This is where you mount the feed assembly and head electronics, normally by means of three or four support arms that provide rigidity and accurate alignment. The offset type of dish focuses the incoming signal at a point to one side of the dish. It's somewhat more efficient since the feed assembly, the head electronics and their supports don't obscure the incoming signal. Prime-focus dishes are usually spun or pressed to shape and are available in standard sizes ranging from 60cm to 3m. The usual sizes used in domestic installations for reception of low-power satellites, i.e. not Astra, are 90cm and 1.2m, though the sizes continue upwards through 1.5m, 1.8m, 2m, 2.5m and 3m. A 60cm dish is suitable for Astra's signals. Clearly the larger sizes will tend to dominate the location, hence the popularity of 90cm and 1.2m dishes. Provided you don't live in a conservation area a 90cm dish can be installed in a garden or on a house without the need for planning permission. The larger sizes require such permission in theory, but if the dish is in a very large garden and is not visible from outside your boundary who's to know? Offset dishes are usually formed in fibre-glass.

## Mounts

The dish requires support. It can be fixed to a patio mount aligned for reception from a single satellite or attached to a tracking mount that gives reception from

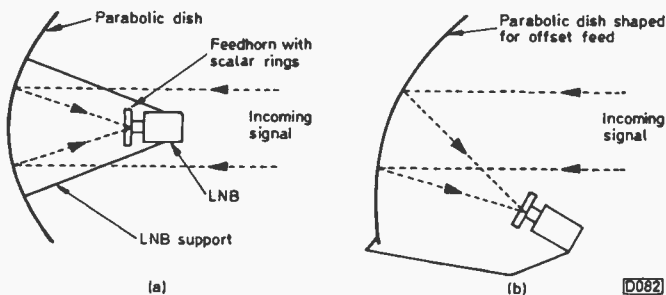


Fig. 1: Prime-focus (a) and offset (b) dishes.

several satellites. The patio system supports the dish rim via a rear prop arm that's adjustable for elevation. At its lower end the rear prop arm is welded to a steel hoop which is normally bolted down to the patio, flat roof or elsewhere. Once the system has been aligned for reception from the desired satellite the hoop is fixed (azimuth alignment) and the elevation adjustment is limited.

The satellites that transmit TV are in geosynchronous orbit above the equator, i.e. they are stationary relative to any point on the Earth's surface. To view these satellites in the UK we need to look to the south east/south/south west. If the dish is supported by a polar mount it will, once correctly set up, provide correct tracking of the equatorial arc. This is the recommended system.

## Polar Mount Alignment

Unless you have experience, setting up a polar mount can be difficult. It's a task that must be done carefully. Normally the dish/mount supplier will provide alignment details. Two adjustments are required in the vertical plane. Elevation has already been mentioned. In addition, declination offset has to be taken into account. This is usually measured between the back of the dish (on a flat spot) and a section of the mount such as the axis bar. In the southern UK the declination angle is 7.3°. The declination adjustment lowers the dish sight on to the satellite arc. Elevation is adjusted to the site latitude.

Thus the polar axis angle (local latitude) is first set, followed by the declination offset. Appropriate screw/bolt adjustments are provided at the rear of the dish. The dish assembly on its stand is then aligned on a north/south line, so that the axis of the polar mount is correct. For this adjustment, refer to a flat plane on the dish and use this for sighting. Once as nearly correct as possible N/S alignment has been achieved an additional offset angle is added. This is for magnetic declination and adds a further 7° adjustment to the west. Most dish stands have appropriate locking bolts and swivel action for this. All this sounds rather complicated!

## Preferred Method

My own method is to set the declination offset (polar axis) using a made-up aluminium angle. The dish is then set on an approximate N/S line and the magnetic offset is added. The Intelsat bird at 1°W is used as a signal source. After setting the dish to the approximately correct angle for 1°W the signals will soon be found. The dish is then swung between 27°W and 13°E where other satellites provide signals. With these three satellites used to provide reference signals I find that only azimuth correction is required. This is done simply via the swivel system, which locks to the stand base and is usually a large bolt. By checking the alignment at 27°W and 13°E — gently pushing or pulling the lower rim of the dish and noting the rise/fall of the signals, making adjustment as necessary — you can gradually set the tracking arc of the dish mounting so that it coincides with the equatorial arc, thus obtaining optimum signals. This is simpler than it sounds, though



effort is needed. Once you've got the tracking right efficient reception will be attained.

### Head End

The feed tube/horn which is connected to the LNB (low-noise block down-converter) is fitted at the focal point of the dish. The tube conveys the signal at the focal point to the LNB's pickup probe. It's often fitted with a scalar ring assembly which is used for fine tuning, maximising pickup of the wanted signal while minimising pickup of unwanted signals/noise from the sides. The ring assembly peaks quite positively, giving a further 0.5dB or so of gain.

The signals in the 10.9-11.7GHz band used by the low-power satellites and the medium-power Astra satellite are plane polarised, i.e. they are either vertically or horizontally polarised. To change from reception of a vertically polarised to a horizontally polarised signal the LNB can be rotated through 90°, thus rotating the pickup probe, or a polarotor can be fitted. The standard polarotor has a movable metal pickup probe within a waveguide feed tube, driven by a small motor. This is an effective way of changing the reception polarisation but introduces an insertion loss of around 2-3dB. A more recent device is the ferrite-based polarotor, e.g. the IRTE Paris. This has no moving parts and contributes an insertion loss of just 0.2-0.3dB. It costs about twice as much as a traditional mechanical polarotor however. The polarotor fits between the feed tube and the LNB.

LNBs are available at a wide variety of prices depending mainly on the noise figure. Thus an LNB with a noise figure of 2dB, typically with a gallium arsenide f.e.t. front end, costs in the region of £65 trade while an LNB with a noise figure of 1.3dB, using hemt devices, will cost perhaps £140 trade. Very recently an LNB with a noise figure of 0.6dB has been introduced — the catalogue says price on application! The gain provided by a domestic type Ku-band LNB is around 50-60dB.

Apart from remote switching for vertical or horizontal polarisation there are generally no controls for the head electronics either outdoors or indoors. Associated with the polarisation switching there may be an indoor skew control to give variable control.

### Feeder

The LNB provides a wideband output of 950-1,750MHz via either a standard US domestic F connector socket or a

**Table 1: Typical dish gain at 12GHz**

Diameter	60 per cent efficiency	70 per cent efficiency	80 per cent efficiency
0.5m	33.75dB	34.41dB	34.99dB
1m	39.77dB	40.40dB	41.02dB
1.5m	42.91dB	43.29dB	44.54dB
2m	45.79dB	46.46dB	47.04dB

Prime-focus dishes of good quality have efficiencies up to 70 per cent. The efficiency of offset parabolic dishes can exceed 80 per cent.

Beamwidths (at the -3dB points) of prime-focus dishes at 12GHz are: 0.5m 3.43°; 1m 1.72°; 1.5m 1.14°; 2m 0.86°.

We are indebted to the Echosphere Corporation for the above information.

professional N socket — the F connector is more usual. It's possible to connect low-loss coaxial cable such as RF125 to an F connector by carefully soldering the screen braid to the outside ring of an F plug with the inner conductor serving as the connection to the LNB's signal path. RF125 has the same loss figure as UR67 but is somewhat cheaper — and is vastly cheaper than most of the "correct" coaxial cable sold for this purpose. Since my own cable run is only 60ft the loss can be tolerated — inexpensive line amplifiers with a gain of typically 10dB are available to overcome losses and maintain optimum noise performance.

### Receivers

The receiver/tuner market is vast. You can pay several hundred pounds for the best all-singing, all-dancing remote-control receivers. I'm still using a basic knob and switches receiver: the tuning is by means of a large knob calibrated 1-24! I've added variable bandwidth switching via an outboard unit connected to an i.f. loop with access at the rear of the receiver.

### In Conclusion

The dish I now use tracks accurately using the cheapest Drake controller and actuator arm. It was collected from a nearby company (Metspin) where you can actually see the things being made. Perhaps I was fortunate: Metspin has manufactured dishes for Marconi and for military use for some years and the domestic market represents a natural spinoff — many of the tight government specifications are retained (there are not many domestic spun dishes that have a minimum 2mm thickness).

In closing this short guide to practical satellite TV reception I'd like to mention several companies that have provided help. North East Satellite Systems provided a great deal of help but now supply only professional users. Micro-X has a vast range of equipment and supplies have been very prompt. Alston-Barry provided the Drake equipment: they were similarly prompt in supplying equipment and in sorting out a small problem. I would recommend the *Echosphere Dealer Handbook* which covers the theory and provides practical guidance on installation, with lots of illustrations. I got my copy from North East Satellite Systems: it's expensive but perhaps the best. For what's in the sky the *World Satellite Almanac 1988* is excellent but costs £30.

One thing I've not mentioned so far is flat aerials. Although much work is being done in this field most of those shown so far have been dummies. The main problem appears to be that of achieving quantity production at a competitive price.

### Addresses

Addresses of the firms mentioned in this article are as follows:

Alston-Barry International, Units 4/5, Winborn Building, Convent Drive, Waterbeach, Cambridge CB5 9PB (trade only).

Metspin Ltd., 94b New Brighton Road, Emsworth, Hants PO10 7QS.

Micro-X, Unit 2, Drury Way Industrial Estate, Lacton Close, Neasden, London NW10 0TG (trade only).

North East Satellite Systems, Cropton, Pickering, North Yorkshire YO18 8HL.

# Servicing the Ferguson TX10 Chassis

K. Rutherford

The Ferguson TX10 was the first large-screen chassis in the TX series. Some radical ideas were incorporated in its design, mainly in deriving the e.h.t. from the chopper transformer but also in the design of the chopper circuit itself. Mounting the RGB output stages on the c.r.t. base panel is nowadays commonplace, but the TX10 was amongst the first to have them there.

Helped by its 65W power consumption, which keeps the temperature inside the cabinet at a very reasonable level, the TX10 is an inherently reliable chassis. The picture quality is such that the chassis has been approved for monitor use in broadcasting studios, though not for quality assessment – it has found use as a monitor by outside broadcast commentators, and was to be seen in numbers serving guests at the wedding of The Prince and Princess of Wales. Its reasonable pedigree would suggest long and dedicated service, which is certainly true of this chassis. Commonly-found faults are very few: more often the faults encountered tend to be obscure and baffling. After power supply faults, remote-control system troubles are the next most common ones.

## The Power Supply

The TX10 has a synchronous chopper power supply that converts the 360V from the mains bridge rectifier to e.h.t. at 25kV (the focus voltage is derived from this), 205V for the RGB output stages, 26V for the field timebase chip, 22V for the audio output stage(s) and an input to the 12V regulator which supplies the low-power stages of the receiver, the supply for the c.r.t.'s heaters, and the 150V supply for the line output stage. The latter is the one that's monitored by the TDA2582 chopper control chip.

In the Mk III version of the chassis, which has the PC1560 main panel with plastic mounting frame as distinct from the earlier versions with a metal frame, R813 is a troublesome component. It forms part of the potential divider that monitors the 150V line, supplying an error voltage to pin 8 of the TDA2582 chip. In every case of field roll and intermittent tripping, check the 150V rail. If the voltage is high, suspect R813. It's a critical component which should be replaced with the recommended type from Ferguson or one of the official stockists. A convenient pin at which to monitor the 150V rail is on the signals panel, between the tuner and the large plug at the left-hand end of the board. A reading of 75V at the 150V test pin generally indicates that R813' has gone open-circuit or at least very high in value.

I find an analogue meter to be best for measuring voltages in TV receivers because it's relatively unaffected by the large quantities of line-frequency garbage sometimes present. One digital meter I tried was accurate to the nth degree but gave a reading that varied considerably depending on the proximity of the meter to the chassis. This applied not just with the TX10 but also with other manufacturer's models. You can't beat the good old industry standard Avo 8, but whatever you use should have a sensitivity of 20k $\Omega$ /V or better.

Power supply tripping is fairly common with the TX10. It can be produced by a number of causes. The trip inputs

sense excessive chopper transistor current, excessive beam current and excessive back-e.m.f. voltage. If the receiver trips at switch-on the cause is almost certainly excess chopper transistor current. Check the various supply rails for a short-circuit, using the ohms range of your meter. If the trip occurs after a very brief delay you can add excessive flyback voltage to the list of possibilities.

Reduce the setting of the "set-h.t." potentiometer RV801 in an attempt to stop the tripping. If the receiver operates but the 150V rail is low, check the capacitors in the chopper transistor's emitter circuit – C711 and C712. Should the tripping occur after the c.r.t. has warmed up, obvious things to check are the c.r.t. supplies and the beam limiting system. In my experience however the main cause of tripping is the focus control assembly. An improved type is used in later models. This is distinguishable by its tall thin shape in contrast with the somewhat squat, rectangular shape of the earlier type. The new control requires adaptation to fit the chassis – a kit is normally supplied with the replacement unit.

Other causes of tripping can include a faulty insulator on the line output transistor TR831, i.e. a puncture caused by a flashover or minute particles of metal or even grit. The connection to the c.r.t. Aquadag is also important. Check it right through to the chassis. Short-circuit turns in the line output transformer can result in tripping. Older models can exhibit a tendency to trip randomly, particularly after fitting a replacement c.r.t. In this event check whether R706 is fitted (between the junction of T703/D727/D733 and chassis) and its value – it needs to be 22k $\Omega$ .

Failure of the earlier focus control was the result of its insulation breaking down, allowing the focus voltage to flash over to the chassis metalwork – or your hand when you attempt to adjust it! Focus control arcing can also cause spurious channel changing etc., see later.

If the power supply doesn't come on, check that 22V is present at the cathodes of D721 and D722, check for 11.5V at the emitter of the 12V regulator transistor TR801 and for 6.2V at the cathode of zener diode D801. If pin 5 of IC801 is at 5.5V the receiver has fast tripped and something is seriously wrong in the set, e.g. the line output transistor is short-circuit or one of the rectifier diodes connected to the secondary windings on the chopper transformer is dud. Take care when attempting to measure IC801's pin voltages – a mere slip of the probe can cause a lot of extra work! Pins 6 and 8 are particularly sensitive. The power supply will trip when a meter probe touches pin 6. When pin 8 is touched with the probe the set may not trip but hand capacitance to the meter probe introduces hum into the power supply. Hum is deliberately introduced via R819 (2.2M $\Omega$ ) to cancel ripple on the 360V rectified mains supply. A faulty 12V regulator circuit (TR801, D802) can be the cause of the set switching off after a few seconds.

An oscilloscope is a great help when fault-finding in this area, but when looking at the drive waveform at the base of TR701 remember that you are on the live side of the mains isolation barrier, so the earth lead must not be connected to the isolated side of the chassis. Make sure that your scope is not earthed, and if you have to delve

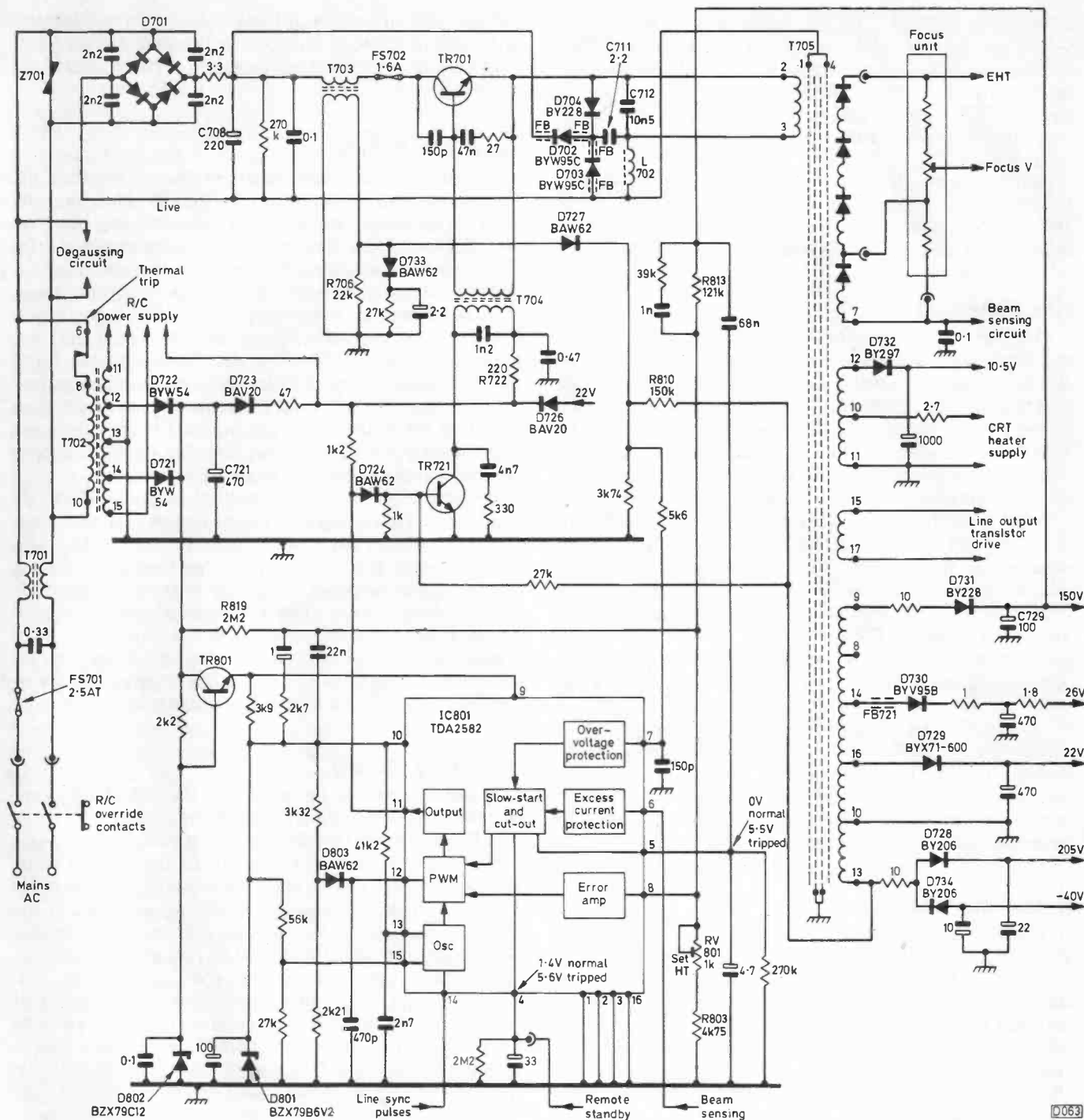


Fig. 1: The chopper power supply circuit used in the Ferguson TX10 chassis. The chopper transistor TR701 is type BU208B or S518T with panels PC1500 and PC1550 (due to shortages other types were used) and type BU508A with panel PC1560. On all panels the driver transistor TR721 is type BC639 and the 12V regulator transistor TR801 is type BC547. Surplus energy in the chopper's output circuit is returned to the mains bridge rectifier's reservoir capacitor C708 via D702, increasing the circuit efficiency. T703 senses the chopper current. The e.h.t. is monitored at the anode of D728, via R810. Beam current is monitored at the earthy end of the chopper transformer's diode split winding. D701 type SKB2/08/L5A or 4 × BY133GP.

into the non-isolated part of the chassis use an isolating transformer. Isolated chassis are all very well, but they can give you a false sense of security – constant care must be exercised. If your workshop's bench mains supply is not isolated, get it done!

The line-frequency output from IC801 to the chopper driver transistor TR721 is at pin 11. If a trip condition has removed the drive from IC801 pin 11 will go low, holding TR721 cut off. If pin 11 is high and the driver transistor is on, with R722 getting hot, IC801 has passed away.

Typical d.c. resistance readings for the four main supply rails derived from the chopper transformer, taken with the

Avo meter's negative (red) lead connected to chassis, are as follows: 205V rail 30kΩ, 150V rail 30kΩ, 26V rail 4.5kΩ, 22V rail 17kΩ.

The most frequent problem on the primary side of the chopper transformer is instant destruction of the chopper transistor TR701. D704 can be the cause of this, as can C711 being open-circuit or C712 being dry-jointed. On the subject of dry-joints, it's wise to resolder the pins of the chopper transformer T705 whenever a TX10 enters the workshop – it could save you a callback. Don't forget that one of the pins is hidden beneath the chassis brace. Dry-joints on the primary winding pins 2 and 3 can cause

intermittent failure of TR701. Dry-joints on the heater supply pins can give intermittent loss of picture. Tripping and intermittent spurious control action, such as switching to standby, are other effects produced by dry-joints around T705. Arcs around ferrite bead FB721 can cause very intermittent field roll and tripping on/off – resolder it clear of the PCB.

Before leaving the power supply, problems with the thermistor in the degaussing circuit can cause fuse blowing and impurity. This occurs with the round, white thermistor. Use the black type with rounded-off corners.

### Line Deflection

The line output transistor TR831 is a BU208B. Protection diode D831 in its base circuit has given trouble. It has also been indirectly responsible for a loud line whistle – to stop this, glue the ferrite beads on its leads firmly in place. In the PC1560 series version the line output transistor is TR821, type BU508A, while its protection diode is D743 – this can also produce the line whistle problem, so have a go with glue here as well.

Apart from the line output transistor and its protection diode the only troublesome component in the line output stage is the transformer T721. Symptoms of its failure include tripping, a non-linear scan, line tearing and screeching from the scan coils, and instant destruction of TR831. Sometimes T721 burns out because D831 has gone leaky – check it by substitution. When D831 goes open-circuit severe line ringing will be noticed, the picture width will decrease and eventually the receiver will go into the trip mode. Don't run the set for longer than necessary in the condition before the trip operates as this will damage TR831. The remainder of the circuit, including the first anode supply and the EW raster correction system, has proved to be reliable. Sometimes the width control RV851 changes value to give reduced width.

### Field Deflection

Troubles in the field deflection circuit have been few. In the earlier sets with PC1500 and PC1550 main panels a TDA1044 field timebase chip is used in conjunction with a two-transistor output stage. In cases of insufficient height and slow flyback, take a look at C781 (100 $\mu$ F) and TR771 (ZTX450K). Various stages in the decline of C781 will result in varying degrees of field foldover. With the PC1560 series panel a TDA3652 chip is used as field driver and output stage.

### The Sync Processor Chip

Three different types of sync processor/line timebase generator chip have been used, the TDA2576 (IC791) in earlier versions of the PC1500 panel, the TDA2576A (IC741) in later versions of the PC1500 panel and the PC1550 panel, and the TDA2578A (IC742) in the PC1560 panel. The TDA2576A has an improved sandcastle pulse generator plus 50/60Hz switching while the TDA2578A also incorporates the field generator. Occasionally a later type signals panel may be paired with a main panel that has a TDA2576 chip. This will give rise to flickering colour due to the value of R627, which should be 15k $\Omega$  with the TDA2576A and TDA2578A and 820 $\Omega$  with the TDA2576.

Some problems arose with the TDA2578A chip. To overcome line tearing with some VCRs, R756 was changed to 6.8k $\Omega$ . For bent verticals at high contrast

settings, add an underboard link between the earthy ends of C742 and C745. If line lock is disrupted at switch on, especially in cold weather, exchange C742 (220 $\mu$ F) and C745 (100- $\mu$ F).

### Tuner and IF Strip

To improve reliability many engineers replaced the Ferguson SC4 tuner with an ELC1043/05. Now that the latter is no longer available the situation has been reversed. It's obvious that the SC4 has been modified – far fewer fail than was the case a year or two ago. The r.f. amplifier stage appears to be the most vulnerable stage, and thunderstorms can wreak havoc. The tuner is followed by an eight-pin Plessey SL1430 or SL1432 i.f. preamplifier chip, IC50. This can be responsible for a peculiar fault: the signal fades into severe noise patterning. Where an SL1430 is used this must be replaced. If an SL1432 is fitted, try connecting a 220k $\Omega$  resistor from pin 1 to chassis before condemning the chip. Note that these two chips are not interchangeable.

The rest of the i.f. strip is centred around a TDA2540 chip, IC51. This is highly reliable, though lightning damage can include this device. Less reliable is the 12V regulator chip IC621. Lack-lustre performance, shifting grey scale and weak sound are the symptoms during this device's dying throes. The replacement should be well supplied with heatsink compound. As previously mentioned, picture fade out can be caused by a dry-joint on the chopper transformer's c.r.t. heater supply pins. We've had fade out followed after a few seconds by fade in.

### Checks by Muting

A trouble-shooting tip relating to the TDA3560 colour decoder chip IC601 requires the use of a small 1.5V torch cell. If you suspect that the cause of a picture disturbance is in the pre-RGB output stage areas, the internal RGB switches in IC601 can be operated by applying 1.5V at pin 5 of plug 18 on the rear edge of the signals panel. If the resultant blank raster is undisturbed (wind up the brightness a little) it's likely that the RGB output stages are o.k. This method does not kill the sync input to the sync processor chip, so the timebases remain synchronised. It can also be used to mute the sound i.f. (but not to disable the demodulator, the volume control or the audio output stage(s)) by applying 1.5V to point C (point W with the PC1551 and PC1561 signals panels) and also to mute the vision i.f. by applying 1.5V to point K. The ability to isolate trouble by using this simple switching technique can be a real time-saver.

### RGB Output Stages

The major source of trouble on the c.r.t. base panel has always been the tendency of the BF460 RGB output transistors TR654/5/6 to go short-circuit base-to-emitter. The effect of this on the receiver's performance is not immediately apparent, though it does cause a very slight shift in the grey-scale, the direction depending on which of the transistors has failed. It also causes vision buzz on sound by putting video on the 12V line. The long term effect however is that the RGB output stages' green LED biasing diode D657 will be slowly destroyed. This results in a rise in the voltage across D657, with a corresponding decrease in brightness until the tube is eventually cut off. Replacing D657 will restore the vision but not cure the fault. Measuring the current flowing through D657 will

produce a reading of 90mA instead of the correct 25-30mA. Finding which transistor of the three is faulty is a simple ohmmeter job. The normal voltage across D657 is 2.1V.

Failure of one of the driver transistors TR651/2/3 will flood the relevant gun, i.e. failure of TR651 will produce a blue flood etc.

### Sound Problems

Sound problems with the TX10 are very few. L531 (later L561) occasionally requires a tweak to stop slight intercarrier buzz and you get the odd rattling loudspeaker, but generally the audio section is trouble free.

### Remote Control

Problems with the remote control system, where fitted, can produce the occasional complaint that the normalised volume setting steadily rises. The answer to this is to change D101 to a silicon type – Ferguson's widely used PH425 is ideal. Spurious remote-control system operation is another problem that's given the writer more than a few headaches over the years. Sudden unwanted changes of volume, contrast, saturation, brightness or channel, or equally mysterious dropping into the standby mode, are symptoms of impulsive interference getting into the remote control processing circuitry and being interpreted as commands. Internal sparking in the receiver can do this – due to a defective focus unit for example, or imperfect Aquadag contact – but the interference can also come from the mains. Ferguson's answer to this is to add a link beneath board PC1515 from pin 12 of IC101 (SAA5012) to the earthy end of C106. This diminishes the amount of transient pickup in the earth tracks and prevents interference clocking itself into the SAA5012.

In receivers that use the PC1548 remote control receiver board striations can occur due to inadequate decoupling – change C915 to 10 $\mu$ F. The SAA5012's clock oscillator on panel PC1536 can sometimes fail to start – it often does so when the set has aged. The result is loss of text. Changing R1131 to 47k $\Omega$  will restore the vital signals. Another peculiar fault in some sets equipped with teletext is loss of sync due to poor contact at pin 3 of SK19A, as a result of which the looped through sync signal on the text panel is lost.

### Tuning Drift

Finally, tuning drift with eight-channel remote-control TX10s can sometimes be baffling, all channels but one showing the fault. The cause of this is a leaky diode that couples the voltage from the slider of a tuning potentiometer to the tuning line. It doesn't matter when the leaky diode is the one in use, but when another channel is selected the diode will affect the turning voltage, causing random drift as its reverse leakage current varies.

### The Tube

There must be many TX10s that have been put aside due to failing tubes and/or obscure faults. The 30AX tubes used in this chassis are expensive to replace but give an impressive performance when new, especially with teletext. Retubing a TX10 is a good proposition when the replacement tube is not too expensive and performs to the original standard – sadly very few of them do.

# next month in

# TELEVISION

## Extra Next Month – the HRS Astra Satellite TV Guide

Details of the Astra transmissions and equipment for reception.

(Inclusion of this guide depends on the successful launch of Astra).

### ● SERVICING CAMCORDERS

The camcorder, packing a lot of electronics and mechanical engineering into a small space, adds a new dimension to the problems of servicing consumer electronic equipment. New techniques are required, but provided these are understood and the correct equipment is available servicing can be done profitably. Start of a new series by Steve Beeching, T. Eng.

### ● AN INTRODUCTION TO j NOTATION

You cannot get far in electronics without having to carry out various calculations. When it comes to circuits using resistive and reactive components, the use of j notation greatly simplifies the calculations. A simple, clear introduction to this system, with the emphasis on its practical use.

### ● SERVICING THE SANYO 80P CHASSIS

The 80P colour TV chassis was used by Sanyo for some time in a variety of popular models. John Coombes provides a fault-finding guide for these sets.

### ● HEAD POSITION CHECKER

A simple strobe unit that can be used to check the position of video heads. The circuit uses the head switching pulse to trigger a timer chip used as a monostable. This in turn drives a yellow LED.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW:

TO.....  
(Name of Newsagent)

**Please reserve/deliver the February issue of TELEVISION (£1.50), on sale January 18th, and continue every month until further notice.**

NAME .....

ADDRESS .....

.....

.....

# At the Japan Electronics Show

George Cole

Japanese consumers were faced with a plethora of television sets and broadcast systems, not to mention other domestic electronics equipment, at this year's Electronics Show, held at Tokyo's Harumi fairground.

## HDTV

Many companies, including JVC, Sony, Hitachi, Panasonic, Mitsubishi, Sharp, Toshiba and NEC, held demonstrations of the Japanese 1,125-line/60-field HDTV system, now commonly referred to as Muse (multiple subnyquist encoding) after the technique used for bandwidth compression. Although Europe and America seem to have abandoned the idea of adopting Muse, the system is being heavily promoted in Japan where it's being sold under the banner "Hi-Vision", which certainly sounds more consumer-friendly!

I managed to take a look at the HDTV demonstrations provided by all the above companies and also one put on by the EIJA (Electronic Industries Association of Japan). My general impression is that Muse is very good under certain conditions but under others its defects are all too apparent. The first Muse demonstrations some time back used 30in. c.r.t.s: the pictures were sharp, detailed and clear, with the improvement over NTSC (and indeed PAL) clearly visible. This time companies also held "AV theatres" where Muse was shown on 120in. screens using back-projection systems. These were held in the dark, presumably to emulate a cinema atmosphere. The problem was that one couldn't avoid the comparison between Muse and 35mm film.

One of the biggest surprises was the huge variation in picture quality. Some companies, notably Sony, JVC and Sanyo, produced fairly impressive large-screen demonstrations. NEC's pictures were marred by noise, low contrast and poor colour however.

The large-screen demonstrations tended to suffer from three faults. First there was an increase in grain, which was clearly visible from a distance. Secondly colour shimmering was evident. With some material this was very distracting. The third problem occurred whenever a camera panned across a scene. In the Hitachi demonstration for example the camera followed a woman as she walked across a room. As the camera moved the woman went out of focus, and when she stopped there was a slight pause before the camera locked in focus. I managed to talk to several Japanese TV engineers about this focusing problem. They readily acknowledged that it was a Muse defect. Apparently the problem is worse with cameras that have a pickup tube, since tubes are more prone to image lag: the new-style CCD Muse cameras (see below) claim to improve if not cure this condition.

Japanese electronics and broadcasting companies are gearing up for Muse and have embarked on a number of Hi-Vision/Muse promotional activities, including a Hi-Vision week that started on November 25th (11/25, get it?!) The first full-scale Muse broadcasts from the BS3 DBS satellite are planned for 1990.

There is still some work to be done to develop l.s.i. chips for Muse signal processing. The current Muse decoders are larger than the 30in. receivers and, while wandering around the back of one Muse demonstration, I

came across a mass of electronics watched over by an army of technicians!

Most of the Muse pictures were sourced from one-inch VTRs, though there is now a standard for half-inch Muse VCRs. These recorders use helical scanning and employ newly developed video heads. The cassette dimensions are 205 × 121 × 25mm (slightly larger than for VHS), the tape being of the metal particle type. Playing time is an hour. The recording system uses analogue base-band f.m. for the video signal, with a luminance bandwidth of 20MHz and a chrominance bandwidth of 7MHz. The audio is PCM digital, with a 48kHz sampling frequency and 16-bit quantisation. Up to four audio channels can be recorded.

Sanyo displayed a Muse video disc player which plays 30cm discs made from plastics or glass. It measured 440 × 515 × 182mm and weighed 22kg. The disc's CLV playing time is an hour per side. Sanyo also showed a Muse/NTSC decoder which can be used to convert Muse into a standard NTSC signal. It was a massive 480 × 600 × 384mm, weighing 66kg! After much miniaturisation Sanyo expect to have such decoders for sale at around £45.

Companies are working on Muse still picture systems. JVC has developed one that stores HDTV pictures digitally on an AHD (audio high density) disc. Fuji uses a WORM (write once read many times) optical disc to hold 500 fields of Muse video images. Sanyo displayed its HDV1100 videograph at the show.

One of the problems with Muse cameras is their insensitivity at low light levels. NHK (the Japanese Broadcasting Corporation) has however developed a HARP  $\frac{2}{3}$ in. CCD imager that improves the sensitivity by a factor of ten. HARP? — high-gain, avalanche-rushing, amorphous photoconductor!

## EDTV and IDTV

Regular Muse transmissions may still be a couple of years away, but Japanese consumers can already buy TV sets that improve the quality of standard NTSC. These are for use with EDTV (extended definition TV), a broadcast system in which a high-frequency signal is multiplexed on to the standard luminance signal to give improved resolution. The chrominance bandwidth is also extended with EDTV. Unlike Muse, EDTV (called "Clear Vision") is compatible with standard NTSC equipment. Another system is the receiver-based IDTV (improved definition TV).

Both systems employ 3D filtering and sequential scanning to improve the vertical resolution and reduce cross-colour and dot interference, but I can't say that I was overly impressed with what I saw. The pictures looked cleaner, and there was a slight improvement in definition, but neither system was a great advance on standard NTSC.

## LCD Screens

At the other end of the market there were numerous pocket-sized TV sets using LCD screens. Many companies had two- and three-inch models. Toshiba showed four and 6.5in. screens. The smaller screens looked sharper.

Sharp showed its 14in. LCD panel (see Teletopics, October 1988) which pushes current LCD screen technology to the limit — and shows it.

Some companies, such as Sharp and Toshiba, have turned the concept of large, flat LCD screens on its head and produced LCD projectors. Sharp's 100in. LCD projection TV uses three 3in. LCD RGB panels as the picture source, four dichroic mirrors, three condenser lenses plus a mirror and a projection lens. The LCD panels are insulated against heat and light. They use cyclohexane high-purity liquid-crystal material and amorphous silicon thin-film transistors.

### Portable AV Equipment

LCD screens are also being used in portable video equipment, including Sony's GV-8 "Videowalkman" (see Teletopics August and October 1988). The Walkman has a smaller head drum than the standard 8mm type, 20mm instead of 40mm, with an extended tape wrap and faster drum speed (3,000 r.p.m. for PAL). Sony's Betamovie system with miniature drum used a single head with time compression to increase the scanning rate: the cost was loss of in-camera playback. The Walkman has two heads placed on the same side of the drum and dispenses with fast scanning to allow normal playback. Sony is also pushing 8mm software — over 400 titles are available in Japan. For Europe, Sony has reached licensing deals with Warner, CBS-Fox and CIC.

Casio showed a portable VHS "TVCR", Model VF3000, which has an LCD screen, a TV tuner and plays full-size VHS tapes. It sells for the equivalent of about £560 and weighs 2kg.

Panasonic's NV-1 Videowalkman uses Super VHS-C cassettes and has nine heads, a 3in. colour LCD TV, hi-fi sound, twin speeds, a TV/radio tuner and speaker. It sells for the equivalent of about £840 and weighs 1.5kg. The NV-1 is a very impressive machine, hampered only by its short playing time of just one hour in the LP mode. JVC and Matsushita are working on thinner S-VHS-C and VHS-C tape to increase the playing time to two hours in the LP mode.

### S-VHS

Second generation S-VHS machines were in evidence. JVC's HR-S10000, selling at the equivalent of around £1,340, features a number of improvements to the S-VHS system. These include a new Y/C processor chip, a colour response improvement circuit to reduce colour edging, a twin skew corrector circuit with separate wideband CCDs for the luminance and chrominance signals, a dynamic colour level control circuit, a new noise-reduction circuit, a linear phase aperture correction chip, a new tape guide-roller, a tape stabilising head drum, impedance rollers for smoother tape running and a newly-developed tape guide roller supported by a ball bearing for the supply reel. Hi-fi sound quality has been improved by a new head switching noise-reduction circuit, gold-plated connectors, a PCB exclusively for audio processing and new audio capacitors. The HR-S10000 also includes a new editing feature called VOS — video-on-sound recording. This allows hi-fi VCRs to record linear and hi-fi sound tracks independently of the video signal, which can be dubbed on top after the sound tracks have been recorded.

JVC also demonstrated a VHS editing deck, the RV-1000, which includes insert edit, assembly edit, audio dub and VOS for the equivalent of about £180.



The Panasonic NV-1 Videowalkman, with headband camera.

Panasonic's NV-M50 at around £930 is an S-VHS-C camcorder with hi-fi sound, nine heads, the VISS index system, a three-speed fast shutter,  $\times 6$  zoom and a stereo microphone.

### 8mm Video

Sony's Video 8 EVC-X10 at an equivalent price of around £1,473 has a C-mount exchange lens. The CCD-V88 at around £959 has a miniature transport system (one third the standard size) that enables Sony to produce a lightweight (0.9kg) camcorder with full features.

Fuji has announced the first high-grade 8mm tape. It uses super fine metal particles and the same coating as professional M11 tape. The cost is £7 for two hours and £3 for fifteen minutes.

Sony is rumoured to have available the first Super 8mm camcorders but instead opted to display Super hi-band and hi-band Beta equipment. These systems lie midway between the standard Super Beta with 270 lines resolution and ED Beta (extended definition) with 500 lines resolution. SHB Beta has a carrier deviation of 4.8-6MHz with a resolution of 300 lines. The HB resolution is 288 lines. Sony says that both systems are strictly for NTSC markets.

### Other Equipment and Systems

Sony also showed four own-made VHS recorders, all with hi-fi sound. Top of the range was Model SLV-7 at the equivalent of about £625 while for the equivalent of about £290 you could get the SLV-P3 video player.

Compact disc video (CDV) was widely represented, all the major companies (apart from JVC who stuck with its VHD system) showing players. There are no less than ten CDV players in the Sony range.

Satellite TV is being pushed in Japan, particularly the forthcoming Muse transmissions. In addition to set-top tuners many companies offered VCRs and TV sets with integrated satellite TV tuners. Sony, Hitachi and Panasonic also displayed flat-panel satellite TV aerials.

Still video cameras were in abundance. Prices showed great variation, ranging from £311 for Sony's MAVICA to £1,116 for Panasonic's AG-ES10. Picture quality was quite good, though still not as good as 35mm film.

The latest video craze in Japan is the videophone. Most units cost around £250 and produce a coarse black-and-white still picture, though Sharp had a model with colour pictures.

So it looks as though several new items will eventually be joining the TV sets, VCRs, camcorders and CD players on the service bench!

# VCR Clinic

*Reports from Eugene Trundle, Nick Beer, Philip Blundell, Eng. Tech., Chris Plaice, Ian Bowden, Alfred Damp and Joe Cieszynski*

## Panasonic NV-M5

We couldn't believe that this fault could happen! After the machine had been running for a while the pictures it recorded (displayed in the viewfinder) rolled sideways in a "loss of line lock" condition rarely seen nowadays. Some of the electronics in this machine must have been designed with genlock in mind since the CCD H drive chip has its own VCO, phase-locked to the camera's SSG output. This phase-locked loop was going out of sync — blowing warm air into the region of the CCD drive chip would cause loss of line lock while a blast of cold air would restore it. Normal operation at all times and temperatures was restored when the PLL trimmer on the image-sensor panel had been adjusted. This job requires much dismantling and — in theory anyway! — a set of board extension leads. E.T.

## Sanyo VHR1100

An intermittent fault on this machine took some time to trace and cure. The machine would sometimes thread up then immediately unthread again, with the head drum turning too slowly. Sometimes during play the drum and capstan would both slow down dramatically to give a screen full of noise and very slurred sound. Any attempt at diagnosis would restore normal operation. We finally found that the cause of the trouble was loss of the subcarrier reference feed at pin 42 of the servo jungle chip IC4001. The feed capacitor C1102 was going open-circuit intermittently. E.T.

## B and O VHS82-2

The complaint with this new stock machine was no E-E sound and distorted linear (longitudinal) sound playback. The loss of E-E sound was simply due to the fact that the record-level slider controls were set to minimum. Playback from the linear (lo-fi) sound track was weak and unstable, with a background whistle and hum. The problem lay in the audio head record/playback electronic switch, which was failing to earth the top of the head winding during playback. Under subpanel P550 (top of deck, adjacent to the audio head assembly) there are several surface-mounted components. The collector of T7003, which is amongst these, was not soldered to the print. E.T.

## Sony CCD-F330

The customer brought this machine back the following day, complaining that the autofocus didn't work. Sure enough it didn't — not pilot error as had been suspected. As it's a brand new model (replacing the CCD-V50) the manual hadn't arrived. Nevertheless the autofocus board (AF prefix) was soon found, the fault being traced to a dry-joint on the AF motor connection plug. The number of screening cans in camera heads seems to be increasing: to get to the AF board you have to remove the bottom one, under the lens, and remove the PCB inside to gain access to the screw that holds the bottom half of the can to the frame. With this removed you can get to the AF PCB.

The complaint with another of these machines was of no colour in the E-E and playback modes and, you've

guessed it, no autofocus. We dismantled the camera head and found two joints that had never been soldered on the large FPC: there was also a connector that had not been fitted correctly, half in and half out, between the camera and recorder sections. Having restored colour I delved into the AF PCB and found that the trouble here was a break in FPC135 as a result of which there was no AF on to the PCB. The break had occurred because the FPC had been bent at an adverse angle during assembly and when tightened up it had cracked. Meanwhile the manual had arrived, enabling us to order the part by number — getting it by description could have been tricky.

Less than a week later another of these machines came into the workshop. It was the shop's demonstration model and the complaint was of a ticking noise when the unit was on. It occurred whenever there was drum rotation, as a loom was mislocated and was catching on the bottom of the DD unit. A fair amount of dismantling was again required, just to fit a bit of Himelton which should have been done at the factory! While running the camera on test the picture disappeared. A sharp tap on the side brought it back. Another dry-joint, on the wide FPC. After reassembling it the camera wouldn't switch on due to a moulding fault in the camera standby switching assembly. N.B.

## Panasonic G Deck

Since my article on the G deck appeared in the September 1988 issue we've had several of the new range of G deck machines (Models NV-G40/G45/G48) with high back-tension. In each case the error has been corrected by replacing the back-tension arm spring with a new one from the Panasonic spares department. The new springs are a different colour, duller and not as silvery in appearance, and are minutely shorter. Only a small number of machines in this range seem to be affected. Note that the back-tension specification has been altered. Measure it with a tentelometer at the beginning of a three-hour cassette: the reading should be between 22.5-27.5g. This applies only to the G mechanism. N.B.

## Ferguson FV20

These new machines are very popular and have excellent reliability. The fault with this one was no sound. In fact there was just a buzz in the E-E and playback modes but when going through the scart socket into my monitor the sound was o.k. A new r.f. converter put matters right. N.B.

## Panasonic NV-M7

The drum would sometimes judder and stop while running and intermittently wouldn't start. The drives didn't disappear so it seemed that the DD unit itself was at fault. Fitting a replacement restored correct operation. N.B.

## Grundig VS180

The fault reported on one of these machines was "spots on play". The spots were confined to the centre of the



screen and gave the impression of a tape path fault. When the off-tape f.m. waveform was scoped however it showed that this was not the case. Adjusting the tracking had no effect of course, so I suspected a faulty drum motor. When the motor baseplate was removed the cause of the trouble could be seen — grease had built up on the brushes. When this was cleaned off the spots had gone.

A note in the March 1988 issue reported that leaky capacitors in positions C301 or C305 would result in the reel motors running all the time. In the case I had the capacitor was very slightly leaky and the reel motor rotated only when the on/off switch at the front of the machine was in the off position! **P.B.**

### **Philips VR6561/6362/6468**

Most Philips dealers will by now be dab hands at replacing the rack slider on the current models. It looks a daunting task, but is quite straightforward if you follow the guidelines in the manual. The only tips I would add are as follows. With the deck removed from the machine, use a 9V battery on the control motor to get the mechanism to the position for dismantling. And check that you've got it assembled correctly afterwards! When refitting the top plate I put the pinch roller metal crank into position first then fit the plate, finally using a wire hook to get the belt over the control motor pulley. **P.B.**

### **Hitachi VT8500**

Tape stops while playing is a common fault with these machines. Often it's because the ring magnet that operates the reel rotation sensor is loose or metal debris have stuck to the magnet causing it to jam. **P.B.**

### **Philips VR6561**

If it's powered up without a cassette this machine usually moves the tray in and then out again. With this one the tray moved in and after a few seconds the machine switched off. No, it wasn't a mechanical fault this time: the control motor drive chip IC7251 (L293b) was faulty. **P.B.**

### **Recent Ferguson VCRs**

Here are a few problems we've had with late-model Ferguson VCRs.

**Model FV11:** Intermittent playback picture — L15 faulty (off pin 13 of IC101). Poor or intermittent tracking — IC2 (VC2023A) faulty. Low gain on high channels — try repositioning the aerial lead that connects the tuner to the aerial splitter.

**Model FV12:** No functions — ICP1 open-circuit.

**Model FV14:** No E-E sound — ICP2 on the demodulator panel open-circuit.

**Model FV21:** Note that early machines have no cover over the mains fuse which is always live. **C.P.**

### **Ferguson 3V55/3V57**

When this machine was plugged into the mains the capstan motor would immediately start up and run for approximately one second. There was no clock display. The on/off LED went on and off correctly when the power button was pressed. If a tape was inserted it would be taken in and down by the carriage, but would then be sent straight out again. Also in the E-E mode all that

could be seen on the monitor was hum.

The loss of clock display was due to lack of a reset pulse for the clock/display chip IC202. If this was provided manually, by momentarily shorting across C207, the display would appear correctly. Then in the E-E mode a distorted, low-contrast picture with hum across it would be seen.

All these faults were caused by an open-circuit — not blown — fuse (F2) in the unregulated 18V power supply. When the fuse is open it disconnects one end of the transformer's centre-tapped secondary winding but the bridge rectifier still provides nearly the correct voltage from the other end. In fact with the fuse open-circuit the 18V supply is approximately 16V in standby and 13.5V in the on condition. **I.B.**

### **Sanyo VTC5600**

The capstan motor slowed. We found that there was no pulse input at pin 19 of the CX143 capstan servo chip Q413. This was in turn due to the CX186 drum servo chip Q401 being faulty. **A.D.**

### **Ferguson 3V29**

Uncontrollable and overloaded E-E video and no playback video were caused by a fault in the playback equalising filter EQ201. **A.D.**

### **Pye DV468/Philips VR6862**

This VCR would accept a tape then immediately eject it. The cause of the fault was traced to point 9B3 not being grounded by switch COD3. The switch itself was in order, the trouble being a broken lead at the deck terminal connection. **A.D.**

### **Sony SLC6**

The complaint with this machine was of intermittent noisy rewind — it made a sound like tape chewing. We found that the large fast-forward pulley (item 424) had moved sideways, twisting the fast-forward belt, because of wear in the fast-forward arm assembly. Replacing the arm assembly (item 421) cured the trouble. **A.D.**

### **Ferguson 3V36/JVC HRD225**

This machine functioned correctly apart from the fact that when unthreading the supply spool wasn't driven in order to pull in the tape as the loading arms retract. Now although this model has a reel idler to drive the spools it doesn't have a reel motor. Instead the idler is driven by a pulley which in turn is driven by a belt from the capstan. Whilst unthreading the capstan motor wasn't being driven and we found that in this mode the drive transistor Q206 was without base bias, though the 5.7V bias was present in the play and fast wind modes. A study of the circuit diagram showed that in play the capstan drive comes from the servo chip, in fast wind it comes from the CPU chip IC201 and during unthreading it's switched by the expander chip IC202 (pin 38). This pin was found to be permanently low, all the other ports relating to capstan motor operation being correct. So, having encountered a number of faulty expander chips in this model, I replaced the i.c. This made no difference! Further checks revealed that R272 (10k $\Omega$ ), a bias resistor in the drive transistor's base circuit, was open-circuit. **J.C.**

# ECONOMIC DEVICES PO BOX 15, WOLVERHAMPTON, WV2 4AZ

15808	3.30	SC1826	0.67	AN206	2.58	BC207	0.14	BDV548	2.16	BU205	1.15	HAI1395	7.43	MC1351P	2.95	SA55607	5.42	STR40	4.78	TBA940	1.87	TDA431	2.27
15859	3.20	SC1827	0.67	AN206	2.58	BC207	0.14	BDV548	2.16	BU205	1.15	HAI1395	7.43	MC1351P	2.95	SA55607	5.42	STR40	4.78	TBA940	1.87	TDA431	2.27
17052	5.61	SC1875	4.50	AN210	2.28	BC121L	0.10	BDX63A	1.95	BU207	1.67	HAI306	2.22	MC1357P	2.50	SA55705	2.61	STR43	8.16	TBA950	1.84	TDA440	3.25
17053	5.30	SC1893	4.02	AN211	3.25	BC214	0.10	BDY20	1.21	BU208	1.20	HAI3402	7.87	MC1358P	1.35	SA5580	2.25	STR45	4.95	TBA990	1.98	TDA450	4.75
17074	9.60	SC1906	0.98	AN214Q	4.00	BC225	0.80	BDY81	1.05	BU208.02	1.97	HAI3342	6.67	MC1401	2.40	SA56000	1.33	STR620D	5.25	TBA990L	1.98	TDA460-2	2.10
17089	3.45	SC1921	1.37	AN220	3.92	BC237	0.10	BF115	0.40	BU208A	1.12	HAI3365	4.02	MC14013	0.41	SA56020	2.97	TG20V	5.75	TCA2700	1.85	TDA460	6.88
17127	2.50	SC1922	1.30	AN226	5.72	BC238	0.10	BF117	0.86	BU208B	0.95	HAI3366WR	1.51	MC14014	0.51	SA56025	0.75	TG20V	5.75	TCA2700	1.85	TDA460	6.88
17176	2.50	SC1929	1.30	AN226P	2.25	BC239	0.10	BF119	0.86	BU209	0.98	HAI3369	1.51	MC14015	2.15	SA56070	2.96	TG20V	0.67	TCA2705G	1.85	TDA460	6.88
1N4001	0.04	SC1944	1.55	AN241	1.71	BC239B	0.25	BF121	0.25	BU226	2.45	HAI368R	2.45	MC14497	3.46	SA56110	2.21	TG307	2.11	TCA280A	2.39	TDA570	2.75
1N4002	0.06	SC1959	1.65	AN245	4.50	BC251A	0.31	BF123	0.25	BU226	2.00	HAI368	1.76	MC14510BAL	3.30	SBA750	1.61	TG644V	0.97	TCA280A	2.16	TDA7205	2.25
1N4003	0.06	SC1967	1.90	AN253	1.80	BC254	0.50	BF127	0.13	BU230A	2.20	HAI370	3.00	MC14511BCP	1.10	SC8420	1.95	TG645	1.20	TCA280A	2.24	TDA8190	2.75
1N4004	0.05	SC1953	1.93	AN260	3.85	BC200	0.35	BF137	0.29	BU406	1.49	HAI374	4.30	MC14528BCP	2.15	SC9540P	1.46	TG645	1.45	TCA280	2.24	TDA940	3.15
1N4005	0.05	SC1962	1.93	AN272	8.25	BC301	0.45	BF153	0.58	BU406G	1.79	HAI377	3.80	MC14529	1.15	SC9540P	1.46	TG645	1.45	TCA280	2.24	TDA940	3.15
1N4007	0.07	SC1983	2.21	AN301	2.00	BC303	0.53	BF154	0.25	BU407	0.72	HAI377	1.75	MC1512	19.50	SDA211/2	12.85	TG646	0.81	TCA280	2.24	TDA940	3.15
1N4148	0.03	SC2185	1.55	AN302	1.93	BC307A	0.80	BF158	0.18	BU426A	1.13	HAI389	2.39	MC781BC	2.18	SG613	10.75	TG646V	1.05	TCA280	2.24	TDA940	3.15
1N4448	0.05	SC2009	0.34	AN320	3.20	BC308A	0.11	BF159	0.18	BU500	1.45	HAI392	2.17	MC106-5	0.95	SG629	8.25	TG646V	1.28	TCA280	2.24	TDA940	3.15
1N5401	0.14	SC2029	2.31	AN315	1.29	BC309	0.17	BF169	0.31	BU508A	1.25	HAI394	1.95	MC82207	2.28	SG633	11.36	TG646V	1.40	TCA280	2.24	TDA940	3.15
1N5402	0.15	SC2028	2.11	AN316	3.50	BC317A	0.13	BF169	0.31	BU508	1.25	HAI394	1.95	MC82207	2.28	SG633	11.36	TG646V	1.40	TCA280	2.24	TDA940	3.15
1N5403	0.16	SC2063	0.89	AN318	4.41	BC327	0.15	BF173	0.15	BU513	0.48	HAI398	1.80	MC82206	0.26	SI125HD	18.35	TG646V	2.42	TCA280	2.24	TDA940	3.15
1N5404	0.15	SC2078	3.11	AN320	5.47	BC328	0.10	BF177	0.35	BU505	2.95	HAI406	1.30	ME102	0.28	SI163HD	20.50	TG646V	1.82	TCA280	2.24	TDA940	3.15
1N5408	0.35	SC2253	2.25	AN321	2.25	BC337	0.09	BF178	0.40	BU806	1.79	HAI452	0.85	ME801	0.34	SKE2F104	1.39	TG646V	1.98	TCA280	2.24	TDA940	3.15
1N814	0.04	SC2085-Q	1.65	AN327	5.85	BC338	0.10	BF179	0.36	BU807	0.80	HD4538	2.07	ME411	0.75	SKE2G304	0.85	TG646V	1.45	TCA280	2.24	TDA940	3.15
1S1555	0.31	SC2209	1.30	AN337	5.37	BC368	0.24	BF189	0.36	BU825A	1.95	HD302D-A2	2.95	ME4201	3.30	SKE2G304	0.85	TG646V	1.45	TCA280	2.24	TDA940	3.15
1S44	0.11	SC2314	2.17	AN340P	1.61	BC369	0.24	BF181	0.36	BU825A	1.95	HD302D-A2	2.95	ME4201	3.30	SKE2G304	0.85	TG646V	1.45	TCA280	2.24	TDA940	3.15
1S271	0.11	SC2156	1.98	AN355	5.96	BC441	0.44	BF182	0.34	BU834	1.00	HD302D-A2	2.95	ME4201	3.30	SKE2G304	0.85	TG646V	1.45	TCA280	2.24	TDA940	3.15
2M219A	0.33	SC2216	0.89	AN322	1.32	BC454	0.36	BF183	0.38	BU835	1.10	HD3080A05	14.09	ME4201	4.90	SKE4F210	1.24	TG646V	0.74	TG2F00HP	4.15	TP120	1.06
2M365	0.35	SC2233	1.80	AN370	3.95	BC460	0.42	BF184	0.43	BY126	0.13	HD480A05	19.59	ME4201	1.89	SKE4G202	0.96	TG646V	0.49	TD101B	2.31	TP121	0.54
2M366	0.99	SC2226	1.65	AN5111	3.43	BC461	0.35	BF185	0.39	BY127	0.10	HIS1010	0.89	ME4201	1.25	SKE4F310	1.60	TG646V	1.25	TD103GA	2.25	TP122	0.50
2M365	0.81	SC22278	1.89	AN5120N	4.50	BC462	0.45	BF186	0.14	BY133	0.12	HIS1002	0.59	ME4201	0.45	SI130T	3.14	TG646V	1.74	TD106GA	2.11	TP126	0.75
2M367	1.50	SC2214	2.17	AN5152	5.38	BC463	0.41	BF195	0.14	BY136	0.14	HIS1002	0.59	ME4201	0.45	SI130T	3.14	TG646V	1.74	TD106GA	2.11	TP126	0.75
2N3702	0.14	SC2235-K	12.85	AN520	4.40	BC478	0.22	BF196	0.17	BY176	0.52	HME6231	9.81	ML221	3.33	SL1437	0.80	TG646V	0.81	TD101AF	4.25	TP132	0.99
2N3703	0.18	SC2251	1.26	AN5610	5.50	BC479	0.41	BF197	0.18	BY179	1.08	HME6232	5.25	ML222B	3.01	SL414	3.69	TG646V	0.80	TD1011	0.95	TP137	1.50
2N3705	0.16	SC2252	1.32	AN5612	2.30	BC532	0.28	BF198	0.17	BY182	0.95	HME6251	5.25	ML227B	2.51	SL432A	3.44	TG646V	0.71	TD1012	1.28	TP139	0.84
2N3706	0.14	SC2570	2.80	AN5613	4.20	BC546	0.80	BF199	0.17	BY187	0.77	HMT102	4.85	ML228	3.77	SL432	3.44	TG646V	1.27	TD1011A	1.03	TP155	0.95
2N3707	0.16	SC2577	1.80	AN5630	3.95	BC547	0.10	BF240	0.10	BY210	0.37	HMT102	4.85	ML228	3.77	SL432	3.44	TG646V	1.27	TD1011A	1.03	TP155	0.95
2N3717	0.16	SC2579	1.80	AN5630	3.95	BC547	0.10	BF240	0.10	BY210	0.37	HMT102	4.85	ML228	3.77	SL432	3.44	TG646V	1.27	TD1011A	1.03	TP155	0.95
2N3717	0.16	SC2579	1.80	AN5630	3.95	BC547	0.10	BF240	0.10	BY210	0.37	HMT102	4.85	ML228	3.77	SL432	3.44	TG646V	1.27	TD1011A	1.03	TP155	0.95
2N3717	0.16	SC2579	1.80	AN5630	3.95	BC547	0.10	BF240	0.10	BY210	0.37	HMT102	4.85	ML228	3.77	SL432	3.44	TG646V	1.27	TD1011A	1.03	TP155	0.95
2N3717	0.16	SC2579	1.80	AN5630	3.95	BC547	0.10	BF240	0.10	BY210	0.37	HMT102	4.85	ML228	3.77	SL432	3.44	TG646V	1.27	TD1011A	1.03	TP155	0.95
2N3717	0.16	SC2579	1.80	AN5630	3.95	BC547	0.10	BF240	0.10	BY210	0.37	HMT102	4.85	ML228	3.77	SL432	3.44	TG646V	1.27	TD1011A	1.03	TP155	0.95
2N3717	0.16	SC2579	1.80	AN5630	3.95	BC547	0.10	BF240	0.10	BY210	0.37	HMT102	4.85	ML228	3.77	SL432	3.44	TG646V	1.27	TD1011A	1.03	TP155	0.95
2N3717	0.16	SC2579	1.80	AN5630	3.95	BC547	0.10	BF240	0.10	BY210	0.37	HMT102	4.85	ML228	3.77	SL432	3.44	TG646V	1.27	TD1011A	1.03	TP155	0.95
2N3717	0.16	SC2579	1.80	AN5630	3.95	BC547	0.10	BF240	0.10	BY210	0.37	HMT102	4.85	ML228	3.77	SL432	3.44	TG646V	1.27	TD1011A	1.03	TP155	0.95
2N3717	0.16	SC2579	1.80	AN5630	3.95	BC547	0.10	BF240	0.10	BY210	0.37	HMT102	4.85	ML228	3.77	SL432	3.44	TG646V	1.27	TD1011A	1.03	TP155	0.95
2N3717	0.16	SC2579	1.80	AN5630	3.95	BC547	0.10	BF240	0.10	BY210	0.37	HMT102	4.85	ML228	3.77	SL432	3.44	TG646V	1.27	TD1011A	1.03	TP155	0.95
2N3717	0.16	SC2579	1.80	AN5630	3.95	BC547	0.10	BF240	0.10	BY210	0.37	HMT102	4.85	ML228	3.77	SL432	3.44	TG646V	1.27	TD1011A	1.03	TP155	0.95
2N3717	0.16	SC2579	1.80	AN5630	3.95	BC547	0.10	BF240	0.10	BY210	0.37	HMT102	4.85	ML228	3.77	SL432	3.44	TG646V	1.27	TD1011A	1.03	TP155	0.95
2N3717	0.16	SC2579	1.80	AN5630	3.95	BC547	0.10	BF240	0.10	BY210	0.37	HMT102	4.85	ML228	3.77	SL432	3.44	TG646V	1.27	TD1011A	1.03	TP155	0.95
2N3717	0.16	SC2579	1.80	AN5630	3.95	BC547	0.10	BF240	0.10	BY210	0.37	HMT102	4.85	ML228	3.77	SL432	3.44	TG646V	1.27	TD1011A	1.03	TP155	0.95
2N3717	0.16	SC2579	1.80	AN5630	3.95	BC547	0.10	BF240	0.10	BY210	0.37	HMT102	4.85	ML228	3.77	SL432	3.44	TG646V	1.27	TD1011A	1.03	TP155	0.95
2N3717	0.16	SC2579	1.80	AN5630	3.95	BC547	0.10	BF240	0.10	BY210	0.37	HMT102	4.85	ML228	3.77	SL432	3.44	TG646V	1.27	TD1011A	1.03	TP155	0.95
2N3717	0.16	SC2579	1.80	AN5630	3.95	BC547	0.10	BF240	0.10	BY210	0.37	HMT102	4.85	ML228	3.77	SL432	3.44	TG646V	1.27	TD1011A	1.03	TP155	0.95
2N3717	0.16	SC2579	1.80	AN5630	3.95	BC547	0.10	BF240	0.10	BY210	0.37	HMT102	4.85	ML228	3.77	SL432	3.44	TG646V	1.27	TD1011A	1.03	TP155	



# TV Fault Finding

*Reports from Philip Blundell, Eng. Tech., Mick Dutton, B. Ross, Bob McClenning, John Coombes, J.S. Ruwala, J.L. Howard, Ray Vesey and David Botto, J. Olijnyk and Nick Beer*

## Philips G11 Chassis

Hum ripple on the 153V h.t. supply is a common fault on these sets. If it occurs after the BU208A line output transistor has gone short-circuit either the BD201 active filter transistor is leaky or one of the safety resistors in this circuit is open-circuit. Otherwise C4040 (40 $\mu$ F) or maybe C4029 (470 $\mu$ F) has dried up. Scope checks are helpful here: look for 12V of 100Hz ripple across C4029 and 1V of 100Hz ripple (with minimal line ripple) across C4040.

P.B.

## Grundig GSC100 Chassis

There was foldover at the bottom of the screen and cramping at the top. The +D supply to the field timebase module was slightly low at 17V instead of 18.5V. This is derived from the line output transformer, so I checked the e.h.t. by measuring the voltage at pin C of the transformer. This was also low and adjustment of the width control HS had no effect. The width control is mounted on the e.h.t. control module and checks here revealed that R2522 (2.2k $\Omega$ ) which is in series with the control had gone high in value.

P.B.

## Luxor SX9 Chassis

This set wouldn't give a real-time clock display on ITV. We scratched our heads over this one, as did Luxor's UK technical department. The Swedish head office knew the answer right away however. The customer had programmed an unused page number into the text memory. The number was used on each channel except ITV, which meant that the text decoder was searching for something that didn't exist. This was confusing to the clock.

M.D.

## Ferguson TX90 Chassis

The complaint with this set was tripping. We'd not previously had this problem with the TX90, but when we checked the power supply we found that the h.t. was high. A resistor that had gone high in value, causing poor regulation, was suspected. We were surprised to find that R225 (33k $\Omega$ ) and R222 (10k $\Omega$ ) were both open-circuit.

M.D.

## Philips 14TX3504 (TX3 Chassis)

This set suffered from field collapse. We found that the field driver transistor's load resistor R423 (33k $\Omega$ ), which is fed from the 110V rail, had gone open-circuit.

M.D.

## Philips 10CK1120

These sets are proving to be very reliable. We've sold about 120 of them and the only fault we've had was when T9629 (BUZ71) in the battery converter unit went short-circuit due to dry-joints around the line output stage.

M.D.

## ITT CVC1150 Chassis

There was a dark screen though the sound was o.k. Checks around the colour decoder chip showed that the

amplitude of the sandcastle pulse was low at 8V. When we lifted the field blanking at pin 18 of the TDA1940 chip a picture with flyback lines appeared. Clamping diode D402 (1N4148) had gone leaky.

M.D.

## Philips KT3 Chassis

The picture would occasionally oscillate in size. It was a very intermittent fault and quite a time was required to prove that the tripler was the cause.

M.D.

## Philips G8 Chassis (550 Series)

The fault report on this set was "loses brightness during the evening: a tap on the cabinet four inches from the left-hand side used to provide a cure but no longer does". The set was found to be working normally and thoughts turned to the 12V zener diode in the beam limiter circuit. Poor connections on plug J to the line scan unit were the cause of the trouble however.

B.R.

## Some Mitsubishi

**Mitsubishi Model CP1424B:** The trouble with this set was vertical ringing at the left-hand side of the screen. The cause was a poor earth connection to C905 (33 $\mu$ F) in the power supply section, close to the line driver.

**Mitsubishi CT186:** There was no luminance though the chroma was all right and the contrast control had some effect. The voltage at pins 16/17/18 of IC101 should be 11.8V but was found to be about 15V and varying. The cause of the fault was the 2SC2236 12V regulator transistor Q231.

**Mitsubishi CT2101:** For poor remote control operation check first that the infra-red window is of the modified, slightly larger type. Then if necessary replace the line filter coil L992 in the power input circuit with the modified type.

**Mitsubishi CT2227BM:** For no sound or raster first check the mains input circuitry. If this is in order check the l.t. supply at the remote control panel – the safety resistor R7A0 (1.2 $\Omega$ ) tends to go open-circuit.

**Mitsubishi CT2027TX:** In the event of no sound or intermittent sound check for a high-resistance connection at pin 4 of IC351 ( $\mu$ PC2002) – preferably replace the chip as a precaution. No colour or intermittent loss of colour can be due to the RGB demodulator but the usual cause is a leaky blanking diode, D209 (1S2076) – check by replacement.

J.C.

## Sony KV2752 (RX Chassis)

I've had a very interesting fault on these sets on three occasions during the past year. Customers complain of no remote control operation and no teletext. The clue to what's wrong is that the 6V supply is slightly low at 5V. When I first encountered the problem I suspected the teletext board and found that the remote control system worked when the board was unplugged – the 6V supply returned to normal. A new teletext panel made no difference however. To cut a long story short the culprit turned out to be C655 (220 $\mu$ F) on the power board.

Replacing it cleared the faults. On one occasion the same capacitor blanked out the picture, leaving just a vertical moving line down the centre of the screen. **J.S.R.**

### Sony RM Chassis

This set would work for five minutes after which the picture disappeared. Voltage checks revealed that in the fault condition the -30V supply was missing. The cause was that coil L810 went open-circuit when the set warmed up. **J.S.R.**

### Beovision 33XX Chassis

Here are a few faults we've had with these sets:

- (1) Grey-scale tracking variations were caused by 4R18 (1.8M $\Omega$ ) which had gone high in value. It's mounted on the c.r.t. base panel.
- (2) The remote control handset volume button worked correctly but sound mute didn't. Replacing diode 1D4 on the tuner/i.f. panel cured the trouble.
- (3) Pulsing on and off was traced to loose screws on the chopper transistor 6TR1.
- (4) No luminance can be caused by high-resistance contacts on the tuner/i.f. contact strip or the same item in the decoder. It can also, often intermittently, be caused by dry-joints on the inductors that form the luminance delay line.
- (5) An insensitive remote control handset was due to one of the LEDs being open-circuit. **J.L.H.**

### Tandberg CTV3 Chassis

Pumping on this chassis can be caused by failure of any one of a dozen components on the line output panel. High on the list of items to check for this condition is diode CR738 on the power supply panel. An RS BYW56 is a satisfactory replacement for the BY127 used in this position. **J.L.H.**

### Salora Models 1F3K and 1F0

When the memory crashes with remote control versions of these sets the result is a picture that lacks punch – for want of a better word. The adjustments can be restored as follows:

- (1) Set the customer controls to mid-position.
- (2) Adjust the brightness, contrast, colour and sound to the required levels using the remote control handset.
- (3) Press the front button on the  $\mu$ P board.
- (4) Press the normal button on the remote control handset.
- (5) Press the store button on the TV set *twice*. **J.L.H.**

### Panasonic TC2213

Difficulty in selecting a channel using either the channel change button or the remote control handset, coupled with difficulty in storing a station, was corrected by replacing the TMS3452N2L chip. Remember to take anti-static precautions when changing it. **J.L.H.**

### Sony KV2752

A new and rather nasty fault on one of these sets puzzled us recently for quite a few hours. It occurred on the RX chassis but the effect is the same with the PE version. The symptoms were a blank raster with sound present. Extensive checks were made around the TDA3562A colour

decoder chip IC301 but nothing amiss was found. The correct signals were entering the chip and the sandcastle pulse at pin 7 was of exactly the correct shape. Feeling that IC301 just had to be faulty we decided to change it, but this made no difference. Eventually we decided to replace IC551 (TDA2578A) which contains the sandcastle pulse generator circuit. The pulse now looked exactly the same but was of greater amplitude. To our relief this restored the picture. Another example of an easy fault – once you know what it is! **R.V. and D.B.**

### Philips/Pye KT3/30/35 Chassis

One of these sets suddenly refused to produce a picture, leaving just a smear of chroma. The trouble was that all voltages and waveforms seemed to be in order and panel swapping made no difference. There was a strange waveform on the -20V line at C464 (100 $\mu$ F) however. The -20V supply reservoir capacitor C586 (100 $\mu$ F) was the cause of the trouble – it had gone open-circuit. **B.McC.**

### Some Quickies

**Thorn 9600 Chassis:** This set came in dead. We found that one of the rectifiers (W518, type SKE2G2/02) fed from the chopper transformer was badly leaky – almost short-circuit in fact.

**Thorn 1694 Chassis:** This monochrome portable had lost its picture. The e.h.t. overwinding was getting warm because the e.h.t. rectifier, which is built into it, was short-circuit. A new overwinding put the set right.

**GEC PIL Chassis:** Another dead set – this time the line output transistor was short-circuit. **J.O.**

### Sony KX20PS1 Monitor

This set had an overbright picture with flyback lines. R638 (270k $\Omega$ ) in the first anode network on the tube base was open-circuit. **N.B.**

### Sony KX27PS1 Monitor

When a signal was fed in via the BNC video input socket there was no display. The sound was o.k. and a raster was present. Going out to the job I had visions of faulty leads/plugs etc. but everything appeared to be in order. Buffer transistor Q352 turned out to be short-circuit. **N.B.**

### Panasonic TC2205 (U2 Chassis)

Panasonic manuals can cause almost as much trouble as a faulty set. In this case the c.r.t. was cut off and we eventually traced the cause to the diodes in the 12V regulator transistor's base circuit – they were both leaky. This is in fact a not uncommon problem with these sets. But the circuit diagram in the manual shows both these diodes as ordinary types, the parts list says they are both zener diodes (no voltage given) while the board layout diagram shows one as being a zener diode and the other not. In fact they are both 6V zener diodes and the blanking circuit is fussy about this – the correct types should be fitted. I proved the point by using two 6.2V zener diodes. **N.B.**

### Sony KX20PS1 Monitor

Intermittent chroma dropout was corrected by adjusting the PAL delay potentiometer RV308. **N.B.**

# Test Report: Grundig Oscilloscopes

Steve Beeching, T.Eng.

I have recently had for evaluation two of the oscilloscopes, Models M022 and M053, in the current range of Grundig test equipment. On unpacking them the first impression was of the very attractive and well laid out control panels. The colour can only be described as fawn with a hint of green, the lettering being white. This proved to be very easy on the eye. The M022 has a bandwidth of 20MHz while the more comprehensive M053 has a bandwidth of 50MHz. We'll deal with the M022 first.

## Model M022

During the time I spent using this oscilloscope I was impressed by the ease with which I could glance up from a circuit test point and locate a control or a switch to change ranges. The controls are very easy to read and adjust and avoid the confusion that is so often present with a clutter of controls, symbols, etc. I suppose the term "user friendly" would sum up the familiarity I felt after just a few minutes' use.

The M022's control panel is divided horizontally into upper and lower sections, the lower section for vertical controls being subdivided into three sections while the upper section for the timebase controls is subdivided into four sections. The tube controls are at the lower left - focus, intensity, trace rotation (preset), push-button on/off plus a calibration test point. Two further sections cater for the ch. 1 and ch. 2 inputs for the dual traces. These inputs are identical except for an additional earthing point on ch. 1. Each input consists of a standard BNC plug, the impedance being  $1M\Omega$  shunted by  $25pF$ . Maximum input is 400V, including any d.c. There's a slide switch for a.c., O and a.c./d.c.: the a.c. setting blocks the d.c. component, O is an open input internally clamped to ground via  $68\Omega$  while a.c./d.c. is a straight input.

The input sensitivity selector ranges are from 5mV/cm to 20V/cm in 1, 2, 5 steps, i.e. 0.5V, 1V, 2V, 5V, 10V etc. In addition to vertical shift and variable/calibrate controls there's an inverter push-button. Vertical shift ranges from well below the screen to well above, quoted as +6cm to -6cm from the mid-point, the screen being calibrated to + or -4cm. The rotary calibrate control varies from a fixed position fully anticlockwise to up to 2.5 times the selected V/cm setting.

## Triggering Facilities

A four-position lever switch for the triggering mode gives "automatic", "normal" (with an additional variable level control), "TV vertical" and "TV horizontal", with a push-button to select triggering on the positive- or negative-going slope of transition edges. The push-button is not marked: it's in for negative and out for positive, with indication by positive and negative "S" curves. Above the variable trigger level control there's a green LED which lights when the scope triggers from a signal, as an aid to setting the trigger level for repetitive triggering.

A second four-way lever switch selects a.c., d.c., l.f. or h.f. triggering - l.f. is for frequencies below 8kHz and h.f. for frequencies above 10kHz. A third four-way switch selects the trigger source, ch. 1, ch. 2, the 50Hz mains ("line") or external. These three switches, mounted to-

gether, give a wide range of trigger sources and types covering most TV and video needs plus general-purpose inputs, as follows:

- (1) ch. 1/ch. 2/line/ext
- (2) auto/normal/TV field/TV line
- (3) a.c./d.c./l.f./h.f.

This indicates the trigger options, first the source on switch (1), then the type on switch (2) and lastly the signal parameter on switch (3). Note that these switches have no function when the source is TV sync pulses.

## The Traces

In the centre of the panel there's a trace selector switch for ch. 1, ch. 2 or both, i.e. dual traces. "Both" is written in darker green, indicating that it refers to the switch to the right giving chopped or alternate traces or ch. 1/ch. 2 addition.

Each of the ch. 1 and ch. 2 inputs has an invert option. Thus when used in conjunction with the add setting ch. 1 can be subtracted from ch. 2 or vice versa. This is useful for setting up camera tubes.

A second timebase, referred to as "B", has two lever switches for trigger and display selection, a rotary control covering  $0.5\mu\text{sec/cm}$  to  $2\text{msec/cm}$  and a delay control. The first lever switch has three positions, A, "B INT D" and B. Position A displays the A timebase while the unusual "B INT D" position displays the A trace with a brightened portion which is the delayed B timebase section. The timebase range selector expands the brightened portion to cover more of the A trace, while the delay control moves it sideways through the A display. The third position of the switch changes the display to the brightened portion and expands it to fill the time scale. Thus at the flip of a switch you can display A, A brightened by B, or B only. The main purpose of this delayed timebase arrangement is to enable a portion of the A trace to be selected and expanded for closer study.

The second lever switch selects timebase B's trigger mode - free run, A or not A. In the free-run mode the B timebase starts after the delay period has elapsed, i.e. at the start of the brightened portion. In the A position it starts after the next positive or negative trigger slope - determined by the position of the A slope polarity control. In the not A position the B timebase starts at the inverse of the next slope selected by the A setting.

## Auto-ranging Timebase

Without doubt the best feature of the oscilloscope is the auto-ranging timebase, which selects the best time scale from  $0.5\mu\text{sec/cm}$  to  $200\text{msec/cm}$  in eighteen ranges. The signal has between two and a half and five and a half cycles displayed on the screen, depending on the time scale used, the latter being indicated by one of nine green LEDs in a horizontal row - calibrated 0.5, 1, 2, 5, 10, 20, 50, 100, 200 similarly to the vertical calibration. Two more LEDs light to indicate whether the row is  $\mu\text{sec/cm}$  or  $\text{msec/cm}$ , giving the total of eighteen scales in the range.

There are two further controls, a fine control that provides up to 2.5 times the indicated display, with a

central detent position for the calibrated display, and a manual range control. The latter has an auto-ranging position when fully counter clockwise: when turned each green LED lights up in turn to indicate the scale. The operation of this control seems at first strange as it's linear instead of being a stepped switch, but it's pleasant when you get used to it – and not hard on the wrist!

In addition to the horizontal shift control there's a hold-off control whose function is to provide a "pause" between the completion of a trace sweep and the next trigger point to start the following sweep. It's variable and enables complex waveforms to give a stable display. An example is the display of TV lines that have shadowing in the background due to the half-line offset – this can be cleared with the hold-off control. Also, asynchronous digital signals such as bursts of serial data can be more clearly displayed by preventing unwanted sweeps that mix up the display by overlaying unwanted pulses.

## Performance

I could quote the various tolerance figures for d.c. drift etc., but they are so low as to be unnoticeable in normal use. For measurement purposes the timebase is accurate to  $\pm 3$  per cent while the vertical calibration is accurate to  $\pm 3$  per cent with a 0-20MHz bandwidth ( $-3$ dB).

The main question of course is what is the scope like to use? I put it through its paces for a week or so on VCRs, camcorders and compact disc players in order to be able to compare its capabilities with my Philips oscilloscopes.

There were no problems at all when searching through servos or signal paths, and I was able to set up the "eye" patterns on JVC CD players easily. At times the auto-ranging timebase got in the way and I went to manual but at other times it was a blessing. The timebase triggering is excellent – it never missed a beat. For signal checks around colour processing circuits where it's difficult to trigger from a signal I locked the second channel to a suitable video signal point and traced around with ch. 1. To set shading characteristics with cameras it's very useful to be able to subtract ch. 2 from ch. 1: the M022 is very good in this respect.

## VCR Head Switching Adjustment

The worst and most frequent use with a VCR is to set the video head switching points. For this, ch. 2 is triggered by the head switching signal and ch. 1 monitors the video signal. The timebase is then expanded to view the field sync pulses, so that the switching point can be set to 6.5 lines before the start of the field sync period. As the trace is fully expanded, the brightness decreases and the focus gets worse – stretching the tube to its fullest. The reason I've used Philips oscilloscopes is the 10kV post-deflection acceleration operation of the tube, which keeps the beam stable when fully expanded. The M022 has only 2kV and I expected it to fail in this task, but not so. While the brightness falls off, the trace is viewable except when too much ambient light falls on the screen. Focus is maintained as a result of the "automatic focus" achieved by high-voltage regulation. In addition, I understand that a hood is available as an optional extra.

## Model M053

The M053 is a higher grade version. It has an 11kV tube acceleration voltage and 50MHz bandwidth and is better able to cope with the problem of setting video head

switching. The layout is similar to that of the M022 but is not so attractive. Being more comprehensive, it takes a bit more driving. In fact it comes within the category of professional equipment.

The vertical range is from 2mV/cm to 10V/cm and the inputs are positioned in the same part of the front panel as with the M022, i.e. the lower half. Each range switch has an outer knob for selection and an inner knob for variable sensitivity – it pulls out for amplifier invert. With the inputs are the vertical trace selectors ch. 1/both/ch. 2 and alt/chop/add and the vertical shift and a.c./d.c. input selection controls, also a single alternate sweep separator which really belongs with the timebase controls above.

The main tube controls are on the lower left: dual-purpose rotary on/off with intensity, single-button beam finder, trace rotation and calibration test point. The focus and tube graticule illumination controls are together, rotary for focus and pull out for illumination. Unlike the M022, I sometimes found that I sat waiting for the trace to appear after switching on because I'd not rotated the control sufficiently to brighten it.

The main timebase A has auto/normal/TV/ $\times 1$  trigger modes. A reset button allows  $\times 1$  to provide a one-shot sweep. A separate switch selects V1/V2/Horiz which apply only in the TV mode: V1 triggers twenty lines before field sync in field one and V2 at the same point in field two, the Horiz position being for TV line sync. There's also a d.c./a.c./l.f./h.f. selector as in the M022. Trigger slope is also selected by a single in/out push-button but with green LEDs to indicate the trigger slope. This is mounted next to the variable trigger sensitivity control along with a green LED to indicate triggering.

Two switches act together for trigger source ch. 1/both/ch. 2 and internal/line/external/external  $\div 10$ . Both are similar to those described for the M022 except for the external  $\div 10$ , which gives an extra factor of trigger level from an external source, and "both" – if two signals on ch. 1 and ch. 2 are without interrelated timing (non-synchronous) they can both be displayed as stable signals by alternately triggering from each (this is not effective in the chop mode).

Delayed timebase B has a ten-turn precision potentiometer for the delay time and a single-turn control for trigger level with a free-running position fully anticlockwise. The slope is always the same polarity as selected for A. The display facilities are much more comprehensive however, via the timebase selector switch positions.

The A/alt/B/X, Y switch operates as follows. In the A position there's normal display of ch. 1/ch. 2, alternate or chopped. The alt position gives display of Ach. 1, Ach. 2, Bch. 1 and Bch. 2, i.e. four traces, two main and two delayed, with the main traces carrying a bright-up portion representing the section that's displayed by the delayed traces. This is where the alternate sweep separator comes into its own, adjusting the vertical separation of the four traces. The third switch position B gives a display of the delayed traces only, and finally the X, Y position puts ch. 2 into operation as an X amplifier with limited bandwidth (about 1MHz).

As with the M022, the M053 has an auto-ranging main timebase with optional manual control, this time in 21 ranges from 0.1 $\mu$ sec/cm to 500msec/cm with the 1, 2, 5 scales previously mentioned. A comprehensive digital display shows the time/cm, with an indicator on the left showing A or B timebase and indicators on the right showing nsec/cm,  $\mu$ sec/cm and msec/cm. Two push-buttons step through the range manually, one for up and one for down, with a single button for auto/manual and a red

LED to indicate manual.

Finally there are along the upper part of the control panel a  $\times 10$  timebase expansion button with a red LED, a variable time-scale control with a calibrate detent, a hold-off control as described for the M022 and a horizontal shift control.

## Conclusion

The M053 is a much more comprehensive oscilloscope than the M022, with better display facilities and a complexity designed to suit the proficient engineer. It can

be recommended as a main, wideband workshop oscilloscope for the serious user. The crunch is that you will have to pay something like £950 for the M053 while the M022 costs around £500, which without doubt makes it excellent value for money — what more can I say than that an M022 now graces my camera setting bench, along with a broadcast standard vectorscope and a Grundig VG1000 broadcast standard pattern generator. The equipment is available to Grundig dealers via their local Technical Liaison Officer. In case of difficulty, these items can be obtained from Newark Video Services, Grove Farm Estate, Barnby-in-the-Willows, Newark, Notts NG24 2SG.

# Long-distance Television

Roger Bunney

There was a lot of DX-TV propagation during October, via Sporadic E, auroras, F2/TE, the troposphere and the daily meteor scatter. It looks as though things are getting better, especially with F2 as a result of the increasing sunspot count — hopefully we'll be experiencing a productive winter. The general SpE log for the month is as follows:

4/10/88	TVE (Spain) chs. E2, 3; +PTT (Switzerland) ch. E3.
5/10/88	TVE E3.
7/10/88	NRK (Norway) E2; DR (Denmark) E3, 4.
10/10/88	TVE E2.
11/10/88	+PTT E3.
12/10/88	TVP (Poland) R1; TVE E2, 3.
14/10/88	TVE E2, 3, 4.
17/10/88	TVE E3.
21/10/88	TSS (USSR) R2.
22/10/88	TVE E2, 3, 4; TDF/C+ (Canal Plus — France) L3.
25/10/88	RTP (Portugal) E2.
26/10/88	TVE E2, 3, 4.
27/10/88	TVE E2.
28/10/88	TVE E2.

Auroral reception was reported by Iain Menzies (Aberdeen) as follows: NRK/TSS Band I signals on the 6th leading to RUV (Iceland) ch. E3 early on the 7th; NRK on the 9th; NRK/TSS on the 11th; NRK again on the 18th.

A stable high-pressure system over the UK from the middle through to the end of the month gave enhanced tropospheric propagation in Band III and at u.h.f., with particularly spectacular signals over the 15th-17th. On the 15th Band III/u.h.f. signals from West Germany plus the more usual French/Benelux stations were received in south/central UK. The 16th was the most significant day, with reception over most of the UK from West/East Germany, Scandinavia (Norway chs. E5-9, Sweden chs. E8, 9 and 30), the Benelux countries, France and RTE (Ireland). DFF (East Germany) was received in N.W. Wales on chs. E5, 6, 11, 12 and 34 while u.h.f. signals from the expanding French fifth and sixth networks were received in the north Midlands. Many enthusiasts reported reception of RTL+ (Luxembourg) ch. E7 and AFRB (American Forces) ch. A80. Conditions declined on the 17th, though many West German Band III/u.h.f. signals were received along the south/east coasts.

Undoubtedly the most interesting point however is that the increasing m.u.f. has resulted in the first F2/TE reception of the present solar cycle in the UK. Roger Fussel (Torpoint) received TE signals from NTA (Nigeria) on the 9th, from 1650-1720: first a grey-scale test pattern, then programme material with music. The signals suffered from severe fading and smearing, a characteristic of this mode of propagation. On the 25th, 27th, 29th and 30th Garry Smith (Derby) logged early morning F2 signals on chs. R1 and E2 at varying times between 0750-0912. The signals were strong at times though with smeary video — the R1 signals were from the USSR with the E2 signals on the 30th thought to be of Arabic origin. On the 31st Cyril Willis (Kings Lynn) received very strong ch. R1 signals from the USSR, first the test card, then programmes from 1115 with ch. E2 vision buzz (no pictures could be locked), followed by a locked line sawtooth on ch. E2 at 1245 and then captions and football, fading out at 1300. It all looks good!

With an increasing number of European countries allowing Amateur Radio operation in the 50MHz band we should be getting a closer insight into the possibilities of DX propagation at these frequencies. Contacts have already been made between the UK and the USA, also South Africa. Those with equipment tunable over 30-50MHz may, under suitable conditions, hear interesting communications signals from various parts of the world, e.g. rural US highway patrols, fire brigades, Middle Eastern communications, etc.

Meanwhile Anthony Mann in Perth, W. Australia reports a remarkable F2/TE opening on the 29th, with reception from China on channels up to C4 (77.25MHz vision). During most of the evening the signals were at very high levels, particularly on ch. C2. There was a general fade-out at 2400, after some four hours of reception. Other TV channels received were on frequencies 48.25MHz, 49.75MHz, 55.25MHz (E3 and A2), 56.25MHz, 59.75MHz, 61.25MHz and 62.25MHz. It seems that some of the signals were given an SpE boost over their final path to Perth. SpE reception had been prevalent during the day, with the 50MHz amateur band open to Hawaii. On the 15th a mid-afternoon SpE opening produced signals at up to 56.25MHz. In eastern Australia Robert Copeman and Todd Emslie report enhanced F2/TE conditions, with China ch. C1 received in Sydney on three occasions early in the month and many low-band v.h.f. communications signals received from the USA, Mexico and China, also the Korean Broadcasting System f.m. links at 30.4MHz. Incidentally Robert reports that TVQ has moved from ch. 0 to Band III while DDQ on Darling Downs has moved from ch. 10 to ch. 0 — one to look out for if the F2 conditions improve considerably. I recall one day during the last sunspot cycle when three ch. 0 signals were present floating over each other — it



does happen!

Hugh Cocks reports from the Algarve, Portugal, that TE conditions were excellent during September and early October, with ZTV (Zimbabwe) ch. E2 being received on most evenings from 1600-2000 BST, Nigeria/Ghana ch. E2/3/4 signals often being present and on good days ch. A2 signals from Brazil. Picture quality appalling of course, with multiple imaging and smearing.


We hear that during the excellent tropospheric opening on September 9/10th two DXers in Holland received TVE-2 signals on chs. E37 and E42. The same opening produced really intense ducting farther to the south, with amateur radio contacts between the Canaries and the UK in the 144MHz band, reaching also (just) to the Norwegian coast. According to a report in the RSGB's *VHF/UHF Newsletter* a Leicester amateur (G4GLT) noted regular reception of Zimbabwe TV at 48.258MHz via TE during a twelve-day period in September, at various times from 1640-2100 but mainly between 1800-1930. I assume that this reception was at scanner level within a narrow a.m. bandwidth rather than the 2-3MHz bandwidth that TV-DXers would use in order to be able to lock the video signal. It's common here at Romsey to hear a low-level video buzz from the south within a 5kHz bandwidth at times appropriate for TE reception of ZTV, though with the signal well below the noise threshold even using a 1.5MHz TV bandwidth.

An active and interesting month then. My thanks to the following for sending in reception reports: Roger Fussell (Torpoint), Garry Smith (Derby), Hugh Cocks (Portugal), Simon Hamer (Powys), David Oliver (Birmingham), Peter Schubert (Rainham), Tim Anderson (St. Leonards), Bill Cotterill (Tipton), Anthony Mann (Perth), Cyril Willis (Kings Lynn) and Iain Menzies (Aberdeen).
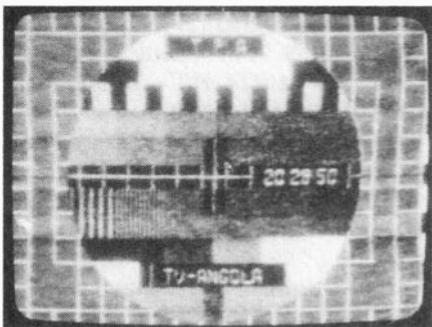
### News Items

**Belgium:** A local TV station, TeleBruxelles, opened in early October on ch. 36 with horizontal polarisation. The 10m high transmitter mast is atop an eight-storey building with the main beam apparently to the N/NW. A half hour local news/magazine programme is repeated from 1800-2400 weekdays with an omnibus edition at weekends from 1200.


**France:** The BDXC has kindly sent us a list of Canal Plus transmitters in Band I. Note that some of these stations are relays. Ch. L2 Drap H, L'Arbresle H, Amiens H, Bastia V, Chartres V, Nemours V; Ch. L3 Le Plessis H,



Yes, Angola does use the PM5544 test pattern! Seen here via a Gorizont (14°W) Band C downlink on its global beam. Photo of reception by Ian Waller, Lincoln.

## AERIAL TECHNIQUES
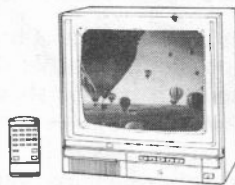
### A FURTHER ADVANCE IN RECEIVER TECHNOLOGY FOR ONLY £299.00



Another hi-tech exclusive scoop from Aerial Techniques. For UNDER £300, the answer to the multi-standard colour tv market.

The Yoko model RB1637 is a 14" PAL/SECAM FULL VHF/UHF infra-red remote control TV with audio/video access (via a 21 pin Skart socket) and covering SYSTEM I (6MHz sound for UK/Eire/South Africa) SYSTEM B/G (5.5MHz sound for Europe, Middle East, Australasia and other parts) AND SYSTEM L FRENCH standard (6.5MHz AM sound). The highly sensitive low noise tuner covers VHF TV/cable channels in - low - 47 - 120MHz; high - 120 - 300MHz and UHF 470-862MHz, giving complete coverage.

Full colour and sound on UK/overseas programmes - including France (switchable SECAM on B/G/L and PAL B/G/I) with crisp colour from the blackstripe slotted mask in-line CRT; switchable AFC; digital display channel readout; sharp SAWF IF selectivity; channel up/down scanning; low level colour/sync lock; 75 ohm coaxial aerial input and an audio jack for headphones are just some of the exciting features on this remarkable receiver, it also boasts a 16 channel memory.

Highly suitable for the TV-DXer, Continental travel and the Middle East/Gulf market, demand will be high at the low price quoted (ring for FOB/export quote), first shipment just in stock.

The Yoko RB1637 costs only £299 including Vat - collected from our office, add £8.75 for carriage & insurance UK mainland, other areas and Overseas please ask for quotation.

Our full range of aerials, amplifiers, rotators, filters and all aerial technology is detailed in our comprehensive 22 page illustrated Catalogue at 75p, send for your copy today. Customer advisory service also available, ring or write (include SAE).

All prices inclusive of VAT  
Delivery normally 7-10 days.



ACCESS & VISA Mail and Telephone orders welcome.



11, KENT ROAD, PARKSTONE, POOLE, DORSET BH12 2EH  
Tel: 0202 738232

Carcassonne V, Besancon V; Ch. L4 Mont Vial H, Mont Brian H, Ussel H, Quimperles H, La Roche/Yon H, Etempes H, Rennes V, Orange V. H = horizontal, V = vertical polarisation.

We regret having to report the death of Michel Dubernat, a well-known and very active TV-DX enthusiast over many years.

**Teletext adaptor:** A French firm is producing a teletext adaptor whose output plugs into a TV set's scart connector. It's a dual-standard decoder able to handle both UK and French teletext. The cost is 2,200 French francs, but French VAT may be deductible at 18.6 per cent. Enquiries, with return postage, can be sent to Societe Reinau Audio Visual, 1 bis rue Pernoux, 92160 Antony,

## IRISH T.V. DEALERS

VIDEOS UHF-VHF Ferguson, Sharp, ITT, Panasonic, Nord, etc fully serviced. Top Loaders, from £150 each. Front Loaders from £175 each.

TV's UHF-VHF Most makes in stock 8,16, and multi Channel remotes. Fully serviced from £75 each, untested off the pile £30 each.

## EXPORT SPECIALISTS

"Sets modified for African transmission"

T.V. TRADE SALES

E.D.I. HOUSE, KYLEMORE PARK WEST,  
DUBLIN 10. TEL. 0001 264139 or 263517

Paris, France. An r.f. output version is under development.

### Meteor Shower Dates for 1989

Our grateful thanks to George Spalding of the Meteor Section, the British Astronomical Association, for providing us with meteor shower information for the coming year as follows:

- Quadrantids January 1-6th peaking on the 3rd at 1500 ± 3 hours.
- Lyrids April 19-25th peaking on the 22nd.
- May Aquarids April 24th-May 20th peaking on May 5th.
- Delta Aquarids July 15th-August 20th peaking over July 28-30th.
- Perseids July 23rd-August 20th peaking on August 12th at 1400 ± 12 hours.
- Orionids October 16-27th with a flat peak over the 20-23rd.
- Taurids October 20th-November 30th with a flat peak over November 1-8th.
- Leonids November 15-20th peaking on the 17th.
- Geminids December 7-16th peaking on the 13th at 2100 ± 6 hours.
- Ursids December 17-25th peaking on the 22nd.

### New EBU Listings

Station	Service	Channel	Output
<b>France</b>			
Toulouse/Pic du Midi	TDF-5	E29	80kWH
Clermont Ferrand	TDF-5	E30	100kWH
Laval/Mont Rochard	TDF-6	E30	20kWH
Marseilles Grand Etoile	TDF-5	E32	150kWH
Clermont Ferrand	TDF-6	E33	100kWH
Laval/Mont Rochard	TDF-5	E33	20kWH
Brest	TDF-5	E34	100kWH
Le Mans Mayet	TDF-6	E35	150kWH
Orleans	TDF-6	E36	20kWH
Marseille Grand Etiole	TDF-6	E38	100kWH
Toulouse/Pic du Midi	TDF-6	E38	80kWH
Villiers	TDF-5	E39	25kWH
Mezieres	TDF-6	E41	5kWH
Bourges	FR3	E43	30kWH
Chartres	TDF-6	E44	50kWH
Sens	TDF-6	E44	40kWH
Mezieres	TDF-5	E44	5kWH
Bayonne	TDF-6	E45	40kWH
Chartres	TDF-5	E47	50kWH
Sens	TDF-5	E47	40kWH
Tours-Chissay	TDF-6	E54	80kWH
Bourges	TDF-6	E56	130kWH
Le Havre	TDF-6	E56	20kWH
Villers-Cotterets	TDF-6	E57	25kWH
Lyon Mont-Pilat	TDF-5	E59	250kWH
Brest	TDF-6	E60	100kWH

### West Germany:

Wesel Ind. E52 200kWH  
 H = horizontal, V = vertical polarisation.

### Satellite TV

The first high-power European TV satellite, the French TDF1 at 18°W, is now in orbit and testing — I received it here on November 15th. The D2-MAC transmissions included colour slides and an identification with date.

With a 1.5m dish the 62dBW signals were extremely strong. They are right-hand circular, a linear LNB showing no signal variation when switched between vertical and horizontal polarisation. Reception was at 11.727GHz, the extreme h.f. end of the European DBS band. During the previous week I received the PanAm satellite at 45°W with coverage of the US elections — this despite the fact that a neighbouring house almost obscured the dish. Test patterns and programmes from this satellite have been noted at 11.515 and 11.479GHz. When Ian Waller contacted the uplink site in the USA he was told that CNN is considering a business video channel but that apart from this the main TV transmissions are at present to South America, in Band C.

MTV is using an Intelsat transponder at 27.5°W, with both vertical and horizontal polarisation. Radio Nova is carried on a subcarrier with vertical polarisation, its previous "home" on a subcarrier of the now deceased Canal 10 being vacant. Universa, a Spanish-language service from the USA, may be downlinked via ECS4 at 13°E from early 1989. Scansat/TV3 is to launch a second channel to compete with TV2 — the latter started on October 1st for the Danish market. The new link will be via Astra. Gorizont at 14°W has been testing a new scrambling system on its Band C spot beam — there's little sign of any video transmissions from this craft's 11GHz transponder.

A new, easy to use satellite guide listing programmes, satellite downlinks and languages is available from Tele-Audiovision Medien GmbH, PO Box 801965, D-8000 Munich 80, West Germany for only one IRC. The information includes the latest Eutelsat changes, Astra, etc. Ask for *Europas Satelliten Ubersichtstabelle*. Highly recommended, and a very generous offer!

Thanks to Ian Waller of Lincoln for reporting on various satellite news items.

Maplin Electronic Supplies can supply F plugs, sockets, female in-line barrels and F male to BNC female adaptors at lowish cost for anyone using TVRO equipment with American F outputs/inputs. I was able to connect low-loss coaxial cable directly to an F plug by soldering the screen to the plug body (after pretinning the body). Two layers of heatshrink covering were then applied to provide physical support. With care an efficient termination can be made, giving a low insertion loss compared to the use of adaptors.

The British Amateur Television Club recently published material from US amateur Henry B. Ruh of Des Plaines, Illinois, in which he discusses the possibility of amateur TV operation on future space missions. The suggestion is to use fast-scan TV with reduced bandwidth and f.m. video at 434MHz or say 439.25MHz (the latter suggested by Motorola). The Americans are seeking comments from interested parties in the amateur field and a working committee of experienced ATV operators is being formed to give the matter further consideration and make recommendations to NASA.

### Miscellany

It's to the bottom of the class for me. Two readers who have purchased my TV-DX book have pointed out that the photograph showing double-hop multipath SpE reception on page 12 is from Jordan TV, not Syria.

A reader in Portland is seeking a photocopy of the circuit for a Bush Model R130 valve radio. Can anyone help?

# Service Bureau

*Requests for advice in dealing with servicing problems must be accompanied by a £2 cheque or postal order (made out to IPC Magazines Ltd.), the query coupon and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.*

## PHILIPS G11 WITH TELETEXT

This set works fine for about twenty minutes then the brightness starts to decrease and the teletext starts to play up. Eventually the picture loses colour lock and goes into bars. I've tried replacing the teletext panel, the chroma/luminance can and the colour decoder chips without success. The colour finally disappears altogether, though not on all channels. On text all I get when the fault is present is a vertical row of P100s down the left-hand side.

The teletext decoder will function correctly only when it sees valid data, so the problem that upsets the brightness etc. is also degrading the received vision signal. This suggests that the voltage on the LT2 line is varying. First check that the LT1 line (17.5V) is present and correct when the fault is present. If not, suspect C3150 (150µF) and possibly C5067 (10µF). If the LT1 voltage is correct, suspect the 12V stabiliser chip IC5073 (TDA1412).

## GRUNDIG CUC720 CHASSIS

There appears to be an a.g.c. fault on this set. The picture is good for most of the time but when there's a bright object, e.g. captions or something bright in the scene, the rest of the picture goes very dark and no amount of contrast control adjustment will make it any better. The fault is also intermittent: it's sometimes there when the set is switched on while at other times it appears only after the set has been working for a time. The voltages around the TDA5500 i.f. chip have been checked and seem to be within 1V or so of those shown on the circuit diagram.

First check the a.g.c. decoupler C2216 (1µF, 63V). If it's o.k. you will need to hook a d.c.-coupled scope to pin 21 of the tuner/i.f. module to check for correct signal level and video/sync ratio (should be 7:3). If this check shows wrong levels for waveform five (should be 2.2V peak-peak) replace the TDA5500 or fit an exchange module. If the waveform is o.k. when the fault is present the cause of the problem could be loss of clamping/black level in the decoder module. The Y signal is a.c.-coupled to pin 10 of IC2515 and is internally clamped by the pulse that enters at pin 8. Check C2541 (2.2µF, 50V) etc.

## PANASONIC NV370

When a tape is loaded and play is selected, instead of normal forward tape movement the tape usually runs at the correct speed but in reverse, thus looping and chewing the tape. This fault is intermittent – sometimes playback is normal, but going into reverse is more common. Also when play is selected the machine goes into pause/still picture – there seems to be no set sequence to it. The digital readout on the display/counter sometimes runs backwards when

playing or recording. When the tape is loaded and rewind/forward is pressed the readout will show correctly but nothing happens. Then after about four seconds the machine goes into the stop mode. When rewind/forward is again pressed the machine works correctly.

For the play backwards fault, check whether pin 39 of IC6001 rises above 1V. If it does, IC6001 is suspect, though IC2002 could be responsible – isolate the appropriate pins to prove which chip is causing the trouble. The other faults will probably be cured by fitting a new mode select switch (VES0246) and idler arm unit (VXP0521).

## FERGUSON TX9 (PANEL PC1040)

The colour is normal when the set is first switched on but after about half an hour it disappears. Freezing the 4.43MHz crystal restores the colour, but changing the crystal, the decoder chip and adjusting the oscillator has failed to cure the fault.

We've encountered this puzzling fault on more than one occasion. In each case the cause has been that the direct-path gain control RV67 in the chroma delay line circuit has a high-resistance or open-circuit track.

## GEC C1402H

This set worked well for six years then started to take some time to come on. Eventually it failed altogether. Some defective components were found in the switch-mode power supply: when these were replaced power was restored but only a poor monochrome picture was obtained, with perfect sound but no operation of the contrast, brightness and colour controls. Eventually the power seemed to fade away and the sandcastle pulse feed transistor T873 (BC238B) on the decoder panel blew.

First check the 12.6V line at C706. You'll probably find it high – if so replace the 7812 12V regulator chip IC700 in the power supply. If the fault remains, note that T873 is an emitter-follower feeding pulses to IC800 (TDA2151) and IC870 (TDA2140), both of which represent emitter loads. One or other of these is likely to be defective – check by substitution.

## SHARP VC8300

The loading motor goes backwards. Sometimes the recorder will load, but it then unlaces before the take-up spool has rotated by more than a quarter of a turn. The cassette lamp lights up, the head drum rotates and all the sensors seem to be all right. The head switching pulse is not being fed into the microcomputer chip, i.e. there's no 30Hz rectangular waveform at pin 58 of I801. The play, record and fast forward lamps light up but the mechanism doesn't respond.

The pulse waveform at pin 58 of I801 should in fact be 25Hz. It comes via I808 pin 10, I802 pin 5, I701 pin 20 (TP708), Q702, connectors AB1 and K11 on the drum

## QUERY COUPON

Available until 18th January 1989.  
One coupon, plus a £2 (inc. VAT)  
cheque or postal order, must accom-  
pany EACH PROBLEM sent in accor-  
dance with the notice printed above.

TELEVISION JANUARY 1989

motor. Check this path. Reversed operation of the loading motor could be due to faulty loading switches or failure of 1805.

### **FERGUSON 3787**

**When this set is switched on there's no sound or raster, the c.r.t.'s heaters don't glow and the fusible resistor RU05 gets excessively hot.**

The usual cause of RU05 overheating is a short-circuit or leakage across the U1 (290V) rail. Check this with an ohmmeter – the flyback thyristor DA12, which incorporates a reverse diode, is in particular suspect. Another possibility is that conduction via the start-up diode DR03 is being sustained because thyristor DU04 doesn't come on – check DU04, TU07 etc.

# TEST CASE

## 313

*Each month we provide an interesting case of TV/video servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.*

The repairs inwards bench can sometimes be a depressing sight. Take the other Monday morning: a Bang and Olufsen with intermittent pumping ("seen by engineer, customer very angry"); a Decca "not right since last repair, free of charge please"; a rental Mitsubishi, repossessed due to arrears, about fit for the scrap heap; a Ferguson TX model reeking of cat's pee, "estimate for insurance"; and so on. Amongst this lot there was a little Pye 14in. colour set with the simple comment "low height" on its job card. We pounced on it!

Its Model number was 37KT2060/05W and it was fitted with the CTX chassis – the CTX-S version. Tuned in to a test card the set displayed a picture that was centred but decidedly lacking in height – say 60 per cent of full height. The width was correct and the field linearity fine. Our first action was obviously to wind up the preset height control to see what it would do. The height could certainly be turned up, but the potentiometer had to be at nearly maximum before the picture reached the top and bottom of the screen, and at this point the sides of the raster bowed out. So we restored the height control to its original setting and consulted the manual.

The field amplifier and output stages are within a TDA3651 chip, IC7400: tests commenced here. IC7400's supply voltage comes from the line output stage. It measured correctly – 26V at the anode of D6400. The field oscillator is in another chip, a TDA2577, which also contains the sync separator and line generator stages. The voltages at the pins relevant to the field timebase were found to be reasonably close to those quoted in the manual. Out with the scope! The sawtooth provided by the output stage, at pin 5 of IC7400, was way down in

amplitude compared to the waveform shown on the circuit diagram. Our next check was at IC7400's input, pin 3, where the waveform did not resemble that shown in the manual. We proved that it was low in amplitude by whipping the back off our VCR monitor, which has a similar chassis.

Resisting the temptation to continue swapping notes between the two sets, we pressed on with our diagnosis. Negative feedback from the output stage is fed back to the sawtooth generator in the TDA2577 chip, and we suspected trouble here. Accordingly the series resistors R3404 and R3409 were checked. They were o.k. At this point we discovered the fault-finding tree on page 18 of the manual. Was there any effect on the raster sides it asked us? Yes, the bowed-out sides moved when the height control was adjusted. Check the height control and the field output chip said the tree. We checked the height control, which was o.k., but balked at chip replacement at this stage.

Time for coffee. As is so often the case, when we returned to the job fresh after our break we had a new insight into the problem, which was solved almost at once. Thinking about all the symptoms together led us to the answer: low height with excessive EW pincushion distortion correction; both chips apparently working correctly; a height control which forms part of a negative feedback loop. One small component was fetched from the stores and dabbed across two points in the CTX circuit. When this was done the height shot up beyond normal. What was the component? For the answer, see next month's issue.

### **ANSWER TO TEST CASE 312** – page 129 last month –

Last month's fault, on a Sony KV2204UB, was a strange one. At intervals, particularly when the set had warmed up, the picture brightness would decrease while the sound level increased. There had to be a common cause, but the main factors common to the relevant circuits, such as the supply line voltages and the analogue control chip IC003, had all been eliminated by making voltage measurements.

The audio and video signal processing chips are IC203 and IC301 respectively. Each has a control pin for output level, 5 and 4 respectively. The chips were responding correctly to the control commands when the fault was present – the voltage at pin 5 of IC203 rose while that at pin 4 of IC301 fell.

The cause of the problem turned out to be in the mute circuit. When the muting transistor Q001 conducts it pulls down the cathodes of D201 and D304 to cut off both the sound and vision. What was happening here was that some strange leakage or similar effect intermittently occurred in D201. This bled some of the brightness control voltage to the audio control line, increasing the latter from its typical figure of 3-4V while simultaneously reducing the voltage at pin 4 of IC301. The fault could be made to come and go by heating and cooling D201. It was permanently cured by replacing D201 and, just in case, D304.

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by The Riverside Press Ltd., Thanet Way Whitstable, Kent. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £18, overseas (surface mail) £21 per annum, payable to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to currency exchange, fluctuations and VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever. ISSN 0032-647X.

**A MESSAGE FROM PARADISE BEACH:  
 "START NOW, BUY FROM PRO-VISION AND  
 SPEND NEXT NEW YEAR ENJOYING YOUR  
 EXTRA PROFITS WITH US!"**

**From: PRO-VISION'S REGULAR CUSTOMERS:**

**QUESTION**

ARE YOU STILL  
 TRAVELLING ALL OVER  
 THE COUNTRY SORTING  
 THROUGH MOUNTAINS  
 OF STOCK TO FIND A  
 HANDFUL OF SETS  
 WHICH ARE UP TO  
 YOUR STANDARD?

**SOLUTION**

VISIT OUR WAREHOUSE —  
 UPGRADE YOUR CURRENT  
 STOCK AND KEEP YOUR  
 CUSTOMERS HAPPY.  
 REPUTATION AND PROFITS  
 GO HAND IN HAND AND ALL  
 THE SMART DEALERS BUY  
 FROM US. THE AMAZING  
 THING IS — THEY KEEP IT  
 TO THEMSELVES.  
 WELL WOULDN'T YOU, IF  
 YOU FOUND AN OASIS IN A  
 DESERT?

**QUESTION**

DO YOU STILL  
 SPEND PRECIOUS TIME  
 AND PROFITS ON  
 SERVICE CALLS  
 BECAUSE THE RIGHT  
 QUALITY OF STOCK  
 IS NOT AVAILABLE?

TELEVISIONS &  
 VIDEOS  
 FROM HOTELS AND  
 PRIVATELY OWNED  
 RENTAL COMPANIES  
 — HITACHI, GRUNDIG,  
 ITT, SONY,  
 PANASONIC  
 PLUS MANY OTHER  
 MAKES

**STILL ARRIVING**

Latest  
 DECCA/ TATUNG  
 MICRO-MONITORS  
 STANDARD, REMOTE,  
 TELETEXT

— OPEN —  
 Monday to Friday  
 10am to 5.30pm  
 all other times by  
 appointment

**PRO-VISION**

BREEDON CROSS STORAGE  
 DALE ROAD  
 SELLY OAK  
 BIRMINGHAM  
 B29 6AQ

**021 471 5116**



AA12	5P	BB199	52P	BB226	52P	BB253	52P	BB280	52P	BB307	52P	BB334	52P	BB361	52P	BB388	52P	BB415	52P	BB442	52P	BB469	52P	BB496	52P	BB523	52P	BB550	52P	BB577	52P	BB604	52P	BB631	52P	BB658	52P	BB685	52P	BB712	52P	BB739	52P	BB766	52P	BB793	52P	BB820	52P	BB847	52P	BB874	52P	BB901	52P	BB928	52P	BB955	52P	BB982	52P	BB1009	52P	BB1036	52P	BB1063	52P	BB1090	52P	BB1117	52P	BB1144	52P	BB1171	52P	BB1198	52P	BB1225	52P	BB1252	52P	BB1279	52P	BB1306	52P	BB1333	52P	BB1360	52P	BB1387	52P	BB1414	52P	BB1441	52P	BB1468	52P	BB1495	52P	BB1522	52P	BB1549	52P	BB1576	52P	BB1603	52P	BB1630	52P	BB1657	52P	BB1684	52P	BB1711	52P	BB1738	52P	BB1765	52P	BB1792	52P	BB1819	52P	BB1846	52P	BB1873	52P	BB1900	52P	BB1927	52P	BB1954	52P	BB1981	52P	BB2008	52P	BB2035	52P	BB2062	52P	BB2089	52P	BB2116	52P	BB2143	52P	BB2170	52P	BB2197	52P	BB2224	52P	BB2251	52P	BB2278	52P	BB2305	52P	BB2332	52P	BB2359	52P	BB2386	52P	BB2413	52P	BB2440	52P	BB2467	52P	BB2494	52P	BB2521	52P	BB2548	52P	BB2575	52P	BB2602	52P	BB2629	52P	BB2656	52P	BB2683	52P	BB2710	52P	BB2737	52P	BB2764	52P	BB2791	52P	BB2818	52P	BB2845	52P	BB2872	52P	BB2899	52P	BB2926	52P	BB2953	52P	BB2980	52P	BB3007	52P	BB3034	52P	BB3061	52P	BB3088	52P	BB3115	52P	BB3142	52P	BB3169	52P	BB3196	52P	BB3223	52P	BB3250	52P	BB3277	52P	BB3304	52P	BB3331	52P	BB3358	52P	BB3385	52P	BB3412	52P	BB3439	52P	BB3466	52P	BB3493	52P	BB3520	52P	BB3547	52P	BB3574	52P	BB3601	52P	BB3628	52P	BB3655	52P	BB3682	52P	BB3709	52P	BB3736	52P	BB3763	52P	BB3790	52P	BB3817	52P	BB3844	52P	BB3871	52P	BB3898	52P	BB3925	52P	BB3952	52P	BB3979	52P	BB4006	52P	BB4033	52P	BB4060	52P	BB4087	52P	BB4114	52P	BB4141	52P	BB4168	52P	BB4195	52P	BB4222	52P	BB4249	52P	BB4276	52P	BB4303	52P	BB4330	52P	BB4357	52P	BB4384	52P	BB4411	52P	BB4438	52P	BB4465	52P	BB4492	52P	BB4519	52P	BB4546	52P	BB4573	52P	BB4600	52P	BB4627	52P	BB4654	52P	BB4681	52P	BB4708	52P	BB4735	52P	BB4762	52P	BB4789	52P	BB4816	52P	BB4843	52P	BB4870	52P	BB4897	52P	BB4924	52P	BB4951	52P	BB4978	52P	BB5005	52P	BB5032	52P	BB5059	52P	BB5086	52P	BB5113	52P	BB5140	52P	BB5167	52P	BB5194	52P	BB5221	52P	BB5248	52P	BB5275	52P	BB5302	52P	BB5329	52P	BB5356	52P	BB5383	52P	BB5410	52P	BB5437	52P	BB5464	52P	BB5491	52P	BB5518	52P	BB5545	52P	BB5572	52P	BB5599	52P	BB5626	52P	BB5653	52P	BB5680	52P	BB5707	52P	BB5734	52P	BB5761	52P	BB5788	52P	BB5815	52P	BB5842	52P	BB5869	52P	BB5896	52P	BB5923	52P	BB5950	52P	BB5977	52P	BB6004	52P	BB6031	52P	BB6058	52P	BB6085	52P	BB6112	52P	BB6139	52P	BB6166	52P	BB6193	52P	BB6220	52P	BB6247	52P	BB6274	52P	BB6301	52P	BB6328	52P	BB6355	52P	BB6382	52P	BB6409	52P	BB6436	52P	BB6463	52P	BB6490	52P	BB6517	52P	BB6544	52P	BB6571	52P	BB6598	52P	BB6625	52P	BB6652	52P	BB6679	52P	BB6706	52P	BB6733	52P	BB6760	52P	BB6787	52P	BB6814	52P	BB6841	52P	BB6868	52P	BB6895	52P	BB6922	52P	BB6949	52P	BB6976	52P	BB7003	52P	BB7030	52P	BB7057	52P	BB7084	52P	BB7111	52P	BB7138	52P	BB7165	52P	BB7192	52P	BB7219	52P	BB7246	52P	BB7273	52P	BB7300	52P	BB7327	52P	BB7354	52P	BB7381	52P	BB7408	52P	BB7435	52P	BB7462	52P	BB7489	52P	BB7516	52P	BB7543	52P	BB7570	52P	BB7597	52P	BB7624	52P	BB7651	52P	BB7678	52P	BB7705	52P	BB7732	52P	BB7759	52P	BB7786	52P	BB7813	52P	BB7840	52P	BB7867	52P	BB7894	52P	BB7921	52P	BB7948	52P	BB7975	52P	BB8002	52P	BB8029	52P	BB8056	52P	BB8083	52P	BB8110	52P	BB8137	52P	BB8164	52P	BB8191	52P	BB8218	52P	BB8245	52P	BB8272	52P	BB8299	52P	BB8326	52P	BB8353	52P	BB8380	52P	BB8407	52P	BB8434	52P	BB8461	52P	BB8488	52P	BB8515	52P	BB8542	52P	BB8569	52P	BB8596	52P	BB8623	52P	BB8650	52P	BB8677	52P	BB8704	52P	BB8731	52P	BB8758	52P	BB8785	52P	BB8812	52P	BB8839	52P	BB8866	52P	BB8893	52P	BB8920	52P	BB8947	52P	BB8974	52P	BB9001	52P	BB9028	52P	BB9055	52P	BB9082	52P	BB9109	52P	BB9136	52P	BB9163	52P	BB9190	52P	BB9217	52P	BB9244	52P	BB9271	52P	BB9298	52P	BB9325	52P	BB9352	52P	BB9379	52P	BB9406	52P	BB9433	52P	BB9460	52P	BB9487	52P	BB9514	52P	BB9541	52P	BB9568	52P	BB9595	52P	BB9622	52P	BB9649	52P	BB9676	52P	BB9703	52P	BB9730	52P	BB9757	52P	BB9784	52P	BB9811	52P	BB9838	52P	BB9865	52P	BB9892	52P	BB9919	52P	BB9946	52P	BB9973	52P	BB1000	52P	BB1001	52P	BB1002	52P	BB1323	5
------	----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	-------	-----	--------	-----	--------	-----	--------	-----	--------	---




★ FOR SPARES OR REPAIR 3V30 VCRs FROM £20 ★ ALL PRICES SUBJECT TO VAT AND QUANTITY ★

Working 9000 R-C £20  
 Working 9900 R-C £30  
 Working 9600 R-C £25  
 GEC Starline £25

Working TX9 £35  
 Working KT3 £35  
 Working K30 £40  
 Philips G11 £25

Working TX Text £70  
 Working Philips G11 Text £55  
 Working KT3 Text £70  
 Working Toshiba Text £75

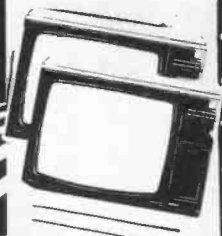Working 3V29/30 £80  
 Working JVC 7200 £80  
 Working 8940 £80  
 Front Loaders £80



**NOW OPEN**

Electricvision  
 29 Lonsdale Street  
 Stoke  
 ST4 4DT  
 Tel 0782 48153 / 744105



\*\*\*\*\*  
 \* MERRY CHRISTMAS AND A \*  
 \* SUCCESSFUL NEW YEAR TO ALL OUR \*  
 \* PRESENT/NEW CUSTOMERS \*  
 \*\*\*\*\*

95 Langworthy Rd  
 Salford  
 Manchester  
 M6 SPH  
 Tel 061 736 6333  
 061 745 8048

ALL PRICES SUBJECT TO VAT & QUANTITY

**HUGE STOCKS**  
 WORKING & GENUINE  
 UNTESTED TV'S & VCR'S

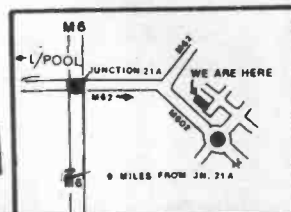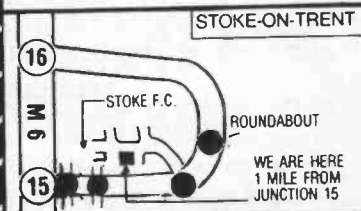**YOU'LL HAVE TO SEE US TO BELIEVE US !!**



**NGK**

UNIT 18  
 TILE CROSS TRADING ESTATE  
 TILE CROSS ROAD  
 MARSTON GREEN  
 B33 0NW

ELECTRONICS  
 C.T.V.'s  
 VIDEO's  
 AUDIO

EXPORT  
 ENQUIRIES  
 WELCOME

**A VERY PROSPEROUS NEW YEAR**  
TO ALL THE TRADES

Working Stock  
 from £18.00  
 with 7 days  
 "GUARANTEE"  
 All Working Stock  
 from £100.00  
 with 28 days  
 "GUARANTEE"

IF YOU WERE UNFORTUNATE ENOUGH NOT TO TRY NGK IN 1987 OR MAY BE HAD NOT THE TIME TO TRY US IN 1988, WHY NOT SAVE YOURSELF TIME BY TRYING NGK IN 1989, IT'S WELL WORTH THE VISIT TO JUDGE FOR YOURSELF.

WE ARE HERE — FULLY QUALIFIED STAFF — TO SOLVE YOUR PROBLEMS WITH GUARANTEED PERSONAL SERVICE.

TRADE  
 SERVICE  
 AVAILABLE  
 AT ALL TIMES  
 ON ALL MAKES  
 COURTEOUS SERVICE

RING    NORMAN    GLORIA    PAUL

on

021 779 5734  
 021 779 5465  
 021 779 5466

P.S.  
 STILL  
 TEA OR  
 COFFEE



# TELEPRICE

LIMITED

**SIMPLY THE BIGGEST  
WHOLESALE SUPPLIER  
OF THE BEST EX-RENTAL  
T.V.'s & VIDEO RECORDERS  
IN THE UNITED KINGDOM**

**RING OUR LOCAL MANAGER FOR DETAILS**

## FARNBOROUGH WAREHOUSE



**CLIFF PARSONS**  
0252 540814

7/8 KINGSGROVE INDUSTRIAL EST.  
INVINCIBLE ROAD  
FARNBOROUGH  
HANTS. GU14 7QS

**5 MAJOR  
REGIONAL**

**WAREHOUSES  
AT YOUR SERVICE**

## AVONMOUTH WAREHOUSE



**KARLA HEATH**  
0272 235093

5 PORTVIEW ROAD  
AVONMOUTH  
BRISTOL BS11 7LQ

## AINTREE WAREHOUSE



**IAN McCLELLAND**  
051 530 1285

UNIT 2, RACECOURSE IND. EST.  
ORMSKIRK ROAD  
AINTREE  
LIVERPOOL L9 5AL

## LINWOOD WAREHOUSE



**IAN DORAN**  
0505 29284

1a LYON ROAD  
LINWOOD INDUSTRIAL ESTATE  
LINWOOD  
RENFREWSHIRE PA3 3BQ

## SUNDERLAND WAREHOUSE




**BRIAN CADE**  
091 523 5554

9A/B  
94 CARRMERE ROAD  
LEECHMERE INDUSTRIAL EST.  
SUNDERLAND SR2 9TE

## REDIFFUSION TRANSLATOR


No. 847038

£4.99

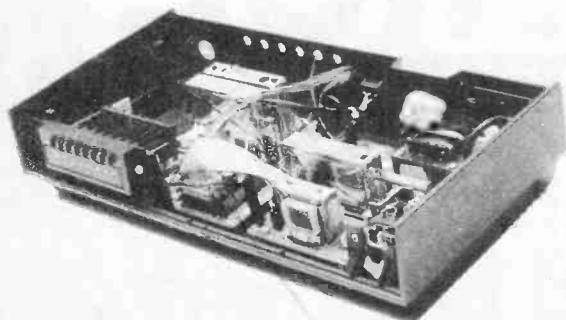

8-way "Preomat" T.V. Tuning of band 1-111 & UHF with AFC (less VHF tuner), Mains power supply 240V, in cabinet 14 x 7½ x 3½ inches. The TRANSLATOR may be used directly or modified to convert wired T.V. to normal use with Monitor (iV P-P), T.V. Sound tuner, (HI-FI), with any V.C.R. These units are guaranteed in perfect working order and A1 condition £4.99. P&P £3. Circuit & Modification £1 extra
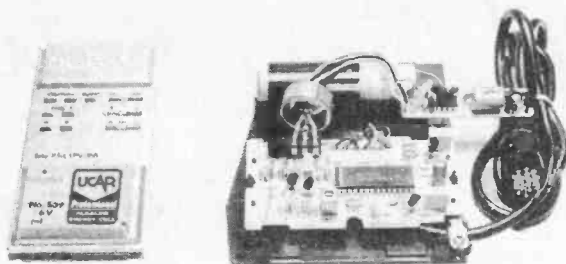
## GRUNDIG INFRA-RED REMOTE CONTROL VIF-K1 £4.99



(13 function) consists of transmitter TPV355 & receiver VIF-E1, suitable for use with GRUNDIG VIDEO 2 x 4 Super & Stereo. Brand new & boxed, complete with battery. £4.99. P&P £2. VIF-E1 receivers in boxes of 10. £9.99. P&P £3.50

**VIDEO HEAD CLEANERS** VHS or BETA £1.99 with full instructions. P&P £1

**V2000 VIDEO TAPES** "MEMOREX". All brand new & boxed. VCC360 £6.99. VCC480 £7.99. P&P £1

**C.B. CONVERTER** 40 channel, works in conjunction with standard car radio (A/M). Brand new & boxed. £2.50. P&P £1

**"VIDEOLAB" VIDEO TAPES** Premium quality VHS, which we recommend & guarantee one for one exchange. Brand new & boxed. £1.99. P&P £1

**BETA VIDEO RECORDER** "SONY" C5 & C7 "SANYO" etc. Perfect working order. £39.50

PRICES INCLUDE VAT.

PLEASE NOTE WE ARE INTERESTED IN PURCHASING ALL TYPES OF EQUIPMENT.

# STAN WILLETTS

DEPT. TWS

37 HIGH STREET, WEST BROMWICH,  
WEST MIDLANDS B70 6PB

TEL. 021 553 0186 021 559 1437

## W.TREE TRADE TVS SPECIALS

G11 OFF THE PILE .....	£10.00
G11 TEXT OFF THE PILE .....	£25.00
KT3 OFF THE PILE .....	£15.00
G11 WORKING.....	£18.00
G11 TEXT WORKING .....	£50.00
KT3 WORKING.....	£30.00

## QUANTITY DISCOUNTS

G11 TX9 TX10 KT3 GRUNDIG  
BUSH DECCA TATUNG TOSHIBA  
ITT SONY HITACHI HINARI  
GEC PANASONIC JVC

## HUGE SAVINGS

VIDEO  
VHS WORKING FROM £70.00  
HURRY WHILE STOCKS LAST

## NEW EX DEMONSTRATION CTV'S FST'S VIDEOS MOST BOXED

### Hoover 1100 Auto Washers £85

W. TREE TRADE TVS,  
UNIT 1 SUNSHINE MILLS,  
WORTLEY ROAD, LEEDS 12.  
TEL: 0532 638804.

**ALL PRICES PLUS V.A.T.**

# WEST MIDLAND TV & VIDEO WHOLESALEERS NOW OPEN IN WALSALL

**OVER 3000 TV's & VIDEO's  
IN STOCK AT**

**UNBEATABLE PRICES – HURRY NOW.**

**HUGE STOCKS  
WORKING & GENUINE  
UNTESTED TV's & VIDEO's**

**LOTS OF SPECIAL  
OPENING OFFERS  
WHILST STOCKS LAST**

## CTV's

	<i>Working</i>	<i>Non-Working</i>
PHILIPS G11	£20	£12
G11 TEXT	£50	£40
TX9	£35	£30
TX TEXT	£70	£60
BUSH T20	£20	£12
STEREO TEXT	£90	£80

## VIDEO's

	<i>Working</i>	<i>Non-Working</i>
FERGUSON 3V29	£75	£65
JVC 7200	£75	£65
PANASONIC	£75	£65
SHARP	£80	£70
MECHANICAL	£45	£35

**BLOCKS OF  
10 SETS  
FROM £40**



**ALSO LARGE  
SELECTION OF  
CTV'S UNTOUCHED  
TO CLEAR  
FROM £4**

2 MINUTES FROM JUNCTION 9 M6

**TRADE SHOWROOM  
LARGE QUANTITY OF READY  
TO SELL VIDEO's & TV's.  
CALL IN — YOU WILL BE DELIGHTED.**


**WAREHOUSE IN PASSAGE  
OFF LITTLE LONDON  
CALDMORE, WALSALL  
TEL. 0922 724542**

**OPENING TIMES: MONDAY TO SATURDAY 9 A.M. – 7 P.M. SUNDAY 10 A.M. – 2 P.M.  
DELIVERY CAN BE ARRANGED**

**ALL PRICES SUBJECT TO V.A.T. & QUANTITY**
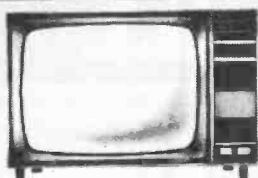
# ZonePort TV & VIDEO WAREHOUSE

We are one of Southern England's foremost Trade suppliers of top quality ex-rental TV and Videos. A good range in Philips, JVC, Sony, Toshiba, Hitachi and National Panasonic colour TVs including portables, teletxt and remote control models



## CHEAP BUT DEFINITELY NOT NASTY!!



We specialise in supplying working stock that has been professionally refurbished to a high standard. Our engineers pay special attention to the cosmetics as well as the electronics, so come to us for competitively priced stock that is *genuinely* ready for your showroom.

**NOW IN STOCK**  
EX-GRANADA  
MODELS  
FINLANDIA/REDIFFUSION  
Mk 3, 4 & 4A  
BASIC, REMOTE &  
TELETEXT VERSIONS

**BRIGHTON**  
**CUSTOMERS**  
CONTACT SIMON HEALY


☎ (0273) 571672

REDIFFUSION TRANSLATOR NO. 847038  
£3.99 plus £3 P&P inc. VAT

**UNIT N2**

London Road Trading Estate  
Sittingbourne, Kent.  
CONTACT BRIAN MOLLETT

☎ (0795) 28166

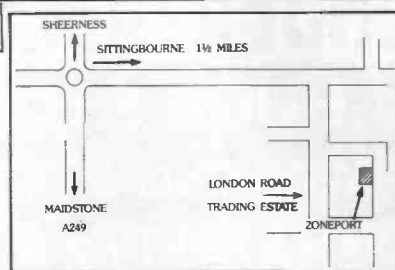

# CREWE WHOLESALE TELEVISION

**CHESHIRE'S LARGEST WHOLESALEERS - OVER 18,000 SQ. FT.**

15 MINUTES FROM JUNCTION 17, M6

(Including hundreds of text working and off the pile) G11's, G11 Text, Bush T-20 upwards, Finlandia, G.E.C., K30, KT3, Grundigs, ITT's, Trimlines, 800, CVC 40 and 30's, Decca 80's and 100's, Doric 3's, 3A's and 4's, and cable with translators. Philips KT30 - 3 - 45 stand & text.

## LORRY LOADS DIRECT FROM SOURCE

### VIDEOS

VHS - Mechanical Hitachi  
Electronic Nat/pan, Hitachi  
Sharp and Thorn

BETAMAX - Sony, Sanyo,  
Toshiba, etc.  
(Working or untouched)

50 Mixed of your  
choice

ITT30/32  
Decca 80's and 100's  
Doric series 3  
GEC 2110/2111

AT £250.00 + VAT  
GUARANTEED UNTOUCHED

**RING NOW FOR THE LATEST PRICES ON TV's & VIDEOS**

## CREWE WHOLESALE TELEVISION

(2 lines)

**Williams Street Warehouse, Crewe, Cheshire. ☎ 0270 582924**

# FAST VIDEO SPARES FAST

ALL STOCK ITEMS ARE DESPATCHED BY RETURN OF POST

## VIDEO HEADS

### REPLACEMENTS

All our replacement heads are brand new precision Japanese heads not refurbished.

<b>Panasonic</b>	
3HSS(N)	£19.90
Fits model numbers: NV2000, NV2010, NV7000, NV7200, NV333, NV8600, NV8610.	
3HSS-UI(N)	£29.90
Fits model numbers: NV370 & Philips VR6460.	
3HSS(4N)	£46.50
Fits model number: NV366	
3HSS(4NB)	£54.60
Fits model number: NV730	
<b>Ferguson</b>	
3HSS(V)	£19.90
Fits model numbers: 3V00, 3V16, 3V22, 3V29, 3V30, 3V31, 3V35, 3V36, 3V38, 3V39, HR3300, HR3330, HR3360, HR7200, HR7300, HRD120.	
3HSS4VB	£54.60
Fits model numbers: 3V32.	
<b>Sharp</b>	
3HSS(SP)	£29.90
Fits model numbers: VC9100, VC9300, VC9500, VC9700, VC381, VC8381, VC383, VC388, VC482.	
<b>Toshiba</b>	
PS3B(T)	£31.90
Fits model numbers: V9600, V31B, V33B.	
<b>Hitachi</b>	
3HSS(H)	£26.50
Fits model numbers: VT8000, VT9300 etc.	
<b>Sony</b>	
PS3B(S)	£24.90
Fits model numbers: SLC5, SLC6, SLC7, SL3000 also various NEC models.	
P84B(2S)	£34.50
Fits model numbers: SLC20, SLC30, SLC40, SLF1.	
PS5B(3S)	£44.20
Fits model numbers: SLC9, SLT50, SLC8, SLF60.	
<b>Amstrad/Saisho</b>	
3HSS(R)	£29.50
Fits model numbers: VCR7000 and all models using Orion chassis.	
3HSS(F)	£34.50
Fits model numbers: VCR4500, VCR5200, VCR9000 etc.	
<b>Fisher/Fidelity</b>	
3HSS(SF)	£29.90
Fits model numbers: FVHP615, FVHP710, V1000.	

### GENUINE HEADS

<b>Panasonic</b>	
NV2000, NV2010	£44.00
NV7000, NV7200	£44.00
NV333, NV370	£44.00
NV366	£64.50
NV688, NV777, NV788	£64.50
NV730	£67.50
All others available P.O.A.	
<b>Ferguson</b>	
3V00, 3V16, 3V22	£59.90
3V29, 3V30	£59.90
3V32	£66.90
3V35, 3V36, 3V38, 3V39	£59.90
<b>Sharp</b>	
VC7300, VC7700, VC7750	£69.90
VC8300	£69.90
VC9300, VC9500, VC9700	£62.00
VC381, VC383, VC386	£62.00
VC482	£62.00
All others available P.O.A.	
<b>Sanyo</b>	
VTC5000, VTC5150	£39.90
VTC5300, VTC5400	£39.90
VTC9300	£39.90
<b>Sony</b>	
SLC5, SLC6, SLC7	£49.50
SL8000, SL8080	£49.50
SLC20, SLC30	£54.50
SLC9	£54.50
<b>Toshiba</b>	
V9600	£59.90
V8600	£69.90
V31, V33	£59.90
V55, V56	£59.90
<b>Hitachi</b>	
VT5000, VT5500	£49.50
VT6500, VT8000, VT8300	£49.50
VT8500, VT8700	£49.50
VT9300, VT9500, VT9700	£49.50
VT11E, VT14E	£45.50
VT17E, VT19E	£54.60
VT33E	£49.50
<b>Philips</b>	
VR6460	£44.00
VR6462	£44.50
Please call if your model is not listed.	

## GENUINE

<b>Panasonic</b>	
NV2000, NV2010	£6.50
NV7000, NV7200	£6.50
NV333, NV366	£6.50
NV370, NV830, NV850	£2.80
NV688	£6.50
NV777, NV788	£4.70
NV8600, NV8610	£6.50
NV730	£1.90
NV230, NV430, NV870	£2.80
NV870, NV810	£2.80
<b>Ferguson</b>	
3V00, 3V16, 3V22	£6.50
3V23	£3.90
3V29, 3V30	£4.90
3V35, 3V36, 3V38, 3V39	£2.90
<b>Sanyo</b>	
VTC5000, VTC5150	£1.99
VTC5300, VTC5400	£4.50
VTC9300	£6.50
<b>Sony</b>	
SLC5, SLC7	£6.50
SLC6	£7.50
SL8000, SL8080	£6.50
<b>Sharp</b>	
VC7300, VC7700, VC7750	£6.50
VC8300	£3.30
VC9100, VC9300, VC9500	£6.50
VC381, VC383, VC386	£6.50
<b>Hitachi</b>	
VT5000, VT5500	£5.50
VT8000, VT8300, VT8500	£2.90
VT9300, VT9500, VT9700	£3.30
VT11E, VT14E, VT17E, VT19	£6.50
VT33E	£6.50
<b>Akai</b>	
VS9700	£6.50
VS2, VS3, VS4, VS5	£4.90
VS9300, VS9500, VS9700	£6.50
Many others available	

## BELT KITS

### REPLACEMENTS

<b>Panasonic</b>	
NV2000, NV2010	£3.50
NV7000, NV7200	£3.00
NV333, NV366	£3.00
NV8600, NV8610	£3.95
<b>Ferguson</b>	
3V00, 3V16, 3V22	£3.50
3V23	£2.90
3V29, 3V30	£3.50
3V35, 3V36, 3V38, 3V39	£2.90
<b>Sanyo</b>	
VTC5000, VTC5150	£1.00
VTC5300, VTC5400	£2.50
VTC9300	£4.25
<b>Sony</b>	
SLC5, SLC7	£3.60
SLC6	£4.95
SL8000, SL8080	£4.25
<b>Sharp</b>	
VC7300, VC7700, VC7780	£3.50
VC8300	£3.90
VC9100, VC9300, VC9500	£3.90
VC381, VC383, VC386	£3.90
<b>Hitachi</b>	
VT5000, VT5500	£4.50
VT8000, VT8300, VT8500	£1.50
VT9300, VT9500, VT9700	£1.50
VT11E, VT14E, VT17E, VT19	£3.90
VT33E	£3.90
<b>Akai</b>	
VS9700	£3.90
VS2, VS3, VS4, VS5	£3.95
VS9300, VS9500, VS9800	£3.50
Many others available	
<b>SENSOR LAMPS</b>	
All Panasonic	£1.80
All Ferguson/JVC	£0.65
Sharp VC9300 etc.	£2.90
Sharp VC7300 etc.	£1.80
Amstrad 7000	£2.30
All Hitachi	£1.80
<b>SENSOR L.E.D.'s</b>	
All Panasonic	£2.90
All Ferguson/JVC	£2.90
All Hitachi	£5.75
<b>END SENSORS</b>	
Hitachi VT64E	£1.20 each
<b>REEL MOTORS</b>	
Sharp VC9300, VC381 etc.	£18.20
Amstrad/Saisho etc.	£18.20
Panasonic NV333, NV366	£16.80
Sanyo VTC5000, 5300, 5400	£9.90
Panasonic NV7000, 7200	£19.80
<b>DRUM MOTORS</b>	
Ferguson/JVC 3V00, 3V22 etc.	£29.90
Sharp VC7300, VC7700	£26.40
Sharp VC8300	£26.40
Hitachi VT5000	£24.80
<b>CAPSTAN MOTORS</b>	
Sharp VC8300	£39.90
Sharp VC7300, VC7700	£29.30
Ferguson/JVC 3V00, 3V16, 3V22	£29.90
Ferguson/JVC 3V29, 3V30	£34.50
Ferguson/JVC 3V35, 3V36, etc.	£25.80
Hitachi VT5000	£24.80
Hitachi VT8000, 8500, etc.	£34.50
Hitachi VT9300, 9500, etc.	£34.50
Hitachi VT11, VT14, VT17	£26.80
Sony CS, C7	£29.90
Akai VS1-V55	£29.90
Many, many more!	
<b>IDLER WHEELS</b>	
Panasonic	
NV2000, NV2010	(Replacement) £0.95
NV2000, NV2010	(Genuine) £2.90
NV7000, NV7200	(Genuine) £2.90
NV333, NV366	(Genuine) £2.90
NV370, NV230, NV430	(Genuine) £4.50
NV777, NV788	(Genuine) £3.45
NV730	(Genuine) £4.50
<b>Ferguson/JVC</b>	
3V00, 3V16, 3V22 (Large clutch)	£5.95
3V00, 3V16, 3V22 (Small clutch)	£6.95
3V29, 3V30, HR7200, HR7300	£3.90
3V35, 3V36, 3V38, 3V39, HRD120	£3.90
<b>Sanyo</b>	
VTC9100, VTC9300	£1.90
VTC5000 Reel drive pulley	£6.50
VTCM10 Reel drive pulley	£9.90
<b>Sony</b>	
SLC5, SLC7	Rewind kit £4.95
SLC6	Rewind kit £4.95
<b>Sharp</b>	
VC9100, VC9300, VC9500 (Genuine)	£3.90
VC381, VC383, VC386 (Genuine)	£3.90
VC482, VC483, VC581 (also Saisho) (Genuine)	£3.90
VC482 etc. (Equivalent)	£2.98
VC9300, 381 etc. (Equivalent)	£2.98
<b>Hitachi</b>	
VT8000, VT8300, VT8500	£4.72
VT9300, VT9500, VT9700	£4.75
VT11E, VT14E, VT17E, VT19	£3.96
VT33, VT63, VT64, VT65	£3.96
<b>Akai</b>	
VS2, VS3, VS4, VS5	£4.50
<b>Fisher</b>	
FVHP615, FVHP710, FVHP725 etc.	£6.90
We also carry all play idlers and clutches etc. for models listed plus many more.	

CREDIT CARD ORDERS BY TELEPHONE RECEIVED BY 4 PM. ARE DESPATCHED SAME DAY



WE CARRY HUNDREDS OF VIDEO SPARES INC. PLAY IDLERS, CLUTCHES, MOTORS, SERVICE MANUALS, TENSION BANDS, BELTS AUDIO/CONTROL HEADS, ALIGNMENT TOOLS AND TAPES ETC. \*\*SPECIAL ORDER FACILITIES\*\* \*\*FOR NON-STOCK ITEMS\*\*

### PINCH ROLLERS

<b>Panasonic</b>	
NV2000, NV2010, NV7000, NV7200	£4.95
NV333, NV366, NV370, NV430	£4.95
NV730	£7.95
<b>Ferguson/JVC</b>	
3V00, 3V16, 3V22, 3V23, 3V24	£4.95
HR3300, HR3360, HR3660, HR2200	£4.95
3V29, 3V30, HR7200, HR7300	£4.95
3V35, 3V36, 3V38, 3V39, HRD120	£4.95
<b>Sanyo</b>	
VTC9100, VTC9300	£4.95
VTC5000, VTC5150, VTC5300, VTC5400	£4.95
<b>Sony</b>	
SLC5, SLC7	£5.95
SLC6	£5.95
SL8000, SL8080	£5.95
<b>Sharp</b>	
VC7300, VC7700, VC7750	£4.95
VC8300	£4.95
VC9100, VC9300, VC9500	£4.95
VC381, VC383, VC386	£4.95
VC651 etc.	£4.95
<b>Hitachi</b>	
VT5000, VT5500	£5.95
VT8000, VT8300, VT8500	£4.95
VT9300, VT9500, VT9700	£4.95
VT11E, VT14E, VT17E, VT19	£4.95
VT33E	£5.95
<b>Akai</b>	
VS9700	£6.95
VS2, VS3, VS4, VS5	£6.95
VS9300, VS9500, VS9700	£4.95
<b>Amstrad</b>	
VCR4500, 4600 Pinch Roller mod kit	£9.95

LARGE RANGE OF IC's & SEMI-CONDUCTORS AVAILABLE FOR TV, AUDIO & VIDEO

## THIS MONTH'S SPECIAL VIDEO SERVICE TOOL KIT

INCL. ALIGNMENT TAPE, TORQUE GAUGE, GREASE, TAPE GUIDE ADJUSTING TOOL, CIRCLIP PLIERS, etc.

was £239

now £189 + VAT

TELEVIDEO SERVICES

## TELEVIDEO SERVICES

UNIT 3, PLESSEY BUSINESS PARK, TECHNOLOGY DRIVE, BEESTON, NOTTINGHAM NG9 2ND  
 TEL: 0602-226070 FAX LINE: 0602-431097  
 24HR ANSWERING SERVICE FOR ORDERS PLACED AFTER 5.30 p.m.  
 Please add 70p post & packing and then add 15% VAT to total  
 OFFICIAL ORDERS ACCEPTED FROM SCHOOLS, COLLEGES, ETC. EXPORT ENQUIRIES WELCOME.  
 ALL ENQUIRIES SHOULD BE ACCOMPANIED BY STAMPED ADDRESSED ENVELOPE

# A.Z. ELECTRICS

Access & Visa Accepted

Stock items despatched by return

## VIDEO HEADS

**Ferguson**  
3HSSV - JVC/Ferguson most models £18.00  
3HSSVA - Ferguson 3V42/44/45/46 etc. £38.00  
3HSS4VB - Ferguson 3V3 HR7655 £45.00  
3HSS4VC - Ferguson 3V48 HRD565 £46.00

**Panasonic**  
3HSSN - Panasonic most models £18.00  
3HSSU1N - Panasonic NV370/380/100 Philips VR6460 £20.00  
3HSSU2N - Panasonic NV230/470/480 G9/G10 G11/G15PX £34.20  
3HSSU3N - Panasonic NV430/460 £22.75  
3HSS3N - Panasonic NV777/330 £32.20  
3HSS4NB - Panasonic NV730 £46.00  
3HSS4NA - Panasonic NV366 £45.00

**Hitachi**  
3HSSHA - VT8000/9500 etc. £22.00  
3HSSHB - VT11/33/63 etc. £22.00

**Amstrad**  
3HSSR - VCR4600, 7000, 9000 also Saisho, Orion, Triumph etc. £24.10  
PSF1 - VCR4500/5200 £22.85

**Sanyo**  
3HSSSY - VHR1100/1110/1300 £39.50  
3HSS3SY - VHR1500 £52.00

**Other Models**  
3HSSSP - Sharp VC9300/9500 etc. £22.00  
PS3B - Sony SLC5 C6/C7/8000 etc. £22.00  
PS3BT - Toshiba V9600/31/33 £23.75  
3HSSSF - Fisher FVH710/510 etc. £24.50

## VIDEO MOTORS

**Drum Motors**  
Ferguson/JVC (Mechanical models) £21.45  
Sharp VC7300/7700/7750/8300 £24.63

**Reel Motors**  
Sanyo VTC5000/5150/5300/5400 £7.90  
Sharp VC9300/9500 etc. £15.90  
Panasonic NV333/366 £13.20  
Ferguson 3V29/30 JVC HR200/7300 £22.70

**Capstan Motors**  
Ferguson/JVC (mechanical models) £21.45  
Ferguson 3V35 £22.50  
Sony SLC7/C5 (BHF1100D) £28.20  
Sharp VC7300/770/7750 £30.50

## REMOTE CONTROLS

Ferguson, Grundig, ITT, Philips, Pye, Sony and Hitachi various models TV & Video £13.50

## CAR RADIO/AUDIO MOTORS

6V, 9V, 12V and 13.2V clockwise or anticlockwise. Three sizes available

(1) Shaft 10mm, Height 34mm, Width 38mm £3.50  
(2) Shaft 7mm, Height 21.5mm, Width 34mm £3.50  
(3) Shaft 8mm, Height 25mm, Width 36mm £3.50

## LINE OUTPUT TRANSFORMERS

Decca 100 £8.50  
ITT CVC 25/30/32 £8.50  
Rank Bush T20A £9.25

## OTHER SPARES

IC STR620 Mod. kit for Hitachi CPT1471/1473 £6.95  
Universal Video Copying Kit £3.60  
Universal Video Copying Kit (scart) £5.20  
Video Cassette Lamp suitable for Ferguson/JVC with/without plug £0.50  
Cassette Lamps suitable for Sharp/Panasonic £0.50  
Cassette Lamp suitable for Sharp 9300 etc. complete with plastic moulding £1.25  
Cassette Lamp suitable for Amstrad 7000 £0.50  
Cassette Lamp suitable for Hitachi 9300/9500 £0.50  
Universal Cassette Lamps 40ma or 60ma £0.50  
CRT Anode Caps £0.60  
Universal Tripler £4.50  
Thom TX10 Focus Unit £8.50  
Video Tape Splicing Kit £6.95  
Hitachi TV Frame Module HM6251 £4.60  
Cassette Housing Assembly for Ferguson 3V35/36/38/39/42/43/44/43 etc. £25.25

## TV ON/OFF SWITCHES

ITT, Philips, Decca, Thorn, Fidelity, Grundig, Sony etc. State model and part number for price.  
Sony Universal with two brackets £3.75  
Philips G11, G8 plastic £0.95  
Thom 1690, 3000, 3500, 8000, 9000, TX9 etc. £0.90

\*\*\*\*\*  
ORDER FACILITY FOR ORIGINAL SHARP, SONY AND PANASONIC SPARES  
AVAILABLE. PLEASE QUOTE MANUFACTURERS PART NO.  
\*\*\*\*\*

## BELT KITS

Many Models From £0.80  
Sanyo VTC5000 £0.55

## PINCH ROLLERS

Many Models £2.70

## ZENER DIODES

BZX85 - 1.3W Most values in stock £0.10

**TRANSISTORS**  
BC107B £0.10  
BC108B £0.10  
BC147A £0.07  
BC172C £0.07  
BC214A £0.07  
BC214B £0.07  
BC237 £0.07  
BC238 £0.07  
BC308B £0.07  
BC327-25 £0.07  
BC328-40 £0.05  
BC337 £0.07  
BC547A £0.07  
BC548 £0.07  
BC549 £0.07  
BC559B £0.07  
BD237 £0.22  
BD238 £0.22  
BD243C £0.30  
BD244 £0.30  
BD244C £0.30  
BF195 £0.07  
BF196 £0.15  
BF197 £0.15  
BF198 £0.07

## INTEGRATED CIRCUITS

TBA120S £0.50  
TBA530 £1.00  
TBA560 £1.00  
TBA800 £0.85  
TBA820M £0.45  
TBA920S £1.00  
TDA1044 £1.00  
TDA1170S £1.20  
TDA1190Z £1.90  
TDA1412 £1.00  
TDA1940 £1.80  
TDA2521/3 £3.65  
TDA2560 £1.80  
TDA2581/2581Q £1.55  
TDA2590 £2.75  
TDA2653A £3.80  
TDA2600 £1.00  
TDA2611A £1.00  
TDA3560 £3.40  
TDA3561 £2.50  
TDA3562A £2.80  
TDA3565 £3.50  
TDA3562 £2.50  
TDA3950 £3.80  
TDA4500 £3.80  
TDA8180 £4.45  
TDA9503 £2.95  
UPC1365 £3.50

## IDLER ASSEMBLIES

Sharp VC9300/9500 etc. £1.75  
VC481/581 etc. £1.90  
VC9300/9500/481/581 etc. (NDL005GEZZ or NDL006GEZZ) Original £4.00

## Hitachi

VT11/33/14/17/19/63 etc. £1.75  
VT9300/9500 etc. Play Idler £3.65  
VT9300/9500 F/F Idler £1.50  
VT8000/8300/8500/8700 F/F Rew Idler £1.90  
VT8000/8500 etc. Play Idler Assembly £2.85  
VT8000/8500 etc. F/F Rew Pulley £0.70

## Ferguson

Take up Clutch (mechanical models) £4.95  
3V29/30 Take up Idler £1.20  
3V29/30 Take up Clutch £2.10  
3V29/30 Reel Idler £2.50  
3V35 Reel Idler £2.40  
3V35/36/38/39 Take up Clutch £2.00

## Sanyo

VTC5000/5150/6500 Idler roller assembly £1.95  
VTC5000/5150/6500 Reel Drive Pulley Unit £5.00

## Panasonic

NV370 (VXP0521) £1.75  
NV8600/8610 Play Idler (VXP0243) £0.95  
NV332/777/788 Idler Unit (VXP0463) £3.95  
NV600/688 Idler (VXP0515) £3.75  
NV333/366 Idler Arm (VXL0997) £3.10  
NV8400/8600/8610/8620 (VXP0245) £0.70  
NV333/366 etc. (VXP0401) NV700/7200/7800 (VXP0344) NV2000/3000 (VXP0331) (VXP0329) £0.70

## Fisher

FVHP615 Idler Assembly £5.40  
FVHP615 Gear Idler Assembly £4.35  
FVHP905/910 Gear Idler Assembly £3.30  
FVHP520/530 Idler £2.60  
FVHP520/530 Pulley £0.70

## REWIND KIT

Sony C5/7 Rewind Kit £4.20

CALLERS BY APPOINTMENT

Please add 75p per order for p&p and then add 15% VAT.

183 Acre Lane, Northampton NN2 8DX. Telephone: (0604) 847800



# BARGAINS IN SOUTH WALES

## VIDEO

	Working	Non-working
Electronic	From £75	£40
LP Electronic	From £95	£45
Beta	£20 as they come	
Philips	£8 as they come	

## COLOUR TV

	Working	Non-working
Pil	From £20	£10
R/C	From £35	£18
Text	From £65	£40
Colour Portable	From £65	£35
FST when available	From £115	£75

RANGE OF NEW HANDSETS IN STOCK

## BITEL

UNIT 11, TAVERNER TRADING EST. CAERLEON, NEWPORT, GWENT  
Leave M4 Junct 25, B4236 to Caerleon. 3 miles from M4.

**RING BOB ON 0633 430040 FOR QUANTITY DISCOUNTS**

Prices inclusive of VAT

# TRADE ANNOUNCEMENT BY GAMMA UK LTD

## NEW WAREHOUSE NOW OPEN IN BIRMINGHAM

Special offer on TX10 stereo	£85
TX9 and TX10 text	from £70
Philips and Pye G11 text	from £50
Decca and Tatung	from £15 to £55
Pye G11	from £25
TX9 and 10	from £35
Philips KT3 and KT30	from £30
Sony Hitachi and various other Japs	from £35

Many other makes and models also available  
Working 3V23, 29 and 30 VCRs from £75

ALL TV'S AND VIDEOS IN PERFECT WORKING ORDER

We are small enough to care and large enough to handle

So ring us or call today. We are nice friendly people. You may know us from past dealings with us. Ask for Mick (formerly from Chromavision).

**MERRY CHRISTMAS AND A HAPPY NEW YEAR TO ALL OUR PAST, PRESENT AND FUTURE CUSTOMERS**

RING US ON

**021-458-4093**


or call personally at:  
1750 to 1754 PERSHORE ROAD,  
COTTRIDGE, BIRMINGHAM

ALL PRICES PLUS V.A.T.
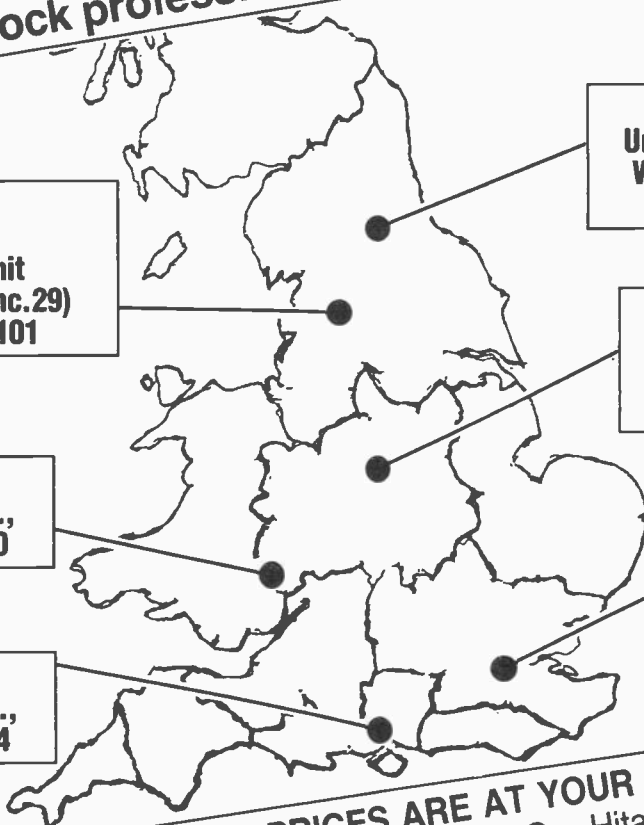
# HUSSAIN CENTRAL TV LTD.

We are still The UK's LARGEST  
 INDEPENDENT WHOLESALER OF  
 EX-RENTAL TV & VIDEO  
 TRADE ONLY

**MORE THORN RANGE THAN EVER BEFORE**  
**EXAMPLE CTV's: 9K - 9900, TX TEXT/STEREO/PROFF**  
**VCR's: 3V23 - 3V35, + VARIOUS LATE THORN**  
**All working stock professionally serviced to showroom standard**



**PRESTON**  
 Unit 439  
 Walton Summit  
 Preston (M6, Junc.29)  
 Tel: 0772 312101

**LEEDS**  
 Unit 2, Copley Hill Est.,  
 Whitehall Road, Leeds  
 Tel: 0532 422774

**BIRMINGHAM**  
 48-52 Pershore St.,  
 021-622-1023  
 021-622-1517

**CHEPSTOW**  
 Bullwark Ind. Est.,  
 Tel. 0291 271000

**LONDON**  
 Royal London Est.,  
 North Acton Road,  
 Tel: 01-961 5005

**SOUTHAMPTON**  
 500 Millbrook Rd.,  
 Tel. 0703 777254

**THE BEST STOCK AT THE BEST PRICES ARE AT YOUR LOCAL BRANCH NOW**  
 Choose from Thorn - Philips - Pye - Sony - JVC - Hitachi - Toshiba - Etc.  
 Please contact Tel: 021-622 1023 - Telex: 333599 HCTVUK.  
 Export and bulk enquiries welcome.  
 Delivery Service available, select your stock then we deliver it.

**"FORGET THE REST AND DEAL WITH THE BEST"**

\*\*\*\*\*STOP PRESS\*\*\*\*\*  
 \* ALL BRANCHES HAVE \*  
 \* EXCELLENT TEST FACILITIES \*  
 \* FOR YOU TO TRY YOUR STOCK \*  
 \*\*\*\*\*

\*\*\*\*\*STOP PRESS\*\*\*\*\*  
 \* BRAND NEW HANDSETS \*  
 \* SUPPLIED WITH MOST OF \*  
 \* OUR WORKING STOCK \*  
 \*\*\*\*\*

\*\*\*\*\*STOP PRESS\*\*\*\*\*  
 \* CONTACT YOUR NEAREST \*  
 \* BRANCH FOR UP-TO-DATE \*  
 \* STOCK APPRAISAL \*  
 \*\*\*\*\*

**We have become No. 1 through our policy of supplying a good quality  
 product with efficient and friendly service.**  
**WHY NOT RING YOUR LOCAL BRANCH NOW**

## **VHS VIDEOS** **FERGUSON**

3V00, 3V22, 3V23, 3V16, 3V29,  
3V30, 3V31, 3V32, 3V35

**HITACHI**  
5000, 8000

**NATIONAL PANASONIC**  
NV8600, 8610, 2000, 7000,  
370, 333, 2010

**SHARP**  
620, 630, 640, 2300 H T/P  
Untested from £70

## **BETAMAX VIDEOS** SANYO VTC 9300, 5300

SONY C5, C6, C7  
Untested from £25

HITACHI VHS TUNER/TIMER £10,  
HITACHI VHS BATTERY CHARGER  
£10, ROBERTS VHF RADIOS £5  
VHS/Beta tapes used –  
from 40p each

Sorry must collect as we do not send  
through the post.

### PLUS

17" 18" 20" 22" 26" Hybrid/  
Solid State from £8. Also available  
CTVs Remote Control & Teletext  
All prices subject to 15% VAT

**Discount for Quantities**

**Complete loads delivered from pick up point**

**JOHN CARTER**  
**(Electrical) LTD**  
**FURNACE ROAD,**  
**GALLOWS INN,**  
**ILKESTON**

**Phone: 0602 303124**

**DISPLAY**  
**ELECTRONICS LTD.**

- ★ Do you use cathode ray tubes?
- ★ Can't find a replacement or shocked by the cost?
- ★ It may well be that a rebuilt tube will solve your problem.

Come to one of the most experienced firms in the business. We have been rebuilding cathode ray tubes for industry, broadcasting authorities, major airlines, M.O.D. universities, and, of course, the TV trade in general since the '60's.

**WHY NOT TELEPHONE**  
**UXBRIDGE (0895) 55800**  
**TO DISCUSS YOUR**  
**REQUIREMENTS. DAVE**  
**DYSON WILL HELP YOU WITH**  
**DOMESTIC TV TUBES. TERRY**  
**SMITH DEALS WITH**  
**COMMERCIAL/**  
**PROFESSIONAL**  
**TYPES.**

We are currently redeveloping our factory and have temporarily transferred production facilities to a factory unit in nearby Iver (Bucks). We have made arrangements for the Uxbridge 55800 telephone to be rerouted to the Iver factory at the exchange, but if you should wish to dial directly, the Iver number is (0753) 630137. During the temporary period of relocation we shall maintain goods handling facilities at Uxbridge. It would be appreciated if intending visitors telephone us first to be sure that technical staff are available at Uxbridge if required. We greatly appreciate the confidence placed in us by our customers which has enabled our business to grow and look forward to being of continued service in the future.

**DISPLAY ELECTRONICS LTD.**  
SWAN WHARF,  
WATERLOO ROAD,  
UXBRIDGE, MIDDLESEX.



AN103	£1.95	AN6610	£1.95	BA1320	£1.25	HA11749	£4.75	LA4440	£2.75	STK080	£7.50	STR4211	£6.75	TD2611A	£1.35
AN1270	£2.20	AN6676	£7.50	BA1330	£1.75	HA11750	£5.00	LA4445	£2.75	STK082	£7.75	STR6020	£6.75	TD2653A	£3.80
AN203	£2.20	AN6677	£6.30	BA1360	£1.80	HA11753	£8.50	LA4460	£1.80	STK084	£7.60	TA7063P	£1.50	TD3505	£5.20
AN210	£2.10	AN6780	£2.30	BA102A	£2.75	HA11758	£8.50	LA4461	£1.80	STK086	£7.50	TA7068P	£1.50	TD3540	£3.80
AN211A	£2.30	AN6811	£1.60	BA5209	£2.75	HA11768	£4.50	LA4500	£2.80	STK431	£2.95	TA7073P	£1.50	TD3541	£3.60
AN217B	£2.20	AN6875	£3.50	BA5402A	£2.75	HA11788	£4.50	LA4505	£2.80	STK433	£2.95	TA7074P	£1.50	TD3550	£4.50
AN228W	£2.90	AN6884	£2.75	BA5406	£3.20	HA11816	£6.50	LA4507	£2.25	STK435	£3.50	TA7122AP	£0.90	TD3560	£4.50
AN236	£2.50	AN7105	£2.50	BA6104	£2.80	HA11828	£3.50	LA4520	£2.85	STK436	£3.25	TA7136P	£1.50	TD3561A	£4.95
AN240P	£1.50	AN7106K	£2.95	BA6124	£2.80	HA12001	£3.50	LA4570	£3.75	STK439	£3.95	TA7140P	£1.75	TD3562A	£5.80
AN241P	£1.50	AN7110	£2.95	BA6208	£2.95	HA12002	£2.95	LA5112	£1.65	STK441	£2.95	TA7156P	£2.50	TD3651	£2.70
AN259	£2.75	AN7111	£1.50	BA6209	£2.75	HA12035	£9.50	LA5527	£1.95	STK443	£2.95	TA7193P	£4.00	TD3652	£3.30
AN260P	£2.70	AN7112E	£2.95	BA6304	£2.20	HA12038	£6.75	LA6324	£2.50	STK457	£6.50	TA7205AP	£1.00	TD4420	£3.75
AN262	£1.60	AN7114E	£2.50	BA6342	£5.00	HA12402	£2.95	LA6358S	£1.20	STK459	£6.75	TA7207P	£1.75	TD4450	£3.95
AN264	£3.75	AN7115E	£1.60	HA1124A	£2.75	HA12413	£2.75	LA6450	£1.20	STK461	£7.50	TA7208P	£1.75	TD4600-20	£2.95
AN271A	£2.50	AN7116	£1.50	HA11240S	£2.50	HA13001	£2.95	LA7016	£2.75	STK463	£3.40	TA7222AP	£1.60	TD4600-20	£2.95
AN274	£2.75	AN7120	£1.50	HA1125	£1.75	HA13007	£4.95	LA7032	£4.50	STK465	£3.80	TA7223P	£2.30	UPC1032H	£0.60
AN277	£2.50	AN7131	£2.75	HA1137W	£4.25	HA13402	£4.95	LA7075	£4.50	STK501	£6.25	TA7225P	£2.30	UPC1031H	£1.95
AN295	£3.60	AN7140	£2.20	HA1151	£2.50	HA13432	£4.50	LA7212	£2.75	STK0025	£4.95	TA7225P	£2.30	UPC1010H	£2.20
AN301	£3.50	AN7143	£2.95	HA1155W	£2.10	LA1111	£0.95	LA7224	£2.95	STK0029	£4.75	TA7227P	£2.30	UPC1018C	£2.95
AN302	£3.30	AN7145M	£2.95	HA1167	£1.75	LA1130	£2.75	LA7505	£2.95	STK0039	£4.75	TA7227P	£2.30	UPC1025H	£2.30
AN303	£2.75	AN7146M	£2.80	HA1196	£1.75	LA1140	£2.20	LA7507	£2.95	STK0040	£6.25	TA7229P	£2.30	UPC1031H	£1.95
AN305	£3.50	AN7149N	£2.80	HA1197	£1.75	LA1222	£1.00	LA7520	£3.95	STK0049	£5.50	TA7230P	£1.95	UPC1225H	£2.75
AN313U	£2.95	AN7154	£1.90	HA1199	£1.85	LA1230	£1.50	LA7521	£4.50	STK0059	£7.00	TA7232P	£2.95	UPC158H	£0.95
AN315	£2.30	AN7156N	£2.50	HA1219	£1.85	LA1231	£2.00	LA7571	£4.75	STK0060H	£9.50	TA7233P	£2.95	UPC1181H	£1.10
AN316	£3.75	AN7158N	£3.25	HA1219	£1.85	LA1240	£1.95	LA7575	£4.20	STK0060H	£9.50	TA7233P	£2.95	UPC1182H	£1.10
AN318	£4.95	AN7160	£3.75	HA1366WR	£1.85	LA1260	£2.95	LA7800	£1.95	STK1060	£9.95	TA7240AP	£2.95	UPC1185H	£2.50
AN337	£5.25	AN7161	£3.75	HA1367	£1.85	LA1353	£2.50	LA7801	£1.95	STK1060	£9.95	TA7241AP	£2.95	UPC1188H	£2.75
AN340P	£1.50	AN7168	£2.75	HA1368	£1.90	LA1365	£1.50	LA7802	£2.95	STK2028	£7.50	TA7270P	£2.75	UPC1234C	£4.75
AN360	£1.30	AN7178	£2.95	HA1368R	£1.95	LA1368S	£2.50	LA7808	£2.95	STK2029	£9.75	TA7271P	£2.75	UPC1230H	£2.50
AN362L	£1.60	AN7213	£1.95	HA1370	£3.70	LA1387	£3.60	LA7910	£2.75	STK2038H	£9.50	TA7272P	£2.95	UPC1263C	£2.50
AN363N	£3.50	AN7218	£1.75	HA1372	£3.50	LA1460	£2.50	LA7920	£2.20	STK2125	£6.75	TA7273P	£2.95	UPC1277H	£2.75
AN366P	£1.70	AN7222N	£1.50	HA1374	£2.50	LA1464	£3.20	LA7920	£2.20	STK2129	£6.75	TA7274P	£2.95	UPC1278H	£2.75
AN374P	£2.00	AN7223	£3.95	HA1377	£2.75	LA1465	£2.20	LA7920	£2.20	STK2129	£6.75	TA7280P	£2.75	UPC1363C	£2.75
AN377	£2.00	AN7224	£3.50	HA1384	£3.95	LA2100	£2.95	LA7920	£2.20	STK2240	£9.50	TA7281P	£2.95	UPC1364C	£4.75
AN610P	£1.80	AN7256	£3.50	HA1388	£3.50	LA3160	£1.50	LC7130	£3.50	STK3041	£6.50	TA7282AP	£2.95	UPC1365C	£3.60
AN612	£1.80	AN7273	£3.95	HA1389	£2.20	LA3201	£0.95	LC7137	£3.75	STK3042	£6.50	TA7283AP	£2.95	UPC1384C	£3.50
AN65010	£4.75	AN7310	£3.25	HA1389R	£2.20	LA3210	£0.75	LC7137	£4.00	STK3044	£9.95	TA7288P	£2.95	UPC1387C	£2.95
AN6519N	£6.50	AN7311	£1.20	HA1392	£2.50	LA3220	£2.95	LC7136	£3.75	STK3044	£9.95	TA7299P	£2.95	UPC1391H	£1.50
AN6525	£1.00	AN7310	£3.00	HA1394	£2.95	LA3300	£1.65	LC7137	£4.50	STK362H	£3.95	TA7317P	£2.75	UPC1394C	£1.95
AN65410	£5.50	AN7415	£2.95	HA1396	£3.75	LA3301	£1.30	LC7800	£3.95	STK4026	£6.75	TA7343AP	£2.95	UPC1455C	£0.90
AN65411	£3.50	AN7420	£2.95	HA1397	£2.75	LA3310	£2.75	M5134P	£3.25	STK4131H	£6.75	TA7358P	£2.80	UPC1455C	£0.90
AN65430	£2.95	BA301	£0.80	HA1398	£2.20	LA3350	£1.30	M5155P	£1.85	STK4141H	£6.75	TA7607AP	£2.95	UPC1455C	£0.90
AN65510	£2.75	BA311	£0.95	HA1457W	£2.75	LA3361	£1.20	M51102L	£3.95	STK4151H	£7.50	TA7608CP	£3.95	UPC1455C	£0.90
AN65612	£2.95	BA313	£0.80	HA1457W	£2.75	LA3370	£1.80	M5104L	£2.80	STK4332	£5.75	TA7608CP	£3.95	UPC1455C	£0.90
AN65612	£2.95	BA314	£2.20	HA11215	£4.95	LA4030P	£2.00	M51513	£1.80	STK4352	£6.50	TA7628P	£2.95	UPC1455C	£0.90
AN6520X	£3.50	BA318	£1.50	HA1221W	£1.90	LA4031P	£1.95	M51514	£1.95	STK4392	£7.50	TA7640AP	£1.75	UPC1455C	£0.90
AN5701	£1.80	BA328	£2.50	HA11223W	£1.90	LA4032P	£1.90	M51515BL	£2.50	STK4803	£9.50	TA7658P	£1.75	UPC1455C	£0.90
AN5722	£1.60	BA333	£1.50	HA11225	£3.85	LA4100	£1.20	M51516BL	£2.80	STK4833	£9.50	TA7658P	£1.75	UPC1455C	£0.90
AN5730	£1.85	BA335	£3.60	HA11226	£4.50	LA4101	£1.00	M51517L	£2.80	STK4843	£9.95	TA7658P	£1.75	UPC1455C	£0.90
AN5732	£1.85	BA340	£2.95	HA11235	£2.30	LA4102	£1.40	M51518L	£2.20	STK4843	£9.95	TA7658P	£1.75	UPC1455C	£0.90
AN5750	£3.75	BA343	£2.75	HA11251	£1.90	LA4110	£1.75	M51521L	£1.90	STK5211	£6.75	TA7613AP	£2.95	UPC1455C	£0.90
AN5753	£1.95	BA402	£0.95	HA11401	£2.80	LA4112	£1.75	MB3705	£1.80	STK5324	£6.75	TA7613AP	£2.95	UPC1455C	£0.90
AN6250	£2.30	BA403	£1.95	HA11423	£2.75	LA4120	£2.95	MB3712	£1.50	STK5325	£6.75	TA7613AP	£2.95	UPC1455C	£0.90
AN6326N	£3.70	BA511A	£1.85	HA11440	£3.95	LA4125	£2.20	MB3713	£1.60	STK5421	£6.50	TA7613AP	£2.95	UPC1455C	£0.90
AN6327	£4.75	BA514	£1.80	HA11701	£3.50	LA4126	£2.60	MB3714	£1.95	STK5451	£6.75	TA7613AP	£2.95	UPC1455C	£0.90
AN6328	£4.20	BA516	£1.90	HA11703	£6.50	LA4137	£1.95	MB3722	£3.50	STK5471	£6.50	TA7613AP	£2.95	UPC1455C	£0.90
AN6330	£2.95	BA521	£1.80	HA11704	£5.20	LA4140	£3.90	MB3730	£2.50	STK5476	£6.75	TA7613AP	£2.95	UPC1455C	£0.90
AN6340	£7.85	BA524	£2.75	HA11705	£4.45	LA4145	£1.70	MB3731	£3.50	STK5720	£6.80	TA7613AP	£2.95	UPC1455C	£0.90
AN6341N	£4.00	BA526	£3.50	HA11706	£4.75	LA4160	£2.40	MB3756	£2.60	STK5730	£4.25	TA7613AP	£2.95	UPC1455C	£0.90
AN6342N	£2.50	BA527	£1.75	HA11710	£3.75	LA4170	£3.50	MB3759	£3.00	STK7216	£6.50	TA7613AP	£2.95	UPC1455C	£0.90
AN6344	£4.75	BA532	£1.60	HA11711	£9.50	LA4178	£2.50	MB3759	£3.85	STK7216	£6.50	TA7613AP	£2.95	UPC1455C	£0.90
AN6350	£7.50	BA536	£2.50	HA11714	£6.50	LA4182	£2.20	STK011	£3.95	STK1404	£9.95	TA7613AP	£2.95	UPC1455C	£0.90
AN6356N	£3.85	BA546	£2.20	HA11717	£4.75	LA4192	£1.95	STK015	£5.20	STK8250H	£10.75	TA7613AP	£2.95	UPC1455C	£0.90
AN6357N	£4.95	BA547	£2.50	HA11717	£5.75	LA4201	£1.60	STK016	£6.25	STR380	£5.80	TA7613AP	£2.95	UPC1455C	£0.90
AN6360	£4.50	BA612	£1.80	HA11718	£4.75	LA4220	£1.50	STK020	£5.75	STR440	£5.80	TA7613AP	£2.95	UPC1455C	£0.90
AN6362	£5.50	BA631A	£1.75	HA11724	£9.25	LA4230	£2.25	STK025	£7.50	STR441	£5.80	TA7613AP	£2.95	UPC1455C	£0.90
AN6363	£8.50	BA636	£4.50	HA11727	£9.50	LA4230	£2.25	STK043	£10.50	STR451	£5.80	TA7613AP	£2.95	UPC1455C	£0.90
AN6371	£4.25	BA643	£4.00	HA11745	£9.00	LA4242	£1.75	STK077	£6.75	STR2012	£6.75	TA7613AP	£2.95	UPC1455C	£0.90
AN6387	£5.95	BA1310F	£1.75	HA11747	£9.00	LA4430	£1.50	STK078	£6.50	STR4090	£6.75	TA7613AP	£2.95	UPC1455C	£0.90

# T. POWELL

16 PADDINGTON GREEN,  
LONDON W2 1LG  
Tel: 01-723 9246

## VIDEO HEADS

JVC/FERGUSON 3HSS	£16.00
SHARP 4HSS	£21.00
HITACHI VT11/14/33	£21.00
HITACHI VT5000	£22.00
HITACHI VT8000/9000	£21.00
UPC1018C	£38.00
UPC1025H	£22.00
UPC1031H	£22.00
UPC1032H	£36.00
UPC1158H	£22.00
UPC1181H	£22.00
UPC1182H	£22.00
UPC1185H	£22.00
UPC1188H	£22.00
UPC1225H	£22.00
UPC1230H	£22.00
UPC1263C	£22.00
UPC1277H	£22.00

# LRC (SPARES)

## VIDEO SPARES FAST ex-stock!

ORDERS BEFORE 4.00 P.M. - SAME DAY DESPATCH!  
LIST PRICES EXCLUSIVE OF VAT  
ORDERS UNDER £50 ADD £1.00 P&P

# 01-388 1714



90B CLEVELAND STREET, LONDON W1P 5DR

VIDEO HEADS REPLACEMENT HEADS	
JVC FERDUSON ETC 3HSS-V	18.50
TOSHIBA 9600	25.10
PANASONIC NV-366 (4 HEAD)	44.50
PANASONIC NV-330 777	38.45
SHARP UNIVERSAL	19.10
SONY SLC5 6 7 8000	25.60
SONY SLC9	39.42
SONY SLC20 30 40 F1	25.50
FISHER FWH-615 ETC.	34.10
SANYO VTC5000 5150 5300	31.60
SANYO VTC9300	31.60

Many More Replacement Heads in Stock

HITACHI ORIGINAL HEADS	
VT5000	5458109 41.65
HT8000 9000	5458161 41.65
VT11 14 33	5458415 44.71
VT6354	5459152 41.65
VT65	5459282 60.84
VT129	5457471 48.15
VT130	5457472 48.15
VT150	5457473 48.15

PANASONIC ORIGINAL HEADS	
NV100 200	VEH0171 41.40
NV180	VEH0252 62.10
NV230	VEH0296 41.40
NV333	VEH0103 41.40
NV366	VEH0174 62.10
NV370 688	VEH0210 62.10
NV777	VEH0177 62.10
NV430	VEH0286 41.40
NV730	VEH0267 62.10
NV788	VEH0201 70.38
NV810	VEH0294 69.11
NV830	VEH0356 70.38
NV850	VEH0265 70.38
NV870	VEH0288 93.84
NV2000 2010	VEH0103 41.40
NV3000 7000 7200 8610	VEH0121 41.40
NV8600	VEH0115 41.40
NV870	VEH0296 41.40
NV910	VEH0287 62.10

SONY ORIGINAL HEADS	
VE180 2630 5030 ETC.	RV 89.46
EV3000 EV5700 (RED OR BLUE)	DVR-04R 88.82
EV3000 EV5700 (GREEN OR BLACK)	DVR-04R(0) 88.82
SL-HF90	OSR-78R 132.26
SL-HF100	OSR-49R 52.36
SL-F1 C20 30 40	OSR-36R 46.60
SL-C9	OSR-21R 48.60
SL-C5 6 7 8000	OSR-36R 48.60

### SONY '5' SERIES UMAT SERVICE KIT 127.60

ORIGINAL PANASONIC VIDEO SPARES	
NV333 366 IDLER	VXP0491 1.24
NV333 366 (PLAY/TAKE UP)	VXP0433 3.06
NV370 430 IDLER	VXP0521 2.56
NV810 30 50 70 IDLER	VXP0515 3.18
NV930 688 IDLER	VXP0581 3.18
NV788 IDLER	VXP0463 3.18
NV2000 SERIES IDLER	VXP0329 1.24
NV2000 (PLAY/TAKE UP)	VXP0331 1.24
NV7000 SERIES IDLER	VXP0344 1.24
NV7000 (PLAY/TAKE UP)	VXP0343 5.76
NV7 G10 IDLER	VXP0521 2.56
P ROLLER NV333 366	VXP0432 8.51
P ROLLER NV730	VXL1154 7.93
P ROLLER BV730	VXL1209 7.58
P ROLLER NV2000	VXP0330 10.56
P ROLLER NV7000	VLP0776 7.85
TENS BAND NV333 66 777	VXZ0129 2.08
TENS BAND NV370 730	VXZ0165 1.95
TENS BAND NV2000 2020	VXZ0076 5.92
TENS BAND NV7000 7200	VXZ0075 3.00
REEL MOTOR NV333 366	MYN13V5L 15.03

ORIGINAL SONY VIDEO SPARES	
F4 & REW ASSY SLC20/30/40/HF100	5.40
GUIDE PIN KIT SLR1 C9/C20/30/40	6.65
DCDC CONVERTER SLC9	22.53
CARRIAGE MOD KIT SLC9	6.40
CARRIAGE COMPLETE SLC9	69.10
UPPER DRUM UNIT SLC9/SLF1	22.75
CAPSTAN MOTOR SLC5/7	33.56
IDLER KIT SLC5/7	4.80
IDLER KIT SLC6	3.68
FWD LIMITER ASSY SLC5/7	2.72
FWD LIMITER ASSY SLC6	3.68
PINCH ROLLER SLC5/6/7	2.48
PINCH ROLLER SLC9/C20/F1/F25/HF100 ETC.	7.85
TENSION BAND ASSY SLC5/6/7	3.48
LOADING PULLEY SLC6	1.80

PLEASE ASK FOR ANY PARTS NOT LISTED

OTHER MANUFACTURER'S ORIGINAL PARTS	
SANYO REEL MOTOR VTC5000	8.97
SANYO REEL DRIVE PULLEY VTC5000	6.50
FISHER IDLER ASSY PMP615	5.97
HITACHI FFR9R ARM VT1133	2.85
HITACHI HMG2 FRAME QP M00	4.50
SHARP REEL MOTOR VC9300 ETC.	17.70
SHARP REEL DR IDLER VC9300 ETC.	2.95
SHARP REEL DR IDLER VC461 ETC.	2.85

### ORIGINAL JVC VIDEO SPARES

CAPSTAN MOTOR HR3660 3V22	24.75
CAPSTAN MOTOR HRD120 3V35	24.75
DRUM MOTOR HR3660 3V22	24.75
TAP IDLER (LARGE) HR3660	5.50
TAP IDLER (SMALL) HR3660	5.50
REEL IDLER HR7200 3V29	1.30
TAP CLUTCH HR7200 3V29	2.20
REEL IDLER HRD120 3V35	2.90
TAP CLUTCH HRD110 120 125	2.90
CASSETTE CARRIAGE 3V45 ETC.	31.28
PINCH ROLLER (ALL MODELS)	3.90

### VIDEO BELT KITS (ORIGINAL)

PANASONIC NV333 366	3.65
PANASONIC NV777 776	2.32
PANASONIC NV230 430 870	1.45
PANASONIC NV370 830 850	1.52
PANASONIC NV688	4.18
PANASONIC NV-2000 SERIES	3.65
PANASONIC NV-7000 SERIES	3.65

### VIDEO BELT KITS (REPLACEMENT)

SANYO VTC-5000	1.65
SANYO VTC-5500	2.10
SANYO VTC-5500	2.20
SANYO VTC-8500	1.78
JVC HR-3330 3360 3660 3V16 22	2.50
JVC HR-7700	2.10
JVC HR-7650	2.10
HITACHI VT11	1.70
HITACHI VT5000	1.30
HITACHI VT8000	2.51
SHARP VCT3000	2.20
SHARP VCS300	2.20
SHARP VCS300	2.20
TOSHIBA 7540	2.80
TOSHIBA 9600	1.80
SONY SLC6	1.85
SONY SLC5/7	2.25

### REMOTE CONTROL UNITS (SONY)

RM604B KV1612 MK12204	28.59
RM615P KV2056 2212/16 2705 ETC.	37.50
RM632 KV2062 96221/16 17 ETC.	28.59
RM641A KV2092/2096	28.59
RM651 KV1442	19.38
RM661A KV218R	28.59
RM711 SL1	37.50
RM7213 SLC9	37.50
RM7216 SLC20 30 40/HF100 GREY	30.44
RM7216 SLC20 30 40/HF100 SILVER	32.49
RM730 SL30	37.50
RM740C EVS60070	37.50

ALL OTHER SONY REMOTES AVAILABLE

### REMOTE CONTROL UNITS PANASONIC

NV333 370	BLACK DR SILVER	10.39
NV366	V500257	11.21
NV370	V500357	30.58
NV777	V500177	30.58
NV7000	V500117B	36.07
NV2000	BLACK DR SILVER	40.66

ALL OTHER PAN. REMOTES AVAILABLE

### GOODIES SELECTION

SONY BETAMAX ALIGNMENT TAPE	36.55
PANASONIC VHS ALIGNMENT TAPE	88.10
SONY V-BATTERY PACKS NP22H	29.86
SONY ECCENTRICITY GAUGE+JIGS	69.51
SONY OPK2038 TEXT BOARD	60.84
OPK113 TB0ARD+LEADS - KV1442	60.84
OPK202A SECAM ADAPTOR	53.20
SONY REM. RUBBER PAD-RM632/6	6.40
TELESCOPIC AERIAL KV1400 1612	7.85
TELESCOPIC AERIAL KV1421 1430	9.34
VIDEO COPYING KIT (UNIV.)	4.25
SCART KIT (UNIV.)	5.60

### MANUALS (0 VAT RATED)

SONY TV MANUALS	6.30
SONY VIDEO MANUALS	10.86
PANASONIC & JVC MANUALS	P.O.A.

### SONY SWITCHES

POWER TV REMOTE (QUOTE MODEL)	4.98
POWER TV NO-REMOTE (QUOTE MODEL)	4.10
POWER KV1421/182 SOLENOID	21.64
TIMER SWITCH C5-7	1.03
RELAY SOUND SLC5/7	4.98

### SONY SEMICONDUCTORS

SG613 SG6533	9.95
SG614	4.98
PSU KIT SLC7	10.86
25C867A	4.15
25C114 - 25C145A	6.40
25C114 TRS. ASSY	7.85
25C1413A	7.47
25C153	5.20
25D1386 25D1397	4.15
25D1398	5.20
25D1497-02 25D1497-06	5.20
SI1225	17.46
TD142129	17.46
TD24578A	3.58
TD3A552	4.98
TD4000	6.40
UPC1355C	10.86
UPC1394C	3.98

### OSCILLOSCOPES

TELEQUIPMENT D83 Dual Trace 50MHz Delay Sweep Large Tube With Manual	£350
COSSOR OSCILLOSCOPE CDU150 Dual Trace 35MHz Delay Sweep Solid State Portable 8 x 10cm Display With Manual NOW ONLY £180 each	
Optional Front Protection Cover containing 2 Probes & Viewing Hood	£10
SCOPEX 4010 Dual Trace 10MHz With Manual S.E. LABS SM111 Dual Trace 18MHz Solid State Portable AC or External DC operation 8 x 10cm display with Manual	£150
TELEQUIPMENT D43 Dual Trace 15MHz With Manual	£100
TELEQUIPMENT S54A Single Trace 10MHz Solid State With Manual	£90
COLLD ADVANCE OS255 Dual Trace 15MHz With Manual	£225
ADVANCE OS250TV Dual Trace 10MHz With Manual	£150
SCOPEX 456 Single Trace 6MHz With Manual	£65

### MULTIMETERS

AVO 8 Complete with Batteries & Leads From	£45
AVO 8 MKV Complete with Batteries & Leads	£90
AVO TEST SET No 1 (Military version of AVO 8) Complete with batteries & leads	£65
TEST LEADS suitable for AVOMETERS. Red & Black with 2 Croc-Clips & 2 Prods. (p&p £3)	£5
Black "Ever-Ready" case for AVOs Unused (P&P £4)	£20

### LABGEAR CROSSHATCH GENERATOR Type CM6038-0B

Crosshatch Grey Scale Blank Raster, Mains or BATTERY	Unused £18. Used £12 (P&P £3)
Marconi AF Power Meter TF893A 20Hz-35KHz 20MW-10W with Manual (P&P £7)	ONLY £35
Marconi RF Power Meter TF1152A 1 DC-500MHz 0.5 to 25 Watts 50 ohm with Manual. (P&P £7)	ONLY £45
MARCONI ATTENUATOR TF2162 DC-1MHz 600 ohm 0-111 Db in 0.1 Db steps. (P&P £7)	£35
HATFIELD ATTENUATOR DC-250MHz 50 ohm 0-100 Db. (P&P £4)	£60
240V In - 240V Out 500VA	£15 each P&P £5
240V In - 240V Out 100VA	£6 each P&P £3
240V In - 24V Out 200VA	£5 P&P £4
240V In - 24V Out 500VA	£6 P&P £5
240V In - 24V Out 100VA	£4 P&P £4

### ISOLATING TRANSFORMERS

USED EQUIPMENT - WITH 30 DAYS GUARANTEE. MANUALS SUPPLIED IF POSSIBLE. This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for Lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to Total of Goods & Carriage.	
240V In - 24V Out 500VA	£15 each P&P £5
240V In - 24V Out 100VA	£6 each P&P £3
240V In - 24V Out 200VA	£5 P&P £4
240V In - 24V Out 500VA	£6 P&P £5
240V In - 24V Out 100VA	£4 P&P £4

### SPECIAL OFFER AT ONLY £300 EACH

TELEQUIPMENT D755 (NATO approved version of D75) DUAL TRACE Delay Sweep 50 MHz.

TRIO RF SIGNAL GENERATOR Type SG402 100KHz-30MHz Unused (P&P £7)	ONLY £75
COLOUR BAR GENERATOR Type PAL MC-101 8 patterns Flick Size. Rechargeable batteries. Complete with Battery Charger/Mains Adaptor. Unused (P&P £4)	ONLY £90
COLOUR BAR GENERATOR Type PAL MC321. 8 patterns. Video Sound Output. Unused (P&P £7)	ONLY £175
LABGEAR FIELD STRENGTH METERS £80 (P&P £7)	£125
DECCA Colour Bar Generator type 82514	£125
PHILIPS COLOURBAR GENERATOR type 5508. Video Output. Many functions.	£150
Labgear Colour Bar Generator KG1 8 Test Patterns. Unused (P&P £4)	ONLY £40 each
ADVANCE SG62B. AM. 150KHz-220MHz (P&P £7)	£45

### AVO TRANSISTOR ANALYSER MK 2 (CT446)

Suitcase style. Complete with batteries & operating instructions. ONLY £25 each (P&P £7)

### AVO VALVE TESTER CT160

Suitcase style. 22 Bases. (P&P £7) ONLY £25 each

### NEW EQUIPMENT

HAMEG OSCILLOSCOPE 604. Dual Trace 60MHz. Delay Sweep. Component Tester & 2 Probes	£575
HAMEG OSCILLOSCOPE 203.6. Dual Trace 20MHz. Component Tester & 2 Probes	£314
All Other Models Available.	
BLACK STAR FREQUENCY COUNTERS P&P £9	
Meteor 100-100MHz	£99
Meteor 600-600MHz	£126
Meteor 1000-1GHz	£175
BLACK STAR JUPITOR 500 FUNCTION GENERATOR. Sine/Square/Triangle. 0.1Hz-500KHz P&P £4	£110
BLACK STAR ORION. PAL TV VIDEO COLOUR PATTERN GENERATOR	£199
HUNG CHANG DMH 7030. 3 1/2 digit. Hand held 28 ranges including 10 Amp AC/DC 0.1%. Complete with batteries & leads. P&P £4	£39.50
AS ABOVE. DMH 6010. 0.25%. P&P £4	£33.50
CARRYING CASE FOR ABOVE	£3 each
OSCILLOSCOPES PROBES. Switched x1: x10. P&P £3	£11

# APOLLO LANCASHIRE

## NATIONWIDE MAIL ORDER

### LOCAL DELIVERY - 2 YR GUARANTEE

A47 342/343X - 470 BC822/CTB22/BGB22/	£39
470-ESB22/EFB22/ERB22/FTB22	£56
A51-220X/192X	£39
A51-161X/162/163/168	£56
510-JKB22/JEB22/JDB22/JGB22/ALB22/GLB22	£56
510-VLB22(E55) DTB22/001/RFB22/RCB22/SFB22	£56
A51 590 New	£56
A51 570X/580/001/210/241	£56
A56-120X/123/140/410	£39
560-DZB22(E56)/HB22/AKB22/TB22/AWB22	£55
560-ETB22/DTB22/CSB22/DMB22/DNB22	£56
A56-611X/615X	£56
A66-120X/A67-120X/140/150/200/410	£39
20AX - A56-500X/510X - A66-500X/510X	£56
30AX - A56-540X - A66-540X	£56

## PHONE FOR QUOTE

### SONY TYPES £69

470DLB22/FWB/KHB/KTB	
KL8-520SB22/NB/RB/XB	
A49JHT00X-570DB22/EB/HB	
GB/JB-A53JBW01X/JCJG00X	
JB00X-680CB22/DB/EB	
14" PORTABLES £59	
3708UB-AXT37001-	
37-550/2/3/4-A37-570/580/590	
CASH PAID FOR ALL SIZES SONY GLASS + 66-510/540 560 DZB PIL TYPES	

PLEASE PHONE BEFORE CALLING  
LOCAL DELIVERY FROM ACCRINGTON, LANCs.  
Phone enquiries and letters to:  
**Apollo, The Potters Wheel,**  
Mullion Cove, Mullion, Nr. Helston, TR12 7ET.  
0326 240781

## POST-A-PART

ELECTRONICS

TRANSISTORS

DIODES

CAPACITORS

TRANSFORMERS

RESISTORS

VIDEO SPARES

TUNERS

INTEGRATED CIRCUITS

SEND FOR CATALOGUE (S.A.E. PLEASE)  
TELEPHONE ORDERS, MAIL ORDER, OR CALL AT SHOP  
126 HIGH STREET, CANVEY ISLAND, ES

# MARSTALL LTD

TV & VIDEO WHOLESALERS

38 HORNSBY SQUARE SOUTHFIELDS IND. ESTATE, LAINDON, ESSEX

**FOR A LARGE SELECTION OF  
RECONDITIONED EX-RENTAL  
THORN TVs + VIDEOS  
PLUS MANY OTHER MAKES AT  
MOST COMPETITIVE PRICES**

NEW & SECOND HAND SPARES ALSO AVAILABLE


QUANTITY  
DISCOUNTS

**OPEN 9 a.m. - 6 p.m.  
MONDAY - SATURDAY**





DELIVERY SERVICE  
THROUGHOUT UK

*OUR STAFF ARE FAMILIAR WITH EXPORT REQUIREMENTS AND  
WOULD WELCOME YOUR ENQUIRIES.*

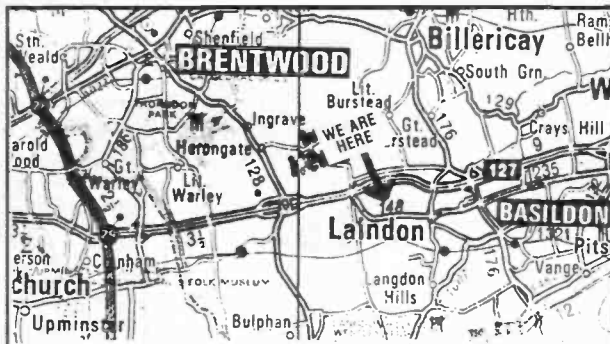**COME AND PAY US A VISIT  
AT OUR NEW LARGER  
PREMISES**



(JUST OFF M25  
JUNCTION 29)

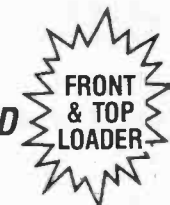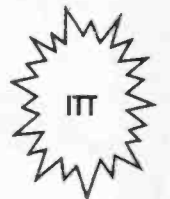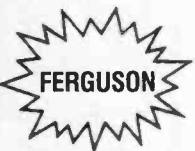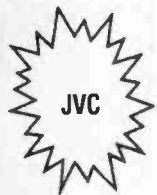

**Don't Delay Phone TODAY!  
0268-412711**





# WILTSGROVE LTD

28-29 RIVER STREET  
DIGBETH  
BIRMINGHAM 5

Tel: 021-772-2733  
FAX: 021-766-6100



**MERRY XMAS HAPPY NEW YEAR**

To all our Customers

Export Enquiries are Welcome

YOU'LL HAVE TO SEE US TO BELIEVE US !!

### VIDEO RANGE

AMSTRAD - AKAI - FERGUSON - HITACHI  
JVC - MITSUBISHI - SHARP - PANASONIC



Ex. Rentals  
Graded T.V.'s  
and Video's  
Stereo T/T  
Graded T/T  
Ex. Demo.  
Portables

IF YOU'RE TIRED OF BEING OFFERED BUTCHERED JUNK LOOK NO FURTHER CALL OR VISIT SATISFACTION GUARANTEED


**A SUPERB CHOICE OF ELECTRONIC VHS**

TV RANGE  
BUSH - DECCA - PHILLIPS - PYE - GRUNDIG  
GEC - FERGUSON - TOSHIBA - Also Portables



BRAND NEW  
14" Colour  
with  
UHF/VHF Tuner  
Only £95.

TELETEXT TV -  
From only £40.

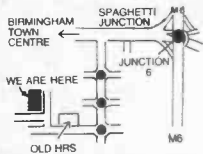


**HUGE STOCKS  
WORKING & GENUINE  
UNTESTED TV'S & VCR'S,**

ALL OFFERS  
ARE SUBJECT  
TO V.A.T. &  
AVAILABILITY  
CASH ONLY

NEW LIFE THORN 1  
9K tubes available  
with guarantee for  
only £15.

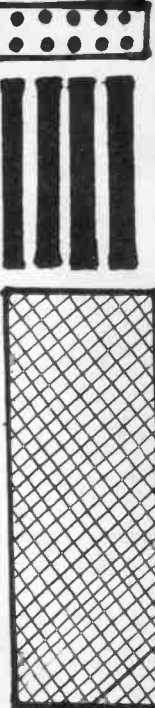EX RENTAL N.E.C  
Complete Satellite  
systems at keen  
prices



Thousands of  
late models  
also available  
Direct loads  
from source  
at low prices

## Universal Semiconductor Devices Ltd.

UNIT 4, SPRINGFIELD ROAD,  
CHESHAM, BUCKS. HP5 1PU, ENGLAND.



TEL. 0494 791289/TELEFAX. 0494 791296

TELEX 837707 usdco g

WE OFFER ONE OF THE LARGEST RANGES OF SEMICONDUCTORS AT HIGHLY ECONOMICAL PRICES. THE FOLLOWING SEMICONDUCTOR TYPES ARE AVAILABLE FROM STOCK. IF WE DON'T STOCK WHAT YOU NEED THEN WE CAN GET IT FAST FROM OUR FACILITIES IN WEST GERMANY AND USA UPON REQUEST.

TRANSISTORS - BIPOLARS - GERMANIUM AND SILICON  
SMALL SIGNAL  
POWER  
DARLINGTONS - ALL SHAPES AND SIZES  
VHF/UHF DEVICES - ALL SHAPES AND SIZES

FETS - POWER MOSFETS  
UNIUNIONS



DIODES - GERMANIUM AND SILICON  
RECTIFIERS AND BRIDGES  
OPTO-ELECTRONIC DEVICES  
LEDS OF ALL SHAPES AND SIZES



THYRISTORS AND TRIACS - ALL



SHAPES  
SIZES  
RATINGS

INTEGRATED CIRCUITS:  
CONSUMER - DIGITAL/ANALOGUE  
MICROPROCESSORS AND PERIPHERALS  
IC SOCKETS



**JAPANESE  
COMPONENTS**  
VAST RANGE HELD OF  
DISCRETES &  
CONSUMER  
IC'S

### CATALOGUE

Please send £1 cheque, postal order or stamps for 1988 catalogue. The catalogue is sent free of charge to all schools, Government Institutions and businesses when requested on official letterhead.

PLEASE ENQUIRE FOR QUANTITY DISCOUNTS.

WE WELCOME TELEPHONE, TELEFAX AND TELEX ENQUIRIES!

# REBUILT COLOUR TUBES

Delta - 20AX - 30AX - In Line

**N.G.T. ELECTRONICS LTD.**

120, Selhurst Road, London SE25 6LL

**PHONE: 01-771 3535**

First Independent Rebuilder with B.S.I. Certification

## RELAY

OMAGH LTD

COMPUTER SOFTWARE

### DO YOU RENT TELEVISIONS?

DO YOU STILL USE A CARD SYSTEM?

DO YOU FIND IT DIFFICULT TO KNOW YOUR ARREARS TOTAL AT ANY GIVEN TIME?

If you do then we recommend our new computer TV and Video Rental package. This package includes

- ★ automatic updating of each customer's record
- ★ alphabetical print-out of each customer's arrears and payments missed
- ★ total arrears immediately available
- ★ easy to use and operate.

Operates on all IBM compatibles running under MS-DOS. Free demonstration disc available.

# CONTACT


**WILLIAM J THOMPSON**  
Donaghane Post Office  
Beragh Co. Tyrone  
Telephone Beragh 214 (0662 72)

# CENTRAL

LONDON  
LEICESTER

TV & VIDEO WHOLESALE (UK) LTD.  
BIGGEST SELECTION - KEENEST PRICES

BIRMINGHAM  
BOLTON

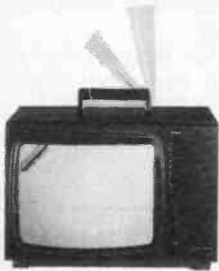


14" COLOUR PORTABLE  
8 CHAN - UHF - VHF

PRICES BASED  
ON QUANTITY



HUANYU

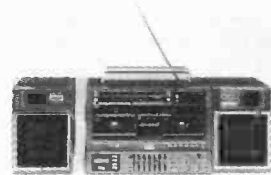

STEREO PORTABLE COMPO - TWIN  
CASS - HI SPEED DUB - APLD -  
BUILT IN MIC - AUTO PROG SEARCH -  
7 BAND GRAPHIC - L.C.D. SLEEP  
CLOCK - SIX SPEAKERS -  
MW/FM/SW1/SW2



HI-GRADE TAPES  
FULLY-GUARANTEED

A newly appointed Huanyu distribution for Huanyu Electrical Limited. Stocking the full range of products from colour televisions, audio units, VHS Video Tapes, batteries etc . . . Stock immediately available at very attractive prices. Next year Video's and Microwaves.

**EXPORT ORDERS REQUIRED FOR THESE GOODS**

## EX-RENTAL T.V. & VIDEO — ALL TOP MAKES IN STOCK

RECONDITIONED - GENUINE OFF THE PILE - GRADE 'B' - NEW - YOU CANT BUY BETTER

**DIRECT TO TRADE PRICES DELIVERY FROM SOURCE**

WORKING TVs	WORKING VHS VIDEO	NEW AND 'B' LINES NOW IN STOCK
Basic Thorn/Granada £15 From: FERG, GEC, ITT, DECCA, PHILIPS, DORIC, FINLANDIA etc. Thorn 9.6k £15 TX9/10 STEREO TEXT IN STOCK TX Text from £50 Text Sets from £35 Grundig from £35 Portables from £45 Sony from £55 KT3/30 from £35	Basic Electronic Thorn/Japs £65 Mechanical £50 Beta £25 IN STOCK 3V23/29/30/40/31/32/35/38 3V43 - STEREO - HiFi - 2 SPEED Sharps 7.3/8.3/9.3 Hitachi VTH/8.3/9.3 Panasonic 333/336/7.2/777 Akai VSI/VS2/VS4 and many more	Slim F/L Basic/Remote £120 14" Colour Portable £95 20" ITT Remote P.O.A. 20" Remote/Monitor Style P.O.A. BW Portable £26 Microwave Ovens from £45 Ferguson 22B5 Professional Series P.O.A. Ferguson 59B7 F.S.T. P.O.A. Finlux 28" F.S.T. P.O.A. Luxor F.S.T./Solara P.O.A.
Prices based on availability - quantity + 15% VAT.	Mercury Telecraft Set Top Aerials & Audio Video Accessories	NEW THORN HEADS £15.00 NEW HANDSETS £9.50

FOR SINGLE OR BULK PURCHASES - CALL US NOW,  
LOCAL AND DISTANT DELIVERY SERVICE AVAILABLE

**AGENTS REQUIRED**

FOR THE UK AND FOR EXPORT

BULK  
ENQUIRIES ETC.  
HEAD OFFICE:

C.T.V. LONDON  
Eley Estate, Noble Rd,  
Edmonton N.18  
01-807 4090, 01-884 1314

C.T.V. BOLTON  
Nile St., Unit 1,  
Bolton, Lancs.  
0204 384 868

C.T.V. LEICESTER  
St. Georges Mill,  
Humberstone Rd. LE1  
0533 515299

C.T.V. BIRMINGHAM  
369 Stratford Rd,  
Sparkhill B11  
021 772 1591

## SETS & COMPONENTS

UNTESTED TV's VIDEOS from £5. Video 2000. spares services working from £29.95. New tapes. Phone 0354 8304.

OCHRE MILL TECHNICAL SERVICES are now on 0666 (Marlmesbury) 823228. Grundig TV spares. all models to 1983. Fast, friendly, helpful service, sensible prices.

BUSH T20-22-26 PANELS Repairs/Exchange Service. Ring Letchworth 0462.

JAPANESE TV'S MITSUBISHI. Panasonic. Sony. JVC. Toshiba, fully refurbished. PEARSON TELEVISION 0484 863489. Delivery arranged.

## WIZARD DISTRIBUTORS MANCHESTER TV & VIDEO SPARES

We stock spares for PHILIPS, PYE, RANK, GEC, SHARP, SONY, HITACHI, HINARI & DECCA

And also THORN & ITT FIDELITY SPARES MAIN DISTRIBUTOR.

Did you know we also stock

FUSES	I.Cs
TUBES	TOOLS
AERIALS	VIDEO LEADS
AEROSOLS	AUDIO LEADS
RESISTORS	SEMICONDUCTORS
CAPACITORS	SERVICE MANUALS
VALVES	TEST EQUIPMENT
HANDSETS	TV/VIDEO TROLLEYS
VIDEO HEADS	TELEPHONE ACCESSORIES

Counter open Monday-Friday 9am-4.45pm  
Mail Order-Access/Visa

### TRADE ONLY

EMPRESS STREET WORKS,  
EMPRESS STREET,  
MANCHESTER M16 9EN.

Tel: 061-872 5438; 061-848 0060.

# TELEVISION

No other consumer magazine in the country can reach so effectively those readers who are wholly engaged in the television and affiliated electronic industries. They have a need to know of your products and services.

The prepaid rate for semi display setting £8.50 per single column centimetre (minimum 2.5cms). Classified advertisements 55p per word (minimum £10),

## HALTON TV TRADE DISPOSAL

# NOW!

WORKING TVs AND  
UNTESTED  
WORKING FROM £15.00

Mon-Fri 10-5  
Sat 10-1

St Michaels Industrial Estate, Widnes  
Tel. 051 423 1577

## ADMIN TELEVISION

PHILIPS G11 BASIC  
£14 INC

PYE G11  
£16 INC

TX9/10s K30/KT3  
£25 INC

WKG PAN RC/TEXT  
FROM £70 INC  
WORKING F/LOAD VIDEOS  
£105 INC

ELECTRONIC TVs  
FROM £5

PHONE 051-548 4414  
UNIT J, ADMIN BUILDINGS,  
KIRKBY, LIVERPOOL L33 7JX

# INDEPENDENT TELEVISION & VIDEO CO.

DON'T TRAVEL THE COUNTRY LOOKING AT "BUTCHERED JUNK". ALL OUR COLOUR TELEVISION'S & VIDEOS ARE IN EXCELLENT CONDITION, WITH UNMARKED CABINETS AND ARE SUPPLIED WITH REMOTE CONTROL. WE ALWAYS HAVE 1000s IN STOCK OF ALL FAMOUS MAKES. WE DON'T JUST SAY THAT - SEE FOR YOURSELF AT YOUR LOCAL BRANCH. FRANCHISES NOW AVAILABLE WITH MINIMUM INVESTMENT

### BULK PURCHASE:-

V.H.S. Electronic Working	From £75.00	Mechanical V.H.S. Video's Untested	£35.00
V.H.S. Electronic Untested	From £55.00	Mechanical V.H.S. Video's For Spares	£25.00
V.H.S. Electronic For Spares	From £35.00	All Beta Videos	From £10.00

WE ARE EXPERIENCED IN EXPORT MARKET REFURBISHED TELEVISIONS & VIDEO'S  
Enquiries welcome C.I.F. & F.O.B. Prices - Telex: 378414 BLBIRDG - Fax: 0602 861027

TELEVISIONS	CTV'S WORKING FROM £8	WORKING	UNTESTED
Thorn 9000	.....	£20.00	£15.00
Thorn 9200	.....	£25.00	£18.00
Thorn 9600	.....	£25.00	£18.00
Thorn TX9-TX10	.....	£50.00	£40.00
Decca 80 & 100	.....	£20.00	£15.00
G.E.C.	.....	£20.00	£10.00
I.T.T. R/C	.....	£30.00	£20.00
Philips G11 & Pye G11	.....	£28.00	£18.00
Philips G11 & Pye G11 Text with Handset	.....	£55.00	£45.00
KT3	.....	£50.00	£40.00
KT3 Text with Handset	.....	£70.00	£45.00
KT35	.....	£55.00	£45.00
KT35 Text with Handset	.....	£90.00	£65.00
TX9 & TX10 Text with Handset	.....	£70.00	£60.00
Grundig	.....	£55.00	£45.00
Grundig Text with Handset	.....	£90.00	£65.00
I.T.T. - Ferguson Stereo Text	.....	£130.00	£105.00

PLUS MANY MORE LATE MODEL T.V.'s TOO LONG LIST TO LIST THEM ALL - ALL PRICES ARE PLUS 15% VAT.

### NOTTINGHAM

(10,000 SQ. FEET WAREHOUSE)  
UNIT 3-3A MEADOW TRADING EST.  
MEADOW LANE  
NEAR NOTTS. COUNTY FOOTBALL GROUND  
IN NATIONAL TYRE YARD, NOTTINGHAM NG2 3WQ.  
TELEPHONE: (0602) 864627

### SHEFFIELD

(6,000 SQ. FEET WAREHOUSE)  
2 MIN FROM JUNC. 34 OF THE M1  
UNIT 17, MEADOWHALL TRADING EST.  
27 AMOS ROAD, SHEFFIELD 4  
TELEPHONE: (0742) 422633

# SERVICE PAGES

box number £1.00 extra. All prices plus 15% VAT. All cheques, postal orders etc., to be made payable to Television, and crossed "Lloyds Bank PLC". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Television Room 2331, IPC Magazine Limited, Kings Reach Tower, Stamford Street, London SE1 9LS. (Telephone 01-261 5942).

## F.T. SERVICES

QUALITY WORKING TV'S  
AND VIDEOS TO INCLUDE

9600's .....	£25
TX9's, TX10 Basic .....	£40
TX Teletext .....	From £70
TX Stereo Text .....	£95
VIDEO'S 3V29/30 .....	£75
3V23/8940 .....	£75
NEW H/UNITS, eg. Tx Text .....	£12
NEW HEAD, eg. JVC J/L .....	£14.50
VIDEO STAND .....	From £5

Also Sony, Pan, Philips, Pye, Hit etc. available

ALL PRICES PLUS VAT

779 STOCKPORT ROAD,  
LEVENSHULME,  
MANCHESTER  
Telephone: 061-224 7279  
061 224 6521

Open

Mon./Fri. 10-8  
Sat. 10-6



## LINCOLNSHIRE AREA


FED UP WITH TRAVELLING FAR AND WIDE FOR YOUR EX-RENTAL TV AND VIDEO'S?



THEN WHY NOT TRY US FIRST?
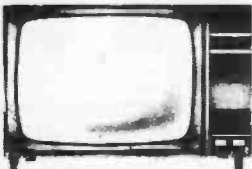
### BUDGET TV

Unit 4,  
Exchange Road  
Lincoln LN6 3JZ  
Tel.  
Lincoln 500413



## REPAIR YOUR OWN HI-FI SPEAKERS

Send large stamped addressed envelope for catalogue of replacement drive units from stock to:

### RTVC LTD.

21 High St., Acton, London W3 6NG.  
Tel: 01-992 8430  
and 323 Edgware Rd., London W2.  
Tel: 01-723 8432

**RCS VARIABLE VOLTAGE D.C. BENCH POWER SUPPLY**  
1 to 24 volts up to 1/2 amp. 1 to 20 volts up to 1 amp. 1 to 16 volts up to 1 1/2 amps A.C. Fully stabilised. Twin panel meters for instant voltage and current readings. Overload protection.

Fully variable.  
Operates from 240V A.C.  
Compact Unit.  
size 9x5 1/2x3ins.



£39 incl. VAT + Post £2.

### RADIO COMPONENT SPECIALISTS

ACCESS 337 WHITEHORSE ROAD, CROYDON SURREY, U.K. Tel: 01-684 1665 VISA  
List, Large S.A.E. Delivery 7 days Callers Welcome Closed Wednesday

Colour TVs from  
Clean and tidy

£5 each

G11s

20" 22" & 26"

FROM

£12

KT3

FROM

£25

Philips and Pye types

Teletext

FROM

£30

Always around 200+ fully working colour TVs and Videos available. All in clean condition and ready for immediate sale or rent.

Phone us for models available today.

**Cash sales only**

Prices based on quantity plus VAT

Video 2000 system FROM £15

Phone for availability

Video Beta

FROM

£8

VHS Video

FROM

£20

Spares machine electronic

Electronic VHS

FROM

£50

Various makes — changing daily

## GENERAL FACTORS

UNION STREET, DONCASTER, SOUTH YORKS  
Excellent motorway access from M1, M18, A1M

**0302-349583**

(24 hour Ansaphone Service)


**THE**  
**Stun**

★  
**WORLD  
EXCLUSIVE**  
★
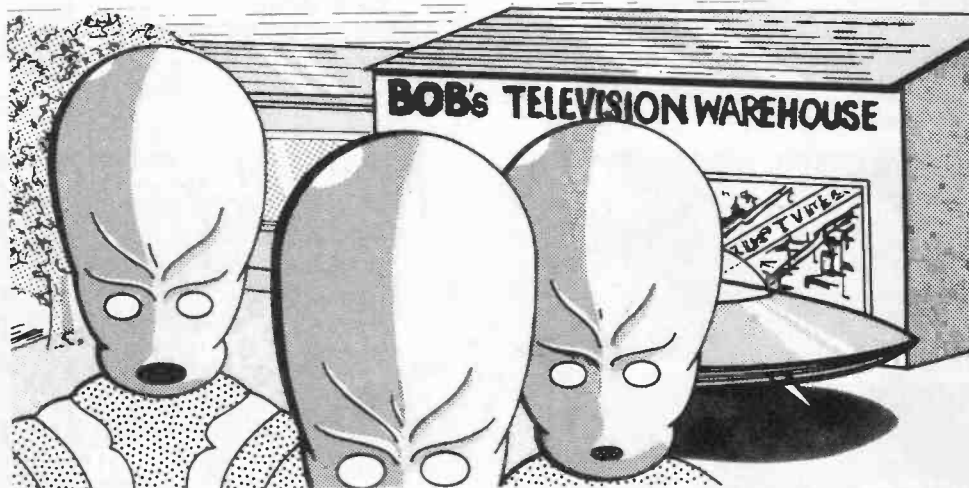
# ALIENS SEEN IN BASILDON

A space ship was seen today outside a local television warehouse in Basildon.

Passers by were held spellbound by the sight of three space aliens appearing from within the store, carrying what appeared to be Television sets and video recorders.



**BOBS**  
*Television Warehouse*  
**PROBABLY  
THE LOWEST PRICES AROUND  
FOR ALL LEADING MAKES OF  
TELEVISIONS & VIDEO RECORDERS**

WE CARRY A LARGE RANGE OF  
"OFF THE PILE" TO FULLY  
REFURBISHED READY TO  
INSTALL UNITS.

TEL: Basildon  
(0268) 728966

**LARGE DISCOUNTS  
FOR QUANTITY  
PURCHASES!**

In an exclusive interview with one of the aliens, our reporter was told that they had travelled a great distance across our galaxy to this particular T.V. store, because as they said "Bobs T.V. & Video deals cannot be beaten". They were also particularly impressed by the large selection of reconditioned sets

The Alien went on to say that as a main dealer for T.V. equipment on his

own planet Trinitron, he found that the trip to earth was justified and rewarding due to the amazing deals he found at Bobs.

Two of the aliens were also impressed by the variety of makes including Ferguson, Philips, National Panasonic, Hitachi, Sharp, Grundig etc. plus B grade Philips machines.

**1 Swinborne Court,  
Burnt Mills Ind. Est  
Basildon, Essex SS13 1QA.**



# NORTH WEST ELECTRONICS

## XMAS STOCKS NOW IN!

GOOD SELECTION OF THORN TV'S & VIDEOS FROM STANDARD TO STEREO TEXT AT KEEN PRICES!

### WORKING TV's

Bush T20/22, T24/6 .....	£25
Pye G11 .....	£25
Pye KT3 .....	£35
Pye K30 .....	£40
Ferguson TX 9/10 .....	£40
Grundig .....	£20
Hitachi 226 etc. ....	£55


### WORKING VIDEO's TRY BEFORE YOU BUY!

Sharp Electronic 7300 ...	£65
Ferguson 3V29 .....	£75
Sharps 8300 .....	£80
National Panasonic .....	£75
Ferguson 3V30 .....	£80
Sharp 9300 .....	£95

## BRADFORD

SPRING MILL STREET,  
MANCHESTER ROAD,  
BRADFORD 5  
5 MINS FROM MOTORWAY

**NORTH  
WEST  
ELECTRONICS**

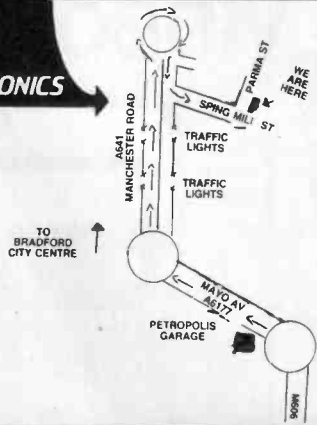

**QUANTITY OF BRAND  
NEW TOWER SYSTEMS,  
MIDI SYSTEMS,  
PERSONAL RADIOS  
ETC — TERRIFIC  
FOR CHRISTMAS**

### IN STOCK NOW

K35/K30 TEXT  
TX10 & HITACHI TEXT

### TELETEXT BARGAINS

**FROM  
£60**

### WORKING EX-EQUIPMENT PANELS

IF	Con- verger	De- coder	Line scan	Power	Frame
T20/22X	5	14	18	17	14
T26 X	5	16	20	17	X
718	7.50	5	14	20	3 14.00
Philips					
G11	14.50	5	12	20	20 11.50

All prices include Postage & Packing.  
But + VAT

### TRADE SHOWROOM

LARGE QUANTITY OF READY TO  
SELL VIDEO's & TV's

CALL IN, YOU WILL BE  
DELIGHTED!

### LATER VIDEO's NOW IN STOCK

3V35/44/65, Hitachi VT33  
Philips 6660/64, UR 60,  
AND MANY MORE

100's PX  
HOOVER JUNIOR  
VACS

All models in stock

### UNTESTED TV's

Bush T20/22 .....	£15
Pye G11 .....	£15
Pye KT3 .....	£30
Pye K30 .....	£35
Ferguson TX9/10 .....	£30
Grundig .....	£10
Hitachi 226 etc. ....	£35
Thorn 9000 .....	£10

Plus many more; GEC, ITT,  
etc from £5

### UNTESTED VIDEO's

Sharp 7300 .....	£35
Ferguson 3V29 .....	£50
Sharp 8300 .....	£50
National Panasonic .....	£45
Ferguson 3V30 .....	£55
Sharp 9300 .....	£55
Betamax all makes from	£10

## MANCHESTER

UNIT 3,  
MERSEY ROAD NORTH  
INDUSTRIAL ESTATE,  
FAILSWORTH



Tel (0274)

308186

ALL PRICES ARE PLUS VAT & BASED ON QUANTITY

CHEQUES  
ACCEPTED WITH  
BANKERS CARD

ACCESS/VISA  
WELCOME

OPEN

6 DAYS  
SAT 9-5.30

Tel

(061-683)  
4612

# DHOUPER'S TVs




Seasons  
Greetings

UNIT 3, ARMOURY ROAD,  
SMALL HEATH INDUSTRIAL ESTATE,  
SMALL HEATH, BIRMINGHAM. 021 772 2743

**OVER 1,000 TVs & VIDEOS IN STOCK**



**NOW**

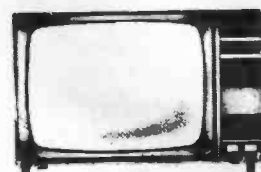

**Mechanical Videos**

**From £25**

**Front Loading Videos**

**From £50**

**Text TVs**

**From £45**

**Portable TVs**


**From £40**

★ **NEW STOCK WEEKLY** ★

**GET YOUR TVs AND VIDEOS**



**NOW FOR**

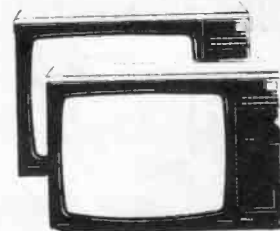

**CHRISTMAS,**

**WHILE STOCKS LAST**





# NEWCASTLE UPON TYNE

## COLOUR TELEVISIONS

THORN-8,800  
9,000  
9,600  
TX9-TX10

DORIC-MK1, MK111, M4.

PHILIPS-G11, KT3, KT30.

ITT-Various Models.

GEC-Various Models.

## VIDEOS

THORN-3V23  
3V29  
3V30

NAT PAN-Various Models.

HITACHI-Various Models.



TRADE WORKERS ALWAYS AVAILABLE

# P.V.S.

35, Nunsmoor Road, Fenham,  
Newcastle-Upon-Tyne.

Phone: (091) 2722 303

VIDEOSPOT  
T/A

# TRADE TV'S

NOW OPEN

GOOD NEWS FOR SCOTTISH TRADERS.  
WE ARE A NEW INDEPENDENT WHOLE-  
SALER OF QUALITY EX-RENTAL, BANK-  
RUPT, AND SURPLUS STOCKS OF TV'S  
AND VIDEO'S.

THE PRICES ARE RIGHT, VERY COMPETI-  
TIVE, THORN AND NON-THORN RANGE.

*Workers or non-workers.  
Fresh stocks every week.*

Why not pay us a visit  
Prices based on quantity.  
All prices subject to 15% V.A.T.

**TRADE TV'S (near the Barra's)**  
239 LONDON ROAD, GLASGOW.  
Telephone: 041 553 1714

# MIDLAND TELEVISION

QUALITY SETS SINGLES OR QUANTITY SUPPLIED AT THE BEST PRICES

## C.T.V.

## VHS

Phillips	Non Working	Working	Ferguson	Non Working	Working
G11 Text	£35.00	£50.00	3V23	£55.00	£80.00
G11 Basic	£12.00	£20.00	3V30	£55.00	£80.00
KT3 Text	£50.00	£68.00	R/C 3V31	£60.00	£85.00
KT30 Text	£55.00	£75.00	R/C 3V35	£65.00	£90.00

THORN	Non Working	Working
880	£5.00	£11.00
9000 R/C	£12.00	£18.00
9600 R/C	£14.00	£20.00
TX9-TX10 Text	£55.00	£70.00
TX9-TX10 R/C	£30.00	£45.00
TX9-TX10 Basic	£25.00	£40.00

SHARP, HITACHI, ETC FROM:  
Non Working £55.00, Working £80.00

### SPECIAL OFFER

Buy 15 or more of any above  
and receive 10% reduction  
i.e. 15 x 3V30 in full  
working order £72.00 + VAT

PRICES SUBJECT TO VAT  
ALL SETS QUOTED AND SUPPLIED  
WITH HAND SETS

15 MIN M1 JUNC. 22  
Nationwide Delivery Service Available  
UNIT 11, MARKET STREET,  
COALVILLE, LEICESTERSHIRE  
TEL: 0530-810836/7

## T.V. SPARES, PANELS AND MANUALS PHILIPS

TELEVIEW 01-994 5537  
194, Acton Lane, London W.4.

### JOMILL ENTERPRISES

173 Dalston Lane, Hackney, London E8

VHF/UHF Televertas £22.50

Quantities P.O.A. Ceramic filters for UK and  
export conversion NTSC decoder for replace-  
ment of Chip TDA3560/1 £47.50

Add cost of posting and packing.

## SUFFOLK TV & VIDEOS

Large stocks always available

GEC, Fineline KT3, KT30, Hitachi,  
Nat Pan, working stocks in our  
showroom from £20.00.

Text £85.00 with handset.

**0934 670115**

Bridge Road, Felixstowe,  
Suffolk IP11 7FL

# REBUILT TV TUBES

DIRECT FROM THE FACTORY  
WHERE THE BEST COSTS LESS

## FINEST QUALITY LOWEST PRICES

### SPECIAL DISCOUNTS FOR BULK BUYERS

2 YEAR GUARANTEE, 4 YEAR OPTIONAL

ALL MAKES INC. SONY  
NATIONWIDE DELIVERY

### PHONE NOW FOR FREE LISTS

## SHERWOOD TUBES LTD

60A PEVERIL STREET, NOTTINGHAM NG7 4AH.  
Tel. 0602 786896

## C.T.V.

2 NORTON ROAD, STOURBRIDGE,  
WEST MIDLANDS - 0384 390706

QUANTITIES AVAILABLE 9k 9.6 TX9,  
TX10 TELETEXT.

Portable complete range of VHS, also quantities of  
Philips, GEC, ITT and Japanese CTV's.

DIRECT LOADS AVAILABLE.

All at Competitive Prices.

### Telephone: 0384-390706

## PICTURE TUBE REPAIR EQUIPMENT BMR 90

Versatile and reliable.  
Although many things have  
become cheaper, picture  
tubes are still expensive. So  
utilize tubes fully by using our  
new generation machine.

- Regenerates picture tubes  
even better · Also IN-LINE ·
- Removes short-circuits,  
even between cathode and  
filament · Measures beam  
current, emission current, life  
expectancy, etc.

can pay for itself in 4 weeks, if you are not using BMR 90  
you are making less profit than you could.

BLE IDOWN LIMITED, Bank House, 17 Rhos Road,  
Rhos on Sea, Clywd, Wales

Fax (0492) 47880

Telex 21506 ULTCU TG



COPY  
DATE  
FOR  
FEBRUARY  
ISSUE  
PUBLISHED  
JANUARY  
IS  
14th DEC

FOR  
FURTHER  
INFORMATION  
ON SERIES  
DISCOUNTS  
AND RATES  
CALL PAT  
01-261 5942  
CLASSIFIED

**D.I.Y. SCRATCH REMOVAL + TUBE POLISHING KIT**  
First class results can be obtained every time  
with this kit. The kit, which comes with full  
instructions is especially useful on ex-rental  
work for those sets with excellent cabinets  
and good but scratched tubes which may be  
had at very much reduced prices. The kit could pay for itself  
with your first job!  
Introductory price £35 inclusive Electric drill required  
**PC TV SERVICES**  
8 ORCHARD CLOSE TEL. 0920 871474 \* MAIL ORDER \*  
Stanstead Abbots, Herts SG12 8AH \* CALLERS STRICTLY  
BY APPOINTMENT \*

**NEW AND SECONDHAND**  
TV - VIDEO - RADIO SPARES, PANELS AND  
COMPONENTS, NEW RECORD DECKS, TRAN-  
SCRIPTION AND AUTOCHANGE £10 EACH. VA  
214 NICAD BATTERIES 12 VOLT £16 EACH.  
VIDEO HEADS £15 EACH.  
Ring Southport (0704) 76828  
(ANYTIME 24 HRS 7 DAYS)

Thorn 3000/3500  
Thorn 9000  
**UNIVERSAL**  
1 year guarantee

**TRIPLERS** inc. p&p  
**£4.95**

The UNIVERSAL TRIPLER can be used in most  
G.E.C., I.T.T., Pye, Rank, Decca & Continental sets.  
**WING ELECTRONICS**  
15 Waylands, off Tudor Rd., Hayes End, Middlesex

## AERIALS

**SATELLITE TV  
RECEPTION EQUIPMENT**

LNB's, Receivers, Dishes, polar mounts and  
accessories.

Japanese LNBS from	£95.00
Japanese RX from	£169.00
Ku Band feedhorns from	£5.99
'F' Connectors only	0.20
'N' - 'F' Adaptors only	£1.40
10db line amps only	£12.00
Prices excl. VAT. SAE for leaflets.	

**DX ANTENNA**

**KESH ELECTRICS LTD.**  
Main St., Kesh, Co. Fermanagh, N.I.  
Tel: 03656 31449 Tlx: 747412

**The Theory and  
Practice of PAL Colour  
Television in three  
important Video  
Cassette Programmes**

Part 1.  
**The Colour Signal**

Part 2.  
**The Receiver Decoder**

Part 3.  
**Receiver Installation**

VHS★★★★V2000★★★  
BETAMAX★★★★UMATIC

For full details telephone  
0253 725499 (Day)  
0253 712769 (Night)

Or send for precise details  
**FLINTDOWN CHANNEL 5**  
339 CLIFTON DRIVE SOUTH,  
LYTHAM ST ANNES FY8 1LP  
(including this advert)

NAME.....  
ADDRESS.....  
TEL:.....

## METERS

**METERS.** Reconditioned 10p/50p available from stock. Contact THE METER CO. (Poole) LTD. (0202) 683498.

### AVON METERS

**50p or £1 TV meters from £5.95 each plus V.A.T.**

(Discount for Quantity)

We also repair and buy unwanted meters.

1 Year Guarantee - Phone now:

28 Station Road,  
Yate, Bristol BS17 5HW  
Tel. 0454 321953

## WANTED

### SURPLUS/REDUNDANT ELECTRONIC COMPONENTS WANTED

I/Cs - Tuners - Transistors - Valves - Diodes etc, any quantity considered - immediate payment.

ADM Electronic Supplies

Tel. 0827 873311.

Fax 0827 874835

**PHILIPS CTX-E** main circuit board, must be in good condition. Tel. (0977) 683832.

**WANTED GRUNDIG 26"** Text model A8400 or later. Any condition. 06845 64607.

**WANTED.** Televisions and Videos surplus components, disposal agency considered. Hatfield 07072 73195.

## MAIL ORDER ADVERTISING

### British Code of Advertising Practice

Advertisements in this publication are required to conform to the British Code of Advertising Practice. In respect of mail order advertisements where money is paid in advance, the code requires advertisers to fulfil orders within 28 days, unless a longer delivery period is stated. Where goods are returned undamaged within seven days, the purchaser's money must be refunded. Please retain proof of postage/despatch as this may be needed.

### Mail Order Protection Scheme

If you order goods as a private individual from Mail Order advertisements in this magazine and pay by post in advance of delivery, Television will consider you for compensation if the Advertiser should become bankrupt or go into liquidation provided:

- (1) You have not received the goods or had your money returned; and
- (2) You write to the Publisher of Television summarising the situation not earlier than 28 days from the official on sale date of the publication and not later than three months from that date. (Please retain proof of payment).

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the Advertiser has become subject to bankruptcy proceedings or gone into liquidation up to a limit of £4,050 per annum for any one Advertiser so affected and up to £12,150 per annum in respect of all advertisers.\*

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine (not, for example, payment made in response to catalogues etc., received as a result of answering such advertisements. All display advertisements are covered but only boxed trader classified advertisements are included. Advertisements as loose inserts are not covered.

## SERVICE SHEETS

### ACCESS

## TECHNICAL INFO SERVICES (T) MASTERCARD EUROCARD

76 Church St., Larkhall, Lanarkshire ML9 1HE

PHONE 0698-884585 Mon-Fri 9-5, 0698-883334 any other time, FOR FAST QUOTES

IMMEDIATE DESPATCH of all Phone Orders by ACCESS, etc. or to Listed Customers

WORLD'S LARGEST COLLECTION OF SERVICE MANUALS . . . from £3.50 to £50 . . . Most unobtainable elsewhere

Every issued FULL SIZE SERVICE SHEET in stock; CTV's or Combinations £3.50/Singles £2.50; Plus LSAE

LSAE for any Quotation, plus FREE large Catalogue, STREE Review, Pricelists, etc.

A small selection from titles in stock . . . some only obtainable from TIS via mailorder POST FREE:

Practical TV Repairs by Tunbridge	£12.95	Colour TV Servicing by King	£12.95
Practical Radio, Repair & Service Course	£9.95	Servicing Personal Computers by Tooley	£20.00
Video Recorders, Servicing by Beeching	£20.00	Spectrum Repair & Service Guide	£5.00
Oscilloscopes, How to Use/How they Work	£6.95	Servicing Radio, HiFi, TV Eqpt by King	£9.95
Servicing Mono Portable TV by Wilding	£20.00	Video Techniques 2nd ed by G White	£30.00
Video Techniques 1st ed	£20.00	Refrigeration & Air Conditioning	£7.95
1987 Brit CTV Repair Manual by Tunbridge	£8.95	Domestic Eqpt Repair & Service	£16.95
Principles of Compact Disc	£2.95	VHS Common Faults	£3.50
The PAL System from Thorn Research	£6.50	Practical Transistor (Clearance offer)	£1.95
Audio & HiFi Engineers Pocketbook	£9.95	TV & Video Engineers Pocketbook	£9.95
Questions & Answers on Radio Repair	£3.95	Audio Equipment Tests by King	£12.95
Almost any Video Service Manual	£15.00	Almost any Colour TV Service Manual	£9.50

11 Big Colour TV Repair Manuals covering the British & many Foreign from 1970 to 1987	£90.00
20 Fault Finding Booklets covering most Videos from 1979 to 1986	£45.00
The Set of Thorn's own 10 Video Circuit Description Manuals from 3V00 to 3V43	£40.00
8 Giant Binders containing Circuits & Layouts for Brit & Foreign, Mono & CTV from 1970-87	£175.00
4 Giant Binders containing Circuits & Layouts for most Videos from 1979 to 1986	£90.00

All prices subject to VAT

Send now for

Full details of our Famous Complete Integrated Repair Systems for TVs, Videos & Domestic Equipment

These systems contain all the circuits & data needed to cover repairs and servicing for anyone in business or wishing to start up their own business. All the Diagrams, Repair, Service & Technical Data needed. At a fraction of the normal cost of buying such data. Terms are also available.

The Circuit/Layout Set for almost any Video . . . £7 each, CTVs . . . £4 each

For £3 . . . Comprehensive Service Manuals & Sheets Catalogues PLUS 1988 Chassis Guide & £4 Vouchers

## FULL WORKSHOP SERVICE MANUALS

Any Video Recorder £12.00

All other equipment, Colour TV, Mono, Audio, Test Equipment, Vintage Valve, Military Surplus, etc., etc. £6.00

Please state make/model/type and if known chassis number with all orders. Prices include postage/packing. Prompt despatch from stock with most orders.

FREE Catalogue — Unique Repair and Data Guides with all orders or LSAE for your copy.

### MAURITRON ELECTRONICS LTD (TV)

8 Cherry Tree Road, Chinnor, Oxfordshire OX9 4QY.

Telephone: (0844) 51694

## GERMAN SERVICE SHEET SPECIALISTS

Our connections are world-wide. We furnish any kind of German, European and Japanese service sheet or manual. Thousands of different sheets and manuals in stock. For any enquiries:

### DÖNBERG ELECTRONICS

Schoolmasters House, Rannafast,  
Co. Donegal, Republic of Ireland.  
Phone: 075 48275

## SITS VACANT

**SKILLED TECHNICIAN WANTED.** Good pay rates apply. JOMILL ENTERPRISES. 173 Dalston Lane. E8. Tel. 01-533 2229.

## SERVICE MANUALS

VCR - CTV - MTV - AUDIO etc.

### Examples - VCR

VSP10X = Saisho VR1200HQ/Matsui VX820 £12.75  
Memorex VR1200/Casio VCR6500 - Daewoo  
VCR30/50 - Funai VCR4000 £14.75  
Sharp VC581-582-583-585 - VC.5F3 £10.50

### CTV manuals for

NEC/Loewe/Metz/Seischo/Casio  
Orion/Okata/Admiral etc.

from £4.50

Manuals for many other makes and models well known or obscure - some unobtainable elsewhere.

Prices are all inclusive. No VAT or P/P.  
For list send £1.00. No SAE required.

DATA-GO 112 AMEYSFORD RD., FERNDOWN,  
DORSET BH22 9QE. Tel: 0202 894207

FOR SALE

# For All SHARP GRUNDIG PHILIPS

Fidelity and Thorn  
Genuine replacement spare parts  
you need only one phone call on

**0734-876444**

or

**061-682-1415**

Same day despatch before 2.30 pm.

Over 55,000 parts in stock

## Willow Vale Electronics Ltd

Sole UK Parts distributor for Grundig and Sharp. Main Philips UK Distributor

EURO-SAT SUPPLIERS TO H.M.F. - M.O.D. MANUFACTURERS OF G.R.P. DISH ANTENNAS			
1-0M DIA	£58	2-0M DIA	£180
1-2M DIA	£78	2-3M (PETAL)	£248
1-2M OFF SET	£88	3-0M DIA	£637
1-5M OFF SET	£158	FEED SUPPORT	
1-6M DIA	£98	ASSEMBLY	£21
1-8M (PETAL)	£157	POLAR MOUNT	£122

PLEASE NOTE: We are dish manufacturers only and do not supply systems.  
Please enclose S.A.E.

EURO-SAT, 107 CROSS ST., SALE,  
CHESHIRE, M33 1JW, ENGLAND  
TEL: 061-437 2631 = 061-881 4249


WIRELESS WORLD MAGAZINES from June 1947, reasonable offers for 380 copies. 0352 780367.

NEW TOSHIBA/MATSI Spares in quantity. H/sets, units splrsspkr, transformers, cables loptx, pcb's cabinet fittings etc. Brand new. Tel. (0752) 225946 Details/wants.

ISOLATION TRANSFORMERS 240v 300w (500w intermittent) £6.95 inc p&p; power supplies 0-15w, 1.5A with meter and overload protection £14.95 inc p&p equipment. A.S.A.E. 5 St Josephs Park, Ballicruttle, Downpatrick BT30 7EN.

### A NEW PUBLICATION!

# Satellite TV Installers Be Prepared

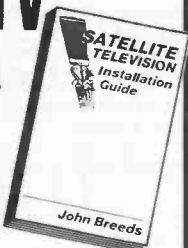

A fully illustrated satellite installers' guide. Easy-to-read style; no complicated theory or mathematical formulae involved; designed for European installers; 13 detailed sections covering all aspects of direct-to-home satellite TV.

**'Satellite Television-  
Installation Guide'**  
by John Breeds. Price **£8.95**  
plus 95p p&p.

Swift Television Publications, 17 Pittsfield,  
Cricklade, Swindon, Wilts. SN6 6AN.

## THE DOMESTIC VIDEO RECORDER SERVICING BOOK

### 3rd EDITION IN HARDBACK — THE ENGINEERS BIBLE —

With chapters on Hi-Fi, Digital Servos, Fieldstores, Luminance & Chrominance Signal Circuits, CCD's, Camcorders, 8mm, S-VHS & VHS 'C' Formats, Auto Focus Systems, Camera Signal Processing.

**A MUST FOR ALL VIDEO REPAIRERS AND STUDENTS.  
THE COMPLETE REFERENCE TO VIDEO CIRCUITS.**

**ORDER YOUR COPY NOW**  
(while stocks last)

**£21.00 inc. P&P (UK + N.I. only)**  
From: **NEWARK VIDEO SERVICES**  
GROVE FARM ESTATE, LONG LANE,  
BARNBY-IN-THE-WILLOWS, NEWARK,  
NOTTS. NG24 2SG.  
Access & Visa

**Tel. 0636 84327.**

## Ku BAND SATELLITE TV THEORY, INSTALLATION AND REPAIR

This 383 page manual by Baylin & Gale of USA covers dish theory, uplinks, footprints, site survey, installation and adjustment, descrambling, cable TV, even includes a computer program for finding your satellite. Second Edition £23.

**SATELLITE AND CABLE SCRAMBLING AND  
DESCRAMBLING.** Basic theory, 2nd Ed. 280p ..... **£19**  
**VIDEO SCRAMBLING & DESCRAMBLING.** Advanced theory and circuits, 246 pages by Graf & Sheets ..... **£21**  
**HOME SATELLITE TV INSTALLATION VIDEOTAPE,** 40 minutes. VHS PAL ..... **£27**  
**HIDDEN SIGNALS ON SATELLITE TV.** Teletext, telephone channels, teletype ..... **£20**  
**SATELLITE, OFF-AIR & SMATV.** By F. Baylin ..... **£25**  
**WORLD SATELLITE ALMANAC.** All footprints, 650 pages, second edition by M. Long ..... **£32**  
**COMMUNICATION SERVICES VIA SATELLITE.** By G.E. Lewis. Microwave, TVRO, Encryption ..... **£45**

Price includes P&P UK. Airmail Europe **£2.** Outside Europe £6.00 extra per item.

Pay by cheque, ACCESS MASTERCARD, or COD  
J. VINCENT TECHNICAL BOOKS,  
24 RIVER GARDENS, PURLEY, READING RG8 8BX.  
TEL: 0734 414468 (Answerphone)

HMV 25" C.T.V. Working, good cabinet with doors. Plus spares. Offers Brewood 851133.

### BUSINESS FOR SALE

TV RETAIL RENTAL repairs business. Cleveland. Ill health forces. £6,000. Telephone 0642 670433/0642 608420.

### REPAIR SERVICE

ONE MAN Jack of all trades electronic electrical servicing (including marine). West Highlands. Replies to: Box No. 249.

AVO'S OSCILLOSCOPES & TEST EQUIPMENT  
Repaired. Manuals available. J.R. COAD ELEC-  
TRONIC SERVICES Phone 01-340 0230.

## INDEX TO ADVERTISERS

ADM Electronic Supplies	237
Admin Televisions	228
Aerial Techniques	207
Apollo	224
Audio Electronics	169
Audio Visual Services	170
Avon Meters	237
A-Z Electronics	220
Bi-Tech	177
Bi-Tel	220
B.K. Electronics	164
Blendown Ltd	236
Bob's TV Warehouse	230
Budget TV	229
Bull, J & Electrical	171
Campion Wholesale Ltd.	239
Carter, John (Electrical) Ltd.	222
Celltel	165
Central TV & Video Wholesalers Ltd.	223
Centrevision	223
Chromavac Ltd.	169
Chromavision	214
Crewe Wholesale TV	218
Crofton Electronics	167
C.T.V.	236
Data-Go	237
Dhouper Vision	232
Display Electronics Limited	222
Donberg Electronics	237
East Cornwall Components	172
East London Components	233
Economic Devices	200, 201
Electron TV & Audio	239
Euro-Sat	238
Express TV Supplies	223
Flintdown Channel 5	236
F.T. Services	229
Gamma U.K. Ltd	220
General Factors	229
G.G.L. Components	168
Grandata Ltd.	212, 213
Griffon Emission Ltd.	239
Haiton TV Trade Disposals	228
Hussan Central TV Ltd	221
ICS	227
I.T.V.C.	228
Jornil Enterprises	235
Kesh Electronics Ltd.	236
London Electronics College	239
LRC (Spares)	224
Manor Supplies	Cover II
Marshall Ltd.	225
Mauritron Electronics	237
Midland TVs	235
Newark Video Services	238
NGK	214
N.G.T. Electronics Ltd	225
North West Electronics	231
Omega Electronics	177
PC TV Services	236
Post-a-Part Electronics	224
Powell, T.	223
Promerc Marketing	236
Pro-Vision	211
P.V.S.	235
P.V. Tubes	162, 163
Radio Component Specialist	229
Relay Omagh Ltd.	226
Riscomp Ltd.	177
R.T.V.C. Ltd.	229
Sendz Components	178, 240 Cover III, Cover IV
Sheerwood Tubes Ltd.	236
Sonic TV Distributors	234
Southside TV	167
Stewart of Reading	224
Suffolk TV & Video	235
Supersision	166
Swift Televisions	238
Taylor Bros (Otham) Ltd.	184
Technical Advisory Systems	239
Technical Information Services	237
Teleprice Ltd.	215
Televideo Services	219
Televue	235
Tidman Mail Order Ltd.	223
Todd Trading	169
Trade TVs	235
Tree, W., Trade TVs	216
TV Trade Sales	207
Universal Semiconductor Devices Ltd.	226
Vincent, J. Technical Books	238
West Midland TV & Video	217
Willets, Stan	216
Willow Vale Electronics	238
Wiltsgrove Ltd.	226
Wing Electronics	236
Wizard Distributors	228
Zoneport	218



# FULL-TIME TRAINING COURSES

## 2 YEAR

### BTEC NATIONAL DIPLOMA

Electronics and  
Communication  
Engineering

(TV, Computers, Programming, IT)

## 1 YEAR

### BTEC NATIONAL CERTIFICATE

1. Electronic Equipment Servicing  
(TV, Video, CCTV)

2. Computing Technology  
(Microprocessor, DataComms, Interfacing)

3. Information Technology  
(Telecomms, Satellite TV, CD, Networks)

4. Software Engineering  
(Assembler, BASIC, PASCAL, CAD/CAM)

### COURSES COMMENCE

Monday 9th January 1989

## LONDON ELECTRONICS COLLEGE

Dep: T.V., 20 Penywern Road,  
London SW5 9SU. Tel: 01-373 8721

# VIDEO MACHINE REPLACEMENTS

We Specialize in all types at

## UNBEATABLE PRICES!!!

### VIDEO HEADS

3HSS-V	16.00
3HSS-N	16.00
3HSS-A	21.00
3HSS-B	20.00
3HSS-H	20.00
3HSS-(A)	20.00
3HSS(SP)B	25.50
3HSS-PB	20.00
3HSS4-NA	40.00
3HSS4N-C	44.00
3HSS4V-C	44.00

### WE SUPPLY WORLDWIDE... FAST!!

3HSS-U1N	17.50	PS3BS-1	16.25
3HSSU-N	30.00	PS3BS-2	16.25
3HSS-3N	27.00	PS3BT	21.00
3HSS-SP	20.00	PS4B-2S	30.50
3HSS-R	21.50	PS5B-3S	35.50
3HSS-Y	30.00	PSF-1	20.00
3HSS-SF	21.75	VT5000	30.00
3HSSU-2N	30.00	VT9300	30.00
3HSS6-NA	60.00	VT33E/	20.00
3HSS4V-A	44.00	3HSS4V-B	44.00
3HSS3-SY	46.00	3HSS L/J	16.50

AND MANY MORE... PLEASE ENQUIRE... DISCOUNTS FOR TRADE ACCOUNTS

### BELT KITS

SONY C6	0.82
SONY C7	1.33
SONY C9	1.38
SONY SL	1.50
FERG.3V22	1.30
FERG.3V23	0.37
FERG.3V29	0.90
FERG.3V31	0.71

### PLEASE ASK FOR OUR FULL LISTS

SHARP 7300	1.38	SANYO 5000	0.50
SHARP 8300	1.38	SANYO 5300	0.80
SHARP 9300	1.38	SANYO 5500	1.00
TOSH. 7540	1.08	SANYO 9300	1.50
TOSH. 9600	0.66	N.PAN 300	1.25
HIT. VT11	0.83	N.PAN 777	1.16
HIT. 5000	1.50	N.PAN 7000	0.85
AMST. 7000	0.60	N.PAN 8600	1.28

AND MANY MORE... SINGLE BELTS... CAPSTAN BELTS... DRUM BELTS... ETC...

### PINCH ROLLERS

### IDLERS

### MOTORS

### ALL MAKES

ALL OUR COMPONENTS ARE NEW AND GUARANTEED

### VIDEO DISPLAY CORPORATION

Griftronic Emission Limited  
Unit 2, Avenue Farm Ind. Est.  
Stratford-upon-Avon  
Warks. CV37 0HU.

Minimum Order £5.00  
Phone (0789) 295883  
298510  
Telex 31470  
Fax (0789) 415243

please add 75p per order for Postage Charges plus VAT

## NEW PRODUCT ANNOUNCEMENT introducing the UNIVERSAL



## ELECTRON VIDEO REPAIR CASSETTE

A great time saving device for the bench or field service engineer for hands free video inspection or repairs. Simply insert the cassette and experience its many advantages to aid fault diagnosis.

**No** need to remove the tape carriage for routine servicing

**No** more taping of sensors and transmitters during servicing

**No** need for manual operation system switches etc. during servicing or repair

# PRICE: £9.99

Supplied with cleaning buds and fluid

To obtain your cassette please send cheque or p.o. to:

**ELECTRON T.V. & AUDIO**  
36 Gifford Road, Stratone Village,  
Swindon, Wilts.  
Tel. 0793-39363

## INCREASE YOUR PROFITS

by saving hours & hours POSSIBLY DAYS OF FRUSTRATION locating faults on VHS VIDEO RECORDERS.

WE OFFER YOU THE HELP YOU NEED with HUNDREDS & HUNDREDS of 'STOCK' and the 'HARDER' faults along with their SYMPTOMS. All experienced and collated from MANUFACTURERS/SERVICE DEPTS/WORKSHOPS/CONSULTANTS and TECHNICIANS.

Covering

ALL POPULAR MAKES & MODELS including:-  
FERGUSON/PHILIPS/JVC/PYE/PANASONIC/  
HITACHI/AKAI/MITSUBISHI/SHARP/SANYO/  
FIDELITY etc etc etc.

**SYMPTOMS/DIAGNOSTICS/FAULTS/  
PROCEDURES/MODIFICATIONS**

All well tried & PROVEN as a great TIME SAVER & ESSENTIAL for ALL service departments & personnel. Collated & indexed in UP-DATING binders for QUICK & EASY reference.

Will immediately recover the outlay costs.

ATTRACTIVE up-to-date BINDERS covering MANY HUNDREDS of FAULTS & their SYMPTOMS.

**YOU WILL WONDER HOW YOU  
MANAGED WITHOUT THIS  
ONLY £73.00 (inclusive)**

Regular monthly updates just £30 per year.  
Also available on COMPUTER DATA-BASE

Payment with order to:-  
**TECHNICAL ADVISORY SYSTEMS**  
33 FOXCOTE, ASTLEY VILLAGE,  
CHORLEY, LANCASHIRE PR7 1XE.  
Telephone: (02572) 75667

## CAMPION WHOLESALE LTD.

## QUALITY USED T.V. & VIDEO

Serviced, Untested,  
or Direct Loads.  
For Collection, or  
Free Delivery Service  
to Most Areas of the U.K.

I.T.T. 20"/22" CS 600 (CVC32 Chassis)  
Bush 20"/22" T20/T22  
Rediffusion 20"/22"/26" Mk III  
**£12 each or LESS!**  
PLUS OUR USUAL RANGE OF STOCK

## CAMPION WHOLESALE LTD.

UNIT 80, BARRACKS ROAD,  
SANDY LANE INDUSTRIAL ESTATE,  
STOURPORT-ON-SEVERN,  
WORCESTERSHIRE DY13 9QB

Just 10 Mins from  
M5 Junct. 6 Worc's North

# 02993-79642 & 79643

Hill Intercom £10	CV 8617 10p	T 9004 40p	Varia Batteries 2.4V 100M/A 50p	Ni.CD 5 Hours Battery Charger with battery test £6	Regulated Power Supply 3-12 volts 1 amp in box with switch and mains lead £4
Philips small stereo headphones £4	Y 716 30p Y 729 10p Y 730 20p	T 9005 40p ZTX 107 10p ZTX 108c 10p	TV Battery 1.2V NC 2.4V NC. 50p each	Hill Deluxe Universal Ni-Cad Charger £6	Philips' Video Cleaning Cassette SBC461 £6
Rank UHF 4 push button tuner £4	Y 827 6A/1KV 20p Y 860 30p Y 933 5p Y 969 50p	ZTX 109k 5p ZTX 213 5p ZTX 341 10p	4 amp-1.2V Nickel Cadmium Battery D Cell £1.00	Nickel Cadmium Battery Charger AA-C-D-PP9 £4.50	Philips' Headphones Compact Disc Stereo Type £10
GRC power supply PC743B £10	Y 997 75p Min 12 volt Relays R 1038 40p R 1039 40p R 2009 80p R 2010b £1 R 2029 50p R 2210 60p R 2257 60p	ZTX 342 10p ZTX 384 10p ZTX 451 10p ZTX 550 10p MJ 2253 60p MJE 3040 60p MJE 2209 10p SP 8385 50p SAB 3205 £1.00 SAB 4209 £1.00 300M + 700 320V £1.80 200 + 100 + 100 + 50 300V 50p 150 + 200 + 250M 300V 50p	3.25V Battery 50p 12V Video Battery Packs 4Amp U2 Cells £10	12 Volt Aerial Charger over Relays 144 Mc/s 45 watts 50p	ITT Display Tube 58705 50p 8 Seg Display FND500 20p
Rank front panel Z950 £5	R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 30p R 2540 £2 R 2737 40p R 2738=TTP41 30p R 2775=TTP41c 40p R 3129=TTP47 40p R 3050 £1.00 S 2008b 80p S 25D898B 80p S 25C1942 £1	Computer Transformer 20v/2.25A; 20w/1.5A; 17/1.5A; 19/1.5A; 28/0.5A £3	24V 4Amp (100VA) Trans £4.00	6 Push Button Unit for GEC 2100 Series Replacement for Touch Button Unit £8	Model 3000 Pocket Personal D.M.M. Volts range AC, DC 200M/V to 40V. Res. 2000kM £20
GEC IF tuner panel PC786B £12.50	R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 30p R 2540 £2 R 2737 40p R 2738=TTP41 30p R 2775=TTP41c 40p R 3129=TTP47 40p R 3050 £1.00 S 2008b 80p S 25D898B 80p S 25C1942 £1	TX004F £3.50 TX005GN £3.00 TX904 £3.00 X908 £4.00 MM2102AN £2.00	Mains 240V (100VA) to 240V out fully shrouded £5.00	8 SEG LED Display with driver I.C. LM1017 50p	Export PYE731 6 Push Button unit with (UHF-VHF) band switch £4
Rank IF 742 £3	R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 30p R 2540 £2 R 2737 40p R 2738=TTP41 30p R 2775=TTP41c 40p R 3129=TTP47 40p R 3050 £1.00 S 2008b 80p S 25D898B 80p S 25C1942 £1	TX004F £3.50 TX005GN £3.00 TX904 £3.00 X908 £4.00 MM2102AN £2.00	ITT CVC45 8 way resistor unit for w/cap £3	PHILIPS' MIN. HEAD PHONES £1.50	ITT Micro Phone M5 50p with switch
TX10 8 Button Unit £10	R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 30p R 2540 £2 R 2737 40p R 2738=TTP41 30p R 2775=TTP41c 40p R 3129=TTP47 40p R 3050 £1.00 S 2008b 80p S 25D898B 80p S 25C1942 £1	Computer Transformer 20v/2.25A; 20w/1.5A; 17/1.5A; 19/1.5A; 28/0.5A £3	Book on An Introduction to Satellite TV £5.95 No VAT	Electronic Buzzer 6 volt, 12 volt 40p	1/2 Volt Sub Min Relays 25p
6 Button Unit Rediffusion Mark 3 £5	R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 30p R 2540 £2 R 2737 40p R 2738=TTP41 30p R 2775=TTP41c 40p R 3129=TTP47 40p R 3050 £1.00 S 2008b 80p S 25D898B 80p S 25C1942 £1	TX004F £3.50 TX005GN £3.00 TX904 £3.00 X908 £4.00 MM2102AN £2.00	Book TV DX Handbook by R. Bunny £5.95 No VAT	15V, 015V, 1A Print Type Trans £1	Philips Solar Scientific SBC1730 Calculator £12
Rediffusion Mark 4 & 7 Push Button unit £10	R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 30p R 2540 £2 R 2737 40p R 2738=TTP41 30p R 2775=TTP41c 40p R 3129=TTP47 40p R 3050 £1.00 S 2008b 80p S 25D898B 80p S 25C1942 £1	Computer Transformer 20v/2.25A; 20w/1.5A; 17/1.5A; 19/1.5A; 28/0.5A £3	Electronics Hobbyists Handbook £4.95 No VAT	12v DC Relay 1 1/2 x 1 1/2 x 2 print type 10 amp D.P. Changeover £1	15v-0-15v 1 Amp Transformers £1
Tuner IF Cans ITT CMR200 £10	R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 30p R 2540 £2 R 2737 40p R 2738=TTP41 30p R 2775=TTP41c 40p R 3129=TTP47 40p R 3050 £1.00 S 2008b 80p S 25D898B 80p S 25C1942 £1	Computer Transformer 20v/2.25A; 20w/1.5A; 17/1.5A; 19/1.5A; 28/0.5A £3	Hills £4.50	Multi Core 60-40 Solder 500G 20 SWG £5.00 15 Watt Stereo Amp Sanyo Module with Data 50p	THORN RGP80G 30p DOUBLE 7 SEG Displays £10 for 10 or 15 for £1
ITT SEL HF Modul 2 UK IF Tuner £8	R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 30p R 2540 £2 R 2737 40p R 2738=TTP41 30p R 2775=TTP41c 40p R 3129=TTP47 40p R 3050 £1.00 S 2008b 80p S 25D898B 80p S 25C1942 £1	Computer Transformer 20v/2.25A; 20w/1.5A; 17/1.5A; 19/1.5A; 28/0.5A £3	PHILIPS 25 Watt Solder Iron £4.00	PHILIPS 25 Watt Solder Iron £4.00	Various Tools and Accessories
4 types of front panels Fidelity 2000/3000 types £5	R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 30p R 2540 £2 R 2737 40p R 2738=TTP41 30p R 2775=TTP41c 40p R 3129=TTP47 40p R 3050 £1.00 S 2008b 80p S 25D898B 80p S 25C1942 £1	Computer Transformer 20v/2.25A; 20w/1.5A; 17/1.5A; 19/1.5A; 28/0.5A £3	PHILIPS 25 Watt Solder Iron £4.00	PHILIPS 25 Watt Solder Iron £4.00	Various Tools and Accessories
CVC20, CVC32 I.F. CVC40 Cans £5 CMR800/3 NEW £20	R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 30p R 2540 £2 R 2737 40p R 2738=TTP41 30p R 2775=TTP41c 40p R 3129=TTP47 40p R 3050 £1.00 S 2008b 80p S 25D898B 80p S 25C1942 £1	Computer Transformer 20v/2.25A; 20w/1.5A; 17/1.5A; 19/1.5A; 28/0.5A £3	PHILIPS 25 Watt Solder Iron £4.00	PHILIPS 25 Watt Solder Iron £4.00	Various Tools and Accessories
20AX Line in coil 50p	R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 30p R 2540 £2 R 2737 40p R 2738=TTP41 30p R 2775=TTP41c 40p R 3129=TTP47 40p R 3050 £1.00 S 2008b 80p S 25D898B 80p S 25C1942 £1	Computer Transformer 20v/2.25A; 20w/1.5A; 17/1.5A; 19/1.5A; 28/0.5A £3	PHILIPS 25 Watt Solder Iron £4.00	PHILIPS 25 Watt Solder Iron £4.00	Various Tools and Accessories
GEC switch mode trans 20AX ITT mains CVC9 to CVC33 print type 60p	R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 30p R 2540 £2 R 2737 40p R 2738=TTP41 30p R 2775=TTP41c 40p R 3129=TTP47 40p R 3050 £1.00 S 2008b 80p S 25D898B 80p S 25C1942 £1	Computer Transformer 20v/2.25A; 20w/1.5A; 17/1.5A; 19/1.5A; 28/0.5A £3	PHILIPS 25 Watt Solder Iron £4.00	PHILIPS 25 Watt Solder Iron £4.00	Various Tools and Accessories
ITT 2,800 mains remote switch 50p	R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 30p R 2540 £2 R 2737 40p R 2738=TTP41 30p R 2775=TTP41c 40p R 3129=TTP47 40p R 3050 £1.00 S 2008b 80p S 25D898B 80p S 25C1942 £1	Computer Transformer 20v/2.25A; 20w/1.5A; 17/1.5A; 19/1.5A; 28/0.5A £3	PHILIPS 25 Watt Solder Iron £4.00	PHILIPS 25 Watt Solder Iron £4.00	Various Tools and Accessories
NEW	R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 30p R 2540 £2 R 2737 40p R 2738=TTP41 30p R 2775=TTP41c 40p R 3129=TTP47 40p R 3050 £1.00 S 2008b 80p S 25D898B 80p S 25C1942 £1	Computer Transformer 20v/2.25A; 20w/1.5A; 17/1.5A; 19/1.5A; 28/0.5A £3	PHILIPS 25 Watt Solder Iron £4.00	PHILIPS 25 Watt Solder Iron £4.00	Various Tools and Accessories
2110 GEC Sound O/P Panel £1	R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 30p R 2540 £2 R 2737 40p R 2738=TTP41 30p R 2775=TTP41c 40p R 3129=TTP47 40p R 3050 £1.00 S 2008b 80p S 25D898B 80p S 25C1942 £1	Computer Transformer 20v/2.25A; 20w/1.5A; 17/1.5A; 19/1.5A; 28/0.5A £3	PHILIPS 25 Watt Solder Iron £4.00	PHILIPS 25 Watt Solder Iron £4.00	Various Tools and Accessories
2110 GEC L.O.P.T. Panel £6	R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 30p R 2540 £2 R 2737 40p R 2738=TTP41 30p R 2775=TTP41c 40p R 3129=TTP47 40p R 3050 £1.00 S 2008b 80p S 25D898B 80p S 25C1942 £1	Computer Transformer 20v/2.25A; 20w/1.5A; 17/1.5A; 19/1.5A; 28/0.5A £3	PHILIPS 25 Watt Solder Iron £4.00	PHILIPS 25 Watt Solder Iron £4.00	Various Tools and Accessories
2110 GEC Power Panel £5	R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 30p R 2540 £2 R 2737 40p R 2738=TTP41 30p R 2775=TTP41c 40p R 3129=TTP47 40p R 3050 £1.00 S 2008b 80p S 25D898B 80p S 25C1942 £1	Computer Transformer 20v/2.25A; 20w/1.5A; 17/1.5A; 19/1.5A; 28/0.5A £3	PHILIPS 25 Watt Solder Iron £4.00	PHILIPS 25 Watt Solder Iron £4.00	Various Tools and Accessories
Line o/p frame panels GEC 20AX £10.00	R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 30p R 2540 £2 R 2737 40p R 2738=TTP41 30p R 2775=TTP41c 40p R 3129=TTP47 40p R 3050 £1.00 S 2008b 80p S 25D898B 80p S 25C1942 £1	Computer Transformer 20v/2.25A; 20w/1.5A; 17/1.5A; 19/1.5A; 28/0.5A £3	PHILIPS 25 Watt Solder Iron £4.00	PHILIPS 25 Watt Solder Iron £4.00	Various Tools and Accessories
ITT CVC40 Push Button Unit & Mains Switch £12	R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 30p R 2540 £2 R 2737 40p R 2738=TTP41 30p R 2775=TTP41c 40p R 3129=TTP47 40p R 3050 £1.00 S 2008b 80p S 25D898B 80p S 25C1942 £1	Computer Transformer 20v/2.25A; 20w/1.5A; 17/1.5A; 19/1.5A; 28/0.5A £3	PHILIPS 25 Watt Solder Iron £4.00	PHILIPS 25 Watt Solder Iron £4.00	Various Tools and Accessories
Pve Teletext Adaptor Model 7056 with Hand Set £90	R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 30p R 2540 £2 R 2737 40p R 2738=TTP41 30p R 2775=TTP41c 40p R 3129=TTP47 40p R 3050 £1.00 S 2008b 80p S 25D898B 80p S 25C1942 £1	Computer Transformer 20v/2.25A; 20w/1.5A; 17/1.5A; 19/1.5A; 28/0.5A £3	PHILIPS 25 Watt Solder Iron £4.00	PHILIPS 25 Watt Solder Iron £4.00	Various Tools and Accessories
Tuner & IF Panel. Complete 6 button and preset IF with s/wave filter and tuner. Mullard M342 5"x6 1/2" £6.00	R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 30p R 2540 £2 R 2737 40p R 2738=TTP41 30p R 2775=TTP41c 40p R 3129=TTP47 40p R 3050 £1.00 S 2008b 80p S 25D898B 80p S 25C1942 £1	Computer Transformer 20v/2.25A; 20w/1.5A; 17/1.5A; 19/1.5A; 28/0.5A £3	PHILIPS 25 Watt Solder Iron £4.00	PHILIPS 25 Watt Solder Iron £4.00	Various Tools and Accessories
POTS	R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 30p R 2540 £2 R 2737 40p R 2738=TTP41 30p R 2775=TTP41c 40p R 3129=TTP47 40p R 3050 £1.00 S 2008b 80p S 25D898B 80p S 25C1942 £1	Computer Transformer 20v/2.25A; 20w/1.5A; 17/1.5A; 19/1.5A; 28/0.5A £3	PHILIPS 25 Watt Solder Iron £4.00	PHILIPS 25 Watt Solder Iron £4.00	Various Tools and Accessories
BA 301 £1 TA 4127 £1 HD 3884 2A23 £3 TA 4184 £1 TA 2125 £1 TA 4190 £1 TA 4138 £1 TA 4196 £1 TA 4174 £1 TA 4139 £1 TA 4198 £1 TA 4167 £1 TA 4199 £1 BA 536 £1 BA 538 £1 TA 4176 £1 TA 4145 £1 TA 4191 £1 HA 11710 £1 TA 4188 £1 TA 4197 £1 TA 4183 £1 TA 4197 £1 TA 4183 £1 TA 4197 £1 TA 4188 £1 TA 4175 £1 TA 4177 £1 TA 4192 £1 TA 4146 £1 TA 7265 £3 TA 7699P £3	R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 30p R 2540 £2 R 2737 40p R 2738=TTP41 30p R 2775=TTP41c 40p R 3129=TTP47 40p R 3050 £1.00 S 2008b 80p S 25D898B 80p S 25C1942 £1	Computer Transformer 20v/2.25A; 20w/1.5A; 17/1.5A; 19/1.5A; 28/0.5A £3	PHILIPS 25 Watt Solder Iron £4.00	PHILIPS 25 Watt Solder Iron £4.00	Various Tools and Accessories
The Service Engineers Guide to Teletext £2	R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 30p R 2540 £2 R 2737 40p R 2738=TTP41 30p R 2775=TTP41c 40p R 3129=TTP47 40p R 3050 £1.00 S 2008b 80p S 25D898B 80p S 25C1942 £1	Computer Transformer 20v/2.25A; 20w/1.5A; 17/1.5A; 19/1.5A; 28/0.5A £3	PHILIPS 25 Watt Solder Iron £4.00	PHILIPS 25 Watt Solder Iron £4.00	Various Tools and Accessories
4 Types Fidelity front panels with i.c. & pats £2 each	R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 30p R 2540 £2 R 2737 40p R 2738=TTP41 30p R 2775=TTP41c 40p R 3129=TTP47 40p R 3050 £1.00 S 2008b 80p S 25D898B 80p S 25C1942 £1	Computer Transformer 20v/2.25A; 20w/1.5A; 17/1.5A; 19/1.5A; 28/0.5A £3	PHILIPS 25 Watt Solder Iron £4.00	PHILIPS 25 Watt Solder Iron £4.00	Various Tools and Accessories
BB 103 10p BB 105A x 12 £1 BB 105B x 12 £1 BB 105G x 12 £1 BB 121a 10p 47 10p each	R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 30p R 2540 £2 R 2737 40p R 2738=TTP41 30p R 2775=TTP41c 40p R 3129=TTP47 40p R 3050 £1.00 S 2008b 80p S 25D898B 80p S 25C1942 £1	Computer Transformer 20v/2.25A; 20w/1.5A; 17/1.5A; 19/1.5A; 28/0.5A £3	PHILIPS 25 Watt Solder Iron £4.00	PHILIPS 25 Watt Solder Iron £4.00	Various Tools and Accessories
1A/1600V 10p DG3P EQV-BY228 10 for £1 2 amp bridge rec. wire end 15p	R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 30p R 2540 £2 R 2737 40p R 2738=TTP41 30p R 2775=TTP41c 40p R 3129=TTP47 40p R 3050 £1.00 S 2008b 80p S 25D898B 80p S 25C1942 £1	Computer Transformer 20v/2.25A; 20w/1.5A; 17/1.5A; 19/1.5A; 28/0.5A £3	PHILIPS 25 Watt Solder Iron £4.00	PHILIPS 25 Watt Solder Iron £4.00	Various Tools and Accessories
	R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 30p R 2540 £2 R 2737 40p R 2738=TTP41 30p R 2775=TTP41c 40p R 3129=TTP47 40p R 3050 £1.00 S 2008b 80p S 25D898B 80p S 25C1942 £1	Computer Transformer 20v/2.25A; 20w/1.5A; 17/1.5A; 19/1.5A; 28/0.5A £3	PHILIPS 25 Watt Solder Iron £4.00	PHILIPS 25 Watt Solder Iron £4.00	Various Tools and Accessories
	R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 30p R 2540 £2 R 2737 40p R 2738=TTP				

# SENDZ COMPONENTS

## TO ORDER SEE BACK PAGE

Matsushita PY34220 Tuner	£7	K35 Decoder	£8.00
C. Cam Decoder with TDA3591	£4	K35 Sound OP	£4.00
Toshiba VHF/UHF EGS22F	£6	Thick Film Daughter KT3 3122-127-43891	£3
Mitsumi MEC1-F51	£5	12 C.H. K30 Tex Rec Front Panel with I.C.	£5
		K35 IF	£5.00
<b>Thorn Spares</b>			
New 9000 Decoder	£8.50		
9000 Frame panel	£8		
9000 Cyclops panel	£1.50		
8800 convergence panel	£6		
8500 convergence panel	£6		
4000 Power supply	£3		
1600 Mains lead, switch	10p		
T605 1vNPN T066 80v/6A	£1		
9000 Sound output panel	£1		
3500 Focus unit	£1.50		
3500 Mains Trans	£1		
3500 cut out	10 for £4		
3500 IF panel	£2		
3500 Frame panel	£3		
3500 Line panel	£3		
3500 A1 Diode	20p		
Export 3500 IF panel	£2		
IC board with set of SN74LS	£4		
4000 Tube base	50p		
3500 A1 pots	£1.50		
Beam limiter panel	£1		
3500 Power panel with Y969	£1		
3 Way regulated adaptor 240V 7.5V/300mA	£3.50		
Rank/Toshiba preh unit 0354	£9.50		
4 Push button unit preh	£1.00		
6 Push button VHF/UHF for v/cap. GEC/Decca type	£7.00		
7 Push button for CVC5 ITT	£8.00		
KT3 12 Push button unit	£2.00		
KT3 (Export) 12 P.B.U.	£2		
6 Push button Unit Thorn	£1.00		
6 Push button GRC	£6.00		
6 Push button PVE 731	£6.00		
Hearing aid unit	£3		
Rank Z718 4 P/B/Unit MECH	£4		
7 Button Unit GEC with Lamps	£7		
697 Push Button Unit	£6.00		
Z916B panel	£5.00		
TS13AF panel	£5.00		
<b>Mains Droppers</b>			
Pve 731 3+56+27R	50p		
Thorn 50/17/1K5	£1.00		
120/20/20/48/117	£1.00		
270/106 for Thorn 4000	£1.00		
18/320/70/39	£1.10		
Thorn 50-40R-1K5	50p		
Ac Socket & Lead	25p		
GEC, ITT, Philips, Pve	£1		
7x3/4 Thorn	£1.50		
Thorn 1600-1700	£1.50		
Rank Toshiba Tube Bases	30p		
20,000 Per Volt			
HT420 Hills Meter			
10 Amp AC/DC			
1,000 and ohms range £10			
4 ohms ranges 0-1000 volt AC/DC			
AEG KT2000/641-005			
<b>Hand Sets</b>			
Fidelity All Types			
£15 to £35			
<b>KT3-K30</b>			
OF-425	10p		
OF-550	10p		
OF-513	10p		
OF-557	50p		
<b>DIODES</b>			
BY 126	10p		
BY 127	10p		
BY 133	10p		
BY 134	10p		
BY 179	40p		
BY 184	25p		
BY 187	10p		
BY 190	40p		
BY 196	30p		
BY 198	10p		
BY 204/4	10p		
BY 206 - BY 407 Eqv.	8p		
BY 208/800	8p		
BY 210/400	8p		
BY 210/800	10p		
BY 223	60p		
BY 224/600: 4.8A/600v bridge	50p		
BY 226	15p		
BY 227	15p		
BY 228 1500v	20p		
Flat BY229 black	20p		
BY 299 Red	20p		
BY 229/400	20p		
BY 299/60p Tag	30p		
BY 237	5p		
BY 254	10p		
BY 255	30p		
BY 298	10p		
BY 299	10p		
BY 406	8p		
BY 527	20p		
BY 407a	10p		
BY 448	10p		
BY 527	10p		
BY 602	10p		
BYV 26C	10p		
F 247	10p		
GP20G	5p		
GRP80G (TX10)	60p		
XK 3102	20p		
BYV 28/200	50p		
Bridge TX10 800/3 amps	30p		
KBF35-02 Bridge	30p		
Bridge Rec. D35B10	40p		

G8 LOPT Panel	£12.00		
Rank T20 Z136 Panel	£6.00		
NEW GEC 20AX Power Supply Switch Mode	£12.00		
Field + Jungle panel for GEC 3133/3135	£1.50		
GEC 2110 line panel with transformer	£7.00		
GEC 2110 tuner unit + IF Panel	£12.00		
Pve/Chelsea Line op panel	£12.00		
Pve 205 Tuner	£9.90		
Pve 713 IF panel and tuner	£7.00		
Pve 713 Chroma	£10.00		
Pve/Chelsea Timebase panel with LOPTI	£10.00		
Pve 731 Frame Panel	£5.00		
Pve 731 Convergence Panel	£5.00		
Pve 731 Chroma	£10.00		
Pve 731 IF panel + tuner	£10.00		
GEC portable chassis + LOPTI 2114 New	£4.00		
G9 Power Panel	£6.00		
Mono RANK Chassis 127A NEW	£10.00		
NEW G9 Frame Panel	£4.00		
NEW G11 IF Panel	£10.00		
G8 Tuner Unit + Panel	£4.00		
G8 IF & Chroma	£6.00		
G8 Chroma	£3.00		
G11 IF Detector	£3.00		
G11 Selector gain module	£3		
Complete GEC 825 Chassis (both panels)	£40.00		
AEC V/Cap Resistor Unit UHF with IC	£3.00		
SAS660 SAS670	£3.00		
Z714 RANK IF Panels 6MHz 1 I.C.	£3.00		
SL437F	£3.00		
Z909B RANK IF Panels	£3.00		
Export 5.5MHz 2 I.C.'s	£2.50		
TBA1205B TCA2705Q	£2.50		
K35 IF	£6.00		
Z743 RANK IF Panel	£2.25		
Export 5.5MHz 3 I.C.'s	£2.25		
TBA750+SC9504P+	£1.50		
SC9503P	£1.50		
Pve G11 Front panel with transducer, pots, tuner pots, 6 pb switch+lead	£5.00		
Pve 6 button switch portable	£1.00		
GEC V/cap VHF/UHF tuner and IF+	£12.00		
sound O/P PC 706B3 (Export)	£11.00		
GEC Line O/P PC 659B3	£6.00		
2110 GEC Power Panel	£8.00		
CVC 20 Front panel with sliders +	£4		
CVC 40 PUSH BUTTON ASSY with sliders: complete with lamp assy + pots	£9.00		
8 button units	£9.00		
CVC9 slider pots panel	50p		
Universal Focus. Fits Pve, Thorn and			
Decca Units.			
T147 Rank tube base on panel	£1.00		
Z718 Focus Unit	£1.50		
T20 Focus Unit	£1.00		
Large Type	75p		
Decca Small	75p		
KT3 Focus Pot	75p		
K30 Focus Pot	75p		
K30 Tube base on panel	£1.00		
TX10 Focus Units	£8.50		
CVC 32 Focus Unit	75p		
Fidelity Focus Unit 14R-14S	75p		
3500 Thorn Focus Unit	£1.00		
ITT Small for use with Split	£2.00		
Z718 Bush Focus	£2.00		
Diode	50p		
Remo TV125P	50p		
1600 Thorn EHT Rec and Lead	50p		
TV14	50p		
TV20	£1.00		
TV45	50p		
Thorn 14/1500 rec stick	5p		
TX10 8 Button Unit	£10.00		
TX10/TX100 16 Button	£10.00		
G11 drawer ASS 3 pots Mains switch and lead	£2.00		
K30 Drawer Ass with pots cable forms	£1.00		
TX10 Drawer with 8 way pots, ass.	£2.50		
TX10 Ex. port with band switch (drawer)	£2.50		
Line O/P panel GEC 2217/2218/2213/2214/2226/2227/2228	£10		
<b>PHILIPS BATTERIES (Small Types) HAND SETS</b>			
SR41	25p		
SR44	25p		
SR45	25p		
SR54	25p		
LR43	25p		
LR44	25p		
LR54	25p		
CR2032	25p		
10 500PF 2KV	20p		
22/1000	20p		
1/250AC	5p		
1/100	5p		
IMFD-250AC	25p		
TAA7750	£1.00		
HA411485	£1.00		
UPC1373	50p		
M50143	£1.00		
M491BB1	£1.00		
M58657P	25p		
M5044/550	£1.00		
M58658P	£1.00		
Delay Line TDK Small	10p		
CVC 20-25-30 Mains Switches			
Infra Red and Ultrasonic G11 Teletext Decoder Panel			
RANK & ITT Mains Remote On-Off Switch (720R)			
RANK & ITT Remote Switch 2800 ohm			
G11 Mains Switch	50p		
4 amp Mains Switch	25p		
GEC Mains Switch 4 amp	£1.00		
KT3 Mains switch	75p		
G8 Mains Switch	75p		
G11 Preh Red LED P/Button for C.H. Change	50p		
RANK TOSHIBA Transducers T.PC-2011	50p		
Mains Switch ITT Long Type Print	75p		
Mains Switch Philp Long Type TAG	75p		
Mains Switch GEC Long Type TAG	75p		
2000 Chassis Fidelity Mains Switch (4 TAG)	60p		
250V/4A White Lorlin Mains Switch	60p		
KT3-K30 K35 Full Remote Mains Switch (6 TAG)	£12.00		
Teletext Adaptor Kit TY-500 Panasonic	£12		

**25% OFF ALL PANELS**

<b>Multi-Caps</b>			
220 MFD Sprague 385V	50p		
350V 300M + 300M	£1.00		
400V 400M	60p		
350V 400M	60p		
Thorn 3500	£1.00		
175/100/100/350v	£1.00		
KT3/200/25/25/385v	£1.00		
KT3-K30 220+40+40	75p		
200+200+75+25M 325V	£1.00		
300+300+150+100+50MFD	£1.00		
350V	£2.00		
G11 CAP 470/250	£2.50		
47/22/235v	60p		
150V/100/100/100/320v	£2.00		
2500/2500/63v	50p		
150/200/200/300v	70p		
300V/100/100/6275v	1.00		
100/200/325v	40p		
150V/50/100/375v	£1.50		
200/200/75/25M 375V	£1.00		
Thorn TX9 Caps 500+500M 175V	2.00		
300/300/100/32/32/300v	£1.00		
150V/200/30v	50p		
150V/100/100/320v	£2.00		
100/350 + 300/200/100/16/275v	£2.00		
225+25/380 GEC	70p		
200/100/100/350v	1.50		
500/500/75v	50p		
150V/100/300v	75p		
200V/150/150/300v	1.00		
ITT 8 and 6 Push Button	£1.00		
Pve 725 LOPTS	£6.00		
Pve 731 LOPTS	£6.00		
Thorn 8500-8800 LOPTS	£5.00		
CMC 301 front panel	£5.00		
CMC 303 front panel	£5.00		
CMC 302 Panel with TC mains switch etc	£5.00		
CMD 800 Decoder	£8.00		
G11	£1.50		
1 I.C. Receiver Panel	£3.00		
3 I.C. Power Supply G11 Full Remote Receiver Panel	£3.00		
<b>PHILIPS SBC 469 Stereo Microphone</b>			
Meters Hills 520	£23.00		
Meters Hills 420	£17.00		
Hills HD5000 Digital Meter 1000V DC	£25.00		
750AC 10 Amp 20 MRG Rangers	£28		
HT100 Multimeter	£6.75		
HT300 Multimeter	£7.75		
HT500 Multimeter	£9.75		
HT700	£15.00		
HD1000 Digital	£20.00		
HD3000 Digital	£25.00		
HD5000 Digital	£25.00		
HD5500	£29.00		
HD6000 Digital	£32.00		
HD8000 Digital	£37.00		

# SENDZ COMPONENTS

63 Bishopstretton,  
Shoeburyness, ESSEX SS3 8AF  
SAME DAY SERVICE

All items subject to availability. Technical Information by telephone only. No Accounts: No Credit Cards  
Postal Order/Cheque with order  
Add 15% VAT, then £1 Postage  
Add Postage for overseas

Callers: To shop at 212 London Rd.,  
Southend, Tel. 0702 332992, Fax 0702 338805

Open 9-1.20.94. GVMT + school orders accepted on official headings add 90% handling charge.

Tuner Units	
Thorn TX Tuner V/Cap eqv. to ELC1043	£4.50
Min. UHF Tuner 40dB gain	
2x172xV2	£1.50
VHF-UHF with Data Tuner MECL-F51	£3
F400 Family with Data Mosfet	
Thorn TX10 Export V/Cap UHF VHF	£3
V/Cap Rank UHF Z767/Unit	
V/Cap Rank VHF Z773/Unit	£6
NEW G8 Tuner V/Cap	£3.50
T20 6 Push Button Unit	£7
ELC2000 on Panel	£2.50
GEC 2110 V/Cap	£5
FE6180	£26.00
ELC1042 NEW	£6.00
ELC1043 (Ext Panel)	£3.75
ELC2000	NEW £4.00
ELC2004	NEW £8.00
ELC2003	£4.00
ELC2006	NEW £4.00
GEC Tuner V/Cap Hitachi After	
1979 ETS48, ETS47, ETS41B	£8.00
ETS46	£6.00
ET1614 UHF Tuner	
ET1566P UHF Very Small	£2.50
ET1598P VHF/UHF Very Small	£5.00
UHF ET566P, small	£6.00
ASTEC UM1183	£10.00
V314 (VHF)	£5.00
U321	£6.00
U322	£8.00
U341 UHF	£6.00
U342 (UHF)	£5.00
U343 Phono	£5.00
U343C	£6.00
U344C	£10.00
U411 UHF	£4.00
U.V. 411 Tuner	£8.00
U.V. 412	£10.00
U.V. 415	£7.00
U.V. 417	£7.00
U.V. 418	£10.00
U.V. 617	£10.00
U.V. 618	£12.00
U743 Tuner	£7.00
Fidelity and Amstrad 2000 V/Cap Tuner	£5.00
Small V/Cap Mitsumi	
UHF	£4.00
VHF	£3.00
VHF & UHF ET1598P Tuner	£6.00
Portable & rotary Tuners Sanyo & Mitsumi	
UHF	£5.00
NSF-UHF/VHF Vancap (old type)	£8.00
Mosfet UHF/VHF (new type)	£8.00
UEZ-B31 Fidelity V/Cap T Unit	£6
UHF-VHF V/Caps on panel	£3.00
HITACHI 20 Turn Pot	£4.00
U321 on panel	£6.00
Tuner unit VHS Sylvania GTR Videom	
M75 900	£2.50
Toshiba VHF-UHF EG525F	£5.00
Mullard Video Modulator. Application video tape recorders, TV cameras, video games, closed circuit TV, C.C.I.R. system. Data supplied.	£10.00
4 button Rank Z18 Tuner	£4.00

UHF Tuner GTR Sylvania F4714A	£2
VHF Tuner GTR Sylvania F3720B	£2
Sylvania UHF F4720B	£6.00
Sylvania VHF 900	£6.00
Small Tuner DX 175-220MHz	
Auto Changeover	£5.00
9000 Thorn Tuner on Panel	£7.00
Change over switch co-ax type box with lead	50p
THORN 1590 4P B. Mech. Tuner	
THORN 3500 4P B. Mech. Tuner	
All new & boxed.	£4.00 each
Delay Lines	
DL700	£1.00
KT 3 Luminescence	75p
Luminescence Delay Line (CVC 45)	
Co-Ax Joint	15p
Co-Ax Belling Lee Plug	12p
Co-Ax Splitter	£1.00
UHF Modulator CCR	£3.00
UHF Modulator Astec 1286	£2.50
Infra Red Emitting Diode	20p
NE286H Small Neon Lamps GEC & Philips	5p
Mullard 5 Watt Amps. LP1162	
New	75p

T.V. Tubes	
12" 90% black and white	£10
12" 110% (No Post)	£10
12" 110% 315/10	Post £2.50 £5
12" A31300 Hitachi	
S.W. Filters	
HW2013	50p
SW453	50p
SW150	£1
HW2013	50p
RW303	50p
SY2153	50p
S.W. Filters	
SW185	£1
SW153A	50p
SW154	50p
SW173	50p
FI035B	50p
FI045A	50p

BD464	50p
BD676A	30p
BD807	20p
BD826	30p
BD933	30p
BD939	30p
BD948	30p
BDT31A	50p
BDX75	20p
BDY64B	50p
BDU65	50p
BF761	30p
BF769	30p
BF788	20p
BF819A	30p
BF825A	30p
BF869	30p
BF871	30p
BF872	7p
BF871	15p
BF860	10p
BFT42	20p
BFT57	20p
BFW11	20p
BFX85 100V. 1amp	30p
BSD215	50p
MR1366	20p
AN6350	£2.00
BRC-M-200	40p
BRC-M-300	50p
BRC 1693	£1.00
BRC 3064	£1.00
BTT822	£1.00
BTT601	£1.20
BTT601B/ML237B	£1.50
BTT6218	£1.50
BTT8124	£1.00
BTT8224	£1.00
12" 110% 315/10	Post £2.50 £5
CA270AE	50p
CA270CW	50p
CA270CE	50p
CA310	£1.00
CA306	50p
CA306S0	50p
CA309AAE	50p
CA3123	40p
CA3146	£1.00
CA3189	40p
CD4558	30p
CD4510	30p
CD4555BE	30p
DM7492	50p
HA1135A	40p
HA1196	40p
HA1370	£2.00
HA11223	40p
HA11423	40p
HA11440	30p
HA11484	£3.00
HA11485 Ant	£1.00
HA17458	50p
HEF4001	10p
HEF4011AF	10p
HEF4053B	30p
HEF4060P	30p
HEF4528	20p
HD3890C	£3.00
KT31D 1001012	£1.00
LA3220	50p
LA4102	£1.00
LA7830	£2.00
LA7831	£2.00
LM1011N	£3.00
LM1111N	£1.00
LM1017N	25p
LM1765	30p
PCF8571P	£5.00
M913	£2.00
M1024-SAA	£2.00
M1024-SAA	£2.00
MC4766	£1.00
MC1307	75p
MC1312	30p
MC1340S	£1.00
MC1352	£1.00
MC1496	50p
MC1498	50p
MC1499	50p
MC14013	25p
MC14016	25p
MC14086	30p
MC14576	30p
MC1748	80p
MEM4956	£1.00
ML231	£2.50
ET16016	£2.00
ML232	£1.00
ML236E	£1.00
ML237B	£1.00
ML238B	£2.00
ML239	£2.00
ML926	£1.00

Thyristors	
Philips Kits OTL21	50p
IR105A	15p
BT106	80p
BT106 Plastic	80p
BT106 Metal	80p
BT119	£1.20
BT120	£1.00
BT121	£1.00
BT122	£1.00
BT300	£1.00

Thyristors	
Philips Kits OTL21	50p
IR105A	15p
BT106	80p
BT106 Plastic	80p
BT106 Metal	80p
BT119	£1.20
BT120	£1.00
BT121	£1.00
BT122	£1.00
BT123	£1.00
BT124	£1.00
BT125	£1.00
BT126	£1.00</