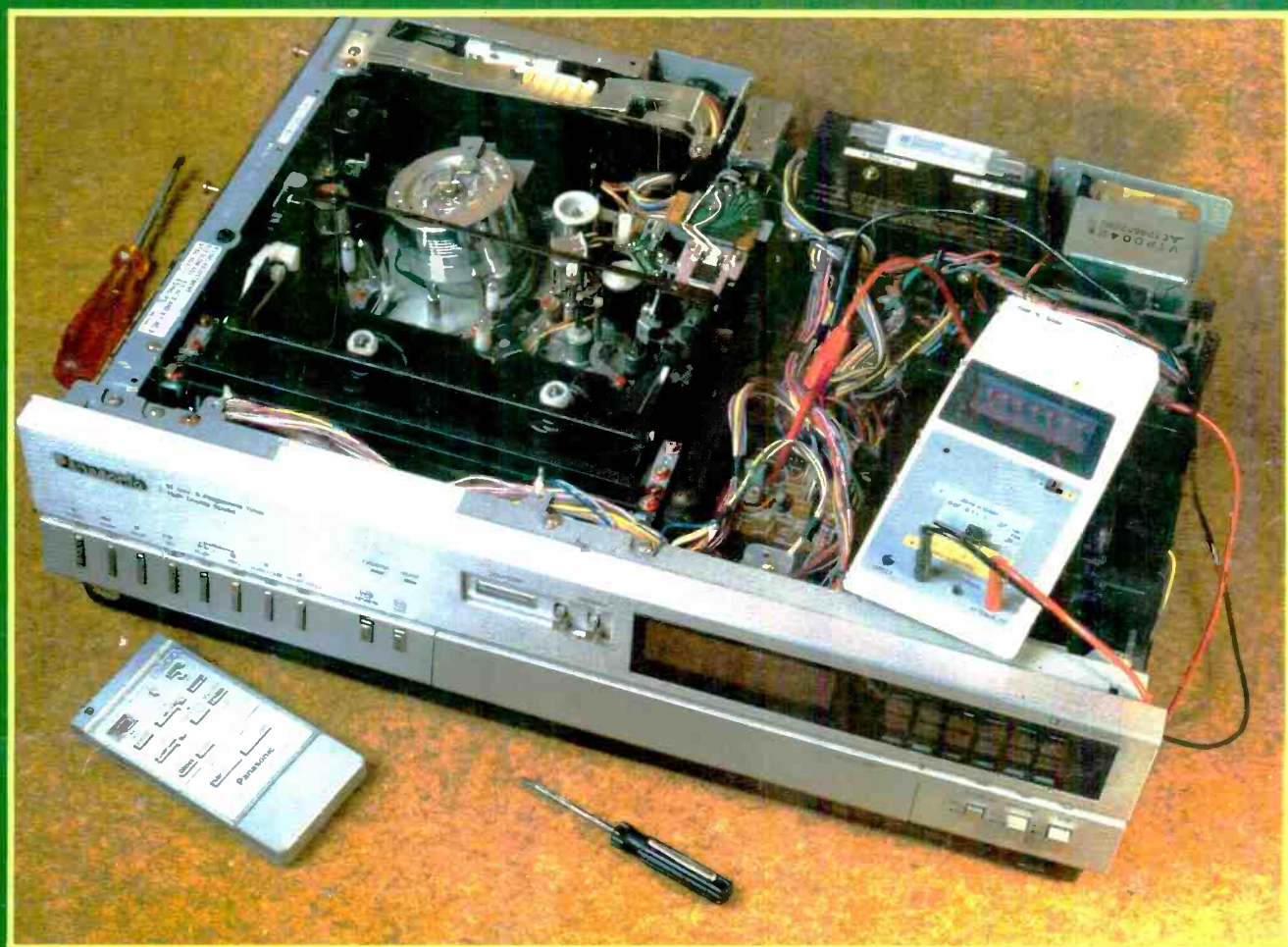


JULY 1986

Australia \$2, New Zealand \$50, Malaysia \$5.75 £1.20

TELEVISION

SERVICING·PROJECTS·VIDEO·DEVELOPMENTS



**Servicing the Panasonic NV7000
Colour CRT Electron Gun Technology
Servicing Notes on Sonatel and
Morphy Richards Mono Portables
Line Output Stage Operation
The Grundig CUC Chassis • DX-TV
VCR Clinic • TV Fault Finding**

MANOR SUPPLIES

MKV PAL COLOUR
TEST GENERATOR FOR TV & VCR.

TEST
DEMONSTRATIONS
AT 172
WEST END LANE




- ★ 40 different patterns and variations.
- ★ Broadcast transmission accuracy (fully interlaced sync pulses with correct picture blanking).
- ★ EBU colour bars, BBC colour bars, whole rasters & split bars (specially useful for VCR service), white, yellow, cyan, green, magenta, red, blue and black.
- ★ Chequerboard.
- ★ Mono outputs with border castellations, cross hatch, grey scale, vertical lines, horizontal lines and dots. UHF modulator output plugs straight into receiver aerial socket.
- ★ Additional video output for CCTV & VCR.
- ★ Facilities for sound output.
- ★ Easy to build kit, standard parts. Only 2 adjustments. No special test equipment required.
- ★ Mains operated with stabilised power supply.
- ★ All kits fully guaranteed with back-up service.
- ★ Also available with VHF Modulator.

Price of Kit **£70.00**
Case (10"×6"×2¼") app. **£8.60**
Optional Sound Module (6MHz or 5.5MHz) **£3.90**
Built & Tested in Case including Sound Module **£108.00**

SPECIAL TEST
REPORT
'TELEVISION'
DEC. 1982

Post/Packing £2.50
Add VAT 15% TO ALL PRICES

PAL COLOUR BAR GENERATOR (Mk4)

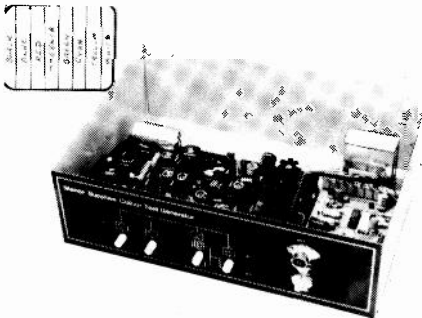

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars R-Y, B-Y etc.
- ★ Cross-hatch, grey scale, peak white and black level.
- ★ Push button controls, battery or mains operated.
- ★ Simple design, only five i.c.s on colour bar P.C.B.

PRICE OF MK 4 COLOUR BAR GENERATOR KIT
**£30.00. CASE £8.60. BATT HOLDERS £4.20. MAINS
SUPPLY KIT £4.20 (Combined P&P £2.20).**

MK 4 (BATTERY) BUILT & TESTED **£58.00 + £2.20 P & P.**
MK 4 (MAINS) BUILT & TESTED **£68.00 + £2.20 P & P.**
VHF MODULATOR (CH 1 to 4) FOR OVERSEAS **£5.75.**
EASILY ADAPTED FOR VIDEO OUTPUT & C.C.T.V.

ADD
VAT
15%

THORN TX9 MK2/3, TX10, teletext
Mullard Decoder panel + Interface **£35.00 p.p. £1.80**
THORN TX10, PHILIPS G11 PRESTEL, TELETEXT
Mullard Units VM 6230, 6330 plus Line Coupler & Interface **£38.00 p.p. £2.50**

EXTERNAL TELETEXT ADAPTOR
(RADOFIN) with cable remote control. Fully tested. **£150.00 p.p. £3.00.** Plugs into aerial socket of any T.V.
SPECIAL OFFER (shop customers only).
SURPLUS 'AYR' TELETEXT EXTERNAL ADAPTOR UNITS.
Ideal for experimental use **£50.00.**

TV SERVICE SPARES

BACKED BY TWENTY YEARS EXPERIENCE & STAFF OF
TECHNICAL EXPERTS

LOPTs, TRIPLERS, PANELS, TUNERS, SELECTORS ETC.
SPECIAL OFFER Ex rental T.V. Sound & Vision Tuner Units. Ideal as fronts end for Monitors, Portable Video, HiFi, etc. Deluxe Cabinet, mains operated, 8 position selector, Saw Filter IF. Only **£15.00 p.p. £2.80.**
SPECIAL OFFER Mullard/Philips quality UHF modulator (audio & video input) ex new equipment **£5.00 p.p. £1.00.**

PHILIPS G11 PANELS (tested).
Power, frame, IF, decoder **£18.00** each p.p. **£2.00.** Scan Panel **£28.00 p.p. £2.80.**
PHILIPS G11 PANELS ex rental (untested).

Power, frame, IF, decoder **£10.00** each p.p. **£2.00.**
PHILIPS HANDSETS Ex rental, Teletext, Untested. KT3, K30, CTX, KT4, K35 etc. **£5.00 p.p. 80p.**

THORN 9000 Fault Finding Guide **£1.00 p.p. 30p.**
THORN REMOTE CONTROL HANDSETS

8800/9800 (2-button) **£10.00;** TX9 ULTRASONIC (3-button) **£15.00;** TX9, TX10 Infra red **£18.00;** TX9, TX10 Infra red Teletext **£20.00 p.p. £1.20.**
TX10 Remote & Tuning control panel (1515) **£9.40 p.p. £1.50**
TX9/TX10 Teletext interface panel (1524) **£5.00 p.p. 80p.**

THORN TX9 Ultrasonic Remote/Control/Receiver panels. **£8.50 p.p. £1.50.**
THORN TX10 Series Facia Control Panel with 8 position Channel Selector **£6.50 p.p. £1.50.**

SAW FILTER IF AMPLIFIER PLUS TUNER complete and tested for T.V. Sound & Vision. **£28.50 p.p. £1.20.**

THORN TX9, TX10 Saw Filter IF Panel. **£5.00 p.p. 80p.**

PAL DECODER KIT (Video to RGB) for Monitors **£27.00 p.p. £1.00.**
PAL ENCODER KIT (RGB to Video) **£18.50 p.p. £1.30.**

TELETEXT DECODERS New & Tested Mullard VM 6101 **£30.00,** Texas XM11 **£40.00,** KT3 Tested **£30.00,** Untested **£5.00 p.p. £1.60**

CROSS HATCH UNIT KIT, Aerial Input type, incl. T.V. sync. and UHF Modulator, Battery Operated, also gives Peak White & Black Levels, can be used for any set. **£12.00 p.p. 80p.** (Alum. Case **£2.90,** De Luxe Case **£6.80 p.p. £1.40.)** ADDITIONAL GREY SCALE Kit **£2.90 p.p. 45p.**

UHF SIGNAL STRENGTH METER KIT **£22.00** Alum. Case **£2.90.** De Luxe Case **£8.60** (Built & Tested **£48.00**) p.p. **£2.30.**

CRT TESTER & REACTIVATOR KIT For Colour & Mono complete with Case, Panel Meter Indicator - can be adapted for latest CRTs **£29.50 p.p. £2.80.**

BUSH A823 Convergence, Time Base Panels **£5.00** each. p.p. **£1.80.**
BUSH 2718 BC6100 series IF Panel **£5.00 p.p. 90p.**

BUSH A816 IF Panel (Surplus) **£1.00 p.p. 90p,** 5 for **£4.00 p.p. £1.40.**
GEC 2040 Decoder Panels, **£1.50 p.p. £1.80.**

GEC 2110 PANELS Frame **£8.50 p.p. £1.40.** Sound **£2.50** (tested) p.p. **80p.**
GEC 20AX Line Time Base **£18.00.** IF-Decoder **£12.50 p.p. £2.00.**

PYE 691-7 CDA Panels. Makers tested stock. **£6.00 p.p. £1.45.**
THORN TX9 Panels ex factory for small spares. Includes I.C.s & Semicomponents etc. **£3.00 p.p. £1.80.**

THORN TX9 Panels salvaged ex factory for spares incl. LOPT & Mains Transformers. **£10.00 p.p. £2.80.**

THORN TX9 Panels ex factory salvaged complete cond. **£20.00 p.p. £2.80.**
THORN 8000, 8500, 8800 IF Decoder Panels Tested **£10.00 p.p. £2.30.**

THORN 8000/8500 IF/Decoder Panels salvaged **£3.20 p.p. £1.80.**
THORN 9000 IF/Decoder Panels Salvaged. For spares **£2.50 p.p. £1.80.**

THORN 9000 Frame Time Base **£8.50 p.p. £1.80.**
PHILIPS G8/G9 IF/Decoder Panels for small spares incl ICs **£2.50 p.p. £1.60.**

PHILIPS G8 Line Driver Panel incl. Equalizing Coil. **£1.00 p.p. 60p.**
G11 PANELS, Ex Rental SCAN (incl LOPT) **£28.00 p.p. £2.50** (tested).

G11 PANELS, Power, Frame, IF, Decoder. **£18.00** each. p.p. **£2.00** (tested).
GRUNDIG 8630 Series Varicap Tuners **£5.00 p.p. £1.00.**

U321. ELC1043/5 **£7.80 p.p. 80p.** Makers Controls PYE CT200 4PSN **£7.50,** BUSH 4PSN **£4.80,** DECCA 4PSN **£5.80,** 6PSN **£6.80 p.p. 80p.** etc.

BUSH "TOUCH TUNE" Varicap Control Z585, 710 **£3.80 p.p. £1.00.**
VARICAP UHF-VHF ELC 2000S **£9.80 p.p. £1.00.**

UHF/625 TUNERS, many different types in stock. DECCA Bradford 5 position, MULLARD 4 position **£2.50,** JAP Rotary **£4.80 p.p. £1.80.**
TV SOUND IF Panels **£6.80 p.p. £1.00.**

LOPT TESTER, Service Dept approved **£15.90 p.p. £1.20.**
LOPTS New and guar. P/P Mono **£1.35,** Colour **£1.50,** Bobbins **80p.**

BUSH, MURPHY 774 series **£9.80**
BUSH, MURPHY A816 series **£9.80**

FERG., HMV, MARCONI, ULTRA
1500, 1590, 1591, 1612, 1613, 1712 **£4.80**

THORN 1600, 1615, 1690, 1691 **£9.15**
GEC series 1 & 2 **£8.00**

INDESIT 2024EGB **£7.65**
ITT/KB VC200, 300 **£7.90**

PHILIPS 170, 210, 300 series **£7.65**
PYE, INVICTA, EKCO,
368, 169, 569, 769 series **£7.65**

SPECIAL OFFER
DECCA 1700, 2001, 2020, 2401, 2420 **£3.80**

GEC 2114/Junior Finline **£2.80**
PHILIPS 320 **£2.80**

RBM A823 **£4.80**
GEC 2028, 2040, 2100 **£4.80**

PYE 713, 715 **£6.80**
PHILIPS 570, 571 **£6.80**

R.B.M. T20, T22 **£9.80**
R.B.M. T20, T22 Bobbin **£5.60**

DECCA Bradford (state Mod No) **£8.80**
DECCA 80, 100 **£8.80**

FIDELITY ZX2000, 3000 **£16.00**
GEC 2110 series **£10.60**

ITT CVC5 to 9, CVC20 **£9.80**
ITT CVC25, CVC30 series **£8.80**

ITT CVC45 **£9.80**
PYE 691-697 (state model no.) **£10.00**

PYE 725 (90P) 731 to 741 **£9.20**
PHILIPS G8 **£8.80**

PHILIPS G9 **£8.80**
PHILIPS KT3 **£9.80**

THORN 3000/3500 SCAN, EHT **£6.90**
THORN 8000, 8500, 8800 **£12.80**

THORN 9000 to 9600 **£12.90**
THORN 9800 **£19.80**

THORN TX9 **£14.80**

OTHERS AVAILABLE, PRICES ON REQUEST.
TRIPLERS Full range available. Mono & Colour.

Special Offer: THORN 3000/3500 EHT Tripler **£2.50 p.p. £1.30.**
6-3V CRT Boost Transformers for Colour & Mono **£5.90 p.p. £1.40.**

THORN TX10 focus control **£8.80 p.p. 80p.**
CALLERS WELCOME AT SHOP PREMISES

THOUSANDS OF ADDITIONAL ITEMS, ENQUIRIES INVITED
LARGE SELECTION TESTED COLOUR PANELS POPULAR MODELS


Goods available if in stock immediately over shop counter (Mail order between 3 days and 1 week from receipt of order). ADD VAT 15%

Telephone 01-794 8751, 794 7346

MANOR SUPPLIES

172 WEST END LANE, LONDON, NW6 1SD
NEAR: W. Hampstead Tube Stn. (Jubilee) Buses 28, 159, C11 pass door
W. Hampstead Brit. Rail Stn. (Richmond, Dalston, Stratford, N. Woolwich)
W. Hampstead Brit. Rail Stn. (St. Pancras, Bedford)

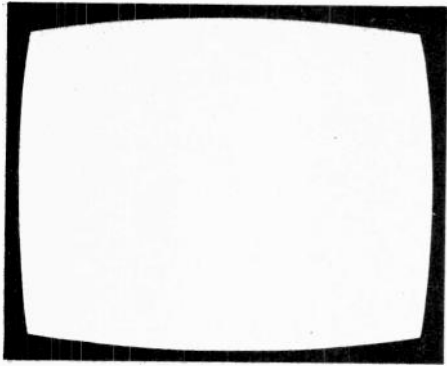Access from all over Greater London.
Mail Order: 64 GOLDERS MANOR DRIVE, LONDON NW11 9HT
PLEASE ADD VAT 15% TO ALL PRICES INCL P+P



TELEVISION

July
1986

Vol. 36, No. 9
Issue 429

COPYRIGHT

© IPC Magazines Limited, 1986. Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., King's Reach Tower, Stamford Street, London SE1 9LS.

SUBSCRIPTIONS

An annual subscription costs £14 in the UK, £17 overseas (by surface mail). Send orders with payment to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex, RH16 3DH.

BINDERS AND INDEXES

Send orders for binders (£4.50) and indexes (75p) to the Editorial Office, Television, IPC Magazines Ltd., King's Reach Tower, Stamford Street, London SE1 9LS. Prices include VAT and postage. Add 60p for overseas orders.

BACK NUMBERS

Some back issues published during the last six months are available from the Editorial Office at £1.40 inclusive of postage and packing. Address as above.

QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope.

Requests for advice on dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Service Bureau". Send to the address given above (see "correspondence").

this month

- 557 Leader**
- 558 Long-distance Television** *Roger Bunney*
Reports on DX reception and conditions, news and a wideband DX aerial design for Bands I/III.
- 563 Servicing Sonatel and Morphy Richards Monochrome Portables** *Ian M. Rees*
Fault notes on these popular portables which sold widely through retail chains and mail order catalogues. Details of an a.g.c. modification for some models.
- 565 TV Fault Finding**
Reports from Steve Illidge, Mick Dutton, Chris Avis, Philip Blundell, Eng. Tech., Paul Hardy and D. R. Bracknell.
- 567 Thorn 8000 Series PSU Modifications** *Tony Livesley, G8JAI*
How to modify earlier sets to use the more reliable dropper assembly employed in later models.
- 568 Teletopics**
News, comment and developments.
- 570 Return of the French Lady** *Les Lawry-Johns*
The French Lady, the Lad's Mother-in-Law, Beardy's Brother - the owners give almost as much trouble as the sets themselves
- 571 Next Month in Television**
- 572 Servicing Sinclair Microcomputers, Part 3** *Ken Taylor*
A start on the Spectrum, with details of the digital computing and supply generator circuits.
- 575 Letters**
- 578 VCR Clinic**
Reports from Derek Snelling, Les Grogan, Mick Dutton, Steve Beeching, T. Eng. and Philip Blundell, Eng. Tech.
- 582 Modern Receiver Circuitry, Part 4** *J. LeJeune*
Operation of the line output stage and EW modulator and generation of the e.h.t.
- 584 The Grundig CUC Series Chassis** *Peter Stubb and Steve Beeching, T. Eng.*
Most troubles with these chassis relate to the switch-mode power supply. How it works, how to tackle faults and some symptoms to note.
- 586 The Development of Colour Tubes, Part 2** *Eugene Trundle*
Tube gun and electron lens design. Operation of the neck magnets.
- 590 Servicing the Panasonic NV7000** *David Botto*
Fault notes on this popular VHS machine with a full account of the power supply arrangements.
- 595 Service Bureau**
- 596 Test Case 283**

OUR NEXT ISSUE DATED AUGUST WILL
BE PUBLISHED ON JULY 16

SUMMER SAVERS!

LONDON WAREHOUSE ONLY

5000 VCR'S MUST GO!
VCR MECHANICALS
IN 25 LOTS

£60

EACH

HOSPITALITY SUITE — 11 AM TO 3.00 PM DAILY
 FREE WINE, BEER AND SANDWICHES

ALL COMPLETE — MANY WORKING

VISIT THE LARGEST EX RENTAL WAREHOUSE
 IN THE UK!! 10,000 sq ft of VCR's & CTV's AT
 UNREPEATABLE SUMMER PRICES

OPEN 6 DAYS WEEKLY AND SUNDAY BY APPOINTMENT AT

ALL WAREHOUSES
 SLIGHTLY SUBSTANDARD **VCR'S**
 (Some Trims and Flaps Missing etc)

IN LOTS OF 25

£40
EACH



BRADFORD
TRITEL TV
 1043 Leeds
 Road
 Thornbury
 Roundabout
BRADFORD

Tel: 0274 665670

LEEDS
TRITEL
DISCOUNT
STORES
 Long Row
 Horsforth
LEEDS

Tel: 0532 590252

SCOTLAND
TRITEL TV
 Unit 4
 Peacock Cross
 Industrial Estate
 Burnbank Road
HAMILTON

Tel: 0698 282141

UNIT E1,
WATERLOO
ROAD,
STAPLES CORNER,
LONDON NW2
Tel: 01 208 2063
OR 01 208 2042



Kent Ledgerwood Wholesale Ltd.

P. V. TUBES

104 ABBEY STREET, ACCRINGTON, LANCOS BB5 1EE.
 Tel: 0254 36521/32611 Telex: 635562 Griffin G (For P.V.)

WE CAN NOW SUPPLY ON AN
EXCHANGE "HEAD FOR HEAD" BASIS

ONLY
£22
 + VAT
 inc P&P



Newlife
VIDEO HEADS

THORN EMI VIDEO HEAD

UPPER DRUM ASSEMBLIES

ORDER FROM 3 VHS TYPES

	L	or	J	or	M
JVC MODELS	HR 3660 HRD 110 HR 7650 HRD 120 HR 7700		HR 7200 HR 7300 HR 7350		HR 3320 HR 3300 HR 3330 HR 4100
AKAI MODELS	VS 9700 VP 77 VS 9800				VS 9300
FERGUSON MODELS	3V16 3V31 3V23 3V35 3V24 3V36 3V38 3V39 3V49		3V29 3V30		3V01 3V00 3V22 3292
BAIRD MODELS	8904 8943 8924 8944 8941		8930 8940		8900 8928 8902 8922
DECCA MODELS	8400 8500		8300		
TATUNG MODELS	8400		8300		
I.T.T MODELS	VR3605 VR3905		VR3913		

SEND YOUR
 OLD HEAD
 PACKED UP
 CAREFULLY
 AND WE
 WILL SEND
 AN
 EXCHANGE
 ONE BY
 RETURN
 POST

P.V.
NAMES
TO
TRUST



New Life Upper Drum Assemblies have been thoroughly life tested and carry a 12 month guarantee covering normal domestic use.

TELEPART



Telegen-1

PRICE £18.35 (Inc. VAT)
 * EXCEPTIONALLY LIGHT AND DURABLE
 * POCKET SIZE FOR OUTSIDE SERVICE
 * PP3 BATTERY POWER SOURCE
 * FIVE DIFFERENT TEST PATTERNS FOR
 COLOUR & MONO TV
 * CROSSHATCH GRID * DOT MATRIX
 * WHITE RASTER
 * HORIZONTALS * VERTICLES
 * 3.5mm JACK SOCKET FOR OPTIONAL
 P.S.U.

A lightweight, extremely portable and versatile pattern generator for black/white and colour T.V. alignment and service at the customer's home. At the turn of a switch, the generator can provide five essential test patterns for correct installation, fast checks and repairs. Pattern stability is first class and compares favourably with other more costly bulky generators only suitable for bench work. The generator is pocket size measuring 10 x 7.5 x 4 cm and weighs only 190 grams. Switched 3.5 mm jack socket allows use of external power supply with battery in situ.

Telegen-2

PRICE £34.45 (Inc. VAT)
 * EXCEPTIONALLY LIGHT & DURABLE
 * COMPACT 10 x 12 x 4.5 cms
 * RED RASTER * GREEN RASTER
 * BLUE RASTER
 * COLOUR BARS
 * 3.5 mm JACK SOCKET FOR P.S.U.
 * PROVIDES UHF SIGNAL APPROX.
 CHANNEL 35



Telegen 2 is a colour bar generator at a very modest price and yet is extremely effective, stable and durable. It is the perfect compliment to Telegen 1, giving colour bars arranged in the following sequence: white, yellow, cyan, green, magenta, red, blue and black. The unit provides a signal in the UHF band approx. Channel 35 and requires a supply of 14 to 18 volts D.C.

Power Supply

A switchable power supply ideally suited to both Telegen 1 and Telegen 2.
 PRICE £4.55 (Inc. VAT)

ALL ITEMS POST AND PACKING £1.44 (Inc. VAT)
 All goods should be delivered within 4 working days.

32 TEMPLE STREET, WOLVERHAMPTON
WV2 4AN. TEL: (0902) 29022

HUSSAIN CENTRAL TV LTD

SALE SALE SALE OF THE CENTURY

BEST QUALITY AT THE LOWEST PRICES IN BRITAIN TODAY

G11 · 660	£25	ITT CVC 20/30	£15
PYE G11	£30	DECCA 80/100	£15
G11 REMOTE (with hand set)	£45	ITT REMOTE (with hand set)	£30
G11 TEXT (with hand set)	£55	TX TEXT (with hand set)	£55
G11 ELECTRONIC TUNER	£30	THORN 9000 REMOTE	£15
THORN 9600	£25	THORN 9200	£27
THORN 8800	£10	THORN 9800	£15
PYE 222	£10	G8 22"	£10
GEC SOLID STATE	£10	GEC STARLINE	£15

**MANY MORE LATE MODEL TVs IN STOCK INC.
REMOTE, TEXT, STEREO TEXT AND 14", 16" PORTABLES**

All TVs have excellent cabinets

VHS: Working. Bring your own tape and try them yourself at **£65**

Untested Electronic VHS £90

Working Electronic VHS £135 Ferguson 3V29, Hitachi 8000, J.V.C. 7200

ALSO IN STOCK

PANASONIC 7200, 7000, 2000, 2010, 366, NV777

HITACHI VT14, VT11, 9700, 9500, 8700, 8500, 8300

FERGUSON 3V31, 3V30, 3V23

ELECTRONIC Beta Full working £60

Untested Beta from £35

PLUS MANY MORE LATE MODEL VIDEOS IN STOCK

Prices are subject to 15% VAT


*Deliveries arranged on quantity or call at our branches
for fast and friendly service from the professionals*

BIRMINGHAM
48-52 PERSHORE ST.
021-622 1023
021-622 1517

PRESTON
UNIT 439
OAKSHOTT PLACE
WALTON SUMMIT IND. EST.
M6 JUNCTION 29.
0772 312101

LONDON
CEDAR HOUSE
NOBEL RD.
ELEY ESTATE
EDMONTON N18 3BH.
01-807 4090
01-884 1314

CHEPSTOW
UNIT 4
BULWARK IND. EST.
GWENT.
0291 271000

WE WILL ONLY SUPPLY TOP QUALITY, BRANDED COMPONENTS. REPUTATION COUNTS WITH US			G.G.L. COMPONENTS 108 SCOTLAND ROAD, CARLISLE, CUMBRIA CA3 9EY PHONE (0228) 20358/39693			BUY WITH 		E.H.T. TRAYS	
INTEGRATED CIRCUITS			TRANSISTORS			THORN/SONY		DIODES	
TYPE			TYPE			LARGE RANGE OF SPARES FOR ABOVE		PRICE	
PRICE (£)			PRICE (£)			MAKES OF TV/VIDEOS INCLUDING INSTRUCTION AND SERVICE MANUALS. PHONE OR WRITE FOR NEW LISTS. WE CAN ALSO SOURCE & SUPPLY OVER THREE THOUSAND I/Cs & SEMI CONDUCTORS.		PRICE	
AN214	1.95	STK0039	3.25	BD701	.85	2N3055	.50	BY127	.10
AN301	3.45	STK0050	5.95	BD707	1.05	2N3773	3.45	BY133	.15
AN303	3.45	STK077	7.25	BF337	.28	15/80H	2.25	BY164	.40
AN305	3.50	STK082	7.45	BF338	.30	15/85R	2.25	BY179	.65
AN7110	1.93	STK2129	8.50	BF458	.30	2SA 771	2.35	BY210/800	.86
AN7114E	2.33	STK415	9.66	BF459	.36	2SA 835	1.55	BY227M	.33
AN7115	2.37	STK430	7.75	BF542	.75	2SB 618	2.45	BY229/600	.27
AN7116	2.35	STK4332	5.95	BF757	.25	2SB 618	2.45	BY298/400	.84
AN7145	3.25	STK433	6.50	BFR90	1.60	2SC 867A	3.25	BY299/800	.25
BA312	1.25	STK435	6.75	BR100	.18	2SC 1034	4.85	BYX10	.20
BA511A	1.95	STK437	7.25	BR101	.32	2SC 1061	1.15	BYX55/600	.26
BA521	1.85	STK439	7.55	BR103	.55	2SC 1114	4.75	BYX71/600	.53
BA532	1.95	STK441	8.50	BR303	2.95	2SC 1124	.97	SKE42/706	.80
BA536	2.55	STK459	7.35	BT106	1.15	2SC 1316	3.20	SKE53/10	1.45
HA1166	2.65	STK461	7.95	BT116	1.30	2SC 1413A	3.95	W005	.55
HA1322	2.10	STK463	9.30	BT151/	1.10	2SC 1492	2.95	1N4001-7	.07
HA1338	2.78	TA7153P	4.30	800R	1.78	2SC 1962	1.65	1N4001-8	.16
HA1342A	2.20	TA7204P	1.90	BU126	1.10	2SC 1969	1.95	1N4501	.67
HA1365 W/W/R	1.95	TA7205AP	1.40	BU205	1.42	2SC 2078	1.55		
HA1374	2.45	TA7208P	1.95	BU208A	1.45	2SC 2335 (Kit)	7.55		
HA1377	3.80	TA7223P	1.85	BU208D	1.85	2SC 2369	3.25		
HA1388	4.20	TA7224P	2.85	BU326A	1.48	2SC 257	2.45		
HA1397	3.90	TA7227P	2.95	BU407	1.12	2SD 588A	1.97		
LA1201	1.75	TA7310	1.55	BU407D	1.45	2SD 725	7.95		
LA1230	2.30	TA7313	1.45	BUC37	35	2SD 770	5.95		
LA1365	2.45	TAA550	.43	BC638	25	2SD 780			
LA3350	1.65	TAA550	.43	BC639	25				
LA4101	1.50	TBA120SB	.90	BD124M	1.05				
LA4102	1.95	TBA120T	1.25	BD131	.33				
LA4400	2.50	TBA120U	1.00	BD132	.33				
LA4430	2.45	TBA520	1.30	BD222	.50				
LA4440	3.55	TBA530Q	1.00	BD225	.55				
LA4445	2.65	TBA540	1.37	BD235	.32				
LA4460	2.95	TBA550	2.45	BD236	.43				
LA4461	2.95	TBA560	1.60	BD237	.40				
MB3712	2.30	TBA720A	2.65	BD238	.39				
MB3713	2.25	TBA750	2.45	BD410	.50				
ML231B	2.35	TBA800	.80	BD437	.70				
ML232B	2.55	TBA810	1.35	BD438	.78				
SAA1250	3.85	TBA820	1.40	BD439	.70				
SAA1251	4.95	TBA890	2.95	BD677	.70				
SAA5010	5.10	TBA920	1.55						
SAA5012	5.70	TBA950	2.65						
SAF1032P	3.25	TCA270	1.55						
SAF1035P	4.55	TCA940	1.55						
SAS560S	1.95	TDA2030	1.95						
SAS570S	1.95	TDA2190M	6.95						
SAS580S	2.40	TDA2576A	3.95						
SAS590S	2.40	TDA2577	4.85						
SL1430	1.95	TDA3651A	3.75						
SL1432	1.75	TDA3652	4.35						
				TV ELECTROLYTICS		PUSH BUTTONS/ NEW TUNERS			
				DECCA 30(400/400)350V	3.99	DECCA/ITT 6 way	8.50		
				DECCA 80-80/100(400)350V		PHILIPS G8 S/L	14.90		
				(800)250V	3.99	PHILIPS G8 S/Q	14.75		
				PHILIPS G8(600)300V	2.65	PYE-G11 P/B	8.50		
				PHILIPS G9(2200)63V	1.45	HITACHI 4 way	8.95		
				PHILIPS G11(470)250V	2.20	ITT CVC5 7 Button	10.40		
				RBM A823(2500/2500)30V	1.65	ITT CVC8/9	12.80		
				RBM T20A(220)400V	2.35	1043/05	8.95		
				THORN1690/1(4700)25V	.94	U321	8.75		
				THORN3500(1000)70V	.99	U322	7.40		
				THORN9000(400)400V	3.10				

SONY SPARES	
C5/C7 Rewind Kit	4.65
C5/C7 Belt Kit	3.50
C6 Rewind Kit	4.35
C7 Pinch Roller	4.05
SG 613/6533	8.95
CX 143A	6.95
TDA 3652	4.35
Large range of Sony spares available	








LINE O/P TR.	
DECCA 80	7.95
DECCA 100	8.50
ITT CVC 20	8.85
ITT CVC 25/30/32	8.95
ITT CVC 45	8.45
PHILIPS G8	8.75
PHILIPS G11	13.50
PHILIPS KT3	9.95
PHILIPS K30	16.50
RBM T20A	10.35
THORN 1615	12.35
THORN 1690/1	9.65

VALVES	
PCF802	1.09
PCL82	1.07
PCL85	.93
PCL86	1.03
PL504	1.59
PL508	2.99
PL509/519	5.99
PY500A	2.25

SUNDRIES	
G8 TRANSISTOR	2.25
G8 ON/OFF SW	1.40
G11 E/W Coil	1.65
G11 Lin Coil	1.80
G11 Bridge Coil	1.35
G11 EHT Lead	2.25
PYE IF Gain MOD	7.85
ITT On/Off SW	1.10
THORN On/Off SW	1.00
CUT OUT 2A	1.95
TX10 FOCUS UNIT	8.95
VCR Pilot Bulb	.70

HITACHI I/Cs	
STR 441	6.95
STR 451	6.95
STR 6020	7.90

SUNDRIES	
G8 TRANSISTOR	2.25
G8 ON/OFF SW	1.40
G11 E/W Coil	1.65
G11 Lin Coil	1.80
G11 Bridge Coil	1.35
G11 EHT Lead	2.25
PYE IF Gain MOD	7.85
ITT On/Off SW	1.10
THORN On/Off SW	1.00
CUT OUT 2A	1.95
TX10 FOCUS UNIT	8.95
VCR Pilot Bulb	.70

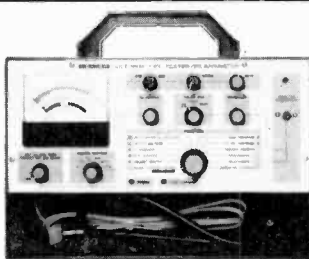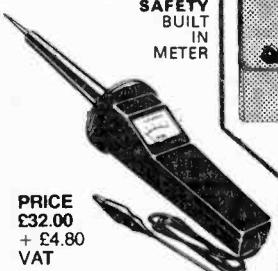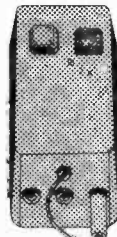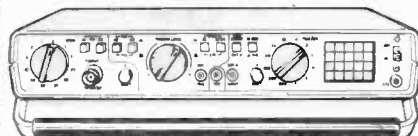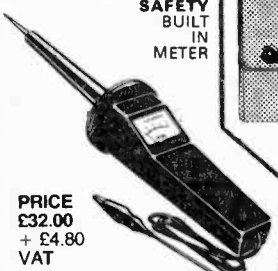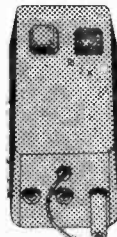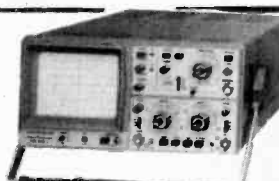INCREASE YOUR PROFITS IMPROVE YOUR SERVICE WITH RELIABLE COST EFFECTIVE TEST EQUIPMENT		
<p>LEADER LCT-910A C.R.T. TESTER-REJUVENATOR</p> <p>Our top selling instrument is designed to readily test the various characteristics and rejuvenation of both colour and B/W C.R.T's.</p> <ul style="list-style-type: none"> Tests for shorts and leakage between electrodes. Tests cathode emission characteristics. Separately checks condition of guns. Removal of shorts and leakage between electrodes. Checks heater warm-up characteristics. Rejuvenation of low emission cathodes with automatic timing. Super rejuvenation with manual control. Complete with tube base adaptors. <p>Size: H 230mm W 330mm D 120mm.</p>	 <p>PRICE £260 + £39 VAT</p>	<p>ALSO AVAILABLE</p> <ul style="list-style-type: none"> Analogue Multimeters Digital Multimeters Oscilloscopes Signal Generators Digital Frequency Meters Pattern Generators CRT Tester/Rejuvenator T.V. Field Strength Meter Digital Capacitance Meter <p>LARGE S.A.E. FOR COMPLETE LIST.</p>
<p>LEADER HIGH VOLTAGE METER EHT PROBE</p> <p>Measures up to 40 K.V. D.C. with SAFETY BUILT IN METER</p>  <p>PRICE £32.00 + £4.80 VAT</p> <p>* FULLY GUARANTEED</p>	<p>LOPT TESTER</p> <p>BK's REVOLUTIONARY DYNAMIC 'LOPT' TESTER</p> <p>Revolutionary L.O.P.T. tester. Operates in dynamic mode which actually tests the L.O.P.T. under high voltage conditions without de-soldering or removal. Size 75x100x40 mm. Supply 240V AC</p>  <p>PRICE £25.99 + £3.90 VAT</p>	<p>THE VERY LATEST SC110A LOW POWER, FULLY PORTABLE OSCILLOSCOPE.</p>  <p>The new Thandar SC110A represents a break-through in oscilloscope development. The SC110A is ONLY TWO INCHES thick and weighs under two pounds, yet retains the standard features and controls of a bench oscilloscope.</p> <p>FITS IN A BRIEFCASE</p> <p>Full Sized Performance</p> <ul style="list-style-type: none"> * 10 MHz bandwidth * Full trigger facilities are provided including TV frame, or TV filtering. * Runs on 4 to 10V DC via disposable batteries, re-chargeable cells, or AC adaptor. * Size 255mm x 148mm x 50mm. <p>PRICE £165.00 + £24.75 VAT</p> <p>Accessories: Carry Case £5.95 + £0.89 V.A.T. x 1 Probe £7.50 + £1.13 V.A.T. x 10 Probe £8.50 + £1.28 V.A.T. x 1/x 10 Switched Probe £10.50 + £1.58 V.A.T. AC Adaptor £6.95 + £1.04 V.A.T.</p>
<p>LEADER HIGH VOLTAGE METER EHT PROBE</p> <p>Measures up to 40 K.V. D.C. with SAFETY BUILT IN METER</p>  <p>PRICE £32.00 + £4.80 VAT</p> <p>* FULLY GUARANTEED</p>	<p>CRT TESTER-REJUVENATOR</p> <p>BK's C.R.T. TESTER-REJUVENATOR</p> <p>Tests and rejuvenates blue, green & red guns separately. Fitted with delta and P.I.L. sockets. Compact size 120x65x60 mm. Supply 240V AC</p>  <p>PRICE £32.00 + £4.80 VAT</p>	<p>HAMEG HM 203-5 20MHZ DUAL TRACE OSCILLOSCOPE</p>  <p>SPECIFICATION:</p> <ul style="list-style-type: none"> * BANDWIDTH DC-20MHz * SENSITIVITY CH1, CH2 2mV-50V/DIV * TIMEBASE 40ns to 0.25 CM * TRIGGER DC-40MHz Auto-Normal-TV * CALIBRATION OUTPUT * CH1 ADD AND INVERT FACILITY * ALT/CHOP SWITCH * LARGE RECTANGULAR SCREEN 8 x 10 cms. * BUILT IN SEMICONDUCTOR COMP. TESTER * SIZE 285mm x 145mm x 380mm. * SUPPLY 110-125-220-240V AC 50-60Hz <p>2 YEAR WARRANTY</p> <p>WITH COMPONENT TESTER</p> <p>PRICE £270.00 + £40.50 VAT</p> <p>Optional probes as above</p>
<p>U.K. Post Paid, Export orders welcome, please deduct V.A.T. and enquire for Overseas carriage cost. Barclaycard/Access orders welcome, or Cheque, Bank Draft, etc., with order please. Large S.A.E. for technical leaflets of complete range. Delivery normally within 7 days.</p>		
<p>B. K. ELECTRONICS Dept. 'T'</p> <p>UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX. SS2 6TR TEL: 0702-527572</p>		

LINEOUT TRANSFORMERS					
3600	DECCA 100	7.95	4866	ELC 1043/30 EXCH TUNER	6.00
3601	DECCA 110	9.80	4867	ELC 1043/30 NEW TUNER	8.25
3604	DECCA 1730/1830	5.50	4972	ELC 2100 EXCH TUNER	12.50
3599	DECCA 80	7.50	5534	GEC 2100 TYPE REPAIR CHGE	10.25
3727	DECCA MS1700-2420	10.13	4675	PHILIPS GE EXCHANGE TUNER	7.50
3729	FIDELITY FTV12/TVR120	15.50	4679	RII RANGERTZ/EXCH TUNER	9.75
5528	FIDELITY ZX3000 Z2	14.50	4680	RII 720 NEW TUNER	12.40
3936	FIDELITY ZX2000/3000	14.50	4678	RII RANGERTZ/NEW TUNER	12.15
3731	GEC 2100-2000	5.50	4666	U321 EXCH TUNER	6.50
3732	GEC 2114	3.50	4667	U321 TUNER NEW	6.25
3734	GEC 3133	3.60	4670	U322 EXCHANGE TUNER	6.50
3733	GEC M1201/M1501H	13.25	4668	U322 NEW TUNER	9.95
3614	GRUNGIUM 5010/5010ETC	12.95	4673	U341 EXCHANGE TUNER	7.25
3755	INDESTI 24E6G	11.25	VALVES		
3617	ITT CV230	7.95	3883	DY802 VALVE	0.75
3618	ITT CV245	9.75	3932	PCF802 VALVE	0.95
3615	ITT CV25-8	10.25	3938	PC202 VALVE	1.05
3620	KORTING A21100 90° HYBRID	14.95	3936	PC184 VALVE	0.85
4508	PHILIPS E2 CHASSIS	10.00	3937	PC186 VALVE	0.95
2862	PHILIPS G9	10.95	3940	PL200 VALVE	1.20
5305	PYE 691 W/RED	5.00	3943	PL504 VALVE	1.40
3628	PYE 725 58V	9.50	3944	PL508 VALVE	2.05
3629	PYE 731 110°	8.95	3945	PL509 VALVE	2.50
3632	RANK A823	5.50	3946	PL519	5.95
3634	RANK T16A	6.95	4670	PL802 VALVE	4.95
3636	RANK T26A	12.95	3950	PY500A VALVE	2.25
3726	RANK 126A	15.50	3951	PY801 VALVE	0.95
3637	RANK 2178	11.25	THORN SPARES		
3770	REDIFUSION MK1 CHAS	9.30	2897	T1590 MAINS TRANSFORMER	9.80
3771	REDIFUSION MK3 CHAS	14.95	2920	TX10 FOCUS UNIT	7.54
3775	SANYO CT7501	16.50	4930	T1800 MAINS TX	7.92
THORN 1400 SERIES	5.95	5430	T1890 MAINS TRANSFORMER	6.20	
3644	THORN 1500 2ST	5.95	4973	T1890 SLOW MOT. TUN. P.D.T.	3.90
3645	THORN 1500 3ST	5.95	2906	T3000/3500 A1 SWITCH	0.68
3646	THORN 1600 SERIES	10.85	2904	T3000/3500 MAINS TX	5.00
3647	THORN 1600 SERIES	10.85	2908	T3000/3500 METAL CUT OUT	2.34
3648	THORN 1615 SERIES	8.95	4957	T3500 100R CONVERG POT	0.85
3649	THORN 1690/91 SERIES	10.95	3777	T3500 200R CONVERG POT	0.56
3713	THORN 1790	8.95	4978	T3500 200R CONVERG POT	0.56
3714	THORN 3187	15.25	4865	T3500 30R CONVERG POT	0.85
3652	THORN 3K 3KS EHT TX	8.95	2905	T3500 5MEG A1 POT	1.17
3651	THORN 3K 3KS	8.95	4569	T3500 SPARK GAP 1/1500	0.51
6172	PHILIPS GB SPECIAL	7.90	2907	T3500 THICK FILM VID. LOAD	1.45
2868	PHILIPS KT3	10.95	4412	T3800 MAINS ON/OFF SW.	7.10
EHT TRAYS					
5400	BG1895-641	7.50	3203	T818 220V BRIGHT CTRL UNIT	2.18
5403	BG1897-642	7.50	2909	T818 220V FOCUS CTRL UNIT	2.56
5404	BG2091-642/333	7.50	4411	T8500 MAINS CHoke	17.45
3663	DECCA 1230	7.95	2910	T8500 MAINS TX	14.15
3665	DECCA 1830	7.11	2918	T8500 PLASTIC CUT OUT	3.72
3667	GEC 1026/C5108	3.95	2916	T8500 FOCUS UNIT	3.80
3677	ITT CV245	7.50	4142	T9000 FOCUS CONTROL UNIT	2.85
3675	ITT CV25-9	7.95	3273	T9818 220V BRIGHT CTRL UNIT	2.18
3678	KORTING H/RF BRD	7.95	2909	T9818 220V FOCUS CTRL UNIT	2.56
3683	PHILIPS 570 (5 LEAD)	4.50	2911	T8500 MAINS CHoke	17.45
3684	PHILIPS G9	4.00	2915	T8500 FOCUS UNIT	3.80
3685	PHILIPS KT3	6.95	4429	T8500 MAINS CHoke	17.45
3686	PYE 691/897	6.95	4437	TX10 0.022 VCAP	0.25
3688	PYE 725/731/741	8.95	4658	TX10 0.022 TUNING POT	0.64
5395	SEIMANS W181965	8.50	2938	TX10 CHOPPER DRIVER TX	3.27
5393	SEIMANS W1952	8.95	4427	TX10 SW. NONRETR. CONT.	2.82
4696	SEIMENS TX1961/17	11.95	2922	TX10 LINDER DRAWER ASSY	1.95
5406	TCE 1400 LARGE SCRIN	4.95	4859	TX9 4" RND 15R SPEAKER	6.95
3636	TCE 1500 17"-19"	5.65	2937	TX9 INPUT CHOKE L65	12.05
3697	TCE 1500 22" & 24"	4.95	2936	TX9 L64 BILIFEAR CHoke	4.25
3698	TCE 1600 SERIES	7.95	DECCA SPARES		
3702	TCE 4003	2.85	4616	DECCA 100 0.01 2KV CAP	0.98
3703	TCE 9000	2.85	2933	DECCA 100 80EGE TX	2.25
3699	TCE 3000/3500	7.95	2932	DECCA 100 FOCUS CONTROL	0.75
3706	TV11 EHT STICK	0.65	4615	DECCA 100 LINE DRIVE TX	2.77
3709	TV25 EHT STICK	2.45	2924	DECCA 100 LINE DRIVE TX +VOL	2.85
5275	TV48 EHT STICK	2.45	4603	DECCA 2230 10R FUSIBLE	2.15
3705	UNIVERSAL EHT TRAY U.K.	4.95	2930	DECCA 2233 PSH PSH SH	5.14
TV ELECTROLYTICS					
3547	DECCA 1030 400K2/350V	2.90	2926	DECCA 30 SER 3RS RESIS.	1.10
3549	DECCA 1030 100+300 350/250V	4.65	2924	DECCA 30 SER MAINS TX	2.92
4864	DECCA 80/100CHAS 100/400V	6.00	2929	DECCA 4001 SER 47K SH+VOL	2.45
5304	FIDELITY ZX2000 300 385V	4.95	2938	DECCA 80 470R SH+VOL	2.45
5303	FIDELITY ZX3000 220 385V	3.95	RESISTORS		
3557	ITT CV20/RII T20 220/400	1.20	CARBON		
3556	ITT CV25-9 200K2+25+75ETC	3.25	STANDARD RANGES		
3560	PHILIPS G11 470U/7250V	1.70	1/2 WATT X 10		
3559	PHILIPS G9 2200/63V	1.65	1/4 WATT X 10		
3561	PHILIPS G9 200A+25K2/385V	2.55	0.25 4787 ITT CV20 MAINS SWITCH		
3554	PHILIPS G9/GEC 2110 600/300V	3.16	0.45 4876 ITT CV25 8W2 2KV CAPS		
3558	PHILIPS G9/PYE 731 600/300 PC	3.16	0.60 4789 ITT CV25 8W2 LOAD CAPS		
3562	PYE 725/731 800/250V	2.90	4.567 ITT CV25/30 MAINS SW.		
3564	PYE 691/897 200+300/250V	2.90	2.969 ITT CV23 DRIVER TX		
3575	RII A823 2500K2/25V	1.48	0.74 4568 ITT CV32 REMOTE MAIN SH.		
3588	TCE 3000/3500 1000/70V	0.89	0.89 2971 ITT CV32 SH MDDE TX		
3585	TCE1500 150X2+100 300V	1.90	4.795 ITT CV24S ON/OFF SWITCH		
3587	TCE3000 200+100K2/350V	2.86	3.268 ITT CV25 1MFD 250V CAP		
MIXED DIELECTRIC CAPACITORS					
4270	010 600V X5	0.75	3279	2MΩ HV FOCUS RESISTOR	0.46
4272	022 1KV X5	1.05	3280	27MΩ HV FOCUS RESISTOR	1.65
4273	033 1KV X5	1.40	3281	33MΩ HV FOCUS RESISTOR	1.50
4274	047 600V X5	0.85	3282	47MΩ HV FOCUS RESISTOR	1.50
4275	047 1KV X5	1.80	3283	56M HV FOCUS RESISTOR	1.50
4276	01 600V X5	1.20	MAINS DROPPERS		
4277	01 1KV X5	1.95	3025 MAINS DROPPER RANK A640		
4278	01 1250V X5	2.00	3013 MAINS DROPPER DECCA 80/100		
4279	01 2KV X1	0.75	3016 MAINS DROPPER GEC 2010		
4280	02 600V X5	1.45	3030 MAINS DROPPER THORN 3600		
4281	02 1KV X1	0.74	3030 MAINS DROPPER THORN 1500		
4282	04 1KV X1	1.02	4910 MAINS DROPPER DECCA 100 27R5		
4283	4700P/1.5KV X5	1.89	3034 MAINS DROPPER THORN 9800		
4271	001 1KV X5	1.60	3027 MAINS DROPPER THORN 1400		
SLIDE CONTROLS					
4883	100K LIN STD TV	0.55	3026 MAINS DROPPER RANK A823		
4884	100K LIN STD TV	0.55	3028 MAINS DROPPER THORN 1300		
4885	15K LIN STD TV	0.55	3018 MAINS DROPPER PHILIPS G8		
4874	1K LIN STD TV	0.55	3022 MAINS DROPPER PYE 725/731		
4881	2K LOG STD TV	0.55	3017 MAINS DROPPER PHILIPS G9		
4875	3K3 SEMI LOG STD	0.55	3019 MAINS DROPPER PHILIPS G8 47R		
4885	470R LOG STD TV	0.55	3033 MAINS DROPPER THORN 6500/8000		
4719	470R LM STD TV	0.55	5386 MAINS DROPPER DECCA 80		
4877	4K7 LIN STD TV	0.55	5633 PYE CT200 PHILIPS 579 DROPPER		
4878	4K7 LOG STD TV	0.55	UNIVERSAL CONVERGENCE POTS		
PRESETS					
STANDARD RANGES					
VERTICAL STANDARD X 5					
HORIZONTAL STANDARD X 5					
VERTICAL MINI X 5					
HORIZONTAL MINI X 5					
TUNER UNITS					
4662	DECCA 300 SERIES MECHANICAL	4.95	4662	ELC 1043/30 EXCH TUNER	6.50
4664	ELC 1043/30 EXCH TUNER	8.00	4663	ELC 1043/30 NEW TUNER	8.25

PLEASE ADD £1.25 POST & HANDLING THEN 15% VAT TO TOTAL.

QUICK SAVE TV SPARES THE COACH HOUSE, MUXTON LANE, TELFORD, SALOP

FULL LIST OF OVER 3000 ITEMS SENT WITH ORDER OR SEND 9" x 4" SAE. PLEASE USE STOCK NUMBER WHEN ORDERING, OR USE SET MAKER'S PART NUMBER. ACCESS AND VISA ACCEPTED. OFFICIAL ORDERS FROM GOVERNMENT OR SCHOOLS WELCOMED. ALL GOODS ARE STOCK ITEMS.



CHROMOVAC

**QUALITY
REBUILDS**

**SPECIAL
OFFERS!**
ON
INLINE

Get on the hot-line today!

SUPERIOR QUALITY TUBES **061**
DELTA RE-BUILDS 681 2959
most types of Inline Re-builds or
new ex-stock PRICES SUBJECT TO
GLASS EXCHANGE

Delta Rebuilds

Up to 19" £28
Up to 22" £30
Up to 26" £34
110° up to 22" £34
110° up to 26" £38
Low focus +£2
A47 342 New £28
17FHP New £30
470EHB New £30
Delta only. Less 5% 5+

Inline Rebuilds

Up to 22" ... From £40
Up to 26" ... From £45
A56 - 540x £56
A66 - 540x £58
Bonded Coil +£5

ALL SIZES OF NEW AND
REBUILT MONO TUBES
AT COMPETITIVE PRICES

IN LINE TYPES EX-STOCK SELECTION NOT REBUILDS

Please enquire types not listed

370 HFB-A37-590 £45	AXT 56-001 £62
370 HUB £45	660 AB £65
AXT 37-001 £45	A67-701 £65
420 CSB £45	670 CZB £65
420 EDB-A42-590 £45	A66-540 with coil £85
420 EZB £45	420FSB £55
420 ERB £45	
470 KUB £50	
510 UFB/A51-590 £55	
510 VSB £60	
AXT 51-001 £60	
560 DYB-560 DTB £62	
560 EGB £62	
560 CGB £62	
560 DMB £62	

MIN. CARRIAGE £5
10+ CARRIAGE PAID
TERMS
Cash with order
ALL PRICES
EXCLUSIVE OF VAT

QUANTITY
DISCOUNT
AVAILABLE
Ask for details

★ ASK FOR DETAILS. OUR TECHNICAL DEPT.
WILL ADVISE YOU ON PROBLEMS YOU MAY
ENCOUNTER ON FITTING INLINE TUBES
DELIVERY: Ex stock items immediate dispatch on receipt of order.
Others allow 14 days.

THE COMPANY WHO PUT HIGH STANDARDS FIRST

CHROMOVAC

CHROMAVAC LTD., PUMP STREET,
HOLLINWOOD, OLDHAM OL9 7LR

Ask for Mr Butterworth ON: 061-681 2959

LOOK AHEAD!

WITH MONOLITH MAGNETIC TAPE HEADS

DOES YOUR VCR GIVE WASHED OUT NOISY
PICTURES - ITS PROBABLY IN NEED OF A NEW
HEAD - FAST FROM OUR EX-STOCK DELIVERIES.
SAVE £££'s ON REPAIR CHARGES.

Our replacement video heads
fit most models of VHS or
Betamax VCR's. Following our
replacement guide and with a
practical ability, you can do the
whole job in your own home
with our head replacement kit.

**VIDEO HEADS
AT LOW LOW
PRICES!**

VIDEO HEAD REPLACEMENT KIT



VMC-02 KIT ONLY £19.95 inc. VAT. + £2.50 p&p
(Kit does not include video head)

TELEPHONE US NOW FOR INFORMATION OF THE
REPLACEMENT HEAD FOR YOUR VIDEO RECORDER.
CATALOGUE: For our full Catalogue of Replacement
Video and Audio Cassette/Reel to Reel Heads, Motors,
Mechanisms, etc. Please forward 50p p&p.

THE MONOLITH ELECTRONICS CO. LTD.
5-7 Church Street, Crewkerne, Somerset TA18 7HR, England.
Telephone: Crewkerne (0460) 74321 Telex: 46306 MONLTH G

TRADERS
**GET ON THE
BALL!**

FOR THE
WORLD CUP '86

CELTEL

WE HOLD A LARGE STOCK OF
EX-RENTAL TV'S & VIDEO'S

TV's
TX 9/10, 9660
MANY MORE SETS
AVAILABLE ON
REQUEST.

TOP
QUALITY
SETS

VCR's
VHS AND BETA
WORKING STOCK
TO ORDER SPECIAL
DISCOUNTS FOR
QUANTITY



CELTEL

2 BREACH RD, WEST THURROCK.
Tel: Purfleet (0708) 861404

AN127Q	£1.75	CX143A	£7.50	HA11788	£4.50	M54543L	£2.75	TA7136P	£1.00	UPC1028H	£3.90	2SA899	£0.75	2SC1427	£3.30
AN203	£2.20	CX157	£3.95	HA11816NT	£6.50	M45481	£5.75	TA7137P	£3.80	UPC1031H	£1.80	2SA940	£0.80	2SC1505	£0.70
AN210	£1.75	CX158	£3.50	HA11828NT	£3.50	M3705	£1.60	TA7139P	£1.50	UPC1032H	£3.50	2SA952	£0.35	2SC1546	£0.30
AN211A	£2.25	CX162	£2.50	HA12035	£3.50	M3730	£1.50	TA7145P	£1.80	UPC1035C	£1.20	2SA1011	£0.30	2SC1664	£2.50
AN214Q	£1.80	CX161A	£2.50	HA12413	£2.50	M3732	£1.75	TA7146P	£2.50	UPC1037H	£0.75	2SA1103	£0.75	2SC1682	£0.30
AN217B	£2.20	CX162	£3.40	HA13402	£3.50	M3733	£1.75	TA7150P	£1.80	UPC1043C	£1.20	2SA1103	£1.90	2SC1741	£0.30
AN228W	£2.75	CX170	£6.50	HA13403	£3.50	M3734	£2.60	TA7152P	£1.70	UPC1156H	£1.40	2SA1104	£1.90	2SC1815	£0.25
AN236	£2.50	CX181	£8.50	HA13430A	£7.50	M3735	£3.50	TA7173P	£1.60	UPC1158H	£3.60	2SA1105	£2.25	2SC1826	£0.60
AN239Q	£3.80	HA1124A	£2.75	LA1111P	£0.80	PLO1A	£2.30	TA7176P	£1.50	UPC1161C	£3.50	2SA1106	£2.50	2SC1849	£0.30
AN240P	£1.50	HA1125	£1.50	LA1201	£0.80	PLO3A	£2.30	TA7189P	£3.50	UPC1163H	£0.60	2SA1198	£0.35	2SC1945	£3.50
AN241P	£2.50	HA1127	£1.75	LA1222	£0.80	STK111	£0.50	TA7200P	£2.00	UPC1167C	£0.70	2SB22	£0.30	2SC1946A	£3.50
AN247P	£2.50	HA1149	£1.40	LA1230	£1.50	ST1-1125H	£0.75	TA7201P	£2.00	UPC1168C	£0.90	2SB24	£0.70	2SC1957	£0.80
AN259	£2.75	HA1151	£2.50	LA1240	£1.75	STK011	£3.75	TA7202P	£2.00	UPC1170H	£0.75	2SB24	£0.70	2SC1969	£1.30
AN262	£1.50	HA1156	£1.10	LA1320	£1.50	STK013	£6.25	TA7203P	£1.80	UPC1171C	£1.50	2SB341V	£2.60	2SC2021	£0.30
AN271A	£2.50	HA1166	£1.60	LA1365	£1.50	STK014	£6.25	TA7204P	£1.10	UPC1176C	£1.20	2SB405	£0.80	2SC2026	£0.65
AN274	£2.50	HA1196	£3.75	LA1368	£2.20	STK015	£5.00	TA7207P	£1.50	UPC1180C	£1.00	2SB426	£2.60	2SC2028	£0.75
AN285	£2.50	HA1197	£1.75	LA1420	£2.20	STK016	£4.75	TA7208P	£1.50	UPC1182H	£1.40	2SB471	£3.50	2SC2075	£0.25
AN303	£2.50	HA1199	£1.40	LA4200	£1.75	STK020	£4.50	TA7210P	£2.00	UPC1181H	£1.00	2SB492	£0.75	2SC2078	£0.75
AN313U	£2.75	HA1306W	£1.60	LA3011	£1.60	STK022	£5.25	TA7214P	£2.50	UPC1182H	£1.00	2SB5090	£1.70	2SC2091	£0.60
AN315	£2.00	HA1319	£2.00	LA3155	£0.95	STK025	£6.75	TA7215P	£1.80	UPC1183H	£1.20	2SB534	£0.60	2SC2092	£0.95
AN316	£3.50	HA1322C	£1.60	LA3160	£0.90	STK041	£6.50	TA7215P	£1.20	UPC1185A	£2.20	2SB536	£0.95	2SC2098	£0.95
AN318	£4.75	HA1398A	£1.60	LA3201	£0.95	STK077	£3.95	TA7220P	£1.75	UPC1185A	£0.80	2SB546	£1.50	2SC2166	£0.95
AN331	£2.75	HA1342A	£1.70	LA3300	£1.40	STK078	£5.50	TA7222AP	£1.20	UPC1187V	£1.90	2SB561	£0.95	2SC2238	£0.65
AN360	£1.60	HA1366W	£1.50	LA3301	£1.20	STK080	£7.20	TA7223AP	£1.20	UPC1190C	£0.95	2SB698	£0.95	2SC2278	£0.70
AN362L	£1.30	HA1366WR	£1.50	LA3350	£1.20	STK082	£7.75	TA7224P	£2.75	UPC1191H	£0.95	2SB754	£0.95	2SC2335	£1.50
AN366P	£1.50	HA1367	£3.25	LA3361	£2.00	STK086	£9.25	TA7225P	£2.50	UPC1198H	£0.70	2SB770	£0.90	2SC2365	£4.25
AN610P	£1.75	HA1368	£1.60	LA4030P	£1.20	STK430	£4.75	TA7226P	£2.20	UPC1200V	£0.85	2SB772	£0.95	2SC2370	£1.75
AN612	£1.75	HA1368R	£1.65	LA4031P	£1.40	STK435	£5.00	TA7227P	£1.90	UPC1211V	£1.90	2SC372	£0.30	2SC2540	£12.75
AN5722	£1.50	HA1370	£2.75	LA4032P	£1.40	STK443	£6.95	TA7227P	£1.50	UPC1215V	£1.25	2SC373	£0.30	2SC2570	£0.70
AN5730	£1.85	HA1374	£2.50	LA4051P	£1.50	STK443	£6.95	TA7227P	£1.50	UPC1215V	£1.25	2SC380A	£0.95	2SC2577	£1.90
AN5732	£1.85	HA1377A	£2.30	LA4100	£1.00	STK437	£6.30	TA7230P	£1.75	UPC1216V	£1.40	2SC458	£0.20	2SC2578	£2.20
AN5753	£1.95	HA1388	£2.35	LA4101	£1.20	STK439	£5.50	TA7310P	£1.40	UPC1217G	£1.60	2SC480	£0.20	2SC2579	£2.20
AN6250	£2.30	HA1389	£1.75	LA4102	£1.20	STK441	£6.00	TA7312P	£3.30	UPC1218H	£1.50	2SC481	£0.30	2SC2580	£2.20
AN6344	£4.75	HA1389R	£1.40	LA4110	£1.40	STK443	£6.95	TA7313AP	£1.75	UPC1222C	£0.95	2SC503Y	£1.75	2SD24	£0.50
AN7105	£2.20	HA1392	£2.30	LA4112	£1.30	STK443	£6.95	TA7315AP	£1.75	UPC1225H	£1.60	2SC537	£0.25	2SD187	£0.60
AN7110	£1.46	HA1394	£2.75	LA4120	£2.50	STK457	£3.50	TA7315AP	£1.75	UPC1226C	£1.25	2SC537	£0.25	2SD187	£0.60
AN7114E	£1.60	HA1387	£2.50	LA4125	£1.00	STK459	£5.75	TA7325P	£0.85	UPC1229V	£1.60	2SC620	£0.50	2SD313	£0.95
AN7115E	£1.60	HA1398	£2.40	LA4140	£0.70	STK460	£7.50	TA7328	£1.60	UPC1229V	£1.25	2SC632	£0.30	2SD325	£0.65
AN7120	£1.40	HA1457W	£0.90	LA4182	£2.00	STK461	£6.50	TA7607AP	£2.75	UPC1230H	£2.50	2SC681	£1.00	2SD348	£4.50
AN7130	£1.50	HA11215A	£2.30	LA4192	£1.95	STK463	£7.40	TA7808	£3.50	UPC1230H	£2.50	2SC681	£1.00	2SD348	£4.50
AN7145M	£1.80	HA11221	£4.25	LA4200	£1.90	STK465	£8.50	TA7809P	£2.75	UPC1238V	£0.85	2SC681A	£1.00	2SD352A	£0.50
AN7146M	£1.95	HA11223W	£3.80	LA4220	£1.20	STK025	£4.95	TA7611	£1.50	UPC1277H	£2.75	2SC710	£0.30	2SD3717	£1.30
AN7154	£1.75	HA11225	£1.95	LA4230	£1.75	STK0029	£4.95	TA7658P	£1.50	UPC1278H	£2.50	2SC732	£0.30	2SD401	£1.50
AN7156N	£2.40	HA11235	£2.00	LA4400	£1.90	STK0039	£4.25	UHC1001	£4.80	UPC1350C	£1.30	2SC733	£0.30	2SD467B	£0.30
AN7158N	£3.25	HA11423	£4.75	LA4420	£1.40	STK0040	£5.50	UHC1004	£4.80	UPC1356C	£2.20	2SC792	£2.85	2SD4688	£0.50
AN7168	£2.50	HA11701	£4.50	LA4422	£1.20	STK0049	£3.75	UPC20C	£6.00	UPC1356C	£2.20	2SC799	£1.75	2SD716	£1.50
AN7310	£0.80	HA11702	£4.90	LA4430	£1.20	STK0059	£6.00	UPC21C	£1.80	UPC1358H	£1.60	2SC828	£0.20	2SD816	£0.30
AN7311	£1.00	HA11703	£4.50	LA4440	£1.30	STK0080	£6.50	UPC22C	£1.25	UPC1360C	£1.95	2SC840	£1.50	2SD916	£0.95
BA301	£1.75	HA11704	£4.60	LA4460	£1.75	STK0209	£3.75	UPC22C	£1.25	UPC1363C	£3.00	2SC867	£2.75	2SD1133	£1.75
BA311	£0.95	HA11705	£6.50	LA4461	£1.50	STK2230	£6.00	UPC555	£0.60	UPC1365C	£1.50	2SC900	£0.35	2SD1276	£1.50
BA313	£0.75	HA11706	£4.75	LA4500	£2.50	STK342	£6.95	UPC568H	£0.60	UPC1367H	£1.50	2SC930	£0.35	2SD49	£4.00
BA318	£1.30	HA11710	£5.50	LA4505	£2.50	STK342	£6.95	UPC571	£1.95	UPC1368H	£1.95	2SC945	£0.35	2SD50	£4.00
BA402	£0.75	HA11711	£9.50	LA6458	£0.90	STK3042	£6.50	UPC571	£1.95	UPC1370C	£1.95	2SC1034	£3.75	2SK19	£0.50
BA511A	£1.80	HA11713	£6.00	TA7800	£1.95	STK5211	£6.75	UPC575H	£1.00	UPC1373H	£1.95	2SC1061	£0.95	2SK38A	£2.70
BA514	£1.75	HA11714	£5.75	TA7806	£2.50	STK541	£6.50	UPC575H	£1.75	UPC1382C	£2.50	2SC1096	£0.60	2SK49	£0.60
BA521	£1.50	HA11715	£5.25	LC7120	£3.50	STK5451	£6.75	UPC575H	£1.00	UPC1382C	£2.50	2SC1114	£3.50	2SK120	£0.90
BA527	£1.50	HA11716	£6.25	LC7130	£3.50	STK5720	£6.80	UPC575H	£1.00	UPC1458H	£4.50	2SC1115	£3.75	2SK134	£4.00
BA532	£1.50	HA11717	£6.25	LC7131	£3.75	STK5730	£6.75	UPC577	£0.70	UPC1458H	£4.50	2SC1124	£0.80	2SK135	£4.00
BA536	£2.25	HA11718	£4.75	LC7136	£2.75	TA7050P	£0.80	UPC577	£0.70	UPC1384C	£2.50	2SC1162C	£0.80	SK22	£1.75
BA612	£1.80	HA11724	£18.25	LC7137	£2.75	TA7051P	£0.80	UPC577	£0.70	UPC1384C	£2.50	2SC1170B	£2.95	SK345	£0.60
BA1310	£1.75	HA11725	£16.00	M5106P	£1.75	TA7054	£1.70	UPC582	£0.95	2SA1013	£0.60	2SC1170B	£2.95	SK388	£0.50
BA1320	£1.75	HA11726	£16.00	M5115P	£2.25	TA7054	£1.70	UPC582	£0.95	2SA1013	£0.60	2SC1170B	£2.95	2DA1515	£4.30
BA1330	£1.75	HA11727	£9.50	M5134P	£2.75	TA7066	£1.50	UPC595C	£1.70	2SA430	£0.35	2SC1308	£2.70	2DA2002	£0.90
BA3604	£2.20	HA11736	£16.00	M5135P	£2.30	TA7070P	£1.25	UPC596	£1.50	2SA499	£0.35	2SC1316	£2.95	2DA2003	£0.90
CK0642	£8.50	HA11745	£9.50	M5153L	£1.50	TA7073	£2.40	UPC1001H	£2.00	2SA539	£0.30	2SC1317	£0.30	2DA2004	£2.20
CK0658	£2.50	HA11747	£9.50	M5153L	£1.50	TA7074P	£1.95	UPC1009C	£1.20	2SA562	£0.35	2SC1342	£0.75	2DA2005	£2.75
CK075B	£2.20	HA11747ANT	£9.50	M5154AL	£1.75	TA7074P	£1.95	UPC1017G	£1.30	2SA634	£0.65	2SC1364	£0.40	2DA2006	£2.20
CK095C	£2.80	HA11749	£4.50	M5155BL	£2.50	TA7108	£1.50	UPC1018C	£1.25	2SA643	£0.35	2SC1364	£0.40	2DA2006	£2.20
CK100D	£5.75	HA11750	£5.00	M51561L	£2.50	TA7109	£2.30	UPC1020	£1.75	2SA673	£0.70	2SC1417	£0.30	2DA2007	£1.40
CK101G	£2.75	HA11753NT	£8.50	M51571L	£2.50	TA7119	£1.75	UPC1023H	£2.30	2SA699A	£1.95	2SC1417	£0.30	2DA2030	£1.40
CK130	£4.50	HA11758NT	£8.50	M51581L	£1.75	TA7120P	£1.50	UPC1025H	£2.30	2SA762	£1.95	2SC1419B	£0.75	2DA2030	£1.40
CK136	£5.50	HA11768	£4.50	M51521AL	£1.75	TA7130P	£0.80	UPC1026C	£1.00						

T. POWELL

16 PADDINGTON GREEN,
LONDON W2 1LG
Tel: 01-723 9246 (Answerphone)

VIDEO BELT KITS		LATE EXTRA	
AKAI VS-2EG/5EG (5)	£1.50	ANS033	£5.25
AKAI VS 9700EG (6)	£1.75	ANS620X	£6.25
FISHER VBS 7			



EAST CORNWALL COMPONENTS



NEW 1986 CATALOGUE is now available — range of components greatly increased — over 136 pages fully illustrated. Price £1.00 per copy (free upon request with orders over £15). Includes 50p Credit Note, Special Offer Sheets, Order Form and Pre-Paid Envelope. Order your copy now — will be sent within 7 days.

ORVX PORTASOL
PORTABLE GAS SOLDERING IRON
 Powered by ordinary lighter fuel. 60 mins. cont. use, adj. temp.
 106/5W. Price **£13.90**

CHART RECORDER SPECIAL
 Brand new 3 channel pen recorders complete with charts. Full spec. upon request. Once only price **£40 + £10 p&p + VAT**.

SERVICE AIDS

Switch Cleaner **1.24**
 Circuit Freezer **1.40**
 Foam Cleanser **1.22**
 Aero Klene **1.14**
 Plastic Seal **1.34**
 Excel Polish **1.16**
 Antistat Spray **1.48**
 Aero Duster **1.48**
 Super 40 **1.86**

Fire Extinguisher **1.10**
 Silicone Grease **3.28**
 Aero **1.50**
 Ditto Tube **1.66**
 Heat Sink **1.40**
 Compound **1.70**
 Solids Mop **0.12mm**
 Ditto 0.6mm **0.76**
 Industrial Reel **1.10**
 0.12mm length **£2.90**

SONY T.V. & VIDEO SPARES

Ilder Kit SLC5.7 (Rewind Kit) **A-670-634-8A £4.80**
 SLC6 (Rewind Kit) **A-670-638-1A £3.06**
 Video Head SLC9UB **A-676-208-8A £45.05**
 SLC5C6/C7 **A-676-212-9A £43.05**
 Motor Kit MT Gensec **X-354-931-4A £14.44**
 Limiter Assembly SLC7UB **X-365-331-00 £2.45**

Power Switch KV General **1-554-820-11**
 Diodes ICs Thyristors Belts Transistors **£55.50**
 Remote Controls Instruction & Service Manuals


POTENTIOMETERS

Carbon Track Rotary 0.25W Log & 1 in values. All 1/4in Spindle 20ml body dia Shaft 2" long
 4K7-2M2 Single Gang Log **.40 10/3.50**
 1K - 2M2 Single Gang Lin **.30 10/3.50**
 5K - 2M2 Single Gang DP Switch Log **1.05 10/3.50**
 5K - 2M2 Double Gang Log & Lin **1.25 10/10.50**

VALUES

Enquiries are well-coming for any other value not listed here.

Type	Price (£)	Type	Price (£)
AZ31	4.50	PC300	1.40
AZ41	1.98	PC301	1.40
DAF96	1.00	PC302	3.00
DF96	0.78	PC303	3.00
DK96	2.65	PC304	1.40
DM71	1.38	PC305	1.40
DY96/87	0.65	PC306	1.40
DY96/2	0.86	PC307	1.40
CV950	2.50	PC308	1.40
CV4015	2.00	PC309	1.40
EV180	6.50	PC310	1.40
EAB80	0.98	PC311	1.40
EA42	1.50	PC312	1.40
EB91	0.80	PC313	1.40
EB91	0.80	PC314	1.40
EB91	0.80	PC315	1.40
EB91	0.80	PC566	1.40
EB91	0.80	PC567	

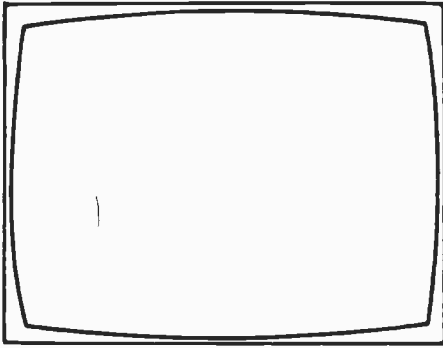

TELEVISION

Broadcasting Changes

The control of broadcasting seems to be a perennial concern of governments and politicians. Rigid government control is of course a feature of totalitarian societies where broadcasting is a state organ used primarily to inform the population of the state's views, edicts and wishes, with some state approved entertainment thrown in to leaven the mixture. Many democratic countries do little better. Some try ever so hard and end up with monumental dullness. One thing we can be proud of in the UK is the independence of our broadcasters, both from detailed control by the government of the day and excessive commercial interests, and the general quality of the services they provide. The tradition of independence was established by the early leaders of the BBC and has been strengthened in more recent decades by the IBA. The system has served us well and we should be grateful for it.

But this doesn't stop governments and politicians from questioning the system and generating a certain amount of fuss from time to time. This usually starts when the subject of financing the broadcasters comes up for review. Primarily this means the licence fee and the BBC's budget. The rapid inflation of the seventies made matters a lot worse since the BBC kept having to ask for substantial increases. Last time round the problem wasn't so much money as the hope of a section of the advertising world that it could persuade the government to open up the BBC's services to advertising. This would have meant lots of work for agencies but in the event has been largely discounted by the view that spreading advertising, which is unlikely to expand greatly in total, too thinly across the various services would simply jeopardise the existing independent TV operators. Be that as it may the government's reaction last time round, in March 1985, was to set up the Peacock Committee on the future financing of the BBC.

The Committee is due to report to the Home Secretary this month (June), with publication of the report likely in July. In view of the amount of leaking and press comment on the Committee's deliberations the report should contain few surprises. It's understood that the main conclusions will be that advertising on BBC television would not be of overall benefit to TV broadcasting in the UK, that the BBC's licence fee should be linked to the cost of living for the next ten years, that Channel 4 should be financed independently of the rest of the ITV network, and that the radio broadcasting arrangements should be altered.

There's good reason to review the broadcasting arrangements from time to time. After all what's appropriate at one time is not necessarily suitable at another. Times change and in particular broadcasting technology is likely to evolve rapidly over the next few years as satellite systems are established. The BBC has been with us for nearly 60 years and the IBA was set up 30 years ago. They continue to do a good job and the Peacock Committee's recommendations don't sound particularly alarming. More like minor adjustments here and there. Publication of the report is nevertheless quite likely to cause a stir. That's inevitable considering the publicity conscious nature of broadcasters and the fact that a few interests are likely to feel they've not been treated fairly.

On the technical side the Peacock Committee may recommend joint transmitting operations for the BBC and the IBA services. It was logical to combine the provision of programmes with the technical side in the early days of broadcasting when the overriding concern was to put the two on a secure financial footing. It's less logical that the two should be so closely linked in today's changed circumstances. Both the BBC and the IBA run impressive technical operations that have been responsible for many major developments. Would their efforts be any less effective by being run on a joint basis? The decision appears to be one that will have to be taken on administrative rather than technical grounds.

The IBA's operations have also been in the public eye recently. Speaking at the Royal Television Society's recent dinner the IBA's director-general John Whitney called in question the present system of awarding eight-year franchises to the ITV companies. He proposed a system of "rolling contracts", with more rigid enforcement of public service broadcasting obligations and less strict control over the ownership of ITV companies. The present system in which the franchises have to be advertised every eight years is hardly popular. As the IBA's chairman Lord Thomson put it after the last franchise round "there has got to be a better way". The problems relate to the time, effort and expense required in making franchise applications and the fact that whatever it decides the IBA will come in for criticism. Just how do you judge a collection of promises and proposals? The present system is essentially a compromise that was considered to be a suitable approach in the early days of ITV. A different compromise would seem to be more appropriate in today's changed circumstances. Mr. Whitney also criticised the levy imposed on ITV profits, something that at its present level seems to reflect reaction to the earlier period of the famed "licence to print money".

Meanwhile changes are also afoot on the other side of the channel. The new French government plans to privatise TF-1, the largest and oldest network which is heavily indebted. The status of the regional network FR3 is to be reviewed. On the satellite TV front the government has decided to revise the financial arrangements and wants to cancel the agreements made by the previous government for the operation of the channels.

EDITOR

John A. Reddihough

Please note that the telephone numbers below are for contact with the advertisement departments only. Editorial enquiries should be sent to the editor at the address given on page 545.

ADVERTISEMENT MANAGER

David W.B. Tilleard
01-261 6671

SECRETARY

Janet Reeve
01-261 6671

CLASSIFIED ADVERTISEMENTS

Pat Bunce
01-261 5942

ADVERTISEMENT COPY AND MAKE-UP

Ron Scorey
01-261 6035

CAN YOU HELP?

Does anyone know where spares and/or service data can be obtained for Winthronics monochrome portables?

FRONT COVER

This month's cover photograph shows a Panasonic NV7000 with the top casing removed. See servicing article on page 590.

Long-distance Television

Roger Bunney

Following months of winter gloom April at last produced increased reception. During the first half of the month there was little SpE or indeed any other activity apart from the usual meteor shower pings but the second half was considerably more active.

For those who made a note of the meteor shower predictions given in the February issue April 22nd was very rewarding. The active MS conditions lasted into the evening and reports were received from several enthusiasts. Since many of the signals received consisted of programme material identification was difficult. Those stations/countries definitely identified were as follows: RTP (Portugal) chs. E2 and 3; TVE (Spain) E2; TVP (Poland) R1, 2; TSS (USSR) R1, 2; CST (Czechoslovakia) R1. Unfortunately no Band III signals were reported.

SpE propagation improved towards the end of the month, suggesting a good season ahead. From 23 years of DX-TV experience I've noted that a good opening in April usually means that the summer months will be productive. There were excellent openings on the 28th and 29th at around midday. The SpE log is as follows:

- 10/4/86 SR (Sweden) ch. E3; NRK (Norway) E2; RUV (Iceland) E4.
24/4/86 TSS R1; MTV (Hungary) R1; SR E2, 4; NRK E2; DFF (E. Germany) E4.
25/4/86 CST R1.
27/4/86 TVP R1.
28/4/86 RAI (Italy) IA, B; RTP E3; SR E2; CST R1; TSS R1; TVP R1.
29/4/86 TVE E2, 3; RAI IA, B; ORF (Austria) E2a; JRT (Yugoslavia) E3; CST R1, 2; +PTT (Switzerland) E3; ARD (W. Germany) E2, 3, 4; TVP R1; DFF E4; DR (Denmark) E4; SR E3.
30/4/86 CST R1; DR E4.

Thanks to Cyril Willis (Norfolk), Simon Hamer (Powys), David Martin (Poole), Iain Menzies (Aberdean), Derek Juniper (Angus), Bill Cotterill (Tipton), Tony Privett (Basingstoke) and Roger Pates (Nottingham) for sending in reception details.

Two things to look out for. First TVP-2 transmits Polish

teletext for some ten minutes after close down, with about 25 pages. Secondly amongst the increasing number of French TV5 and TV6 stations being received in the UK there's now a Band I outlet: a French DXer reports that a ch. L4 transmitter is now operating in the Lille area, carrying TV6.

During the first few days of May Halley's comet passed by: increased MS reception had been expected but monitoring during the early morning hours was very unproductive.

News Items

UK: The first programmes from London's latest pirate TV station Network 21 were transmitted on March 21st, using ch. E21. The transmission lasted for about half an hour from 2400 and the station has been on air on subsequent Fridays. There have been no reports to date of reception by DXers.

Spain: A bill being introduced will break TVE's present monopoly, at least three private channels being envisaged. There will be ten year contract periods with funding by either Spanish or EEC organisations. Several Spanish and one Italian group have already expressed interest.


France: The new government is considering substantial revision of the arrangements for TV services.

Belgium: TV-Team, a subsidiary of RTL, could well start a third network. RTBF has encountered strong opposition to the installation of a high-power transmitter at Ittre, 20km south of Brussels, as a replacement for Wavre (ch. E28). A new site may have to be found.

In brief: Commercials are now included in the Saudi English service (Channel 2), though initially only for locally produced goods . . . Nepal-TV began operations on December 29th last, with a fifteen minute daily news programme and other material received via satellite downlinks. The service area is at present restricted to the Kathmandu valley . . . Ghana TV (GBC-TV) began colour transmissions in early May.

New Products

Tim Healey (Plymouth) tells us that he recently erected an inexpensive lattice mast produced by a small local company run by Ken Arnold of Portland Cottage, Pensilver, Cornwall. The range of towers is anti-corrosion painted but not galvanised, the prices being some 30-40 per cent below those of conventional communications masts. Examples include a telescopic lattice tower to say 42ft using 1in. vertical seamless pipe, 3/8in. strut and tiltover at £260 (usually around £410); a 40ft square tube tiltover with winch and ground post at £160 (usually

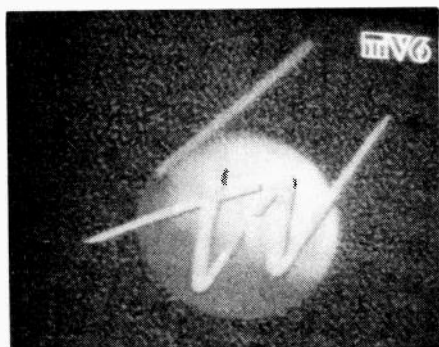

Left: French TV6 network logo received by Dave Shirley (Hastings) from Lens on ch. E54. Centre: MTV-2 (Hungary) received in Holland by Ryn Muntjewerff - an advertisement on ch. R37. Right: Advertisement received from Hungary on ch. R9 by Keith Chaplin at Barrow-on-Soar, Leics. Both Hungarian signals were received on October 27th 1985.

around £260); and a 32ft lattice tiltover at £160. Delivery can be arranged. For details write enclosing a foolscap s.a.e. plus two 12p stamps (UK only).

Brian Lee of 31 Merton Avenue, Farsley, Pudsey, W. Yorkshire LS28 5DX (0532 567 642) has produced a wall rotor bracket in 1/4in. thick mild steel using a very strong triangular configuration. The upper bracket is fitted with two plastic bearing units that fit snugly around a 1 1/2in. o.d. mast, the two bearings being welded in parallel to prevent side-by-side motion. The rotor fits at the bottom of the bracket: thus the plastic bearings replace the conventional alignment bearing. Each bracket is tailor-made to customer's dimensions (i.e. wall stand-off etc.) and variations in the brackets can be supplied. The wall rotor bracket costs £23.50 plus £4.50 post and packing, UK mainland. Please include s.a.e. with any enquiries.


Satellite Scene

Channel Master is now selling a VideoCipher-II unscrambler in the USA at \$395. Scrambling is a controversial matter in N. America at present. CNN recently reported that an HBO downlink was being jammed by an anti-scrambling lobbyist who beamed a signal on the 6MHz uplink frequency, resulting in complete loss of the 4GHz downlink signal. The VideoCipher-II system is likely to be adopted as an industry standard in the USA.



Tony Dunnett of SAT-Tel, Motueka, New Zealand is now receiving good signals from AUSSAT-1's transponder 7 (eastern time ABC network) and transponder 5 (SBS - intended for distribution, at 12W). He reports that Intelsat V at 180°E provides several programme sources in the 4GHz band, including CNN/NBC, JISO (Japan news feed from the USA), CBS/ABC, AFRTS and an Australian-New Zealand news feed. Most channels provide entertainment quality reception using a 5m dish, 55°K LNA and a home produced 27MHz bandwidth receiver.

Table 1 shows satellite TV signals at present available in the UK. ECS-1 is at 13°E, ECS-2 at 7°E, Intelsat V at 60°E and Intelsat VA-F11 at 27.5°W. The listing was accurate at the time of compilation (end April) but changes keep taking place.

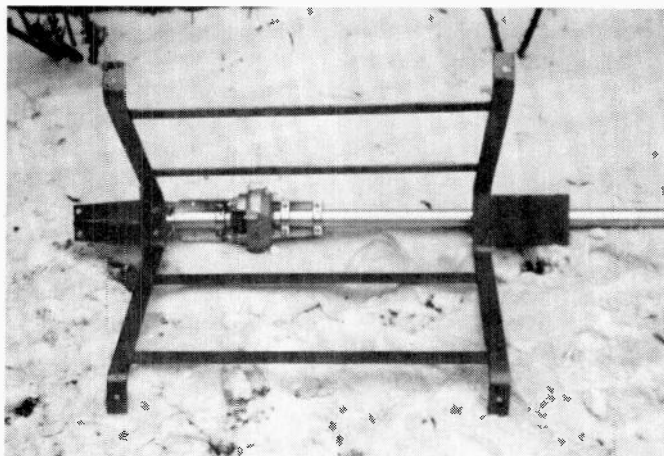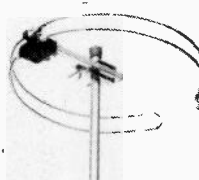The Neville Cresdee satellite location/bearing/azimuth service for all known TV transmitting satellites above your horizon in both the 4GHz and 11/12GHz bands now runs to twelve pages and includes predictions of solar "out-rages" - when the sun aligns itself with the focal point of your dish, producing solar noise interference. The cost is £20 (\$36 US), from 14 Arminers Close, Clayhall,



Wall rotor bracket available from Brian Lee.

TRIAX OMNI-FM AERIAL FRINGE FM RADIO AMPLIFIER

The **TRIAX OMNI-FM** represents fine value in omni-directional reception. This high quality aerial gives a level pick-up from all directions - ideal for locations where diverse transmitter sites are available.

For increased omni-directional gain (unity), 2 similar aerials can be stacked one above the other, a further advantage being reduced pickup above/below the aerials (gives reduced aircraft flutter and household electrical interference). No complicated phasing harness needed - just equal feeder lengths to a **TRIAX** Stripline stacking filter!

To compliment the above systems we recommend the new **FRINGE ELECTRONICS 'FM RADIO SET-BACK AMPLIFIER'**. Very low noise (1.9dB), HIGH gain (20dB) and with excellent signal handling characteristics are the essential features of this attractively housed mains powered unit.

Indoor use allows optional amplification on weak signals only and for DXing - we suggest also very low loss coaxial feeder to maintain optimum low noise input performances. When thinking FM, Think **TRIAX**.


TRIAX OMNI-FM, Horizontally polarised 88-108MHz balun matched aerial..... **£12.33**
TRIAX Twin OMNI-FM Aerials, higher output system which includes the Triax 721/BI stripline stacking filter/combiner **£35.00**
FRINGE Electronics FM Radio set-back amplifier, High 20dB Gain, very Low Noise figure only 1.9dB, mains powered..... **£18.60**
TRIAX 'Stereo 8' 88-108MHz 'Continental' Style 8 element high quality FM Antenna with Twin reflectors, Gain 9.5dB..... **£39.95**

WHETHER YOUR NEED IS FOR LOCAL OR FRINGE RECEPTION, ALTERNATIVE CHANNELS, TV/FM DXING, OR FOR A DISTRIBUTION SYSTEM, AERIAL TECHNIQUES IS THE 'ONE STOP' ADDRESS FOR ALL EQUIPMENT.


AERIAL TECHNIQUES IS UNIQUE -
OUR HIGH QUALITY CATALOGUE COSTS ONLY 65p.

Send for your copy today - please include an SAE with all enquiries.
 All prices inclusive of VAT and carriage Delivery 7-10 days.
ACCESS & VISA Mail and Telephone orders welcome

AERIAL TECHNIQUES (T)



11 Kent Road, Parkstone,
Poole, Dorset BH12 2EH. Tel: 0202 738232



Gosport, Hants PO12 2HB - send an s.a.e. with enquiries and if ordering include the co-ordinates of your location or, if these are not known, sufficient details to enable your location to be established.

Not exactly a DX-TV matter perhaps but worth men-

Table 1: European satellite TV transmissions

Programme/polarisation	Frequency GHz	Satellite
Teleclub (V)	10.9866	ECS-1
RAI-1 (H)	11.005	ECS-1
WDR-3 (H)	11.015	Intelsat V
Premiere/ Children's Channel (H)	11.015	Intelsat VA-F11
3-SAT (H)	11.057	ECS-1
RTL+ (V)	11.087	ECS-1
Worldnet (H)	11.093	ECS-2
Music Box (H)	11.135	Intelsat V
Screen Sport/Life Style/ ARTS (H)	11.135	Intelsat VA-F11
Filmnet/ATN (H)	11.1403	ECS-2
Eurovision (V)	11.142	ECS-2
CNN (V)	11.155	ECS-2
BR3 (H)	11.175	Intelsat V
Europa (H)	11.175	ECS-1
MirrorVision (H)	11.175	Intelsat VA-F11
EBU (H)	11.176	ECS-2
SVT-1 (V)	11.468	ECS-2
New World/TV5 (H)	11.472	ECS-1
SAT-1 (V)	11.507	ECS-1
Worldnet (H)	11.512	ECS-1
SVT-2 (V)	11.635	ECS-2
NRK (H)	11.642	ECS-2
Sky (H)	11.650	ECS-1
Music Box (V)	11.674	ECS-1

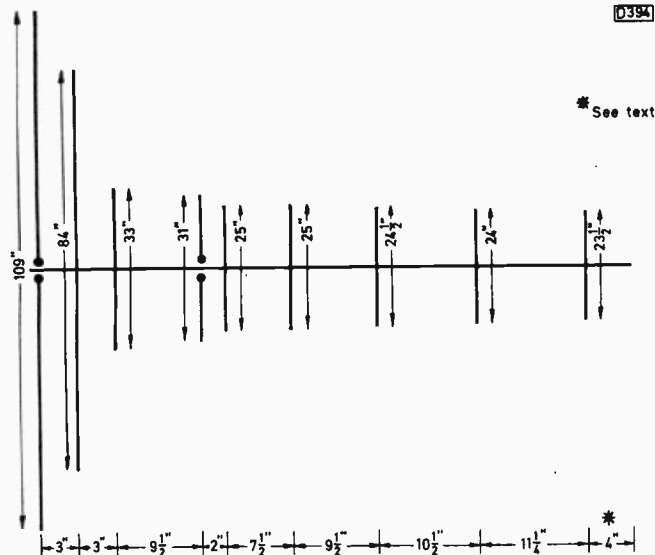


Fig. 1: Basic wideband Band I/III DX-TV aerial design with u.h.f. add-on option.

tioning I feel: photographs of the UK taken from the Landsat satellite, using its thematic mapping system, are now available. The photograph of central, southern UK covers from Swanage to Chichester and from the coastline to Warminster and Haslemere. Even roads can be seen. A 10 × 8in. photograph costs £5, a 20 × 16in. photograph £20. If interested, enquire about your area at Space Frontiers Ltd., 30 Fifth Avenue, Havant, Hants PO9 2PL, enclosing a stamped, addressed envelope.

From our Correspondents . . .

David Patuzzo (Nottingham) has sent us a report of his activities. He's been DXing for two and a half years and has assembled a wide range of equipment. The indoor part of his installation fits inside a wardrobe and consists of four TV sets – a system I Hitachi set, Plustron TVR5d, JVC CX601GB and a Sandra system L Band I/III/IV/V set purchased on a day trip to Boulogne. He uses a four-element Band I array, a ten-element Band III array and a Wolsey Colour King, with a variety of Fringe masthead amplifiers etc. David broke new ground with in-flight TV-DX using a 1in. Sony Walkman at 33,000ft while flying to Majorca. Using its telescopic whip he received French, W/E German, Swiss and Spanish stations. Particular catches were TVE-Catalunya and EBT in northern Spain – TVE was logged half way across France! All signals were in Band III or at u.h.f. Special permission for the set to be operated was given by the aircraft's captain. An unusual DXing feat!

Dave Shirley (Hastings) was the first UK TVDXer to receive the new French fifth and sixth network signals, from Lens in northern France. The accompanying photograph shows his TV6 reception on ch. E54: the fifth network signal consisted of the PM5544 pattern with identification RES.5.

Compact DXing Aerial

Band I/III aerials tend to be rather conspicuous nowadays, with the result that it's often necessary to seek a compromise between signal performance and environmental impact. We've recently designed an aerial to meet these requirements – see Fig. 1. It's ideal for use on a flat balcony, as a portable aerial for a field day excursion or as an unobtrusive aerial for house/chimney fixing.

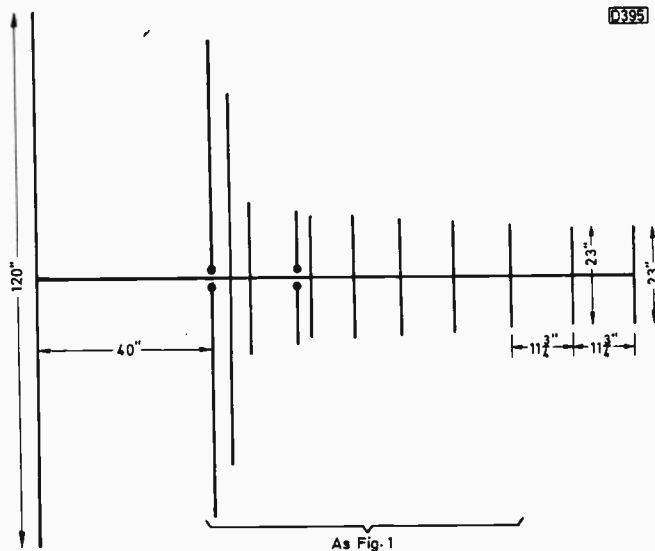


Fig. 2: Wideband Band I/III DX-TV aerial with two-element Band I section and eight-element Band III section.

The signals received in Band I will generally be propagated via SpE or MS, with tropospheric reception as well in the east/south east. For this a wideband dipole should suffice. The array uses the proven unity-gain B1 design which gives coverage of 48-68MHz. Band III operation on the other hand calls for a measure of gain and directivity, especially in view of PMR signals. The Band III section of the array consists of a wideband (175-230MHz) six-element design based on the Tru-match dipole system (Antiference patent). The version shown should provide a gain of 5dB at 175MHz rising to 7dB at 230MHz, with a front-back ratio of typically 20dB and a -3dB beamwidth of 60° at mid-band. The boom extends ahead of the first Band III director to allow a lightweight clamp holding a 4in. or so vertical stub to be added to permit rear clamping of an Antiference TC10/W wideband u.h.f. Yagi array (obtainable from Tandy stores under the Archer label), thus creating an in-line boom array with wideband capability over Bands I/III/IV/V. The performance specification for the Antiference system is approximately 5.5dBd gain on ch. 21, 12dBd gain on ch. 60 with a front-back ratio of 21-25dB. For the more adventurous DXer Fig. 2 shows a design with a two-element Band I section and eight-element Band III section. This should provide a gain of 3dBd at 60MHz and 7dBd at 175MHz, rising to 9dBd at 230MHz.

The v.h.f. output can be taken via individual feeders or diplexed into a single downlead. It's recommended that the u.h.f. output be kept separate. A diplexing amplifier could be used to advantage provided it has good signal-handling capability and a low noise level – these characteristics are much more important than high gain.

The prototype has a 1in. o.d. boom – the 6ft × 1in. o.d. standard TV alloy mast is ideal. The elements are made of 1/2in. o.d. seamless tubing. Lengths of this are available from aluminium stockists, though these are usually upwards of 4m. The element ends should be plugged to stop whistling in the wind. For Band I hard-drawn should be regarded as essential, though this is more expensive. The Jaybeam 9892 alloy 1in. to 1in. clamp is recommended as a stub mast clamp.

If sufficient interest is expressed there's a possibility of obtaining dipole insulators etc. for the project (1in. boom, 1/2in. element fixtures only). Those interested should write in, with s.a.e., indicating requirements.

POST A PART ELECTRONICS
6 CHAPMAN COURT, CHARFLEETS ROAD,
CANVEY ISLAND, ESSEX SS8 0PQ.

Telephone 0268 690868
Telex 99305



TRADE COUNTER OPEN

ORDERS DESPATCHED SAME DAY
 ADD 75p P&P, THEN 15% VAT.
 ADD POSTAGE FOR OVERSEAS ORDERS.
 ORDERS WITH AEROSOLS, PLEASE ADD 25p PER CAN.

Thorn 10Ω 20W (3500) R751 Safety Resistor	75p
Pye 713 Speaker 5" x 3" 70Ω	1.00
Pye 713 Complete Tube Base Panel	2.75
with Focus Slider & Leads	1.25
Pye 725 Complete Tube Base Panel	2.75
TX9 Complete Tube Base Panel	3.75
TX10 Complete Tube Base Panel	4.75
TX90 Complete Tube Base Panel	4 for 50p
Pye 713 Control Knobs	45p
Tube Base Socket ITT CVC32	50p
Tube Base Socket Thorn 3000/8000 etc	50p
IC Inserter 16 Pin	50p
Large IC Extractor	90p
Crystal 4.43MHz	50p
EHT Lead & Cap for Split Diode Loop	47p
Anode Cap	65p
Sanyo Anode Cap Assy + Lead. 12TCD-CT-1G	25p
Degauss VDR E299D/HP230 3000/8000	1.80
Degauss Thermister C8-ROH (TX90)	4 for 2.00
Control Knob Thorn TX90	85p
On/Off Knob Thorn TX90	9.80
Push Button Assy Thorn TX90	5.00
EHT Cable Correction Assy. 20AX AT1081	Metre
EHT Cable	14p
BF259 with Heatsink	40p
TIP110 with Heatsink	10p
1L29/130/131 Coil	25p
6MHz Ceramic Filter	1.00
DL700 (Philips) Chroma Delay Line	1.00
OL50 Chroma Delay Line	1.00
T9006A Lum Delay Line	1.00
8K5/9K Lum. Delay Line	65p
Plastic Cover for 3K5 SP8385	5p
TX9 Back Ground Control 10K	15p
TX9 Gain Control 100R	15p
Thorn 2000 Focus Pot	1.00
Thorn 5000 Focus Pot	3.75
Thorn 9500 Focus Pot	2.00
Thorn 8K5 Focus Pot	2.40
Thorn 4000 Focus Pot	2.75
Thorn TX10 Focus Pot (New Type)	9.00

SERVICE AIDS	
Amberrill M54 Silicone Grease	12oz 2.15
Amberrill Freezer	12oz 1.99
Amberrill Amberlube	6oz 1.88
Amberrill Ambertron	16oz 2.25
Amberrill Anti-Static Screen Cleaner	7oz 1.95
Amberrill 40+ Protective Lubricant	14oz 2.15
Amberrill Amberculens Foaming Cleaner	13oz 1.26
Amberrill Circuit Lacquer	14oz 2.15

THICK FILM RESISTOR UNITS	
3500 Thorn (5 Pin Connection) video	1.70
4000 Thorn (4 Pin Connection)	1.90
725/731 Pye (6 Pin Connection)	2.20
713 Pye (6 Pin Connection)	2.20

FUSES			
50MA	10 for 70p	250MA	10 for 65p
250MA	10 for 50p	750MA	10 for 65p
315MA	10 for 50p	7A	10 for 50p
500MA	10 for 50p	10A	10 for 50p
2.5A	10 for 1.00	20A	10 for 50p
3.15A	10 for 1.00	50A	10 for 50p

Thorn Mains TX 3000/3500	7.50
Thorn Mains TX 8000/8500	10.00
Thorn Mains TX 9000 (T701)	10.00
Thorn Mains TX 9600 (T512)	10.00
Thorn S.O.P.T. 8000/9500	3.50
Thorn Scan TX 3000/3500	6.00
Thorn EHT TX 3000/3500	6.00
Thorn LOPT 9000	10.00
Thorn LOPT 9600	12.00
Thorn LOPT 1530/91	7.25
Thorn LOPT 1630/91	7.25
Thorn LOPT 8000	9.80
Thorn LOPT 8500	9.80
Thorn LOPT TX9	9.85
Thorn LOPT TX10	19.00
Thorn LOPT TX90	13.75
Pye LOPT 713	9.85
Pye LOPT 725	10.18
Pye LOPT 731	8.80
Philips LOPT G9	13.75
Philips LOPT G11	7.40
GEC LOPT 3113	14.75
Diode Split LOPT AT2076/35	6.75
Sanyo LOPT AM-WM-21	9.80
Sanyo LOPT AM-WM-4	7.80
Philips LOPT G8	5.00
Sanyo LOPT (CW21) 4-2751-44700	9.80
ITT LOPT CVC3-9	8.75
ITT LOPT CVC30	9.75
ITT LOPT CVC45	10.25
Baird 8750	10.25
Baird 8752	3.00
Thorn Line Drive TX. TX9 (T2)	1.85
Thorn Line Drive TX. 8K etc. (T402)	3.75
Thorn Line Drive TX. 9K (T705)	3.75
Thorn Switch Mode TX. 9K6 (T511)	4.00
Thorn Input Choke TX9 (L64)	2.95
Thorn Choke TX90 (L120)	

300 Mixed Resistors	1.50
300 Mixed Capacitors	1.50
150 Mixed Electrolytics	2.00
100 W/W Resistors	1.00
20 Mixed Conv Pots	1.00
40 Mixed Pots	1.50
20 Mixed Sliders	1.00
40 Mixed Presets	60p
20 Mixed VDR & Thermistors	1.00
100 Mixed Ceramic Discs	1.00
20 Mixed Valve Bases	1.00

AC128	39	BC174B	23	BCX33	22	BF154	25	BFR52	31	NKT276	20
AC131	40	BC177	24	BCX34	22	BF167	24	BFR62	28	NKT453	1.65
AC138	40	BC182LB	12	BD1115	49	BF179	32	BFR81	29	OT112	1.92
AC142K	39	BC183L	12	BD1131	30	BF181	30	BFR87	25	OT121	2.08
AC149K	38	BC194	13	BD1132	46	BF184	30	BF890	1.74	R1038	80
AC153	39	BC197	24	BD1133	59	BF185	30	BF91	2.08	R2008B	1.40
AC176	33	BC204	15	BD1139	36	BF194	16	BFX38	40	R2010B	1.40
AC176K/	33	BC208	9	BD1140	38	BF196	16	BFY50	30	R2030	70
AC128K	33	BC212L	9	BD1144	1.70	BF196	16	BFY51	34	R2305	80
AC188	38	BC213L	12	BD1150	50	BF197	15	BFY52	34	R2322	50
AD142	1.18	BC237	12	BD1163	98	BF198	19	BRC116	1.50	R2443	25
AD143	1.08	BC238B	8	BD201	74	BF199	15	BRC1693	1.43	RC164446	30
AD149	98	BC238L	8	BD203	78	BF223	18	BU105	1.00	RC16599	1.25
AD161	32	BC250A	15	BD204	99	BF224	19	BU126	1.10	RC16600	1.40
AD162	32	BC251	8	BD222	48	BF238	20	BU207	1.05	RC16799	1.13
AD263	1.05	BC252A	20	BD225	52	BF240	9	BU208	1.15	RC16800	1.42
AF127	45	BC294	37	BD232	60	BF241	21	BU208A	1.15	RC16802	1.38
AF138	38	BC301	32	BD233	60	BF255	19	BU326A	1.30	RC16815	1.20
AF239	41	BC303	31	BD234	60	BF266LB	38	BU407	1.70	SP838	2.65
BC107	15	BC307	10	BD237	55	BF266S	20	BU408	2.76	S1299	2.25
BC108	15	BC308	8	BD238	65	BF267	28	BU500	2.30	S2800	1.25
BC109	15	BC309	14	BD241	59	BF269	28	BU526	2.46	T6050V	1.30
BC115	16	BC327	18	BD244	85	BF271	25	BU806	1.80	T6052V	1.30
BC117	21	BC328	18	BD28A	81	BF274	11	BU807	2.94	T9003V	1.25
BC125	26	BC337	17	BD386	68	BF337	29	C1129	9	T9010V	1.45
BC126	23	BC338	17	BD433	71	BF338	34	C1172B	9	T9053V	1.30
BC139	27	BC347	8	BD437	83	BF355	40	ES386	54	T9054V	1.00
BC141	34	BC394	8	BD592	1.20	BF362	50	E9003	28	T9039V	1.10
BC142	30	BC454	8	BD598	1.20	BF391	21	E9005	25	TIC45X	50
BC143	31	BC455	8	BD677G	1.35	BF394	16	ME0404	10	TIC46	48
BC147	12	BC456	10	BD679	1.42	BF422	47	ME0412	10	TIC106C	40
BC148	12	BC460	10	BD701	1.04	BF423	53	ME042	10	TIP29	42
BC149	12	BC463	22	BD702	1.12	BF450	43	MJ2501	2.26	TIP30	42
BC153	16	BC546	8	BD707	95	BF453	53	MJ3001	2.21	TIP31	35
BC1540R	16	BC547	12	BD708	95	BF458	37	MJE340	5.00	TIP32	43
BC154YL	16	BC548	12	BD839	1.30	BF459	40	MJE520	5.00	TIP33	61
BC157	12	BC549	8	BDX10	93	BF461	59	MJE2955	1.40	TIP41	42
BC158	12	BC557	10	BDY20	1.09	BF566B	35	MJE3055	1.50	TIP42	45
BC159	15	BC558	10	BDY82	99	BF586	59	NKT241V	8	TIP110	61
BC171	9	BC559	8	BF137	20	BF694	16	NKT241G	8	TIS91	25
BC172	9	BC595	8	BF153	20	BF757	62	NKT241Y	8	ZTX550	30

INTEGRATED CIRCUITS							
BRC1330	1.40	SN7613ND	1.80	TBA530	1.26	TDA2030	2.10
BRC3064	1.00	SN76203N	1.80	TBA540	1.00	TDA2522	2.10
BRC/M/200	1.00	SN76033N	2.00	TBA560C	1.50	TDA2540	3.50
BRC/M/300	1.00	SN76115	2.00	TBA641	2.05	TDA2580	3.50
CA3060	1.58	SN76131N	1.58	TBA651	2.50	TDA2581	3.00
LMI303P	1.48	SN76226N	1.25	TBA720A	2.49	TDA2581A	3.00
LM231B	2.20	SN76227N	1.00	TBA750	2.20	TDA2611A	1.95
LM237B	2.00	SN76530P	1.30	TBA800	1.62	TDA2640	2.90
LM239B	2.00	SN76622N	1.00	TBA810S	1.80	TDA2690A	1.50
MC1327AP	1.25	SN76660N	80p	TBA810SA	2.00	TDA3560	5.00
MC1358P	1.30	SN76666N	75p	TBA920	2.00	TDA4500	6.00
MC1455P	18p	SN76744	1.52	TBA950	2.50	TDAS903	2.90
MC14516BCP	60p	SN76744	2.50	TBA1440	1.92	TEA1009	1.95
SA11025	7.20	TA7117P	1.00	TCA270SA	1.05	MC14426P	4.80
SA11124	4.50	TA7109AP	2.80	TCA270C	1.05	MC14429P	4.50
SA15010	6.00	TAA611	1.40	TCA270C0	1.05	MC14514	5.00
SL432A	1.80	TBA120C	1.20	TDA1035T	3.50	UA758PC	2.50
SL432	2.50	TBA120Q	1.20	TDA1037	2.72	ULN2165	1.30
SN15846N	60p	TBA120S	70p	TDA1170	2.15	ULN2216A	1.25
SN74123N	65p	TBA120U	1.00	TDA1200	1.76	UPC1365C	5.75
SN74154N	1.40	TBA395	1.00	TDA1270	2.42	SC9488P	1.40
SN76001N	1.40	TBA480Q	1.40	TDA1327	2.53	SW153	2.50
SN76110N	1.14	TBA510	1.90	TDA2002	2.80		

Thorn 8/8K5 ex equip panels	Thorn 3/3K5 ex equip panels	Thorn 4000 Convergence panel
untested	untested	ex-factory
PSU	PSU	Thorn 4000 PSU panel ex-
FTB	FTB	factory
Decoder	Video	Thorn 3K5 beam limiter board
	Chroma	new
Thorn 9K ex equip panels		
untested		
PSU	12.00	
Decoder	5.00	
	Conv. 3K	
	Conv. 3K5	
Thorn 9K6 ex equip panel		
untested	Autovox Decoder FG/01	
Decoder	boxed	

UHF TV Aerial for portable	50p	Coax Plugs	10 for 1.65
Indoor Aerial With Reflector	40p	Band Change Switch Assy, Pye 725	40p
to Help Combat Ghosting Problems	2.50	Coax Cable Low Loss	per Metre 2.2p
Line Connectors	38p	Switched Flush Fitting Aerial Outlet	1.00

10 Spark Gaps	1.00
10-16 pin Quil IC Socket	90p
20 Assorted TV Knobs	1.00
10-16 pin Quil to Dil IC Socket	

3 WEEK FULL-TIME

COURSES

HIGH PERCENTAGE OF PRACTICAL WORK
INTENDED FOR QUALIFIED SERVICE ENGINEERS.

VCR SERVICING

NEXT COURSE STARTS ON JUNE 30th – TUITION FEE £575

MICROCOMPUTER SERVICING

NEXT COURSE STARTS ON JULY 21st – TUITION FEE £690

(MSC grants available on JTS/ATS training schemes, subject to approval. If you are unemployed, or are currently employed and require retraining, or updating, you or your employer may be eligible for financial assistance under one of the above schemes.)

Further details from:

LONDON ELECTRONICS COLLEGE (VC Dept.)

20 Penywern Road, Earls Court, London SW5 9SU

Tel: 01-373 8721

TV LINE OUTPUT TRANSFORMERS

PRICES INCLUDE VAT & CARRIAGE

Delivery by return of post.

BAIRD: 8290, 8752, 8773	12.00	ITT: VC200 to VC402	9.20
RANK BUSH MURPHY		CVC1, CVC2 (FORGESTONE)	11.50
A774 with stick rectifier	9.78	CVC5, CVC7, CVC8, CVC9, CVC20	10.35
A816, T16, T18, Z712, Z715	10.35	CVC25, CVC30, CVC32, CVC40,	
T20, T22, T26, Z179, A823	11.50	CVC45	9.20
Z718 Basic unit	13.50	CVC800, 1100, 1150	P.O.A.
DECCA: 1210, 1211, 1511	11.50	CVC1200, 1204, 1210, 1215, 2600	P.O.A.
1700, 2001, 2020, 2401, 2404	9.20	PYE: 169, 173, 569, 368	9.20
CS1730, 1733, 1830, 1835	9.20	CT200, CT200/1, CT213	10.35
30, 70, 80, 90, 100, 120, 130	9.20	725-731, 735, 737, 741	9.78
FERGUSON, THORN: 1590, 1591	9.20	PHILIPS: 170, 210, 300	9.20
1690, 1691, built in rect.	9.78	320 series	9.78
1600, 1615, 1700, 1790	P.O.A.	TX, T8, TX2, TX3 mono	P.O.A.
3000, 3500, 8000, 8500, 8800	P.O.A.	G8 and G9 Series	£9.20
9000, 9200, 9300 series	12.00	KT2, KT3 series	9.20
9500, 9600, 9650 series	10.99	CTX G11, K30, split diode	P.O.A.
9800, TX9, TX10 series	P.O.A.	BINATONE: 9909, 9860, 9488	P.O.A.
MOVIESTAR 3781, 3787	12.00	DORIC Mk3, Mk1	11.50
TX10 focus unit	10.25	SONY KV 1400, 1612, 2000	P.O.A.
FIDELITY: FTV12 mono	10.35	GRUNDIG: most models in stock	P.O.A.
ZX2000 ZX3000	P.O.A.	NORDMENDE: 8290, Z206, Z306	P.O.A.
G.E.C. 2047 to 3135 mono	9.20	SANYO: 5101, 5103, 7118	P.O.A.
1201H, 1501H, 2114, 3133, 3135	9.20	SHARP: C1851H, C2051H	P.O.A.
DUAL & SINGLE hybrid col.	10.00	TOSHIBA: C800, C800B	P.O.A.
SINGLE STD solid state	12.00	TANDBURG: 190, CTV2, CTV3	P.O.A.
SINGLE STD split diode	P.O.A.	TELEFUNKEN: most models in stock	P.O.A.
INDESIT: 24EGB, 12LGB, 12SGB	10.35	HITACHI: 1471, CPB260, 2501	P.O.A.
WINDINGS		SIEMANS: FF series	P.O.A.
TYNE: main winding	6.80		
RBM: T20, T22, T26, Z179	6.33		
WALTHAM: W125 eht winding	2.37		
WALTHAM: W190, W191 eht coil	6.90		
KORTING: hybrid winding	6.90		
THORN: 8000, 8500, 8800 eht	6.70		

Tidman Mail Order Ltd.,
236 Sandycombe Road,
Richmond, Surrey.

Approx. 1 mile from Kew Bridge.

Phone: 01-948 3702

Mon-Fri 9 am to 12.30 pm &


1.30-4.30 pm

Sat 10 am to 12 noon.

SADELTA

FIELD STRENGTH METER MODEL TC-402

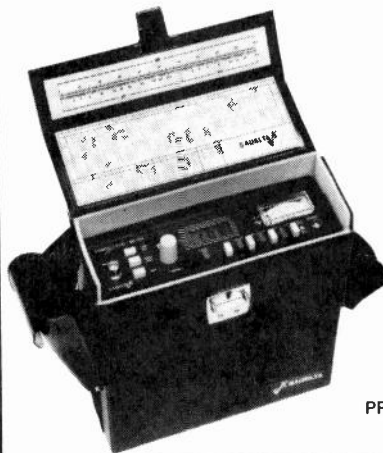THE SADELTA FIELD STRENGTH METER TC-402 has been designed to measure the signal levels delivered by the antenna to a TV or FM receiver, in order to test the performance of the antenna and evaluate the best conditions during installation etc. To facilitate measurements, the tuning frequency readout is shown on a digital display.



FEATURES

- Covering FM and all TV bands (UHF/VHF) including CATV freq.
- Digital tuning display (3 digits) for direct frequency readout.
- Accurate 10 turn tuning potentiometer.
- Built-in loudspeaker enables monitoring of sound in AM/FM.
- Meter measurement in voltage and dB from 20uV (26dB/uV).
- Continuity tester 0-500 Ohms.
- Fully portable (battery).
- Sturdy carry case.

PRICE £249 + £37.35 VAT

U.K. POST PAID, export enquiries welcome, Visa/Access or cheque with order, payable to B.K. Electronics. Official orders welcome from Govt. Depts., Colleges, P.L.C.s etc. Large S.A.E. for technical leaflets of complete range delivery normally within 7 days.

B. K. ELECTRONICS Dept. 'T'

UNIT 5, COMET WAY, SOUTHEND-ON-SEA,
ESSEX. SS2 6TR TEL: 0702-527572

Servicing Sonatel and Morphy Richards Monochrome Portables

Ian M. Rees

The brand name Sonatel was used by House of Carmen, the monochrome portables sold under this name being amongst the first to break the £50 price barrier. They were sold widely through the big retail chains and mail order catalogues. When House of Carmen took over the electrical goods manufacturer Morphy Richards the Sonatel brand name was dropped in favour of the well known Morphy Richards name.

Range Covered

The original Sonatel Model T750 12in. monochrome portable was at first continued in a restyled Morphy Richards cabinet and was given the model number T730. This chassis was of discrete component design. A subsequent chassis used mainly i.c.s: this was put in the T730 case and given the model number T730/2. When ordering spares for these models, be very careful to state whether the parts are for the T730 or the later T730/2. Model T739 followed, incorporating a digital clock/timer and a modified T730/2 chassis.

Sonatel Model T750

We'll start with the T750 which employed conventional technology and apart from a few quirks was very reliable.

The fault you'll encounter most often is failure of the line output transistor TR801, especially if it's a BU409. Replace it with the better BU407. Other alternatives often fail after a time.

If the 15Ω, 0.5W feed resistor R716 in series with the line driver transformer shows signs of overheating, with no line drive, check the driver transistor TR703 and the associated components.

The B+ voltage (stabilised l.t. rail) should be set at 11.6V (VR901) otherwise the efficiency diode D801 (V06C) will fail – it becomes discoloured.

A gaggle of repetitive dry-joints occur on this chassis, showing up after movement of components or heavy handling of the set.

Intermittent line hold when tapped is usually the result of a poor joint on C801 (2,200μF) which decouples the supply to the line output and driver stages.

No line lock can be traced to a poor joint at pin 8 of the line output transformer (pulse feedback to the flywheel sync discriminator circuit).

For no line scan examine the connections to the line scan coupling capacitor C805 (6.8μF, 25V).

Horizontal cramping is caused by mis-setting of the line hold control T701 which has a wide locking range. The most accurate way to set it is to disable the sync input to the flywheel sync circuit by connecting an 0.1μF capacitor between the base of the phase-splitter transistor TR701 and chassis, then adjust T701 for a stationary lock.

The power supply gives few electrical faults. Rough handling causes the plastic battery panel to break, making the power supply chassis drop down and putting a strain on the front panel. Beware when working on the power supply panel as live mains is present at fuse F901 (0.5A).

Failure of this fuse can be caused by a faulty primary winding on the mains transformer: the d.c. resistance should be a nominal 65Ω. Absence of the B+ supply is usually due to dry-joints at the external supply socket or failure of the socket itself.

A low-gain transistor in position TR604 (2SD476B) in the field output stage causes cramping at the top of the picture.

Some sets went out with the wrong value resistor in position R621 in the field flyback blanking circuit. If flyback lines are visible check that the value is correct (100Ω).

An improvement in field linearity can be made by increasing the value of the field scan coupling capacitor C611 from 1,000μF to 2,000μF.

No or distorted sound is in nearly every case due to failure of the pnp transistor TR403 (2SA673C) in the audio output stage. Loss of sound can also be due to failure of the earjack speaker cutout to remake after jack insertion. Note that this model uses a 25Ω speaker.

A very dark picture can be caused by incorrect a.g.c. level setting (VR301). This is adjustable from under the set with the back on.

Vertical black lines on the picture can be easily cured by repositioning the c.r.t. cathode lead away from the line output transformer.

A blank raster with flyback lines visible and low or no sound should direct attention to the 1N60 vision detector diode D101 and filter coils L106, L107 and L108 which go open-circuit. If the picture only is affected, check coil L203 in the video output stage.

Sound breakthrough on vision can be due to a dry-joint on C403 (100μF) which decouples the supply to the audio circuits: alternatively C403 may be open-circuit.

An effect similar to soot and whitewash can be due to peaking coil L202 in the video output stage being open-circuit – or, dare I say it, a faulty tube...

A small i.f. preamplifier stage rides on the back of the tuner. This is present to compensate for the loss of gain a v.h.f. tuner in a different version would have given. If the output coil L002 is not correctly set you can get a multitude of symptoms from lack of gain through to instability and ringing. A slotted adjustment tool is re-

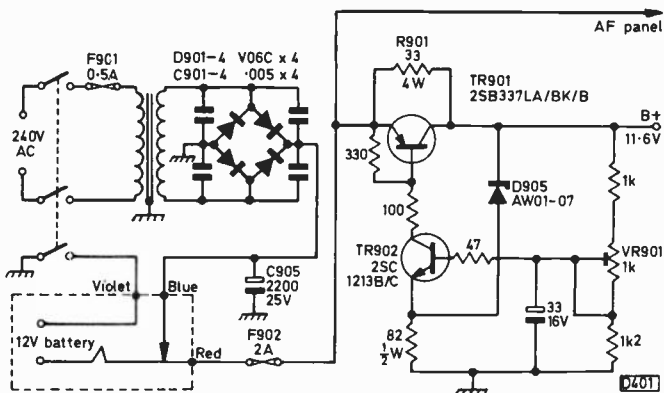


Fig. 1: Power supply circuit used in the Sonatel Model T750 and Morphy Richards Model T730.

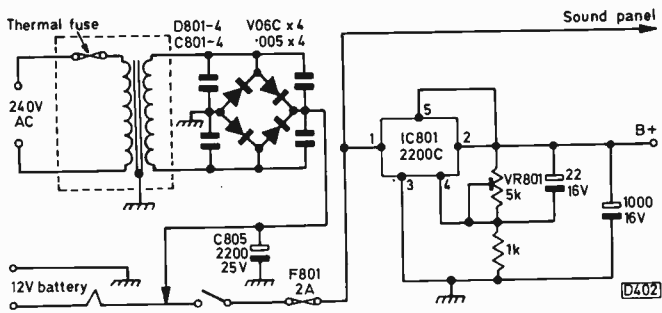


Fig. 2: Power supply circuit used in the Morphy Richards Model T730/2.

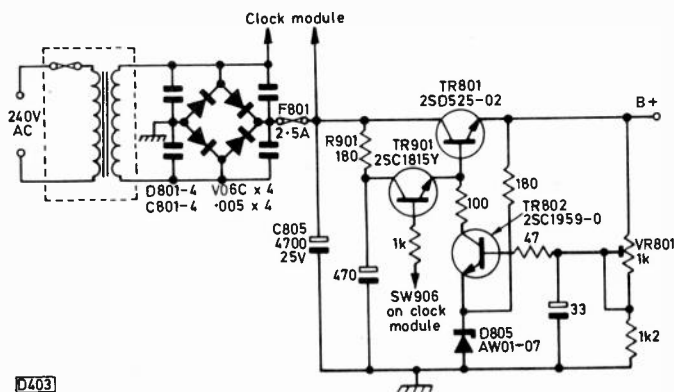


Fig. 3: Power supply circuit used in the Morphy Richards Model T739 which incorporates a digital clock/timer.

quired to reset the core, which will break if the locking wax is not softened before adjusting. Don't screw the core down as it will jam against the PCB and be very difficult to remove. Normal setting will be found near the top of the former or even with the core protruding.

Transistors TR1 (2SC1070) and TR2 (2SC1730) in the tuner do give trouble and can be replaced provided care is taken to fit the replacements in exactly the same position (a new tuner is expensive). Look out for poor or unsoldered connections on the aerial panel and the phono type connector on the tuner in the event of low gain.

Morphy Richards Model T730

The comments above also apply to the Morphy Richards Model T730. Spares should be distinguished by model however.

Morphy Richards Model T730/2

The newer chassis used in Model T730/2 uses some of the same parts as the earlier chassis, including the c.r.t., the tuner, the line output transformer and the scan coils. As with any new model this one suffered from teething problems which were overcome in later production.

The most perplexing fault came about as a result of flashover in the tube, particularly when new. This will cause loss of most of the i.c.s and the tuner and some of the transistors. To reduce the likelihood of this pin 7 of the c.r.t. should be disconnected and linked to the earthy end of the heater. This is shown as pin 4 on the circuit diagram but in practice it may be pin 3.

To improve the field lock change C301 from $1\mu\text{F}$ to $0.1\mu\text{F}$ - this is the sync separator transistor's input coupling capacitor.

Video and field breakthrough on sound require a number of actions. Video breakthrough can be simply

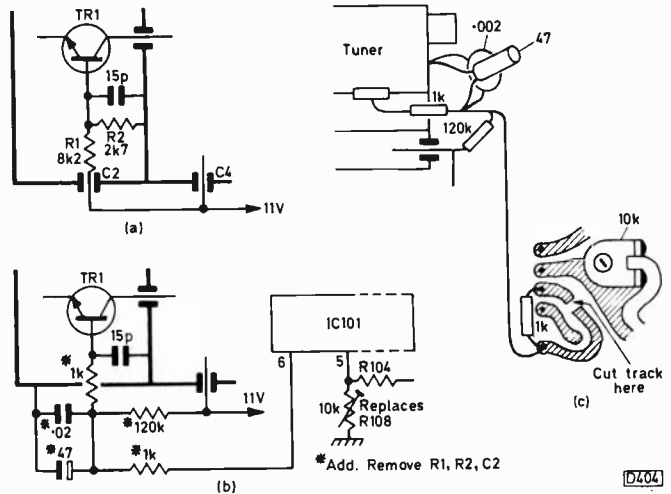


Fig. 4: Tuner a.g.c. modification. (a) original circuit, (b) modified circuit, (c) physical details.

adjustment of the sound detector coil L401 or filter coil L201 (if L201 won't peak, check C201/2 - both 47pF). If still in trouble dress the video output transistor TR201 and coupling capacitor C207 away from the TDA3190 sound chip (IC401) by bending them and trapping the video lead to the c.r.t. between, taking care not to take it too close to the line output transformer. The problem can also be due to a defective video output transistor (2SC2229-0) or vision i.f. chip IC101 ($\mu\text{PC1366C}$).

A blank raster with flyback lines can be caused by IC101, TR201 or TR301 (2SA1015-Y) in that order of likelihood.

If C705 ($3,300\mu\text{F}$, 16V) which decouples the supply to the line output stage becomes disconnected or faulty two or three vertical lines or bars will appear on the picture, visible only on certain scenes.

No line timebase operation with a charred 10Ω l.t. feed resistor R601 means a new TDA1180P line generator chip (IC601).

Check that the boost diode D702 (V09E) isn't overheating: if it is, check the boost capacitor C704 ($330\mu\text{F}$) for dry-joints.

The sound chip seems to be reliable but unstable or harsh sound can be due to C406 ($47\mu\text{F}$, 10V) in the feedback circuit being faulty. The speaker is a 16Ω type this time.

Failure of choke L105 in the l.t. line will give a blank raster, flyback lines and no B+ supply to the i.f. section.

The previous notes on tuner faults (Models T750/T730) also apply to this set.

The solid-state regulator chip IC801 (2200C) seldom fails but it should be noted that there is no switch in the supply to the mains transformer which has an internal thermal fuse (not removable). If the transformer fails, check the diode bridge and associated components and that the wiring to the 2A d.c. fuse F801 is in order.

Morphy Richards Model T739

Apart from the power supply and the addition of a clock the T739 is identical to the T730/2, so the previous comments apply.

In later production additional modifications to those incorporated in the T730/2 were included in this model. These should be made to any set returned for service.

Drifting hum bars that move slowly down the screen can be cured by isolating the negative side of the mains

bridge rectifier D801-4 by cutting the track. Make the connection via a short jump lead directly to the negative tag of the reservoir capacitor C805. If R901 (180Ω) overheats and falls in value, causing increased ripple on the supply, replace it with a 1W resistor. If R905 is positioned between the clock PCB and the front panel it should be removed and soldered on the top side to prevent it melting the plastic front.

The clock is built on a small PCB and mounted with its set switches directly on the front panel. A few problems do occur with this unit which by nature of its construction is difficult to service. The set buttons can get stuck in the on position, jamming in their cutouts. Release the PCB fixings and manipulate the panel until free operation is achieved. If the clock steps forward by itself this is usually because either C902 or C903 (both 0.01μF) is leaky.

Replacement of the Texas clock i.c. or display is tricky. It's probably better to replace the complete module.

If the set is dead but the fuses are intact have a look for a short between the clock PCB and the chassis.

AGC Modification.

Late production versions of the T730/2 and T739 had improved a.g.c. fitted to compensate for very strong or weak reception conditions. This so improves performance that all sets will benefit from incorporating it. The change involves modifying the tuner to accept a.g.c. at the base of

the r.f. amplifier transistor TR1: the a.g.c. comes from the vision i.f. amplifier chip.

Fig. 4 shows the relevant parts of the tuner and main PCB print. Proceed as follows:

- (1) Open the top of the small i.f. preamplifier fitted to the tuner. If a 150Ω resistor is fitted in series with the output from the tuner remove it and terminate directly at C001/L001. Reset L002 as previously described.
- (2) Remove the tuner from the chassis. Open the cover and carefully remove R1, R2 and C2.
- (3) Fit a small-bodied 1kΩ resistor as shown in Fig. 4, allowing the body to come through the side of the tuner (without shorting).
- (4) Add an 0.02μF capacitor, a 47μF (10V) electrolytic and a 120kΩ resistor external to the tuner as shown.
- (5) Cut the track on the main PCB and add a 1kΩ resistor and 10kΩ preset as shown (the preset has to be reversed on the T730/2 – the diagram shows the T739).
- (6) Connect an unscreened flylead as shown.
- (7) Set the preset for best a.g.c. action, using strong and weak signals and noting the background grain.

Spares

Spare parts for Sonatel and Morphy Richards sets are available from Morphy Richards Consumer Products Ltd., Technical Services, 6 Albany Parade, Brentford, Middlesex (01-560 5331).

TV Fault Finding

Reports from Steve Illidge, Mick Dutton, Chris Avis, Philip Blundell, Eng. Tech., Roger Burchett, Paul Hardy and D.R. Bracknell

Hitachi NP81CQ Chassis

The card was completely blank under the column marked "fault": the shop assistant had obviously intended this one to be a surprise! In fact the set was dead. In the past I've found that the best way to prove that the power supply in these sets is all right is to disconnect it from the rest of the set and provide it with a load consisting of a 100W bulb. We did this, switched on and found that the bulb lit and the h.t. was correct at 110V. To be able to work on the line timebase separately we connected an external 110V supply to the set. With the exception of a little hum on the picture caused by our supply's poor regulation the set worked perfectly. So why wouldn't the set work with its own power supply? The only conclusion we could come to was that the power supply wasn't able to deliver sufficient current to start the line output stage. Taking a closer look we discovered that the surge limiter resistor R901 measured 11Ω instead of 7.7Ω – though it looked as new as the day it was made. A replacement cured the fault. S.I.

Lloytron 142C

A fault we've had on several of these colour portables is failure to start from cold – the power supply can be heard ticking. The problem is caused by R228 (1kΩ) going open-circuit or by dry-joints around this resistor or the line driver transformer. M.D.

Fidelity ZX3000 Chassis

By now we are quite familiar with the chopper transistor going short-circuit at switch on when the collector load

simulation resistor (usually 270kΩ) has gone high in value or open-circuit in self-oscillating chopper circuits using the TDA4600 control i.c. We were surprised to find that the relevant resistor (R91) in the Fidelity ZX3000 chassis is a tiny little half or even third watt type. In one set that came our way this resistor was open-circuit, the TDA4600 chip had been destroyed, the BU426A chopper transistor had gone short-circuit and R90 (22Ω) between the BU426A's base and emitter was open-circuit.

We've had to change a number of line output transformers in these sets. The symptoms in each case were no results with the h.t. low and the power supply making a noise to show its distress. A point to note is that the 20" and 22in. chassis use different transformers.

An improved mains filter panel was introduced to prevent medium-wave radio interference. M.D.

Panasonic TC361

This set was tripping. It's an elderly model with a thyristor line output stage, but it has proved to be very reliable. The tripping problem with this one was due to the 24V supply rectifier D554 being short-circuit. M.D.

Philips TX Chassis

This portable gave no results, though there was hum from the speaker. The 11V line was found to be high at 15V and couldn't be reduced. After fruitless checks on the transistors in the regulator circuit realisation dawned that there was no line whistle. The set was then powered more

safely from the 11V bench supply and attention was turned to the line timebase. A scope check showed that there was line oscillation at the base of the line driver transistor but not at its collector. A replacement BC337 cleared the fault and restored correct regulation. To improve the e.h.t. regulation, the error detector transistor in the series regulator circuit samples the 26V boost line instead of the 11V rail. With no line drive the boost voltage was absent and the regulator circuit inoperative – the supply was coming via the parallel, unloaded resistor, hence the misleading 15V. C.A.

Sanyo CTP6132 (80P Chassis)

At switch on or anything up to four hours later line lock would suddenly go out beyond the range of the main hold control. Adjusting the preset VR410 would then produce a locked picture displaced about 4in. to the right. A previous repairer had already replaced the LA7800 sync/timebase generator chip so the fault had to be elsewhere. Various strange faults on this chassis can sometimes be caused by poor connection of the metal strap from the line output transistor heatsink, but unfortunately not this time. After a lengthy search the culprit was found to be an erratically open-circuit capacitor (C4012, 0.039 μ F) in the "AV Control-2" circuit on the deflection subpanel. C.A.

Teleton CPL144

This colour portable gave no picture until the sub-brightness preset VR305 was wound up, producing plenty of monochrome picture but no colour. Backing off the killer bias preset VR304 then produced unlocked colours. Waveform checks around the μ PC1365 colour decoder i.c. revealed a lack of line pulses at pin 19. These pulses come from the line oscillator on the timebase subpanel via a 15mH filter choke, L502, which was open-circuit. C.A.

ITT CP9210

This oddball 14in. portable of W. German origin had no line lock. Positive- and negative-going pulses from a centre-tapped winding on the line output transformer are fed to the flywheel line sync discriminator circuit via two 22k Ω resistors, R518 and R519. Both were open-circuit. The owner later confirmed that the picture had been "wriggling for several weeks". . . C.A.

Philips CTX-S Chassis

I knew I'd got trouble as soon as I took the back off this one: there was the mains fuse, wrapped in blackened silver paper! The chopper transistor was short-circuit but when it was replaced the set was still dead. The trip transistors Tr7330 and Tr7331 were both short-circuit and the associated resistors R3334/7/8 were open-circuit: coil L5355 which is in series with the chopper transistor was also open-circuit. P.B.

Thorn 3000 Chassis

This case is ideal as a reminder of what some people will put up with before requesting service. The trip was operating and the following faults were dealt with. The tripler had a number of pinholes; one video output transistor was short-circuit; all three driver transistors were leaky; one of the thick-film unit load resistors was

open-circuit; two of the first anode supply switches were leaky; one of the 1M Ω first anode control feed resistors was open-circuit; most of the electrolytics in the field timebase had dried up; the volume control was noisy. Any idea what the owner could see on the screen? R.B.

Philips G8 Chassis

I had a filthy, smelly, nicotine filled G8 in for overhaul recently and decided to add D.R. Bracknell's soft-start circuit suggestion (September 1985, page 613). I can confirm that the h.t. supply now builds up slowly and without the tendency to overshoot he describes, so I'll be modifying other suitable candidates that come in. Thanks Mr. Bracknell!

The problem with another G8 was picture size variations. The h.t. voltage was found to be varying and an examination of the power supply revealed that one of the charging/phase shift resistors, R1373, had a burn nearly right round. It was rated at 0.5W though all the panels I've checked since have had 1W resistors in this position. The h.t. reservoir capacitor C1385 (600 μ F) had already dried up. R.B.

ITT CVC9 Chassis

Les isn't the only one (page 698, October 1985) to have trouble with the power supply electrolytics not being earthed: intermittent fuse blowing can be traced to an arc at the tags if these are dry-jointed. R.B.

Grundig GCS100 Chassis

I must admit that I never got to the bottom of this one. The complaint was low contrast, and sure enough the picture had a washed out look with the customer contrast control doing nothing. It seemed that the beam limiter might be operating, but disconnecting this made no difference. Discrete component checks on the RGB board revealed nothing, so we decided to change the TDA2800 matrixing i.c. This is not the most common of chips, but I eventually found that Telepart of Wolverhampton had some. By this time I'd noticed an intermittent fault in the blue output stage and as business was pressing I decided to get a new RGB board. Sendz Components were able to supply a board at a much cheaper price than the Grundig exchange service (they were in short supply at Grundig anyway). Fitting this restored normal operation but whether it was the chip or the board that was at fault remains a mystery. Any comments? R.B.

Sony KV1810UB

To remove teletext interference on these sets check all the electrolytics in the field timebase, replacing any that are suspect. If this doesn't work increase the value of C559 from 1 μ F to 4.7 μ F. P.H.

Sony KV1820UB

The problem with this set was a ripple on the line scan accompanied by a loud whistle from the power supply five-ten minutes after switching on. A check on the h.t. line during the fault condition revealed that the voltage was normal: reducing it by means of VR601 cleared the fault, producing a stable but smaller picture. Although the switch-mode power supply is normally locked to the line frequency I decided to check it out of circuit using a 100W

bulb as the load, across pins 1 and 3 of connector CNF3. When operated in this way the power supply worked correctly, with an adequate range of h.t. adjustment. The same results were obtained using a 200W bulb as the load. It seemed therefore that the fault was independent of the output voltage and load.

After much examination of the power supply panel D612 in the kick-start circuit was found to be shorted, but

replacing this didn't clear the fault. The pulse-width modulator waveforms were o.k. – but not when the power supply was restored to the set, with the line sync feed connected. There was now ripple, whistle and a horrible waveform. Further checks revealed that the 18V supply to the pulse-width modulator had a 2V ripple on it. Replacing the reservoir capacitor C612 (3.3 μ F, 25V) restored normal, "quiet" operation. **D.R.B.**

Thorn 8000 Series PSU Modifications

Tony Livesley, G8JAI

The Thorn 17in. 8000 chassis has been around for a long time but continues to give good service – apart from its notorious power supply. Most of the trouble here is caused by failure of two h.t. resistors that are vertically mounted on the panel – R727 and R729. In the later 8000A/8500/8800 chassis these resistors are part of the mains dropper assembly. The fact that the 8000's power supply is not interchangeable with those used in its larger-screen relatives is also a problem.

Most 8000 chassis will by now have been fitted with a replacement dropper of the 8000/8000A type which has four sections. When this type of dropper is used in the 8000 chassis the 1k Ω and 56 Ω sections are not used – in this chassis they are the previously mentioned vertically mounted R727 and R729. Using these sections of the dropper in the 8000 chassis gives improved reliability however: details are given below. The two types of dropper are shown in Fig. 1. A further modification enables the 8500 or 8800 power supply to be used in the 8000 chassis. This is the best course to adopt since it means that only one type of power supply needs to be kept in stock.

First the modification to use all sections of the dropper in the 8000's power supply. Having succeeded in coaxing the power supply from the bowels of the set, remove resistors R729 (1k Ω) and R727 (56 Ω). Check the panel carefully for faulty connections and cracks, especially at plugs PL8/9/10 and resistors R701, R730 and R704. Refit the power supply in the set and turn the h.t. preset R725 fully anticlockwise (minimum h.t.). Disconnect and isolate the lead that goes to the collector of the line output transistor VT401 – this will ensure that it's not damaged in the event of excessive h.t.

Using the continental metric type push-on terminals at each end, make up a 2.5in. wire link covered with heat-resistant sleeving. Fit one end of this on to the double tag at one end of the 47 Ω section of the dropper resistor. The existing lead here should be yellow: it goes to C704 (700 μ F). Fit the other end of the new link to the centre of the 56 Ω /1k Ω sections of the dropper.

Using another terminal and sleeve, run a length of wire from the top tag of the dropper's 56 Ω section to either one of the right-hand tags on L406, which is fixed to the chassis frame at the bottom of the timebase panel adjacent to the contrast control. The existing lead on the tag required is red/grey or red/white – depending on how faded the colour is!

By the same method fit another length of wire to the lower tag of the dropper's 1k Ω section and run this across the bottom of the chassis: solder it to the print side of pin 5 on plug 11 at the bottom of the timebase panel.

Now check your wiring! Monitor the h.t. at the double

tag on the 47 Ω section of the dropper. The reading should be about 120V when the set has been switched on. If o.k., switch off and reconnect the lead to the collector of VT401. Power up again and adjust the h.t. for a reading of 170V. This completes the dropper modification.

Now for the modification to enable an 8500/8800 power supply to be used in an 8000 chassis. You will first have to carry out the modification just described.

Remove the red/yellow lead and its socket pin from position one of plug 10 on the power supply. This can be done by inserting the blade of a very small screwdriver or a hat pin between the socket pin and plug moulding at the opposite end to the wire outlet and carefully pressing down the small tab which can be seen through the plug's semi-opaque material. Be careful not to distort the socket during this operation as it will then be impossible to remove.

By the same method remove the brown wire and its socket pin from position 8 of plug 10. Slightly retension the tab and insert this brown wire into position one of plug 10 – where the red/yellow lead previously went.

If difficulty is experienced the leads can be cut, the one from 10/1 about an inch from the top of the plug, that from 10/8 flush with the top. The brown wire can then be joined to the remaining stub of the red/yellow wire. A neater way of going about this is to remove the previously described wire to pin 5 of plug 11 on the timebase panel, shorten it as required and join it to the now dormant red/yellow wire that originally went to pin one of plug 10 on the power supply.

Now fit an 8500 or 8800 power supply to the set. Adjust R725 for minimum h.t. and set up as described for the 8000 panel.

Some 8000 series power supply panels can be converted to the 8500 arrangement simply by refitting R730 (8.2k Ω) in the alternative horizontal position indicated. R727 and R729 will of course have to be removed.

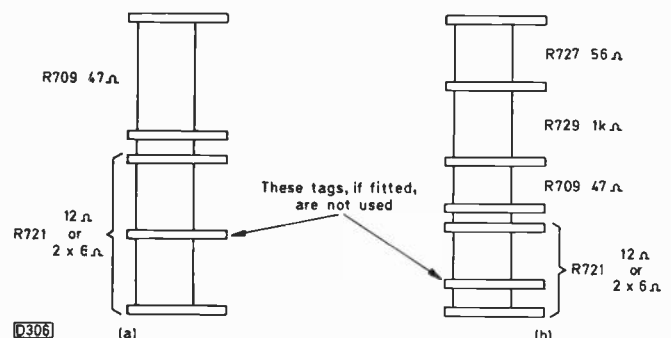


Fig. 1: Different types of dropper used in the Thorn 8000 chassis. (a) Early type. (b) 8000A type.

Teletopics

RESULTS FOR '85

1985 was another good year for CTV sales in the UK. Deliveries of colour sets to the trade rose by 4.3 per cent to 3,670,000, following a rise of 2.2 per cent in 1984. In contrast to 1984 however stocks at the end of 1985 were in line with current trading levels. An increase in sales of large-screen sets is put down to the advent of the FS tube. The percentage of imported sets fell to 34.5 per cent. VCR deliveries increased from 1,417,000 to 1,656,000 following a sharp fall (34.4 per cent) in 1984. Twenty per cent of the VCRs were UK manufactured. Deliveries of teletext equipped sets rose to 745,000 – 15 per cent of homes now have a teletext set. Camcorder deliveries increased to 50,000. Elsewhere CD player deliveries rose from 33,000 to 147,000 while deliveries of home computers fell from 1,700,000 to 945,000.

JAPANESE FIRMS HIT BY YEN

The rise in the value of the yen, up from 214 to the dollar last October to about 160 to the dollar at present, has knocked the profits of many Japanese electronics firms. Most firms end their financial year on March 31st. Hitachi has reported a profit decrease of 38.2 per cent, the first for eleven years, Toshiba a 44 per cent decrease, JVC a 51 per cent drop, Mitsubishi a 52.6 per cent fall, Casio Computer a 21.1 per cent decrease and Fujitsu a fall of 68 per cent. All these percentages are on the pre-tax figures. Sharp on the other hand managed a 1.6 per cent increase. The profit falls are despite increased sales in many cases. Since the rise in the value of the yen occurred in the latter part of the year further profit falls are expected this year. Sony's chairman Akio Morita summed up the situation in pointing out that "at 200 yen to the dollar the hourly wages in our San Diego and our Japanese factories are the same". Despite all this Japanese firms have been slow to increase their prices in overseas markets: it seems that market share is the prime consideration, to maintain factory loading. Various measures are being taken to mitigate the effects of the increased value of the yen. Several firms have announced steps to increase overseas production. Sharp is to try to change its export/home sales ratio from 60:40 to 40:60. As a defensive measure Sanyo plans to merge with its associated company Tokyo Sanyo Electric.

THORN SERVICE DEPARTMENT TO MOVE

Thorn EMI Ferguson Ltd. has announced plans to move the firm's service department from Edmonton, North London to a new location at its Enfield complex. An investment of some £1.5m is being made in the company's service activity. The new site will be designed and equipped to speed up the delivery of spares to dealers and improve the turnaround time of customers' repairs. This will be achieved through automated spares handling procedures, new computer systems and additional test and repair equipment. The project is due for completion by the end of the year.

24-HOUR TV

The IBA has given Yorkshire Television permission to transmit all-night TV for a three-month trial period

starting in June. Programmes from Virgin's Music Box pop music satellite TV channel are being broadcast from 12.30 a.m. to 6.15 a.m. when TV-a.m. comes on air. Advertising is being sold to cover the service's cost. YTV has a 20 per cent stake in Music Box.

Channel 4 has announced plans to move gradually to a 24-hour service over the next two years. IBA approval would be required. Channel 4 hopes to use the increased transmission hours for further educational broadcasts and programme repeats to enable viewers to record programmes they've missed.

NO WORLD STANDARD FOR HDTV

The International Radio Consultative Committee (CCIR), meeting in Dubrovnik, Yugoslavia during May, failed to adopt a world standard system for high-definition TV. The Japanese developed 1,125 line, 60Hz system, which was backed by the USA and Canada, did not receive the necessary support due to opposition by European countries which favour the enhanced C-MAC system. The next plenary session of the CCIR will take place in 1990.

CABLE TV DOES BETTER

According to the latest figures from the Cable Authority the number of UK households connected to a cable TV service increased by 12.8 per cent during the first quarter of 1986, to 143,877. The proportion of households connected to a cable TV service has risen to 14.5 per cent – almost a million homes now have access to a cable service.

Robert Maxwell's company British Cable Services is to be reorganised. The aim is to restore the older systems to profitability and develop new franchises. A senior management team from the US cable company Viacom is to join BCS on a contract basis.

TV BRANDS

Fidelity's parent company Caparo Industries has entered into an agreement with Great Universal Stores' subsidiary company J.J. Silber to use the Murphy brand name on TV and video products. Silber, who acquired the brand name from Rank Radio International in 1981, will continue to sell Murphy branded merchandise including audio and telecommunications equipment. Silber had previously licenced the brand name to Rediffusion and a number of Murphy sets were sold fitted with the Rediffusion Mark 4 chassis. Fidelity have in the past had the rights to use the HMV brand name – the last HMV sets fitted with Fidelity chassis appeared in 1984. Caparo's chief executive James Leak says the firm will not rush into the release of Murphy brand sets: "a sensible, well thought-out marketing plan" is to be devised. The sets could be of UK manufacture though not necessarily produced in the Fidelity plant – Mr. Leak points out that "it's not going to be a simple job of badge engineering".

A 16in. transportable colour set is now being sold under the Hinari brand by Hinari Consumer Products Ltd., 20-22 Payne Street, Port Dundas, Glasgow G4 0LF (0413 327 795). The firm has also sold sets under the Trical brand name.

Network is now selling a range of Korean produced TV sets under the NEI brand name. During the course of May Network Industries and its associated company Network Marketing went into receivership and were subsequently bought by Network Electronic Industries.

Heron Electronics has given up the Thomson franchise

which will probably be taken over by Oxford Audio. Heron will continue to market Ingersoll and York equipment.

A further correction to our TV/VCR spares guide (April 1986) is required. The Amstrad phone number should have been given as 0277 230 222 (the final 2 was omitted).

IEE's TV CONFERENCE

An international conference on the history of television, from the early days to the present, is to be held by the Institution of Electrical Engineers at its headquarters, Savoy Place, London WC2 from November 13-15th 1986. The IEE is organising the conference to commemorate the 50th anniversary of the start of the world's first high-definition TV service in 1936. It will cover progress from the first proposals for television through the experiments of the twenties and the subsequent low-definition transmissions to the realisation of high-definition TV in the thirties and all subsequent advances. Contributions to the conference have been invited from people with first-hand experience of TV development, including its commercial and political aspects, in all parts of the world.

LCD TV SETS

Matsushita (Panasonic) expects to launch a pocket TV set with a 3in. colour liquid-crystal display panel next year in Japan. The LCD panel has 89,280 pixels and the price of the set is expected to be around \$300. The individual pixels (240 × 372) are driven by thin-film transistors integrated on to the panel. Colour filters are used to produce triangular RGB elements which are set against a black background. Six AA alkaline cells would provide a viewing time of some five and half hours.

Citizen (see article on page 512 last month) is at present producing LCD TV sets at a rate of 50,000 a month, 20 per cent with colour. Production is to be doubled by the end of the year. It expects the price of monochrome LCD sets to fall to around £50 by 1988 as volume production builds up.

NEW FROM MULLARD

Mullard has introduced a new delay line comb filter, type CF873, for use in European PAL standard VCRs. It offers optimum filtering, low insertion loss and low spurious reflection. Based on the DL872 the new delay line differs in incorporating a direct path resistor matched to the line. The nominal frequency at 25°C is 4.433619MHz with a minimum -3dB bandwidth of 1MHz: the delay time is 128µsec. The CF873 consists of a very thin slab of zero temperature coefficient glass provided with a split transducer, mounted in a shock-proof housing.

The new Mullard TDA4565 colour decoder chip features improved colour transient performance, reduced chroma bandwidth and enhanced definition and gradations.

UNDERWATER CAMCORDER

An accessory pack has been introduced by Sony to enable its Handycam 8mm camcorder to be used for underwater filming - to a depth of 130ft. The MPKM8 marine pack sells at £450 and includes a piezoelectric microphone. Optional accessories include the HVL80D underwater lamp (£300), NP3000 battery (£70) and LC780 carrying case (£138) which holds the kit and a battery charger.

THE FULL THORN RANGE now available from **SOUTHPARK DISTRIBUTORS**

**Unit 4 Rubastic Road,
Southall, Middlesex
01 574 4631 EXT 28**

**9K-9K6-TX9-TX10 TEXT &
FULL REMOTE ALSO VIDEOS
V.H.S. & BETA. LOTS OF
WORKERS FOR BUSY DEALERS**

The alternative SPKM8 sports pack, at £80, is described as splashproof and is intended to provide protection for outdoor use.

ATV AERIAL

On-glass Aerials Ltd. have developed a range of u.h.f. aerials that feature no-hole fixing. Though developed primarily for the private mobile radio market the OW432 version can be used on the 70cm band by amateurs not wishing to drill holes in their vehicles. The price is around £35 plus VAT and a v.h.f. version (2m band) is expected to become available shortly. Enquiries should be sent to B.D. Price G4DVB, 93 Highview, Vigo Village, Kent DA13 0TG.

FAST ACCESS TELETEXT

It's hoped that a new chip plus new editorial techniques at Ceefax/Oracle will enable FAT - fast access teletext - to be introduced next year. The system gives instant access to four pages related to a selected page: cue marks appear at the bottom of the screen, relating to colour-coded buttons on the remote-control unit. The extra chip is used to keep the cue pages in store. A FAT decoder would add about £20 to the cost of a set. Work is at present being carried out on developing the editorial techniques required.

SATELLITE TV EQUIPMENT

A new company has entered the satellite TV field. Satellite Technology Systems Ltd., Satellite House, Blackswarth Road, Bristol BS5 8AU (0272 554 535) has introduced two TVRO terminals, one aimed at the domestic market and the other providing for signal distribution to up to 200 standard TV sets. The domestic STS300 series system comprises a 1.2m offset parabolic dish aerial, low-noise converter and SSR7700 receiver unit. It sells at around £1,000. A polarotor is available as an optional extra. The company has set up a training centre for dealers at its Bristol headquarters.

Connexions Satellite Systems (125 East Barnet Road, New Barnet, Herts EN4 8RF (01-441 1282) is now offering a "starter" satellite TV receiving system at £895 including VAT. It has a 1.2m offset polar mounted dish that can be motorised at a later date if required.

Carlton Communications plans to market 10,000 satellite TV receiver systems in the UK and Europe this year through its Skyscan subsidiary. The system will include a 1.2m motorised dish aerial and the suggested price is around £1,150 including installation.

Return of the French Lady

Les Lawry-Johns

You may recall the French lady whose ex-husband taught Scottish rig workers how to swim (she said). She has another set now and it's giving trouble. A Pye 731 which also gave me trouble, mainly because I didn't want to carry it from her flat, round the square and out to the car.

The Pye 731

First there was intermittent sound which I thought was due to a dry-joint. It turned out to be a poor plug/socket connection. After getting this right the sound still wasn't clear – it sounded as if the speaker was rubbing. So I said I'd be back with another speaker as soon as I could. Shortly after I was back with a nice new speaker with a free floating cone and proceeded to fit it. She was nattering away and I vaguely heard something about the picture going off. With the speaker fitted the sound was fine and the picture showed no sign of going off. I tapped around but it wouldn't do anything wrong. So I left it at that.

Next day she phoned again and read out a long list of the times when the picture had gone off, apparently for very short periods and with no regular pattern. So I sallied forth again and this time managed to make the picture go off by applying pressure to the TBA990 chip on the decoder panel. I immediately resoldered every joint in the vicinity. After this I couldn't make it go off so I departed, thinking that that was the last of the matter. It wasn't. I had to return several times subsequently, replacing in turn the line output transformer, the BU208 line output transistor, the tripler and for good measure the 0.1 μ F first anode supply reservoir capacitor C563 (1.25kV). It was a nightmare and every time the phone rings I dread hearing that voice "allo, allo, this is ze French woman talking". And talking, and talking.

Mother-in-law's Set

A young fellow brought in this ITT hybrid colour set (CVC8 chassis) and said it belonged to his mother-in-law. I'd no idea whom he was talking about. The repair took some time as the boost capacitor had gone short-circuit (as usual) but had this time taken the PY500A boost diode and 56 Ω h.t. feed resistor with it. I did all that was necessary and wrote out the bill, charging fifteen pounds. A fortnight later all hell broke loose.

A voice which I vaguely recognised phoned to say that the TV set I'd "thoroughly overhauled" was giving trouble after being moved round the room. So I got the car out and nipped over to see what I could do. I was appalled when she opened the door. I knew her all right, and knew the language to expect. Talk about that young girl with the long blonde hair, she was a saint in comparison. Leaving aside the language, the woman was demanding to know why a set that had been "overhauled" so recently should give trouble so soon. She waved the bill in my face.

"Look at this, fifteen **** quid. You should be ashamed of yourself."

"If I'd known it was your set I wouldn't have touched it in the first place" I bawled back.

Anyway, she insisted that I saw the set working. The

picture was wavy and the colour was in bars. I thought that moving the set had disturbed a poor earth connection. It transpired however that the AD161 l.t. regulator transistor (left side) was leaky. I had one with me and it was in before you could say knife. The picture was now perfect.

"I wonder how long that will last. You people certainly know how to rob us poor ****s."

"Well this poor **** is going off now, having performed a miracle in front of your eyes. I don't intend to repeat the performance. Goodbye."

I got to the car while she stood at the garden gate waving the bill in the air and bawling about wanting her money back.

Beardy's Brother

I thought I'd seen the last of beardy and hope I have. His brother came in however, struggling with a 26in. TX10. The back cover was held on by Sellotape and I felt sorry for myself.

"This television you see, there's very little wrong with it. Just a little something that stops it working properly. I'll leave it with you and call back later when you've fixed it for me."

I switched it on and the tube's heaters glowed. Oh well, that's a start. He'd left the remote control unit and although I pressed the brightness button no raster appeared. The first anode voltage was low at about 200V. I smelt a rat – someone had been messing about. I turned up the first anode control until the voltage measured 400V. The raster was now present but with an aerial plugged in there was no picture. I checked the tuning but nothing could be resolved. The tuner was suspect but a new one had recently been fitted. So I turned my attention to the i.f. module. Fitting a replacement made no difference. Back with the original and out with the tuner, using a yard of desoldering braid because whoever had fitted it had been over generous with the solder. I fitted a new 1043 and got a picture that was very grainy. A.G.C. I thought, so I adjusted the small preset on the i.f. panel and it made no difference at all.

I thought the new tuner might be faulty and like a fool fitted another. Again no difference. The aerial socket may be? I connected a new one to the tuner, just hung it on so to speak. The picture was best with only the inner connected, the braiding left off. This confused me so I fitted another aerial socket which did the same thing. I left it for a moment to serve a customer who wanted to know why he was getting severe interference in the shape of another picture floating around on top of the one he wanted.

"Continental interference" we advised him. "Leave it alone and it'll go away."

When I got back to the TX10 I'd forgotten what conclusion I'd reached, and came to the conclusion I'd not reached one. I then injected signals into the i.f. module and found that the output was weak. So I refitted the new one. This restored normal reception and I wrote out a bill for a very reasonable (I thought) £20. I was prepared for a performance and I got one.

"Both these things faulty? One I can understand but not two. Are you sure?"

"Yes I am sure and it took me long enough to work it out. In any case I've only charged you for one."

"Twenty pounds is a lot of money. Can you make it fifteen?"

"I'll make it nothing" I snapped, tearing off the Sellotape that held the rear cover. "I'll put back your tuner and your i.f. unit and you can take it elsewhere."

"Oh no, no. I was only joking. Here's your twenty pounds. I never argue about money."

I refitted the Sellotape and off went beardy's brother, nattering away in a language I didn't understand.

Fidelity Portables

The 14in. Fidelity portables (ZX2000 chassis) are now using up line output transformers at a rate of knots. If you handle them you must keep a couple of transformers in stock, complete with the small subpanel that enables the newer type to be fitted to the older type of panel. A leaflet explains the steps to be taken – remove the focus unit and first anode control etc.

One came in the other day with the complaint that though it chattered away in various tongues it didn't show a picture. I didn't at first associate this with the line output transformer as the fuse usually fails when the transformer is defective. In this case it hadn't because the 10 Ω , 2W h.t. smoothing resistor, in the feed to the line output stage, had gone instead. This left the chopper working and the supply to the TDA3190 sound i.c. intact.

Mrs Steadfast's New Set

Mrs Steadfast has bought a new Fidelity from us. She complained because it didn't have a carrying handle and I complained because of the tuning arrangement. It has three buttons at the rear: up the scale, down the scale and store. It would have been easier if these had been at the front or on the side. It's easy once you've had a bit of practice however. Her old set, a 26in. Swedish monster, had to be carried out through the door, along a corridor and into the back room. I did it alone, though there was a male who didn't lend a hand present. I'll remember that Harold: the set was very heavy, and me in my condition. But I didn't complain. I never do.

Whatever Next?

I had a shock the other morning. I got up fairly early to let the dog out and was pottering around in the kitchen when I heard a knock on the shop door. There was a large van outside, with Sheepless Nights on the side. The man at the door asked whether it would be all right to bring the bed in.

"I haven't ordered a bed" I said.

"I did" came Honey Bunch's voice from the toilet.

So in came this great big bed, which she assembled later in the day, and out went my nice comfortable favourite.

As we sat there that evening H.B. asked why I was knocking back the whisky (Cutty Sark this time).

"So I can face getting into that high, firm monster in there" I growled.

"We'd had that old one for twenty years. It had a dip in your side and was all misshapen."

So we went to bed and had a good night's sleep, much to my surprise. New bed – what next?

next month in

TELEVISION

● INSTALLING TVRO TERMINALS

Part 1 of a new series by Harold Peters on the principles and practice of satellite TV reception. Next month's instalment deals with basic installation – dish mounts and siting and tuning in the receiver.

● THE ELECTRIC MOTOR

The large numbers of VCRs nowadays being handled by service departments have brought with them a need to know something about electric motors. Mike Phelan's new series explains their operation and, since they can be expensive items, provides hints on ways of repairing them. The many different types of electric motor will be described.

● TIMEBASE SYNCHRONISATION

J. LeJeune deals with sync circuits, from the simple one-transistor sync separator stage to the complex arrangements used in modern sync processing i.c.s. Flywheel line sync will be explained, also the generation and use of sandcastle pulses.

● RGB INTERFACING CIRCUIT

Brian Webb presents a simple circuit that can be used to interface a microcomputer with RGB plus sync outputs to an older set with a delta-gun tube. An inexpensive way of obtaining an RGB monitor.

● SCAN YOKES FOR COLOUR TUBES

In Part 3 of his series on colour tube technology Eugene Trundle takes a look at the scan yoke and the ways in which yoke design has evolved to meet the needs of modern self-converging and pinfree tube systems.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW:

TO.....
(Name of Newsagent)

Please reserve/deliver the August issue of TELEVISION (£1.20), on sale July 16th, and continue every month until further notice.

NAME

ADDRESS

.....

.....

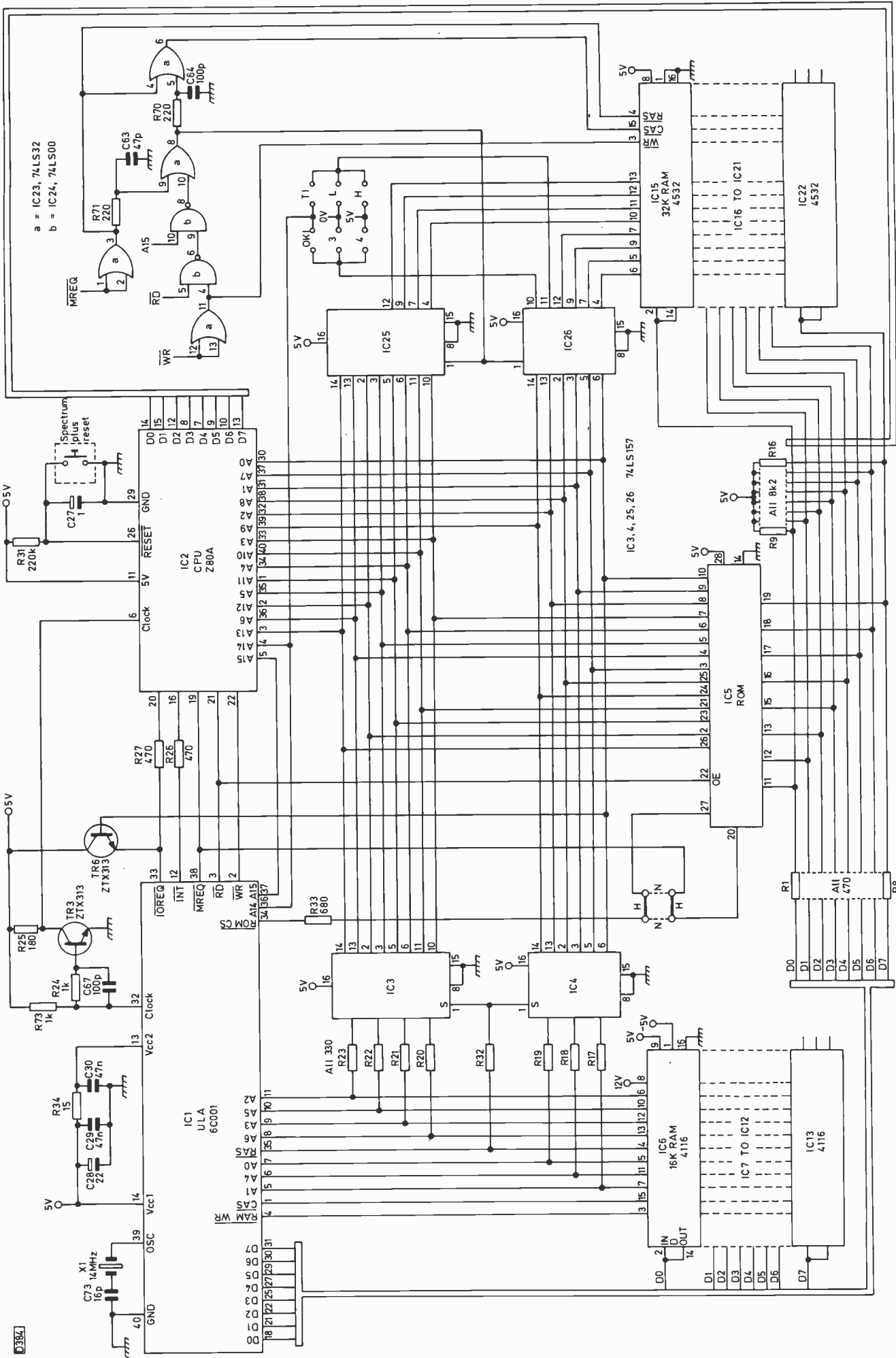


Fig. 1: The basic digital computing circuitry used in the Sinclair Spectrum microcomputer, issue 3 version.

Servicing Sinclair Microcomputers

Part 3

Ken Taylor

This month we start on the Spectrum. Let's first take a quick look at the development of this machine over the past few years. There have been four standard PCBs marked issue 1, 2, 3 and 3B. After each change a few modifications were generally required to make the new design operational or to implement further improvements – even the 3B board has now been modified. It's often possible to determine the issue number without opening the case. The clues are as follows:

- (1) If the rubber keys are a light fawn colour it's an issue 1 board.
- (2) If the keys are dark grey, look into the edge connector slot to see whether an aluminium heatsink is visible – especially at the power socket end. If you don't see the heatsink it's an issue 2 board which has the heatsink near the forward corner of the board, under the keyboard.
- (3) If the heatsink is visible it's an issue 3 or 3B board – there is very little difference between them.

The Spectrum Plus usually has an issue 3B board, but watch for earlier models that have been fitted with a Spectrum Plus keyboard kit – this can now be obtained separately.

In this write-up I shall be dealing primarily with issue 3 and 3B models, though I hope to mention the earlier models where the differences are important.

dedicated i.c. (type LM1889) which also provides the video output in colour. This latter arrangement explains why with an otherwise dead machine a vertical striped pattern of "bricks" flickers up and down the screen and goes on working even when the CPU has been removed.

Which reminds me – I haven't explained why we're not providing a block diagram for the Spectrum. I don't see that this would be of much advantage. Apart from illustrating the two differences I've just mentioned it would be much the same as the block diagram given for the ZX81. Instead I'm showing most of the circuitry, which by now should be fairly self-explanatory.

The first circuit section is shown in Fig. 1. This includes the basic digital computing circuitry. For clarity, most of the decoupling and smoothing capacitors have been omitted. The input/output circuitry, including the TV output, tape input and output and the keyboard connections have also been omitted: these will be shown later.

Fig. 2 shows the layout of the issue 3 Spectrum to enable you to find the main components as we refer to them. The differences between this and the issue 2 board are not very great. Because of the changed position of the heatsink, the keyboard socket at the right-hand side of the board has been moved slightly rearwards and the regulator is in the middle of the right-hand edge. Most of these features become obvious when you compare an earlier issue board with the layout shown in Fig. 2.

Circuitry

The Spectrum differs from the ZX81 (see last month) in two major respects. First it's designed to carry the full memory (48K RAM) on the PCB. Secondly the TV display is serviced automatically by the ULA chip and a

Access

You can't do that however till you open up the machine, so here goes:

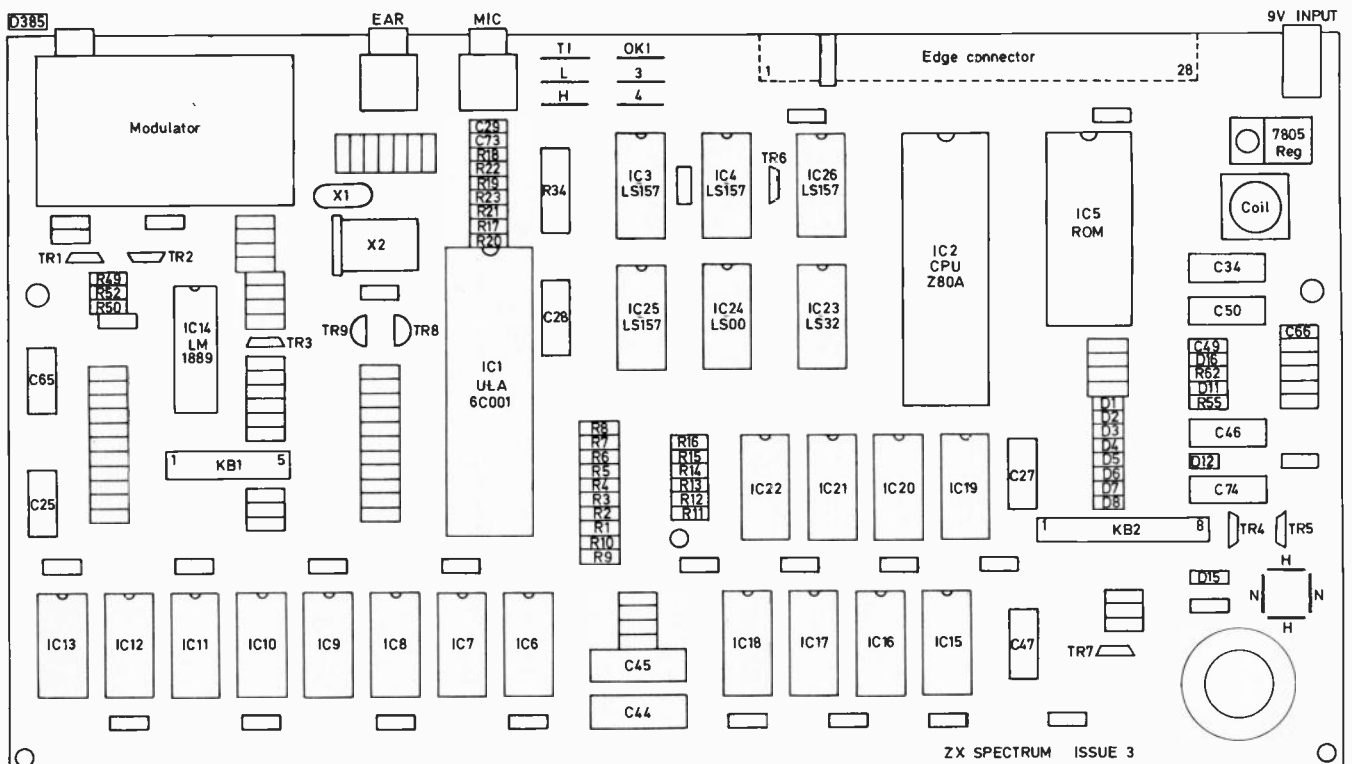


Fig. 2: Layout of the issue 3 Spectrum panel.

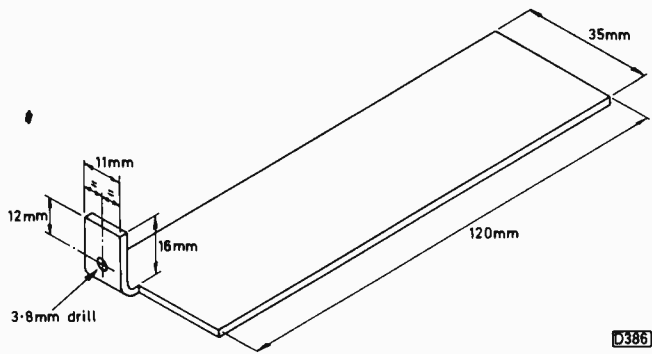


Fig. 3: Temporary heatsink for use when carrying out servicing work on the Spectrum.

- (1) Turn the machine over and remove the five screws – eight with the Spectrum Plus.
- (2) Turn it back, carefully holding the two parts together. Lift the top, tipping it on to its rear edge so that the keyboard tails can be removed from their sockets. Remember what we said when dealing with the ZX81 about the fragile nature of these tails: the Spectrum is just as vulnerable in this respect.
- (3) As with the ZX81, the machine should still initialise when the keyboard has been disconnected, and on start up should display “c 1982 Sinclair Research Ltd.” on the bottom line. The keyboard can be left disconnected until this has been achieved.
- (4) Before much serious work can be undertaken the heatsink must be removed to provide access to the components beneath. This is even more important with issue 3 and 3B models which have a larger heatsink that covers many of the more important components. The temporary heatsink I use when working on any Spectrum board is shown in Fig. 3. Don't worry if you cannot find a piece of copper or aluminium exactly the right size – the only important section is the little bent-up end which has to fit under the regulator. Even here, if your metal is too thin you can stick another shim of metal to the back so that the regulator legs are not distorted when you screw the heatsink underneath it.

Fault Finding

The internal voltage generator circuit is shown in Fig. 4. This is one of the circuit areas that often suffers when a fault develops. It consists of a 5V regulator and a blocking oscillator (TR4) whose output is rectified to produce the 12V and -5V lines required by the 4116 memory i.c.s that provide the initial 16K of RAM. An interesting regulation technique is used: the blocking oscillator's timing capacitor(s) are charged by the constant-current transistor TR5 whose base is controlled by feedback from the 12V line. The outputs are taken to the edge connector and perhaps this is the problem. It seems that TR4 dies when there's the slightest extra load. This is often caused by a joystick interface being removed or fitted while the machine is switched on and probably shorting out one of the supplies. But the 4116 memory i.c.s sometimes develop shorts and then the problems start.

I've shown the oscillator current in Fig. 4. It's often necessary to supply the board from a bench supply and monitor this current. With a supply provided for the 5V rail, wind up the supply to the oscillator slowly from zero. Monitor the current drawn by the oscillator: if the reading exceeds 300mA switch off quickly and remove one/some of the memory i.c.s or cut the 12V supply tracks to pins 8.

Finding the faulty memory or memories is very hit and miss but if you've a good record at pontoon or the football pools you may be lucky!

Earlier circuits were slightly different from the issue 3/3B circuit shown but the differences were often only in the component values and it's worth noting that all issues use the same component reference number for components in the same circuit position.

One more point. Because of the omission in earlier versions of the asterisked 22µF electrolytic capacitor, unless you have the 3B version the 12V line will be at about 11V even when the oscillator is not working. This can present a very confusing situation, so ensure that your first check is always on the -5V line, which will be absent if the oscillator isn't working. The frequency of oscillation, which isn't very critical – or stable – is about 6.6kHz.

Having eliminated faults in the voltage generator circuit and hopefully in any of the 16K RAMs, why doesn't the thing work? Assuming that you are still getting the flickering vertical columns the ULA and the TV video generator chip appear to be o.k., so what else? Remember that your check on the memory i.c.s, made whilst

Table 1: Signals on the i.c. pins

Pin	IC1	IC2	IC5	IC6	IC15
1	P	P	OC	L	L
2	PH	PH	PH	P	P
3	P	P	P	PH	PH
4	PH	P	P	P	P
5	P	P	P	P	P
6	P	P	P	P	P
7	P	P	P	P	P
8	P	P	P	H	H
9	P	P	P	H	H
10	P	P	P	P	P
11	P	H	P	P	P
12	PH	P	P	P	P
13	H	P	P	P	P
14	H	P	L	P	P
15	P*	P	P	P	P
16	P*	PH	P	L	L
17	PH	H	P		
18	P	H	P		
19	H	P	P		
20	H	PH	P		
21	P	P	P		
22	P	PH	P		
23	H	H	P		
24	H	H	P		
25	P	H	P		
26	H	H	P		
27	P	P	P		
28	L	P	P		
29	P	L			
30	P	P			
31	P	P			
32	P	P			
33	PH	P			
34	P	P			
35	P	P			
36	P	P			
37	P	P			
38	P	P			
39	†	P			
40	L	P			

P = pulse, high and low LEDs lit.
 P* = pulse LED only lit.
 PH = pulse and high LEDs lit.

H = high LED lit.
 L = low LED lit.
 OC = no LED lit.
 † = display affected.

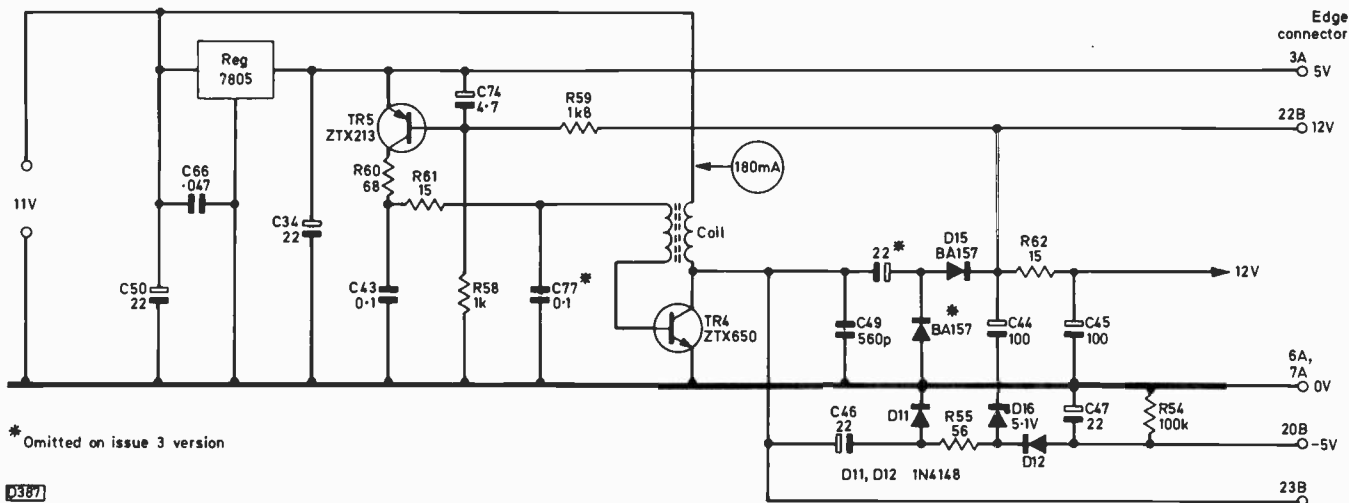


Fig. 4: Voltage generator circuit used in the Spectrum – issue 3B version. With the issue 3 version R60 is 270Ω, C49 is 47nF and the asterisked components are omitted. Edge connector numbers suffixed A are on the underside of the board, those suffixed B are on the component side (top). The input from the power supply is approximately 11V on load (650mA).

repairing the voltage generator (if necessary), detected only those i.c.s taking excessive current, not those with other faults. So first try the piggy-back check I suggested for the ZX81 last month. Clip a good 4116 on top of each of the remaining original memories and see whether this makes a difference. If the extension memory chips (IC15-IC26) are fitted they can be turned off either by removing the memory chips or IC25 (one of the 74LS157 multiplexer chips). Alternatively the 5V supply track to pin 16 of this i.c. can be cut, but this is not easy with the issue 3 board as the track is thicker than usual.

The 4116 memories are also addressed via the 74LS157 multiplexers IC3-4. You may recall our earlier comment that dynamic RAMs such as the 4116 are addressed by a row/column sequence so that only half the theoretically required number of address pins are needed. The internal system stores the first half of the address and then combines it with the second half to provide the full 16-bit address. The ULA has this facility built in, so it doesn't

require multiplexers to address the RAMs.

Note the buffer resistors in the address lines between the ULA and multiplexers IC3-4. These allow the ULA to take control of the address bus when the screen needs updating, irrespective of the demands of the CPU. These buffer resistors are very useful when you are fault finding. Any loss of signal tends to be isolated to one side of the buffer, enabling the faulty i.c. to be detected. In this case, if the fault is on the ULA/RAM side removing the ULA or cutting the track will usually pinpoint the fault.

If you still have a fault, it's probably in the CPU or the ROM and a full check on the circuit will be necessary. Table 1 shows the signals that should be present at each pin of the main i.c.s, with the keyboard disconnected and the Sinclair logo displayed, when monitored using a logic probe (a Tandy Micronta was used). This should enable you to isolate and replace the faulty i.c.

Next month we'll look at the rest of the circuit and some of the variations and modifications.

Letters

SERVICING MATTERS

I would like to add some comments to S. Simon's note about the Thorn 1690 chassis (May issue, page 444). He is quite right in saying that when the e.h.t. rectifier goes short-circuit the line output transformer's windings are damped and the l.t. supply is severely reduced. But he fails to say what to do if, after removing the anode cap from the tube, normal operation is not restored. The answer is simple. Undo the two nuts on top of the transformer, lift off the overwinding, replace the top C core on the transformer and retighten the nuts. Switch on and you should find that the l.t. supply is back to normal. The reason for this is that when the e.h.t. rectifier diode goes short-circuit the overwinding overheats and does the same thing.

He also mentions adding an external diode, well insulated, when the internal diode has gone short-circuit. This is bad practice and not to be recommended when you are dealing with voltages of some 11kV, especially when a new overwinding with diode, lead and anode cap can be obtained from Sendz for only £2.50 and fitted in minutes.

In the April issue Alan Shaw mentioned loss of colour in the Rank T24 chassis when the pulse feed resistor R229 goes high in value (TV Fault Finding, page 372). We had this fault some months ago but the symptoms were more obscure. The initial complaint was loss of colour on changing channels. After a period of time on soak test the symptoms started to change: there was random colour drop-out, followed later by intermittent Hanover bars. As we were working without a manual many hours were spent on wild goose chases before R229 was located and changed – it was completely open-circuit.

Michael Dranfield,
Buxton, Derbyshire.

RANK Z179 CHASSIS

We had a strange fault recently with an old Rank set fitted with the Z179 chassis. There are still a few of these sets around, producing acceptable pictures. This one wasn't – in fact it was brought into the workshop with the report "dead".

When we pressed the reset button the h.t. began to rise. Then "click" and the cutout had tripped. On disconnecting the cutout protection circuit, using the link provided in the crowbar thyristor's gate drive circuit, and switching the set on a picture was present and sound as well. A

check on the h.t. voltage, using an Avo 8, produced a reading of some 290V – over 100V more than the correct figure of 187V. Thus the e.h.t. was running at a steady 36kV. In view of X-ray radiation the set was switched off pronto.

To cut a long story short, when the set e.h.t. control 4RV18 (1.5kΩ) was set to minimum e.h.t. the actual voltage was still 32kV. So we fitted a 3.3kΩ preset and were able to reduce the e.h.t. to approximately 24.8kV. Phew!! The h.t. was now correct.

I've mentioned this to several engineers in the Devon area and it seems that the fault is not unknown. Maybe just a few sets are prone to this, but I've not seen it mentioned before in *Television*.

Mike Austin, Austin Electronics,
Bere Alston, Devon.

GRUNDIG 6010 SOUND PROBLEMS

In the April issue Service Bureau it was mentioned that gradually rising sound in the Grundig Model 6010 can be caused by leakage in either the paddle switch or the memory cell. It can also be caused by whistle from the line timebase. To check, disconnect the NS transducer from the TD panel. It appears that a harmonic and a subharmonic could be producing a beat frequency – the line frequency $\times 5/2$ (third harmonic minus second subharmonic maybe?) gives 39.06kHz: the control frequency for sound increase is 38.5kHz.

I've also recently experienced a faulty PCL86 audio valve in an ITT set fitted with the CVC5 chassis – the triode's cathode had shorted to the pentode's cathode. The PCL86 has a shield between the two sections, connected to the pentode's cathode. The wire from the triode's cathode to pin 2 is dressed around this shield and in the faulty valve it was touching the shield. I hope these observations will be of help.

Incidentally woodglue is very good for damping the cores of line output transformer's etc. when whistling is suspected.

S. Pearson,
Chipping Norton, Oxon.

GEC C2110 SERIES TIP

I recently had a GEC 2015H whose field timebase refused to lock. All the obvious checks proved fruitless so the relevant tracks etc. were visually examined using a magnifying glass. Pin 7 of the TBA 920Q sync separator/line generator chip (IC401) was found to have little solder around it: making this good restored normal operation.

D. C. Robinson, Stronsay, Orkney.

LED INDICATION FOR BOOSTERS

Many tube reactivator designs have been published in *Television* over the years, most of them based on the circuit using a 15W pygmy sign bulb first published in the sixties. Two comments: first, many tubes won't respond to the process unless the heater voltage is raised; secondly a pulsed method is quicker.

I use a treasured antique sold in the early days under the name Radar. Its heater supply has six outputs switchable 2-13V plus a four-way switch that boosts the heater voltages by up to 50 per cent. When I bought it the booster was useless: it languished in my loft until that first booster article was published in *Television*. It was then "recycled" and has been in use for many years. Few tubes

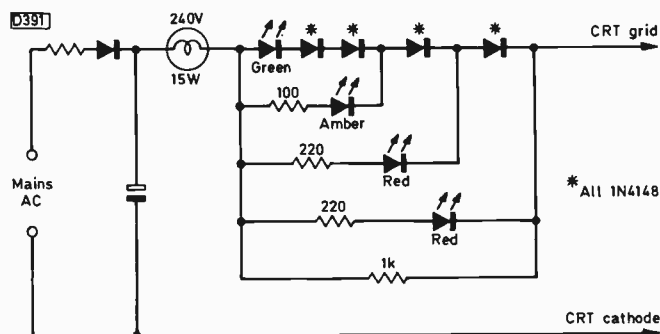


Fig. 1: Use of LEDs to give goodness indication with a tube reactivator.

have failed to respond and none have been spoilt, despite the dire warning given with some designs.

The reappearance of a circuit of this type in the May issue made me think about possible improvements. A LED goodness indicator seemed a good idea (see Fig. 1). This may appeal to engineers using a booster when the punter is present. Four 5mm LEDs, two red, one amber and one green, work in traffic light sequence, the green LED indicating good cathode emission. Check the LEDs before fitting: a red 5mm LED should draw 20-25mA when operated with a 2V supply, the other colours requiring a slightly higher voltage.

This is an inexpensive addition. I've used it with the design published in the April 1978 issue but it's suitable for use with any similar reactivator.

William Harrison
Windsor, Berks.

TEST CIRCUIT FOR THE COMMODORE 64

Alignment of the Commodore 64 microcomputer's cassette deck is made very difficult by the fact that it's powered from and controlled by the computer itself. If a load error is detected the computer stops the tape.

We've found that the easiest way to check the alignment is to use the test circuit shown in Fig. 2. If the circuit is made up on a small piece of tagstrip it's possible, with a bit of ingenuity, to make a plug connector to match the tape deck socket and connect the two with flexible leads. I used an old Siemens 365 daughter board to make my plug connector. The connections are 1 0V, 2 5V, 3 cassette motor, 4 cassette read – 5 and 6 are not used. The locating lug is between pins 2 and 3.

To use, all that's necessary is to plug the test circuit into the tape deck, insert an alignment tape and press play. The azimuth adjustment is then made for steady illumination of the LED. If a scope is available it can be used to monitor the test point where a continuous squarewave should be present.

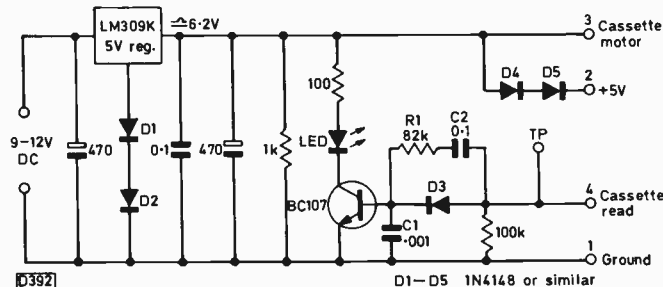


Fig. 2: Cassette deck test circuit for use with the Commodore 64 microcomputer. Any type of LED can be used.

The circuit's electronics are simple. An LM309K 5V regulator chip is used to provide a stable supply – since its earth pin is raised to 1.2V by diodes D1 and D2 the output is approximately 6.2V. This is used to power the deck motor. The deck's electronics require 5V which is obtained by using D4 and D5 to provide a 1.2V drop. The pulses coming from the deck are rectified and shaped by D3, C1, R1 and C2 and used to drive transistor Tr1 which in turn drives the LED. They are available for visual examination at the test point. When an azimuth tape is being played back there should be a square waveform with an even mark-space ratio at this point. If the azimuth is wrong either the mark-space ratio will change or dropouts will appear in the waveform. If alignment seems to be very critical the head is probably faulty. If the output waveform is noisy check whether the cassette motor is the cause by disconnecting it.

One further point. It's always worth making a final check that the deck loads, and especially saves, using a computer. We had a customer who brought in a six months old Sinclair machine with the complaint that it wouldn't save. In fact the machine hadn't saved a programme since the day it was made – the output coupling capacitor hadn't been fitted! Presumably it had spent the first six months of its life just playing games...

*Peter Richards,
Criccieth, Gwynedd.*

G8 CONVERGENCE PANELS

There were a couple of articles on the Philips G8 chassis in *Television* last year. Both mentioned the poor performance of the later (550 series) convergence panel compared with the more reliable, front mounted 520 series panel. Some time ago I bought a batch of ex-rental 550 series sets and noticed that one of them had been fitted with a 520 series convergence panel hung down and mounted on the chassis crosspiece. As the set was performing correctly with good convergence I've since then on many occasions used the older type panel to replace a later type panel. All the plugs and sockets match up and the only action required is to drill one extra hole to match the panel and fasten the extra wiring carefully in the harness clips on the existing chassis. I hope that this tip proves useful to other readers.

*P. Smith,
Hathersage, Sheffield.*

SPECTRUM ADD-ONS

Quite a lot on the Spectrum microcomputer has appeared in *Television* recently. Some add-ons can cause the computer to either crash or not work with various games. The Currah Microspeech and the Kempston interface are but two examples. Both of these can be successfully, easily and cheaply modified to work with all games however. First the Microspeech. Some games won't work because the game and the Microspeech try to occupy the same section of memory, so the computer crashes. The cure is to earth line A3: the Microspeech stays connected but the Spectrum ignores it. As this is a dead-ended device with no through connector most people who want to use more than one add-on will use some form of extender, the usual sort being a 56-way socket to fit the Spectrum's rear connector and two or more sockets on the end of a piece of ribbon cable. These extra sockets will require a printed circuit "back-to-back" to connect them to whatever accessory is being used. It's this piece of back-to-back that's

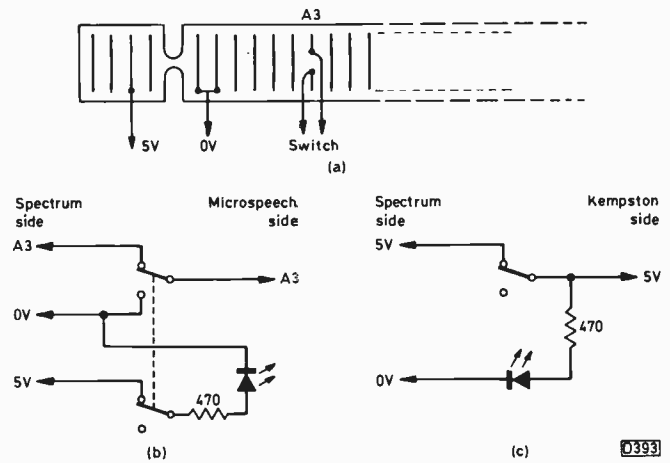


Fig. 3: Modifications for use with Spectrum add-ons.

modified. This has several advantages, the main ones being that modification can be done without connection to either the computer or the Microspeech, so that a careless solderer won't do any damage, and that neither the computer nor the Microspeech has to be dismantled so no guarantees are nullified.

Back to the Microspeech. Break the A3 line. Counting from the double-earth connections (taking these as one and two) at one side of the keyway A3 is the seventh – see Fig. 3(a). Fit a double-pole, two-way toggle switch with sufficient wire to enable it to be taped to the side of the Microspeech's case. Two poles are used – see Fig. 3(b) – so that one pole can be used for a LED to indicate on or off. The slider of one pole goes to the A3 line for the Microspeech, the fixed contacts going to earth and the A3 line from the Spectrum respectively. The other pole is used to connect a LED with a resistor of about 470Ω in series between the 5V line (the second edge connector from the keyway on the same side as the double earth) and 0V. Irrespective of whether the Microspeech is on or off the Spectrum sound will come from the TV set's speaker – and so sound a lot better than the Spectrum's own feeble beep.

The next device is the Kempston interface for joysticks. You'd think that games designers would take this into account as it has become an "industry standard" joystick interface, but no. The game "Chickin Chase" (their spelling, not mine!) will crash if the Kempston is connected. This modification – see Fig. 3(c) – is very simple. Just switch off the 5V supply to the interface and the Spectrum will ignore it. Although it's a bit late now the game "Ghostbusters" will, despite having a Kempston option in the menu, crash if the Kempston is connected – unless you moan to Activision who will replace the game with a Kempston compatible one (and also refund your postage if you ask nicely). To test the Kempston interface use the following short program:

```
10 PRINT IN 31;:PRINT " ";:PAUSE 25: GOTO 10
With the interface switched off the answer should be 255.
With it switched on you should get the following: up 8;
down 4; left 2; right 1; fire 16 – or combinations thereof.
```

I know that the alternative to these modifications is to keep unplugging the devices but I feel sure that the Spectrum's rear connector was not designed for constant plugging and unplugging. I hope that Amstrad, having taken over Sinclair's computer range, will repackage the 128K and 48K with a built-in joystick interface.

*Michael Harris,
Cheadle, Cheshire.*

VCR Clinic

Reports from Derek Snelling, Les Grogan, Steve Beeching, T. Eng., Mick Dutton and Philip Blundell, Eng. Tech.

Ferguson 3V29

On changing channels this machine would sometimes appear to drift off tune. Closer inspection however showed that the fault was more like a.g.c. instability. In addition the tuning was very critical and prone to smeary video, and the r.f. gain control wasn't working correctly. As the a.g.c. voltage to the tuner was correct we first tried a new tuner. This made no difference. The fault turned out to be due to the AN5111 i.f. chip. **D.S.**

Mitsubishi HS318

There was a rather unusual fault with this machine: the TV picture went low gain when the VCR was switched on, though the channels through the machine were fine. A faulty aerial booster can cause this sort of problem but it doesn't usually depend on whether the machine is switched on or not. A check on the supply to the booster/converter showed that instead of being 9V it was at 10-12V with the VCR off, falling when the machine was switched on and the load on the lines increased. A new 9V regulator cleared the fault. **D.S.**

Booster/converter Units

We've had four booster/converters fail recently, two in Toshiba V65Bs and two in Finlux VR1010s – all within a couple of miles of each other. Perhaps there's some environmental factor at work here. Like the Panasonics whose boosters would fail when there was a thunderstorm in the area. **D.S.**

Mitsubishi HS304

This machine wouldn't play because the capstan motor didn't rotate, though all other functions appeared to be in order. A check at pin 17 of IC4A0, the capstan reverse output, revealed that this was permanently high. Disconnecting the pin proved that the high was coming from elsewhere – it was traced to an inverter in IC4A2. Replacing this i.c. cured the problem. **D.S.**

Toshiba V65B

No play was the complaint with this machine. When play was selected the machine would lace up then after a few seconds it would unlace and stop. A quick check showed that the head drum wasn't rotating, though slight pressure on the plug and socket to the lower drum assembly would start it up. We stripped down the assembly and resoldered all the joints. This failed to produce a cure and no cracks could be found. A replacement lower drum assembly cured the fault. **D.S.**

Mitsubishi HS700

Here's a tip for anyone with one of these machines that has a broken camera socket. This item is available from Mitsubishi only if you order a complete Y/C board. The later Model HS710 uses a similar camera socket however – in fact it's a better quality, metal one. This is available as

part of a terminal assembly that's very reasonably priced. Simply remove the socket from the assembly and fit it as a direct replacement in the HS700. **D.S.**

Grundig VS180

The symptoms were no tape transport, with the winding motors running fast. This fault is indicative of a power supply line failure. Water was evident on the inside of the bottom plate however – corrosion too. Some water was found around the upper case edges but as it had been raining heavily when Andy brought the machine in we didn't worry too much. The power supply lines were all correct at the power supply edge connectors, but there were tide marks about and it was damp beneath the tuner – green with open-circuit, corroded print. It took about half a day to strip everything out, repair the print, relacquer and test.

As it was a rental machine I was concerned about where the water had come from. More to the point I kicked up merry hell with the customer for spilling water/gin/vodka or whatever into the machine. Denials all round. The wife didn't like flowers in the house and the VCR was kept within a cabinet, so it was a mystery where the water had come from. When the VCR was returned to the customer he found water inside his cabinet and inside the aerial connectors which had been plugged together in the absence of the VCR. The water was coming down through the cable, which had to be replaced. **S.B.**

Sony SLC7

The problem with this machine was that it wouldn't change channels after it had warmed up – the trouble was intermittent. It looked like a difficult fault and we approached it with trepidation. When the fault was present the machine wouldn't change channels and the programmable timer couldn't be set, though the clock could be. Panic set in! When a channel is selected the decoder chip IC1 on the tuning panel sets the binary conditions on lines ABCD. IC1 on the timer panel counts, and when its ABCD output back to the tuning panel matches the selected channel the count stops. Count start/stop is controlled by an AND gate in IC7 (pins 1/2/3). In the fault condition the output at pin 3 of IC7 was high, indicating count, but IC1 (timer panel) wasn't counting. Why? Because it was busy doing something else. One of its strobe inputs, pin 33, was active. This could be traced back to switch S20 (clear) which was faulty, with no spring return. It opened and closed when it felt like it, stopping the channel change. **S.B.**

Grundig 2 × 4 Super

This machine came in for a new on/off switch – the latching spring was missing. I was not prepared for what followed. After completing the switch repair a check was made and we found that the drum servo wasn't locking up. Better lock was obtained as the machine warmed up, but the drum motor would then suddenly slow down. Everything was checked and we found that the trouble

seemed to be associated with the comparator IC1501: a replacement made no difference however and for some reason output pin 13 would inexplicably go high, slowing the drum motor. Nothing was wrong with the inputs and nothing seemed to be amiss on the power panel. As a last resort agent 003-5, Grundig Pete, was contacted.

Pete said it was the power supply. Either C446 or C447 – or maybe both – had dried up. But you can't put just any capacitor in – it has to be a high-current PCB type, better still a direct Grundig replacement. Anyway replacements were fitted – and the problem remained. Pete was around like a shot. We found that there was about 0.5V peak-peak ripple across C447 – and at the chassis-connected negative pin! I didn't like this at all. Pete fitted a replacement power panel to prove that the cause of the trouble was on this panel, confirming that it was. So it was a case of narrowing down the source of a 32kHz ripple (it's a switch-mode power supply) that appeared to be everywhere on the faulty panel. It was Pete who discovered that the cause of the trouble was the 15V supply decoupler C451 (1,000 μ F) even though we had to put in a 470 μ F type temporarily until the correct type could be obtained. S.B.

JVC HR7200/Ferguson 3V29

No sound on E-E and recordings was due to D14 on the audio-video board being leaky. This diode forms part of the circuit used to mute the sound in the still and shuttle modes. L.G.

Hitachi VT8000

We've had a couple of faults recently on these machines. First no functions with the operate LED out was due to R054 (1.5k Ω) being open-circuit. This resistor biases the regulator transistor Q053. Secondly absence of E-E sound and video with a normal test signal was due to the not-PB 12V line being absent – ZD053 in the regulator circuit was short-circuit. L.G.

Sharp VC8581

Intermittent recording on one of these machines was traced to a defective HA11744NT1 video processor chip (IC401). A scope check revealed that the luminance was arriving at pin 20, but there was no f.m. oscillator signal at pin 12 – and thus no f.m. output to the video heads. L.G.

Sharp VC7750

It's not very often that you get an electrical fault on this model – most faults are mechanical. This one was dead due to an open-circuit Darlington transistor, Q908. A replacement was fitted but on switching on the supplies were found to be low and the chopper transformer was making a squealing noise. C920 had gone low in value. P.B.

Ferguson 3V32

This machine had a cassette inside. When this was played it looked as if the recording consisted of line tearing. An accompanying note said that the fault was intermittent and that when it occurred a noise came from within the machine. Sure enough after an hour or so of playing this tape a noise could be heard. So while it was still playing

the top was removed. The noise was coming from the area of the audio/control head. No it wasn't the head (as with the early Hitachis) but a wire rubbing against the tape! P.B.

JVC HR7200/Ferguson 3V29

Intermittently stops was the complaint with this one – every so often the capstan would stop, and it wasn't dry-joints around Q216 either! We found that the pause control line went high when the fault occurred. This comes from the mechacon board where Q17 had a dry-joint at its emitter. P.B.

Ferguson 3V35

There was no colour on playback or record. A check at test point TP402 revealed that the amplitude of the 625kHz signal was low. Voltage checks at the pins of the HA11741 colour signal processing chip were then carried out. The voltage at pin 15 was found to be low due to C433 (0.022 μ F) being short-circuit. Several other cases of no colour with these machines have been traced to filter BPF401 – resoldering its connections often provides a cure. P.B.

Hitachi VT9300

This machine would load but there was no tape rotation. We removed the top cover and noticed that the capstan wasn't moving. When we removed the bottom covers we found that the capstan motor wasn't running because its bearings had seized almost solid. Removing it, cleaning and oiling provided a cure. M.D.

Ferguson 3V24

This portable would intermittently go into the alarm mode, with the mode indicators flashing sequentially. This would sometimes happen when the machine was switched on from standby, or if rewind or fast forward was selected. Play was normal but when we tried to select picture search the machine went into the alarm mode and we couldn't get it back into play. The machine had to be unloaded by hand before we could get anything to work. Checks were carried out on the various sensor inputs to the microcomputer chip: eventually we found that the pinch solenoid switch S17 was intermittently sticking on. Retensioning this provided a cure. M.D.

Panasonic Clock Faults

The NV2000 seems to be prone to clock failure – we've changed four over the past few months for faults ranging from no display to alternating between 12- and 24-hour operation. Other Panasonic machines also suffer. We've had a couple of defective clock i.c.s in the NV333 – the symptom in both cases was no display. An NV366 came in with the same fault – no display. The 36V rail was found to be missing due to the 10 Ω safety resistor R7632 being open-circuit. When this was repaired there was no hours display and the clock wouldn't set. We were just about to order a chip when we noticed a deposit on the print. Further investigation revealed that the back-up battery had gone rotten and leaked down the panel. A careful clean up and a new battery cured the problem. M.D.

ECONOMIC DEVICES, PO BOX 228, TELFORD TF2 8QP

15/80H	3.30	2SA940	1.81	2SC535	0.79	AF180	0.55	BA656	0.39	BC580C	0.14	BDX63A	1.96	BFY2	0.27	BYX71-350	0.72
15/85R	3.30	2SA940-2	2.14	2SC536	0.41	AF181	0.53	BA7100	10.85	BC635	0.36	BDY20	1.21	BFY79	0.49	BYX94	0.14
16039	0.79	2SA950	0.72	2SC537	0.54	AF186	0.53	BA841A	16.72	BC636	0.42	BDY81	1.10	BFY90	0.61	BYX56	1.20
16181	1.04	2SA951	1.26	2SC605L	1.16	AF239	0.43	BA843	3.96	BC637	0.24	BF115	0.48	BLY49	2.20	BZ530C30	1.86
16182	1.04	2SA966-Y	1.16	2SC620	1.46	AF279	0.88	BA854	5.76	BC639	0.24	BF117	0.66	BR00	0.22	BZ98 RANGE	0.10
16334	0.98	2SA999	1.16	2SC643A	1.54	AL113	1.36	BAV18	1.36	BC640	0.24	BF118	0.67	BR01	0.75	BZ61 RANGE	0.18
16335	0.94	2SB774	1.15	2SC668	0.67	AN115	3.98	BAV19	0.11	BC879	0.39	BF121	0.25	BR03	1.26	BZ79 RANGE	0.10
16446	0.98	2SB185	1.13	2SC681	4.40	AN155	1.89	BAV20	0.31	BC880	0.31	BF123	0.13	BR03	0.13	C106D	0.46
16600	1.38	2SB375	3.87	2SC682	1.88	AN206	2.58	BAV21	0.34	BCX34	0.40	BF127	0.13	BRC116	0.67	C106M	0.76
16802	1.27	2SB400	0.40	2SC684	1.65	AN208	3.55	BAW62	0.19	BCY70	0.30	BF137	0.23	BRC300	2.01	C1129	0.58
17052	5.61	2SB405	1.03	2SC693	0.63	AN210	2.28	BAX12	0.44	BCY71	0.21	BF153	0.58	BRC5296	0.77	CA3046	2.06
17053	5.61	2SB407	3.24	2SC710	0.69	AN211	3.25	BAX13	0.11	BCY72	0.20	BF154	0.26	BRC6109	0.83	CA3089	0.83
17074	9.30	2SB449B	6.93	2SC711A	0.50	AN214Q	2.75	BAX16	0.11	BD115	0.46	BF157	0.33	BRC82	1.06	CA3090AQ	3.25
17089	5.35	2SB511	2.50	2SC717	1.28	AN231	14.65	BC107	0.13	BD116	0.46	BF158	0.18	BRC83	2.19	CA3131EM	2.20
17127	3.51	2SB54	1.39	2SC734	1.43	AN234	5.92	BC107A	0.11	BD124	1.31	BF159	0.18	BRC84	2.08	CA3131EM	3.12
17376	1.58	2SB546	3.75	2SC761-Y	0.95	AN236	3.78	BC107B	0.18	BD124P+KIT	0.69	BF160	0.31	BRX44	0.81	CBF16848N-071	1.56
17523	1.32	2SB56	2.80	2SC783	3.98	AN239	6.95	BC108	0.15	BD131	0.42	BF167	0.38	BRX49	0.53	CD4001	0.38
17524	1.32	2SB618A	2.22	2SC790Y	1.64	AN240P	1.52	BC108B	0.15	BD132	0.42	BF173	0.34	BRX39	0.69	CD4002	0.27
1N4001	0.06	2SB631	3.25	2SC828	0.28	AN241	1.71	BC109	0.12	BD133	0.53	BF177	0.35	BSS38	0.87	CD4008	1.35
1N4002	0.06	2SB643	0.54	2SC867A	3.05	AN245	4.49	BC109B	0.15	BD135	0.36	BF178	0.40	BSTBD140G	5.25	CD4011	0.29
1N4003	0.06	2SB669	3.67	2SC876	0.96	AN253	2.97	BC109C	0.12	BD136	0.26	BF179	0.36	BSTC0246	7.25	CD4012	0.24
1N4004	0.06	2SB681	3.96	2SC930	0.54	AN260	3.85	BC113	0.14	BD137	0.36	BF180	0.36	BSTC0233	7.25	CD4013	0.47
1N4005	0.08	2SB695	1.98	2SC935	4.13	AN262	1.98	BC119	0.26	BD138	0.46	BF181	0.32	BSTCC0143	3.07	CD4016	0.46
1N4006	0.08	2SB75	1.04	2SC936	8.66	AN272	7.92	BC126	0.30	BD139	0.34	BF182	0.34	BSTD1043	2.85	CD4017	0.82
1N4007	0.07	2SB774	0.65	2SC940	4.68	AN281	6.65	BC132	0.14	BD140	0.37	BF183	0.38	BSTV57B	3.49	CD4020	1.23
1N4148	0.04	2SB819	0.89	2SD1128	2.60	AN295	5.52	BC135	0.14	BD144	1.70	BF184	0.43	BSW68	0.60	CD4021	0.39
1N4448	0.05	2SC1034	6.75	2SD1138	0.99	AN301	5.55	BC137	0.18	BD150	1.25	BF185	0.39	BSX19	0.34	CD4023	0.28
1N5401	0.14	2SC1050	5.06	2SD1273	1.25	AN302	3.99	BC138	0.34	BD157	0.69	BF194	0.14	BSX20	0.34	CD4025	0.64
1N5402	0.15	2SC1096	1.16	2SD1453	0.75	AN303	4.39	BC139	0.28	BD160	1.60	BF195	0.14	BSY52	0.51	CD4028	0.84
1N5403	0.16	2SC1104	3.96	2SD152K	2.64	AN305	9.47	BC140	0.45	BD163	0.71	BF196	0.17	BSY79	0.51	CD4040B	0.85
1N5404	0.15	2SC1106	4.54	2SD198	3.87	AN315	2.46	BC141	0.34	BD165	0.62	BF197	0.16	BT100A	1.61	CD4047	1.06
1N5408	0.35	2SC1114	6.75	2SD234	0.49	AN316	5.53	BC142	0.39	BD166	0.62	BF198	0.17	BT106	1.55	CD4049	0.46
1N914	0.04	2SC1116	1.95	2SD235	0.60	AN318	6.27	BC143	0.33	BD168	0.73	BF199	0.17	BT108	1.45	CD4052	0.75
1R3403	5.00	2SC1124	4.26	2SD24	2.29	AN320	5.47	BC147	0.08	BD175	0.60	BF200	0.37	BT119	1.76	CD4066	0.38
1S1565	0.20	2SC1129	0.34	2SD257	2.94	AN321	2.25	BC148A	0.10	BD179	0.49	BF218	0.36	BT120	2.17	CD4069	0.29
1S44	0.10	2SC1131	0.50	2SD292	2.59	AN322	5.85	BC148B	0.13	BD181	0.98	BF224	0.17	BT121	2.48	CD4070	0.66
1S5012A	0.81	2SC1158	3.33	2SD313	2.59	AN331	4.59	BC148C	0.11	BD182	0.98	BF237	0.65	BT123	1.98	CD4081	0.35
1S921	0.10	2SC1162	1.05	2SD325D	1.95	AN337	5.37	BC149	0.11	BD183	0.99	BF240	0.17	TBA970	3.06	CD4093	0.72
2N1303	0.38	2SC1172	2.22	2SD348	16.13	AN340P	1.17	BC149B	0.13	BD184	1.21	BF241	0.17	BT151-800R	1.15	CD4511	1.10
2N2219A	0.40	2SC1195	3.26	2SD350	5.20	AN355	5.98	BC153	0.14	BD187	0.97	BF245	0.50	BT16018	2.42	CD4528	2.04
2N2222	0.38	2SC1212A	0.97	2SD350A	2.80	AN362	1.75	BC154	0.14	BD189	0.69	BF245A	0.37	BT18124	4.89	CD4556	3.47
2N2646	0.80	2SC1213	1.09	2SD353	7.50	AN370	3.95	BC159	0.36	BD190	0.69	BF245B	0.49	B0	2.48	CRO2AM-8	1.55
2N2904	0.36	2SC1226	1.46	2SD389	2.41	AN5010	5.70	BC160	0.40	BD201	0.53	BF246A	2.52	BU108	1.50	CV12E	3.07
2N2905	0.43	2SC1293	0.90	2SD401	2.55	AN5111	2.92	BC161	0.28	BD202	0.60	BF255	0.20	BU109	2.25	COX95D	3.14
2N2906	0.38	2SC1306	1.96	2SD414	1.98	AN5120N	4.50	BC168	0.36	BD203	0.50	BF256	0.28	BU110	5.69	CX104	9.64
2N2926	0.15	2SC1316	4.14	2SD471	2.13	AN5132	4.39	BC169C	0.16	BD204	0.59	BF256LB	0.42	BU111Y	4.16	CX108	10.50
2N3053	0.27	2SC1317	0.87	2SD560	2.95	AN5250	2.89	BC170	0.16	BD207	1.79	BF256LC	0.42	BU125	2.68	CX109	7.86
2N3054	0.99	2SC1364	4.09	2SD588A	1.99	AN5435	3.08	BC171	0.11	BD208	1.23	BF257	0.34	BU126	1.55	CX130	8.76
2N3055	0.61	2SC1383	1.20	2SD600	3.25	AN5610	7.43	BC172	0.13	BD222	0.49	BF258	0.36	BU137	9.25	CX134	11.04
2N3442	1.56	2SC1391	2.45	2SD601R	0.65	AN5612	3.81	BC172B	0.27	BD225	0.49	BF259	0.34	BU205	1.08	CX136	11.49
2N3702	0.14	2SC1398	0.94	2SD613	1.03	AN5613	3.80	BC173	0.17	BD228	0.63	BF262	0.57	BU206	1.27	CX139	11.83
2N3703	0.14	2SC1413A	3.05	2SD621	12.85	AN5630	3.95	BC174B	0.27	BD229	1.05	BF263	0.57	BU207	1.65	CX157	4.84
2N3705	0.16	2SC1446	1.25	2SD636	0.55	AN5701N	1.66	BC177	0.20	BD232	0.50	BF271	0.34	BU208	1.12	CX158	4.10
2N3706	0.14	2SC1447	2.07	2SD639-R	0.85	AN6250	2.95	BC178	0.26	BD234	0.42	BF273	0.20	BU208/02	1.97	CX177	6.75
2N3707	0.16	2SC1475	0.37	2SD655	0.98	AN6300	7.80	BC179	0.26	BD237	0.47	BF274	0.20	BU208A	1.12	CX187	5.26
2N3711	0.11	2SC1505	1.00	2SD657	2.85	AN6310	8.74	BC182	0.09	BD238	0.39	BF324	0.23	BU208D	1.95	CX755	12.95
2N3771	2.04	2SC1514	1.41	2SD661A	0.80	AN6320N	4.28	BC182L	0.10	BD239	0.46	BF336	0.33	BU209	1.93	CX885A	6.85
2N3772	1.71	2SC1573Q	1.25	2SD731	2.46	AN6340	6.46	BC182LB	0.14	BD240	0.37	BF337	0.40	BU226	2.56	DECI	2.20
2N3773	2.29	2SC1578	8.74	2SD773	0.33	AN6341	2.40	BC183L	0.11	BD241	0.39	BF338	0.44	BU326	2.20	DEC2	2.20
2N3819	0.42	2SC1583	1.17	2SD811	5.54	AN6342	1.61	BC183LB	0.26	BD242	0.39	BF355	0.49	BU326A	2.00	DS3486N	4.33
2N3823	1.17	2SC1617	3.89	2SD823	1.98	AN6363	16.00	BC184	0.13	BD243A	0.37	BF362	0.66	BU326S	2.20	DS3487N	4.30
2N3904	0.62	2SC675	1.01	2SD837	1.20	AN6371	9.24	BC184L	0.14	BD243C	0.60	BF363	0.60	BU406	1.49	E1222	0.40
2N3908	0.62	2SC1678	1.98	2SD841	3.65	AN6387	7.95	BC184LB	0.26	BD244	0.51	BF371	0.50	BU406D	1.79	E5024	0.28
2N4101	1.33	2SC1741	1.25	2SD856	2.25	AN6531	1.95	BC186	0.27	BD244C	0.79	BF391	0.25	BU407	0.82	E5386	0.25
2N4240	3.30	2SC1810	1.76	2SD857Q	1.84	AN6551	1.35	BC187	0.28	BD245C	0.99	BF417	0.84	BU407D	1.09	E9003	0.46
2N4444	1.73	2SC1815	0.60	2SD882	0.68	AN6552	0.68	BC204	0.16	BD246C	0.89	BF418	1.87	BU412	1.95	E9005	0.50
2N5293	0.50	2SC1826	0.65	2SD894	1.50	AN6610	2.40	BC207	0.14	BD253	1.05	BF422	0.29	BU426A	1.67	ESM310BP	4.15
2N5294	0.50	2SC1829	2.22	2SD898	5.46	AN6677	6.60	BC212	0.11	BD278A	0.50	BF423	0.52	BU500	1.95	FPO500	5.78
2N5296	0.49	2SC1875	5.19	2SK105H	2.15	AN7111	1.45	BC212B	0.26	BD317	2.60	BF450	0.35	BU508A	1.89	GC274	1.65
2N5297	0.50	2SC1881K	2.98	2SK152	2.95	AN7114E	5.94	BC213L	0.10	BD318	2.05	BF451	0.29	BU509	5.80	GQ343	4.95
2N5298	0.61	2SC1893	3.02	2SK34	0.76	AN7115	1.75	BC213BL	0.15	BD375	0.						

TEL 0902 712083 TELEX 338490

HA1374	4.80	LR3419	9.37	NE565N	1.33	SKE4F2/08	1.24	STK3042	11.05	TA7312P	2.45	TD62105P	2.50	TDA3560	5.25	TUA2000	8.98
HA1377	2.95	LR3471	9.27	NE645BN	3.65	SKE4F2/06	1.85	STK3044	5.75	TA7313AP	1.50	TD62106P	2.50	TDA3571Q	2.97	TV106	1.76
HA1389R	3.06	LU1141	7.37	NP1106	1.20	SKE4F2/10	0.24	STK4019	4.50	TA7314	5.94	TD62706P	4.50	TDA3576	7.09	TY60108	2.97
HA1389	2.39	LU52012	5.95	OA202	0.11	SKE4G2/02	0.96	STK430	11.75	TA7323P	3.15	TD61001B	2.31	TDA3590	5.79	U06G	1.14
HA1392	3.90	LU52011	4.95	OA47	0.14	SKE5F3/10	1.60	STK433	5.45	TA7325P	1.15	TDA1003A	2.25	TDA3591	6.45	ULN2204	11.45
HA1394	3.76	LU03112	12.37	OA91	0.09	SKS1/10	2.15	STK4332	8.25	TA7339P	1.35	TDA1005A	2.12	TDA3650	7.50	UPA33C	4.94
HA1397	3.95	M193	12.75	OA95	0.09	SL1310	0.14	STK435	5.94	TA7340P	5.06	TDA1006A	2.22	TDA3652	5.44	UPC1003	4.95
HA1398	2.98	M21C	1.00	OC28	2.95	SL1430T	2.15	STK4352	12.25	TA7607AP	13.90	TDA1010AP	4.25	TDA3651AQ	2.96	UPC1009C	6.32
HA1406	1.63	M23C	0.83	OC29	2.15	SL414	3.69	STK437	7.21	TA7609	3.28	TDA1011	4.98	TDA3651	3.30	UPC1025H	2.90
HA1452	1.53	M283	9.15	OC36	1.28	SL432A	2.44	STK4372	7.80	TA7611AP	4.80	TDA1010	1.15	TDA3651A	2.96	UPC1026C	1.24
HBF4030AF	2.48	M5115P	5.24	OC44	0.35	SL439	3.89	STK4372	3.85	TA7616P	5.25	TDA1011A	5.25	TDA3950	4.68	UPC1028H	2.00
HD14538	2.07	M51203L	6.35	OC45	0.18	SL471	4.78	STK439	8.31	TA7622AP	8.94	TDA1028	2.45	TDA4050B	3.95	UPC1020H	2.77
HD38702-A2	7.45	M51231P	3.15	OC72	0.44	SL480	4.14	STK441	11.28	TA7628P	5.62	TDA1034B	2.42	TDA4280	7.20	UPC1020H	0.62
HD38750A3	8.71	M51231P	3.15	OC75	0.44	SL490	2.37	STK443	10.29	TA7629P	7.50	TDA1035S	2.95	TDA4290	4.47	UPC1042C	8.95
HD38750A-7	10.25	M5134-9341	4.13	ON236	1.06	SL901B	1.06	SL901B	13.45	TA7630P	2.98	TDA1035T	2.56	TDA4400	2.27	UPC1025H	2.96
HD3880A50	14.09	M51353P	5.25	ON782	1.95	SL918A	9.97	STK460	14.83	TA7640AP	1.19	TDA1037	1.98	TDA4420	5.01	UPC1158	5.84
HD44801A05	18.25	M51381P	4.50	PT6042	2.45	SN16861AN0	4.95	STK461	9.68	TA7672P	1.75	TDA10370	2.05	TDA4422	8.32	UPC1156H	5.40
HEF4001BP	0.57	M51393AP	7.78	PT8504	2.45	SN16862AN	2.98	STK463	11.53	TA7676P	2.61	TDA1044	4.62	TDA4427S	9.00	UPC1182H	1.82
HIS1010	6.50	M51394P	11.97	R1038	2.19	SN18966AN	10.25	STK466	11.77	TA7726P	10.25	TDA1047	2.10	TDA4431	2.27	UPC1186H	1.40
HIS1004	9.00	M5142P	5.49	R1039	2.19	SN29717N	7.19	STK4833	16.95	TAA320A	1.27	TDA1058B	0.80	TDA4440	4.87	UPC1181H	1.25
HIS1002	6.50	M5144P	4.25	R2008B	1.33	SN29716N	3.61	STK501	6.32	TAA350A	0.80	TDA1054M	1.21	TDA4442	2.85	UPC1184H	1.94
HM6231	9.81	M51513L	2.95	R2009	1.98	SN29715N	6.04	STK502	5.74	TAA570	1.74	TDA1060	2.60	TDA4500	7.30	UPC1188	6.95
HM6232	8.89	M51515BL	3.23	R2010B	1.33	SN29722AN	11.95	STK5314	9.48	TAA621AX1	2.65	TDA1062	3.25	TDA4600	2.84	UPC1232C	0.99
HM6251	5.70	M51517	3.71	R2010B	1.33	SN29723AN	7.85	STK5370	3.95	TAA621A12	2.14	TDA1151	1.22	TDA4610	4.80	UPC1212C	1.72
HM7103	2.46	M5192L	2.20	R2019	1.33	SN29764AN	1.36	STK7216	12.67	TAA661B	2.62	TDA1170S	2.25	TDA4620	4.78	UPC1225H	3.25
HM9032	3.22	M5194AP	5.74	R2257	3.71	SN29770B	4.98	STK772	6.95	TAA691	8.58	TDA1190	3.96	TDA4630	2.60	UPC1230	7.24
HM9012	3.24	M5231L	1.93	R2265	1.49	SN29772B	4.91	STK772B	4.91	TAA700	4.87	TDA1200	3.50	TDA4640	2.25	UPC1238	2.98
HM9015	3.24	M5274P	1.33	R2305	1.18	SN29771B	4.93	STR4090	11.75	TAA830	7.05	TDA1200	3.88	TDA4720S	3.45	UPC1263	3.45
HT4207	17.16	M54532P	2.15	R2322	0.59	SN29791N	1.67	STR441	6.50	TAA970	2.83	TDA1235	3.00	TDA4727S	2.27	UPC1277H	5.85
HT4208	18.25	M54544L	4.75	R2323	0.76	SN29798N	5.56	STR451	4.95	TAA970	2.52	TDA1236	3.76	TDA4903	3.15	UPC1278H	4.85
IN5401	0.11	M58478P	6.75	R2354A	2.01	SN2709	0.44	STR453	7.16	TAA110	0.73	TDA1270	3.76	TDA9403	2.92	UPC1351C	1.81
IN2403	4.25	M58485P	10.74	R2354B	2.01	SN7400N	0.34	STR453	8.50	TAA110	1.06	TDA1327A	1.33	TDA9513	5.44	UPC1350C	1.40
IR2C05	4.25	MA05	1.07	R2443	0.88	SN7401N	0.36	STR6020	8.31	TAA120AS	1.24	TDA1412	1.05	TDB1035	6.68	UPC1353	7.85
IR3P06	2.25	MA8001	0.82	R2461	1.50	SN7402N	0.96	STR6020	8.31	TBA120S8	1.05	TDA1420	1.56	TDE1081	6.61	UPC1355C	2.13
IR3P08	4.95	MA8003	1.16	R2540	2.31	SN7404N	0.24	T6035V	0.73	TBA120T	0.95	TDA1440	3.15	TE626	1.49	UPC1363	4.20
IR94558	6.25	MB3705	1.98	R2540X	3.30	SN7408N	0.27	T6036	0.63	TBA120U	2.50	TDA1470P	4.26	TEA1002	3.47	UPC1362	7.75
IS751	0.18	MB3712	1.05	R2615	0.67	SN7410N	0.27	T6037	2.11	TBA120A	1.05	TDA1470P	4.15	TEA1009	1.86	UPC1367	6.98
ITT425	2.85	MB3713	1.69	RC1A16029	2.01	SN74121	1.60	T6044V	0.97	TBA120A	2.03	TDA1506	7.45	TEA1014	3.15	UPC1366	7.25
I200303E	5.37	MC13002	3.25	RC1A16800	1.38	SN74131N	0.67	T6045	1.25	TBA1440	1.62	TDA1510	5.20	TEA1020SP	8.21	UPC1366	4.51
I200202E	5.53	MC13002	3.25	RC1A16800	1.38	SN74141N	2.85	T6049	1.40	TBA1440G	5.20	TDA1512	2.96	TIC106C	0.61	UPC1378H	4.25
K1749P	3.46	MC1310P	2.25	RC1A17074	6.60	SN74151AN	1.51	T6052V	0.87	TBA1441	1.75	TDA1515	16.60	TIC106M	0.77	UPC141C	3.75
KA2101	2.92	MC1327P	1.33	RC1A17376	1.58	SN74154AN	1.27	T6058	0.59	TBA1441	1.62	TDA1670	4.15	TIC116Y10M	2.07	UPC1458	8.66
KC581C	3.32	MC1330P	1.69	RC1A17524	0.83	SN74190	2.00	T6059	0.65	TBA1441	1.10	TDA1770	6.76	TIC4	0.72	UPC151C	2.96
KC582C	6.97	MC1350P	1.61	RC1A17523	0.83	SN7420N	0.34	T9003V	1.25	TBA1440G	0.80	TDA1700	1.65	TIC4	0.72	UPC2002	1.48
KC583C	5.94	MC1351P	3.95	RC1A2060	2.00	SN7430	0.49	T9005V	2.39	TBA1440G	0.80	TDA1905	1.65	TIC4	0.72	UPC2002	1.48
L200CV	1.58	MC1352P	2.50	RGP01-15	0.70	SN7440N	0.27	T9011V	2.48	TBA1440	0.80	TDA1905	1.65	TIC4	0.72	UPC300C	2.51
LA1201	1.56	MC1357P	1.15	RGP10	0.50	SN7472	1.54	T9013V	2.98	TBA1440	0.80	TDA1908	1.97	TIC4	0.72	UPC324C	4.70
LA1210	2.87	MC1358P	2.15	RGP30M	0.59	SN7474N	0.44	T9014V	7.60	TBA1440	0.80	TDA1940	2.45	TIP210	1.06	UPC324C	4.94
LA1230	2.87	MC14001	2.40	RT402	1.58	SN7490AN	0.93	T9016	1.02	TBA1440	0.80	TDA1940	2.45	TIP210	1.06	UPC324C	4.94
LA1320	2.87	MC14001	2.40	RT402	1.58	SN7490AN	0.93	T9016	1.02	TBA1440	0.80	TDA1940	2.45	TIP210	1.06	UPC324C	4.94
LA1352	1.75	MC14013	0.41	RT905A	2.38	SN74LS26N	0.53	T9019W	1.98	TBA1440	0.80	TDA1940	2.45	TIP210	1.06	UPC324C	4.94
LA1357N	11.07	MC14493P	3.44	S1299	5.74	SN76001N	1.65	T9034V	1.38	TBA1440	0.80	TDA1940	2.45	TIP210	1.06	UPC324C	4.94
LA1363	7.02	MC14493P	3.44	S1299	5.74	SN76001N	1.65	T9034V	1.38	TBA1440	0.80	TDA1940	2.45	TIP210	1.06	UPC324C	4.94
LA1364	3.25	MC14493P	3.44	S1299	5.74	SN76001N	1.65	T9034V	1.38	TBA1440	0.80	TDA1940	2.45	TIP210	1.06	UPC324C	4.94
LA1365J	3.44	MC14510BAL	3.75	S2802D	2.07	SN76023N	5.15	T9051	7.15	TBA1440	0.80	TDA1940	2.45	TIP210	1.06	UPC324C	4.94
LA1385	1.94	MC14511BCP	1.10	S2802	5.54	SN76023ND	3.96	T9054V	1.45	TBA1440	0.80	TDA1940	2.45	TIP210	1.06	UPC324C	4.94
LA1387	7.60	MC14528BCP	2.70	S2818	3.47	SN76033N	4.15	T9057V	0.70	TBA1440	0.80	TDA1940	2.45	TIP210	1.06	UPC324C	4.94
LA13155	1.25	MC1712	3.08	S3702S	6.15	SN76110N	0.90	T9062V	0.49	TBA1440	0.80	TDA1940	2.45	TIP210	1.06	UPC324C	4.94
LA3301	1.63	MC5192	10.89	S400V	1.61	SN76115AN	1.91	T9064	1.61	TBA1440	0.80	TDA1940	2.45	TIP210	1.06	UPC324C	4.94
LA3350	1.45	MC7724CP	3.18	S6080B	8.80	SN76227N	1.33	TA7027	4.80	TBA1440	0.80	TDA1940	2.45	TIP210	1.06	UPC324C	4.94
LA3361	1.23	MC7818C	2.18	S6080B	5.17	SN76226DN	1.98	TA7050	1.74	TBA1440	0.80	TDA1940	2.45	TIP210	1.06	UPC324C	4.94
LA3365	3.98	MCR1007	1.65	SAA1006	1.75	SN76228N	3.27	TA7051	1.74	TBA1440	0.80	TDA1940	2.45	TIP210	1.06	UPC324C	4.94
LA3390	4.25	MCR106-5/6	0.95	SAA1020	4.78	SN76242	8.95	TA7054	2.55	TBA1440	0.80	TDA1940	2.45	TIP210	1.06	UPC324C	4.94
LA4030P	3.20	MCR207	2.28	SAA1025	4.40	SN76243	5.23	TA7060AP	0.71	TBA1440	0.80	TDA1940	2.45	TIP210	1.06	UPC324C	4.94
LA4031P	3.20	ME0402	0.17	SAA1024	2.81	SN76296	2.96	TA7061AP	1.27	TBA1440	0.80	TDA1940	2.45	TIP210	1.06	UPC324C	4.94
LA4032P	2.35	ME0404/2	0.47	SAA1075	6.25	SN76533N	2.47	TA7069	1.13	TBA1440	0.80	TDA1940	2.45	TIP210	1.06	UPC324C	4.94
LA4100	1.25	ME0411	0.28	SAA1121	5.14	SN76532N	2.95	TA7070P	3.83	TBA1440	0.80	TDA1940	2.45	TIP210	1.06	UPC324C	4.94
LA4101	1.30	ME6002	0.26	SAA1124	3.25	SN76545N	4.87	TA7072P	2.57	TBA1440	0.80	TDA1940	2.45	TIP210	1.06	UPC324C	4.94
LA4102	2.81	ME6102	0.26	SAA1130	4.59	SN76546N	4.87	TA7073P	5.86	TBA1440	0.80	T					

Modern Receiver Circuitry

Part 4: Line Output Stage Operation

J. LeJeune

The line scan and e.h.t. generator sections of a TV set have been linked since the early days of television, though many sets produced in the thirties and forties derived the e.h.t. from a mains transformer. This was a dangerous arrangement and had to be respected by the engineers of the day. The danger was reduced when the e.h.t. came to be produced by rectification of the line flyback pulse, though contact with the 10kV or so produced by early flyback e.h.t. systems was still a very unpleasant matter – and it's the same today. The other bonus of flyback e.h.t. is greater efficiency. This is also true of the technique of using an efficiency diode to recover the flyback energy to contribute to the scan. In older sets the line output transformer did what its title suggests, driving the scan coils via a secondary tap. The component that goes under the same title today acts mainly as a feed choke between the h.t. supply and the line output transistor.

Before we consider the line output stage it's as well to make clear that although the screen is scanned from the left-hand side to the right-hand side, with a rapid flyback to the left-hand side to start the following line, the scanning spot's rest position is at the centre of the screen. This is the position where the current flowing in the scan coils is zero.

Basic Circuit

The basic elements of a modern transistor line output stage are shown in Fig. 1. Inductance L_y represents the scan coils which are connected in series with capacitor C_s . The latter is commonly referred to as the scan-correction capacitor or d.c. blocking capacitor: both terms are correct but the capacitor does more than this, as we shall see. T_l is the line output transformer, Q the line output transistor, D is the efficiency diode and C_t provides flyback tuning.

With transistor Q switched off capacitor C_s will be charged from the h.t. rail via T_l and L_y . When C_s has fully charged no current will flow in the scan coils and the spot will rest at the centre of the screen. To move the spot across to the right Q is switched on, discharging C_s via L_y . The transference of energy from C_s to L_y is what shifts the spot to the right-hand side. At this point Q is switched off to initiate the flyback. C_t , which had previously been short-circuited by Q , is now rapidly charged by the energy stored in L_y . The current flow is reversed, with the result that the spot moves rapidly from the right-hand side to the centre rest position. We want it back at the left-hand side of course, and since C_t and L_y form an oscillatory circuit this is precisely what we get from the second part of the half-cycle of oscillation that occurs when Q is switched off. During the flyback, a positive-going voltage pulse is produced at the junction of C_t and C_s . The second half-cycle of oscillation would produce a negative-going pulse at this point. The efficiency diode D is then forward biased, damping the tuned circuit C_t/L_y . The resultant decaying current flow moves the spot back from the left-hand side towards the centre of the screen.

During the forward scan, either D or Q is conductive. The charge on C_s is replenished during the flyback period,

when both Q and D are off. C_s is in series with C_t but has little effect on the flyback action since its value is forty to fifty times that of C_t . The value of the latter capacitor is chosen so that it will receive and return all the energy stored in L_y during the $12\mu\text{sec}$ allowed for the flyback. D remains conductive for about the first 45 per cent of the forward scan, after which Q is switched on. In some designs the line output transistor's collector-base junction provides the efficiency diode action.

Looked at another way, L_y is made to resonate at two widely different frequencies – see Fig. 2. The forward scan is really a portion of a low-frequency sinewave ring produced by C_s and L_y . Since the value of C_s is large the frequency is low, probably just under half the line scan frequency. The portion of scan achieved by this action is shown between A and C in Fig. 2. At C the line output transistor is switched off, D is already off and C_t appears in series with C_s . C_t and L_y then provide a half-cycle of oscillation at a much higher frequency to produce the flyback. Switching between the two resonant frequencies is provided by D and Q . Flyback tuning is generally at an harmonic of the line scan frequency, up to the seventh.

Flyback EHT

During all this action T_l plays the part of a feed choke, but more can be got from it. With D or Q conducting, the full h.t. appears across T_l 's primary winding. Current flows in the primary, causing a build-up of magnetic flux in the transformer's core. When Q is switched off to start the flyback the field rapidly collapses, producing a large back-e.m.f. in the primary and any secondary windings. By using a secondary winding with many more turns than the primary winding a useful e.h.t. voltage with adequate current for the c.r.t. is generated. The value of the e.h.t. voltage produced in this way depends on the flyback time. Thus if the flyback time varies for any reason the e.h.t. will also change. Returning to Fig. 1, diode G rectifies the flyback pulse produced across the secondary winding, charging the capacitance formed by the Aquadag coatings on the inside and outside of the c.r.t. bowl (with the glass as the dielectric). In many respects the operation of a flyback e.h.t. generator is that of a chopper circuit without any stabilisation measures.

Raster Correction

Raster correction is required with most 110° tubes. The cause of the problem is illustrated in Fig. 3, which shows that uncorrected scanning produces a pincushion-shaped raster. When the electron beam is scanning the top or bottom line of the raster, A and C, the distance of the beam from the centre of the deflection coils to the screen is greater than when the beam is scanning the centre line B. With present-day 90° tubes the design of the yoke provides the compensation required, but this is more difficult with 110° tubes. Yokes for 110° tubes provide north-south correction but east-west correction must be done in the deflection circuit.

The fact that with a wide-angle tube the deflection centre is much closer to the screen than the screen radius

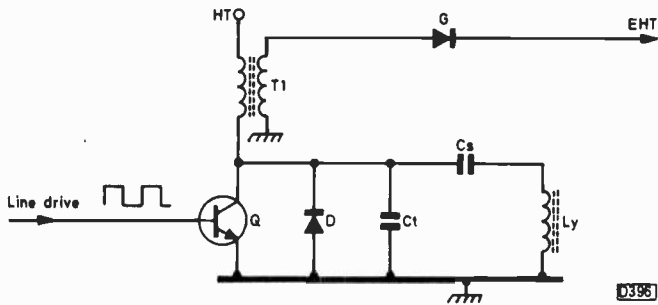


Fig. 1: Basic transistor line output stage circuit.

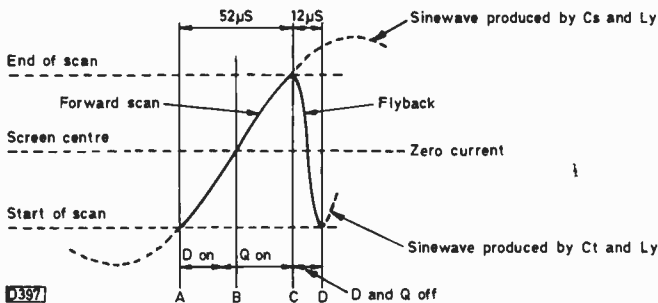


Fig. 2: One cycle of line scan, showing the two resonant frequencies for scan and flyback.

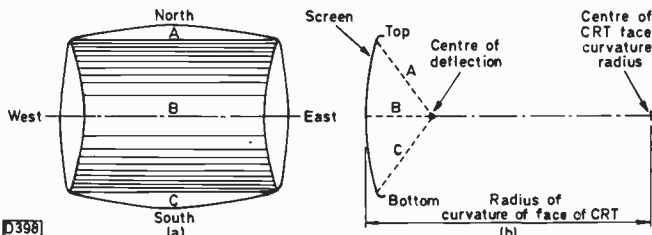


Fig. 3: Pincushion distortion with a wide-angle tube. (a) The effect on the display. (b) Showing how the distance from the deflection centre to the screen varies during the course of the scan.

also means that without correction the speed of the spot will vary as it scans the screen, i.e. the raster would be stretched towards the left- and right-hand sides. Correction for this is achieved by making the value of C_s less than that needed to give a linear scan waveform. This imposes curvature on the line scan ramp waveform – the effect is shown in Fig. 2.

Diode Modulator Circuit

Whilst scan-correction is simple to achieve the way in which east-west pincushion distortion is overcome is somewhat less easy to follow. We come now to the EW modulator. In essence this places a variable impedance in series with the scan coils to modulate the scan current. Fig. 4 shows a typical arrangement. One of the problems with adding an impedance in the line scan circuit is that the flyback time will be altered. This will in turn vary the e.h.t. and thus the raster size. The diode modulator is designed to prevent this.

If the circuit shown in Fig. 4 is compared with that shown in Fig. 1 it will be noticed that the line scan coils L_y are now returned to chassis via L_b and C_b . You'll recall that C_s is charged during the flyback time, when Q and D are off. This charge will now be shared by C_s and C_b , i.e. the charge on C_s is reduced. Q1 provides the variable element. When fully conductive C_b is shorted out: hence the charge on C_s is increased and so is the width. By

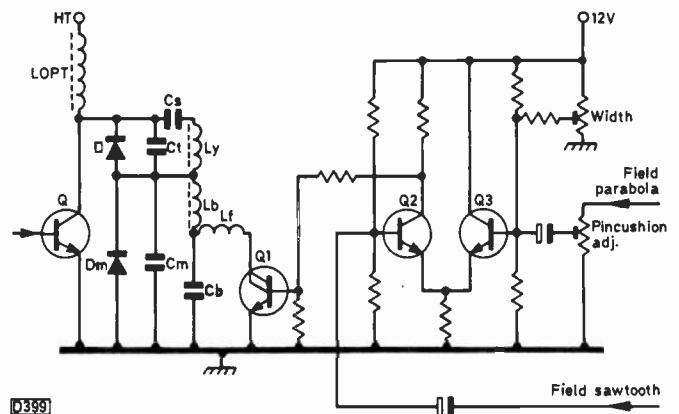


Fig. 4: Diode modulator circuit to provide EW correction.

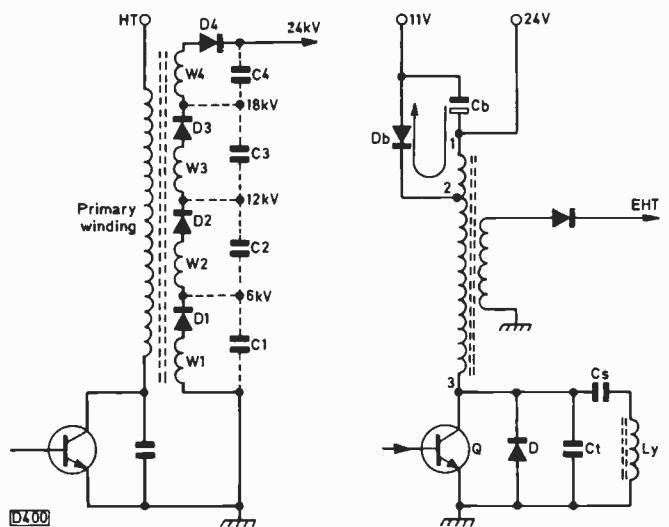


Fig. 5 (left): Diode-split e.h.t. generator.

Fig. 6 (right): Line output stage with boost diode D_b .

applying a variable field-frequency parabolic drive to the base of Q1 width correction throughout the field scan period is achieved. C_m is added in series with C_t and L_b in series with L_y to maintain the correct flyback tuning conditions. C_m and C_b have the same sort of relationship as C_t and C_s . L_f is simply a filter choke to protect Q1 against line-frequency transients.

The drive circuit is straightforward, consisting of the differential amplifier Q2/3. The width control sets the d.c. level at the base of Q3: since Q3/2/1 are d.c. coupled, moving the slider towards the 12V end increases the conduction of Q1 and thus the line scan amplitude. A field-frequency parabola is a.c. coupled to the base of Q3 via the pincushion control, which is adjusted to produce a raster with straight sides. A field-frequency sawtooth waveform is fed to the base of Q2 to counteract keystone distortion. Links to the h.t. line and to a point sensitive to beam current changes are often provided to stabilise the width.

Diode-split LOPT

Trouble-free e.h.t. generation is a feature of modern colour sets and is very largely due to the use of a line output transformer with a "diode-split" e.h.t. winding. Fig 5 shows the arrangement. The e.h.t. secondary is divided into four identical windings each of which delivers a quarter of the required e.h.t. voltage. Each winding has

its own built-in rectifier and is wound on a precision bobbin which controls the capacitance between the bottom ends of each of the four windings.

When the line flyback occurs the high pulse voltage developed by the primary winding causes each of the secondary sections W1-4 to produce a 6kV pulse. These pulses are rectified and added to give a final output of 24kV which, because of the good insulation, is available with greater safety – and also at a substantially lower output impedance than was available with previous methods of e.h.t. generation. The diodes are operated well within their ratings and the separate capacitors used in a tripler, with their attendant insulation problems, are done away with. Present day diode-split line output transformers go a step further in incorporating the first anode and focus controls within the transformer's encapsulation.

Circuit with Boost Diode

Transistor line output stages in colour sets are normally operated from a stabilised h.t. supply of around 120V. With a mains-battery monochrome portable the main stabilised supply rail is only around 11V. It's desirable to

operate the line output stage at a higher voltage than this and the incorporation of a boost diode and capacitor will provide an effective supply of around 24V which can also be used in other parts of the set. The boost technique was originally developed for valve receivers, where a single diode acted as both the boost and efficiency diode, providing energy recovery to contribute to the scan and a supply of up to 1kV for the output stage and other purposes.

Fig. 6 shows the type of circuit generally used in monochrome portables. D is the efficiency diode and Db the boost diode. During the forward scan either D or Q is conductive and pin 3 of the transformer is at chassis potential. Db is forward biased. By simple autotransformer action pin 1 of the transformer will be at a voltage multiplied by the turns step-up ratio. Db provides conventional rectifier action with current flowing in the direction shown. As a result a voltage of about 13V is developed across the boost capacitor Cb. This voltage is in series with the 11V supply, giving a total of 24V with respect to chassis. During the flyback Q, D and Db are all off and the charge on Cs is replenished from Cb. Thus in effect the line output stage is operated from the 24V boost line.

The Grundig CUC Series Chassis

Peter Stubb and Steve Beeching, T.Eng.

CUC? Yes, it stands for Compact Universal Chassis. As my mate Steff said you either know these Grundigs or trust to luck. Well, as every engineer should know luck plays a very small part in electronics servicing. So to help understand these confounded Grundigs we'll provide a run-down on the section that's the usual cause of concern, the switch-mode power supply. The whole CUC range uses a simple but effective flyback converter circuit. The main elements in this are a transformer, a chopper transistor and a Siemens TDA4600 control i.c.

Circuit Operation

The circuit is shown in much simplified form in Fig. 1. When the chopper transistor T634 switches on current flows in the primary winding of transformer TR651. As a result energy, in the form of a magnetic field, is stored in the transformer. During this process the h.t. rectifier D656 and the l.t. rectifier D661 are reverse biased. Therefore the secondary windings can draw only a maximum current whose value is related to the energy stored in the transformer while T634 is switched on. When T634 is switched off C634 provides circuit continuity and the rectifier diodes are forward biased by the collapsing field. The reservoir capacitors C657 and C662 are thus charged.

Pulse feedback is taken from pin 13 of the transformer to the bistable in the TDA4600. This toggles, switching T634 on when the magnetic field has completely collapsed. Thus T634 is automatically switched on and the only problem that remains is to time its switch-off to provide regulation. The on time is determined by the secondary current required.

Regulation is determined by feedback from winding 13-15 on the transformer. This monitors the rate of change of flux during T634's off period, providing a voltage propor-

tional to the current being drawn. If the secondary current is low the induced voltage is high and vice versa. D647 provides rectification, producing across C647 a voltage which is subtracted from the reference voltage at pin 1 of the i.c. The resultant voltage is applied to the non-inverting input of the voltage comparator within the i.c. The output from this comparator resets the bistable and turns off T634 once the ramp voltage at its inverting input (pin 4) exceeds the voltage at its non-inverting input (pin 3).

The ramp is produced by C646 which is charged by R646 from the mains-derived 300V line – this gives stabilisation against mains voltage variations. This ramp forms part of T634's drive waveform. For correct timing, C646 must start at 0V at the beginning of each duty cycle. The second output from the bistable triggers a transistor within the i.c. to discharge C646 during T634's off time.

The output voltages obtained from the circuit are adjusted by setting R647 which controls the feedback to pin 3 of the i.c. With the CUC chassis this is always set with reference to the +A voltage (h.t.) required. This is the supply for the line output stage and varies according to the screen size and tube beam current requirements.

By counting the variable mark-space switching pulses the i.c. can ascertain the set's working conditions. The frequency of operation is approximately 35kHz for normal operation with a nominal load. For protection the i.c. checks this frequency which falls to about 20kHz if the load increases: if the load increases further the i.c. switches the bistable itself at a rate of about 18kHz, limiting the maximum output current. The power supply will run even with a short-circuit line output transistor, though a PTC thermistor ensures that a load of greater than 100Ω is present at all times.

For over-voltage protection, if a supply from the trans-

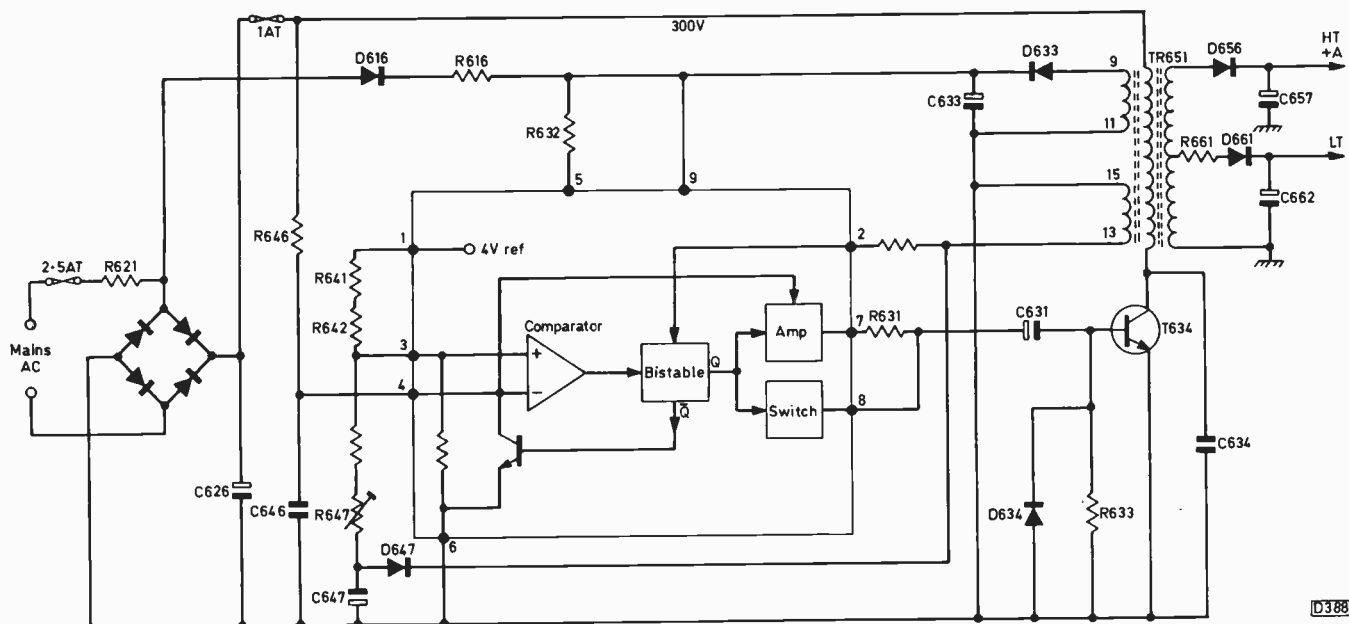


Fig. 1: Switch-mode power supply used in the Grundig CUC series chassis – simplified circuit.

former goes missing so that less current is drawn the frequency of operation increases. The upper limit is 60-70kHz, which equates with a remote control set in the standby condition or running the power supply with no load.

Note however that if all the rectifier diodes connected to the transformer's secondary windings are disconnected the result will be instant destruction of the power supply. This is because the transformer is without damping and the collapsing field is so large that the voltage pulses generated destroy T634 and the i.c.

In the event of the drive coupling capacitor C631 going low in value the i.c. will shut down: it will then cycle and keep trying to restart.

Further protection is necessary because the i.c. can operate effectively only with mains inputs between 165V and 265V. This protection is coupled with the start-up system. The i.c.'s supply pin 9 is provided with a start-up supply by D616. This supply is 9V with an internal cut-off at less than 7V. Further protection is provided by the link to pin 5 via R632. If the voltage here is less than 2.2V the i.c. shuts down. Because of the slow-start action the voltage across C633 does not initially reach 9V: the i.c. will try to get going five or six times before the charge on C633 rises above 7V. Once the circuit has started up D633 charges C633 to just over 12V.

Fault Finding

So much for basic operation, now for fault conditions. With all chassis that use this type of circuit the charging resistor connected to pin 4 of the i.c. is notorious. If R646 goes high in value or open-circuit T634 is left switched on and instantly turns into a piece of wire. If C646 goes open-circuit switching will occur at a very high frequency – too fast for the i.c. to regulate – and T634 will turn into a heating element before again turning into wire. C631 or R631 open-circuit will cause the power supply to shut down and hunt, as will C633 low in value or D633 open-circuit.

Checking is best done in a systematic fashion as follows: (1) Check the voltage at pin 9 of the i.c. To start up it must be greater than 7V and for normal running it should

be 12V. If it's at 40V the i.c. is open-circuit.

(2) The voltage at pin 5 (safety circuit) of the i.c. must be greater than 2.2V.

(3) During start-up 4V squarewave pulses should be present at pin 1 of the i.c.

(4) Check that a squarewave of greater than 1V is present at pin 7 of the i.c. and the base of T634.

(5) If still in doubt check the frequency at which the power supply is running.

Some Symptoms

Finally a résumé of symptoms with the power supply running.

Uncontrollable h.t.: D647 or C647 leaky or open-circuit.

Intermittent start-up from cold: C633 low in value (it was increased to 220 μ F in later production) or R647 intermittently open-circuit (faulty connecting rivet, usually with 110° remote control sets).

Relay on 110° remote control sets chatters at switch on: R647 faulty.

All components in the power supply o.k. but won't start up: One of the diodes fed from the transformer's secondary windings short-circuit.

Screen patterning which varies in frequency with the brightness/contrast: H.T. or l.t. reservoir capacitor open-circuit, i.e. 35kHz ripple on the l.t. line.

Set intermittently goes to standby (C range remote control models): D661 going high-resistance. Replace R661 at the same time and upgrade D661 to a Motorola MR824-400 or Siemens GI824.

D634 and R633 should be checked whenever it's necessary to replace T634. If T634 goes short-circuit base-to-collector C631 and the i.c. should also be replaced.

Voltage Conditions

All voltage checks on the primary side of the power supply circuit are with reference to the -300V line, i.e. the negative side of C626: all voltage checks on the secondary side of the circuit, including the setting of R647, are with respect to chassis.

The Development of Colour Tubes

Part 2

Eugene Trundle

Last month we provided a brief outline of colour tube evolution, looking at the main features of successive types of tube. We intend next to consider in greater detail the various items that go to make up a tube and its deflection system. The best place to start is where the beams themselves do, at the electron gun.

The gun is an assembly of electrodes that produce, modulate, accelerate and focus an electron beam. The electrons that go to make the beam are produced at the coated surface of the cathode, as a result of thermal agitation caused by the heating element inside. The beam is controlled by the grid (really a cylinder or plate with a pinhole in its face) and accelerated towards the screen by a series of cylindrical anodes which together form an electron lens. We should perhaps qualify the phrase "controlled by the grid". The beam is modulated by varying the voltage applied between the cathode and the grid. So we can hold the cathode at a fixed voltage and vary the grid voltage or hold the grid voltage steady and vary the cathode voltage. The latter technique is generally used.

Heater-cathode Assemblies

The heater is a spiral of tungsten wire coated with an insulating layer of alumina (aluminium oxide). The first colour tubes used gun assemblies similar to those in contemporary monochrome tubes, and for many years each colour tube heater drew 300mA at 6.3V. The cathode assembly was large and thermally inert, taking some thirty seconds to reach operating temperature. Modern heater-cathode assemblies are very small and light, with a typical energy requirement of 33mA each, corresponding to about 0.65W – see Fig. 14. The active part of the heater is concentrated in the "hot spot" immediately beneath the centre of the small, light cathode. This runs cooler than a conventional cathode while the operating temperature is reached in about five seconds – the normal operating temperature for a tube cathode is around 1,100°K. The cathode is coated with oxides, typically of barium and strontium, which at high temperatures are prolific emitters of free electrons.

The grid, still sometimes called a Weinhelt cylinder, is a cup-shaped nickel shroud or plate. For small spot size its central hole is of typically 0.5mm diameter. For high gain, i.e. lowest voltage drive requirement, the grid-cathode spacing when hot is around 0.1mm – not a lot!

Electron Lens

In an optical lens system the paths of the light rays are modified by the characteristics of the glass through which they pass. In manipulating an electron beam the same

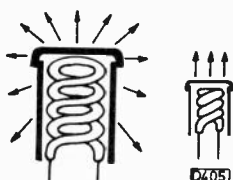


Fig. 14: Progress in heater-cathode design. Left a 2W assembly, right the 650mW type.

effects are achieved by electrical fields produced by (usually) cylindrical anodes – hence the term electron optics. Except in the Trinitron, separate lenses are provided for each of the beams in a colour tube, whether the tube has separate (delta, 20AX and 30AX) or unitised (PIL, 45AX etc.) gun assemblies. In the description that follows we are concerned with focusing an individual beam to form a sharp spot at the tube's phosphorescent screen. Aiming the three separate beams so that the coloured images they produce overlay (convergence) is a deflection rather than a focusing process and will be dealt with separately.

Effect of Potential Gradient

Lines of electric force exist in the space between two electrically charged plates, each line forming an imaginary voltage boundary in similar fashion to the contour lines on a geographical map. When an electron, which has a negative charge, is present in this region it will be attracted to the positive plate. If it's travelling through the lines of force however (see Fig. 15) the effect will depend on its direction. When the electrons in a beam are travelling up a potential gradient, i.e. through regions of increasing voltage, the effect will be to straighten the beam and direct it at right-angles to the lines of force. The electrons are accelerated and set on a converging path to form a point of focus at some plane beyond the lens. Conversely when a beam is travelling through a field of decreasing electrical strength, i.e. travelling down a potential gradient, the electrons will experience a lateral deflection force that tends to align them with the lines of electric force.

Unipotential Gun

A simple electron lens system is shown in Fig. 16. After leaving the cathode the electrons travel on a diverging path through the pinhole in the cylinder grid and are then rapidly accelerated by the high voltage applied to the first anode. The cathode-grid-first anode combination forms a strong positive lens (steep potential gradient) that brings the beam to a point of sharp focus in the vicinity of the first anode disc. This region is often called the prefocus lens, and since the spot at the tube's screen is an image of this beam crossover point it's important to have minimum aberration here.

After passing through the first anode disc the diverging beam is greatly accelerated by the second anode which, like the fourth anode, is at the full e.h.t. potential. As it approaches the third (focus) cylinder, which has about 500V applied to it, the beam finds itself travelling down a potential gradient. As a result, it decelerates and diverges. It soon comes under the influence of the fourth (final) anode which produces an increasing potential gradient, sending the outer electrons in the beam on a converging path, the focal point being at the screen. The A3 (focus electrode) region is called the main lens: its focal point can be varied by adjusting the voltage applied to this electrode. This is the principle of the unipotential lens, as used

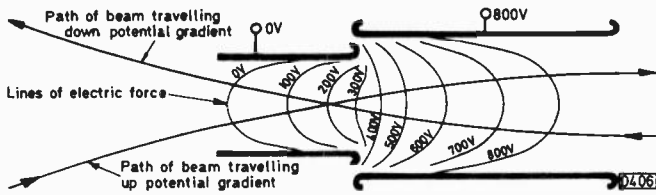


Fig. 15: Electron trajectories through electric fields. The electron travelling to the left is decelerated and takes a divergent path. That travelling to the right is accelerated and aligned along the axis of the cylindrical electrodes.

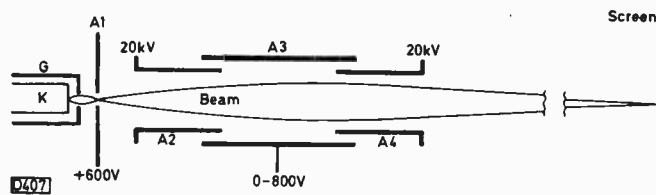


Fig. 16: Unipotential electron gun.

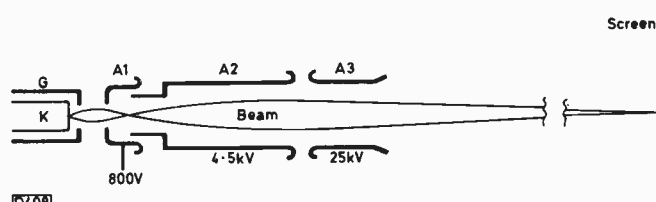


Fig. 17: Bipotential electron gun.

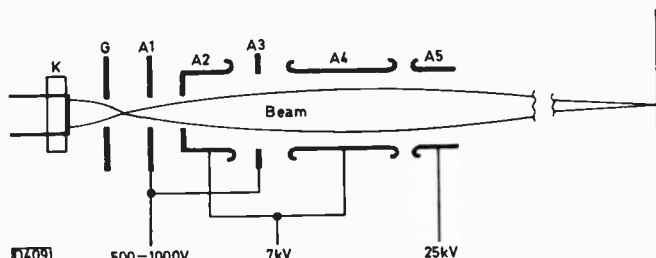


Fig. 18: Hybrid lens with coupled unipotential and bipotential sections.

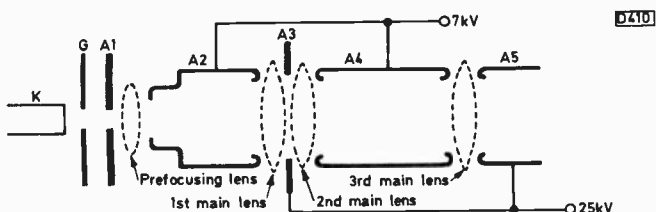


Fig. 19: Multistage system consisting in effect of three bipotential lenses in series.

in monochrome, many Trinitron and some types of delta-gun tubes. They are characterised by a low and non-critical focus voltage which is sometimes provided by fixed voltage taps rather than a potentiometer.

Bipotential Gun

The widely used bipotential gun system requires a focus voltage approximately 20 per cent of the final anode voltage. See Fig. 17. Here the focus anode (A2) comes directly after the first anode and takes the form of a long cylinder, often with its rear end protruding into the cup-shaped first anode to give a steep potential gradient at this point. The final anode A3, at about 25kV, gives the

electrons in the beam tremendous acceleration and sets them on a converging path.

High Bipotential System

A refinement of the bipotential lens system is the high-bipotential focus (HBF) system in which the focus cylinder (A2) is made much longer (hence a longer gun and neck) to form a weaker lens with less beam aberration. This involves the use of a higher focusing voltage (between 27 and 32 per cent of the e.h.t. potential) and is capable of better performance. It's used in certain 90° PIL type tubes and also in 30AX tubes, which accounts for the longer tube neck and higher voltage requirement for these compared to the 20AX.

Multi-lens Systems

There are more elaborate electron-lens systems in which multistage (compound) lens principles are used. A hybrid lens is formed by coupling a unipotential lens to a bipotential type, see Fig. 18. A multistage focus system can be made up as shown in Fig. 19. These more elaborate gun systems are generally required only for high-definition tubes with small screens, though consumer tubes with large deflection angles and narrow necks sometimes use them to compensate for the necessarily small lens diameter in mini-neck (22.5mm) systems – as in light optics, the larger the lens diameter the better the performance.

Refinements

Since the lenses in modern tubes are side-by-side the diameter of each is limited to slightly less than one third of the internal diameter of the tube neck. In their 45AX system Mullard/Philips use a specially designed unitised gun incorporating an aberration reducing triode (ART) focusing system. With this the prefocusing lens is designed so that the aberrations in the cathode image, prefocus and main lens partially cancel each other: the main lens is a high-bipotential type requiring 31 per cent of the e.h.t. potential – approaching 8kV.

The design of the electron gun varies considerably between different manufacturers and depends on many variables – screen size, neck diameter, phosphor dot pitch and particularly the yoke characteristics. Sometimes the gun is called upon to predistort the beam shape to compensate for deflection distortion: this can be achieved by providing slit apertures rather than circular holes in certain of the gun's electrodes.

Neck Diameter

The choice of tube neck diameter is a very difficult one. A wide neck (36.5mm) permits relatively large diameter electron lenses for minimum spot size and least aberration. The widely spaced beams are difficult to converge however, since they take such different paths through the deflection field. Much deflection power is needed to generate the required field strength in the large neck cross-section, particularly with wide-angle tubes. Narrow neck (29mm) and mini-neck (22.5mm) tubes require much less deflection energy and their closely spaced beams need less convergence correction. Their necessarily small diameter electron lenses do not make for a small spot size however, hence the multistage focus lenses described

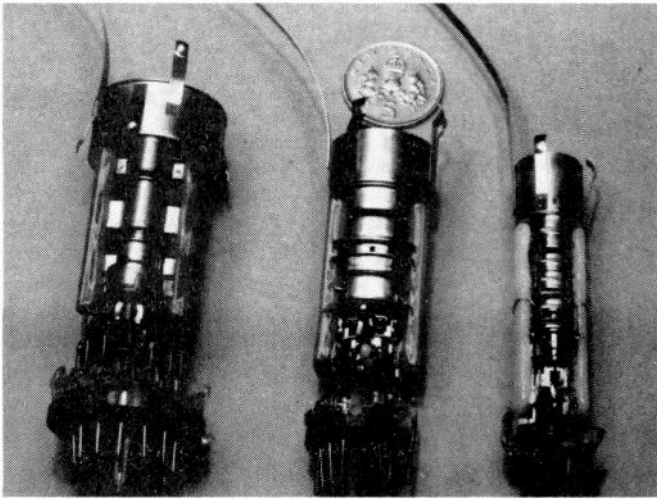


Fig. 20: The three sizes of gun for in-line tubes – 36.5, 29 and 22.5mm. Note that the gun on the right has a multi-stage electron lens.

above. New electron lens technology permits the effective lens discs to overlap each other however. In this way the 5.5mm lens diameter typical for a 29mm neck is effectively increased to 8.2mm (plus 50 per cent). Similar improvements have been made in mini-neck guns. Fig. 20 shows the three basic gun types – large, narrow and mini.

Gun Flashover Protection

Two main flashover phenomena exist in a picture tube. They show up mostly during the first few hundred hours of operation. The rocky-point discharge (as it was called for many years) is due to high electrostatic field strength at a micro-protrusion on an electrode. This can break down the vacuum insulation to an adjacent electrode, the result being sparking. The likelihood of this is reduced by providing a high surface finish to all electrodes, by rounding the ends of anode cylinders (see gun on left in Fig. 20) to prevent steep voltage gradients, and by spot-knocking – the deliberate use of excessive voltage to induce flashovers and break down micro-protrusions.

The second main cause of flashovers is called the trigger arc and arises from a complex insulator charging phenomenon. It takes place on the inside surface of the glass neck, or more commonly on the multifurcated glass rods that support and space the gun electrodes. To prevent it the glass rods are fitted with an electrically floating conductive path or a wire conductor from a nearby anode. This prevents the build-up of high static charges and forestalls trigger arcing. The wires around the two support beads can be seen on the gun on the right in Fig. 20. More flashover-reduction technology will be described later in this series.

Neck Magnets

On their journey through the tube's neck the beams encounter a series of carefully tailored fields produced by

permanent magnets whose function is to prealign the beams so that they enter the deflection region correctly aligned and at the right angles. With in-line tubes the fields are provided by pairs of ring magnets which are adjusted and sealed by the tubemaker or at the TV factory.

Purity

First we must orientate all three beams so that they pass through the points in the deflection centre corresponding to the positions of the light sources used to fix the phosphor on the screen. This requires a pair of two-pole ring magnets, see Fig. 21, by means of which the strength and direction of a simple vertical field can be set to move all three beams together horizontally so that they strike the correct phosphor stripes. This is the purity adjustment of course.

Static Convergence

Since the centre beam (which we'll assume to be green) is always on the tube axis it undergoes least geometrical distortion in the scanning process and can be likened to the single beam in a monochrome tube. The images formed by the two outer beams, blue and red, are made to conform to that of the green beam in the convergence process, so the magnetic fields generated by the other rings (the static convergence rings) are designed to affect only the paths of the outer beams – no flux is set up at the tube's axis, so the trajectory of the centre, green beam is not affected.

To align the blue and red rasters so that they overlay the green raster exactly we need complete control over the positioning of the outer beams. First comes a pair of four-pole ring magnets (Fig. 22). Both are identical, so that by rotating them with respect to each other the effective fields can be cancelled or doubled to get the required field intensities: the direction of the fields thus established can be adjusted by rotating both magnets together. As the intensity of the four-pole fields is varied the outer beams are moved differentially in a horizontal plane: as the direction of the four-pole fields is varied the outer beams are moved differentially in a vertical plane. Thus by relative and co-adjustment of the four-pole rings the blue and red beams can be superimposed to give a magenta cross at the centre of a crosshatch display. This will not necessarily coincide with the green cross however, and this where the third ring magnet pair comes in.

The correction fields required this time come from a six-pole ring magnet pair. Once again the strength and direction of the fields can be set by relative and co-adjustment of the two rings as described for the four-pole pair. The six-pole pattern is shown in Fig. 23, where it can be seen that the outer beams only can be deflected together in the vertical and horizontal planes as required. This superimposes the magenta on the green cross at screen centre to complete the static convergence process.

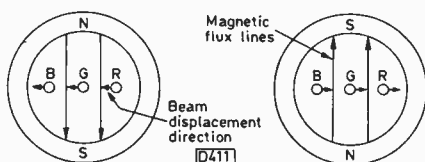


Fig. 21: Effect of a two-pole ring magnet.

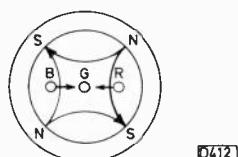


Fig. 22: Effect of a four-pole ring magnet.

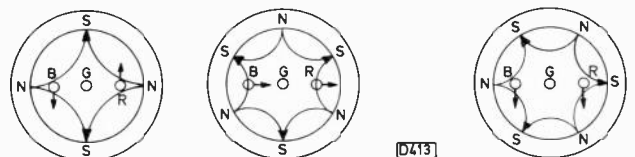


Fig. 23: Six-pole field pattern.

PROTECTION FOR WORKSHOP & HOME

A COMPLETE SECURITY SYSTEM FOR ONLY £39.95 + V.A.T.

contains:
Control Unit
Enclosure & mechanical fixings
Key Switch & 2 keys
LED's
5" Horn Speaker
4 high quality surface mounting Magnetic Switches

With only a few hours of your time it is possible to assemble and install an effective security system to protect your family and property at the amazingly low cost of £39.95 + V.A.T. No compromises have been made and no corners have been cut. The outstanding value results from volume production and direct supply. Assembly is straightforward with the detailed instructions provided. When installed you can enjoy the peace of mind that results from a secure home. Should you wish to increase the level of security the system may be extended at any time with additional magnetic switches, pressure pads or ultrasonic sensors. Don't wait until it's too late! order today!
Order Code: CS 1370

ALARM CONTROL UNIT CA 1250

Price £19.95+V.A.T.

The heart of any alarm system is the control unit. The CA 1250 offers every possible feature that is likely to be required when constructing a system, whether a highly sophisticated installation or simply controlling a single magnetic switch on the front door.

- Built in electronic siren drives 2 loud speakers
- Provides exit and entrance delays together with fixed alarm time
- Battery back up with trickle charge facility
- Operates with magnetic switches pressure pads ultrasonic or IR units
- Anti tamper and panic facility
- Stabilised output voltage
- 2 operating modes full alarm anti tamper and panic facility
- Screw connections for ease of installation
- Separate relay contacts for external loads
- Test loop facility

TIMER SWITCH & POWER SUPPLY MODULE DP 3570 Price £13.95 + V.A.T.

The DP 3570 consists of an adjustable timer switch and stabilised 12V power supply for use in a wide range of applications including security, lighting control and automatic switching. The timer section of the module provides switching of loads up to 3A for pre-set times, the duration of which may be set by the user to between 10 seconds and 5 mins. The timed period may be triggered by the opening of a door or the closing of external contacts with the timed period commencing instantaneously or delayed to provide a form of entrance delay. The power supply section of the module provides a 12V output of up to 250mA which is sufficient for most applications. The module operates from either 240V a.c. supply or a 12V battery for which trickle charge facilities are included. Connections to the module are by means of screw terminal connectors with no soldering needed.

For mounting the unit an attractive moulded enclosure is available.
ME 357 only £2.85 + V.A.T.

INFRA-RED SYSTEM IR 1470 only £25.61+V.A.T.

Consisting of separate transmitter and receiver both of which are housed in attractive moulded cases, the system provides an invisible modulated beam over distances of up to 50ft operating a relay when the beam is broken. Intended for use in security systems but also ideal for photographic and measurement applications.
Size 80 x 50 x 35mm

EXTENDED SYSTEM CS 1480 Price £62.50 + V.A.T.

This system contains in addition to the CS 1370, an ultrasonic detector type US 5063 - its enclosure, an additional horn speaker, and a further 2 magnetic switches. This system represents outstanding value for money for the high level of security provided.
Order Code: CS 1480

HARWARE KIT HW 1250

only £9.50 + V.A.T.

This attractive case is designed to house the control unit CA 1250 together with the appropriate LED indicators and key switch. Supplied with the necessary mounting pillars and punched front panel the unit is given a professional appearance by an adhesive silk screened label.
Size 200 x 180 x 70mm

DIGITAL ULTRASONIC DETECTOR US 5063

only £13.95 + V.A.T.

- 3 levels of digitalisation against false alarms
- Crystal control for greater stability
- Adjustable range up to 25ft
- Built in delay
- 12V operation

This advanced module uses digital signal processing to provide the highest level of sensitivity whilst discriminating against potential false alarm conditions.

ULTRASONIC MODULE ENCLOSURE

only £2.95 + V.A.T.

Suitable metal enclosure for housing an individual ultrasonic module type US 5063 or US 4012. Supplied with the necessary mounting pillars and screws etc. For US 5063 order SC 5063 for US 4012 order SC 4012.

SELF-CONTAINED ULTRASONIC ALARM UNIT CK 5063

only £37.00 + V.A.T.

Requires no installation. Easily assembled using our professionally built and tested modules.

- Adjustable range up to 25ft
- Built in entrance and exit delay
- Built in timed alarm
- Key operated switch Off/ Test and Operate
- Provision for an extension speaker
- Fully self contained
- Uses US 5063 PSL 1865 Key Switch 3901
- 3" Speaker 3515

Now you can assemble a really effective intruder alarm at this low price using tried and tested Riscomp modules. Supplied with full instructions, the kit contains everything necessary to provide an effective warning system for your house or flat. With a built in LED indicator and test position the unit is easily set up requiring no installation. It may simply be placed on a cupboard or desk. Movement within its range will then cause the built in siren to produce a penetrating 90dbs of sound or even 110dbs with an additional speaker. All parts included and supplied with full instructions for ease of assembly. Size 200 x 180 x 70mm. Order as CK 5063.

SIREN & POWER SUPPLY MODULE PSL 1865

only £9.95 + V.A.T.

A complete siren and power supply module which is capable of providing sound levels of 110dbs at 2 metres when used with a horn speaker. In addition the unit provides a stabilised 12V output up to 100mA. A switching relay is also included so that the unit may be used in conjunction with the US 5063 to form a complete alarm.

RISCOMP THE SECURITY SPECIALISTS!

Add 15% to all prices
Add 75p pos. and packing to all orders. Saturday 9.00 to 1.00 p.m. SAE with all enquiries.
Units on demonstration Shop hours 9.00 to 5.30 pm Closed Wednesdays
Please allow 7 days for delivery.

FULL RANGE OF ACCESSORIES STOCKED SEND SAE FOR DETAILS

RISCOMP LIMITED

Dept TV7
51 Poppy Road,
Princes Risborough,
Bucks. HP17 9DB
Princes Risborough (084 44) 6326

Fig. 24 shows the order of the ring magnets on the neck of a typical PIL type in-line gun tube (Hitachi).

Raster Symmetry Magnet

The same two-, four- and six-pole fields are used with 20AX tubes. Also required is an additional ring magnet pair with a two-pole field to generate horizontal lines of force to deflect all three beams vertically. This raster symmetry control compensates for any curvature of the

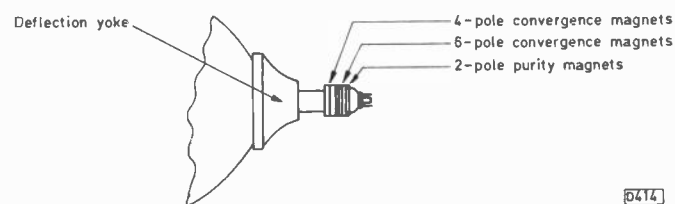


Fig. 24: Assembly of magnets on the neck of a 90° PIL type colour tube.

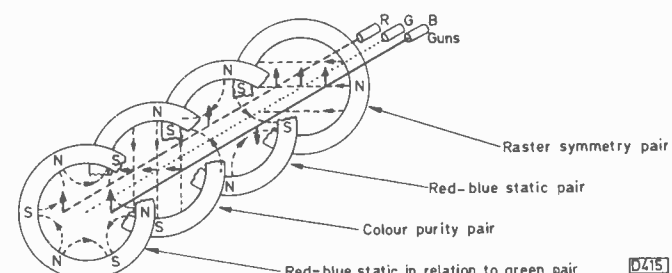


Fig. 25: Multipole cluster on the neck of a 20AX tube, showing the effects on the electron beams.

horizontal centre line of the raster due to the barrel-shaped vertical deflection field acting on an off-centre beam formation – the three individual guns used in this type of tube cannot be assembled and positioned with as much accuracy as with a unitised gun system.

The 20AX multipole assembly, as the ring-magnet cluster is called, incorporates gearwheels to give automatic contra-rotation of each ring pair, with the gearwheel frame rotatable by a second lever in each case. This greatly simplifies purity and convergence adjustments on the rare occasions when they're required. The sequence and effect of the ring magnets in the 20AX system is shown in Fig. 25.

Internal Magnet System

In later Mullard/Philips designs the multipole assembly is dispensed with altogether. The 30AX (triple gun) and 45AX (unitised gun) tubes have a single magnetic ring mounted at the end of the gun assembly. At a late stage in manufacture all beam-alignment tolerances are taken up by a computer-controlled magnetising jig which prints into the ring a combination of two-, four- and six-pole fields to bring beam alignment to centre tolerance. This not only eliminates all manual adjustments on the tube neck but also permits any 30AX/45AX deflection yoke (of the correct type for the tube size) to be used.

Red Gun Centre

Note that with some PIL type tubes the red gun is the centre one. Next month we will be considering deflection yokes.

Servicing the Panasonic NV7000

David Botto

We've handled a fair number of these popular VHS machines which enjoyed a wide sale. Before tackling any repairs you'll find a little time studying the circuitry a good investment. We'll consider the various sections of the NV7000 and some of the fault conditions that can occur.

Access

To gain access for servicing is straightforward. First remove the two non-magnetic screws from the cassette cover. These are special screws, so be careful not to lose them. Next remove the two screws at the top corners at the back of the machine. You'll then be able to lift off the whole top portion of the case. Should you need to remove the bottom metal plate to expose the printed boards at the bottom of the case, place the machine upside down on a soft surface, remove the six screws that hold the plate and lift it away. Of the two PCBs thus exposed the smaller is the servo and subsystem control board and the larger the luminance and chrominance signal processing board.

To open the bottom printed panels remove three screws at the front and three at the rear. These screws are usually reddish-gold, making them easy to identify. By pushing back the front of the boards to clear the knobs and jacks etc. the boards are freed and can be swung outwards (hinged at the rear of the machine) for inspection. To remove the VCR's front panel - don't do this unless it's essential - remove three screws at the top and gently ease the panel off. It's best to start by removing just the cassette cover and top casing however.

In servicing these VCRs a special rubber bench mat, such as those supplied by Philips, RS Components, etc., is almost essential to avoid scratching or damage to the machine. You'll also find that a special magnetic screwdriver speeds things up and avoids screws being dropped into sections of the machine where they are difficult to retrieve.

Power Supply Arrangements

Looking into the top of the machine with the top casing removed you'll see the power supply board (VEP0177A) mounted upright at the rear left-hand side. A plate behind it holds IC1501 (HA17806) and transistor Q1501 (2SA1061).

The power supply circuit, together with operating voltages, is shown in Fig. 1. The mains supply is fed via the power switch at the rear of the machine to connection points 13 and 14 on the panel, passing via the fuse, filter coil L1001 and connector P1008 to the mains transformer T1001 which has its windings so arranged that selector S1002 can provide adjustment for inputs from 110V to 240V a.c. - always check that the setting is correct.

T1001 has three secondaries providing a.c. outputs of 20V, 12V and 38V which are fed back to the board via connector P1007.

The 20V a.c. supply is fed via fuse F1002 (4A) to D1006 which produces 20V across C1007 and bridge rectifier D1001-4 which produces approximately 18.3V across C1002.

The voltage across C1002 is applied to two separate regulators. First Q1003 whose base voltage is held steady by zener diode D1015. The voltage at the emitter of Q1003 goes to pins 6 and 7 of P1002 and via D1008 to pin 1 of P1003. Secondly Q1501, via P1001/1, which produces a stabilised 12V supply at its collector. This voltage is present at P1001/5 and at pins 1-4 of P1004. The base of Q1501 is driven by a conventional control circuit whose main elements are Q1001, Q1002 and zener diode D1012. Preset R1007 provides adjustment. To set up, connect a digital voltmeter between the 12V line and chassis and adjust for exactly 12V with the machine in the stop mode. Recheck after half an hour. Get it accurate to within 0.1V. Always check this voltage before tackling obscure faults.

The 12V at pin 1 of P1003 goes via pin 1 of connector P1507 to power switch S1507 on the power/timer/NR select board which lives at the right-hand side of the front of the machine, behind the front panel. The switches on this little board are operated by three small pushbuttons on the front right-hand side of the machine. Pins 6/7 of P1002 supply pin 1 of connector P704 on the TV demodulator section board which is on the extreme right looking into the top of the machine.

The regulated 12V supply at P1004 goes to various parts of the VCR as follows. Pin 1 feeds pin 2 of connector P3007 on the luminance/chrominance board. Pin 2 feeds pin 1 of connector P2005 on the servo and subsystem panel. Pin 3 supplies pin 2 of connector P6203 on the system control II board. Pin 4 supplies pin 2 of connector P704 on the TV demodulator section.

The unregulated 20V supply produced across C1007 passes via pins 4/5 of connector P1006 to pin 3 of connector P2005 on the servo and subsystem control board and pin 1 of connector P6203 on the system control II board (this board is cunningly folded together with the system control I board and hidden inside the machine on the right-hand side, under the two main bottom PCBs - the larger is the I board and the smaller the II board). The 20V supply is also fed via the 4.7Ω, 10W resistor R1501 and connector P1006/3 to pin 2 of connector P2005 on the servo and subsystem board.

The 20V a.c. winding on the transformer also supplies pins 1-2 of P1006. This supply goes to pins 1-2 of connector P3008 on the luminance/chrominance board, emerging from this board at pins 1-2 of connector P003 to power the PTC heater inside the little cast fitting near the back of the video heads.

The output from the 12V winding on T1001 is fed via F1003 (1A) to a second bridge rectifier, D1009-10, which develops 12V across the reservoir capacitor C1013. This supply goes to pins 5-6 of connector P1004. Pin 5 supplies pin 1 of connector P1515 on the power transistor panel while pin 6 supplies pin 4 of connector P7501 in the timer section. It also goes to pin 4 of connector P1001, then to regulator IC1501 whose 6V output appears across C1027. This supply goes via P1003/2 to P7501/5 in the timer section. It's also reduced to 5V via D1007 and is then fed via P1003/3 to P6001/1 on the system control I board.

The output from the 38V winding on T1001 goes via

1984). With the mains supply removed and the plugs disconnected from the power board you can effectively test every transistor, diode and capacitor in minutes.

Programmable Timer Board

We'll look now at some of the boards that have given us problems, starting with the programmable timer board. First ensure that all the supply voltages are present and correct. Measured between connector P7501 and chassis you should get readings of 3V a.c. at pin 2, -45V at pin 3, 12V at pin 4 and 6V at pin 5.

The usual cause of failure on this board, giving rise to various weird symptoms, is a faulty microcomputer chip. There are two, IC7505 (MN1400VL) and IC7506 (MN1405VM). A logic probe is ideal for fault tracing on this board: Table 1 shows the readings to expect at the pins of IC7505/6.

Before fitting a new microcomputer chip it's a good

Table 1: Microcomputer pin conditions.

IC7505		IC7506	
Pin	Reading	Pin	Reading
1	0V	1	0V
2	L	2	L
3	L	3	L+P
4	L	4	H
5	H+P	5	L
6	H+P	6	L
7	H+P	7	L
8	H+P	8	L
9	H+P	9	L
10	H+P	10	L
11	H+P	11	L
12	H+P	12	L
13	L	13	H
14	L	14	L
15	H	15	L
16	H+P	16	L
17	Slow pulse	17	L+P
18	L+P	18	P
19	H+L+P	19	P
20	H+L+P	20	Slow pulse
21	L+P	21	H+P
22	H+P	22	L+P
23	H+P	23	H+P+L
24	L	24	H+P+L
25	L+P	25	L+P
26	L	26	L+P
27	H	27	L
28	H	28	H
29	L+P	29	H
30	H+P	30	L+P
31	H+L+P	31	L+P
32	H+L+P	32	L+P
33	H+L+P	33	L+P
34	H+L+P	34	L+P
35	H+L+P	35	L+P
36	H+L+P	36	L+P
37	H+L+P	37	L+P
38	H	38	L+P
39	5V	39	5V
40	H+P+L(osc.)	40	H+P+L(osc.)

Notes: H=high, L=low, P=pulse.

Taken with front on button pressed but no function button pressed. Clock operating normally, reading Sun 1-07 when the readings were taken.

idea, after carefully removing the old one using a small, temperature-controlled soldering iron and good quality desoldering braid, to fit a forty-pin holder. If the fault should turn out to be elsewhere you can then easily replace the original chip – besides, it might fail at a future date . . .

If things seem to be otherwise in order but the clock display is rather strange the usual cause is one of the TA57 i.c.s (IC601-3). Check them with your logic probe or by replacement. There are four DN852 i.c.s on the board, IC7501-4, but we've so far never had any problems with these.

After you've carried out any repairs necessary on this board always check fuse F7601 (1AT). The clock will operate if this fuse is open-circuit but the back-up battery system won't.

The various diodes and transistors on the board can be quickly checked – they rarely fail – with your component tester. When testing be sure to desolder one end of each diode and two connections to each transistor. The small electrolytics dry up and corrode, causing mystifying faults, so examine them carefully for drying out.

Luminance/Chrominance Panel

Fortunately few problems occur with the luminance/chrominance panel. When a fault does occur however it can be extremely puzzling due to the complex circuitry used. First a warning: don't disturb the highly critical adjustments on this panel unless this is absolutely essential – if you do you may well spend many a happy hour getting them right again!

A fault that can occur – first make sure that it's not due to the video heads – is the luminance being poorly recorded or not recorded. With a colour-bar input to the VCR, observe the waveform at TP3001 – all test points on this panel are clearly labelled. Use a 10:1 probe with the scope. You should see the complete picture signal. From here the signal goes via R3002 and C3002 to pin 1 of IC3001 (AN6310) which can fail – this i.c. contains the a.g.c., sync separator, f.m. modulator, clamp and emphasis clip stages. The signal emerges at pin 24 of this i.c. and goes via L3001/C3003 and C3005 (0.047µF, type VCY25473KX, order specially from Panasonic) back to pin 5 of the i.c. The output at pin 24 also goes via C3006, Q3031 etc. to pin 21, emerging at pin 22 and then going via the deviation control R3019 and C3018 (47µF, 6V) to pin 19. Make sure that C3018 has not dried out or lost capacitance. After passing through an internal amplifier the signal reappears at pin 18 and is then fed via a non-linear emphasis circuit and emitter-follower to pin 16. After clamping the signal goes to the emphasis clip section (see Fig. 2). The white and dark clip presets are connected to pins 10 and 12 – both these adjustments are critical. C3022 between pins 13 and 14 provides frequency adjustment (3.8-4.8MHz). Understanding what happens in this i.c. is important when servicing the luminance/chrominance panel. The output at pin 9 goes via C3025 to TP3009, where you should see the f.m. signal waveform (at approximately 5V p-p), then via the record level preset R3025 to the record amplifier which consists of transistors Q3005 (2SC2377), Q3006 (2SC2206), Q3007 (2SB641) and the associated components. Should you ever need to replace any of these transistors (they rarely fail) do use exact replacements or you may get all kinds of puzzling results.

The chrominance circuitry is reliable and despite the numbers of these VCRs we've serviced not many prob-

lems have been encountered. IC8001 (AN6360), a device used in various VCRs, can fail however. Whenever we meet this i.c. we regard it with suspicion. Perhaps we've just been unlucky.

Record signals arrive at pin 1 of IC8001 via filter FL8001 (VLF0113), the playback signals going to pin 18 via FL8002 (VLF0085). These filters – there are a number on the board – sometimes cause problems, but check the soldered joints before condemning them. You should see the standard cotton-reel colour-bar signal with burst information at TP8001 (pin 7 of IC8001).

A good monochrome playback signal with no colour may mean that the a.p.c. preset (C8050) and/or the reference oscillator preset (C8024) needs very slight adjustment. Don't turn either of these to find out because if the fault should prove to be elsewhere you'll make yourself a lot of work. Insert a tape, switch to record and set the input select switch (front of the VCR next to the tracking control) to the camera position. Connect a digital frequency counter to TP8008 via a 10:1 probe. It should indicate 4.433619MHz to within ± 50 Hz (the figure in the service manual, 4.435572 MHz, is incorrect). Next switch to the stop mode. With the counter connected to TP8002 a reading of 4.433619MHz ± 10 Hz should be obtained. If either or both of these frequencies is incorrect carefully adjust the preset capacitors as necessary. If the waveform at TP8002 is missing suspect IC8002 (AN6352). Before changing any i.c. on the board however always check the small surrounding electrolytics.

Puzzling effects can occur if one of the connector plugs on the board is not pushed right home into its socket. Check them all.

System Control Boards

The system control I board contains the microcomputer chip IC6001 (MN1400VP) together with a variety of i.c.s packed with logic gates, inverters and other types of logic, plus the usual diodes and transistors. The only practical

TVS TRADE SERVICES BROMSGROVE

Large selection of quality clean TV & Video always in stock, including:

BUSH T20/24 DECCA 80/100
GEC STARLINE
HITACHI ITT (full remote)
PHILIPS G8
PHILIPS G11 PHILIPS KT3
THORN 9600 including TELETEXT
THORN 8800 THORN 9000 (remote)
THORN TX

VHS VIDEO from £85 (working)

We specialise in working sets, fully serviced and ready to deliver to your customer's home. Spares back up service available to customers. You've seen the junk, so why not now come and pay us a visit – we think you will be pleasantly surprised by our prices and the quality of our equipment. Delivery service available.

STOP PRESS

Electronic Video including Ferguson 3V29/30, Amstrad 7000, Sharp 9300, now in stock at unbeatable prices. We also specialise in direct loads delivered to your door direct from source.

For further details phone:

COLIN BROOMFIELD,
UNIT 7, STATION STREET,
BROMSGROVE, WORCS.
(0527) 37037/71186



way to fault-find is to use a logic probe (see details given on pages 22-23 in the November 1985 issue) after first checking the board's supply voltages. All sorts of interesting problems can occur, such as indicator LEDs flashing on and off when they shouldn't, functions refusing to

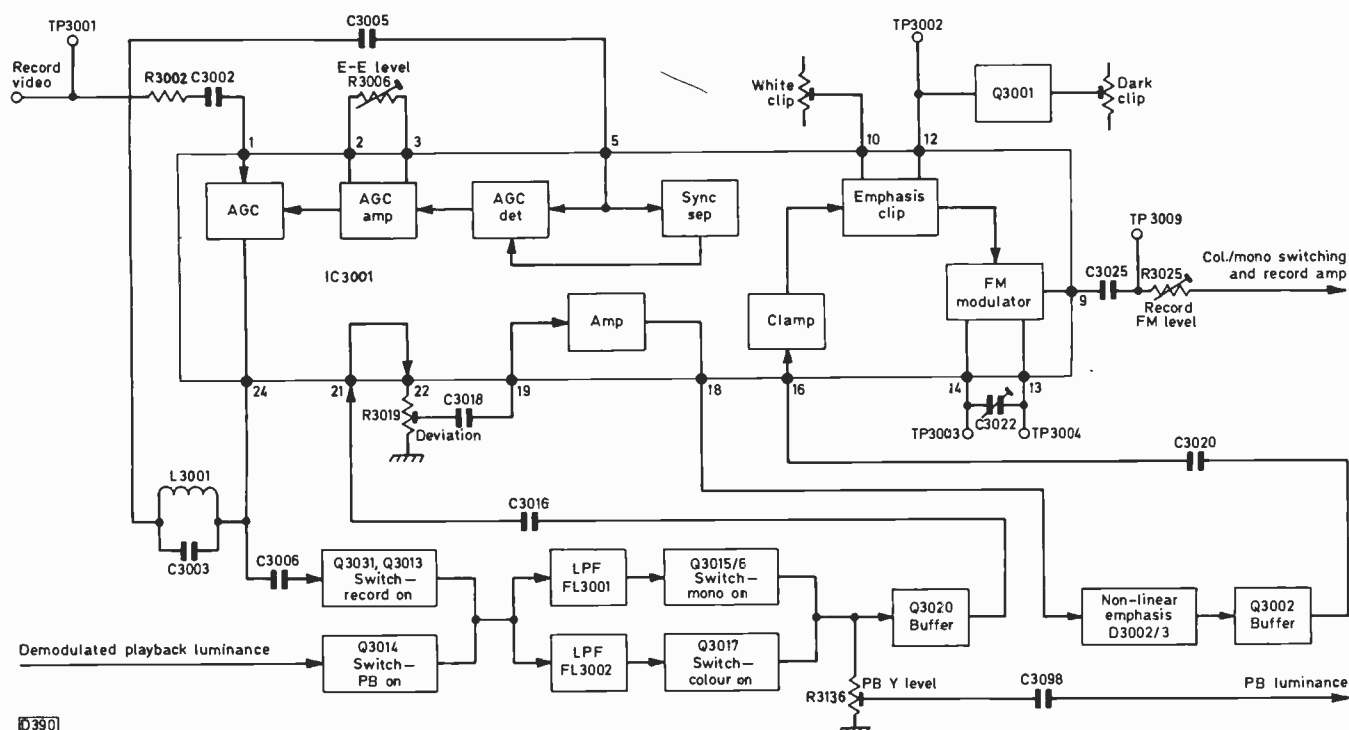


Fig. 2: Block diagram showing the luminance signal processing in the record mode.

work, motors turning on and off when they feel like it, etc. Often the fault lies in IC6001, but it can be due to a faulty logic gate or inverter in one or other of the various logic i.c.s. Favourite logic i.c.s to fail seem to be IC6002 (4081), IC6003 (4049) and IC6004/5 (both 4503s).

Interestingly, with so many of our customers owning NV7000s we've had no problems yet with the system control II board, nor with the little front panel that holds the selector switches operated by the front panel function select buttons.

In later models the system control I and II panels were replaced by a single board using a new specially developed microcomputer chip (IC6001, type MN1405VK). This seems to be more reliable than the system control I board microcomputer chip. You'll probably mostly encounter the two-board version however.

Audio and Still Boards

The audio board has not troubled us yet and we've only rarely had faults on the still board. This latter board contains mostly NAND, AND, and OR gates plus D-type flip-flops so you need use only your logic probe and for the individual transistors your component tester.

Servo and Subsystem Board

If the drum motor is running very fast indeed replace capacitors C2033 (0.01 μ F, 50V ceramic) and C2034 (0.068 μ F, 50V mylar) connected to pins 14 and 13 of IC2001 (AN6350). When the motor won't lock in properly first check diodes D2009/10 (both type MA150) and capacitors C2036 and C2037 (both 0.1 μ F, 50V mylar) connected to pins 11 and 9 of the i.c. If these components are in order you'll have to try replacing the i.c.

Other servo problems that cause failure of the drum motor to lock properly can be caused by IC2008 (μ PD4011C) which contains four NAND gates and is thus easily checked. Watch out for sneaky tricks caused by diode D2012 (MA165) which is connected between pin 2 of this i.c. and chassis.

Problems in IC2002 (AN6677) can result in failure of the drum to rotate. Check Q2019 (2SD389) first however.

If the capstan motor doesn't lock in correctly the suspects are IC2001, IC2004 (AN6341) and IC2007 (μ PD4528C). The quickest way to find out which is the culprit is by replacement.

Various Faults

When the tape loads and then immediately unloads after pressing the play button the loading belt is probably at fault. If you need to replace this belt it's best to fit a complete new set of belts to prevent future troubles.

Noise bands running up and down the recorded picture can be caused by a faulty tracking control – this is usually due to a heavy-handed user.

If the tape won't play make sure that the cassette lamp isn't open-circuit. I know that this is an obvious fault – but one can still get caught.

If the tape unloads when a cassette is played and the counter reads 0006 to 0007 it's possible that the Hall-effect i.c. (DN838) under the supply reel is at fault. It's best to replace this by cutting the legs off the old i.c., then soldering the new one to these – this is the official instruction we had from Panasonic. This is also a good place to say how helpful the engineers at Panasonic have

been whenever we've phoned them for advice. It's appreciated, believe me!

A much more likely cause of trouble when the tape halts at 0006/7 is the capstan motor. These motors are expensive however. So carefully unplug the connector to the motor, unbolt and remove it from the machine. Take out the three screws that hold it together and separate the pieces. Don't lose any of the special parts that make up the motor. Lubricate the bearings with just the slightest trace of Castrol DWF lubricant. When reassembling lubricate the spindle – again the slightest trace – where it passes through the top plastic washer (this washer looks like an inverted top hat when removed from the motor). Don't push it down too far when reassembling. You'll nearly always find that the problem has been cured when the capstan motor is refitted.

The Heads

Provided they are regularly cleaned the video heads enjoy quite a long life. Clean the whole video drum thoroughly before condemning them – also the audio/control and erase heads. Clean the entire tape path using only a proper video head cleaning kit and fluid. Good heads are easily ruined by incorrect cleaning materials.

A fair picture from a prerecorded cassette but a poor one from a recording made by the machine can be a sign of worn heads. You can check the heads by playing the Panasonic alignment tape (part no. VFM8100H3D) and observing the f.m. envelope at pin 10 of IC3002 (AN6320) on the luminance/chrominance board, using a scope with 10:1 probe. Make sure that the tracking control is in its fixed position. We find however that the best method, provided you've a spare drum to hand, is to try a new set of video heads. This is quick and reliable – it's done in minutes, just two screws and four soldered connections. The leads are colour coded, so it's difficult to wire them incorrectly. It's been done though! If you get a winding reversed you can end up with a nice monochrome picture, i.e. no colour.

It's always best to fit the correct heads supplied by Panasonic. You'll find it cheaper in the long run because with the correct heads fitted no or minimal adjustments should be necessary.

Tuner/Demodulator Panel

The tuner never seems to fail but it can drift off tune after an hour or so. If this occurs first check for 12V at pins 1 and 2 of connector P704 and 45V at pin 4. Then check D7011 (RD5-1EB) and D7013 (μ PC574JK), also transistors Q7007 and Q7019 (both type 2SA684). Another suspect is D7026 (MA150). On rare occasions IC7001 (AN5701) gives trouble.

A dusty picture in the E-to-E mode only is caused by a faulty r.f. booster unit (part no. ENPE702). Replace the unit, don't waste time trying to repair it.

General Advice

In conclusion I'll repeat my usual advice about applying a little circuit varnish to any joints you may have resoldered – but use a tiny brush to do so. The Panasonic alignment tape is well worth having as it will save you much time in servicing and any necessary adjustments. For voltage measurements I recommend using only an accurate digital multimeter.

Service Bureau

Requests for advice in dealing with servicing problems must be accompanied by a £1-50 cheque or postal order (made out to IPC Magazines Ltd.), the query coupon and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.

TOSHIBA V9600

The picture is full of snow except for two inches or so at the bottom of the screen. This part is viewable but has no colour. The sound doesn't seem to be affected and the fault sometimes clears after a short run.

It sounds as if most of the f.m. envelope is missing in the fault condition – the machine is probably not lacing up correctly. When the fault doesn't clear while the machine is running it's possible that the back-tension pole is outside the tape. The pole is adjustable. Otherwise observe the lacing action with the cover off: the back-tension arm could be sticking up or reaching its stop before contacting the tape.

THORN 1590 CHASSIS

The problem is bottom fold-up and bent verticals. Also the picture rolls when the video content changes – adjusting the field hold control restores field lock.

Poor field sync can be caused by a number of things in this chassis: failure of the sync phase-spitter transistor VT8 or its base bias resistor R46 (100k Ω); C1, C2 (both 10 μ F) or C17 (4.7 μ F) in the a.g.c. circuit drying up; incorrect setting of the preset contrast control R2; or C36 (4.7 μ F) in the video driver transistor's base bias circuit drying up. Ideally you need a scope to check the vision detector's output (waveform B in the manual) – look at the quality of the field sync pulse. Careful examination of this will direct you back to the i.f. amplifiers or forwards to the video and sync departments. If the bottom foldover remains when the sync problem has been solved check the setting of the regulated l.t. supply then if necessary check the lower field output transistor VT20, the field scan coupling capacitor C78 (1,000 μ F), and C80 (change to 10 μ F if 25 μ F) in the field linearity feedback circuit.

SANYO VTC5300P

There are intermittent noise bars and field jitter. The noise bars usually start at the top of the picture: adjusting the tracking control removes them but they return soon after. The picture is otherwise o.k. I've gone through the setting up procedure in the manual several times and can't find anything wrong, though I did notice that the pinch roller is very sloppy on its spindle.

The pinch roller is given some play to enable it to align with the capstan shaft. If you've cleaned the heads, guides and entire tape path, set up the guides using an oscilloscope to view the envelope pattern with an alignment tape, and in particular checked and adjusted the back-tension as specified, it's likely that the head disc itself is in need of replacement.

SONY KV1320B

The problem is foldover at the bottom of the picture. No adjustment of the controls removes this effect and I suspect a leaky capacitor in the field timebase. Any ideas?

First check that the h.t. voltage is correct – there should be 115V at the emitter of the series regulator transistor Q903. If this is correct check the following electrolytics in the field timebase in this order: C511 (1,000 μ F, 16V), C506 (33 μ F, 16V), C507 (2.2 μ F, 10V). If the problem persists and adjustment of the vertical bias control VR503 doesn't clear it check the field output transistor Q901 (2SC867) and the driver transistor Q502 (2SC633A) for leakage.

ITT CVC20 CHASSIS

When this set is switched on with the correct h.t. setting there's no sound or picture, just a 1kHz whistle. If the h.t. is increased and pin 3 or 4 of the TBA920 line oscillator chip is touched the set will start with the e.h.t. high (28-30kV). Backing this down to 25kV will give normal operation.

The whistle you describe indicates that the line output stage is drawing no current. This is almost certainly due to lack of drive to the base of the BU208 line output transistor. First check the earthing of the line driver transistor's emitter (T13). This is connected to the metal chassis frame via a lug at the top left of the chassis. If this is o.k. the driver transistor itself is suspect – its collector voltage should be 117V.

SONY SL5

When play is selected the machine shuts down, though the LED indicator remains lit. The fault can be cleared by turning the mains supply off and then on again – the machine will then operate normally for quite a time. The play solenoid has been adjusted and all belts and pulleys have been cleaned.

This symptom is normally the result of the threading ring failing to rotate. The cause could be belt slippage, failure of the capstan motor or a fault in the capstan motor's drive circuit. If the tape does thread up before deck shutdown, check the operation of the slack sensor lever and reed switch.

PANASONIC U1 CHASSIS

There's sound only on this set. I'm told that the picture sometimes appears but I've yet to see it.

The usual cause of this fault is failure of zener diodes D818/9. In this event the voltage at pin 9 of IC301 (TDA2530) will be in excess of 12.6V. Replace both diodes (type QA106SB) and change their feed resistor R819 to 560 Ω , 0.5W.

QUERY COUPON

Available until 16th July 1986.
One coupon, plus a £1-50 (inc. VAT) cheque or postal order, must accompany EACH PROBLEM sent in accordance with the notice above.

TELEVISION JULY 1986

SANYO VTC5000

This machine is slow on rewind and stops before the tape is completely rewound, sometimes leaving a tape loop protruding from the cassette. If the reel brakes are held off manually the tape will fully rewind, though a little slowly.

The back end of the deck used in this machine is a fairly common source of problems. A complete cure will be obtained by replacing the reel motor and reel drive pulley unit and roughening the surfaces of the reel brakes. The parts required are not too expensive or difficult to fit.

TEST CASE

283

Each month we provide an interesting case of TV/video servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

As we said in test case 279 (March) the Hitachi NP8CQ chassis is very reliable. Even so, a dealer who looks after large numbers of these sets will inevitably see them in the workshop from time to time – and when they do come in they seem to have such interesting faults!

The set featured this month is an Hitachi Model CBP220. The fault seemed straightforward enough: the complaint was of a smeary picture and a technician was despatched forthwith to the address given. When our man arrived he found a very messy display on the screen. The picture was dark at the left, bright at the right and ill defined. It seemed certain that the c.r.t.'s cathodes were being modulated by a line-frequency sawtooth waveform and the most likely source of this was the line output transformer derived 180V rail which powers the RGB output transistors. A 10 μ F, 250V electrolytic capacitor was dug out of the spares box and dabbed across points K2 (180V) and K3 (chassis) on the tube base panel. Hey presto!, our technician was rewarded with a clear, sharp and evenly illuminated picture. It was the work of minutes to remove the decaying 180V supply reservoir capacitor C719 (4.7 μ F) on the main PCB and fit a new one in its place. Replacing the volume control potentiometer, which was found to be "crackly", took somewhat longer!

Some money and a cup of tea changed hands and our technician went on to his next call. The next call after that was to the recently repaired Hitachi – "goes all bright with lines across the screen" was the telephoned complaint. When our technician returned the set was behaving itself and couldn't be provoked into the fault condition. After a careful check on the work just done and a look at the connections to the relevant pins (3 and 10) on the line output transformer he hoisted the set into the car and brought it back to the workshop.

The fault didn't show up till the set was switched on

next morning. The screen then lit up brightly, with prominent flyback lines: the brightness next fluttered up and down at random before the set returned to normal operation. During these capers the brightness control had very little effect. The workshop worthies hooked a meter to one of the tube's cathode pins and another one to the common first anode pin. The readings obtained were around 110V and 500V respectively, but the picture was now normal.

The set was powered once more after lunch and sure enough the high brightness condition had returned. A check on the meters revealed that the cathode and first anode voltages were both marginally lower than before. Excessive first anode voltage was thus ruled out as a cause of the fault, while the very slight reduction in cathode voltage could not have been responsible for such a large brightness increase. The only other relevant tube electrode seemed to be the grid, and since this is connected to chassis there's no circuitry to check. In theory an internal leak in the tube can cause this type of fault, but grid-cathode leaks rarely appear from cold and disappear as the temperature rises – the opposite is usually the case.

As it turned out the tube was innocent though the root of the fault was not very far away from it. In fact the problem area is prominently shown in the June 1985 issue cover photo! See next month for the solution.

ANSWER TO TEST CASE 282 – page 524 last month –

The poor trainee struggling with the Pye 725 would probably not have found the answer to his problem in his college courses. The set had come in because of an intermittently snowy picture, but on the bench the dominant symptoms were low h.t., a small fluttering picture and a squealing noise from the power supply panel – in fact from the mains feed choke L909.

Many checks had been made and all Techno-Supersleuth's suggestions had been followed up. The trainee was in fact wasting his time because there was nothing wrong with the set's power supply department, as he would have seen had he looked at the waveform at the anode of the rectifier/regulator thyristor D888. The waveform would have had big "bites" missing from it at each firing point of the thyristor. So would the waveform at the mains input fuse F913, where there should be a perfect sinewave.

It's a characteristic of this type of half-wave rectifying thyristor circuit that large, short-term gulps of current are taken from the mains supply. Fine on "raw" mains, though the electricity supply authorities don't like it, but in this case the supply was via a 200W isolating transformer. Though this was theoretically adequate in terms of power rating it wasn't providing a "stiff" enough a.c. power source: the impedance of its secondary winding limited the charging current available for the h.t. reservoir capacitor C880.

The intermittently snowy picture? Bad joints at the front end of the vision i.f. strip, as usual.

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by the The Riverside Press Ltd., Thanet Way Whitstable, Kent. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £14, overseas (surface mail) £17 per annum, payable to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to currency exchange fluctuations and VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever. ISSN 0032-647X.

JUNCTION 11

A NEW COMPANY IN THE NORTH WEST
OFFERING A FRIENDLY, FIRST CLASS SERVICE
TO THE TRADE AT COMPETITIVE PRICES


OUR RANGE INCLUDES

G.E.C. PYE PHILIPS I.T.T. DECCA R.B.M.

Now in stock V.H.S. V.C.R.s from £60 plus full range of Thorn remote control including T/Text

★ **DISCOUNT FOR QUANTITY** ★

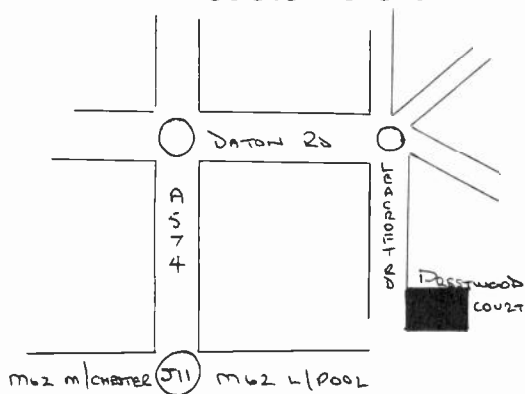The directors of this new company assure all our prospective customers of a warm welcome, and a fair deal.



**COME TO JUNCTION 11, M62,
YOU'LL FIND US HERE**

**JUNCTION 11
TV TRADE DISPOSALS LTD.,
Unit 11, Prestwood Court,
Leacroft Road,
Birchwood, Warrington.
Phone 0925 826387.**

Open 6 days 9 - 5.30 (later by appointment)

SPRING SPECIALS

10 BUSH 2 CHIP	£50
10 BUSH T20	£250
10 REDIFFUSION MARK 3	£250
10 REDIFFUSION MARK 1	
REVAMP	£120
10 THORN 8000 17"	£150

**LARGE QUANTITIES
OF BETA VIDEOS
RING FOR SPECIAL PRICES**

ALL + VAT

TELETRADERS

Forde Road, Brunel Industrial Estate,
Newton Abbot, Devon
Telephone: (0626) 60154
THE NO. 1 WHOLESALE IN THE SOUTH

TV LINE OUTPUT TRANSFORMERS

FAST RETURN OF POST SERVICE

RANK BUSH MURPHY A816 solid state mono 9.00 CROWN 14CX25 15.00	PHILIPS 170 series dual std mono 8.00 210 300 series mono 8.00 G8 & G9 series colour 8.00
DECCA MS1700200120202401 mono 7.00 MS2404 2420 2424 mono 7.00 CS1730 1733 colour 9.00 CS1830 1835 colour 9.00 '30' series Bradford colour 9.00 80 series colour 8.00 100 series colour 8.00	PYE 368, 169, 569, 769 mono 8.00 725-741 colour 8.00 SANYO 5101 & 5103 10.00 REDIFFUSION Doric Mk.3 10.00
FERGUSON HMV MARCONI 1600 8.00	WINDINGS Autovox 2282 2693 8.00
G.E.C. 2047 to 2105 7.00 2000 to 2064 dual std mono 7.00 2147 single std 9.00	RANK BUSH MURPHY A640, A793, A774 overwind 6.00 T20a T22, T26 Pri & Sec 6.00 Z718 primary state 18" or 22" 6.00 Z718 EHT overwind 8.00 SONY 1320UB overwind 15.00
Indesit 20EGB 24EGB mono 8.00	SOVEREIGN FARA £15.00 14" colour overwind
KB - ITT VC200 VC205 VC207 mono 8.00 CVC5 CVC7 CVC8 CVC9 col. 9.00 CVC20 series colour 8.00 CVC30 CVC32 series colour 8.00 CVC45 8.00 FT100 FT110 state p/no. 10.00 TXV80 10.00	ULTRA THORN 1690-1691 EHT overwind 7.00 Waltham 190 EHT overwind 6.00
PRICES INCLUDE P.P. & 15% VAT	

All lopts and windings are new and guaranteed

Open Mon.-Fri. 9 to 5.30 pm
Delivery by return.

**PAPWORTH
TRANSFORMERS**

80 Merton High Street,
London SW19 1BE

REWIND SERVICE
S.A.E. all enquiries
Barclaycard and
Access welcome



For orders placed at the post office
Trans cash
506 4856

01-540 3955

SPECIAL OFFER THIS MONTH

**PHILIPS YEARS AHEAD
THE CREDIT CARD CALCULATOR
SOLAR POWERED £6.00**

NEW PHILIPS SBC 1R33 Solar & Battery Powered Calculator **£10.00**

NEW PANELS

G8 100K Pots on Panel & Lead for 6 Push Button Unit	£2.00
K30 Mains Switch remote	£1.00
K35 Mains Switch remote	75p
K35 Aerial Socket and Plug in Lead to Tuner	£1.50
KT3-K30 Slider Pots 4.7k/47k	20p each
LARGE Foacs Pots Fits Pye, GEC, ITT, Decca	50p
G8 Power Supply Panel	£4.00
THORN 4000 LOPT Panel	£15.00
THORN 9000 Line Panel	£12.00
THORN 8000-8500-8800 Decoder	£10.00
GLASS BEADS Diodes 200v/1.2A	25 for £1.00
G11 IF Panel	£8.00
THORN 9600 Line Panel	£12.00
G11 Decoder Panel	£8.00
POWER SUPPLY 731	£6.00
G11 611 Condenser 470/250V ITT	£1.50
G9 Power Panel	£3.50
G8 Line Panel	£12.00
G8 6 Push Button	£9.00
KT4-KT3-K30 Handset Replacement	£8.00
HIT520 METER 20,000 Fuse Diode Protector Logic Test Facility	£15.90
9000 SERIES Decoder 01 929 014 080 Thorn	£5.00
THORN TX remot panel. 51.C. ML923-SL490-MC14528B-MC14493P-SL470 & Main Trans	£5.00
20AX GEC LOPT Panel with Split Diode	£4.00
LOPT Split Diode 2432871	£7.00
RANK T20 Fouces Pot	75p
RANK 718 Fouces Pot	£1.00
THORN 9000 LOPT Panel	£12.00
26' LOPT Split Diode 2432301	£8.00
16' LOPT Split Diode 2433481	£6.00
Ex Panel Split Diodes 2432871/2432981	£5
HITACHI Mains Switch	50p
HITACHI AE Socket	30p
-1 CONDENSER Axial Leads 450 A/C 1200 D/C	15p
MAINS TRANSFORMER 240v in/200v/8v	£1.00
GREEN FLAT, NEC, LED's	3p each 100 for £2
12+12V 2.8VA Print 1"x1"	75p
8+8V 1 Amp Print	75p
HITACHI 6 x 4 - 8Ω Speaker	50p
ET596 UHF V/CAP Tuner, small	£2.50
FIDELITY Panels with I.C.	£1.00
FIDELITY LOPT Split Diode AT2076/80	£3.00
FIDELITY FBS 1245AE LOPT Mono	£1.00
FIDELITY Split Diode FCC2015BE	£5.00
HI-FI MICROPHONE N8501 Philip	£8.00
G8 TUNER V/CAP on Panel	£3.50
G8 SPEAKER	75p
4000 TRIPLERS	£3.50
9,000 SPEAKER	£1.00
5 AMP METERS, AC, DC	£2.00
THORN 9000 Sound OP Panel	£30p
ONE I.C K35 Decoder	£7.00
THICK FILM, Hitachi RB-32 4A	£2.00
K30 IF/K35 IF	£3.00
THICK FILM, Hitachi Frame	£5.00
THORN Lopt 8500-8800	£4.00
TX9 THORN Tuner Panel with ICS Pots	£3.00
80 Ω THORN Speaker	15p
Split Diode 2433752	£6.00
BY223 Replacement	30p
THORN CHASSIS 1600-1700 Series Mono	£10.00
THORN 1600 Rec- & Anode Cap	50p
KT3-K30 Slider Pots 4.7k/47kC	£1.00 for 10
ET-614 UHF V/CAP Tuner	£2.00
6 x 2 1/4 SPEAKER 5W Hitachi 80	50p
K35 20 Turn Pots	50p each
HITACHI & GEC 20K Pots	20 for £1.00
KT3 K30 Speaker	30p
K35 Sound O/P Panel Plug in	£3.00
K35 12 way Push Button Unit	£1.50
K35 L.O.P.T. Split Diode	£6.00
RANK T20 Front Panel	£6.00
G8 6 Button Unit, New Type	£9.00
6 off LED DISPLAYS, Mixed	£1.00
HAND SET TESTER, Infra Red	£8.00
PHILIPS SBC 471 2 Way Stereo Headphone with Volume Controls	£17.00
AERIAL SPLITTER with filter	£1.00
DYNAMIC STEREO HEADPHONE EM 6146	£10.00
PHILIPS UNI DIRECTIONAL Dynamic Microphone	£10.00
20 TURN POTS with Band Switch	10p
PUSH BUTTON Mains Switch with Screw Holes Fixing	4 for £1
PYE 713 Line Trans	£4.50
PYE 731 Line Trans	£3.50
800v DIODES at 3 amps. Glass Beads	6p each, 20 for £1.00
PYE 6 Touch Button Unit for G11 with IC and Cable Forms	£10.00
KT3 Line Output Transformer	£5.00

SENDZ COMPONENTS

63 BISHOPSTEIGNTON,
SHOEBURYNES, ESSEX SS3 8AF.

SAME DAY SERVICE

All items subject to availability. No Accounts: No Credit Cards. Postal Order/
Cheque with order. Add 15% VAT, then £1 Postage. Add Postage for Overseas.
Callers: To shop at

212 LONDON ROAD, SOUTHEND. Tel. 0702-332992

Open 9-12.30-6. GVMT + school orders accepted on official headings. Add 10% handling charge.

CRICKLEWOOD ELECTRONICS LTD

FREE!
catalogue

SUMMER EDITION OUT NOW

It's no secret...

...that there is a *real difference* at *Cricklewood Electronics*. That's why you should never be without the *FREE CRICKLEWOOD ELECTRONICS COMPONENTS CATALOGUE*, for sheer variety, *competitive prices* and *service* from the U.K.'s number one 100% component shop. No gimmicks, no gadgets or computers, just components, millions of them, all easily available by mail order, calling or credit card telephone orders. Just pick up the phone (or a pen) to get your *FREE* copy now (no SAE required). You have nothing to lose.

CRICKLEWOOD ELECTRONICS LIMITED

40 Cricklewood Broadway, London NW2 3ET

Tel: 01-450 0995/01-452 0161

Telex: 91 4977




TV



SADELTA

TV COLOUR PATTERN GENERATOR MODEL PAL MC 11B UK

THE SADELTA TV HAND HELD COLOUR PATTERN GENERATOR is intended for use in production, installation and service of both colour and monochrome TV sets. In order to control and adjust the various parameters of the colour TV, eight switchable patterns are provided. The technician has ready access to laboratory workshop and field use as the generator has been designed using the latest micro technology to achieve a truly pocket size instrument.

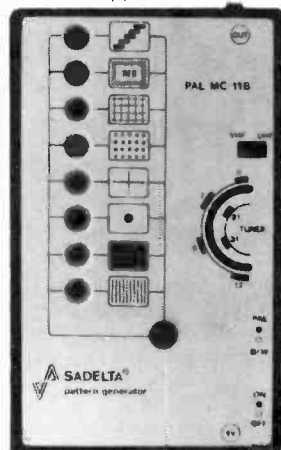

FEATURES

- PAL System I
- Eight switchable patterns:— colour bar, grey scale, red, crosshatch, dots, centre cross, centre dot, white and vertical lines.
- Sound output.
- Band IV (21-34) Band III (5-12)
- Output 10mV into 75 Ohms.
- Internal rechargeable Ni-Cd battery.
- Supplied with soft carry case and 9 volt power supply/charger.
- Pocket size 131 x 81 x 23mm.
- Weight only 250 gms.

PRICE £124.95 + £18.74 VAT

Also available to special order SECAM, Video Composite, and R.G.B. versions. Details available upon request.

U.K. POST PAID, export enquiries welcome, Visa/Access or cheque with order, payable to B.K. Electronics. Official orders welcome from Govt. Depts., Colleges, P.L.C.s etc. Large S.A.E. for technical leaflets of complete range delivery normally within 7 days.

B. K. ELECTRONICS Dept. 'T'

UNIT 5, COMET WAY, SOUTHEND-ON-SEA,

ESSEX. SS2 6TR TEL: 0702-527572

HITACHI VHS COLOUR CAMERAS

Mains Only Tested/
Working

VHS VIDEOS

FERGUSON

3V00, 3V22, 3V23, 3V16, 3V29,
3V30, 3V31, 3V32, 3V35

NATIONAL PANASONIC
NV8600, 8610, 2000, 7000,
370, 333, 2010

SHARP

620, 630, 640, 2300 H T/P

BETAMAX

SANYO VTC 9300, 5000, 5300

SONY C5, C6, C7, C9
and SL F1UB T/P

Also Bush, Toshiba, Hitachi and Blau Punkt

PLUS

17" 18" 20" 22" 26" Hybrid/
Solid State CTVs

Remote Control & Teletext

Discount for Quantities

Complete loads delivered from pick up point

**JOHN CARTER
(Electrical) LTD
FURNACE ROAD,
GALLOWES INN,
ILKESTON**

Phone: 0602 303124

CINEMA VISION PROJECTION UNITS

★ ★ ★ ★

Philips, Grundig,
Toshiba, National
Panasonic and ITT. 40",
45" and 78" screens.

Floor and suspended
models. New boxed and
used. Quantity of test
equipment.

Oscilloscopes, cross
hatch – pattern – colour
match – colour bar –
and signal generators.

Avo and Taylor test
meters. Televerters slot
meters.

RADIO TELEPHONE SYSTEMS

★ ★ ★ ★

**John Carter (Electrical) Ltd.,
Furnace Road,
Gallows Inn,
Ilkeston,
Derbyshire.
Phone 0602 303124**

AA117	9p	BC337	6p	BF184	20p	BFY57	26p	TP32A	24p	2N.1131	28p	BY296	20p	7818	35p	PC1805	55p	LA-4461	180p	TBA560	100p	74LS22	17p
AA119	9p	BC338	6p	BF185	20p	BFY64	26p	TP32C	24p	2N.1132	28p	BY298	20p	7824	35p	PFL200	55p	LA-5112	120p	TBA750	100p	74LS24	38p
AA132	9p	BC357	6p	BF194	20p	BFY90	45p	TP33	24p	2N.1613	24p	BY299	20p	7905	35p	PL36	80p	LM301	26p	TBA900	35p	74LS26	17p
AC107	25p	BCY32	180p	BF196	6p	BLV49	85p	TP34	50p	2N.1711	24p	BY478	90p	7812	40p	PL82	45p	LM311	35p	TBA105	60p	74LS27	17p
AC126	17p	BCY42	20p	BF198	7p	BR100	14p	TP41A	22p	2N.2102	50p	BYX10	15p	7915	40p	PL83	45p	LM324	35p	TBA200	100p	74LS28	17p
AC127	15p	BCY44	150p	BF199	7p	BR101	43p	TP42A	22p	2N.2160	300p	BYX55/350	30p	7918	40p	PL84	50p	LM334	35p	TBA250	100p	74LS29	17p
AC128	15p	BCY45	20p	BF200	7p	BR102	43p	TP42B	22p	2N.2218A	24p	BYX55/600	30p	7924	40p	PL95	140p	LM335	45p	TBA290	100p	74LS30	17p
AC129K	15p	BCY56	18p	BF201	7p	BSX26	18p	TP42C	22p	2N.2219	24p	BYX70/300	25p	7812	25p	PL96	140p	LM338	45p	TBA300	100p	74LS31	17p
AC141K	30p	BCY71	18p	BF240	15p	BSX29	18p	TP47	40p	2N.2221	23p	BYX70/500	32p	7815	28p	PL98	170p	LM348	60p	TBA350	100p	74LS33	17p
AC142K	30p	BCY72	18p	BF241	15p	BSX29	18p	TP48	40p	2N.2222	23p	BYX70/500	32p	7818	28p	PL99	170p	LM380	100p	TCA800	200p	74LS37	17p
AC153K	23p	BD115	26p	BF255	12p	BSX29	18p	TP50	60p	2N.2369	16p	BYX70/900	36p	7818	28p	PL99	170p	LM381	150p	TCA900	100p	74LS38	17p
AC156	18p	BD136	20p	BF256	12p	BT109	90p	TP52	120p	2N.2484	18p	BYX70/1600	80p	7815	28p	PL99	170p	LM382	150p	TDA1170	100p	74LS40	17p
AC176K	20p	BD142	19p	BF257	12p	BT110	90p	TP53	120p	2N.2646	40p	OAA7	60p	7815	28p	PL99	170p	LM383	150p	TDA1170	100p	74LS42	35p
AC187	15p	BD124	110p	BF257	12p	BT116	80p	TP53	120p	2N.2904	20p	OAA9	40p	7912	45p	PL99	170p	LM384	150p	TDA2002	100p	74LS47	60p
AC187K	20p	BD128	35p	BF258	18p	BT119	100p	TP54	140p	2N.2905	20p	OAA9	40p	7915	48p	PL99	170p	LM385	150p	TDA2003	100p	74LS48	60p
AC188	17p	BD131	25p	BF259	18p	BT120	100p	TP55	140p	2N.2906	20p	OAA9	40p	7915	48p	PL99	170p	LM386	150p	TDA2004	100p	74LS49	60p
AC188K	23p	BD136	20p	BF263	18p	BU100	100p	TP106	65p	2N.2907	18p	OAA20	7p	7812	40p	PL99	170p	LM387	150p	TDA2005	100p	74LS51	17p
ACY18	48p	BD135	20p	BF263	18p	BU104	100p	TP107	65p	2N.2926	6p	IN.914	2p	7812	40p	PL99	170p	LM388	150p	TDA2006	100p	74LS52	17p
ACY19	48p	BD136	20p	BF270	18p	BU105	80p	TP110	47p	2N.3019	28p	IN.4001	4p	7812	40p	PL99	170p	LM389	150p	TDA2007	100p	74LS53	17p
AD142	19p	BD138	20p	BF273	18p	BU108	80p	TP111	47p	2N.3053	18p	IN.4002	4p	7812	40p	PL99	170p	LM390	150p	TDA2008	100p	74LS54	17p
AD149	48p	BD139	20p	BF273	18p	BU110	110p	TP112	40p	2N.3054	35p	IN.4003	4p	7812	40p	PL99	170p	LM391	150p	TDA2009	100p	74LS55	17p
AD161	22p	BD139	20p	BF284	25p	BU111	140p	TP115	45p	2N.3055	35p	IN.4004	4p	7812	40p	PL99	170p	LM392	150p	TDA2010	100p	74LS56	17p
AD162	22p	BD140	20p	BF336	20p	BU124	60p	TP116	45p	2N.3055H	18p	IN.4005	4p	7812	40p	PL99	170p	LM393	150p	TDA2011	100p	74LS57	17p
AF124	25p	BD144	90p	BF337	20p	BU126	70p	TP117	45p	2N.3440	58p	IN.4006	4p	7812	40p	PL99	170p	LM394	150p	TDA2012	100p	74LS58	17p
AF125	25p	BD157	38p	BF355	20p	BU205	70p	TP120	43p	2N.3442	85p	IN.4007	6p	7812	40p	PL99	170p	LM395	150p	TDA2013	100p	74LS59	17p
AF126	25p	BD158	38p	BF356	20p	BU205	70p	TP121	43p	2N.3702	9p	IN.4008	6p	7812	40p	PL99	170p	LM396	150p	TDA2014	100p	74LS60	17p
AF127	25p	BD159	38p	BF357	20p	BU205	70p	TP122	43p	2N.3703	9p	IN.4009	6p	7812	40p	PL99	170p	LM397	150p	TDA2015	100p	74LS61	17p
AF128	25p	BD166	30p	BF367	13p	BU208	70p	TP123	43p	2N.3704	9p	IN.4010	6p	7812	40p	PL99	170p	LM398	150p	TDA2016	100p	74LS62	17p
AF129	25p	BD177	30p	BF374	17p	BU208	70p	TP124	43p	2N.3705	9p	IN.4011	6p	7812	40p	PL99	170p	LM399	150p	TDA2017	100p	74LS63	17p
AF139	22p	BD177	30p	BF374	17p	BU208	70p	TP125	43p	2N.3706	9p	IN.4012	6p	7812	40p	PL99	170p	LM400	150p	TDA2018	100p	74LS64	17p
AL112	70p	BD177	30p	BF374	17p	BU208	70p	TP126	43p	2N.3707	9p	IN.4013	6p	7812	40p	PL99	170p	LM401	150p	TDA2019	100p	74LS65	17p
AL113	80p	BD177	30p	BF374	17p	BU208	70p	TP127	43p	2N.3708	9p	IN.4014	6p	7812	40p	PL99	170p	LM402	150p	TDA2020	100p	74LS66	17p
AS125	100p	BD177	30p	BF374	17p	BU208	70p	TP128	43p	2N.3709	9p	IN.4015	6p	7812	40p	PL99	170p	LM403	150p	TDA2021	100p	74LS67	17p
ASZ17	100p	BD181	45p	BF421	21p	BU325	55p	TP127	43p	2N.3710	9p	IN.4016	6p	7812	40p	PL99	170p	LM404	150p	TDA2022	100p	74LS68	17p
AU110	110p	BD182	45p	BF422	21p	BU325	55p	TP128	43p	2N.3711	8p	IN.4017	6p	7812	40p	PL99	170p	LM405	150p	TDA2023	100p	74LS69	17p
AY102	180p	BD183	45p	BF423	21p	BU400	75p	TP129	43p	2N.3712	9p	IN.4018	6p	7812	40p	PL99	170p	LM406	150p	TDA2024	100p	74LS70	17p
BA145	10p	BD187	30p	BF440	19p	BU407	75p	TP130	43p	2N.3713	10p	IN.4019	6p	7812	40p	PL99	170p	LM407	150p	TDA2025	100p	74LS71	17p
BA145	10p	BD187	30p	BF440	19p	BU407	75p	TP131	43p	2N.3714	10p	IN.4020	6p	7812	40p	PL99	170p	LM408	150p	TDA2026	100p	74LS72	17p
BA148	10p	BD202	38p	BF455	19p	BU408	75p	TP132	43p	2N.3819	18p	IN.4021	6p	7812	40p	PL99	170p	LM409	150p	TDA2027	100p	74LS73	17p
BA154	6p	BD204	42p	BF459	19p	BU426	120p	TP133	43p	2N.3903	11p	IN.4022	6p	7812	40p	PL99	170p	LM410	150p	TDA2028	100p	74LS74	17p
BA157	12p	BD222	31p	BF461	62p	BU426	120p	TP134	43p	2N.3904	11p	IN.4023	6p	7812	40p	PL99	170p	LM411	150p	TDA2029	100p	74LS75	17p
BB101	13p	BD225	31p	BF462	62p	BU500	110p	TP135	43p	2N.3905	11p	IN.4024	6p	7812	40p	PL99	170p	LM412	150p	TDA2030	100p	74LS76	17p
BB103	13p	BD232	31p	BF463	62p	BU500	110p	TP136	43p	2N.3906	11p	IN.4025	6p	7812	40p	PL99	170p	LM413	150p	TDA2031	100p	74LS77	17p
BB105B	18p	BD234	32p	BF470	28p	BU500	110p	TP137	43p	2N.3907	11p	IN.4026	6p	7812	40p	PL99	170p	LM414	150p	TDA2032	100p	74LS78	17p
BB205B	24p	BD235	32p	BF471	28p	BU500	110p	TP138	43p	2N.4031	25p	IN.4027	6p	7812	40p	PL99	170p	LM415	150p	TDA2033	100p	74LS79	17p
BC107	7p	BD236	30p	BF479	30p	BU500	110p	TP139	43p	2N.4032	25p	IN.4028	6p	7812	40p	PL99	170p	LM416	150p	TDA2034	100p	74LS80	17p
BC108	7p	BD237	30p	BF483	30p	BU500	110p	TP140	43p	2N.4033	25p	IN.4029	6p	7812	40p	PL99	170p	LM417	150p	TDA2035	100p	74LS81	17p
BC109	7p	BD238	24p	BF494	16p	BU500	110p	TP141	43p	2N.4034	25p	IN.4030	6p	7812	40p	PL99	170p	LM418	150p	TDA2036	100p	74LS82	17p
BC115	10p	BD244	50p	BF595	18p	MJ2500	100p	TP142	43p	2N.4443	75p	IN.4031	6p	7812	40p	PL99	170p	LM419	150p	TDA2037	100p	74LS83	17p
BC118	11p	BD245	50p	BF596	18p	MJ2501	110p	TP143	43p	2N.4444	75p	IN.4032	6p	7812	40p	PL99	170p	LM420	150p	TDA2038	100p	74LS84	17p
BC140	19p	BD433	28p	BF597	18p	MJ2555	55p	TP144	43p	2N.5061	20p	IN.4033	6p	7812	40p	PL99	170p	LM421	150p	TDA2039	100p	74LS85	17p
BC141	19p	BD434	30p	BF615	30p	MJ3001	115p	TP145	43p	2N.5296	30p	IN.4034	6p	7812	40p	PL99	170p	LM422	150p	TDA2040	100p	74LS86	17p
BC142	19p	BD435	31p	BF758	41p	MJE29A	30p	TP146	43p	2N.6106	40p	IN.4035	6p	7812	40p	PL99	170p	LM423	150p	TDA2041	100p	74LS87	17p
BC143	19p	BD437	28p	BF869	22p	MJE29A	30p	TP147	43p	2N.8107	11p	IN.4036	6p	7812	40p	PL99	170p	LM424	150p	TDA2042	100p	74LS88	17p
BC147	6p	BD438	38p	BF870	22p	MJE340	25p	TP148	43p	2N.8109	11p	IN.4037	6p	7812	40p	PL99	170p	LM425	150p	TDA2043	100p	74LS89	17p
BC148	6p	BD439	40p	BF872	22p	MJE350	80p	TP149	43p	2N.128	55p	IN.4038	6p	7812	40p	PL99	170p	LM426	150p	TDA2044	100p	74LS90	17p
BC149	6p	BD440	40p	BF89																			

SIGHT & SOUND

185 UTTOXETER ROAD, LONGTON, STOKE-ON-TRENT

STOKE-ON-TRENT 0782 335262

FERGUSON 3V23
NAT-PAN 7200
NAT-PAN 366
HITACHI 8600
HITACHI
NAT-PAN 2010

Factory Reconditioned
Infra Red Video
Cord Remote Video
Infra Red Video
Cord Remote Video
Basic Video

G11
T-20
THORN 9600
G11 TEXT
COLOUR PORTABLES
THORN 9000

200 Always in Stock
100 Always in Stock
Always in Stock
100 in Stock
In Stock
Always in Stock

SATISFACTION GUARANTEED

FRIENDLY SERVICE – NO GIMMICKS

PERSONAL ATTENTION – ASK FOR JOHN SAHOTA

D.I.Y. TV TUBE POLISHING

with our DIY Polishing Kit

The Kit includes everything you need to polish approx. 25" tubes to a high standard. Detailed instructions on how to do the polishing. All you require is an Electric Drill.

Kit Price £49 inc P&P and VAT. Available from Luton only.

**Depends on depth and area to be polished.*

TV TUBES FREE DELIVERY*

5% DISCOUNT ON TUBES COLLECTED FROM LUTON

Quality, High Temperature Reprocessing

TUBE SIZE	DELTA i.e. A51-110X A56-120X A66-120X A67-120X	DELTA SPECIALS i.e. A47-342X 470CTB22 510GLB22 A56-410X A66-410X A67-150X A67-200X	IN LINE & P/L i.e. 470ESB22 470ERB22 A51-161X A51-570X 510JKB22 560AKB22 A56-510X A66-510X	HITACHI IN LINE etc. AXT37-001 AXT51-001 AXT56-001 510VAB22 510VLB22 510VSB22 A51-421X A51-426X A51-580X A51-590X A51-610X A51-701X	HITACHI IN LINE etc. A56-540X A56-615X A56-711X 560BYB22 560DYB22 560ZB22 560FGB22 560GAB22 A66-540X A67-711X	SONY TRINITRON 330AB22 400FB22 470EB22 470DLB22 470FWB22 520KB22 520NB22 520SB22 570EB22 570HB22 680DB22 680EB22
UP TO 20"	£30	£32	£40	£44	£44	£58
UP TO 22"	£34	£36	£42	£46	£46	£64
UP TO 26"	£36	£38	£44	£48	£48	£70

Tube types not listed, please enquire.

All tubes sold with 1 or 2 year guarantee, with optional extension by extra 2 years. Prices shown are for 12 months guarantee. All tubes exchange glass required.

Your good, working tubes with scratches or small chips, can be POLISHED with our purpose built polishing equipment. From £7 per tube.

Delivery charge on colour tubes: Within 40 miles of Luton.

1 or 2 tubes £6. 3 or more tubes FREE DELIVERY*

Nationwide delivery available, charges on application.

Please add 15% VAT to all prices. Callers welcome. Please phone first.

WELL VIEW

114-134 Midland Rd,
Luton, Beds.

Open Mon-Fri 8am-6pm, Sat 9am-1pm. Tel. 0582-410787.

Your Local Tube Stockist:

Well View, Southampton. Tel. 0703 331837.

H. K. Television, London, E.2. Tel. 01-729 1133.

West One Distributors Ltd., Gt. Missenden, Buckinghamshire.

Tel. 024 06 3609

Rushden Rentals Ltd., Rushden, Northants. Tel. 0933 314901

Rea & Holland, Ipswich, Suffolk. Tel. 0473 827562.

Phone between 12-2p.m., & 6-9 p.m.

WANTED A56/A66-510X/540X, Hitachi and Sony, old glass for cash

BOLTEN LTD.

45/46 London House,
271, King Street, London W6 9LZ.
Tel: 01-748 4137 (2 lines)
Telex: 262421 BOLTEN G

Video Heads

Sony C5/C7/T7	£31.95
Ferguson/JVC (Universal)	£30.95
National Panasonic (Universal)	£30.95
National Panasonic (370/380)	£33.95
Hitachi	£33.95
Sanyo	£44.95
Fisher VHS Genuine	£51.95
Akai (most Models)	£30.95
Sharp	£44.95

Heads suitable for many other Brands also available. Please call for full list.

Belt Kits (Most Models)	£3.99
Remote Controls for T.V.	
Grundig/Philips	£16.95
Video Cable Kit (any model to any model)	£7.50
Pinch Wheels (Various Models)	£5.95

Please add 15% VAT plus £1.00 p&p per order.

Delivery within 7-14 days
subject to availability



LONDON'S LARGEST
TELEVISION WHOLESALE...
with over 4½ thousand sq. feet

"TELEMANN"



8-10 RHODA STREET (off Bethnal Green Road)

LONDON E2. FREE CAR PARK

SPECIAL OFFER!!

Parcel of 25 Monos	£1.00 each
Parcel of 10 Philips 22" G8 550	£15.00 each
Parcel of 10 Decca Bradfords (6 buttons)	£12.00 each
Parcel of 10 Japs Colour	£20.00 each

LORRY LOADS DELIVERED DIRECT FROM SUPPLIERS
NO CHARGE FOR DELIVERY IN THE LONDON AREA!

01-739 2707 → 2 LINES ← 01-739 3123

FREE CAR PARK + NO YELLOW LINES OUTSIDE!

TUNERS + TUNERS

- ★ If you repair sets regularly – phone us today and we will dispatch immediately – no need to send cash 'up front'.
- ★ All tuners dispatched by first class post for receipt by you the next day.
- ★ All popular tuners/tuner repairs supplied 'off the shelf'.
- ★ Unusual types repaired same day as received (subject to spares availability).

TELEPART

32 Temple Street,
Wolverhampton WV2 4LJ.
Phone: (0902) 29022.

OSCILLOSCOPES COSSOR CDU150. Dual Trace 35MHz Solid State. Portable 8x10cm display. With Manual £200 TELEQUIPMENT D61 Dual Trace 10MHz With Manual £150 ADVANCE OS250TV. Dual Trace 10MHz With Manual £160 S.E. LABS SM111. Dual Trace 18MHz Solid State. Portable AC or External DC operation 8x10cm display. With Manual £150 TELEQUIPMENT D43. Dual Trace 15MHz. With Manual £100 TELEQUIPMENT S54A. Single Trace 10MHz. Solid State. With Manual £110 TELEQUIPMENT S43 Single Trace 25MHz With Manual £75	LABGEAR COLOURMATCH PATTERN GENERATOR Type CM6038-DB Crosshatch/Grey Scale/Blank Raster. Mains or Battery. ONLY £12 each (P&P £2)
PHILIPS DIGITAL MULTIMETERS 4 digit, auto ranging. Complete with batteries and leads (p&p £5) TYPE PM2517X (LCD) £75	ADVANCE AM/FM SIGNAL GENERATOR Type SG63A 7.5-230MHz £75 ADVANCE AM SIGNAL GENERATOR SG62B. 150 KHz-220MHz £45 ADVANCE AM SIGNAL GENERATOR Type 62. 150KHz-220MHz £30 METRIX WOBBLATOR Type 210. 5-220MHz £20 PHILIPS WOBBLATOR GM2877S 5-220MHz & 440-880MHz £100 LABGEAR COLOUR BAR GENERATOR CM6037 (P&P £4) £60 VIDEO CIRCUITS V31A CRT ANALYSER/BOOSTER (Scratched Case) £50 WAYNE KERR COMPONENT BRIDGE B521 (CT375) 100uH-500KHz; 1pF-5F; 1 milliohm-1000Mohm £35 RACAL 32MHz UNIVERSAL COUNTER TIMER Type 836 with Manual £50 MARCONI TF2604 (Later version of TF 1041 VTVM) 20Hz-1500MHz; AC/DC/Ohms AC 300mV-300V FSD £80 MARCONI VALVE VOLTMETER TF2600 10Hz-10MHz; 1mV-300V FSD £40 PHILIPS COLOURBAR GENERATOR type 5501 (P&P £5) £100 PHILIPS COLOURBAR GENERATOR type 5508. Video out. Many Functions £125 TES FIELD STRENGTH METER type HC661 in Carrying Case (P&P £5) £80
MULTIMETERS AVO 9 Mk4 (Identical to AVO 8 Mk4 but scaled differently) Complete with Batteries & Leads. £55 AVO 8 Mk2 Complete with Batteries & Leads £45 Above Items in GOOD WORKING ORDER - appearance not A1 hence the price. AVO TEST SET No 1 (Military version of AVO 8) Complete with batteries, leads & Carrying Case £65 AVO Model 7x. Complete with batteries, leads & carrying case £40 AVO Model 73. Pocket Multimeter (Analogue) 30 ranges. Complete with batteries & leads £18 AVO 72 - Similar to above but no AC current range. With batteries & leads £10	ISOLATING TRANSFORMER 240V In - 240V Out 500VA £15 each P&P £5 240V In - 240V Out 200VA £8 each P&P £3
AVO TRANSISTOR TESTER TT169 Handled. GO/NO GO for In-situ Testing. Complete with batteries, leads & instructions. (p&p £3) NOW ONLY £12	NEW EQUIPMENT HAMEG OSCILLOSCOPE 605. Dual Trace 60MHz. Delay Sweep. Component Tester £515 HAMEG OSCILLOSCOPE 203.5. Dual Trace 20MHz. Component Tester £270 All Other Models Available.
PROFESSIONAL 9" GREEN SCREEN MONITORS made by KGM for REUTERS Gives quality 80 column x 24 line display. Composite video in. Cased. Good condition ONLY £32 each DISK DRIVE PSU.240V 1H; 5V 1.6A & 12V 1.5A out. Size: W125mm, H75mm, D180mm. Cased. Un-used. Only £10.00 each (P&P £2) Querty keyboard (as in Lynx Micro). Push to make. Cased £5 each (P&P £2) Various 5 1/4" Floppy Disk Drives and Stepping Motors Available.	BLACK STAR FREQUENCY COUNTERS P&P £4 Meteor 100 - 100MHz £99 Meteor 600 - 600MHz £125 Meteor 1000 - 10GHz £175 BLACK STAR JUPITOR 500 FUNCTION GENERATOR. Sine/Square/Triangle. 0.1Hz - 500KHz. P&P £4 £110 HUNG CHANG DMM 6010. 3 1/2 digit. Hand held 28 ranges including 10 Amp AC/DC. Complete with batteries & leads. P&P £4 £33.50 OSCILLOSCOPES PROBES. Switched x1; x10. P&P £2 £11
This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for Lists. Please check availability before ordering. CARRIAGE all units £12. VAT to be added to Total of Goods & Carriage.	
STEWART OF READING 110 WYKHAM ROAD, READING, BERKS RG6 1PL Telephone: 0734 68041 Callers welcome 9 am-5.30 pm Mon.-Fri. (until 8 pm Thurs.)	

BRITAIN'S LARGEST SUPPLIERS

OF

Ex RENTAL TV & VIDEOS

OVER 1500 ARRIVING WEEKLY

*Makes inc. PHILIPS, GEC,
HITACHI, ITT, BUSH,
PANASONIC, SONY, DECCA,
FERGUSON, GRUNDIG etc.*

COLOUR TV from £5
VIDEO RECORDERS from £40

CALL & SEE OUR SELECTION
DELIVERY ARRANGED FOR
BULK PURCHASES
LOAD DIRECT FROM SOURCE
AT VERY KEEN PRICES

FRANK FORD
(TV TRADE DISPOSALS)
SCHOOL LANE
GUIDE
BLACKBURN, LANCs
TEL: 0254 64489

CREWE WHOLESALE TV

77 COLERIDGE WAY, CREWE

Tel: 0270 582924

G11s working £50

GEC. from £11

Delivered in Bulk

BUSH T20 T22 and 24s

ITT CVC 20 Upwards

Series 3 DORIC

working from £40

Remote + Text Available

Large range of

THORN from 8800 upwards.

Price and availability on request

**CASH ONLY UNLESS BY
PRIOR ARRANGEMENT**

ALL PRICES + 15% VAT

HOCKLEY DISCOUNT TELEVISIONS

We give "The Best Deals" that's why we have the cleanest reputation in the trade!!!

Prices start From **£6.00** Working sets From **£12.00**

OR

Lorry loads delivered from **SOURCE**

We have huge stocks of TV's + V.H.S. Videos to offer, including:-

Philips G8's, G11's Thorn 8000, TX9,
 Pye Solid State 9000, 9600, TX10,
 Pye Chelsea Latest Hitachi
 G.E.C. Solid State I.T.T. CVC30, CVC45,
 Rediffusion MkI, MkIII Bush T20, T22

ALSO

VIDEO + T.V. STANDS AVAILABLE!

DON'T HESITATE TO CONTACT US BECAUSE YOU WILL NEVER LOOSE!!

MIDLANDS BRANCH:-
Hockley Discount Televisions,
 94 Soho Hill, Hockley, Birmingham B19 1AE.
 021-551-2233 - Ask for Jazz



NORTH-EAST BRANCH:-
Northern TV Distributors, Unit 2, Pert Court,
 11th Ave, Team Valley,
 Gateshead, Tyne & Wear.
 091-487-5389 - Ask for Joe




DISPLAY ELECTRONICS LTD.



- ★ Do you use cathode ray tubes?
- ★ Can't find a replacement or shocked by the cost?
- ★ It may well be that a rebuilt tube will solve your problem.

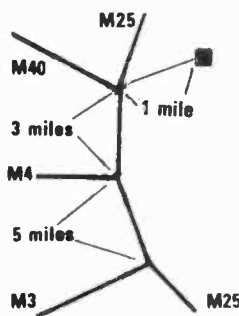Come to one of the most experienced firms in the business. We have been rebuilding cathode ray tubes for industry, broadcasting authorities, major airlines, M.O.D. universities, and, of course, the TV trade in general since the '60's.



WE ARE LOCATED IN UXBIDGE

At probably the most accessible part of S.E. England. The nearest junction of the M25 is only about 1 mile away and we are less than 10 minutes from the interchanges on the M25/M3, M25/M4, M25/M40.

Why not telephone Terry Smith on Uxbridge (0895) 55800, to discuss your requirements?

DISPLAY ELECTRONICS LTD.

UNIT 4, SWAN WHARF,
 WATERLOO ROAD,
 UXBIDGE, MIDDLESEX.

CentreVision

TEL: 0222-44754

SLOPER ROAD, LECKWITH, CARDIFF CF1 8AB
 OPPOSITE CITY FOOTBALL GROUND, 5 MINS FROM M4

FERGUSON VHS VIDEO £65

MANY ELECTRONIC VIDEOS IN STOCK

MANY TOP QUALITY REMOTE CONTROL WORKING TV's

PHONE FOR LATEST PRICES

PRICES SUBJECT TO VAT

OPENING HOURS:

MONDAY - FRIDAY 9.00 - 5.30; SATURDAY 9.00 - 1.00

MAIL ORDER ADVERTISING

British Code of Advertising Practice

Advertisements in this publication are required to conform to the British Code of Advertising Practice. In respect of mail order advertisements where money is paid in advance, the code requires advertisers to fulfil orders within 28 days, unless a longer delivery period is stated. Where goods are returned undamaged within seven days, the purchaser's money must be refunded. Please retain proof of postage/despatch as this may be needed.

Mail Order Protection Scheme

If you order goods from Mail Order advertisements in this magazine and pay by post in advance of delivery, Television will consider you for compensation if the Advertiser should become insolvent or bankrupt provided:

- (1) You have not received the goods or had your money returned; and
- (2) You write to the Publisher of Television summarising the situation not earlier than 28 days from the day you sent your order and not later than two months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the Advertiser has been declared bankrupt or insolvent.

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine not for example, payment made in response to catalogues etc., received as a result of answering such advertisements. Classified advertisements are excluded.

THE WORLD OF . . . "TELEPANELS"

52 Mount Pleasant Road, Chigwell, Essex, 1G7 5ER. Tel: 01-729 0506.



WORKING
PANELS
GALORE!

GRAND OPENING OFFER SUPER WORKING PANELS

FOR THE PHILIPS G11

P+P 1 PANEL £1.75
2 PANELS OR MORE
£3.50

N.B. All panels
despatched by
recorded delivery
to avoid loss.

	IF	TUNER	DECODER	G8/G9 DECODER IF COMBINED	LINE OUTPUT	POWER	CONVERG	FRAME	VIDEO	6 WAY TUNER SWITCH BANK
PHILIPS G.8	5.00	4.50	7.00	15.00	14.00	8.00	5.00	8.00		3.50
THORN 3000/3500	2.00	5.75	4.00		8.00	8.00	5.00	6.00	5.00	1.75
GEC 2110	10.00		5.00		12.00	6.00	5.00	5.00	5.00	5.00
PYE 731			10.00		18.00	10.00	7.00	8.00		4.50
BUSH Z/718	7.50	6.50	14.00		24.00	3.00	5.00	14.00		
BUSH T/20	7.50	6.50	14.00		19.00	19.00	5.00	14.00		
PHILIPS G11	14.50 WITH COMBINED SOUND MODULE		12.00		19.00	19.00	5.00	11.50		
DECCA 80	12.00	POA	14.00		12.00	10.00		14.00		POA

POST OFF YOUR CHEQUE NOW! AND YOUR PANELS SENT BY RETURN OF POST!!!

N.G.T. COLOUR TUBES

First Independent Rebuilder with
B.S.I. CERTIFICATION

DELTA - IN-LINE - PIL - BONDED YOKE
including

AXT Series, DZB series 20AX - 30AX
A56 610/67 610 series, A51 570/580/590X
A51 161X, Sony types etc.

- ★ Rebanded with new adhesives
- ★ Excellent high voltage clean-up
- ★ Accurate alignment of Gun and Yoke for optimum convergence

N.G.T. ELECTRONICS LTD.,
120 SELHURST ROAD, LONDON SE25
Phone: 01-771 3535.

25 years experience in television tube rebuilding.

APOLLO LANCASHIRE

MAIL ORDER GB 3-4 DAYS PHONE FOR COST SONY TYPES
LOCAL DELIVERY - 2 YR GUARANTEE - PILL GLASS BOUGHT

PORTABLES. 37-590, AXT 37001, 370HUB, NEW £65 INC. DELIVERY

A47 342/343X - 470 BC822/CTB22/BGB22/DHB22	£39
470-ESB22/EFB22/ERB22/FTB22	£53
A51-220X/192X	£39
A51-161X/162/163/168	£53
510-JKB22/JEB22/JDB22/JGB22/ALB22/GLB22	£53
510-VLB22(E55) DTB22/001/RFB22/RGB22/SFB22	£53
A51-590 New	£55
A51-570X/580/001/210/241	£53
A56-120X/123/140/410	£39
560-DZB22(E56)/1-B22/AKB22/TB22/AWB22	£55
560-ETB22/DTB22/CSB22/DMB22/DNB22	£53
A56-611X/615X	£53
A66-120X/A67-120X/140/150/200/410	£39
20AX - A56-500X, 510X - A66-500X/510X	£53
30AX - A56-540X - A66-540X	£56

PLEASE PHONE BEFORE CALLING
LOCAL DELIVERY FROM ACCRINGTON, LANCS.

Phone enquiries and letters to:

Apollo, The Potters Wheel,
Mullion Cove, Mullion, Nr. Helston, TR12 7ET.
0326 240781

SPECIAL ANNOUNCEMENT

From:

NORGROVE TV TRADE SERVICES
Water Street, Birmingham B4 6BJ.

Hundreds of TVs and Videos arriving weekly.
Available for sale to the trade.

Most makes in stock including the full
Thorn range, RBM, Philips, Pye, ITT,
Hitachi, Sony, Panasonic, Sharp, Sanyo,
Decca and many others.

Spares available. Deliveries arranged.
Export enquiries welcome.

OPEN SUNDAYS BY APPOINTMENT.

For quotation. Please ring:

021 236 9616

SETS & COMPONENTS

NEW AND SECONDHAND COLOUR TV SPARES.
Panels & Tubes most makes also panel repair service.
Tel. Southport (0704) 74411 anytime (24hr).

GRUNDIG 2x4 SUPER VIDEO remote control VIF-K1 with tele-pilot TPV355. Brand new, boxed. £12.95 p&p £2 (plugs straight in). STAN WILLETTS, 37 High Street, West Bromwich, West Midlands B70 6PB. Tel. 021 553 0186.

CASH PAID Now for your surplus TV spares, transistors, I.C.'s etc. Tel. MR. FORSHAW, 0902 29022.

SPECIAL OFFER New Samsung 14" TV tubes suitable for Fidelity CTV 14R etc and Ferguson TX9. £45 plus VAT complete with scan-coil. Telephone 0204 40918/0254 31934.

GENUINE GRUNDIG SPARES. Fast helpful service. Sensible prices. TELEQUIPMENT PHILIPS Oscilloscopes. Test equipment, manuals. OCHRE MILL TECHNICAL. Stone 0785 814643.

REDIFFUSION SPARES AND PANELS for Mk3 and Mk4 etc, mostly new and refurbished. Approx. 25 large cartons. £1,500. TELESCENE, Nottingham 0602 291665.

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO, 103 South Brink, Wisbech, Cambs. 0945 584188. Immediate settlement.

NORTHERN IRELAND Mechanical videos, VHS, working. Telephone Keady 538604.

HITACHI, MITSUBISHI, Panasonic, Sony, Toshiba, JVC, Sharp, fully refurbished. PEARSON TELEVISION 0484 863489. Delivery arranged.

WIZARD DISTRIBUTORS MANCHESTER TV & VIDEO SPARES

We stock spares for THORN, PHILIPS, PYE, RANK, GEC, SHARP, SONY, DECCA + ITT.

FIDELITY SPARES MAIN DISTRIBUTOR.

Did you know we also stock

FUSES	I.Cs
TUBES	TOOLS
AERIALS	VIDEO LEADS
AEROSOLS	AUDIO LEADS
RESISTORS	SEMICONDUCTORS
CAPACITORS	SERVICE MANUALS
VALVES	TEST EQUIPMENT
HANDSETS	TV/VIDEO TROLLEYS
AND MUCH MORE	

Counter open Monday-Friday 9am-4.45pm

TRADE ONLY

**EMPRESS STREET WORKS,
EMPRESS STREET,
MANCHESTER M16 9EN.**

Tel: 061-872 5438; 061-848 0060.

PRECISION VISION LTD.

For:

- ★ LATE MODEL USED COLOUR TVs
- ★ REFURBISHED TO HIGH STANDARDS
- ★ BECOME ONE OF OUR REGULAR HIGHLY SATISFIED CUSTOMERS
- ★ EARLY COLOUR TVs FROM £5

Unit 10, Chiltern Business Centre,
Garsington Road, Cowley, Oxford
(next to B.L. Works).
Phone 0865 711966

TELEVISION

No other consumer magazine in the country can reach so effectively those readers who are wholly engaged in the television and affiliated electronic industries. They have a need to know of your products and services.

The prepaid rate for semi display setting £6.78 per single column centimetre (minimum 2.5 cms). Classified advertisements 40p per word (minimum 12

PRICE BUSTERS IN BIRMINGHAM FOR

TESTED AND UNTESTED TV'S AND VIDEO'S

ALSO AVAILABLE DIRECT LORRY LOAD

RING - 021-772 2733

WILTSGROVE LIMITED

(Next Door to UNCLE'S DISCOUNT STORE)

128-130 Ladypool Road, Sparkbrook, Birmingham B12 8JA.

CASH ONLY

"STOP PRESS"

NOW IN STOCK ELECTRONIC VIDEO'S AT UNBEATABLE PRICES

STARLITE ELECTRONICS

WILLOWS FARM,
A13 RAINHAM, ESSEX.
Rainham 23225 also
Hornchurch 50238.

**EX RENTAL TVs
UNTESTED FROM £15.00
WORKING TVs £20.00
RE-GUNNING TUBES**



2 year guarantee
Most types available
including Sony



T.V. SPARES, PANELS AND MANUALS PHILIPS · GRUNDIG

**TELEVIEW 01-994 5537
194, Acton Lane, London W.4.**

PHILIPS VIDEO SPARES

Model VR 2324. Brand new unused includes power supply tuner, timer clock, R.F. panels, cabinet, electronics only, no mechanism £35 inc VAT and postage.

EFJAY PRODUCTS
13 Placehouse Lane, Old Coulsdon, Surrey
Phone: Downland (07375) 55287 anytime

EAST ANGLIA SUPPLIES (BARRY T.V. SERVICES)

WE SPECIALISE IN LATE MODEL TELEVISIONS AND V.H.S. VIDEOS.

T.V.'s
G11's, KT3, K30, K35, CTX.
Other makes available.

VIDEOS
Ferg 3V29, 3V30, 3V35, 3V36.
Nat Pan 2000, 2010, 333.
Hitachi 8000.
Mitsubishi - various models.

All items fully serviced and ready for sale or rent in excellent condition. Free delivery for sensible size orders (petrol only charged).

Phone today for prices and availability to:
CAMBRIDGE 69215

SERVICE PAGES

words), box number 70p extra. All prices plus 15% VAT. All cheques, postal orders etc., to be made payable to Television, and crossed "Lloyds Bank PLC". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Television Room 204B (H.H.), IPC Magazines Limited, Kings Reach Tower, Stamford Street, London SE1 9LS. (Telephone 01-261 5942).

COME OVER TO DATEL LTD. FOR GREAT DEALS ON SUPER SETS

- ★ 96 CHASSIS IN 5's £25.00 ★
- ★ 9,000 CHASSIS IN 10's £17.00 ★
- ★ VHS VIDEO'S FROM £50.00 ★

All Thorn range in stock from 8.8 to TX 10 Stereo
Large stocks of working TV's and Video's.

Phone or call in today. You won't be disappointed.

Delivery to you can also be arranged.

Also complete postal service for all Thorn range of panels and spares. All panels and spares for mech. videos.

DATEL LTD.

0245 469779

2 Oyster Place, Montrose Rd., Dukes Park Ind. Est., Chelmsford, Essex

FYLDE T.V. AND VIDEO DISTRIBUTORS

Unit 7, Arkwright Court.

Blackpool/Fylde Industrial Estate
Very End of M55 left at roundabout.

UNLIMITED SELECTION OF

THORN 8800	PHILIPS G11
8800 R/C	G11 R/C
9000	G11 TTX
9000 R/C	GEC S/S
9600 R/C	JVC 20"
9600 TTX	MONO's 20" + 24"

AND MANY MORE

TRADE WORKERS TO ORDER

PHONE BLACKPOOL

(0253) 64413

NORMAN ENTERPRISES LTD
Weston-Super-Mare, Avon.
Tel: 518335

Colour TVs fully engineered
with a special care on tubes

Hitachi 217 Remote Control.....	£85
Thorne 9000 Remote Control	£42.50
Pye G11.....	£47.50
Rank T20.....	£42.50
Pye Chelsea 6 Button.....	£27.50
Pye 725.....	£37.50
Pye 721.....	£27.50
Thorne 9600.....	£45
Thorne 9200.....	£42.50
Bush T20 Remote Control....	£49.50
Bush T24.....	£55.50

ITT 20 INLINE TUBE

£45.00 + VAT.

All above prices include hand sets if available. Ready for sale.

Phone now, limited number each month. All the above off the pile, less a 3rd

IRISH T.V. DEALERS

New re-gunning plant

- TUBES -

Super View - Delta - In-line - P.I.L.

CHRIS KELLEHER'S T.V.

Kanturk, Co. Cork

Large stock G.8 - Decca - Ferg - T.V.'s UHF/VHF

029-50046 - Cash/Carry

Trent Tubes

For Professionally Rebuilt Tubes

From WEST BRIDGFORD ELECTRONICS LTD.
35A RADCLIFFE ROAD, WEST BRIDGFORD, NOTTINGHAM
NG2 5FF TEL: (0602) 813329

TWO year guarantee extendable to FOUR years

ALL STD DELTAS ONE PRICE £32.00

A51-161 - A51-163 **£40.00**

A51-A56-A66/500/510 (20AX)
One price **£43.00**

560DZB 510VLB etc **£48.00**

560DZB22 - 510VLB22 - AXT **£48.00**

A56-A66/540 (30AX) **£49.00**

SONY TYPES FROM £55.00

SPECIALIST SONY SERVICE

1000's more types available. VDUs, MDNDs, Industrials etc.

Suppliers to Broadcasting Authorities,

Government depts & National Companies and Manufacturers

ALL PRICES EX WORKS + VAT & EXCHANGE

WE SPECIALISE IN JAPANESE TYPES

INSURED DELIVERY SERVICE AVAILABLE

QUANTITY DISCOUNTS

TECHNICAL ADVICE SERVICE AVAILABLE

Agents, wholesalers required high discount rates

B.G. COMPONENTS

T.V. & VIDEO SPARES

We supply spares for most makes including Sony and Fidelity all at competitive prices.

We also stock a comprehensive range of rebuilt C.R.T.'s including Hitachi and Sony.

Open Monday-Saturday.

Hill Street, Oldham OL4 2AG.

061-624 1753.

BESCO LTD T/A NORTH WEST ELECTRONICS

25 YEARS SUPPLYING THE TRADE

**NEW TRADE SHOWROOM NOW
OPEN. WORKING TVS AND VIDEOS
ON SHOW.**

H.P. REPOS AND EX. RENTALS COLOUR TV'S AND VIDEOS

Refurbished TV's

BUSH T20/T26£45
G11£50
PYE KT3£65

Others done to
order.

**DISCOUNT FOR
QUANTITY**

Annual Clearance Rock Bottom Prices

PYE G11 EXC CAB.£40
BUSH T20/26 CH.....£35
HITACHI 191.....£20
FERGUSON TX
(NOT D.E.R. Etc.)£65
GEC 2010.....£20
PYE 222.....£20
PHILIPS 550.....£15
BUSH 718.....£20
BUSH 2 CHIP.....£8
GRUNDIG 5010.....£10

PYE KT3.....£50
GEC 2213.....£30
THORN 3000.....£7
GRUNDIG G415/4206

Best Stock in Country
over 2000 in stock (90%
of our TV's Switch on)

Special Price Quoted
For Bulk Purchases
From Source.

Video

SHARPS 7300, 8300
9300, HITACHI,
VT11, FERGUSON
3V29
(Not Ex D.E.R. etc.)
**SANYO, SONY,
BETA**

20/22" BUSH T20/22 MODEL EXC CABINETS IN 100 LOTS £25 EACH + VAT
EX EQUIPMENT BUSH PANELS NO EXCHANGE REQUIRED


	IF	Decoder	Line Scan	Power Supply	Frame
T20/22	X	14	18	17	14
T26	X	16	20	17	X

All prices inclusive of postage but plus VAT
Cheque with order please

LAUREL STREET, LEEDS ROAD,
BRADFORD, W. YORKSHIRE BD3 9TP.

5 MINS FROM MOTORWAY

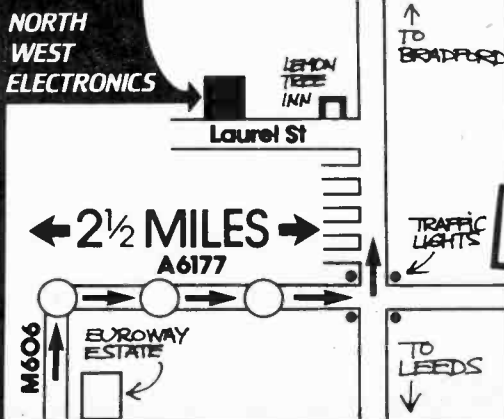100's PX
**HOOVER JUNIOR
VACS**
All models in stock



**P.X. WASHERS
COOKERS
ETC**

CASH ONLY

**OPEN 6 DAYS
SAT 9-5.30**

**Tel (0274)
660995**

SCREENPLAY *Your Friend in the TV Business*

COLOUR SETS FROM £5.00
 MONOS FROM £3.00
 PANELS BY POST - PRE-CALIBRATED
 WORKING SETS TO ORDER

Phone Baldock 894905
 SECTION 3, UNIT 4,
 SERL COMPLEX,
 LONDON ROAD,
 BALDOCK, HERTS.

OPEN 6 DAYS 10-6.30pm/10-5pm SAT.

INDEPENDENT TELEVISION AND VIDEO COMPANY

LARGE STOCKS TO CLEAR EVERY WEEK

COMPETITIVE PRICES

EXAMPLES:

B&W 20"-24" From £1.00
 COLOUR:
 Bush 1-2 I.C. £4.00
 Philips 520-550, 26" £6.00
 Thorn 3500 £6.00
 GEC-Decca-ITT £6.00

Philips 550 22" £10.00
 Pye 18"-20"-22" £10.00
 GEC 20"-22" 26" £12.00
 Thorn 8800-9000-9800 £15.00

Many Other Modern Sets and VHS Videos

PHILIPS G11 - ITT - Bush T20-T22-T26, Hitachi, Nat. Pan. - Sony
 Off Pile from £40

Phone Frank: Nottingham (0602) 864627

Unit 3

Meadow Trading Estate,
 Meadow Lane,
 Nottingham NG2 3HO.

LOOK! IMPORTANT DON'T FORGET WE SPECIALISE IN PHILIPS

PHILIPS 2020/21
 TESTED, WORKING AND BAGGED.
 WITH INSTRUCTION BOOK & CABLES. £45.00
 VHS & BETA MODELS 100's AVAILABLE

COMPLETE Machines for Spares £10.00

TELEVISIONS

	Off Pile	Tested Working Cleaned
G8's	£15.00	£22.00
BUSH T20/22	£35.00	£55.00
PYE G11's	£35.00	£55.00

TELEVISION WORLD,

Thornton Road, Bradford, West Yorkshire
 Telephone 0274 722499

Why Waste Time Ring in an order and it will be waiting.

VIDEO & HI-FI ELECTRONICS

379 EDGWARE ROAD
 LONDON W2

TEL. 01-258 0328

ALL VHS PARTS AVAILABLE. EXAMPLES:

VIDEO HEADS

JVC, Ferguson, Akai, Saba, Telefunken £35.00
 Sony (Betamax) £45.00
 National Panasonic £45.00
 All Hitachi heads from £42.00

INTEGRATED CIRCUITS

UPC 1365C £5.30
 UPD 553C £10.20
 UPD 552C £9.56
 HA 11711 £10.50

All makes of idlers, pressure rollers, clutch assembly and motors in stock.

Many other parts available. Send SAE for list.

ALL PRICES INCLUSIVE OF VAT
 ADD £2.00 FOR P&P

COLOUR BAR GENERATOR

Pal Colour Generator with 11 patterns plus sound. Grey scale, Colour Bars, Red, Green & Blue Raster, Cross-hatch, Dots, Chequer Board, Black Raster, White Raster, Half Black & White, Mains Powered. £75.90

OUTPUTS PROVIDED

UHF OUTPUT
 VIDEO OUTPUT
 SOUND OUTPUT
 LINE PULSE
 FIELD PULSE



Same as above plus RGB output £81.50
 Line Output Transformer Tester £11.50
 B/W Generator, Crosshatch, Peak White, Dots, Half Black & White and Grey Scale UHF output £18.50
 Same as above but with Video Output £20.50
 Capacitance Meter measures 10pF to 1µF complete with moving coil meter £14.75

CRT TESTER/REJUVENATOR SEND S.A.E.

S.A.E. for details. Prices include VAT.
 Postage on Colour Bars £1.75, others 75 pence.

C.M.J. ELECTRONICS

Unit 8, 16 Union Mill Street, Horseley Fields,
 Wolverhampton WV1 3DW.
 Tel: (0902) 871563

HALTON TV TRADE DISPOSAL

Wide range of TVs available.
 Working and non-working.

TRADE ONLY

(We have NO retail outlet)

St Michaels Industrial Estate, Widnes
 Tel. 051 423 1577

Thorn 3000/3500
 Thorn 9000

UNIVERSAL
 1 year guarantee

TRIPLERS
£4.95 inc. p&p

The UNIVERSAL TRIPLER can be used in most G.E.C., I.T.T., Pye, Rank, Decca & Continental sets.

WING ELECTRONICS

15 Waylands, off Tudor Rd, Hayes End, Middlesex

WORKING CTVs THE BEST & CHEAPEST IN LANCASHIRE SPECIAL OFFER

Working Decca Bradford Including Black Fronts

18" 20" 22" 26" ONLY £20.00 each in 6 units

Working GEC Plastic & Wooden. All models 20" 22" 26" ONLY £22.00 each in 6 units

Working Bush 20" 22" 26" ONLY £15.00 each

Philips G8 (520) 22" & 26" ONLY £20.00 each

Plus many more makes & sizes in stock, inc. Tanburg, Nordmende, Thorn.

1st COME 1st SERVED

ALL SETS TESTED & WORKING

CALL

JOHN POWNEY

TRADE TV SALES & SERVICE

Unit 31 Progress Industrial Estate,

Kirkham, nr Preston

(0772) 683392

UNTESTED PANELS FOR ALL MAKES OF TV
 £1.25 per panel plus post & packing

'BOBS'

TELEVISION

WAREHOUSE

A NEW CONCEPT IN EX-RENTAL T.V. & VIDEO

BOB IS BACK AND OPENS HIS NEW WAREHOUSE
IN ESSEX ON **JULY 1ST**

NO FREE HOLIDAYS OR WINE.
JUST THE USUAL GOOD HONEST T.V. & VIDEO AT GOOD HONEST PRICES.
WORKING T.V. AND VIDEO ENGINEERED TO THE HIGHEST
SPECIFICATION READY FOR YOUR SHOWROOM.
NON-WORKING GUARANTEED COMPLETE AND UNCANNIBALISED.


COMPLETE LOAD'S DIRECT FROM SOURCE.
NEW GRADE "B" T.V. & VIDEO AT LOW PRICES.
DELIVERY SERVICE AVAILABLE.

PHONE BOB BEAN ON:

0268 728966

AND DISCUSS YOUR REQUIREMENTS
— ALL MAKES AND MODELS AVAILABLE —

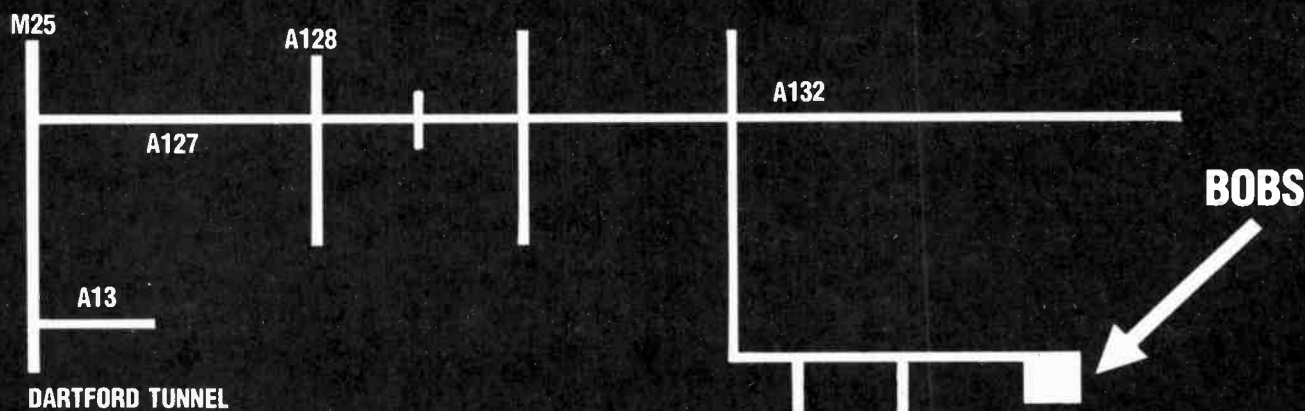BOBS T.V. WAREHOUSE, 1 Swinbourne Ct, Burnt Mills, Basildon, Essex



G.11s Pye & Philips

£35

ITT Full Remote

£35

T/TEXT Infra Red

GEC Modern 2242-2642 Types Mint £35

ALSO ON STOCK

THORN, DECCA, BDFD, 80-88-100, PYE CHELSEA 222, TTT CVC 20, 23, 30, 32 Remote, PANASONIC, HITACHI, TANDBERG, GRUNDIG, GEC 2002, 2242, 2642, 2202, and many others, changing daily.

VIDEO AS AVAILABLE. FROM £20.

VHS HITACHI, 9500, 9300, VT9, 8500, 8300, 8000, PANASONIC, 366, 7200, TRIUMPH 9500, JVC, FERGUSON.

BETAMAX SONY C5-C6, C7, SANYO, 5000, TOSHIBA.

2000 SYSTEM PHILIPS 2020, 2021, 2022, GRUNDIG 244.

STANDS. SLOT METERS, PANELS, SETS FOR SPARES, CLEARANCE COLOURS CHEAP. PRICES BASED ON QUANTITY. ALL PLUS VAT.

GENERAL FACTORS
UNION STREET,
DONCASTER, SOUTH YORKS.
0302-49583

CASH NO CHEQUES.
ONLY 2½ MILES FROM
(A1M) FOR M18-M1.
10 am to 5 pm Daily

BOURNEMOUTH

**LARGE STOCKS OF NICE
CLEAN WORKING SETS,
MOST MAKES AND SIZES.
FAIR PRICES – TRADE ONLY**

WAREHOUSE OPEN:
Mon-Fri 9-1, 2-5

**HILLIER'S, UNIT 2A,
11-15 FRANCIS AVENUE,
WALLISDOWN. TEL: 0202 581932**

WE HAVE FURTHER SUPPLIES OF VCR CASSETTES

BASF LVC £8.00, LVC 150 £6.50, LVC 120 £5.00,
PHILIPS LVC 90 £4.00, LVC 60 £3.00 (Some have
outer wrappings removed but are all new).

Above prices include V.A.T. & P&P. NTSC-PAL-NTSC trans-
fers, VHS, BETA, +UMATIC (Tapes included in price).
Optical transfer 8mm standard & super 8 transfer to VHS 50p
per minute, tape & postage extra. We specialise in the sale &
purchase of NTSC equipment. We also buy and sell Sony edit
equipment & recorder/players.

Mail Order address:

35 Sandy Lane, South Wallington, Surrey.
Telephone 01-669 2511

TRADE TV's & VIDEO'S

Ex-Rental & Repossessed

Video's from £20.00

TV's Colour £5.00

TV's B/W £1.00

Working TV's Colour from £10.00

Spares, Panels from 50p

Tel. Bradford 480281/733373

TELEFIX

1 Ellingthorpe St, Wakefield Rd.,
Bradford 4

SUPERVIEW TUBES

New RF Heat Technique for Jap Blackstripe,
Ferg, Bush in lines G11 GLASS with neck
pinhole, no problem Nissan van munster circuit.

CHRIS KELLEHER'S TV
Kanturk, Co. Cork

Rental dealer supplies 029 50046 10-10pm

PHILIPS G11 AND BUSH T20 regular supplies. For
prices phone 01-845 2036.

EXPRESS PANELS

A highly skilled staff using specialized service jigs and some of
the most up to date techniques and test equipment available
means we can save you time, money and heartache.

EXAMPLES FROM OUR RANGE (exch. basis)

Bush T20/22/26 Sony 1820/2000/2204

power supply power supply

£14.75 £16.75

G11

GEC 20AX/30AX

power supply power supply

£14.60 £14.75

All prices subject to VAT, P&P FREE (if orders over £10.00).
Panels also available for outright sale, discount for quantities
(any mix) all panels guaranteed 3 months, are chemically
cleaned and print re lacquered, and have no damaged print
etc, so they not only work they look good too. Send S.A.E. for
NEW CATALOGUE or ring with your requirements.

TRADE SERVICE AVAILABLE for VCR's.

Callers by appointment only. Telephone orders accepted
using Access & Visa.

021-359 3753

ARGO SERVICES (B.HAM) 53,
Lawley St, B.Ham B4 7XH

WANTED

GOLD PLATED SCRAP WANTED. Scrap edge con-
nectors, circuit boards, anything considered. Contact
P & F TURNER & SONS. Tel. Oxford (0865) 50293.

MACDONALD/NEWNES 81-82 64-65 63-64 61-62.
Good price paid. Ring Ray (0272) 568764.

WANTED FOR CASH. Ex rental colour televisions and
videos. Large or small quantities. Will collect. Tel. 0272
211179.

WANTED

SUPPLIER OF QUALITY USED
COLOUR TV'S AND VIDEOS FOR
NEW WHOLESALE OUTLET IN
THE NORTH OF SCOTLAND.
WE WILL COLLECT FROM ANY
SOURCE IN THE U.K.

Tel: Inverness
(0463) 790994/238695

WANTED

**Ex RENTAL COLOUR
TVs IN BULK
QUICK COLLECTION
Phone 0742 312832
(Sheffield)**

IN STRICTEST CONFIDENCE

WANTED VIDEOS Sanyo VTC 5000. Hitachi 8000 series. Any condition/quantity. Cash paid. Box No. 218.

WANTED VIDEO'S, Portables, colour TV etc. Any quantity. Immediate collection, cash paid. Tel. Stoke on Trent 416401.

CASH PAID now for your surplus TV spares, transistors, I.C.'s etc. Tel. MR. FORSHAW, 0902 29022.

REPAIR SERVICE

INSTRUMENT REPAIRS, Oscilloscopes, generators, multimeters & more. Phone VIKING ELECTRONICS 0394 450006.

BRISTOL - SOUTH WEST SOUTH WALES

Scratched and chipped CRTs can be Re-polished.

Tel: 0454 778635 for details

PRINTED PANEL REPAIR SERVICE

for example: G11 - T20 - AX PSU - £15.00
G11 - T20 - AX - LTB - £16.00

Most makes and models covered.

RING 0934 418545

for price list or quotation

BUSINESS OPPORTUNITIES

CHESTER. Small specialist rental business, 400 plus colour, mostly Decca 100/110. Optional low rental shop in suburban precinct. £60,000. Box 219.

VIDEO AND TV SERVICE BUSINESS for sale with three bedroomed detached house, own driveway and garage workshop 100 sq.ft. Room for expansion. Suit self-employed TV technician. £40,000 o.n.o. Near Bedford. Apply Box No. 220.

TV VIDEO-AUDIO SALES AND SERVICE BUSINESS FOR SALE

Modern premises shop and workshop. Good class North London area. Ideal for ambitious engineer. Established 30 years, new lease.

PRICE £18,500 + S.A.V.

Details: Box 201

WELL ESTABLISHED (19 YEARS) Video, Audio, Hi Fi Sales & Service Business for sale in popular N. Devon resort. T/O £62,000 (without V.A.T.). Only £12,500 for quick sale plus S.A.V. Details. Box No 216.

VIDEO

V.H.S. VIDEO'S 100's IN STOCK

Famous brands:

JVC · PANASONIC · FERGUSON

Also stockists of Grade B Units, Micro-waves, Hi-Fi, Radio/Cassettes etc. etc.

CONTACT MICK ON:

021-772 1591

TELEVISION

GET SHARP PARTS FAST

TELEPHONE

0734 - 876444

TELEX 848953



SHARP

Main U.K. Spare Parts Distributor

Audio-TV-Video ★ Microwave ★ Photo-copier ★ Typewriter

All U.K. model spares available. Same day despatch of orders received before 1pm.

Microwave, photocopier and typewriter spares to authorised service dealers/centres only.

WILLOW VALE ELECTRONICS LTD.,
11 Arkwright Road, Reading, Berks.

MISCELLANEOUS

MAIL ORDER MANUALS

BURROWS SERVICE
33 HANCOCK ROAD,
LONDON SE19 3JN.

£1 LISTS (Refundable on orders)

The Theory and Practice of PAL Colour Television in three important Video Cassette Programmes

Part 1.

The Colour Signal

Part 2.

The Receiver Decoder

Part 3.

Receiver Installation



VHS★★★V2000★★★

BETAMAX★★★UMATIC



For full details telephone

0253 725499 (Day)
0253 712769 (Night)

Or send for precis details

FLINTDOWN CHANNEL 5
339 CLIFTON DRIVE SOUTH,
LYTHAM ST ANNES FY8 1LP
(enclosing this advert)

NAME

ADDRESS

TEL:

SOLE SUPPLIERS TV/VIDEO Repair manuals/circuits, 1000s s/manuals supplied by return. S/sheets £2.50 except CTV/m.centres/stereos £3.50. LSAE with every order/query please brings free price list/magazine inc s/sheet - or phone 0698 884585 (883334 outside business hours) TIST, 76 Church Street, Larkhall, Lanarkshire.

MANOR SUPPLIES MK V Gen, Manor CRT tester, various repair manuals etc. Phone Soton. (0703) 899062.

C.R.T. REBUILDING PLANT AND EQUIPMENT

Installation, commissioning, training and technical after sales assistance.

C.R.T. INTERNATIONAL
136 Badmington Road,
Coalpit Heath,
Bristol BS17 2SZ
Tel: 0454 778635

NOW TOTAL SPARES SUPPORT FOR

FROM



ALL from STOCK (Subject to availability from Fidelity)

Trade Prices subject to official order - all others supplied at retail

**CABINETS ★ KNOBS ★ TUNERS ★ CONTROLS ★ CRT'S ★ TRANSFORMERS
SEMI'S ★ I.C.'S ★ CAPACITORS ★ REMOTES ★ TRIMS ★ END USER PARTS**

Tel:
0734
876444

Willow Vale Electronics Ltd

11 Arkwright Road, Reading, Berkshire RG2 0LU

GENUINE FIDELITY PARTS AT STANDARD FIDELITY TRADE PRICES

Tel:
0734
876444

SERVICE PAGES

SERVICE SHEETS

TECHNICAL INFO SERVICES (T) - 76 Church St., Larkhall, Lanarkshire ML9 1HE.

World's Sole Publishers of Comprehensive TV/Video Repair Manuals & Largest Known Stockists of Service Manuals and Service Sheets for all kinds of equipment both British and Foreign from 1935 to latest issues.

Big Catalogues of thousands of Service Sheets & Manuals + Chassis Guide + £4 Vouchers - saves time and expense £3.

Any published single service sheet for £2.50 + Isae except ctv/mus-c/combis from £3.50 + Isae. A selection from our stocks of thousands of Service Manuals ready for despatch by return post. Any Sony: Hitachi ctv from £8.50. Thorn 3000/3500 £9.50. Thorn 8000/8004/8500/8600 £9.50. Philips G8 complete £9.50. Decca 30/31 £8.50. Ferguson/JVC 1st video £19.50 or 3V00 types basic manual £19.50. Any Finlandia: Tyne CTV £9.50 each. Rank A823 complete £9.50.

COMPREHENSIVE PRACTICAL TV REPAIR MANUAL £9.50 PRACTICAL RADIO SERVICING & REPAIR COURSE £9.50
THE 11 TUNBRIDGE REPAIR MANUALS ONLY £88 THE 5 McCOURT REPAIR MANUALS ONLY £55
ANY SET OF 5 INDIVIDUAL VIDEO REPAIR MANUALS FOR £12.50 OR ALL 3 SETS (15 MANUALS) FOR £38.

UNIQUE COLLECTIONS OF CIRCUITS, LAYOUTS, ETC. . . . FANTASTIC VALUE

British ctv from hybrids to modern (3 binders) £58 Videos, all types (3 binders) £58 . . . any 1 for £20
Mono TV (2) £38 Foreign ctv (2) £38 Domestic Eqpt (2) £38 Portable British ctv (1) £20.

COMPLETE REPAIR SYSTEMS . . . huge savings from published prices

British ctv 3 binders of Circuits plus 6 Repair Manuals plus ref books, etc. for only £140
Foreign ctv 2 binders of Circuits plus 4 Repair Manuals, etc. for only £85
Videos 3 binders plus 15 individual Repair Manuals cover all the commonest models for only £85
Complete Integrated T.V. Repair System only £250 or in 12 sections at £25 per section.
Contents: 8 binders of circuits/16 Repair Manuals/dozens of other manuals . . . Any new publications from us within 1 year of ordering 1st section will be added at no extra charge.

NEW - PRACTICAL TRANSISTOR - **NEW** - VIDEO REPAIR SYSTEM 3 £28 - **NEW**
From beginners/students elementary theory to more advanced. Huge section British/Foreign equivalents/alternatives/other data. £5.80 Post Free. Binder of Circuits alone £29 5 Repair Manuals £12.50
3V31/32 Sharp 2300 to 9700 Philips Laser Disc Pan 7000/7200/7800.

Repair data/Circuits/Service data almost any individual mono tv £12.50 basic ctv £16.00 video £25.00
Repair data/Circuits almost any individual mono tv £10.50 ctv £12.00 video £10.50

LSAE BRINGS ANY REQUESTED QUOTATION - FULLER DETAILS - FREE MAGAZINE - PRICE LISTS ETC.
PHONE 0698 884585 Mon-Fri before 5pm or 0698 883334 any other time - FOR FAST QUOTES

SERVICE MANUALS, SERVICE SHEETS

For Television, Radio and V.C.R. Units. Prices from £2.00.

Send large s.a.e. for free catalogue with your enquiries, Mail Order only.

TECHNICAL DEPARTMENT, YOLANCEN LIMITED,
1 Buckingham Street, York YO1 1DW.

BELL'S TELEVISION SERVICES for service sheets on Radio, TV, etc. £1.50 plus S.A.E. Service manuals on colour TV and Video Recorders, prices on request. S.A.E. with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 505885.

SERVICE PAGES SERVICE PAGES
PLEASE MENTION TELEVISION WHEN
REPLYING TO ADVERTISEMENTS
SERVICE PAGES SERVICE PAGES

TELEVISION SERVICE SHEET SPECIALISTS

Thousands of British, European and Japanese models in stock.

Colour £3.00 Mono £2.00

Manual prices on request.

All our prices include post and packing costs.

Send stamped envelope for free catalogue and any enquiries.

SANDHURST TV SERVICES (MAIL ORDER)

57 High Street, Sandhurst, Camberley, Surrey GU17 8HB.

METERS

AVON METERS

We buy and sell and repair TV coinmeter. Reasonable prices, one year guarantee.

213 Cheltenham Road,
Redland, Bristol.
0272 553817

TELEVISION METERS. All types required for cash. We collect. P & J WALES, Tel. (0803) 25832.

METERS. Reconditioned 10p/50p available from stock. Contact THE METER CO. (Poole) LTD. (0202) 683498.

BOOKS AND PUBLICATIONS

THE DOMESTIC VIDEO RECORDER SERVICING BOOK THE ENGINEERS BIBLE

WITH CHAPTERS ON HI FI, DIGITAL SERVOS, LUMINANCE AND CHROMINANCE SIGNAL CIRCUITS, FAULT GUIDES AND CONNECTION DATA.

A MUST FOR ALL VIDEO REPAIRERS AND STUDENTS. THE COMPLETE REFERENCE TO VIDEO RECORDER CIRCUITS

ORDER YOUR COPY NOW

FOR ONLY £16.95 inc. P&P
FROM NEWARK VIDEO CENTRE

(0636) 71475

OR DIRECT FROM:

GROVE FARM, LONG LANE, BARNBY IN THE WILLOWS, NEWARK, NOTTS.
CHEQUES AND PO'S PAYABLE TO D. BEECHING.

SPECIAL OFFER

MACDONALDS RADIO & TV SERVICING BOOKS, NEW
74-75, 75-76, 76-77, 77-78, 79-80, 80-81, 82-83, 83-84, 84-85.

Macdonalds Price £24.30 delivered
OUR PRICE £22.50 delivered
Two or more £21.00 each
Full set of 10 £199.00

Prices include delivery

U-VIEW, 29 Warmsworth Road,
Doncaster, Yorkshire DN4 0RP.
Tel. 0302-855017. Callers ring first

"RADIO AND TELEVISION SERVICING" books, new editions for the last 6 years usually in stock. Prices on request. BELLS TELEVISION SERVICES, 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 505885.

SUCCESSFUL TELEVISION DEALING, Practical Business Guide, £4. S.A.E. details: J. P. PUBLICATIONS, P.O. Box 213, Wolverhampton WV11 2PQ.

FOR INFORMATION ON CLASSIFIED ADVERTISING PLEASE RING PAT BUNCE 01-261 5942

AERIALS

MULTI-OUTLET/MULTI-CHANNEL Installations. Large or small distribution systems. Equipment and/or consultancy by post or on site. Catalogue (full of trade know-how and trade equipment) £1 (refundable). **WRIGHTS AERIALS, 43 Greaves Sike Lane, Micklebring, Rotherham. (0709) 813419.**

SATELLITE TELEVISION

Buy direct from the manufacturers, low cost, full band satellite TV systems. Full band system £650 + VAT and Carriage

Write or telephone for details or call in at our factory showroom

NETWORK SATELLITE SYSTEMS LTD.
Unit 7-8, Newburnbridge Ind. Estate,
Hartlepool, Cleveland
Tel. 0429 274239 or 869366



Euro-Sat
Parabolic Dish Antennas
(Patent company est. in TV communications since 1969)
SATELLITE TVRO ANTENNAS
TOP QUALITY SOLID GLASSFIBRE DISH ANTENNAS
TRADE PRICES

1M. DIA 11-12.4 GHZ BAND	£77.00
1.2M. DIA 11-12.4 GHZ BAND	£93.00
1.6M. DIA 11-12.4 GHZ BAND	£117.00
1.8M. DIA (PETAL) 11-12.4 GHZ BAND	£157.00
2M. DIA. 11-12.4 GHZ BAND	£215.10
2.3M. DIA. (PETAL) 11-12.4 GHZ BAND	£248.10
3M. DIA 11-12.4 GHZ BAND	£737.00

Euro-Sat
107 Cross Street, Sale, Cheshire, England.
Tel. 061-437 2631 061-881 4249

SATELLITE TV RECEPTION EQUIPMENT

Dishes 0.9 to 2.8m, complete systems 10.9-12.7GHz, 4GHz. LNB's, demodulators, and all those accessories.

Manufacturers and Distributors of high quality satellite TVRO equipment.

KESH ELECTRONICS
Main St., Kesh, Co. Fermanagh, N.I.
Phone: KESH (03656) 31449

FOR SALE

TUBE TESTER - Reactivator/L.O.T. Tester: Willow Vale Type: 6A, triple meter, (similar to B & K 467), nearly new, cost £350. only £190. 0749 76095.

NEW PHILIPS V2000 Head £40.00 leader LCT 910A rejuv £150.00. 0522 38754.

NEWNES RADIO/TELEVISION Servicing complete to 1980, 30 books. Offers. Tyneside 2579792.

VCR I500 Used tapes still available, 1-4 £2.50 each. 5-10 £2.10 each including postage. C.W.O. please to WORRELL, 34, Curlew Close, Beverley HU17 7QN.

2 SETS OF FULLY RECONDITIONED tube re-gunning plants for sale. Training provided. From only £3,995. Tel. 0582-410787.

DEVONICS

**Quality Rebuilt Tubes
2 YEAR WARRANTY**

470 ERB22	£43
510 KCB22	£45
A51-161/500/510/ 570/580/590X	£45
560 AKB/DZB/TB22	£45
A56-500/510X	£45
A56-540X	£53
A66-500/510X	£46
A66-540X	£53
670 XB22	£46

Deltas from £30
Plus carriage and VAT
**2A BARTON HILL ROAD,
TORQUAY TQ2 8JH
0803 - 33035**



Sabaco For a great deal!

**TRY US YOU'LL LIKE US
TOP QUALITY TV'S & VIDEO'S AT
ROCK BOTTOM PRICES**

**VAN LOAD DIRECT FROM SOURCES
ALL SETS & VIDEO'S OFF THE PILE
(Mostly switch-ons)**

**Largest selection of 4000/8800/9000/9200/
9600/Ferg TX9/TX10 Stereo Teletext
Colour Portables**

Mainly teletext and remote with handset.

**Also Pye KT30/G11/T20/T26/Hitachi/
Philips 550/Grundig & many more.
BRAND NEW SETS AT LOW PRICES**

VHS VIDEO'S

**Good Working Order from 3V22, 3V23,
3V29 Portable Video's etc.**



**Also a selection of brand new video &
E180 video tapes**

OPENING HOURS:

**MONDAY TO SATURDAY 9am to 5.30pm
SUNDAY 10am to 4 pm**

**CASH ONLY All goods subject to VAT & availability
PHONE NOW FOR UP TO DATE COMPUTERISED PRICES
AND DELIVERY DAYS, BE HERE WHEN LORRY ARRIVES
FOR FIRST CHOICE — PHONE US NOW ON:**

(0602) 397555

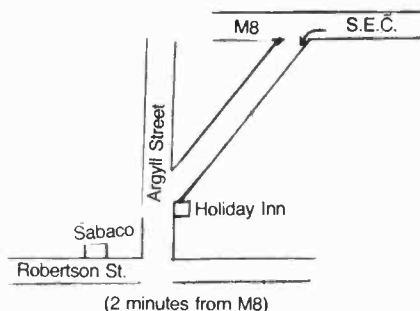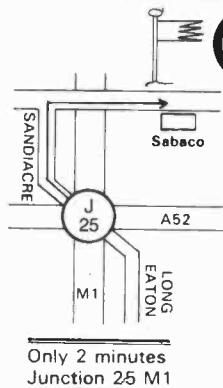

**Head Office:
Sabaco
Saba House,
46A Derby Road,
Sandiacre, Nottingham
(0602) 397555**

**Sabaco
75 Robertson Street,
Glasgow
(041) 221-2146**

INDEX TO ADVERTISERS

Aerial Techniques	605
Apollo	611
Argo Services (B'ham)	612
Asco TV and Video Centre	613
Avon Meters	606
Barry TV Services	608
Besco T/A North West Electronics	607
B. G. Components	552, 562, 598
B. K. Electronics	610
Bobs Warehouse	602
Bolten Ltd.	612
Burrows Service	599
Carter, John (Electrical) Ltd.	554
Cetel	604
Centrevision	554
Chromavac Ltd.	600
Chromavision	609
CMJ Electronics	603
Crewe Wholesale TV	598
Cricklewood Electronics Ltd.	612
C. R. T. International	607
Datel Limited	614
Devonics	604
Display Electronics Ltd.	556
East Cornwall Components	580, 581
Economic Devices	606
Ejlay Products	611
Eurolec (UK)	614
Euro-Sat	612
Flintdown Channel 5	603
Ford, Frank	607
Fylde T.V. and Video Dist.	611
Garton, D. G.	611
General Factors	552
G. G. L. Components	600
Grandata Ltd.	609
Halton TV Trade Disposal	611
Hillier's	604
Hockley Discount Televisions	551
Hussain Central T.V. Ltd.	555
ICS	609
Independent Television and Video Co.	597
Junction 11 T.V. Trade Disposals Ltd.	607
Kelleher, Chris	550
Kent Ledgerwood Wholesale Ltd.	614
Kesh Electronics	562
London Electronics College	Cover II
Manor Supplies	601
Mantel	601
Monitec	554
Monolith Electronics Co. Ltd., The	613
Network Satellite Systems Ltd.	613
Newark Video	605
N. G. T. Electronics Ltd.	605
Norgrove TV Trade Services	607
Norman Enterprises Ltd.	597
Papworth Transformers	561
Post A Part Electronics	555
Powell, T.	609
Powney, John, Trade TV Sales and Service	606
Precision Vision Ltd.	546, 547, 548, 549, 550
P. V. Tubes	553
Quick Save T.V. Spares	615
Repossessed T.V. Centres Ltd.	*
Riscomp Ltd.	614
Sabaco	613
Sandhurst TV Services	598, 616, Cover III, Cover IV
Senz Components	612
S & G Trade and Retail	602
Sight and Sound	*
Southpark Distributors	606, 611
Starlite Electronics	603
Stewart of Reading	613
Technical Information Service	611
Telefix	602
Teleman	605
Telepanels	550, 602, 615
Tele-part	597
Teletraders	555
Televideo Services	606
Television	609
Television World	562
Tidman Mail Order Ltd.	607
Trent Tubes	*
Trent Tubes	615
TVS Trade Services	601
T.V. Trade Sales	613
Universal Semiconductor Devices Ltd.	609
U-View Tubes	602
Video Hi Fi Electronics	612
Well View	606
Willow Vale Electronics Ltd.	609
Wiltsgrove Limited	606
Wing Electronics	609
Wizard Distributors	606
Yolabcen Limited	613

REPOSSESSED T.V. CENTRES LTD.

061-273-2854


YOUR CHOICE

MINT WORKING SETS. These arrive at our premises in A1 working order, cabinets are superb. **£45 to £70**

GUARANTEED UNTESTED SETS. These are just as they arrive, in good condition with plenty of plug in workers. We do not sort them as we have our separate source of working sets. **£10 to £35**

VHS Videos in stock.

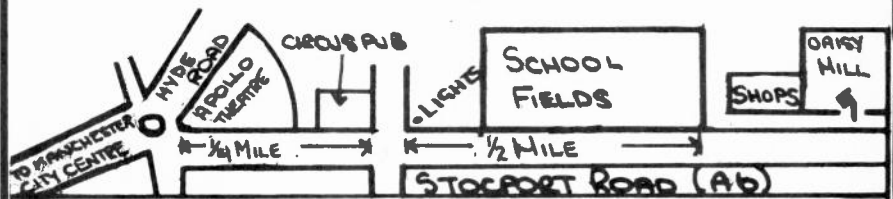*Well stored in large centrally heated premises. Ample viewing space and stored only four high!
Come and have a look round.*



**TRADE WAREHOUSE,
DAISY WORKS,
345 STOCKPORT ROAD,
LONGSIGHT,
MANCHESTER M13 0LF**

**ALSO AT
335-341 STOCKPORT ROAD
(NEXT DOOR)**

IRISH T.V. DEALERS

(PLEASE NOTICE)

LARGE SELECTION OF RECONDITIONED PRECISION-IN-LINE UHF-VHF COLOUR TVs, SOME WITH RE-GUN TUBES FITTED, "CABINETS RESTORED TO A1 CONDITION". PRICES START @ £60.00 VAT INCLUDED. ALSO 20" & 22" RE-GUN TUBES IN STOCK, QUANTITY DISCOUNT, DELIVERY ARRANGED. VIDEO HEADS ALSO IN STOCK.

(EXPORT SPECIALISTS)

**T.V. TRADE SALES
E.D.I. HOUSE
KYLEMORE PK. WEST
DUBLIN 10.
Tel: 0001-264139 (Local calls 01-)**

**ALSO
T.V.T.S.
CLOVER PLACE
COLLEGE ST.
KILLARNEY.
Tel: 064-33655**

**EMCO - EUROSONIC - GRUNDIG - TELETON + ALL BRITISH MAKES
ETC. ETC. ● ALL SPARES READILY AVAILABLE ●**

IMMEDIATE CREDIT AVAILABLE — TRADE ONLY

If you are a trader simply phone for the part you require and we will send it — no quibble — no hold up for status check. Satisfy us over the phone that you are a trader and we will supply almost any TV component by return "off the shelf", e.g. LOPTZ — EHT trays — droppers — OSC coils — switches — cans — smoothers — I.C.'s, etc. etc.

**YOU CAN BE 95% SURE WE CAN SUPPLY ANY
TV COMPONENT BY RETURN
IF YOU NEED SPARES FAST — RING NOW!**

ACCESS AND BARCLAYCARD ACCEPTED.

Applies to U.K. only.

TELEPART (W'TON)

**32 TEMPLE STREET,
WOLVERHAMPTON (0902) 29022**

SENDZ COMPONENTS

TO ORDER SEE BACK PAGE

Thorn Spares New 9000 Decoder £8.50 9000 Frame panel £8 9000 Cyclops panel £1.50 8000/8500 timebase panel £8 8800 convergence panel £6 8500 convergence panel £6 4000 Power supply £3 1600 Mains lead, switch £3 3500 6 push button + cable form £1.50 T605 1V NPN T166 80v/6A £10p 9000 Sound output panel £7 3500 Focus unit £1.50 3500 Mains Trans. £4 3500 cut outs 10 for £4 3500 IF panel £2 3500 Frame panel £3 3500 Line panel £3 3500 A1 Diode £20p Export 3500 IF panel £2 IC board with set of SN74LS £4 4000 Tube base £4 3500 A1 pots £5p Beam limiter panel £1.50 3500 Power output panel £1 3 Way regulated adaptor 240V 6V/7.5V/300mA £3.50 Rank/Toshiba preh unit 0354 £9.50 2 banks of 3 PB unit. Pye 731 £2 4 Push button unit preh £1.00 6 Push button VHF/UHF for v/cap. GEC-Decca type £7.00 7 Push button for CVC5 ITT £8.00 G8 Push Button Unit £10.00 KT3 12 Push button unit £2.00 KT3 (Export) 12 P.B.U. £2 6 Push button Unit Thorn £1.00 6 Push button Unit fits GEC & Decca etc. £6.00 Hearing aid unit £3 Rank Z718 4 P/B/Unit MECH £7 7 Button Unit GEC with Lamps £7 Bush TS15A 6 button unit with Pos & mains lead. 6 bush buttons. Bush £6.00 697 Push Button Unit £6.00		K35 Decoder £8 K35 Sound OP £4 K35 Split Diode 3122-138-35930 £10.00 Fidelity Tube Base with transistor & focus pot £1.50 Bush Tube Base on panel £1.00 Line Transformers Hitachi Split Diode and GEC 1981 to 1984 £13 2 J/Pots 3,500 1 off each type £3.00 G8 Trans. Philips £7.00 G11 Split Diode £12.00 CVC820 Split Diode ITT £10.00 Thorn B/W AD5308F + Stik + Lead £1.50 1690 Thorn EHT over-wind with diode lead & anode cap £2.50 GEC 2040 £3.00 GEC 2110 £7.00 Mullard AT 2036 £1.50 Pye 169 Line Trans £3.00 Pye mono T704A £3.50 Split Diode Trans £7.00 GEC 20 AX Rank Z522 £3 Rank L.O.P.T. Z970 £3.00 CVC 5-8-9 £3.50 AT2000 ITT £5.00 AT2000/15 £5.00 CVC30 ITT £6.00 CVC32 Line Tran £6.00 GEC800 Line Trans £6.00 CVC40 Slip/Diode £12.00 CVC 45 £5.00 GEC Portable G10T2041 £3.00 GEC Portable G10T2046 £3.00 EHT Split Diode Leads ITT £1.00 3500 L.O.P.T. & HT Trans each £2 LOPT Rank Z763 £5 K35 Split Diode 3122/13835930 £7		Rank T20 Z136 Panel £6 NEW Pack THORN 17 off Manual £5.00 NEW 1617 THORN Chassis with ICx & AU113 £5.00 30V Power Supply 500MA 4x2/4 £2.50 Pye 731 Power Panel £13 6 Diode Universal Triplers £4.00 NEW PYE 725 line O/P panel with L.O.P.T. & Tripler £8.00 NEW GEC 20AX Power Supply Switch Mode £12.00 Complete new GEC portable chassis M12011H/M1501H with P.B.U./v/cap/LOPT Field + Jungle panel for GEC 3133/3135 £1.50 GEC 2110 line panel with transformer £7.00 GEC 2110 tuner unit + IF Panel £12.00 Pye/Chelsea Line op panel £12.00 Pye 205 Tuner £9.50 Pye 205 Line op panel £7.50 Pye 713 IF panel and tuner £7.00 Pye 713 Chroma £10.00 Pye/Chelsea Timebase panel with LOPTI £10.00 Pye 731 Frame Panel £5.00 Pye 731 Convergence Panel £5.00 Pye 731 Chroma £10.00 Pye 731 IF panel + tuner £10.00 Pye CDA/205 panel £6.00 GEC portable chassis + LOPTI 2114 New £4.00 Thorn 1613/1713 chassis £9.75 G9 Power Panel £6.00 Mono RANK Chassis 127A NEW £10.00 NEW G9 Frame Panel £10.00 NEW G11 IF Panel £7.00 G8 Tuner Unit + Panel £4.00 G8 Power Supply £5.00 G8 6 Slooping PBU £8.00 G8 IF + Chroma £6.00 G8 Chroma £3.00 1/250AC £20p 1/100 £5p 1/100 x 10 £20p 22/100 £10p 4.7M/100 £20p 470/100 £20p 2000/100 £70p 4700/100 £75p 47/160 £10p G11 Selector gain module £3 Complete CVC 825 Chassis (both panels) £40.00 AEC V/Cap Resistor Unit UHF with IC SAA660 SA5670 £3.00 Z714 RANK IF Panels 6MHz 1 I.C. £10p SL437F £3.00 Z909B RANK IF Panels £3.00 Export 5.5MHz 2 I.C.'s £3.00 TBA1205B TCA2705Q £2.50 K35 IF £6.00 Z743 RANK IF Panel £4.00 Export 5.5MHz 3 I.C.'s £3.00 TBA750 + SC9504P + SC9503P £1.50 Pye G11 Front panel with transducer, pots, tuner pots, 6 pb switch + lead £5.00 Pye 6 button switch portable £1.00 GEC V/cap VHF/UHF tuner and IF+ sound O/P PC 706B3 (Export) £12.00 GEC Line O/P PC 659B3 £6.00 2110 GEC Power Panel £8.00 GEC Power Supply (Export) £10.00 G11 dynamic correction panel £6 CVC 20 Front panel with sliders + mains input panel £4 CVC 40 PUSH BUTTON ASSY with sliders: complete with lamp assy + pots £9.00 V/CV slider pots panel £9.00 CVC 5 Mains on/off + 5 pots £2 Universal Focus. Fits Pye, Thorn and Decca Units. £1.00 T147 Rank tube base on panel £1.00 Z718 Focus Unit £1.50 T20 Focus Unit £1.00 Large Type £75p Decca Small £75p KT3 Focus Unit £75p Focus Pot £75p K30 Tube base on panel £1.00 T310 Focus Units £7.00 CVC 32 Focus Unit £75p Fidelity Focus Unit 14R-14S £30p 3500 Thorn Focus Unit £1.00 ITT Small for use with Split £1.00 Z718 Bush Focus £2.00 Diode £50p TV11 £50p Remo TV12SP £50p 1600 Thorn EHT Rec and Lead £50p TV13 £50p TV14 £60p TV18 £10p TV20 £10p TV45 £50p Thorn 14/1500 rec stick £5p		Tube Thermaph 167 £1.00 Rank Secam Decoder Panel UHF & VHF T115A £13.00 Multi-Caps 220 MFD Sprague 385V 50p 4.700/75 6 amp Rip £2.00 350V 300M + 300M £1.00 400V 400M 60p 350V 400M 60p Thorn 3500 £7.00 175/100/100/350v £1.00 KT3/200/25/25/385v £1.00 300 + 300 + 150 + 100 + 50MFD £1.00 350V £2 47/220/350v 60p 150/150/100/100/100/320v £2.00 2500/2500/63v 50p 150/200/200/300v 70p 400/400/200v £1.70 300/100/100/16/275v £1.50 100/200/325v 40p 150/150/100/375v £1.50 200/200/75/25M 325V 9.75 300/300/100/32/32/300v 2.00 1500/200/30 50p Jelly pot Thorn 00D4013 £3 150/150/100/100/320v £2.00 100/350 + 300/200/100/16/275v £2.00 225 + 25/380 GEC 70p 200/100/100/350v £1.50 500/500/25v 50p 150/150/100/300v 75p 200/150/150/300v 1.00 ITT 8 and 6 Push Button £1.00 Pye 725 LOPTs £6.00 Pye 731 LOPTs £6.00 Thorn 8500-8800 LOPTs £5.00 CMD 800 Chassis. No tuner £20.00 TAG 226/600 £50p BD 650 £50p UPC 574 £50p BSS 38 £30p G11 £1.50 L.I.C. Receiver Panel £1.50 3 I.C. Power Supply G11 Full Remote Receiver Panel £3 Teletext Receiver Model T1 Fits on top of TV with handset. £95 FET Power VN88AF £50p PHILIPS SBC 469 Stereo Microphone 75p Meters Hills 520 £23.00 Meters Hills 420 £17.00 Infra-red Tester Handset £12.00 Infra Red Handset Tester Works at 24 feet - Sound repeater. Works off 9 volt battery Fits in top pocket. £8.00 Repaired Handsets Philips K4-K35, RC5350-RC5300, RC5370, RC5375, repaired same day £10.00 RC4001 Full Remote KT3 K30 Teletext Handsets exchanged £9.00 GEC Full Remote Infra red, 1983 models £10.00 Timers, 60 mins, small £1.00 G11 Touch Unit Full Remote £13 G11 Ultrasonic Teletext Handset £24.00 8 C.H. Ultrasonic GEC Full Remote C2014H/C2219H £15.00 New Replacement for G11 Ultrasonic Full Remote £12.00 Thorn 4000 insert with 7 buttons £5.00 Decca RC 11 £14.00 Decca RC 12 £14.00 G11 Infra-red full teletext £24.00 Dynatron-Full remote CTV 62, 63, 64 £19.00 Hitachi infra red handset £1.00 Philips full remote KT3, 16C 928/20C934, 7228/7324, K12 26C 797/IST 66K 1826 £12.00 G11, Full remote top button assy. £12.00 G11, Full remote repair service (exchange unit) £12.00 Philips infra red full remote 9 channel for 60 CP2605 £6.00 Philips infra red full remote 12 channel for 60 CP2605 £12.00 K35 £30 KT3/K30 T/Text £15.00 KT3/K30 Full remote £15.00 KT3 Power supply £4.00 Hitachi 8 button unit with resistor unit. Last year mod. £7.00 GEC infra-red 2236-2026 £4.00 GEC push pad hand set button blobs 10p each Pye & Philips handset KT3-K30 chassis. No RC5150-RC5176-RC5171-RC5177. Special Price £13.00 ITT Hand Set with TV-Teletext-VCR £12.00 RC4001 KT3 and Teletext £14.00 We have all parts for Philips Handsets	
--	--	--	--	---	--	---	--

Tuner Units	
G8 6 Button Unit	£9
V/Cap Rank UHF Z776/U/Unit	£6
V/Cap Rank VHF Z773/U/Unit	£5
NIW G8 Tuner V/Cap	£3.50
ELC 2000 on Panel	£7
GFC 6 Push Button Unit	£2.50
ITF 6 Push Button Unit	£6
D/ECC 6 Push Button Unit	£6
GFC or Hitachi 6 push button unit	
2110 Conversion	£8
GFC 2110 V/Cap	£5
ELC1043 (Fix Panel)	£3.75
ELC1042 NEW	£5.50
ELC2000 NEW	£4.00
ELC2006 NEW	£8.00
ELC2006 NEW	£6.00
GFC Tuner V/Cap Hitachi After	
1979/ET548, ET547, ET546, ET541B	£8.00
ASITEC UM183	£10.00
V314 (VHF)	£5.00
V317 (VHF)	£5
V334 (VHF)	£5
U321	£6
U341 UHF	£7.00
U342 (UHF)	£5
U411 UHF	£7.00
U.V. 411 Tuner	£10.00
U.V. 415	£10.00
U.V. 417	£7.00
Small V/Cap Mitsumi	
UHF	£4.00
VHF	£3.00
Portable & rotary Tuners Sanyo & Mitsumi UHF	£5.00
NSF-UHF/VHF-Varicap (old type)	£8.00
Moshi UHF/VHF (new type)	£8.00
U/EZ-B31 Fidelity V/Cap/Tuner	£6.00
UHF-VHF V/Caps on panel	£3.00
Thorn Tuner PANEL with 6x100k pots + cursors NO TUNER	£1.00
HITACHI 20 Turn Pot	40p
U321 on panel	£6.00
Tuner unit VHS Sylvania GTR	
Videon MFS901	£2.50
Mullard Video Modulator. Application, video tape recorders, TV cameras, video games, closed circuit TV, C.C.L.R. system Data supplied.	£10.00
VT 100 Sound Tuner Kit. TV	
Visonium. The latest design in low noise fitted with DNR, RF output and audio	£30.00
Sylvania UHF F4720B	£6.00
Sylvania VHF 900	£6.00
Small Tuner DX 175-220MHz	

SENDZ COMPONENTS

63 Bishopsteignton,
Shoeburyness, ESSEX SS3 8AF
SAME DAY SERVICE

**All items subject to availability.
No Accounts - No Credit Cards
Postal Order/Cheque with order
Add 15% VAT, then £1 Postage**

**Add Postage for overseas
Callers: To shop at 212 London Rd.,
Southend. Tel. 0702-332992**

Open 9-12.30-6. GVMT + school orders accepted on official headings add 10% handling charge.

Auto Changeover	£5.00	BT18124	£1.00
9000 Thorn Tuner on Panel	£7.00	BT18224	£1.00
TIHORN 1400 4P.B. Mech. Tuner		BU122A	£1.00
TIHORN 1500 4P.B. Mech. Tuner		CA270AE	50p
TIHORN 1500 4P.B. Mech. Tuner		CA270CW	50p
TIHORN 3500 4P.B. Mech. Tuner		CA270CE	50p
TIHORN 8000 4P.B. Mech. Tuner		CA920AE	£1.00
TIHORN 8500 Mech. Tuner		CA1310	50p
All new & boxed	£4.00 each	CA3046	50p
Delay Lines		CA305Q	50p
DL20A 80p		DL600	£1.00
G8 (Old Type)	£1	DL600	£1.00
DL600	£1.00	G8 (Old Type)	£1
DL700	£1.00	DL600	£1.00
UDL11	80p	DL700	£1.00
UDL11	80p	DM7492	50p
K13 Lummence	75p	HA1196	40p
Lummence Delay Line (CVC 45)		HA1320	£2.00
10x630ma fuse	25p	HA1423	40p
10x500ma	80p	HE14001	10p
10x1 amp	80p	HE1401LAF	10p
Co-Ax Joint	15p	HE14053B	30p
Co-Ax Belling Lec Plug	12p	HE14066	20p
Co-Ax Splitter	£1.00	HE14228	20p
UHF Modulator CCIR	£3.00	HD3890C	£3.00
Infr Red Emitting Diode	20p	K5731D 1001012	£1.00
NE286H Small Neon Lamps GEC & Philips.	5p	LA3220	50p
Mullard 5 Watt Amps. LP1162	75p	LM1011N	£1.00
New		LM831	£2.00
		M913	£3.00
		M913 + SAA	£2.00
		M1025 + SAA	£2.00
		MC476p	£1.00
		MC1307	75p
		MC1312	£2.00
		MC1330	75p
		MC1349	£1.00
		MC1352	£1.00
		MC1358	£1.00
		MC14002	15p
		MC1403	25p
		MC14016	25p
		MC14065	£1.00
		MC14514	80p
		MC1748	50p
		MF-M4956	£1.00
		ML231	£2.00
		ET16016	£2.00
		ML236E	£1.00
		ML237B	£1.00
		ML238B	£4.00
		ML239	£2.00
		ML926	£1.00
		MMS387	£1.50
		MM5611	£1.00
		MMS840	£3.00
		K35 Philips Receiver IC	
		MS8401H-34	£6.00
		MS902N-4	75p
		MMS1308N	£1.00
		MR1366	20p
		N64100	£1.00
		NE555P	60p
		NE555S	60p
		HD38980K	£2.00
		IL41	20p
		OPT600	20p
		OPT601	20p
		SAA661	£1.00
		SAA1030	£1.75
		SAA1021	£4.00
		SAA1024	£2.50
		SAA1025	£2.50
		SAA1073	£3.00
		SAA1074	£3.00
		SAA1075	£3.00
		SAA1124	£2.00
		SAA1130	£2.50
		SAA1174	£3.00
		SAA1176	£3.00
		SAA1250	£3.00
		SAA1251	£3.00
		SAA1272	£3.00
		SAA1276	£3.00
		SAA3021P	£4.00
		SAA3027P	£1.50
		SAA5000A	£1.50
		SAB3013	£2.00
		SAB3210	£2.00
		SAB4209	£2.00
		TBO0124	£1.00
		SAA5000A	£1.50
		SAA5010	£2.20
		SAA5012A	£5.00
		SAA5020	£5.00
		SAA5030	£5.00
		SAA5040	£3.50
		SAA5040A	£3.00
		BT109A	30p
		BT110A Plastic	30p
		BT110A Metal	30p
		BT119	£1.20
		BT120	£1.00
		BR4443	75p
		GT Diastor	60p
		Deca. 84-100	60p
		2N4441	£1.00
		MC R72-6	25p
		OT12	£1.00
		TL230M	£1.00
		H8341	£2.00
		1362	£2.00
		1368H	£2.00
		1368B	£2.00
		SP2M	50p
		MC R72-6	25p
		McR 726	25p
		McR 726	25p
		McR 726	25p
		McR 726	25p

SAA5043	£4.00	SN76550	30p	MJE660	25p
SAA7050	£3.50	SN76552	30p	MJE661	25p
SAA1033	£2.50	SN76570	£1.00	MJE3055	£1.00
SAA1039	£2.00	SN76620	50p	MJE2801	30p
SAS560	£2.00	SN76650	50p	MJE2955	50p
SAS560A	£1.00	SN76600N	40p	MJE13005	50p
SAS5701	£1.00	SN76620AN	50p	Sankiron Diode	30p
SAS660	£1.00	SN76660	£1.00	Philips Cartridges	
SAS670	£1.00	SN76705N	£2	GP412	£6.00
SAS580	75p	SN76707N	75p	GP412/11	£6.00
SAS590	75p	SN76708AN	75p	GP406	£6.00
SAS3210	£2.00	SN76720	£1.00	Transistors	
SL437F	£4.00	SN76709N	£2.00	A1222	15p
SL901B	£4.50	UA783P3C	40p	A1223	15p
SL918	£4.50	BT108A/02	40p	AC106	15p
TAT122	£1.15	BT138-10A	70p	AC121	15p
TAA30A	50p	BT146	30p	AC124	15p
TAA470	£1.50	TAA470	£1.50	AC128	15p
TAA570	75p	TC4270	£1.00	AC137	15p
TAA611B	£1.00	TC4270K	£1.00	AC151	15p
TAA621	£2.00	TC4640	£1.00	AC131	15p
TAA661	£1.00	TC4640	£1.00	AC138	15p
TAA661	£1.50	TC4270S	£1.00	AC152	15p
TA7108P	£1.00	TC4270S	£1.00	AC153K	15p
TA7117	50p	TC4740	£1.00	AC142K	15p
TA720P	50p	TC4800	£5.00	AC169	15p
TA7315AP	50p	TA7420	£1.00	AC176	15p
TA7607AP	40p	TC4940	£1.00	AC170K	15p
TA7609P	50p	TCF1010	£2.25	AC176	15p
TBA120A	40p	ICL120KC	£1.00	AC178K	15p
TBA120AS	40p	TC4440K	£1.00	AC179	15p
TBA120B	40p	TDA1003A	£1.00	AC186	15p
TBA120SB	40p	TDA1010	£1.00	AC187K	15p
TBA120F	50p	TDA1012	£1.00	AC188K	15p
TBA120SO	£1.00	TDA1060A	£1.50	AC188K	15p
TBA120U	75p	TDA1035T	£3.50	AD143	50p
TBA120X	40p	TDA1035SB	£1.50	AD149	50p
TBA120K	40p	TDA1072	£1.00	AD161/162	pair 40p
TBA1441	£1.00	TDA1151	75p	AF17A	25p
TBA231	75p	TDA1190	£1.00	AF139	30p
TBA395Q	50p	TDA1210	£1.00	AF381	£1.00
TBA396Q	£1.00	TDA1270	75p	AF239	25p
TBA397A	75p	TDA1270	£1.50	AF367	25p
TBA440P	£1.00	TDA1420	£1.50	AF302	£1.75
TBA440P	£1.00	TDA1327A	£3.00	AU110	£1.50
TBA480K	£1.00	TDA1365	£3.00	BU161	30p
TBA520	£2.00	TDA1512	£2.00	BD507	50p
TBA530	£2.00	TDA2002	£1.00	BD509	50p
TBA540	£1.00	TDA2003	£1.50	BD510	30p
TBA580Q	£1.00	TDA2004	£2.00	BD517	30p
TBA600K	£1.00	TDA2008	£2.00	BD519	30p
TBA570	£1.50	TDA2010	£1.00	BD534	30p
TBA625	50p	TDA2020	£1.00	BD535	30p
TBA625	50p	TDA2030	£2.00	BD535-44D	30p
TBA661	£2.00	TDA2140	£3.50	BD540	30p
TBA651	£2.00	TDA2160	£1.00	BD610	30p
TBA709	£1.50	TDA2320	50p	BD646	50p
TBA720A	£1.50	TBA780	50p	BD676A	30p
TBA750Q	£1.50	TDA2525	£1.00	BD678	50p
TBA800	50p	TDA2545A	£1.00	BD681	25p
TBA810AP	60p	TDA2600	£5.20	BD807	20p
TBA805	60p	TDA2640	£2.00	BD826	50p
TBA820	60p	TDA2522	£2.00	BD948	50p
TBA890	£1.00	TDA2530	£1.50	BDX75	25p
TBA920	£1.50	TBA920Q	£1.50	BDX76	£1.25
TBA920Q	£1.50	TBA950	£1.50	BDX79	50p
TBA990Q	£1.50	TDA2541	£1.00	BDX49	50p
TMS1000N	£2.00	TDA2560	£1.00	BE115	25p
TMS1943 N2L	£1.00	TDA2571AO	£2.50	BE121	20p
(clockchip)		TDA2575A	£2.00	BE127	20p
TMS9980	£4.00	TDA2577	£2.00	BE137	20p
TMS9941	£1.00	TDA2579	£2.00	BE157	20p
TMS2708JG45	£4.50	TDA2581	£2.00	BE160	20p
TMS2716JL	£1.00	TDA2590	£1.00	BE161	60p
TMS3529	£1.00	TDA2590	£1.00	BE164	60p
TMS3720ANS	£3.00	TDA2591	£1.00	BE179	30p
TMS4014	70p	TDA2600	£1.00	BE180	30p
TX4012	£4.00	TDA2610	£1.00	BE182	20p
ULN2216	75p	TDA2611AO	£1.00	BE184	20p
UPC566H	£1.00	TDA3651A	£1.00	BE184	20p
UPC585C	£1.00	TDA3652	£2.50	BE194	10p
UPC1033H	£2.00	TDA3653	£4.00	BE195	10p
UPC1353C	£2.00	TDA2640	£2.00	BE196	10p
UPC1363C	£2.75	TDA2680	£2.00	BE197	12p
UPC1366C	£3.00	TDA2690	£1.00	BE198	10p
UPC1514C	£3.00	UPC1514C	£3.00	BE199	10p
UPC2002	35p	UPC2002	35p	BE200	20p
UPI884091IC	£2	UPC3540	£4.00	BE202	10p
SN7401	50p	TDA371Q	£1.50	BE221	15p
SN7402N	£1.00	TDA3590	£3.00	BE238	10p
SN7403N	£1	TDA3591	£1.00	BE240	10p
SN7427N	£1	TDA3650	£3.50	BE244	40p
SN74107	£1.00	TDA3651AO	£2.00	BE245B	40p
SN74167	70p	TDA3644Q	£2.00	BE257	10p
SN7472N	20p	TDA3710	£3.50	BE273	15p
SN75108AN	£1.00	TDA9403	£3.50	BE274	15p
SN7601	£1.00	TEA1039	£2.00	BE282	15p
SN7601	£1.00	TEA5114	£1.00	BE283	10p
SN7603	£1.00	UPC1365	£3.00	BE284	15p
SN7605	£1.00	UPC1363C	£2.75	BE285	15p
SN7606	£1.00	TDA3501H	£6.00	BE287	15p
SN7607	£1.00	SN7415 N2AN	£1.00	BE288	15p
SN7608	£1.00	SN7415 N2AN	£1.00	BE293	25p
SN7609	£1.00	SN7415 N2AN	£1.00	BE294	