

JUNE 1994

£2.20

TELEVISION

SERVICING · VIDEO · SATELLITE · DEVELOPMENTS


A REED BUSINESS PUBLICATION

Servicing the Hitachi C2118T/R


**Digital TV –
anti-flicker
displays, PIPs,
noise reduction**

**Servicing the
Hantarex
9000 games
monitor**

NVQ explained

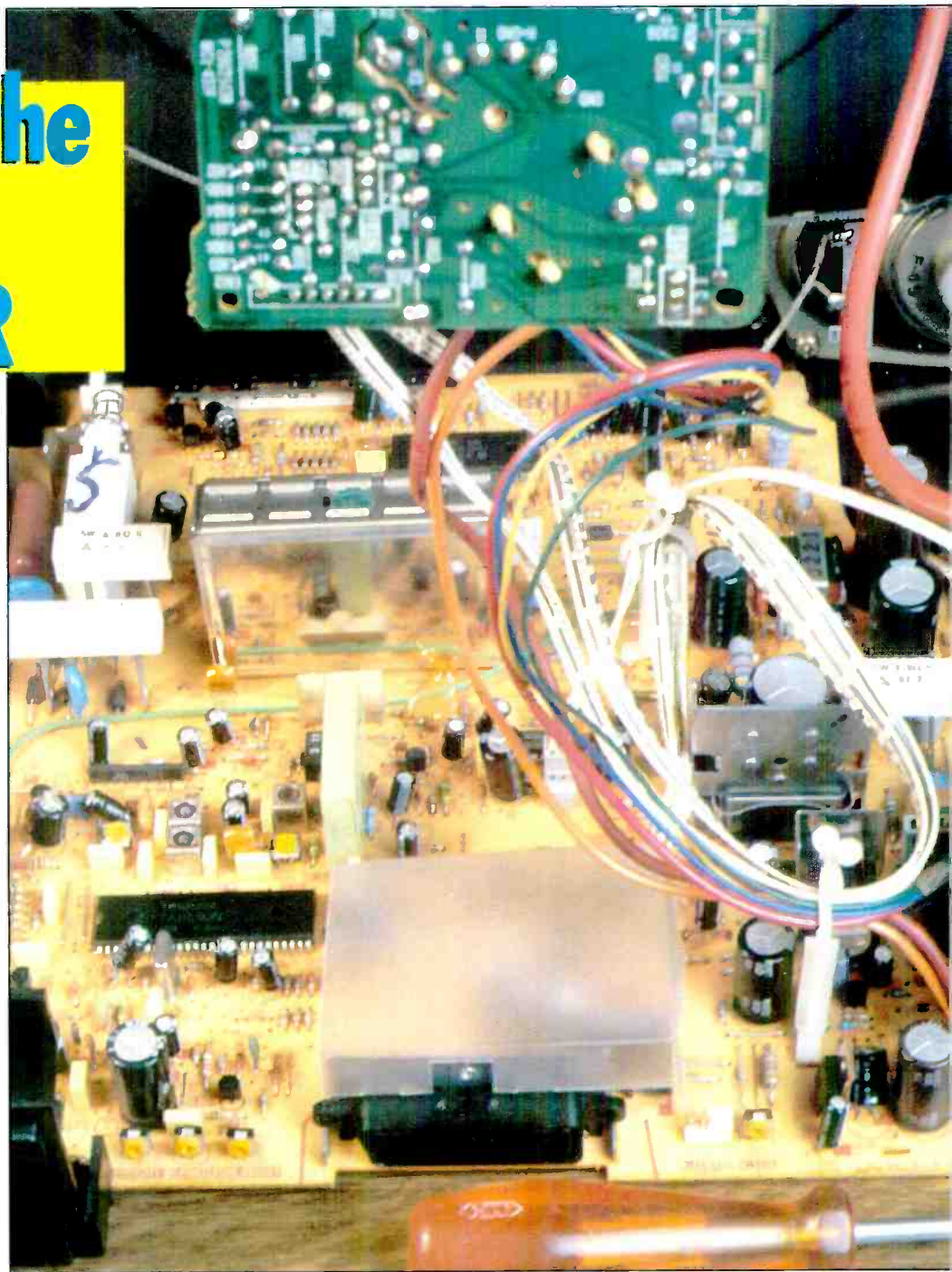

Satellite '94 show report

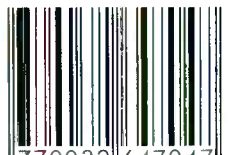

9 770032 647047



06>


WILLOW VALE ELECTRONICS LIMITED

Willow Vale gives you more...

- More technical know-how
- More flexibility
- More commitment to higher stock levels
- More peripheral product support
- More dedication to customer care


Willow Vale supplies parts for all these household names, with over 230,000 different spares available on our C.O.P.S. database system.

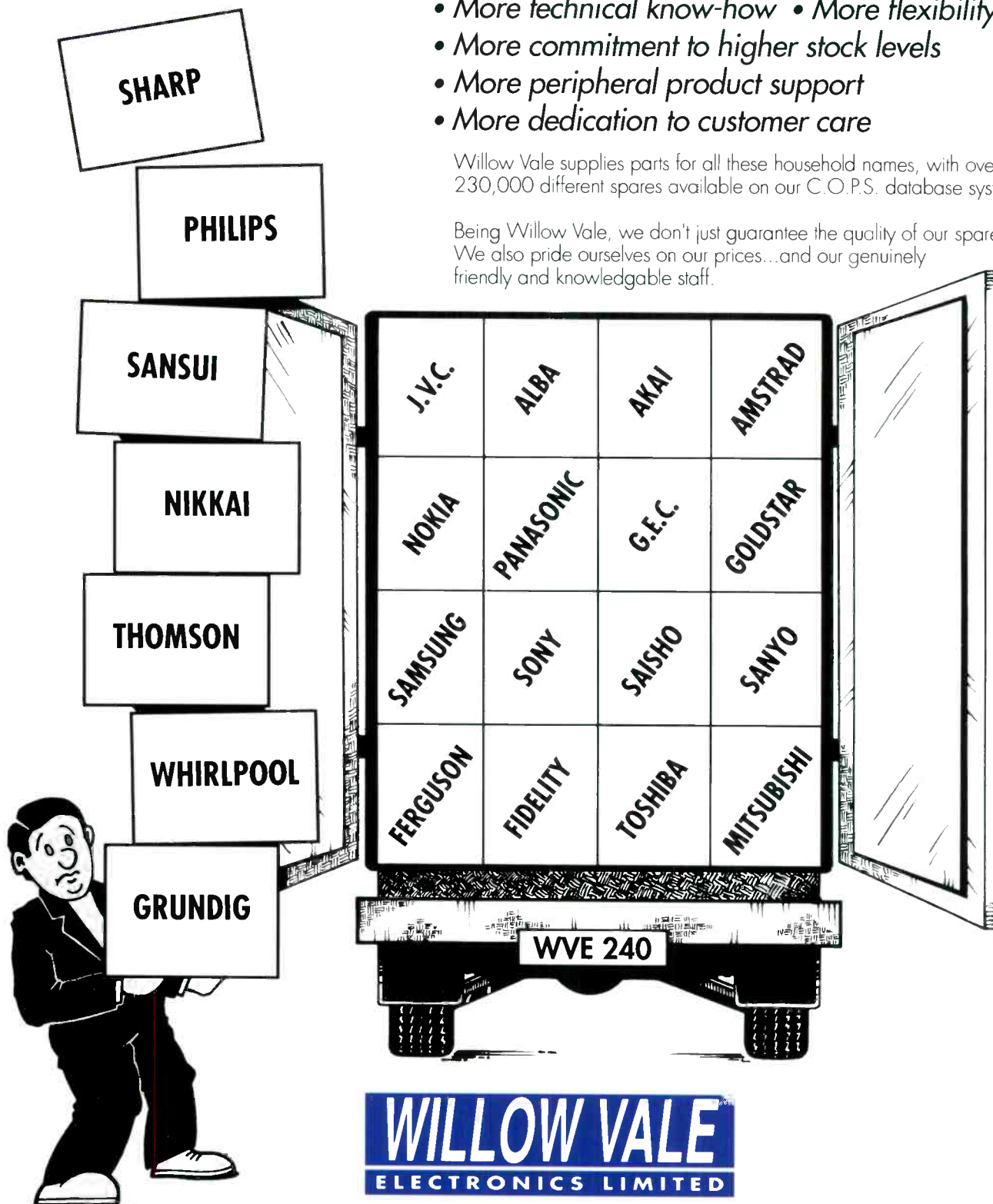Being Willow Vale, we don't just guarantee the quality of our spares. We also pride ourselves on our prices...and our genuinely friendly and knowledgeable staff.



'The Better Choice'

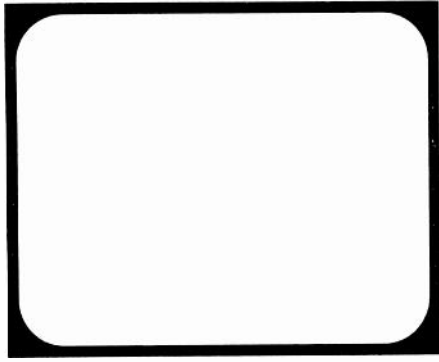Reading (0734) 876444 Manchester (061) 682 1415



TELEVISION

June
1994

Vol. 44, No. 8
Issue 524

On sale May 18th

COPYRIGHT

© Reed Business Publishing Ltd., 1994
Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Editorial correspondence should be addressed to "Television" Editorial Department, Reed Business Publishing, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

INDEXES AND BINDERS

Indexes for Vols. 38 to 43 are available at £3.50 each from Video Interface Products Ltd., who can also supply a five-year consolidated index on computer disk. For further details see page 585.

Binders that hold twelve issues of *Television* are available for £5 each from Television Binders, 78 Whalley Road, Wilpshire, Blackburn BB1 9LF. Make cheques payable to "Television Binders".

SUBSCRIPTIONS

An annual subscription costs £26 in the UK, £37 for Eire/Europe airmail (postage included for all rates). Rest of the world airmail available upon request. Send orders with payment to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex, RH16 3DH.

Subscription hotline for 24-hour ordering with Credit Card telephone 0622 721666 quoting INJ.

BACK NUMBERS

Some back issues are available at £2.75 each from Television Back Issues, Room L323, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Make cheques/postal orders payable to Reed Business Publishing Ltd. See box on page 561.

ISSN 0032-647X

545 Leader

546 Teletopics

News, comment and developments

548 Servicing the Hitachi C2118R/T

Mike Leach

These sets, fitted with the G7PS Mk. 2 chassis, provide excellent results and are reliable. There are one or two points that do give trouble however. Once you know about them, repairs are straightforward and relatively inexpensive.

550 Satellite Fault Notes

Reports from J. LeJeune, Ian Rees and Andrew J. Finn.

552 Letters

554 Modern TV Receiver Techniques, Part 18

Eugene Trundle

This concluding instalment deals with some of the possibilities introduced when AD conversion and a field store followed by DAC are present in a set, including flicker-free 100Hz displays, digital noise reduction, zoom effects and PIPs.

559 Help Wanted

560 What a Life!

Donald Bullock

561 Test Case 378

562 Servicing the Hantarex MTC9000 Monitor

Peter Hubbard

This monitor chassis is widely used in arcade games machines: repairs to this type of equipment can be a worthwhile addition to the normal range of servicing. An outline of the requirements for handling this chassis and some common faults.

563 Next Month in Television

564 Cable and Satellite '94

Ian Martin

566 TV Fault Finding

Reports from Philip Blundell, AMIEE, John Edwards, Nick Beer, Eugene Trundle, Brian Storm, Chris Watton, Michael Dranfield, Gordon Haigh and John Pitt-Francis.

569 Camcorner

Reports from Brian Storm, Keith T. Keeton and David C. Woodnott.

570 Long-distance Television

Roger Bunney

DX conditions and reception, the satellite belt and news from abroad.

574 VCR Clinic

Reports from Eugene Trundle, Colin McCormick, Ian Rees, Della Verita, Gerald Smith, Keith Evans, Graham Richards, Ronnie Boag and David Belmont.

576 The Panasonic Alpha 3 Chassis, Part 4

Ray Meadows

Sound processing, the line and field timebases and various options including the chroma/luminance comb filter.

583 NVQs and the Brown Goods Industry

Joe Cieszynski

What the new training systems will mean for the TV/video servicing trade.

586 Servicing Briefs from Toshiba

OUR NEXT ISSUE DATED JULY
WILL BE PUBLISHED ON JUNE 15

BC107	8p	BD897	50p	SZ800M	72p	DIODES	PCL84	60p	AV3-8910	360p	LA4102	100p	SAA5020	350p	STK4793	800p	STR5041	350p	TD41013A	110p	TD44280	320p	
BC108	8p	BD899	50p	T2800M	52p	Rectifier	PCL85	80p	AV3-8912	400p	LA4103	100p	SAA5030	400p	STK4803	640p	STR5501	500p	TD41015	85p	TD44282	360p	
BC109	10p	BD901	40p	T2800M	72p	Diodes	PCL805	80p	BA301	55p	LA4112	120p	SAA5040	280p	STK4803	700p	STR5504	400p	TD41016	110p	TD44283	360p	
BC110	20p	BD902	45p	TIP29A	15p	Diodes	PFL200	110p	BA311	55p	LA4120	270p	SAA5040B	400p	STK4833	700p	STR5541	325p	TD41020	110p	TD44290	200p	
BC111	20p	BDX33	60p	TIP29C	25p	BY133	8p	PL83	120p	BA313	60p	LA4125	200p	SAA5050	500p	STK4843	720p	STR5901	475p	TD41022	130p	TD44400	175p
BC142	20p	BDX65	60p	TIP30	25p	BY164	40p	PL84	120p	BA340	150p	LA4137	180p	SAB303A	270p	STK4853	730p	STR6001	525p	TD41023	330p	TD44410	175p
BC143	20p	BDW23	50p	TIP30C	25p	BY179	32p	PL95	180p	BA401	60p	LA4140	100p	STA1010	200p	STK4873	850p	STR8145	550p	TD41025	330p	TD44420	175p
BC144	8p	BDW34	50p	TIP31A	25p	BY210	32p	PL504	120p	BA402	50p	LA4160	100p	STA401A	220p	STK4893	1000p	STRD1706	450p	TD41028	175p	TD44427	200p
BC148	8p	BDW93	50p	TIP31C	24p	BY216	20p	PL508	120p	BA403	50p	LA4180	100p	STA405A	270p	STK4913	900p	STRD1806	400p	TD41029	200p	TD44431	150p
BC149	8p	BDW94	50p	TIP32	24p	BY226	11p	PL519	430p	BA514	150p	LA4182	180p	STA405A	270p	STK4913	900p	STRD1806	400p	TD41030	200p	TD44431	150p
BC157	8p	BDY92	100p	TIP32A	21p	BY207	9p	PY81	100p	BA516	150p	LA4190	300p	STA432A	220p	STK5315	500p	T2800D	52p	TD41037	190p	TD44437	150p
BC158	8p	BDY93	100p	TIP32B	21p	BY210	9p	PY82	100p	BA521	100p	LA4192	100p	STA432A	220p	STK5322	500p	T2800D	52p	TD41037	190p	TD44437	150p
BC160	30p	BF167	30p	TIP33	50p	BY226	120p	PY80A	100p	BA526	100p	LA4201	100p	STA432A	220p	STK5322	500p	T2800D	52p	TD41037	190p	TD44437	150p
BC171	10p	BF180	16p	TIP33C	60p	BY227	19p	PY80A	100p	BA526	100p	LA4201	100p	STA432A	220p	STK5322	500p	T2800D	52p	TD41037	190p	TD44437	150p
BC172	10p	BF181	16p	TIP34	50p	BY228	28p	LED's	20p	BA527	70p	LA4220	120p	STA435A	270p	STK5331	300p	T2800D	52p	TD41037	190p	TD44437	150p
BC173	10p	BF182	16p	TIP34	50p	BY228	28p	LED's	20p	BA527	70p	LA4220	120p	STA435A	270p	STK5331	300p	T2800D	52p	TD41037	190p	TD44437	150p
BC178	14p	BF195	7p	TIP35C	60p	BY238	5p	GREEN	8p	BA534	220p	LA4260	230p	STA456C	240p	STK5332	100p	T2800D	52p	TD41037	190p	TD44437	150p
BC179	14p	BF199	8p	TIP36C	65p	BY239	18p	YELLOW	8p	BA536	150p	LA4270	150p	STA456C	240p	STK5333	500p	T2800D	52p	TD41037	190p	TD44437	150p
BC182L	7p	BF200	16p	TIP41A	20p	BYX10	15p	GREEN	8p	BA546	150p	LA4420	140p	STA901M	280p	STK5337	500p	T2800D	52p	TD41037	190p	TD44437	150p
BC183L	7p	BF245	25p	TIP42A	22p	BYX70/500	32p	YELLOW	8p	BA558	150p	LA4440	140p	STA901M	280p	STK5337	500p	T2800D	52p	TD41037	190p	TD44437	150p
BC184	7p	BF254	15p	TIP47	40p	OA40	10p	GREEN	8p	BA684	400p	LA4445	150p	STK0039	600p	STK5361	375p	T2800D	52p	TD41037	190p	TD44437	150p
BC184L	7p	BF254	15p	TIP47	40p	OA40	10p	GREEN	8p	BA684	400p	LA4445	150p	STK0039	600p	STK5361	375p	T2800D	52p	TD41037	190p	TD44437	150p
BC212	7p	BF258	18p	TIP51	120p	OA200	10p	LED's	5p	BA1320	120p	LA4505	220p	STK0059	620p	STK5422	375p	T2800D	52p	TD41037	190p	TD44437	150p
BC213L	7p	BF258	18p	TIP51	120p	OA200	10p	LED's	5p	BA1320	120p	LA4505	220p	STK0059	620p	STK5422	375p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p	IN, 91.4	2p	5mm x 2.5mm	1p	BA1360	120p	LA4507	360p	STK0060	820p	STK5431	550p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p	IN, 91.4	2p	5mm x 2.5mm	1p	BA1360	120p	LA4507	360p	STK0060	820p	STK5431	550p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p	IN, 91.4	2p	5mm x 2.5mm	1p	BA1360	120p	LA4507	360p	STK0060	820p	STK5431	550p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p	IN, 91.4	2p	5mm x 2.5mm	1p	BA1360	120p	LA4507	360p	STK0060	820p	STK5431	550p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p	IN, 91.4	2p	5mm x 2.5mm	1p	BA1360	120p	LA4507	360p	STK0060	820p	STK5431	550p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p	IN, 91.4	2p	5mm x 2.5mm	1p	BA1360	120p	LA4507	360p	STK0060	820p	STK5431	550p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p	IN, 91.4	2p	5mm x 2.5mm	1p	BA1360	120p	LA4507	360p	STK0060	820p	STK5431	550p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p	IN, 91.4	2p	5mm x 2.5mm	1p	BA1360	120p	LA4507	360p	STK0060	820p	STK5431	550p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p	IN, 91.4	2p	5mm x 2.5mm	1p	BA1360	120p	LA4507	360p	STK0060	820p	STK5431	550p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p	IN, 91.4	2p	5mm x 2.5mm	1p	BA1360	120p	LA4507	360p	STK0060	820p	STK5431	550p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p	IN, 91.4	2p	5mm x 2.5mm	1p	BA1360	120p	LA4507	360p	STK0060	820p	STK5431	550p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p	IN, 91.4	2p	5mm x 2.5mm	1p	BA1360	120p	LA4507	360p	STK0060	820p	STK5431	550p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p	IN, 91.4	2p	5mm x 2.5mm	1p	BA1360	120p	LA4507	360p	STK0060	820p	STK5431	550p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p	IN, 91.4	2p	5mm x 2.5mm	1p	BA1360	120p	LA4507	360p	STK0060	820p	STK5431	550p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p	IN, 91.4	2p	5mm x 2.5mm	1p	BA1360	120p	LA4507	360p	STK0060	820p	STK5431	550p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p	IN, 91.4	2p	5mm x 2.5mm	1p	BA1360	120p	LA4507	360p	STK0060	820p	STK5431	550p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p	IN, 91.4	2p	5mm x 2.5mm	1p	BA1360	120p	LA4507	360p	STK0060	820p	STK5431	550p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p	IN, 91.4	2p	5mm x 2.5mm	1p	BA1360	120p	LA4507	360p	STK0060	820p	STK5431	550p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p	IN, 91.4	2p	5mm x 2.5mm	1p	BA1360	120p	LA4507	360p	STK0060	820p	STK5431	550p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p	IN, 91.4	2p	5mm x 2.5mm	1p	BA1360	120p	LA4507	360p	STK0060	820p	STK5431	550p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p	IN, 91.4	2p	5mm x 2.5mm	1p	BA1360	120p	LA4507	360p	STK0060	820p	STK5431	550p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p	IN, 91.4	2p	5mm x 2.5mm	1p	BA1360	120p	LA4507	360p	STK0060	820p	STK5431	550p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p	IN, 91.4	2p	5mm x 2.5mm	1p	BA1360	120p	LA4507	360p	STK0060	820p	STK5431	550p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p	IN, 91.4	2p	5mm x 2.5mm	1p	BA1360	120p	LA4507	360p	STK0060	820p	STK5431	550p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p	IN, 91.4	2p	5mm x 2.5mm	1p	BA1360	120p	LA4507	360p	STK0060	820p	STK5431	550p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p	IN, 91.4	2p	5mm x 2.5mm	1p	BA1360	120p	LA4507	360p	STK0060	820p	STK5431	550p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p	IN, 91.4	2p	5mm x 2.5mm	1p	BA1360	120p	LA4507	360p	STK0060	820p	STK5431	550p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p	IN, 91.4	2p	5mm x 2.5mm	1p	BA1360	120p	LA4507	360p	STK0060	820p	STK5431	550p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p	IN, 91.4	2p	5mm x 2.5mm	1p	BA1360	120p	LA4507	360p	STK0060	820p	STK5431	550p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p	IN, 91.4	2p	5mm x 2.5mm	1p	BA1360	120p	LA4507	360p	STK0060	820p	STK5431	550p	T2800D	52p	TD41037	190p	TD44437	150p
BC214L	7p	BF262	25p	TIP54	120p																		

LINEAR ICs	25A1051	300p	25C536	20p	25C1625	150p	25C2329	480p	25C2938	235p	25C3526	120p	25D784	650p	25D1399	300p	25K197	140p	25K-106	300p	8294	440p			
-Cont.	25A1052	400p	25C558	275p	25C1626	50p	25C2331	60p	25C2939	400p	25C3527	200p	25D785	200p	25D1400	200p	25K214	170p	COMPUTER ICs	8287	8290	650p			
UPC1363	190p	25A1053	100p	25C561	125p	25C1627	250p	25C2332	250p	25C2940	300p	25C3528	100p	25D786	20p	25D1401	150p	25K216	200p	2114	150p	8748	700p		
UPC1363C	350p	25A1069	500p	25C603	400p	25C1628	75p	25C2334	80p	25C2942	50p	25C3529	200p	25D787	30p	25D1402	125p	25K217	35p	2532	100p	2800CPU	100p		
UPC1364C	350p	25A1076	230p	25C605	100p	25C1629	50p	25C2335	75p	25C2943	50p	25C3530	300p	25D788	30p	25D1403	60p	25K218	400p	2537	200p	2800CPU	100p		
UPC1365	250p	25A1077	300p	25C609	100p	25C1630	300p	25C2340	80p	25C2944	80p	25C3531	200p	25D789	30p	25D1404	125p	25K219	50p	2538	200p	2800CPU	100p		
UPC1367	500p	25A1081	300p	25C610	100p	25C1631	300p	25C2341	80p	25C2945	80p	25C3532	200p	25D790	30p	25D1405	125p	25K220	50p	2539	200p	2800CPU	100p		
UPC1370C	500p	25A1082	80p	25C643	500p	25C1674	15p	25C2353	120p	25C2947	160p	25C3533	170p	25D791	33p	25D1406	125p	25K221	50p	2540	200p	2800CPU	100p		
UPC1373	85p	25A1084	100p	25C644	100p	25C1675	90p	25C2353	120p	25C2948	150p	25C3534	200p	25D792	33p	25D1407	125p	25K222	50p	2541	200p	2800CPU	100p		
UPC1373C	85p	25A1085	75p	25C647	300p	25C1678	90p	25C2361	150p	25C2949	150p	25C3535	220p	25D793	45p	25D1408	125p	25K223	50p	2542	200p	2800CPU	100p		
UPC1378	180p	25A1091	100p	25C648	100p	25C1679	100p	25C2362	150p	25C2950	150p	25C3536	200p	25D794	45p	25D1409	125p	25K224	50p	2543	200p	2800CPU	100p		
UPC1382	110p	25A1094	300p	25C683	35p	25C184	35p	25C2365	200p	25C2951	100p	25C3537	200p	25D795	45p	25D1410	125p	25K225	50p	2544	200p	2800CPU	100p		
UPC1384	425p	25A1094	300p	25C708	100p	25C1845	30p	25C2363	6000p	25C2952	300p	25C3538	200p	25D796	45p	25D1411	125p	25K226	50p	2545	200p	2800CPU	100p		
UPC1387C	250p	25A1095	200p	25C710	15p	25C1729	900p	25C2369	100p	25C2953	100p	25C3539	200p	25D797	45p	25D1412	125p	25K227	50p	2546	200p	2800CPU	100p		
UPC1394	120p	25A1096	80p	25C711	15p	25C1730	90p	25C2371	25p	25C2954	125p	25C3540	200p	25D798	45p	25D1413	125p	25K228	50p	2547	200p	2800CPU	100p		
UPC1397	500p	25A1097	100p	25C712	15p	25C1731	90p	25C2373	210p	25C2955	500p	25C3541	130p	25D799	45p	25D1414	125p	25K229	50p	2548	200p	2800CPU	100p		
UPC	25A1103	130p	25C730	350p	25C1740	100p	25C2383	50p	25C3026	550p	25C3636	200p	25D800	55p	25D1428	200p	25K231	40p	2549	200p	2549	200p	2800CPU	100p	
1403CA	650p	25A1104	140p	25C732	40p	25C1741	35p	25C2389	45p	25C3030	300p	25C3651	600p	25D801	55p	25D1429	200p	25K232	40p	2550	200p	2550	200p	2800CPU	100p
1403CA	450p	25A1105	250p	25C733	15p	25C1742	70p	25C2397	100p	25C3032	60p	25C3652	200p	25D802	55p	25D1430	200p	25K233	40p	2551	200p	2551	200p	2800CPU	100p
UPC	25A1111	90p	25C738	15p	25C1758	35p	25C2412K	50p	25C3039	80p	25C3658	120p	25D804	200p	25D1431	200p	25K234	40p	2552	200p	2552	200p	2800CPU	100p	
1421CA	650p	25A1112	150p	25C739	150p	25C1759	30p	25C2413	50p	25C3040	260p	25C3675	100p	25D805	170p	25D1432	400p	25K235	40p	2553	200p	2553	200p	2800CPU	100p
UPC	25A1115	30p	25C761	110p	25C1765	100p	25C2429	100p	25C3042	300p	25C3678	200p	25D806	170p	25D1433	400p	25K236	40p	2554	200p	2554	200p	2800CPU	100p	
1423CA	550p	25A1122	40p	25C762	150p	25C1770	100p	25C2437	1000p	25C3043	300p	25C3679	100p	25D807	170p	25D1434	400p	25K237	40p	2555	200p	2555	200p	2800CPU	100p
UPC1470	200p	25A1124	60p	25C783	85p	25C1781	20p	25C2437	1000p	25C3048	200p	25C3680	380p	25D808	170p	25D1435	400p	25K238	40p	2556	200p	2556	200p	2800CPU	100p
UPC1504C	400p	25A1127	50p	25C790	50p	25C1789	100p	25C2440	200p	25C3059	900p	25C3685	500p	25D809	170p	25D1436	400p	25K239	40p	2557	200p	2557	200p	2800CPU	100p
UPC1505C	400p	25A1133	100p	25C792	390p	25C1809	40p	25C2449	200p	25C3068	200p	25C3686	500p	25D810	170p	25D1437	400p	25K240	40p	2558	200p	2558	200p	2800CPU	100p
UPC	25A1136	100p	25C798	80p	25C1812	250p	25C2459	50p	25C3071	150p	25C3687	500p	25D811	170p	25D1438	400p	25K241	40p	2559	200p	2559	200p	2800CPU	100p	
1514CA	200p	25A1142	100p	25C805A	250p	25C1815	100p	25C2461	400p	25C3088	60p	25C3689	500p	25D812	170p	25D1439	400p	25K242	40p	2560	200p	2560	200p	2800CPU	100p
UPC	25A1143	40p	25C828	20p	25C1819	70p	25C2462	50p	25C3090	35p	25C3692	150p	25D813	170p	25D1440	400p	25K243	40p	2561	200p	2561	200p	2800CPU	100p	
1515CA	250p	25A1145	40p	25C829	15p	25C1826	40p	25C2467	60p	25C3091	35p	25C3693	150p	25D814	170p	25D1441	400p	25K244	40p	2562	200p	2562	200p	2800CPU	100p
UPC1520CA	250p	25A1150	100p	25C839	100p	25C1831	120p	25C2471	120p	25C3092	120p	25C3694	150p	25D815	170p	25D1442	400p	25K245	40p	2563	200p	2563	200p	2800CPU	100p
UPC1536C	250p	25A1156	90p	25C869	120p	25C1829	500p	25C2482	20p	25C3097	120p	25C3717	120p	25D816	170p	25D1443	400p	25K246	40p	2564	200p	2564	200p	2800CPU	100p
ZN423	100p	25A1162	30p	25C870	100p	25C1832	400p	25C2483	120p	25C3098	150p	25C3719	150p	25D817	170p	25D1444	400p	25K247	40p	2565	200p	2565	200p	2800CPU	100p
ZN424	100p	25A1169	500p	25C898	275p	25C1833	40p	25C2484	185p	25C3099	185p	25C3720	150p	25D818	170p	25D1445	400p	25K248	40p	2566	200p	2566	200p	2800CPU	100p
ZN425	320p	25A1175	30p	25C930	15p	25C1844	50p	25C2495	1900p	25C3099	100p	25C3746	100p	25D819	170p	25D1446	400p	25K249	40p	2567	200p	2567	200p	2800CPU	100p
ZN426	260p	25A1184	120p	25C941	15p	25C1845	50p	25C2498	50p	25C3101	100p	25C3747	120p	25D820	170p	25D1447	400p	25K250	40p	2568	200p	2568	200p	2800CPU	100p
ZN427	560p	25A1186	50p	25C943	160p	25C1846	35p	25C2500	25p	25C3102	100p	25C3748	120p	25D821	170p	25D1448	400p	25K251	40p	2569	200p	2569	200p	2800CPU	100p
ZN429	215p	25A1190	60p	25C944	80p	25C1847	45p	25C2501	25p	25C3103	100p	25C3749	120p	25D822	170p	25D1449	400p	25K252	40p	2570	200p	2570	200p	2800CPU	100p
ZN435	40p	25A1206	60p	25C945	100p	25C1855	85p	25C2509	80p	25C3105	3600p	25C3781	150p	25D824	170p	25D1450	400p	25K253	40p	2571	200p	2571	200p	2800CPU	100p
ZN448	510p	25A1208	70p	25C950	40p	25C1856	25p	25C2516	125p	25C3112	35p	25C3783	60p	25D825	170p	25D1451	400p	25K254	40p	2572	200p	2572	200p	2800CPU	100p
ZN450	190p	25A1209	100p	25C959	225p	25C1861	400p	25C2519	60p	25C3116	75p	25C3785	100p	25D826	170p	25D1452	400p	25K255	40p	2573	200p	2573	200p	2800CPU	100p
ZN459	640p	25A1210	100p	25C960	75p	25C1862	250p	25C2520	40p	25C3117	75p	25C3786	100p	25D827	170p	25D1453	400p	25K256	40p	2574	200p	2574	200p	2800CPU	100p
ZN462	260p	25A1215	60p	25C982	20p	25C1870	70p	25C2527	300p	25C3118	120p	25C3789	100p	25D828	170p	25D1454	400p	25K257	40p	2575	200p	2575	200p	2800CPU	100p
ZN463	215p	25A1216	60p	25C983	120p	25C1871	60p	25C2534	150p	25C3122	50p	25C3795	175p	25D829	170p	25D1455	400p	25K258	40p	2576	200p	2576	200p	2800CPU	100p

FLYBACK TRANSFORMERS

FERGUSON			
00D-4208-001	TX9	£14.00	
00D-4208-002	TX9	£14.00	
00D-4235-002 01G	TX90	£14.00	
06D-3-088-001	TX100	£14.00	
GRUNDIG			
Z9201-019-05		£14.00	
Z9201-024-11		£14.00	
PHILIPS			
PS 140-17112	G11	£14.00	
PS 140-10306	G90AE	£11.50	
PS 140-10353	G90B	£15.00	
PS 140-10151	K12	£15.00	
PS 140-10283	K30 K30111	£15.00	
PS 140-10246	K40	£13.00	
PS 140-10247	KT4	£14.00	
PS 140-10149	KT2	£9.00	
PS 140-10161	KT3	£9.00	
PS 140-17033	GB	£10.00	
PS 140-17089	GB	£10.00	
PS 140-10328	NC3	£14.00	
ITT			
	CVC20	£11.50	
	CVC25	£11.50	
	CVC30	£11.50	
HITACHI			
OUTPUT TV MODULE	HM6251 (REF 2370551)	£5.50	
	HM6232	£8.00	

IDLER TYRES

AKAI	M327773	Order Code	T01
AKAI	M3266950J2		T02
GOLDSTAR	VXP021		T03
HITACHI	8861471		T07
HITACHI	8861482		T04
HITACHI	8889871		T05
JVC/FERGUSON	PU48967B		T06
JVC/FERGUSON	PU5138C		T07
JVC/FERGUSON	PU5140A		T08
JVC/FERGUSON	PU5537Z		T10
JVC/FERGUSON	PU5537Z		T11
PANASONIC	VXP0329		T11
PANASONIC	VXP0343		T12
PANASONIC	VXP0344		T13
PANASONIC	VXP0401		T14
PANASONIC	VXP0433		T15
PANASONIC	VXP0463		T16
PANASONIC	VXP0521		T18
PANASONIC	VXP0581		T19
PANASONIC	1430662T115620		T20
SHARP	NIDL0065GEZZ		T21
SHARP	NIDL0066GEZZ		T22
SHARP	NPLV0107GEZZ		T22

Price 18p for pack of 5 for each model Price 15p for pack of 10 for each model

IDLERS & PULLEYS REPLACEMENT

AKAI			
VS1-2, VS4-5, VS15	FF-REW IDLER	M1327773	£4.50
VS3, 6, 12, 56, 58, 59	T-UP IDLER	BV327815	£6.00
VS1-2, VS4-5, VS15	IDLER	BV321979	£6.00
VS3, 6, 12, 58, 59	IDLER ASSY	MZ366960J2	£11.00
V9700	UNLOADING	PU47752	£4.50
VS125, 126, 155,	UNLOADING	PU46381	£4.50
VS165, 240, 244, 245, 247, 248, 250, 512, 515, 516	REW IDLER	PU46380	£6.00
VS22, 38, 105, 112, 115, 116, 205, 220	REW IDLER	PU46380	£6.00
VF7100, VS9300	REEL IDLER	BV327815	£3.00
VS9500, VS9800	REEL IDLER	BV336067	£5.00
VS9500, VS9800	REEL IDLER	BR347731	£5.50
VP77, VS10	CLUTCH	ML373043	£13.00
VP80	CLUTCH	BV321761	£3.00
VS1, 3, 4, 9, 12	FF IDLER	W321762	£4.25
VS23, 35, 37, 53, 55	REW IDLER		
VS56, 75, VS47	REW IDLER		
VS9700	FF IDLER		
VS9700	REW IDLER		
AMSTRAD			
VCR7000	IDLER	150280	£1.50
TVR1, VCR4500	CLUTCH	150873	£3.75
VCR4600, VCR5200, VCR9000	CLUTCH		
TVR1, VCR4500	GEAR HOLDER	761284	£3.50
VCR4600, VCR5200, VCR9000	REF CLUTCH		
TVR1, VCR4600	REF CLUTCH		
VCR5200	CLUTCH	153202	£2.80
VCR6000, VCR6100	CLUTCH		
VCR4500, VCR9000	CLUTCH		
VCR4500, VCR4600	MOD KIT	(TAPE CREATING)	£4.00
VCR4700	MOD KIT TAPE CREATING FOR AMSTRAD		
VCR4500, 4600, 4700	MOD KIT TAPE CREATING FOR AMSTRAD		
FERGUSON			
3V00, 3V01, 3V16	T-UP IDLER	PU47752	£4.50
3V22, 3252, 8900, 8901, 8904, 8906	T-UP IDLER	PU49280	£5.50
3V16, 3V22	T-UP IDLER	PU49280	£5.50
8903, 8905, 8912, 8924	REEL IDLER	PU48967	£2.50
3V23, 3V29, 3V32	REEL IDLER	PU48967	£2.50
3V31, 3V32, 3V35, 8923, 8924, 8929, 8930, 8931, 8940, 8941, 8942	ROLLER ASSY	PU49042A	£4.00
3V22, 3V35, 3V36, 3V38, 3V39, 3V43, 8930, 8931, 8940, 8941, 8942	T-UP IDLER	PU51380	£1.25
3V29, 3V30, 3V31	T-UP CLUTCH	PU51380	£2.25
3V32, 8930, 8931, 8940, 8941, 8942	T-UP CLUTCH	PU51380	£2.25
3V35, 3V36, 3V38	REEL IDLER	PU55374	£2.85
3V38, 3V48, 8943, 8944	T-UP CLUTCH	PU55373	£2.00
3V35, 3V36, 3V38	T-UP CLUTCH	PU55373	£2.00
3V39, 3V48, 8943, 8944	T-UP CLUTCH	PU55373	£2.00
3V58, 3V59, 3V64	IDLER ARM	PU58645	£2.25
RV65, FV10, FV11, FV12, FV13, FV14, FV20, FV21, FV22, FV26	IDLER ARM	PU58645	£2.25
FV30, FV32, FV33, 8950, VC1411	CLUTCH ASSY	PU55822	£13.50
V442, V443	CLUTCH ASSY	PU57658	£11.50
V443, V444, V445	CLUTCH ASSY	PU57658	£11.50
V448, V453, V454, V455, V457, 8947, 8948	T-UP CLUTCH	PU56043-14	£2.80
V442, V443, V444	SUPPORT CLUTCH	PU56044-15	£2.80
V445, V448, V453, V454, V455, V456, V457, 8947, 8948	SUPPORT CLUTCH	PU56044-15	£2.80
3V00, 3V01, 3V16	LOADING IDLER	PU43681	£4.00
3V22, 3292, 8900, 8901, 8902, 8903, 8904, 8906, 8909	LOADING IDLER	PU43681	£4.00
8912, 8922	LOADING IDLER	PU43681	£4.00
3V00, 3V01, 3V16	REW IDLER	PU43680	£6.00
3292, 8900, 8901, 8904, 8906	REW IDLER	PU43680	£6.00
3V16, 3V22, 8902	IDLER	PU49281	£1.70
8909, 8912, 8922	IDLER	PU49281	£1.70
3V16, 3V22, 8902	IDLER	PU49283	£1.00
8909, 8912, 8922	IDLER	PU49283	£1.00

RISHER			
FVHP420, 520, 530	FF-REW PULLEY	H638531	£1.00
FVHP615, 618, 620	COMP. IDLER ASSY	F1430420400300	£2.30
FVHP622, 710, 711, FVHP720, 721, 722, FVHP725, 730, 830	GEAR IDLER ASSY	F1430490400900	£4.50
FVHP905, 906, 907, FVHP910, 911, FVHP915, 916, 918	GEAR IDLER ASSY	F1430410400900	£5.50
FVHP725, 730, 830, FVHP840	REEL T-UP ASSY	F1430420400700	£4.50
FVHP615, 618, 620	REEL T-UP ASSY	F1430420400700	£4.50
FVHP622, 710, 711, FVHP720, 721, 722	GEAR IDLER ASSY	F14304904002400	£4.00
FVHP910, 911, 915, FVHP916, 918	IDLER	F1430420400700	£4.50
FVHP975, 980, 990	IDLER	F12430510404200	£6.00
FVHP990, 5000, 5005	CLUTCH		
FVHP5050, 5075, 5100	CLUTCH		
FVHD40, 55, 140	REEL DRIVE ROLLER		
FVHP10, 20	GEAR		
FVHP975, 980, 990	CLUTCH		
FVHP975, 980, 990	CLUTCH		
FVHP420, 520, 530	IDLER		
FVHP420, 520, 530	TAKE UP IDLER		
FVHP990	LOADING GEAR		
VBS3500	REEL DRIVE PULLEY		
VBS3500	IDLER		
VBS7000	REW IDLER		
GOLDSTAR			
GHV1221, 1232, 1240	CLUTCH GEAR	435038A	£2.50
GHV1241, 1242, 1243, GHV1244, 1245, 1246, GHV1247, 1248, 8000	CLUTCH GEAR		
GHV8200, 8210, 8215, GHV951, VCP4100, 4130	IDLER		
GHV121, 122, 123, GHV124, 125, 126, 127, 975, 976			

JUST ARRIVED

VIDEO HEADS

AKAI	
VSF600, VSF650	3600P
VP7100, VP7200, VP77	1500P
VS155, VS165	2500P
VS20, VS22, VS24, VS25, VS26, VS27, VS422,	
VS425, VS426, VS427, VSF10, VSP8,	
VSP9	1400P
VS240, VSP82, VS202	1350P
VS33	2400P
VSR9	1500P
AMSTRAD	
VCR8800, VCR8804, VCR9340	2400P
DD8900, DD8904, TVR4, VCR6200, VCR8600,	
VCR8602, VR8700	1200P
VCR8603, VCR8604, VCR8704, VCR8714	1350P
BAIRD	
VC14L	3000P
VHS82	7000P
BLAUPUNKT	
CR1000, CR1200, CR1500	4650P
CR1800	4100P
RTV321, RTV322	1700P
RTV330	2300P
RTV333	1000P
RTV338	2800P
RTV348	2700P
RTV404, RTV414	3000P
RTV635	3000P
RTV640	3000P
RTV750, RTV800, RTV900	3500P
RTV810	4400P
RTV910	4500P
JVC	
HRD330, HRD337, HRD440, HRD637, HRD641,	
HRD660, HRFC100	2100P
JVC AND FERGUSON	
8902/8903/8909/8912/8922	1000P
8923/8925/8929/8935	650P
8931/8933	750P
FV43H, HRD860	3800P
VC141L, HRD190, HRD610	3050P
FV44L	2200P
BR1600, HRD142, HRD156, HRD152	1550P
BR6200	720P
HRD154, HRD217, HRD321, HRD350, HRD521,	
HRD522, HRD525, HRD527, HRD550	1700P
HRD580, HRD620, HRD650	2900P
FIDELITY	
VR900, VR910	1500P
FISHER	
FVHD140, FVHD40, FVHP1, FVHP10, FVHP20	
FVHP40, FVHS10	1150P
FVHP200, FVHP210, FVHP300, FVHP310	1800P
FVHP500, FVHP5100, FVHP730, FVHP830	1100P
FVHP980	2500P
FUNAI	
E1100, VIP5000	1100P
VCR5840, VCR8007, VIP2500A, VIP3000A,	
VIP6000, VIP150	2000P
VCR4530, VCR6000, VCR6100	1300P
VCR8103, VCR600, VCR6100	1600P
VCR8103, VCR8107	2200P
VIP300A MKII	1900P
GEC	
V4005H	1500P
GOLDSTAR	
GHV1232, 1233, 1241, 1242, 1243, 1244, 1290,	
1291, 1295, 1296, 1891, VCP4130, 4300, 4301,	
4305, 4306, 4310, 4311, 4315, 4316, 4320, 4321,	
4326	1300P
GRUNDIG	
VS456	1600P
SE6110, SE9100, TVR4510, TVR5510, VS500,	
VS510, VS5180, VS6190, VS700, VS900	1400P
VS790, VS930, VS940	2400P
MVS660, SE6160, VERONA, VS660,	
VS6690	3500P
MVS710, MVS720, MVS910, SE9120, VS800,	
VS810, VS910, VS920, SE7120, VS710,	
VS720	1700P
VS160, VS740	4400P
VS170	4600P
VS680	4600P
HINARI	
VCR34H, VTV200, VXL90	1300P
HITACHI	
VT15, VTP10, VTP30	1000P
VT16B, VT260, VT498	2600P
VT570, VT575, VT576, VT580, VT585,	
VT588	3400P
VT5600	1100P
VT60	1300P
VT660E	2600P
VT6700, VT6800	1200P
VTL30	2000P

VT522, VTM620, VTM622, VTM720, VTM722,	
VTM822	1900P
VTM725, VTM726, VTM728	1400P
ITT	
VR3520, VR3701, VR3719, VR3720, VR3721,	
VR3759, VR9720	2000P
VR3730, VR3731, VR3749,	2500P
VR3907, VR3908	1600P
VR3918, VR3919, VR3938	1500P
VR396B	7000P
VR3984	2300P
VR3958, VR4993	650P
VR4913, VRP3833	650P
LUXOR	
9245, 9251, 9254	1225P
9255, 9256	2150P
9270, 9271, 9273	1800P
9272, 928217	2700P
9252	2500P
928017, 928077, 928097, 929107, 929117	1700P
9253	2500P
9281	2700P
9284, 9295, VR3701, VR3721, VR3731,	
VR3761	2100P
MATSUI	
VX600	1100P
VX750	1500P
VX990	1500P
MITSUBISHI	
HSE12, HSE22, MX1	2200P
HS411EZ, HS411GZ	2900P
HS273	1700P
HSB10, HSB20, HSE10, HSE20, HSE21,	
HSE41	2200P
HSB11, HSB21	2200P
HSB30	2400P
HSE31, HSB31, HSE32	2800P
HSE50	3300P
NATIONAL	
NV8050, NV8051	2800P
AG1000, AG1050, NV260	1600P
AG6010, AG6015	2500P
AG6840	2400P
NV200	725P
NVD80	3900P
NVF65, NVH75	3200P
NVF51	4200P
NVG19	2300P
NVJ33, NVL21, NVJ30	1800P
NVJ35	2500P
NVM1, NVM3, NVM5	4200P
AG2100, AG2200	700P
NVF65	3200P
N.E.C.	
DX2000	3400P
DS6000	3500P
DX1000, DX1600, N9040, N9053, N9055	1300P
DX4000, N9610, DX3000	3000P
N9052, N9530	3400P
N9110, N9120, N914C	2400P
VCP1	1700P
PVC2300, PVC240, PVC740, PVC744, PVC760,	
PVC764	1400P
SAMSUNG	
VM1560, VN1561	2200P
SANYO	
VHR7900	3000P
SHARP	
VC585, VC685	2000P
VC90ET	3900P
VFH815	2800P
SONY	
SLV373UB	2600P
TOSHIBA	
V660	2350P
V880MS	2600P
V700G	3700P
V500G, V509G	2500P
V9680	2900P
V300G, V301, V305, V309G	2550P
V61, V63	1700P
V110, V120, V130, V140, V210, V220	1800P
TELEVISION ON/OFF	
MAINS SWITCHES	
Baur, Normende, Nova, Pioneer, Quelle, Saba,	
Salora, TEC, Thomson & Vega	375P
VIDEO MOTORS	
HITACHI	
VT11, VT14, VT15, VT16, VT17, VT19, VT35,	
VT39, VT57, VT88 (capstan motor)	3100P
BANG & OLUFSEN	
VHS65, VHS90 (capstan motor)	3100P

LOADING MOTOR UNITS

ITT	
VR3605, VR3905, VR3955, VR3985	1500P
VP2826, VR3906, V43926, VR3976	1250P
VP3946, VR3906, VR3948, VR3986, VR3995,	
VR6948	1500P
JVC	
HRD110, HRD111, HRD120, HRD121,	
HRD225	1500P
HRD140, HRD150, HRD157M, HRD158MS,	
HRD160, HRD250, HRD257MS, HRD566,	
HRP50	1250P
HRD455, HRD725, N895	1500P
SABA	
VR6005, VR6014, VR7004, VR7011, VR8011,	
VR8014	1500P
VR6006, VR6007, VR608, VR6009, VR6018,	
VR7007, VR7018, VR9006	1250P
VR6016, VR6038, VR7016	1500P
TELEFUNKEN	
VR1925, VR1930, VR1940, VR1950, VR925,	
VR930, VR940, VR950	1500P
A920, VR2920, VR12970, VR7921, VR7926,	
VR7931, VR7971, VR975	1250P
VR1970, VR1980, VR7970, VR7980, VR970,	
VR980	1500P
THOMSON	
V320, V321, V323, V326, V4200, V4300	1500P
V342, V343, V352, V353, V360, V4210, V4230,	
V4260	1250P
V364, V36B, V4400, V6000	1500P
THORN-FERGUSON	
3V35, 3V36, 3V38, 3V39, 3V49, 8943, 8944	1500P
3V44, 3V45, 3V46, 3V54, 3V55, 3V57, 8947,	
8947B, 8948	1250P
3V43, 9845	1500P
TOSHIBA	
V55, V57	1500P
V65, V66, V67	1250P
V61, V63	1500P

CASSETTE HOUSING

AKAI	
VS35, VS53, VS55, VS66, VS75	2600P
FERGUSON	
FV31R	4300P
JVC & FERGUSON	
HRD515, HRD520, HRD527, HRD540, HRD550,	
HRD580, HRD600, HRD610, HRD620, HRD660,	
HRD670, HRD830, HRD840, HRD850, HRD860,	
HRD405G, HRD6600 & FV37H	2400P

IC TRANSISTORS

M491BB	500P
SAA5243PE	800P
TIP112H	50P
UPC148EH	150P
STR4090A	650P

IC AND TRANSISTORS

BU506DF	120P
BUZ11	200P
BUZ80	200P
M494B1	700P
SAA5231	300P
SAA1293	550P
S2000A3	175P
S2000AF	175P
S2055A	175P
S2000AF	200P
S2530A	100P
TEA201BA	200P
UC3844	100P
UPC1185H2	400P

REMOTE CONTROLS

AKAI	
RC-V10A	1000P
RCV37B	1000P
V25A	1000P
BUSH	
2020T, 2114T, 2321T, 2514T	1000P
2020, 2114, 2321, 2514	1000P
DECCA	
RC70	850P
FISHER	
RC905B	1000P
GRANADA/REDIFFUSION	
UNIVERSAL, 79500C, 986700	850P
SATELLITE	
MK4 TEXT, 70115G, 70133G, 70357E	850P
MK4A TEXT, 70375C	850P
95288E	1000P
94490D	1000P

REMOTE CONTROLS

Description	Order Code	Price
GRUNDIG		
TP160E	RC 107	900p
TP200, TP300	RC 380	800p
TP400	RC 401	800p
TP590-600	RC 600	850p
TP390, TP610	RC 610	850p
TP621	RC 621	850p
TP630, TP650	RC 650	850p
TP660	RC 660	850p
TP661	RC 661	850p
HITACHI		
CLE800-CLE830	RC 140M	850p
A617402/655602	RC 192	875p
A51210/230	RC 900	800p
A514790	RC 901	850p
A5088470	RC 902	800p
A518612	RC903	900p
SCL002	RC904	850p
C2096	RC 905	850p
A511940	RC 906	800p
655602H	RC 907	850p
ITT		
IFB13, 14, 15	RC 143	875p
FS4	RC 148	850p
RG305	RC 305	825p
RG306	RC 306	825p
FS9/1-10/1	RC 307	850p
VS5 RUK	RC 308	825p
VS4-1	RC 310	850p
MULTICONTROL (17C20)	RC 311	800p
KORTING		
18279, 18396, 18460, 18521 SE	RC 108	850p
40540 VTS	RC 108	900p
LOEWE		
DC11	RC 146	850p
MATSUI		
010270601	RC 889	850p
VX770	RC 892	850p
METZ		
JAVA COLOR (6890)	RC 166	850p
COLOR (7156)	RC 183	850p
JAVA (7180)	RC 184	850p
MITSUBISHI		
939P/03607, 939P/03609	RC 140M	850p
NOKIA		
SATELLITE	RC 550	850p
NORDMENDE		
TC2336	RC 351N	850p
CMC1, TC3519	RC 356	875p
OCEANIC		
390C9500	RC 339	900p
ORION		
RC53	RC 892	850p
PANASONIC		
EUR51200	RC 200	850p
TC2200	RC 201	850p
VSQ0357/NV730	RC 202	875p
TNQ1621	RC 203	900p
PHILCO		
CARVEL, CONCORDE, MERCURY, TELESTAR	RC 108	850p
TC10	RC 152	900p
PHILIPS		
RC5002,5154	RC 134	850p
KT3 NON TEXT	RC 135	825p
69117032	RC 178	875p
69117194	RC 180	875p
RC5991-UNIV	RC 300	850p
RC38	RC 301	875p
KT3 TEXT	RC 5301	800p
RC5352	RC 5352	800p
RC5375	RC 5375	850p
RC5 STANDARD	RC 5534	850p
RC5901	RC 5901	850p
RC5903	RC 5903	800p
SABA		
T6772	RC 149	900p
TC319-320	RC 328	875p
TC356	RC 356	875p
TC358	RC 358	850p
TC360	RC 360	800p
TC365	RC 365	800p
SALORA		
SERIES L	RC 190	875p
86173	RC 882	850p
SANYO		
RC218, RC222, RC228, RC238	RC 140M	850p
JXGE	RC 878	850p
JXDE	RC 884	850p
VHR2300	RC 890	850p
RC628	RC 865	900p
SHARP		
G0121CESA, 123CESA, 204, 251	RC 140M	850p
SIEMENS		
FC616	RC 130	850p
FC631	RC 132	850p
FC742	RC 164	900p
SONY		
RM604, RM605, RM606	RC 140	850p
32 CHANNEL	RC 140M	850p
RM613	RC 141	850p
RM632, RM636	RC 160	850p
TATUNG		
FXA	RC 877	850p
RC70	RC 883	750p
FX70 FASTTEXT	RC 894	850p
TELEFUNKEN		
FB632	RC 632 ST	850p
FB639	RC 639 ST	850p
THORN/FERGUSON		
3V35-42	RC 342	850p
3V31-32	RC 344	850p
3V57-58	RC 628	900p
TX10 TEXT	RC 732	750p
TX10 STEREO TEXT	RC 738	750p
TX9-90-100	RC 740	750p
3V55, FV11	RC 783	900p

Description	Order Code	Price
TX100 FASTTEXT	RC 785	800p
TX100 STEREO FASTTEXT	RC 789	800p
PROFESSIONAL	RC 790	800p
TOSHIBA		
CT937	RC 950	850p
CT9117	RC 951	850p
201R48	RC 952	850p
UNIVERSAL PROGRAMMABLE REMOTE CONTROL		
Controls up to 4 different devices which use infra red remote controls including TV, audio, VCR and satellite. (need original remote control TC program)		
Order code: IR100R		Price: 1950p

We stock Remote Controls for over 5000 different models. Ring for further details on 081-900-2329.

BACKUP BATTERIES

Description	Price	Order Code
REPLACEMENT PHILIPS NI-CAD BACKUP BATTERIES		
Replaces Philips Part No's: 138-10138, 138-10313. 1.2V - 90mAh	120p	
Replaces Philips Part No's: 138-10229, 2.4V - 90mAh	200p	
REPLACEMENT FERGUSON NI-CAD BACKUP BATTERIES		
Replaces Ferguson Part Nos: 00E6-066-001, 2.4V		
Used on: 3V35, 3V56, 3V58, 3V65	250p	
Replaces Ferguson Part No: 00E6-067-001, 1.2V		
Used on: TX10	150P	

REPLACEMENT LINE OUTPUT TRANSFORMERS

Description	Price	Order Code
HITACHI 2433752	1500p	LOT01
ORION 3714002	1500p	LOT02
FIDELITY ZX300	1500p	LOT03
FE TX100 90 DEG	1500p	LOT04
SABA 490007182	1500p	LOT05
FE TX90 WHITE	1650p	LOT06
ITT D307/37 EQ	1600p	LOT07
BLAUPUNKT 210	1600p	LOT08
GRUNDIG 2922010	1600p	LOT09
ITT CVC800/1/3	1500p	LOT10
ITTD218/37 EQ	1600p	LOT11
NORMENDE 5255	1600p	LOT12
SABA 81000 200	1600p	LOT13
SALORA T236 EQ	1650p	LOT14
SABA 811-50-24	1600p	LOT15
SABA 770223500	1600p	LOT16
TELEFUNKEN AT1	1450p	LOT17
TELEFUNKEN EQ	1400p	LOT18
SALORA FM0218B	1600p	LOT19
NORMENDE 5255	1600p	LOT20
ITT CVC 1150/1	1500p	LOT21
ITT COMPACT 80	1500p	LOT22
FE TX100 GREEN	1450p	LOT23
HINARI CT4/5 5113	1500p	LOT24
SELECO 6320410	1600p	LOT25
BLAUPUNKT 8667	1600p	LOT26
ITT COMPACT B1	1450p	LOT27
ITT CT3326 MUL	1500p	LOT28
ITT D066/37 EQ	1600p	LOT29
ITT 3546 EQ	1500p	LOT30
LUXOR 5810110	1600p	LOT31
SABA 849380920	1600p	LOT32
HITACHI 2434141 CP	1450p	LOT33
FE TX100 110 D	1700p	LOT34
HANTAREX 28021	1600p	LOT35
SHARP C3700 EQ	1600p	LOT36
HITACHI 2432981 CP	1500p	LOT37
FERGUSON 00D3-508-002	1650p	LOT38
Fits Chassis TX99 41cm + 51cm		
Used On: 51K2, 51J8, 51J7, 41H3, 41H3, 41H2, 51K3		
PANASONIC TLF14567F	1850p	LOT39
Used On: TC2043, TC2243, TX300		
PANASONIC TLF14568F	1850p	LOT40
Used On: TX2231, TX2244		
PANASONIC TLF14584F	2350p	LOT41
Used On: TC2210, TC2160, TX1752, TX2112		
TX2112, TX2162, TXC22		
PANASONIC TLF14586F	2350p	LOT42
TC1651, TC2051, TC2061, TC2253, TC2263, TX5500		
HINARI	1600p	LOT43
Used On: CT15		
HITACHI 2434274	1400p	LOT44
CPT2174, CPT2176, CPT2178, 2434274		

We stock line output transformers for over 100 different models. Please ring 081-900 2329 for more information.

FAULT FINDING GUIDE BOOK

Video Recorders Edition 3, 1994

Lists more than 4000 faults for 43 different brands

Price: £9 45p Only. No VAT
Order Code: BOOK01

Satellite Repair Manual Edition 2

A comprehensive guide to receiver reviewing, featuring stock faults and installation tips.

Price 1475p Only No VAT Postage 100p
Order Code: BOOK03


VIDEO HEAD CLEANING STICKS



Order Code: SP14

Price: 17p Each
15p Each Pack of 10pcs
13p Each Pack of 25 pcs

VIDEO MAINTENANCE TOOLS

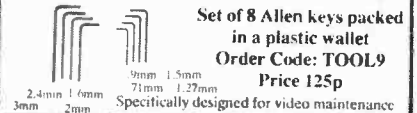

Set of 8 Allen keys packed in a plastic wallet
Order Code: TOOL9
Price 125p

FUSES

Value	TIME LAG (20mm)		QUICK BLOW (20mm)	
	Order Code	Price	Order Code	Price
160mA	FUSE01	75P	FUSE17	60P
250mA	FUSE02	75P	FUSE18	60P
315mA	FUSE03	75P	FUSE19	60P
400mA	FUSE04	75P	FUSE20	60P
500mA	FUSE05	75P	FUSE21	60P
630mA	FUSE06	75P	FUSE22	60P
800mA	FUSE07	60P	FUSE23	60P
1A	FUSE08	60P	FUSE24	60P
1.25A	FUSE09	60P	FUSE25	60P
1.6A	FUSE10	60P	FUSE26	60P
2A	FUSE11	50P	FUSE27	60P
2.5A	FUSE12	50P	FUSE28	60P
3.15A	FUSE13	55P	FUSE29	50P
4A	FUSE14	55P	FUSE30	50P
5A	FUSE15	60P	FUSE31	50P
6.3A	FUSE16	60P	FUSE32	50P

CERAMIC PLUG TOP


3A	FUSE33	100P
5A	FUSE34	100P
13A	FUSE35	100P

ALL THE ABOVE PRICES ARE FOR PACKS OF 10 FUSES

Solder Mop 1.2mm x 10 metres	300P
Tube Silicon Grease 50 gram	200P
Tube Heat Sink Compound 25 gram	150P

UNIVERSAL HEAD EXTRACTOR TOOL

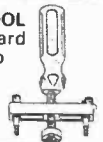
Hand tool designed for extracting hard to remove heads without damage to either the head or the mounting assembly. Adjustable so as to suit various brand heads. PRICE - £7



GRANDATA LTD

K.P. HOUSE, UNIT 15,
POP IN COMMERCIAL CENTRE,
SOUTHWAY, WEMBLEY,
MIDDLESEX, ENGLAND HA9 0HB
Tel: 081-900 2329 Fax: 081-903 6126

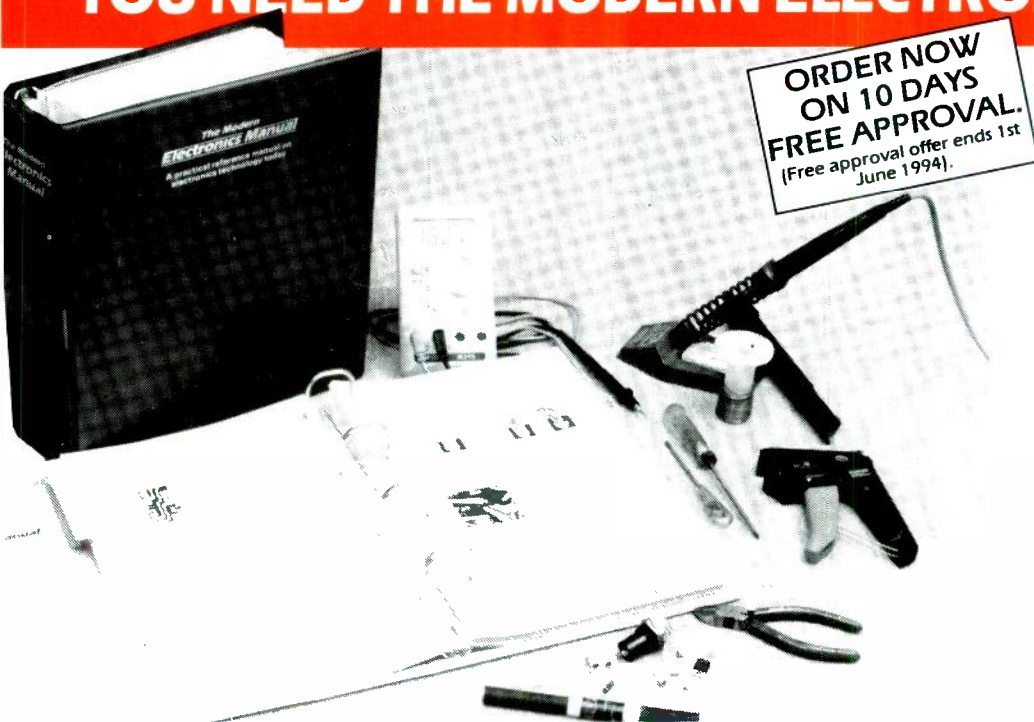WHETHER ELECTRONICS IS YOUR HOBBY OR YOUR LIVELIHOOD . . . YOU NEED THE MODERN ELECTRONICS MANUAL



The essential reference Work

- Easy-to-use format
- Clear and simple layout
- Regular Supplements
- Sturdy ring-binder
- News of latest developments
- Full components checklist
- Extensive data tables
- Detailed supply information
- Ready-to-transfer PCBs
- Comprehensive subject range
- Detailed assembly instructions
- Professionally written

EVERYTHING YOU NEED TO KNOW ABOUT ELECTRONICS!

If the fascinating and fast-changing world of electronics is your livelihood, your study subject or simply your passion, the revised edition of **THE MODERN ELECTRONICS MANUAL** is the reference work for you to have at your side.

The Base Manual contains information on the following subjects:

BASIC PRINCIPLES: Symbols, components and their characteristics, passive component circuits, power supplies, acoustics and electroacoustics, the workshop, principles of metrology, measuring instruments, digital electronics, operational amplifiers, timers, physics for electronics.

CIRCUITS TO BUILD: Construction techniques, radio, telephony, microcomputing, measuring instruments, vehicle electronics, security, audio, power supplies, electronic music (over 25 different projects).

REPAIRS AND MAINTENANCE: Basic circuit operation for radio, television, audio/hi-fi, telephones.

DATA: Diodes, transistors, thyristors and triacs, digital and linear i.c.s, microprocessors.

The Manual also covers **Safety, Specialist Vocabulary with Abbreviations** and **Suppliers**.

OVER 1,000 pages, with over 900 diagrams and photographs, A4 looseleaf format weighing over 3.5kg.

ALL-IN-ONE AND EASY-TO-USE: A sturdy ring-binder allows you to use the Manual on your workbench. The looseleaf format also means you can slot in the regular supplements as they arrive – so all your information is there at a glance.

EXTENSIVE GLOSSARY: Should you come across a technical word, phrase or abbreviation you're not familiar with – simply turn to the glossary included in the Manual and you'll find a comprehensive definition in plain English.

Now – at last – the most comprehensive reference work ever produced at a price you can afford, the revised edition of **THE MODERN ELECTRONICS MANUAL** provides you with all the essential information you need.

Over 1,000 pages of well-organised and clearly explained information is brought to you by an expert editorial team whose combined experience ensures the widest coverage.

Regular supplements to this unique publication, each around 160 pages, mean that you will always be kept abreast of the latest developments from around the world as they occur

REGULAR SUPPLEMENTS

Unlike a book or encyclopedia, the Manual is a living work – continuously extended with new material. Recent or upcoming supplements include radio, superconductors, electric motors, basic electronic building blocks for beginners which can be joined together to construct elaborate circuits, filters, IBM PC and compatibles (including updating/expanding PCs). Supplements are sent to you approximately every two months. Each supplement contains approximately 160 pages – all for only £23.50 + £2.50 p&p. You can of course return any supplement which you feel is superfluous to your needs.

RESPONDING TO YOUR NEEDS

We are able to provide you with the most important and popular, up to the minute, articles in our supplements. Our unique system is based on readers


requests for new information. Through this service you are able to let us know exactly what information you require in your Manual. You can also contact the editor directly in writing if you have a specific technical request or query relating to the Manual.

ASSEMBLING ...

There's nothing to beat the satisfaction of creating your own project. From basic principles to circuit-building, the Manual describes clearly, with appropriate diagrams, how to assemble radios, loudspeakers, amplifiers, car projects, measuring instruments etc. The revised edition of The Modern Electronics Manual contains practical, easy-to-follow instructions for building a wide range of projects. It shows you how to make fun gadgets such as a remote control door opener and a digital rev. counter for your car. It also tells you how to construct useful devices like test gear, security and

baby alarms – plus – many more popular devices.

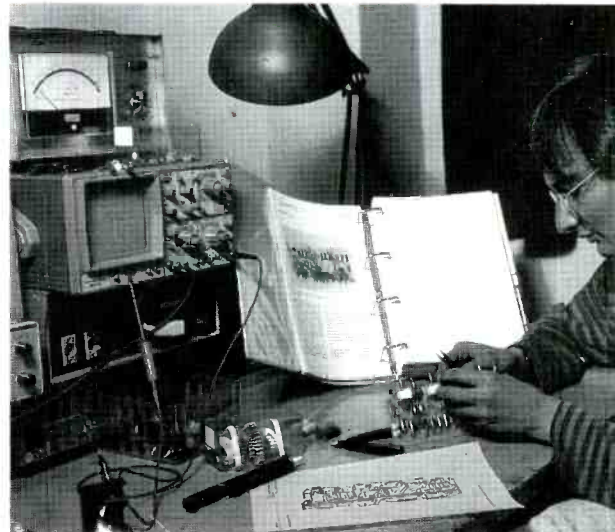**Wimborne Publishing Ltd.,
6 Church St, Wimborne,
Dorset BH21 1JH
Tel: 0202 881749 Fax: 0202 841692**



THE MODERN ELECTRONICS MANUAL

Revised Edition of Basic Work: Now contains over 1,000 pages of information.

Regular Updates: Approximately 160-page supplements of additional information which are forwarded to you immediately on publication. These are billed separately and can be discontinued at any time.

Presentation: Durable looseleaf system in large A4 format (297mm x 210mm)

Price of the Basic Work: £39.95 + £5.50 p&p (to include a recent supplement free).

PLEASE send me on 10 days free approval (offer ends June 1st 1994) **THE MODERN ELECTRONICS MANUAL**. If I decide to keep the Manual, I shall then pay **only £39.95** plus £5.50 postage and packing at the end of the 10 days approval period. (Should I decide **not** to buy the Manual I will return it to you and not owe you anything.) I shall also receive the appropriate supplements several times a year. These are billed separately and can be discontinued at any time.

PLEASE NOTE:

10 DAY FREE APPROVAL OFFER EXPIRES ON JUNE 1st 1994.

FULL NAME
(PLEASE PRINT)

ADDRESS.....

..... POSTCODE

Telephone No:.....
(Required for Manuals on approval – we will not ring you unless there is a problem with supply etc.)

I AM OVER 18

SIGNATURE.....

May 1 (Parent or guardian must sign if under 18)

ORDER FORM

Simply complete and return the order form to the following address:

**Wimborne Publishing Ltd, 6 Church Street
Wimborne Dorset BH21 1JH**

Manuals on 10 days approval may be subject to delay in dispatch; if you require a manual quickly please pay in advance – we offer a 30 day MONEY BACK GUARANTEE – if you are not happy with the Manual simply return it to us for a full refund.

10 day free approval offer ends 1st June 1994.

OVERSEAS ORDERS: All overseas orders must be prepaid but are supplied under a money-back guarantee of satisfaction. If you are not entirely happy with the Manual return it within a month for a refund of the purchase price (you do have to pay the postage). **SEND £39.95 PLUS THE POSTAGE SHOWN BELOW:**

EIRE	AIR MAIL ONLY £11
EUROPE (E.E.C. Countries)	AIR MAIL ONLY £20
EUROPE (non E.E.C.)	SURFACE MAIL £20, AIR MAIL £26
U.S.A. & CANADA	SURFACE MAIL £25, AIR MAIL £32
FAR EAST & AUSTRALIA	SURFACE MAIL £31, AIR MAIL £33
REST OF WORLD	SURFACE MAIL £25, AIR MAIL £44

Note surface mail can take over 10 weeks to some parts of the world. Each manual weighs about 4.5kg when packed.

All payments must be made in £'s Sterling payable to Wimborne Publishing Ltd. We accept Mastercard (Access) and Visa credit cards.

VIDEO SERVICE KITS

AMSTRAD
VCR700
Contents
BELT SET, PINCH ROLLER, REEL IDLER, VIDEO LAMP
Order Code: SK41 £5.50

FERGUSON & JVC
3V2/43
HR0455/HRD725
Contents
BELT SET, PINCH ROLLER, CLUTCH MECHANISM, TENSION BAND
Order Code: SK37 £17.50

Economy Kit Contents
BELT SET, PINCH ROLLER, SUPPLY CLUTCH, TAKE UP CLUTCH
Order Code: SK38 £9.50

3V58/59/64/65
HRD170/180/210/230/300/320/370/400/430/530/700/750
HRSS000
Contents
BELT SET, PINCH ROLLER, IDLER ARM, TENSION BAND
Order Code: SK44 £8.50

3V29/3V30
HR7200/7300/7350
Contents
BELT SET, PINCH ROLLER, TENSION BAND, IDLER TYRES
Order Code: SK05 £6.00

3V35/36 38/39/49
HRD110/111/120/225
Contents
BELT SET, PINCH ROLLER, TENSION BAND, IDLER TYRES
Order Code: SK04 £5.50

3V31/3V42
HR7600/7610/7650/7655
Contents
BELT SET, T/U REEL TABLE TYRE, PINCH ROLLER, REEL IDLER, T/U CLUTCH, T/U IDLER, TENSION BAND, VIDEO LAMP
Order Code: SK33 £12.00

Economy Kit Contents
BELT SET, T/U REEL TABLE TYRE, PINCH ROLLER, REEL IDLER TYRE, T/U IDLER TYRE, T/U CLUTCH
Order Code: SK34 £5.50

3V35/36/38/39/49
HRD110/111/120/121/225
Contents
BELT SET, T/U REEL TABLE TYRE, SUPPLY REEL TABLE TYRE, PINCH ROLLER, T/U CLUTCH, T/U IDLER, REEL IDLER, TENSION BAND
Order Code: SK35 £10.50

Economy Kit Contents
BELT SET, T/U REEL TABLE TYRE, SUPPLY REEL TABLE TYRE, PINCH ROLLER, T/U CLUTCH, T/U IDLER TYRE, REEL IDLER TYRE
Order Code: SK36 £5.80

3V29/3V30
HR7200/7300/7350
Contents
BELT SET, T/U REEL TABLE TYRE, SUPPLY REEL TABLE TYRE, PINCH ROLLER, REEL IDLER, T/U CLUTCH, T/U IDLER, TENSION BAND, VIDEO LAMP
Order Code: SK31 £11.00

Economy Kit Contents
BELT SET, T/U REEL IDLER TYRE, SUPPLY REEL TABLE TYRE, PINCH ROLLER, REEL IDLER TYRE, T/U IDLER TYRE, T/U CLUTCH
Order Code: SK32 £5.10

3V44/45/48/53/54/55/57
HRP50/HRD140/150/158/160
HRD250/257/565/566/755
Contents
BELT SET, PINCH ROLLER, CLUTCH MECHANISM, TENSION BAND
Order Code: SK39 £15.00

Economy Kit Contents
BELT SET, PINCH ROLLER
Order Code: SK40 £9.50

FISHER
FVHP905/906/907/908/910/911/916/918
Contents
BELT SET, PINCH ROLLER, IDLER, GEAR, IDLER UNIT, TENSION BAND
Order Code: SK57 £13.00

Economy Kit Contents
BELT SET, PINCH ROLLER, IDLER TYRE
Order Code: SK58 £5.00

FVHP615/618/620/622/70/71/71.1/71.5/71.6/720/721/722/725/
730/830/840
Contents
BELT SET, PINCH ROLLER, IDLER, GEAR, IDLER UNIT, TENSION BAND
Order Code: SK68 £12.50

Economy Kit Contents
BELT SET, PINCH ROLLER, IDLER TYRE
Order Code: SK69 £3.60

HITACHI
VT11/VT33
Contents
BELT SET, PINCH ROLLER, TENSION BAND, IDLER TYRES
Order Code: SK08 £6.00

VT11/VT33
Contents
BELT SET, T/U REEL TABLE TYRE, SUPPLY REEL TABLE TYRE, PINCH ROLLER, FF/REW IDLER, CLUTCH PLATE, TENSION BAND
Order Code: SK45 £14.00

Economy Kit Contents
BELT SET, PINCH ROLLER, FF/REW IDLER TYRE, T/U REEL TABLE TYRE, SUPPLY REEL TABLE TYRE
Order Code: SK46 £4.50

VIDEO SERVICE KITS (Cont.)

HITACHI
VT52/61/62/63/64/65/85/86/840
Contents
BELT SET, PINCH ROLLER, FF/REW ARM, CLUTCH PLATE, TENSION BAND
Order Code: SK49 £14.00

Economy Kit Contents
BELT SET, PINCH ROLLER, FF/REW IDLER
Order Code: SK50 £3.25

VT400/405/410/13/14/15/18/420/25/26/28/430/31/35/48/450/498/
510/520/25/530/35/36/540/545/45/48/570/75/76/580/85/88
Contents
TIMING BELT, PINCH ROLLER, FF/REW ARM, CLUTCH BASE, TENSION BAND
Order Code: SK52 £11.50

VT100/110/111/113/115/118/120/125/128/130/135/138/145/150/
175/220/225/250/255/258/260/VTL30
Contents
BELT SET, PINCH ROLLER, FF/REW ARM, CLUTCH PLATE, TENSION BAND
Order Code: SK51 £14.00

PANASONIC
NV2000/NV2010
Contents
BELT SET, PINCH ROLLER, TENSION BAND, IDLER TYRES
Order Code: SK03 £6.25

NV7000/NV7200/NV7800
Contents
BELT SET, PINCH ROLLER, TENSION BAND, IDLER TYRES
Order Code: SK02 £5.50

NV300/NV330/NV333/NV340/NV366
Contents
BELT SET, PINCH ROLLER, TENSION BAND, IDLER TYRE
Order Code: SK01 £5.50

NV2000/NV2010
Contents
BELT SET, PINCH ROLLER, FF/IDLER, PLAY IDLER, TENSION BAND, VIDEO LAMP
Order Code: SK13 £8.00

Economy Kit Contents
BELT SET, PINCH ROLLER, IDLER TYRE, PULLEY TYRE
Order Code: SK14 £4.50

NV7000/NV7200/NV7800
Contents
BELT SET, PINCH ROLLER, IDLER UNIT, PLAY IDLER, TENSION BAND
Order Code: SK11 £8.50

Economy Kit Contents
BELT SET, PINCH ROLLER, IDLER TYRE, CLUTCH TYRE
Order Code: SK12 £4.20

NV300/NV330/NV333/NV340/NV366
Contents
BELT SET, PINCH ROLLER, IDLER UNIT, PLAY IDLER, TENSION BAND
Order Code: SK15 £7.50

Economy Kit Contents
BELT SET, PINCH ROLLER, IDLER TYRE, PLAY IDLER TYRE
Order Code: SK16 £4.00

NVG7/NVG9/VNG10/NVG11/NVG12/NVG14/NVG15/NVG16/
NVG18/NVG30/NVG120/NV5130/NVG400/NVH65 (PX/AC)/
AG1810 (PK)
Contents
LOADING BELT, CAPSTAN BELT, PINCH ROLLER, IDLER, TENSION BAND
Order Code: SK27 £8.00

Economy Kit Contents
LOADING BELT, CAPSTAN BELT, PINCH ROLLER, IDLER TYRE
Order Code: SK28 £4.00

NV332
Contents
BELT SET, PINCH ROLLER, PLAY IDLER, FF/REW IDLER, TENSION BAND, FF/REW TYRE
Order Code: SK29 £12.00

Economy Kit Contents
BELT SET, PINCH ROLLER, PLAY IDLER TYRE, FF/REW IDLER TYRE
Order Code: SK30 £5.10

NV230/250/260/280/430/450/460/470/650/810/890/
AG1200PK/AG1500PK
Contents
BELT SET, PINCH ROLLER, IDLER, TENSION BAND
Order Code: SK23 £6.00

Economy Kit Contents
BELT SET, PINCH ROLLER, IDLER TYRE
Order Code: SK24 £3.50

NV600/NV688
Contents
BELT SET, PINCH ROLLER, PLAY IDLER, FF/REW IDLER, TENSION BAND
Order Code: SK25 £12.00

Economy Kit Contents
BELT SET, PINCH ROLLER, PLAY IDLER TYRE, FF/REW IDLER TYRE
Order Code: SK26 £6.00

NV730/NV770
Contents
SLOT IN BELT, LOADING BELT, PINCH ROLLER, IDLER UNIT, TENSION BAND
Order Code: SK19 £6.50

Economy Kit Contents
SLOT IN BELT, LOADING BELT, PINCH ROLLER, IDLER TYRE
Order Code: SK20 £4.00

NV370/NV380/480/630/780/830/850/AG2100PK/AG2200PK
Contents
BELT SET, PINCH ROLLER, IDLER, TENSION BAND
Order Code: SK21 £6.00

Economy Kit Contents
BELT SET, PINCH ROLLER, IDLER TYRE
Order Code: SK22 £3.00

NV777/NV788
Contents
BELT SET, PINCH ROLLER, IDLER UNIT, TENSION BAND
Order Code: SK17 £7.00

Economy Kit Contents
BELT SET, PINCH ROLLER, IDLER TYRE
Order Code: SK18 £4.00

VIDEO SERVICE KITS (Cont.)

SHARP
VC381
Contents
BELT SET, PINCH ROLLER, REEL IDLER, TENSION BAND, VIDEO LAMP
Order Code: SK47 £9.80

Economy Kit Contents
BELT SET, PINCH ROLLER, REEL IDLER TYRE
Order Code: SK48 £4.75

VC500/VC571/VC581/VC582/VC583/VC584/VC5F3
Contents
BELT SET, PINCH ROLLER, REEL IDLER, TENSION BAND
Order Code: SK60 £9.50

Economy Kit Contents
BELT SET, PINCH ROLLER, REEL IDLER
Order Code: SK61 £6.50

VC781/VC7810/VC7822/VC785/VC786/VC793/VC800/
VCA100/VCA102/VCA104/VCA202
Contents
BELT SET, PINCH ROLLER, REEL DRIVE UNIT, TENSION BAND
Order Code: SK64 £13.50

Economy Kit Contents
BELT SET, PINCH ROLLER, REEL DRIVE UNIT TYRE
Order Code: SK65 £6.25

VC681/VC682/VC684/VC685/VC693/VC699/VC6F3/VC700
Contents
BELT SET, PINCH ROLLER, REEL DRIVE UNIT, TENSION BAND
Order Code: SK62 £13.50

Economy Kit Contents
BELT SET, PINCH ROLLER, REEL DRIVE UNIT TYRE
Order Code: SK63 £6.00

THIS MONTHS SPECIAL OFFERS

STK461	£5.50	STK7563F	£8.00
STK5332	£1.80	STK73410	£3.50
STK5333	£5.50	TAB205AH	£2.50
STK5422	£3.75	TAB210AH	£3.00
STK5476	£3.50	TAB215H	£3.00
STK7308	£3.50	TAB216H	£3.75
STK7348	£4.00	TIPL791A	£0.80
STK7358	£4.40		

SONY FUNCTION SWITCH (2 LEG) SPECIAL PRICE £0.50

VIDEO REEL MOTOR PU51381V £15.00
3v29, 3v30, 3v31, 3v32, 3v39, 8930, 8931, 8941, 8942, HR7200, HR7300, HR7600, HR7610, HR7650, HR7655

LIMITER POST
Used in HIJARI, MATSUI, ORION, SAISHO
IDL232 £0.70

BUT11AF £0.55
TDA3654 £1.00
TDA4601 £1.20

UNIVERSAL VIDEO LAMP
9v 80mA (±10mm WIRES) £0.25
UNIVERSAL VIDEO LAMP
9v 80mA (±10mm with plug) £0.40
UNIVERSAL VIDEO LAMP
9v 80mA (±10mm with plug) £0.40
HITACHI TRANSFORMER 2434274 £14.00
OUTPUT TV MODULE HM6251 £5.50

I.C. PROTECTOR

ICPF10	ICPF38	ICPN10	ICPN38
ICPF15	ICPF50	ICPN15	ICPN50
ICPF20	ICPF75	ICPN20	ICPN75
ICPF25	ICPN5	ICPN25	

PRICE: ONLY 30p EACH

AUDIO CONTROL HEAD

AMSTRAD ORIGINAL NO: 150751
Used On: Amstrad TVR1, 2, 3, VCR4600, 4600MIL, 4700, Funai VZ, VCR4600, 4800, 5200, 5600, 8600, VIP3000, 5000
Also Fits: Fidelity, Funai, Hinari, Prcine, Schneider, Towada, Univerum.
Order Code AH01 Price: £13.50

AMSTRAD ORIGINAL NO: 153134
Used On: Amstrad DD8900, 8904, VCR2000, 6000, 6100, 8600, 8602, 8603, VCR8604, 8700, 8704, 8714, 8800, 9005, 9244
Also fits: Anitech, Bondstec, Casio, Crown, Fidelity, Goldhand, Granada, Hinari, Marquant, Omega, Profex, Schneider, SEG, Sentra, Shintom, Tashiko, Tatung, Towada, Univerum
Order Code AH02 Price £14.50

GRANDATA LTD

K.P. HOUSE, UNIT 15
POP IN COMMERCIAL CENTRE, SOUTHWAY
WEMBLEY, MIDDLESEX, ENGLAND HA9 0HB
Telephone: 081-900 2329 Fax: 081-903 6126

Access & Visa Card accepted.

Open Monday to Saturday.

ELC EAST LONDON COMPONENTS
AUDIO TELEVISION VIDEO
COMPONENTS AT VERY KEEN PRICES
TEL: 081-472 4871 FAX: 081-503 5926

REMODEL TYRES 50p 1+, 25p 10+

VIDEO BELT KITS

VIDEO HEADS FROM £6.99

Over 200 models at very attractive prices.
AKAI, AMSTRAD, FERGUSON, FISHER,
GOLDSTAR, HINARI, HITACHI, LOGI,
MATSUI, ORION, PANASONIC, SAISHO,
SHARP AND MANY MORE

VIDEO SPARES

3V29 TAKE UP IDLER	£1.30
3V28 F/F REW IDLER	£2.60
3V5965 FV1014 IDLER	£1.50
3V23 LOADING ROLLER BAR	£1.95
SHARP 005 & 006	£6.99
SHARP VC651 ASSEMBLY	£6.99
VT11/14 IDLER	£1.95
VT11 CLUTCH ASSEMBLY	£6.99
VT100225/260 IDLER	£2.75
NEC 9013 IDLER	£4.99
SANYO VHR3300 IDLER	£3.99
AKAI VS105250 CLUTCH ASSEMBLY	£11.99
SAISHO VR980 CLUTCH	£4.99
MITSUBISHI H5337 F/F IDLER	£2.70
ALBA SENTRA PULLY	£1.50
MATSUI LUMITER POST	£1.25
PANASONIC NV370 IDLER	£1.25
FISHER 615 IDLER	£3.50
FISHER GEAR ASSEMBLY	£4.50
AMSTRAD PINCH WHEEL MOD KIT	£3.99
UNIVERSAL TRIPLER	£4.99
UNIVERSAL TRIPLER WITH FOCUS	£7.99
HITACHI MODULE HM6251	£6.99
CUC2410 TRIPLER	£16.99
TENSION BAND FOR MOST MOD. FROM	£1.99
CIRCUIT PROTECTOR ICP	50p
TX10 FOCUS UNIT	£7.99
PHILIPS BACK UP BATTERY	£1.30
ALBA BATTERY, 1F5.5V	£2.50
TV SWITCHES FOR MOST MOD FROM	0.85p
SONY FUNCTION SWITCH	0.85p

WINE OUTPUT TRANSFORMERS
OVER 100 MODELS AT LOW PRICES

AKAI CT2570E	19.99	MATSUI 16.99	
CT2870	19.99	14400	16.99
ALBA CT17ARS	19.99	1450	16.99
AMSTRAD CTV2200	14.99	1480	16.99
CTV2210	14.99	1480	16.99
TVR12/24	16.99	1480	16.99
BUSH CT2582ETX	16.99	1480	16.99
2020T	16.99	1480	16.99
VS105/250	1.50	1480	16.99
FIDELITY CTX2000	14.50	1480	16.99
ZX3000	12.99	1480	16.99
AMSTRAD FERGUSON	1.80	1480	16.99
VCRA600	1.80	1480	16.99
VCR6000	1.30	1480	16.99
VCR7000	1.30	1480	16.99
FERGUSON WHITE	14.99	1480	16.99
3V22	1.80	1480	16.99
3V29/30/33	£2.60	1480	16.99
3V4285	0.85	1480	16.99
HRD520/830	1.20	1480	16.99
FST	16.99	1480	16.99
YELLOWSPOT	16.99	1480	16.99
3V14	1.99	1480	16.99
BLUE	16.99	1480	16.99
YHYP615/725	1.10	1480	16.99
GYHP905/910	1.10	1480	16.99
GOLDSTAR	16.99	1480	16.99
GRUNDIG	16.99	1480	16.99
VS180	1.45	1480	16.99
VS300	1.90	1480	16.99
VS900	1.75	1480	16.99
HINARI	1.25	1480	16.99
VXL3-20	1.25	1480	16.99
VXL4-35	1.50	1480	16.99
CPT11493	16.99	1480	16.99
CPT1646	16.99	1480	16.99
VT11/33	1.30	1480	16.99
VT12/65	1.75	1480	16.99
VT110/220	1.80	1480	16.99
MITSUBISHI	16.99	1480	16.99
YR546	2.40	1480	16.99
YR567	1.50	1480	16.99
SAMSUNG	16.99	1480	16.99
VX510/520	1.50	1480	16.99
SANYO	2.05	1480	16.99
VHR1300	2.15	1480	16.99
VHR3300	2.05	1480	16.99
SHARP	1.30	1480	16.99
VC381	1.30	1480	16.99
VC651/681	1.25	1480	16.99
VC9300	1.25	1480	16.99

AN3822K	7.99	LA7835	1.99	STK5720	6.00	TDA1518	4.00	UPC1378	2.20	25B705	2.00
AN5435	2.50	M6A2901	2.60	STK5730	6.00	TDA1518	4.00	UPC1394	1.20	25B755	2.50
AN5515	2.99	M8918B1	6.50	STK7216	7.00	TDA1520	4.00	UPC1420	5.25	25B817	2.00
AN5521	2.99	M49481	6.50	STK7226	8.50	TDA1520	4.00	UPC1470	3.00	25B861	0.50
AN5930	2.50	M540A-84	9.99	STK7308	4.25	TDA1670	3.00	UPC1498	3.50	25B882	0.80
AN7171	4.25	M5444A	2.99	STK7356	9.00	TDA1770	4.25	UPC1498	4.25	25B889	1.40
AN7178	2.80	M5444B	2.99	STK8250	6.99	TDA1908	1.00	UPC1498	4.25	25B892	0.90
BA3402	3.99	M5445L	4.25	STK73410	6.99	TDA2003	1.00	UPC1498	4.25	25B892	0.90
BA5402	2.50	M5444A	3.99	STR3125	5.99	TDA2031	1.30	UPC1498	4.25	25B892	0.90
BA8109	1.80	M54647L	3.99	STR4211	5.99	TDA2170	3.00	UPC1498	4.25	25B892	0.90
BA8111	1.99	M54648L	3.99	STR5412	4.50	TDA2270	3.25	UPC1498	4.25	25B892	0.90
BA6129	1.99	M54649L	3.99	STR6020	4.50	TDA2577	2.00	UPC1498	4.25	25B892	0.90
BA6209	2.50	M83730	2.99	STR9012	6.00	TDA2578	3.00	UPC1498	4.25	25B892	0.90
BA6219	2.99	M83731	2.99	STR41090	6.00	TDA2578	3.00	UPC1498	4.25	25B892	0.90
BA6229	2.99	M83732	2.99	STR44115	7.75	TDA2582	3.00	UPC1498	4.25	25B892	0.90
BA6238	1.99	M83733	2.99	STR44115	7.75	TDA2582	3.00	UPC1498	4.25	25B892	0.90
BA6239	2.50	M83734	2.99	STR50020	6.99	TDA2600	5.75	UPC1498	4.25	25B892	0.90
BA6304	1.99	M83735	2.99	STR50103	4.50	TDA2630	3.50	UPC1498	4.25	25B892	0.90
BA6259	2.99	STK457	6.50	STR50115	6.50	TDA2630	3.50	UPC1498	4.25	25B892	0.90
BA10324	1.99	STK461	5.99	STR50511	6.50	TDA2630	3.50	UPC1498	4.25	25B892	0.90
BA10358	1.80	STK465	7.50	STR58041	5.50	TDA2630	3.50	UPC1498	4.25	25B892	0.90
CN10329	4.99	STK465	7.50	STR59041	6.50	TDA2630	3.50	UPC1498	4.25	25B892	0.90
CN795	2.99	STK0029	5.99	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
CN828A	2.99	STK0029	5.99	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
CN983	2.99	STK0209	5.99	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
HA1377	1.99	STK2048	11.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
HA1397	2.80	STK2129	7.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
HA11225	2.80	STK41225	7.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
HA11227	2.20	STK3041	6.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
HA11235	1.99	STK3042II	6.50	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
HA11423	2.20	STK3062II	7.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
HA11718	2.99	STK3062II	7.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
HA11719	4.75	STK41211I	9.99	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
HA11753	5.99	STK4122	6.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
HA11758	5.00	STK41311I	6.50	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
HA12001	1.95	STK4132II	7.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
HA13008	9.99	STK41411I	8.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
HA13108	3.50	STK41412I	7.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
HA13117	2.99	STK41412I	7.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
HA13119	2.99	STK41412I	7.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
HA13402	3.25	STK41611I	9.99	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
HA13403	5.50	STK41612I	9.99	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
LA4445	1.99	STK41711I	9.99	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
LA4446	2.80	STK41811I	9.99	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
LA4447	2.20	STK41811I	9.99	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
LA4448	2.80	STK41811I	9.99	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
LA4449	2.20	STK41811I	9.99	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
LA4450	2.80	STK41811I	9.99	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
LA4451	1.99	STK4372	6.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
LA4452	1.99	STK4392	7.50	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
LA4453	2.99	STK4953	9.99	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
LA4454	2.99	STK5211	9.99	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
LA4455	3.99	STK5325	7.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
LA4456	3.99	STK5325	7.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
LA4457	3.99	STK5325	7.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
LA4458	3.99	STK5325	7.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
LA4459	3.99	STK5325	7.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
LA4460	3.99	STK5325	7.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
LA4461	3.99	STK5325	7.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
LA4462	3.99	STK5325	7.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
LA4463	3.99	STK5325	7.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
LA4464	3.99	STK5325	7.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
LA4465	3.99	STK5325	7.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
LA4466	3.99	STK5325	7.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
LA4467	3.99	STK5325	7.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
LA4468	3.99	STK5325	7.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
LA4469	3.99	STK5325	7.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
LA4470	3.99	STK5325	7.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
LA4471	3.99	STK5325	7.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
LA4472	3.99	STK5325	7.00	STR10006	6.00	TDA2630	3.50	UPC1498	4.25	25B892	0.90
LA4473	3.99	STK5325									

**WE WILL ONLY SUPPLY TOP QUALITY,
BRANDED COMPONENTS.
REPUTATION COUNTS WITH US**

G.G.L. COMPONENTS

PO BOX 72, UNIT 7, SOUTH JOHN STREET, CARLISLE, CUMBRIA CA2 5AL.
TEL: (0228) 39693/20358 Fax: (0228) 515127.

BUY WITH



AERIAL ACCESSORIES

COAX PLUG.....	18
F CONNECTOR.....	20
FLY LEAD 2M.....	75
VIDEO LEAD 2M.....	75
4 WAY DISTRIBUTION.....	18.50
AMPLIFIER MAINS.....	20.25
8 WAY DISTRIBUTION.....	
AMPLIFIER MAINS.....	20.25

FUSES

20mm A S (PKTS OF 10).....	1.20
250MA, 315MA, 500MA, 630MA.....	1.20
800MA, 1A, 1.6A, 2A, 2.5A, 3.15A.....	
20mm Q/B (PKTS OF 10).....	
500MA, 630MA, 800MA, 1A.....	
1.6A, 2A, 2.5A, 3.15A.....	.80

I.C.'s

CNX62A.....	4.75
SA1293.02.....	5.95
SA1293.03.....	7.25
SA1293A.03.....	8.35
SL1432.....	1.95
SK5331.....	4.95
SK5332.....	4.95
SK5333.....	11.25
SK5421.....	3.50
SK5422.....	5.50
SK5481.....	6.95
SK5482.....	4.95
SK5490.....	7.95
STK7308.....	5.50
STK7348.....	5.50
STR421.....	4.50
STR5412.....	4.50
STR50020.....	7.35
STR50103A.....	5.95
STR54041.....	6.95
STR58041.....	5.95
STRD1816.....	5.70
TD11170S.....	1.95
TD12030.....	1.95
TD12170.....	2.95
TD12270.....	2.75
TD12576A.....	5.95
TD12577A.....	3.50
TD12578A.....	2.95
TD12579.....	3.95
TD12581.....	4.50
TD12582.....	2.50
TD12653AQ.....	2.95
TD13330.....	8.50
TD13560.....	4.95
TD13561A.....	4.95
TD13562A (TFK).....	4.65
TD13565.....	3.95
TD13571BO.....	8.95
TD13576B.....	10.25
TD13650.....	8.95
TD136513.....	2.95
TD13651AQ.....	4.75
TD13653A.....	3.50
TD13654A.....	2.95
TD14500.....	4.50
TD14501.....	5.25

BATTERIES

AA (pkt of 4).....	1.20
AAA (pkt of 4).....	1.20
FERGUSON 3V55.....	4.95
PHILIPS MEMORY 1V2.....	1.70
PHILIPS MEMORY 2V4.....	2.50

CAPACITORS

0 115 5v (back-up).....	2.50
63v.....	
47uf at 63v.....	18
100uf at 63v.....	22
220uf at 63v.....	35
250v.....	
1uf at 250v.....	20
4.7uf at 250v.....	25
10uf at 250v.....	35
22uf at 250v.....	40
47uf at 250v.....	65
100uf at 250v.....	1.25
400v.....	
1uf at 400v.....	23
4.7uf at 400v.....	35
10uf at 400v.....	70
22uf at 400v.....	
(ALL PCB MOUNTING).....	.85

DIODES

R2M.....	.95
BY133.....	.95
BY227.....	.95
BY299/800.....	.35
IN4007.....	.10
IN5408.....	.20
BZX61C (pkt of 5) 6v8 7v5 12v.....	
15v 24v 33v 68v 120v 130v.....	1.00

EHT TRAYS

CONTINENTAL 30AX FOCUS.....	8.95
DECCA 120/130.....	7.95
GRUNDIG CUC2410 14.....	13.70
GRUNDIG CUC2410 22.....	13.70
PHILIPS KT3.....	7.95
UNIVERSAL.....	5.95

TRANSISTORS

BC639.....	20
BC640.....	20
BF460.....	95
BU208D.....	1.95
BU426A.....	1.45
BU500.....	2.00
BU508A.....	1.50
BU508AF.....	1.60
BU508B.....	1.60
BU508DF.....	1.95
BU508V.....	1.90
BU807.....	1.75
BUT11AF.....	1.90
BUT56A.....	2.25
BUX84.....	.80
RA050.....	2.95
T9053V/T9054V.....	3.50
T9084V.....	1.95
TIP29C (TO18BV).....	1.95
TIP41C.....	50
TIP42C.....	50
TIP12H (TO187V).....	75
TIP1791A.....	1.95
2SD1497.....	3.95
2SD1497/02.....	4.25
TRANSISTOR EQUIVALENT BOOKS.....	
TVT A-Z & 2N-2SD.....	28.45

PANASONIC OPTS

PANASONIC TLF 14567F.....	19.50
PANASONIC TLF 14586F.....	19.50

REMOTE CONTROLS

FERGUSON T725.....	9.75
FERGUSON T734.....	9.75
FERGUSON T742.....	9.75
FERGUSON T785 FAST TEXT.....	11.95
FERGUSON T789 FAST TEXT.....	11.95
FERGUSON TX100 NON TEXT.....	11.50
FERGUSON TX10 TEXT.....	9.75
FERGUSON TX100 STEREO.....	11.95
FERGUSON TX100 TEXT.....	10.95
FERGUSON ICC5.....	17.95
FERGUSON SFA1.....	13.50
FIDELITY CTV142.....	12.95
FIDELITY CTV22T.....	12.75
FINLUX 1101 TO 2386.....	11.50
GOODMANS TX1100/1200.....	18.95
GRANADA UNIVERSAL.....	12.95
GRUNDIG TP400 TEXT.....	12.90
GRUNDIG TP650 TEXT.....	11.45
GRUNDIG TP660.....	11.45
HITACHI CPT1446.....	11.45
HITACHI CPT12174.....	17.95
HITACHI CPT2188.....	9.75

LINE O/P TRANSFORMERS

FERGUSON TX90 20.....	14.85
FERGUSON TX100 90D.....	16.95
FERGUSON TX100 110D.....	13.80
FERGUSON TX100 FST.....	17.25
FIDELITY ZX2000 + MOD.....	13.95
FIDELITY ZX3000.....	12.95
HINARI CT45.....	15.95
HITACHI CPT1474/1476.....	17.75
HITACHI CPT2174/76/78.....	15.58
HITACHI CPT2276/2278.....	16.45
HITACHI CPT2476 2478.....	17.95
ITT COMPACT 80R/110.....	14.95
ITT CVC1200/1.....	19.95
ITT PICO 1/1A s.....	17.75
MATSUI 1410/20/40.....	18.95
PHILIPS CP90.....	17.95
PHILIPS CTX14720.....	20.35
PHILIPS 2A.....	18.50

SERVICE MANUALS

AMSTRAD 4600.....	9.95
AMSTRAD 6000.....	9.95
FERGUSON TX85.....	9.95
FERGUSON TX59.....	13.95
FERGUSON 3V65.....	13.95
FERGUSON FV11.....	13.95

SWITCHES

FIDELITY CTV140.....	1.50
GRUNDIG CUC731.....	3.50
ITT TX SERIES.....	4.95
KT4/CTX REMOTE.....	1.75
TX9/10 STANDARD.....	1.00
TX9/10 REMOTE.....	1.75
TX90/100 STANDARD.....	1.50
TX90/100 REMOTE.....	1.75

**NEW LISTS NOW
AVAILABLE.
PLEASE REQUEST**

ALBA VIDEO SPARES

VCR4000.....	
BELT KIT.....	1.95
CAPACITOR BACK-UP.....	1.85
PINCH ROLLER.....	3.95
REEL IDLER.....	3.95
REEL PULLEY.....	1.95

AMSTRAD VIDEO SPARES

VCR4500.....	
BELT KIT.....	1.95
GEAR ASSEMBLY.....	9.95
MODIFICATION KIT.....	5.50
PINCH ROLLER.....	3.50
VCR4600.....	
BELT KIT.....	1.95
GEAR ASSEMBLY.....	9.95
MODIFICATION KIT.....	5.50
PINCH ROLLER.....	3.50
VCR6000.....	
BELT KIT.....	1.95
PINCH ROLLER.....	3.95
CLUTCH.....	3.95

FERGUSON VIDEO SPARES

3V29/30.....	
BELT KIT.....	1.95
CAPSTAN MOTOR.....	29.50
CASSETTE LAMP.....	7.95
LOADING BELTS (5).....	1.00
PINCH ROLLER.....	3.95
REEL IDLER.....	2.95
TAKE UP CLUTCH.....	2.95
TAKE UP IDLER.....	1.95
3V35/39.....	
BELT KIT.....	1.95
CAPSTAN MOTOR.....	21.50
CASSETTE HOUSING.....	28.95
LOADING BELTS (5).....	1.95
MAINS TRANSFORMER.....	23.95
PINCH ROLLER.....	3.95
REEL IDLER.....	2.95
TAKE UP IDLER.....	1.95
TAKE UP CLUTCH.....	2.95
3V44/45.....	
BELT KIT.....	1.50
CASSETTE HOUSING.....	28.95
PINCH ROLLER.....	3.95
3V65/FV11.....	
BELT KIT.....	1.75
CAPSTAN MOTOR.....	27.50
CASSETTE HOUSING.....	27.50
PINCH ROLLER.....	3.95
REEL IDLER.....	2.75

FISHER VIDEO SPARES

FVH5000.....	
BELT KIT.....	2.20
REEL IDLER.....	5.50
PINCH ROLLER.....	3.50
TENSION BAND.....	2.60
FVH615/720.....	
BELT KIT.....	1.95
CLUTCH ASSEMBLY.....	5.95
PINCH ROLLER.....	4.50
REEL IDLER.....	5.95
FVH905/910.....	
BELT KIT.....	1.95
CLUTCH ASSEMBLY.....	5.95
REEL IDLER.....	5.95

HITACHI VIDEO SPARES

VT8000/8700E.....	
BELT KIT.....	1.95
FF/REW IDLER.....	2.95
FF/REW PULLEY.....	95
PINCH ROLLER.....	3.95
PLAY IDLER.....	3.95
REEL TABLE.....	3.95
TENSION BAND.....	2.95
VT9300/9700E.....	
BELT KIT.....	1.95
FF/REW IDLER.....	2.75
FF/REW PULLEY.....	95
PINCH ROLLER.....	3.95
PLAY IDLER.....	3.95
VT111/33E.....	
BELT KIT.....	1.95
CAPSTAN MOTOR VT11E.....	27.50
CAPSTAN MOTOR VT33E.....	23.95
CLUTCH ASSEMBLY.....	7.95
FF/REW IDLER GENUINE.....	2.50
PINCH ROLLER.....	3.95
VT63/64E.....	
BELT KIT.....	1.95
CAPSTAN MOTOR.....	27.50
CLUTCH ASSEMBLY.....	7.95
FF/REW IDLER.....	2.50
PINCH ROLLER.....	3.95
VT120/130E.....	
BELT KIT.....	1.95
CAPSTAN MOTOR.....	24.95
CLUTCH ASSEMBLY.....	7.95
FF/REW IDLER.....	3.75
PINCH ROLLER.....	3.95

PANASONIC VIDEO SPARES

NV230/430.....	
BELT KIT.....	1.95
PINCH ROLLER.....	3.95
REEL IDLER GENUINE.....	3.30
NV333/366.....	
BELT KIT.....	1.95
PINCH ROLLER.....	3.95
PLAY IDLER GENUINE.....	5.50
REEL IDLER GENUINE.....	1.35

NV370

BELT KIT.....	1.95
MODE SWITCH.....	3.95
PINCH ROLLER.....	3.95
REEL IDLER GENUINE.....	3.30
NV730.....	
BELT KIT.....	1.95
PINCH ROLLER.....	3.95
REEL IDLER GENUINE.....	4.30
NV777.....	
BELT KIT.....	1.95
PINCH ROLLER.....	3.95
REEL IDLER GENUINE.....	4.30
NV2000/2010.....	
BELT KIT.....	1.95
PINCH ROLLER.....	3.95
PLAY IDLER GENUINE.....	1.35
REEL IDLER GENUINE.....	1.35
NV7000/7200.....	
BELT KIT.....	1.95
PINCH ROLLER.....	3.95
PLAY CLUTCH GENUINE.....	6.15
REEL IDLER GENUINE.....	1.35
NV7/10/12.....	
BELT KIT.....	1.95
MODE SWITCH.....	3.95
PINCH ROLLER.....	3.95
REEL IDLER GENUINE.....	3.30
NV919/NVJ35/NVL28.....	
PINCH ROLLER.....	5.25

PHILIPS VIDEO SPARES

VR6480/6520.....	
BELT KIT.....	1.95
PINCH ROLLER.....	3.95
REEL IDLER.....	3.30
REPAIR KIT.....	14.50
VR6462/6560.....	
CASSETTE HOUSING.....	12.95
PINCH ROLLER.....	14.75
REEL IDLER GENUINE.....	4.95
REPAIR KIT GENUINE.....	21.50
BELT KIT.....	2.95
CASSETTE HOUSING.....	10.98
PINCH ROLLER ARM ASSY.....	7.50

SANYO VIDEO SPARES

VTC5000.....	
BELT KIT.....	1.00
REEL MOTOR GENUINE.....	7.95
REEL PULLEY GENUINE.....	5.95
VHR1100/1300.....	
BELT KIT.....	2.25
PINCH ROLLER.....	3.95
REEL DRIVE ROLLER.....	5.90
VHR3100/3700.....	
BELT KIT.....	1.95
PINCH ROLLER.....	3.50
REEL DRIVE ROLLER.....	5.95

SHARP VIDEO SPARES

VC9300/381.....	
BELT KIT.....	2.50
PINCH ROLLER.....	3.95
REEL IDLER GENUINE.....	3.95
REEL MOTOR GENUINE.....	16.95
TENSION BAND.....	2.95
VC481/482.....	
BELT KIT.....	2.50
PINCH ROLLER.....	3.95
REEL IDLER GENUINE.....	3.95
REEL MOTOR GENUINE.....	17.95
VC581/582.....	
BELT KIT.....	2.50
REEL IDLER GENUINE.....	3.95
PINCH ROLLER.....	3.95
VC681.....	
BELT KIT.....	2.50
PINCH ROLLER.....	3.95
REEL PULLEY GENUINE.....	7.95
VC140/VCT72.....	
BELT KIT.....	2.95
PINCH ROLLER.....	3.95
REEL PULLEY GENUINE.....	7.95

SONY VIDEO SPARES

C5/6/7.....	
BELT KIT C5/7.....	2.50
BELT KIT C6.....	1.95
PINCH ROLLER.....	4.50
REWIND KIT C5/7.....	4.95
REWIND KIT C6.....	3.95
VIDEO TAPES.....	
FERGUSON 3V00/22.....	50
FERGUSON 3V29.....	80
PANASONIC NV2000.....	95
SHARP 930C.....	1.50
UNIVERSAL.....	50

VIDEO LEADS

SCART LEAD FULLY WIRED.....	4.95
SCART LEAD TO 6 PINS.....	4.95
SCART COPYING KIT.....	5.95
SCART TO S SCART SKT.....	5.95
SCART TO 5 SCART SKT.....	6.95
VIDEO COPYING KIT.....</	

TECHNICAL BOOKS

A selection from our range of books for the repair trade

TELEVISION CHASSIS GUIDE

Full cross reference for all models.
Order MP-18. £6.00

TELEVISION EQUIVALENTS

Lists models which are the same.
Order MP-150. £6.00

FAULT LISTS FOR TELEVISIONS

Hundreds of specific faults for dozens of different makes and models.
Order MP-205. £7.00

TELETEXT REPAIR MANUAL

Covers SAA range of boards.
Order MP-38. £7.00

TELEVISION REMOTE CONTROL CIRCUITS

Dozens of Diagrams on many remotes.
Order MP-167. £10.00

TV POWER SUPPLY CIRCUITS

Dozens of P.S. circuit stages.
Order MP-219. £10.00

SCART EUROCONNECTOR SYSTEM

Comprehensive details of the system.
Order MP-21. £3.00

P.C. HARD DISC DRIVE REFERENCE MANUAL

Comprehensive Drive Details.
Order MP-84. £5.00

P.C. DIAGNOSTICS SOFTWARE

Dozens of programs to aid you in diagnostics of PC's and Drives etc.
2 sets of 7 x 3.5" Discs per set.
Set 1. Order MP-250. £12.50
Set 2. Order MP-251. £12.50

VIDEO RECORDER AND CAMCORDER EQUIVALENTS

Full Cross-reference guides.
Makes A-J. Order MP-218. £6.00
Makes K-Z. Order MP-219. £6.00

FAULT LISTINGS FOR VIDEO

Lists Hundreds of Faults for dozens of makes and models.

Volume 1. MP-206. £7.00
Volume 2. MP-228. £7.00

VHS VIDEO RECORDER PRINCIPLES

Detailed guide on how it works.
Order MP-58. £4.00

VIDEO TEST JIG

Special cassette lets you operate the machine in test mode.
Order VTJ. £15.00

VIDEO HEAD CLEANING KIT

Special kit with comprehensive instructions on how to service heads.
Order VHCK. £5.00

VIDEO RECORDER FAULTS

Unique repair guide for beginners
Order MP-5. £3.00

WIRE ANTENNAS FOR H.F. OPERATORS

THE Aerial book for Amateurs.
Order MP-243. £5.95

REEL TO REEL TAPE RECORDER SERVICING

Theory and circuits for repairs.
Order MP-201. £4.95

TRANSISTOR RADIO REPAIR GUIDE

Comprehensive servicing charts.
Order MP-7. £1.95

RECORDER PLAYER SPEED DISC

Get your phonograph up to speed.
Order MP-8. £0.95

SWITCH MODE POWER SUPPLY I.C. TYPE TDA-4600

Circuitry and operation explained.
Order MP-37. £6.00

VOLTAGE REGULATORS, STABILISERS & POWER SUPPLIES

Identification and specifications.
Order MP-9. £3.00

CMOS DATABOOK

Pinouts and circuits for 4000 series.
Order MP-10. £5.00

TTL DATABOOK

Pinouts and circuits for 7400 series.
Order MP-34. £5.00

TRANSISTOR EQUIVALENTS

Includes details on testing them.
Order MP-24. £3.00

OFFICE EQUIPMENT EQUIVALENTS

Photocopiers & Fax machines covered.
Order MP-200. £6.00

TELEPHONE CODE LOCATION GUIDE

Find the Town from the Phone Code.
Order MP-19. £4.00

MANUFACTURERS EQUIVALENTS

What makes are the same.
Order MP-220. £3.00

The above selection are just a few of the Hundreds of Unique Repair and Data Guides shown in our FREE catalogue - Yours for the asking. Sent FREE with all orders or send 2 x 1st class stamps for your copy TODAY!

P.V. TUBES
104 ABBEY STREET, ACCRINGTON
LANCS BB5 1EE
☎ 0254 236521/232611
FAX 0254 395361
24 Hr Answering Service

SEND LARGE S.A.E. FOR TRADE CATALOGUE

WE ARE CLOSED ALL DAY WEDNESDAY

CALLERS WELCOME AT TRADE COUNTER MON-FRI 9-5pm SAT 9-1pm

BRAND NEW TV's and VIDEOS
We have a full range of TV's and Videos - Multisystems and PAL sets available in stock now. 25" and 29" Stereo Nicam sets including stand plus full warranty

BEAT THE BURGLARS
NOW A REMOTE CONTROL HOME SECURITY SYSTEM WITH CORDLESS DETECTORS
COMPLETE STARTER KIT £183.00 + VAT
• Easy to install
• Advanced Radio & Microchip Technology
• Transmitting on FM wavelength
• Fully protected against radio signal jamming
• Expandable to most requirements including smoke detectors
• Intelligent keypad control panel
• Full step by step instructions
• Installation Helpline
• Conforms to DIY Intruder Alarm Standards BS6707 and Wireless Standard BS6799 (Class IV/Part A)

NEW COMPLETE D.I.Y. BURGLAR ALARM SYSTEM - ALL YOU NEED, INCLUDES DIGITAL 4 ZONE PANEL (2 DETECTORS AND THE REST!) ONLY £99 + VAT

WE CAN'T LIST EVERYTHING THAT WE STOCK, OUR RANGE IS EXTENSIVE. WE HAVE A TRADE CATALOGUE ON REQUEST WE ARE ALSO ON LINE WITH "MOVIES" TO ORDER ANY PHILIPS PART QUICKLY JUST SOME OF THE THINGS WE SELL - AERIALS, BRACKETS, BATTERIES, CABLE CONNECTORS, CMOS CAPACITORS, COMPUTER ACCESSORIES, DISCS, DIODES, ELECTRICAL ACCESS, FUSES, ICs, LOOPT, LEADS, MANUALS, PUSH BUTTON LIGHTS, PHONES, PHONE ACCESS, POTENTIOMETERS, RELAYS, SEMICONDUCTORS, STRIPBOARD, STRIP, SMOKE DETECTORS, SWITCHES, TUNERS, TV BATTERY LEADS, TV WALL BRACKETS, TOOLS, TEST EQUIPMENT, VALVES AND EVERYTHING YOU NEED FOR VIDEO REPAIRS - HEADS, IDLERS, TYRES, PINCH ROLLERS, CLEANERS, TEST CASSETTES, VIDEO TAPE (Inc BETA and V2000) etc.

THE COMPANY WHERE NO QUERY IS TOO SMALL
EX-RENTAL TV's/VIDEOS ALWAYS AVAILABLE FROM TRADE COUNTER
OFFER
SURFACE SINGLE COAX OUTLET 10 for **£4.00**

HOW TO ORDER: Up to 1K ADD £2.00 per order P+P (U.K.). Heavier parcels, e.g. cables, service aids, degassing coils please allow £4.00 P+P (U.K.). Export orders charged at cost. First Class Mail is used whenever possible. Add 17.5% VAT to total except where it states zero rate. Over 3K will be sent by carrier £12.00 + VAT (up to 15K (except tubes)). We do not despatch on Saturdays.

Goods are despatched on the day we receive your order. If for any reason we are out of stock we will try to inform you as quickly as possible. We try our best to give a speedy, fair and efficient service. VAT invoice on request. Give us a ring - we'll give you service. Please ask if what you need is not listed - we will try to help. Prices are subject to change without notice in some cases we may have to supply an equivalent. We need expiry dates for credit card orders. MIN. ORDER £5

VALVES
NEW - Branded Boxes - full range - (matched pairs available)

ECC81	£2.90	ECC82	£2.90
ECC83	£4.90	ECC85	£3.00
ECC88	£3.24	ECL82	£3.37
ECL86	£3.50	EL34	£7.00
EL84	£3.00	EL519	£6.50
GZ34	£5.00	KT66	£9.75
KT88	£18.00	PCL805	£2.70
PCL86	£3.00	PC504	£3.00
PLS19	£5.90	PY500A	£2.95
128Y7A	£5.50	6L6GC	£5.31
6L6GT	£5.31	6K D6	£12.95

SATELLITE EQUIPMENT

Powermid remote extender	£51.00
Pace 900 receiver only	£158.00
Pace 900 & 60cm dish/LNB	£220.00

Full range of cable, connectors etc.
Akai Sat System with 60cm Dish/LWB **£170.00**

REMOTE CONTROLS for SATELLITE REC's

PACE 800/900	£12.95
AMSTRAD SRX 200/SRD400	£12.95
MASPRO 250/350	£12.95
FERGUSON SRA1	£12.95
AMSTRAD SRD 510/520	£12.95

PLEASE ASK FOR OTHERS

One for all 4 remote control	£19.95
Degaussing Coil	£27.50

Custom made leads - we can make up leads to your own requirements - just ask

WANTED INSTALLERS FOR WIRELESS SECURITY SYSTEM RING SUE OR CHRIS

SONY TUBES RE PROCESSED WITH ORIGINAL SONY GUNS

HIGH TEMPERATURE RE-PROCESSING of Sony, Mullard 45AX, 30AX, In-line, PiL, Mini (22.5) Neck and FST Tubes.

SPECIAL OFFER - Clearance while stocks last

3701B22	£20.00	5600YB22	£38.00
3702B22	£38.00	A34EAC00X	£38.00
370KR22	£38.00	A51 EBD 10X	£52.00
370LH22	£38.00	A51 JCC 30X	£52.00
5106B22	£38.00	A51 JFC 61X	£52.00
5109B22	£38.00	A51 JXS 95X	£52.00
510YB22	£38.00	AXM37-001	£38.00

400EFB22 Sony	£54.00	A56-701X ITT	£48.00	A51JAR00X	£58.00
520SB22 Sony	£54.00	A66-540X Mullard	£56.00	A51JK000X Sony	£74.00
570HB22 Sony	£54.00	A67-701X ITT	£56.00	A51JUH10X Sony	£74.00
680DB22 Sony	£85.00	A34JBU10X Sony	£64.00	A53JBW00X Sony	£64.00
680EB22 Sony	£85.00	A44JFZ10X Sony	£78.00	A59EAF00X	£64.00
A36JAR00X01	£48.00	A49JHT00X Sony	£64.00	A59EAK00X Philips	£64.00
A38EAP00X01	£48.00	A49JLV10X Sony	£74.00	A59JWC00X Sony	£95.00
A51-231X ITT	£46.00	A51EAF00X	£58.00	A64JKJ10X Sony	£95.00
A51-570X Mullard	£46.00	A51EAK00X	£58.00	A66EAF00X	£74.00
A51-580X Mullard	£46.00	A51EAL00X	£58.00	A66EAK00X Philips	£74.00
A51-590X Mullard	£46.00	A51EBD00X	£58.00	AXT51-001	£46.00
A56-540X Mullard	£52.00	A51EBV10X01	£58.00		

All Tubes Guaranteed 12 Months	Please add 17½% VAT	Callers welcome. Please phone first.
--------------------------------	---------------------	--------------------------------------

D.I.Y. Television Tube Polishing Kit
Contains everything you need to Polish scratches and small chips on your CRT screens. All you require is an electric drill. Written instructions are provided. Guaranteed to work. Worldwide Delivery **Total Price £63.00 includes P&P and VAT**

WELL VIEW
114-134 Midland Road,
Luton, Beds. U.K. LU2 0BL.
Tel/Fax: 0582 402499 (Est. 1978)

Order TODAY using Access/Visa for immediate despatch. All order plus £2.35 Post and Packing. (Overseas £5.00)

MAURITRON TECHNICAL SERVICES (6TV1)

47A High Street, Chinnor, Oxfordshire OX9 4DJ.

Tel: 0844-351694. Fax: 0844-352554.

TELEVISION



REED
BUSINESS
PUBLISHING

NVQs

For as long as one can remember the City and Guilds of London Institute has set the pattern for technical training in our industry. Its approach has served us well and has proved to be adaptable as the technology has evolved. The City and Guilds qualifications are respected, and those who hold them consider the effort to have been worthwhile. Now, as an article by Joe Cieszynski on a later page relates, all this is to change. We are to move to a system called National Vocational Qualifications, which will be based on an assessment of candidates' competence in carrying out set tasks. Assessment will be a problem in itself, apart from educational considerations. How will it be practical, at a reasonable cost, to carry out workplace assessments as envisaged? The logistic problems will be formidable to say the least. So formidable that the system may never get off the ground. In which case the system would atrophy and we would be worse off than before. But it is the educational aspects that are the main concern. Here again there is good cause to suspect that we shall end up worse off than before.

There seem to be several fundamental fallacies about the NVQ approach. One is the assumption that technologies are all fundamentally the same and can be learnt and students' abilities assessed in a similar manner. The real debate concerns how much

theory one needs to know. One doesn't need a degree in agronomy to be able to plough a field competently. Nor does one need a knowledge of the finer aspects of electronic circuit design to be able to fault find effectively. One does however need to know how circuits work if one is to fault find at component level. Maybe the idea is that such fault-finding ability is no longer necessary or economic. Since most circuitry is today hidden away in anonymous-looking plastic lozenges, perhaps it's thought that the 'black-box' approach is adequate. Check the listed voltages and clear/condemn on that basis alone. This overlooks the interactive nature of much circuitry, particularly in TV sets. D.C. connections, feedback loops, shut-down systems, dependence on the presence of pulses for identification purposes, clamping, gating and so on mean that much of what goes on in TV and video equipment cannot be checked on the black-box approach alone. You have to be able to see a TV or video chassis as a complex system with many parts that depend on each other for the successful operation of the whole. I'm far from sure that an assessment of a few basic technical competences – say the use of test equipment, being able to carry out and assess the results of measurements, changing components and so on – is an adequate foundation for technological sleuth work. All right, with a bit of luck it may work for much of the time. But even when it does, time spent on methodical

checking can be saved if one has a deeper appreciation of how the equipment concerned works.

I recall someone who once ran a successful rental/repair operation telling me how he deliberately restricted his staff's knowledge. His main concern with the raw recruits he took straight from school was their ability to maintain good customer relations. He taught them how to do field servicing on one or two particular chassis by panel swapping (that was before the setmakers spoil things by putting most of the circuitry on one panel). By doing this he had staff who could just about carry out first-line servicing – and would never be pinched by other firms because they would be useless to anyone else! Anything that didn't respond to panel swapping could be handled by himself.

The danger is that the NVQ system will produce the equivalent of a generation of panel swappers. All because those who set themselves up to decide what needs to be done and how don't themselves know what is involved. Perhaps, the assessment process being what it is, it would be possible to cobble on extra bits indefinitely as the basic deficiencies of the system became apparent. But it would be better to take the existing approach and improve/develop it as necessary than move to something totally different that might work in some fields but seems to be inherently defective where complex technology is involved.

EDITOR

John A. Reddihough

PRODUCTION EDITOR

Tessa Winford

EDITORIAL OFFICE

081 652 8120

Fax 081 652 8956

Note that we are unable to answer technical queries over the telephone and cannot provide information on spares other than that given in our Spares Guide.

ADVERTISEMENT MANAGER

Carol Nobbs

081 652 8327

SALES EXECUTIVE

Pat Bunce

081 652 8339

Fax 081 652 8931

TELEVISION JUNE 1994

ADVERTISING PRODUCTION

Brian Chapman

081 652 8681

Fax 081 652 8917

PUBLISHING DIRECTOR

Susan Downey

SUBSCRIPTION ENQUIRIES

0444 445 566

SUBSCRIPTION HOTLINE

24-hour subscription ordering with credit card number. Phone 0622 721 666 and quote reference INJ.

COVER PHOTO

This month's cover photograph shows the Hitachi G7PS Mk. 2 chassis. See servicing article on pages 548-550.

Teletopics

CONSUMER DIGITAL VCR STANDARDS

The fifty members of the HD Digital VCR Conference have agreed, at a meeting in Tokyo, to standards for domestic digital VCRs. There are two, for standard and high-definition pictures. Members of the Conference include Matsushita, Philips, Sony, Thomson, Toshiba and computer companies Apple and IBM – they are involved because a digital VCR can be used to store computer data. The new generation of VCRs will store the video information in digital form using a cassette about two thirds the size of a standard VHS cassette – playing time will be four and a half hours. Initial models could be launched some time next year. Prices in the region of £2,000 have been suggested.

SATELLITE TV

Launch of the Astra 1D satellite this autumn could see fourteen new channels in operation by the end of the year, bringing the total number of Astra channels to 64. SES is reserving only one or two of Astra 1D's transponders for experimental digital TV transmissions.

Eutelsat has carried out, via its II F1 satellite at 13°E, the first European demonstration of a high-quality digital and analogue TV simulcast using a single 36MHz transponder. It has confirmed that an analogue channel with multiple sound subcarriers can occupy 27MHz of the bandwidth of a Eutelsat transponder simultaneously with a digital channel that uses the remaining 9MHz to provide a video signal exceeding normal broadcast quality with near-CD sound and auxiliary data. Thus broadcasters can at no extra cost transmit digital and analogue TV via a single satellite channel. The digital compression equipment used in the demonstration was provided by NTL.

NTL and Pace Micro Technology Ltd. have formed a new company to market a range of digital TV products to the MPEG-2 standard in time for the start of digital satellite transmissions next year. The new company is known as Pace-NTL Technology Ltd. and will operate on a world-wide basis.

BT has launched Europe's first TV distribution service using digital compression, via Intelsat 601 at 332.5°E. The service can cut broadcasters' costs by up to sixty per cent in comparison with the current rate for similar analogue distribution services. BT plans to launch a digitally-compressed transatlantic TV service later this year.

Swift Television Publications has introduced the *Mk. 2 Satmaster Pro for Windows* program, written by D.J. Stephenson, to enable installers, designers, system engineers, managers and enthusiasts to design satellite systems at virtually the touch of a button: the program enables a system's performance to be tested prior to installation; generates all the necessary look angles for fixed and motorised dishes at any location in the world; lists all visible satellites and their longitudinal position from any receiving site; calculates multiple full link budgets, indicating minimum dish size; has over thirty satellite footprints in its graphics file; displays beam-width and lobe patterns for various dish sizes, graphs, tables etc.; and contains a 20,000 word Hypertext technical guide with fault-finding notes, cable specifications and so on. Users can add project notes

and scan in extra footprints. The program is available at £99 (plus postage, £1 in the UK, £2 to Europe, £4 elsewhere) from Swift Television Publications, 17 Pittsfield, Cricklade, Swindon, Wilts SN6 6AN (0793 750 620, fax 0793 752 399). A DOS version is available at £69 plus postage.

BUSINESS NEWS

Daewoo is to invest £17m to increase VCR output at its Antrim plant in Northern Ireland. Production will be increased by thirty per cent when the programme has been completed in 1996.

Sony is to invest £4m at its Bridgend plant in South Wales to enable the factory to produce the steel frames used to support the aperture grill in Trinitron tubes. The investment is part of Sony's plan to spend some £147m on its plants at Bridgend and Pencoed.

Distribution of Crown brand products in the UK is now being handled by Crown Corporation UK, a subsidiary of HI Group plc. Spares continue to be handled by Datapart (see Spares Guide, April).

The NEI Spares Division (Nikkai, Dansai etc.) is now located at Unit 6, Southfork Business Park, Dartmouth Way, Leeds LS11 5JL (0532 774 310, fax 0532 774 312).

AZ Electrics, listed in the general/miscellaneous parts suppliers section of our Spares Guide (April issue), has moved to 183 Acre Lane, Northampton NN2 8DX (telephone/fax 0604 841 871).

THE FIELD BLANKING INTERVAL

Additional uses of the field flyback blanking interval are under investigation. Audio Descriptive Services (ADS) would add a separate sound channel for those with impaired vision. A trial service is to be started this year. Trials of an anti-ghosting system are also due to be started this year: an echo-cancelling reference signal will probably be inserted in line 318 to enable suitably-equipped receivers to cancel ghosts with delays of up to 40µsecs. The BBC is developing, for OB and news gathering purposes, a narrow-band (150Hz-3-6kHz) talkback system using two compressed audio data channels. A widescreen switching signal may be added on line 23 to enable future receivers to adjust the aspect ratio and positioning of subtitles automatically when a 16:9 format picture is being transmitted.

BS415:1990 SUPERSEDED

The British Standards Institution has just published BS EN 60065:1994 (also known as BS415:1994), *Safety requirements for mains-operated electronic and related equipment for household and similar general use*. It supersedes BS415:1990 which will remain current until September 15th 1995. Products that comply with BS415:1990 prior that date can continue to use the certification until September 15th 1999. Copies of the new standard are available from BSI Customer Services, Publications, Linford Wood, Milton Keynes MK14 6LE at £86.50 each (£43.25 to BSI subscribing members).

CINEMA SOUND FROM NOKIA


Nokia has introduced, at a suggested price of around £400, the HCS1000 Home Cinema Sound System. It enables a Nicam stereo colour TV receiver to produce four-channel Dolby Pro Logic Surround Sound. The system consists of a three-channel decoder/amplifier and three extra speakers, a centre sound unit and two surround sound units.



ELECTRONIC TEST EQUIPMENT

Audio - Video - Television - Satellite TV - Telecommunications

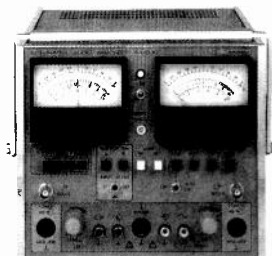The manufacturer who cares about quality & features rather than being lowest in price !



Audio Analyser Model AA-930

Multi-function meter. Measures distortion, wow & flutter, stereo power, signal levels in & out; generates audio test signals. Features include large clearly marked analogue meters. Performs the work of many individual instruments. £ 490




Function Generators Models GF-230 & GF-232

Two versions available: 0.1 Hz to 1 MHz and 0.2 Hz to 2 MHz. Producing sine, triangular and square waveforms, with variable symmetry. Excellent performance. £ 153 & £ 206

Low Distortion Generator Low Frequency Model GB-212


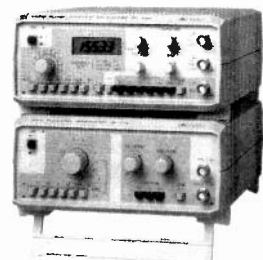
20 Hz to 200 kHz, harmonic distortion 0.02 % maximum over audio band. Frequency counter resolution as high as 0.1 Hz. 600 ohms impedance. Output level attenuation range 60 dB, with analogue meter for setting accuracy. Excellent output level flatness. £ 219



Television Pattern Generator Model GV-698/11


32 patterns, 32 internal memories. PAL/NTSC/SECAM standards, with I, B, G, H, M, N, D & K, NICAM, teletext all in one instrument.

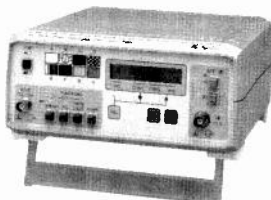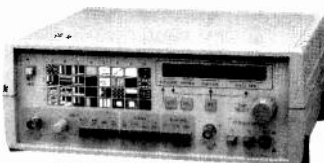Optional on screen logotype. (Other pattern generators available from £ 210). £ 1428



Television Pattern Generator Model GV-298

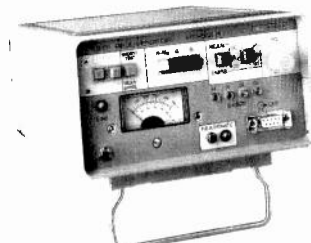Compact high performance generator, RF and video outputs. Frequency range same as GV-698/11, 37 to 865 MHz. Circle pattern included. £ 433



CRT Rejuvenator Model TA-903

Similar to TA-901, but has three meters to monitor cathode current. Special technique allows repeated rejuvenation of CRT. Supplied in attache style case, for easy field and workshop use. £ 498

CRT Rejuvenator Model RT-501 B

An essential tool for every TV workshop. Promax have made many thousands. Supplied complete with a set of base adaptors. £ 235




TV & Satellite Level Meter Model MC-360

Ideal instrument for the professional installer of FM/TV aerials and satellite TV dishes. Covers 48 to 856 MHz and 950 to 2050 MHz. Lightweight, compact and rechargeable battery operated. £ 654



TV/FM Level Meter Model MC-160 B

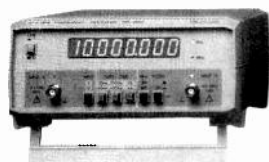The aerial installers best friend. Calibrated for accurate signal level measurements. Digital frequency display ensures correct signal selection and identification. Built-in demodulator for easy station ident, and audible tone for easy positioning. This meter is light in weight, but has outstanding technical features. £ 354





Frequency counters Models FD-250 & FD-252

FD-250 covers 20 Hz to 160 MHz and FD-252 covers same, plus 100 MHz to 2.4 GHz. Large L.E.D. display. Wide performance at low cost. £ 153 & £ 206


R.F. Spectrum Analyser Model AE-566

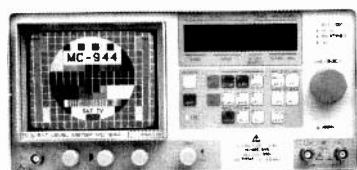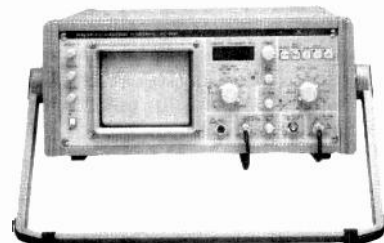1 to 1000 MHz, with 950 to 1750 MHz option. Built-in tracking generator. Offers spanwidths from 1 MHz to 1000 MHz. Includes normalizer. This analyser is ideal for production and educational applications, as well as R+D. £ 2800



TV & Satellite Level Meter Model MC-944

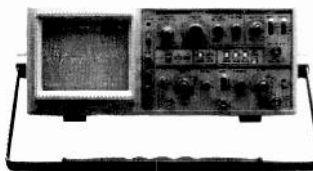This meter has everything for the top flight installer of aerials, dishes, CCTV, MATV, SMATV and other systems. Features include TV monitor, spectrum analyser, sync pulse, teletext, printer output, 99 memories, tuneable audio subcarriers, etc. Full autocorrection for superb, unequalled accuracy! RS-232 as standard. £ 1895



Oscilloscopes

We are able to supply a complete range of oscilloscopes. These include both analog and digital types, covering bandwidths of 20 MHz to 100 MHz. We are able to prepare quotations for a specified quantity.



The company has been producing test equipment in Spain for over thirty years, earning a strong reputation for excellent engineering, quality performance at budget prices. The equipment is supported by Alban Electronics from their St Albans facility. These products are suitable for only professional and educational applications and enquiries.



Prices shown exclude VAT, but includes UK delivery. Most items available for immediate despatch.



ALBAN ELECTRONICS LIMITED
4U - St Albans Enterprise Centre - Long Spring
Porters Wood - St Albans - Hertfordshire - AL3 6EN
Tel: 0727 832266 - Fax: 0727 810546

Servicing the Hitachi Models C2118R/T

Mike Leach

The Hitachi Models C2118R and C2118T (G7PS Mk. 2 chassis) were introduced in 1990. From the reliability point of view they've proved to be reasonably good, and the picture quality is excellent. The sets have definitely turned out to be good little earners for those retail outlets that chose to put them out on rental. Now, four years or so on, these sets are coming back into workshops as ex-rental receivers: in most cases the tubes are in very good condition for their age, also taking into account the heavy use that many rental sets get. Why then write an article about them if they are so good? Because, as with even the most reliable of sets, there are some common faults. Fortunately they are fairly easy and straightforward to put right and the sets can, in most cases, be fixed reasonably economically.

The chassis is compact (see front cover photograph) and very easy to work on. We all know that most modern sets can be very difficult to service, with many leads that have to be disconnected from wiring looms in order to get the chassis clear of the tube. This is not the case with the G7PS Mk. 2 chassis. The leads are all long enough, and access to the component and print sides of the PCB is easy. As the on/off switch is mounted on the main PCB there are no extra screws or brackets to remove or get in the way in the unlikely event that a replacement has to be fitted.

The two areas of the chassis that give most trouble are the power supply and the field output stage. You get the odd fault in other parts of the set, but not to the extent that any regular fault patterns have emerged.

The Power Supply

The power supply (see Fig. 1) is of discrete component design, being basically a self-oscillating series chopper. Mains bridge rectifier D901-4 develops about 320V across its reservoir capacitor C904. This voltage appears at the collector of the chopper transistor Q903 which, along with the primary winding (between pins 2 and 3) of the chopper transformer T901, is connected in series with the supply. T901 thus acts as an inductive reservoir, the regulated 112V output being smoothed by C905. The 130V zener diode ZD903 provides over-voltage protection. D906 acts as an efficiency diode, conducting when Q903 switches off and the voltage at its emitter swings negatively. Current flow is thus maintained, with the energy applied to the circuit depending on Q903's on/off times.

Q903 is connected as a blocking oscillator, with feedback to its base from the secondary winding (between pins 2 and 4) on the transformer via R904, R914, C908 and R908/C907. When the circuit is initially powered the bias applied to Q903's base via R902 and R903 switches it on. The feedback is then positive, and Q903 saturates. At this point C908 has charged negatively and Q903 switches off. C908 discharges via R908, R902 and R903: when the voltage at Q903's base is sufficiently positive it switches on again. The free-running frequency of operation is set by the time-constant of C908 and the associated resistors. Regulation is achieved by controlling Q903's on and off times.

This is done by Q904, Q905 and their associated components, which set the d.c. condition at the base of Q903 and thus C908's discharge time. D905 and C906 develop a voltage that's proportional to the output. This is used by the error sensing transistor Q905 to control the regulation. VR901 in its base circuit sets the h.t. voltage.

Standby switching is provided by Q902 and Q901. In the standby mode Q902 is switched on by the microcontroller chip IC001. Its low collector voltage is applied via D908 and R906 to the base of the pnp transistor Q901 which also switches on, shorting the base and emitter of Q903 which is then held cut off.

This means that a second supply, for IC001, has to be generated from the mains input. This supply is produced by the rectifier circuit D907, C913 and the following regulator circuit ZD001, Q007. LED D001 indicates that the set is on. When the set is in the on timer mode transistors Q001 and Q006 are switched on and off by the output at pin 12 of IC001. As a result the LED flashes to indicate that the set is in this mode. D007 supplies 50Hz pulses to IC001 to control its timer functions.

With the 'no results' complaint you are likely to find that D001 is lit. A good place to start is the over-voltage protection diode ZD903. Check whether it's short-circuit. If so the h.t. voltage has obviously risen above 130V. The most likely cause is that R909 (39k Ω , 0.5W) has gone high in value. It does so slowly over a period of time, the h.t. eventually rising above 130V. Replace R909 and ZD903, which must be of the correct type (P6KE130A). The customer may complain that the set has tended to trip in recent weeks, as R909 slowly deteriorates. This is only a possibility however and is not always the case. When the set is working again adjust VR901 for 110V at pin 3 of T901.

If the set is stuck in the standby mode, check the bias resistors R902 and R903 (both 82k Ω , 0.5W). If one of them goes open-circuit the set will appear to be dead with D001 alight. Usually only one of these resistors fails but it's best to replace them as a pair. Discharge C904 before replacing them – it's something I'm prone to forget to do!

Failure of the BUT12AF chopper transistor Q903 is rare, though I have come across this on occasions. I believe that the cause is deterioration of R909.

The other semiconductor devices in the power supply are very reliable. They are unlikely to fail other than in extreme circumstances such as a thunderstorm.

The Line Timebase

The line timebase is also reliable, though there are one or two things that are worth mentioning. The most common fault in the output stage is a whacking great dry-joint at one end of the 200V supply reservoir capacitor C711 (47 μ F). This item is easy to see towards the back of the chassis when the rear cover has been removed. The reported fault will usually be 'a very bright picture with lines' – the symptom is a peak white raster with flyback lines. Nine out

with flyback lines in the portables. In two cases the cause of the trouble was definitely a faulty tube, which fortunately failed during the guarantee period. The large-screen tubes have been very good.

As with the large-screen sets, tuning problems are generally caused by the tuner or the 33V zener diode. In one case however the cause was C033 (0.1 μ F) in the tuning voltage filter circuit.

If a portable set is stuck in standby it's very likely that, as with the large-screen sets, the two 82k Ω resistors R902/3 are the cause.

While similar to that in the large-screen sets the field timebase circuit in the portables is not prone to any particular faults.

In Conclusion

The large- and small-screen chassis are both very reliable. Hopefully any faults you encounter will have been covered in this article. If not, let us know! As promised earlier, here's the list of useful part numbers:

ZD903 over-voltage protection diode	2344121M
Type U743 tuner	E710019
LA7835 field timebase chip	2381662
MC7809 regulator (IC703)	T900489
TA8691N chip (portables)	T900486
Remote control unit (remote only)	2572281
Remote control unit (with teletext)	2572282

Satellite Fault

Notes

Amstrad SRD510

This unit failed to start. The two start-up resistors R602/3 had gone very high in value. Replacements should have a working voltage rating of 500V. There's a repair/update kit available for the power supply – it's well worth fitting this. **J.LeJ.**

Amstrad SRD400

If there's no LNB power supply from the aerial input socket check whether RP506 (6.8 Ω , 2W wire-wound) is open-circuit. **I.R.**

Pace SS6000

There were no pictures or sound, just a large patterning effect down the screen, with the vertically polarised channels. The channels with horizontal polarisation were o.k. We found the cause of the fault in the vertical LNB supply, where C75 and C69 were open-circuit. They are both 10 μ F, 25V types. **A.J.F.**

Finlux SR5100

This receiver had 'SC' flashing in its front display. Obviously stands for short-circuit. On investigation in the LNB supply we found that one leg of the preset was being earthed by the double-sided print. Normal operation was restored when we soldered the preset slightly away from the board. **A.J.F.**

Pace SS6000

When replacing the U2829B audio demodulator chip U1, note that the replacement should be type TBA229-2. Also replace C23 and C24, both 1 μ F, otherwise the chip could fail again. Has anyone else noticed the increase in sound level between these two chips? **A.J.F.**

Salora 5902

"Decoder stops working" was the complaint with this receiver. Sure enough the screen went blank when we tried Sky Movies. After switching to an unscrambled channel and back a few times the receiver worked all right for a while. I

Reports from John LeJeune, Ian Rees and Andrew J. Finn

thought it might be the relay, which could be heard switching, but no. There was no baseband output when this was checked with a scope, so we started to dismantle the receiver. Getting it to work out of its case on the bench while upside down involved removal of the lot, including the mains transformer. Then the receiver worked faultlessly for two days! Eventually it did fail and we found that TV30, a BC817-25 surface-mounted transistor, was the cause of the trouble. For a surface-mounted device it runs rather hot. Maybe the manufacturer should have used a conventional transistor. **A.J.F.**

Pace SS9000

The complaint was that there were small diagonal white dots on the screen with decoded channels. Changing the decoder made no difference. We eventually found that the culprit was C29, a high-temperature 100 μ F capacitor on the secondary side of the chopper transformer. **A.J.F.**

Salora 5902

When this receiver was switched on a loud buzzing could be heard from relay REL1. In addition only the top half of the number 1 in the front display was visible. When the PCB was removed we found that there was a very nice dry-joint at the 4,700 μ F reservoir capacitor CP16. Resoldering this put everything right. **A.J.F.**

Finlux SR3000

This nice receiver displayed only snow. Checks around the tuner showed that the tuning voltage was missing. As the transistor in the integrating network was o.k. we monitored the tuning output at pin 18 of the SDA3202-3 chip IC1. With the receiver in the scan mode only 0.4-0.5V was present here. The inputs to this chip are at pins 4 and 5, which are connected to the SDA and SCL lines respectively. Oh no! As far as I could tell the conditions here were correct (how do we know for sure?), so a new SDA3202-3 chip (part no. 4400 3001-027) was ordered and fitted. Fortunately for me this cured the fault – I'm not too keen on fast-moving digital pulses. **A.J.F.**

Finlux SR5100

There was sound but just a blank screen. This was a simple one: the 1 μ H choke L7 in the video feed through the de-emphasis network was open-circuit. **A.J.F.**

MANOR SUPPLIES

MKV PAL COLOUR TEST GENERATOR FOR DOMESTIC TV & VCR.

TEST DEMONSTRATIONS AT 172 WEST END LANE



- ★ 40 different patterns and variations.
- ★ Fully interlaced sync pulses with correct picture blanking
- ★ EBU colour bars, BBC colour bars, whole rasters & split bars (specially useful for VCR service), white, yellow, cyan, green, magenta, red, blue and black
- ★ Chequerboard
- ★ Mono outputs with border castellations, cross hatch, grey scale, vertical lines, horizontal lines and dots. UHF modulator output plugs straight into receiver aerial socket.
- ★ Additional video output for CCTV & VCR.
- ★ Facilities for sound output.
- ★ Easy to build kit, standard parts. Only 2 adjustments. No special test equipment required.
- ★ Mains operated with stabilised power supply.
- ★ All kits fully guaranteed with back-up service.
- ★ Also available with VHF Modulator.

Price of Kit **£79.00**
Case (10" x 6" x 2 1/4") app **£19.00**
Optional Sound Module (6MHz or 5.5MHz) **£5.90**
Built & Tested in Case including Sound Module **£129.00**
Post/Packing £4.50
Add VAT 17.5% TO ALL PRICES

PAL COLOUR BAR GENERATOR (Mk4)

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars R-Y, B-Y etc.
- ★ Cross-hatch, grey scale, peak white and black level.
- ★ Push button controls, battery or mains operated.
- ★ Simple design, only five i.c.s on colour bar P.C.B.
- ★ Backup service available.

PRICE OF MK4 COLOUR BAR GENERATOR KIT **£39.00. CASE £5.80. BATT HOLDERS £4.20**

MAINS SUPPLY KIT £5.80
(Combined P&P £4.50)

VHF MODULATOR (CH1 to 4) FOR OVERSEAS £6.80.
EASILY ADAPTED FOR VIDEO OUTPUT & C.C.T.V.

ADD
VAT
17.5%

LINE OUTPUT TRANSFORMER TESTER

- ★ Service Aid.
- ★ Saves time and money.
- ★ Checks short turns.
- ★ Simple to use.
- ★ Reliable.
- ★ Battery operated.
- ★ Pocket size.

PRICE **£24.00**
POST/PACKING **£2.50**

ADD
VAT
17.5%

INFRA RED REMOTE CONTROL TESTER

- ★ Pocket size.
- ★ LED + audible indication.
- ★ Simple to use.

PRICE **£20.00**
POST/PACKING **£2.50**

KITS AND PROJECTS

SAW IF AND TUNER UNIT complete and tested for video & audio outputs **£28.50 p.p. £1.80.**
PAL DECODER KIT (Video to RGB) for Monitors **£27.00 p.p. £1.80.**
PAL ENCODER KIT (RGB to Video) **£20.00 p.p. £1.80.**
CRT TESTER & REACTIVATOR KIT For Colour & Mono complete with Case, Panel Meter Indicator - can be adapted for latest CRTs **£45.00 p.p. £4.50.**

TV & VIDEO SPARES

REMOTE CONTROLS

Replacement for: Ferguson, Hitachi, Philips, Panasonic, Grundig, I.T.T., Sony, Saisho, Granada, Saisho - many others

Phone for make and model no.

IC SELECTION

140N487	£15.80	SAF1032	£4.50	TA7600AP	£5.80	TDA2581	£6.80	TDA4600	£3.85
AN5521	£3.80	SAF1039	£2.20	TA7681P	£7.80	TDA2582	£2.80	TDA4601	£2.80
AN5900	£2.20	SL4704/471	£4.80	TA7698P	£6.80	TDA2593	£1.80	TDA4603	£2.20
BA6209	£3.80	SL486	£3.20	TB7339P	£4.50	TDA2594	£3.80	TDA4610	£6.80
BA6219	£3.80	SL490	£3.80	TBA120S	£1.20	TDA2595	£4.80	TDA4950	£1.60
BA6229	£3.80	SL1430	£2.40	TBA750	£2.20	TDA2600	£6.80	TDA5510	£12.50
BA6238A	£2.80	SL1432	£2.40	TBA920	£2.80	TDA2611A	£1.90	TDA5850	£2.80
BA6239	£3.80	SN76226DN	£1.80	TBA950	£2.20	TDA2604	£3.20	TDA7052	£2.50
CCUFRG07	£14.40	SN7670S	£9.80	TBA2800	£1.80	TDA2653A	£5.80	TDA8153	£7.80
CN362	£4.80	STK5322	£21.80	TCA270	£1.80	TDA2654	£5.70	TDA8170	£3.00
HA11211	£2.80	STK5325	£6.80	TCA800	£6.80	TDA2655B	£16.60	TDA8172	£12.95
HA11233	£2.80	STK5326	£6.80	TDA316A-P	£4.80	TDA3270	£3.20	TDA8175	£2.50
HA51338SP	£21.50	STK5332	£6.80	TDA1035T	£2.40	TDA2680	£3.80	TDA8180 Kit	£7.50
LA4445	£3.80	STK5333	£8.80	TDA1037	£1.90	TDA2690	£3.80	TDA8190	£3.80
LA4520	£3.80	STK5338	£6.80	TDA1044	£2.90	TDA2700	£6.80	TDA8305	£9.80
LA7800	£1.80	STK5337	£7.80	TDA1215	£3.80	TDA2811	£4.20	TDA8341	£4.20
LA7520	£2.80	STK5339	£6.80	TDA1082	£4.80	TDA3301	£6.80	TDA8372A	£8.40
LA7801	£3.50	STK5342	£4.80	TDA1170S	£1.80	TDA3303	£19.80	TDA9403	£3.80
LA7820	£3.80	STK5372H	£7.80	TDA1180	£2.20	TDA3330	£12.50	TDA9503	£3.80
LA7830	£3.80	STK5431	£7.80	TDA1202	£2.80	TDA3350	£2.80	TDA9513	£4.80
LA8781	£6.80	STK5421	£6.80	TDA1190Z	£2.20	TDA3505	£4.50	TEA1009	£2.20
M293B1	£15.80	STK5422	£8.50	TDA1432P	£5.70	TDA3510	£9.80	TEA1014	£3.50
M490BB1	£16.80	STK5471	£6.50	TDA1512	£3.20	TDA3540	£2.50	TEA1039	£2.80
M491BB1	£9.80	STK5481	£6.80	TDA1548	£4.50	TDA3541	£3.50	TEA2018A	£2.20
MU04B1	£5.80	STK5482	£5.80	TDA1524	£3.80	TDA3561A	£5.80	TEA2026	£5.80
MU13002P	£5.80	STK5490	£7.80	TDA1670A	£6.20	TDA3562A	£5.80	TEA2029	£5.80
MDA2062	£3.80	STK6962	£3.80	TDA1701	£3.80	TDA3565	£3.80	TEA2164	£3.95
MU137	£3.80	STK7308	£6.80	TDA1309A	£9.20	TDA3566	£3.80	TEA2165A	£6.80
MN103	£15.80	STK7348	£10.80	TDA1870	£6.80	TDA3571	£4.20	TEA5115	£6.80
MN1542S	£15.80	STR3125	£4.80	TDA1872	£9.80	TDA3576B	£9.80	TMS100N21	£6.80
SAA1024	£5.80	STR441	£15.80	TDA1908	£2.80	TDA3640	£5.20	TMP47432AP	£6.80
SAA1025	£3.80	STR450	£11.40	TDA1940	£3.20	TDA3650	£3.20	UC2829B	£1.95
SAA1024	£3.80	STR451	£7.80	TDA1950	£3.50	TDA3651	£4.20	TMP47C432AP	£4.80
SAA1250	£3.80	STR454	£14.80	TDA2004	£2.80	TDA3653A	£3.80	UC3844	£1.50
SAA1251	£8.40	STR4090	£13.50	TDA2006	£2.80	TDA3653B	£3.20	TMP47C434N	£4.80
SAA1293.02	£8.80	STR4211	£6.80	TDA2009A	£2.80	TDA3654	£3.20	3555	£16.80
SAA193.03	£3.80	STR5412	£9.80	TDA2030A	£4.80	TDA3810	£5.50	TMP47C434N	£2.20
SAA5000	£6.80	STR40090	£6.80	TDA2030A	£3.80	TDA4420	£2.20	3559	£15.80
SAA5010	£5.80	STR50020	£6.80	TDA2040	£7.80	TDA4426	£3.20	TUA2000	£8.50
SAA5012	£5.80	STR50103	£5.80	TDA2050	£4.80	TDA4427	£3.20	UC2829B	£6.50
SAAS020	£6.80	STR5041	£5.80	TDA2050A	£3.20	TDA4442	£2.80	U4666	£14.80
SAAS030	£6.80	STR54041	£6.80	TDA2270	£3.80	TDA4443	£7.80	UC3844	£2.50
SAAS040	£6.80	STR55041	£10.50	TDA2450	£2.20	TDA4500	£5.80	UPC1363C	£5.80
SAAS050	£11.80	STR58041	£6.80	TDA2450A	£5.80	TDA4501	£7.80	UPC1363CA	£2.80
SAAS231	£4.80	STR9041	£11.80	TDA2570A	£7.80	TDA4502A	£13.50	UPC1378	£1.90
SAAS243	£23.50	STR6020	£7.80	TDA2577A	£4.80	TDA4503	£5.80	UPC1394	£3.80
SAB3035	£9.80	STRD4420	£4.80	TDA2578	£3.80	TDA4505	£6.80	UPC1420CA	£12.20
SAB3037	£8.80	STRD6108E	£5.80	TDA2579	£3.80	TDA4555	£9.80	UPC1480	£3.20
								IPD1397C	£4.80
								IC p-p 90p	

LINE OUTPUT TRANSFORMERS p.p. £1.80

ALBA CTV74RS	£23.80	PHILIPS K40	£27.50
ALX2500/2800 AT2077/81	£23.50	PHILIPS 3A	£20.00
BUSH AT2079/10	£34.80	PHILIPS 2B	£20.00
DECCA/TATUNG 145, 146, 147 PNR853786	£21.80	PHILIPS CF1	£23.80
FIDELITY ZXC200	£15.50	PHILIPS CP90	£15.50
FIDELITY ZX300	£18.50	PHILIPS CT110	£32.00
FIDELITY ZX3000 22"	£21.80	PHILIPS GR1AX	£25.90
HINARI CT4, CT5	£14.00	PHILIPS NC3	£22.50
HITACHI CPT1455, 1456, 1476, 2434/41	£11.50	SAISHO CT14B, CT141, 3714002	£19.80
HITACHI CPT1446, 1626, 2432981	£18.60	SAISHO CT14B, CT142B, 3214009	£23.80
HITACHI CPT1714, 2176, 2178, 2434274	£17.50	SANYO CBP2144, 2145	£39.80
HITACHI CPT2476, 2478, 2434002	£21.80	SANYO CPT7132, 7135	£19.50
HITACHI CPT3074, 2274, 24335	£19.80	SOLAVOX 14R19	£16.50
ITT/NOKIA Compact B, 110"	£17.80	SOLAVOX 16R19	£15.50
ITT/NOKIA Compact 80, 110"	£15.00	SOLAVOX 20T19	£21.80
ITT/NOKIA Compact 80, 90"	£14.70	SOLAVOX 22R19	£15.00
ITT/NOKIA Compact 80, 70" FS	£19.80	SOLAVOX 22S19	£15.00
ITT/NOKIA CVC 25, 30, 32	£19.00	SOLAVOX 22T19	£15.00
ITT/NOKIA CVC 800, 801, 803	£14.95	SONY KV1412	£21.80
ITT/NOKIA CVC1100, Picos	£18.50	SONY KV1440, 1460	£20.00
ITT/NOKIA CVC1200, 1201, Mim 2	£21.80	SONY KV1882	£22.80
ITT/NOKIA CVC1204	£11.50	SONY KV2056, 2062	£32.00
ITT/NOKIA CVC1210/12/15/17	£15.80	SONY KV2092/96	£24.80
ITT/NOKIA Dgg 3, 110"	£15.80	SONY 2212, 2216, 2217	£22.80
ITT/NOKIA Core 110" 4515-03-46	£19.80	SONY KV21XRTU	£52.00
ITT/NOKIA Core 110" FST	£19.80	SONY KV2252/56, 2257.56, 2762/66 P.E3	£29.00
LOEWE C9000, Art1, Art 21, Art 228, Contur	£5.90	SONY KV2704	£29.00
S124, S127, S128, S24, S28, Profi S28	£22.80	SONY KV27XR1U	£25.50
LOEWE Classic M124, M27, Contur M27	£24.40	THORN/FERG TX9	£19.80
LOEWE Profi M21	£24.40	THORN/FERG TX10 (Chopper)	£19.80
LUXOR 5810110.01	£27.60	THORN/FERG TX85, R6	£19.80
MATSUI 1440A, 1480A, 3714002	£19.80	THORN/FERG TX89	£23.50
MATSUI 1420B, 1440B, 3214009	£19.80	THORN/FERG TX90 4", T9031, Red Spot	£17.80
MATSUI 1455	£32.20	THORN/FERG TX90 20", T9044, White Spot	£19.80
MATSUI 1465	£21.80	THORN/FERG TX100 110" T6033L, Green Spot	£14.00
PANASONIC TLF14520F, TLF 14568F	£24.80	THORN/FERG TX100 90P, T6031, Blue Spot	£15.00
PANASONIC TLF14521F	£24.80	THORN/FERG TX100 110" FST, T60451	£16.80
PANASONIC TLF14584F	£29.00	THORN/FERG TX107 Chopper Tx	£15.80
PANASONIC TLF14586F	£29.00	THORN/FERG IC5P7	£32.00
PHILIPS KT3	£12.90	THORN/FERG IC55, 44076100	£28.80
PHILIPS K30	£22.80	THORN/FERG IC55, 47235901	£21.80
PHILIPS CTX-E/S	£23.80	THORN/FERG IC55, 47238700	£18.00
PHILIPS KT4	£22.50	THORN/FERG IC55, 59M5	£28.00
PHILIPS 2A	£32.00		

MANY OTHER OPTS IN STOCK, PLEASE PHONE WITH MAKE AND MODEL NUMBER

TRIPLERS EHT MULTIPLIERS p.p. £1.80

CONTINENTAL UNIVERSAL TVK & BG RANGE (Quote exact no.) £13.80	DECCA/TATUNG BG 200/44 TYPE £7.80
TVK 96-1 £13.80	GRUNDIG BG 2077-642-1003/1004 £16.80
TVK 96-3 £18.00	GRUNDIG BG 2087-642-1001/1002/1006 £16.80
U.K. UNIVERSAL (best quality) £7.80	GRUNDIG BG 2000-641 £13.80
	THORN 9000 £9.80

MISCELLANEOUS p.p. £1.80

MAINS TRANSFORMERS: 6.3 Volts CRT boost £6.80 p.p. £1.80	VCR FAULT FINDING GUIDE £14.80
Mains Isolating 500VA £51.25 p.p. £5.25	HITACHI FRAME MODULE HM 6251, HM6232 £9.80
455 CRYSTALS for handsets, 4 for £2.00 p.p. 80p	HITACHI THERMISTOR TH902 £2.85
DEGAUSSING ROD £33.75 p.p. £3.50	FERGUSON TX10 FOCUS UNIT £8.50 p.p. £1.80
TRANSPARENT VIDEO SERVICE CASSETTE £6.80 p.p. £1.80	PHILIPS BACK UP BATTERY: 2.4V £3.00, 1.2V £2.00 p.p. 90p
TV FAULT FINDING GUIDE £14.80	

HOW TO ORDER: ADD p&p TO ORDER + VAT 17.5% TO THE TOTAL
PRICES ARE SUBJECT TO CHANGE WITHOUT NOTICE

Telephone 071-794 8751/794 7346
Fax 071-431 5778

MANOR SUPPLIES

172 WEST END LANE, LONDON NW6 1SD

CALLERS WELCOME AT SHOP

Mon-Fri 9.30-6pm - Thurs 9.30-1pm - Sat 9.30-5pm

Letters

THE COWBOY ELEMENT

Various letters have been published over the last year or so on the subject of the 'cowboys' in our trade. I'd like to add my views, but first let me explain the situation in which I find myself.

My business went into liquidation some two years ago. I had sold new products and some second-hand units, and carried out repairs both to items we sold and generally. A number of authorised dealer agencies had been secured. I feel that the reasons for the collapse of my business, apart from the recession, relate to something-for-nothing cowboys and more importantly a certain manufacturer who was unable to abide by, or ensure that his dealers do, the manufacturer's contract. A letter in the May 1993 issue of *Television* complained of lack of technical support for certain manufacturers' products the writer sold. The point is that he shouldn't have been selling them and shouldn't have been able to obtain them: the dealer who acted as a wholesaler was in breach of his contract which states "that you will sell only to an end user or another authorised dealer". In order to be granted an agency by the manufacturer concerned one has to meet certain requirements. Our business did so, but a shop across the road didn't. To make matters worse they put up a sign bearing the manufacturer concerned's logo (there were also other manufacturers' logos), implying to the public that the shop was an authorised dealer. It took the manufacturer several months to force the other shop to remove the sign, by which time it was too late for us.

A number of people who call themselves TV/video repairers and advertise as such cannot repair the products and either bodge or farm the work out. Here are a couple of examples.

A man phoned me one day. He told me he'd been led to believe that the servicing trade can be lucrative, but he didn't know enough about servicing. He could clean heads and resolder dry-joints. Could he bring the other work to me? He charged about £50 to clean heads, and about £80 to replace the limiter post assembly in a Matsui VCR! His problems started when he quoted £80 to replace the memory chips in a Philips TV set (back-up battery problem), then he encountered a set fitted with the Thorn 9000 chassis. He knew that as a check you can disconnect the tripler then switch on. But he didn't know which lead to disconnect – he switched on after disconnecting the e.h.t. cap!

A local repairer who advertises "free estimates" in a local paper charged a young lady £120 to repair her Philips VCR. When it jammed up two months later he wanted another £120 to replace the rack. So she came to me. The original repairer had replaced the pinch roller and fitted a service kit. The VCR's owner decided to try, with my help, to retrieve some of her money. When she issued a county court writ it transpired that the 'repairer' had subcontracted the work to someone else who had in turn subcontracted it to a trade repairer. If each person in the chain charges £40 it's easy to see how a bill for £120 can arise. To make matters worse, the first two 'repairers' live opposite each other.

Another repairer left a Philips G11 in a very dangerous state. He also repaired an Amstrad TV set in such a way that it started to burn.

In all the above cases, including the shop across the road from mine, the Trading Standards people wouldn't get involved. They even told the lady with the Philips VCR that it was just tough.

So what should be done? Be under no illusion. These cowboys are stealing our business. They shouldn't be allowed to represent themselves as repairers or advertise their 'services' when they are clearly not able to fulfil such functions – unless they clearly state that the work will be subcontracted out.

Licensing could be an effective way of dealing with the problem. In the USA for example you have to show the authorities that your business is competent before you can carry out work and provide services. This applies to car repairers, TV repairers, plumbers, builders – even hair-dressers. The trade should consider this, possibly setting up its own body to regulate the industry.

After losing thousands of pounds I'm now employed by a national Service company. I earn a regular salary but don't get anything like job satisfaction.

Name and address supplied.

TECHNICAL BACK-UP

I'd like, as an avid, long-term reader, to say how much I agree with Michael Cordner of M & M Video (letters, April) who expressed his concern at the decline of technical back-up from manufacturers, especially to those of us who are small businessmen and are not associated with specific manufacturers.

If however, like me, you have an account with Willow Vale you'll find that this company provides a very good service through its Technical Department. Alan Dyson in particular seems to have a wealth of information at his fingertips and is only too willing to assist those of us who require some technical help from time to time, especially with some of the not-too-often seen clones. As an ex-Grundig engineer he can be especially helpful with this company's products.

Well done Willow Vale, and thank you Alan for all your assistance in the past. Keep it up!

A.E. Somerville, Grad. I.E.I.E., Tony's TV, Southampton.

LESS HASSLE

I recently ran into an old trade colleague – from about twenty years ago. Last time we met was about five years ago, when he was trying to decide between taking up a job offer in a nearby town or setting up on his own. He tells me that he has now left the trade altogether to become a traffic warden. He says there's less hassle!

*John C. Priest,
Blankpool, Lancs.*

SPARES PRICES

Michael Cordner (letters, April) complained about spares price increases that are implemented without warning. I would urge others to check prices before ordering. In a spare moment I looked back through last month's invoices and checked the prices against those in the 1994 catalogue of a well-known supplier. At least two had gone up by around 12 per cent, another by a little less. Then came the final blow! A package containing just a few cassette belts arrived on the doormat – a back order from about a month before. Ten had originally been ordered at 23p each. Twenty had been sent at £1.28 for two (64p each). Not

only had the price been almost tripled, twice as many had been sent!

A quick call was made to the company's sales department. I was told that it has no control over the prices charged by its suppliers and that it would not be practical to advise customers of price increases on back orders. I was given a returns note number and sent the belts back, insisting that the 30 per cent charge normally levied on returned orders wasn't charged. Inflation is still running at under five per cent a year. I'm wondering whether the steady prices we've enjoyed over the past few years have finally come to an end now that we appear to be emerging from the recession.

*M.J. Goodall,
Littleport, Cambridgeshire.*

FAULT-FINDING SYSTEMS

When I bought an expensive fault-finding system recently I thought I was getting access to manufacturers' database material and could be as smug as their technical support teams. But I was fooled.

The system boasted availability in several languages, though I'm not really sure which one was used by the system I was sent. I think it was translated by Manuel. "It's the Lines Output Transformer Mr. Fawltly. It's gone slightly open-circuit. I learn it from a book". Many of the remedies have the vagueness of a horoscope, telling you for example to resolder the legs of a capacitor without mentioning which particular one. There are strange resistors that switch off, and even stranger TV sets that won't change stores. What are they supposed to do – pop next door to Rumbelows?

The little red and blue Datatech books have the same information without all the gobbledegook and at a fraction of the cost. And yes your own fault index is of course excellent and we all love it very much!

Why can't manufacturers make their databases available for sale? Then those that still do provide free advice wouldn't be pestered so much.

*P. Barry, Teletechs,
Bedale, North Yorkshire.*

FUN WITH AN AMSTRAD CTV2200

The untidy chassis of the Amstrad CTV2200 has never been one of my favourites. This one came in with the chopper and line output transistors and C845 (4.7µF, 250V), which smooths the 180V supply for the RGB output stages, all short-circuit. The h.t. was o.k. when the power supply was tested using a lamp as the load. There was no line drive from the LA7800 timebase generator chip unless the protection pin (pin 4) was connected to chassis. After blowing another pair of transistors I replaced the line output transformer. Nothing happened for about a minute, then the new C845 fizzed and blew up. Monitoring the voltage across its replacement (uprated to 350V) with the collector of the line output transistor disconnected produced an astonishing reading of 360V!

To cut a very long story short, because of partial failure of the 100µF h.t. smoothing capacitor C520 the line output transformer was being driven by the power supply. I don't know whether the original LOPT had been damaged – I didn't feel inclined to risk putting it back. Other damage as a result of the basic fault was failure of both audio output transistors and the sound chip. Incidentally there are several inaccuracies in the circuit diagram, which shows both the main h.t. and the RGB output h.t. lines as being

112V. The block diagram shows the former as 150V and the latter 180V, which is correct. The voltages shown around the TDA3652 field output chip are also incorrect.

One is accustomed to thinking that with the line output transistor disconnected the transformer is inactive: it was scary to find that in this case it was more than usually active, producing very high output voltages. I wonder whether this can happen with any other models? The fact that the chopper circuit used is of the series type could be relevant.

*L.P. Watkinson, Telesonic Services,
Holsworthy, Devon.*

A SALUTORY TALE

There can be very few occupations where a minor lapse in concentration can have such frightening consequences as occur in our trade. One slip of a test prod or screwdriver and you can be up to your ears in it! This was brought home to us recently when a Samsung V18220 VCR came in with the complaint that there was a buzz on the sound when tapes were being played. The cause turned out to be a dry-joint on C102 in the power supply. Having carried out the repair, we connected the machine to the mains supply and switched on. There was a smell of burning and the thing went dead. Too late we realised that the earth lead that's anchored to the case when the bottom cover is in place had been left floating around and had found its way under the main PCB. This meant that the machine now had a fault which was probably several times worse than the original one.

As we didn't have the manual, we had to play this one by ear. So checks were initially made in the power supply, where R101 (1Ω) was found to be open-circuit. When this item had been replaced the machine displayed good playback pictures, but with no sound and a blank, noise-free raster in the E-E mode. As there was no 12V supply at the tuner, we traced the print back from the B+ pin. This led us to Q106 which was short-circuit. A replacement restored normal working and produced sighs of relief all round, as the potential for damage in such an event can be horrendous.

The lesson of course is to check, check and check again before switching on!

*Ed Rowland,
Luton, Beds.*

CITY AND GUILDS

The City and Guilds as Mickey Mouse (letters, November 1993)? Hardly – I speak as a C&G stalwart from 1967 through to 1993 (full 48 and 224 TV and video), with twenty years at the sharp end, an original Colour Tech on G6s and 2000s etc. and as a good Telly Man before that, with a pocket-full of PL81s and PL36s. Perhaps C&G by itself could be considered M. Mouse, but it was always intended as a supplement to practical experience in a job. A full-time HND takes two years at four days a week on a £40 student grant and a garage for the paperwork. The colleges are full of professional students who, if asked, couldn't fix their bottoms to a seat!

HND or not, the Telly Man has always needed the heart of a lion, the brain of Einstein and the strength (in the old days) of Charles Atlas. Also an encyclopaedic street knowledge and the ability to make a TV van fly. M. Mouse indeed!

*K. Wells,
Liverpool.*

Modern TV Receiver Techniques

Part 18: Field-store Systems

Eugene Trundle

The analogue transmission and scanning systems currently used for broadcast TV were established many decades ago, suiting the circumstances and hardware of the day. They represented an excellent compromise between performance, use of spectrum space and picture flicker rate and have served us well – they will continue to do so for many years yet.

Impairments

There are several shortcomings however with all three of the established broadcast systems – PAL, SECAM and NTSC. The main one is large-area picture flicker, which is particularly noticeable with large screens and is at its worst with bright displays and at peripheral viewing angles. It arises from the inability of the human eye/brain to integrate fully successive pictures that have a 'flash rate' of 50Hz, as currently used in Europe. In the USA, Canada and Japan, where a 60Hz field rate is standard, the flicker effect is less perceptible. As the field rate is increased, the perceived flicker is lessened: at a flash rate of about 90Hz it disappears under all picture brightness, viewing angle and ambient light conditions. It would be very wasteful of broadcast spectrum space to transmit 90 fields per second however; while the use of a quadruple-interlace system to achieve the same effect would result in intolerable line flicker.

Other problems with current TV systems are interline flicker where sharp horizontal edges of objects in the picture and fine horizontal lines have a 25Hz repetition rate, cross-colour which produces coloured interference patterns where fine vertical detail is present, and cross-luminance which results in a fine dot pattern in the region of sharp colour

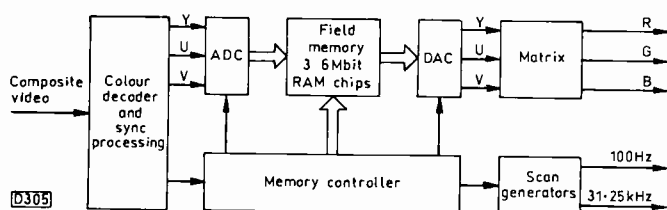


Fig. 1: Block diagram of a 50-100Hz converter for flicker-free TV pictures.

transients. These last two conditions arise as a result of the need to interlace the luminance and chrominance signals so that they share a common channel bandwidth, and can be minimised (at a price) by the use of sophisticated comb filter techniques in the receiver. The flicker effects, which are inherent in the basic analogue TV systems, show up because it's traditional for the display to be presented in synchronism with the transmission. The advent of large capacity, high-speed memory chips at reasonable prices has overcome the need for the scanning rates to be tied to the transmission standard, opening the way to the removal of the flicker problems.

100Hz Pictures

To arrange for the receiver to display the transmitted pictures at a 100Hz field scan rate a device that can store a

complete field of video information is required – and it's not practical to store the video information in analogue form. Thus digital memories are used. For a high-quality picture on a large screen a total memory capacity of about 3Mbits is required – in the most sophisticated and expensive sets that use this technique the storage provided is up to 6Mbits.

The basic idea, shown in Fig. 1, is simple. The video signal is converted from analogue to digital form, the video data being fed into the memory at the 50Hz broadcast rate. It's read out of the memory at the faster rate of 100Hz, converted from digital to analogue form and displayed on the screen at double-speed line and field scan rates.

The transmitted field sequence is ABCD etc., the double-rate memory read out giving us AABCC etc. as shown in Fig. 2. This eliminates large-area flicker, but interline flicker remains. The rate of change of the actual picture information is still 25Hz, corresponding with the transmitted 25Hz interlace rate. To eliminate interline flicker the interlace rate has to be increased to 50Hz, which involves the display of two different fields in each 20msec period. Thus the field readout sequence becomes ABABCDCD, as shown in Fig. 3. It's clear from this that to operate this scheme we need two complete field memories, with alternate readings from each at 10msec cycles.

Once the line flicker problem has been solved in this way a new problem arises. While the ABABCDCD sequence produces excellent still pictures, with a moving image the change in the order of the transmitted fields gives rise to a strange juddering effect – because of the continuous hopping to and fro in time. The best current solution to this problem is a compromise one, using a processor to compare the contents of the successive transmitted fields on a pixel-by-pixel basis in order to detect motion. The system is referred to as a median filter, and works by selecting picture elements from each of the two memories to make up the alternate 100Hz fields. With a still picture the sequence remains ABAB etc. Where there is movement in the picture it becomes AB'A'B, as shown in Fig. 4, the A' and B' fields being assembled from pixels in both the A and B fields transmitted. The interlace rate remains at 50Hz, so that interline flicker is eliminated all the time.

Television transmission of cine films presents a special case. In the telecine converter each film picture is scanned twice, producing two identical fields before moving on to the next frame. There is however no fixed relationship between the field pairs and interlacing, so that identical pairs may form fields AB or BC. Sets that use the median-filter system incorporate a special detector that identifies a film transmission and the sequence of identical field pairs. This facilitates perfect reproduction on an ABAB or BCBC basis, free of all line and field flicker.

Not all 100Hz sets incorporate the double-memory interline flicker reduction system, which increases the cost and complexity.

AD Conversion

A single analogue-to-digital converter (ADC) could be used to convert the composite video signal, chroma subcarrier and all, to digital form. In practical 100Hz designs

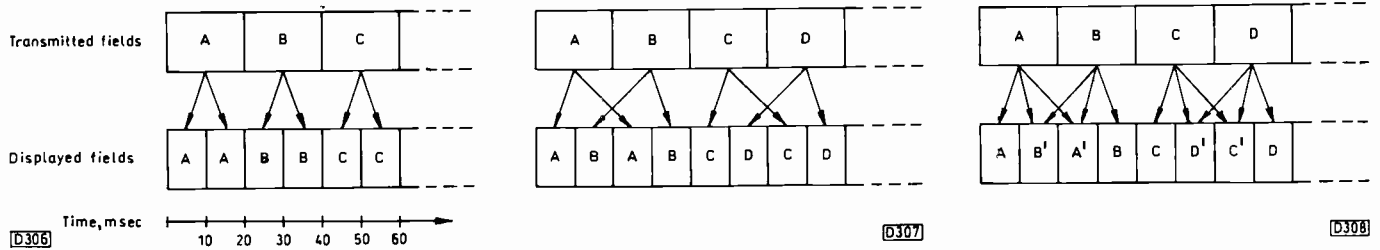


Fig. 2 (left): Simple field rate doubling by repeating fields.
 Fig. 3 (centre): Interlacing at 100Hz: this removes interline flicker but produces blurred, shaky motion.
 Fig. 4 (right): 100Hz interlaced fields with interpolation using a median filter.

however the PAL (or whatever) signal is first filtered and decoded, by analogue or digital means, producing the separate luminance and colour-difference (YUV) signals. These are then separately converted to digital form and stored. At the end of the chain they are matrixed to provide the usual RGB signals to drive the tube.

The ADC used for this relatively high-speed application is known as the 'flash' type, see Fig. 5. It provides an eight-bit output, using 256 separate comparators. Each

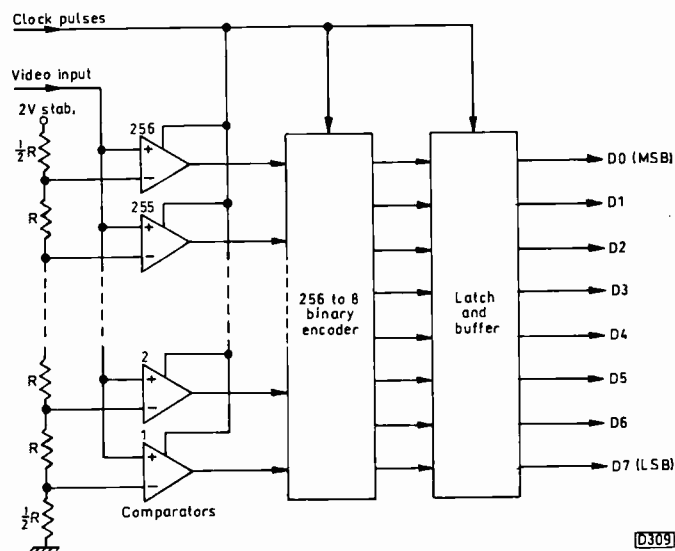


Fig. 5: Operating principle of a fast 8-bit ADC of the type used for video signals.

comparator has two inputs. One of these is connected to its own individual tapping point in a chain of 256 equal-value resistors. The other inputs are all connected together and receive the video input signal. A stable voltage, here exactly 2V, is maintained across the resistor chain so that each resistor has across it one 256th of the total voltage. The video input is gain controlled at precisely 2V peak-to-peak, its black level or sync tip being clamped – see Fig. 6(a) – at a fixed level so that the peak white video level just turns on the topmost comparator in the chain. As the video signal swings from black through grey to white, progressively more comparators are turned on in 256 steps of 7.8mV.

When a clock pulse arrives, the outputs (0 or 1) of the 256 comparators are loaded into a 256-to-8 binary encoder. This converts the 'quantised' samples into eight-bit bytes which are passed to a latched buffer. With each clock pulse a fresh sample is taken and a new eight-bit byte is produced. The frequency of the sampling clock is typically 13.5MHz. To avoid aliasing and spurious effects, a Nyquist filter limits the luminance input to less than half this frequency – it cuts off at 6.5MHz. At 13.5MHz we get 676 samples per 52µsec active line period. Increasing the clock frequency or omit-

ting the line blanking interval enables a greater number of samples to be taken. There's no fixed sampling rate. In some sets the sampling/write clock runs at 16MHz, but in all cases the read clock is twice as fast. The frequency depends mainly on the speed (access time) of the memory chips being used.

The U and V colour-difference signals are similarly AD converted. Because they can swing positively or negatively with respect to zero, their clamping point is at the centre line – see Fig. 6(b). Since the bandwidth of the colour-difference signals is only about a quarter of that of the luminance signal they require less frequent sampling and less memory

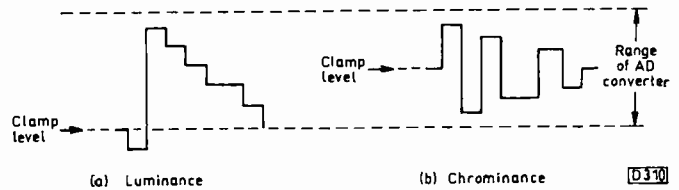


Fig. 6: Clamp points for (a) the luminance and (b) the U/V signals on their way to the AD converters.

capacity. In practice they are often sampled at the same 13.5MHz (or similar) clock rate, after which three in four samples are discarded by clocking the signals out of the

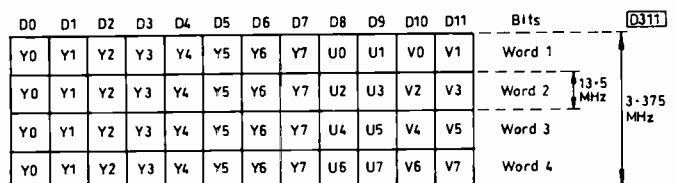


Fig. 7: Interleaving the Y, U and V data bits to produce the 12-bit words that are fed into the memory. The effective sampling rate for the Y signal is 13.5MHz, that for the U and V signals being 3.375MHz. This diagram depicts four Y samples and one each U and V samples, all with 8-bit resolution. The four words run in succession.

shift register at a quarter of the basic rate, i.e. 3.375MHz.

Thus for every eight-bit luminance byte there are two bits of U data and two bits of V data, complete U and V bytes being produced during the time taken for four luminance bytes. A complete YUV 'bundle' consists of twelve bits, with interleaved data streams – see Fig. 7. This bit interleaving is carried out by 'formatting logic' between the ADCs and the 12-bit memory-write register.

Memory Access

The AD conversion and memory-write clocks are controlled by the video signal's sync pulses. We must next see how a single memory bank can be simultaneously

written into and read from without tripping over itself as it were. Fig. 8 shows the principle, using a simple frame with only eight scanning lines. The write pointer, representing a sequential address generator, starts at point B1 in the broadcast field and feeds the eight lines of the field into the memory. At the start of this field the write and read pointers are both positioned at point A1/B1. They set off clockwise, the read pointer rotating at twice the speed of the write

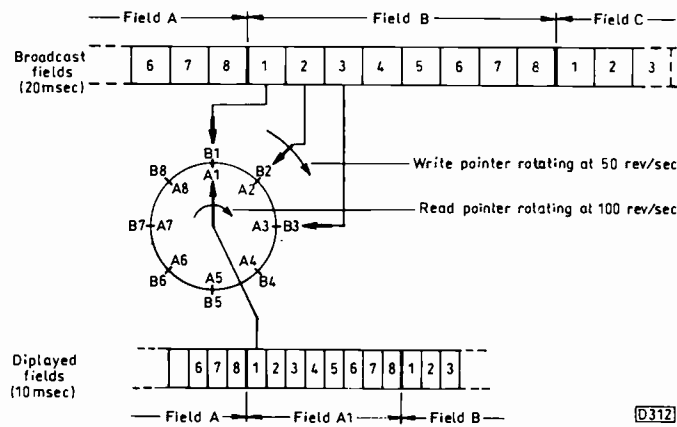


Fig. 8: Writing into and reading from the memory at different rates. The write and read pointers represent the operation of the addressing section of the memory-control chip.

pointer. At the end of read-out field A1 the read pointer has returned to position A1 while the write pointer has reached position B5. 10msec later the read pointer overtakes the write pointer at point A1/B1 to start the second read-out field (B) while the write pointer is inserting field C into the memory. The cycle is repeated continuously.

Memory Chips

The memory chips used are very fast DRAMs (dynamic random access memories) with sequential addressing. The 3Mbits capacity required usually consists of three 1Mbit

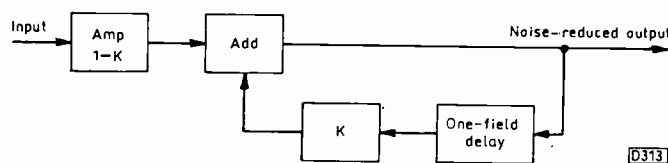


Fig. 9: Principle of noise reduction by integrating successive fields. Although shown simply here, in practice the process is a complex, digital one.

memory chips each arranged as 256K by four bits. They are connected in parallel, with one chip storing the four least significant bits, the second the four middle bits and the third the four most significant bits of the 12-bit time-multiplexed YUV data (Fig. 7).

There are several ways in which the memory system can be arranged: 8-bit Y data can be stored in its own 2Mbit (i.e. 2 x 4 bits x 256K) section while the 4-bit UV data is held separately in another 1Mbit chip; or three 2Mbit stores can be provided, one each for Y, U and V data, as in the Sony KV-FX29. While this latter system requires an expensive 6Mbits of memory it provides a YUV sampling ratio of 4:4:4 and full bandwidth in all three channels, which is

useful for RGB operation. With the 4:1:1 ratio scheme the RGB inputs have first to be filtered then matrixed to obtain YUV form and finally stored, being reconverted to RGB form after digital-to-analogue conversion in the 100Hz part of the circuitry. This is not as bad as it may sound: no encoding, modulation or interleaving is required, and with an RGB signal much of the information in the three channels is common to them all and is thus redundant.

Digital Noise Reduction

There are several causes of noise in an analogue video signal, amongst them weak signal reception and tape noise with VCR playback. Noise is random, with no correlation between successive video fields. With a still picture the video fields have total correlation. Thus if several video fields are integrated the noise cancels to virtually zero while the picture-signal components add. The integration can be carried out with the signal in analogue or digital form – or indeed using a photographic camera's film (take a one-second exposure of a noisy, stationary TV picture and see how, in the photograph, the noise has disappeared as if by magic!).

Electronic noise reduction can be carried out in a field-store TV set by progressive integration of the current and previous field. Fig. 9 shows the basic idea in block diagram form. The block marked K is a 'recursive filter' whose characteristic (K factor) determines the noise reduction as follows:

K factor	0	0.25	0.5	0.75
Noise reduction	0dB	2.2dB	4.8dB	8.5dB

The noise reduction requirements of the Y and U/V circuits differ: for U and V the optimum K factor is 50 per cent greater.

Unfortunately for noise reduction, most TV pictures don't stand still; and with picture features that move there's little or no time for successive integration. This is overcome by using the arrangement shown in Fig. 10, where a motion detector modifies the action (K factor) of the recursive filter in accordance with the rate of change of individual picture features, typically in eight steps between 0 and 1. The effect of this is that the longer an object in the picture remains still, the better and more noise free it appears.

With a single-memory TV set the noise-reduction circuit works digitally on a pixel-by-pixel basis at the 50Hz rate, using two memory data readout ports, one at 50Hz for noise reduction and one at 100Hz for the display as shown in Fig. 11. With a two-field memory noise reduction can be carried out at 100Hz: Fig. 12 shows the arrangement.

There is less definition loss with a digital noise reduction (DNR) system than with the analogue system described in

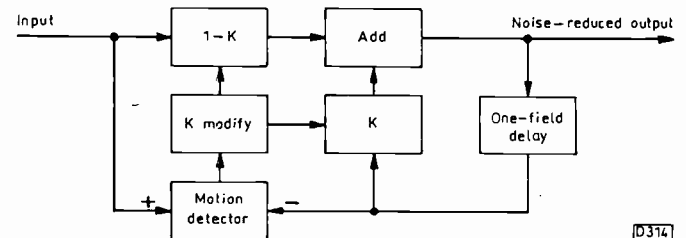


Fig. 10: To cater for movement in the picture a motion detector is used to reduce the K factor in proportion to the rate of change of individual pixels in successive fields.

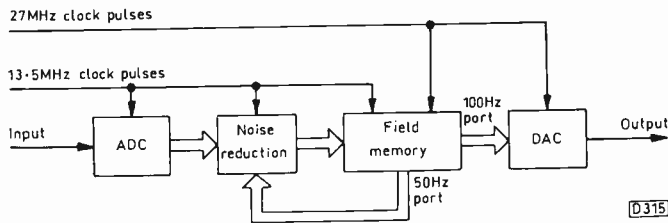


Fig. 11: Noise reduction with a single memory bank. The memory section has two readout ports, one operating at 50Hz for noise reduction and the other at 100Hz for the display.

Part 7 (page 624, July 1993). But provision is usually included for control of the digital noise reduction by the

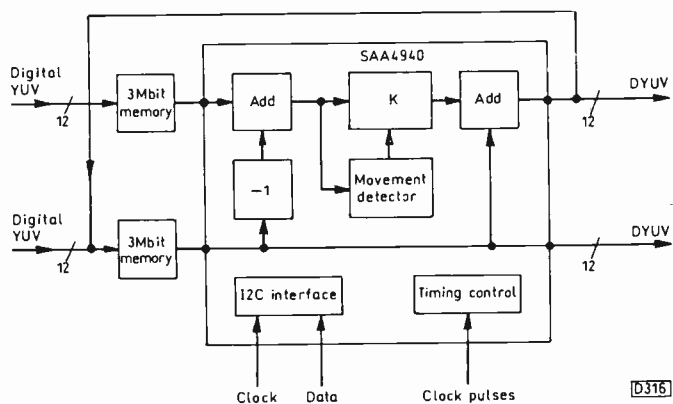


Fig. 12: 100Hz DNR using two separate memory banks.

viewer, in one or more stages – perhaps on an individual channel basis with the setting stored in the EEPROM and implemented by I2C bus control of the DNR chip.

Memory Readout

A memory controller chip governs the read and write processes and generates the sync pulses for the 100Hz/31-25kHz timebases. Fig. 13 shows in block diagram form a sophisticated system that has two sets of field memo-

ries, DNR at 100Hz, 4:4:4 ratio sampling and field and line flicker reduction. The sampling and read/write clock rates can be selected by the setmaker: this gives an idea of the chip set's flexibility. At the higher rates the definition is better than that called for by the CCIR standard, but all rates call for very short DRAM access times. If the time-constant of the VCO that controls the memory readout is long, the system takes on the characteristic of a timebase corrector (TBC) ironing out timing jitter. This will, for example, provide better off-tape picture stability. Plainly it's not possible to combine this with effective DNR because the pixels in successive fields are no longer time coincident.

Other features of the system shown in Fig. 13 are worth mentioning. The delay in the Y data stream is part of the bit interleaving/data formatting system that produces the 12-bit YUV words. The SAA4940 chip carries out noise and cross-colour reduction by recursive filtering. The next chip downstream, the SAA7158, implements the three-point median filtering described earlier for interline flicker removal. It also carries out U and V signal reformatting, digital colour transient improvement (similar in effect to the system described in Part 7) and Y signal peaking, and contains the cine-mode detector mentioned earlier and three high-speed DACs. Two additional features of this chip are called Zoom 1 and Zoom 2. The former provides vertical picture expansion so that 4:3 aspect ratio letterbox pictures can be displayed correctly on a 16:9 aspect ratio c.r.t. Zoom 2 gives magnification by two of the displayed picture, both horizontally and vertically, as a user feature. All the memory-control and post-memory processing functions can be software controlled via an I2C bus.

DA Conversion

Where necessary the data from the memory is de-interleaved to separate it into its Y, U and V components for application to three separate digital-to-analogue converters. Each of these works on the principle shown in Fig. 14. The first step is serial-to-parallel conversion: the 8-bit serial data words are stepped through a register by the bit-clock pulses at the memory-read rate, e.g. 27MHz. The eight bit words are loaded into a slave register at the byte clock pulse rate, thus making parallel data words available to the actual DAC. Each bit in the word being converted controls a two-

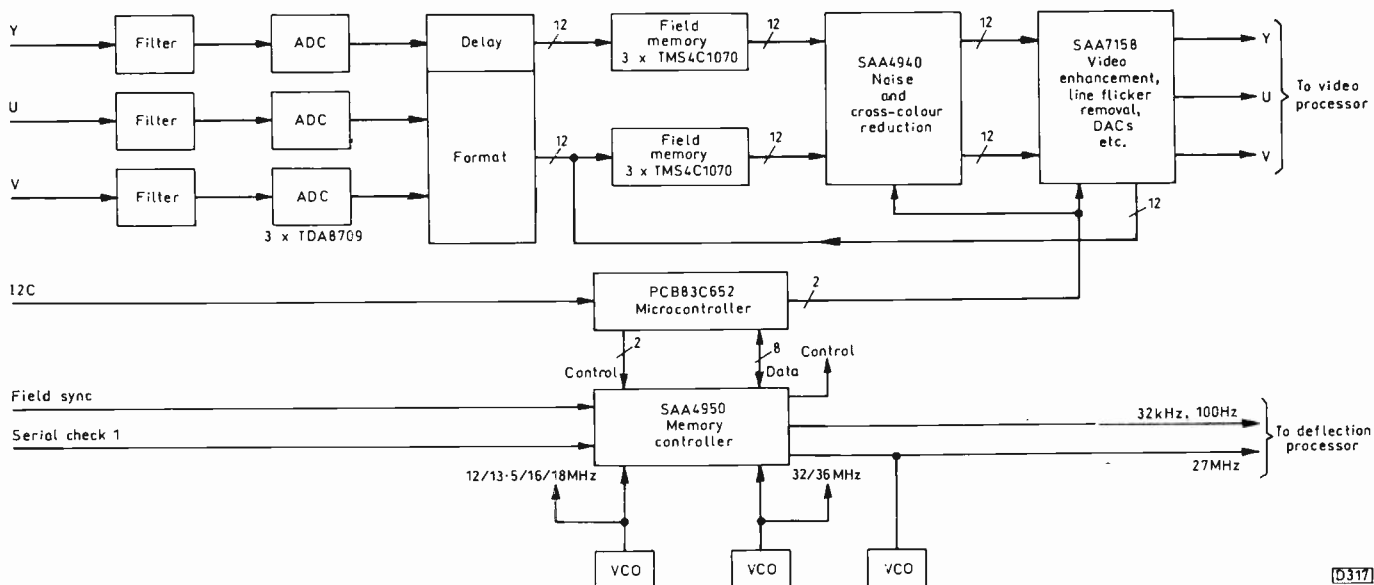


Fig. 13: A Philips full-feature, flicker-free processing system using 6Mbits of memory.

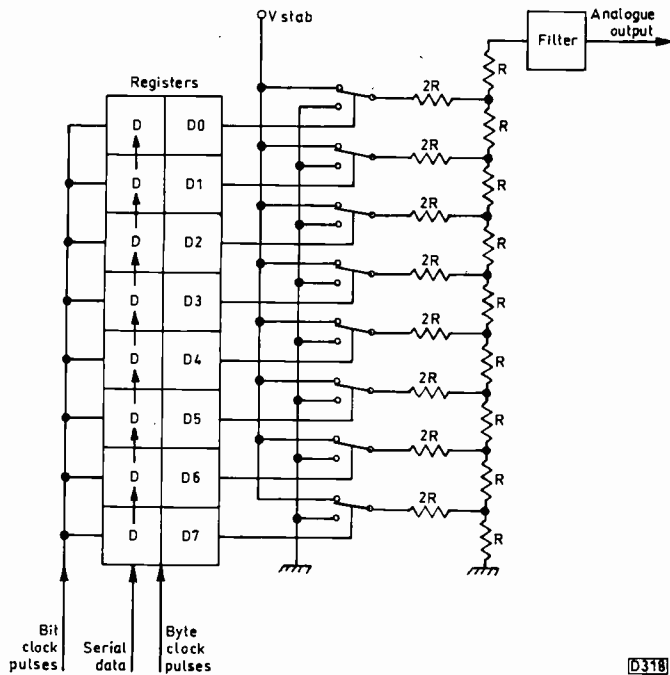


Fig. 14: Operating principle of an 8-bit DAC.

way switch connected to an R/2R ladder network with eight 'rungs'. The ladder has a fixed, closely regulated voltage across it. The effect of each bit in the word depends on the position of its switch along the resistive ladder. Thus the most significant bit (MSB) D0 at the top of the chain commands 50 per cent of the output voltage swing, the next significant bit D1 25 per cent and so on down to the least significant bit (LSB) which influences the output voltage by only 1/256th or 0.4 per cent.

A 256-step video signal waveform cannot be distinguished from a non-processed analogue video waveform by the human eye. The other advantage of 8-bit processing (you can get away with 6- or 7-bit quantisation) is that the noise introduced by the digital system is very low at -54dB - a low noise figure is essential for a high-quality, flicker-free TV picture.

DA conversion is followed by a sharp cut-off analogue filter (usually an LC type) that smooths out the quantisation steps and eliminates the remnants of the clock frequency. The Y signal filter cuts off sharply at about 12MHz. Since the frequency of the U and V signals is so much lower than the DAC clock rate their filter requirements are much less demanding. To capture all the picture detail the bandwidth of the analogue circuits that follow the Y converter and the RGB channels between the matrix and the c.r.t. must be around 12MHz.

Effects

In addition to the zoom features mentioned above various effects are possible in a TV set with a field store. The first and most obvious is a perfect freeze-frame facility: the memory writing process is halted while the 100Hz readout continues as long as the viewer requires. Other possibilities are pixelation, in which the DAC clock rate can be progressively slowed (in practice progressively halved) by the viewer to give the picture an increasingly mosaic-like appearance; and solarisation, where the two, three or four least significant bits of the 8-bit words are removed by clamping them at zero in the DAC. This reduces the number of analogue video signal levels, giving the displayed picture a surreal effect. While pixelation and solarisation are of

little practical consequence, a PIP (picture-in-picture) feature is rather more worthwhile.

PIP

Whether or not the set has a 100Hz display system, a PIP facility calls for a digital field store of sorts - it need not have the capacity of those used for full-screen processing. The basic idea is to decode the video signal from a second source into YUV form and then AD convert it, discarding two out of every three scanning lines and two out of every three video samples. The remaining data can provide, after DA conversion, only a coarse, liny picture with about eighty lines each of which carries typically 200 luminance pixels and 32 each U and V pixels. Converting the signal to 6-bit form calls for only 230Kbits of memory to store the necessary two fields; 300Kbits or so are required with 8-bit quantisation. The memory-write operation has to take place in real time, so each field store takes 20msec to fill. The readout can be much faster, with the lines of YUV information read out in about a third or a quarter of the time occupied by the original scanning lines, be they at 15.625kHz (conventional TV) or 31.25kHz (flicker-free).

If the PIP memory's 'fast' readout is geared to the display scanning rate and the input to the YUV-to-RGB matrix is switched to the PIP DAC's output whenever this is taking place, the auxiliary picture will be inserted into the main one at a point that's determined by the line and field phasing of the electronic PIP switch (in practice the memory control chip). The little picture is generally positioned in one corner of the screen. With a TV set the YUV outputs from the PIP section can go straight to the RGB matrix. With a VCR or video effects unit however the PIP picture must be restored to composite encoded form. This calls for the use of a colour (e.g. PAL) encoder that uses the main picture's colour subcarrier as the reference.

Fig. 15 shows in block diagram form a PIP processor for use with a 100Hz TV set. The secondary picture signal, in composite video form, is first fed to a TDA9140 colour decoder that produces YUV outputs. These are fed to a TDA8706 chip that contains a clamp, a triple analogue

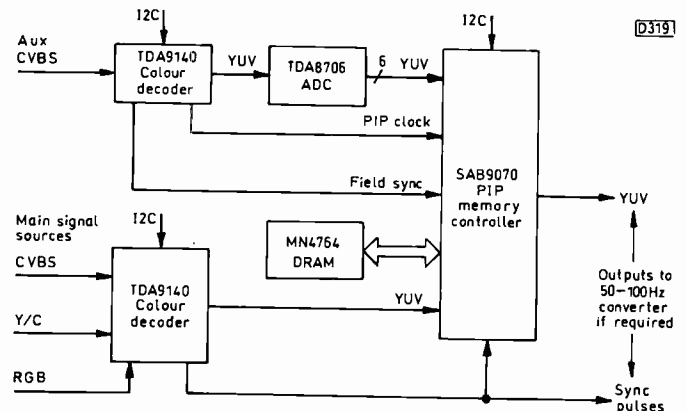


Fig. 15: PIP processing prior to the main scan-rate converter. A separate DRAM is used for storage and time-compression of the PIP data.

multiplexer and a single 6-bit ADC. The MN47464 DRAM that's used as the PIP memory is a 64K x 6-bit device that's governed by the SAB9070 PIP memory controller under 12C control.

Meanwhile the main picture signal, whether in composite video, Y/C or RGB form from a scart socket, is separately decoded, entering the memory controller chip in analogue

YUV form. Within this chip the reassembled, time-compressed PIP data is DA converted and inserted into the main picture signal. What emerges is the composite PIP/main picture, in analogue YUV form at the 50Hz field rate. It can be fed to a flicker-free processor.

The SAB9070 chip used in this particular arrangement has many built-in features. Amongst them are multistandard (PAL/SECAM/NTSC) capability, user control of the PIP contrast and saturation via the I2C bus, and luma key, pixelation and solarisation effects.

100Hz Teletext

In earlier 100Hz sets the RGB outputs from a conventional teletext decoder character generator chip had to be up-converted. There's now a teletext processor chip (type SAA9042) that generates output signals in 100Hz form for

feeding directly to the wideband RGB stages in a flicker-free TV design.

Similarly, chips have been developed to generate the 100Hz/32kHz timebase waveforms required. In principle they are no different from those described in Parts 10 and 12 of this series.

In Conclusion

Well, that's it! The present series has run for longer than any other one in this magazine and has gobbled up lots of pages. I hope that it has achieved its object and not been too difficult to digest. Maybe the next time that we undertake anything on this scale we will be concerned wholly with digital TV broadcasting and reception – with not a capacitor or coil in sight except maybe at the input to the tuner!

Help Wanted

The aim of the Help Wanted column is to assist readers who require a part, circuit etc. that's not generally available. Requests are published at the discretion of the editor. Send them to the editorial department – do not write to or phone the advertisement department about this feature.

Wanted: Manual/photocopy/info on the Custom Sound CS700A mixer amplifier. C. Faulkner, 10 Bryngoleu Avenue North, Holyhead, Gwynedd LL65 1AD. 0407 740 070.

Wanted: LOPT for the Sanyo CPT3131. M. Grant, J & M Electronics, Unit 16, Centenary Business Centre, Hammond Close, Attleborough Fields Industrial Estate, Nuneaton, Warks CV11 6RY. 0203 325 761.

Wanted: RGB module for the Huanyu 37C-3 (on tube base). Also first anode preset (RV831) for the Ferguson TX10 chassis. V. Jeremy, 7 Tai Penyard, Penyard, Merthyr Tydfil, Mid-Glamorgan CF47 0LP.

Wanted: Scrap or damaged JVC GRS505 camcorder with serviceable mechanism. Robert Scarfe, 2a, Portland Street, Norwich NR2 3LF. 0603 622 792.

Wanted: LOPT for the Binatone Model 01/9014 – the type with serial number ending CF82. E. Longton, 47/49 Back Victoria Street, Fleetwood, Lancs FY7 6EJ. 0253 778 338.

Wanted: Help with getting a Heathkit AOIU waveform generator to work (no sinewave output). J. Stephens, 108 Dudley Road, Grantham, Lincs NG31 9AB.

Wanted: Remote control unit for the Osume Model CTV1484R. Peter Ward, Petgra, Forest Corner, Ringwood, Hants BH24 3JW. 0425 475 445.

Wanted: Line output transformer for the Atari SM125 monitor. Harry Hughes, 16 Dalton Drive, Goose Green, Wigan, Lancs WN3 6TQ. 0942 824 417.

Wanted: 30M-P23 output pentode (B7G – 42 – base) for a Sony TC200 tape recorder. The 30A5 seems to be a near equivalent. Loan of a circuit diagram and user instructions for the Cossor CDU150 scope. A mains transformer for the EMI

RE301/E tape recorder. Gordon Madgwick, Thursdays, Whitmore Vale, Hindhead, Surrey GU26 6JA. 0428 604 942.

Wanted: Small panel with eight square buttons and six wires to one plug – behind the touch-button unit – for the Ferguson 20A2 (TX9 chassis). Whole unit would do. C.F. Walker, 3 Stevenson Place, Littleover, Derby DE23 7EX. 0332 772 460 (evenings).

Wanted: LOPT for the Hitachi Model 1455 and base connector 14157/3CC for an A51X427X tube. Donald Bills, 69 Greenfields Road, Kingswinford, DY6 8EG.

Wanted: Programming information for the Connexions CX8520R satellite receiver/positioner, especially V/H switching and a.f.c. offset. C. Thorne, 27 Edgcumbe Green, St. Austell, Cornwall PL25 5EE. 0726 67 585.

Wanted: Non-working but complete Toshiba V73B VCR. K.L. Skilton, 119 Mill Road, Burgess Hill, West Sussex RH15 8AY. 0444 235 086.

Wanted: Akai RC-V77A universal remote control unit. PCBs for the Akai VSA77 VCR (or complete machine). Remote control unit for the Sony C9. Dave Hodgkinson, 42 Victoria Avenue, Cliftonville, Margate, Kent CT9 2UB. 0843 297 276.

Wanted: Instructions for assembly and alignment of the tape loading gear in the Amstrad VCR4700. The manual doesn't help. L.P. Watkinson, Regent House, Week St. Mary, Holsworthy, Devon EX22 6UJ. 0288 84 254.

Wanted: NTSC video player, preferably Panasonic NVJ45 or a machine with similar specification. Duncan Werner, 4 Lea Crescent, Riddings Alfreton, Derby DE55 4AQ. 0773 602 601.

Wanted: Manual/circuit or any information on the Bradley Model 234 frequency counter/timer (1973 vintage). S.J. Sheppard, 12 Bedford Road, Harrow, Middx HA1 4LZ. 081 863 5150.

Wanted: Working power supply panel for the Akai VS25EK. Working mains bottom board for the ITT VR3905. Mains transformer for the Ferguson TX90 chassis. Keith M. Twamley, 25 Davena Drive, Weoley Castle, Birmingham B29 5UL.

What a Life!

Donald Bullock

I woke up early one morning. The sun was shining, the birds were singing and it felt good to be alive. Then I remembered that I was in TV/VCR repair, and that Walter Windpipe had called the night before, at half past ten, with a Samsung VCR.

"Sorry to call so late Mr. Bodger" he slurred. "I've had this in the car a couple of days and remembered it only when I left the, er, club. It's the wife's Sing-Song. Can't be much – it was all right before it seized up."

Walter's Sing-Song

When I got to the workshop I opened Walter's Sing-Song, an SI1260 that was quite new. Its carriage had jammed because the brittle plastic cog assembly had been stripped by the coarse-toothed metal slider that meshes with it. The two never did mesh well in this series of models. A look in the manual gave the part number as 65203-605-310, but it proved to be no longer available. The recommended replacement is part number 65203-605-330, which costs 63p. Samsung have a £3 minimum order charge so, in view of the potential business out there, we ordered six. The spares came quickly and we had the machine right in no time. I have to say that Sing-Song certainly try harder and their service people have always been good to us.

I've referred on previous occasions to a pair of troublesome diodes in this machine, D109 and D110, both type O54001. They go leaky or short-circuit. As a result the voltage on the 5V line falls, the consequences being loss of the E-E vision (the sound remains) and no drum or capstan drive. If they are only slightly leaky the symptom is intermittent cassette ejection. Specimens like Windpipe then force the carriage. So while we were at it we replaced these diodes with some tougher ones.

A Ferguson A51F

My first caller that day was Mrs. Simper. She swept in followed by a scruffy lad with a TV set in his arms.

"Put it down there" she ordered him. As he put it on the bench he knocked down our drawer of assorted screws. "You oaf" she said. He stood there blinking and I started to pick up the screws.

"Smokes" she said, "all the bloody time". I looked at the fellow. "Not him" she continued, "the set. He's a telly addict, not a smoker. Can't be much wrong with the set. Snoddies said it was a condenser and quoted a quid."

I straightened up. "Perhaps you should take it there then?" I suggested.

"They can't do 'em."

So I ended up with the set, which is fitted with the IKC2 chassis. This frightens me to death. When I plugged the set in it made three spirited attempts to start then smoke began to belch from beneath the line output transformer, close to the core. Like the ICC5 and ICC7, this chassis seems get through line output transformers – and they're not cheap. We paid up, got one, fitted it and to our relief the set worked.

When Mrs. Simper returned with her lad to collect the set we told her that the charge was £40. She looked at us with contempt and said to him "pick it up, you dummy – wish you

could make money like these people instead of watching telly all day."

While Mrs. Simper was attending to the payment he picked the set up, gave us a wink and made a disgusting sign behind her back.

The Philips K35 Chassis

Half an hour later I noticed that Steven was grunting and rubbing his eyes as he worked on a set. "What's up?" I asked.

"Partial field collapse with this K35 set of Rupert's" he said, "but the BD437/BD438 field output pair TS530/TS532 test perfectly after being removed."

"Nevertheless, try a new pair" I said. He did, and up came the picture.

"Aren't I clever?" I added. Then we stopped for our tea break. I made the tea – it's one job I can do well without having to use my tired brain. As we were finishing, two odd fellows came along in quick succession. One had tiny eyes and a permanent leer, the other looked like the hunchback of Notre Dame.

Strange Fellows

I'm Terence Stoaate" leered the first, "of Stoaate, Weasel and Fleecem, solicitors. I've a 20in. Ultra Model V2001 in the car. TX90 chassis, you know. I've made a note of the serial number. Can you get it out? – I have back trouble. It just groans."

That I understood. As I struggled in with the set Steven was accepting a Panasonic NVL20 VCR from the other man. "Call back this afternoon, Mr. Huckmore" he smiled.

"Er – how come the new confidence?" I asked.

"It's dead, no functions or display" he replied. "I think it'll be the 1µF, 400V electrolytic in the switch-mode power supply down to about 0.005µF." He was right.

I went to the house for some Asprins, then put Mr. Stoaate's set on the bench and opened it up. The chassis was immaculate. He'd been into it and removed every speck of dust. Some of the larger components had a red felt-pen spot on them. When I plugged the set in nothing happened apart from a groan from the speaker. I decided to make a few cold checks, but there was nothing obviously amiss. Steven boxed up the NVL20 then came over as I plugged the set in again. While he was peering at the chassis the line output transformer suddenly exploded, covering him with a sticky resin.

"What was it?" he asked when his ears had stopped ringing, "and how do I get all this off?"

"It's the first time I've had a line output transformer explode" I said. "Phone HRS for another – ask for a TX90 white spot."

When it arrived Steven got busy fitting it while I looked out the manual and linked the set to the mains supply via the variac. We connected a d.c. voltmeter across the h.t. line and turned the set-h.t. control to minimum. Then we wound up the set slowly, standing well back – me behind Steven. As the voltage rose the set pulsed two or three times and up came a raster. After plugging in an aerial we had a picture. It wasn't bad, except for the verticals on the right-hand side – they were wobbling and rippling. We tried to adjust the h.t. voltage, which was low, but the control had no effect. So we switched off quickly and checked around in the power supply/line output stage circuit. Sure enough the BD839 boost voltage regulator transistor TR107 was short-circuit. All was well when we fitted a replacement. We took care to set the h.t. correctly, boxed up the set and put it on soak test. Later we pronounced it fit.

Mr. Huckmore subsequently called to collect his NVL20. "Funny-looking chap that was here last time I came in" he said.

"So many are, Mr. Huckmore" I said.

As he departed Mr. Stoate came in.

"Odd cove that one" he commented.

"We seem to attract all the oddballs" I said, smiling thinly.

A Grundig CUC60

There was only one job left to be done that day, a Grundig

TV set fitted with the CUC60 chassis. Apparently there was occasional field collapse and "the line gets brighter and brighter".

"Shall I have a go at it or will you?" asked Steven.

"You have a go" I said.

The chassis has subpanels mounted on the main PCB. Steven pulled out the field timebase panel and checked D2758, a pretty little SKE2F diode. It was open-circuit. He fitted a new one, checked the panel for dry-joints and resoldered C2758 (100µF, 35V). "That'll put it right" he said. It did.

He was just lucky.

Test Case 378

Mr. Miles cursed his remote control zapper for the twentieth time that week. Stabbing irritably at the keys, and lining the unit up exactly with the front of the TV set, he at last got ITV. He was on his second new set of batteries this year. Later he arrived at the Test Case service department with his zapper in his hand. After fitting two new AAA cells we tested the handset with one of those magic mirrors and sent him on his way – with the advice that he might be buying stale batteries and that it was best to get them fresh from a shop with fast-moving stock.

It wasn't many weeks before Mr. Miles was back in service reception with the same problem. This time we kept the zapper for investigation and supplied a loan handset which, a subsequent phone call confirmed, worked perfectly. So the set (an Hitachi C2875TN as it happened) was all right and the problem was with the handset. It's similar to most modern types, with a matrixed keyboard, a single encoder/driver chip and a single transistor to drive the IR transmitting LED. Power is provided by a pair of series-connected AAA cells that supply 3V. It was here that Roger started to make his checks. The way we test these batteries is to connect them directly, but momentarily, across the probes of an Avo Model 8 switched to its 10A d.c. range. Both produced well over 1A and were thus perfectly well able to drive the circuit. To be doubly sure, we checked them in another handset. They worked perfectly.

By using a little photodiode gadget that plugs straight into the oscilloscope's Y input socket Roger was able to check directly the amplitude of the invisible IR output pulses. The faulty unit produced pulses that were of about half the amplitude of those provided by a known good handset at a similar range and angle. So there was no doubt that a problem existed, and it wasn't cleared by cleaning the front filter window. A set of brand new cells produced some improvement, but the pulses were still not up to the standard of those from the comparison handset. Roger next selected a replacement LED from a huge box of scrapped, polluted and broken zappers and fitted it to the problem unit. There was no perceptible improvement in the emission power. A new driver transistor made no difference either. Maybe the chip lacked drive power? An oscilloscope check showed that it saturated the driver transistor's base-emitter junction, and that the transistor, which acts purely as a switch, bottomed on each pulse – the reading across its collector and emitter leads was over 3V peak-peak, so the transistor was switching on and off hard and clean.

What else was there? The battery contacts were found to be free of corrosion, and the wires from them to the PCB were in good condition and firmly soldered at each end.

Time to do a current check. A known good zapper drew an imperceptible current in the quiescent state and over 20mA when transmitting. The faulty unit produced a strange result indeed. Off-load there was no measurable current consumption: when a key was pressed the Avo 8's needle read a mere 2.5mA. The IR light output virtually disappeared, the scope recording only a few random low-level pulses. With the meter disconnected the handset returned to its previous condition: correct but low-power code emission. The mains-driven bench power supply was next brought into operation. Its output was set to 3V with the croc-leads connected to the battery contacts. When the zapper was activated the power supply's built-in digital current meter flickered uncertainly, never registering more than 3-4mA. Once again the IR output had virtually disappeared.

What was happening here? This little bunch of electronics seemed to be breaking all the rules! In a flash of inspiration Roger realised what the cause of the trouble was, and had the handset working correctly a few minutes later. The solution? See page 579.

BACK COPIES

We have available a limited stock of the following back issues of Television:

1992 February, April, May, July, August, September, October, November and December

1993 January, February, April, May, June, July, August, September, October, November and December

1994 January, February, March, April and May

Copies are available at £2.75 each including postage. Send orders to:

Reed Business Publishing,
Television Back Issues,
Room L323,
Quadrant House,
The Quadrant,
Sutton,
Surrey SM2 5AS.

Make cheques/postal orders payable to Reed Business Publishing Ltd.

Servicing the Hantarex MTC9000 Monitor

Peter Hubbard

One industry that didn't seem to suffer much from the recession was games arcades. While some television engineers may not be familiar with the technology used on games logic boards, such things as monitors, power supplies, lamp and reel driver boards should be well within the scope of the average TV workshop.

The larger arcades employ their own engineers, who repair logic boards and keep the machines running but often prefer to leave the monitors with their nasty high voltages to someone else. Smaller arcades generally don't employ engineers at all. Both like to have repairs done locally, as this saves time and money. The postage and insurance costs for items returned to the supplier can easily double the cost of a repair. Sometimes the item won't work after so much travelling, so the process has to be repeated at further cost.

A wide range of monitors has been used in arcade games machines, but one of the most commonly encountered ones is the Hantarex MTC9000, the subject of this article. We'll consider first the equipment required if you propose to service these monitors

Equipment Required

Two items are essential, a 120V a.c. supply with a suitable plug to match the tiny power connector on this chassis, and a tube assembly. The monitors are difficult to remove from the machines, so you usually get just the chassis. I use a Hantarex chassis frame and tube from a discarded machine. Having the 120V transformer mounted on the baseplate where the chassis belongs adds stability by balancing the weight of the tube face. The transformer feeds a bridge rectifier on the PCB.

One other item that's sometimes missing from the chassis is the panel with the line and field timebase controls. It plugs into a socket on the main board, but can be used with an extension lead. This enables the panel to be mounted in the games cabinet, where you can make adjustments from the normal viewing position. Either make sure that the panel comes with the chassis or acquire a spare one – the monitor won't work without it.

Inputs

Don't overlook the fact that there's no video drive once the monitor has been disconnected from the logic board, so you'll not see a raster unless you either provide an input signal or advance the setting of the screen (first anode) control on the line output transformer until a raster appears. This is not as bad as it sounds (see set white procedure later, under RGB output stages).

RGB video input signals should be between 1V and 5V peak-to-peak; line and field sync, positive- or negative-going, either composite or separate, between 1.5V and 5V peak-to-peak. The ganged potentiometers P1 adjust the video input level (switches may be used in some versions) while switch SW4 caters for positive- or negative-going sync pulses.

Connections

The chassis has both 240V and 120V inputs. Ignore the 240V input, which is used to power the degaussing circuit, feeding your 120V supply to the inner pair of pins of the four on the power connector.

There are also two sockets for the deflection yoke plug. Either can be used – this arrangement allows the picture orientation to be changed to cater for different games formats.

The Power Supply

The output developed by the bridge rectifier is fed to a conventional series regulator circuit. It's always worthwhile carrying out a visual check for any obvious faults. If the 2AT input fuse F1 is well blackened it's likely that one or more of the bridge rectifier diodes D19/20/21/22 or the series regulator transistor TR20 is faulty. Type 1N4004 diodes make suitable replacements. The transistor is type TIPL762.

Another frequent and obvious fault is a swelling around the middle of the line output transformer, indicating that a replacement is required.

If all seems to be well, switch on and check for 130V at the link in the deflection yoke plug. If you get a reading of only about 18V here this usually means one of three things: the line output stage is drawing excessive current or TR20 is either open-circuit or held cut-off. In all cases the 330Ω, 30W resistor which is connected in parallel with TR20 and is mounted on the side of the chassis will be getting very hot. I've never found one of these resistors that has gone open-circuit, but they get very black and the silica falls out when they overheat. If you find that the resistor is in this condition it should be replaced to ensure future reliability.

TR20, an npn device with the input at its collector and the output at its emitter, is easy to check with a meter. If it is all right check the value of the 33kΩ, 0.5W resistor R110 – it has a habit of going high. Do this with the resistor out of circuit. If not you will get a false sense of security – R110 always has the right value in circuit!

Apart from this the power supply is very reliable. Note however that the two 16kΩ resistors R113 and R114 in the error-sensing network are 1% types: they must be of correct value to obtain an h.t. voltage of 130V – there's no manual h.t. adjustment.

The Line Output Stage

If the power supply is working but the h.t. is low, check the BU508A line output transistor TR15. If this device is o.k., check that only pins 5, 6 and 10 of the line output transformer TH2 are connected to chassis. The transformer has a habit of shorting between windings. If you get a reading from any of the other pins, carefully remove all the solder from pin 5 with solder braid and check for continuity between pins 1, 3 or 9 and pin 5. If there's a reading replace the transformer. The transformer pins are numbered clockwise from the gap when looking at the underside of the PCB.

No Line Drive

An h.t. voltage reading of between 60V and 90V usually

means that there is no line drive. Rectifier diode D18 (BYD33G) sometimes goes open-circuit: it's hidden between the line output transformer and the heatsink near TR20 and is very difficult to get at. The trick here is to switch off, then switch on while monitoring the voltage at pin 15 of the TDA2595 chip IC2. If there's no brief voltage rise from the kick-start circuit, suspect either the 12V zener diode ZD1 (ZPY12) or the 470µF, 16V electrolytic capacitor C16. If there is a rise, carefully remove all solder from pin 14 of the TDA1670A field timebase chip IC1 and try again. If you are lucky, the monitor will then come on with the proverbial white line across the screen. If not, get your long-nose pliers out and struggle with D18.

A rare cause of no line drive is operation of the over-voltage (X-ray) protection circuit. This operates as follows. A reference voltage obtained from the line output stage is fed via a resistor chain to pin 8 of the TDA2595 chip where it's compared with an internal reference voltage. If the e.h.t. is excessive, the line oscillator is inhibited. This state continues until the fault is rectified. The power has to be switched off to reset the protection circuit. The usual cause of excessive e.h.t. is a slightly leaky line output transistor (TR20). On one occasion R113 in the power supply proved to be the culprit (see previous note under the heading Power Supply).

No Field Output

Loss of field output is a common fault. The TDA1670A field timebase chip IC1 dies and sometimes, as mentioned above, takes the 26V supply with it.

RGB Output Stages

The only other regular faults we've had have been dry-joints on the tube base, usually around the RGB output stages. Sometimes one of the output transistors goes open-circuit. The BF459 is a suitable replacement.

To set the white level after working on the output stages, proceed as follows:

Remove any input signal then adjust the preset brightness control RV7, which is hidden inside the heatsink near a 2.2Ω, 17W resistor, for maximum brightness.

Set the black-level controls RV203 (red), RV204 (green) and RV205 (blue) to minimum (clockwise).

Reduce the brightness, using the G2 (screen/first anode) control on the line output transformer, until only the dominant colour shows.

Adjust the black-level controls for the best white.

The G2 potentiometer acts as the brightness control!

In Conclusion

As these monitors lead a hard life it's worthwhile, in the interests of increased reliability, changing any components that look tired. You will find the customer happy to pay to get his machine back earning its living – though he might do so with 50p pieces from the coin box!

Spares are available from Hantarex UK Ltd., Unit 7, 243 Kangley Bridge Road, Sydenham, London SE26 5BA (telephone 081 778 1414, fax 081 659 9348). Compatible line output transformers are available from CPC Ltd., Component House, Faraday Drive, Fulwood, Preston, Lancs PR2 4PP (0772 654 455).

Next Month in TELEVISION

BUILDING A PERSONAL COMPUTER

Next month David Botto presents a DIY PC building project. Why assemble a PC rather than buy one ready-made? There's money to be saved, so that a superior machine can be afforded; you become familiar with computer hardware and how it works; and there's the satisfaction of having built a powerful, top-quality computer that won't easily become outdated. Only leading brand parts are specified. This ensures maximum reliability and optimum ease of use. Close attention has nevertheless been given to the total cost.

NOTES ON THE SONY CCDF335

Keith T. Keeton provides a fault guide for the Sony CCDF335 camcorder.

A DOMESTIC MATV SYSTEM

Modern homes are often packed with electronics. Use of a common aerial system will provide improved signal quality and flexibility while reducing aerial/dish duplication. Ian Martin outlines the various possibilities, including dual-satellite systems, and describes best practice.

FERGUSON FAULT NOTES

A resume of faults that have been experienced with Ferguson TV and video equipment, including some official modifications.

TUNING SATELLITE RECEIVERS

A follow-up to Gordon McCrea's article in the May issue deals with the Nokia SAT1700 Mk. 2 and linking memory units to a PC to provide vastly extended storage capacity.

CD PLAYER REPAIRS

Les Austin on laser power adjustment and other servicing matters.

ORDER FORM

To.....
(Name of Newsagent)

Please reserve/deliver the July issue of TELEVISION (£2.20), on sale June 15th, and continue every month until further notice.

Name.....

Address.....

.....

Cable & Satellite '94

Ian Martin

This year's Cable and Satellite Show took place in the Grand Hall, Olympia on April 11-13th. As on previous occasions there was a record number of exhibitors and visitors. The show seems to have matured to become a more businesslike affair, with more solid information and equipment and fewer glossy presentations.

Satellite Channels

Most of the current satellite channels were represented, many on the large stands of the satellite operators. In addition some new channels were being introduced, including the Travel Channel which has already started to broadcast via Intelsat 601 and hopes to move to Astra later this year. Another new Astra broadcaster, the Chinese Channel, revealed that its transmissions are to be scrambled later this year, using Cryptovision. Decoders, developed in conjunction with Tandberg, will be available from Pace. The Children's Channel and rival Nickelodeon both had high-profile displays.

Over at the Eutelsat stand the programme schedule of the revamped NBC Superchannel was revealed, along with the schedules for MBC and the other operators. More new channels are promised at 13°E with the launch of a new Eutelsat Hot Bird later this year.

Digital radio was again being promoted by DMX. This service is currently available via Intelsat and many cable systems: Astra services, in conjunction with BSkyB, are promised by the end of the year. Music Choice revealed its plans for a fifty-channel Digital Satellite Radio service via Intelsat, again due to start this year. To enable the channels to share a single transponder, Dolby ADM digital compression will be used.

Information on the long-awaited Orion Atlantic satellite was released at the show. The plan is to launch the satellite this October, stationing it at 37.5°W. This mid-Atlantic position will suit simultaneous transmissions from Europe and the USA, mainly for news and commercial feeds. Transatlantic TV signals intended for cable distribution will use digital compression. Advanced services such as high-definition TV are also planned.

Satellite Receivers

As last year Pace had one of the largest stands, situated right inside the entrance. The centre-piece of the display was again the MSS1000 integrated receiver-decoder with a built-in Dolby Pro Logic decoder and a four-channel audio amplifier. Although this model has only recently become available variants are already appearing. The first is Model MSS500, a full-feature receiver with the same styling but without the Dolby and extra amplifier circuits. Two new 'basic' receivers are the MSS200, in versions with and without VideoCrypt, and the MSS300 which has a large fluorescent display to indicate the programme name and other information. The ever-popular PRD800 and PRD900 were on show in their new 'Plus' versions. All Pace Astra receivers are now 1D compatible, using the SES agreed 22kHz LNB switching signal. An add-on positioner panel for the MSS1000 was shown: it fits inside the receiver. I hope to test it in a follow-up review. A D2MAC/Eurocrypt SM module is to be made available later. It's not intended as an upgrade.

Amstrad showed a similarly-specified Dolby Pro Logic IRD with built-in four-channel amplifier. This sleek unit, the SRD2000, features dual 'enhanced wideband' i.f. inputs, a large fluorescent display and true Wegener Panda 1 sound de-emphasis. A non-VideoCrypt version, Model SRX2002, will also be available. More information is due to be released soon.

Amstrad showed a range of world satellite receivers on its stand and in a special 'enhanced wideband' brochure. They are aimed at the growing East European, Middle East and Far East markets. Enhanced wideband means an i.f. input range of 700-2,050MHz. This ensures that the receiver's front-end is suitable for Astra 1D reception whether it's used with a standard 10GHz LNB or an enhanced 9.75GHz type. The new UK Models SRD540 and SRD545 have this feature along with a 22kHz switching signal.

A new player in the UK satellite receiver market is Grundig, whose Select receivers are being made at Llantrisant in South Wales. There are three models, the GRD150, GRD250 and GRD350, the numbers indicating the programme presets available. All models have a low-threshold tuner (6dB or better), an integrated VideoCrypt decoder, on-screen displays and channel naming and Astra 1D compatibility. Model GRD250 will also be available in a stylish white- or wood-finish cabinet. A review of this receiver is also intended.

Cambridge showed its ARD200 series receivers, which have 200-position programme memories. The standard model has an integrated VideoCrypt decoder, a 2GHz i.f. input and on-screen displays. Model ARD200T also has the 22kHz switching signal necessary for Astra 1D switched LNBs while Model ARD200E has a VideoCrypt II decoder suitable for Filmnet via Astra transponder 63. Models ARD250 and ARD350 are similar but have larger programme memories.

Echostar's new SR5700 receiver has a built-in dish positioner and an optional VideoCrypt decoder. Its 2GHz i.f. input makes it suitable for use with an enhanced Astra LNB (for 1D) or a triple-band LNB (for multi-satellite reception). A D2MAC/Eurocrypt version is to be introduced. The popular Model SR70 receiver is to be replaced by the SR70 Plus, which again has a 2GHz tuner to add Astra 1D capability.

Other receiver manufacturers present at the show included Chaparral, Digital Vision, Drake, Maspro, Mimtec, Nokia, Palcom and Strong. There were many new offerings.

Aerials and Accessories

Satellite aerials from around the world were on show. Exhibitors included IRTE from Italy, Metsa from Mexico, DH Satellite from the USA and the local companies Channel Master and Lenson Heath. Lenson's 98cm dish, which I reviewed in a previous issue of *Television*, is now available with a new profile. This improves the phase response and is claimed to increase the gain by more than 1dB.

LNB makers included Cambridge, Continental Microwave and Chaparral. The latter had a new ultra wideband LNB that covers the whole Ku band.

Zeta, which is famous for its Clearial transparent dishes, unveiled some new products including the Dual card reader which enables one VideoCrypt card to be used with two decoders, the Select-A-Sat motorised LNB holder and the Megasound powered sub-woofer TV stand. The latter was

AC188	0.70	25A777	0.35	25D325	0.35	STK1050	7.25
AD161	0.50	25A841	0.40	25D355	0.45	STK2029	4.75
AD162	0.50	25A893	0.50	25D400	0.18	STK3042	4.20
BC108	0.07	25A1011	1.35	25D467	0.15	STK3042/2	4.75
BC141	0.30	25A1102	1.60	25D525	0.60	STK4191/5	18.50
BC142	0.20	25A1123	0.49	25D600	0.40	STK5325	4.45
BC307	0.08	25A1175	0.40	25D612	0.80	STK5332	1.80
BC337	0.07	25A1282	0.80	25D636	0.10	STK5422	4.20
BC546	0.07	25B1207	1.50	25D716	0.95	STK5475	4.00
BD131	0.30	25B242	0.40	25D725	3.50	STK7348	3.15
BD132	0.30	25B254	0.65	25D836	0.75	STK73410	1.00
BD243	0.38	25B541	1.90	25D856	0.55	STA401	3.50
BD246	0.65	25B546	0.55	25D1136	0.50	STA411	3.80
BOR33	0.50	25B618	3.05	25D1273	0.70	STA441	2.50
BOR34	0.50	25B641	0.11	25D1275	0.58	STRA41	4.75
BF197	0.20	25B649	0.38	25D1278	0.58	STR5412	4.40
BF259	0.70	25B717	0.52	25D1398	1.40	STR41090	5.90
BF494	0.16	25B866	1.50	25D1426	2.05	STR50041	6.40
BF681	0.30	25B1015	0.60	25D1441	3.50	TA7157	1.20
BFY51	0.80	25B1016	1.10	AN318	4.40	TA7270	2.00
BFY90	2.00	25C372	0.70	AN5011	3.50	TA7280	2.25
BU124	1.35	25C458	0.68	AN5512	1.35	TA7604	2.35
BU180	1.90	25C681	3.20	AN5521	1.35	TA8205	2.90
BU206	0.85	25C741	3.00	AN6367	3.90	TA8207	1.65
BU208	0.68	25C867	3.00	AN6673	2.25	TA8210	3.50
BU209A	0.70	25C941	0.12	AN7115	1.40	TA8214	3.40
BU407	0.65	25C998	3.05	BA318	1.75	TA8215	3.00
BU409	1.10	25C1008	0.20	BA658	3.60	UPC574	0.50
BU426	1.50	25C1103	0.50	BA1330	1.50	UPC1020	2.00
BUS08A	0.85	25C1123	0.45	BA5466	2.50	UPC1032	0.60
BUS08B	1.35	25C1222	0.11	BA6219	1.20	UPC1230	1.90
BUS08C	1.05	25C1327	0.78	HA1156	1.35	UPC1363C	1.50
BUS08D	1.35	25C1382	0.30	HA1377	1.40	UPC1378	1.80
BUS36	1.05	25C1429	0.55	HA11227	1.50	UPC1394	1.50
BUS36	1.45	25C1447	0.80	KA2101	1.00	UPC4556	0.90
BUS08AF	1.20	25C1514	0.42	KA265	1.00		
BUS08BF	1.35	25C1569	0.55	LA1352	1.45		
BUT11A	0.70	25C1674	0.16	LA1460	2.05		
BUT11AF	0.85	25C1767	0.36	LA182	1.55		
BUT12A	0.85	25C1815	0.12	LA4200	1.50	7305	0.20
BUT12AF	1.10	25C1859	0.49	LA4440	1.18	7906	0.20
BUT15A	0.90	25C1914	0.15	LA4460	1.30	7812	0.20
TIP30C	0.25	25C1953	0.50	LA7700	4.40	7815	0.20
TIP31A	0.25	25C2002	0.22	LA8274	1.90	7820	0.20
TIP32B	0.30	25C2027	2.20	LM118	1.15		
TIP41A	0.30	25C2076	1.10	LM723	0.45		
TIP47	0.45	25C2236	1.00	LM6402	5.25		
TIP110	0.45	25C2347	0.18	MS143P	1.40	13/00	3.20
TIP112	0.85	25C2500	0.25	MS220	1.75	13/00	3.20
TIP142	0.90	25C2579	1.25	MS1172	2.60	RI103	0.30
TIP191	1.30	25C2603	0.12	MS3864	4.50	RI151	0.30
TIP295	0.50	25C2658	0.10	MR3731	2.50	TC1050	0.40
MIE340	0.25	25C2688	0.30	MR3732	2.45		
MIE521	0.35	25C2838	3.00	MR3756	2.20		
2N2222	0.20	25C2979	2.00	MC127	0.55		
2N3035	1.10	25C3182	1.50	MC14475	2.50		
2N3773	1.50	25C3262	3.60	MC14493	0.50	IM4001	0.03
2N6130	0.40	25C3345	1.00	SA11293A	4.85	IM4007	0.03
2SA350	0.60	25C3506	3.40	SA11293-2	5.15	IM4008	0.10
2SA626	2.85	25C3883	2.80	SA11293-3	5.15	BY127	0.10
2SA679	1.95	25C4242	1.40	SA6510	4.95	BY133	0.10
2SA722	0.62	25D198	1.60	SA65243P-E	7.15	MR454	0.10
2SA748	0.85	25D2340	0.45	STK61	6.00	MR856	0.12

SPECIAL OFFERS

STARTS 16/5/94 – ENDS 15/6/94

- 1) Sony Switch 26mm remote grey 2 p/c at.....£4.50
- 2) Phillips VR6760 pinch roller assem.....£4.80 each
- 3) Sharp 005GE22 original idler£2.85 each
- 4) Video head puller.....£6.50 each
- 5) 3V29/HR7200 pinch roller 3 p/c.....£6.00
- 6) 3V35 capstan motor.....£24.50
- 7) TA8215H 2 p/c at.....£5.60
- 8) STK 463.....£7.25 each

NEW – NEW – NEW

Hey look time is money, if your workshop is computerised then ask for FREE evaluation disc with your next order on:

"WORKSHOP MANAGER PLUS"

Only available from us.

Ask for 1994 full catalogue

being demonstrated in use with a Pro Logic surround sound system. The company also has a range of TV sets with integrated satellite receivers. Screen sizes range from 21in. to 33in.

Flat-plate TV and f.m. radio aerials were a feature of the Maxview stand. These set-top units, along with amplifiers, splitters, outdoor aerials etc., are described in the company's booklet *A Guide to Terrestrial TV & FM Radio Broadcasting*. It contains useful information about r.f. distribution in the home, showing typical systems, and a UK map of the main transmitter locations.

Global Communications continued its Astra 1D ready philosophy with the ADX Astra 1D i.f. extender, TE4 top-end i.f. extender and HOPAD i.f. shifter modules. These will enable those with standard LNBs and unenhanced receivers to tune in the new channels when they become available.

One of the few freebies at the show was available from Tratec – the company's 'Waterlock' LNB connector cover. Hirshmann had another good protection idea: a dual-output Astra LNB with an outer, snap-over weatherproof box. One of the most unusual items advertised was the Perfect 10 satellite dish from the States: it's disguised as a boulder, being available in stone grey or brown!

Test equipment on show ranged from hand-held signal-strength meters and compasses to transmission quality generating and measuring equipment. At the latter end of the market, both Rohde and Schwarz and Tektronix showed impressive product ranges.

Dealers and Other Services

Eurosat and Satellite Solutions both displayed new catalogues and product ranges. BBC Engineering was offering

consultancy and uplink facilities. IDB Broadcast offered airtime and remote production. NTL demonstrated its video compression and uplink technology. Eldon Technology had a decoder which displayed an MPEG-originated digital video picture: the company considers that the MPEG compression system will be used with the Astra 1E satellite. Multichoice Developments was promoting the use of VideoCrypt II, for which it has exclusive rights.

The Confederation of Aerial Industries (CAI) invited companies to apply for membership: details of training courses, including SMATV installation, were available, also a range of technical publications. Servicing books and technical journals were available from U-View, 21st Century Publishing and WV (What Video) Publications.

Summary

Some 200 companies were present at the show: our apologies to the many we have not been able to mention here.

Forward planning for Astra 1D seemed to be the main aim of the satellite receiver manufacturers. The cable part of the show was larger than in previous years, with a greater emphasis on signal distribution and head-end equipment. Digital video compression for satellite transmissions, teleconferencing and video-on-demand is now a reality: many companies had related products and services on offer. There was almost no sign of MAC, PAL-Plus or wide-screen TV.

Such was the emphasis given to Astra 1D readiness that I feel it will soon be impossible to sell receivers without 64-programme (or more) memories, two smart-card slots and extended i.f. At any rate this should ensure a healthy demand for upgrade receivers and installations.

TV Fault Finding

*Reports from Philip Blundell, AMIEE,
John Edwards, Nick Beer,
Eugene Trundle, Brian Storm,
Chris Watton, Michael Drandfield,
Gordon Haigh and John Pitt-Francis*

Sony 27XRTU

There was no synchronisation with this set. A scope check showed that there was no video input at the sync separator (pin 5 of IC501). We traced back to the teletext board where the SAA5230 chip had no video output at pin 1. In addition the chip was overheating, as a result of which the 12V regulator Q002 had gone short-circuit. Replacing these two items restored the picture. **P.B.**

Grundig CUC3500 Chassis

For no sound or vision with the +C voltage low at 80V instead of 196V, check whether D635 (BAT86) has gone short-circuit. **P.B.**

Philips GR1-AX Chassis

There was no sound or raster. The 95V h.t. supply was present at the line output stage but there was no line drive. We found that the line drive stage was inactive as its supply was missing. Coil L5524 had gone open-circuit. **P.B.**

Toshiba 199R4B

If the symptoms are intermittent loss of the sound and vision, with just a whistling noise coming from within the set, check the pins of the line output transformer for poor contact with the print. **P.B.**

Sentra STX600

My next door neighbour's TV set went to one of my competitors because of field foldover. A week later they brought it back saying that they couldn't do it! The set was now dead. . . E.H.T was present, but there was no sound or vision and a squealing sound came from the power supply. I found that R448 (4.3 Ω , 1W fusible) was open-circuit while there was a short between the 11.7V line and chassis. Resistance checks enabled me to chase the cause of the short to the front end, where RV68 was leaning against the tuner's can. Bending RV68 away cleared the short, so R448 was replaced. The set now fired up but there was just snow on the screen and no sound. The 5V supply was missing because of a crack in the print leading to the emitter of Q805. I now had the original fault back, field foldover. C313 (2.2 μ F) was open-circuit. **P.B.**

Sony KV1612

If there's no sound or vision and the main supplies are all correct, check the 12V supply to the tuner. It's derived from the line output transformer and follows a complex path, via the surge limiter R811, the rectifier diode D811, connector D5, connector A12 (pin 1) and stabiliser transistor Q207. The most likely cause of the fault is that R811 (4.7 Ω) has gone open-circuit. **J.E.**

Matsui 2890/Saisho CM2880TX

This set was dead with no channel display. Checks showed

that there was no a.c. supply to the bridge rectifier as relay RY101 wasn't being energised by a low signal from pin 30 of the microcontroller chip IC103. This was hardly surprising as IC103's 5V supply (pin 52) was missing. It comes from the 5V regulator IC106 which was very hot. A resistance check showed that there was a short-circuit across the 5V line. The cause turned out to be the 5.6V zener diode D142, which is on the print side of the PCB, connected between pin 52 of IC103 and chassis. The set worked well once this item had been replaced. **J.E.**

Philips K35 Chassis

This set suffered from EW bowing because the 5 Ω resistor connected to the collector of transistor TS490 was open-circuit. The position of this resistor is marked as a link on the PCB, so it doesn't have a circuit reference number. It is easy to recognise however as it's mounted on long legs well clear of the PCB. We checked the associated transistors, found them to be o.k., then replaced the resistor. This restored a normal raster. **J.E.**

Toshiba 284T8B

This set would search for a channel correctly but wouldn't stop when a channel was found. Pin 9 of the microcontroller chip QA01 was receiving line sync pulses. The other requirement for it to recognise a station, a.f.t. pulses at pins 8 and 30, was not being met however. These pulses come from pins 2 and 4 of the tuner/i.f. module, which had to be replaced. A more common cause of this symptom is D172 (1N4148). When it's leaky it distorts the a.f.t. pulses. **J.E.**

Hitachi C14-P216 (G7P Mk 2 Chassis)

There was normal sound but only a grey raster with flyback lines and a white line from the top to the bottom of the screen, about half way between the left-hand side of the screen and screen centre. Fortunately when I opened the set up I noticed that C711 (47 μ F, 200V), which is near the line output transformer, was bulging and had leaked. It's the reservoir capacitor for the h.t. supply to the RGB output transistors. A new capacitor and board clean up cured the fault. **J.E.**

Ferguson TX9 Chassis (PC1040)

Because of low h.t. there was lack of height and width. Someone had simply turned the set-h.t. control RV185 to maximum and still hadn't got the correct voltage. The simple cause was that R186 (12k Ω) in the potential divider network had risen in value to 15k Ω .

There was also no colour. I found that the 470 Ω chroma delay balance preset RV67 was open-circuit. **N.B.**

Hitachi CPT1476R

This set wouldn't tune: there was a very low, fixed voltage at the tuner's tuning pin. The voltage rose and varied

slightly when tuner pin BT was disconnected, but the tuning still wasn't correct. Despite the fact that it measured perfectly when checked cold, resistor R1533 (39k Ω) on the remote-control PCB (PC279) was going open. It's in the tuning voltage filter circuit. **N.B.**

Panasonic TC1785 (Z3 Chassis)

There was a field scan fault with this set: the top of the raster was expanded while the bottom was compressed, but with no foldover. The cause was C458, which is listed in the manual as being 4.7 μ F, 50V but turned out to be 10 μ F, 50V. **N.B.**

Salora K Chassis

For the first ten seconds or so after switch-on there was a severe blanking fault: a large horizontal band was blanked from the picture. The band gradually shrank, leaving a normal picture. I had the feeling that this was a capacitor fault, and was right. When the super-sandcastle pulse was monitored I could see the blanked portion varying in size. Use of freezer soon narrowed the cause to C574, which is beside the field output chip. A new 100 μ F capacitor put matters right. **N.B.**

Solavox 141 (Nikkai TLG88/99 Chassis)

This set, which comes in many guises, was stuck in standby. A quick check showed that there was no start-up supply as R128 was open-circuit. The circuit diagram shows a single 150k Ω resistor, R110, in the start-up feed. There were two resistors here however, R110 and R128, both 82k Ω . To be on the safe side I replaced the pair. **N.B.**

Hitachi CPT2476

If you get one of these sets with a green or flashing-green picture, or with green fingers reaching out from the left-hand side of the screen, replace the caption/on-screen display generator chip. **E.T.**

Panasonic TX24T1 (Alpha 2 Chassis)

There was a text fault with this set. Initial checks showed that the channel flag was present and stable, but there were no bar graphs for colour, sound etc. When the set was switched to the teletext mix mode however a perfect text display was produced. As usual the cause of the trouble was a 10nF ceramic capacitor, this time C3526 which is connected to the base of Q3506 in the teletext contrast circuit. It was leaky. **B.S.**

Rediffusion/Doric Mk 4 Chassis

The customer complained that there was no on-screen channel display when either the recall or the programme button was pressed. In fact the display did appear, but then disappeared in the blink of an eye. As a new SAA1276 display generator chip made no difference we had to make a more detailed investigation. We found that 8C16 (1 μ F, 25V) in the timer section was open-circuit. It determines the time during which the display is visible. **C.W.**

ITT Digi 3 Chassis

A whistle could be heard and the channel indicator lit for a second or two, then the electronic fuse operated. We discon-

nected the scan coil plug, connected a 60W bulb between the 145V line (pin 4 of the scan coil plug) and chassis and switched on again. This confirmed that the power supply was working correctly. Checks in the line output stage then showed that there was a short-circuit across the -13V supply. Diode D547 (BA158), the TDA2170 field output chip IC401 and C548 (1,000 μ F, 16V) were all short-circuit. **C.W.**

Matsui 2190

We've had several faults with this model recently. No sound with R312 (330 Ω) burning up was simply due to one of the TDA2030 audio output chips, in this case IC302. Flat out brightness was the fault with another set: the supply to the RGB output stages comes via R613 which was open-circuit - it's in the line output stage.

Two power supply faults. C808 (1 μ F, 63V) was the cause of a fluctuating output. R810 (100 Ω) being open-circuit was the cause of a dead set. It's in the 12V supply to the TDA4601 chip once the start-up phase has been completed and runs quite hot. The correct replacement should be obtained and fitted. **C.W.**

Boots CTV14

There was no colour for the first ten minutes after which a very liny magenta cast appeared. If the channel was changed the picture would sometimes return to normal, with correct colour. On other channels there would be only a monochrome picture. The TDA3560 colour decoder chip and several electrolytic capacitors in this area were replaced, but this made no difference. Eventually we found that the chroma delay line was the cause of the trouble: resoldering the pins inside the case provided a complete cure. **C.W.**

Boots CTV10R/Nikkai Baby 10

The set was dead and a quick check at the output of the infamous potted regulator produced a reading of only 6.8V. Connecting an external 10.6V from the bench power supply still produced no results however, and on further investigation we found that the print between the regulator's output and its destination was open-circuit. When this was repaired the original regulator was found to be in order. These regulators produce a low output when unloaded. **C.W.**

Philips CP90 Chassis

There was a very bright line across the screen. Unusual these days, as field collapse usually causes blanking by upsetting the sandcastle pulses etc. In this case however the 8.2 Ω safety resistor R3623 in the 163V supply was open-circuit, removing the feed to the RGB output stages and the field output stage bias. It seems odd that the same resistor should be involved with both feeds, since its failure will produce uncontrolled maximum beam current and field collapse, with tube damage unless the set is switched off pretty quickly. **C.W.**

Hitachi CPT1444 (NP84CQ Chassis)

This 14in. portable was dead with the 800mA fuse FS903, which is on a little panel between the tuner and the power supply heatsink, open-circuit. We usually find that the cause of this is a short-circuit 2SD1453 line output transistor (Q703). Unfortunately there was also a hole in the line output transformer while Q902 (BU806), Q903 (BF422),

the 36V zener diode ZD901 and the LM317T regulator IC901 in the power supply were all short-circuit. When we got the set going we found that the tube's emission was low. **C.W.**

Sony KV2217

This set was stuck on channel 6, with no sound or picture. All the supplies were present and correct, the line output stage was working and the tube's heaters were alight. Checks in the control section at the top of the cabinet revealed that the volume minus button was short-circuit. Replacing this restored all functions. **C.W.**

Osaki P21H

This set had us fooled for a while. There was sound but no picture. We noticed that the c.r.t.'s heaters were not alight, but they had continuity. Perhaps a dry-joint somewhere? Still no luck. We disconnected pin 10 of the line output transformer, which provides the heater supply, but again there was continuity. Then the penny dropped – the line output stage wasn't working! The cause was simply a dry-joint at the line driver transformer EM115. The line output transformer is obviously not the main source of l.t. voltages in this non-remote set! **M.Dr.**

Matsui 1440A

A common fault with these sets is noisy volume, colour, brightness and contrast controls, though most customers only complain about uncontrollable sound. We've found that repeated application of switch cleaner fails to cure the problem. The best thing to do is to remove the whole potentiometer bank and dismantle each one in turn, cleaning the wiper and carbon track with a powerful solvent such as RS 554-153 1.1.1. trichloroethane. **M.Dr.**

Matsui 1455

If the set is dead with no output from the power supply, check the 180k Ω start-up resistors R903 and R904 first. If these are o.k. it's likely that either C613 (0.0047 μ F, 1kV) or C614 (0.0022 μ F, 1kV) is faulty. They are both small blue disc capacitors that are connected in parallel with the h.t. rectifier D607 on the secondary side of the chopper transformer.

For no luminance, another very common fault with this set, check the luminance emitter-follower Q202 (2SA562TM-Y). If this is o.k. it's likely that either Q407, Q408 (both type 2SC1815Y) or D417 (1N4148), which are behind the AV board, is faulty. As a quick check, for a picture to be produced Q408's collector voltage must be low at 0.13V. We've never had to replace the TA7698AP colour decoder/timebase generator chip IC202. **M.Dr.**

Samsung CI347FF

There was intermittent sound that often cut off completely. By panel probing we found that the faulty area was ahead of the a.f. transistors. We then had to remove the tin screen on the print side of the PCB. Resoldering IC101 and all other joints in this area cured the fault. **G.H.**

Ferguson TX100 Chassis (Non-remote)

This set tripped when the rotary brightness control was advanced. As the on/off switch had just been replaced I checked to see whether there was something amiss in this area. There was! The four rotary customer controls have

exceptionally long, bendable legs. Two of the brightness control's legs were touching. Separating them cured the fault, but it's easy to cause this sort of trouble by accidental mishandling in this area – it could happen to the volume, contrast or colour. **G.H.**

Saisho CM16R

This set was dead with the 2A fuse on the side unit blown. A visual check showed that C510 (1 μ F, 50V) was weeping electrolyte. After replacing this and the fuse the set worked all right.

The STK7305 regulator chip in these sets has a bad reputation for failure. Symptoms are standby indicator alight but set dead, set intermittently dead, bad power supply output fluctuations and D510 across the 103V rail going short-circuit. **G.H.**

Sony KV2756UB

There was no raster, just a black screen. The actual cause of the symptom was field collapse. A sticker on the back identified the set as being an RX chassis version, with discrete transistor field driver and output stages. I found that there was a spot burn on the 1.2 Ω resistor in series with D804, as a result of which it was open-circuit. A replacement held. D804 is fed from the line output transformer. **G.H.**

Matsui 2160

The power supply produced no outputs. We found that the five-legged STR58041 chip was faulty. **G.H.**

Matsui 1440A

We've had two of these sets with the same problem. They worked perfectly from cold, then tripped out after a minute. In both cases the STR50103A chopper chip IC501 was the culprit. We've also had the R2M over-voltage protection diode D508 cause tripping with this popular portable. **J.P-F.**

Ferguson TX10 Chassis

The cause of white spots on the picture and loud screeching on sound was traced to a hairline crack in the track leading from the earth point on the c.r.t. base PCB. **J.P-F.**

Akashi 1450/Etron EC142

This ageing portable out of the Network/Nikkai camp had failed during a thunderstorm. We found that the regulating thyristor Q811 was short-circuit. It happily accepted the TAG626 we fitted – it's slightly more rugged than the original SF8J41. **J.P-F.**

Hitachi CPT2216

There was a severe field linearity fault – stretching at the top and no scan at the bottom. The cause was traced to C614 (2.2 μ F), a blue tantalum! **J.P-F.**

Luxor 6159

Our customer asked us whether the tube was faulty. The focus had been poor since a previous repair. Good contrast and the focus potentiometer at one end gave the game away. The previous repairer had fitted the 20AX instead of the 30AX version of the e.h.t. tripler assembly! **J.P-F.**

Panasonic NVFV1

When powered up this laptop model would just spool and switch off. It's basically an NVM10 in a different box, with a 5in. LCD screen tacked on top. This led us to conclude that the M54543AL loading motor drive chip IC6005 was faulty. When a replacement was obtained and fitted the mechanism shuffled, the laptop stayed on and all things were bright and beautiful. **B.S.**

Sony TR75

This model is very similar to the TR45 and TR55 and is subject to similar faults. The following faults are additional to those listed on Model TR55 (see *Television* March 1994).

No E-E colour, playback o.k.: Replace IC201 on board VS72.

No playback, head rotating in reverse direction – all fuses may be blown: Replace d.c.-d.c. converter and fuses.

No playback or record colour: Signal o.k. at IC203 on board VS67, no voltage at pin 14 of IC204 (colour killer). Caused by faulty capacitor(s) – C352/3/4 – usually only one. Replace capacitors one at a time to find faulty one(s). **K.T.K.**

Mitsubishi HSC35B

The report with this S-VHS machine said "dead with no functions". The customer thought that it may have been connected to an "unsuitable power source"! Investigation showed that there had been a severe overload in the power supply, with IC902, Q904/5, Z800 etc. the worse for wear. Fortunately the power supply is not the usual unrepairable d.c.-d.c. converter. Also at the time of the repair Mitsubishi had available a replacement power supply at little more than the cost of the chip! One was obtained, fitted and set up as per the note that comes with the assembly. One other item had to be replaced, the CCP2E-25 circuit protector on the main VTR PCB. No other fault was evident, the power supply having taken the brunt of the overload. **D.C.W.**

Sanyo VMD6P

There were no functions and a tape was jammed in the mechanism. It's common for one or more of the loading drive gears to lose a tooth. Usually a replacement gear is all that's required. It's a straightforward job as gear failure doesn't upset the timing of the mechanism. **D.C.W.**

Fujix P600AF/Sony CCDV50

Playback was o.k. but there was no camera picture. The cause of the fault was the camera d.c.-d.c. converter being inoperative and fuselink PS901 open-circuit. **D.C.W.**

Panasonic NVMS90

When play or record was selected there was a 'wobbling' picture accompanied by a 'screeching' noise from within.

Thoughts of capstan motor failure (a flaking rotor) came to mind but the cure was much simpler. The cassette lid safety lever assembly had been fitted incorrectly and was fouling the top edge of the upper drum. Fortunately the drum hadn't been damaged, a quick refit of the offending part saving the day. **D.C.W.**

Canon E110E

Everything worked apart from the fact that the viewfinder picture disappeared almost before it arrived! Checks in the relevant circuitry proved inconclusive, though the problem was persistent. A new tube cured it. Just what was going on inside the old tube remains a mystery. **D.C.W.**

Sony CCDV50E

This middle-aged machine had lost its ability to record sound from the microphone or provide E-E sound. Playback audio was fine. The UPC4522 chip IC451 on the microphone amplifier PCB was faulty. A straightforward repair: the worst bit was getting to the PCB! **D.C.W.**

Hi-8 Tapes

The reported symptoms with a Sony CCDTR705E Hi-8 palmcorder were "intermittent 'screeching' noises from the mechanism and 'wobble' on the playback picture". We've noticed these symptoms on several occasions with certain brands of Hi-8 tapes. Only ME tapes produce this effect, MP tapes performing correctly in both the Hi-8 and the 8 mode. The fact that the machine was a Sony model was not relevant to the condition. **D.C.W.**

Panasonic NVM10

Complete failure of these full-sized VHS machines to operate is often caused by a loading drive problem. Not this time! The main 2A fuse was open-circuit, indicating that a heavy overload had occurred. Indeed a near short-circuit could be measured across the main 12V line. The only thing for it was an unplugging session to try to establish the location of the fault. Eventually (it's always the last one you try, isn't it?) we arrived at the hi-fi audio PCB, where C4542, a 68µF, 16V electrolytic, had leaked. As a result there had been arcing between its pins. After removing the faulty item and cleaning the electrolyte from the PCB we had to carry out a little surgery to save the slightly charred board. A replacement capacitor and fuse (VSF6059) completed the repair, restoring the machine to its former glory. **D.C.W.**

Sony CCDTR705E

The viewfinder picture was intermittent because the cable was damaged. Abrasion had been caused by the bracket assembly that swivels as the viewfinder is moved. A new cable and removal of a burr at the edge of the bracket put matters right. It might be worth checking this when one of these models comes in for service. **D.C.W.**

Long-distance Television

Roger Bunney

Conditions during march and at the time of writing this in early April have continued to be very poor, with few signals. By the time that this is being read the Sporadic E season should have started and we can then hope for something better. My extensive Band I monitoring over the Easter period produced virtually a blank. The dismal SpE log for March is as follows:

8/3/94	TVE (Spain) ch. E3.
9/3/94	DR (Denmark) E3.
13/3/94	TVE E2.
19/3/94	RAI (Italy) IA; DR E3; TVE E3.
20/3/94	NRK (Norway) E2.
27/3/94	TVE E3; DR E3.

Low-level tropospheric signals from Spain were received on the 8th, on channels E5, 34 and 37. And that's about it!

Bandula Gunasekera reports from Sri Lanka that interference to reception of the Ekran satellite's Asianet u.h.f. programming is being experienced from terrestrial ch. E56 transmissions.

A new edition of my *TV-DXers Handbook*, long out of print, is due to be published by Babani in mid-summer. Amongst other things the satellite section has been enlarged and rewritten.

Satellite Sightings

It could be worth checking frequencies near to that of the MTV transponder (11.658GHz V) on Eutelsat II F1 at 13°E: we understand that NTL may be carrying out video compression tests at adjacent frequencies.

Eutelsat I F4 at 25.5°E has been brought back to life with CNNI taking a lease on the 11.093GHz H transponder. As an east spot beam is used, reception in the UK is weak. This seems to be a temporary measure following the loss of the Turksat satellite. While checking at 25.5°E, try tuning to 10.978GHz and 11.011GHz H for ITN news feeds. These are prime spots to monitor for late news. Another place to look is at 16°E, where Sky News has been using the 12.537GHz V transponder aboard Eutelsat II F3.

Several readers have commented on sports material from

the USA via Intelsat K at 21.5°W. The signals are normally clear, though many are in NTSC form. Best checks are at 11.499GHz H (NTV), 11.532GHz V and 11.559GHz V (both Reuters). From time to time an originating OB or sat linking company may insert an identification in the field blanking interval. An example of this occurred on March 15th when the Key Biscayne tennis finals were being transmitted via the Atlantic Express transponder (11.017GHz H) aboard Intelsat 601 at 27.5°W: the NTSC signal carried the clearly visible identification 'Crawford Truck'. CNNI sometimes uses this technique for OB links.

While Maurice Hillier (Salisbury) was checking Italian election night offerings on March 28th he received via Eutelsat II F3 at 16°E a splendid caption with coloured globe and the lettering 'test transmission' for 'World Tamil Television' (see below). No further information on the signal source has come to light so far.

March 14th produced 'EBU MOGADISHU NEWS-FORCE 1 625 PAL'. I've no idea who or what Newsforce 1 is: can anyone help?

News Items

Band III: Public network operators have requested that the use of the remaining Band III PMR sub-band channels be reviewed, the idea being to gain new regional licences in London, Manchester and Birmingham along with additional channels for general PMR use. New Band III and upper u.h.f. (854-862MHz) radio-microphone frequencies have been announced. The Band III channels are 191.9, 199.7, 203, 208.3 and 216.1MHz with e.r.p. levels of 10mW for handheld and 50mW for body-worn apparatus.


Czech Republic: A 2.5GHz microwave distribution (MMDS) system is to be started in Prague this September, with sixteen channels. Five will carry Czech material and the others satellite feeds.

Hungary: New regional commercial TV licences are being issued, covering the main towns including Budapest. Up to ten franchises will be available in the capital, including MMDS channels.

Cyprus: Since early May the Nicosia based Pay-TV channel Lumiere has extended its services, at u.h.f., to Famagusta, Limassol and Larnaca.

Finland: The YLE TV1 service is now on-air 24 hours a day with either programmes or test patterns. YLE TV2/3/4 services vary, generally starting at 0900.

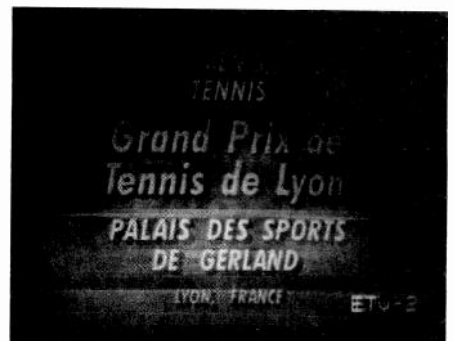Australia: Robert Copeman, 10 Cratloe Road, Mount Waverley, Victoria, Australia 3149 has formed the International Correspondence TV/FM DX Club (ICDX), with an informal news letter called Crossfire. Anyone interested should write to Roger directly: the club is mainly intended for Australasian enthusiasts though others farther afield will



Left: World Tamil Television on test via Eutelsat II F3 at 16°E, photograph from Maurice Hillier (Salisbury). Centre: BBC World Service news being broadcast via the Sri Lankan ETV-1 service, channel E31. Right: Prime Sports via Sri Lanka ETV-2, channels E35/56. Sri Lanka TV photographs from Bandula Gunasekera.

also be welcome to join.

MMDS: There is increasing MMDS activity in the 2.5GHz band, particularly in Ireland and central Europe. We would be interested in hearing from anyone with experience of DX reception at such high frequencies. In the USA the maximum MMDS range is reckoned to be about 35 miles, subject to terrain/obstructions and transmitted power.

Satellite News

Good news for satellite enthusiasts across Africa/Central Asia/Australasia. PanAmSat has changed the specification for PAS-4, which is due to be put into orbit at 68/72°E in mid-1995. It will have sixteen 54MHz bandwidth C band transponders and, for Ku band, sixteen 27MHz bandwidth and eight 54MHz bandwidth transponders.

Sony has developed a video compression standard, called SPEG, which is claimed to be an improvement on MPEG-2. It's described as being "broadcaster friendly", offers compression ratios up to 20:1 with digital component signals and should be ready by mid-1995.

The four Spanish TV channels (Canal +, Tele 5, Antena 3 and TVE) which will be transmitted via the Hispasat craft from the autumn are to use the Canal Plus type of encryption, allowing Canal Plus viewers simply to add an extra dish to their existing equipment.

The Russian GAL-S satellite is now in orbit at 44°E – test pictures have already been seen in Germany. It's to provide a six-channel Ku band DBS service for the CIS area, starting next year. GAL series satellites will have in-orbit stabilisation and an expected life of at least five years – relatively short.

GloboStar Satellite Communication Systems (CIS) is to launch three Coupon satellites giving world-wide coverage. Coupon-1 is due up in October this year, at 55°E. Coupon-2 will follow in April 1995 at 9.5°W and Coupon-3 in October 1995 at 162°E. The satellites will have transponders in the 3.7-4.18GHz, 11.096-11.2GHz and 11.46-11.7GHz bands. DTH services will have e.i.r.p.s up to 50dBW, those for broadcaster use (SNG etc.) up to 38dBW (for 1m and 1.5-2m dishes respectively).

More on Knife-edge Refraction

Knife-edge refraction (KER), or Mountain Bending, a form of propagation that allows reception of distant v.h.f. signals across paths with mid-point obstructions such as mountains, has been discussed in the last two columns. Robert Cooper (ZL4AAA, New Zealand) has sent us several papers that cover the theory and practice of KER at great depth, also his own observations and notes on his experience of the phenomenon. It seems that for UK readers KER remains something to talk about rather than see, though those in Wales/Scotland could experience the effect – if so, please let us know.

KER was first confirmed in 1950 by a radio amateur at Tanana, Alaska: he regularly received, at consistent signal levels, an Anchorage 100MHz f.m. broadcasting transmitter some 420km distant over an obstructed path. An IRE paper in 1955 confirmed KER, with the startling observation that the signal path via KER could achieve a signal gain of up to 25dB at the receiving zone as a result of the focusing action of the refraction. For KER to work there must be a line-of-sight (LOS) path from the transmitter to the mountain top and from there to the receiver. Thus if the obstruction is some gigantic peak the potential KER distance increases considerably. An example is amateur ZL3TY in Greymouth, NZ (100m a.s.l.) who receives signals from the ZL4NQ(-1) packet repeater (2,286m a.s.l.) some 356km distant, the signals being consistent with little fading. Mount Cook (3,764m a.s.l.) some

NEW PRODUCTS




Kansai TVR51K 21" Multi-system Colour TV

Aerial Techniques brings you two new products to complement our already extensive range

- "Personal Preference" memory function – (Volume, Colour, Brightness, Contrast and Hue)
- 5-System. PAL-B/G, PAL-D/K, PAL-1, SECAM B/G, SECAM D/K and NTSC 3.58/4.43
- Infrared Remote Control
- 90 Preset Channels
- Automatic Tuning
- On Screen Display – Volume, Colour, Brightness, Contrast, Hue and Channel
- EURO-AV (SCART) Socket
- Sound Muting Function
- Presettable Off Timer (15-120 Minutes)
- Automatic Power Off Function – when no broadcasting signal is received within 10 minutes
- Full VHF/UHF Coverage
- Cable Tuner
- Single or Dual Digital Control

£269.00

COMING SHORTLY

Exclusive to Aerial Techniques, new enthusiasts manually tuned DXing satellite receiver. Features variable video bandwidth 8 – 26MHz via front control for extreme weak signal work. SAE for details.

Grundig GV469M

Multi-system video recording and playback in PAL/MESECAM, SECAM L (for FRANCE), NTSC 3.58/4.43 MHz

- ▷ Tuner reception: B/G, 1, D/K, K1, M, L, L. 48 channels can be memorised.
- ▷ NICAM HiFi. ▷ 6 Heads
- ▷ On Screen Display
- ▷ On Screen user menu guide in 3 languages
- ▷ High Speed Drive Mechanism, approximately 2 min to rewind E180 tape
- ▷ On screen programming, timer can be programmed for 8 events in 31 days.
- ▷ Infra-red remote control for operation of all major VCR functions plus selected TV functions (TV functions may not operate all Grundig TV models)
- ▷ Auto Head Cleaner
- ▷ Digital Auto Tracking
- ▷ Long Play Operation 8 hour recording time with 4 hour tape. Super long play in NTSC mode, 6 hours recording with T120 2 hour tape
- ▷ One Touch Recording (OTR) in 30 minute steps up to a maximum of 4 hours
- ▷ Automatic Program Finder (VISS) index search system searches up to 20 recordings forwards or reverse.
- ▷ Assemble editing
- ▷ Daily/Weekly recording mode
- ▷ Multifunction display
- ▷ Connections: Rear 2 Euroscart sockets Front Phono AV sockets
- ▷ Dimensions: 43.5x8.9x30cm
- ▷ Mains Voltage 90V to 240V AC

£629.00

(All prices are inclusive of Vat, Carriage & Insurance delivery £9.00 on large items). Full range of satellite equipment supplied.

Our CATALOGUE at £1 samples some but not all that we can supply, send for your copy today. UK & overseas despatch normally ex stock within 24 hours, we'll accept the usual credit cards, cash, cheques. POs – as convenient. Ring daytime with your query or late on our 24 hr 'phone or send in your fax and we'll get back to you shortly.



11 Kent Road, Parkstone, Poole, Dorset BH12 2EH
Tel: 0202 738232 Fax: 0202 716951

155km south of ZL3TY provides the refraction.

KER propagation can occur at v.h.f. and u.h.f. The more sharply defined the ridge, the more likely it is that there will be usable signal refraction. Bare mountains, i.e. without trees etc., provide the best refraction: snow covering reduces the effect and foliage is a further detraction. The mountain peak should be perpendicular to the signal path, with the thinner sides facing the transmitter and receiver sites. A rounded mountain peak gives less efficient refraction. It's interesting that the actual refracting edge can be small, perhaps a few wavelengths long relative to the incident signal. It seems that gain may increase with frequency – good news for u.h.f. signals! An 80km path can produce a signal lift of 25dB, a 250km path a gain of 80dB, relative to normally propagated signals without the obstruction.

During his travels across Northland, North Island Robert has carried out many KER experiments. Extensive KER reception is possible in the North Island, both TV (u.h.f. and v.h.f.) and v.h.f. f.m. radio. Auckland f.m. radio and TV broadcasts can be reliably received several 100km away, some u.h.f. TV signals being present at quite spectacular signal strengths. By marking the focus points on maps and co-relating to larger-scale ones Robert found that dual-hop refraction sometimes occurs, with two mountain peaks/ridges in the signal path. For optimum exploitation of KER signals the receiving aerial needs to be clear of 'ground clutter', which varies with frequency – not unlike a form of ducting that can be experienced with tropospheric propagation via long signal paths.

I've quoted extensively from Robert's notes and appreciate his help in providing information on this unusual mode of signal propagation.

ECONOMIC DEVICES 32 TEMPLE STREET, WOLVERHAMPTON, WV2 4AN

15/80H	3.83	ZSC1398	0.80	ZSD401	3.46	BAX14	0.28	BD189	0.48	BF870	0.23	BYV96D	0.27	LM393N	1.19	SDA2112	11.80	TA7122BP	0.63	TD41170N	1.30	TD49503	2.13
15/85R	3.84	ZSC1413A	2.70	ZSD438	0.34	BB1058	0.24	BD190	0.31	BF959	0.10	BYW56	0.46	M1921C	1.86	SG264A	10.62	TA7146P	1.70	TD41170S	1.16	TEA1002	4.98
17052	3.85	ZSC1509	0.72	ZSD476	0.97	BC107B	0.20	BD201	0.40	BF960	0.27	BY55600	0.20	M21C	1.65	SG613	10.79	TA7176P	7.70	TD41190Z	4.08	TEA1009	1.61
17053	2.38	ZSC1520	0.54	ZSD525	1.27	BC108	0.15	BD203	0.46	BF966	0.61	CA3109E	0.70	M293	14.83	SGSF344	0.83	TA7193AP	6.77	TD41200	0.91	TEA1014	1.87
17088	2.38	ZSC1573	0.36	ZSD551	3.58	BC109A	0.16	BD232	0.45	BF970	0.38	CA309A	3.06	M490	15.30	SKE4F104	0.87	TA7193P	7.09	TD41200	1.79	TEA1039	2.15
17089	3.39	ZSC1573Q	0.26	ZSD613	0.94	BC109B	0.15	BD234	0.30	BF939	0.43	CD4001	0.21	M491	7.94	SKE4F210	0.87	TA7205AP	1.68	TD41412	0.77	TEA2018A	1.40
17127	1.77	ZSC1675	0.09	ZSD636	0.19	BC117	0.14	BD237	0.34	BF941	0.44	CD4011	0.21	M50115AP	3.24	SKE5F310	1.68	TA7207P	1.68	TD41506	4.59	TEA2164	2.68
1M4001	0.84	ZSC1685	0.21	ZSD637	0.16	BC139	0.33	BD238	0.24	BF990	0.71	CD4013	0.34	M51102L	1.77	SL1430	1.57	TA7210P	1.50	TD41510	3.40	TEA2165	6.26
1M4002	0.07	ZSC1740	0.12	ZSD667	0.39	BC140	0.33	BD239	0.29	BF990A	0.66	CD4016	0.16	M51231P	2.83	SL1431	1.70	TA7214P	3.74	TD41512	3.17	TC1060	0.82
1M4003	0.05	ZSC1741	0.17	ZSD669	0.63	BC141	0.34	BD241	0.41	BF991	0.60	CD4021	0.43	M51393AP	4.84	SL1432	0.54	TA7217AP	1.37	TD41515A	2.54	TC106M	0.75
1M4004	0.07	ZSC1815	0.17	ZSD669A	0.63	BC147A	0.06	BD243	0.39	BF996	0.53	CD4052	0.29	M51515L	2.81	SL471	1.70	TA7222	1.68	TD41516Q	3.56	TC45	0.59
1M4005	0.09	ZSC1826	1.70	ZSD716	1.46	BC148	0.12	BD243A	0.43	BF992A	0.48	CD4053	0.39	M51521L	1.54	SL490	2.64	TA7222AP	1.87	TD41518Q	3.32	TC65	0.52
1M4006	0.06	ZSC1827	1.00	ZSD718	2.21	BC148A	0.06	BD243C	0.44	BFX85	0.55	CD4066	0.30	M521.8L	0.59	SN29754AN	1.99	TA7227P	2.29	TD41670A	2.81	TP110	0.76
1M4007	0.06	ZSC1845	0.26	ZSD734	0.24	BC148B	0.04	BD244A	0.34	BFY50	0.34	CD4069	0.17	M5231L	0.55	SN7474AN	0.98	TA7230P	1.80	TD41701	3.67	TP12H	0.31
1M4148	0.04	ZSC1846	0.51	ZSD762	1.78	BC149	0.04	BD244C	0.42	BFY51	0.34	CD4070	0.21	M53216P	2.70	SN76013ND	7.99	TA7233P	1.85	TD41870	3.37	TP12H	0.58
1M4448	0.06	ZSC1923	0.14	ZSD774	1.15	BC149C	0.04	BD245C	0.92	BR100	0.27	CRK2A	3.83	MS4543L	1.97	SN76227N	1.87	TA7240P	2.46	TD41904	1.21	TP120	0.57
1M5061	0.38	ZSC1942	3.57	ZSD787E	0.46	BC157	0.13	BD246C	0.97	BR101	1.15	CRK2M	3.44	MS4544L	2.41	SN76666N	2.28	TA7241	2.30	TD41905	1.27	TP121	0.42
1M5402	0.12	ZSC1959	0.11	ZSD837	0.90	BC159	0.06	BD278A	0.56	BR103	0.53	CRD2AM	2.17	MS4548L	4.95	SN76705AN	1.70	TA7250	2.02	TD41940	2.77	TP132	0.46
1M5404	0.13	ZSC1969	2.46	ZSD841	1.45	BC161	0.27	BD317	1.20	BR303	1.22	CV12E	4.49	MS4644BL	3.30	STA311M	2.54	TA7267P	1.00	TD41950	3.42	TP126	0.48
1M5406	0.12	ZSC1983	1.87	ZSD856	1.83	BC167	0.42	BD318	1.29	BR444	1.82	DX10910	7.05	MS4648L	6.87	STA401	4.10	TA7270P	1.95	TD42002	0.85	TP295	0.83
1M5408	0.12	ZSC2001	0.22	ZSD869	5.10	BC171B	0.30	BD380	0.34	BRYS6	0.30	BRYS6	0.13	MS4898AP	20.45	STA441C	2.80	TA7271P	2.65	TD42004	1.44	TP29C	0.30
1M914	0.04	ZSC2073	0.77	ZSD870	3.81	BC177	0.14	BD433	0.29	BS338	0.33	DTA144EF	0.17	MS8485P	5.95	STK0029	12.84	TA7273P	3.84	TD42005	1.44	TP29E	0.46
1S1555	0.24	ZSC2078	0.85	ZSD871	5.08	BC178	0.25	BD4348	0.34	BT120	1.28	ER1400	6.45	MB3730	2.38	STK0039	7.11	TA7273P	2.72	TD42006	1.06	TP3055	0.94
1S2076	0.28	ZSC2141	1.48	ZSD880	0.48	BC182L	0.06	BD435	0.38	BT129	4.38	HA11235	1.95	MB3731	2.88	STK0040	7.48	TA7274P	2.69	TD42009	2.29	TP30C	0.37
2M2219A	0.27	ZSC2166	1.27	ZSD882	0.43	BC182LB	0.06	BD436	0.32	BT139600	1.87	HA11244	5.04	MB3732	3.85	STK0059	9.75	TA7280	2.63	TD42020	3.72	TP31A	0.12
2M2222	0.22	ZSC2168	0.85	ZSD898	7.70	BC184	0.09	BD437	0.32	BT151500R	1.10	HA1124A	0.98	MC13002P	7.69	STK025	10.58	TA7313AP	0.62	TD42030H	1.94	TP31B	0.30
2M2905	0.21	ZSC2236	0.36	ZSD904	5.95	BC184L	0.06	BD438	0.31	BT151800	1.15	HA11423	2.81	MC1310P	0.85	STK042	7.19	TA7313AP	0.62	TD42030V	1.05	TP31C	0.44
2M2926G	0.37	ZSC2271	0.36	ZSD973	0.38	BC184LC	0.10	BD441	0.18	BU205	1.87	HA11440	3.46	MC1327AP	1.62	STK062	0.88	TA7317P	0.83	TD42170	3.81	TP32A	0.39
2M3053	0.36	ZSC2274	0.31	7AL500	0.21	BC204	0.14	BD442	0.29	BU208A	1.44	HA1166X	3.43	MC1330AP	1.82	STK1131	7.79	TA7325P	1.83	TD42170	3.81	TP32C	0.38
2M3054	0.98	ZSC2274K	0.31	7805	0.49	BC207B	0.23	BD510	1.34	BU208D	1.36	HA11713	2.12	MC1350P	1.82	STK141	12.46	TA7343AP	0.72	TD42270	3.03	TP32Z	0.39
2M3055	0.86	ZSC2314	0.33	7808	0.51	BC212B	0.06	BD529	1.81	BU326A	1.61	HA11741	0.48	MC1352P	1.45	STK142	0.21	TA7358P	0.88	TD42530	4.24	TP33A	0.92
2M3442	1.00	ZSC2335	1.43	7812	0.30	BC212L	0.06	BD530	1.10	BU406	0.68	HA11745	5.49	MC1358P	1.59	STK162M	9.51	TA7358P	0.70	TD42540	1.12	TP33C	0.80
2M3702	0.11	ZSC2458	0.12	7815	0.82	BC213	0.11	BD535	0.40	BU406D	1.82	HA13001	1.89	MC14528BCP	3.56	STK171	13.20	TA7670AP	2.43	TD42541	1.10	TP34C	0.89
2M3704	0.14	ZSC2482	0.34	7818	0.41	BC214L	0.09	BD536	0.48	BU407	0.57	HA13108	3.56	MDA2062	1.70	STK1811	15.97	TA7699P	2.99	TD42560	4.81	TP41A	0.38
2M3773	1.27	ZSC2547E	0.24	7905	0.34	BC237	0.10	BD675	0.30	BU407D	0.83	HA13118	1.87	MDA2062	3.89	STK1811	12.46	TA7630P	1.87	TD42576A	5.95	TP41C	0.43
2M3819	0.55	ZSC2565	0.81	7912	0.43	BC237B	0.08	BD677	0.32	BU426E	0.06	HA13119	2.83	MD29550	0.97	STK332	5.38	TA7640AP	0.68	TD42577A	4.25	TP42A	0.42
2M3904	1.12	ZSC2570A	0.29	AN119	0.36	BC238	0.11	BD707	0.51	BU426E	2.13	HA13403	5.80	MD802	2.37	STK352	1.70	TA7676P	4.25	TD4258A	2.55	TP42C	0.43
2M4444	3.22	ZSC2577	9.99	AN143	0.13	BC238B	0.05	BD839	0.68	BU500	2.80	HA1377	0.85	MU13005	0.85	STK437	10.58	TA7680AP	4.58	TD42581	7.52	TP47	0.51
2M6292	0.62	ZSC2581	3.95	AC127	0.11	BC239	0.04	BD901	0.51	BU508A	0.95	HA1388	2.52	MU2955	0.88	STK4392	5.92	TA7698AP	5.93	TD42581Q	14.54	TP491A	1.14
2SA1015	0.10	ZSC2632	0.43	AC114K	0.46	BC252B	0.07	BD902	0.51	BU508AF	1.37	HA1389	2.83	MU3055	0.61	STK441	14.43	TA7705P	1.58	TD42582	1.95	TS43	0.99
2SA1016	0.26	ZSC2655	0.31	AC176K	0.38	BC300	0.48	BD911	0.41	BU508D	1.27	HA1392	1.81	MU923	0.50	STK459	11.17	TA7769P	3.81	TD42591	2.27	TL011CP	1.36
2SA1020	0.43	ZSC2671	0.58	AC187	0.16	BC301	0.28	BD912	0.32	BU508DF	1.87	HA1397	2.83	MC14528	14.76	STK461	12.29	TA8205	3.09	TD42593	0.75	TL071CP	0.38
2SA1020Y	0.43	ZSC2688	0.52	AC187K	0.33	BC302	0.36	BD913	0.26	BU508Y	1.16	HA1398	2.33	MN1405VKF	14.58	STK4843	15.46	TA8210H	4.74	TD42594	2.21	TL494	1.61
2SA1095	7.44	ZSC2785	0.36	AC188	0.36	BC303	0.22	BD944C	1.29	BU526	1.81	HA1452	4.80	MN1435VK	14.35	STK5211	15.78	TA8215	4.57	TD42595	3.19	TMP47C432AP	11.24
2SA1102	2.54	ZSC2791	5.44	AC188K	0.82	BC307	0.06	BD993C	0.59	BU536	1.80	HM6232	10.46	MN1435VXB	10.86	STK5322	0.35	TA8691N	7.81	TD42600	5.38		
2SA1143	0.17	ZSC3150	1.53	AD149	0.52	BC307A	0.06	BD994C	0.59	BU508	1.44	HM6251	0.52	HM650	3.23	STK5325	58.15	TA8626	1.35	TD42611A	0.84	TMP47C432AP	11.24

SPECIAL OFFERS - ENDS 30/05/94 OR WHILE STOCKS LAST

BU208A x 5	3.99	TDA 3654 x 2	2.50
BU 426A x 5	3.75	TDA 4601 x 2	2.55
BU 508A x 5	3.60	STANDARD VIDEO SENSOR LAMP x10	2.50
BU 508AF x 5	5.00	STANDARD VIDEO SENSOR LAMP	
BUT 11AF x 5	3.25	PLUG x:10	4.00
TV FAULT FINDING GUIDE	9.99	VTE ETC. BELT KIT x5	5.50
VIDEO FAULT FINDING GUIDE	9.99	3V29 ETC. BELT KIT x 5	4.50
SATELLITE FAULT FINDING GUIDE	14.95	3V35 ETC. BELT KIT x 5	4.25
CO AXIAL AERIAL PLUGS x 25	3.75		

ZSA1175	0.25	ZSC3153	2.37	AD161	1.82	BC307B	0.06	BDX32	1.70	BU705	1.81	HM7103	10.44	MPSA42	0.23	STK5326	0.76	TBA120	0.53	TD42611AQ	2.57	3555	17.87
ZSA1186	7.20	ZSC3156	6.61	AD162	0.96	BC308	0.11	BDY20	2.13	BU806	0.82	ICH281	0.26	MPSA56	0.12	STK5331	2.31	TBA120AS	0.90	TD42640	4.13	UC3844	4.19
ZSA1208	0.34	ZSC3182	2.49	AF124	0.77	BC308A	0.09	BF115	0.41	BU806A	0.80	K2101	0.83	MPSA93	0.80	STK5332	2.90	TBA120S	0.89	TD42652	14.32	UP81C	1.12
ZSA1265	2.96	ZSC3225	0.																				

Part No.	Price	3-Y-57	Part No.	Price	3-Y-57
AWVA					
Video Head	VD 2546	£15.34	Video Head	VD 2573	£14.00
Pinch Roller	VD 1755	£3.03	Pinch Roller	VD 1757	£3.15
Belt Kit	VD 1519	£2.00	Belt Kit	VD 1540	£2.00
Idler Replacement Set	VD 1001	£2.00	Clutch Mechanism	VD 1083	£15.00
Idler	VD 1005	£2.12	Capstan Motor	VD 2188	£45.00
Capstan Motor	VD 2160	£25.00	Loading Motor	VD 2167	£14.11
Tension Band	VD 1423	£3.05	Front Loading Motor	VD 1961	£1.50
Reel Table Rubber Tyre	VD 1335	£1.19	Cassette LED	VD 1388	£2.12
CTL Unit	VD 2637	£11.56	Repair Kit	VD 1315	£21.00
			Cassette Housing	VD 1315	£21.00
Video Head	VD 2546	£15.34	PV-100		
Pinch Roller	VD 1755	£3.03	Video Head	VD 2580	£18.73
Belt Kit	VD 1519	£2.00	Pinch Roller	VD 1817	£5.50
Idler Replacement Set	VD 1001	£2.00	Belt Kit	VD 1564	£3.81
Idler	VD 1005	£2.12	Idler Arm	VD 1097	£2.18
Capstan Motor	VD 2160	£25.00	Reel Motor	VD 2193	£16.24
Tension Band	VD 1423	£3.05	Capstan Motor	VD 2190	£24.72
Reel Table Rubber Tyre	VD 1335	£1.19	Loading Motor	VD 2412	£8.37
CTL Unit	VD 2637	£11.56	Front Loading Motor	VD 1961	£1.50
			Cassette LED	VD 1388	£2.12
			Tension Band	VD 1315	£21.00
			Repair Kit	VD 1315	£21.00
AKAI			PV-12L		
VS-8000			Video Head	VD 2581	£20.00
Video Head	VD 2511	£16.74	Pinch Roller	VD 1757	£3.15
Pinch Roller	VD 1756	£3.23	Belt Kit	VD 1564	£3.81
Belt Kit	VD 1506	£1.70	Idler	VD 1091	£3.10
Take Up Idler	VD 1025	£5.27	Idler Arm	VD 2193	£16.24
Reel Motor	VD 1026	£6.71	Capstan Motor	VD 2412	£8.37
FF Rubber Tyre	VD 1029	£0.85	Front Loading Motor	VD 1961	£1.50
FF Rubber Tyre	VD 1030	£0.85	Cassette LED	VD 1386	£0.85
Unloading Idler	VD 1207	£0.83	Repair Kit	VD 1315	£21.00
Rubber Tyre	VD 1207	£0.83			
Capstan Motor	VD 2120	£28.20			
Capstan Motor	VD 2120	£28.20			
Capstan Motor	VD 2120	£28.20			
Cassette Lamp	VD 1943	£0.35			
Tension Band	VD 1391	£1.85			
Repair Kit	VD 1391	£15.27			
Take Up Rubber Tyre	VD 1026	£0.84			
ALBA			PV-12L		
VCR-6000			Video Head	VD 2502	£15.51
Video Head	VD 2713	£16.30	Pinch Roller	VD 1758	£3.15
Pinch Roller	VD 1756	£3.23	Belt Kit	VD 1564	£3.81
Belt Kit	VD 1506	£1.70	Idler	VD 1091	£3.10
Idler	VD 1049	£3.44	Idler Arm	VD 2193	£16.24
Cassette LED	VD 1981	£1.53	Capstan Motor	VD 2412	£8.37
Tension Band	VD 1399	£2.04	Front Loading Motor	VD 1961	£1.50
			Cassette LED	VD 1386	£0.85
			Repair Kit	VD 1315	£21.00
AMSTRAD			PV-12L		
VCR-6000			Video Head	VD 2558	£44.82
Video Head	VD 2676	£13.77	Pinch Roller	VD 1803	£3.82
Pinch Roller	VD 1758	£3.15	Idler	VD 1096	£2.46
Belt Kit	VD 1592	£1.75	Tension Band	VD 1431	£4.85
Idler	VD 1049	£3.44	Remote Control	IR 9034	£14.52
Cassette LED	VD 1981	£1.53	Repair Kit	VD 1390	£12.56
Tension Band	VD 1399	£2.04			
AMSTRAD			PV-12L		
VCR-6000			Video Head	VD 2558	£44.82
Video Head	VD 2676	£13.77	Pinch Roller	VD 1803	£3.82
Pinch Roller	VD 1758	£3.15	Idler	VD 1096	£2.46
Belt Kit	VD 1592	£1.75	Tension Band	VD 1431	£4.85
Idler	VD 1049	£3.44	Remote Control	IR 9034	£14.52
Cassette LED	VD 1981	£1.53	Repair Kit	VD 1390	£12.56
Tension Band	VD 1399	£2.04			
AMSTRAD			PV-12L		
VCR-6000			Video Head	VD 2558	£44.82
Video Head	VD 2676	£13.77	Pinch Roller	VD 1803	£3.82
Pinch Roller	VD 1758	£3.15	Idler	VD 1096	£2.46
Belt Kit	VD 1592	£1.75	Tension Band	VD 1431	£4.85
Idler	VD 1049	£3.44	Remote Control	IR 9034	£14.52
Cassette LED	VD 1981	£1.53	Repair Kit	VD 1390	£12.56
Tension Band	VD 1399	£2.04			
AMSTRAD			PV-12L		
VCR-6000			Video Head	VD 2558	£44.82
Video Head	VD 2676	£13.77	Pinch Roller	VD 1803	£3.82
Pinch Roller	VD 1758	£3.15	Idler	VD 1096	£2.46
Belt Kit	VD 1592	£1.75	Tension Band	VD 1431	£4.85
Idler	VD 1049	£3.44	Remote Control	IR 9034	£14.52
Cassette LED	VD 1981	£1.53	Repair Kit	VD 1390	£12.56
Tension Band	VD 1399	£2.04			
AMSTRAD			PV-12L		
VCR-6000			Video Head	VD 2558	£44.82
Video Head	VD 2676	£13.77	Pinch Roller	VD 1803	£3.82
Pinch Roller	VD 1758	£3.15	Idler	VD 1096	£2.46
Belt Kit	VD 1592	£1.75	Tension Band	VD 1431	£4.85
Idler					

VCR Clinic

**Reports from Eugene Trundle,
Colin McCormick, Ian Rees, Della Verita,
Gerald Smith, Keith Evans,
Graham Richards, Ronnie Boag
and David Belmont**

JVC HRD560

Fast forward and rewind were painfully slow – an E180 tape took over thirty minutes! Throughout this time the tape remained fully laced with the drum rotating. The cause of the fault was failure of the supply reel spool rotation sensing optocoupler, circuit reference PS2. In addition it's a good idea to change the slider mode switch and ensure that the new type of main cam is fitted – this can be identified by its black colour. **E.T.**

Hitachi VT520

We've recently had three of these VCRs in which the capstan motor would stop momentarily every few seconds when the machine had been in operation for between thirty minutes and an hour. In each case the motor-mounted coil-drive chip was too hot to touch and a new capstan motor had to be fitted. **E.T.**

Sanyo VHR4350

Unreliable cassette front loading has been the trouble with several of these VCRs we've had in. With an afflicted machine there's an even chance that a proffered tape will be drawn in then spat out again. The usual cause is simple: loss of tension in the two finger springs that hold the cassette firmly in the front-loading cradle. **E.T.**

Tatung VR8530

About every third time this Akai-based machine was asked to play or record it would lace up then shut down, with the head drum trembling and throbbing on the spot instead of rotating. There were very strange waveforms at pins 8 and 9 of the on-board drive chip (type BA6413) at all times, and even when it did get started the drum motor took a long time to run up to speed. The chip may or may not have been faulty. Since it's not listed separately as a spare a new stator assembly, including the coils, chip, Hall sensors, etc., had to be obtained and fitted. **E.T.**

Saisho VR1100

Intermittent E-E audio was the problem with this very tatty example of the VR1100. When I connected an external audio input I found that the machine switched the audio source to external while leaving the tuner as the video source. In the camera position the tuner-camera switch provides a high output to the audio switching chip: in the tuner position it provides a high output to the video circuitry. It was actually supplying a drifting voltage to the audio circuit as a result of liquid spillage on the front PCB. **C.McC.**

Sony SLC20

This smart Beta machine intermittently destroyed the tape when ejecting a cassette. A chattering noise accompanied this. Once a tape has been loaded, the machine stays laced: so it was clear that when the fault occurred unlacing was not being completed before cassette ejection. The first suspect for this sort of thing is, with many machines, the reel idler.

But as the reel idler in the SLC20 is of the gear type, the friction to swing it from side to side being provided by internal magnets, I did not initially suspect it. Repeated operation of the mechanism however showed that very occasionally the idler failed to meet the supply spool for rewind during the unlace operation. Presumably the magnets had become weak – a new reel idler cured the fault. As the one supplied was different from the original, I added a spacer on the shaft so that it wouldn't collide with other deck parts. Strangely, Sony call the reel idler an 'arm block assembly pendulum'! **C.McC.**

Ferguson FV31R

For no or unstable playback check whether the insulating washer beneath the head of the screw that secures the top PCB is missing. If it is, tracks short-circuit to chassis. **I.R.**

JVC HRD700EK

If one of these machines comes in dead, check whether R1 (10Ω fusible) beneath the mains transformer is open-circuit. **I.R.**

Ferguson FV32L

There was irregular jumping between the LP and SP modes and finally the machine creased a tape. It had already received attention from someone who had resoldered several connections on the servo PCB. After a bit more resoldering around the capstan chips the machine seemed to work all right. But after an hour I gave the board a push and the fault returned. This time I was able to localise the source of the fault to the area around the LM393 capstan speed comparator chip IT45. Checks here showed that there was a jumping voltage at pin 2. When a spotlight was trained on the area I found a very small crack in the print between pin 2 of IT45 and CT48 (1µF). Repairing this finally cleared the fault. So you not only have to look out for soldering problems with this range of VCRs but also keep a watch out for cracked tracks. **D.V.**

Samsung SI3240

There was no clock display though the machine worked correctly in every other respect. Checks showed that the 3.4V a.c. supply across the end pins of the fluorescent display was missing. The cause of this was defective pads (10 and 11) at the mains transformer. Hardwiring these connections cured the fault. **G.S.**

Mitsubishi HS347

Intermittent failure to make a timer recording was the complaint with this machine. We found that this would happen when the tape was at the beginning after a rewind: after full-speed rewind the tape leader was left showing and the low-speed forward take-up didn't take the tape back in. Thus when the timer recording started the tape leader showed at the take-up end sensor and the unit stopped.

Although the take-up torque and the fast forward/rewind torque were o.k. the low-speed take-up torque was very low. A new reel idler cured the problem. **G.S.**

Toshiba V611

This machine was dead (no functions). Replacing the 400mA fuse F801 and resoldering dry-joints around Q821 got it going again. **G.S.**

GoldStar GHV1296I

The complaint with this machine was that it damaged tapes. As the capstan was inoperative there was no play, fast forward or rewind. Checks showed that the regulated 12V supply was low at around 6V. The DTC124ES transistor Q103, which is part of the power control arrangement, turned out to be faulty, a replacement restoring normal operation. **G.S.**

Grundig VS440

This machine had lost its ability to tune in stations. A defective tuner was the first thought that occurred to us, but a closer study of the circuit diagram revealed a cheaper possibility – the SDA3202-3 PLL chip. It's housed within the tuner assembly, and is fairly easy to replace. After doing this normal operation was restored. **K.E.**

Hinari VXL8

Although this machine was several years old it had hardly been used. The complaint was that the playback speed was faster than the search mode – in fact selecting fast search slowed the capstan down. There was obviously something wrong in the servo department. Several chips can influence the capstan speed, but voltage checks in this area were inconclusive in relation to the figures given in the manual. The Gods must have been smiling at us on that day however as an identical Orion machine came in for service. After making some comparison voltage checks with both machines in the playback mode we replaced the digital servo chip IC102. All was then well. **K.E.**

Akai VS422/VS425

If one of these machines won't accept a cassette or there's a cassette jammed in the mechanism, check the condition of the 'arm damper' assembly. When its spring retainer spigot breaks off you get jamming etc. The part number is ML-391745J1 – it's on the left-hand side of the cassette housing. **G.R.**

Samsung SI3260

The tuning had disappeared. When search tuning was tried it took a long time to search and when a signal was found it was very unstable with what looked like hum bars across the picture. In addition the tuning drifted. A check on the 30V tuning supply produced a reading of only 16V. The 30V regulator is fed from a 40V rail via R108 (1k Ω) and was zenering at 16V! A new 30V regulator put matters right – we replaced R108 as well as it had become discoloured. **G.R.**

Sony SLF30

There was fast, erratic tape movement and no E-E video or sound. After some time checking around we found that the

800mA fuse PS001 on the bottom video board was open-circuit. No shorts were present and the fault occurred when the customer was removing a jammed cassette.

If one of these machines doesn't switch on, check the alignment of the cassette housing – where the switch is situated. **G.R.**

Toshiba V109

A laced-up tape was jammed in this machine. Checks showed that the on/off 9V supply was missing. The repair consisted of replacing IC811 in the power supply and, as a precaution, the mode switch. **R.B.**

JVC HRD830

There were no timer recordings with this machine. It went through the motions then, after loading up, ejected the cassette. Manual recording was o.k. A replacement record inhibit switch cured the fault. **R.B.**

GoldStar GHV1296I

There were erratic functions with < > showing in the display. A replacement mode switch restored normal operation. **R.B.**

Panasonic NV333

There was a snowy r.f.-r.f. signal, no E-E output and no reception. The cause of all this turned out to be a dry-joint at pin 1 of plug P7003 on the TV demodulator PCB. **R.B.**

Amstrad VCR4600

When a deck function was selected the mechanism started to operate then shut down. This happened whichever function was selected. A clue was that the clock would also reset. Whenever a function was selected the 5V supply went low. Replacing the bridge rectifier and the fuse to the 5V supply cured the fault. **D.B.**

Sony SLV425

This machine failed to record sound. The cause was the bias oscillator, which in these machines is separate from the erase oscillator. CY1255 (47 μ F, 63V) was open-circuit. **D.B.**

Aiwa VXT1010

Very intermittently this machine would shut down while playing a tape. Lack of the drum flip-flop pulses was the cause. The drum produced a good pulse output, the culprit being IC2001. **D.B.**

Hitachi VTM830

This machine would go into some rather odd modes at random. We found that the microcontroller chip IC751 was dry-jointed. After resoldering all the connections and a long soak test all functions worked correctly. **D.B.**

Saisho VR905

There was intermittent loss of reel drive. For once the reel idler and motor were blameless: Q2101 was going open-circuit intermittently. **D.B.**

The Panasonic Alpha 3 Chassis

Part 4

Ray Meadows

This concluding instalment will deal with the audio and scanning circuits and the other remaining parts of the chassis, including some of the options such as the comb filter. We will be following up with some fault information later.

The Audio Path

In Part 2 we looked at the f.m. and Nicam sound circuits and the AV switching. After the switching the selected audio passes to the ambience circuit and tone controls on panel C (see Fig. 1) and finally the power amplifier on panel K. The circuitry is basically the same for the A2 and W2 versions of the chassis except that A2 models have an additional tone shaping circuit to match the frequency response of the dome speakers: this circuit is switched out to maintain a flat response when normal, external speakers are being used.

The ambience circuit is based on the Philips TDA3810 chip, which can be switched to give four different sound modes, mono, stereo, pseudo-stereo and ambient stereo. The pseudo-stereo and ambient stereo modes are produced by

processing the mono and stereo signals: frequency-selective filtering is used at the input, the result of this being phase shifted then mixed with the original input signals. The effect with a mono signal is to make it sound wider, with a stereo feel. The sound can be widened further and ambience effects enhanced with a stereo source, but much depends on the original sound content.

In the Alpha 3 chassis the ambience effect is switched on and off by the main microcontroller chip (pin 20). The ambience processor chip's mono/stereo inputs are also tied to this pin, so that ambience is allowed with mono but not stereo sources. 'Stereo' sources are of course frequently monophonic, so all four modes may be encountered. Muting is applied to the inputs, by means of Q2403/4/7. When the microcontroller's audio mute pin goes high, Q2403/4/7 switch on.

In A2 models the ambient processor's outputs are passed to frequency-response shaping circuits that use operational amplifiers, usually type XRA15218N. These circuits provide considerable fixed bass and treble boost. As mentioned above a bypass switch is incorporated to obtain a flat frequency response when external speakers are being used: each switch is mechanically linked to the external speaker switch by means of a small metal strap.

The audio signals next enter a Philips TDA8184P tone control chip which contains bass/treble and volume/balance control blocks for each channel. Control signals from the microcomputer chip's bass, treble, volume and balance DACs enter the TDA8184P's control block, setting the boost and cut levels. A speech/music control signal is provided by pin 18 of the microcomputer chip. In the speech mode the frequency response is restricted. This is said to improve the clarity of the spoken word. Q2405/6 are switched on in this mode. The tone controls still operate, but their range is limited. In the music mode the tone control circuits operate normally. As the additional tone shaping for

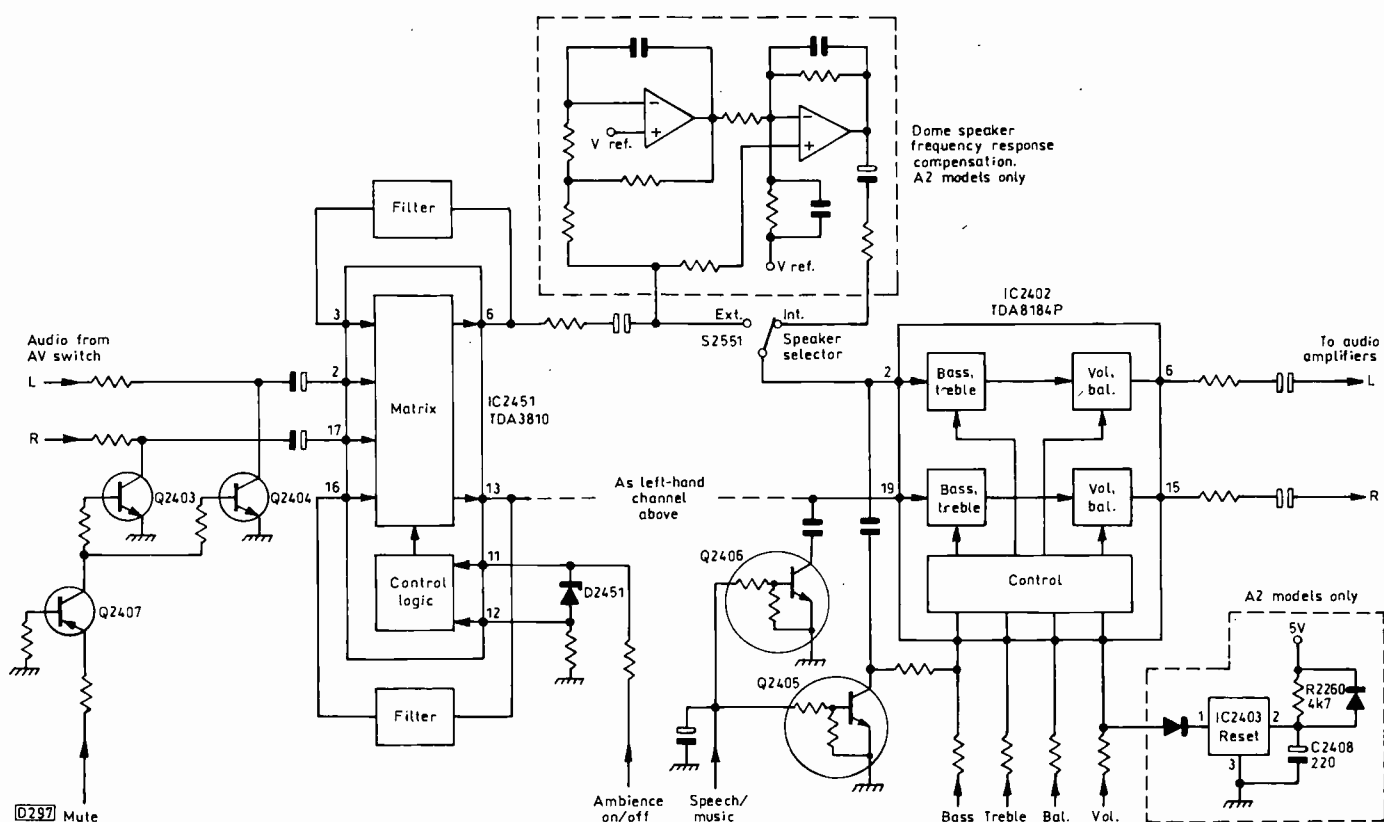


Fig. 1: The audio signal path to the output stages.

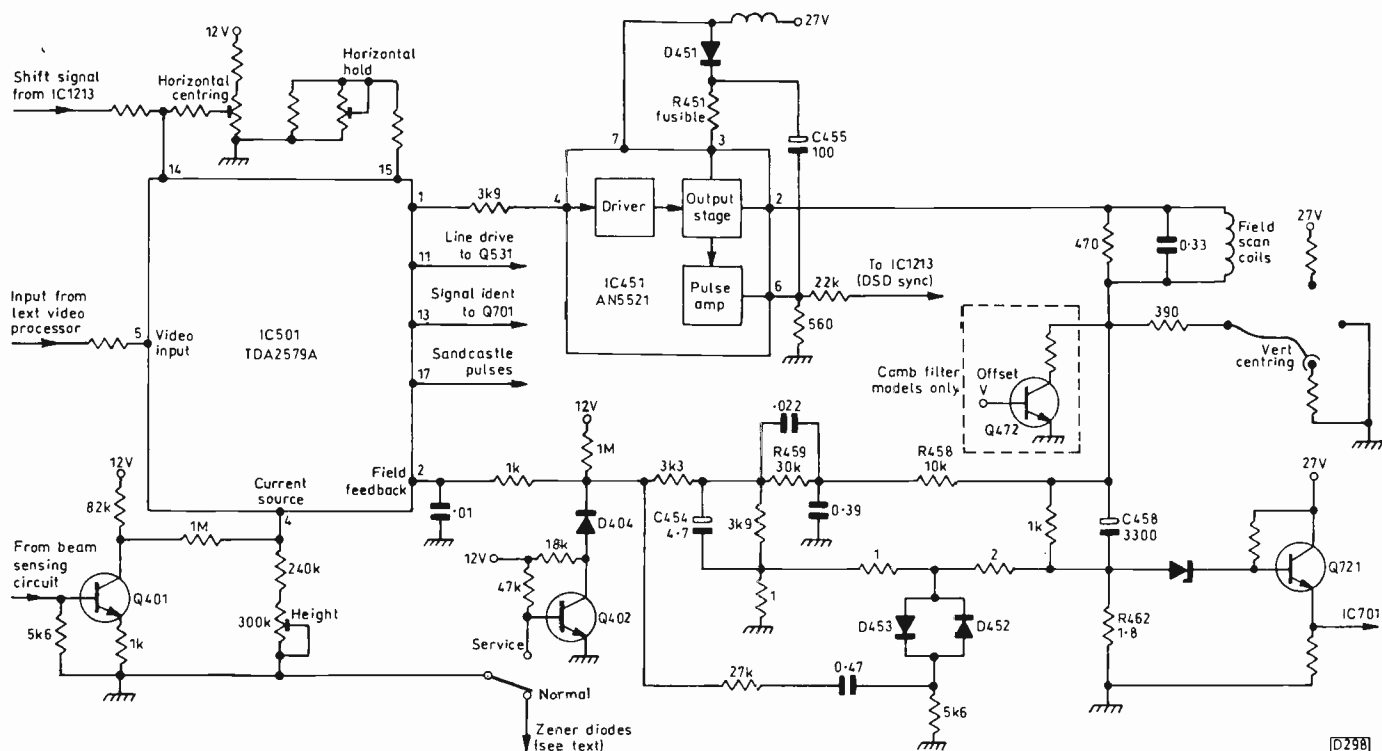


Fig. 2: Main items in the timebase generator and field output sections of the chassis.

the dome speakers in A2 models significantly increases the l.f. response, additional switch-on thump muting is provided. This is carried out by the reset chip IC2403, which momentarily holds the volume control DAC at minimum – for a time determined by C2408 and R2260.

After tone control processing the signals head for the audio amplifier on panel K. Although the dome speakers in A2 models are rated at 10W while the speakers in W2 models are rated at 20W, the same amplifier circuit is used in both versions, with an STK4392 chip in 25 and 28in. models and an STK4432 chip in 33 and 37in. models. Model TX33A2 has a slightly different circuit providing 15W per channel through its dome speakers. There are a few differences between A2 and W2 models in the peripheral circuitry, and further changes were introduced during the life of the chassis. This was partly a cost-saving exercise, with the deletion of filter inductors in series with the main speakers.

The output signals make the final trip to the speakers via panel L, where the headphone socket is situated. Early models had the inductors just mentioned and crossover components mounted on this panel. The signals then go back to the internal/external speaker switch on panel C. After this they at last go to the speakers themselves!

Sync and Scan Generation

The video signals from the AV switch on panel H are passed to the SAA5231 teletext video processor chip IC3501. In the TV mode this chip provides a composite video output: in the teletext mode it provides locally-generated composite teletext sync. These signals are passed back to pin 5 of the TDA2579A sync/timebase generator chip IC501 on panel E (Panasonic call this the 'jungle i.c.'). It's one of the oldest parts of the set, the chip first being used in the U5 chassis. Fig. 2 shows the main components in this area.

IC501 contains a sync separator and line oscillator, the field-frequency signals being generated by dividing down

from the line frequency. A phase detector locks the generated signals to the video signal, with the aid of line and field flyback pulses. The phase detector has three modes, to cater for the different requirements of normal and weak off-air signals and VCR signals. Internal black-level detection reference signals and noise inversion ensure stable operation of the sync separator. There are only three adjustments: vertical output gain, line frequency (horizontal hold) and horizontal phase (horizontal centring). Pin 14 receives a horizontal shift signal from the microcomputer chip: this centres the picture in the text and external RGB input modes. Outputs include line drive (pin 11), field drive (pin 1), signal identification (pin 13) and sandcastle pulses (pin 17).

Field Output and EW Correction

The field drive output from IC501 is fed to pin 4 of the AN5521 field output chip IC451 on panel D. Although this device is operated at 27V, use of the voltage doubler formed by D451 and C455 enables it to generate a field output waveform of around 50V peak-to-peak amplitude.

Gain is set by the feedback circuit which runs back to pin 2 of IC501. There are both d.c. and a.c. paths, providing linear and non-linear correction. The d.c. path is via R458/9 while the a.c. path is via C458. D452/3 provide a simple form of NS correction. In the event of failure of the field scanning there's no feedback to IC501 and the drive is cut off. The service switch is also connected to pin 2. In the service mode Q402 is switched off, forward biasing D404: the field feedback is then blocked, resulting in field collapse. The beams are enabled however, via zener diodes connected to the RGB outputs from panel E. Vertical centring is adjusted by a plug and socket arrangement with three positions. This varies the d.c. level at the earthy side of the scan coils, introducing a small vertical offset.

The height control is connected to pin 4 of IC501. This pin is also connected to Q401, whose base is linked to the beam current sensing circuit (at pin 2 of the line output transformer). Large increases in beam current cause slight

breathing: the action of Q401 counters this effect, stabilising the height.

A field-frequency signal is tapped from the junction of C458/R462, buffered by Q721 and used to drive the SGS-Thomson TDA8145 EW correction processing chip IC701 on board D (see Fig. 3). This drives a conventional diode modulator circuit. Although parabola (R704) and keystone correction (R713) controls are provided it's seldom possible to eliminate scan distortion completely, particularly at the extreme top and bottom of the screen. R708 provides width adjustment: it varies the amplitude of the line flyback pulses fed to the rectifier circuit D701/C705. A switching transistor, Q701, is connected to the pulse feed. It's controlled by the ident output from IC501 (pin 13) via Q504 (not shown) and is used to adjust the width when a 60Hz signal is being received.

The Line Output Stage

The line driver and output stages are conventional, with Q531 the driver transistor and Q551 the output transistor. Fig. 3 shows the main components in this area. The circuit has proved to be quite reliable, though there have been a number of cases of failure of the line output transformer T551. If you have to replace the transformer note the orientation of the two leads to connectors D19 and D20 (see Fig. 2, page 320, March). If these leads are reversed the power supply will not receive the correct synchronising pulses and will not run. In addition take care not to knock the linearity coil L553 which is near the edge of panel D: it is quite easy to snap its top off!

Model 33A2 has a different D panel to the 25 and 28in. models. The most obvious difference is in the position of the parabola, trapezoid and width controls. The circuitry is

almost identical however, with updated components in the power supply and scan output circuits.

The line output stage also generates some of the receiver's supplies - 6.3V for the c.r.t.'s heaters, an 8V supply for the teletext circuit (via a 5V regulator) and a 210V supply for the RGB output stages.

Protection

Excess-current protection is provided by Q543, see Fig. 4, which is powered by the 11V output from the standby power supply. Q543's base is linked to the 8V supply obtained from pin 3 of the line output transformer via rectifier D553/C557. If the load on the line output transformer is excessive, the voltage on the 8V line will fall and Q543, being a pnp device, will switch on. This will in turn switch on the standby transistor Q825, shutting the set down. In the normal standby mode Q544, which is driven by the same output from the microcomputer chip as Q825, is switched on. This reduces the supply to Q543, overriding the excess-current control.

Beam-current limiting is carried out in the video control chip IC303. The earthy end of the diode-split section of the line output transformer determines the charge on C545 (4.7µF). With excessive beam current the charge on C545 swings negatively. This negative voltage swing is applied to the contrast control circuit, thus reducing the tube drives.

Scan-velocity Modulation

The scan-velocity modulation system is similar to that used in the Euro 1 chassis (see page 18, *Television* November 1993). Positive-going video transients slightly accelerate the horizontal scanning while negative-going

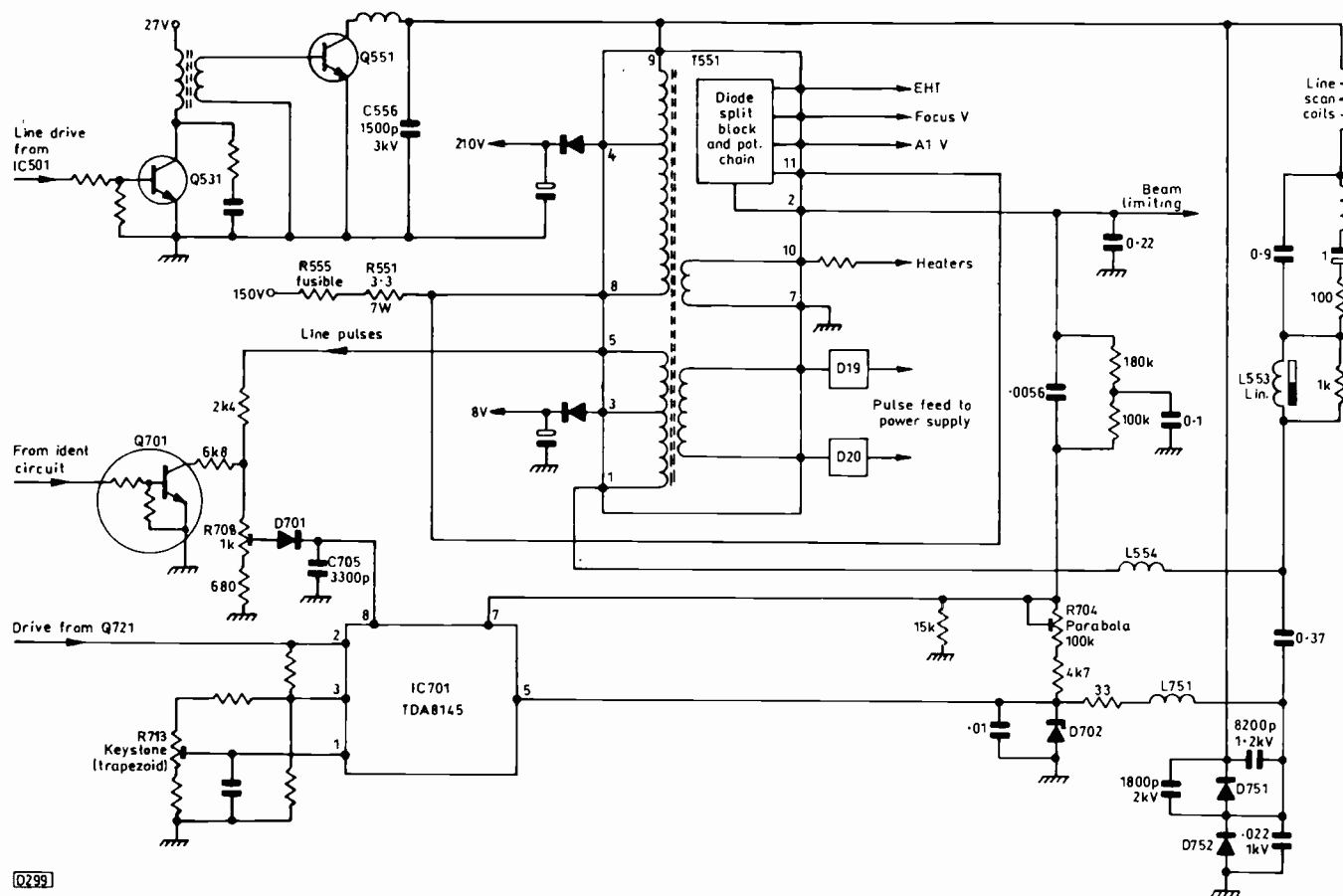


Fig. 3: Basic line output and EW correction arrangement.

transients decelerate it. This sharpens the transients by reducing their width.

The circuit, on panel S, contains a differentiating network, a high-pass filter and a push-pull output stage to drive the scan-velocity modulation coil on the tube's neck. The difference between the Euro 1 and the Alpha 3 circuits is that the latter operates with a luminance input while the Euro 1 operates with RGB inputs and thus caters for teletext and on-screen graphics displays. As the signals do not pass right through the circuit in the Alpha 3 however a compensating delay is not required.

Comb Filter

Originally all 33in. sets incorporated a comb filter for improved luminance/chrominance signal separation without the need for traps. Because of the cost however it was dropped from all but the German Model TX33A2C. The comb filter consists of an AN5346K control chip (IC1310) with filter circuits and switches, all on panel F, and four Sony CX1009P charge-coupled device (CCD) delay lines (IC1306-9) on panel FA. Both panels are completely enclosed in shield cases, the assembly plugging into sockets on panel E.

The input to the circuit is composite PAL video, which is taken from just after the AV switch on panel H (NTSC signals cannot be processed in this way and bypass the filter). The comb-filtered luminance signal is fed to the black-level expander chip while the filtered chroma signals pass to the multistandard decoder chip (compare with Fig. 3 last month). Because of the attenuation introduced by the comb-filter module the sub-colour and sub-contrast settings have to be at higher levels than in other models. And because of the improved YC signal separation the picture sharpness control is preset to have a smaller range – the picture noise reduction feature is then used to turn the comb filter on and off.

The system works by comparing successive lines of the video signal, four lines at a time being stored in the CCD chips. Filtering consists of addition and subtraction of the lines to provide selectivity. Thus there's no need for traps. The technique does however cause problems on transitions between lines with colour and those without. This can produce an unwanted horizontal dot-crawl effect, though it's much less irritating than the 'normal' PAL dot crawl. To take into account the slight vertical shift caused by the line delay a small offset is added in the field output stage (by Q472, see Fig. 2) when the comb filter is in operation.

Model TX37A2G

This Japanese made set is labelled as being fitted with the Alpha 3 chassis but there's a lot more in there! Basically it's equipped with all the options described in this series, including the comb filter, satellite tuner etc. There is also 100Hz field scanning. Dynamic focusing is used with the giant 37in. Mitsubishi tube, so a special line output transformer with dynamic astigmatism adjustment is required.

Extra panels include DD, which houses the RGB matrix, RGB switches and an extra on-screen display generator, and MM which contains the flicker-free circuit with field stores. Chips on this panel consist of the CXD2000Q flicker-free generator IC5008, the CXA1260Q DAC IC5007, the three CXD1175M ADCs IC5001-3, the three CXD2001Q noise-reduction processors IC5004-6 and the CXK1206M RAMs IC5010-5 – these are all Sony devices.

The panel processes the video signals in colour-difference form. This is not as strange as it may seem, as the

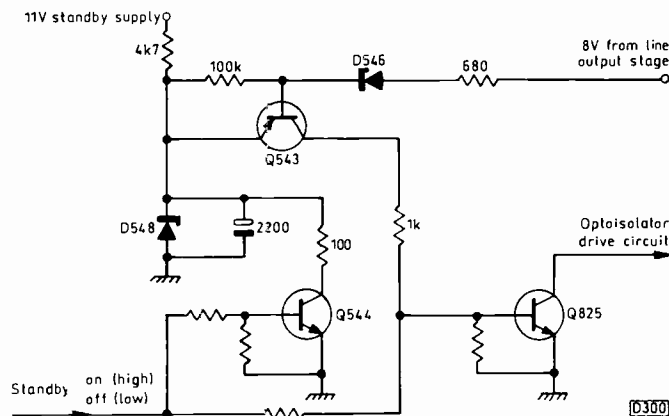


Fig. 4: The excess-current trip circuit.

comb filter works with YC signals, the chroma component being converted to colour-difference form by the decoder and digital line memory. The only problem is that text and external RGB signals must also be processed on the MM panel. So these are converted to colour-difference form by IC5501.

After processing on the flicker-free panel the 100Hz (120Hz if NTSC) signals return to panel DD where they are converted back to RGB form and mixed with the on-screen display signals.

Conclusion

This concludes our look at the Alpha 3 chassis. Though production stopped in 1993, there are still many of these sets in the shops. Subsequent large-screen analogue models were fitted with the Alpha 4 chassis.

Answer to Test Case 378

– see page 561 –

The current that flows through an IR emitting diode when it produces a 'flash' is surprisingly high – well in excess of an amp. If anything restricts the flow of current via the output stage the diode's peak current, and thus its emission, is reduced. If the batteries are in good condition and the diode and driver transistor are o.k., what could limit the diode's current? In fact the current is drawn, in the short term, from an electrically large electrolytic reservoir capacitor that's connected across the battery: a low 'average' current from the battery charges this capacitor.

Because of its internal resistance and that of the contacts, the wires (nearly a foot of wire in this case) and the soldered joints, the small two-cell battery is unable by itself to sustain the high-current pulse output. When the Avo was brought into use to check the current there were even more wires and contacts: the same was true when a test was made with the bench power supply. Hence the almost total loss of emission when the tests were being carried out. If the total source resistance seen by the LED is just 1Ω, and the required current is say 1A, 33 per cent of the battery voltage is lost outside the diode and over half its power is lost.

The reservoir capacitor had of course gone open-circuit. It's a 220μF, 6.3V type that's mounted close to the LED. When a replacement had been fitted the zapper came to life fully and Mr. Miles' TV set once more responded quickly and positively to his instructions from the armchair.

A Z ELECTRICS

183 ACRE LANE, NORTHAMPTON NN2 8DX

Telephone/Fax: (0604) 841871

BELT KITS

A range of belt kits in stock from 60p to £2.40. Makes for most models available including: Alba, Akai, Amstrad, Ferguson/JVC, Fisher, Funai, GEC, Goldstar, Granada, Grundig, Hinari, Hitachi, Mitsubishi, NEC, Orion, Panasonic, Philips, Saisho, Samsung, Sanyo, Schneider, Sharp, Sony, Tensai, etc. - Please state model and make.

VIDEO MOTORS

A range of **Reel Motors** made by Ferguson, Hitachi, Sanyo, Sharp & Panasonic are available, please state model and make.

We stock **capstan motors**, makes include Ferguson/JVC, Hitachi and Sharp.

Also available are **Ferguson Mode Control Motors**, please state make, model.

Mode Motor Assembly 3V35-49 at £12.50

Sharp Reel Motor Pulley only £1.20

Replacement of plastic pulley on a number of Sharp Reel Motors with the above metal pulley gives better rewind/FF performance.



REMOTE CONTROLS

Bush, Ferguson, Grundig, ITT, Philips, Pye, Sony, Hitachi, Matsui, Logik, Panasonic, Saisho, Salaria, Samsung, Tashiko, Tatung, Toshiba. Various models TV & Video. From £7.50

MANY HITACHI TV REMOTE CONTROLS NOW IN STOCK.

STATE MODEL FOR PRICE
One for all Mk 3, 4, 6, From £18.50
Topel Universal R/C £28.00
Fox £22.50

TRIPLERS

Universal Tripler £6.20
 Universal Tripler with focus unit £9.50
 Decca 120/130 series tripler £8.50
 Thorn TX10 Focus Unit Kit £10.00
 Grundig Trips POA

MAINTENANCE KITS

Available for Alba, Amstrad, Ferguson, Fisher, Goldstar, Goodmans, Granada, Hinar, Hitachi, JVC, Matsui, Mitsubishi, Nikkai, Panasonic, Philips, Saisho, Salaria, Schneider, Sentra, Sharp, Sony, Tashiko, Toshiba



LINE OUTPUT TRANSFORMERS

LOPT Hitachi 2174, 76, 78 £17.50
 LOPT Hitachi CPT1476 £18.00
 LOPT Hitachi CPT2276 etc. £19.00
 LOPT Matsui 1440 £18.00
 LOPT Matsui 1450 £22.00
 Decca 100 £9.50
 ITT CVC25/30/32 £16.75
 ITT Compact 80 Series 110 £19.75
 ITT Compact 80 Series 90 £19.75
 ITT CVC1204 £21.50
 ITT CVC800/1/3 £21.50
 ITT CVC1100 £16.50
 ITT CVC1150/1175 £20.00

Other ITT transformers available

Fidelity all models up to 20" ZX3000 £15.50
 Fidelity Panel for ZX2000 £1.00
 Fidelity 22" ZX3000 £18.50
 Hinari CT4/5 & TVA1 £17.50
 Philips KT3 £12.95
 Thorn TX100 Green Spot 110 £14.50
 Ferguson TX90 LOPT specify size screen £17.75
 Sony - Please state model for price

VIDEO HEADS

AMSTRAD, FERGUSON, HITACHI, PANASONIC, SANYO, SHARP, FISHER, HINARI, ALBA, MITSUBISHI, ORION, SAISHO, SAMSUNG, TOSHIBA. State Model No. Price from £7.50

PINCH ROLLERS

A range of Pinch Rollers is in stock, most of them @ £2.80. Makes include Akai, Amstrad, Ferguson, Fisher, Funai, GEC, Goldstar, Grundig, Hinar, Hitachi, ITT, JVC, Marantz, Mitsubishi, NEC, Nordmende, Orion, Panasonic, Philips, Samsung, Sanyo, Schneider, Sharp, Sony, Tensai, Thomson, Toshiba etc. Please state model and make.

Philips Pinch Roller for models VR6180, 6185, 6285, 6362, 6367, 6467, 6468, 6470, 6561, 6670, 6760, 6761, 6870 £6.00

BACK-UP BATTERIES

Philips 1.2V Back up Battery £1.75
 Philips 2.4V Back up Battery £2.80
 Ferguson TX10 £2.00
 Ferguson TX10 1.2 £2.10
 Ferguson TX10 2.4 £3.58
 5.5V Back Up Cap £1.85

TV ON/OFF SWITCHES

ITT, Philips, Decca, Thorn, Fidelity, Grundig, Sony and Hitachi. State model for price.



SONY PUSH SWITCH

80p
 Limiter Post Assembly £1.75
Makes & Models: Hinari VXL4, Matsui VX730, 735, 735A, 755, 770, 800A, 810, 820, 880, 990, Saisho VR1100, 1200, 1200HQ, 1600, 2500, 3200, 3300, 3300X, 3500, 3600, 3700

OTHER SPARES

Universal Video Copying Kit £4.25
 Universal Copying Kit (Scart) £5.20
 Universal Camcorder Kit £8.00
 Video Cassette Lamps from £0.50
 CRT Anode Caps £0.60
 Video Tape Splicing Kit £6.95
 Hitachi TV Frame Module HM6251 £8.00
 Hitachi TV Frame Module HM6232 £10.50
 Cassette Loading Roller Assembly 3V23, 3V31, 3V32 £4.50
 Degaussing Positor Blue £4.00
 Degaussing Positor White £1.30
 Degaussing Positor Hitachi £3.40
 Degaussing Positor Philips £3.00
 End Sensor for Hitachi VT63, 64, 65 (Pair) £2.75
 Cassette LED Sensor for Panasonic etc £1.60
 I.C. Circuit Protectors £0.60

Clear Service Cassette £5.90
 Video Idlers Spring Kit £7.50
 Video Washer & E Clip Kit £6.00
 Universal Video head Puller From £7.90
 Akai VS22 Series Power Board £26.00

CASSETTE HOUSING

Cass. Carriage 3V35 £30.50
 Cass. Carriage 3V42 £30.50
 Cass. Carriage 3V58, 59, FV11 £21.00
 Cass. Carriage HRD 500, 30, 700, FV10, 12 £22.50
 Cass. Carriage HIT. VT 11 £15.00
 Cass. Carriage HIT. VT 64 £19.50
 Cass. Carriage Philips VR6462 £16.85
 Cass. Carriage Philips VR6362 £11.00
 Akai Carr. Kit £10.25

MANY OTHER VIDEO AND TV SPARES IN STOCK

Back Tension Bands in Stock for Akai, Fisher, Hitachi, Ferguson, JVC, Mitsubishi, Panasonic, Sanyo and Sharp.

IDLER ASSEMBLY

FERGUSON, FISHER, HITACHI, PHILIPS, PANASONIC, SANYO, SHARP, AKAI, SAMSUNG, MITSUBISHI, NEC, In Stock.
 Price on Application **Wide Range Available**

SATELLITE SPARES

SAT. DISHES, LNBS, CABLES, SAT. FINDER KITS, INSTALLATION KITS, etc NOW IN STOCK


Special Offer 1.2 DB £29.50

AUDIO, VIDEO CABLES, SCART LEADS, AND SATELLITE BRACKETS IN STOCK

A LARGE RANGE OF SEMICONDUCTORS IN STOCK. POPULAR STDs, STRs, TAs, TDAs, 2SAs, 2SBs, 2SDs, ETC. IN STOCK. PLEASE TEL FOR PRICES ETC.

Prices subject to change without notice. Please add £1.25 per order for p&p and then add 17.5% VAT. POSTAGE VARIES ON HEAVY ITEMS. SEND A4 SAE FOR LIST (MAIL ORDER ONLY)

QUILTED PROTECTIVE TRANSIT COVERS

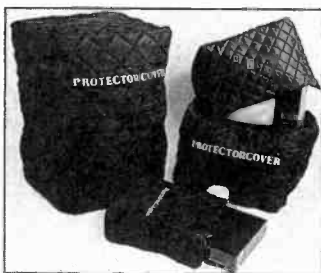

- ★ Padded covers for all types of electrical goods
- ★ Standard range of brown/white goods covers
- ★ Made to measure also available
- ★ Company name/logo printed
- ★ Direct from manufacturers

Substantial Discounts Available Now.

For Further Details:-

PROTECTOR COVER



Lynwood Business Centre, Lynwood Terrace
 Newcastle upon Tyne NE4 6UL.
 Tel: (091) 273 2233 Fax: (091) 226 0876

INFRA RED REMOTE CHECK CARDS

★★

Both same price £7.66 each plus VAT

No minimum order charge No P&P!

Magic Mirror

◀ INFRA-RED DETECTOR ▶



IR 5 CREDIT CARD SIZE BULK BUYERS BARGAINS NO P&P!

10 x BU 508A	£11.00	10 x BU 526	£9.00	A
10 x BU 508AF	£12.00	25 x BYV 96D	£5.00	L
10 x BU 508DF	£13.00	10 x BYW 96E	£8.00	L
10 x BU 508V	£15.00	25 x BY 228	£10.00	
10 x BUT 11A	£12.00	25 x BY 299	£5.00	P
10 x BUT 11AF	£9.00	5 x ONX 62A	£8.00	L
10 x BU 326A	£9.00	5 x TDA 3654	£8.00	U
10 x BU 407	£9.00	5 x TEA 1039	£7.50	S
10 x BU 426A	£10.00	5 x X2402P	£7.50	
3 x TDA 3562A	£11.10	3 x TDA 8180	£15.00	V
3 x MDA 2062 Bush	£12.00	3 x STR 54041	£11.10	A
3 x MDA 2062 Clear	£9.00	3 x SAA 1293A03	£21.00	T
3 x SAA 129303	£15.00	3 x STR 6020	£19.00	
5 x S2000AF	£13.00	10 x S2000A2	£12.00	

Send cheque or postal order to E.C.S. Dept. P
 6 NETHERSOLE STREET, POLESWORTH, TAMWORTH B78 1EE
 No post and packing charges. Please add VAT
 Phone: (0827) 330392 Fax: (0827) 331041



Above also available from TVRS 30 Marsh Hill
 Erdington, Birmingham B23 7EH.
 Tel: 021 377 8451

EXPORT ENQUIRIES INVITED



*UK Spares
Reference Book*

Hoopwell
Hoopwell
Hoopwell
Hoopwell
Hoopwell
Hoopwell
Hoopwell
Hoopwell
Hoopwell
Hoopwell
Hoopwell
Hoopwell
Hoopwell
Hoopwell
Hoopwell

OUT NOW

NEW FOR 1994 THE UK SPARES REFERENCE BOOK

OVER 400 PAGES OF TV AND VIDEO SPARE PARTS
FROM AIWA TO ZANUSSI ... FROM AUDIO HEADS TO ZENERS.

DESIGNED WITH THE SERVICE ENGINEER IN MIND - PUBLISHED IN
REFERENCE BOOK FORMAT A5 SIZE - HUNDREDS OF
ILLUSTRATIONS - THOUSANDS OF SPARES AND COMPONENTS.

THE BOOK ALSO CONTAINS FOUR 10% DISCOUNT VOUCHERS
SAVE £££'s ON PARTS

TO ORDER YOUR COPY SEND £5 BY CHEQUE OR POSTAL ORDER OR
TELEPHONE QUOTING YOUR CREDIT CARD NUMBER TO:

HOOPWELL LTD. UNIT B9, LARKFIELD TRADING ESTATE,
LARKFIELD, MAIDSTONE KENT ME20 6SW
TEL: 0622 882285 OR FAX: 0522 882287

**ORDER
YOUR COPY
NOW**

DO YOU KNOW?

A COMPANY WHO CAN REPAIR/REALIGN ANY UHF TUNER.

A COMPANY WHO CAN REPAIR ALMOST ANY BOOSTER/MODULATOR BE IT VIDEO OR
SATELLITE.

A COMPANY WHO CAN REMANUFACTURE ALMOST ANY VHS VIDEO HEAD.

A COMPANY WHO CAN REMANUFACTURE ALMOST ALL POPULAR LNB'S ON THE
MARKET.

A COMPANY WHO CAN REPAIR AND TURN ROUND 90% OF GOODS RECEIVED THE
SAME DAY BY 1ST POST.

A COMPANY THAT CAN CONSISTENTLY CUT YOUR SERVICING COSTS

**PHONE OR FAX THE NUMBERS BELOW
FOR YOUR FREE WALL CHARTS/PRICE LIST.**

**WHO
MCES**

OF COURSE

FAX
061-746 8136

PHONE:
061-746 8037/8

15 LOSTOCK ROAD, DAVYHULME, MANCHESTER M31 1SU.

ATTENTION ALL ELECTRICAL / ELECTRONIC WORKSHOPS

TRADING STANDARDS OFFICERS are actively enforcing the Consumer Protection Act throughout the UK. This act requires that all electrical goods which have been repaired or modified and are sold to the public in the course of trade are tested for electrical safety.

Previously, suitable Portable Appliance Testers have been expensive and often out of the reach of the smaller retailers. Our survey has shown that many are operating without any acceptable means of testing the products they sell.

EVERYTHING YOU NEED TO PROTECT YOU & YOUR CUSTOMER

DATAPART have now produced a low cost Portable Appliance Tester at a very low price which will enable even the smallest retailer to comply with the requirements of the act and avoid the possibility of prosecution.

Manufactured in the UK these units are robustly constructed and housed in a strong aluminium carrying case and are supplied with a probe unit, operating manual, pass labels, failed labels, log cards, low value fuses, a pen and a neon screwdriver. All units carry a twelve month return to base guarantee against component failures or faulty workmanship.


SPECIFICATION

Size 254 x 180 x 105 mm, Weight 4.85kg
Supply 250v. 50 cyl. AC. Four test modes
Earth Bonding, Continuity, Insulation, Run
and leakage. Indication by analogue meter
Probe unit facility. Output to appliance by
integral 13 amp socket or optional adapter.

EARTH BONDING - applied voltage 5v AC
Test current 4 amps. [Intermittent Use]
CONTINUITY - applied voltage 200V AC Test
current 1 milliamp.
FLASH TEST - applied voltage 1.3KV. OR
400V Test Current 1 milliamp
R UN / LEAKAGE - applied voltage 250v AC
50 cyl. Max. current 10 amps. Leakage Test 2
milliamps 0 - 250v.

CONTENTS

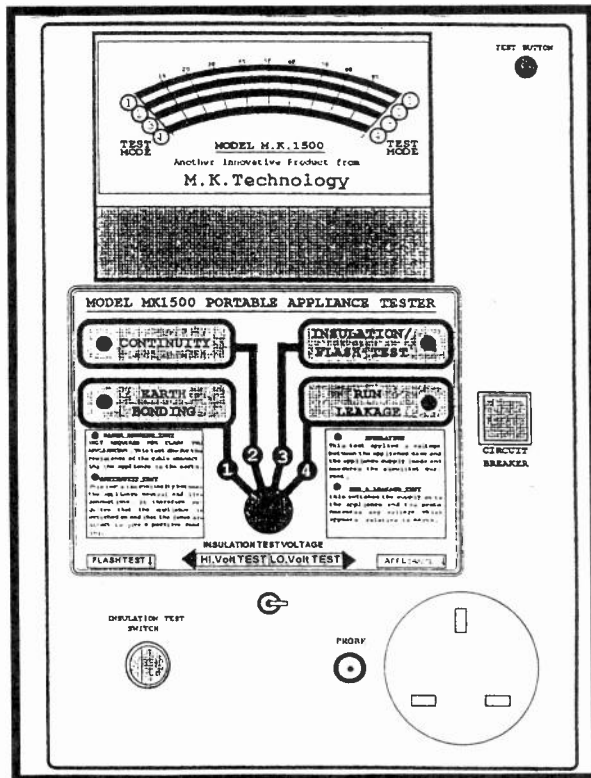M K1500 PORTABLE APPLIANCE TESTER
PROBE UNIT
INSTRUCTION MANUAL
100 PASSED LABELS
50 FAILED LABELS
50 LOG CARDS
10 3 AMP FUSES
10 5 AMP FUSES
1 PEN
1 NEON SCREWDRIVER
**ALL HOUSED IN A ROBUST
ALUMINIUM CARRYING CASE**



ORDER CODE - PATMK1500KIT
PRICE - £275.96 INC VAT

▷ DATAPART LTD

**ELECTRON HOUSE,
100 GREAT BARR STREET
BIRMINGHAM B9 4BB**



**SALES DESK 021 766 5551 24
FAX FREE 0800 373 459 HOURS**

NVQs and the Brown Goods Industry

Joe Cieszynski

A number of letters relating to training and the brown goods industry, in particular TV and VCR servicing, have been published in recent months in the correspondence pages of this magazine. While some valid points were made, it seems that those working in our industry are largely oblivious to the dramatic changes that are about to take place in training and qualification. These changes will affect us all, so I felt that it would be a good idea to outline the current situation.

How it is now

The City and Guilds of London Institute has always been the main provider of training in our industry. Until the late Seventies, C and G offered both Technician and Craft level qualifications, the technician one being the higher qualification with possible progression to HNC and HND courses. During the latter half of the Seventies a major change occurred when the government of the day set up the Business Technician Education Council (BTEC). This council became the examining body for all technician level courses, as well as HNC and HND. C and G continued as the examining body for all craft courses relating to engineering.

So it was that the C and G 224 Electronic Servicing course became the most widely recognised qualification in the fields of TV, VCR and audio servicing. Although BTEC options are available, 224 is by far the most popular course – no doubt because of its high-profile practical element allied to a sound theoretical content. To sum this up, 224 is the BTEC technician course without the maths and with a far greater practical content.

Mention should also be made of the Electronics Examination Board (EEB – formerly the RTEEB). This body provides essential practical tests at all levels of the 224 course: a 224 candidate cannot obtain a C and G certificate unless he/she passes both the theory papers and the EEB test.

How it will be

To be honest it's difficult to say exactly how training in our industry will be organised in say five years' time, because some of the bodies I'll be mentioning in a moment are still in the process of devising the new course. What I can provide is a clear outline of the direction in which all training in the UK is moving, and the general form of the new training initiative.

The key player in England and Wales is an organisation known as the National Council for Vocational Qualifications (NCVQ). It was set up by the Department of Employment in 1986, with the job of unravelling the labyrinth of qualifications and standards on offer from some 300 awarding bodies. An equivalent body called SCOTVEC was set up in Scotland for the same purpose.

The NCVQ has not simply merged the present examining bodies however. The old bodies remain, but must accept and fall into line with a wholly different approach, put forward by the NCVQ, to assessing the ability of individuals. What has emerged is the National Vocational Qualification (NVQ), which is to replace all other craft/technician qualifi-

cations. It's not an updated C and G or BTEC syllabus: the award is based on a quite different philosophy.

The NCVQ Approach

The NCVQ frequently quotes the driving test as being the best example of the direction in which it intends to take training and assessment in the UK. During the driving test you have to perform to a certain standard. If you do you are a competent driver: if you don't you have yet to reach the level of competence and have to try again on a later occasion. The driving test includes a small amount of oral questioning: the purpose of this is not to test your knowledge of theory but to cover circumstances that might not have arisen during the test. There is no syllabus for driver training, and the examiner is not interested in whether you were trained by a large motoring school or your next door neighbour.

The government's decision to make NVQs the only valid qualifications means that the NCVQ has been able to impose its philosophy on all aspects of training and thus on the entire prospective UK workforce. No one else has a voice in this. If you challenge the NCVQ, as the BTEC tried to do, you will simply be wiped out (the BTEC almost was, eventually capitulating and adopting the new GNVQs).

"The NVQ framework will send shockwaves through the whole system. We have turned the educational model on its head". That's how Dr. Gilbert Jessup, the Deputy Director of the NCVQ, put it in *All Our Futures*, a Channel 4 dispatches report on education.

It certainly has. You may have noticed that I've used the word 'training' rather than 'education' above. This is because education, in the opinion of many including myself, will no longer take place. Individuals will be trained to undertake specific sets of tasks and will be assessed on their ability to do so, with no written examinations. Assessment will consist of checking whether a person can do a particular job to a set standard on a number of occasions. If he can, he's regarded as being competent. But what about testing his understanding of what he's doing? Not necessary, says the NCVQ: if a person can do a job correctly, he knows what he's doing.

How it will be Applied

The NCVQ has divided the UK's training needs into eleven sectors, within each of which there are five NVQ levels. The sectors are as follows: tending animals, plants and land; extracting and providing natural resources; construction; engineering; manufacturing; transportation; providing goods and services; providing health, social care and protective services; providing business services; communication; developing and extending knowledge and skill. Our industry comes under engineering.

Each of these sections can be broken down into specific trades or professions. For example under engineering there are consumer electronics and domestic appliance servicing (that's us!), motor vehicle servicing, electrical installation,

intruder alarm installation and so on.

For each award there are five levels: foundation; craft; technician/supervisor; higher technician/junior management; professional/managerial. And for each industry the NCVQ has set up an Industry Lead Body (ILB). This consists of people from the particular industry invited to write what, in simple terms, can be called an assessment plan for their industry. It's made up primarily of company managers and training officers, with representatives of the traditional awarding bodies such as C and G having a voice, albeit a rather small one. The list for our industry is as follows: Thorn EMI UK Rentals; Grundig International Ltd.; Vestel (UK) Ltd.; R.F. Electrics; Philco Ltd.; AMDEA; Scholtes Ltd.; Appliance Care Ltd.; Electrolux Ltd.; D.R. Cooker Hoods Ltd.; VAX Appliances Ltd.; Mitsubishi Electric UK Ltd.; Sony UK Ltd.; JVC Ltd.; Mastercare Ltd.; R.H. Plumb and Sons Ltd.; BREMA; AEG (UK) Ltd.; NVCS; D.H. Haden Ltd.

The point to note is that the ILB doesn't write a syllabus: it simply decides what should be assessed, practically. As Dr. Jessup explains: "Take a plumber. First you think of what a plumber needs to do, then you specify the functions and finally you devise a training programme. No longer can second-rate educational courses stand in for the real needs of employers. The important things we learn in life are not done in classrooms." It is up to the tutor (trainer) who provides the course to decide what an individual needs to know, or be taught, to achieve the standard.

I must agree with Dr. Jessup when he talks about second-rate courses. Although there have been some excellent courses/syllabuses with some trades and industries, with others the syllabuses have been loaded with irrelevant subject matter. An advantage of the new initiative is that tutors are no longer tied to what may be out-of-date syllabuses: they can teach what is up-to-date and relevant. On the other hand however there was nothing to prevent the old syllabuses being upgraded.

The main problem about being without syllabuses is that huge differences between the academic levels at different colleges are bound to arise. But the NCVQ is not interested in academic levels, its argument being that academic knowledge is largely irrelevant. To quote Dr. Jessup again: "Nobody uses precisely the knowledge they've gained in A levels or degree courses. It doesn't matter too much what you know, but you do need to show that you can operate at an intellectual reasoning level."

The problems that arise from having no syllabuses are further compounded by the changes introduced by the government in the way in which colleges are funded. From April 1st 1993 all colleges became independent of local education authorities. They are now paid on a sort of productivity basis. Money is awarded for every student that enrolls, then more money is awarded for each student that leaves with an NVQ level 2 within two years. This means that there's pressure to teach the bare minimum so that the 'productivity' of the system is maximised.

The ILB is to appoint awarding bodies, whose responsibilities are to record candidate entries for particular NVQs, to appoint the army of assessors, internal verifiers, external verifiers and a national chief verifier to oversee the assessment process, and at the end to award the certificates. For our industry the awarding body will probably be the C and G, in conjunction with the EEB.

The Assessment Process

The assessment procedure will be as follows. Each candidate will have a log book in which his/her progress is

recorded. At the time of writing no such log book has been devised for the TV industry. I can however provide a good guess as to the form this book will have from my experience with the 1864 Intruder Alarm Installation NVQ, with which I became closely involved three years ago.

We won't go into the boring details here. Basically, the job for which a person is being trained is broken down into 'units' and 'elements': a unit might be something like VCR mechanism servicing; an element is one part of a unit, say replacing a video head. Every step in this process is identified in the log book, and at assessment time the assessor checks that the step has been performed. If a single step is missed, or performed incorrectly, the individual hasn't 'achieved the standard' (we can't use the word 'failed' - it's supposed to make people feel bad) and the whole process must be repeated on another occasion.

To prove their competence candidates have, for example, to fit the head more than once. With intruder alarm installation each task has to be performed correctly four times on four different occasions. For our industry the number of times has still to be decided.

To get an idea of the enormity of the assessment process, just consider the number of different tasks there are with a VCR - including fault-finding on the PCBs. Bear in mind that each of these tasks has to be assessed on a number of occasions.

The NCVQ decided that only a limited amount of assessment could be simulated in the intruder alarm field. It has to be done for real at the workplace. As a result, any unemployed person is automatically excluded from ever becoming qualified in any way. The NCVQ does however emphasise that NVQs must be open to everyone. Its solution to the unemployment problem is that each industry should offer work placements for the unemployed so that they can be assessed. I'm not sure that this will work on a large scale. I hope, for the sake of the many who wish to train or retrain but are currently unemployed, that I'm proved to be wrong.

Work-based assessment has merits. It's far more realistic. You can never simulate the real world of TV/VCR servicing in a college or training institution. However many faults you introduce you can't simulate a power supply that's blown up and taken half the rest of the circuitry with it, or say intermittent chroma caused by spillage in a VCR. Nor can you introduce awkward customers easily, or the pressures that so often go with field servicing.

A disadvantage is that work-based assessment can be costly: an assessor coming to a place of work could cost as much as £100 a day. But the assessor doesn't have to come from outside: he could be someone, such as a workshop manager, who has undergone special assessor training approved by the NCVQ. Then again the cost of this training, plus the cost incurred by the company in applying for centre approval, can exceed £1,000 (I base this on my experience with the intruder alarm NVQ). For large companies such as Comet or Granada this might not be too bad. It would hardly be acceptable for smaller companies.

Why Bother?

Many engineers who work for small- and medium-sized companies will probably ask this. In reply, to start with there's no alternative to the NVQ. No other examination offered by any body will be acceptable in the EC as a qualification. So trainees will have to be assessed to NVQ

level. This doesn't mean just engineers: it includes secretaries, typists, managers, service managers, installers – in fact the entire workforce.

Why can't you just ignore it? Many will be able to do so. It depends on whether or not government and industry leaders implement certain ideas which, at the moment, remain just ideas. In some countries it's illegal to work on services such as electricity, water, gas etc. unless you are qualified, and fines can be heavy. There's been talk of implementing the same laws in the UK. Once you adopt this approach, where do you stop? Maybe make it illegal for someone to service a TV set unless he's qualified to do so? Possibly this wouldn't be too bad an idea. But we'd all be unqualified initially.

Is this scaremongering? I hope so! But in the intruder alarm industry pressure is being put on all companies to have their engineers NVQ assessed. Insurance companies won't cover premises that don't have an alarm system which has been fitted by a company with trade association approval. Many trade associations are looking for BS5750 quality assurance approval. Put simply, an alarm company can't get the big contracts, which is where the money is, unless it's qualified. I recently spoke to the manager of a small company desperate for NVQ assessment. When I quoted him £450 he simply said "when can we begin?" And that £450 was just to assess himself.

Perhaps the pressures in our industry won't be so great

– we don't have Big Brother insurance companies looking at our work so intently. But only time will tell.

Summary

I've attempted to highlight the good things about the NVQ system, primarily the emphasis on being able to prove that you can actually do the job and not just talk about it, also the removal of irrelevant syllabus content. But after being involved with NVQ training and assessment for about three years I find it difficult to overcome my misgivings about the overall NCVQ philosophy. These stem from a genuine concern that the long-term result of having a workforce trained to a minimum level of understanding will be stagnation as individuals won't be able to adapt to new technology. They will have to be retrained virtually from scratch, involving more costs.


No doubt an NCVQ person who might read this will write me off as an oldie who's past his best. Would they really be convinced that those trained (not educated) to an NVQ level have the reserves of understanding to be able to tackle the new and novel technology they'll inevitably encounter?

No doubt those who have read this far will be forming their own opinions about the NVQ approach. Some may disagree with my personal reservations. But I hope at any rate that I've prepared you for what lies ahead when the NVQ in electrical and electronic equipment servicing arrives.

TELEVISION INDEX & DIRECTORY

and

REPRINTS SERVICE

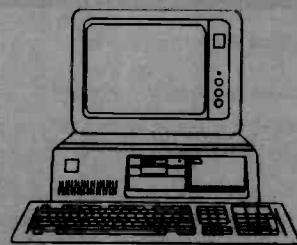

Version 2 of the computerised index to *TELEVISION* magazine, covering volumes 38 to 43 (1988 – 1993), is now available. There are over 5000 references to TV/VCR fault reports and articles, with synopses. A TV/VCR spares guide, an advertisers list and a directory of trade and professional organisations are included. The software is easy to use and very quick. It runs on any IBM or compatible PC with 512K RAM and a hard disc.

Price: £30 (specify 5.25" or 3.5")

Those with version 1 discs can have them upgraded for £12 each: return the disc quoting its serial number.

Reprints of articles from *TELEVISION* back to 1986 are also available: ordering information is provided with the index, or can be obtained from the address below. Hard copy indexes of *TELEVISION* are available for volumes 38 to 43 at £3.50 each.

Please allow up to 28 days for delivery. All the above prices include UK postage and VAT where applicable. Add an extra £1 postage for overseas EC orders, or £5 for non-EC overseas orders. Cheques should be made payable to Video Interface Products.

Video Interface Products Ltd., 1 Vineries Close, Cheltenham GL53 0NU, UK.

Service Briefs from Toshiba

Continued from the April issue: further TV items and notes on older and newer Toshiba VCRs

TELEVISION

Model 289T6B

Brightness flicker at the top of the screen: Reduce the value of C205 from 0.47 μ F to 0.027 μ F.

Model 1400TBT

Intermittent field collapse (h.t. voltage fluctuates when set is warm): Replace Q803 (2SC3425) in the power supply. Part no. A6361601.

Low h.t. voltage or stuck in standby: Q803 faulty (see above).

Model 1510RB

Dead set with buzzing noise: Replace Q803 (2SC3425), part no. A6361601.

Model 1721TB

Set stuck in standby: Replace transistors Q803 (type 2SC2023, part no. 23314246) and Q804 (2SA1321, part no. A6547303).

Models 2100RBT/2100TBT

Set dead, chopper transistor Q802 fails repeatedly at switch on: R810 (330k Ω) is either open-circuit or high in value.

Hum on chroma (varies with setting of colour control): Replace C515 (22 μ F, 50V, part no. 24636220).

Models 2112DB/2512DB/2812DB

Power supply trips in any mode: Replace D807 (BYD33J, part no. 23118479) which is open-circuit.

Power supply trips in normal operation, o.k. in standby: Replace the 13V zener diode D812 (part no. 23316337) which is leaky or short-circuit, reducing the voltage at pin 5 of IC801 below the standby threshold.

Set won't go into standby: Replace transistor Q845 (2SC2023, part no. 23314246) which is short-circuit.

Field jitter and picture breathing: Replace transistor Q833, type S1854, part no. A6907751.

Loud crack from both speakers when set is turned off (Model 2112DB only): C639 (100 μ F, 25V) in the audio mute circuit is open-circuit. Fit a replacement.

Models 2505DB/2805DB

Set won't come out of standby: Replace memory chip

ICA07, part no. 23319016. At power on voltage at pin 37 of the microcontroller chip drops low then reverts to 5V.

Models 2527DB/2927DB/3327DB

Set dead, power and timer LEDs flashing, h.t. at 40V and varying: Replace transistor Q828 (type 2SC2230A-Y, part no. A6325067).

Set stuck in standby: Replace circuit protector ZP82 (part no. 23144450) which is open-circuit, removing the supply to pin 40 of IC501 and thus the line drive.

Crackle on Nicam, f.m. and external audio: Replace the TA8776N audio processor chip ICG07 on the back terminal PCB. Part no. B0383935).

No audio from the rear speakers in the DSP, Dolby Surround or pseudo-surround modes: Replace CG25 (10 μ F, 16V).

VCRs

Information on some of the following machines will also be found on pages 52-3 of our November 1993 issue.

Models V55B/57B

Intermittent recorded sound: Check for poor plug/socket contact at the audio-control-erase head assembly.

Intermittent recorded sound with coloured patterns on the picture: Check for open-circuit leads at the full erase head. If the bias/erase oscillator doesn't start, increase the value of C27 to 8,200pF.

Noisy playback – looks like worn heads: Q504 in the E-E supply is leaky, allowing about 3V to reach the head amplifier chip during playback.

Distorted verticals/poor sync, changes with E-E picture content: The i.f. a.g.c. decoupling capacitor C7 (0.047 μ F) is open-circuit.

Playback speed slow: Check whether the voltage at pin 6 of IC401 is low – this won't show with use of a DMM. If so D206 is leaky.

Drum servo slow to lock: Drum discriminator adjustment potentiometer R463 is noisy.

Intermittent stopping in rewind/review: C1 across the start sensor is short-circuit.

Intermittent stopping and reverting to rewind in play/fast forward: C1 across the end sensor is short-circuit.

Machine dead with no clock display or function lights: Check whether circuit protector CP2 on the servo/logic PCB is open-circuit.

Stops intermittently in play or record: Replace the take-up reel sensor (optocoupler).

Models V65B/66B

Machine won't switch on – channel lights only: If the switched 5V and 12V supplies are low, check D3. Note that when this diode is only slightly leaky the machine will work but the counter runs in stop. If there's no switched 5V supply at pin 6 of CN3, CP4 is open-circuit.

No standby mode with the take-up spool and capstan running: If there are no switched 5V and 12V supplies and pin 9 of CN3 (CTL in) is at 3.2V instead of 1.8V, IC602 is faulty.

Intermittent drum rotation: Check for a dry-joint at Q1.

No clock display: If the –30V supply is missing, fusible resistor R2 in the power supply is open-circuit.

Half loads then unloads: D408 leaky.

Drum doesn't rotate but twitches backwards and forwards: D408 leaky.

Intermittently ejects and switches off: Replace loading mode sensor part no. 70673470.

Remote control unit doesn't work when near an ordinary light: Add an extra IR filter. Details available from Toshiba Technical

No record, o.k. on OTR and remote: IC101 faulty.

Intermittent stopping in rewind/review/play/fast forward: See notes on these faults under Models V55B/V57B.

Drum runs backwards: R501 open-circuit and D408 leaky.

No CTL pulse amplification (TP401): C405 is open-circuit.

Plays for three seconds then stops, with counter not working: Replace the take-up reel sensor.

Intermittent recorded sound: See notes under Models V55B/V57B.

Models V71B/73B

Earthing screw problem: Always ensure that an earthing screw is fitted to the reel motor plate to prevent static charge from the reel pulley. This charge can damage the following i.c.s on the logic/servo PCB.

Servo chip IC501: Symptoms no servo lock in record (unlocked head switching point) and no playback servo control (varying speed and poor tracking).

Logic chip IC601: Symptoms no fast forward or reverse reel rotation because of incorrect logic levels at pins 19 and 20. Note: When replacing a TMP4746N5758 chip with a TMP4746N5759, remove and discard the logic-2 unit fitted to the i.c.

Loading drive chip IC602: Symptoms no motor functions, the power supply shuts down after ten seconds and IC602 draws excessive current (the motor +B and switched 12V supplies are over-current sensed).

Reel switching chip IC603: Symptoms no reel rotation in any mode. The i.c. may show signs of overheating, and drive transistor Q625 should be checked.

Reel sensor chip IC604: Symptoms no fast forward/rewind tape count, returns to the stop mode; no play/record tape count, returns to the stop mode and the power supply shuts down.

Cam switch faults: The following very intermittent faults can be caused by a defective cam switch. (1) Fast play operation with pinch roller not engaged (sound is fast). (2) Runs fast in the record mode, hence playback is slow. (3) When review is selected the machine goes to pause. (4) Arms stop in the half-loaded position. The switch is part no. 70901769.

Reel motor fault: A defective reel motor can be the cause of intermittent stopping in play or record. In the play mode a new reel motor should take a current of 90mA (350mA across R643). The take-up torque will then be correct.

Servicing note: If a machine is operated with the cassette housing removed and not earthed, (1) the auto switch won't work, (2) power on inserts a tape but the power supply then shuts down, (3) power on ejects a tape then reinserts it and the power supply shuts down.

Models V71B/73B/81B/83B/85B/86B/93B, DV80B/90B

To reduce mechanical noise a new head drum earth brush, part no. 70903022, was introduced.

To overcome reel idler stop post damage, a new stop post assembly, part no. 70901865, was introduced. Fitting instructions are available from Toshiba Technical.

Models V81B/83B/85B/86B/DV80B

Intermittent stopping in the play/record modes: Faulty reel motor – this is more common with Model V83B.

Intermittent cam switch problems: A modified cam switch was introduced.

Low-gain E-E signals in weak reception areas: Readjust the r.f. a.g.c. control R51.

Won't accept a cassette and returns to standby after ten seconds with the cassette indicator flashing: Replace timer chip ICX01.

Failure of F803: Cause is probably poor F802 fuseholder contact or a dry-joint at the junction of D801/2/chassis.

When the machine is switched on tape is immediately loaded around the drum then the machine returns to standby: Check for dry-joints at the cam switch socket on the main PCB and at the cam switch pull-up resistors.

Models V93B/DV90B

No display, no E-E operation (power on/off o.k.): Circuit

protector ZL62 on the timer-2 PCB is open-circuit. Check the inside of the d.c./d.c. converter Z802 as the small metal cap on the transformer can become unglued and fall off, causing a short-circuit.

Intermittent stopping in play/record: Replace the reel motor.

Patterning with E-E signals and recordings: Check the adjustment of the r.f. a.g.c. control.

No cassette insertion, no test signal: F804 (1.6A) is open-circuit.

Models V110B/210B

Picture pulses in the E-E mode: Replace the 2.4V back-up battery XK03 on the key display PCB (part no. 70010166).

Model V211B

Won't accept tapes: Replace faulty U2561B FG/CTL pulse amplifier chip IT18, part no. 70010166.

Models V212B/312B/412B

Failure to erase the previous sound track and slight coloured patterning on recorded pictures: This is a fairly common condition that may be permanent or intermittent. If the fault is permanent, you might find that RL02 (10 Ω) is open-circuit and that transistor TL01 (BC337) is short-circuit. Whether the fault is permanent or intermittent, the following steps should be taken: fit replacement kit part no. 70903796, change the value of RT102 from 56k Ω to 39k Ω (part no. 24872393), and improve the connections at the full erase head plug and socket by soldering the wires directly to the terminals at the back of the head.

No E-E or playback pictures: Replace the MC14094BD shift register chip IW20, part no. 70010981.

Slow, jerky tape ejection. Tape reaches front flap, stops then reloads, or may stop during the unloading cycle: Loading motor has dead spots on its commutator. Test by removing the belt. Motor part no. is 70011062.

No playback colour, record colour o.k.: Standby 12V supply is low at 9.6V because the 10V zener diode DP86 is faulty and the 27 Ω resistor RP86 is open-circuit. Replace these items, part nos. 70010959 (DP86) and 70041074 (RP86).

No E-E or playback sound and will not stop on station when search tuning: Audio mute is activated because of no field sync pulses at pin 31 of IA40. Replace the TDA8128 field sync pulse processing chip IA01, part no. 70010967.

No functions, goes to standby after two minutes: Replace cam 1 photosensor GT22, part no. 70010960.

Power supply tripping after half an hour: Replace the 6.2V zener diode DP08, part no. 70010958.

Snaps tape in rewind/fast forward, with no counter operation in these modes: No FG output at pin 15 of the U2565B CTL/FG pulse amplifier chip IT40 in fast forward and rewind. Replace IT40, part no. 70010979.

Model V300B

No display, no E-E outputs, playback o.k.: Circuit protector Z803 is open-circuit. D.C.-d.c. converter Z801 (logic PCB) may be shorted because of high output from IC820 (power 2). If the +6.5V supply is o.k., check whether the small metal cap on the transformer in Z802 has become unglued and fallen off, causing a short (see same symptoms under Models V93B/DV90B).

Intermittent audio erasure: The two-wire lead at either the full erase head PCB or the audio-control-erase head PCB has poor plug-socket connections.

Model V312B

Picture continually switches between play and E-E in the playback mode: Cause is corrupt control data from the servo chip IT01 to the shift register chip IW85. Replace IT01, part no. 70011398.

Model V411B

Intermittent random switching between SP and LP in the play mode: Replace the U2561B FG/CTL pulse amplifier chip IT10, part no. 70010166 (PG waveform at pin 11 has superimposed hum).

Model V703B

No test signal and no playback: Replace the ICP-N5 circuit protector ZP681, part no. 23118122. When this goes open-circuit the ever 5V supply is missing at Q688 and Q685.

Models V703B/813B

Installation problem with the Amstrad SRD400 satellite receiver: Under the following conditions it's not possible to make recordings from the receiver: (1) full scart connection using the VCR for loop-through; (2) record mode selected using line input LI; (3) TV/VTR switch is in the VTR position; (4) the sound and picture are being monitored. All you get is black and white lines with no sound. This is because, when pin 8 is enabled, the SRD400's scart socket can be used to connect a decoder: with the TV/VTR switch set to VTR the VCR supplies a +12V control voltage to both scart sockets. The remedy is to disconnect pin 8 of the scart lead between the VCR and the SRD400 or leave the TV/VTR switch in the TV position and, if you want to monitor the recording, do so by using the input select button on the TV handset.

VIEWDATA RETURNS £6 made by Tandata, includes 1200.75 modem, k/bd, RGB and comp o/p, printer port. No PSU. £6 MAG6P7

IBM PC CASE AND PSU Ideal base for building your own PC. Ex equipment but OK. £14.00 each REF: **MAG14P2**

SOLAR POWER LAB SPECIAL You get TWO 6"x6" 6v 130mA solar cells, 4 LED's, wire, buzzer, switch plus 1 relay or motor. Superb value kit just £5.99 REF: **MAG6P8**

SOLID STATE RELAYS Will switch 25A mains. Input 3.5-26v DC 57x43x21mm with terminal screws £3.99 REF: **MAG4P10**

300DPI A4 DTP MONITOR Brand new, TTL/ECL inputs, 15" landscape, 1200x1664 pixel complete with circuit diag to help you interface with your projects. JUST £24.99. REF: **MAG25P1**

ULTRAMINI BUG MIC 6mmx3.5mm made by AKG, 5-12v electret condenser. Cost £12 ea. Our? four for £9.99 REF: **MAG10P2**

RGB/CGA/EGA/TTL COLOUR MONITORS 12" in good condition. Back anodised metal case. £39 each REF: **MAG99P1**

GX4000 GAMES MACHINES returns so ok for spares or repair £9 each (no games). REF: **MAG99P1**

C64 COMPUTERS Returns, so ok for spares etc £9 ref: **MAG99P2**

FUSELAGE LIGHTS 3 foot by 4" panel 1/8" thick with 3 panels that glow green when a voltage is applied. Good for night lights, front panels, signs, disco etc. 50-100v per strip. £25 ref: **MAG25P2**

ANSWER PHONES Returns with 2 faults, we give you the bits for 1 fault, you have to find the other yourself. BT Response 200's £18 ea REF: **MAG18P1**, BT Response 400's £25 ea REF: **MAG25P3** Suitable power supply £5 REF: **MAG5P12**

SWITCHED MODE PSU ex equip, 60w +5v @ 5A, -5v @ 5A, +12v @ 2A, -12v @ 5A 120/220v cased 245x88x55mm IEC input socket £6.99 REF: **MAG7P1**

PLUG IN PSU 9V 200mA DC £2.99 each REF: **MAG3P9**

PLUG IN ACORN PSU 19v AC 14w. £2.99 REF: **MAG3P10**

POWER SUPPLY fully cased with mains and o/p leads 17v DC 900mA output. Bargain price £5.99 ref: **MAG6P9**

ACORN ARCHIMEDES PSU +5v @ 4.4A. on/off sw uncased, selectable mains input, 145x100x45mm £7 REF: **MAG7P2**

GEIGER COUNTER KIT Low cost professional twin tube, complete with PCB and components. £29 REF: **MAG29P1**

SINCLAIR C6 13" wheels complete with tube, tyre and cycle style bearing £6 ea REF: **MAG6P10**

AA NICAD PACK encapsulated pack of 8 AA nicad batteries (tagged) ex equip, 55x32x32mm. £3 a pack. REF: **MAG3P11**

13.8V 1.9A psu cased with leads. Just £9.99 REF: **MAG10P3**

360K 6.25 brand new half height floppy drives IBM compatible industry standard. Just £6.99 REF: **MAG7P3**

PPC MODEM CARDS. These are high spec plug in cards made for the Amstrad laptop computers. 2400 baud dial up unit complete with leads. Clearance price is £5 REF: **MAG5P1**

INFRA RED REMOTE CONTROLLERS Originally made for hi spec satellite equipment but perfect for all sorts of remote control projects. Our clearance price is just £2 REF: **MAG2**

TOWERS INTERNATIONAL TRANSISTOR GUIDE. A very useful book for finding equivalent transistors, leadouts, specs etc. £20 REF: **MAG20P1**

SINCLAIR C6 MOTORS We have a few left without gearboxes. These are 12v DC 3,300 rpm 6" x 4", 1/4" OP shaft. £25 REF: **MAG25**

UNIVERSAL SPEED CONTROLLER KIT Designed by us for the above motor but suitable for any 12v motor up to 30A. Complete with PCB etc. A heat sink may be required. £17.00 REF: **MAG17**

VIDEO SENDER UNIT. Transmits both audio and video signals from either a video camera, video recorder, TV or Computer etc to any standard TV set in a 100' range (tune TV to a spare channel) 12v DC op. Price is £15 REF: **MAG15** 12v psu is £5 extra REF: **MAG5P2**

***FM CORDLESS MICROPHONE** Small hand held unit with a 500' range! 2 transmit power levels. Reqs PP3 9v battery. Tuneable to any FM receiver. Price is £15 REF: **MAG15P1**

LOW COST WALKIE TALKIES Pair of battery operated units with a range of about 200'. Ideal for garden use or as an educational toy. Price is £8 a pair REF: **MAG8P1** 2 x PP3 req'd.

***MINATURE RADIO TRANSCENVERS** A pair of walkie talkies with a range of up to 2 kilometres in open country. Units measure 22x52x155mm. Complete with cases and earpieces. 2x PP3 req'd. £30.00 pair REF: **MAG30**

COMPOSITE VIDEO KIT. Converts composite video into separate H sync, V sync, and video. 12v DC. £8.00 REF: **MAG8P2**

LQ3600 PRINTER ASSEMBLIES Made by Amstrad they are entire mechanical printer assemblies including printhead, stepper motors etc in fact everything bar the case and electronics, a good stripper! £5 REF: **MAG5P3** or 2 for £8 REF: **MAG8P3**

SPEAKER WIRE Brown 2 core 100 foot hank £2 REF: **MAG2P1**

LED PACK of 100 standard red 5mm leds £5 REF: **MAG5P4**

JUG KETTLE ELEMENT good general purpose heating element (about 2kw) ideal for heating projects. 2 for £3 REF: **MAG3**

UNIVERSAL PC POWER SUPPLY complete with flyleads, switch, fan etc. Two types available 150w at £15 REF: **MAG15P2** (23x23x23mm) and 200w at £20 REF: **MAG20P3** (23x23x23mm)

***FM TRANSMITTER** housed in a standard working 13A adaptor! the bug runs directly off the mains so lasts forever why pay £700? or price is £26 REF: **MAG26** Transmits to any FM radio.

***FM BUG KIT** New design with PCB embedded coil for extra stability. Works on any FM radio. 9v battery req'd. £5 REF: **MAG5P5**

***FM BUG BUILT AND TESTED** superior design to kit. Supplied to detective agencies. 9v battery req'd. £14 REF: **MAG14**

TALKING COINBOX STRIPPER originally made to retail at £79 each, these units are designed to convert and ordinary phone into a payphone. The units have the locks missing and sometimes broken hinges. However they can be adapted for their original use or used for something else? Price is just £3 REF: **MAG3P1**

100 WATT MOSFET PAIR Same specs as 2SK343 and 2SJ413 (8A, 140v, 100w) 1 N channel, 1 P channel. £3 a pair REF: **MAG3P2**

VELCRO 1 metre length of each side 20mm wide (quick way of fixing for temporary jobs etc) £2 REF: **MAG2P3**

MAGNETIC AGITATORS Consisting of a cased mains motor with lead. The motor has two magnets fixed to a rotor that spin round inside. There are also 2 plastic covered magnets supplied. Made for remotely stirring liquids! you may have a use? £3 each REF: **MAG3P3**

BULL'S BULLETIN BOARD

100MHZ DUAL TRACE OSCILLOSCOPES JUST £259 RING FOR DETAILS

MASSIVE

WAREHOUSE CLEARANCE FANTASTIC £20.00 REDUCTION REFURBISHED PC BASE UNITS COMPLETE WITH KEYBOARD FROM ONLY £29.00 AMSTRAD 1512 BASE UNITS GUARANTEED PERFECT WORKING ORDER.

A LOW COST INTRODUCTION TO THE HOME COMPUTER MARKET.

AMSTRAD 1512SD

1512 BASE UNIT, 5.25" FLOPPY DRIVE AND KEYBOARD. ALL YOU NEED IS A MONITOR AND POWER SUPPLY. Was £49.00

NOW ONLY £29.00 REF: MAG29

AMSTRAD 1512DD

1512 BASE UNIT AND KEYBOARD AND TWO 5.25" 360K DRIVES. ALL YOU NEED IS A MONITOR AND POWER SUPPLY. Was £69.00

NOW ONLY £39.00 REF: MAG39

SOLAR POWER PANELS

3FT X 1FT 10WATT GLASS PANELS 14.5v/700mA NOW AVAILABLE BY MAIL ORDER £33.95

(PLUS £2.00 SPECIAL PACKAGING CHARGE)

TOP QUALITY AMORPHOUS SILICON CELLS HAVE ALMOST A TIMELESS LIFESPAN WITH AN INFINITE NUMBER OF POSSIBLE APPLICATIONS, SOME OF WHICH MAY BE CAR BATTERY CHARGING, FOR USE ON BOATS OR CARAVANS, OR ANYWHERE A PORTABLE 12V SUPPLY IS REQUIRED. REF: **MAG34**

FREE SOFTWARE!

Brand new, UNUSED top quality Famous brand licensed software discs. Available in 5.25" D5DD or 5.25" HD only. You buy the disk and it comes with free BRAND NEW UNUSED SOFTWARE. We are actually selling you the floppy disc for your own "MEGA CHEAP" storage facilities, if you happen to get software that you want/need/like as well..... you get a "MEGA BARGAIN" too!

D5DD PKT18 £2.99 REF: **MAG37** PKT100 £16.00 REF: **MAG16**

*****WE BUY SURPLUS STOCK*****

TURN YOUR SURPLUS STOCK INTO CASH. IMMEDIATE SETTLEMENT. WE WILL ALSO QUOTE FOR COMPLETE FACTORY CLEARANCE.

1994 CATALOGUE.

PLEASE SEND 45P, A4 SIZED SAE FOR YOUR FREE COPY. MINIMUM GOODS ORDER £5.00 TRADE ORDERS FROM GOVERNMENT, SCHOOLS, UNIVERSITIES, & LOCAL AUTHORITIES WELCOME. ALL GOODS SUPPLIED SUBJECT TO OUR CONDITIONS OF SALE AND UNLESS OTHERWISE STATED GUARANTEED FOR 30 DAYS. RIGHTS RESERVED TO CHANGE PRICES & SPECIFICATIONS WITHOUT PRIOR NOTICE. ORDERS SUBJECT TO STOCK. QUOTATIONS WILL ONLY BE GIVEN FOR QUANTITIES HIGHER THAN THOSE STATED.

*SOME OF OUR PRODUCTS MAY BE UNLICENSABLE IN THE UK

BULL ELECTRICAL

250 PORTLAND ROAD HOVE SUSSEX BN3 5QT
MAIL ORDER TERMS: CASH PO OR CHEQUE WITH ORDER PLUS £3.00 POST PLUS VAT.

PLEASE ALLOW 7-10 DAYS FOR DELIVERY

TELEPHONE ORDERS WELCOME

TEL: 0273 203500

FAX: 0273 323077



TOP QUALITY SPEAKERS Made for Hi Fi televisions these are 10 watt 4R Jap made 4" round with large shielded magnets. Good quality general purpose speaker. £2 each REF: **MAG2P4** or 4 for £6 REF: **MAG6P2**

TWEETERS 2" diameter good quality tweeter 140R (ok with the above speaker) 2 for £2 REF: **MAG2P5** or 4 for £3 REF: **MAG3P4**

AT KEYBOARDS Made by Apricot these quality keyboards need just a small modification to run on any AT, they work perfectly but you will have to put up with 1 or 2 foreign keycaps! Price £6 REF: **MAG6P3**

XT KEYBOARDS Mixed types, some returns, some good, some poor etc but all good for spares! Price £2 each REF: **MAG2P6** or 4 for £6 REF: **MAG6P4**

PC CASES Again mixed types so you take a chance next one of the pile £12 REF: **MAG12** or two the same for £20 REF: **MAG20P4**

COMMODORE MICRODRIVE SYSTEM mini storage device for C64's 4 times faster than disc drives, 10 times faster than tapes. Complete unit just £12 REF: **MAG12P1**

SCHOOL STRIPPERS We have quite a few of the above units which are 'returns' as they are quite comprehensive units they could be used for other projects etc. Let us know how many you need at just 50p a unit (minimum 10).

HEADPHONES 16P These are ex Virgin Atlantic. You can have 8 pairs for £2 REF: **MAG2P8**

PROXIMITY SENSORS These are small PCB's with what look like a source and sensor LED on one end and lots of components on the rest of the PCB. Complete with flyleads. Pack of 5 £3 REF: **MAG3P5** or 20 for £8 REF: **MAG8P4**

SWOOPERS EAR? Original made to clip over the earpiece of telephone to amplify the sound-it also works quite well on the cable running along the wall! Price is £5 REF: **MAG5P7**

DOS PACKS Microsoft version 3.3 or higher complete with all manuals or price just £5 REF: **MAG5P8** Worth it just for the very comprehensive manual! 5.25" only.

DOS PACK Microsoft version 5 Original software but no manuals hence only £3 REF: **MAG3P6** 5.25" only.

FOREIGN DOS 3.3-German, French, Italian etc. £2 a pack with manual. 5.25" only. REF: **MAG2P9**

CTM644 COLOUR MONITOR Made to work with the CPC464 home computer. Standard RGB input so will work with other machines. Refurbished £59.00 REF: **MAG59**

P/R DETECTOR Made by famous UK alarm manufacturer these are hi spec, long range internal units. 12v operation. Slight marks on case and unboxed (although brand new) £8 REF: **MAG8P5**

WINDUP SOLAR POWERED RADIO AM/FM radio complete with hand charger and solar panel £14 REF: **MAG14P1**

COMMODORE 64 TAPE DRIVES Customer returns at £4 REF: **MAG4P9** Fully tested and working units are £12 REF: **MAG12P5**

COMPUTER TERMINALS complete with screen, keyboard and RS232 input/output. Ex equipment. Price is £27 REF: **MAG27**

MAINS CABLES These are 2 core standard black 2 metre mains cables fitted with a 13A plug on one end, cable the other. Ideal for projects, low cost manufacturing etc. Pack of 10 for £3 REF: **MAG3P8** Pack of 100 £20 REF: **MAG20P5**

SURFACE MOUNT STRIPPER Originally made as some form of high frequency amplifier (main chip is a TSA5511T 1.3GHz synthesiser) but good stripper value, an excellent way to play with surface mount components £1.00 REF: **MAG1P1**

MICROWAVE TIMER Electronic timer with relay output suitable to make enlarger timer etc £4 REF: **MAG4P4**

MOBILE CAR PHONE £5.99 Well almost complete in car phone excluding the box of electronics normally hidden under seat. Can be made to illuminate with 12v also has built in light sensor so display only illuminates when dark. Totally convincing! REF: **MAG6P6**

ALARM BEACONS Zenon strobe made to mount on an external bell box but could be used for caravans etc. 12v operation. Just connect up and it flashes regularly! £5 REF: **MAG5P11**

FIRE ALARM CONTROL PANEL High quality metal cased alarm panel 360x165x80mm. With key. Comes with electronics but no information. sale price 7.99 REF: **MAG8P6**

SUPER SIZE HEATSINK Superb quality aluminium heatsink. 365 x 183 x 61mm. 15 fins enable high heat dissipation. No holes! sale price £5.99 REF: **MAG6P11**

REMOTE CONTROL PCB These are receiver boards for garage door opening systems. You may have another use? £4 ea REF: **MAG4P5**

6"X12" AMORPHOUS SOLAR PANEL 12v 155x310mm 130mA. Bargain price just £5.99 ea REF: **MAG6P12**

FIBRE OPTIC CABLE BUMPER PACK 10 metres for £4.99 ref: **MAG5P13** ideal for experimenters! 30m for £12.99 ref: **MAG13P1**

LOPTX Line output transformers believed to be for hi res colour monitors but useful for getting high voltages from low ones £2 each REF: **MAG2P12** bumper pack of 10 for £12 REF: **MAG12P3**

SHOP OPEN 9-5.30 SIX DAYS A WEEK

PORTABLE RADIATION DETECTOR £49.99

A Hand held personal Gamma and X Ray detector. This unit contains two Geiger Tubes, has a 4 digit LCD display with a Piezo speaker, giving an audio visual indication. The unit detects high energy electromagnetic quanta with an energy from 30K eV to over 1.2M eV and a measuring range of 5-9999 UR/h or 10-99990 Nr/h. Supplied complete with handbook.

REF: **MAG50**



FUZZY PLAYBACK?

EURAS SYSTEM WILL BRING IT INTO FOCUS

Video technology is changing fast. New models get introduced with alarming regularity, each with the latest enhancement. So it's not surprising to find models and faults you've not encountered before.


The problem is you can spend costly, unchargeable time searching for elusive faults, which is where Euras System can help.

The Euras System is Europe's largest repair tips database for Video, Television and CD.

With over 120,000 repair tips for 14,000 models from 270 manufacturers you are sure to find the solution quickly. And because it is frequently updated, it always covers the latest models.

For a FREE demonstration diskette to run on your PC or details of Euras System in manual form, clip the coupon or phone **0272 860900**.

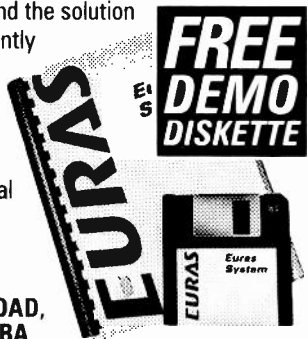EURAS INTERNATIONAL LTD
EURAS HOUSE, 51 BRISTOL ROAD,
KEYNSHAM, BRISTOL, BS18 2BA



EURAS

TV5/94C

Solutions at your fingertips

PLEASE SEND ME A FREE DEMONSTRATION DISKETTE
PLEASE SEND ME DETAILS OF EURAS SYSTEM IN MANUAL FORM

NAME _____

TITLE _____

COMPANY _____

ADDRESS _____

POSTCODE _____

RENTAL FINANCE

Expand your CTV and VCR rental business with no capital outlay and increase your profitability.

Broughfame has the solution and their rental finance plan will provide facilities from £2,500 upwards.

For further details ring or write to Bob Wickham at the address below:

BROUGHFAME LIMITED

39 SOUTH STREET, TARRING

WORTHING, WEST SUSSEX BN14 7LG

TEL: Worthing (0903) 821020

FAX: Worthing (0903) 821194

WE HAVE THE WIDEST CHOICE OF USED OSCILLOSCOPES IN THE COUNTRY

TEKTRONIX 7000 SERIES OSCILLOSCOPES AVAILABLE FROM £200 Plug-ins sold separately		
TEKTRONIX 2235 Dual Trace 100MHz Delay Sweep	£800	
TEKTRONIX 475 Dual Trace 200MHz Delay Sweep	£550	
TEKTRONIX 465B Dual Trace 100MHz Delay Sweep	£500	
TEKTRONIX 465 Dual Trace 100MHz Delay Sweep	£450	
TEKTRONIX SC504 Dual Trace 80MHz in TM503B As new	£500	
H.P. 1740A Dual Trace 100MHz Delay Sweep	£350	
TEKTRONIX 455 Dual Trace 50MHz Delay Sweep	£400	
HTACHI V650F Dual Trace 60MHz Delay Sweep	£400	
HAMEG 405 Dual Trace 60MHz Delay Sweep	£400	
PHILIPS PM3217 Dual Trace 50MHz Delay Sweep	£400	
GOULD OS3351 Dual Trace 30MHz TV Monitor Oscilloscope	£375	
TRIO CS130 Dual Trace 30MHz Delay Sweep	£200	
GOULD OS1100 Dual Trace 20MHz	£160	
WATSU SS5702 Dual Trace 20MHz	£225	
GOULD OS300 Dual Trace 20MHz	£200	
GOULD OS2598 Dual Trace 15MHz	£125	
TEKTRONIX 2430 Dual Trace 150MHz Digital Storage	£1750	
TEKTRONIX 466 Dual Trace 100MHz Delay Sweep Analogue Storage	£450	
H.P. 1741A Dual Trace 100MHz Delay Sweep Analogue Storage	£450	
GOULD OS4000 Dual Trace 10MHz Digital Storage	£225	
THIS IS JUST A SAMPLE - MANY OTHERS AVAILABLE		
PHILIPS PM5193 Programmable Synthesiser/Function Generator 0.1MHz-50MHz IEEE-488 As new	£1500	
MARCONI 2018 Synthesised AM/FM Sg Gen 80KHz - 520MHz	£800	
H.P. 8640B Signal Generator 20KHz - 102MHz (opts 001/002/003)	£1500	
H.P. 8620C Sweep Oscillator with 86245A 9 - 12.4GHz	£750	
H.P. 8620C Sweep Oscillator with 86220A 10 - 1300MHz	£750	
RACAL 9081 Synthesised AM/FM Sg Gen 1.5 - 520MHz	£600	
LYONS PG73N Pulse Gen PRF 1Hz - 20MHz 5 nanoseconds	£150	
LYONS PG71N Pulse Gen PRF 1Hz - 5MHz 10 nanoseconds	£75	
FARNELL PG101 Pulse Gen 100ns 0-9MHz (Sec 1Hz)	£125	
RACAL 9301A True RMS Millivoltmeter 1KHz - 1.5GHz	£300	
KIKUSUI AMV23 AC Dual CH Voltmeter 10KHz - 500KHz	£100	
LEADER PMV181A AC VPM 5Hz - 1MHz	£75	
MARCONI TF3208 Mod Meter AM/FM 4MHz - 1.3GHz	£100	
PHILIPS PM6309 Distortion Meter 0.1019	£300	
DYMAR 2065 Distortion Factor Meter 0.019	£150	
MARCONI TF893B Audio Power Meter Serial	£250	
SPECTRUM ANALYSERS		
HP 141T with 8555A & IF plug-in 10MHz-18GHz	£1800	
HP 141T with 8554B & 8552B 500KHz - 250MHz	£1300	
HP 140T with 8554L & 8552A 500KHz - 250MHz	£1000	
HP 141T with 8556A & 8552B 20KHz-300KHz	£1000	
HP 140T with 8553L & 8552A 1KHz-110MHz	£800	
HP 182C with 8558B 100KHz-1500MHz	£1500	
HP 3582A 0.01Hz-2.55KHz	£2000	
MARCONI TF 2370 1KHz-110MHz	£1500	
FARNELL ISOLATING TRANSFORMERS GU500 240V 500VA, un-used		£50
Isolating Transformer 500VA, un-used	£30	
DATRON 1061A - 6 1/2 digit Autocal Multimeter with True RMS AC Current		£1250
DATRON 1065 - 5 1/2 digit Autocal Multimeter AC/DC/Ohms with IEEE	£600	
HEWLETT PACKARD 3490A Bench Multimeter 5 1/2 digit AC/DC/Ohms	£200	
PHILIPS PM2534 Multi Function DMM 6 1/2 digit with GPIB/IEEE	£450	
SOLARTRON 7150 - 6 1/2 digit DMM with IEEE	£400	
MARCONI Digital Frequency Meter 2430A 10KHz-80MHz	£125	
MARCONI Digital Frequency Meter 2431A 10KHz-200MHz	£150	
MARCONI Universal Counter Timer 2437 DC-100MHz	£175	
MARCONI Universal Counter Timer 2438 DC-520MHz	£225	
BLACK STAR Jupiter 500 Sine/Sq/Tri 0.1Hz - 500KHz	£70	
FEEDBACK FG600 Sine/Sq/Tri 0.01Hz - 100KHz	£60	
THANDAR TG101 Func. Gen. 0.02Hz - 200KHz Sine/Sq/Tri	£60	
TTI	£60	
MULTIMETERS Handheld M2355-32 ranges AC/DC 10Amps Diode/Transistor Tester, Freq. Counter	£32.50	
SOLARTRON/SCHLUMBERGER 1250 Frequency Response Analyser		£3500
HP 8690B Sweep Osc with 86974 Plug-in 26.5-40GHz	£300	
RACAL/DANA RF Power Meter 9104	£400	
RACAL/DANA 9341 Databridge Automatic LCR & Q	£350	
WAYNE KERR 8905 Automatic Precision Bridge 0.05%	£900	
WAYNE KERR 8424 Digital Component Meter LCR	£125	
WAYNE KERR 8605 Automatic Component Bridge 0.1%	£350	
FARNELL PSU TV570Hz, 70V 5A/30V 10A	£300	
FARNELL PSU H4025 0-40V, 0-25 Amps Metered	£400	
FARNELL PSU L306 0-30V, 0-5 Amps Metered	£80	
FARNELL B3020 0-30V, 20 Amps	£250	
FARNELL B3010 0-30V, 10 Amps	£200	
H.P. 6235A 0-40V/0-1.5 Amps Metered	£130	
H.P. 6209B 0-320V, 0.0-1 Amps Metered	£125	
BRANDENBURG 472R PSU +/- 2kV	£200	
MARCONI TF2700 Universal LCR Bridge Battery from	£150	
AVO Valve Tester CT160	£75	
FARNELL LAS20 RF Power Amp 1.5-520MHz 300W	£175	
RACAL 9100 Absorption Wattmeter 1MHz-1GHz 3W	£100	
NEW EQUIPMENT		
HAMEG OSCILLOSCOPE HM1005 Triple Trace 100MHz Delay Timebase	£847	
HAMEG OSCILLOSCOPE HM1604 Dual Trace 60MHz Delay Sweep	£653	
HAMEG OSCILLOSCOPE HM203.7 Dual Trace 20MHz Component Tester	£363	
HAMEG OSCILLOSCOPE HM205 3 Dual Trace 20MHz Digital Storage	£653	
All other models available - all oscilloscopes supplied with 2 probes		
BLACK STAR EQUIPMENT (P&P all units £5)		
APOLLO 10 - 100MHz Counter Timer Ratio/Period/Time Interval etc.	£222	
APOLLO 100 - 100MHz (As above with more functions)	£225	
METOR 100 FREQUENCY COUNTER 100MHz	£119	
METOR 600 FREQUENCY COUNTER 600MHz	£145	
METOR 1000 FREQUENCY COUNTER 1GHz	£189	
BURTON 500 FUNCTION GENERATOR 0Hz-500Hz Sine/Sq/Tri	£119	
ORION COLOUR BAR GENERATOR Pal/TV/Video	£229	
All other Black Star Equipment available		
OSCILLOSCOPE PROBES		
Switchable x1 x10 (P&P £3)	£12	

Used Equipment - Guaranteed. Manuals supplied if possible. This is a VERY SMALL SAMPLE OF STOCK. SAE or telephone for list. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to Total of Goods and Carriage.

STEWART OF READING

110 WYKEHAM ROAD, READING, BERKS RG6 1PL
Telephone: 0734 268041 Fax: (0734) 351696
Callers Welcome 9am-5.30pm Mon-Fri (until 8pm Thurs)



**COMPONENTS
For TV ★ Video
Audio ★ Computer**

THIS IS JUST A SMALL SAMPLE OF STOCK
We can supply spares for many makes of equipment. **WRITE**
(Encl. s.a.e. please) or **PHONE**
FOR A 'PRICE & AVAILABILITY'
on your requirements. **0452 526883**

IC SELECTION

AN5753	£3.68	TA7280P	£4.99
BA6109	£1.35	TA7281P	£5.21
A738912/P	£7.74	TA7288P	£3.59
BA4236L	£3.92	TA7324P	£2.69
BA5408	£2.90	TA8400P	£4.95
BA9259N	£2.99	TA8100K	£4.87
CA741CE	£0.29	TB4530	£1.74
COP6818AE	£7.24	TA7343AP	£3.49
CHX62A	£3.55	TB4810P	£1.16
DS1488N	£1.85	TB4810S	£1.62
DS75150N	£1.85	TC4940	£3.33
DS75154N	£1.85	TD1001B	£2.86
H1113	£2.88	TDA1020	£2.64
HA1137W	£3.61	TDA1035T	£2.59
HA12006	£3.09	TD1170D	£4.98
HA12413	£4.75	TD1180P	£3.49
HA13007	£5.12	TD1516C	£4.63
HE3645SP	£15.18	TD1198A	£2.06
KA7217AP	£2.47	TD2003	£2.44
LA3160	£2.28	TD2541	£2.49
LA3361	£1.79	TD2593	£3.45
LA4490	£3.86	TD3653	£3.33
LA7016	£2.99	TD4420	£2.71
LA7910	£2.62	TD4510	£3.75
LM1203N	£10.99	TD4600-2	£2.95
LM3309	£2.55	TD4601	£2.49
LM853	£1.79	TD4890	£2.15
M54544L	£3.38		
M54548P	£5.29		
MA9846P	P.O.A.		
MA9849H	£2.37		
MB61416-12	£4.99		
MK4564N	£2.45	TD48140	£3.49
MP4604	£5.94	TD48170	£3.47
MSM8242B	£1.77	TEA2000	£4.33
MC1377P	£7.32	TL431	£1.85
MC14052BCP	£0.78	TMP47C	P.O.A.
NE555CDP	£0.29	UM8272A	£14.09
PE25A	£2.85	UPC1277	£4.23
PC713V	£2.99	UPC1378H	£2.45
SA1124	£3.88	UPC1397C	£3.94
SD9420CAC	£15.68	UPD8039LC	£12.38
STK4332	£7.71	Z64003APS	£4.63
STK5451	£3.29	14DN476G	£19.25
STK5482	£6.99	27C256-200	£2.98
TA7226P	£3.76	4116-2N	£1.89

**MANY MORE
FROM STOCK**

COMPUTER SPARES

AMSTRAD		Serv. Manual CM11342	£8.51
Cap. Capacitor 2200p/4Kv	£1.85	Power Switch CM9C73	£8.63
Printer Armature	£4.20		
(PCV) 95121	£4.95		
User Manual (CPC464)	£10.95		
Serv. Manual (PCW9512)	£14.99		
Keyboard (CPC464)	£29.99		
PHILIPS		Serv. Manual CM8833	£7.82
Serv. Manual BM7513	£3.49	MONITOR LEAD	£14.99
Serv. Manual CM8833	£7.82	Amiga to Scart L/P	£8.29
Serv. Suppl. CM38xx	£3.00		

TRANSISTORS

2SA1706	£1.85	2SK301	£1.85
2SA2331	£1.59	BUV48A	£4.99

TV/MONITOR LINE OUTPUT TRANSFORMERS

AMSTRAD, IBM, DIGITAL, etc			
COMMODORE 1084-P/SP etc			
PHILIPS CM6533/CM8833 etc			
PHILIPS CM11342/62 (CM8833 MK II)			
Ferguson TX90 14" 90"			
Ferguson TX100 20" 90"			
Ferguson TX100 22"/26"/110"			
Ferguson TX100 51cm FST			
GEC C2089H/90H/C2288 to 2291H/C2294H			
Hitachi CPT1463/CPT1623/24/26/44/46			
Hitachi CPT2308/46/79/78/CPT2234/36/CPT2246/78			
Panasonic TL14567/594F			
Saisho/Matsui (Supply No. on L.O.T.)			

AUDIO SPARES

AMSTRAD MX200/CDX400 (FUNAI) CASSETTE DOOR	£3.64
B.T. FREEWAY TELEPHONE - REPLACEMENT AERIAL	£3.65
PHILIPS CST427 SERVICE MANUAL	£4.50
PHILIPS D9458 SERVICE MANUAL	£3.49
SHARP RGF278, 281, 284 MAIN BELT	£1.40
TOSHIBA STU2L MAINS TRANSFORMER	£9.99

TV SPARES

AMSTRAD TVR2 SERVICE MANUAL	£17.39
GEC/HITACHI FRAME MODULE HM6251	£9.29
PHILIPS 96009 Deg. POSISTOR (White)	£1.34
GOLDSTAR C15436/14441/01/2152/2172X 0/0 SWITCH	£6.49
SAMSUNG C1537V/CX558W/T. ON/OFF SWITCH	£8.05

VIDEO SPARES

Large range of Video Heads, Idlers, Belt Kits, Pinch Rollers from stock - plus much, much more. Please contact us.
We also stock REMOTE CONTROLS + Many General Components.

We are pleased to serve both the Trade and End User.
DO NOT ADD VAT TO THE PRICES SHOWN - BUT PLEASE ADD £1.25 P&P

**HOME COMPUTER CHIPS
★ SPECIAL OFFER ★**

CO25913	DMA (ST)	(1-1)	£32.99	(5+)
KEYBOARD	CPU (ST)		£23.50	
6569	VIC (C64)		£13.49	£9.99
TM54532N1.4	DRAM (Spec)		£0.99	£0.89
ZX8302	ULA (QL)		£6.49	£4.99
ZX8401	ULA (Spec)		£5.44	£4.89
40054	ROM (+2)		£11.69	£9.99
74LS00	TTL (QL)		£0.15	£0.10
74LS157	TTL (Spec)		£0.30	£0.25
74LS245	TTL (QL)		£0.39	£0.35

All items subject to availability - Prices can change without notice.

ORDER BY POST OR PHONE

We accept payment
by **VISA**, **Access**,
DELTA, **SWITCH**,
Cheque or **P.O.**

**MAIL ORDER ONLY to:
MARAPET (TVF)
1 HORNBEAM MEWS
GLOUCESTER GL2 0UE**

FREE

TV and VCR

COMPONENTS CATALOGUE

HUGE RANGE OF SPARES

COMPETITIVE PRICES

PLUS

TV TUBES

**RE-PROCESSED
NEW
B GRADE**

Over 150 Types in Stock
VISTA are BSI approved

**FAST DELIVERY
EFFICIENT SERVICE**



FOR CUSTOMER CARE AND SERVICE CALL

TUBES: 0429 837100

COMPONENTS: 0429 838057

FAX: 0429 837101



Vista Electronics Ltd

Unit 1B, Wingate Grange Industrial Estate, Wingate, Co. Durham, TS28 5AH.

EST. 1977

J.W. HARDY
YOUR ONE-STOP-SHOP

FOR THESE FINE BRANDED PRODUCTS
- AND SO MUCH MORE . . .

Wolsey SMATV

DIAMOND AERIALS UHF/FM

GLOBAL COMMUNICATIONS FIRST IF, SMATV

J.W. HARDY communications UHF AERIALS
UHF AMPLIFIERS

Labgear Cablevision SMATV

LENSON HEATH SATELLITE
ANTENNA

PACE SATELLITE
RECEIVERS,
DECODERS **PALCOM** SATELLITE
RECEIVERS

PROMAX TEST EQUIPMENT

Spit fixings BOLTS
PLUGS **mungo** BOLTS
PLUGS

Telestet SMATV
TRIAx U.K. UHF/VHF
AERIALS **TOWER** CLIPS

UNI-FIX CLIPS **VOLEX
RAYDEX** COAX CABLES

● WE PROVIDE FULL TECHNICAL ASSISTANCE AND SERVICE BACK UP
ON ALL OUR PRODUCTS
● SMATV - DISH SHARING - DESIGN CONSULTANT

Trace Price List available to bona fide TV Aerial and Satellite Dealers
on proof of trading.

J.W. Hardy, 231 Station Road, Stechford,
Birmingham B33 8BB. Telephone: 021-784 8478

JUST



Each Month

£2.50

FAULT
FACT
FILES

Brings You all this.....

- ◆ At least 150 TV & VCR faults, colour coded and collated for fast, easy access.
- ◆ Equivalent Guides for TV Chassis and VCR Decks.
- ◆ Time Saving tips - complex procedures made simpler
- ◆ Money Saving tips - reduce repair and spares costs
- ◆ Substantial Discounts when using the Vision-On Help-Desk

Vision On

For more information and samples send a SAE

(TV1), 16 Hillview Park, Newtownabbey, BT36 8HW

Payment by cheque/PO/Visa/Mastercard accepted (£30 for 1 Yr minimum) Overseas add £10pa (airmail)


3 GREAT NEW BOOKS!

The Satellite Book

A Complete Guide to Satellite TV Theory and Practice

3rd Edition John Breeds

- ✓ Acknowledged by leading reviewers as the best work of its kind.
- ✓ How to set up a motorised dish in less than 5 mins! All angles given.
- ✓ Includes comprehensive details of new digital TV systems.
- ✓ Written in easy-to-read style with over 300 illustrations on 300 pages of large A4!
- ✓ Covers directly related practical aspects such as tools for the trade, customer care, wall fixing systems, signal meters, cable types, fault-finding, site survey etc!
- ✓ Explains relevant theoretical subjects such as IF distribution, SMATV, Frequency Modulation, EIRP levels, satellite footprints, ASTRA and EUTELSAT satellites, antenna design, link analysis, microwaves, plus lots more!

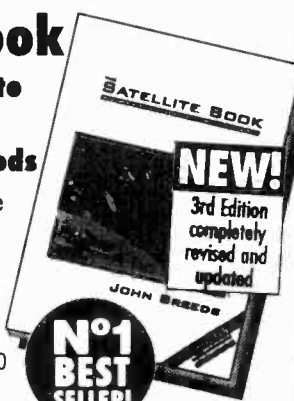

N°1 BEST SELLER!

A bible for the satellite TV industry... includes invaluable hints, tips and tricks of the trade.

Interspace

... All in all most of the information you'll ever need or want to know about satellite television is at your fingertips.

What Satellite

... the most comprehensive, inclusive and informative book ever published on satellite television.

Satellite Trader

ONLY £32

ISBN 1 872567 05 3

Postage:- UK: £2.50 Europe: £5 Rest of World: £15

1994 World Satellite YEARLY by Dr Frank Baylin

- ✓ Affordable standard reference book. Footprints, programming and technician use.
- ✓ 680 pages divided into 4 easy-to-use sections.
- ✓ Detailed information on over 350 worldwide satellites - past, present and planned.

ONLY £59

Postage:- UK: £2.50 Europe: £5 Rest of World: £15



World Satellite Update THE YEAR IN REVIEW

- ✓ Provides latest footprint maps and technical descriptions for the world's newest satellite systems.
- ✓ Includes several feature articles by noted author and satellite expert Mark Long.
- ✓ Complements Mark Long's World Satellite Almanac (also available from Swift).
- ✓ 14 chapters jam-packed with essential, up-to-date information.

ONLY £35

Postage:- UK: £2.50 Europe: £5 Rest of World: £15



Send stamped, addressed envelope for complete list of satellite books, videos and software ...

SWIFT TELEVISION PUBLICATIONS

17 Pittsfield, Cricklade, Wilts, SN6 6AN, England
Tel 44 (0)793 750620 Fax 44(0)793 752399



W.M.T.V.


THE LARGEST INDEPENDENT WHOLESALERS
IN WALSALL – SUPPLIERS OF HIGH QUALITY
EX-RENTAL TVs AND VIDEOS TO THE TRADE
AT COMPETITIVE PRICES

ALSO AVAILABLE: NEW B-GRADE PRODUCTS –
TVs, VIDEOS, AUDIO & MICROWAVES –
ALL TESTED & BOXED

1/2 Mile of Junction 10 M6. Easy Parking Facilities

UNIT 3, BENTLEY LANE BUSINESS PARK
BENTLEY LANE, WALSALL WS2 8TL
Tel: 0922-724542. Fax: 0922-722208
Mobile: 0831-811633 (24 Hours)

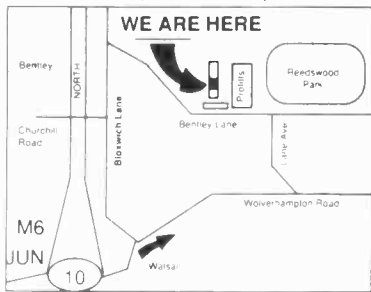OPEN:
MON-FRI,
9-6pm
SAT 9-2pm
SUNDAY BY
APPOINTMENT
DELIVERY
SERVICE
THROUGHOUT
THE COUNTRY



TUBES

Spring Stock Clearance

14" tube to replace
37-570, 37-573,
37-554, 3701B22

only £19

14" tube to replace
37-590
370HFB22 3708B22
AXT37-001, 370HUB22

only £29

14" tube to replace
almost any
narrow-necked crt

only £39

16" tube to replace
42-590, AXT42-001,
4202B22

only £29

17" FST tube
to replace
41JAR, 41EAM

only £69

16" tube to replace
38EAC, 420FSB,
420GAB, 420GJB,
420GUB

only £29

20" tube
51-590 **only £39**
510UFB22

NEW only £59

20" tube
51-580
AXT51-001

NEW only £69

20" tube Hitachi
Instaview
510VLB22

NEW only £35

21" FST tube for
Tashiko, Hinari etc
51JAR21X, 51JAR65X,
51JAR96X

only £45

25" Mullard New
59EAKOOXOI
Seconds (phosphor
defect), Good Value
only £49

New Mono Tubes
20" **only £10**
14" **only £5**
12" **only £5**

Ring Irene or Jane with
your tube number for
latest price and availability

Carriage and VAT
extra




EXPRESS TV

The Mill, Mill Lane,
RUGELEY, Staffs WS15 2JW

Tel: 0889-577600
Fax: 0889-575600

FANTASTIC SAVINGS ON METERS

AND MORE !!!

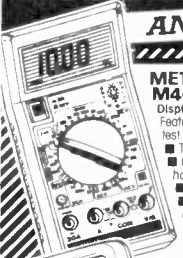

**METEX 4x DIGIT DMM
M4630** ■ 30 Range 4x Digit
Display 17mm ■ 0.05% Accuracy
Features: ■ 5 range capacitance
test ■ 5 ohms ranges to 20M
■ Transistor and Diode Test
■ Continuity LED and buzzer ■ Data
hold switch ■ 5-ranges AC/DC Volts
■ AC/DC current to 20 Amps
■ With leads, battery, instructions
and hard case (was £84.95)
NOW ONLY £59.95



TL34 ■ 33 Range ■ 3x digit
24mm Large Display
Features: ■ 5 Capacitance ranges ■ 6
resistance ranges to 20M ohm ■ Diode
and transistor test ■ 5 AC/DC volts
ranges Basic 0.5% accuracy
■ 5 ranges AC/DC current to 20 Amps
■ With leads, battery and instructions
(was £32.95)
NOW ONLY £29.95



MX190
■ 19 Range 3x Digit Features
■ AC/DC volts 0.7% ■ 0.1-10 ADC
current ■ 0.2/2/2MEG ohms/resistance
■ Diode test ■ Signal injector function
■ With leads, battery and
instructions
£14.95
(was £16.95)

ALL PRICES INCLUDE VAT

TEST METERS

LCR Meter ■ 3x Digit ■ 7 Cap ■ 6
inductance ■ 7 resistance ranges **£69.95**
Capacitance Meter ■ 3x Digit
■ 9 ranges ■ 18mm LCD display **£69.95**
Digital Lux Meter
■ 3 ranges ■ 3 1/2 digit LCD ■ Data hold
output terminal **£68.95**
Sound Level Meter
■ 40 to 120 db ■ Two ranges **£51.95**
Analogue Clamp Meter
■ 0/300 amps ■ AC 5 ranges ■ 0/750
VAC 0/75V DC ■ 0/200 K OHM **£36.95**
Digital Clamp Meter
■ 3x Digit ■ 11 ranges incl temperature
■ Data hold etc **£63.50**
AC/DC Current Clamp
■ 0/2000 amps AC/DC two ranges for
use with Dmm's **£58.95**
Temperature Measurement
■ Dual input 3 1/2 Digit °C/°F with
thermocouple (X1) **£45.95**
BENCH INSTRUMENTS
Digital LED Capacitance autorange
bench meter 0.1% **£99.95**
LCR bridge **£126.00**
7 Digit frequency 10HZ to 200MHz **£89.95**

POWER SUPPLIES

single meter *with meter
0/24v dc 0/3amps **£79.95**
0/24v dc 0/5amps **£97.00**
0/30v dc 0/3 amps **£145.00**
Twin version **£265.00**
5-15v dc 0/4 amps **£57.95**
SIGNAL SOURCES 20/240V AC
6 range RF Gen 100 KHZ to 150 MHz
(350MHz Harmonics) **£124.00**
5- range Audio Gen 10HZ to 1 MHz
Sine/square **£110.00**
0.5HZ to 500KHZ Function Gen
Sine/Sq/Triang **£26.00**

ALL PRICES INCLUDE VAT
OPEN 6 DAYS A WEEK

HENRY'S
AUDIO ELECTRONICS
(Reg. Prop. Cubegate Ltd)

204 Edgware Rd, London W2 1ED
Tel: 071-724 3564/071-258 1831
Fax: 071-724 0322

Discounts for quantity and education




HOW TO INCREASE YOUR PROFITS, IMPROVE YOUR SERVICE, WITH COST EFFECTIVE TEST EQUIPMENT.

HAMEG OSCILLOSCOPES

HAMEG are Europe's top selling DUAL TRACE OSCILLOSCOPES. Select from four superb models. All, with the exception of the HM 1005, incorporate a useful COMPONENT TESTER. Size - all models - 285mm x 145mm x 380mm. Clear display 8cm x 10cm. Mains supply: 110/220, 240V AC 50/60Hz. All supplied with 2 PROBES, a COMPREHENSIVE MANUAL and a 2 YEAR WARRANTY.

HM203-7 20MHz STANDARD

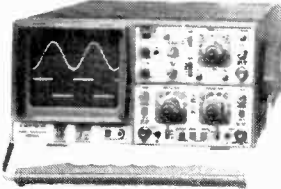

SPECIFICATION


- * 2 Channels
- * Bandwidth: DC - 20MHz
- * Sens: Ch.1, Ch.2, 1mV/cm
- * Timebase: 0.1s - 20ns/cm
- * Triggering: DC - 40MHz
- * Active TV - Sync - Separator
- * Variable hold-off
- * Trigger LED indicator
- * Calibrator: 1KHz Square wave
- * Component tester
- * Plus many features

Price £362.00 + £63.35 V.A.T. FREE Specialist Carrier Delivery

SPECIFICATIONS

- * 2 Channels
- * Bandwidth: DC - 60 MHz
- * Sens: Ch.1, Ch.2, 1mV/cm
- * Timebase: 2.5s - 5ns/cm
- * Triggering: DC - 80MHz
- * Active TV - Sync - Separator
- * After delay trigger
- * Sweep delay
- * Delay line
- * Trigger LED indicator
- * Calibrator: 1KHz & 1MHz Sq. Wave
- * Component tester

HM604 60MHz UNIVERSAL

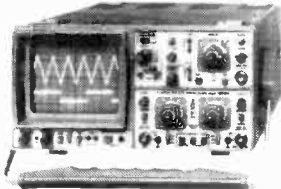


Price £653.00 + £114.28 V.A.T. FREE Specialist Carrier Delivery

HM1005 100MHz UNIVERSAL

3 CHANNELS - UP TO 6 TRACES

SPECIFICATION

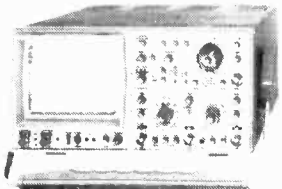- * 3 Channels
- * Bandwidth: DC - 100MHz
- * Sens: Ch.1, Ch.2, Ch.3, 1mV/cm
- * Timebase A: 2.5s - 5ns/cm
- * Timebase B: 0.2s - 5ns/cm
- * Triggering DC - 130MHz
- * After delay trigger
- * Delay line
- * Trigger LED indicator
- * Overscan LED indicator
- * Active TV - Sync - Separator
- * Calibrator: 1KHz & 1MHz Sq. Wave




Price £847.00 + £148.23 V.A.T. FREE Specialist Carrier Delivery

HM205-3 20MHz DIGITAL STORAGE

SPECIFICATION

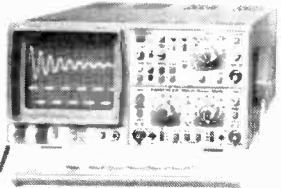- * Digital Storage
- * Analogue real time (Same as 203-7)
- * Bandwidth: DC - 20MHz
- * Sens: Ch.1, Ch.2, 1mV/cm
- * Timebase Digital: 5s-1µs/cm
- * Triggering DC - 40MHz
- * Active TV - Sync - Sampling
- * Max sampling rate: 2 x 20MHz
- * Memory: 2 x 2048 x 8 Bit
- * Dot joiner
- * Printer/plotter output



Price £653.00 + £114.28 V.A.T. FREE Specialist Carrier Delivery

**BLACK STAR COLOUR PATTERN GENERATOR
THE 'ORION' THREE-IN-ONE
PAL VHF/UHF - PAL VIDEO COMPOSITE - R.G.B.**

The Orion is a compact, bench instrument offering a wide range of patterns and facilities at a truly low cost.

In addition to a switchable sound carrier facility which allows use with the majority of PAL TV systems, the Orion provides highly flexible TGB outputs, ensuring compatibility with most video monitors.


More than 50 pattern combinations can be selected, including those for testing static and dynamic divergence, video amplifier linearity, colour purity, general colour performance, focus etc.

A separate video input to modulate camera signals; fully variable RF and video output levels facilitating AGC testing; trigger output allowing easy triggering of difficult oscilloscope waveforms; external sound modulation input via DIN connector for frequency response testing of TV sound systems; adjustable wide frequency coverage of VHF and UHF TV bands.

Indispensable in the manufacture, test, and servicing of televisions, and computer and video monitors

FEATURES

- * Colour bars, purity, greyscale, crosshatch, dots, focus, etc.
- * VHF/UHF Channels.
- * 5.5MHz, 6.0MHz, 6.5MHz Sound Carriers.
- * Internal/External Sound.
- * External Video Output.
- * Trigger Output.
- * PAL B,D,G,H,I,K.
- * Separate R, G, B and sync. O/P's.
- * RGB @ TTL & 1V.
- * Green + 0.3V Syncs.
- * Composite Video Output.
- * Variable RF/Video Output.
- * Switchable Video Polarity.
- * Mains powered 220/240V AC 50/60Hz.
- * Size: 98 x 219 x 240mm.

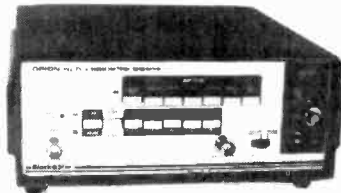

Price £229.00 + £40.08V.A.T.

NEW! DEGAUSSING COIL


A very effective degaussing coil, ideal for degaussing TV tubes, computer monitors, oscilloscopes etc. Mains Power: 220/240 50/60Hz. Size: 355 x 355 x 24mm.



Price £46.00 + £8.05V.A.T.

B & K PRECISION CRT ANALYSER-RESTORER

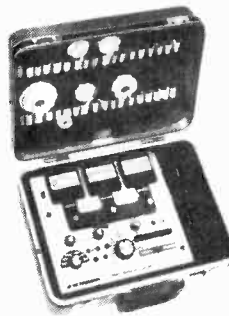The number one CRT Test Instrument. Over 5000 U.K. Television engineers wouldn't be without it.



- * All CRT's checked identically, including all in-line and one gun types
- * Tests all three guns of colour CRT's simultaneously under actual operating conditions (model 490)
- * Exclusive multiplex technique (model 490)
- * Measure true dynamic beam current that actually passes through G1 aperture to screen
- * Measures all shorts and leaks - preserving more CRT's
- * Tests focus electrodes lead continuity finding faults that other testers miss
- * Uses most powerful restoration method known with minimum damage to CRT
- * Rejuvenated CRT's guaranteed as new for two years
- * Obsolescence proof - perpetual set up chart, updated and new adaptors developed
- * Tests and rejuvenates VDU's and oscilloscope tubes
- * A range of over 40 CRT base adaptors available
- * Increase profit
- * Pays for itself in months.

Prices

- Model 490 Tri-dynamic three meter instrument inc. 6 common adaptors..... £559.00 - £97.83V.A.T.
- Without adaptors..... £496.00 - £86.80V.A.T.
- Model 480 Single meter instrument inc. 6 common adaptors..... £425.00 - £74.38V.A.T.
- Without adaptors..... £360.00 + £63.00V.A.T.

SADELTA SIGNAL STRENGTH METERS

The Sadelta Field Strength Meters have been designed to facilitate the dish alignment of satellite TV systems and aerial alignment of VHF/UHF television and radio systems. Signal levels can be accurately measured on the TC402-D, TC90 AND TC80, allowing the evaluation of signal conditions for satisfactory operation. All models have a clear LCD direct frequency readout, coupled to a multiturn tuning control enabling precise channel identification.

TC402-D VHF & UHF

FEATURES

- * Three bands:
 - Low VHF: 45-170MHz
 - High VHF: 170-450MHz
 - UHF: 450-862MHz.
- * Digital display for direct frequency readout.
- * Built-in monitor loudspeaker AM/FM.
- * Signal measurement from 20µV to 3V.
- * Powered by eight 1.5V AA batteries.
- * Fully portable with sturdy carrying case.



Price £289.00 + £50.57 V.A.T.

TC90 VHF-UHF- SAT.


FEATURES

- * Five bands:
 - Low VHF: 45-110MHz
 - High VHF: 110-300MHz
 - Hyper VHF: 300-470MHz
 - VHF: 470-862MHz
 - Satellite: 950-1750MHz.
- * Digital display for direct frequency readout.
- * Signal measurement VHF/UHF 20µV to 3V.
- * Signal measurement satellite -70dBm to -10dBm.
- * Audible indication of satellite signal level.
- * Built-in-monitor loudspeaker AM/FM (not satellite).
- * Powered by rechargeable battery (complete with charger 220/240V AC).
- * Fully portable with sturdy carry case.



Price £499.80 + £87.47 V.A.T.

NEW! TC80 SATELLITE

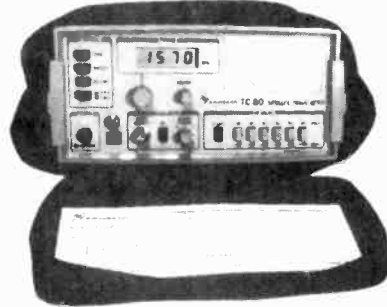

TC-80 IN ITS STURDY CARRY CASE



TC-80, USING A LCD TV AS A MONITOR

The TC80 incorporates three unique features: video composite output; audio output with built in loudspeaker; ramp and RF signal outputs, which enable an oscilloscope to be used as a spectrum analyzer.

- * 4 digit LCD freq. display
- * Freq. range 950 to 1750MHz
- * Sweep mode sweeps entire freq. band for rapid satellite location
- * Tone select switch for audible tone proportional to signal strength
- * Measurement from 40 to 100dBuV
- * Audio demodulation with internal loudspeaker
- * Video demodulation
- * Rear SCART connector for A/V connection
- * Oscilloscope/spectrum analyzer output
- * Sound tuning 5 to 8MHz
- * LNC PSU 14V or 18V
- * LNC current measurement
- * Internal rechargeable battery with charger

Price £490.00 + £85.75V.A.T.



U.K. POST PAID, export enquiries welcome. Visa/Access or cheque with order, payable B. K. Electronics. Official Orders welcome from Govt. Depts., colleges, P.L.C.s etc. Large (A5) S.A.E. for technical leaflets of complete range. Credit card orders are accepted by 'phone, fax or post. Delivery normally within seven days.



B. K. ELECTRONICS
UNITS 1 & 5 COMET WAY, SOUTHEND-ON-SEA
ESSEX SS2 6TR
Tel.: 0702 - 527572 Fax.: 0702 - 420243

DSD DISTRIBUTION

STOCKIST OF BRANDED B. STOCK

Sony, Panasonic, Hitachi, Sanyo, Toshiba etc.

Ex-Rental TV's + Videos

Basic TV's from £10
working Video's from £25

Our own Brand 'DUOTRON'

Midi + Midi Hi-Fi, CD's, Clock Radios,
Radio Cassettes, Walkmans



Unit 1, Eagle Works
Springcroft Road, Hall Green
Birmingham B11 2PP
Tel: 021-778 5825

WESTERN TRADE SERVICES

EST 14 YEARS

**SUPPLIERS OF EX-RENTAL
TV & VIDEO
THORN AND NON THORN**

SOUTH WEST

2A Barton Hill Road, Torquay,
Devon TQ2 8JH

Tel: 0803 312222

Fax: 0803 326767

Delivering throughout Devon and
Cornwall weekly

WALES

Unit 6, Islwyn Workshop,
Portymaester Ind Est, Risca,
Gwent

Tel: 0633 612667

C.T.V.

UNIT 5, THE PHOENIX BUILDING, RUSHOCK
TRADING ESTATE, DROITWICH ROAD,
NEAR KIDDERMINSTER
TELEPHONE: 0299-251522
0836-585829/0860-809673 (24HR)

**SUPPLIERS OF HIGH QUALITY
EX-RENTAL TELEVISIONS AND VIDEOS
LARGE STOCKS ALWAYS AVAILABLE
ALL AT COMPETITIVE PRICES**
Also available: 'B' Grade Products,
Audio, Microwaves and Complete Range
of Televisions and Videos
OPEN: MON-FRI - 9.30-5.30

TEL: 0299-251522
0836-585829/0860-809673 (24HR)
Fax: 0299-251543 EXPORT ENQUIRIES WELCOME

TELEPRICE

LIMITED

THE LEADING SUPPLIER OF EX-RENTAL
TELEVISION, VIDEO AND AUDIO EQUIPMENT
TO THE WHOLESALE TRADE

CALL US FOR LATEST PRICES
AND NEAREST CONTACT ON:

Tel: 0793 421141 Fax: 0793 432478

1st Floor 52/54 Cricklade Road Swindon Wiltshire SN2 6AF



WILTSGROVE LTD

Your One Stop Warehouse



RECONDITIONED WORKING STOCK

VIDEO

Top Loading VCR £35.00
Front Loaders with R/C £45.00
Twin Speed VCR with R/C £55.00
Ferguson FV11R with R/C £65.00

Basic CTV's from £15.00
Remote CTV's from £25.00
Teletext CTV's from £35.00
FST's from £65.00

TELEVISION

T.V.

20" Remote £125.00
20" Nicam Fast Text £159.00
21" Nicam Fast Text £179.80
14" Teletext £109.00

"B" GRADE WORKING STOCK

AUDIO (Sharp)

RG292 Car Radio £16.75
RG296 Car Radio £19.25
JC105 Cass/Player £5.45
JC130 Cass/Player £6.99

NEW 14" Remote Control Portable CTV 12 months Guarantee £99.95

*SONY VIEWDATA SYSTEMS with Keyboard £59.00

E-180 EXTRA GRADE VIDEO TAPE (min 50) £0.79

1000's OF QUALITY SPARES AT PRICES HARD TO BEAT!

LOPTS (REPLACEMENT)

Ferguson TX100 (Green Spot) 22B1, 22B2, 22B3, 22D1, 22D2, 22D3, 26D1, 26D2, 26D3, 22G2 etc £12.75

PANASONIC

TLF14567F, TLF14520F, TLF14568F, TLF14521F, TC1631, TC1641, TC2031, TC2033, TC2043, TC2232, TC2233, TC2243, TX1632, TX1642, TX2034, TX2044, TX2200, TX2230, TX2231, TX2234, TX224, TX2244, TX2636, TX3300 ONLY £17.95

HITACHI

2434274, 2434593, CPT2174, CPT2176, CPT2178 etc £14.95

FERGUSON/JCV BELT KITS

Models 3V29, 3V30, 3V35, 3V36, 3V38, 3V49, HRD110, HRD111, HRD120, HRD121, HRD225, HR7200, HR7300, HR7350, 8930, 8940, 8944 etc ONLY ALL STOCK SUBJECT TO VAT, AVAILABILITY & CARRIAGE £0.99



28, 29 RIVER STREET, DIGBETH,
BIRMINGHAM B5 5SA



Tel: 021-722 2733 - Fax: 021-766 6100

OPEN MONDAY TO SATURDAY 9AM - 6PM

SWITCH ON TO B' GRADE AT PRICES SECOND TO NONE

14" Remote Portables.....	85
14" Teletext Portables.....	105
14" Fastext Portables.....	115
20" Remote CTVs.....	110
20" Teletext CTVs.....	125
20" Fastext CTVs.....	135
21" Fastext CTVs.....	145
20" Nicam Fastext.....	160
21" Nicam Fastext.....	175

All stock tested & working and boxed
with remote & instructions

Also 7000 sq ft of returned TV,
Video & Hi-Fi. Too many to list.
Don't delay phone today
to make an appointment

GOGGLEBOX TEL: LEEDS
0532-310359

DISCOUNT ELECTRICAL WAREHOUSE ASK FOR ROBERT

ALL ABOVE PRICES PLUS VAT AT 17.5%

**FAX: 0274
722229**

**BESCO LIMITED
T/A
NORTH WEST ELECTRONICS
ENTIRE RANGE OF EX-RENTAL TVs & VIDEOS**

NEW STOCKS EVERY DAY, WORKING OR OFF THE PILE

makes include: Sharp, Hitachi, Ferguson, Pye, NAT PAN, ITT etc.

Late models always available.

KNOCKOUT PRICES ON COLOUR TVs

FERGUSION, PYE, HITACHI, PHILIPS, BUSH, ITT, etc.

TELETEXT BARGAINS FROM **£30.00** (WORKING).

FERGUSION TX TELETEXT ONLY **£45**. PHILIPS/PYE TEXT ALWAYS AVAILABLE

OVER 1000 COLOUR TV AND VIDEOS AVAILABLE

RING OUR HOTLINES NOW FOR PRICES OR CALL IN, YOU WILL BE DELIGHTED

Working Ex-Equipment Panels

IF	Converger	Decoder	Line scan	Power	Frame
T20//22X	5	14	18	17	14
T26 X	5	16	20	17	X
Phillips G11 14.50	5	12	20	20	11.50

All prices include Postage & Packing. But + VAT

★ IF THE PANEL YOU REQUIRE IS NOT LISTED PLEASE ASK ★

Visa Welcome

Prices are plus VAT
and based on quantity

Cheques accepted

Walker House, 16 Bottomley Street, Bradford BD5 7LJ

Ring Tony 0274 308186 – Open 6 days – 9am-5pm

TRADE ANNOUNCEMENT



GAMMA (UK) LTD

Gamma (UK) Ltd have a new warehouse opened in Nottingham. Over 1,000 Televisions and Videos in stock. Refurbished, working and un-tested stock always available. Fresh deliveries every week.

Specialists in export to the African Continent (export enquiries welcome)

HEAD OFFICE:

1501-1503 Pershore Road, Stirchley,
Birmingham B30 2JH

Tel: 021-458-4093 Fax: 021-486-2980

Opening Hours:

10am to 6pm Monday to Saturday

Nottingham Branch:

256 Derby Road, Stapleford, Nottingham
NG9 7BG

Tel: 0602 392231

Opening Hours:

10am to 5pm Monday to Friday

C.T.V. (NORTH EAST)

9A/B, 94 Carrmere Road

Leechmere Ind. Est.

Sunderland

SR2 9TE

**No.1 in the North East
for all makes and models
of high quality ex-rental
televisions and video recorders
at very competitive prices**

**For Further Information
Please Contact Nick or Brian on
091-523 5554**

Fax: 091-523 8035

Export Enquiries Welcome.

GREATER MANCHESTER'S NO 1 WHOLESALER

RED BANK UNIT 20

HERE

STRUGGLING FOR STOCK?

WE HAVE GOT WHAT YOU NEED

THORN and GRANADA PORTABLES and F.S.T's AVAILABLE NOW!!

Televisions from £5, F/loading Videos from £20
Working Teletext from £35, 1,000s of TVs and Videos in stock

FRESH STOCK ARRIVING DAILY
RING NOW FOR STOCK UPDATE


*Export Enquiries Welcome

Open 10am - 5pm Mon-Fri

**UNIT 20, RED BANK ARCHES,
MANCHESTER M4 4HF**

— CHEQUE — ACCESS — VISA —

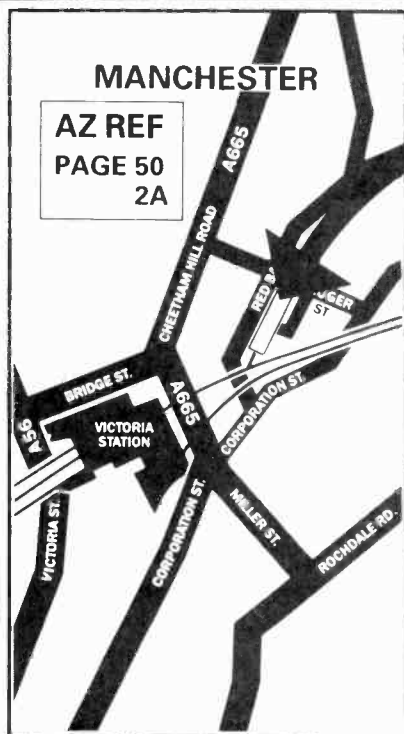PHONE 061 832 4220
FAX 061 834 6368
PRICES SUBJECT
TO VAT



B-grade Stock All Boxed, working
If you require one item please read on:

10" R/C Portable	£95
14" Basic Portable	£85
14" R/C Portable	£95
20" R/C	£119
20" Text	£139
21" FST R/C	£145
21" Fastext FST	£165
21" Nicam	£219
25" Nicam	£259
L/P Videos	£99
Stereo Midi System	£110
Microwave Oven	£50
TV & Video Stands	£3

**DISCOUNT
ON
QUANTITY**

CD Midi Systems working (RRP £279) all boxed £129
CD radio cassette, working £49

Customer returns in block.

Example. Untested 3x21" FST 3x25" FST
6x F/L Videos £40 each. Total £480+VAT

This price does not include handsets.
Some in need of repair. Some working.

ELECTROLUX
Built in ovens

Unused and working £119

W TREE WAREHOUSE
UNIT 1, SUNSHINE MILLS, WORTLEY RD, LEEDS 12
TEL: 0532 638804 FAX: 0532 310275

MANUFACTURERS 'B' GRADED STOCK

**Televisions, Videos
Audio, Music Centres
Microwave Ovens**


Complete, reboxed, working
Current model stock

Turner Lyons Enterprises Ltd
9 Howard Place,
Shelton
Stoke on Trent ST1 4NN


Phone David or John

0782 285416

BRITAIN'S LARGEST INDEPENDENT PRESENTS

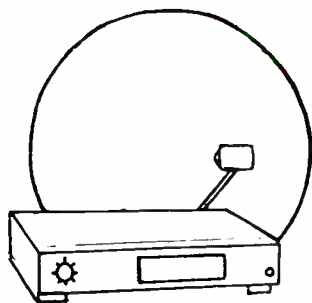

LTD

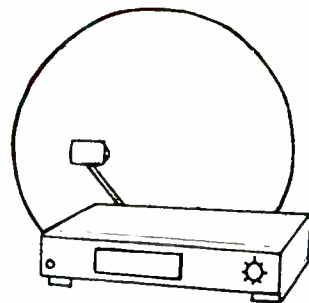

**MASSIVE PRICE REDUCTIONS – SPECIAL STOCK CLEARANCE
ON MANUFACTURERS B-GRADE STOCK**

21" R/C – £110

21" TEXT – £150

21" NICAM – £185

25" TEXT – £175

25" NICAM – £215

28" TEXT – £225

28" NICAM – £250

**LARGE
QUANTITIES
OF LISTED
ITEMS
AVAILABLE**

**NEW
PRODUCT LINES
NOW IN
STOCK**

**EXTENSIVE
CHOICE OF
GRADED STOCK
SEE BELOW**

**NEW SOUTHAMPTON WAREHOUSE
OPEN MONDAY 23rd MAY – Tel: 0703 512540**

**Home Computers
Telephones
Clock Radios
Calculators
CD Midi Systems**

**Radios
Still Cameras
Car Radios
Toasters
Personal Stereos**

**Satellites
Televisions
Electric Fires
Personal CDs
Midi Systems**

**CD Mini Systems
VCRs
CD-Radio Cassettes
Home Security Systems
Portable Audio**

DON'T MISS OUT, PAY US A VISIT

PRESTON

139 Oakshott Place
Walton Summit
Ind Est
Preston (M6 Junc 29)
Tel: 0772 312101

BIRMINGHAM

208 Bromford Lane
Erdington
Birmingham B24 8DL
Tel: 021-327 3273 Fax: 021-322 2011

LONDON

Unit 2
The Royal London Est
29/35 North Acton Road
London NW10
Tel: 081-961 5005

AERIALS

FOR TV & FM RADIO, PLUS
1000's OF MASTS,
BRACKETS, LASHING KITS,
CLAMPS, PLUGS, CABLES,
OUTLETS, DIPLEXERS ETC.

AMPLIFIERS

FOR DISTRIBUTION
SYSTEMS AND DOMESTIC.
MAST HEAD OR SET BACK.
WE HAVE ONE OF THE
LARGEST RANGES,
AVAILABLE FROM STOCK

MAIN DISTRIBUTORS

FOR ANTIFERRENCE,
LABGEAR, WOLSEY
FRINGE, TRIAX, TELEVES,
VOLEX-RAYDEX, KUBLER
+ MANY MORE

**COASTAL
AERIAL
SUPPLIES**

UNIT X2 Rudford Industrial Estate
Ford, Arundel

0903 723726

NO MINIMUM ORDER VALUE
NEXT DAY DELIVERY ACROSS UK
CARRIAGE FREE ON ORDERS £250+



**CAMPION
WHOLESALE LTD.**

**QUALITY USED TV
& VIDEO**

COMPLETE RANGE OF
TV's AND VIDEOS
MOST MAKES AND
MODELS AVAILABLE

STOCK ARRIVING DAILY

TV's from £3.00
Videos from £30.00

Prices Ex-VAT

Free Delivery Service
to most areas of the UK

UNIT 75, BARRACKS ROAD,
SANDY LANE INDUSTRIAL ESTATE,
STOURPORT-ON-SEVERN,
WORCESTERSHIRE DY13 9QB

Just 10 Mins from
M5 Junct. 6 Worcs North

UK's LARGEST EXPORT
WHOLESALE. CONVERSIONS
TO MOST COUNTRIES

0299-879642 (3 lines)

FAX: 0299 827984

ANGLIAN TV WHOLESALE


EX-RENTAL TVs & VCRs

**THORN
AND
GRANADA
STOCK**

NEW 'B' GRADE
TV, VIDEO
AUDIO, MICROWAVE

BEST POSSIBLE PRICES
RING FOR DETAILS

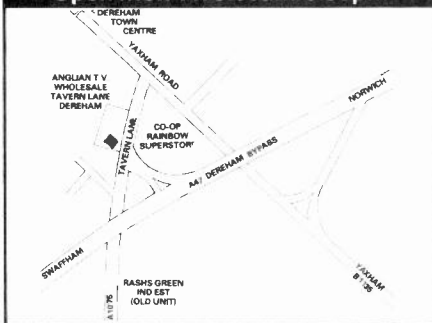ANGLIAN TV WHOLESALE,
UNIT 4, BRECKLANDS BUSINESS
CENTRE, TAVERN LANE, EAST
DEREHAM, NORFOLK
TEL/FAX (0362) 691611
Open Mon-Fri 9.30am-5.30pm



**NOW OPEN
ON....**

TEESSIDE

- ★ Ex-rental TV & Videos
- ★ Best deals on working and non-working stock

SUPERSCREEN

184 Linthorpe Road,
Middlesbrough

Telephone:
0642-250850

**TRADE TV's
BASIC,
REMOTE,
TEXT**

**Telephone
Roy Smith**

**Mon-Fri
10am-5pm**

**0302-349583
0836-368878**

**A. R.
International
Union Street
Doncaster
off
St Sepulchre
Gate West**

TELEPLACE SCOTLAND

TV & VIDEO WHOLESALE.

**Working Faulty
Refurbished Stock
Delivered.**

**8, Colquhoun Park
Hillington Industrial
Estate
Glasgow
G52 1XX**

041-883 2610

VISIONCARE

**THE NEW NAME IN HAMPSHIRE
FOR GOOD QUALITY EX-RENTAL,
NEW AND "B" GRADE STOCK**

RECONDITIONED WORKING EX-RENTAL STOCK

Top Loaders	£35.00	Basic CTVs.....	from £15.00
Front Loaders with R/C	£45.00	Remote CTVs.....	from £25.00
Twin Speed VCR	£55.00	Teletext.....	from £35.00
Ferguson FV11R R/C	£65.00	FST.....	from £65.00

★ "B" GRADE WORKING TELEVISIONS

20" Remote Control	£125.00
20" Nicam Fast-text	£159.00
21" Nicam Fast-text	£179.00
14" Teletext Portable	£104.00

Please call Phil or Martin for more opening offers.

**40 Invincible Road (ex-Teleprice unit),
Farnborough,
Hampshire GU14 7QV**

Tel: 0252 512161 Fax: 0252 524388

CENTRAL TV



EX-RENTAL

- ▶ SUPERB RANGE OF TVs & VCRs
- ▶ THORN & GRANADA

▶ DIRECT LOADS
AVAILABLE FROM SOURCE

EXPORT ENQUIRIES WELCOME

'B' GRADE

**FERGUSON FV61LV
VIDEOPLUS - CENTRE DECK**

QTY PRICE - £169.99

PHONE TODAY FOR BEST RESULT

* Stock arriving daily, TVs from £3.00. Videos from £25.00.
Quality ex-rental TVs & Videos. Most makes and
models available.

		QTY 1	QTY5+
	Microwave	£69.00	£60.00

	Ferguson Surround Speakers	£35.00	£25.00
---	----------------------------	--------	--------

Ferguson TV Stereo Speakers
Special 1 Price! £15.00 - min 15

TV/stand - mixed sizes	£5.00	£3.00
------------------------	-------	-------

Portable colour 14" new B/grade	£95.00	£90.00
---------------------------------	--------	--------

20" colour remote control	£120.00	£115.00
---------------------------	---------	---------

20" colour Fasttext	£135.00	£129.00
---------------------	---------	---------

Ferg B59N Nicam Stereo TV -	special price	£300.00
-----------------------------	---------------	---------



Ferg FV61LV Video Plus, LP Centre design	£199.99	£185.00
--	---------	---------

Ferg FV62LV as above + 2 Scart	£290.00	£200.00
--------------------------------	---------	---------

Ferg FV67HV as above + Nicam	£279.00	£235.00
------------------------------	---------	---------

plus FV70B, FV71LV, FV72LV P.O.A.

TVs 51cm, Ferg, C51N, Nicam P.O.A.

plus C51NX, B59N, B59NX, B78N1 P.O.A.

plus A10R, B14R, B14C, B39F P.O.A.

B49F, B51F, C51F, B59F P.O.A.

* Toshiba TVs, Videos P.O.A.

Samsung TVs, Video, Microwave P.O.A.

ALL PRICES plus VAT




**CENTRAL TV WHOLESALE
DISTRIBUTION LTD**



London contact: John
Eley Estate, Nobel Road
Edmonton N1B
Tel: 081-807 4090
Fax: 081-884 1314

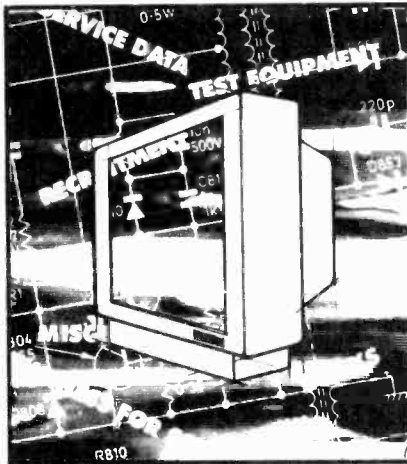Birmingham contact: Mick
369 Stratford Road, Sparkhill
Birmingham B11
Tel: 021-772 1591
Fax: 021-766 6383



TELEVISION CLASSIFIED

No other consumer magazine in the country can reach so effectively those readers who are wholly engaged in the television and affiliated electronic industries. They have a need to know of your products and services.

The prepaid rate for semi display setting is £12.00 per single column centimetre (minimum 3 cm). Classified advertisements £8.40 per line, box number £22.00 extra. All prices plus 17½% VAT. All cheques, postal orders etc., to be made payable to Reed Business Publishing. Advertisements, together with remittance, should be sent to The Television Classified, 11th Floor, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.



PHONE 081-652 8339 FAX 081-652 8931



SERVICE DATA

SERVICE MANUALS

We have what is probably the largest range of Service Information available anywhere. From the Earliest Valve Wireless to the Latest Video Recorders. Colour Televisions, Test Gear, Audio, Computers, Amateur Radio, in fact practically anything. Originals or Photostats as available.

Also available. Our **FREE** catalogue detailing Hundreds of Technical Books and Repair Guides available.

Now Available. Our Service Manuals Index on P.C. Disc (3.5") for use on your Computer. Just £3.50 with FREE everlasting Updates. Order MP-285.

Mauritron Technical Services (5TV),
47A High Street, Chinnor, Oxon OX9 4DJ
Tel: 0844 351694 Fax: 0844 352554.

Please forward your latest catalogue for which I enclose 2 x 1st Class Stamps. or £3.50 for the Technical Books Catalogue plus Manuals Index on PC Disc(s).

NAME _____
Address _____

POSTCODE _____



INFOTECH



76 Church Street, Larkhall, Lanarkshire ML9 1HE

Tel: (0698) 883334 – (0698) 888343

Fax: (0698) 884825

Send a large SAE for your FREE catalogue of our other publications

HOW WOULD YOU LIKE TO GET ANY SERVICE MANUAL YOU WANTED FOR ONLY £8.50?

WELL, NOW YOU CAN!

We are running a very special offer of any 20 manuals for only £170. No catches! Order as you need them (no time limit) including all those expensive manuals you couldn't previously afford. No hidden expenses like post & packing (that's included in the price).

And if that isn't enough!

We are giving away our Data Reference Manual FREE with every subscription to this 20 manuals for £170 offer!

EUROPEAN SCRAMBLING SYSTEMS NEW 3rd Edition

European Scrambling Systems is the "bible" of the black arts of signal security. Now in Euro' Scrambling 3, John McCormac analyses all of the latest hacks and scrambling systems

Only £32.00 inc. P&P

PRACTICAL GUIDE TO BUYING, SELLING, REPAIRING AND SERVICING USED CD's, TVs and VCRs

They cover everything from choosing good ex-rentals to covering more stock faults for common ex-rentals than elsewhere at many times the cost. These are brilliantly practical and inexpensive repair and service systems

Only £9.95 each or £25.00 for all three

SERVICE MANUALS

For most U.K. European, Far East & USA makes

Thousands of different models available

Prices (Stock Items):-

VCR, VCP, Camcorder, TV/Vid – £13.50
CTV, Colour Monitor, Camera – £8.50
MTV, Mono Monitor, SAT, MWV – £6.00

Add P/P £1.50 for first item then 50p for each additional item – no VAT

Cheque/PO with order only please.

D-TEC

PO BOX 1171, FERNDOWN, DORSET BH22 9YG

Tel: 0202 870656

TRAINING

If you require a home study course in the fundamentals of electronics, either to begin a career, pursue a hobby, or refresh your knowledge, a

BASIC ELECTRONICS

course, from the Direct Personal Learning scheme, could be just what you're looking for. Contact:

K. Sparrow etc. . . 11 Claydon Green
Whitchurch BRISTOL Avon BS14 0NG
Telephone: (0275) 835669

FAST FIX Fault Index

Now in NEW A4 Format, containing over 150 pages.

If you keep back copies of 'Television', FAST FIX is for you. Edition 3 lists over 8000 fault symptoms and hundreds of technical references from 12 years of Television. References are arranged alphabetically listing make, model, fault symptom and page reference. Covering the years 1982-Dec 1993. FAST FIX could pay for itself after just one repair. Regular updating takes place and all customers will be notified.

Complete FAST FIX index £16.00 inc. Overseas orders please add £3.00

MONEY BACK GUARANTEE IF YOU ARE NOT COMPLETELY SATISFIED

Send Cheques/Postal Orders, payable to J. Humphreys, 13 Mansfield Avenue, St. Johns Park Hawarden, Clwyd CH5 3SB N. Wales
For further details, tel: 0244 532961

INDEXES! INDEXES!

THOUSANDS SOLD WORLDWIDE

EDITION 10 of the complete indexes now published containing over 8,000 Faults listed in 12 Years of Television Magazine

Indexes are alphabetically listed by Make, Model, Fault, Ref and are now Available for just :

£8.00 For Television & Satellite Faults

£8.00 For Video, Camcorder & CD Faults

Or

£15.00 For both sets complete

Please add £1.50 (UK), £3.00 (Overseas) to total order to cover post & packing.

A LOW COST UPDATE SERVICE IS ALSO AVAILABLE. FULL DETAILS DESPATCHED WITH ORDER.

To secure your copy/s please make Cheques/Postal Orders payable to:

E.C.S. 31 PRENTON ROAD WEST,
PRENTON, BIRKENHEAD,
MERSEYSIDE L42 9PY

No! For Fault/Repair Guides & Circuits

Giant Fault Guide

Akal, Alba, Amstrad, Arston, Bendix, B&O, Bush/Rank, Decca/Tatung, Dorec, Ekco, Ferguson, Fidelity, Finlux, Fisher, GEC, Grundig, Hitachi, Hiran, IIT, JVC, Karling, Lowe, Luxor/Skanic, Mitsubishi, Murphy, Nordmende, Orion, Panasonic (basic), Philips, Sanyo, Semtra, Sharp, Sony (basic), Telefunken, Toshiba, Triumph, Zanussi

Giant Compendium has all of the above for only £9.95 (Normally £16.95)

(Fault & Diagnostics Pocketbook for Ferguson TX90/TX100 Only £4.95)

TV AR Fault & Servicing Guides (£16.95 each)

VOL 1: The CTV's covered by this volume include—Alba 10-14, Conic, Decca/Tatung to 89, Etron, Hiran, CT4 to 8, IIT 1100/1200 plus Digivision to 89, Laytron, Philips KT4/K40. The CD's covered range from Alba to Sony incorporating Philips, Ferg, Hitachi and others. Lastly, there are over 50 more different audio sets covered as well as the CD players.

VOL 2: Covers—The CTV's covered in this volume include Ferg TX 85 to TX-100 (plus all variants and the TCCS), Philips 2A & 3A chassis, Sharp's P57 Chassis and others including Telefunken and Nordmende. This volume also has info on various satellites including Amstrad, Ferguson and Pace. The Aton 51 (520/1040) is covered as well as a wide selection of VHS-C camcorders including Ferguson, Amstrad and Philips.

Each book has a binder full of the matching Circuits Available at £39.50 each

CTV CIRCUIT COLLECTIONS

Each Collection Contains All the Circuits of the Most Popular Chassis

ALBA	£25	AMSTRAD-FIDELITY	£25	B&O	£25
DECCA-TATUNG	£25	ETRON GROUP	£12	FERGUSON-BAIRD	£45
GRANADA	£25	GEC	£25	GOLDSTAR	£15
GRUNDIG	£40	HINARI	£20	HITACHI	£40
IIT-NOKIA	£45	JACKSON	£10	JVC	£20
LOHJA	£50	MATSUI-SAISHO	£40	MITSUBISHI	£50
NEC-NWC	£15	NORDMENDE	£15	PANASONIC	£60
PHILIPS	£75	PIONEER	£8	RANK	£20
REDIFFUSION	£20	SANYO	£35	SONY	£75
TELEFUNKEN	£15	TOSHIBA	£40	TRIUMPH	£20
WALTHAM	£15	ZANUSSI	£20		

Video Fault Finding Guides (5 books per series)

Series 1: Ferguson 3V00/01, 3V16, 3V22 23 Baird 8924, JVC HR-4001, Philips N-1500/N-1502, N-1700/N-1702

Series 2: Ferguson 3V29/30, Baird 893H/40, Philips 2000, Sanyo, VTC5000/5300, VTC9300, Toshiba V5970 & Clones

Series 3: Baird 8931/42, Ferg 3V31/32, Pan NV7000/8000, Philips 22VP600/700, Sharp VC2300/7750/8300/9700

Series 4: Fidelity VTR1000 & Clones, Pan NV100, NV8600/8610, Philips VR6460, VR6560, Sharp VC108/408/651/681

Series 5: Ferg 3V35/36/38/39/43/44/45/48/53, Hitachi VT11, VT8000/8500, GEC V4100, Pan NV370, Philips 6920

Series 6: Grundig V5300 to 380, Hiran VXL8/9/10, Hit VT410 to VT450, Pan NV730 to 788, Sanyo VHR3100/3800

Series 7: Ferg 3V58 to FV11/12, Goldstar GHV/GSE 1290-1296, Pan D Deck, G/G1 Decks, Sharp VC381 to VC387

(Please Note: The above are not Full Listings, only the main models from each series, they actually contain more info)

Only £12.95 per Series or £79.95 for all



INFOTECH



76 Church Street, Larkhall, Lanarkshire ML9 1HE

Tel: (0698) 883334 – (0698) 888343 – Fax: (0698) 884825

Please add £2.00 For Post & Handling



INFOTECH



76 Church Street, Larkhall, Lanarkshire ML9 1HE

Tel: (0698) 883334 – (0698) 888343

Fax: (0698) 884825

Or Send a large SAE for your FREE catalogue of 100's of publications. Please add £2.00 for Post & Handling on any order (post free on orders over £30.00)

We have the world's largest collection of:

"SERVICE MANUALS",

"SERVICE SHEETS",

"CIRCUIT DIAGRAMS",

"FAULT-FINDING GUIDES",

"REPAIR GUIDES",

"CIRCUIT DESCRIPTIONS"

For CTVs, VCRs, CDs, Satellites, Midi Systems, Computers, Amps, Oscilloscopes, Mono TV's, Radios, Camcorders, Walkmans, Car Stereos, Tape Decks, Printers, Photocopiers and almost everything else!

!!We've got the lot!!

Data Reference Guide (4th Edn.) Only £5.95

With over 120 pages and incorporating a full "chassis guide" and Cross-references on every piece of CTV, CVR, Audio, Domestic and Test Equipment we can find! It is still the best guide on the market.


We Also Run the Largest Data Library in the United Kingdom (Please ask for details)

Phone/Fax or write for a FREE quote on any model Orders usually sent "same day" as the order is placed

P.C. DIAGNOSTICS SOFTWARE



Now Available - What is probably the most COMPREHENSIVE selection of diagnostics software for the P.C. currently available. A vast collection of programs and utilities to help you get the most from your system. Covers such useful information as IDE Drive parameters, PC System memory diagnostics, Low Level formats for Hard Discs, Jumper settings, Compatibility tests for modems, Data recovery programs, FAT Table analysis, Analyse modify disk boot sectors, Keyboard buffer tests, Motherboard diagnostics, System Exercisers, Setting up CD-ROM's etc etc etc. In all over 20Mb of useful information compacted onto 14 Discs with 2 reference books. If you need to get more information from your PC then this set is for you. Order TODAY.

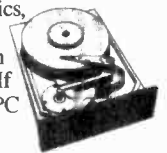

Just £25.00 + p/p. Order MP-250/251.

All orders will include a copy of our FREE catalogue detailing the full range of Technical Books and Repair Guides we publish.

MAURITRON TECHNICAL SERVICES (TV2501),



47A High Street, Chinnor, Oxon, OX9 4DJ

Tel:- 0844-351694. Fax:- 0844 352554.



Please forward _____ sets of MP-250/251 at £25.00 each + p/p

I enclose Cheque/Postal Order or please debit my Visa/Access Card

Card No. _____ Expires ____/____

NAME _____

ADDRESS _____

POSTCODE _____

Please add £2.35 (Overseas £5.00) to all orders to cover Postage & Packing

CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED

JOULE A-400 CAR RADIO DECODER/RE-PROGRAMMER

features

Plugs directly into your IBM or compatible computer. Remove the baseplate from the radio, place the probe onto the PCB and the security code is instantly displayed. Changing the code or even fully re-programming is just as easy.

ABSOLUTELY NO MODIFICATIONS TO YOUR COMPUTER ARE REQUIRED

The A-400 can use either Comms 1 or Comms 2, connected via the serial lead supplied

Two levels of password protection (user selectable) to prevent unauthorised use.

Each decode is recorded and may be accessed at any time, again, to prevent unauthorised use.

Operates from 12 volt supply, either from mains (via any regulated mains adapter) for bench use or, via vehicle cigarette lighter socket, for on site use.

Easy to use software includes on-screen PCB layouts for probe location, very detailed help screens and information on how to enter codes into the radio once the set has been decoded.

Supplied complete with connecting lead, purpose designed probes and a comprehensive instruction manual.

Technical help line available to all registered users

PRICE: £375.00 + VAT

Package includes software for most popular brands of radio

PHONE NOW FOR FREE DEMONSTRATION DISK AND INFORMATION PACK

(Please state either 3.5" or 5.25" disk)

The Joule A-100 is a factory built Hi-Tech design made to a very high standard of workmanship which is set to become the industry standard for car radio decoding equipment and is available from:

ELECTRONIC SOUND SYSTEMS

62 High Northgate, Darlington, Co. Durham DL1 1UW Tel: 0325 484089 Fax: 0325 465921 Mobile: 0860 221 099

WIZARD DISTRIBUTORS

Spares + Components
Always in stock
Video heads for over 500 models
Spares for over 20 manufacturers
Hand sets for over 200 models
TV Tubes new + regunned
Plus much much more
Empress St Works
Empress St
Manchester M16 9EN
061-872 5438, 061-848 0060
Fax: 061-873 7365

SURPLUS/REDUNDANT ELECTRONIC COMPONENTS WANTED

I/Cs - Tuners - Transistors - Valves - Diodes etc. any quantity considered - immediate payment.

ADM Electronic Supplies

Tel. 0827 873311. Fax 0827 874835

SERVICE MANUALS

- Have you turned work away for want of a Service Manual?
- Have you ever bought a Service Manual and never use it more than once?
- Then why not join

"THE MANUALS LIBRARY"

For details and Membership Application Form

Write, Phone or Fax

HARVEY ELECTRONICS

43 Loop Road, Beachley, Chepstow, Gwent, NP6 7HE
Tel: 0291-623086 Fax: 0291-628786
VISA, ACCESS accepted

AMSTRAD, LOGIK, MATSUI-SAISHO FAULT FINDING GUIDE

Covers hundreds of faults on a wide range of television and video recorders. Professionally compiled in easy to locate format. SAVES TIME AND MONEY by pin pointing faults in record time.

SEND £9.95 + £1.00 p.p.
TO

R. ROWLAND
438 Poynters Rd, Luton,
Beds. LU4 0TW

TEK-HELP

HOTLINE FOR TV & VIDEO
REPAIRS THOUSANDS OF
FAULTS & CURES ALL MAKES
JUST THE COST OF
A PHONE CALL

0891 516 434

48p PER MIN 36p CHEAP RATE

SERVICE INFORMATION

CIRCUITS & SERVICE MANUALS FROM 1930s - 1990s: radios, amps, radiograms, tuners, CDs, TVs, videos, cassette radios, ICE etc. LARGE QUANTITY USED TV PANELS. BACK COPIES PW, TV MAG.

Give details of your needs to:

DAVE WILLIAMS

Tel & Fax 0302 857526

23 Florence Ave, Balby,

Doncaster, South Yorkshire DN4 0QB

CAR RADIO SECURITY DECODING SOFTWARE

The most comprehensive software package ever for only £599.99+VAT

This package is fully upgradeable to any model of radio currently on our radio decoding list. Please phone for comprehensive radio decoding list and free demonstration disc (3 1/2")

Upgrades will even cover the latest radio's on the market. We can supply/design a package to decode any radio that you choose. Updated software available absolutely free.

Package comprises models including:-

Ford, Philips, Blaupunkt, Clarion, Pioneer, Panasonic, Grundig, Hitachi, Volvo, J.V.C. In fact over 50 models covered including Ford RDS V1 & V2, Grundig SC303

Interface & all necessary probes for connection to the radios are also supplied. Installed in seconds, no modification to your computer required.

Features:-

Fully IBM or compatible, to run on all computers including lap tops, note books and even palm tops. Requires graphics capability for P.C.B. layouts. Runs from parallel port of LPT1.

1. Full user friendly menu's
2. Help screens with P.C.B. layouts for exact positioning of probes
3. Help screens to show you exactly how to enter the codes after decoding the radio
4. Error messages to advise possible fault occurrences (e.g. incorrectly fitted probe)
5. Adjustable for either b&w or colour monitors (Useful for notebooks, laptops etc.)

6. Fully reprograms blank or corrupted eeproms (using internal database)
7. Customised with your company details
8. Security coded with your choice of code to stop unauthorised access
9. Runs from C drive
10. Keeps a record of all codes (date, time, make, model)
11. Fully upgradeable

Upgrades:- Check this out?

Memphis SQR 88, CDP09, Bremen, Atlanta, Montreux, Symphony, Koln, Philadelphia, Toronto, Montreal, Paris, Peugeot PF3, Vauxhall CD300, SC202, Berlin, Frankfurt, Barcelona, Stockholm, Kingston, Nashville, Woodstock, and many many more. POA.

RADIO DECODING SERVICE:-

WE COVER ALL MODELS STARTING FROM £10.00 + CARRIAGE (£4.20 EACH WAY) + VAT. That's only £16.69 or £21.62. If we arrange collection, all you have to do is make sure its boxed and adequately protected.

Eeprom re-programming service:-

All eeproms are decoded for as little as £5.00 including VAT. Please send all eeproms in a padded envelope, to stop damage.

CDH ELECTRONICS, keeping up with the times

3 Common Walk, Huntington, Cannock, Staffs. WS12 4NB

Tel: 0543 572 523 VAT Reg No 636 876 011

CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED

CRT FOR MONITOR, SCOPES, RADAR ETC (not domestic TV)

2J 3D P1	£12.00	1424A G1	£43.50
CV3946	£12.00	D14-270GH/50	£79.50
F21-12LC	£125.00	M31-190GR	£61.50
3JP1	£18.00	95447GM	£79.50
CV8897	£69.00	D15-100GH/97	£79.50
F31-12LD	£132.00	M31-191GW	£61.50
3RP1A	P.O.A.	CME1431W	£21.00
D10-210GH	£53.00	D16-100GH/67	£79.50
LD708	£61.60	M31-271W	£61.50
3WP1	£18.00	CME1523W	£27.00
D13-611GH	£53.00	DG7-5	£53.00
LD729	£61.50	M31-325BH	£29.00
5AP7	P.O.A.	CME2024W	£21.00
D13-611GM	£79.50	DG7-6	£61.50
M7-12OW	£15.75	M36-141W	£61.50
7ABP33A	£18.00	CME3132GH	£31.50
D13-630GM	£53.00	DG7-32	£28.80
M14-100GH	£18.00	M40-120W	£61.50
12CSP4	£27.00	CRE1400	£27.00
D14-150GH	£79.50	DG7-36	£12.00
M14-100LC	£23.50	M44-120LC	£61.50
89L	£27.00	CV1587	£29.00
D14-173GM	£79.50	E4412-B-9	£29.00
M17-151GVR	£112.00	MV6-5	£47.00
190CB4	£43.50	CV1976	£47.00
D14-173GR	£79.50	F16-101GM	£61.50
M23-112GV	£61.50	SE5FP31	£41.00
1074H	£43.50	CV2302	£79.50
D14-181GM	£79.50	F21-130GR	£41.00
M31-182V	£41.00	SE5JP31	£41.00
1396P	£43.50	CV2472	£61.50
D14-200GM	£79.50	F28-130LDS	£41.00
M31-184W	£41.00	SE32BP31	£41.00

Please add £5 p&p. in UK and 17.5% VAT For overseas p&p please enquire. 10,000 pieces in stock, 400 types. Please enquire for any type not listed above. We also have in stock camera tubes, image intensifiers, magnetrons, vidicons and audio valves. We wish to purchase valves type KT66, KT77, KT88, PX4, PX25, DA100. Minimum order £50 UK, £100 Export. Callers strictly by appointment only.

BILLINGTON EXPORT LIMITED Unit 1E,
Gillmans Industrial Estate,
Billingshurst, W Sussex,
RH14 9EZ, UK.
Tel: 0403 784961
Fax: 0403 783519

WANTED:

1000 lamps, 14V 40mA T-1, for car audio work - would import if necessary. Other non-specific car audio spares also wanted.

Geoff Davies,
13 Bowen Road,
Rugby CV22 5LF.

Tel: 0788 574774

Special Special Special

FOR BULK PURCHASERS -
A LIMITED QUANTITY OF ICs

TDA 8703	Price each = £7.50
TDA 8702	= £1.60
SA 5231	= £2.65
TC 5565	= £5.85
TA 7227	= £1.25
MAB 8461P W104	= £9.50
SAB 8052	= POA
P 8052AH/9252	= POA

ALSO BRAND NEW

TATUNG Automatic dehumidifiers	
Auto-Dri 2000A	£85 each
TATUNG Monochrome monitors	
VLMF 1024x768	£79 each

CDC ELECTRONICS

463 Green Lanes
LONDON N4 1HE
Tel: 081 341 5129
Fax: 081 341 5129

TV VIDEO SATELLITE FAULT GUIDE LINE FRYERNS

Most makes covered old and new. This service offers technical advice and cure plus Schematic diagram all for the price of £3.50
Access and Visa Fax Service
Phone 0268 558938 Anytime
4 Piney Mead, Basildon, Essex SS13 3BW

TUBES

REBUILT CRTs

VDU - MONITOR - TV

Image Burn-In Removed From Screen Phosphors

B.S.I. Certification

N.G.T. ELECTRONICS LTD
120, Selhurst Road, London SE25 6LL

PHONE: 081-771 3535

Britain's Oldest Established Tube Rebuilder

FOR SALE

Superb Opportunity!

to Expand & Diversify Your Business in Security

Installing an international award winning wirefree alarm system.

Buy direct from UK manufacturer at the lowest possible prices.

Massive demand - over 17 million untapped customers.

Very high profit margins available.

Excellent Free Factory Training

Tel: 061 257 3175

or Fax: 061 256 3024 or write to PAS,
Bankley House, Bankley Street,
Levenshulme, Manchester, M19 3PQ.



LINEAGE

AVO MULTIMETER Model 8, £45.00. 500 volt meters £30.00. Prices plus VAT and p&p. Send SAE for lists of Surplus instruments & Scopes etc. A.C. Electronics, 17 Apleton Grove, Leeds LS9 9EN. Tel: 0532 496048.

OCHRE MILL Technical Services, Grundig TV spares for most models to 1985, fast, friendly, helpful, sensible prices. Gt. Lype Farm, Charlton, Nr. Malmesbury, Wilts SN16 9DR. Tel: 0666 823228.

BREAKING VIDEOS many modern makes ring for prices 0952 883073.

PRIVATE RETAILER has excellent part exchange colour televisions and videos to clear. Tel: 0494 814317.

VIDEOCRYPT DECODER Service sheet with smartcard contact details Eurocrypt card interface £12. E.M.O. Ramsbottom, Lancs BL0 9AG. Tel: 0706 823036.

WANTED USER HANDBOOK or copy for the Mitsubishi VCR HS400B Contact Mr Neville on 0734 690945.

FOR SALE

BUSINESS FOR SALE Television/Video sales repairs, established 10 years, good stock, £10,000, includes stock. Unique position call 0322 526453.

BUSINESS FOR SALE TV/VIDEO Sales & Repair Leicestershire. T/O £75,000 P.A. L/H, L/Up shop £26,000 + s.a.v. (0602) 423588.

BUSINESS FOR SALE

FOR SALE

in High St Gwent

Well established TV/Video & Satellite retail business, 7 miles from Newport, consisting of freehold premises with 2 self contained flats, small shop area and workshops, small rental income, T/O £90,000 pa - **£100,000** for further details call 0633 615300.

TELEVISION CLASSIFIED LINEAGE

advertisements can be submitted on this coupon with a cheque made payable to Reed Business Publishing, Television Classified Room 11th Floor, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. The charge is £8.40 per line plus 17½% (minimum £33.60 + VAT.)

For Issue Dated or next available. Total insertions Total of Cheque £.....

Name Address.....

Post Code Tel Num Signature



Debit my Access/
Visa Card (delete)



Expiry Date VAT Reg. No. 238 8937 10

CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED CLASSIFIED


TEST EQUIPMENT

MÜTER · AT2 · BMR95 · BMR700

AT 2, Audi-Multi-Tester, 16 test-circuits for loudspeakers, tuners, amplifiers, headphones, tape recorders, mikes, boosters.



BMR 95
BMR 700

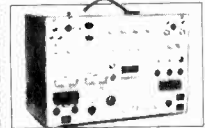

Regenerating Computers & Measurers for CRT's with cathode protection, gas clean-up aid, short repair: exhausted CRT's becomes bright and sharp again even if all other machines do not succeed.

car radios, CD-players; measurement of millivolt, drift, watt, performance; with generator, radio, signal tracer/injector, 13 volt supply etc.

United Kingdom: **P & E Services**, Llandudno, Tel. (0492) 549246, Fax 547880.
Ireland: **Dönberg Electronics**, Ranafast, Co. Donegal. Tel: 353 75 48275 and 48532. Fax: 353 75 71031.
New Zealand: **TDON Ltd.**, Onehunga, Auckland. Tel. 6 68-9 07, Fax 668-4 99.
Germany: **Ulrich Müter**, Oer-Erkenschwick, Fax (0 23 68) 5 70 17.

TRANSFORMERS

TV LINE OUTPUT TRANSFORMERS

PHONE 081-948 3702 FAX: 081-332 0583

ALBA · AMSTRAD · BUSH · DECCA · DORIC · BLAUPUNKT · FERGUSON · FIDELITY · GEC · GRUNDIG · GRANADA · HITACHI · HINARI · INDESIT · ITT · KIMARA · NIKKAI · MATSUI · MURPHY · OSAKI · NORDMENDE · LOEWE-OPTA · PANASONIC · PYE · PHILIPS · SANYO · SAISHO · SHARP · SONY · SOLOVOX · SUSUMU · TANDBERG · TELEFUNKEN · THORN · TRIUMPH · THOMSON · GOLDSTAR · BINATONE

FULL RANGE OF KONIG: VIDEO HEADS, BELT KITS, IDLERS, PINCH ROLLERS, TENSION BANDS.
LARGE RANGE OF REMOTE CONTROLS IN STOCK

TIDMAN MAIL ORDER LTD · 236 SANDYCOMBE ROAD · RICHMOND · SURREY · TW9 2EQ

Approx. 1 mile from Kew Bridge.

Mon-Fri 9 am to 12.30 pm & 1.30-4.30 pm

LOOK - CHEAP STOCK - MAKE EXTRA PROFIT

ALL STOCK IS NEW. A1. No 'B' Grade

Examples of This Month's Deals:-


NEW Midi Hi Fi: Twin Tape decks, Radio, Graphic, Belt drive record deck, speakers **£39.95**

NEW Walkman Headphones - Various Types **50p, £2.50, £3.45**

NEW Midi Hi Fi: CD, Twin Tape, Graphic, Radio, speakers only **£94.50**
Gold and Black living room clocks **£3.75**

AA Batteries **£1.65 per Dozen** AAA Batteries **£1.65 per Dozen**
PLEASE SEND S.A.E. OR FAX US FOR LATEST LIST.

The C.E.D./Semaht T101 CRT TESTER

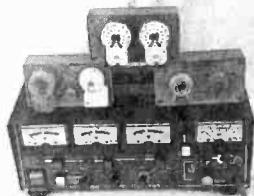

The T101 is a quad meter unit enabling all three guns on a colour CRT to be tested in Unison and then any guns that need re-activating can be done. The unit is user friendly and does not require elaborate setting up procedures. The unit employs CMOS IC circuitry and incorporates spike suppression and overload foldback protection measures, this coupled with

the unit being housed in a steel instrument case makes the unit robust. The T101 comes with plug-in base units, thus making it obsolete proof. The unit measures 12" x 8" x 5" and weights approx. 8lbs. Price: **£379.99**

Single meter version available: **£269.99**
PLEASE FAX OR SEND S.A.E. FOR FULL SPEC.

S. T. A. WHOLESALE

107 Riverview,
Chadwell St Mary, Grays
Essex RM16 4BA

Tel: 0375 856666
Fax: 0375 841540

PRICES AND STOCK CORRECT AT TIME OF GOING TO PRESS

MISCELLANEOUS

HOW THEY WORK! HOW TO TEST! HOW TO REPLACE!

Designed specifically for Domestic Appliance Engineers who want to enter the fast growing microwave Industry.

Packed full of useful information, presented in a simple yet informative style with comprehensive diagrams and illustrations. Fault finding procedures are included at the end of each section.


The book contains easy to follow electronic control systems

SWIFTPARK LIMITED

113 LONDON ROAD, HORNDEAN, WATERLOOVILLE, HANTS. PO8 0BJ

£14.95
plus £1.25 P. & P

ORDER YOUR COPY TODAY!

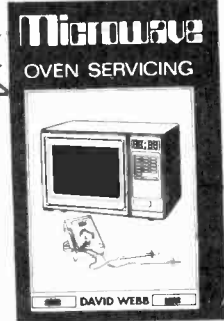


We also supply microwave oven components

Microwave Oven Component Parts

Guaranteed Quality

Guaranteed Products

Competitive Price

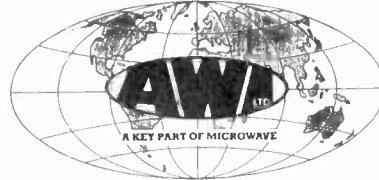

AWI Ltd, 29 Mariners View, Dodnor Ind Estate, Newport, Isle of Wight, PO30 5FA
Tel (0983) 520121 Fax: (0983) 520122

WANTED

Ex Rental TV & Videos, fast collection, fair prices paid.
Tel: 0742 312832.

FOR SALE TV/VCR REPAIR BUSINESS

In Historic Yorkshire. Leasehold shop, with luxury one-bed flat above. T/O £80K +. Very high profit margin, superb area to live and work £15,000 o.n.o. + S.A.V
NO TIME WASTERS PLEASE
Box No A4384.

SOUTH LONDON TRADE WAREHOUSE

NOW OPEN

BEST STOCK

MAJOR BRAND NAMES

BEST PRICES

WHOLESALE

OF THORN + NON-THORN EX-RENTAL TV's & V.C.R., TESTED + UNTESTED 'B' GRADE + LIQUIDATION STOCK

AUDIO: Stocks of Audio, Midi + Mini Hi-Fi CD's

Radio Cassettes, Walkmans, ALL TOP BRAND NAMES AT FRACTION OF RETAIL PRICE

STOCK ALWAYS CHANGING

TEPCO ELECTRONICS LTD

TEL 081-769 6149 Ask for Chris
071-924 1606 Ask for Tony
081-677 5749 Warehouse Line

FAX 081-769 4952

OPEN MON-SAT 9.30 TO 6pm

**NEW
 EDITION**

VIDEO SERVICING 1991-92

Three Volume Set. Covers 322 Models From 44 Manufacturers. ISBN 095 3897 5 0 - £195.00

AIWA HV DK950 HV E506MK2 HV E555 HV F85 HV F125 HV G50 HV G51 HV G53 HV G71 HV G73 HV G75 HV M110 HV MG330 AKAI VS F10 VS F11 VS F15 VS F30 VS F33 ALBA KVCP 9000 VCP 2000 VCR 2222 VCR 6100 VCR 6300 VCR 6400 VCR 6700 VCR 6800 VCR 6900 VCR 7800 VCR 7900 VCR 7950 VCR 8800 AMSTRAD DD8900 DD8904 VCR 3000 VCR 3002 VCR 8800 VCR 9000 VCR 9004 VCR 9140 VCR 9340 BUSH VCR 174 VCR 185 VCR 190T VCR 3402	BUSH VCR 3452 CATHAY 7110 DANSAI VCR 803 DECCA DVR 6611 DVR 6621 DVR 6651 DVR 6641 DE GRAAF WHS HY2 WHS HY4 FERGUSON FV 41R FV 42L FV 43H FV 44L FV 45X FV 46T FV 50B FV 51R FV 52L FV 54LX FV 58T FV 60B FV 61LV FV 62LV GV 67HV FIDELITY VCR 200 VCR 201 VCR 3000 FINLUX VR 4300 VR 4500 VR 5250 VR 5350 GOLDSTAR D-09 MECH D-16 MECH GHV 1891 I GHV 4400 I GHV 7430 I GHV 9400 I GSE 1290 IQ GSE 1291 IQ GSE 1292 IQ	GOLDSTAR GSE 1293 IQ GSE 1295 IQ GSE 1296 IQ GSE 1297 IQ GSE 1298 IQ GSE 1891 I GSE 2000 IQ GSE 2001 IQ GSE 2005 IQ VCP 100 I GOODMANS 2700 V DX 3600 PX 2400 TX 1200 TX 3650 GVR 3450 GVR 6750 VCP 600 GRANADA VWHS KT2 VWHS KT5 VWHS JQ4 VWHS HJ2 VWHS HNG VWHS HP1 VWHS HP3 VWHS GP1 VWHS GP3 VWHS GP6 VWHS GP7 VWHS JS6 VWHS KS5 VWHS HS2 VWHS HY3 VWHS JY2 VWHS KY3 GRUNDIG G2 MECH GG1-II MECH VS 505 VS 510 VS 540 NC VS 600 VS 610 VS 620 VS 630 VS 640	GRUNDIG VS 660 VS 700 VS 710 VS 720 VS 800 VS 810 VS 900 VS 901 VS 910 GB VS 910 VS 920 HARWOOD VCR 44 HINARI HIT 2V HITACHI VT F150E VT F770E VT F780E VT F860 VT M140E VT M112E VT M720 VT M722E VT M740 VT M753E VT M640E VT M620 VT M622 VT M630 ITT/NOKIA VR 3701 VR 3721 VR 3731 VR 3731 JK VR 3731 VPS VR 3742 VR 3742 UK VR 3742 VPS VR 3761 VR 3761 NICAM VR 3761 UK VR 3761 VPS VR 3799UK JVC HR D520 HR D540	JVC HR D560 HR D580 HR D620 HR D640 HR D660 HR D720 HR D820 HR D860 HR D910 HR D960 KOYOTO VCR 170 LUXOR VR 3701 LX VR 3721 LX VR 3731 LX VR 3761 LX NICAM MATSUI VCP 500 VCP 550 VX 1000 VX 1000Y VX 1000Y'P VX 2000 VX 2000Y VX 2500 MITSUBISHI HS B12 HS B16 HS B27 HS B31 HS B32 HS B52 HS M34 HS M54 HS M55 HS M61 NEC N 9077K NS 7000K NIKKAI J-2 JVP-01 NVR 3 ORION D 500X D 1500	ORION D 1500X PANASONIC NV F55 NV F65 NV F75 NV J40 NV J42 NV J45 NV J47 PHILIPS VR 25B11 VR 201 VR 202 VR 203 VR 211 VR 212 VR 213 VR 215 VR 223 VR 302 VR 303 VR 311 VR 312 VR 313 VR 322 VR 323 VR 3210 VR 3219 VR 3229 VR 412 VR 415 VR 502 VR 6290 VR 6293 PHILIPS VR 6390 VR 6393 VR 6485 VR 75B02 VR 702 VR 703 VR 712 VR 713 VR 6585 PIIONEER VR 737	PYE DV 291 DV 391 20 DV1 20 DV2 30 DV2 21 DV1 31 DV1 41 DV2 ROADSTAR VCR 7620 RUMBELOWS VCR 9500 SAISHO 140T SALORA SV 601 SAMSUNG PI 990R PI 991R PI 992R SI 1240 SI 1260 SI 3260 SI 3261 SI 3240 SI 7220 SI 7230 V 1560 V 3560 VI 8220 VX 1860 VI 1860 SANYO VHR 135 VHR 120 VHR 141 VHR 150 VHR 153 VHR 171 VHR 190E VHR 205 VHR 251E VHR 290 VHR 291E VHR 7200 VHR 7200R VHR 7250	SANYO VHR 7260 VHR D4710 VHR D4880 SENTRA VCR 7620 VCR 7620L SHARP VC A113HM VC A30 HM VC A40 HM VC A33 HM VC A43 HM VC A48 HM VC A45 HM VC A60 HM VC A63 HM VC A215HM VC A615 HM VC H81 HM VC H84 HM VC H86 HM SONY SLV 262 SC/MP SLC 270 UB SLV 353 UB SLV 373 UB SLV 415 UB SLV 315 UB SLV 615 SLV 715 SSANGYONG SVR 101 TATUNG TVR 6112 TVR 6113 TVR 6114 TVR 6122 TVR 6141 TVR 6151 TOSHIBA V 110B V 210B V 211B V 411B V 610B V 611B V 711B VCP B1B
--	--	---	--	---	---	---	--

TELEVISION SERVICING 1991-92

Covers 247 Models From 43 Manufacturers. ISBN 0 951 3897 7 7 - £89.00

AKAI CT 2569 CT 2579N CT 2869 CT 2870N CT 2879N CT 2158 CT 2158 CT 2160 ALBA CTV 52 CTV 56 CTV 57 CTV 703 CTV 704T CTV 711 CTV 712 CTV 713 CTV 741 CTV 742 CTV 743 CTV 744 CTV 746 CTV 747 CTV 748 CTV 752	BAIRD RF6890 BOOTS CTV 1414 CTV 1414 CTV 1010 BEON 3214S 1412 BUSH CTV 100 DE GRAAF C36JS2 C51HS4 C14HSB C59JZ5 D41HS4 D51HS4 D51HZ5 D59HS4 FERGUSON 41 P3 A 51F 66 M3 78 M5 J59 P8A Repair Hints 2914	BUSH 2921 2921T 3014 3114 3114T 3214S 4414 CTV 100 DE GRAAF C36JS2 C51HS4 C14HSB C59JZ5 D41HS4 D51HS4 D51HZ5 D59HS4 FERGUSON 41 P3 A 51F 66 M3 78 M5 J59 P8A Repair Hints 2914	FIDELITY CTV 920 FINLANDIA C51HZE D59HZ5 D66HZ5 FINLUX 3815 3821 GOLDSTAR CIT 2168 CIT 2168F CIT 2190F CIT 2191F CIT 4902 CIT 9902F GOODMANS 145 TT 2032 GRANADA C 51GV2/4 CUC 3840 CUC 4400 CUC 4401 CUC 4410	GRUNDIG CUC 4500 CUC 4510 CUC 4511 CUC 5300 CUC 5820 CUC 5835 CUC 5836 CUC 5866 CUC 5880 CUC 5891 HARWOOD 9014R HINARI HIT 10R HIT 14 HIT 14S HIT 14T HIT 14RS HIT 14R HIT 20R HIT 51T HITACHI C14 P216 C 14 P218 C 1709 C 2118R	HITACHI C 2118T C 2519TG CFT 2196 CFT 2198 CFT 2578 CFT 2596 CFT 2598 CFT 2598A INDIANNA 219R 100MKI & MKII ITT/NOKIA 26 29 2560 2860 3670 5551 5581 5581 UK 6351 6361 6387 6856 6887 7161	JVC AV 21F1EK AV 25F1EK AV N280BKT LOGIC 4698 L JXOR 6392 MATSUI 219T 1420 1420B 1435 1435B 1435C 1440 1440B 1445 1445 1455 1480B 1481 1481B 2180 2180JTTA 2185 2899N	NEI 2180TTA 2185 2899N 1451R 1451TX 1481B 2180 TX 21V1 1551TX 2131TR 2131TX NIKKAI NT 14 NT 20 TLG 200 TLG 601 TLG 2121 TLG 2122 TLG 2800 2155 2156T ORION 14ARX 14ARXS 14ARXG 14AT 14VR	OSAKI 3214S OSUME CTV 1474R PANASONIC TC 21R1 TX 21T1 TX 21V1 TX 24A1 TX 25W2 TX 25W2A TX 28W2 TX 28A1 TX 33A1G TC 1100G TC 1485 TC 1785 TX 1788 PERDIO P 408 P 2004 P2005 P2101 P2102 S'X 400 PHILIPS 2070	PHILIPS 2080 1021 1221 2331 2341 2554 2752 5560 5664 5668 5762 5764 5772 8840 8841 9666 9762 9762 9762 9762 9637 9762 9762 9762 9762 C 1210R	P-HILIPS 9772 P ONEER SJ 21AV SJ 25AV SJ 28AV PVE 1240 1342 1328 2825 2525 2529 SAISHO CM 215TS CM 2080T CT 141 CT 141B CT 143 CT 144B CT 144R CT 146TX CT 149TXA PST 212TA SAMSUNG C 1210R C 13312Z C 15012Z C 15013T C 15322T SALORA 21 D 61 21 D 81 25 D 61 26 A 42 28 D 81 SANYO CBP 2572 CBP 2573 CBP 2872 CBP 2873 CBP 2558 CBP 2559 CBP 2162 SHARP C 1430H C 1431H C 3720H	SHARP DV 51083H DV 59083H DV 66083H SV 2588H SV 2888H SV 2199H SV 2599H SV2889H SV 3220H 218 D9B 217 D9B2 218 D9B 219 F9B 219 T9B 256 T9B 329 T7B 1400 RBT 1400 RBW 1400 TBT 1400 TBW 2100 RBT 2100 TBT 2500 TBT 2501 TBZ 2505 DBT 2805 DBT 0014	TATUNG A Series TOSHIBA 216 F9B 216 F9B2 216 T9B 216 T9B2 217 D9B 217 D9B2 218 D9B 219 F9B 219 T9B 256 T9B 329 T7B 1400 RBT 1400 RBW 1400 TBT 1400 TBW 2100 RBT 2100 TBT 2500 TBT 2501 TBZ 2505 DBT 2805 DBT
---	---	---	--	--	--	---	--	--	---	--	--	---

SATELLITE SERVICING 1987-90 - £59.00

Covering 127 Models From 42 Manufacturers ISBN: 0 951 3897 6 9

SATELLITE SERVICING 1991-92 - £65.00

Covering 251 Models From 68 Manufacturers ISBN 0 951 3897 8 5

TELEVISION SERVICING 1989-90 - £69.00

Covering 461 Models From 43 Manufacturers ISBN: 0 951 3897 1 8

VIDEO SERVICING 1989-90 - £145.00

TWO 336 Page Volumes Covering 236 Models From 44 Manufacturers ISBN: 0 951 3897 2 6

Send For Brochure Listing Other Books Available From U-View

All Prices Include JK Post, Packing & Insurance



ALL BOOKS CONTAIN

Circuit Diagrams: Scope Readings: Voltage Tables: Essential Part Nos: Alignments & Adjustments: Trouble Shooting Guides

U-VIEW

4 South Parade, Bawtry, Doncaster,
 Yorkshire, England. DN10 6JH
 Tel: 0302 719997 Fax: 0302 719995

MARCONI COMPACT L.N.B. 1.DB £30 10.7 TO 11.7GHZ		60cm BACK MESH DISH £20, £5 post		12v Satellite Receiver with hand set £30 Switched Mode Trans 3112. 338. 32642 Ferguson £1 Philips switched mode transformers for K40 £5		VIDEO AMSTRAD HANDSETS (HOME MARKET) £7.00 (EXPORT) £2.50 WILL WORK IN HOME MARKET		SEND FOR DATA D2 MAC SATELLITE RECEIVER £35 (£10 Post)			
SATELLITE RECEIVERS - New Ferguson BSB Chassis with Tuner, Modulator etc £10 Hand Set £1.50 £4 Post			SAT RECEIVER EARLY BIRD £25 33V33, 3V37 BATTERY £10 Postage £5			TX100 HAND SRT (785) £10 Power Supply 0-15 Volts 0-30 Volts 3 Amps with Meters £34 Post £5		New Eprom for converting Ferguson BSB Receivers to D2 MAC and PAL - 99 channel is tunable and each one can be put into memory - also has menu. £20 PAL panel (to convert to PAL) £20 SEND FOR DATA			
SMALL SATELLITE TUNERS (950 to 1750 MHz), L.F. frequency 4000MH £9.00 each VHF/UHF S.BAND TUNER £3.00 DAM MAINS CHASSIS AMSTRAD MONITOR C £10 UNIVERSAL TRIPLER. NEW TYPE £4.00 VIDEO LEADS 80p AMSTRAD Line O.P. Transistors with Diode 2SD/453 £1.00 VIDEO LAMPS. Long Lead 24p HITACHI & GEC FRAME, Thick Film £6.00 FIDELITY SPLIT DIODE FCC2215AE £20 FCC2015BE £10 FCC2215BE £10 K30 FRONT PANEL TEL-TEX TYPE £5.00 NEW G11 LINE OP PANEL £8.00				CAMRECORDER SANYO NP22 6v 1300mah Rechargeable Battery Pack £6.00		LEADS Scart to Scart all pin connected £2.00		Gas Soldering Irons New Type £10.00 Variety Nickel Cadmium Batteries from Telephone Type to Sub-C.50p per cell. Mainly in packs of 6 to 8.		TELEPHONE BATTERY SANYO 3.6V 250/MA - £2 VARTA 3.5V 280 M/A £3.00 FEEDHORN FOR OFFSET ANTENNA £8.00 HITACHI U/V HAND SET VIDEO £10	
PHILIPS YEARS AHEAD THE CREDIT CARD CALCULATOR Solar Powered £3.75 NEW PHILIPS SBC 1833 Solar & Battery Powered Calculator £8.00 THORN PANEL TX9 REC & REMOTE PANELS with Mains Trans £5.00 TX10 REC & REMOTE PANELS with Mains Trans £5.00 TX100 FRONT PANEL £5.00 TX10 TUBE BASE ON PANEL £3.00 TX91F £2.00 THORN PANEL No. 515-353, 548, 02, 565-01, 509/102, 515/173, 508/161 £1.00 THORN TX STEREO SOUND O.P. PANEL (I.C. TA727P) £1.00 THORN VIDEO AERIAL AMP 01 M4-597-001 £6.00 ULTRASONIC TRANSDUCER 15p				SATELLITE UNIT Video Out/Audio Out, L and R Polariser ± 35M/A and Decoder Socket £10		HITACHI UHF-VHF SMALL TUNER ETS98A £5.00 ETS95A £5.00		GREY OR BLACK £1.50 SAMP MAINS LEAD WITH PLUG SOCKET FOR TEST EQUIPMENT ETC.		THORN M494B1 on Remote Panel £5 THORN TDA 3652 IS OBSOLETE REPLACEMENT TDA 3654 £2.00	
TX100 REMOTE PANEL No.564131C M293B/and SAA5012 £10 etc		144MHz Changed Over Relay Aerial 50p		PHILIPS UNIVERSAL BATTERY TESTER SBC 1695 £3.00		NEW DETECTOR £10.00 PHONE HOME TO CHECK WHETHER YOU HAVE AN INTRUDER SEND FOR DATA WITH TELEPHONE £20 00		TX100 SWITCH MODE TRANS 5157/48 £5 AND 00D4252001 06D3082001			
TX100 REMOTE PANEL IC £10		6251 FRAME O/P THICK FILM HITACHI GEC £9.00 THICK FILM HITACHI HM9205A £4.00		REGULATED PWR. SUP. 500MA/1 5V-12V DC switched + & - £5.00		MADE BY PLESSEY - MADE IN ENGLAND New public telephone exchange original price cost £299.00 Network exchange line (at home or in a small business) has two telephones and cables and NS5107 control unit SPECIAL PRICE £40 Send for data		STEREO SOLAR RADIO VHF AND MW £10.00 G11 470 MFD 250v £1.35 3V33 HAND SET £10 12 Volt Relays 20p with D/P changeover PHONO I/O LEADS 3 Metre 30p LEAD SCART TO D PLUG 50p			
NICAM UNIT - Ferguson made for ICC5 Chassis - home market and export - has circuit diagram and can be converted to most sets - £15. TOSHIBA Nicam panel & IF export only has the Toshiba chip set £7.00		TX10 REMOTE PANEL £5 TX9-TX100 FRONT PANEL £5 WITH REMOTE £10 NON REMOTE 8 push button £10		LARGE Foacs Pots. Fits Pye, GEC, ITT, Decca 75p		DECODER C-CAM PHILIPS MADE for K40 CHASSIS IC No. TDA 3590 £5.00		BRIDGES RECTIFIER Mixed BR-31 to 34 2 Amp to 5 Amp 8 for £1.00 1 METRE SCART LEAD £1.00 BURGLAR ALARM USE INFRA RED DETECTOR WIDE AND SHORT ANGLE WALL MOUNT £8 WITH RELAY TUNER U/V 616 £10 TUNER U/V 816 £10 POWER SUPPLY KIT 0.28 volts 1 1/2 amps with 2 meters £12 Printed circuit board and components MODULATOR KIT £5 5v to 12v for all cameras etc			
BSB SAT/REC NEW. CHASSIS, TUNER AND MOD £5 + Post £3		PHILIPS NEW TYPE U/V HANDSET £10		MIXED TOSHIBA HAND SETS FIVE FOR £12		56420A 20A/600V THYRISTOR £1.75 ITT BG2032-642A TRIPLER £5.00 ITT/KOKIA HF IF MODULE 24K No 5828-04-10 £15.00 Tere 7-098A - 115-B-2010 ECC-2885PLE TEEF 1-030A UHF, VHF TUNER - SMALL TYPE £4 EACH BRIDGE RECTIFIERS - MIXED 10 FOR £1 TVK 186-5 TRIPLER £3.50 TVK 76-5 £3.50		Have you got Acid Rain in your garden? PH METER £5.00 Post £5 Actuator Antennemotor £15.00			
G11 LOPT Panel £4.00 G11 Tip Switch £20.00 G11 IF Panel £3.00 G11 Decoder Panel £2.00 G8 Push Button Unit £2.00 G8 Con/Panel New Back Type £4.00		TX100 FRONT PANEL £5 8 Button SALORA SAT RECEIVER CONVERSION KIT For models 24M60, 25M90, 28M90, SB1206E, SB1365 £15 TX90 TO TX100 8 BUTTON UNIT £4.00		LATEST VIDEO For Latest Philips, GEC, Pye and Hitachi, Front panel with memory chip and push button and pots and LED's £6.00 NEW		FERGUSON CHASSIS IKC-2000 £20 TX86 Chassis £14 NEW TX100 CHASSIS YELLOW SPOT £20 TX90 CHASSIS WHITE SPOT £20 NEW TX10 CHASSIS £20 Post each, £6 TX80 CHASSIS £20		SHARP MSHIFCF09 £10 FIT MOST SETS New Thorn 0004-235 Hand Set 002-01 Type u/v (£10) VIDEO MOTOR for VT568 type VMC2DD8 £8.00 AMP TUNER IF for VT568 Hitachi & GEC £9.00			
LNC 11GHZ NOKIA - LNB FOR OFFSET DISH £13.00 ELECTROMAGNETIC POLARIZER 10.95 - 12.75 GHZ £9.00 11GHZ LOW NOISE BLOCK DOWN CONVERTER SCE 975 MADE BY MASPRO £14.00 5 Mixed AMSTRAD VIDEO MOTORS £5.00 SATELLITE TUNER UNIT 2427611 with Base Band, Video Out £8.00 TX10 8 way button unit £8.00 24v 0.24v 3amp MAINS TRANSFORMER £3.00 10 MIXED FERGUSON CIRCUIT DIAGRAMS £5.00 MSHIFCF09 £7.77		TX85 36761 36881 2435701 2434393 2435016 2435014 £10 2436797 2434494 £15		TRANSFORMERS 24357/01 £10 2435012 £10 FERGUSON 47003481 £10 AMSTRAD TVR3 LPTS £10 TFB3069D EQU TFB4009AN		AT2036/00 AT2076/55 AT2048/11 AT2076/11 AT2055 RCO ST CA3325 AT2076/35 OT2041 AT2076/38 FB165KA Orion AT2076/51 2076/51 CVC 820 2432461 2433451 CVC 800		BRIDGE RECTIFIERS 10 FOR £1.00 4 Amp for Video Power Supply			
2433752 £20 2432964 2432871 2432301 2435016 2433952 2434993 2432211 T9048A DSTR5B243 TFB3069D K4 L.O. P.T. K40 2433452 2432904 2434451 £14		SPLIT-DIODE 2433752 £15 TX100 Green Spot £15.00 TX100 Yellow Spot L.O.P.T. £10.00 TX90 White Spot L.O.P.T. £15.00 Split Diode 110° £12.50 Orion 65-3M GEC 85-9793-6 TX9 Thorn 2432101-2 £5 2434141 EACH £10 2434492 2434493		DST 8IN243 36761 TFB4023AD £10.00 MSHIFPT131 £12.00 MSHIFWB27 £12.00 DST186N243 £10.00 3220029 £10.00 13651 36072 36342 36482 36761 36831 36832 36833 36921/79 36922/79		AT2036/00 AT2076/55 AT2048/11 AT2076/11 AT2055 RCO ST CA3325 AT2076/35 OT2041 AT2076/38 FB165KA Orion AT2076/51 2076/51 CVC 820 2432461 2433451 CVC 800		BRIDGE RECTIFIERS 10 FOR £1.00 4 Amp for Video Power Supply			
SATELLITE TUNER 950MHz-1750MHz £5.00 TTT PANEL CMC 301 CMC 113 CMC 302 CMC 115 CMC £5.00 303 CMC 964 VIDEO LEADS 4 for £1 SEL ITT 1FB254F/2 Front Panel £15.00 DECCA - GEC - ITT 6 push button £5.00		BURGLAR ALARM £2.00 with siren 9 VOLT 25 Way Plug and Socket with Case £1.50		PHILIPS HAND SET G11 TEXT ULTRASONIC £10 PHILIPS RC5 EASY CONTROL £10 INFRA RED DETECTOR (for outside use) with Time Control & Distance Control £12 Sensitivity Adjustment Control Nigh Adjustment Time Delay Adjustment TRV3 Amstrad Cassette Mechanisms. New with 2 motors and sound head. £15 £5. Amstrad Television Tuner UHF. Small, Fits most Amstrads. £6.		U/V 6, DIODE TRIPLERS £2.00 4600 TO 8600 AMSTRAD VIDEO HAND SET WITH LCD £10 NICAM M418 KIT MODULE £20.00 with data Burglar Alarm Has time delay to set £2 Mains Transformer £4.00 240v in 110V to 120v out 1 amp post £3					
SENDZ SEE BACK PAGE											

SENDZ COMPONENTS

0702 338894
(To order see back page)

LA11440	£1.00	TUNER UNITS TX90/TX190 Tuners with AE socket Thorn TX Tuner V/Cap eqv. to ELC1043 £4.50 Thorn TX10 Export V/Cap UHF VHF £3.00 ENV 5783G2F UHF/VHF Small NEW G8 Tuner V/Cap £3.50 ELC200 on Panel £7.00 EG613F £6.00 VHF/UHF 2 BEOT545A £6.00 ELC2000 NEW £4.00 EI C2003 £4.00 GEC Tuner V/Cap Hitachi Alter 1979 E1548, E1547, E1541B £8.00 E1546 £6.00 E1598A UHF/VHF Miniature Tuner Hitachi £5.00 EI C1042 £6.00 FLC1043 £6.00	Turntable Satellite Modulator TV Sound 5.5MHz MPM 1001 £1 Sound 6.0MHz MPM 1040 £1	PHILIPS RCS410P £8 HAND SET
M584N4P HA51338 SP TAA7750 HA11485 ANT UPC1373 MS5857P M491BB1 M5041/550 MS5858P M50430 - 850 SP M50143 011P	£2 £3 50p £2.00 50p £1.00 £3.00 £1.00 £1.00 £1	TX90/TX190 Tuners with AE socket Thorn TX Tuner V/Cap eqv. to ELC1043 £4.50 Thorn TX10 Export V/Cap UHF VHF £3.00 ENV 5783G2F UHF/VHF Small NEW G8 Tuner V/Cap £3.50 ELC200 on Panel £7.00 EG613F £6.00 VHF/UHF 2 BEOT545A £6.00 ELC2000 NEW £4.00 EI C2003 £4.00 GEC Tuner V/Cap Hitachi Alter 1979 E1548, E1547, E1541B £8.00 E1546 £6.00 E1598A UHF/VHF Miniature Tuner Hitachi £5.00 EI C1042 £6.00 FLC1043 £6.00	FEROX Cost £2.50 RF Filter Clamp for CoAx Cable Circuit for detecting R.F. Send for circuit using clamp (25p each)	ICC5 E/W COIL £2
Receiver TX100 Panel I.C. No. SAB3035 —MAB844P D066 —SAA1094 —PCF8871P	£10	Monitor Astec UM1233 50p	Ferguson Switch Mode Transformer TX85, TX86, TX100 £3.50 each	EARLY BIRD SAT TUNER WITH 950-1750 MHz BASE BAND £6 WITH DATA
20 off £2.00 High Voltage Condenser 1N5 to 8N2, 1500V to 2KV	£2	L3E33-B01 Amstrad UHF Tuner £5.00 VHF/UHF EG522F £6.00 AS/TEC UM1183 £10.00 V314 (VHF) £5.00 V334 £4.00 U321 £6.00 U341 UHF £6.00 U342 (UHF) £5.00 U343 Photo £6.00 U344 Coax £6.00 U343C £6.00 U344C £10.00 U411 UHF £4.00 UVF10 £8.00 UV411 Tuner £8.00 UV417 £5.00 UV418 Tuner £5.00 UHF/VHF Tuner 1500 DKO £3.50 U3743 Tuner £5.75 U944 Tuner £5.75 Fidelity Amstrad 2000 V/Cap Tuner Small V/Cap Mitsumi - UHF £4.00 - VHF £3.00	ICC5 Ferguson Switch Mod Trans 3112-338-32642 £4.00	FERGUSON LOPT FST 24" TX100 - 260482 £15
TX9 C CAM Decoder	£5.00	Portable & Rotary Tuners Sanyo & Mitsumi UHF £5.00 Mullard UHF VHF (new type) £8.00 U12 B31 Fidelity V/Cap Tuner £6.00 UHF-VHF V/Caps on panel £3.00 HITACHI 20 Turn Pot 40p U321 ca panel £6.00	12v DC and 24v DC power supply regulated ICC5 L.O.P. 1. DN1 88B243 DN1 85B243 Thorn Mixed £10.00 each £10.00	LOPTS AMSTRAD 3714016 £5 3216001 £5
BB 103 BB 105A x12 BB 105B x12 BB 105G x12 BB121a	10p £1.00 £1.00 £1.00 10p	Change over switch co-ax type box with lead 50p	Ferguson Hand Set ICC5 IK3000 IK3001 £5	TOSHIBA REMOTE CT9123 £4
1A/1600V DG3P EQV - HY228 2 amp bridge rec. wire end SKE4 (200) Eqv. BYX71 600 500ms	10p 10 for £1.00 15p 15p	UF7496 Tuner £5 EF 321 £5 EG 311F £5 UF744 BAV £3 UF745 BAV £3 UHF Tuner and IF in one can (small) £5.00	Special Price £13.00 RC4001 KT3 and Teletex £14.00 TX10 Hand Set Text £12.50 TX9 with Text £12.50 TX9 & TX10 button print £1.00 TX10 Focus Pots £5.50	AMSTRAD SANKYO CAPSTAN MOTOR 6,000 £3 AMSTRAD LOADING MOTOR 6,000 £1
6 Push button switch FT1 GEC CVC45 ETC	£3.00	Co-Ax Belling Lee Plug Co-Ax Splitter £1.00 Intra Red Emitting Diode 20p NE266H Small Neon Lamps GEC & Philips 5p	Mains Stand By Switch with Coil £1.00	GRUNDIG TRIPLER BG-2032-642-3002 £5
Hitachi TV IC HA51338SP/3	£3.00	WE HAVE OVER 250 TYPES OF STK AND STR I.C.S. SEND FOR LIST	PHILIPS UNIVERSAL HAND SET £12.00 RC5 KT3 - K45 - £10.00	HAND SETS FOR 8600 SERIES AMSTRAD FOREIGN ORIGIN WITH L.C.D. £3
TT14 GEC TEX-DECODER 13 IC Panel with cable form	£9.50	85-4538-3 Tatung GEC 8 Button Unit Print Type 1990 to 1992 £5.00	PHILIPS K35-K4 HAND SET Repaired for £5.00	FERGUSON PAY HAND SET 4 FOR £1
PHILIPS Decoder SAA IC S120-S130 S140B-S150	£4.00	Philips Handset IC SAA3010P £3.00 MAB8461V063 £3.00	PHILIPS RC5171 (HAND SET) £12.00	TOSHIBA REMOTE CT9233 AND CT938 £3
K40 Text Panel	£4.00	BG 2087 - 642 - 1005 Tripler Grundig £7	PHILIPS RC5177	TOSHIBA T/V TUNER. IF ENV 5783 G2F £3
ICC5 TUBE BASE ON PANEL ICC5 DECODER PANEL ICC5 TEXT PANEL	£5.00 £15.00 £15	Philips Handset IC SAA3010P £3.00 MAB8461V063 £3.00	TEXT-TYPE Replace Hand Set for Philips KT3-K20, K4 etc £12.50	HITACHI STAND BY MAIN TRANS £10 2213881 AND L210049
K35 Decoder K35 Sound OP Thick Film Daughter Kt3 33122-127-43891	£8.00 £4.00 £3.00	85-4538-3 Tatung GEC 8 Button Unit Print Type 1990 to 1992 £5.00	THORN HAND SETS 9000 - 9600 - TX9 - TX10 - TX100 Text and Non-Text £10.00	PHILIPS K35 ETC 12 WAY SWITCH WITH KNOBS 50p
12 CH K30 Tex Rec. Front Panel with I.C.	£5.00	Philips Handset IC SAA3010P £3.00 MAB8461V063 £3.00	PHILIPS RC5177	60.40 SOLDER 500G £4
K4 Focus Pot K40	£1.00	85-4538-3 Tatung GEC 8 Button Unit Print Type 1990 to 1992 £5.00	PHILIPS RC5177	HIGH GAIN T/V ANTENNA UHF-VHF BUILT IN 32DB AMP 12V DC/220 AC £9.25
Fidelity Tube Base with transistor & focus pot	£1.50	Philips Handset IC SAA3010P £3.00 MAB8461V063 £3.00	PHILIPS RC5177	AMSTRAD VIDEO FRONTS WITH FLAP LONG CHASSIS ALL MODELS MADE IN 1991 TO 1992 AND DECCA PRO LINE £3
TX10 Tube Base on Panel	£3.00	Philips Handset IC SAA3010P £3.00 MAB8461V063 £3.00	PHILIPS RC5177	(ATAD) £20 AUTOMATIC TELEPHONE ALARM DIALER SEND FOR DATA
PHILIPS HAND SET K35-K4-K30, etc	£10	Philips Handset IC SAA3010P £3.00 MAB8461V063 £3.00	PHILIPS RC5177	AMSTRAD 6000 HEAD WITH MOTOR LP £10
Universal Tripler with small focus pot. Green type	£7.00	Philips Handset IC SAA3010P £3.00 MAB8461V063 £3.00	PHILIPS RC5177	AMSTRAD - LONG CHASSIS AND SHORT CHASSIS POWER SUPPLY £4 MODELS 1991 TO 1992
THORN CASSETTE HOUSING PAS2680SU	£18.00	Philips Handset IC SAA3010P £3.00 MAB8461V063 £3.00	PHILIPS RC5177	AMSTRAD - DOUBLE DECKER SWITCH MODE £8 POWER SUPPLY
LITHIUM BATTERY BR-2/3 Vols	20p	Philips Handset IC SAA3010P £3.00 MAB8461V063 £3.00	PHILIPS RC5177	AMSTRAD - DOUBLE DECKER PANELS £5 each. DOUBLE DECKER FRONT £6 with flaps
TUNER, SAT 2000 KHC	£8	Philips Handset IC SAA3010P £3.00 MAB8461V063 £3.00	PHILIPS RC5177	AMSTRAD LONG CHASSIS DISPLAY PANEL 1992 TO 1993 £4
HITACHI IC D1514C 036 D1514C 146 MN1250BJC ST6393 B10Y 11D614808A90 1MP47C1637N M59442-5538P	£3 E A C H	Philips Handset IC SAA3010P £3.00 MAB8461V063 £3.00	PHILIPS RC5177	AMSTRAD TUNER UE33-B01 £3 IF £2
International Rectifier IFT Diodes G7701 HV349KV3 for 8p 6A/600V Stud Diodes 20p B17W 92800K £3.00 D1 701 50p 6A/1000V Stud Diodes 20p 2A4A73 PNP/C/P 10p DL 711 Mullard 50p		Philips Handset IC SAA3010P £3.00 MAB8461V063 £3.00	PHILIPS RC5177	6 FOR £10 TX10 FOCUS UNIT
		Philips Handset IC SAA3010P £3.00 MAB8461V063 £3.00	PHILIPS RC5177	CONVERSION KIT IFT TELETEx £8 HURGLAR ALARM SIREN 12 VOLT 50p
		Philips Handset IC SAA3010P £3.00 MAB8461V063 £3.00	PHILIPS RC5177	HANDSETS AMSTRAD EASY CONTROL MODELS 4600 TO 8600 £3 each
		Philips Handset IC SAA3010P £3.00 MAB8461V063 £3.00	PHILIPS RC5177	FERGUSON THOMSON SAT HANDSET SRD1 TO SRD4 £2 each
		Philips Handset IC SAA3010P £3.00 MAB8461V063 £3.00	PHILIPS RC5177	AMSTRAD NEW VIDEO DISPLAY PANELS ETC. YEAR OF MODELS 1991 TO 1992 - 20 FOR £10
		Philips Handset IC SAA3010P £3.00 MAB8461V063 £3.00	PHILIPS RC5177	1993 TOSHIBA FAST TEXT HAND SET £3.50
		Philips Handset IC SAA3010P £3.00 MAB8461V063 £3.00	PHILIPS RC5177	AMSTRAD IC FOR VIDEOS 6206 TO 8600 DISPLAY IC 14 DN 728 AND 14 DN 513 £3 each
		Philips Handset IC SAA3010P £3.00 MAB8461V063 £3.00	PHILIPS RC5177	AMSTRAD 6000 MODULES IC MN616 3AS AND 6367S £6 each
		Philips Handset IC SAA3010P £3.00 MAB8461V063 £3.00	PHILIPS RC5177	TOSHIBA HEAT SYNC COMPOUND £6 FOR KILO DRUM

DIODES

Table listing various diodes such as Bridge KBF-08, BY 126, BY 127, etc., with their respective quantities and prices.

Voltage Regulators

Table listing voltage regulators like +5V UA78P05CC, +5V 78M05, etc., with prices.

Ferguson ICs

Table listing Ferguson ICs like F1X982, 1MP47C 634N 2685, etc., with prices.

ICCS Main ICs

Table listing ICCS Main ICs like CCUR-RC07, CCUR-RC09, etc., with prices.

Hitachi sets etc.

Table listing Hitachi sets and other components like S1R454, S1R620, etc., with prices.

SENDZ COMPONENTS logo and contact information including address (53 Bishopstapleton, Shoeburyness, Essex S53 8AF), phone, and fax numbers.

Table listing various electronic components like M8658P, 2436792, 2436797, etc., with prices.

S.W. Filters

Table listing S.W. Filters like HW2011, HW2013, SW483, etc., with prices.

THYRISTORS

Table listing thyristors like Philips Krs OT121, IR106A, etc., with prices.

Table listing various electronic components like BD046, BD1933, BD939, etc., with prices.

Table listing various electronic components like M8658P, 2436792, 2436797, etc., with prices.

THYRISTORS

Table listing thyristors like Philips Krs OT121, IR106A, etc., with prices.

Table listing various electronic components like ML926, MAB400B-C, MAB410 P-D070, etc., with prices.

Table listing various electronic components like TBA1440C, TBA480Q, TBA500, etc., with prices.

Large vertical advertisement for I.C.A. TRANSISTORS with a 15% DISCOUNT ON ALL I.C.A. TRANSISTORS. Includes a list of transistor models and their prices.