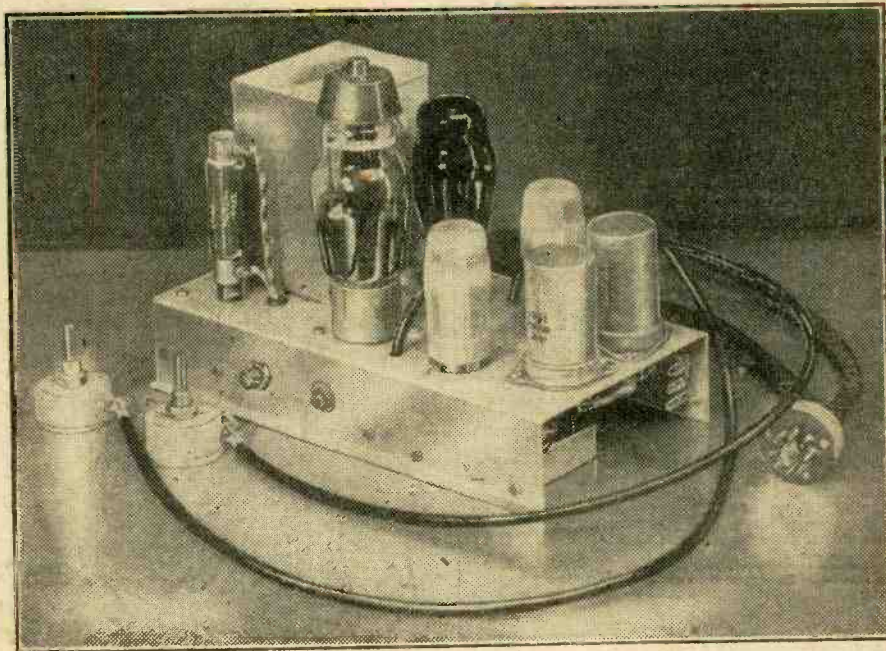


Practical Wireless

9^D
EVERY
MONTH

AND PRACTICAL TELEVISION

Vcl. 25. No. 512. || Editor: F. J. CANN || MARCH, 1949



See Page 110

PRINCIPAL CONTENTS

Building a Television Receiver
Compact 3-Band Superhet
Civilian Walkie-Talkies
Remote Control of Your Receiver

D.C. Oscillograph Amplifier
Using Metal Rectifiers
New Developments in Broadcasting
Television News

PITMAN'S

for PRACTICAL BOOKS

Radio Mains Supply Equipment

By E. M. Squire. A survey of the principles of design and operation of the mains supply equipment. Practical radio engineers will find this book invaluable in dealing with faults in the supply equipment. Illustrated. 12/6 net.

Electronics

By F. G. Spreadbury, A.M.Inst.B.E. The most up-to-date, comprehensive and reliable guide yet published to theory and applications alike. With numerous diagrams. 700 pages. 55/- net.

Radio Receiver Servicing and Maintenance

By E. J. G. Lewis. Here is reliable, up-to-date assistance for the radio dealer and service engineer. A handy fault-finding summary forms a useful feature of the book. Fourth Edition. 8/6 net.

PITMAN, Parker Street, Kingsway, London, W.C.2



FOR THE RADIO SERVICE MAN, DEALER AND OWNER

The man who enrolls for an I.C.S. Radio Course learns radio thoroughly, completely, practically. When he earns his diploma, he will KNOW radio. We are not content merely to teach the principles of radio, we want to show our students how to apply that training in practical, every-day, radio service work. We train them to be successful!

Write to the I.C.S. Advisory Dept., stating your requirements. It places you under no obligation

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 94, International Buildings,
Kingsway, London W.C.2

Please send me your free booklet describing I.C.S. instruction in the subject marked X.
 Complete Radio Engineering Elementary Electronics
 Radio Service Engineers Elementary Radar
 Radio Service and Sales Advanced Short-wave
 Elementary Radio Radio
 If you wish to pass a Radio examination, indicate it below
 British Institute of Radio Engineers
 P.M.G. Certificate for Wireless Operators
 City and Guilds Telecommunications
 R.A.F. Wireless Operator and Mechanic

Examination students are coached until successful

Name Age

Address
(USE BLOCK LETTERS)



"INEXPENSIVE TELEVISION"

For the Home Constructor.

The above now famous booklet can be supplied by us, price 1/6d. Uses War Surplus equipment. The following major items required are available.

IC/SPN LORAN INDICATOR UNIT. Complete with C/R Tube 5CP1 in original mounting 14 valves, 6SN7, 8 6H6, 3 6SL7, 1 6SJ7, 100 kc/s crystal, and a multitude of condensers, resistors, etc. etc., £8 19/6 (carriage and packing, 7/6).

C/R TUBE, VCR97. Each tube brand new, suspended in manufacturer's original packing case, guaranteed complete with printed data sheet. Only 35/- (Reg. carriage and packing, 7/6).

TUBE ENLARGING LENS. For VCR97 or 5CP1. Double your picture area, without distortion. Easy fixing. Really amazing in performance. Only 29/6 (plus 1/6 postage and packing).

R1355 RECEIVER. Complete with 8 valves, VR65, 1 5U4G, 1 VU120, condensers, resistors, etc. etc., 30/- (carriage and packing, 5/-).

TYPE 85 R.F. UNIT. Complete, ready for use in R1355 receiver, 12/- (carriage and packing, 1/6).

E.H.T. TRANSFORMERS. These transformers have been specially wound for us for use with this circuit. For VCR97, input 210-230-250 v.; output 2,500 v., 4 v., 1.1 a., 2-0-2 v. Only 37/6.

For 5CP1, input 210-230-250 v.; output 2,350 v., 6.3 v., 0.6 a., 2-0-2 v. Only 39/6. Both of these above transformers are of first-class manufacture, fully impregnated and guaranteed by us.

P.M. SPEAKERS WITH TRANSFORMERS, R and A. 5/11n, only 13/- 8/1n, R and A, only 21/-. Not repeatable at these prices. Brand new.

INDICATOR TYPE 157. Complete with VCR97 tube, 16 valves, SP81, 2FB34, 2 EA50, potentiometers, 75 kc/s crystal, Murrhead dial, etc. etc., at £2 19/6 (plus 5/- carriage and packing).

MAINS TRANSFORMERS. 250-0-250, 80 m/a, 5 v. 2 a., 6.3 v. 6 a., for vision receiver unit, only 28/6. For time base unit, 350-0-350, 80 m/a, 5 v. 2 a., 6.3 v. 3 a., 28/6. Both chassis mounting.

EX-GOVT. VALVES. The following brand new and guaranteed ex-Govt. valves are all available. All prices inclusive of Purchase Tax. VU111, 8T4, 5B4, 6F7, all at 10/-, 5Z4, 5Y3, 6K7, 6K8, 6J7, 12SR7, 12SJ7, 12SK7, 6SL7, 6SC7, 6C6, 6V6, 7C7, 7H7, 7Y4, 7S7, 7B6, 7C5, 1299A, 1R5, 8D2, 8D2, 15D2, 6AC7, all at 7/6, 6L6, 12/6, 3003, 1N5, 6J5, all at 6/6, 1S5, 1T4, 4D1, all at 5/-, 354, 194, all at 9/-.

If unable to call, please send stamp for our New Issue price list. This is probably the most comprehensive component list in the trade.

TRADE SUPPLIED.

HENRY'S, 5, Harrow Road, W.2.

FAD. : 1008.9.

Manufacturers
SPECIFY IT BECAUSE IT IS
THE FINEST CORED SOLDER
IN THE WORLD

MULTICORE SOLDER

FOR RADIO ELECTRICAL AND ALL HOUSEHOLD PURPOSES

CONTAINS 3 CORES OF FLUX

NO EXTRA FLUX REQUIRED

You
WILL PREFER TO USE
IT BECAUSE IT MAKES
PRECISION SOLDERING
SO SIMPLE

SPECIAL HANDY CARTON

6

ENOUGH FOR 100 AVERAGE JOINTS

MULTICORE SOLDERS LTD. MELLIER HOUSE, ALBEMARLE STREET, LONDON, W.1

VALLANCE'S UNBEATABLE VALUES!

THE "BRITAN" DIAL AND DRIVE ASSEMBLY
An excellent All-wave Dial of the Airplane type. Covers 16-50 metres. 200-500 metres. 900-2,000 metres. CALIBRATED IN WAVE LENGTHS AND STATION NAMES. Glass Dial with calibrations in Green, Yellow and White with white pointer. Size 8 1/2 in. x 5 1/2 in. Supported on rubber cushions by black back plate with brackets for mounting on chassis. Complete with 1 1/2 in. drive drum to fit in. condenser spindle, and cord drive lead with 1/2 in. bush, and 1/2 in. spindle 1 1/2 in. long. Price 18/6, including post and packing.

A.M.C. DIAL AND DRIVE ASSEMBLY
A fine three-waveband Dial Assembly for superhet work. Scale finished in brown and cream and calibrated in frequency wave-lengths and station names. S.W. 16-50 metres. M.W. 200-550 metres. L.W. 800-2,000 metres. Size of opening required, 10 1/2 in. x 4 in. Completely assembled ready for use. 22/9 post free.

J.B. "SQUARE PLANE" DIAL AND DRIVE
A square celluloid dial for TRF receivers, calibrated for Medium and Long Waves in wavelengths and station names in black. Mechanical specification similar to the full Vision Dial. Supplied complete with Glass and escutcheon. Size of opening required, 4 1/2 in. x 3 1/2 in. Price 12/9 post free.

J.B. "ROUND PLANE DIAL" AND DRIVE
Exactly similar to the "Square Plane" Dial, but the Scale, Glass and escutcheon are round. Price 12/9 post free.

DIAL ACCESSORIES

EPICYCLIC DRIVES.—5:1 Ratio, complete with Pointer. 2/3 post free.

CORD DRIVE HEADS, with 1/2 in. spindle and 1/2 in. bush. 2/- each, post free.

DRIVE DRUMS, 2 1/2 in. to fit 1/2 in. spindle. 2/3 post free.

POINTERS.—Bronze push on—centre pivot. 1/11. Silver, centre pivot. 4/4. Black end pivot. 1/10. each. Small brass centre pivot. 3/4. each. Post and packing 6d. extra (minimum).

DRIVE CORD.—Superior quality. 2d. yard.


DRIVE SPRINGS, 1d. each.

M.F.M.I. COMPACT MAINS TRANSFORMER
This small drop through transformer is ideal for V.F.O.s. Test instruments, midget receivers and a host of other applications where size is the limiting factor.
Primary.—200/250 v. A.C. (Screened).
Secondaries.—4.3 volt at 1.5 amps.
1 or 5 volt at 2 amps, tapped.
280-0-280 volt 60 m.a.
Dimensions.—3 1/2 in. x 2 1/2 in. x 3 1/2 in. high. Price 23/-, post and packing 1/-.

SPEEDY POSTAL SERVICE. C.W.O. or C.O.D.
When sending C.W.O. please include sufficient extra for post and packing.

VALLANCE & DAVIDSON, LTD., Department P.W.
144, Brigade, Leeds, 1. Phone 29428/9
Staff call signs : G2HHV, G3ABD, G3CML.

W.D. TELEVISION RECEIVER

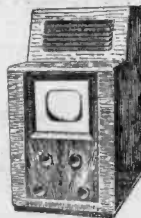

WE INVITE YOU to call any day during television transmitting time, to see this excellent little receiver working. You can make this from Government surplus radar equipment. Send 7/6 without delay for the easy-to-follow instructional data. All components are available ex stock again. Total cost approx. £18.

ORDER WITHOUT DELAY

Is a TRANSMITTER worth 6/6 ?

You can have an ex-R.A.F. transmitter type 22, brand new, for this silly figure.

There is only one snag: these have been made inoperative (Government Orders) by the removal of the valves. But what a load of useful parts are left. You will have hours of amusement making all sorts of radio, electrical and mechanical gadgets. It would take the whole page to adequately describe every part of this transmitter, so we will just briefly mention that there are: valve holders—switches—coil formers—silver-plated wheels—springs—knobs—rods—contact arms—relay—lamp holder—condensers—resistors.

Send only 6/6, plus 1/9 carriage, for this amazing bargain.

W. D. SALES 7, Electron House,
42-46, Windmill Hill, Ruislip Manor, Mdx.

MATT Special Offers ALL NEW AND GUARANTEED

- TRUVOX P.M. SPEAKERS**, 8in. W/Trans. 18/6; 8in. Less Trans. 14/6; 6in. L/Trans. 12/6; Trans. to match. 3/3 each.
- LINE CORD**, 2-way, 1/6 per yd., 3-way, 2/- per yd., 60 ohms per ft.
- TUNING CONDENSERS**, Midg., .0005 W Trims and S motion drive, 11/- each.
- TUNING CONDENSERS**, Ultra Midg., .0005, 2-gang, 10/6 each.
- VOL. CONTROLS CENTRALAB**.—All values w/s, 4/9 each; L/s, 3/6 each.
- CONDENSERS, CANNED TYPES**, 8 mfd. 450 v., 3/- each; 16 mfd. 350 v., 2/9 each; 25 mfd. 25 v., 1/9 each; 16 mfd. (T.C.C.), 7/9 each; 32 mfd. 275 v., 3/9 each; 16+8, etc., etc.
- MULTI RATIO TRANS.**, 12 ratio, 7/8 each.
- MAINS TRANS.**, 6 v. and 4 v., 26/6 each (Shrouded).
- VIBRATORS**, Mallory, 4-pin, 6 v., 4/11 each.
- HEADPHONES**, ex-Govt., W/Jack Plug, 3/11 per pair.
- WEARTELETYPE COILS**, all types, 3/- each.
- RESISTANCES**, "ERIE," Types, 1 w., 4d. each; 1 w., 8d. each.
- SILVER MICA CONDENSERS**, all values, 12/- per gross, assorted.
- PICK-UPS**, B.T.H. Magnetic type, 40/- each. "DE LUXE" Rothermal Crystal, 85/- each, including purchase tax.
- COLLARO**, A.C. Gram. Motors, W/pick-up complete, £5 13s. 4d. each.
- COLLARO**, A.C./D.C. Gram. Motors, w/turn-table, only £3 3s. 6d. each.
- PLESSEY**, A.C. Gram. Motors, auto changers complete, £18 7s. 6d. each.

All Orders under £1 postage extra.
Let us have all your Radio requirements.

Largest Stock of B.V.A. and American Valves in Surrey.

MATT RADIO SERVICE
KINGSTON 8353
29 Castle St. Kingston-on-Thames, Surrey.

TELEVISION CONSTRUCTION FROM EX GOVT. GEAR is becoming all the rage. We can supply full constructional details for a TV Receiver using Radar Units costing £61/10/0. The data is 7/6, but if the units are purchased is supplied gratis, or the cost will be allowed if the purchase is made within 14 days. A combined H.T. and E.H.T. Mains Transformer is £51/10/0, but if bought with the Radar Units the total cost is £111/10/0, showing a saving of 10/-, WE CAN ALSO supply the "Radio Constructor" Inexpensive Television Data priced at 1/6. Please add 12/6 carriage, plus 10/- deposit on returnable packing case.

1 1/2 METRE SUPERHETS APW 4790.—Contains 1 each valve RL7 and RL16, 6 of SP61 and 1 EA50. Has 6 I.F.T.s of 12 megs with 4 meg bandwidth, and variable tuning. All are BRAND NEW, but some have had coils removed by the makers in preparation for fitting others of a different range. With these we supply three 11 mm. formers with brass core, enabling coils to be wound for ranges required. ONLY 59/6 (carriage, etc., 5/-).

MODULATOR AND MIXER UNIT W 6331.—An ex-Admiralty Unit containing a host of gear, including a 231 VA transformer, 1 valve 5U4G, 2 of 6J5G, 3 of P61, 1 of SP61, and 1 EB34. BRAND NEW. ONLY 19/6 (carriage, etc., 5/-).

INSULATION TESTERS (MEGGERS).—Ex-R.A.F. BRAND NEW testers by Evershed & Record. Readings up to 20 megs at 500 v. Pressure. Listed at over £12. Our Price is ONLY £8/10/0.
C.W.O. please. S.A.E. for Lists.

U.E.I. CORP.

THE RADIO CORNER

138, GRAY'S INN ROAD, LONDON, W.C.1

(Phone: TERminus 7937.)

We are 2 mins from High Holborn, 5 mins from King's Cross. Open until 1 p.m. Saturdays.

WORKSHOP • KITCHEN • DINING ROOM • LOUNGE • BEDROOM


—switch the radio on or off from wherever you are!

The 'LONG ARM' REMOTE CONTROL

The warm welcome accorded the "Long Arm" when it reappeared just before Christmas showed how much listeners need the added convenience of remote control.

Remember that this Whiteley "exclusive" operates any number of "Stentorian" speakers (Senior, Junior or Cadet models) from any radio receiver, and costs only 35/-. (Suitable speakers from £4.0.0.)

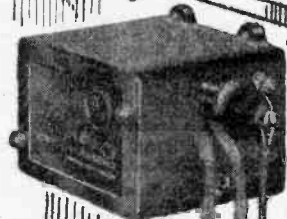Other Whiteley products include Loudspeaker Chassis Units, Microphones, Valveholders, Switches, Transformers and Chokes.




BROUGHT BACK
BY POPULAR DEMAND

Stentorian

LOUDSPEAKERS & RADIO COMPONENTS

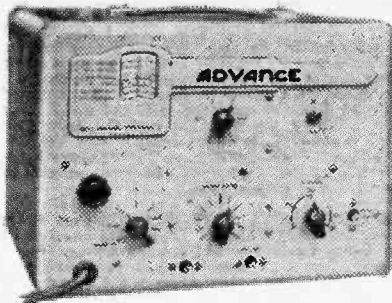WHITELEY ELECTRICAL RADIO CO. LTD. - MANSFIELD - NOTTS



RANGE: 100 Kcls—60 Mc/s on fundamentals

ACCURACY: Guaranteed within $\pm 1\%$.

ATTENUATION: Constant impedance system embodying a matched 75 ohms transmission line.

STRAY FIELD: Less than 3 microvolts at 60 megacycles.

ILLUMINATED DIAL: Total scale length 30in.

POWER SUPPLY: 110-210-230-250 volts.

DIMENSIONS: 13in. x 10½in. x 7½in. deep.

WEIGHT: 15 lbs.

★ Send for fully descriptive pamphlet.

Accurate enough for the Lab!
Sturdy enough for the works...
Inexpensive enough for the
average user

THIS important addition to the "Advance" range of Signal Generators places an instrument of laboratory class within the financial scope of every radio service engineer and experimenter.

The discerning engineer will appreciate its accuracy and stability, its *exceptionally wide range* which covers all frequencies required for radio and television receivers, and its accurate attenuating system which enables sensitivity measurements to be made on highly sensitive

receivers up to 60 Mc/s.

Advance

Type 'E' SIGNAL
GENERATOR

ADVANCE COMPONENTS LTD., Back Road, Shernhall St., Walthamstow, E.17 LARKSWOOD 4366-7-8.

Practical Wireless

17th YEAR
OF ISSUE

and PRACTICAL TELEVISION

EVERY MONTH
VOL. XXV. No. 512 MARCH, 1949

Editor F.J. CAMM

COMMENTS OF THE MONTH

BY THE EDITOR

The Wireless Telegraphy Bill

THE Radio Industries Council has sent to all Members of Parliament a memorandum explaining the causes of electrical interference with radio and television services, so that those concerned with the new Wireless Telegraphy Bill may appreciate the importance of dealing with the problem now.

It is noted that no reference is made to the very serious trouble caused by public service vehicles, and we challenge the Radio Industries Council's original statement that 90 per cent. of interference with television is caused by car ignition systems. We do not think that they have any justification for such an "estimate," and we suggest that it is just a wild guess.

Public service vehicles, electrically propelled, cause very serious interference. Why has this not been mentioned in the memorandum? This states that many kinds of industrial and domestic electrical equipment produce, inadvertently, when operating quite normally, signals at radio wavelengths in much the same way as the B.B.C. radiate programmes. They give as examples of equipment which produce such signals, certain types of electric motors, electric vacuum cleaners, electric razors, certain types of electric water-heaters, irons, bed-warmers and refrigerators, motor vehicle ignition systems, and electro-medical and industrial H.F. heating equipment.

Unlike radio signals, which can be controlled, the signals radiated by this equipment are uncontrolled, and instead of being confined to one fixed wavelength are transmitted over a wide band of wavelengths.

As an example, consider two signals being radiated simultaneously, one a B.B.C. programme, and the other a signal produced by a vacuum cleaner. When the receiver is tuned in to the B.B.C. programme it is received at a fixed point on the dial, but the other can be received anywhere on the dial, and so the signal from the vacuum cleaner will also be heard as an unwanted and interfering signal.

This interfering signal may travel through the ether and along electric cables, wires, pipes and other metal objects. Not

every piece of electrical equipment causes interference; only those which produce signals at radio wavelengths.

The memorandum goes on to suggest how interference can be suppressed. It can be suppressed on the receiving apparatus, by means of internal screening and by the use of a special aerial which must be very high so as to be outside the range of interference. This is, however, expensive, and not generally practicable for the ordinary public.

In cases when the interfering signal occurs on the same wavelength as the wanted signal, which it does in most cases, it is not possible to suppress it in the receiver. The practicable method, therefore, is to suppress interference on the apparatus which causes it and, as we have pointed out before, this can be effected by means of a simple device fitted to the equipment. The device is cheap and easily fitted.

Increasing use is being made of radio and radar as navigational aids, and the vital importance of preventing interference with these services, where safety of life is involved will be fully appreciated. There is no reason why one user of electrical apparatus should be favoured at the expense of any other, but we concur in the view that it is desirable that full use should be made of scientific

knowledge and technical experience to ensure that all electrical appliances and radio services work efficiently for the good of the public. If measures are taken to ensure that equipment producing interference is properly suppressed, the public will derive the fullest enjoyment from the large sums of money spent by the B.B.C. to give the best in radio and television entertainment.

Practical Television

ELSEWHERE in this issue readers will notice that we have re-introduced the Practical Television Supplement. In this feature, which will appear monthly, we shall give the latest television news, reviews of television receivers, and constructional details of apparatus.

Readers interested in the subject will appreciate the grouping of television subjects within the pages of the supplement.

Editorial and Advertisement Offices:
"Practical Wireless," George Newnes, Ltd.,
Tower House, Southampton Street, Strand,
W.C.2. "Phone": Temple Bar 4303.

Telegrams: Newnes, Rand, London.
Registered at the G.P.O. for transmission by
Canadian Magazine Post.

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Wireless." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, "Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. "Practical Wireless" incorporates "Amateur Wireless."

ROUND THE WORLD OF WIRELESS

Broadcast Receiving Licences

THE following statement shows the approximate numbers of licences issued during the year ended 30th November, 1948.

Region	Number
London Postal	2,121,000
Home Counties	1,496,000
Midland	1,627,000
North Eastern	1,771,000
North Western	1,482,000
South Western	1,004,000
Welsh and Border	660,000
Total England and Wales ..	10,161,000
Scotland	1,075,000
Northern Ireland	186,000
	11,422,000

British Railways to Test Radio

BRITISH RAILWAYS are to carry out tests with radio to ascertain whether it would facilitate any traffic or engineering operations.

Announcing this, the Railway Executive report that in addition to fixed radio stations, tests will be carried out with transportable equipment,

portable sets, for use on vehicles and by staff on the ground.

The tests envisaged will, for example, determine the possible value of wireless for:

Communication between shunting-engine drivers, ground staff and control towers in marshalling yards.

Communication between staff during extensive engineering operations.

Communication from a central depot to road cartage collection and delivery vans.

Working trials will take place as soon as the radio equipment now on order becomes available.

Tests are also in hand, using ultra-high-frequency to determine the possibility of providing radio communication through tunnels, to facilitate engineering operations in these difficult locations.

Additional Frequency Bands for Amateurs

THE Postmaster General announces that as from the 1st January, 1949, holders of amateur wireless station licences may, subject to the conditions of their licences, use in addition to the frequencies they already use, frequencies within the bands 5,650 to 5,850 Mc/s and 10,000 to 10,500 Mc/s and, on a non-interference basis, the frequencies 144 to 145 Mc/s, and 1,215 to 1,300 Mc/s.

Only amplitude modulation may be used with frequencies in the 144 to 146 Mc/s band but in the other new bands frequency modulation or amplitude modulation may be used. Amateurs who hold licences which restrict them to using telegraphy or a maximum power of 10 watts will be required to observe the same restrictions when using the new bands and the 145 to 146 Mc/s and 420 to 460 Mc/s bands released earlier, but other amateurs will be allowed to use any of these frequencies for telegraphy and telephony at powers not exceeding 25 watts. Licences will be formally amended by a notice in the London Gazette. The continued use by amateurs of frequencies in the 58.5 to 60 Mc/s band will be permitted until a date not later than the 31st March, 1949, which will be announced in due course.

Radiotelephone Service With R.M.S. "Caronia"

THE Postmaster General announces that telephone service is now available with the R.M.S. *Caronia*.

The charges for calls to the *Caronia* are the same as those for calls to other liners.

The British Institution of Radio Engineers

THE London Section held a meeting at the London School of Hygiene and Tropical Medicine recently when a paper was read by J. B. Birks, B.A., on "The Physical



Main Equipment Rack at the Institution for the Blind. The radio receiver and record player are immediately below the loudspeaker grille, with the "programme" timeswitch at top of the right-hand rack. A microphone for local announcements can be seen on the wall.

Applications of Microwaves." Mr. Birks is the lecturer in Natural Philosophy at the University of Glasgow and made a special journey from Scotland in order to give this paper.

A major part of the physicist's knowledge of the structure of matter has been derived from the study of the interactions between electromagnetic radiations and matter. The major war advances in microwave experimental technique and apparatus have provided the physicist with important new research tools, and have encouraged fresh investigations of the properties of matter in the centimetre wave region. The paper reviewed the progress made in such physical applications of microwaves.

Big Ekco Development in India

E. K. COLE, LTD., announce the successful conclusion of negotiations with the great Tata organisation of India for the manufacture and distribution of radio receivers in India, in the following statement:

"E. K. Cole, Limited, and National Radio and Engineering Company, Limited, of Bombay (a Tata affiliated company) announce that they have entered into an agreement for the establishment and development of radio manufacture and distribution in India. This will embrace radio receivers, components and electronic devices generally. Plans are well advanced for the production of a range of radio receivers, the first of which it is expected will appear shortly."

Radio Relay Installation at Institution for the Blind

AN automatic time signal and radio relay system of a flexible character has recently been made and installed by the G.E.C. for the Royal Dundee Institution for the Blind.

The assembly illustrated houses a radio receiver, gramophone with automatic record changer and microphone input panel, as well as the main 60-watt amplifier and power supply equipment.

The apparatus is intended chiefly for the relaying of radio and gramophone programmes but microphones are available to enable announcements to be made. There is also provision for locally-generated time signals to announce the beginning and ending of work periods.

The entire equipment is switched on and off automatically and provision is made for music to be reinstated automatically after time signals or microphone announcements have been made.

"Electric Eye" Banishes Smoke

IT is reported that an "electric eye" for the control of the smoke nuisance is in use in Australia. It controls fuel supply and regulates smoke volume automatically. Hospitals and factories in Melbourne, Victoria, are installing it and the inventor claims that it is capable of

dealing with the smoke nuisance from municipal power stations.

Picture Transmission

ULTRAFAX, a new method for high-speed transmission of pictorial or printed material, was demonstrated to the public for the first time last month, according to *Radio Electronics*. Feature of the demonstration was the sending in just two minutes and 21 seconds of the complete text of "Gone With the Wind," the famous 1,047-page novel.


A picture of each page is transmitted via television to a TV receiver and is copied on microfilm. Thirty of these pictures per second are sent. A war-developed system of high-speed photography delivers film ready for printing or projecting in 45 seconds.

Television Points to the North-west

ONE hundred feet above the heads of passers-by, on the roof of the old Museum telephone exchange in Cleveland Street, off Tottenham Court Road, workmen are erecting a giant television transmission aerial. The aerial is the first part of the B.B.C. project to bring television to the many people who live outside the range of the London transmitters, and is the London link to relay programmes to the new television station at Sutton Coldfield, for re-transmission to the Midlands and the North. A cable will carry the programmes from Alexandra Palace to Cleveland Street.

"Detector" Medical Aid

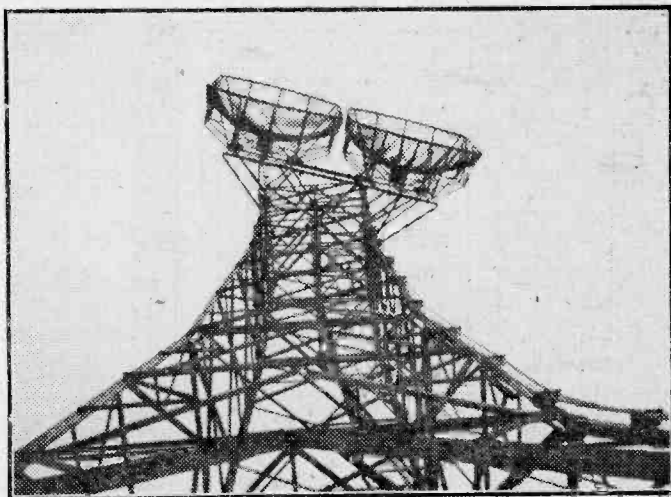A NEW device for the detection of metal is designed to locate foreign objects in animals. A bit of baling wire swallowed by a cow or a bullet accidentally fired into a farm animal or pet may be located by passing the detector over the animal's body. Developed by the U.S. Army Medical Department, the device is awaiting final clinical tests.



The new Relay Aerials in London. Note that the reflectors are made from strips instead of being solid—in order to reduce wind resistance.

Compact Three-band Superhet

A 4-valve Battery Receiver of Simple Design Built From Standard Parts

By R. V. LUMBARD

A BATTERY receiver capable of receiving both short-wave and home stations was recently needed. Such a receiver was to be compact, at the same time using standard components to the fullest extent. Since the set might frequently be used with a 20ft. throw-out aerial, sensitivity adequate to receive the more powerful short-wave stations was required.

The four-valve superhet circuit was decided on, as giving a good overall performance. Simplicity of operation is ensured by reducing controls to a minimum. The 4in. P.M. loudspeaker provides volume and quality sufficient for usual needs with this class of receiver. Limiting the number of valves to four assists in battery economy.

Since the set was designed as a semi-portable, an earth is not used. The addition of an earth on medium waves does make a marked difference to signal strength, although sensitivity is adequate without. Overall size is approximately 13in. by 8½in. by 8½in. deep. Broad details of construction are given, all minor points of receiver assembly and construction being left to personal discretion.

Two-volt valves are used. First, a triode-hexode frequency changer to maintain a good short-wave performance. A four-pin variable-mu H.F. pentode follows as I.F. Then a double-diode-triode for detection, A.V.C. and audio-frequency amplification. Finally, an output tetrode of moderate slope, to give a favourable compromise between sensitivity and quality.

There are only two connections to the 120-volt H.T. bias, for the output valve is automatic, resulting from the volts-drop across R13. The resistor R7 was connected across the volume

control R14 to reduce the diode D.C. load, since the value of the available 1-megohm volume control on its own was considered too high. The A.V.C. voltage is taken from the primary circuit of the second I.F. transformer, full A.V.C. being fed to frequency changer and I.F. valves.

The choice of coil unit used is left to the constructor. A large section of the chassis is removed to allow the coil unit to be fitted. If necessary, the unit can project above the level of the chassis. There is ample clearance below the two-gang condenser. The space will readily accommodate the average three-waveband unit, or, if preferred, the constructor's own coils, together with wave-change switch, trimmers and padders. The writer's present coils are of the "P" type, covering 12-35, 35-100 and 200-550 metres. An alternative is to use the three-waveband iron-dust core coils to cover long, medium and short, and these, besides covering the worthwhile short-wave broadcasts, will enable the 1,500 metres Light programme to be heard.

The Circuit

The complete theoretical diagram of the coils and switching is shown in Fig. 3 (a). Values of trimmers and padders are omitted, since they depend on coils used and wave ranges covered. An alternative oscillator-anode circuit can be tried, and is shown in Fig. 3 (b). It was found in the writer's receiver (a) gave best performance on the lowest wavelengths. Excessive oscillation on any one waveband can be cured by artificial damping on the coil concerned. The inclusion of a series resistor of 200-1,000 ohms between the anode winding of the coil and the switch contact will stabilise things. A further resistor of

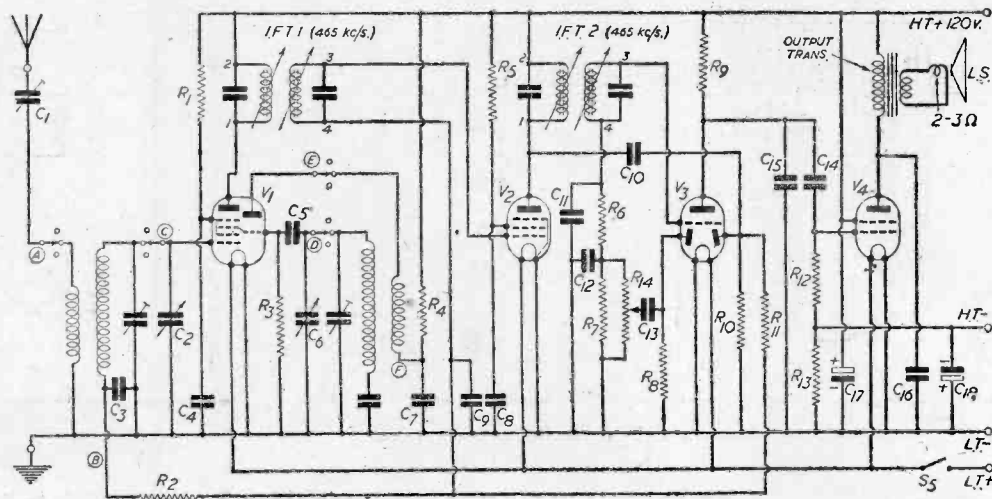


Fig. 1.—Theoretical circuit diagram complete with basic coil unit components for single waveband.

30,000-100,000 ohms, connected across the tuned winding, should cure any remaining instability.

It is possible to arrange that an additional resistor is switched into the oscillator-anode circuit when not on short waves. This makes for greater

tuning dial, volume and wave-change controls, and insulated aerial terminal. Other holes to be drilled are for speaker fixing, and 2 B.A. for attaching chassis to panel; and, finally, holes for screw-fixing the panel to front of cabinet.

The steel chassis is made separately, being joined to the panel by four 2 B.A. bolts. The outside dimensions are 11 1/2 in. by 5 1/2 in. deep. The chassis height is 2 1/2 in., there being a clearance of 1/4 in. between the bottom of the chassis and the bottom of the front panel. This permits chassis and panel, when assembled complete, to be slipped bodily into the cabinet.

Large sections of the chassis top and front must be cut away. The main sections are for the coil-unit and base of the speaker; also volume-control/on-off switch. Next come the holes for valveholders and I.F. transformers. Finally, the 2 B.A. bolt holes to line up with panel, the aerial terminal holes, and fixing holes for the

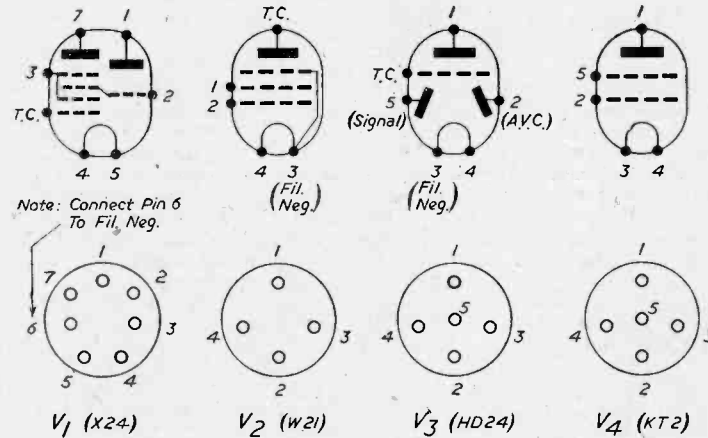


Fig. 2.—Valve base data.

H.T. economy, without seriously affecting sensitivity.

The size of the steel front panel is 12 1/2 in. by 8 in. The main apertures to be made are for the speaker,

two-gang condenser bracket, valveholders and I.F. transformers. All fixed condensers and resistors are supported in the wiring, so no holes are needed.

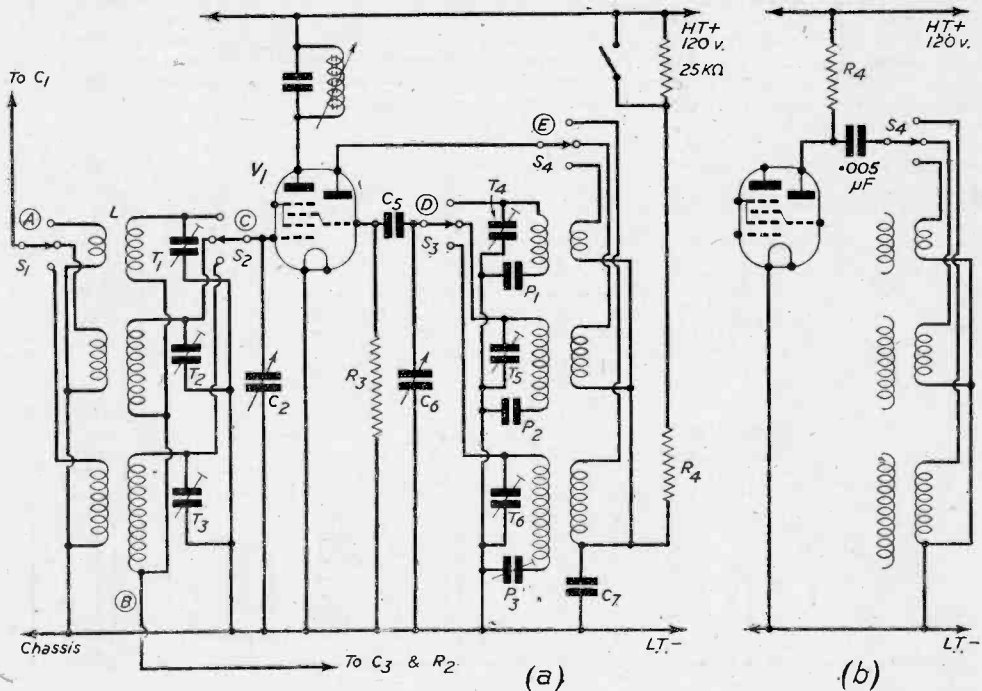


Fig. 3.—On the left is a diagram of a three-band coil unit with additional switched resistor inserted on normal broadcast (not S.W.) band. On the right is an alternative oscillator-anode circuit.

The Cabinet

The construction of a suitable cabinet should not be difficult. Either five-ply or $\frac{3}{4}$ in. wood is suitable. There is only a top, bottom, and two sides. Two runners are screwed underneath. The carrying handle is a matter for personal choice. With the cabinet complete, both chassis and panel can be bolted together and checked for fit by sliding into the cabinet.

The assembly of valveholders, I.F. transformers, coil-unit, volume-control, tuning condenser, dial, loudspeaker, etc., is followed by wiring. A guide to the relative positions of components is given in Fig. 4. In the writer's receiver it was not necessary to screen any of the grid or anode leads.

of all but the battery leads is best kept as short and direct as possible. Doubts may be felt about the leakage current through C17 when the set was switched off. But with a good reliable make of condenser the leakage is negligible. A three-point or double-pole on-off switch will remove any leakage when the set is off, but volume-controls with either are more difficult to get.

Before connecting batteries, the wiring should be checked for obvious faults, safeguarding valves against possible damage. The H.T. and L.T. can then be plugged in and alignment commenced. To avoid any headaches, it is best to get the I.F.T.s lined to 465 kc/s at the beginning, using a signal

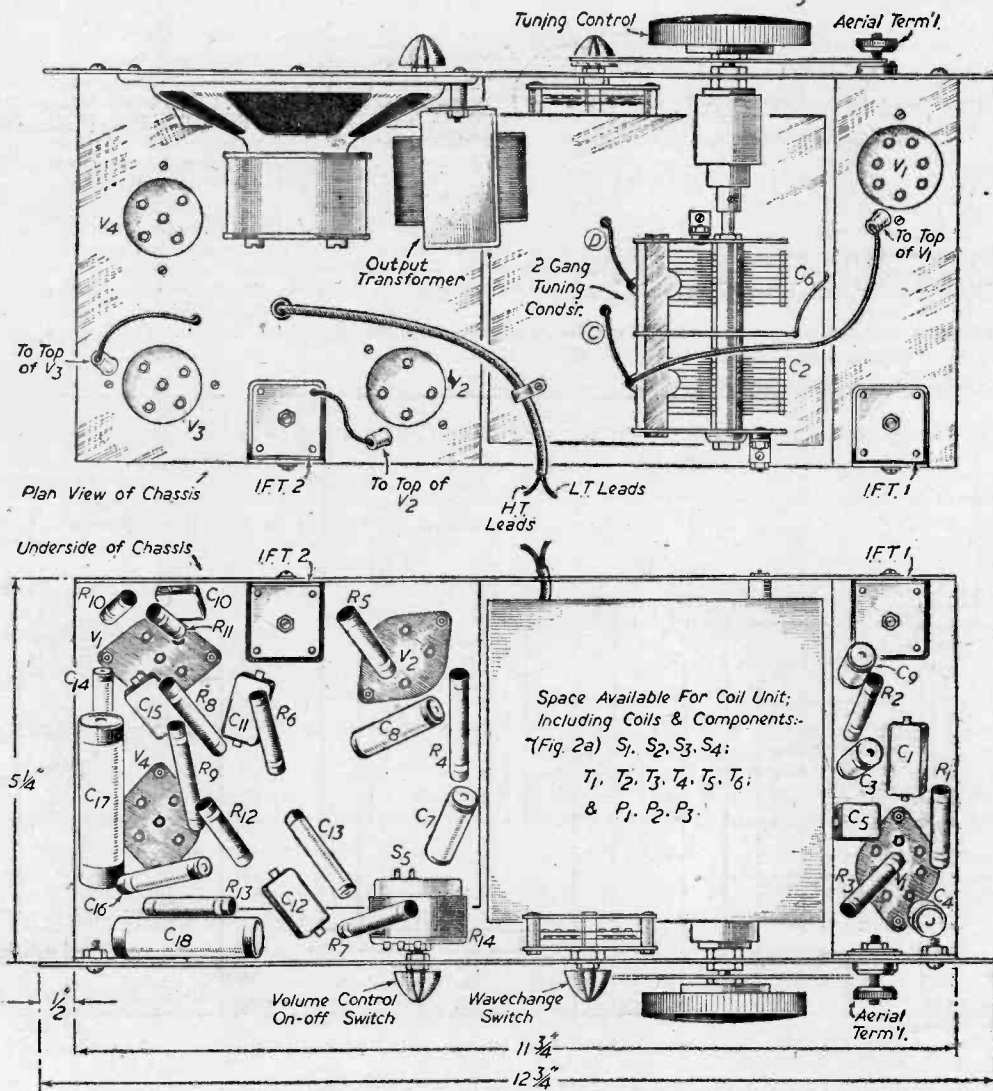


Fig. 4.—Practical above- and below-chassis diagrams showing layout and positions of all components.

generator. Aligning can be done by "hit-and-miss," but the procedure is as tedious as it is long; even then one is not certain of proper alignment.

The use of a signal generator is also a great asset for trimming and padding the signal and oscillator circuits of the frequency changer.

LIST OF COMPONENTS

CONDENSERS

C1	.0002 μ F Trimmer (Ceramic)
C2 and C6	Two-gang .0005 μ F variable
C3	.05 μ F Tubular
C4	.1 μ F Tubular
C5	.0001 μ F Mica
C7	.05 μ F Tubular
C8	.1 μ F Tubular
C9	.05 μ F Tubular
C10, C11, C12	.0001 μ F Mica
C13	.01 μ F Tubular
C14	.05 μ F Tubular
C15	.0001 μ F Mica
C16	.005 μ F Tubular
C17	8 μ F Tubular Electrolytic
C18	25 μ F Tubular Electrolytic

RESISTORS

R1	40,000 ohms
R2	.1 megohm
R3	50,000 ohms
R4	10,000 ohms
R5	25,000 ohms
R6	20,000 ohms
R7	.5 megohm
R8	2 megohms
R9	.1 megohm

R10, R11	1 megohm
R12	.5 megohm
R13	300 ohms
R14	1-megohm volume control

VALVES

V1	Triode-hexode (Marconi/Osram X24)
V2	V.M. Pentode (4-pin) (Marconi/Osram W21)
V3	D.D. Triode (5-pin) (Marconi/Osram HD24)
V4	Output Tetrode (Marconi/Osram KT2)

5in. P.M. loudspeaker of 2-3 ohms.

O.T. small output transformer, ratio about 70 : 1. Precision slow-motion dial, complete with reduction drive and 2 $\frac{1}{2}$ in. knob.

I.F.T.1. and I.F.T.2 small type 465 kc/s intermediate frequency transformers with adjustable iron-dust cores.

Three-waveband coil-unit to constructor's own requirements, complete with trimmers and padders, also necessary switches.

Valveholders: 7-pin, one; 4-pin, one; 5-pin, two.

Batteries: 120-volt high-tension (standard capacity); 2-volt dry accumulator.

New Home Battery Charger

THE possession of a home battery charger can no longer be considered a luxury. In fact, it is true to say that the present system of petrol rationing, with its attendant mileage restrictions, puts the battery charger amongst the indispensable items of garage equipment for motorists. For without it no motorist can to-day guarantee that his battery will be correctly maintained.

With the arrival of winter this difficulty is considerably worsened. Not only is the battery called upon to provide ignition facilities for the engine, but it has also to cope with the prolonged burning of side, tail and head lamps, together with the additional burden of cold starting. Thus, the need for an efficient home battery charger becomes imperative. The listener who relies upon battery equipment, but who has mains facilities available, will also find a good battery charger a valuable adjunct.

Such an instrument is now marketed by The General Electric Co., Ltd. Costing only £5 12s. this new G.E.C. charger is simple to operate and is suitable for use on A.C. (single-phase supplies) with frequencies between 40 and 100 cycles, and can be adjusted easily by the user for 100/110, 200/220 or 230/250 volt circuits. Movement of a single screw plug enables a 2-, 6- or 12-volt battery to be charged as desired.

A novelty incorporated in the charger is a thermally operated combined cut-out and indicator. This device protects the transformer and rectifier unit against excessive overload or accidental short-circuiting of the output leads, while the pointer,

which passes over a scale reading "LOW," "MED" and "HIGH," indicates the relative output of the charger. The state of the battery automatically controls the rate of charge.

When the battery is in a discharged condition, the charger will deliver its full output of 2 amps. but as the charge in the battery builds up, so the rate of charge decreases.

Further protection for the transformer is given by the provision of double-pole fuses on the primary side. Operating costs are negligible, as the unit only consumes approximately the same current as the average domestic electric lamp.

Enclosed in an attractive, cream-finished case with red pilot lamp, and supplied with electrical leads, battery clips and instruction leaflet, the G.E.C. home battery charger can be relied upon.



The G.E.C. charger which provides 2-, 6- or 12-volt outputs.

Civilian Walkie-talkies

Advance Details of a New American Midget Transmitter-receiver

THE first portable radio transceivers for public use between homes, cars, offices, plants, farms and many other person-to-person radio-telephone applications are now in pilot plant production, according to Al Gross of the Citizens Radio Corporation, which has received the first F.C.C. type approval for equipment to be used on the 465 megacycle band allocated for civilian use.

The equipment, according to Gross, is one fourth the size of the famous wartime walkie-talkie and is the result of more than two years of research and engineering in which many new techniques, including sub-miniature tubes and the use of silver-on-ceramic circuits, have been perfected for practical push-button, person-to-person radio communication for public use.

Experimental units, he said, have been given exhaustive field tests between car and home; home and office; boats and shore; planes and ground; and person-to-person on city streets. They have also been tested for communication between cemetery ground keepers; hunters; mountain climbers; farm and field; and surveyors. He also predicted that this revolutionary type of personal two-way radio will soon become a standard means of eye-witness reporting of sports and spot-news events to radio and television audiences and newspapers.

The transceiver, two of which are required for person-to-person air contact, is housed in a tiny case measuring only 6in. by 2½in. by 1½in., topped by a small folding aerial. This pocket-sized radio station includes all necessary equipment except a tiny headphone and batteries carried in a separate

case about the size of a miniature camera.

As may be seen in the centre of the control panel, there are only two controls, that on the left being for volume and that on the right for tuning. They are of the edge-operated type.

The cut-out grille on the lower portion carrying the letters "R.C." is, in fact, the opening over the microphone, and the ornamental panel is thus a protective cover as well as carrying out a useful function.

Development of the citizen's radio, Gross said, was made possible largely through the availability of sub-miniature tubes manufactured by Sylvania Electric Products Inc. and the co-operation of Sylvania's advanced development laboratories. However, he admitted that many practical design problems, without which F.C.C. type approval CR-401 could not have been obtained, were solved in the laboratories of the Citizens Radio Corporation.

He described the model 100-B citizen's radio as a transceiver for Class B stations only; operating at 465 Mc/s, tolerance 0.4, input 3 watts, emission A-3 with 30 per cent. maximum modulation. The transmitting section uses a Sylvania 6K4 sub-miniature oscillator and the receiver is a super-regenerative using three Sylvania IV5 sub-miniature tubes. The transceiver weighs only 11 ounces

including aerial, and total station equipment including batteries is only two-and-one-half pounds.

At the moment the apparatus is available only on the American market and we are unable to give any further details of the equipment. If and when it becomes available in this country an announcement will be made in these pages.



The transmitter and receiver, seen above, includes microphone, aerial and four sub-miniature valves for oscillator and super-regenerative receiver. On the left the equipment is seen in use, and on the right is the audio section.

New Developments in Broadcasting-2

Concluding the *Precis* of the Presidential Address Delivered Recently at the Junior Institution of Engineers by SIR NOEL ASHBRIDGE, F.K.C., B.Sc.(Eng.), M.I.C.E., M.I.E.E., F.I.R.E.

Ultra-short-wave Broadcasting

THE other major development which I wish to speak about is ultra-high-frequency, or ultra-short-wave broadcasting. Almost everyone knows, of course, that home broadcasting is carried out on what are known as long and medium waves. Such waves have one main disadvantage: in darkness they are reflected from the ionosphere, which not only gives rise to the well-known distortion due to fading but causes severe interference between stations using the same wavelength at very considerable distances. It is true that this also makes long-distance reception possible, but for a high-quality home broadcasting service such reception cannot be regarded as satisfactory. The existence of indirect ray transmission means in effect that, generally speaking, high-power stations, say, on the Continent of Europe, cannot normally satisfactorily share the same channel unless they are separated by well over 1,000 miles.

This naturally gives rise to the very serious overcrowding of the available frequency bands and to the necessity of allowing only 9 kc/s spacing between channels, which is not sufficient for really high-quality reception except when the received strength from the wanted station is high.

If the tendency to increase the number and power of broadcasting stations throughout Europe continues it may even be necessary still further to reduce the spacing to secure an internationally agreed wavelength plan, without which a condition of chaos would almost certainly develop. Thus, at the recent European Regional Broadcast Wavelength Conference at Copenhagen there was at first strong pressure to adopt a 10 kc/s separation between channels, but in the end, in order to secure agreement, it became necessary to adopt 9 kc/s as the standard spacing. Even so, it was necessary to space a few of the channels at the high-frequency end of the medium-frequency band at 8 kc/s in order to fit in the very large number of stations which had to be accommodated.

In these circumstances it may well be asked what are the prospects of good broadcasting in the future. Fortunately, the answer in this case is favourable; without much doubt the future to a large extent depends on the development of broadcasting on ultra-high frequencies. Since, however, the shortage of channels has existed for more than 20 years, with steadily increasing severity, the question naturally arises, why has this expedient not been adopted before?

Increasing the Range

The answer is that prior to the introduction of television on carrier frequencies as high as 45 Mc/s, as a matter of necessity, to accommodate the very wide modulation frequency band, it was thought

that these very high-frequency waves would be limited in range to "line of sight" transmission and would be subject to masking and shadow effects from hills, large buildings, and other obstructions. In fact some doubts were expressed as to whether such frequencies were really practicable for a broadcasting service at all.

To an extent these fears are realised in practice, but certainly not to the serious extent anticipated. Moreover, it has been found that by siting stations on carefully chosen high ground—and I might mention here that the choice is not necessarily the same as it would be for a medium or a long wavelength station—and by placing the radiating system at the top of the highest mast it is practicable to build, these limitations in coverage can be very greatly reduced.

Again, the radiating system for these frequencies can be designed to concentrate the energy in the required direction in the vertical plane to such an extent as to give the effect of several times the apparent power. The result is that the maximum effective range of a 25 kW sound broadcasting station working on say 90 Mc/s may prove to be roughly equal to that of a similar station on, say, 1,000 kc/s. But this is perhaps rather a broad statement and the exact nature of the terrain to be covered must be taken into account. For example, the general coverage of a mountainous district would in the ordinary way not be feasible, although the technique of using a number of low-power stations of this type in populated mountainous areas may be found quite satisfactory. Again, there may be, and almost certainly will be, some strictly local difficulties in cities with tall buildings. It is anticipated, however, that these effects will not be important enough to prevent the development of broadcasting on these frequencies. The band which is at present earmarked for the purpose in this country is 87.5 Mc/s to 95 Mc/s.

Benefits of Frequency Modulation

Many people refer to this kind of broadcasting in a general way as F.M., which, of course, means frequency modulation. Many millions of words have been written on this method of modulation, both extolling the advantages and pointing out the difficulties. When a transmitter is frequency modulated it means that the carrier wave is modulated by the audio frequency programme input by varying its frequency instead of its amplitude, which is normal for broadcast transmitters. The advantages of the former method, put very briefly, are that it reduces to a considerable extent parasitic interference of most kinds, giving a remarkably silent background even when the field strength is comparatively low. It is this fact which makes it possible to adopt a lower field strength

as the working limit and so obtain a range comparable with that obtained on lower frequencies where the rate of attenuation is much less. The main disadvantage is that to get the full advantage from a F.M. transmitter, the modulation bandwidth—that is the overall frequency swing of the carrier—must be of the order of 150 kc/s, whereas the highest possible quality of sound transmission using amplitude modulation requires, say, 30 kc/s channel width overall. Frequency modulation, therefore, cannot be used on medium or long waves because of the wide band necessary if it is to be effective.

It is thought by many people that the time will soon be reached when the ultra-high-frequency bands are as congested as are the medium- and low-frequency bands at the present time. This, however, is unlikely, unless it is found that in practice interference between stations at a distance, due to tropospheric propagation which is liable to occur on these frequencies, is more severe than is anticipated at present. It should be explained that by tropospheric propagation is meant reflection or refraction, at much lower levels than the ionosphere, caused by sharp variations in atmospheric temperature and humidity with height. Nevertheless, the fact that frequency modulation uses five times the band width necessary for amplitude modulation might conceivably cause a set-off to its main advantage, namely that good reception can be obtained at a much lower field strength.

Perhaps it should be made clear that were there no such thing as frequency modulation it would still be possible to develop the use of ultra-high frequencies for broadcasting, using amplitude modulation, although at the moment general, if not quite universal, opinion is in favour of exploiting ultra-high-frequency broadcasting using a frequency-modulated carrier.

The advantages of frequency modulation for high-frequency broadcasting began to be realised in the U.S.A. at about the beginning of the late war and it was developed there to a limited extent during the war years. It has now obtained a firm hold in America and expansion is extremely rapid both with regard to transmitters and receivers.

Present Experiments

So far as broadcasting was concerned it was not possible to do any practical work on this development during the war in this country, but as soon as the end was in sight the B.B.C. started experimental work, using two or three low-powered stations in areas which were chosen to give typical conditions which would have to be met in practice. Valuable, but not complete, data has been obtained, and before committing a very large sum for development on a country-wide basis it was decided to construct a high-power station near London which would be regarded to a considerable extent as experimental.

This station will have two transmitters, each with a power of about 25 kW. (which is somewhat higher than is commonly used in America) and the maximum height of mast allowed by the Air Authorities, 500ft. It has been constructed in such a way as to facilitate comparative experiments between two transmitters working under different modulation conditions and with the object of making measurements on which it would be

reasonable to base a scheme for general coverage. Its experimental nature does not, however, imply that there is any real doubt as to the feasibility and importance of ultra-high-frequency broadcasting generally, and, in fact, the station at Wrotham, Kent, will be the first of a chain of such stations throughout the country.

Ultimately it will, of course, be necessary for listeners to provide themselves with new receivers, or possibly adaptors, and with this in view close liaison with industry is being maintained. It is hoped that suitable receivers will be produced at the right time which will cover the low-, medium-, and ultra-high-frequency bands.

It is always dangerous to make forecasts concerning the distant future, especially when the relative data is incomplete. However, it can be said that it is not anticipated that ultra-high-frequency broadcasting will, in the foreseeable future, entirely replace the use of medium and low frequencies, at any rate in this country. In a consistently flat country this might well be feasible, assuming, of course, that listeners had provided themselves with suitable receivers. However, where mountainous or very broken country is to be covered, serious difficulties may well be encountered and the ultra-high-frequency development should be regarded more as an extremely welcome auxiliary to the existing services, rather than as a replacement of them. Above all, their use can fortunately be regarded as a solution in the future to the steadily increasing international difficulties with regard to the sharing out of channels which arise from the limitations of the low- and medium-frequency bands. At the same time the new bands would, in general, make possible improved reception, giving greater artistic possibilities for the future.

The New Wavelength Plan

As already mentioned, a conference of European countries has just succeeded in producing a new wave plan to which a large majority of the countries present have agreed. It is to be applied in March, 1950, and normally there should be five or six years before this plan would come up for revision. However, taking into account the extreme difficulty of obtaining an agreement at this conference and the fact that broadcasting, especially in certain countries, is now being rapidly developed for the first time on a basis of high-power stations, the prospects of obtaining future agreement would not be at all promising were it not for the fact that in future some of the development should be absorbed by the use of wavebands not so far taken into use.

Thus it is most satisfactory that we can, quite apart from television, look forward to the further development of sound broadcasting, a possibility which even 10 years ago appeared to be rapidly disappearing.

SAVE THAT CARTON

Every empty breakfast-food, sugar, cigarette, soapflake packet is urgently needed for salvage.



ON YOUR WAVELENGTH

By THERMION

Crooning—80 Years Ago

CROONING does not appear to be a modern disease, for Charles Reade had something to say about it in "The Cloister and the Hearth," written in the year 1860, and I am indebted to Mr. A. J. Sweeney, of Gloucester, for drawing my attention to it. This is what Reade says:

"Those whining slurs, now sold so dearly by Italian songsters; yet every jackal in India delivers them gratis to his customers all night. Frequently gets shot for them and always deserves it."

"Sound and Fury"

LAST month I reviewed "Caesar's Mistress," a book extremely critical of the B.B.C., and this month I review Maurice Gorham's book "Sound and Fury," which is a record of his 21 years' service with the B.B.C., that is to say, the period from 1926 to 1947, when he left.

In 1926 the B.B.C. was a company owned by the radio manufacturers and chiefly run by the wireless pioneers. Gorham saw the change-over to a public corporation, the growing bohemianism of Savoy Hill, the return to ultra-respectability in new Broadcasting House, the great work which the B.B.C. did during the war, and its gradual reversion to iconoclastic aloofness once the charter had been renewed.

Maurice Gorham should be a reliable recorder of facts, for he worked under five director-generals, edited *The Radio Times*, ran the B.B.C.'s wartime broadcast to America, started the A.E.F. programmes for the troops, the Light Programme, and finally the post-war television service. Towards the latter end of his career he was in the inner councils of the B.B.C. In this book, which is a fair exposition of his experience, he deals with the men who control the B.B.C. and the reasons which led him to resign.

Although one feels that he left under a genuine grievance, this does not unduly obtrude. It is impossible to come to any other conclusion after reading the book than that Gorham thinks the departure of Reith from the B.B.C. was a good thing for broadcasting.

Here are a few extracts: "The B.B.C. had never been so pompous, self-righteous, and aloof. . . . The B.B.C. considered nobody's opinion but its own. . . . Reith professed not to read the newspapers. . . . What the Press thinks is not the final test, it is what we ourselves round this table think of our work. . . . Administration was a stumbling block because Reith and Carpendale made it unduly strong. . . . They thought that everybody doing a productive job was childish and irresponsible and needed controlling by somebody who was concerned only with In-and-Out trays. . . . I do not think of Reith as a great organiser. By the time he left in 1938 the B.B.C. was getting musclebound. . . .

The direction of the Corporation lacked common sense. . . . Reith suffered increasingly from a sub-conscious horror lest the listener should have too good a time. Giving pleasure to the ungodly was not amongst his objectives for the B.B.C. If they liked it too much it could not be doing its job. Listener research came at last, but not until Reith had gone. . . . Reith still disapproves of this."

The fact has to be admitted that Reith was not popular either in the B.B.C., outside the B.B.C., nor with the Press.

As one of the earliest of the radio journalists I came into contact with the B.B.C. from its beginning, and from personal knowledge I can support much of what Gorham has written. The criticism of those who ruled the B.B.C. never ceased, and it is noteworthy that it is a happier organisation altogether to-day. I recommend every reader to purchase a copy of Maurice Gorham's book, which, apart from criticisms and comments, gives a great deal of history hitherto unpublished. He deals with life among the artists, and interesting facts about the stuffed shirt era, *The Radio Times* programme arrangement, the inner circle, Alexandra Palace—in fact, the whole history of the B.B.C.

Gorham is fair in his comments, and gives praise where it is due.

A Survey of Noise in British Homes

NOISE in homes has been the subject of complaint for about a hundred years. The noise problem occurred with flats to an even greater extent than with houses, and the inadequacy of party walls as a protection against noise was a particular subject of complaint. Although it could fairly be assumed that such a large history of complaints had a foundation in hard fact, there was no data on which to work. There was no basis, other than personal experience or complaints registered in the Press, on which an appraisal could be made of the extent and severity of the noise nuisance.

An opportunity was therefore taken to include several questions on noise in a survey carried out during the war by the Government Social Survey, and the answers to these questions are now made available.

While the interpretation of the results of such a survey is in itself a matter requiring some skill, the survey figures do give a first real measure of the problem, at least for the purpose of comparing different sources of noise and different buildings.

Among the interesting points shown by the replies is the fact that the noise of radio, though "noticed" by the largest proportion of people, was considered much less troublesome than what was called "banging of doors"; and in the comparison of buildings, noise was found to trouble about one person in four in houses, one person in three in old-fashioned flats, and two people in three in flats of modern construction.

Remote-control of Your Receiver

Making the Extension Listening Point More Efficient

By J. R. DAVIES

VERY often in the average household there occurs the need to use the radio receiver in a room other than that in which it is installed. Sometimes this requirement is met by the provision of an extension speaker. This, however, has its disadvantages in so far as it is necessary to keep returning to the set to change the station or the volume level, or to switch it on and off.

Various commercial firms have introduced methods of remote control of the receiver, some expensive and some cheap. To the constructor, however, is opened an engrossing field of experiment and design in which he may make all the equipment necessary to control the functions of his set from a distance. There is something fascinating in the realisation that, by pressing a button in, say, one's bedroom, a slave circuit in the living-room follows one's requirements instantaneously and reliably.

In this series, the writer will review the various means that may be adopted in controlling the

Nowadays, it is the custom to use a low-impedance outlet to the external speaker as shown in Fig. 1(b). This saves both a condenser at the receiver and a transformer at the distant speaker. The internal speaker may be silenced by the switch S if desired. The impedance of the speech coil at the distant speaker should be approximately that of the local one to avoid any serious mismatching. The connection of one of the leads to earth or chassis (as shown in Fig. 1(b)), is not necessary, but occasionally tends to remove any chance of instability, particularly in a T.R.F. set, where the extension speaker leads may run close to the aerial. The use of the earthed connection also assists in the wiring of the other control circuits, as it may be utilised as a common return lead, thereby reducing the number of wires between the receiver and the remote point.

Both methods of connection have their disadvantages. In the high-impedance method of Fig. 1(a), the resistance of the wires is not of great importance

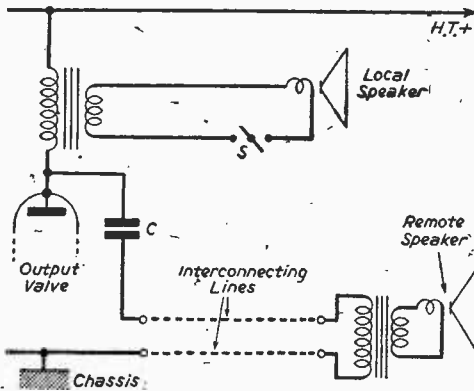


Fig. 1(a).—Showing method of connecting extension loudspeaker, using a high-impedance output from the receiver.

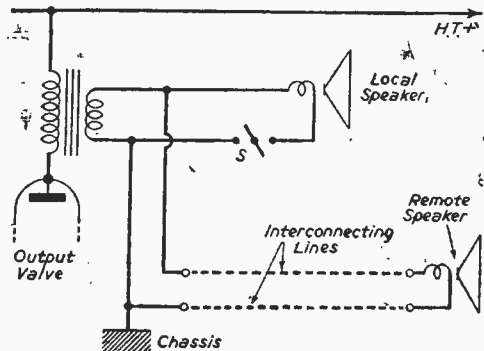


Fig. 1(b).—Low-impedance speaker connections.

receiver remotely, bearing in mind the reliability, economy and suitability of the methods.

Connecting the Remote Speaker

First things first! Before fitting in any system, it is obvious that we must consider the best method of connecting the extension speaker.

Some years ago, and particularly when high-impedance moving-iron loudspeakers were still in use, the usual method of connecting the external speaker was that shown in Fig. 1(a), in which the connection is made via the condenser C and earth. If the speaker in the set needed to be silenced the switch S was opened, the primary of the output transformer in the set acting as an anode choke, and the output impedance being developed across the remote speaker. The condenser C should be a paper component having a capacity of at least $4\mu\text{F}$ to permit full reproduction of bass.

and ordinary bell wire may be used quite satisfactorily. The capacity between the lines, however, may prove troublesome if long runs are used, and will tend to attenuate the higher frequencies. The condenser C has surprisingly high voltages impressed on it during loud passages of music, particularly if there are any resonances in either of the speakers, and should have a working voltage of twice the H.T. voltage of the set. The low-impedance method of Fig. 1(b), whilst saving the cost of the condenser and speaker transformer, introduces an extra expense, in so far as the wire between the two speakers has to have as low a resistance as possible. If really good quality reproduction is desired, the connecting link should consist of, at least, 5-amp. lighting flex or similar wire.

Controlling the Volume Remotely.

A remote control of volume is the next requirement. This may be done at the speaker itself, and various methods are used. Fig. 2(a) shows a good practical method in which the impedance presented

to the set and to the speaker remains constant at all positions, thereby eliminating the chance of distortion due to mismatching. Looking at this diagram, it will be seen that a three-gang six-position switch is used giving six positions of volume. The direction of the arrows alongside the sliding arms indicates the direction in which they move to reduce the volume. The values given at

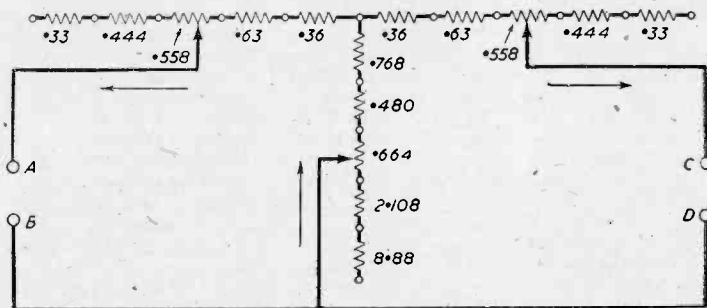


Fig. 2(a).—Circuit of a constant-impedance volume control. The figures indicate resistance values in ohms. The impedance between A and B and between C and D both equal 3 ohms.

each resistance indicate its resistance in ohms; the impedance between A and B and between C and D always remaining constant at 3 ohms.

Fig. 2(b) shows a potentiometer circuit which may be used with high-impedance outlets, as in Fig. 1(a). This method of connection cannot always ensure consistently good quality, however, owing to the inevitable mismatching which will result.

An alternative method of volume control may be utilised by controlling the gain of one of the receiver valves from the remote point. This can be done quite simply and with the addition of only one interconnecting wire. Fig. 3(a) shows the grid circuit of an H.F. valve in a T.R.F. (or non-A.V.C.-

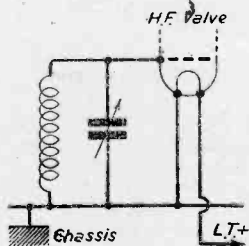


Fig. 3(a).—Normal grid circuit of battery H.F. valve.

controlled superhet). If the valve is of the vari-mu type, its amplification factor can be controlled by the simple process of varying the bias voltage on its grid. Fig. 3(b) and (c) show two simple methods of doing this. The resistance R and the condenser C in these two diagrams are for decoupling the lines and preventing any hum picked up on them from affecting reception. The condenser C in Fig. 3(b) is used also to complete the tuned circuit. The batteries used for varying the bias are kept at the remote control point. The current taken from them by the volume potentiometer is almost negligible, but it is advisable

to switch them off when not in use by the switch S. This switch may be ganged with the remote switch used to switch the set on and off, and which is discussed later. Another method of controlling the bias, particularly when a mains valve is used, is shown in Fig. 3(d). This system is applicable to mains-type valves only and has the advantage of not needing the batteries required in Figs.

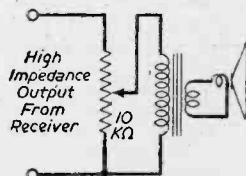


Fig. 2(b).—Simple potentiometer volume control for a high-impedance extension speaker.

3(b) and (c). The interconnecting wire used for the circuit of Fig. 3(d) should have a fairly low resistance, whilst that used in Figs. 3(b) and (c) should be well insulated from earth, its resistance not being so important a factor.

If the set in use is a superhet. with A.V.C., it is not very practicable to control the volume by altering the bias on an R.F. valve. The control will have to be effected in the A.F. circuits after detection. Fig. 4 shows one way of doing this. An octode frequency-changer, such as the Mullard EK32, is used as an A.F. amplifier in place of the

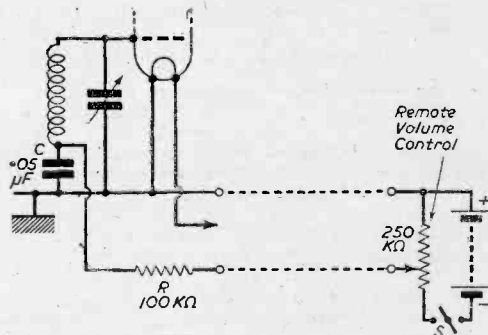


Fig. 3 (b)—One method of applying bias to the valve of Fig. 3(a), so that its amplification factor may be varied remotely.

usual triode after the double-diode. The A.F. voltage is applied to the signal grid, whilst the biasing voltage is applied to the oscillator grid. The values of screen resistor, etc., are shown in the diagram. The valve should be connected immediately after the double-diode so that the biasing circuit will have the greatest control. Some

experimenting may be necessary to find the value of bias battery voltage which gives best results.

Control of Tone

A tone control of the top-cut variety may easily be fitted at the remote speaker. If the connection

high impedance at the condenser network, the various degrees of attenuation being "reflected" to the speech coil.

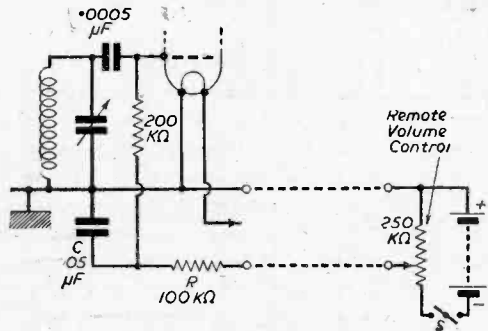


Fig. 3(c).—Another method of controlling bias remotely.

is of the high impedance type shown in Fig. 1(a), a circuit as shown in Fig. 5(a) will meet the requirements, the switch in this diagram connecting the various capacities (or no capacity at all) across the transformer primary and giving varying degrees of high note attenuation. The capacities suggested in the figure will meet most needs, but if additional cut-off is required a larger condenser may be

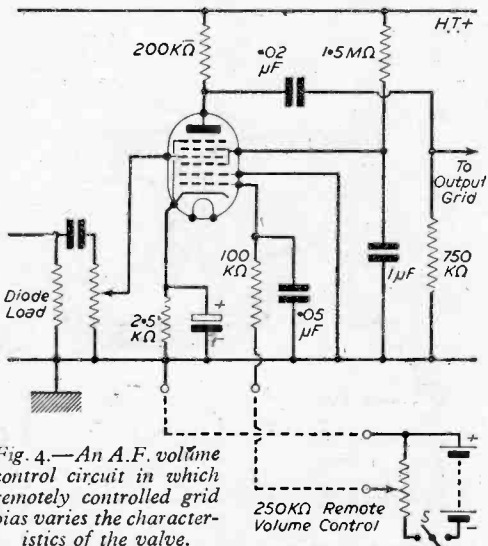


Fig. 4.—An A.F. volume control circuit in which remotely controlled grid bias varies the characteristics of the valve.

fitted in place of the .05μF. condenser, its value being found by experiment.

If a low impedance circuit (see Fig. 1(b)) is used the tone control presents a slightly harder problem. It is not advisable to connect condensers across the speech coil, and the best solution is to fit another speaker transformer at the extension speaker, as shown in Fig. 5(b). This presents a

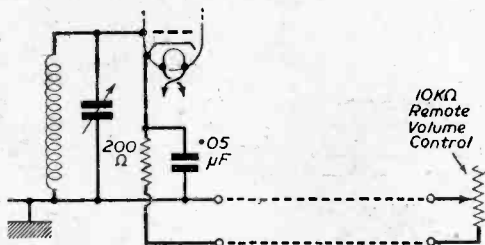


Fig. 3(d).—An alternative method of volume control. As the external volume control puts more resistance in circuit so the cathode becomes more positive, thus increasing the relative negative bias on the grid.

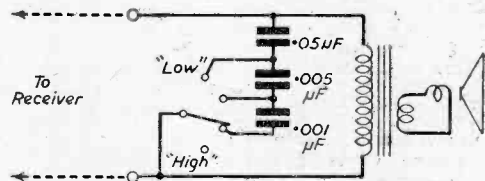


Fig. 5(a).—A tone control circuit that may be connected at the remote loudspeaker.

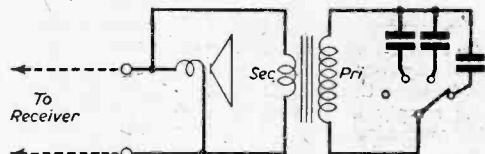


Fig. 5(b).—How the tone control may be connected if a low-impedance outlet from the receiver is used.

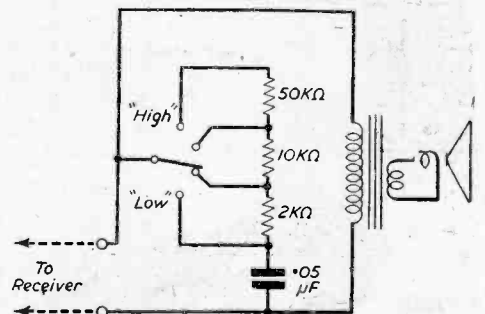


Fig. 5(c). An alternative to the arrangement shown in Fig. 5(a).

An alternative to the condenser switching circuit is shown in Fig. 5(c). In this circuit, various resistors are switched to limit the effect of the single .05μF. condenser.


(To be continued.)



TRUVOX


There is something fascinating about the sound of silver clinking into a bag—and it is the true reproduction of the "noises-off" that mean so much when listening to a favourite programme—Home, Light or Third. It has taken us 18 years to achieve such realism... it's yours to-day. A range of three extension cabinet speakers is in the dealers' shops already, "Monobolt" speaker chassis in four sizes are there, too, you can hear them now. High fidelity pickups and "Wafer" speakers are well on the way. A postcard will bring full details.

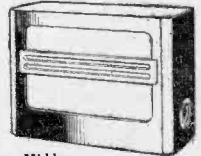MODEL BX105. One of the new range of Truvox Extension Cabinet Speakers. This model incorporates 10in. Monobolt chassis, volume control recessed in side. Beautiful Walnut cabinet with contrasting chamfers and fret motif in Maple. List Price, £5 10s.



Truvox Engineering Co., Ltd., Truvox House, Exhibition Grounds, Wembley, Middx.

TK35A

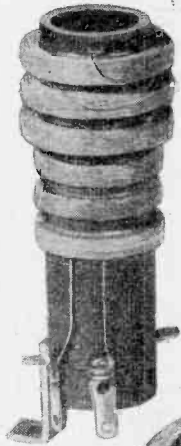


RM

HIGH Q. T.R.F. COILS TYPE 34/5

The choice of coils decides the performance of a T.R.F. Receiver. Users of these R.M. Coils acclaim them as the finest available. Try them yourself.

15/- PER PAIR

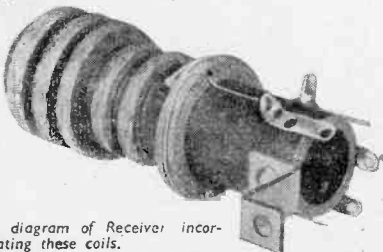

Send for circuit diagram of Receiver incorporating these coils.


R. M. ELECTRIC LTD.
TEAM VALLEY, GATESHEAD, 11

For the *Connoisseur* pick-up


GRAMOPHONE NEEDLES NOW 20 for 2'10" INCLUDING P.T.



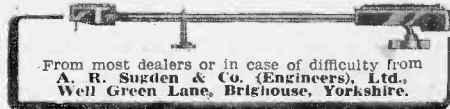Now half price—hard chromium-plated needles with green shanks. Radius of needle point guaranteed accurate within the tolerance of .002in./0.003in. Each needle will play 20 sides and up to 50 without damage to record.



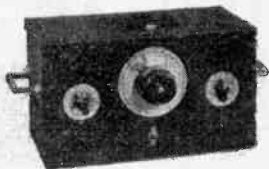From most dealers or in case of difficulty from A. R. Sugden & Co. (Engineers), Ltd., Well Green Lane, Brighouse, Yorkshire.



"Q-MAX" Short Wave Four. All-Dry Battery receiver. Range 11-350 metres (plug-in coils). Price £15 9s. 5d., incl. P. Tax. (Speaker, Battery and Coils extra).

GRAM. MOTORS, Garrard or Collaro, A.C., £5 18s. 6d. The new 12in. Celestion Speaker, 75/-.
Lead-in tubes. 6in., 1/-; 12in., 1/6.

AMPLIFIERS, complete in metal cabinets. 3 v. A.C. or 3 v. A.C./D.C., 4 watts, 10 Gns. 4 v. A.C. or 4 v. A.C./D.C., 7½ watts, 14 Gns.

SIGNAL GENERATORS. BPL, £21. Advance, £23 10s. TAYLOR £15 10s.

AVO METERS, No. 7, £19 10s. Universal Avo, £8 10s. Avominor, £4 4s. **AVO TEST BRIDGE** £11.

MAINS TRANSFORMERS. 350-0-350 v. 6.3/4v. 3 A., 6.3/4v. 2 A., 5/4v. 3 A., 120 mA., 49/6; or 150 mA., 59/6. 250-0-250 v. or 350-0-350 v. 6 v. and 5 v. 80 mA., 32/6. PIP Output 5, 8, 10 and 12K ohms CT. 3, 6, 10 or 15 secs. 10 w., 32/6.

BERRY'S
(SHORT WAVE) LTD.

25, HIGH HOLBORN, LONDON, W.C.1



MAINS TRANSFORMERS & CHOKES

All "Varley" products are manufactured from the highest quality materials.

Transformers, etc., are individually wound and have interleaved windings with ample insulation, ensuring freedom from breakdown.

The comprehensive range of Shielded and Open type Transformers available meets the requirements of every circuit.

Write for list, etc.

Made by

OLIVER PELL CONTROL LTD
CAMBRIDGE ROW · WOOLWICH · S · E · 18

Telephone: WOOLWICH 1422

CLYDESDALE

For Ex-Services Electronic Bargains.

Brand New

Receiver and Units of SCR-269-G Radio Compass. BC-433G Receiver. BC-434A Control Box. flexible drive, Indicators 1-81-A, 1-82-A, and Service Inst. Book.

CLYDESDALE'S PRICE ONLY **£6. 15s.** per set. CARRIAGE PAID.

Ideal as S.W. Converters.

R.F. Unit 26 for 65-50 mcs. Variable tuning.

R.F. Unit 27 for 65-65 mcs. Variable tuning.

Brand new in maker's carton at 35/- each, or used, good condition, 19/6 each, post paid.

R.F. Unit 24 for 26-30 mcs. Switched tuning.

R.F. Unit 25 for 40-30 mcs. Switched tuning.

Brand new in maker's carton at 19/6 each, or used, good condition, 12/6 each, post paid.

Ex R.N. D.C./A.C. Converter.

Input 24 v. D.C. Output, 182/302 v. A.C. at 75 watts. Complete in decast case, 18in. x 12in. x 11in.

CLYDESDALE'S PRICE ONLY **£6 19s. 6d.** each CARRIAGE PAID.

Brand New Ex R.A.F.

Battery Amplifier A1368.

2 stages, 2 valves, intercom., pre-amp. and Xmtr mod. unit, complete (less batteries), with circuit metal case, 7in. x 4in. x 4in. Improved version of A1134.

CLYDESDALE'S PRICE ONLY **11/6d.** each. POST PAID.

Brand New Ex R.A.F.

Vernier S.M. Drive, 38-1 dia. 3in. as used in R.F. 26 and 27, at 9/6 each, post paid.

Send now for 112 page List No. 5. Print name and address.

CLYDESDALE SUPPLY CO LTD

2 BRIDGE STREET - GLASGOW - G.5

Phone : SOUTH 2706/9


Visit our branches in Scotland, England and Northern Ireland.

6 VALVE SUPERHET

Receiving Unit of the TR1196 which covers 4.3 to 6.7 mc/s. Among the many useful components are : 1 pr. standard I.F. Transformers (460 Kc/s), Iron Dust Cores, two 1 mid. 500-volt working condensers ; 4 1 metal tubular Condensers ; 1 MIC Transformer ; 1 Phone Output Transformer, 2 Pot. meters.

10 Fixed Condensers, standard values ; more than 2 doz. resistors, 200 ohms to 1 megohm ; 6 International Octal Valve Holders ; 2 tag Boards ; 1 Yaxley Switch ; 4 pre-set 0.001 Condensers and Tuning Coil. Steel chassis, size 8 1/2in. x 6in. x 2 1/2in.

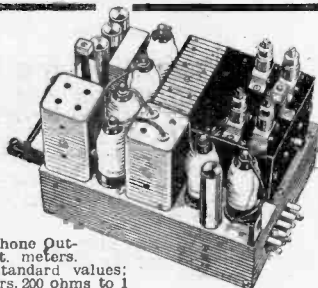Data Book giving circuit diagrams, component values and valves used, etc., post free 1/6.



Less Valves. **10/-** post free.

With Valves, plus 2/6 packing and ins. **29/6**

Television Bargains

R1355 RECEIVER for construction of inexpensive television. Complete with R.F. unit type 25, 47/6 plus 5/- carriage.

8 M.F.D. CONDENSERS. 450 volt working. Post free 1/9 each.

H.V.U. 1 E.H.T. Rectifier. Post free 8/-.

E.H.T. TRANSFORMER to give 2,500 volts, and 4 volts at 3 amps, and 63 volts at 3 amps. Post free, £2/10/0.

"INEXPENSIVE TELEVISION" BOOKLET at 1/6. Shows how to make your Television from Ex-Govt. Units listed above.

MAINS TRANS. Stand-up and Drop-through type. Primary 200-250 volts. Secondary 350-0-350 80 mA. 5 volts 2 amps, 4 volts 3 amps. Post paid. **£1**

NUTS, BOLTS, WASHERS small sizes for model making. Three gross assorted. **7/6**

SCREENED FLEX Suitable for mikes, 100ft. **10/-**

Write Dept "R."

INSTRUMENT CO.
244, HARROW ROAD,
LONDON, W.2. CUN. 0598.

D.C. Oscillograph Amplifier

A Two-valve Unit With Stabilised Power Supply

By B. F. WALKER

A D.C. coupled amplifier has many advantages, namely:

(1) No distortion of low-frequency square waves due to the time constants of coupling resistances and condensers.

(2) No phase shift at low frequencies.

(3) Instantaneous shift control, since there is no delay in waiting for coupling condensers to charge as in an A.C. coupled amplifier.

In addition it may be used as a rough D.C. and A.C. valve voltmeter for frequencies up to about 100 kc/s.

The Circuit

As shown, the input goes via S, which inserts a 2 μ F condenser when it is necessary to block any D.C. present when examining say the signal on the anode of a valve. There is a 20/1 attenuator operated by S2, and the small trimming condenser over the 2 M Ω resistor is used to compensate for the loss of high-frequencies due to the unevenly

distributed capacities over the attenuator. The 1 M Ω potentiometer P1 is the fine gain control feeding into the 6J5 cathode follower. This has its anode strapped to the screen of the 6J7 and they are both supplied from +130 volt stabilised supply from a Cossor S130 stabiliser. The cathode of the 6J5 is joined to 25 k Ω potentiometer, P2, which acts as the shift control by varying the bias on the 6J7 and hence the anode voltage. The anode is attached directly to one of the plates of the cathode-ray tube, therefore any variation in anode voltage moves the spot on the screen. The 500 k Ω pre-set potentiometer is adjusted so that the spot is central on the screen when the shift potentiometer is about midway in its travel.

The 1 k Ω cathode resistance of the 6J7 provides negative feedback at low frequencies, and it is shunted by a condenser "C" which reduces the feedback at high frequencies and hence improves the H.F. response. An approximate value for this is .0025 μ F, but, if possible, it should be adjusted by applying a few thousand cycles/sec. square wave to the input and finding the value which gives the best waveform.

The anode of the 6J7 is coupled to the cathode-ray tube plates by a 100 k Ω resistor. If desired a smoothing choke, Ch1, may be inserted between the resistor and H.T., but it is questionable if this gives any great improvement in H.F. response. Anyway the H.F. response is limited to about 100 kc/s by the varying capacitance of the slider of the gain control to earth, which shunts high frequencies to earth.

The amplifier is not push-pull, the other C.R.T. plate being fed from a potentiometer of two .25 M Ω resistors across the H.T. line, but I have used the amplifier in an oscillograph for some time now and find that trapezium distortion and astigmatism are very slight with both the VCR135 (Mullard ECR35) and VCR97 (Mullard ECR60).

Expanded Trace

With the values shown five screen diameters shift are obtainable on a VCR138 using 1,000 volts on the final anode. There are identical X and Y amplifiers and I have adjusted the output from the time-base (a Phantastron) so that I can use the gain control to expand the trace to five screen diameters.

This is a great convenience when examining a waveform, as the trace can be expanded to five screen diameters and any part brought on to the screen for detailed examination.

On the Y plates the spot can be swept from one edge of the screen to the other by the application of 1.5 volts (from a torch battery) to the input terminals. The same happens on the X plates by the application of 3 volts, since the Y plates have twice the sensitivity of the X plates.

The power supplies for cathode-ray tube (-1,000 volts), time-base (+350 volts) and amplifiers (+350 volts, +130 volts, -130 volts), are all taken from one 350-0-350 volt 60 mA. transformer. There is a 4 volt 1 amp. winding for the C.R.T. This requires high insulation and I obtained an old 400-cycle transformer (ex R.A.F.) cheaply and had the core re-wound to my specification. There

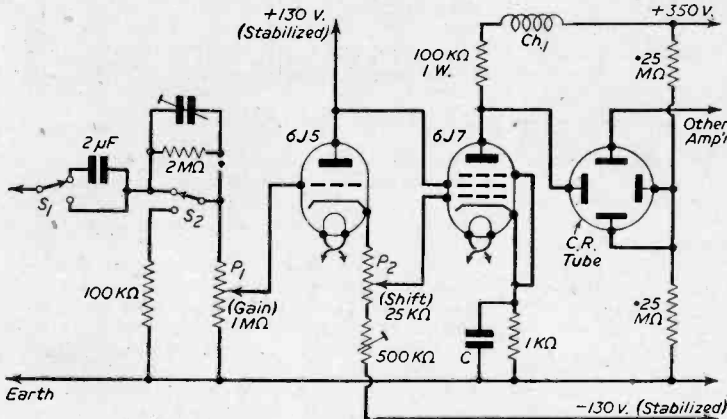


Fig. 1—Theoretical circuit of the amplifier.

distributed capacities over the attenuator. The 1 M Ω potentiometer P1 is the fine gain control feeding into the 6J5 cathode follower. This has its anode strapped to the screen of the 6J7 and they are both supplied from +130 volt stabilised supply from a Cossor S130 stabiliser. The cathode of the 6J5 is joined to 25 k Ω potentiometer, P2, which acts as the shift control by varying the bias on the 6J7 and hence the anode voltage. The anode is attached directly to one of the plates of the cathode-ray tube, therefore any variation in anode voltage moves the spot on the screen. The 500 k Ω pre-set potentiometer is adjusted so that the spot is central on the screen when the shift potentiometer is about midway in its travel.

The 1 k Ω cathode resistance of the 6J7 provides

are many firms who undertake rewinds. Alternatively a small high-insulation heater transformer could be used.

Transformer Windings

A voltage of 6.3 at 3 amps should be sufficient for amplifiers and time base and another winding is needed for the rectifier, which could be a 5Z4 or similar valve. The smoothing condensers ($8+32\ \mu\text{F}$) were a Hunts $8+16+16\ \mu\text{F}$ 450 volt can with the two $16\ \mu\text{F}$ sections in parallel. A $10\ \text{k}\Omega$, 5 watt resistor feeds a Cossor S130 neon stabiliser which supplies the 130 volt positive for the amplifiers. The stabiliser is shunted by a $.1\ \mu\text{F}$ condenser to bypass H.F. currents. A small metal rectifier over half the H.T. winding supplies 130 volts negative bias for the amplifiers. The only smoothing necessary is an $8\ \mu\text{F}$ condenser on the rectifier side of the $20\ \text{k}\Omega$ 5W resistor. However, if any trouble is experienced a $2\ \mu\text{F}$ condenser on the other side of the resistor should suffice.

The 1,000 volt negative for the C.R.T. is obtained by means of a circuit similar to that described in these pages early last year. A $1\ \mu\text{F}$ 2,000 volt working condenser is put across the 350-0-350 volt winding in series with a C.R.T. metal rectifier, and another rectifier is attached to the junction, and the output is taken from the other side of this. The smoothing is accomplished by a $.25\ \text{M}\Omega$ resistor and two $.1\ \mu\text{F}$ 2,000 volt condensers. It is important that the metal rectifiers used for supplying the 1,000 volts for the C.R.T. are capable of handling the voltage, so they must be television types or several receiving types in series.

I find the H.T. drain of the whole oscilloscope to be only 30 mA. and thus a small transformer can be used.

There is also no appreciable interaction between amplifiers and time-base if a $32\ \mu\text{F}$ condenser is used for smoothing, as shown.

It is not necessary to use Cossor S130s. Most common stabilisers will do if the burning voltage is over 90 volts.

Adjustment

To adjust the amplifiers, the $500\ \text{k}\Omega$ preset potentiometers should be set at maximum and the shift controls midway in their travel. One set of plates can be shorted to the final anode, and a good voltmeter connected to measure the H.T. on the other valve anode. The $500\ \text{k}\Omega$ preset is then adjusted till the voltage is the same as that on the tapping of the potentiometer of two $.25\ \text{M}\Omega$ resistors, from which the other plate is fed. This should be about 170 volts. The spot should then be visible on the screen. The same procedure is then repeated for the other amplifier.

The condenser "C" over the cathode resistor of

the 6J7 should be adjusted by means of a square wave generator, if available, otherwise $.002\ \mu\text{F}$ or $.003\ \mu\text{F}$ should be satisfactory. The same applies for the trimmer over the $2\ \text{M}\Omega$ input potentiometer. This should be a 60 pF trimmer.

After the first few minutes when it has warmed up the amplifier is quite stable and does not drift with mains fluctuations. The frequency response

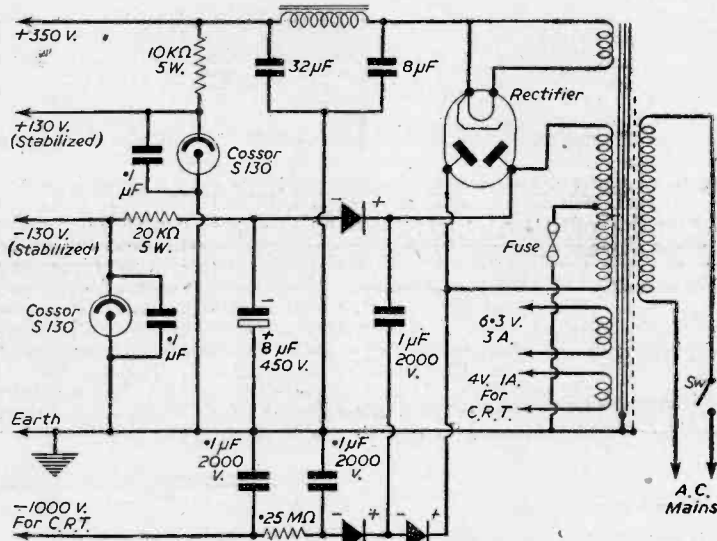


Fig. 2—Circuit of the power pack with values marked.

is reasonably linear from D.C. to 100 kc/s and hence it is admirably suited for all audio frequency work and gives a good enough response for pulse examination. The gain falls appreciably beyond 400 kc/s.

Another device I have found useful is a neon tube synchronising circuit for the time-base.

A small neon lamp (it need not be a stabiliser) is connected over half the 350 volt winding in series with a $1\ \text{M}\Omega$ resistor. There is a difference of about 20 volts between the striking and burning voltages of the neon, and thus there are alternate +ve and -ve pulses every one-hundredth of a second. This provides good synchronising on large multiples and sub-multiples of 50 cycles where a sine wave would not work well and would cause erratic synchronising.

WORKSHOP CALCULATIONS TABLES AND FORMULÆ

Eighth Edition

by F. J. CAMM

A handbook dealing with methods of calculation, solutions to workshop problems, and the rules and formulæ necessary in various workshop processes. It contains all the information a mechanic normally requires.

From all booksellers, 6/- net,
by post 6/6 from the publisher.


GEORGE NEWNES, LTD. (Book Dept.),
Tower House, Southampton Street, W.C.2.

Practical Hints

A Quickly-made Tag Board

FOR this device you will require a strip of red fibre or other insulation material about 1/16in. thick, and some brass paper clips. The length and width of the strip depend upon the number of tags and the size of paper clips.

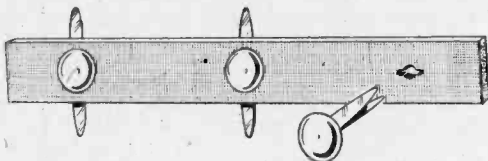Scribe a line down the centre of the length of strip, divide into number of tags required, leaving a small space between each. At each position drill a small hole right on the centre line, and slightly smaller in diameter than the width of the legs of the paper clips. Using the centre line already scribed as a guide, cut, with a Swiss file or fretsaw, a very small slot, each



Mr. Percy's idea for home-made tag-boards.

side of the hole dead on the centre line, of such a depth as to allow the paper clip to be pushed in the hole and slots each side of the hole. The slots will prevent the clip from turning.

Pull the clips tightly into the holes, and bend back the legs, one up, one down, on the back of the strip.

By fitting two small brass angle brackets, one each end of the strip, first, and drilling through these brackets as well as the strip, the first and last tags may be earthed to the chassis through the brackets. In this case one leg is bent down as before, the other is bent up and soldered to the bracket or clamped under it.—H. L. PERCY (Coves, I.O.W.).

THAT DODGE OF YOURS!

Every Reader of "PRACTICAL WIRELESS" must have originated some little dodge which would interest other readers. Why not pass it on to us? We pay half-a-guinea for every hint published on this page. Turn that idea of yours to account by sending it in to us addressed to the Editor, "PRACTICAL WIRELESS," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Put your name and address on every item. Please note that every notion sent in must be original. Mark envelopes "Practical Hints."

SPECIAL NOTICE

All hints must be accompanied by the coupon cut from page iii of cover.


Cutting Sheet Aluminium

CUTTING out an aluminium chassis with a small pair of shears is not a satisfactory method, as the metal has to be bent to clear the hinge of the shears. There is also the risk of cut hands when operating the shears between the two sharp edges one has cut.

The writer has found that a much neater job can be done with the tool shown below. It was made from a 6in. flat file, the end of which was ground smooth and shaped, as in the drawing,

on a small hand grindstone.

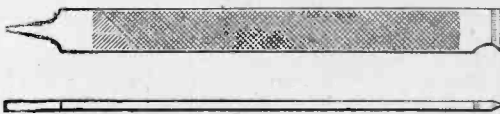In use the tool is drawn several times along a straight edge until the aluminium is cut nearly through. Then it is bent backwards and forwards a few times until severed. The edge is afterwards trimmed with a file.




A useful tool for "cutting" aluminium.

Switch Indicator

I HAVE no doubt that many readers have made up a multi-range meter using an ex-Government instrument. Many of these meters have "awkward" scales for calibration, and it is usually found that each scale division represents a different value on the various ranges. Here is an idea I am using, and I find it minimises error due to faulty readings.

A piece of stiff card is cut into a circle and a 1/4 in. hole made in the centre. This is now glued or pinned to an ordinary spindle coupler, with their holes corresponding. It is then slipped over the range switch spindle and tightened up. A small window and a spindle hole are now made to correspond with the card and switch spindle respectively. The switch itself can be mounted on a suitable bracket. Now the required information can be written on the card for the various ranges in the different positions. Such information might be: 0-100 volts, 1 division=2 volts, and thus it will always be seen on any particular range what calculation to make. If desired a small piece of glass can be placed behind the window to make a "finish."

—G. D. RUDRAM (Lancing).

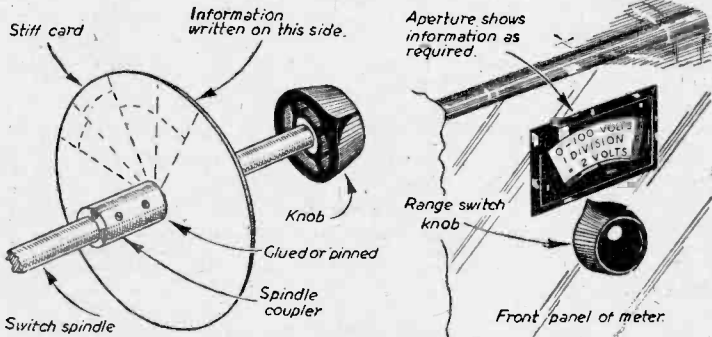

How an indicating dial may be made up and fitted to a rotary type of switch in a multi-range meter, to provide a "scale" for each setting.

Theoretical Details

WE now turn to the unit which, apart from the vision chassis, is probably the most important part of a complete television receiver, namely, the time-base chassis, shown in theoretical form in Fig. 1.

The unit in the present receiver is a six-valve section, V11 to V16 inclusive, the first pair of valves constituting the synchronising separator and limiter stages. V13 is the line discharger valve with V14 as line amplifier, and V15 is the frame discharger valve with V16 as frame amplifier. The amplifier valves feed the deflector coils with correctly-shaped pulses to build up the raster on the screen of the cathode-ray tube.

Turning to details, V11, which is an EF50 (VR 91) strapped screen to anode, operates as the synchronising separator proper by working with a very low anode voltage which brings the working point of the characteristic on to the bend of the curve. The vision signal which is applied from the anode of the phase-splitter V10 in the vision unit is negative-going in sign, with the result that only the synchronising pulses feed the valve into the conducting regions of the characteristic, and the output from the anode thus consists only of negative-going synchronising pulses freed from the vision signal itself. Fig. 2 (a) shows the actual oscillogram on the anode of V11. This output is applied to the grid of V12 through the normal RC network of C2 and R4, and V12 itself functions as a straightforward amplifier and inverter, producing at the screen and anode positive going sync. pulses for triggering the line and frame thyatron discharger valves.

The output from the anode is applied to a short time-constant differentiating stage consisting of C7 and R11. C7 is a home-made component and is illustrated in Fig. 3. The construction is in no way critical, and with care can be made in a couple of minutes. Good insulation is the main item of importance. R11 is 270k Ω . in value, and in conjunction with C7 splits up the positive sync. pulse of Fig. 2 (b) into a series of alternate

Building a Tele

This Month Constructional Data on the S

By S.

positive- and negative-going spikes of extremely short duration. The positive spike is used to trigger the line thyatron V13, and so synchronise the picture with the transmitter. (Fig. 2 (c)).

The line thyatron valve is the Mazda T41, a reliable and popular discharger for this sort of work, and in the unsynchronised condition i.e., in the absence of a signal, is a free-running sawtooth oscillator working at a frequency between 9 and 11 kc/s. C8 is the actual charging condenser which charges through R13 from the H.T. line, and VR2 is used to control the frequency by the simple method of adjusting the cathode resistance. The synchronising pulses from C7 when applied lock the frequency very firmly to that of the transmitter (10,125 cycles per second), and so ensure a steady picture on the screen.

The saw-tooth output at line frequency from V13 is fed to the line amplifier valve, a power tetrode type 807, chosen on account of its reliability and the fact that it has a top-cap anode connection. This latter is almost a necessary condition in line amplifiers in view of the very high voltage appearing at the anode during the line fly-back. In single-ended valves spark-over troubles are almost inevitable if used as line amplifiers. The gain of the stage, and thus the width of the picture, is controlled by VR1, which is a pre-set control of 250 Ω value and functions by virtue of varying the negative feedback on the stage. This form of control tends to improve linearity, for which reason R14 is also included in series with the charging condenser. The output from the anode is shown in Fig. 2 (d) and although this looks terrifying it is quite suitable for feeding the line deflector coils which modify it through

LIST OF COMPONENTS

R0, R12, R24—3.3 k Ω .

R1, R4, R17—1M Ω .

R2—27k Ω .

R3—110k Ω .

R5, R23—470k Ω .

R6, R8—47k Ω .

R7, R9—25k Ω .

R10—4.7k Ω .

R11—270k Ω .

R13, R25—220k Ω .

R14—470 Ω .

R15—2.5k Ω .

R16, R29—1k Ω .

R18—160 Ω .

R19—47 Ω .

R20—200k Ω .

R21, R22—100k Ω .

R26—1.5k Ω .

R27—0.5M Ω .

R28—200 Ω .

R30—3.5k Ω .

Eric Ceramic, etc.

(All resistors $\frac{1}{2}$ watt type except R15 which is 1 watt and R30 which is 15 watts.)

C1—4 μ F.

C2, C12, C14—1 μ F.

C3, C4, C13—5 μ F.

C5—25 μ F. (25v. working).

C6—0.05 μ F.

C7—See text.

C8—0.02 μ F.

C9—0.1 μ F.

C10, C11—0.01 μ F.

C15—0.005 μ F.

C16—16 μ F. Electrolytic (500v. working).

T.C.C. mica, etc.

(All condensers above 0.005 μ F should be of the 500 volt working type, except where otherwise stated, and those of 0.005 μ F and below are of mica.)

VR1 (Width)—250 Ω .

VR2 (Line hold)—2.5k Ω .

VR3 (Frame hold)—2.5k Ω .

VR4 (Height)—0.5M Ω .

Valveholders—2 Mazda Octal, paxolin; 2

Belling-Lec, B9G; 1 International Octal;

1 5-pin U.X. type.

Valves—2 EF50 (V.R.91); 2 T41 Mazda; 1

807; 1 EL33.

Line Transformer—4.5 to 1. (Midco Radio, Wellingborough.)

Chassis—12in. x 6in. x 2in.

Wire, sleeving, nuts and bolts, tag strips.

ision Receiver-2.

nsing Separator and Time-base are Given
NIGHT

their self-inductance. T1 is the line transformer, a very important component. This has a ratio of 4.5 to 1 and is made so that the connection to the top-cap of V14 is direct and well insulated. It is specially matched to the deflector coils to be specified later on, and so any type just won't do.

Going back now to V12, at the screen the sync pulses (similar to those appearing at the anode) are fed to a frame integrator network consisting of R20, R21, C10 and C11. This layout works in a manner opposite to that of the differentiator circuit, in that it "bunches" the frame pulses at the end of each half-frame into one long pulse, at the same time destroying completely the high-frequency line pulses. The frame discharger valve V15, which otherwise functions in exactly the same way as V13, is thus only triggered at the end of the half-frames, with the result that the generated saw-tooth has a frequency of 25 cycles per second.

When the stage is free-running in the absence of a signal, the frequency is variable by VR3 and may be anything between 20 and 100 cycles per second, the charging condenser in this case being C13. When the stage is synchronised the saw-tooth output is locked to the transmitter just as the line thyatron is locked by the line pulses.

The output at frame frequency from V15 is fed to the frame amplifier through C14, and a correcting network C15 and R27, and the gain of the amplifier V16 (EL33), is adjusted by VR4, which thus varies the height of the picture. The cathode resistance R28 is unbypassed to assist linearity, and the output appearing across R30 (a 15-watt resistance), is passed through C16, a 16 µF electrolytic, to the frame deflector coils. These coils, together with the line coils, are, of course, located in the tube unit, and will be described later in the series.

There are two heater inputs to this unit, one of 6.3 volts at 3 to 4 amps., and one of 4 volts at 3 amps. The other side of all heaters returns directly to chassis.

Construction

The photograph shows the general appearance of the finished unit, which is small and neat. The

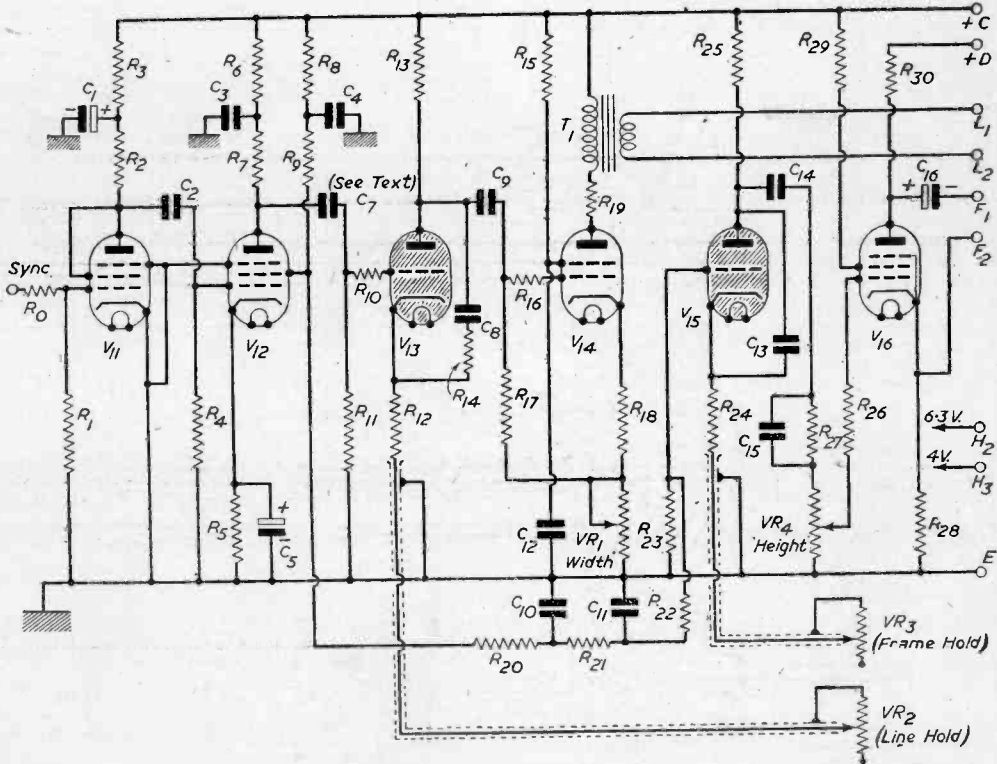


Fig. 1.—Theoretical circuit of the synchronising separator and time-bases. The illustration on our cover shows the completed unit.

chassis size is 12in. by 6in. by 2in. deep, and is made from heavy gauge aluminium. A larger chassis size may, of course, be used if one is conveniently to hand, provided the general layout remains the same. Fig. 4 shows the underchassis layout of components; tag strips are used wherever junctions have to be made, otherwise resistances and condensers are wired directly from pin to pin. There is nothing particularly critical about the actual building of this unit, but good separation of line and frame input pulses to the thyratrons should be aimed at (physical separation, that is) to avoid any unwanted interaction.

VR1 and VR4, respectively the "Width" and "Height" controls, are presets and are mounted at the side of the chassis as seen in the photograph. Once set during test they need be touched no more. VR2 and VR3 on the other hand are respectively the "Line Hold" and "Frame Hold" controls and must be made available for setting up at the beginning of each programme. They are accordingly brought away from the main chassis through about 18in. lengths of screened lead (the thin type of coaxial cable is admirable), as the photograph shows. Later, if and when the whole set is fitted into a cabinet, these controls can be conveniently mounted on to the front panel. The self-capacity of the lead is not critical, and the screening is used as the earth return.

The anode resistance of the frame amplifier,

R30, is a 15-watt resistance of value 3,500Ω. This is mounted above chassis next to the line transformer, and the photograph shows this clearly. No heat is thus generated unnecessarily below chassis. The line amplifier also has a high-voltage protective top connector included, in which is the 47Ω stopper resistance, though such a connector is not absolutely necessary. It is, however, advisable, in view of the flyback voltage developed at this point.

The line and frame outputs are brought out through a four-way cable to an eight-pin Octal plug, alternate pins being those used. The cable length depends on how far away the tube unit is going to be, but 18in. should prove adequate for most cases. The heater and H.T. inputs are brought through a similar length of five-way cable, fairly heavy leads being used for the earth and heaters. All leads, both those going to the deflector coils (L1, L2 and F1, F2), and those coming from the power supply +C, +D, E, H2 and H3), connect to the main chassis on tag strips mounted along the far edge.

The only other points of importance are: all earth connections should be short and well made, components should be rigidly mounted, and a substantial gauge of aluminium used for the chassis itself.

All resistances are rated half-watt except R15, which is 1 watt and R30 which, as previously

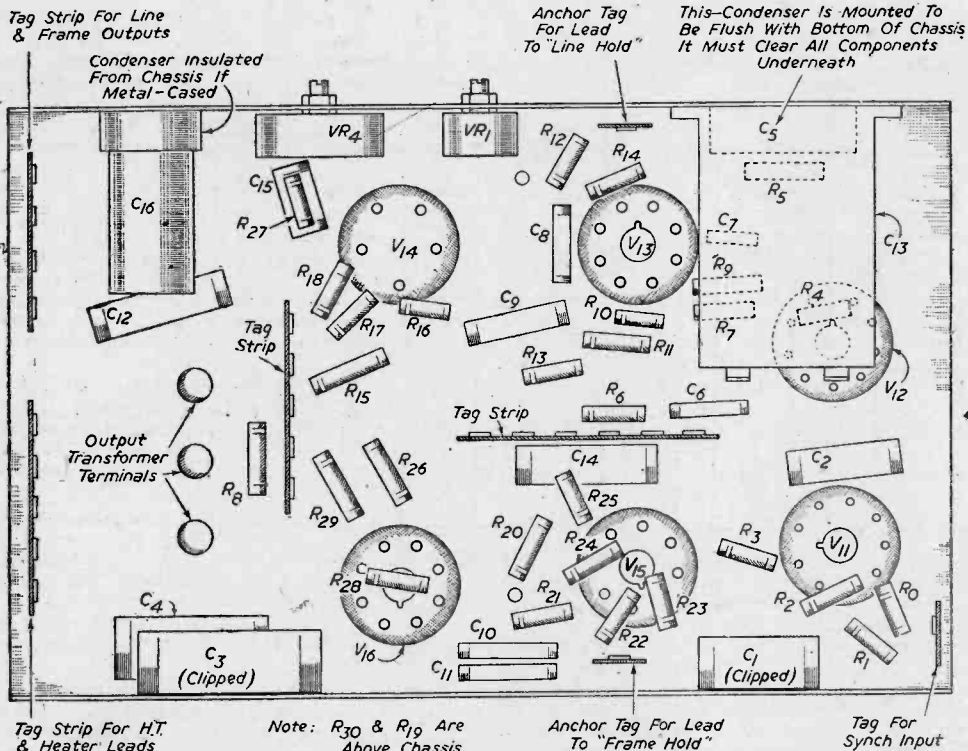


Fig. 4.—Underchassis layout of the time-base unit. In practice the chassis is more "cramped" than appears here, and some slight differences in position are permissible.

mentioned is 15-watt. Note carefully that C16 is an electrolytic (500 volt working), and that if a metal cased component is used it *must* be carefully

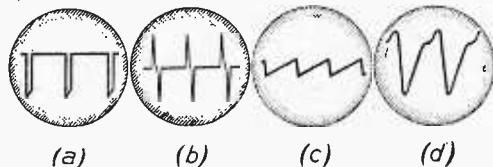


Fig. 2.—Typical traces obtained on the oscilloscope at various points in the time-base.

and adequately insulated from the chassis. A few turns of insulating and Empire tape between the can and the clip are essential, and insulation should be checked before H.T. is applied to the unit. The positive terminal goes to the valve anode.

All condensers must be rated with regard to working voltage depending upon their position in the unit; C1, C2, C3, C4, C6, C8, C9, C12, C13,

C14, should all be 500 volt types, with those of value below $0.005\mu\text{F}$. of the mica type. Other condensers not listed above should be of the mica

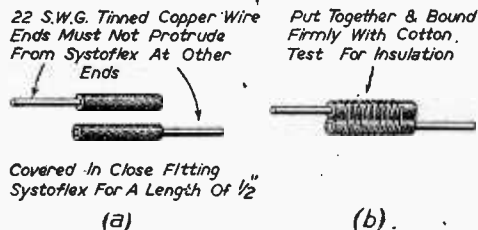


Fig. 3.—Stages in the making of a low-capacity for the line differentiator.

type, except C5, which is an ordinary 25-volt bias electrolytic.

This completes the time-base unit, and the next section to be described will be the sound receiver—a five-valve chassis.

(To be continued.)

Trade Notes

Taylor Tester

TAYLOR ELECTRICAL INSTRUMENTS, LTD., are in the very near future introducing a modified version of the popular Taylor Model 70A. This model will be known as No. 70B. The object has been, by means of mass-production methods, to produce an instrument approximately to first-grade standard and available at a popular price.

Model 70B will have a total of 50 ranges available and fitted with a Taylor Moving-coil Meter. A mirror scale and knife-edge pointer will be fitted and the sensitivity on both A.C. and D.C. volt ranges will be 1,000 ohms per volt. Provision is made for six decibel ranges and a self-contained buzzer is incorporated for quick continuity tests. The price of this instrument will be £14 14s.

A radio-frequency measuring instrument, mains operated, for frequency measurements in all amateur bands up to 60 Mc/s with an accuracy of better than ± 0.1 per cent., is also announced.

The equipment comprises a stable variable frequency oscillator calibrated from 1.6 to 2.0 Mc/s, a 100 kc/s crystal-controlled oscillator, a detector valve to enable beats to be heard in headphones, and power supply.

The variable frequency oscillator is inherently stable and has ceramic insulation throughout. Its calibration can be checked against harmonics of the crystal oscillator and small corrections made by a panel trimmer. A set of tuned circuits is provided, each pre-tuned to the centre of an amateur band, so that by selecting any one the harmonics over that band are greatly intensified. On the 10 and 6 metre bands, where several harmonics can be heard, a simple chart enables positive and instantaneous harmonic identification without calculations.

The instrument may be used to measure transmitter frequency; to calibrate receivers over the amateur bands; to monitor transmissions; and to measure frequency drift of transmitters and receivers.

The instrument is 12in. by 8in. by 6in., and the mains consumption approximately 8 watts.

Carlton Coils and Transformers.

MANY amateurs have been converting ex-government equipment to amateur use, and for some considerable time the Carlton Coilwinding Co., of Birkenhead, have been manufacturing chokes, coils and transformers for the conversion of ex-government equipment to A.C. mains operation, with the minimum amount of alteration to internal wiring.

The transformer for the B.C.348 has a 26-volt filament winding and is of such a physical size that it can be mounted, together with their standard choke, type CLF/100 and the rectifier valve, on the platform which is normally occupied by the dynamotor.

Transformer type CBC/453 has two filament windings, together with the usual H.T. and rectifier filament windings. One of the L.T. windings is 25 volts at .45 Amp. for use with the B.C.453, 454 or 455, and the other, 6.3-volts at 3 Amps. is intended to heat the filaments of a converter such as R.F.26 or R.F.27 when used in conjunction with the B.C.455.

Of special interest to the amateur wishing to build a cheap broadcast reception set is the medium-wave coil unit type CMW/453 to convert the B.C.453 receiver for operation on medium waveband. These are supplied complete with connecting data and retail at 10s. each.

Using Metal Rectifiers

Hints on Replacing a Valve in Certain Circuits

By F. G. RAYER

IN some circuits metal rectifiers can be used with advantage, types being available which may be used for detection, A.V.C. and mains rectification. They may also be used for accumulator charging, and for adding A.C. ranges to D.C. meters, but as these particular aspects do not come into the design of receivers, they are not dealt with here.

Here the rectifier has been connected directly to the primary of the transformer. This causes no appreciable loss of efficiency if the component is a good quality one with a high primary impedance. Usually the self-capacity of the primary is sufficient to enable rectification to be achieved, but if necessary a condenser of about .0001 μ F may be shunted across it.

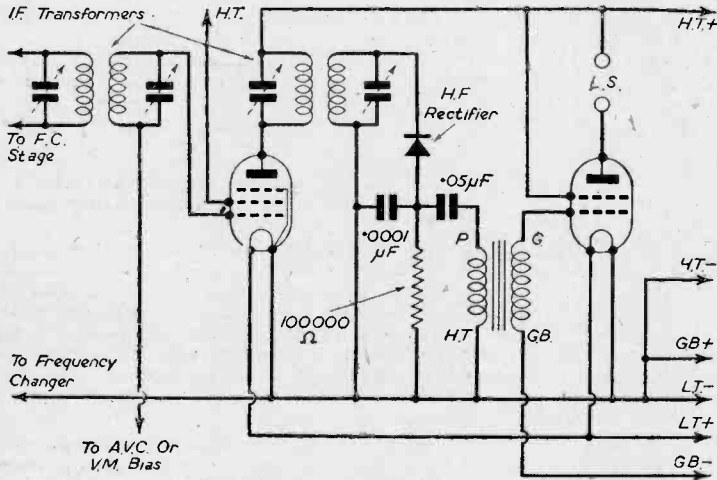


Fig. 1.—Using a metal rectifier as the second detector in a superhet circuit.

Rectifiers for Detection

Fig. 1 shows a suitable circuit for a superhet, only the last I.F., detector, and output stage being shown. For a simple receiver this avoids having to use an extra valve for the detector, or a multiple valve. It gives good results because the rectifier is preceded by a fair degree of amplification.

In this circuit, the 100,000 ohms resistor is the rectifier load, and it is by-passed by a .0001 μ F condenser to allow proper rectification. The .05 μ F condenser couples the rectifier to the primary of the transformer, and is followed by a low-frequency amplifier in the usual way.

It is usual to wire the rectifier so that the positive end is connected to the I.F. transformer secondary (or tuning coil in the case of T.R.F. receivers).

In Fig. 2 a T.R.F. or "straight" circuit is shown.

The rectifier may be taken to a tapping on the tuning coil to lessen damping on the second tuned circuit. This is also possible with the circuit in Fig. 1, if a centre-tapped I.F. transformer is used.

Other parts of the circuit follow normal lines and other forms of coupling between H.F. and rectifier, and rectifier and L.F. stages, may be used.

Mains Rectification

Fig. 3 shows a circuit quite satisfactory where only moderate H.T. voltages are needed, such as in an H.T. battery eliminator. It may also be used for an all-mains receiver, the valve heaters being fed from a small transformer, or connected in series with a suitable dropper resistor.

The resistor in series with the smoothing choke (which should be capable of carrying the necessary current, and of 20 to 40 henrys inductance) is only needed when H.T. is being supplied to battery-operated valves. (The maximum anode voltage for these usually being

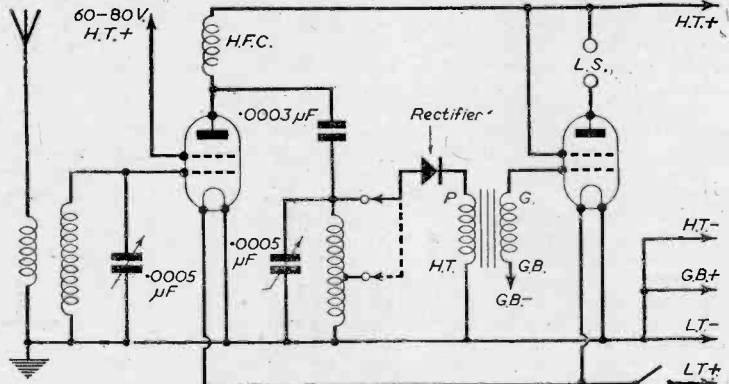


Fig. 2.—A "straight" circuit in which a metal rectifier is used in the detector stage.

150 volts.) If further low-voltage tapings are required, additional resistors may be wired as shown. The value may be determined from Ohm's Law, or from the following table:

Current Flowing	Voltage to Drop	Resistor Required
1 mA.	100	100,000 ohms
1 mA.	50	50,000 ohms
1 mA.	25	25,000 ohms
2 mA.	100	50,000 ohms
2 mA.	50	25,000 ohms
2 mA.	25	12,500 ohms
5 mA.	100	20,000 ohms
5 mA.	50	10,000 ohms
10 mA.	100	10,000 ohms
10 mA.	50	5,000 ohms
10 mA.	25	2,500 ohms

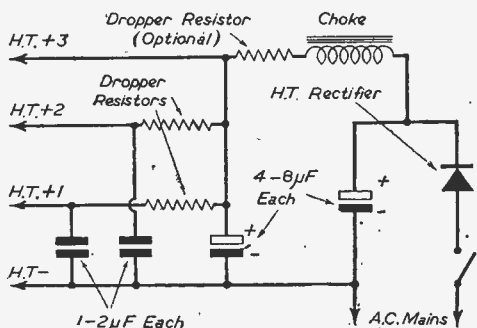


Fig. 3.—A simple H.T. Unit, in which a half-wave rectifier is used.

Voltage-doubling

Where higher voltages are required, the circuit shown in Fig. 4 may be used. It has the advantage over the circuit in Fig. 3 that H.T. minus is not connected directly to one mains lead.

The 4 µF condenser connected between H.T. plus and H.T. minus may be an electrolytic component. Note that both the other 4 µF condensers are not returned to H.T. minus, so that if metal-cased components are used they should not be bolted to a metal chassis unless the condenser casing is "dead."

Various rectifiers are available, depending upon the voltage and current required. The type H.T.16 will provide 300 volts at 60 mA., which is ample for most mains receivers.

Bias with H.F. Rectifiers

Sensitivity to weak signals may be increased by applying a small bias, as shown in

the simple circuit in Fig. 5. The polarity depends upon the way the rectifier is wired, and connections to the battery may be reversed to obtain the desired result. The best voltage should be found by trial.

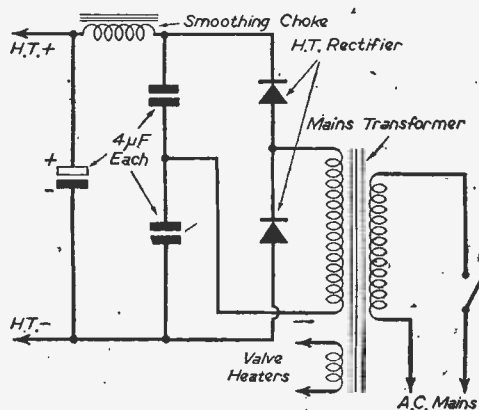


Fig. 4.—In this mains unit, two half-wave rectifiers are connected to provide full-wave rectification.

For use in a receiver with little or no H.F. amplification the type WX6 is most suitable. Where the rectified current may exceed .12 mA type W6 may be used, the maximum rectified current for this component being .28 mA. Because of this type W6 is used in receivers with more than two stages of pre-detector amplification.

For A.V.C.

A portion of the signal may be rectified to provide A.V.C., as shown in Fig. 6. Here it is important the rectifier be connected in the correct polarity so that a negative bias is obtained. The bias

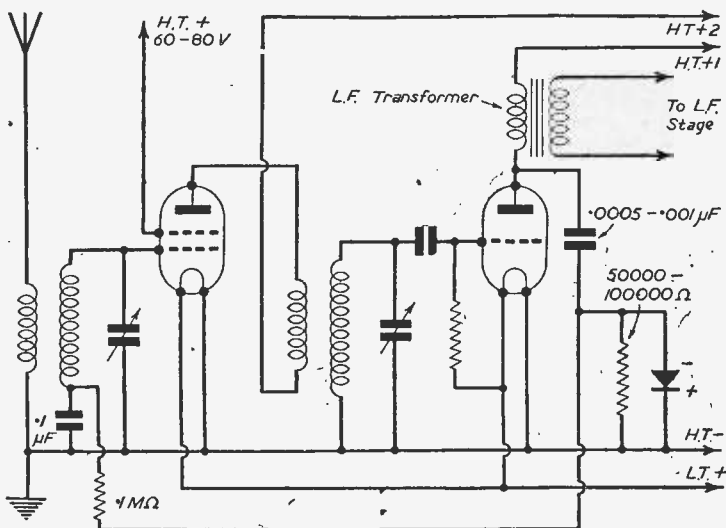


Fig. 6.—In this circuit a voltage for A.V.C. purposes is obtained from a half-wave rectifier.

is developed across the 100,000 ohms resistor and by varying the value of this, and the capacity of the associated fixed condenser, some control over the A.V.C. action is possible.

The degree of control will not be large with only one H.F. stage, but the same circuit may be used with superhets, or straight receivers where two or more valves may be controlled. As will be seen, the necessary addition may be made to an existing receiver quite simply.

Each controlled H.F. stage should, of course, be decoupled as shown by a $.1 \mu\text{F}$ condenser and a $.1 \text{ M}\Omega$ resistor.

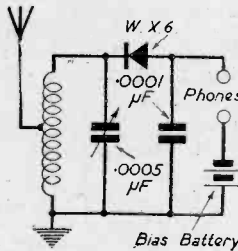


Fig. 5.—A simple receiver circuit in which an H.F. metal rectifier takes the place of the usual crystal detector.

Radio Communication for Aircraft

IN anticipation of legislation regarding "communication facilities" in civil aircraft, E. K. Cole, Limited, have developed a complete twin-channel ground and air installation which meets the recommendations of the International Civil Aviation Organisation now in course of implementation by the Ministry of Civil Aviation. Many owner pilots, flying clubs and aerodrome operators have been waiting for just such equipment as Ekco now offer.

The company promise delivery in approximately three months from the date of order, and their own engineering department will undertake the initial installation. A complete and immediate service of replacements has been planned at the Ekco Works, Southend-on-Sea. The company are organising a nation-wide coverage for installation and maintenance which aims to provide air charter companies, flying clubs and aerodrome operators, wherever they may be located, with the personal attention of E. K. Cole engineers. All orders and enquiries will be handled by the Radio Sales Division, Aircraft Radio Section, Southend-on-Sea.

In marketing this new equipment, E. K. Cole, Limited, are prepared to extend a full and detailed advisory service to all enquirers, and their organisation assures that users of the equipment will at all times have behind them the immediate and ready assistance of the manufacturers in maintaining their installation at full efficiency.

Complete Equipment

The Ekco Aircraft Communication Equipment consists of:—

(1) Crystal controlled twin channel aircraft transmitter-receivers of the V.H.F. type, with selector switch control, weighing approximately 12 lbs.

(2) An aerodrome installation comprising two transmitters and two high gain receivers covering, for example, the Universal Guard frequency, and the frequency of the local aerodrome, or any two frequencies in the 118/128 megacycles V.H.F. band.

Ekco have also developed, in conjunction with the Communication Equipment, a complete D.F. installation which can be immediately and automatically tuned to the frequencies on which the main transmitters and receivers are working.

Aircraft Equipment

The equipment is a lightweight Transmitter/Receiver, suitable for installation in private and club-type aircraft. It is self-contained and operates from a 12 volt battery (other voltages can be covered if required), and has a power consumption of 3.75 amps at 12 volts.

Provision has been made for transmitting and receiving on two crystal controlled frequencies, one of which would normally be set to the Civil Aviation Guard frequency of 118.1 Mc/s, whilst the other would usually be set to the frequency allotted to the local aerodrome from which the aircraft operates and within the band 118-128 Mc/s.

Circuit

The set contains sixteen valves, plus rectifier and is divided into two crystal multiplier chains, two R.F. and frequency changing chains, and a common I.F., detector, L.F. and modulator chain.

Controls

The two frequencies are pre-set and crystal controlled and the only manual controls necessary are:

- Channel frequency selection switch.
- Send/Receive switch.
- On/Off switch.

making for extreme ease of operation.


The above switches are all mounted in the small Control Unit, which can be installed on the dashboard or any other convenient position.

Provision is made for the use of two sets of microphone and headphone attachments from the Junction Box.

The Junction Box is fitted with an additional supply socket to enable overriding transmitter switch operation, and this may be used as remote control by either pilot or passenger.

WATCH YOUR DUSTBIN

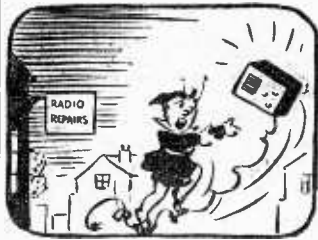Waste Paper, Cartons, Cardboard should be kept separate, dry and clean for salvage.



The "Fluxite Quins" at Work.
"That's the tenth we've mended to-day,
Now Ol, be off on your way.
Come on, show some speed!
Look out! Mind the lead!...."
"More FLUXITE needed" bawled EH.

See that FLUXITE is always by you—in the house—garage — workshop — wherever speedy soldering is needed. Used for over 40 years in government works and by the leading engineers and manufacturers. Of all iron mongers—in tins, 10d., 1/6 and 3/-.

To CYCLISTS: For stronger wheels that will remain round and true, there's a time tested tip. Tie the spokes where they cross with fine wire and SOLDER. It's simple — with FLUXITE — but IMPORTANT.

The FLUXITE GUN puts FLUXITE where you want it by a simple pressure. Price 1/6, or filled, 2/6.



ALL MECHANICS WILL HAVE
FLUXITE
IT SIMPLIFIES ALL SOLDERING

Write for Book on the ART OF "SOFT" SOLDERING and for leaflets on CASE-HARDENING STEEL and TEMPERING TOOLS with FLUXITE, also on "WIPED JOINTS." Price 1d. EACH.

FLUXITE LTD. (DEPT. W.P.), BERMONDSEY ST., S.E.1.

SPARKS' DATA SHEETS

Provide detailed Instructions with Clear, Full-size Assembly Plans of TESTED AND GUARANTEED DESIGNS.

- THE "POCKET PAK." An All-dry 1 Valve Med. Wave Portable. ... 2/9
- THE "JUNIOR." 1 Valve All-dry M/L Compact Set. Fine range on short aerial. Safe any area. 2/6
- THE "TINY TWO." 2 Valve Portable. Med. waves. Speaker results on "Local" Stations. Widely used. 2/6
- THE "ALL-DRY LO'S PORTABLE." 3 Valves. M/L waves. Good Speaker results on "Locals." Very Popular. 2/6
- THE "CRUISER." 3 Valve All-dry T.R.F. Set. M/L waves on short aerial. 2/6
- THE "CHALLENGER." An exceptional A.C./D.C. M/L wave Portable. Praised by all. First-class results. 2/9
- THE "CONQUEST." A.C./D.C. Superhet. All-wave. P.U. 4 watts Output. 2/9

MANY OTHER DESIGNS. SPARKS' DATA SHEETS cover Portables, Midgets, R/Grams, Amplifiers, etc. etc., for Mains and Battery. Send Stamp for Latest List. Components Supplied.

"YOU ARE SURE OF A SQUARE DEAL FROM SPARKS."

L. ORMOND SPARKS (P),
9, Phoebe Road,
Brockley, S.E.4
(Phone : Lee Green 0220.)

INDUSTRIAL FINISHING

CRACKLE STOVE ENAMEL ALL COLOURS

Stoving ovens and spray service at your disposal. Prompt return after final inspection. Chassis, Panels, Cabinets, Photographic equipment, etc.
Black 1/- . Colours 1/3 per sq. ft. Carriage extra. Special quantity quotations. We make anything in metal to your requirements.
Buccleuch Radio Manufacturers
6 Wheatfield St., Edinburgh, 11
'Grams : "Therm." Phone 64596

COLD WEATHER NEWS!


Fresh supplies of the thermostatic switch which has proved so successful in frost warning and control circuits are now in stock.

THERMOSTATIC SWITCH

makes contact at approx. 35 deg. F. (with adjusting screw to vary up to 90 deg. F.). Q.M.B. action, up to 3 amps. 250 v. A.C. Circuit diagrams and directions sent with each switch. 3/6 each, 37/6 per doz., post free.
A. McMILLAN, 5, Oakfield Road, Bristol, 8.



Meters

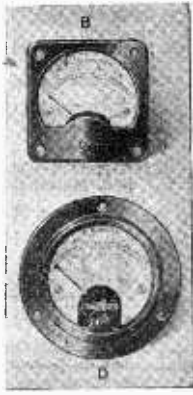

NEW and BOXED ..

MOVING COIL type 'B'

- 0/5 mA. D.C.....5/9 each.
- 0/5 amp. R.F.....5/9 each.

Four of the above meters :
(2 of 0/5 mA. and 2 of 0/5 R.F.) 21/-
0/150 mA. D.C.....6/6 each.

MOVING IRON type 'D'

- 0/20 volts A.C./D.C.....8/6
- 0/15 volts A.C./D.C.....8/6

I. F. TRANSFORMERS

WEBB'S 465 Kcls.
A new line, offering a highly efficient transformer ("Q" = 140) at a reasonable price. 3 1/2 in. high by 1 1/2 in. square. Price each 6/- Per pair 11/9

Please add 1/-d. postage and packing on all post orders.

WEBB'S RADIO, 14, SOHO ST. OXFORD ST., LONDON, W.1

Note our SHOP HOURS: 9 a.m. to 5.30 p.m. Sats. 9 a.m. to 1 p.m.

Telephone: GERrard 2089

QUALIFY FOR A BETTER POST

—BY POST!

Let the most progressive, most successful College in the world coach you by correspondence. Choose your career or be advised by us. We take a personal interest in all our students and provide the friendly individual training that quickly leads to success. Make the first move NOW—write for free particulars.

CHOOSE YOUR CAREER NOW

Blue Prints.
Book-keeping, Accountancy
and Modern Business
Methods.
Building, Architecture and
Clerk of Works.
Cambridge Senior School
Certificate.
Carpentry and Joinery.
Civil Engineering.
All Commercial subjects.
Television.
Shorthand (Pitman's).
Telecommunications (City
and Guilds).

Draughtsmanship, all
Branches.
Heating and Ventilating.
Radio Service Engineering.
Languages.
Mathematics.
Matriculation.
Municipal & County
Engineers.
Plastics.
Wireless Telegraphy and
Telephony.
Structural Engineering.
Surveying.
Teachers of Handicrafts.

If you do not see your own requirements above, write to us on any subject. Full particulars free.

Direct Mail to Dept. 104

The
Bennett College
SHEFFIELD



ALLEN AND GOULD

NEW BOXED VALVES: 6B8C, 4/9, 6SH7 4/6, 7193 3/6, 6H6 2/6, 6K7G 8/6, 6Q7G 8/-, 6F6 9/-, 6G6G 8/2, EF50 (VR91) 6/6. FERRANTI push-pull input transformer with split secondary, 11/6.

LARGEST stock of speakers in South London, including Rola, Celestion, Goodmans, Plessey, R. and A., Elac, etc., at lowest prices.

COLLARO gram. motor and pick-up with auto stop and start. £5/14/6 complete.

WIDE RANGE of components and valves in stock for the Home Built Television. Mains transformer £3/15/-, EHT transformer £3/5/0, line transformer 27/6, scanning coils 30/-, focus coil 32/6, complete set of coils and chokes 18/6, sound chassis 9/6, vision 10/6, time base 14/6, valves, EF50 6/6, T41 12/10, pen 45 12/10, pen 46 18/3, EL33 12/7, EBC33 11/5, U6s 18/3, HVR2A 24/4.
SELENIUM rectifiers. 230v. 50 ma. 3/11. 60 ma choke 5/-.

Please include postage.

ALLEN AND GOULD.
5, Obelisk Parade, Lewisham, S.E.13 (opposite Gaumont Cinema). Telephone: LEE GREEN 4038.

H.A.C.

Short-Wave Equipment

Noted for over 15 years for

Short-Wave Receivers and Kits of quality

One Valve Kit, Model "C" ..	Price 20/-
Two " " " " "E" ..	" 43/-

These kits are complete with all components, accessories, and full instructions. Before ordering send stamped, addressed envelope for descriptive catalogue.

Note new sole address:—

"H.A.C." SHORT-WAVE PRODUCTS

(Dept. TH) 66 New Bond Street, London, W.1

LASKY'S RADIO

Brand New in Maker's Wood Transit Case
EX. A.M. FREQUENCY/METER TYPE
W1181

Frequency range, 100 kc/s to 20 mc/s, in 8 switched bands covering all intermediate frequencies.

Utilises 4 valves and 100 kc/s. crystal. Unit contained in smart grey enamel case complete with hinged lid and web carrying strap. Battery operated L.T., 2 volts. H.T. 60 volts. Each unit is supplied complete with calibration chart and working instructions. This meter is accurate to 0.1 per cent. and with crystal control, 0.01 per cent.
LASKY'S PRICE £5/19/6, COMPLETE.
Carriage in crate, 10/- extra.
Spare kit of matched valves, 20/- extra.

SPEAKER SPECIALS

All P.M., Moving Coil, 3 ohm Speech Coil. With output transformers.
6in. Rola, 13/6; 9in. Plessey, 16/6; 8in. R.A., 17/6; 8in. Celestion, 21/-; 10in. Plessey, 25/-; 10in. Goodmans, 27/6.
Postage 1/- per speaker extra.

VALVE SETS


5 Brand new guaranteed valves as follows:
6K8C, 6K7G, 6Q7G, 6V6G, 6Z4G.
LASKY'S PRICE, 35/- THE SET. Post 1/- extra.

AERIAL RODS

The sectional type, as used in the Walkie Talkie Mk. 58. Each rod is steel heavily copper plated, sprayed khaki. Length 14in. Any number of rods can be fitted together. LASKY'S PRICE, 3/- per doz., post free.
A 2d. stamp will bring you our bulletin by return. Name and address in block letters please. Why not pay us a visit? Our staff will be only too pleased to help you with your queries. We carry a comprehensive stock of valves and other components for the experimenter service man, and amateur. No order too late or too small that we will not give our full attention to.

LASKY'S RADIO

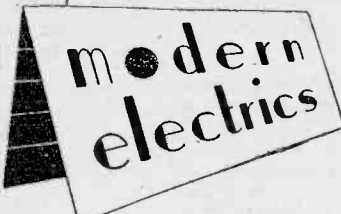370, Harrow Road, Paddington, London, W.9.
(opposite Paddington Hospital)
Telephone: CUNNINGHAM 1979.
Hours: Mon. to Sat., 9.30 a.m. to 6 p.m.
Thursday, Half Day.



SPECIAL OFFER.—Universal Avomnior, £7/10/- D.C. Avomnior, £3/15/- New. Boxed, Guaranteed. All other Av instruments available ex-stock, including new Electronic Meter at £35.

TAYLOR TEST EQUIPMENT.—The entire range of test equipment by this famous maker is now available on hire purchase. S.F.E. for catalogue and terms.

P.A.C. RADIOMETERS.—0-6v. and 0-240v. A.C./D.C. 25/-

STROBOSCOPES.—Single-speed, 78 r.p.m., 50 cycles, 6d. each (8d. post free).

GRAM MOTORS.—Collaro A.C. motor and 12in. plate, less Pick-up, £5/18/4; Collaro A.C./D.C. motor and 12in. plate, less Pick-up, £5/5/-; Collaro A.C. motor and 12in. plate with Pick-up and Auto-stop, £9/13/6; Collaro A.C./D.C. motor and 12in. plate with Pick-up and Auto-stop, £12/18/10; Garrard A.C. "S" unit, including Pick-up and Auto-stop, £5/19/3. Auto-changers by "Collaro," "Garrard," "Plessey." Let us have your requirements.

SOLOID SOLDERING - IRONS. — 65w., straight bit, reduced to 18/6; 65w., pencil bit, 21/-.

TELEVISION MAGNIFYING LENS.—All sizes, £6/16/6. State size of tube or make of television.

Under 20/- C.W.O. only. C.O.D. or C.W.O. over 20/-. When ordering C.W.O. please allow sufficient for postage and packing.

MODERN ELECTRICS LTD.

164 Charing Cross Road, London, W.C.2
Tel: TEMple Bar 7587.

MIDLAND INSTRUMENT CO.

Brand New Govt. Surplus Stock.
Electric Time Clocks, run for over one year from a 3v. cycle battery, 44-day and 2-hour setting, also sec. hand. Exceptionally fine jewelled movement, size 3 1/2 in. dia., by 3 1/2 in., brand new, boxed, 25/-, post 9d. Mains Transformers, input 230v., output 50v. 11 amp, 25/-, carr. 6/-, Interphone Amplifiers, P.C.-212-D., complete with two 6C5 valves, input and output transformers, switch, etc., in smart metal cases, 5in. x 4 1/2 in. x 2 1/2 in., operates from 6v. or 12v. L.T., 220-230v. or 350v. H.T., with circuit, 20/-, post 9d. Magnetic Compasses, Type P-8, alcohol fluxgate, engraved 360 deg., luminous cross-wires, in wood carrying cases, 10/-, post 1/-. Motors, fitted overload clutch and 4ft. flexible drive, 24v. A.C./D.C. 1 h.p., exceptional offer, 20/-, post 1/4. Electric Pumps, centrifugal self-priming type, suitable for water supply, garden fountains, bilge pumps, etc., two models, 12v. or 24v. A.C./D.C. 25/-, post 1/4. Walkie Talkie Aeriums, copper, collapsible, 9 sections, 7 1/2 in. long, 1 1/2 in. diam., taper to 3/32 in., also makes good fishing rod, 2/6, post 6d. Dimmer Switches, variable wire-wound resistors, with "off" position, in bakelite cases, 1/-, post 4d. Enam. Copper Wire, 33 s.w.g., 15 oz. reels, 2/6, post 9d. Browns 4,000 ohm headphones, web headband 5/-, post 9d. Moving Coil headphones, with moving coil microphone, fitted switch, 10/-, post 9d. Headphone leads, fitted high or low impedance transformer matching unit, switch adjustment, 2/6, post 6d. Telephone Sets, consist of two combined mikes and 'phones, 25ft. twin connecting wire, giving perfect two-way communication, self-energised, no battery required, set complete, 7/6, post 9d. Burgess Micro Switches, make and break, 1/6, post 3d. Terminal Strips, contain 28 plated brass terminals on bakelite strip, 1/6, post 11d.

Send for our new Jan./Feb. lists now available, 2d. with s.f.e. Order, over 30/- paid, orders too heavy for post, carriage extra in all cases. Our C.O.D. service is cancelled for the time being.

Moorpool Circle, Birmingham, 17.

Tel.: HARborne 1308 or 2664.

Programme Pointers

In This Month's Article MAURICE REEVE Looks at Television, the Symphony Concerts and the Brains Trust

MUCH ink is spilled and breath used up in telling of what is wrong with wireless, the films, art, and, in fact, the world in general. A thinks it is this and B that, whilst C is certain he knows the remedy. But radio was so quick to solidify into its present conglomerate mass—quicker, even, than the films, from which it derived so much that was both good and bad—that, like the body politic itself, change must in the nature of things be slow.

A point of similarity, with a difference, that I seldom see mentioned is one which, I think, contains the gravamen of the problem, to wit, that whereas both cinema and radio quickly made themselves non-stop shows covering many hours, the radio cannot keep repeating itself like its sister amusement does. Where a film show is practically always good or always bad, four times a day, according to the programmes being shown, the wireless is constantly alternating from the sublime to the ridiculous, and midway between, for short snippets of time the whole clock round, said snippets being chucked at us from all points of the compass.

No wonder much of it is bad, or, to put it more mildly, stupid, inane, mildly amusing or mildly instructive, as the case may be. And so long as it remains a twenty-four hour a day service, which, I suppose, will be for ever, so long must we expect a service which never seems quite so good as it might be. I do not think it was ever meant to be such, and the result is what it was bound to be: best summed up in the classic story of the housewife who "always turns the wireless on but seldom listens to it."

I am sure the quality of both programmes and listening would go up if we hadn't quite so much of a good thing. The fact seems to remain: that, in spite of the inclusion of the present host of outside broadcasts, the broadcasting of films, church services, darts matches, repetitions, etc. etc., there is still not nearly enough first-class material to see the day through. Also, certain regular features like Music Hall and the Brains Trust, have sadly deteriorated. Ought, therefore, the B.B.C. to decide, even if regretfully, that in the interests of the quality of their programmes, they intend to sacrifice quantity and limit the number of broadcasting hours. Or should they, in fact, preach *laissez faire* and say, "We'll give you all of the best that's going, and if you don't like the rest, then we're afraid we can do nowt abaht, it!" To expect two programmes, each of about eighteen hours' length, with a third of about six hours, plus the rest of the world, everlastingly packed with first-class material whenever we turn the knob is, of course, to ask for the impossible.

Television in the Future

Surprising things happen in the course of evolution: things never intended at the commencement and not wanted in development. But when they

are quick to take root, as the cinema and the wireless, they willy nilly become our masters. So who knows whether, during the next generation, the perfect television system may not solve everyone's troubles. By combining perfect listening with perfect vision, television could, at one blow, kill either the cinema or the wireless. If it became the public entertainment of the future, room would be made for the restoration, with modern improvements, of the better features of the old family life which set up such nostalgic memories in the breasts of those who remember them. Whilst, should it supersede wireless in the home, it would probably leave the theatre and the concert free to regain their pristine glories, which the film and the radio so gravely damaged. In fact, everything in the garden may be perfect, with only an atom bomb to guard against.

The Symphony Concerts

Of the three B.B.C. symphony concerts from the Albert Hall, conducted by Barbirolli, Beecham and Kubelik respectively, I preferred Beecham's. The orchestra always seems to play with just that little bit more intensity and snap for Sir Thomas than for most others. His Sibelius No. 7 and Delius's "Song of the High Hills" were magnificent, whilst Tortellier, in Dvorak's gorgeous cello concerto, beautifully accompanied, proved him only a little behind the irreplaceable Casals. Kubelik's Ninth Schubert was fiery virtuosity, but though the great music swept on with ever-increasing surge, there was not quite the cohesion and balance of the former concert. The Italian violinist, Gioconda de Vito—a name to conjure with in its own right, if ever there was one—played Mozart superbly, but with abominable cadenzas. The applause savoured of the Highbury Stadium and the winning Arsenal goal. Barbirolli's Fourth Brahms was a noble effort, and he also revealed the likeable brilliance of Bartok's Concerto for orchestra to an extraordinary degree.

There was some lovely eighteenth century chamber music on the Third by Pergolesi, Gluck, and others, given by the London Harpsichord Society—the third of six programmes. I also liked the Trout Quintet by the Bayrilli combination, plus the irrepressible Peter Stadlen.

Brains Trust

I cannot quite agree with my *Radio Times* colleague *apropos* the Brains Trust. In the issue of November 25 he says that "after a disappointing start, they have settled down and, in doing so, have mellowed." I presume he is complimenting them, and that is why I differ. As, later in his article, he also says "... I was astonished last week to hear him (the chairman) rap out the precise opposite to the jury's verdict on a question regarding the purchase of clothes," one wonders what they are exactly meant to be these days. To

me they have become extremely stuffy, boring and dull, completely lacking their former wit and sparkle, and, for the most part, discussing fatuous and naïve questions.

In this repetitious age, the making of broadcast dramas from film sound tracks had to come. As they are usually and understandably the good films which are thus treated, it is an odd pastime to listen for an hour to a film which you have either already seen at your local celluloid tabernacle, or thoroughly intend to in the very near future. Films without the films, Betty Grable minus Betty Grable! If a lot of opening and shutting of doors and commentary in place of visual action can create any excitement comparable to the real thing, then "Call Northside 777" was very good, and just the right type of film which can be divorced from its better half without undue grief or shedding of tears. With all respect to the excellent Mr. James Stewart, none of the scenery was vitally missed. It made a good number for Picture

Parade. But I saw the film and found it vastly superior in tenseness and realism.

After the weekly reminder, December 11, that "Music Hall" is rapidly becoming one of the most banal and hackneyed of features, Saturday Night Theatre presented a powerful stimulus to one's dormant brain with R. and M. Pertwee's "The Paragon," adapted for radio by M. Pertwee. The story, not everyone's meat, of how a dotting father is going to honour the memory of his worthless son, announced killed in the war, until the son turns up, a deserter and blackmailer, was well played by all, and dramatically produced by Archie Campbell. Edward Chapman was particularly good as the blind father, and his change of mood from silent worship (he intends spending half a million pounds on memorials to his memory) to a full realisation of having been deceived by an utter and complete cad, was convincingly portrayed. We also felt the inherent cowardliness and worthlessness of the son, by Hugh Burden.

News from the Clubs

LOTHIANS RADIO SOCIETY

Hon. Sec. : I. Mackenzie, 41, Easter Drylaw Drive, Edinburgh. THE next regular monthly meeting will be on February 24th, 7.30 p.m., at the Chamber of Commerce Rooms, Charlotte Square, Edinburgh.

Mr. W. R. Hadie (GM440) will deliver a lecture. Subject: "Aerial Theory and Practice, with particular application to Multi-Element V.H.F. Beams."

READING AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec. : L. Watts, G6WO, 817, Oxford Road, Reading.

THERE was only one meeting of the society during the month of December. The programme at this meeting consisted of a Brains Trust.

On February 12th, Mr. J. Dee, G3BJE, will give a talk on oscilloscopes.

THE WEST MIDDLESEX AMATEUR RADIO CLUB

Hon. Sec. : C. Alabaster, 34, Lothian Avenue, Hayes, Middlesex.

THE club continues to be very much alive in all aspects of radio and electronics. Recent meetings were concerned with the electron microscope, the strobolash, a junk sale and lectures on interference, the latter being particularly timely in view of the new Wireless Telegraphy Bill.

The future programme includes lectures on valves, amplifiers and V.H.F. equipment.

Meetings are held on the second and fourth Wednesdays of every month at the Labour Hall, Uxbridge Road, Southall, Middlesex, at 7.30 p.m.

STOURBRIDGE AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec. : W. A. Higgins, 35, John Street, Brierley Hill, Staffs.

A MEETING of the above society was held at King Edward's School, Stourbridge, on Tuesday, December 7th, 1948. Mr. B. Whitehouse (G6WP) was in the chair. Following general business, in which the secretary gave details of future meetings, Mr. K. H. Varney (G3IMV), of G.E.C., Ltd., gave a most interesting talk on the "Photo Electric Cell and its Application in Industry." The talk was illustrated with lantern slides and a display of apparatus. Members were shown how the photo cell was used for burglar alarms, counting and sorting, automatic door and gate opening, and testing smoke density. Mr. Varney was accorded a hearty vote of thanks for an excellent talk. Further particulars may be obtained from the secretary.

ROMFORD AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec. : D. Coppedale (G3BNI), 9, Morden Road, Chadwell Heath, Essex.

AFTER 12 years as secretary to the Romford and District Amateur Radio Society, G3FT, his wife and family have left for Canada, complete with 10-metre transmitter, and hope to be working back to local "Gs" in the near future.

The position of secretary has been taken over by G3BNI, to whom all matters concerning the R.A.D.A.R.S. should be addressed.

Two nights a week are devoted now to radio—Tuesday, normal radio lectures, demonstrations, junk sales, etc., whilst Wednesday nights one can learn about television. The Wednesday evening meeting is proving very successful and shortly it is hoped to have a TV of our own.

NOTTINGHAM SHORT WAVE CLUB

Hon. Sec. : N. W. Adcock, "Bryn-Gates," Harlaxton Drive, Long Eaton, Nottingham.

THE club now has a new secretary as above, and new premises have been found owing to increased membership. Meetings are held every Monday evening at 7.15 p.m. at "The Old Boys' Club," Middle Street, Beeston, Notts. The club Tx, G3EKW, was officially opened on Monday, December 6th, by Mr. F. R. Sharp, Radio Editor of the *Nottingham Evening Post*. The Tx is situated at Chilwell, Notts, and is active at present [on 1-7 Mc/s only. New members are always sure of a welcome, either personally or by contacting the secretary. Morse tuition is available as well as technical theory and practice in relation to the A.R.E.

SOLIHULL AMATEUR RADIO SOCIETY

Hon. Sec. : G. Flaving, 121, Bradbury Road, Olton, Birmingham.

THE A.G.M. of this society was held on January 12th, and marked the election of new officers, these being: Hon. sec., G. Flaving, G3EQL; hon. treas., J. Tucker, G5TU; pres.: M. Filgate, and a committee of five.

The programme committee outlined their future programme, which began on January 26th with a lecture on radar by Mr. Smith, G6EK.

Future lectures include "V.H.F.," by G5BJ, "The Radio Valve," by G5TU, and many more by members of the society. It is hoped in the future to deal more with the constructional side, as younger members have suggested. Meetings are held on alternate Wednesdays at 7.30 p.m. at the Manor House, High Street, Solihull, and visitors and new members will be welcomed.

DERBY AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec. : F. C. Ward, G2UVV, 5, Uplands Avenue, Littleover, Derby.

THE society's first annual dinner and social will be held on Wednesday, February 9th, at the Grandstand Hotel, Racecourse, Nottingham Road, Derby.

Future meetings will be held on February 2nd and 16th respectively in the Club Room, 67b, London Road, Derby.

THE HOUNSLOW AND DISTRICT RADIO SOCIETY

Hon. Sec. : A. Pottle, B.Sc., 11, Abinger Gardens, Isleworth, Middlesex.

PLANS for 1949 were fully discussed at a recent meeting. Future activities will be concentrated upon transmitting, receiving and television. The society's transmitter has now been completed and will operate under the call sign G3FHD. Prospective members should contact Mr. A. Pottle, whose address is given above.

TELEVISION

Why not make
your own?

"THE HOME BUILT TELEVISOR"
Book of instructions, wiring diagram and full list of parts 6/6 post free.
Full scale blueprints shortly available.

UNITS SUPPLIED READY WIRED
E.H.T TRANSFORMERS: £3.7.6
FOCUS COILS. £1.17.6
LINE TRANS. £2.2.0
SCANNING COILS. £1.12.8
9" WHITE MASKS. 12.0
12" WHITE MASKS. £10.0.0

Send now to:-

TELERADIO.
157, Fore St.,
Edmonton, N.18.
Phone: TOT 3386.

THE LEADING KIT SUPPLIERS

COVENTRY RADIO

Dunstable Road, Luton, Beds.

New 1st. Grade Components


8 mfd., 450 volt Condensers, metal electrolytic, 3/-; 16 mfd. ditto, 3/9; 8-8 mfd. ditto, 4/9; 25 mfd., 25 volt Condensers, tubular electrolytic, 1/6. Mains Transformers, 275-0-275 v., 80 m.a., 6/3 v., 5v., 19/6; 350-0-350 v., 120 m.a., 6/3 v., 5v., 25/6. I.C. Chokes, standard 75 m.a., 4/8. Metal Rectifiers, 240 volt, 45 m.a., half wave, 4/6. Resistors, best make, 1 watt, kit, 100 assorted, 10/6. Condensers, tubular and mica 12/6. Oak Switches, 4-way, 6-wafer, 8in. long, 2/-.
Send for 1949 list, 6d. post paid. For Express Service, phone: Luton 2877.

RADIOELECTRON

22, Frances Street, Scunthorpe, Lines.
New Goods Only. No W.D. Surplus.
CONDENSERS, B.I. Electrolytic, also Duplicator and T.C.C., all as January issue of E.W. Tub, up to .0005, 7/-; up to .005, 8/4; up to .1, 11/-; 1 mfd., 2/2; Tuning, small, 1 gang, 4/3; 2-gang, 11/-; 2-gang with Ts., 12/-. All .0005 mfd.
RESISTORS, Carbon 1 watt, 40s; 1 watt, 7d.; Wire Wound 1 watt, 1/-; 5 watt, 1/6; 20 watt, 3/-; Mains Droppers, 2A, 4/4; 3A, 4/11.
VOLUME CONTROLS, Lr. Spdls., 3/3; with Sw., 5/-; Wire Wound, less Sw., 5/-.
TRANSFORMERS, Output, Pow/Pen., 5/8; Multiratio Universal, 7/3; Intervalve Dir. Feed, 3 or 5/1 ratio, 6/-; Class B driver, 7/-; Q.P.F. driver, 8/6; Para. Feed Intervalve, 5/-; Mains, shrouded, interleaved and impregnated, for 200-250 v. mains, 4 v. or 6.3 v. and 5 v. L.T.s 250 v. 100 m/a; 350 v. 100 m/a, 29/6.
TUBS RADIOMETERS, 25/-.
Terms: Cash with order, Orders over 10/-, post free, under 40/- C.O.D. extra 2/4. stamp will bring you copy of our list

2 AMAZING OFFERS!

IDEAL FOR CRYSTAL SETS, VALVE SETS, HOSPITALS ETC
EX-ARMY HEADPHONES BRAND NEW AND BOXED
Post Free 5/6
Per Pair
Two Pairs 10/-
Lots of 100 3/-
Per Pair (over extra)



PRECISION MADE INSTRUMENTS, BALANCED ARMATURE UNITS, REED DRIVEN CORRUGATED ALUMINIUM DIAPHRAGMS, DOUBLE HEADBANDS, 8ft. CORDS and PLUG, D.C. RESISTANCE 80 ohms. High Impedance. They are worth about 42/- per pair.

Fractional H.P. ex-R.A.F. ELECTRIC MOTORS, 1/4 H.P. BRAND NEW, made by Hoovers. ONLY 37/6 each. Plus 2/6 carr.



NOT TO BE CONFUSED WITH SMALLER AND CHEAPER TYPES. Size 1 1/2" x 5 1/4" x 5 1/4". Weight 18lbs. Volts 200/250 A.C., 2,000 r.p.m.
IDEAL FOR PERIPEX POLISHING, GRINDERS, BUFFING, Etc. Converted by us from Rotary Transformers (Input 24 v. D.C. and Output 1,200 v., 200 mA and supplied as such at 35/- if preferred). These Mains Motors are worth treble and have a dozen uses. Existing Spindle is 1/4" diam., 1/4" long. All-purpose Extn. Spindles, to screw on, 7/6 pair extra.

AUTO COLLECTIONS LTD., 15, LAWRENCE ST., Northampton. Send 1d. S.A.E. for our Radio/Electric List.

A FREE BOOK on Morse Code Training



There are Candler Morse Code Courses for Beginners and Operators.

Send for this Free "BOOK OF FACTS" It gives full details concerning all Courses.

THE CANDLER SYSTEM CO. (G.L.Q.)
121, Kingsway, London, W.C.2
Candler System Co., Denver, Colorado, U.S.A.

WE OFFER

A large range of used and new Test Equipment, Converters, Recorders, Amplifiers, Motors, Transformers, etc.
All guaranteed and at very attractive prices.

We buy good modern used equipment of all types for spot cash.

UNIVERSITY RADIO LTD.
22 LISLE STREET, LONDON, W.C.2
Tel.: GER 4447 and GER 8582

ALEC DAVIS SUPPLIES LTD.

18, Tottenham Court Road, London, W.1. Tel. MUS. 4339 and MUS. 2453

Special Offer of SURPLUS Valves

All tested and fully guaranteed. Postage and special packing 9d. per valve and 2d. for each additional valve.

- EF50 —R.F. Pentode ... 6/-
(Or special offer of 10 for 50/-)
- EA50 —6.3 volt Diode ... 4/-
- D1 —4 volt Diode ... 3/6
- 65L7 —Twin Triode ... 9/6
- 65N7 —Twin Triode ... 9/6
- VR105/30 —Stabiliser ... 7/6
- 65K7 —Variable Mu ... 6/6
- 6H6 —Double Diode ... 2/6
- 65H7 —R.F. Pentode ... 4/6
- KT44 —Tel. Pentode ... 7/6
- 6B4 —Output Triode ... 8/6
- 6J5 —General Purpose Triode ... 4/6
- DET20 —VHF Triode ... 3/6
- 1T4 —1.4 volt R.F. Pentode ... 7/6
- 6AC7 —Telesvisor Pentode... 6/-
- 5P61 —R.F. Pentode ... 3/-
- 2X2 —H.V. Rectifier 4 1/2 kv. 7 1/2 mA. 2.5 volt 1 1/2 amp. Heater ... 7/6
- 35T —Transmitting Triode, 70 watt dissipation, 5 volt 4 amp. Heater ... 35/-

INSTRUMENT WIRE

Enamelled, Tinned Copper, Cotton Covered, and Silk Covered.
ENAMELLED, 16, 17, 18, 19, 20 swg., 1/6 per 1 lb. reel, 21, 22 swg., 1/9 1/2 lb., 23, 24 swg. 2/- 1 lb., 25, 26 swg. 2/8 1 lb., 27, 28 3/3 1 lb., 29, 30, 3/4 1 lb., 32, 2/6 1 lb., 34, 3/6 1 lb., 36, 3/- 1 lb., 39, 3/4 1 lb., 40, 3/9 1 lb., 41, 2/3 2 ozs., 42, 2/6 2 ozs. 2-oz. reels half above + 3d.
COTTON COVERED, 16, 17 swg., 2/6 1 lb., 18, 19, 1/6 1 lb., 20, 1/8 1 lb., 21, 22 1/10 1 lb., 23, 24, 2/- 1 lb., 25, 26, 2/3 1 lb., 27, 28, 2/6 1 lb., 30, 2/9 1 lb., 32, 3/- 1 lb., 34, 3/6 1 lb., 36, 4/3 1 lb. (Please add 3d. towards postage)
MANY OTHER SIZES IN STOCK. Send S.A.E. for full range. (Trade enquiries welcomed.)
SPECIAL OFFER. (High Resistance) HEADPHONES with adjustable headband and plated holders for ears. Splendid value at 12/6 per pair. Send for yours now, while stocks last.
LATEST RADIO AND TELEVISION BOOKS. Send S.A.E. for details.
MORTONS, 13, CAMDEN ROAD, WALTAMSTOW, LONDON, E.17.

TELEVISION

The advance in Radio Technique will offer unlimited opportunities of high pay and secure posts for those Radio Engineers who have had the foresight to become technically qualified. How you can do this quickly and easily in your spare time is fully explained in our unique handbook.
Full details are given of A.M.I.E.E., A.M.Brit.I.R.E., City & Guilds Exams, and particulars of up-to-date courses in Wireless Engineering, Radio Servicing, Short Waves, Television, Mathematics, etc., etc. We guarantee "NO PASS—NO FEE." Prepare for to-morrow's opportunities and future competition by sending for this very informative 112-page guide NOW—FREE and without obligation.
BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Dept. 248),
17, Stratford Place, London, W.1.

SURPLUS BARGAINS

R.C.A. AMPLIFIERS. 4 x 6J7, 2 x 6L6, 1 x 5U4; 200/250 v. 50 cps. input; pre-amp; crackle finish steel case; complete with mic mike. £12, plus 10/- carr.

NOISE SUPPRESSORS. Diode suppressor, with all parts and instruction book; ready to fit. Only 5/-, 6d. post.

78 RECEIVERS. 5 (6.3 v.) valves. Temp. controlled bandspread oscillator tuning, 2.4/13 mcs, 100 kcfs Xtal. **BRAND NEW,** in wooden crates, 30/-, 3/- carr.

STROBE UNITS. 6EF 50's, 5EA50's and V872, 6 pots., relays condensers, resistors, etc., in sealed cases, 35/-, 3/- carr.

BC347. Amplifier with 6F8 (double triode), transformers, etc., in attractive aluminium case, 5/-, post 9d.

POWER UNIT, TYPE 4. 4 metal H.T. rectifiers, 3 8uf x 500 V.D.C. electrolytics, 2 smoothing chokes, 4 x 1 condensers, vibrator transformer, etc. Soldered, but sacrificed at 10/-, plus 3/- carr.

BRAND NEW m/c mikes, 2/6; mic 'phones, 5/-; 0/300 V.D.C. mic meters, 5/-.

SLIGHTLY SOILED 0/3.5 A. thermocouple meters, 3/6; 0/100 mA mic meters, 3/6; post on above, 9d.

RADIO EXCHANGE CO(P).

9, Cauldwell St., Bedford.

('Phone: 5568)

RADIO UNLIMITED,

16, CARNARVON ROAD, LEYTON, E.10.

"Return of Post" Mail Order Service. "Money back" Guarantee of Satisfaction. Outstanding Bargains selected from hundreds worthy of your attention. Detailed list, 1d. stamp.

New and Boxed. Motor generator, 12 v. to 480 v., complete with conversion instructions, 12/6 post free.

New and Boxed M/coll Meters. 0-50 v., 0-40 amp., 4/6 each.

Test panel, containing a 0-20 v. and 0-5 amp. meter, etc., 12/6.

60 ohm Headphones, new, 2/11, soldered. 1/6. M/coll. 5/-.

15 watt A.C. Amplifier, listed at £26, offered at 12 gns.

A.C. Radiogram chassis. 3 waveband, £14 10s., inc. tax.

A.C. Electric Gramophone Motor and Table, £3 11s., inc. tax.

STOP PRESS

Ex Govt. I.F.F. sets complete with 10 valves, 12-. Brand new Morse Key and Buzzer Trainer Unit, 4/-, 2/11 post free.

L-R-S IN STOCK

CASH or EASY TERMS

GOODMANS 12in. & Axiom Speakers.

Wharfedale Speakers.

COLLARO Gram Unit & pick-up.

COLLARO auto. record changer.

STUART ELECTRIC PUMPS, compact and efficient-centrifugal pumps for clearing cesspools and stove-holes, etc.


★ All available for cash or easy terms, also many other items. Please let us have your enquiries. Particulars and leaflets on request.

The London Radio Supply Co.

(Est. 1925)

BALCOMBE, SUSSEX

THE LATEST IN KITS!

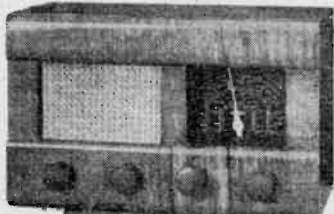

Complete in every detail including Beautiful Walnut Cabinet 13in. x 8in. x 6in. for **£7-17-6d.**

All main components mounted on chassis and wired. Simplest instructions for completing in one hour. 3 valves plus rec. AC/DC mains. 4 controls: Vol./Off—Tone—W/c—Tuning (slow motion).

12 WATT QUALITY AC/DC AMPLIFIER

Complete and in kit form from **£8-5-0**

Write for details.

C.O.D. or C.W.O. and Enquiries from:

LEWIS RADIO CO.

(Dept. F2), 322, High Road, Wood Green, London, N.22. 'Phone: BOW 5997

SUPER RADIO CO. (BFD) LTD.

39 Bank Street, Bradford, Yorks

SPECIAL NON-GOVT. SURPLUS OFFERS

A.F. Amplifier, 2 valve (Triode and Q.P.P.), 2v. L.T., 120v. H.T.	12/6
Radar Indicators, G. Unit, V.C.R. 97 Tube, 22 Valves	£3/-
Post	7/6
Magnetic Navigation Compass. ex-R.A.F.	12/6
Headphones, ex-U.S. Army, Low impedance	2/6
35-50 Meter Receiver, with dynameter, BC 455 B.	£115/-
Remote Transmitter Control Units, C.W.S. System	12/6
Relay Unit, 5-Way Changeover 24v. operated	3/6
Radio Compass B.C. 433 G.	£31/-

GOVT. SURPLUS

Star Identifier Charts. Ex-U.S. Army	3/6
Star Identifier Charts. Ex-R.A.F. Dial Drive, 100-l Reduction, 1155 Type	3/-
R.C.A. Model D.Z.I., Aircraft Direction Finder Equipment, inc. D.F. Aerial	£7/10/-
Post	10/-
Dinghy Aerial Balloons	3/-
V.H.F. Receiver, B.C. 357 P. 2 Valve, 12SQ7 and 12CB	10/-
7-Way Cable Bundle of 12 5ft. lengths	3/-

THESE ARE IN STOCK

TELEVISION FOR HOME CONSTRUCTION using War Surplus Equipment. 1s. 6d. Postage 2d.

PRACTICAL WIRELESS SERVICE MANUAL by F. J. Camm. 8s. 6d. Postage 4d.

RADIO RECEIVER DESIGN, Part I. K. R. Sturley. 28s. Postage 6d.

NEWNES TELEVISION MANUAL by F. J. Camm. 7s. 6d. Postage 4d.

RADIO COMMUNICATION TRANSMITTERS by J. J. Hupert. 30s. Postage 6d.

INTRODUCTION TO TELEVISION by A. Polwell. 9s. 6d. Postage 4d.

PRINCIPLES OF RADAR by M. I. T. 33s. Postage 9d.

RADIO TUBE VADE-MECUM, 1948 edition, by P. H. Brans. 5s. Postage 6d.

RADIO HANDBOOK SUPPLEMENT by R. S. G. B. 2s. 6d. Postage 9d.

RADIO UKEEP AND REPAIRS, by A. T. Witts. 7s. 6d. Postage 4d.

RADIO RECEIVER CIRCUITS HANDBOOK, by E. M. Squire. 6s. Postage 4d.

THE MATHEMATICS OF WIRELESS, by Ralph Stranger. 7s. 6d. Postage 4d.

RADIO SERVICE TEST GEAR, by W. H. Cazaly. 6s. Postage 4d.

CLASSIFIED RADIO RECEIVER DIAGRAMS, by E. M. Squire. 10s. 6d. Postage 4d.

We have the finest stock of British and American radio Books. Complete list on application.

THE MODERN BOOK Co.

(Dept. P.3), 19-23, Praed Street, London, W.2.

RADIO G200 ANNOUNCES

These Special Bargains

VIBRATOR. Unit No. 4. 12 volts D.C. in—250-300 volts at 100 mA. or more out, 4 metal rectifiers. These are the power unit from the famous No. 22 set, are ideal for car radio etc. Fully suppressed, a bargain at only 19/6.

ALTIMETER. ARN1. This American-built transmitter-receiver unit contains 4 ACORN 1 VR150/30 and 8 metal octal tubes exquisitely built, is very useful to the 420 mc. enthusiast. Brand new in original packing for only 70/-.

GENEMOTORS. 11.5 volts D.C. in 250 volts 125 ma. D.C. out. G200s, price 19/6. 11.5 volts D.C. in 490 volts, 65 ma. D.C. out (this gives about 250 volts when run from a 6 volt car supply). G200s, price only 19/6.

Please note new address where callers can see hundreds of other desirable bargains.

A. C. HOILE,

55, Union Street, Maidstone

DUNK & HEALEY

S.G. Brown's headphones, 5,000Ω, 12/6

PAPER CONDENSERS, in metal case. 4 mfd., 1,500 v.w., 6/8; 750 v.w., 4/-; 500 v.w., 2/-; 0.5 mfd., 1,000 v.w., 1/-; 0.1 mfd., 500 v.w., 6d.; 0.25 mfd., 600 v.w., 10d.; 0.01 mfd., 350 v.w., mica. 6d.; 0.0003 mfd., 350 v.w., mica, 4d.

ROLA—64in. P.M. with O.P. trans, 21/-, 6 v 6 G brand new and guaranteed. 7/6. EP50, in original manufacturers' cartons, 7/6. Westinghouse metal rectifier, 250 v, 60 ma., 7/6.

SMOOTHING CHOKES—10 h. 80 m.a. 120Ω, 5/6; 10 h. 120 ma. 100Ω, 6/9; 10 h. 300 ma. 100Ω, 12/6.

40 v. 2 a. transformers, cast shrouds, 230 v. 50 cya., heavy job 18/-

Please add 8d. for post; money back guarantee—mail order only.

67, OSNABURGH STREET,

LONDON, N.W.1.

Impressions on the Wax

Review of the Latest Gramophone Records

OUTSTANDING among the recent releases is a recording of Schubert's "Great" Symphony played by the Vienna Philharmonic Orchestra conducted by Herbert Von Karajan on *Columbia LX1138-43*. There are many points in this last and greatest symphony of Schubert's that compel admiration. The general conception is splendid, and it is magnificently handled by Herbert Von Karajan, who is especially successful with the big driving theme in the finale. It was not until seven years after Schubert's death that this symphony saw the light of public performance, and then only the last movement was given. These six records are sold with a booklet of analytical notes, and are a welcome addition to the Columbia Masterwork Series.

Another highlight is a recording of Handel's Organ Concerto No. 9 in B Flat, Op. 7, No. 3, on five sides of three 12in. records played by George Thalben-Ball accompanied by the Philharmonia Orchestra conducted by Walter Susskind—*H.M.V. C3814-6*. The records supply lively and vital music in the best Georgian tradition. On the reverse side of *H.M.V. C3816*, George Thalben-Ball plays his own arrangement of Allegro Moderato from Concerto No. 6 in B Flat Major.

Ida Haendel, who has recently signed a three-year contract with H.M.V., makes her second recording under the contract with Brahms Hungarian Dance, No. 17, arranged by Kreisler. This violin solo is coupled with Wieniawski's Polonaise Brillante in D Major, Op. 4, on *H.M.V. C3818*. She is accompanied on the piano by Gerald Moore in both recordings.

Walter Gieseking, the distinguished pianist, makes a welcome return to Columbia with a recording of Danse and La plus que lente, both by Debussy, on *Columbia LX1146*. This is his first recording since the war, and for a long time he has been the most important pianist in Germany and has given recitals under the auspices of the Allied authorities in recent years.

Popular Sadler's Wells Opera

The production of Verdi's Simone Boccanegra, which was undertaken by Sadler's Wells in October last, was the first performance of the work to be given in England. An English translation of the Italian libretto was made by Norman Tucker, chairman of the Sadler's Wells Directorate. These two records—*H.M.V. C3824-5*—are important additions to the repertory of opera in English, and the artists concerned in these excerpts are all members of the Sadler's Wells Opera. Simone Boccanegra is not given frequently even in Italy, and the Sadler's Wells Company's production is typical of their enterprise and exploratory policy.

"In a Monastery Garden" must share pride of place with "In a Persian Market" as Ketelbey's most widely known work. It has been presented often on the organ and by various instrumental combinations, and it has now been given a new

arrangement for the famous Melachrino Strings on *H.M.V. B9714*. For a coupling George Melachrino has chosen the peaceful "Bells Across the Meadow."

"Petite Suite de Concert" and "Hiawatha" are the two works which keep Coleridge-Taylor's name most often before the public. Each of the pieces in the Petite Suite have been perfectly recorded on *Columbia DB2479-80* by Sidney Torch conducting the Queen's Hall Light Orchestra, who have provided four sides of really attractive orchestra playing.

Andre Kostelanetz and his Orchestra have once again made a delightful recording. Kostelanetz has chosen two Viennese waltzes, "Gypsy Love," by Franz Lehár, and "Gypsy Baron," by Johann Strauss, and both receive subtle handling on *Columbia DX1540*.

Variety

Of all the numbers featured by Danny Kaye during his phenomenal variety season at the London Palladium last year, none was a bigger laughter maker than his hilarious satire on a light operatic tenor and a soprano. Now, under the title of "The Fairy Pipers," he lampoons lyric tenor and coy coloratura in a performance which ranges from the fanciful to the fantastic—*Columbia DB2481*. On the reverse side he sings "Farming" from Cole Porter's "Let's Face It."

A newcomer to the Columbia lists is Lynn Mason, who makes her debut with two sentimental ballads, "Let us be Sweethearts Over Again" and "When the Silver Threads are Shining," on *Columbia FB3449*. She is at present attached to Chappie d'Amato's Orchestra.

French-Canadian Jean Cavall, cabaret star and popular broadcaster, has recorded this month "Ah, but it Happens" and "Quand Meme," the latter being sung in English and French. Jean's neat presentation of "Quand Meme" on *H.M.V. B9715* may well make it a successor to the popular, "Darling, je vous aime beaucoup."

"If you had all the World," on *H.M.V. BD1233*, is a tailor-made number for Perry Como, who knows how to coax all the sentiment from a song without getting mawkish. The soft strings of the Russ Case Orchestra provide an effective background to the singer. Johnny Green's "Body and Soul" is resurrected on the reverse side.

Both of Geraldo's latest hit tunes, "Worry, Worry, Worry" and "Big Brass Band from Brazil," on *Parlophone F2330*, swept to the top of the Hit Parade in America last year. "Worry, Worry, Worry" is by the team that gave us "Woody Woodpecker," while "Big Brass Band from Brazil" became a best seller within a few months of its issue in the United States. Both come under the term novelty songs, and arranger George Evans, who is heard singing with the Geraldo Quartette, renders the lyrics with a grand swing to well-drilled playing by the orchestral ensemble.

MAINS TRANSFORMERS

Improved Machines improve Production and lower Costs. OUR NEW MULTI WINDERS are turning out thousands of Mains Transformers each week. HENCE we can pass this saving on to our many friends. LOOK !

Primary: 200/250 v. Sec. 350-0-350 v. 80 m.a., 6.3 v. 3 a., 5 v. 2 a.; or 250-0-250 with 4 v. or 6.3 v. heaters. All fully shrouded.

Prices better than pre-war.

Drop thro' chassis type ... 17/6
Chassis Mounting ... 19/6

Postage, 1/1d.

H. W. FIELD & SON LTD.,
Cable Works, Station Road,
Harold Wood, Essex.
Ingrebourne 2642

YOU can become a first-class RADIO ENGINEER

We are specialists in Home-Study Tuition in Radio, Television and Mathematics. Post coupon now for free booklet and learn how you can qualify for well-paid employment or profitable spare-time work.

T. & C. RADIO COLLEGE
KING EDWARD AVE., AYLESBURY

Post in unsealed envelope 1d. postage.
Please send me free details of your Home-Study Mathematics and Radio Courses.
NAME
ADDRESS
P. 96

GALPINS

ELECTRICAL STORES
408 High Street, Lewisham, London, S.E.13.
(Near Lewisham Hospital.)
PHONE: LEE GREEN 0309.
TERMS: CASH WITH ORDER. (NO C.O.D.)

EX-GOVERNMENT MAINS TRANSFORMERS. Input, 230 v., 50 cycles, output 450/0/450 v., 250 m.a., 6.3 v., 8 a., 6.3 v., 8 a., 6.3 v., 4 a., 6.3 v., 4 a., 5 v., 4 a., 45/- each, carriage 5/-, another same input, output 350/0/350 v., 180 m.a. twice, 5 v., 4 a. twice, 6.3 v., 5 a., three times, 47/- carriage 5/-, another same input, output 350/0/350 v., 250 m.a., 50/0/50 v., 100 m.a., four 6.3 v. at 5 a., one 5 v. at 4 a., 42/6 each, carriage 5/- (size and weight of these transformers is approximately 7 1/2 in. x 7 1/2 in. x 6 1/2 in. 20 lb.).

MAINS TRANSFORMERS, Input 230 v., 50 cycles, output, 42 to 50 v. at 100 a., £15 each, carriage 10/-, another input, 200/250 in steps of 10 v. Output tapped 6, 12, 18 and 24 v. at 10/12 a., 45/- each, carriage 2/-; another 230 v. input, output 12 v. at 8 1/2 a., 25/- each, carriage 2/-; another 220 v. input, output tapped 12 1/2, 25, 37 1/2, 50, 60, 75, 87 1/2, 100, 110 v. at 1,100 watts, £41/5/0 each, carriage, 7/6. (These Transformers are all double wound.)

MAINS TRANSFORMERS, all 200/250 v., 50 cys., 1 phase, input, output 700/0/700 v., 70 m.a., 4 v., 2 1/2 a., 12 v., 1 a., 30/- each. Another 525/525 v., 150 m.a., 6.3 v., 5 a., 5 v., 3 a., 37/- each. Another 2,350 v. at 500 m.a., 85/- each. Mains Smoothing Chokes, 10 Hy. 100 m.a., 6/-; 150 m.a. 8/6; 350 m.a., 25/-; 5 Hy. 250 m.a., 17/6.

EX-GOVERNMENT (G.E.C.) ELECTRIC FANS. 12 v. a.c./d.c. laminated field, complete with 5 1/2 in. impeller. New, boxed, 20/- each, post 1/-.

MAINS VARIABLE RESISTANCES (slider type), new, ex-Govt., 14 ohms carry 1 to 4 amps., graduated, useful as dimmers, etc., 17/6 each; another 0.4 ohms, carry 25 amps., 17/6 each, post 1/6. Ex-Govt. Moving-coil Cell Testers, 3-0-3 v. (new), 15/- each.

EX-R.A.F. MICROPHONE TESTERS (new). These consist of a Ferranti 0 to 450 mlamp. 2 1/2 in. scale meter shunted to 1 m.a. incorporated Westinghouse Rectifier, the whole encased in polished teak case, calibrated at present 0 to 10 v., 25/- each.

ELECTRIC LIGHT CHECK METERS (Watt Hour). A.C. 50 cys., 200/250 v., 5 amp. load, 18/6, post 2/-; 10 amp., 21/-, post 2/-; 20 amp., 25/-, post 2/-; also a few only Pre-Payment II-slot type, 20 amp. load, less coin box, complete with synchronous motor, 35/- each, carriage 3/6.

EX-NAVAL (CROMPTON PARKINSON) TONG-TESTERS, 0 to 100, and 0 to 400 amps., new, in leather carrying case, 90/- each. A.C. V/Meters, 0 to 300 6in. scale, calibrated 50 cys., 37/6 each.

SPECIAL OFFER METERS, all new, boxed. Moving Coil, first grade instruments, 0 to 20 v., 10/- each, or 3 for 25/-; 0 to 40 v., 12/6 each; 0 to 10 amps., 15/- each, all 2in. scale. 0 to 20 v., A.C., calibrated 50 cycles, 25/- each; 0 to 40 amps., thermo-coupled, 25/- each.

CHARGING SWITCHBOARDS, size 17 1/2 in. x 16 1/2 in. x 8 in., containing 5 circuits, 5 Moving Coil 0 to 15, Ammeters, 10 to 50 V/Meter, 4 1-Ohm, 12 amp. Resistances, 1 14-Ohm 1.4 amp. Resistance, all variable, also Switches, Fuses, etc., condition as new, £41/0/0 each, carriage 10/-.

PRE-PAYMENT II-SLOT ELECTRIC LIGHT CHECK METERS, 200/250 volts, 50 cys. 1 ph., 2 1/2 amp. load, 30/- each, carriage 3/6; 5 amp. load, 35/-, carriage 3/6. Also D.C. type 10 amp. load, 200-250 volts, 25/- each, carriage 3/6.

TELE-RADIO (1943) LTD.

177, EDGWARE ROAD, W.2.

1.6 meg. I.F. Transformers ...	each	5/-
Coaxial cable, 3/16 dia., 22ft. length (Ex-V.V.D.) ...		5/-
Large brass terminals ...		4d.
" plated brass terminals ...		6d.
Sprague Condensers, .01 1,000v. ...		8d.
" 5 350v. ...		9d.
Ceramicon " 10 mfmfd. ...		9d.
Ceramic Disc, 25 mfmfd. ...		1/3
Dubilier mica, 75 mfmfd. ...		6d.
" .001 mfd. ...		6d.
Paper tubular condenser, .02 mfd. ...		9d.
Tubular Condenser .005 mfd. 1,000 v. ...		9d.
Silver mica, .0005 mfd. 350v. ...		9d.
Two gang miniature condenser, 50 mfmfd. ...		1/6
Two gang miniature condenser, 75 mfmfd. ...		1/6
Two gang standard condenser, 160 mfmfd. ...		5/-
Three gang standard condenser, 500 mfmfd. ...		10/6
Four gang standard condenser, 500 mfmfd. ...		10/6
Carbon potentiometers, 500 ohms ...		3/-
" 250k. ohms ...		3/-
Linear " ...		3/-
Carbon potentiometers, 25k. ohms ...		3/-
Aluminium chassis, 17 x 10 x 2 ins. ...		11/-
" 17 x 10 x 3 ins. ...		11/6
" 11 x 6 1/2 x 2 1/2 ins. ...		9/6
" 8 x 6 1/2 x 2 ins. ...		7/6

Please include sufficient for postage and packing. 1949 Catalogue now available, 9d., post free.

Telephone: AMB. 5393 PAD. 6116
 PAD. 5606

LYONS RADIO

3, Goldhawk Road,
Shepherds Bush, W.12
Telephone: Shepherds Bush 1729.

MOVING-COIL LOUDSPEAKERS
6 1/2 in. R. & A., with transformer, 15/-, 5in. Flessey, with transformer, 13/6. Brand new and fully guaranteed.
(Postage extra 1/-).

L.F. CHOKES
10H at 75 m.a. D.C. res., approx. 150 ohms, Brand new and fully guaranteed.
Price 7/6 (postage 9d.).

"ELECTRO" ELECTRIC SOLDERING IRONS
220-230v. A.C./D.C., with spare bit. Ideal weight for radio work.
Price 10/- (postage 9d.).

C-150 m.a. MOVING-COIL MILLIAMMETERS
2 1/2 in. square case. Flush fitting. Brand new and fully guaranteed.
Price 6/- (postage 6d.).

STEEL DEED CHESTS OR SAFES
For the safe keeping of documents and valuables. Size: 17 1/2 in. x 13 1/2 in. x 12 1/2 in. Fitted with strong lock (2 keys supplied), and folding handles on sides.
Price 30/- (carriage 3/6).

BRAND NEW METAL-CASED CONDENSERS
0.5+0.5 mfd., 1,500v. working. Size 5in. x 3 1/2 in. x 1 1/2 in. Price 2/9 each (postage 6d.).

DESK MICROPHONE
Similar to those used on R.A.F. ground stations. 12in. high pedestal with adjustable head. Fitted with sensitive carbon insert. Complete with lead. As new.
Price 7/6 (postage 1/6).

Open to Discussion

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

6K7 Pocket Receiver

SIR,—Having taken PRACTICAL WIRELESS for about two years, I am at last prompted to write to you. And the subject is that set using one 6K7 that you have mentioned several times.

I made this up and, using it at Great Yarmouth, succeeded in getting Hilversum. Owing to the "marvellous" B.B.C. coverage over that way, I couldn't get them at all. Then I started experimenting on my own account.

My first mod. was to use a flat battery for heaters and a 9-volt G.B. for H.T. Then, as I reasoned, the .3 A. of the 6K7 is higher than the .15 A. of a 956. I changed over to that valve, and I think it is better than the 6K7. Since I have been here near Bedford I have heard both Home and Light programmes without any trouble. Any time now the heater consumption is going back to .3 A., as I'm going to use another 956 as A.F. amplifier. The small physical size is a good thing for this latest scheme.—C. J. GRICE (Bedford).

R1355 and Television

SIR,—I am writing this letter because I feel the information may be of use to those intending to build television receivers.

Certain retailers are advertising ex-R.A.F. receivers type R1355 (10/13032) as "suitable for television," with "4 Megacycle bandwidth." Now, this is misleading. The actual bandwidth is ± 6 Mc/s. for 6 db. down, i.e. 1.2 Mc/s. bandwidth, a very different thing from 4 megs. The I.F. of the R1355 is 7.5 Mc/s., and the I.F. coils are damped by fixed resistors. The R.F. Units 25, 26, 27, etc., are very suitable for television as they stand.

I trust this will be of some help to someone.—K. BERRY (Surbiton).

Old Receiver Performance

SIR,—In the December, 1948, issue of PRACTICAL WIRELESS you state that a set that is more than 10 years old has a lower standard of reception than a new set.

It may interest you to know that my parents have a certain console, price £20, bought in 1934, which has had a great deal of use and, apart from having the wavechange switch cleaned, has never gone wrong and has its original valves.

The specification may also interest you. It has nine valves, 10 watt push-pull output, 12in. M.C. speaker, a tuning device that, as soon as a station is roughly tuned, pulls the station dead on tune, a modern-styled console cabinet, the walls of which are lined with sound-absorbing material. The result is a set which has superb tonal quality and good sensitivity, selectivity and a noise level lower than the majority of modern sets. The only sets I have heard with as a good a performance are very expensive £200 radiograms.

You mention improvements in design and

manufacture in the past ten years. I have examined the circuits and construction of many post-war sets, and they all follow conventional five or (if you are lucky) six valve superhet circuits. An imposing radiogram costing over £100 turns out to have only five valves. The local radio dealer, of all people, states that in only one make of receiver are the fixed condensers reliable. To demonstrate his point he tested a representative sample of British condensers. They all had leaks varying from .5 M Ω to 2 M Ω . This is a serious matter, especially from the export point of view. On the other hand, he tested a sample of American condensers and they had no leaks.


In fact, I challenge you to point out the improvements in design and manufacture which you say have taken place in the last ten years.—T. R. LAIDLAW (Rugby).

Measuring Meter Resistance

SIR,—Further to recent correspondence re meter resistance, and to the methods employed in obtaining same, I find the enclosed circuit sufficient.

Let R_s be the limiting resistor to prevent possible damage to the instrument.

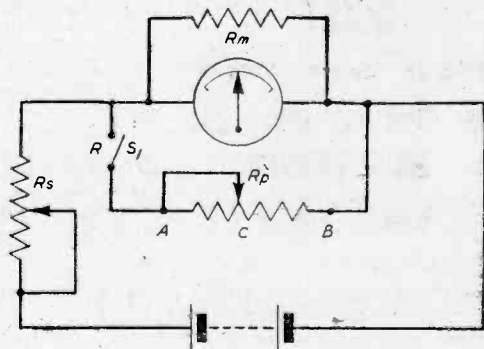With the switch S_1 open, adjust R_s until the instrument indicates F.S.D.



Mr. Palmer's arrangement for measuring meter resistance.

Now close S_1 to bring R_p into circuit, and adjust R_p until the instrument indicates half F.S.D.

When this condition is reached the resistance of the instrument is $R_m = R_p$, or $R_m = R_c B$, to be more precise.

The resistance of S_1 , shown as R , is usually low enough to be ignored.

However, for special purposes, this may be found beforehand.

Therefore $R_m = R_c B + R$.

Thanking you for a most interesting Journal.—F. C. PALMER (Highbury).

"Caesar's Mistress"

SIR,—May I trespass upon your space to comment upon "Thermion's" article in the February issue? He apparently dislikes "Schools" broadcasts and, rather than have so much dance music during the day, would have the B.B.C. cut out daytime programmes altogether.

Regarding the Schools programmes, these are, surely, very often both informative and entertaining even for adults, and regarding daytime programmes in general, there are very many worthwhile items as, for instance, the midday orchestral hour.

But my main point is that the B.B.C. should, as it does, endeavour to provide broadcasts whenever people may want to listen. One has, after all, not got to listen because programmes are on the air, and to many people daytime programmes are a boon, especially to the sick and to housewives on their own all day. It helps to stop them feeling lonely, or so my wife tells me.

No, sir. There is too much already of this "I don't like it, you shan't have it" attitude abroad in the country. If Thermion does not like daytime programmes he can switch off—but why seek to deny them to people who do?—H. J. BOWER (Kent).

Home-recording Equipment

SIR,—Mr. Sixsmith's letter in February's PRACTICAL WIRELESS reminds me that I, too, sat down and wrote you a letter on this subject recently. Unfortunately the letter was mislaid, and was out of date by the time it was found.

Apparently quite a number of us would like to try our hands at recording now that L.F. amplifiers of ample power output and good quality form part of our equipment.

The main bother, of course, is a recording head and a tracking arm. These things are available—but at what a price! Low-priced versions of these were available in pre-war days, and it would be interesting to know whether any manufacturer is or will be sufficiently enterprising to bring them out again. I, for one, would be content with gear and results somewhat short of professional standards (and within the capacity of my pocket) rather than be able to do nothing at all.—W. MACKINTOSH (Putney).

Ex-Government British Valves

SIR,—Nowadays a large number of amateurs and experimenters are using ex-Government surplus valves. Such valves usually have certain letters prefixed to the type numbers which will help many readers to identify when purchasing such valves. The letters which are prefixed are given below with their meanings:

AR	= Army Receiving (Valves)
ARDD	= " " Double diode.
ARH	= " " Heptode.
ARP	= " " Pentode.
ARS	= " " Screen grid.
ARTP	= " " Triode-pentode.
AT	= " " Transmitting.
ATP	= " " Pentode.
ATS	= " " Screen grid.
AU	= " " Rectifying.

—MOHAMEDALI A. SHAIKH (Poona).

No. 18 Receiver

SIR,—Concerning the No. 18 Mk. III set, I agree with both Mr. Moore, of Solihull, and Mr. Hearon, of S.E.15, that this receiver works quite well from an ordinary aerial, and, as Mr. Moore states, it is better to omit the untuned R. F. stage when a long aerial is used. I would very much like to hear from any readers who own a R.1224A set. I have one of these, and I am very disappointed with its performance. As a five-valve superhet I am surprised how insensitive it is. I have replaced the power valve with a Mullard Pen. P.M.22D, and although it now works a speaker fairly well, it has no "punch"—even the Light programme is not at all loud. In "station pick up" it does not compare with a three-valve straight which I have. Can anyone explain this and help me to improve results? I have had it "run over" by a radio expert, and he says it is quite O.K., but agrees with me that it lacks sensitivity. I will answer all letters.—RAYMOND R. RADMORE, JNR., 9, Parsonage Road, Northam, Southampton, Hants.

"Utility 4"

SIR,—I was extremely interested in the "Utility" Four in February's PRACTICAL WIRELESS.

My brother and I have just completed a very similar receiver, which cost even less to make. It was built on the chassis of a Type 24 R.F. adaptor now obtainable so cheaply.

The five-point switch was left intact apart from the third (oscillator) section, which was sawn off by a hacksaw blade. The trimmers in this compartment were removed, and in this space a 25A7 valve (pentode + rectifier) out of the junk cupboard mounted. In the original H.F. and lower valve spaces are mounted two EF50's. We thus have three 0.3 amp. valves fulfilling the functions of Mr. Delaney's four. In series with these is arranged a good 60-watt lamp (a cheap make was found to pass about 50 watts and the rectifier filament was underrun, dropping the H.T. badly). The H.T. is taken straight off the mains, and the smoothing condensers 24 + 16 μ F are in the original oscillator valve compartment.

The two remaining portions of the switch and the original trimmers, with suitable miniature fixed condensers in parallel, form the fixed tuning apparatus, and five different medium-wave stations are obtainable.

I have the 10,000 ohms variable bias resistance in the H.F. stage but have not yet adapted Mr. Delaney's ingenious connection of one end to the aerial coil. I also have resistance-controlled reaction on the detector. If this is not near oscillation tuning is not disturbed, and it improves volume and selectivity.

The method used is a 10,000 ohm wire-wound resistance in series with the standard reaction coil, and a fixed condenser. Both 10,000 resistors are on the front panel in the H.F. valve partition.

The detector circuit employed has identical screen and plate resistors to Mr. Delaney's, but no grid condenser or leak, and a 3,600 ohm cathode resistance found by trial to be most effective.

If necessary, it can be mounted in a wooden box with only the knobs protruding.—H. S. BRODRIBB, M.D., St. Leonards-on-Sea.

CLASSIFIED ADVERTISEMENTS

RATES: 3/- per line or part thereof... minimum 2 lines. Box No. 6d. extra. Advertisements must be prepaid and addressed to Advertisement Manager, 'Practical Wireless', Tower House, Southampton St., Strand, London, W.C.2.

R.S.G.B. TECHNICAL PUBLICATIONS. The following are of special interest to transmitting amateurs and short-wave enthusiasts.

VALVETECHNIQUE. Presents the calculations associated with the application of thermionic valves. 104 pages. Fully illustrated. 3/9 post free.

V.H.F. TECHNIQUE. Comprehensive account of techniques employed for generation, propagation and reception of frequency between 30 and 300 Mc/s. 96 pages. Fully illustrated. 3/9 post free.

MICROWAVE TECHNIQUE. Describes theory and practice of microwave technique. 68 pages. Fully illustrated. 2/3 post free.

THE TRANSMITTING LICENCE. Second edition. How to obtain an amateur licence. 32 pages. 1/- post free.

R.S.G.B. BULLETIN. Monthly publication of R.S.G.B. 1/6 post free. (Free to Members.)

THE RADIO SOCIETY OF GREAT BRITAIN

28, Little Russell Street, London, W.C.1

RADIO Constructor's Catalogue. 20-page Catalogue, packed with hundreds of items of interest to the constructor, service engineer and experimenter, plus details of our Technical Query Service. Price 4d., post free.—Hessing and Light, Ltd., The North's Leading Radio Engineers, King's Square, York.

RECEIVERS & COMPONENTS

RADIO FOR 37/- (tax paid) special design, short wave; Works off 9v. G.B. for H.T. and U.2. 1.5 v. for L.T. No earth needed. only short aerial. Complete kit, parts, valve, drilled and punched chassis, screws, instructions, etc. Brand New. Sent instantly on receipt of Cheque or P.O.—Supreme Radio, 43, Melbourne St., Stalybridge, Cheshire.

CHEAP. leaky condensers are dear at any price! Only the best components are worth of this new Radio or Amplifier. We supply only the best. Order C.O.D. or C.W.O. Anything in Radio you may require. All goods new at manufacturer's List Price! All goods as per February issue still available. Prompt Personal Attention. Send us, or List.—Radio Service (W. Tanner), East Cliff, Lyme Regis, Dorset.

RAYMAX are your suppliers for Radio, Television and Gramophone equipment, components, kits, chassis. All at prices you can afford. Table radiograms, player or auto-changer, kits, cabinets. Stamp for list which will cover all your requirements.—RAYMAX, Ltd., 126, Norwood Road, London, S.E.24.

RADIO and electrical bargains—Brand new Garrard and Collaro, etc., radiogram motors—autochangers, record players with amplifiers—radio sets—clocks—irons—radio spare parts, etc. at bargain prices. Send S.A.E. for list to Radio Bargains, 261, Lichfield Road, Aston, Birmingham.

BRAND NEW.—R28/ARC5 10-valve 100-150 mc/s, with circuit, 45/-; Receiver 76. 150-505 kc/s, 27/6; BC442A Metered Aerial Relays, 6/-; Creed Highspeed Relays, 21/-; Metal Rectifiers, 60w., 30 m.A., 3/-; 200v. 100 ma., 5/-; 12v. 1a., 2/6; Headsets, 30 m.c. with mic., 6/-; Chokes, 300-ohm, 100 ma., 4/6; Variable resistances, 12-ohm 5 amp., 200-ohm .5a., 7/6; Bulkhead Insulators, 1/-; Bakelite pulleys, 9d.; Crystals 7010, 8090, 7/6; 5-8 mc/s, 5/-; Condensers, 30 mF, 100v., 1/3; .01 mF, 1,000v., 9d.; .001 mF, 500v., 6d.; .001 mF, 2,000v., 9d.; .25 mF, 500v., 9d.; 3-valve Modulator Units, 15/-; Yaxley's pole 3-way, 3-bank, 3/-; 2-pole 11-way, 3/-; 4-pole 2-way, 2/6; Indicator lampholders, 1/3 (MBC); BC339G Control boxes, 7/6; Meters, amps 0-1, 5/-, 0-21, 7/6; Flexible couplers, 1/-; Epicyclic drives, 1/3; Bulgin Tunnin holders, 1/-; VIBRATOR EB34, SP14, SP81, EA50, 3/-; 6SN7, 6SL7, 5R4GY, EF50, RL37, 6AC7, 5/-; 3in. knobs 1/-; Push-pull Driver Transformers, 5/6; Transceivers, No. 38, 6-9 mc/s, 65/-; S.a.e. enquiries, Benson, 308, Rathbone Road, Liverpool, 13.

MAINS TRANSFORMERS 16/6 POST PAID

NEW GOODS NOT SURPLUS FULLY GUARANTEED

- Primaries for 200/250v. Drop through chassis type with no shroud. Interleaved and wax impregnated windings. Screened primary. (a) 250-0-250v. 60 mA., 6.3v. 3 A., 5v. 2 A., 16/6 (b) 250-0-250v. 60 mA., 4v. 4 A., 4v. 2 A., 16/6 Following Types have UNIVERSAL L.T. Windings, 0-4-3, 4 A. C.T. 0-4-5v. 2 A. This means that either 4v. or 6.3v. valves may be used with either 4v. or 5v. rectifier. (c) 250-0-250v. 80 mA. ... 19/- (d) 300-0-300v. 80 mA. ... 19/- (e) 350-0-350v. 80 mA. ... 22/- (f) 250-0-250v. 100 mA. ... 19/- (g) 300-0-300v. 100 mA. ... 22/- (h) 350-0-350v. 100 mA. ... 22/- Upright Types Fully Shrouded. (i) 350-0-350v. 150 mA., 0-4-6.3v. 6 A. C.T. 4/2. 3 ... 39/- (j) 425-0-425v. 180 mA., 6.3v. 4 A. C.T. 6.3v. 4 A. C.T. 5v. 3 A. ... 44/6

10,000 VALVES IN STOCK

Get the valve you want by return C.O.D. at standard B.O. prices.

MINE DETECTOR AMPLIFIERS

3 valve R.C. Midget Amplifiers with three IT4 valves in ceramic holders, 22/6.

3 AMP LINE CORD

60/70 ohms per ft. 2-way, 1/3 yd.; 3-way, 1/6 yd.

EX GOV. BARGAINS

In response to many requests from clients all over the country we have decided to stock carefully selected items of ex Govt. equipment—NO JUNK—all in new condition and at the best value in the U.K. If interested please include extra 2ld. stamp for ILLUSTRATED LIST.

NEW GOODS ONLY. C.W.O. or C.O.D. POST FREE OVER 5/-

"COULPHONE RADIO"

The Return of Post Mail Order Service. 58, Derby Street, Ormskirk, Lancs.

Send 2ld. stamp for 32 page catalogue.

HIGHSTONE UTILITIES

Crystal Sets.—Our latest Model is a real radio receiver, fitted with a permanent crystal detector. Why not have a set in your own room—9/6, post 6d. De Luxe Receiver in polished or cabinet, 15/6, post 1/-; Spare Permanent Crystals, 2/- each. Where Ordered separately, 2/6. With clips and screws, 2/10, post 3d. Headphones, reconditioned and in good order, 5/6, post 6d. (better quality, 7/6). New Doubletunes, 10/- 3 pair, post 6d. Balanced armature type (very sensitive), 12/6 a pair, post 6d. New Single Earpieces, 3/6. Bal. armature type, 4/6; ex-R.A.F. earpiece, 2/-, post 6d. All headphones listed are suitable for use with our crystal sets. Hand Microphones, with switch in handle, and lead, 4/-; Similar instrument moving coil, 7/6, post 6d. Sparking Plug Neon Testers with vest pocket clip, 3/3, and with case, 3/6, post 3d. Soldering Irons. Our streamlined Iron is supplied with two interchangeable bits, one each straight and curved; 200-250 50 watts, 9/-; Standard Iron with adjustable bit, 6/6, 250-300 50 watts, 9/6 Heavy Duty Iron, 150 watts, 12/6, all post 6d. S.B.C. Neon Indicator Lamps, for use on mains, showing "live" side of switches, etc., 3/6, post 4d. Telephone Hand Generator with handle, 7/6, post 1/6. Bell, 4/6, post 6d. EX-R.A.F. 2-Valve (2-volt) Amplifiers, can be used to make up a deaf aid outfit, intercommunication system, or with crystal set, complete with valves, 20/-; Soldering 1/6. Ditto, less valves, 10/-. Wooden box to hold amplifier, 2/- extra. Meters, 0-300 mA. 2in., m.c. 7/6. 3.5 amp., 2in., T.C. 5/4 amp., 2in., thermo coupled in case with switch, 7/6; 30 mA. 2in., m.c. 6/-; Double reading 40/120 mA. 2in., m.c. 8/-; 20 amp., 2in., m.f. 9/6; 15 volt 2in., m.c. 9/6; 15v. 2in., m.c. 10/-; 15 v./500 v. double reading, 2 in., m.c. 8/-; 300 v. 2in., m.f. 12/6; 6,000 v., 3in., m.c. 57/6; 3,500 v., 3in., m.c. 20/-; Meter movements, 2in. size with magnet (500 micro-amp), 2/6. Post Extra. Money refunded if not completely satisfied.

HIGHSTONE UTILITIES

58, New Wauve Road, London, E.11.

Letters only. Illustrated Lists sent on requests with 1d. stamp and s.a.e.

RF UNITS, TYPE 24, 8/6; 25, 10/6; 27, 21/- ea., plus 1/3 post. Panel assembly with 23 res., 10.0 tubars, 5 mks. 9. Westectors, 6/- ea., 6 valve RF, and IF strip, with 3 x 12 m.c. IFTs and RF and Osc. coils, to receive TV sound, 6 ceramic VHS, 8/6. Stamp trimmers, 3d. ea., 24 on panel, 3/6. Yaxley type switches, 9 v. single bank, 1/6; 5 w., 5 b. 4/-; Self-engraved magnetic controls with switch, 2/6. Phons. L.R., 3/6 pr. Reed type, 7/6 pr.; M.C., 7/6 pr., or with M.C. mike, 10/6. Plugs and jacks, 1/6 pr. One-hole type, 2/- Jones plugs for 24, 5, 6, 7. Frequency meters, 1/- ea.; 15s and others, 1/6 ea. Most types WD plugs and sockets in stock. Midget output tranny for 45 ohm. M.C. earpiece, 3/-; Res. and cons. on pax panels, 50 assorted, 5/6; 100, 8/6. A.C. 230 v. power units, type 392, 600 v., 12ma., 12 v. 1 a., with 2 rec. valves, 43, carr. paid. Tannoys 24in. PA horns, 30/- ea. Tuning condensers, .0003, 2 G, 3/6; .00015, 3 G, 3/6. S.W. and UHF chokes, 6 different, 3/-; UHF coils, dust tuned with ceramic air-spaced trimmers, 7/6. R.C. type T49, on-off, 1/-; Bulgun dial, 2/-; R1124 receivers with valves, 19/6 carr. paid. Indicator units with 97, etc., 9 types in stock. Receivers of all types in stock, including H.R.C. Hallcrafters, Marconi and WD types. Frequency meters, R.C. type T49, crystal controlled, 250 kc/s, 25 m.c., see no. 2615-4-e. Valves, EF39, EF36, 6Q7, 6K7, EB33, EK32, EA50, EB34, SP14 (4 or 6 v.), 8D2, 9D2, 15D2, 4D1, all at 5/-; EF50, 12/54; V137, 6SHT, 6AC7, A84, VT4a, at 6/-; 12A6, 7193, 6J5, 12J5, 7/6; 6N7, 6V61, 807, 6L6, Pen. 46, Pen. 45, 6SN7, 6SL7, 6X130 and 105, EF32, KT33c, VU111, AUG5, U539 (4 or 5 v.), VP41, 2X2, 6V6, 68G7, 68B, 68K, 68L, 68M, 68N, 68P, 68Q, 68R, 68S, 68T, 68U, 68V, 68W, 68X, 68Y, 68Z, 68AA, 68AB, 68AC, 68AD, 68AE, 68AF, 68AG, 68AH, 68AI, 68AJ, 68AK, 68AL, 68AM, 68AN, 68AO, 68AP, 68AQ, 68AR, 68AS, 68AT, 68AU, 68AV, 68AW, 68AX, 68AY, 68AZ, 68BA, 68BB, 68BC, 68BD, 68BE, 68BF, 68BG, 68BH, 68BI, 68BJ, 68BK, 68BL, 68BM, 68BN, 68BO, 68BP, 68BQ, 68BR, 68BS, 68BT, 68BU, 68BV, 68BW, 68BX, 68BY, 68BZ, 68CA, 68CB, 68CC, 68CD, 68CE, 68CF, 68CG, 68CH, 68CI, 68CJ, 68CK, 68CL, 68CM, 68CN, 68CO, 68CP, 68CQ, 68CR, 68CS, 68CT, 68CU, 68CV, 68CW, 68CX, 68CY, 68CZ, 68DA, 68DB, 68DC, 68DD, 68DE, 68DF, 68DG, 68DH, 68DI, 68DJ, 68DK, 68DL, 68DM, 68DN, 68DO, 68DP, 68DQ, 68DR, 68DS, 68DT, 68DU, 68DV, 68DW, 68DX, 68DY, 68DZ, 68EA, 68EB, 68EC, 68ED, 68EE, 68EF, 68EG, 68EH, 68EI, 68EJ, 68EK, 68EL, 68EM, 68EN, 68EO, 68EP, 68EQ, 68ER, 68ES, 68ET, 68EU, 68EV, 68EW, 68EX, 68EY, 68EZ, 68FA, 68FB, 68FC, 68FD, 68FE, 68FF, 68FG, 68FH, 68FI, 68FJ, 68FK, 68FL, 68FM, 68FN, 68FO, 68FP, 68FQ, 68FR, 68FS, 68FT, 68FU, 68FV, 68FW, 68FX, 68FY, 68FZ, 68GA, 68GB, 68GC, 68GD, 68GE, 68GF, 68GG, 68GH, 68GI, 68GJ, 68GK, 68GL, 68GM, 68GN, 68GO, 68GP, 68GQ, 68GR, 68GS, 68GT, 68GU, 68GV, 68GW, 68GX, 68GY, 68GZ, 68HA, 68HB, 68HC, 68HD, 68HE, 68HF, 68HG, 68HH, 68HI, 68HJ, 68HK, 68HL, 68HM, 68HN, 68HO, 68HP, 68HQ, 68HR, 68HS, 68HT, 68HU, 68HV, 68HW, 68HX, 68HY, 68HZ, 68IA, 68IB, 68IC, 68ID, 68IE, 68IF, 68IG, 68IH, 68II, 68IJ, 68IK, 68IL, 68IM, 68IN, 68IO, 68IP, 68IQ, 68IR, 68IS, 68IT, 68IU, 68IV, 68IW, 68IX, 68IY, 68IZ, 68JA, 68JB, 68JC, 68JD, 68JE, 68JF, 68JG, 68JH, 68JI, 68JJ, 68JK, 68JL, 68JM, 68JN, 68JO, 68JP, 68JQ, 68JR, 68JS, 68JT, 68JU, 68JV, 68JW, 68JX, 68JY, 68JZ, 68KA, 68KB, 68KC, 68KD, 68KE, 68KF, 68KG, 68KH, 68KI, 68KJ, 68KL, 68KM, 68KN, 68KO, 68KP, 68KQ, 68KR, 68KS, 68KT, 68KU, 68KV, 68KW, 68KX, 68KY, 68KZ, 68LA, 68LB, 68LC, 68LD, 68LE, 68LF, 68LG, 68LH, 68LI, 68LJ, 68LK, 68LL, 68LM, 68LN, 68LO, 68LP, 68LQ, 68LR, 68LS, 68LT, 68LU, 68LV, 68LW, 68LX, 68LY, 68LZ, 68MA, 68MB, 68MC, 68MD, 68ME, 68MF, 68MG, 68MH, 68MI, 68MJ, 68MK, 68ML, 68MM, 68MN, 68MO, 68MP, 68MQ, 68MR, 68MS, 68MT, 68MU, 68MV, 68MW, 68MX, 68MY, 68MZ, 68NA, 68NB, 68NC, 68ND, 68NE, 68NF, 68NG, 68NH, 68NI, 68NJ, 68NK, 68NL, 68NM, 68NN, 68NO, 68NP, 68NQ, 68NR, 68NS, 68NT, 68NU, 68NV, 68NW, 68NX, 68NY, 68NZ, 68OA, 68OB, 68OC, 68OD, 68OE, 68OF, 68OG, 68OH, 68OI, 68OJ, 68OK, 68OL, 68OM, 68ON, 68OO, 68OP, 68OQ, 68OR, 68OS, 68OT, 68OU, 68OV, 68OW, 68OX, 68OY, 68OZ, 68PA, 68PB, 68PC, 68PD, 68PE, 68PF, 68PG, 68PH, 68PI, 68PJ, 68PK, 68PL, 68PM, 68PN, 68PO, 68PP, 68PQ, 68PR, 68PS, 68PT, 68PU, 68PV, 68PW, 68PX, 68PY, 68PZ, 68QA, 68QB, 68QC, 68QD, 68QE, 68QF, 68QG, 68QH, 68QI, 68QJ, 68QK, 68QL, 68QM, 68QN, 68QO, 68QP, 68QQ, 68QR, 68QS, 68QT, 68QU, 68QV, 68QW, 68QX, 68QY, 68QZ, 68RA, 68RB, 68RC, 68RD, 68RE, 68RF, 68RG, 68RH, 68RI, 68RJ, 68RK, 68RL, 68RM, 68RN, 68RO, 68RP, 68RQ, 68RR, 68RS, 68RT, 68RU, 68RV, 68RW, 68RX, 68RY, 68RZ, 68SA, 68SB, 68SC, 68SD, 68SE, 68SF, 68SG, 68SH, 68SI, 68SJ, 68SK, 68SL, 68SM, 68SN, 68SO, 68SP, 68SQ, 68SR, 68SS, 68ST, 68SU, 68SV, 68SW, 68SX, 68SY, 68SZ, 68TA, 68TB, 68TC, 68TD, 68TE, 68TF, 68TG, 68TH, 68TI, 68TJ, 68TK, 68TL, 68TM, 68TN, 68TO, 68TP, 68TQ, 68TR, 68TS, 68TT, 68TU, 68TV, 68TW, 68TX, 68TY, 68TZ, 68UA, 68UB, 68UC, 68UD, 68UE, 68UF, 68UG, 68UH, 68UI, 68UJ, 68UK, 68UL, 68UM, 68UN, 68UO, 68UP, 68UQ, 68UR, 68US, 68UT, 68UU, 68UV, 68UW, 68UX, 68UY, 68UZ, 68VA, 68VB, 68VC, 68VD, 68VE, 68VF, 68VG, 68VH, 68VI, 68VJ, 68VK, 68VL, 68VM, 68VN, 68VO, 68VP, 68VQ, 68VR, 68VS, 68VT, 68VU, 68VV, 68VW, 68VX, 68VY, 68VZ, 68WA, 68WB, 68WC, 68WD, 68WE, 68WF, 68WG, 68WH, 68WI, 68WJ, 68WK, 68WL, 68WM, 68WN, 68WO, 68WP, 68WQ, 68WR, 68WS, 68WT, 68WU, 68WV, 68WW, 68WX, 68WY, 68WZ, 68XA, 68XB, 68XC, 68XD, 68XE, 68XF, 68XG, 68XH, 68XI, 68XJ, 68XK, 68XL, 68XM, 68XN, 68XO, 68XP, 68XQ, 68XR, 68XS, 68XT, 68XU, 68XV, 68XW, 68XX, 68XY, 68XZ, 68YA, 68YB, 68YC, 68YD, 68YE, 68YF, 68YG, 68YH, 68YI, 68YJ, 68YK, 68YL, 68YM, 68YN, 68YO, 68YP, 68YQ, 68YR, 68YS, 68YT, 68YU, 68YV, 68YW, 68YX, 68YY, 68YZ, 68ZA, 68ZB, 68ZC, 68ZD, 68ZE, 68ZF, 68ZG, 68ZH, 68ZI, 68ZJ, 68ZK, 68ZL, 68ZM, 68ZN, 68ZO, 68ZP, 68ZQ, 68ZR, 68ZS, 68ZT, 68ZU, 68ZV, 68ZW, 68ZX, 68ZY, 68ZZ.

EXTRA HIGH-GRADE Amplifiers and Receivers designed and constructed to individual requirements. No standard models. Let us quote for something that is different.—Dennis Bryan, 30, Windsor Drive, Timperley, Cheshire.

YOU CAN afford a Personal Portable! Build it yourself to the Nuplans circuit; all standard parts, really small, really works. Circuit, layout, notes, etc. 2/6. Do you need a super signal tracer, a good signal generator, a fine oscilloscope, a wonderful set of pocket testgear to carry anywhere? You can build it with Nuplans. Each plan 2/6, or s.a.e. for list to Bradley, Whinnie Knowles, 6, Greenway, Ormskirk, Just Out—The Nuplans Valvetester!

AMAZING BARGAIN.—9/6. Complete kit parts for 3 W.B. superbet coil pack, including Yaxley Coils, Chassis, Trimmers, etc. I.F.T.s, 465-9/- pair. Eyelets tags, etc., 50 p.c. S.A.E. for list to Bradley, Whinnie Knowles, 6, Greenway, Ormskirk, P.F. 2d., 01 mica, 21d., Octal Amphenol valvetolders, 4/1. Send for cheapest list in England.—Sussex Electronics, Ltd., (P), Beveandean, Brighton, Tel.: 4446.

EVERYTHING for the wireless constructor. Send stamp for price list.—H. Tabner, 118, Nightingale Road, Hitchin, Herts.

EVERYTHING for Radio Constructors. Condensers, Coils, Valves, Resistors, etc. Send stamp for list.—Smith, 98, West End Road, Morecambe. Quick service.

TELEVISION KITS. Radio Kits and Complete Chassis. Amplifiers, 5-500 watts. Feeder Units. The complete range of Products for the latest 400-100 PF. 2d., 01 mica, 21d., Octal Amphenol valvetolders, 4/1. Send for cheapest list in England.—Sussex Electronics, Ltd., (P), Beveandean, Brighton, Tel.: 4446.

EVERYTHING for the wireless constructor. Send stamp for price list.—H. Tabner, 118, Nightingale Road, Hitchin, Herts.

EVERYTHING for Radio Constructors. Condensers, Coils, Valves, Resistors, etc. Send stamp for list.—Smith, 98, West End Road, Morecambe. Quick service.

TELEVISION KITS. Radio Kits and Complete Chassis. Amplifiers, 5-500 watts. Feeder Units. The complete range of Products for the latest 400-100 PF. 2d., 01 mica, 21d., Octal Amphenol valvetolders, 4/1. Send for cheapest list in England.—Sussex Electronics, Ltd., (P), Beveandean, Brighton, Tel.: 4446.

TELEVISION KITS. Radio Kits and Complete Chassis. Amplifiers, 5-500 watts. Feeder Units. The complete range of Products for the latest 400-100 PF. 2d., 01 mica, 21d., Octal Amphenol valvetolders, 4/1. Send for cheapest list in England.—Sussex Electronics, Ltd., (P), Beveandean, Brighton, Tel.: 4446.

ELECTRIC HAWAIIAN GUITAR: A real musical instrument which can be built successfully by YOU, from my complete data and drawings, 7/6 post free.—C. W. CRAIG (W), 48, High Street, Oatham, Rutland.

VALVES. Pen46 new and guaranteed only 9/11 each, 6d. post. 10 set phone kit, containing set of 6 phones and micro 2 control boxes (full of gear) and haversack in original packing, 12/11, post 1/4. 1 mA. meter M.C. new and boxed, 6/8 and Westinghouse 1 mA. meter bridge rectifier, new 5/11, post 6d. Amphenol wide range with 9 valves, 1/6 and P.O. transformer (P.P.), complete 5/-; 100. Aerials, telescopic feather-weight 9d. aerials collapses to 14in. at 5/11, post 9d. C.W.O., write or call (Saturday to 7.30 p.m.) for list for Radio, 36a, Dalston Lane, London, E.8.

YOUR ORDER despatched by return C.W.O. or C.O.D. The B.N.R.S. Service. A.C. 230-250 v. motor, 10 in. 75/-; Colloredo ditto 110-250 v. var. speed, and 12n.t.t. £5; ditto with universal autostop. 14n.6.3; Colloredo combined R/G Units with pickup and autostop for A.C. 110-250. Model A47, 12n.t.t. var. sp. £9; model RF49 rim-drive, 10n. 1n. £5.4s. 9d.; Garrard ditto (model "S"), £5 18s. 4d. Colloredo A.C./D.C. R/G Unit. £12 18s. 9d. Plessey, new, super-quick A.C. Mixed Record Changer with mag. pickup, our special offer, £18. Leaflet on request. Extensive constructional Manuals, enabling even beginners to build a 5-valve 3 waveband Superhet of exceptional power and range, A.C. only or A.C./D.C. model, 5/-; All-dry Battery model, 3/-. Special offer: The Gee Products 4-valve All-dry Battery kit complete 6in. speaker, only £6. F.E. Home-built Television, book 2/6. Parts list, 2/1d. Send 2/1d. for Bargain List of Kits, Components and range of Amplifiers 6-10-4-watt etc. 100 types. 100 types. 100 inputs, volume, tone and neg. feedback controls, operation A.C. 110-250 v. Special offer, £5 19s. 6d. Loudspeakers—high-flux p.m.s. 5in., 12/6; 6in. Celestion and P.A., 16/-; 8in. A.P. 18in. 26/-; Rotating transformers, 5/- extra; Wharfedale Golden 10in. 3r or 15 ohms 75/-; New surplus Valves, guaranteed: EF50, 7/6; EF36, EF39, EL32, ECH35, EBC39, 5Z4, 8/-; any 3, 22/6; 6K8, 6K7, 6Q7, 6V6, 6X5, 6SN7, KT3C, 6U4, 6X4, 6W5/500, 6V4, 25/6; 10/-; any 3, 27/-; 6L6, HV2, 12/6; PX25, 15/-; matched pairs supplied. Special offer of loose (tested 100%) valves: 6J5 or 6L3, 4/- each; 6 for 18/6. Electrolytics, 8 mfd., 350 v., 2/6; 8 or 16 or 16 in 640 v. set metal, 2/6; recs., 250 v., 40 mfd., 2/6. Three-wave Superhet Coil Packs—Osmor "Q" Coil Pack, 33/-;—N. R. S., 102, Parkhill Road, London, N.W.3. Gulliver 1453.

TELEVISION EXPERIMENTERS. Old-church Laboratories have everything you need. For those using the V.C.R.97 and similar tubes, we have introduced a special E.H.T. Transformer, delivering 2,000v. at 1 1/2 ma. and 4v. C.T. 2A. Price 30/-. V.R.91 and V.R.95 Valves, each 10n. Guaranteed perfect. Special components for "Electronics" Television, E. H. T. Trans., 65/-; Heater and H.T. Trans., 75/-; Focus Coils, 33/-; Adjustable Scanning Coils, 35/-; Complete Set of specified Dust Cored 15-7-15-7-15-7 Chassis, 8/6; set metal Base Chassis, 18/9; Vision Chassis, 22/6; Our T.S.74 and T.S.73 Conversion Data still in great demand. Price £1 for 4 Blueprints and Instruction Booklet. Our Versatile Transformers, as previously advertised, still available at 7/6 each. Send 2/1d. for our latest list.—L. P. Dismore, 52c, Oldchurch Road, Chingford, E.4.

ALL NEW REGULAR COMPONENTS. ELECTRONIC ENG. Television Chassis. complete all pieces, 47/8 10/-.

TRIMMOR A.V. Superhet 3 W.B., S.M.L. Coil Pack, 33/-; 2 W.B. M. and L. TRF Coil Pack, 30/-; Set of four TRF Coils, 12/-; All above with circuit. I.F. 465 kc/s Coils, 12/6.

TRIMMERS. Ceramic 50 P.F. single 6d., double 9d., three 1/-.

PADDERS. Double, 150 P.F. x 350 P.F., 30 x 250, 150 x 350, 750 x 750, 1/- each.

MIDGET SWITCHES. Superhet W.C. type 4F3W, TRF 2F2W. Gram-ratio 1P2W, 2/- 1/6 each.

DROPPERS. 3 a. 600 ohms, 750 ohms; 2 a. 1,000 ohms, 4/6; 15 a., 1,500 ohms, 4/9. Low heat type.

VCR97 35/- Oil-filled lens for VCR97 2/6.

CLEARANCE LINES.

50 ONLY A.C. Superhet Chassis, 5 v. A.W., S.M.L., with valves. Switched gram. input, 100-250 volts input, £10 each.

MAINS FILTERS. Double choke and condens. circuit, in metal case, 8/6 each.

YANLEY WAFERS 2P. 4W. 2P. 5W., 3d. each.

PHILCO A.C. Transformers, 230 v. input, 350 v. 2, 6.3v. and 5 v., chassis mounting, £1. 2/6; 11 W. BK. 3, 115-3-way 2/6.

PAX Coil Formers, 2in. x 1in., 2/-; 4in. x 1in., 4/- each.

SLYDLOC Panel Fuses, 5 amps., 1/6.

YANLEY WAFER SWITCHES, new, 11 W. BK. 3, 11 W. 4 BK. 6/6, NSF P. 10 W. BK. 6/6.

CARDED RESISTANCES, 24 6/2 to 220K assorted 1 and 1 w., 7/6 lot.

17H PANOLIN PANELS, Approx. 16in. x 4in., 13in. x 4in., 1/- each. Strips 13in. x 1in., 6d.

Please allow for packing and postage on orders under £5.

FRED'S RADIO CABIN, 77, Newington Butts, Elephant and Castle, S.E.11. Telephone Rodney 2190.

97/6. CHARGING SWITCHBOARDS. 12V/32V, 500 and 1,200 watts, volts, amps., 240 v. fuses, resistances, etc., 4 take-offs, superb unit, in case; or send £5 carriage paid.

75/- DYNAMOS, 24 volts, 1,000 watts, 9in. by 7in., 1in. spindle; 80/- carriage paid. 75/-, 230V/150, 15/h.p. ELECTRIC MOTORS, incorporating 1,250 cyclic converter; 80/- carriage paid.

58/- MAINS TRANSFORMER SWITCHBOARDS, 230V., A.C. to 12V., 5 separate take-offs, complete distribution panel, all switches, fuses, amps., etc., brand new, 60/- carriage paid.

55/- ELECTRIC MOTORS, 12v. and 24v., 1 h.p., 4in. by 8in., with 1in. spindle for drive, beautiful job; 60/- carriage paid. 70/- Reduction geared ELECTRIC MOTORS, 24v., 10 h.p., 2-stage, enclosed 2 r.p.m., superb precision instrument.

45/- DYNAMOTOR UNITS, containing 14v., 24v., 130v. and 300v. D.C. dynamo, or suitable as 6v., 12v. or 24v. motor, approx. 100 D.C. makes 100 v. with 24v. supply, small grindstone, mop, etc., also contain adjustable 24v. cut-out, 12v. automatic voltage control, smoothing condenser, resistances, etc., with 210.24 D.C. mains in the 100 D.C. makes 120 v. Battery charger, at the 14v. output, 14 amps., 50/- carriage paid.

£39 ROTARY MOTOR CONVERTERS, 220V. D.C. to 230V/150 A.C., 3 kVA. £19.10/- MAINS TRANSFORMERS, 5 24V. A.C. 115-230V., 50, 75, 100, 150, 200. From £4 ALTERNATORS, 230V./150, 11 to 10 kVA.; also separate D.C. GENERATORS, 500 watt, 12.35 v. to 7.5 kW., 110v. and 220v., new and unused.

12E.T. 200 W. Summerley Street, Earlsfield, S.W.18. WIM, 3833 (100 yds. S. Rly. Electric Line: 10 minutes Waterloo.)

CONDENSERS.—Valves—Speakers—18 + 16 mfd. at 500 v. D.C. at 3/6; 8 + 16 mfd. at 450 v. D.C. at 3/6; 16 mfd. at 3/-; .5, .25, 1, .0001 mfd. at 6d.; .0005 (variable) at 2/-; .0005 twin and triple gangs at 6/6. Speakers—5in. less transformer, 9/6; 6in. with transformer, 12/6; 6in. less transformer, 13/-; 6in. with transformer, 15/-; 8in. less transformer, 18/6; 8in. with transformer, 18/6; 10in. less transformer, 22/-; Valves—All our usual ones from 3/6.—Duke and Co., 219, High Lane, Hford, Essex.

10 H.V. 100 mA. CHOKES, 7/6; 115-230V. 10 H.V. Transformer, 50n. 1s. 1/6; 11W, 22/6; mains Transformers, tapped primary 250-0-250v. 80 mA., 0-4-6.3v. 4 a., 0-4-5v. 2 a., shrouded, 30/-; drop through, 29/6; filament Transformers, 0-4-6.3v. 4 a., 0-4-5v. 3 a., 20/6; mains Transformers for BC343, 30/-; BC459 31/6, BC.221 28/-; 8 mfd. 350 mA. RF Chokes, 5/-; 30 watt multi-ratio modulation Transformers, 45/-; medium-wave coil unit for BC453, with data, 10/-; Transformers and chokes manufactured to specification by following Service.—Carlton Coil-winding Co., Carco Works, Church Road, Birkenhead.

HIGH FIDELITY Speaker Bargains. Limited offer of Goodman's Axion Twin Cone 12n., 15-ohm, £7/17/6; T21205, Single Cone, 12n., 15-ohm, £6/2/6; Celestion P44, 12n., 3-ohm, 75/-; Wharfedale, 10in. Golden, 3r or 15-ohm, 75/-; All carriage paid, satisfaction guaranteed. All new components available at Gift Prices. State requirements for a keen quotation. Mail orders only.—Wilding, 43, Oxford Road, Felixstowe.

CLEARANCE.—Avometers Model 7, £17. Avominors Universal, £7 5s. 0d. Avominors D.C., £3 12s. 6d. Auto Valve Tester, £15. Hunts Capacity Analyzer, £15. All instruments brand new, perfect. Post free. C.W.O. please.—Young, 134, Old Shoreham Road, Southwick, Sussex.

REWINDS.—Radio Transformers repaired. Return post service C.O.D. only.—H. Pugh, Radio Rewind Service, Brithdir, Nr. Dolgellau, Mer.

REPAIRS to loud-speakers. Cones, coils and magnets altered or rewound. Output transformers, clock coils. No mains trans. accepted. Prices quoted. Satisfaction guaranteed.—L. S. Repair Service, 49, Trinity Rd., Upper Tooting, S.W.17. Closed Saturdays. Phone: Balham, 2359.

REWIND SERVICE.—Armatures, Gram. motors, Vacuum Cleaners, Drill and all small motor Transformers—Fields, Pick-ups, Speakers—New Cones and Speech Coils fitted—New Vac. Cleaners supplied. All work guaranteed and promptly executed. Special terms to the Trade. Send S.A.E. for Price List and Radio Spares.—A. D. S. 101, 3-5, Lichfield Road, Acton, Birmingham, 6.

I.F. TRANSFORMERS.—465 kc/s, iron core, 10" pair, Carriage paid.—W. Patrick, 229, Beconite Avenue, Bagenham, Essex.

LT77, quantity 27/38 EBCD for disposal, cheap. Stanwell & Leatherbarrow, Ltd., 6, Stanley Street, Liverpool.

12V. OAK Vibrators, UX4 Base, v.6512 2/6 each, Post Paid.—Electron Works, 6, East Ham, London, E.6.

24 hr. TELEVISION (not Radar Conversion). Uses V.C.R. 97 Tube. Send S.A.E. T.H. PRODUCTS, 92, Leatherwalk Rd., S.W.11, EAT. 4889.

WANTED.—Particulars and Indicator, CS-55ACB. Can any reader oblige?—Jackson, 40, Sutherland Avenue, Hull.

BARGAIN.—58 Set. All Accessories, Cost £19.10. As new, £16.—Carver, 90, Barnsley Road, Darfield, nr. Barnsley, Yorkshire.

R1116.—With Valves, Dipole, Phones, Accumulator. Good order, transit case. Offers.—Box No. 176.

ALUMINIUM chassis and Panels for all 10V. and your own designs. Holes punched for valveholders, etc. Estimates free. T.R.F. 2 waveband coil pack with circuit 12/6. 2 gang Condenser 9/9. Superhet coil packs, I.F.T.'s, etc., stamp for details. Note new address: EAD, 18, Broad Road, Lower Willingdon, Sussex.

CRYSTAL Microphone Inserts (Cosmocond Mic-4) Guaranteed Brand New, 12/6 post free.—Radio Aid, Ltd., 29, Market Street, Watford. Phone: Watford 5988.

SPLIT STATOR condensers 20 yf silver-plated ceramic mounted 2in. x 2in. x 2in. heavy construction, 250 disc, rotation, 100 yf ceramic mounted 2in. spindle, 1/6, postage extra.—Skillman, 63CSD, Franchise St., Weymouth.

TUITION

RADIO OR RADAR.—Full-time training for career in Air or Marine Services as Radio Officer (M.C.A. or P.M.G. Licences), Radio Mechanic, or Radio Engineer. Residential courses at Radio and Radar School, Britain's Air University, Enquiries to the Commandant, Air Service Training, Hamble, Southampton.

THE BRITISH NATIONAL RADIO SCHOOL (Estd. 1940) for New World Ideas and Old World Ideals! The Urge to Serve and the Knowledge How! Home Study Specialists with the Personal Tutor Radio, Radar, Maths, Physics. The B.N.R.S. Four Year Plan covers the full syllabus of A.M.I.E.E., A.M.Brit.I.R.E. and City and Guilds Radio and Telecommunications Exams. Six months' trial period without obligation to continue. Day classes in all subjects, including P.M.G., recommending shortly. Send for free booklet to:—Studies Director, British National Radio School, 66, Addiscombe Road, Croydon. (Phone: Addiscombe 3511).

WIRELESS.—Television, Postal Courses Radio Amateur Radio Transmitting Licence also Television for Radio Trades diploma. Apply British School of Telegraphy, Ltd., 179, Clapham Road, London, S.W.9. (Forty years' experience in training students in Wireless and allied subjects.)

WIRELESS (sea and air) TELEVISION, Broadcasting, Radar, etc., offer tremendous opportunities. Students, both sexes, are all upwards, trained for appointments in all branches of Radio. Low fees, boarders accepted, 2d. stamp for pros.—Wireless College, Colwyn Bay.

"RADIOCERTS." (Regd.)—Postal instruction in Wireless Telegraphy for Merchant Navy. Short course of coaching by experts.—"Radiocerts," "Radio House," 21, Manor Gardens, Holloway, N.7.

THE INSTITUTE of Practical Radio Engineers have available Home Study Courses covering elementary, theoretical, mathematical, practical and laboratory tuition in radio and television engineering. The text is suitable coaching matter for I.P.R.E. Service entry and progressive exams.; tuitionary fees at pre-war rates are moderate. The Syllabus of Instructional Text may be obtained, post free, from the Secretary, Fairfield Road, Crouch End, N.8.

A.M.I.Mech.E., A.M.I.E.E., City and Guilds, etc., on "No pass—no fee" terms. Over 95% successes. For details of Exams, and courses in all branches of Engineering, Building, etc., write for 108 page Handbook free.—B.I.E.T. (Dept. 242B), 17, Stratford Place, London, W.1.

Practical Television

Vol. 1. No. 1

NEW SERIES

MARCH, 1949

The Advance of Television

OLDER readers will remember our monthly journal *Practical Television*, which we published before the war but which was suspended owing to the war and the closing down of the B.B.C.'s television transmitters.

The time has arrived when readers of this journal are entitled to expect a greater proportion of television news and technical articles. For the science has advanced to a stage where it is quite within the ability of many radio enthusiasts to construct a television receiver for themselves.

We have, in fact, given a fair amount of constructional data in recent issues. It is thought, however, that there is sufficient movement in the television industry for such matter to appear under its own title and as a supplement continuing the work of the suspended journal, until such time as it is possible to issue it as a separate publication.

We may hope that the paper position, which has hampered the publishing trade and prevented the dissemination of technical knowledge for so long, may change in the not-too-distant future. But in the meantime this supplement is intended as a temporary stop-gap so that those readers whose main interest is in the visual programme may have a section devoted entirely to their interests. It is hoped, also, that the supplement will prove useful to those at present new to the science. We shall herein collect each month news of the television world, of new developments in this country and abroad, and we shall give constructional articles dealing with the building of television receivers.

Home-made Receivers

We have for some time past been experimenting with home-constructed television receivers and accumulating data for the assistance of our readers. The trade, too, discerning the trend, are now supplying components so that the old difficulty of obtaining the necessary parts has gone. It must not be presumed from this that a television receiver can be built with the same ease, facility and simplicity as with an ordinary broadcast receiver. The alignment of a television receiver is in itself a difficult task, calling for a fair amount of test gear and instruments.

We hope the guidance which will be given in this supplement will take the reader through those difficult stages, as we did in the earlier days of radio.

A Word of Caution

With television, high voltages are used, and we do not suggest that the construction of a television receiver should be lightly undertaken by the very unskilled. Moreover, the cost of the parts is still

high—the tube, of course, being the most expensive item.

We cannot expect any radical change in television broadcasting technique for some years. The B.B.C. policy has been clearly stated to be that of continuing the system which was in use up to the time of its cessation at the beginning of the war.

So readers may make, or purchase, a television receiver confident that it will not be made obsolete by some capricious change in the technical departments of the B.B.C.

The new Sutton Coldfield station is due to open this year, and it will carry the delights of the visual programme for the first time into the provinces. Other stations are planned still further to cover the country.

Our Midlands readers will therefore welcome this expansion of our editorial policy. We encourage suggestions from readers for articles, and we shall be happy to consider contributions from those who have experience of the subject.

We shall review the latest productions of manufacturers and advise our readers who prefer to purchase rather than make. The time is not far distant when television will outstrip ordinary broadcasting. At present the spread of television is hampered chiefly by finance, labour shortage, and the economic position. Manufacturers are at present expected to concentrate on exports and selling our wares abroad. They cannot concentrate on the production of goods intended only for the home market.

The supply of television receivers, however, is improving, and the number of viewers, according to the B.B.C. statistics, increases weekly. It is estimated that the total number of viewers in the area served by Alexandra Palace exceeds 70,000. That is approximately the number of television receivers which are in operation, so the viewing public will be at least three times that number. It is small, of course, measured against the background of ordinary listening, but it is here to stay and to expand, just as broadcasting did.

Newnes' Television Manual

We may usefully here draw the attention of television readers to *Newnes' Television Manual*, which costs 8s. by post. This forms a practical introduction to the subject. Now in its 7th Edition, it deals with all the known television systems and contains the list of terms agreed by the Television Committee of the Radio Manufacturers Association. Orders should be sent to the Book Department, George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

Underneath the Dipole

Television Pick-ups and Reflections.

By "THE SCANNER"

THE power of the professional critic is a very real one. The Letters of Junius, the trenchant views of Dr. Johnson, Pepys's Diaries, Ruskin's monographs and Agate's dramatic criticisms have their modern counterpart in the weekly comments of Shulman, Lejeune, Collie Knox, Marsland Gander, and others. Each has his following and a few of them have acquired a sense of power proportional to the vitriolic content of the ink in which they dip their pens. Many a promising play, book or film has been damned at the outset by the comments of a few journalistic camp followers of the arts. On the other hand, it must be admitted that there have been occasions when the critics' chorus of approval has had a most beneficial effect.

Too often, the newspaper critic is preoccupied with contriving a wisecrack, and in the process of so doing will cheerfully drive playwrights, publishers and film producers to desperation, drink or Carey Street. Some of them would metaphorically boil their grandmothers to achieve a smart line and are quite willing to risk a face-slap in the Savoy Grill or a legal battle in the Law Courts. Satiation has given them a point of view which is frequently far removed from public taste, for which they have the utmost contempt. They are, indeed, a law unto themselves.

Television Critics

It is not true to say that critics are unsuccessful exponents of the arts they criticize. St. John Ervine demonstrated his brilliance as a playwright, for instance, and Pat Mannoek has written many fine film scenarios. Critics, even film critics, have to live, however, and they are expected to say something more than, "I think it was very nice" in order to earn their pay-packets.

These ruminations, by the way, are neither a justification nor an excuse for the attitude taken in this article month by month, especially in respect of B.B.C. television. Praise and blame, bouquets and brickbats may creep into it from time to time, but such items are random reflections underneath the dipole. I have in mind the changing attitude of the lay press to television. Up to now there has been very little serious criticism of television in the daily and weekly newspapers, and comments upon individual television plays have usually been wedged into the last few lines of the radio correspondents' columns. But television has now well and truly arrived in the London area and is installed in nearly 100,000 homes—a fact which has been noticed by the London *Evening Standard*, which led the way with regular television comments and criticisms separate from the "blind radio" column. Of course, the radio correspondent of the *Daily Telegraph*, L. Marsland Gander, has given considerable attention to television for a long time, and even before the war his radio column contained many references, both technical and otherwise, which were well worth reading. Mr. Marsland Gander can, therefore, be looked upon as the first

television critic, with over ten years longer experience of the medium than any of the dozens of regular television critics now writing for the newspapers of Britain and America. The writings of some of the new critics will probably induce a smile or two from veteran viewers; but we wish them all the very best of luck—for their professional existence is a proof and a sign that television has well and truly arrived!

Large Screen Television

Up to now large screen television has been presented to paying audiences in the manner of a magician demonstrating the Indian Rope Trick. Many, many years ago, there were the stage demonstrations of Baird at the London Coliseum and, later on, at the Metropole Cinema, Victoria, where an attempt was made to reproduce the finish of the Derby before a packed audience. That was in the days of very-low-definition television, when miracles were accomplished with incredible hay-wire hook-ups, whizzing wheels and bull's-eye lantern optical systems. Big screen television is now an accomplished fact, and very rapid improvements in the results have been obtained in the last few months by Cinema Television, Ltd., and Pye Radio in England, and by R. C. A. in America. I don't think that big screen television will be put on in a London cinema again as a stunt; to start with, it will be installed in two or three Odeon cinemas, including a newsreel theatre, on a permanent basis, ready for relaying a big sporting event, such as a top-line boxing match. In the U.S.A., big screen television has been operated using the "hot" intermediate film process. The received picture and its associated sound is recorded on film, which passes immediately through developing, printing and fixing baths, and the resultant negative is scanned, electronically turned into positive and projected. The developing process is very rapid and the wet film is passed through a special gate which enables the picture (and sound) to be reproduced within five minutes. It is then speedily dried and is available to be circulated to other cinemas in the same district. Leading technicians in this country do not think this system very practical for the average cinema, quite apart from the heavy expense in film and highly skilled operating personnel. Scanning 25 frames per second, it uses 93ft. of expensive negative film stock per minute, pick-up and recording equipment for sound and picture, processing plant and developing solutions together with the special projectors for dealing with wet film; and last, but not least, the special enclosures and fire precautions insisted upon under the Cinematograph Films Act. R. H. Cricks, technical consultant of the *Kinematograph Weekly*, prefers the direct system, but considers that the British scanning standard of 405 lines to be too low for satisfactory big screen results. The French experimental system of 819 lines, in his opinion, is much nearer the mark. Transmission difficulties, including the huge band-width occupied, render

this standard impracticable at the moment, though fine results have been achieved on "closed circuit." It is probable that 625 lines will be adopted as the British cinema standard, and I understand that the Cinematograph Exhibitors Association have already applied to the authorities for six wavebands for cinema purposes—three for sound and three for picture. In any case, the film industry will undoubtedly insist upon complete independence from the B.B.C., with its own definition standards and wavelengths, to ensure that its transmissions are not available to the private home viewer. If these requests are granted, the cinemas will still be able to reproduce B.B.C. 405-line transmissions, and experimental apparatus is already existing which enables a

405-line picture to be re-scanned on 625-line equipment.

My own impressions of the Cinema Television Company's 405-line big screen results was mentioned in this article a month or so ago. I thought the results were first class, though it was quite obvious that the type of picture transmitted from the Alexandra Palace, designed for reproduction on small home screens, was cramped and suffered from a preponderance of close-ups. Within the next few months the British film industry will decide upon the standards to be used, and my forecast is 625 lines, with a likelihood of sequential scanning in place of interlaced scanning. The wave-bands to be allocated to cinemas? Well, your guess is as good as mine!

Latest Television Receivers

New Ekcovision Console

E. K. COLE, LTD., announce the release of Ekcovision Model TSC91—a high-definition television receiver incorporating the chassis of the popular Ekcovision Model TS46 in an attractive and substantial console cabinet of sapele mahogany.

Particular attention has been paid to the framing of the tube face in a neat plastic moulding round the inner picture mask. An exceptionally wide angle of vision is ensured. The entire cabinet can be easily moved, being mounted on large diameter concealed wheels under the plinth.

The features of the TS46 9in. tube chassis are already well respected throughout the television area—high sensitivity on both vision and sound, efficient suppression of interference, high standard of picture definition and tonal contrast, maximum reliability ensured by careful selection and pre-testing of components.


The main controls in the case of the console model are conveniently located in a recessed panel at the side. The chassis is very accessible for servicing. The price is £75 (including £13 18s. purchase tax).

Ekco are also releasing a new indoor television aerial—Model TA94. This consists of three rods already assembled on a base plate to which it is only necessary to connect the cable to the receiver


Installation cost and time is reduced to the absolute minimum. The aerial may be either screwed to a joist or can be hung from a beam if more convenient. A modified version TA94/1 is available for the Birmingham area. The price is 30s.

New Ultra Television Receivers

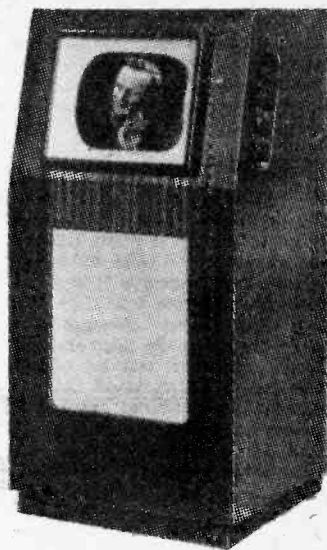THE latest television receivers produced by Ultra Electric, Ltd., comprise three console models. The largest of these new television receivers



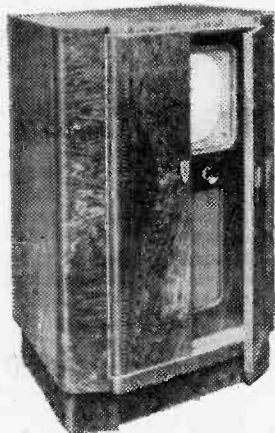The new Ekco Model TSC91, which has an exceptionally wide angle of vision, and a high standard of sound reproduction.



This new Ultra television receiver is characterised by the folding doors which conceal and protect the screen when the receiver is not being used.

is Model D.570 and is rightly described as "Television de luxe." It is of the superheterodyne type and employs a 12in. cathode-ray tube and 21 valves. Designed for operation on A.C. mains 200-260 volts (60 cycles), this model gives a pure black and white picture measuring 10in. by 8in., characterised by extra picture detail and particularly stable time bases. The chassis is constructed on the tri-unit principle, features being: automatic frequency control, automatic volume control on sound, new and improved time bases and noise suppression. The sound side is characterised by an 11½in. elliptical moving-coil loudspeaker, the audio output being 4.5 watts.

The magnificent cabinet is of hand-selected, figured and straight-grained walnut and has two perfectly matched, hinged doors. Brightness/on-off and volume are placed immediately below the screen, while four occasional controls are placed between them and concealed by a simple shutter. The glass view panel may be raised to facilitate easy access to the tube face and protective glass for cleaning purposes. The cabinet is mounted on smooth-running wide tread castors, the over-all dimensions being 41in. high, 28in. wide and 23in. deep.

Model D.5704 contains 22 valves, but is otherwise similar, and is specially designed for use on the fringe of the service area.

Prices are: Model D.570, £141 15s. 6d. (tax paid) and Model D.5704, £144 7s. (tax paid).

Console Model W.570 is technically similar to model D.570, and the fringe area model W.5704 is technically similar to model D.5704.

The cabinet, however, is without doors and has selected straight-grained and figured walnut front

and top panels. The black and white picture is 10in. by 8in. and the cabinet is provided with smooth-running wheels, the over-all dimensions being 37in. high, 20in. wide and 18in. deep.

Prices are: Model W.570, £90 4s. 6d. (tax paid) and Model W.5704, £92 16s. (tax paid).

Model W.470 is somewhat similar in appearance to Model W.570, but is slightly smaller, the black and white picture being 7½in. by 6½in. It is of the superheterodyne type and employs 20 valves (21 in Model W.4704), and incorporates tri-unit chassis construction with automatic frequency control, automatic volume control on sound, new and improved form of time bases and noise suppression.

The walnut-finished cabinet has carefully selected, figured and straight-grained panels in front and on top. The over-all size is 33in. high, 18in. wide and 18in. deep, and the cabinet is fitted with smooth-running wheels. Prices: Model W.470, £77 6s. 8d. (tax paid), Model W.4704, £79 18s. 2d. (tax paid).

World News and Views

Russian Progress

IT is reported in a European technical journal that the Soviet Union claim that by the end of this year a large number of television stations will be in operation, including some radiating pictures in colour. No technical details are given, nor is there any indication as to the types of receiver which will be available to the public.

Dutch Projection System

THE Philips Company of Holland are using a new system for the projection of pictures in the domestic receiver. The tube end is made to project through a plane mirror set at 45 deg. and the image on the tube end is thrown back on to the mirror by a concave mirror in front of the tube. The reflected image is then directed upwards from the plane mirror through a Schmidt correcting-plate and is finally seen on a cloth screen which is drawn up when the lid of the cabinet is raised. The system permits of the use of a more or less standard size cabinet housing an ordinary all-wave radiogram, but providing a picture approximately 12in. by 10in. The actual image on the tube in this case is about 1½in. by 1¼in.

Children's Television Competition

THE result of the recent Children's Television Competition was announced recently in "Picture Parade."

The first prize, a television receiver, was presented by Mr. G. W. Godfrey, Chairman of the Television Promotion Committee of the Radio Industry Council, in conjunction with Miss Joan Gilbert, Editress of "Picture Page," to thirteen-year-old Barbara Nichols, 54, Harvey Road, N.3.

The competition was sponsored by the British Radio Equipment Manufacturers' Association as part of the "Better Listening" campaign held in September.

Second prize, a table model radio receiver, was won by twelve-year-old Elizabeth Wiggins, 6, Cloudesley Place, N.1, and a personal model radio receiver, third prize, went to Gillian Osborne, aged 12, 1, Kenmore Drive, Mitcham, Surrey.

Need for Trained Technicians for Television Servicing

THE need for trained technicians to service the increasing number of television receivers was the keynote of an address by Max F. Balcom, president of the Radio Manufacturers' Association and vice-president and treasurer of Sylvania Electric Products, Inc., to a town meeting of radio technicians held at Hotel Bradford recently.

"The radio technician to-day," he said, "is one of the most important factors in the rapidly expanding television field. Unless the television set owner can get proper servicing, he may soon lose his initial enthusiasm for this new medium for home entertainment. A shortage of qualified television servicemen may prove to be a deterrent to television set buying and thus reduce receiver production and sales."

"Suicide on Wheels"

THIS was the description given to television receivers in cars by the National Safety Council of America last month. "Keeping one's eye on the road ahead and on traffic behind and on both sides is the first essential of safe driving," a council statement said. The council said its staff would make a further study of television installations visible to passengers only.

Television for Export

BRITISH Television manufacturers are actively contacting many overseas Governments to secure contracts for installation of British Television Transmission Equipment in preference to foreign systems. Acceptance of British Television System would probably result in considerable subsequent sales of British Television receivers.

The E.M.I. Television System, as used here by the B.B.C., created tremendous interest amongst Dominion and foreign visitors during the Olympiad broadcasts. An illustrated folder featuring the outstanding efficiency of the British System on this memorable occasion, is being circulated throughout the world.


Further information on this subject, if required, can be obtained from the E.M.I. at Hayes, Middlesex.

Fault Finding Simplified

The New Taylor

CIRCUIT ANALYSER Model 20A

The 20A traces the signal through the receiver stage by stage from aerial to loudspeaker. A midget pentode detector is contained in the probe, used for R.F. oscillator and I.F. checks, followed by an amplifier and loudspeaker in the instrument with a "magic eye" to give visual indication of signal strength. The latter is used for D.C. checking on A.V.C. lines or oscillator self-bias. For A.F. Checking the input is taken directly to the amplifier which can be switched to feed either the loudspeaker or the magic eye. The selector switch enables the internal speaker to be used for test purposes either as a low or high impedance speaker. A.C. mains operated, 110 volts and 200/250 volts, 40/100 c.p.s.

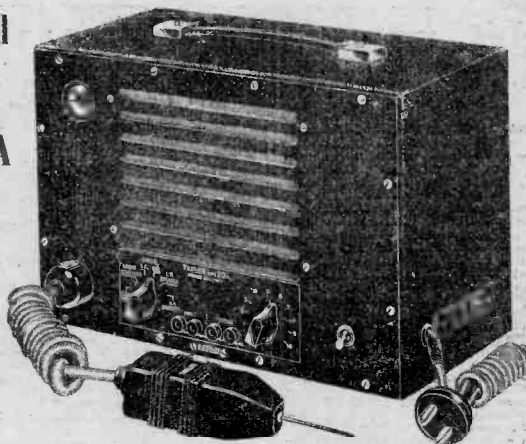

PRICE **£15.15.0** H.P. TERMS: £1. 10. 5 DEPOSIT & 11 MONTHLY PAYMENTS OF £1. 10. 2.

IMMEDIATE DELIVERY

TAYLOR PRODUCTS INCLUDE: MULTIRANGE A.C. D.C. TEST METERS • SIGNAL GENERATORS • VALVE TESTERS • A.C. BRIDGES • CIRCUIT ANALYSERS • CATHODE RAY OSCILLOGRAPHS • HIGH AND LOW RANGE OHMMETERS • OUTPUT METERS • INSULATION TESTERS • MOVING COIL INSTRUMENTS

TAYLOR ELECTRICAL INSTRUMENTS LTD
419-424 MONTROSE AVENUE, SLOUGH, BUCKS. ENGLAND

Telephone SLOUGH 21361 (4 lines)
Grams & Cables TAYLINS SLOUGH

PREMIER RADIO CO.

MORRIS & CO. (RADIO) LTD.

MOVING COIL EARPIECES. Comprise a 1 1/2 in. Moving Coil Loudspeaker fitted with noise excluding rubber caps. Make excellent Mikes, Phones or Speakers, 2/- each, 18/- doz.
PLESSEY AUTO CHANGER with magnetic pick-up. A.C. 200/250 v. 8-records mixed. £18/8/8.
GARRARD ELECTRIC GRAMOPHONE UNIT with magnetic pick-up, A.C. 100/250 v. £5/19/6. Collaro Auto Changers with magnetic pick-up, A.C. 100/250 v. £22/4/4.
COLLARO ELECTRIC GRAMOPHONE UNIT with magnetic pick-up and auto stop, A.C. 100/250 v. £8/13/6. With crystal pick-up, £11/2/2.
COLLARO ELECTRIC GRAMOPHONE MOTOR with 12in. turntable. A.C. 100/250 v. £5/13/4.
CONRAD ELECTRIC GRAMOPHONE MOTOR, 9in. turntable, 200/250 v. A.C. £7/6.

All above motors include Purchase Tax.
COLLARO AUTO CHANGERS. Mixer/Changer Rim Drive. High fidelity crystal pick-up. Repeat reject mechanism. £14/8/8.
COLLARO A.C./D.C. GRAMOPHONE MOTORS, with turntable but without pick-up or auto stop. £5/5/6.
H.T. ELIMINATOR AND TRICKLE CHARGER KIT. Consists of a complete kit of parts to construct an H.T. Eliminator with an output of 120 v. at 20 mA. and provision for Trickle Charging a 2 v. Accumulator. Two Metal Rectifiers are employed. With circuit. 35/-.

SPECIAL OFFER OF ELECTROLYTIC CONDENSERS.

15-16 mf. 500 v. working Cardboard	4/11
8+8 mf. 500 v. " "	4/11
32+32 mf. 350 v. " All Cans	5/11
32 mf. 350 v. " " "	2/6
16 mf. 350 v. " " "	2/6
16 mf. 450 v. " Cardboard	3/9
8 mf. 450 v. " " "	3/-
4 mf. 500 v. " " "	2/-
10+8 mf. 450 v. " All cans	4/11

MINE DETECTOR PANELS. include three IT4 valves, 12-1 Midget Trans., three ceramic valveholders, 18 condensers and resistors, etc., 20/-. Without Valves, 5/-.

WIRE WOUND RESISTORS. 50K 200 watt, 4/-, 20K 200 watt, 4/-, 2K +12K 150 watt, 4/-, 75K 100 watt, 4/-, 350 ohms 75 watt, 2/-, All vitreous enamelled.

GOVERNMENT SURPLUS MAINS TRANSFORMERS. All are for use on 250 volt 50 cycle Mains.

Type 33 38 v. 2 a. Tapped at 32, 34, 36 v.	15/-
42 500-0-500 v. 170 mA 4 v. 4 a.	25/-
44 10 v. 3 a., 10 v. 5 a., 10 v. 5 a.	25/-
50 12 v. 70 a. An Ideal Transformer for soil heating or welding	60/-
51 350-0-350 v. 60 mA., 6.3 v. 1 a., 6.3 v. 2-5 a.	12/6
53 250+250 v. 60 mA. 5 v. 2 a., 6.3 v. 2-3 a.	15/-
54 275+275 v. 60 mA. 5 v. 2 a., 6.3 v. 2-3 a.	15/-
55 250+250 v. 100 mA., 5 v. 2 a., 6.3 v. 2-3 a.	17/6
56 330+330 v. 70 mA., 5 v. 2 a., 6.3 v. 2-3 a.	17/6
57 300+300 v. 70 mA., 4 v. 2 a., 4 v. 3-5 a.	17/6

LOUDSPEAKERS BY FAMOUS MAKER

5in. P.M. 2-3 ohms	10/11	10in. P.M. 2-3 ohms	23/6
6in. " 2-3	16/6	12in. " 16	35/-
8in. " 2-3	17/6		

TELEVISION MAGNIFYING LENS. Suit any 5in. Cin. or 7in. tube. Increase picture size considerably. 29/6.

FERRANTI AF3C P.V. DRIVER TRANS. Split Sec., super quality, 10-12. Tank Aerials. Seven 2 1/2 lengths of tube which fit into each other, making a very efficient aerial. 2/6 each. Rubber Bases to fit 2/6 each.

NEW 2-VALVE ALL WAVE KIT. 16 to 2,000 metres. Switched Coil. Pack ready wired and tested. 2 Mazda H.E.3 Valves, Phones, H.T. and L.T. Batteries, Condensers, resistors, diagrams and steel case, all ready to assemble. £3/10/-, including Purchase Tax.

NEW 1948 MIDGET SUPERHET RADIO KIT, with Illuminated Glass F Dial. All parts, including Valves, M/C Speaker and instructions, 4 valves plus Metal Rectifier. 16-30 metres and 200-557 metres. 200 to 250 v. A.C. or A.C./D.C. mains. State which is required. Size, 10in. x 6in. x 6in., £8/5/-, including Purchase Tax.

MIDGET RADIO CABINETS in Brown Bakelite. Can be supplied for the above Midget at 25/-, including P.T.

NEW MIDGET T.R.F. RECEIVER. Special offer of completely built and tested T.R.F. Receivers in bakelite cases. Medium and Long Wavebands. Size, 12in. x 6in. x 6in. Two models are available, in A.C. and an A.C./D.C. Both for 200-250 v. mains. These are offered at the pre-war price of £7/19/6, including Purchase Tax.

POST ORDERS TO 167, LOWER CLAPTON RD., E.5. 'Phone : Amherst 4723.
CALLERS TO 152/3, FLEET ST., E.C.4. Central 2833.
NEW BRANCH : 207, EDGWARE RD., W.C.2. Ambassador 4033.
This Branch is open until 6 p.m. on Saturdays.

Our 1948 List is available. Please send 2d. stamp for copy.