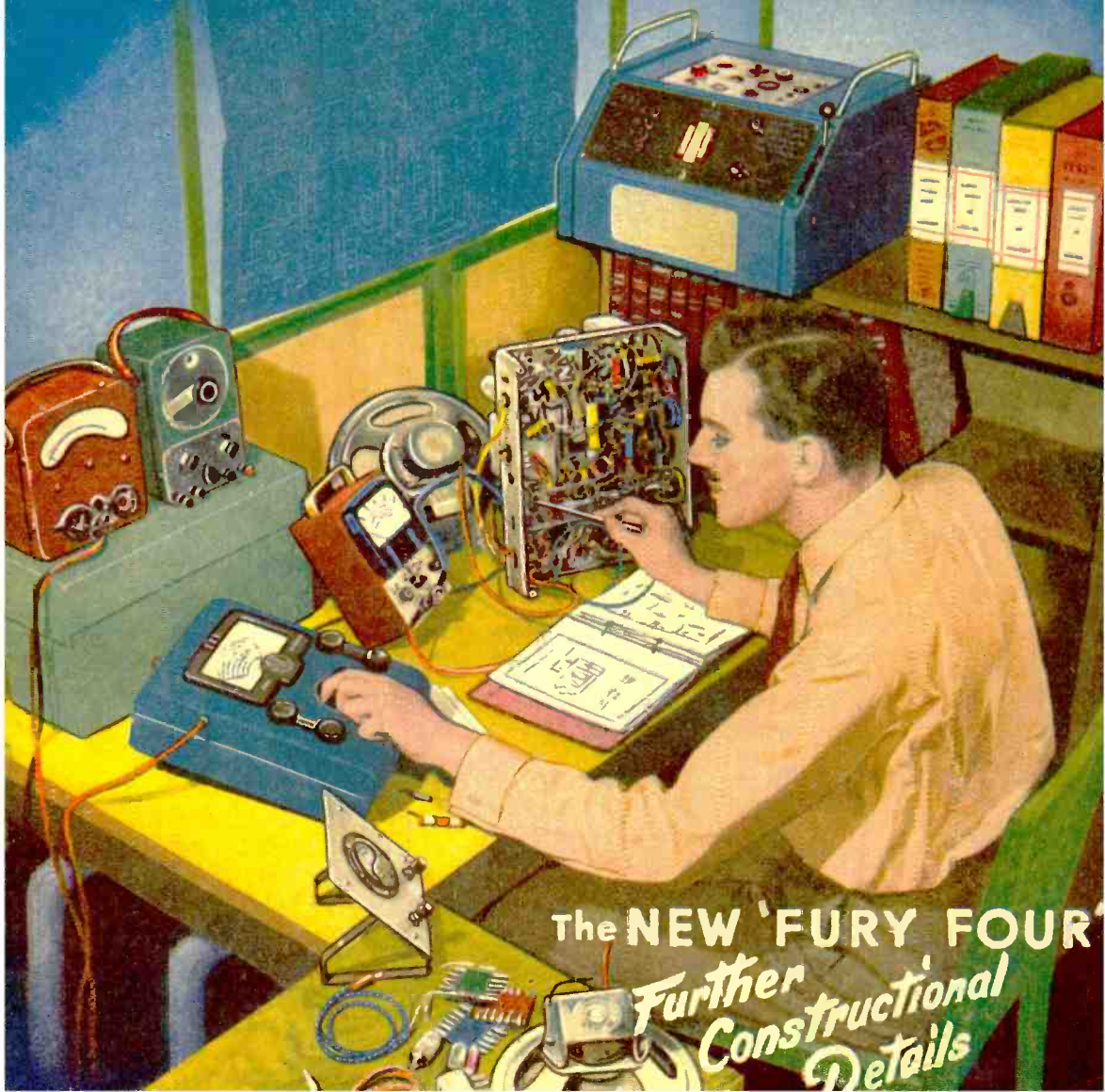


• USING TEST INSTRUMENTS •

PRACTICAL WIRELESS

JANUARY
1955
EDITOR: F.J. CAMM









The NEW 'FURY FOUR'
*Further
Constructional
Details*

Bring your equipment up to date with **ACOS** REPLACEMENT PICK-UP HEADS

If you already own a fine radiogram or record-player you now have the opportunity of rejuvenating it — of bringing it right up to date for a quite modest sum. Acos Hi-g crystal pick-ups are now available in a range of specially designed "plug-in" models to suit most famous makes of record reproducing equipment.

These Acos "Hi-g" pick-ups, you will find, represent a truly phenomenal advance in pick-up design — with regard to both reproduction and tracking characteristics (so important with many of the new microgroove recordings). Ask your Dealer!

MODEL		
HGP 37-1 Collaro		A Hi-g pick-up head incorporating the HGP 37-1 turnover cartridge with cantilever sapphire styli. Designed for both standard and microgroove records. Will fit Collaro units RC 532 : AC 534 : AC3/534 : 3RC 532 and the Studio pick-up. Available in cream or walnut. <i>Ask for Data Sheet No. 4800.</i>
HGP 37-1 Garrard		A Hi-g pick-up head incorporating the HGP 37-1 turnover cartridge with cantilever sapphire styli. Designed for both standard and microgroove records. Will fit Garrard units RC 75M : RC 80M : RC 90 : RC 111 : Model TA. <i>Ask for Data Sheet No. 4800.</i>
HGP 39-1		Hi-g pick-up heads incorporating cantilever sapphire styli. Separate heads for standard and microgroove records. Will fit the Acos GP 20 pick-up arm and the Garrard C type adaptor. Used on the following units: RC 72A ; RC 75A ; RC 80 ; and the Model M unit. Can be used on any units which at present use the GP 19 heads. <i>Ask for Data Sheet No. 4400.</i>
HGP 35-1		Separate plug-in type Hi-g heads for standard and microgroove records ; fitted with cantilever sapphire styli. The crystal unit is identical to that of the HGP 39-1 above. Can be used on Garrard units RC 75M ; RC 80M ; RC 90 ; RC 111 ; and the TA player. <i>Ask for Data Sheet No. 4000</i>
HGP 41-1		Separate Hi-g plug-in type heads for standard and microgroove records incorporating the crystal unit as used in the HGP 39 pick-up head. Will fit Collaro units RC 532 ; AC 534 ; AC3/534 ; 3RC 532. Available in cream or walnut. <i>Ask for Data Sheet No. 4500.</i>
HGP 45		Separate Hi-g pick-up heads for either standard or microgroove records. The crystal unit is identical to that used in the HGP 39-1 head. Will fit Garrard units RC 80 ; RC 72A ; RC 75A ; and the Model M player. Can be used on any unit which at present uses the Garrard C adaptor with GP 19 heads. <i>Ask for Data Sheet No. 4600</i>



... always well ahead

PRICE 32/6 (PLUS 10/5 P.T.)
for all types except HGP 39
models which are
32/- (PLUS 10/3 P.T.)

ACOS devices are protected by patents, patent applications and registered designs in Great Britain and abroad.

COSMOCORD LIMITED ENFIELD MIDDLESEX


BUILD THIS HIGH QUALITY LOW COST AMPLIFIER

★ Circuit designed by Mullard research engineers.

★ Specified components available from most radio dealers.



Here's an entirely new amplifier circuit which brings high quality sound reproduction within the reach of thousands more enthusiasts. It has been designed by Mullard research engineers with special regard for easy construction and low cost. Full details of the circuit are included in the 2/6 book which is obtainable from radio dealers or direct from Mullard Ltd. Valve Sales Department—2/10 post free. Get your copy now.

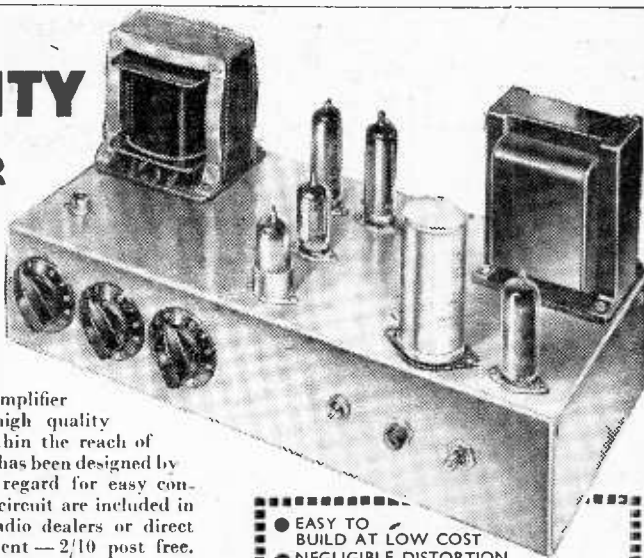

- EASY TO BUILD AT LOW COST
- NEGLIGIBLE DISTORTION AT ALL OUTPUT LEVELS
- UNIFORM FREQUENCY RESPONSE IN AUDIBLE RANGE
- GOOD TRANSIENT RESPONSE
- LOW OUTPUT RESISTANCE
- LOW HUM AND NOISE
- DESIGNED ROUND 5 MULLARD MASTER VALVES — EF86, ECC83
2 x EL84, GZ30 or EZ80

Mullard



MULLARD LTD., CENTURY HOUSE, SHAFTESBURY AVENUE, LONDON, W.C.2


MVM308A

MAXI-Q

REGD.

We GUARANTEE these seven Coil Packs to be the finest of their class in the Country. Mechanical precision, design and technical performance unsurpassed

CP.4/L & CP.4/M

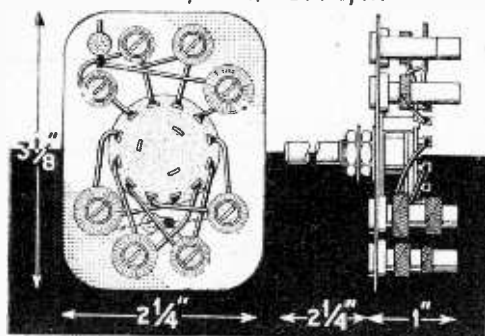


These compact 4-station Coil Packs are available for use with — 1 Long wave and 3 Medium wave stations (CP.4/L) or 4 Medium wave stations (CP.4/M). They are fully wired and require only four connections for use with any standard frequency changer valve.

Retail Price of each unit : 25/-, plus 8/4 P.T.—Total 33/4. With Gram. Position : 31/- plus 10/4 P.T.—Total 41/4.

Send 1/- in stamps for General Catalogue. Obtainable from all reputable Stockists or in case of difficulty direct from works.

CP.3/370 pF. & CP.3/500 pF.

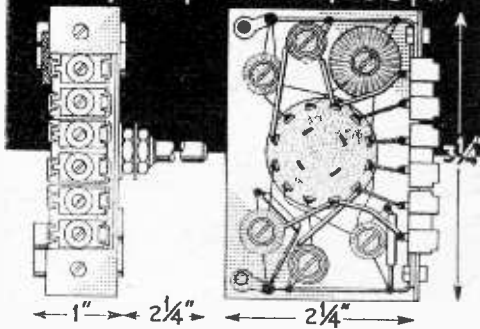

These 3 waveband Coil Packs are available for use with either 370 pF or 500 pF tuning condensers. The coverages are : Long wave 800-2,000 metres, Med. wave 200-550 metres, Short wave 16-50 metres. Designed for use with Jackson Bros. Full Vision Drive or SL.8 Spin Wheel Drive. Retail Price of each unit :

32/-, plus 10/8 P.T.—Total 42/8. CP.3/G with Gram. Position suitable for use with 500 pF tuning condenser :

39/-, plus 13/- P.T.—Total 52/-.

DENCO (CLACTON) LTD., 357/9 OLD ROAD, CLACTON-ON-SEA

STOP PRESS : "Mullard" "Five-Ten" High Quality Amplifier Chassis, 14/6. Bronze Front Panel for same, 6/6. "Osram" "912" Amplifier Chassis, 14/6. Bronze Front Panel, 6/6.

HENRY'S (RADIO LTD.)

We have over 20,000 American and B.V.A. valves in stock ALL VALVES NEW AND GUARANTEED

SETS OF VALVES

Ten EF50 (Ex-Brand New Units), 5/- each ... 45/- Set

6K8G, 6K7G, 6Q7G, 5Z4G, 6V6G ... 37/6 ..

1R5, 1S5, 1T4, 1S4, or (3S4 or 3V4) ... 27/6 ..

TP25, HL23/DD, VP23, PEN25 (or QP25) ... 25/- ..

6K8G, 6K7G, 6Q7G, 25A0G, 25Z5 or 25Z6G, ... 37/6 ..

12K8GT, 12K7GT, 12Q7GT, 35Z4GT, 35L6GT or 50L6GT 37/6 ..

12A7GT, 12S3K7GT, 12S07GT, 35Z4GT, 35L6GT or 50L6GT 37/6 ..

CRYSTAL MICROPHONE INSERTS

8/6  **8/6**

POST FREE

Ideal for tape recording and amplifiers. No matching transformer required.

Brand New R.F. UNITS

RF24 20-30 mcs 15/- post free

RF25 40-50 mcs 18/6 post free

RF26 50-65 mcs 35/- post free

1A5GT	10/-	6AK5	9/-	35Z4GT	8/6	TD2A	8/6	PCC81	12/6
1A7GT	12/6	6J7G	6/6	35Z5GT	8/6	DK40	11/-	PCF82	12/6
1R5GT	11/-	6K7G	6/6	25A6	8/6	UL41	11/-	PEN25	6/6
1LD5	7/6	6K8G	9/-	35L6GT	8/6	UY41	11/-	PEN46	7/6
1S4	7/6	6L6G	10/-	50L6GT	8/6	D41	5/-	QP25	6/6
1S5	7/6	6U5	7/6	42	8/6	KT2	5/-	SP61	4/-
1S5	7/6	6N7GT	7/6	43	8/6	U52	8/6	SP41	4/-
1T4	7/6	6Q7GT	8/6	75	8/6	U19	10/-	HL23/DD	6/6
1C5	8/-	6S1JGT	8/6	80	8/6	V63	8/6	VP23	6/6
3A4	9/-	6X3G	8/6	866A	15/-	MU14	8/6	VP41	7/6
3V4	7/6	6SA7GT	8/6	T240	37/6	PL81	11/-	U22	8/6
3S4	12/6	6S07GT	8/6	931A	50/-	PL82	10/-	ATP4	4/6
5Z3G	8/6	6S6GT	7/6	EA50	2/-	PX25	12/6	TP22	8/6
5U4G	8/6	6S8K7GT	7/6	ECH35	12/-	PY81	10/-	TH23	10/-
5Z4G	8/6	6SL7GT	8/-	EF34	6/-	PY82	8/6	41MP	7/6
6A7G	8/6	6SN7GT	9/-	EB34	3/6	KT33C	10/-	42SP7	6/-
6AC7	6/6	6S7GT	10/-	EBC33	8/6	KT66	12/6	21SSG	4/6
6A9G	8/6	6V8GT	7/6	EF36	6/6	GU50	12/6	MS/PEN	7/6
6AM6	9/-	6AG7	12/6	EF39	6/6	XP2V	4/-	MS/PENB	7/6
6B8	7/6	12K7GT	8/6	EF31	12/-	4/6	1.5	4/6	7/6
6C5GT	5/-	12K8GT	8/6	EK32	6/6	VU111	4/-	VT501	7/6
6C6	6/6	12Q7GT	8/6	EF91	9/-	VU133	4/-	AC/PEN(7)	7/6
6D6	8/6	12SA7GT	8/6	EL33	10/-	VU120A	4/-	10/-	10/-
6F6G	8/6	12S3K7GT	8/6	EL32	7/6	QP230	8/6	PENDD4020	12/6
6G6T	6/6	12S3J	8/6	EF50	10/-	VR105/30	8/6	FC13C	10/-
6H6GT	5/-	12S3K7	8/6	Red Syl.	10/-	VR150/30	8/6	VP4(7)	8/6
6J3GT	5/-	12SR7	7/6	EF50	5/-	CK510AX	5/-	ID5	8/6
6J6	9/-	25Z6GT	8/6	SP2	8/6	DI	2/-	EP80	8/6
6L7	7/6	25Z5	8/6	VP2	8/6	AC06EN	6/6	ECL30	10/6

MORSE PRACTICE BUZZER

Complete with tapper and 4 volt buzzer on baseboard. 6/-, brand new. Post paid.

R.F. OSCILLATOR COIL UNIT

6-18 kv., including EX51 valve. 37/-.

CRYSTALS

200 kc/s, 2-pin (U.S.A.) ... 10/-

465 kc/s, 2-pin (U.S.A.) ... 10/-

500 kc/s, 2-pin (British) ... 15/-

T.C.C. 1.5/7,000 v. wkg.

Type CP5800. Bakelite Case. 7/6 each.

INDICATOR UNIT TYPE 182A

This unit contains VCR517 Cathode Ray Sin. tube, complete with Mu-metal screen, 3 EF50, 4 SP61 and 1 5U4G valves, W/F volume controls, resistors and condensers. Suitable either for basis of T.V. or Oscilloscope. "Radio Constructor" Scope constructional circuit included. 67/6 (plus 7/6 carr.).

Kit of necessary parts, including "182A" Unit, for constructing "Radio Constructor" Oscilloscope. **£8/18/5.**

CATHODE RAY TUBES (Brand New)

VCR97 (slit cut-off) 15/-

VCR97, guaranteed full T.V. Picture ... 40/-

VCR17C, guaranteed full T.V. Picture ... 35/-

VCR199A, guaranteed full T.V. Picture ... 35/-

3BP1, guaranteed full T.V. Picture ... 30/-

Carr. & packing on all tubes. 2/-.

DINCO P.M. FEEDER UNIT

Finest Audio available. Complete kit of parts, including drilled chassis. 5 valves: types 6AM6, 12AH8, EB81 and 2 6AB9. Also complete circuit and wiring diagram. **£6/7/6.**

Or assembled and aligned. **£8/10/-.** Alignment only. 7/6. Demonstration daily.

8-page Catalogue, 3d. Open Mon.-Sat. 9-6. Thurs. 1 p.m.

5 HARROW ROAD, PADDINGTON, LONDON, W.2 TEL: PADDINGTON 1008/9, 0401.



ALPHA

INVITE YOU TO BUILD THIS PORTABLE FOR ONLY

6 1/2 GNS.

Full details, circuit diagram, point to point wiring instructions, and complete list of components. Available 2/- ea. Case can be supplied separately. Available in the following attractive colours:

- Lizard Grey;
- Blue;
- Maroon;
- Brown.

Dial, 1/3 each. Chassis, 3/-.

VALVES GUARANTEED AND BOXED

0Z4	6/-	6A75	9/-	6K7G	6/-	7H7	8/-	12Q7GT	9/-
1A3	9/-	6AK5	9/-	6K7GT	6/6	7Q7	8/6	12R6T	7/6
1A6GT	6/-	6AL5	7/6	6K7M	6/6	7R7	8/6	12RH7	5/6
1C5GT(DL35)	6/6	6AM6	7/6	6K8G	9/-	787	8/6	12S17	8/6
1L4 (DF93)	7/6	6AO5	8/6	6L6G	9/6	7Y4	9/6	12SK7	6/6
1LD5	6/6	6AT6	8/-	6L7M	7/6	77	8/6	12SO7	8/6
1R5	7/6	6B4	6/-	6L18	11/-	80	8/6	12SR7	7/6
1R4	7/6	6B8G	4/-	6N7	7/6	807	7/6	20D1	10/6
1R5	7/6	6B4G	8/6	6Q7G	9/6	812	2/6	20F2	12/6
1T4	7/6	6B6G	8/-	6Q7GT	9/-	9001	5/6	20I1	15/-
1U5	8/-	6BR7	9/6	6R7G	8/-	9002	5/6	25AR3	9/-
220V8G	6/6	6BW6	8/6	6SA7GT	8/6	9003	5/6	25L6GT	8/6
243	6/6	6C4	8/-	6S17	7/6	9004	5/6	25U4GT	12/-
2X2	5/-	6C5GT	7/6	6S17	6/6	9006	6/-	25Y5	9/6
3A4	8/-	6C6	6/6	6S74T	8/-	954	2/-	26Y6G	9/6
304	9/-	6C9	8/-	6SK7	6/3	955	4/6	25Z4G	9/6
305	10/-	6D3	7/6	6SL7	8/-	956	3/6	25Z5	9/6
316	5/-	6D6	7/6	6SN7GT	9/-	10P1	10/-	25Z6GT	8/6
384	8/6	6F6G	7/6	6S07	8/-	10L1D11	11/-	35L6GT	8/6
3V4	8/6	6F6G	8/6	6S67	8/-	10P13	11/6	35V4	10/-
4D1	3/-	6F8G	7/-	6S7T	7/6	10P14	11/6	35Z4GT	8/6
42	8/-	6F13	12/6	6U4GT	15/-	12A6	6/6	50L6GT	8/6
5R4	9/6	6P15	11/6	6U5G	8/6	12AH8	11/6	AC/P	6/6
5T4	8/6	6P8G	6/6	6U7G	9/-	12AT7	9/-	AC/PEN	5/6
5Y3GT	8/6	6Q6G	3/6	6V6G	7/6	12A7	9/-	ATP4	6/6
5Z3	3/6	6J6G	5/-	6V6GT	7/6	12AX7	10/-	CL33	12/6
5Z4G	8/6	6J5GT	5/6	6X4 (U78)	8/-	12C8	8/6	CV71	10/-
6A7	10/-	6J5M	6/6	6X8GT	7/6	12H6	5/-	CV12	10/-
6A8G	10/6	6J6	8/-	7B7	8/6	12J5	6/6	CV28	7/6
6A9T	6/6	6J7	8/6	7C5	8/6	12K7	9/6	DH73M	10/-
6A15	7/6	6K6GT	6/6	7C6	8/6	12K8GT	9/6	EB41	11/-

THE COMPACT TELEVISION AERIAL BY ANTIFERRENT LTD.

Supplied complete with universal mounting and backplate in neutral brown finish. Overall length 5ft. 6in. Packed in carton 3ft. 4in. long. Complete with full instructions. Cat. No. CD4. Original price 50/-. Our price..... 2/6

Post, etc., 2/6.

TERMS: Cash with order or C.O.D. Postage and Packing charges extra, as follows: Orders value 10/- add 9d.; 20/- add 1/-; 40/- add 1/6; 25 add 2/-, unless otherwise stated. Minimum C.O.D. fee and postage 2/6

WHEN ORDERING PLEASE QUOTE "DEPT. P.W."

MAIL ORDER ONLY

ALPHA RADIO SUPPLY CO.

5/6 VINCES CHAMBERS, VICTORIA SQUARE, LEEDS 1.

Positively the 2 BEST T/Vs yet built for the Home Constructor!

The STERN'S "TELE-VIEWERS"

5 CHANNEL SUPERHET RECEIVERS

Suitable for any transmitting channel and for which commercial adaptors will be available.

PERFECT PICTURE QUALITY

SIMPLE DIAGRAMS MAKE CONSTRUCTION EASY



PERFECT FRINGE AREA RECEPTION

BETTER RECEPTION AT HALF COMMERCIAL COST

The "WIDE-ANGLE" TELE-VIEWER


* This is the most efficient large screen TV yet offered to constructors.

* Excellent Time Base efficiency producing 15 to 16 Kv with ample scanning power for C.R.T.'s up to 17 inch.

CAN BE COMPLETELY BUILT FOR

£33 - 0 - 0

(Plus cost of C.R.T.)

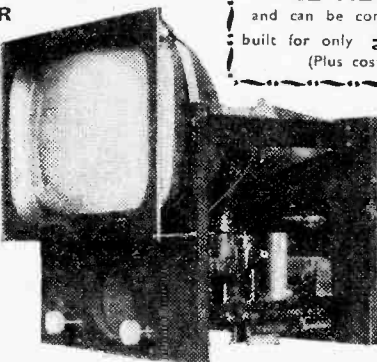


This is the 12"

TELE-VIEWER

and can be completely

built for only **£28 - 16 - 4**

(Plus cost of C.R.T.)

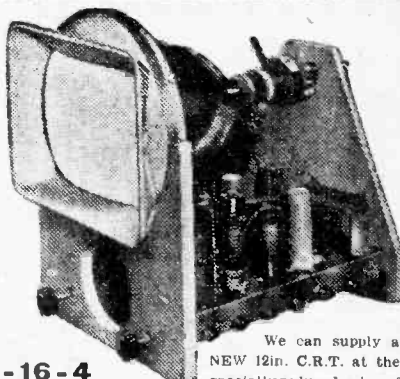

We can supply a NEW 12in. C.R.T. at the specially reduced price of

£12.19.6. (Carr. & Ins., 15/- extra.)

The complete set of ASSEMBLY INSTRUCTIONS for these T/Vs are available for 5/- each. They include really detailed PRACTICAL LAYOUTS, WIRING DATA AND COMPONENT PRICE LIST. ALL COMPONENTS ARE AVAILABLE FOR INDIVIDUAL PURCHASE. AN ATTRACTIVE TABLE MODEL CABINET FOR THE 12in. Model IS AVAILABLE FOR **£6-19-6.**

STERN RADIO LTD.

109 & 115, FLEET STREET, E.C.4.

Tel.: CENTRAL 5812-3-4.

BARTON'S (Radio)

We are pleased to inform our customers both old and new that our Mail Order Dept. has been transferred to more spacious premises at 44, Tottenham St., London, W.1 (first turning left from Goadge Street, underground). This move was made necessary by the ever-increasing demand for our goods. Due to the improved facilities at our new premises we can once again assure customers of immediate despatch.

BUILD YOUR OWN RADIO!

We can supply all the parts (including valves, 5in. moving coil speaker, cabinet, chassis, and everything down to the last nut and bolt) to enable YOU to build a professional-looking radio. The chassis is punched and drilled ready to mount the components. There is a choice of any of three attractive cabinets 12in. long, 5in. wide by 6in. high, as



follows: either ivory or brown bakelite, or wooden, finished in walnut. Complete and easy-to-follow point-to-point and circuit wiring diagrams supplied.

MODEL 1. T.R.F. RECEIVER

This is a 3 valve plus metal rectifier T.R.F. receiver with a valve line-up as follows: 6K7 (I.F.), 6Z4 (D-F) and 6V6 (Output). The dial is illuminated and when assembled the receiver presents a very attractive appearance. Coverage is for the Medium and Long Wave bands. Operates on 200/250 volts A.C. Mains.

Plus 2/6 Packing, Carriage, Insur. **£5.10.0**

T.R.F. RECEIVER We can supply this Receiver ready built at **£6 15s. 6d.** plus 3/6 p.o.

ALL COMPONENTS SUPPLIED ARE GUARANTEED FOR ONE YEAR

Instruction Booklet and priced Parts List for either of the above available separately at 1/-. This money will be refunded if circuit diagram is returned as NEW within 7 days. When ordering please state Model No.

WE CARRY LARGE STOCKS OF COMPONENTS AND WELCOME YOUR ENQUIRIES.

TERMS OF BUSINESS: Cash with order (or C.O.D. Post items only); all orders for small items totalling over £2 post free unless otherwise stated. Money back Guarantee on all goods.

Office: (Dept. P.W.), 34, Montpellier Rise, London, N.W.11. Telephone: Meadway 1736

Works and Despatch Dept.: 44, Tottenham Street, London, W.1. Lougham 1151.

PERSONAL CALLERS WELCOMED

4-watt AMPLIFIER KIT

This is a 3 valve 3 stage Amplifier for use with Gramophone, Microphone or Radio. Valve line-up is as follows: 6SL7, 6V6, 5Z4. Negative feed-back. Tone control. Voltage adjustment panel incorporated. 4 watts output. For operation on A.C. Mains 200/250 volts.


The complete Kit includes every item down to the last nut and bolt, drilled and punched chassis, and comprehensive point-to-point wiring circuit diagram. Chassis dimens.: 8in. x 8in. x 2 1/2in.

ALL COMPONENTS SUPPLIED ARE GUARANTEED FOR ONE YEAR

PRICE

£4.5.0

Plus 2/6 Pkg. Carr. & Ins.

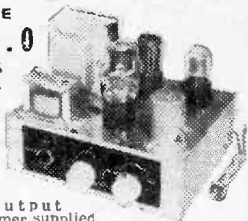

The Output Transformer supplied

is for use with a loudspeaker of 3 ohms impedance and we would suggest that the output of the completed amplifier justifies the use of one of the latest W.B. H.F. Speakers which can be supplied as follows: 8in., 60/6; 9in., 67/-; 10in., 73/6. All plus 2/6 pkg., carr. ins.

Circuit Diagram only, available separately at 1/-. To those who require this Amplifier ready-built we can supply it at **£5.1.0** plus 3/6 pkg., carr., ins.

Prices slashed at Clydesdale

TI154B TRANSMITTER UNIT

Medium/High powered for C.W.-M.C.W. R/T 3 ranges, 10-5.5 mcs., 5.5-3 mcs., 500-200 kcs. Complete with 4 valves, etc., in metal case 14in. x 16in. x 8in. External Power Supply required.
Ask for P/E5A.

39/6 each
Circuit, 2/3. Plus 7/6 carriage.

VISUAL INDICATOR TYPE 1

Ref.: 100/2.

Dual reading left/right D.F. meter for R1155, 2 1/2in. Scale overall dim.: 3 1/2in. x 2 1/2in., in used condition.

Ask for P/H862A. **12/6** each Post Paid.

S.440-B V.H.F. TRANSMITTER CHASSIS

Part of the Station P40 Equipment. Partly stripped by the M.O.S., less valves, inductances and Crystal, but otherwise a good basis for reconstruction, compact size 14in. x 8in. x 7in. Original frequencies 85-95 Mc/s.

Ask for P/H517. **15/-** each Carriage Paid.
Circuit 1/3.

WS-18 RECEIVER CHASSIS

Complete with valves, 3/AR12 (VP23), AR6 (HL23DD), I.F. 465 kcs. Range 6-9 mcs., (Battery operated.) Chassis 8 1/2in. x 5in. x 1 1/2in. Front panel 9 1/2in. x 5 1/2in.

Ask for P/H22. **25/-** each. Post Paid.
Circuit and Data, 2/3.

RECEIVER UNIT TYPE 25

Ref.: 10P/1L.

Part of TR1196. Range 4.3-8.7 mc/s. with valves 2/VR33 (EF38), 2/VR36 (EF38), VR55 (EBC 33), VR57 (EK32), 2L.F.T. 460 kc/s., etc., in metal case 8 1/2in. x 6 1/2in. x 6 1/2in.

Ask for P/11299. **25/-** each. Post and Packing, 3/6 extra.
Circuit and Data 1/6.

ELECTRONIC IGNITION TESTER

Type V.E.D. Patt. 533562 by English Electric, in original wood case. A Cathode Ray tester for checking ignition of internal combustion engine, while engine is operating, will operate from 6, 12 or 24 volts D.C. or 230 v. A.C.

Built into black crackle case with hinged front and carrying handle, dim. 15 1/2in. x 8 1/2in. x 11 1/2in.

No leads or instruction book available. Ask for P/H535. **£15** each Carriage 10/- extra.

R.F. UNIT TYPE 24

In original carton.

With valves 3-VR65 (SP61), Range 20-30 Mc/s., switched tuning. Dim.: 9 1/2in. by 7 1/4 in. x 4 1/2in. Wgt. 7 lbs.

Ask for P/H850. **10/-** each Post 1/6 extra.
Circuit 1/3.

R.F. UNIT TYPE 25

In original carton.

Range 40-50 mcs. Otherwise as R.F. 24. Post 1/6 extra.

Ask for P/H874. **12/6** each. Post 1/6 extra.
Circuit 1/3.

R.F. UNIT TYPE 27, WITH BROKEN DIAL

Range 65-85 mc/s. Valves 2-VR135 (EF54), VR137 (FC52), etc. Dim. and Wgt. as R.F. 24. Variable Tuning.

Ask for P/E771. **£1.9.6d.** Post 1/6 extra.
Circuit 1/3.

SUPPRESSOR UNIT 5C/570

Contains 4 H.F. chokes and 4 tubular condensers 0.1 mfd. 250 v. D.C., carrying 5 amps. (2 sets on each lead), each choke and condenser separately screened in compartments of aluminium alloy box 4 1/2in. x 2in. x 4 hole fixing.

Ask for P/H907. **2/6d.** each. Post 1/- extra.

WIRELESS REMOTE CONTROL UNIT D

No. 2 Mk. 2, ZA.20991. Wooden box 7 1/2in. x 6 1/2in. x 6 1/2in., with hinged lid, containing 3 relays, 1 make, 500 ohms. 1 make 20 ohms, and H.D. double coil type 1,750 ohms, coil makes, 200 ohms. coil breaks, plus QMB switch and 5 brass terminals.

Ask for P/H003. **7/11d.** each. Post Paid.

5 WAY GROUPBOARDS

Parolin panel 2 1/2in. x 2 1/2in., with tabs for mounting condensers or resistors, two hole fixing.

Ask for P/H991. **6d.** each Post 2d.
Or 3 for 1/6. post paid.

CO-AXIAL CABLE

Any lengths supplied 52 ohms. 12 mm. dia., price 5d. per yard. Minimum 12 yards at 5/- post paid. Ask for P/E 987.

THROAT MICROPHONE

Ref.: ZA.13935.

Pair Electro Magnetic lozenge-shaped pieces (7.5 ohms) with strap, lead and jackplug.

Ask for P/E14. **3/11d.** each Post 6d. extra.

THROAT MICROPHONE

Ref.: ZA.19734.

Pair Electro Magnetic lozenge-shaped pieces (7.5 ohms) with strap, lead and jackplug.


Ask for P/H955. **4/11d.** each. Post 6d. extra.

Order direct from —

CLYDESDALE SUPPLY CO. LTD.

2, BRIDGE STREET, GLASGOW, C.5.

Phone: South 2706/9

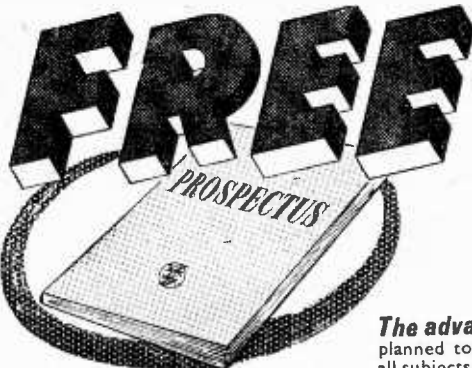

POST THE COUPON TODAY FOR OUR BROCHURE ON THE LATEST METHODS OF HOME TRAINING FOR OVER 150 CAREERS & HOBBIES

PRIVATE AND INDIVIDUAL TUITION IN YOUR OWN HOME

City and Guilds Grouped Certificates in Telecommunications: A.M. Brit, I.R.E. Examination, Radio Amateur's Licence, Radio and Television Servicing Certificates, General Radio and Television Courses, Radar, Sound Recording, etc. Also Courses in all other branches of Engineering and Commerce.

The advantages of E.M.I. training. ★ The teaching methods are planned to meet modern industrial requirements. ★ We offer training in all subjects which provide lucrative jobs or interesting hobbies. ★ A tutor is personally allotted by name to ensure private and individual tuition. ★ Free advice covering all aspects of training is given to students before and after enrolling with us.

NEW LEARN THE PRACTICAL WAY.

With many of our courses we supply actual equipment. Courses include: Radio, Television, Electronics, Draughtsmanship, Carpentry, Photography, and Commercial Art, etc.

Courses from
15/- per month

POST THIS COUPON TODAY

Send without obligation your FREE book.
E.M.I. INSTITUTES, Dept. 32K
43 Grove Park Road, London, W.4.
Phone: Chiswick 4417/8.

NAME

ADDRESS

JAN.

SUBJECT(S) OF INTEREST

EMI INSTITUTES

The only Postal College which is part of a world-wide Industrial Organisation.

Great Britain's Valve Mail-Order House

One Year's Guarantee

1R5	16/5	ECH25	20/2
1S5	16/5	ECH42	20/2
1T4	14/6	ECL80	20/2
354	14/6	ECL90	20/2
3V4	14/6	EF30	23/4
6A	7/4	EF37A	19/6
1A4	13/3	EF37A	19/6
1B4	13/3	EF37A	19/6
1F4	10/2	EF37	22/1
1R5G	12/1	EF30	16/5
1P5G	11/4	EF40	22/1
136G	13/1	EF41	16/5
5Y3GT	13/3	EF50	22/1
6A4	15/1	EF80	22/1
6AL5	11/4	EF91	22/1
6AQ5	11/5	12AT7	22/1
6AT5	15/1	12AU7	22/1
6AU6	22/1	12AX7	22/1
6BA6	16/5	12AGT	22/1
6X4	13/3	12SK7GT	20/2
6W6	31/6	12SQ7GT	16/5
6SA7GT	20/2	12SL7GT	15/1
6SK7GT	16/5	25L6GT	15/1
6SQ7GT	16/5	35Z5GT	16/5
6V6GT	15/1	AZ4	13/3
7B7	16/5	AZ50	13/3
AZ4	13/3	AZ50	13/3
AZ50	13/3	(DW4)	13/3
CBL1	22/1	80	12/1
CL4	20/2	83	13/3
CB11	13/3	81	18/11
EB1	11/4	71A	8/10
EB91	11/4	112A	12/1
(6AL5)	11/4	1A7GT	21
EB3C3	11/4	IC5GT	18/11
EBL1	22/1	IH5GT	14/6
EBF90	14/6	50Y5	22/1
ECC40	13/11	IN5GT	954
EA4	22/1	344	19/11
ECH3	22/8	Post 9d.	13SPA

SALE (2,000 101) TYPES FROM 2/-



DEMOBBED Valves "Manual" 2/3

Giving equivalents of British and American Service and Cross Reference of Commercial Types with an Appendix of B.V.A. Equivalents and Comprehensive Price List. We have still some Valves left at very old Budget Rates (33%) which are actually sold at the old price. (1951 rate).

PIFCO

All-in-one Radio-meter A.C./D.C. Tests everything in Radio. Complete with Test prods. 29/6. Post 1/6.



TYANA TRIPLE THREE

Small Soldering Iron Latest development. Complete with detachable bench stand. 19/6

Electric PAINT STRIPPER

Outdates blow-lamp! It's a unique foot-pedal electric tool. Easier and Faster. Clean and safe. Old paint goes like magic. Cost 1d. per hour. A.C./D.C. Complete. Guaranteed.



B.T.H. GERMANIUM CRYSTAL DIODE. Complete with Blueprint and operating instructions. 2/-

Q MAX RADIO



Allen screw. The operation is quite simple. Prices incl. key: fin. 12/4; 1in. 12/4; 1in. 13/4; 1in. 14/1n. and 1in. 16/- each; 1in. and 1in. 18/- each; 1in. 19/9; 2 1/2 in. 31/9; 2 1/2 in. 36/9; 1in. square 24/3. Post 1/-

BULLS VALVES

Chassis Cutters with Keys

The easiest and quickest way of cutting holes in sheet metal. The cutter consists of three parts: A die, a punch and an Allen screw. The operation is quite simple. Prices incl. key: fin. 12/4; 1in. 12/4; 1in. 13/4; 1in. 14/1n. and 1in. 16/- each; 1in. and 1in. 18/- each; 1in. 19/9; 2 1/2 in. 31/9; 2 1/2 in. 36/9; 1in. square 24/3. Post 1/-

Deposit and Monthly 10/- A.C. ELECTRIC PAINT SPRAYER

Just plug in and spray. Easier than a brush and twice as fast. Post 2/- Ceiling Adaptor Free. Cash 75/-

ROD Antennas. 1ft. sections interlocking and extending. copper plated steel. BARGAIN. dozen 2/6



SERVICE SHEETS

The one you require enclosed if available in a dozen assorted of our best choice. 10/6.

TUBES 20/- VCR 97 NEW

EMISCOPE Type 4/1

3" Electrostatic 20/-

12" Type 511 Electrostatic, same base as VCR 97 £4 - 10 - 0 carr.

TAYLOR METERS on EASY TERMS. Ask for Catalogue:



"2000" AUTOMATIC BLOWLAMP

Burns methalated spirit. Completely Automatic. Absolutely safe. Suitable for all kinds of tinsmith and silver soldering, glass bending, etc. 2,000 deg. Fahrenheit name. Post 9d.

RADIO SUPPLY CO. (Leeds) LTD.

32, THE CALLS, LEEDS, 2

Terms C.W.O. or C.O.D. No C.O.D. under £1. Postage 1/- extra under 10/-. 1/6 extra under £1. 2/- extra under £2. 2/6 extra under £3. Open 9 to 5.30. Sats. until 1 p.m. Catalogue 6d. Trade List 5d. S.A.E. please with enquiries.

CHASSIS (Undrilled Aluminium) 18 s.w.g. amplifier (4-sided). 12in. x 9in. x 2 1/2in. 6/11 14in. x 9in. x 2 1/2in. 6/11 16in. x 10in. x 3in. 8/3 18 s.w.g. receiver. 12V. 6in. x 3 1/2in. x 1 1/2in. x 5 1/2in. x 2in. 3/11 7 1/2in. x 4 1/2in. x 2 1/2in. 2/6 11in. x 6in. x 2 1/2in. 3/11 16 s.w.g. receiver type. 12in. x 8in. x 2 1/2in. x 5 1/2in. 6in. x 8in. x 2 1/2in. 7/6 20in. x 8in. x 2 1/2in. 8/11 16 s.w.g. amplifier type, 4-sided. 12in. x 8in. x 2 1/2in. 7/11 16in. x 8in. x 2 1/2in. 10/11 20in. x 8in. x 2 1/2in. 13/6 14in. x 10in. x 3in. 13/6

EX-GOVT. TRANSNS. 230 v. 50 c/s. Following suitable for chargers, etc.: 8.8 v. 4 a. 9/9; 0-11-22 v. 30 s. 72/6; 0-11-22 v. 15 a. 35/9; 0-16-18-20 v. 25 a. 79/6; 7.7 v. 7 a. C.T. 4 times 25 a.

Misc. Types 48 v. 1 a. 9/9; 400 v. 200 mA. 6.3 v. 5 a. 27/9; 400 v. C.T. 150 mA. 4 v. 3 a. 8.3 v. 6 a. 6.3 v. 0.6 a. 4 v. 6 a. 4 v. 3 a. 4 v. 3 a. 5 v. 2 a. 25/9; 1.220 v. 350 mA. 610-0-610 v. 150 mA. 300-0-300 v. 150 mA. 29/9; 665-775-690-0-690-775-985 v. 500 mA. 29/9; 4 v. 2.5 a. 4 v. 4 a. 3 a. H191 Ins. 7/9 250-0-250 v. 200 mA. 6.3 v. 2.5 v. 3 a. 25/9 300-0-300 v. 150 mA. 6.3 v. 4 a. 5 v. 3 a. 22/9

AMPLIFIER OR CHARGER CASES Size approx. 15 x 6 1/2 in. high. Strongly made in perforated steel. Finished in grey enamel. 9/6

AMMETERS Moving Coil G.E.C. 0-5 amps, 2in. scale. 11/9.

SILVER MICA CONDENSERS. 50, 10, 15, 20, 25, 30, 35, 40, 50, 100, 120, 150, 200, 230, 300, 400 pfd, 1,000 (501 mfd.), 2,000 pfd. (.002 mfd.). 6d. each; 3/9 doz. One type.

EX-GOVT. AUTO TRANSFORMERS Double Voltage, 50 c/s.

10-0-200-220-240 v. to 10-0-275-295-315 v. 1,000 watts. 69/6; 0-230 v. to 0-230 v. tapped every 11 volts from 57.5 v. 6,000 watts (21 amps.). 28/15/- Where 110 v. input or output is required primary and secondary windings can be connected in series. Single winding 0-110-100-230 v. 1,400 watts 49/6. 15-10-5-0-195-215-235 v. 500 w. 27/9

EX-GOVT. SMOOTHING CHOKES

250 mA. 10 H 50 ohms 14/9 250 mA. 10 H 100 ohms 14/9 150 mA. 10 H 100 ohms 11/9 100 mA. 10 H 150 ohms Trop. 6/9 50 mA. 5-10 H 200 ohms 2/9 L.T. type 1 amp. 2/9

EX-GOVT. METAL BLOCK (PAPER) CONDENSERS

4 mfd. 500 v. 2/9; 4 mfd. 750 v. 3/9; 4 mfd. 1,500 v. 4/9; 4 mfd. 2,000 v. 7/9; 6 mfd. 400 v. 5/11; 8-8 mfd. 600 v. 6/11; 4 mfd. 400 v. plus 2 mfd. 250 v. 1/11; 3 mfd. 500 v. 5/9; 15 mfd. 500 v. 6/9

EX-GOVT. E.H.T. SMOOTHERS

.02 mfd. 8,000 v. cans 1 1/2; .25 mfd. 4,000 v. Blocks. 4/9; .5 mfd. 2,500 v. Blocks. 3/9; .5 mfd. 2,500 v. cans. 2/3; 1.5 mfd. 4,000 v. Blocks. 5/9; .1 mfd. plus .1 mfd. large Blocks 8/0 v. 8/6

RF28 UNITS BRAND NEW. CARTONED. Only 39/6. Carr. 2/6.

EX-GOVT. TRANSMITTER-RECEIVERS. Type TR9D, complete with all valves. 47/6. carr. 5/-

EX-GOVT. ACCUMULATORS

With Non-Spill Vents. Unused and guaranteed 2 v. 16 A.H. 5/9 each or 3in. wood carrying case 9/7. 5ins. 14/9. plus 5/- carr.

MIDGET MAINS TRANSFORMER. Manufacturer's Surplus. Primary 220/240 v. Secs. 275-0-275 v. 70mA. 6.3 v. 2 a. Only 11/9.

TV. PREAMPLIFIER (Piezoe) For Fringe Areas. Brand New. Complete with 6F13 valve. Only 22/6.

LANDEN RELAYS For 230 v. 50 c/s. mains input. 4/9

R.S.C. MASTER INTERCOM. UNIT with provision for up to 4 "Listen-Talk Back units" individually switched. A high gain amplifier allows speech emanating from the rooms containing remote control units to be heard at the master control. The unit is in kit form and point-to-point wiring diagrams are supplied. A walnut veneered wood or brown bakelite cabinet is included. Mains input is 200-250 v. 50 c/s. I.T.T. line 300 v. CHASSIS IS NOT ALIVE. Ideal also for use as "Baby Alarm." Sound amplification 4 watts. Price only 25/19/6. "Listen-Talk Back Unit" in walnut veneer or bakelite cabinet can be supplied at 35/- each. Full descriptive leaflet 10d. The Master Unit can be supplied assembled and tested for 30/- extra.

EX-GOVT. VALVES (NEW)

Each	Each	Each
1T4	7/9	6SK7Met 7/9
1R5	7/9	6C7G 9/11
1S5	7/9	6SN7GT 9/9
3V4	7/9	6V8C 8/9
354	7/9	6V8GT 7/9
5Y3G	8/9	6X5GT 8/9
5Y4G	10/6	8D2 2/11
6Z4G	9/6	807 7/11
6F6G	7/9	9D2 2/11
6AM6	7/9	12A6 7/9
6J5G	5/9	12K7GT 10/6
6J7G	6/6	12Q7GT 10/6
6K7G	5/11	15D2 4/9
6K8G	8/11	25Z4G 9/6

I.T.T. ELIMINATOR AND TRICKLE CHARGER KIT. Input 200-250 v. A.C. Output 120 v. 40 mA. fully smoothed, and rectified supply to charge 2 v. acc. Price with steel case and circuit. 29/6. Or ready for use. 8/9 extra.



OSMOR

radio products Ltd.

(Dept. P.55) 418 BRIGHTON ROAD, SOUTH CROYDON, SURREY. Telephone: Croydon 5148/9

These really powerful units in compact form give quality and performance right out of proportion to their midget size and modest cost. Osmor "Q" Coilpacks have everything that only the highest degree of technical skill can ensure—extra selectivity, super sensitivity, adaptability. Size only 1½ x 3½ x 2½ with variable iron-dust cores and Polystyrene formers. Built-in trimmers. Tropicalised. Pre-aligned Receiver-tested and guaranteed. Only 5 connections to make. All types for Mains and Battery Superhets and T.R.F. receivers. Ideal for the reliable construction of new sets, also for conversion of the 21 Receiver, TR1196, Type 18, Wartime Utility and others. Send to-day for particulars!

SEPARATE COILS 4/-

A full range is available for all popular wavebands and purposes. Fully descriptive leaflets and connection data available. (Optional) new simple fixing 2d. extra. Just note these "5 Star" Features. * Only 1in. high. * Packed in damp-proof containers. * Variable iron-dust cores. * Fitted tags for easy connection. * Low loss Polystyrene formers. L or M.W. T.R.F. REACTION COIL TYPE QR 11-12 4/9.

A range of coils for F.M. Receivers shortly available.


A special design of coils now available for reflex circuits.



OSMOR STATION SEPARATOR

The Separator may easily be tuned to eliminate any one station within the ranges stated and fitting takes only a few seconds. Sharp tuning is effected by adjusting the brass screw provided.

Aerial plugs in here

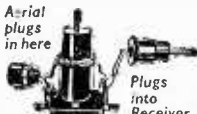

Plugs into Receiver

7/6

COMPLETE

NO. METRES

- 1—141-250
- 2—218-283
- 3—267-341
- 4—319-405
- 5—395-492
- 6—455-567
- 7—1450-1550
- 8—410-550 k/c.

CHASSIS CUTTER



Type	Hole Sizes	Prices
1	1in. x 1½in.	19/6
2	1in. x 1½in.	18/9
3	1½in. x 1½in.	22/6
4	1½in. x 2½in.	27/3

Illust. list on request.

I.F.s. 465 k/c. Permeability-tuned with flying leads. Standard size 1½in. x 1½in. x 3½in. For use with OSMOR coilpacks and others, 14/6 pair. Midget I.F.s. 465 k/c. 1½in. x 1½in. x 2½in. 21/- pair. PRE-ALIGNED. 1/6 extra, both types.

FREE!

Send 5d. (stamps) for fully descriptive literature including: "The really efficient 5-valve Superhet Circuit and practical Drawings"; "E-valve ditto, 3-valve (plus rectifier) T.R.F. circuit, Battery portable Superhet circuit, Coil and Coilpack leaflets, Chassis Cutter leaflet, and full radio and component lists, and interesting miniature circuits, etc.

DIALS—VARIOUS DIALS. CALIBRATED TO COILS

Metal dials, overall size 5½in. square. Cream background. 3-colour Type M1, L.M.S. waves, M2, L & M. waves, M3, M, and 2 S. waves. Price 3/6 each. Pointer 1/6. Drum, Drive, Spring and Cord. 3/2. Type A glass dial assembly, measuring 7in. x 7in. (9½x9½ overall). Mounts in any position. Choice of two 3-colour scales, 24/6. P. & P. 1/6.

OUR TECHNICAL DEPT. WILL BE PLEASED TO ANSWER (BY LETTER ONLY) ANY ENQUIRY RELATING TO CIRCUITS WHICH OSMOR COILS OR COIL PACKS ARE USED OR ARE INTENDED TO BE USED.

WE ENDEAVOUR TO KEEP ABREAST OF THE TIMES BY BUILDING THE VARIOUS CIRCUITS PUBLISHED IN "WIRELESS WORLD," "PRACTICAL WIRELESS," "RADIO CONSTRUCTOR," ETC. WE KEEP STOCKS OF THE COMPONENTS SPECIFIED

"PRACTICAL WIRELESS"

Coronet Four; Beginners' Superhet; Modern High Power Amplifier 2; Attache Case Portable; RL155 Converter; A.C. Band-Pass 3; Modern 1-Valver; 3-speed Autogram, modern reflex, etc.

"WIRELESS WORLD"

"No Compromise" TRF Tuner, "Midget Mains Receiver," Sensitive 2-valve Receiver, Television Converter (special coils in cans available), Midget sensitive T.R.F., etc.

"RADIO CONSTRUCTOR"

Converting the TR1196 receiver to a general purpose s/het receiver simple crystal diode set. Radio feeder units. Economy 8 W.P.F. Amplifier. Circuit and details available for adding push-pull to the 5/6 valve Osmor superhet.


A LIST OF FIXED CAPACITIES AS REQUIRED FOR SWITCH-TUNING AVAILABLE ON APPLICATION

"Q" COIL UNITS MAKE EASY SWITCHING

Wavebands may be added or changed in a few minutes. Switching arrangements can be increased as required. Multi-waveband Coilpacks may be easily made up. The Coil Unit consists of Aerial and Oscillator Coils and Trimmers wired and ready to connect to switch.

THE SIMPLEST AND MOST CONVENIENT METHOD OF SET BUILDING SO FAR DEvised FOR THE AMATEUR:

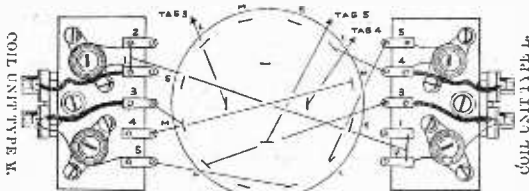15/- PER UNIT including 4 foolproof drawings



DESIGNERS ARE ASSURED OF FULL CO-OPERATION

PLEASE LET US KNOW YOUR REQUIREMENTS

NEWCOMERS TO RADIO. WE HAVE A NEW DEPARTMENT READY AND WILLING TO HELP SEND US YOUR PROBLEMS

PRACTICAL WIRELESS

EVERY MONTH
VOL. XXXI, No. 579, JANUARY, 1955

EDITOR: F. J. CAMM

23rd YEAR
OF ISSUE

COMMENTS OF THE MONTH

BY THE EDITOR

Jubilee of the Thermionic Valve

ON November 16th, 1904, Mr. (later Sir) Ambrose Fleming filed his famous patent application for the thermionic valve. In view of the vast development which has taken place in valve technique in the passage of 50 years, Fleming's invention may to-day seem unimportant. The fact is, however, that it was a basic invention, which paved the way for the development of the now important electronics industry. We must not forget that the rectifying properties of the valve had been discovered previously by Edison and, indeed, Fleming himself as well as many others were aware of this. J. J. Thomson had identified the electron which carries the current; Richardson had evolved a formula for electron emission. Wehnelt had in 1904 patented a rectifier embodying the oxide-coated cathode, later to assume great importance. Notwithstanding all this, it was Fleming who discerned its possibilities as a detector for wireless telegraphy, and lifted it from the laboratory to become in time an instrument of everyday use and destined for mass production. Fleming undoubtedly led the way to the development in radio telegraphy and telephony, and the first cardinal event in the sequence occurred in 1907, when de Forest introduced the control grid, which greatly increased the usefulness of the vacuum valve. It remained to develop and improve manufacturing methods, and Langmuir and his associates with the American General Electric Co. studied valve making materials and how to treat them, as well as problems of vacuum technique using high-speed pumps. Just before 1914, development in the U.S.A. was intensified, but it was stimulated in Britain by the wartime need for rapid and efficient communications. It is possible that the first thermionic triode produced in this country was made in 1915 in the B.T.H. laboratory. The first valves were bright emitters, with tungsten cathodes. The use of thoriated tungsten resulted in the production of the first dull emitter valve. Although Wehnelt had produced his improved cathode with the oxide coating in 1904, it was over 20 years before it came into general use.

In subsequent developments, the valve has become more complicated. The addition of one grid to Fleming's diode enlarged its usefulness, and new types appeared, incorporating more and

more electrodes, giving improved control, and wider fields of application, enabling individual valves to perform multiple duties.

Thus, by 1939, the valve was ready for the later developments of which we are all aware, and the second World War stimulated new developments, none more important than that of the cavity magnetron, an outstanding British achievement.

In his patent, Fleming had stated that a very high vacuum should be contained in the bulb, but by comparison with present standards the early valves were "soft." This set in line new developments leading to a wide range of vacuum valves from the sub-miniature to the high-power, water-cooled transmitter valves for radio, and to thyratrons for power control. In valves for radio a high vacuum is necessary, but the gassy triodes developed into the thyatron for use in the low-frequency application of industrial control. The thyatron was introduced into this country by the British Thomson-Houston Co., who developed a range of valves for many industrial purposes, including the mercury vapour thyatron.

During the second World War, radar development introduced a new use for the thyatron, in the switching of high energy pulses and present-day radar makes still greater demands.

It is unlikely that Sir Ambrose Fleming realised to the full the importance of this invention nor where it would lead in 50 years. He could not have anticipated in 1904 that the valve would bring sound and vision into the home, transform the phonograph into an instrument for high-class musical production, result in the "animated picture," control industrial machines, perform intricate calculations for the mathematician and arm the nations with apparatus for defence and deadly power to strike.

He certainly could not have envisaged television in 1904, but oak trees from little acorns grow, and the credit which is his is no less because the modern developments of his basic invention were not due to his work. After all, these developments are only improvements, and without the basic idea improvements would not be possible. Marconi has been accorded the lion's share of the credit, but he and Fleming should share it.—F. J. C.



Round the world of WIRELESS



By "QUESTOR"

Broadcast Receiving Licences

THE following statement shows the approximate number of broadcast receiving licences issued during the year ended September, 1954. The grand total of sound and television licences was 13,527,864.

Region	Number
London Postal	... 1,529,633
Home Counties	... 1,426,283
Midland	... 1,209,943
North Eastern...	... 1,596,968
North Western	... 1,227,619
South Western	... 992,084
Wales and Border Counties	... 616,154

Total England and Wales	... 8,598,684
Scotland	... 1,032,308
Northern Ireland	... 219,076

Grand Total ... 9,850,068

Trade Name Changed

AS "Voltastat" is similar in name to that of another electrical product, Winston Electronics, Ltd., of Hampton Hill, have discontinued its use. Instead "Constavolt" will be used when

the stabilised voltage control equipment is designed for battery charging and "Magnetrol" when it is used for rectification or as a battery eliminator.

Pye Marine Limited

BECAUSE of the vast increase in the marine radio and electronic business conducted by the Pye group of companies through their subsidiary company Rees Mace Marine, Ltd., the name of that company has been changed to Pye Marine Limited.

"Have a Go!"

THE latest series of "Have A Go!" with Wilfred Pickles, heard each Tuesday, with repeats on Saturday and Sunday, will run for 26 weeks.

More Marconi Equipment

IN accordance with plans for nation-wide coverage with the Home, Light and Third services

by a chain of V.H.F. frequency-modulated broadcasting stations, the BBC has placed a further order with Marconi's Wireless Telegraph Co., Ltd. The new contract calls for 24 combining units and 24 changeover switches with the associated interconnecting feeders. This comprises equipment for six three-programme stations.

Drop in Listening Figures

RECENT figures issued by the BBC Audience Research Department indicate that the number of listeners to sound radio in the July-September quarter of this year was approximately 26,000,000 on an average evening, two million fewer than in the same quarter last year.

British Institution of Radio Engineers

THE following meetings of the Institution will be held during December:—

London Section.—Wednesday, December 29th, 6.30 p.m., at the London School of Hygiene and Tropical Medicine, Keppel Street, W.C.1. Discussion meeting on "Education and Training of Radio Engineers."

North-eastern Section.—Wednesday, December 8th, 6 p.m., at Neville Hall, Westgate Road, Newcastle-upon-Tyne. "Logic, Algebra and Relays."—Prof. Emrys Williams, B.Eng., Ph.D., M.Brit.I.R.E. (University College of South Wales).

West Midlands Section.—Wednesday, December 8th, 7.15 p.m., at Wolverhampton and Staffordshire Technical College, Wulfrana Street, Wolverhampton. "Industrial Applications of Electronic Control."—J. A. Sargrove, M.Brit.I.R.E. (Sargrove Electronics, Ltd.).

Lifeboat Radio

SIXTY-NINE Ellerman Lines vessels are to be provided with portable radio transmitter-receivers for use in their lifeboats, in case of emergency. The equipment to be supplied is the "Salvita," recently produced by the Marconi International Marine Communication Co., Ltd. It is waterproof



"Archie's The Boy," the new Archie Andrews series, began on November 11th. Left to right: Benny Hill, Peter Madden, Archie and Peter Brough, the main stars of the show.

and buoyant and requires no batteries, being powered by a hand-driven generator.

Sound Revival

IT is learned that the BBC Light Programme and Home Service programme planners will be concentrating on converting TV viewers back to sound radio listening this winter, now that television does not need subsidising so much as in its earlier days. The additional finance will be used to improve the quality of sound programmes.

M.C.C. Tour of Australia

THE dates and listening hours of commentaries in this country for the four remaining test matches in Australia are as follows: Sydney, December 17th-23rd, 7-7.40 a.m.; Melbourne, December 31st-January 6th, 7-8 a.m.; Adelaide, January 28th-February 3rd, 7-8.40 a.m.; Sydney, February 25th-March 3rd, 7-7.40 a.m. These commentaries will all be heard on the Light Programme.

Daily reports during the second, third and fifth matches will be heard in the Home Service at 8.10 a.m. and at noon in all five.

Training College Completed

THE new Marconi College is now virtually completed. New lecture, tutorial, laboratory and administrative accommodation is now contained under one roof and every facility for technological training in the field of electronics for nearly 100 students and residential accommodation for fifty is provided.

The college now possesses two lecture rooms, ten laboratories, a workshop, a drawing-office school, a technical library and a quiet room.


No South-east Service

THE BBC has stated that the commencement of operation of the Wrotham Hill V.H.F. transmitting station will not mean a new regional service for South-east England.

Contract from Thailand

PYE LIMITED have received a contract from Thailand for over £100,000 worth of telecommunications equipment, including a large quantity of new 60-watt H.F. sets.

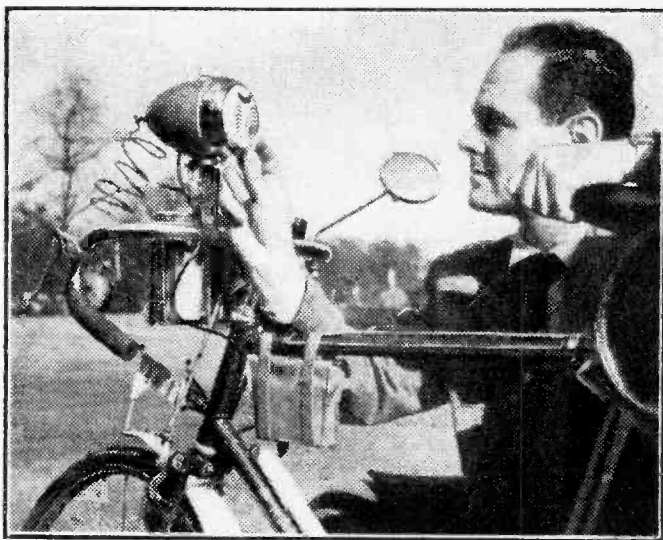The Thai police, who placed the order, have had a quantity of Pye V.H.F. radio-telephone gear in use for the past year.



Mr. Eric Braun, of Hornchurch, Essex, adjusts the bicycle radio receiver which kept him company on his recent 2,000-mile cycling tour of Europe.

Coming of Age

ON November 20th, in the Home Service, "In Town To-Night" celebrated its twenty-first birthday and 737th sound broadcast.

The first edition of the programme was broadcast on the night of Saturday, November 18th, 1933, with the late A. W. Hanson as producer. He was succeeded in 1936 by C. F. Meehan until Peter Duncan, the present producer, took over in the autumn of 1947.

Interference in Wales

AT a recent meeting of the South Wales and Monmouthshire branch of the Rural District Councils Association, it was suggested that a direct approach be made to the East German authorities in an attempt to rid the Welsh Home Service reception of interference.

No Personal Appearances

BBC radio announcers, most of whom earn approximately £1,000 a year, have been told that they will no longer be able to accept outside engagements that involve personal appearances.

No official reason has been given for the introduction of the new rule.

Northern Radio Show

CLOSED-CIRCUIT demonstrations of the new V.H.F. radio system to be employed

eventually in this country will be given by leading manufacturers at the Northern Radio Show to be held at the City Hall, Manchester, from May 4th to 14th, under the auspices of the Radio Industries Council.

Valves Talk

A TRADE talk and film show was given recently by Mullard Limited, to members of the Isle of Man Radio Dealers' Association.

The evening's programme included a lecture on valves and their application, illustrated by Mullard's new film, "The Manufacture of Radio Valves," and a discussion on topics arising from questions put forward by members of the audience.

Record for August

THE Radio and Television Retailers' Association has announced that sales of radio receivers in August were the highest ever recorded for that month.

Obituary

THE death took place, in Canada, on November 7th, 1954, of Mr. A. H. Ginman, a former President of the Canadian Marconi Company. He was 79.

Mr. Ginman was born in Surrey on December 14th, 1874, and first joined the Marconi Company at the age of 27, working with Marconi himself. He retired in January, 1951.

AMPLIFIER DESIGN

10.—UNTUNED AMPLIFIERS—CONTINUED

By R. Hindle

(Continued from page 754 December 1954 issue)

IN practice, two Dubilier 700 Ω 70-watt dropper resistors in series are used. These are adjustable and so other chassis can later be run from the same droppers. An anode limiting resistor R3 is included in the rectifier circuit in accordance with the makers' recommendation to protect the valve.

Construction

The chassis, 7in. x 4in., is identical with that used for the A.C. version, and the drilling diagram for the components used in the prototype is given in Fig. 40. As before, the components should be obtained and checked to the diagram before drilling the chassis in case of slight deviations. Another point is that the small holes for fixing valveholders and electrolytic condensers are not shown. The best way is to drill the large hole (preferably using a punch) and then to insert the component and turn it round until the tags are in the relative positions as shown on the wiring diagram. Then the positions of the holding-down bolts can be marked through the holes in the component and subsequently drilled.

To help the less-experienced constructor the sequence of wiring is again given in Fig. 41, and as the wires are put on it is a good plan to mark them out either on the wiring diagram or on the circuit diagram.

1. Input socket to pin 1 (V1).
2. R1, 220 K Ω . From pin 1 (V1) to earth tag by input socket.
3. Pin 3 (V1) to pin 3 (V2).
4. Pin 4 (V1) to pin 3 power output socket.
5. Pin 6 (V1) to pin 5 (V1) to one primary tag of output transformer.
6. R2, 300 Ω } Both from
C1, 50 μ F } pin 2 (V1)
to earth tag.
7. Pin 4 power output socket to earth tag.
8. Pin 5 power output socket to furthest tag on electrolytic smoothing capacitor to other tag on primary of output transformer.
9. One side of smoothing choke to pin 5 of power output socket.
10. Other side of smoothing choke to nearest tag of electrolytic smoothing capacitor to tag 7 (V2).
11. R3, 150 Ω . From tag 1 (V2) to tag 5 (V2).
12. Connect together the top tags of the two dropper resistances.
13. The lower adjustable tag on one dropper to pin 4 (V2).

A Series of Articles Dealing with the Theoretical Considerations of Amplifier Design, and Containing a Later Stage Constructional Details of Various Types of Amplifier.

14. The lower adjustable tag of other dropper to pin 1 (V2).
15. Mains lead to pin 1 (V2) and other side of mains to earth tag.

The remarks concerning the use of the amplifier to this model except, of course, that as the heaters are in series the voltage amplifier will have to be connected to the universal output chassis before continuity of heater circuit can be tested, whereas the A.C. version output stage can be tested by itself before connecting the voltage amplifier to it.

No provision has been made for switching the mains in either version. This switch is most likely to be fitted to equipment to be used along with this amplifier, and the mains lead of the amplifier is then connected to the side of such a switch away from the mains. If used as an amplifier alone, a switch can be mounted in any convenient position and the amplifier mains lead connected via this to the mains supply. A particular word of warning should be given about the universal version, however. As usual with such equipment, the chassis is directly connected to the mains, and if practicable measures should be taken to ensure that the neutral side of the mains is always connected to chassis. The switch used in the mains lead in this case should be the two-pole type.

The amplifiers described will be very useful for a compact gramophone player and will have endless uses on the workbench. With the R.F. amplifiers later to be described they can be incorporated into complete receivers, or the reader may like to design

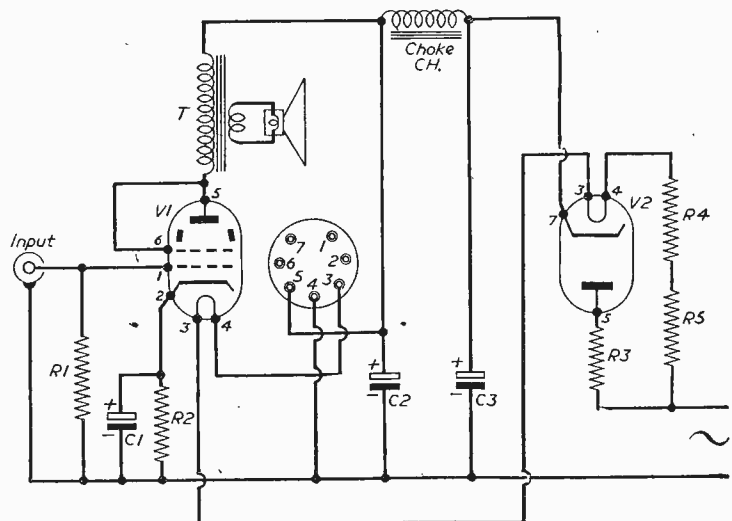


Fig. 39.—Complete circuit for a triode power amplifier—Universal mains version.

his own tuner to go with them. A compact switched unit would be particularly appropriate.

The universal mains version will require the dropper resistances to be adjusted to their correct value and in the first place the power amplifier and the voltage amplifier, without any other units, will be used. The required resistance, as we have seen, is 1,150 ohms, and the best way is to use an ohmmeter (or the resistance position of a multi-purpose meter) without the mains being connected, of course, across the dropper connections (i.e., between pin 1 and pin 4 of V2), whilst the lower adjustable contacts on the droppers are moved up the resistors. A final check should be made by reading the current flowing (which should be .15 amps), temporarily breaking one of the connections and inserting the meter there. A convenient point is at the link at the top of the resistors. This link can be removed and the ammeter connected in its place. If the constructor has not the necessary meters, no doubt the supplier of the resistors will adjust them to the appropriate value for him. It will be realised that if later more valves are added to the chain (as will be explained in subsequent articles), the positions of these taps will have to be readjusted.

Output Transformer

The miniature components such as are used for these amplifiers do not offer a great deal of choice in ratios, and we have seen that this is not very critical so long as the error, if any, is towards a larger load. The valves used want a load of 4,000 ohms, but the nearest ratio available matched the speaker to 5,000 ohms. This was used and was quite convenient, because 5,000 ohms is the correct load for the valve working as tetrode, and conversion was thereby made easier.

Tetrode and Pentode Output Stages

The ordinary tetrode is useless as a power output valve because the permissible anode voltage swing is limited by the kink in the valve characteristic where the anode voltage runs lower than the screen voltage. This kink was found to be a disadvantage often in R.F. amplifiers and the pentode was developed to avoid the kink for both applications. The advantage of the pentode from a power output point of view chiefly rested with its greater efficiency whereby a greater proportion of the power consumed from the H.T. supply was converted into audio power. It had also a greater sensitivity, i.e., it required a smaller input signal for a given power output than did the triode. The price that had to be paid for these advantages was a higher degree of distortion, particularly third harmonic distortion which is more disturbing to the ear than the second harmonic distortion given by the triode. The beam tetrode was later developed in which the secondary emission

LIST OF COMPONENTS FOR FIG. 36

- R1—220 K ($\frac{1}{4}$ w. Dubilier).
- 2—300 Ω (5 w. wirewound Dubilier A11).
- 3, 4—150 Ω ($\frac{1}{4}$ w. Dubilier).
- C1—50 μ F, 12 v. (Dubilier BR).
- 2—16-16 μ F, 350 v. (Dubilier CT).
- 3—
- T1—Output TRF Elstone MO/T.
- T2—Mains TRF, 6.3 v., 250-0-250 v. Elstone MT/MI.
- CH—15H, 50 mA. Elstone SC/M.
- V1—6AQ5, Brimar.
- V2—6X4, Brimar.
- 3—Valveholders, B7G. McMurdo.
- 1—Coaxial socket. Aerialite.
- 4—Grommets.
- 1—Miniature plug for B7G base.
- Mains flex.

COMPONENT LIST FOR FIG. 39

- R1—220 K ($\frac{1}{4}$ w. Dubilier).
- 2—300 Ω (5 w. Wirewound Dubilier A1/I).
- 3—150 Ω (1 w. Dubilier).
- 4, 5—700 Ω (70 w. adjustable, with mounting rods, Dubilier, HYA).
- C1—50 μ F, 12 v. (Dubilier BR).
- 2—16-16 μ F, 350 v. (Dubilier CT).
- 3—
- V1—19AQ5, Brimar.
- 2—35W4, Brimar.
- T—Output transformer to match speaker to 5,000 Ω . Osmor.
- CH—15H, 50mA. Elstone SC/M.
- 3—Valveholders, B7G. McMurdo.
- 4—Grommets.
- 1—Coaxial Plug and socket. Aerialite.
- 1—Miniature plug for B7G base. Elpreq.
- Mains flex.

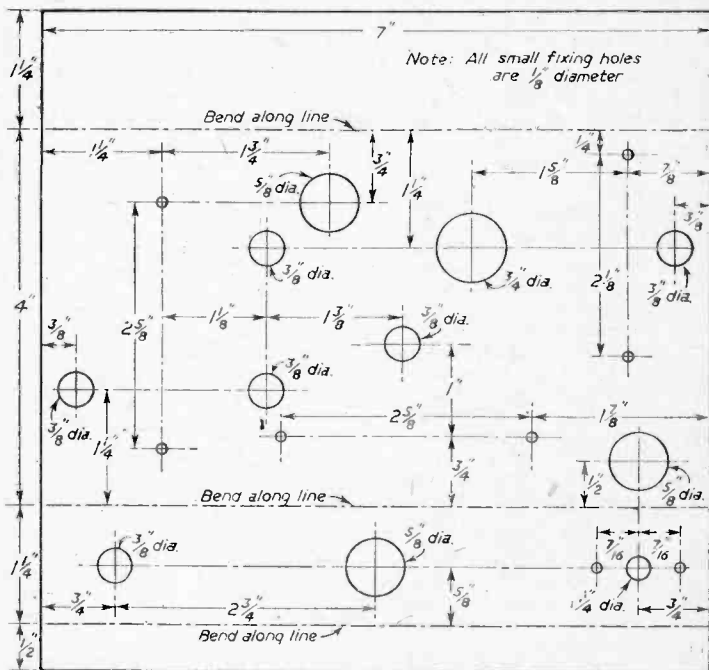


Fig. 40.—Chassis drilling and bending diagram for Fig. 36. Fig. 37 was the chassis data for Fig. 39.

from the anode that caused the objectionable kink in the characteristic of the straight tetrode was eliminated without resort to a third grid. This construction reduces the proportion of third harmonic as compared with the pentode and also allows the anode voltage excursion to go nearer the zero volts position.

Our choice of valve, the 6AQ5 (or the 19AQ5 for universal working) is a beam tetrode and the anode volts/anode current curves for tetrode connection are given in Fig. 42. It will be noticed that the slope of the curves is considerably less than was the

tetrode condition is 5,000 ohms which, by Ohm's Law, is a slope of 5 volts to 1 mA. A peak current of 45 mA (from the signal and superimposed on the static state current) will run the total current down to zero and will be equivalent to a peak voltage swing of $5 \times 45 = 225$ volts, taking the anode up to $250 + 225 = 475$ volts. The second point to be plotted, then, is 475 volts 0 mA, and the two points are joined together and the line extended to give the load line for 5,000 ohms. This appears in Fig. 42.

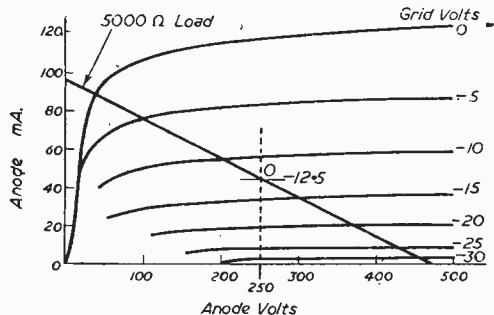


Fig. 42.—Characteristic of 6AQ5 tetrode connected.

case with a triode and it can be seen why the tetrode is looked upon as a more or less constant current device; its use in this connection is often found in timebase circuits. The curves for different grid voltages are seen to be less evenly spaced, giving rise to the increased distortion already mentioned.

A load line is needed again to help in the interpretation of the curves and the method is, as before, to plot the static point O on the 250 volt H.T. line where this cuts the curve for the grid bias to be applied—here we have taken the figure of -12.5 volts recommended in the Brimar data and at this point the anode current is 45 mA. The load specified for

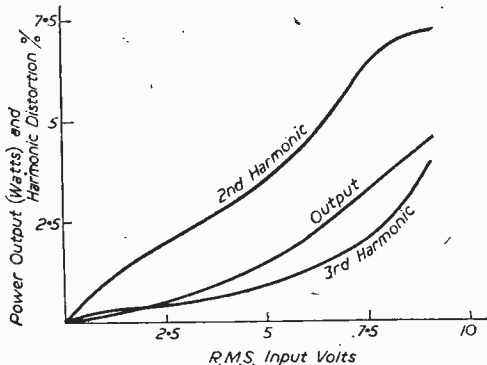


Fig. 43.—6AQ5 output harmonic distortion.

The makers rate this valve to give a maximum output of 4.5 watts with H.T. at 250 volts and Fig. 43 is interesting in showing how the output and the distortion (separate curves are given for second and third harmonic distortion) vary with the input signal. The input voltage is given here in R.M.S. values; these have to be multiplied by $\sqrt{2}$, of course, to give peak values. Nine volts R.M.S. is seen to be required to give the maximum output of 4.5 watts and this is equivalent to a 12.5 peak grid swing, i.e., running the grid down to zero volts. It is interesting to see that

with this valve and for an output of 1 watt the third harmonic is well under 1 per cent.; second harmonic is higher at approaching 3 per cent. but this is not so distressing as third harmonic and, in fact, the valve is very satisfying for a simple amplifier. It is quite reasonable to talk of a power output of 1 watt because very rarely would this be exceeded for purposes for which this type of amplifier would be used. For instance, for domestic radio, only the loud passages of music would require more.

The analysis on the basis of Fig. 42 assumed a fixed bias and this is not quite true when the usual cathode bias resistor is used, for the voltage must change slightly. Fig. 43 is taken, however, with a cathode resistor and not with fixed bias and so represents the actual conditions of work. The difference is only very slight and consequently it is quite justifiable to work on the basis of fixed bias when considering the anode characteristics.

(To be continued)

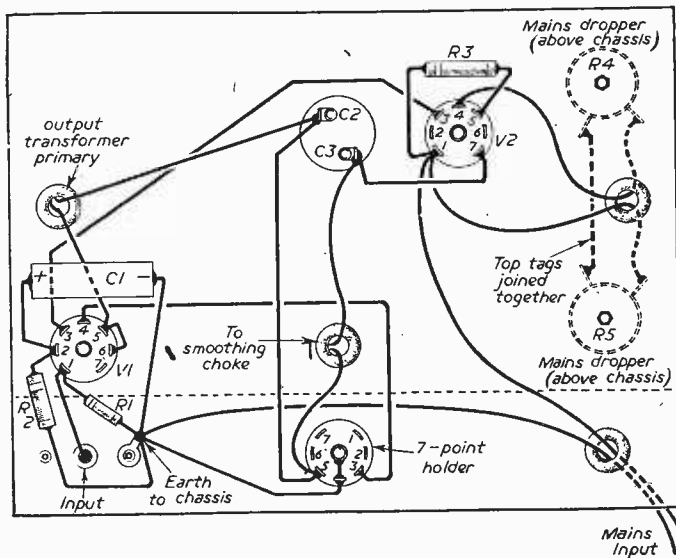


Fig. 41.—Wiring diagram of the arrangement shown in Fig. 39.

Using TEST INSTRUMENTS



Part 1 of a New Series of Articles
Dealing with the Practical Application
of Standard Test Equipment

By Gordon J. King, A.M.I.P.R.E.



THIS series of articles is mainly intended for the experimenter and constructor who, being in possession of either home-made or commercial test instruments, is desirous of reaping full benefit from them. From time to time in these pages constructional details are given on test gear that can be of immense value if properly used, although they might well represent boxes of mystery and potential sources of bewilderment to the experimenter if used without premeditation.

It is not here intended to discuss the merits or demerits of any particular make of instrument, nor dwell on the design considerations involved; our aim will be to focus attention primarily on how various pieces of test gear can best be used, and to bring to light any traps into which the unwary might be likely to stumble.

The Multi-range Meter

Nearly all constructors have a multi-range meter of some kind or other. In its simplest form it may consist merely of a moving-coil meter movement and a box of resistors of pre-computed values that can be arranged in series or in parallel with the movement to provide either current or voltage tests.

In its finished and polished form it is really no more, even though it boasts the added feature of a rotary switch, or a set of sockets, that can be readily used to select and introduce the desired resistor in series or in parallel with the movement according to the range setting.

Before we continue it will be as well to emphasize the fact that the meter movement itself is a current-operated device, and actually deflects in proportion to the current which flows through it. Therefore,

when we set the range switch to a "volts" position and make an appropriate test, we are taking current from the circuit under test to provide energy for the deflection, but since the current flowing through the coil of the meter is precisely proportional to the voltage across the coil and associated resistance, the needle deflection is also proportional to the VOLTAGE across the coil, and as a consequence the meter scale can be calibrated directly in volts.

Either the milliammeter or the microammeter forms the basis of any multi-range instrument. The choice of the meter will be determined by the lowest reading that is likely to be required, and also, as we shall see later, on the desired sensitivity of the instrument on the volts range.

Let us suppose that the movement in our multi-range meter has a full-scale deflection (f.s.d.) of 1 milliampere. To provide a f.s.d. on the 10 milliampere range, then, the movement will need to have in parallel with it a resistor to by-pass the extra 9 milliamperes, so that when the meter records 1 milliampere the current flowing will actually be 10 milliamperes.

In order to calculate the precise value of the shunt resistor—let us call it R_s —we shall first need to know the internal resistance of the meter movement, including any internal resistors. Usually this value is not very high, commonly in the region of 20 to 100 ohms—let us suppose that our meter has a resistance of 45 ohms.

Now on the 10 milliampere range 9 tenths (9 milliamperes) of the external circuit current must pass by way of R_s , and 1 tenth (1 milliampere) by the meter itself. This set-up is illustrated in Fig. 1, which shows the multi-range meter adjusted for 10 milliamperes within the dotted square, and an external circuit passing 10 milliamperes.

In this particular case one can quickly realise that R_s will need to be 5 ohms, since the meter resistance—

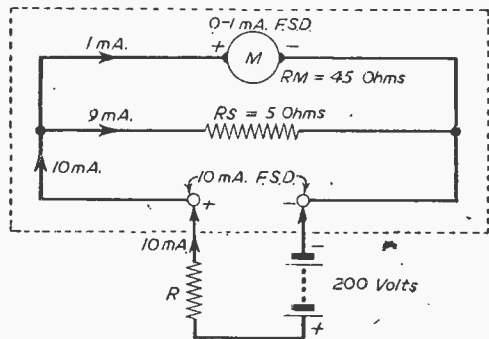


Fig. 1.—A multi-range meter (in dotted square) using a movement of 1 mA F.S.D. arranged to provide a F.S.D. of 10 mA.

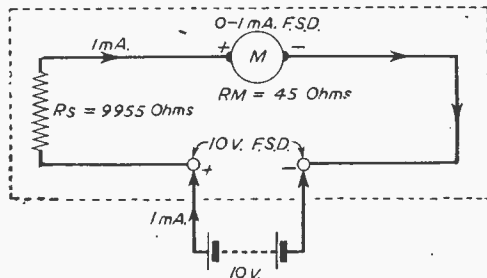


Fig. 2.—A multi-range meter using a movement of 1 mA F.S.D. arranged to provide a F.S.D. of 10 volts.

let us call this R_m —is 45 ohms. In less readily computed cases, however, the value for R_s can be acquired from the following formula, where n is the ratio by which the current range is to be extended: R_s equals $R_m/(n \text{ minus } 1) \dots \dots (1)$

Any number of current ranges—above 1 milli-ampere f.s.d.—can thus be given to the meter by introducing the corresponding value of R_s .

When our multi-range meter is set to a "volts" range, however, things are a little different, for now a resistor is introduced in SERIES with the meter movement. When it is set to, say, the 10 volts range it might well look like the circuit of Fig. 2.

We can clearly see, then, that the total resistance of the circuit (R_s plus R_m) must be of such a value that when connected across a 10-volt source—such as the battery shown—a current of 1 milliampere is permitted to flow through the meter movement to give rise to f.s.d. We can easily find the total resistance value from Ohms Law—for example, R (total) equals Voltage/Current equals $10/0.001$ equals 10,000 ohms. 45 ohms of this value is, of course, contained in the meter itself, so subtracting this figure from 10,000 indicates that R_s possesses a value of 9,995 ohms.

The general formula used to calculate the value of the series resistor is as below:

$$R_s \text{ equals } E/Im \text{ minus } R_m \dots \dots (2)$$

where E is the f.s.d. voltage reading required, and Im is the f.s.d. reading of the meter movement in amperes.

Apart from measuring current and voltage, our multi-range meter will almost certainly have a switch position marked "ohms"—and also probably positions "ohms $\times 10$," "ohms $\times 100$," and etc. This switch position simply introduces a battery in series with a resistor and the meter as a means of testing continuity or measuring resistance. The meter, which on this range is directly calibrated in ohms, measures the current which a known voltage will drive through an unknown resistance. A variable resistor—marked "ohms adjust"—is also generally incorporated in the circuit and is so adjusted that the needle rests on "zero ohms" when the leads are shorted (see Fig. 3).

Since a moving-coil meter is incapable of measuring alternating current and voltage, a small metal rectifier is used to give the instrument an A.C. range, and thus make it universal in application. On the A.C. range, therefore, the appropriate scale may not be perfectly linear, since the scale must be calibrated with regard to the characteristics of the rectifier employed.

On A.C. current ranges measurement is often carried out through a current transformer housed within the instrument, or in some cases, particularly if high A.C. currents are to be measured, used external to the instrument. Such a feature reduces the inherent resistance of the instrument when set on A.C. current ranges.

Voltage Testing

As we have already seen, the meter is strictly a current-operated device and needs to draw energy from the circuit under test to incite deflection. This is all very well provided the circuit is capable of supplying the additional current without its balance being disturbed.

Testing the voltage across the terminals of a H.T. battery or power-pack, for instance, by means of an ordinary voltmeter, will extract such little current from a large current-giving source that the battery or

power-pack will be unaffected in supplying it.

For any power source to be able to supply considerable current means that the internal resistance of the source must be kept at a low value. A new H.T. battery, for example, has a very low internal resistance and is, therefore, able to permit the passage of a relatively large current—clearly, since the current is equal to the voltages divided by the resistance. As the battery ages, however, its internal resistance rises, the value of which, even when the battery is called upon to supply only a small current, gives rise to a considerable voltage-drop, and thus provokes a fall in the voltage appearing at its terminals.

Now let us look at this problem in a different way. Fig. 4 depicts two 1 megohm resistors (R_1 and R_2) connected across a voltage source, which has an internal resistance of negligible value as compared with the combined values of R_1 and R_2 . We can thus rest assured that the actual terminal voltage of

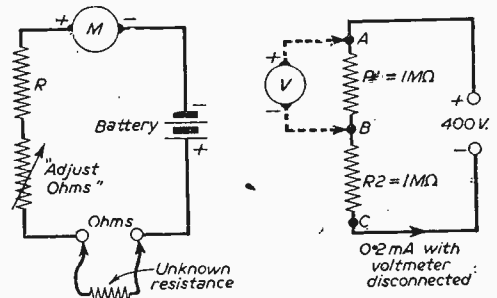


Fig. 3 (left).—Showing how a meter, calibrated in ohms, can be used to measure the current which a known voltage will drive through any unknown resistance. Fig. 4 (right).—The voltmeter V will not indicate the true voltage across R_1 .

the source appears between points A and C . Let this be 400 volts, then by employing Ohms Law (I equals V/R) we discover that a current of 0.2 milliampere is flowing through the series combination. It is obvious that, since R_1 and R_2 are of the same value, the same voltage will appear across each resistor. This will, of course, be half the supply voltage; or in other words, 200 volts will exist between points B and A , and B and C .

This we know as fact and can be readily proved by Ohms Law, but let us now endeavour to measure the voltage across, say, points A and B . We gaily set our multi-range meter to the 200 volts range, apply the prods to the circuit, only to find that we get but a glimmer of a deflection on the meter. We try another meter and most likely find that we get more or less the same results. We try switching to a lower voltage range, but even this hardly has any further effect on the needle deflection. We might or might not be mystified. If we are not, then we are aware of the shunting effect the internal resistance of the instrument has on the circuit under test.

(To be continued)

WIRELESS COILS, CHOKES & TRANSFORMERS
 8th Edition
 6/- or 6/4 by Post from
GEORGE NEWNES, LTD.
 Tower House, Southampton Street, Strand, London, W.C.2



'On Your Wavelength'

BY THERMION

Car Radio

THE number of private cars in this country equipped with broadcast radio receivers has now passed the 250,000 mark. More than 500,000 car radio receivers have been produced by British manufacturers since the war and about half that quantity have been exported. Direct exports amount to 100,000 and about 150,000 have been exported fitted to cars. Production is running at about the rate of 8,000 sets a month, of which nearly 5,000 have sold at home, half of them to the public and half to car manufacturers. The present rate of production is thus higher than in any previous year except 1951. It is noteworthy that all cars coming from British factories to-day have special provision for fitting car radio or at least space for it.

At the recent Motor Show four manufacturers exhibited car radio receivers—E. K. Cole, Motorola, Pye and S. Smith and Sons. Their exhibits included a new receiver costing only £14, plus £5 16s. 8d. purchase tax, and this included fitting charges. It is an optional standard fitting in the Ford Popular and receives the BBC Home, Light and Third Programmes, in addition to many Continental stations. E. K. Cole offered instantaneous selection of three preset stations or normal tuning on medium and long waves on a set designed for cars of any make or year, and the prices range from £26 10s. to £28 15s. Motorola have marketed a telescopic aerial which emerges from its socket when the set is switched on and disappears when it is switched off. Strangely enough, car radio has never greatly interested amateurs, probably because of the special problems involved. In the first place, a car radio has to be heavily screened from the engine ignition and other electrical parts which might cause interference and output noises. Even screening the set by use of a metal cabinet is not sufficient entirely to eliminate interference. This has involved the production of special coils and circuits. There are, indeed, some almost insurmountable difficulties which arise when one commences the task of building a car radio. The size of the completed apparatus, decided by the space available, is an important factor. Miniature components are, of course, available, but the arrangement and spacing of these on the chassis is critical, if stray coupling between the stages is to be avoided.

A car radio is expected to operate off a very short aerial with a consequent loss of signal strength. This means that the set must be provided with a method of amplifying the received signal before it is passed on to the H.F. stage of the set. Although a tuned radio frequency circuit may be used the number of stages to be employed is limited to the H.F. section, due to interaction between them setting up oscillation. Thus the superhet is the only possible circuit to employ, as the number of stages is not limited. Here again, however, snags arise. Intermediate-frequency transformers have to be correctly aligned for their intended frequency or else trouble will arise with poor reception, and this involves the use of costly

alignment equipment. The use of such equipment requires specialist knowledge. The construction of a car radio receiver is thus likely to be more costly in the long run than buying a commercial receiver. The power supply for a car radio is another big problem.

As far as running a domestic portable from the car battery is concerned, the volume would be inadequate to overcome the noise of all but the quietest of cars; a frame aerial would not be satisfactory. A vibrator can be obtained which converts the 12 volts from the car battery to 90 volts H.T. and 1.5 volts or 7.5 volts L.T., as required, for about 25s., and an ordinary car aerial can be fitted. All sources of interference on a car will have to be suppressed as for a normal car radio.

One alternative is to modify one of the Government surplus American communication sets. The average commercial car radio uses a superhet circuit employing H.F. mixer, one or two I.F. stages, second detector, L.F. amplification and output stages. The construction of such a set is probably beyond the scope of most amateurs. It might be possible to evolve a simpler superhet circuit using mixer, I.F. and super regeneration, followed by starved grid pentodes and output stage. This, however, would not give good H.F. gain, but the L.F. gain would be considerable. Also, the background noise would be fairly high, but this would be offset by the engine noise anyway.

The average battery portable must have a frame aerial and this means that, as the car winds its way round our roads, fading will take place. One way out of the problem is to modify an A.C./D.C. set by changing the valves to 6 volt or 12 volt filament types, and deriving the H.T. from a motor generator or rotary transformer with 6 volt or 12 volt input and 230 volt 60 mA output.

In our January and February, 1951, issues we gave details of a car radio receiver which, readers have reported, has given very satisfactory results. I would, however, suggest some modifications. It was rather bulky by comparison with present-day standards. I think it should be constructed in three units—tuning control box, power pack and speaker. If smaller components, which are now more readily available on the market, such as B8A and B9A based valves are used in place of the more bulky octal-base type and a miniature two-gang condenser were substituted, the tuning control box could be compressed into a unit comparable in size to any ready-made receiver. I suggest also that the home-made coils be substituted where possible for proprietary coils.

A NEW HANDBOOK

"PRACTICAL TELEVISION CIRCUITS"

288 pages, 156 illustrations

15/- net or 15/6 by post from :

GEO. NEWNES LTD.

Tower House, Southampton Street, Strand, W.C.2

TRANSMITTING TOPICS

MORE ON PI NETWORK TANKS

By O. J. Russell, B.Sc.(Hons.), A.Inst.P. (G3BHJ)



FROM correspondence received it is clear that Pi network tanks are a subject of supreme interest among the amateur fraternity. This is largely due to their excellent reputation as a cure for TVI troubles. A few further notes on the use and refinements of Pi network tank circuits may be of interest.

First, however, it must be made quite clear that a Pi network tank circuit by itself is no guarantee of a cure of either TVI or of the radiation of spurious frequencies. The Pi tank is a powerful aid in the reduction of TVI causing harmonics, and coupled with a little elementary assistance in the form of screening and coaxial line feeds, will generally secure immunity from TVI. However, a point of some importance is that while the Pi tank strongly discriminates against high-frequency harmonics, largely because of its capacity output, it does NOT necessarily by itself guard against "sub-harmonic" radiations. Thus, if the P.A. is on say 40 metres, and is driven by a doubler stage, an appreciable amount of 80 metre energy may find its way to the P.A. anode. This 80 metre R.F. will not be very much attenuated by the 40 metre Pi tank, and may indeed reach the aerial. This does often happen, and a strong signal may be radiated in some cases upon the next lowest band to the one actually being used. This state of affairs may be responsible for the phenomenon of S9 plus signals on top-band calling "CQ Eighty Metres!" In fact, top-band stations have actually been heard calling stations who were radiating a strong fundamental of 80 metres and a strong "sub-harmonic" on 160 metres! In view of the strict control upon 160 metre emissions and the possibility of interference with vital services sharing

If this is done, the additional discrimination of the link and tuned circuits reduces spurious radiations, and in fact is essential if "sub-harmonic" radiation is to be avoided. A further specific against "sub-harmonics" is to drive the P.A. from a straight amplifier rather than from a doubler.

While the device has not caught on to any extent in this country, it should be noted that in the U.S.A.

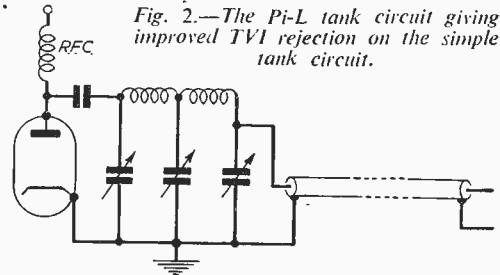


Fig. 2.—The Pi-L tank circuit giving improved TVI rejection on the simple tank circuit.

the use of the "Pi-L" tank circuit has been popularised as a measure to give an even better rejection of spurious frequencies than the straightforward Pi tank. It must be remembered that the use of high power and the general use of several alternative channels for TV, makes the TVI question in America much worse than at present over here. However, the institution of VHF FM broadcasts, and an alternative TV programme in this country will naturally intensify and complicate the TVI and interference problems facing the British amateur. Accordingly, more drastic measures than the straightforward Pi network may well become needed. As may be seen from Fig. 2, the "Pi-L" network consists of a straightforward Pi network feeding into an L network. By this means a further substantial reduction of high-frequency radiation is secured, although the effect upon "sub-harmonics" is not very great. Readers of an experimental turn of mind may care to experiment in this direction, although the "Pi-L" tank is naturally a complication if multi-band operation is desired.

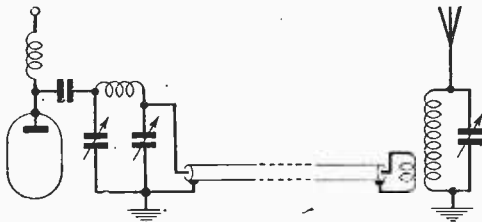


Fig. 1.—Link coupling the network to an aerial tuner.

that band, not to mention the possibility of radiation on frequencies outside the authorised amateur bands, it is essential that measures be taken to prevent the likelihood of such happenings.

Fortunately this is not a difficult matter. It is strongly urged that a Pi tank output never be coupled directly into an aerial. In all cases an auxiliary aerial tuner should be used. This should be coaxially linked to the output of the Pi tank as shown in Fig. 1.

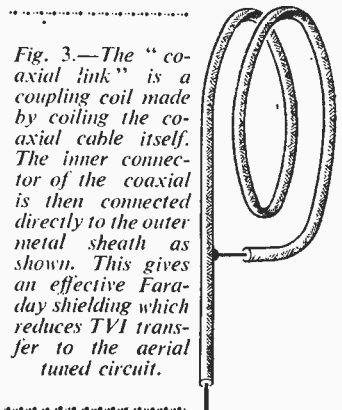


Fig. 3.—The "coaxial link" is a coupling coil made by coiling the coaxial cable itself. The inner conductor of the coaxial is then connected directly to the outer metal sheath as shown. This gives an effective Faraday shielding which reduces TVI transfer to the aerial tuned circuit.

Some Dodges

However, before complex networks become necessary in the future, there are a number of dodges that may help in the reduction of TVI where a straightforward Pi tank link-coupled into an aerial tuning unit does not provide enough TVI reduction. One device capable of assisting in TVI reduction, is the "coaxial link," as shown in Fig. 3. In effect, this provides a Faraday shield for the link coil, and

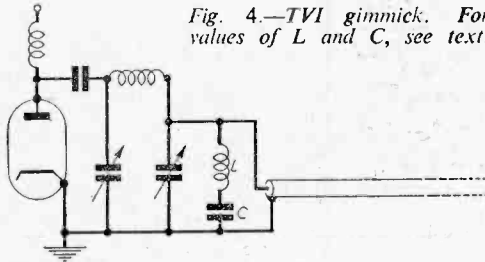


Fig. 4.—TVI gimmick. For values of L and C, see text.

virtually eliminates capacitive transfer of TVI harmonics from the link winding to the aerial loading or tuning coil. In the case of a tightly-coupled link coil of the unshielded variety, there may be an appreciable capacitive coupling to the aerial coil, which may suffice to transfer TVI causing harmonic frequencies to the aerial and hence into neighbouring TV receivers. The menace of TVI is highlighted by the recent report of TVI from a transistor top-band transmitter, so that the reader may rest assured that TVI is not necessarily cured by the application of just one measure! In fact, TVI is generally only to be cured by the application of several methods. The "coaxial link" therefore is a very useful weapon in the armoury of "anti-TV I" devices!

A further device of proven merit in increasing the efficacy of Pi network tank circuits, is the "TVI Gimmick." In this case part of the output capacity of the tank circuit is a small capacitor say of 50 pF. This may be wired directly across the coaxial output socket. However, in flat defiance of the edict that "R.F. leads must be short," the lead to one side of the condenser consists of a few turns of wire of say 1/16 in. diameter made by coiling the lead round a suitable former such as a pencil. Four or five turns is a useful size to start with, at any rate for London area transmissions. For the higher frequency TV channel areas three or four turns only may be required. If a "grid dip" oscillator is handy, the "gimmick" is resonated to the local TV channel by squeezing or pulling apart the turns of the coiled lead. In fact, with a "grid dipper" the "as is" frequency of the "gimmick" may be measured, which will immediately indicate whether the coil needs adjustment. If the "dip" frequency is higher than the TV channel, the coil needs to be squeezed to bring up the inductance, or a slightly larger coil may be needed. If the "gimmick" "as is," tunes to too low a frequency, pull out the turns until it does resonate on the TV channel, or, if necessary, fit a smaller coil. Final adjustment may be made by watching the screen of a TV receiver, while squeezing the coil to

adjust inductance. In the case of TVI, where a grid dipper is not available, the coil must be adjusted while watching the receiver for minimum TVI. The "gimmick" operates as a series resonant circuit for TVI frequencies, and effectively prevents them from being passed along the coaxial cable. The final line up of the "gimmick" is best carried out with the coaxial cable attached to the output socket, in order that the circuit be resonated under actual working conditions. Fig. 4 illustrates the "gimmick" connections.

Tuning Units

In view of the importance of using a suitable aerial tuning unit to back up the Pi network tank, it may be as well to review some of these. In the case of a simple series-tuning unit for loading up a wire in the Marconi fashion, Fig. 5, illustrates one way in which this is often done. The coaxial output link is taken directly into the series-tuned circuit.

In Fig. 6, is illustrated one way in which the parallel tuned version of Fig. 5 might be directly coupled by a tapped-in coaxial feeder to the Pi network output. Neither of these arrangements is to be recommended, as TVI frequencies might be directly transferred to the aerial. Such arrangements might, in fact, be satisfactory in a few cases in areas where the TV signal is strong enough to over-ride TV, or, in fact, might be just adequate on the lower frequency bands such as 160 metres and 80 metres

where TVI is less pressing than upon the higher frequency bands. Accordingly the link coupled versions shown in Figs. 7 and 8 are recommended as the use of link coupling, particularly if of the "coaxially shielded" type of link coil, gives further discrimination against TVI.

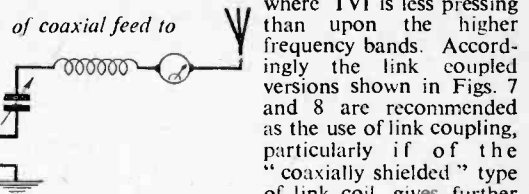


Fig. 5.—Direct connection of coaxial feed to a series-tuned circuit. This is not recommended from the TVI viewpoint.

In this connection of aerial coupling, the feeding of conventional centre-fed or end-fed aerials offers little difficulty. However, in some locations, especially where the shack is located at the top of a house, the question of long earth leads may arise. For Marconi-operated systems, the earth lead forms part of the

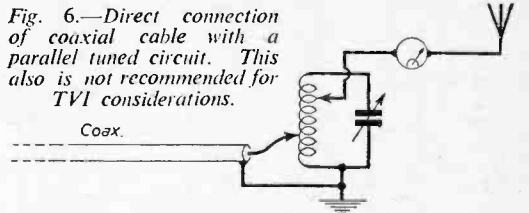


Fig. 6.—Direct connection of coaxial cable with a parallel tuned circuit. This also is not recommended for TVI considerations.

aerial, so that it is inadvisable to earth the transmitter to the lead used for the aerial return. Moreover, depending upon circumstances, it may be found that the earth lead may be dispensed with. In general the use of balanced two-wire centre-fed systems will be found more satisfactory than unbalanced systems wherever there is difficulty in obtaining a good, short earth lead. Balanced systems do not depend upon an efficient earth connection for correct operation, and may often work better without an earth lead at all in cases where a long earth lead or an inefficient earth is involved.

Novel Scheme

One interesting arrangement that has arisen as a result of correspondence, is the aerial shown in Fig. 9. This is a top length of 88ft. overall, including a 73ft. length outside, and a 15ft. length of lead in to the shack. While such a length might be fed directly from a Pi tank on some band by connecting directly to the coaxial output of the Pi network, this is not recommended. An earth lead of some 14ft. in length is also included. An odd length of wire of this amount offers some problems in feeding. On top band and on 80 metres, it can be loaded up as a Marconi with a series-tuned circuit. However, on 80 metres, it could also be loaded up fairly well with a parallel-tuned circuit. In fact, the top length could be either series- or parallel-tuned on 40 metres, 20 metres and 28 Mc/s and the earth lead would be needed at any rate for the series tuning connections. On 21 Mc/s the top definitely requires parallel tuning as it is four half wavelengths long, and the earth would probably not be required. This example is a further illustration of the fact that exact resonant lengths of wire are not necessarily required, provided that the tuning and feeding arrangements are correctly adjusted.

From the radiation viewpoint for simple single wire aerials, there is no advantage in an exact resonant length, provided that R.F. is effectively fed to the aerial. Resonant lengths merely happen to be easy to load in some cases. However, it is not generally realised that an aerial which "draws well" is usually far from resonant and its good "drawing" properties depend largely upon the impedance and reactance it presents to the coupling unit. In fact with feeder systems "good" "drawing" properties are usually the hallmark of a high standing-wave ratio. This point is raised, as it is generally considered a bad thing to have a high standing-wave ratio on feeders. However, a feeder of the open wire resonant type with a high standing-wave ratio may be more efficient than some coaxial cables correctly matched. This may not please the purists, but it is also a fact that radiation from a balanced open wire line has little to do with the standing-wave ratio. It is unbalance that is responsible for excessive radiation. Coaxial cable may not be free from radiation, in fact

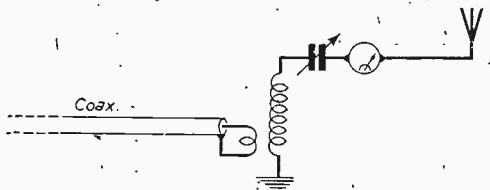


Fig. 7.—Link coupling of the series-tuned circuit offers advantages from the TVI standpoint.

the practice of feeding a dipole with coaxial usually ensures that the outer cable sheath carries a sizeable amount of R.F. and the cable certainly radiates!

The significance of the above observations is that radiating feeders may carry TVI interference close to TV aerials, so that a further source of trouble may be apparent. It is unfortunately true that the dogmatic acceptance of legends and fallacies may obscure

the solution of TVI problems. Therefore, do not assume that resonant open wire feeders are necessarily potent radiators. Moreover, do not assume that coaxial feeders are free from radiation. If the outer sheath carries R.F. it will inevitably radiate.

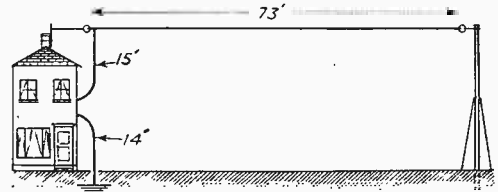


Fig. 9.—A problem aerial that can be fed from a tuning network: link coupled to a Pi tank transmitter. 1.8 Mc/s: Use series-tuned aerial circuit. 3.5 Mc/s, 7.0 Mc/s, 14 Mc/s, 28 Mc/s: Use either series or parallel tuning. 21 Mc/s: Use parallel tuning.

If a dipole is to be fed from coaxial cable, ensure that a balance to unbalance transformer is used at the dipole, so that the possibility of R.F. travelling backwards over the outside of the sheath is minimised.

Finally, if you are troubled with TVI, and have turned to a Pi network tank circuit as a relief, arm yourself with a few essential instruments to check TVI emissions. One such item is a grid dip oscillator which will enable valuable measurements and observations to be made. In the absence of a sensitive receiver covering the TV channels, a TVI "sniffer" should be acquired, borrowed or made. This consists

of a couple of R.F. stages tunable over the TV channels together with a crystal diode detector and microammeter. The sniffer will locate leaks of R.A. from screens, leaks around the transmitter cabinet, TVI R.F. transferred out of the transmitter and the presence of TVI harmonics at the aerial coupler, on the coaxial sheath and on the aerial itself. The adjustment of trap circuits, TVI "gimmicks," and link suppressors is greatly facilitated by these two indispensable aids. Without them the use of a Pi network to eliminate TVI is little more than a pious gesture of faith. With them the elimination of TVI is made a very much more certain proceeding.

Earth Connection

While from an R.F. point of view the use of an earth connection may be optional, it is certainly not so from two important points. Audio equipment such as a modulator may definitely need an earth connection for one thing. For another, it is essential that an earth be available so that aerials when not in use may be earthed to avoid the accumulation of static, and also in the presence of thunder storms. Even a small aerial can collect a dangerous charge in thundery weather. Therefore, do not neglect the provision of the best and heaviest and most direct earth connection possible. In any case, gear, particularly expensive receivers, may be badly damaged from the effects of induced static charges. An earthed aerial by dissipating static charges may in fact prevent a discharge of lightning striking the neighbourhood.

Osram

AUDIO VALVES

The following valves are outstanding in the current range of Osram audio valves and offer unsurpassed performance, reliability and long life to the discriminating user.

★ **Z729** 1st stage voltage amplifying amplifier pentode. The valve which has set the standard in its class where minimum hum and microphony are essential.

★ **B309 (12AT7) B329 (12AU7)** Double triode voltage amplifiers.

★ **N709** The high output pentode for all domestic amplifier purposes.

KT66 The world famous beam tetrode specified for the Williamson amplifier. The standard output valve for all medium power high quality amplifiers.

KT61 An efficient output beam tetrode for domestic receivers and small amplifiers.

KT33C An efficient output beam tetrode for DC/AC equipment.

PX4 The popular directly heated power triode which made true high quality sound available to the home constructor.

★ **DA42** A new indirectly heated high power Class B triode for industrial amplifiers.

★ Specified for the OSRAM 912 high quality amplifier.

Write to the Osram Valve and Electronics Department for full technical information, circuit and application data.


THE GENERAL ELECTRIC COMPANY LIMITED, MAGNET HOUSE, KINGSWAY, W.C.2

NEW!

EXPERIMENTAL KITS in Radio, T.V. etc.

LEARN THE PRACTICAL WAY

Specially prepared sets of radio parts (which you receive upon enrolment) with which we teach you, in your own home, the working of fundamental electronic circuits and bring you easily to the point when you can construct and service radio sets. Whether you are a student for an examination; starting a new hobby; intent upon a career in industry; or running your own business — these Practical Courses are intended for YOU — and may be yours at very moderate cost.

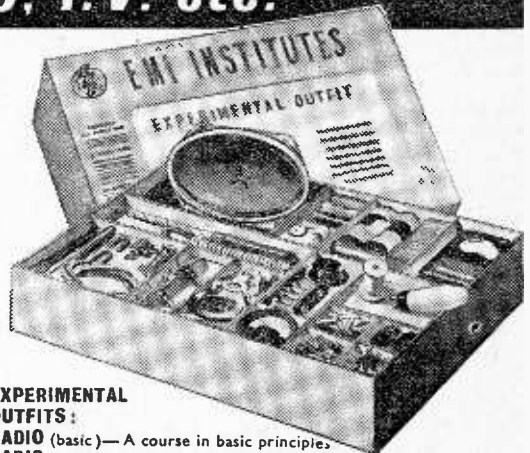

EASY TERMS FROM 15/- A MONTH

All lessons and equipment supplied immediately and become your own property.

POST THIS COUPON TODAY

Please send me your FREE book on Practical Courses:
To: E.M.I. INSTITUTES, Dept. 32X, Grove Park Road, London, W.4.

NAME

ADDRESS

SUBJECT(S)

EXPERIMENTAL OUTFITS:

RADIO (basic) — A course in basic principles.

RADIO — Instruction and equipment from which you build a Radio Receiver.

TELEVISION — Instruction and equipment for building a Television Receiver.

Also for Mechanics, Electricity, Chemistry, Photography, Carpentry, Draughtsmanship, Commercial Art, Amateur S.W. Radio, Languages.

E.M.I. INSTITUTES The only Postal College which is part of a world-wide Industrial Organisation

Smith's for Technical Books



Books on the theory and practice of electronics, new developments, circuit design, and other specialized subjects can be quickly supplied through your local Smith's shop or bookstall.

Your copies of *PRACTICAL WIRELESS* can be bound into attractive volumes; and all your stationery and printed matter supplied through our local branch.

W. H. Smith & Son

for **SPECIALIST BOOKS**

• Head Office: Strand House, London, W.C.2

G2AK

Season's Greetings

G2AK

RACK SIZE CHASSIS.—17in. long x 2½in. deep x 12in., 16/6; x 10in., 15/-; x 8in., 14/- P. & P. 1/- All 16 s.w.g. ALI.

POCKET VOLTMETERS. Dual range, 0-15 v. and 0-250 v., 345 O.P.V., M.C. Worth 50/- Our price 17/6 post free.

CRYSTAL HAND MICROPHONES. High quality, very sensitive. Chrome finish, complete with screened lead and standard jack plug. Our price only 25/- ea. Few only. **VALVES.** B7G base, 1T4, 1S5, 1R5, 1S4, 3S4, 3V4, 7/6 ea. or 4 for 27/6. 807's, 10/- ea. or 2 for 17/6. Most of the 1.4 v. B7G range available at 8/6 ea.

HEADPHONES. Low resistance type CLR No. 3, 9/6. DLR No. 2, 13/6. High resistance CHR Mark 2, 17/6, and the most sensitive of all DHR, No. 5B, 18/6 per pair: P. & P. 1/- pair.

METERS.—0-5 ma. 2in. square, 10/- 0-50 ma., 7/6. 0-10 A., D.C., 7/6. 0-1 ma., 20/- 0-350 ma. thermo., 7/6. 0-4 A., 5/- 2½in. flush 0-100 ma., 0-10 ma., 12/6 ea. **Germanium Diodes,** 2/- ea., or 6 for 9/- **Deaf-Aid Crystal** mike units, 12/6 ea.

V.H.F. FANS. Air Space Co-axial Cable, 150 ohm, good to 600 Mc/s; normal price, 3/11 per foot. Our Price, 20 yard coil, £1. Very limited quantity available.

FISK SOLARISCOPIES.—Complete with charts. Give World time, light and darkness paths. Invaluable to the DX man. List 21/-, our price 7/6, post free.

PANL Home Crackle. Black, Brown or Green, 3/- tin. P. & P. 8d.

TEST METER. 7 ranges as follows: 1.5 v. 3 v. 150 v. 6 ma., 60 ma., 5,000 ohms, 25,000 ohms, 2½in. Dia. scale M.C. meter. Rotary selector switch. Black bakelite case, 6 x 4½ x 4½, fitted with removable lid, also provision for internal batts., ranges can be easily extended. Bargain Price, 30/-, plus 1/6 post.

NEW MULLARD QUALITY AMPLIFIER. Chassis and all specified parts, available from stock. Postage free on all orders over £1 except where specifically stated. **PLEASE PRINT YOUR NAME AND ADDRESS.**

C. H. YOUNG, G2AK

All callers.

110, Dale End,
Birmingham 4 (CEN 1635)

Mail Orders to Dept. "P"

102, Holloway Head,
Birmingham 1 (MID 3254)

SOUTHERN RADIO'S WIRELESS BARGAINS

TELESONIC 4-Valve Battery Portable. Complete with Hivac Valves. In Metal Carrying Case. Simply converted to Personal Portable. £2 including Conversion Sheet.

TRANSMITTER-RECEIVERS. Type "18" Mark III. COM-PRISING SUPERHET RECEIVER and TRANSMITTER. TWO UNITS CONTAINED IN METAL CARRYING CASE. Complete 8-Valves. BARGAIN CLEARANCE OF REMAINING STOCK, £4/10/0

RECEIVERS TYPE "109." 8-VALVES WITH VIBRATOR PACK FOR 6-volts BUILT-IN SPEAKER. 1.8 to 8.5m/cs. Contained in Metal Case. Perfect. 100 ONLY, £5. Bargain Clearance of Remaining Stock.

BOMBSIGHT COMPUTERS. Ex-R.A.F. New. Contains Gyro Motors, Rev. Counters, Gear Wheels, etc. etc. Ideal for Model Makers, etc., £3/5/0, plus 10/- carriage.

CRYSTAL MONITORS. Type 2. New in Transit Case. Less Crystals, 8/- each.

LUFBRA HOLE CUTTERS. ADJUSTABLE ½in. to 3½in. For Metal, Wood, Plastic, etc., 6/6.

RESISTANCES. 100 Assorted. Useful Values, Wire end, 12/6 per 100.

CONDENSERS. 100 Assorted. Mica, Metal Tub, etc., 15/- 100.

PLASTIC CASES. 14in. by 10½in. Transparent, ideal for Maps, Photos, Display, etc., 5/6.

STAR IDENTIFIERS. Type 1 A-N. Covers both Hemispheres. In Case, 5/6.

CONTACTOR TIME SWITCHES. Complete in Sound Proof Case. 2 Impulses per sec. Thermostatic Control, 11/6.

REMOTE CONTACTORS for use with above, 7/6.

MORSE TAPPERS. Standard Type ex-Govt., 3/6. Heavy Duty Type "D", 8/6. COMPLETE MORSE PRACTICE SET with BUZZER, 6/9.

DIMMER CONTROLS. Bakelite. Wire Wound. New, 1/3 each.

MAGNETIC RELAYS SWITCH. Bakelite, 5 c/273, 2/6 each.

METERS AND AIRCRAFT INSTRUMENTS. Only need adjustment or with broken cases. TWELVE INSTRUMENTS (including 3 brand New Aircraft Instruments), 35/- for TWELVE ITEMS.

Full List of RADIO BOOKS, 2½d.

SOUTHERN RADIO SUPPLY LTD.,
11, LITTLE NEWPORT STREET, LONDON, W.C.2


GERrard 6653

SHORT-WAVE SECTION

BUILDING COMMUNICATIONS RECEIVERS

2.—THE INTERMEDIATE-FREQUENCY STAGES

(Continued from page 630, October issue)

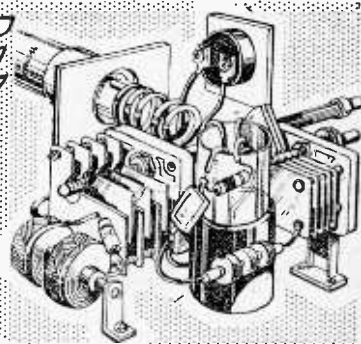

THOUGH the I.F. stages of a simple communications receiver may not differ greatly from general receiver design, there will usually be a number of added features, while larger receivers may employ very complex circuits. Additional sensitivity and selectivity will normally be required, with high gain, often manually controlled, and variable selectivity. Because no variable tuning is required, the I.F. stages of a receiver lend themselves well to modification. If space is available, there is usually little difficulty in adding one or more extra I.F. stages to an existing receiver, or making other changes. Such alterations can greatly improve sensitivity and selectivity, though the overall performance of a receiver is not, of course, wholly governed by the I.F. amplifier section.

Fig. 1 shows a circuit which is typical of many of the smaller communications type receiver, and which is capable of giving excellent results. (Though the popular 6K7 valve type is indicated, any other variable-mu R.F. pentode type can be employed.) This circuit is very straightforward, the only departure from general receiver design being in the

provision of an I.F. gain or sensitivity control. A 50 K potentiometer is used for this, operating in the first I.F. stage. If both I.F. stages are to be controlled, the potentiometer may be common to both cathode circuits. In some cases A.V.C. is not applied to the stage thus controlled, the I.F. transformer secondary being returned directly to the H.T.—line.

Such a circuit may give high gain for the number of valves employed. The transformers may be air-cored, with pre-set trimmers; or, alternatively, dust-cored types with adjustable cores. The latter are more general, in view of their small size and high efficiency. For general purposes, an intermediate frequency of 465 kc/s is satisfactory, and enables readily obtainable "unit" signal-frequency and oscillator coils to be used in R.F. and F.C. stages, for all bands.

As each I.F. transformer will be contained within its own screening can, stability may easily be maintained. Grid and anode leads should be short and direct, and may be screened. If the valves are of the clear glass type, they should be contained within screening cans. The detector is of ordinary type, and a double-diode-triode is equally suitable.

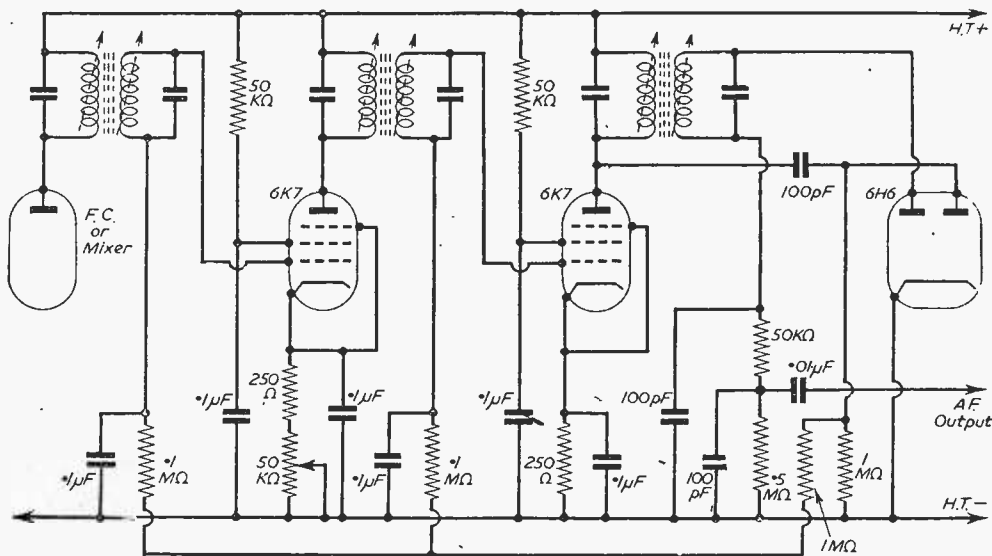


Fig. 1.—A two-stage I.F. amplifier.

of any transmitter essential are best reserved for use solely when conditions require.

As mentioned, variable selectivity is possible with the circuit in Fig. 2 by adjusting the capacity of C1 or C2, or both. This also applies to the circuits in Fig. 3. With that at "B" a variable-selectivity control may readily be arranged by using coupling windings with one or two tapings, the number of turns being selected by means of a rotary switch. As the number of turns is reduced, selectivity will increase.

In other cases it may be more feasible to cut out some stages of the I.F. amplifier, and a circuit enabling this to be done is shown in Fig. 4. Here the degree of selectivity at the "Sharp Tuning" switch position will depend primarily upon the values of C1 and C4, and may be very high. At the "Medium" switch position, two I.F. transformers are eliminated, and selectivity is to some extent adjustable by changing the capacity of C2. At the "Flat" position, both top-capacity coupled I.F. stages are cut out, and the degree of selectivity obtained is that usual with the standard superhet circuit with one I.F. stage and two I.F. transformers. If the top-capacity couplings are loose, the overall gain may remain reasonably uniform for all settings of the selectivity switch.

When a large number of I.F. transformers are employed, correct alignment is very necessary. With such selective circuits, signals may be greatly weakened, or become inaudible, if one stage is incorrectly trimmed. With the selectivity control (if used) at maximum, all the I.F. transformers should be peaked so that any further adjustment to any trimmer or core only reduces volume. This will be the normal operating setting, except when the selectivity and gain are sufficiently high to enable a "flat-topped" response to be obtained by slightly staggering the exact frequencies to which the I.F. transformers are set.

When several I.F. stages are used, a good layout,

with adequate screening, becomes necessary. Any instability by back-coupling through the H.T. circuits may be avoided by decoupling each stage, as shown in Fig. 4. Provision for manual control of I.F. gain, and for rendering the A.V.C. inoperative, will usually be included, as explained, in conjunction with the features in Figs. 2, 3 and 4.

Crystal Filter

A circuit for this will be given next month (Fig. 5) and it employs a 465 kc/s quartz crystal. (If an I.F. other than 465 kc/s is employed, the frequency of the crystal would be chosen accordingly.) Such circuits permit of a very high degree of selectivity, though adequate selectivity can be secured without the use of a crystal. Its main advantage lies in providing high selectivity without making a large number of I.F. transformers necessary.

C1 should be about 2 to 20 pF, and is fully variable, being a phasing control able to operate because the secondary of the I.F. transformer is centre-tapped. If such a tap is not available, and cannot be provided, a "butterfly" condenser may be used for trimming the I.F. secondary, the rotor being wired to earth. C2 is the coupling condenser, and may be fixed, pre-set, or variable, as already described.

The characteristics of crystals of this type are such that gain is high at the exact crystal frequency, but very low at other frequencies so that side-band interference is eliminated. The effect had upon sidebands is to some extent controllable by adjusting C1, but the selectivity will normally be too high for speech reception. This difficulty is most simply overcome by the fitting of a "Crystal In," "Crystal Out" switch, which may be an on/off switch wired in parallel with C1.

Double Superhets.

In the next issue, double superhets will be dealt with.

(To be continued)

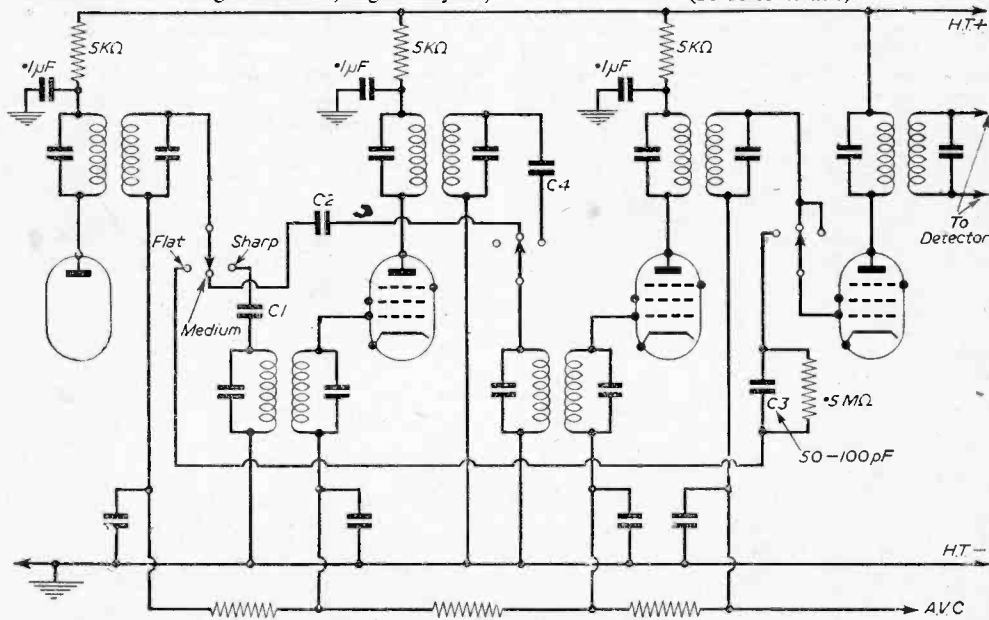


Fig. 4.—A variable-selectivity circuit

Surplus Bolometer Indicators

DETAILS OF COMPONENTS AVAILABLE ON THE SURPLUS MARKET

By E. G. Bulley

THESE tubes have a pure tungsten filament which is kept as straight as possible and is welded to two leads which are sealed to a glass envelope. The diameter of the filaments is extremely small and is usually in the order of one half of a thousandth of an inch. One will, therefore, appreciate the fragility of such tubes. The leads to which the filament is secured are sometimes "dumet" or some similar alloy which matches the coefficient of expansion of the glass envelope. Such indicators are, however, exhausted to a high degree of vacuum. This is essential to prevent ionisation occurring during the actual use of the tube. This point will be appreciated by the reader when he realises that such indicators are designed for use in or near R.F. fields. A typical Bolometer indicator is shown in Fig. 1, and for the interest of the reader the approximate dimensions are given so that he can appreciate their size.

An important rating of such tubes is what is termed the cold resistance. This applies to the filament, and is the resistance of the filament at a current value of something like 2 or 3 mA, the value naturally depending upon the tube type.

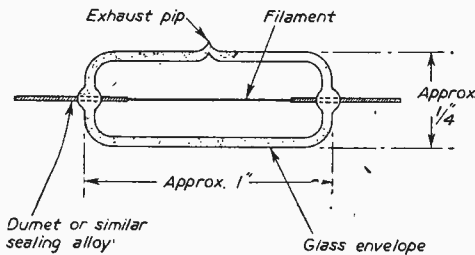


Fig. 1.—A typical Bolometer tube.

Such filaments, however, dissipate only milliwatts, and in actual operation they glow a very dull red.

Another important factor when using such tubes is that of the air temperature surrounding the glass envelope. Too high or too low a temperature will undoubtedly affect the characteristics of the tube, and it is essential, therefore, that the tube should be operated at or within the limits of the temperature rating of the tube in question.

Application

The application of these indicators is for the measurement of small radio frequency currents or power, and they are, therefore, used in laboratories engaged on research or development.

A basic laboratory bridge circuit in which a Bolometer tube is used is shown in Fig. 3, and is more or less an adaptation of the Wheatstone bridge. The latter is shown in Fig. 2, but is given only for reasons of comparison and will not be discussed in this article. However, for the convenience of the reader the Bolometer bridge will be explained, but before proceeding it is interesting to note that both bridge circuits are more or less the same, with

the exception that R1 in the Wheatstone bridge is replaced by a Bolometer tube in the other circuit shown in Fig. 3.

To operate such an instrument one must first balance the bridge circuit. This must be done by first ensuring that the instrument is not coupled or

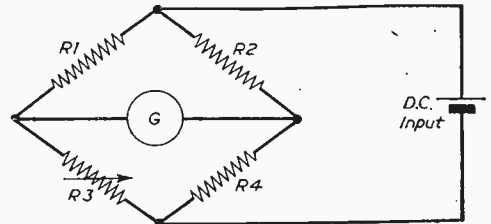


Fig. 2.—Basic Wheatstone bridge.

connected to an R.F. source. The actual balancing is accomplished by adjusting VR1 and noting the results on the milliammeter marked M. When this instrument is connected to an R.F. source R.F. current will flow through the Bolometer tube (BT) and in so doing the cold resistance of the filament alters and the bridge becomes unbalanced. This unbalancing effect can be seen on the milliammeter; a record or mental note should then be made on the amount of deflection that is shown on the meter. The instrument should then be disconnected from the R.F. source and a known direct current injected in its place until a similar meter deflection is recorded. The latter reading does, therefore, give an indication of the amount of R.F. current that has been generated. Nevertheless, one must ensure, as in all bridge circuits, that the D.C. voltage across the bridge is constant at all times, that is to say, the current passing through the bridge must be the same when both sets of readings are taken.

An important point to remember when experimenting with R.F., however small, is the prevention of R.F. being fed into parts of a circuit where it is not required. R.F. chokes must be included on either side of the indicator tube and should be as low a resistance as possible, otherwise the bridge will be unbalanced.

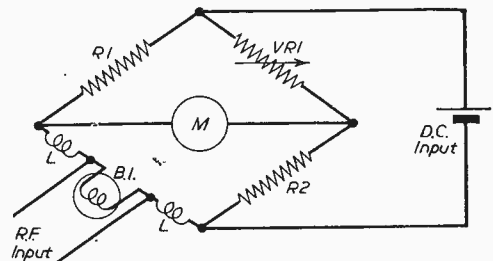


Fig. 3.—A basic laboratory bridge circuit using a Bolometer tube.

Radio Component Show, 1955

GROSVENOR HOUSE, APRIL 19TH TO 21ST

As a result of a ballot for space in the Radio Component Show, 131 stands have been allotted and 11 more will be allotted shortly, a record total. A preliminary list of exhibitors shows seven newcomers to the exhibition. The Ministry of Supply will again be exhibiting although no stand is yet allotted.

An innovation this year is that instead of circulating admission tickets, application cards will be issued, one to be filled in and forwarded by each intending visitor, in return for which he will receive a ticket if his application is approved. Prospective overseas visitors, however, will receive their tickets as in

previous years without application.

Considerable overseas interest in the exhibition is again expected, the exports of British radio and electronic components in the first nine months of 1954 having shown an increase in value of 30 per cent. as compared with 1953.

The full title of the exhibition is the Twelfth Annual Private Exhibition of British Components, Valves and Test Gear for the Radio, Television, Electronic and Telecommunication Industries. It is organised by the Radio and Electronic Component Manufacturers' Federation, 22, Surrey Street, Strand, London, W.C.2.

Member Firm	Stand No.	Member Firm	Stand No.
A.B. Metal Products, Ltd.	41	Ferranti, Ltd.	44
Advance Components, Ltd.	30	Fine Wires, Ltd.	114
Aerialite, Ltd.	85		
*A.K. Fans, Ltd.	123	Garrard Engineering & Manufacturing Co., Ltd.	64
Richard Allan Radio, Ltd.	8	Goldring Manufacturing Co. (Great Britain), Ltd.	17
Antiference, Ltd.	56	Goodmans Industries, Ltd.	47
Associated Electronic Engineers, Ltd.	92	Gresham Transformers, Ltd.	21
Associated Technical Manufacturers, Ltd.	88	Guest Keen and Nettlefolds, Ltd.	115
Automatic Coil Winder and Electrical Equipment Co.	72		
		Hallam, Sleigh & Cheston, Ltd.	117
Bakelite, Ltd.	127	Hassett & Harper, Ltd.	141
Belling & Lee, Ltd.	16	Hellermann, Ltd.	89
Sydney S. Bird & Sons, Ltd.	53	W. T. Henley's Telegraph Works Co., Ltd.	136
Geo. Bray & Co., Ltd.	109	A. H. Hunt (Capacitors), Ltd.	23
British Electric Resistance Co., Ltd.	35		
British Insulated Callenders Cables, Ltd.	57	Igranic Electric Co., Ltd.	12
British Mechanical Productions, Ltd.	76	Alfred Imhof, Ltd.	25
British Moulded Plastics, Ltd.	2	*Insulating Components & Materials, Ltd.	122
British Physical Laboratories, Ltd.	78		
A. F. Bulgin & Co., Ltd.	70	Jackson Bros. (London), Ltd.	74
Bullers, Ltd.	1	J. Beam Aerials, Ltd.	80
		Langley London, Ltd.	130
Carr Fastener Co., Ltd.	75	London Electrical Manufacturing Co., Ltd.	36
H. Clarke & Co. (Manchester), Ltd.	116	London Electric Wire Co. and Smiths, Ltd.	61
Collaro, Ltd.	10	Long & Hambly, Ltd.	31
Colvern, Ltd.	55		
Connollys (Blackley), Ltd.	9	Magnetic & Electrical Alloys, Ltd.	110
Cosmocord, Ltd.	79	*Mallory Batteries, Ltd.	97
Creators, Ltd.	105	Marrison & Catherall, Ltd.	132
		McMurdo Instrument Co., Ltd.	39
Daly (Condensers), Ltd.	100	Micanite & Insulators Co., Ltd.	101
Dawe Instruments, Ltd.	73	*Minnesota Mining & Manufacturing Co., Ltd.	126
Thomas De La Rue & Co., Ltd. (Plastics Division)	83	Morganite Resistors, Ltd.	15
Diamond H. Switches, Ltd.	6	Mullard, Ltd.	65
Dubilier Condenser Co. (1925), Ltd.	45	Mullard Overseas, Ltd.	94
Duratube & Wire, Ltd.	52	Mullard (Valves), Ltd.	95
		Multicore Solders, Ltd.	69
Edison Swan Electric Co., Ltd.	42	Murex, Ltd.	137
Egen Electric, Ltd.	37	Mycalex Co., Ltd.	3
Electro Acoustic Industries, Ltd.	40		
Electronic Components	108	James Neill & Co. (Sheffield), Ltd.	90
Electrothermal Engineering, Ltd.	120	N.S.F., Ltd.	49
H. J. Enthoven & Sons, Ltd.	58		
Erg Industrial Corporation, Ltd.	119	Painton & Co., Ltd.	46
Erie Resistor, Ltd.	29	Parmeko, Ltd.	27
Ever Ready Co. (Great Britain), Ltd.	125	Partridge Transformers, Ltd.	24

Member Firm	Stand No.	Member Firm	Stand No.
Plessey Co., Ltd.	67	Telcon-Magnetic Cores, Ltd.	111
Plessey International, Ltd.	68	Telegraph Condenser Co., Ltd.	54
Radio Instruments, Ltd.	84	Telegraph Construction & Maintenance Co., Ltd.	66
Reliance Electrical Wire Co., Ltd.	26	Telephone Manufacturing Co., Ltd.	33
Reproducers & Amplifiers, Ltd.	32	Thermo-Plastics, Ltd.	11
Resolound, Ltd.	50	Transradio, Ltd.	124
Rola Celestion, Ltd.	77	Truvox, Ltd.	28
Ross Courtney & Co., Ltd.	104	Geo. Tucker Eyelet Co., Ltd.	81
Salford Electrical Instruments, Ltd.	34	Tufnol, Ltd.	129
* Joseph Sankey & Sons, Ltd.	128	Vactite Wire Co., Ltd.	7
Geo. L. Scott & Co., Ltd.	118	Vitavox, Ltd.	86
Simmonds Aerocessories, Ltd.	140	Walter Instruments, Ltd.	18
F. D. Sims, Ltd.	133	Wego Condenser Co., Ltd.	63
Spear Engineering, Ltd.	121	Welwyn Electrical Laboratories, Ltd.	22
Stability Radio Components, Ltd.	51	Westinghouse Brake & Signal Co., Ltd.	13
Standard Insulator Co., Ltd.	142	Weymouth Radio Manufacturing Co., Ltd.	14
Standard Telephones & Cables, Ltd.	62	Whiteley Electrical Radio Co., Ltd.	138
Standard Telephones & Cables, Ltd. (Valves)	62	* Henry Wiggin and Co., Ltd.	87
Static Condenser Co., Ltd.	112	Wimbledon Engineering Co., Ltd.	59
Steatite & Porcelain Products, Ltd.	38	Wingrove & Rogers, Ltd.	71
Stocko (Metal Works), Ltd.	131	Wireless Telephone Co., Ltd.	20
Stratton & Co., Ltd.	60	Woden Transformer Co., Ltd.	82
Suffix, Ltd.	48	Wright & Weaire, Ltd.	4
Swift, Levick & Sons, Ltd.	139	* Zenith Electric Co., Ltd.	
H. D. Symons & Co., Ltd.	113		
Taylor Electrical Instruments, Ltd.	19		

* New exhibitors.

News from the Clubs

NEWARK AND DISTRICT AMATEUR RADIO SOCIETY
Hon. Sec.: Mr. R. Clayton, 160, Wolsey Road, Newark, or Mr. G. Bark (G3ITG), 7, Park Crescent, Newark, who is the hon. publicity officer.

THE Club continues its winter programme with a meeting on Sunday, December 5th, at the "Northern Hotel" (7 p.m.) with a talk on "Valve-voltmeters," by A. Hall. There will be practical demonstrations accompanying this. Arrangements for the Christmas Social Evening are in the hands of the committee, and members look forward to a very enjoyable evening at the "Northern Hotel." New members are always welcome and may contact the club secretary.

SOUTHEND AND DISTRICT RADIO SOCIETY

Hon. Sec.: J. H. Barrance, M.B.E. (G3BUJ), 49, Swanage Road, Southend-on-Sea, Essex. Telephone: 68545.

MR. K. F. CRISPIN, technical adviser to the Society, gave a talk on the "Function of Crystals in Modern Apparatus" at a recent meeting. Mr. Crispin pointed out that crystals, which were the only known means of detecting radio signals in the early days, and which later were replaced by valves, have now become adjuncts to valves. By new angles of cut and new methods of mounting, the natural quartz crystal can be made to produce oscillations of pre-determined frequencies; depending chiefly on the thinness to which the crystal has been ground. These frequencies are extremely accurate and reliable.

LEICESTER RADIO SOCIETY.

Hon. Sec.: W. N. Wibberley, 21, Pauline Avenue, Belgrave, Leicester.

THE Annual General Meeting of the Society was held in the Club Room at "Holly Bush Hotel," Belgrave Gate, Leicester, on October 11th. After receiving a report from the hon. secretary and the hon. treasurer, which showed both an increase in membership and finance over the past year, the election of officers of the Society followed.

For the year 1954/1955 the following were elected:

Hon. Founder President (in recognition of 25 years unbroken service to the Society): L. Ridgeway (G2RI); President: R. Frisby (G2CFC); Chairman of Meetings: W. McQueen (G3DVP); Hon. Secretary: W. N. Wibberley; Hon. Treasurer: D. Hoff (G3AWM).

A new committee of five members was elected, and the programme of the first session fixed.

On Sunday, December 12th, an inter-Society contest has been arranged with the Derby Radio Society on the Top Band, and it is hoped that all Midland stations will take part.

Transistor Experimental Group.—All members have been taking part in experimental transmissions and new equipment has been developed by G3CCA and preliminary tests have been carried out.

WARRINGTON AND DISTRICT RADIO SOCIETY (G3CKR)

Hon. Sec.: G. H. Flood, 32, Capesthorpe Road, Orford, Warrington, Lancs.

RECENT lectures have been on "Radio Control for Models," with a demonstration of Mr. W. Sanson's home-constructed motor launch, and an example of the G.P.O. "Two-Motion Type Selector Unit," by Mr. A. Pearson. A visit to a local automatic exchange is being arranged.

COVENTRY AMATEUR RADIO SOCIETY

Hon. Sec.: J. H. Whitty, 11, St. Patrick's Road, Coventry.

AT the Annual General Meeting held on September 27th, 1954, the following officers were elected:

President: L. Gardner (G5GR); Chairman: D. W. Harries (G3RF); Secretary: J. H. Whitty (G3HDB); Treasurer: K. Barber (G3HDP).

TORBAY AMATEUR RADIO SOCIETY

Hon. Sec.: L. H. Webber (G3GDW), 43, Lime Tree Walk, Newton Abbot.

IN the absence of the chairman (G2GK), the October meeting was held under the chairmanship of the hon. Secretary (G3GDW).

A hearty welcome was extended to ZC4GT, who is home on leave, and who was making enquiries as to the full list of countries whose amateurs are licensed to work on Top Band. G3GDW gave a short account of the recent Low Power Field Day in which he took part.

A discussion followed, on the possibility of a Social Supper being held—some time in the New Year—for members and their ladies. Further information to follow.

The TV Interference Committee of the Society—recently formed under the leadership of G3AVF, has reported that it has successfully co-operated with the authorities in the case of complaints of T.V.I. against one of the members.

Any visitors to the district are always welcome.

Volume Controls

Midget Elliptical type. Long spindles. Guaranteed 1 year. All values 10,000 ohms to 2 Meg-ohms.

80 ohm COAX

STANDARD 1/4 in. diam. Spindles. Guaranteed 1 year. GRAIN-1/4 IN. ONLY 8d. yd.

BALANCED TWIN FEEDER per yd. 6d. } 80
TWIN SCREENED FEEDER per yd. 1/4 } ohms
50 OHM COAX CABLE, 8d. per yd. 1/4 in. dia.

SPECIAL. 8 em-l-a-r spaced, polyneus. 80 ohm Coax 1/4 in. diam. Stranded core. Losses out 50% 9d. (just released) yd.

RESISTORS.—All values: 10 ohms to 10 meg., 1/2 w., 4d.; 1 w., 8d.; 1 w., 8d.; 2 w., 1/4; High Stability, 1 w., 1/2. Preferred values 100 ohms to 10 Meg.

ALL WAVE RADIOGRAM CHASSIS THREE WAVEBANDS FIVE VALVES S.W. 16 m.—50 m. LATEST ORHAM M.W. 200 m.—550 m. X79, W77, DE77. G.W. 800 m.—2,000 m. N78, U78.

WIRE-OUND RESISTORS.—Heat Makes Miniature Ceramic Type—5 w., 15 ohm to 4 K., 1/2; 10 w., 20 ohm to 6 K., 2/3; 15 w., 30 ohm to 10 K., 2/9; 3 w. Vitreous, 12 K. to 25 K., 3/4.

Brand New and Guaranteed w/ 10in. P.M. Speaker, A.C. 200/250 Four position Wave-change Switch. Short-Medium-Long-Grain. Slow Motion Tuning. Speaker and Pick-up connections.

WIRE-OUND T.V.S. 3 WATT FAMOUS MAKE Standard Size Pots. 2 1/2 in. Spindles. High Grade. All Values. 100 ohms to K. 3/- ea. 50 K., 4/-. Ditto Carbon Track 50 K. to 2 Meg., 3/-. O.P. TRANSFORMERS.—Heavy duty 70 ma., 4/6. Small Tapped variety, 3/9.

High Q iron-dust core coils, 465 kc/s I.F. Latest circuit technique delayed. A.V.C. and Negative feedback. Output 4.2 watts. 8 ohms output transformer on chassis. Chassis size 13 1/2 x 5 1/2 in. Glass Dial—10in. x 4 1/2 in. horizontal or vertical type available. lit by 2 Pilot Lamps. Colour Black & Station names. J.W. Green, M.W. Red, B.W. White. Four Knobs supplied. Walnut or Ivory to choice aligned and calibrated. Chassis isolated from mains. PRICE £10/15/0. Carriage and Insurance, 4/6. (Without 10in. speaker, £9/15/0. Carr. & Ins., 4/6.)

L.F. CHOKES 10 h. 65 ma., 5/-; 20/25 h. 100/150 ma., 12/6; 5 h. 240 ma., 15/-; 1 h. 100 ma., 10/6. LYNX, 3h. 250 ma., 13/6. SIMPLEX, 10h. 150 ma., 10/6. MAINS TRANS.—Made in our own workshops to high grade specifications. Fully inter-locked and impregnated. Tapped from 230 v./250 v., Heater Trans., 6.3 v., 11 amp., 7/8; ditto 6.3 v., 3 amp., 10/6; ditto, 12 v., 75 amp., 7/8; 350-0-350, 80 ma., 6.3 v., 4.4, 5 v., 2.4, ditto 300-0-300, ditto 250-0-250, 21/-; AMPLIFIER TRANS. 250 v., 60 ma., 2 w., 4.3 v., 2.5 w., 1/2 w., 1/2 w., 1/2 w. master Auto Type, 35/-; Teleking, 30/-; LYNX, 30/-; Coronet, 30/-; Simplex, 35/-; Rewinds and Specials to requirements

Control 10/2, 3/9.

SOUNDMASTER SPECIALS.—Mains Trans., 35/-; L.F. Choke, 10/6; O.P. Trans., 5/6; Envelope, 6/6. Specialised Knobs, 3/9.

NEW BOXED VALVES GUARANTEED 1R6 8/- 6K74 6/6 12BH7 5/6 EC91 7/6 1S5 8/- 6K8 9/- 35L6 10/6 EF36 7/6 184 8/- V7127 9/- OZ1 8/6 EF39 9/- 1R5 8/- Pent4 9/- 807 10/6 EF30 Equip 384 9/- EF90 10/6 ECH12 12/6 516 5/6 3V4 8/- 6L6 10/6 6BE6 7/6 British 7/6 304 2/6 6125 15/- 6C9 12/6 Sylvania 506 10/6 6Q7 9/6 6BG6 12/6 Red 10/6 5Z4 9/- 6X4 8/6 6F4 11/6 EF91 8/- 6X4 7/6 6BH7 9/6 EF41 11/6 EF92 9/6 6AC7 8/6 6BK7 8/6 613 9/- 7C9 9/6 6AL5 7/6 6AL7 9/- 6V6 3/6 EF61 12/6 6AM6 9/- 6AN7 11/- DK91 8/- HV24 7/6 6AT6 10/6 6U6 (Y638) DP91 8/- PV9 11/6 6B8 7/6 6V6 8/- 1A F91 8/- PV2 10/6 6BA6 8/6 6X5 9/- DL92 9/- PNC25 8/6 6BD6 10/6 6AK5 10/6 DL94 8/- SP61 8/6 6BW6 10/6 7Y7 9/6 E1148 4/6 U22 9/6 6C4 7/6 912 5/6 EA30 2/- U25 12/6 6B9 9/6 12A6 7/6 6AL5 7/6 MU4 9/6 6HM8 3/6 12AX7 10/6 EB34 2/6 ECI80 12/6 6J5 7/6 12AT7 8/6 EF35 12/6 12AH8 10/6 6J7 8/6 12A16 10/6 EB91 7/6 PL81 12/6 6K7M 8/6 12Q7 10/6 EB33 9/6 8/0 9/-

WOODEN WALNUT CABINET.—12in. x 7in. x 5in. Tilt or super-tilt, comp punched chassis, dial, backplate, drive, pointer, etc., 28/6, plus post 2/6. TUNING.—Midget soldering iron, 200/250 v., or 230/250 v., 14 1/2 in. TYANA TRIPLE TRIF. Complete with detachable bench stand, 19/6. NEW SOLO MIDGET IRON.—25 w., 19/6. IDEAL FOR RADIO CONSTRUCTORS

Value Stock D.V.A. Valves at 1951 low tax prices. SPECIAL PRICE PER SET 1R5, 1T4, 1R3 and 384 or 3V4 ... 30/- 6R8, 6K7, 6Q7, 6V6, 5Z4 or 6X5 ... 37/6

C.T. HEATER ISOLATION TRANSFORMER.—Low leakage winding with 25% sec. boost. Ratio 1:1.25, 2 v., 10/6; 4 v., 10/6; 6.3 v., 10/6; 12 v., 10/6. MAINS PERFORMERS and Specials to Order, from 10/6 each.

MIKE TRANS.—Ratio 50:1, 3/9 ea., new and boxed.

W/OLDERS.—Pax: Int. Oct., 4d.; EF50, EA30, 6d.; B1A CRT, 1/3. Moulded: Int. Oct. 6d.; B7G, 9d.; with screening can, 1/6; B8A, B8Q, B9A, 1s.; VC197, 2/8. Ceramic: EF50, B7G, 1s.; ENG. and AMER. 5/-, 7- and 9-pin, etc., 1/-; TAG STRIPS, 2 or 3-way, 3/- or 5-way, 3d.; 6-way, 4d.; 9- or 10-way, 6d., etc.


T/V PRE-AMP.—Channel 1. Easily modified for other Channels or Converter use. Midget Chassis, 4 1/2 x 2 1/2 in. Complete with EF42 valve, coax. lead and plug. Price 1/6. Brand New Mfrs. surplus. Listed £12.5a. Special Clearance Price, 27/6; p. & p., 1/6.

TOGGLE SWITCHES EX-GOVT.—"On-off," 8d. Erson M.c. solder 60/40, 16 g. or 18 g., 5/8 lb. tin, 4d. yd. T.C. wire, 15 to 25 g.w., per yd., 1/4. T.C. Connecting wire, 10 colours, 8 strands, 24 in., 2d. yd. 2 K. 5 w. H.D. w/w Pots, 6/6, 10, 25 K., Colvern w/w Pot, 1 1/2 in. spindle, 3/6. SCREENED GRID CAPS 1 Oct., or Mazda, 6d. ea. BULGIN HIGH VOLTAGE VALVE CAPS, 1 Oct., 1/-.

FUSES.—11in. all values 60 ma. 4d 10 s., 6d. ALADDIN FORMERS and cores, 1 1/2 in., 8d.; 1 in., 10d. SLOW MOTION DRIVERS.—Epicure type ratio 1:1, 2:1, 2:1. OCTAL CABLE PLUG (8-pin), with cover, 1/3. 200-250 Volt SELECTOR SOCKET (2 1/2 in. x 1 1/2 in.) with 1/4 in. PILOT LAMPS.—6.3 v., 3a., 8d.

SPRING FEET.—Expanded and nickel metal, 1 1/4 in. by 3/4 in., 3/-; EXT. L.—Switched Socket, on-off and parallel switching, complete with plug, 2/6.

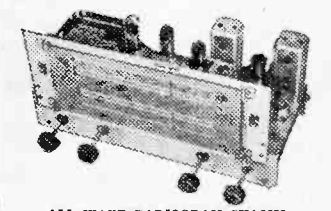MAIN DROPPERS. 3 in. x 1 1/2 in. Adj. Siders, 3 amp, 750 ohms, 4/9. 2 amp, 1,000 ohms, 4/3. LINE CORD. 3 amp, 60 ohms per foot, 2 amp, 100 ohms per foot, 2 way, 1/4 a yard; 3 way, 1/4 a yard.



ALL WAVE RADIOGRAM CHASSIS THREE WAVEBANDS FIVE VALVES S.W. 16 m.—50 m. LATEST ORHAM M.W. 200 m.—550 m. X79, W77, DE77. G.W. 800 m.—2,000 m. N78, U78.

Brand New and Guaranteed w/ 10in. P.M. Speaker, A.C. 200/250 Four position Wave-change Switch. Short-Medium-Long-Grain. Slow Motion Tuning. Speaker and Pick-up connections. High Q iron-dust core coils, 465 kc/s I.F. Latest circuit technique delayed. A.V.C. and Negative feedback. Output 4.2 watts. 8 ohms output transformer on chassis. Chassis size 13 1/2 x 5 1/2 in. Glass Dial—10in. x 4 1/2 in. horizontal or vertical type available. lit by 2 Pilot Lamps. Colour Black & Station names. J.W. Green, M.W. Red, B.W. White. Four Knobs supplied. Walnut or Ivory to choice aligned and calibrated. Chassis isolated from mains. PRICE £10/15/0. Carriage and Insurance, 4/6. (Without 10in. speaker, £9/15/0. Carr. & Ins., 4/6.)

BARGAIN OFFERS RECOMMENDED FOR ABOVE CHASSIS GREAT REDUCTIONS

Brand New Plessey 3-speed Autohancer Mixer Unit for 7, 10 and 12in. Records. Twin Hi-Fi Xial Head with Dupont magnet, stylus. Plays 4,000 records. Sprung mounting. Superb Quality. Bargain Price 91 kns., post free.

Table with columns: NEW BOXED VALVES GUARANTEED. Lists various vacuum tube types and their prices, such as 1R6 8/-, 6K74 6/6, 12BH7 5/6, etc.

SUB MINIATURE VALVES WIRE ENDS

Table listing sub-miniature valves with wire ends and their prices. Includes R.F. Pent. .026 v. Fil., L.F. Pent. 1.25 v. Fil., and various types like XPW 10, XPY 11, etc.

VCR97 £2 TESTED FULL PICTURE

P. & P. 2/-

CRYSTAL DIODE.—Very sensitive. G.E.C., 3/6. H.R. PHONES.—(Hi-grade Amer.), 15/6 pr. 8/6. BROWN'S, 4,000 ohms, 15/6 pr.

T.R.S. RADIO SPECIALISTS

70 1855. Buses 130, 190 and 133 pass door. THO, BRIGSTOCK RD., THORNTON open all day HEATH, SURREY. SATURDAY 10.00-12.00. £1 orders post free. Lists 3d. ALL MAINS TRANS.—1/- extra postage.

PYE Aerial Plug and Socket, 1/6 pr. 5in. RADIO SCREWDRIVERS.—Sheffield made blade, 2 1/2 in. x 1/4 in. Ins. handle, 3,000 v., 41d. each. CONDENSERS.—New Stock .001 mica, 6 kv., T.C.C. 5/8. Ditto, 12.5 kv., 9/8; 2 pf. to 500 pf. Mica, 6d.; .001, Mica or Tub. T.C.C. 500 v., .01 Sprague 500 v., .02 N.B.F. 500 v., 1 mfd. 350 v. Micramould Tub. 6d.; Hunts Moldair 500 v., 100 pf. mica, 1/2; 500 pf. mica, 1/2; 100 pf. mica, 1/2; 25 mfd. 1.6; 1 mfd., 600 v., 1/3; Tubular 5 mfd. 350 v., 1/8. SILVER MICA CONDENSERS.—10% 5 pf. to 500 pf., 1/2; 500 pf. to 3,000 pf., 1/3. DITTO 1% (ex stock) 1.5 pf. to 500 pf., 1/9. 515 pf. to 1,000 pf., 2/10.

ELECTROLYTIC ALL TYPES NEW STOCK.

Table listing electrolytic capacitors with specifications like Tubular Wire ends, 50/25 v. Plessey 1/9, 50/30 v. Plessey 2/-, etc.

SPECIALS.—Can Types. 500 mfd. 12 v. 3/-; 1,000 mfd. 4, 6, 10, 15, 20, 25, 30, 40, 50, 60, 75, 100 mfd. 6 v. 5/8; 1,500 mfd. 6 v. 4/0; 1 mfd. 1.5 kv. 7/6.

SENTERCEL RECTIFIERS. E.H.T. TYPE FLY-BACK VOLTAGES.—K3/25 2 kv., 4/3; K3/40 3.2 kv., 6/-; K3/45 3.6 kv., 6/8; K3/50 4 kv., 7/3; K3/60 4.5 kv., 12/6; K3/100 14 kv., 16/-. MAINS TYPE.—RM1, 125 v., 60 ma., 4/-; RM2, 100 ma., 4/9; RM3, 120 ma., 5/-; RM4 250 v., 275 ma., 16/-. KNOBS, GOLD ENGRAVED.—Walnut or Ivory, 1 1/2 in. diam., 1/8 each. "Focus," "Contrast," "Brilliant," "Brilliance On-Off," "On-Off," "Volume," "Vol. On-Off," "Tone," "Tuning," "Tretle," "Bass," "Wavechange," "Radio-gram," "S. M., L., Gram," "Record-Play," "Brightness." Ditto not engraved, 1/- each. POLYMER KNOBS.—Brown with white marking 1 1/2 in. diam., 1/8 each.

COLLS.—Wearite "P" type, 2/8 each. Demor "R" type, all dia. cond. 3/8 each. All ranges. REACTION COND.—0001, 0003, 0005 mfd, 3/6 ea.

BANKRUPT STOCK PEN TORCHES.—Drycell, chromium plated with vest pocket clip. Complete. New battery and bulb. 1/6 each. 8 or 9 pen torches, 1/6 each.

HANDLELITE.—Drycell, pocket or handbag flashlight. Complete. Battery and lens bulb. Listed 3/5. Our Price 2/6.

ALUMINIUM CHASSIS.—18 s.w.g. Plain, undrilled, folded 4 sides and riveted corners. lattice fixing holes. Strong and soundly constructed with 2 1/2 in. sides. 7in. x 4in., 4/6; 1 1/2 in. x 7in., 6/6; 1 1/2 in. x 9in., 8/6; 1 1/2 in. x 1 1/2 in., 10/6; and 13in. x 16in. x 3in., 16/6.

CHARGER TRANS. PRIM.—0/20-250 v. Sec. 0-9 v.-15 v. (for charging 6 v. and 12 v.) 1.5a., 13/0 2a., 16/0; 3 a., 18/6; 4 a., 21/-; 5 a., 26/-. FULL WAVE BRIDGE SELENIUM RECTIFIERS.—6 or 12 v. 11 amp., 8/9; 2 1/2 in., 11/3; 3 a., 12/6; 4 a., 15/-; 6 a., 23/6. Ditto F.W. only 6v., 1 a. (9 v.-0-9 v. A.C.) 5/8.

ACID HYDROMETER.—New ex-Govt. Unbreakable. Packaged in metal case, 7in. x 1 1/2 in. dia., 4/9. MIDGET CHOKES.—14 H.D. 2/8 each. 1 kv. 2/6.

BRIMISTORS.—C21 for 3 a. heater chains, 3/6. C22 for 1.5 a., or 2 a., 2/8. C23 (Pilot Lamp), 1/6. COPPER ENAMEL WIRE.—1 lb. 14 to 20 s.w.g. 2/6; 22 to 28 s.w.g., 2/3; 30 to 40 s.w.g., 3/6.

SWITCH CLEANER FLUID, 500 ml. 3/9. TWIN GANG TUNING CONDENSERS.—0005 mfd. midget with trimmers, 8/6; 375 pf. midget less trimmers and feet, 9/-; 0005 Standard size with trimmers and feet, 9/-; less trimmers, 8/6; ditto, solid, 2/3.

VIBRATOR POWER PACK (Jock Travis U.S.A.)—Compact Metal Can 7in. x 2 1/2 in. x 4 1/2 in. Input. Output 90 v. H.T., 8 v. and 1.5 I.T. Complete, 25/-; p. & p., 2/6. Rechargeable Battery Portable Sets.

LOUDSPEAKERS P.M., 3 OHM. 3in. Plessey, 12/6. Goodmans 4in. square, 15/6. 5in. 14/6. 6in. 16/-. 7in. Elliptical, 18/6. 8in. H. & A. 17/6. 10in. Plessey, 25/-; 6 1/2 in. with trans., 7/00 ohms to 3, 19/6.

I.F. TRANSFORMERS

465 Kc/s Slug tuning Miniature Circular Can, 2 1/2 in. by 1 1/2 in. diam. Fits octal W-holder out. out. High Q and good bandwidth. By Pye Radio. Two mounting feet. BRAND NEW, 6/9 PAIR

PREMIER RADIO COMPANY

B. H. MORRIS & CO., (RADIO) LTD.

OPEN TILL
6 P.M. SATURDAYS

(Dept. P.W.) 207, EDGWARE ROAD, LONDON, W.2

Telephone:
AMBASSADOR 4033
PADDDINGTON 3271-2

BUILD THESE NEW PREMIER DESIGNS

3-BAND SUPERHET RECEIVER

MAY BE **£7.19.6** Plus 2/6 Pk.
BUILT FOR & Carr.
Latest type Superhet Circuit using 4 valves and metal rectifiers for operation on 200/250 volts A.C. mains. Waveband coverage—short 16-50 metres, medium 160-550 metres, and long 900-2000 metres. Valve line-up 6K8 freq. changer, 6K7 IF, 6Q7 Detector AVC and first AF, 6V6 output. The attractive cabinet to house the Receiver size 12in. long, 6 1/2in. high, 5 1/2in. deep can be supplied in either WALNUT or IVORY BAKELITE or WOOD. INSTRUCTION BOOK 1/- post free, which includes assembly and wiring diagrams, also a detailed stock list of priced components.

CABINETS—PORTABLE

Model PC/1
Brown Rexine covered, 22/6.
Overall dimensions 15in. x 13 1/2in. x 5in.
Clearance under lid when closed 2 1/2in.
Model PC/2
Grey Lizard Rexine covered, 45/-.
Overall dimensions 15in. x 13 1/2in. x 6in.
Clearance under lid when closed 2 1/2in.
Model PC/3
Rexine type covering in various cols., 69/6.
Overall dimensions 16 1/2in. x 14 1/2in. x 10 1/2in.
Clearance under lid when closed 6 1/2in.
All the above Cabinets are supplied with Panel, Carrying Handle and Clips. Packing and Postage 2/6.

Send for details of the Premier Wide angle Television design which may be built for £30.

TRF RECEIVER

MAY BE **£5.15.0** Plus 2/6 Pkg.
BUILT FOR & Carr.
The circuit is the latest type TRF using 3 valves and Metal Rectifiers for operation on 200/250 A.C. mains. Wave band coverage is 180/550 metres on medium wave and 800/2,000 metres on long wave. The dial is illuminated and the Valve line-up is 6K7 H.F. Pentode 6J7 Detector and 6V6—Output. The attractive Cabinets to house the Receiver size 12in. long, 6 1/2in. high, 5 1/2in. deep, can be supplied in either WALNUT or IVORY BAKELITE or WOOD. INSTRUCTION BOOK 1/- (post free) which includes Assembly and wiring diagrams, also a detailed Stock List of priced components.

DECCA MODEL 37A

DUAL SPEED RECORD PLAYER
Includes turnover crystal pick-up with sapphire stylus and a light-weight plastic spring balanced arm. Heavy gauge pressed steel case with brown enamel finish in good quality for operation on A.C. mains 200/250 v. 50 c.p.s. Supplied complete, £6.19.6. Plus pkg. and carr. 5/-.

GARRARD S5

GARRARD Rim Drive 78 r.p.m., complete with magnetic pick-up and turntable, £4.19.6, plus 2/6 pkg. and carr.

TERMS OF BUSINESS: CASH WITH ORDER OR C.O.D. OVER £1.

4-WATT AMPLIFIER

MAY BE **£4.10.0** Plus 2/6 Pk.
BUILT FOR & Carr.
Valve line-up 6SL7, 6V6 and 6X5, FOR A.C. MAINS 200/250 VOLTS. The output Valve is of the beam type and feeds 4 watts into a specially designed output Transformer which is suitable for either 3 ohm or 15 ohm Speakers. Negative feedback is applied from the secondary of the output Transformer over the whole Amplifier to the input stage giving an excellent frequency response. Due to the high gain and wide range tone controls any type of pick-up may be used. Overall size 9 x 7 x 5in. Price of Amplifier complete, tested and ready for use, £5/5/-, plus 3/6 pkg. and carr.
INSTRUCTION BOOK 1/- (post free) which includes Assembly and wiring diagrams, also a detailed Stock List of priced components.

C. R. TUBES

VCR 517C 6 1/2in. picture. This tube is a replacement for the VCR57 and VCR517. Guaranteed full size picture. PRICE, 35/- Plus 2/6 pkg., carr., ins. VCR 516 9in. Blue picture. Heater Volts 4, Anode 4 Kv., in Manufacturer's original Carton. Plus 5/- pks., carr., ins. PRICE, £1.19.6.



COMPONENTS AVAILABLE FOR THE MULLARD AND OSRAM AMPLIFIER DESIGN

- T/V TECHNOLOGY
- RADIO ENGINEERING
- ELECTRONICS
- RADIO SERVICING

There's a big future in T/V and Radio. Act now! Increase your knowledge. Back up experience with a sound theoretical background. I.C.S. offer courses of instruction in—

T/V TECHNOLOGY
ADVANCED SHORT-WAVE RADIO
RADIO ENGINEERING
RADIO SERVICE ENGINEERING
RADAR
ELEMENTARY ELECTRONICS
FREQUENCY MODULATION

I.C.S. will also coach you for the following examinations:—

B.I.R.E.; P.M.G. Certificate for Wireless Operators; Radio Servicing Certificate (R.T.E.B.); C. & G. Telecommunications, etc., etc.

DON'T DELAY—WRITE TO-DAY for free descriptive booklet, stating which subject or examination interests you. Fees include all books needed. Examination students coached until successful. Reduced terms for H.M. Forces.

Dept. 170D, I.C.S., 71, Kingsway, W.C.2.

INTERNATIONAL CORRESPONDENCE SCHOOLS,
(Dept. 170D), International Buildings, Kingsway,
London, W.C.2.

Please send booklet on.....

Name..... Age.....
(Block letters, please)

Address.....



SOLDERING - SAFE - SIMPLE - SPEEDY

with the sensational

70/-
post free



PRIMAX—★

BALANCED GRIP SOLDERING GUN

★ NOW IN A NEW UNBREAKABLE CASE

The PRIMAX-SOLDERER is the ideal tool for any RADIO-TV-TELEPHONE mechanic or amateur. Just the tool for service calls and small jobs on the bench. A current of high amperage produced in the transformer will heat the soldering tip within 6 seconds. For semi-continuous soldering. Available for 110, 200/220 and 220/250v. A.C., 50/60 cycles (60w.). One year guarantee. Specially designed for easy soldering on hard-to-reach jobs.

- ★ TRIGGER CONTROL for semi-continuous use.
- ★ EXCLUSIVE ALLOY TIP—never needs re-tinning or filing lasts indefinitely under normal use and care.
- ★ INSTANT HEATING—Ready for soldering in 6 seconds.
- ★ COMPACT LIGHTWEIGHT—slips into pocket or tool-kit, weighs only 24 ounces.

Sole Distributors:—

S. KEMPNER, 19 Ebury Street, London, S.W.1

Tel. SLOANE 2447 & 3586 Through wholesalers and retailers

A VALVE TESTER

A COMPREHENSIVE TEST UNIT WHICH MAY BE USED ALONE OR IN CONJUNCTION WITH AN OSCILLOSCOPE

By R. Wilkinson

(Concluded from page 717 December issue)

THE next item required is:—

2. Mains Transformer. A discarded standard type mains transformer should be obtained with a sound primary winding. All secondary windings are removed, noting the turns/volt ratio for the L.T. windings removed. Secondary windings required are then wound over the old primary, using the turns/volt ratio obtained. Anode/screen winding should be wound first, followed by the grid winding and then the filament. Use waxed paper taken from a Mansbridge type condenser for insulation between layers. In choosing the gauge of wire the space available should be considered, attempting to fill the space if possible with active windings and necessary insulation. 34 s.w.g. enamel wire should suffice for anode/screen windings and the grid 15 volt supply. The L.T. windings should be 20 s.w.g. for 6.3 volt and below, 28 s.w.g. for 16 down to 6.3 volt, and 32 s.w.g. for 50 down to 16 volt winding.

3. Pin-connecting Panel. This consists of six horizontal brass strips, representing anode, screen, grid, cathode and two filament circuits connected to the tester. Mounted over these strips and insulated from them are nine vertical strips, representing pins 1 to 9, wired to the valve bases, and a tenth connected to the top cap socket. At each point where a horizontal and a vertical strip cross holes are drilled through, the bottom holes being tapped 6 B.A. and holes in the vertical strips and insulation drilled 6 B.A. clear. Suitable connections can thus be made to the valve to be tested by inserting shorting terminals into the panel, making the required circuit connections. The diagrams give the principal dimensions of a suitable panel. The six horizontal strips should be $\frac{1}{16}$ in. thick, to allow about six threads for good connection. The vertical strips are brass and are shaped and slotted into the middle paxolin panel to prevent sideways movement and resultant shorts between adjacent strips. All paxolin panels should be $\frac{3}{32}$ in. thick. Shorting terminals are made from a short length of 6 B.A. threaded rod, using top terminals from old type valves, and 6 B.A. nut or collar to complete.

4. Rectifier. Any half-wave selenium rectifier rated at about 50 mA can be dismantled and its elements rearranged to form a bridge. Two rectifier elements are required for each arm, and three extra connection tags are necessary. The tightness of the clamping nuts is not critical.

5. Switches. All switches should be of the


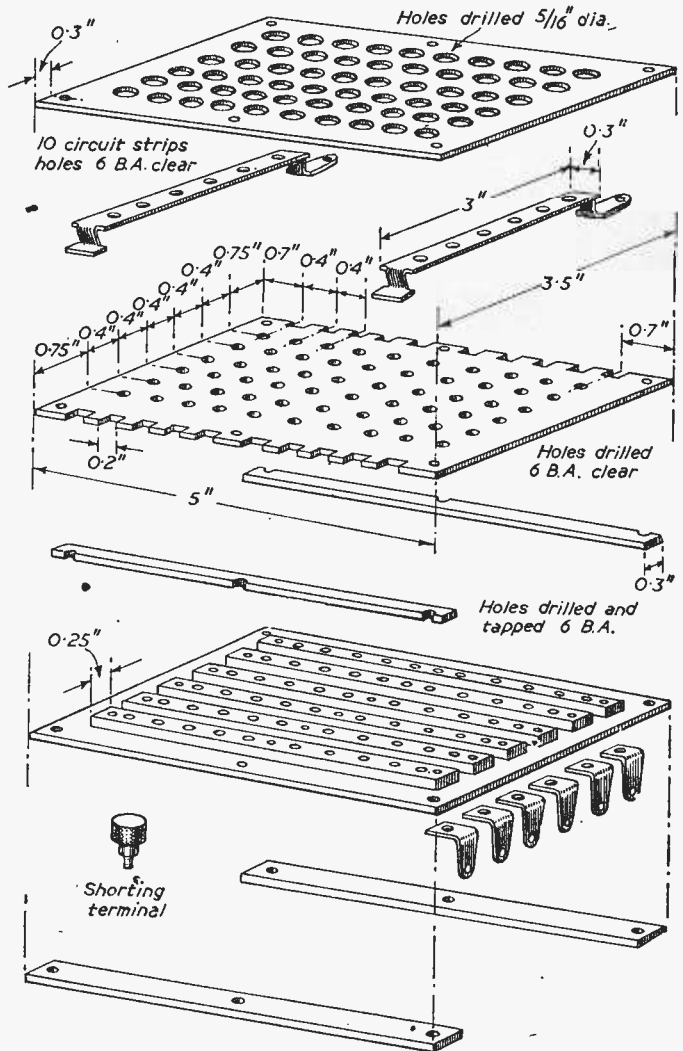


Fig. 7.—Details of the pin-connecting panel.

type which has "break before make" action.

Panel dimensions and layout of components are shown in the diagrams, ample space being provided for the storage of test leads and adapters. Suitable brackets must be made to support the 1.5 battery, rectifier and VRI. Graduated dials for switch positions, etc., are easily made from clear Perspex, cut to shape and painted, black on the back and white on the front. Graduations can then be marked with a scribe, the white paint removed revealing the black backing. The panel should be painted grey on which the white dials and black meter case and knobs contrast. Meter shunts are adjusted to give correct f.s.d. for the appropriate ranges, checking each against an accurate millimeter.

Fig. 8 (right).—Details of the scale.

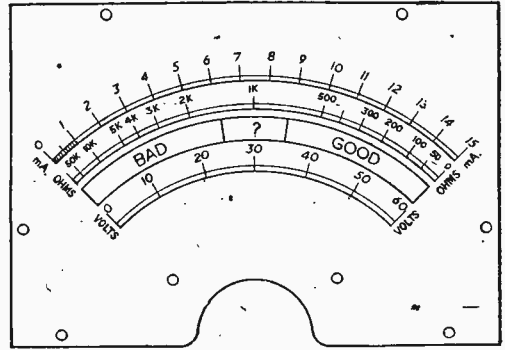

Walkie-talkies for Gasholder Inspections

TESTS have recently been carried out by Mr. L. C. Grant, a leading consulting engineer in Liverpool, to find out how walkie-talkies could be used for the inspection of gasholders. Subsequent to these tests the consulting engineer has ordered equipment, and the following report on its use has been sent by a Pye representative who was present.

"Following a recent request by a leading north western gas consulting engineer, who required communications from inside gasholders for the purpose of maintenance and suchlike, a series of tests was carried out using the standard Pye battery-powered transportable, together with a standard walkie-talkie.

"The transportable 'Reporter' was set up approximately 50ft. away from the gasholder at ground level, working on frequencies of 85.875 Mc/s and 72.375 Mc/s. Tests were then made and two-way communication loud and clear was established to the walkie-talkie, working on similar frequencies to the transportable.

"At this stage one of the Gas Board engineers was fitted up with the walkie-talkie and made his way up the side of the gasholder, maintaining communication at intervals, loud and clear signals being received at all points up the side and on top of the gasholder. The engineer having descended to ground level, a second series of tests was made.

"The engineer entered the gasholder through a steel door into the airtlock, which was then shut and secured, fully readable signals being obtained loud and clear. During the progress of the engineer into the airtlock, a running commentary was given on his actions and every syllable was fully readable.

"The engineer passed through the second door of the airtlock into the gasholder proper, closing this door behind him and again maintaining fully readable signals with those outside. Various instructions were passed to the engineer, who was by this time established on a raft which was floating inside the gasholder, and the engineer was instructed to pole this raft to various positions in and around the interior of the gasholder. At all times fully readable, full strength signals were obtained.

"It should be noted that the gasholder used for these tests was under repair and was filled with compressed air, no breathing apparatus being needed.

Britain's Sapphire Needle Industry

IN the middle of the biggest-ever boom in the gramophone record industry throughout the world, Britain has cornered the market in the now universally used sapphire needles (called "styli" in the trade).

What was formerly a monopoly of the Swiss has been stolen by a London engineering firm, Sapphire Bearings Limited, with a process for the automatic manufacture of these minute styli, which is being hailed as a "miracle of engineering." Britain has switched from being an importer to the world's largest exporter of these styli—and this firm holds export orders calling for deliveries at more than 100,000 styli per week.

The plant is now being doubled in size to cope with increased export demand and by June (1955) output will be at the rate of 20 million a year; worth £750,000. This achievement has been accomplished in a factory not much bigger than a large drawing room. The whole year's output would just fill a pint mug!

Fifty workpeople now work round the clock in this baby factory in London's Bow Road, living in a microscopic world. The finished stylus is less than one-twentieth of an inch long and one fiftieth of an inch in diameter.

It is necessary to polish a cone a mere fifteen-thousandths of an inch long, and then turn the pointed tip into a spherical shape accurate to within one-hundred thousandth of an inch of true sphericity. This has to be done not ONCE—but 40,000 times a day.

With British sales of gramophone records alone reaching an all-record level of 40 million a year, and with British manufacture of record players now well over one million a year, the demand for sapphire styli is rising by leaps and bounds.

With the advent of the long play record—with its tiny grooves measuring 325 to the inch—the old steel needle proved too soft to use. It wore out long before it traversed one tenth of the record.

The search for harder materials finally led to sapphire, the second hardest known material (diamond being hardest), because of its durability and high polish. Now sapphire is used universally in commercial gramophone pick-ups, with diamond styli used in only the luxury gramophones.



THE NEW Fury Four

THE LATEST VERSION OF OUR POPULAR TWO-R.F. RECEIVER, WHICH IS FULLY ADAPTABLE FOR MANY PURPOSES

(Continued from page 735 December issue.)

AN ECC83 should not be used for V.3 in view of the distortion which may result from the very much increased gain of this particular type of valve. Normal R.C. coupling is used between the A.F. stage and the output pentode, and all the preceding anode circuits are adequately decoupled. The output from the pentode is taken to a loud-speaker through the usual transformer and it will be noted that this is not included on the chassis. It should be placed at any convenient part of the cabinet which is finally chosen for the receiver, and then, if the special tone-control circuit is used, the leads to the speaker will be included in the final feed-back loop. It will be seen that the tone control forms a more or less normal feed-back circuit, and if included the earth connection should be removed from the junction of the bias resistor and condenser of the first A.F. valve and a 56 ohm resistor connected in place of it.

The other parts. Knobs have been specified for all the controls, but if, for instance, the first R.F. stage is omitted, then the R.F. gain control will not be required, which will be one knob less, and so on. No attempt should be made to use condensers other than those specified for the aerial and earth isolating condensers, and for the .05 across the mains transformer. In the case of all the other parts the physical size plays an important part in the layout, and for this reason any departure may lead to trouble due to modifications in the layout or wiring.

Cabinet Design

As already mentioned, the receiver may be made up in any desired form, and if included in a radiogram cabinet the on/off switch may be included on the side of the cabinet, or may be part of the R.F. or A.F. volume control. It would be in the latter position if the receiver is mounted in a small table-type cabinet, or it may be omitted entirely and the ordinary house switch used at the point into which the receiver is plugged. It will be seen, therefore, that there are a number of points which must first be decided before the components are purchased, and the component list which is included below the circuit on page 734 gives the parts which we used and does not include the on/off switch, but does include all

Construction

Having fully described the circuit and the principles underlying the design, we may now proceed to the actual constructional work. Firstly, the chassis will be standard type, no matter which of the

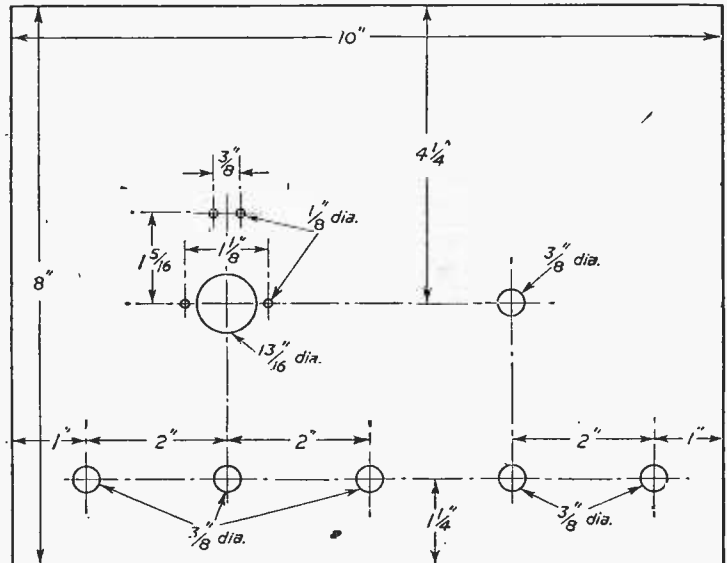


Fig. 2.—Panel drilling details. See special note on p. 32 under 'Warning'

alternatives the constructor decides to build. The original which we used was a standard Denco model, measuring 10in. by 6in. with 2½in. runners. If it is desired to construct this at home a square foot of aluminium of 16 s.w.g. should be used. The full drilling and bending data is given in Fig. 6 on page 34, and it will be noted that the sides are merely ¼in. projections. If a thinner gauge of metal is employed these should be the full 2½in. and should be provided with a turnover which may be bolted to the front and rear runners to provide rigidity. As already mentioned, there are a number of alternatives in the circuit and the final design will govern the panel layout, shown for the full circuit, in Fig. 2 on page 31. This provides for the special slow-motion drive specified and the full range of controls. If any

of these are to be omitted, the appropriate hole will of course, not be drilled. When drilling the holes in the front runner of the chassis, care should be taken to see that they line up with those in the panel, and some constructors may prefer to drill the panel first and place it in position on the front runner of the chassis, using a bolt at each end, and then drill the chassis runner.

Warning

It should be emphasised at this point that the receiver does not utilise an isolating mains transformer, and by reason of this the chassis is "live" to one side of the mains. Consequently, a metal panel must not be employed. All of the specified volume and tone controls are provided with metal cases which

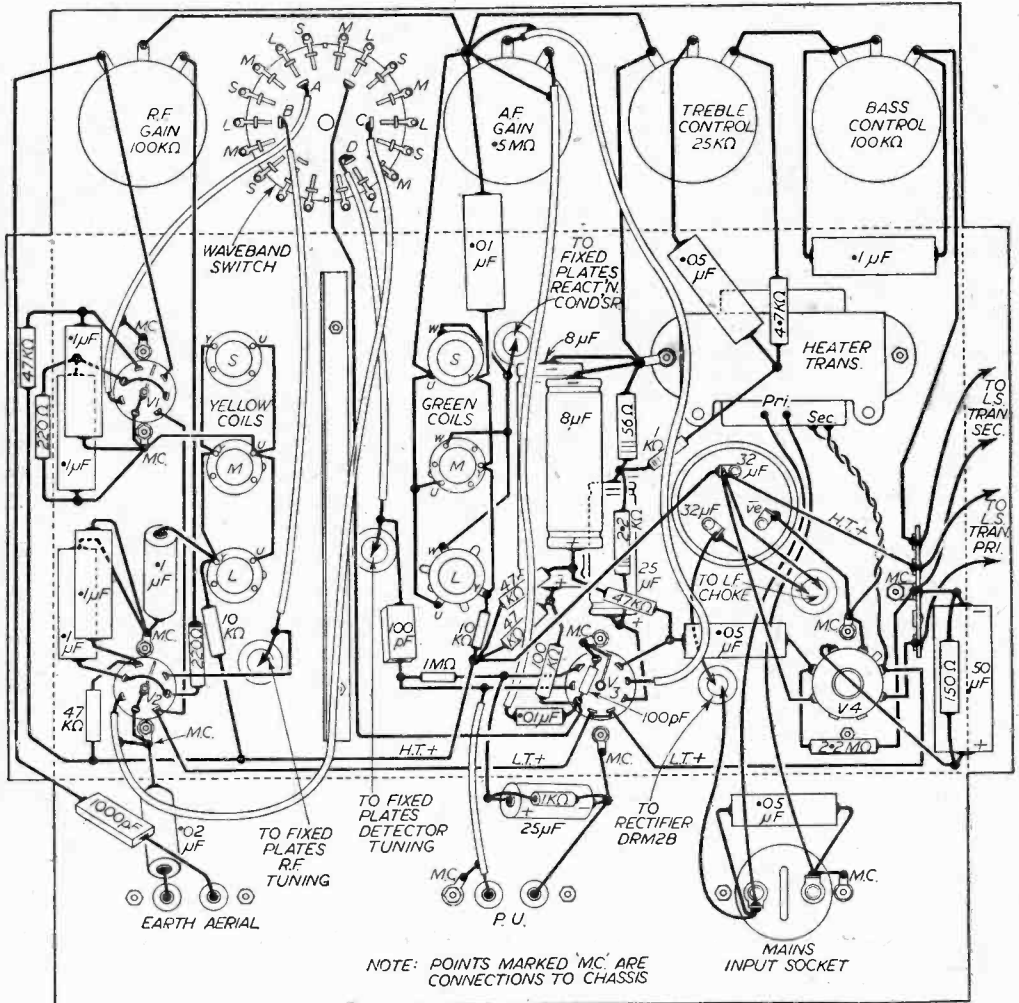


Fig. 3.—Wiring details. Note that for clarity only part of the coil wiring is shown, the remainder being given in Fig. 4.

will automatically be "earthed" when the lock nuts are tightened. This is essential for screening the components. The lock nuts will, therefore, also be "live," and the knobs which have been specified have a centre portion which will effectively cover these, whilst at the same time the grub screws are deeply recessed. The main slow-motion drive is isolated

rear runner and the screen for some of the wiring. Even if only one range is to be employed, this screen will still be necessary in the interests of stability. A special flexible coupler is specified for connecting the slow-motion drive to the variable condenser as it may be found that even with the measurements given the spindles may not be in exact line and the flexible coupler will take care of any discrepancy.

Mount the valveholders and other parts as shown in the wiring diagram (Fig. 3), making certain to get the valveholders round the right way. As a guidance the separating point between pins 1 and 7, 1 and 9 and 1 and 8 for the different valveholders has been shown in the wiring diagram, and in Fig. 5 we give a view of the underside of the valveholders and the various electrodes of the different valves. If the set is not to be used for record reproduction the pick-up socket strip will be omitted.

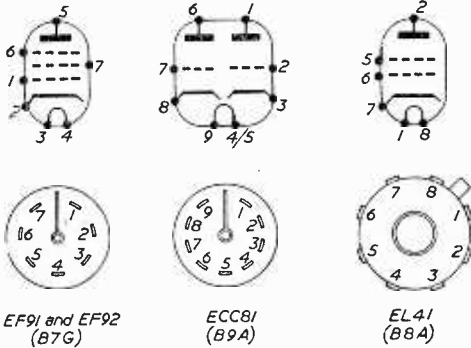


Fig. 5.—Valve base data.

from the tuning condenser by the special coupler, and the reaction condenser also has the dial attached to a "live" lock-nut. In the event of a metal panel being used, therefore, it would be difficult to isolate the lock-nut of this component so that the small dial is not actually in contact with the panel. These precautions will be obvious to those who are familiar with A.C./D.C. types of receivers but are emphasised for those who may not be aware of the risks of this type of equipment. All the precautions are, of course, rendered unnecessary if a paxolin, Perspex or similar material is used for the panel. A thin panel of wood will be adopted by many, stained and polished to match a cabinet, or as an alternative a standard mains transformer with a 250 volt secondary, in addition to the 6.3 volt winding may be employed, and this will effectively isolate the receiver.

All the holes shown in the chassis will be needed for the full circuit, and it would probably be preferable to drill all of these even if only part of the receiver is to be used. For instance, three holes are shown for the two sets of coils, although if only the medium- or long-wave coil is to be used, two of the holes will not be needed. It would be simpler to drill all at the beginning, and then if at a later date it is decided to add a coil or make any other modification the hole will be ready.

Coil Screening

One further piece of aluminium is needed to provide a screen between the two sets of coils. This strip should be as deep as the chassis (2½ in.) and have a ½ in. turnover along one edge. Its length is 5 in. and the bent-over edge should be drilled with two holes, and if it is desired to use the wave-change switch this should be fitted to the front runner and then the screen placed as close to the switch as possible, before the holes are marked through to the chassis. The screen actually screens the projecting lugs of the switch and then leaves sufficient room between the

Wiring

The receiver is now ready for wiring and one can follow either the theoretical circuit given last month or the wiring diagram in Fig. 3. Note the fact that the latter is for the full circuit and, therefore, any omissions decided upon will affect the wiring. In this connection the tone-control network is taken back to the bias resistor for the second half of the double-triode. If the network is omitted a wire must be connected from the nearest earthing tag to the negative end of the 25µF condenser across which is connected the 2.2 KΩ resistor. This is shown as a solid line in the theoretical circuit, but it is, of course,

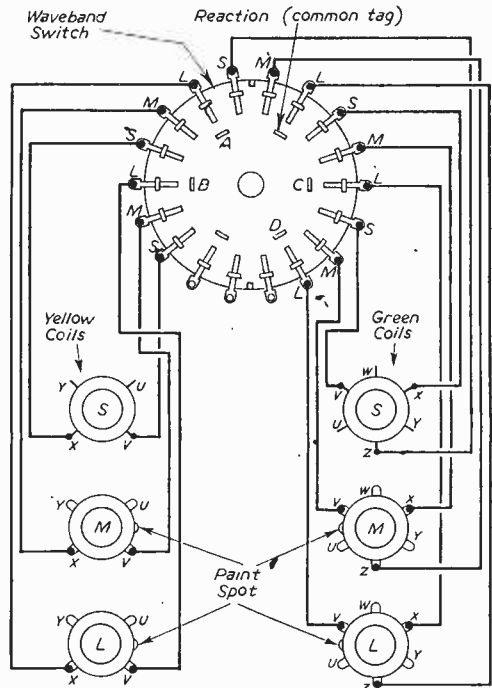


Fig. 4.—Coil and switch wiring—not shown in Fig. 3.

omitted if the tone-control network is fitted, and as the wiring diagram shows the tone controls in circuit this lead is automatically left out. It will also be noted in the wiring that the anode lead is joined to one of the switch arms, and the three reaction windings are taken to three of the contacts on the switch. This was omitted in the theoretical circuit given last month.

It should also be mentioned again that there is no on/off switch in the receiver. If the set is to be built as it stands, then the A.F. gain control should be of the type having a double-pole on/off switch fitted, and then the two leads from the rear of the mains input socket would be taken to one pair of contacts on the switch, and the other pair of contacts would be joined to the primary of the mains transformer. As an alternative, a length of twin flexible mains lead may be attached to the input socket and taken to a double-pole switch conveniently sited on the cabinet or installation and a similar length of twin lead taken from the primary of the mains

transformer to the remaining contacts on the switch. If an isolating mains transformer is fitted, the switch need only be of the single-pole type.

Coil Switching

To facilitate wiring of the coils and switch a separate diagram is given in Fig. 4 on page 33, and this indicates a fixed layout of the connecting points on the coils. In actual fact, some short-wave coils are provided with wire ends to the coils only and in this connection the maker's leaflet which is supplied with each coil should be carefully studied. As already mentioned, coils may be selected for any desired waveband and although the connecting points are standardised the actual layout may be slightly different. The leads shown on the wiring diagram in hollow form (as distinct from the solid leads generally employed) are to represent standard 80 ohm coaxial cable as used for television aerial lead-in. This should be bared and cut with the minimum of

(Continued on page 42)

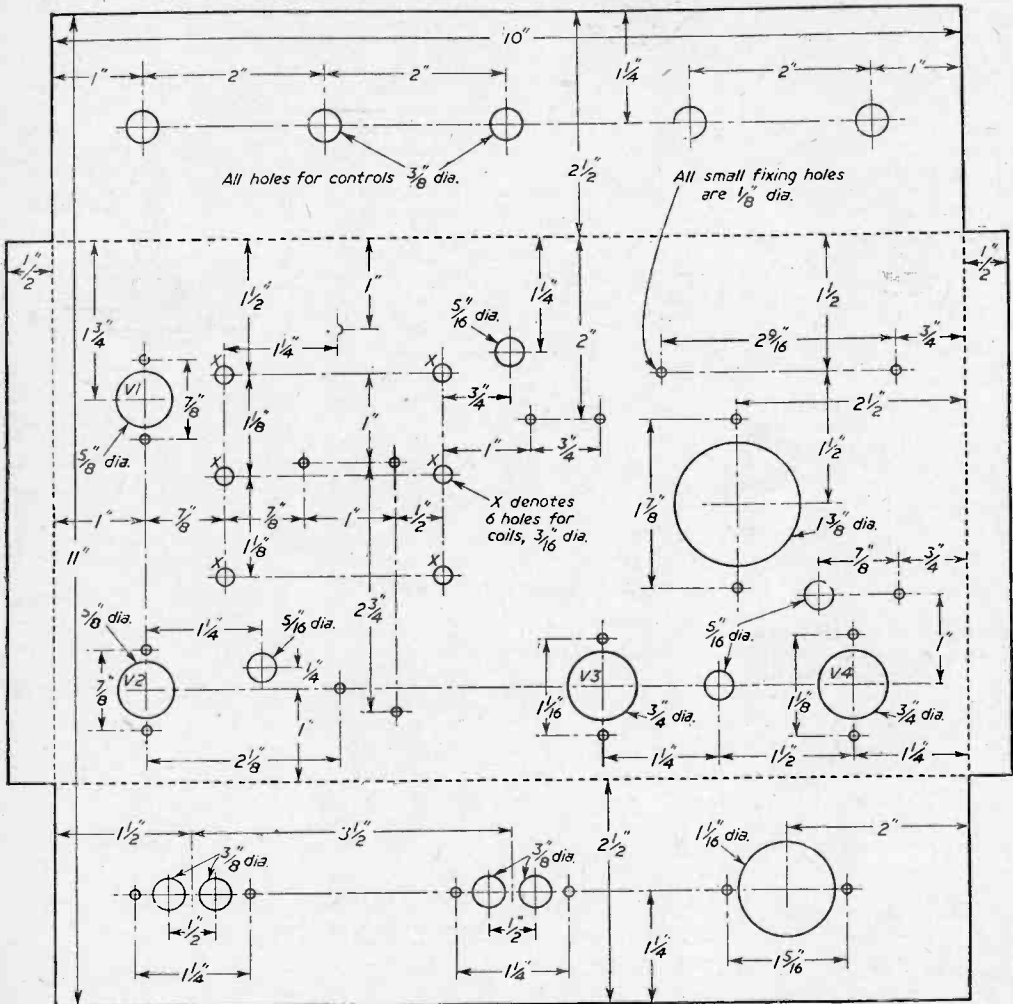


Fig. 6.—Chassis drilling and bending details.

'CHIMELITE'



CHIMELITE

It is a hall light as well as a double chime and you can make it in a couple of evenings for the total cost of only 19/6, including instructions. Post, etc., 2/-. Data available separately, price 2/-.



CHASSIS ASSEMBLY

3 colour, 2 waveband scale covering standard Long, Medium and Short wavebands, scale pan, chassis punched for standard 5 valve superhet, pulley driving head, springs, etc., to suit. Scale size 14in. x 3 1/2in. Chassis size, 15in. x 5in. x 2in. deep. Price 15/-, plus 1/6 post.

TABLE RADIO CABINET

Very fine cabinet, size approx. 16 x 16 x 7—walnut veneered and satin finished, 39/6, carriage and packing 3/6. This cabinet is the correct one for the chassis above.



226 FLUORESCENT LIGHTING
40 WATT
Kit control unit, starter lamp holders, clips and wiring diagram. Price, less tube, 22/6, plus 1/6 post. With tube, 30/-, plus 3/6 carriage and insurance.

1 inch MICROMETER

Exceptional purchase enables us to offer a 1in. precision micrometer at the very low price of 10/-. A micrometer is an essential part of an engineer's equipment. You, no doubt, will have found the need for one on many occasions in the past for measuring wire gauge, etc. If you act quickly you can acquire one now at the remarkably low price of 10/-, post free.



CABINET 19/6

You can make an excellent bass reflex cabinet with this well-veneered and polished walnut cabinet. Limited quantity offered at 19/6. Carriage, etc., 3/6.




A.C./D.C. THREE, 19/6

A remarkable bargain (mainly operated). Totally self-contained powerful receiver for Long and Medium waves. All parts including valves, coils, resistors, etc., but not loudspeaker and cabinet will cost you only 19/6, post, etc., 1/6. Data available separately 2/-, post free.



TWO NEW CABINETS THE BUREAU

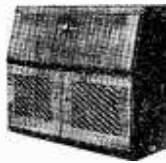This is a really beautiful cabinet elegantly veneered in walnut and finely polished. The control board revealed when the front is dropped down is ample for the larger than average radio chassis or amplifier and alongside there is a space for a tape recorder or auto record changer mechanism. Both the radio board and the control board are left uncut to suit your own equipment.



Size approximately 30in. high, 21in. wide, and 16in. deep. Price £16.16.0. Carriage 12/6.

THE CONTEMPORARY



Also in the modern trend is this very stylish contemporary console. Veneered in oak with contrasting mouldings this has the "G" plan look and is ideal for use with this furniture or with other contemporary fittings or furnishings. The radio and motor board is again uncut and its size 30in. x 15in. provides ample room for all equipment. Price £8.15.0. Carriage, etc., 12/6.

TAPE RECORDINGS ULTRA MODERN TAPE DECK

The latest Truvox incorporates every modern refinement, plays H.M.V. and other pre-recorded tapes. Has azimuth head adjustment 50-10,000 c.p.s. response. Provision for foot control (dictating letters, etc.) is undoubtedly one of the best tape decks available today. Price £23.2.0. Hire purchase terms if required. Send a deposit of 15% or more, balance spread over 12 months. Carriage and insurance 10/-.




CLEVELAND WIDE-BAND TAPE AMPLIFIER

Truvox co-operated in designing this amplifier and fully approve it. Two separate inputs for mixing programmes. Suitable for radio recordings from crystal set or tuner, crystal or magnetic microphones or pickups. Magic eye indicates depth of recording. 4 watt amplifier—uses five midrange powerpack on separate chassis. Price £15. Hire Purchase terms if required, deposit not less than 15%, balance spread over 12 months. Carriage and insurance 7/6.


FINE MODERN RADIO

THE CLEVELAND ORGANTONE

5 valve 3 waveband superhet covering Long, Medium, and Short waves—built to attain highest performance of sensitivity, fidelity and output—Ocran miniature valves—low loss iron coils—permeability tuned I.F.S.—full A.V.C.—variable negative feed-back—gram. position on wave change switch—4 watts output—particularly fine tone especially on gram. Chassis size 7 x 7 approx. scale size 4 x 4 approx. Tested in difficult areas where exceptional results have been obtained. Price £11.10.0, or £3.16.0 deposit. Carriage, etc., 7/6.

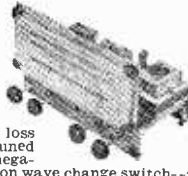

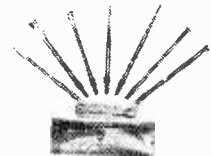THIS MONTH'S SNIP A SILVER STEEL TOOL ROLL



This most useful kit contains three sizes of standard screwdrivers, two sizes of Phillips screwdrivers, a taper reamer and a taper spike. All designed to slip into a 10,000-volt-tested handle, and all made from specially hardened tool steel, complete in wallet tool roll. Price 12/6, post free. This is an invaluable set of tools for everyone who uses tools.

INFRAY LAMP

Means real comfort in bed as it emits infra Red Rays which warm and keep you healthy.
● Economical.
● Costs only 1d. per hour (elec. at 1d. per unit).
● Absolutely safe, no health or fire risk.
● Ideal for many other uses—over pet's basket, rearing pup, chicks, over desk, work bench, etc.
● All complete and ready to work. Price 36/- plus 2/- post & packing.



THE F.M. FEEDER UNIT



All the parts necessary to make the Denco F.M. Unit are now available. The unit gives an A.F. output suitable for feeding in at the pickup sockets of any standard broadcasting receiver and superior results can be expected. The full constructional details as prepared by the Denco technicians are available—price 1/6, post free. Alternatively they will be given free to those ordering all the parts which come to £37.6, plus 2/6 post and packing. Note: four valves and everything, including a prepared metal chassis is supplied. Approximate chassis measurements are 6 x 6 x 1 1/2.

MULLARD AMPLIFIER

A high Quality Amplifier designed by Mullard engineers. Robust, high fidelity, with a power output exceeding 10 watts and a harmonic distortion less than .4% at 10 watts. Its frequency response is extremely wide and level being almost flat from 10 to 20,000 C.P.S.—three controls are provided and the whole unit is very suitable for use with the Collaro Studio and most other good pickups. The total cost of the amplifier is around £11. For 30/- extra a unit completely made up and tested can be supplied. Carriage in either case is 10/- extra. Data will be provided with all orders for components. Send for the "Mullard Amplifier Shopping List."

ELECTRONIC PRECISION EQUIPMENT, LTD.

Post orders should be addressed to Dept. 7, RUISLIP.

Personal shoppers, however, can call at:


42-46, Windmill Hill, Ruislip, Middx.
Phone: RUISLIP 5783
Half day, Wednesday.

152-3, Fleet Street, E.C.4.
Phone: CENTRAL 2633
Half day, Saturday.

29, Stroud Green Road, Finsbury Park, N.4.
Phone: ARCHWAY 1049
Half day, Thursday.

and at 243, KILBURN HIGH ROAD, KILBURN. (Now Open)

GET ON THE BEAM! 2 YEARS' GUARANTEE

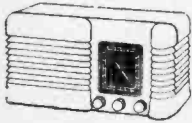

... with the
METEOR III
GUARANTEED
A.C. Mains Set.

SIMPLICITY ITSELF!

Complete KIT only

95/-

plus 2/6 for
postage & packing.

Instructions, Point to
point Diagrams and
Parts List sent for 1/-,
Post FREE.


You could almost do this job with a knife and fork—it's so simple! Screwdriver, pliers and soldering iron will make this spot-on 3 valve, 2 wave band set. Complete Kit includes valves. Ready-to-use Chassis Brown or Ivory Moulded Cabinet. A.C./D.C. Universal Model available at 97/6, plus p. & pkg., at 2/6. Visit our new branch at 97, Stratford Rd., Sparkbrook, to inspect our range of T.V.s, Radios, Cabinets and Components for Home Instructors.

NORMAN H. FIELD
68, Hurst St., Birmingham 5.

SATISFACTION—or we REFUND your CASH!

with the
BURGOYNE
8 VALVE Radiogram Chassis

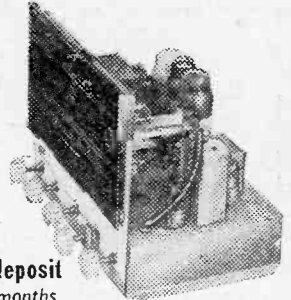With a push-pull output giving 8 watts of undistorted quality reproduction and using negative feedback, this fine chassis is supplied for those connoisseurs wanting only the best, at a price within their means!



20C-250 v. A.C. **22 GNS.**

Carriage and packing 7/6.

YOURS for ONLY 46/3 deposit
balance over 12 or 18 months.

SPECIFICATION ★ Illuminated full vision coloured tuning scale 1½ in. x 6½ in. ★ Separate bass and treble controls for cut and lift. ★ Wavebands 16-50; 190-550; 1000-2000 metres. ★ Magic eye tuning indicator and precision: flywheel tuning. ★ Speech coil impedance 3 or 15 ohms. ★ Extension speaker sockets. ★ Size 9½ in. high x 13 in. wide, 8 in. deep—chassis height 2½ in.

E. & G. MAIL ORDER SUPPLY CO. The Radio Centre
33, Tottenham Court Road, London, W.1. MUSEum 6667

FREE! to YOU! -if you seek SUCCESS!

Can you find your mind the way to SUCCESS?

WHAT'S YOUR LINE?

Building	Accountancy Exams.
Carpentry	Auctioneer's Exams.
Commercial Art	Book-keeping
Diesel Engines	Civil Service
Draughtsmanship	Costing
Electrical Eng.	English
Fire Engineering	General Education
Mechanical Eng.	Journalism
Motor Engineering	Languages
Quantity Surveying	Mathematics
Radio Eng.	Police Subjects
Surveying	Salesmanship
Surveyor's Exams.	Secretarial Exams.
Telecommunications	Shorthand
Textiles	Short Story Writing
Wireless Telegraphy	and many others

GENERAL CERT. OF EDUCATION

If you lack the qualifications which would get you a better job; more pay and quicker progress; if you wish to know how The Bennett College can guarantee to teach you up to qualification stage by one of the easiest, quickest and soundest methods of mind training; if you wish to learn how Personal Postal Tuition can prove that you are cleverer than perhaps you think you are — if you like the idea of studying in your own time, at your own pace, with your own tutor guiding you, helping you, teaching you by post — send at once for this recently published important book—'Train your mind to SUCCESS'. It is quite free. Just fill in the coupon below and name the subject you are interested in (some of the many Courses available are listed here). Then send in the coupon to us TODAY. You will never, never forget it. But do it today. Act NOW!

BENNETT COLLEGE
(DEPT. A 104F), SHEFFIELD

Please send me, without obligation, a free copy of "Train your mind to SUCCESS" and the College Prospectus on:

SUBJECT _____

NAME _____

ADDRESS _____

AGE (if under 21) _____

Please write in Block Letters

THIS DAY
COULD BE THE TURNING-POINT IN YOUR LIFE.

THIS COUPON
COULD BE YOUR PERSONAL PASSPORT TO SUCCESS.

Send it NOW!

REP HIGH GAIN COILS

Dual Range Miniature Crystal Set Coil with Circuit. Type DRX1 ... 2/6
Dual Range Coil with Reaction with 2 mains and 2 battery Circuits. Type DRR2 4/- Matched Pair Dual Range T.R.F. Coils with Reaction; with battery and mains circuits. Type DRM3 Pair 8/- (Regd. Design)

- ★ All Coils wound on Low-loss Formers
- ★ Individually Tested and Guaranteed
- ★ Post 3d. on all Orders
- ★ Trade Supplied

RADIO EXPERIMENTAL PRODUCTS LTD
33 MUCH PARK STREET COVENTRY

SPECIAL OFFER

G.E.C. & B.T.H.
GERMANIUM CRYSTAL DIODES
1/- each. Postage 2½d.

Diagrams and three Crystal Set Circuits Free. A large purchase of these fully GUARANTEED diodes from the manufacturers enables us to make this attractive offer.

POST RADIO SUPPLIES,
33, BOURNE GARDENS, LONDON, E.4.

The Beginner's Guide to Radio



The Twenty-first Article of a Series Explaining the Fundamentals of Radio Transmission and Reception. This Month Mains Valves and Practice are Dealt With.

By F. J. CAMM

THE resistance should be screwed down on to a flat piece of wood covered with white paper. Mark out a scale on the paper, dividing up the length of the resistance into 10 equal parts, so that each division represents a resistance of 1,000 Ω. This provides a temporary and inexpensive variable resistance. Now take the bared end of a lead as shown in Fig. 91 and press it on to the resistance at the first mark nearest the meter terminal, representing a resistance of 1,000 Ω. Take a note of the meter reading, and take similar readings of all the other markings on the resistance scale, and make a small table of them as below :

Anode volts = 100		Grid bias = 1.6
Resistance (ohms)	Current (milliamp)	Valve output (milliwatts)
1,000	8.0	64
2,000	7.0	98
3,000	6.2	115
4,000	5.8	134
5,000	5.2	136
6,000	4.8	138
7,000	4.5	141
8,000	4.2	140
9,000	3.8	130
10,000	3.5	123

These figures will, of course, only provide data for the first two columns, and we must calculate from these two columns the figures for the third column. The watts absorbed by the resistance equals resistance multiplied by the square of the current. For example, the first reading is 8, the square is 8 × 8, which equals 64; multiplying this by 1,000 = 64,000 Ω; but this must be divided again by 1,000 to bring it to milliwatts (1,000 milliwatts equals 1

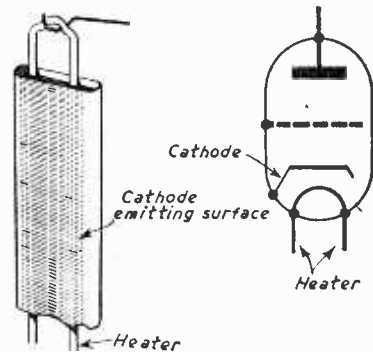


Fig. 94.—An indirectly-heated cathode and the elements of an indirectly-heated valve.

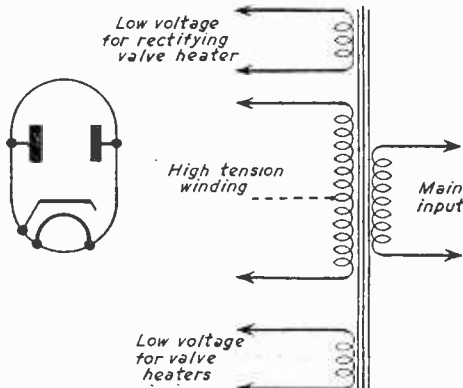


Fig. 93.—Theoretical circuit of a mains transformer and a full-wave rectifier.

watt), so the answer is 64 milliwatts, which is put down in the third column. The second line will be : $\frac{7^2 \times 2000}{1000} = \frac{49 \times 2000}{1000} = 98$ milliwatts.

and so on for all the other readings. If you can use a slide rule you can read off all the answers direct; otherwise you must calculate them.

The next step is to plot a graph representative of milliwatts for any value of resistance. Mark the milliwatts scale on the left of the squared paper and the resistance scale at the foot (Fig. 92); using the figures of the table (yours will, of course, be a different set of figures), trace the pencil up the vertical line representing a resistance of 1,000 Ω and make a dot where it intersects the 64 milliamp line. Repeat this for all the other values and then connect the points with a free-hand curve. Almost certainly you will not be able to draw a smooth curve touching all the dots. This is probably due to inaccuracy in your

reading, but a curve which "averages" the dots will give the approximate mean of all the results. The highest point on this curve represents the highest or optimum of the valve under the conditions of this test. In the graph it is shown that the optimum is at about 7,000 Ω , and this should be the impedance (impedance is the resistance plus the inductance) of the speaker.

Knowing the optimum load for the valve, on referring to your table you will find that at this load the current is, say, 4.5 milliamps. By connecting up the milliammeter in series with the speaker while it is working, if the meter reads 4.5 milliamps, the speaker is right. The figure 4.5 will probably be different in your case and is only given here as an example.

When two or more speakers of the moving-coil type are to be operated from one receiver it is often found most satisfactory to use a single output transformer to feed them all. In that case the speaker speech coils should be of similar impedance, when they may be connected in parallel. The transformer ratio should naturally be selected to match the combined impedance of all the speakers added together.

Mains Valves

Hitherto, I have chiefly dealt with battery sets and battery valves. When a set, however, is intended for operation on the mains, different types of valve are needed, and although the fundamental principle is the same, the methods of heating the filament vary. In a battery the filament or cathode is connected directly to the low-tension source of supply—the accumulator. Most mains valves to-day, however, have *indirectly-heated* cathodes, which means that the emitting surface is not directly connected to the supply. There are of course valves with directly heated filaments, and in this respect they are similar to ordinary battery-operated valves. The emitting surface in the latter case is a wire coated as already described, and it may be heated by a raw alternating current supply. An indirectly-heated valve is indicated in Fig. 94.

In a mains receiver, the alternating current from the mains is connected to the heater, and surrounding this is the cathode.

Consequently, a mains power section must be included, and this is the main difference between a battery receiver and mains receiver. The power pack for an alternating current receiver consists of a mains transformer to convert the voltage of the mains supply to a desired value, which may be 250, 350, 500 volts or even higher, and a low-tension supply—usually of 6.3 volts, to heat the cathodes.

Most mains valves to-day are designed for 6.3 volt working, and it is necessary therefore to recapitulate to some extent the principle of the transformer. It is an instrument for stepping up or stepping down an A.C. voltage, in this case for the purpose of feeding the heaters and anodes of the valves. Alternating current is extremely valuable as a basis of design of mains receivers, because the voltage can be changed to any required figure with the greatest ease, whilst it is, of course, impossible to step up D.C. All that is needed in the case of A.C. is a step-up or a step-down transformer. As we have seen earlier a transformer consists essentially of an iron core on which are placed the primary and secondary windings. The type of core most frequently used for small transformers is that consisting of U and T shaped alloy stampings. The T fits inside the U, forming a semi-solid core with two "windows" and a central limb upon which the windings are placed.

The number of turns per volt for both primary and secondary windings depends upon the cross-sectional area of the winding limb and the frequency of the mains supply. For example, if the area is 1 sq. in., and the frequency 50 cycles, 8 turns should be allowed for every volt. If the area is half this, the number of turns must be doubled and vice versa. On the other hand, if the frequency is doubled, the turns should be halved and vice versa.

This rule is invariable, and is the basis of all mains transformer design.

In order to ascertain the most suitable size of stamping, it is necessary to know the power, in watts, which the transformer has to handle. For example, assume that the transformer has to supply 20 volts at 2 amperes; the wattage would be 20 multiplied by 2, or 40 watts, assuming an efficiency of 100 per cent. But as the actual efficiency is only about 80 per cent., it is necessary to increase the valve by about 25 per cent., which gives the power to be handled as 50 watts.


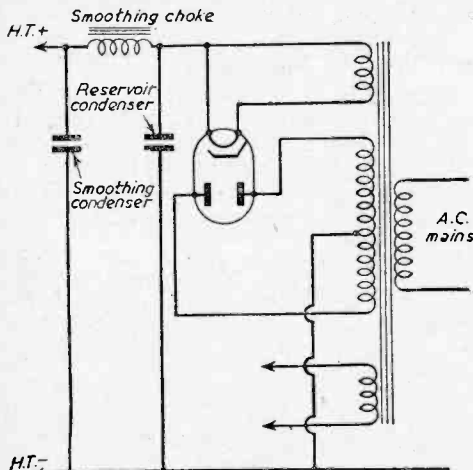


Fig. 95.—Practical and theoretical diagrams of a standard A.C. power pack.

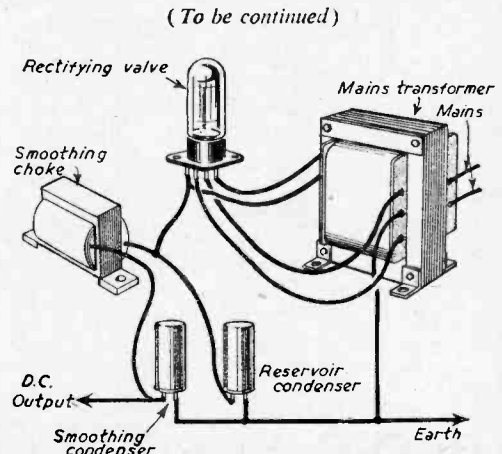

R.S.C. A4 HI-FIDELITY 25 WATT AMPLIFIER

A new design for 1955. "Push-Pull" output. "Built-in" Tone Control Pre-amp. stages. Increased sensitivity. Even further improved performance figures. Includes 7 valves specially designed sectionally wound output transformer, block paper reservoir condenser and reliable small condensers of current manufacture. TWO SEPARATE INPUTS CONTROLLED BY SEPARATE VOLUME CONTROLS allow simultaneous use of "Mike" and Gram. or Tape and Radio, etc. etc. INDIVIDUAL CONTROLS FOR BASS AND TREBLE "Lift" and "Cut." Frequency response ± 3 db. 30-30,000 c/s. Six negative feedback loops. Hum level 66 db. down. ONLY 20 millivolts INPUT required for FULL OUTPUT. Certified harmonic distortion only 0.35% measured at 10 watts. Comparable with the very best designs.

ENTIRELY SUITABLE FOR SMALL HOMES OR LARGE HALLS, CLUBS, GARDEN PARTIES, DANCE HALLS, etc.

H.N.V. LONG PLAYING RECORD TUNABLE WITH CRYSTAL PICK-UP (Sapphire Stylus). Speed 33 $\frac{1}{3}$ r.p.m. For A.C. mains 200-250 v. Limited supply. Brand New Cartoned. Perfect. Only £3/19/6. Plus carr. 5-. (Normal price £8 approx.)

BATTERY SET CONVERTER KIT. All parts for converting any type of Battery receiver to All Mains. A.C. 200-250 v. 50 c/s. Kit will supply fully smoothed H.V. of 120 v. or 90 v. at up to 40 mA, and fully smoothed L.T. of 2 v. at 0.4 to 1 a. Price complete with circuit, wiring diagrams and instructions, only 48/9. Or ready to use, 8/8 extra.

PERSONAL SET BATTERY SUPER-FEEDER KIT. A complete set of parts for construction of a Unit (housed in metal case) to replace Batteries where A.C. Mains supply is available. Input 200-250 v. 50 c/s. Outputs 90 v. 10 mA and 1.4 v. 250 mA, fully smoothed. For 4-valve receivers. Price complete with circuit. Only 35/9. Or ready for use, 42/6. Size of unit, 5 $\frac{1}{2}$ x 4 x 1 $\frac{1}{2}$ in.

BATTERY CHARGER KITS For mains 200-250 v. 50 c/s. To charge 6 v. acc. at 2 a., 25/6. To charge 6 or 12 v. acc. at 2 a., 31/6. To charge 6 or 12 v. acc. at 4 a., 49/9.

Above consist of transformer, full wave rectifier, fuses, fuseholders and steel case. Any type assembled and tested, 6/9 extra.


THE SKY CHIEF T.R.F. RECEIVER. A design of a 4-stage, 3-valve 200-250 v. A.C. Mains receiver with selenium rectifier. It consists of a variable Mu high gain H.F. stage followed by a low distortion grid detector triode. The next stage is a further triode amplifier with tone correction by negative feedback. Finally comes the output stage consisting of a parallel connected double triode giving ample output at an extraordinarily low level of distortion. Point to point wiring diagrams, instructions, and parts list, 2/6. This receiver can be built for a maximum of £4/15/- including attractive Brown or Cream Bakelite or Walnut veneered wood cabinet 12 x 6 $\frac{1}{2}$ x 5 $\frac{1}{2}$ in.

ELECTROLYTICS (Current producer. Not ex-Govt.).

Tubular Types		
8 μ F 350 v.	1/9	16 μ F 450 v.
8 μ F 450 v.	1/11	24 μ F 350 v.
8 μ F 500 v.	2/11	32 μ F 350 v.
16 μ F 350 v.	2/3	32mf. 450 v.
16 μ F 450 v.	2/9	40 μ F 450 v.
24 μ F 350 v.	3/6	64 μ F 450 v.
32 μ F 350 v.	3/6	8 μ F 450 v.
25 μ F 5 v.	1/3	8-16mf. 450 v.
50 μ F 12 v.	1/3	8-16 μ F 450 v.
50 μ F 50 v.	2/3	16-32 μ F 350 v.
8mf. 350 v.	1/3	32-32 μ F 450 v.
8 μ F 450 v.	2/3	

RECORDING TAPE. Best Quality. Plastic, 1,200 ft. Reels only 18/9.

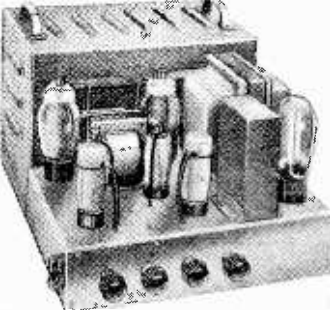Terms: C.W.O. or C.O.D. NO C.O.D. under £1. Post 1/- extra under 10/- 1/6 Open 9 to 5.30; Sats. until 1 p.m. List 6d. Trade List 5d.



etc. For ELECTRONIC ORGAN or GUITAR. For STANDARD or LONG-PLAYING RECORDS. FOR ANY TYPE OF "MIKE" or PICK-UP.

A PUSH-PULL 3-4 watt HIGH-GAIN AMPLIFIER For £2/19/6. For mains input 200-250 v. 50 c/s. Complete kit of parts including circuit, point to point wiring diagram, and instructions. Amplifier can be used with any type of Feeder Unit or Pick-up. This is not A.C./D.C. with "five" chassis, but A.C. only with 400-400 v. trans. (Output is for 2-3 ohm speaker.) Supplied ready for use for 21/- extra. Carr. 2/6. Descriptive leaflet, 7d.

P.M. SPEAKERS. All 2-3 ohms, 6 in. Goodmans, 16/9. 8 in. Plessey, 15/9. 10 in. Plessey, 18/6. 10 in. R.A., 26/9. 10 in. Rola with trans., 29/6. 10 in. W.B. "Stentorian" 3 or 15 ohm type HF1012 10 watts. Highly recommended for use with any of our amplifiers, £3/13/6.

PLESSEY 3-SPEED MIXER AUTO-CHANGERS. With crystal pick-up. Duo point alloy stylus (switched) for standard or long playing records for Mains 200-250 v. 50 c/s. Brand New £10/10/-, Carr. 5/-.

MICROPHONES. Crystal type, good quality. Recommended for use with our amplifiers. Hand type, 50/-; Stand type, with adjustable stand, £6/19/6.

R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Interleaved and Impregnated. Primaries 200-230-250 v. 50 c/s Screened

TOP SHROUDED, DROP THROUGH

250-250 v. 70 mA, 6.3 v. 2.5 a	12/11
250-250 v. 70 mA, 6.3 v. 2 a, 5 v. 2 a	14/11
350-350 v. 80 mA, 6.3 v. 2 a, 5 v. 2 a	17/9
275-275 v. 80 mA, 6.3 v. 2 a, 4 v. 2.5 a	14/11
250-250 v. 100 mA, 6.3 v. 4 a, 5 v. 3 a	21/9
300-300 v. 100 mA, 6.3 v. 4 a, 5 v. 3 a	21/9
350-350 v. 100 mA, 6.3 v. 4 a, 5 v. 3 a	21/9
350-350 v. 100 mA, 6.3 v. 4 a C.T.	
0-4-5 v. 3 a	22/9
350-350 v. 150 mA, 6.3 v. 4 a, 5 v. 3 a	27/9
350-350 v. 150 mA, 6.3 v. 2 a, 6.2 v. 2 a	
5 v. 3 a	29/11

FULLY SHROUDED UPRIGHT

250-250 v. 60 mA, 6.3 v. 2 a, 5 v. 2 a	
Midjet type 21-3-3in.	16/9
350-350 v. 70 mA, 6.3 v. 2 a, 5 v. 2 a	18/9
250-250 v. 100 mA, 6.3 v. 4 v. 4 a	22/9
250-250 v. 100 mA, 6.3 v. 6 v. 3 a	22/9
For R1350 conversion	29/9
300-300 v. 100 mA, 6.3 v. 4 v. 4 a	
C.T. 0-4-5 v. 3 a	22/9
350-350 v. 100 mA, 6.3 v. 4 a, 5 v. 3 a	22/9
350-350 v. 100 mA, 6.3 v. 4 v. 4 a	
C.T. 0-4-5 v. 3 a	23/9
350-350 v. 150 mA, 6.3 v. 4 a	
0-5 v. 3 a	31/6
425-425 v. 200 mA, 6.3 v. 4 a C.T.	
6.3 v. 4 a C.T., 5 v. 3 a, Suitable	
Williamson Amplifier, etc.	47/9
450-450 v. 250 mA, 6.3 v. 6 a, 6.3 v. 6 a	
5 v. 2 a	69/9

ELIMINATOR TRANSFORMERS Primaries 200-250 v. 50 c/s. 120 v. 40 mA 7/9 130 v. 50 mA, 6 v. 3 a ... 14/9

Size approx. 12-9 $\frac{1}{2}$ in. For A.C. mains 200-230-250 v. 50 c/s. Outputs for 3- and 15-ohm speakers. Kit is complete to last nut. Chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied. Unappreciable value at 9/6, or ready for use, 50/- extra. If required cover as illustrated can be supplied for 17/6.

R.S.C. 10 WATT "PUSH-PULL" HIGH-FIDELITY AMPLIFIER A3

Complete with integral Pre-amp. Tone control stage (as A4 amplifier), using negative feedback, giving humproof individual bass and treble lift and cut tone control. Six Negative Feedback Loops. Completely negligible hum and distortion. Frequency response ± 3 db 30-20,000 c.p.s. Two independently controlled inputs. Six B.V.A. valves, A.C. mains 200-230-250 v. input only. Outputs for 3 or 15 ohm speakers. Kit of parts complete in every detail. £7/19/6, plus 5/- carriage, or ready for use, 45/- extra. Illustrated leaflet, 7d.

FOUR STAGE FEEDER UNIT. Design of a High Fidelity Tuner Unit. L. & M. Wave. Full decoupling. Self contained heater supply. Detailed wiring diagrams, parts list, and illustration, 2/6. Total building cost, £3/15/-.

COAXIAL CABLE. 75 ohms, $\frac{1}{2}$ in. 7d. yard. Twin Screened Feeder, 9d. yard.

M.E. SPEAKERS. All 2-3 ohms. 6 in. Rola. Field 600 ohms. 11/9. 8 in. R.A. Field 600 ohms. 12/9. 10 in. R.A. Field 1,000 or 1,500 ohms. 23/9.

VOLUME CONTROLS with long (1 $\frac{1}{2}$ in.) spindles, all values, less switch, 2/9, with S.P. switch, 3/9. D.P. sw., 4/9.

SELENIUM RECTIFIERS

L.T. Types	6/12 v. 19 a.	£5/-
2/6 v. 1 a. H.W. 1/9	2/4 v. 10 a.	59/6
6/12 v. 1 a. H.W. 2/9	H.T. Types H.W.	
F.W. Bridge Type	150 w. 40 mA	3/9
6/12 v. 1 a.	RM2 125 v. 100 mA	1/9
6/12 v. 1.5 a.	7/8	3/11
6/12 v. 2 a.	8/9	RM3 125 v. 125 mA
6/12 v. 3 a.	12/3	5/9
6/12 v. 4 a.	14/9	250 v. 50 mA
F.W. Bridge Type	250 v. 30 mA	7/9
(contd.)	RM4 250 v. 250 mA	
6/12 v. 6 a.	19/9	11/9

FILAMENT TRANSFORMERS All with 200-250 v. 50 c/s Primaries: 1.5 a, 5/9; 2.5 a, 7/6; 0-4-6-3 v. 2 a, 7/9; 2 v. 1 a, 7/11; 6.3 v. 4 a, 8/11; 6.3 v. 6 a, 17/6; 12 v. 3 a or 2.4 v. 1.5 a, 17/6.

CHARGER TRANSFORMERS All with 200-230-250 v. 50 c/s Primaries: 0-9-15 v. 1 a, 18/9; 0-9-15 v. 3 a, 16/9; 0-9-15 v. 4 a, 18/9; 0-9-15 v. 6 a, 22/9.

SMOOTHING CHOKES
250 mA 3-5 H 50 ohms ... 11/9
150 mA 7-10 H 250 ohms ... 11/9
100 mA 10 H 175 ohms Potted ... 9/9
80 mA 10 H 350 ohms ... 8/9
60 mA 10 H 400 ohms ... 4/11

E.I.T. TRANSFORMERS 2,500 v. 5 mA, 2-0-2 v. 11 a, 2-0-2 v. 1.1 a, tor VCR57, VCR57, etc. ... 26/6

OUTPUT TRANSFORMERS Midjet Battery Pentode 66:1 for 354, etc. ... 3/9
Small Pentode 5,000 Ω to 3 Ω ... 3/9
Standard Pentode, 5,000 Ω to 3 Ω ... 4/9
Standard Pentode, 778,000 Ω to 3 Ω ... 4/9
Standard Pentode, 10,000 Ω to 3 Ω ... 4/9
Multi-ratio 40 mA, 30:1, 45:1, 60:1, 90:1, Class B Push-Pull ... 5/9
Push-Pull 10-12 watts 6V5 to 3 Ω or 15 Ω ... 16/9
Push-Pull 10-12 watts to match 6V6 to 3-5-8 or 15 Ω ... 18/9
Push-Pull 20 watts, sectionally wound, GL6, KT66, etc., to 3 or 15 Ω ... 47/9
Williamson type exact to spec. ... 95/-
extra under £1.2/- extra under £3. S.A.E. with all enquiries.

RADIO SUPPLY CO. 32, THE CALLS, LEEDS, 2

SOLDER THE "PRIMAX" WAY FOR 8/7 DEPOSIT and 8 monthly payments of 8/7. (CASH PRICE 70/-)
 (Instant Heating—ready for use in 8 seconds, and weighs only 23 oz.)
OTHER SOLDERING EQUIPMENT AS FOLLOWS:
HENLEY SOLON TYPE 625, 19/8 CASH OR 2/8 deposit and 8 monthly payments of 2/8. 65 WATT TYPES, OVAL BITS, 23/8 CASH OR 3/11 and 8 x 2/11. 125 WATT TYPES (OVAL BITS) 40/4 or 4/11 and 8 x 4/11. 340 WATT TYPES (OVAL BITS ONLY) 66/- or 8/1 and 8 x 8/1.
SOLO SOLDER TOOL ready to be run off a 6-volt battery (car or motorcycle battery) 37/6 CASH or 4/7 deposit and 8 x 4/7. The transformer is available to enable the tool to be run off 230-230 v. A.C. mains at an additional 28/3 or 3/6 and 8 x 3/8. A combined De Luxe unit consisting of the Tool and Transformer permanently mounted and wired, in handsomely finished cartons, 85/- or 10/5 and 8 x 10/5. (Send stamp for Leaflet.)
ADCOLA, 25/0 or 3/2 deposit and 8 monthly payments of 3/2.
 Also Handyman's tools as follows: B. & D. jin. Electric Drill 13/11 deposit and 8 monthly payments of 13/11 (£5.19.6 CASH). jin. Electric Drill Kit 27/11 and 8 x 27/11 (£11.17.6). Craftsman Lathe, 12/3 and 8 x 12/3 (£5.5.0). jin. Sander Polisher Kit 25/- and 8 x 25/- (£9.17.6). (This list is not complete.)
 We also stock Wolf, Bridges, Burgess products, etc. Send stamp for leaflet. If you have any particular item in mind, please let us know, we can probably obtain for you and quote our terms.
Desk 95, LAPCO COMPOUNDS LTD.,
 3, Corbets Passage, Rotherhithe New Rd. S.E.16. BFR 4341 (Ext. 1)

"ADCOLA" SOLDERING INSTRUMENTS

Regd. Trade Mark



Read Design No. 800302
 (British, U.S. and Foreign Patents)

For Wireless and Television Assembly

The advanced design of the Adcola Instruments meets the modern requirements of Television, Telecommunication and Radar Engineers

SUPPLIED FOR ALL VOLT RANGES FROM 6/7v. to 230/250v.
 3/16in. dia. Bit. Standard Model ... 25/6
 1/4in. dia. Bit. Standard Model ... 28/-
 3/16in. dia. Detachable Bit. Model ... 33/6

Sole Manufacturers:

ADCOLA PRODUCTS LIMITED

GENERAL OFFICES & WORKS : CRANMER COURT, CLAPHAM, HIGH STREET, LONDON, S.W.4. (MACaulay 4272)

Special!

NEW Miniature Electrolytics

cardboard tubular 500 vw
 8 MFD 2/9d. each
 16 MFD 3/9d. each

NEW

In makers' boxes 6K6GT (Beam tetrode slightly less powerful than 6V6) only 6/- each.

Send stamps for lists—

A. McMILLAN,
 5, OAKFIELD RD., BRISTOL 8.

Fidelia

HAND BUILT RADIO UNITS

THE FIDELIA MAJOR 10

Hand built high quality radiogram chassis at economic price, 10 valve, model illustrated, 232-8-4, De-luxe 9 valve model £25-5-0, 7 valve £21-12-0, valve £24-18-4

Technical data sheets free.
 Electro Acoustic Developments, 2, Amburst Road, Telcombe Cliffs, Sussex.

STAN WILLETTS

43, SPON LANE, WEST BROMWICH, STAFFS. TEL: WES 2392

"CONNISSEUR" Pick-up, miniature moving iron, complete with matching trans. Brand New, Boxed, 27/9. P. & P. 1/-

"ACMS" Crystal pick-up (GP10). Brand New, Boxed, 24/6. P. & P. 1/-

"CYLON" 5 channel switched teletuners, complete with valves, EP80, ECC81. Brand New, Boxed, 22/6. P. & P. 1/-

GERMANIUM XTAL DIODES—G.E.C. Brand New 1/- each; 10/9 doz. P. & P. 3d.

VALVES—Brand New, every one guaranteed. 6K7C, VT52 (EL32), CV136 (EL81 N77) 5/-; 6V6GT, 6X5GT, 6/9; 87/- doz. 6SN7, 6SL7, EP39, KT44, 12SL7, 7R7, 7/6, 6KPC, 2/6; 90/- doz. BK34, 2C34, 1/9; 18/- doz. 954, 1/6. ATP4, 2/9. VR65 (SP6), 2/9. E581.

Short Wire Ends, 11.6, EC52, 4/8. EA50, 1/9. 6AT6, DH77, 6/9. 12SL7, 6/9. P. & P. 6d. 1T4, 1S5, 1R5, 354, or 1S4, 4/ for 24/9; 6/9 each. P. & P. 6d.

TRIPLITT 1 m/a meter rectifiers. Brand New, 5/6; 3 for 15/- P. & P. 4d.

THE POCKET LOUDSPEAKER SET

Using our clear drawings and instructions you can build a midset loudspeaker receiver small enough to fit in the jacket pocket. This receiver is fully self-contained—no aerial, earth, or external power supply being required. The midset batteries used are of the new, larger type specially produced by a famous British maker for this class of receiver. Only one single-rang midset variable condenser is used for tuning and the receiver requires no alignment. The midset components chosen are current British production, not surplus or foreign. Instructions and Drawings, including Theoretical Circuit and Point-to-Point Wiring Diagram.

PRICE 3/6 POST FREE

This offer applies only to Gt. Britain, Irish Republic and Northern Ireland.

SWIFT RADIO

102, BATH RD., WILLSBRIDGE, NR. BRISTOL

Orders by post only.

FURY FOUR

We can supply all the items required. Send for list.

OSRAM AND MULLARD AMPLIFIERS

Instruction books. Osram 3/6. Mullard 2/6. Detailed lists available.

FULL HIRE PURCHASE FACILITIES ON ANY OF THE ABOVE KITS.

Only 2/- in the £ deposit.

WATTS RADIO,

8, Apple Market, Kingston-on-Thames, Surrey

1/4" Black & Decker

PORTABLE ELECTRIC DRILL

200W OR 250W AC
 COMPLETELY SUPPRESSED FOR RADIO AND TV INTERFERENCE
 FULLY GUARANTEED

MANY ACCESSORIES ALSO AVAILABLE

SENT POST FREE FOR DEPOSIT AND NINE FURTHER MONTHLY PAYMENTS OF 12/6. CASH PRICE £5.9.6.

Frith Radiocraft Ltd
 PHONE 58927
 69-71 CHURCH GATE LEICESTER

Television, Radio, Record CABINETS MADE TO ORDER

ANY SIZE OR FINISH
 CALL OR SEND DRAWINGS FOR QUOTATION

B. KOSKIE
 (DEPT. C.)

72-76 Leather Lane, Holborn, E.C.1
 Phone: CHAncery 6791/2

TELEKIT SUPPLY

MAIL ORDER DEPT.
 Chantry Lane Works, Chantry Lane, Bromley, Kent. Phone: Rav. 5845.
 Please mention P.W. and enclose 6d. postage

VALVES, NEW & SURPLUS, GUARANTEED.

OZ4	4/-	6BA6	6/6	11D3	6/-
1L4	5/6	6BE6	6/6	12A6 1295	6/-
1LN5 (soiled)	6/6	6BS7	7/-	(soiled) 5/6	
IS5	5/-	6BW6	6/6	12BE6	7/-
IT4	6/6	6CH6	6/6	6SH7 (soiled)	4/-
IL5	6/6	6X4	6/6	15D2	5/-
3V4	6/6	6X5	7/6	19AQ5	10/-
5763	8/-	7D5	6/-	AL69	4/6
6A8	8/-	7D8	6/-	CV181	6/-
6AL5	7/8	7E7	6/-	EF50	5/-
6AM6	6/-	757	6/-	VR21	3/-
6AT8	7/8	91D2	5/-	W77	6/8
6B8	6/-	9D6	6/6	1B24	50/-

BECKENHAM, KENT

THE SHOP FOR THE CONSTRUCTOR NOW OPEN AT 104, HIGH STREET.

Low-Cost HI-FI

MODIFYING EXISTING RECEIVERS AND EQUIPMENT FOR BETTER REPRODUCTION AT MINIMUM COST

By W. J. Delaney

MANY readers are interested in modern hi-fidelity equipment, but on the grounds of expense, or that they already own a receiver, are unable to take advantage of the idea. Dual speakers, cross-over networks, and specially designed cabinets are the main features of modern hi-fi equipment, but when one already has a favourite receiver (in either a table or console cabinet), it is not thought desirable to scrap it and build a completely new outfit. At the same time, the feeling remains that perhaps a modern arrangement might sound so much better that it would be worth while, and the user is left in doubt when receiving a musical programme, as to whether a hi-fidelity installation would sound so much different. Actually the user of an ordinary commercial or home-made installation can often do quite a lot in the way of improving things, without undue expense, and in many cases with the minimum of labour. First, what is actually meant by hi-fi? The term covers quite a wide field, and what to one listener is hi-fidelity might be considered by another as too harsh or too deep. In most cases the term is applied to reproduction of a much wider range of tone than is normal with a standard type of receiver. This means that there is more top and more bass than in the average case and, therefore, any improvement must be in the form of accentuated treble or bass, if the circuitry is not to be modified.

Improved Top

The average receiver utilises a medium or small type of speaker which is very good for the higher frequencies but usually lacking in bass. There should thus be little difficulty so far as concerns the top, but this *appears* to be lacking in most receivers for two or three reasons. First, the position of the loud-speaker is generally too low. If a console type of cabinet is employed, the speaker will be a foot or so from the floor, and one has only to bend down so that the ear is on a level with the speaker to note the improved top-note response. The reason for this is that the higher frequencies are directed more or less in a straight line from the diaphragm, and do not radiate in the same manner as the low frequencies. If, therefore, the speaker can be directed upwards to the level at which the ears normally are found (depending, of course, on the particular chair and listening point), the improvement will be noted immediately. If there is no gramophone turntable in the equipment the front of the cabinet may be raised from the floor, tipping back the cabinet and effecting the desired tilting of the speaker. In the case of a table model, the receiver may be placed on some extra packing to bring it to the desired level, and neither of these modifications calls for any constructional work. Where the equipment is home-made, or access may easily be gained to the interior, the speaker itself may be tilted by placing some packing at the top, after loosening the holding screws (Fig. 2).

Where a receiver gives a boomy effect as a result of undue cabinet resonance, this idea will remove the boom whilst at the same time improving the upper register. Alternatively, the speaker may be removed and placed in quite a small cabinet placed on a special shelf to give the desired height and direction. The effects of modern cabinet design may here be roughly obtained by making the cabinet of fairly stout wood, with a close-fitting back, and packing the cabinet with kapok or similar material to deaden any resonance. An alternative is to mount the speaker on a small triangular board and fit this to the top corner of the room so that it is directed downwards toward the normal listening point. (Fig. 3).

Improved Bass

*All the ideas just mentioned aim at improving the *effect* of top-note response, although they do not actually improve the response. To effect the latter some circuit changes must be made, and in many cases it will be noted that there is a top-note cut fitted to the output circuits, usually a fixed condenser across the speaker or output transformer, and it may be found that this may be removed—generally to be

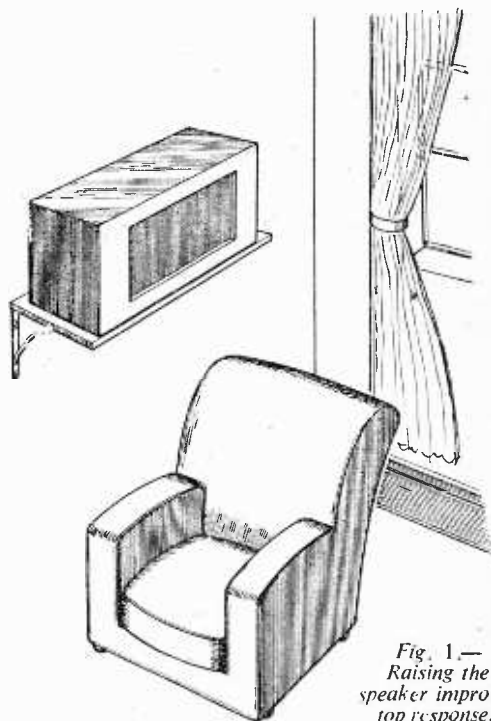


Fig. 1.—
Raising the
speaker improves
top response.

accompanied by some change to strengthen the lower frequencies. Usually, this can only be effected by changes in circuit values or in the actual valves, etc., but the simplest change would be to use larger capacity coupling condenser(s) in the L.F. circuits. Most standard receivers will have condensers of .01 to .05 μ F, and this may in most cases be increased to .1 μ F, any larger capacity, whilst perhaps giving improved bass response, involving the risk of grid choking due to a grid leak of too high a value. Some measure of improvement might also be effected in a simple manner by removing any bias by-pass condensers which may be fitted—again, the change involving the risk of instability in some circuits. No changes should be made which might affect the H.T. current drain as these may result in instability, and this means that anode-load resistors and bias resistors must not be touched. Neither must a valve be changed for one of lower impedance, in an endeavour to obtain improved bass response—unless the extra current can be handled by the power pack which is fitted.

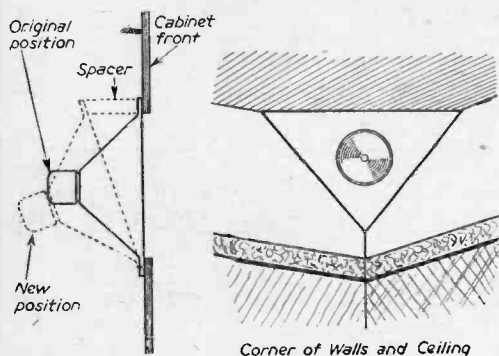


Fig. 2 (left).—Tilting a speaker to improve "top."

Fig. 3 (right).—Mounting the speaker in a corner to provide better baffling.

Tone Controls

Where any or all of the above-mentioned changes are made, and it is felt that the result, whilst it is an improvement on some types of music, is not desirable

THE FURY FOUR

(Continued from page 34)

bare wire at the end for connection and if there is any risk of the braiding not being effectively soldered a short piece of Scotch tape or a Hellenes's rubber sleeve should be put over the end to guard against short-circuits. Earth these leads at one end only. The two leads to the tuning condenser are shown in similar form but not with earth points. In the original model these leads were merely inserted in insulated sleeving, but in some layouts there may be a risk of instability and, therefore, these two leads also may be of coaxial cable. It will be found desirable to attach these leads to the variable condenser before this is mounted and the leads should then be pushed down through the grommets and the other ends finally cut off as required. Note particularly that the two condensers specified for isolating the aerial and earth must be of the voltage rating specified.

Testing

Insert the valves in the sockets making sure that

on others, an adjustable tone control will become necessary. In fact, in many cases the reader may desire to fit such a device to an existing receiver, and the simplest form of this is shown in Fig. 5. It consists merely of a fixed condenser and a variable resistor joined between the anode of the output valve and the chassis line. If there is already a fixed condenser across this point, or across the output transformer primary, it should, of course, be removed. The values will have to be found by experiment to suit the particular tastes of the listener, but condenser C should be between .01 μ F and .1 μ F and the variable a 5,000 or 10,000 ohms component. This only cuts the upper frequencies, but if these have been improved by one of the first methods described this will be found desirable on some items, and if the values chosen result in severe cutting the effect of bass boosting will be obtained by comparison. There is

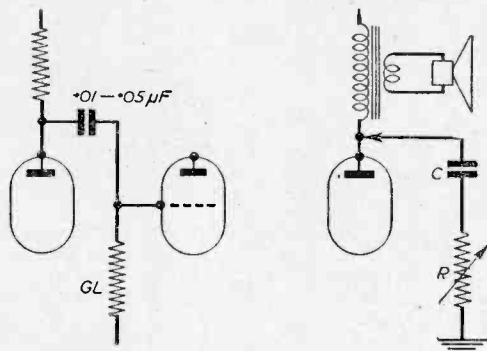


Fig. 4 (left).—Increasing the grid condenser will improve "bass" but the grid leak may restrict the range of adjustment possible.

Fig. 5 (right).—A simple tone control.

no effective way of controlling bass without drastic changes in circuitry, and if such changes are contemplated it would be preferable to build a new amplifier to take advantage of all the resources of modern tone control and improved quality.

the EF91 is nearest the panel, plug into the mains and switch on. All controls should be turned fully anticlockwise which will result in the variable condenser and reaction control being at minimum and all other controls backed right off. Turn the wave-change switch to the medium waves if the three coils are of the long, medium and short type or otherwise set it to the medium-wave band. Turn the R.F. gain about half on, turn up the A.F. gain until a rushing noise can be heard in the loudspeaker, and then rotate the main tuning knob until a signal is heard. Turn this to its loudest point and then adjust R.F. gain to the lowest position consistent with adequate signal strength when the A.F. gain is nearly full on.

These two controls need adjusting together, the R.F. gain to avoid overloading in the case of a powerful local station and also to provide adequate selectivity. The A.F. gain is similarly used to avoid overloading the EL41 on loud signals from either radio or pick-up.

The reaction control should be used when receiving C.W. or for boosting very weak signals. It will, of course, affect tuning slightly.

EX-A.M. RECEIVER TYPE R.1155



5 Frequency ranges : 18.5-7.5 Mc/s ; 7.5-3.0 Mc/s ; 1,500-600 kc/s ; 500-200 kc/s ; 200-75 kc/s. Supplied in maker's original wood transit case.


LASKY'S PRICE
BRAND NEW. £11.19.6.
Secondhand. Grade 1. £9.19.6.
Secondhand. Grade 2. £7.19.6.
Carriage 17/6 extra, including 10/- returnable on packing case.

ASSEMBLED POWER PACK/OUTPUT STAGE FOR R.1155 RECEIVER
For use on 200-250 v. A.C. mains. Complete with 2 valves. In metal case size : 7 1/2 x 5 1/2 ins. **LASKY'S PRICE** 12/6. Carr. 5/- extra.
Power Pack as above. Fitted with 6in. p.m. speaker. **LASKY'S PRICE**, £5.5.0. Carriage 5/- extra.

SPECIAL OFFER TAPE RECORDING HEADS BY "PHIDELTY"
High Impedance single hole fixing. Twin track. Record/Playback ... 22/6
Erase 22/6
Low impedance erase 22/6
Limited quantity only.
Size 1in. diam. 1in. high.
PAR BELOW ACTUAL MANUFACTURING COST.
LESS THAN HALF USUAL PRICE.

TELEVISION SELENIUM RECTIFIERS
The very latest "Sentercel" S.T.C. range.
K3/40, 3.2 kv. 6/-
K3/45, 3.6 kv. 8/2
K3/50, 4.0 kv. 8/8
K3/100, 8.0 kv. 14/-
K3/160, 12.8 kv. 21/6
K3/200, 16 kv. 28/-

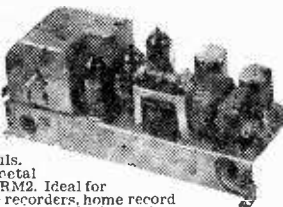3-WATT MIDGET AC/DC AMPLIFIERS PUSH PULL VERY HIGH GAIN



4 valves : 2 U1A1 in push pull, 1 UCH42 and 1 UAF2. Input voltage 100/110 A.C./D.C. Very easily converted to 230 volts. Supplied with circuit diagram and full details. Size : 9 x 4 x 5ins. Uses 2 metal rectifiers, 1 each RMI and RM2. Ideal for ships' record players, tape recorders, home record players, baby alarms, etc. etc. Supplied complete, fully assembled and wired, with 4 valves. 65/- POST FREE.

GANGED TUNING CONDENSERS .0005MFD.
Standard 2-gang. Size : 2 1/2 x 1 1/2 x 2 1/2in. 1in. Spindle 5/-
Standard 3-gang. Size : 2 1/2 x 1 1/2 x 3 1/2in. 1in. Spindle 7/6
Midget 2-gang with trimmers. Size : 1 1/2 x 1 1/2 x 2 1/2in. Spindle 7/6

A COMPLETE 5 VALVE RADIO CHASSIS.
Brand New and Unused. A.C./D.C. Mains. 230/250 volts.
* I.F. 465 kc/s. * A.V.C.
* 4 Watts output.
* 3 Station Pre Set.
* Frame aerial.
* Fully aligned.
* Chassis size only 10ins.x5 1/2ins. Max. height 5 1/2ins.
Completely wired and ready for use, with the addition of a speaker and output transformer
Two controls—Volume and Station switch. Valves used : 10C1, 10F9 or UF41, 10LD11, 10P14, U404 or UY41.

LASKY'S PRICE, 69/6, less Valves. Postage 3/6 extra. **PRICE COMPLETE, £5.19.6.**

METAL RECTIFIERS
6 and 12 volt F.W.
2 a. ... 9/- R.M.2 ... 4/3
4 a. ... 12/- R.M.3 ... 5/-
6 a. ... 19/6 R.M.4 ... 16/-
6 Volt 12 Volt
1 amp. ... 2/6 1 amp. ... 3/11
1 amp. ... 4/8 1 amp. ... 6/6
R.M.1 ... 3/10

RESIN CORED SOLDER.
7/6 per 1-lb. reel.

I.F. TRANSFORMERS
MINIATURE 1 x 1 1/2 x 1 1/2ins. PRICE 10/6 pair.
WEARITE TYPE 550. 445-520 kc/s. 8/6 per pair.
WEARITE TYPE 500. 450-470 kc/s. 8/6 per pair.

LASKY'S RADIO CONSTRUCTOR PARCELS
NO. 1. A.C. SUPERHET.—4 valves plus metal rectifier. Long, medium and short wavebands. In very attractive cabinet, either walnut veneer or ivory or walnut plastic. For 200/250 v. 50 c.p.s. All components, valves, mains transformer, cabinet, dial and metalwork. **LASKY'S PRICE**, £8.5.0.
NO. 2. A.C. T.R.F.—3 valves plus metal rectifier. L. & M. wavebands. For construction in attractive wood or plastic cabinet, walnut or ivory finish. For 200/250 v. 50 c.p.s. All components, mains transformer, cabinet, dial and metalwork. **LASKY'S PRICE**, £5.15.0.
NO. 3. 4-WATT A.C. AMPLIFIER.—Uses 1 each 6SL7, 6V6 and 5Z4. All components, chassis, valves, output trans., mains trans. **LASKY'S PRICE** £4.5.0.

Instruction books for the above Kits, price 1/- each.

LASKY'S RADIO, (New Branch), 42, Tottenham Court Road, London, W.1.

One minute from Tottenham Court Road and Goadge Street Underground Stations.
Telephones : MUSEum 2605 and LANgham 1152.

All our usual lines, plus everything for the serviceman, ham and home constructor. Radio, Television, Hi-Fi, Electronics, P.A. Equipment, Recorders, etc.



NOW OPEN. SAVE MONEY AT LASKY'S

Wharfedale, Stentorian, Goodmans, Baker's, Leak, Cosmo-cord, Vitavox, Hunts, T.C.C., Dubilier, Acos, Garrard, W/B., G.E.C., Grundig, etc. etc.

WE HAVE PLEASURE IN OFFERING YOU HIRE PURCHASE TERMS ON CERTAIN ITEMS. Down payments can be arranged to suit yourself. Send us details of your requirements.

SPECIAL OPENING OFFER FOR PERSONAL CALLERS ONLY :
Moving Coil Microphone. Switch Incorporated. Listed at £5.5.0.
LASKY'S PRICE.....59/6

100K. CARBON POTENTIOMETERS. Less switch. **SPECIAL OFFER.** 1/6 each.

PLASTIC ESCUTCHEON MASKS
With dark screen filter.
12in. 12/6
16in. 25/-

BRIMISTORS
Type CZ.1, 1/6 each. CZ.3, 10/4d. each or 9/- doz.

LASKY'S RADIO,
LASKY'S (HARROW ROAD) LTD.,
370, HARROW ROAD, PADDINGTON, LONDON, W.9.
Telephones : CUNningham 1979-7214.

POST ORDERS TO HARROW ROAD ADDRESS.
Hours : Mon. to Sat. 9.30 a.m. to 6 p.m. ; Thurs. half day, 1 p.m. Postage and packing charges (unless otherwise stated) : on orders value £1—1s. 0d. extra ; £5—2s. 0d. extra ; £10—3s. 6d. extra ; over £10 carriage free. All goods fully insured in transit.

L. & M. WAVE T.R.F. COILS. With Circuit, 4/6 pair.

L. & M. DUAL WAVE Superhet Coils. Aerial and oscillator 5/11 pair.

AERIAL ROD SECTIONS. Steel, heavily copper plated. 12ins. long, 1in. diameter. Any number may be fitted together. **PRICE** 2/6 per doz. Post free.

The 6CH6 for Audio

USING A VIDEO OUTPUT PENTODE FOR NORMAL AUDIO WORKING

By S. A. Money

THE majority of amateur radio constructors when faced with the prospect of building an audio output stage almost immediately think in terms of the 6V6 or some similar valve. Whilst the 6V6 makes an excellent output stage, there are other valves which can give an equal if not better performance, although not specifically designed for this purpose. Such a valve is the Brimar 6CH6.

The 6CH6 is a pentode designed for use in video amplifiers and similar applications. When used in these circuits it is important that the valve should have a high mutual conductance. In the case of the 6CH6 the phenomenal value of 12 mA/V has been

noticed that the cathode bias resistor is of somewhat lower value than usual. This is due to the short grid base of the valve, only 4.5 volts of bias being required instead of the more usual 13 volts.

The speaker transformer must be arranged to present an anode load of 6,000 ohms. This gives a ratio of about 40 : 1 if a three-ohm speaker is being used. The power output is 3 watts with harmonic content of around 8 per cent. This compares favourably with the 6V6, which gives an output of 4.5 watts with 8 per cent. distortion.

The input signal required at the grid for maximum output is only 3.5 volts peak. Such a signal would be available at the detector of an average radio receiver. This enables us to drive the output stage direct from the detector, thus saving a stage of A.F. amplification.

The 6CH6 can be substituted for a 6V6 simply by changing the valveholder and reducing the cathode resistor to 100 ohms. A point which must be watched, however, is the value of anode voltage used. The valve is designed to take 40 mA of anode current at 250 volts, under which conditions the anode will dissipate 10 watts. This is almost the maximum rating, and if the voltage were increased to, say, 300 volts the anode dissipation becomes excessive, causing overheating and possible damage to the valve. Most radio receivers have an H.T. rail of 200 to 250 volts, but in some circuits using the 6V6 an H.T. line of 300 volts or more is used. In such cases the voltage must be reduced if a 6CH6 is to be substituted.

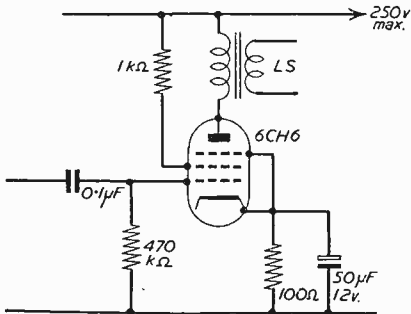


Fig. 1.—A single-ended stage.

attained. Such a high slope implies the use of a larger cathode, and this in its turn requires a larger amount of heater power. The heater of the 6CH6 consumes 0.75 amps at 6.3 volts, almost twice as much as a 6V6. An interesting point about this valve is that the peak cathode current, under pulsed operation, is no less than 1.5 amps.

Construction is of the modern all-glass type on a B9A "noval" base. The overall dimensions are 2½ in. high and ¾ in. diameter. Despite its small physical size the valve has a maximum anode dissipation of 12 watts. The small size and high power dissipation cause the valve to run quite hot. In fact, the bulb temperature under normal running conditions may well be in the region of 200 deg. F. Apparently this is quite in order since the manufacturers quote a maximum safe bulb temperature far in excess of this figure.

What is the advantage of using such a valve for an audio output stage? Since the valve has a short grid base and a high slope, it requires a smaller input signal for the production of a given output power. This means that it is possible to drive the output stage directly from a diode detector.

Single-ended Operation

Let us first consider the normal single valve output stage as used in the majority of domestic radio receivers. This usually consists of a pentode operating under Class A conditions. A circuit suitable for use with the 6CH6 is as shown in Fig. 1. It will

A Bedside Radio

Owing to its high sensitivity, the 6CH6 can be used to make a novel single-valve receiver. The valve is made to work as a combined detector and power amplifier. A normal reacting detector circuit is used, with the exception that a loudspeaker transformer is connected into the anode circuit. On local stations an output of some ½ to 1 watt can be obtained, giving ample volume from a 5in. loudspeaker. By adding a metal rectifier for the H.T. supply this could be made into an ideal receiver for use as a bedside radio.

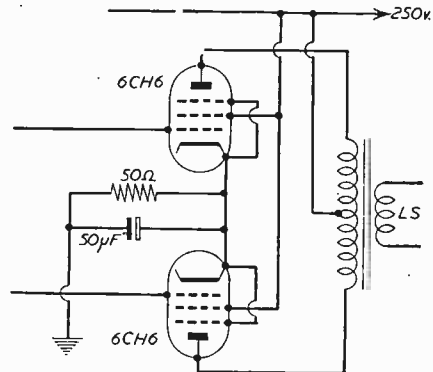


Fig. 2.—A push-pull stage.

Push-pull Operation

For those people who like to have more power from their amplifiers, push-pull operation can be adopted. The circuit for a pair of 6CH6's in Class A push-pull is given in Fig. 2. The bias resistor is again lower than usual for the same reason as before.

The anode-to-anode load presented to the valves should be 9,000 ohms. Taking again the case of a 3-ohm loudspeaker, the transformer ratio will need to be 55 : 1. The output obtained from this circuit would be about 8 watts with a harmonic distortion of 7 per cent. This should give ample volume for a large room or small hall. If still more power is required, the valves can be run in Class AB₁, in which case an output of some 12 watts should be obtainable.

No input circuit has been shown on the diagram,

since either a transformer or a phase-splitting stage can be used. The grid-to-grid input required in either case will be 9 volts peak for Class A operation. For Class AB₁ operation an input of 15 volts peak will be needed. It is not advisable to run the valves in AB₂, where grid current flows, since the permissible grid dissipation of these valves is small.

Operation as a Triode

The 6CH6 can be used as a triode by connecting the screen-grid to the anode through a 100-ohm resistor. For Class A single-ended operation the anode circuit must be matched to an impedance of 4,000 ohms. Output is much lower than for the pentode, being only 0.8 watt with 4 per cent. harmonic distortion. The input voltage must also be raised to 4.5 volts peak.

A Cascaded Twin-triode R.C.-coupled Amplifier/Mixer

THE circuit shown in Fig. 1 utilises a 12AT7 double-triode with the two halves individually operated as negative feedback triode amplifiers, each with an approximate voltage gain of 18.5. The signal at the *a* anode is fed into the opposite grid via the .01 μ F coupling capacitor, and the final output is taken from *b*-section anode. Since both amplifiers have the same gain, the overall voltage gain of the cascaded pair is the square of the composite gains (i.e., approximately 340).

At the same time a second signal can be injected into the *b*-grid to appear at the output (gain 18.5) mixed with the signal originated at the first grid. Thus the circuit has a wide variety of practical applications, some of which are "straight" amplification and mixing or monitoring amplifiers.

The immediately obvious use is a twin-channel mixing pre-amplifier wherein the microphone channel is fed via an appropriate input transformer to the *a*-grid and simultaneously the gram. channel put in at the *b*-grid, the resultant mixed signal, appearing at the second anode, being taken to the main amplifier. This has been successfully tried by the writer, the 270 K Ω grid leaks being replaced by 470 M Ω potentiometers. On the microphone channel the secondary of a 100 : 1 input transformer was connected straight across the potentiometer, and on the gramophone channel the pick-up output was similarly connected, with the addition of a 220 k Ω resistor between the wiper and the *b*-input, to avoid shorting out the microphone signal when the gramophone gain was turned to zero. Using this arrangement, gains of approximately 1,800 and 18 were obtained on the microphone and gramophone channels respectively.

A large value of grid-stopper is used to discourage parasitic oscillations, but even so care is required to keep all leads as short and direct as possible.

Increased Gain

The gain of the circuit could be increased, if desired, by using higher anode loads, or by putting 50 to 100 μ F by-pass

capacitors across the cathode-loads (i.e., removing negative feedback). The writer, however, experienced serious instability troubles on attempting this, apart from which microphony and overload distortion inhibit excessive gain values.

A further application would be to increase the cathode-load on the second half to 47 k Ω , and take an additional output lead from this cathode, as shown in the circuit of Fig. 2. Also the coupling-capacitor, grid-stopper and grid-leak are dispensed with and the first anode D.C.-coupled to the second grid. Hence the second half can function either as a cathode-follower, giving a low-impedance output to earth, or as a cathode-anode follower phase-splitter giving a paraphase signal across the two outputs for use in push-pull driving circuits.

It should be noted that the gain of a cathode-follower cannot exceed unity and so the maximum gain of the two last-mentioned circuits cannot exceed 18.5.

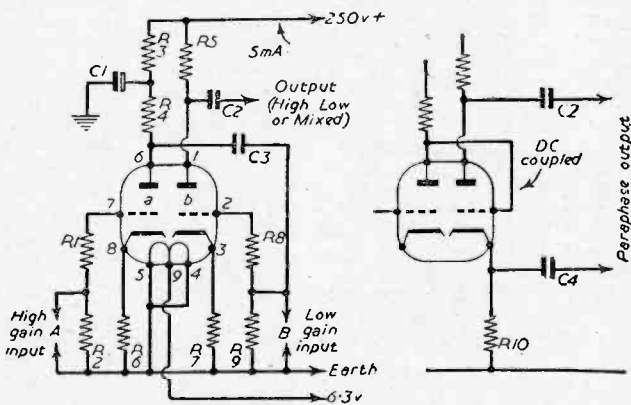


Fig. 1.—Main circuit.

Fig. 2.—A modification.

R ₁ , R ₈	27 K Ω	(1 watt.)
R ₂ , R ₉	270 K Ω	($\frac{1}{2}$ watt.)
R ₃ , R ₄ , R ₅ , R ₁₀	47 K Ω	($\frac{1}{2}$ watt.)
R ₆ , R ₇	1 K Ω	($\frac{1}{2}$ watt.)
C ₁	Electrolytic 8 μ F.	(350 v. wkg.)
C ₂ , C ₃ , C ₄	0.01 μ F.	(350 v. wkg.)

PLASTIC CABINET as illustrated, 11½ x 6½ x 5½ in., in walnut or cream. **ALSO IN POLISHED WALNUT**, complete with T.R.F. chassis, 2 waveband scale, station names, new waveband, backplate, drum, pointer, spring, drive spindle, 3 knobs and back, 22/6. P. & P., 3/6.

As above with Superhet Chassis, 23/6. P. & P., 3/6.

As above complete with new 5in. speaker to fit and O.P. trans. 37/6. P. & P. 3/6 with Superhet Chassis, 39/3. P. & P. 3/6.



Used metal rectifier, 230 v. 50mA., 3/6; gang with trimmers, 6/6; M. & L. T.R.F. coils, 5/-; 3 Govt. valves, 3/6 and circuit, 4/8; heater trans., 6/-; volume control with switch, 3/8; wave-change switch, 2/-; 32 x 32 mfd., 4/-; bias condenser, 1/-; resistor kit, 2/-; condenser kit, 4/-.


M & L Superhet Coils with circuit, 6/6; iron cored 465 IFS, 7/6; min. gang, 5/6; volume control with switch, 4/-; wave-change switch, 2/6; heater trans., 7/6; 4 v/h. 1/6; 4 Ex Govt. valves, metal rectifier and Xtal diode, complete with circuit, 14/6; 25 x 25 mfd., 1/-; 16 x 16 mfd., 3/3; condenser kit (17). 7/6; resistor kit (14). 3/6.

Medium and Long Wave Crystal set, in attractive plastic cabinet incorporating Germanium diode, 16/-.

Headphones to match above, per pair 7/6.

COMPLETELY BUILT SIGNAL GENERATOR

Coverage 120 Kc/s-320 Kc/s. 300 Kc/s-900 Kc/s., 900 Kc/s-2.75 Mc/s., 2.75 Mc/s-8.5 Mc/s., 8.5 Mc/s-25 Mc/s., 17 Mc/s-50 Mc/s., 25 Mc/s-75 Mc/s. Metal case 10 x 6½ x 4½ in., size of scale 6½ x 3½ in., 2 valves and rectifier, A.C. mains 200-250 v. Internal modulation 400 c.p.s. to a depth of 30%. Modulated or unmodulated R.F. output continuously variable 100 milli-volts. C.W. and mod. switch, variable A.F. output and moving coil output meter. Black crackle finished case and white panel, £4/19/6, or 34/- deposit and 3 monthly payments of 25/-. Post and packing 4/- extra.

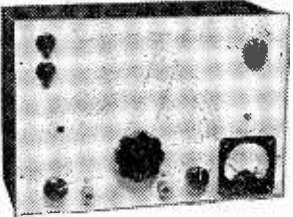

High impedance plastic recording tape by famous manufacturer. 1,200 feet complete on spool, 17/6. P. & P. 1/6. 600 feet 8/-, P. & P. 1/-.

Pr. 200/250 v., secondary 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 and 30 volt at 2 amps. Drop thro' 200-230, 200 mA., 6 v. 5 amps., 5 v. 3 amps., 27/6.

Terms of business: Cash with order. Despatch of goods within three days from receipt of order. Where post and packing charge is not stated, please add 1/6 up to 10/-, 2/- up to £1 and 2/6 up to £2. All enquiries S.A.E. Lists 5d. each.

Heater Transformer. Pri. 230-250 v. 6 v. 11 amp., 6/-; 2 v. 21 amp., 5/-.

R.I. MAINS TRANSFORMERS, chassis mounting, feet and voltage panel. Prices 230/250.

350-0-350 m.A. 6.3 v. 3 a. tap 4 v. 6.3 v. 1 a., 13/6.	
350-0-350 70 mA. 4 v. 5 a., 4 v. 2.5 a., C.T., 18/6. P. & P. on above transformers 2/-.	
500-0-500 120 mA. 4 v. C.T. 4 a. 4 v. C.T. 4 a. 4 v. C.T. 2.5 a., 27/6.	
500-0-500 250 mA. 4 v. C.T. 5 a. 4 v. C.T. 5 a. 4 v. C.T. 4 a. 39/6.	
P. & P. on the above transformers 3/-.	
32 mfd., 350 wkg.	2/-
16 x 24 350 wkg.	4/6
4 mfd. 230 wkg.	1/3
40 mfd., 250 wkg.	3/6
16 x 8 mfd., 500 wkg.	4/6
15 x 16 mfd., 500 wkg.	4/6
8 x 16 mfd., 450 wkg.	5/9
32 x 23 mfd., 350 wkg.	4/6
32 x 32 mfd., 350 wkg. and 25 mfd., 25 wkg.	6/6
25 mfd., 25 wkg.	11/4
250 mfd., 12 v. wkg.	1/-
16 mfd., 500 wkg. wire ends	2/3
8 mfd., 500 v. wkg., wire ends	3/6
8 mfd., 350 v. wkg., tag ends	1/6
50 mfd., 25 v. wkg., wire ends	1/9
100 mfd., 350 wkg.	4/-
100+200 mfd., 350 wkg.	4/-
16 x 16 mfd., 350 wkg.	3/6
Ex Govt. 8 mfd. 500 v. wkg., size 31 x 11, 2 for 200 v.	2/6
60+100 mfd., 250 v. wkg.	7/-
16+32 mfd., 350 wkg.	6/9
50 mfd., 180 wkg.	1/9
65 mfd., 220 wkg.	1/6
8 mfd., 150 wkg.	1/6
80+100 mfd., 230 wkg.	1/6
50 mfd. wkg. min. 275 wkg.	11/4
32+32 mfd., min. 275 wkg.	4/-
50 mfd., 50 wkg. 8 mfd., wkg., wire ends	1/9

Miniature wire ends moulded 100 pl., 50 pl., and 100 ea. 7/4.
 200-0-200 mA. 4 v. 4 a. twice 2 v. 2 a. 19/6
 250 v. 350 mA. 6.3 v. 4 a. twice 2 v. 2 a. 19/6
 Auto-trans. input 230/250 HT 500 v. 250 mA. 6 v. 4 a. twice 2 v. 2 a. 19/6
 250-0-250 mA. 6.3 v. 1.5 a., 0-5-6.3 v. 10/6

PATTERN GENERATOR 40-70 Mc/s. direct calibration, checks frame and line time base, frequency and linearity, vision channel alignment, sound channel and sound rejection circuits, and vision channel band width. Silver plated coils. Black crackle finished case, 10 x 6½ x 4½ in., and white front panel. A.C. mains 200-250 volts. This instrument will align any TV receiver. Cash price, £3.19.6 or £1.9.0 deposit and 3 monthly payments of £1. Post and packing 4/- extra.

TV. CONVERTER for the new commercial stations, complete with 2 valves. Frequency can be set to any channel within the 186-196 Mc/s. band. I.F. 5—will work into any existing TV receiver, designed to work between 42-68 Mc/s. Sensitivity 10 Mu/v. with any normal TV set. Input—arranged for 300 ohm feeder. 80 ohm feeder can be used with slight reduction in R.F. gain. Circuit EF80 as local oscillator, ECC81 as R.F. amplifier and mixer. The gain of the first stage, grounded grid R.F. amplifier, 10 db.

Direct power supply of 240 v. P.C. at 25 mA., 6.3 v. A.C. at 0.6 amp. Input filter ensuring complete freedom from unwanted signals. 2 simple adjustments only. £2.10.0. Post and packing 2/6.

Volume Controls. Long spindle less switch, 50 K., 500 K., 1 meg. 2/6 each. P. & P. 3d. each.

CONSTRUCTOR'S PARCEL MEDIUM & LONG-WAVE A.C. MAINS 230/250 2-VALVE PLUS METAL RECTIFIER, 22/6. Comprising chassis 10½ x 4½ x 1½ in., 2 waveband scale, tuning condenser, wave-change switch, volume-control, heater trans., metal rectifier, 2 valves and v/h holders, smoothing and bias condensers, resistors and small condensers, and medium- and long-wave coil. I.tz wound. Circuit and point-to-point, 1/3. Post and packing, 2/6 extra.

Volume Controls. Long spindle and switch, 1, 1 and 2 meg., 4/- each; 10 K. and 50 K., 3/6 each, 4 and 1 meg., long spindle, double pole switch, miniature, 5/-.

Standard Wave-change Switches, 4-pole 3-way, 1/9; 5-pole 3-way, 1/9. Miniature 3-pole 4-way, 1-pole 3-way, 2/6; 2-pole 11-way twin wafer, 5/-; 1-pole 12-way single wafer, 5/-.

Valveholders. Paxolin octal, 4d. Moulded octal, 7d. EF50, 7d. Moulded BTG, 7d. Loctal amphenol, 7d. Loctal pax., 4d. Mazda Amph., 7d. Mazda pax., 4d. B8A, B9A amphenol, 7d. BTG with screening can, 1/6. Duodecal paxolin, 9d.

Twin-gang .0005 Tuning Condensers, 5/-. With trimmers, 6/6.

Midget .00037 dust cover and trimmers, 8/6.

RADIOGRAM CHASSIS,—5 valve A.C./D.C. 3-way band superhet, 195/255 volts 19-49, 200/550 and 1,000-2,000 metres, fly-wheel tuning frequency, 470 Kc/s iron-cored coils and I.tz. Size of chassis 13 x 6½ x 2½. Complete with valves and 8in. P.W. speaker. p. & p. 5/-, £8.17.6.

Constructor's parcel, comprising chassis 12½ x 8 x 2½ in., cad. plated, 18 gauge v/h, I.F. and trans. cut-outs, back-plate, 2 supporting brackets, 3-waveband scale, new wavelength stations names. Size of scale 11½ x 4½ in., drive sp. drum, 2 pulleys, pointer, 2 bulb holders, 5 pax 1.0, w/h, 4 knobs and pair of 465 IFS, twin gang, 16 x 16 mfd. 350 wkg., mains trans. 250-0-250 mA. 6.3 v. 2 amp., 5 v. 2 amp. and 6in. M.E. speaker with O.P. trans. P. & P. 3/6. 39/6.

R. & A. M.E. 6in. speaker with O.P. trans., field coil 175 ohms, 9/6. P. & P. 2/6.
 R. & A. 6in. M.E. speaker with O.P. trans., field 440 ohms. 10/6. P. & P. 2/6.

Battery Charger, input 230/250 v., output 6 & 12 v. 1 amp. Black crackle finished case size 10 x 6 1/4 in. P. & P. 3/-, 21/6.

Potato & Vegetable Peeler, by famous manufacturer, capacity 4 lbs., complete with water pump. All aluminium construction, white stove-enamel finish. Originally intended for adaption on an electric food-mixer, can be easily converted for hand operation. 39/6. P. & P. 3/-.

Primary, 200-250 v. P. & P. 2/-.
 350-0-300 100 mA., 6 v. 3 amp., 5 v. 2 amp., 82/6.

Drop thro' 350-0-350 v. 70 mA., 6 v. 2.5 amp., 5 v. 2 amp., 14/6.

Drop thro' 250-0-250 v. 80 mA., 6 v. 3 amp. 5 v. 2 amp., 14/6.

Drop thro' 280-0-280, drop through, 80 mA., 6 v. 3 amp., 5 v. 2 amp., 14/6.

250-0-250 80 mA., 6 v. 4 amp., 14/-.

Drop thro' 270-0-270, 80 mA., 6 v. 3 amp., 1 v. 1.5 amp., 13/6.

Drop thro' 270-0-270 60 mA., 6 v. 3 amp., 11/6.

Auto Trans. Input 200/250. H.T. 350 v. 350 mA. Separate L.T. 6.3 v. 7 a., 6.3 v. 1½ amp., 5 v. 3 amp., 25/-, P. & P. 3/-.

Pri. 200/250, Secondary 9 v. 3.5 amp., 6.3 v. 3 amp., 12/6.

Pri. 230 v. Sec. 500-0-500 and 500-0-500 250 mA. both windings. 4 v. 3 amp., 1 v. 3 amp., 39/6. P. & P. 5/-.

Mains Transformer, fully impregnated, input 200, 220, 230 and 240. Sec. 600-0-600 275 mA., and 200 v. at 30 mA., complete with separate heater transformer. Input 210, 220, 230, 240. Sec. 6.3 v. 2 amp. three times, 0, 4, 6.3 v. at 3 amp. and 5 v. 3 amp., 45/-, P. & P. 5/-.

Mains Transformer, fully impregnated, input 210, 220, 230, 240. Sec. 350-0-350, 100 mA., with separate heater transformer. Pri. 210, 220, 230, 240. Sec. 6.3 v. 2 amp., 6.3 v. 3 amp., 4 v. 6 amp., and 5 v. 2 amp., 30/-, P. & P. 5/-.

D. COHEN, RADIO AND TELEVISION COMPONENTS
 Frequency, 23, HIGH STREET, ACTON, W.3. (Opposite Granada Cinema)

Hours of Business: Saturdays 9-5 p.m. Wednesdays 9-1 p.m. Other days 9-4.30 p.m.

VALVES *Same Day Service*

All Guaranteed New and Boxed

1A7GT	6K8C	8/6	35L6GT	EP01	6/9
11/6	6K8GT	9/-	8/6	EP02	5/6
1C5GT	7/9	6K25	11/-	35Z4GT	8/6
1H5GT	6LD20	9/6	8/6	EL31	7/9
1N5GT	11/6	6P25	12/6	35Z5GT	EY31
		8P28	17/6	8/6	EZ40
		607GT	9/-	50L6GT	EZ41
1R5	7/3	6SN7GT	8/6	8/6	PW4/500
1S4	7/3		8/6	8/6	
1S5	7/3	6U4GT	8/6	304 (Bar)	KT83
1T4	7/3		17/6	8/6	MU14
304	7/6	6V6G	7/6	8/6	N78
3Q5GT	11/6	6V6GT	7/6	AZ31	10/9
			8/6	1D77	6/9
354	7/3	6X5GT	6/9	DAC32	PL81
3V4	7/3	7B7	7/6	8/6	PL82
5Y3GT	8/6	7C8	7/6	DAF96	8/6
5Z4G	8/6	7C8	7/6	DF33	11/6
6AL5	6/9	7H7	7/6	DF96	8/6
6AM5	7/9	7H7	7/6	DH77	7/9
6AM6	6/9	7Y4	8/6	DK32	11/6
6ATJ	9/6	10C1	11/6	DK32	7/6
6BAJ	6/6	10P1	10/-	DK96	9/6
6BF6	6/6	10D11	DL33	11/6	U50
6BH6	6/6	10/-	DL35	7/9	U78
6BJ6	6/6	10P13	10/-	DL96	8/6
6BW6	7/6	10P14	11/6	EB91	9/6
6BW7	9/6	12AH8	10/-	EBC33	7/6
6CH6	9/6	12AT7	9/-	EBC41	10/-
6C4	7/9	12AU6	7/6	EBF010/8	10/8
6C9	9/6	12AU7	7/6	ECC81	9/-
6F1	10/6	12K7GT	10/6	ECH42	10/6
6F6G	7/6	12K7GT	10/6	UF41	9/-
6F12	6/9		9/-	ECH81	9/-
6F13	13/6	12K8GT	10/6	10/8	UL41
6F14	13/6		10/8	ECL80	9/-
6F15	10/6	12Q7GT	10/6	EP37A	16/6
6J6	3/6		9/-	17/-	VP4B
6L7GT	7/6	20D1	8/6	EP29	6/6
6K7G	8/-	20F2	9/6	EP41	9/-
6K7GT	8/-	25Z4G	9/6	EP50	7/6
		25Z6G	8/6	EP80	10/-

Postage 4d. per valve extra.

READERS RADIO
 24, COLBERG PLACE, STAMFORD HILL, LONDON, N.16. STA. 4587

L. J. T.

MAIL ORDER SUPPLIES
 119, WESTBOURNE GROVE, LONDON, W.2.

VALVES

6X5	7/-	3V4	7/6	7C6	9/-
EA50	1/9	354	7/6	12K8	9/-
80	8/6	1L4	7/6	12K7	9/-
6K7	5/3	1U5	7/6	EB91	7/6
5Z4	8/6	6V6	7/6	EP91	6/6
6Q7	8/9	6K8	8/6	12BE6	5/6
35Z4	8/9	757	9/-	6AQ5	8/-
35L6	8/9	787	9/-	6BV6	8/-
1T4	7/6	7Q7	9/-	6X4	7/6
1R5	7/6	7H7	9/-	35V4	7/6
1S5	7/6	7C5	9/-		


ELECTROLYTICS Mould Seals
 8+16 450 v. 3/- .05 71d.
 32+32 450 v. 4/4 .04 7d.
 8-450 200MA 450 v. 2/3

Resistors.— $\frac{1}{2}$ watt, 1 $\frac{1}{2}$ d.; $\frac{3}{4}$ watt, 2d.; 1 watt, 3d.; minimum, 12 each.

3 Valve Amplifiers.—A.C. only. 4 watts Output, Tone Control, etc. Few only (suitable all types Pickups), £3 7s. 6d. each.

Radio Cabinet Kit.—Complete, size 11 $\frac{1}{2}$ in. x 7in. x 5in., 26/6 each.

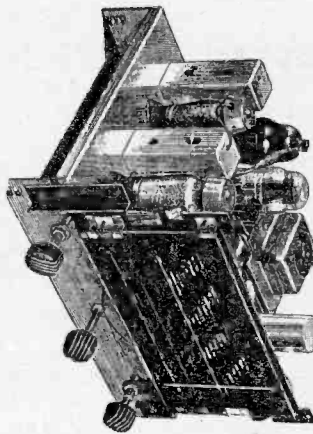All goods offered subject to being sold. Equivalents will be supplied unless otherwise stated. All valves guaranteed. Terms: Cash with Order or C.O.D. Packing Free. Postage at cost on orders under £5.



THE CORONAM TOWER
 is but one of the many outstanding Feeders, Receivers, Amplifiers and Test Gear (see previous ads. for list) fully described together with blueprint circuits and complete parts lists in the famous
+ RODING HOME CONSTRUCTOR'S HANDBOOK
 which for ONLY 2/6d. just about represents the finest value the radio enthusiast can get to-day. Printed on finest glossy art paper it also contains Set Building and Servicing Hints, Facts and Formulae, Resistance Colour Code, Symbols, etc., AND our current Catalogue. **SO DON'T DELAY—SEND TO-DAY!** Remember! Our Superhet Tuning Units are pre-aligned and sealed for maximum efficiency—no test gear being required by the Constructor. All components and chassis are available from us at reasonable prices and are fully identified. **FREE "ABC" Construction Sheets available (see Handbook for details).**
RODING LABORATORIES (Dept. CF2) BOURNEMOUTH AIRPORT, CHRISTCHURCH, HANTS.
 + Also obtainable from leading booksellers and component stockists.

W. B. SUPPLIES 100, Oldham Street, MANCHESTER, 4. Tel.: CENTral 4246.

Terms: Cash with order. Orders under 20/- add 6d. postage, etc., over 20/- add 1/-.
RECTIFIERS.—250 volts, 60 Mcls. 5/-; 75 Mcls. 7/6.

GERMANIUM DIODES.—G.E.C. 1/3 each. Valves VS70, Voltage Stabilizer, 2/-; 6V6GT American, 6/11.

YANLEY TYPE SWITCHES.—2 pole 6 way (2 bank), 2/3; 4 pole 3 way midget, 1/6; 5 K. wire wound pre-set pots, 1/-; midget pre-set pots, 5/6, 9d., 10d., 1/1.

SPEAKER FRET.—Woven, 12in. x 12in., 2/6. Expanded metal (gold), 12in. x 12in., 4/6; 12in. x 18in., 6/9.

METERS.—20 amp. charge/discharge, centre zero D.C., 7/6; 40 volts D.C. meters, 6/-.

VOLGE HOLDERS.—UX4, pavolin, 2/-; 200V, 10/6.

CHOKES.—10 Hys. 60Mls., 6/6; 80 Mls., 6/6; 100 Mls., 7/6; 5 Hys 200 Mls., 7/6.

INTERFERENCE SUPPRESSORS for radio, complete with instructions, 5/-.

H.T. BATTERIES.—Midget, 60 volt + 1 $\frac{1}{2}$ volt, tested, 2/- each.

CAN CONDENSERS.—8 mfd., 500 volts, 1/-; **FILAMENT TRANSFORMERS.**—New stock, mains input 6.3 volts 2 amps, output, 6/11; 12 volts 1 amp., 8/6; 12 volts 2 amps, 13/6.

WIRE WOUND RESISTANCES.—Tapped 300 Ω 2in. long with 1/3.

VARIABLE CONDENSERS.—Air spaced, 50 pF, 1/-; 115 pF, 2/6; 500 pF, 5/-.

CRYSTAL SET COILS.—Medium wave, 1/3; long and medium wave with reaction, with circuit, 3/9.

SPECIAL OFFER, CAR TYRES.—Ex W.D., as new, 59/6; with tube, carriage 3/-, size 500 x 19 only.

BENTLEY ACOUSTIC Corp., Ltd.
 38, Chalcot Road, N.W.1. PR/mrose 9090.

0Z4	6/-	6U7	8/6	13	8/6	HL1920	6/8
1A5	8/-	6V6G	7/6	57	8/6	KF35	8/8
1D9	8/6	6X4	7/6	58	8/6	KT2	5/6
106	6/6	6X5	7/-	22	4/6	KTW62	5/8
1L4	6/-	6Z4	6/6	76	7/-	KTW63	6/8
1L105	4/6	706	7/6	77	8/-	KTZ63	6/8
1LN5	4/6	706	7/6	83	8/-	KTZ66	12/8
1R5	7/-	7D8	6/6	84	2/6	MR4	5/8
1R5	7/-	7H7	7/6	807	7/6	Mepen	5/6
1T4	7/-	7Q7	8/-	955	5/-	Mwpen	7/6
2D91	8/6	7R7	8/6	6763	8/-	N77	6/8
2X2	4/6	7N7	7/6	9002	5/6	OD3	8/8
306	2/6	4D2	2/6	9003	5/6	PC84	12/8
309	10/-	9D2	3/-	ACT33	10/6	PCF80	12/8
5U4	8/-	10C2	10/6	AL60	4/6	PEN46	7/6
5Y3	7/6	10P1	10/-	AP4	7/6	PL38	18/-
5X4	8/6	10L11	10/-	ATP4	3/-	PL81	10/6
6A7	8/6	10P13	10/-	BL63	7/6	PL32	10/6
6AB7	6/-	11D3	6/-	CHL1	17/6	PM12	4/6
6AC7	6/6	12A6	6/6	DL73	9/6	PM12M	7/6
6AK5	7/6	12AH7	12/6	DL83	8/-	PY80	10/6
6AM6	6/6	13AT7	7/-	EA30	16/6	PY82	8/8
6AQ5	9/-	13A17	9/-	EA76	10/6	Q123	12/8
6AT6	6/-	13AX7	6/-	EC91	9/6	Q87020	10/8
6BA6	6/6	12BE6	6/6	EX34	1/6	Q815015	
6BE6	6/6	12C8	7/6	EB01	6/-		10/8
6BJ6	6/6	12EL1	30/-	EBC33	7/6	RM4	12/6
6BW6	7/6	12H6	2/6	EC01	7/-	RP4	7/6
6C4	7/6	12K3	8/6	KCC35	9/-	RF41	2/8
6CH6	6/6	12K3	8/6	KCC35	9/-	RF61	2/8
6F17	9/6	12S17	7/-	ECC82	10/6	8130	5/8
6F32	6/-	128K7	6/6	ECC91	7/6	TP22	8/8
6F33	9/6	128Q7	8/6	ECH42	10/-	U229	12/8
6H6G	6/6	128R7	7/6	EP28	4/6	U4E42	12/6
6H7	5/-	12Z3	8/6	EP39	6/6	UBL21	10/8
6J6	7/6	1311	8/-	EP50E	5/-	UP41	9/-
6J7	5/-	14H17	10/6	EP50A	8/-	UL41	9/6
6K6G	6/6	14R7	10/6	EP54	5/-	UV6	10/-
6K7G	5/-	15D2	4/-	EP73	10/6	UY41	9/6
6K8	8/8	8/-	8/-	EP80	10/6	VP2	8/8
6L7G	7/6	19H11	10/-	EP91	6/6	VP2B	10/8
6N7	7/6	19F4	35/-	EL32	6/6	VP4	8/8
6R7G	8/6	20L1	11/6	EL38	20/-	VP33	6/8
6SA7	8/6	35L6	8/6	EL41	6/6	VP41	7/8
6SH	5/6	309	7/6	EM34	10/6	VR53	5/-
6SJ7	8/-	30L1	11/6	EY51	11/-	VT501	6/6
68K7	6/-	35L6	8/-	EY71	7/6	X24	10/8
68N7	8/6	42	8/-	PC2	10/6	X69	10/6
6U5(UX)	7/-	42Mpt	15/-	H39	5/-	Z77	7/6

Post 6d. each. 24 hour C.O.D. service. All boxed and guaranteed. Complete list free S.A.E.

Oscillatory Circuits

AN EXPLANATION OF THE WORKING OF THE VALVE AS AN OSCILLATOR

By F. E. Apps

OSCILLATORS can be said to be in two different classes. One is the type that is required to give large power output such as R.F. heating apparatus or transmitters, and the other is the type that gives stable frequency output with very little power output. The latter is used in superheterodyne receivers. Continuous oscillations can be set up in an oscillatory circuit in several ways. They are the H.F. Goldschmidt generator, the Poulsen arc, the thermionic valve and the Rochelle salt crystal, and including, of course, the latest device, the two-point contact transistor. The Goldschmidt generator and the Poulsen arc are now obsolete. For the purpose of this article we will deal with the thermionic valve and its circuit or circuits.

For a circuit to be in a state of oscillation it is necessary to have two parts of the circuit capable of storing energy and passing this energy from one part to another at the natural frequency of the circuit. These two parts of a circuit are the inductance, which stores energy by means of its magnetic field, and the condenser, which also stores energy in its electrostatic field. In Fig. 1 we see an oscillatory circuit in combination with a three-electrode valve. When the D.C. voltage to the anode is made anode current commences to flow through L1, which is magnetically coupled with L2, so that as the anode current increases an increase of flux from L1 cuts across L2. This induces a voltage in L2 which is applied between the grid and cathode of the valve. Oscillation of the grid circuit will now take place at its natural frequency. This will cause the grid of the valve to vary its potential from positive to negative, and thus cause fluctuations of the electron stream, thus varying the anode current of the valve at the frequency of the grid circuit. Now if the coupling of L1 L2 is sufficiently close the effect of the varying potential of the grid circuit upon the anode current, and the alteration of anode current through L1 upon the grid circuit via L2, will, if correctly arranged, cause the circuit automatically to fall into oscillation at the frequency of the grid circuit, and oscillations will be maintained.

Maintenance of Oscillations

Oscillations will be maintained only when the power fed back is equal to or greater than the power dissipated in the circuit. This can be expressed as follows:—

When the anode coil supplies energy in phase with the oscillatory current in the circuit—Energy introduced into the LC circuit = $(\omega MI_a)I$ watts.

Net loss of energy in LC circuit is at the rate of $I^2R - (\omega MI_a)I$ watts = $I^2 \left(R - \frac{Mgm}{C} \right)$ since $V_g = \frac{1}{\omega C}$.

This shows that when M is equal or greater than CR/gm oscillations will be continuous.

The foregoing, with Fig. 1, applies only to small oscillators where large power is not required. When a large output, as for a transmitter, is required the circuit is then modified as Fig. 2. It will be noticed in this case that the feed-back coil is in the grid circuit, so that more power can be drawn from the oscillatory circuit which is in the anode lead. The action of the two circuits is very similar. On switching on the H.T. a shock is given to the circuit by the slight change in current, and oscillations are set up. To maintain the oscillations the coupling between the two coils must be such as to allow the grid/cathode voltage variations to supply enough power to make good losses through damping.

The Hartley Oscillator

Generation of oscillations is possible when the oscillatory grid voltage V_g is more than 90 deg. out of phase with the anode oscillatory voltage V_a . Also the energy supplied to the oscillatory circuit must be in the correct phase and be sufficient to overcome the losses through damping. The action is as follows (see Fig. 3). The oscillation set up in the tuned circuit produces an oscillatory voltage across that part of the coil which is between grid and cathode. Now for self oscillation this voltage must be in antiphase to the anode/cathode voltage, i.e., the voltage across that part of the coil between anode and cathode. In Fig. 3 it will be noticed that this is

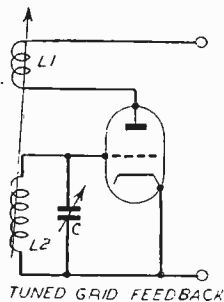


Fig. 1.

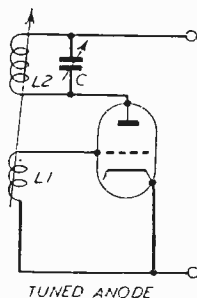


Fig. 2.

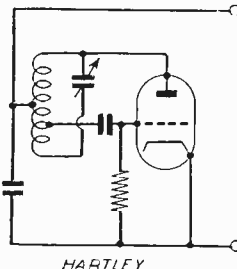


Fig. 3.

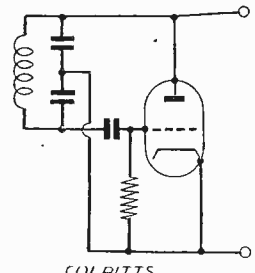


Fig. 4.

Some standard oscillator circuits.

done by connecting the cathode to a point on the coil between the points connected to anode and grid. This point is obviously always at an intermediate potential between the anode and grid points. Thus, if at any instant the anode point on coil is positive to the cathode point, then the grid point must be negative to the cathode point at the same instant, and so the voltages from anode to cathode and grid to cathode are always in opposite directions. The grid condenser and grid leak are to isolate the grid from the H.T., and to produce an automatic negative bias for the valve so as to increase its efficiency.

The Colpitts Oscillator

The Colpitts oscillator, Fig. 4, is similar in action to the Hartley. The circuit differs from the Hartley in that the grid excitation is direct capacitive, whereas the Hartley is direct inductive. When an oscillatory voltage is developed across the tuned circuit the cathode potential is intermediate between the anode

and grid potentials, V_a and V_g are in antiphase and the circuit is self-oscillatory.

When the circuit is used on high frequencies it is found sufficient to place the LC circuit between anode and grid and rely upon the inter-electrode capacity of the valve to provide grid excitation.

Frequency Variation

Now although the frequency at which a valve will oscillate may be stated as

$$f = \frac{10^6}{2\pi\sqrt{LC}}$$

this is, in fact, not exactly the truth because frequency also depends on the valve constants μ and g_m . It also depends upon the LC values of any circuits coupled to the oscillatory circuit, and the inter-electrode capacities of the valve. Unless all these remain constant frequency variation will occur.

(To be continued)

Portable Lifeboat Radio

THE Marconi International Marine Communication Co., Ltd., now has in production a new portable radio transmitter and receiver for use in ships' lifeboats. Known as the "Salvita," it is completely self-contained and watertight and will float after having been thrown into the sea from the deck of a ship in distress.

As long ago as 1931 the Marconi Marine Co. designed and produced a small portable transmitter for use in small boats, such as the dories used in line-fishing on the Newfoundland Banks, where sudden fog so often hid the dories from their parent craft.

The new "Salvita," descendant of these earlier sets, meets the requirements of the latest G.P.O. specification for this type of equipment, and has successfully undergone most stringent tests simulating the worst conditions likely to be encountered at sea anywhere in the world.

A specimen "Salvita" was operated while being continuously shaken on a special vibrating table. Then followed a bump test during which it was subjected to 500 jolting bumps at the rate of one per second with a free drop of 1in., after which it still functioned perfectly. Its next ordeal, under dry-heat conditions, consisted of 10 hours in a temperature of 70 deg. C., followed by two hours of continuous working at 55 deg. C.

Perhaps the most dramatic test to which the "Salvita" was subjected was the 30ft. drop test in which the set was actually thrown from a height of 30ft. into water, and operated at full efficiency after it had surfaced and been recovered.

The "Salvita" is housed in a cylindrical case a little over 2ft. in height and painted bright yellow for easy recognition in water, and is fitted with stout carrying handles which are also used to pass lashings round to hold the "Salvita" steady for operation. The upper portion of the case contains a medium- and short-wave transmitter and medium-wave receiver, all the operating controls being placed on the circular top panel and covered by a watertight lid when not in use. The transmitter, which is crystal-controlled, can be switched to either 500 kc/s or 8,364 kc/s.

New Hi-fi Recording Tape

E. M.I., who were the first to institute immediately after the war the new technique of magnetic tape-recording for all "His Master's Voice," Columbia and Parlophone records also pioneered the manufacture of the tape itself, and their plant, at Hayes, is the largest and most up-to-date production unit in the country.

They now introduce a new high-quality recording tape for professional or general use; the same tape, in fact, which is used in the studios for the initial recordings for all "His Master's Voice," Columbia and Parlophone discs, as well as for the recently-released "His Master's Voice" and Columbia tape records.

Outstanding features of the new Emitape are high sensitivity, marked anti-static characteristic, and freedom from curl—the latter ensuring uniform and close contact with the head and, therefore, uniformity in recording and reproduction. In addition, the P.V.C. base used instead of cellulose acetate gives high tensile strength (7½ lbs. per ¼in. width) and yield point (4½ lbs. per ¼in. width); very low elastic elongation (less than 0.5 per cent. at 1 lb. load, 15 secs. application) and longitudinal temperature co-efficient (4×10^{-5} per degree F); negligible humidity expansion.

Sensitivity is considerably higher than previous tapes (9 dB above H50 tape); the print signal is at least 60 dB below the test signal after close contact for five minutes; the basic unweighted noise from a properly erased tape is at least 65 dB below peak recording level, and modulation noise at least 50 dB below peak modulation at 2 per cent. total harmonics.

Prices

Typical prices are: 5in., double-sided, plastic spool, with 600ft. of tape—type 88 at £11.0, and type 77 at £11.0; 7in. spools (1,200ft.) cost £11.50 and £2.8.0, respectively.

A comprehensive range of editing and jointing accessories are also available.

Emitape is marketed by E.M.I. Sales and Service, Ltd. (Recording Equipment Division), Hayes, Middlesex.

MIDGET RADIO CABINETS



This well-known cabinet of which thousands have been sold is ideal for every constructor. Complete with chassis, dial, backplate, cord drive, pointer and dial drum.
Price 27/6 each.


CHOKES

20H, 250 Ω , 60 mA. Clamp construction..... 6/- ea.
10H, 200 Ω , 20 mA. Clamp construction..... 9/3 ea.
3H, 250 mA., 200 Ω . Fully shrouded..... 18/3 ea.

TRANSFORMERS FOR BATTERY CHARGERS

220 v. Input Tapped 6-12 v. 1 amp..... 13/6 ea.
220 v. Input Tapped 6-12 v. 3 amp..... 18/- ea.
(Both with tap on Primary for 2.5 v. Pilot light)

LOUDSPEAKER CABINETS

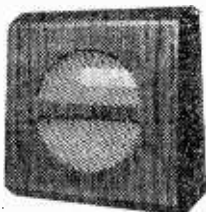

This attractive white finished cabinet is suitable for 8in. or 8in. speaker units. Metal speaker fret, complete with back and rubber feet.
6in. type:
M-anses 8 1/2in. x 4in. x 4in. at base. Price 15/6 each.

8in. type:
Measures 10 1/2in. x 10 1/2in. x 5in. at base. Price 19/6 each.

CARRYING CASE

Suitable for use as a projector or recording case, size 15in. 9 1/2in. x 13in. Internal dimensions: 1 1/2in. long, 1 1/2in. deep, 2 1/2in. broad. H.T. 8 1/2in. rear H.T. With a black resin finish. Weight 8 1/2lb. 13/6 ea.
Post and packing 2/6.

"CLEM" Travelling Iron with Arbestos Stand.

Size 4in. x 2in. x 2 1/2in. including handle, complete with lead and switch to enable it to be used on any voltage between 110 and 250 v. A.R.C. adapter is fitted on the lead, it can be available: Blue, Green, etc.) ... 17/6 ea.

SENTERCEL RECTIFIERS

RM1, 3/9 ea.; RM2, 4/2 ea.; RM3, 5/- ea.; RM4, 18/- ea.

TERMS: Cash with order or C.O.D. Postage to be added to orders as follows: 9d. up to 10/-; 1/- up to 20/-; 1/6 up to 40/-; 2/- up to £5. MAIL ORDER ONLY: Send 6d. in stamps for illus. catalogue.

ALPHA FOR VALVES

BBC41	11/-	M8/PEN	5/-	VR33	4/6
EPF90	11/6	N78	16/6	VR34	2/-
EPH4	11/6	P41	9/-	VR35	7/6
EPH42	10/6	EPN25	9/-	VR36	4/-
EPH50	11/6	PEN46	8/6	VR37	11/6
EPH51	10/-	PEN220A	4/-	VR38	2/6
EPH80	11/6	PL33	9/6	VR39A	11/6
EPH9	12/6	PL34	12/6	VR39	11/6
EL41	11/6	PL32	11/6	VR91	11/6
EL42	11/6	PL35	20/-	VR91	11/6
EM41	9/-	PL3M	20/-	VR92	11/6
EPY91	13/6	LY50	21/-	VR192/30	5/6
EZ40	10/-	PY81	11/6	VR110	4/-
EZ41	11/-	PY84	10/6	VR119	4/-
EL143	2/-	PN27	15/-	VR193	4/6
FW 1/300	10/-	QP21	7/6	VR120	2/-
H90	11/6	Q10	8/6	VR117	6/3
H90(FD)	7/9	SP229	8/6	VR115/20	11/6
H12HDD	7/6	TP26	9/-	VR111	8/6
H210-SP2	6/9	U10	9/-	VR112	2/6
H210	6/9	U11	14/0	VR194A	11/6
KB5	8/6	U12	14/0	VR113	3/6
KF3	8/6	U13	10/6	VR114	11/6
K143	8/6	U14	14/6	X18	11/6
KL13	8/6	U21	10/6	X63	11/6
KT4	8/6	U403	10/6	X99	11/6
KTM1	13/6	U404	10/6	X19	11/6
KT74	8/6	U4F2	12/6	X79	11/6
KT741	6/0	UB41	9/-	Y63	6/-
L10D0	6/9	UB41	11/-	Z61	10/-
LP251	6/9	UC42	11/-		
M14	5/6	UF41	11/-		
MH14	6/9				

"ALPHA" FOR SETS OF VALVES

Two VR91 (EP50) Valves Ex. Knud new units, 6/- each, 45/- set.
6K84, 6K74, 6Q74, 5Z40, 6V04, 37/6 set.
1R5, 1R5, 1T1, 1R4, or 1V4 or 3R4, 30/- set.
6K82, 6K70, 6Q70, 2V40, 2Z40, 5Z10CT, or 5010CT, 37/6 set.
Ten 6AM5 (EP91), 75/- set.
7B7, 7B7, 7C6, 7C5, 7V4, 42/- per set.
EUCH2, EP41, EBC41, EL41, EZ40, 59/- per set.
UC42, UF41, EBC41, UL41, UL41, 50/- per set.

SOLDERING IRONS

Solon type 994 Fitted Oval Bit ... 18/11 ea.
Solon type 968 Fitted Pencil Bit ... 19/11 ea.
Both types are complete with approx. 6ft. of Heuley 3-core cable and are suitable for 230/250 v.

SOLDERING PASTE

Large tin soldering paste by Type Chemical Co. Approx. 1lb., 3/9 per tin.

METAL RECTIFIERS

12 v. 1 amp., 3/6 ea.; 12 v. 1 amp. 4/6 ea.; 2 v. 1 amp., 3/- ea.; 250 v. 45 mA., 6/3 ea.; 250 v. 75 mA., 7/6 ea.; 300 v. 60 mA., 7/6 ea.

MAINS DROPPING RESISTORS

72 Ω Welwyn 2 section 40 Ω 32 Ω ... 1/9 ea.
725 Ω Erie tap at 600 Ω ... 1/6 ea.
650 Ω taps at 375 Ω 500 Ω 5 Ω 390 Ω ... 2/6 ea.
750 Ω Mains Dropper for Midget Radios with a tap at 125 Ω size 3/16 long 6 1/2 in. dia ... 1/3 ea.
Dagole Mains Dropper 3A, cement coated with 2 sliders ... 3/8 ea.
2 amp. as above 1,200 Ω ... 3/9 ea.
Green Vitreous Mains Dropper 1,228 Ω 2 taps 1/3 ea.
Zenith Mains Dropper 910 2/- ea.

PANELS, etc.

Resistor and Condenser Panels, over 50 items guaranteed, including wire wound resistors ... 4/- ea.
Resistor and Condenser Panels, over 36 items guaranteed ... 2/6 ea.
Tagboard, latest type vertical mounting, with resistors and condensers ... 1/- ea.
Tagboard, containing 2 watt resistors, wire wound resistors and condensers ... 2/- ea.

PLUGS AND SOCKETS

Bolgin 2-pin plug and chassis mounting socket, for mains ... 2/6 ea.
Non-reversible 7-pin plugs and sockets ... 1/3 ea.
3-sockets on a panel 2in. x 1 1/2 in. to take wander plug ... 22/- ea.
EKO Local/Distant plugs and sockets ... 3d. ea.
Bolgin 7-pin Plug and Chassis Mounting Socket 2/- ea.

TAG BOARDS, ETC.

2 Tag Type and Earth ... 2/d. ea.
4 Tag Type and Earth ... 3/d. ea.
Tag Board No. 4 ... 1d. ea.
Group Tag Board, 3/d. per inch, any length cut up to 1 yard.
GROUP TAG BOARD
9-way Open Type 4in. long with fixing feet ... 10d. ea.

MAINS TRANSFORMERS

3-WAY MOUNTING TYPE MT1
Primary: 200-220-240 v.
Secondary: 275-0-275 v.
80 MVA 0-6.3 v. 4 amp. 0-5 v. 2 amp. Both tapped at 4v. ... 17/6 ea.

MT2
Primary: 200-220-240 v.
Secondary: 250-0-250 v.
80 MVA 0-6.3 v. 4 amp. 0-5 v. 2 amp. Both tapped at 4v. ... 17/6 ea.

MT3
Primary: 200-220-240 v.
Secondary: 200 v. 2 amps. Taps at 3 v., 4 v., 5 v., 6 v., 8 v., 9 v., 10 v., 12 v., 15 v., 15 v., 20 v., 24 v. ... 17/6 ea.

EX GOVERNMENT AND SURPLUS CONTROLS

This popular range is suitable for all Television constructors, etc. Keep your costs down when building the "Argus" or "Simplex" receivers Available: 500 Ω , 600 Ω , 1,000 Ω double type, 2K Ω , 5K Ω , 10K Ω , 20K Ω , 25K Ω , 50K Ω , 200K Ω , 100K Ω , 1 meg Ω , 1 meg Ω , 1 meg Ω , 2 meg Ω , 50K Ω double type. All 1/2 each

COLVERN PRE SET CONTROLS
Type CLR 1106/78 1,000 Ω 3/8 ea.
Type CLR 1126/78 250 Ω ... 1/8 ea.

WHEN ORDERING PLEASE QUOTE "DEPT. P.W."



Best Buy at Britain's

COMMUNICATIONS RECEIVER TYPE R1155.—For world-wide reception. WE ARE ONCE AGAIN ABLE TO OFFER THESE FINE RECEIVERS ABSOLUTELY BRAND NEW ORIGINAL TRANSIST CASE AT £11/19/6, plus 10/6 carr. This delivery is in really fine condition. If you are contemplating the purchase of one of these receivers in the near future, we advise you not to delay in order to secure a really "MINT" receiver.

A few slightly soiled models still available at £7/19/6, plus 10/6 carr. A.C. Mains power packs for same at £4 10/-, £5/5/- and £6 10/-, carr. 3/6. Send S.A.E. for full details or 1/3 for circuit, etc.

RECEIVER TYPE CR100.—A super communications receiver covering 60 kc/s to 30 mc/s in six bands. Built-in A.C. mains power pack. 2 R.F. stages, 3 I.F. stages, variable selectivity Xtal Filter, B.F.O., etc. Good condition, complete with new valves and air tested. A bargain at £27/10/-, plus £1 carriage.

TR1196 RECEIVERS (25/73).—This is a six-valve superhet receiver with 465 kc/s I.F.'s. Complete with all valves—2 F393, 1 EK32 2 EF36, 1 EBC32. In Good Condition with full conversion data. ONLY 27/6 each, plus 2/6 post.

POWER PACK TYPE 801.—Contained in a neat black case size 8 1/2 in. x 4 1/2 in. x 6 1/2 in. Input for 220-250 volts A.C. 50 cps. Outputs 250-0-250 v., 6.3 v. at 2.8 amps., 6.3 v. ut. 6 amps. for 6X5 rectifier, 31 v. at 3 amps. supplies metal rectifier for bias. The transformer is a massive job. Price ONLY 37/6, plus 2/6 post.

E.M.I. OUTPUT METER.—Desk Type. consists of a 2 1/2 in. 1 mA. meter with full wave bridge rectifier. Range 0-500 mWatts and 0-5 watts. Brand New and Boxed. ONLY 35/- each, plus 1/6 post.

BRAND NEW METERS.—2 1/2 in. barrel circular flush panel meter. Moving Coil 1 mA. at 22/6. 100 micro-amp at 42/6. 200 mA. at 10/6. Ditto Moving Iron 15 volts 50 cycles at 8/6. 2 in. square panel meter. Moving Coil 20 volt at 7/6. 150 mA. at 7/6; 5 mA. at 7/6; 500 mA. thermo-couple at 5/-.

VALVE BARGAINS.—Brand New boxed EL50 heavy duty output pentode 6.3 v. 8.8 watts. at 7/6. 1193, same as 6J5 with top grid and anode at 6 for 10/6, post paid.

HEAVY DUTY TWIN CIRCULAR POLYETHENE CASE for extension mains leads, etc. Price 7/6 per dozen yards or 100 yards for only 39/6, plus 3/6 carr.

ROVARY POWER UNIT TYPE 104.—Input 12 v., Output 230 volt 60 mA. and 6.3 v. at 2.5 amp. Fully filtered and smoothed and noise suppressed. Ideal for car radio, etc. Only 15/- each.

CRYSTALS
465 kc/s S.T.C. 1/2 in. pins suitable for crystal gates, I.F. checking, etc. Brand new, boxed, 10/- each.
200 kc/s American G.E.C. 1/2 in. pins suitable for crystal calibrators, etc. Brand new, boxed, 10/- each.

6 VOLT H.R.O. VIBRATOR PACK.—Gives 165 volts at 80 mA., smoothed D.C. Uses Malloy Vibrator 6X5G, heavy duty smoothing choke, etc. In black crackle, cabinet size 7 in. x 7 in. x 5 in. Brand new, only 29/6.

TRANSFORMER BARGAINS. Brand new ex-manufacturers' surplus drop through. Primary 220-250 volts 50 cps. Secondary 310-0-310 v. 70 mA. 6.3 v. at 3 v. at 2 a. Can be used with either 4 v. or 6.3 v. rectifier. Only 9/6, plus 1/6 post.

METAL RECTIFIERS.—Heavy duty Selenium 10 1/2 in. long with 3 1/2 in. square plates. Two are required for a full wave bridge giving 48 volts at 10 amps. Brand new and ridiculously cheap at only 57/6 per pair, plus 2/6 post. R.M. 4, 250 volts 250 mA. Only 12/6. R.M. 2, 4/3 each or 2 for 8/-, Selenium, 300 volts 100 mA. Brand new, ex-W.D., 6/9 each.

CHARLES BRITAIN (RADIO) LTD.
11, Upper Saint Martin's Lane, London, W.C.2. TEM 0545
Shop hours, 9-6 p.m. (9-1 p.m. Thursday)
—OPEN ALL DAY SATURDAY—

COPPER WIRE

COTTON COVERED			SILK COVERED		
S.W.G.	2 ozs.	4 ozs.	2 ozs.	4 ozs.	
16	1/4	2/-	1/4	2/-	
17	1/4	2/2	1/4	2/1	
18	1/4	2/2	1/4	2/1	
19	1/5	2/3	1/5	2/5	
20	1/5	2/4	1/7	2/8	
21	1/5	2/5	1/8	2/10	
22	1/6	2/6	1/9	3/-	
23	1/7	2/7	1/10	3/2	
24	1/7	2/8	1/10	3/2	
25	1/8	2/9	1/11	3/4	
26	1/9	2/11	2/-	3/6	
27	1/10	3/1	2/1	3/8	
28	1/10	3/2	2/2	3/10	
29	1/11	3/4	2/3	4/-	
30	2/-	3/6	2/4	4/2	
31	2/1	3/7	2/5	4/4	
32	2/1	3/8	2/7	4/8	
33	2/3	3/11	2/10	5/2	
34	2/4	4/2	2/11	5/4	
35	2/6	4/5	3/1	5/8	
36	2/7	4/8	3/3	6/-	
37	3/-	5/6	3/5	6/4	
38	3/4	6/2	3/7	6/8	
39	—	—	3/10	7/2	
40	4/6	8/-	4/1	7/8	

POSTAGE EXTRA.
POST ORDERS ONLY PLEASE.
Send stamp for comprehensive lists.

CRYSTAL SET INCORPORATING THE SILICON CRYSTAL VALVE
Adjustable Iron Coiled Coil.
RECEPTION GUARANTEED.
Polished wood cabinet 15/-, post 1/-
A REAL CRYSTAL SET, NOT A TOY
POST RADIO SUPPLIES
33 Bourne Gardens, London, E.4

BENSON'S BETTER BARGAINS

METERS — BRAND NEW — BOXED

FSD	Scale	Size	Type	Fit	Price
25.0-250/A		2 1/2 in.	MC Pr.Rd.	35/-	
300/A		3 1/2 in.	MC Fl.Rd.	35/-	
100.0/100/A	Blank	3 1/2 in.	MC Pr.Rd.	29/-	
100/A	2v. AC	3 1/2 in.	MC Fl.Rd.	22/6	
1mA	Various	3 1/2 in.	MC Fl.Rd.	17/6	
1mA	0-10	2 1/2 in.	MC Pr.Rd.	13/6	
2mA		2 1/2 in.	MC Pr.Rd.	12/6	
5mA		2 1/2 in.	MC Fl.Sq.	8/6	
5mA	Lines	2 1/2 in.	MC Fl.Sq.	5/6	
10mA		3 1/2 in.	MC Fl.Rd.	7/-	
10mA		4 1/2 in.	MC Fl.Rd.	20/-	
20mA	200A	3 1/2 in.	MC Fl.Rd.	7/-	
25mA	50A	3 1/2 in.	MC Fl.Rd.	7/-	
30mA		2 1/2 in.	MC Pr.Rd.	8/6	
40/120mA		2 1/2 in.	MC Fl.Sq.	8/6	
100mA	300mA	2 1/2 in.	MC Fl.Sq.	5/6	
100mA		3 1/2 in.	MC Fl.Rd.	7/-	
150mA		3 1/2 in.	MC Fl.Rd.	7/-	
150mA		2 1/2 in.	TC Fl.Sq.	7/-	
200mA		3 1/2 in.	MC Fl.Rd.	7/-	
250mA		3 1/2 in.	MC Fl.Rd.	7/-	
500mA		3 1/2 in.	MC Fl.Rd.	7/-	
1A		2 1/2 in.	TC Pr.Rd.	7/-	
1A		2 1/2 in.	MC Pr.Rd.	7/-	
2.5A		2 1/2 in.	MC Pr.Rd.	5/-	
3A		7 in.	MC Fl.Rd.	25/-	
3A		2 1/2 in.	TC Pr.Rd.	8/-	
4 or 8A		2 1/2 in.	MI Pr.Rd.	8/-	
8A		2 1/2 in.	MC Fl.Sq.	19/-	
20A		3 1/2 in.	MI Fl.Rd.	8/6	
20.0-20A		2 1/2 in.	MC Fl.Sq.	8/6	
30A		2 1/2 in.	MC Pr.Rd.	7/-	
50A		6 in.	MI Pr.Met.	30/-	
40-60 (230v.)		8 in.	AC Pr.Met.	80/-	
2v. AC		3 1/2 in.	MC Fl.Rd.	22/6	
15v.		3 1/2 in.	MI Fl.Rd.	8/-	
10v.		3 1/2 in.	MI Fl.Rd.	8/-	
15.0, 15v.		3 1/2 in.	MC Fl.Rd.	7/-	
20v.		2 1/2 in.	MC Fl.Sq.	8/-	
20v.		3 1/2 in.	MI Fl.Rd.	8/-	

List and enquiries, S.A.E. please! Terms: Cash with order. Postage extra. Immediate despatch

Callers and Post.
W. A. BENSON (PW),
308, Bathbone Road,
Liverpool 19.
STO 1604

Callers only
SUPERRADIO
(W'chapel), LTD.
118 Whitechapel,
Liverpool 1. ROY 1130

COMMUNICATIONS RECEIVER R.1155. The famous ex-Bomber Command Receiver known the world over to be supreme in its class. Covers 5-wave ranges 18.5-7.5 mc/s. 7.5-3.0 mc/s. 1,500-600 kc/s. 500-200 kc/s. 200-75 kc/s. and is easily and simply adapted for normal mains use. Full details being supplied. Aerial tested before despatch these are BRAND NEW IN MAKER'S ORIGINAL TRANSIST CASES. ONLY £11/19/6.

A.C. MAINS POWER PACK OUTPUT STAGE.—In black metal case enabling the receiver to be operated immediately without any modification, can be supplied as follows—Less Speaker, £24 10/-; with 6 1/2 in. P.M. Speaker, £25 10/-.

DEDUCT 10/- ON PURCHASING RECEIVER & POWER PACK TOGETHER. Please add carriage costs of 10/6 for Receiver and 6/- for Power Pack.

TRANSFORMERS.—Manufactured to our specifications and fully guaranteed Normal primaries, 425v.-0-425 v. 250 ma., 4.3 v. 4 a., 6.3 v. 4 a., 5 v. 3 a. ONLY 50/-; 430 v.-0-330 v. 160 ma., 6.3 v. 6 a., 6.3 v. 3 a., 5 v. 3 a. ONLY 42/6; 250 v.-0-250 v. 100 ma., 6.3 v. 6 a. ONLY 32/6; 350 v.-0-350 v. 150 ma., 6.3 v. 5 a., 0-4.5 v. 3 a. ONLY 32/6. The above are fully shrouded upright mounting. 5.5 kv. E.H.T. with 2 windings of 2 v. 1 a. ONLY 72/6; 7 kv. E.H.T. with 4 v. a. ONLY 82/6. PLEASE ADD 2/- POSTAGE FOR EACH TRANSFORMER.

CRYSTALS.—British Standard 2-pin 500 kc/s 15/-; Miniature 200 kc/s and 465 kc/s 10/- each.

6 VOLT VIBRATOR PACKS.—Made by H.R.O. of America. Output 165 v. 80 ma., 6.3 v. 3 a. Contains 6X5 rectifier and full smoothing. Self contained in black crackled cabinet size 7 in. x 7 1/2 in. x 6 in. ONLY 29/6 (postage, etc., 2/-).

AMERICAN ROTARY TRANSFORMERS.—12 v. D.C. input, output 255 v. 65 ma. A. Useful for car radio, or tuning electric shaver from car battery, etc. ONLY 22/6.

VACUUM PUMPS.—These are ex-R.A.F. rotary vane type and are ideal for handymen and model makers, etc. New and Unused. ONLY 22/6 (postage, etc., 2/-).

INDICATOR UNITS, TYPE 6.—Contain VCR97 Tube with mu-metal screen, 4 valves: EF50 and 2 of EB34. NEW CONDITION. ONLY 59/6 (carriage, etc., 7/6).

"PYE"—45 Mcs. I.F. Strips. The strip that is ready made for the London Vision Channel. Complete with 6 valves, EF50 and 4 of 1E450. BRAND NEW. ONLY 70/-.

R.F. UNITS TYPE 26 & 27.—For use with the R1355 or any receiver with a 6.3 v. supply. These are the variable tuning units which use 2 valves EF54, and 1 of EC52. Type 26 covers 65-50 Mcs. (5-6 metres) and Type 27 covers 85-65 Mcs. (3.5-5.0 metres). Complete with valves and BRAND NEW IN MAKER'S CARTONS. ONLY 35/- each.

MODEL MAKER'S MOTOR.—Only 2 1/2 in. long and 1 1/2 in. diameter with 1 1/2 in. long spindle. Will operate from as low as 43 volt dry battery. ONLY 10/6.

CHASSIS OF INDICATOR 233.—Contains VCR97 C.B.T. holder, 11 valve-holders, resistors, condensers, etc. etc. BRAND NEW ONLY 10/- (carriage, etc., 5/-).

METERS

F.S.D. SIZE AND TYPE	PRICE
1 mA. D.C. 2 1/2 in. Flush square	15/-
1 .. D.C. 2 1/2 in. Flush circular	22/6
1 .. D.C. 2 1/2 in. Desk type	25/-
5 .. D.C. 2 in. Flush square	7/6
100 .. D.C. 2 1/2 in. Flush circular	12/6
150 .. D.C. 2 in. Flush square	7/6
500 .. thermo 2 in. Flush square	5/-
500 .. thermo 2 in. Proj. circular	5/-
20 amps D.C. 2 in. Proj. circular	7/6
40 amps D.C. 2 in. Proj. circular	7/6
200-300 amp D.C. Car type meter	35/-
15 volts A.C. 2 1/2 in. Flush, circ., mov. iron 8/6	

All meters Brand New in Maker's Cartons
Amounts given for carriage refer to inland only.

U.E.I. CORPORATION,
133, Gray's Inn Road, London, W.C.1
(Phone: TERMINUS 9387)
(Open until 11 a.m. Saturdays. We are 2 mins. from High Holborn (Chancery Lane Station) and 5 mins. by bus from King's Cross.)

Programme Pointers



Oscar Wilde Centenary

THE centenary of the birth of Oscar Wilde was honoured by an excellent production of his "An Ideal Husband," which probably ranks a long way behind "The Importance of Being Earnest" as second of his four major dramatic works. The play itself is based on a clever enough, if too period, a story and it glitters with some of the master's choicest epigrams. "To love oneself is to start a lifelong romance," and "I always pass on good advice. It's the only thing to do with it. It's never any use to anyone," are two that remained in my memory. But the situations, particularly the bracelet and the eavesdropping ones, are contrived with frightful artificiality and the play lacks the spontaneity and virtuosity of the immortal "Importance," in which the continuity of thought and purpose never flag for an instant.

The piece was brilliantly handled and given all the necessary period brashness and cynicism by Janet Burnell, Ursula Howells, Dorothy Primrose, Malcolm Keen, Monica Gray, Christine Bocca, Michael Ingrams, Richard Bebb and others.

Other Plays

The implications of our reactions to learning that our father had been hanged for murder formed the basis of a most interesting play, "A Question of Fact," by Wynyard Browne, in *Saturday Night Theatre*. Angela Baddeley played the part of the mother who reveals the secret, and another as well, with great éclat and verve. This was the role in which Gladys Cooper was so successful in the stage production last winter. Patrick Barr brought out all the horror and pathos of his ancestry and Joan Hart backed him up nobly as his wife.

The *Curtain Up* series of thrillers were of varying vintages. Best of the lot, I thought, was "The Brothers" by Rex Reinitz. At least it had a purpose, in addition to setting out to merely excite. The compassion of Stephen Wayne, a police officer, for his worse than ne'er-do-well brother Larry gave the otherwise fairly normal thriller a moral tone and a quality absent from most plays of this genre. The scamp Larry was engagingly played by Richard Bebb and his higher-minded brother excellently handled by Hamilton Dyce. Sheila Burrell made much of an undeservingly forgiven wife.

"Fever Bark" was a laborious effort at telling, in documentary form, the story of the discovery and development of quinine. There didn't seem to be anything like enough interesting material to hold one for fifty-five minutes. I hope we are not given a similar type of programme dealing with castor oil!

As Forecast

The 8 a.m. weather forecast one Monday contained the following sentence: "Only a moderate drying day can be expected." This seems to me to be the most practical and sensible justification I have ever

Our Critic, Maurice Reeve, Reviews Some Recent Programmes

heard contained in one of these plaguy nuisances. Also, on that particular morning, it was exactly correct. But, on second thoughts, I wonder if the British housewife was being assisted in what must be one of her most arduous duties? Or did it relate to the harvest or something quite different? Anyhow; be that as it may, if she did take it as being for her especial benefit, she must have found it very useful.

"Any Answers" is Freddy Grisewood's postscript to his "Any Questions" programme and seems to be the substitute, half as long, to "Dear Sir." In it, listeners send in their comments on what they have heard the previous Friday. Is your answer really necessary?

Gilbert Harding has commenced a bi-weekly series of 15-minute interviews with famous people who would seem to be "in town to-night," though, in reality, interviewer and subject may be many miles apart. The BBC welcomes suggestions for interviewees. The first two I heard were very urbane and pleasant. Mr. Harding is, of course, a past-master at this sort of thing, and given suitable subjects for interviewing the new feature should prove a popular success.

A Question of Time

An interesting, if saddening, reflection on the relative estimation in which the public holds the various avocations and pursuits of mankind was recently provided by the time allotted to two consecutive items. I say "in which the public holds" advisedly because, although it was not consulted beforehand as to how much time it would like given to each of the subjects, any more than it was asked whether it even wanted the subjects at all, the BBC, having chosen them, was doubtless perfectly correct in apportioning to each the duration it did.

The two items were, first, 15 minutes to "A Great Management," the story of the Vedrenne-Barker management at the Court Theatre, London, commencing in 1904, followed by 45 minutes of "A Man and his Music," a personal tribute to the late Carroll Gibbons.

Now, the Vedrenne-Barker era at the Court was probably the most famous managerial enterprise in the history of the British theatre. Amongst its achievements were the first productions of some of Shaw's finest works. In any case, the theatre is a not unimportant part of our national life affecting our prestige and standing among the nations. On the other hand, Mr. Carroll Gibbons and his music was, well, just Mr. Carroll Gibbons and his music. What would you do, chums?

50th Anniversary of the Invention of the Thermionic Valve

SIR AMBROSE FLEMING, whose birthday anniversary was on November 28th, reporting on his experiments in a personal letter to Marconi, remarked in conclusion, "I have not mentioned this to anyone yet as it may become very useful." Just how useful it was to become the future had yet to reveal.

His immediate objective had been to find a more sensitive and reliable method whereby the high-frequency alternations of the feeble current in a receiving aerial could be rectified, or caused to flow in one direction only, so that the current might be capable of operating instruments such as an ordinary galvanometer, whereby the strength of the signal could be measured with accuracy.

Recalling the results of experiments which he had made some years before when associated with the original Edison Electric Light Co. of London, Fleming saw that in them lay a possible solution of his problem. These investigations had concerned the passage of electric currents through rarefied gases. It had been noted that if two electrodes were separated in a partial vacuum and one of them such as a carbon filament was made hot, current would flow across the space between them provided that the potential of the cold electrode was made positive in relation to that of the hot one. If the polarities of the electrodes were reversed no ordinary voltage would cause any current to flow at all.

Nothing was known of electrons in those days, and it had been assumed that the current was conveyed by particles of negatively charged carbon thrown off from the incandescent filament. In 1899, however, Sir J. J. Thompson had proved that it was, in fact, particles of "disembodied electricity" unassociated with matter in atomic form and far smaller than any atoms.

Fleming connected up one of his old experimental bulbs, with its hot and cold electrodes, in a receiver circuit using a mirror galvanometer as an indicator. At the other side of the room he pressed the key of his little spark transmitter and the spot of light reflected from the mirror of his galvanometer leapt across the scale to proclaim the immediate success of the world's first wireless valve. That was in November, 1904.

Biographical Notes

Sir Ambrose Fleming, F.R.S., was born near Lancaster on November 29th, 1849. He was brought to London at the age of five years. At 14 he went to University College School, which was then conducted in a wing of the College in Gower Street. Decided on engineering as a career, at age of 17, and worked for B.Sc. degree in the University of


London by private evening study while helping to maintain himself by taking a post as clerk on the Stock Exchange. He was one of the only two in the

First Class in the degree list of 1870, when not quite 21 years old. Took post of Science Master at Rossall College, and, after 18 months, entered the Science Schools just established in South Kensington, studying for three years under Dr. Frankland. In 1881 he


was appointed Professor of Physics and Mathematics at University College, Nottingham, soon, however taking a post as scientific adviser to the Edison Electric Light Company.

He took a leading part in the design of the powerful transmitting equipment at Poldhu, Cornwall, which Marconi was preparing for his successful attempt to span the Atlantic by wireless in 1901. He continued to lecture until nearly 90 years of age.

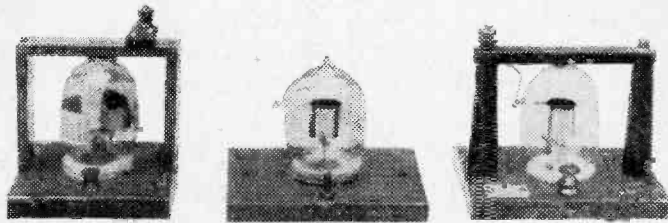He died in his 96th year on April 18th, 1945, at Sidmouth, where he had spent in retirement the last few years of his intensely active life.




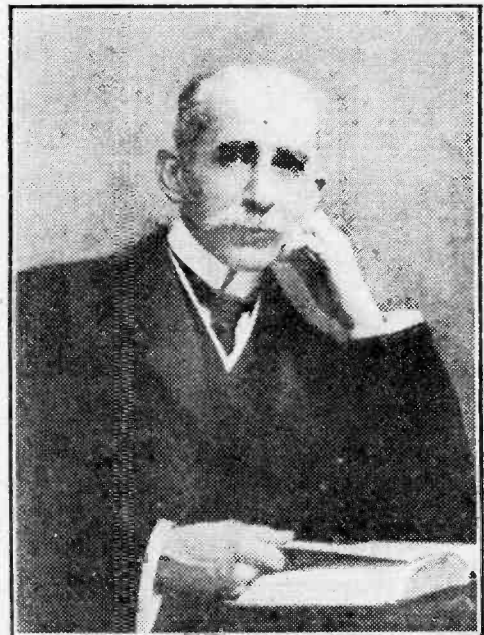Some early production models of the Fleming diode, forerunner of the valve of to-day.



Sir John Ambrose Fleming, M.A., D.Sc., F.R.S.

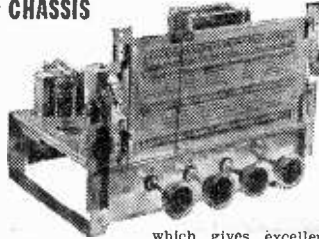THREE COMPLETELY ASSEMBLED "ALL-WAVE" SUPERHET CHASSIS




which gives excellent clarity of speech and music on both gram, and radio, making them the ideal replacement chassis for that "old Radiogram," etc.

- Model B3. A 5-valve 3 waveband receiver. £12.12.0. (Plus 7/6 carr. and ins.) H.P. Terms £3.4.0 Dep. and 12 Months at 17/8
- Model B.3.P.P. A 6-valve 3 waveband Receiver with PUSH-PULL OUTPUT. £15.15.0. (Plus 7/6 carr. and ins.) H.P. Terms £3.19.0 Dep. 12 Months at £1.2.2.
- Model B.3.P.P./R.F. A 7-valve 3 waveband Receiver, incorporating an R.F. stage with PUSH-PULL OUTPUT. £18.18.0 (Plus 7/6 carr. and ins.) H.P. Terms £4.13.0 Dep. 12 Months at £1.6.9.

Modernise your old Radiogram

The three receivers are for operation on A.C. mains, and employ the very latest miniature valves. They are designed to the most modern specification, great attention having been given to the quality of reproduction

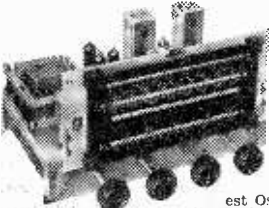A BULK PURCHASE ENABLES US TO OFFER THIS "PUSH-PULL" 7-VALVE SUPERHET RECEIVER




for only £12.19.6. (Plus 7/6 carr. and ins.) H.P. Terms £3.4.6 Dep. 12 Months at 18/4.

Model AW3-7 Receivers are made by a well-known manufacturer and incorporate the latest Osram Valve line-up, having two Nuis's in Push-Pull for approx. 10 watts output. They cover 3 wavebands and are for operation on A.C. mains. They make an excellent replacement radio-gram chassis. **THEY ARE BRAND NEW AND FULLY GUARANTEED.**

Send S.A.E. for our Illustrated and Descriptive leaflet of various Radio Radiogram Chassis, Autochange Units, Amplifiers, etc.

TWO COMPLETE HI-FI AMPLIFIER KITS

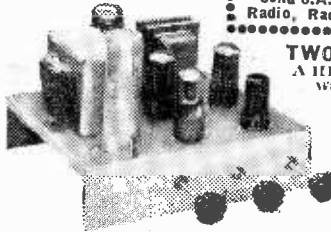

A HIGH QUALITY 8-10 watt AMPLIFIER

THE IDEAL AMPLIFIER FOR GENERAL HOME USE AND FOR SMALL HALLS, etc.

PRICE OF COMPLETE KIT, INCLUDING VALVES AND DRILLED CHASSIS £7.10.0. (Plus 2/6 carr. and ins.) **WE WILL SUPPLY IT COMPLETELY BUILT FOR £9.10.0** (Plus 5/- carr. and ins.) Designed for high quality reproduction up to an output level of 10 watts, having 6V6's in Push-Pull and incorporating negative feedback. Suitable for use with all types of Pick-ups and most types of microphones and the output transformer provides for use of 3 and 15 ohm speakers. **BRIEF FEATURES:**

- Valve line-up 6J5, 6SN7, 5Z4, with 6V6's in push-pull.
- First class reproduction of radio (where a tuning unit is used) and record playing.
- Separate Bass Boost and Treble controls provide an excellent range of frequency control.

The **ASSEMBLY MANUAL** is available for 1/- and includes detailed layouts and component Price List.


A 12-Watt "HIGH FIDELITY" Push-Pull AMPLIFIER

Comprising a Main Amplifier Chassis and a Remote Control Pre-Amplifier-Tone Control Unit. The remote control unit measures only 7in. x 4in. x 2in. and contains four controls, being: Bass-Treble, Volume and a Radio, Gram, Microphone Switch control. It incorporates its own feedback circuit on the Bass Channel. Loop negative feedback is employed on the Main Amplifier which has a valve line up of 6J5-6N7-5U4 with two 6X25's in push-pull and 6J5 and 6SN7 are used in the remote control unit. **THE COMPLETE UNIT ASSEMBLED AND READY FOR USE £17.0.0.** (Carr. and Ins. 3/- extra.) H.P. Terms £4.5.0 Dep. 12 Months at £1.3.11. This Amplifier compares well with the Williamson and similar designs at a fraction of their cost. The complete set of assembly instructions are available for 2/-.



THE COMPLETE KIT IS AVAILABLE FOR £14.0.0. (Carr. and ins. 3/- extra.)

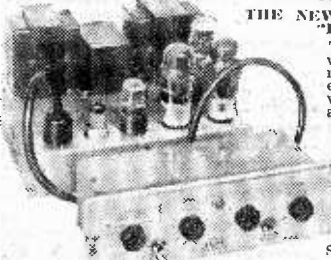THE NEW "LEAK" TL10 AMPLIFIER AND "POINT ONE" PRE-AMPLIFIER



This amplifier has a maximum output of 10 watts and maintains in every respect the world renowned LEAK reputation for precision engineering; fine appearance and fastidious wiring. The Pre-Amplifier will operate from any make or type of pick-up.

- (a) **THE COMPLETE AMPLIFIER with Pre-Amplifier** £28.7.0 or £7.2.0 Dep. and 12 Months at £2.
- (b) **THE TL10 MAIN AMPLIFIER** only £17.17.0 or £4.7.0 Deposit and 12 Months at £1.5.4.
- (c) **The "POINT-ONE" PRE-AMPLIFIER** only £10.10.0 or £2.12.6 Dep. and 12 Months at 15/-.

S.A.E. FOR DESCRIPTIVE LEAFLET.

WE HAVE IN STOCK THE

DENCO F.M. FEEDER UNIT consisting of a 5 valve Superhet design incorporating R.F. (6AM6) and F/C (12AH8) Stages followed by Two 1.Fs (6BA6's) and Ratio Discriminator, 6 AL 5, the coverage provided being 80-100 Mcs.

THE COMPLETE KIT, including VALVES and DRILLED CHASSIS available for £6.13.6. (Plus 4/- carr. and ins.)

COMPLETELY ASSEMBLED CHASSIS, READY FOR USE, ALIGNED AND TUNED, £8.17.8. (Plus 6/- carr. and ins.)

Suitable for use with any type of High Fidelity Amplifier. Descriptive manual, including circuit and component layout, etc. available for 1/6.




A GENUINE SPECIAL OFFER!

This **THREE SPEED AUTOCHANGER** is by a famous manufacturer and is offered for **£11.10.0.** (Plus 7/6 carr. and ins.) Normal price £16.10.0. H.P. Terms £2.17.6 Dep. and 12 months at 16/4.

- Complete with High Fidelity Crystal "Turnover" Head which incorporates separate stylus for L.P. and 78 r.p.m. records.
- Will autochange on 7in., 10in. and 12in. records, not inter-mixed.
- Brand New in Maker's Cartons, complete with mounting instructions. **WE ALSO HAVE "MIXER" UNITS**

The "SUPER-SIX" A DESIGN FOR HOME CONSTRUCTORS

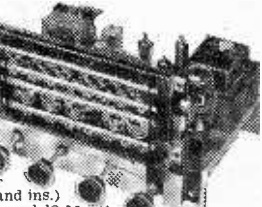A compact and highly efficient superhet Radiogram chassis of outstanding quality for operation on A.C. mains. **YOU CAN BUILD IT FOR £10.7.6.** We will supply it assembled and **READY FOR USE** for £13.13.0. (Plus 7/6 carr. and ins.) H.P. Terms £3.10.6 Dep. and 12 Months at 19/-.



This Receiver incorporates the new B.V.A. miniature valve line-up, and is designed to the very latest specification. Great attention has been paid to the quality of the reproduction of both Radio reception and Record playing, and excellent clarity of speech and music is obtained. ● Covers 3 wavebands. ● Employs 6 valves having PUSH-PULL for 5-6 watts output. ● A 4 position Tone Control operates on both Radio and Gram. **THE INSTRUCTION & ASSEMBLY MANUAL** is available for 2/-.

LYONS RADIO LTD.

3, GOLDHAWK ROAD, Dept. M.P.,
SHEPHERDS BUSH, LONDON, W.12.

Telephone: SHEPHERDS Bush 1729

TELEPHONE SETS TYPE D MK. V Housed in metal boxes 10 x 6 x 4 1/2 in. with hand set, similar to the standard P/O type, loud call buzzer and press key, extra ear-phone, etc. Two 1.5 v. cells are required for operation. Ideal for 2-way communication (more with suitable switching) in the Home, Factory, Office, etc. In good condition and working order. PRICE per instrument 32/6, post 2/6, carriage for 2, 4/3.

2-RANGE POCKET VOLTMETERS. Moving coil. 345 ohms per volt. 2 1/2 in. dia. Calibrated 0/15v. and 0/250 v. D.C. Fitted with test lead and prods. An accurate meter, as new in case. PRICE ONLY 12/6, post 1/3.

WAVEMETERS TYPE W.1239. Frequency coverage 39 to 51 Mc/s. Rectifier type employing one each of the following valves: VR22, 6J5, V1103, 6X5. The tuning control is fitted with a Muirhead slow-motion drive with a calibrated white escutcheon and vernier scale. Contains its own built-in power pack for A.C. mains operation from 200/250 v. 50 cps. Housed in copper-lined wooden instrument cases 15 1/2 x 10 x 9 1/2 in. with hinged lid. A useful addition to any Test Room or Laboratory or as an inexpensive basis for constructing other test gear. Condition is as new and unused, supplied in maker's transit case. PRICE ONLY 69/6, carriage 6/6.

HEATER STRIPS. Metal clad, black heat, size 22 1/2 x 3 1/2 in. Rated at 230 v. 475 watts. With fixing hole each end and two connecting terminals at the same end. PRICE 4/6 each. Please add postage: 1/3 up to 6; 7 to 12, 2/6.



Don't scrap that failing car battery or radio cell. Try Renewbat conditioner. Works like a charm. Simple and safe to use. Full instructions. Car size 3/-, p.p. 6d.; Radio size 1/9.

CHAMPION PRODUCTS,
43, Uplands Way, London, N.21.
Phone: LAB 4457

Introducing the:—

TYANA TRIPLE THREE

MAKE SOLDERING
A PLEASURE

SMALL
SOLDERING IRON
Complete with detachable
BENCH STAND 19/6

The smallest high-power
soldering iron. Length
only 8 1/2"; adjustable long
bit dia. 3/16"; mains vol-
tages 100/110, 200/220,
230/250.

The "STANDARD"
Popular Soldering Iron
now reduced to 14/11.
Replacement Elements and
Bits for both types always
available.

KENROY LIMITED
152/297 UPPER ST.,
ISLINGTON, LONDON,
N.1.

Telephone:
Canonbury 4905-4663

Rea. Design
No. 1867B04

20

CIRCUITS
for 2/6 only

Our **Supa-Handbook**, "The Home Constructor" with its supplements (68 pages altogether) now incorporates

- ***20 CIRCUITS**—Superhets, T.R.F. Test Equipment, Feeder Units, etc.
- ***ST PERNETS**—Full constructional details, sup-simplified diagrams for building superhets.
- ***COIL-PAK**—Full constructional details for building a superhet pack.
- ***CAR RADIO**—Full constructional details.
- ***RADIO GUN**—Pages of information, Resistance Colour Code, Formulae, and "know-how."
- ***RADIO CONTROL**—Supplement with theoretical, sup-simplified diagrams.
- ***INFORMATION LETTERS**—The latest issues of our popular Information Letters.
- ***CATALOGUE**—Profusely illustrated catalogue and price list.

YOU CAN'T GET BETTER VALUE! IT'S TOPS!
"The most helpful book in the Trade."

And, of course, our famous iron-volute at 3/- ea. 10-30, 16-50, 30-75, 75-200, 190-550, 800-2,000 metres. Aerial H.F. or Osc.

SUPACOILS (Dept. P.1)
21, Markhouse Road, London, E.17

ALFRED PADGETT

40 MEADOW LANE, LEEDS, 11

(Established 20 years)

SELENIUM METAL RECTIFIERS.—Small in size. 250 volts 100 mA. Brand new. 6/6. 50/- per doz.

SCOPE ALL-UNIT MADE. BC229 Tube Unit complete with 3BP1 Tube. 2K2, 6X5, 6SN7S, 6H6, 6Q6. £312/6 carriage free.

F.W. BRIDGE TYPE. 612 volts at 1 Amp. 4/9. Post Free. 40/- per doz.
STEP-DOWN TRANSFORMER. 200-250 50 cycles. Sec. Winding: All at 2 amps. 30, 24, 20, 18, 15, 14, 12, 10, 9, 8, 6, 5, 4, 3 volts. Worth Double. 12 months guarantee. 17/- Post Paid.

POTENTIOMETERS.—Less switch. Box of 1 doz. assorted values (our selection). 5/6 per doz. Post Free.

SINGLE HEAD PHONES.—Low resistance. 1/6. Post Free.

NEW MAINS TRANSFORMERS.—12 mths guarantee. Primary 200-250 50 cycles. Sec. 350 volts at 80 mA. 6.3 at 4 amps. 5 volts at 2 amps. Electrostatic screened. Will mount in any position. 17/- Post Paid.

WAR SURPLUS VALVES.—Fully guaranteed. All Post Free. 654, 1/9; 6K7, 4/-; 6K7 Metal, 6/8; 6V6GT, 6/6; VR91, 3/6; VR65, 1/6; VR58, 4/-; VR54, 1/3; 6SK7 Metal, 6/6; 6H6 Metal, 2/6; 307 Yankee, 8/-; 8D2, 1/3; VU111, 2/-; VS110 3/6.

MIXED RADIO PANELS.—Very popular. Full of resistors and condensers 4/6. Post Free. Not to be missed.

WAXLEY SWITCHES.—Two-pole 2-way One bank. Spindle length fin. 1/6. Post Paid.

TYPE 1125 SETS.—Complete with two 8D2 valves. New. 6/8. Post 2/4.

MULTIMETER KITS. 2 1/2 in. M/C meter. Reads D.C. volts 3-30-150-300/600 mA. (4-50 ohms 0-5-000. With Bakelite Case. 27/6.

6V. VIBRATOR PACKS. Self contained in Steel Box. Output 150 v. 30 mA. 22/6. Ideal for Battery Radios.

TYPE 6C "SCOPE" UNIT with VCR 138/3 1/2 in. C.R. Tube, etc., and Conversion Circuit. 58/6.

FISHING ROD AERIALS. 12ft., Set 3. 7/6. Mounting Base, 3/6.

0.5 AMPMETERS, 2 1/2 in. square M/C. 11/-.

GERMANIUM DIODES, 3/9.

FREQUENCY CRYSTALS, 9,100 and 4,500 Kc., 10/6; 4,860, 4,800, 2,400, 594, 561, 560, 559 Kc. 6/6. 4 in. Space Pins.

SELENIUM RECTIFIERS. F.W. 6 or 12 v. 4 A. 22/6; 6 A. 30/-; 3 A. 14/6; 100 mA. 3/6; 1 A. 8/6; 2 1/2 A. 30/-; 250 v. 100 mA. H.W., 9/-; 250 v. 275 mA. 17/6; 250 v. 60 mA. 6/6.

TRANSFORMERS. 200-240 volts. Tapped 3-4-5-6-8-9-10-12-15-18-20-24 and 30 volts at 2 A. 21/6. Tapped 17-11-5 volts 5 A. 22/6; Tapped 17-11-5 volt 11 A. 16/6; 6.3v. 21 A. 8/6. One year guarantee.

M/C MICROPHONES AND TRANSFORMERS. 15/6.

EX-W.D. PHONES. Low Resistance, 9/6.

NEW OAK 6v. 4-pin Vibrators. 10/6.

MORSE KEYS, 3/-; BUZZERS, 3/-.

12.24V. BLOWER MOTORS, 14/6. A.C./D.C.

CARBON TWIST DIALS. Sets of 6. 1/16th to 1 or 1/16th to 3/16th. 3/6.

U.H.F. AERIALS. 180-200 Mc/s. covering band, complete with case. 6/6.

OVERLOAD SWITCHES. Breaks at 1 Amp. 3/6.

TR1196. Transmitter Section. New and complete. 4.6/6.8 Mc/s. Easily converted. Less valves. 15/-; with valves. £2.

Throat Microphones with cord. 4/-.

ALL POST PAID IN U.K.

THE RADIO & ELECTRICAL MART

253b, Portobello Road, London, W.11
Phone: Park 6026.

TELETRON SUPER INDUCTOR COILS

Originators of Type HAX selective Xtal diode coil, as Radio unit

in Tape and quality

Amplifiers, 3/- ea. Dual

wave TRF coils (illus-

trated), matched pair, 7/-.

FERRITE ROD Aerials. MW.

8/9; Dual wave, 12/9. I.C.T.O.

Coils, I.F.T.'s, etc. Stamp for list

and circuits. The Teletron

Co., Ltd., 266, Nightingale

Rd., London, N.9.

HOW 2527



The OSRAM NINE - ONE - TWO

Amplifier Instruction
Book and Highest
Quality Components

Available from

COVENTRY RADIO
189, Dunstable Road,
LUTON. Phone 2677

Price 3/6, plus 3d. postage.

also

Our 1954-5
Component Catalogue at 1/-

Open to Discussion



Amplifier Design

SIR,—I hope that Mr. R. Hindle will deal fully with "Cathode Follower" Output before completing his series of articles.

After trying this and doing my best to compare it with the very latest speakers and amplifiers, I think it is *still* unsurpassed for quality.

Example: A Williamson Amplifier, using 6V6 output valves in pull-push (instead of KT66) and with 250 volts (instead of 450) circuit unchanged. Considerable volume, probably 6 to 8 watts.

I cut the cathode connections and took one to each end of an 84s. size sectionally-wound output transformer. Heaters to separate mains transformer. Anodes to H.T. provided with a pair each of resistors (33K and 10K were used). Centre of output transformer to earth. Speaker 15 ohms. (No alterations to output transformer.)

Violins sound like violins—not tin whistles: and so on. Speaker, by the way, was the fairly new one—"Cambric" cone, 10in., price about £4.

Earlier experiment with a small amplifier (2 6J5's and a 6V6) led me to think that provided the output transformer primary provides suitable cathode resistance, very excellent quality can be obtained without unduly expensive equipment. I use no tone control, and do not pen-in my speakers, but do mount on a baffle.

I may say that when the pull-push amplifier was changed over to cathode output, the first trial occurred on a Sunday evening when Mr. Charles Mackerras was conducting the BBC Concert Orchestra. His orchestra played, as we then thought, so magnificently that we wanted to sit down and write our appreciation. The next Sunday I had changed the amplifier back to ordinary anode output and—believe it or not—the contrast was so considerable when compared with the memory of the previous superb performance that I had to switch off and cut the cathodes again, reverting to cathode output. There is nothing to touch it yet for violins. But, the volume must be kept down. Only up to about 2 watts from a 10 watt amplifier; and with a small amplifier, which can sound very beautiful, the volume must be kept well down to perhaps a ¼ watt. The clarity, however, is amazing. Using the superhet part of a 17-year-old eight-valver (output removed) the reproduction was even clearer (if possible) than anything I have heard using a crystal detector, and seemed to be of better quality, particularly with violins, but, of course, the "Cambric" (is it?) speaker would contribute to this. Earlier speakers had a "clouding" effect on reproduction, just as bass knobs on a volume control do—they should be called "smother" controls on most sets. (They certainly do not produce "bass," but only some electronic deepness, which is not "bass.")

You will appreciate, therefore, that I would like some knowledgeable observations on the use of "Cathode Follower" Output; and also would like to have the observations of transformer manufacturers on suitable transformers, and valves, and volts for use with certain transformers.

It is true that if the secondary (one side only) of an output transformer is connected to the cathode-earth of an output valve, the programme can be heard—but badly. I think that a suitable transformer could be cheaply produced, and the only question would be the resistance value of the wire used in the primary, to suit a certain anode voltage. Wide latitude is permissible in matching. 20 to 1 and 30 to 1 might perhaps give equally good results from same circuit, but I would not of course assert this.

Thanking you and PRACTICAL WIRELESS for many happy hours, and with final advice to those who may have read "Experimental Circuits" not to include the intervalve transformer as therein suggested, if they try this output.—O. G. KERSLAKE (Orpington).

A Variable H.T. Unit

SIR,—I was interested to read the above article by Mr. Stewart in the current issue but feel that he dismisses too lightly the certainty of short-circuiting windings of the transformer at several settings of the three switches, especially as the connections can easily be arranged to avoid it.

The problem of switching the three windings is merely that of arranging the circuit to give three

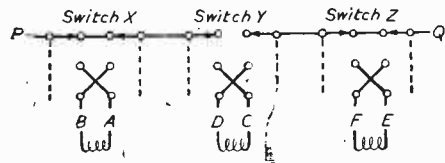


Fig. 1

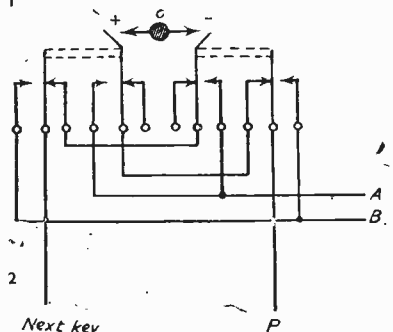


Fig. 2

Next key
Mr. d'Assis-Fonseca's switching suggestion.

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for receivers described in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of cover.

different connections to each, as follows:—

1. Winding bypassed.
2. Winding connected in circuit aiding.
3. Winding connected in circuit opposing.

With each winding switched in this manner the three switches are then connected in series. Fig. 1 shows the arrangement.

Many wafer switches bridge adjacent contacts during transit and this is undesirable with almost any switching arrangement. Using the switches specified in the above article a dead position can be left between working contacts, thus avoiding bridging the latter.

As an alternative to wafer switches any non-bridging three-position switch can be used, such as the Post Office lever-type telephone key found on some service equipment and readily available at the disposal stores. Two changeover spring sets are needed on each side of the key and Fig. 2 shows typical wiring of one such key.—H. D'ASSIS-FONSECA (New Barnet).

For the Deaf

SIR.—I thought that the following might perhaps suggest an article in your excellent publication which would interest quite a lot of your readers.

An elderly relative of mine is deaf, and, although wearing his National Health deaf aid, does not appear to be able to hear my Hi-Fi Radiogram very well. To avoid driving the rest of the household to distraction while he was staying with us, I plugged in a single 4,000 ohm earpiece in place of the audio amplifier into the R.F. feeder unit, holding the earpiece to his deaf aid with a rubber band, when he could hear very well indeed.

It seems to me, however, that this is a wasteful method and it might be possible to plug his D.A. earpiece into the R.F. feeder unit direct, with suitable matching arrangements.

Then came another snag. When he returned to his room where he has no radio (and his landlady does not approve of aerials or wires around the place) he feels lost without it and wants me to try to fix him up with a small set which he can take around with him. Cost is a real problem as he would need something very sensitive in this area to cover the medium Regional and long wave Light programmes. He has A.C. mains and it might be possible for him to use them. A superhet seems necessary as he would be fogged if he had to operate reaction to get a satisfactory sensitivity, and would most likely run it oscillating without knowing it.

Perhaps, at some future date, you will be able to include an article on these lines.

Also, we see plenty of 5- and 6-valve A.C. designs for receivers, but I feel that a good D.C./A.C. 6-valve job would be appreciated. The R.F. stage would give that little bit extra. We poor creatures on D.C., and positive earthed at that, are still tearing our hair and making unavailing requests to be changed over to

A.C. when we will be able to construct gear to your articles without limit.—E. W. LARK (Lowestoft).

Modern One-valver

SIR.—As a beginner in wireless construction, and as perhaps other beginners may be interested, I have built your "Modern One-valver" published in PRACTICAL WIRELESS, No. 552, of October, 1952, but used a miniature 1T4 valve in place of 1N5 as specified.

In addition, I have wound my own coil of 6 turns on a lin. tube for short-wave reception, and deleted the wave-change switching. The aerial coil was interwound on the same former using the same number of turns as for the tuning coil. Selectivity is good using the reaction just under oscillation point. The battery used is a Vidor L5504 of 69 volts H.T. with 1½ volts L.T.

One of the first stations received was Radio Sweden on about 30 metres, and plenty of other stations were available. This arrangement makes a good and inexpensive receiver for any beginner interested in short-wave working.—H. DRANSFIELD (Luton).

"What is Hi-fi?"

SIR.—Your contributor "Grid Current," in his article "What is Hi-fi?" in your December issue, is described as a critic. This he certainly is, and some of his comments are to the point, but I feel that he misses it when he describes the emphasis on the reproduction of the higher frequencies in present-day "High Fidelity" equipment as "curious" because, as he says, the similar extension of the lower frequency range in the past was not described as "High Fidelity."

The extension of the bass frequencies without a corresponding extension of the treble resulted in unbalanced reproduction which, despite the satisfaction of the enthusiasts in their technical achievement, did not give pleasing results. Present-day equipment extends both the bass and the treble ranges, giving a balanced reproduction which when properly used can give very pleasing and indeed inspiring results on music. Your contributor must not tar all Hi-fi enthusiasts with the same brush because some of those that he has come into contact with have been more interested in their achievement in extending their treble range than in maintaining a balance.

That this question of balance is of more importance than that of extended range is evident from the undoubted fact that many wireless receivers have a limited range falling off at perhaps 100 cycles in the bass and 6,000 in the treble, as compared with 50 to 12,000 or an even wider range with present Hi-fi equipment, and yet give very pleasing results. As he says, when the lower frequencies only were extended the result was "bangs, thumps and resonant booms."—S. T. PINDER (Weston-super-Mare).

P.S.—Had he said *over-emphasis* I would have agreed with him.

Editorial and Advertisement Offices :
 "Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Phone : Temple Bar 4363.
 Telegrams : Newnes, Rand, London.
 Registered at the G.P.O. for transmission by Canadian Magazine Post.

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Wireless." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, "Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. "Practical Wireless" incorporates "Amateur Wireless."

WEYRAD

**COILS
COIL PACKS
I.F. TRANSFORMERS
AND TV. COMPONENTS**

Among the very wide range of components which we produce, types will be found to meet the majority of requirements:

"H" TYPE COILS

Individual iron-cored, Aerial, H.F. Transformer, and Oscillator types providing continuous coverage from 12-2,000 metres.

"B" SERIES COIL PACKS

Miniature 3-band units covering Long, Medium and Short Wave bands or Medium and 2 Short Wave bands. Alternative tuning capacities 365 pF or 483 pF.

P.4. I.F. TRANSFORMERS

Improved types are being introduced to maintain even higher standards of performance and reliability. For frequencies in the range 460-470 kc/s. Dust-core Trimming.

ILLUSTRATED CATALOGUE - 6d.

**WEYMOUTH RADIO MFG. CO., LTD.,
CRESCENT STREET - WEYMOUTH.**

HOME RADIO OF MITCHAM

FOR ALL YOUR

**Recording Tapes and
Accessories**

**ALL FURY
FOUR PARTS
in stock.**

S.A.E. for LIST.

Ferrovoice 300'	8	6
Ferrovoice 1200'	22	6
New Scotch Boy 600'	21	0
New Scotch Boy 1200'	35	0
Emitape "88" 1200'	35	0
Ferrograph 1200'	45	0
Ferrograph 1750'	60	0
Agfa 1200'	37	6
Magneto BASF 850'	34	0
Magneto BASF 1200'	40	0
Gaveart 1200'	37	6

SPECIAL OFFER (LIMITED QUANTITY)
Well known make 1200' 22 6

SPARE SPOOLS
Scotch Boy 600' ... 3 6 Scotch Boy 1200' ... 4 6
Ferrograph 1200' ... 7 6 Ferrograph 1750' ... 9 6
Joining Compound, 4/6. Strip, 6/6.

MULLARD "5/10" AMPLIFIER and G.E.C. "912."
All parts including selection of transformers for these popular amplifiers are in stock.

"SOUNDMASTER" TAPE RECORDER. Constructional details, 6/6. All parts from stock.

S.A.E. for detailed price list of components for "5/10" and "912."

HOME RADIO OF MITCHAM, 187, London Road, Mitcham, SURREY.
MIT. 3282.

"We stock those DIFFICULT components."



TEST INSTRUMENTS

ON "NO INTEREST"
HIRE PURCHASE

All Taylor instruments are now available on the easiest of H.P. terms, including the new 3 month scheme with full refund of interest on completion of payment on due date. Alternatively, you can spread payment over 10 or 15 months.

Taylor
Model 120A



MULTIRANGE
UNIVERSAL
METER

A small versatile 19-range instrument of sturdy construction. Sensitivity 1,000 o.p.v. A.C. and D.C.

Ranges:

Volts D.C.	Volts A.C.	Milliamps D.C.	Resistance
0-.25	0-10'	0-1	0-2,000 ohms
0-10	0-50	0-10	0-200,000 ohms
0-50	0-250	0-50	These ranges can
0-250	0-500	0-500	be extended by
0-500	0-1,000		using external
0-1,000	0-2,500		battery.
0-2,500			

PRICE £9-10-0 PROMPT DELIVERY

HIRE PURCHASE TERMS

3 month Deposit £1/8/6d. and 3 monthly payments of £3/1/7d.
10 month Deposit 19/5d. and 10 monthly payments of 19/1d.
15 month Deposit 19/5d. and 15 monthly payments of 13/6d.

MORE TYPICAL HIRE PURCHASE TERMS

71A Multirange Meter.—3 month: Deposit £1/17/6d. and 3 monthly payments of £3/19/8d.; 10 months: Deposit £1/15/8d. and 10 monthly payments of £1/5/1d.; 15 months: Deposit £1/15/8d. and 15 monthly payments of 17/9d.
66A Signal Generator.—3 months: Deposit £3/3/0d. and 3 monthly payments of £6/13/11d.; 10 months: Deposit £2/2/3d. and 10 monthly payments of £2/2/3d.; 15 months: Deposit £2/2/3d. and 15 monthly payments of £1/9/11d.
45B Valve Tester.—3 months: Deposit £3/16/6d. and 3 monthly payments of £8/6/4d.; 10 months: Deposit £2/12/2d. and 10 monthly payments of £2/12/2d.; 15 months: Deposit £2/12/2d. and 15 monthly payments of £1/16/3d.

WRITE FOR CATALOGUE ILLUSTRATING
FULL RANGE OF TAYLOR TEST GEAR

TAYLOR ELECTRICAL INSTRUMENTS LTD.

Montrose Avenue, Slough, Bucks. Telephone: Slough 21381

The Mullard 5 Valve 10 Watt HIGH QUALITY AMPLIFIER

as demonstrated at the Radio Show
can now be heard at

Smith's
of
EDGWARE ROAD

Component Specialists since Broadcasting started.
who can supply all the parts for under £8
(less valves)

16 gauge aluminium chassis drilled and punched to
Mullard specification, 17/6.

Priced parts list available.

Full details are contained in a booklet by Mullard
technical experts, price 2/6 from

H. L. SMITH & CO. LTD.

287/289 Edgware Road, London, W.2.

Tel. : Paddington 5891

Hours 9 till 6 (Thursday, 1 o'clock)

Near Edgware Road Stations, Metropolitan and Bakerloo.

Enormous Purchase of "MEDRESCO" DEAF-AIDS

We have purchased from the Ministry of Supply thousands of "Medresco" Deaf Aids type OL10 as supplied by the Government under the National Health Act.

THE RADIO-MINDED AMATEUR will at once see the possibilities of converting this unit into many interesting devices such as:

Miniature Radio Receiver—Model Control Equipment
—Baby Alarm—Pre-Amplifier—Intercom Telephone,
etc., in addition to its original application.

WE OFFER the "Medresco" unit in perfect working order (every one checked by experts) complete with Crystal Microphone and incorporating three Miniature Valves at the Remarkably Low Price of 27/6. Postage 1/-.
Price without crystal microphone 23/6. Post 1/-.

ACCESSORIES

Miniature crystal earpiece, complete with lead and plug. 8/6;
Ever-Ready Batteries: 1.5 v. L.T. (Type D 19), 8d.; 30 v. H.T. (Type B119), 4/3; 45 v. H.T. (Type B199), for greater gain and output, 7/8.

See our wide range of surplus lines including:
Radio Components—Valves—Receivers, etc.—Transmitters
Instruments—Electrical Accessories.

APM INDICATOR UNITS, complete with 5CP1 tube, 26 valves and crystal, £8.15/0. Crg. & Pkg., 7/6. Send 10/- for Wireless World "TV. Oscilloscope Conversion," for above.

MOVING-COIL METERS. Centre-Zero. 2in. square, basic 750-3-750 microamps. (Originally air thermometer), 4/6.

IRON-CLAD METERS. Moving iron, projecting 6in. scale, 300 v. 50 cycles, 37/6. P. & P. 2/-.

It will pay you to pay a visit to

The Walk-around Shop

NOTE: Orders and Enquiries to Dept. 'P'

PROOPS BROS. LTD. LANGLEHAM 0141.
52, Tottenham Court Road, W.1.

OPEN ALL DAY SATURDAY Shop hours 9 a.m.-6 p.m.

Finest Soldering? Always specify ERSIN MULTICORE to be precise

Wherever precision soldering is essential, manufacturers, engineers and handymen rely on MULTICORE. There's a MULTICORE SOLDER just made for the job you have in hand. Here are some of them.

SIZE 1 CARTON

4 specifications for
radio enthusiasts.

5/-



**HANDYMAN'S
CARTON**
Sufficient for
200 average
joints.
6d.

TAPE SOLDER MELTS WITH A MATCH!

Real tin/lead solder
cores of Ersin
Flux. Needs no
soldering iron
or extra flux.

1/-
PER CARD



BIB WIRE STRIPPER AND CUTTER

The 3 in 1 tool. For stripping insulation
without nicking wire, cutting without leaving
rough edges and splitting
extruded flex. **3/6 EACH**

MANUFACTURERS ARE INVITED TO
WRITE FOR DETAILS OF BULK PACKS AT BULK PRICES

MULTICORE SOLDERS LTD.

MULTICORE WORKS, HEMEL HEMPSTEAD, HERTS (BOXMOOR 3636)

A MERRY CHRISTMAS

XMAS GIFT VALVE REDUCTION

ONE MONTH ONLY

SP61 2 x 2 2/- SP41, PEN220

EF50	4/-	6B4	4/-	D1	2/-	EAS0	2/-
EF36	4/-	EC52	5/-	EF39	7/-	EL22	7/-
EF54	5/-	EC54	4/-	6SK7	3/9	6J5	5/-
6H6(m)	3/6	6SH7(m)	5/-	6SA7	7/8	6SL7	8/-
6Q7	8/6	6V6	8/6	6SJ7	6/8	6K7	8/-
12A6	6/6	LR210	2/-	SG215	2/8	EBC33	7/6
ML5	5/-	PT15	7/-	6X5	7/6	6SN7	9/-
6K8	11/-	5U4G	8/6	5Z4	8/6	5Z3	8/6
35Z4	9/-	35L8	9/-	50L5	9/-	VT501	5/6
CV63	5/6	12J5	5/-	6AL5	6/-	6AM6	7/6
IT4	7/-	1R5	2/-	154	7/8	155	7/6
8S4	8/6	9Q4	8/6	3A4	7/-	U22	7/6
HL2	2/6	VP11	2/6	HL41	3/6	EB34	2/-
Pen.46	4/6	S130	5/6	807	6/-	VU111	3/-
6BW6	8/6	6AT6	7/6	9BW6	8/6	P2	6/-
CV201	8/-	CV187	9/-	CV288	8/-	CV287	8/-
VT62	9/-	10530	7/-	1Z40	13/-	VU508	9/-
CV19	30/-	VT98A	50/-	9001	4/-	9002	4/-
6J6	7/6	6AG5	7/-	2D21	12/-	1298A	6/-

CONDENSER ELECTROLYTIC. 450 volt wk'g B.E.C. 8 mfd. 2/-; 8+8 mfd. 3/9; 16+16 mfd. 4/6. 32+32.6 k. DUBILIER W.E. 500 volt 20 mfd. 3/-; 32 mfd. 5/-. BIAS 25/25 2/-; 50/50 2/- 25/12 volt 1/3.

POTENTIOMETERS.—All values to 2 meg. at 2/6. No. 38 Set 6mc.-9 mc. Trans/Rx. 2 volt Fil. with valves 38/- L/Valves at 15/-. New Valve holders, ass'd dozen, at 5/-.
RESISTORS & CONDENSERS.—Mixed, our selection generously assorted at £1 per 100.

VINER'S (Middlesbrough),
26, EAST STREET, MIDDLESBROUGH.
Telephone: MID 3418

SUPERIOR RADIO SUPPLIES

!!! CONSTRUCTORS !!!
OBTAIN "SUPERIOR RESULTS" WITH THESE RECEIVERS

THE SUPERIOR T.R.F. RECEIVER (BUILDING COST £7/5/-). Suitable M.C. Mains 220/240 volts. Medium and Long Wavebands. Attractive walnut veneered cabinet. Finished top contrasting colours. All brand name components, available individually for construction. Valve line-up: 6S67, 6S67, 6V6GT, 6X5ct. Complete construction booklet with theoretical and practical diagrams, also price list of recommended parts. 1/6 post free.

THE SUPEREX "ATTACHE" ALL DRY PORTABLE (BUILDING COST 7/15/-). A really superb 4 VALVE SUPERHET receiver, giving first-class results on Long and Medium Wavebands. Cabinet is compact (Size 11 1/2" x 8 1/2" x 4 1/2"). Of attaché case type, covered twin colours, high quality leatherette. Wright complete receiver less batteries 8/10s. All components used of highest grade: OSMOR HIGH Q COILS and FRAME-AERIAL, Plesey-Amplion Midget I.F.T.s. Provision also made for 7 1/2" x 4 1/2" Elliptical speaker. Valve line-up: 1R5, 174, 1R5, 3V4. Sent for BOOK-LET giving full building details and practical wiring diagrams. 1/6 post free.

THE SUPEREX UPRIGHT PORTABLE (BUILDING COST £7/15/-) Chassis assembly and components also identical to attaché model with exception of cabinet. This is of the upright model with large speaker aperture in front, dial and controls under lift-up lid in top of cabinet. Covered twin colours, leatherette. Cabinet size: 10 1/2" x 8 1/2" x 4 1/2". Send for BOOKLET, 1/6 post free.

S.R. 2-4 WATT AMPLIFIER KIT (BUILDING COST £4/15/-). Designed on attractive lines and incorporating Base, Treble, Middle, and Volume controls. Suitable for most types pick-ups. Chassis hammer-finish, mottled grey or bronze and given professional finish with engraved control knobs. Complete P.U. and L.S. panels, O/P Transformer, Mains Transformer, etc. Valve line-up: 6S67, 6X5ct, 6V6GT. For A.C. Mains 200/240 volts. Send for LEAFLET giving home construction details. 6d. post free. The above amplifier is available ready built and tested, price 15/5/- post free.

Large range of Radio and Television components and special purpose valves at competitive prices. Send 6d. for current price list.
TERMS: Cash with order or C.O.D. Extra charge for C.O.D. please add postage. (U.K. and N. Ireland only.) **OPEN:** 9 a.m. to 6 p.m. Monday to Saturday, 1 p.m. Thursday. **PERSONAL CALLERS WELCOME.**

SUPERIOR RADIO SUPPLIES


37, Hillside, Stonebridge, London, N.W.10.
Phone: EL6ar 3644.

DIRECT FROM THE MANUFACTURER

DULCI RADIO/RADIOGRAM CHASSIS
Built to Highest Technical Standards

FULLY GUARANTEED

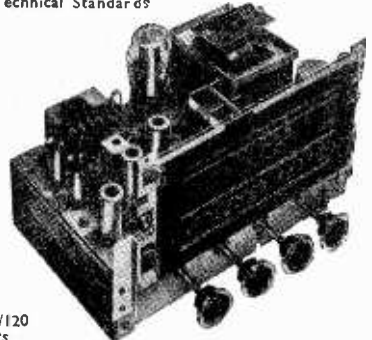All chassis 11 1/2" x 7 1/2" x 8 1/2" high. Latest type valves 6BE6, 6BA6, 6AT6, 6BW6, 6X4. Flywheel tuning. Negative feedback over entire audio section. Engraved knobs. 3 tone positions for radio and gram.



For A.C. Mains 100/120 and 200/250 volts

- Model B3.—Long, Medium, Short 5 Valves. Output 3 1/2 watt **£12/12/0**
- Model B3.—Plus Push Pull Stage 6 Valves. Output 6 watt **£15/15/0**
- Model B3.—Double Feature with P/Pull & R.F. Stage. 7 Valves. Output 6 watt **£18/18/0**
- Model B6.—Six Wavebands, Med., Long, 4 Short. (3 Bands spread.) 5 valves. Output 3 1/2 watt **£15/15/0**
- Model B6.—Plus Push Pull Stage 6 Valves. Output 6 watt **£18/18/0**
- Model B6.—Double Feature with P/Pull & R.F. Stage. 7 Valves. Output 6 watt **£23/2/0**

ALL PRICES TAX PAID

Escutcheon for 5 1/2" x 5 1/2" dial, 4/9 extra. Matching speakers P.M. type 3 ohms. 8in. or 10in. available. Chassis sent under money back guarantee conditions against remittance. Free particulars from the manufacturers.

THE DULCI CO. LTD.,

99 VILLIERS RD., LONDON, N.W.2. Telephone: Willesden 7773

HANNEY of BATH offers: —

OSRAM 912 Erie resistor-pot. kit with ceramic tube resistors, very highly recommended, 29/6; Lab resistor kit, 32/4; T.C.C. condensers, 55/-; **PART BUILDING** Components, with loose lead terminations, Mains trans., 44/-; Smoothing Choke, 29/6; Output trans., 78/9. Price includes Partridge carriage/packing charge. Printed panel, 14/6. W.B. chassis, 34/6. Send for complete list.

MULLARD 5 VALVE, 10 WATT AMPLIFIER T.C.C. Condensers, 45/-; Erie resistor-pot. kit, 37/6; Elstone Mains trans., 36/-; Elstone Output trans., 45/- (both types); Denco chassis, 12/6. Small parts as per our list. Matched pairs of valves are available for both the above designs.

All Components for the . . .

NEW FURY FOUR and the P.W. TAPE RECORDER.
Send for priced parts list.

COILPACKS: DENCO, CP 4/L and CP 4/M, 33/4; CP 3/370 pf. and CP 3/500 pf., 42/6; OSMOR Q 110, 45/-; L.M. 40/-; Batt., 50/-; TRF, 30/-; HF stage for HO pack, 20/-; ETA 4-Station pack, 43/8. We stock COILS by Weymouth, Osmor, Wearite, Denco, Teletron and R.E.P.

EISTONE Mains Trans. for the SIMPLEX TV, 48/-.

VIEWMASTER, WIDE ANGLE VIEWMASTER CONVERSION. Complete set of parts for converting existing Viewmaster to W.A., less valves, tube and mask, £14/18/6. W.A. Conversion instructions, 3/6; WB133, 48/6; WB14, 23/6; WB5, 42/-; WB16 and WB17, 7/6 each; WB18, 22/6; WB19, 26/6; WB21, 3/6; WB24, 10/6; Westinghouse 76EHT, 30, 17/-; Plus condensers and resistors as per our general list.

WIDE ANGLE COMPONENTS. ALLEN, Teleking Chassis, 50/-; Coilssets (TK & Super-visor), 44/6; LO.308, 40/-; FO.305, 21/-; DC.300c, 38/6; FC302, 31/-; GL.16 & 18, 7/6 each; SC.312, 21/-; AT.310, 30/-; OP.117, 9/-; BT.314, 15/-; DENCO Chassis Magnaview, 37/8; Chassis, Super-visor, 51/6; Coilssets, Magnaview, 41/2; WA/DCA1, 43/-; WA/PCA1, 31/-; WA/LCI and WC1, 7/6 each; WA/FMAL, 21/-; WA/LOT1, 42/-; WA/PBT1, 16/-; Send 6d. stamps for our General List of components for Viewmaster, Soundmaster, Williamson Amplifier, Teleking, Magnaview (Brimar & English Electric large screen TV), Super-visor, Mullard Universal, Close tolerance Silver Micacs, etc. etc. Please add 1/- postage to orders under 4/-.

L. F. HANNEY

77, LOWER BRISTOL ROAD, BATH

Tel.: 3811

BUILD THIS AMAZING RADIO
AN IDEAL XMAS GIFT

FOR **30/-**
POST FREE

- Selective tuning.
- Acorn low drain valve.
- Loud clear tone.
- Long range.
- No earth.
- Short aerial, 2ft.
- Welded steel case
- Easy to assemble.
- All parts for this set are sold separately

Ideal for:

- Fishing, Camping
- Cycling, Touring
- On the beach, etc

MAIL ORDER ONLY

This little set was designed to give you a real personal portable radio that you can enjoy anywhere without disturbing others. Use it on camping trips, in bed, in your office, or just anywhere. Send 2/- for layout, Wiring diagram and Component Price List.

Details of our 30/- Short Wave Receiver are now ready. Send 2/- for Layout, Circuits and Component Price List.

R. C. S. PRODUCTS (RADIO) LTD.,
11, OLIVER ROAD, LONDON, E.17



ELECTROLYTICS, capacity, voltage, size, type of mounting, price, post paid. 8. 450v. 1 x 2, clip. 2/-; 50. 12v. 1 x 12, tag. 1/6; 150. 25v. 1 x 12, clip. 2/-; 250. 12v. 1 x 12, wire. 2/3; 40 x 40. 275v. 1 x 2, clip. 3/3; 24 x 24 + 16. 350/425v. 1 x 2, clip. 4/9; 60 + 200. 275/350v. 1 x 1, clip. 6/6; 1. 150v. 1 x 1, clip. 1/1; 500. 12v. 1 x 12, tag. 2/3; 150. 25v. 1 x 2, clip. 1/9; 32 + 32. 350/425v. 1 x 2, clip. 5/-; 8 + 16. 450/525v. 1 x 2, clip. 4/-; 2. 450/525v. 1 x 1, tag. 1/6; 8. 450v. 1 x 2, clip. 1/9; 32 + 32. 450/525v. 1 x 3. W/E. 5/6; 16 + 16. 450/525v. 1 x 3. W/E. 4/6; 1.000 + 1.000. 6v. 1 x 3. Lug. 3/3. all alicans. Some with sleeves all voltages wkg. surge where marked new stock guaranteed. Set of 3 Components comprising line output trans. with E.H.T. winding to give 7K5 using EY51 (heater winding for EY51 also included) and fitted with width control. Scanning coils, low impedance line and frame, focus coil high (10,000 ohms). Set of 3. 42/- plus 2/- postage. Diagram of line trans. supplied. Mains Trans. PRI 0.210-240. SEC. 0.250-170v. 80ma; 6.3v. 2.5a. 6.3v. 12v. 40v. 14/6 speakers 6in. P.M. New boxed. 14/6

RADIO CLEARANCE LIMITED, 27 Tottenham Court Road, London, W.1. (Telephone: Museum 9188.)

RADIO UNLIMITED offer. Coilpacks L. M. and S. with Grain. sw. 24/6; M and L TR coils 5/9 pr. Crystal diodes 4/6; P1/Trans. 200/240 6v at 1.5a 5/6; Mains trans. 275/275. 6v-3a. 5v-2a. 80 ma. 21/6; TRF chassis kit, drilled chassis, dial, drive, backplate, pointer, etc. 9/-. New valves. 6V6. 6K7. 6K8. 6Q7. 5Z4. 29/6 set plus 1/3 post. Amplifier kit. AC or AC/DC. Complete to last nut, incl. valves and circ. 50/-. Fresh stock: 25mf/25v 1/2. 50/50 1/6. 8mf/450 1/8. 16/450v 2/16 x 16-450v 3/6; 32 x 32-350v 4/1. V/ Cntrs. all values 2/9. SP/sw 3/9. Mic trans. 2/-. P.M. Quakers 9999. 2/9. Co-ax cable 8/6 doz. yds. Door-rod aerial with lead 17/6. New boxed valves. 6KT6 5/6. 5U4G 8/-, 6V6M 8/-. 6SN7 8/-; 1A7 9/-. 1N5 and 3Q5 7/6. 13,000 valves actually in stock. Lists. **RADIO UNLIMITED**, Elm Road, London, E.17. Keystone 4813. New branch now at 50, Hoe St., E.17. (Lar 6377.)

EVERYTHING for radio constructors. Condensers. Coils. Valves. Resistors, etc. Send stamp for list. SMITH, 98 West End Road, Morecambe. Quick service.

S.W. BAT. comm. Rx; all bands; spread, econ. portable, perf. Offers. S.A.E. Box 251.

R.F. UNITS, types 26 at 32/6. 25 at 16/6. 24 at 12/6, brand new in original cartons with valves; postage 2/6. E.W.S. Co. 69, Church Rd., Moseley, Birmingham.

GERMANIUM DIODES, 1/- each. Quantities cheaper. BDC. 591. Green Lanes. London, N.8.

A.F. GEN. 15 c/s-150 kc/s 1 1/2. atten. etc. 27; R.F. Sig. Gen. 0.5-36 Mc/s 5/-; 5 bands. atten. etc. 56/10/-. Both good make; as new guar. Complete Tape Amplr. unused only 47. S.A.E. details. J. ROSS, 15. Redburn St., Chelsea. S.W.3.

OSMOR for really efficient Coils. Coilpacks and all Radio Components as specified for many "Practical Wireless" circuits. See advert. on page 6 for free circuits offer or send 5d (stamp) to OSMOR RADIO PRODUCTS LTD. (Dept. PCI P6) 418, Brighton Road, South Croydon, (Tel.: Croydon 5148/9.)

RATES: 5/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 11 extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless", Tower House, Southampton St., Strand, London, W.C.2.

RADIO and T.V. Sheets from 2/3. List 1/-, 4,000 Sheets available. RATEL 171, Norris St., Preston.

WALNUT Radiogram Cabinets of distinction; stamp details. R. SHAW, 69, Fallop Rd., E.11.

VALVE BARGAINS, 1R5, IS5, 3V4, 6/- each. 1T4 5/-. **MISC. BARGAINS**, Germanium Diode, 1/3; cabinet, walnut veneered, ideal for that spare set or bedroom radio with s/het. chassis and dial and 3 knobs, 18/-, cabinet separate 16/-. Dim. 12 x 6 x 6. All items new, money back guarantee. Post paid. A. BLACKBURN, Central House, Bury Wharf, Bury St., Ruislip, Mdx.

INSULATED Metal Probe Cases with 3in. point accessible compartment 4 x 4in 5/-. Bth. Germanium 1/9. WILKINSON, 42, Frances Rd., Windsor, Berks.

TAPE RECORDING

CLOSING DOWN, £250 worth brand new items, Truvox Tape Deck, Scotch Boy Tape, Transmitter, etc. cheap. Lists available. Box 250.

TAPE RECORDER MOTORS (all 200/250 A.C.): Hoover S.P.202. 15/-; S.E.M. H12G2. 17/6; Garrard (governed 78 r.p.m.). £2/10/-; Tamsa Tape Heads, B/H1682. £1; 5Y3GT. 7/-; 6BR7. 9/6; N78. 7/-; B9A Valveholder and Can. 3/-. All new equipment. Post and packing 1/- up to £1. Mail order only. HENRY A. PATTERSON & PARTNERS LTD., 156, High Holborn, W.C.1.

P.W. and SOUND MASTER Tape Recorder, all specified components available. Stamp details. FRANKLIN & HALL, 371, Havant Road, Farnlington, Portsmouth.

SITUATIONS VACANT

The engagement of persons answering these advertisements must be made through a Local Office of the Ministry of Labour or a Scheduled Employment Agency if the applicant is a man aged 18-64, inclusive, or a woman aged 18-59, inclusive, unless he or she, or the employment, is exempt from the provisions of the Notification of Vacancies Order, 1952.

T/V AND RADIO—A.M. Brit. I.R.E., City and Guilds. R.T.E.B. Cert., etc. on "no pass—no fee" terms. Over 95% successes. Details of exams. and home training courses in all branches of radio and T/V; write for 14-page handbook—free. B.I.E.T. (Dept. 242G). 29, Wright's Lane, London, W.8.

CITY AND GUILDS (Electrical, etc.) on "no pass—no fee" terms. Over 95% successes. For full details of modern courses in all branches of Electrical Technology send for our 144-page handbook—free and post free. B.I.E.T. (Dept. 242A). 29, Wright's Lane, London, W.8.

A.M.I. Mech. E., A.M. Brit. I.R.E., City and Guilds, etc., on "no pass—no fee" terms; over 95% successes. For details of exams. and courses in all branches of engineering, building, etc., write for 144-page handbook, free. B.I.E.T. (Dept. 242B). 29, Wright's Lane, London, W.8.

LOUDSPEAKERS repaired promptly. MODEL LOUDSPEAKER SERVICE, Bullington Rd., Oxford.

VALVES

XMAS VALVE BARGAINS, all guaranteed. SP61 at 2/6 each. EA50 at 1/- each. EB34 (Equ. 6H6) at 1/- each. EF50 (VR91) at 3/6 each. 807 at 4/6 each. 6A7 at 7/6 each. 80 at 7/6 each. 6J6 at 7/6 each. New Books just arrived: "Transistors and Crystal Diodes," what they are and how to use them 5/-; "Unit Construction of TV Receivers," by Bradley, 6/-; "TV Circuit Refinements," how to improve your TV, contains information by 25 leading TV manufacturers. 5/-; **SERVIO RADIO**, 156-8, Merton Rd., Wimbledon, S.W.19. (LIBerty 6525.)

VALVES, New, Tested and Guaranteed. Matched Pairs, KT66. 25/-; 6V6G and GT. 17/- per pr.; 6K8G. 6Q7G. 6SN7GT. 6SL7GT. 6AT6. 6BE6. 6BR7. 6BS7. 6SA7. 6S7GT. 6SK7. 6X4. 6XSGT. 8/-; 1R5. 1T4. IS5. 3V4. 6AM6. 5763. Y63. 6U5. 7/6; EB33. EZ40. KT33C. 25A6G. 12AT7. 8/6; PL81. PL82. ECL80. 1H5. 1N5. 10/6; 12AX7. 6/9. Coax cable, stranded, 75 ohms/in. 6d. yd. R. J. COOPER, 32, South End, Croydon, Surrey. (CRO. 9186.)

WINWOOD FOR VALUE, 12 Carnarvon Road, Leyton, E.10. New boxed valves. Return of post service. Lists issued. 1T4. 1S4. 1S5. 1R5. 1N5. 3S4. 3V4. 6V6. 6F6. 6BE6. 6BA6. 6SL7. 6N5. EF39. EBC33. EL32. 6X5. 5Y3. EF91. EB91. 807. EL91. all at 7/9 each. 6L6 6K8. KT33C. 6Q7. 1A7. EF37A. ECL80. EF80. EBC41. EP41. 9/- each. SP61. SP41. 6J5. EF50. 8H6M. 5/- each. 6K7G 4/6 each. Isolation trans. 2v. 4v or 6v. all 25% boost. 6/6 each. All Teletron coils stocked. Full range REP coils available. Send to-day for comprehensive catalogue. (Mail only).

BENTLEY ACOUSTIC FOR VALVES. 1E7 6/6. 2D13C 4/-. 3B7 8/6. 4D1 3/-. 5R4G 9/6. 6A6G 6/6. 6AL5 6/-. 6AM5 7/6. 6B4G 7/6. 6B7 7/6. 6B8 4/-. 6BX6 10/6. 6C6 6/6. 6C8 8/6. 6D6 6/6. 6F5 10/6. 6F6 7/-. 6F7 6/6. 6F12 6/6. 6G6 6/6. 6J8 10/6. 6L5 7/6. 6M2 11/-. 6Q7 8/6. 6SC7 10/-. 6SG7 7/6. 6SL7 8/-. 6SQ7 8/6. 6SS7 7/6. 6ST7 7/6. 6T6 8/-. 7B5 8/6. 7F7 10/6. 11D5 7/6. 12AT6 10/6. 12BT 7/6. 12K7 8/6. 12Q7 8/6. 12SC7. 7/6. 12UG7 7/-. 13D3 9/-. 15D1 10/6. 19AQ5 12/6. 19BG6 12/6. 19Y3 8/6. 25A6 8/6. 25Y5 8/6. 4. 10/6. 50L6 8/-. 5Y6 8/6. 61BT 10/6. 78 8/6. 210DDT 8/6. 210LF 2/6. 215SG 4/-. 220B 10/6. 240B 10/6. 220VSG 6/6. 240QP 10/6. 813 7/0-. 1626 8/6. 1629 7/-. 2051 10/6. 7193 2/6. AC/P 14 volt 6/6. AC/P (6 volt) 6/6. AC/GEN 5/6. AC/T 17/6. AC/JD 8/-. AZ 12/6. CBL31 17/6. CL4 14/-. CL33 11/-. CV6 1/6. CV73 4/6. D77 6/-. DET19 2/-. DH30 15/6. DH77 8/6. DL74 9/6. DPT 15/6. EI148 1/6. EBC3 10/6. EBF80 10/6. ECTO 10/6. ECL80 10/-. EF9 10/-. EF37 10/6. EF55 12/6. EL2 11/6. EZ35 9/-. FC13 9/-. GZ32 14/-. H42 7/6. H63 7/6. HZ 3/-. H123DD 6/6. KK32 10/6. L22 4/6. M16 6/6. MU12 8/6. N78 10/6. OM5 7/6. P41 3/-. P61 3/-. P215 3/6. PEN25 6/6. PEN26 16/-. PEN1340 6/-. PL83 11/6. PY81 10/-. QP21 7/6. QP25 6/6. QV047 (ex-units) 10/6. SD6 7/6. TP2620 17/6. UR3C 10/6. U9 12/6. U22 8/-. U24 13/6. U403 10/-. VR105/30 8/6. VS70 7/6. VU120A 3/-. W6 8/6. X22 10/6. X55 10/-. Y63 7/6. Special offer of sub-miniatures: XFY10. XFY12. XFY23. XFW10. XSG15. XH15. CK505AX. CK525AX. CK523AX. all 7/- each. Further selection of valves on page 48.

ALUMINIUM CHASSIS made to your requirements; 16 & 18 gauge; any quantity, large or small. We will be pleased to quote. **MACHINE CONTACTS**, Building 336, Hurn Airport, Christchurch, Hants.

BOOKS

I.P.R.E. TECHNICAL PUBLICATIONS. 6,500 Alignment Peaks for Superheterodynes, 5/9, post free. Data for constructing TV Aerial Strength Meter, 7/6. Sample copy The Practical Radio Engineer, quarterly publication of the Institute, 2/-; membership and examination data, 1/-; Secretary, I.P.R.E., 20, Fairfield Rd., London, N.8.

BOOKLETS. "How to Use Ex-Gov. Lenses and Prisms." Nos. 1 and 2, price 2/6 ea. Ex-Govt. Optical lists free for s.a.e. H. ENGLISH, Rayleigh Rd., Hutton, Brentwood, Essex.

AMERICAN MAGAZINES.—One-year "Audio Engineering," 35/-, specimen copy. 3/6; "Popular Science," 28/6; "High Fidelity," 50/-, specimen copy. 4/6. Free booklet quoting others. WILLEN LTD., Dept. 40, 101, Fleet Street, London, E.C.4.

WANTED

45/- OFFERED for 813 Type Valves; any quantity purchased. Write: **PYPE-HAYES RADIO**, 606, Kingsbury Road, Birmingham, 24.

NEW VALVES WANTED, small or large quantities: PL81, EY51, KT61, 5Z4G, 5R4, 5U4, 3G5, all television; prompt cash. **WM. CARVIS LTD.**, 103, North St., Leeds, 7.

VALVES WANTED. EB91, EF80, ECL80, PL81, EY51 and all TV types, 5Z4G, 6Q7, etc., etc. Brand new only, prompt cash. Send us your offers. **RADIO HAM SHACK LTD.**, 155, Swan Arcade, Bradford, 1.

ALL TYPES OF Valves required for cash. State quantity and condition. **RADIO FACILITIES LTD.**, 38, Chalcot Road, N.W.1. (PRImrose 9090.)

MORSE CODE Training

Send for the **Candler BOOK OF FACTS**

It gives details of all Courses which include a Special one for securing amateur licence. **CANDLER SYSTEM CO.** Dept. 5LO 52b, Abingdon Road, London, W.8. Candler System Co., Denver, Colorado, U.S.A.

ANNAKIN'S BARGAINS

Transformers, U.S.A. Mike 10 : 1 screened, 11d. U.S.A. AF. Osc., screened, 11d. TV 1 : 1 Blocking, 2/-, AF. 6k-40, ohms, 9d. AF. 2 : 1, screened, 6d. AF. 2k-500 ohms, screened, 6d. Tone chokes, 1/-, Valve holders, Mctal. 3d, BCG, 3d, Br7 cer., 2d. Resistance Coils, 49 ohms, 4d, 2k 4d, 6-7k, 4d, TagBds., 2-2w, 1-1w, 3d, 4-1w. Res., 3d. Quantity discounts. Above Post extra. C.W.O. only. Money Back Guarantee. Write now for Wonderful Free List.
25, Ashfield Place, Otley, Yorks.

HIGH FIDELITY

COMPONENTS IN STOCK FOR THE **MULLARD 5-10 OSRAM 912 AMPLIFIERS**
Price lists and 48-page catalogue free on request to **J. T. FILMER,** MAYPOLE ESTATE, BEXLEY, KENT
Tel: Bexleyheath 7267.

ACCUMULATOR CHARGERS, 16/- each, to clear. 45, Weelsby Street, Grimsby, Lincs.

AMERICAN RADIO Plans and Devices Now available. Hundreds of new and startling devices you can make. Only designs of this type available in U.K. Receivers, walkie talkies, amplifiers, recorders, magic eye alarms, etc., etc. Full lists, data, illustrations free for stamp. Send to-day.—A.P.S. (PW), Sedgeford, King's Lynn.

ARE YOU STUCK on Electrical or Radio Control? Large stock of Transformers, Rectifiers, Lamps, Rotary Converters, Motors, Technical Books, S.A.E. for bargain lists. **LAWRENCE**, 134, Cranley Gardens, N.10. (CLI. 6841.)

EDUCATIONAL

THE INSTITUTE of Practical Radio Engineers Home Study Courses are suitable coaching text for I.P.R.E. and other qualifying examinations. Fees are moderate. Syllabus of seven modern courses post free from **SECRETARY, I.P.R.E., 20, Fairfield Road, London, N.8.**

MERCHANT NAVY and Air Radio.—Here is an opportunity to train as Radio Officer. The big liners are open to you, but you must qualify for the P.M.G. Certificate, Day Evening and "Radiocerts" postal courses. Estd. 30 years; s.a.e. for prospectus from Director, **THE WIRELESS SCHOOL**, 21, Manor Gardens, London N.7. (Tel.: ARC. 3694.)

FREE! Brochure giving details of Home Study Training in Radio, Television, and all branches of Electronics! Courses for the hobby enthusiast, or for those aiming at the A.M.Brit.I.R.E., City and Guilds Telecommunications, R.T.E.B., and other professional examinations. Train with the College operated by Britain's largest electronic organisation; moderate fees. Write to Dept. **PW28, E.M.I. INSTITUTES, London, W.4.**

WIRELESS.—Day and Evening Class instruction for P.M.G. Certificate of Proficiency and Amateur Wireless Licence. Morse instruction only if required, also postal courses. Apply **B.S.T. LTD.**, 179, Clapham Rd., London, S.W.9.

SEE THE WORLD as a Radio Officer. Short training; low fees; scholarships; boarding/day students. Stamp for prospectus. **WIRELESS COLLEGE, Colwyn Bay.**

MERCHANT NAVY Wireless School Overseas House, Brooks' Bar, M/er 16.

BEST AND CHEAPEST!

Group B valves are unbeatable for value in reliable service, whilst you cannot buy better than Group A.

Type	A	B	Type	A	B	Type	A	B
5Z4G	8/8	6K7GT	5-4/-	EA50	2/-			
6AK5	8/6	6Q7	8/3	EB34	2/-			
6AM6	6/3	6Q4GT	10-8/9	EB91	7/3			
6P6A	7/6	6BH7	5/6	EB31	3/6			
6H6	3/6	6BK7	6/9	EB21	7/-			
6J5GT	5/-	6V6GT	8/6	EBL80	10-6			
6L7	7/-	6V8A	6-9	EB90	10-6			
6K5GT	7/-	6V6	7-9	KY241	5-9			
6K7	6/9	12H6	2-9	KK34	23-1-9			
6K7G	5/6	7193	2/6	VU111	3/-			

VALVEHOLDERS.—I.O., M.O., B7G, 9d. **NUTS, BOLTS, ETC.** (Prices for 3 doz. or 1 gr. pkt.)
1in. bolts 4 B.A. 10d. 2/6 6 B.A. 8d. 2/-
1in. " " " 1/3 2/6 " " 10d. 2/6
" " " 1/8 5/- " " 15 1/3
Washers " 6d. 1/5 " " 5d. 1/3
Tags " 8d. 2/- " " 8d. 2/-
FUSES all values, 4d. Holders, single, 6d., double 9d. Midget tubulars (tested) 0-04, 0-01 mfd. 3/6 doz. Full list, 3d. Orders over 10/- post free.
REED & FORD, 2A, BURNLEY ROAD, AINSDALE, SOUTHPORT


16 S.W.G. All 4 full-sided Chassis. 6in. x 4in. x 2in., 4/-; 7in. x 5in. x 2in., 4/6; 9in. x 8in. x 2 1/2in., 6/-; 10in. x 8in. x 2 1/2in., 7/-; 12in. x 8in. x 2in., 7/6; 12in. x 9in. x 2 1/2in., 8/6; 14in. x 10in. x 2 1/2in., 9/6; 16in. x 10in. x 3in., 11/6. A. Receiver type. 10in. x 6in. x 2in., 3/9; 12in. x 7in. x 2 1/2in., 5/-; 14in. x 8in. x 2 1/2in., 7/-; 18 S.W.G. 4-sided, 6in. x 4in. x 2in., 3/-; 7in. x 5in. x 2in., 3/3; 10in. x 8in. x 2 1/2in., 5/-; 12in. x 9in. x 2 1/2in., 6/6; 14in. x 10in. x 2 1/2in., 7/-.
Receiver type. 18 S.W.G., 7in. x 5in. x 2in., 2/6; 10in. x 6in. x 2in., 3/-; 12in. x 6in. x 2 1/2in., 3/6. Post 1/-.
Mould plastic Cabinet in walnut or ivory, chassis, 2 W/B dial, back plate, 3 knobs, back, fixing clips, pointer, drive head, drum, spring and motor cord, 27/6. 2/- Circuit, 1/9. post free. **E.L.M.O. PRODUCTS,** 230a, Utting Ave., Liverpool, 4.

AMPLIFIERS

NEW VERSION of the custom built Quality Amplifier, comprising three B7G valves in ceramic holders. Volt. Tapped, screened mains trans.; neg. fcbk.; vol. and tone controls. In strict rotation at £4/5/- carr. pd. E.K.E., 47, Arksey Lane, Bentley, Doncaster.

MIDGET AMPLIFIERS, £3/19/6, D & P. 2/6 having built-in power-pack for 200-250v A.C. Dimensions 10 x 3 x 2 1/2, fits all normal record players leaving room for speaker. 4 watts quality output, suitable for all speakers and with standard or L.P. pickups. Valves 6J7 and 6V6 available at 20/- per pair extra if required. Other models from £4/12/6, also cabinets and accessories. **SPECIAL:** Our new RDJ midget, 4 watt amplifier to fit into the Philips "Disc Jockey" is now available. Send 6d. for new 8 page illustrated catalogue. **ELECTRO-ACOUSTIC LABORATORIES,** Tain, Ross-shire, Scotland.

TESTSCOPE Mains Tester



For high and low voltage testing—1-30 and 100-450 volts A.C. or D.C. Write for interesting leaflet 29F 16 page manual (how to make 50 electrical tests) 1/- post free.

RUNBAKEN MANCHESTER

ASTRAL RADIO PRODUCTS

"HOME RADIO," 32-page booklet fully illustrated. Simple wiring instructions for Crystal Set, 1-, 2-, 3-Valvers, etc. 2/-, postage 3d.
T.R.F. COILS for All Day 2, Band 3, Push-button 4, etc. 6/6 pair, postage 6d.
"K" COILS A.C. Bandpass 3, 3/3 each, postage 6d.
FRAME AERIALS, m.w., 5/-, Postage 4d.
138, THE RIDGWAY, WOODINGDEAN, BRIGHTON, 7

1-Finger Pianists

Build your own electronic keyboard and play everything! Send for free leaflet. Guitar, cello, flute and trumpet are all easy. Write now...

C & S, 10 Duke St., Darlington, Co. Durham

Practical Wireless

BLUEPRINT SERVICE

PRACTICAL WIRELESS

No. of
Blueprint

No. of
Blueprint

CRYSTAL SETS

- 1/6d. each
- 1937 Crystal Receiver ... PW71*
- The "Junior" Crystal Set ... PW94*
- 2s. each
- Dual - Wave "Crystal Diode" ... PW95*

STRAIGHT SETS

Battery Operated

- One - valve : 2s. each
- The "Pyramid" One-valver (HF Pen) ... PW93*
- The Modern One-valver ... PW96*
- Two-valve : 2s. each.
- The Signet Two (D & LF) ... PW76*
- 3s. each.
- Modern Two-valver (two band receiver) ... PW98*
- Three-valve : 2s. each.
- Summit Three (HF Pen, D, Pen) ... PW37*
- The "Rapid" Straight 3 (D, 2 LF (RC & Trans)) ... PW82*
- F. J. Camm's "Sprite" Three (HF, Pen, D, Tet) ... PW87*
- 3s. each.
- The All-dry Three ... PW97*
- Four-valve : 2s. each.
- Fury Four Super (SG, SG, D, Pen) ... PW34C*

Mains Operated

- Two-valve : 2s. each.
- Selectone A.C. Radiogram Two (D, Pow) ... PW19*
- Three-valve : 3s. 6d. each.
- A.C. Band-Pass 3 ... PW99*
- Four-valve : 2s. each.
- A.C. Fury Four (SG, SG, D, Pen) ... PW20*
- A.C. Hall-Mark (HF Pen, D, Push Pull) ... PW45*

SUPERHETS

- Battery Sets : 2s. each.
- F. J. Camm's 2-valve Superhet ... PW52*
- Mains Operated : 3s. 6d. each.
- "Coronet" A.C.4 ... PW100*
- AC/DC "Coronet" Four ... PW101*

SHORT-WAVE SETS

Battery Operated

- One-valve : 2s. each.
- Simple S.W. One-valver ... PW88*
- Two-valve : 2s. each.
- Midget Short-wave Two (D, Pen) ... PW38A*
- Three-valve : 2s. each.
- Experimenter's Short-wave Three (SG, D, Pow) ... PW30A*
- The Perfect 3 (D, 2 LF (RC and Trans)) ... PW63*
- The Band-spread S.W. Three (HF, Pen, D, (Pen), Pen) ... PW68*

PORTABLES

- 1s. 6d.
- The "Mini-Four" All-dry (4-valve superhet) *

MISCELLANEOUS

- 2s. each.
- S.W. Converter-Adapter (1 valve) ... PW48A*
- (2 sheets), 7s. 6d.
- The P.W. 3-speed Autogram ... *
- The P.W. Electronic Organ (2 sheets), 7s. 6d. *

TELEVISION

- The Practical Television Receiver, (3 sheets), 10/6
- The "Argus" (6in. C.R. Tube), 2/6*
- The "Super-Visor" (3 Sheets) 7/6*
- The "Simplex" ... 3/-*

All the following blueprints, as well as the PRACTICAL WIRELESS numbers below 94 are pre-war designs, which in circulation for those amateurs who wish to utilise old components, which they may have in their spares box. The majority of the components for these receivers are no longer stocked by retailers.

AMATEUR WIRELESS AND WIRELESS MAGAZINE

STRAIGHT SETS

Battery Operated

- One-valve : 2s.
- B.B.C. Special One-valver ... AW387*

Mains Operated

- Two-valve : 2s. each.
- Consoelectric Two (D, Pen), A.C. ... AW403

SPECIAL NOTE

THESE blueprints are drawn full size. The issues containing descriptions of these sets are now out of print, but an asterisk denotes that constructional details are available, free with the blueprint.

The index letters which precede the Blueprint Number indicate the periodical in which the description appears. Thus P.W. refers to PRACTICAL WIRELESS, A.W. to Amateur Wireless, W.M. to Wireless Magazine.

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

No. of
Blueprint

SHORT-WAVE SETS

Battery Operated

- One-valve : 2s. each.
- S.W. One-valver for American ... AW429*
- Two-valve : 2s. each.
- Ultra-short Battery Two (SG, det Pen) ... WM402*
- Four-valve : 3s. each.
- A.W. Short Wave World-beater (HF Pen, D, RC Trans) ... AW436*
- Standard Four-valver Short-waver (SG, D, LF, P) ... WM383*

Mains Operated

- Four-valve : 3s.
- Standard Four-valve A.C. Short-waver (SG, D, RC, Trans) ... WM391*

MISCELLANEOUS

- Enthusiast's Power Amplifier (10 Watts) (3/-) WM387*
- Listener's 5-watt A.C. Amplifier (3/-) ... WM392*
- De Luxe Concert A.C. Electrogram (2/-) ... WM403*


QUERY COUPON

This coupon is available until Jan. 3rd, 1955, and must accompany all Queries, sent in accord with the notice on page 57. PRACTICAL WIRELESS, Jan., 1955.

9 Octave

realism...

from a single unit

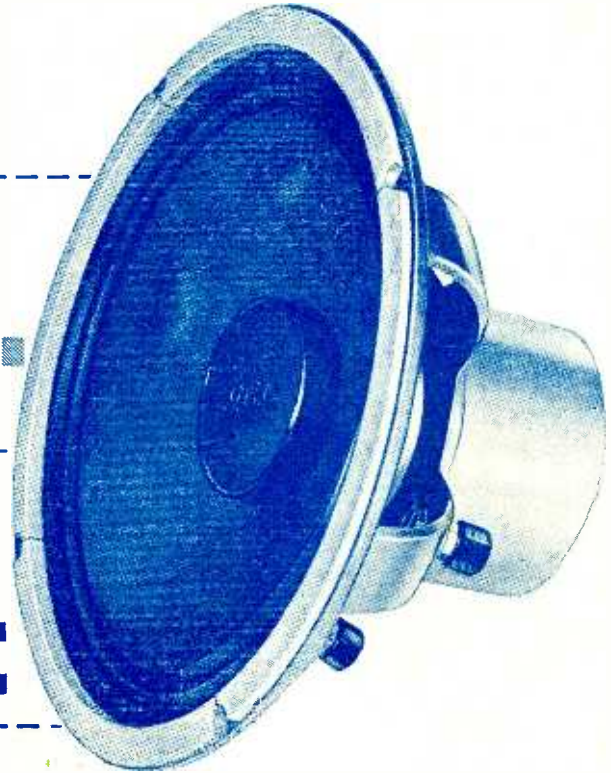

The G.E.C. metal cone loudspeaker gives lifelike reproduction of any type of sound over a range of 9 octaves. This includes the entire musical fundamental range together with overtones which give tonal quality and character to the performance of each musical instrument. The sound engineer will appreciate the simplification and improvement in performance which has been achieved by combining the following attributes in a single unit.

- Smooth response over a range of nine octaves with extremely good low frequency response
- Negligible inter-modulation
- Unequalled transient response due to special coil and cone construction

£8·15·0

TAX PAID

For the Home Constructor

This is a professional instrument and must be used under the correct conditions to obtain the optimum results. Cabinets have been designed for use with this loudspeaker, details of which will be available shortly.



Metal Cone Loudspeaker

THE GENERAL ELECTRIC COMPANY LTD., MAGNET HOUSE, KINGSWAY, W.C.2