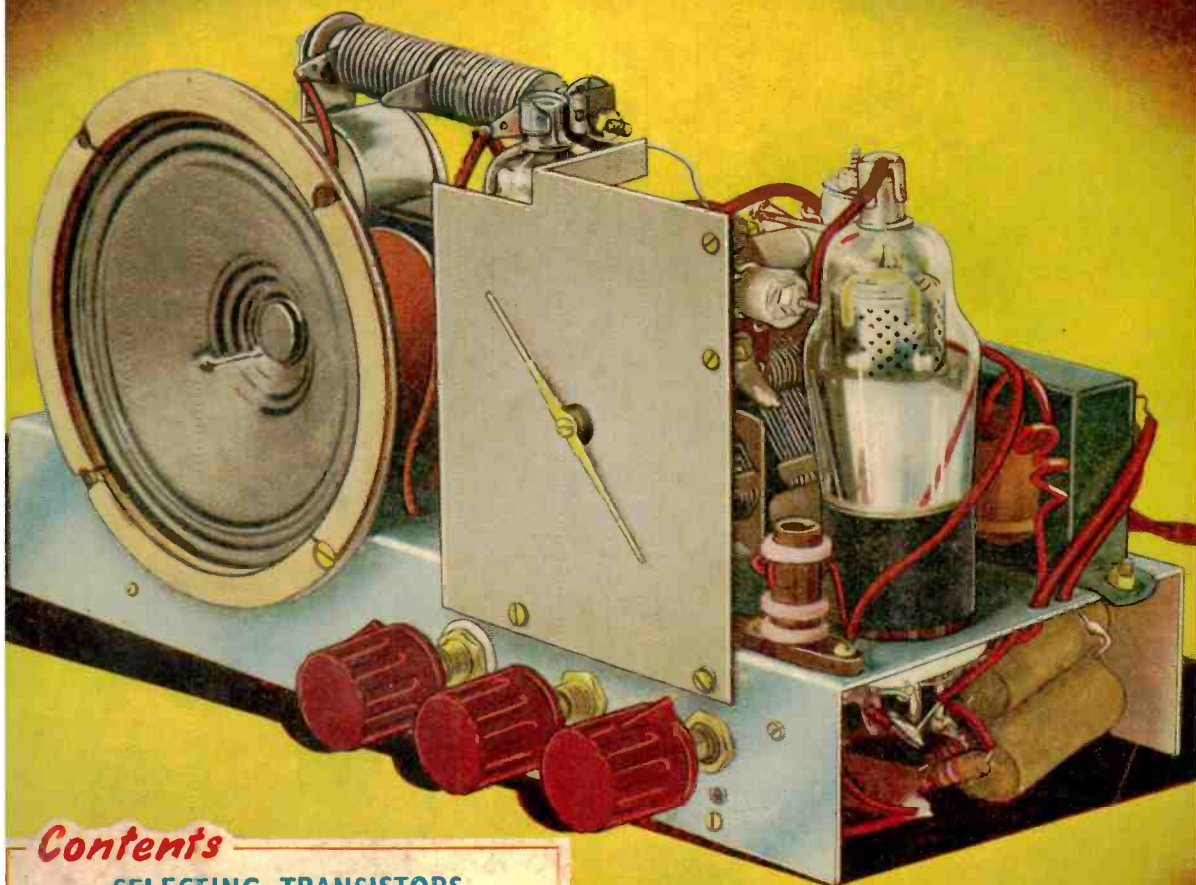


A TRANSISTORISED "N" CIRCUIT

# PRACTICAL 1/6

DECEMBER  
1959

# WIRELESS



## *Contents*

- SELECTING TRANSISTORS
- A BEAT FREQUENCY OSCILLATOR
- IMPROVING SUPERHETS
- A TRANSISTORISED PRE-AMPLIFIER
- A STEREO AMPLIFIER

*A Mains 3-Valver*



# miniature TUBULAR ELECTROLYTIC condensers

Types  
CEI32 &  
CEI34

Illustrated  
actual size

**These ranges** of miniature condensers are additional to the many types of T.C.C. electrolytics already available, and will appeal to all concerned with the design and servicing of equipment in which space is limited.

**They are constructed** similarly to the well-proved T.C.C. Micropack electrolytic, with aluminium tube and neoprene-faced disc end seals. Terminations are 22 s.w.g. wires, 1 1/4" long, hot solder coated, making them suitable for printed circuit assembly.

**The short length** of these condensers permits horizontal mounting on printed circuit panels with hole centres as close as 1". Insulating Sleeving to cover the metal case (as illustrated in the top photo) is desirable for horizontal mounting and should be specified in such applications.

**Temperature Rating:** ability to work satisfactorily at 70° C without voltage derating.

*A sub-miniature range for hearing aid and transistor circuitry is also available.*

| Capacity in $\mu$ F | Capacity Tol in % | Peak Wkg Volts DC | Ripple mA | Dimns. in ins. |     | T.C.C. Type No. |
|---------------------|-------------------|-------------------|-----------|----------------|-----|-----------------|
|                     |                   |                   |           | L.             | D.  |                 |
| 100                 | -20-100           | 6                 | 15        | 1 1/2          | 1/2 | CEI32AE         |
| 100                 | -20-100           | 12                | 35        | 1 1/2          | 1/2 | CEI34BE         |
| 50                  | -20-100           | 12                | 15        | 1 1/2          | 1/2 | CEI32BE         |
| 50                  | -20-100           | 25                | 35        | 1 1/2          | 1/2 | CEI34CE         |
| 25                  | -20-100           | 25                | 15        | 1 1/2          | 1/2 | CEI32CE         |
| 25                  | -20-100           | 50                | 35        | 1 1/2          | 1/2 | CEI34DE         |
| 12                  | -20-100           | 50                | 15        | 1 1/2          | 1/2 | CEI32DE         |
| 8                   | -20-50            | 150               | 30        | 1 1/2          | 1/2 | CEI34FC         |
| 4                   | -20-50            | 150               | 15        | 1 1/2          | 1/2 | CEI32FC         |
| 2                   | -20-50            | 350               | 7         | 1 1/2          | 1/2 | CEI32LE         |
| 1                   | -20-50            | 450               | 7         | 1 1/2          | 1/2 | CEI32PE         |



## THE TELEGRAPH CONDENSER CO LTD

RADIO DIVISION: NORTH ACTON · LONDON · W.3 · Tel: ACORN 0061



### RADIO & TV TABLES

**"WELBECK"** (as illustrated) measures 20" x 20" x 20" and is fitted with self adjusting gliders.

Price £3. 15. 0 (inc. P.T.)

**"SHERWOOD"** will accommodate the largest television receivers; measures 23" high x 25" wide x 22" deep.

Price £5. 5. 0 (inc. P.T.)

**"SENIOR"**, of ample dimensions (18" x 24" x 25" high).

Price £4. 18. 9 (inc. P.T.)


**"JUNIOR"** measures 21" high and 20" square. Price £4. 10. 0 (inc. P.T.)

**"FOREST"**, a new table in contemporary style; measures 20" x 20" x 20". Price £3. 10. 0 (inc. P.T.)

All are supplied packed flat ready for instant assembly and with the exception of the Welbeck have easy running 2" castors.



*The symbol of extra High Quality*

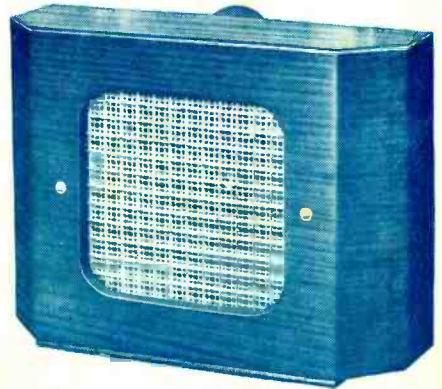

# Stentorian

## EXTENSION SPEAKERS

These well designed speakers demonstrate the traditional Whiteley quality at really competitive prices. This range of extension speakers has finger-tip volume control, is superbly finished in polished walnut veneer and provides excellent reproduction.

**WHITELEY ELECTRICAL RADIO CO. LTD.**  
MANSFIELD · NOTTS

**WITH THE EXCLUSIVE FINGER-TIP VOLUME CONTROLS**

- 'BUDE' 60/-
- 'BEDFORD' 72/-
- 'BRISTOL' 86/6

Prices include P.T.

# ETCH YOUR OWN PRINTED CIRCUITS



You can now make your own printed circuits in the comfort of your own home. Etch-your-own kits do not require any skill or additional equipment, errors can be corrected at any stage, and can be completed within 1 hour. Each kit contains more than 60 square inches of laminated board and sufficient chemicals to make dozens of printed circuits. Highest quality materials and completely safe to handle. Absolutely any schematic can be made to printed circuit. This kit opens a whole new field for the radio constructor, hobbyist, etc., no matter how limited his skill. Complete kit, with comprehensive manual containing advice and illustrated examples on translating ONLY 19/6 P. & P. 16. schematics into printed layouts, etc. Fully guaranteed.

## SPECIALLY DESIGNED MINIATURE KITS FOR OUR ETCH-YOUR-OWN PRINTED CIRCUIT KIT

|                                 |     |     |     |     |     |     |     |               |
|---------------------------------|-----|-----|-----|-----|-----|-----|-----|---------------|
| 1 Transistor diode pocket radio | ... | ... | ... | ... | ... | ... | ... | 24 6. p.p. 16 |
| 2 valve 3 watt mains amplifier  | ... | ... | ... | ... | ... | ... | ... | 49 6. p.p. 26 |
| 3 Transistor Super Pocket Radio | ... | ... | ... | ... | ... | ... | ... | 72 6. p.p. 26 |

All kits supplied entirely complete with full wiring and assembly details. Fully guaranteed.

**POCKET MULTI - METER.** 2,500 o.p.v. Multi range 630/120/300/120 v. A.C., ditto D.C. 0-1 K., 0-1 megohm; 400 MicroA., 12 mA., 300 mA., -00 to +64 DB. 5 ranges; 3in. x 4 1/2in. x 1 1/2in. Large clear dial. Leads supplied. List Price \$6.19s. OUR PRICE £4.7s. Saving you £2.12s. P. & P. 2/6.

**CONVERT TO V.H.F.** Within minutes you can extend the frequency of your receiver to cover V.H.F. by using our brand new V.H.P. Converter.

R.F. 26 covers 50-65 Mc/s. vernier calibrated tuning, 20/-  
R.F. 25 covers 40-50 Mc/s. Switched tuning, 9/6. Circuits supplied. P. & P. 3/6 on each.

**TRANSMITTER B 625.** Covers 100/156 Mc/s, will deliver 15 watts. consists of seven valves (2-832), 3 for modulation, 4 for R.F. Complete with operating details and circuits. ONLY 25/- P. & P. 6/-.

**D.V.M. 34.** America's finest little dynamotor offering 12 v. in with 220 v. out at 80 mA. With suppression and smoothing mounting base. Size 4 1/2 x 2 1/2 in. Original packing. ONLY 35/- P. & P. 3/6.

**V.H.F. MOBILE AERIAL** and base, as used by Taxis, Police, etc., 7/6. P. & P. 2/6.

**LIGHTWEIGHT HEAD SETS.** These H.S. 30 phones are the smallest used by the U.S. Air Force. 250 imp. using soft rubber miniature ear moulds for maximum music and voice reproduction of the finest quality. Supplied free is a small transformer unit with cord and plug which steps impedance up to 4,000 ohms. ONLY 15/- P. & P. 2/6.

**VERDIK HI-FI AMPLIFIER.** 10-watt push-pull ultra-linear feedback. Beautifully styled in green stove enamel. Provision for tuner, bass and treble, 5-position selector for radio, tape, mike, tape, L.P. and std. records. List price 20 gns. OUR PRICE £13.19.6. P. & P. 7/6.

**MICROPHONES - BRAND NEW.** Throat magnetic 4/6; Throat carbon 3/6; No. 8 carbon with switch 6/6; No. 7 moving coil 6/6. Tannoy power mikes only 5/-.



## INSTANT VALVE FILAMENT TESTER MODEL VT-41

Pocket-size—battery operated  
**GIVES INSTANT CHECK OF:**

- All Receiver Valves.\*
- All T.V. Valves.\*
- All T.V. Radio Set Fuses.
- All Pilot Lamps.
- Has built-in miniature 7 and 9-pin valve straighteners and battery test.
- \* International Octal, B9, B9, B7 Battery and Mains types.

Beautifully styled—precision made. Supplied complete. Fully guaranteed.  
**ONLY 30/- P. & P. 2/6**

## PORTABLE TRANS/RECEIVER SET




**ONLY 60/- EACH**  
P. & P. 4/-

Consisting of trans receiver covering 7.4-9 Mc/s, range up to 10 miles, complete with 5 valves, headphones, microphone, junction box & 6ft. telescopic aerial. Only requires 120 v. & 3 v. dry battery. These magnificent trans/receiver sets (as used by H.M. Forces) are ideal for any application and can be operated with ease.

**TWO FOR £6 POST FREE.**

## WIRELESS SET NO. 19 MK. II

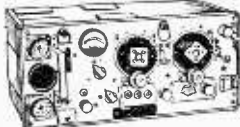

Incorporates "A" Set—TX/RX covering 2-8 Mc/s (37.5-150 metres). "B" Set—VHF TX/RX covering 230-240 Mc/s (1.2-1.3 metres) and intercom, amplifier. Complete with 15 valves, 500 microamp check and tuning meter, circuit and instruction book. (American manufacture.) in used condition, 65/- Carr. 10/-.

**BUILD AN F.M. TUNER** with 4his miniature 9.72 Mc/s I.F. Strip. Has 6 modern miniature valves, I.F.T.s, etc., supplied with full F.M. Tuner conversion details. Hailed by all our previous purchasers as a wonderful F.M. Tuner. Brand new, only 40/- P. & P. 3/6.

**COLLINS T.C.S. EQUIPMENT.** T.C.S. Transmitter, £9.10.0, carr. 15/-; T.C.S. Receiver, £8.10.0, carr. 15/-; S.A.E. for further details.

**HI-FI CO-AX SPEAKERS BRAND NEW—U.S.A. MADE** 12in. Coaxial Speaker. The woofer uses 6.8 oz. Alnico 5 magnet. Has 3in. tweeter and an electronic crossover network to separate the speaker functions. Frequency response: 40-17,000 cycles. Output 12 watts, impedance 8 ohms. **ONLY 160/-**  
8in. 2 1/2in. tweeter, 10 watts, etc., 90/-  
P. & P. 4/- on each.

**COMPLETE MORSE TRAINING UNIT.** Complete Code Set, contains key, buzzer, headphones, pitch control, operating internal battery, housed in portable wooden case. Brand New, only 12/6, carr. 5/-; Battery 1/6 extra.

**ACCUMULATORS.** 2 volts 16 A.H. (unspillable). Ideal for 6 and 12 volts supply, etc. Brand new. Original cartons. Size 4in. x 7in. x 2in., 5/6 each. P. & P. 1/6, 3 for 15/-; P. & P. 3/6. 6 for 27/6. P. & P. 5/-.

**F.M. TRANS / RECEIVERS B.C.620.** 20-28 Mc/s, crystal controlled, contains 14 valves, filament plate, alignment and voltage meter, volume control, and 12 volt supply unit and dry battery case. Complete station, £8.10.0, carr. 20/-; U.S.A. Hand Set, 20/- extra.


**VISIT OUR STAND No. 6**  
at the Radio Hobbies Exhibition

# ALL BAND RECEIVER R107

AMATEUR—SHIPPING—BROADCAST


This magnificent 9-valve 3-wave band receiver gives world wide reception over 1.2-17 Mc/s (19-250 metres). The sensitivity is 1 micro volt on C.W., and 2-6 microvolts on R.T. Panel controls include Band width switch ("Wide" or "Narrow"), choice of A.V.C. and B.F.O., Audio Filter, R.F. Gain, Aerial Trimmer. Has built-in Output stage with internal speaker. Headphones sockets. Incorporates internal A.C. mains power unit (100-250 v. A.C.) and 12 volts D.C. vibrator pack. Size 24 x 13 x 17in. These sets are extensively tested prior to despatch. **SUPPLIED COMPLETE AND READY FOR IMMEDIATE USE.**

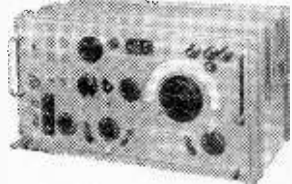**MODEL 1.** Slightly used appearance **£8.10.0.**  
**MODEL 2.** Very good appearance **£10.10.0.**  
Carr. 20/- (England and Wales), rest of U.K. extra.



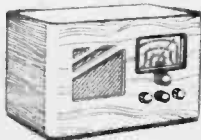Callers: 87, TOTTENHAM CT. RD., LONDON, W.1.  
Mail orders: (DEPT. P), 32a, COPTIC STREET, LONDON, W.C.1.  
Telephone: MUSEUM 9607.  
**WOT!** You don't own a Kelda catalogue! It's terrific and fully illus. Only 1/3.



**HOME RADIO 79/6**

A.C./D.C. Universal mains 5 valve octal superhet 3 waveband receiver can be adapted to gram p.u. In attractive wooden cabinet. 9½ x 18½ x 11½ in. Ins. carr. 4/6.

**FAMILY RADIO 99/6**

5 valve (octal) superhet. A.C. 3 waveband and gram. position. 4 controls. Modern attractive cabinet size 15½ x 18 x 10½ in. in cream and brown. Carr. & ins. 8/6.

**BAKELITE CABINETS**

Brand new. Colour brown. Attractive design. Size 12 x 7 x 5½ in. Ideal for small receivers, converters, etc. P. & P. 3/9.


**SUPER SUPERIOR RADIO 89/6**

4 waveband. 5 valve superhet radio. 2 tone covered metal cabinet size 24½ x 12 x 10 in. 4 control knobs. Positions for gram p.u. and extension speaker. A.C. only. Ins. carr. 8/6.

**OUR LATEST ADDITION TO THE CHASSIS RANGE****A COMPLETE & WORKING 17" T.V. CHASSIS 24 GNS.**

Latest chassis including 17 in. tube, permanent magnet speaker, 13 channel Turret Tuner (any two selected channels fitted). Other channels supplied on request at 7/6 each. 13 valves. Chassis and valves guaranteed for three months. CRT for 12 months' full guarantee. Sound I.F. 19.5 Mc/s. Vision 16 Mc/s. A.C. only. Ready and working to fit into your own cabinet. Carr. & ins. 25/-.

As above with 14 in. tube complete and working £19.19.0.

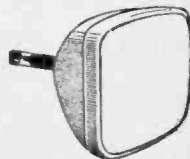
**REPLACEMENT RE-BUILT T.V. TUBES**

Cash price **£8.10.0**


OR YOURS for 8/6 initial payment (plus carr. & ins.) and 19 weekly payments of 8/6.

**★ 12 months' full guarantee.**

All sizes except 10 in. Completely re-built gun assembly, new cathode, heaters, etc., giving the high standard required for long picture life, quality and value. Carr. & ins. 15/6.

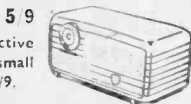**SUPER CHASSIS 79/6**

5 valve superhet chassis including 8 in. P.M. speaker and valves. Four control knobs (tone, volume, tuning, w/change switch). Four wavebands with position for gram. p.u. and extension speaker. A.C. Ins. carr. 5/6.

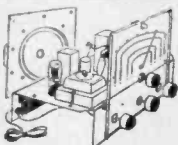**★ T.V. CHASSIS AT CLEARANCE PRICES ★ THE POPULAR 12" PLESSEY CHASSIS 9/6**

A bargain for anyone wanting to make up their own T.V. at a very low cost. A chassis in one unit. Less valves and tube. Chassis size 12 x 14½ x 11 in. I.F.'s 10.5—14 Mc/s. Can be adapted for a 12 channel Turret Tuner and modified to take a larger tube. Carr. & ins. 10/6.

**SOUND/VISION AND I.F. STRIP 7/9**

Plessey. I.F.'s 10.5 Mc/s sound. 14 Mc/s vision. 8 valveholders. Less valves. Size 8½ x 5 x 4½ in. Circuit incl. The tuner unit plugs directly into this chassis. P. & P. 2/6.

**TIME BASE 2/9**


Containing scanning coils, line transformer, etc., less valves. Drawings free with order. P. & P. 2/6.

**IDEAL RADIO CHASSIS 39/6**

5 volt superhet A.C. Radio or Radiogram chassis. 3 waveband and gram. switched 8 in. P.M. speaker included. Valve line-up: 6K8; 6K7; 6Q7; 6V6; 5Z4 (not included). Chassis size 19½ x 7½ x 9 in. Knobs 2/- extra. Set of valves 45/9 extra. Complete £45.0. Ins. carr. 5/6.

**CHASSIS 1/-**

6 or 8 valve latest type midge valve design for A.M. or F.M. Brand new. Cadmium plated. Size 12½ x 7½ x 2½ in. P. & P. 1/9.

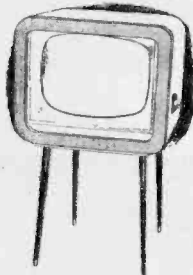**★ 17" T.V. 19 GNS. CASH PRICE****FEATURES:**

- ★ Beautiful latest finish cabinet in contemporary style covered and washable.
- ★ Polished legs 18 in. optional extra for 25/-.
- ★ 17 in. Rectangular Tube. Guaranteed fully for 12 months.
- ★ 12 channels "Turret Tuned" — 1TV/BBC. (Extra coils at only 7/6 a pair with order.)

Chassis. 14 B.V.A. Valves. Salvaged but re-conditioned and guaranteed 3 months. Carr. & ins. 30/-.

Due to overwhelming demands, some delay may occur. Please enquire when ordering.

**EXPRESS DESPATCH SERVICE**


Please phone to confirm Tube in stock. Send Telegraph Money Order. Tube despatched Passenger Train same day. This service only available with remittance by a Telegraph Money Order and cash sales, not terms.

**13 CHANNEL TURRET TUNER 65/-**

Brand new. Well known manufacturer. 38 Mc/s. Complete with valves PCF80 and PCC84. 3 series line-up and channel coils covering channels 1, 2, 3, 4, 5, 8 & 9. Carr. & ins. 3/6.

**SOLO SOLDERING TOOL 12/6**

110 v., 6 v. or 12 v. (special adaptor for 200/250 v. 10/- extra). Automatic solder feed including a 20ft. reel of Ersin 60/40 solder and spare parts. It is a tool for electronic soldering or car wiring. Revolutionary in design. Instantly ready for use and cannot burn. In light metal case with full instructions for use. Post 3/6.

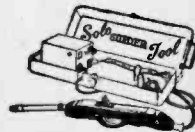**TRANSFORMERS****MAINS TRANSFORMER 5/9**

Primary 200-250. Secondary 0-100-250. 150 mA. Suitable for small amplifier with .1 series valves. 2½ x 1½ in. P. & P. 1/9.

**OUTPUT TRANSFORMER & SMOOTHING CHOKE COMBINED 4/9**

2½ x 1½ in. Suitable for EL84s in single or push-pull output. P. & P. 1/9.

**T.V. AERIALS 23/6**

For all i.T.A. channels. Outdoor or loft. 3 elements. P. & P. 2/6.

**AERIALS 15/6**

B.B.C. indoor type. Folded dipole with 12ft. co-ax. cable fitted. Post 1/9.

**T.V. AERIALS 7/9**

For all channels. Complete with co-ax. cable. For use indoors or in the loft. Post 1/3.

**CO-AX CABLE 6d. yd**

Cut to any length. Good quality. Post 1/6 on 20 yds.

**CATALOGUES FREE**

**DUKE & CO.**

★ EASY NO DEPOSIT INTEREST FREE DEFERRED TERMS ON ALL OUR GOODS—arranged purely for your convenience—SEND FOR DETAILS.



R.P.6

**RECORD PLAYER CABINETS**  
Here's Unrepeatable Value **29/6**

Elegant cabinet, cloth covered in grey or red with sunken control panel and speaker fret. Size 13 x 17 x 8in. deep. Takes a B.S.R. Monarch 4 Speed Autochanger ; 7 x 4in. elliptical speaker and most of the modern portable amplifiers. Carr. & ins. 4/6.

A beautifully styled cabinet. Made by a famous manufacturer. In polka dot cloth with clipped lid and carrying handle. Size 16 x 14½ x 8½in. deep. Will take B.S.R. Monarch 4 speed Autochanger and 7 x 4in. elliptical speaker and most of the modern portable amplifiers. Carr. & ins. 4/6.

R.P.2

**69/6**



★ **AMPLIFIERS** ★  
12 months' guarantee.

**PORTABLE AMPLIFIER MK. D.1.** 59/6

Brand new. Latest design with printed circuit. Dimensions 7 x 2½ x 5in. A.C. only. Mains isolated. 2-3 watts output. Incorporating EL84 as high gain output valve. Volume and tone controls. Knobs 2/6 extra. P. & P. 3/6.

**PORTABLE AMPLIFIER MK. D.2.** 79/6

Printed circuit. Latest design. Dimensions 7 x 2½ x 5in. A.C. only. Mains isolated 3-4 watts output. Incorporating the latest ECL82 triode pentode output valve giving higher undistorted output. Volume and tone controls. Knobs 2/6 extra. P. & P. 3/6.

**PORTABLE AMPLIFIER MK. D.3.** 89/6

De luxe model. Printed circuit. Latest design. Dimensions 7 x 2½ x 5in. A.C. only. Mains isolated 3-4 watts output. Incorporating the latest ECL82 triode pentode output valve giving higher undistorted output. Volume, treble and bass control. Knobs 3/6 extra. P. & P. 3/6.

**PORTABLE AMPLIFIER MK. D.5.** 39/6

Simple circuit employing ECL80 triode pentode output valve giving 2-3 watts output. A.C. only. Mains isolated. Single control for volume and on/off switch with knob. P. & P. 3/6.

**STEREOPHONIC AMPLIFIER** £7.19.6

Beautifully made for portable stereophonic record players. Latest design with printed circuit. Dimensions 3 x 5½ x 9½in. A.C. only. Mains isolated. Twin amplifiers each side giving 3-4 watts output. Incorporating ECL82 triode pentode valve. Full tone, volume and balance controls. Complete and ready to fit. Knobs 3/6 per set extra. P. & P. 3/6.

**B.S.R. FUL-FI CRYSTAL TURNOVER CART-RIDGES** 19/6

Brand new. Including sapphire needles for L.P. and Standard, giving fullest range and finest tone obtainable for any player. Can be fitted to all standard pick-up arms. P. & P. 9d.

*The New Continental Type*  
**RECORD PLAYER CABINETS**

In gay two-tone colours, as follows:—

**P.L.10 CABINET.** 39/6

Size 14½ x 12½ x 6in. Takes B.S.R. T.U.9. 4-speed record player unit. 8 x 3in. elliptical speaker, single control amplifier.

**C.H.I. CABINET.** 69/6

Size 14½ x 16½ x 8½in. Takes B.S.R. U.A.8. 4-speed autochanger, 7 x 4in. elliptical speaker. Most of the modern portable amplifiers. Attractive speaker grille and recessed control panel.

**T.W.I. CABINET.** 79/6

Size 15½ x 19½ x 10½in. Takes B.S.R. U.A.8. 4-speed autochanger. 8in. round speaker. 3 control amplifier. Carr. & ins. on all above 4/6.

R.P.3



**69/6**

A delightful looking cabinet 14½ x 17½ x 8½in. in 2-tone leatherette. Will take a B.S.R. Monarch 4-speed autochanger and 6½in. round speaker. Carr. & ins. 4/6.

R.P.4 **79/6**

Stylish cabinet by famous manufacturer. Cloth covered in contrasting colours (red & grey). Grilled front controls panel. Size 15 x 19 x 8½in. deep. Beautifully made—a cabinet you can be really proud of. Takes 4-speed B.S.R. Autochanger. 6½in. round or 7 x 4in. elliptical speaker. Room for any amplifier of your own choice. Carr. & ins. 4/6.



*World's Finest*  
**AUTOCHANGER**

**U.A.8. B.S.R. MONARCH 4-SPEED AUTOCHANGER**  
**£6.19.6**



**COLLARO CONQUEST 4-SPEED AUTOCHANGER** 26.19.6.  
**U.A.12. Latest B.S.R. MONARCH 4-SPEED MIXER** 28.9.6.  
**COLLARO CONQUEST STEREO AUTOCHANGER** 11 gns.  
**T.U.9. B.S.R. 4-SPEED SINGLE PLAYER** 89/6.

P. & P. on all the above 5/6.

★ **EXTENSION SPEAKERS,** 19/9



Polished oak cabinet of attractive appearance. Fitted with 8in. P.M. speaker W.B. or Goodmans of the highest quality. Standard matching to any receiver (2-5 ohms). Switch and flex included. Ins. Carr. 3/9.

**IDEAL FOR STEREOPHONIC SOUND**

8in. P.M. Speakers, 8/9. Post 2/6.  
6½in. P.M. Speakers, 12/6. Post 2/6.  
7 x 4in. Elliptical speaker, 19/6. Post 2/9.  
9½ x 4½in. Elliptical speaker, 22/6. Post 2/9.


**DUKE & CO.**

(Dept. D.12)

621-3, Romford Road, Manor Park, E.12.

Tel.: ILFord 6001-3



# NEW! EASY-TO-BUILD AND

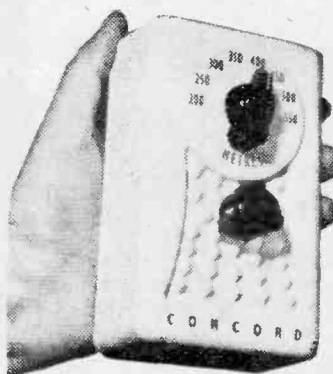

The new, exciting De Luxe "Gold Star" Pocket Radio in beautiful moulded plastic case—choice of four lovely colours, Red, Green, Blue and Pink. This model is a highly sensitive, self-contained set covering all medium waves. Uses modern miniature "button-base" valve and specially designed high efficiency coil. Exceptionally easy to build from our step-by-step plans—the case is supplied ready drilled! Size of radio only 4 1/2 in. x 2 1/2 in. x 1 1/2 in. —and batteries fit inside. We can supply all parts including case, detachable aerial, instruction book, screws, wire, etc., for only 48/- plus 2/- Post and Packing. C.O.D. 2/- extra. (Parts sold separately, priced parts list 1/9.)

Choice of beautiful walnut veneered cabinet or ivory bakelite. This is the lowest possible price consistent with high quality. No radio knowledge whatever needed

... can be built by anyone in 2-3 hours, using our very simple, easy-to-follow diagrams. The terrific new circuit of the "Ocean-Hopper" covers all medium and long waves, has razor-edge selectivity and exceptionally good tone. Price also includes ready drilled and punched chassis, set of simple-to-follow plans—in fact everything! Parts tested before despatch! Uses standard octal-base valves. (Low running costs—approximately 18 watts.) Size 12 in. x 6 in. x 5 in. Build this long-range powerful midget NOW. **TOTAL BUILDING COST INCLUDING PLANS, ETC., £5 7/6.** (Post and Packing 3/6.) Parts sold separately. Priced parts list and plans, 1/9. C.O.D. 2/- extra.

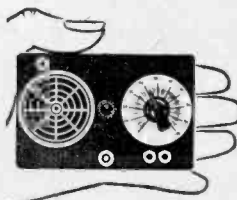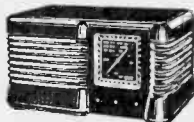

**THIS TRANSISTOR SET** Can Be Built For Only 29/6. The "Sky-Scout" Pocket two-stage transistor set, size only 1 in. x 3 1/2 in. x 4 1/2 in. Covers all medium waves and works entirely off tiny "penlight" battery which costs 6d, and fits inside case. All parts tested before despatch. Can be built for 29/6, plus 2/- Post and Packing, INCLUDING CASE, TRANSISTOR, STEP-BY-STEP

PLANS FOR ABSOLUTE BEGINNERS, nuts, bolts, etc. (C.O.D. 2/- extra.) Parts sold separately, priced parts list and plans, 1/6. VERY SIMPLE TO BUILD.



Our engineers have designed a novel Wrist-Watch Radio using latest Transistor Techniques. Size only 1 1/2 in. x 1 in. x 1 in. !!!—"Feather-weight"—yet gives clear, crisp, personal-phone reception over all medium waves. Tiny battery inside lasts months—costs 5d. No Snags, anyone can build it in an hour or two using our pictorial step-by-step simple plans. All parts supplied (including case and strap) for only 29/6 (add 2/6 Post, etc.). C.O.D. 2/- extra. (All parts sold separately, priced parts list 1/6.) Send Now!




This amazing "Tiny-Tim" model—no larger than a matchbox—costs nothing to run—ever! No batteries! No Valves! No electricity! Will never run down or burn out. Uses the latest TRANSISTOR TYPE GERMANIUM DIODE, receives local stations anywhere—without extra aerial. Clear, Crisp Tone. No snags, anyone can build it within an hour using our step-by-step instruction book, etc., for only 17/6, plus 1/6 Post and Packing (C.O.D. 2/- extra). (Parts sold separately, priced parts list 1/9.)

Learn Electricity by building a low cost Concord Model! Concord models include the latest electronic advances and are constantly being modernised by Concord's own research department. Concord designs are years ahead. Every latest advance finds its way into the educational and highly practical Concord Models. Special instruction books describe minutely every step in the assembly. Build, Learn from AND USE Concord Designs. TRADE ENQUIRIES INVITED. WE BULK PURCHASE ELECTRONIC COMPONENTS AND EQUIPMENT.

ADDRESS ON OPPOSITE PAGE →

# FUN-TO-MAKE CONCORD RADIOS

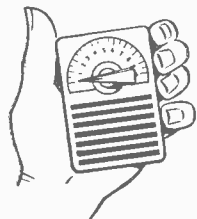

Postage, etc., 2/- (C.O.D. 2/- extra.) (Parts sold separately. Priced parts list and plans 1/6.) **R U S H Y O U R ORDER TODAY!**

**TWO-TRANSISTOR POCKET SET.** Can Be Built for 45/-. BUILD THE "SKYGNOME" VEST-POCKET TWO TRANSISTOR RADIO which gives a superb performance and is highly sensitive. Weight under 7 ozs.—yet it is a THREE-STAGE receiver covering all medium waves, working entirely off a "penlight" battery. Every part tested before despatch! **SPECIAL STEP-BY-STEP PLANS FOR ABSOLUTE BEGINNERS.** Total building cost including case, transistors, etc.—everything down to the last nut and bolt—**ONLY 45/- with plans.**

## BUILD THIS POCKET RADIO

Can Be Built for 39/6.



Anyone can build this beautiful precision Pocket Radio in an hour or two. No knowledge whatever needed. Our simple pictorial plans take you step-by-step! Remarkably sensitive—covers all medium waves, inc. Luxembourg, Home, Light, Size only 2in. x 3in. x 5in.—Not a Toy! But a Real, Personal-phone, Valve Radio With Detachable Aerial! **IDEAL FOR BEDROOM, GARDEN, etc.** We supply ALL parts necessary, together with plans, etc., for the special price of 39/6, plus 2/6 post and packing. (C.O.D. 2/- extra.) **BUILD YOURS NOW!** (All parts sold separately, priced parts list 1/9.) Send Today! Money refunded if parts returned intact within 7 days.


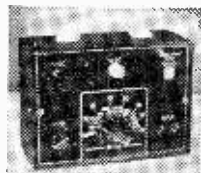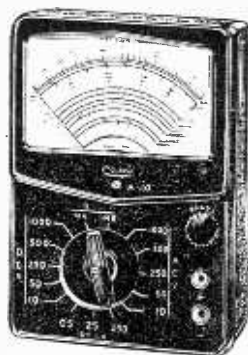
## The "COMPANION" PRINTED CIRCUIT POCKET SET.

BUILD THIS 3 TRANSISTOR POCKET RADIO... **PRINTED CIRCUIT VERSION!** The "Companion" is comparable in sensitivity to a three-valve battery set. It is exceptionally small in size (4 1/2 in. x 3 in. x 1 1/2 in.) and is a self-contained pocket radio that does not need aerial or earth. It has built-in speaker and covers medium and long waves. This unique little set can be built **FOR ONLY 97/6. EVERYTHING INCLUDED!** (Plus post and packing 2/6.) All parts sold separately, price list, etc. 6d. C.O.D. 2/- extra.

**LIMITED QUANTITY ONLY!**—Never before such amazing value! A high grade universal testmeter. Large scale (3 1/2 in.), highly sensitive movement (500 MicroAmps!) Measures A.C. Volts, D.C. Volts, D.C. Current, Ohms, Decibels, Inductance and Capacitance! Ranges: D.C. Volts—0-10 v., 50 v., 250 v., 500 v., 1,000 v. A.C. Volts—0-10 v., 50 v., 250 v., 500 v., 1,000 v. D.C. Current—0-500 MicroAmps, 25 MilliAmps, 250 MilliAmps. Resistance—0-10 K ohms and 1 Megohm. Decibels—-20 dB. to +22 dB. and -20 dB. to -36 dB. Capacitance—100 pfd. to 0.6 mfd. Inductance—10 to 1,000 Henries (also with external D.C. voltage will measure to 100,000,000 ohms!). A beautiful, strongly-made instrument. Brand New, not a kit, at only 97/6, including test prods, instruction book and internal batteries (replacements cost only 6d. each). Plus 2/6 Post and Packing. (C.O.D. 2/- extra.)




Can Be Built for 47/6. Build this exceptionally sensitive high efficiency personal phone radio. Uses unique assembly system and can be built by anyone without any radio knowledge whatever in 45 minutes. Handsome black-crackle steel case with specially made black and gold dial with stations printed. Size of radio only 6 1/2 in. x 5 in. x 3 in. Covers all medium and long waves. H.T. consumption only 1 to 1.5 mA. Ideal for Bedroom, Garden, Holiday, etc. **BUILD THE "SKY-ROMA" NOW!** Total building cost—everything down to the last nut and bolt, 47/6 (Postage, etc., 2/-) with full set of clear, easy-to-follow plans. (Parts sold separately. Priced parts list and plans 1/6.) C.O.D. 2/- extra.

ing cost! Covers all the medium waves with the very latest circuitry bringing in stations from all over Europe—without fuss. Easy as A.B.C. to assemble, using our step-by-step instruction manual. Size only 4 1/2 in. x 2 1/2 in. x 1 1/2 in.—a fascinating little pocket radio. We can supply all the parts including beautiful two-tone case, detachable aerial, instruction book, screws, wire, etc., for only 29/6 (plus 2/- post and packing). C.O.D. 2/- extra. (Parts sold separately, priced parts list 1/9.)



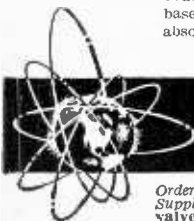The sensational "Silvertone" model! A highly compact self-contained miniature "button-base" valve pocket radio at absolute "rockbottom" build-



## CONCORD ELECTRONICS

210, Church Road, Hove, Sussex

Dept. PW13

Orders receive prompt attention. Cheques accepted. Cash on delivery 2/- extra. Please print name and address in block letters. Suppliers to Schools, Universities, Government and Research Establishments. Complete range of components and valves stocked. Regret no C.O.D. abroad.

# BENTLEY ACOUSTIC CORPORATION LTD.

THE VALVE SPECIALISTS. 38 CHALCOT ROAD, LONDON, N.W.1. Telephone: PRIMROSE 9090

EXPRESS POSTAL SERVICE! ALL ORDERS DESPATCHED SAME DAY AS RECEIVED. FOR ONLY 2/- EXTRA TELEPHONE FOR THAT URGENT ORDER TO BE DESPATCHED IMMEDIATELY BY OUR SPECIAL C.O.D. SERVICE.

|       |       | ANY ORDER INSURED AGAINST DAMAGE IN TRANSIT FOR ONLY 8/- EXTRA. |       |        |       |          |       |           |        |         |       |         |         |         |          |        |       |          |          |  |
|-------|-------|---|-------|--------|-------|----------|-------|-----------|--------|---------|-------|---------|---------|---------|----------|--------|-------|----------|----------|--|
| 0B2   | 17/6  | 6C8   | 12/6  | 6X4    | 6/6   | 19H1     | 10/   | AC/PEN    | DL94   | 7/6     | EL33  | 12/6    | KTZ63   | 10/6    | QP25     | 15/-   | UCH81 | 9/6      |          |  |
| 0Z4   | 6/-   | 6C9   | 12/6  | 6X5GT  | 8/-   | 20F1     | 15/3  | 5-pin     | DL96   | 9/-     | EL34  | 15/-    | L63     | 6/6     | QS150/15 |        | UCL82 | 11/6     |          |  |
| 1A3   | 3/-   | 6C10  | 10/6  | 6/30L2 | 10/-  | 20F2     | 26/4  | 7-pin     | DL10   | 10/6    | EL38  | 26/6    | LN152   | 10/6    |          |        | UCL83 | 19/3     |          |  |
| 1A5   | 6/-   | 6CD6G   |       |        | 12/6  | 20L1     | 26/4  | AC2PEN    | DM70   | 7/6     | EL41  | 9/-     | MH4(C)  | 7/-     | R12      | 9/6    | UF41  | 9/6      |          |  |
| 1A7GT |       |   | 29/10 | 7B7    | 19/3  | 20P1     | 26/4  |           | EA50   | 2/-     | EL42  | 13/11   | MHL4    | 7/6     | R18      | 14/-   | UF42  | 12/6     |          |  |
| 1C5   | 21/11 | 6CH6  | 12/6  | 7B7    | 8/6   | 20P3     | 23/3  | AC2PEN    | EABC80 | 9/-     | EL81  | 12/6    | MHLD6   | 12/6    | R19      | 19/11  | UF80  | 10/6     |          |  |
| 1D6   | 10/6  | 6D3   | 19/11 | 7C5    | 8/-   | 20P5     | 23/3  | DD        | 26/6   | EAC91   | 7/6   | EL84    | 8/6     | ML4     | 12/6     | SD6    | 12/-  | UF85     | 10/6     |  |
| 1H5GT | 11/-  | 6E5   | 12/6  | 7D8    | 23/3  | 25LG2T   | 10/-  |           | EF42   | 2/6     | EL91  | 5/-     | MX40    | 15/-    | SP4      | 13/6   | UF89  | 9/-      |          |  |
| 1L4   | 6/-   | 6F1   | 26/6  | 7H7    | 8/-   | 25U4     | 16/7  | AC5PEN    | EB41   | 8/6     | EL95  | 10/6    | N37     | 19/11   | SP42     | 12/6   | UL41  | 9/-      |          |  |
| 1LD5  | 5/-   | 6F6G  | 7/-   | 7R7    | 12/6  | 25Y5     | 10/6  |           | EB91   | 5/6     | EM34  | 10/6    | N78     | 19/11   | SP61     | 3/6    | UL44  | 26/6     |          |  |
| 1LN5  | 5/-   | 6F6GT   | 8/-   | 7S7    | 10/6  | 25Y5G    | 10/-  | AC6PEN    | 7/6    | EB33    | 23/3  | EM71    | 23/3    | N108    | 19/11    | SU25   | 26/6  | UL46     | 14/6     |  |
| 1N5GT | 11/-  | 6F8   | 12/6  | 7V7    | 8/6   | 25Z4G    | 9/6   | AC/P4     | 8/6    | EB33    | 7/-   | EM80    | 9/6     | N308    | 20/7     | SU61   | 9/6   | UL84     | 8/6      |  |
| 1R5   | 7/6   | 6F11  | 47/3  | 7Y4    | 8/-   | 25Z5     | 10/6  | AC/S3     | 23/3   | EB41    | 8/6   | EM81    | 9/6     | N339    | 29/10    | T41    | 23/3  | UM4      | 17/3     |  |
| 1S4   | 9/-   | 6F12  | 5/6   | 7Z4    | 18/7  | 25Z6G    | 10/-  | AC/TP     | 33/2   | EBF81   | 8/6   | EM84    | 10/6    | OA70    | 4/-      | TTD4   | 24/7  | UR1C     | 9/-      |  |
| 1T5   | 7/6   | 6F13  | 11/6  | 8D2    | 3/6   | 25Z6GT   |       | AC/VP1    |        | EBF80   | 10/-  | EN31    | 37/-    | OA71/81 | 4/-      | TH48   | 15/-  | UU6      | 19/11    |  |
| 1Y4   | 6/-   | 6F14  | 26/6  | 8D3    | 5/6   |          | 16/7  | 7 pin     | 15/-   | EBF83   | 13/11 | EY51    | 9/6     | OC72    | 17/-     | TH41   | 26/6  | U07      | 16/7     |  |
| 1U5   | 10/-  | 6F15  | 15/3  | 9BW6   | 15/3  | 27S5     | 19/11 | AC/VP2    | 23/3   | EBF89   | 9/6   | EY83    | 16/7    | P61     | 3/6      | TH233  | 33/2  | U08      | 26/6     |  |
| 2A7   | 10/6  | 6F16  | 9/6   | 9D2    | 4/-   | 28D7     | 7/-   | ATP4      | 5/-    | EBL21   | 23/3  | EY84    | 14/-    | PABC80  |          | TH2321 | 20/7  | U09      | 7/6      |  |
| 2P    | 26/6  | 6F17  | 12/6  | 10C1   | 12/-  | 30C1     | 8/-   | AZ1       | 18/7   | EBL31   | 23/3  | EY86    | 10/-    |         | 13/11    | TP22   | 15/-  | UY1N     | 18/7     |  |
| 2X2   | 4/6   | 6F32  | 10/6  | 10C2   | 26/6  | 30F5     | 7/-   | AZ31      | 10/-   | EC52    | 5/6   | EZ35    | 6/-     | PCC84   | 8/6      | TP25   | 19/6  | UY21     | 16/6     |  |
| 3A4   | 7/-   | 6F33  | 7/6   | 10D2   | 12/-  | 30FL1    | 10/-  | AZ41      | 13/11  | EC54    | 6/-   | EZ40    | 7/6     | PCC85   | 9/6      | TP2620 | 33/2  | UY41     | 7/6      |  |
| 3A5   | 10/6  | 6G6   | 6/6   | 10F1   | 17/6  | 30L1     | 8/-   | B36       | 24/7   | EC70    | 12/6  | EZ41    | 7/6     | PCC88   | 23/3     | TY86F  | 13/6  | UY85     | 7/6      |  |
| 3B7   | 12/6  | 6H6GTG  | 3/-   | 10F9   | 10/6  | 30P12    | 8/-   | BL63      | 7/6    | EC92    | 13/3  | EZ80    | 7/-     | PCC89   | 14/-     | U12/14 | 12/-  | VM54B    | 23/3     |  |
| 3D6   | 5/-   | 6HG6TM  | 3/6   | 10LD3  | 8/6   | 30P16    | 8/-   | CI        | 12/6   | ECC32   | 10/6  | EZ81    | 7/-     | PCF80   | 8/6      | U16    | 12/-  | VP27     | 12/6     |  |
| 3Q4   | 7/6   | 6J5G  | 5/-   | 10LD11 | 3/6   | 30PL1    | 11/6  | C1C       | 12/6   | ECC33   | 8/6   | FC2A    | 24/7    | PCF82   | 11/6     | U18/20 | 9/6   | VP28     | 15/-     |  |
| 3Q5GT | 9/6   | 6J5GTG  | 5/6   |        | 15/11 | 31       | 7/6   | CBL1      | 26/6   | ECC34   | 24/7  | FC4     | 15/-    | PCL82   | 12/6     | U22    | 29/10 | VP4B     | 14/6     |  |
| 3S4   | 7/6   | 6J5GTM  | 6/-   | 10P13  | 15/6  | 33A/158M |       | CBL31     | 23/3   | ECC35   | 8/6   | FC13    | 26/6    | PCL83   | 11/6     | U24    |       | VP13C    | 7/6      |  |
| 3V4   | 7/6   | 6J6   | 5/6   | 10P14  | 19/3  |          |       | CCH35     | 23/3   | ECC40   | 23/3  | FC13C   | 26/6    | PCL84   | 12/6     | U25    | 10/-  | VP23     | 6/6      |  |
| 5R4GY | 17/6  | 6J7G  | 6/-   | 11D3   | 24/7  | 35/51    | 12/6  | CK506     | 6/6    | ECC81   | 8/6   | FV4/500 |         | PEN4DD  |          | U36    | 10/-  | VP41     | 6/6      |  |
| 5U4G  | 8/6   | 6J7GT   | 10/6  | 12A6   | 6/6   | 35A5     | 21/3  | CL33      | 19/3   | ECC82   | 7/6   |         | FV4/800 |         | PEN25    | 19/11  | U33   | 26/6     | VR75/30  |  |
| 5V4G  | 11/-  | 6K6GT   | 8/-   | 12AC6  | 15/3  | 35L6GT   | 9/6   | CV63      | 10/6   | ECC83   | 8/6   |         |         | PEN36C  | 10/6     | U35    | 26/6  |          | 17/6     |  |
| 5X4G  | 12/6  | 6K7G  | 5/-   | 12AD6  | 17/3  | 35V4     | 7/6   | CV271     | 10/6   | ECC84   | 8/6   |         |         |         | G230     | 10/6   | U37   | 26/6     | VR105/30 |  |
| 5Y3G  | 8/-   | 6K7GT   | 8/-   | 12AE6  | 13/11 | 35Z3     | 10/6  | CV429     | 30/6   | ECC85   | 8/6   |         |         | PEN40DD |          | U43    | 9/6   |          | 9/-      |  |
| 5Y3GT | 7/6   | 6K8G  | 8/-   | 12AH7  | 8/6   |          | 6/6   | CY1       | 18/7   | ECF91   | 5/6   | G232    | 12/-    |         |          | U45    | 9/6   | VR150/30 |          |  |
| 5Y4   | 12/6  | 6K8GTG  |       | 12AH8  | 12/6  | 35Z5GT   | 9/6   | CY31      | 16/7   | ECF80   | 11/6  | G234    | 14/-    |         |          | U25    | 10/-  |          |          |  |
| 5Z3   | 12/6  |   | 12/6  | 12AT6  | 7/6   | 41MTL    | 8/-   | D1        | 3/-    | ECF82   | 10/6  | H30     | 5/-     | PEN44   | 26/6     | U50    | 8/6   |          | 9/-      |  |
| 5Z4G  | 10/6  | 6K25  | 19/11 | 12AT7  | 8/-   | 42       | 23/3  | D15       | 10/6   | ECH3    | 26/6  | H63     | 12/6    | PEN45   | 19/6     | U52    | 8/6   | VT61A    | 5/6      |  |
| 5Z4GT | 12/6  | 6L1   | 23/3  | 12AU6  | 23/3  | 43       | 12/6  | D63       | 5/6    | ECH21   | 23/3  | HABC80  |         | PEN45DD |          | U54    | 19/11 | VT501    | 5/6      |  |
| 6A7   | 26/6  | 6L6G  | 9/6   | 12A7   | 7/6   | 50C5     | 12/6  | D77       | 5/6    | ECH35   | 9/6   |         |         |         | 26/6     | U76    | 6/6   | W61M     | 26/6     |  |
| 6A8   | 10/-  | 6L6M  | 12/6  | 12AV6  | 12/6  | 50CD6G   |       | DAC32     | 11/-   | ECH42   | 10/6  | HL23    | 10/6    | PEN46   | 7/6      | U78    | 6/6   | W76      | 6/6      |  |
| 6AB7  | 8/-   | 6L7GT   | 12/6  | 12AX7  | 8/-   |          | 29/10 | DAF91     | 7/6    | ECH81   | 9/6   | HL23DD  |         | PEN383  | 23/3     | U107   | 16/7  | W81M     | 6/6      |  |
| 6AB8  | 10/6  | 6L18  | 13/-  | 12BA6  | 8/6   | 50L6GT   | 9/6   | DAF96     | 9/-    | ECH83   | 13/11 |         | 17/3    | PEN45DD |          | U191   | 16/7  | W107     | 15/3     |  |
| 6AC7  | 6/6   | 6L19  | 23/3  | 12BE6  | 10/-  | 53KU     | 19/11 | DC90      | 13/11  | ECL80   | 10/6  | HL41    | 12/6    |         |          | U201   | 16/7  | W729     | 18/7     |  |
| 6AG5  | 6/6   | 6LD3  | 8/6   | 12BH7  | 21/3  | 72       | 4/6   | DD41      | 13/11  | ECL82   | 10/6  | HL41DD  |         | PEN/DD  |          | U251   | 14/-  | X24M     | 24/7     |  |
| 6AK5  | 8/-   | 6L20  | 15/11 | 12E1   | 30/-  | 75       | 24/7  | DDT4      | 24/7   | ECL83   | 19/3  |         | 19/3    | 4020    | 33/2     | U281   | 19/11 | X31      | 26/6     |  |
| 6AL5  | 5/6   | 6N7   | 8/-   | 12J5GT | 4/6   | 77       | 8/-   | DF33      | 11/-   | EF9     | 23/3  | HL42DD  |         | PL33    | 19/3     | U282   | 22/7  | X41      | 15/-     |  |
| 6AM6  | 5/6   | 6P1   | 19/3  | 12J7GT | 10/6  | 78       | 8/6   | DF66      | 15/-   | EF22    | 14/-  |         | 19/3    | PL36    | 14/4     | U301   | 23/3  | X42      | 15/-     |  |
| 6AQ5  | 8/6   | 6P25  | 12/6  | 12K5   | 17/11 | 80       | 9/-   | DF70      | 15/-   | EF36    | 6/-   | HN309   | 24/7    | PL38    | 26/6     | U329   | 14/-  | X61(C)   | 12/6     |  |
| 6AT6  | 8/6   | 6P28  | 26/6  | 12K7GT | 6/6   | 83       | 15/-  | DF91      | 6/-    | EF37A   | 8/-   | HV2     | 20/7    | PL81    | 12/6     | U339   | 16/7  | X61M     | 26/6     |  |
| 6AU6  | 10/6  | 6Q7G  | 8/-   | 12K8GT | 14/-  | 85       | 12/6  | DF96      | 9/-    | EF39    | 5/6   | HVR2A   | 6/-     | PL82    | 8/6      | U403   | 16/7  | X63      | 10/6     |  |
| 6AV6  | 12/7  | 6Q7GT   | 11/-  | 12Q7GT | 6/6   | 85A2     | 15/-  | DF97      | 9/-    | EF40    | 15/-  | KF35    | 8/6     | PL83    | 9/6      | U404   | 8/6   | X65      | 12/6     |  |
| 6B7   | 10/6  | 6R7G  | 10/-  | 12SA7  | 8/6   | 150B2    | 15/-  | DH63      | 8/-    | EF41    | 9/6   | KK32    | 21/11   | PL84    | 12/8     | U801   | 29/10 | X66      | 12/6     |  |
| 6BBG  | 4/6   | 6SA7GT  | 8/6   | 12SC7  | 8/6   | 185BT    | 33/2  | DH63(Met) |        | EF42    | 11/6  | KL35    | 8/6     | PL820   | 18/7     | UA020  | 16/7  | X76M     | 14/6     |  |
| 6BBGT | 5/-   | 6SC7  | 10/6  | 12SG7  | 8/6   | 185BTA   | 33/2  |           | 17/6   | EF50(A) | 7/-   | KL32    | 24/7    | PM2B    | 12/6     | UA8C80 |       | X78      | 21/3     |  |
| 6BA6  | 7/6   | 6SG7GT  | 8/-   | 12SH7  | 8/6   | 304      | 10/6  | DH76      | 6/6    | EF50(E) | 5/-   | K72     | 5/-     | PM12    | 6/6      |        | 9/6   | X79      | 21/3     |  |
| 6BE6  | 7/6   | 6SH7GT  | 8/-   | 12SJ7  | 8/6   | 305      | 10/6  | DH77      | 8/6    | EF54    | 5/-   | K733C   | 10/-    | PM12M   | 6/6      | UAF42  | 9/6   | X101     | 33/3     |  |
| 6BG6G | 23/3  | 6S7GT   | 8/-   | 12SK7  | 8/6   | 402Pen/A |       | DH101     | 28/6   | EF73    | 10/6  | K736    | 29/10   | PM24M   | 21/3     | UB41   | 12/-  | X109     | 17/3     |  |
| 6BH6  | 9/-   | 6S7GT   | 8/-   | 12SQ7  | 12/6  |          | 23/3  | DH107     | 13/11  | EF80    | 7/-   | K741    | 26/6    | PX4     | 26/6     | UBC41  | 8/6   | XD(1.5)  | 6/6      |  |
| 6B16  | 7/6   | 6SL7GT  | 8/-   | 12SR7  | 8/6   | 807      | 7/6   | DK32      | 21/11  | EF85    | 7/-   | K744    | 15/-    | PX25    | 59/8     | UBC81  | 11/6  | XF(1)    | 6/6      |  |
| 6BQ7A | 15/-  | 6SN7GT  | 6/6   | 12Y4   | 10/6  | 956      | 3/-   | DK40      | 21/3   | EF86    | 12/6  | K761    | 12/6    | PY31    | 16/7     | UBF80  | 9/6   | XFY34    | 17/6     |  |
| 6BR7  | 23/3  | 6SO7GT  | 9/6   | 14H7   | 23/3  | 1821     | 16/7  | DK91      | 7/6    | EF89    | 9/6   | K763    | 7/-     | PY32    | 11/6     | UBF89  | 9/6   | XHG(1.5) | 6/6      |  |
| 6BV6  | 10/6  | 6SSGT   | 8/-   | 14S7   | 27/10 | 5763     | 12/6  | DK92      | 10/6   | EF91    | 5/6   | K766    | 15/-    | PY80    | 7/-      | UBL21  | 23/3  | XHG(1.5) | 6/6      |  |
| 6BW7  | 7/6   | 6U4GT   | 12/6  | 15D1   | 26/6  | 7193     | 5/-   | DL33      | 9/6    | EF92    | 5/6   | K788    | 22/6    | PY81    | 9/6      | UCC84  | 14/7  |          | 6/6      |  |
| 6BX6  | 7/-   | 6U5G  | 7/6   | 18     | 23/3  | 7475     | 7/6   | DL66      | 15/-   | EF98    | 13/3  | KTW61   | 8/-     | PY82    | 7/-      | UCC85  | 9/-   | Y63      | 7/6      |  |
| 6C4   | 7/-   | 6U7G  | 8/6   | 19AQ5  | 10/6  |          |       | DL68      | 15/-   | EF92    | 8/6   | KTW63   | 8/-     | PY83    | 9/6      | UCF80  | 16/7  | Z63      | 10/6     |  |
| 6C5G  | 6/6   | 6V6GT   | 7/-   | 19BG6G |       |          |       | DL68      | 15/-   | EF92    | 8/6   | KTW63   | 8/-     | PY83    | 19/11    | UCH21  | 23/3  | Z66      | 20/-     |  |
| 6C6   | 6/6   | 6V6GTG  | 8/-   |        | 23/3  | 9006     | 6/-   | DL92      | 7/6    | EL32    | 5/6   | KTZ41   | 8/6     | QP21    | 7/-      | UCH42  | 9/6   | Z77      | 5/6      |  |

## NEW METAL RECTIFIERS—FULLY GUARANTEED

|        |      |      |      |       |      |        |     |      |      |          |      |      |          |     |
|--------|------|------|------|-------|------|--------|-----|------|------|----------|------|------|----------|-----|
| DRM-1B | 15/4 | RM-2 | 9/-  | WX3   | 3/6  | 14A100 | 6/6 | 27/- | 14A  | 1-2-8-2  | 17/6 | 16RE | 2-1-8-1  | 8/6 |
| DRM-2B | 16/2 | RM-3 | 9/6  | WX4   | 3/6  | 14A124 |     | 28/- | 14A  | 1-2-8-3  | 21/- | 18RA | 1-1-8-1  | 4/6 |
| DRM-3B | 23/3 | RM-4 | 16/- | WX6   | 3/6  | 14A163 |     | 38/- | 14A  | 2-1-16-1 | 21/- | 18RA | 1-1-16-1 | 6/6 |
| LW7    | 21/- | RM-5 | 19/6 | 14A86 | 17/6 | 14B130 |     | 35/- | 16RC | 1-1-16-1 | 8/6  |      |          |     |



# Stern's "fidelity" TAPE EQUIPMENT

## THE FINEST RANGE OF TAPE EQUIPMENT FOR THE HOME CONSTRUCTOR

### A SELECTION OF HIGH FIDELITY PORTABLE TAPE PREAMPLIFIERS

Adds "Hi-Fi" TAPE RECORDING TO YOUR EXISTING AUDIO INSTALLATION

IN ALL MODELS WE INCORPORATE THE TYPE "C" PREAMPLIFIER

AND OFFER IT COMPLETE IN CASE WITH . . .

- (a) The new COLLARO "STUDIO" 3 Speed Deck Deposit. £7.8.0. 12 months £2.13.6 **£36.10.0**
- (b) The COLLARO Mk. IV "Transcriptor" 3 Speed Deck Deposit. £8.6.0. 12 months £3.0.11 **£41.10.0**
- (c) The New TRUVOX Mk. VI. Tape Deck. Deposit. £8.14.0. 12 months £3.3.10 **£51.10.0**
- (d) The BRENNELL Mk. V 3 Speed Deck. Deposit. £10. months £3.15.7 **£61.0.0**
- (e) The WEARITE MODEL 4A. Tape Deck. Deposit. £12.4.0. 12 months £4.9.5.



YOU CAN BUILD A COMPLETE HIGH QUALITY RECORDER LIKE THIS for **£39.15.0**

### STERN'S MULLARD TYPE "C" TAPE PREAMPLIFIER-ERASE UNIT


INCORPORATING THE NEW FERROXUBE POT CORE PUSH-PULL OSCILLATOR and 3-SPEED TREBLE EQUALISATION by means of the latest FERROXUBE POT CORE INDUCTOR. PRICES INCLUDING SEPARATE SMALL POWER SUPPLY COMPLETE KIT **£14.0.0**

ASSEMBLED AND TESTED **£17.0.0**

Depo-it £3.8.0 and 12 months of £1.4.11.

ALSO AVAILABLE EXCLUDING POWER SUPPLY UNIT FOR **£11.15.0** and **£14.10.0**, respectively.

(Carriage and Insurance is 5/- extra). WHEN ORDERING PLEASE STATE MAKE OF TAPE DECK TO BE USED. We present this "Hi-Fi" Preamplifier strictly to Mullard's specification incorporating ONLY NEW HIGH-GRADE COMPONENTS and the SPECIFIED NEW MULLARD VALVES. It comprises a COMPLETELY SELF-CONTAINED UNIT, all components and valves being contained in a well-ventilated Box-Chassis neatly finished in Hammered Gold with a very attractively engraved PERSPEX FRONT PANEL.

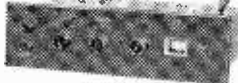

### FOR PERMANENT HIGH QUALITY INSTALLATIONS WE ALSO OFFER (excluding case)

- (a) The COLLARO Mk. IV TAPE DECK and the MULLARD TYPE "C" PREAMPLIFIER & Power Unit assembled, tested **£35.0.0**
- (b) As in (a) above but the Type "C" supplied as COMPLETE KIT OF PARTS **£32.0.0**
- (c) The TRUVOX Mk. VI TAPE DECK and the assembled Type "C" Preamplifier and Power Unit H.P. Deposit £8.0.0 and 12 months £2.18.3 **£40.0.0**
- (d) As above but the Type "C" supplied as complete KIT OF PARTS **£36.10.0**
- (e) The BRENNELL Mk. V DECK and the assembled Type "C" PREAMPLIFIER and POWER UNIT H.P. Deposit £9.4.0 and 12 months £3.7.6 **£46.0.0**
- (f) As above but the Type "C" supplied as complete KIT OF PARTS **£43.0.0**
- (g) The WEARITE 4A DECK with TYPE "C" assembled and tested H.P. Deposit. £11.4.0 and 12 months £4.2.1 **£56.0.0**

(Carriage and Insurance on above quotes 10/- extra.) PLEASE ENCLOSE S.A.E. WITH ALL CORRESPONDENCE.

**STERN RADIO LTD.**  
709 & 115 FLEET ST., LONDON, E.C.4  
Telephone: FLEET STREET 5812/3/4

### WE OFFER THIS SELECTION

- (a) The COLLARO Mk. IV TAPE DECK with the assembled and tested HF/TR3 Amplifier **£34.10.0**
- (b) As above but the HF/TR3 supplied as KIT OF PARTS **£30.15.0**
- NOTE: Messrs. Collaro when supplying the Mk. IV Deck do not wire up the Deck Switch backs. We will do this for £1 or supply a wiring diagram to the Home constructor
- (c) The TRUVOX Mk. VI TAPE DECK with the assembled and tested HF/TR3 amplifier **£39.10.0**
- (d) As above but the HF/TR3 supplied as KIT OF PARTS **£36.0.0**
- (e) The BRENNELL Mk. V DECK with the assembled and tested HF/TR3 amplifier **£45.0.0**
- (f) As above but the HF/TR3 supplied as KIT OF PARTS **£41.10.0**
- (g) THE PORTABLE CASE illustrated here (25" x 1.200ft. EMITAPE (35-), ACOS CRYSTAL MIKE (35-), ROLA 10 x 6in. LOUDSPEAKER (30-) ALL FOR **£9.0.0**

Carriage and Insurance on each above 10/- extra. WE HAVE THE NEW 2 SPEED TWIN TRACK TRUVOX Mk VI TAPE DECK IN STOCK **£26.5.0** DEPOSIT: £5.5.0 and 12 MONTHS: £1.18.6


### THE MODEL HF/TR3 TAPE AMPLIFIER

INCORPORATING 3-SPEED TREBLE EQUALISATION by means of the latest FERROXUBE POT CORE INDUCTOR.

PRICE FOR COMPLETE KIT OF PARTS **£12.15.0**

PRICE FULLY ASSEMBLED & TESTED **£16.10.0**

HIRE PURCHASE. Deposit £3.6.6 and 12 monthly payments of £1.4.2. A very high-quality Amplifier based on the very successful TYPE "A" design completed in the MULLARD LABORATORIES. ONLY NEW HIGH-GRADE COMPONENTS are incorporated including MULLARD VALVES and a GILSON OUTPUT TRANSFORMER. Other features are—Magic Eye Recording hand indicator—Selective Tone Control—Monitoring and Extension Speaker Sockets—Has own Power Supply and can be used as independent Amplifier for direct reproduction of Gram Records or from Radio Tuner. Overall size 11in. x 6in. x 6in. Can be supplied for use with Truvox—Collaro—Lane—Brenell or Motok Decks. Please specify which. Send S.A.E. for leaflet or 2/6 for complete Assembly Manual.

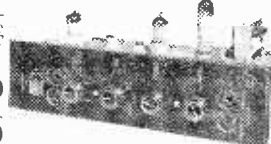

### The New B.S.R. "MONARDECK"

INCORPORATING A CORRECTLY MATCHED PREAMPLIFIER Deposit **£3.12.0** **£17.17.0** 12 months **£1.6.2.**

Designed to operate through the Pick-Up Sockets of the standard RADIO RECEIVER through which first-class results are obtained. It consists of a single speed Twin Track Tape Deck, incorporating matched Pre-amplifier, and operates at 31in. Carr. sec. speed. & ins. 10-



The equipment is supplied fully tested and completely assembled on attractive wood plinth. It can therefore be "dropped" directly into an existing Cabinet and only requires connections to the mains supply and the Pick-Up Sockets, for which purposes "floating" leads are incorporated on the Preamplifier.

# MULLARD DESIGNS


*Still by far the  
finest value*

Designed by MULLARD—presented by STERNS strictly to specification.  
COMPLETE KIT OF PARTS—
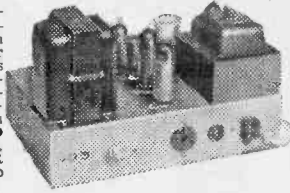
## MULLARD "5-10" MAIN AMPLIFIER

For use with the MULLARD 2-stage pre-amplifier (described below) with which an undistorted power output of up to 10 watts is obtained. This combination is thoroughly recommended to "Hi-Fi" enthusiasts who contemplate a versatile and very high quality home installation. We supply SPECIFIED COMPONENTS AND NEW MULLARD VALVES, including PARMEKO MAINS TRANSFORMER (which has extra Power available to drive Radio Tuner) and the choice of the latest Ultra-Linear PARMEKO or the PARTRIDGE Output Transformer.

PRICE COMPLETE KIT (PARMEKO) £10.0.0 Alternatively we supply ASSEMBLED and TESTED, £11.10.0.  
ABOVE INCORPORATING PARTRIDGE OUTPUT TRANSFORMER, £1.6.0 EXTRA.



## MULLARD'S PRE-AMPLIFIER TONE CONTROL UNIT

Employing two EF88 valves, and designed to operate with the MULLARD 3-3 and 5-10 MAIN AMPLIFIERS, but also perfectly suitable for other makes.

PRICE, COMPLETE KIT OF PARTS, £6.6.0 ASSEMBLED AND TESTED £8.0.0 (Carriage & Insurance, 5/- extra.)

Our kit is strictly to MULLARD'S SPECIFICATION and incorporates:

- Equalisation for the latest R.I.A.A. characteristics.
- Input for Crystal Pick-ups, and variable reluctance magnetic types.
- Input: (a) Direct from High Imp. Tape Head. (b) From a Tape Amplifier or Pre-amplifier.
- Sensitive Microphone channel.
- Wide range BASS and TREBLE Controls.





## COMPLETE MULLARD 5-10

The popular and very successful complete "5-10" Incorporating Control Unit providing up to 10 watts high quality reproduction. Input channels for high output pick-ups and all modern Radio Tuning Units only Specified Components and new MULLARD VALVES are supplied, including PARMEKO MAINS TRANSFORMER and choice of the latest PARMEKO or PARTRIDGE ULTRA-Linear Output Transformers.

Adequate power available to drive Radio Tuner. £11.10.0

Alternatively we supply ASSEMBLED and TESTED £13.10.0  
HIRE PURCHASE (Assembled Amp. only) DEPOSIT: £2.14.0.  
12 MONTHS: 19/10.

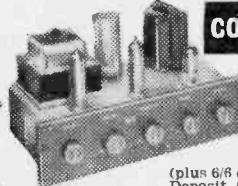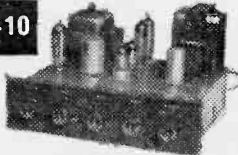ABOVE incorporating PARTRIDGE OUTPUT TRANS., £1.6.0 extra.



## COMPLETE MULLARD 3-3

THE IDEAL AMPLIFIER FOR A SMALL HIGH QUALITY INSTALLATION

COMPLETE KIT OF PARTS £7.10.0  
Alternatively supplied ASSEMBLED and FULLY TESTED £8.19.6

(plus 6/6 coverage and insurance) H.P. Terms: Deposit £2.0.0 and 8 Months at £1.0.0. Developed from the very popular 3-valve 3-watt design. Complete to MULLARD'S SPECIFICATION including Mullard valves and a PARMEKO OUTPUT TRANSFORMER.

Only new HIGH GRADE Specified Components and MULLARD VALVES are supplied.


# MULLARD — STERN STEREO DESIGNS

## DUAL "3-3" MAIN AMPLIFIER

Comprises two "3-3" MAIN AMPLIFIERS (described above) on one chassis and is designed to operate with our DUAL CHANNEL PRE-AMPLIFIER for both STEREOPHONIC or MONAURAL operation.

PRICE: COMPLETE KIT OF PARTS £10.0.0

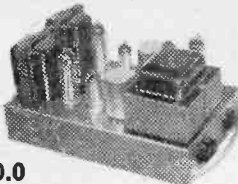Alternatively ASSEMBLED AND TESTED £11.15.0 H.P. Terms: Deposit £2-7.0 & 12 months at 17/4. Its output power is 6 watts (3 watts per channel) and together with our PRE-AMPLIFIER provides a very acceptable STEREO installation.



## DUAL CHANNEL PRE-AMPLIFIER

This model incorporates two 2-valve Pre-Amplifiers (described above) combined into a Single Unit, enabling it to be used for both STEREOPHONIC or MONAURAL operation. It is designed primarily to operate with our range of MULLARD MAIN AMPLIFIERS but will also operate equally well with any make of Amplifiers requiring an input of 250 m/volts.

COMPLETE KIT OF PARTS £12.10.0 ASSEMBLED AND TESTED £15.0.0

It will operate equally well for MONAURAL only operation with one "3-3" or one "5/10" Main Amplifier to which the second Main Amplifier can at any time be added, thus very easily providing for both STEREO or MONAURAL reproduction. Recommended combinations for STEREO operation:

- The DUAL CHANNEL PRE-AMPLIFIER together with the Dual "3-3" MAIN AMPLIFIER.
  - The DUAL CHANNEL PRE-AMPLIFIER together with two "5/10" MAIN AMPLIFIERS.
- THE ASSEMBLY MANUAL is available for 2/6.




## COMPLETE STEREO AMPLIFIER

A thoroughly recommended design that very effectively meets the many requests for a low-priced but good quality DUAL CHANNEL STEREOPHONIC AMPLIFIER. PRICE: COMPLETE KIT OF PARTS £8.10.0

ALTERNATIVELY ASSEMBLED AND TESTED £10.10.0

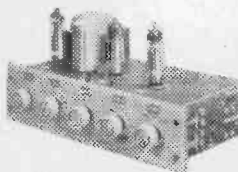Two MULLARD ECL82 Triode Pentode Valves are incorporated in the design. They form a "CLASS A" single-ended output stage in each channel. The input sensitivity is 300 m/volts, therefore when used with most STEREO Crystal Pick-Ups, or Radio Tuning Units, an output of 2 watts per channel is achieved, or similarly when switched to MONAURAL Pick-Up position a combined output of 4 watts is produced.



Please enclose S.A.E. if ILLUSTRATED and DESCRIPTIVE LEAFLETS are required... alternatively the COMPLETE ASSEMBLY MANUALS are available at 1/6 each.

# STERN RADIO LTD.

# Stern's "fidelity" TAPE RECORDERS

**BEFORE YOU BUY—HEAR THESE RECORDERS THEY ARE COMPARABLE TO THE MUCH HIGHER PRICED MODELS**

**MODEL CR3/S.** Incorporates the New **£41.00**  
COLLARO "STUDIO" TWIN TRACK 3-Speed Deck  
H.P. Terms: Deposit **£8.4.0** and 12 months of **£3.0.2.**

**MODEL CR3/T.** Incorporates the very popular 3-Speed  
COLLARO Mk. IV "TRANSCRIPTOR" Deck **£49.10.0**  
which has both upper and lower tape tracks.....  
H.P. Terms: Deposit **£9.18.0** and 12 months of **£3.12.7.**

**MODEL TR3/Mk. VI.** Incorporates the New **£49.10.0**  
TRUVOX Mk. VI TWIN TRACK 2-Speed Tape Deck .....  
H.P. Terms: Deposit **£9.18.0** and 12 months of **£3.12.7.**



Each Model incorporates the highly successful HF TR3 Amplifier (described opposite) thus ensuring truly "Hi-Fi" record and playback facilities.

All prices quoted provide for the COMPLETE RECORDER including CRYSTAL MICROPHONE and 1,200 ft. Spool of Tape.

There are no better value for money Tape Recorders on the market—if you can't call and hear them, send S.A.E. for fully descriptive leaflets.

## "MODERNISE YOUR OLD RADIOGRAM"

**IT IS CHEAPER AND BETTER VALUE TO REPLACE YOUR OLD CHASSIS AND GRAM UNIT !! RADIOGRAM CHASSIS !! !! RECORD PLAYERS !!**

**ARMSTRONG "STEREO TWELVE"..... £37.16.0**

The most complete AM FM unit yet produced for Stereo, giving 6 watts high-fidelity push-pull output on each channel, 12 watts for monaural.

**ARMSTRONG "JUBILEE"..... £29.8.0**  
An AM/FM chassis with nine valves and with push-pull output stage providing 6 watts.

**ARMSTRONG AM/FM "STEREO 44"..... £28.7.0**  
Provision is made for Stereo and monaural playback from pick-up or tape. Outputs provided for Stereo or Monaural tape recordings.

**DULCI MODEL FMT/2..... £19.17.6**  
A complete self-powered F.M. Tuner incorporating automatic frequency control.

**ARMSTRONG "S.T.3" AM/FM UNITS..... £27.6.0**  
A semi-powered high-fidelity Tuner covering full VHF, medium, and long wavebands with automatic frequency control on VHF.

**DULCI "H/T" AM/FM UNIT..... £23.15.8**  
A 4 waveband self-powered high-fidelity tuner covering the VHF, FM transmissions plus the long, medium and short wavebands.

**NEW HIRE PURCHASE TERMS** are available on all above. Illustrated leaflets available—send S.A.E.

**THE DULCI DUAL CHANNEL STEREO PREAMPLIFIERS**  
**THE "STEREO EIGHT" PREAMPLIFIER £23.2.0**  
**THE "STEREO TWO" PREAMPLIFIER..... £9.9.0**  
(Carr. and ins. 5/- extra.)

**THE LATEST MODELS ARE IN STOCK MANY AT REDUCED PRICES !!**

SEND S.A.E. FOR ILLUSTRATED LEAFLET  
**B.S.R. MONARCH UA8**  
4-speed mixer Autochanger with Crystal Pick-up  
**£6.12.6**

The NEW COLLARO MODEL R/594 4-speed Single Record Player, Studio Cartridge **£9.18.9**



The COLLARO "CONQUEST" 4-speed Autochanger, Studio Pick-up..... **£7.10.0**

The latest COLLARO "CONTINENTAL" 4-speed MIXER Autochanger Studio "O" Pick-up..... **£8.10.0**

The COLLARO 4-speed Single Record Player, Studio Pick-up..... **£6.6.0**

THE NEW B.S.R. Model UA12 is in Stock. A 4 "SPEED" MIXER AUTOCHANGER..... **£8.7.6**

UA12 also available incorporating the B.S.R. STEREO Pick-up, plays L.P. and 78 Records..... **£10.10.0**  
B.S.R. MODEL TU9 4-speed Single Record Player, complete with separate Crystal Pick-up..... **£4.4.0**  
Carriage and Insurance on each above 5/- extra.

### A SPECIAL CASH ONLY OFFER !!

This very attractive PORTABLE AMPLIFIER CASE together with a good quality GRAM AMPLIFIER and a matched P.M. SPEAKER.

ALL for ONLY **£87.6** (Plus 7/6 Carr. & Ins.)

The Amplifier consists of a 2-stage design incorporating 3 modern E.V.A. valves and has separate BASS and TREBLE CONTROLS. The Portable Case will also accommodate almost any make of Autochanger and is attractively finished in Mushroom Grey Revine.

WE ALSO SUPPLY SEPARATELY—

(a) The 2-stage (plus 1000 Hz) Rectifier) AMPLIFIER **£4.2.6** (b) The PORTABLE CARRYING CASE **£3.17.6**

(c) P.M. SPEAKER **18/9** Carriage and Insurance 4/- extra



### STERN'S MK. II "fidelity" F.M. TUNING UNIT

PRICE **£14.5.0** (Plus 5/- Carr. and Ins.)

HIRE PURCHASE: Deposit **£2.17.0** and 12 Monthly Payments of **£1.0.11.**

Incorporates the latest MULLARD PERMEABILITY TUNING HEART and the corresponding MULLARD VALVE LINE-UP. A really first-class Tuner very attractively presented and comparable to many offered at much higher prices. Power consumption is only 1.5 amps. at 6.3 volts and 25 m.a. at 250 volts.

**HOME CONSTRUCTORS! YOU CAN BUILD THIS TUNING UNIT FOR ONLY £10.10.0** (Plus 5/- Carr. & Ins.) Please send S.A.E. for fully descriptive leaflet, or the Assembly Manual is available for 1/6.



### HIGH-FIDELITY UNITS ARE ALSO IN STOCK . . . as follows:

GARRARD MODEL 301 . . . 4HP . . . TA Mk.II . . . RC98 . . . RC12 4 . . . T.P.A.12 PICK-UP . . . etc.

Send S.A.E. For Leaflet.

**NEW HIRE PURCHASE TERMS ARE AVAILABLE ON ALL EQUIPMENT VALUE £9.0.0 AND OVER.**

### SPECIAL CASH ONLY BARGAIN

A\* bulk purchase enables us to offer this very useful **INTERCOM SET OR BABY ALARM for only £5.5.0** (Plus 5/- carriage & Insurance.)

Consists of MASTER UNIT (Illustrated) and one EXTENSION, providing 2-way TALK-LISTEN facility. Complete in polished wood cases, size of each only 7 1/2 x 4 1/2 x 6 in. high.



### HOME CONSTRUCTOR

A RANGE OF "EASY TO ASSEMBLE" PREFABRICATED CABINETS

Designed by the W.B. "STENTORIAN" COMPANY for "Hi-Fi" Loudspeaker systems or to accommodate high-quality equipment. The acoustically designed Bass Reflex Cabinets containing the very successful "Stentorian" Speakers give really first-class reproduction and are well recommended. Models are also available to accommodate high-quality



Amplifiers, Preamplifiers, Tuning Units, Record Players, etc. All models are very easily assembled, in fact, only a screwdriver is required. Fully illustrated leaflets are available including complete specifications of the various STENTORIAN LOUDSPEAKERS. PLEASE ENCLOSE S.A.E. WITH ALL CORRESPONDENCE.

**109 & 115 FLEET ST., LONDON, E.C.4**

Telephone: FLEET STREET 5812/3/4

Brand new, individually  
checked and guaranteed  
**VALVES**

|           |      |       |      |           |      |          |      |          |       |       |      |        |      |         |      |        |      |
|-----------|------|-------|------|-----------|------|----------|------|----------|-------|-------|------|--------|------|---------|------|--------|------|
| AC/DD     | 2/6  | DLS10 | 4/6  | EY91      | 4/6  | OZ4A     | 5/-  | VR78     | 4/-   | 5U4G  | 5/-  | 6SC7GT | 6/-  | 39/44   | 6/-  | 956    | 2/9  |
| AC/HL     | 2/6  | E1148 | 2/-  | EZ40      | 7/-  | P61      | 2/6  | VR99     | 8/-   | 5V4   | 7/-  | 6SG7   | 5/-  | 41FP    | 1/9  | 1619   | 6/9  |
| AC/P      | 2/6  | EAS0  | 1/6  | EZ80      | 7/6  | PCC84    | 8/-  | VR105/30 | 7/6   | 5Y3GT | 6/9  | 6SH7   | 5/-  | 524G    | 8/-  | 1625   | 6/6  |
| AC/PI     | 2/6  | EAC91 | 4/6  | FA15      | 4/-  | PCC85    | 8/-  |          |       | 5Z3   | 8/6  | 6SJ7   | 6/9  | 53A     | 3/-  | 1626   | 3/6  |
| AC6/PENS/ |      | EB34  | 1/6  | FW4/500   | 8/-  | PEN25    | 4/6  | VR150/30 | 6/-   | 5Z4G  | 8/-  | 6S7G   | 6/6  | 58      | 6/-  | 1629   | 4/6  |
| AC/SP3    | 4/6  | EBC33 | 6/-  | H30       | 5/-  | PEN46    | 5/6  |          | 4/3   | 6A6   | 5/-  | 6SK7   | 5/6  | 59      | 6/-  | 4242A  | 6/6  |
| AL60      | 2/6  | EC52  | 3/9  | H63       | 3/6  | PEN65    | 6/6  | VR150/30 | 6/-   | 6AB7  | 5/-  | 6SL7GT | 6/9  | 71A     | 4/6  | 7193   | 1/9  |
| AR6       | 2/6  | EC54  | 3/6  | HP4101    | 6/-  | PEN141   | 4/6  | VS110    | 4/-   | 6AC7  | 4/3  | 6SN7GT | 4/6  | 77      | 6/-  | 7475   | 5/6  |
| AR8       | 5/-  | ECC32 | 4/-  | KBC32     | 5/-  | PEN220A  | 6/-  | VT25     | 8/6   | 6AG5  | 4/6  | 6SQ7   | 6/6  | 80      | 6/3  | 8010AR | 22/6 |
| ARRD5     | 2/-  | ECC81 | 6/-  | KF35      | 5/-  |          | 3/-  | VU111    | 3/-   | 6AG7  | 10/- | 6SR7   | 6/6  | 82      | 8/-  | 8020   | 6/-  |
| ARP3      | 3/-  | ECC82 | 6/9  | KT30      | 7/-  | PEN1340  | 6/-  | VU120    | 3/3   | 6AK6  | 7/6  | 6SS7   | 6/6  | 83      | 9/6  | 9001   | 5/-  |
| ARP4      | 3/6  | ECC83 | 7/-  | KT31      | 8/-  | PENDD/   | 3/-  | VU133A   | 3/-   | 6AK7  | 10/- | 6VG6   | 5/6  | 83V     | 12/- | 9003   | 5/6  |
| ARP12     | 2/9  | ECC84 | 7/9  | KT33C     | 7/-  | 1360     | 9/6  | W31      | 7/-   | 6AM5  | 5/-  | 6V6GT  | 6/-  | 84      | 12/6 | 9004   | 4/-  |
| ARP24     | 3/6  | ECC91 | 4/-  | KT66      | 8/-  | PL82     | 8/-  | W42      | 7/-   | 6AM6  | 6/3  | 6X5GT  | 6/6  | 89      | 6/-  | 9006   | 4/-  |
| ARP31     | 5/6  | ECL80 | 9/6  | KT241     | 9/-  | PL83     | 9/-  | Y66      | 8/-   | 6BG4  | 4/6  | 7SAZ   | 2/9  | 210FT   | 3/-  |        |      |
| SRP34     | 4/6  | EF8   | 6/-  | KTW63     | 6/-  | PMDX     | 3/-  | Z31      | 6/-   | 6B8   | 5/6  | 8D2    | 2/6  | 210VPT  | 3/-  |        |      |
| STP4      | 2/9  | EF22  | 7/3  | L30       | 4/-  | PT25H    | 7/6  | IA3      | 3/6   | 6B8B  | 2/6  | 9D2    | 3/-  | 217C    | 17/6 |        |      |
| ATP7      | 5/6  | EF32  | 5/-  | MH4       | 4/-  | PY82     | 8/-  | IA5GT    | 5/-   | 6C4   | 4/-  | 11E5   | 5/-  | 220VSG  | 3/-  |        |      |
| AU1       | 5/-  | EF36  | 3/6  | MH40      | 6/6  | QP21     | 6/-  | IB23     | 11/-  | 6C5   | 6/-  | 12A6   | 5/-  | 350B    | 8/-  |        |      |
| AW3       | 4/-  | EF39  | 4/6  | MH41      | 6/6  | QP25     | 5/3  | IB24     | 12/11 | 6C6   | 4/6  | 12AH7  | 7/-  | 393A    | 25/- |        |      |
| B30       | 3/6  | EF50  | 2/6  | MHL4      | 2/6  | R10      | 12/6 | IB26     | 11/-  | 6CBG  | 5/-  | 12AT7  | 6/6  | 446A    | 14/- |        |      |
| BL63      | 6/-  | EF52  | 5/-  | ML4       | 4/6  | RG1-240A |      | IB32     | 10/-  | 6F6   | 7/-  | 12A07  | 6/9  | 446B    | 14/- |        |      |
| D41       | 3/3  | EF54  | 3/6  | ML6       | 6/-  |          | 17/6 | 4DBGT    | 6/-   | 6FR8  | 6/6  | 12AX7  | 7/-  | 705A    | 17/6 |        |      |
| D42       | 4/-  | EF55  | 6/-  | MC/PEN    | 6/-  | RG3-250  |      | 1L4      | 3/9   | 6FI2  | 4/6  | 12CB7  | 7/6  | 715B    | 97/6 |        |      |
| D77       | 4/3  | EF70  | 4/-  | MC/PEN6A/ | 6/-  | 17/6     |      | 1LD5     | 3/6   | 6G6G  | 3/-  | 12E1   | 22/6 | 717A    | 8/6  |        |      |
| DA30      | 12/6 | EF80  | 6/9  | MS/PEN/T  | 6/-  | RG4-1250 |      | 1R5      | 6/9   | 6HG6  | 2/3  | 12H6   | 2/6  | 801     | 6/-  |        |      |
| DD41      | 4/6  | EF85  | 8/10 |           | 6/-  |          | 9/-  | 1S5      | 6/-   | 6HG7  | 1/9  | 12J5GT | 3/6  | 803     | 22/6 |        |      |
| DD620     | 4/6  | EF89  | 8/9  | N34       | 8/-  | RK34     | 2/6  | 1T4      | 4/-   | 6J5   | 3/6  | 12SC7  | 4/6  | 805     | 30/- |        |      |
| DET5      | 20/- | EF91  | 4/10 | NR15A     | 3/-  | RL37     | 3/6  | 2A3      | 8/-   | 6J6   | 4/3  | 12SG7  | 6/6  | 807AMER |      |        |      |
| DET18     | 30/- | EF92  | 5/10 | NR61      | 7/-  | SP4B     | 7/6  | 2A6      | 7/-   | 6K6GT | 6/6  | 12SH7  | 4/9  | 808BR   | 3/9  |        |      |
| DET19     | 2/6  | EL32  | 3/9  | MT37      | 6/-  | SPI3C    | 4/6  | 2A6      | 7/-   | 6K7G  | 2/3  | 12S7   | 6/-  | 813     | 70/- |        |      |
| DET20     | 2/6  | EL41  | 8/3  | (4033A)   | 14/- | SP41     | 2/6  | 2C34     | 2/6   | 6K7GT | 5/3  | 12SK7  | 5/7  | 815     | 80/- |        |      |
| DH76      | 4/9  | EL91  | 7/6  | OZ4       | 5/-  | SF61     | 2/6  | 2DA4     | 4/-   | 6K8G  | 6/6  | 12SL7  | 7/-  | 816     | 30/- |        |      |
|           |      |       |      |           |      | SU2150A  | 4/9  | 2X2      | 4/-   | 6L5G  | 6/-  | 12SR7  | 6/-  | 816     | 30/- |        |      |
|           |      |       |      |           |      | T41      | 19/- | 3A4      | 6/-   | 6L6   | 10/- | 15D2   | 6/-  | 829A    | 30/- |        |      |
|           |      |       |      |           |      | TT11     | 3/-  | 3B34     | 3/-   | 6L6G  | 6/6  | 15E    | 8/-  | 833A    | £14  |        |      |
|           |      |       |      |           |      | U18      | 3/-  | 3E29     | 6/-   | 6L6GA | 6/6  | 15R    | 7/6  | 843     | 7/6  |        |      |
|           |      |       |      |           |      | U19      | 7/-  | (829B)   | 60/-  | 6L6GA | 4/6  | 19E2   | 5/-  | 866A    | 10/- |        |      |
|           |      |       |      |           |      | UU4      | 4/6  | 3Q5GT    | 9/-   | 6N7GT | 7/-  | 28D7   | 8/-  | 827A    | 35/- |        |      |
|           |      |       |      |           |      | V2D33B   | 8/-  | 4A1      | 4/6   | 6Q7G  | 6/3  | 3T3    | 30/- | 930     | 8/-  |        |      |
|           |      |       |      |           |      | VP23     | 5/-  | 4D1      | 2/6   | 6SC7G | 5/6  | 35Z3GT | 7/-  | 954     | 2/-  |        |      |

Cathode  
Ray Tubes  
3BP1 25/-  
SCPI 42/6  
SFF7 45/-  
PG75 15/-  
VCR517 19/  
VCRX25B  
(with scanning coil) 45/-

Special Valves  
2J31 45/-  
3A/14B1 45/-  
3J/170/E £35  
3J/192/E £37.10

723AB 52/6  
726M 27/6  
ACT25 40/-  
CV691 60/-  
KR3 45/-  
VKX110 15/-  
WL417A15/-

**AND MANY OTHERS IN STOCK**

Brand new original spare parts for AR88 Receivers.  
**Tuning Mechanism** (gear), £2/10/-, post free.  
Please write your other requirements.  
**Low Resistance Headphones**, brand new, type CLR, 5/-, Balanced Armature, 7/6. P. & P. 1/-.  
**Microphone Transformers**, Balanced input 30 or 250 ohms. U.S.A. manufacture, 7/6. P. & P. 1/6.  
**813 Ceramic Valveholders**, 3/- each. P. & P. 1/6.  
**Vacuum Condenser** 32,000 V. 50 pF 15/-. Post free.  
**Modulation Transformers** (U.S.A. Collins), primary imp. 6,000 ohms. C.T., secondary 6,000 ohms, 20 W., 9/6 each. Post free.  
**Carbon Inset Microphone**, G.P.O. Type 7/6. P. & P. 1/-.  
**Telescopic Aerial Masts**, 7 sections, total 11 yards. Immediate erection. £4/10/- each or £8 per pair. Post free.  
**Light Headgear Assembly**, ideal for mobile use. Headphones 600 ohms carbon microphone, 18/- P. & P. 3/-.  
**Signal Generator Type TS. 14/AP.** 3,200-3,370 mc/s. Fully guaranteed, £85.  
**Thermo-Couple Heating Element.** 0.75 Amp in bakelite housing. Made for aerial current meters D.W.52 (G.E.C. made) or other purposes, 10/- P. & P. 1/-.  
**Avominors.** In leather case, with leads, fully tested, £5/10/-. Packing and carriage 2/6.  
**R109 Receiver.** Covering 2-8 mc/s 6 v. D.C. New and Tested, £4/5/-. Carriage paid.  
**R109A Receiver.** Covering 2-12 mc/s 6 v. D.C. New and Tested, £5/5/- Carriage paid.  
**Variometers** for W/S No. 19. Fully tested and working, 12/6. P. & P. 2/6.

All U.K. Orders below 10/-, P. & P. 1/-; over 10/-, 1/6; Orders over £2 P. & P. free.  
C.O.D. 2/- extra. Overseas Postage extra at cost.

**Block Condensers.** 0.1 mfd. 12,000 v. D.C. test, 12/-; 0.0044 mfd., 20,000 v. D.C. test, 8/-; 0.5 mfd., 8,000 v. D.C. test, 8/-; 7.5 mfd. 400 v. D.C. test, 3/-.  
**Electrolytic Can Type.** 250 mfd., 12 v. D.C. VKG, 2/6; 150 mfd. 25 v. D.C. VKG, 2/6; 8+8 mfd. (block) 450 v. D.C. VKG, 3/6.  
**Filament Transformers.** Primary 0.190-210-230-250 v., 50 C. Sec. 1 2.5 v. C.T. at 10 amps.; 2.25 v. C.T. at 10 amps.; 3 10.5 v. C.T. at 11 amps., 4,000 v. insulation. -Price £2.19.0. P. & P. 5/-. Primary 0.190-210-230-250 v., 50 C. Sec. 1 10 v. C.T. at 4.5 amps.; 2 10 v. C.T. at 4.5 amps, 4,000 v. insulation. £1.16.0. P. & P. 5/-. Primary 230 v. 50/60 c 67 v. amps. Sec. 1 6.3 v. 1.6 amps.; 2 6.3 v. C.T. 3 amps.; 3 6.3 v. C.T. 3 amps.; 3 6.3 v. C.T. 3 amps.; 4 6.3 v. C.T. 3 amps. £1.12.0. P. & P. 5/-.  
**Driver Transformers.** Primary 500 ohms imp. Sec. to match two 805 in push pull. £1.7.6. P. & P. 5/-.  
**Transformers.** Relay supply. Primary 230 v. Sec. 0.27-28-31 v. at 0.5 amps. 15/-. P. & P. 5/-.  
**I.F. TRANSFORMERS** 4.5 mc/s, American Made in black crackle finish housing, 6/- P. & P. 1/-.  
**SCR.522 Receivers** (BC624), 100-156 mc/s, including all valves, 25/- P. & P. 5/-.  
**Vibrator Unit.** 12 v./180 v. 60 mA/A. Exceedingly well filtered and smoothed, excellent for car radios. New, including one OZ4 valve and vibrator, 12/6. P. & P. 5/-.

**P. C. RADIO LTD.**  
170 GOLDHAWK RD., W.12  
SHEPHERDS BUSH 4946

**Famous U.S.A. Field Telephones** in canvas or leather case, type EEB, £9 per pair. Post free.  
**No. 62 Transmitter-Receiver.** 1.6-12 mc/s in two ranges. Ideal for mobile use. Total 11 valves. Rx—A super with separate mixer and local oscillator. Tx uses QV04-7 as power amplifier VFO or switched selected crystals. C.W., phone (grid modulation) metered for operation and valve testing. Pi output to match rod aerials or long wire. "Press to send" operation from mike. Size 8in. x 7 1/2 in. x 1 1/2 in. weighs only 29 lb. Completely self-contained with internal power unit for 12 v. operation. Power consumption 4.4 amps on send, 3.4 amps on receive. As new condition, tested, complete with operation instructions. Price, £17/10/-. Delivery included.  
**Transreceivers.** 68T mc/s together with aerial rods, microphone, H.R. headphones. Key in full working order. £6/15/-. P. & P. 5/-.  
**Complete V.F.O. Unit** from TX53. Freq. range in 4 switched bands from 1.2-17.5 Mc/s. Two V.T. 501s as oscillator and buffer, 807 as driver, two 5130s as voltage stabilizers. Output sufficient to drive two 813s in parallel. Slow motion drive directly calibrated in Mc/s. Provision for crystal control, metering of buffer and driver stage. Power requirements 400 v. and 6.3 v. D.C. Can also be used as low power transmitter. In excellent condition with valves and circuit diagram, £5. P. & P. 15/-.  
**AR88D and L.F. Receivers**, completely overhauled and tuned, £60 and £57/10/- respectively. Completely rebuilt with P.V.C. wiring, £85.  
**HRO Mains power pack**, input 115/250 v. A.C.; output 250 v., 75 mA. and 6.3 v. 3.5 amps. £3, inc. carr.

**PERSONAL CALLERS WELCOME**



INTERNATIONAL

# radio hobbies exhibition

## CQ . . . . CQ . . . . CQ



Radio Society of Great Britain

**ROYAL HORTICULTURAL OLD HALL**  
Vincent Square London SW1

Wednesday to Saturday  
**NOVEMBER 25th to 28th**

11 a.m. to 9 p.m. Admission 2/-

CQ

CQ

CQ

HOME CONSTRUCTION  
DO-IT-YOURSELF FEATURES

Kits of Parts to BUILD . . .  
*Receivers, Transmitters, Televisors,  
Hi-Fi Amplifiers, Test Gear, Tape Recorders,  
and Transistor Equipment*

**FEATURE OF WORLD'S  
COMMUNICATIONS RECEIVERS**

Six Technical Book Stands

Live Radio Station - Home Television Station

Army, Navy and Royal Air Force Displays

**£110**

**WIN A WORLD FAMOUS  
EDDYSTONE 888A  
COMMUNICATIONS RECEIVER**

Free entry form at door in exchange for this Advertisement

Further details from P. A. Thorogood G4KD 35 Gibbs Green, Edgware, Midd:esex


### Band III Converters

Suitable Wales, London, Midlands, North, Scotland etc. All the parts including 2 EP80 valves, coils, fine tuner, contrast control, condensers and resistors. (Metal case available as an extra.) Price only 19/6, plus 2/6 post and insurance. Data free with parts or available separately 1/6. Please send two more kits, the one you sent last week is performing magnificently. We receive this sort of letter every day of the week, so if you have hesitated because you thought our kits too cheap you need hesitate no longer.


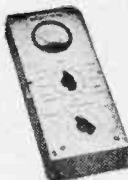
### A.C./D.C. Multimeter Kit


Ranges: D.C. volts 0-5, 0-50, 0-100, 0-500, 0-1,000. A.C. volts 0-5, 0-50, 0-100, 0-500, 0-1,000. D.C. milliamperes 0-5, 0-100, 0-500. Ohms 0-50,000 with internal batteries. 0-500,000 with external batteries. Measures A.C./D.C. volts, D.C. current and ohms. All the essential parts including metal case, 2in. moving coil meter, selected resistors, wire for shunts, range selector, switches, calibrated scale and full instructions, price 19/6, plus 2/6 post and insurance.


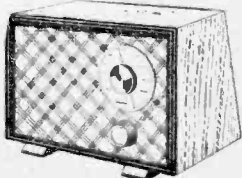
### 1960 All Mains Amplifier




Undoubtedly finest value obtainable in amplifiers—powerful three valve circuit ideal for dances, parties, etc. Complete with valves, mains transformers, volume and tone controls, but less chassis, speaker and cabinet. Price only 29/6, plus 2/6 post and ins. Data free with parts or available separately 1/6.



### New Improved Circuit for the 1960 Skysearcher

This is a three valve receiver kit using modern circuitry. Ideal as a second set for the bedroom, workshop, etc. All parts including mains transformer, valves, resistors, coils, etc., but not cabinet, chassis or speaker. 29/6, plus post and ins. 3/6. Data free with parts or available separately 1/6.

### Inductor Fluorescents

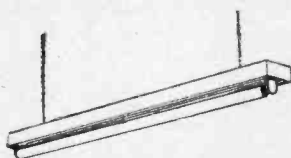

These represent today's best value in lighting. All models are complete with polyester filled chokes (so far as we know not available in any other low priced fittings), all are made from heavy gauge sheet steel stove enamelled white, all use canister type plug-in starters, and all are fitted with interference suppressors. Guaranteed for two years.

Inductor 80 for 5ft. 80 watt lamp. 39/6 plus 5/- carriage and insurance.

Inductor 40 for 4ft. 40 watt lamp. 32/6 plus 4/6 carriage and insurance.

The Three Forty for 3ft. 40 watt lamp. 31/6 plus 3/6 carriage and insurance.

Inductor 20 for 2ft. 20 watt lamp. 29/6 plus 2/6 carriage and insurance.

Circle Light for 40 watt circular lamp. 49/6 plus 3/- carriage and insurance.

Note: Prices do not include tube but these are the latest bi-pin type easily obtainable from your local electrical shop or if you wish direct from us.

SPECIAL OFFERS:  
Inductor 40 complete with tube ready to work. 39/6 plus 5/6 carriage and insurance.

Three Forty complete with tube ready to work. 39/6 plus 4/6 carriage and insurance.

### The Dulci F.M.T/2 Hi-Fidel'ity F.M. Tuner



The Tuner which includes every feature and refinement for perfect reception, reliability and simplicity of operation. An exclusive feature Automatic frequency control makes this the finest tuner available. Uses 7 valves and metal rectifier, has its own internal power supply and sockets for audio output and aerial input. Limiting on two stages provides constant output free from interference and is therefore ideal for tape recording. Engraved copper face and modern styling completes a perfect tuner. Size approx: 2 1/2in. x 3 1/2in. x 9 1/2in. Highly suitable for working with DPA10 amplifier. Price £19.17.6. H.P. terms and full technical specification on request.


### Unique Opportunity to build Fine Transistor Set



29/6, plus 2/6 post. Suitable for your own circuit or to build original circuit. All parts available at highly competitive prices. Do not miss this tremendous bargain.

Constructor's parcel: to build Pocket 6 Transistor Set as currently being sold at £17.17.0. Parcel comprises motified, two-tone cabinet as illustrated, tuning dial, two gang tuning condenser, combined bakelite chassis/printed circuit and easy-to-follow circuit. Costing value 57/6—offered while supplies last at only

### 12-Channel Turret Tuner

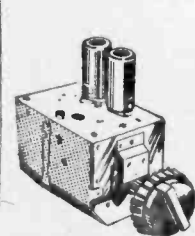

Ideal for converting an old or building into new T.V. These are brand new stock, not surplus, supplied complete with valves and coils for local Band I and Band III stations.


Model 1 I.F. Output 33 38 Mc/s series heaters (parallel heaters, 5/- extra).

Model 2 I.F. Output 16 19 Mc/s parallel heaters (series heaters, 5/- extra). With instructions and circuit diagram. 79/6, knobs 3/6 extra. Postage and insurance 2/6.

FOR ADDRESS SEE NEXT PAGE
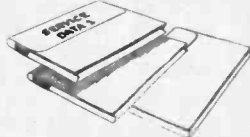
### BEGINNER'S SUPERHET

All the components including valves, metal rectifier, coils, tuning condenser, etc. etc., required to build the "Beginner's Superhet" as described in the January, 1958 issue, are available as a parcel. Price £3 plus 3/- post and insurance.




### Service Data

100 service sheets, covering British receivers which have been sold in big quantities and which every service engineer is ultimately bound to meet. The following makers are included: Acrodyne, Alba, Bush, Cossor, Ekco, Ever-Ready, Ferguson, Ferranti, G.E.C., H.M.V., Koister-Brandes, Lissen, McMichael, Marconi, Mullard, Murphy Philco, Philips, Pye, Ultra. Undoubtedly a mine of information invaluable to all who earn their living from radio servicing. Price £1 for the complete folder.
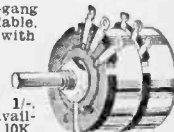
### Morganite Potentiometers


Single and 2-gang types available. Standard size with good length spindle, all new and boxed.



Single types 1/- each, values available: 5K, 10K, 25K, 50K, 100K, 250K, 1 meg., 2 meg., 5 meg.

Gang type 3/- each—values available: 5K, 5K, 100K, 100K, 1 meg., 1 meg., 2 meg., 2 meg.

### Instantus Heater

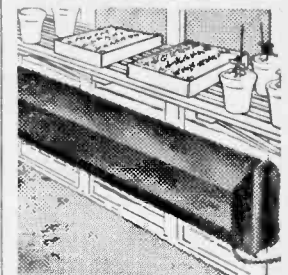

Convactor heater. Made from heavy gauge sheet steel (galvanised). For greenhouse, workshop, aviary, etc. 500 watt, £112.6; 1,000 watt, £210.0. 1,000 watt with wired but separate thermostat, £317.6. 2K watt free standing or wall mounting, £319.8; 2K watt with built-in thermostat, £419.6. Carriage and insurance 5/- per heater. ALL ARE GUARANTEED FOR 5 YEARS.

### Avo Prodclips

The advantage of these test prods is that by pressing the trigger at the side they become crocodile clips and can be left in circuit. This is a great time saver when servicing. Price 15/- Pair.



**Thermostats**




Useful for the control of appliances such as convectors, gluepots, vulcanisers, hot plates, etc. Adjustable to operate over temperature range 50-350 deg. F., fitted with heavy silver contacts. 8/6. Other types: 1 amp. 3/6; 5 amp. 8/6; 2 amp. QMB. 5/6; 15 amp. QMB. 15/-; 15 amp., enclosed wall mounting type. 29/6.

**Yaxley Switches**

|                      |        |     |
|----------------------|--------|-----|
| 1 Pole 3 way         | ... .. | 1/6 |
| 1 Pole 11 way        | ... .. | 2/6 |
| 2 Pole 2 way ceramic | ... .. | 2/6 |
| 2 Pole 4 way         | ... .. | 2/- |
| 2 Pole 6 way         | ... .. | 2/6 |
| 2 Pole 8 way         | ... .. | 3/6 |
| 2 Pole 12 way        | ... .. | 4/6 |
| 3 Pole 3 way         | ... .. | 1/6 |
| 3 Pole 6 way         | ... .. | 3/6 |
| 4 Pole 4 way         | ... .. | 3/- |
| 6 Position shorting  | ... .. | 2/6 |
| 6 Pole 3 way         | ... .. | 3/6 |
| 6 Pole 3 way ceramic | ... .. | 3/6 |
| 8 Pole 2 way         | ... .. | 2/- |
| 8 Pole 3 way         | ... .. | 2/6 |
| 12 Pole 2 way        | ... .. | 2/- |

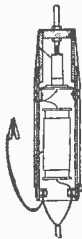**Radio Stethoscope**

This can be slipped into the pocket rather like a fountain pen. With it in most districts a receiver can be checked from the grid of the first valve right through to the output without a signal generator, the stethoscope will operate in both L.F. and H.F. circuits without alteration. It is a complete fault-finder.



All the necessary parts to make this tracer 9/6. post 1/-.

**Crystal Mike by Acos**




Model 391 this is ideal for tape or general amplifiers complete with screened lead 39/6, plus 1/- post, desk stand 2/6.

**Special This Month**

**Battery Charger Rectifier.** Selenium 12-15 v., 5 amp., 9/6.  
**Blank Metal Chassis.** All 2 1/2 in. deep from 18 gauge aluminium. Sizes: 6 in. x 2 in., 4/6; 7 1/2 in. x 5 in., 6/-; 13 1/2 in. x 9 in., 10 in. x 7 1/2 in., 7/-; 11 1/2 in. x 7 1/2 in., 8/-.  
**Metal Chassis.** Punched for Mullard 510 Amplifier, complete with inner screening sections and stove enamelled, 6/6 set.  
**Geiger Counter Tubes.** 20th Century type. Type No. C24, with circuit of geiger counter, 29/6.  
**Twin Twisted Lighting Flex.** Equivalent 14/39, rubber insulated, cotton covered, 17/6 per 100-yard coil.  
**Heavy Duty Test Prods.** Red and black with plug-in lead attachments, 8/6.  
**Filament Transformer.** 6.3 v., 1 1/2 amps., 6/6.

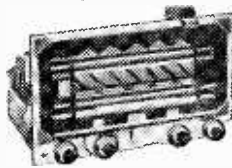**Dulci AM/FM Radiogram Chassis**

Chassis Model H.3. This has three wave-bands. F.M. 87-101 Mc/s. Medium Wave 137-540 metres and Long Wave 1,000-2,000 metres, uses 7 of the latest miniature valves and built-in ferrite aerial. Why not modernise your Radiogram, get the best from modern records with this hi-fi 4 watt output chassis? Price, £19.17.6 or £22 down and 20 fortnightly payments of £1.0.6; Hi-Fi Model H4 P.P., £27.16.6 or £22.16.6 down and 20 fortnightly payments of £1.2.0. (Note: Hire-purchase figures include insurance for 12 months.)



**Six Useful Articles**


Our 1960 catalogue now ready gives constructional hints and circuits for the following items:  
 Moisture operated switch.  
 Simple but clever signal tracer.  
 Versatile power pack costing only 10/-.  
 Instantaneous heater for workshop or den.  
 Six transistor pocket superhet.  
 Photo-flood controller.  
 Send for this catalogue to-day, price 2/6 refundable from purchases.

**Components Would Cost More**

**Car Battery Charger**—ready-made high output battery charger in stove enamelled sheet steel louvered case. New, complete and ready to work. Rated at 12 v 4 amps, and variable rate selector for trickle charging, also a meter to show charging rate. Suitable for 230/250 A.C. mains. Special snip price of 55/-, plus 3/6 post and insurance.




**£100 Worth of Equipment 19/6**

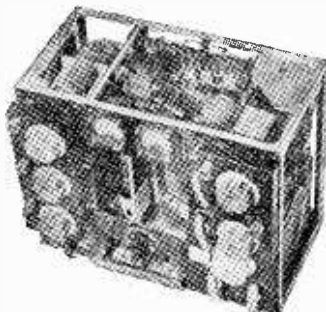

The famous R1154—unused but slightly soiled. Covers 200-500 kc/s., 3-5.5 Mc/s and 5.5-10 Mc/s. Has unique "click stop" mechanism. Wonderful breakdown value—meters, relays, switches. Complete with valves—real bargain at 19/6, plus 10/- carriage.

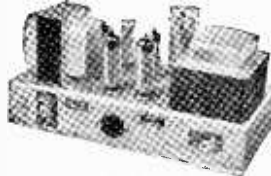**Dulci DPA10 Amplifier**

Made by the Dulci Company. It is laboratory designed, and is of the highest fidelity. It has superb reproduction and complete freedom from hum, high output sensitivity, 10 watt output and ample feedback all combined to give a truly linear output. Uses all-glass miniature valves, including two EL84s in push-pull. Price £12.12.0 or 25/- down and 26 fortnightly payments of 10/-, Carr. & Ins. 6/6.



**Special This Month**

**Moving Coil Meters:**  
 0-500 microamp, 2 1/2 in. flush ... 17/6  
 250-0-250 microamp, 2 1/2 in. surface 27/6  
 750 microamp, 2 1/2 in. surface ... 17/6  
 5-0-5 microamp, 2 1/2 in. flush ... 17/6  
 0-30 milliamp, 2 1/2 in. flush ... 17/6  
 0-100 milliamp, 2 1/2 in. flush ... 15/-  
 0-300 milliamp, 2 1/2 in. flush ... 15/-  
 0-500 milliamp, 2 1/2 in. flush ... 15/-  
 0-1 milliamp, 2 1/2 in. flush ... 25/-

**Luminous Switch.** Double pole designed for electric blankets, neon indicators glow when appliance is switched on. 10/-

**Unbreakable Mains Lead.** Type of lead fitted to electric razors makes fine lead for test meters and any other devices where subject to continuous bending. Twin figure eight construction, soft cream p.v.c. covered. Normally costs 2/- per yard. Three feet leads for 2/-.

**Metal Rectifier.** Equivalent RM5. 12/6.

**Metal Rectifier.** 60 80 mA 250 300 v., 4/6.

**Output Transformer.** Standard Pentode. 4/6. Multi ratio. 6/6.

**Bi-metal Strip.** With heavy duty contact, ideal for thermostat, fire lamp, etc., etc., 2/6.

**Neon Lamp.** Midget wire ended, ideal mains tester, etc., 2/-, ex. gov. 1/6.

**Philips Trimmers.** 0-30pF. 1 - each. 9/- doz.

**Set of 8 Allen Keys.** 3/6.

**Install those extra Points.** 3.029 twin flat T.R.S. cable. Big purchase enables us to sell this at 45/- per 100 yds. carriage 3/6.

**Low Resistance Head Phones.** Ideal crystal sets, etc., 7/6, plus 2/6.

**Goodmans Multi Ratio Output Transformer.** 6 watt. 8 ratios, from 12-1 to 72-1. Centre tapped for push pull, 7/6 plus 1/-.

**Ditto unbranded.** 6/6, post 1/-.

**Cold Cathode Valve CV413.** Voltage regulator or trigger switch—unused but ex-equipment. 2 - each.

**Tag Panels.** Ideal for constructors, experimental circuits, etc., 3 of each of 12 different types, 5/-, post 1/6.

**Syltlok Panel Mounting Fuses** with carrier, 5 amp. 2 - each, 15 amp. 2/6 each.

**Belling Lee 2BA** fully insulated terminals for mounting through metal panels 2/- each.

**Terminal Heads.** insulated 4BA, 2 - doz.

**.1 mFd. 350 v.** Small tubular metal cased condensers made by Dulliber, 2/6 doz.

**50 Assorted Resistors.** Well mixed and useful values 1 and 1/2 watt, 5 for 50.

**Ditto, but 1 watt.** 6/6 for 50.

**Mains Transformer.** Standard 230 v. input 250-0-250 at 80 mA., 6.3 v. at 5 A., 12/6.

**Toggle Switch.** Standard metal body type with round dolly, fixing ring and on/off indicating plate, 1/3 each or 12 - doz.

**Screened Cable.** Rubber covered, flexible with metal braiding, ideal for microphone or gramophone extensions, 4d. per yd., 30/- per 100 yds.

**Miniature Microphone**

American made. Dynamic type, real bargain at 2/6, plus 6d. postage.



All items advertised can be obtained from the following Companies. If ordering by post, address your order to the Company nearest to you and please include postage.

**Electronics (Ruislip) Ltd.**  
 42-46, Windmill Hill,  
 Ruislip, Middx.  
 Phone: RUISLIP 5780.  
 Half day Wednesday.

**Electronics (Croydon) Ltd.**  
 266, London Road,  
 Croydon.  
 Phone: CRO 6558.  
 Half day Wednesday.

**Electronics (Finsbury Park) Ltd.**  
 28, Stroud Green Rd.,  
 Finsbury Park, N.4.  
 Phone: ARCHWAY 1049.  
 Half day Thursday.

**Electronics (Manor Park) Ltd.**  
 520, High St., North,  
 Manor Park, E.12.





# ***BUILD YOUR OWN***

## **20,000 OHMS/VOLT**

# **MULTIMETER**

The TAYLOR MULTIMETER 127A is available, from the College, as a kit of parts with comprehensive instructions on soldering and assembly compiled by a very experienced member of the College staff.

**EASY ASSEMBLY,  
NO ADJUSTMENTS,  
NO CALIBRATION NECESSARY—**

**BUILD** these outstanding features into your meter:

Sensitivity: 20,000 ohms per volt D.C., 1,000 ohms per volt A.C., 20 Ranges.

D.C. Current:

0-50 $\mu$ A, 1mA, 10mA, 100mA, 1A.

D.C. Volts:

0-0.3, 2.5, 10, 25, 100, 250, 1000V.

A.C. Volts:

0-10, 25, 100, 250, 1000V.

3 Resistance Ranges from 0-20 Megohms (Self-contained).


*As available to our full-time students.*

*Kit of parts with full instructions —  
£7.10.0d. cash with order.*

*Factory assembled multimeter 127A  
also available — £10.0.0d. cash with order.*

*Postage and packing 3/- (U.K. only).*

*Immediate delivery, from:—*

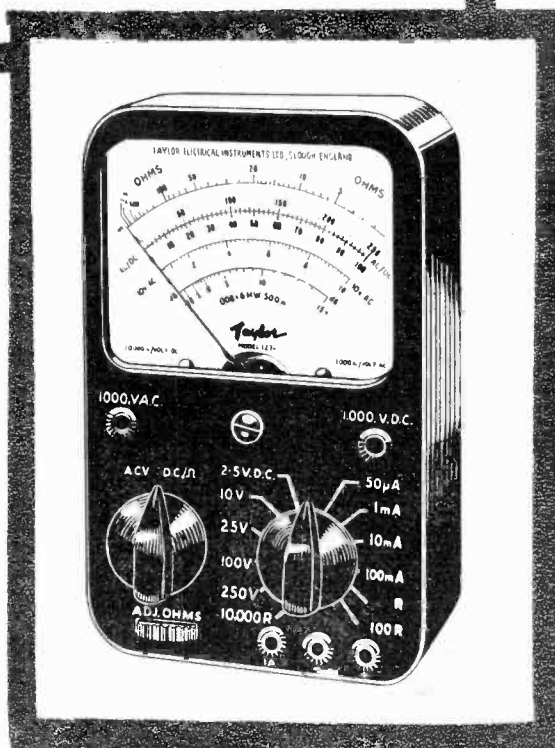

**THE PEMBRIDGE COLLEGE OF ELECTRONICS**

34a Hereford Road, London, W.2. BAYswater 9117

# RETURN-OF-POST SERVICE

## NEW ILLUSTRATED LISTS

New illustrated lists are available on all the following. Any will be sent free upon request.

**GRAMOPHONE EQUIPMENT.** Details of many types of Auto Changers, Single Record Players and Transcription Units including all the latest models. Many at special prices.

**TEST GEAR.** Test meters, Signal Generators, etc., by AVO, Jason, Pullin and Taylor.

**LOUDSPEAKERS.** Full details of Goodmans, Whiteley, Wharfedale and Elac types.

**TAPE DECKS.** All popular makes with a special offer.

**RECORDING TAPES.** A very wide range of all tapes and accessories.

## LATEST AVO TEST METERS



**AVOMETER MODEL 8.** The finest multi-range meter available. 20,000 ohms per volt on D.C. ranges. Eight D.C. Voltage ranges 2.5 v. to 2,500 v. Seven D.C. current ranges 50 microamps. to 10 amps. Seven A.C. Voltage ranges 2.5 v. to 2,500 v. Four current ranges 100 mA. to 10 amps. Three resistance ranges. Fully detailed leaflet available. Price £23.10.0. H.P. Deposit £4.14.0 and 12 monthly payments of £1.14.6. Price with leather carrying case, £27.8.0. H.P. Deposit £5.8.0 and 12 payments of £2.0.4.

Other AVO Meters available include the Model 7, £19.10.0. H.P. Deposit £3.18.0 and 12 payments of £1.3.8 and the Multimeter price £9.10.0. H.P. Deposit £1.18.0 and 12 monthly payments of 14.4.

## CRYSTAL DIODES

Brimar. GD3, GD4, GD5, GD6, GD8, 7/6.  
G.E.C. GEX34, GEX35, 4/- Surplus type, 1/3.  
Mullard. OA78, OA81, 4/-.

## TRANSISTORS

All at the new reduced prices.

**AUDIO.** B.T.H. Red Spot, 7/6; G.E.C. Yellow/Green, 7/6.  
BRIMAR. TS1, 10/-; TS2, 21/-; TS3, 13/6.  
EDISWAN. XB102, 10/-; XB104, 10/-.  
MULLARD. OC70, 14/-; OC71, 14/-.  
GOLDTOP. V10, 15A, 15/-.

**AUDIO OUTPUT.** Matched Pairs. Mullard OC72, 34/-; Ediswan XC101, 32/-.

**RF.** G.E.C. Yellow/Red, 15/-.

EDISWAN. XA101, 23/-; XA102, 26/-; XA103, 15/-; XA104, 18/-.

MULLARD. OC4, 28/-; OC45, 23/-.

All transistors post free.

## TRANSISTORISE YOUR CRYSTAL SET


A kit to construct a single transistor amplifier for any Crystal Set. Increases the volume many times. No soldering required and full instructions supplied. Complete kit with brand new Transistor, 21/6. Post free.

## VALVES

All available types by Mullard, Brimar, Mazda, G.E.C., Osram, Cossor or Emtron can be supplied. Many types have been recently reduced in price. Any type sent C.O.D. or quotation given as you prefer.

## JASON FM TUNER

FMT1

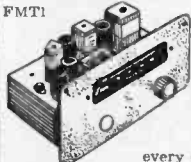


There are no less than five different Jason FM Tuner Kits now available to the Home Constructor. Brief details are given here and individual lists on any are available free.

**MOST IMPORTANT.** We take great pains to see that the kits we supply are absolutely complete in every detail and also that all components

supplied are entirely suitable in every way. This accounts for differences in price you may notice between our prices and those of some of our competitors. **THIS SHOULD BE BORNE IN MIND WHEN COMPARING PRICES.**

Hire Purchase Terms available.

FMT2 & 3

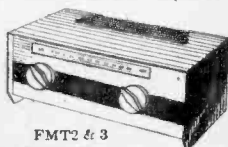

## STANDARD TUNERS

**STANDARD TUNER. FMT1.** The very popular tuner which is supplied with a chassis assembly fitted with a gold hammer finish front panel and glass dial. Employs four EF91 valves. External power supply is required. Complete Kit £8.19.6. Power pack kit, 39/-.

**STANDARD TUNER IN SHELF MOUNTING CASE. FMT2.** This is a new version of the above tuner. The circuit has been brought up to date and is built into the very attractive shelf mounting case of the new Fringe Tuner mentioned below. The circuit uses four EF80 valves and the power supply can be built into the case if desired. Complete Kit £7.17.6 without power supply components. £9.16.0 with power supply.

**MERCURY SWITCHED TUNER.** This is a tuner in chassis form which has a three position switch for the three BBC programmes. Uses one EC980 and four EF80 valves. External power supply is required. Complete Kit £9.19.0. Power Pack Kit 39/-.

## FRINGE TUNERS

**NEW FRINGE TUNER IN SHELF MOUNTING CASE. FMT3.** This is an entirely new Fringe Tuner and is supplied complete with a very attractive green shelf mounting case with Perspex dial. The tuner is fitted with variable AFC. Internal power supply if desired. Valves used are one ECC81 and five EF80. Complete Kit £9.19.6 without power supply components. £11.18.0 with power supply.

## TV SOUND FM SWITCHED TUNER

This tuner, also supplied in an attractive shelf mounting case, has a TV type Coil Turret fitted to provide TV sound from any BBC or ITV Sound channel as well as the three BBC FM programmes. Fitted with internal power supply. Valves: one ECC81, one EC980, one EF80, one EF89, one EM81 and one E78E. Complete Kit £15.15.0.

## INSTRUCTION MANUALS

All our kits include the appropriate instruction manual. All available separately as follows:— Manual covering both Standard Tuners and the new Fringe Area model, 2/10; "Mercury," 2/3; TV Sound/FM, 3/-.

All post free.

## MULLARD TAPE PRE-AMPLIFIER

This unit is intended for use with an existing amplifier and provides all the circuits necessary for tape recording and playback. Instruction manual, giving full constructional information is available price, 2/10, post free. **COMPLETE KIT** containing every item required down to the last nut and bolt. First-class items only included. £14.7.0. H.P. Deposit £2.17.0 and six monthly payments of £2.2.6. Kit less valves, £10.19.6. H.P. Deposit £1.19.6 and six payments of £1.13.4. Power Unit kit, £9.19.6.

## AMPLIFIER KITS

We carry in stock all the items needed for the following amplifiers. Fully detailed lists are available.

**MULLARD** 3-3 and 510 Amplifiers.  
Two- and Three-valve Pre-Amplifiers.  
Four Channel Mixer Unit.

**G.E.C.** 912 Plus Amplifier.

**JASON.** Jupiter and JSA2 Stereo Amplifiers.

Publications giving full details of the above are available as follows: Mullard "Circuits for Audio Amplifiers," 9/4; G.E.C. 912, 4/6; Jason Jupiter, 2/10; Jason JSA2, 2/4. All post free.

# WATTS RADIO (MAIL ORDER) LTD.

We offer a really efficient Mail Order Service on all items stocked. All cash orders are dealt with on the day of receipt. Hire Purchase orders are subject to slight delay but this is kept to the absolute minimum.

**GRAMOPHONE EQUIPMENT**

| ALL LATEST MODELS                               | Cash Price |          | Hire Purchase |         |
|---|------------|----------|---------------|---------|
|   | Price      | Deposit  | Mthly.        | Pmnts.  |
| <b>RECORD CHANGERS</b>                          |            |          |               |         |
| <b>COLLARO Conquest</b><br>(Studio O PU) ...    | £7.19. 6   | £1.12. 0 | 6 of          | £1. 4.7 |
| <b>GARRARD RC121</b><br>(GC8 PU) ...            | £9.19. 6   | £1.19. 6 | 12 of         | 15-     |
| <b>GARRARD RC88</b><br>(GC8 PU) ...             | £16. 8. 0  | £3. 6. 0 | 12 of         | £1. 4.0 |
| <b>GARRARD RC98</b><br>(GC8 PU) ...             | £18.12. 8  | £3.15. 8 | 12 of         | £1. 7.3 |
| <b>B.S.R. U48 Monarch</b><br>(TC8 PU) ...       | £7. 5. 0   | £1. 9. 0 | 6 of          | £1. 2.8 |
| <b>BSR UA12 Monarch</b><br>(TC8 PU) ...         | £9.19. 6   | £1.19. 6 | 12 of         | 15/-    |
| <b>BSR UA12 Monarch</b><br>(TC8S Stereo PU) ... | £10.17. 6  | £2. 3. 6 | 12 of         | 16/2    |
| <b>SINGLE RECORD PLAYERS</b>                    |            |          |               |         |
| <b>GARRARD RP584</b><br>(O, P or T PU) ...      | £8.10. 0   | £1.14. 0 | 12 of         | 13/-    |
| <b>BSR TU9 (TC8 PU)</b> ...                     | £4.10. 0   | £1. 5. 0 | 3 of          | £1. 5.0 |
| <b>COLLARO RP584</b><br>(O, P or T PU) ...      | £8.18.11   | £1.15.11 | 12 of         | 13/7    |
| <b>COLLARO RP594</b><br>(O, P or T PU) ...      | £9.18. 9   | £1.18. 9 | 12 of         | 15 -    |
| <b>TRANSCRIPTION UNITS</b>                      |            |          |               |         |
| <b>COLLARO 4T/200</b><br>(TX88 PU) ...          | £18.13. 0  | £3.15. 0 | 12 of         | £1. 7.4 |
| <b>COLLARO 4TR/200</b><br>Motor only ...        | £12.18. 3  | £2.15. 3 | 12 of         | £1. 0.5 |
| <b>GARRARD 4HF</b><br>(GC8 PU) ...              | £18. 9. 9  | £3.15. 9 | 12 of         | £1. 7.0 |

Many of the above can be supplied for stereo working. See our Gramophone Equipment List for details.

**GRAMOPHONE STYLI**

AC08, GP15, GP25, GP27, GP29, GP59, GP61, HCP33, HGP35, HCP37, HGP39, HGP41, HGP45, HGP55, HGP57, HGP63. All 6/8 each.  
 B.S.R. TC3, TC8, TC8S. All 5/9 each.  
 DECCA. XMS. 14-  
 GARRARD. G02, GC8, 5 7 - TOM1, TOM2, 17.11, Miniature Magnetic, 7-  
 HI-FI PU, 12 1  
 IMPORTANT.—Please state Std. or LP when ordering.

**STEREO PICK-UP CARTRIDGES**

**RONETTE DC284.** For all Collaro Models to replace the Studio Cartridge. Turn-over for 78LP/Stereo. £3.19.6.  
**B.S.R. TC8S.** Will replace the TC8H or TC8M in any Monarch Changer. Plays 78LP/Stereo records. £3.6.0.

**LOUDSPEAKERS**

| GOODMANS              | Cash Price |         | Hire Purchase |        |
|-----------------------|------------|---------|---------------|--------|
|                       | Price      | Deposit | Mthly.        | Pmnts. |
| New Axiom 110 10"     | £5. 0.0    | £1.10.0 | 3 of          | £1.6.8 |
| New Axiom 112 10"     | £5.10.0    | £1.14.0 | 6 of          | £1.6.0 |
| Axiom 300 12"         | £11. 5.9   | £2. 5.9 | 12 of         | 16.8   |
| Axiom 400 12"         | £16. 1.0   | £3. 4.0 | 12 of         | £1.3.7 |
| Axiette 8"            | £6.12.0    | £1. 6.0 | 6 of          | £1.1.0 |
| Trebax Tweeter        | £6. 4.0    | £1. 4.0 | 6 of          | £1.0.0 |
| N05000 Crossover Unit | £1.19.0    | —       | —             | —      |
| <b>WHITELEY</b>       |            |         |               |        |
| HF1016 10"            | £7.12.3    | £1.10.3 | 6 of          | £1.3.8 |
| HF1012 10"            | £4.10.0    | £1.10.0 | 3 of          | £1.5.0 |
| HF816 8"              | £6.10.6    | £1. 6.6 | 6 of          | £1.0.8 |
| HF817 8"              | £10.18.6   | £2. 3.6 | 12 of         | 16.1   |
| TS16 Cone Tweeter     | £3. 3.9    | £1. 3.9 | 6 of          | £1.0.0 |
| T10 Tweeter           | £4. 4.0    | £1. 4.0 | 3 of          | £1.3.4 |
| T359 Cone Tweeter     | £1.13.3    | —       | —             | —      |
| Crossover CX3000      | £1.10.0    | —       | —             | —      |
| Crossover CX1500      | £1.18.3    | —       | —             | —      |

Other Goodmans and Whiteley Speakers available, also full Wharfedale range.

**CATHODE-RAY TUBES**

**BRAND NEW STOCK. NOT REBUILDS. 12 MONTHS' GUARANTEE**  
 We can supply all BVA branded tubes at the new reduced prices. This includes Brimar, Cossor, Emiscope, Emित्रon, Ferranti, G.E.C. Mazda and Mullard. Full list of all available types sent on request.  
**MULLARD.** 12in. and 14in. types. £10.10.0. H.P. Deposit £2.2.0 and 12 monthly payments of 15.8. 17in. Types (except MW43/43) £12.0.0. H.P. Deposit £2.8.0 and 12 payments of 17.8. 17in. MW43/43 £14.0.0. H.P. Deposit £2.16.0 and 12 payments of £1.0.8. 21in. Types £18.0.0. H.P. Deposit £3.12.0 and 12 payments of £1.6.6.  
 All tubes sent carriage free and safe delivery guaranteed.

**LATEST CABY TEST METERS**

Now in stock. CABY SUPREME MULTI-RANGE METERS. Made abroad. We can confidently recommend these meters as being accurate, well made and very good value for money.

**MODEL A-10.** Sensitivity 2,000 ohms per volt A.C. and D.C. Five voltage ranges 10-1,000 volts A.C. and D.C. Three D.C. current ranges 5-250 ma. Two resistance ranges. Size 5 1/2 in. x 3 1/2 in. Price, £4.17.6. H.P. Deposit £1.7.6 and three monthly payments of £1.6.8.



**MODEL B-20.** Sensitivity 4,000 ohms per volt A.C. and D.C. Voltage ranges—Five D.C. 10-1,000 volts. Four A.C. 10-1,000 volts. Four D.C. current ranges. 5-250 ma. Four resistance ranges. Price £6.10.0. H.P. Deposit £2 and three monthly payments of £1.13.4.

Illustrated leaflet giving full details of both models free upon request.

**RECORDING TAPE**

**DOUBLE PLAY**  
**BASE.** 300ft. (3in.), 14"; 600ft. (3in.), 25"; 1,200ft. (5in.), 42"; 1,800ft. (5in.), 52 1/2"; 2,400ft. (7in.), 77.6.  
**SCOTCH BOY 200.** 400ft. (3in.), 17"; 1,200ft. (5in.), 45/-; 2,400ft. (7in.), 80/-.  
**FLIPFLIP NIKEN.** 1,200ft. (5in.). In plastic container. 35/-; 2,400ft., 72/6.

**LONG PLAY**  
**RA.** f. 1,200ft. (3in.), 9"; 850ft. (5in.), 28 -; 1,200ft. (5in.), 35/-; 1,800ft. (7in.), 50 -.  
**EMITAPE 99.** 250ft. (3in.), 9/6; 850ft. (5in.) 28 -. In Emicase, 30/6. 1,200ft. (5in.), 35/-. In Emicase, 37/6. 1,800ft. (7in.), 50 -. In Emicase, 52/6. 2,400ft. (8in.), 72/6.

**GELONO.** 430ft. (3in.), 16 -.  
**GRUNDIG.** 1,200ft. (5in.), 35/-; 1,800ft. (7in.), 50/-.  
**MSS.** 225ft. (3in.), 9/6; 450ft. (4in.), 14/6; 850ft. (5in.), 28/-; 1,200ft. (5in.), 35/-; 1,800ft. (7in.), 50/-; 2,400ft. (8in.), 70 -.  
**PHILIPS.** 850ft. (5in.). In plastic container, 28/-; 1,800ft. (7in.), 50/-.  
**SCOTCH BOY 150.** 300ft. (3in.), 9/6; 900 ft. (5in.), 28 -; 1,275ft. (5in.), 35/-; 1,800ft. (7in.), 50/-.  
**SPECIAL OFFER.** 1,200ft. Standard Tape. Brand new. Famous maker. Fully guaranteed, 25/-, Four for 95/-.  
 Full range of standard tape and accessories also stocked. Send for list. All tape post free.

**TRIPLE TONE AMPLIFIERS**

We particularly recommend the Tripletone ready-built Amplifiers. The performance is very good, construction excellent and they represent excellent value for money.

**HI-FI MAJOR.** Push-Pull stage gives 12 watt output. Separate tone controls for Treble, Middle and Bass. Input for Microphone. Frequency response 15-20,000 cycles.

Price £15.18.9d. H.P. Deposit £3.3.9 and 12 monthly payments of £1.3.5.

**POPULAR.** Three valve amplifier giving three watts output. Separate tone controls for Bass, Middle and Top. Price, £6.19.6. H.P. Deposit £1.0.6 and six monthly payments of £1.3.2.

**HIRE PURCHASE**

H.P. Terms are available on any item. Repayments may be spread over 3, 6 or 12 months. Details as follows: Three months; Deposit 6/- in the £. Service charge 5%, but minimum charge 10/-. Six and Twelve months; Deposit 4/- in the £. Service charge 10%, but minimum charge 20/-.

**Terms of Business.**—Cash with order or C.O.D. Postage extra under £3. We charge C.O.D. orders as follows. Up to £3. postage and C.O.D. fee minimum 2/8. Over £3 and under £5. C.O.D. fee only 1/6. Over £5 no charge.

54 CHURCH STREET, WEYBRIDGE, SURREY.

Telephone: Weybridge 4556

PLEASE NOTE: POSTAL BUSINESS ONLY FROM THIS ADDRESS.

## R.S.C. HI-FI TAPE RECORDER KIT

**REALISM AT INCREDIBLY LOW COST. CAN BE ASSEMBLED IN 1 HOUR**  
The Recorder incorporates the Latest Collaro Mark IV Tape Transcriber listed £25. The Linear LT45 High Quality Tape Amplifier listed £12.12.0. High Flux P.M. Speaker listed 30/-, empty Tape Spool, a Reel of Best Quality L.P. Tape (850ft.) listed 28/6, and a Handsome Portable carrying Cabinet finished in veneered walnut, size 18in. x 13in. x 9in. high, listed £4 10.0. and circuit. Total cost if purchased individually over £45. Performance equal to units in the £80-£90 class.


**29/2 GNS. U.P. TERMS.** Deposit 17/6. Carr. 3 gns. and 12 monthly payments 53/9.

## R.S.C. A8 HIGH FIDELITY 12 WATT AMPLIFIER

Ultra Linear Push-Pull Amplifier with "Built-in" Tone Control. Pre-amp stages, high sensitivity. Includes 5 valves (8H) outputs. High Quality sectionally wound output transformer, specially designed for Ultra Linear operation, and reliable small condensers of current manufacture. **INDIVIDUAL CONTROLS FOR BASS AND TREBLE** "Lift" and "Cut." Frequency response +3 db. 30-30,000 c/c. Six negative feedback loops. Hum level 71 db. down. ONLY 70 millivolts INPUT required for FULL OUTPUT. Suitable for use with all makes and types of pick-ups and practically all microphones. Comparable with the very best designs.

**For STANDING or LONG - PLAYING RECORDS.** For **MUSICAL INSTRUMENTS** such as **STRING BASS, GUITARS, etc.** **OUTPUT SOCKET** with plug provides 300 v. 33 mA. and 6.3 v. 1.5A. For supply of a **RADIO FEEDER UNIT.** Size approx. 12-7 1/2 in. For A.C. mains 230-250 v. 50 c/c. Outputs for 3 and 15 ohm speakers. Kit is complete to last nut. Chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied. Unapproachable value, at £7 15/- or factory built 45/- extra. Carriage 10/-  
If required louvered metal cover with 2

**£7-15-0**

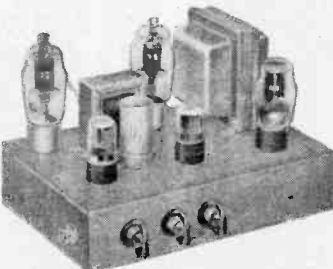

carrying handles can be supplied for 18/9. Additional input sockets, with associate Vol. control so that two different inputs such as Gram and 'Mike' or Tape and Radio can be mixed, can be provided for 13/- extra. Guaranteed 12 months.  
**TERMS** on assembled two input model: **DEPOSIT** 18/9 and 12 monthly payments, 18/9.  
**HIGH FIDELITY MICROPHONES and SPEAKERS** in stock. Keep cash prices or credit terms if supplied with amplifier.

**ACOS CRYSTAL 'MIKE' INSERTS.** Approx. 1in. square. Ply lead connections. Only 5/11 each. Brand New.

**PICK-UP ARMS** complete with Hi-Fi turnover crystal head. Acos GP54. Limited number brand new, perfect, at approx. half price. Only 35/9.

**ACOS CRYSTAL MICROPHONES.** Type 33-1, hand or desk. List price 53/-, Brand new, cartoned, 35/9.  
39-1 Stick type, list price 5 gns. Brand new, 39/6.

### EXTENSION SPEAKERS

Ready for use in walnut veneered cabinet.  
6 1/2 in. 2-3 ohms. 29/11.  
8 in. 2-3 ohms. 35/9.  
10 in. 2-3 ohms. 58/9.  
Very limited number.



**10 WATT AMPLIFIERS.** Unused and in good order but slightly store soiled. For 200-250 v. A.C. mains input. Output for 15 ohm speaker. Inputs for "mike" and Gram. Limited number, complete with Mullard valves. Only £6.15.0 carr. 5/-.

## R.S.C. MAINS TRANSFORMERS ( FULLY GUARANTEED )

Interleaved and Impregnated. Primaries 200-250 v. 50 c/s. **SCRATCHED TOP SHROUDED DROP THROUGH**  
250-0-250 v. 70 mA. 6.3 v. 2a. 5v. 2a. ... 16/9  
350-0-350 v. 80 mA. 6.3 v. 2a. 5v. 2a. ... 18/9  
250-0-250 v. 100 mA. 6.3 v. 4a. 5v. 3a. ... 23/9  
300-0-300 v. 100 mA. 6.3 v. 4a. 5v. 3a. ... 23/9  
350-0-350 v. 100 mA. 6.3 v. 4a. 5v. 3a. ... 23/9  
350-0-350 v. 100 mA. 6.3 v. 4a. 4a. C.T. ... 23/9  
0-4-5 v. 3a. ... 23/9  
350-0-350 v. 150 mA. 6.3 v. 4a. 5v. 3a. ... 29/9  
**FULLY SHROUDED UPRIGHT**  
250-0-250 v. 60 mA. 6.3 v. 2a. 5v. 2a. ... 17/6  
Midjet type 21-3 in. 4a. 5v. 3a. ... 26/9  
300-0-300 v. 100 mA. 6.3 v. 4a. 5v. 3a. ... 26/9  
350-0-350 v. 100 mA. 6.3 v. 4a. 5v. 3a. ... 26/9  
300-0-300 v. 139 mA. 6.3 v. 4a. 6.3 v. 1a. ... 35/9  
For Mullard 510 Amplifier ... 35/9  
350-0-350 v. 150 mA. 6.3 v. 4a. 5v. 3a. ... 33/9  
350-0-350 v. 150 mA. 6.3 v. 2a. 6.3 v. 2a. 5v. 3a. ... 35/9  
425-0-425 v. 200 mA. 6.3 v. 4a. C.T. ... 48/9  
6.3 v. 4a. C.T. 5 v. 3a. Suitable Williamson Amplifier, etc. ... 48/9

## COSSOR VHF/FM RADIO RECEIVER KITS

Including 6 valves, Printed Circuit and Goodman's 10" x 6" Elliptical Speaker. Made to retail at 15 GNS. Limited  
number at **£8-19-6**

## A SIX TRANSISTOR "POCKET" SUPERHET RADIO

All parts including Transistors Printed Circuit. Attractive Cream or Coloured Plastic case. Ferrite aerial. 2 1/2 in. P.M. Speaker, etc., etc. and full instruction booklet. Size 5 1/2 x 3 1/4 in. completed. Long and Medium Wavebands 250 M.W. push-pull output. Demonstrated at our counter premises.  
**£9.19.6**

## R.S.C. BATTERY TO MAINS CONVERSION UNITS

Type BM1. An all-dry battery eliminator. Size 5 1/2 x 4 1/2 in. approx. Completely replaces battery supplying 1.4 v. and 90 v. where A.C. mains 200-250 v. 50 c/s is available. Suitable for all battery portable receivers requiring 1.4 v. and 90 v. This includes latest low consumption types. Complete kit with diagrams. 39/9. or ready to use, 48/9.



Type BM2. Size 8 x 5 1/2 x 2 1/2 in. Supplies 120v. 90 v. and 60 v., 40 mA. and 2 v. 0.4 a. to 1 amp. fully smoothed. Thereby completely replacing both H.T. batteries and L.T. accumulators when connected to A.C. mains supply 200-250 v. 50 c/s. **SUITABLE FOR ALL BATTERY RECEIVERS.**  
VERS normally uses 2 v. accumulator. Complete kit of parts with diagrams and instructions. 49/9. or ready for use, 59/6.

### ELIMINATOR TRANSFORMERS

Primaries 200-250 v. 50 c/s.  
120 v. 40 mA. 5-0-5 v. 1a. ... 15/9  
130 v. 15 mA. 4-0-4 v. 100 mA. ... 9/9

### SMOOTHING CHOKES

150 mA. 7.10 H 250 ohms. ... 11/9  
100 mA. 10 H 200 ohms. ... 8/9  
80 mA. 10 H 350 ohms. ... 8/9  
60 mA. 10 H 400 ohms. ... 4/11

### CHARGER TRANSFORMERS

All with 200-230-250 v. 50 c/s Primaries:  
0-9-15 v. 1 1/2 a. 11/9. 0-9-15 v. 3 a. 16/9.  
0-9-15 v. 5 a. 19/9. 0-9-15 v. 6 a. 23/9.

### AUTO TRANSFORMERS. 50 watt

0-110-115-230/250 v. 8/11 each.

### COLIARO CONQUEST 4-SPEED AUTO-CHANGER with high fidelity

Studio pick-up. Latest model. Brand new. Cartoned. For 200-250 v. 50 c/s. A.C. mains. Our price £7.19.6. Carr. 5/6.

### GARRARD 4-SPEED AUTO-CHANGERS

Type R.C.120H. Very limited number at 9 gns. (approx. half price). Carr. 5/6.



**R.S.C. A12 STEREOPHONIC AMPLIFIER KIT**

A complete set of parts to construct a Stereo amplifier with an undistorted output total 6 watts. For A.C. mains input of 200-250 v. Outputs for matched 2-3 ohm speakers. Sensitivity 130 m.v. Ganged Vol. and Tone Controls. Preset balance control. Full instructions and point-to-point wiring diagrams supplied. Only good quality Carr. and pkg. 5-components and latest high grade valves used. Exceptionally realistic reproduction can be obtained at ample volume for the home, as can be demonstrated in typical surroundings at our County Area premises. A really sensational offer.

**£3-19-6**

**STEREO EQUIPMENT OFFER.**  
Comprising A12 Kit, 2 matched 8in. L/Speakers, and Acos T70 Stereo head with diamond stylus suitable most pick-ups.

**£6-19-6**

Carr. 7/6

**LINEAR L145 HIGH QUALITY TAPE DECK AMPLIFIER.** With "built in" power pack and oscillator. Ready for stage. For Tape Decks Use ONLY with High or Low Impedance, Playback and Erase Heads, such as Lane, Truvox, Collaro, Brennel, Carr. 7/6 etc. For A.C. Mains 230-250 v. 50 c/s. Linear frequency response of +3 db. 50-11,000 c/s. Negative feedback equalisation for 31, 74 and 151in. per sec. Output 4 watts. Send S.A.E. for leaflet.

**12 GNS.**

**R.S.C. 30 WATT ULTRA LINEAR HIGH FIDELITY AMPLIFIER A10**

A highly sensitive Push-Pull high output unit with self-contained Pre-amp. Tone Control Stages. Certified performance figures compare equally with most expensive amplifiers available. Hum level 70 db. down. Frequency response ±3 db. 30-30,000 c/s. A specially designed sectionally wound ultra linear output transformer is used with 807 output valves. All components are chosen for reliability. Six valves are used, EF86, EF86, ECC83, 807, 807, GZ33. Separate Bass and Treble Controls are provided. Minimum input required for full output is only 12 millivolts that A.C. KIND OF MICROPHONE OR PICK-UP IS SUITABLE. The unit is designed for CLUBS, SCHOOLS, THEATRES, DANCE HALLS OF OUTDOOR FUNCTIONS, etc. For use with Electronic ORGAN, GUITAR, STRING BASS, etc. For standard or long-playing records. OUTPUT SOCKET PROVIDING L.T. and H.T. for a RADIO FEEDER UNIT. An extra input with associated vol. control is provided so that two separate inputs such as Gram and 'Mike' can be mixed. Amplifier operates on 200-250 v. 50 c/s. A.C. Mains and has output for 5 and 15 ohm speakers. Complete kit of parts with fully punched chassis and point-to-point wiring diagrams and instructions. If required cover as for A8 can be supplied for 18/9. The amplifier can be supplied, factory built with 12 months' guarantee, for £13.19.6. TERMS: DEPOSIT 24/9 and 12 monthly payments of 24/9.

**11 GNS.**

Carr. 10/-

**LINEAR 'DIATONIC' 10-14 WATT HIGH FIDELITY PUSH-PULL ULTRA LINEAR AMPLIFIER.** For 200-250 v. A.C. mains. Valves ECC83, ECC83, EL84, EL84, EZ81. Self-contained Pre-amp Tone Control stage. Separate Bass and Treble Controls. Independent 'Mike' and Gram input sockets. Outputs for 3 and 15 ohm speakers. Only 12 c/s. Or Deposit 22/3 plus 10/- carr. and 12 monthly payments of 22/3. Send S.A.E. for leaflet.

**LINEAR 150 50 WATT P.A. AMPLIFIER.** High quality and sensitivity. 19 GNS. Send S.A.E. for leaflet.

**GARRARD 4-SPEED AUTO-CHANGERS.** Type RC120H. Very limited number at only 9 gns. (approx. half price). Carr. 5/6.

**R.S.C. 3-4 WATT A7 HIGH-GAIN AMPLIFIER.** For 200/250 v. 50 c/s. Mains input. Appearance and Specification, with exception of output wattage, as A5 amplifier. Complete kit with diagrams. £3.15.0. Carr. 3/6.

**R.S.C. BRADFORD, MANCHESTER and LEEDS**

(Leeds) Ltd.

**LINEAR L45 MINIATURE 4/5 WATT QUALITY AMPLIFIER.** Suitable for use with any record playing unit, and most microphones. Negative feedback 12 db. Separate Bass and Treble Controls. For A.C. mains input of 200-250 v. 50 c/s. Output for 2-3 ohm speaker. Three miniature Mullard valves used. Size of unit only 6-5-5 1/2 in. High. Guaranteed for 12 months. Only £5/19/6. Send S.A.E. for illustrated leaflet. Terms. Deposit 22/6 and 5 monthly payments of 22/6.

**R.S.C. 4-5 WATT A5 HIGH-GAIN AMPLIFIER**

A highly-sensitive 4-valve quality amplifier for the home, small club, etc. Only 50 millivolts input is required for full output so that it is suitable for use with the latest high fidelity pick-up heads, in addition to all other types of pick-ups and practically all 'mikes'. Separate Bass and Treble Controls are provided. These give full long-playing record equalisation. Hum level is negligible being 70db. down. 15 db. of negative feedback is used. H.T. of 300 v. 25 mA. and L.T. of 6.3 v. 1.5 a. is available for the supply of a Radio Feeder Unit, or Tape-Deck pre-amplifier. For A.C. mains input of 200-230-250 v. 50 c/s. Output for 2-3 ohm speaker. Chassis is not alive. Kit is complete in every detail and includes fully punched chassis (with baseplate) with blue banner finish and point-to-point wiring diagrams and instructions. Exceptional value at only £3/15/-, or assembled ready for use 25/- extra, plus 3/6 carr.; or Deposit 22/6 and 5 monthly payments of 22/6 for assembled unit.

**R.S.C. PORTABLE GUITAR AMPLIFIERS**

**Junior 5 watts High quality output.** Separate Bass and Treble 'Cut' and 'Boost' controls. Sensitivity 15 m.v.; High Flux 8in. Loudspeaker 'built-in'. Handsome, strongly made Cabinet (size approx. 14 x 14 x 7in.) finished in satin walnut, and fitted carrying handle. **£8-19-6** Carr. 7/6

**Senior 10 watts High Fidelity output.** Separate Bass and Treble 'Cut' and 'Boost' controls. Twin separately controlled high gain inputs so that two instruments such as Guitar and String Bass can be used at the same time. Two loudspeakers are incorporated, a High Flux 12 in. for Bass notes and a 7 x 4 m. elliptical for Treble. Cabinet is well made and finished satin walnut. Size approx. 18 x 18 x 8 in. H.T. Terms. Deposit 23/6 and 12 monthly payments of 23/6. Both models for 200-250 v. A.C. mains. **13 GNS.** Carr. 10/-

**12in. 10 WATT HIGH QUALITY LOUD-SPEAKERS IN POLISHED WALNUT FINISHED CABINET**

Gauss 12,000 lines. Speech coil 3 ohms or 15 ohms. Only £4.19.6. Carr. 5/-

and 9 monthly payments of 11/-


**12 in. 20 WATT HI-FI LOUD-SPEAKERS IN CABINETS.** Size 18 x 18 x 8 in. Finish as above. Terms. Deposit 13/10 and 12 monthly payments of 13/10. Only £7.19.6. Carr. 8/6.

**COLLARO 4-SPEED SINGLE PLAYER.** Separate pick-up (GP54). Only £3.15.0. Twin sapphire stylus. 200-250 v. A.C. mains.

TERMS: C.W.O. or C.O.D. No C.O.D. under £1. Post 1/9 extra under £2; 2/9 extra under £5. Open 9 to 6. Weds. until 1 p.m. Trade supplied. S.A.E. with all enquiries.

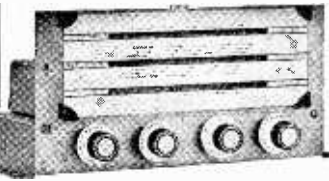**AM/FM RADIOGRAM CHASSIS HIGH QUALITY 6-8 WATT PUSH-PULL OUTPUT**

For 200-250 v. Mains. Long wave, Medium, F.M. and Gram. Complete with 8 B.V.A. valves. Guaranteed 12 months. Only 29 GNS. Or Deposit £2.12.0 and 9 monthly payments of £2.12.0.



**PLESSEY DUAL CONCENTRIC 12in. 15 ohms HIGH FIDELITY SPEAKER**

(12,000 lines) with built-in tweeter (completely separate elliptical speaker with choke, condensers, etc.), providing extraordinarily realistic reproduction when used with our A8 or similar amplifier. Rated 10 watts. Price only £5/17/6.

**ACOS Hi-Fi Crystal Cartridges.** Turn-over type with sapphire stylus. HGP59 Standard replacement for Garrard and B.S.R. Only 19/9. B.S.R. Ful-fi. 17/9. Garrard GC2. 19/9.

**COLLARO Mk. III 15 GNS. 3-SPEED TAPE TRANSCRIPTORS**

Limited number brand new cartoned. Carr. 7/6

**P.M. SPEAKERS.** 2-3 ohm. 2 1/2 in. Perdio 25/9. 5in. 17/9. 6in. 16/9. 8in. 19/9. 8 x 5in. 25/9. 10in. 26/9. 10 x 6in. 29/9. 12in. 29/11. 10in. W.T. 29/11. 3 or 15 ohms type HF1012 10 watt hi-fidelity type. Recommended for use with our A8 Amplifier. 4 gns. 12in. Plessey 3 ohms 10 watts (12,000 lines). 59/6.

**TWEETERS.** Plessey 3 ohms 19 9. Rola-Celestion 7.5 ohms 25/9.

**LG3 MINIATURE 2-3 WATT GRAM AMPLIFIER.** For use with any single or auto-change unit. Output for 2-3 ohm speaker. For 200-250 v. 50 c/s. A.C. mains. Over-all size 6 1/2 x 4 1/2 x 2 1/2 in. Controls: Vol. and Tone with switch. Guaranteed 12 months. Only 57/9.

**SUPREMET FEEDER UNIT.** Design of a high quality Radio Taper Unit (especially suitable for use with any of our Amplifiers). Delayed A.V.C. employed. The W.Ch. Sw. incorporates Gram position. Controls are Tuning, W.Ch. and Vol. only 25/6. 15 mA. H.T. and L.T. of 6.3 v. 1 amp. required from amplifier. Size of unit approx. 9-6-7in. high. Simple alignment procedure. Point-to-Point wiring diagrams, instructions and printed parts list with illustration. 2/6. Total building cost £4.15/-. For descriptive leaflet send S.A.E.

**E.M.I. 4-SPEED SINGLE RECORD PLAYER UNITS** with turn-over crystal head for Stereo and Monaural. Only £7.15/-, carr. 4/6.


Mail Orders to 29-31 Moorfield Rd., Leeds 12. Callers to 5 and 7 County (Mecca) Arcade, Briggate, Leeds 1, and 8-10 Brown St. (Market St.), Manchester 2, or 56, Morley Street, (Next to Majestic Ballroom) Bradford.

# Here are some new models



**F.M. TUNER**  
£13.12.6

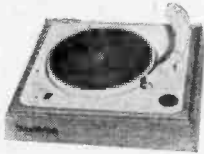**R.F. TUNING UNIT and I.F. AMPLIFIER AVAILABLE SEPARATELY**



**RP-1U**  
£12.10.0

**TRANSCRIPTION RECORD PLAYER.** Embodies new Collaro RP594 unit with the Ronette Stereo Pick-up. Gives excellent results on stereo or mono. (33, 45 L.P. or 78 r.p.m.) discs. Detachable head and supplied with wooden plinth.

**THE 'COTSWOLD.'** An acoustically designed 3-unit Speaker System capable of doing justice to finest programme sources. Range 30-20,000 c/s. All parts left "in the white" for finish to personal taste.

**THE "GLOUCESTER"** cabinet has been specially designed to meet the varying needs of different homes. Mk. I houses Record Player Stereo Amplifier, F.M. Tuner and records, etc. The Mk. II will house a Tape Deck in addition.



## "PACKAGED DEALS"

The above models and others, can be obtained as parts of "packaged deals" of **MATCHED STEREO HI-FI EQUIPMENT**, thereby saving you additional money.



**THE "COTSWOLD"**  
£19.18.6



**THE "GLOUCESTER"**  
Mk. I £15.18.6  
Mk. II £17.8.6

**FREE DELIVERY IN U.K. DEFERRED TERMS AVAILABLE OVER £10.**

## Why not send for Free Catalogue!

Other models include

**TRANSISTOR PORTABLE** model UXR-1. This dual-wave, 6 transistor portable radio, strikingly styled in handsome solid leather case, is universally admired. The tone is rich and brilliant and it performs well everywhere, including in a car. Easily built in 6 hours..... **£15.18.6**

**TRANSISTOR JUNIOR RADIO** model UJR-1. Ideal for youngsters. Novel circuit gets lots of stations..... **£2.16.6**  
(Additional amplifier stage, 16/6 extra)

**HI-FI 16 W. STEREO AMPLIFIER** model S-88. World's finest 16 Watt Stereo amplifier regardless of price. 0.1% distortion at 6 W./chnl. The attractively styled S-88 has many excellent features ..... **£25. 5.6**

**HI-FI 6 W. STEREO AMPLIFIER** model S-33. World's best value in low-price Stereo. 0.3% distortion at 2.5 W./chnl. Ideal for average room..... **£11. 8.0**

**HI-FI SPEAKER SYSTEM** model SSU-1. Ideal for Stereo in average living-room where cost must be low. Two speakers in the enclosure..... **£10. 5.6**  
(Legs, £1.7.0 extra)

**R/C BRIDGE** model C-3U. Measures Capacitance, 10 pF (0.00001 µF) to 1,000 µF; Power Factor; Resistance, 100Ω to 5 MΩ and indicates leakage. Automatic Discharge Safety-Switch ..... **£7.19.6**

**AUDIO SIGNAL GENERATOR** model AG-9U. 10 c/s to 100 Kc/s. Sine-wave output 10 V. f.s.d. down to 3 mV. f.s.d. Less than 0.1% distortion (20 c/s to 20 Kc/s). Decade frequency selection. Decibel ranges, -60 to +22. 1% precision resistors ..... **£19. 3.0**

**VALVE VOLTMETER** model V-7A. World's most popular VVM. Measures volts, ohms and decibels. Sensitivity 7,333,333 ohms per Volt ..... **£13. 0.0**

**5 in. OSCILLOSCOPE** model O-12U. This fine general-purpose 'scope has "Y" sensitivity of 10 mV/cm, and covers 3 c/s to over 5 Mc/s. Rise time is 0.08 µ secs or less. Timebase 10 c/s to 500 Kc/s in 5 steps. Electronically stabilised. Voltage calibrator ..... **£34.15.0**

**DIRECT READING CAPACITANCE METER** model CM-1U. 4½ in. meter scale calibrated in µF and pF. Full scale deflection 100 micro-microfarads, 1,000 micro-microfarad, 0.01 microfarad, 0.1 microfarad ..... **£14.10.0**

**DX-100U AMATEUR TRANSMITTER.** The most popular Amateur transmitter in the world. 100-140 watts output. 160, 80, 40, 20, 15 or 10 metres..... **£78.10.0**

**DX-40U AMATEUR TRANSMITTER.** 40 Watts to aerial. 75 W. C.W., 60 W. pk. C.C. 'phone. Provision for V.F.O. Designed by "Hams" for "Hams" ..... **£29.10.0**

Without obligation please send me **FREE CATALOGUE (Yes/No)**.....

Full details of model(s)..... **Deferred Payments (Yes/No)**.....

**NAME**  
(BLOCK CAPITALS) .....

**ADDRESS**.....

**DAYSTROM LTD., DEPT. PW. 12, GLOUCESTER, ENGLAND**

A member of the Daystrom Group, manufacturers of  
**THE LARGEST-SELLING ELECTRONIC KITS IN THE WORLD.**

# Practical Wireless

VOL. XXXV, No. 634, DECEMBER 1959

Editorial and Advertisement  
Offices:

**PRACTICAL WIRELESS**

George Newnes, Ltd., Tower House,  
Southampton Street, Strand, W.C.2.

©George Newnes Ltd., 1959.

Phone: Temple Bar 4363.

Telegram: Newnes, Rand, London.  
Registered at the G.P.O. for trans-  
mission by Canadian Magazine Post.

## SUBSCRIPTION RATES

including postage for one year

Inland - - - - £1.3.0. per annum

Abroad - - - - £1.1.6. per annum

Canada - - - - 19s. per annum

## Contents

|  | Page |
|--|------|
| Editorial .....  | 637  |
| Round the World of Wireless .....                        | 638  |
| Miniature Audio Test Oscil-<br>lator .....               | 640  |
| 27Mc/s Pocket Transmitter .....                          | 641  |
| Beginners' Test Meter .....                              | 643  |
| Amateur Radio for Beginners<br>Selecting Resistors ..... | 647  |
| On Your Wavelength .....                                 | 651  |
| Improving Superhets .....                                | 653  |
| Experimental "Super" Transis-<br>tor Receiver .....      | 654  |
| Simple B.F.O. ....                                       | 659  |
| Choosing Resistors .....                                 | 661  |
| Mains 3-Valver .....                                     | 662  |
| A Charger and D.C. Unit .....                            | 664  |
| A Stereo Amplifier .....                                 | 668  |
| A Transistorised 'N' Circuit .....                       | 673  |
| A Transistor Pre-amp .....                               | 677  |
| Caravan and Car Radio Cir-<br>cuits .....                | 681  |
| News from the Clubs .....                                | 682  |
| Open to Discussion .....                                 | 686  |
|  | 690  |

The Editor will be pleased to consider articles of a practical nature. Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor PRACTICAL WIRELESS, George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in PRACTICAL WIRELESS is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. PRACTICAL WIRELESS incorporates "Amateur Wireless."

## INTERFERENCE

WHEN radio broadcasting first began, the problem of mutual interference of stations did not arise. Initially there were only one or two stations operating and these for only short periods of the day, and therefore even with somewhat crude receiver circuits it was always possible to ensure that good reception of all of the stations could be obtained. The novelty of radio as a medium of entertainment did not disappear for some years and reception of any sort of radio signal was tended to be regarded as a great achievement.

This is no longer true; radio today has established itself as a means of recreation and learning. Now that there are several hundreds of broadcasting stations operating in Europe alone, many on identical wavelengths, the quality of the reception is marred. The situation is worse in the evening on the most used wavelengths which lie in the medium waveband. The BBC has done much to improve the enjoyment of its programmes by building chains of transmitters operating with frequency modulation in the V.H.F. bands. This policy has definitely improved the status of sound radio in this country, but while clear reception of the BBC by most of the community has thus been assured, little has been done to alleviate conditions on the medium and long wavebands.

Many listeners enjoy broadcasts from abroad; there are, for instance, concerts and performances of operas and other items of cultural interest for which the barrier of languages does not exist. However, in the evenings, when most of the interesting broadcasts are given, the mutual interference on these wavebands completely spoils listening enjoyment.

Obviously the solution employed for improving local broadcasts in this and other countries is of no use where foreign broadcasts are concerned. Frequencies of the order of 80 Mc/s can only be used for comparatively short range transmissions. Thus the overcrowding on the medium and long wavebands can only be remedied by closer control of the frequencies used and the number of stations operating.

### THE "P.W." AND "P.T." FILM SHOW

WE are pleased to announce that another film show, sponsored by this journal and our companion journal *Practical Television*, is to be held at Caxton Hall, Westminster, on Friday, January 22nd, 1960, at 7.30 p.m., when the Editor will take the chair. Admission will be by ticket only. The event is being arranged in conjunction with Mullard Limited.

The films are entitled "Mirror in the Sky," "From Us to View" and "Photo Emission." "Mirror in the Sky" deals with events leading up to the experiments by Sir Edward Appleton to confirm the existence of the Heaviside Layer. It continues with the discovery of the Appleton Layer and the subsequent development of the pulse techniques that became the basis of radar. The film concludes with a description of further developments in this field up to the introduction of the radiotelescope.

Applications for tickets should be made now. Please mark your envelopes "Caxton Hall" in the top left-hand corner, and include a stamped addressed envelope for the tickets.

Our next issue, dated January, 1960, will be published on December 4th

# Round the World of Wireless

## POTENTIAL AND CURRENT NEWS

### Broadcast Receiving Licences

THE following statement shows the approximate number of Broadcast Receiving Licences in force at the end of August, 1959, in respect of wireless receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland. The numbers include licences issued to blind persons without payment.

| Region                           | Total     |
|----------------------------------|-----------|
| London Postal ... ..             | 876,799   |
| Home Counties ... ..             | 872,844   |
| Midland ... ..                   | 645,621   |
| North Eastern ... ..             | 740,630   |
| North Western ... ..             | 593,581   |
| South Western ... ..             | 520,656   |
| Wales and Border Counties ... .. | 320,022   |
| Total England and Wales ... ..   | 4,570,153 |
| Scotland ... ..                  | 554,735   |
| Northern Ireland ... ..          | 156,693   |
| Grand Total ... ..               | 5,281,581 |

### Linear Accelerator for Australian Hospital

A FOUR million electron-volt linear accelerator for X-ray treatment of deep-seated tumours is being built in this country by Mullard Equipment Ltd. for the Cancer Institute Board of Victoria. Valued at £60,000 it will be installed at the board's Peter MacCallum Clinic in Melbourne in the middle of next year. This is the fourth medical linear accelerator to be built by the Company. The accelerator will give an X-ray output more than ten times greater than that of a normal, 250kV therapy machine, and will enable treatments to be given at the rate of 60 a day—about three times the number possible with the conventional apparatus. The high voltage rating of the accelerator also produces an X-ray beam of greater penetration, making it possible to reach tumours seated too deep for effective treatment with conventional machines. Damage to the patient's skin, which can be a serious problem when low-voltage X-rays are used, is virtually eliminated, and there is less side-scattering of the beam during its passage through the body. The accelerator is



The aerial head of the Marconi long range and terminal area surveillance radar system now operating at Jersey Airport. This new radar will fulfill the dual role of airways surveillance and approach control. Operating on a 50cm. wavelength it is virtually unaffected by weather.

mounted on a rotatable gantry, which enables the X-ray beam to be directed precisely to the diseased area and at exactly the required angle.

### Berec in East Africa

BEREC INTERNATIONAL LTD., the Exports Sales Division of The Ever Ready Company (Great Britain) Ltd., have made radio history in East Africa by the inauguration of the first-time commercial sponsored radio programme produced in East Africa for their battery products. The programme, which features the famous and popular "Jambo Band" is being heard each Friday evening at 6.30 p.m. on the National programmes of the Kenya Broadcasting Service which covers the whole of Kenya and other parts of East Africa. The programme is scheduled to continue until April, 1960, and further extensions of the plan are envisaged, which will create even greater interest as it is Berec's desire not only to effect bigger and better sales of their products in East Africa, but also to provide the best in entertainment for all radio listeners.

### New BBC Publication

THE BBC have recently published No. 26 in their series of Engineering Monographs entitled "Transistor Amplifiers for Sound Broadcasting." The

author is Mr. S. D. Berry, Associate I.E.E., of the Designs Department BBC Engineering Division. It deals with the application of transistors to the audio-frequency amplifiers used in sound broadcasting, for which a high standard of performance is required. The principles followed in the design of such amplifiers are discussed and five examples of various types are described and illustrated together with performance details. The operating conditions of D.C. feedback pairs and of "super-alpha" pairs are analysed and some numerical evaluations given. Finally, some conclusions are drawn regarding the use of transistors in high-performance amplifiers of this nature. BBC Engineering Monograph No. 26 can be obtained, price 5/- post free, from BBC Publications, 35, Marylebone High Street, London, W.1, or through newsagents and book-sellers.

### Hungarian Radio

HUNGARY'S radio services are developing more links with foreign stations. Western stations are mainly interested in recordings of works by Kodály, Bartók and contemporary Hungarian composers. The American C.B.S. recently broadcast Hungarian recordings of Bartók's "Duke Bluebeards Castle" and Kodály's "Székely Spinnery." The BBC has asked to hear

recordings of a recently discovered Haydn opera "L'Infidelta delusa" which was performed during the 75th anniversary celebrations of the Hungarian State Opera House. Radio programmes are exchanged regularly with most of the socialist countries, including China and the national stations of 11 Soviet republics. Programmes are also being exchanged with the Japanese State Radio and with radio stations in India, Ghana and Iraq. Though most foreign stations are mainly interested in taking musical programmes, one Canadian station has asked for details of Hungarian radio games.

#### Industrial Maser

A MASER amplifier, thought to be the first working assembly to be built in this country by an industrial laboratory, came into operation recently at Mullard Research Laboratories, Salfords, Surrey. Construction of the Maser and investigation of its properties and performance has been carried out in the Laboratories' Solid State Physics Division where considerable work on semiconductor effects at low temperatures is being done by a group of scientists led by Dr. J. C. Walling. Maser amplifiers are a recent scientific development which make use of the natural oscillations of the paramagnetic ions in certain crystalline substances—ruby for example. One of their chief uses lies in their ability to give useful amplification of very weak radio signals without producing unwanted signals which would otherwise swamp them. The Mullard Maser, which was constructed in co-operation with the Royal Radar Establishment, Malvern, operates at a wavelength of 10 cm in the "S" band and at a temperature of 1.7°K (approximately -271 deg. Centigrade).

#### British Clock for Australia

A CLOCK which will not gain or lose more than a second in 25 years is to be installed in the Australian Post Office Research Laboratories at Melbourne by a team of British Scientists. The clock, known as an ammonia maser has been constructed at the Ministry of

Supply Signals Research and Development Establishment, Christchurch, Hants, and is accurate to within one ten thousandth of a second per day and will be the first of its kind in the Southern Hemisphere. One job for which the maser will be used is the measurement of the rate at which electric pulses sent out by a radio transmitter near Rugby are received in Melbourne, some 15,000 miles away. Although the transmitting rate is constant the pulses are not received at a constant rate, owing to variations in the ionosphere, the radio "mirror" which surrounds the earth. The maser will be used to measure these variations, providing more information about the ionosphere.

#### Largest Recording Club

THE British Recording Club, 145, Fleet Street, London, E.C.4, has now, by agreement, absorbed the British Tape Recording Society and in future the full name of the organisation will be "The British Recording Club Incorporating the British Tape Recording Society." This makes the B.R.C. the largest organisation of its kind in the world with direct links with thirty-six countries. This is a milestone in the tape club move-

ment and starts a new era of unified co-operation to further the interests of tape enthusiasts and users everywhere.

#### UNESCO Study

RECENTLY published by UNESCO is a study entitled "Broadcasting without Barriers" which reviews the state of broadcasting throughout the world. Its author is Mr. George A. Coddling who has worked for the international telecommunication union in Geneva and is now assistant professor of political science at the University of Pennsylvania U.S.A.

Mr. Coddling traces the development of broadcasting and shows its varied role as a medium of information and entertainment. The author also describes the different ways in which broadcasting is controlled and relates in detail the long history of the ITU's effort to secure agreement on the distribution of frequencies of broadcasting.

In a foreword to the book, UNESCO points out that "uncertainty within governments and among radio broadcasters themselves prompted the conclusion that a study on an international scale would be of help to those concerned."



The use of two-way radio communication systems is increasing rapidly. An unusual application is illustrated above. Walter H. Malcolm, haulage contractors, of Renfrewshire, have had their Chaseside loading shovel fitted with a two-way radio. Head office maintains constant contact with the operator who can be instructed to move quickly from site to site to deal with urgent loading.



# Audio Test Oscillator

A ONE-TRANSISTOR CIRCUIT

By A. M. Shafford

**T**HIS audio oscillator has its own power supplies and is small enough to slip into a pocket. Naturally in so small a space, only a simple circuit is possible, and therefore the unit is designed to operate on a single fixed frequency. However, if a small increase in size is acceptable, the addition of a few extra components will permit the selection of any one of a number of fixed frequencies over quite a wide range.

## Uses

Some obvious uses for the unit include the checking of amplifiers (including the audio sections of radio and TV receivers); as a morse-code practice oscillator; as a source for an A.C. bridge or, in conjunction with a pair of head-


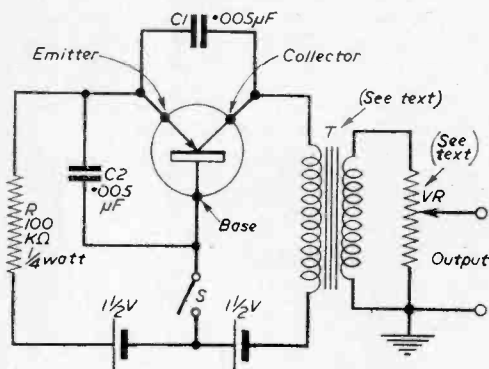


Fig. 1.—Circuit for a fixed frequency

phones, as a continuity checking device. Many other applications will suggest themselves, once the unit has been constructed and some experience gained in handling it. The great merit of this oscillator, apart from its small size, is the fact that it is always ready for use at the turn of a switch since its single transistor requires no warm-up time and oscillation commences immediately the internal batteries are applied. Furthermore, the output leads with their crocodile-clip terminations are permanently soldered into the circuit making it unnecessary to search for pieces of wire to connect up the unit before making a test.

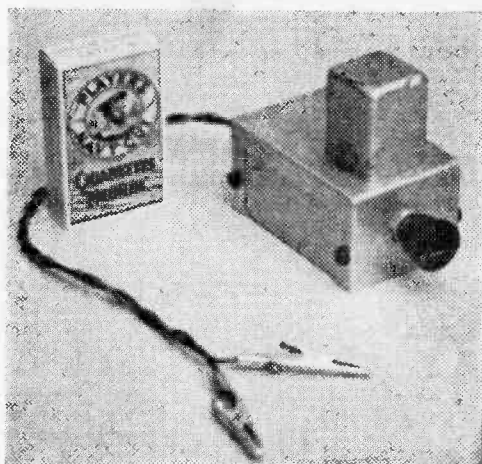The cost of the unit is small, even if all the components have to be purchased, although most junk boxes will provide everything that is needed with the possible exception of the transistor.



A completed oscillator

## Size

The illustration shows the construction and small size of the unit built by the writer, but since there is nothing critical in either the component values or the layout, the constructor can make up the circuit in any convenient form to suit his requirements. No part of the circuit operates at a voltage above 3, and therefore no insulation problems arise and no special precautions need be taken in arranging the spacing between components.

The circuit of the oscillator is shown in Fig. 1. It is powered by two 1½ penlight cells connected in series, and the base of the transistor is connected to the junction of the two batteries through the on/off switch which is part of the output control potentiometer VR.

## Components

The transformer is not very critical. The one used in the model illustrated is a blocking oscillator transformer, but any audio transformer will suffice. Most suitable would be an interstage transformer with a ratio of about 2:1 or 3:1, the winding with the smallest number of turns being used as the output side. A miniature loudspeaker transformer will operate quite successfully, but the large turns-ratio results in a loss of output owing to the step-down action. Since the oscillator develops only a few millivolts of audio, this step-down may be undesirable. However, when the unit is used to test an audio amplifier, very small outputs are required.

For a given transformer the frequency can be controlled by varying C2. Quite a range can be

(Continued on page 685)


### COMPONENT VALUES FOR FIG. 1

- C1—0.005 μF.
- C2—0.005 μF.
- R—100,000 ohms ¼ watt.
- VR—See Text.
- T—See Text.
- S—On Off switch (on output level control).

# 27 Mc/s Pocket Transmitter

A SHORT-RANGE UNIT OPERATING FROM BATTERIES

By F. Gray

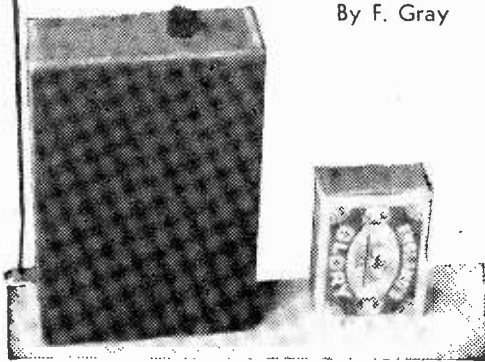

**T**HIS transmitter was made for indoor or other short-range work, and is self-contained, with batteries. For short distances, with a sensitive receiver, the usual type of one-valve model control transmitter has ample output. Indeed, adequate control can often be maintained with a very low H.T. voltage. These facts have been responsible for the pocket transmitter described here, which uses a single B7G output valve, with 45V H.T. supply from two 22½V deaf-aid type batteries. As a result, the whole unit, with H.T. and filament batteries, can be accommodated in a case of which the inside dimensions are only 4in × 2½in. × 1in.

### Consumption

The H.T. drain is about 8mA, this current only being taken when the transmitter is actually keyed to radiate. The filament current is 0.1A, from a single dry cell, also required intermittently for a few seconds only, when keying. The batteries will thus have quite a long life.

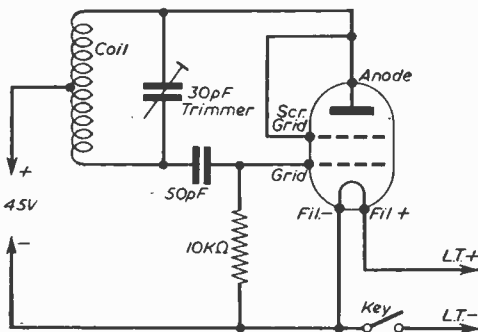


Fig. 1.—Circuit diagram.

The output from the transmitter is not sufficient for the control of a model at range. It is primarily intended for the radio control of a broadcast receiver (station selection and volume) but will also control models at short range. If the actuator or control device in the model requires rapid keying, then a filament switch will have to be provided in the transmitter, and the keying contacts will then be wired in the H.T. circuit.

With a purpose in view such as that previously mentioned, rapid keying is not necessary. Wiring the key contacts in the filament circuit then has the advantage that the transmitter filament is also off, when the transmitter is not in use, and no operation of a separate filament switch is required.

Other output valves than that shown are equally suitable. The holder being wired for the actual type fitted. Suggested valves include the 3S4, DL92, N17, CV820, 3V4, CV783, and similar battery output tetrodes or pentodes.

### Building Details

If 3/16in. ply is used for the case, two pieces will be required 1in. × 2½in.; two 1in. × 4½in., and two 2½in. × 4½in. Wood of this thickness can be secured with small panel pins, glue being smeared on meeting surfaces first. Four small screws hold the back in place.

The transmitter circuit is shown in Fig. 1, the valve being triode connected. Figs. 2 and 3 show the layout, wiring, and valvholder and coil details. Insulated leads are best attached to the holder

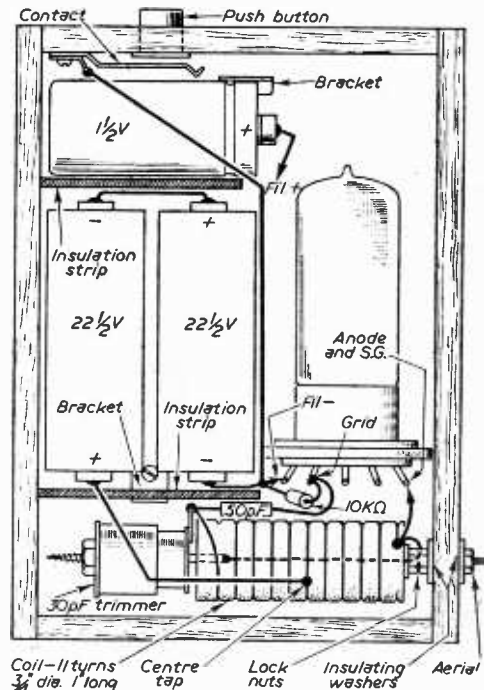


Fig. 2.—Layout of the parts.

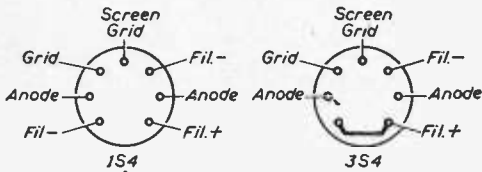


Fig. 3.—Valve base details.


tags before fitting the holder, and sufficient space should be left above the valve for its removal.

The batteries are held in place by brackets and each other, but leads are secured to them with a touch of solder. This avoids any trouble from poor contact, and the batteries only need renewing after a long interval.

To save space, the beehive trimmer has its centre leg soldered to a long 6BA bolt, which passes down through the coil. To bring the transmitter on to frequency, this trimmer can be rotated a little at a time with the fingers. (This is not recommended with larger H.T. voltages.) The alternative is to cut a small "spanner" from paxolin, unless there is no objection to drilling a clearance hole in the side of the case for the usual trimming tool.

For short-range control, with a sensitive receiver, no aerial need be used. But for longer range, or a less sensitive receiver, a short vertical rod can be added. This can be some 6in. to 9in. or more, according to the purpose in view. Very long aerials will stop oscillation.

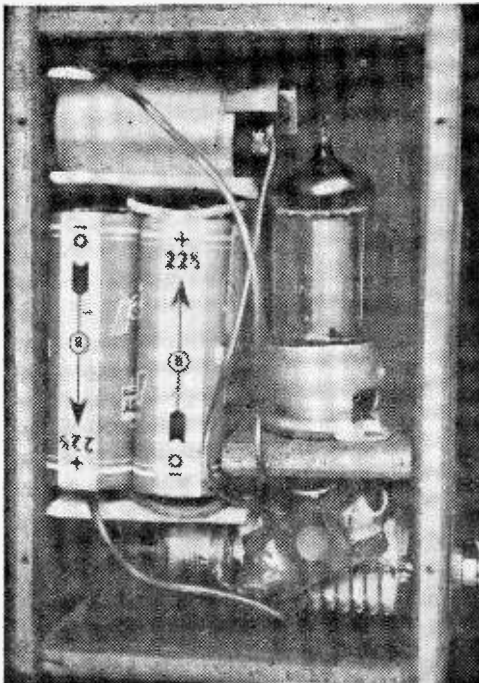The transmitter must be tuned to frequency with the actual aerial which will be used, because



Internal view (see Fig. 2).

### COMPONENTS LIST

Valve: 3S4, D192, N17, CV820, 3V4, CV783 or a similar battery output tetrode or pentode.  
Resistor: 10k  $\frac{1}{2}$ W.  
Condensers: 30pF trimmer.  
50pF ceramic or mica.  
Battery: Two 22 $\frac{1}{2}$ V deaf-aid types in series.

changing the aerial will slightly modify the frequency.

### Tuning Procedure

The output is not sufficient to give an indication with a bulb meter. However, the frequency meter circuit shown in Fig. 4 is satisfactory, and this unit can easily be made up. With the meter coil in line with the transmitter coil, and about 1in. away, a reading of about 1mA may be expected. The frequency meter is tuned to the middle of the 27Mc/s band, and the transmitter trimmer is then rotated for maximum reading on the meter. If the fingers are used for tuning, remove the hand well away between adjustments, and check that no change is required to the frequency meter tuning, for maximum reading.

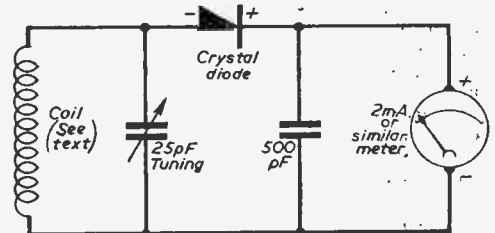


Fig. 4.—Simple frequency meter circuit.

It is possible to use a bulb meter if this has a low voltage, low current bulb, and if a higher battery voltage is temporarily used with the transmitter. If this method is chosen, a H.T. current check should be made to see that the maximum rating of the valve is not exceeded. No modification must be made to the aerial after tuning and, for these reasons, the circuit in Fig. 4 will be more convenient.

### CHRISTMAS GIFT FOR RADIO ENTHUSIASTS

Send them **PRACTICAL WIRELESS**, of course. A year's subscription will bring them a reminder of your good wishes every month throughout 1960 . . . and all through the year they'll thank you for the interest and help it contains.

Simply send your friends' names and addresses, together with your own and remittance\* to cover each subscription, to The Subscription Manager (G.2), "Practical Wireless," Tower House, Southampton Street, London, W.C.2. An attractive Christmas Greetings Card will be sent in your name to announce each gift.

\* RATES (INCLUDING POSTAGE) FOR ONE YEAR (12 ISSUES):—U.K. £1.3.0, OVERSEAS £1.1.6, CANADA £0.19.0, U.S.A. \$3.00.

# Beginners' Test-Meter

## No. 4—MAKING THE SHUNTS AND USING THE NEW CURRENT RANGES By E. V. KING

**B**EFORE the wiring of the current ranges can be carried out, it is necessary to check the basic (1mA) range of the meter. It is assumed that the wiring given last month has been carried out and that the voltage ranges are working correctly. Turn the range switch to position 6. Here is the test procedure: do not depart from it unless you are experienced or you will suffer the loss of the meter movement. Clip the positive crocodile clip to the short (positive) tag of  $4\frac{1}{2}$ V flat battery. Now clip the negative crocodile on to one end of a 10,000 ohm resistor, and very gently and quickly flick the free end of the resistor on to the long tag of the battery. The meter will move. While testing verify that the needle does not go right over to the stop. If it does something is amiss and it must be found before proceeding. If the needle moves to about half way over, all is well. If a 9,000 ohm resistor of good accuracy is used instead of the 10,000 the result will be almost exactly  $\frac{1}{2}$ mA flowing. Fig. 18 shows the circuit used.

### Accuracy

This range, i.e., 1mA, uses the basic meter movement and its accuracy (and all others too) is dependent on the movement and will probably be about 2 per cent. In this respect the longer the scale, the better and the human element in viewing becomes less. A mirror scale, of course, makes accurate readings easier.

### The 10mA Shunt

The making and accurate wiring in of the shunts is the hardest part of this multi-meter construction: the accuracy of the finished meter will depend on the care with which the job has been done.


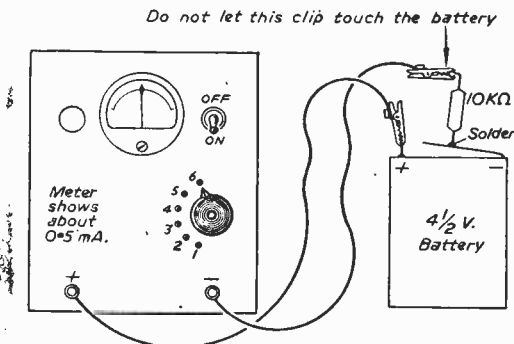


Fig. 18.—Procedure for testing the 1mA range.

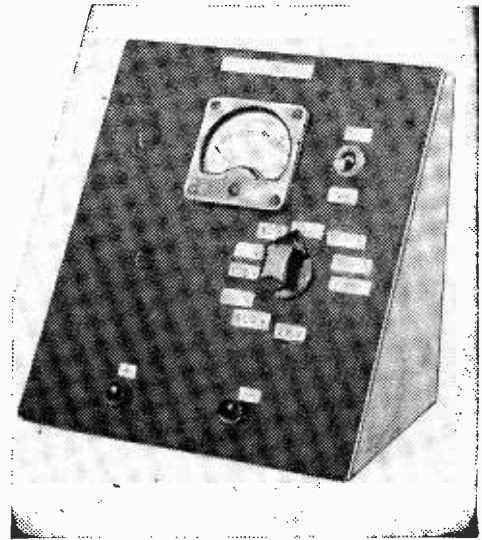

The meter after the current ranges have been added.

Leave the meter switched to the 1mA range just tested. Put S1 off. Wire up as shown in Fig. 19. Here is the procedure. Verify that S1 is off and connect the red lead by the clip to the short tag of the battery. Solder a short lead to the other tag and take it to the bottom tag of a 10k potentiometer held in the position shown in the diagram. Take the positive clip to the central tag of the potentiometer. The top tag is not used.

### Potentiometer

Now, holding the potentiometer in the position shown in Fig. 19 turn the knob fully anti-clockwise. If you are in doubt, study the working of the potentiometer. When set it must be such that the maximum resistance is introduced into the circuit. The value of 10k is a good one, but you can use one of up to 100k if you are very careful when you adjust it. A large knob would be a help whereas with the 10k you could use the spindle alone quite easily.

Do not proceed until you are quite sure the above conditions have been produced. Switch on S1. The meter may move a little. As you adjust the 10k pot. carefully, the meter will move over little by little (if it jerks about the potentiometer is faulty and must be replaced). Set it as accurately as possible for 1mA reading. 1mA is now flowing through the circuit.

### Resistance Wire

Switch off S1. Fix two short clean tinned copper wires to the terminals of the multi-meter (see Fig. 19). Switch on S1. Verify the meter

reads accurately 1mA. Make sure that in the work to be done the negative crocodile clip cannot be moved accidentally to touch the negative tag of the potentiometer.

Take about 9in. of 41 or similar gauge resistance wire, clean one end and solder it to the copper wire attached to the positive terminal of the meter (see Fig. 19 for clarity). Scrape  $\frac{1}{8}$ in. off the other end and hold it tightly with the fingers to the

## Results

When the 10mA range is completed these conditions will obtain: circuit as in Fig. 19 but without the wire shunt; range 6 (1mA) potentiometer set to give meter reading of exactly 1mA; range 7 (10mA) meter should read exactly 0.1mA with potentiometer left as set.

The resistor can be any value in the brown, red or yellow ranges. It is quite unimportant and serves only a convenient former to hold the fine wire. The wire gauge is also relatively unimportant as long as it is of a "hair-like" type and is not copper.

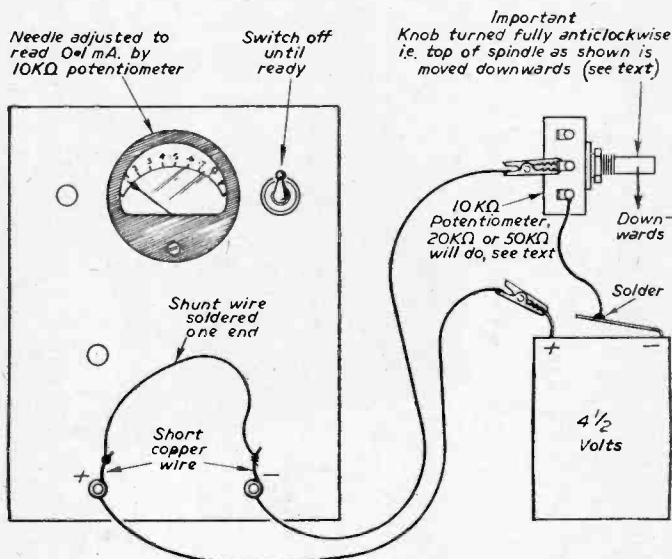


Fig. 19.—Making the shunt for the 10mA range.

copper wire attached to the negative meter terminal. Some current is then by-passed through the wire shunt. The reading on the meter will drop from 1mA to say .2mA. Gradually scrape and clean the free end of the wire ( $\frac{1}{8}$ in. at a time) until it is shortened to such a degree that when it is held to the copper wire attached to the meter terminal the meter moves to exactly 0.1mA. That is, 1mA is flowing through the potentiometer, but only 0.1mA through the meter. It will then take 10mA to move the meter right over.

## Soldering the Shunt

Switch off S1. Note the exact length of shunt necessary and allow an extra  $\frac{1}{8}$ in. for further adjustment. Remove the copper wires temporarily attached to the terminals. Refer to Fig. 20 and make up the resistor, R6, using the length of wire found in the above experiment. Solder one end of the fine wire permanently, but the other end only temporarily. Now solder in the resistor (R6) as shown in Figs. 16 and 17 (given last month).

Switch the range to 10mA, i.e., contacts on tag 7. Leave the potentiometer and associated circuit alone, as Fig. 19 (with the shunt removed). The meter should read about 0.1mA. If it is not exactly 0.1mA switch off S1. If the meter reads too high, shorten the wire round R6; if too low the wire will have to be replaced by a slightly longer one. Check that 1mA is still passing, by turning range switch to 1mA position.

## Testing the 10mA Range

Put S1 off. Set range to 7 (10mA). Wire up as shown in Fig. 18. The meter should only move about one-twentieth of full scale. If it moves half-way something is wrong. If all is well put S1 off and replace the 10k resistor with one of 500 ohms. Use the flick test first always. The meter should now read just about 10mA, most likely a little under. If the meter does not do this the shunt is not working properly (assuming the 500 ohm resistor and battery are all right).

## The 100mA Shunt

This is prepared by reference to the 10mA range already fixed up. The accuracy depends for the most part on the accuracy of the

previous range. The method described will be accurate enough for most purposes.

Fix up Fig. 19 again, taking care that the potentiometer is in the position stated at first. If you have a 5k potentiometer at hand use that, if not the 10k one already used will do. One of a higher value is hardly suitable as the knob would have to be turned very little for a large variation in current. Put the range switch on to number 7 (10mA). Put S1 on.

## Adjustment

Now carefully adjust the potentiometer until the meter shows 10mA, i.e., full scale deflection,

Any resistor (over 5 ohms) prototype uses 470KΩ

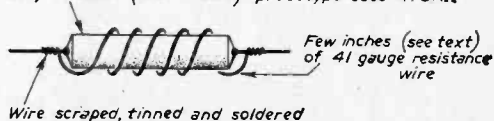


Fig. 20.—The finished 10mA shunt. A resistor (any value over 5 ohms) is used as a former.

exactly. 10mA is now flowing through the circuit. Take about 2ft. of 26 gauge resistance wire. Adjust it in a loop so as to cause no shorts and hold it between the two copper wires attached to the multi-meter terminals. The meter reading will drop. Gradually shorten the length of wire until it drops to show 0.1mA on the scale (i.e., 1mA will then be flowing since the meter is on the



10mA range). Allow  $\frac{1}{4}$  in. each end for soldering and cut the wire to length. Wind it very tightly in a single layer on an old control spindle (Fig. 21) or  $\frac{1}{4}$  in. former and gently pull the "spring" to separate the turns by as small a gap as possible. Refer to Figs. 16 and 17 and solder in position allowing the solder to run only along the  $\frac{1}{4}$  in. allowed at each end.

Approx. 21 turns of 26 gauge Contra wire

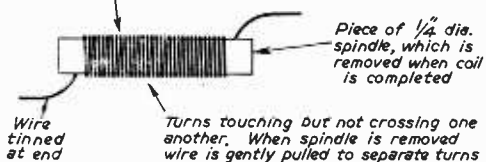


Fig. 21.—The 100 mA shunt. The shunt is wound on a  $\frac{1}{4}$  in. spindle which is then removed.

If you want your meter to be rather more accurate, in the above operation, adjust the meter to read 0.09 on the scale, not 0.1mA. This then allows for the fine shunt which is not finally in circuit, but was during the test.

**Testing the 100mA Range**

Switch the range to position 8. Fix up the circuit of Fig. 18 but use a 47 ohm resistor. Use the "slick test" first. The reading should be round about the full scale, i.e., 100mA will flow but only 1mA through the meter, the other 99 going through the resistance wire shunt.

**The 500mA ( $\frac{1}{2}$  ampere) Shunt**

This is prepared by reference to the 100mA range just wired in and in turn its accuracy will be governed by the previous ranges in the meter.

Fix up the apparatus of Fig. 19 again, using a 1,000 ohm (1k) potentiometer (one will be needed in this meter later on, so you could buy one knowing it will be used permanently). Take the precautions previously stated. Put range on 8 (100mA). Switch on S1 and adjust the potentiometer carefully to obtain exactly 100mA flowing (work as quickly as possible as the battery will not deliver this current without a voltage drop for more than a few minutes). Take about  $\frac{1}{2}$  in. of 26 gauge resistance wire and hold it between the copper reading wires on the meter terminals. The meter reading will drop. Carefully adjust the length of wire so that the meter reads exactly 0.2 on the scale. Remove the shunt made and, allowing  $\frac{1}{4}$  in. as before for soldering, fix it as shown in Figs. 16 and 17. Make sure the wire cannot touch the adjacent resistor already made and fixed. Adjust as on other ranges.

**Greater Accuracy**

If you wish for greater accuracy when making the shunt, arrange that the meter moves back to 0.17 instead of 0.2mA on the scale. This allows for the shunt R7 which was in circuit during the test, but is not in circuit finally in the completed meter on that range.

**Testing the 500mA Range**

Fix up the apparatus of Fig. 18, putting the range on to number 9 (500mA). Use a small 3.5 volt flashlamp for the resistance. Carry out the flicking test first. The meter should move

over to somewhere between 0.3 and 0.8. This depends on the bulb and battery in use. Thus if the reading is 0.3mA on the scale it means that 167mA is passing (for the full scale range is 500mA, and 0.3 of 500 is 167).

**Making and Wiring in the 1 Amp Shunt**

This range is fitted purely as a safety device as mentioned earlier, and is not designed to give continuous operation or to be of very great accuracy. This range has very few uses in ordinary radio servicing. The suggested method of finding the correct shunt is not quite the same as for the other ranges as a torch battery will not supply 500mA for long enough for the operation to be performed.

Put the meter on range 9 and wire up as in Fig. 19, but use the flashlamp bulb in place of the potentiometer. Switch on S1. Note the reading of the meter (between .3 and .8mA with ordinary bulbs). Now take a few inches of 26 gauge resistance wire and hold it across the copper wires fixed to the multi-meter terminals. The meter

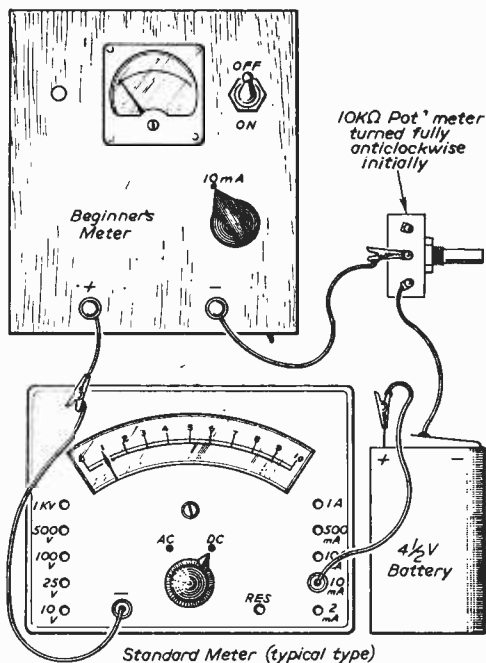


Fig. 22.—Calibrating the beginner's meter against one of known accuracy.

reading will drop, adjust so that the drop is half the existing reading. The current ranges are now completed by soldering this short shunt in position allowing exactly  $\frac{1}{4}$  in. each end.

**Accuracy**

If you wish for greater accuracy you may allow for R8 being in circuit in the test and not in the completed meter by adjusting the shunt for one third the reading.

The meter is now completed for the D.C. voltage and current ranges. The beginner must be very careful when using current ranges or the

meter will be burnt out. Always start on the 1 amp range, switching off S1 before altering the range switch.

Make quite sure the shunts are firmly in circuit. If a multiplier becomes unsoldered no harm can occur, but if a shunt fails the meter will almost certainly be ruined.

**Adjusting the Shunts With the Aid of Another Meter**

If you have a friend with an accurate multi-meter you can, after the preliminary work already given, adjust your meter to finer limits. For instance, the circuit shown in Fig. 22 can be wired up using your meter on the 10mA range and your friend's on a similar range of current. A potentiometer of 10k and a 4½V battery are also needed. Make sure that the potentiometer

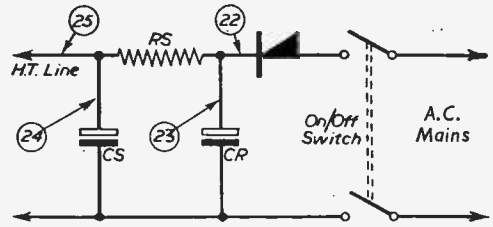


Fig. 24.—A.C./D.C. power pack with metal rectifier.

Sometimes when H.T. is present (21) and the voltage across Rk (20) is low (bias) the valve itself is suspected. From a service sheet or the maker's valve data, the anode current for the valve is often known. The meter is used to check this. If the voltages are correct and the number of milliamps passing is low, then the valve is faulty. The meter for such a test may be inserted in the H.T. line to Ra, that is, unsolder Ra on the H.T. side. Clip the positive meter lead to H.T. line and the negative to Ra (not earth as when using volts ranges). All current now taken by the anode passes through the meter. Set the range to 1 amp. and then switch on S1. If the meter only moves a little try the next range and so on until you obtain a reasonable deflection of the

**CHART TO SHOW THEORETICAL LENGTHS OF WIRE SHUNTS (100-ohm Meter)**

| Range   | Shunt     | Length 42g' of Eureka | Length of 26g Eureka |
|---------|-----------|-----------------------|----------------------|
| 1mA     | NO SHUNT  | —                     | —                    |
| 10mA    | 11.1 ohms | 7in.                  | Too long to use      |
| 100mA   | 1.01 ohms | 0.7in.                | 13in.                |
| 500mA   | 0.2 ohm   | Too small to use      | 2.6in.               |
| 1,000mA | 0.1 ohm   | Too small to use      | 1.3in.               |

is in the position of maximum resistance and switch on both meters. Adjust the potentiometer (carefully) until your friend's meter shows 10mA exactly. Your meter should also read 10mA; if it does not, then lengthen or shorten the shunt as necessary. Of course you must switch off at each adjustment and make sure that the wire is resoldered, otherwise the meter will be damaged when making the test. Before finally testing make sure that the resistance wire has cooled down, because its resistance alters with temperature. When you solder the wire, remember that if solder runs down the wire the shunt is in effect shortened.

The other ranges of the meter may be adjusted in a similar manner but the beginner is advised to adjust the meter initially, using the methods described earlier, and leave the accurate adjustment against the standard meter until practice has been obtained in using the meter. In any case, the accuracy achieved by the second method is hardly necessary from the beginner's point of view.

**How to Use the Multi-meter Milliamp. Ranges**

Refer to Fig. 23 for a normal pentode circuit. The voltage test points of such a circuit have already been discussed.

Fig. 23.—Circuit and check points for a pentode valve (omitting capacitors).

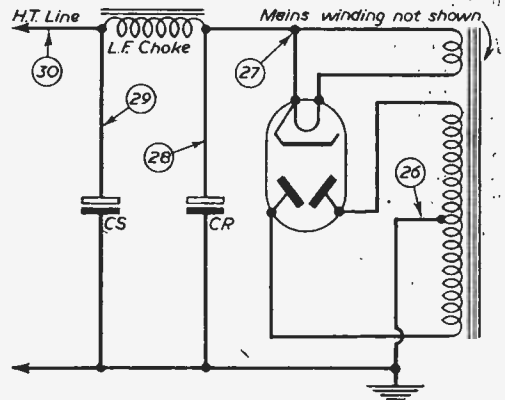
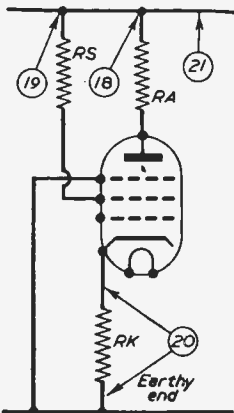


Fig. 25.—Normal A.C. power pack with valve rectifier.

needle. The anode current is then read. Output valves usually draw between 25 and 60mA, L.F. amplifiers about 10mA, detectors very little. If you wish to know the screen current, it may be checked similarly by unsoldering Rs. Sometimes the introduction of a meter will cause oscillations, etc., and it is best to check the cathode current. This is the sum of the anode and screen currents and can be tested by

(Continued on page 648)

# Becoming an Amateur

No. 4.—LEARNING MORSE

By J. D. Pearson, G3KOC


THE Morse code is a subject which many people feel they could never master, without ever having really made an attempt. The reader will find, no doubt, in pursuit of the subject, that there are differing opinions as to the best way to tackle the problem. The mode often used in the services is to shut a number of students in a room, day after day, with an instructor and a code oscillator until they emerge either as proficient operators or nervous wrecks. One could find fault with any system because so much depends on the individual. If one approaches the problem as an irksome task, a necessary evil towards obtaining an Amateur Licence, then a subconscious hindrance is planted at the outset in the mind of the student. The mental attitude should be such that one is possessed of a keen desire to acquire the ability to read all those mysterious dots and dashes one hears on the short wavebands.

## Procedure

The first essential, of course, is to memorise the various groupings of symbols which make the letters of the Morse alphabet. It will be seen from the table that instead of being represented by a series of dots and dashes the letters of the alphabet are matched by the equivalent morse sounds. The letters "di" represent a dot and the letters "dah" a dash. The two words hyphenated thus: "di-dah" equal the letter "a"; the group "di-dah-dah-di" the letter "p" and so on.

The reason for giving the Morse alphabet in this somewhat unusual manner is as follows: if the student learns the Morse alphabet from a printed list of dots and dashes, when hearing morse he automatically sees in his "mind's eye" a sequence of dots and dashes; he then has to convert these mentally into the letters they represent. Now supposing he had learned the Morse alphabet as being represented by a series of sounds, as given here phonetically; when hearing the sound "di-dah-di," for instance, he immediately recognises the letter "r"—the additional mental step of converting "dot-dash-dot" into its corresponding letter is avoided.

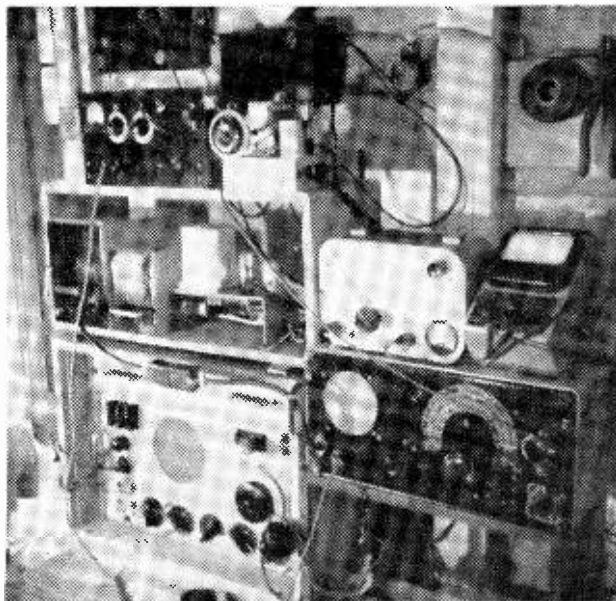The anomaly arises, of course, because one is learning by sight a language which will be used solely by ear. The ideal method obviously is to learn the Morse alphabet "by ear," without ever consulting any printed matter. The method out-



The den of Mr. J. Mitchell of Warminster.

lined here is given for the benefit of those who, as was the case with the writer, are compelled to resort to self-tuition.

## Progress

The beginner should aim to learn at least four letters of the Morse alphabet each day. The letters should be taken consecutively and not by learning "all the dot only letters" or "all the opposites" as the writer has seen recommended: this merely leads to eventual confusion.

At the end of a fortnight the beginner should be able to think of any given letter and be able to say to himself its equivalent sound in morse. Practice whenever possible by translating passages from newspapers, cartoons and hoardings into morse. Do this audibly at first (and when alone, of course; or one's friends and relatives are apt to give one curious glances). Weakness on any particular letter will be revealed when translating.

When the reader can ask a second person to say at random various letters of the alphabet in fairly rapid succession, and himself immediately think of the equivalent morse sound, he can consider that he knows the Morse alphabet. This means he can read morse at about four words per minute.

## Practice

The next step is to listen to *good* morse as frequently as possible. Most of the C.W. the beginner will hear on the short wavebands is much faster than his present 4 w.p.m. Regrettably also, not all of it is good morse. This applies to amateur, as well as other stations.

There are several ways in which the beginner may tackle the bridging of the gap between 4 and 12 w.p.m. If there is a radio club in his

District he will find no doubt that "slow" morse classes are already in progress, or that they can be arranged on request. For the enthusiast who cannot contact a club there are the R.S.G.B. Slow Morse Transmissions which are undertaken by licensed amateurs situated in various parts of the country. A decent communications receiver is almost always capable of pulling in one or other of these transmissions given reasonable conditions. The dates, times, call-signs and frequencies of these transmissions appear in the monthly journal of the R.S.G.B.

### Another Method

For the unfortunate who cannot avail himself of any of the above methods there is but one tutor left—his receiver. Between the frequencies of 3-13Mc/s, there are innumerable C.W. transmissions of varying speeds. Some of these are commercial point-to-point stations who "idle" on their working frequency between traffic-handling sessions in order to keep the channel open. The "idling" consists often of long strings of V's interspaced with the letters "de" (meaning from), followed by a composite alphabetical/numerical call sign and possibly various "Q-code" groups. The morse is fast (by beginners' standards) but of excellent quality. Despite the speed, the beginner will, with perseverance and owing to the repetitive nature of the transmissions, eventually be able to copy them without error.

As with most things, constant practice is essential to proficiency. Half an hour each day

## A BEGINNERS' TEST-METER

(Continued from page 646)

unsoldering Rk at the earthy end and connecting meter negative to earth and meter positive to Rk in the same way as stated for the anode check.

Another method is to put the meter in the H.T. line by breaking the wire at the point 21, positive of meter going to the right and negative to the left (Ra and Rs, etc.). The meter reading is then the total of screen and anode currents. If the valve is now removed, under normal conditions the meter should show no reading. If it does, providing there is no bleeder network, etc., between H.T. and earth, a condenser is probably at fault. Note that all condensers have been omitted in the simple diagram given.

### Checking a Simple A.C./D.C. H.T. Supply

Refer to Fig. 24. The voltage test points have already been discussed. If the meter is inserted at point (25), by cutting or unsoldering the wire, the total consumption of the valves in the set will be given. If the meter is then placed in the circuit at (22) the reading may be greater. This is the leakage current through the condensers Cs and Cr—it should not be greater than about 5mA. The meter may be inserted in the condenser leads at (23) or (24) when the leakage current of each condenser may be read. It will normally be about ½mA for each but could be, say, 2½mA. The total current taken by the

TABLE 1: INTERNATIONAL MORSE CODE

|                   |                   |
|-------------------|-------------------|
| A—di-dah.         | N—dah-di.         |
| B—dah-di-di-di.   | O—dah-dah-dah.    |
| C—dah-di-dah-di.  | P—di-dah-dah-di.  |
| D—dah-di-di.      | Q—dah-dah-di-dah. |
| E—di.             | R—di-dah-di.      |
| F—di-di-dah-di.   | S—di-di-di.       |
| G—dah-dah-di.     | T—dah.            |
| H—di-di-di-di.    | U—di-di-dah.      |
| I—di-di.          | V—di-di-di-dah.   |
| J—di-dah-dah-dah. | W—di-dah-dah.     |
| K—dah-di-dah.     | X—dah-di-di-dah.  |
| L—di-dah-di-di.   | Y—dah-di-dah-dah. |
| M—dah-dah.        | Z—dah-dah-di-di.  |

### NUMERALS

|                       |                        |
|-----------------------|------------------------|
| 1—di-dah-dah-dah-dah. | 6—dah-di-di-di-di.     |
| 2—di-di-dah-dah-dah.  | 7—dah-dah-di-di-di.    |
| 3—di-di-di-dah-dah.   | 8—dah-dah-dah-di-di.   |
| 4—di-di-di-di-dah.    | 9—dah-dah-dah-dah-di.  |
| 5—di-di-di-di-di.     | 0—dah-dah-dah-dah-dah. |

is much more beneficial than, say, three hours each week-end.

It will be noted that so far no mention has been made of a morse-key or "tapper," as this instrument is often mis-called. This is deliberate and the beginner is advised to learn to read morse before any attempt is made at "sending" practice. When he knows what good, correctly spaced morse sounds like he is in a much better position to develop from the outset a perfectly spaced, rhythmic manner of sending.

valves may also be checked by inserting the meter at one end of Rs (which could be a choke).

### Checking a Full Wave Rectifier H.T. Supply

Refer to Fig. 25. The total consumption of the valves may be found by inserting the meter in the H.T. line, broken at point (30). If one or more valves are removed the current taken by individual valves may be checked (in most cases this can do no harm). This should be done rapidly and the valves put back as soon as possible. The total consumption may also be taken by insertion in the circuit at points (27) and (26). Of these perhaps (26) is the better to take. The reading may be a little higher due to the leakage current of the condensers Cs and Cr which may be tested by insertion at points (29) and (28) in a similar way.

### A Warning Note

Never be tempted to connect the meter with S1 on; never guess the range beforehand, always start with one amp. or 1,000 volts and work down; always check that everything is correct before switching on S1. If you follow this advice, your meter will give you years of good service.

## REFRESHER COURSE IN MATHEMATICS


8/6, by post 9/9. 5th Edition.

By F. J. CAMM

From: GEORGE NEWNES, LTD.

Tower House, Southampton Street, Strand, W.C.2

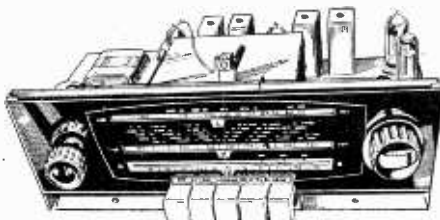**BRAND NEW AM/FM (V.H.F.) RADIOGRAM CHASSIS AT £13.6.8. (P. & P. 10/-)**



Why buy a F.M. Tuner at the same price?  
Tapped input 220-225 v. and 226-250 v. A.C. ONLY.  
Chassis size 15" x 6 1/2" x 5 1/2" high. New manufacture.  
Dial 14 1/2" x 4" in gold, red and deep brown.  
Pick-up, Extension Speaker, Ae., E., and Dipole sockets. Five "plano" push buttons—OFF, L.W., M.W., F.M. and Gram. Aligned and tested. With all valves & O.P. Transformer.  
Covers 1,000-1,900 M.; 200-500 M.; 88-99 Mc/s.  
Valves E280 rect., ECH81, EF89, EABC80, EL84, ECC35. Speaker & Cabinet to fit, polished, with back, 67/6.  
10" x 8" ELLIPTICAL SPEAKER, 20/-. Tone Control fitted.  
**TERMS:**—(Chassis) £4.16.8 down + 10/- carr. and 6 Monthly Payments of 30/-, or with Cabinet & Speaker £5.9.2 down and 7 Monthly Payments of 35/-.

**"READY TO USE" I.T.A. CONVERTER**

I.T.A. high gain converter. ALL CHANNELS—ALL AREAS—ALL SETS. Direct switching (I.T.A. to B.B.C.); internal power pack; valves PCF90 and FCC94; moulded cabinet 8 1/2" x 4" x 6". No alteration to your set; fitted in 10 mins. 12 months' guarantee.

**£5.5.0** P. & P. 3/-



**AUTOMATIC RECORD CHANGERS COLLARO CONQUEST**

with manual play also. Turnover crystal pick-up, 4-speed, A.C. mains 200-250 v., see illus.

**£7.10.0** (5/- P. & P.)

**B.S.R. 4-SPEED AUTO-CHANGER UA8** only **£6.12.6** (5/- carr.)



**COMPLETE RADIO FOR ONLY £12.12.0** carr. pd.

Size 19" x 13" x 7 1/2" or Chassis and dial for £9 (carr. pd.). Chassis Size 15" x 6 1/2" x 5 1/2"; 1,000-2,000 M.; 200-550 and 16-54 M. Mains (200-250 v. A.C.) and O.P. Trans. (3 ohm); Gram., Aer., E., Ext., L.S. Sockets. New Mullard Valves ECH42, EF41, EBC41, EL41, E740 and Magic Eye EM81. Dial 15" x 3". Fully aligned. Fantastic value for money.



6 1/2" or 6" x 4" speaker fitted to cabinet.



**GRAMOPHONE AMPLIFIER** with 5 In. SPEAKER. On Fabric-covered Baffle 12 1/2" x 5". Mains and Output Transformers, Metal Rectifier, ECL82 Valve, Tone and

Volume Controls. On/Off switch. Plenty of Volume. Fully Guaranteed. Two Knobs supplied. Ready to play. Useful for Stereo.


**ONLY 57/- post 2/.**

**BATTERY ELIMINATOR.** Converts your Battery Set to Mains. For 4 Low Consumption Valves (DK range). 90 v. 15 ma. and 1.4 v. 125 ma. 42 6 (2 6 post). 200-250 v. A.C. Size 5 1/2" x 3 1/2" x 2". Also for 250 ma. 1.4 v. and 90 v. 15 ma. at same price. Specify which.

**BATTERY CHARGER KITS** with mains leads and clips. 6 v. and 12 v. in one case. (P. & P. 3/-). 1 amp. 21/-; 3 amp. 30/- (or assembled, 5 - each extra).

**AERIALS F.M.** Aerials single dipole room mtr., 17/6; ditto loft mtr., 20/-; "H" with chimney lashings, 65/-. Co-axial low loss cable 80. yard or 20 yds. 12/6, all these items carriage paid.

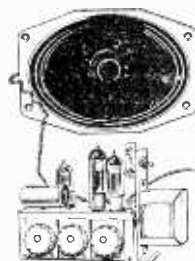**50 SILVERED MICA AND CERAMIC CONDENSERS, 10 - 50 RESISTORS, 5/- ALL DIFFERENT VALUES.**



**3-VALVE AMPLIFIER (INCL. RECT.).** Capable of giving 6 watts. 8" x 5" Speaker wired-in. Mains and output transformers. Valves ECC81, EL84 and Rect. 3 Controls, volume, bass and treble. On/Off switch. Fully guaranteed. Chassis size 6 1/2" x 3" x 2 1/2". 67/- (3/- P. & P.).

**BEREC "PIONEER" RADIO IN MAKER'S CARTON.** Valves DK96, DF96, DAF96, DL96. Berec Ever-Ready Battery B103, 18/6 extra. Two Short Wavebands 2.5 to 7 Mc/s and 6.5 to 17 Mc/s. Cabinet, 12" x 7 1/2" x 6". **ONLY £4.15.0** (2/6 p. & p.). In kit form with instructions and fully wired coil pack. Two Short Wavebands £4. One M.W. and S.W. £4.5.0. Plus 2/6 p. & p. Separate items supplied.




**YOU CAN HAVE** the sprayed case (grey and blue), back, chassis, (without components or coil pack), bracketry, dial cover for dial, and speaker baffle for only 15/- carr. pd. Illust. as above.

**TAKE A CHANCE.** We have surplus to present manufacturing requirements tens of thousands of resistors, silvered mica, tubulars, volume controls, electrolytics, valve holders, etc. **SEND US 20/-** for a bargain parcel of new goods. Our good name is your guarantee. Money back if not satisfied. State preference of types of goods.

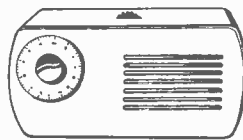**SIX TRANSISTOR SUPERHET KIT £8.19.6**

Med. and L.W.; Printed Circuit; Instruction Book. Internal aerial. All items supplied separately. Write for price list. Battery, 9 v., PP4, 2/6.



Send 6d. (stamps will do) for our illustrated catalogue of the above items and others. All New Goods. Delivery by return. **Terms:**—One-third down and balance plus 7/6 in four equal monthly payments. Postage with down payment. (C.O.D. 2/- extra.) **SEE SPECIAL TERMS FOR A.M./F.M. CHASSIS.**

Large selection of complete Radiograms, ready built in cabinets, with 4-speed Autochanger. Write for details, giving approximate size required. Price from £25 for A.M. only, or £36 for A.M. F.M.


**GLADSTONE RADIO—58A, HIGH STREET, CAMBERLEY, SURREY. Tel. 22791**



# Armstrong AF208

VHF/MW  
RADIOGRAM  
CHASSIS

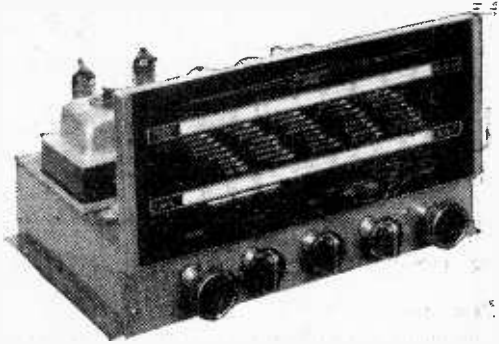**A new, economically priced chassis of traditional Armstrong quality price 22 gns**



Full VHF band (87-108 mc/s) and medium waveband.  
 ● 5 watts output. ● Frequency Response 30-22,000 c.p.s. ± 2 dB. ● Negative Feedback 15 dB. ● Harmonic Distortion 0.5%. ● Hum Level 60 dB down.  
 ● Separate wide range bass and treble controls. ● Output for tape recording. ● Tape playback input for use with tape recorder or tape deck with tape pre-amplifier. ● Two compensated pick-up inputs (switched, to allow two separate pick-ups to be connected). ● Continental reception of good programme value. ● Absolute freedom from drift on VHF. ● Satinised brass dial surround and veneered fascia board available. ● Dimensions 12in. x 8in. x 7in. high.

Other models in our range of radiogram chassis

- STEREO-TWELVE** 36 GNS
- STEREO 44** 27 GNS
- JUBILEE** 28 GNS

The name ARMSTRONG is the registered trade mark of  
**ARMSTRONG WIRELESS & TELEVISION CO. LTD.**  
 WALTERS RD., LONDON N.7. TEL. NORTH 3213

Post this coupon or write for descriptive literature and details of Home Trial facilities. Hire Purchase Terms and Guarantee or call at our Holloway Showroom for full unhurried demonstration and professional advice on your installation. Open 9-6 weekdays and 9-5 Saturdays.

NAME .....

ADDRESS .....

PD8

## EXPRESS ELECTRONICS ROSEDENE LABORATORIES KINGSWOOD WAY, SELSDON, SURREY

**VALVES NEW, TESTED AND GUARANTEED**

|           |             |            |            |            |
|-----------|-------------|------------|------------|------------|
| 1C1 7/6   | 6BR7 10/6   | 12Q7GT 7/6 | EB91 5/6   | N17 7/6    |
| 1C3 8/-   | 6BW6 7/6    | 16A5 9/-   | EB41 10/-  | N18 8/-    |
| 1F1 8/-   | 6BW7 7/-    | 25A6G 10/6 | ERF80 8/6  | N19 7/6    |
| 1F3 7/6   | 6C10 9/-    | 25L6GT 9/- | ECC81 7/6  | POC84 9/-  |
| 1FD1 8/-  | 6D2 5/6     | 25Z4G 9/-  | ECC82 7/6  | PCF80 9/-  |
| 1FD9 7/6  | 6P12 4/6    | 30C1 8/-   | ECC83 7/6  | PCF82 10/6 |
| 1L4 6/6   | 6J7GT 8/6   | 30L1 8/-   | ECC84 8/6  | PCLS2 10/6 |
| 1P1 8/-   | 6K7G 5/6    | 35L6GT 9/- | ECP80 10/6 | PL38 22/6  |
| 1P10 7/6  | 6K8G 7/6    | 35W4 8/6   | ECP82 10/6 | PL81 12/-  |
| 1P11 7/6  | 6L6G 10/6   | 35Z4GT 8/- | ECH42 9/-  | PL82 9/-   |
| 1R5 7/6   | 6Q7G 7/6    | 53KU 11/6  | ECH81 10/- | PY81 8/6   |
| 1R5 7/6   | 6R17GT 7/6  | 5763 10/6  | ECL80 10/6 | PY82 7/6   |
| 1Y4 7/6   | 6SN7GT 5/-  | DAF91 7/6  | EP41 9/-   | U32 7/6    |
| 1U5 6/-   | 6V6G 7/6    | DAF96 8/-  | EP80 8/6   | U76 7/6    |
| 3A5 10/6  | 6X4 7/-     | DF91 7/6   | EP86 11/-  | U78 7/-    |
| 3Q4 8/-   | 6X3GT 6/-   | DF96 8/-   | EP91 4/6   | UBC41 8/6  |
| 3M4 7/6   | 6D3 4/6     | DH76 7/6   | EP92 5/6   | UCH42 8/6  |
| 3V4 7/6   | 12A8F 10/6  | DH77 7/-   | EL38 22/6  | UF41 8/6   |
| 5Y4G 7/6  | 12AT6 8/6   | DH142 8/6  | EL41 9/6   | UL41 8/6   |
| 5Y3GT 7/6 | 12AT7 7/6   | DH150 10/- | EL54 8/6   | UV41 7/6   |
| 5Z4G 9/6  | 12AU7 7/6   | DK91 7/6   | EY51 10/6  | W76 6/6    |
| 6AK6 6/6  | 12AX7 7/6   | DK92 8/-   | EZ40 7/6   | W142 8/6   |
| 6AL5 6/6  | 12BH7 14/6  | DK96 8/-   | EZ80 7/-   | X142 9/-   |
| 6AM6 4/6  | 12P7GT 10/- | DL92 7/6   | EZ81 8/-   | X150 9/-   |
| 6AT6 7/6  | 12K7GT 6/6  | DL94 7/6   | EZ81 8/-   | Z77 4/6    |
| 6BA6 7/-  | 12K8GT 12/6 | DL96 8/-   | KT33C 9/6  | ZD17 7/6   |
| 6BE6 7/-  |             | EABC80 8/6 | KT66 11/6  |            |

VOLUME CONTROLS MIDGET SIZE LONG SPINDLES D.P. switch, 3/9; N.P., 3/3; Less switch, 2/6. Values 10K to 2M. Pre set 2/6.

**MATCHED PAIRS**

EL84 21/-, 6V6G 17/-, KT66 27/6, 6BW6 13/- Per pair. Push Pull O.P. Transformers for above 3-12 14/6, 12" P.M. Speakers 3Q 24/6.

**SETS OF VALVES**

|                                       |      |
|---------------------------------------|------|
| DK91, DF91, DAF91, DL92 or DL94.....  | 27/6 |
| DK96, DF96, DAF92, DL96.....          | 32/- |
| 1C3, 1F1, 1FD1, 1P1.....              | 32/- |
| 1R5, 1T4, 1R5, 3R4, or 3V4.....       | 27/6 |
| 6K8, 6K7, 6Q7, 6V6, 3Z4G or 6X3G..... | 27/6 |

Postage and packing 6d. Over £1 post free. C.O.D. 2/6.

## ADCOLA

(Regd. Trade Mark)


### SOLDERING EQUIPMENT

THE INSTRUMENTS CREATED FOR THE DISCRIMINATING USER.

British & Foreign Pats., Regd. Designs, etc.

- ILLUSTRATED Protective Shield (Cat. No. 68)
- Instrument  $\frac{1}{8}$ " Bit (Cat. No. 70)

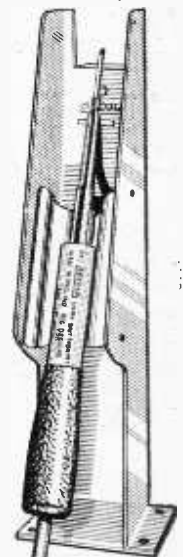The ideal combination for transistor and other intricate work.



Apply direct for catalogue :-

**ADCOLA PRODUCTS LTD.,**  
 GAUDEN RD.,  
 CLAPHAM HIGH ST.,  
 LONDON, S.W.4.

Telephones  
 MACaulay 4272 and 3101

# SELECTING TRANSISTORS

## BASE CONNECTIONS AND USES

By J. Brown

UNLIKE valves, which usually may be used for several different purposes with success, transistors usually need to be selected carefully for the purpose in mind. In this article we are concerned with transistors likely to be of use to the amateur constructor and not with the special types intended for computers and switching devices and similar equipment.

### Procedure

In using transistors it is important to follow carefully the manufacturers' data; transistor circuitry tends to be rather more critical than that for valves and, to obtain the best possible results, transistors must be used only for their designed purpose. In some instances, circuits may employ certain transistors for a different

purpose than that given in the manufacturers' information. However, it is usually found that to secure adequate operation, the transistors have to be specially selected for certain properties from a large batch—hardly a procedure open to the amateur.

There are few *real* equivalents among the ranges of different manufacturers as yet and in following a particular design it is generally wise to employ the specified transistors. It is always wise to check on the ratings of the transistors when designing one's own circuit.








### "Surplus" Types

There are available now so-called "surplus" transistors. These are in general transistors which in some way did not conform with the manufacturer's specification when they were tested. Used with care they will give excellent service and are, of course, of especial interest to the amateur as they are available at very low prices.




The charts in this article include details of most of the transistors commonly encountered and information is also included on surplus transistors in view of the interest in them. As stated previously, it is best to use "new" transistors (as opposed to "surplus" transistors) by the various makers for the intended purpose, but surplus types can often be used for different purposes; for example, audio types may sometimes be used in I.F. stages.

The charts also include data of the base wiring of the various types of transistor as many amateurs are not always certain of the connections.

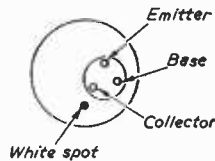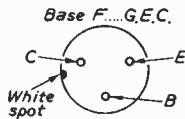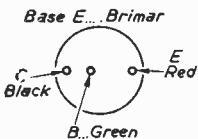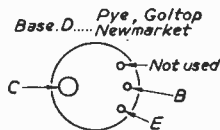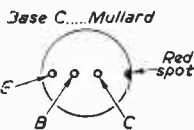
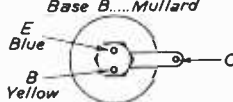
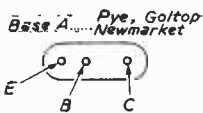
Abbreviation for charts  
 RF/IF suitable for RF or IF stages  
 IF/LF suitable for IF/LF stages  
 Audio LF suitable for Audio or Driver stages  
 Abbreviation C...Collector B...Base E...Emitter



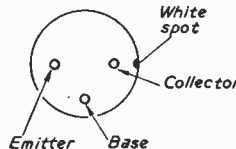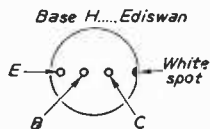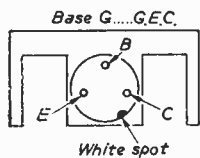Base connections for  
 Pye, Goltop and  
 Newmarket types  
 V15/201P  
 V30/201P  
 V60/201P  
 Now known as  
 Intermediate  
 Power types



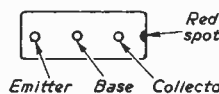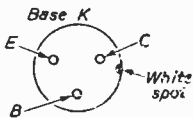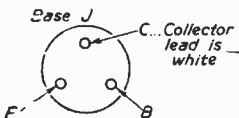Base data for Brimar  
 types TS1, TS2, TS3, TS4  
 TS7, TS8, TS9, TS13, TS14  
 and TS15



Base data for B.T.H.  
 types GT1 GT2 GT3

Details of base connections for various makes of transistor.

## CHART OF ESSENTIAL TRANSISTOR DATA

| Manufacturer | Type        | Base       | Max. Freq.        | Application             | Manufacturer | Type     | Base       | Max. Freq. | Application    |
|--------------|-------------|------------|-------------------|-------------------------|--------------|----------|------------|------------|----------------|
| Ediswan      | XB104       | H          | Gen. Pur.         | Audio                   | G.E.C.       | GET871   | F          | 5 Mc/s     | R.F.           |
|              | XA102       | H          | 8 Mc/s            | R.F.                    |              | GET872   | F          | 10 Mc/s    | R.F.           |
|              | XA101       | H          | Gen. Pur.         | I.F.                    |              | GET873   | F          | 5 Mc/s     | R.F./I.F.      |
|              | XB103       | H          | Audio             | L.F. amp.               |              | GET874   | F          | 10 Mc/s    | R.F.           |
|              | XC101       | H          | Power             | Audio                   |              |          |            |            |                |
| Mullard      | OC44        | C          | 12 Mc/s           | R.F.                    | Pye          | V10/15A  | A          | 1,000 Kc/s | L.F./I.F.      |
|              | OC45        | C          | 6 Mc/s            | R.F./I.F.               |              | V10/30A  | A          | 1,200 Kc/s | L.F./I.F.      |
|              | OC71        | C          | Gen. Pur.         | L.F./audio              |              | V10/50B  | A          | 2,000 Kc/s | L.F./I.F.      |
|              | OC72        | C          | Power             | Audio                   |              | V6/R2    | A          | 4 Mc/s     | R.F./I.F.      |
|              | OC16        | B          | Power             | Audio                   |              | V6/R4    | A          | 8 Mc/s     | R.F.           |
|              |             |            |                   |                         |              | V6/R8    | A          | 10 Mc/s    | R.F.           |
| Brimar       | TJ1         | E          | 500 Kc/s          | Audio/<br>L.F.          |              | V15/10P  | D          | Power      | Audio          |
|              | TJ2         | E          | 600 Kc/s          | Audio/<br>L.F.          |              | V15/20P  | D          | Power      | Audio          |
|              | TJ3         | E          | 800 Kc/s          | Audio/<br>L.F.          |              | V15/30P  | D          | Power      | Audio          |
|              | TS1         | E          | 500 Kc/s          | Audio/<br>L.F.          |              | V30/10P  | D          | Power      | Audio          |
|              | TS2         | E          | 600 Kc/s          | Audio/<br>L.F.          |              | V30/20P  | D          | Power      | Audio          |
|              | TS3         | E          | 800 Kc/s          | Audio/<br>L.F.          | V30/30P      | D        | Power      | Audio      |                |
|              | TK20A       | J          | 3-8 Mc/s          | R.F.                    |              |          |            |            |                |
|              | TK25A       | J          | 8 Mc/s            | R.F.                    |              |          |            |            |                |
|              | TK21A       | J          | 200 Kc/s          | L.F.                    |              |          |            |            |                |
|              | TK24A       | J          | 200 Kc/s          | L.F.                    |              |          |            |            |                |
|              | TK23A       | —          | 200 Kc/s          | L.F.                    |              |          |            |            |                |
|              | TK26A       | J          | 200 Kc/s          | L.F.                    |              |          |            |            |                |
|              | TK27A       | J          | 200 Kc/s          | L.F.                    |              |          |            |            |                |
|              | TK40A       | —          | 1.5 Mc/s          | R.F./I.F.               |              |          |            |            |                |
|              | TS7         | K          | 1 Mc/s            | I.F./R.F.               |              |          |            |            |                |
|              | TS8         | K          | 1 Mc/s            | I.F./R.F.               |              |          |            |            |                |
|              | TS9         | K          | 600 Kc/s          | Audio                   |              |          |            |            |                |
| TS13         | K           | 500 Kc/s   | Audio             |                         |              |          |            |            |                |
| TS14         | K           | 500 Kc/s   | Audio             |                         |              |          |            |            |                |
| TS17         | K           | 600 Kc/s   | Audio             |                         |              |          |            |            |                |
| B.T.H.       | GT1         | See text   | 800 Kc/s          | Audio/<br>L.F.          | Goltop       | V10/15A  | A          | Power      | Audio/<br>I.F. |
|              | GT2         |            | 800 Kc/s          | Audio/<br>L.F./<br>I.F. |              | V10/15   | A          | Power      | Audio/<br>I.F. |
|              | GT3         |            | 1 Mc/s            | R.F./I.F.               |              | V15/10P  | A          | Power      | Audio          |
|              | GT11        |            | 4 Mc/s            | R.F./I.F.               |              | V6/R2    | A          | 3 Mc/s     | R.F./I.F.      |
|              | GT12        |            | 6 Mc/s            | R.F./I.F.               |              | V15/10P  | A          | Power      | Audio          |
|              | GT13        |            | 10 Mc/s           | R.F./I.F.               |              | V15/20P  | A          | Power      | Audio          |
| Hivac        | XFT2        | See text   | 500 Kc/s          | I.F./audio              |              | V30/10P  | D          | Power      | Audio          |
|              |             |            |                   |                         |              | V30/20P  | D          | Power      | Audio          |
| G.E.C.       | GET114      | F          | 500 Kc/s          | I.F./audio              |              | V30/30P  | D          | Power      | Audio          |
|              | GET106      | F          | 1/2 Mc/s          | Audio                   |              | V60/201P | D          | Power      | Audio          |
|              | GET103      | F          | Gen. Pur.         | Audio                   |              | V15/201P | D          | Power      | Audio          |
|              | GET104      | F          | —                 | Industrial              |              |          |            |            |                |
|              | GET115      | G          | Low Power         | Audio                   |              |          |            |            |                |
|              | GET116      | G          | Low Power         | Audio                   |              |          |            |            |                |
|              | GET105      | G          | Low Power         | Audio                   |              |          |            |            |                |
|              | GET110      | G          | —                 | Industrial              |              |          |            |            |                |
|              | GET120      | G          | —                 | Industrial              |              |          |            |            |                |
|              |             |            |                   |                         |              |          |            |            |                |
| Ediswan      | XA104       | H          | 6 Mc/s            | R.F./I.F.               | Newmarket    | V6/R2    | A          | 4 Mc/s     | R.F./I.F.      |
|              | XA103       | H          | 4 Mc/s            | R.F./I.F.               |              | V6/R4    | A          | 4.8 Mc/s   | R.F./I.F.      |
|              | XB102       | H          | Audio             | L.F. amp.               |              | V6/R8    | A          | 8 Mc/s     | R.F./I.F.      |
| G.E.C.       | GET3/D      |            | Audio             | L.F. amp.               | V6/R1        | A        | 3 Mc/s     | I.F.       |                |
|              |             |            |                   |                         | V10/15A      | A        | 1,000 Kc/s | L.F./audio |                |
| Surplus      | Yell./Red   | Paint spot | 8 Mc/s            | Mixer/<br>R.F.<br>Audio | V10/30A      | A        | 1,200 Kc/s | I.F./audio |                |
|              | Yell./Green | Paint spot | Power<br>600 Kc/s | Audio                   | V10/50B      | A        | Low Power  | Audio      |                |
|              | Red Spot    | Paint spot | 800 Kc/s          | L.F./audio              | V30/20P      | D        | Power      | Audio      |                |
|              | White Spot  | Paint spot | 5 Mc/s            | R.F./I.F.               | V30/30P      | D        | Power      | Audio      |                |
|              |             |            |                   |                         |              |          |            |            |                |
|              |             |            |                   |                         |              |          |            |            |                |


**Colour-coding**

The leads of some manufacturers' transistors are colour coded; for example in BTH transistors the collector is coloured white and the next connection reading clockwise is for the base and the remaining one is for the emitter. In the Hivac XFT2 the base is the central lead and the collector is colour coded red.

Although some of the transistors given in the charts are obsolete, having been replaced by more efficient types, they are included for the

sake of completeness. The transistors mentioned in the charts are today employed in many kinds of circuit and will be found in all types of electronic equipment.

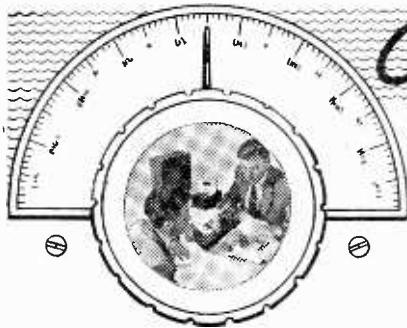Many firms other than those mentioned above manufacture transistors; e.g., Semiconductors Ltd., Texas Instruments Ltd., etc. Generally these firms produce semiconductor devices for use in specialised electronic equipment and their products will rarely be encountered by the amateur.



# On Your Wavelength

BY THERMION

IT is now many years since I made my first receiver; a simple crystal receiver it was and well do I remember the hours of hard work and perseverance that went into its construction. In those days, radio amateurs were a different breed; we enjoyed our hobby and took a great pride in building as much as possible of our receivers. Initially, of course, this policy stemmed from necessity rather than from personal preference; we were unable to buy parts, we *had* to make them if we wanted to build a set. How many of you remember winding coils on wooden mangle rollers? I do for one. There was the question of obtaining raw materials; where to find wire for coil winding; what to use for a detector—we used all manner of substances, ranging from coal, through carborundum to galena—; what to use for a baseboard, and so on. Yes, those were the days! Then, there was always what might be termed a spirit of adventure among the radio enthusiasts; a sort of bonhomie which is entirely lacking today. The hobby has now become a trade and everything is bought. If you have recently built a set, pause and reflect how much of the construction was your own unaided work. Precious little I am certain. You may argue that you have no time to spare and have to buy ready made items. Nonsense: in my day, we had even less time; we did a hard day's work and came home ready to spend an evening, or rather enjoy an evening, experimenting with our latest project. Where is this spirit today?

The main reason for lack of enthusiasm is the lack of new inventions or discoveries in the world of amateur radio today. When radio first began, hardly a day went by without details being given or talked about concerning some new station, some new combination of crystals, etc. Nowadays, everything is over; there is nothing left to discover. Any amateur with the money and inclination can talk to Australia if he so desires. In that preceding sentence lies the answer: money. Today, any item of radio gear or any component can be bought and as is often said, more cheaply than making the item and, of course, much more quickly. In the old days, one had to be a millionaire to buy radio parts and it was impossible to see many items, let alone purchase them. I mentioned another aspect of the modern trend above; the fact that not only can components be bought more cheaply than made, but also they can be bought quickly. This is often given as

an excuse for buying costly parts. Why is there this insistence on speed? Is the modern way of life so different to that of thirty years ago that the virtues of patience and perseverance have disappeared? Surely not. This is the basic difficulty. Every new idea must be completed quickly. What does it matter if the building of a receiver takes six months if afterwards you can say that you built three-quarters of it? How few people now take a pride in their construction work. "It may look awful," they say "but it works". This sentiment is typical of many in these times and is spreading like a blight through the world of amateur radio.

It has, in fact, been in evidence for some time in many radio shops selling components. How many of you can say that your local dealer knows you and is prepared to help you out of your difficulties? Very few dealers of my acquaintance would be prepared to help their customers in this way. Why not? They never tell me. Perhaps it is the fault of the customer and not of the dealer. However, from the outside, all that is in evidence is a great lack of goodwill and understanding between most dealers and constructors. What a great pity it is! So many of the dealers are old hands and should be willing to help their customers to share their knowledge. It is this fact that makes me suspect that faults lie on both sides.

However, all is not lost. I have found when talking to young enthusiasts—many of them still attending school—that their attitude is different. They take a pride in their sets; they build many of the parts—they have to on 1s. to 10s. per week pocket money. They enjoy the hobby for the hobby's sake; it is not so much a means to an end as an end in itself. It is curious, too, that dealers are often particularly willing to help these young people. Why is this? Could it be that they are learning their hobby in the same atmosphere of discovery that the dealer encountered in his youth? Perhaps this establishes a common bond; at any rate there is a startling affinity.

## Radio Dens

I AM still receiving a steady stream of photographs and negatives in response to my appeal some time ago for pictures of readers' radio dens.

On page 686 of this issue the den of Mr. T. Fuller, of Beaminster, is illustrated. Mr. Fuller is 16 years old and his enthusiasm can be judged by his equipment.

The den of Mr. J. Mitchell, of Warminster, is illustrated on page 647. Shown in the picture are on the left a modified R208 and on the right a PCR3. Above, the R208 are the two receiver power packs and a spare unit. Above the power packs on the left is a home-made top band TX and on the right an R.F. converter used as a front end with the PCR3.

# Improving Superhets

SIMPLE MODIFICATIONS FOR BETTER RESULTS

By J. Johnston

WHEN an ordinary superhet receiver is primarily used for long distance or short wave reception, a number of useful additions can be made to increase selectivity and sensitivity, simply tuning, etc. Some features of this kind will be present in a communications receiver, but not in the more straightforward

sensitive receiver, this can be quite low in value; say 25pF, or even less. The increased selectivity in the aerial circuit will then help to reduce second channel interference, which can be troublesome on the short wave bands.

Optimum adjustments of the panel trimmer will not be necessary with powerful stations, and it can thus be left untouched during normal reception.

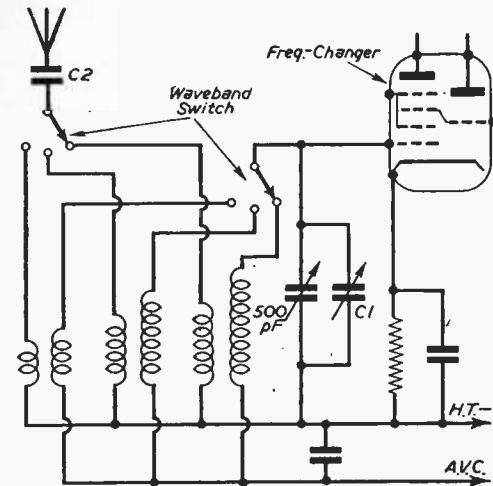


Fig. 1.—Using a trimmer (C1) in parallel with the aerial tuning section of the gang condenser.

conventional all-wave set. The improvements will, of course, be equally effective on long and medium waves, giving improved reception, or a more accurate indication of correct tuning.

## Aerial Trimming

In many average receivers alignment between aerial and oscillator tuning is not exact throughout each waveband. This can be so even when trimming and core adjustment are correct, and arises from slight variations in gang condenser capacity, etc. The loss of efficiency is unimportant with strong signals, but can be material with weak signals.

Loss of sensitivity from this cause can be overcome by wiring a small panel-operated trimmer across the aerial tuning section of the gang condenser, as shown at C1 in Fig. 1. The pre-set trimmers fitted to the coils should be unscrewed, or removed, so that the panel trimmer is normally at about half capacity. Slight final adjustments can then be made with this control, as necessary, when listening to very weak stations. A maximum capacity of 30pF or 50pF will normally be suitable, and a small S.W. type air-spaced variable condenser will be convenient.

At the same time it may be worth while reducing damping on the aerial coils, by including a small pre-set or fixed condenser, C2. With a

## Bandsread Tuning

With the usual 500pF or similar gang condenser, tuning becomes very critical and crowded on the S.W. bands. This can be overcome by adding a bandsread tuning condenser in parallel with the main gang condenser, as shown in Fig. 2. Any particular S.W. band can then be explored readily, and stations can be recorded by dial reading if the main condenser is returned to a particular setting. Two-way conversations between amateurs can also be followed, because the readings of each transmitter can be noted, and returned to as needed.

For general use on 25, 31, 40m and higher bands, a maximum capacity of about 25pF or 30pF will be satisfactory. If more attention is given to lower bands, a maximum capacity of 15pF will be sufficient. Wiring to the condenser should be reasonably short. It may be possible to match up the control knob and dial with existing controls. If a large dial knob can be

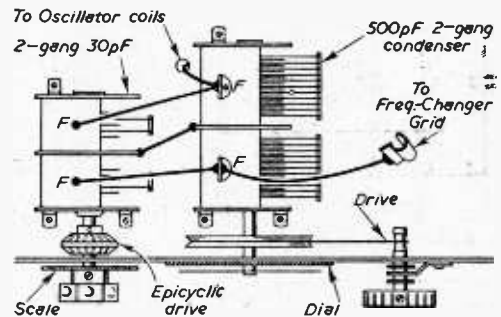


Fig. 2.—Using a bandsread tuning condenser in parallel with the main gang condenser.

used, the epicyclic reduction drive is not essential. With a 25pF condenser, the full 180 deg. rotation will give a similar wavelength coverage to roughly 9 deg. rotation of the 500pF condenser.

## Tuning Indicators

A tuning indicator will show if alignment and trimming are correct, besides showing the tuning point for stations. A 1½ in. to 2 in. or similar moving coil meter will provide a very sensitive and exact indication of tuning, if wired to an A.V.C. operated stage, such as the I.F. amplifier as in Fig. 3.



The meter and shunt should be so chosen that the meter can be set to show full-scale deflection, with no signal tuned in. A 1mA, 2mA or 5mA meter can be shunted so that the usual 6mA to 10mA anode current of the I.F. stage valve gives a full scale reading. The 0.05μF by-pass condenser is necessary to preserve stability.

The 100 ohm or similar variable resistor should be set to a low value, and the receiver tuned until no signal is heard. The resistor is then adjusted until the meter reads full scale. When a station is tuned in, the reading will fall. The correct tuning position is that giving lowest reading on the meter.

Improvements which increase sensitivity, such as adjustment of aerial trimming, or I.F. transformers, will also give a further reduction in meter reading. The receiver has thus been adjusted for optimum results when no further fall in reading can be obtained, with a given station. External improvements, such as those to aerial or earth, will also be shown by the meter reading, and this can be very useful indeed.

will be satisfactory, and its heater rating can be chosen to suit the receiver supply. The circuit shown in Fig. 5 is an easy one to adjust, and requires practically no modification to the main

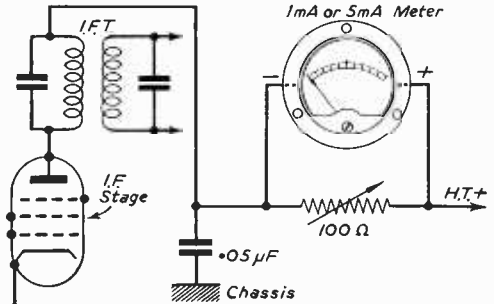


Fig. 3.—A simple tuning indicator.

part of the receiver. Values are suitable for a 6K7, or any average R.F. pentode.

The B.F.O. coil should be tunable to a frequency near that used by the receiver I.F. stages. If the receiver employs 465kc/s, as is usual, the B.F.O. can be tuned to 466kc/s, or 464kc/s, to produce an audible tone of 1kc, or 1,000c/s. In practice, variable tuning is useful in the B.F.O. stage. The beat frequency can then be varied at will, to avoid monotony, and to give maximum readability over interference. The upper or lower beat frequency can also be selected, according to whether an interfering station occupies the upper or lower side-band.

**Coil**

In Fig. 5, C1 is a pre-set condenser, and it is adjusted until no beat note is produced, with the 25pF variable condenser at half capacity. The higher or lower frequency can then be selected and adjusted by means of the 25pF condenser control knob. The B.F.O. coil may consist of one winding from a discarded 465kc/s I.F. transformer, with about two extra turns, close wound, to provide a tapping, or any aerial, oscillator, or home-wound coil tunable to 465kc/s (approximately 645m) can be used.

The B.F.O. stage is best built in a screening can, especially if the coil is not screened. The

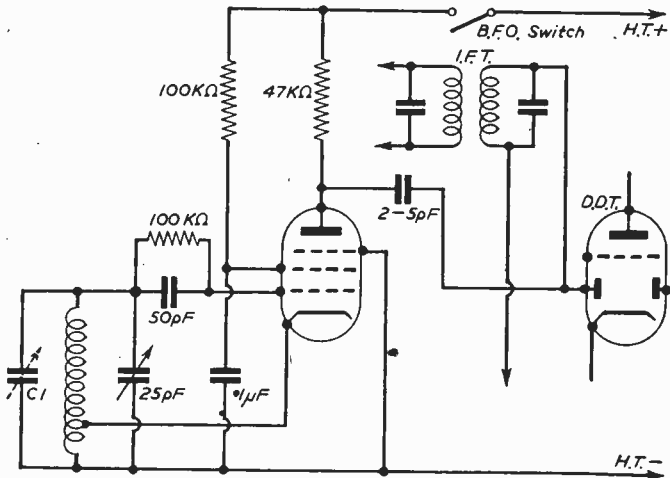


Fig. 5.—Circuit of a simple beat frequency oscillator.

With fading stations, the meter will tend to rise and fall, owing to the A.V.C. action. With very weak stations and delayed A.V.C., no indication may be obtained. This can be largely overcome, if desired, by increasing I.F. gain in the manner described later.

A magic eye may also be used for tuning indication, and pin connections for a 6U5G are shown in Fig. 4. This is convenient for guidance in correct tuning, but is less suitable when an exact note needs to be made, as with the meter.

**Beat Frequency Oscillator**

With unmodulated continuous wave Morse, reception is impossible with an ordinary superhet, because there is no local oscillation to beat with the received signal and thus produce an audible tone. With communications receivers, a local beat frequency oscillator is used for this purpose. Any small triode, or pentode valve,

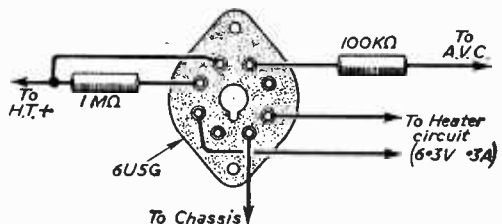


Fig. 4.—Wiring a 6U5 as a tuning indicator.

25pF condenser can be operated by an extension spindle, if necessary. The coupling capacity to the D.D.T. stage must be small, as shown. An insulated wire wound round the diode connection will usually provide enough coupling, or a very small pre-set can be incorporated, and adjusted

degree of A.V.C. is required, the valves should therefore have their screen grids operated from a divider, as provided by R1 and R2 in Fig. 6. The overall value of these resistors should be fairly low—say, not over 25k in all. This, however, will depend on the H.T. current available, because of the consumption of the two resistors in parallel with the H.T. supply. It is necessary to take the values for R1 and R2 from the valve maker's data, or to ascertain the S.G. voltage, and calculate the values from this, and screen grid current.

Very many receivers have only one I.F. stage, and it is usually easy to add an extra I.F. stage to these, thereby securing a very worthwhile increase in sensitivity and selectivity. Fig. 6 shows a complete I.F. stage, which can be added between existing F.C. and I.F. stages.

#### Cathode Resistor

The I.F. transformer must be for the correct frequency (usually 465kc/s). Wiring should be short and direct, or instability may arise. As the gain may easily be too high for normal listening, a variable cathode resistor, with panel control knob, should be provided. With many valves, a 25k or 50k potentiometer will be satisfactory. The usual fixed bias resistor R3 is also included, so that normal bias is present when the I.F. gain control is set for maximum gain (e.g. minimum resistance). With some receivers, decoupling of the H.T. circuit will not be necessary. With others, this may be required in the feed to the frequency changer.

The additional transformer is adjusted for maximum sensitivity, as indicated by the tuning meter. If instability arises, evidenced by an abrupt fall in meter reading, with no signal tuned in, and with the I.F. gain control approaching maximum, then the layout of this extra stage needs improving. The valve may be placed in a screening can, and anode and grid leads may be shortened and screened.

#### Selectivity

If the receiver is often used for musical programmes, the I.F. transformers should be staggered slightly, or the number of I.F. circuits present will make tuning too sharp for good reception.

When additional amplification is made available in this way, the delay voltage may be removed from the A.V.C. circuit, if desired. It will then begin to operate even with weak signals. Most receivers employ a double-diode-triode, with the triode cathode bias acting as A.V.C. delay voltage. The delay voltage can then be removed by shorting the cathode to chassis, the bias resistor being eliminated. At the same time the triode grid resistor is increased to 8 to 10M $\Omega$ , so that triode bias is obtained by grid rectification. The effects arising from this modification will be particularly apparent when a tuning meter has been fitted.

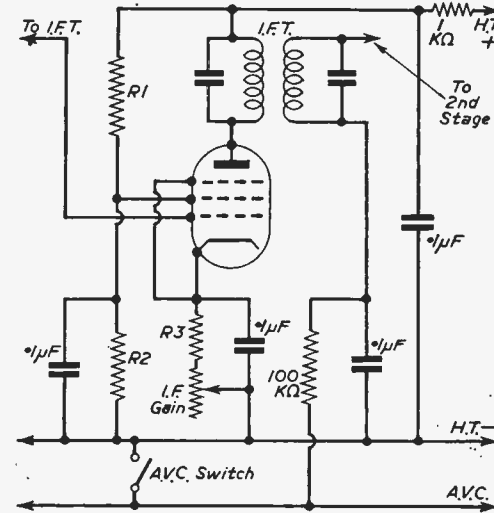


Fig. 6.—Adding an A.V.C. switch.

for best results. The value is in no way critical.

The B.F.O. stage must be rendered inoperative for reception of speech and music, and a B.F.O. control switch is thus included in the H.T. supply to the valve. In battery sets, a filament switch would be more suitable.

#### A.V.C. Circuit Modifications

When unmodulated C.W. morse is received, the tuning meter or eye will endeavour to follow the signal. This, and the erratic operation sometimes caused, can be eliminated by fitting an A.V.C. switch, as shown in Fig. 6. Component values in the F.C. and I.F. stages should be such that the valves receive optimum bias when the A.V.C. line is shorted to chassis. Such a switch is sometimes ganged with the B.F.O. switch, so that when the B.F.O. is operating, the A.V.C. is inoperative. If not, the A.V.C. switch should be closed when the B.F.O. is switched on.

With the A.V.C. off, critical adjustment of an aerial trimmer like that in Fig. 1 will be simplified without a tuning meter because gain will be constant. But there will, of course, be no compensation for fading, and overloading may arise with powerful stations. The A.V.C. is thus normally left in action, except when receiving morse.

In many receivers the F.C. and I.F. stage valves draw screen current from a series resistor wired to H.T. positive. When the A.V.C. circuit develops bias, the valve anode currents drop. This usually causes a drop in S.G. current. The S.G. series resistor then passes less current, so that the S.G. voltage rises. To some extent this offsets the A.V.C. action. When the best possible

OUR COMPANION JOURNAL  
**Practical Television**  
 1/6 Every Month

**C.R.T. ISOLATION TRANSFORMERS**  
**TYPE A. OPTIONAL 25% and 50% BOOST.**  
**2 V. OR 4 V. OR 6.3 V. OR 10.8 V. OR**  
**13.3 V. 12/60 MAINS INPUT.**  
**OUR LATEST PRODUCT**  
**TYPE A2. HIGH QUALITY LOW CAPACITANCE.**  
**10/15 pF. OPTIONAL BOOST 25%, 50%,**  
**75%, 10/6 EACH. MAINS INPUT.**  
**TYPE B. MAINS INPUT. MULTI OUTPUT 2,**  
**4, 8, 8, 7, 5, 10 AND 13 VOLTS. BOOST 25%**  
**AND 50%. LOW CAPACITANCE 21/-.**

**TRIMMERS.** Ceramic. 30, 50, 70 pf., 9d.; 100 pf., 1.50 pf.; 1/3; 250 pf., 1/6; 500 pf., 750 pf., 1/9.  
**RESISTORS.** Preferred values. 10 ohms to 10 meg. 1/2 w., 4d.; 1 w., 4d.; 1 w., 6d.; 1 w., 8d.; 2 w., 1/4.  
**HIGH STABILITY.** 1/4 w., 1% 2/1. Preferred values. 100 ohm to 10 meg. Ditto, 5%, 100 ohm to 5 meg. 0. 8d. 5 watt) **WIRE-WOUND RESISTORS** (1/3 10 watt) 25 ohms-10,000 ohms (1/8 15 watt) 250 ohms-50,000 ohms. 5 w. 1/9; 10 w. 2/3.


**GEVART GEVASONOR**  
 Long play plastic tape. 1,700 ft. Tin. Reel. 35/-; 850ft. 5in. reel. 21/-; M.S.S. 255ft. 3in. reel. 7/6.  
**SUPERIOR 1,200 ft. Plastic Tape on 7" Plastic**  
**Reels 24/-; 800ft. 5in. reel, 15/-.** Long play  
**1,200 ft. 5in. reel, 28/-.**  
**SPARE REELS. ALL SIZES. 3/-.**  
 "Instant" Bulk Tape Eraser and Head De-fluxer. 200/250 v. A.C., 27/6. Leadat. S.A.E.

**O.P. TRANSFORMERS.** Heavy Duty 50 mA. 4/6. Mullinix, push-pull. 7/8. Miniature. 35d. each. 4/8.  
**L.F. CHOKES** 15/10 H. 60/65 mA. 5/-; 10 H. 83 mA. 10/6; 10 H. 150 mA. 14/-.

**MAINS TRANSFORMERS 200/250 v. A.C.**  
**STANDARD.** 250-0-250, 80 mA., 6.3 v. 3.5 a. tapped 4 v. 4 a. Rectifier 6.3 v. 1 a. 5 v. 2 a. or 4 v. 2 a. ditto, 350-0-350 ... 22/8  
**MINIATURE.** 200 v. 20 mA., 6.3 v. 1 a. 10/8  
**MIDGET.** 250 v. 45 mA., 6.3 v. 2 a. 15/8  
**SMALL.** 250-0-250, 100 mA., 6.3 v. 3.5 a. 19/6  
**STANDARD.** 250-0-250, 65 mA., 6.3 v. 3.5 a. ... 17/8  
**HEATER TRANS.** 6.3 v. 1 1/2 amp. ... 7/6  
 Ditto, tapped sec. 2, 4, 6.3 v., 1 1/2 amp. 8/8  
 Ditto, sec. 6.3 v. 3 amp. ... 10/8

**ALADDIN FORMERS and core, 1in., 8d.; 1in., 10d.**  
**0.3in. FORMERS 5937/8 and Cans V1/2.** 4in. sq. x 1in. and 1in. x 1in. 2/- ea., with cores  
**T.Y.A.N.A.-Midget Soldering Iron, 230 v. 20 w., 16/9.**  
**REMPLY Instrument Iron, 230 v. 25 w., 17/6.**  
**MAINS DROPPERS.** 3in. x 2in. Adj. Sliders. 0.3 amp. 750 ohms. 4/3. 0.2 amp. 1,000 ohms. 4/3.  
**L.I.C. COIL.** 3 amp., 60 ohms per foot. 2 amp., 160 ohms per foot. 2-way. 6d. per foot. 3-way. 7d. per ft.  
**LOUDSPEAKER P.M. 3 OHM.** 5in. Rola, 17/6. Min. Plessey, 19/6. 6in. x 4in. Rola, 18/-; 4in. Rola, 18/6. 8 x 5in., 21/-; 10 x 6in., 27/6. 10in. Rola, 30/-; Hi-Fi Tweeter, 25/-; 12in. R.A., 30/-; 12in. 15 ohm 10 w. Plessey, 45/-  
**STENTORIAN HF1012 10in. 3 to 15ohm 10 w., 95/-; 12in. Baker 15 watt 3 ohms, or 15 ohms, 105/-; CRYSTAL DIODE G.E.C., 2/-, GEX34, 4/6; HIGH RESISTANCE FORMERS, 4,000 ohms, 18/6 per  
**MIKE TRANS. 5V1, 3/6 ea.; 100/1. Potted, 10/6; SWITCH CLEANER.** Fluid squirt spout. 4/3 tin.  
**TWIN GANG TUNING CONDENSERS.** 365 pf. miniature 1in. x 1 1/4in. 11in., 10/-, .0005 Standard with trimmers, 9/-; less trimmers, 8/-; midget, 7/6.  
**SINGLE.** 60 pf., 2/6; 80 pf., 100 pf., 160 pf., 7/-; Solid dielectric 100, 300, 500 pF., 3/6.  
**SOULDR FRET. GOLD CLOTH.** 17in. x 25in., 5/-; 25in. x 35in., 10/-; Tyezan 4 1/2in. wide, 10/-; 2in. 3in. wide, 5/- ft. Sampler, 3/6.  
**New and Broken VALVES 90-day Guarantee.****

|       |      |       |      |        |      |        |      |
|-------|------|-------|------|--------|------|--------|------|
| 1R5   | 8/6  | 8K6   | 8/6  | EABC50 | 10/6 | HABC80 | 10/6 |
| 1R5   | 8/6  | 8Q5   | 8/6  |        | 10/6 |        | 10/6 |
| 1R4   | 4/6  | 6B7M  | 7/6  | EBR1   | 6/6  | HV124  | 7/6  |
| 2X2   | 3/6  | 6G7   | 10/6 | EBC33  | 8/6  | MCR12  | 10/6 |
| 3B4   | 8/6  | 6A7A  | 7/6  | EBC41  | 10/6 | P61    | 6/6  |
| 3V4   | 8/6  | 6B7J  | 10/6 | EBF80  | 10/6 | PCC84  | 12/6 |
| 5U4   | 8/6  | 6B8A  | 8/6  | EBC84  | 12/6 | PCF50  | 11/6 |
| 5Y3   | 8/6  | 6V6G  | 7/6  | EFCF60 | 11/6 | PCLS2  | 11/6 |
| 5Z4   | 10/6 | 6X4   | 7/6  | ECH42  | 10/6 | PE25   | 6/6  |
| 6AM6  | 8/6  | 6X5   | 7/6  | ECL82  | 12/6 | PLS2   | 10/6 |
| 6B8   | 5/6  | 12A7T | 9/6  | EPF9   | 7/6  | PV80   | 8/6  |
| 6BE6  | 7/6  | 12AU7 | 9/6  | EPF41  | 10/6 | PE31   | 10/6 |
| 6BH6  | 10/6 | 12AX7 | 9/6  | EPF50  | 8/6  | PV82   | 8/6  |
| 6BW6  | 10/6 | 12BE6 | 10/6 | EPF90  | 10/6 | 8P61   | 5/6  |
| 6P6   | 7/6  | 12K7  | 8/6  | EPF91  | 8/6  | UBC41  | 10/6 |
| 6P9   | 7/6  | 12Q7  | 8/6  | EPF92  | 8/6  | UCH42  | 10/6 |
| 6P6   | 3/6  | 3E6   | 8/6  | EL32   | 5/6  | UL41   | 10/6 |
| 6P5   | 3/6  | 3A4   | 9/6  | EL84   | 10/6 | UL41   | 10/6 |
| 6P6   | 7/6  | 80    | 10/6 | EM81   | 12/6 | U341   | 8/6  |
| 6J7   | 8/6  | 807   | 6/6  | EZ40   | 8/6  | U22    | 10/6 |
| 6K6GT | 6/6  | 954   | 16/6 | EZ80   | 8/6  | VR105  | 8/6  |
| 6K7G  | 5/6  | EA50  | 1/6  | EL148  | 1/6  | VR150  | 8/6  |

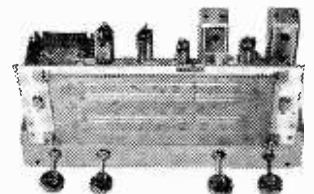

**1959 RADIOGRAM CHASSIS**  
**THREE WAVEBANDS. FIVE VALVES**  
 S.W. 16 m.-50 m. LATEST MULLARD  
 M.W. 200 m.-550 m. ECIN1, EP80, EBCN1,  
 L.W. 800 m.-2,000 m. EL84, EZ80,  
 12-month guarantee.  
 A.C. 200/250 v. 4-way Switch; Short-Medium-Long-  
 Gram. A.V.C. and Negative feedback  
 4.2 watts. Chassis 13 1/2 x 5 1/2 x 2 1/2 in. Glass dial  
 horizontal or vertical size 10in. x 4 1/2 in.  
 Aligned and calibrated. Isolated Chassis.  
**£9.10.0** Carr. & Ins. 4/6.

**TERMS:** Dep. £5.5.0 and five months of 81.  
**MATCHED SPEAKERS FOR ABOVE CHASSIS.**  
 8in., 17/6; 10in., 25/-; 12in., 30/-.  
**NEW AM-FM MODEL**  
**£18.19.6**



**BSR**  
 The Brilliantly Successful  
**Monarch 955**  
**£6.19.6**  
 World's first 4-speed Autocchanger  
**TERMS:** Dep. £2.10.0 and four months of 21.  
**Stereo Model UA3 28.19.6 UAL2 £10.10.0.**

**BUILD THIS REPRODUCER**  
**BARGAIN SINGLE PLAYER KIT**  
 Ready for immediate assembly.  
 4-speed Collura "Junior" Unit ..... £4 12 6  
 Handsome case, 17 1/2 x 13 1/2 x 7in.,  
 with room to play 12in. records ... £2 5 0  
 Ready-built 3-watt amplifier with  
 two valves and loudspeaker ..... £3 12 6  
 or **£9.15.0** complete kit post free.

**LATEST E.M.I. 4-SPEED SINGLE RECORD**  
**PLAYER.** Acos 73 hi-fi stereo and normal Xtal  
 pick-up. silent motor heavy turntable.  
**Special Offer 28.19.6.** Post 3/6.

**ALUMINIUM CHASSIS.** 18 s.w.g. un drilled.  
 With 4 sides, riveted corners and lattice living  
 holes. 2 1/2in. sides, 7 x 4in., 4/8; 9 x 7in., 5/8;  
 11 x 7in., 8/8; 13 x 9in., 8/6; 14 x 11in., 10/6;  
 15 x 14in., 12/6; 18 x 16 x 3in., 16/6.

**TRANSISTORS. GENUINE EDISWAN**  
 R.F. 4 Mc/s, 18/-; 2 Mc/s, 15/-. Audio, 10/-.  
 Complete data sheets supplied.

**CRYSTAL MIKE INSERT** by Acos. precision  
 engineered. Size only 1in. x 2 1/16in., 6/6.

**HI-GAIN BAND 3 I.T.A. PRE-AMP KIT.**  
 Cascade circuit with valve EC84. Price 29/6,  
 With Power Pack. 49/6. Plans only 6d.  
 Band 1 B.B.C. version same prices.

**BBC. T.V. TRANSISTOR RADIO. M. & L. wave.**  
 Complete kit 32/6, phones 7/6 extra. Deal Aid  
 Earpiece 12/6. Special Lead 2/6. Details 6d.

**GARRARD 48P. SINGLE PLAYER**  
**AUDIO PERFECTION**  
 Designed to play 16, 33, 45, 78 r.p.m. Records  
 7in., 10in., 12in. Lightweight Xtal pick-up.  
 GC2 turnover head, two separate sapphire styl.  
**OUR PRICE £7.10.0** each. Post Free  
 Model TA Mk. II 88-10-0. Model 4HF £18-0-0  
 With Plug-in Normal Heads.  
 (Stereo heads £2 extra).

**Volume Controls 80 ohm CABLE COAX**  
 Long spindles. Guaranteed 1 year. Midget 5K ohms to 2 Meg. No sw. D.P.S.w. Fringe Quality Linear or Log Tracks. **1/6** yd.

**COAX PLUGS 1/- LEAD SOCKET 2/-**  
**PANEL SOCKETS 1/- OUTLET BOKES 4/6**  
**BALANCED TWIN FEEDER yd. 6d. 80 or 300 ohms.**  
**DITTO SCREENED per yd. 1/6. 80 ohms only.**  
**WIRE-WOUND POTS, 3 WATT. Pre-set Min. 1/2 Type.** All values 25 ohms to 25 K., 2 1/2 ea. 30 K. 50 K., 4/-, (Carbon 30 K., to 2 meg., 3/-).  
**WIRE-WOUND 4 WATT Pots. Long Spindle.**  
 Values, 100 ohms to 50 K., 6/8; 100 K., 7/6.  
**CONDENSERS.** New Stock. .001 mfd., 7 kv. T.C.C., 5/8; Ditto, 20 kv., 9/8; 1 mfd., 7 kv., 9/8;  
 Tubular 500 v. 0.01 to .05 mfd., 9d.; 1 1/2-, 25, 14/6;  
 .5/50 v., 1/9; 1/350 v., 9d.; 1/1000 v., 1/9  
 .01/2,000 v., 1/9; 1 mfd., 2,000 volts, 3/6.  
**CERAMIC CONDS.** 500 v., .3 pf. to .01 mfd., 9d.  
**SILVER MICA CONDENSERS.** 10% 5 pf. to 500 pf. 11-1,000 pf. 15/-; Close tolerance (± 1 pf.) 1.5 pf. to 47 pf., 1/6. Ditto 1% 50 pf. to 815 pf., 1/9; 1,000 pf. to 6,000 pf., 2/-.

**I.F. TRANSFORMERS 7/6 pair.**  
 465 Kc/s Sing. Induct. Miniature Can. 2 1/2in. x 1 1/2 in. H. 2000 Hz. 2000 Hz. bandwidth.  
 By Frye Radio. Data sheet supplied.  
 Weirite M800 I.F. 465 Kc/s. 12/6 per pair.  
 Weirite 550 I.F. 465 Kc/s. 12/6 per pair.

**NEW ELECTROLYTICS. FAMOUS MAKES**  
**TUBULAR CAN TYPES**

|          |     |             |     |               |      |
|----------|-----|-------------|-----|---------------|------|
| 1/550v.  | 2/- | 64/350v.    | 5/6 | 8/500v.       | 3/-  |
| 1/245v.  | 2/3 | 100/225v.   | 2/- | 16/500v.      | 4/-  |
| 4/450v.  | 2/3 | 250/225v.   | 2/6 | 32/350v.      | 4/-  |
| 8/450v.  | 2/3 | 500/12v.    | 3/- | 100/270v.     | 5/6  |
| 8/500v.  | 2/9 | 84/8450v.   | 4/6 | 12,500/3v.    | 4/-  |
| 16/450v. | 3/8 | 84/8450v.   | 5/- | 50,000/6v.    | 5/6  |
| 16/600v. | 4/4 | 84/16450v.  | 5/- | 50-120/350v.  | 7/6  |
| 32/450v. | 5/6 | 84/16450v.  | 5/6 | 60+50/350v.   | 7/6  |
| 25/270v. | 1/9 | 16+16/450v. | 5/6 | 64+120/270v.  | 7/6  |
| 50/270v. | 2/- | 32+32/350v. | 6/6 | 64+120/350v.  | 11/6 |
| 50/500v. | 2/- | 32+32/500v. | 7/6 | 100+200/270v. | 12/6 |

**SELENIUM RECTIFIER.** 300 v x 85 mA., 7/6.  
**CONTACT COOLED** 250 v. 300 mA., 7/6; 60 mA., 8/6;  
 85 mA., 9/6; 200 mA., 81/-; 300 mA., 27/8.  
**COILS** Weirite "P" type, 3/- each. Osamor Midget "Q" type adj. dust core from 4/-. All ranges.  
**TELETRON.** L & Med. T.R.F., with reaction, 3/6.  
**FERRITE ROD AERIALS.** M.W., 8/8; M.L., 12/6.  
**T.R.F. COILS** 4/6. Hi-Fi CHOKES, 2/6.  
**FERRITE ROD.** 7in. x 3/8in. dia., 2/6.

**JASON F.M. TUNER COIL SET, 28/-.** H.F. coil, aerial coil. Oscillator coil, two I.F. trans. 10.7 Mc/s. Ratio Detector and booster choke. Circuit book using four 6AM6, 2/6.  
**COMPLETE JASON F.M. KIT WITH VALVES, 68.15.0.** Fringe area kit, 22/6 extra.

**FULL WAVE BRIDGE SELENIUM RECTIFIERS:**  
 2, 6 or 12 v. 1 1/2 amp., 8/9; 2 a., 11/3; 4 a., 17/6.  
**CHARGER TRANSFORMERS.** Tapped input 200/250 v. for charging at 2, 6 or 12 v., 1 1/2 amps., 3/6.  
 2 amp., 17/6; 4 amp., 22/6. 12/6 includes:  
**VALVE and T.V. TUBE** equivalent box, 5/-  
**TOGGLE SWITCHES.** S.P. 2/-, D.P. 3/6, D.P.I.T. 4/-  
**WAVECHANGING SWITCHES**  
 5 p. 4-way 2 water long spindle ..... 6/6  
 2 p. 2-way, 4 or 3 p. 2-way, 4 or 3 p. 2-way, 4 or 3 p. 2-way, 4 or 3 p. 2-way long spindle ..... 2/6  
 2 p. 6-way, 4 p. 2-way, 4 p. 3-way long spindle ..... 3/6  
 3 p. 4-way, or 1 p. 12-way long spindle ..... 3/6  
**VALVEHOLDERS.** Pax. Int. Oct., ad. EP50, EA50, 6d. B2A, CRT, 1/3. Eng. and Amer. 4, 5, 6, and 7 p. 11/.  
**MOLDED WAZZA** and Int. Oct., 6d.  
 BTG, BS4, BG, BOA, 6d. BTG with can, 1/6.  
 B9A with can. 1/8. CERAMIC EP50, BTG, B9A, Int. Oct., 1/-, S/Caus. B71, B9A, 1/-.  
**TELETRON "TRANSDYNE"**  
**MIDGET SUPERSET PORTABLE** 5" x 4" x 1 1/2" 6 transistors, printed circuit. Ferrite aerial. All parts and cabinet, 211.19.6.  
 We include 6 Ediswan or Mullard Transistors for maximum performance. Details 6d.

**RADIO COMPONENT SPECIALISTS**  
 OUR ONLY ADDRESS  
 337 WHITEHORSE RD.,  
 WEST CROYDON

48 Hour Postal service. 1/-, over £2 free. (Export Extra.) C.O.D. 1/6. (Wed. 1 p.m.) Catalogue 1/6. THO 1665. Buses 133 or 68





**EF86**  
Low hum, low noise voltage amplifying pentode.



**ECC83**  
High  $\mu$  double triode with separate cathodes.



**EZ81**  
Full wave indirectly heated rectifier with maximum output of 150 mA.



**GZ34**  
Full wave indirectly heated rectifier with maximum output of 250 mA at  $V_a$  (r.m.s.) = 2 x 450V.

*Made for music*

Mullard Audio Valves have been acclaimed for their superiority all over the world, and are fitted by leading equipment manufacturers both in this country and overseas.

Whether you buy or build your audio equipment, make sure it is fitted with Mullard Audio Valves.



**EL34**  
Output pentode with 25W maximum anode dissipation.




**EL84**  
Output pentode with 12W maximum anode dissipation.

**MULLARD LTD., MULLARD HOUSE, TORRINGTON PLACE, LONDON W.C.1.**  
MVM 412
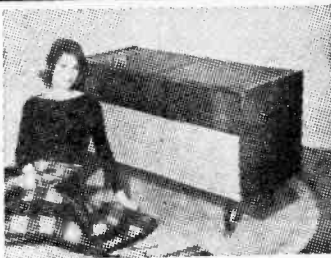
## Build your own HI-FI!

*At last! A specially selected and designed HI-FI Sound Installation for your home at really reasonable cost!*



You save because you assemble everything yourself following our step by step instructions. You gain because you learn about the equipment as you build and are able to service and maintain it afterwards.

Best of all—you'll have fun building it and be thrilled with the finished instrument which will bring you an entirely new experience in the enjoyment of sound. No previous skill or experience is needed. Post coupon now for full details, without any obligation. Easy terms available.

Equipment includes: Luxury Cabinets · Top Quality Amplifier suitable for stereo or non-stereo reproduction · V.H.F./F.M. Radio Units · Record Player · Tape Recorder · Hi-Fi Speaker system.

**FREE BROCHURE — POST TODAY**

Radiostructor (Dept. H34), 46 Market Place, Reading, Berks.  
Please send Brochure without obligation to:

Name \_\_\_\_\_ **BLOCK CAPS PLEASE**  
Address \_\_\_\_\_

309 12.59  
*We do not employ representatives*

RADIOSTRUCTOR

BRITAIN'S LEADING RADIO TRAINING ORGANISATION

### AMPLIFIER IN CABINET



Vol. tone, on-off.  
82/6 (3/- p. & p.)

Beautifully finished wood cabinet with "gold" and brown dividing strip and "gold" finished fabric front. Size 13" x 7½" front to back 4½". 5" P.M. speaker. ECL82 valve with metal rectifier. Cabinet only 20/-, plus 2/- post.

### COILPACK




I.F. 465-470 kc/s.; complete with two-gang tuner; fully aligned and tested.

Type 1. For 41M-120M, and 16-49 M. Price 20/-.  
Type 2. For 25-75 M. and 200-550 M. (22/6.)

BOTH POST PAID
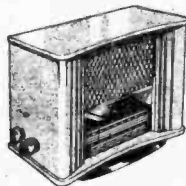
### COMPLETE V.H.F./A.M. RADIO FOR £12.12.



Brand new set, in superb walnut cabinet (size 19" x 8½" x 14½" high). Covering 80-100 Mc/s, 16-49 M., 200-500 M. and 1,200-2,000 M. Mains trans. 200-250 v. with 3 tapings. Ferrite rod aerial for A.M. Controls: volume on/off, tone, tuning, w/change, Gram. and ext. speaker position provided. Fully

guaranteed. Post and packing 10/- extra. Terms: £3.12.0 down (inc. carr.) and 5 monthly payments of £2. Indoor V.H.F. aerial 10/- extra, cash.

**UNIC Ltd., 25 Wordsworth Rd., Worthing, Sussex.**

# An Experimental "Super" Transistor Receiver

AN UNUSUAL DESIGN USING A "BASKET" COIL  
By Capt. R. F. Graham

THE basic circuit of this receiver gives phone reception without any aerial or earth. This, however, is not advisable because only a very small maximum output is permissible from an R.F. transistor. In the practical circuit an audio transistor is therefore added. Phone reception is then very loud from a BBC station 50 miles distant.

### Circuit

This circuit was evolved by simplifying the superhet first stage mixer. Instead of the many separate coils (which have many snags), taps and auto-transformer methods were tried, gradually reducing coils to one with an untuned end tending to produce a lower frequency. I.F. and other frequencies which vary with tuning. A diode is therefore used to rectify all the frequencies and a sort of reflex action is thereby added. The transistor amplifies both R.F. and A.F. and output is increased enormously. Local stations come in perfectly, but weaker ones need boosting by feedback which produces partial super-regeneration.

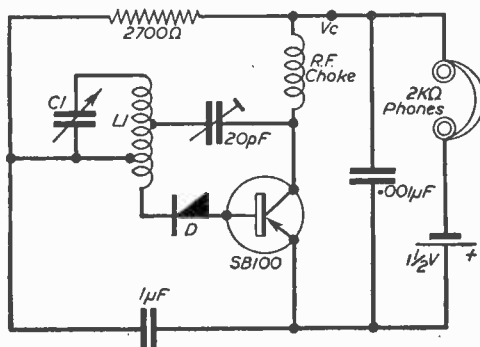




Fig. 1.—The basic circuit.

### The Practical Circuit

Variable condenser C1 (500pF) tunes part of L1, a directional loop coil. R1 (270k) supplies bias to Tr1 base, through the other part of L1 and diode D. Input is from the untuned section of L1, to base and emitter, through C3 (1μF). Output is from collector and common emitter. R.F. from collector is stopped by R.F. choke L2 but the audio passes through to C5 (8μF) and on to Tr2 base. C4 (0.001μF) by-passes stray R.F. and prevents overloading of Tr2. C2 (20pF trimmer) controls R.F. feedback into L1. This increases both sensitivity and selectivity. The output load for audio Tr2 is R2 (5,600 ohms) in parallel with the R3 (22k) and R4 (2.7k). The voltage divider resistors supplying bias to Tr2. These three are high in value and necessitate stabilising Tr2 but since 2k phones are used, peak currents are limited to a safe value, and the total battery drain is less than one milliamp.
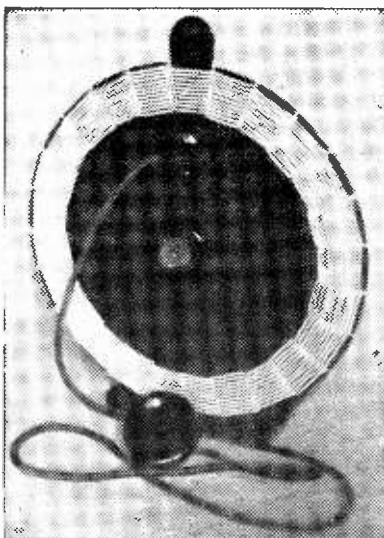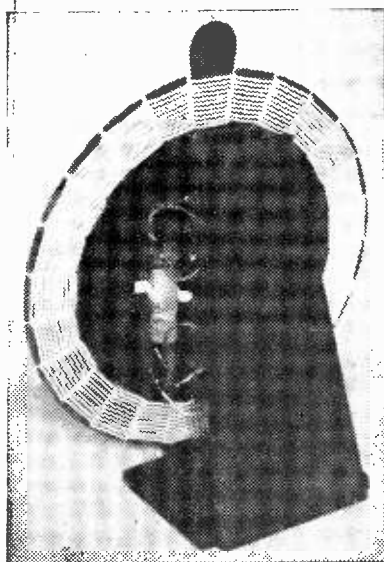
### Aerial Circuit

The A and E circuit is for Continental or weak signals. It is not needed for local broadcasts. It is in a separate box with a loop coil on top, like L1, but without extra untuned turns. C (500pF) tunes L (200μH). An indoor aerial should be at least 10 yards long and connected to the third turn from the earthed end. For an outdoor aerial one turn suffices. The optimum coupling between coils is obtained when they face each other 1ft. apart. Less spacing reduces selectivity and gain may fall. More spacing reduces sensitivity but increases selectivity. Care must be used, even while tuning slowly, to



Front and rear views of the author's receiver which shows clearly the construction of the tuning coil.

avoid suddenly overloading the receiver. Coils should be far apart, 2 to 3ft. usually, for phone reception. Do not connect an aerial direct to the receiver. It is important to note that L can add considerably to signal input, if it faces L1 the correct way round. However, L can also absorb signal from L1 if the aerial or earth are poor.

This unit can be used without an aerial and earth, as an absorption meter, for station identification if C is calibrated. Place L about 18in. from L1 and tune L until the station is hardly audible; then read frequency in kc/s (calibrated on C). To calibrate C tune to known stations and draw a graph.

### Tests and Details

The diode and the transistors must be really good to cope with small signals. The best way to test, more accurately than some expensive testers, is as follows:— use a high resistance volt meter on the 2.5 volts D.C. range, with its positive lead connected to the positive terminal of a 2 volt accumulator. Connect the negative lead on to the diode cathode (red end) and touch the negative accumulator terminal with the anode end of the diode.

### Bias— $I_c$ , Vc

Since Tr1 bias affects feedback, it may be desirable to replace R1 by 180k or 220k in series with a variable 100k for adjusting  $I_c$  from 0.1 to 0.3mA but usually 0.2mA is best. This is measured between the junctions of L2-C4 and R2-R3 where  $I_c = 0.2mA$  is shown on the circuit. Voltage drop across R2 provides Tr1 with  $-1.3$  volts. This can be measured at point Vc on the circuit.

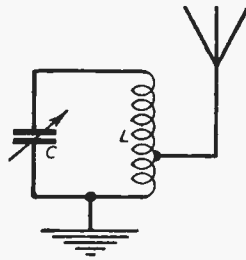


Fig. 2.—A and E circuit.

Tr2 works at an  $I_c$  of between 0.5 and 0.6mA measured between phones and (—).

### Feedback

The trimmer C2 must not short at any adjustment. A fixed 20pF mica or ceramic in series with about 50pF variable may be preferred, or better still, a small reaction type with rotating vanes in between two sets of fixed plates, one of which is connected to (+) for bypassing excess RF. This C2 should be on the panel, with C1 and switch S, because it needs readjusting slightly at the higher frequencies where most transistors do not amplify so well. It should be borne in mind that the following alterations increase feed-

back or produce turns ratios tending to create oscillations: (1) Increasing C2; up to 10pF should suffice in all cases. (2) Increasing turns for C2; from 10 to 11 turns. (3) Increasing bias, from 0.1 to 0.3mA Tr1,  $I_c$ . (4) Reducing turns between D and C3 (from seven to six). (5) Making C1 tune two or three more turns; crossing over the tap for C3.

These readjustments should be tried in the order given, testing the receiver at high and low

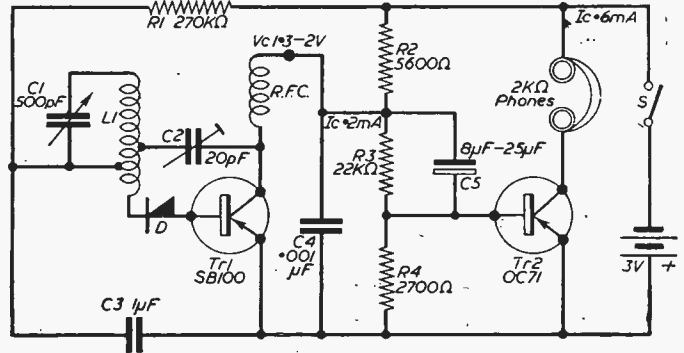


Fig. 3.—The practical circuit.

frequencies each time, reverting to the best as soon as instability becomes apparent. Do not exceed by more than one turn the recommended numbers, except for C2 tap—a few extra turns may be needed if the choke or Tr1 is poor. Note, diode is connected to the inner end of the coil. With the circuit as given, best results are C2 varying from zero to about 8μF and taps fixed at 11th and 7th turn counting from the diode end; Vc, 1.3 volts; Tr1- $I_c$  0.2mA; Tr2- $I_c$  0.6mA and the total current from the battery is less than 1mA when giving loud phone reception. It is possible to tune in stations from lowest obtainable frequency to nearly one megacycle without readjusting C2 if it has been correctly pre-set.

Strictly avoid turning C2 full on as all kinds of oscillations will be produced from whistles to growls which cause  $I_c$  to jump to over 1.5mA.

### R.F. Choke

The R.F. choke may be any high Q type of I.F. coil, if it has no capacitor across the windings, or it can be wound on a piece of three-eighth diameter ferrite rod with about 200 turns of thin wire, and if the layers are interleaved with thick paper strips, so much the better.

### The Loop Coil

The loop coil is easy to make, but time and care are needed for it to be pleasing to the eye. Cut a 12in. square of 1/16in. insulating material or 1/4in. fibreboard as used by builders. Draw the two diagonals to locate the centre and from this describe five circles: 1/4in., 8in., 8 1/2in., 9in. and 12in. diameters. With a protractor at the centre, mark off 25 points for 25 radial lines at equal angles of 14.4 degrees (360/25). The readings from zero will be: 14.4—28.8—43.2—57.6—

(Continued on page 663)



# A Simple B.F.O.

USE THIS UNIT WITH THE DOMESTIC SUPERHET

By R. H. Wright

**M**ANY enthusiastic listeners to the short wave bands using the domestic receiver are hampered by the fact that only modulated signals are rendered audible and so, on the amateur bands in particular, many choice

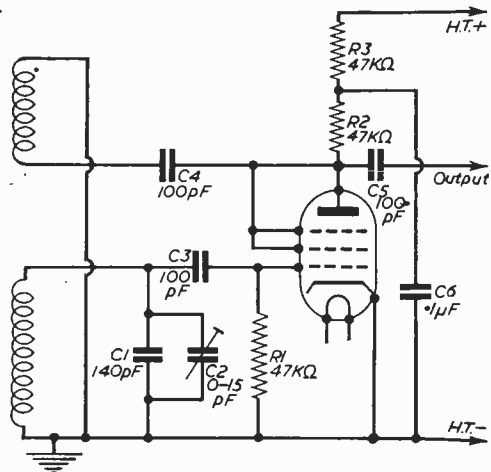


Fig. 1.—The circuit diagram.

“DX” stations are missed. However, there are two ways in which C.W. signals can be made audible thereby increasing the listening pleasure of those who have mastered the morse code. The first method is to make the intermediate frequency amplifier of the receiver oscillate, but as this involves circuit modification it is probably best left alone by all but the skilled service engineer. The second method is by use of a Beat Frequency Oscillator (B.F.O.).

Briefly, the function of a B.F.O. is to produce an oscillation differing from the intermediate frequency of the receiver by about one kilocycle per second. These two oscillations will now “beat” together to produce a third frequency equal to the difference between the two. For example, if the receiver I.F. is, say, 460kc/s and another oscillation of 461 or 459kc/s is injected into the receiver, an oscillation of 1kc—which is audible—will result and will be reproduced in the loud-speaker. This is the system employed in communications receivers.

### COMPONENT LIST

- C1—140 pF fixed capacitor } See
- C2—0.15 pF trimmer } text
- C3, C4, C5—100 pF fixed capacitor.
- C6—0.1 μF, 350 V.W.
- R1, R2, R3—47,000 Ω (1 watt).
- Valve—See text.
- Coil—Denco B.F.O. coil, type BF02/465.

A B.F.O. unit for use with most receivers can be constructed easily and a suitable circuit is shown in Fig. 1. The oscillator coil is a special beat frequency oscillator coil manufactured by Messrs. Denco (Clacton) Ltd., of Clacton, Essex. It may be obtained through any good component supplier. The complete unit may be constructed on a small chassis measuring 2½in. × 2½in. × 1½in. and so fit inside the cabinet of most receivers. The valve used in the prototype was an EF91, triode connected (anode, suppressor grid and screen grid pins joined together at the valveholder base). Power requirements are extremely modest being 250V at 5mA for H.T. and 6.3V at 0.3A for L.T. In many cases these supplies may be obtained from the receiver itself. Alternatively a separate power supply may be used. For readers with mains power supply difficulties who may wish to use the unit with a battery receiver, a battery powered version of the oscillator is just as effective. The circuit of this unit is shown in Fig. 2 and here the valve used was a Mullard DF92. A single U2 type cell provides L.T., and H.T. may be obtained from a dry battery of 45V.

With either unit, the capacitor arrangement shown in the grid circuit of the oscillator enables the unit to tune to any frequency between 450 and 470kc/s thus covering the I.F. bands.

To bring the unit into operation a length of insulated wire should be taken from the output point and allowed to lie near the I.F. section of the receiver. The best position to give a suitable degree of coupling can only be found by trial

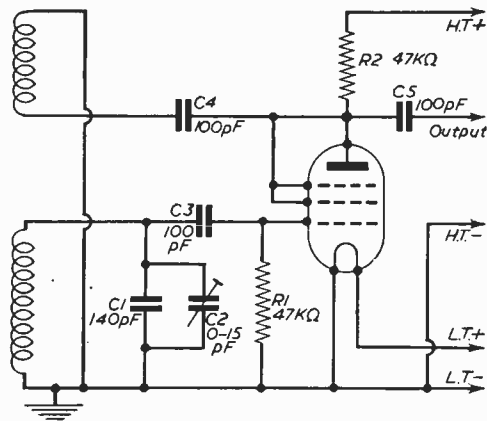


Fig. 2.—A battery version.

and error. Now tune to a signal on the receiver and adjust the trimming capacitor (or variable, if used) until a beat note is heard. C.W. signals will now be received, but for telephony or broadcast reception, the unit must be switched off. When first adjusting the unit, note particularly if it causes a marked reduction in the strength of the signal being received. If so, the B.F.O. is adding to the action of the Automatic Gain Control and therefore coupling between the unit and the receiver should be reduced. On the other hand, if the beat note is very weak, coupling should be increased.

# Choosing Resistors

PROPERTIES OF VARIOUS TYPES OF RESISTOR

By J. B. Dance, M.Sc.

**T**HE two most important features of a resistor are its power rating and the resistance value. If these two quantities are chosen correctly, the resistor will normally function satisfactorily in simple low frequency circuits, but for some applications it is necessary to choose a resistor more carefully.

therefore, be used as load resistors in the early stages of high gain audio amplifiers.

## H.F. Frequencies

Composition resistors are the best type for use at radio frequencies. Nevertheless, the resistance at high frequencies is usually less than that at low frequencies. At 30Mc/s a normal 1M resistor only presents an impedance of a little over 1/10M. This effect is less for resistors which have a small value and for frequencies which are not too high. If the resistance in ohms is multiplied by the frequency and the product obtained is not greater than about  $5 \times 10^9$ , then the resistance at that frequency will be approximately equal to the resistance to direct current. For example, a 1M resistor may be expected to have an approximately constant resistance up to about 50kc/s, a 10,000 ohm resistor up to 5Mc/s and a 100 ohm resistor up to 500Mc/s. Generally resistors for use at high frequencies should be long rather than have a large diameter and the connections should be short.

Resistors for use at high voltages (over 2,000V) should be long. It is better to use two or more resistors in series than to use a single resistor for very high voltages in order to reduce the possibility of flashover.

**TABLE I.**  
Typical sizes of ordinary composition resistors.

| Power Rating (W) | Diameter (in.) | Length (in.) |                 |
|------------------|----------------|--------------|-----------------|
| 1/10             | 0.15           | 0.4          | Ceramic tube    |
| $\frac{1}{2}$    | 0.25           | 0.7          | Ceramic tube    |
| 1                | 0.25           | 1.25         | Ceramic tube    |
| 2                | 0.4            | 2.0          | No ceramic tube |
| 5                | 0.7            | 2.5          | No ceramic tube |

The power rating of a resistor in watts is the voltage across it multiplied by the current in amps passing through it. If excessive power is dissipated in a resistor, it will become hot, will probably change in value and may burn out completely if the overload is very great. Calculations of the power rating which a resistor should have for a particular purpose was discussed more fully on page 402 of the July, 1959, issue of PRACTICAL WIRELESS by F. G. Rayer.

## Carbon Composition Resistors

The ordinary cheap composition resistor usually consists of a composition carbon rod inside a ceramic tube. There are brass caps at each end of the carbon rod and connecting wires are fastened to these caps. The body of the resistor (consisting of the ceramic tube) is colour coded and is an insulator. There are certain types, especially for high power ratings, in which the ceramic tube is omitted. Care must then be taken to prevent the body of the resistor from touching the chassis or any wire.

If the power rating of a resistor is unknown, the approximate rating may be found from its size. Table I shows the actual sizes of some resistors of various power ratings. If the resistor becomes too hot, a waxy material may often be seen dripping from it.

The composition resistor usually generates from ten to one hundred times as much noise as the cracked carbon type of resistor and the noise increases with the amount of power being dissipated in it. Composition resistors should not,

**TABLE II.**  
Typical sizes of high stability cracked carbon resistors.

| Power Rating (W) | Diameter (in.) | Length (in.) |
|------------------|----------------|--------------|
| $\frac{1}{2}$    | 0.17           | 0.75         |
| $\frac{1}{2}$    | 0.18           | 1.1          |
| 1                | 0.32           | 1.3          |
| 2                | 0.32           | 2.0          |

## Cracked Carbon Resistors

Cracked carbon resistors are also known as high stability or grade 1 resistors and are much more expensive than composition resistors. They consist of a ceramic tube with a thin carbon film deposited on it by means of a special process. Metal caps are fitted over the ends for making connections. A spiral cut is made in the carbon film so that the current has to go a longer distance through the carbon. The value of the resistor can thus be raised somewhat as desired. A coating is painted over the carbon track, but the insulation is not always very good and it is advisable to keep the body of the resistor away from the chassis and other metal objects. Measured sizes of some typical grade 1 resistors are shown in Table II. These resistors are not usually made in 1/10W size.

Grade 1 resistors normally have a tolerance not greater than 5 per cent. and even though they may be marked with this tolerance, they are almost always within 1 per cent. or at least 2 per cent. of their marked value. The value and tolerance are normally written on them, i.e., they are not colour coded. The value of these resistors remains very constant during use—hence the name high stability. Grade 1 resistors should always be used when accurate values are required, e.g., in certain devices such as filters which depend on accurate phase changing.

### Noise

The noise generated by a cracked carbon resistor increases with applied voltage approximately as shown in Fig. 1. The graphs are for one particular value of resistor. It will be noted that there is some noise even when no voltage is applied across the resistor. This noise is called

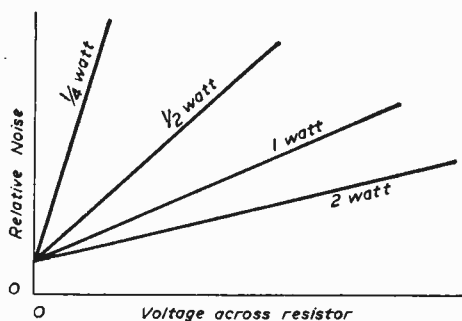


Fig. 1.—Graph of noise generated by a cracked carbon resistance against applied voltage.

“Johnson noise” and it can be shown theoretically that it is not possible to make a resistor which generates less noise than this. Grade 1 resistors are very useful in the anode circuits of the early stages of high gain amplifiers where minimum noise is important. A resistor of much larger power rating than the actual power which it will have to dissipate should be used when any current is passing through it. When the current is extremely small, however, a  $\frac{1}{4}$ W grade 1 resistor gives no more noise than a 2 watt resistor (see Fig. 1).

Cracked carbon resistors have the disadvantage that they possess considerable inductance owing to the fact that the current has to pass along the spiral carbon track which acts as a coil. They are not, therefore, very suitable for use at high frequencies.

### Vitreous Resistors

Vitreous resistors are wire wound resistors, the wire normally being wound on a ceramic tube and being covered with a green or blue vitreous enamel. This type of resistor is always made for high power ratings, as vitreous resistors operate satisfactorily at temperatures up to several hundred degrees centigrade. They are smaller than carbon resistors of the same power rating because they can work at a high temperature;

TABLE III.  
Typical sizes of vitreous resistors.

| Power Rating (W) | Diameter (in.) | Length (in.) |
|------------------|----------------|--------------|
| $4\frac{1}{2}$   | 0.27           | 1.5          |
| 6                | 0.30           | 1.5          |
| 10               | 0.43           | 2.3          |

typical sizes of vitreous resistors are shown in Table III. This type of resistor normally has a tolerance of 5 per cent. or better. Vitreous resistors have a considerable inductance because of the number of turns of wire on them and are not therefore suitable for use at high frequencies. The inductance of a vitreous resistor is high enough for it to be used as a combined choke and resistor for certain purposes.

### An Experimental “Super” Transistor Receiver

(Continued from page 660)

72.0—86.4—100.8—115.2—129.6—144.0—158.4—172.8—187.2—201.6—216.0—230.4—244.8—259.2—273.6—288.0—302.4—316.8—331.2—345.6—360.0. Draw radii through these points. Add two parallel lines  $\frac{1}{4}$ in., one at each side from the  $8\frac{1}{2}$ in. diameter circle to the edge of the board. Cut out 25 radial slots  $\frac{1}{4}$ in. wide, between the two parallel lines, from the edge to the 9in. or  $8\frac{1}{2}$ in. or 8in. if necessary. File the saw cuts smooth and round off all the sharp edges. If the coil is wound into this square frame, it can be used for the back cover of the receiver. If it is fibreboard, apply two coats of varnish.

### Plug-in Coils

If it is to be a plug-in coil, cut off two opposite corners around the 12in. diameter circle. Shape one end for holding the coil and the other end for fixing on to a block with four valve pins, to which tap leads can be soldered. The coil is wound with 20 s.w.g. 0.036 wire (plastic insulated). Starting from the plug-in corner, pass the wire into a slot from the front and back out of the next slot, pull and flatten the wire at the back, against the board, then into the third slot and out of the fourth, zig-zag all round, pulling and flattening the wire at each section to make a neat, evenly spaced coil almost up to the 12in. diameter circle. There should be 28 turns.


The coil for the aerial, if wanted, should have 20 turns up to the 12in. diameter circle. Ferrite rod coils were tried, but did not give good results even when Litz wound with spaced turns.

### Construction

The construction is not critical; a small panel may be used or the components may be mounted on to the middle of the coil board. The R.F. choke should be near to the collector of Tr1 and C2, with its turns not magnetically coupled to the loop but at right angles, or screened.
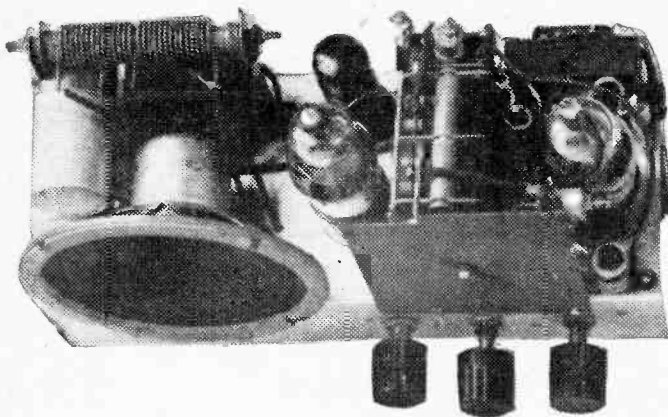
# A Mail

*This design allows c  
of valves and other c*



very low, due to the modulation hum filter aerial circuit, the type of detector, and additional H.T. smoothing to the latter.

### Valves

The cheap surplus 9D2 is used in the R.F. stage, but direct equivalents such as the 13VPA, C50N, and VP1322 can be inserted instead. Octal types such as the 12K7 and KTW74M are virtually equivalent except for the change of holder. All these may be run from a 12.6V heater transformer. In the 6.3V types, the 6K7, OM6 and KTW63 all give similar results. Any of the foregoing may be used in the R.F. position with no wiring changes.

**T**HE circuit is shown in Fig. 1, and details of alternative valves of suitable type are given later. A standard 3-valve T.R.F. receiver of this kind can provide a good selection of stations. Either air- or dust-cored coils can be fitted, the latter being recommended. The volume control reduces input, as well as increasing cathode bias applied to the R.F. stage, and this allows even a powerful local station to be kept at low volume if required. An anode bend detector and triode connected power output stage follow. Hum is

For detector, a 13SPA may be inserted instead of the 8D2. The 12J17, with octal holder, is also suitable for 12.6V. In the 6.3V range, the 6C6, 6J7 and 6BR7, with appropriate holders, have equivalent characteristics.

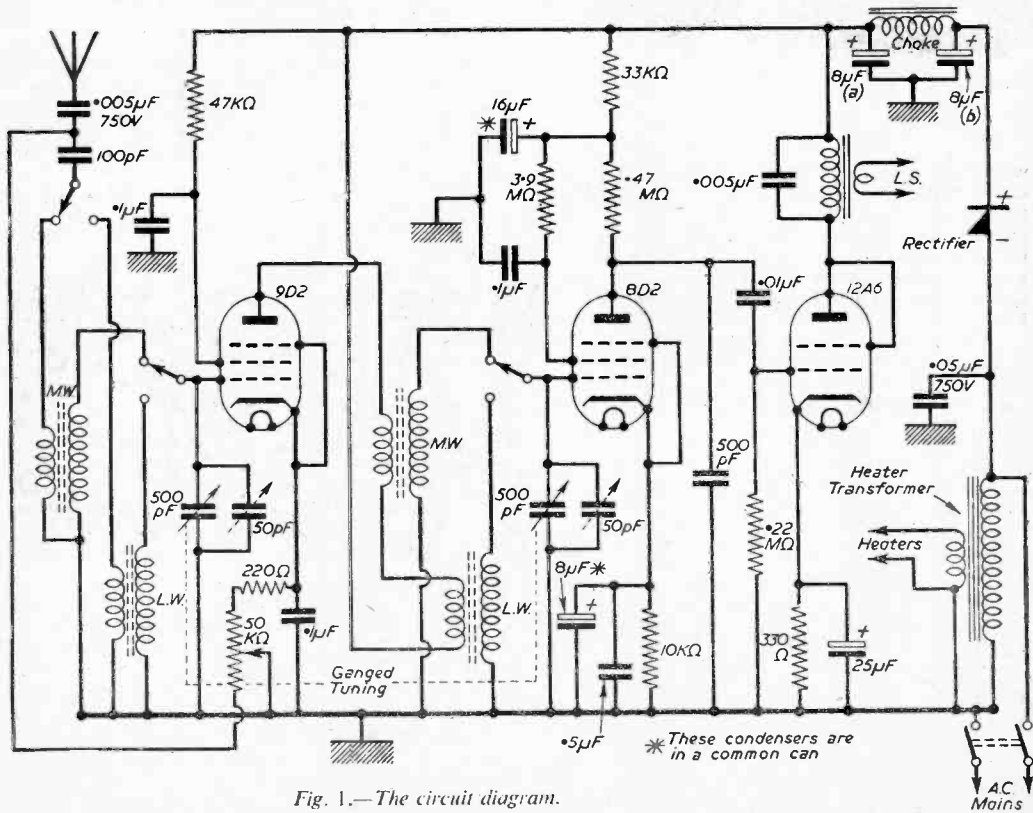



Fig. 1.—The circuit diagram.

# s: 3-Valver

siderable latitude in the choice  
omponents By F. G. Rayer
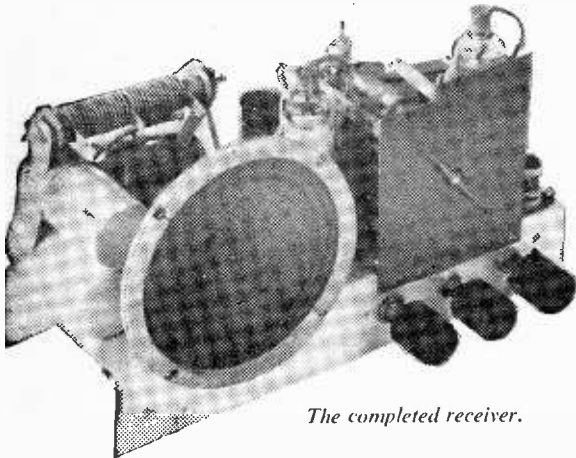
## Output Valve

For output purposes, the 12A6 is intended for a 12.6V heater supply, and gives good results, requiring an anode load of about 7.5k. and a 350 ohm bias resistor. For 6.3V operation, a 6V6, 6AQ5, or 6BW6 may be used, with 5k transformer, and 270 ohm bias resistor. A 6F6, with 7k load, and 440 ohm bias resistor, or 6K6G,



The completed receiver.

with 7.6k load and 500 ohm bias resistor. will be satisfactory, if to hand. These optimum loads are for normal pentode or tetrode operation, and a transformer of rather lower ratio will be found to give best results when the valve is triode wired, by joining anode and screen grid, as in Fig. 1.

For 6.3V valves, a 6.3V transformer should be used. For two 6.3V valves, with 12.6V output valve, a 12.6V transformer is required, the R.F. and detector heaters being wired in series. The various 12.6V and 13V valves listed also require a 12.6V transformer.

## Chassis Drilling

Fig. 2 shows the receiver layout, a chassis about 10½ in. X 4½ in. X 2 in. deep being just large enough to accommodate the components. The positions of valveholders, etc., can often be adjusted to suit a ready-drilled chassis. If not, all large holes should be completed before mounting any components. The speaker is best left until last.

The rectifier can be mounted on brackets as shown in Fig. 3. One bracket is bolted to the top of the output transformer, the outer shaped

section being temporarily removed for drilling, and countersunk 6 B.A. bolts inserted from below. The second rectifier bracket can be bolted or soldered to the long clip which secures the two smoothing condensers, as also shown in Fig. 3. Rectifier tags or fins must not touch other parts, and the positive rectifier tag must be taken to the smoothing circuit.

If a small cabinet is to be used, a cut-out will be required to accommodate the bottom of the

## COMPONENTS LIST

### Fixed condensers.

100pF; 500 pF; 0.005µF 750V.W.; 0.01µF (mica); 0.05µF 75V.W.; three 0.1µF 350V.W.; 0.5µF; three 8µF 350V.W. 16µF 350V.W.; 25µF 25V.W.

Two-gang 500pF tuning condenser. Drum, pointer, cord, spring and drive. Three knobs. Two 50pF trimmers.

### Resistors:—

220 ohms; 10k; 33k; 47k; 270k; 470k; 3.9M (all ½W). 350 ohm 1W.

50k potentiometer with double pole mains switch. 3-pole 2-way switch. Pair M.W. Aerial and Detector coils, ditto L.W.

### Valves:—

9D2, 8D2, 12A6. Two British 7pin holders and one Octal holder.

12.6V 0.75A heater transformer for 200/250V mains.


60mA 250V metal rectifier.

Permanent magnet speaker with output transformer for mains valve.

speaker unit, as in Fig. 2. Cutting and drilling will be much easier with an aluminium chassis than with the steel type. Suitable holes should also be drilled to match up with tuning condenser, heater transformer, and other parts, and to clear the tuning drive cord.
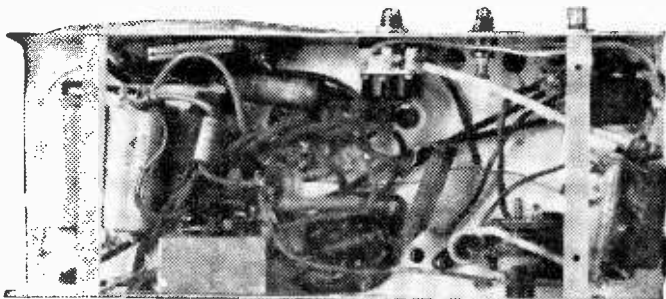
## Wiring

Most connections and small parts are shown in



Underchassis view.

Fig. 4; holder wiring being for the valves indicated in Fig. 2. The heaters should be wired first, for 6.3V or 12.6V running, one side of the heater circuit being returned to chassis. Other parts may then be added. All connections should be short and direct, and protected with insulating sleeving. If joints are sound, and checked as they are wired, the set should be properly as soon as it is completed.

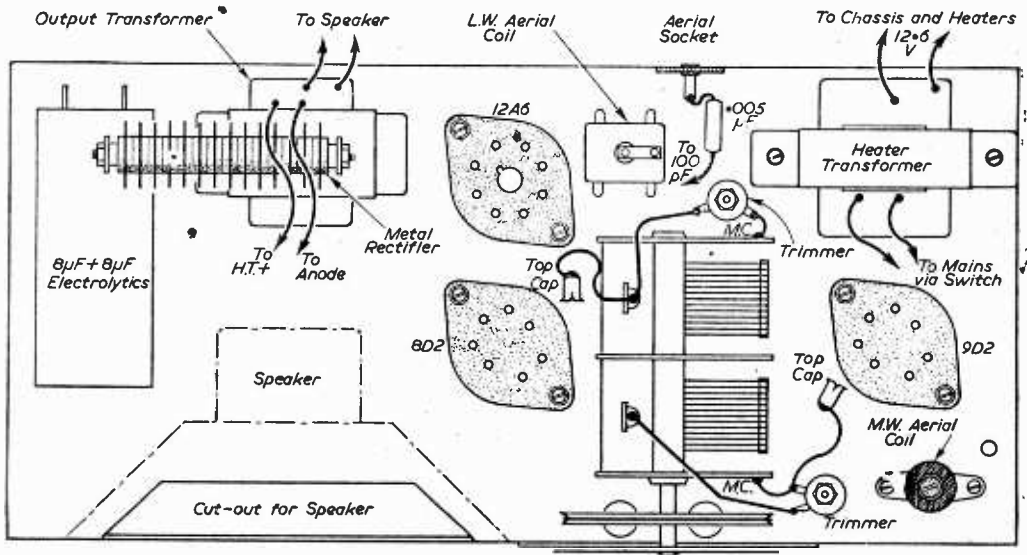


Fig. 2.—Above-chassis layout.

marked M.C. are soldered to tags bolted tightly to the chassis.

The two 750V condensers should be of high quality. The 0.005µF component serves to keep mains voltages out of the aerial, while the 0.05µF condenser must withstand the mains voltage. As shown in Fig. 4, a 16-plus-8µF condenser is used for detector cathode by-pass, in conjunction with a 0.5µF paper condenser, and also for anode decoupling and smoothing. Separate condensers are equally suitable. The electrolytic alone is not sufficient for cathode by-pass, with this circuit, for best results, but the paper condenser can be reduced to 0.1µF or 0.05µF, if this is to hand. The correct polarity must be observed when wiring up the electrolytic condensers.

In the receiver illustrated, the M.W. coils were

of different manufacture to the L.W. coils. This is not important, provided a pair of matched coils, for aerial and detector, is used for each waveband.

**Coil Connections**

Coil connections are shown in Fig. 5, and the tags can be identified from the maker's leaflet. Referring to the aerial coils, 1 is the aerial connection, 2 and 4 earth (chassis) connections, and 3 the R.F. grid connection. With the detector coils, 1 indicates R.F. anode, and 2 H.T. positive, these windings being connected in series, with no switching. As with the aerial coils, 3 indicates grid, and 4 chassis, or earth.

The aerial coils must be on top of the chassis, and the detector coils below, to avoid instability; Leads pass up through the chassis to the gang condenser, as in Fig. 5. Short lengths of flex are taken from the upper tags of the condenser, to the R.F. and detector valve caps, as in Fig. 2. Coil and switch wiring should be short and direct, and aerial coil wiring should be clear of the detector coil connections.

A 50pF trimmer is required in parallel with each section of the gang condenser, as shown in Fig. 2, unless trimmers are already fitted to this component.

**Mains Supply and Testing**

If the receiver is inserted in an insulated cabinet, with no exposed metal parts, the standard of safety will be that usual with A.C./D.C. sets, or A.C. sets drawing H.T. directly from the mains. If possible, it is best to use a non-reversible supply plug (e.g., three-pin) and to wire this so that the receiver chassis is taken to mains neutral. No shock will then be felt on touching the chassis. When the set is switched off, the double-pole switch completely disconnects it from the mains.

If the "live" main is taken to chassis, the

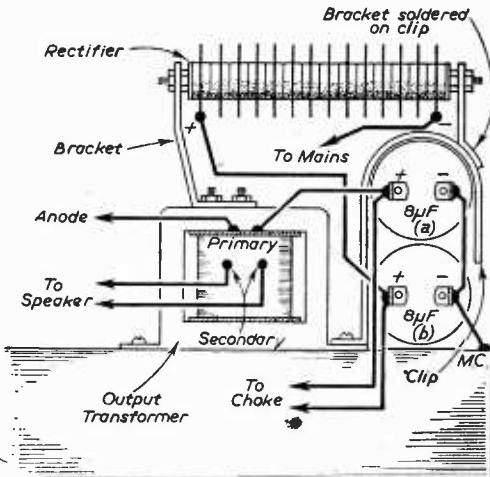


Fig. 3.—The power supply.



receiver, speaker, etc., will be at mains voltage above earth, and in no circumstance should they then be touched.

Alignment is extremely easy. The set should be switched to the M.W. band, and the trimmers are then adjusted for best volume from a station received at about 200 to 250m. A station around 450 to 500m. should then be tuned in, and the M.W. coil cores are adjusted for best reception. The procedure should be repeated once or twice, until no further improvement is possible. The L.W. coil cores are then adjusted for best L.W. reception.

**Dial Reading**

Pointer readings can be matched up with a printed dial by careful adjustment of trimmers and cores. With a surplus gang condenser, exact readings throughout the wavebands may be impossible, however. Trimmer settings will most influence low-wavelength readings, while high-wavelength readings, will be most readily modified by changing the coil core positions.

It was found that the use of a clear glass valve in either R.F. or detector positions resulted in the receiver just going into oscillation, at the maximum setting of the volume control. In such circumstances, adding a valve-screening can, bolted to chassis, removed oscillation. Oscillation is unlikely with screened valves, unless wiring

Above Chassis

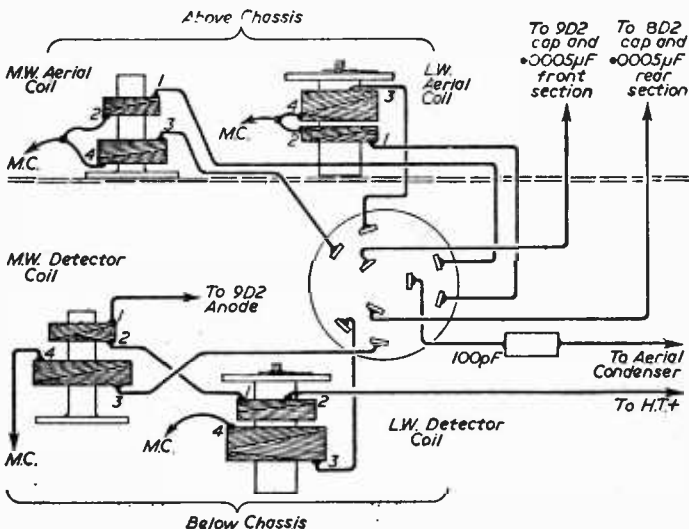


Fig. 5.—Coil and wavechange switch wiring.

causes stray coupling between aerial and detector circuits.

A few feet of flex or other insulated wire will form a suitable indoor aerial. Reception of weak stations will, of course, be improved with a longer or outdoor aerial, but the latter is by no means essential.

It will be noted that one side of the mains is connected to the chassis of this receiver. Accordingly, no earth connection must be made to the chassis and no part of the receiver should be touched when it is switched on.

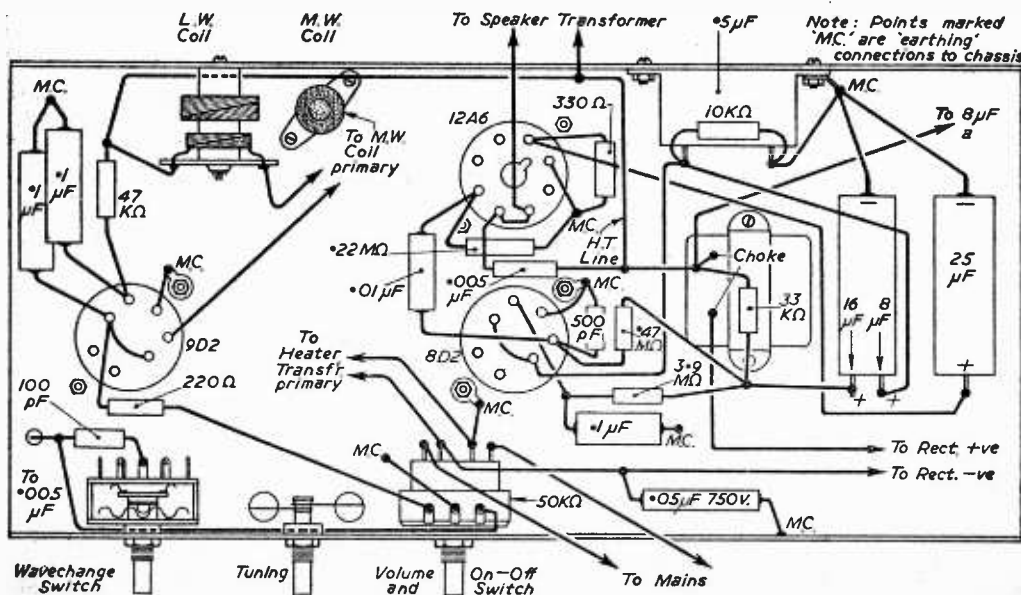


Fig. 4.—Under-chassis layout and wiring.

# A Charger and D.C. Unit

TAPPINGS PROVIDE SEVERAL OUTPUT VOLTAGES

By E. G. Heath

THIS unit is for use with A.C. mains, and gives any required direct current output up to a maximum of approximately 20V at 2A. It may thus be used as a charger for the accumulators employed to run models, etc. The output is also sufficient for charging motor-cycle or scooter batteries, or keeping large 6V or 12V car batteries in good condition.


## Models

With models having permanent magnet motors (such as electric trains) the unit allows running from the mains, with no battery. It may also be used to run model motors with wound field and armature, and to provide current for illuminated models, though in these cases A.C. taken directly from a transformer would serve.

The circuit is shown in Fig. 1, and the transformer has a tapped secondary so that various voltages may be selected. In addition to the voltages provided by adjacent tappings, two or more sections may be in use, to obtain other figures. For example, 2 and 4 provide 8V, 1 and 3 supply 10.5V, 1 and 4, 15V, 3 and 5, 18.5V, and so on. The 5 ohm variable resistance gives further adjustment, so that any voltage can be obtained. The maximum will depend on the rectifier rating, and there is normally no point in using a rectifier with a higher voltage rating than the highest voltage which will ever be required.
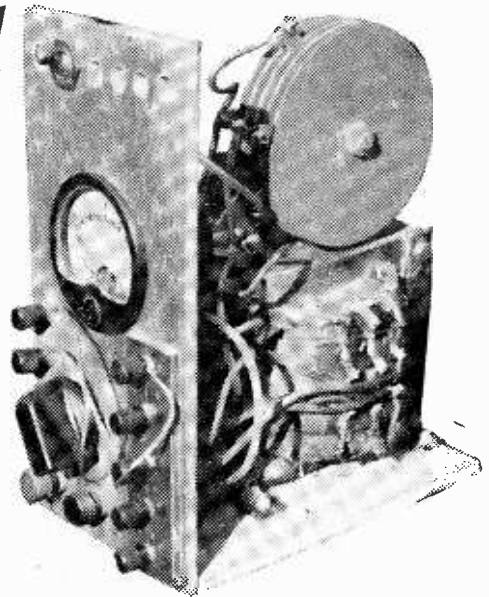
## Operation

To run a model, an approximate voltage is selected by fitting the two flexible leads to the



Construction of the unit.

terminals. The resistance control knob is then adjusted until the model runs at normal speed. If the voltage needed is not known, it can easily be found by trial, beginning with a low voltage and increasing until the model works normally.

For accumulator charging, select 4.5V for 2V accumulators, 10.5V for 6V accumulators, and 18.5V for 12V accumulators, slowly turning the control knob from maximum resistance, until the meter indicates the required charging current. For trickle charging, or to restore a cell left standing in a sulphated condition, a lower voltage can be selected.

## Transformer and Rectifier

Ready made transformers of this type can be purchased, and it does not matter if the secondary voltages are somewhat different from those given in Fig. 1. For a maximum output of up to 2A both transformer and rectifier should be rated for this current, at least. A rectifier intended for an input of up to 18V to 20V, or so, will be large enough for charging 12V accumulators.

If a transformer is to be wound 32s.w.g. enamelled wire can be used for the primary and 17s.w.g. or 18s.w.g. for the secondary. There is, of course, no reason why slightly thicker gauges should not be used provided the bobbin can accommodate the wire. If the transformer core has a cross-sectional area of 1sq.in. then eight turns per volt may be used for primary and secondary. That is, the centre stack of core

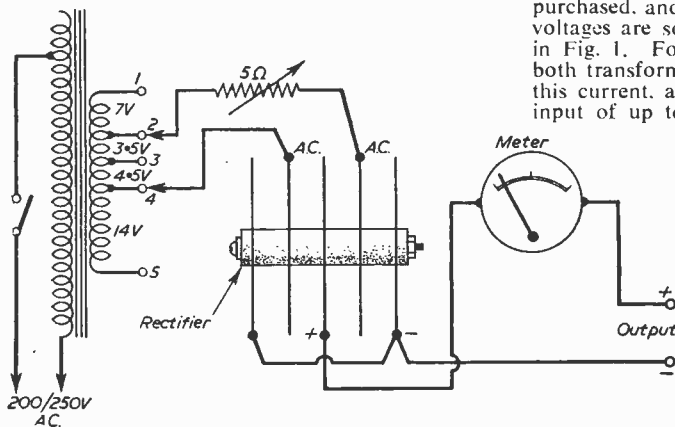


Fig. 1.—The circuit diagram.

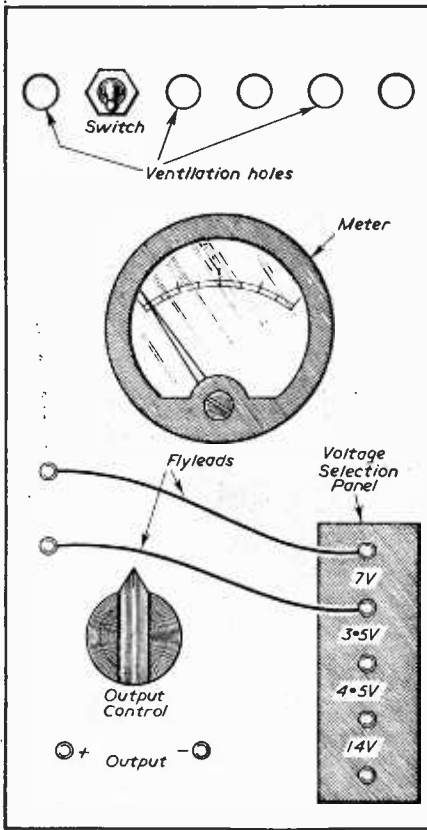


Fig. 2.—Control panel layout.

stampings would be 1in. X 1in., and the primary would have 1,600 turns for 200V, 1,840 turns for 230V, or 2,000 turns for 250V. Tappings for mains voltages other than that of the actual supply need not be provided, and a few turns more or less will be unimportant. Similarly, eight turns are used for each one volt required from the secondary. That is, 56 turns for 7V, then 28 turns for 3.5V, followed by 36 turns for 4.5V, and finally 112 turns for 14V. All turns must be in the same direction, and layers of insulating paper should be placed over each layer of wire. Ample insulation must be provided between primary and secondary.

**The Meter**

This can be purchased with the required range, or adapted from a cheap surplus meter. Thermocouple meters are among the least expensive, if one is to be used, it should be opened and the thermocouple taken out. The meter prongs or terminals are then used for connections directly to the meter moving coil, and the instrument is replaced in its case. It will then have a full-scale deflection of some 2mA to 5mA or so (the figure depends on the actual meter) and *must* be equipped with a shunt, before it can be used to read 0 to 2A. The shunt is a piece of wire, of

very low resistance, securely soldered across the meter terminals, as in Fig. 3. A few inches of 20s.w.g. copper wire will usually prove suitable.

The length of wire to use for the shunt can be found by trial. If a calibrated meter reading up to 1A or 2A is available, wire this in series with the output of the unit, then adjust the length of wire in the shunt so that the meter indicates the same current as the calibrated meter. Switch off each time the shunt is removed for adjustment. If the unit meter reads higher than it should, this indicates that the length of the shunt wire is too great.

If no calibrated meter is to hand, a lamp taking a known current can be connected to the output terminals. For example, a 6W 6V lamp will pass approximately 1A. The shunt is then adjusted as already described, until the meter indicates 1A. Other markings will then be proportional, as shown in Fig. 2.

**Construction**

With the layout shown in Fig. 2, a three-plate panel 3½in. X 7½in. will be suitable, but this can

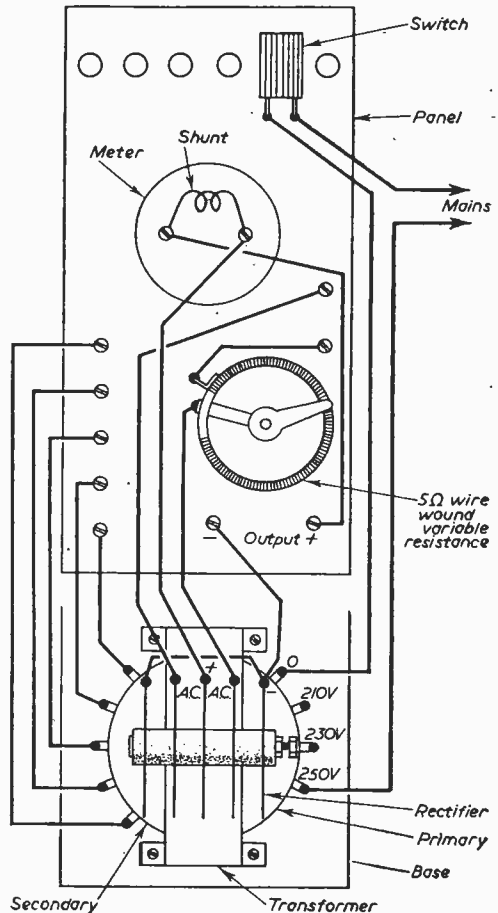


Fig. 3.—Wiring diagram.


be modified to suit an existing case or box. Terminals may be mounted directly on the wood, or on a terminal strip. The exact position of the various parts does not matter in a unit of this kind.

A clearance hole will be needed for a flush mounting meter. Some ventilation holes are also required, as indicated, unless these are present in the top and bottom of the case, or in the back near top and bottom.

Fig. 3 shows connections. Panel and base can be joined with angle brackets, and the transformer and rectifier must clear the resistance and meter. The rectifier can be mounted by securing it to two wooden or metal strips which are bolted to the transformer.
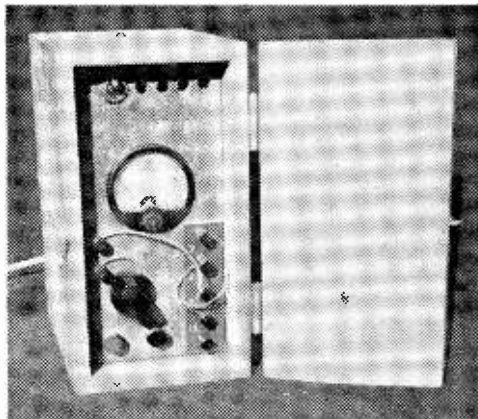
### Connections

Insulated flex can be used for all connections. The actual markings on the rectifier should be followed, because tags are sometimes placed in different positions. Green is sometimes used to indicate the "A.C." tags, with red for positive and black for negative. The rectifier fins should be vertical, to assist cooling. Very little heat will be generated with small outputs but when maximum output is required the transformer and rectifier will eventually warm up slightly.



*The unit in its case.*

A containing case is required, both to protect the unit and avoid any chance of mains connections being touched. If a three-pin plug can be used, the transformer core and one secondary terminal should be wired to the earth pin. When current is taken from a 13A point, a low-rating fuse can be inserted in the plug.

## British Institution of Radio Engineers

THE Council of the British Institution of Radio Engineers has announced the Awards which are to be made for outstanding papers published in the Institution's Journal during 1958. The senior award, the Clerk Maxwell Premium, goes to Mr. C. Powell and Mr. D. A. Hendley (Decca Navigator Company Limited) for the paper "Dectra: A Long Range Radio Navigation Aid" which was read at an Institution Meeting in March of last year and published in the May, 1958, journal.

Other awards are as follows:—The Heinrich Hertz Premium, which is for the most outstanding paper on the mathematical or physical aspects of radio is to be presented to Mr. K. Foster, (Cossor Radar and Electronics Limited) for the paper, "The Characteristic Impedance and Phase Velocity of High-Q Triplate Line." (Published in December, 1958.)

For the third successive year the Sir Louis Sterling Premium for an outstanding paper on Television Technique is to be awarded to Dr. A. van Weel (Philips, Eindhoven). His paper "Design of Detector Stages for signals with Symmetrical or Asymmetrical Sidebands," concludes his detailed examination of the design of successive stages of the television receiver.

The Sir J. C. Bose Premium is being awarded to three Indian physicists from Andhra University, South India. They are Dr. B. Ramachandra Rao, Dr. M. Srirama Rao and Mr. C. Abhirama Reddy. Their paper is entitled "Magneto-ionic Fading in Pulsed Radio Waves reflected at Vertical Incidence from the Ionosphere" and was published in November, 1958. Dr. M. S. Rao is now with the National Research Council of Canada.

The Brabazon Premium is for an outstanding paper on Electronic Aids to Aircraft Safety and it is to be awarded for two associated papers by members of the Electrical Engineering Department of Birmingham University—Professor D. G. Tucker, D.Sc., Dr. V. G. Welsby, Mr. R. Kendall and Mr. D. E. N. Davies, M.Sc. The papers are entitled "Electronic Sector Scanning" and "Radar Systems with Electronic Sector Scanning."

The Marconi Premium is the third of the Institution Premiums this year to be awarded to overseas engineers. It goes to Dr. Morton B. Prince and Mr. M. Wolf of Hoffman Electronics Inc., Evanston, Illinois, U.S.A. Their paper, "New Developments in Silicon Photo-voltaic Devices" was read at a meeting in London in June, 1958.

The award of prizes to outstanding candidates in the Graduateship Examination of the British Institution of Radio Engineers during 1958 has been announced as follows:—

The President's prize for the most outstanding candidate in Section B of the Examination is to be awarded to Kenneth Henry Green (now an Associate Member) of Woodmansterne, Surrey.

The S. R. Walker prize for the most outstanding candidate in Section A of the Examination is to be awarded to Dennis Grant Skinner of Romford, Essex.

The Electronic Measurements prize for the most outstanding candidate taking the Part optional subject of Electronic Measurements is to be awarded to Ian Frederick Howard Goult (now an Associate-Member) of Enfield, Middlesex.

**FULLY  
UP-TO-DATE  
EDITION**

**FOR  
READERS OF  
"PRACTICAL  
WIRELESS"  
AT REMARKABLY  
LOW COST!**

# RADIO, TELEVISION & ELECTRICAL REPAIRS


**SAVES YOU POUNDS!**

Here is just the practical, at-a-glance guidance YOU need, whether you wish to know how to service radio and TV sets, install an extra lighting point, or repair any domestic electrical appliance—from a bell or an iron to a vacuum cleaner or washing machine. Explains, in simple language, basic principles and working of modern radio and TV sets and electrical appliances. Shows how to test for faults and carry out maintenance and repair work by the most modern methods. Special section on the operation and servicing of frequency modulated receivers. 480 pages. Over 400 illustrations. Amazing value—Standard Edition, 18/-, De Luxe, Leathercloth, 20/- inc. postage, packing, etc.

## ESSENTIAL TO EVERY SERVICE ENGINEER, ENTHUSIAST AND HANDYMAN!
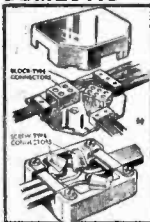
### GETTING THE BEST FROM RADIO AND TV SETS


Here is expert advice that will enable you to make the necessary adjustments or repairs in order to get the best possible performance from any radio or TV set. **All you need to know about DOMESTIC WIRING**



Learn from these helpful pages how to carry out all kinds of installations and extensions — with efficiency and safety! Complete guidance on conductors, insulation, safety regulations, conduits, cables, earthing, practical work, fuses, flexible cords, etc.
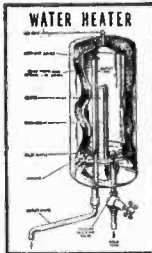
### BASIC RADIO CIRCUITS

All you want to know about circuits, so that you can find your way around modern sets without hesitation. How components form various types of set; gives circuits for one-valve receiver, 3-valve receiver, battery TRF receiver, 4-valve superhet, Universal sets, etc.



### FIRES & SPACE HEATERS


Full, easy-to-follow instructions for servicing small domestic fires—whether of the radiant, reflector or convector type.

### WATER HEATING

All you should know about the various types of electric water-heaters and how to install them and keep them in perfect working order. Advice that will save you POUNDS!
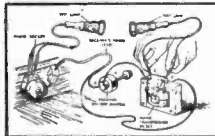
### TRACKING DOWN TROUBLE

This grand book is invaluable for tracing faults in radio and TV sets. Tells you all you want to know—from how to carry out Preliminary Tests to how to align R.F. and I.F. circuits. Shows how to carry out Dynamic Testing. Also shows how to trace the cause of Noises, Distortion and Instability and deal with the trouble. Gives detailed information on Components and Loud-speakers and how to deal with any faults that may develop.



### DO THIS NOW!

Simply fill in form and post in 2d. stamped, unsealed envelope to Dept. H.F.35, People's Home Library, Basted, Sevenoaks, Kent. Offer applies in U.K. and Eire only, closes Dec.31

**FULL SATISFACTION or No Charge GUARANTEED**



**480  
PAGES  
OVER  
400  
ILLUSTRATIONS**

## ALL THIS—AND MORE—IN ONE GREAT VOLUME

*Comprehensive Contents Include:*

Current, Voltage, and Resistance. Coils, Capacitors and Valves. Basic Radio-receiver Circuits. Preliminary Tests. Instruments for Set Testing. Locating Faults. Dynamic Testing. Tuned Circuit Alignment. Noises, Interference, Distortion and Instability. Components. Loudspeakers. Pick-ups. Gramophone Motors. Frequency Modulation. Television Circuits and Test Gear. Television Faults, Symptoms and Cures. Aerials and Pre-amplifiers. Maintenance of Domestic Electric Wiring. Small Appliances. Fires and Space Heaters. Vacuum Cleaners and Polishers. Rewinding Small Motors. Cookers and Boiling Plates. Washing Machines. Refrigerators. Electric Water Heaters. Battery Charging, Testing and Repair, etc.

The book that cuts out guess-work! **TV FAULTS—their SYMPTOMS AND CURES**

# POST FORM NOW!

Dept. H.F.35, People's Home Library, Basted, Sevenoaks, Kent.

WITHOUT OBLIGATION reserve me "Radio, Television and Electrical Repairs" and send Invoice with "100% Satisfaction or No Charge" Guarantee. Standard: De Luxe. Cross out Edition NOT wanted.

BLOCK LETTERS

NAME .....

Full Postal ADDRESS .....

Firmly affix 2d. stamp in margin

H.F.35/Dec. '59.




Disconnecting Boiling Plate on Cooker

See how to maintain Vacuum Cleaners and Floor Polishers, Refrigerators, Cookers and Boiling Plates, Washing Machines, etc.

**Do your own BATTERY CHARGING**  
Here are clear, complete instructions.
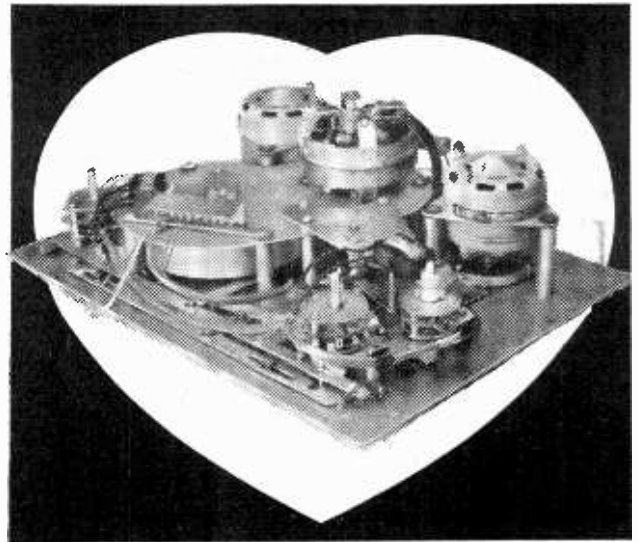
## The Heart of a good tape recorder is its DECK!

For the enthusiast who loves to experiment — who wishes to build up his own tape recording unit—to construct into his own furniture or to add to existing hi-fi equipment, the Brenell Mk. 5 Deck presents truly remarkable value. Its versatility of application has firmly established the Brenell in the hi-fi market as a general purpose deck with immense advantages. Superbly made, it is conclusive evidence of the skilful design for which Brenell are noted.



Four recording speeds : 1½, 3½, 7½ and 15 i.p.s. Permits use of 8½in. reels (3,600ft. of D.P. tape at 1½ i.p.s. plays over 12 hours) ; three independent motors (B.T.H.). Special foolproof interlocking controls. Instant stop without spillage. Pause control. Digital rev. counter. Fast rewind (1,200ft. in 45 secs.). Tape Deck with provision for extra heads. 28 Gns. Extra erase heads, £2.4.0 inc. pressure pads. Extra rec./playback heads (upper or lower track), £2.4.0 inc. pressure pads. Stacked stereo rec./playback heads, £10 inc. pressure pads. Also rec./playback amplifier with power unit, £24.




Performance is true-to-life performance

**BRENELL ENGINEERING CO. LTD.,** 1a, Doughty Street, London, W.C.1. Tel. CHA 5809, HOL 7358.

### A.M./F.M. RECEIVER


In beautiful Walnut Cabinet, 5 valves, internal Ferrite Aerial. Long, Medium and Short Wave, and F.M. Wave Bands. Price

**£12.12.0.** p. & p. 5/-

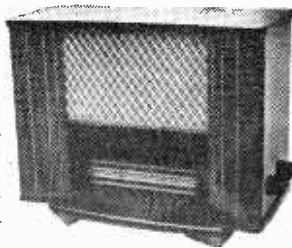

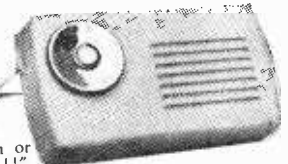
### POCKET TRANSISTOR SET

A six Transistor Radio to fit your pocket, the latest type printed circuit. Internal Ferrite Aerial operating 9 volt p.p. 4 battery, highly sensitive on medium wave band, housed in an attractive plastic cabinet in Red, Cream or Blue, size 5½" x 3½" x 1½", weight 12 oz.



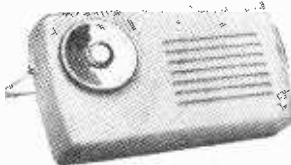Unrepeatable at the price of **£8.19.6.** p. & p. 2/6.



### TRANSISTOR KIT

A six Transistor pocket radio, can be built for


**£9.19.6.**

plus 3/6 post. Full medium and long wave superhet. Printed circuit construction, using latest miniature components. 2½" moving coil speaker, Ferrite Aerial. Choice of an attractive plastic cabinet in Cream, Blue or Red. Complete easy to build instruction book included. All Parts Sold Separately.

### AMPLIFIER AND CABINET

3-watt Amplifier, using an ECL82 Valve and Metal Rectifier, housed in a modern attractive styled walnut cabinet with 5" P/M Speaker and on/off and tone controls.

**£4.5.0.** p. & p. 3/6.

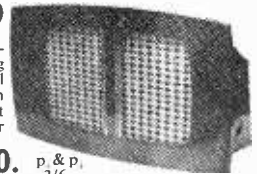

### RECORD CHANGERS

Collaro Conquest: 4-speed Auto Changers, turn over still, £7.19.6. Collaro AC4/564: Rim drive 4-speed player, turn over still, £6.9.6. Collaro Junior: 4-speed Single Player, Separate Pick-up £3.15.0, B.S.R. UA8 4-speed Auto Changer, Manual and Auto Control Dual turn over still, £6.19.6. Garrard RC120/D Mark 2, 4-speed Auto and Manual Controls, using GC2 Cartridge, price £9.9.0. Post and Packing 3/6.

We hold large stocks of Condensers, Resistors, Ceramics, Volume Controls, Speakers, etc.

**PLEASE SEND FOR OUR CURRENT PRICE LIST**

## WIRECOMP ELECTRONICS

**378 HARROW ROAD, LONDON, W.9. Tel.: CUNNINGHAM 9550**  
Hours of business : 9 a.m.-6 p.m. Open all day Saturday.



# A Stereo Amplifier

A SINGLE PUSH-PULL AMPLIFIER FOR BOTH STEREO CHANNELS HAVING  
MATRIXING OUTPUT TRANSFORMERS

By A. G. Bourne

IN the U.S.A. this circuitry has created considerable interest, and references have begun to appear over here. Without going deeply into the mathematics of the subject, one need just say that it stems from the simplex technique used for many years by broadcast line engineers.

complete push-pull amplifier with an inexpensive output transformer doing the job of two separate push-pull amplifiers is definitely desirable if cost, space and electronic simplicity is considered.

### Circuit

In effect, an ordinary monaural push-pull amplifier is two separate amplifiers, all valves and components being duplicated. The exception is that one pushes and the other pulls, the ties being at the input or phase inverter, outputs and power output transformer. Therefore, each side can be used for one of the stereo channels. The two channels of information in the stereo groove are referred to as right and left, but they really depend on the degree of vertical and horizontal motions; it is a relationship of sum and difference signals.

Without further ado, one fact, a limitation if

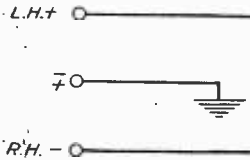


Fig. 1.—The required input phasing.

It has now been re-introduced for stereo application by the Columbia Broadcasting Company, though with several modifications. It enables one push-pull amplifier to amplify both channels of a 45/45 stereo recording. The idea of one

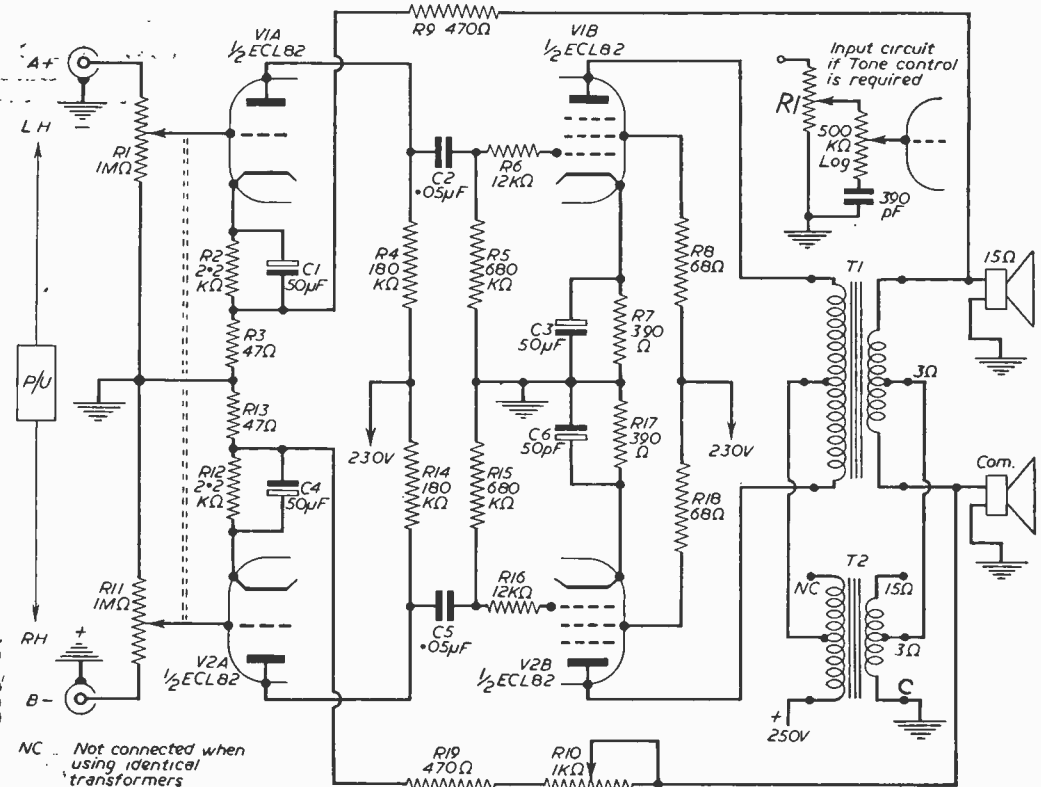


Fig. 2.—The circuit diagram.

you like, must be mentioned. Most stereo cartridges are phased in such a way that lateral motion gives two positive outputs, but with this circuit, it is necessary to reverse one set of leads. In other words the pick-up is connected with one

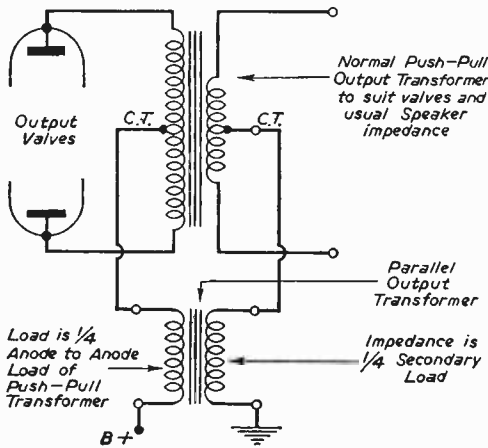


Fig. 3.—Using a single-ended output transformer for the parallel channel.

output positive and the other negative to supply the necessary input phasing. A four terminal cartridge is therefore needed and three terminal types which are not phased specially for this simplex operation cannot be used. The phasing of the two inputs is shown in Fig. 1.

**Valves**

It will now be apparent that one can, within reason, use valves for both high or low power output, and the author has constructed a very simple unit based on a medium power output, using ECL82s and an EZ80 rectifier, from which an acceptable output with adequate sensitivity is possible. The circuit is shown in Fig. 2. Again, 6V6s and EL84s have been tried with consequently higher outputs, adding one ECC83, an EZ81, and a further ECC83 with tone controls.

In the prototype, both transformers are push-pull types since they were on hand, but as pre-

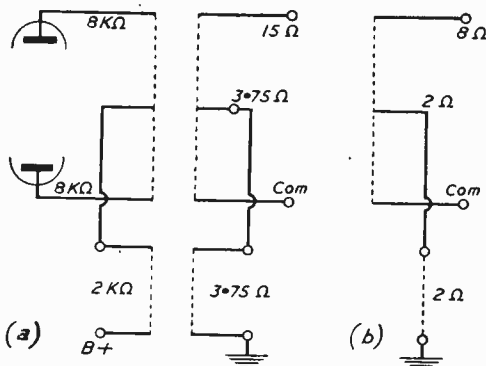


Fig. 4.—Examples of transformer connections.

viously mentioned a single-ended version would do equally well for the parallel channel provided the centre tap arrangements of primary and secondary were reasonably accurate (Figs. 3 and 4); nevertheless negative feedback does help in this direction. A balance control has been specified in one negative feedback chain, but, alternatively, separate volume or gain controls could have been chosen, and fixed negative feedback used for both channels.

**Loudspeakers**

The choice of speakers is left entirely to the constructor. Several methods have been tested with inexpensive and high fidelity types, either as separate full range units, or a combined bass speaker with two additional types for frequencies above 250c/s and crossover (see Fig. 5). Little if anything is lost by this latter configuration. In every instance satisfactory performance has been achieved. Perhaps a word might be necessary here to say that this design was not intended to compete with its much more expensive brothers. However, the overall quality from this compact system is very good. After one has played with express trains and racing cars, one settles for a compromise in the spacing of speakers. Theoretically, it seems, one should space these


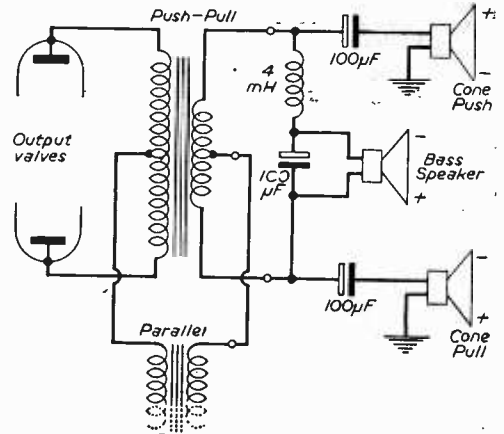


Fig. 5.—“Combined” bass speaker system for frequencies below about 250 c/s with separate loudspeakers for frequencies above 250 c/s. Signs plus and minus refer to a cone “pushing” and a cone “pulling” when checked with a torch battery for phasing. Some speakers are marked with a red line for the “push” condition.

six, eight or ten feet apart, situated equidistant from each. However, it's your home not an audio fair booth or dealer demonstration room! Likewise a pure 100W is necessary, etc., etc. Of course, some of the “gimmick” attraction for the benefit of friends is lost with close spacing of speakers, but there still remains the depth and clarity so noticeable with stereophonic reproduction of music, and the system shares the room with the furniture rather than replacing it. The choice is yours.

## D.C. OSCILLOSCOPE

A.C. MAINS 200-250 VOLTS

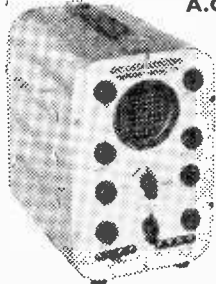

**SIMPLIFIED SERVICING PROBLEMS WHEN USING THE 'TESTGEAR' SCOPE**  
3in. D.C. OSCILLOSCOPE

Engineered to precision standards, this high-grade instrument is made available at the lowest possible price, incorporating the essential features usually associated with luxury instruments.

This "SCOPE" will appeal particularly to Service Engineers and Amateurs. A high gain, extremely stable, differential Y-amplifier (30 mV/C.M.). Provides ample sensitivity with A.C. or D.C. inputs. Especially suitable for measurement of transistor operating conditions where maintenance of D.C. levels is of paramount importance. Push-pull X amplifier; Fly-back suppression; Internal Time-base Scan Waveform available for external use; pulse output available for checking P.V. and CRT. Provision for external N.I.P. and CRT. Brightness Modulation. Size 10in. high, 6in. wide, 9in. deep. Wgt. 1 1/2 lbs. £15.15.0. plus P. & P. 7/6, or 30/- deposit, plus P. & P. 7/6 and 12 monthly payments of 9/6.

**FULL 12 MONTHS' GUARANTEE INCLUDING VALVES AND TUBE.**



### 8-WATT PUSH-PULL AMPLIFIER

**COMPLETE WITH CRYSTAL MIKE AND 8in. LOUDSPEAKER**

A.C. mains 200-250 v. Size 10 1/2 in. x 6 1/2 in. x 2 1/2 in. Incorporating 6 valves, H.F. pent., 2 triodes, 2 output pens and rectifier. For use with all makes and type of pick-up and mike. Negative feed back. Two inputs, mike and gram, and controls for same. Separate controls for Bass and Treble lift. Response flat from 40 cycles to 15 Kcs..

± 2 dB : 4 db down to 20 Kcs. Output 8 watts at 5% total distortion. Noise level 40 db down all hum. Output transformer tapped for 3 and 15 ohm speech coils. For use with Std. or L.P. records, musical instruments such as **£4.19.6** Plus P. & P. 7/6. Guitars, etc. Or 20/- deposit Plus P. & P. 7/6, and 4 monthly payments of 23/-.

### 6-WATT PUSH-PULL AMPLIFIER

A.C. Mains 200/250 v., incorporating 4 valves and metal rectifier. 2 inputs, high and low, and controls for same. Separate controls for Bass and Treble lift. Size of chassis 11in. x 4 1/2 in. x 2 1/2 in.

**59/6** Plus P. & P. 5/-.

### 2-TRANSISTOR POCKET RADIO

Plus Germanium diode, fully tuneable over medium and long waves. Size 3 1/2 in. x 4 1/2 in. x 1 in. Complete set of components including case and 2 transistors, earpiece and wiring diagram (less batteries).


**19/6** Plus P. & P. 1/6.

### PUSH-PULL OUTPUT STAGE

Inclusive of transistors with input and output transformers to match 3 ohm speech coil, suitable for use with the above kit. Complete kit of parts including transistors and wiring diagram.

**19/6** Plus P. & P. 1/6.

### AC/DC POCKET MULTI-METER KIT

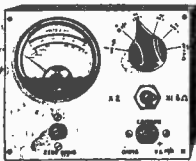


Comprising 2in. moving coil meter, scale calibrated in AC/DC volts, ohms and millamps. Voltage range AC/DC 0-50, 0-100, 0-250, 0-500. Milliamps 0-10, 0-100. Ohms range 0-10,000. Front panel, range switch, wire-wound pot (for ohms zero setting), toggle switch, resistor and rectifier. In grey hammer finish case.

**19/6** Plus P. & P. 1/6 Built and tested 7/6 extra.

Point to point wiring diagram 1/-, free with kit.

## SIGNAL GENERATORS

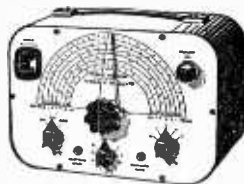


Cash **£6.10.6** or 25/- deposit and 6 monthly payments of 21/6. Post and Packing 5/- extra.

Coverage 100 Kc/s-100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Metal case 10in. x 6 1/2 in. x 5 1/2 in., grey hammer finish. Incorporating three miniature valves and Metal Rectifier. A.C. Mains 200/250 v. Internal Modulation of 400 c.p.s. to a depth of 30%; Modulated or C.W. and mod. switch, variable A.F. output. Incorporating magic eye as output indicator. Accuracy plus or minus 2%.

Cash **£4.19.6** or 25/- deposit and 4 monthly payments of 21/6. Plus Postage and Packing, 5/-.

Coverage 100 Kc/s-84 Mc/s. Metal case 10in. x 6 1/2 in. x 4 1/2 in. Size of scale, 6 1/2 in. x 3 1/2 in. 2 valves and rectifier. A.C. mains 200-250 v. Internal modulation of 400 c.p.s. to a depth of 30%, modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch variable A.D. output and moving coil output meter. Grey hammer finished case and white panel. Accuracy plus or minus 2%.

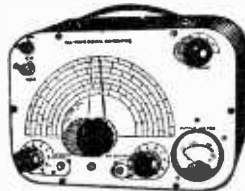

### B.S.R. MONARCH UA8 WITH STEREO HEAD



4-speed plays 10 records 12in., 10in or 7in. at 33, 45 or 78 r.p.m. Inter-mixes 7in., 10in. and 12in. records of the same speed. Has manual play position; colour brown. Dimensions: 12 1/2 in. x 10 1/2 in. Space required above baseboard 4 1/2 in. below baseboard 2 1/2 in. Fitted with Full-Fi turnover crystal head.

**£7.19.6** Plus 5/- Postage & Packing.

### PLAYER CABINET

Finished in 2-tone leatherette, will take B.S.R. UA8, with room for amplifier and 7in. x 4in. speaker. Overall size, 15 1/2 in. x 13 1/2 in. x 9 1/2 in.

**39/6** Plus 5/- P. & P.

Similar to the above in **POLISHED WALNUT** will take Collaro **39/6** Plus 5/- P. & P.

### MAINS TRANSFORMERS

All with tapped primaries. 200-250 volts. 0-160, 180, 200 v., 60 ma., 6.3 v. 2 amps. 10/6. 320-0-320 v. 75 ma., 6.3 v., 2.5 amp., 5 v., 2 amp., 10/6. 280-0-280, 80 ma., 6.3 v. 2 amp., 6.3 v. 1 amp., 10/6. Postage and packing on the above 3/-.

### F.M. TUNER UNIT

Permeability tuned, by famous German Manufacturer. Coverage 88-100 Mc/s. Complete with ECC85. Size 4in. x 2in. x 2in.

**25/-** Plus P. & P. 3/6.

Circuit diagram 1/-, free with unit.

### I3 CHANNEL TUNER

34 to 38 Mc/s. Complete with PCF90 and FCC94. These have been removed from chassis.



**23/-** Complete with knobs. P. & P. 3/6 extra.

as above, 16-19 Mc/s. complete with knobs less valves, 13/- Plus P. & P. 2/6.

### IMITATION LOG FIRE EFFECT

Size 14 inches x 11 inches **19/6** Plus P. & P. 2/6.

## RADIO & T.V. COMPONENTS (Acton) LTD.

23 HIGH STREET, ACTON, LONDON, W.3.

All enquiries S.A.E.

Goods not dispatched outside U.K.



Whether you're building your own amplifier or servicing a complete installation—for fault finding on anything from pre-amplifier to speaker—you'll find the MULTIMINOR to be "just right." You'll enjoy using this neat pocket instrument giving readings over nineteen ranges on a clear open scale. A.C. and D.C. voltage, D.C. and Resistance measurements are made by means of only two sockets. The robust, easy-to-read range selector has a smooth, clean, positive action.

"Can you afford it?" Let's say rather—"Can you really afford to be without it?"

Designed and Manufactured by

**AVO LTD** AVOCET HOUSE • 92-96 VAUXHALL BRIDGE RD. • LONDON • S.W.1

MM.10

## A television course for you to study at home

Entirely new! Practical!  
Bang up to date!

### THE FAMOUS BENNETT COLLEGE OFFERS YOU THIS

An entirely new course of study based upon up-to-date techniques has now been prepared by The Bennett College.

The course is non-mathematical, and contains clear diagrams, starting from the very beginning (even including the basic principles of sound radio receivers, if desired) and covering all that you need to know!

This is what you've been looking for! A home-study course includes: production

of the signal, scanning and reproduction of picture from signal. Aerials, types and purpose. The cathode-ray tube. Time-base oscillators, and output circuits. Synchronisation. Video frequency amplifiers. The TV tuner, turret, incremental, etc. Television test gear. Television faults.

For more details, fill in the coupon below. Your studies cost little, the book you need is included in the cost.

To THE BENNETT COLLEGE (Dept. M 104 TV Sheffield)

Please send me details of the new  
TELEVISION SERVICING COURSE

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

AGE \_\_\_\_\_

# Indispensable

THE

# MULTIMINOR

## 19 Ranges

D.C. Voltage : 0-1,000V in 7 ranges

A.C. Voltage : 0-1,000V in 5 ranges

D.C. Current : 0-1A in 5 ranges

Resistance : 0-20,000  $\Omega$ , 0-2M  $\Omega$ .

Pocket Size : 5½ x 3½ x 1½ inches.

Weight : 1 lb. approx.

List Price **£9 : 10s.**

Complete with Test Leads and Clips.

Leather Case if required 32/6.

Sensitivity :

10,000 ohms per volt on D.C. voltage ranges.

1,000 ohms per volt on A.C. voltage ranges

Accuracy :

On D.C. 3% of full scale value.

On A.C. 4% of full scale value.

To meet special requirements, instruments can be supplied to a higher degree of accuracy for a small additional charge.

Telephone : VICTORIA 3404 (12 lines)

### GENUINE GUARANTEED BRITISH TRANSISTORS RED SPOT 5/- WHITE SPOT 6/3

COMPLETE WITH ONE, TWO AND THREE TRANSISTOR CIRCUITS. DON'T DELAY—THESE PRICES CAN'T LAST.

GREEN/YELLOW, 7/6 RED/YELLOW, 15/-  
EDISWAN.—Set of 7 Transistors, one XA102, two XA101, one XB102, one XB103, two XC101. Limited quantity.  
3/- SET, XB104, 10/-; XA104, 18/-; XA103, 15/-  
MULLARD.—All at the NEW PRICES. OC18, 54/-; OC44, 28/-; OC45, 23/-; OC79, 14/-; OC71, 14/-; OC72, 17/- etc., also BRIMAR Transistors.  
Transistor Holders, 1/3. ARDENTE sub-miniature, 1/9.

CRYSTAL DIODES STILL ONLY 1/- EACH.

FERRITE ROD.—1in. diam. 6in. long. 2/9; 5in. long. 2/6.

COILS.—Repanco DRR/2, 4/-; DRX/1, 2/6; Teletron HAX. 3/-.

All complete with circuits.

TUNING CONDENSERS.—500 pf. (0005 mfd.). Variable, solid dielectric, 4/- each; 300 pf. (0003 mfd.), 3/9 each. .0001 mfd. 3/-.

TRANSISTOR CIRCUITS.—THE NEW MINI THREE three-transistor set. Will fit in your pocket, no aerial needed, 1/3.

Mini —7 Mark II, 1/6; Major —7 (7in. x 4in. speaker), 1/6;

Three Dec (three transistor), 11d.; REP car radio, 2 watt output, 2/-.

MAXI "0" (6 transistor), 8d. Teletron Transidyne 11d.

BEGINNER'S 1-VALVE BATTERY SET, 11d. Circuit & Plans.

RESISTORS.—All values, 10%  $\pm$  watt, each 6d. 1 watt 8d. each.

CONDENSERS.—Miniature. .001 mfd., .002 mfd./100 v., 8d.; .01/100 v., 10d.; 1 mfd./100 v., 1/2; .035 mfd./350 v., 11d.; Ceramic disc, 1,000 pf., 3,000 pf., 10 k (0.1), 9d. Standard size: .01/1,000 v., 8d.; .1/350 v., 9d.; 1/500 v., 10d.; 5/350 v., 1/11.

ELECTROLYTIC (Can Type).—32-32/450 v. 8/6; 50-50/400 v., 7/-; 100-200/275 v., 8/9; 60-250/275 v., 8/9; 64-120/350 v., 9/8; 60-100/275 v., 7/-; 24-24/350 v., 4/6. Triple section: 100-100-200/275 v., 13/-; 60-50-50/350 v., 9/10. Wire ended: 16 mfd./450 v., 2/4; 16-16/450 v., 4/-; 8-8/450 v., 2/9; 8-16/450 v., 2/9; 50 mfd./50 v., 1/6; 25 mfd. 25 v., 1/9. 100 mfd. 6v. 2/3.

Miniature: 25 mfd. 25 v., 2/6; 50 mfd. 12 v., 2/3. 8 mfd 2/9.

Sub-miniature: 25 mfd., 8 mfd., 16 mfd., 5 mfd., 4 mfd., 2 mfd., 3/8; 100 mfd., 2/9; 1 mfd. T.C.C., Type CE88D 4/-.

TERMS : Cash with Order (or C.O.D. on orders over £2).

ALL OUR PRICES ARE

POST PAID.

**OAKFIELD RADIO**

THE TRANSISTOR PEOPLE

Mail Order Only

44 Oakfield Road,

Stockport, Cheshire.

YOU CAN SAVE 1/- in every £1. Send 1/6 for our 56-page Catalogue and receive your order number for the Amazing Credit Coupon Schemé. Free Lists, Bargain Offers, Latest News, etc., etc. ORDER NOW. Don't Delay.

# A Transistorised "N" Circuit

A NEW APPLICATION OF AN OLD CIRCUIT

By J. Saunders

SOME years ago, PRACTICAL WIRELESS published a very interesting series of articles by W. Nimmons entitled "Old Circuits Reviewed." Amongst the circuits dealt with was the Lodge "N." I have constructed all the circuits mentioned and found the Lodge "N" could be adapted for use with transistors.

place when the "N" resonator is tuned to a frequency different from that of the incoming signals. If the difference is very slight the incoming signals will build up to an amount in accordance with the energy curve of a tuned circuit and heterodyning will take place in the circuit. The aerial, being a collector only, and out of tune with the incoming signals, cannot respond, and therefore cannot radiate. This is why the "N" circuit is non-radiating. In any case, the amplitude factor is so low when using transistors that the problem is not serious.

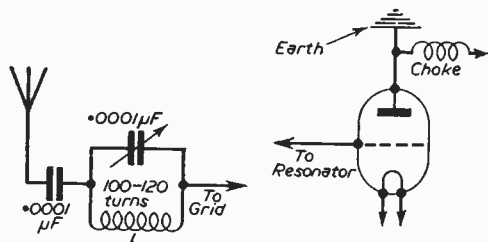


Fig. 1.—(Left) The "N" resonator.  
Fig. 2.—(Right) Valve circuit.

Mr. Nimmons wrote, "In the 'N' circuit we have a closed resonator consisting of a relatively large inductance coil and a relatively small capacity. This is stimulated by impulses conveyed to it by a single wire and builds up only those oscillations to which it is itself in tune.

Referring to the circuit in Fig. 1, the inductance is about 100/120 turns, and the capacity  $0.0001 \mu F$ . The condenser in the aerial lead is a fixed one of  $0.0001 \mu F$ .

"The frequency at which the resonator is tuned is called the 'N' frequency.

"Now, if a suitable choke is placed in the anode circuit of the valve (Fig. 2), and if the grid has alternating potentials of a frequency

Unfortunately, the circuit as shown in Fig. 3 allows strong signals to force their way through to the grid. To remedy this, Lodge inserted a choke coil between aerial and earth. The purpose of this coil is to shunt unwanted signals to earth

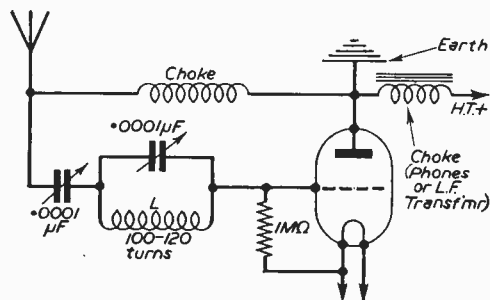


Fig. 4.—Wiring a choke between aerial and earth.

and it should have about 40 fewer turns than the "N" coil (Fig. 4).

Transistors will not oscillate and detect well at the same time, but this was easily overcome by placing a crystal diode between the "N" resonator and the emitter (Fig. 5).

## Results

The set gives excellent results like this but strong signals persist in breaking through to the base, making the reception of distant stations difficult. A wave-trap would cure this fault, although it was found that a tuned circuit could be placed between the aerial and earth (Fig. 7) without interfering with the operation of the "choke" or the "N" resonator. This improves the tuning, making for greater selectivity.

The coils are, as Mr. Nimmons recommended, on  $2\frac{1}{2}$  in. formers. The "choke" and tuning coil are wound with 60 turns of 26 s.w.g. enamelled copper wire, while the "N" coil is wound with 100/120 turns (I used 100 turns). These coils should be arranged at right angles to each other as shown in Fig. 6. The construction of the coils is not critical; no tappings are necessary which

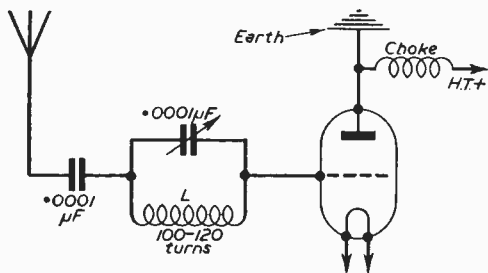


Fig. 3.—Combination of the circuits of Figs. 1 and 2.

'N' applied to it, and if the plate is earthed, then the earthed plate will pulse gently at that frequency."

## Regeneration

When these two circuits are combined (Fig. 3) the "N" circuit builds up energy both from the aerial by collection and from the capacity effect between aerial and earth. Regeneration takes

simplifies winding. The coils could be wound on smaller formers, but since most transistor sets

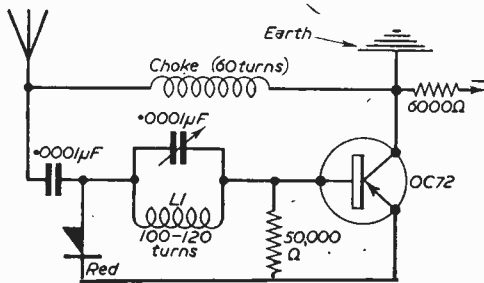


Fig. 5.—The use of a crystal diode between the "N" resonator and the emitter.

work best with a large loudspeaker, there is really no less room inside a cabinet with large coils than with small coils. Also, large coils are more efficient.


**Transformer Coupling**

In the amplifier I used resistance-capacity coupling, but transformers could be used here if preferred. Originally, a 0.0005µF condenser was included in the aerial lead in order to prevent the possibility of the signal overloading the transistors. Although in practice it was found not to be necessary even though I am within a mile of the BBC Welsh transmitter. The 0.0001µF condenser in series with the aerial and the "N" resonator controls the regeneration.

Oscillation of the set is quite stable—in fact, stations come through at full volume with the reaction condenser set at a low value—so that local stations can be tuned in without the necessity of producing howls from the receiver.

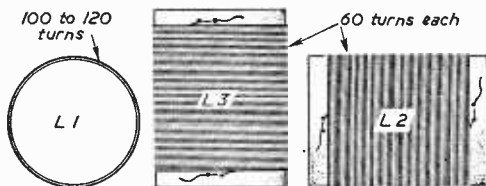**Battery**

In the circuit diagram (Fig. 7) the battery is a 9V type, although other voltages can be used. However it may be found that too high a voltage will make the



Coils wound on 2 1/2" diameter formers

Fig. 6.—Details of the coils.

circuit unstable, so I suggest that a battery of between 9 and 18 volts be used. The H.F. choke in the collector lead of the first transistor is important because Sir Oliver Lodge stressed the desirability of a load in the circuit at this point.

Tuning is mostly achieved through C3, the 0.0001µF condenser (C1) brings the signal up to strength. Reaction is controlled in the usual way, that is, the knob is tuned until oscillation begins, and then tuned so that the set is just on the threshold of oscillation, when the signal should be heard clear of interference.

**Quality**

One thing that is very noticeable about most regenerative receivers, and the Lodge "N" circuit is no exception, is that there is a marked difference in the quality of the sound produced when compared with other sets. There is less background noise and music is reproduced with a good resemblance to the original at the broadcasting station.

The set is very easy to construct, being quite a simple affair to put together. I have given no details of the size of cabinet used because this will depend on the components to hand and on

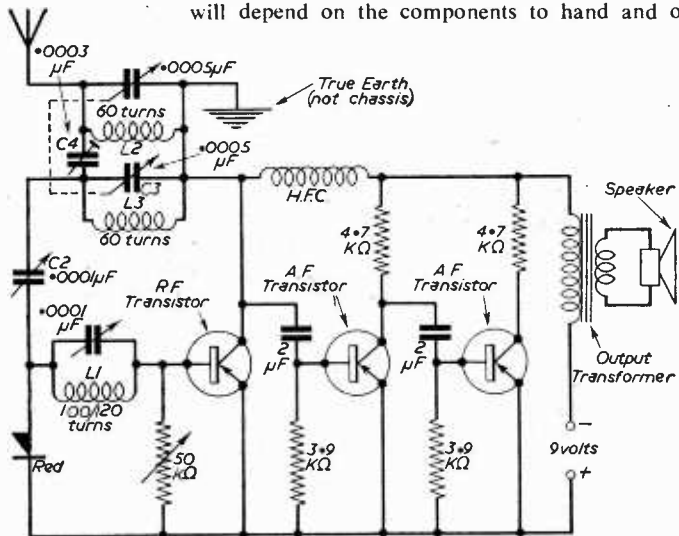


Fig. 7.—The final circuit diagram.

the type of amplifier used, although the set does give quiet volume with one transistor and a 6in. speaker, provided a good aerial and earth are used. Selectivity is much the same as a "straight" set using two or three tuned circuits, but there is more volume.

**PRACTICAL WIRELESS CIRCUITS**  
17th Edition

By F. J. CANN 17/6, by post 18/7


from  
**GEORGE NEWNES, LTD.,**  
Tower House, Southampton Street, Strand, W.C.2.



**TRS**

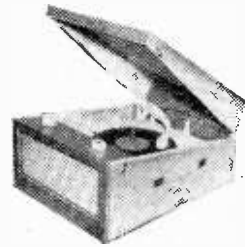**RECORD PLAYER BARGAIN OFFER**

A self-contained portable unit comprising the latest Collaro 4-speed Auto Changer Record Player, incorporating the famous High Fidelity Studio "O" Xtal Pick-up with Turnover Cartridge, and fitted with L.P. and 78 Sapphire styli. An internal 2 valve amplifier of modern design with variable tone and volume controls is fitted. This, together with a quality 6in. P.M. speaker, ensures a high standard of reproduction. The whole is housed in a robust wooden cabinet attractively styled in a maroon contemporary leather cloth with contrasting polka dot relief. A fortunate bulk purchase enables us to offer this commercially styled Player at the following attractive breakdown Unit prices :



- Collaro 4-speed autochanger, £6.19.6 + 4/6 carr.
- 2-valve, 2-stage amplifier, ready wired, complete with speaker, etc., £3. 7.6 + 2/6 carr.
- Cabinet with mounting board, etc. Size 18 1/2 in. x 13 3/4 in. x Ht. 8 1/2 in. £2.12.6 + 3/6 carr.

This 'complete 3 unit "Do-it-yourself" Record Player Kit offered at amazing bargain price of

**£12. 19. 6**  
carriage free.

This is a recommended bargain buy and when present stock is exhausted cannot be repeated. Originally built to be sold at 17 gns.

**2 Waveband Car Radio Kit**

12 v. operation Med. & Long Waves Development of the famous Trinar Hybrid vibratorless Car Radio Circuit. 5 latest type low voltage valves and Power Transistor. R.F. stage and permeability pre-aligned Cydon Tuner Unit provide extremely good sensitivity and Signal/Noise ratio. Printed circuit and 7in. x 4in. Speaker. Self-contained in neat Metal Cabinet Bin. x 7in. x 2 1/2 in. with attractive dial. Speaker and Power Transistor stage mounted separately, approx. 8in. x 5in. x 3in.

**RECOMMENDED BUY**  
Complete Kit **£12. 19. 6**

B. & P. 3/6.  
Instruction Booklet and Parts List available shortly 2/3 post free.


**RE-GUNNED TV TUBES**

New Reduced Budget Prices New Heater, Cathode and Gun Assembly fitted to all tubes. Reconditioned virtually as new. Now 12 months' guarantee to highest standards—as used by our own Service Dept.

12in. £6. 14in. £7. 17in. £8.10.0.  
Most Mullard & Mazda types ex-stock Carr. & ins. 10/-

10/- Part Exchange allowance on your old tube.

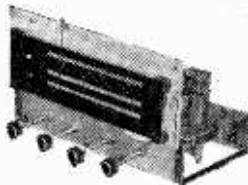**7-VALVE AM/FM RADIOGRAM CHASSIS**  
Surplus Bargain Offer



Valve Line up: ECC85, ECH81, EF89, EABC80, EL84, EM81, E280.  
3 waveband and switched gram positions. Med. 300 m.-500 m., Long 1,000-2,000 m., VHF/PM 88-95 Mc/s.

4 Controls. Vol., On-off, Tone, Tuning, Wavechange. P.U., Ae. and E., and speaker sockets. Magic eye tuning, Philips continental (tuning insert with permeability tuning on FM, and combined AM/FM IF transformers, 460 Kc/s and 10.7 Mc/s. Dust core tuning all coils. Latest circuitry, including AVC and Neg. Feedback. 3 watt output. Sensitivity and reproduction of a very high standard. Chassis size 13 1/2 in. x 8 1/2 in. Height 7 1/2 in. Edge illuminated glass dial 1 1/2 in. x 3 1/2 in. Vertical pointer. Horizontal station names, gold on brown background. A.C. 200/250 v. operation.

**£13. 10. 0**

Carr. and ins. 5/-  
Complete with 4 knobs—walnut or ivory to choice.

**PERDIO POCKET TRANSISTOR "6"**

(as extensively advertised)  
Med. & L.W. TRANSISTOR PORTABLE. Modern sensitive superhet circuit—6 Transistors and 1 Xtal Diode. Lightweight and compact, only 5 1/2 in. x 3 1/2 in. x 1 1/2 in. Weighs 14 ozs. Complete kit incl. cabinet and 2 1/2 in. speaker, £9.18.6. P. & P. 2/6.

**RECORD PLAYER BARGAINS**

NEW RELEASE by E.M.I.—4-speed Single Player Unit fitted with latest stereo and monaural Xtal cartridge and dual sapphire styli. Auto stop and start. A fidelity unit and bargain buy at only £8.10.0.

BSE—De luxe UA12 Model.—1-speed autochanger with stereo/monaural turnover cartridge, etc. Bargain £8.19.6.

Garrard—Latest RG121/D/MK 2—fitted with GC8 Xtal cartridge, plug-in monaural head. Auto/manual selector, etc. The connoisseur's choice for audio perfection.

Limited bargain offer only 9! gas. Plug-in stereo head GC8/10 £2 extra.

All above are brand new, fully guaranteed models. Carr. and ins. 4/6.  
Comprehensive bargain range of Collaro, BSR and Garrard Units in stock. Send for comprehensive bargain lists.

**COAX 80 OHM CABLE**

Stand 1/2 in. diam.

Low Loss Semi-air Spaced AERAXIAL polythene ins. SPECIAL REDUCED PRICES. 20 yds., 12/6. 40 yds., 22/6. 60 yds., 32/6. P. & P. 1/6. P. & P. 2/- P. & P. 3/-  
All other lengths 8d. per yd.  
Coax Plugs, 1/-. Sockets, 1/-. Couplers, 1/6. Cable End Sockets, 1/6. Outlet Boxes, 4/6.

**JASON FM TUNER UNITS**

(87-105 Mc/s)

Designer-approved kits of parts for these quality and highly popular tuners available as follows. STANDARD MODEL (FMT)—as previously extensively advertised.

COMPLETE KIT, 5 gns., post free.

Set of 4 spec. valves, 30/-, post free.

LATEST MODEL (FMT2)—attractively presented self mounting unit in enclosed Metal Cabinet with Built-in Power Supply.

COMPLETE KIT, £7. p. & p. 3/6.

Set of 5 spec. valves, 36/6.

NEW JASON COMPREHENSIVE F.M. HANDBOOK

2/6 post free.

48 hr. Alignment Service, 7/6, p. & p. 2/6.

**MULLARD "3-3" AMPLIFIER**

Quality built to Mullard's specification, with special sectionalised O/P Trans. Complete kit with front panel only £8.19.6, p. & p. 3/6.

| NEW BOXED    | VALUES     | NEW REDUCED PRICES |
|--------------|------------|--------------------|
| 1B5, 174 7/8 | DF96       | 9/- EF89           |
| 1B5          | 7/8 DK96   | 9/- EF86           |
| 3A4, 3V4 8/8 | DL86       | 9/- EF91           |
| 6Z4          | 9/8 35L6   | 9/8 EL41           |
| 6K7          | 5/8 EABC80 | 9/8 EL34           |
| 6K8          | 8/8 EBC41  | 9/8 EM85           |
| 6Q7          | 8/8 ECC83  | 9/8 EY51           |
| 6SN7         | 8/8 ECC84  | 10/8 EY86          |
| 6V6          | 7/8 ECF80  | 11/8 EZ80          |
| 6X4          | 7/8 ECF82  | 11/8 EZ81          |
| 7C5          | 8/8 ECH81  | 10/8 MU14          |
| 7Y4          | 8/8 ECL80  | 10/8 PCC84         |
| DAF96        | 9/- ECL82  | 11/8 PCC80         |
|              |            | 10/8 UF11          |

Send for List.

**SPECIAL PRICE PER SET**  
1B5, 174, 1B5, 3B4 or 3V4 ... .. 27/6  
DK96, DF96, DAF96, DL96 ... .. 35/-  
6K3, 6K7, 6Q7, 6V6, 5Z4 or 6X3 ... .. 35/-

**NOW! The TOURIST Portable**

4 valve, Med. & L.W. 1/2 weight battery Radio. Size only 8in. x 5 1/2 in. x 4in. Weight 3 1/2 lb. with battery. Complete receiver component kit £7/6, p. & p. 1/6. Set 4 miniature valves (96 series) 35/-, p. & p. 9/4. 8in. Speaker & O/p Trans. ... 21/-, p. & p. 1/6. Cabinet, Dial and Knobs, etc. ... 22/6, p. & p. 2/-  
Complete kit—BARGAIN—only £6.10.0, post free.  
Latest superhet circuitry, delayed AVC and A.F. Neg. feedback.

Terrific performance—  
Remarkable size—  
Staggering value  
Send for Booklet NOW! 1/6 post free.

Listed above are only a few items from our very large stock. Send 3d. stamp today for Complete Bargain List.

Terms: C.W.O. or C.O.D. Kindly make cheques, P.O.s, etc., payable to T.R.S. Post/Packing up to 1/6 7d., 1lb. 1/1, 3lb. 1/6, 5lb. 2/-, 10lb. 2/6. Hours: 9 a.m.-6 p.m. 1 p.m. Wed. Open all day Saturday.

**TRS**

**RADIO COMPONENT SPECIALISTS (Est. 1946)**

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY (THO 2188)

50 yards Thornton Heath Station.

Buses: 130A, 133, 159, 166 and 190

Visit the City's popular acoustically designed

# HI-FI Centre

COME AND HEAR THE LEADING MAKES IN AMPLIFIERS AND TUNERS

**AMPLIFIERS BY**  
VERDIK  
ARMSTRONG  
ROGERS  
DULCI

GOODSELL  
QUAD  
LEAK  
W.B., etc.

**V.H.F. TUNERS BY**  
ARMSTRONG  
LEAK  
QUAD

T.S.L.  
DULCI  
GOODSELL  
ROGERS, etc.

**HI-FI SPEAKERS BY**  
GOODMAN  
PLESSEY  
WHARFEDALE  
LORENZ, etc.

W.B.  
T.S.L.  
G.E.C.

**ANOTHER SNIP OFFER  
AT THE  
LOW  
PRICE  
29/6**



and 4/-  
post and  
packing.  
Surplus to  
manufacturers  
requirements, well  
made 2-tone

colour portable player cabinets,  
will take non-auto player. Amplifier  
and 4in. or 5in. speaker.

The above portable cabinet, Colloar  
4-speed player & pup, 2 watt amplifier,  
and 6 x 4 elliptical speaker,  
making an ideal portable player at  
special price of £8.5.0, plus 7/6 post  
& pkg.

### GARRARD RC121 Mk. 2

Autochanger wired for stereo with new  
plug-in head using the popular GC8  
turnover cartridge for L.P. and 78in.  
records. Our price, £9.19.6. P. & P. 5/-.

### SPECIAL OFFER IN TRANSISTORS

Audio PNP transistors type, 5/- each.  
Sensitive diodes type GD3, 2/6 each.  
Ediswan x B104, 9/6.  
" " x B103, 12/6.  
" " x A104, 17/6.  
General-purpose diodes 10d, each.  
Single earphones, 4/6 each. 1/- P. & P.  
Crystal earpieces with lead and ear plugs.  
Our price, 12/6. 1/- P. & P.

### BUILD THIS YOURSELF

The Transette Medium Wave, 2 transistor,  
pocket portable. Neatly designed, using 2  
transistors and diode. Simple to assemble.  
Enlarged working diagram. All components  
colour coded. Ferrite wound aerial. Will  
play indoors and outside with self-contained  
aerial. All components and diagram,  
complete, 62/6. Post & Pkg. 1/6.  
Plug-in ear piece, 13/6.  
Single phone, 5/6.  
Battery, 2/-.

All components available separately.  
Stamped, addressed envelope for details.

## Electronics (FLEET ST.) Ltd

Dept. E, 152/3, FLEET STREET, LONDON, E.C.4.

Business Hours: Weekdays 9-6. Saturdays 9-1. Tel.: FLEET 2833

The COMPLETE introduction to the  
theory and applications of F.M.

## PRINCIPLES OF FREQUENCY MODULATION

by B. S. Camies

This new book gives in concise form and  
logical sequence a comprehensive account of  
the fundamentals of frequency modulation and  
its applications. It covers f.m. receivers, f.m.  
in transmitters, and the use of f.m. in micro-  
wave links, in radar, in telegraphy and in  
facsimile transmission. Many numerical ex-  
amples show how simple design calculations  
may be performed.

21s net by post 21s 10d

from leading booksellers

Published for "Wireless World"  
by Iliffe & Sons Ltd.,

Dorset House, Stamford Street, London, S.E.1.

## Special Bargain Offers

**MULTI-RANGE TESTMETERS.** R.C.P. U.S.A. 1,000  $\Omega$ /volts,  
20 ranges, 0-5,000 v. A.C. and D.C., D.C. m/A and amps.  $\Omega$  and dB.  
In light oak polished wooden case, 6 1/2 x 6 1/2 x 4 1/2 in. Complete with  
leads and instructions. BRAND NEW. £23.19.6. Post 3/-.  
**WESTON F772 ANALYSERS.**—Multimeter. Current,  
0 to 100 microamps 1, 10, 50, 100, 500 m/A., D.C. 0 to 1/2, 1, 5  
Amps. A.C. volts, 0 to 2.5, 10, 50, 250, 1,000 D.C. and A.C. Resist-  
ance 0 to 100, 1,000, 100 K., 10 M  $\Omega$ . In "Rexine" covered  
case, with leads and battery. \*Guaranteed. £7.19.6, carr. 4/6.

**GRAMOPHONE MOTORS.** A.C. mains. Garrard AC-6, 78 r.p.m.  
For replacements. BRAND NEW. Boxed, 35/-. Post 2/6.  
**VITAVOX PRESSURE UNITS.** TYPE N. 20 watts. P.M. Heavy  
duty. BRAND NEW. Boxed, 89/6, carr. 5/6.  
45" r.r. (EC-433 Command Receiver). Covers 190-550 Kc/s (IF 85 Kc/s).  
Ideal for double superhet conversion, etc. Supplied BRAND NEW  
in original cartons, with all 6 valves and CIRCUIT. 89/6. Post 3/6.  
**R-109 RECEIVERS.** 8 valve superhet using 5 ARP12s and 3  
AR6's. 1.8-8.5 Mc/s (34-168 m.). Internal 3in. speaker and 6 v.  
vibrator pack (takes 14 amps). In metal case 13 x 12 x 1 1/2 in. Aerial  
tested. Good condition. Circuit supplied. 79/6, carr. 7/6.  
**R-1155-B.** with latest drive, first-class condition. £7.19.6.  
**R-1155-L.** £12.19.6. Power Packs, £6.10.0. S.A.E. details.  
**CR100 COMMUNICATION RECEIVERS.** Covers 60 kc/s—  
30 Mc/s in 6 bands. 11 valves, 2 R.F. and 3 I.F. stages. Crystal gate,  
B.F.O., etc. Ready for 200-250 v. A.C. mains 21 watts output for  
3 ohm speaker. **SUPERB CONDITION AND OUTSTANDING**  
**PERFORMANCE FOR ONLY £21.** S.A.E. for illustrated details.  
**HRO COMMUNICATION RECEIVERS,** complete with 9 coils.  
From 18 gns. S.A.E. for full particulars.

**RCA AR-89 SPEAKERS.** 30 8in. P.M. speaker in heavy gauge  
black cracked steel cabinet 11 x 10 x 6in., with rubber feet. A  
**SUPER QUALITY** unit. BRAND NEW, for ONLY 45/-. Post 3/6.

**INVICTA LOUDSPEAKERS.**—Good quality 10in. unit (imped-  
ance 3 ohms) in wooden cabinet 17 x 17 x 6in. Complete with 50ft.  
lead and jack plug. BRAND NEW, 39/6, carr. 5/6.  
**MOVING COIL PHONES.**—Finest quality Canadian, with  
Chamois ear-muffs and leather-covered headband. With lead and  
jack plug. Noise excluding, supremely comfortable, 19/6, post 1/6.  
**R.F. UNITS.** R.F.24, 12/6; R.F.25, 17/6; R.F.27, 22/6. Good  
condition. Post each, 3/6.

PLEASE ADD POSTAGE OR CARRIAGE ON ALL ITEMS

**CHARLES BRITAIN (RADIO) LTD.**

11 Upper Saint Martin's Lane, London, W.C.2

TEMPle Bar 0545

Shop Hours 9-6 p.m. (9-1 p.m. Thursday). Open All Day Saturday.

# A Transistor Pre-amp


THIS UNIT WILL DRIVE THE DIRECT-COUPLED OUTPUT STAGE DESCRIBED LAST MONTH

By J. S. Kendall

**T**HIS pre-amplifier has an input impedance of some 5,000 ohms and an output impedance of under 2,000. The power gain of the unit is between 50 and 60dB. If it is used as a voltage amplifier a useful gain of some 500 times may be achieved. The noise level in the output is extremely low; an advantage over valve amplifiers for similar gain.

The unit may be used for driving the direct-coupled transistor amplifier stage described on page 569 of the November issue. This com-

pute the values of the decoupling condenser and resistor required. The cathode voltage of the valve should be measured and also the current taken by the transistor pre-amp, using a battery of 6V. Then suppose the cathode voltage of the output valve were 9V, then a voltage drop of three would be necessary so that if the current taken by the pre-amp, were 3mA then the unit could be decoupled from the valve by a 1,000 ohm, half watt resistor and, say, a 100 $\mu$ F capacitor. The working voltage of this capacitor need only be 6.

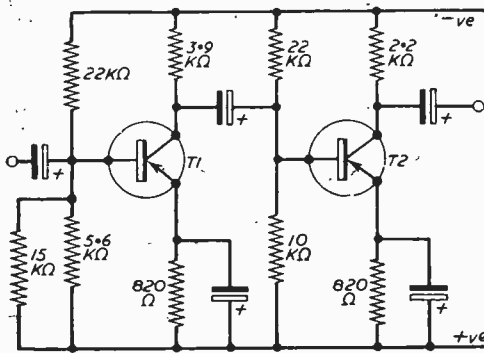

All capacitors 10 $\mu$ F Electrolytics 12V WKG.

Fig. 1.—The circuit diagram.

binated circuit will give the advantage of eliminating transformers between the pre-amp and the loudspeaker. Thus four transistors can be used to give about 1W output, all stages being resistance-capacity coupled.

## Circuit

The circuit diagram of the unit is shown in Fig. 1. The two transistors used are a V10/15A and a V10/30A. The voltage required to operate the unit is low: 3 to 6, depending on the output required. Batteries form an easy source of power for the unit but if required the supply can be taken from the cathode of an output valve if the pre-amp is to be used with a conventional valve amplifier. Here the negative of the supply will be connected to the chassis and the input to the pre-amplifier must be connected to the input capacitor and the chassis and the output taken from the output capacitor and chassis, no signal connections being made to the positive line.

It will be noted from the circuit diagram that the lower resistor for the base potential divider of T1 is made up of two resistors in parallel, viz. 15k and 5.6k as no preferred value is suitable.

## Power Supply

If the circuit is powered from a cathode circuit of an output valve, then it is necessary to

## Lower Voltages

However, suppose the cathode voltage were only 6 or less, as may be the case. Then, it will be necessary to use a lower voltage for the pre-amplifier and a resistor of 560 or 470 ohms could be used together with a 1000 $\mu$ F capacitor for decoupling. Although this will reduce the output, it should still be sufficient for most amplifiers.

If the unit is to be used for the direct-coupled output stage, then the same power supply can be used for both the output stage and the pre-amplifier. The supply for the pre-amplifier should be decoupled with a 220 ohm resistor and a large capacitor. For example, 1,000 $\mu$ F. If the decoupling is not adequate there will be a tendency to motorboating which may damage the transistors. The gain when the pre-amplifier is used with direct-coupled output stage is high enough for a crystal receiver with a good aerial and earth to load the amplifier.

## Lay-out

The circuit is simple and the layout of the components can to a large extent follow the layout of the circuit diagram. When soldering, a good hot soldering iron is essential and cored solder should be used. Bare wires can be covered with sleeving to avoid possible shorts. When soldering the transistors a heat shunt can be used or the author's method of using the fingers to hold the wire being soldered can be employed. This method ensures that the transistors are not damaged by the heat of the soldering. Base connections for the transistors are easy to remember; the three connections are in line, with the base connection in the middle. The emitter is the connection closer to the base and the remaining connection farther from the base is for the collector.

## PRACTICAL WIRELESS CIRCUITS

17th Edition

By F. J. CAMM

17/6, by post 18/7

from

GEORGE NEWNES, LTD.,  
Tower House, Southampton Street, Strand, W.C.2.



# HOME RADIO OF MITCHAM

(Dept. P), 187 LONDON ROAD, MITCHAM, SURREY. MIT 3282

Shop Hours: 9 a.m.—6.30 p.m. Wednesday 9 a.m.—1 p.m.


We are stockists for Eddystone Short Wave Receivers and Components, Denco and Teletron Coils, and all Jason Kits for Tuners, Amplifiers, and Test-gear.



### JASON FMT2 FM/VHF TUNER


Crystal clear Hi-Fi reception at all times. Modern slide rule scale, easy tuning, and neat case. Full constructional data and price list, 2/9, post paid. Complete kit with power unit, £9.8.0.

## COMPLETE "JUNIOR STEREO" HI-FI SYSTEM

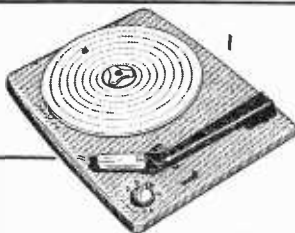
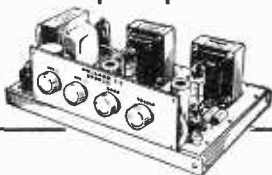
### PHILIPS AG2009

4-speed transcription player unit. Accurately machined turntable with variable speed control. Hi-Fi crystal pick-up for 78 and LP records. Leaflet on request. PRICE £10.10.0, carriage 2/-. Extra for Stereo plug-in head, £1.10.0.



### MULLARD "3-3" PRINTED CIRCUIT STEREO AMPLIFIER

Easy to build and perfect results every time. Full constructional drawings and price list, 1/9, post paid. Complete Kit £16.0.0. All parts sold separately.



Two WB STENTORIAN HIGH FIDELITY HF1012 10" SPEAKERS. Die cast chassis. Response 30 to 14,000 cycles. Universal speech coil. Price now Only £4.15.0 each, plus 2/- post. Leaflet on request.



### R.C.S. "PERSONAL TWO" PORTABLE



2-valve dry battery personal portable with rod aerial. Ideal for bedroom, etc. Smart metal case. Easy to build from data sheets. Price 2/- post paid. Parts for set cost 41/-. Also all parts in stock for SW1 short waver, 35/-. See October issue.



### "GLOBE-KING" SHORT WAVE RADIO KITS

Real long-distance radio at minimum cost. This is a scientifically designed equipment for the real short-wave enthusiast who desires the best results. Produced up to a standard—not down to a price. Every item brand new and best quality. As easy to build as a mecano model. Complete kit for 1 valve set with three coils covering 10 to 100 metres, 79/6. Travel the world from your own armchair. Send stamped, addressed envelope for full details today. "THE BEST WINTER HOBBY OF ALL."

### CABY SUPREME (Empire Made) MULTI-RANGE TEST METERS.

Supplied complete with test prods, instructions and batteries.



#### MODEL A.10

Sensitivity 2,000  $\Omega$ /volt 5 voltage ranges 10 to 1,000 volts A.C. and D.C. 3 D.C. ranges. .5 mA to 250 mA. 2 resistance ranges 10K and 1 meg. Accuracy 2% D.C. and 3% A.C.


PRICE £4.17.6. post 1/6.



#### MODEL B.20

Sensitivity 4,000  $\Omega$ /volt. 7 D.C. voltage ranges .5 v. to 1,000 v. 4 A.C. voltage ranges 10 v. to 1,000 v. 4 D.C. ranges .5 mA to 250 mA. 4 resistance ranges 2K, 200K, 2 meg., and 20 meg. Accuracy 2% D.C. and 3% A.C.

PRICE £6.10.0. post 1/6.

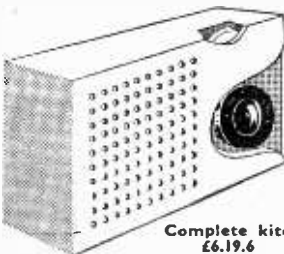

### MINI-3

An entirely new reflex circuit using only three transistors in a pocket portable with 2 1/2 in. loudspeaker. Simple to build and no alignment difficulties. Internal ferrite rod aerial for local station reception. Full constructional data and price list 1/6 post paid.

Complete kit £6.19.6

### SOLDERING IRONS



Brand new instrument soldering irons. Ideal for all radio work. 3/16th detachable bit. Neon indicator lamp in handle. 220 to 240 volts only. Limited quantity. PRICE 18/6, plus 9d. post.

### CONDENSERS



16 mfd. 350 v. tubular condensers. 1/- each or 6 for 5/- add 6d. post to order.

We are stockists for:—

EDDYSTONE COMPONENTS


JASON KITS

MULLARD DESIGN COMPONENTS

BRAND NEW RADIO COMPONENT CATALOGUE. Just out! 128 pages and hundreds of illustrations. Get yours today. PRICE 2/- plus 9d. post.

THE WORD **MAXI-Q** IS THE REGISTERED TRADE MARK  
 OF DENCO (CLACTON) LIMITED  
 IT IS ALSO A GUARANTEE OF  
 WORKMANSHIP & TECHNICAL PERFORMANCE

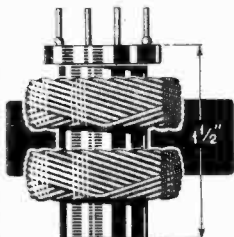OUR RANGE OF PRODUCTS IS SO GREAT THAT WE NOW HAVE TO REQUEST THE AMOUNT OF 1/4d FOR OUR GENERAL CATALOGUE AND, TO SAVE YOU POSTAL ORDER POUNDAGE CHARGE WE REQUEST (SEND 1/4d. IN STAMPS).




Two types are available :

LDN.1 for 3 ohm Speakers, Price 7/6 each.

LDN.2 for 15 ohm Speakers, Price 10/- each.

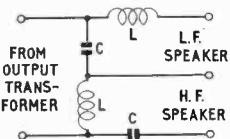In both cases the cross-over frequency is 2.5 kc/s and with the constant resistance circuit recommended, the attenuation beyond the cross-over frequency will be 12 dbs. per octave.



|                           |            |
|---------------------------|------------|
| FOR 3 OHM SPEAKERS LDN.1  |            |
| L = 0.135 mH.             | C = 30 μF. |
| FOR 15 OHM SPEAKERS LDN.2 |            |
| L = 0.675 mH.             | C = 6 μF.  |

### LOUDSPEAKER DIVIDER NETWORK COILS

Loudspeakers designed to reproduce the whole audio range are usually very expensive and results comparable with much more expensive units can be achieved by the use of two normal loudspeakers. One is used to reproduce the lower frequencies, the other caters for the higher frequencies where the response of the larger unit will have fallen off. It is clearly necessary to include a frequency dividing network between the speakers and output transformer in order to distribute the low and high frequencies to the appropriate speaker.

The frequency at which the cross-over takes place may lie between 800 c.p.s. and 5 kc/s depending upon the relative performance of the two loudspeakers used. A reasonable compromise which will suit most pairs consisting of an 8in. to 12in. unit and a 2½in. to 6in. unit, is 2.5 kc/s.

PLEASE SEND S.A.E. WITH ALL ENQUIRIES.

**DENCO (CLACTON) LTD. (DEPT. P.W.), 357/9, OLD ROAD, CLACTON-ON-SEA, ESSEX**


# Premier RADIO

23, TOTTENHAM COURT ROAD, LONDON, W.1.

TEL.: MUSEUM 3451/2

Visit our New Branch at: 309, EDGWARE ROAD, LONDON, W.2.

TEL.: PAD 6963

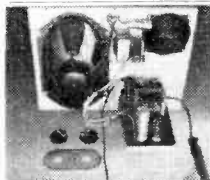

The Famous Cossor 3 watt  
**AUDIO AMPLIFIER KIT 562K**  
 Original Price £9.15.0.

OUR PRICE **£5.19.6** p. & p. 2/6.

This Kit assembled will provide a compact versatile Amplifier which incorporates the most up-to-date pre-assembled printed circuit and is suitable for operation from Radio, Microphone or Gramophone. The circuit design includes negative feedback, valve line-up 6V4, 6BQ5, EF86. Two Loudspeakers are used, i.e., 10in. x 6in. Elliptical and 4in. Treble, ensuring high quality output, suitable for use on 200/250 v. A.C. mains. All items are supplied, including Loudspeakers, Knobs and Escutcheon, with full assembly instructions and in makers' original cartons.

The Cossor Printed Circuit Model 701K VHF/FM Radio Receiver Kit

Original Price 15 gns.

OUR PRICE **£8.19.6**, p.p. 2/6

This Kit is easily assembled and will provide a complete Radio Receiver for reception of VHF/FM transmission. The Receiver utilises the latest type printed circuit, for use on A.C. or D.C. mains, incorporating UCC85, UF89, UF89, UABC80, UL84, UY85 Valves. All components are supplied including a Goodman's 10in. x 6in. Elliptical Speaker, full assembly instructions and presented in manufacturers' original cartons.



### THE BERIC

The 'Beric' Battery Receiver for only **£4.19.6**, plus 5/- p. & p., or **£1.0.0** deposit and 5 mthly pymts of 19/-. This receiver is ideally suitable for use in the home or where normal electricity supply is not available, remarkable reception on the med. and short wavebands, using the following latest type min. Battery Valves: DK92, DF92, DAF96, DL96 and operates on an external B.103 Battery or equiv. The receiver is housed in an attractive, two tone metal case. Size 11½ x 7½ x 5½in. BATTERY EXTRA 18/6.



### Quality at low cost!

A well designed Amplifier incorporating printed circuit of the latest type, using two ECL82, triode-pentode valves and Metal Rectifier, ganged volume and tone controls and separate balancing control, output 3 watts per channel and suitable for Speakers of 3 ohms impedance. The Amplifier is an attractive black metal Cabinet with Engraved Front Panel, overall dimensions 10½ x 7½ x 4½in. Price, **£8.19.6**, plus p. & p. 5/-.



### HI-FI SPEAKER

A 12in. Loudspeaker of high fidelity quality, made by a famous manufacturer, 3 ohms impedance, 15,000 lines, plus 2/6d. p. & p. with cloth suspended cone.



★ GENEROUS H.P. TERMS AVAILABLE ★

**Aerials**

The signal pick-up of most vehicle aerials is not very great, and this can give poor volume. A sensitive receiver helps to compensate for the poor signal, but with the simpler type of receiver the aerial may be very important indeed.

Signal strength is best when the aerial is as high as possible, reasonably long, and well clear of chassis, bodywork and other metal items. A vertical telescopic rod aerial is thus usually among the most satisfactory. The best fixing position depends on the vehicle, and it can be tried temporarily in various positions, before being permanently fixed, if necessary. The aerial and lead-in should be reasonably clear of vehicle wiring, and especially spark coil, distributor, and sparking plug leads. Suppressors will usually be needed, unless the radio is only to be used when the car or caravan is stationary.

With a receiver used for camping or in a parked caravan, a permanent aerial need not be fitted because a throw-out aerial, consisting of a few feet of insulated wire, can usually be hooked up. The height of this wire, and its proximity to metalwork, will greatly influence results. If one end can be kept a few feet high, signal pick-up will usually be sufficient.

**Earth**

With a camp or stationary caravan radio, an earth is often feasible. A metal spike or pointed rod, with a few feet of flexible wire ready attached, can be used for this. It is pushed into the ground, and will often give quite good volume when used as an aerial connection. Or, if an aerial is available, it can act as the normal earth, being taken to the receiver chassis. With sensitive receivers an earth is scarcely worth

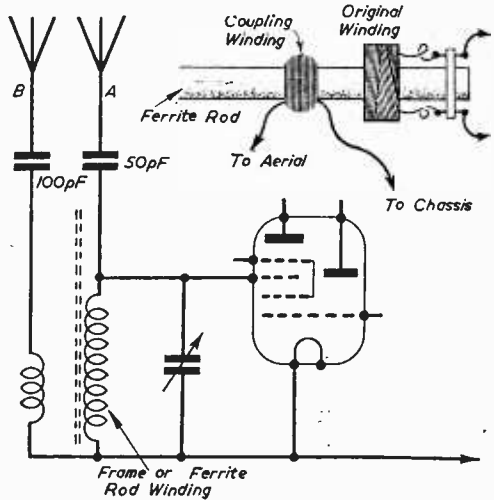


Fig. 6.—Using an external aerial with a frame or ferrite-rod aerial circuit.

while, because the vehicle chassis connection made through the accumulator circuit has a similar effect.

For temporary use there is no need to fix the receiver in place, but it should not be overlooked that the chassis in a receiver such as that in Fig. 5 is negative, while the vehicle chassis and metal parts will usually be positive. Direct contact must thus be avoided. If the receiver is permanently mounted, insulated fixing bushes can be used, or a wooden panel or securing strips can be provided, so that there is no direct contact between receiver and vehicle.

**AUDIO TEST OSCILLATOR**

(Continued from page 640)

covered by choosing C2 somewhere between 0.001 and 0.005  $\mu$ F.

**Output**

The value of the output control VR depends to some extent on the transformer used. If an interstage transformer of, say, 3:1 turns ratio is employed, the output will be high impedance and VR should be about 100,000 ohms. If a speaker transformer is used, then the low impedance output will permit the use of much lower values of VR, e.g., 1,000 ohms. As previously mentioned, this control should also incorporate the on/off switch, so that to operate the unit it is necessary only to turn the control knob to actuate the switch and adjust the output to the desired level.

At the frequency of operation of this oscillator

(about 400 to 1,000c/s), almost any transistor will work satisfactorily. The red-spot type on sale for a few shillings is quite suitable, also the OC71 and any type designed for audio applications.

A modification to provide operation on more than one frequency by switching C2 is shown in Fig. 2. The values of the additional condensers can be chosen by experiment, but those shown in Fig. 2 should give a good frequency coverage.

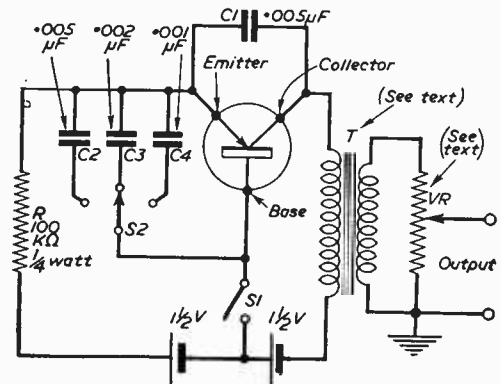


Fig. 2.—Circuit for three different frequencies

**COMPONENT VALUES FOR FIG. 2**

- C1—0.005  $\mu$ F.
- C2—0.005  $\mu$ F.
- C3—0.002  $\mu$ F.
- C4—0.001  $\mu$ F.
- R—100,000 ohms  $\frac{1}{4}$  watt.
- S2—Rotary switch, single pole, 3 position.



# NEWS FROM THE CLUBS

**ALDRSHOT AND DISTRICT AMATEUR RADIO CLUB**  
Hon Sec.: J. E. Fuller (G310E), 9, Laws Terrace, Aldershot, Hants.

MEETINGS are held fortnightly as from November 11th at the Cannon Hotel, with Morse practices and lectures. The meetings start at 7.30 p.m. New members are welcome. Morse practices are held every Saturday afternoon at the Hon. Sec's QTH.

## BLACKBURN AMATEUR RADIO CLUB

Hon. Sec.: F. Bird (G3GXE), 14, Old Bank Lane, Whinney Heights, Blackburn, Lancs.

THE club has now taken over a room annex at the Corporation Park Hotel, Renridge Road. A committee has been formed to deal with the club's aeriels and a Morse class has been started for beginners. It is hoped to include a class on radio theory at a later date for those wishing to sit for the R.A.E. The club has applied for a transmitting licence and it is on the air on Forty and Top Band 'phone. Plans are in hand for the building of a new 150W rig.

## THE BRITISH INSTITUTION OF RADIO ENGINEERS

9, Bedford Square, London, W.C.1.

A COPY of the programme booklet for meetings during the first half of the 1959-60 session can be obtained on application to the Institution at the above address.

Meetings for November, 1959:

**London Section.**—Meetings held at the London School of Hygiene and Tropical Medicine, Keppel Street, Gower Street, W.C.1.

November 11th at 6.30 p.m.—Medical Electronics Group Meeting. "Physiological and Acoustical Aspects of Hearing," by Dr. R. P. Gannon, B.Sc., M.B., Ch.B.

November 18th at 3 p.m. and 6 p.m.—Half-day Symposium on "Electronic Digitizing Techniques" to be opened by G. J. Herring, M.Sc.

**Bristol—South-western Section.**—At School of Management Studies, Unity Street.

November 18th at 7 p.m.—"Data Recording and Presentation," by D. W. Thomasson (Associate Member).

**Cheltenham—South Midlands Section.**—Meetings are held at North Gloucestershire Technical College.

November 27th at 7 p.m.—"A Vidicon Television Camera Channel," by B. J. Pover (Associate Member).

**Edinburgh—Scottish Section.**—Meetings are held at the Department of Natural Philosophy, The University, Drummond Street.

November 12th at 7 p.m.—"The Transistor and its Uses in Communication and Control Equipment," by E. Wolfendale, B.Sc.

**Glasgow—Scottish Section.**—Meetings are held at the Institution of Engineers and Shipbuilders, 39, Elmbank Crescent.

November 11th at 7 p.m.—"The Transistor and its Use in Communication and Control Equipment," by E. Wolfendale, B.Sc.

**Liverpool—Merseyside Section.**—Meetings are held at the University Club, 2, Mount Pleasant.

November 10th at 7 p.m.—"The Use of Transistors in Communications and Control," by E. Wolfendale, B.Sc.

**Manchester—North-western Section.**—Meetings are held at Reynolds Hall, College of Technology, Sackville Street.

November 12th at 6.30 p.m.—"Progress in Permanent Magnet Materials," by J. E. Gould.

**Newcastle-upon-Tyne—North-eastern Section.**—Meetings are held at the Institution of Mining and Mechanical Engineers, Neville Hall, Westgate Road.

November 11th at 6 p.m.—"Electronic Welding Controls," by C. R. Bates (Associate Member).

**Wolverhampton—West Midlands Section.**—Meetings are held at Wolverhampton and Staffordshire College of Technology, Wulfruna Street.

November 11th at 7.15 p.m.—"Recent Developments in Semiconductor Rectifiers."

## LEEDS AMATEUR RADIO SOCIETY

Swarthmore Education Centre, 4, Woodhouse Square, Leeds 3. Hon. Sec.: D. Dinsdale, 8, Quarry Mount Street, Leeds 6.

Forthcoming events:

November 11th.—Visit to Spen Valley Amateur Radio Society, George Hotel, Cleckheaton.

November 18th.—Demonstration of Simple S.W. Superhet, by W. Ripley.

November 25th.—Visit to see Electron Microscope in Dept. of Biomolecular Structure.

December 2nd.—Snag night.

December 9th.—Discussion for social.

December 16th.—Social evening.

January 6th, 1960.—Visit to see electronic computer in Leeds University.

January 13th.—Junk sale.

January 20th.—Tape recorders by Philips Electrical Ltd., George Hotel, Cleckheaton.

January 27th.—Film show in Psychology Dept.

February 3rd.—Rag chew.

February 10th.—Some simple items of test gear. E. Sollitt and W. Ripley.

February 17th.—Visit to Mains Radio Gramophones Ltd., Bradford, 7 p.m.

February 24th.—Receiver contest night.

March 2nd.—Demonstration of Photo Electric Devices. E. Sollitt.

March 9th.—Film show in Dept. of Psychology.

March 16th.—Demonstration of hi-fi equipment by Fane Acoustics Ltd..

March 23rd.—Practical demonstration of home-built table top transmitter, by W. Ripley.

March 30th.—Visit to Leeds Police Information Room, 7.30 p.m.

April 6th.—Radio controlled models.

April 27th.—Visit to Roneo Ltd., 7.30 p.m.

May 4th.—Film show in Dept. of Psychology.

May 11th.—Tape recorders.

May 18th.—Field day discussion.


May 25th.—Bring and buy sale for club funds.

June 1st.—Annual general meeting.

## THE SLADE RADIO SOCIETY

The Church House, High Street, Erdington, Birmingham 23. Hon. Sec.: C. N. Smart, 110, Woolmore Road, Erdington, Birmingham 23.

(Continued on page 689)

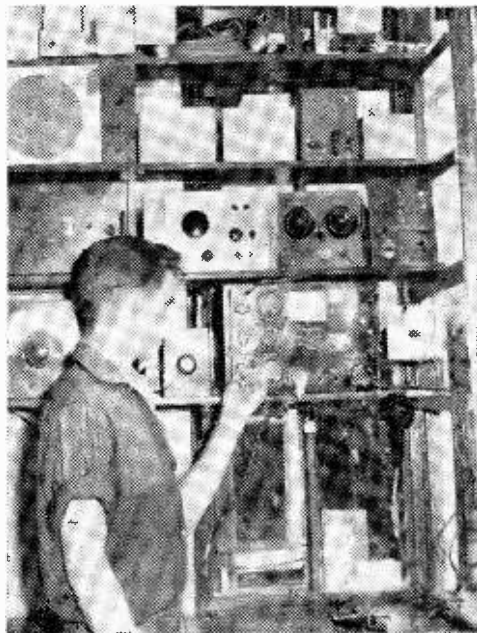

T. Fuller of Beaminstor in his den.

# NEW!

## DO-IT-YOURSELF TRAINING TECHNIQUE in RADIO & ELECTRONICS

### You LEARN while you BUILD...

#### SIMPLE...PRACTICAL...FASCINATING...

**ANNOUNCING**—after many years of highly successful operation in the U.S.A. and in Europe—the latest system in home training in electronics is now introduced by an entirely new British training organisation.

**AT LAST**—a comprehensive and simple way of learning—by practical means—the basic principles of radio and electronics, with a minimum of theory.

**YOU LEARN BY BUILDING** actual equipment with the components and parts which we send you. You advance by simple steps using high quality equipment and performing a whole series of interesting and instructive experiments. No mathematics!

**INSTRUCTION MANUALS** and our teaching staff employ the latest techniques for showing clearly how radio works in a practical and interesting manner. You really have fun whilst learning! And you end by possessing a first rate piece of home equipment with the full knowledge of how it operates and—very important—how to service and maintain it afterwards. A full library of magnificent illustrated textbooks are included with the Courses.


**IN FACT** for the "Do-it-Yourself" enthusiast, the hobbyist, or those wanting help with their radio career training, or to set up their own full or part-time servicing business—then this new and exciting instructional system is exactly what is needed and it can all be provided at very moderate cost. Easy payments available. Post the coupon now, for full details. There is no obligation of any kind.

**BUILD YOUR OWN:** ● RADIO EQUIPMENT ● HI-FI INSTALLATION ● TEST GEAR—AND LEARN AS YOU DO IT!


**LOTS OF INSTRUCTIVE EXPERIMENTS AT HOME!**



Power supply circuits

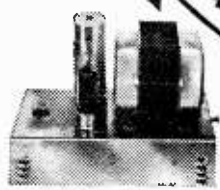

Test equipment supplied

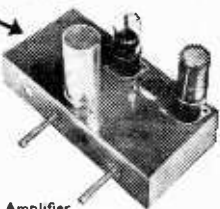

Amplifier, oscillator and detector circuits



Basic 1st stage receiver

Servicing of commercial receivers



# FREE-POST TODAY

## No Mathematics!

To RADIOSTRUCTOR (Dept. G30)  
46 MARKET PLACE, READING, BERKS.

Please send full details of your Radio Equipment Courses without any obligation to:

Name .....

Address .....

# RADIOSTRUCTOR



BRITAIN'S LEADING RADIO TRAINING ORGANISATION

801 BLOCK CAPS PLEASE We do not employ representatives. 12.59
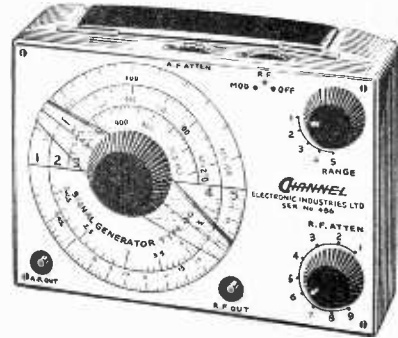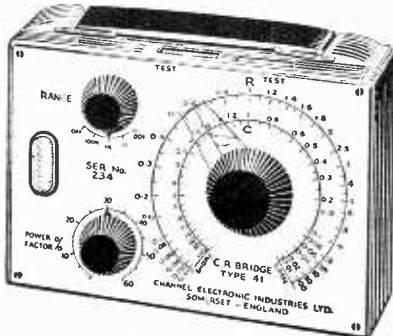
## NEW! UNIQUE! MINIATURE TRANSISTORIZED SIGNAL GENERATOR TYPE 40

- ★ Up to 20 Mc/s on fundamentals.
- ★ R.F. and Audio Output, Attenuated.
- ★ Accuracy better than 2%.
- ★ Miniature size only 4½in. x 3½in.

PRICE NET **£5.15.0.** Battery 2/6 extra.  
Post (C.O.D. or C.W.O.), 2/6.



## MINIATURE TRANSISTORIZED R.C. BRIDGE TYPE 41

- ★ Capacitance 5 μF to 20 μF.
- ★ Resistance 5 Ω to 20 MΩ.
- ★ Magic Eye Balance Indicator.
- ★ Calibrated Power Factor Check.
- ★ Miniature Size—Light Weight.

PRICE NET **£5.10.0.** Battery 3/3 extra.  
Post (C.O.D. or C.W.O.), 2/6.


SEND S.A.E. FOR LEAFLETS, OR ORDER TODAY, FROM—

**CHANNEL ELECTRONIC INDUSTRIES LTD.** DEPT. P. DUNSTAN RD. BURNHAM-ON-SEA, SOM.
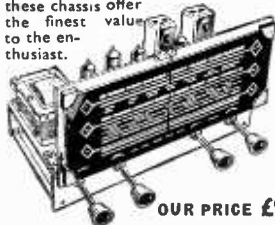
# KINGSMERE SUPPLIES LIMITED

Insured Post 1/-, over £2 Free. (Export extra.) MAIL ORDER HOUSE TERMS: Remit with Order or C.O.D.

Built to the highest specifications, these chassis offer the finest value to the enthusiast.



**ALL BRITISH RADIOGRAM CHASSIS. 3 WAVEBANDS**  
5 MULLARD VALVES  
ECH81, EF89, EBC81, EL84, EZ80  
Brand new and guar. A.C. 200/250 v. Short-Medium-Long-Gram. P.U. High Q dust core coils. Latest circuit technique. AVC and neg. feedback. 4 watts. Chassis size 13½ x 6 x 7in. high. Aligned and calibrated ready for use. Quality at Low Cost. Chassis isolated. H.P. Dep. £5 and five monthly of £1.

OUR PRICE **£9-9-0** AM-FM MODEL £18-18-0



**BRAND NEW AND BOXED**

OUR PRICE **£6-19-6**

**U.S.A. WORLD'S FINEST 4-SPEED AUTOCHANGER**  
IDEAL FOR USE WITH OUR CHASSIS  
H.P. Dep. £3.10.0 and four monthly of £1.  
Stereo-monaural model £2 extra

Matched Speakers, 5in., 6in. x 4in., 6½in., 8in. 17/6 ea. 10in. 25/-.

**90-DAY GUARANTEE VALVES ALL BRAND NEW**

|      |       |        |       |
|------|-------|--------|-------|
| 6/6  | 7/6   | 1/6    | 5/6   |
| 5U4  | 6Q7G  | 954    | 1S5   |
| 6K8G | 12AX7 | EA50   | 1T4   |
| 6N7M | EF41  | E1148  | 6K6GT |
| 6V6G | EL41  | 6H6GT. | 807   |
| 6X5G | EL84  | 2/6    | SP61  |
| 6AM6 | EZ40  | 6K7G   | 6AC7M |

**SPECIAL PRICE PER SET**  
6K8G, 6K7G, 6Q7G, 6V6G, 6X5G ... 27/6  
1R5, 1T4, 1S5, 3V4 or 3S4 ... 27/6  
Matched Pairs 6V6G, 15/-, EL84, 17/6  
Valve Boxes, All Sizes ... 2/- doz.  
Carbon Pots, 5K to 2M, 2/6; DP, 4/-  
**BSR 4-SPEED SINGLE PLAYER Model TU9.** Our bargain price, 90/-  
Cut out board, 12½in. x 16½in., 5/-.

## ALFA MULTIMETER

Pocket size 5½ x 3½ x 1½in.  
300 microamp F.S.D. 3in. Scale.  
17 Ranges. 3,330 ohms per volt.  
A.C. Volts. 0 to 1,200 v. in 5 ranges.  
D.C. Volts. 0 to 1,200 v. in 5 ranges.  
D.C. Current. 0 to 300 m.a. in 3 ranges.  
Resistance. 0 to 20 K and 0 to 2 meg.  
Decibels. —20 to +23 db. and +20 to +37 db.

Complete with leads and prods. Use No. 8 battery. Fully Guaranteed.

**REDUCED PRICE £5-19-6**

## "GEVAERT GEVASONOR" LONG PLAY PLASTIC RECORDING TAPE

On universal fitting plastic spools, for all recorders single and double track. 50% extra play at standard prices.  
7in. spool 1,700ft. tape, our price 35/-  
5in. spool 850ft. tape, our price 21/-  
MSS 3in. spool 225ft., price 7/6

## STANDARD PLASTIC TAPE

7in. spool 1,200ft. tape, 24/-  
5in. spool 600ft. tape, 15/-  
Long Play 5½in. 500ft. 28/-  
Satisfaction guaranteed or cash refunded.

**FOAMCOURT WAYE, FERRING, WORTHING, SUSSEX**

**PROGRAMME for November and December, 1959.**

November 20th.—Annual general meeting.

December 4th.—"Colour Organs"—a talk and demonstration of this fascinating branch of Electronics and Music, by D. T. Wilson (Member).

December 18th.—"Fun and Games"—presented by L. H. Blackwell and G. L. Turner.

All meetings are held at 7.45 p.m. Full details from the secretary.

**SPEN VALLEY AMATEUR RADIO SOCIETY**

George Hotel, Cleckheaton.

Hon. Sec. : N. Pridle, 100, Raikes Lane, Birstall, Leeds.

**FUTURE events :**

November 11th.—Lecture on The Coupling of Aerials to Transmitters, by the Senior Maintenance Engineer of Holme Moss.

November 25th.—Talk on printed circuits by a member of the development staff of Mains Radio Gramophones Ltd., Bradford.

December 9th.—Demonstration and talk on aerial problems, by A. R. Bailey, B.Sc.

Classes are now being held for those wishing to take the R.A.E.

**THE TEES SIDE AMATEUR RADIO CLUB**

Settlement House, Newport Road, Middlesbrough.

At the annual general meeting the following officers were elected : chairman, J. B. Harding (G3YH); secretary, A. L. Taylor (G3MMO); treasurer, A. E. Moon (G3KBM).

A good attendance was made at the recent visit to the Pontop Pike BBC Television Transmitting Station and the BBC staff were very helpful.

**Future events :**

November 13th.—The Panadaptor—G3JMO.

November 27th.—A tape-recorded lecture.

December 12th.—Annual dinner.

All meetings are held at Settlement House, Newport Road, Middlesbrough, at 8 p.m. For further details write to the hon. sec. at 12, Endsleigh Drive, Acklam, Middlesbrough, Yorks.

**WELLINGBOROUGH AND DISTRICT RADIO & TELEVISION SOCIETY**

Silver Street, Wellingborough.

Hon. Sec. : D. J. Trusler, 87, Irchester Road, Rushden, Northants.

It is announced that Mr. G. Abrams, A.M.I.P.R.E., A.M.T.S., has accepted the presidency of the society.

**Future events :**

November 12th.—Members' slide night.

November 19th.—"Tape recorders," G. E. Shaw.  
December 3rd.—"A brief history of electric lighting," J. Farr.

December 10th.—Three films on the "Application of Steel."

December 17th.—Annual Christmas dinner at the Hind Hotel.

January 7th, 1960.—Annual general meeting.

Meetings are held every Thursday at 7.30 p.m. in the club room above the W.L.C.S. Fruiterer's in Silver Street, Wellingborough. Visitors and new members are always welcome.

**CLIFTON AMATEUR RADIO SOCIETY**

225, New Cross Road, S.E.14.

Hon. Sec. : C. Bullivant (G3DIC), 25, St. Fillans Road, Canford, S.E.6.

At the annual general meeting of the society the chairman, W. Martin (G3FVG), hon. secretary C. Bullivant (G3DIC), hon. treasurer N. Moore and committee, Messrs. E. Godsmark (G3IWL), R. Poppi and R. Schilling, were re-elected for the coming year. An Audio Section was formed to cater for members interested in hi-fi amplifiers and tape recorders under the guidance of Mr. D. Reed. This section will be pleased to hear from prospective members interested in this field. The recent Club Transmitting Field Day was won by C. Hatfull (G3HZI).

Club meetings are held every Friday evening and the club-room opens Sunday morning and Wednesday evenings. Plans are in hand to extend the facilities of the club station to include a V.H.F. operating position and also a SWL position.

**Forthcoming event :**

November 13th.—Grand Junk Sale.

**BURTON-ON-TRENT AND DISTRICT RADIO SOCIETY**

Club Room, Stapenhill Institute.

Hon. Sec. : J. A. Morris, 9, Rosliston Road South, Drakelow.

Burton-on-Trent, Staffs.

SOME interesting lectures have been planned for the winter months and a programme of forthcoming events may be obtained from the secretary. Meetings are held every Wednesday at 7.30 p.m. at Stapenhill Institute and lectures are held on the second Wednesday in every month. Every week a general get-together is held when the TX is put into use. New members are always welcome.

**Forthcoming event :**

November 18th.—Annual Dinner.

## Aligning Tape Heads

### NO INSTRUMENTS ARE NEEDED

ABOUT a year or so ago when experimenting with a tape recorder, I was surprised to find that the high frequencies were highly attenuated when the alignment of the R/P head was slightly upset whilst playing back. Alignment in this case meaning that the length of the head gap is at right angles to the length of the tape in the plane of the tape. With a slightly misaligned head there would be little loss of quality when playing back one's own recordings, although the "gap" would be effectively wider, but the reproduction from pre-recorded tapes would be bound to suffer. The method I adopted to ensure that the head was aligned is as follows:

**Method**

First make a recording in the normal way on the end of a tape (see Fig. 1), and run the tape off the left hand spool; music with tinny percussion gives best results. Now play the recording back

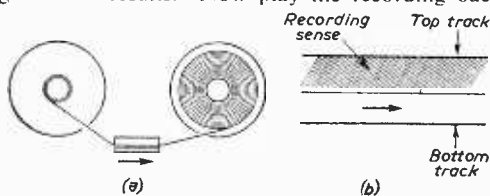


Fig. 1.—Recording

By G. Tully

with the back of the tape against the head, i.e., do not turn the tape "over," but change over the spools (see Fig. 2). The left-hand spool will now run in the reverse direction so do not use the rewind control. The recording is now heard backwards and some of the signal is lost due to tape thickness. Note the existing position of the head and assuming there is an adjusting screw,


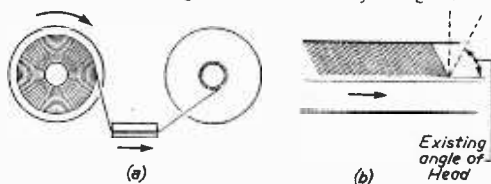


Fig. 2.—Playing-back

count the number of turns required to give the highest frequency response. Now move the head so it is exactly between these positions, i.e., half the number of turns back. The head is now correctly aligned but it is as well to repeat the process again as a check. This method works best with double-play tape as the adjustment is not very sharp when playing backwards through standard thickness tape. Of course, the alignment may also be adjusted while a professionally pre-recorded tape is being played back.

# Open to Discussion

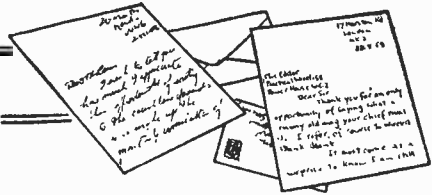

The Editor does not necessarily agree with opinions expressed by his correspondents.

### Mains Polarity

SIR.—Seeing the letter from Mr. Kingdon in last month's issue on earth connections brought to mind a point in connection with the mains which I have not yet had fully explained. I am on A.C. and have a simple A.C./D.C. type of set with resistance smoothing. The house is wired with two-pin sockets and consequently the set plug has two pins and may thus easily be reversed in the socket. I found that with the plug in one way round, reception is clear and undistorted, but if the plug is turned round the signal has a ripple on it giving a sort of bubbling with speech or music. This is presumably due to the smoothing not being too effective on account of the resistance in place of a good choke. To ensure that the set always gave good reception the plug and socket were marked with a spot of red cellulose paint. The set is fitted in a bedroom cabinet and one morning when switched on, the reproduction was "bubbly," and thinking that the plug was in the wrong way round I went to change it, but found that it was correct—according to my red marks. Since this happened I have found on many occasions that the plug has to be turned round from time to time, indicating, I think, that the phase at the power station is somehow changed. How can this be done with the present system of frequency-controlled mains, etc. I thought that the system was fool-proof, but cannot see any other explanation for the ripple, other than changes in "Live" and "Neutral" wiring at the power station, unless there is some other explanation?—G. F. WATIS (N.W.9).

### Rectification

SIR.—My father tells me that in his young days when crystal sets were the only ones used, pieces of coal, etc., were used as crystals, and rectification seemed to take place under the most unusual conditions. When valves came into use, a similar state of affairs existed, and in many cases one could obtain a signal without any grid leak or condenser, the essentials for rectification apparently existing in the material from which the valveholder was made. Could this account for a peculiar reception I am getting on my tape recorder, where, if I run a lead to an upstairs room I can get the BBC programmes? I cannot see otherwise where rectification is taking

place, as none of the valves is surely working at voltages or conditions relative to detection, and I would have thought that the audio conditions and components would have precluded rectification.—G. R. E. (Bristol).

### Transistors on V.H.F.

SIR,—I have tried to make up a pocket transistor set to receive the TV sound programmes, but so far without much success. On the continent there are dozens of V.H.F. transistor sets, and I cannot find one in this country. I know the ordinary red spot doesn't go down very low, but surely an ordinary good one should be capable of receiving TV sound. The aerial need only be very small, and I would think that there would be a good demand for a small set of this type. What is the snag? Have any of your

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying commercial or surplus equipment. We cannot supply alternative details for receivers described in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of cover.

readers made a set of this type which works satisfactorily? If so, perhaps they could pass on the details, as I am sure there are many who would be interested.—G. PARRISH (Eastbourne).  
[Whilst it might be possible to make a set with existing transistors to function on the Band I television stations, so far as we are aware there are no suitable components to enable a Band III receiver to be constructed. If any readers have successfully tackled this problem we should be glad to receive details, and if suitable to pass them on to our readers.—ED.]

### M.W. Reception

SIR.—I have been a S.W.L. for a number of years, both to Ham and BBC stations and would now like to obtain DX on M.W. I understand that it is possible to obtain U.S.A. stations on M.W. and would be pleased to hear from anyone who has done so, giving details of the best time and frequency to use, etc.—E. R. WILKS (Streatham House, High Street, Wilden, Beds).

### High Fidelity


SIR.—Each year on my visit to the Radio Show I make a point of attending demonstrations of Hi-Fi given by various exhibitors. I am not a musician but this so-called high fidelity is quite unacceptable to my ears. True, some of the reproducers gave a very pleasant rendering of bass and middle registers, but nearly all gave

(Continued on page 693)
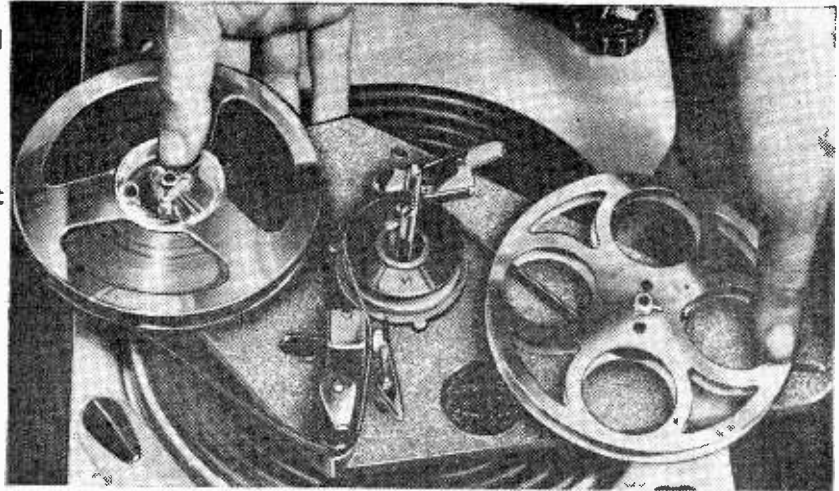
# A-REVOLUTIONARY NEW BRITISH INVENTION!

- ★ Uses standard tapes
- ★ Plays at 7½" per. sec. or 3 other speeds
- ★ Records direct from radio or microphone
- ★ Erase and fast rewind

Results equal to a £50 recorder — yet costs only £13-12 (or £17-11 complete with special moving-coil microphone and 600 ft. reel of tape.)  
**EASY TERMS**



## Instantly turns any gramophone into a first-class Tape-Recorder and back into a record-player in a moment!

Gramdeck is completely *new* . . . a revolutionary and ingenious invention that instantly turns your gramophone into a tape-recorder and back into a gramophone at will! Slip the Gramdeck on to your turntable and you have the finest tape-recorder you've ever heard! Lift it off . . . your gramophone is ready to play records again. There are no motors or valves to go wrong—and you get a quality that has to be heard to be believed! Everyone is praising the Gramdeck.

"The quality is at least equal to that obtained from a good microgroove disc," says a leading professional journal.

"Simple—simple . . . why on earth did no one think of it before!"—THE TAPE RECORDER.  
 "Ingenious and robust."—BRITISH SOUND RECORDING ASSOCIATION JOURNAL.

"Quality of reproduction excellent . . . real hi-fi results . . . potential is tremendous . . . both designer and manufacturer should be congratulated."—BRITISH RADIO & TV RETAILERS REVIEW.

"Better than many so-called hi-fi recorders . . . robust . . . carefully designed . . . excellent value."—AMATEUR CINE WORLD.

### WORKS FROM ANY RECORD-PLAYER OR RADIOGRAM

Gramdeck records and reproduces with a wonderful depth and breadth of tone. Because it uses equipment that is already in your gramophone it only costs a fraction of the high-quality tape-recorder you would normally require. Full details, specifications, photographs, easy terms, etc., are given in the Gramdeck Book. Send for your FREE copy, today.

MADE BY THE FIRM THAT MAKES MICROWAVE WAVE-GUIDES FOR VISCOUNTS & BRITANNIAS

### FREE BOOK—POST NOW!

I would like to know how to turn my gramophone into a first-class tape-recorder . . . please send me the Gramdeck Book—FREE and without obligation.

(Write if you prefer not to cut coupon)

NAME .....

ADDRESS .....

Gramdeck (Dept. PA 803) 29 Wright's Lane  
 Kensington, London, W.8

**Gramdeck**  
 GRAMOPHONE TAPE RECORDER  
 HIGH QUALITY TAPE-RECORDING FOR EVERY HOME

**GRAMDECK TURNS A TURNTABLE INTO A TAPE-RECORDER**



# LASKY'S RADIO

**Now Ready! The Finest Components Catalogue**

for the home constructor.  
100 pages, 8½ x 5½ in.,  
copiously illustrated.  
PRICE 2/- Post 6d.  
Send for your copy today!



## CHRISTMAS BARGAINS

### TAPE DECK OFFERS

Latest B.S.R. "MONODECK." Single speed, 3½ i.p.s. Takes 5½ in. spools. Simple controls. LASKY'S PRICE £9.19.6.

TRUVOX MK. III, 2-sp., 3½ and 7½ i.p.s., 3 shaded pole, B.T.H. motors. Takes 7in. spools. Push-button controls. £14.19.6.

Latest COLLARO Studio Tape Transcriber. 3-sp., 1½, 3½, 7½ i.p.s. Fitted digital counter. Takes 7in. spools. Push-button controls. £15.19.6.

COLLARO MK. 4 Tape Transcriber, fitted digital counter. Few only. £17.19.6.  
Carriage and Insurance all Tape Decks. 12/6.

### LOWEST-PRICED TAPE-RECORDER ever offered.

For 200/250 v. A.C. 2-sp., 3½ and 7½, twin track. 60 min. playing time at 3½; 30 min. at 7½. Inputs for mike and tuner. 5in. Speaker. Smart blue/grey case, 12½ x 9½ x 7½ in. LASKY'S PRICE, including 5in. spool of tape, empty spool, crystal hand mike and radio jack.

**21 GNS.**

Carr. and Insur., 12/6.

### SINGLE PLAYERS

E.M.I. 4-sp., wired for STEREO and fitted Acos stereo t.o. cartridge.

**£6.19.6.**


Post 5/-.

COLLARO Junior 4-sp. Motor and separate pick-ups.

**75/-** Post free.

### 4-SPEED MIXER AUTO-CHANGERS

Brand New in makers' cartons

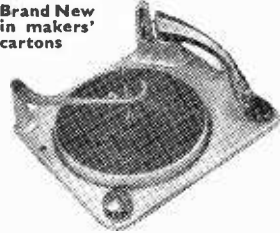

B.S.R. type UAB, complete with latest "ful-fi" pick-up. £6.19.6. Post 5/-.

Ditto, wired for STEREO, and complete with stereo cartridge, £7.19.6.

B.S.R. latest type UA12, wired for STEREO and complete with stereo cartridge. £8.19.6. Post 5/-.

Ditto, monaural cartridge, £7.19.6.

COLLARO: complete with Studio crystal pick-up and sapphire stylus. £7.19.6. Post 3/6.

GARRARD 4-sp. Auto-changers, monaural, from £9.19.6.

Wired for STEREO and complete with stereo cartridge, from £11.19.6.

### LASKY'S (HARROW ROAD) LTD.

Open All Day Saturday. Early Closing Thurs. Mail Orders to Edgware Road, please.  
42, TOTTENHAM COURT ROAD, W.1. † 207, EDGWARE ROAD, LONDON, W.2.  
Telephone: MUSEUM 2865. PADdinton 321.2 and CUNningham 1979.

### SOUTHERN RADIO'S WIRELESS BARGAINS

ATTACHMENTS for "18" Transreceivers. ALL BRAND NEW. HEADPHONES, 15/6; HAND MICROPHONE, 12/6; AERIALS, 5/-; SET OF 6 VALVES, 30/-.

CONDENSERS, 100 Assorted, Mica, Tubular, etc. NEW, 15/-.  
CONTACTOR TIME SWITCHES, 2 impulses per sec., in case .....11/6

REMOTE CONTACTOR. For use with above.....7/6  
LUBBRA HOLE CUTTERS. Adjustable ¼ to 3½". For Metal, Plastic, etc.....7/-

MAGNETS, Strong Bar Type, 2" x ½", 1/6 each.  
MORSE PRACTICE SET, TAPPER with BUZZER on Base. Complete with Battery. BRAND NEW.....12/6

MORSE TAPPERS, Midget Type, 2/9. Standard, 3/6. Heavy Type on Base, 5/6. ALL BRAND NEW.

PACKARD-BELL AMPLIFIERS. Complete BRAND NEW with Valves; Relay, etc., etc. 17/6 each.

QUARTZ CRYSTALS. Types F.T.241 and F.T.243, 2-pin, ½ Spacing. Frequencies between 5,675 Kc/s and 8,650 Kc/s. (F.T. 243) 20 Mc/s, and 38.8 Mc/s. (F.T.241) 54th Harmonic, 4/- each. ALL BRAND NEW. TWELVE ASSORTED CRYSTALS, 45/-.

Holders for both types, 1/- each. Customers ordering 12 crystals can be supplied with lists of frequencies available for their choice.

RECORDING BLANKS. New "Emidisc," ready for use. 13" 6/- each. Quantity of 15 in metal case £4.

RESISTANCES, 100 Assorted useful values. New wire end, 12/6.  
SPECIAL OFFER, 12 ASSORTED METERS. Slightly damaged. Mainly broken cases (perfect movements). Including 3 Brand New Aircraft Instruments. 12 for 45/-.

STAR IDENTIFIERS, Type I A-N Covers both Hemispheres, 5/6.  
TI154 TRANSMITTERS. Complete, NEW condition, in Transit case.....£2.5.0

TRANSPARENT MAP CASES, Plastic, 14" x 10½". Ideal for Maps, Display, etc.....5/6

TRANSRECEIVERS. Type "38" complete with 5 valves, etc. New condition, untested by us, but serviceable, no guarantee. 22/6 each.


ATTACHMENTS for Type "38" Transreceivers. ALL BRAND NEW. PHONES, 15/6; THROAT MICROPHONES, 4/6; JUNCTION BOXES, 2/6; AERIALS, No. 1, 2/6; No. 2, 5/-; WEBBING, 4/-; HAVERSACKS, 5/-; VALVES, A.R.P.12, 4/6; A.T.P.4, 3/6. Set of FIVE VALVES, 19/- the set.

POST OR CARRIAGE EXTRA. FULL LIST OF RADIO BOOKS, ETC., 3d.

### SOUTHERN RADIO SUPPLY LTD.

11, LITTLE NEWPORT ST., LONDON, W.C.2. GER. 6653
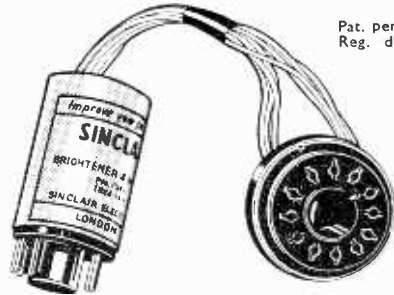
## IS YOUR T.V. TUBE DIMMING? YOU CAN EXTEND THE LIFE OF THAT TUBE AND IMPROVE THE PICTURE



Pat. pending.  
Reg. design.

PRICE **30/-**

Package & Postage 2/6.  
(Postal Orders.  
C.V.O. C.O.D.)

- NO SOLDERING
- NO WIRING
- JUST PLUG IN
- IT'S AUTOMATIC
- IT'S GUARANTEED!

One of the most common T.V. Tube faults is low emission, resulting in loss of brightness, contrast, definition and focus. The Sinclair Unit restores the cathode emission and corrects the above faults for a very low cost. Applicable to all sets operating off A.C. mains.

IMPORTANT. State make and model No. of set and tube in block capitals, please. If not satisfied money refunded if returned within 7 days.

## SINCLAIR ELECTRONICS,

18, NEWPORT COURT, CHARING CROSS ROAD, W.C.2. Phone: REGent 5520



a very nasty "edge" to the treble. On some, the sound from the violins appeared to come via comb and tissue paper. How can this be termed high fidelity when it does not resemble the original sound.—A. E. EVANS (Pulborough, Sussex).

#### Simple Tone Controls

**SIR**—With reference to Fig. 7 in the above article in the June issue, I found on building the control for a crystal pick-up the treble control. R5 did not alter the treble content of the signal at all. By experiment, I found that by disconnecting the track of R5 from the join of C3 and R4, and connecting a 470pF capacitor between R5 and earth the simple treble-out circuit enabled excellent results to be obtained. Using a Garrard G.C.2 crystal T.O. cartridge, the bass response and control is superb, and superior to that obtained by the circuit given in the "High Quality Record Player," which I have successfully built.—A. R. WILLS (Wallington, Surrey).

#### Adding an "S" Meter

**SIR**—I have been a regular reader of PRACTICAL WIRELESS for many years and have been looking back through some of my issues for 1943 for articles on the S meter. However, the only thing I could find was the Communication Receiver. I operate a R107 receiver, and would like to add an S meter for station comparison. Could any reader supply information on this modification, also the alignment details?—J. W. BARNETT (77, The Crescent, Dunsroft, Nr. Doncaster).

#### Correspondence Wanted

**SIR**—I would like to communicate with other readers of PRACTICAL WIRELESS who are interested in short wave radio.—JAMES RYAN (Sgmm.) ("Signals" Customer Bks., Althlone, Co. Westmeath).

#### Earth Connections

**SIR**—With reference to the letter from G. Y. Kingdon, of Norbury (November, 1959), there are two main reasons for using an earth connection to radio receivers. One is to provide a good path to earth (ground) of the signal picked up by the aerial. The more direct this path the better. If the power point earth was used for this purpose, it would in the majority of cases be long, acting perhaps as a counterpoise earth, which is not a good thing except for specialist work. Being laid alongside the mains supply wires, it can pick up mains interference readily. The second reason is safety, again in reference to radio. One point I think is overlooked is where earth leakage circuit breakers are installed in a house. The general public is unaware of this theory. If a radio set, A.C. type, with a 3-core lead is connected to a mains earth system with a circuit breaker, and its owner connects an outside earth lead to the earth terminal of the set, then the circuit breaker coil is short-circuited and, in theory, cannot trip if an earth leak occurs in any other appliance connected within the house.—W. PASCOE (Truro).

#### Transistors v. Valves

**SIR**—May I, too, enter the discussion about transistors v. valves? I am one of the "Younger Radio Set" who started seriously with transistors. When I started I knew nothing about their susceptibility to heat, reversed polarity, etc., and was in consequence often connecting them with wrong polarity. None of them has ever broken down from this cause, and this is perfectly understandable, since the reason for this breakdown is that the emitter and collector junctions have different heat dissipating capabilities. However, the transistor is almost always well within the maximum dissipation of both the junctions, and consequently it is only in badly designed circuits or when the transistor is working near to its maximum dissipation that any harm is liable to occur, and then only when the polarity is kept reversed for a long time.

As to their sensitivity to heat, this is definitely overrated, since I have known transistors become too hot to touch. Once indeed, I accidentally laid a very hot soldering iron on one, and by the time I noticed it the transistor was too hot to touch. I despairingly tried it, and to my surprise it worked as well after this treatment as before.

Furthermore, another aspect of transistors that has been greatly overrated is their cost. It is true that most valves have an almost standard price, transistors have not. If the constructor insists on buying the most expensive, of course, he will be led to believe that they are expensive. Very few people seem to be aware that one manufacturer sells R.F. transistors which are neither surplus nor out of date for 8s. 6d.! Audio types can also be bought for 7s. 6d., and valves are at least twice the price.

The last point that I wish to emphasise is the interchangeability of transistors, for very nearly any similar type of transistors can be interchanged for any other with good results so long as they are of similar type.—R. J. TORRENS (Sherborne).

**SIR**—In reference to the letter by R. Kerr in your November issue, I would like to comment on some points. Firstly, I have known transistors to be very hot and not to be damaged. I have known an output transistor to have its base shorted to earth so that the transistor was smoking yet it works as well as it did before.

I have known the polarity of a set to be reversed and no harm to be done. Transistors are now being built with metal walls and even if they are glass it is simplicity itself to screen them. Transistors do not mean midget sets, they mean that the receiver part can occupy smaller space and hence remove obstructions to sound from behind the set. A definite advantage is that all lethal voltages are removed and danger of fire and sparking is removed. R. Kerr's comment on a one-valve set is also wrong as the PCF80 is two valves in one and a lot more components are needed such as mains transformers and rectifiers. My transistor portable is not a midget as it measures 10in. × 5in. × 4in. and gives very good reproduction. Incidentally, R. Kerr comments on a crystal set which is a form of semi-conductor set.—K. PYROL (Redhow).

SPECIAL OFFERS

V.H.F./F.M. RADIO RECEIVER KIT. List price 15 gu. Our price £8/19/-.

AMPLIFIER KIT Famous make. Our price £5/15/-

RECORD PLAYER CABINETS 18in. x 13 1/2in. £3/10/- (Two-tone) 8 1/2in.

COLLARO "CONQUEST" Hi-Fi, 4-speed, 10 record Autochanger. Brand new, unused. £6/19/6 Limited Quantity. or Carton containing 2 Players £13/-/-

STEREO equipment 4-speed Single Player, famous make. Just received. Limited Quantity £6/19/- Carr. 3/-

A RADIO SET, complete 29/- 5K7, 6K8, 6G7, 6V8 with plus 5/- speaker and 6-volt vibrator pack! Suitable for adaptation as car radio.

CO-AXIAL CABLE

Semi-Air-Spaced low loss. 1-10 yds., 7d. per yd., p. & p. 17s. 20-30 yds., 6d. per yd., p. & p. 1/9.

50 YARD DRUMS 22/6. P. & P. 2/-.

VALVES ALL GUARANTEED 3 MONTHS.

PL81 SOILED, AMAZING VALUE AT ONLY 7/-

EY51 SHORT 7/- U25 SHORT 7/-

100 CONDENSERS 10/-

Due to huge purchase we can offer a wide, well balanced range of mainly the latest miniature Ceramic and Silver Mica Condensers from 1 pF to 10,000 pF. LIST VALUE OVER £5. A must for your spares box. Only 10/-.

PM SPEAKERS STANDARD 3 OHM Texted, top makes, performance guaranteed. 6 1/2in. 7/- 5in. 11/- 6 1/2in. 13/- 5in. 7/4

G73: Signal generator and wavemeter, precision attenuator. Top make. Operates from 100-230 v. A.C. mains. Size 1 1/2in. x 1 1/2in. x 8in. 79/- Carr. 6/-

TUBES

FACTORY REVACUUMED. ALL GUARANTEED 6 MONTHS. Carriage and insurance 12/6. Enquiries welcomed for any types not listed. Due to the high quality of our tubes, we are able to maintain the following unusually low prices. 6501, 6504, 6505, CRM91, CRM92, MW22-7, MW22-14, MW22-14C, £2/15/- MW22-17, MW22-18 £2/15/- 12EFM, CRM12, CRM12A, CRM12B, MW31-7, MW31-14C, MW31-18, £3/5/- T12-54 3/16, 3/31, 14KP4, 14KP4A, 108K, 121K, 141K, 7201A, 7202A, 7203A, AW36-21, C14FM, CRM141, CRM12, MW31-16, MW31-74, £3/15/- ME36-24, MW36-44, T12-54H 17AP, MW34, 8706A, C17FM, CRM171, CRM172, MW43-43, MW43-84, £4/10/- 7401A 3/6A, 4/15, 6801A, C14BM, C17BM, CRM151, CRM152A, CRM152B, CRM153, MW41-1, MW43-80, T41B, TR14-2, £5/5/- MW43-89 C21HM, C21HM, CRM211, CRM212, MW53-20, MW53-80 £6/15/-

REGUNNED TUBES

ALL GUARANTEED 12 MONTHS. Excellent workmanship. Carr. and ins. 12/6. MW31/18, MW31/74, 121K, £5/10/- 12KP4, CRM121B £5/15/- MW36-24, MW36-21, 141K, 14KP4, CRM141, CRM142 £6/15/- CRM152A, CRM152B, CRM153, CRM171, CRM172, MW43-64, 171K, 175AP4 £6/15/- MW53-20, MW53-80, CRM211, £9/10/- CRM212

NEW TV TUBES: SPECIAL OFFER

Frustrated export. Guaranteed 12 months. (Carriage and Insurance 12/6.) MW31-74, MW36-24 £7 10 0 MW43-64 £9 10 0

C.R. TUBES

Similar to the Acos HP65. Excellent reproduction ... 17/6 Cartridge only ... 15/- 2. As above, with Acos GP65 cartridge ... 22/- Cartridge only ... 19/6

XTAL PICK-UPS

STAAR GALAXY. Single-hole mounting, lightweight adjustable needle pressure. For any 3- or 4-speed turntable. Amazing value. 1. With latest Steig and Reuter or Sontone cartridge. Interchangeable with similar to the Acos HP65. Excellent reproduction ... 17/6 Cartridge only ... 15/- 2. As above, with Acos GP65 cartridge ... 22/- Cartridge only ... 19/6

ACOS HGP37 Cartridges ... 19/6 Standard Tuning Condensers, Twin gang, 1005, 4/-

H.T. RECTIFIERS

280J1779A (240 v. 80 mA.), 6/- R.M1. 6/- R.M2. 6/8. R.M3. 9/- R.M4 (E.R.), 15/6. R.M5 (E.R.), 21/- 14A86. 17/- 14A97. 23/- 14A100. 25/- 18RA 1-11-16-1. 7/9. 14RA 1-2-3-2. 18/- 18R1 2-3-2-4. 19/- 14RA 1-2-3-3. 22/-

BURWELL T.V. AERIALS. Complete Illustrated Price List of 1 to 12 element Band I and III aerials at amazing competitive prices (5d. stamp). TRANSISTORS AND DIODES RED SPOT. Transistors for I.F., L.F. and Output up to 800 kc/s. 5/- ea. (4/6 each in dozens). WHITE SPOT. R.F. and I.F. 2.5 Mc/s, 7/6 (7/- each in dozens). XA103. 15/-; XA104. 17/6; XB104. 10/-; G6T15. 25/-; V15/107. 4/01. TOP. 15/- GERMANIUM DIODES. General purpose famous make. 9d. 8/- doz. DIODES. Equivalent to GEX44. 3/9.

FREE TRANSFORMERS

To the purchaser of each manufacturer matched pair of GET15 Power 1 watt Power Transistors, price 50/-, we give free of charge the correct Push-Pull INPUT AND OUTPUT TRANSFORMERS of High Grade construction. Will transform your existing receiver or amplifier into a truly "Mains Volume" outfit.

L.T.V. CONVERTERS WITH INTERNAL POWER PACK

Well-known make, at a very competitive price, completely enclosed. Finished in hammered gold. Very compact. Can be put inside practically all T.V.s. Gain and Trimming controls. Listed at £7.0.0. £3/10/- Carr. 3/6 Or special price of £3 if purchased with any of the above T.V. sets.

TRANSMITTER POWER PACKS. 230v. A.C. 2 separate smoothed outputs 375, 550 or 620 v. 200/230 mA., 6.3 v. 5 A. Boved. 4 5U4G, £7/10/-, Less valves 26/10/-

TBS9: Transmitters 26/10/-, Carr. 5/- Receivers 24/10/-, Carr. 5/- OR 29/10/- pair, Carr. paid. 80ms modulating 80ms. 100-150 Mc/s. Ideal for conversion to 2 metres.

SCR522: Transmitter receivers. U.S.A. standard aircraft type. 100-140 Mc/s., less valves. 25/-, Carr. 5/-

RECTIFIER UNITS

Suitable for charging. 230 v. in. 24 v. 1.2 A. bridge. 35/-, Carr. 4/-

Transmitter/receiver: 12 volt D.C. CMY2: or 230 volt A.C. 3 wavebands. Cost originally over £200. £12/10/-, Carr. 6/-

LINE OUTPUT TRANSFORMERS. Most types available. From 22/6.

Table of vacuum tube types and prices. Columns include tube type (e.g., 1A5RT, 1A7-7, 10C5T), price in guineas (e.g., 6/6, 12/6), and other specifications.

VALVES PRICES REDUCED

GUARANTEED 3 MONTHS. 24 HOUR SERVICE FREE TRANSIT INSURANCE. All valves are new or fully guaranteed ex-Government or export equipment origin. Satisfaction or Money Back Guarantee on goods if returned unused within 14 days. 4d. FOR LIST OF 800 TYPES. 10% DISCOUNT SPECIAL OFFER to PURCHASERS of any SIX VALVES marked in black type (15% in dozens). Post: 1 valve, 6d.; 2-11, 1/-.

Table of vacuum tube types and prices. Columns include tube type (e.g., E650-BR, 6X4, 6X5), price in guineas (e.g., 12/6, 12/6), and other specifications.

Post: 2 lbs., 1/6, 4 lbs. 2/-, 7 lbs. 2/9, 15 lbs. 3/6. No C.O.D. Callers always welcome (E.C. Wenz.) ALL ITEMS LESS 5% AND POST FREE IN DOZENS.

TECHNICAL TRADING CO. P.O. BOX 21(P), 350-352, FRATTON ROAD, PORTSMOUTH

# SKILLED MEN!

## USE YOUR KNOWLEDGE IN A WORTHWHILE JOB

VACANCIES  
FOR  
LINEMEN  
DRIVERS  
DISPATCH RIDERS  
DRAUGHTSMEN  
DRIVER  
ELECTRICIANS  
RADIO  
MECHANICS  
TECHNICAL  
STOREMEN  
TELEGRAPH  
MECHANICS  
OPERATORS  
in  
**THE ROYAL  
SIGNALS**

*Up to £25 tax-free Bonus  
plus first-rate wages for  
two weeks of your time*

**A**RE you in a skilled trade? Then you can probably add a tidy sum to your income by joining the Army Emergency Reserve. For one thing, you get pay and allowances at full Regular Army rates whilst in camp. And the more your skill's worth in civilian work, the higher your Army rank and pay. Better still, you also get £9-£25 bonus tax-free.

For this you just spend 14 days a year at a camp, working on your own speciality. And money's not the only profit you get from that. You get a grand refresher course, giving you a lot of new ideas, and putting you right in touch with the latest Army developments. And you

get a welcome break from the usual routine, with sports, games and a great social life. For the place is full of people with the same interests as yourself. Don't miss this chance! Send off the coupon now to: H.Q. A.E.R. (R. Sigs.), Blacon Camp, Chester.

### POST THIS OFF RIGHT AWAY!

*Please send me—without obligation—the illustrated booklet telling me  
all about the Army Emergency Reserve.*

NAME .....

ADDRESS .....

TRADE ..... (PW/AER)

**RECEIVERS & COMPONENTS**

**VALVES**, new and used, from 1/6 each, all guaranteed. All types Radio Television Components. Lists free. **HAMILTON RADIO**, 237, Sedlescombe Rd. N. Hastings.

**CALLING 9IN. TELEVISION OWNERS**—Brand new factory fresh 9in. Ferranti Tubes, originally £14/10/-, will replace Mazda. Brinar, G.E.C., etc., £4/10/- each; 6 months' guarantee. **TOMLINS**, 127, Brockley Rise, Forest Hill, S.E.23.

Well known FM Tuner Kits. Complete kit ready to assemble, less valves... £3.15.0. Complete with valves ... 25. 5.0. Easy to follow Building Plans and Instructions ... 3s. 6d. **Prv Only**: Sets of FM Coils, I.F.s R'Det., etc., with circuit, and instructions £1. 0.0. S.A.E. for enquiries.

**R.C.R. 89, DERLEY ROAD, SOUTHALL, MIDD.**  
Callers at R.T.S. Goldhawk Rd., Seven Stars, London, W.12.

**RESISTORS**—100 new, wire ended, assorted, all types, 7/6 box, post free. **COOK'S OF BEDFORD**, 29, St. Mary's St., Bedford.

**RECLAIMED VALVES**, tested and perfect; huge stocks, all one price, 5/-, plus 6d. postage each. Delivery by return. **LEWIS**, 57, Chalford Walk, Woodford Green, Essex.

**TELEVISION TUBES**

**GUARANTEED** and fully tested replacement tubes for T.V. Every tube is rebuilt by skilled craftsmen and fitted with a complete new gun assembly. 12 months' full guarantee with every tube. Prices: ALL TYPES

12in. .... £5.17.6  
14in., 15in., 16in., 17in. .... £6.10.0

21in. on application.  
Carriage and Insurance 12/6 extra. **C.W.O. R. HAINSWORTH (Dept. P.)**, 31, Airedale College Mount, Undercliffe, Bradford 3, Yorks

**H.M.V. 15IN.**, English Electric 15in., Ultra, etc., Televisions, not working, originally £175 each. £5/10/- **TOMLINS**, 127, Brockley Rise, Forest Hill, S.E.23.

**ANNAKIN**

**Pamphonic Hi-Fi Amplifiers**, 10 watts. Selector switch, Bass, Treble, Volume, and Contour controls, Inputs, Tape, Radio, Mike, Gram (3 equalisation positions), 3i and 15 ohm output. Type 1004. List 25 gns. Our price 15 gns., post free. A first-class job we can really recommend.

**Fane and Wharfedale Speakers**. List prices.

**Hendix TA12G Transmitters**, 300 Kc-9 Mc. in 4 bands, 7 valves. A fine job. At the bargain price of £5, carr. 15/-.

**Periscope Prisms**. (Not triangular.) As used in tanks. Viewing space 4in. x 1 1/2in. 2 prisms needed for periscope. Only 3/- per pair of prisms, post 1/6. Also soiled condition at only 2/- pair, post 1/6.

**Receiver No. 71**. (Part of No. 1143 unit.) Bent and solid metal work. Useful for spare parts. (Over 100.) A real snip. Only 2/6 ea., post 3/6. Less xtals and valves.

**Phones**. L.R. single, Headband, 2/-, post 1/3.

**Micros**. Carbon. Cord. plug, 3/-, post 1/6.

**Relays**, 8,000 ohm, 1 make, 3/6, post 10d.

**Switches**, 3-pole 6-way rotary, 1/-, post 6d. Slider type 250 v. 3 a. O.K. for vacs. 1/-, post 6d.

**Power Units**. For 19 or 22 set, £1, carr. 6/6.

**Magnets**, 1in. D. x 4in., 2/6 doz., post 6d. Trade. Discount for quantity. Mainland only. No export. Free lists.

25 ASHFIELD PLACE, OTLEY, YORKS.

**RATES**: 5/6 per line or part thereof, average five words to line, minimum 2 lines. Box No. 1—extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless", Tower House, Southampton St., Strand, London, W.C.2.

The Famous Telephone type F in excellent condition. Works up to 3 miles with any twin wire. 60/- each, carr., etc., 10/-.

10 Line U.C. exchanges for use with any buzzer or magneto calling phones, £5, carr. 4/-.

Sets of 120 new American crystals from 5675 Kc to 8650 Kc in steps of 25 Kc except for 5725 and 5950. Must have cost £300. Offered at £5, plus p. & p. 5/-.

30 watt pressure type loudspeaker units. Unused. £3, plus carr., etc., 5/-.

4 of any of the following valves for 10/-: 6B91, EF91, EF92, 6K7, KTW61, 210SP1, 210VPT, 210DDT. Post 1/-.

PO relays 2,000 ohm coil, 2 make, 1 break. New. 5/-, p. & p. 1/-.

Vibrator Power packs. New, fully smoothed in black crackle case with croc. clips, etc. 6 v. input, output 160 v., 40 m.a. 25/-, p. & p. 3/6.

Life jacket lights. These consist of a battery container which takes a U2 battery and a small red lamp which can be attached by means of a powerful crocodile type clip. The whole thing is contained in a single rear lamp. New and boxed, 10/- per doz., 2/6 p. & p. or sample 2/- post paid.

**ELECTROSURE**

118, FORE STREET, EXETER

Phone: Exeter 56687.

**ALUMINIUM CHASSIS**, brackets, accessories, circuit printing. Write for catalogue. 25, Leach St., Prestwich, Manchester.

**COMPONENTS**, Valves, Tubes, etc. Write or phone for free list. **ARION TELEVISION**, 4, Maxted Rd., Peckham, S.E.15. (New X 7152.)

**SPEAKER REPAIRS**, Cones/Fields fitted. Clock Coils Wound. **L.S. REPAIRS**, Pluckley, Ashford, Kent.

40in. American Stainless Steel Whip Aerials, one piece with mountings and special loading coil in base in effect increasing height to 12 feet. 30' (5-). 250 Watt U.S.A. R.F. Amplifiers, raises output of small transmitter to 250 watts. Includes 2-HK-257 valves in push pull. Weight 88 lbs. New in case, £8 10 (15-). **Interphone Amplifiers**, 4 valves, 28 v. D.C. input easily convertible, 25/- with valves (5/-). **Kurman Plate Relay**, 7,000 ohms S.P.D.T. 12/6 (2/6). **Boeing Beehive Insulators**, white, 3 1/2in. x 1 1/2in. Ideal for H.F. 1/- (9d.). **Microswitches**, S.P.S.T. 1/6 (6d.). **S.P.D.T.**, 2/- (6d.). **D.P.D.T.**, 2/6 (6d.). **Chokes**, Freed 9 H., 270 m.a., 36 ohms, 5 P.D.T. 12/6 (3/-), 15 H. 60 m.a., 260 ohms, 8' (2-), Chicago 5/25H., 200 m.a., 7 lbs., 10/6

40-page List of over 1,000 different items available.

(2/6) 5'20 H., 300 m.a., 14 lbs., 20' (4-). **Germanium Rectifiers**, IN-52, 2 (6d.). **Klixon Circuit Breakers**, give automatic protection, 35 amps break, simply push to re-set, 5 P.D.T. 12/6 (3/-). **100k Insulators**, heavy, 10 1/2in. dia., 6 1/2in. feed through, 15/- (3/6). **Eimac VT-127A Valves**, 5 v. 10 amp, 100 watts, 300 mc/s. 25/- (3/-). **Plywood 25ft. Tripod Base**, self-supporting Aerial Masts, 65 (20-), 60 to 110 Meters Adjustable Calibrated 3 Element Beam Arrays, on adjustable boom for 2in. dia. mast with 100 feet, 1in. co-ax. lead in, 90' (15-).

We have lots of bits and pieces—please send your requirements—we can probably help. All enquiries answered. Amounts in brackets are carriage England and Wales.

**P. HARRIS**  
ORGANFORD, DORSIN

**POWER IN PACKETS**—"18" set owners... good stocks of 162 x 12 x 3v. H.t.s. at 10/9 delivered; but don't forget the shortage. Order an extra for spare. Also 84 x 64 x 4 1/2v. 10/9. A few 6v. Receivers left, 55/- ea., delivered. Same Receiver, less valves and Vib. reduced to clear at 29/- See advert. last month. Stamp for new lists of bargains. **Stob Press**—Just arrived... 90 x 1 1/2v. H.t.s. 10/9; 90 x 7 1/2v. H.t.s. 5/-; 1 1/2v. L.t. specials, 1/6; inc. p. & p. **DIGGINS**, 129/133, Radnor St., Hulme, Manchester 15.

**FM-AM STEREO****Radiogram chassis-CB8**

Paired output 6 watts Plain or Stereo Records. A hand-built quality unit with two speakers

ONLY £20.

**BEL SOUND PRODUCTS CO.**, Marlborough Yard, London, N.19. ARC. 5078.

**SAVE ON REPAIRS**.—100,000 Salvaged Radio and TV Spares. Valves, Tubes for practically any set made since 1936. Prices from:

Lot. 17/6; F.O.T., 7/6; Osc. Tr., 6/-; Sound, 2/6; Mains, 10/-; E.H.T. Mains, 50/-; Def. Coils, 12/6; Speakers, 5/-; Tubes, Mullard, Mazda, etc., 9-10in., 30/-; 12-14in., £2/19/6; 17in., £3/19/6; all picture tested, fitted free or sent subject to 14 days money-back guarantee; Mullard 6 months guarantee. Valves: 1,000 types from 1/6; EF91, EB91, 6J5, 2/6; EF80, U22, 10F1, 6F1, 6SN7, 3/6. We can save you pounds!

Send s.a.e. with enquiries or for complete list. **ST. JOHN'S RADIO**, 156, St. John's Hill, S.W.11. (Bat 9838.)

**NEW MINIATURE** Printed Resistors, 6d. **RAY**, 4, Dalton Ave., Whitefield, Manchester.

**TURRET TUNERS**, "Brayhead" make, £8/15/- post free; few only; state model. **A1 RADIO COMPONENTS**, 14, The Borough, Canterbury.

**KINGSLAND ELECTRONIC COMPONENTS****Stupendous Offer**

**FREE**: Set of drills from 1/16in. to 1in. or Set of two-way screwdrivers in plastic cases. With bargain pack consisting of:— One pair throat microphones, 50 assorted resistors, approx. 150 assorted screws, one dial pointer 2in. 2in. screened lead with sockets, one 5 Henry 200 m.a. choke, two electrolytic condensers, radio knobs, toggle switches, Octal valve bases, vibrators, one pair M.C. earphones, one waveband switch, four Co-ax. plugs, one box of assorted coils, cartridge files, three potentiometers, one WW multiplier, 24 assorted condensers, one Festoon lamp and holder, one coil PVC wiring-up wire.

All this for 35/-, p.p. 4/6. **A RADIO CHASSIS WITH OVER 200 USEFUL PARTS**, consisting of condensers, resistances, valve holders, chokes, switches, relays, coils, nuts and bolts, etc., 10/6, p.p. 4/6.

**100 ASSORTED RESISTANCES**, including W.W., 10/-, p.p. 1/9.

**50 ASSORTED CONDENSERS**, 10/-, p.p. 1/9.

**ONE 5 HENRY CHOKE**, 2 amp. Ideal for radio or TV smoothing, 5/6, p.p. 1/6.

**SIX ASSORTED POTENTIOMETERS**, 5/-, p.p. 1/6.

Open Saturday until one o'clock. Personal callers welcome.

182, KINGSLAND RD., SHOREDITCH, E.2. Tel.: SHO 6572. Sorry U.K. only.

**RECEIVERS & COMPONENTS**  
(Continued)

**TRANSISTORS.**—OC11/72/73. GT12. 15/- each; OC44/76/77/8 22/6 each; OC72, matched pairs, 30/-. Return of post service. V. W. WARD, 142, Raiton Rd., London, S.E.24.

**FIX IT YOURSELF!** Pre-assembled ready for instant fitting. Clip-on SE1, 30/-; 8EL 42/6. **FRINGE AREA MODELS** for high gain Double 5 Array, 72/6; Double 8 Array, 100/-. Fringe area super low-loss Coaxial, 1/3 yd. Standard low-loss, 71d. vtd. **NEW T.V. TUBES** 1-3 TEARS' GT. ANTENNE. Suitable 'Plug-in' replacement for Mullard, Mazda, etc. 14in. all types, £10.10.0; 17in. all types (except CRM), £12; 17in. CRM types, £13.10.0. S.A.E. for CRT and Aerial List. Satisfaction or money refunded within 10 days. All items carriage paid C.W.O.

**HASE SUPPLIES**

34, Prince St., Bristol (Dept. P.W.)

**FOR SALE**

**SPECIAL OFFER.**—Famous Pye Invicta 12in., 13 channel, Televisions (without tubes) valves, £2/15/-; otherwise complete. Each one with walnut cabinet, and Pye 13-channel turret. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23.

**BENDIX RECEIVERS, RA-10.** 4-band. Superhet. 150 kc/s-10 mc/s. Valves: 6SK7. RF. 6K8. F/C. two 6SK7 IF. 6R7 second det. 6C5 BFO. 6K6 OP. 6H6 diode. Built-in PU 24v. D.C. size 6 1/2in. x 15 1/2in. easily converted to mains as described on Page 453 of Sept., 1957. P.W.: £4 plus p.p. 10/- American Beacon Tx-Rx RT37/PPN-2. Brand new, composed of transmitter-receiver with 9 valves (5-3A5, 3-1S5, 1-1R5), built-in 2v. vibrator pack, spare vibrator, headset, connector leads and 10ft. collapsible aerial. Frequency 214/238 mc s. £3/15/-, plus p.p. 7/6. E.W.S. CO., 69, Church Rd., Moseley, Birmingham, 13.

**SATISFACTION ASSURED.**—12in. Televisions £9/10/-, 14in. £16, 17in. £19/10/-. Write for quotation, stating requirements. We guarantee satisfaction. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23.

**AMAZING VALUE.** Philco Shortwave Car Radio Converters, originally £10; fit to any existing car radio, and add six extra wavebands, 16.19-25-31-49 metre bands, also standard broadcast, 6/12 volts; compact under dash counting; chromium control panel with six press-buttons. Complete all fittings and instructions, easily fitted, 45/- post free. Each instrument brand new with Mullard valves. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23.

**EQUIPMENT & CABINETS BY STAMFORD**

Write for our NEW LISTS for HI-FI EQUIPMENT AND COMPLETE SYSTEMS TERMS: Cash, Credit or Hire Purchase.



GP57

Write for Catalogue of Cabinets and Enclosures.

**A. L. STAMFORD LTD.** (Dept. J.29), Showrooms: 84/86/88, Wy-mouth Terr., Hackney Road, London, E.2. No. 6 bus from Liverpool Street, book to Odeon, Hackney Road, and walk back two turnings.

**SAVE 30%.**—The Tape King makes possible the impossible: once more Agfa-Wolfen Tape, 1.800ft. L.P. on 7in. spools, would be 50/-, only 35/-; limited quantity; also Tape bargains in sizes from 3in. to 8 1/2in.; many second-hand recorders: all new makes, S.A.E. for list. Once again a few only of the famous E.M.I. Professional Tape Deck at a fractional cost. 7 1/2in. per sec. 7in. spool; same price as before, only 22 gns.; or terms, E. C. F. KINGSLEY & CO., 132, Tottenham Court Rd., London, W.1. (EUS 6500.)

**G.P.O. TELEPHONES,** latest modern desk type, Ref. 326C.B. complete with internal bells, dozens of uses as extension units, intercoms, etc.; list price £15, our price, few only, surplus to contract, brand new, 35/-, post 3/6. K.E.P. PRODUCTS LTD., Ashmead Rd., London, S.E.8.

**ASTOUNDING VALUE.**—9in. Televisions 45/-, 12in. Televisions 70/-, 14in. £9 10/-, 15in. £5/10/-, 17in. £14. Complete but not guaranteed working, as received in part exchange. TOMLINS, 127, Brockley Rise, Forest Hill, London, S.E.23. All famous makes available, carriage 7/6.

**100 BAYS** of, brand new adjustable steel Shelving, 72in. high x 34in. wide x 12in. deep; stove enamelled, dark green, sent unassembled; 6-shelf Bay, £3/15/-; sample delivered free; quantity discounts. N. C. BROWN, LTD., Eagle Steelworks, Heywood, Lancs. (Tel.: 69018.)



**INDEPENDENT 200/240 volt MAINS SUPPLY**

**AMERICAN DYNAMOTOR UNIT.** Input 12 volts, output 200/240 volts at 100 to 130 watts and 180 watts.



Runs **RADIOS, TELEVISIONS, MAINS LIGHTING, ELECTRIC DRILLS** and **THOUSANDS OF APPLIANCES.**

Runs anything 200/250 volts universal AC/DC.

Built for heavy continuous duty. Will last a lifetime. Brand new condition. Fully tested and ready for immediate use.

**SIMPLY PLUG IN.**

**COST AMERICAN GOVERNMENT £40 each.**

**OUR PRICE ONLY £4.**

Carriage, packing and insurance, 20/-, SEND S.A.E. FOR FULL DETAILS.

**Dept. D, SCIENTIFIC PRODUCTS**

Manor Works, Manor Drive, CLEVELAYS, BLACKPOOL, Lancs.

**RADIO**

**AT LAST VHF, FM/AM** for the family man. Astonishing De Luxe VHF/FM Radio offer. Merging of world famous Co., enables us to offer £24 DE LUXE VHF, FM/AM Radios for £15.10.0. Factory Fresh. Maker's Guarantee, extra thrilling quality. All features including Ferrite aerials. Our satisfaction guarantee or purchase price refunded. AC/DC 200/250v. Smaller radio with VHF, FM/AM, £13.10.0 originally £21, or Miniature Superhet two-wave model £8.10.0.

**TOMLIN ELECTRICAL,** 127, Brockley Rise, London, S.E.23.

**WANTED**

**ALL TYPES** of Valves wanted. PL81, ECL80, EY51, U25, PCF80, P230, U801, etc., etc. best cash price by return. **STAN WILLETT'S,** 43, Spon Lane, West Bromwich, Staffs. (Tel.: WES 2392.)

**A PROMPT CASH OFFER** for your surplus Brand New Valves, Speakers, Components, Test Instruments, etc. R.H.S., 155, Swan Arcade, Bradford, 1.

**URGENTLY REQUIRED,** new Radio, Television or Industrial Valves. Also old and obsolete types. Cash prices offered for any quantity. Write call or phone: MIT 6202, 201, Streattham Rd., Mitcham, Surrey.

**WANTED VALVES**

All types for prompt cash. Must be new State quantity.

**WILLIAM CARVIS LTD.** 103, North Street, Leeds, 7.

**SERVICE SHEETS**

**SERVICE SHEETS.**—Radio and TV, 2/6 ea. List 1/-, S.A.E. with enquiries, please. **GLOBE SUPPLIES,** BCM/Electrique, Monomark House, London, W.C.1.

**FAULTFINDER FILES (TV),** showing common faults that each receiver is prone to, and other useful servicing information. 2 - ea. List 9d., plus postage. **S. P. DISTRIBUTORS** 11, Old Bond St., London, W.1.

**SERVICE SHEETS**

**RADIO and Television** Over 100,000. S.A.E. for List, Large stock of obsolete Radio and Television Valves.

**JOHN GILBERT RADIO,** 20, Extension Shepherd's Bush Market, London, W.12 SHE 3052

**SERVICE SHEETS** for sale. TV 4/-, Radio 3/-; immediate delivery. S.A.E. with enquiries. Callers welcomed. **SULTAN RADIO,** 6, Mt. Ephraim Rd., Tunbridge Wells, Kent. (Phone: 22710.)

**SERVICE SHEETS,** Radio, T.V., 5,000 models. Lists 1/-, S.A.E. enquiries. **TELRAY,** 11, Maudland Bk., Preston.

**SERVICE SHEETS** for sale, all types, from 1/- each. Also Radio, Television Books. Lists free. 100 Television Service Sheets, covering 330 popular models, 18/6. **HAMILTON RADIO,** 237, Sedescombe Rd. N., Hastings.

**SERVICE SHEETS.**—We have the largest stock of Radio and TV Service Sheets in the country for sale at 4/- ea. and for hire. Why tolerate delay in obtaining Service Sheets when we will despatch by return? List 1/-. S.A.E. with enquiries, please. **S. P. DISTRIBUTORS,** 11, Old Bond St., London, W.1.

(Continued overleaf)

## PUBLIC APPOINTMENTS

**RADIO (METEOROLOGICAL) TECHNICIANS** required by the Meteorological Office. Qualifications: basic knowledge of radio and radar and experience in maintenance/operation of radar equipment including oscilloscopes. Successful applicants serve in United Kingdom and overseas. Commencing London salary £690 at age 25 or over rising annually to £820 subject to deductions for each year below age 25, provincial salary £40 to £50 lower. Overtime, night duty allowance, etc. Applications should be sent to Meteorological Office (M.O.10 R/M/T), Victory House, London, W.C.2.

**AIR MINISTRY REQUIRE EXAMINERS** (unestablished) for Aeronautical Inspection Service, Radio Division and Electrical and Instruments Division at R.A.F. Units at Aldergrove (Northern Ireland), Carlisle, Sealand, Henlow (Beds), Hartlebury (Worcestershire) and in the Gloucester and Wiltshire areas. Opportunities may arise for serving a tour of duties overseas. Quals.: C. and G. Intermediate Group certificates in telecommunication engineering or O.N.C. electrical or equiv. theoretical knowledge with experience in industry or Services. Commencing salary age 28 and over £720 to £850 to £850 (men). Prospects of promotion and establishment. Age up to 35 years. Application to Air Ministry (C.E.4(a)), Cornwall House, Stamford St., London, S.E.1, or any Ministry of Labour and National Service Office, quoting Borough Order No. 2030.

## EDUCATIONAL

**LEARN RADIO AND ELECTRONICS** the new practical way! Hosts of absorbing experiments carried out at home under expert guidance to teach you radio in a new, enjoyable and interesting way. Construction, servicing and fault finding on equipment made easy for the first time! No previous experience needed. No mathematics used. Free brochure from: Dept. PW11. RADIO-STRUCTOR, 46, Market Place, Reading, Berks.

**WIRELESS.** See the world as a Radio Officer in the Merchant Navy: short training period; low fees; scholarships, etc., available. Boarding and Day students. Stamp for prospectus. WIRELESS COLLEGE, Colwyn Bay.

**THERE IS A NATIONAL SHORTAGE** of Mercantile Radio Officers. Why not make Communications your career? You can be assured of a sea-going appointment after qualifying at the School of Marine Radio and Radar (A.S.T.), Hamble, Southampton. For details apply to the COMMANDANT.

**AT LAST**—at a reasonable cost—quality Hi-Fi in your home by building it yourself under our new system. Free brochure from: Dept. PW21. RADIO-STRUCTOR, 46, Market Place, Reading, Berks.

**EASY MATHEMATICS.**—Course 21/- for Radio/TV. Write: TUTORIALS, 200, Buchanan St., Glasgow, C.1.

## BOOKS &amp; PUBLICATIONS

**BOOKS** for C. and G. exams: Tels. Principles, A and B, 9/6; Tels. (Principles), 1 and 2, 10/6; Maths for Tels., 1, 7/-; Maths for Tels., 2, 5/-; all post free. RIDDFORD, 384, Tilehurst Rd., Reading.

## MISCELLANEOUS

**MAKING YOUR OWN TELESCOPES,** Enlargers, Projectors, Viewers, Microscopes, Episcopes, etc., then our booklets "How to Use Ex-Gov. Lenses and Prisms," Nos. 1 and 2 at 2/6 ea., will show you easily and quickly how to achieve the finest possible results at lowest possible cost. The most comprehensive lists of optical and scientific equipment in the British Isles is free for s.a.e. H. W. ENGLISH, Rayleigh Rd., Hutton, Brentwood, Essex.

**LOUDSPEAKERS,** Electric Clocks and Shavers repaired promptly. MODEL LOUDSPEAKER SERVICE, Shipton on Cherwell, Oxford.

**FREE LANCE AGENTS AND REPS.** calling on the Electrical and Television Trade required to sell specialised sets of equipment. Minimum commission £125, max. £250 per sale. Box No. 22, c/o PRACTICAL WIRELESS.

## SITUATIONS VACANT



# The Royal Air Force

## PILOTS, NAVIGATORS AND AIR ELECTRONICS OFFICERS COMMISSIONS IN THE GENERAL DUTIES BRANCH

Vacancies now exist for fit young men of character and good education and who are capable of taking responsibility, to train as pilots, navigators or air electronics officers in the general duties branch of the Royal Air Force.

### Methods of Entry

**University Entry**—University graduates may enter on permanent or four-year short-service commissions. Permanent commissions carry an ante-date. University students may be accepted subject to graduation. Age limits: 19 to 24. (26 for short-service commissions.)

**Direct Commissions**—The direct commission scheme offers the choice of a permanent career leading to a pension, or a twelve-year commission with the option of leaving after eight years. Age limits: 17½ to 25.

**Short-Service Commissions**—The short-service commission is for

five years and there are opportunities for transfer to either form of direct commission. Age limits: 17½ to 21.

**Pay and Gratuities**—Pay is high and terminal gratuities are generous. For example, a Flight Lieutenant of 25 can earn, with full allowances, nearly £1,700 a year. The tax-free gratuity paid at the end of a twelve-year commission is £4,000.

Write for further details, stating age and education, and the method of entry in which you are interested to the Air Ministry, (PW562a), Adastral House, London, W.C.1.



## A Career in Telecommunications with good pay and all found, as a WIRELESS or TELEPRINTER OPERATOR in the Royal Air Force

Vacancies for suitable men now. Train for a responsible job in the vital R.A.F. communications system. Good chances of promotion, full allowances; month's leave a year; chance to travel, and all the wider interests of Service life. Call or write for details to: Central Recruiting Office, (PW535), Victory House, Kingsway, W.C.2.

SITUATIONS VACANT

(Continued)

PYE

Telecommunications of Cambridge Research Department require

2 DEVELOPMENT ENGINEERS

with experience of Domestic Receiver Design with particular reference to Car Radio. Applicants must have had some laboratory experience and possess O.N.C. or equivalent technical qualifications.

The Company is in the forefront of Research and Development and offers excellent progressive opportunities for men of the right calibre.

Residence in Cambridge combines the amenities of a flourishing University City (good shopping, ample recreational facilities, etc.) with easy access to the pleasant surrounding countryside.

Apply in writing giving details of age, experience and salary required to:—

The Personnel Manager PYE TELECOMMUNICATIONS LTD.

Ditton Works, Newmarket Road, Cambridge

A.M.I. Mech. E., A.M. Brit. I.R.E., City and Guilds, G.C.E., etc., bring high pay and security. No pass—no fee terms. Over 95% success-rate. For details of exams and courses in all branches of Engineering, Building, Electronics, etc., write for 148-page handbook, free. B.I.E.T. (Dept. 242B), London, W.8.

THERE IS A NATIONAL SHORTAGE of Mercantile Radio Officers. Why not make Communications your career? You can be assured of a sea-going appointment after qualifying at the School of Marine Radio and Radar (A.S.T.), Hamble, Southampton. For details apply to the COMMANDANT.

CITY AND GUILDS (Electrical, etc.), on "No pass—no fee" terms. Over 95% successes. For details of Electrical Engineering, Applied Electronics, Automation, etc., send for our 148-page handbook, free and post free. B.I.E.T. (Dept. 242A), 29, Wright's Lane, London, W.8.

SOUND RECORDING

TAPE/DISC/TAPE TRANSFER for trade and private. Tape sales. For quality work use Unimixers. Sound News, 10, Clifford St., London, W.1.

STAMP COLLECTIONS

STAMP COLLECTIONS or accumulations, valued and purchased at highest prices. Send to JOHN LISTER LTD., 186/8, Shaftesbury Ave., London, W.C.2.

TRANSISTORS

RED SPOT or YELLOW/GREEN, 5/6 each, 3 for 15/-. WHITE SPOT, 6/6. RED/YELLOW, 14/-. VARI-LOOPSTICK COIL. M.W. with Transistor Circuit, 4/6. CRYSTAL SET COILS. M. & L. with Circuit, 2/6. DRR2 COIL. M. & L. with Transistor and Valve Circuits, 4/- each. Crystal Diodes, 1/- each. G.E.X.34, 4/- each. Reaction Condensers, .0003 or .0005, 4/-. Miniature Electrolytics, 15 volt in 2, 5, 8, 25, 50 or 100 mfd., 3/- each. NEON MAINS TESTERS, 3/9 each. All sent post free in U.K. by

PETHERICKS RADIO SUPPLIES, 22, High Street, BIDEFORD, N. Devon.

MODEL RADIO-CONTROL

New, revised and enlarged edition. Dealing with planes, boats and autos. Covers coders, transmitting and receiving systems, decoders, power control circuits, servomotors. latest miniaturized and transistor circuits. 192 pages.

By E. L. Safford, Jnr.

21/- Postage 1/-

RAPID RADIO REPAIR, by G. W. Heath, 23/- Postage 9d.

RADIO CIRCUITS. A step by step survey, by W. E. Miller, revised by E. A. W. Spreadbury, 15/- Postage 1/-

TELEVISION ENGINEER'S POCKET BOOK, by J. P. Hawker, 12/6. Postage 6d.

MULLARD MAINTENANCE MANUAL, 10/6. Postage 1/-

BRITISH TRANSISTOR MANUAL, by E. N. Bradley, 12/6. Postage 9d.

RADIO VALVE DATA, by "WW," 6th Ed. 5/- Postage 9d.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books

19-23 PRAD STREET, LONDON, W.2.

Complete catalogue 6d.

Phone : PADdington 4185.

Open 6 days 9-6 p.m.

VALVES

SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS 1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DK92, DL92, DL94, any 4 for 25 - DAF96, DF96, DK96, DL96 ... .. 4 for 32.6 - 6K7G, 6K8G, 6Q7G, 6V6G, 6X5G or 5Y3G ... .. 5 for 27 -

Table listing various vacuum tube types and their prices, organized in columns.

READERS RADIO

24, COLBERG PLACE, STAMFORD HILL, LONDON, N.16.

STA. 4587

Post 6d. per valve extra. Any Parcel insured Against Damage in Transit 6d. extra. Any C.O.D. Parcel 2/6 extra.



# WEYRAD

## COILS AND TRANSFORMERS FOR A 2-WAVE TRANSISTOR SUPERHET WITH PRINTED CIRCUIT AND FERRITE ROD AERIAL

LONG AND MEDIUM WAVE AERIAL—RA2W

On 6in. rod, 7/16in. diameter, flying lead connections, 208 pF tuning ... .. 12/6

OSCILLATOR COIL—P50/1AC

Medium wave in screening can. For 176 pF tuning condenser ... .. 5/4

1st AND 2nd I.F. TRANSFORMERS—P50/2CC

470 Kc/s operation with 250 pF tuning in cans. 1 1/16in. diameter by 3/4in. high ... .. 5/7

3rd I.F. TRANSFORMER—P50/3CC


Last stage transformer to feed diode detector. Size as P50/2 ... .. 6/-

DRIVER TRANSFORMER—LFDT2

Upright mounting with six connecting tags—1 1/16 in. x 5/8 in. x 1 1/4 in. ... .. 9/6

PRINTED CIRCUIT—PCA1

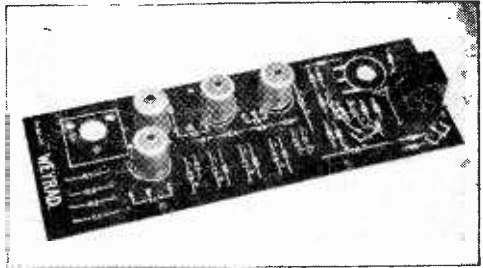Size 2 1/4 in. x 8 1/4 in. Ready drilled and printed with component positions ... .. 9/6



THESE COMPONENTS ARE APPROVED BY TRANSISTOR MAKERS AND PERFORMANCE IS GUARANTEED.

Constructor's Booklet with full details, 2/-.

**WEYMOUTH RADIO MANUFACTURING CO., LTD.**  
CRESCENT STREET, WEYMOUTH, DORSET

Now . . . in your own home, **LEARN**

# RADIO - TELEVISION - ELECTRONICS

**NO PREVIOUS TECHNICAL EXPERIENCE NEEDED!**  
**PRACTICAL EQUIPMENT (INCLUDING TOOLS) GIVES YOU A REAL LABORATORY TRAINING**

*"The trained electronics engineer has a great career ahead of him."*

Valuable **FREE** Book shows how E.M.I. Institutes School of Electronics can train you for today's wonderful opportunities.

Radio, Television and Electronics provide an exciting field for the trained man—high pay, a prosperous future—or if you prefer it—*independence in your own business.* If you are trained at home by E.M.I. Institutes you will be in the hands of *specialists* who know the quickest way to prepare you for one of the fine jobs open to trained electronics-men. Whether you are a beginner or an advanced student with an examination in mind, E.M.I. Institutes School of Electronics has a Course exactly suited to your needs—with or without practical equipment—from electricity and magnetism to automation techniques.

Practical Radio  
Radio & Television Servicing  
Practical Electronics  
Electronics Engineering Automation  
Basic Practical and Theoretic Courses for beginners in Radio, T.V., Electronics, Etc.  
A.M.Brit.I.R.E., City & Guilds Radio Amateurs' Exam.  
R.T.E.B. Certificate  
P.M.G. Certificate  
**"NO PASS—NO FEE"**

**We Definitely Guarantee "NO PASS—NO FEE"**

Full details of the Courses, Practical Equipment, convenient monthly payments, our Employment and Advisory Depts., and much other helpful information is given in our Guide to Careers in Electronics. Write for your copy today. There is no obligation and the book will be sent to you quite free of charge.

**FREE BOOK - POST NOW!**

Please send me a free copy of your Guide to Careers in Electronics.

NAME .....

ADDRESS .....

Subject or Exam .....



**E.M.I. INSTITUTES**

# SCHOOL OF ELECTRONICS

The Specialist Electronics Division of the British Institute of Engineering Technology.

(DEPT. SE/21), COLLEGE HOUSE, 29-31, WRIGHT'S LANE, KENSINGTON, LONDON, W.8.

# R.S.C. MANCHESTER BRADFORD & LEEDS (Leeds) LTD.

Terms C.A.O. or C.O.D. No C.O.D. under £1. Post 1/9 under £2. 2/9 under £5.

## EX. GOVT. MAINS TRANSFORMERS

|   |       |
|---|-------|
| Primaries 200-250 v. 50 c.p.s. A.C.                       |       |
| 150 v. 60 m.a., 6.3 v. 2 a.                               | 10 11 |
| 175-0-275 v. 120 m.a., 6.3 v. 7 a. 5 v. 3 a.              | 21 9  |
| 300-0-300 v. 60 m.a., 6.3 v. 2 a.                         | 11 9  |
| 300-0-300 v. 100 m.a., 6.3 v. 2 a. 5 v. 2 a.              | 18 9  |
| 350-0-350 v. 160 m.a., 6.3 v. 5 a. 5 v. 3 a.              | 27 9  |
| 450-0-450 v. 250 m.a., 6.3 v. 3 a., 6.3 v. 1 a. 5 v. 6 a. | 49 9  |

## SELENIUM RECTIFIERS

|               |      |                 |
|---------------|------|-----------------|
| 15 v. BRIDGE  |      | H.T. Types H.W. |
| 6 12 v. 1 a.  | 9 11 | 150 v. 40 m.a.  |
| 6 12 v. 2 a.  | 6 11 | 250 v. 50 m.a.  |
| 6 12 v. 3 a.  | 9 9  | 250 v. 60 m.a.  |
| 6 12 v. 4 a.  | 12 3 | 250 v. 80 m.a.  |
| 6 12 v. 6 a.  | 15 3 | 250 v. 250 m.a. |
| 6 12 v. 10 a. | 25 9 |                 |
| 6 12 v. 15 a. | 35 9 |                 |
| 24 v. 2 a.    | 14 9 |                 |

Mail Orders to 29-31 Moorfield Rd., Leeds, 12. Callers to 5 and 7 County (Mecca) Arcade, Briggate, Leeds 1. 8-10 Brown St. (Market St.), Manchester 2, or 56, Morley Street, Bradford.

## SPECIAL OFFER OF BRAND NEW EX. GOVT. SELENIUM RECTIFIERS TELEVISION TYPE

250 v. 200 m.a. 6/9  
**HEAVY DUTY TYPE**  
 24 v. 15 amp. F.W. Bridge, with large square aluminium coolers—27/9 ea.

# R.S.C. BATTERY CHARGING EQUIPMENT

## ASSEMBLED CHARGERS

|                       |      |
|-----------------------|------|
| 6 v. 1 amp.           | 19 9 |
| 6 v. or 12 v. 1 amp.  | 27 9 |
| 6 v. 2 amps.          | 29 9 |
| 6 v. or 12 v. 2 amps. | 38 9 |
| 6 v. or 12 v. 4 amps. | 56 9 |

Above ready for use. With mains and output leads. Carr. 3/6.



## Assembled 6 v. or 12 v. 4 amps.

Fitted Ammeter and variable charge rate selector. Also selector plug for 6 v. or 12 v. charging. Louvered steel case with stove blue hammer finish. Fused 6/9 and ready for use with Carr. 5/- mains and output leads. Terms: Deposit 13/11 and 5 monthly payments 13/11.

## ASSEMBLED CHARGER

6 v. or 12 v. 2 amps.  
 Fitted Ammeter and selector plug for 6 v. or 12 v. Louvered metal case, finished attractive hammer blue. Ready for use. With mains and output leads. Double Fused. Only Carr. 3/9. **49/9**

## All for A.C. Mains 200-250 v., 50 cps

Guaranteed 12 months KITS  
**BATTERY CHARGER KITS**  
 Consisting of Mains Transformer, F.W. Bridge, Metal Rectifier, well ventilated steel case. Fuses. Fuse-holders. Crommets, Panels and circuit. Carr. 3/6 extra.  
 6 v. or 12 v. 1 amp. 22 9  
 As above, with Ammeter... 32 9  
 6 v. 2 amps. 25 9  
 6 v. or 12 v. 2 amps. 31 6  
 6 v. or 12 v. 2 amps. including Ammeter... 49 9  
 6 v. or 12 v. 4 amps. 53 9  
 6 v. or 12 v. 4 amps. with Ammeter and variable charge rate selector. 59 9  
**CHARGER AMMETERS.**  
 0-5 a., 0-5 a., 0-1 a., 0-7 a., 0-25 a., 0-50 a., 8/9.

## HEAVY DUTY CHARGER KIT.

6/12 v. 6 amps. variable output. Consisting of Mains Transformer 0-200-200-250 v.; F.W. (Bridge) Selenium Rectifier; Ammeter; Multi Position Switch with Knob; Panels, Plugs, Fuses, Fuseholder, and circuit. 59-9. Carr. 4/6.

**EX-GOVT. CASES.** Size 14-10-8 in. high. Well ventilated, black crackle finished, undrilled cover. **IDEAL FOR BATTERY CHARGER OR INSTRUMENT CASES.** OR COVER COULD BE USED FOR AMPLIFIER. Only 9/9, plus 2/6 postage. 2 v. 16 a.h. **EX-GOVT. ACCUMULATORS.** New, boxed. Only 5/6 each, 3 for 15/-, post 2/6. 6 for 27/6, carr. 3/6.

**PHILCO V.H.F. F.M. RADIO TUNERS** with self-contained Power Pack. For 110-250 v. A.C. mains. Inc. 6 valves (Magic eye tuning indicator). Housed in beautiful polished walnut veneered cabinet. List price £20. Limited stocks, brand new, 12/9, carr. 7/6, or on H.P. terms. Deposit 2/6 and 12 monthly of 2/6.

**D.C. SUPPLY KIT.** 12 v. 1 a. consisting of partially drilled metal case, mains trans., F.W. Bridge Rectifier, 2 fuseholders and fuses. Change Direction switch, variable Speed regulator and circuit. For 200-250 v. A.C. mains. Suitable Electric Trains, etc. Limited number available at 29/9.

**RE-ENTRANT SPEAKERS.** Tannoy, 8 watt, 7.5 ohms. Only 19/6 each.

**LITTLE STAAR BATTERY-OPERATED RECORD-PLAYING UNITS COMPLETE WITH PICK-UP.** To take 45 r.p.m. records. As used by leading manufacturers in Transistorised Record Players. Brand new, £3-19/9 only.  
**STANDARD JACK PLUGS.** With 4ft. screened lead, 1 1/11 cu. **STANDARD MOULDED JACK SOCKETS,** 2/9 ea.  
**5 CORED FLEX.** Rubber insulated. 14.36, 1/3 yd., 50-50 v. **TRANSISTORS.** Audio Type, 6 6; R.F., 12/6; Power type, 2 watts. V15/10P, 16 9. Mullard OCT1, 10/-, OCT2, 16 9; XB102, 10/- Most types at bargain prices. **0A81 Diode,** 3/9.  
**REPAIRING INSTRUTIONAL ENVELOPES AND PARTS IN STOCK.** Parts for 3 Dee 3 Transistor Radio, £3-6/6. Hi-wayman Portable, £7-15/-, Mini-Seven 7 Transistor Pocket Portable, £9-19/6.  
**ARDENTE DEAF AID EARPIECES.** Brand new complete with ear insert and lead. Only 15/6 each.  
**TURNOVER STEREO MONAURAL PICK-UP HEADS,** by Acos. Suitable for normal 78, 45, or 33 1/3 r.p.m. records or for stereo type. Sapphire Stylus. Will fit Garrard B.S.R., Collaro and Staar Galaxy Record Changers. Only 49/9.

# Fully guaranteed and tested before despatch VALVES Postage 6d up to 3 valves, 9d 4 to 6. Above six subject to our usual terms.

|            |            |             |             |             |              |             |            |
|------------|------------|-------------|-------------|-------------|--------------|-------------|------------|
| 1AB6 9 9   | 6D2 6 9    | 7C6 7 9     | 65ME 8 9    | EB91 5 9    | FW 500 9 9   | PEN383 8 9  | UF42 10 6  |
| 1AH5 9 9   | 6D6 5 9    | 7S7 7 9     | 11TH 8 9    | EB3C 6 9    | G220 9 9     | PL33 9 9    | UB41 11 9  |
| 1AJ4 6 9   | 6F1 11 9   | 8D2 3 3     | 171DDP 8 9  | EB34 9 9    | G232 11 9    | PL38 16 9   | UC41 9 9   |
| 1CIEM 6 9  | 6F12 6 9   | 8D3 6 9     | 311SU 8 9   | EB50 11 9   | G233 10 9    | PL81 13 9   | UF80 9 6   |
| 1C8 9 9    | 6F14 11 9  | 9D1 7 9     | 4419 7 9    | EB78 9 9    | G234 13 9    | PL82 8 9    | UC85 10 6  |
| 1FD1 6 9   | 6F15 11 9  | 9D2 3 9     | 451PT 7 9   | EBF89 9 6   | G237 9 9     | PL83 9 9    | UC86 10 9  |
| 1FD9 6 9   | 6H6 2 3    | 9C8 6 9     | AC6PEN 5 9  | ECC35 7 9   | HL41DD11 9 9 | PX31 11 9   | UC82 14 9  |
| 1F1 6 9    | 6J5 4 9    | 10E1 13 9   | B36 8 9     | ECC81 7 9   | IW1350 9 9   | PY80 7 9    | UF42 8 9   |
| 1F2 6 9    | 6J7G 4 6   | 10F1 17 9   | B35 8 9     | ECC82 7 9   | IW4500 8 9   | DY81 9 9    | UF89 9 9   |
| 1F3 6 9    | 6L6 4 6    | 10P1D3 7 9  | B152 8 9    | ECC83 9 9   | KT32 8 9     | PY82 8 9    | UL41 9 9   |
| 1F4 5 11   | 6L7G 5 9   | 10LD12 15 9 | B309 8 9    | ECC84 9 9   | KT33 9 9     | PY83 8 9    | UL46 14 9  |
| 1P1 6 9    | 6K7G 4 9   | 10LD14 15 9 | B419 8 9    | ECC85 9 6   | KT36 9 9     | PZ20 16 9   | UL84 9 9   |
| 1P10 6 9   | 6K7MET 5 9 | 10P13 9 9   | B329 8 9    | ECC91 4 9   | KT44 14 9    | R2 9 9      | U03 8 9    |
| 1P11 8 9   | 6K8G 8 9   | 10P14 9 9   | B339 8 9    | ECCF80 12 9 | KT45 9 9     | R3 9 9      | U04 9 9    |
| 1R5 7 9    | 6L1 9 9    | 10P18 9 9   | B719 8 9    | ECCF82 12 9 | KT61 11 9    | R12 11 9    | UY41 9 9   |
| 1S5 7 9    | 6L3 9 9    | 12A6 8 9    | D1 8 9      | ECCF81 8 9  | KT63 4 9     | SD61 1 9    | UY45 7 9   |
| 1T4 5 11   | 6L3D 9 9   | 12A7 7 9    | DAF91 5 11  | ECH181 10 9 | KTZ1 4 9     | SP19 9 9    | UC85 10 6  |
| 1A4 6 9    | 6LD12 8 9  | 12A7T 7 9   | DAF91 5 11  | EC182 11 9  | LA3 4 9      | SP42 11 9   | VF1322 3 9 |
| 1C4 6 9    | 6LD20 8 9  | 12AUG 7 9   | DAF96 9 9   | EF39 5 9    | LN152 9 9    | SP61 2 9    | VS110 3 9  |
| 1C5 7 9    | 6L12 8 9   | 12AUG 7 9   | DF91 7 9    | EF41 8 11   | LN309 16 9   | SP64 8 9    | VU120A 3 9 |
| 1V4 8 9    | 6L18 11 9  | 12AX7 8 9   | DF92 8 9    | EF42 9 9    | MH4 5 9      | SU61 11 9   | W17 5 11   |
| 1DL 15 9   | 6L19 9 9   | 12B7GT 8 9  | DF93 9 9    | EF50 4 9    | MU12 16 9    | TD1 16 9    | W147 5 11  |
| 1U4G 9 9   | 6L9G 8 11  | 12SFA 3 9   | DG3 2 3     | EF54 5 11   | MU14 9 9     | TR1 20 9    | W150 9 9   |
| 1Y3G 7 9   | 6L19 11 9  | 13VPA 3 9   | D77 5 11    | EF80 7 9    | N17 7 3      | L22 7 9     | W179 9 9   |
| 1Z4G 9 9   | 6M1 6 9    | 15A6 10 9   | D152 8 9    | EF85 7 3    | N19 9 9      | U24 7 9     | W279 9 9   |
| 1AB8 12 9  | 6N8 8 9    | 16A5 9 9    | DD6 11 9    | EF86 16 9   | N37 18 9     | U25 13 9    | W727 9 9   |
| 1AC7 5 9   | 6P25 11 9  | 16A9 7 9    | DD41 8 9    | EF89 9 9    | N77 4 9      | U25 13 9    | WD142 9 9  |
| 1AG6G 11 9 | 6P28 7 9   | 17Z3 9 9    | DH68 6 9    | EF91 9 9    | N82 9 9      | U31 9 9     | WD65 9 9   |
| 1AK8 8 9   | 6Q7G 9 9   | 19X3 9 9    | DH77 11 9   | EF93 9 9    | N144 4 9     | U35 9 9     | WD709 9 9  |
| 1AK9 8 9   | 6S7G 6 9   | 19Y3 9 9    | DH109 10 6  | EK90 9 9    | N148 7 9     | U43 11 9    | X17 9 9    |
| 1AL5 5 9   | 6SK7 6 9   | 20D1 14 9   | DH142 8 9   | EL32 4 9    | N152 13 9    | U46 9 9     | X142 9 9   |
| 1AM5 4 9   | 6SL7GT 7 9 | 20F2 8 9    | DH147 6 9   | EL33 11 9   | N154 9 9     | U50 8 9     | X279 9 9   |
| 1AM6 6 9   | 6SN7GT 7 3 | 20L1 9 9    | DH150 8 9   | EL34 16 9   | N329 9 9     | U52 6 9     | Y63 5 9    |
| 1AC6 7 9   | 6T4CT 12 9 | 20P1 12 9   | DH119 9 9   | EL41 15 9   | N709 9 9     | U74 10 9    | Z63 8 9    |
| 1AC8 7 9   | 6U5G 6 9   | 21A6 13 9   | DK91 7 9    | EL41 10 9   | N727 9 9     | U78 9 9     | Z63 8 9    |
| 1AT6 7 9   | 6U8 8 9    | 25L6 8 9    | DK96 9 9    | EL84 9 9    | OM1 6 9      | U99 9 9     | Z77 7 6    |
| 6B8 3 11   | 6V4 8 9    | 30L1 8 9    | DL92 7 3    | EL90 9 9    | P61 2 9      | U112 9 9    | Z142 9 9   |
| 6BE6 9 9   | 8V6CT 7 9  | 30P16 9 9   | DL93 7 9    | EL91 9 9    | PCC84 9 9    | U151 11 9   | Z145 9 9   |
| 6BG6 16 9  | 6V8G 6 9   | 35Z4 6 9    | DL94 8 9    | EA19 4 9    | PCF80 12 3   | U152 9 9    | Z150 9 9   |
| 6BE 9 9    | 6HML 6 9   | 41MHL 6 9   | DL96 9 9    | EX1 11 9    | PCF82 9 9    | U153 9 9    | Z152 5 9   |
| 6BX6 6 6   | 8X4 6 9    | 53KU 10 9   | EA50 1 9    | EX86 13 9   | PCL82 12 6   | U154 9 9    | Z159 5 9   |
| 6BY5 9 9   | 6X5 5 11   | 54KU 11 9   | EABCB80 9 9 | EZ36 9 9    | PC183 16 9   | U319 9 9    | Z719 5 9   |
| 6BY7 7 9   | 7AN7 8 9   | 62DDT 8 9   | EAF42 8 9   | EZ80 8 9    | PC184 8 9    | U381 9 9    | Z729 16 9  |
| 6C9 11 9   | 7B7 8 9    | 82VP 7 9    | EB34 2 3    | EZ81 8 11   | PEN45 7 9    | U403 9 9    | ZD17 9 9   |
| 6D1 1 9    | 7C5 7 9    | 93ME 6 9    | EB41 7 6    | EZ90 6 9    | PEN46 6 9    | U4BC80 10 6 | ZD152 5 9  |

# Let **I.C.S.** train YOU!



**COURSES ON:—**

- RADIO and TELEVISION
- SERVICING · ELECTRONICS

**EXAMINATION COURSES FOR:—**


- C. & G. Radio Servicing Certificate (R.T.E.B.)
  - C. & G. Radio Amateurs' Exam. (Amateurs' Transmitting Licence)
  - British Institution of Radio Engrs., etc.
- Whether you plan to have your own business, to become an electronics engineer or to take up a career in industry, an I.C.S. Course will help you to success. You learn at home in your own time, under expert tuition. Moderate fees include all books.

**LEARN - AS - YOU - BUILD**

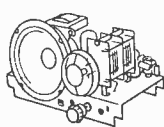
**Practical Radio Course**

- A basic course in radio, electronic and electrical theory backed by thorough practical training. You build a 4-valve T.R.F. and a 5-valve superhet radio receiver, signal generator and multi-tester.

Other Learn-as-you-build radio courses are available



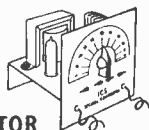**MULTI-TESTER**  
(Sensitivity 1,000 ohms per volt)



**5-VALVE SUPERHET RECEIVER**

**RF/AF SIGNAL GENERATOR**

**Post this Coupon TODAY!** for FREE book on careers in Radio, etc., and full details of I.C.S. Courses.

**INTERNATIONAL CORRESPONDENCE SCHOOLS**

(Dept. 171), Intertext House, Parkgate Road, London, S.W.11.

Name..... Age.....  
(Block Letters please)

Address .....

Occupation..... 12-50

**INTERNATIONAL CORRESPONDENCE SCHOOLS**

Get these **FREE** CIRCUITS & WIRING DIAGRAMS

T.R.F. Circuits  
Battery Circuits  
Portable Circuits  
S'het Circuits  
Mains Circuits  
Filter Circuits  
F.M. Tuner

T.V. Converter Circuits, etc.  
etc.

Send Postage 1/- (stamps)

OSMOR COILS are regularly used and recommended by designers writing in "Practical Wireless," "Wireless World" and "Radio Constructor." Why not follow the experts?

- "Q Coils" All ranges
- Potted Coils
- F.M. COILS
- TAPE COILS
- ROD AERIALS
- Speaker Cross-over Coils
- Coils and I.F.s for Transistor Circuits
- SUB-MINIATURE COILS
- Midget I.F. Trans. With ferrite cores



418 Brighton Road, South Croydon.

Telephone: CRO 5148/9

**G2AK: This Month's Bargains**

**VARIABLE CONDENSERS**

All Brass with Ceramic End Plates and Ball Race Bearings. 50 pf., 5/9, 100 pf., 6/6; 160 pf., 7/6; 250 pf., 8/6; and 300 pf., 9/6. P. & P. 1/6. Designed for the S.W. constructor.

**REPANCO MINIATURE COMPONENTS**  
Full Range in Stock.

**VOLTMETERS.** Dual range 0-5 V. and 0-100 V. M.C. 1,000 o.p.v. Ranges easily extended. With test prods and leads. Complete in solid leather carrying case, 6 1/2 in. x 5 in. x 2 1/2 in. **A GIFT** at 25/-, post free.

**HEADPHONES H.R. TYPE.** 4,000 ohms., very sensitive. **ONLY** 12/6 pr. P. & P. 1/6. C.L.R. Type (low res.), 8/6. P. & P. 1/6.

**ABSORPTION WAVEMETERS.** 3.00 to 35.00 Mc/s. in 3 switched bands, marked on scale. Complete with indicator bulb. **A MUST** for any Ham shack. **ONLY** 17/6, post free.

**MINIATURE ROTARY CONVERTERS**

12 v. D.C. Miniature Rotary Converters. Size only 4 1/2 in. x 2 1/2 in. overall. Output 360 v., 30 mA. cont. rating, 310 v. 70 mA intermittent. **ONLY** 12/6 each or 22/- for two. P. & P. 2/-.

**Rotary Converters.** 6 v. input, 250 v., 125 mA. output. **ONLY** 17/6, P. & P. 3/-.


**CHAS. H. YOUNG LTD.**

THE COMPONENT SPECIALISTS

Dept. "P," 110, Dale End, Birmingham 4. (CEN 1635)

(No C.O.D. under £1 please) (By return Service)

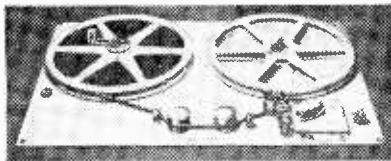Build your own  
**TAPE RECORDER**  
 "ASPDEN"  
 Tape Deck and Amplifier Kits



**TAPE DECKS.** 2-speed, twin track, easy to assemble kits with finest motor. Ferroxcube heads and full instructions.

Model 582 for 5in. spools, kit £8.5.0.

Model 782 for 7in. spools, kit £9.5.0.

Either model assembled and tested, 30/- extra.

**AMPLIFIER kit,** 2 $\frac{1}{2}$  watt, record/replay, 2 recording positions, neon indicator, etc., £5.18.0. Power Pack kit for above. £2.18.6 (both without valves). Carr. and packing extra.

Mr. R. White of Omagh, N. Ireland, writes:

"The performance of the recorder is very good, and I recommend it to all those who wish to get first class performance at approx. half the cost."

Send STAMP for full particulars to:—

**W. S. ASPDEN** Stanley Works, Cleveon Road, Blackpool, Lancs.

## REPANCO

### HIGH GAIN TRANSISTOR COMPONENT

**Ferrite Slab Aerial Type FS3.** Medium Wave only. With fixing grommets. Size 3in. x 7in. x 5/32in., 7/6.

**Long Wave Loading Coil for the FS3 Type XLI., 3/6.**

**Oscillator Coil Type X08** for 176 pF gang. Ferrite core. Size 2in. sq. x 11/16in., 5/-.

**Oscillator Coil Type X015** for 365 pF gang. Ferrite core. Size 2in. sq. x 11/16in., 5/-.

**I.F. Transformer Type XT6.** Suitable for 1st and 2nd I.F. 455 Kc/s. Size 2in. sq. x 11/16in. 10/-.

**I.F. Transformer Type XT7.** Designed for 3rd I.F.T. or detector I.F.T. 455 Kc/s. Size as XT6, 10/-.

**Push Pull Interstage Transformer Type TT9.** Ratio 1 : 1 C.T. Radiometal Core. Size 2in. x 2in. x 13/32in., 12/6.

**Push Pull Output Transformer Type TT10.** Ratio 8 : 1 C.T. Matched to 3 ohm speaker. Size as TT9, 12/6.

Practical and Theoretical circuits enclosed with each Repanco Transistor Component.

#### REPANCO EASY-TO-BUILD RECEIVERS

**Mini-7.** 7 Transistor pocket receiver. Size 5 1/2in. x 3 1/2in. x 1 1/16in. Long and medium wave. Envelope, 1/6.

**Major-7.** New Portable 7 transistor receiver. 9in. x 7in. x 4in. Long and medium wave. Envelope, 1/6.

**Car Radio Receiver.** 7 transistors. Long and medium wave. 2 watt output. R.F. stage. A.G.C. and auxiliary A.G.C. circuits. 12 volt or 6 volt. Envelope, 2/-.

Mail Order and Trade:  
**RADIO EXPERIMENTAL PRODUCTS, LTD.**  
 33 Much Park St.  
 COVENTRY  
 Tel.: 62572

Wholesale Enquiries and Export:  
**REPANCO, LTD.**  
 O'Brien's Buildings,  
 203-269 Foleshill Rd.,  
 COVENTRY  
 Tel.: 40594

### COMMUNICATIONS RECEIVER R1155

The famous Bomber Command receiver known the world over to be supreme in its class. Covers 5 wave ranges 18.5 to 7.5 Mc/s, 7.5 to 3 Mc/s, 1.500 to 800 Kc/s, 500 to 200 Kc/s, and 200 to 75 Kc/s, and is easily and simply adapted for normal mains use. Full details being supplied. All sets thoroughly tested and in perfect working order before dispatch, and on demonstration to callers. Fitted latest type super slow-motion tuning assembly. Have had some use but in excellent condition. ONLY £7 19/6.

**A.C. MAINS POWER PACK OUTPUT STAGE,** in black crackle case to match, enabling it to be operated immediately, by just plugging in, without any modification. With built-in 9in. P.M. speaker. £5 10/-, or de-luxe with 6in. speaker. £6 10/-.

**DUCT-10-IP PURCHASING RECEIVER AND POWER PACK TOGETHER.** Send S.A.E. for illustrated leaflet, or 13 for 14-page booklet which gives technical information, circuits, etc., and is supplied free with each receiver. Add carriage 10 6 for Receiver, 5- for Power Unit.

**RECEIVER R107.** A further purchase since our "sell out" last year. 9 valves, 3 wavebands, covering 1.2-17.0 Mc/s (18-230 metres), incorporating built-in speaker and power packs for 100-250 volts A.C. and 12 volts D.C. Size 24in. x 13in. x 17in. Complete, ready to switch on, thoroughly tested and checked before dispatch. IN NEW CONDITION. ONLY £13.10 (carriage 20/-).

**RCA 488 RECEIVERS.** Reconditioned and in perfect working order. "LF" Model, covers 75-140 Kc/s and 1.2-30 Mc/s. ONLY £50. "D" Model, covers 300 Kc/s-31 Mc/s. ONLY £55 (carriage, etc.), 25/-.

**RCA 9in. P.M. SPEAKER** in heavy black crackled metal case, designed for use with above receiver, or can be used as normal 3 ohms extension. Size 11 1/2in. x 10in. x 6in. NEW IN MAKER'S CARTONS. ONLY 45/- (post 3 6).

**"Q FIVER" COMMAND RECEIVER.** The famous American BC153, covering 100-550 Kc/s, I.F.s being 85 Kc/s. Complete with all 6 valves and circuit. NEW IN MAKER'S CARTONS. ONLY 89 6 (post 3 6).

**AIRBORNE TRANSMITTER-RECEIVERS TYPE 1986.** 10 Channel Mobile Units, complete (less external attachments) in metal case, with all 21 latest type midrange valves and 21 volt Rotary Power Unit. Crystal controlled. I.F. Bands with 23 Kc/s. Size 15 1/2in. x 7 1/2in. x 8 1/2in., weight 26 lbs. Used but in first-class condition. ONLY £6.19.6 (carriage, etc., 10 6).

**MONITOR TYPE 6L** for conversion to an Oscilloscope. Employs 3 1/2in. C.R.T. type VCR138A, and built-in A.C. Mains Power Unit for 115/230 volts. Modern design. Full modification data supplied. Condition as new. ONLY £27.19.6 (carriage, etc., 15/-).

**TCS TRANSMITTERS.** These magnificent American units cover 5-12.0 Mc/s in 3 switched bands. Complete with 7 valves; 3 of 12A6 Osc.; 1625 Buffer; 2 of 1825A; 1025 VFO. Provision for Crystal Control, C.W. or R.T. Has Plate and Aerial Current meters. New condition internally, but externally store soiled. £7.19.6 (carriage, etc., 15/-).

**HRO MAINS POWER UNITS.** Input 115 230 volts A.C. D.C. Output (fully smoothed) 230 volts 75 mA., and 6.2 volts 3.5 amps. Complete in black crackle case. ONLY 60/-.

**POWER UNITS TYPE 234.** Primary Input 200 250 v. 50 cycles. Outputs of 250 v. 100 mA. and 6.3 v. 4 amps. Fitted double smoothing. For normal rack mounting (or bench use) having grey front panel size 1 1/2in. x 7in. BRAND NEW. ONLY 59 6 (carriage, etc., 7 6).

**12 VOLTS AMERICAN DYNAMOTOR.** Delivers 220 volts at 100 mills. Ideal for running Car Radio or Electric Shaver, etc., from Car Battery. ONLY 32 6.

**6 v. VIBRATOR PACKS.** Output approx. 130 v. at 30 mA., fully filtered and smoothed. Complete. BRAND NEW. ONLY 12 6.

**R1155 SUPER SLOW-MOTION TUNING ASSEMBLY.** As used on all late model 1155s. Easily fitted to "A" sets, etc. BRAND NEW. ONLY 12 6.

**HEAT TRANSFORMERS.** 5.5 kV. (Rect.) with 2 v. 1 a. 79 6. 1 kV. (Rect.) with 2 v. 1 a. 89 6. 2.5 kV. (Rect.) with 2 1/2 v. 1.1 a. 2-0 2 v. 2 a. (for VCR9 tube, etc.) 42 6 (postage 2- per trans.).

**POCKET VOLTMETERS.** Read 0-15 volts and 0-300 volts A.C. or D.C. BRAND NEW AND UNUSED. ONLY 18 6.

**CRYSTALS.** British Standards 2-pin 500 Kc/s, 15/-; Miniature 200 Kc/s, 10/-.

**MAINS ISOLATING TRANSFORMER.** Manufactured by Vortexion. Fully shrouded. Will provide true 1 : 1 ratio from nominal 230 v. Primary. Rated at 100 watts. BRAND NEW. ONLY 22 6. (Post 2 6).

**SPRAGUE CONDENSERS.** Metal cased, wire ends. New, 0.01 mfd. 1,000 volt, and 1 mfd. 500 volt, 7 6 per dozen. Special quotes for quantities.

## HARRIS ELECTRONICS

(LONDON) LTD.

138 Gray's Inn Road, London, W.C.1.

(Phone TERMINUS 7937)

Please include carriage costs on All items.

(Open until 1 p.m. Saturdays. We are 2 mins. from High Holborn (Chancery Lane Station) and 5 mins. by bus from King's Cross.)

**RST**

**MAIL ORDER DEPARTMENT**  
 211 Streatham Road, Mitcham, Surrey.  
**ALL VALVES LISTED ARE NEW STOCK**  
 • Terms C.W.O. or C.O.D. Postage 3d. per valve.  
**MITCHAM 6201.**

|              |            |                  |                   |              |
|--------------|------------|------------------|-------------------|--------------|
| AC/TH1 34/9  | ECC85 9/6  | FW4/500          | PY32 15/6         | X78 21/-     |
| AC/TP 32/6   | ECF80 12/6 | GZ30 10/-        | PY80 8/6          | X79 21/-     |
| AZ1 15/6     | ECF82 12/6 | GZ32 11/6        | PY82 8/-          | Z77 5/-      |
| AZ31 10/6    | ECH3 12/6  | GZ34 13/6        | PY83 8/6          | IA7 14/6     |
| U35 21/-     | ECH35 10/- | HABC80           | PZ30 18.6         | IC1 9/6      |
| C1C 8/8      | ECH21 10/- | HF93 9/-         | SP41 3/6          | IC2 9/6      |
| CBL31 21/-   | ECH22 22/- | HK90 9/6         | (Ex. Gov.)        | IN5GT 10/8   |
| CH35 12/6    | ECH35 22/- | HK90 9/6         | SP61 3/6          | IP1 9/-      |
| FL33 18/6    | HL35 10/-  | HL41DD 13/6      | (Ex. Gov.)        | IL3 9/-      |
| CY1 15/9     | ECH81 9/-  | HL133DD 10/-     | TH48 27/6         | IS4 9/6      |
| CY31 15/9    | ECH83 9/6  | HY90 10/-        | TY86F 15/6        | IS5 9/-      |
| D41 12/6     | ECL89 9/-  | IW4/350 10/-     | U10 18/6          | IS6 8/-      |
| D77 8/6      | ECL92 12/6 | IW4/500 10/-     | U41 15/9          | IS8 10/6     |
| DA32 6/-     | ECL83 15/6 | EP8 21/-         | U18 20 10/-       | IS9 7/-      |
| DAF91 7/6    | EP8 21/-   | EP87A 8/6        | U24 29/6          | IS10 9/6     |
| DAF96 9/6    | EP87A 8/6  | KT33C 10/-       | U25 16/6          | IS13GT 8/6   |
| DF33 10/6    | EF37A 8/6  | KT55 22/6        | U26 12/6          | IS14 10/-    |
| DF91 5/-     | EF37A 8/6  | KT66 17/6        | U52 7/-           | SATC 18/6    |
| DF92 7/-     | EF40 15/-  | MKT4- 7 pin 17/6 | U78 7/-           | SAME 5/-     |
| DF96 9/6     | EF42 10/6  | MKT4- 5 pin 17/6 | U91 20/-          | SHW7 6/6     |
| DH77 8/3     | EF50/A 4/6 | MU14 9/-         | U403 11/6         | 6BX6 7/-     |
| DK32 21/-    | EF50/E 4/- | N78 17/6         | U801 29/6         | 8F10 4/-     |
| DK91 9/-     | EF80 7/-   | N39 25/6         | UABC80 6.15GT 4/6 | 8F10GT 9/6   |
| DK92 9/6     | EF88 13/6  | N89A 17/6        | UAF42 9/6         | 8K7C 4/-     |
| DK96 10/-    | EF89 10/-  | N709 9/6         | U41 9/-           | 8SC7 7/6     |
| DL33 9/-     | EF91 5/-   | PABC80 12/6      | UBC41 9/6         | 8W7C 9/-     |
| DL35 12/6    | EF92 5/-   | PCB89 9/6        | UBC81 4RL7GT 6/6  | 8Y7C 8/6     |
| DL91 9/6     | EF96 7/6   | PC85 18/6        | UBF80 9/6         | 6SN7GT 5/6   |
| DL92 8/6     | EF98 9/6   | PC85 12/6        | UBF89 8/6         | 6U4GT 11/6   |
| DL94 9/-     | EF98 9/6   | PCC85 12/6       | UCC84 18/6        | 6V6G 5/-     |
| DL96 9/6     | EF98 9/6   | PCC88 20/-       | UCC85 10/-        | 7B7 8/-      |
| DW4/500 12/6 | EL33 18/6  | PCC89 12/6       | UCF80 19/6        | 7C7 8/-      |
| EABC80 7/6   | EL37 18/6  | PCF80 10/6       | UCH21 10/6        | 7D7 10/6     |
| EAF42 10/-   | EL41 10/6  | PCF82 11/6       | UCH21 21/-        | 7E7 7/6      |
| EB41 7/6     | EL42 10/6  | PCF82 11/6       | UCH42 9/-         | 12AH8 10/-   |
| EB91 5/-     | EL81 14/9  | PL82 11/6        | UCH81 9/-         | 12AT7 8/-    |
| EBC33 7/6    | EL84 9/6   | PCL83 12/-       | UCL82 12A17 9/6   | 12B17 15/-   |
| EBC41 9/6    | EM30 10/-  | PCL84 14/6       | UCL82 12/6        | 12B7 15/-    |
| EBB81 10/6   | EM34 10/-  | PEN40D 22/6      | UCL83 23/6        | 25A6 12/6    |
| EBC90 8/3    | EM81 10/-  | PEN44A 17/6      | UF41 9/-          | 25L6GT 9/6   |
| EBF80 9/6    | EM84 12/6  | PEN25 10/6       | UF42 11/6         | 25Z4G 9/6    |
| EBF83 9/6    | EM85 12/6  | PEN4A 10/6       | UF85 9/-          | 25Z5 9/6     |
| EBF89 9/6    | EN51 9/-   | PL36 17/6        | U86 14/6          | 25Z6GT 10/6  |
| EBL21 22/-   | EN53 14/6  | PL36 15/-        | UF89 9/-          | 35L6GT 10/6  |
| EBL31 21/6   | EN56 14/6  | PL38 23/9        | UL4 24/6          | 35W4 8/-     |
| ECC34 15/6   | EN58 7/-   | PL81 23/9        | UL44 24/6         | 40SUA15 15/- |
| ECC40 21/-   | EZ40 7/6   | PL82 8/-         | UL46 21/-         | 50CD6G 15/-  |
| ECC81 8/-    | EZ81 7/6   | PL83 10/6        | U8 26/-           |              |
| ECC82 9/6    | EZ90 7/6   | PM24M 21/9       | UY21 15/6         |              |
| ECC83 9/6    | FC2 21/-   | PX4 21/-         | UY41 7/6          |              |
| ECC84 9/6    | FC13C 21/- | PX25 30/-        | UY85 7/6          |              |
|              |            |                  | W81 22/6          |              |

**RECTIFIERS**

|          |            |            |             |               |
|----------|------------|------------|-------------|---------------|
| RM1 6/-  | RM4B 16/6  | DRM2B 14/6 | 14A97 23/6  | (14RA1-2-3-3) |
| RM2 7/9  | RM5 22/-   | DRM3B 21/- | 14A100 24/- | FC101 17/6    |
| RM3 8/6  | DRM1B 12/6 | 14A86 16/- | FC31 21/-   | (14RA1-2-9-2) |
| RM4 16/6 |            |            |             |               |

SEND FOR LISTS. Quotations given for any types not listed. Obsolete and old types a speciality.

**For Safety's Sake**  
 use  
**AVO Prodclips**

Pat. No 748811

with Trigger-Action Spring-Loaded Clips

PRESS TRIGGER TO OPEN

RELEASE TO GRIP

Safety first every time with these patented spring-loaded AVO Prodclips.

Cleverly designed for use as insulated tools, they are invaluable for reaching and holding test points which are difficult of access.

Post Free  
**15/-**  
 per pair.

**AVO LTD** AVOCET HOUSE,  
 92-96 VAUXHALL BRIDGE ROAD, LONDON, S.W.1.  
 PC 2 VICTORIA 3404 (12 lines).

**Just Released!**

**REPANCO MINI-3**

A new local station pocket transistor receiver  
 5in. x 3 1/2 in. x 1 1/2 in.

- Three Transistors.
- Loudspeaker reception.
- Regenerative R.F. reflex circuit.
- Dual Ferrite Aerials.
- Long and Medium Wave.

Send Now 1/6 (Post free) for easy wiring plans and instructions.

**RADIO EXPERIMENTAL PRODUCTS, LTD.**  
 33, Much Park Street, Coventry.

A 3d. stamp will bring you a copy of our latest

**RADIO & TELEVISION COMPONENT Catalogue**

**JAMES H. MARTIN & CO.**  
 FINSTHWAITE, NEWBY BRIDGE,  
 ULVERSTON, LANCs.

**AUDIOPHILES**

Building for Hi-Fi? Then this is for you. Small compact F.M. (front end, 85-102 mc/s, output 10.7 mc/s. Tubes in anywhere. Highly sensitive. Single valve (ECC85). Price, including circuit and data, but excluding valve, £2 12 3. plus 2/- postage. Delivery ex stock.

(Department E/2), **ROTOPONS LTD.**,  
 54, Beddington Lane, Croydon, Surrey.

**Practical Transistor Receivers, Book 2.** by Sinclair. 7/6. postage 9d.

**Experimental Radio Engineering.** by Rapson. 4th Ed. 12.6. postage 1/-.

**TV Engineers' Pocket Book.** by Hawker. 12.6. postage 9d.

**TV Servicing, four volumes.** by Patchett. 23/- complete, postage 1/3.

**Trimer Valve and Tele Tube Manual.** No. 8. 6/-, postage 9d.

**Radio Circuits.** by Miller. new edition. 15/-, postage 1/-.

**Principles of Transistor Circuits.** by Amos. 21/-, postage 1/-.

**Collins Radio Diaries.** 1960. 5/9. postage 6d.

**Oscilloscope at Work.** by Haas. 15/-, postage 1/-.

**UNIVERSAL BOOK CO.**  
 12 Little Newport Street, London, W.C.2  
 (adjoining Lisie Street)

**ASTRAL RADIO PRODUCTS**

**HOME RADIO.** 32-page illustrated booklet. Simple wiring instructions for Crystal Set, 1, 2, 3 Valves, 2/-, post 3d. TRF COILS, 7/-, pr., post 6d. DUAL WAVE HF Coil with REACTION. Specified for 'Summer All Dry Portable'. A.C. Double Triode 1, etc., 4/6, post 3d. HTS Miniature, 1" x 1 1/2" x 2 1/2" in cans. Extra high 'Q'. Special offer, 9/-, pr., post 6d. Crystal Set Coils, L. & M.W. 2/6, post 3d.

**82 Centurion Road, Brighton**

**RES/CAP. BRIDGE 37/-**  
 p. & p. 2/-  
 Checks all types of resistors, condensers 6 RANGES

Built in 1 hour. Direct reading  
**READY CALIBRATED**  
 Stamp for details of this and other kits.

**RADIO MAIL (Dept. PT)**  
 Raleigh Mews, Raleigh Street, Nottingham

# THE LINEAR LI/10

A 10-WATT HIGH FIDELITY ULTRA LINEAR AMPLIFIER WITH INTEGRAL PRE-AMP

Full advantage has been taken of latest component miniaturisation developments to produce a 10-watt Hi-Fi push-pull amplifier incorporating tone control pre-amplifier stages within the measurements of 9 x 7 x 5 ins. In addition two high impedance input sockets are provided for microphone and gram., etc. With selector switch and vol. control, five B.V.A. valves are employed ECC83, ECC83, EL84, EL84, EZ81. H.T. and L.T. power supply point is included for a radio tuner.

**FREQUENCY RESPONSE**  
± 1 d.b., 30-20,000 c.p.s.

**MAXIMUM POWER OUTPUT**  
In excess of 14 watts.

**SENSITIVITY**

L.P. 25 m.v. for 10 watts. 78 r.p.m. 30 m.v. for 10 watts. Radio/Microphone 6 m.v. for 10 watts.

**TREBLE LIFT CONTROL**

+ 10 d.b. to -22 d.b. at 12,000 c.p.s.

**BASS CONTROL**


+ 14 d.b. to -10 d.b. at 50 c.p.s.

**HUM LEVEL**

Referred to maximum output and including integral pre-amp. -70 d.b.

**NEGATIVE FEEDBACK**

21 d.b. in main loop

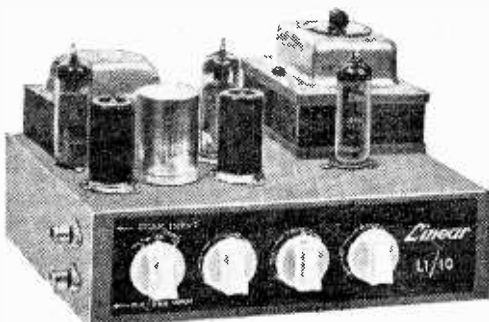

**HARMONIC DISTORTION** Less than 0.1% measured at 8 watts at 1000 c.p.s. Weight 10 lbs. Power consumption 90 watts. For 200-230-250 v. 50 c.p.s. A.C. mains. Outputs for 3- and 15-ohm speakers. Chassis finish stoved Gold hammer.

**HIGHEST QUALITY!** Retail price

**MAXIMUM RELIABILITY!**  
**AT A PRICE YOU CAN AFFORD.** 13 GNS.

Send S.A.E. for descriptive literature.

**TRADE ENQUIRIES to**

**Also Available—THE L45. A compact High Quality 4.5 watt amplifier.** Size approx. 7.5-5.3in. high. Sensitivity is 28 millivolts so that the input socket can be used for either microphone or gram., tape, radio tuner, etc. B.V.A. valves used are ECC83, EL84, EZ80. Controls are: Vol. Treble and Bass with mains switch. The Tone controls provide full compensation for long playing records. Output matching for 3 ohm loudspeaker. Retail price £5/19/6.

**THE LT45 TAPE DECK AMPLIFIER.**

A complete unit (power pack and oscillator incorporated) ready for connection to A.C. mains. 3 ohm loudspeaker and practically any make of deck. Negative feedback equalization adjustment by multi-position switch for 3, 7, and 15in. per set. Retail price 12 gns.

**DIATONIC 10-14 WATT.** High Fidelity amplifier with integral pre-amplifier. Retail 12 gns.

**CONCHORD 30 WATT.** Hi-Fi amplifier with two separately controlled inputs. Retail 15 gns.

**L3/3 STEREO PHONIC AMPLIFIER.** Sensitivity 150 m.v. Output 3 watts on each channel. Retail 7 gns.

**L5/5 STEREO AMPLIFIER.** 5 + 5 watt. 11 gns.

**LINEAR PRODUCTS LTD. ELECTRON WORKS, ARMLEY, LEEDS.**

## SOLDERING EQUIPMENT

BY



**PRECISION SOLDERING INSTRUMENTS for the ELECTRONICS INDUSTRY**

- Comprehensive range
- Robust & Reliable
- Light weight
- Rapid heating
- Bit sizes 3, 32in. to 3 8in.
- 'Permabit' or Copper bits
- All voltage ranges 6 7v. to 230 250v
- Prices from 19 6

Illustrated is the 25w. 3/16in. replaceable bit model with safety shield.

British and Foreign Patents. Registered designs. Suppliers to H.M. and Foreign Governments. Agents throughout the world.

Brochure No. S.10 sent free on request. Sole proprietors and manufacturers:

**LIGHT SOLDERING DEVELOPMENTS LIMITED**

28, Sydenham Road, Croydon, Surrey.

Phone: CROYdon 8589 Grams: Litesold Croydon



## Training in Radio and Television Servicing

The Pembridge College of Electronics provides a full-time One Year course in the basic principles of Radio and Television for prospective servicing engineers. This course is also suitable for those wishing to maintain all types of industrial electronic equipment.

The next course commences on 5th January, 1960. Following courses commence on 26th April and 6th September, 1960.

Evening course in Television servicing commences on 12th January, 1960.

For details of these courses, write for prospectus and admission forms to:

The Principal Dept. Pro,  
THE PEMBRIDGE COLLEGE  
OF ELECTRONICS  
34A, Hereford Road, London, W.2.  
Telephone: BAYswater 9117

pc's



### IDEAL XMAS GIFT RECORD PLAYER CABINET

29/6

Elegant in grey or red washable rexine with sunken control panel and speaker fret. Size 13in. x 17in. x 8in. deep. Takes B.S.R. Monarch 4-speed autochanger. Elliptical speaker and most of the modern portable amplifiers.


RP6

Carr. &amp; Ins., 4/6.
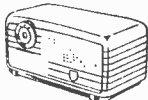
### TWO OUTSTANDING BARGAINS STURDY CASE

12/6

(Ideal record case.) Covered in burgundy and grey washable rexine. Size 8 1/2 in. x 7 1/2 in. x 3 1/2 in. deep. Strong clasp, hinges and carry handle. Ideal for portable radio or transistor set. Can be adapted as a record carrying case to hold 18 E.P. 7in. records. P. & P. 2/6.



### BAKELITE CABINET

5/9 Brand new. Attractive design. Size 12in. x 7in. x 5 1/2 in. Colour brown. Ideal for small receivers, etc. P. & P. 3/3.

### ★ BATTERY PLAYER UNIT 99/6

Takes any size record, has latest turn-over crystal pick-up. Base 9 1/2 in. x 1 1/2 in., weight 3 1/2 lb. Colour Ivory. Current cons. 60/70 ohms. 6 or 9 volt. 4 speed. P. & P. 4/6.

### ★ VALVE BATTERY AMPLIFIER 39/6


Ideal for use with player above. 14 volt L.T. 60 or 90 volt H.T. O.P. Imp. : 3 ohms. P. & P. 3/6.

### ★ 3 TRANSISTOR AMPLIFIER 79/6

9 volt. O.P. Imp. : 3 ohms. OC71 driving 20C72. P. & P. 3/6.
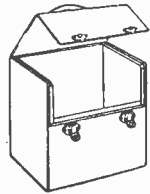
### RECORD CASE A GIFT FOR ALL AGES

Beautifully made in various colours covered in washable leatherette. Strong modern case and carry handle. Hinged top, plated clip fasteners. P. & P. 2/6. To hold 30 E.P. 7in. records, 21/9. To hold 40 E.P. 7in. records, 23/9. To hold 20 10in. or 12in. records, 22/6. To hold 50 10in. records, 24/6. To hold 50 12in. records, 27/6.



FOCUS MAGNETS. 9/9. Brand new 38 mm. Incorp. picture shift control. P. & P. 1/3.

ELAC FOCUS MAGNETS. 12/9. New. 35 38 mm. P. & P. 1/3. 17in. T.V. MASKS. 7/9. White, blue or pink plastic. New. P. & P. 2/3.

INSULATING TAPE. 1/6. Good quality. 75ft. x 1/2 in. wide in sealed metal tin. P. & P. 9d.

VOLUME CONTROLS. 2/6 doz. Mixed parcel of volume and tone controls taken from working chassis. P. & P. 2/-.

T.V. AERIALS. 7/9. Fitted with 9ft. co-ax. cable. B.B.C. For door rod or loft. P. & P. 1/3.

B.B.C. Indoor type. 15/6. Folded dipole with 12ft. co-ax. cable fitted. P. & P. 1/9.

I.T.A. or B.B.C. 23/6. 3 element. P. & P. 2/6.

O.P. TRANSFORMERS. 1/3. Std. size. 2-5 ohms. P. & P. 1/-, 20 for £1. Post 3/6.

8in. P.M. SPEAKERS. 5/9. Has a slight cone repair, not affecting the quality. Tested and guaranteed. Limited quantity. P. & P. 2/9; on two 3/6.



DEPT. XII.

**COMPONENTS LTD.**

219, ILFORD LANE, ILFORD, ESSEX

Stamp for FREE Catalogue

Phone ILF. 0295

## The ideal book for every serious model maker . . . RADIO - CONTROLLED MODELS

by F. J. Gamm

Contents  
Include

Simple Steering Control Gear : A Single-valve Super-regenerative Receiver : A Two-valve Transmitter for Radio Control : Control Box : Wavemeter, Interference, Layout : Obtaining a Second Channel Using the "Mark/Space" System : A Proportional Steering Circuit and Reversible Sequence Engine Control Gear : Radio-controlled Boat using a Glow-plug Engine and an Electric Motor in the Power Unit : A Six-valve Super-heterodyne Receiver for Model Control : A Single-valve Crystal-controlled Transmitter : Radio Control for Model Aircraft (Sequence System) : Tuned Reeds and Audio Control : More About Model Actuators : Tuning Model-control Transmitting Aerials : A Bulb Model-control Frequency Meter : An Auto-switch for Model-control Transmitters : A Radio-controlled Model Battleship : Building a Radio-controlled Model Aircraft.

Fully illustrated with circuit details, diagrams and photographs.

12s. 6d. FROM ALL  
BOOKSELLERS

... or in case of difficulty 13s. 6d., by post from C. ARTHUR PEARSON LTD., Tower House, Southampton Street, London, W.C.2.

PEARSON



## "GLOBE-KING"

WORLD-FAMOUS KITS AND RECEIVERS for the Radio Amateur and S.W. Listener. Catalogue Free, enclose stamp for Postage. Kits from 79/6 at your dealers, or direct from sole manufacturers :  
**JOHNSONS RADIO**  
St. Martins Gate, Worcester

## New Hi-Fi Publications

JASON FM TUNERS 2s. 6d.  
MULLARD AMPLIFIER MANUAL 8s. 6d.  
MULLARD TAPE PRE-AMP. C 2s. 6d.  
QUALITY AMPLIFIERS 7 designs 4s. 6d.

52-page Catalogue available on request.

**J. T. FILMER 82, DARTFORD ROAD  
DARTFORD, KENT.**

Tel. Dartford 4057

## PRECISION WIREWOUND RESISTORS

1 watt. 1 to 1,000 ohms, 1%, 2/9; 0.25, 4/3; to 5 K., 1%, 3/3; 0.2%, 4/9; to 20 K., 1%, 4/-; 0.2%, 6/-; to 50 K., 1%, 4/3. Your value wound to order.

1% Shunt for 1 mA., 100 ohm Meter.— Ranges 10, 100, 1,000 mA., 8/6. For 500uA 500 ohm meter, ranges 5, 50, 500 mA., 8/6. We can quote for shunts, with ranges to your specification.

Meter Rectifiers.—New Salford Bridge, 1 mA., 7/6; 5 mA., 7/6. Ex-Govt. Bridge M3, 5-50 mA., 3/6; 250 v., 50 mA., 1 wave, 6/9. Switches, Standard Size.—1 p. 11 w., 3/11; 1 p. 18 w., 7/6; 2 p. 11 w., 6/3; 2 p. 9 w., 7/6. Meter, Multimeter Sealed.—2 1/2 in. scale, 0-1 mA., flush mtg., with 25 range A.C./D.C. multimeter oct., 32 6. p. & p. 1/6. All parts available.

Circuits.—25 range for 1 mA., 100uA. and 500uA meters, 40 range for 500uA, 9d. each. 1000 stab. resistors, all 1%, 100, 1 K., 5 K., 9 K., 10 K., 50 K., 90 K., 100 K., 500 K., 5 M., 10 M. All at special low price of 1/6 each. Postage extra. S.A.E. with enquiries, please.


**PLANET INSTRUMENT CO.**  
25, Dominion Avenue, Leeds, 7



**HOME BARBER KIT**  
  
**COMPLETE 24/6**

Family Haircuts are expensive but one modest outlay for our Kit saves £8 £8 £8 every year. Besides "Home-Barbering" is so easy and pleasing. Pictorial Step-by-Step Guide teaches shaving, graduating & Hair-styling. *Just try & see. Guaranteed.*

**PIFCO**  
 All-in-one Radiometer  
 A.C./D.C.  
 ★ **CIRCUIT TEST.**  
 ★ **L.T. and H.T. TESTS.**  
 ★ **mA TEST.**  
 ★ **VALVE TEST.**



Continuity and Resistance Tests. Complete with Test Leads. Post 1/- Guaranteed. **32/6**

**PIFCO Illuminating Soldering Iron**  
  
 Designed and constructed with a complete understanding of the technical need for making a perfect soldering job in the quickest time. The Pifco Soldering Iron incorporates in its red plastic handle a 6.3 volt lamp directing a beam of light directly on to the soldering point, enabling easy manipulation in the darkest and most difficult places. The lamp also acts as a safety eye ensuring the iron is not left on unintentionally. The bit is 3/16in. diameter and of the pencil type, acknowledged as the most valuable for all general purposes. Chrome plated rivet allows the hot iron to stand on the table or may be used as a hanger. Element 35 watts. Six feet grey 3-core flex fitted. Length 10 inches. For 200/250 volts A.C./D.C. Complete **22/6**

**TALK on your Own Radio -SING**  
  
**RADIOMICROPHONE**

Connects to your Radio Pick-up or gram socket. Easy to fix. Ideal for Dances, Meetings, Socials, Parties, Lectures, Clubs, etc. Limited Ex-Govt. Quantity. Order **Immediately. P.P. 2/6. 13/6**

**DEMOBBED VALVES 2/6**  
 Giving equivalent of British and American Service and Cross Reference of Commercial Types with an Appendix of B.V.A. Equivalents and Comprehensive Price List. We have still some Valves left at very old Budget Rates (331%) which are actually sold at the old price (1951). Also ready out


**NEW COMPREHENSIVE LIST**

**RADIO BEGINNERS' REPAIRS BOOK 4/-**  
 Colour code indicators. Price 1/9

**RADIO BULLS VALVES**  
 246, HIGH ST. HARLESDEN WY.  
**Chassis Cutters (with key)**  
  
 The easiest and quickest way of putting holes in sheet metal. The cutter consists of three parts: a die, a punch and an Allen screw. The operation is quite simple. Price incl. key: 1in. 1in. 15/9; 1in. 3/4in. 14/9; 1in. 1/2in. 14/9; 1in. 17/6; 1in. 1in. 19/6; 1in. 1 1/2in. 22/6; 2in. 32/6; 2 1/2in. 35/9; 3in. 40/9; 1in. square. 30/6. Post 1/- dozen at **10/6**

**Service Sheets**  
 1in. 22/6; 2in. 32/6; 2 1/2in. 35/9; 3in. 40/9; 1in. square. 30/6. Post 1/- dozen at **10/6**

**All prices are with keys**

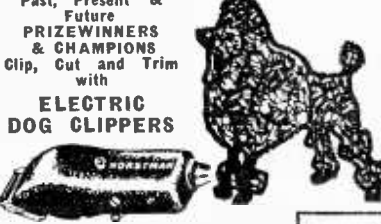**Past, Present & Future PRIZEWINNERS & CHAMPIONS**  
 Clip, Cut and Trim with **ELECTRIC DOG CLIPPERS**  
  
 As used in leading kennels by breeders and Dog Lovers. Will save you cash. Professional trim in minutes. Silent operation. Your pet will love it. Guaranteed 12 months. Instr. & free guide to 4 Poodle Clips incl. **Prompt Delivery from Stock and guaranteed.**

8/- down 17 weekly payments of 10/- or £8 cash

**TRANSISTORS**  
 Brand New and Guaranteed Not Surplus or Rejects **LOOK AT THESE PRICES FOR HIGH GAIN TRANSISTORS**  
 RF/IF/OSC: Red/Yell (6 mc/s), 12/6; White Spot (4 mc/s) 9/-; Audio: Yell/Green, 7/- (pair in P.P. 250 m/W, matched pair 14/6); Red Spot 7/-.  
**MINIATURE 3-STAGE 4 TRANSISTORS AMPLIFIER.** P.P. output 250 m/W. 2-3 ohms speaker output for gram., radio, mike, baby alarm, etc. High gain, excellent quality, low consumption from small 6 volt dry battery. Easy assembly. Full kit, matched transistors, base panel, complete instructions. **BRAND NEW COMPONENTS.** 59/6. p.p. 1/6. Circuit diagram, assembly instructions, etc., 2/6.  
**SUB. MIN Electrolytics.** 2, 4, 8, 25, 50, 100, 15 V.W. 2/9 each.  
**MIDGET RESISTORS.** 1 1/2 Watt. All approved values. 10 ohms to 12 Megs. 31d. each.  
**MIDGET VOLUME CONTROLS.** L.P. 5 K to 2 Megs., 2/10. Full range with S/P. and D.P. switches available.  
 (All our components are new and guaranteed.)  
**ATTRACTIVE PLASTIC BOXES** with hinged lid. Pastel Cream, for Midget Receivers. 4 3/16" x 5 1/2" x 1 1/2", 2/6, p.p. 1/-; 5 3/8" x 3 1/2" x 1 5/16", 3/3, p.p. 1/-; 7 1/2" x 5 1/2" x 1 1/2", 4/9, p.p. 1/3.  
**PERSPEX BLANKS** 6" x 3" x 1/8". Ivory, 1/-, p.p. 6d.  
**PLEASE INCLUDE SUFFICIENT POSTAGE WHEN ORDERING.**  
 Send 3d. stamp for Full List of Complete Range of New Components.

**BURLAND RADIO ACCESSORIES**  
 G3JRE Est. 1947. G3JZ  
**ANN'S PLACE, SOUTHWICK, SUSSEX**

**A WONDERFUL OPPORTUNITY**  
 Build a 1st Class 3-valve + Rectifier T.R.F. Radio.  
 ★ Operates from A.C. mains.  
 ★ Everything you require is supplied.  
 ★ Point to point diagram for easy construction.  
 ★ 7in. x 4in. Elliptical speaker.  
 ★ All components guaranteed.  
 ★ Terrific value at **£4-4-0** plus P. & P. 3/-.

**SPECIAL OFFER !**  
**A Mains Neon Tester, a must for the home constructor FREE with each kit.**

**FOURWAYS TELEVISION SERVICE,**  
 246, Dalston Lane, London, E.8.  
 Tel.: AMHerst 9901.

**1-Finger Pianist**  
 Build your own electronic keyboard and play everything! Send for free leaflet. Guitar, cello, flute and trumpet are all easy. Write now . . .  
**G & S, 20 Maude Street, Darlington, Co. Durham.**

**ALFRED PADGETT**  
 40, MEADOW LANE, LEEDS, 11  
 Tel.: CLECKHEATON 2886

**SPECIAL OFFER OF RECONDITIONED ULTRA TV SETS, MODEL 815, A 14in. TV for all B.B.C. and I.T.V. Stations.** Perfect results and sold with a money-back guarantee. For £12 only. Tube in separate carton. Carriage per B.R.S., 17/-.  
**RECEIVER TYPE 3645.** The cleaned up 1355. Complete with 7 VR65, 1 VR91 valves. With valves, 12/- Less valves, 6/- Carriage per B.R.S., 7/6.  
**BT SH TV 24C 12in. TV, B.B.C. and I.T.V.** Perfect pictures, £9. Carr., 17/-.  
**BT SH-PYE-ULTRA. 12in. B.B.C. only** Perfect pictures, 26. Carr., 17/-.  
**TWELVE INCH TV CHASSIS,** complete with L.O.T. focus coils, etc., less valves, 15/- Pye, Ultra, Plessey, Banner, Ekco, Marconi, etc. Carriage per B.R.S., 5/- Chassis less L.O.T. and focus coils, 5/- Carr. 4/-  
**SPEAKERS FROM TV SETS,** All Perfect - 7 x 4, 10" x 5 Bin., 6/6; 6in., 6/6. Post 2/-  
**KEY SWITCHES,** 1/3. Post 1/3. 15/- per doz., post free.  
**JACK PLUGS,** 1/6. Post 1/- Six for 8/- post free.  
**RELAYS,** 3000 Type, 2/- Post 1/3. 20/- per doz., post free.  
**MAINS TRANSFORMER - EX-R.A.F.** 250 x 250 volts at 30 m.a., 6.3 at 1.5 amp. 5 volts at 2 amp. 230 volt Prim. 6/6. Post 2/6.  
**NEW VALVES, POST FREE.** U50, 6/-; U14, 5/-; DL50, 1/6; KT63, 5/-; DH63, 5/-; 6K8, 5/-; 6C4, 2/6; 6J5, 2/6; 6AG5, 2/6  
**RACOM 2-** 655, 2/6; 900, 1/3; 12SH7M 2-; 12SJ7M, 2/-; 12A6M, 4/-; 12HM, 1/3; 2X2, 1/9.  
**EQUAL TO NEW TV VALVES.** Three Months' Guarantee. Post free. 10P1, 5/-; 6P1, 3/-; 6AM6, 3/-; EP80, 3/- S.A.E. for valve list.


# CONSTRUCTORS CORNER

## ENSURE SUCCESS WITH R.C.S.

Explore the world on short-wave radio (10-100 m)


FOR ONLY **35/-**

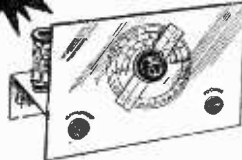Construction price includes valve and one coil covering 40-100 m.  
 ● Can be converted to 2v. or 3v.  
 ● Receives speech and music clearly from all over the world.  
 Send 2/- for diagram and price list.


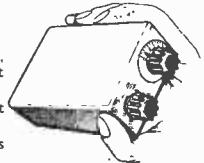
### SENSATIONAL RESULTS WITH 2 TRANSISTORS

- ★ No aerial or earth.
- ★ Dial tuning with mini .0005.
- ★ Drilled chassis, colour coded, components, simple layout for beginners.
- ★ Special small case fits shirt pocket.
- ★ Soldering iron and pliers are only tools needed.





Finest results ever obtained with 2 transistors and diode layout. The ideal radio to carry with you everywhere. PARTS PRICE LIST & EASY LAYOUT PLANS, 2/- Total building cost, including transistors, wire, even solder, etc., but excluding headphone. **62/6**

### BUILD THIS AMAZING RADIO POWERFUL! PERSONAL! PORTABLE!

- ★ Sturdy metal case.
- ★ No holes to drill.
- ★ Detachable rod aerial.
- ★ All batteries self contained.
- ★ Can be built in 1 hour.
- ★ Covers medium waves.
- ★ Loud clear tone.
- ★ Selective tuning.
- ★ All parts are sold separately.

FOR ONLY **35/-**

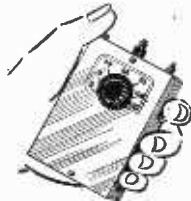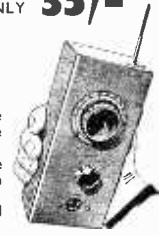This delightful set is designed to give you a completely personal portable radio. Bronze-finished case. Ideal for the beach, the bedroom, the office—in fact, anywhere. Send 2/- for wiring diagram and component price list.



### TRANSISTOR POCKET RADIO

Two-stage circuit using variloopstick coil.

- Ideal for the beginner.
- Can be built in 30 minutes.
- Works for months off 7d. battery.
- Fits into palm of your hand.

The ideal low-cost transistor pocket radio for the beginner. Send 2/- for data and list of components.

ONLY **30/-**

### CRYSTAL RECEIVER

Covers M/W Band for All components including case for **10/6** Ideal for the beginner

Trade Enquiries Welcomed

**R.C.S. PRODUCTS (RADIO) LTD. 11, OLIVER RD., LONDON, E.17.**

Mail Order Only

## FREE TO AMBITIOUS ENGINEERS!

The latest edition of "Engineering Opportunities"



Have you sent for your copy?

### 'ENGINEERING OPPORTUNITIES'

is a highly informative guide to the best-paid Engineering posts. It tells you how you can quickly prepare at home on "NO PASS—NO FEE" terms for a recognised engineering qualification, outlines the widest range of modern Home-Study Courses in all branches of Engineering and explains the benefits of our Employment Dept. If you're earning less than £20 a week you cannot afford to miss reading this unique book. Send for your copy to-day—FREE.

FREE COUPON  
 Please send me your FREE 148-page "ENGINEERING OPPORTUNITIES"

### WHICH IS YOUR PET SUBJECT?

- Mechanical Eng.
  - Electrical Eng.
  - Civil Engineering
  - Radio Engineering
  - Automobile Eng.
  - Aeronautical Eng.
  - Production Eng.
  - Building, Plastics, Draughtsmanship, Television, etc.
- GET SOME LETTERS AFTER YOUR NAME!  
 A.M.I.Mech.E.  
 A.M.I.C.E.  
 A.M.I.P.E.  
 A.M.I.M.I.  
 L.I.O.B.  
 A.F.R.Ae.S.  
 B.Sc.  
 A.M.Brit.I.R.E.  
 CITY & GUILDS  
 GEN. CERT.  
 OF EDUCATION  
 etc., etc.

NAME .....  
 ADDRESS .....  
 Subject or Exam. that interests me.....  
 British Institute of Engineering Technology  
 409B, College House, 29-31, Wright's Lane, Kensington, W.8.

## GOVERNMENT SURPLUS AND MANUFACTURERS CLEARANCE

METERS, 0-1 m/A. 2 1/2 in. diam., 20' each. 500-0-500 microamp. 3 1/2 in. diam. 37/6 each.  
 I.T.A. AERIALS, New and Boxed, 3 element, 22/6, 5 element, 27/6. CO-AXIAL CABLE, 6d. per yd. AIR SPACED, 9d.  
 GERMANIUM CRYSTAL DIODES, 1/-, 10/- per doz.  
 HEADPHONES, Moving iron, low impedance, 8/-, high, 9/-.  
 Bal. auto. low, 10/-, high, 15/-. Moving coil, low only, 10/- pair.  
 VOLUME CONTROLS LONG SPINDLE MIDGET, 10K to 2 Meg. Less switch, 3/-. D.P. switch, 4/6.  
 CONDENSERS, Twin Gang .0005 Standard 5/6. Midget, 6/6.  
 VERNER SYNCHRONOUS A.C. MOTORS, 200/250 v. for clocks, models, etc., 12/6 ea.  
 KEY SWITCHES, D.P.C.O. each way, 2/6 ea.  
 RELAYS, High speed, 1,000+1,000 ohms, plat. cont., 7/6.  
 ELECTROLYTICS, Canned, 20+20 mfd. 450 v., 2/6 ea. 25' doz.  
 12-WAY PVC CABLE, Screened and PVC Cov., 2/6 vd.  
 V.A.R. SLIDERS, 10 ohm 30 w., for chargers, trains, etc., 3/- ea.  
 VALVES, All valves tested before despatch on MULLARDS latest ELECTRONIC TESTER.

|      |     |      |     |       |      |       |     |          |      |
|------|-----|------|-----|-------|------|-------|-----|----------|------|
| 1L4  | 5/- | 6D2  | 6/- | 6X4   | 7/-  | EA50  | 1/6 | EY51     | 5/6  |
| 1T4  | 6/6 | 6F1  | 7/6 | 6X5   | 7/-  | EAB80 |     | EY51     | 8/-  |
| 1U4  | 6/- | 6F6  | 7/6 | 8D2   | 4/6  |       |     | P61      | 4/-  |
| 3A4  | 6/- | 6F13 | 7/6 | 9D2   | 5/-  | EB41  | 7/6 | PEN45    | 7/6  |
| 5Z4  | 9/- | 6J5  | 6/- | 10E1  | 7/6  | ES91  | 5/6 | SP46     | 7/-  |
| 4D1  | 4/- | 6J8  | 6/- | 12A6  | 7/6  | ECH42 | 8/- | SP61     | 4/-  |
| 6AG5 | 5/- | 6J7  | 6/- | 12AH8 | 8/-  | ECL80 | 9/- | SP81     | 4/-  |
| 6AL5 | 5/- | 6K7  | 4/6 | 12AT7 | 6/-  | EF36  | 5/- | VR150/30 |      |
| 6AM5 | 5/- | 6L6  | 6/6 | 12AU7 | 7/-  | EF50  | 3/6 |          | 5/-  |
| 6AM6 | 6/- | 6SA7 | 6/- | 12AX7 | 7/-  | EF50  | 5/- | UL84     | 9/-  |
| 6AC5 | 6/- | 6SC7 | 4/6 | 12BH7 | 10/- | EF57  | 9/- | VCR97    |      |
| 6AU6 | 7/- | 6SJ7 | 5/- | 12SH7 | 5/6  | EF99  | 5/6 |          | 15/- |
| 6BA6 | 8/- | 6SK7 | 5/- | 12SJ7 | 6/6  | EF80  | 9/6 | VCR138A  |      |
| 6BE6 | 5/6 | 6SL7 | 6/- | 12SK7 | 5/-  | EF61  | 6/- |          | 25/- |
| 6BH6 | 5/- | 6SN7 | 7/- | 15D2  | 6/6  | EF92  | 7/- |          | 25/- |
| 6BW6 | 6/6 | 6T5  | 6/6 | 50C5  | 10/- | EL32  | 5/- |          | 25/- |
| 6C4  | 5/- | 6V6  | 6/6 | 807   | 6/-  | EL91  | 5/6 |          | 25/- |


OBsolete TYPES, LARGE STOCKS. ENQUIRIES INVITED. SECONDHAND VALVES, YOUR CHOICE, £1.0.0 for EIGHT PL81, ECL80, 6C4, 6AM6, 6AG5, 6J6, EF50, 6BE6, 3A4, PCF80, EF80, SP61, P61, 6J5, PY80, PY82, PCC84, Z77, 6AL5, 6K7, 6SJT, EL32, EF42, 6D2.

## BIET

## HUGGETT'S LIMITED

2-4 PAWSONS ROAD, WEST CROYDON

# TELETRON TAPEJAK

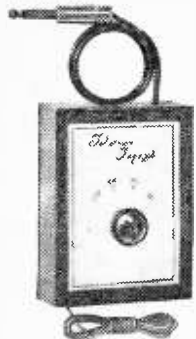

The first Transistorized Radio Tuner, specially designed for use with Tape Recorders. Converts your Recorder to a high quality Radio receiver. Direct Recording on Tape.  
5" x 3 3/4" x 1 1/2".

- \* High sensitivity.
- \* Twin Tuned Circuits.
- \* Pre-setting for M.W. Programmes.
- \* Fixed Tuned for 1,500 M.
- \* Switched programme selector.
- \* Self powered.

Tested and ready for use.  
**£5.9.0. BATTERY EXTRA.**

**THE TELETRON CO. LTD.,**  
112B, Station Rd., London, E.4  
Phone : SIL. 0836.

# LYONS RADIO LTD.

Dept. M.P., 3, GOLDHAWK ROAD,  
SHEPHERD'S BUSH, LONDON, W.12  
Telephone : SHEpherd's Bush 1729

**METAL RECTIFIERS.**—Selenium, full-wave bridge type, 12 v. 1 A. PRICE ONLY 4/3, post 1/-.

**TRANSFORMERS.** Pri. 200/250 v. Sec. tapped 3.5, 9 and 17 v. for providing, used with rectifier, 2, 6 or 12 v. D.C., respectively PRICE ONLY 10/6, post 1/6.

**RECTIFIER AND TRANSFORMER** together. 15/8 post paid. Wiring diagram supplied.

**SUPPLY UNITS.** No. 19. Mk. 2. Rotary transformer units in metal cases. 10 x 8 x 6 in. Input 12 v. D.C. Output smoothed D.C. 500 v. at 50 mA. and 275 v. at 110 mA. Supplied with input and output plugs. PRICE ONLY 45/-, carriage 7/6.

**I.F.F. UNITS.** Contain a wealth of useful components including relays and 10 valves (6-6SH7, 2-7193, 2-6H6) and a rotary converter rated at 18 v. D.C. input for 480 v. D.C. output. With 12 v. D.C. input, 250 v. D.C. at 80 mA. output is obtained. One end of converter is fitted with blower fan with gear box at other end. Both can easily be removed if desired. Two driving shafts protrude from gear box and rotate at approx. 3 and 16 r.p.m. Input or at half this speed for 6 v. input. A real snip for model maker or experimentalist. PRICE ONLY 27/6, carriage 5/-.

**SWITCHES.** Bulgin pattern, single hole fixing. Double pole change-over (brand new condition), 250 v. 1 A. with slotted dolly. 3 for 6/6, 6 for 11/-, doz. for 21. Ex equipment. Single pole, 250 v. 3 A., 6 for 5/6, doz. for 9/6. Double pole, 250 v. 1 A. 6 for 7/-, doz. for 11/6. Substantial reductions for orders of 50 and more.

**HEAVY-DUTY L.T. TRANSFORMERS.** Pri. 180/230 v. 50 cps. Sec. 4.2 v. at 10 A. twice. Ex Govt. as new. PRICE ONLY 17/6, post 3/6.



## NEW PRIMAX B60 watts and PRIMAXA 100 watts

Both Soldering guns with Spotlights

Ready for use in 6 secs., and you see what you solder.

PRIMAX B60 w. PRIMAXA 100 w.

**80/8**

Post Free

**104/8**

Post Free

The Primax B60 and the Primaxa 100 are supplied in all voltages.

One year's Guarantee except on bits and lamps  
Sole Distributors

**S. KEMPNER LTD.**  
29, Paddington Street W1  
Telephone HUNTER 0755

## WIRING ACCESSORIES

Return of Post Service. Lowest Possible prices consistent with high quality. Money back guarantee.

| PVC Cable Flat Twin with E. 3 Core | 1.044    | 3.029    | 3.036    | 7.029    |
|------------------------------------|----------|----------|----------|----------|
|                                    | £2. 1. 8 | £2.15. 1 | £2.19. 4 | £2.19. 0 |
|                                    | £2.14. 2 | £2. 8.11 | £3.19. 0 | £4.10. 9 |
|                                    | £3.18. 5 | £4.10. 9 | £5.10.10 | £6.11. 8 |

### TRS CABLE

|       |          |          |          |
|-------|----------|----------|----------|
| 1.044 | £2. 3. 5 | £2.13.11 | £3. 0.10 |
| 3.029 | £2.15. 9 | £3. 6.10 | £4. 5. 4 |
| 3.036 | £3.15. 2 | £4. 8. 5 | £5. 8. 7 |
| 7.029 | £4.13.10 | £5.18. 2 | £6.18. 7 |

Prices per 100 yds. All sizes stocked. Supplied in 25, 50, 75 or 100 yd. lengths. 7.029 and above cut to length—no cutting charge. Carriage paid on all orders over £2. Full range of accessories available. Send for complete lists.

## ELECTROSURE 118, FORE STREET, EXETER

Phone : Exeter 56687.

## H.A.C. SHORT-WAVE EQUIPMENT

Noted for over 25 years for S.W. Receivers and Kits of Quality.

Improved designs with Denco coils. As supplied to Technical Colleges, etc. One-Valve Kit, Model "C." Price 25/- Two-Valve Kit, Model "E." Price 50/- New Addition: Model "K." Super sensitive "All Dry" Receiver. Special incl. price. Complete Kit, 77/-.

All kits complete with all components, accessories and full instructions. Before ordering call and inspect a demonstration receiver, or send stamped, addressed envelope for descriptive catalogue and order form.

"H.A.C." SHORT-WAVE PRODUCTS (Dept. TH), 11, Old Bond Street, London, W.1.



## TRANSISTOR AUDIO AMPLIFIERS

**250 mW** Class B push-pull using GET114 transistors, operating from a 6V supply. Class B single-ended push-pull (Transformerless) using GET114 transistors, operating from a 9V supply.

**500 mW** Class B push-pull using GET114 transistors operating from a 6V supply. Class B single-ended push-pull (transformerless) using GET114 transistors, operating from a 9V supply.

**1 W** Class B push-pull using GET114 transistors, operating from a 6V supply. Class B single-ended push-pull (transformerless) using GET114 transistors, operating from a 12V supply.

**2 W** Class B push-pull using GET116 transistors, operating from a 12V supply.

**3 W** Class B single-ended push-pull (transformerless) using GET115 transistors (mounted on 3" x 3" fins) operating from a 12V supply.

These are a selection from the range of audio amplifier circuits using G.E.C. transistors. For details of any of these circuits or information on the wide range of G.E.C. transistors, please write to :

### G.E.C. SEMICONDUCTOR DIVISION

School Street, Hazel Grove,  
STOCKPORT, CHESHIRE.


## Look at the NEW MOTEK K10 TAPE DECK

☆☆☆☆☆

TAPE DECK

Incorporating many new  
features and a greater  
frequency response

21GNS

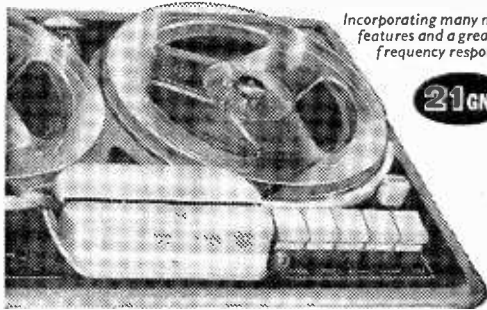

Now restyled in two tones of grey—you must see the new, attractive Motek K.10.

★ Enlarged drive wheel on the rev. counter ensures accurate tape positioning.


★ Non-slip push buttons.

★ Frequency response better than 40 c/s—12,000 c/s at 7.5" per sec. with extremely low hum pick-up.

Please send for brochure More and more manufacturers  
of K.10 are installing Motek Tape  
Patents pending. Decks in their recorders.

MODERN TECHNIQUES  
Widmore, 24-ect., London, N.19 Tel: AHChway 3114

## BUILD YOUR OWN

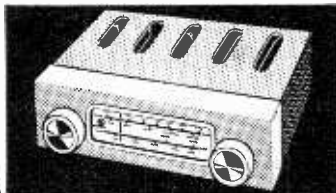

## MAYKIT TRANSISTORISED CAR RADIO

- EASY TO BUILD ON PRINTED CIRCUIT.
- 5-VALVE SUPERHET WITH TRANSISTOR.
- STANDARD 7 x 2" for 12 VOLT BATTERY.

First tested Do-it-Yourself Car Radio, acclaimed by the Press. Uses low voltage valves and printed circuit. Negligible "fade," no buzz, only 1.5 amp. consumption. Complete with full instructions, diagrams, etc. Servicing and free advice on request. Also Jason Car Radios. Send 3/6 for Car Radio booklet.

Can be built for **£13.10.0** plus 5/- post./ins. and pack.  
Cash with order or BUY-AS-YOU-BUILD details and leaflet.

Dept. N., MAYRA ELECTRONICS LTD.  
118 Brighton Rd., Purley, Surrey. Tel.: BYW 1263.

## TRANSISTOR SUPPLIES BARGAINS

Teletron Transidyne Pocket Transistor Set. All parts £11/10/- (Post 2/6).  
Mini 7 Transistor Pocket Receiver. Complete kit, £9/2/6 (post 2/6).

Red Spots, 5/-; White Spots, 7/6;  
Green/Yell., 5/9; Ediswan XB104,  
8/6; XA104, 16/-; XA103, 14/-.

Moving Coil Earpiece (use as miniature speaker), 5/-.

Super Coax, 6d. yard. Var. Air Condenser, 365 p.f., 3/-; Subminiature Electrolytics (15 volt), 2, 5, 8, 25, 50  $\mu$ f., 3/-; Submin. Transformer Interstage, 5-1, 8-1, 7/6.

Power Packs: 200/250 v. in.; 300 v. 200 mA. and 12 v. A.C. out., 50/- (carr. 7/6). 6v. D.C. in., 120 v. 60 mA. (vibrator) out., 17/6 (carr. 5/-). Receiver 78, 35/- (carr. 5/-).

TERMS—Cash with order. Post extra. Morco Reflex Circuit—Best 2 Transistor. Send 8d. stamps for our Notes.

## MORCO EXPERIMENTAL SUPPLIES

8 & 10, Granville Street, Sheffield, 2  
Tel.: 27461

## Morse Code operating . . . . . . as a PROFESSION

45 years of teaching Morse Code is proof of the efficiency of the Candler system.

Send 3d. stamp for Payment Plans  
and full details of all Courses.

CANDLER SYSTEM CO. Dept. 51.O  
52b, Abingdon Road, London, W.9.  
Candler System Co., Denver, Colorado, U.S.A.


## BENSON'S BETTER BARGAINS

INDICATORS, type 277, with lin. C.R.T., 4/VR91, 2 VR92, 37/6 (p.p. 3/6). Type 101, with VCR530 66 lin. Blue, magnetic. Octal base, and 2/EB91, 2/EP91, 2/R10; new com. 30/- (Post 3/6). Type 1, with VCR263, 2/EP92, 5/4J6, 1/8V6, 1/8V51, 2/EB91, 3/EP91; with RF EHT Generator and 28 kcs. xtal. 45/- (Rail 7/6). Type 97 with VCR17, 10 valves, 30/- (Rail 7/6). HEAD-PHONES, C.R. with carbon breast-mic., 10/8. C.R. with Noise limiter assemblies, with valve, 3/8. NEW M.C. METERS, 3 1/2 in. round bush, 50  $\mu$ A., 70/-; 100  $\mu$ A., 65/-; 1 mA., 55/-; 2 mA. (rectified), 45/-; 2 1/2 in., 1 mA., 22/8; 2 in., 100 mA., 200 mA., 300 mA., each, 8/6. 2 1/2 in., 20 v. A.C. 8/6; 2 in., 40 v. 8/6; 300 v. A.C. 2 1/2 in., 15/-; 2 in. square, 150 A.-150 A. (dies shunt), 10 mA., 7/6. VIBRATORS, Mallory G634C 12 v. 4-pin, 7/6. R1155B, good condition, tested, with handbook, £7/10/- (Rail 10/-). SCR522 Modulation or Driver Trans., either 7.8. CONVERTERS (ROTARY), 24 v. 1b.C. to 50 v. A.C. 4 A., 40/- (Rail 7/6). MORSE TRAINER SET with buzzer and key wired for 4 1/2 v. battery, 8/6. DRIVES: slow-motion Admiralty 200:1 ratio, geared 0-100, 5/6. R1155 S.M. "N" type, new, 10/8. DYNAMOTORS, Type 2 A. Input 12 v. Outputs 300 v., 240 mA., 150 v., 10 mA., 6 v., 5 A. Filtered, cased, 25/- TRANSFORMERS, vibrator, 11 v. to 285 v., 7/6. Morse Key, covered with plng. 5/6. Potentiometers, miniature wirewound, 6  $\Omega$ , 100  $\Omega$ , 1k or 2k, each 1/-; CROKES, I.F. 10H 200 mA., 8/6; Potted 10H 100 mA., 7/6; C-5H 400 mA., 10/6. SWITCHES, toggle, U.S.A., DPDT, 16. METAL RECTIFIERS: 240 v., 100 mA., 4/-; 240 v., 30 mA., 3/6; 600 v., 20 mA., 5/6; 240 v., 80 mA., 5/6; 30 mA., 1,000 v., 7/6. Mic. inserts, G.P.O. carbon, 2/8. bal. armature type, 2/8. VALVE HOLDERS, U.S.A. Octal, doz., 4/-; POTENTIOMETERS, 100 k or 500 k, new, doz., 5/-; ACCUMULATORS, 2 v., 4AH 2 1/2 x 1 1/2 x 3 1/2 in., 7/8. TX. VAR. CONDENSERS, 2kV. test; 50 or 100 p.f., 7/6. MONITOR Type 56 (2 units—(Oscilloscope and power unit), £5/13/- (rail 20/-). LIST AND ENQUIRIES: N.A.B. please, Terms, C.W.O. Postage extra. Immediate despatch.

Callers and Post: W. A. BENSON (PW), 136  
Rathbone Road, Liverpool, 15. SEE 6853  
Callers: SUPERADIO (Whitechapel), LTD., 116,  
Whitechapel, Liverpool, 2. HOY 1130
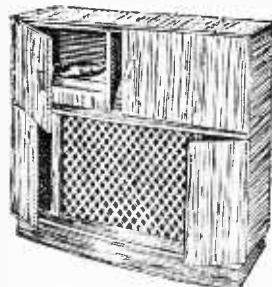
## GABINETS & HI-FI EQUIPMENT

We can supply any Cabinet to  
your own specification.



## The Continental £29.10.0

This is only one example taken from our extensive range of stock cabinets. Write for our NEW 24 page fully illustrated catalogue on:  
THE LARGEST RANGE OF CABINETS IN THE COUNTRY. Equipment is also our speciality and we now offer, in a novel book form:  
A NEW EQUIPMENT COMPARATOR Illustrating our range of radio chassis, speakers, tape decks, single players and autochangers.  
SEND TODAY for a copy of these two books, which are absolutely FREE.

## LEWIS RADIO

120 (PW129) Green Lanes, Palmers Green  
London, N.13. BOWes Park 1155/6  
(Nr. The Cock Tavern)

# RECO KITS



**"RECO" MIDDY ONE TRANSISTOR KIT**

(M/L or M/S WAVES)

4 3/4 in. x 3 1/2 in. x 1 1/2 in. Vari Q Ferrite Rod Aerial.

Variable Sensitivity Control. Sonotone Earpiece. Complete with Ediswan Transistor £2.

**"RECO" PUSH-PULL FIVE (M/L & Trawler Band)**

Indoors or outdoors this brilliant radio brings Home, Light and Continental Stations to your finger-tips. 3in. Speaker. Ferrite Rod Aerial. MULLARD OC45 R.F. Stage and 4 Ediswan Transistors. Push-Pull Output Stage. Gleaming Pale Blue Polystyrene Case with Contrasting Speaker Grille in Red. Complete Kit: M/W & Trawler Band £67.6. M/W, L/W & T.B. £6.10.0. P/P 2/6. Case size as Transigen Three.

**"RECO" TRANSIGEN THREE (M/L & Trawler Band £3.17.6. M/W & T.B. only £3.15.0.)**



Size only 6 1/2 in. x 4 1/2 in. x 1 1/2 in. Case as PP5. Entirely self-contained (no external aerial required).

High Q Ferrite Rod Aerial R.F. Stage with MULLARD OC45 followed by 1st GRADE Ediswan Transistors. On Test: Third, Home, Light and after dark Radio Luxembourg, A.F.N. and many others. The Prototype was tested at approx. 50 miles from LONDON. COMPLETE KIT with easy build diagrams and B.A. Reproducer which, with a reasonable signal, gives very clear reproduction; it may also be used as personal phone. We can supply a 3in. Speaker (which fits under red Spkr. grille) for good reception areas. 25/-, X/mr. 6/6.

**"RECO" TRANSIGEN TWO (M/L Waves) Case as PP5**

A fine kit with Ediswan Transistors and Ferrite Rod Aerial. For good reception areas. Complete Kit with Personal Phone, 59/6. P/P 2/6. Med. Waves only 56/6, P/P 2/6.



**"RECO" PUSH-PULL FOUR**

(M/L Waves with two S.W. Coils FREE).

Push-Pull Output Stage. 3in. Speaker. 4 EDISWAN Transistors. Gleaming Pale Blue Polystyrene Case with Speaker Grille in red. Size as PP5. COMPLETE KIT M/Waves 99/6; M/L Waves £53.6. P/P 2/6.

**AFTER SALES SERVICE**

Circuits and Price List for the above kits 2/6.

**RADIO EXCHANGE CO.**  
27 HARPUR ST., BEDFORD

Telephone 2367.

Closed 1 o/c Saturdays.

# FIRST-CLASS RADIO COURSES...

**GET A CERTIFICATE!**

**QUALIFY AT HOME—IN SPARE TIME**

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification. Prepare for YOUR share in the post-war boom in Radio. Let us show you how!

**FREE GUIDE**

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success-compelling qualifications as A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.C. Radi Amateurs, Exams., Gen. Cert. of Educ., London B.Sc. (Eng.), A. M. I. P. E., A.M.I.Mech.E., Draughtsmanship (all branches) etc., together with particulars of our remarkable Guarantee of **SUCCESS OR NO FEE**

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

**FOUNDED 1885—OVER 150,000 SUCCESSSES.**

**NATIONAL INSTITUTE OF ENGINEERING**

(Dept. 461), 148, HOLBORN, LONDON, E.C.1.

S. Africa: P.O. Box 8417, Jo'burg. Australia: P.O. Box 4570, Melbourne

## B.B.C. - I.T.V. - F.M. AERIALS



**B.B.C. (BAND 1).** Telescopic loft, 19/6. External. S.D. 26/3.

**I.T.V. (BAND 3).** 3 Element loft array, 24/-, 5 Element, 39/6. Wall mounting, 3 Element, 33.9. 5 Element, 41/3.

**COMBINED B.B.C. + I.T.V.** Loft 1+3 Element, 41.3. 1+5 Element, 48.9. Wall mounting, 1+3 Element, 56/3. 1+5 Element 63/9. Chimney and mast mounting units also available.

**F.M. (BAND 2).** Loft "H," 28/-, 3 Element loft, 52/6. S/D loft, 12/6. External S/D 26/3. State channel when ordering. C.W.O. or C.O.D. P.P. 2/6. Coaxial cable, 8d. yd. Coaxial plugs, 1/3. Send 6d. stamps for illustrated lists.

**K.V.A. ELECTRONICS (Dept. P.W.)**  
38, Godstone Road, Kenley, Surrey

# SHORT WAVE KITS

H.A.C. were the original suppliers of SHORT-WAVE RECEIVER KITS for the amateur. Over 10,000 satisfied customers.

PRICES FROM 25/- TO 77/-.

**POST THIS COUPON NOW!**

To: H.A.C. Short-Wave Products, 11, Old Bond Street, London, W.1. Please send me FREE and without obligation your 1959 literature.


NAME .....

ADDRESS .....

# CABY
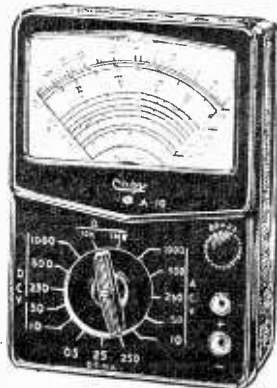
## SUPREME TEST INSTRUMENTS

Solve your problems with speed and accuracy.



Meter A-10

**MEASUREMENT RANGES:**

D.C. volt (sensitivity 2,000  $\Omega$  per volt), 10v., 50v., 250v., 500v., 1,000v.  
A.C. volt (sensitivity 2,000  $\Omega$  per volt), 10v., 50v., 250v., 500v., 1,000v.  
Resistance  $\Omega$ : 10K ohm, 1 megohm.  
D.C. Current: 0.5 mA., 25 mA., 250 mA. Will also measure decibels.  
Size of meter: 5 1/2 in. x 3 1/2 in. x 1 1/2 in. Weight of meter: 1 lb. 1 oz. (Freshly imported.)  
PRICE: (Inclusive of batteries, inst. book and test prods.)

£4.17.6 plus 2/- P. & P.



Meter B-20

**MEASUREMENT RANGES:**

D.C. volt (sensitivity 10,000  $\Omega$  per volt), 0.5v., 2.5v.  
D.C. volt (sensitivity 4,000  $\Omega$  per volt), 10v., 50v., 250v., 500v., 1,000v.  
A.C. volt (sensitivity 4,000  $\Omega$  per volt), 10v., 50v., 250v., 1,000v.  
Resistance  $\Omega$ : 2K ohm, 200K ohm, 2 megohm, 20 megohm.  
D.C. Current: 100 microamp, 2.5 milliamp, 25 milliamp, 250 milliamp.  
Will also measure decibels.  
Size of meter: 5 1/2 in. x 3 1/2 in. x 2 1/2 in. Weight of meter: 1 lb. 8 oz. (Freshly imported.)  
PRICE: (Inclusive of batteries, inst. book and test prods.)

£6.10.0 plus 2/- P. & P.

Orders to:

**SERVICE TRADING CO.**

9, Little Newport Street, London, W.4.2  
Trade enquiries only to sole importers:  
**HOUSEHOLD ELECTRIX LTD.**  
47-48, High Street, Kingston-on-Thames

# IDEAL PRESENTS: BUY NOW FOR CHRISTMAS

SEE BACK PAGE

SEND FOR NEW FREE VALVE, TRANSISTOR, CRYSTAL AND COMPONENTS LISTS

## TRANSISTOR CRYSTAL MARKER (5.5 Mc/s to 9 Mc/s)

Uses new 25 Mc/s transistor, high efficiency oscillator. Complete with 1-FT243 crystal between 5.650 Mc/s and 8.650 Mc/s.

30/- P.P. (7 to 7.3 and 8 to 8.3 2/6 extra)  
1/- FREE LIST AND DIAGRAM

## 25 Mc/s SURFACE BARRIER TRANSISTOR

SB305 15/- each.  
OCI70, 70 Mc/s., 50/- each.  
Other types available.

## CAR RADIO 2-watt Amplifier

A permanent power transistor stage complete with 7 x 4 in. speaker. May be used with any battery portable using a 3-ohm or 15-ohm speaker. Use it with the "B." Complete set of parts ... 65/- P.P. 2/6  
Unit built up and tested... 77/6 P.P. 2/6  
(See "RC," December, 1959)  
SEND FOR FREE LIST.

## RF AND IF GENERATOR

Pocket size Test Unit. Harmonic output 450 kc/s to 2 Mc/s. Ideal for aligning all Receivers. Size 2 1/2 x 1 1/2 x 1 in. All Components ... 25/- P.P. 1/-  
SEND FOR FREE LIST AND DIAGRAM.

## TOP BAND TRANSISTOR TRANSMITTER

Pocket size 150 to 160 metre Transistor Transmitter. Range up to 100 ft. on 3 ft. aerial. Ideal for Short Range Communication, Car to Car, etc. Complete Set of Parts ... 57/6 P.P. 1/6  
MICROPHONE INPUT: SEND FOR FREE CIRCUIT AND LIST.  
See "RC," Jan., 1960.

## TYPE 38 TRANSMITTER/RECEIVER

Complete with 5 valves. In new condition. These sets are sold without guarantee, but are serviceable. 22/6 P.P. 2/6  
Headphones 7/6 pair, Junction Box 2/6, Throat Mike 4/6, Canvas Bag 4/-, Aerial Rod 2/6.

## V.H.F. TRANS/RECEIVER TYPE 1986

★ 9.72 MC/S IF ★ 10-CHANNEL CRYSTAL CONTROLLED  
★ 23 KC/S BANDWIDTH ★ 124.5 to 156 MC/S COVERAGE

| Sub-units               | Type | With valves | Less valves | P.P. |
|-------------------------|------|-------------|-------------|------|
| TRANSMITTER ...         | 81   | 60/-        | 25/-        | 2/6  |
| RECEIVER ...            | 114  | 25/-        | 7/6         | 2/6  |
| IF Amplifier ...        | 476  | 32/6        | 12/6        | 2/6  |
| Modulator ...           | 105  | 20/-        | —           | 2/6  |
| 24v. Rotary unit ...    | 3    | 15/-        | —           | 2/6  |
| 10-way Control unit ... | 382  | 6/-         | —           | 9d.  |

All the above are in absolute new condition. Full circuits available. 1/9 post free.

## V.H.F. TRANS/RECEIVER TYPE TR1920

★ 9.72 MC/S IF ★ 4-CHANNEL CRYSTAL CONTROLLED  
★ 40 KC/S BANDWIDTH ★ 100 to 120 MC/S COVERAGE


Unit complete with 21 valves: crystal; 24 volt rotary power unit, etc., in metal case. In new condition with full circuit diagram.  
£6.10.0. Carriage 10/6. Circuits separately, 1/9 post free.

## R.C.A. VALVE-VOLTMETER

Type 165-A  
D.C. ELECTRONIC VOLTMETER  
6-Ranges 3-1,000 Volts.  
Input Res. 11,000,000 ohms.  
Sensitivity 3,666,666 o.p.v. on 3V scale.  
A.C. VOLTMETER  
5-Ranges 0-1,000 volts.  
Sensitivity 1,000 o.p.v.  
ELECTRONIC OHMMETER  
6-Ranges from 0.1 ohms to 1,000 Megohms.  
Movement 200 Microamperes D.C.  
Accuracy ± 2%  
110/250 v. A.C. input.

BRAND NEW  
With Instruction Book and Test Prods.  
£12.10.0 P.P. 3/6

LIMITED STOCKS—BUY NOW

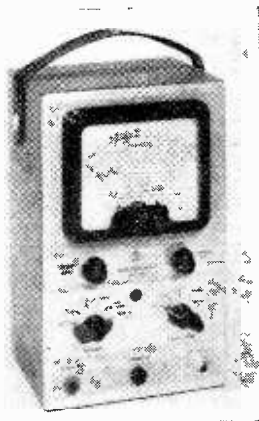

## AC/DC PORTABLE RADIO

- ★ 5 valve superhet
- ★ Built-in frame aerial
- ★ Size 10 in. x 10 in. x 4 in. deep
- ★ All Marconi valves
- ★ Med., long and short waveband OR Med. and two short wavebands
- ★ Gram. sockets (for crystal or magnetic pick-ups)
- ★ 7 in. x 4 in. elliptical speaker
- ★ Slow motion tuning
- ★ Ideal for a radiogram

ONLY £7.12.6 post 7/6

Portable polished cabinet ... 27/6  
Super portable rexine cabinet ... 37/6



## "373" MINIATURE IF STRIP 9.72 Mc/s

The ideal F.M. conversion unit as described in "P.W." April/May, 1957. Complete with 6 valves, three EF91s, two EF92s and one EB91, I.F.T.s, etc., in absolutely new condition. With circuit and conversion data.

12/6 (less valves) 37/6 (with valves)  
Postage and packing 2/6 (either type)

## TRANSMITTER/RECEIVER

Army Type 17 Mk. II. Complete with Valves, High Resistance Headphones, Hand Mike and Instruction Book and Circuit. Frequency Range 44.0 to 61 Mc/s. Range approximately 3 to 8 miles. Power requirements: Standard 120 v. H.T. and 2 v. L.T. Ideal for Civil Defence and communications.

BRAND NEW 45/- P.P. 5/-

44-61 Mc/s calibrated wavemeter for same, 10/- extra.

**HENRY'S (RADIO) LTD. (Dept. P.W.D.)** 5, HARROW ROAD, EDGWARE ROAD, PADDINGTON, LONDON, W.2.

Opposite Edgware Road Tube Station. PADDington 1008/9.

OPEN MONDAY to SAT. 9-6. THURS. 1 o'clock.



# Practical Wireless

## BLUEPRINT

## SERVICE

ALL OF these blueprints are drawn full-size and although the issues containing descriptions of these sets are now out of print, an asterisk in the list below denotes that constructional details are available free with the blueprint.

The index letters which precede the Blueprint Number indicate the periodical in which the description appeared. Thus PW refers to PRACTICAL WIRELESS; AW to *Amateur Wireless* and WM to *Wireless Magazine*.

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to

PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

### SPECIAL NOTE

THE following blueprints include some pre-war designs and are kept in circulation for those constructors who wish to make use of old components which they may have in their spares box. The majority of the components for these receivers are no longer stocked by retailers.

| Title                                     | Number | Price |
|---|--------|-------|
| <b>CRYSTAL SETS</b>                       |        |       |
| Junior Crystal Set ... ..                 | PW94*  | 2/-   |
| Dual-wave Crystal Diode ... ..            | PW95*  | 2/6   |
| <b>STRAIGHT SETS</b>                      |        |       |
| Battery Operated                          |        |       |
| Modern One-valver ... ..                  | PW96*  | 2/6   |
| All-dry Three ... ..                      | PW97*  | 3/6   |
| Modern Two-valver ... ..                  | PW98*  | 3/6   |
| <b>SUPERHETS</b>                          |        |       |
| Mains Operated                            |        |       |
| A.C. Band-pass Three ... ..               | PW99*  | 4/-   |
| A.C. Coronet-4 ... ..                     | PW100* | 4/-   |
| A.C./D.C. Coronet ... ..                  | PW101* | 4/-   |
| <b>MISCELLANEOUS</b>                      |        |       |
| The PW 3-speed Autogram ... ..            | —*     | 8/-   |
| The PW Monophonic Electronic Organ ... .. | —      | 8/-   |
| <b>TELEVISION</b>                         |        |       |
| The PT Band III Converter ... ..          | —*     | 1/6   |

| Title                               | Number | Price |
|-------------------------------------|--------|-------|
| A.C. Fury Four ... ..               | PW20*  | 2/6   |
| Experimenter's Short Wave ... ..    | PW30a* | 2/6   |
| Midget Short Wave Two ... ..        | PW38a* | 2/6   |
| Band-Spread Three (Battery) ... ..  | PW68*  | 2/6   |
| Crystal Receiver ... ..             | PW71*  | 2/-   |
| Signet Two (Battery) ... ..         | PW76*  | 2/6   |
| Simple S.W. One-valver ... ..       | PW88*  | 2/6   |
| Pyramid One-valver ... ..           | PW93*  | 2/6   |
| BBC Special One-valver ... ..       | AW387* | 2/6   |
| Short-Wave Two ... ..               | AW429* | 2/6   |
| Short-Wave World Beater ... ..      | AW436* | 3/6   |
| Standard Four Valve S.W. ... ..     | WM383* | 3/6   |
| Enthusiast's Power Amplifier ... .. | WM387* | 3/6   |
| Standard Four Valve ... ..          | WM391* | 3/6   |
| Listener's 5-Watt Amplifier ... ..  | WM392* | 3/6   |
| <b>TELEVISION</b>                   |        |       |
| Argus Television Receiver ... ..    | —*     | 3/-   |
| Simplex Television Receiver ... ..  | —*     | 3/6   |

### QUERY COUPON

This coupon is available until 3rd December, 1959 and must accompany all queries in accordance with the notice on our "Open to Discussion" page.

PRACTICAL WIRELESS, DECEMBER, 1959



# DO-IT-YOURSELF! NO EXTRAS NEEDED: FREE LISTS ON ANY MODEL: COMPLETE AFTER SALES SERVICE

All Components Guaranteed.

**PRICE REDUCTION! NOW IN ITS 3rd YEAR! FIRST AND BEST!**

## "THE TRANSISTOR-8"

Push-Pull Portable Superhet

- ★ Tunable over medium and long wavebands.
- ★ 250 mW output push-pull.
- ★ 8 Ediswan Transistors; Transistor holders.
- ★ Internal Ferrite aerial.
- ★ Highly sensitive and selective.
- ★ Good quality 7 x 4 in. speaker.
- ★ Components identified and carded.
- ★ Pre-drilled cabinet and chassis.
- ★ Easy-to-follow layout diagrams.
- ★ Use it as a car radio

Complete set of parts including cabinet and all components.

**£10. 19. 6.**

P. & P. 2/6.

All parts sold separately. FREE BOOKLET.



Car radio components. 8-: 325 mW version with matched XC101's, £11.11.6. P. & P. 2/6. A.V.C., 4/3.

Size 9 x 7 x 3 1/2 in. Weight 4 lb.

### MAJOR-2

(Two-transistor Pocket Radio)



**69/6** COMPLETE  
P.P. 1/6.

- ★ 4-stage reflex!
- ★ Medium wave: tunable!
- ★ Very sensitive!
- ★ No aerial or earth!
- ★ Complete layout!
- ★ Over 6 months on one battery.
- ★ 4 1/2 x 3 x 1 1/2 in.
- ★ Weight only 4 ozs.
- ★ Personal 'phone.

### RED-SPOT TRANSISTORS

**5/- EACH**

### WHITE-SPOT

**8/6**

FREE LIST ON REQUEST

### MAJOR-3



(AS DESCRIBED IN "R.C." SEPT. '59)

- ★ 5-stage Reflex Circuit.
- ★ No Aerial or Earth.
- ★ Min. Volume Control.
- ★ 3 Ediswan Transistors.
- ★ Medium Wave Tuning.
- ★ Size 4 1/2 x 3 x 1 1/2 in.
- ★ Personal 'phone.

NEW BOOKLET FREE: All components sold separately.


**GOOD RECEPTION ANYWHERE!**

COMPLETE **87/6** P.P. 1/6 FREE BOOKLET

**FANTASTIC OUTPUT, TERRIFIC RECEPTION. GUARANTEED ANYWHERE**

### SUPER 6

SIX TRANSISTOR MEDIUM AND LONG WAVES

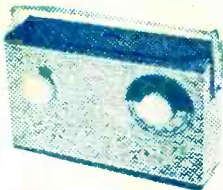

- ★ Plessey Printed Circuit
- ★ Mullard Transistors
- ★ 3-inch Speaker
- ★ Full Medium & Long Waves
- ★ Size 7 x 4 1/2 x 2 in.

Recommended by us as being the easiest to build 6-Transistor printed circuit superhet receiver ever offered.

LIMITED QUANTITY ONLY FREE LIST ON REQUEST

Complete set of parts including attractive Cabinet and all Components.

ONLY

**£9.10.0** P.P. 2/6

All parts sold separately.

### NEW "ADDON" STAGE

- ★ 2 Ediswan Transistors
- ★ Push-Pull up to 250 mW
- ★ 3 inch ELAC Speaker
- ★ Cabinet 5 1/2 x 3 1/2 x 1 1/2 in.

A unit for use with major 2 and 3 or any earpiece pocket-portable to give full speaker output; complete set of parts with cabinet.

**59/6** P.P. 1/6

FREE LIST AND DIAGRAM

### AUDIO GENERATOR

- ★ XB104 Transistor
- ★ Size 2 1/2 x 1 1/2 x 1 in.
- ★ Ideal modulator

**25/-** P.P. 1/6

Complete with all parts.

SEE OTHER ADVT. INSIDE

Ideal pocket Tester. Free Circuit.



### THE MINOR



All components with case and 'phone 49 6 pp. 1 6.

All parts sold separately. Diagram and List Free.

- ★ 3 x 2 x 1 1/2 in.
- ★ Medium wave
- ★ 3-stage reflex
- ★ Internal aerial
- ★ Smallest yet

### SIGNAL TRACER

R.F., I.F. and Audio

- ★ 2-XB104 Transistors
- ★ Headphone output
- ★ Easy to Build
- ★ Simple to use

All parts. 37/6. P.P. 1/6. Free Diagram.

**HENRY'S (RADIO) LTD. (Dept. P.W.D.)** 5, HARROW ROAD, EDGWARE ROAD, PADDINGTON, LONDON W.2.  
Opposite Edgware Road Tube Station. PADDington 1008/9 OPEN MONDAY to SAT. 9-6, THURS. 1 o'clock.