


PRACTICAL WIRELESS

MAY
1966

216

FREE INSIDE

- 1 RESISTOR COLOUR
CODE CALCULATOR
- 2 24-PAGE BOOKLET
GUIDE TO VALVE CIRCUITS

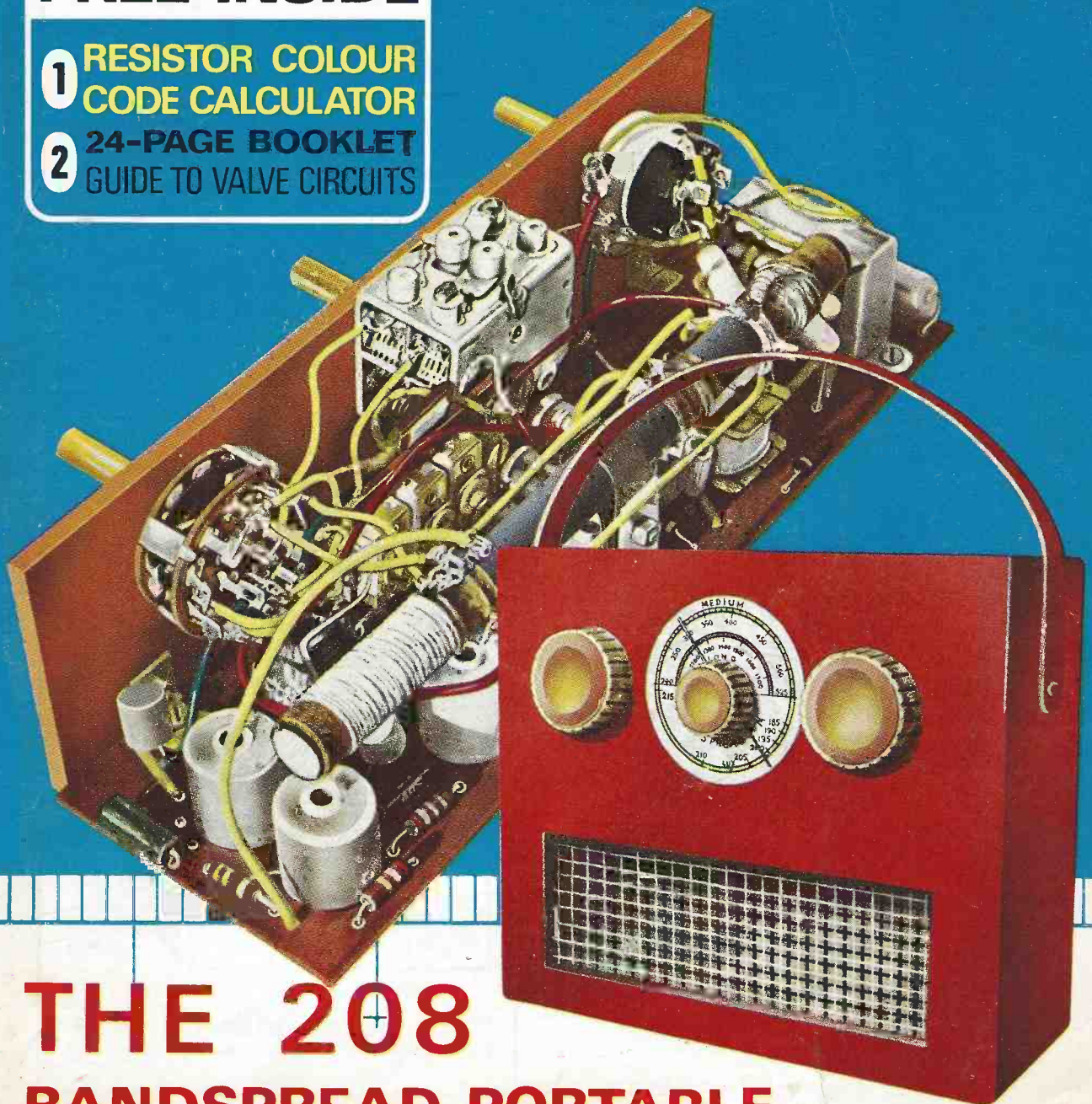


THE 208

BANDSPREAD PORTABLE



SOLDERING EQUIPMENT

FOR
THE
RADIO
CONSTRUCTOR

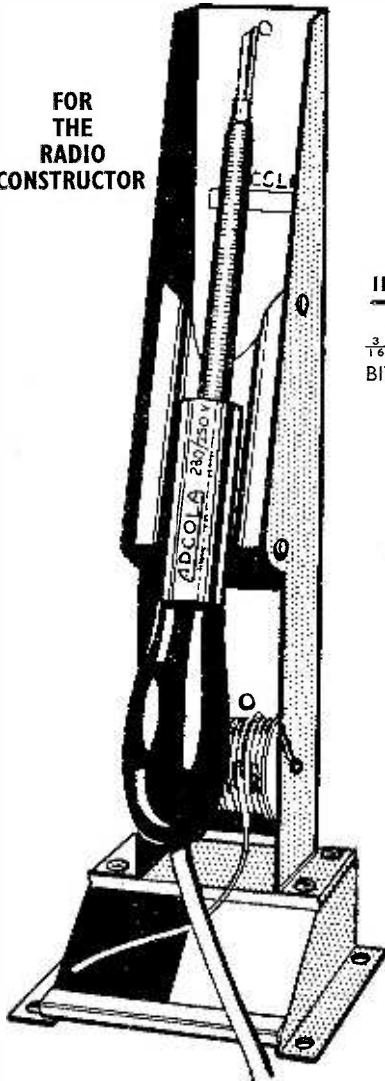

ILLUSTRATED

$\frac{3}{16}$ " DETACHABLE
BIT INSTRUMENT
(List No. 64)
IN
PROTECTIVE
SHIELD
WITH
ACCESSORIES
(List No. 700)


FOR CATALOGUES APPLY DIRECT

**ADCOLA PRODUCTS LTD.,
ADCOLA HOUSE,
GAUDEN ROAD,
LONDON, S.W.4**

Telephones:
MACaulay 3101
4272

Telegrams: "SOLJOINT" LONDON SW4

NOMBREX INSTRUMENTATION

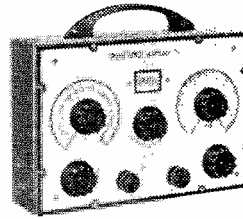

**WIDE RANGE
TRANSISTORISED
INDUCTANCE
BRIDGE 66**

- ★ 1 μ H to 100H.
 - ★ Q and tan δ .
 - ★ Meter Balance.
 - ★ Direct Scale Calibration.
- £18.6.9


Also available:

R.F. Signal Generator 27 £10.16.9
Audio Generator 63 £17.1.9
Power Supply Unit 61 £6.14.6

All Prices include Battery, Post and Packing

Wide-range Transistorised
C.R. BRIDGE—Model 62
6 Ranges: 1 Ω to 100M
1pF to 100 μ F

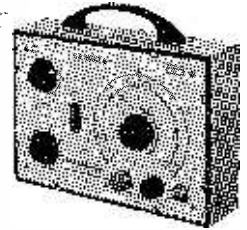- ★ Visual null indicator
 - ★ Power factor check
 - ★ Electrolytic leakage test
 - ★ Battery operated
- £9.6.9.



S.A.E. for Trade & Export Prompt
Leaflet Enquiries Invited Delivery

NOMBREX LTD INSTRUMENTS
DIVISION
Estuary House, Camperdown Ter., Exmouth, Devon



**For quick, easy
faultless
soldering**

Ersin Multicore 5-core solder is easy to use and economical. It contains 5 cores of non-corrosive flux, cleaning instantly heavily oxidised surfaces. No extra flux is required. Ersin Multicore Savbit Alloy considerably reduces the wear of copper soldering iron bits.



HANDY SOLDER DISPENSER

12 ft. of 18 s.w.g.
SAVBIT alloy in a
continuous coil, used
direct from free-
standing dispenser.
2/6 each




LOW TEMPERATURE SOLDER

Size 9 pack contains
24 ft. of 60/40 high
tin quality 22 s.w.g.
2/6 each
Size 10 pack 212 ft.
15/- each.



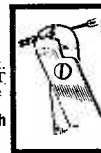**SAVBIT
SIZE 1 CARTON**
Contains approx. 30 ft.
of 18 s.w.g. SAVBIT
alloy. Also available
in 14 and 16 s.w.g.
5/- each



**BIB WIRE
STRIPPER
AND CUTTER**
Strips insulation,
cuts wire cleanly.
Adjusts to any size.
4/- each

Available from all Electrical and Hardware shops.
If unobtainable write to:

MULTICORE SOLDERS LTD.

Multicore Works, Hemel Hempstead, Herts. Hemel Hempstead 3636
M.4/B

VALUE IN VALVES

GUARANTEED 3 MONTHS BY RETURN OF POST

Satisfaction or Money Back Guarantee on goods if returned unused within 14 days. ALL VALVES ARE NEW UNLESS OTHERWISE INFORMED. FREE TRANSIT INSURANCE. POSTAGE 1 valve 8d., 2-11 1/8. Free over 12.

024	4/8	6KSQT	8/3	1487	14/6	EBC41	6/8	E240	6/8	P230	9/6
147GT	9/6	6L25	5/6	18AQS	7/8	EBC41	5/8	E241	5/8	P190	9/6
105GT	7/8	6L1	6/8	80D1	5/8	EFB80	5/8	E280	5/8	SP41	3/3
155GT	8/9	6L6	7/6	20F2	9/6	EFB89	7/9	E281	6/1	SP61	2/9
1N5GT	8/9	6L6G	6/6	20L1	16/-	EEL21	9/9	FC4	8/1	T41	6/9
1R5	4/9	6L13	7/9	30P1	9/6	EEL31	19/6	GZ32	7/8	TDD4	7/7
1S4	7/8	6L19	12/8	30P8	11/-	ECS2	4/9	KP38C	3/9	U14	7/6
2E21	5/6	6LD20	7/9	20A	13/-	ECS2	4/9	KP38	14/-	U18	7/6
344	4/1	6P25	8/6	25A6G	7/8	ECS24	9/1	KT44	4/1	U22	6/9
3A5	6/1	6P25	9/9	25L6GT	7/9	ECC40	9/9	KT45	8/6	U24	12/6
3D8	4/1	6Q 6	4/1	25Z4G	7/1	ECC41	4/9	KT61	8/6	U25	8/3
3Q4	5/1	6Q7GT	8/1	30F5	4/9	ECC42	4/9	KT63	5/9	U26	7/1
5R4GT	8/1	6SA7	5/9	30FL1	9/6	ECC43	5/9	KT66	12/1	U35	12/6
5V4G	4/1	6S47	4/9	30FL5	3/8	ECC44	7/8	KT78	8/9	U50	4/8
5Y3G	4/8	6SK7	5/1	30P4	9/6	ECC45	4/1	KT88	17/8	U107	12/6
5Y3GT	4/1	6SL7GT	5/6	30P12	7/1	ECC48	9/6	KTW61	5/9	U191	9/1
5Z4	9/1	6SN7GT	6/9	30P12	9/3	ECC49	6/1	KTW63	5/1	U281	8/6
5Z4G	7/1	6SQT	5/9	35C5	8/6	ECC49	3/3	KTZ63	7/1	U282	15/1
5Z4GT	9/6	6S4GT	8/1	35L6GT	8/1	ECH21	11/6	MU14	7/1	U301	12/6
6 30L2	9/1	6S4	6/6	35W4	6/1	ECH25	10/8	NU35	10/8	U301	8/6
6A5G	7/9	6V6GT	6/1	35Z4GT	5/6	ECH42	3/8	N78	13/1	U301	19/1
6AK5	4/3	6X4	4/6	50L6GT	8/6	ECH81	7/1	N108	13/1	UAC80	7/7
6AQ5	5/1	6X5G	5/1	80	5/1	ECH83	6/3	PC86	10/1	UAF42	7/9
6AT6	5/1	6X5GT	5/6	185BT	19/6	ECL80	6/6	PO97	7/8	UB41	6/6
6AU6	7/1	7B6	9/1	185PTA	19/6	ECL82	8/1	PC84	6/6	UB41	7/6
6AV6	6/1	7B7	6/6	30T	7/6	ECL83	14/8	PC85	6/6	UB50	6/6
6RA6	5/8	7C5	7/3	813	4/9	ECL86	10/8	PC88	11/9	UBF80	9/6
6BE6	5/6	7C6	7/6	866A	12/6	EF36	3/1	PC89	8/6	UBF89	9/6
6EG6G	15/1	7H7	5/1	954	3/6	EFG39	4/6	PO189	13/6	UB21	9/6
6EH6	5/1	7H7	14/6	955	2/3	EF40	11/1	PCF80	6/9	UC92	7/9
6EJ6	5/1	7Y4	4/8	966	2/1	EF41	3/1	PCF82	6/1	UC85	7/8
6ER7	8/6	10V1	9/1	9001	1/6	EF61	3/8	PCF84	12/1	UC81	6/6
6EW6	6/9	10C8	14/8	9002	4/9	EF80	6/9	PCF86	7/8	UC81	9/3
6W7	5/1	10F1	4/9	9003	5/6	EF85	6/1	PL82	7/9	UC82	7/8
6C4	2/3	10L1D1	14/6	ATP4	2/6	EF86	7/6	PL83	9/1	UC81	7/1
6C5	5/6	10P13	8/6	AZ31	6/1	EF89	6/9	PL84	7/3	UC82	8/1
6C6	5/6	10P14	9/6	AZ41	7/1	EF91	3/1	PL85	7/8	UC83	10/1
6C9	11/1	10V1	7/1	9001	1/6	EF92	3/8	PL86	10/6	UC81	6/6
6C9DG	17/1	12AH8	9/1	9002	4/8	EF93	3/9	PL87	17/6	UC81	14/1
6D6	3/1	12AT6	6/6	CL33	9/1	EF183	9/9	PN25	8/9	UF42	4/9
6E1	4/9	12AT7	4/9	CY31	7/8	EF184	9/6	PN45	8/6	UF80	6/6
6E6G	3/8	12AU6	9/1	DAF91	4/6	ELE32	3/8	PN46	4/6	UF85	7/6
6E13	4/8	12AU7	4/9	DAF96	7/8	ELE33	6/6	PL33	8/6	UF89	5/9
6E14	9/8	12AV6	6/9	DE91	3/1	EL34	11/6	PL36	9/6	UL41	7/6
6E15	9/8	12AX7	6/1	DF92	3/1	EL35	12/6	PL81	7/9	UL46	8/3
6E23	6/6	12BA6	7/1	DF96	7/8	EL41	8/1	PL82	6/6	UL84	7/1
6J5G	3/1	12BE6	6/6	DK91	5/6	EL42	7/9	PL83	6/6	UR10	7/6
6J5GT	4/8	12BH7	8/9	DK92	7/1	EL44	6/6	PL84	7/6	UR80	9/6
6J6	2/6	12E1	17/6	DK96	7/8	EM34	8/6	PY31	3/1	UR10	11/1
6J7G	4/9	12K7GT	8/1	DL92	8/1	EM30	7/9	PY32	9/6	UT41	5/6
6J7GT	7/6	12K7GT	4/1	DL94	6/6	EM81	6/9	PY32	9/6	UY21	9/6
6K6GT	6/1	12K8	9/9	DL96	7/8	EM84	8/9	PY80	6/6	UY41	6/1
6K7	5/9	12KSQT	9/6	EABCS0	6/6	EM85	8/6	PY81	5/9	UY85	5/1
6K7G	1/1	12K7GT	5/1	EAF42	3/3	EY51	7/6	PY82	5/9	VR105	5/9
6K7GT	4/6	12SA7	6/8	EB41	5/1	EY66	7/3	PY83	8/9	VR150	7/9
6K9	3/6	12SK7	8/6	EB41	5/1	EY66	7/3	PY82	9/1	X36	7/9
6K9G	5/1	12SQ7	7/6	EBC33	4/9	EY88	5/6	PY800	6/3	Z66	8/6

TUBES

Carr. & Ins. 12/6

SATISFACTION GUARANTEED

	6 Months	12 Months	NEW TYPES
MOST MULLARD, MAZDA, COSSOR, EMITRON, EMI-SCOPE, BRIMAR, FERRANTI TYPES PROCESSED IN OUR OWN FACTORY	12in. £2. 0.0 14in. £2.10.0 15-17in. £3. 5.0 19in. £3. 5.0 21in. £3.15.0 23in. £3.15.0	£3. 0.0 £3.10.0 £4. 5.0 £4. 5.0 £5.15.0 £5.15.0	AW47-91 £5.15.0 AW59-91 £7.10.0 AW49-90 £5. 5.0

100 HI-STABS 1% to 5% 100Ω to 5mΩ 9/6

CO-AX. low loss, 6d. yd., 25 yds. 11/6; 50 yds. 22/1; 100 yds. 42/6. Co-ax Plugs. 1/3. Wall outlet boxes 3/6.

100 RESISTORS 1/2-3 watt 6/6

MICROPHONE CABLE. Highest quality black, grey, white, 1/- yard

100 CONDENSERS 9/6

Miniature Ceramic, Silver Mica etc. 3pF to 1µF. LIST VALUE OVER 25.

10 x 5in. SPEAKERS

Ceramic High Flux, "pancake" magnets. Hammered gold finish. Most 25/- excellent reproduction 3Ω.

DULCI(VHF) FM TUNERS

MODEL FMT/5. Self powered 200/250 v. A.C. A.F.C. High sensitivity for fringe and long distance reception. Size 1 1/2 x 8 1/2 in x 3 1/2 in. Weight 7 1/2 lb. In case finished in satin chrome and black. We can offer these high fidelity instruments. Normally £21.13.5. Limited number only at 15 Gns.

LOUDSPEAKERS. 3Ω Top Makes.

6 1/2in. 7/6 5in. 8/6 7x4in. 8/6

MAINS TRANSFORMERS

Excellent Quality Guaranteed Upright mounting 250 v., 60mA, 6.3v., 3A. Primary 230v. 350-6-350v. 120mA, 6.3v. 5A 5v. 3A. Super quality Ditto 50mA. 39/1-29/1

STEREO PORTABLE CABINETS

Latest black and silver metal finish. Consisting of centre cabinet size 16 1/2 in x 13 1/2 in. 8in. deep with lift up lid together with two 10 x 6 speaker cabinets which clip on ends of main cabinet size 4 1/2 in x 8 1/2 in. making overall size of 25 1/2 in x 13 1/2 in x 8 1/2 in. High quality chrome fittings. Will take most autochanger or tape decks. Half price. £3.19.0

STEREO PORTABLE CABINETS

DITTO but with vinylite 7 x 4 speaker cabinets. 59/1

TRANSISTOR GAR RADIOS

Latest Autolux fully transistorised complete with speaker and fittings. Large purchase enables us to sell these superb sets (normally approx. 14 gns.) at the amazing price of 9 Gns.

GELOSO 100W AMPS.

110-240v. AC twin mike and twin gram inputs full mixing, base, treble controls. Fully enclosed case, matches all speaker impedances. Weight 38lbs. Hi-Fi quality output. Normally 42 Gns. 56 gns., few only

STEREO AMPLIFIERS

AC262 3-4 watts per channel, excellent control panel, excellent quality finish. AC mains. Valve at 6 Gns.

SPEAKER FABRIC

Superior Gold/Brown Vinylite with small holes, gilt at 2/6 sq.ft. or 12 sq.ft. (4 x 3)

HITACHI PORTABLE TAPE RECORDER

Latest Hitachi. Fabulous quality reproduction of music. 6-transistor. 1 1/2 in. and 3 1/2 in. speeds. Output 500 mW high quality speaker. Fast forward and rewind. Battery level and record level meter. Precision capstan drive. Size 8 1/2 in x 3 1/2 in. Genuine normal price of 35 gns. Unrepeatable. All spares available. With tape, tape reel, 19 Gns. mike, etc.

HITACHI 4 TRACK MODEL TRA-5053

This superb 48 gns. recording machine is in limited very special offer. Two channel recording. Plays stereo tapes, 1 1/2 in. and 3 1/2 in. per sec. One track can be listened to on an earphone whilst recording on the second track, and thereafter both tracks played simultaneously through the loudspeaker. Ideal for languages, singing to music, etc. Excellent reproduction through high-fidel elliptical speaker. A.C. erase. Dimensions: 11in. x 1 1/2 in. x 5 1/2 in. Weight 12 lb. Dynamic mike. Sound level meter. Footage indicator. 29 Gns. Two mixed inputs. 29 Gns.

MODEL TRA-722

Large 2-track semi-professional model with freq. response 50-13,500 C.P.S. on 7in. reels with mike 'tape' large speaker, latest single hand controls, elegant. Weight 20lbs. 29 Gns.

TRANSISTORS GUARANTEED TOP QUALITY

Huge reduction. Red Spot standard LF type now only 1/6
Millard Matched Output Kits OC81D and 2-OC81 R.F. Kits OC44, OC45 (2) 9/6
3 transistors
AF14 8/- OC96 9/- OC81 5/6
AF15 7/- OC98 14/- OC81D 6/6
AF118 7/6 OC44 5/6 OC82 6/6
AF117 6/- OC45 5/- OC170 8/6
AF127 7/6 OC72 5/- OC171 8/6

GERMANIUM DIODES

General Purpose miniature detector A.V.C. etc. 6/6 doz. Gold Bonded highest quality Individually tested 9/6 doz. 1/-

SILICON RECTIFIERS

Guaranteed performance. Top makes. Tested 250 v. working. 120 ma. 500 ma. (3 for 8/6) 3/9 (3 for 19/6) 7/6

CRMI141. CRMI142. Special bulk purchase enables us to offer these tubes at this low price (carr. 9/-). 39/1-

25 WATT BASE SPEAKERS

Very heavy coned 12in. cast chassis. There is nothing to touch it for power handling and quality at the price. Plus 9/- p.p. £4.19.0

CONNECTING WIRE

P.V.C. Bright Colours. Five 25ft. coils only. 4/1

Stockists of Leak, Quad, Chapman, Goodman, Armstrong, Tripletone, Linear, Rodgers, Trusvox, Ferrograph, T.S.L. Wharfedale, W.B., etc., etc. for value and service.

Post: 11b. 1/6, 11b. 2/6, 21b. 2/9, 31b. 3/1, 41b. 3/3, 51b. 3/6, 61b. 4/1, 81b. 4/6, 141b. 5/6

TECHNICAL TRADING CO.

ALL MAIL ORDER AND RETAIL SHOP AND ROBOPHONE ORDERS
DEVONIAN COURT, PARK CRESCENT PLACE, BRIGTON. Tel. 880722

★ LONDON
★ PORTSMOUTH
★ SOUTHAMPTON

10 Tottenham Court Road, Tel. MUSEUM 2639.
350-352 Fratton Road, Tel. 22034.
72 East Street, Tel. 25851

...COMMENT

CAMBRIDGE RELAY STATION

The BBC's new television and v.h.f. sound relay station to serve Cambridge was brought into service on 7th March. It transmits BBC-1 television on Channel 2 with horizontal polarization, and the three sound programmes on v.h.f., also horizontally polarized, on the following frequencies: Midland Home Service 93.3 Mc/s, Light Programme 88.9 Mc/s, Third Network 91.1 Mc/s.

RECORDING EQUIPMENT DEMONSTRATED IN AMERICA


Sound recording equipment developed by EMI Electronics Ltd. aroused wide interest among leading sound engineers during recent demonstrations in the United States and Canada.

EMI senior sales engineer S. G. Griffiths held the demonstrations during a four-week sales and market evaluation tour of the two countries.

Mr. Griffiths visited major television companies in New York and the leading film studios in Hollywood. In Canada he met sound engineers in the major broadcast centres of Toronto and Montreal.

"Everywhere I went the interest shown in our equipment was tremendous," said Mr. Griffiths. "Our new L4 professional portable tape recorder received particular attention and one Hollywood studio has taken an option on 40 of the machines."

MARCONI COMPUTER FOR SAUDI ARABIA

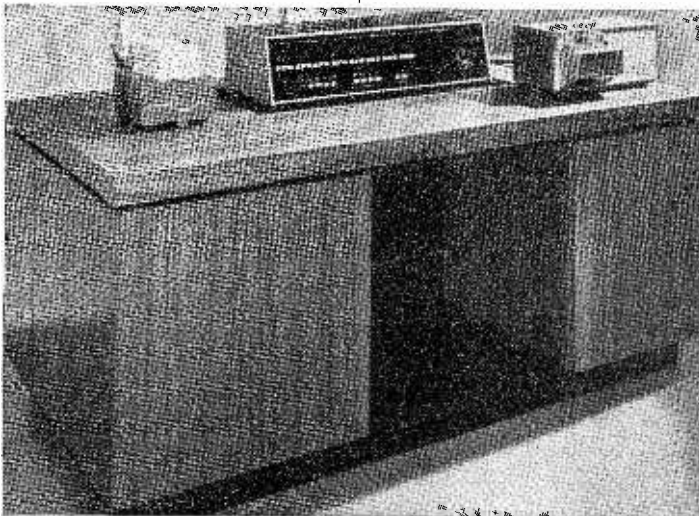

This photograph shows one of the new Marconi Myriad computers of the type which will be used in the radar data handling systems for the Saudi Arabian defence system.

This computer which has been designed by Marconi for radar data processing and other on-line applications, features the latest techniques in microelectronics.

The complete machine is housed in this single desk unit which measures 6ft. x 3ft. x 2ft. 9in. high. All controls and indicator lights are mounted in the low superstructure of the desk top, which provides the operator with full facilities for machine operation and programme checking.

Good Old Henry

I AM now what many people regard as an "oldster" and you and your colleagues are what Ibsen described as "Youngsters knocking at the door".

So I feel that I must congratulate you on the wisdom, the balance and the up-to-dateness of the article by "Henry" entitled Oh, but it Hertz! This is what I call technical journalism at its best.

So, as a westerning planet, I salute the dawn of a new dispensation.

Percy Wilson.

Headington,
Oxford.

We are grateful for this tribute from veteran technical journalist Percy Wilson who, as many readers will know, was for many years Technical Editor of "The Gramophone". He has now established a Consortium of Audio Consultants, in which endeavour we wish him every success.—Editor.

Tapespondent Wanted

I WOULD like to tapespond with anyone, anywhere of my own age (15) who is interested in amateur radio, short wave listening and radio construction generally. My tape recorder is a National 2 track 1 $\frac{7}{8}$ and 3 $\frac{1}{4}$ i.p.s. All tapes will be answered

John Adams.

74 Spring Street,
Sandringham,
Victoria,
Australia.

Ham or Sham

WHAT type of person is worried about the "Radio Amateur"—why the concern? If a person is sufficiently interested in radio communications then he would not ask the "Ham or Sham" question. He would know that in amateur radio "Sham" cannot exist, because the operator is fully qualified to operate any equipment he may own, whether it be home constructed or commercial. This "amateur" tag may have been all very well in the far distant past when capacitors and all other equipment had to be hand-made, but of course even when an operator builds his own home-made gear, the components are all commercial.

I say to the Citizens band agitators and the like; put in some hard work and try for the R.A.E. and long before you pass, the "Ham or Sham?" will have disappeared from your minds.—You will know better!

E. W. Phillipson, G3NVE.

Goole,
Yorkshire.

More News and Comment on Page 44.

Fully guaranteed Individually packed VALVES

AC/HL 4/6	DH63 5/6	EF37A 7/6	F/6063 4/6
AC/PL 4/6	DK92 6/6	EF40 7/6	F/6063 4/6
AC6PEN 5/6	DK96 6/6	EF50 2/6	F/6063 4/6
AL60 5/6	DL92 4/6	EF92 6/6	G1/2963 9/6
ARF3 3/6	DL93 3/6	EF93 4/6	G1/370K 20/6
ARF12 2/6	DL94 10/6	EF94 4/6	G50/2G 5/6
ARF24 3/6	DL96 6/6	EF71 7/6	G120/2M12/6
ARS 5/6	DLS10 3/6	EF72 5/6	GM4 45/6
ARTP1 6/6	DLS19 15/6	EF73 5/6	GM4 45/6
ATP4 2/6	ES0F 23/6	EF74 4/6	GM4 45/6
ATP7 5/6	ES8CC 12/6	EF80 5/6	GM4 45/6
AU7 56/6	ES90C 10/6	EP81 6/6	GM4 45/6
AZ31 9/6	EL148 2/6	EP85 5/6	G23 10/6
B6H 15/6	EL196 5/6	EP86 6/6	G23 10/6
BD78 40/6	EL145 30/6	EP89 5/6	G23 10/6
BL63 10/6	EL152 12/6	EP91 4/6	G23 10/6
B84 3/6	EA30 1/6	EP92 2/6	G23 10/6
B85 20/6	EA78 2/6	EP93 2/6	G23 10/6
B884 37/6	EABCS0 5/6	EP83 8/6	G23 10/6
B2184 26/6	EA91 3/6	EP184 8/6	G23 10/6
BT19 15/6	EAF42 3/6	EHT1 300/6	G23 10/6
BT35 25/6	EB34 1/6	EL32 3/6	G23 10/6
BT45 150/6	EB39 3/6	EL34 10/6	G23 10/6
BT82 35/6	EBC23 1/6	EL36 5/6	G23 10/6
CC3L 2/6	EBC41 8/6	EL38 17/6	G23 10/6
CO13 9/6	EBC81 5/6	EL41 7/6	G23 10/6
CV71 3/6	EBF80 6/6	EL42 3/6	G23 10/6
CV77 5/6	EBF83 7/6	L50 3/6	G23 10/6
CV102 1/6	EBP89 6/6	EL81 1/6	G23 10/6
CV103 2/6	EC33 4/6	EL82 3/6	G23 10/6
CV4004 7/6	EC58 12/6	EL84 5/6	G23 10/6
CV4014 7/6	EC70 4/6	EL85 5/6	G23 10/6
CV4015 5/6	EC90 2/6	EL91 4/6	G23 10/6
CV4025 10/6	EC91 3/6	EL95 5/6	G23 10/6
CV4049 6/6	ECC81 4/6	EL300 20/6	G23 10/6
CV731 6/6	EC92 4/6	EL36 5/6	G23 10/6
D1 1/6	ECC83 6/6	EM81 7/6	G23 10/6
D41 6/6	ECC84 5/6	EM84 6/6	G23 10/6
D61 6/6	ECC85 6/6	EN31 10/6	G23 10/6
D77 3/6	ECC88 9/6	ESU74 8/6	G23 10/6
DA30 12/6	ECC91 4/6	ESU208 6/6	G23 10/6
DAF96 6/6	EC93 5/6	EV51 6/6	G23 10/6
DD41 4/6	ECH42 9/6	EY86 6/6	G23 10/6
DEB5 2/6	ECH81 5/6	EY91 3/6	G23 10/6
DEH23 8/6	ECH83 7/6	EZ40 6/6	G23 10/6
DEH25 15/6	ECL80 4/6	EZ41 6/6	G23 10/6
DEH73 2/6	ECL82 7/6	EZ80 5/6	G23 10/6
DF1 3/6	ECL83 10/6	EZ81 3/6	G23 10/6
DF92 3/6	ECL86 10/6	F/6067 5/6	G23 10/6
DF96 6/6	EPF36 3/6	F/6061 5/6	G23 10/6

PFL20017/6	U26 11/6	L1C6 7/6	6AK7 6/6	6L6M 11/6	12Q7GT 3/3	220TH 4/6	C.V. Tubes
PL36 1 7/6	U27 8/6	1LH4 4/6	6AL5 3/6	6L7G 4/6	13SA7 7/6	225DU 9/6	CV1596
PL38 16/6	U50 4/6	1N21B 4/6	6AL5W 7/6	6L8 4/6	12S07 4/6	307A 5/6	(084) 55/6
PL41 7/6	U52 4/6	1N43 4/6	6AM3 2/6	6L120 5/6	12S67 3/6	310C 28/6	B4504/E16
PL42 5/6	U191 11/6	1N70 4/6	6AM6 4/6	6N7 6/6	12SH7 3/6	350B 8/6	VCR97 28/6
PL43 6/6	U801 18/6	1R4 2/6	6AQ5 5/6	6N7G 5/6	12SJ7 5/6	357A 7/6	VCR138A
PL44 6/6	UABCS0 6/6	1R5 3/6	6AQ5W 9/6	6P25 12/6	12SK7GT 3/6	368A 5/6	VCR138A
PL500 15/6	UAF42 9/6	1R4 5/6	6AS6 4/6	6Q7G 6/6	12SN7GT 6/6	398A 15/6	VCR138A
PLM24A 5/6	UAC41 6/6	1R5 5/6	6AS6W 9/6	6R7 5/6	6R7 5/6	445A 8/6	VCR138A
PLM1 10/6	UB2 10/6	1R5 5/6	6AS7 7/6	6S47 7/6	12SR7 5/6	487 30/6	VCR15735
PL25 10/6	U191 11/6	1R70 4/6	6AT6 3/6	6SA7GT 6/6	12V4 2/6	705A 10/6	VCR517B
PL25H 7/6	UBF89 6/6	1R26 8/6	6B26 4/6	6AU6 7/6	12L7 7/6	715B 60/6	VCR517C
PL25M 7/6	UBL21 11/6	2C26 7/6	6B26 4/6	6AX4 8/6	15D2 6/6	717A 3/6	VCR517C
PL25N 7/6	UC55 6/6	2C26A 3/6	6B26 4/6	6B7 6/6	19R2 15/6	724A 15/6	VCR517C
PL25P 7/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19G3 10/6	843 3/6	VCR517C
PL25Q 7/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	801 6/6	VCR517C
PL25R 7/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	803 22/6	VCR517C
PL25S 7/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	807 8/6	VCR517C
PL25T 7/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	808 8/6	VCR517C
PL25U 7/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	811 22/6	VCR517C
PL25V 7/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	813 65/6	VCR517C
PL25W 7/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL25X 7/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL25Y 7/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL25Z 7/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C

PL26 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL27 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL28 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL29 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL30 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL31 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL32 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL33 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL34 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL35 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL36 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL37 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL38 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL39 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL40 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C

PL41 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL42 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL43 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL44 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL45 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL46 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL47 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL48 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL49 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL50 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL51 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL52 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL53 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL54 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL55 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C

PL56 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL57 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL58 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL59 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL60 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL61 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL62 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL63 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL64 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL65 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL66 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL67 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL68 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL69 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C
PL70 1/6	UC81 6/6	2C26A 3/6	6B26 4/6	6B7G 5/6	19H7 5/6	815 35/6	VCR517C

MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves. All U.K. orders below £1, P. & P. 1/-; over £1, 2/-; over £3, P. & P. free. C.O.D. 2/6 extra. Overseas Postage extra at cost.

THERMAL PULSE MECHANICAL CIRCUIT BREAKER FOR A.C. & D.C. Current 1 amp. Protects against shorts (instantaneous cut out at approximately 8 amps.) and against overloads: 1.8 amp. 30 seconds, 2.1 amp. 15 seconds, 2.5 amp. 8 seconds. Delayed cut off may be adjusted to different currents and times. Separate pair of contacts to indicating device. Dimensions 3 1/2 x 1 1/2 x 7/8 in. Price 12/6. P. & P. 2/6.


"CONNECT AND FORGET, CANNOT OVERCHARGE" "ESSTRON" MARK I AUTOMATIC BATTERY CHARGER. Initial charging rate 6-7 amps. The charging rate automatically adjusts itself to the charge in the battery. Automatic current and voltage control. Patented application of magnetic amplification to battery charging. Indicator lights show battery fully charged, receiving charge incorrectly connected or faulty cells. Mains voltage 200/250 v. Built for 6 or 12 lb. batteries. Measurements 7 x 5 x 5 1/2 in. Weight 8 1/2 lb. Price £7.19.6. P.P. 3/6.

2 KW ULTRASONIC GENERATOR together with power supply unit for 200-250 v. A.C. Complete two chassis with interconnecting cables. Frequency 37 to 43 kc/s adjusted by fine control. Peak output 2 kw., average output 500 w. Completely new valves and manual £65 carriage paid U.K. Large selection of mains and Heavy Duty L.F. TRANSFORMERS. **VARIMETER** for No. 19 sets, 17/6. P. & P. 3/6.

MARCONI SIGNAL GENERATOR TYPE TF 801B/3/S. Frequency range 12-485 Mc/s. in five ranges. Directly calibrated frequency dial. Output waveform: C.W. sine wave A.M., pulse A.M. (from ext. source only). Internal modulation frequency 1,000 c/s. Output: a, normal—continuously variable directly calibrated from 0.1 µv.—0.5 v. b, high: up to 1 v. modulated or 2 v. unmodulated, output impedance 50 ohms. Fine frequency tuning control, carrier on/off switch, built-in crystal calibration for 2 Mc/s. and 10 Mc/s. Stabilised voltage supply. In excellent "as new" condition. Fully checked and guaranteed. £115. Carr. 30/-.

C.R. 100 RECEIVER. 60kc—420kc, 500kc—13mc. In 6 bands, 2 HF stages, 3 IF stages, AVC on both phone and CW. Excellent condition, correctly tuned and guaranteed. £31. Carr. 30/-.

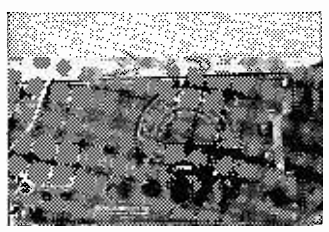WELL PROVEN RELIABLE COMMUNICATION RECEIVER P.C.R.3



(Made by Pye.) 3 bands, 1 medium wave, 2 120-43m, 3 43-13m. Overall sensitivity 1-2µv. 5/Noise ratio 10 dB at 6µv. Circuit incorporates an RF stage, two I.F. stages, tone control, A.V.C. antenna trimmer, 6V6 output. Set in fully working condition together with headphones and speaker, plus £9.12.6. With vibratory supply unit, 12v, £10.15.0. With specially built in P.S.U. for 210-250v A.C., £11.17.6. Carriage either set 15/-.

H.R.O. SENIOR TABLE MODEL TYPE 5A with "S" meter and crystal filter in excellent fully checked and tested condition together with set of 8 general coverage coils and mains P.S.U., £33. Carriage and packing 30/-.

Ditto, but model "M", £28. Carriage and packing 30/-.

P. G. RADIO LTD.

170 GOLDHAWK RD., W.12
SHEPHERD'S BUSH 4946

Open 9-5.30 p.m. except
Thursday 9-1 p.m.

PERSONAL CALLERS WELCOME

TELEPHONE HANDSET. Standard G.P.O. type, new 12/-, P. & P. 2/-.

INSET MICROPHONE for telephone handset, 2/6. P. & P. 2/-.

EVERSHED MEGGER CIRCUIT TESTER 2 ranges. 0-1,000 ohms. 100-200,000 ohms with test leads leather carrying case. Tested £49.19.6. P. & P. 3/6.

A.R.88D. RECEIVERS. Fully reconditioned, £55. Rebuilt model, £85. Carriage paid U.K.

MARCONI TF 868 UNIVERSAL BRIDGE. Capacitance 1µs to 100µ

Why

NOT BUILD ONE OF OUR PORTABLE TRANSISTOR RADIOS...

BACKED BY OUR SUPER AFTER SALES SERVICE

All components used in our receivers may be purchased separately if desired. Parts price lists and easy build plans available separately at prices stated. Overseas post 10/-.

FIRST FOR QUALITY, PERFORMANCE AND PRICE!

NEW ROAMER SEVEN Mk IV

7 WAVEBAND PORTABLE OR CAR RADIO

Amazing performance and specification

★ Now with PHILCO MICRO-ALLOY R.F. TRANSISTORS


FULLY TUNABLE ON ALL WAVEBANDS

● 9 stages—7 transistors and 2 diodes

Covers Medium and Long Waves, Trawler Band and three Short Waves to approx. 15 metres. Push-pull output for room filling volume from rich toned 7 x 4in. speaker. Air spaced ganged tuning condenser. Ferrite rod aerial for M & L waves and telescopic aerial for S waves. Real leather look case with gilt trim and shoulder and hand straps. Size 9 x 7 x 4in. approx. The perfect portable and the ideal car radio. (Uses PP7 batteries available anywhere).

★ EXTRA BAND FOR EASIER TUNING OF PIRATE STATIONS etc.

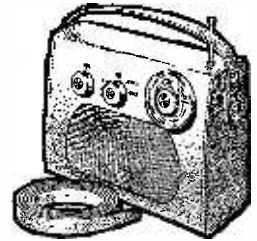Total cost of parts now only **£5.19.6** P. & P. 5/6
Parts Price List and easy build plans 3/- (FREE with kit)



MELODY SIX

"...amazed at volume and performance... has really come up to my expectations" S.G. Stockton-on-Tees.

● 8 stages — 6 transistors and 2 diodes

Our latest completely portable transistor radio covering medium and long waves. Incorporates pre-tagged circuit board, 3in. heavy duty speaker, top grade transistors, volume control, tuning condenser, wave change slide switch, sensitive 6in. ferrite rod aerial.

Push-pull output. Wonderful reception of B.B.C. home and Light, 208 and many Continental stations. Handsome leather-look pocket size case, only 6½ x 3½ x 1½in. approx. with gilt speaker grille and supplied with hand and shoulder straps.

Parts Price List and easy build plans 2/- (FREE with kit)

Total cost of all parts now only **£3.9.6** P. & P. 3/6


POCKET FIVE

● 7 stages—5 transistors and 2 diodes

Covers Medium and Long Waves and Trawler Band, a feature usually found in only the most expensive radios. On test Home, Light, Luxembourg and many Continental stations were received loud and clear. Designed round super-sensitive Ferrite Rod Aerial and fine tone 2½in. moving coil speaker, built into attractive black case with red speaker grille. Size 5½ x 1½ x 3½in. (Uses 1289 battery available anywhere).

Parts Price List and easy build plans 1/6 (FREE with kit)

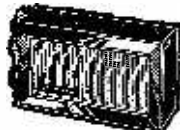Total cost of all parts now only **42/6** P. & P. 3/-.



NEW ROAMER SIX

NOW WITH PHILCO MICRO-ALLOY R.F. TRANSISTORS

● 6 WAVEBAND !!



● 8 stages—6 transistors and 2 diodes

Listens to stations half a world away with this 6 waveband portable. Tuneable on Medium and Long waves, Trawler band and two Short Waves. Sensitive ferrite rod aerial and telescopic aerial for short waves. Top grade transistors, 3-inch speaker, handsome case with gilt fittings. Size 7½ x 5½ x 1½in. Carrying strap 1/6 extra.

★ EXTRA BAND FOR EASIER TUNING OF LUX, ETC.

Parts Price List and easy build plans 2/- (FREE with kit)

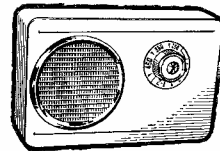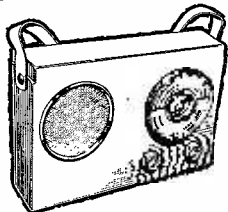Total cost of all parts now only **£3.19.6** P. & P. 3/6



NEW TRANSONA FIVE

"Home, Light, A.F.N., Lux., all at good volume." G.P. Durham

● 7 stages—5 transistors and 2 diodes

Fully tunable over Medium and Long Waves and Trawler Band. Incorporates Ferrite rod aerial, tuning condenser, volume control, new type fine tone super dynamic 2½in. speaker etc. Attractive case. Size 6½ x 4½ x 1½in. 1289 battery available anywhere.)

with red speaker grille. (Uses Total cost of all parts now only **42/6** P. & P. 3/6

Parts Price List and easy build plans 2/- (FREE with kit)

TRANSONA SIX

● 8 stages—6 transistors and 2 diodes

This is a top performance receiver covering full Medium and Long Waves and Trawler Band. High-grade approx. 3in. speaker makes listening a pleasure. Push-pull output Ferrite rod aerial. Many stations listed in one evening including Luxembourg loud and clear. Attractive case in grey with red grille. Size 6½ x 4½ x 1½in. (Uses PP4 battery available anywhere.) Carrying strap 1/- extra.

Total cost of all parts now only **59/6** P. & P. 3/6

Parts Price List and easy build plans 1/6 (FREE with kit)



SUPER SEVEN

● 9 stages—7 transistors and 2 diodes

Covers Medium and Long Waves and Trawler Band. The ideal radio for home, car or can be fitted with carrying strap for outdoor use. Completely portable—has built-in Ferrite rod aerial for wonderful reception. Special circuit incorporating 2 R.F. Stages, push-pull output, 3in. speaker (will drive large speaker). Size 7½ x 5½ x 1½in. (Uses 9v. battery, available anywhere.)

Total cost of all parts now only **£3.19.6** P. & P. 3/6

Parts Price List and easy build plans 2/- (FREE with kit)

RADIO EXCHANGE CO.

61 HIGH STREET, BEDFORD

Telephone: Bedford 52367

Callers side entrance Barratts Shoe Shop open 9-5 p.m. Sats. 10-12.30 p.m.


HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT Type TA1

- Peak output in excess of 1 1/2 watts
- All standard British components.
- Built on printed circuit panel, size 6 x 3in.
- Generous size Driver and Output Transformers.
- Output transformer tapped for 3 ohm and 15 ohm speakers.
- Transistors (GET 114 or 81 Mullard OC81D and matched pair of OC81 o/p).
- 9 volt operation.
- Everything supplied, wire, battery clips, solder, etc.
- Comprehensive easy to follow instructions and circuit diagram 1/6 (Free with Kit). All parts sold separately.

SPECIAL PRICE 45/-. P. & P. 3/-. Also ready built and tested, 52/6. P. & P. 3/-. A pair of TA1s are ideal for stereo.

STEREO AMPLIFIER

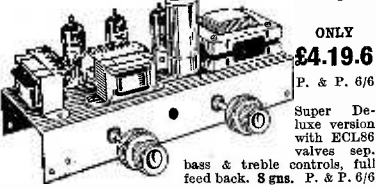Incorporating 2 ECL82s and 1 EZ80, heavy duty, double wound mains transformer. Output 1/2 watts per channel. Full tone and volume controls. Absolutely complete.



ONLY **£4.19.6**
P. & P. 6/6

Super Deluxe version with ECL86 bass & treble controls, full feedback. 8 gns. P. & P. 6/6

HARVERSON'S F.M. TUNER Mk. I

- F.M. tuning by famous maker
- Guaranteed non-drift.
- Permeability tuning
- Frequency coverage, 89-100 Mc/s
- Balanced diode output
- Two I.F. stages and discriminator.
- Attractive maroon and gold dial (7 x 3in. glass).
- Self powered, using a good quality mains transformer and valve rectifier.
- Valves used ECC85, two EF80s, and EZ80 (rectifier).
- Fully drilled chassis.
- Size of completed tuner 8 x 6 x 5 1/2in.
- All parts sold separately. Set of parts if purchased at one time £5.19.6, plus 8/6 P. & P. ins.
- Circuit diagram and instructions 1/6 post free. Mark II Version as above but complete with magic eye, front panel and brackets, £6.12.6. P. & P. 8/6.
- Mark III Version as Mark I but with output stage (ECL82) and tone control, £7.7.0. P. & P. 8/6.

SPECIAL PURCHASE! TURRET TUNERS by famous maker. Brand new and unused. Complete with PC084 and PCF80 valves 34-39 Mc/s I.F. circuits for Channel 1 to 5 and 8 and 9. Circuit diagram supplied. ONLY 22/- each. P. & P. 8/6.

GÖRLER F.M. TUNER HEAD

88-100 Mc/s 10.7 Mc/s I.F., 15/-, plus 2/- P. & P. (ECC85 valve, 8/6 extra).

6 TRANSISTOR AND DIODE SUPERHET

A first-class 2 waveband transistor superhet. ● Printed circuit panel (size 8 1/2 x 2 1/2in.). ● 3 pre-aligned I.F. transformers. ● High-gain Ferrite Rod Aerial. ● All First-grade transistors. ● Car aerial winding. ● Push-pull output. ● All parts supplied with simple instructions. All parts sold separately. Set of parts if purchased at one time ONLY £4.5.0. P. & P. 2/6 (Circuit diagram 2/-. Free with set of parts.)

35 OHM SPEAKERS

Suitable for use with above. 2in. Goodmans Ideal replacement for most pocket portables. 8/6; 3 1/2in. 12/6; 7 x 4in., 21/-; P. & P. 2/- per speaker.

Portable CABINET

Size approx. 9 1/2 x 6 1/2 x 3 1/2in. Suitable for above using. 3 1/2in. speaker, 25/-; P. & P. 2/6.

COIL AND TRANSFORMER SET FOR TRANSISTOR SUPERHET

3 I.F. transformers one oscillator coil one driver transformer and wound Ferrite aerial (incl. long and car aerial coupling). 92/6 complete post 2/-. 6 transistor printed circuit board to match 8/6. Post 1/-. Circuit diagram 1/6 extra.

TWIN TELESCOPIC AERIAL. Comprising two 2-section heavily chromed rods. Closed 12in. each extending to 32in. Completely adjustable from vertical to horizontal. Supplied complete with universal mounting bracket, coax lead and plug. Suitable for F.M. or TV. 12/6. P. & P. 2/-.

QUALITY RECORD PLAYER AMPLIFIER
A top-quality record player amplifier. This amplifier (which is used in a 29 gn. record player) employs heavy duty double wound mains transformer, ECC85, EL84, EZ80 valves. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w. x 2 1/2in. d. x 5 1/2in. h. Ready built and tested. PRICE 69/6. P. & P. 4/9.

ALSO AVAILABLE mounted on board with output transformer and 6in. speaker ready to fit into cabinet below. PRICE 89/6. P. & P. 8/9.

QUALITY PORTABLE R/P CABINET

Uncut motor board. Will take above amplifier and B.S.R. or GARRARD Autchanger or Single Record Player Unit. Size 18 x 14 x 8 1/2in. Price £3.9.6. Carr. 7/6.

4-SPEED PLAYER UNIT BARGAINS

All brand new in maker's original packing.

SINGLE PLAYERS
B.S.R. TU/12 £3.9.6. Carr. 5/6.
GARRARD SP25 De Luxe £12.10.6. Carr. 5/6.
B.S.R. GU7 with unit mounted pickup arm. £4.18.8. Carr. 5/6.

AUTO CHANGERS

Latest B.S.R. UA25 Super slim £6.2.6
GARRARD Autoslim (4 pole motor) plug-in hd. £5.10.0
GARRARD AT6 £9.10.0. Carr. 6/6 on each.
All the above units are complete with t/o mono head and sapphire stylus or can be supplied with compatible stereo head for 12/6 extra.

BRAND NEW CARTRIDGE BARGAINS!

RONETTE STEREO 105 CARTRIDGE. Stereo L.P.73 complete with two saphires. Original list price 67/9. Our price 24/- P. & P. 1/-.
ACOS GP87-1. Mono complete. List price 21/- Our price 13/6. P. & P. 1/-.

BRAND NEW 3 OHM LOUSPEAKERS

5in. 12/6; 6 1/2in. 15/-; 8in. 21/-; 10in. 25/-; 12 in. 27/6; (12in. 15 ohm x 20/-). 10in. x 6in. 26/-.
E.M.I. 1 1/2 x 8in. with high flux ceramic magnet, 42/- (15 ohm, 45/-). P. & P. 4" & 5" 2/6, 6 1/2" & 8" 2/6 10" & 12" 3/6 per speaker.

BRAND NEW HEAVY DUTY 12in. SPEAKERS

Response 45 c/s-13 Kc/s. 1 1/2in. voice coil. Available in 3 or 15 ohms. Guaranteed full 15 watts British rating. Heavy cast aluminium frame. These are current production by world famous maker and as they are offered well below list price we are not permitted to disclose the name. LIMITED NUMBER ONLY. UNREPEATABLE at 89/6. P. & P. 5/-. Also 25 watt Guitar Model available at £5.5.0. And 35 watt Guitar Model £8.8.0.

VYNAIR AND REXINE SPEAKER AND CABINET FABRICS

Approx. 54in. wide. Usually 35/- yard. OUR PRICE 13/6 per yard length. P. & P. 2/6 (min. one yd.) S.A.E. for samples.

MAINS TRANSFORMER For transistor power supplies.

Tapped pri 200-250V. Sec. 40-40 at 1 amp (with electrostatic screen) and 6.3v at 5 amp for dial lamps etc. Drop thru mounting. Stack size 1 1/2" x 3 1/2" x 3 1/2" 27/6. P. & P. 4/6. Also for use with above 4000 mid. 40v. Smoothing condenser size 1 1/2" dia x 3 1/2" high. 3/6 each. P. & P. 1/6 and 2800 mid. 25v. 1 1/2" dia x 3" high 3/6. P. & P. 1/6.

MATCHED PAIR OF 2 1/2 WATT TRANSISTOR DRIVER AND OUTPUT TRANSFORMERS

Stack size 1 1/2" x 3 1/2" x 1 1/2" in. Output trans. tapped for 3 ohm and 15 ohm output. 10/- pair plus 2/6 P. & P.

7-10 watt OUTPUT TRANSFORMERS to match pair of ECL 86's in push-pull to 3 ohm output. ONLY 11/- P. & P. 2/6.

7-10 watt ULTRA LINEAR OUTPUT TRANSFORMERS to match pair of ECL 82's in push-pull to 3 ohm output. ONLY 15/- P. & P. 2/6.

BRAND NEW TRANSISTOR BARGAINS

GET 15 (Matched Pair) 16/-; V15/10p, 10/-; OC71 5/-; OC76 8/-; AF117 7/6.
Set of Mullard 6 transistors OC44, 2-OC45 OC81D matched pair OC81 25/-, ORP12 Cadmium Sulphide Cell 10/6.

EDISWAN MAZDA


PXA101 6/6; XA103 6/6.
R.F.I. Pack: 1-PXA102 Mixer; 2-PXA101 I.F. Amp. (Equiv. OC44 and OC45) 10/6
R.F. 2 Pack: 2-PXA101 I.F. 1-PXA102 Osc. 12/6
PXA102 Mixer. 12/6
L.F. Pack: Consisting of PXB115 Driver Matched pair. PX171 mounted complete with heat sinks (Equiv. OC81D and OC81) 12/6

ALL TRANSISTORS POST FREE.

HEAVY DUTY NON-INDUCTIVE D/P MICRO SWITCH. Conservatively rated 10 amps at 250v. Standard one-hole fixing. Body size 1 1/2 x 1 1/2 x 1 1/2 in. deep inc. terminals 8/6 each. P. & P. 1/6 (6 or more post free).

NEON A.C. MAINS INDICATOR. For panel mounting, cut out size 1 1/2 x 3/4 x 3/4 in. deep inc. terminal. White case with lens giving brighter light. For mains 200/250v. 2/6 each P.P. 6d. (6 or more post free).

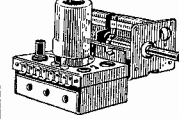ANOTHER HARVERSON SCOOP! FM/AM TUNER HEAD



Beautifully designed and precision engineered by Dorrer and Wadsworth Ltd. Supplied ready fitted with twin .0005 tuning condenser for AM connection. F.M. section covers 86-102 Mc/s. I.F. output 10.7 Mc/s. Complete with ECC85 wound mains transformer and output transformer matched for 3 ohm speaker, separate Bass, Treble and volume controls. Negative feedback line. Output 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls.

(6L12) valve and full circuit diagram of tuner head. All brand new and realigned F.M. Another special bulk purchase enables us to offer these at 27/6 each. P. & P. 3/-. Order quickly!

3-VALVE AUDIO AMPLIFIER MODEL HA34




Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2in. w. x 4 1/2in. d. x 4 1/2in. h. Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker, separate Bass, Treble and volume controls. Negative feedback line. Output 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls.

The HA34 has been specially designed for us and our quantity order enables us to offer them **£4.5.0** and tested for only P. & P. 6/-.
and tested for only P. & P. 6/-.

HSL 'FOUR' AMPLIFIER KIT

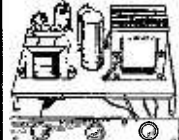
A.C. Mains 200/250v., 4 watt, using ECC83, EL84, EZ80 valves.



● Heavy duty double-wound mains transformer with electrostatic screen.
● Separate Bass, Treble and Volume controls, giving fully variable boost and cut with minimum insertion loss.
● Heavy negative feedback loop over 2 stages ensures high output at excellent quality with very low distortion factor.
● Suitable for use with guitar, microphone or record player.
● Provision for remote mounting of controls or direct on chassis.
● Chassis size only 7 1/2in. wide x 4in. deep. Overall height 4 1/2in.
● All components and valves are brand new. ● Very clear and concise instructions enable even the inexperienced amateur to construct with 100% success. ● Supplied complete with valves, output transformer (3 ohms only), screened lead, wire, nuts, bolts, solder, etc. (No extras to buy.) PRICE 79/6. P. & P. 6/-.

Comprehensive circuit diagram, practical layout and parts list 2/6 (free with kit).
This kit although similar in appearance to HA34 it employs entirely different and advanced circuitry.

10/14 WATT HI-FI AMPLIFIER KIT

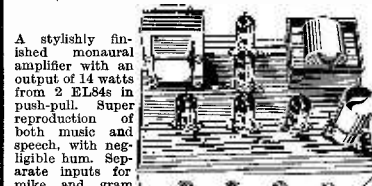

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86, and EZ80 rectifier. Simple instruction booklet 1/6. (Free with parts.) All parts sold separately. ONLY 27.0.6. P. & P. 8/6. Also available ready built and tested complete with std. input sockets, £9.5.0. P. & P. 8/6. Carrying case for above 29/6. P. & P. 7/6.

B.S.R. MONARDECK (Single speed) 3 1/2in. per sec., simple control, using 3 1/2in. spools, £6.15.0 plus 7/6 carr. and ins. (Tapes extra).

LATEST COLLARO MAGNAVOX

363 TAPE DECK DELUXE. Three speeds, 2 track, takes up to 7in. spools. 10 gns. Plus 7/6 Carr. & ins. on each (Tapes extra).

ACOS CRYSTAL MIKES. High imp. For desk or hand use. High sensitivity, 18/6. P. & P. 1/6.
TSL CRYSTAL STIOLK MIKE. Listed at 45/-. Our price 18/6. P. & P. 1/6.

PORTABLE TAPE RECORDER CASE

Beautifully made and expensively finished in dark grey heavy grade rexine. Satin Chrome metal grille front and chrome fittings. Speaker aperture 9" x 4". Overall size 15 1/2" x 15" x 7 1/4" h. Will take any standard tape deck or single record player. Limited number only. Worth at least £5. OUR PRICE 49/6. P. & P. 5/-. Brand new and unused.

Open all day Saturday
Early closing Wed. 1 p.m.
A few minutes from South Wimbledon Tube Station.

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, S.W.19 CHERRYWOOD 3985
SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)
PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY P. & P. OVERSEAS ORDERS CHARGED EXTRA.

EXCLUSIVE TO PRACTICAL WIRELESS READERS MORE TERRIFIC OFFERS FROM CONCORD!

TRANSISTOR POCKET RADIOS WITH LOUDSPEAKER




**BULK PURCHASE
ENABLES US TO
MAKE THIS
FANTASTIC
OFFER**

ONLY 28/6

The "SAN REMO" is so tuned that it brings the voices of star vocalists dramatically to life — in your home, office, etc. Only 4 1/2 x 2 1/2 x 1 1/2 in. Fits easily into your pocket or handbag. Works for months off 1/2d. battery. Should last a lifetime, anyone can assemble it in an hour or two with our easy plan. Miniature speaker—everything, only 28/6, 2/6 P. & P. (Parts can be bought separately). Limited supply—so rush your order before it's too late.

SAVE YOUR LEGS! INTERCOM

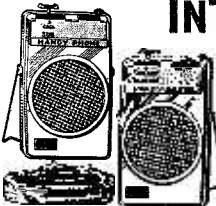

**OUTFIT
&
BABY
ALARM
Ready Built**

**LIMITED
QUANTITY
SAVE £3.16.6**

ONLY

49/6

Robustly made, brand new current models. You get 2 separate fully transistorised intercommunicating sets — each can speak or listen to the other — complete with 60ft. connecting wire. Fixed in a flash. Ends baby-crying worries. Ideal for Workshop to House, Sickroom, hundreds of uses! Hangs on wall or stands up. Our absurd price 49/6, battery 2/6 extra. Post, etc. 3/6. Money refunded if not 6 guineas value!

MAKE 5 DIFFERENT TRANSISTOR RADIOS for 35/-




**NO EXPERIENCE
NECESSARY.**

No Soldering.
Only 8 connections
for first radio to work.


Just look, you get Easy ABC Plans, Cabinet, Loud-speaker (alone 17/6). Earphone, 4 Semi-conductors, Coils, Condensers, Resistors, Tuner, Switch, Screws, etc. **YES—EVERYTHING!** Loud clear English and Foreign reception. As supplied to Educational Authorities, H.M. Forces, etc. **TESTIMONIALS GALORE.** Mr. R. O'D of Londonderry, writes: "... I received your components and I must say that I am very satisfied with them. I have it already set up!" **COMPLETE HOME/RADIO COURSE.** Originally £6 SEND ONLY 35/- plus 3/6 post, etc.

IT HAD TO COME EVENTUALLY! THE "SKYSCRAPER" PERSONAL COMMUNICATIONS RECEIVER. Highly sensitive. World-wide short-waves reception including news in English and countless other broadcasts from RUSSIA, AMERICA, etc., etc. Take it anywhere — it's featherweight! 6in. x 3 1/2 in. x 1 1/2 in. Bandspread Tuning, Vernier Dial, Miniature Valve Circuits, Plug-in Coils, Own Rod Aerial, etc. 50% of production to be exported. Anyone can assemble it with 2 hours—only a few connections to make—experience unnecessary. Parts incl. Case, Personal phone. Easy-to-follow plan—49/6, plus 6/6 Post, etc.

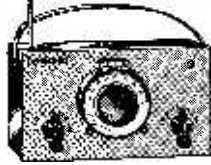

**MINIATURE
PRECISION
SPY CAMERA**
Only 12/6 Post 2/6

Offered at a fraction of its Real Worth. Brand new precision made photographic instrument in chromed steel and leather. Two speed shutter, 2 1/2 in. x 1 1/2 in. Easily concealed in palm-of-hand and takes crystal clear photographs. The range of Angles offered at the absurd price of 12/6, incl. solid leather case—add 6/- for pack of 6 films which give 60 photos, superb craftsmanship in miniature. Send immediately.

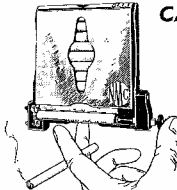


**CAR CIGARETTE
LIGHTER—
DISPENSER**

ONLY

18/6

High Class Stores sell at 3 gns. — save £2.4.6
Top quality chromium Car cigarette lighter — Dispenser. Fixed in a jiffy — Pressing Button delivers ready-lit Cigarette into your hand! Takes 10 cigarettes — King size or any size! As fitted to luxury cars. Safe, fool-proof. 3 1/2 x 4 x 1 1/2 in. Lifetime tested, ready to use. Refund if not worth 3 gns. 750 only. 18/6 plus 1/6. P. & P. (state 6 or 12v.).

AUTOMATIC POCKET CALCULATOR

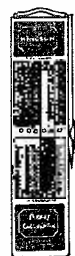

Adding and Subtracting up to 999,999 at your finger tips for

ONLY 8/6 plus 1/6 P. & P.

This superfast, lightweight calculator is simple to operate yet fantastically accurate. Precision engineered by craftsmen and factory tested for reliability. Ideal for use in Offices, Shops, Stores, During Games, etc. Complete with carry case. Slips easily into the jacket pocket or purse. Decimal tables, included for engineers — A terrific bargain that you'll enjoy using.

Read what just a few of our Satisfied customers say:—

R.C. of Harringay writes Received with thanks Skyroma... Very pleased. Working well, **B.M. of Harrogate writes**... I would like to thank you... It was a real bargain.

L.S. of London W.8 writes... given it a good try out and I am very pleased with the results.

S.B. of Somerset writes... delighted with this radio... glad if you could send one more. **T.F. of Stevenage writes**... I would just like to say how pleased my son is with this radio.

UNIQUE NEW FULLY TRANSISTORISED

READY BUILT

**PORTABLE
RADIO**



**NOW A FRACTION
OF THE NORMAL
PRICE ONLY 35/-**

WHY PAY MORE?
All the latest refinements are packed into this new MULTI-STATION ALL transistor radio — the internal aerial picks up even remote stations and the powerful built-in speaker gives room filling volume. Individual tuning, first-class reception. Purchase with confidence — packed in original manufacturer's cartons. (Personal earpiece and battery 4/6). Send 35/- plus 4/6 P. & P.

NEW RADIO

**NO SOLDERING
VOLKSRADIO
ANYONE
CAN BUILD
IN 2-3 HOURS**



19/6

EVEN THE OLDER CHILDREN BUILD THEM!... no soldering — only 16 connections! then hear it reach out bringing in station after station, loud and clear Palm-of hand size 4 1/2 x 2 1/2 x 1 1/2 in. Many Testimonials **M.H. of Bradford, writes:** "... I have just completed one of your sets successfully, it is the first time I have ever tackled anything like a radio, and I must state here and now, I am amazed how easy it is to a layman like me." Your instructions and plan have obviously been very carefully thought out so that even the most dim can follow them... **Direct from Manufacturers to You, Send 19/6 plus 2/6 post, etc PARTS AVAILABLE SEPARATELY**

NO SOLDERING

**AMAZING
CIGARETTE
RADIO**



**ONLY
18/6**

Yes a perfectly ordinary packet of cigarettes! — but watch your friends' astonishment on hearing it fetch in station after station, loud and clear! Still holds 10 cigarettes — yet cleverly conceals highly sensitive, fully transistorised circuit (including tiny battery). Even a young boy can assemble it in under 2 hours. No soldering. No experience necessary. Only 16 connections to make. Ideal for taking to work with you. From our bustling testimonial file. **Mr. D.B. of Huddersfield, writes:** "... I have fitted the parts in and it is working wonderfully..." **ALL PARTS** including Semi-Conductors, A.B.C. Plans, etc. **ONLY 18/6 plus 2/6 post, etc. PARTS AVAILABLE SEPARATELY**

CONCORD ELECTRONICS LTD

(Mail Order Only)
(DEPT. P.W.30) 77 NEW BOND ST.,
LONDON, W.1

LASKY'S RADIO

FOR THE FINEST VALUE TO HOME CONSTRUCTORS

We consider our construction parcels to be the finest value on the home constructor market. If on receipt you feel not competent to build the set, you may return it as received within 7 days when the sum paid will be refunded less postage.

TRANSISTOR PORTABLES

THE SKYROVER RANGE
7 transistor and 2 diode superhet portables—covering full med. plus 6 SW Bands.

The SKYROVER Mk III.
(Illustrated). Now supplied with redesigned plastic cabinet in black, grey and chrome with edgewise controls.

Controls: Waveband Selector, Volume Control with on/off Switch, Tuning Control. In plastic cabinet, size 10 x 6 1/2 x 3 1/2 in. with metal trim and carrying handle.


Can now be built for **£8.19.6** Post 5/- extra

H.P. Terms: 45/- deposit and 11 monthly payments of 18/9. Total H.P.P. £9.16.3.

The SKYROVER De Luxe
Tone Circuit is incorporated, with separate Tone Control in addition to Volume Control. Tuning Control and Waveband Selector. In a wood cabinet, size 11 1/2 x 6 1/2 x 3 in. covered with a washable material, with plastic trim and carrying handle. Also car aerial socket fitted.

Can now be built for **£10.19.6** Post 5/- extra
H.P. Terms: 55/- deposit and 11 monthly payments of 16/11. Total H.P.P. £12.1.1.

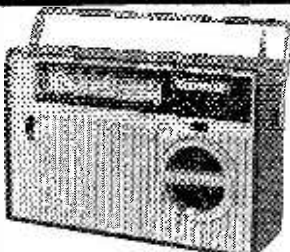Data for each receiver: 2/6 extra. Refunded if you purchase the parcel. Four U2 batteries 3/4 extra. All components available separately.



★ LONG WAVEBAND COVERAGE IS NOW AVAILABLE FOR THE SKYROVER

A simple additional circuit provides coverage of the 1100/1950M. band (including 1800M. Light programme). This is in addition to all existing Medium and Short wavebands. All necessary components with construction data.

Only 10/- extra Post Free.


This conversion is suitable for both receivers that have already been constructed.

REALISTIC SEVEN

Fully tunable long and medium bands. Uses 7 Mullard Transistors; plus Diode OA70.

STAR features:

- 7 Transistor Superhet. ● 350 Milliwatt output 4in. high flux speaker. ● All components mounted on a single printed circuit board, size 5 1/2 in. x 3 1/2 in. in one complete assembly. ● Plastic cabinet, with carrying handle, size 7 in. x 10 in. x 3 1/2 in., in blue/grey. ● Easy to read dial. ● External socket for car aerial. ● I.F. frequency 470 Kc/s. ● Ferrite rod internal aerial. ● Operates from PP9 or similar battery. ● Full comprehensive data supplied with each Receiver. ● All coils and L.F.s, etc. fully wound ready for immediate assembly. An outstanding Receiver.

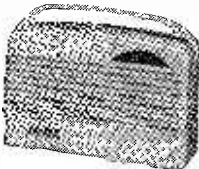

Can be built for **£5.19.6**
P. & P. 4/6

REALISTIC SEVEN De Luxe

With the same electrical specification as standard model—PLUS A SUPERIOR WOOD CABINET IN CONTEMPORARY STYLING covered in attractive washable material with super-chrome trim and carrying handle. Also a full vision circular dial, externally mounted to further enhance the pleasant styling. ONLY 2/- EXTRA

Both models: Battery 3/9 extra. (All components available separately.) Data and instructions separately 2/6, refunded if you purchase parcel.

RECORD PLAYERS

4-Speed Autochangers

B.S.R.

BRAND NEW AT LOWEST EVER PRICES

- Brand new and fully guaranteed—complete with cartridge and stylus.
- UA14 4 speed mains model £4. 9 6
 - UA16 4 speed mains model £4.19.6
 - UA16 9v. battery model £5.19.6
 - UA20 4 speed mains model £5.19.6
- Add 5/- carriage and packing on each.

GARRARD AUTOCHANGERS

- | | |
|---|---------------------------------------|
| Auto-Slim Mono £4 19 6 | AT60 less cartridge £10 19 6 |
| AT6 Mono £5 19 6 | A70 less cartridge £19 19 0 |
| AT6 Stereo £9 0 0 | A50 less cartridge £9 14 6 |
| 3000LX with stereo cartridge £3 8 0 | A1000 with GC8 cartridge £8 6 0 |
| SP25 Mono £9 19 6 | A2000 with GC8 cartridge £7 7 0 |
| SP25 Stereo £10 19 6 | Postage on all above 5/- |

SPECIAL OFFER—GARRARD AT5 AUTOCHANGERS

4-speed mains model—brand new and fully guaranteed
LASKY'S PRICE with Mono Crystal Cartridge £5 19 6
with Stereo Cartridge £8 9 6 Post 5/-.

207 EDGWARE ROAD, LONDON, W.2 Tel: PAD 3271
33 TOTTENHAM CT. RD., LONDON, W.1 Tel: MUS 2605
Both open all day Saturday. Early closing Thursday.

Mail Orders and correspondence to 3-15 Cavell Street, Tower Hamlets, London, E.1. Tel: STEpney Green 4821/2

LASKY'S FOR SPEEDY MAIL ORDER SERVICE

TAPE RECORDERS


MAGNAVOX-COLLARO 363 TAPE DECKS

The very latest 3 speed model—17, 31, 7 1/2 i.p.s., available with either 1/2 track or 1/4 track head. Features include: pause control; digital counter; fast forward and rewind; new 4 pole fully screened induction motor; interlocking keys. Size of top plate 13 1/2 x 11 in. x 5 1/2 in. deep below unit plate. For 200/250 v. A.C. mains, 50 c.p.s. operation. New unused and fully guaranteed.

Lasky's Price 1/2 track **£10.10.0**

Lasky's Price 1/4 track **£13.9.6**

Carriage and Packing 7/6 extra.

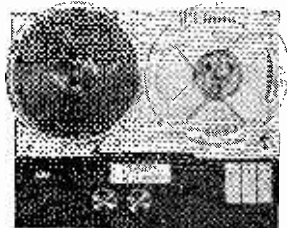

JUST ARRIVED—THE NEW GARRARD TAPE DECK

Fitted with 3 heads—1 track Stereo/mono; three speeds; takes 7 in. spools; p. key controls; digit counter; pause control etc. Send S.A.E. for full details. LASKY'S PRICE 29s. C. & P. 10/6.

CONSTRUCTORS BARGAINS

TRANSISTOR RADIO CHASSIS

Superhet chassis, fully built—by famous British manufacturer—on printed circuit. Uses 7 Newmarket transistors giving 500 m/w push-pull output—3 I.F. stages, ferrite rod aerial. Covers full, long and medium wavebands—200/500M and 1200/2000M and switched band spread on 205M (Luxembourg), 4 1/2 in. speaker; fitted: volume control on/off switch, tuning dial and position for car aerial socket. Uses any 9V battery. Overall dimensions—7 in. x 4 1/2 in. x 2 in. Absolutely complete except for cabinet.

LASKY'S PRICE **6/9** Post 5/-.

Recommended battery PP6 2/9 or PP7 3/3 extra.



TRANSISTORS

ALL BRAND NEW AND GUARANTEED

GET 81, GET S5, GET S6 2/6; 873A, 874P 3/6; OC45, OC71, OC81D 4/6; OC 44, OC 70, OC 76, OC 81 5/6; (match pair 10/6); AF 117, OC 75, OC 200 6/6; OC 42, OC 43, OC 73 OC 82D 7/6; OC 201, OC 204 16/-; OC 206, OC 206 19/6; OC 28 24/6.

TRANSFILTERS By BRUSH CRYSTAL CO. Available from stock.

TO—01B 465 kc/s. ± 2 kc/s.	TO—02D 470 kc/s. ± 1 kc/s.	7/6 each Post 6d.
TO—01D 470 kc/s. ± 2 kc/s.	TF—01B 486 kc/s. ± 2 kc/s.	
TO—02B 466 kc/s. ± 1 kc/s.	TF—01D 470 kc/s. ± 2 kc/s.	

SINCLAIR SUPER MINIATURES

THE MICRO-6 miniature radio only 1 1/2" x 1 x 3 1/2" 1 1/2 in.	£2 19 6
THE SLIMLINE 2-transistor pocket radio	£2 9 6
THE MICRO-FM (tuner/receiver)	£5 19 6
THE X-20 20 watt P.W.M. amplifier	£7 19 6
Available ready built, tested and guaranteed	£9 19 6
THE X-10 10 watt amplifier and pre-amp	£5 19 6
Available ready built, tested and guaranteed	£6 19 6

SPECIAL INTEREST ITEMS!

INTERNATIONAL TAPE

Famous American Brand—Fully Guaranteed

3in. Message tape, 150ft.	2 6	5 1/2 in. Long play, 1,200ft. Acetate.	12 6
3in. Message tape, 225ft.	3 9	5 1/2 in. Standard play, 850ft. PVC.	11 6
3in. Message tape, 300ft.	7 6	5 1/2 in. Long play, 1,200ft. Mylar.	15 0
3 1/2 in. Triple play, 600ft., Mylar.	15 0	5 1/2 in. Triple play, 2,400ft., Mylar.	45 0
4in. Triple play, 900ft., Mylar.	17 6	7 in. Standard play, 1,200ft., Acetate 10 0	0
5in. Double play, 1,200ft., Mylar 15 0	7 in. Standard play, 1,200ft., Mylar 12 6	7 in. Long play, 1,800ft., Mylar 19 6	6
5in. Long play, 900ft., Acetate.	10 0	7 in. Double play, 2,400ft., Mylar 25 0	0
5in. Standard play, 600ft., PVC.	8 6	7 in. Long play, 1,800ft., Acetate 15 0	0
5in. Triple play, 1,800ft., Mylar.	25 0	7 in. Triple play, 3,600ft., Mylar.	58 6
5 1/2 in. Double play, 1,800ft., Mylar 22 6	7 in. Triple play, 3,600ft., Mylar.		

P. & P. 1/- extra per reel. 4 reels and over Post Free.

GORLER UT 340 FM/VHF TUNING HEART

Permeability tuned—covering 87 to 108 Mc/s. For use with one ECC85 valve. In metal case, size 3 x 2 1/2 x 1 1/2 in. Circuit supplied.

LASKY'S PRICE 15/11 Post 2/-
ECC85 valve 9/- extra.

U.H.F. TUNERS

Only a few available. Complete with PC86 and PC88 valves. We regret no circuit or data is available. Knobs included.

LASKY'S PRICE **59/6** Post 2/6



**LASKY'S
RADIO**

GREAT REBUILDING SALE

Due to complete rebuilding
and modernisation of our
premises at 207 EDGWARE
ROAD, W2, we are able
to offer thousands of
unrepeatable bargains
in all departments!

Too many items to list—all at rock bottom prices
PERSONAL CALLERS ONLY to
207 EDGWARE RD., W2
(Open all day Sat.—Early closing Thurs.)
**THIS MONTH
ONLY!**

FREE TO AMBITIOUS ENGINEERS

—THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?

ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio and Electronic Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

SATISFACTION OR REFUND OF FEE

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £30 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

**BRITISH INSTITUTE OF ENGINEERING
TECHNOLOGY**

(Dept. 344B), 29 Wright's Lane, London, W.8

WHICH IS YOUR PET SUBJECT?

Mechanical Eng.,
Electrical Eng.,
Civil Engineering,
Radio Engineering,
Automobile Eng.,
Aeronautical Eng.,
Production Eng.,
Building, Plastics,
Draughtsmanship,
Television, etc.

GET SOME LETTERS AFTER YOUR NAME!

A.M.I.Mech.E.
A.M.I.C.E.
A.M.I.Prod.E.
A.M.I.M.I.
A.I.O.B.
B.Sc.
A.M.I.E.R.E.
City & Guilds
Gen. Cert. of Education
Etc., etc.

PRACTICAL EQUIPMENT

Basic Practical and Theoretic
Courses for beginners in
Radio, T.V., Electronics, etc.,
A.M.I.E.R.E., City & Guilds,
Radio Amateur's Exam
R.T.E.B. Certificate
P.M.G. Certificate
Practical Radio
Radio & Television Servicing
Practical Electronics
Electronics Engineering
Automation

INCLUDING TOOLS!

The specialist Electronics
Division of B.I.E.T.
NOW offers you a real
laboratory training at
home with practical
equipment. Ask for
details.

**B.I.E.T.
SCHOOL OF
ELECTRONICS**

POST COUPON NOW!

Please send me your FREE 156-page
"ENGINEERING OPPORTUNITIES"
(Write if you prefer not to cut page)

NAME

ADDRESS

SUBJECT OR EXAM
THAT INTERESTS ME.....



344B


THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD

BSR MONARCH UA16 with FULL-FI HEAD

4-speed, plays 10 records, 12in., 10in. or 7in. at 16, 33, 45 or 78 r.p.m. Intermixes 7in., 10in., and 12in records of the same speed. Has manual play position, colour, brown. Dimensions: 12½ x 10½in. Space required above baseboard 4½in., below baseboard 2½in. Fitted with Ful-Fi-turn-over crystal head. P. & P. 7/6. **£4.19.6**




CHANNEL TUNER I.F.

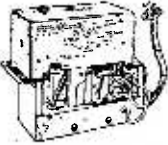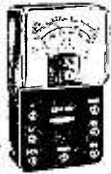16-19 Mc/s. Continuously tunable from 174-216 Mc/s. Valves required—PCF80 and PC84 (in series). Cover BBC and ITA ranges. Also Police, Fire and Taxis, etc. Brand new by famous maker, 10/-, P. & P. 3/-. 

POCKET MULTI-METER

Size 3½ x 2½ x 1½in. Meter size 2½ x 1½in. Sensitivity 1,000 O.P.V. on both A.C. and D.C. volts. 0-15, 0-150, 0-1,000, D.C. current 0-150mA. Resistance 0-100kΩ. Complete with test leads, battery and full instructions, 42/6. P. & P. 3/6. **FREE GIFT** for limited period only. 30 watt Electric Soldering Iron value 15/- to every purchaser of the Pocket Multi-Meter.



8-WATT 5-VALVE PUSH-PULL AMPLIFIER & Metal RECTIFIER

Size: 9 x 6 x 1½in. A.C. Mains, 200-250v, 5 valves. For use with Std. or L.P. records, musical instruments, all makes of pick-ups and mikes. Output 8 watts at 5 per cent total distortion. Separate bass and treble lift control. Two inputs, with controls for gram, and mike. Output transformer tapped for 3 and 15 ohm speech coils. Built and tested, **£3.19.6**. P. & P. 10/-.



"MAYFAIR" 5-Transistor TAPE RECORDER

Capstan-driven, battery operated. 7½ and 3½ in.s Precision made. Push-button controls. High quality 2½in. speaker. Push-pull circuit. Output 400 mW. Frequency response: 200-7,000 k/s. Fast rewind. Up to 1 hour twin track playing time. Automatic erasing for re-recording. Dimensions: 5in. x 11in. x 3½in. Weighs only 7lb. Takes 5in. spools. plus 7/6. P. & P.



£11.11.0




FIRST QUALITY P.V.C. TAPE


5½in. Std. 850ft. 9/-	5in. L.P. 850ft. 10/6
7in. Std. 1200ft. 11/6	3in. T.P. 600ft. 10/6
3in. L.P. 240ft. 4/-	5in. T.P. 1500ft. 25/6
5½in. L.P. 1200ft. 11/6	5½in. T.P. 2400ft. 32/6
7in. L.P. 1500ft. 13/6	7in. T.P. 3600ft. 42/6

P. & P. on each 1/6, 4 or more post free.

MOTOR

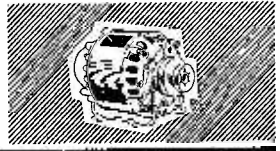½ H.P. 1440 revs., **£2.10.0**.
1/3 H.P. 1440 revs., **£2.18.6**.
P. & P. 10/-.
These have been removed from equipment but are fully guaranteed. Single-phase 230/250V. 

40W FLUORESCENT LIGHT KIT

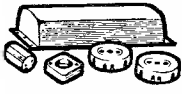


Incorporating GEC Choke size 8½in. x 1½in., 2 bi-pin holders, starter and starter holder. **11/6** P. & P. 4/6.

Similar to above: 80W. Fluorescent Light Kit incorporating GEC choke size 11½in. x 1½in. **17/6** P. & P. 5/6.

2 bi-pin holders, starter and starter holder.

POWER SUPPLY KIT

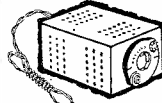


In metal case, size 3½in. x 2½in. x 2in. incorporating mains transformer, rectifier and condensers. 230/250 A.C. Mains Output: 9v. 100 mA. Price 10/6 plus 3/-. P. & P.

CYLDON A.M./F.M. PERMEABILITY TUNER FOR ALL TRANSISTOR OPERATION

Size 2½in. x 2½in. approx. By famous manufacturer. A.M.-I.F. 470 kc/s. F.M.-I.F. 10.7 Mc/s. A.M. coverage from 1,620 kc/s-525 kc/s, F.M. coverage 108 Mc/s-88 Mc/s. Circuit diagram 2/6. **FREE** with Tuner. 1st, 2nd and 4th F.M.-I.F.'s, V.H.F. Osc. choke A.M.-F. traps. All the above are the R.F. end of an A.M./F.M. receiver car radio etc. **£2.10.0**

The above is:

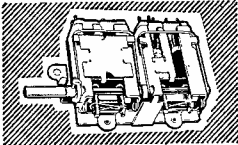

SILICON RECTIFIERS 250 v. P.I.V. 750 milliamps. Six for 7/6, post paid.



MAGNAVOX COLLARO


Set of three Tape Deck Motors. These are made for 110 v. but suitable auto. transformer is supplied. Three motors. 39/6, P. & P. 6/-.

CYLDON U.H.F. TUNER


Complete with PC.88 and PC.86 Valves. Full variable tuning. New and unused. Size 4½ x 5½ x 1½in. Complete with circuit diagram. **35/-** plus 2/6 P. & P.

35/-


plus 2/6 P. & P.

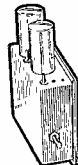

3 to 4 WATT AMPLIFIER KIT

Comprising chassis 8½in. x 2½in. x 1in. Double wound mains transformer, output transformer. Volume and tone controls, resistors, condensers, etc. 6V6, ECC81 and metal rectifier. Circuit 1/6, free with kit. 29/6 plus 4/6. P. & P. 

Fixed Frequency SIGNAL GENERATOR

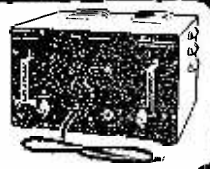Crystal control in metal case, size 10in. x 6in. x 6in. Incorporating 2 FC15 valves, mains transformer, metal rectifier, choke, indicator lamp, crystal and numerous components. Modulated and unmodulated output sockets. Originally used for I.T.V. frequencies. Brand new, 39/6, plus 7/-, P. & P. A.C. Mains 200/250 volts. 


RADIO & T.V. COMPONENTS (ACTON) LTD.

21B HIGH STREET, ACTON, LONDON W.3

SHOP HOURS 9 a.m. to 6 p.m. EARLY CLOSING WEDNESDAY

Goods not despatched outside U.K. All enquiries stamped addressed envelope. Terms C.W.O.

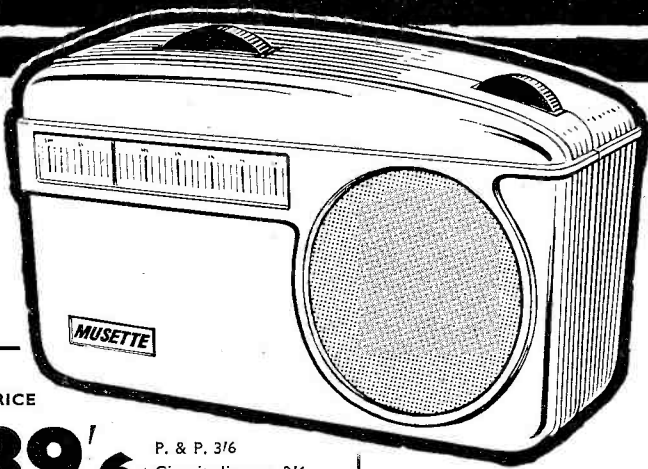MUSETTE 6 TRANSISTOR SUPERHET PORTABLE RADIO



PRICE


39'6

P. & P. 3/6
Circuit diagram 2/6.
Free with parts.

INCLUDING CARRYING STRAP.

- 2 1/4" Speaker.
- 6 Transistors Superhet Output 200mw.
- Plastic Cabinet in red, size 4 3/4" x 3" x 1 3/8" and gold speaker louvre.
- Horizontal Tuning Scale.
- Ferrite Rod Internal Aerial.
- IF 470 Kc.
- All components, Ferrite Rod and Tuning Assembly mounted on printed board.
- Operated from PP3 Battery.
- Full comprehensive instructions and point-to-point wiring diagram.
- Printed Circuit Board.
- Tunable over medium and long wave band. Car aerial and ear piece socket.

NEW TRANSISTORISED SIGNAL GENERATOR

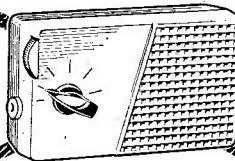

Size 5 1/2" x 3 1/2" x 1 1/2". For IF and RF alignment and AF output 700 c/s frequency coverage 460 Kc/s to 2 Mc/s in switched frequencies. Ideal for alignment to our Elegant Seven and **39/6** P. & P. Musette. Built and tested. 3/6

Elegant Seven Mk II

COMBINED PORTABLE And CAR RADIO

The Radio with the STAR features

- ★ 4in. Speaker.
- ★ 7-transistor superhet. Output 350mW.
- ★ Wooden cabinet, fitted handle with silver coloured fittings. Size 12 1/2 x 8 1/2 x 3 1/2 in.
- ★ Horizontal tuning scale, size 11 1/2 x 2 3/8 in. in silver with black lettering.
- ★ All stations clearly marked.
- ★ Ferrite-rod internal aerial.
- ★ I.F. neutralisation on each stage 460 kc/s.
- ★ D.C. coupled output stage with separate A.C. negative feed back.
- ★ All components: ferrite rod and tuning assembly mounted on printed board.
- ★ Operated from PP9 battery.
- ★ Full comprehensive instructions and point-to-point wiring diagrams.
- ★ Printed circuit board, back printed with all component values.
- ★ Fully tunable over medium and long waveband.
- ★ Car aerial socket. Full after-sale service.

ONLY £4.4.0

Plus 6/6 P. & P. Parts list and circuit diagram 2/6. FREE with parts.



POWER SUPPLY KIT

To purchasers of "Elegant Seven" parts, incorporating mains transformer, etc. A.C. mains 200-250v. Output 9v. 50mA. 7/6 extra.

ALL ENQUIRIES STAMPED ADDRESSED ENVELOPE

RADIO & TV COMPONENTS (ACTON) LTD
21C HIGH STREET · ACTON · LONDON · W.3

OPEN 9 a.m.—6 p.m. INCLUDING SATS. EARLY CLOSING WED. GOODS NOT DESPATCHED OUTSIDE U.K. TERMS C.W.O.

The new magazine for the experienced amateur and the beginner



MAY ISSUE
OUT NOW

2/6

DON'T MISS IT!

OTHER OUTSTANDING FEATURES

HOW TO MAKE A DRESSING
TABLE AND STOOL
CONSTRUCTING A
DROP-LEAF TABLE
WOODTURNING FOR
PLEASURE AND PROFIT
WOODWORKING TOOLS
WAYS WITH FIBREBOARD
MODERN CARVING IN RELIEF

EXTRA!
EXTRA!

To tackle all those home woodworking jobs you need **PRACTICAL WOODWORKING**—the great new practical monthly packed with ideas and instructions on the whole field of working in wood. Make sure of the May issue with this invaluable **FREE Booklet** and extra features inside!

FREE! 16-PAGE BOOKLET **GUIDE TO WOOD SECTIONS & SIZES**

All you want to know to select the right wood from timber yard ranges for any woodworking project. Sections on Machined Mouldings — Hardboards — Wallboards — Flooring — Door Styles — Fencing — Rough-Sawn Wood.

Fold-out Sheet to build

- ★ Saw Sharpening Clamps
- ★ Hop-up Steps and Decorators' Trestles

DATA SHEET for BOLTS,
FASTENERS and HINGED FITTINGS

PRACTICAL
WOODWORKING

PRACTICAL WOODWORKING
SELLS OUT FAST
GO FOR YOURS NOW!



MAIL ORDERS TO:
102 Henconner Lane
Bramley, Leeds 13

Terms: C.W.O. or C.O.D. No C.C.I. under £1. Postage 2/9 extra under £2. 4/6 extra under £5. Trade Supplied. S.A.E. with all enquiries please. Personal shoppers welcome at any branches below. Open all day Saturday.

BRADFORD 10 North Parade. Tel. (Half-day Wed.) 25349
BRISTOL 14 Lower Castle Street (Half-day Wednesday) Tel.: 22904

BIRMINGHAM 30/31 Gd. Western Hill Station. CENTRAL 1279. No half-day

DERBY 26 Osmaston Rd., The Spot (Half-day Wed.) Tel.: 41361

DARLINGTON 13 Post House Wynd (Half-day Wednesday) Tel.: 68043

EDINBURGH 133 Leith Street, (Half-day Wed.) Tel.: 41361

GLASGOW 326 Argyle St. Tel.: (No half-day) CITY 4158

HULL 51 Savile Street (Half-day Thursday) Tel.: 20505

LEICESTER 32 High Street (Half-day Thurs.) Tel.: 56420

LEEDS 5-7 County (Mecca) Arcade (No half-day) Tel.: 28252

LIVERPOOL 73 Dale St. (No half-day) Tel.: CENTRAL 3573

LONDON 238 Edgware Road, W2 (Half-day Thursday) Tel.: PADDINGTON 1629

MANCHESTER New large store. (No half-day) 60A-60B Oldham St. Tel.: CENTRAL 2778

MIDDLESBROUGH (Half-day Wednesday) Large walk-round store. 106 Newport Road. Tel.: 47096

SHEFFIELD 13 Exchange Street Castle Market Bldgs. (Half-day Thursday) Tel.: 20716

STAFF REQUIRED. Full or part-time at various branches. Experience unnecessary.


ARMSTRONG, TRUVOX, LEAK, QUAD, ROGERS, LINEAR, W.B., FANE, WHARFEDALE, GOODMAN, GARRARD, GOLDRING, GRAMPIAN, LUSTRAPHONE, SHURE, RESLO, TANDBERG, FERROGRAPH Products stocked. Usual credit terms available.

EX GOVT. SELENIUM RECTIFIERS 12v 15 AMP (BRIDGE) F.V. ONLY 19/9

TRANSISTOR SALE Mullard OC71 2/11, OC45 3/11, OC44 3/11, OC72 2/11, OC81 1/11, OC171 8/9, AF117 6/9, Ediswan XA101 3/9, XA112 3/9, XC101A 3/9. Postage 6d. for up to 3 transistors.

INTRODUCING A NEW RANGE OF HIGH FIDELITY LOUDSPEAKER UNITS

AUDIOTRINE PETITE Really astounding performance. Size only 10 1/2 x 6 1/2 x 7 1/2 in. Rating 8 watts. Frequency range 45-20,000 c.p.s. Cabinet beautifully finished in Teak (light) or Walnut (medium). Fitted specially designed Heavy cast 6in. speaker with large pole pieces, extra long voice coil and plastic treated surround. Impedance 3 ohms or 15 ohms. Or Deposit 29/6 and 9 monthly payments of 19/10 (Total £10.8.0). **9 Gns.** Carr. 7/6

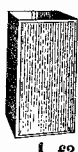

The AUDIOTRINE MINI-TEN Size only 12 1/2 in. High, 6 1/2 in. Wide, 8 1/2 in. Deep. Rating 10 watts. Impedance 15 ohms. De-luxe Teak or Walnut finished cabinet acoustically lined. Heavy cast 5 1/2 in. Bass speaker with extra high flux density ceramic magnet plastic treated surround and long voice coil giving low fundamental resonance. Cross-over and Tweeter. Really astounding performance. Frequency range 45-20,000 c.p.s. Or Deposit 29/6 and 9 monthly payments 27/9 (Total £14.9.0). **12 Gns.** Carr. 8/6

The GLOUCESTER Handsome "slimline" cabinet, acoustically lined. Size 24in. High, 20in. Wide, 6 1/2 in. Deep. Finished light Teak or medium Walnut. 12in. high flux 12,000 line speaker, Cross-over unit and Tweeter. Rating 10 watts. Smooth response 40-20,000 c.p.s. Impedance 15 ohms. Or Deposit 36/- and 9 monthly payments 24/8 (Total £12.18.0) **11 Gns.** Carr. 15/-



The BRONTE Handsome cabinet of modern styling. Acoustically lined and finished Teak or Walnut. Size 22in. High, 15in. Wide, 7in. Deep. Fitted Wharfedale Super 8 RSDD Speaker, with Roll surround and dual cone. Rating 6 watts. Impedance 15 ohms. Or Deposit 39/- and 9 monthly payments 26/10 (Total £14.0.6). **12 Gns.** Carr. 15/-

The DORCHESTER Attractive cabinet in luxurious Teak or Walnut finish. Acoustically lined. Size 24in. High, 15in. Wide, 7in. Deep. Incorporating specially designed 10in. Heavy cast speaker with massive 2in. pole pieces and dual cone with plastic treated surround. Frequency response 20-20,000 c.p.s. Rating 15 watts. Impedance 15 ohms. Or Deposit 48/- and 9 monthly payments 33/- (Total £17.7.8). **15 Gns.** Carr. 15/-



The STANWAY Attractive contemporary styled cabinet finished Teak (light) or Walnut (medium). Acoustically lined. Size 24in. High, 20in. Wide, 8 in. Deep. Fitted 12in. high flux Bass speaker with plastic treated surround giving extremely low fundamental resonance and high sensitivity. The smooth frequency response 20-20,000 c.p.s. is achieved by addition of high flux tweeter and cross-over unit. Rating 20 watts. Impedance 9 ohms. Or Deposit 33/- and 9 monthly payments 43/4 (Total £22.18.0). **19 Gns.** Carr. 17/6

AUDIOTRINE HIGH FIDELITY LOUDSPEAKER ENCLOSURES
All types of pleasing modern "slimline" design acoustically lined and ported in alternative finishes of light Teak or medium Walnut.



SE8. Designed for optimum performance with any HI-FI 8in. speaker. Size 22in. High, 15in. Wide, 7in. Deep. Or Deposit 18/- and 9 monthly payments 12/3 (Total £6.5.3). Carr. 7/6

SE10. For 10in. High Fidelity Speaker with provision for tweeter. Especially recommended for use with Audiotrine HF100D speaker. Size 24in. High, 15in. Wide, 7 1/2 in. Deep. Or deposit 21/- and 9 monthly payments of 15/- (Total £7.16.0). Carr. 10/-
SE12. For outstanding performance with any 12in. HI-FI Speaker but especially suitable for types with low fundamental resonance. A tweeter cut-out is provided. Size 24 x 20 x 7 1/2 in. approx. ONLY Or Deposit 27/- and 9 monthly payments of 17/10 (Total £9.7.6). Carr. 10/- **8 Gns.**


AUDIOTRINE HI-FI SPEAKER SYSTEMS
Consisting of matched 12in. 12,000 line, 15 ohm high quality speaker; cross-over unit (consisting of choke, condenser, etc.) and Tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. Standard 10 watt rating. Or Senior 20 watt inc. Fane **\$4.19.9**
122/10 speaker, £6.19.9. Carr. 5/6
7/6. Or Dep. 21/- and 9 mthly pmts of 15/- (Tot £7.16.0).



JASON FM11. VHF/FM Radio Tuner design. All parts including valves, tuning dial, esutcheon, etc. Carr. 5/- **\$6.19.9**

COMPLETE POWER PACK KIT
Consisting of Mains Transformer, Metal Rectifier, Electrolytics, smoothing choke, chassis and circuit. 200/250v. A.C. mains. Output 250v. 60mA, 6.3v. 2a or with metal cover 25/- **19/11**

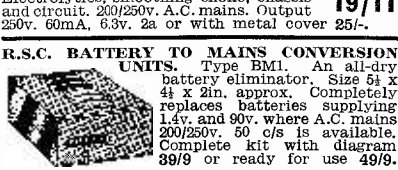R.S.C. BATTERY TO MAINS CONVERSION UNITS. Type BM1. An all-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2in. approx. Completely replaces batteries supplying 1.4v and 6v. where A.C. mains 200/250v. 50 c/s is available. Complete kit with diagram 39/9 or ready for use 49/9.



AUDIOTRINE HF100D 10in. 15 watt HI-FI Loudspeakers. Heavy cast construction. Dual cone. Smooth frequency response 20-20,000 c.p.s. Speech coil or 15 ohms. Exceptional value at **\$5.15.0** Carr. 5/9



FANE HEAVY DUTY HI-FI SPEAKERS
12in. 20 watt. Type 122/10. Post 5/6. ONLY **5 Gns.**

W.B. "STENTORIAN" HIGH FIDELITY P.M. SPEAKERS HF1012. 10 watts rating. Where a really good quality speaker at a low price is required we highly recommend this unit with an amazing performance. Please state whether 3 or 15 ohms required. **\$4.19.9**

TANNOY RE-ENTRANT LOUDSPEAKERS. For outdoor or factory use, 8 ohms, 8 watts. **27/6** Carr. 4/6


R.A. 12in. DUAL CONE 3 ohm LOUDSPEAKERS. Ideal for Stereo. **39/9. Carr. 4/6**

R.S.C. BABY ALARM OR INTERCOMM KIT
Parts with diagrams, etc. in two polished Walnut finished cabinets. 3-4 watts output. High sensitivity. For 200-250v. A.C. mains. Fully isolated. Controllable at both units. A unit of this class would normally cost £20-£30. Only 89/6. Carr. 5/- Ready for use, 6 Gns.

R.S.C. SUPER 15 HI-FI AMPLIFIER WE PROUDLY INTRODUCE R.S.C. SUPER 30 STEREO AMPLIFIER

FULLY TRANSISTORISED 200/250v. A.C. Mains Operation.
OUTPUT 10 WATTS R.M.S. into 15 ohms.
15 WATTS R.M.S. into 3-4 ohms.
Maximum instantaneous Peak power output 28 watts
PRINTED CIRCUIT CONSTRUCTION.
LATEST MULLARD TRANSISTORS. AD149, AD149, OC12Z, OC81Z, OC44, OC44, OC81Z, OC44, AC107
3 POSITION INPUT SELECTOR SWITCH EQUALISATION to Standard R.I.A.A. and C.C.I.R. Characteristics for Gram and Tape Heads.
FULL TAPE MONITORING FACILITIES.
SENSITIVITIES: Magnetic 12.4 mV, Crystal or Ceramic P.U. 400 mV, Microphone 4.5 mV, Tape Head 2.5 mV. Radio/Aux or Ceramic P.U. 110 mV
FREQUENCY RESPONSE: 20-20,000 c.p.s.
TREBLE CONTROL: +15dB to -14dB at 10 Kc/s.
BASS CONTROL: +12dB to -15dB at 50 cps.
HARMONIC DISTORTION at 10 Watts R.M.S. 1,000 c.p.s. 0.35%. **HUM LEVEL:** -75dB.
NEGATIVE FEEDBACK: 52dB.
Complete Kit of parts with full constructional details and point to point wiring diagrams. Carr. 10/- **10 1/2 GNS.**
Or Kit with Printed Circuit wired and tested 30/- extra, or Deposit 72/- and 9 monthly payments of 29/6 (Total £14.14.6).
Attractive Walnut or Teak finished cabinet 5 gns, or Deposit 17/- and 9 monthly payments 11/- (Total £5.16.0). Or unit factory built and tested, complete with cabinet and with our usual 12 months guarantee. Or Deposit £13.9.0 and 9 monthly payments 22 (Total £21.9.0). **18 1/2 GNS.** Carr. 12/6

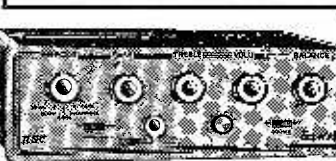COMPLETELY NEW UNITS WITH TECHNICAL SPECIFICATIONS COMPARING MORE THAN FAVOURABLY WITH SIMILAR AMPLIFIERS AT 2-3 TIMES THE COST




IMPORTANT NOTE. Rated output figures are given in R.M.S. and not speech and music or I.H.F.M., otherwise we could obviously quote much higher outputs.

A DUAL CHANNEL VERSION OF THE SUPER 15. Employing Twin Printed Circuits. Close tolerance Ganged Pots. Matched Components.
CROSS-TALK: -52dB at 1,000 c.p.s.
CONTROLS: 5 position Input Selector, Bass Control, Treble Control, Volume Control, Balance Control, Stereo/Mono Switch, Tape Monitor Switch, Mains Switch.
INPUT SOCKETS (Matched Pairs). (1) Magnetic P.U. (2) Ceramic or Crystal P.U. (3) Radio/Aux. (4) Tape Head/Microphone.
Operation of the Input Selector Switch assures appropriate equalisation.
Rigid 16 s.w.g. Chassis. Size approx. 12in. Wide, 3in. High and 8in. Deep.
Attractive Facia Plate and Matching Knobs. Neon Panel Indicator.
Above facilities, etc., except for Ganging and Balance Control, apply also to Super 15.
THESE UNITS ARE EMINENTLY SUITABLE FOR USE WITH ANY MAKE OF PICK-UP OR MICROPHONE (Crystal, Ceramic, Magnetic, Moving Coil, Ribbon) CURRENTLY AVAILABLE REGARDLESS OF THE COST. SUPERB SOUND OUTPUT QUALITY CAN BE OBTAINED BY USING WITH FIRST RATE ANCILLARY EQUIPMENT. All required parts, point to point wiring diagrams and detailed instructions. 3 required printed circuits can be supplied with appropriate components assembled, soldered and tested for £3 extra. Terms: Deposit 6 Gns, and 9 monthly payments 38/6 (Total £23.12.6). Carr. 12/6 **18 GNS.**
Attractive Walnut or Teak finished cabinet 5 Gns, or Deposit 17/- and 9 monthly payments 11/- (Total £5.16.0). Or unit completely assembled ready for use housed in cabinet. Or Deposit £4.12.0 and 9 monthly payments 64/- (Total £33.8.0). Carr. 15/- **29 GNS.** Send S.A.E. for leaflet.

ALL COMPONENTS ETC. ARE OF A HIGH STANDARD AND SUPPLIED BY LEADING BRITISH MANUFACTURERS.

R.S.C. STEREO 20/HIGH FIDELITY AMPLIFIER

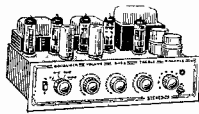

PROVIDING 10/14 WATT ULTRA LINEAR PUSH-PULL OUTPUT ON EACH CHANNEL
 SUITABLE FOR "MIKE", GRAM, RADIO OR TAPE
 Based on a current Mullard design and employing valves ECC83, ECC83, EL84, EL84, ECL86, ECL86, ECL86, E281. Send s.a.e. for leaflet.
 Frequency Response: +2dB 30-20,000 c.p.s.
 Hum Level: 65dB down. Sensitivity: 5 millivolts maximum.
 Harmonic Distortion: (each channel) 0.2%.

- ★ Four-position tone compensation and Input Selector switch.
- ★ Will amplify direct from Tape Heads.
- ★ Stereo/Mono switch.
- ★ Separate Bass "Lift" and "Cut" and Treble "Lift" and "Cut" controls.
- ★ Neon panel indicator.
- ★ Handsome Perspex Frontplate.

Output transformers are high-quality sectionally wound to required specification. Output matching for 3 and 15 ohm speakers on each channel. Complete set of parts with point-to-point wiring diagrams and instructions. Carr. 12/6
 Or factory assembled, tested and supplied with our usual 12 months guarantee. Carr. 12/6
 Or Deposit 57/- and 9 monthly payments 39/10 (Total £20.15.6) Carr. 12/6

AUDIOTRINE HI-FI TAPE RECORDER KIT

REALISM AT INCREDIBLY LOW COST, CAN BE ASSEMBLED IN AN HOUR, ONLY 4 PAIRS OF SOLDERED JOINTS PLUS MAINS.

Incorporating the latest Magnavox Tapedeck. The Audiotrine High Quality Tape Amplifier with switched equalisation for each of 3 speeds. High Flux P.M. Speaker, empty Tape Spool, a Reel of Best Quality Tape and a handsome Portable Carrying Cabinet of latest styling and finished dark grey leathercloth. Size 14" x 17" x 8 1/2". Unit and circuit. Total cost if purchased individually approximately £35. Performance 25 1/2 Carr. equal to units in the £50-£60 class. S.A.E. and 13/6 for leaflets. TERMS: Deposit 4 gns. and 9 monthly payments of 56/- (Total 28 gns.). 4 Track Model 3 gns. extra.



R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER



A highly sensitive Push-Pull high output unit with self-contained Pre-amp./Tone Control Stages. Performance figures compare equally with most expensive amplifiers available. Hum level -70dB. Frequency response +3dB 30-20,000 c/s. A specially designed sectionally wound ultra linear output transformer is used with 307 output valves. All first grade components. Valves EF86, EF86, ECC83, 807, 807, GZ34. Separate Bass and Treble Controls. Minimum input required for full output 12 millivolts so that any kind of Microphone or Pick-up is suitable. The unit is designed for Clubs, Schools, Theatres, Dance Halls or Outdoor Functions, etc. For use with Electronic Organ, Guitar, String Bass, etc. Output Socket provides L.T. and H.T. for Radio Tuner. Two inputs with associated volume controls so that two separate inputs such as Gram and "Mike" can be mixed. 200-250v. 50 c/s A.C. mains. Output for 3 and 15 ohm speakers. Complete kit of parts with fully punched chassis and point to point wiring diagrams and instructions. Carr. 10/-
 Supplied factory built with EL34 output valves, 12 months guarantee for 15 gns. If required perforated cover with carrying handles can be supplied for 31/- Send s.a.e. for leaflet. TERMS: Deposit 48/- & 9 mthly payments of 33/3 (Total £17.7.3).

HIGH FIDELITY 12-14 WATT AMPLIFIER TYPE A11



PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP
 Two input sockets with associated controls allow mixing of "mike" and gram, etc., etc. High sensitivity valves ECC83, ECC83, EL84, EL84, E281. High quality sectionally wound transformer specially designed for Ultra Linear operation and reliable small condensers of current manufacture. INDIVIDUAL CONTROLS FOR BASS AND TREBLE "Lift" and "Cut". Frequency response +3dB 30-20,000 c/s. Six negative feedback loops. Hum level -60dB. SENSITIVITY 23 millivolts. Suitable for Gram or Ceramic P.U. all types of "mikes". Comparable with the very best designs. For Musical Instruments such as String Bass, Electronic Guitars, etc. Output Socket provides 300v. 30mA, and 6.3v. 1.5a. for supply of a Radio Tuner. Kit complete to last nut. Chassis fully punched. Full instructions and point-to-point wiring diagrams supplied (or factory built 51/9 extra). Carr. 10/-
 Metal covers with 2 carrying handles can be supplied for 42/-
 TERMS: Deposit 33/3 and 9 monthly payments of 24/1 (Total £12.10.0). Send S.A.E. for illustrated leaflet detailing Cabinets, Speakers, Mikes, etc.

R.S.C. STEREO/TEN HIGH QUALITY AMPLIFIER



A complete set of parts for the construction of a stereo amplifier providing 10 watts output on each channel (total 20 watts). Sensitivity is 50 millivolts. Suitable all crystal or ceramic stereo heads. Ganged Bass and Treble Control give equal variation of "Lift" and "cut". Provision is made for use as straight (monaural) 10 watt amplifier. Valve line-up ECC83, ECC83, EL84, EL84, E281. Outputs for 2-3 ohm speakers. Point to point wiring diagrams and instructions supplied. Send S.A.E. for leaflet. Full constructional details and price list 2/6. Carr. 8 Gns.
 Or supplied factory assembled with 12 months' Carr. 10/-
 guarantee for £11.7.6. Terms: Dep. 2 gns. and 9 mthly pmts 24/2 (Total £12.19.6).

R.S.C. 4/5 watt A5 HIGH GAIN AMPLIFIER



A highly-sensitive 4-valve quality amplifier for the home, small club, etc. Suitable for all crystal or ceramic P.U. heads and practically all "mikes". Separate Bass and Treble controls giving "Lift" and "cut". Hum level 71dB down. Negative Feedback 15dB. H.T. of 300v. 25mA and L.T. of 6.3v. 1.5a. available for supply of Radio Tuner or Tape Deck pre-amp. For A.C. mains 200-250v. Speaker output 3 ohms. Kit is complete in every detail with fully punched Hammer finished chassis, point-to-point wiring diagrams and instructions. Exceptional value £4.15.0
 or assembled ready for use 25/- extra, plus 3/6 carr. Deposit 22/6 and 5 monthly payments of 22/6 (Total £6.15.0) for assembled unit.

COMMUNICATION RECEIVERS RX 60 DE LUXE



4 BAND. 220/240v. 50/60 c.p.s. A.C. mains operation. Frequencies covered 1600 Kc/s to 30 Mc/s continuous. Incorporates 5in. speaker. Slide rule tuning dial 'S' meter. Internal ferric aerial 55in. section for short waves. Five sockets for optional outdoor aerial. Headphones external speaker socket. Other features are electrical hand-spread tuning. Noise limiter, A.V.C., B.F.O., stand-by switch. Size approx. 12 1/2 x 5 1/2 x 8 1/2 in. Handsome crackle finished metal cabinet. Brand new with full instructions manual. Usual guarantee. Carr. 10/-
 Or Deposit £5 and 9 monthly payments 37/8 (Total £21.19.0).

R.S.C. A15 20 WATT (R.M.S.) HI-FI TRANSISTOR AMPLIFIER with integral pre-amp tone control stages

Output for 3, 7.5 and 15 ohm speakers. Kit of parts consisting of Printed Circuit and all components for same including 9 Mullard or Newmarket latest type semi-conductors. Heat sink and full wiring instructions or with printed circuit fully wired and tested £2 extra.
 Frequency Response: +1dB 20-20,000 cps. Carr. 10/-
 Harmonic Distortion: 0.1% measured at Post 5/-
 1000 c.p.s. Hum and Noise: -30dB. Sensitivity: 2 mV.
 Bass Control: +9dB to -14dB at 40 c.p.s. Treble Control: +8dB to -13dB at 10 Kc/s. Suitable Power Pack Kit 39/6 or ready built 59/6.



£6.19.9

R.S.C. COLUMN SPEAKERS

Covered in two-tone Rexine/Vynair. Ideal for vocalists and Public Address. Normally supplied for 15 ohm matching but can be supplied for 100v. line for 35/- extra.
 Type C38, 15-20 watts. Fitted five 8in. high flux speakers. Overall size approx. Carr. 12 1/2 Gns.
 42 x 10 x 3 1/2 in. Or Deposit £2 and 9 monthly pmts 27/9 (Total £14.9.9) Carr. 10/-
 Type C42, 40 watts. Fitted four 12in. 12,000 line 10 watt speakers. Overall size Carr. 15/-
 56 x 14 x 9in. approx. Carr. 15/-
 Or Deposit 3 gns. and 9 monthly payments of 43/2 (Total £11 gns.).



18in. 60 WATT EXTRA HEAVY DUTY LOUDSPEAKERS

Famous make. Normal price over £25. Very limited number to clear with full guarantee. Terms available. Carr. 15/-

30 WATT HI-FI AMPLIFIER for Lead, Rhythm, Bass Guitar, Vocal or Instrumental Groups

A Four input, two volume control Hi-Fi unit with separate Bass and Treble 'cut' and 'boost' controls. Latest type valves. Housed in strong Rexine covered cabinet with twin carrying handles. Attractive black and gold perspex fascia plate. For 200-250v. A.C. mains. Output for 3 or 15 ohm speakers. Send S.A.E. for leaflet. Deposit £3 and 9 monthly payments of 37/- (Total £19.13.0). Carr. 12/6



17 Gns.


INTEREST CHARGES REFUNDED

on H.P. and Credit Sale Accounts settled in 6 months.

LINEAR TAPE PRE-AMPLIFIER. Type LP/1. Switched Equalisation Positions for Recording at 1in., 3in., 7in. per sec. and Playback, EM84 Recording Level Indicator. Designed primarily as the link between a Magnavox Tape Deck and Hi-Fi amplifier, suitable almost any Tape Deck. S.A.E. for 9 1/2 Gns. leaflet.


CORNER CONSOLE CABINETS

Strongly made. Beautiful polished walnut veneered finish. Pleasing design. Junior Model. For up to 8in. speaker. Approx. 20 x 11 x 8in. Carr. 5/6 49/9
 Standard Model. To take up to 10in. speaker. Size 27 x 18 x 8in. Carr. 7/6 5 Gns.
 Senior Model. To take up to 12in. speaker and with 'Tweeter cut-out. Size approx. 30 x 30 x 15in. (Recommended for use with Audiotrine speaker system.) Carr. 8/6 8 Gns.
 Terms available. Carr. 8/6

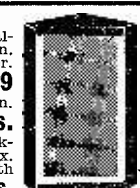

12in. HIGH QUALITY LOUDSPEAKERS

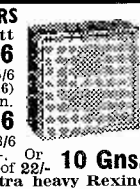In walnut veneered cabinet. 10 Watt Model. Gauss 12,000 lines. £4.19.6
 Speech coil 3 or 15 ohms. Carr. 5/6
 Terms: Deposit 15/- and 9 Carr. 8/6
 monthly payments of 10/10 (Total £5.12.6)
 20 Watt Model. 15 ohm. Size 18x18x10in.
 Terms: Deposit 24/6 and 9 Carr. 8/6
 monthly payments of 17/- £7.19.6
 (Total £8.17.6).



R.S.C. JUNIOR BASS REFLEX CABINET.

Designed for above speaker, but suitable for any good quality 8in. or 10in. speaker. Acoustically lined and ported. Medium Walnut veneer finish. Size 18 x 12 x 10in. Strongly made. Handsome appearance. Superb reproduction. Carr. 5/-

SELENIUM RECTIFIERS F.W. (BRIDGED)

6/12v. 1a, 3/11; 6/12v. 3a, 9/9; 6/12v. 6a, 15/3; 6/12v. 2a, 6/11; 6/12v. 4a, 12/3; 6/12v. 10a, 26/9.

R.S.C. GRAM AMPLIFIER KIT. 3 watts output.

Negative feedback. Controls: Vol., Tone and Switch. Mains operation 200-250v. A.C. Fully isolated chassis. Circuit, etc., supplied. Only 39/9. Carr. 3/9.


R.S.C. 4 WATT GRAM AMPLIFIER KIT. Complete set of parts to build a good quality compact unit suitable for use with any record playing unit.

Mains isolated chassis, separate Bass and Treble controls. Output for 2-3 ohm speaker. For 200-250 v. A.C. Carr. 59/9



For addresses see page 11

R.S.C. BASS-REGENT 50 WATT AMPLIFIER

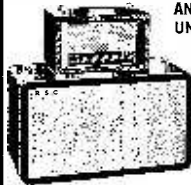

AN EXCEPTIONALLY POWERFUL HIGH QUALITY ALL-PURPOSE UNIT For lead, rhythm, bass guitar and all other musical instruments. For vocalists, gram, radio, tape and general public address

- ★ UNUSUALLY POWERFUL LOUDSPEAKER-COMBINATION consisting of a FANE HIGH FLUX 15in. 30 watt unit PLUS a FANE 12in. 20 watt unit with extended frequency response. ★ 4 Jack Inputs and two Volume Controls for simultaneous use of up to 4 pick-ups or "mikes".
- ★ Cabinets covered in two-tone Rexine/Vynair with gold trimming. Fitted carrying handles. ★ Separate Bass and Treble Controls giving "lift" and "cut". Send S.A.E. for leaflet. Or call at one of our many branches and compare the Bass-Regent with units at more than three times the cost.

49 Gns.
Carr. 25/-
Or deposit £7.18.0 and 9 monthly payments of £5.8.8 (Total 54 gns.)



R.S.C. MAINS TRANSFORMERS

FULLY GUARANTEED

Interleaved and Impregnated. Primaries 200-230-250 v. 50 c/s. Screened.

MIDGET Clamped Type 2½ x 2½ x 2½in.
250v. 60mA. 6.3v. 2a ... 13/9
250-0-250v. 60mA. 6.3v. 2a ... 14/9

TOP SHROUDED DROP THROUGH
250-0-250v. 70mA. 6.3v. 2a. 0-5-6.3v. 2a 17/9
350-0-350v. 80mA. 6.3v. 2a. 0-5-6.3v. 2a 21/9
250-0-250v. 100mA. 6.3v. 2a. 6.3v. 1a ... 21/9
250-0-250v. 100mA. 6.3v. 3.5a C.T. ... 19/9
300-0-300v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a 28/9
300-0-300v. 100mA. 6.3v. 4a. 6.3v. 1a. for Mullard 510 Amplifier ... 35/9

300-0-300v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a 28/9
350-0-350v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a 28/9
350-0-350v. 150mA. 6.3v. 4a. 0-5-6.3v. 3a 37/9

FULLY SHROUDED UPRIGHT
250-0-250v. 60mA. 6.3v. 2a. 0-5-6.3v. 2a. ... 18/9
Midget type 2½ x 3 x 3in. ... 29/9
250-0-250v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a 29/9
300-0-300v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a 29/9
300-0-300v. 130mA. 6.3v. 4a. C.T. 6.3v. 1a. for Mullard Amplifier ... 36/9
350-0-350v. 100mA. 6.3v. 4a. 0-5-6.3v. 3a 29/9
350-0-350v. 150mA. 6.3v. 4a. 0-5-6.3v. 3a 38/9
425-0-425v. 200mA. 6.3v. 4a. C.T. 5v. 3a 57/9
425-0-425v. 200mA. 6.3v. 4a. Twice 5v. 3a 59/9
450-0-450v. 250mA. 6.3v. 4a. C.T. 5v. 3a 69/9

FILAMENT TRANSFORMERS
200-250v. 50c/s primaries 6.3v. 1.5a. 6/6; 6.3v. 2a. 7/6; 12v. 1a. 7/11; 6.3v. 3a. 8/11; 6.3v. 6a. 17/6; 12v. 1.5a. twice. 17/6.

OUTPUT TRANSFORMERS
Standard Pentode 7,000Ω to 3Ω ... 6/6
Standard Pentode 7,000Ω to 3Ω ... 6/6
Push-Pull 8 watts, EL84, or 6V8 to 3Ω or matched to 15Ω ... 9/9
Push-Pull 10-12 watts to match 6V6 or EL84 to 3-5-3 to 15Ω ... 19/9
Following types for 3 and 15Ω speakers:
Push-Pull 10-12 watts, 6V6 or EL84 ... 18/9
Push-Pull 15-18 watts, 6L6, KT66 ... 22/9
Push-Pull Mullard 510 Ultra Linear ... 28/9
Push-Pull 20 watts, sectionally wound 6L, KT66, EL84 etc. ... 49/9

SMOOTHING CHOKES
60mA. 10H. 400Ω 4/11. 100mA. 10H. 220Ω 8/9
80mA. 10H. 350Ω 5/9. 150mA. 10H. 250Ω 11/9

CHARGER TRANSFORMERS
All with 200-240-250v. 50 c/s Primaries:
0-9-15v. 11a., 12/8; 0-9-15v. 2a. 14/9; 0-9-15v. 3a. 16/9; 0-9-15v. 5a. 19/9; 0-9-15v. 6a. 23/9; 0-9-15v. 8a. 28/9.

AUTO (Step up/Step down) TRANS.
0-110/120-230/250v. 60-90 watts, 13/9; 150 watts, 27/9; 250 watts, 49/9; 500 watts, 99/9.

R.S.C. B20 MULTI-PURPOSE AMP. especially suitable for Bass Guitar.

Incorporating massive 15in. high flux loudspeaker. Rating 25 watts. Individual bass and treble controls. Two jack inputs separately controlled. Substantial cabinet attractively finished in Rexine and Vynair. Size approx. 24 x 21 x 11in. Send S.A.E. for leaflet. Or Deposit £4.14.6 and 9 monthly payments of 64/2 (Total 32 gns.).

29½ Gns.
Carr. 17/6



R.S.C. G15 15 WATT AMPLIFIER for Lead or Rhythm Guitar, Mike, Gram or Radio

High-fidelity output. Separate bass and treble controls. Twin separately controlled inputs so that two instruments or "mike" and pick-ups can be used at the same time. Heavy Duty 12in. 20 watt Speaker. Cabinet covered in attractive Rexine/Vynair. Size approx. 18 x 18 x 8in. Or Deposit 3 gns. and 9 monthly payments of 43/2 (Total 21½ gns.). S.A.E. for leaflet.

19½ Gns.
Carr. 12/6

R.S.C. BATTERY CHARGING EQUIPMENT

All for A.C. Mains 200-250 v. 50 c/s

Assembled 4 amps 6/12v. Fitted Ammeter & variable charge rate selector. Also selector plug for 6v. or 12v. charging. Louvered steel case with stoved grey hammer finish. Fused and ready for use with mains and output leads and clips. Or Deposit 12/- and 5 monthly pmts 12/- (Total 23.12.0). Carr. 4/6

59/9

Heavy Duty Charger Kit
6/12v. 6 amps., variable output. Consists of Main Transformer 0-200-230-250v.; FW (Bridge) Selenium Rectifier; Ammeter; Variable Charge Rate Selector Panels, Plugs, Fuses, Fuseholder and circuit. Carr. 5/6.

PRICE 59/9.

Guaranteed 12 months BATTERY CHARGER KITS

Consisting of Mains Transformer, F.W. Bridge, Metal Rectifier, well ventilated steel case, Fuses, Fuseholders, Grommets, panels, Heavy Duty Clips, circuit. Carr. 3/6.

6v. or 12v. 1 amp. ... 22/9
As above with ammeter. ... 28/9
6v. or 12v. 2 amps. inclusive of ammeter ... 25/9
6v. or 12v. 2 amps. inclusive of ammeter ... 35/9
6v. or 12v. 4 amps with Ammeter and variable charge rate selector ... 52/9

CHARGER AMMETERS
0-1.5a., 0-4a., 0-7a., 8/9 each

TRANSISTORISED SOUND MIXER

Enables mixing of up to 4 standard jack inputs. i.e., microphone, tape, gram, tuner, etc., into single output. Compact and completely self-contained. Uses standard 9v. battery

49/9

LINEAR TREMOLO PRE-AMP UNIT

Suitable for use with any of our Amplifiers. Controls are Speed (frequency of interruptions), Depth (for heavy or light effect). Volume and

4 Gns.

HI-FI 12 WATT AMPLIFIERS

BRAND NEW EX-GUITAR AMPLIFIERS Carr. 7/6 **£7.19.9**

Manufacturers' discontinued Model. Push-pull output. Latest high efficiency valves. Dual separately controlled inputs for "Mike" and gram. Separate Bass and Treble Controls. High Sensitivity. Output for 3 or 15 ohms speaker. Guaranteed tested and in perfect working order.

THE
PEMBRIDGE
COLLEGE
OF ELECTRONICS
PROVIDES TRAINING
IN RADIO
AND TELEVISION

FULL-TIME COLLEGE COURSE IN RADIO AND TELEVISION

Our Course has now been extended to sixteen months' duration to include theoretical and practical instruction on transistor television receivers, U.H.F. television receivers and colour television.

Next course commences 19th April, 1966.

This Course is recognised by the Radio and Television Servicing Certificate examinations.

Provides excellent practical experience on valve and transistor radio receivers and all well-known makes of television receivers.

To:
The Pembridge College of Electronics (Dept. P11)
34a Hereford Road, London, W.2.

Please send, without obligation, details of the Full-time Course in Radio and Television.


Name _____

Address _____

CMP3

STERN-CLYNE ELECTRONIC CENTRES

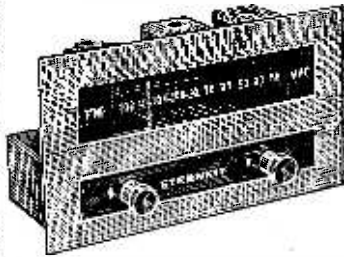HI-FI AND TAPE EQUIPMENT ● RADIO ● KITS ● ELECTRONIC COMPONENTS



SUPERB NEW STERN-CLYNE FMI VHF TUNER

Specially designed for the Amateur builder, a new sensitive tuner unit that provides stable, interference-free reception of BBC FM transmissions. High quality output signal ensures optimum performance from any Hi-Fi audio system; superb styling makes for harmonious installation with existing equipment.

Reliable easily aligned circuit employs RF stage, tuned anode tuned grid frequency changer, 2IF's, Noise Limiter and Ratio Detector. Input sens. 100mV for 40 db. Distortion less than 1% at full deviation. Power req. 200 at 20 mA and 6.3v at 1.8A. Panel black and silver-grey, size 8 x 5 in.


FMI Kit of parts **£7.9.6** Carr. 4/-
Assembled and tested **£10.9.6** Carr. 4/-
Optional Power Pack available.

EXCLUSIVE OFFER OF TOP QUALITY RECORDING TAPE

New American branded tape by world renowned manufacturers and equal in quality to the best obtainable anywhere. Guaranteed splice free, red oxide coated, with full frequency response and uniform output. Resistant to moisture, heat, cold and abrasion. Available in a wide range of Acetate and Polyester qualities, each distinctively boxed and cellophane wrapped in colour coded cartons showing recording times at 7½, 3½ and 1½ i.p.s. Compare the prices!


Range available:		Acetate
3½in. 600ft. Double Play 11/6	5in. 600ft. Standard 8/6	
7in. 1,200ft. Standard 12/6	5in. 900ft. Long Play 10/-	
5in. 1,200ft. Double Play 15/-	5½in. 1,200ft. Long Play 12/6	
7in. 1,800ft. Long Play 20/-	<i>Both types post and packing 1/- per reel. Four or more reels post free.</i>	
5in. 1,800ft. Double Play 22/6		
7in. 2,400ft. Double Play 25/-		

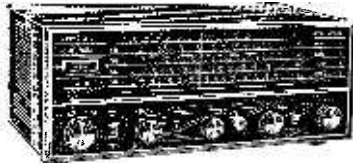TUNE INTO THE WORLD WITH THIS COMPACT PROFESSIONAL STYLE RECEIVER 20 Gns.



portable radio proportions and a performance comparable with many highly expensive professional receivers. Continuous frequency coverage from 540 kc/s to 30 mc/s takes in all broadcast bands, shipping, world-wide short wave and amateur bands. Built in super features include extra large dial, 'S' meter, variable pitch BFO, Noise Limiter, extra quality loudspeaker, extending rod aerial to receive all but most distant stations. Extras include phone output, standby switch, etc. Uses ultra modern mini valves 12BE6, 12A U6, 12BA6, 600C5 and silicon rect. Meticulously constructed and handsomely finished in attractive metal case. Only 18½ x 5 x 8in. deep. Essential for all serious listeners yet cheaper than many commercial sets. For 200/250 volts mains operation.

THE SUPERB VERITONE VEGA

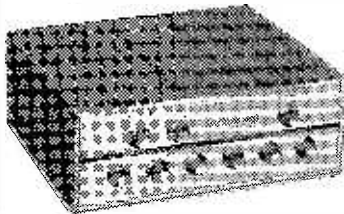

Solid-state Stereo Amplifier with integrated Pre-amplifier/control unit. The Vega is a new, solid-state amplifier that provides great purity of sound — comparable with the best valve amplifiers — plus all the advantages accruing from semi-conductor design employing the latest techniques. Important advantages, such as improved reliability, absence of high working temperatures, lack of valve noise, elimination of the

output transformers, and design freedom that permits spacious layout within an optimum overall size to suit modern installation requirements. And the Vega is styled and finished in impeccable taste — totally enclosed in a handsome teak case with comprehensive controls functionally arranged on a clear silver grey and black panel. Outputs — 13 watts per channel. Freq. response 40 to 20,000 c/s ± 3 db. Distortion less than 0.5% at 10W. For 200/240v AC. Size 11 x 4½ x 6½in. deep. Price **£44.2.0.** Without Teak Case **£40.19.0**

Carr. 8/6.



3. TEISCO CM-30 CRYSTAL

Compact lightweight crystal stick microphone in machined aluminium body with integral thumbswitch. Size overall 5in. long x 1½in. diameter. Attractive machined matt finish. Complete with stand adaptor and 6ft. detachable screened cable. **29/6 P. & P. 1/6**

Top value offers from our wide range, suitable for use with moderately priced equipment up to the finest obtainable.

1. PLANET CM-61 CRYSTAL

Handsomely styled in two-tone grey plastic case with silver trim, and intended for use with most tape recorders and small amplifiers. Fold out stand permits hand or table use. Complete with 4ft. insulated screened lead and moulded standard phono plug. **12/6 P. & P. 1/6.**

2. DUVIDAL DM-391 DYNAMIC

High-grade dynamic insert in tough, black plastic body with grey grill and silver trim. Fitted with pull-out stand for desk use. Direct replacement for many recorders; standard 50 K ohms impedance permits use with most other equipment. Size 2½ x 1½ x 1½in. deep. Complete with 4ft. cable and standard phono plug. **23/- P. & P. 1/6.**


4. TEISCO DM-107 DYNAMIC

A really superior stick microphone employing a high quality moving coil insert in a beautifully styled, black anodized body with heavy chrome head and grill. Fitted with integral thumbswitch and removable stand adaptor. Size overall 7in. long x 1½in. diam. With 6ft. screened cable and connector. Standard 50 K ohms impedance. **23.9.6 P. & P. 2/6.**

5. DUVIDAL DM-51 DYNAMIC

A superb, non-directional microphone incorporating features normally found only in extremely expensive professional units. An excellent frequency response of 50-15,000 cycles permits use in high quality recording, high-fidelity reproduction and all general microphone usage. Robust, engine turned body has integral slide switch. Beautifully styled with fluted detachable head, matt black and satin silver finish. Complete with desk stand and clamp, floor stand adaptor, and 6ft. lead and plug. In fitted pack: **26.19.6 P. & P. 3/6**

The Remarkable VERITONE 300

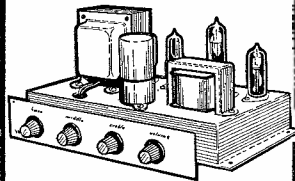

ONLY **£6-6-0** Carr. 5/-

A small size, quality constructed amplifier with a big 4 watts output that is adequate for all domestic uses. Features include separate Bass and Treble controls and, when used a good quality speaker, results are indistinguishable from many more expensive outfits. Ideal for quality home-build reproducers, portable lead guitar amplifiers, etc. Size only 8½ x 4 x 1½in. Grey hammer finish with brushed aluminium front panel. For 200/250 V AC mains.

Special offer of 12 inch LOUD-SPEAKERS



39/6

Carr. 3/6
High quality, all-British units with built-in tweeter cone, and a high flux magnet that ensures wide range reproduction. Handles 6 watts easily. Heavy pressed steel construction. Available for 15 ohms or 3 ohms impedance.

GARRARD 3000 AUTOCHANGER

Intended for use with high compliance cartridges and featuring a low mass arm that minimizes record wear. Four standard speeds. Finished dark grey with chrome relief. Clearance required 12½in. wide x 12½in. front rear. Above board 4½in. below 2½in. For 100/130v and 200/250v AC. Complete with 9TA/HG cartridge. **£8.3.0** Carr. 5/-

TEST 8 MULTIMETER 57/6

Carr. 2/-



Compact all purpose tester with 12 specially selected ranges for all home and motor car wiring and servicing, amateur radio, TV fixing, electronic hobby work, etc. Extremely robust construction employs rugged large scale meter movement and plug-in range selection to obviate switch wear defects and ensure trouble-free life. In tough metal backed plastic resting case. Ranges: 0-10, 250-500-1,000v. A.C. and D.C. (sens. 1,000 ohms per volt) 0.1-250 mA D.C. current. 0-10,000-100,000 ohms resistance. Size only 4½" x 3½" x 1½" deep. Complete with test leads and battery.

TEST 7 POCKET MULTIMETER




39/6

Carr. 2/-

A really versatile instrument that makes a handy pocket-size tool. Measures AC or DC voltage in three ranges of 0-15-150-1,000v. Resistance 0-100,000 ohms, and Current 0-150 mA. DC Size only 3½ x 2½ x 1½in. with ingenious dial design providing a clear, easily read scale. Complete with battery and test leads.

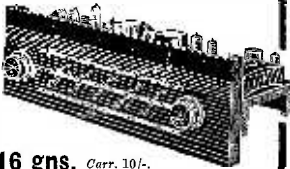
EXCEPTIONAL OFFER OF AM/FM Radiogram Chassis



16 gns. Carr. 10/-.


Superb new six valve unit covering long and medium wave on FM and all BBC VHF transmissions on FM. Highly sensitive AM circuit receives most stations through internal aerial, separate FM input employs famous Gorder tuning heart. Uncluttered fascia covers whole frontal area and simplifies adaptation to existing cabinets or building into contemporary bookshelf units. Extra large illuminated dial and dual concentric controls for volume, tone selection and tuning simplify operation, enhance appearance. Powerful 4W. output matches standard 3 ohm speaker. Inputs provide for external AM and FM aerials and gramophone pickup. For 200 250 V. A.C. operation. Size overall 15in. x 6 1/2in. x 7 1/2in. deep.

MAGNAVOX 363 TAPE TRANSPORTER

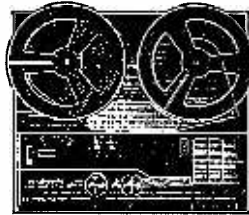

Manufactured to precise limits that permit recording and tape playback to the highest standards set by the Music Industry. Simple reliable design employs a single high-duty motor with heavy flywheel. Features include fast wind on and rapid rewind, pause control, 3-speed selection with interlock, built-in revolution indicator, piano key controls. Speeds 1 1/2, 3 1/2 and 7 1/2 i.p.s. Wow and flutter 0.15% on 7 1/2 i.p.s. Max. spool size 7in. Playing time up to 120 min. per track from 1,200ft. standard tape. Size 13 1/2 x 11in. plus 5 1/2in. below mounting board. With 1/2 track heads, £10.10. With 1 track heads, £13.19.6. Add 10/- carriage and insurance.

HF/TR3 TAPE AMPLIFIER

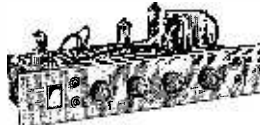


Easily the best complete tape amplifier available to the home builder. Supplied already matched for the Magnavox 363 tape deck, but may be readily matched to most other decks. Features include: switched equalization for all speeds (OCIR standards at 7 1/2 i.p.s.) Treble boost incorporated during Record. Bass boost during playback, speaker output matched for 3, 7.5, and 15 ohms, additional outputs for extension speaker, phone monitoring on Record and Hi-Fi playback through existing systems, inputs for Mic, Pickup, and VHE Radio. Valves: EF86, ECC83, EL84, EM81, EZ81. Size overall: 11 x 6 x 6in. (Panel 13 1/2 x 8in.). Power pack on separate chassis size 7 1/2 x 3 x 4 1/2in. Amp. and power pack. Kit of parts £18.19.5. Assembled and tested £19. Add 7/6 carriage. Carrying Case specially designed to take Magnavox 363 and HF/TR3 unit. Superbly constructed finish, dark grey cloth. £5 extra. 10in. x 6in. elliptical speaker suitable for use with above.

TAPE PRE-AMP AMPLIFIER TYPE 'C'




Specially developed by Mullard Laboratories for use with high quality replay systems, and supplied specifically matched for use with the Magnavox 363 tape deck. Features include: ferroxcube pot core inductors for treble equalization, push pull oscillator incorporating ferroxcube transformer, adjustable output for matching to existing high-quality amplifier systems, inputs for Mic, Pickup, Radio, etc. Valves: 3 x EF86, EC82, and EM81. Totally enclosed in case size 11 1/2 x 6 1/2 x 3 1/2in. high. (Panel 11 1/2 x 8 1/2in.) Power supply of 300 vdc at 25 mA. and 6.3 v. at 1.5 A. is on separate sub-chassis size 6 1/2 x 4 1/2 x 4 1/2in. high to facilitate remote location from tape heads. Pre-amp and power pack Kit of parts £14. Assembled and tested £19. 10s. Add 7/6 carriage.

HIGH INTENSITY LAMP 49/6

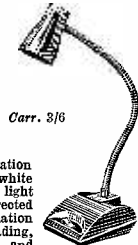


Provides a concentration of intense pure white glarefree, shadowless light that can be directed straight on to illumination area. Ideal for reading, needlework, stamp and minute object examination, delicate craft work and watch repair, table-top photography, etc. Ingenious design combines function with attractive appearance: tough plastic base has on/off switch and is weighted by built-in transformer that reduces mains voltage to permit use of enormous headlamp power of car bulb over small area. 21 watt lamp actually provides greater light intensity than conventional 100 watt bulb with electrical consumption less than one-fifth of usual mains lamp. Gold anodised flexible pillar facilitates light direction from any angle. For 200/240v. AC only: spare bulbs readily obtainable. Base 2 1/2in. x 3 1/2in. x 2in. Height overall 16in.

NEW PORTABLE TAPE RECORDER

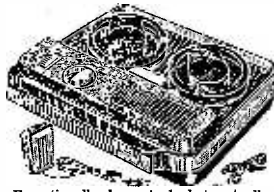

Exceptionally low-priced, but actually a robustly made reliable instrument which can be used anywhere for note taking, idea recording, dictation, etc. Mechanism solidly built on to rigid steel chassis and housed in tough grey plastic case with carrying strap and clear plastic tape deck cover. Fitted with single multi-selector function switch and volume control. Hand microphone has Stop/Start thumbswitch for remote control of record and playback transcription. Complete with tape and spare spool, mike and miniature earpiece. Size only: 8 x 7 1/2 x 2 1/2in. £6.19.6 high. Carriage 4/6.

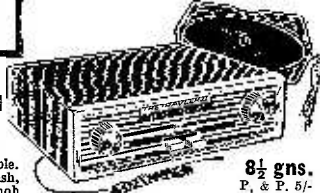TRAVLER 2 Fit your own transistorised car radio at a fraction of the usual cost



Easily the finest value in car radio obtainable. Robust, all British manufacture with stylish, uncluttered fascia that presents simple, 2-knob control and push-button change for medium and long wave. Heavy chrome esentochrome and illuminated dial in black and gold trim. Overall size of 7 x 2 x 7in. and standard location of fixing screws permits simple installation to almost any car. Improved circuit design utilises best features of valves and transistors to ensure high performance with greatest reliability. Complete with 7 x 4in. speaker and baffle trim, brackets, standard fuse coupling and filter, all nuts and bolts, and easy to follow, foolproof fitting instructions. 8 1/2 gns. P. & P. 5/-

VANDAL-PROOF CAR AERIAL 39/6 P. & P. 2/6

Automatically locks below wing when pushed down—withdraws only with special key. Very heavily chromed, 5-draw telescope aerial extends to 4ft., retracts into concealed, tough plastic tube. Fits any wing contour. Complete with fitted lead and standard plug, 2 keys, key-ring and fitting instructions.

STERN-CLYNE ELECTRONIC CENTRES... most exciting shops in Britain!

Member of the Pantiya Group of Companies.

LONDON:
15 Tottenham Court Road, W.1
23 Tottenham Court Road, W.1
309 Edgware Road, W.2
109 Fleet Street, E.C.4.
162 Holloway Road, N.7.
9 Camberwell Church Street, S.E.5.
220 Edgware Road, W.2.

MUS 5029/0095
MUSEum 3451
PADddington 6963
FLEEt Street 5812/3
NORTH 7941
RODney 2375
PADddington 5607

MAIL ORDER & ALL ENQUIRIES TO: DEPT. PW, 3-5 EDEN GROVE, HOLLOWAY, LONDON, N.7. Tel. NORTH 8161/5

GROUYDON: 12 Suffolk House, George Street.
BRISTOL: 26 Merchant Street, Bristol 1.
LIVERPOOL: 52 Lord Street.
MANCHESTER: 20/22 Withby Grove, M/c 4.
SHEFFIELD: 125 The Moor.
NOTTINGHAM: Eastown House, Lincoln St.

MUNICIPAL 3250
Bristol 20261
Royal 7450
Blackfriars 5379/5246
Sheffield 29993
Nottingham 45889

HIRE PURCHASE? CERTAINLY!

Easy payment terms available on all kits and assembled equipment value £10 or more. Let us have your enquiry.



Identical pocket-size units in cream plastic and gold anodised trim, each unit fitted hinged desk stand or wall hanger. Powerful two-transistor amplifier has sensitivity of 55db plus, consumes only 7mA at no signal condition. With 9V PP3 battery, instructions, and 50 ft. lead with phono plug ends for instant connection. In distinctive yellow and gold hinged gift box. £2.15.0. Post & Packing 2/6.

DE LUXE INTERCOM

Superb professional style, compact transistor intercom for executive desk and office or home. Compact master unit and identical sub-stations, magnificently styled in pearl white and dark beige plastic case with black and gold anodised trim. Powerful 3-transistor amplifier has 200mW output, but operates 4-5 months on 9V PP3 battery. Master station has Volume, On/Off and Listen/Talk controls. 66ft. cord with phono plugs each end for immediate installation, staples, cable location tape, battery and instructions in attractive gift carton. £4.9.6. Post & Packing 2/6.



JORDAN WATTS SPEAKER SYSTEM



Hand waxed teak or walnut veneered bookshelf system featuring the famous Jordan-Watts modular unit and specially recommended for use with the Veritone Vega. Ideal also for all Hi-Fi systems with outputs up to 12 watts, and impedance of 7.5 and 16 ohms. Frequency response 30-20,000 c/s ± 6 dB. Size overall 16 1/2 x 8 x 4in. deep. Speaker grille finished with black/silver weave.

£17.12.6 Carr. 10/-

GUARANTEED BY STERN-CLYNE—Value for money, Quality Facility. Merchandise offered by Stern-Clyne is critically selected and exhaustively tested before it is offered for general sale; where suitable equipment does not exist, certain items are exclusively manufactured to our own rigid specifications. In all cases, Stern-Clyne offers are value and quality selected. Satisfaction guaranteed.

LEARN ELECTRONICS —AS YOU BUILD

over **40** **CIRCUITS**
EXPERIMENTS
TEST GEAR



including . . .

● CATHODE RAY OSCILLOSCOPE

- | | |
|--------------------------------|--------------------------|
| ● Valve Experiments | ● Square Wave Generator |
| ● Transistor Experiments | ● Morse Code Oscillator |
| ● Electro-magnetic Experiments | ● Simple Transmitter |
| ● Basic Amplifier | ● Electronic Switch |
| ● Basic Oscillator | ● Photo-electric Circuit |
| ● Basic Rectifier | ● Basic Computer Circuit |
| ● Signal Tracer | ● Basic Radio Receiver |
| ● Simple Counter | ● A.C. Experiments |
| ● Time Delay Circuit | ● D.C. Experiments |

The full equipment supplied comprises valves, transistors, photo-tube, modern type chassis board, printed circuit board, full range resistors, capacitors and inductors, transformers, potentiometers, switches, transistors, valves, all hardware, wiring and every detail required for all practical work plus CATHODE RAY OSCILLOSCOPE for demonstrating results of all experiments carried out. All practical work fully described in comprehensive PRACTICAL MANUALS. Tutor service and advice if needed.

This complete practical course will teach you all the basic principles of electronics by carrying out experiments and building operational apparatus. You will learn how to recognise and handle all types of modern components; their symbols and how to read a completed circuit or schematic diagram. The course then shows how all the basic electronic circuits are constructed and used, and HOW THEY ACTUALLY WORK BY USING THE OSCILLOSCOPE PROVIDED. An application is given in all the main fields of electronics, i.e. Radio; control circuits; computers and automation; photo-electrics; counters, etc., and rules and procedure for fault finding and servicing of all types of electronic equipment.

- | | | |
|--------------------------------|---------------------------|--|
| ● NO PREVIOUS KNOWLEDGE NEEDED | ● NO MATHS USED OR NEEDED | ● REASONABLE FEE—NO EXTRAS REQUIRED |
| ● SENT IN ATTRACTIVE BOX | ● COMPLETE ADVICE SERVICE | ● EVERYTHING REMAINS YOUR OWN PROPERTY |

A completely NEW up-to-date home study experimental course by

**BRITISH NATIONAL
RADIO SCHOOL —**
Britain's Leading Electronic
Training Organisation.

POST NOW FOR FREE BROCHURE

To BRITISH NATIONAL RADIO SCHOOL, READING, BERKSHIRE. Please send free Brochure, without obligation, to

NAME

ADDRESS

Block Capitals Please

OR WRITE IF YOU PREFER NOT TO CUT COUPON

PW 5.66

PRACTICAL WIRELESS

VOL 42 No 1

issue 711

MAY 1966

TOPIC OF THE MONTH

Face Lift

WELL, here it is! A newly styled and, we hope, improved Practical Wireless. The larger page size will not only allow a more attractive layout of articles but will also make for easier reading. The better quality paper will permit far better reproduction of photographs, which will be of great benefit in constructional articles. In order to carry out these improvements it has been necessary to slightly increase the cost of the magazine, but this is, we trust, a small price to pay for the considerable advantages reaped.

Regular readers need not feel anxious that this face lift will reflect on the general structure of the magazine. All the popular regular features will be retained and we will continue to balance the magazine with a good selection of material contrived to appeal to all the various interests in our hobby. The basic policy will remain as before and there will be no shifting of emphasis except where considered necessary from time to time in the light of our own experiences and the wishes of readers as expressed in correspondence.

Since 1932, Practical Wireless has held a unique position in the realm of amateur radio and through the years has served faithfully the interests of those who are interested in this absorbing hobby. At times, during these eventful 33 years, Practical Wireless has had, for some reason or other, to take stock of the existing situation and, where desirable, to initiate changes.

Such a time has recently passed. And as we start off on Volume 42 we are safely launched on another stage of the development of the magazine. And yet, in essence there is no division, for the fundamental objectives of the present staff are the same as those of the pioneers in the early 1930's—to present each month in the best possible way a magazine dedicated to the interests of all who derive enjoyment from one or more of the facets of amateur radio.

W. N. STEVENS, Editor

NEWS AND COMMENT

Leader	17
News and Comment	18, 44
On the Short Waves <i>by John Guttridge and David Gibson, G3JDG</i>	25
Practically Wireless <i>by Henry</i>	54
Club Spot—Verulam Amateur Radio Club, G3STA	57

CONSTRUCTIONAL

208 Receiver <i>by F. G. Rayer, G3OGR</i>	20
Comprehensive A.T.U. <i>by David Gibson, G3JDG</i>	27
Pickup Booster <i>by Gordon J. King</i>	36
Simplified Cabinet Design <i>by R. W. Lawrence</i>	40
Electronic Gate or Trace Doubler— Part 2 <i>by H. T. Kitchen</i>	50

GENERAL ARTICLES

Micro to Meger <i>by B. L. Burrough</i>	43
Volume Expansion <i>by G. R. Wilding</i>	46
Oscillator Circuitry—Part 3 <i>by R. Leyland</i>	58

The JUNE ISSUE WILL BE PUBLISHED ON MAY 5th

All correspondence intended for the Editor should be addressed to: The Editor, "Practical Wireless", George Newnes Ltd., Tower House, Southampton Street, London, W.C.2. Phone: TEMple Bar 4363. Telegrams: Newnes Rand London. Subscription rates, including postage: 36s. per year to any part of the world. © George Newnes Ltd., 1966. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

Were Pre-War Sets Better?

MR. L. WELCH complains of poor quality sound from sets he has made, and also from high priced commercial sets he has heard (P.W. March, 1966).

Most modern sets use inadequate speakers and the cases are undersized and flimsy. Pre-War sets with larger speakers and heavier cases were much better, although they were generally "boomy".

For high quality reproduction, our friend must forget about a "set" and keep the radio equipment separate from the speaker enclosure. The speaker should be of good quality and mounted in a properly designed enclosure placed where it gives the best possible results. The output, as Mr. Welch realises, must be large enough to deal with peaks without distortion.

He writes that no commercial set offers the kind of specification he asks for. Although I would not wish to put him off building such equipment, I must point out that several makers produce tuner-amplifiers which give all he asks for and more. Connected to good speakers, they give results that are really something.

R. E. Barker.

Stockton-on-Tees,
Co. Durham.

R220 MODS

THERE are a lot of R220 crystal-controlled v.h.f. receivers about and radio friends and myself have spent many hours trying to modify this set to make it tunable in the range 120-140Mc/s.

If any readers have managed to do this, we would be most grateful to learn the secrets of their success.

S. M. Giblions.

77 Windlehurst Road,
High Lane,
Stockport,
Cheshire.

How About a Swop?

I REQUIRE the March 1962, December 1963 and January 1964 issues of PRACTICAL WIRELESS, and in order to obtain them, I am willing to exchange some 42 old copies of PRACTICAL WIRELESS, PRACTICAL TELEVISION and WIRELESS WORLD, all between 1949 and 1951.


If any readers are interested, would they please write to me first before sending copies, enclosing a stamped addressed envelope.

J. Currie.

156 Hillhead Road,
Kirkintilloch,
Near Glasgow,
Scotland.

NEWS AND..

PRODUCTS FOR AUDIO FAIR

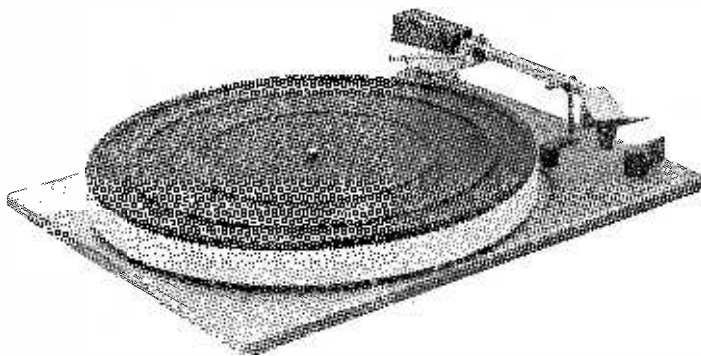

Shown for the first time at the Audio Fair will be the Model GL.68 Transcription Unit (see also photograph above) which also has as a feature infinitely variable speed adjustment, and which is fitted with a new pick-up arm Model G.65. This arm is of low mass tubular design and has counter-balanced stylus pressure adjustment and removable headslide.

In addition, the well-established Model GL.70 will be on view, as well as the inexpensive Turntable Unit Model G.66.

A new pick-up cartridge will be shown, namely the CS.91/E, which is a high quality Stereo Ceramic Cartridge fitted with an elliptical diamond stylus.—Goldring Manufacturing Co. (Great Britain) Limited, 486-488 High Road, Leytonstone, E.11.

ADVERTS SPEEDED UP BY STC

An automatic control system has been installed by Standard Telephones and Cables Ltd., in the Classified Advertisement Department of the "Liverpool Daily Post and Echo", which will now be able to deal with the relevant customer telephone inquiries much more promptly and efficiently.

The STC equipment "scans" 30 operator positions and connects the incoming call to the first free position that it finds. The operator at that position deals straight away with the call if it is a general inquiry. If, however, the caller wants to book space in one of the specialised columns, the call is transferred to the operator who deals specifically with that section. In this way calls are routed to the proper place in the minimum of time.

BALUN FOR HAM BAND INSTALLATIONS

K. W. Electronics Ltd., of 1 Heath Street, Dartford, have just introduced the K. W. Balun, the main features are:

Helps eliminate television interference—Broad band 3-30 Mc/s—Waterproof—For use with all types antennas fed with unbalanced Co-ax—Will handle a kilowatt—Virtually no insertion loss.

The K. W. Balun is designed for 50/70 ohm unbalanced co-ax input with 1:1 impedance ratio. It is intended to be installed at the feed point of a dipole, beam or similar balanced type antenna.


Support it by taping to your beam or dipole "T" insulator and connect the output terminals (marked with a white spot) to the feed point of the antenna with a short length of wire. Connect the co-ax "outer" and "inner" to the terminals marked on the label. The co-ax cable should be suitably sealed to prevent ingress of moisture.

In many cases the installation of the K. W. Balun in balanced antenna systems fed with co-ax cable has improved the efficiency and radiation pattern of the system.

The K. W. Balun is 4in. long and 1¼in. overall diameter. The weight is less than 4oz. and the price is 35s. including postage in the U.K.

208

THE

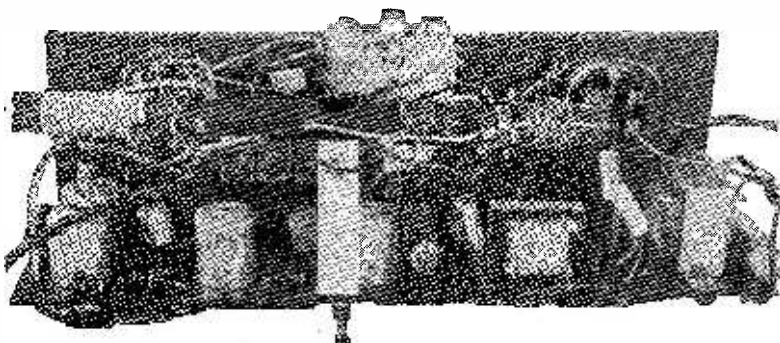

BANDSPREAD PORTABLE

By F. G. Rayer G3OGR

THIS is a six-transistor receiver with high frequency end bandspread, car aerial, tape output and personal phone facilities. A ferrite rod aerial is fitted, tuning long and medium wavebands. With ordinary 2-waveband circuits, many popular and well-received stations are heard over a small section of the high frequency end of the medium waveband. To simplify tuning these stations, a bandspread range is provided (covering about 185-215 metres), this being extended over almost the whole rotation of the tuning capacitor. As a result, it is easy to select Radio Luxembourg and other transmissions in this range.

Bandspread

The bandspread is achieved, without any particular ganging difficulties, by switch section S4, which places the 1 per-cent capacitor C4 in series with the oscillator section VC2 of the ganged tuning capacitor. S1 introduces the trimmer TC2 in series with VC1, for bandspread aerial tuning. Because of the low capacitance present, the bandspread range extends to a somewhat higher frequency limit than the medium wave range.

S2 selects separate base coupling windings, provided on the medium and long wave coils. S3 shorts the l.w. section for m.w. reception, and brings in C3 for l.w. reception, to obtain suitable oscillator coil coverage. The switch thus has three positions, "Long", "Medium" and "Bandspread".

Normal reception is by means of the internal ferrite rod aerial, but an external aerial can be connected to the "car aerial" socket, which has a coupling winding on the aerial rod. An external aerial is often used with a portable in a vehicle, to overcome screening and directive effects of the ferrite aerial.

AF117 transistors are used in mixer and i.f. stages, and need no neutralising. (It should be noted that the oscillator coil and i.f. transformers *must* be of the type intended for AF117's.) The audio signal obtained from the diode D1 may be taken to a tape recorder through the "tape output" sockets. This

gives high quality, and an audio level suitable for the usual recorder. The usual automatic gain control bias reaches Tr2 through R5.

VR1 is the 5k Ω volume control, with on/off switch. The OC81D drives two OC81's, having base bias and feedback resistors R15 and R16. This gives excellent volume and quality from a large number of stations.

For personal listening, earphones or a personal phone can be plugged in, thereby automatically disconnecting the speaker. A low impedance type of phone should be used.

Construction is on a circuit board, with VR1, tuning and switch controls on a small panel, so that the finished receiver can be inserted in a cabinet from behind. With this arrangement, the actual positions of VR1, VC1/VC2, and the switch can be modified without any alteration to the circuit board, so that in some cases an existing cabinet can be used. It also gives plenty of latitude for positioning of the speaker.

Unless very small size is important, a 3½in. diameter (or equivalent oval) speaker unit is recommended, as these usually give slightly better results than midget speakers. Some notes on possible alternative transistors, etc., are given later.

The Circuit Board

This is 8 x 2½in. of 1/16in. thick paxolin, and is drilled as in Figs. 2 and 3 first. All wire ends can pass through 1/16in. holes. The oscillator coil and i.f.t.'s require clearance holes for the pins and can tags, and six holes are needed for T1. T2 is held with two 6BA bolts. Three small right-angle brackets hold the panel, but this is not fitted until the circuit board is wired. Complete as much drilling as possible, before inserting any components.

The i.f.t.'s will only fit one way, and are held by spreading the can tags. The oscillator coil P50/1AC has a coloured spot between pins 1 and 6 and this must face the i.f.t. P51/1 so that pins 1 to 6 fall in the positions in Fig. 3.

The driver transformer T1 has a green spot, placed as in Fig. 2, so that its tags emerge correctly (Fig. 3). T2 has three tags on its primary side, and two on the speaker side.

All the resistors may be placed either way round, but check the values because an error in reading them will probably completely upset results. Small capacitors may also be connected either way. But the electrolytic capacitors C6, C8, C13 and C14 must be placed with positive and negative ends as shown. This also applies to C12, running from R10.

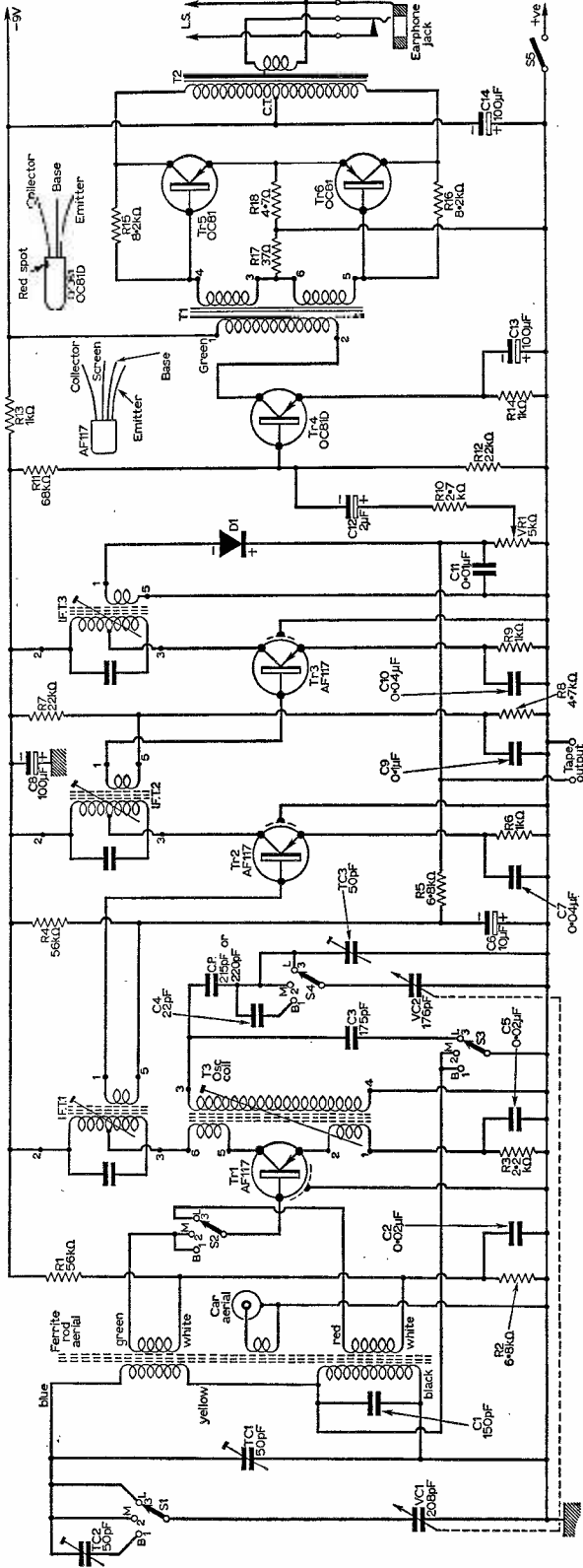


Fig. 1: The Circuit

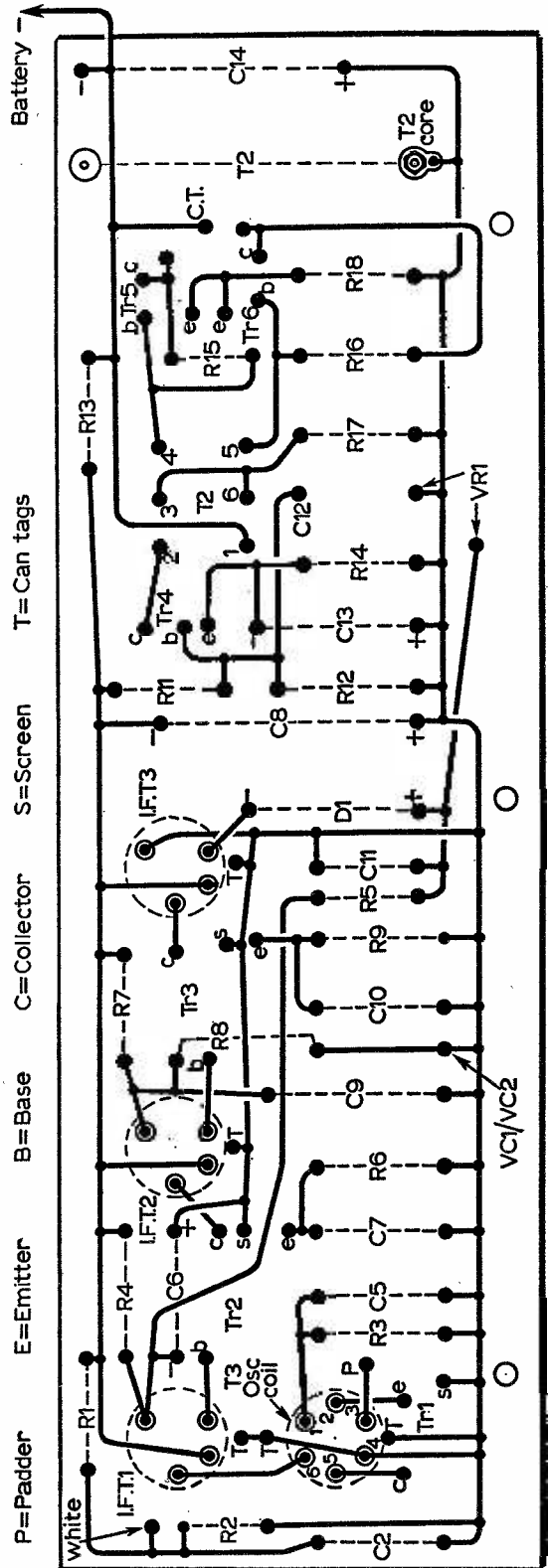


Fig. 2: Wiring of Circuit Board

The circuit layout has been arranged so that no wires cross under the board (Fig. 3). The identification of connections and components is much easier if 1mm, red sleeving is placed on the "earth" or positive line, with black on the negative line, and capacitors having markings upwards. The can tags T are earthed. Solder all joints rapidly but well, and snip off excess wires.

Transistors

These are added when the circuit board is otherwise finished. Identification of the leads is greatly eased by placing lengths of coloured 1mm. sleeving on them. With the AF117's, yellow is suggested for emitter, black for base, and red for collector, the screen wire being left bare. With the OC81D and OC81's, use yellow for emitter, and red for collector. All the pieces of sleeving can be $\frac{1}{2}$ in. long.

There is then no difficulty identifying the leads, as they are threaded through in the positions shown in Fig. 2. Small pieces of sleeving of the appropriate colour can also be slipped on the leads as they emerge as in Fig. 3. The transistor leads should be soldered rapidly, the iron being removed as soon as the joint is made. This also applies to the diode D1.

Panel

This is drilled for the switch, VR1, and ganged tuning capacitor. The latter is fixed with three 4BA bolts. These *must* be very short, or have washers, so that they do not protrude behind the capacitor plate, as this will short circuit or damage this component. Small brackets hold the circuit board and panel together.

VR1 is connected as in Fig. 2. Lead X from the positive line runs to the upper tag metal casing, and switch. Lead Y is from diode positive. R10 and C12 are closely in series, negative on C12 going to R11 and R12.

VC1 is the front section of the capacitor, and has more plates than VC2, the rear section. The frame (moving plates) is connected to the positive line of the circuit board.

Switching

This is quite straightforward, but it is also easy to test the receiver temporarily without the switching, to guard against errors. To do this, take green on the aerial to Tr1 base, white to R1 and R2, blue to VC1, and yellow to positive line. Normal medium wave reception should then be obtained, after rough trimming as described later. If all is well, the switch wiring can then be undertaken.

Connections to the ferrite rod aerial and switch will be greatly eased if leads are of the appropriate colours. These coloured wires are then soldered to the same coloured tags of the aerial. Suitably coloured wire is easily obtained, or leads can be marked with paint, sleeving or any other means.

Switch positions are L, M and B, for Long, Medium, and Bandsread. The switch has four poles, S1, S2, S3 and S4. Connections are shown in Fig. 2, and can be checked as follows:

VC1 to S1. M and L tags to blue, TC1 and TC2. B tag to TC2.

TR1 base to S2. M and B tags to green. L tag to red.

Earth line to S3. M and B tags to C1 and yellow. L tag to C3.

VC2 to S4. M and L tags to C4, CP (215pF or 220pF padder) and TC3. B tag to C4.

The three trimmers have their tags and adjusting screws through holes in a small piece of paxolin, which is secured to the tuning capacitor by a short bolt. Use a soldering tag for frame leads. C3 and CP are soldered together, and sleeving placed on, the lead passing near R3, through a hole, to pin 3 of the oscillator coil. The specified padder is 215pF, but this value may be difficult to obtain. A 1 per cent 220pF capacitor is suitable, and can be readily obtained.

Connections to the switch should be reasonably short and direct, with oscillator circuit leads clear of aerial wiring. The trimmers can be reached from behind when the receiver is in a cabinet.

Aerial

The specified aerial has coloured tags, connected as in Fig. 2. A $1\frac{1}{2}$ in. bracket, cut from aluminium, is bolted vertically near R7, Fig. 2. A 6BA bolt secures the aerial rod to this, using the fitting provided.

The tags should face the rod centre, as in Fig. 2. The white tags of l.w. and m.w. sections are joined together. Yellow on the l.w. coil also goes to yellow on the m.w. coil.

Testing

A test and approximate alignment should be made before fitting the receiver in its case. Note that if the mixer and i.f. sections are working, good 'phone reception of many stations should be possible from the tape output sockets. This test can be made before the audio section is wired, if necessary. Again, if an audio signal is fed in at the tape output sockets, good speaker results will be obtained, if the audio section is working.

The i.f. transformers should be adjusted first. If no signal generator is available, tune in any stable signal, and carefully turn the cores for best volume. Use a properly shaped insulated trimming tool. For final adjustment, use a very weak signal, with VR1 near maximum.

If a signal generator is to hand, apply a modulated signal for all alignment adjustments, and include a meter in one battery lead. Correct alignment then corresponds to an increase in current, though continuous running with a high current should not be allowed. With an unmodulated signal or programme, correct alignment corresponds to minimum current shown on a meter in series with R13. Once the IFT's are touched up for maximum sensitivity, they can be left.

Initially place the aerial coils so that their card tubes are about level with the ends of the rod. Fully unscrew the trimmers. If the tuning capacitor has trimmers, also unscrew these.

TC3 governs the frequency at the h.f. end of the m.w. band, so is adjusted until readings correspond with the tuning dial. Then adjust TC1 for best volume.

Afterwards, tune to the low frequency end of the m.w. band (gang capacitor nearly closed) and, if necessary adjust the oscillator coil core to obtain agreement with the dial. Then slip the m.w. coil along the ferrite rod for maximum sensitivity.

Switch to long waves, tune in a station with the capacitor nearly closed, and move the l.w. coil on the rod, for best results.

After repeating these adjustments, alignment should be roughly correct. Final trimming is then carried out in this order:

- (1) Switch at B. Adjust TC3 for correct position of Luxembourg.
- (2) Switch at M. Adjust TC1 for best volume.
- (3) Switch at B. Adjust TC2 for best volume.

When the receiver is finally in its cabinet, repeat the above until there is no improvement.

Maximum Efficiency

With values as specified, satisfactory results should be obtained at once. But transistors vary somewhat, and in commercially-manufactured receivers it is not unusual for certain resistors of best value to be fitted individually. It is not suggested this be done until the receiver is working correctly, and it may be quite unnecessary.

Should battery drain be under 8mA or so with no signal, and results sound a little distorted, R17 can be increased slightly. This will increase the OC81's

collector current, and battery drain should be about 10–12mA with no signal, peaking up to about 20–30mA with good volume. R17 may be about 47, 56 or 68Ω, to achieve this. The receiver must not be switched on with R17 disconnected, or of such a high value that a heavy collector current flows.

R4 is occasionally modified slightly, to obtain best sensitivity to weak signals, with low background noise. No confusion about the source of any fault in the tuned circuits should arise if the set is first tested with the m.w. coil only, as explained, VC2 then being wired directly to the paddler, which goes to pin 3 of the oscillator coil.

If to hand, popular transistors such as OC71 driver and OC72's for output may be used (maximum power handling capacity is somewhat lower than with OC81's). If so, resistor values in these stages must be those usual for the transistors fitted.

Car Aerial

A coaxial socket is most suitable, so that a screened coaxial lead can be used from an external aerial. No extra licence is needed for a portable used temporarily in a vehicle. Telescopic aerials may be obtained to clip on a window. Such an aerial increases signal strength, which is reduced by the

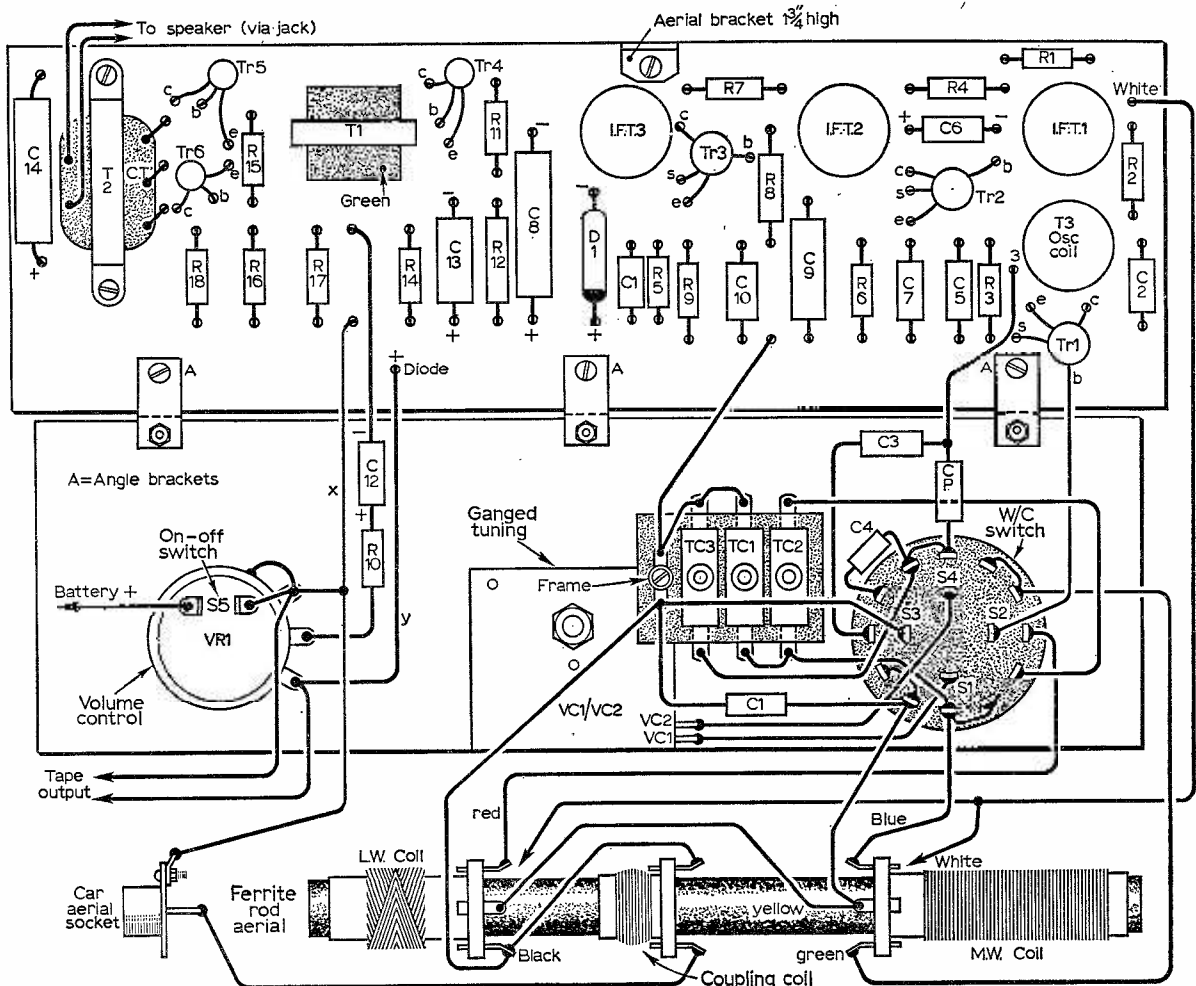


Fig. 3: Layout of components on circuit board and wiring to wavechange switch, ferrite rod aerial and trimmer bank

vehicle screening, and is not directive in the same manner as the ferrite rod.

If a telescopic or other short extended aerial is used merely to boost strength of weak transmissions (e.g., not in a vehicle) then it is better not to screen the connection to it.

Tape Output

These sockets supply an audio signal directly from the diode, at about $5k\Omega$ impedance. Most tape recorders have an input circuit suitable for this, and permit direct recording at high quality. The best method of connecting here is to make up a short screened lead, fitted at one end with a plug to suit the recorder, and at the other with a small audio-type coaxial plug, to fit the receiver; or with separate plugs, if a 2-pin socket strip is provided. The screened lead outer braiding forms the earth circuit return.

The receiver should not be connected to a midget a.c./d.c. type amplifier or any apparatus live to the mains.


Earphone

The actual impedance is not very important, but is best not higher than about 50Ω . The jack and plug may be ordinary size, or miniature. The circuit from the secondary of T2 to the loudspeaker is completed through the jack contacts. These are closed when the plug is out. When the plug is inserted, it opens the contacts, disconnecting the speaker to silence it. Signals then reach the earphone from the sleeve and tip contacts of the plug.

H.T. Whistles

After dark, some inter-channel whistles or interference may occasionally arise, particularly around 200 metres. If necessary, it may be possible to orient the receiver so that directive effects of the aerial reduce this.

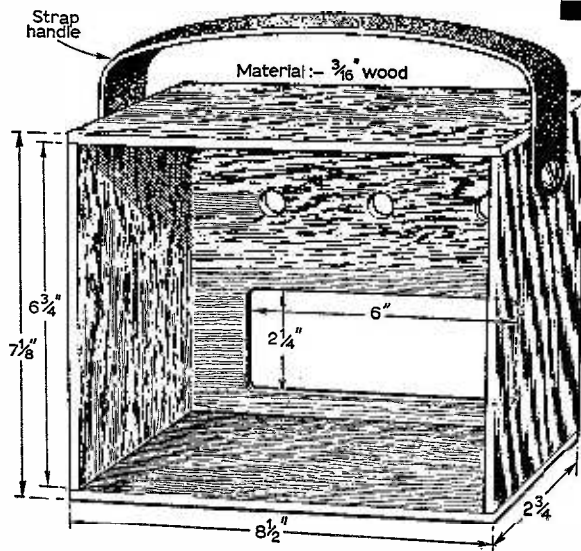Should actual oscillation arise around 200m. it is in order to place a $100-390\Omega$ resistor between pin 6 of the oscillator coil and pin 3 of the i.f. transformer, or to connect a capacitor of about $0.01\mu F$ across R1.



★ components list

Resistors:

R1	56k Ω
R2	6.8k Ω
R3	2.2k Ω
R4	56k Ω
R5	6.8k Ω
R6	1k Ω
R7	22k Ω
R8	4.7k Ω
R9	1k Ω
R10	2.7k Ω
R11	68k Ω
R12	22k Ω
R13	1k Ω
R14	1k Ω
R15	8.2k Ω 5%
R16	8.2k Ω 5%
R17	37 Ω 5%
R18	4.7 Ω
VR1	5k Ω pot. with switch

All fixed resistors 10% except where otherwise specified.

Capacitors

C1	150pF 1% or 3%
C2	0.02 μF
C3	175pF 1% or 3%
C4	22pF 1%
CP	215pF 3% or 220pF 1%
C5	0.02 μF
C6	10 μF
C7	0.04 μF
C8	100 μF
C9	0.1 μF
C10	0.04 μF
C11	0.01 μF
C12	2 μF
C13	100 μF
C14	100 μF

Variable Capacitors:

VCI/2	208/176pF, Jackson type 00 slow motion, with screen
TCI, 2, 3	50pF trimmers

Transistors and Diodes

Tr1	AF117
Tr2	AF117
Tr3	AF117
Tr4	OC81D
Tr5	OC81
Tr6	OC81
D1	GD9, OA70 or OA81

Inductors:


IFT1	Weyrad P51/1
IFT2	Weyrad P51/2
IFT3	Weyrad P50/3V
T1	Weyrad LFD4
T2	Weyrad OPT1
T3	Weyrad P50/IAC Ferrite rod aerial—Weyrad RA2W

Other Components:

3 Ω p.m. loudspeaker. 4-pole 3-way rotary switch. Paxolin ($\frac{1}{8}$ in.) $8 \times 2\frac{1}{2}$ in. (two pieces). Coaxial aerial socket. Output socket. Closed-contact jack socket and plug. Knobs, sleeving, etc.

Fig. 4 (left): Details of a suggested cabinet

Fig. 5 (below): Calibration of dial

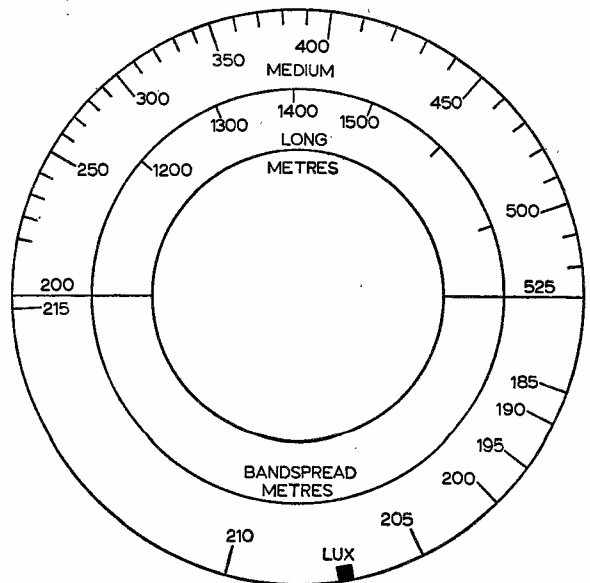

ON THE SHORT WAVES

MONTHLY NEWS FOR DX LISTENERS

Times in GMT
Frequencies in kc/s

THE BROADCAST BANDS

by JOHN GUTTRIDGE

Albania: *Radiodiffusion et Television Albanaise* (Rue Ismail Quemal, Tirana) has new English transmissions at 1200—1230 on 7,265 and 1630—1700 on 9,520. The 0630—0700 transmission is now on 7,265/9,390.

Czechoslovakia: *Ceskoslovensky Rozhlas* (Praha 2, Vinohradska 12) using 5,930/7,345 for English 1900—1930 to Europe. To Africa 1730—1830 on 5,930/7,285/7,345/9,795/11,990. English to North America is carried at 0100—0200 and 0330—0430 on 5,930/7,115/7,345/9,795/11,990. Also on Sundays 1400—1500 on 15,285/15,448/17,825.

France: *O.R.T.F.* (Maison de l'O.R.T.F., 116 Avenue du President Kennedy, Paris 16). For those interested in French domestic stations the latest issue of 'Paris Vous Parle' lists all French medium wave and v.h.f. stations.

Hungary: *Magyar Radio Es Televizio* (Brody Sandor-S.U., 5-7, Budapest VIII) in English 1930—2030 3,995/6,234/7,220/7,305/9,833/15,160; 2200—2230 3,995/6,234/7,220/7,305/15,160; 2330—2400 539/3,995/6,234.

Luxembourg: *Radio Luxembourg* (Villa Louvigny, Luxembourg) may be heard very faintly around 2200 on 15,350 carrying a relay of the 233 kc/s long wave French programme.

Monaco: *Radio Monte Carlo* (16 Boulevard Princesse Charlotte, Monte Carlo) now has a long wave transmitter. Frequency is 215 and power 1,250 kW. On air from 0500—0100 with same programme as 1,466/6,035/7,135.

Portugal: *Emissora Nacional de Radiodifusao* (Rua Sao Marcal, 1-A Lisbon) now uses 7,130/9,645 for the 0730—0900 English transmission.

Spain: *Radio Nacional de Espana* (General Yague 1, Madrid) has English 2020—2050 on 9,360.

U.S.S.R.: *Radio Dushanbe* may be heard around 1900 on 4,640 carrying the programme of Moscow I. *Radio Frunze* heard around 1600 on 4,008. Relays Moscow I at 1700. *Radio Kiev* (Ukrainske Radio, Radio Centre, ul Khreshchatik 24, Kiev, Ukrainian S.S.R.) has formed a Dx club. To qualify for membership listeners must send in three reception reports. Transmits in English Mondays and Thursdays, 1900—1930 on 6020/9,640 and 2230—2300 on 1,241. Also Tuesdays, Wednesdays, and Fridays at 0030—0100 on 7,120/7,140/7,280/7,310/7,330/9,680 and 0430—0500 on 7,180/7,290/7,310/7,330. The 1900 transmission on 6,020 seriously interferes with transmissions from Radio Nederland. *Radio Moscow* (Moscow) now has a 75 m.b. home service transmitter on 3,990. The 2300 English transmission can be heard surprisingly on 4,860 as this programme is intended for North America. The transmission does not appear to be a harmonic of 9,720. *Radio Petropavlovsk* may be heard with relay of Moscow I on 4,055 around 1930. *Radio Vilnius* (Lietuvos T.S.R. Radijas, ul Kanarskio 49,

Vilnius) has English, Sundays and Fridays, 2230—2300 on 7,113. Also believed to use transmitters in 51, 50, 41 and 40 m.bs. *Radio Yerevan* (Armenian Radio, Mravian Street 5, Yerevan 25) has Arabic 1900—1930 on 4,040.

Algeria: *La Voz de la Libertad* (F.P.L.N., 3 Rue Auber, Algiers) on air Sundays and Thursdays in Portuguese, 0015—0100 on 6,080.

Angola: *Radio Comercial de Angola* (Casilla Postal 269, Sa de Bandeira) has replaced 3,995 by 4,795. The station is on the air 1700—2400.

Ascension Island: B.B.C. relay station is expected to begin operations in June. Four 250kW transmitters are being installed.

Bechuanaland. B.B.C. relay station beams programmes to Rhodesia 0400—0730 and 1015—1145 on 7,295 and 1545—2015 on 4,842. Power is 10 kW.

Gambia: *Radio Gambia* (Bathurst) transmits 1710—2030 Mondays—Fridays on 4,820. Can occasionally be heard around 1900.

Morocco: *Radiodiffusion Television Marocaine* (I Rue Pierre Parent, Rabat) has English 2130—2230 on 11,735/15,410.

Nigeria: *Nigerian Broadcasting Corporation* (Broadcasting House, Lagos) has replaced 11,900 by 11,915. Other frequencies used for English 1700—1900 and 2100—2200 are 7,275/9,690/15,255.

Zambia: *Radio Zambia* (Broadcasting House, P.O. Box RW15, Ridgeway, Lusaka) can sometimes be heard between 1730—2000 on 3,270 in English.

China (People's Republic): *Radio Peking* (Peking) has English 2030—2130 in 58-51-48-42 m.b. and 2130—2230 in 51-48-42 m.b.

China (Republic): *Broadcasting Corporation of China* (*Voice of Free China*) (New Park, Taipei, Formosa) has English 0250—0350 7,130/11,825/11,860/15,345; 1000—1045 7,130/9,655/9,685/11,825/11,860; 1530—1610 7,130/9,685/9,720/11,725/11,825/15,125/17,890.

Indonesia: *Radio Republik Indonesia* (P.O. Box 157, Djakarta) has news in English on 9,555 from 1000—1010.

Japan: *N.H.K.* (Tokyo). Results of a poll held among its listeners by N.H.K. to find the station they listened to most, apart from N.H.K., were 1: Radio Australia, 2: B.B.C., 3: Voice of America, 4: Radio Peking, 5: Radio Nederland, 6: Radio Canada, 7: Radio Moscow, 8: Swiss Broadcasting Corporation, 9: La Voz de los Andes, 10: Deutsche Welle.

Thanks for information this month go to M. Barraclough, G. Roberts, I. Black, B. Burling, D. Park, S. Haageman, L. Sapiets, R. A. Adair, S. Ormerod and A. W. T. Moore.

THE good openings on the l.f. bands continue as some of the logs received show. Top band has been particularly good and has produced many W's for those who "listened with intent". Eighty has been noisy with a bit of the long distance "stuff" creeping through the chinks now and again. Forty—even noisier with fewer chinks! Twenty, wide open at times and staying open until quite late. Europeans still audible at 2200 hrs!

Fifteen metres, described by one SWL as the Yo-Yo band. One minute half the world and the next minute—the proverbial Miss Adams.

Ten metres getting better but still a bit patchy, though those that do come through usually do it loud and clear and nearly always on a.m. too. W's are reported at 5 and 9 plus on one or two occasions.

All in all and with a bit of luck the summer looks like being a "good 'un" from the amateur bands point of view. If conditions hold it should be a very lively NFD this year.

Low Frequencies

Steve Wilson went on safari into the wilds of 160. Armed only with an HRO/MX, a BC348R and a dipole cut for 1830 kc/s he captured DJ6TK, DL1FF, DL8AM, DL9KRA, E19J, G, GI, GM, GW, HB9CM, IS1FR, OHØNI (Aaland Is.), OL1AEE, OL8ACC, PAØDC, VE1ZZ, WIBB/1, W2IU, W2GGL, W8RRH, K8MGW ZB2AM, ZB2AJ, 4U1ITU, 9H1AE, 9L1HX, 9M4LP (Malaya).

R. Iball (Worksop), SX28+PR30, 80ft. l.w., K1OYB/1, K2DGT, K8HKB, OE5CR, VE2ATU, VO1FB, W1BB/1, W1HGT, W2FYT, W2GGL, W3ELS, W8FGK, W8HGW, W9EWC, WØVXO, 4U1ITU, all c.w. On 80 metre phone Alan Lattimore (Dartford), CR100, 20ft. whip raised many G's plus CT1MS, KP4AST, K9JWV, YU2NZ. James Brown (Cardiff), 19 set and a dipole logged EA4GZ, IØFGM, K4AP, OX3LP, OY7ML, many VE's including VE6ALQ, VP5AB, VP9DW, many W's, YV5AFH, ZB2AJ. James would like to know the location of VS3EA (so would I!). No reports for Forty this month—sacrilege, so a new heading and on to the h.f. bands.

High Frequencies

K. Evans (Shepperton), HE30, 132ft. l.w., 20 metres s.s.b., KR6UL, VK2JZ, VK3ALB, VK4SB, VK6SA, VK7SM, VP5GU, YV5AIP, ZL1AS. Congratulations on passing the RAE Keith.

Colin Morris (Tenbury Wells), Electroniques front end into homebrew 9 valve s/het, 33ft. l.w., BV1USA, CN8BB, CP1FOF, CR6AC, EP3AM, FR7ZB, HI8 XMT, HK2OQ, HP9FC/MM, JA6NP, KG6APS, KL7EBK, KP4AXC, KR6UL, KV4AB, KZ4PW (no connection with the magazine!), LU5DBS, OX3LP, PY2BFO, PZ1BW, TF2WJK, UA9HA, VE1, 2, 3, 4, 5, 6, 8, Ø, many VK's, VQ9HT, VS9AJR, YS1JRD, ZD8JPL, ZS1VT, ZS6IK, ZL2BE, 7Q7PS, 7X2BG, 9J2AB, all s.s.b. D. Howell, 7 valve receiver, 66ft. l.w., KR6QL (Okinawa), KL7EBK (Alaska), MP4BB (Bahrain Is.), VK2NN, VK5NJ, WØNNI, W7ADS, ZS2NV, ZD8ARP, ZL3UY, ZL4BX, 4X4JU. A rare one from Frank Videan (St. Albans) who reports hearing WA3BYG/AM on twenty, the /AM meaning aeronautical mobile and giving his location as 35N, 78W.

On Fifteen, A4378 (Cardiff), 9v. s/het, 95ft. l.w., heard CN8AD, K2EVG, K9WEZ, W1DUJ, WA1BYA, WA2FQG, W3GTL, YO3TL, 9H1R. A. Trickey (Bristol), 9R-59+PR30, 100ft. l.w., KP4CNF, W1JRY, W2BLQ, W3TDV, YV4BG, 5A3TX, 9G1FL, 9H1AL. Paul Baker (Pantygasseg), HE30, 61ft. l.w., CN8's, CR4AB, CR6CZ, CR7FM, CR8AT, FW8BJ (Wallis Is.), KP4AXC, KZ5AM, MP4BBA, OA4YI, PY1, 2, 3, 5, 9, PZ1BE, SVØWB (Rhodes), SVØWO (Crete), VE1-5, VO1, VP9, W1-Ø, YV1DP, ZB2AG, ZC4AK, ZE2KL, ZE6JL, ZS1BV, ZS6IN, 4X4HB, 5A1TK, 5N2FEL, 5X5FR, 6W8BG, 7X2WW, 9H1R, 9J2DL, 9K2AD, 9Q5GG, 9U5BB, 9X5MW. Paul queries a 9Y4RS claiming his QTH as Trinidad.

Ten metres, Chris Clarke (Farnham), sends in a colossal list which includes K1, 3, W1, 2, 3, 4, 8, WA4, plus 52 G's. A4378 again reports GW's, and ZE3JU, ZS9G.

What and Where

Reports from readers and over the air say the following are to be had for the listening. 4S7IW (Ceylon), around 14200, ZL4CH (Campbell Is.), VKØ (Macquarie Is.) still at it, also around 14200. VK9PL (Papua) on 14 Mc/s, CEØAC (Easter Is.), c.w. end of 20, FU8AG (New Hebrides) ditto, TT8BS (Chad) on 15 c.w. and a TY3 ditto (Dahomey). Contests include May 8th, 144 Mc/s Portable contest, 22nd, D/F qualifying event, 28-29th, 420 Mc/s open contest, 29th 1296 Mc/s contest. June 4th and 5th National Field Day.

PRACTICAL TELEVISION MAY

- ★ Testing Transformers with an Oscilloscope
- ★ Solid State TV
- ★ Line Scan Stage for the Olympic II
- ★ Trimming by Test Card

on sale 21 April

PRACTICAL ELECTRONICS


4 special projects for the motorist:

- LDR Parking Light
- Direction Indicator
- Anti-theft Alarm
- Tachometer

FREE BOOKLET
TRANSISTOR DATA

PLUS
Simple Transistor Tester

May issue on sale 14 April

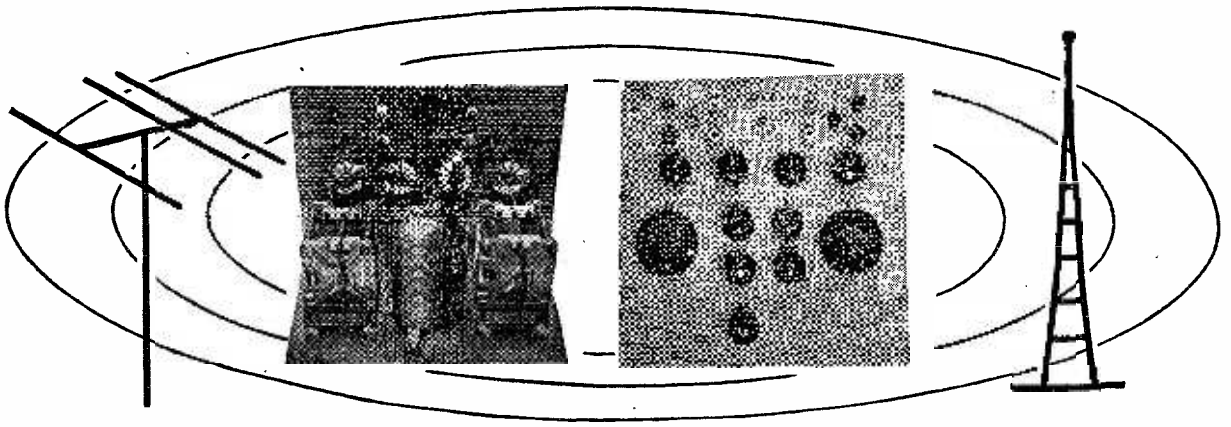

Comprehensive ATU by D.Gibson G3JDG

IT is a strange fact that a very great percentage of people tend to spoil the ship for a "ha'porth of tar". This, unhappily, is all too true in amateur radio. The ham with nice new shiny transmitter, home-built or commercial, will usually have a pi-tank output circuit.

The pi-tank offers many advantages. For instance, it gives good harmonic discrimination against TVI and it will match a variety of impedances. This is another way of saying that it will often tune or load up anything from a dipole to any random length of wire which happens to be to hand. Although this is true, there are drawbacks.

Component values in a pi-network are calculated very carefully and the capacitors and inductor cannot merely be selected to resonate at the desired frequency. As will be appreciated, there are a great number of combinations of L and C which will tune to a given wavelength. How then do we decide which is the correct combination?

Pi Configuration

The pi configuration is often used in low pass filters and again exactly the same problem is present—which combination of inductance and capacitance to use. Fig. 1 shows the circuit in question, and you will notice that, in addition to the two capacitors and inductor, two resistances are shown R_{in} and R_{out} .

These are the flies in the proverbial ointment. R_{in} is calculated from the valve anode voltage and current in the case of transmission, and R_{out} is the impedance of the antenna. A dipole, and indeed most beams and quads etc., are commonly fed with

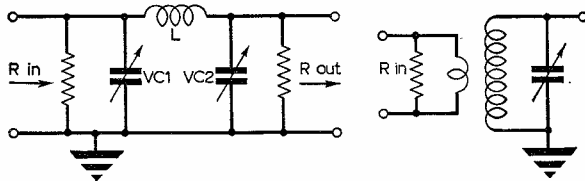


Fig. 1 (left): Pi-network showing input and output impedances.
Fig. 2 (right): Parallel tuned circuit showing link input impedance R_{in} .

75Ω coaxial so that pretty well all pi-networks are designed to feed into 75Ω.

If we now stick the odd length of wire in the output terminal it is highly probable that we can still load it, but it is almost certain that it will not present an impedance of 75Ω. Any transmitting amateur will tell you that a low pass filter will only work efficiently if it is set up correctly and is terminated in the correct impedance.

Although perhaps not generally realised, this is also true of the pi-tank. If you use it to load odds and ends it does not follow that it is working efficiently, or that it will give the same harmonic discrimination, the very thing for which it is often used.

In the case of a parallel tuned circuit Fig. 2, it will be seen that R_{in} is shown as a link coupling. Unfortunately optimum coupling will vary from band to band, so that if any degree of constant efficiency is to be maintained this link will need to be variable not only in the degree of coupling, but also its inductance.

The Solution

In the case of matching an aerial to a receiver or transmitter it is found that no one circuit will suit every single need. Some aeriels are very high impedance and might require a parallel tuned circuit while others are low impedance and would require a series tuned circuit.

Some time ago the writer wrote an article on a S.W.R. bridge (PRACTICAL WIRELESS, Feb., 1965), and contained in the same case was a coil and a capacitor. If high impedance was desired, then the circuit was wired in parallel, if low impedance then it was altered to series tuned with the aid of a soldering iron.

After a short time it became obvious that some form of switching would be a great saving of opening and closing the case at each change of antenna not to mention the "frigging" about with the link coil at each change of band. Accordingly back copies of various magazines were scanned but the same problem came up again and again.

One a.t.u. was fine for tuned feeders but not long wires. Another tuned only three bands or else no

provision was made for varying the link winding. Others had link winding with no alternative input. In short each design, although doing its intended job very well had limitations and the most serious one was lack of flexibility. After writing down all the different desirable properties of the perfect a.t.u. (for the writer) the following was arrived at.

It should be switchable to almost any configuration, and it must match anything from low to high impedance from the longest long wire to the shortest and everything in between. (Yes, even end fed coat hangers and base loaded cufflinks too!) It must have an optional and variable link which should be controllable from the front panel, and be usable with the three main antenna inputs single wire (any length), coaxial feed and tuned feeders. It should also be usable in any of the popular configurations, parallel tuned, series tuned, pi-network, L network, transmatch, balanced transmatched etc.

This unit will do just these things from 1.8Mc/s to 30Mc/s continuous, and it even peaks some of the medium wave band as a bonus. It will also give added discrimination against unwanted harmonics on transmission, and give an extra stage of quite sharp selectivity on reception. *NOTE:* It will not give any gain. However it will match impedances and the difference for the prototype between tuned and untuned peaks up to something like three to four S points.

A six foot length of lighting flex draped across the bench was loaded up on all bands while OK's have been heard on topband. The same set up raised East Coast American stations, plus W6 and W7 and PY.

It will, of course, peak signals on all frequencies between 1.8 and 30Mc/s and is therefore entirely suitable for listening to the commercial bands as well as the amateur bands.

SWL's or those intending to use the unit for reception only can use small Yaxley switches and receiving type capacitors, this will also result in a smaller and more compact unit. The coil too is not critical and some may like to use an inductance which is to hand or wind one themselves. As a guide the inductance of the coil specified is $41\mu\text{H}$.

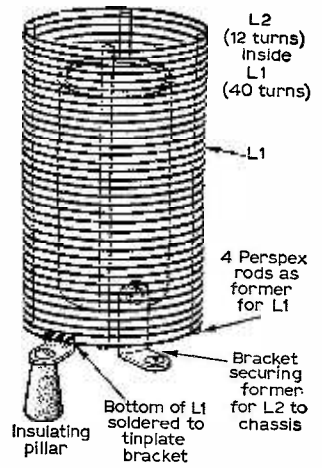


Fig. 4: Mounting details of L1 and L2.

The Circuit

The complete circuit in Fig. 3 shows two coils, three capacitors, eight switches and ten terminals, together with a coaxial socket. The link coil L2 has a variable capacitor VC3 which gives variable loading. Also the link coil itself can be switched to vary its inductance by turning S5.


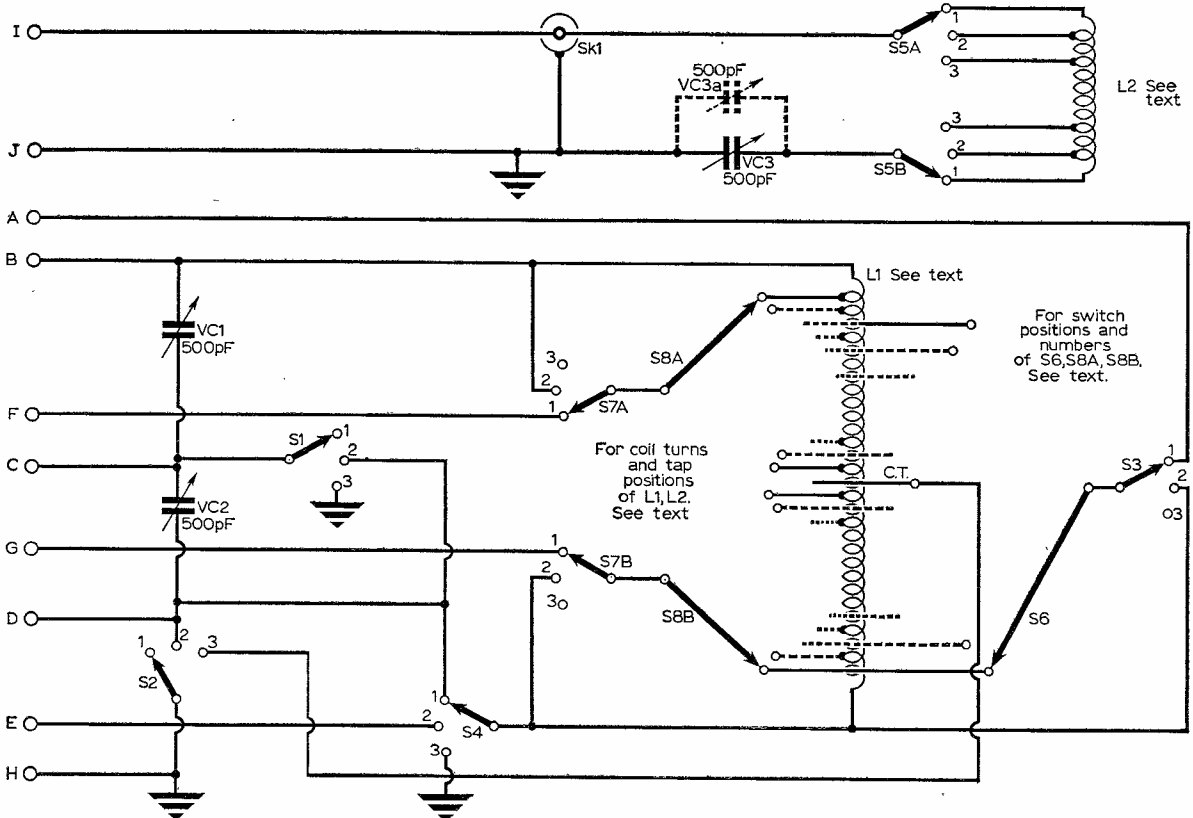


Fig. 3: Complete circuit diagram of the unit.

CODAR — QUALITY

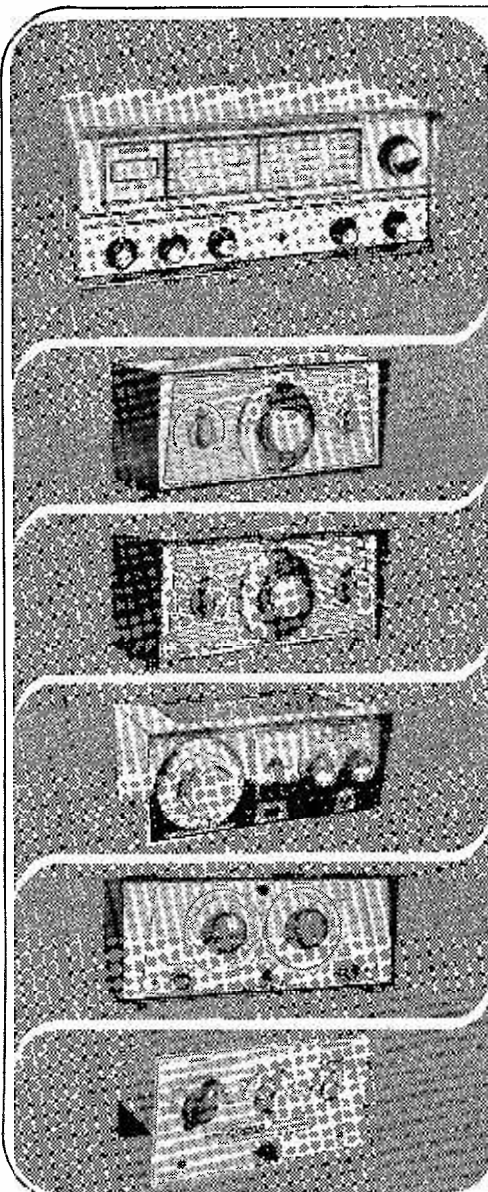

ANOTHER CODAR TRIUMPH!

THE NEW 1966 CR.70A COMMUNICATION RECEIVER

This completely new receiver sets a new high standard for performance and finish unequalled at the price, and is a worthy addition to the outstanding range of CODAR quality communication equipment. Frequency range: 560 Kc/s-30 Mc/s (540-10 metres) in four ranges: 560 Kc/s-1.5 Mc/s; 1.5 Mc/s-4.2 Mc/s; 4.2 Mc/s-11.5 Mc/s; 11.5 Mc/s-30 Mc/s. Slide rule scales for each band calibrated in frequencies plus an additional logging scale in degrees. Two speed vernier tuning control with reverse slow tune action. Unique aerial input stage exclusive to the CR.70A employing High 'Q' Air-spaced CODAR-QOIL Inductor giving extremely high gain with low noise level. Panel aerial trimmer for peaking weak signals. Double tuned I.F. Iron cored transformers: 470 Kc/s with EF183 frame grid valve for maximum gain and selectivity. 5 valves (including two twin triodes) giving 7 valve line-up. Separate B.F.O. stage for CW and SSB reception. Calibrated signal strength 'S' meter, illuminated. Automatic Volume control. Panel phone jack for 'private' listening. 2-3 ohm output for external speaker. Superb styling, metal cabinet in the new Orgranaso Satin lustre finish. Size: 13" x 5 1/2" x 7 1/2". For A.C. 200/250v. Ready built. Not a Kit at the fantastic low price of £19.10.0. Carr. 7/6.

CODAR R.F. PRE-SELECTOR MODEL P.R.30. Considerably improves the performance of any superhet receiver over 1.5-30 Mc/s. Uses EF183 Frame Grid Valve, and provides up to 20dB gain plus substantial image rejection, improved signal/noise ratio and selectivity. Selector switch for either dipole or single wire antenna. Power requirements 180-250 volts 12mA H.T. 6.3 volts. 3 amp L.T. Size 8 1/2 x 5 x 4in. Ready built, complete with cables, plugs and instructions, £5.10.0. Carr. 3/6. **MODEL P.R.30X.** Self powered model for 200-250v. A.C. Also provides 25mA at 200v. H.T. and 6.3v. 1 amp L.T. for other accessories £7.4.0. Carr. 3/6.

CODAR "Q" MULTIPLIER MODEL R.Q.10. For use with any superhet receiver with an I.F. between 450 and 470 Kc/s. Provides considerable increase in selectivity for either peaking or rejecting a signal on AM, CW, or SSB. B.F.O. Size 8 1/2 x 5 x 4in. Power requirements 180-250v. H.T. at 5mA 6.3v. 3 amp L.T. Ready built complete with cables, plugs and instructions. £6.15.0. Carr. 3/6. **MODEL R.Q.10X.** Self powered version for 200-250v. A.C. and also provides 25mA at 200v. H.T. and 6.3v. 1 amp L.T. for other accessories £8.8.0. Carriage 3/6.

CODAR A.T.5. 12 WATT 2 BAND TRANSMITTER. The newest most compact transmitter for fixed or mobile use on 160-30 metres. "The tiny TX with the BIG voice". Size only 8 1/2 x 5 x 4in. (Base area is less than two-thirds of this page!) High stability new type calibrated VFO. 1.8-2.0 Mc/s and 3.5-3.8 Mc/s (up to 4 Mc/s export). Air-spaced CODAR COIL Pi-net output, P.A. Plate current meter plus neon indicator. Plate-Screen modulator. AM/W switch and Panel key jack. Plug changeover for 6 or 12 volt heater supply. Ready built £16.10.0. Carr. 4/- **A.T.5 POWER SUPPLY UNITS.** For 200-250v. A.C. and 12v. Solid state for Mobile use, complete with all Transmit/Receive changeover switching available.

CODAR-KIT CR.45K MAINS T.R.F. SHORT-WAVE RECEIVER. World wide reception—North and South America, Russia, India, Australia, Far East, Amateurs, Shipping, etc. ★ Separate electrical bandspread. ★ 3 slow motion vernier drives. ★ Low loss polystyrene plug-in coils, factory aligned ★ Dials calibrated in frequencies and degrees. ★ Power output 3 watts for 2/3 ohm speaker. ★ Valve line-up: ECC81, EL84, EZ80. Size 12 x 5 1/2 x 7in. **CODAR-KIT CR.45K** complete with valves, 3 coils (10-28, 25-75, 60-176 metres) and 11 page instruction manual, £9.10.0. Carr. 5/6. Extra coils 4/9 each. Instruction manual only 4/- (credited on order). (Can also be supplied ready built—price on request).

CODAR-KIT MINI-CLIPPER—OUR FAMOUS SHORT-WAVE RECEIVER ★ Can be built in one evening ready to switch on and bring the World to your fingertips at very low cost. ★ Supplied complete with valve, one coil 25-75 metres and 4-page instruction manual. PRICE 39/6. Carr. 3/- Extra Coils 4/9 each. Instruction Manual only 4/9 (credited on order). Electrical Bandspread available. Provision to add 2 transistor amplifier.

SEND 6d. IN STAMPS FOR ILLUS. LEAFLETS OF THE CODAR RANGE • H.P. TERMS AVAILABLE • WORLD-WIDE MAIL ORDER SERVICE



CODAR RADIO COMPANY

BANK HOUSE, SOUTHWICK SQUARE
SOUTHWICK, SUSSEX. Tel. 3149

G3IRE G3HGQ

Canada: Codar Radio of Canada, Tweed, Ontario

WEYRAD

COILS & TRANSFORMERS FOR CONSTRUCTORS


Special versions of our P50 Series are now available for AF117 or OC45 Transistors. They can be used in the standard superhet circuit with slight changes in component values, details of which are given in the latest edition of the Constructors' Booklet Priced at 2/-.

Oscillator Coil	P50/1AC (For OC45)	P50/1AC (For AF117).....	5/4
1st I.F. Transformer	P50/2CC (For OC45)	P51/1 (For AF117).....	5/7
2nd I.F. Transformer.....	P50/2CC (For OC45)	P51/2 (For AF117).....	5/7
3rd I.F. Transformer.....	P50/3CC (For OC45)	P50/3V (For AF117).....	6/-
Rod Aerial	RA2W.....		12/6
Driver Transformer	LFDT4/1		9/6
Output Transformer	OPT1		10/6
Printed Circuit	PCAI		9/6


I.F. TRANSFORMERS & COILS FOR VALVE CIRCUITS

Production of Tuning Coils (Type "H") and I.F. Transformers is being continued and details of these and our other components are given in an illustrated folder which will be forwarded on request with 4d. postage please.

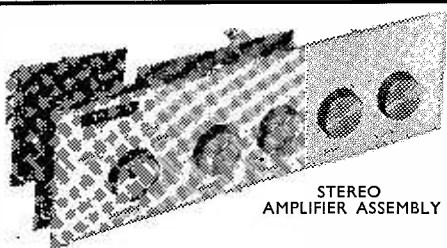WEYRAD (ELECTRONICS) LIMITED
SCHOOL STREET, WEYMOUTH, DORSET



STEREO
AMPLIFIER ASSEMBLY

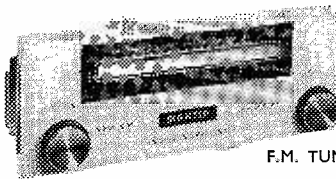

F.M. TUNER

KITS WITH A FUTURE

The Martin Audiokit assembly you own today can become part of an even better hi-fi system tomorrow. No other system allows you to enlarge your installation stage by stage in the way Audiokits do. They comprise a wide range of very well made prefabricated units in which the connections are standardised throughout. Each is rigorously tested to stated specification before despatch. **NEW KITS FOR ADDING ON ARE IN COURSE OF PREPARATION NOW**—so by starting with Martin today, you insure yourself for still better listening tomorrow.

Choose Martin for quality

- Build for 3 or 15 ohm system
- Start with Mono and add Stereo or start completely with Stereo
- Power packs available
- Professionally styled escutcheon plates
- Assembly is easy by following the well presented instructions

- 5 stage input Selector £2.7.6
- Pre-amp. and vol. control £1.17.6
- Pre-amp. with tone controls £3.2.6

Send for leaflet describing entire range

- 10 watt amp. (3 ohms) £5.12.6
- 10 watt amp. (15 ohms) £6.12.6
- Mains power supply £2.15.0



Martin Audiokits and Recordkits are obtainable from good stockists everywhere. In cases of difficulty please write direct.

MARTIN ELECTRONICS LTD., 154/155 HIGH ST., BRENTFORD, M^{SEX}
Phone: ISLeworth 1161/2

MARTIN ELECTRONICS LTD., 154-155 High Street
Brentford Middlesex

Full details of Martin Audiokits please

NAME

ADDRESS

(Block letters)

P.W.5

With S5 acting as a sort of coarse loading and VC3 a fine adjustment a great range of control is available over the link winding and the amount of coupling can be varied between wide limits. R.F. currents circulating in the unused portion of both the link and the main coil were found to have negligible effect on performance.

L2 is wound on a 2in. dia. former and mounted inside L1. This avoids the awkward method of winding it around the outside of L1, a rather difficult task because of the tapping points and numerous lead-off wires coming from L1. Details of the mounting and positioning of L1 and L2 are shown in Fig. 4. VC3a, shown in dotted lines in Fig 3, is an unused gang of a 500pF twin gang and is only included for completeness.

Coil L1

This is the main tuning coil and takes time and patience to wire up. The tapping wires are all lengths of 18s.w.g. tinned copper wire threaded with sleeving. Great care should be exercised as a dry joint or a poorly soldered connection here can prove disastrous later on, especially when the coil is mounted in position and all the taps are soldered on. Fig. 5 gives all relevant information on L1.

One word of warning before passing on. Ensure that none of the taps, i.e. the lead off wires from L1 touch. Failure to observe this will result not in an a.t.u. but a first-class arc welding unit.

Other Components

VC1 and VC2 must be insulated from the chassis and front panel. In the prototype they are large transmitting types and are mounted off the chassis with small Eddystone stand-off ceramic insulators. The holes in the front panel for their spindles were cut with a B7G chassis cutter to allow ample clearance.

The switches are as shown and are straightforward switches obtained from the "surplus" market. If the

Photograph shows rear view of the completed unit.

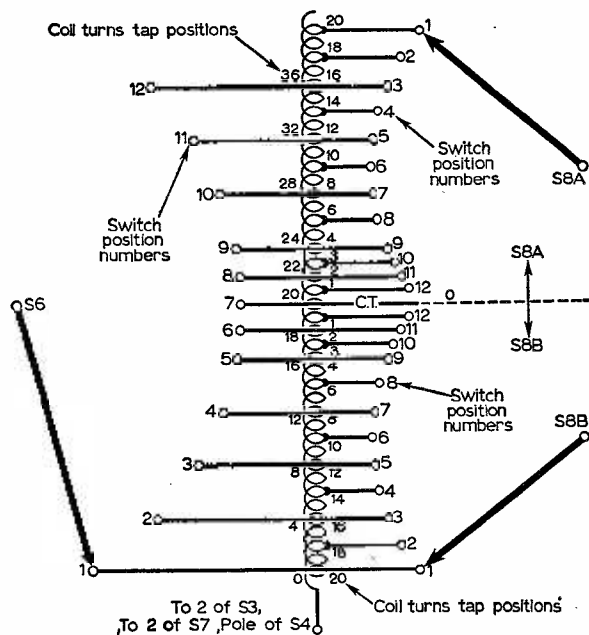
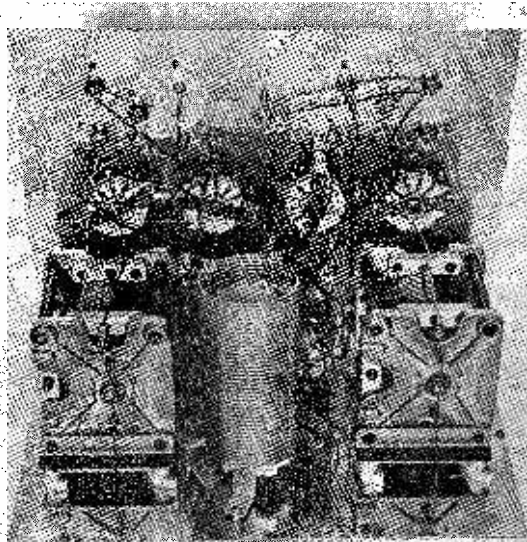


Fig. 5: Positions on main coil L1.

unit is to be used for transmission then these should be ceramic. If, however, it is only to be used for receiving then ceramic or ordinary Yaxley type switches will suffice.

The coloured terminals at the top are arranged in groups of five, the centre one of each bank H and J being earthed. There is also a coaxial socket mounted centrally or if preferred terminal I together with one of the earth terminals may be used. The terminals may be used as either input or output and by this factor alone a large number of permutations are possible without recourse to any switching at all.


S8 allows the coil to be shorted out equally from either end thus the link coil is always at the centre of the main coil. This would not be so if the inductance were varied by shorting out from one end only. As the switch tapped out the coil the link would, in effect, move down towards the tapping point automatically and once the tap had gone above the link there would be very little coupling at all.

Also, of course, in the case of certain aerials it is desirable to tap in equidistant from the ends of the coil. In this instance with S7 in position 1 and the aerial input on terminals F and G, S8 will perform just this function.

S6 is provided to short out L1 from one end only. This is useful when the unit is switched for a pi-network or L network or wherever the inductance is to be tapped or varied. It is also possible to use the tap as an input or output point by using terminal A and switching S3 to position 1.

Configuration

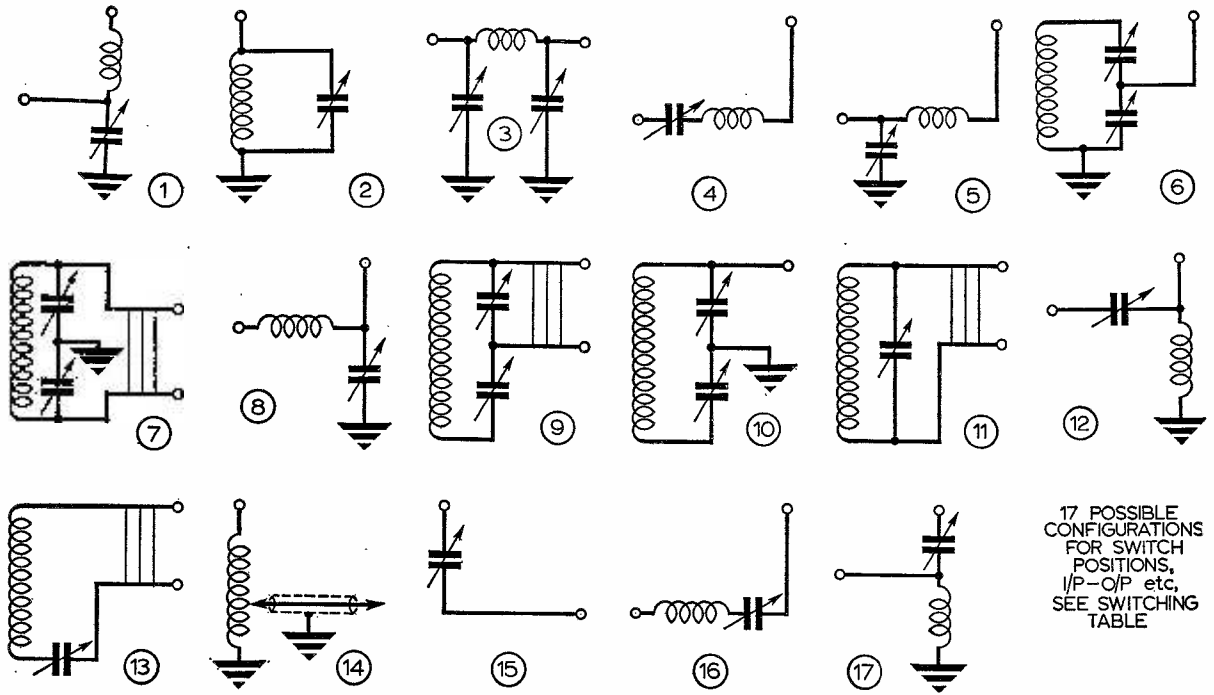The different configurations possible appear to be almost limitless so no claim is made as to the maximum possible number. However some of the circuitry available is shown in Table 1, together with the position of the switches, the terminals to use, and which capacitors are in or out of circuit. With most



Above—Table I shows some of the configurations possible.

Below—Switching and I/P-O/P connections for configurations shown in Table I.

SWITCH NUMBERS											
Diagram Number	I/P	O/P	One	Two	Three	Four	Five	Six	Seven	VC1	VC2
1	B	E	3	2	2	2	VARIABLE DEPENDENT ON BAND E.T.C.	DITTO AS SWITCH FIVE	1	IN	OUT
2	See text	B	3	2	1	3			1	IN	OUT
3	D	B	3	1	2	1			1	IN	IN
4	C	E	1	1	2	2			1	IN	OUT
5	B	E	3	2	2	2			1	IN	OUT
6	See text	C	1	2	1	1			1	IN	IN
7	SKI, I/J	B/D	3	1	2	1			1	IN	IN
8	E	B	3	2	2	2			1	IN	OUT
9	SKI, I/J	B/C	1	1	2	1			1	IN	IN
10	SKI, I/J	B	3	1	2	1			2	IN	IN
11	SKI, I/J	B/C	2	1	2	1			2	IN	OUT
12	C	B	1	1	2	3			2	IN	OUT
13	SKI, I/J	E/C	2	1	2	2			1	OUT	OUT
14	SKI/A	B	1	1	1	3			1	IN	OUT
15	B	C	1	1	1	2			2	IN	OUT
16	E	C	1	1	2	2			2	IN	OUT
17	B	C	2	1	2	3			2	IN	OUT



Why anyone can build a Heathkit model

The success of a Heathkit model is assured by the world-famous Heathkit manual.
Send for the FREE Catalogue giving full details of the complete range.

A KIT FOR EVERY INTEREST . . . HOME — SERVICE WORKSHOP — LABORATORY

TEST & SERVICE INSTRUMENTS



- | | Kit | Assembled |
|--|----------|-----------|
| ● 5in. OSCILLOSCOPE, 10-12U
TB 10 c/s—500 kc/s. ... | £35 17 6 | £45 15 0 |
| ● 3in. OSCILLOSCOPE, OS-2
TB 20 c/s—200 kc/s ... | £22 18 0 | £30 8 0 |
| ● 4½in. VALVE VOLTMETER,
V-7A ... | £13 18 6 | £19 18 6 |
| ● 6in. VALVE VOLTMETER,
1M-13U. ... | £18 18 0 | £26 18 0 |
- RF and HV probes available as extras

- | | Kit | Assembled |
|--|----------|-----------|
| ● REGULATED POWER SUPPLY, IP-20U (Transistor), 0-5-50v D.C. to 1-5A. ... | £35 8 0 | £47 8 0 |
| ● TV ALIGN. GENERATOR, HFV-1, 3-6-220 Mc/s ... | £37 18 0 | £47 10 0 |
| ● RF SIGNAL GENERATOR, RF-1U. (Up to 100 Mc/s fund.) | £13 8 0 | £19 18 0 |
| ● MULTIMETER, MM-1U (V, A, Res, dB) ... | £12 18 0 | £18 11 6 |



V-7A

- | | Kit | Assembled |
|--|----------|-----------|
| ● ELECTRONIC SWITCH, S-3U
Scope Trace doubler ... | £12 18 0 | £18 10 0 |
| ● AUDIO SIGNAL GENERATOR, AG-9U
10 c/s—100 kc/s ... | £22 10 0 | £30 10 0 |
| ● AUDIO SINE/SQ GENERATOR, A0-1U
Sq wave 20 c/s-25 kc/s ... | £14 15 0 | £21 5 0 |
| ● SINE/SQ GENERATOR, 1G-82U
Freq. range, 20 c/s-1 Mc/s ... | £24 10 0 | £36 10 0 |
| ● AUDIO VALVE MILLIVOLTMETER, AV-3U. 10 c/s-400 kc/s ... | £16 10 0 | £22 18 0 |
| ● HAR. DISTORTION METER, 1M-12U ... | £24 15 0 | £34 0 0 |
- Many other instruments available.

AMERICAN HEATHKIT MODELS

- A wide range available including:
- DE-LUXE AM/FM PORTABLE TRANSISTOR RADIO, GR-43. An outstanding Luxury model ... Kit £102 5 0 incl. PT
 - SHORT-WAVE RECEIVER, GR-44E. For short-wave listening at low cost ... Kit £22 10 0
- Send for American Catalogue, 1/- incl. Post.

TRANSISTOR RADIOS

“OXFORD” LW/MW RECEIVER, UXR-2
Kit £14.18.0, incl. P.T.

6 TRANSISTOR PORTABLE, UXR-1, LW/MW
Kit £12.11.0, incl. P.T.

“MOHICAN” GENERAL COVERAGE RECEIVER, GC-1U ... Kit £37 17 6 Assembled £45 17 6

ELECTRONIC WORKSHOP, EW-1 (Experimental Kit) ... £7 13 6 incl. P.T.

JUNIOR RADIO, UJR-1 ... £2 7 6 incl. P.T.
Headphones 30/- extra. Additional amplifier stage (will work speaker), 16/6 extra.

A WIDE RANGE OF BOOKS ON ELECTRONICS AND RADIO. PLEASE SEND FOR LISTS AND PRICES.

● All prices quoted above are Mail Order prices.

WELCOME TO OUR LONDON HEATHKIT CENTRE

In response to the request of many customers, we have opened a showroom and retail stores at 233 Tottenham Court Road. Tel. MUSEum 7349.

WHEN YOU ARE IN TOWN, WE HOPE THAT YOU WILL VISIT US THERE.

AUDIO Hi-Fi



F.M. TUNER

- | | Kit | Assembled |
|---|----------|----------------|
| ● F.M. TUNER (in two parts), 88-108 Mc/s. Total price Kit £16.8.0, incl. P.T. | | |
| ● A.M./F.M. TUNER (in two parts), 88-108 Mc/s, L-M-S waves. Total price Kit £27.5.0, incl. P.T. | | |
| ● 3+3W STEREO AMPLIFIER, S-33H. Inputs for P.U. (Deram) radio, Aux. ... | £15 17 6 | £21 7 6 |
| ● 3+3W STEREO AMPLIFIER, S-33. Inputs for P.U. (crystal) or radio ... | £13 7 6 | £18 18 0 |
| ● 9+9W STEREO AMPLIFIER, S-99. Inputs for radio, tape, Aux., all P.U.s ... | £28 9 6 | £38 9 6 |
| ● 20+20W STEREO AMPLIFIER, AA-22U. Transistor, inputs for P.U. (Mag.) and 4 other | £39 10 0 | (less cabinet) |
| ● 5W MONO AMPLIFIER, MA-5. Inputs for P.U. and radio ... | £10 19 6 | £15 10 0 |
| ● 10W POWER AMPLIFIER, MA-12. For use with Control units, UMC/USC ... | £11 18 0 | £15 18 0 |
| ● 50W POWER AMPLIFIER, MA-50 ... | £19 18 0 | £27 18 0 |
| ● 4 CHANNEL MIXER TM-1. Transistor, battery operated ... | £11 6 6 | £16 17 6 |
| ● TAPE PRE-AMP (MONO) TA-1M. Needs P.S. and Audio Amplifier ... | £19 18 0 | £28 18 0 |
| ● MAGNAVOX 363 DECK, ½ Track ... | | £13 10 0 |

SPEAKER SYSTEMS



Berkeley

- | | Kit | Assembled |
|---|----------|------------|
| ● BERKELEY slim-line, 2-LS, Cabinet, fully finished ... | £18 10 0 | £23 0 0 |
| ● COTSWOLD standard, 3-LS Cabinet (in the white) ... | £25 12 0 | £33 17 0 |
| ● COTSWOLD MFS, 3-LS, Cabinet (in the white) ... | £25 12 0 | £33 17 0 |
| ● SSU-1 Low-priced System, 2-LS Cabinet (in the white, less legs) ... | £11 17 6 | incl. P.T. |

A wide range of other Speakers available.

‘AMATEUR’ EQUIPMENT

A wide range of models including:

- AMATEUR BANDS RECEIVER, RA-1 (160-10m). The ideal fixed station, portable or mobile receiver. Many features incl.: ‘S’ meter. Kit £39.6.6, Assembled £52.10.0



RA-1

- | | Kit | Assembled |
|--|----------|-----------|
| ● COMMUNICATIONS TYPE RECEIVER. RG-1 600-1500 kc/s, 1-7-32Mc/s ... | £39 16 0 | £53 0 0 |
| ● 160-10M TRANSMITTER, DX-100U ... | £79 10 0 | £104 15 0 |
| ● 80-10M TRANSMITTER, DX-40U ... | £33 19 0 | £45 8 0 |
- Other kits in range include: 55B Adaptor, SB-10U £39 5 0

Variable Freq. Oscillator, VF-1U, £10.17.6. Balun Coil Unit, B-1U, £4.15.6. Grid-Dip Meter, GD-1U, £10.19.6. Multiplier, QPM-1, £8.10.0. Reflected Power Meter, HM-11U, £8.5.0.

Also wide range of American models. Please send for details.

To: DAYSTROM LTD., Dept. P.W.-5, GLOUCESTER, ENGLAND

Please send me FREE BRITISH CATALOGUE (Yes/No)


Full details of model(s).....
American Catalogue, 1/- Post Paid (Yes/No)

NAME

ADDRESS



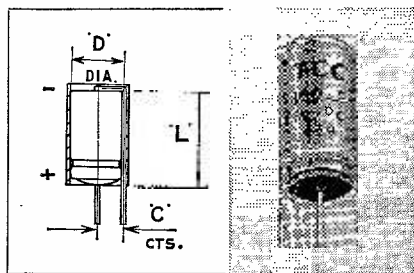Sub-miniature Electrolytics for Transistor Circuits



T.C.C. TYPE No.	Case Size in inches			Maximum D.C. Wkg. Voltages and Cap. (μ F)					
	D	L	C	3V.	6V.	9V.	12V.	15V.	25V.
CE.2 'V' or 'H'	$\frac{1}{8}$	$\frac{1}{2}$	0.07	8	6	4	3	2	—
CE.3 ..	$\frac{3}{8}$	$\frac{7}{8}$	0.1	25	20	15	10	6	4
CE.4 ..	$\frac{3}{8}$	$\frac{1}{2}$	0.1	40	30	20	15	8	6
CE.5 ..	$\frac{1}{4}$	$\frac{7}{8}$	0.14	50	40	25	20	10	8
CE.6 ..	$\frac{1}{4}$	$\frac{1}{2}$	0.14	80	60	40	30	15	12
CE.7 ..	$\frac{3}{8}$	$\frac{1}{2}$	0.18	100	75	50	40	20	15
	D	L	C	3V.	6V.	10V.	15V.	25V.	50V.
CE.8 ..	$\frac{1}{4}$	$\frac{3}{4}$	0.14	100	80	60	40	25	8
CE.9 ..	$\frac{3}{8}$	$\frac{3}{4}$	0.2	250	200	160	100	60	20

V=Vertical Mounting H=Horizontal Mounting

Operating Temperature Range. —20°C. to +60°C.

Connection wires are welded for low resistance contact, and solder-coated for ease of assembly, the standard length being $1\frac{1}{2}$ " for the horizontal range, cropped to $\frac{3}{16}$ " long for the vertical range.

The capacitors are in insulated seamless aluminium cases, and sealed with a synthetic rubber bung.


Cap. Tolerance. The standard tolerance of all capacitors is —20% + 100% of the rated capacitance.

Leakage Current. CE.2-7 may be determined from the following: $1 (\mu A) = 0.1 C.V. + 10$ at applied working voltage and at 20°C. CE.8-9 may be determined from: $0.2 C.V. + 20$ at applied working voltage and at 20°C.

THE TELEGRAPH CONDENSER CO. LTD.

Electronics Division · NORTH ACTON · LONDON · W.3 · Tel. ACOrn 0061 · Telex: 261383

also at CHESSINGTON, SURREY and BATHGATE, SCOTLAND



TECHNICAL TOPICS for the RADIO AMATEUR

By J. Pat Hawker, G3VA

238 circuits and diagrams with associated text, from the very popular R S G B Bulletin series "Technical Topics", have been collated into this 104-page book. Subjects range from fault-finding and accessories to transmitters. Price 10/- (by post 10/8)

R S G B AMATEUR RADIO LOG BOOK

A new R S G B publication for recording radio contacts, based on the earlier Webb's Radio Log Book. 10 x 8in. Trade enquiries invited. Price 6/6 (by post 7/-)

Available from leading booksellers or direct from the Radio Society.

Details of membership of the Radio Society of Great Britain, together with a complimentary copy of the R S G B Bulletin, may be obtained from:

RADIO SOCIETY OF GREAT BRITAIN
Dept. PW, 28 Little Russell St., London, W.C.1.

RETURN - OF - POST

ON CASH OR C.O.D. ORDERS

● GARRARD GRAMOPHONE EQUIPMENT

(Illustrated list sent free)

RECORD CHANGERS	Cash		Credit Terms		Total Credit
	Price	Deposit	Monthly Payments		
Model 50 (GCS Mono PU)	£9.19.6	£2.10.6	12 of 14/6		£11. 4.6
Model 1000 (GCS Mono PU)	£8. 9.6	£2. 2.6	12 of 12/8		£9.14.6
Model 3000 (9TAHC Stereo/Mono PU)	£12.15.0	£3. 4.6	12 of 18/-		£14. 0.0
AT50 (GCS Mono PU)	£12.19.6	£3. 5.6	12 of 18/3		£14. 4.6
A70 (Deram PU)	£25.19.6	£6. 5.6	12 of 37/-		£28. 9.6
LAB80 (Deram PU)	£31.19.0	£8. 0.0	12 of 44/4		£34.19.0

SINGLE RECORD PLAYERS

SP25 (GCS Mono PU)	£12.15.0	£3. 4.0	12 of 18/-		£14. 0.0
SP25 (Deram PU)	£16.10.0	£4. 5.0	12 of 22/8		£18. 0.0

★ **IMPORTANT**—When ordering units with the Decca Deram Pick-Up, please state whether Stereo or Mono required.

● MULLARD AMPLIFIER KITS

We stock many of the components for the Mullard 510 and other designs as described in the Mullard Manual for Audio Circuits. We can supply this publication for 9/6 post free. *Detailed list sent free on request.*

● LATEST TEST METERS

All the latest models from current production. Illustrated list available.

	Cash Price		Credit Terms		Total Credit
	Deposit	12 monthly Payments			
AVO 8, Mk. 3	£25 5.0	£6 6.6	£15 6		£27.12.6
AVO Multimeter Mk. 4	£9.10.0	£2. 8.0	13.11		£10.15.0
Taylor Model 33B	£25.10.0	£6. 7.6	£15.10		£27.17.6
Taylor Model 127A	£10.10.0	£2.13.0	15. 2		£11.15.0
TMK Model 500	£3.19.6	£2. 5.8	13. 3		£10. 4.6

● MARTIN AUDIO KITS

Complete transistorised Hi-Fi Pre-Amplifier and Main Amplifier comprising Unit 1, (Five-way input selector). Unit 4 (Pre-Amp. with volume, bass and treble controls). Unit 7 (10 watt Main Amplifier, 15 ohm output), Unit 8 (Power Unit) and smart plastic Enclosure. All units are assembled and tested and the constructor has only to link the various units together. Full instructions supplied. Cash Price £15.8.0. Credit terms. Deposit £3.17.0 and 12 monthly payments of £1.1.9. Total Credit Price £16.18.0. Stereo and other Mono Units available. Full list free on request.

● MARTIN FM TUNER KIT

Transistorised FM Tuner Kit for use with the above Martin Audio Kit and most other Amplifiers. Supplied ready assembled in unit form and tested. The constructor has only to link together and mount the units. Full instructions supplied. Cash Price £12.17.8. Credit terms. Deposit £3.4.6 and 12 monthly payments of 18/2 Total Credit Price £14.2.6.

All Cash and COD orders are dealt with on day of receipt. Credit orders are subject to only the minimum of delay.

WATTS RADIO (Mail Order) LTD


54 CHURCH STREET, WEYBRIDGE, SURREY

Telephone: Weybridge 47656
Please note: Postal business only from this address.

of the arrangements shown the input side is optional. For instance in 3 the input may be either the link or at terminal D. This is so in a number of other instances.


Conclusion

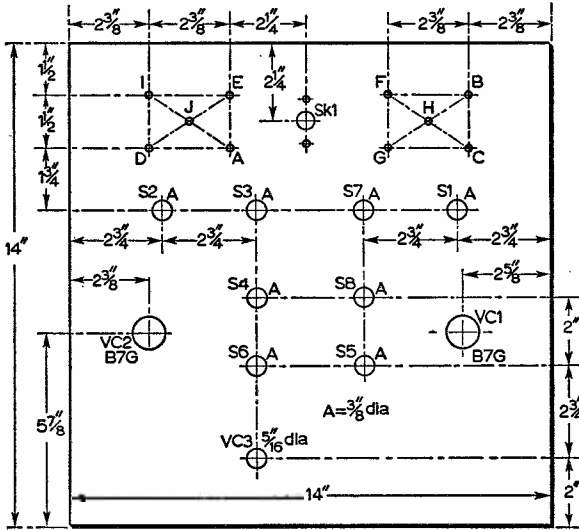A number of antenna have been successfully loaded up. These include dipoles and odd lengths of wire, also some very unlikely ones have been used with marked success. American stations have been



Above—Front panel drilling diagram. Front view.

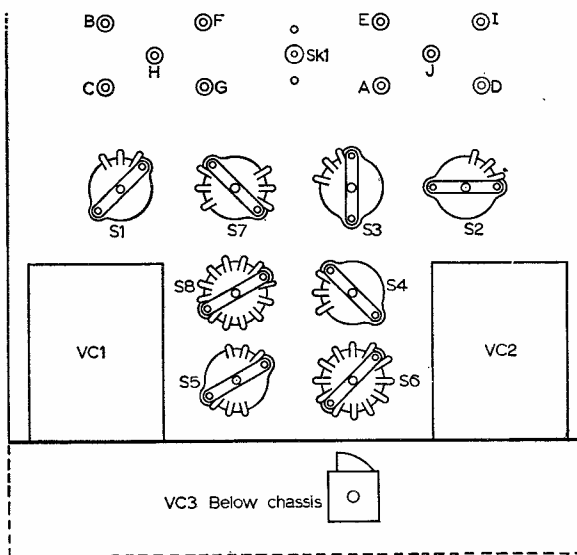Below—Orientation of switches and terminal identification on front panel. Rear view.



worked using the garden fence, and the house guttering also loads up very well on all bands.

There is a strange fascination and also a great satisfaction in plugging in all sorts of things into the unit and watching the s.w.r. go down to 1:1 indicating a near perfect match. Originally the unit was designed to present 75Ω to the transmitter and receiver regardless of the type of antenna used.

The 124 page guide every Motorist needs



GETTING THE BEST FROM YOUR CAR. Step-by-step guide to mechanical overhauls ★ relining brakes ★ simple engine tuning ★ easy starting ★ most-from-the-gallon maintenance ★ basic tool-kit.

PRESERVATION KNOW-HOW. Undersealing — checking corrosion — repairing bodywork — easy stain-removing — inexpensive interior draught-proofing — 10 routine tips for cleaning chrome and paintwork.

DRIVING TECHNIQUES. Tips on safer motoring under all road and weather conditions — the art of reversing — split-second action on mechanical failure — looking for possible dangers ahead.


BEGINNER'S GUIDE TO THE ENGINE. A simple explanation of the functions and operation of the cooling and lubrication systems, carburettor, gearbox, etc.

BUDGET HOLIDAYS. Packed with advice on pre-holiday arrangements—preparing the car — living under canvas — towing a caravan.

BUYING OR SELLING A CAR. How to (a) get value for money; (b) get the best price for your car — tips on running-in.

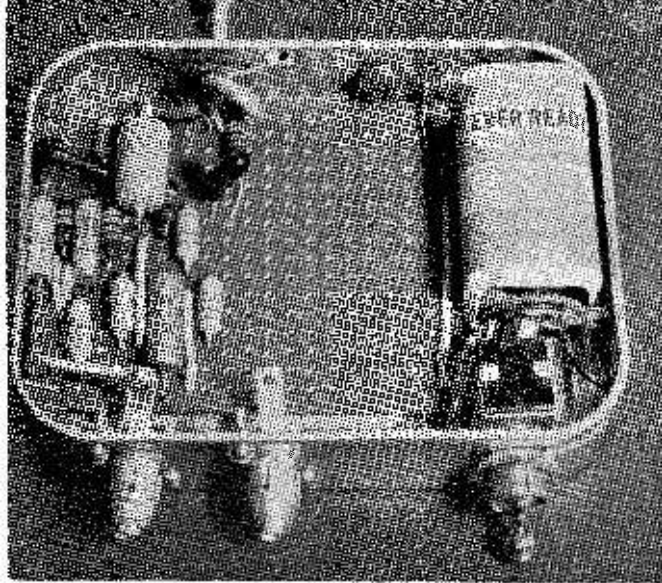REVIEW OF ACCESSORIES. Clear-view and rear-view products ★ anti-theft devices ★ safety belts ★ interior comfort ★ brake boosters ★ roof racks ★ exhaust equipment — auxiliary lighting.





MONO OR STEREO

PICKUP BOOSTER

GORDON J. KING

THE sensitivity of a hi-fi amplifier is expressed as the minimum input signal required to cause the amplifier to deliver its rated output power. The sensitivity often differs between the various signal inputs. For example, the RADIO or AUXILIARY input may demand a signal of 200mV or so, while the GRAM input may need only a few millivolts for full drive.

Many amplifiers, of course, have two pickup inputs, one for "magnetic" and the other for "piezo" (i.e., crystal or ceramic). The magnetic sensitivity is generally higher than the piezo because the signal voltage from a piezo pickup is normally well above that from a good magnetic cartridge.

Pickup output is given in terms of root-mean-square (rms) volts for a certain stylus velocity. A typical specification is 1mV/cm/sec. This means that for each cm/sec of stylus velocity the output is 1mV. As the velocity imparted from the groove to the stylus is continuously changing, so also is the output voltage—to the pattern of the audio signal.

Broadly speaking, the amplifier's sensitivity voltage should be about five times the V/cm/sec output of the pickup. Thus, to cater properly for a pickup of the above specification, the amplifier should have a sensitivity of 5mV. It rarely happens, of course, that the amplifier's sensitivity exactly matches the signal voltage in this way. Often the signal voltage is *above* the input sensitivity of the amplifier.

This is fair enough, for a preamplifier can usually cater for a signal a number of times above its sensitivity voltage before overloading starts to cause significant trouble. This has to be so to handle the dynamic range of music.

When the signal voltage is far above the amplifier's sensitivity voltage, there is not a great deal of trouble involved in attenuating the signal prior to its application to the input. All that is generally required here is a simple resistive attenuator to match the source and amplifier impedances.

The biggest problem is when the signal voltage is considerably *below* the sensitivity voltage of the amplifier input. Say, for example, that we have a magnetic pickup with an output of 5mV/cm/sec, and that the sensitivity of the amplifier is 100mV. For full drive conditions the amplifier sensitivity should be around 25mV so the effect of connecting this pickup to the 100mV input would be a serious lack of drive.

Actually, some sort of reproduction would be possible by turning the amplifier's gain (volume) control full on, but even then full power would not be delivered by the amplifier, and the signal/noise ratio would be bad.

The problem would be resolved either by using a pickup with an output of about 20mV/cm/sec, or by using a booster between the pickup and the amplifier. This article describes such a booster, which can have one or two channels for mono or stereo pickups.


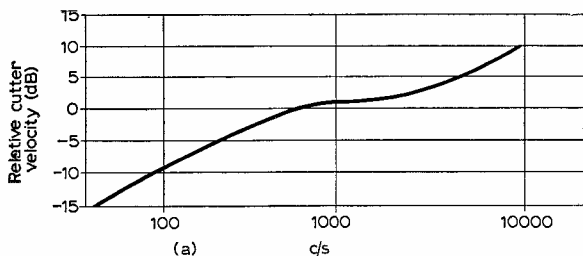


Fig. 1: Standard recording (a) and replay (b) characteristics.

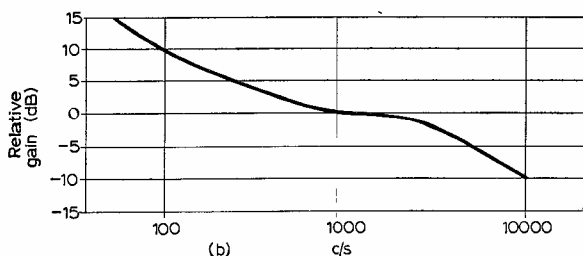

Equalisation

The majority of amplifiers that will be used in conjunction with this booster will possess an *equalised* pickup input circuit. It will be understood, of course, that all magnetic pickups require an equalising circuit because the output voltage from this kind of pickup rises approximately at the rate of 6dB per octave, as shown in Fig. 1(a). Actually here is shown the relative velocity of the cutter stylus over the frequency spectrum. On playing back with a magnetic pickup, therefore, the signal output follows a similar curve.

If nothing is done about this at the amplifier the reproduction sadly lacks bass, and treble has predominance. Pickup equalisation simply means that the pickup channel of the playback amplifier should have a gain/frequency response which is the reciprocal of that of the pickup output. This is shown in Fig. 1(b). The curves in Fig. 1 are in reality associated with the recording characteristics of the disc. These differ from the basic 6dB/octave characteristic

in that at about 1,000 c/s the output rise is checked and controlled treble lift is applied (a) as a means of improving the signal/noise performance of the reproducing system.

Crystal Pickups

Now, how about piezo or crystal pickups? Well, the output from these is not specifically affected by frequency. That is, when they are loaded to a high impedance of about 2M Ω . The output then is proportional to the level of the recording.

In practice, this means that the output from the pickup is substantially "flat" over the normally recorded frequency spectrum. Such a pickup, then, can be connected direct to an *unequalised* input, and this, indeed, is necessary to preserve correct balance over the spectrum. If, for instance, a crystal pickup were connected to a high impedance *equalised* input, there would be far too much bass and too little treble.

However, an output very similar to that from a magnetic pickup is produced by a crystal pickup when it is connected across a relatively low impedance input circuit. This output, incidentally, is often referred to as "velocity", as the output rises with rise in velocity of the stylus.

Now, on some amplifiers the crystal pickup input is of an impedance below that required for true "piezo" pickup action, meaning that the amplifier incorporates some kind of equalisation on the piezo input as well as on the magnetic. Other amplifiers, on the other hand, utilise an "unequalised" crystal input, loaded to a high value of impedance or resistance.

Moreover, the voltage from a "high-loaded" crystal pickup is considerably above that from the same pickup loaded to a relatively low value for velocity operation. To reconcile all these factors in terms of a pickup booster is nigh impossible without a great deal of complexity, which is what the author set out to avoid.

To provide all facilities would be little different from designing an entirely new preamplifier or control unit to cater for a pickup with an output below that of the sensitivity voltage of the existing preamplifier or control unit.

Compromise

Nevertheless, a reasonable compromise has been created in the booster unit now to be described. The circuit of one channel of this is given in Fig. 2. For stereo operation, of course, a pair of identical amplifiers are necessary. The circuit board and unit design are such that two channels can easily be accommodated, as we shall see.

There is nothing particularly new about the circuit which employs a pair of OC75 transistors in common emitter mode and which is used in all kinds of audio applications. The two transistors are directly coupled. This means that the collector of Tr2 is in d.c. connection with the base of Tr2. The avoidance of a coupling capacitor here improves the low-frequency response and the phase characteristics.

The pickup signal is applied direct to the base of the first transistor, via the electrolytic capacitor C1. Appearing across the collector load R4 is thus the amplified signal which is fed to the base of Tr2. Again, further amplification takes place and the

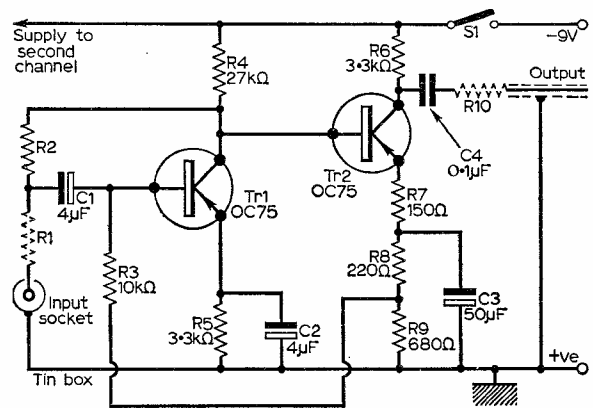


Fig. 2: Circuit of mono booster.

processed signal appears across Tr2 collector load R6. The signal is then passed out of the unit, via C4, and applied to the input of the amplifier which is insufficiently sensitive for direct connection of the pickup in use.

Now, there are several interesting aspects of the booster. Firstly, it arranges the signal from either a magnetic or piezo pickup so that at the output it appears as of "velocity" characteristics. This means that the booster must normally be connected to an *equalised* pickup input of the parent amplifier.

Secondly, the overall gain is adjustable by the negative feedback applied from the collector back to the base of Tr1, via R2. The small value of this resistor, the greater the feedback and the smaller the overall gain.

Thirdly, the first transistor is arranged for a current input from either a magnetic or a crystal pickup. Transistors, of course, are current-operated devices, so the more current that can be injected efficiently into their emitter/base junction the better the noise performance.

Pickup Coupling

Fig. 2 shows a resistor R1 connected in series with the pickup signal. Actually, this resistor is used only with a magnetic pickup. Its value is arranged in conjunction with the inductance of the pickup to provide high-frequency roll-off. In effect, the resistor tends to endow the input towards constant-current operation. The greater the inductance of the pickup, the greater should be the value of R1. For the best results it may be necessary to experiment a little here with resistors from about 2.7k to 10k Ω .

When a piezo pickup is used (either a crystal or ceramic) the input is coupled direct to C1, and R1 is deleted. The source impedance of a piezo pickup is capacitive, and because of this the signal current into the emitter/base junction of the first transistor increases with increase in frequency. It is this effect that provides the basic "velocity" characteristics. Moreover, it ensures that all the available signal current from the pickup passes into the emitter/base junction.

The signal passing into the first transistor does not match perfectly the requirements of equalisation, but it is fairly close and slight modifications to the settings of the amplifier's tone controls should provide the final tailoring to the response.

The frequency response is also affected to some extent by the value of R2, for since this applies the feedback via C1 there is a tendency towards a rising bass response due to the reducing feedback at the lower frequencies. This is countered, however, by the rising degenerative feedback across the emitter resistor R4, for here C2 progressively has less signal bypassing effect towards the lower frequencies. A further, smaller amount of correction in this respect is given by C3 in Tr2 emitter circuit.

A degree of feedback is purposely introduced into Tr2 by the unbypassed emitter resistor R7. Apart from reducing the stage gain, the action of this increases the impedance at the bases of Tr2 and thus provides improved signal transference from Tr1 to Tr2 due to the resulting improvement in matching.

With the booster and pickup connected to the parent amplifier, the value of R2 should be adjusted to produce the correct output with the amplifier's volume control about half on. Of course, any required gain conditions can be achieved by altering the value of R2. There is rarely any possibility of the booster being overloaded by a too strong pickup signal, for if the pickup signal is that strong then a booster would not be needed anyway!

Booster Coupling

It is possible, however, to overload a low-level input on the parent amplifier by the booster delivering too strong a signal, but—as already mentioned—this can be corrected by decreasing the value of R2. This can be set initially at 10kΩ.

Fig. 2 shows a resistor R10 in series with the output signal. This may not be required, depending on the characteristics of the parent amplifier's equalised pickup circuit. Sometimes the equalisation is sensitive to load impedance (or load inductance). This may then make it necessary to put a resistor in R10 position. This usually requires to be about 47kΩ when the equalised magnetic pickup of the amplifier is used.

The booster runs on a 9-volt PP4 or similar type of battery, and the current consumption is approximately 2mA per channel (4mA when a pair of stereo channels are adopted).

The idea has been to produce a booster that is completely self-contained with its own internal battery. A piece of Veroboard was prepared to take both channels and to fit snugly into a 2-oz. tobacco tin, which makes an excellent housing for transistor devices of this nature.

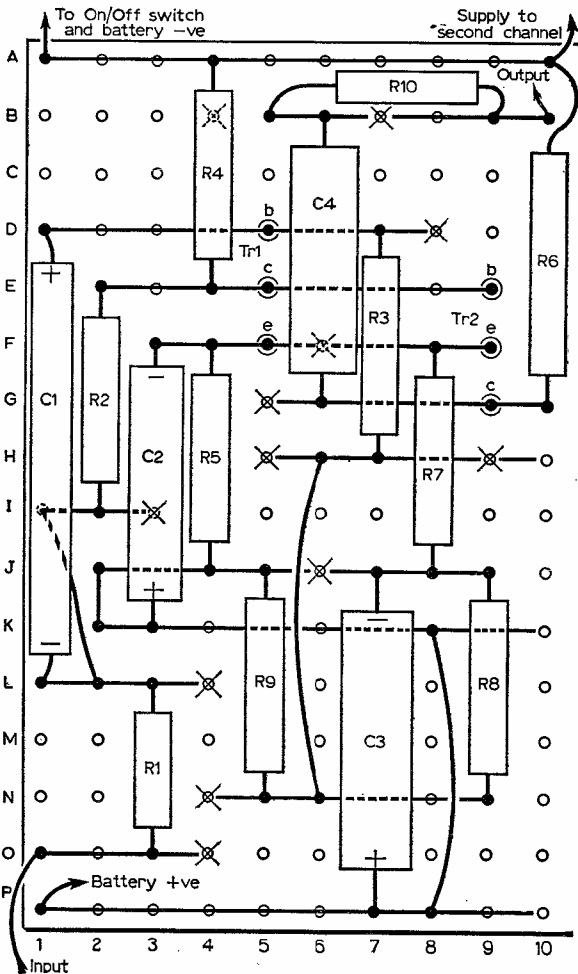


Fig. 3 (left): Layout of components for one channel (Channel A) on Veroboard.

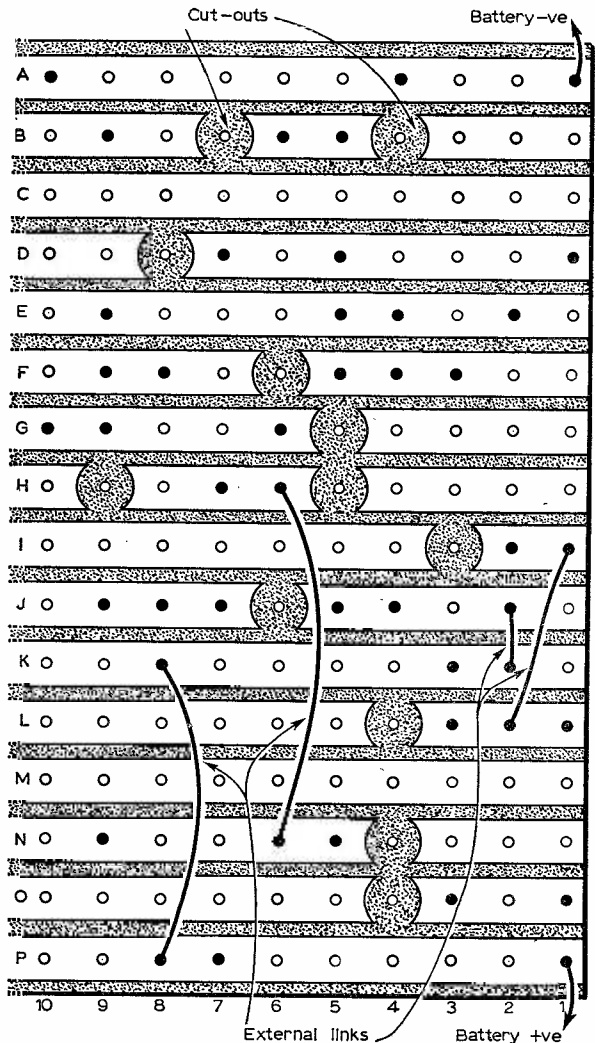


Fig. 4 (right): Underside of Channel A of Veroboard, showing the pattern of the circuit.

Veroboard Circuit

Vero Electronics Limited make available through the retail trade four standard sizes of Veroboard, and the piece chosen was 16-way board of approximately 3½ in. long. About half an inch was cut from the length of the board, giving 21 holes along each metal strip. Thus, the total number of holes in the board is 16 times 21, or 336.

Each amplifier section is accommodated along the length of ten holes over the 16 strips. Thus, the length is divided by 16 holes not employed for either section.

The layout of one amplifier section of the board is given in Fig. 3. The 16 strips are marked "A" to "P" inclusive, while the lines of holes on the other axis are numbered 1 to 10 inclusive. By this means each hole in the board can be identified. The line of holes separating the two sections is marked "O" and then, of course, the numbering starts again to 10 to cater for the other amplifier section, both sections being identical.

The circuit on Veroboard is created by using the metallised strips as the conductors. Thus it is necessary to break some of the strips and interconnect others with external wire links to form the required circuit. A special tool is available for cutting the strips cleanly and without tearing the metallic foil from the insulated laminate.

The reverse of the Veroboard with the holes and strips identified as in Fig. 3 is shown in Fig. 4. This reveals exactly how one section of the board must be processed. Here is shown the foil cut-outs and the external links. The Veroboard should be processed exactly in this way for one section of 10 holes by 16 strips for a single-channel mono amplifier or for two sections of 10 holes by 16 strips for a two-channel stereo amplifier.

It will be seen that there are three strips common to both sections, they are two strips for battery plus and one strip for battery negative. These strips are not severed at the line of holes corresponding to "O" in Figs. 3 and 4.

The "X" marks on the component layout plan in Fig. 3 indicate the foil cut-outs on the reverse side of the board, and these, of course, correspond with the cut-outs indicated on the strip side of the board in Fig. 4.

★ components list

Resistors:

R1, R2 see text
R3 10kΩ
R4 27kΩ
R5 3.3kΩ
R6 3.3kΩ
R7 150Ω
R8 220Ω
R9 680Ω

Capacitors:

C1 4μF electrolytic 6V
C2 4μF electrolytic 6V
C3 50μF electrolytic 6V
C4 0.1μF, 160B or less.

Transistors

Tr1 OC75
Tr2 OC75

All ½W or ¼W high stability type.

Other Parts:

S1—SPST toggle on-off switch.* Veroboard—see text.* One phone socket. One 2-oz. tobacco tin.* One rubber grommet. One 9V battery (PP4 or equivalent).* Length of screened signal output cable. Wire, cork, etc.

Note: The above list is for the mono version; for the stereo version, two of each part mentioned will be required, except for those marked.*

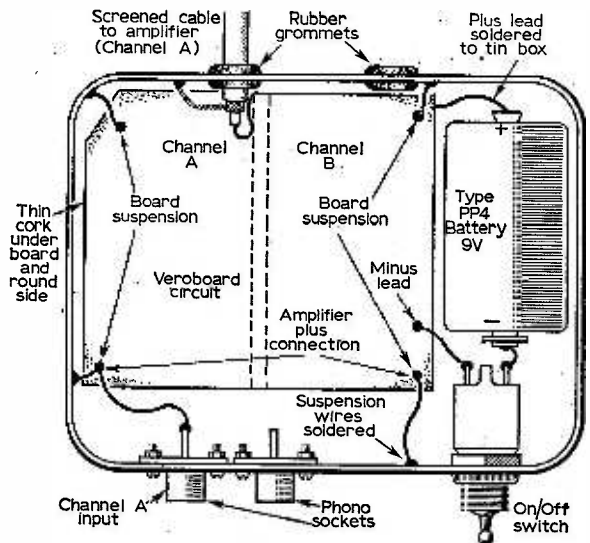


Fig. 5: The arrangement of the Veroboard and other components in the 2-oz. tobacco tin.

The full lines (dotted underneath the components) in Fig. 3 show how the circuit is formed from component to component, and a little study will reveal that this physical circuit follows exactly the theoretical circuit in Fig. 2.

Assembling in Box

Fig. 5 shows how the Veroboard and the remaining components are mounted in the 2-oz. tobacco tin. Phono sockets are adopted for channel A and channel B signal inputs, while screened leads—taken out of the tin through rubber grommets—transfer the boosted signals to the equalised pickup sockets of the parent amplifier.

The positive battery clip wire is soldered direct to the inside of the tin, beneath the Veroboard. The tin box is made common with the supply positive line, this being accomplished by the connection of short lengths of wire from strip "P" on the board to the side of the tin box. Two connections are made here, one to hole P2 and the other to hole P9 on channel B section of the board.


These wires also serve to suspend the Veroboard in the tin box, and balancing suspension wires are soldered on the other side of the board, to the opposite side of the tin box at holes C2 (channel A section) and C9 (channel B section). The strips associated with these two holes are not concerned with the circuit and are thus isolated.

To avoid the circuit side of the Veroboard and the channel A edge from shorting to the tin box, a thin piece of cork is glued to the inside base of the tin, of a size equal to that of the Veroboard, and to the left-hand edge of the tin and corner.

Note also that the outer conductor (braiding) of the signal output leads is soldered to the side of the tin box, the inner conductor being terminated at hole B10. If R10 is not required a wire link is connected between holes B5 and B9.

The "earthy" side of the phono sockets is automatically connected to the tin box and the "live" side of each channel is connected to the strip corresponding to hole O1.

SIMPLIFIED CABINET DESIGN

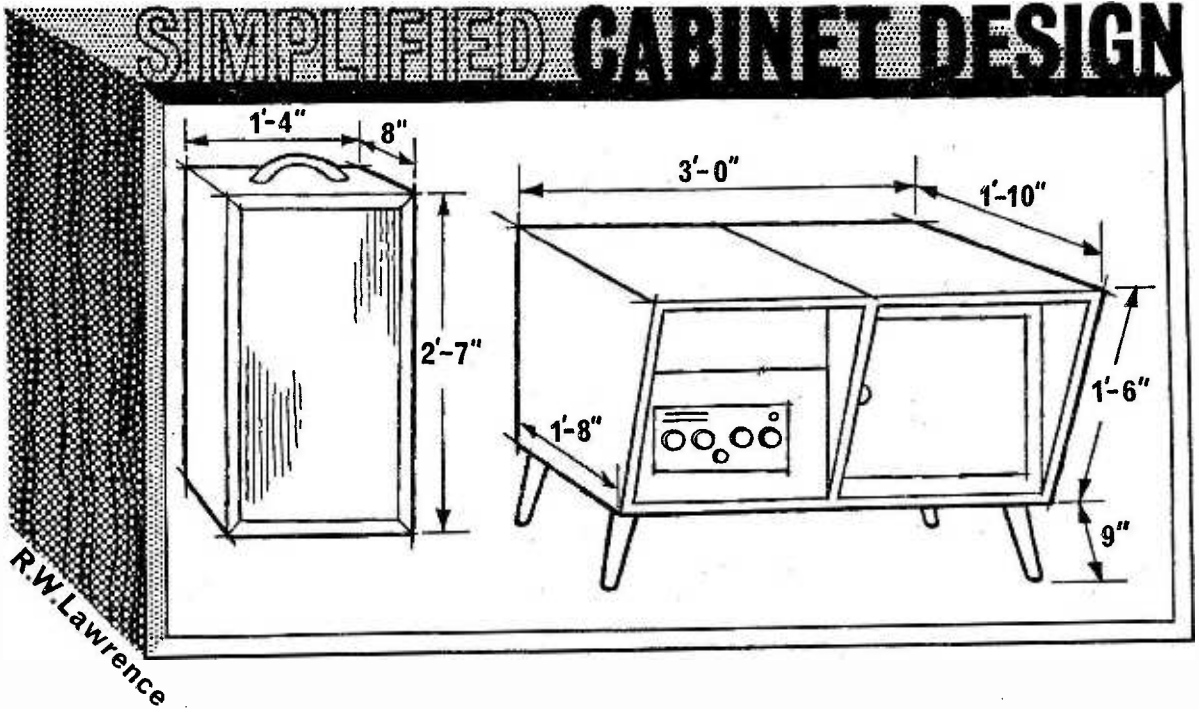

I HAVE been building radios and electronic equipment for a good number of years now and I find, as I am sure a lot of readers do, that the most difficult stage of construction is the cabinet.

I pride myself that I am "mechanically minded" but when it comes to working with wood my skill is very limited indeed. Evening classes on the various arts of woodworking were out of the question (I work shifts). "D.I.Y." books are very good but I found very little of value even in the excellent shelves of the local library. Space in my "den" is very limited, as also is cash for the purchase of expensive carpentry tools.

My friends were envious of my first transistor radio because it worked so well but were amused at the cabinet which almost housed it. The stabilised power pack which has worked so perfectly right from the initial first "plug in", remains unmoved on the bench: the cabinet will not stand the strain of being lifted. Without "plastic wood" and modern adhesives some of my earlier attempts would, I fear, not even be dustproof.

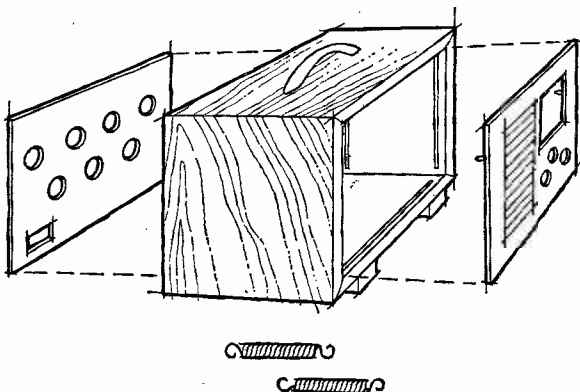


Fig. 1: General view of the radio cabinet as described in the text.

However, all that is now in the dark past, I am pleased to say. I have reorganised my thinking and my methods to produce some examples of cabinet building which has astounded me no less than my friends.

There is, of course, no magic formula, just an application of common sense and the judicial use of a few of the products of the wonderful age in which we live.

I began by reorganising my thinking thus:

1. Keep design strictly simple, this is the modern trend anyway.
2. Be meticulous with your measurements at all stages of construction.
3. Use only new timber. (I found that by careful buying, the extra expense was not large and the results were very much easier to obtain.)

My altered methods consisted of:

1. Using no conventional joints, i.e. dovetail, tenon, butt or mitres. (This was of course my main point.)
2. Keep tools to an absolute minimum, but choose them with care. My basic tool kit consists of: One good quality rip saw, not too coarse and regularly sharpened; one hammer; one fretsaw and good supply of blades; one wheel brace or electric drill with a few twist drills say from $\frac{1}{8}$ in. down to $\frac{1}{16}$ in. and a "rosebud" type countersink; screwdriver and a good selection of screws. Sandpaper or sanding discs; sharp knife; good ruler and metal set square; panel pins and nails.

The main material used in all my cabinets is "blockboard". This is a material consisting of blocks of softwood sandwiched between two layers of plywood and can be obtained usually in three thicknesses, $\frac{1}{2}$ in., $\frac{3}{4}$ in. and 1in. It is easy to saw, never splits when nailed or screwed, extremely strong and has a very smooth finish. If, when buying timber, the

sizes of the pieces required are accurately known, then you may find, as I did, that the shopkeeper will saw them for you and save a lot of effort and sawdust on your part.

Let us consider the construction of a radio cabinet of average size to house a 3 plus 1 set with a 5in. speaker and covering long and medium wave, in fact a typical constructor's piece often discussed in the pages of this magazine. The cabinet would need to be about 18in. by 12in. by 8in.

Saw four pieces accurately of blockboard, two 18in. by 8in. and two 12in. by 8in. and nail them together with long nails (Fig. 1).

Countersink all nails slightly and fill the holes with plastic wood or putty. Sandpaper the edges to make them level (a high finish is not necessary) and check that all angles are true with the set square.


From a length of $\frac{1}{2}$ in. by $\frac{1}{2}$ in. softwood now saw four pieces 16in. long and four pieces 10in. long. These are panel pinned to the cabinet after carefully drawing a line 1in. on both front and rear of the four sides of the inside of the inside of the rectangle formed.

Two pieces of softwood 6in. by 2in. by 1in. are now cut and screwed, after countersinking, on to the bottom of the cabinet about 1in. This raises the cabinet up and a piece of felt glued on to these two pieces make them virtually scratchproof to furniture.


The two sides and top of the cabinet are now covered with "Con-tact" self adhesive plastic finish to your own colour requirements. This very attractive form of finish can be bought in a variety of colours and either in gloss or matt finish.

The back and front are of hardboard and should fit easily in to rest against the four wooden strips inside the cabinet. The back is "vented" to allow for heat dissipation and suitably drilled for aerial, earth, mains lead, etc. The front will of course be cut to suit the position of dial, knobs, speaker and so on and for this the fret saw is used. The front is finally to be covered with "Con-tact" adhesive but before this is done, a word about how the front and back are held in place. I decided against screwing or nailing for two reasons, as I wished to be able to dismantle any piece of equipment easily and quickly for the purpose of repairs or modifications and, for the fact that hardboard does not take easily to being drilled near the edges, I decided to use springs. The type of springs used can be obtained very easily and cheaply from most hardware shops or even from car accessory shops. In the case of our example, a fairly "soft" spring, 4in. long (when closed) will do nicely. Two are usually sufficient, and placed near to the edges of the cabinet can, as a rule, be kept well clear of the radio chassis. Make two small holes in the front piece and thread a loop of stiff tinned copper wire through as shown in Fig. 1. A groove cut with the knife between the two holes allows the wire to lie flat under its final covering of plastic. The wire is now twisted tightly and soldered, it will now be self supporting in a horizontal position which is ideal for our purpose. The fixing for the spring on the back can be one of the holes which were cut for ventilation.

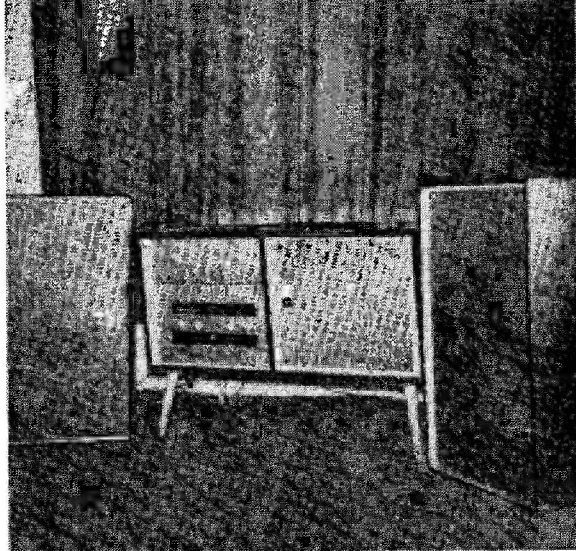The front panel can now be covered with the plastic adhesive (preferably in a contrasting colour) and with the knife cut out the shapes already in the hardboard. If two diagonal cuts are made in each of




The finished stereogram cabinet.

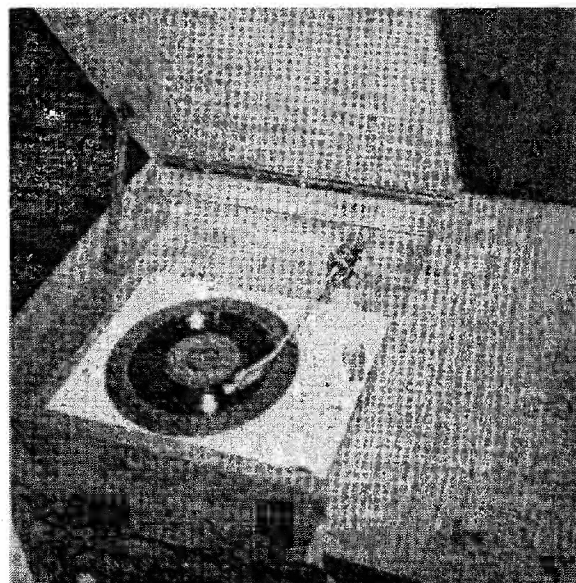

Inside the record player compartment.

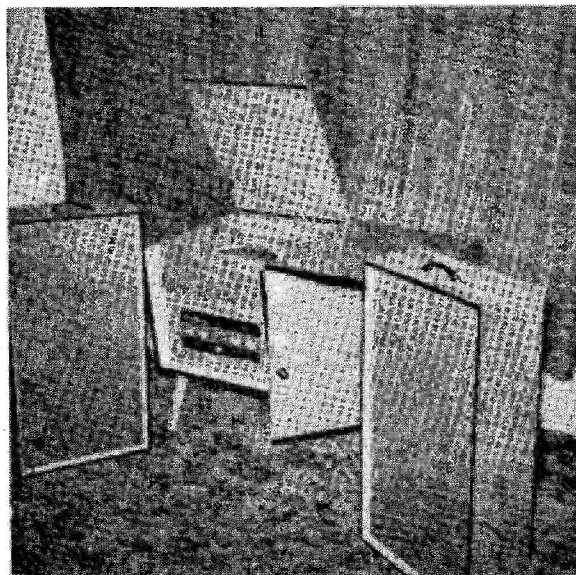Another view of the stereogram cabinet with speaker units.



SIMPLIFIED CABINET DESIGN

the shapes it will be found that the edges can be turned back very neatly.

Attention can now be turned to the front edge of the cabinet which, up to now, has been left unfinished. This edge I cover very carefully with glossy black or black and gold plastic strip. This can be obtained in quarter inch, half inch or three quarter inch widths and is flat on the back and rounded on the front. It is usually fastened with a good quality contact adhesive and if desired can be mitred at each corner. To complete the job, a suitable handle can now be screwed on top for the purpose of making the set "portable". All that remains now is for the radio to be housed in its new and shiny cabinet, the springs to be fastened and the knobs pushed home.

It needs very little imagination to see that almost any type of cabinet can be made in this manner and as there is no paint or varnish involved, no awkward "waiting period" between stages. Blockboard is obtainable in all sizes and I have seen sheets 10ft. square. It has little or no grain to worry about and therefore can be safely sawn and used in any direction. Radio chassis can be screwed directly to it and it does not appear to warp with heat.

After a few trial runs on cabinets of this sort I attempted my most ambitious piece a stereogram. Here as in the other designs, the shape was kept as simple as possible and I carefully measured each piece to be purchased. The pieces were cut for me by the shopkeeper and this ensured a right angle cut on each edge (he used a circular saw). It is essential that the edges are accurately sawn if only nails and screws are to be used. (See heading, page 40.)

The main construction proceeded very quickly and was remarkably easy, long screws were used and each screw hole was drilled and countersunk to give maximum strength to the whole assembly. Screw

and nail heads were hidden by plastic wood and sanded flat as were any imperfection in the sawn edges of the blockboard.

The door for the record cabinet (right hand side) was hung on two brass hinges and is held closed by a magnetic catch. The door itself is blockboard and is slightly larger than the opening, when closed it is "proud" of the door jamb and gives a very attractive appearance as well as being easy to make. The front and back are held in by springs in exactly the same way as previously described.

The two speaker cabinets are in blockboard of two thicknesses, three quarter inch for the baffles and half inch for the sides. Again, screws and nails were used throughout. The inside of each is lined with thick felt (carpet underlay) and the back is quarter inch hardboard panel pinned and stuck with contact adhesive. Connection to each speaker is by standard jack plug. The finished product is covered, as explained, in glossy "Con-tact".

The equipment was bought on a strict budget and was selected for a maximum outlay of under £40. This I just managed to do by being fortunate enough to purchase the speakers second hand. Here is a brief description of the rest of the equipment used. Amplifier, "Heathkit" S33 Stereo/Mono. Turntable, Collaro type RP594 but the original arm has been replaced by one built to my own design by an engineer friend. It has jewelled bearings and a tracking weight of 2 to 8 grammes. Tracking error is negligible and adjustment is possible in all directions to correct stylus error. The speaker "line up" consists of one 10in. and one 5in. in each column capacitor connected. A jack is fitted to allow for headphone listening and the speakers are switched out when this is used.

Results are much better than most commercial models of the £80 to £100 range that I have heard and compares favourably with a few very expensive models. ■

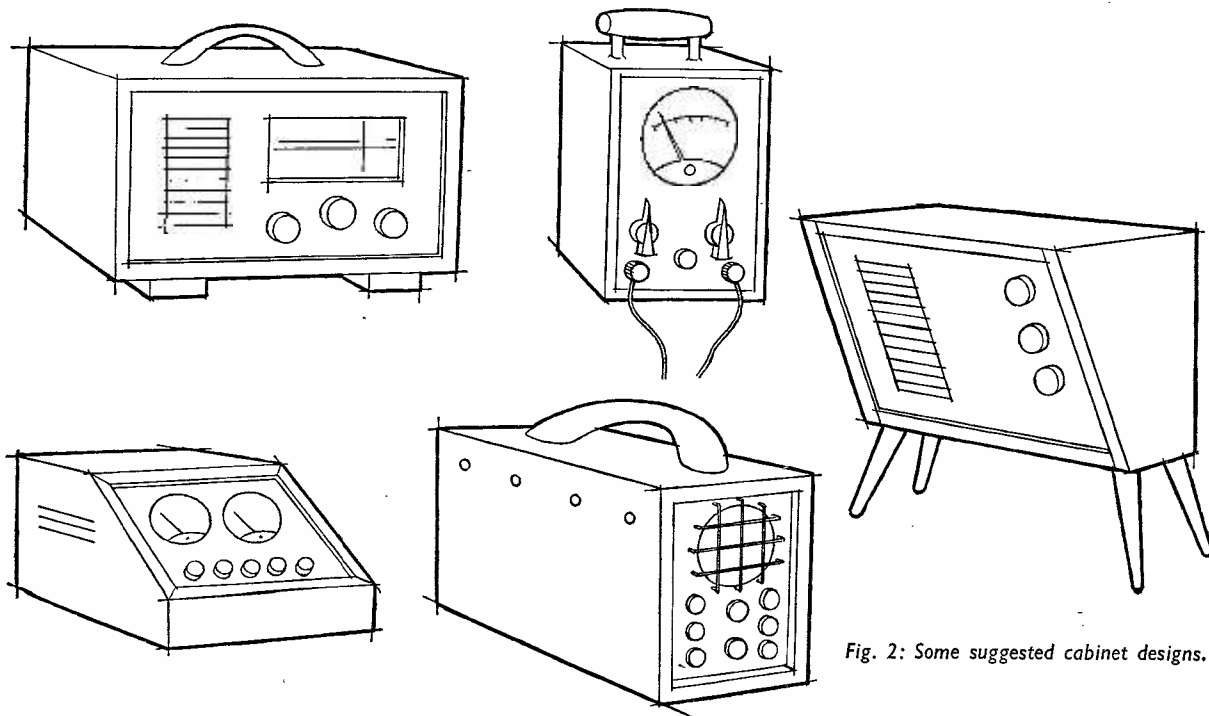


Fig. 2: Some suggested cabinet designs.

MICRO MEGA

TO allow the use of manageable figures in radio and electronics, the basic units are often subdivided or multiplied, providing such terms as megacycle (one million cycles) and millivolt (one thousandth part of a volt).

While the terminology may be quickly recognised, complications may result when the beginner is faced with calculations involving values other than the basic or quoted units, and errors can quite easily be made by dropping or adding the odd nought.

The use of mathematical indices provides a simple and, once properly understood, infallible solution to this problem. It also allows any particular calculation to be carried out from *one* basic formula, irrespective of what pre-fixed values are employed.

INDICES

Consider the expression a^x ; a may be any number and x , the index, may be any number. Basically, it means that a is multiplied by itself x times. For example, 4^3 (four cubed) is $4 \times 4 \times 4 = 64$.

The index x need not be a whole number. If it is a simple fraction a root is indicated, e.g. $4^{\frac{1}{2}}$ is $\sqrt[2]{4}$ (the square root of four) = 2. Extending this a little, $4^{\frac{3}{2}}$ (or $4^{1.5}$) is $\sqrt[2]{4 \times 4 \times 4} = \sqrt[2]{64} = 8$.

Reciprocals are expressed by a negative index; thus—

$$\frac{1}{a^x} = a^{-x} \text{ or } \frac{1}{a^{-x}} = a^x = a^x.$$

Calculations involving indices could not be simpler. In multiplying, the indices are added:

$$a^x \times a^y \times a^z \times \dots = a^{(x+y+z+\dots)}.$$

Note that when dividing or dealing with reciprocals, the signs of the indices must be observed: e.g.—

$$\frac{a^x}{a^y} \times a^z = a^x \times a^{-y} \times a^z = a^{(x-y+z)}$$

The expression $(a^x)^y = a^{xy}$, i.e. the indices in this case are multiplied. For example $(a^x)^2 = a^{2x}$.

Note that $a = a^1$ and *not* a^0 . ($a^0 = 1$, whatever the value of a .) Generally the index is omitted in the expression a^1 , but the 1 must be included when adding the indices.

MULTIPLIERS

In applying multipliers to basic units, multiples of 10 are invariably used; these may be applied directly (as in megacycle) or inversely, by dividing (as in millivolt).

We therefore have the case where $a = 10$ and $a^x = 10^x$. Now 10^2 is 100, $10^3 = 1,000$, $10^4 = 10,000$ and so on. It will be seen that the number of noughts in the resulting number corresponds to the index value.

Similarly $10^{-1} = \frac{1}{10}$, $10^{-2} = \frac{1}{100}$ etc.

It is now apparent that any of the prefixes or multipliers used in electronics can be simply represented by the figure 10 with an index, or 10^x where x is a whole number. The following table gives prefixes commonly used with their corresponding numerical values:

Prefix	Symbol	Multiplier
TERA—	T—	1,000,000,000,000 (10^{12})
GIGA—	G—	1,000,000,000 (10^9)
MEGA—	M—	1,000,000 (10^6)
KILO—	K—	1,000 (10^3)
HECTO—	H—	100 (10^2)
DECA—	DECA	10 (10^1)
deci—	d—	$\frac{1}{10}$ (10^{-1})
centi—	c—	$\frac{1}{100}$ (10^{-2})
milli—	m—	$\frac{1}{1,000}$ (10^{-3})
micro—	μ —	$\frac{1}{1,000,000}$ (10^{-6})
nano	n—	$\frac{1}{1,000,000,000}$ (10^{-9})
micro—micro— or pico—	$\mu\mu$ — p—	$\frac{1}{1,000,000,000,000}$ (10^{-12})

Applying this to actual values, 13Mc/s may be written 13×10^6 c/s, 2mA as 2×10^{-3} A and $8\mu\text{F}$ as 8×10^{-6} F. Going a little further, 300pF may be written as 300×10^{-12} F, but 300 is 3×10^2 and by adding the indices we obtain the value 3×10^{-10} F.

To resolve the result of a calculation in terms of a prefixed unit, just subtract from the index in the answer. Any remainder will normally be incorporated in the value figure. For example

$$4 \times 10^5 \Omega = 400\text{k}\Omega$$

$$3 \times 10^{-11}\text{F} = 30\text{pF}.$$

A decimal may be eliminated or modified by means of a multiplier. Moving the point to the left introduces a positive index corresponding to the number of digits the point is moved. Conversely, moving the point to

—continued on page 49



An explanation of Indices, Multipliers and Roots

by B. L. BURROUGH

Mods for Modulated Light

AFTER reading your article on the Modulated Light Telephone link (Feb., 1966, issue of P.W.) I would like to put forward an idea.

There are certain times when one person in a household may need a bit of peace and quiet and another may want to watch the television. Surely this can be overcome without the use of bothersome wires and equipment by connecting a modulated light transmitter to the sound, together with a switch for normal listening. The receiving unit could be completely transistorised and compact enough to stay unobtrusively on a coffee table. Actual listening would, of course, be by means of an earpiece.

J. Douglas.

Newcastle upon Tyne

★ ★ ★ ★

JUST over two years ago, I carried out similar experiments to those described in the February issue of PRACTICAL WIRELESS.

Although I was only able to obtain a range of up to about 20 yards I would like to offer the following hints to anyone thinking of experimenting in this field.

An ordinary household torch with the minimum of alteration (i.e., breaking the circuit and connecting in the output of the transmitter amplifier), makes an almost ideal transmitter, especially if it is of the type that can be focused. Instead of mirrors (which may be difficult or expensive to obtain) the reflectors from car headlamps, obtainable for a nominal fee from scrap merchants, can be used with great success. For short range experiments, both amplifiers can be simple battery-operated transistor types having an output of about 1W.

B. M. R. Green.

Ripon,
Yorkshire.

U.H.F. and V.H.F. Designs

I ENTHUSIASTICALLY echo the request by S. Peat (P.W. March 1966) for designs on u.h.f. and v.h.f. receivers, though not for the same reasons.

Having built the t.r.f. version he mentions, I feel that the next step is a portable switched band a.m. superhet covering 70—160Mc/s, this covering the amateurs, broadcast and a host of other interesting stations.

How much longer must we put up with the superregenerative hiss?

P. M. Thacker.

Morley,
Yorkshire.

NEWS AND..

IEETE LONDON MEETING

A lecture entitled "Control by Computer" was given by Mr. A. St. Johnston, B.Sc. (Eng.), M.I.E.E., M.I.E.R.E., Joint Managing Director, Elliott-Automation Computers Ltd., to members of the Institution of Electrical and Electronics Technician Engineers and their guests on 7th March in the I.E.E. Lecture Theatre, Savoy Place, London, W.C.2.

The outline of the lecture was that the digital computer is the tool that provides the Auto in automation. The whole technology of computers, not only their electronics, but even more their application, is new.

The power of the computer comes from its quite unique method of operation—the stored programme techniques. The profession of programming is new and offers a completely new career line.

As a control tool, the computer's flexibility holds out a new dimension of "power" in control systems. The ever decreasing size and increasing capability made possible by transistor and microelectric development opens up new fields of application in every walk of life.

1966 PHYSICS EXHIBITION

Mullard Ltd. Educational Service was on stand E.5 at the 1966 Physics Exhibition held at Alexandra Palace, London, from March 28th-31st.

Several experiments designed by the Mullard Educational Service for use in schools, technical colleges and other training establishments were shown. They included a computer demonstration unit, an electronic very high voltage generator, a 1c/s sinewave oscillator, an oscilloscope, a simple timer and a binary adder/subtractor.

NEW LABORATORY PREMISES FOR MULLARD

Many of the 3,000 employees at Mullard Southampton Works—the principal establishment of Associated Semiconductor Manufacturers Ltd., the joint Mullard/GEC manufacturing and development company for Mullard transistors—work in the plant's extensive laboratories.

Two important sections of these laboratories are now moving to new premises on the N.E. outskirts of Southampton. These sections are the reliability and quality laboratories. Both of which form part of the 200-strong team under the technical direction of Mr. L. B. Johnson.

When the move is completed, well over £½ million worth of technical equipment will occupy the 25,000 square feet of space in the new premises.

The West End unit is planned to have a direct link with the new ICT computer at the main factory, which is on Southampton's Millbrook estate. This will enable scientists in the reliability and quality laboratories to feed their problems directly into the new computer.

SELF-ADHESIVE INITIALS

From Convex Ltd., 41 Brecknock Road, London, N.7, come the sets of Myrogram self-adhesive gold coloured plastic initials $\frac{3}{16}$ in. high. These are especially useful for putting that "finishing touch" to front panels of receivers, equipment, etc. The price is 5s. per sheet (26 letters and various ornamental shapes). Further details from the above address.

HEATHKIT CATALOGUES AND BROCHURES

In addition to the distribution of their normal catalogue, which is published quarterly, Daystrom Ltd., Gloucester, now send—to those people interested—special brochures covering the Electronic Instrument field, and the Amateur Radio market. Copies of the latest Heathkit Catalogue may be obtained by writing to Daystrom Ltd., Gloucester.

...COMMENT

ROYAL VISIT TO CABLE SHIP

Her Royal Highness the Princess Margaret Countess of Snowdon and the Earl of Snowdon were the guests of honour at a reception on the Cable and Wireless Ltd.'s cable repair ship CS Cable Enterprise on March 5th, during the Royal Visit to Hong Kong for the British Week.

In the evening, H.R.H. the Princess Margaret and Lord Snowdon attended a charity premiere which included the Cable and Wireless Ltd.'s new 30-minute documentary film, *East-West Island*, which portrays life in Hong Kong and the role of the Company's overseas telecommunications in Hong Kong.


NEW FILTER FOR SHIPS' COMMUNICATIONS

A new magneto-mechanical double sideband filter, trade-named MF 200—0050, was exhibited at the Leipzig Spring Fair last month by VEB Werk für Bauelemente der Nachrichtentechnik 'Carl von Ossietzky' at Teltow in East Germany.

The filter is earmarked for use chiefly in transmitter and receiver units on board ships, and has a medium frequency of 200 kc/s and a 3 dB band width of 500 c/s.

It can be applied both as a high-speed double sideband filter and as an inert carrier frequency filter. A temperature coefficient of 5×10^{-6} degrees Celsius, the manufacturers claim, obviates the use of expensive and space-consuming thermostats.

POCKET RADIO-TELEPHONE TYPE 4B7

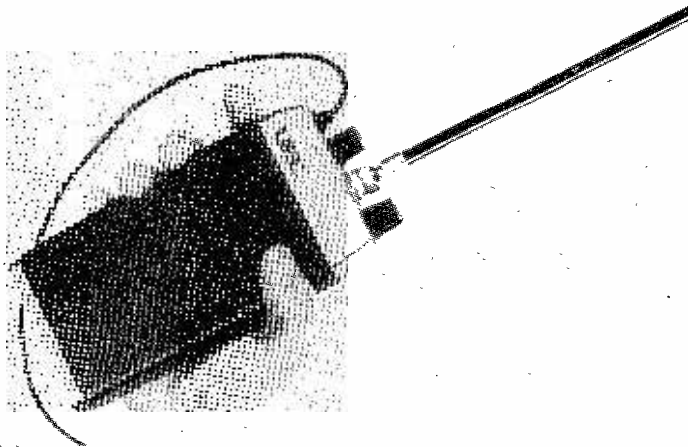

A pocket radio-telephone of only 25 cubic inches and weighing 24 ounces, the *Cub*, is the latest addition to the successful *Vigilant* range of equipment from the Telecommunications Division of Ultra Electronics Limited.

This f.m. two-channel transmitter-receiver provides a minimum of half a watt output power on frequencies between 70 Mc/s and 175 Mc/s. It is designed to operate set-to-set, or in conjunction with a base station. Range is typically one to five miles, dependent on terrain.

The *Cub* is a further extension of the range of portable communications equipment which includes the *Vigilant* walkie-talkie, already in use in large quantities by police, fire services, armed forces and public utility undertakings, and for many commercial applications in Britain and overseas.

Ultra Electronics Limited, Telecommunications Division, Western Avenue, London, W.3.

A Challenge

I REFER to the letter published in the March 1966 issue of *PRACTICAL WIRELESS*. Perhaps few people have noticed one unfortunate fact. In 1935, fifteen pounds represented a fair sum to pay for a radio of sturdy build, excellent cabinet work and a good technical design.

Unfortunately, fifteen pounds now is only equivalent of about three pounds ten then. No one, manufacturer or home constructor, can give you three bands, three watts, an 8in. speaker and a good solid wood cabinet for three pounds ten!

However, give the constructor his chance with sixty pounds, he might produce a valve receiver of comparable performance; with f.m., perhaps slightly better musical reproduction.

Why Mr. L. Welch should want this set to be a transistor type working from the mains, I cannot imagine. I have heard of built-in obsolescence, but please do save us from built-in inferiority. As the Homburg hat is an inferior substitute for a nice head of hair; so is the transistor an inferior substitute for a valve, as far as the matter of music reproduction is concerned.

My 1936 Aerodyne is not as good as it once was, but I could not replace it musically with a transistor set. Snakes are said to hiss, but transistors do hiss. If we were really music lovers, we would have hissed the transistor off the audio stage by now.

A. Biddlecombe.

Ickenham,
Middlesex.

To Build or Not to Build


I COMPLETELY endorse a letter in one of your recent issues where the writer states that the cost of building one's own equipment works out more than buying the finished article.

Admittedly I, as a radio experimenter obtain much pleasure from building my own gear. But let us face it, sooner or later finance must be the deciding factor. Although I consider myself at least average at making a decent job of construction, there is still a lot to be desired when surveying the end product, especially as to a neat and professional-looking front panel which is so often a let-down.

I think that the time is rapidly approaching when price and appearance will count for a great deal and radio construction as such, will be a rich man's hobby.

A. J. Simmonds.

Welling,
Kent.

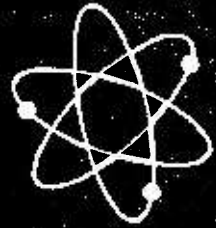

VOLUME EXPANSION

G. R. WILDING

JUST before the war considerable interest was aroused by volume expansion devices in radio receivers, the idea being an attempt to reproduce by the loudspeaker the range of volume level produced in the studio.

As is well known, both in the recording and broadcasting studio, the range of audio volume is compressed, low levels being boosted and high levels attenuated so that a fairly constant output is achieved.

Simple System

If this was not done low-volume levels would insufficiently modulate the carrier or impress the record groove, as the case may be, while loud signals would cause over-modulation or a break through from one record groove to its neighbour.

However, in the interests of good-quality reproduction, which aims to make the speaker output a copy of the original in volume range as well as freedom from distortion, there is much to be said for schemes for restoring, if only partly, the orchestra's wide range of sound output.

Within the confines of the average living-room it would probably be impossible to reproduce, say, a solo artist at adequate strength for comfortable listening and, at the same time, reproduce in full

proportion the sound output from the full accompanying orchestra composed of up to 100 players. But undoubtedly there is a case for some degree of volume expansion, adjustable at will.

The simplest device of all, used by Pye in many pre-war models, was the switching in of a small dial bulb across the speaker itself. On loud passages the bulb would light up and as its hot resistance is higher than its cold resistance it would impose a heavier load on low signals than peak signals and thus expand the volume range.

This simple system had great disadvantages, of course. The loading created by the bulb effected a mismatch between speaker and valve, it absorbed power, transient loud passages of duration shorter than the thermal delay of the bulb failed to create effect and the arrangement did not have a linear input/loading curve. But it was simple and it did work.

For experiment in this direction it is advisable to use a tapped speaker transformer so that various types of bulb can be tried. Ideally the bulb should fully light at peak volume and be completely extinguished at about quarter to one-third of this value. Obviously any bulbs should be of low current consumption and with a fine filament for rapid heating up.

Negative Feedback

By incorporating negative feedback with this simple arrangement its range of operation can be greatly increased. Instead of shunting the bulb directly across the transformer a resistor is placed in series with it of value about equal to the resistance of the bulb when half-lit, and a voltage will be then developed across the resistor which will not rise proportionately with increase of output but will tend to fall off at high volume.

With the bulb half-lit an equal voltage will be developed across bulb and resistor, but as the signal rises the greater fraction of the voltage will be fed across the bulb and less across the resistor. If the resistor voltage is then fed back as a negative feedback signal to the valve grid it will be apparent that the greater the volume the less the feedback.

This circuit lends itself well to adaptation and experiment to suit individual tastes and receiver characteristics. However, the use of a bulb imposes an undue load on the valve and does not provide anything like an ideal device to satisfy the requirements.

Much more satisfactory are voltage dependent

Fig. 1 (left): Simplest volume expansion device. On low volume the bulb acts as a heavy load; when lit on high volume imposes a reduced load.


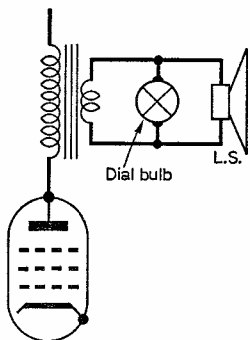


Fig. 2 (right): "Bulb" volume expansion circuit with negative feedback. The greater the volume, the less the feedback.

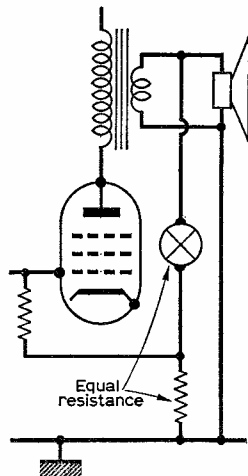



LAFAYETTE HA-63 COMMUNICATION RECEIVER

7 valves plus Rectifier. 4 Bands 550 kc/s-31 Mc/s. "S" Meter—BFO—ANL—Bandspread Tuning. 200/250V. A.C. Brand New 24 Gns. Carr. Paid.

LAFAYETTE HA-230 AMATEUR COMMUNICATIONS RECEIVER

Supersedes model HE-30. 8 valves + rectifier. Continuous coverage on 4 bands. 550 Kcs. 30 Mc/s. Incorporates 1 RF & 2 IF stages. Q Multiplier, B.F.O., ANL. "S" meter, Electrical bandspread. Aerial trimmer, etc. Supplied brand new and guaranteed. £33. S.A.E. for full details. Also available in semi Kit Form. 25 gns.




LAFAYETTE HA-55 AIRCRAFT RECEIVER

108-136 Mc/s. High selectivity and sensitivity. Incorporates 2 RF stages including 6CW4 Nuvistor. 5 tubes for 11 tube performance, solid state power supply, adjustable squelch control, slide ring dial, built in 4in. speaker and front panel phone jack. 220/240V. A.C. Supplied brand new and guaranteed. £19.7.6. Carr. 10/-.



MAIN LONDON AGENTS FOR CODAR EQUIPMENT

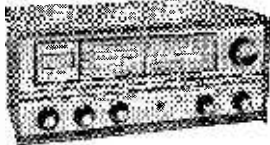CR70A. Communication Receiver £19 10 0
PR30 Preselector £5 10 0
RQ.10 "Q" Multiplier £6 15 0
A.T.5 Amateur TX £16 10 0
Postage extra.
Full details on request.



SINCLAIR TRANSISTOR AMPLIFIERS

X12 Amplifier 8/6; Power Pack 54/-; X10 Amplifier Built £6.19.6, Kit £5.19.6; X10 Power Pack 54/-; X20 Amplifier Built £9.19.6, Kit £7.19.6; X20 Power Pack £4.19.6. Micro FM Radio Kit £5.19.6. Micro 6 5/6; TR750 amp Kit 3/9/6; Micro amp 2/8/6; Micro Injection 2/7/6. Post Paid.



TRANSISTORISED TWO-WAY TELEPHONE INTERCOM.

Operative over amazingly long distances. Separate call and press to talk buttons, 2-wire connection. 1000's of applications. Beautifully finished in ebony. Supplied complete with batteries and wall brackets. £6.10.0 pair. P. & P. 3/6.



2-WAY RADIOS

Superb quality. Complete with all accessories and fully guaranteed.
3 Transistor £7.19.6 pr.
4 Transistor 11 gns. pr.
5 Transistor £8.5.0. pr.
9 Transistor £22.10.0 pr.
10 Transistor 28 gns. pr.
Post extra. (S.A.E. for full details).
These cannot be operated in U.K.



VOLTAGE STABILIZER TRANSFORMERS

Input 80-120v. and 100-240v. Constant output 110v. or 240v. 250 watts. Brand New Guaranteed. £10.10.0. Carr. 7/6.



VARIABLE VOLTAGE TRANSFORMERS

Brand New Guaranteed—fully Shrouded. Input 230v. 50/60 c/s. Output 0-250 Volts.
1 Amp £4.10.0
2.5 Amp £6.17.6
5 Amp £9.0.0
8 Amp £13.10.0
10 Amp £17.0.0
12 Amp £19.10.0
20 Amp £32.10.0
2.5 Amp Portable—Metal Case with Meter—Fuses, etc. £9.17.6.




SILICON RECTIFIERS

200v. P.I.V. 200mA 8/6
400v. P.I.V. 3 amp 7/6
1,000v. P.I.V. 650mA 6/6
800v. P.I.V. 500mA 5/6
800v. P.I.V. 5 amp 7/6
400v. P.I.V. 500mA 3/6
70v. P.I.V. 1 amp 3/6
150v. P.I.V. 165mA 1/-
Discounts for quantities. Post extra.

TEST EQUIPMENT


PORTABLE OSCILLOSCOPE CT.52

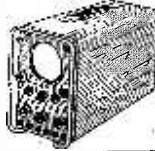A compact (9in. x 8in. x 16in.) general purpose scope. T/B 10c/s-40 kc/s. Band width 1 Mc/s. Sensitivity 40MV/CM. Mullard DG 7/3 2 1/2in. CRT. For operation on 200/250V. A.C. Supplied complete with metal transit case, strap, test leads and view hood. Brand new and guaranteed. £22.10.0. Carr. 10/-. Supplied complete with instructions.



OS/88/U OSCILLOSCOPES

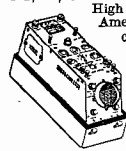High quality Portable American Oscilloscope. 3in. c.r.t. T/B 3 c/s-50 kc/s X Amp: 0-500 kc/s Y Amp: 0.2 Mc/s. Power requirements 105-125V. A.C. Supplied in brand new condition fully tested. £25. Carr. 10/-. Suitable 230/115v. Transformer 15/6.




ERSKINE TYPE 13 DOUBLE BEAM OSCILLOSCOPE

Time base 2 c/s-750 kc/s. Calibrators at 100 kc/s and 1 Mc/s. Separate Y1 and Y2 amplifiers up to 5.5 Mc/s. Operation 110/230 volt A.C. Supplied in perfect working order. £27.10.0. Carriage 20/-.



TE-20 RF SIGNAL GENERATOR

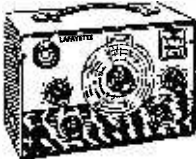Accurate wide range signal generator covering 120 kc/s-260 Mc/s on 6 bands. Directly calibrated. Variable R.F. attenuator. Operation 200/240V. A.C. Brand new with instructions. £12.10.0. P. & P. 7/6. S.A.E. for details.



LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYZER

2 PF—2,000 MFD. 2 ohms—200 Megohms. Also checks impedance, turns ratio insulation 200/250V. A.C. Brand New £15. Carr. 7/6.

LAFAYETTE NUVISTOR GRID DIP METER

Compact, true one hand operation. Frequency range 1.7-180 Mc/s. 230V. A.C. operation. Supplied complete with all coils and instructions. £12.10.0. Carr. 5/-.




CLEAR PLASTIC PANEL METERS

First grade quality. Moving Coil panel meters, available ex-stock. S.A.E. for illustrated leaflet. Discounts for quantity. Available as follows: Type ML, 88P, 1 21/32in square fronts.

100-0-100µA	27/6	200mA	...	22/6	100V D.C.	...	22/6
500-0-500µA	22/6	300mA	...	22/6	150V D.C.	...	22/6
1-0-1mA	...	500mA	...	22/6	300V D.C.	...	22/6
1mA	...	750mA	...	22/6	500V D.C.	...	22/6
2mA	...	1A D.C.	...	22/6	750 D.C.	...	22/6
5mA	...	2A D.C.	...	22/6	15V A.C.	...	22/6
10mA	...	5A D.C.	...	22/6	50V A.C.	...	22/6
20mA	...	3V D.C.	...	22/6	150V A.C.	...	22/6
50mA	...	10V D.C.	...	22/6	300V A.C.	...	22/6
100mA	...	20V D.C.	...	22/6	500V A.C.	...	22/6
150mA	...	50V D.C.	...	22/6	"S" Meter in 22/6	...	22/6

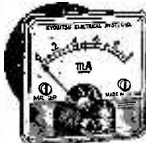POST EXTRA. Larger sizes available—send for lists.



NOMBREX EQUIPMENT

Transistorised Audio Generator 10-100,000 c/s. Sine or square wave. £16.15.0.
Transistorised Signal Generator 150 kc/s. 350 Mc/s. £10.0.0.
Transistorised resistance capacity bridge 1Ω. 100 Meg Ω. 1 pf-100µF. £9.10.0.
Transistorised Induction bridge, 1µN-1000H. £18. Mains operated Transistor power supply unit, output 1-15v. up to 100 mA. £6.10.0.
All above post paid with battery.



TE-51 NEW 20,000Ω/VOLT MULTIMETER

0 / 6 / 60 / 120 / 1,200V. A.C.
0 / 3 / 30 / 60 / 300 / 600/8,000V. D.C.
0 / 60µA / 12 / 300 MA. D.C.
0 / 60K / 6 Meg Ω.
85/-, P. & P. 2/6.



MODEL PV-58 VALVE VOLTMETER

11 meg. input. 7 D.C. volt ranges. 1.5-1,500 v. 7 A.C. volt ranges. 1.5-1,500 v. 4,000 Peak to Peak. Resistance .2 ohm to 1,000 megohm. Decibels -10db to +65db. Supplied brand new with instructions, leads and probe. £12.10.0. P. & P. 3/6.



TS-76 20,000 O.P.V. PUSH BUTTON MULTI-TESTER

Simple operation D.C. volts up to 1,000 v. A.C. volts up to 1,000 v. Resistance up to 10 megohm. Current up to 250 mA. Decibels - 20 to + 36 db. £5.5.0. P. & P. 2/-.



MODEL 500. 30,000 o.p.v. 0.5/1/2.5/10/25 / 100 / 250 / 500 / 1,000V. D.C.
0 / 2.5 / 10 / 25 / 100 / 250 / 600 / 1,000V. A.C.
0 / 50µA / 5 / 50 / 500µA. 12 amp. D.C.
0 / 60K / 6 Meg. / 60 Meg Ω. £8.17.6. Post Paid.


CALLERS WELCOME!

Open 9 a.m. to 6 p.m. every day Monday to Saturday. Trade supplied.

GW SMITH & CO (RADIO) LIMITED

Phone: GERRARD 2504/9155
Cables: SMITHEX LESQUARE
3-34 LISLE STREET, LONDON, W.C.2

SNIPERSCOPE

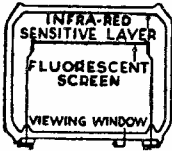

Famous war-time "cats eye" used for seeing in the dark. This is an infra-red image converter cell with a silver caesium screen which lights up (like a cathode ray tube) when the electrons released by the

infra-red strike it. A golden opportunity for some interesting experiments. 5/- each, post 2/-. Date will be supplied with cells, if requested.

MAINS POWER PACK

MAINS POWER PACK designed to operate transistor sets and amplifiers. Adjustable output 6v.-9 to 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries. P.R1, P.P3, P.P4, P.P6, P.P7, P.P9, and others. Kit comprises: mains transformer-rectifier, smoothing and load resistor, 5,000 and 500 mfd. condensers, zener diode and instructions. Real snip at only 14/6, plus 2/6 post.

SPEAKER BARGAIN

12in. High fidelity loud-speaker. High flux permanent magnet type with either 3 or 15 ohm speech coil. Will handle up to 10 watts. Brand new, by famous maker. Price 27/6, plus 3/6 post and insurance.




ACOS GP83 TURNOVER PICK-UP CARTRIDGE



For Stereo—LP—and 78 records fitted with two Styli. This is mounted and is standard replacement for most record players using Garrard—B.S.R.—Collaro, etc., etc. We offer these new and perfect for 15/- (less than the price of stylus), plus 2/- post and insurance.

STUPENDOUS OFFER—£11 for £2

The Princess superhet described below is a very fine little set that has been carefully designed for high performance. Only recently (under another name of course) this was on offer in many radio shops, for £10.19.6, but we have been fortunate in obtaining the parts at a very low price and now pass this saving on to you. If you act quickly you can purchase this for only 39/6 plus 3/6 post and insurance. Note these features: ● Long and Medium Wave ● Long clear dial with travelling pointer and slow motion drive ● Push pull output approximately 350 m.w. ● A.V.C. and feed back ● Dust cored H.Q. I.F. transformers ● High selectivity ferrite aerial ● Six tested and guaranteed transistors ● Printed circuit board for fool-proof assembly ● Economy output circuit gives long life from P.P3 battery ● Permanent magnet moving coil speaker ● Cabinet size 4 1/2 in. x 3 in. x 1 1/2 in. With carrying strap.

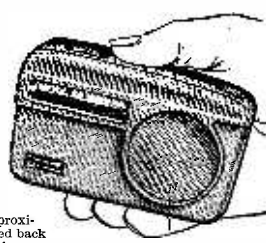

You get over 100 parts (dist value over £10). In fact everything you need and easy to follow wiring and aligning instructions. Don't miss this wonderful offer. Make up several while you have the chance. Use them as presents and you'll be loved for ever. Battery 1/9 extra.

THIS MONTH'S SNIP

GARRARD AUTO RECORD PLAYER Model 2000



This is one of the latest products of the World's most experienced maker of fine record reproducers—It's superior features include—automatic playing of up to 8 mixed size records—stopping and starting without re-feeding—manual playing—pick up pivots to give low stylus pressure—large diameter turn-table for max stability—adjustments include pick-up height—pick-up dropping position and stylus pressure. Size is 13 1/2 in. x 11 1/2 in. clearances 4 1/2 in. above 2 1/2 in. below—fitted with latest hi-compliance cartridge for stereo—and mono., L.P. and 78. Supplied complete with mounting template and service sheet. Offered this month at the Special Snip price of **£6.9.6d.**, plus 7/6 carriage and insurance.

TRANSISTOR BARGAIN

With carrying handle size 10in. x 5in. x 3in. Strongly made from best plywood and covered in two-tone fabric—looks very smart, suitable for receiver—amplifier—extension speaker etc.—Originally listed at 29/6—but offered this month at only 15/- plus 5/- post and insurance; also given free with it is a printed circuit board to suit it and building instructions for fine two-way radios. Don't miss this grand offer.



FOUR-STATION INTERCOM.

Will save time and improve efficiency. Ideal in home—office—shop—surgery, etc.

Complete outfit comprises Master unit and three substations each of which can call the master and have full two-way working. No wiring problems as subs fitted with 60ft. twin flex and they plug into sockets. Also included is packet of staples—and battery. Nothing else to buy—£7.15.0, plus 4/6 post and insurance. **750mW TRANSISTOR AMPLIFIER**




4 transistors including two in push-pull-input for crystal or magnetic microphone or pick-up—feed back loops—sensitivity 5 m/v. Price 19/6. Post and ins. 2/6. Speakers 3in. 12/6, 5in. 13/6; 6in. x 4in. 14/6.

ELECTRONICS (CROYDON) LIMITED

102/3 TAMWORTH ROAD, CROYDON, SURREY (Opp. West Croydon Station)
266 LONDON ROAD, CROYDON, SURREY (Opp. ABC Cinema, West Croydon)
post orders to: Dept. PW, SPRINGFIELD ROAD, EASTBOURNE, SUSSEX

YOURS FREE FOR 7 DAYS

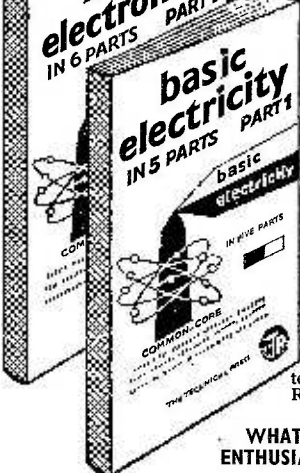

The New 'Picture-Book' way of learning BASIC ELECTRICITY (5 VOLS.) BASIC ELECTRONICS (6 VOLS.)

You'll find it easy to learn with this outstandingly successful new pictorial method—the essential facts are explained in the simplest language, one at a time; and each is illustrated by an accurate cartoon-type drawing.

The books are based on the latest research into simplified learning techniques. This has proved that the Pictorial Approach to learning is the quickest and soundest way of gaining mastery over these subjects.

The series will be of exceptional value in training mechanics and technicians in electricity, Radio and Electronics.

WHAT THIS MONTH'S ENTHUSIASTIC READERS SAY

"I have recently had the pleasure of perusing your excellent publications on **BASIC ELECTRICITY** and **BASIC ELECTRONICS**, which are now available from our (RNZAF) Service libraries . . ." C.W.K., New Zealand.

"I have found **BASIC ELECTRICITY** and **BASIC ELECTRONICS** excellent publications and look forward to future publications as available . . ." P.J.T., Blackburn.

POST NOW FOR THIS OFFER!!

TO SELRAY BOOK CO.

60 HAYES HILL, HAYES BROMLEY, KENT

Please send me **Without Obligation to Purchase**, Basic Electricity/Basic Electronics on **7 Days Free Trial**. I will either return set, carriage paid, in good condition within 8 days or send down payment of 15/- (Basic Electricity) followed by 6 fortnightly payments of 10/-. Down payment of 15/- (Basic Electronics) followed by 6 fortnightly payments of 12/6. Alternatively, I will send 68/- (Basic Electricity—5 parts), 81/- (Basic Electronics—6 parts) post free. This offer applies to United Kingdom only.

Tick against set required (only one set allowed on free trial).

BASIC ELECTRICITY

BASIC ELECTRONICS

Signature

(If under 21, signature of parent or guardian)

NAME
BLOCK LETTERS BELOW

FULL POSTAL

ADDRESS

resistors, since these small components have an internal resistance which decreases rapidly as the applied voltage is increased, have a long working characteristic and do not impose a heavy load on low inputs.

To fully take advantage of the characteristics of VDRs it is best to apply them across a high impedance so that there is maximum variation in applied voltage. In practice this means feeding them from the anode of the output valve via a d.c. blocking capacitor and series resistors.

The blocking capacitor should be sufficiently large to have negligible reactance to the signal compared with the ohmage of the series resistors to avoid any phase change, so a value of at least 0.5μF is indicated.

As shown in the circuit of Fig. 3 the ratio $R3/R1+R2+R3$, without taking into account the effect of the VDR, would determine the percentage of negative feedback. If R3 was 5,000Ω and it was desired to have 5% feedback, then R1 and R2 should have a combined resistance of $5,000 \times 19$ or 95,000Ω.

If R1 and R2 are made equal at 47,500Ω each the shunting of the VDR across R2 and R3 will lower their effective value and thus reduce the degree of voltage feedback, and as output voltage rises on peak volume the VDR's internal resistance will drop still further and decrease feedback accordingly. Thus the louder the volume handled by the output valve the less is the percentage of negative feedback supplied to the grid.

This is probably an ideal way to approach the problem and by making R1 and R2 variable the characteristics of the feedback can be varied to suit individual receivers and choice.

Matching

There are, of course, very many different types of VDR but practically any type will suffice for this purpose and undoubtedly those used in TV for line or field stabilisation will do. However, it is always necessary to match the VDR to R1 and R2, that is if tests indicate that the particular VDR to hand has a high impedance, so should the resistors and vice versa. Obviously if it was thought desirable to treble the value of these components it would be necessary also to treble the value of R3 if the same percentage of feedback was required.

Altogether this circuit offers many opportunities for experiment and by including a switch in the lead to the VDR normal non-expanded results can be readily obtained and contrasted with the modified output.

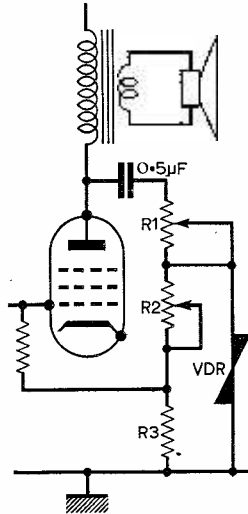


Fig. 3; A volume expansion circuit using a VDR in a negative feedback arrangement. At low volume levels, feedback approximates to $R3/R1+R2+R3$ and reduces rapidly as volume increases.

MICRO TO MEGA

—continued from page 43

the right introduces a negative index. Thus 0.003 is 3×10^{-3} and 7.45 is 7.45×10^{-2} .

More about Roots

From the general expression $(a^x)^y = a^{xy}$ it will be seen that to find the square root of 10^x , the x is divided by 2. Similarly to find the cube root, divide by 3.

One very important consideration in finding roots however. The result of dividing the index by the root divisor must be a whole number and any remainder must be considered separately as shown in the following examples:

$$\sqrt{10^9} = 10^{9/2} = 10^4 \times \sqrt{10}$$

$$\sqrt[3]{10^8} = 10^{8/3} = 10^2 \times \sqrt[3]{1000}$$

Examples

The following examples show simple calculations involving Ohms Law for d.c.

(1) $R = 2k\Omega$; $E = 300V$.

$$I = \frac{300}{2 \times 10^3} = 150 \times 10^{-3} = 150mA.$$

(2) $E = 9V$; $I = 300mA$.

$$R = \frac{9}{300 \times 10^{-3}} = 3 \times 10^2 \times \frac{1}{10^{-3}} = 3 \times 10^1 = 30\Omega.$$

A typical example of a calculation involving a square root is that for determining the resonant frequency of a tuned circuit:

$$f = \frac{1}{2\pi\sqrt{LC}}$$

if $L = 7.8\mu H$ and $C = 100pF$

$$f = \frac{1}{2\pi\sqrt{7.8 \times 10^{-6} \times 100 \times 10^{-12}}}$$

$$= \frac{1}{2\pi\sqrt{7.8 \times 10^{-16}}} = \frac{1}{2\pi \cdot 10^{-8}\sqrt{7.8}}$$

$$= \frac{10^8}{17.55} = 0.057 \times 10^8 = 5.7 \times 10^6 = 5.7Mc/s.$$

Further Uses of Indices

Multiplying base numbers by adding the indices is similar to the multiplication of numbers by adding the logarithms. This parallel is not without justification, for the common logarithm of a number $N = 10^x$ is x , i.e. if $10^x = N$ then $x = \log_{10}N$. Therefore $\log 10 = 1$, $\log 100 = 2$, $\log 1,000 = 3$ etc.

This principle is extended further to produce the slide rule, which in fact is only an adding device whereby logarithms are added together, the scales being logarithmic.

Footnote

A world of warning about the nomenclature of numbers. The term "million" is readily understood as being 10^6 , but there is sometimes confusion about the word "billion". A billion is, strictly speaking, 10^{12} although it is sometimes erroneously attributed the value 10^9 .

An **ELECTRONIC GATE**


or
TRACE DOUBLER

(Continued from page 1081 April)

THE power supply requirements are quite modest and many oscilloscopes should be able to provide them without undue strain. There is no reason, however, why an integral power supply should not be incorporated, though this will almost certainly necessitate an increase in the size of the equipment plus, of course, some provision for ventilation, which was not found necessary in the present equipment, which generates very little heat. Where an external power supply, from the oscilloscope or otherwise, is used, thorough decoupling by means of C18, C19, R16 is essential, otherwise there is a very real danger of the high-amplitude gating waveform interacting with the ancillary equipment or with the oscilloscope's vertical amplifier. It will be noted that two decoupling capacitors, C18 and C19, are used. This is desirable because high value electrolytics have an appreciable self-inductance which renders them less effective at higher frequencies. C19, being a paper component, is less affected and so continues decoupling where C18 leaves off. Some paper capacitors are marked with a band at one end. This is the outer foil and should be connected to chassis.

The gate operated satisfactorily at varying h.t. voltages, these extending from 150V to 350V. At the lower voltages the output was necessarily restricted, whilst the higher values only increased the current consumption, so that an arbitrary value of 250V was selected. This was a convenient value because it allowed a measure of decoupling to be effected from the oscilloscope's h.t. voltage of 270V. The extra 20V was dropped by a 1k Ω 2W resistor R16 which may require some adjustment for differing h.t. voltages.

The metal work is quite straightforward and calls for little comment. The sides are made of aluminium and are 3in. x 5in., whilst the bottom is a piece of aluminium 5in. x 8in. The cover, which is U-shaped, measures 5in. deep x 3in. high x 8in. wide and is best made up after the front and rear panels are made up and joined together by the side pieces. Any errors or alterations can then be allowed for. It must also be borne in mind that components other than those specified may not fit in the available space. The potentiometers and S2 must not exceed 1½in. diameter and the chassis must be spaced sufficiently far from the front panel to allow the valves to be easily removed or replaced. In the prototype a spacing of 2½in. was found to be adequate. The front and rear panels and the chassis are attached to the sides by ¼ in. c/s 6BA screws (and nuts), which then allows the cover to fit snugly all round. This and the

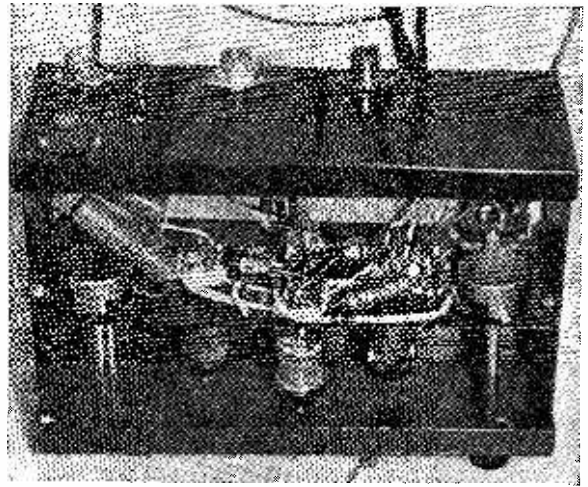

bottom are attached to the front and rear panels by small self-tapping screws, producing a strong and rigid assembly. In the prototype the chassis and front and rear panels were screwed to the sides, the bottom was screwed on and then the remaining edges of the panel were masked off, after which they were sprayed glossy black enamel. The top cover was sprayed black crackle after the inside edges were masked off. All mating surfaces *must* be free from paint so that the electrical continuity necessary for preserving electrical screening can be maintained. Small transfers on the front and rear panels complete the "finishing" of a very presentable little piece of equipment. Note that the "separation" control has been labelled "trace height". This was resorted to after it was found that the transfers did not include "separation" and attempts to make the word up from individual letters proved a dismal failure—except possibly as an exercise in time wasting!

The operation known as "wiring up" should not provide any difficulty to the experienced constructor, though the novice would be well advised to enlist the aid of an experienced friend, particularly when trying the gate out for the first time. A few notes, however, would not come amiss. C11 and C12 must be of small physical size in order to fit into the available space; 200V components, as suggested, should prove suitable, though it is undesirable to reduce their capacity any further unless R5, R6 are increased in proportion to a maximum value of 10M Ω .


Gating Capacitors

The gating speed capacitors C1-C5 and C6-9 are wired in series from tag to tag of S2a/b, whilst C5 and C10 go from the second last tags of both sections to pins 1 and 6 of V1. The switch S1 is wired so that the slowest speeds are obtained with the switch anticlockwise looking from the front and the highest speeds with the switch rotating clockwise. The last position is connected to earth and puts the multi out of action, though two 4.7pF capacitors could be substituted if higher gating speeds were desired. This is an experimental suggestion which has not been tried with the prototype. The outputs from both halves of V4 are connected directly to the output sockets without the usual coupling capacitors since these are already in the oscilloscope. C15 and C16 are wired directly from the input sockets to S2 and are spaced away from the chassis. C14 and C17 are wired from

7 VALVE AM/FM RADIOGRAM CHASSIS

Valve line-up EOC85, ECH81, EF89, EA800, EL54, EM81, EZ80.
Three Waveband and Switched Gram. positions. Med. 200-850 m. Long 1,000-2,000 m. VHF/FM 88-95 Mc/s. Phillips Continental Tuning Insert with permeability tuning on FM and combined AM/FM IF transformers. 400 Kcs and 10.7 Mc/s. Dust core tuning all coils. Latest circuitry including AVC and Neg. Feedback. Three watt output. Sensitivity and reproduction of a very high standard. Chassis size 13 1/2 x 6 1/2 in. Height 7 1/2 in. Edge illuminated glass dial 1 1/2 x 3 1/2 in.

New 1966 Model now available

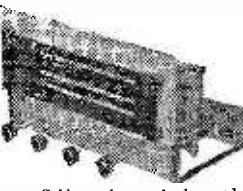

Vertical pointer. Horizontal station names. Gold on brown background. A.C. 200/250V. operation. Magic-eye tuning. Circuit diagram now available. Aligned and tested ready for use £18.19.6. Carr. & Ins. 7/6. Comp. with Tape, O/P socket, ext. spkr and P/U sockets, and indoor F.M. aerial and 4 knobs—wainut or ivory to choice. 3 Ω P.M. Speaker only required. Recommended Quality Speakers 10" R.A., 27/6. 13 1/2" x 8" E.M.I. Fidelity, 42/6. 12", R.A. 32/6. 12" R.A. with cone, Tweeter, 42/6. Carr. 2/6.

MULLARD "3-3" & "5-10" HI-FI AMPLIFIERS

3 ohm & 15 ohm output
"3-3" Amp. 3 valve, 3 watt hi-f quality at reasonable cost. Bass Boost and treble controls quality sectional output transformer, 40 c/s-25 kc/s + 1dB, 100mV for 3W, less than 1% distortion. Bronze scotchwood panel. Complete Kit only 7 gns. Carr. 7/6. Wired and tested £8.10.0.

MULLARD "5-10" AMPLIFIER. 5 valves 10W 3 and 15 ohms output. Mullard's famous circuit with heavy duty ultra-linear quality output transformer £9.19.6 Carr. & Ins. 7/6.

Basic amplifier kit price Ready built 1 1/2 gns.

CONTROL PANEL KIT. Bass, Treble and Volume controls with 4-position selector switch for radio tape and 1 1/2 in. 4 in. scotchwood panel.

AMPLIFIER KIT AND CONTROL PANEL KIT, £11.19.6. Ditto, ready wired, £14.19.6.


2-VALVE PRE-AMP UNIT. Based on Mullard's famous 2-valve (2xEP86) circuit with full equalisation, with volume, bass, treble and 5-position selector switch. Size 9 x 6 x 2 1/2 in. Ready Built £7.19.6. Carriage 3/6.

26 1/2 gn TAPE RECORDER for ONLY £19.10.0


carr. 12/6

Bargain of the Year Offer — cancelled Export Contract

Famous manufacturer's brand new unused and factory tested 2 speed, 3 1/2 and 7 1/2 i.p.s. twin track tape recorder 3 Watt output. Tape recorder Rev.-counter, fast forward and rewind, take 7" reels, mike and gram input. Straight through amplifier facilities. Output sockets for ext. speaker, monitor or external amplifier. Super-imposed switching magic eye recording level and mains nee indicator. Volume and tone controls 7" x 4" speaker. Attractively styled cabinet with detachable lid mike and reel storage facilities. A.C. 200/250 volts operation. Complete with crystal mike, tape spare reel and screen lead etc.

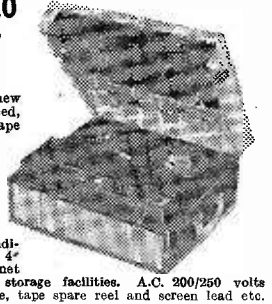

6 VALVE AM-FM TUNER UNIT

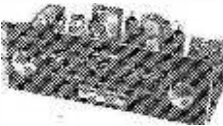

Med. and VHF 190m-550m, 86 Mc/s-103 Mc/s, 6 valves and metal rectifier. Self-contained power unit. A.C. 200/250V operation. Magic-eye indicator, 3 push-button controls on/off Med., VHF, Diodes and high output Sockets with gain control. Illuminated 2-colour perspex dia 1 1/2" x 4", chassis size 1 1/2" x 4" x 5 1/2".

A recommended Fidelity Unit for use with Mullard "3-3" or "5-10" Amplifiers. Now available as complete kit as illustrated, inc. power unit. Carriage 7/6.

Ditto, but less power unit, £8.19.6, carriage 7/6.

Circuit and construction details, 4/6, free with kit.

£10.19.6
Carriage 7/6.

Alumina. Chassis. 18g. Plain Undrilled, folded 4 sides, 2" deep, 8" x 4", 4/8; 8" x 6", 5/9; 10" x 7", 6/9; 12" x 6", 7/8; 12" x 8", 8/-, etc.
Alumina. Sheet. 18g. 6" x 6", 1/-; 8" x 9", 1/6; 8" x 12", 12/-; 12" x 12", 4/6, etc.

Jack Plugs. Standard 2 1/2" Igranite Type, 2/8. Screened Ditto, 3/3. Miniature scr. 1 1/2", 2/3. Sub-min. 1/8. Soldering Irons. Mains 22/220V or 230/250V. Solon 25W Inst. 24/6. Spare Elements, 5/6. Bits, 1/3. 65W, 29/6, etc.

Condensers—Silver Mica, All values 2pF to 1,000pF 6d. each. Ditto Ceramic 9d. Tub. 450V T.C.C. etc. 0.001 mFd to 0.01 and 0.1/350V, 9d. 0.02-0.1/500V, 1/-, 0.25 Hunts 1/6, 0.5 T.C.C. 1/9, etc. etc. Close Tol. S/Micas—10%, 5pF-500pF 8d. 600-5,000pF, 1/-, 1% 2pF-100pF, 9d. 100pF-500pF, 11d. 575pF, 5,000pF, 1/6. Resistors—Full Range 10 ohms-20 meg. ohms 20 1/4 and 1W, 3d., 4W, 5d. (Midget types modern rating) 1W, 5d., 2W, 9d. Hi-Stab. 5% 1W, 6d. (100 ohms-1 meg). Other values 9d. 1% 1W, 1/6 etc. etc.
Phono Plugs, 9d. Phono Sockets (open), 9d. Ditto (closed), 1/-, Twin Phono Sockets (open), 1/8.

JASON FM TUNER UNITS. Designer-approved kit of parts. FHT1, 5 gns. 4 valves, 20V. FMT2, £7.10.0. 5 valves 25V. JTV MERCURY 10 gns. 3 valves 22/6. JTV £18.19.6. 4 valves, 23/6. NEW JASON FM HANDBOOK, 2/6. 48 hr. Alignment Service, 7/6. P. & P. 2/6.

TRIMMERS. Ceramic (Compression Type)—30pF, 50pF, 70pF, 9d.; 100pF/150pF, 1/8; 250pF, 1/6; 600pF, 1/9.

PHILIPS. Bee Hive Type (conc. air-spaced) 2-8pF, 1/-; 3-30pF, 1/-.

KNOBS—Modern Continental types Brown or Ivory with Gold Centre; 1" dia., 9d. each; 1 1/2" each; Conc. knobs Ivory with Gold Centre 1 1/2" dia. 2/9 per pair. Matching ditto 2/6 ea.
LARGE SELECTION AVAILABLE.

Metal Rectifiers—STC. Siemens bridge 250V. 150mA, 14/6. Ditto half wave 250V. 50mA, 7/6. Mullard BY100, 8/6; BY114, 8/6.

TUB-ELECTROLYTICS—CAN 25/25V. 50/12V. 1/8; 8-8/450V. 4/6; 50/50V. 100/125V. 2/-; 32-32/275V. 4/6. 8/450V. 4/350V. 2/3; 50/50/350V. 6/6. 16+16/450V. 6/8; 60/230/275V. 12/6; 33+32/450V. 6/6; 100+200/275V. 12/6.

Volume Controls—5K-2 Meg. ohms. 3in. Spindles. Morganite Midget Type 1 1/2 in. diam. Guar. 1 year. LOG or L.N. ratios less Sw. 3/8. DP. Sw. 5/7. Twin Stereo less Sw. 7/8 100k to 2M ohms with DP Sw. 9/8.
WAJCHANGE SWITCHES. 1 p. 12-way 2p. 2-way, 2 p. 6-way, 3 p. 4-way, 4 p. 3-way, 4 p. 3-way, long spindle, 3/6 ea.

EXPANDED ANODISED METAL—Attractive gilt finish 1/2 in. x 1/2 in. diamond mesh 4/6 sq. ft. Multiples of 6in. cub. Max. size 4ft. x 3ft., 47/6, plus carr. Do. finer pattern mesh 4/6 sq. ft., multiples of 12in. max. size 3ft. x 2ft., 27/6 sheet.

ENAMELLED COPPER WIRE—1lb. reels 14g-20g. 3/-; 22g-28g, 3/6; 36g-38g, 4/8; 39g-40g, 5/- etc.

COAX 80 OHM CABLE

High grade low loss Cellular air spaced Polythene—1" diameter. Stranded cond. Famous mfrs. Now only 6d. per yard.

Bargain Prices—Special lengths:
20 yds. 9/-. P. & P. 1/6.
40 yds. 17/6. P. & P. 2/-.
60 yds. 25/-. P. & P. 3/-.
Coax Plugs 1/-. Sockets 1/-.
Couplers 1/8. Outlet Boxes 4/6.

BONDACOUST Speaker Cabinet Acoustic Wadding (1 in. thick approx.) 18 in. wide, any length cut, 2/3 per ft., 6/- per yard.

TINNED COPPER WIRE, 16-22g. 4/- 1lb. ERSIN MULTICOORE SOLDER, 60/40 4d. per yard. Cartons 6d., 1/-, 2/6 etc.

TYGAN FRET or Vynair, 12 x 12in. 2/-; 12 x 18in. 3/-; 12 x 24in. 4/- etc.

New Boxed	Reduced Bargain Prices
174	3/6 EP80 7/8 PCF80 3/6
175	8/- EF86 8/6 PCL83 10/6
185	9/- EL33 12/6 PCL84 10/-
284	7/- EL24 12/6 PCL85 11/6
374	7/- EL54 7/- PL80 10/8
EOC81	7/- EY51 8/- PLS1 9/8
EOC82	7/- EY86 9/- PLS3 8/-
EOC83	7/- E280 7/- PY83 10/8
ECL80	9/- E281 7/- PY82 7/6
ECL82	10/- G292 9/6 U26 10/8
ECL86	10/8 POC84 3/- UL84 9/-

RECORDING TAPE—Reduced Prices

Famous American Columbia (CBS) Premier Quality Tape at REDUCED PRICES.

A genuine recommended Quality Tape—TRY IT! Brand new, boxed and fully guaranteed. Fitted with leader and stop folia.

5in.	Standard 600ft. 13/-	Long Play 900ft. 17/8	Double Play 1,200ft. 31/6
5 1/2 in.	900ft. 16/- <td>1,200ft. 19/8 <td>1,800ft. 37/6 </td></td>	1,200ft. 19/8 <td>1,800ft. 37/6 </td>	1,800ft. 37/6
7in.	1,200ft. 21/- <td>1,800ft. 28/6 <td>2,400ft. 47/6 </td></td>	1,800ft. 28/6 <td>2,400ft. 47/6 </td>	2,400ft. 47/6

SPECIAL BARGAIN. 3in. Message Tape, 150ft., 3/9. P. & P. 6d. 3in. L.P. 225ft., 4/8. 3in. D.P. 30 ft. 5/6. Plastic Spool Containers ... 3in., 1/3; 5in., 2/-; 5 1/2 in., 2/-; 7in., 2/8; 7 1/2 in., 1/9; 5 1/2 in., 2/-; 7in., 2/8

TRANSISTOR COMPONENTS

Midget I.F.'s—465 Kc/s 9/16in. diam. first, second or third. 5/6
Osc. Coil M. & L.W. 9/16in. dia. 5/-
Midget Drive Trans. 9d. 6/-
Midget Output Trans. Push-Pull 8 ohms 6/-

Elect. Condensers—Midget type 1mFd-50 mFd ea. 1/9, 100 mFd. 2/6-12V. Wkg. 15 Choke, 2/6 each. Condensers 150 v. working: .01 mFd., .02 mFd., .03 mFd., .04 mFd. 9d.; .05 mFd., 1 mFd. 1/-; 25 mFd., 1/8; .5 mFd., 1/8, etc.

Midget Tuning Condensers. J.B. "OO" 208 pF and 178 pF, 8/8, ditto with trimmers, 9/8. J.B. 220 pF and 105 pF conc. slow motion 10/6, 335 pF single 7/8. Sub. min. 3in. Dia/min 100 pF, 300 pF, 500 pF, 7/- each.

FERRITE AERIALS. M. & L.W. car aerial coil 9/8.

Midget Volt. Control with edge control knob, 5 or 10 K/ohms, with switch 4/9; Ditto less switch 3/9s.

Speakers: P.M., 2in. Plessey 75 ohms 15/6, 2 1/2 in. Continental 8 ohms, 13/8. 7 x 4in. Plessey 35 ohms, 23/6.

Ear Plug Phones—Min. Continental type 3ft. lead, jack, plug and socket. High Imp., 8/-, Low Imp., 7/6.

DE-LUXE RECORD PLAYER KIT



Incorporating 4 Sp. Garrard Auto-3 1/2 min unit and Mullard latest 3 watt printed circuit amplifier (ECL 86 and EZ 80), vol. bass and treble controls, with 8" x 5" 10,000 line speaker. Contemporary styled 2-tone cabinet, charcoal-grey and off-white with matching blue-relief. Size 17 1/2" x 16" x 8". A stylish unit capable of quality reproduction. Circuit and const. details 2/6 (free with kit).

COMPLETE KIT £13.19.6
Carr. and Ins. 12/6. Ready wired 90/- extra. Illuminated perspex control panel scotchwood, 7/6 extra. Four contemporary mounting legs 6in. 10/8; 9in. 11/8; 12in. 12/6 extra.

Electrolytics All Types New Stock	
TUBULAR	CAN TYPES
25/25V	1/9 8-8/450V 4/6
50/125V	1/9 16+16/450V 5/6
60/30V	2/- 32+32/275V 4/8
100/25V	2/- 50+50/350V 6/8
3450V	2/3 60+250/275V 12/8
4350V	2/3 100+300/275V 12/8
16+16/450V	5/8 2000+4000/6V 3/6
32+32/450V	6/8
1000/25V	8/8

Erskin Multicoore Solder 60/40, 4d. per yard. Cartons 2/6, etc.



Est. 1949

We manufacture all types Radio Mains Trans., Chokes, Quality O/P Trans., etc. Enquiries invited for Specials. Prototypes for small production runs. Quotations by return. Send for detailed bargain list, 3d. stamp.

RADIO COMPONENT SPECIALISTS

70 Brigstock Rd., Thornton Heath, Surrey. Hours: 9 a.m.-6 p.m., 1 p.m., Wed. THO 2188. Terms C.W.O. or C.O.D. Post and Packing up to 1 lb. 1/-; 1 lb. 1/9; 3 lb. 3/-; 5 lb. 3/9; 8 lb. 4/6.

R.S.T. VALVE MAIL ORDER CO.

144-146 WELLFIELD ROAD, STREATHAM, S.W.16

All valves
brand new
and boxed

Mon.—Sat. 9 a.m.
—5.45 p.m.
No Early Closing
Open Daily to Callers
Tel. STR 0199, 1649

0A2	5/3	6BH6	7/-	6K7G	1/6	7Y4	5/-	20F2	11/-	78	4/6	DK32	7/9	ECH91	19/-	EM84	6/-	PC189	10/-	S180	10/-	UL84	5/6
0C9	5/1	6BJ9	7/6	6K7GT	4/6	7Y6	8/-	20L1	15/-	80	5/1	DK91	5/1	ECH92	13/-	ESU150	20/6	PC189	6/6	SP4	9/-	UM80	1/6
1A7	7/9	6BQ7A	7/6	6K8M	8/6	10C1	12/6	20P4	14/-	85A2	8/6	DK92	7/9	ECH42	8/-	EY91	6/-	PCF82	6/6	SP41	1/6	U6	13/6
1B5	6/1	6BR7	10/6	6K8G	3/-	10C2	12/6	20P5	12/-	150B2	14/6	DK96	6/6	ECH81	5/6	EY86	6/3	PCF84	5/1	SP61	1/1	UU7	13/6
1H5	7/6	6BR8	7/6	6K8GT	3/3	10F1	12/6	2E6	6/6	150C4	12/6	DL70	7/6	ECH83	6/6	EZ35	4/3	PCF86	8/6	SC25	19/6	UD9	8/-
1LD5	5/-	6BS7	15/-	6K25	20/-	10F8	12/-	25L6GT	4/6	801	5/-	DL92	4/9	ECL80	6/6	EZ40	5/6	PCF801	9/9	SC2150	12/6	UY21	7/6
1N5GT	8/1	6BW8	6/6	6L1	9/6	10F9	9/9	25Y5	6/-	807	7/9	DL98	3/6	ECL82	6/6	EZ41	8/-	PCF802	8/9	T41	9/-	UY41	4/6
1R5	5/-	6BW7	8/6	6L6G	7/-	10F18	8/-	25Z4	6/3	818	80/-	DL94	6/-	ECL83	8/6	EZ60	6/6	PCF805	10/6	T44	7/-	UY85	4/9
184	5/-	6C4	1/9	6L18	7/6	10L1	19/-	25Z5	7/-	866	86/-	DL96	6/6	ECL86	8/6	EZ81	3/6	PCF808	12/6	T411	20/-	VMP4G	17/-
1T4	2/6	6C6	3/9	6Q7G	5/6	10L12	11/6	25Z6	8/6	954	4/-	DL98	6/6	EF9	20/-	EZ80	8/6	PCF808	12/6	U10	7/-	VP4B	27/6
3A4	3/6	6C8	3/9	6Q7GT	9/-	10P19	12/6	25D7	5/-	1625	5/-	DM70	5/-	EF36	3/-	EZ82	9/-	PCL82	6/6	U14	7/-	VR106/305/-	
3Q4	6/6	6CD6G	22/6	6SC7	6/6	12A7E	4/6	30C1	6/6	4022AR	15/-	DY98	7/-	EF37A	9/6	EZ84	8/9	PCL83	8/9	U19	30/-	VR150/305/-	
3Q5	6/6	6CH6	8/-	68C7	4/-	12A7T	3/3	30C15	9/6	5763	10/6	DY87	7/9	EF39	5/-	EZ86	22/6	PCL84	7/-	U25	10/-	VT25	28/-
384	4/9	6CW4	14/-	68H7	2/6	12A7U	5/9	30F5	9/-	7193	1/8	B88C	14/-	EF40	6/6	EZ87	17/6	PCL85	7/6	U26	10/-	VT31	58/-
3V4	6/-	6D6	2/9	68T7	5/-	12A7V	5/-	30L11	10/6	7475	2/6	EA50	2/-	EF50	2/-	EZ88	30/-	PCL86	8/9	U78	8/6	VU111	6/-
5R4G	8/-	6E5	5/9	68K7GT	4/9	12AX7	4/6	30L15	12/6	ATP4	1/9	EAB06	5/6	EF80	4/6	EZ89	4/6	PCF84	10/-	U191	11/6	VU120	9/-
5T4G	4/-	6F1	9/-	68N7GT	4/9	12BA6	6/-	30L17	12/6	ATP7	4/6	EB41	4/6	EF86	6/6	EZ90	4/6	PCF84	20/-	U251	11/6	VU508	25/-
5V4G	8/-	6F5G	5/-	68N7GT	4/9	12BE	4/9	30P12	10/-	ATC2	30/-	EB91	3/-	EF89	4/6	EZ91	4/6	PEN45	6/9	U301	12/-	WS1M	5/-
5Y3GT	4/6	6F6G	4/-	68Q7	10/-	12BH7	5/9	30P19	14/-	AC5	6/-	EB92	6/6	EF91	2/9	EZ92	4/6	PEN46	2/9	U409	6/6	X78	26/6
5Z4GT	8/-	6F8G	4/6	6U4GT	10/-	12C8GT	7/6	30P21	11/-	AZ1	8/9	EB94	6/6	EF93	2/9	EZ93	2/9	PL39	5/9	U801	18/6	X79	41/-
6A7	15/-	6F13	12/6	6V6G	7/6	12D1	19/6	30P23	12/6	AZ31	7/9	EB96	3/6	EF98	10/-	EZ94	12/6	PL81	7/-	U803	6/6	XK1-5	5/-
6A8G	19/6	6F14	12/6	6V6G	6/6	12J7GT	7/3	30P24	12/6	CBL31	25/6	EBF80	5/-	EF183	6/6	EZ95	6/6	PL82	5/9	U812	7/6	XP1-5	5/-
6A7C	3/-	6F23	9/6	6V6GT	7/-	12K7GT	3/-	35L6	5/9	CL38	12/6	EBF89	5/9	EF184	6/6	EZ96	6/6	PL83	6/-	U813	6/6	XS01-5	10/-
6AK5	4/6	6G6	2/6	6X4	3/6	12K8GT	8/3	35W4	4/9	CY31	10/-	EBL1	17/6	EF185	6/6	EZ97	6/6	PL84	6/6	U814	6/6	Y63	7/6
6AL5	3/-	6H6	1/8	6X6G	4/9	12Q7GT	3/-	35Z3	10/-	DAC92	7/6	EBL2	10/6	EF186	6/6	EZ98	6/6	PL500	14/6	U815	5/9	Y63	7/6
6AM5	2/6	6J5M	6/6	6X9GT	3/9	12S47	6/6	35Z4GT	3/9	DAF91	3/3	EBL3	27/6	EF187	6/6	EZ99	6/6	PL501	14/6	U816	5/9	Y63	7/6
6AM6	2/9	6J5G	2/6	7B6	11/-	12S47	3/6	35Z5	5/8	DAF96	5/-	EBL4	7/3	EF188	6/6	EZ100	6/6	PL502	14/6	U817	5/9	Y63	7/6
6AQ6	6/-	6J5GT	4/9	7B7	7/-	12SH7	2/9	37	5/-	DEC90	8/-	EBL5	4/6	EF189	6/6	EZ101	6/6	PL503	14/6	U818	5/9	Y63	7/6
6A87	22/6	6J6	3/-	7C6	10/-	12SJ7	3/9	42	4/8	DEC93	8/-	EBL6	4/6	EF190	6/6	EZ102	6/6	PL504	14/6	U819	5/9	Y63	7/6
6A7E	3/6	6J7M	8/6	7C6	6/-	12SK7	2/9	50B5	6/6	D770	2/6	EBL7	4/6	EF191	6/6	EZ103	6/6	PL505	14/6	U820	5/9	Y63	7/6
6A6U	6/-	6J7G	4/3	7D5	8/-	12SR7	5/-	50C5	6/3	DF91	2/9	EBL8	5/8	EF192	6/6	EZ104	6/6	PL506	14/6	U821	5/9	Y63	7/6
6B8G	20/-	6J7GT	8/6	7H7	5/-	12ST7	20/-	50CD6G	35/-	DF92	5/9	EBL9	5/8	EF193	6/6	EZ105	6/6	PL507	14/6	U822	5/9	Y63	7/6
6BA5	4/9	6K9GT	5/-	7R7	19/6	19A05	7/6	60L6GT	5/-	DF96	25/-	EBL10	5/8	EF194	6/6	EZ106	6/6	PL508	14/6	U823	5/9	Y63	7/6
6BE6	4/9	6K7M	5/-	787	18/6	20D1	10/-	75	5/-	DH77	8/6	EBL11	6/6	EF195	6/6	EZ107	6/6	PL509	14/6	U824	5/9	Y63	7/6

SPECIAL 24 HOUR SERVICE
OBSOLETE TYPES A SPECIALITY
QUOTATIONS FOR ANY VALVE NOT LISTED
Postage 6d. per Valve C.V.O. No C.O.D.
Send S.A.E. for list
Manufacturers and Export Inquiries Welcome

Special 24 Hour
Express Mail
Order Service

DAF91	DF91	DK91	DL92	DL94	Set of 4, 19/-
DAF96	DF96	DK96	DL96		Set of 4, 25/-
BRAND NEW TRANSISTORS					
AF114	9/-	OC35	3/6	OC82D	6/-
AF115	7/-	OC24	3/6	OC83	6/-
AF116	8/-	OC45	3/6	OC81M/pr	7/6
AF117	5/6	OC71	4/6	OC200	8/-
OC25	11/-	OC72	6/-	OC81D	4/-
OC28	16/-	OC75	6/-	OC82	6/-

PLEASE NOTE OUR NEW ADDRESS

UNDOUBTEDLY THE FINEST RANGE OF TAPE EQUIPMENT ON THE MARKET FROM **Kedoco**

COMPLETE HI-FI TRANSLATORISED TAPE RECORDING SYSTEM FROM 12 VOLTS
IDEAL FOR BUILDING A TAPE RECORDER IN YOUR CAR OR A PORTABLE UNIT.
NOTE THESE OTHER STAR FEATURES ★ LOW POWER CONSUMPTION ★ SMALL SIZE ★ COMPLETE FLEXIBILITY IN DESIGN FROM SEVEN BASIC UNITS

TAPE PRE-AMP SSTR/7

All silicon transistor. Zero hum. High gain and equalised at 7 1/2 per sec. to give flat response output. Simple mod. described in accompanying instructions allows equalisation at all speeds. Suitable for all medium impedance heads, Collaro, B.S.R. etc. **29/6**
ASSEMBLED

MINICLASSIC PRE-AMP SSPA/50

Tone controlled high gain pre-amplifier designed specially for application with the SS3/10. All silicon transistor. Zero hum, requires 12 volt + H.T. High Fidelity complete with tone and volume controls. Separate inputs for crystal ceramic cartridge and radio. **39/-**
ASSEMBLED

RECORD PRE-AMP SR/3

High gain pre-amplifier designed for use with SSH9/3. Record amplifier will work directly from radio. pre-amp matches to any ribbon or dynamic microphone. **29/6**
ASSEMBLED

RECORD AMPLIFIER SSH9/3

Fully transistorised. High voltage H.T. rail derived from oscillator. Provides substantially constant current record signal. 1 volt input sensitivity. Power consumption 1ma at 12 volts and 1ma at 75 volts. Latter derived from erase oscillator SSO13. **45/-**
ASSEMBLED

POWER SUPPLIES

12 volt, 1 amp and designed to supply complete tape system. 30 volt, 3 amp designed to power Kedoco hi-fi 20 watt power amplifiers.
12 volt 59/-, 30 volt 69/-.



MINICLASSIC SS3/10

High fidelity 4 watt main amplifier; ideal for use with SSTR/7 and makes complete tape amplifier. 16 c/s to 30 kc/s. Requires 12 volt + H.T. and will operate directly from crystal pickup. 8 transistors and two diodes all mounted on precision printed circuit board. Max. music power 4 watts into 3 ohm speaker. **69/-**
ASSEMBLED

MINICLASSIC SS3/10 similar to SS3/10 but requires 18volts and gives greater power. 6 watts peak. Also 69/-.

TAPE OSCILLATOR SSO13

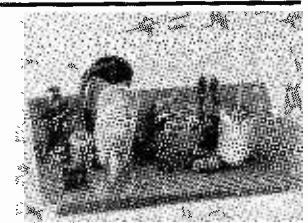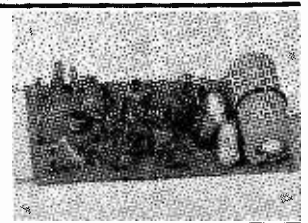Complete unit incorporating push pull transistor oscillator giving adequate erase power and recording bias. Ferrite pot core push-pull oscillator, frequency 60-60 kc. All silicon transistor. Provides high voltage (75v.) D.C. Rail for operating record amplifier. High efficiency unit requiring 12v. D.C. at 20ma. The only unit of the market at such an economical **69/-** price. COMPLETE



ORDER FORM To KEDOCO ELECTRONICS, BEVERSTONE WORKS, TETBURY, GLOS.

Please supply.....

Address.....

Enclose Cheque/P.O. for.....


All KEDOCO products are fully guaranteed and should you not be completely satisfied with your purchase we will gladly refund your money if returned within seven days of receipt.

KEDOCO ELECTRONICS also manufacture a range of 20 watt hi-fi amplifiers. SS207 at 19/6. SS208 at 11/6. SS209 at 11/6. SS210 at 11/6. ★ Subminiature FM Radio Microphone. SS007, 189/- (standard power). SS008, 213. ★ (Extra power). 4V/FM Booster battery operated, bands 1 and 2, 32/3. De Luxe mains model, band III, 42/-. ★ Transistors. Zeners, Resistors and Capacitors. See Practical Electronics for details of these other exciting Kedoco Transistorised products or send S.A.E. for leaflets.

the input sockets to VR2 and VR3 and should be pushed into their respective corners to minimise cross-coupling both mutual and with V4. It is desirable for each stage to have its own earthing point. R1, R2 and the two cathodes of V1 are connected to an earth tag adjacent to V1, to which is also connected the wiper of VR1. R5, R6 are earthed to a tag adjacent to V2, whilst the earthy ends of VR2 and VR3 are connected to a tag adjacent to V3. The centre spigots of V1, V3 and V4 are earthed to their adjacent tags, that of V2 being used as an h.t.+ tie point. This is contrary to commonly accepted practice and was adopted as a convenient way of wiring the various resistors that connect to the h.t. line. R7 is a 1.5 or 2W component and is spaced away from the other components in order that it may safely dissipate its heat. R11, R12 and R13 are connected end-on to the valveholder so that they point towards the sig. o/p socket to which their junction is connected. On the rear panel wiring C18 is held by a clip and has C19 wired across it. The earthy ends of both should be connected to an earth tag on the main chassis. R16, which generates some heat, should be connected between the live end of C18, C19 and a stand-off tag and spaced away from other adjacent components.


The wiring when completed should be checked over for mistakes (we all make them sometimes!) and the gate can then be tried out. The static voltages should be measured with a 20k/V meter and should agree reasonably closely with those given on the circuit. The voltages on V1 anodes were measured with VR1 at its central position and with S1 at the 1,750c/s position. All the other voltages were measured with S1 at "off". At no time was an external signal fed into the Y1 and Y2 input sockets.

The gating square wave should be checked on the oscilloscope and should appear to be reasonably square. Some sag at the 50c/s position and some rounding off at 5kc/s may be evident but is not worth worrying about unless it is really severe. If the square wave does sag or round off to an excessive extent the oscilloscope can also be suspect unless it is known to have a first-class transient response. Rotating VR1 should cause the positive and negative peaks to transpose, the output being at or near zero

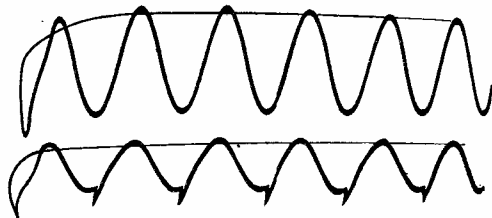


Above—Y1 trace-sine wave as generated 10kc/s. Y2 trace below it is as reproduced at 10W by a 10W amplifier

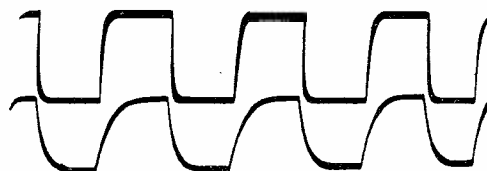Below—Illustration of gating action. Distortion at left due to excessive sync.



Above—25kc/s square wave, rise time $2\mu\text{s}$. Lower trace, ditto reproduced at 1W by a 10W amplifier

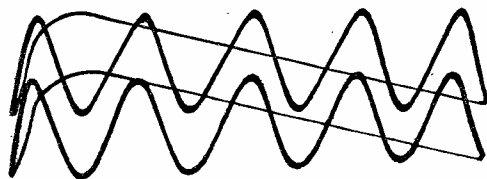Below—200kc/s sine wave fed into both inputs. Gating speed 17kc/s approx.



with VR1 at its mid position. The fact that VR1 is at its mid position for this check shows that the two halves of V2 and V3 are reasonably equal in respect of gain.

If all seems in order the gate can be checked for correct operation. In order to do so the gate's output should be coupled to the oscilloscope input using a short length of coaxial and not ordinary screened wire which has an excessive shunt capacity. The sync o/p should be connected to the "ext sync" input of the oscilloscope. For preliminary tests it is convenient to temporarily connect the Y1 and Y2 inputs in parallel, thereby feeding the same signal to both. This signal should be of fixed frequency and amplitude since this type is the easiest to display. It is most undesirable to experiment with varying or different input signals until some familiarity with the gate's *modus operandi* has been gained, for too many inputs, particularly those varying in frequency or amplitude or both, such as an audio signal, will only tend to confuse.

The oscilloscope's Y amplifier should be set for maximum sensitivity and the timebase adjusted to display a few complete cycles of the input signal. The Y1 and Y2 gain controls can be adjusted as necessary. By setting the oscilloscope's vertical amplifier at its most sensitive position the chances of overloading the gate's amplifier stage is avoided and, also, the separation control need not be used at the ends of its travel, thereby avoiding any possibility of introducing any distortion into the signal due to excessive over or under biasing. Rotating the separation control should cause the two traces to separate, to merge and to transpose without any distortion being evident. If it is the gate should be bypassed and the signal examined directly on the oscilloscope. The effect of the different gating speeds should be noted and then different inputs can be tried, S2 being used to select the input that provides the best sync. If a steady image is difficult to obtain it may be due to it having a direct harmonic relationship to the gating speed and a different gating speed should be tried.

The amount of advice that can be put into print is of necessity limited, whereas careful experiments on the part of the user are not. The operation of the gate is by no means difficult, though it may appear so to the novice. Obviously familiarity with an ordinary oscilloscope is of inestimable value, for then the gate is but an extension of it. ■

practically wireless commentary by HENRY

THERE used to be a fellow down our street who could never put a finger wrong. He was always in demand. Replacing washers, knocking up pelmets, changing tyres or gaskets, putting in windows; from electric bells to herbaceous borders, it was all the same to Mr. B.

He called at the shack to borrow a file, just as I was in the middle of a ticklish piece of amplifier building. "Your fuses—cor!" said Mr. B expressively.

Now it isn't that Henry cannot tackle a blown house-fuse. My wife had called in Mr. B to help with the constructional aspect—replugging the wall. Somehow, when Henry gets hold of a hammer the theory of Relativity takes a twist. I am happier with a soldering iron.

★ ★ ★

In fact, I was wielding that familiar instrument as Mr. B leaned against the shack door, scraping at the blade of his grub screwdriver. He watched my clumsy efforts for a while.

"Why don't you use a clothes-peg to clamp those bits together?" he asked. "Easier than burning your fingers," he added, as I sucked.

Like all the exasperating Mr. B types, he was quite right. Henry just hadn't thought about the



Easier than burning your fingers

simple expedient. Another case of Shute's Mr Honey and the dish-mop. Yet Mr. Honey, faced with the prospect of having to resign from aeronautical research at Farnborough, had been sure of a job at the National Physical Laboratory.

Makes one wonder how many of these industrial computerised assemblies, with their sophisticated servo devices, could be supplanted by a part-time Mr. B with Ready Reckoner in the back pocket of his overalls, and pencil stub behind his ear. Perhaps the boffins had not thought of the obvious.

★ ★ ★

A little while ago, the Autonomics Division of the N.P.L. told us that pattern recognition machines were still a long way short of the ability of the human eye. To quote: "The outstanding performance of the human brain underlines the gap between nature and cybernatic artefacts".

Well, our Mr. B wouldn't know a cybernatic artefact from a wooden leg! But even he could tell at a glance that Auntie Maud's postcard about the weather and her arthritis really meant she would not be coming to babysit next Friday—which is more than any computer could do, despite all its epitoxical semi-planar micro-module flip-chips.

It all comes down to practical know-how in the end. Down to Mr. B with his odd bits of wire and a dash of ingenuity. Soft-landings on the moon are one thing, but without some equivalent comrade B-ski to polish the old solar cells, Lunik 1X would hardly have got so far as a lift-off.

★ ★ ★

What I am getting at—hold your seats, lads, Henry is approaching the point—is that there will always be room for the capable technician. No matter

how complex the design conception, some cost-conscious manufacturer is going to build in a few faults with his flap-happy printed boards and haystack-wired components.

★ ★ ★

In a recent review of a very expensive tape recorder, the remark was made that had it not been for the outstanding performance the machine would



Without some equivalent Comrade B-ski to polish the old solar cells.

have been returned to the maker on account of its atrocious construction. Performance, for how long, Henry would like to ask?

One of our esteemed contemporaries has bemoaned the shortage of "skilled labour" coming forward to answer the adverts of some electronics giants. May we suggest they are aiming too high. Instead of recruiting graduates to refine even more sophisticated hardware, flashing their sliderules for brief spasms, then sitting over the Mephisto crossword while they wait for Mr. B to mend the fuses, we suggest they advertise in these pages for a few "practical types" with enough working knowledge of electronics to take the mysteries within those magic black boxes in their stride!

RADIONIC

IF YOU ARE AN EXPERIMENTER
YOU TEACH RADIO OR ELECTRONICS
YOU ARE A BEGINNER
YOU NEED RADIONIC

Unique and brilliantly simple. Hundreds of educational establishments—Universities, Technical Colleges, Schools, the Armed Forces—are already using Radionic for electronic instruction. Enthusiastic owners range from 9 to 82 years of age. Selected by the Council of Industrial Design for all British Design Centres. Featured in Sound and Television broadcasts.

The system is beautifully engineered from top quality British components. No soldering. No mains. No prior knowledge needed. Simply arrange components on perforated transparent panel, position brass connecting strip underneath, fix with 6BA nuts and circuit works with full efficiency. You can then dismantle and build another circuit. Your results are guaranteed by our Technical Department and News Letter Service. All parts available separately for conversion or expansion of sets.

UNIQUE! Our "No soldering" printed circuit board for superhet portable. Simply insert components and tighten nuts.
 No. 1 Set £5.18.6 14 Circuits (Earphone)
 No. 2 Set £6.19.6 20 Circuits (Earphone)
 No. 3 Set £10.19.6 22 Circuits (7 x 4in, Loudspeaker output)
 No. 4 Set £14.19.6 26 Circuits (include 6 Transistor and reflex superhets)

Prices (Post Free)


Full details from:

RADIONIC PRODUCTS LIMITED
 STEPHENSON WAY, THREE BRIDGES
 CRAWLEY, SUSSEX


Tel.: CRAWLEY 28700

Trade Enquiries Invited

RADIO & ELECTRONIC CONSTRUCTION SYSTEM

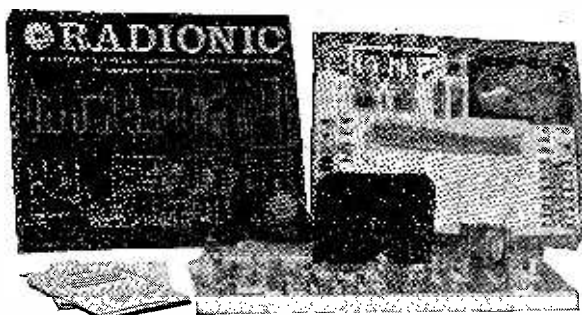

A No. 4 SET and 6-TRANSISTOR SUPERHET

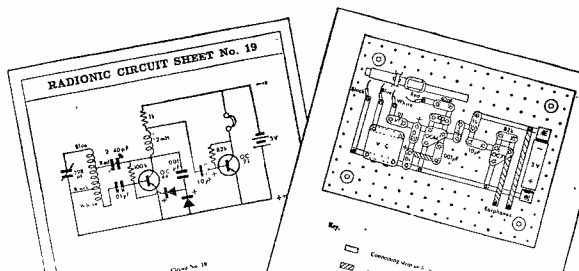

Theoretical Circuit

Practical Layout

Our 'E' Series of basic electronic circuits is available separately. Send for details of E/508 our do-it-yourself computer.

THE Radio Constructor

BUILD THESE

- ★ TRANSISTORISED A.C. MILLIVOLTMETER
- ★ ECONOMY PARKING LIGHT CONTROLLER
- ★ HOME OR OFFICE INTERCOM


IN ADDITION many other first-rate constructional projects are included in the

APRIL ISSUE NOW ON SALE
PRICE 2/3

THE **Radio Constructor**

AMATEUR RADIO CHAS. H. YOUNG LTD.

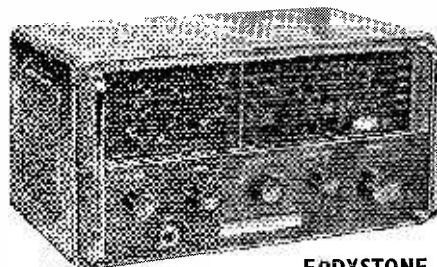The Sensational
ALL-TRANSISTOR!
 Communications Receiver



EDDYSTONE EC10

for use in the home, caravan, car or boat, H.P. facilities. Only £48 Part exchanges.

Write for brochure

170-172 CORPORATION STREET
BIRMINGHAM 4
 Telephone CEN 1635

SERVISCOPE MINOR



Extend the range of your present test instrumentation with this versatile Teleequipment oscilloscope. Simplified operation—minimum controls, automatic time base synchronisation—but top quality construction. 2.75" tube with graticule, contrast filter and rubber light hood. Bandwidth DC-30Kc/s (-3dB); maximum sensitivity 100mV/0.5cm division. Time base continuously variable from 100usecs to 100msecs per 0.5cm division. Mains operated, fully portable. Instruction manual supplied. Descriptive leaflet on request.

Obtainable only direct from the country's largest specialist manufacturer of portable oscilloscopes for science and industry.

Serviscope is a registered trademark

TELE-EQUIPMENT

Teleequipment Ltd., 313 Chase Rd., Southgate, London N.14
Tel: Fox Lane 1166

Please send me, without obligation, the descriptive leaflet on the Serviscope Minor.

NAME.....

ADDRESS.....

PW/5

RESISTOR OFFER

100 GRADE I ASSORTED RESISTORS
5% TOL. 22Ω-2.4M, ½ to 3 WATT.

11/- post inc.

200 AS ABOVE £1 post inc.

1,000 AS ABOVE £5 post inc.

UNREPEATABLE THIS MONTH ONLY

50 1% ASSORTED 49/11 post inc.

Below are just a few of the many items listed in our Surplus Catalogue. Send us your name and address and we will enter you on our FREE Mailing List.

Cat. No. **G12. SPRAGUE** 0.5μF 6000 D.C. tubular condensers at your price 8d., p.p. 6d.
R.C.A. 20 + 20 mFd 450v. D.C. tag mounting condensers—ideal for smoothing circuits 4/-, p.p. 1/6.
G11 METALMITE 0.1 mFd 350v. D.C. 7d., p.p. 6d.
G19 Ceramic 50pF pre-set variables, small type 115 Ceramic, 15pF as above 2/6, p.p. 6d.
G3. One 65-140 mFd ceramic semi-variable condenser plus 3-13pF compression padder trimmer mounted on right angle chassis bracket, ready drilled—perfect for V.F.O.s—SSB—still in the boxes. 3/11, p.p. 1/6.
H26 455Kc/s general purpose I.F. transformers, brand new in boxes, 50+50pF metal-air spaced variables in magnificent condition. 3/6 each or two for 6/6, p.p. 1/-.
F20 10Ω wire wound variable resistors, suitable for speaker muting, etc. 1/9, p.p. 1/-.
Ceramic I.O. valve bases 3d., p.p. 6d.
Ceramic B79 valve bases—can fitting 6d., p.p. 6d.
Multi-purpose **DIMMER SWITCHES**, perfect for lighting, motor speed and a thousand and one uses in control circuits special price. 1/6, p.p. 9d.
V.H.F. I.F. Transformer—small, brand new, contains 2 x ¼ in. dia. Aladdin formers with nine turns each of 18swg and padders of 110pF individually screened, reduced price 2/6, p.p. 6d.
RR7 2-METRE EQUIPMENT—transmitter type 1985, with crystal and valves, as new condition—few only—a real bargain—conversion details have appeared in many popular magazines. 9.72Mc/s I.F. 15/-, p.p. 4/-.
Modulator Unit for above, almost new, miniature valves. Would make a good modulator on its own or with TX1985 15/-, p.p. 4/-.
SPECIAL PRICE 25/- the pair, p.p. 4/-.
Modulator Units as above—no guarantee—can be made to work. Parts worth more than our price or 5/-, p.p. 1/9; must clear.
Single pole single throw switches with self return action, perfect for "test" or "net" switches. 1/11, p.p. 6d.
Single pole single throw panel mounting switches, bakelite toggle—ceramic insulation. **BULGIN** 2/9, p.p. 6d.
LAI FERROXUCUBE ferrite pot cores at less than half the normal price. 8/6, p.p. 9d.
G89. 26-way tag boards, double edged, 2½ in. wide—new 1/6, p.p. 6d.

OUR BEST BARGAIN YET—

Buy a Type 35 Twin Speed, Slow Motion Drive unit, originally intended to increase the bandspeed of the R.1155 but are just as efficient on any receiver—easy mounting—finished in attractive, polished black bakelite—a really professional job—NEW 8/11, p.p. 1/6

BE WISE—DIODEISE !



ST14 is a semiconductor equivalent for valve series **5Z4, 5V4, 5Y3, 5U4, 5W4, etc.**

ST14 employs built in surge limiter — instant warm up — no drift!

ST14 is space saving, has an almost indestructible casing—professional finish.

ST14 is suitable for Audio, Radio, Amateur, HiFi and Electronic equipment.

ST14 is supplied — packed — with full details.

ST14 is 55/- (c.w.o. inc. p.p.)


All our terms are strictly Cash with Order—Postage as indicated.

ST14 is one of the most efficient rectifiers ever invented. **ST14** will fit any rectifier circuit within normal HT ratings. **ST14** is no gimmick but a standard production unit from the U.S.A. which is fast gaining popularity in this country.

K. L. DISTRIBUTORS

"Run by Enthusiasts for Enthusiasts."

6 WINDSOR ROAD TODMORDEN LANCs

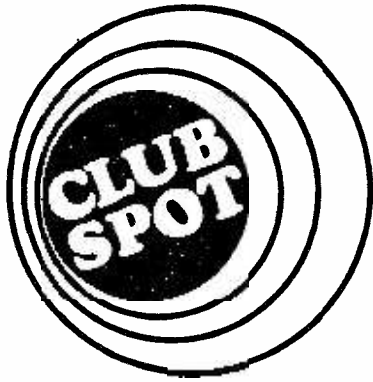

No. 7


VERULAM AMATEUR RADIO CLUB

G
3
S
T
A

THE Verulam Amateur Radio Club came into being towards the end of 1961 when a short wave listener, Brian Cockell, conscientiously, worked through the R.S.G.B. call book, extracted the names of and addresses of some 100 local "Hams" and wrote to each one individually inviting them to a rendezvous at the "Red Lion", St. Albans, with the object of forming an amateur radio club, and partaking of wine in the process.

His efforts were most successful and a committee was duly elected under the steadying hand of C. F. Thomas, G3EKU, whose connection with radio goes back to World War 1, while at one stage he held an Artificial Aerial licence and was connected with airships.

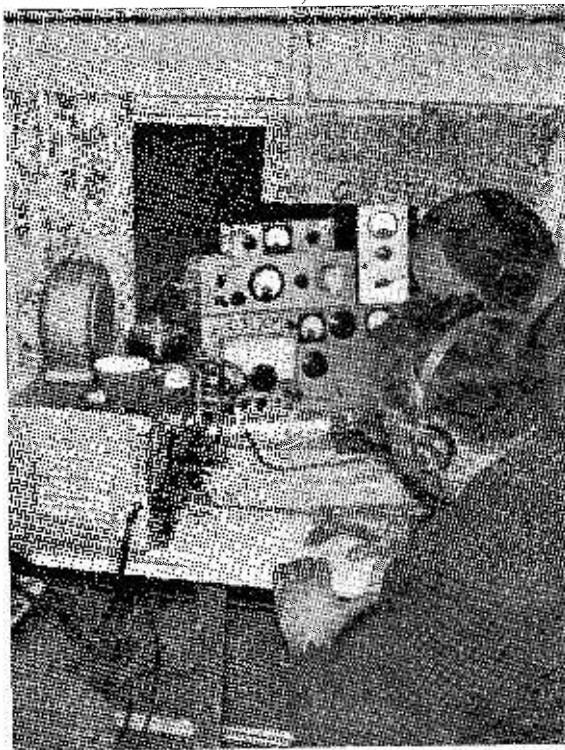The Club membership, which is steadily rising, includes some 36 licensed operators. Meetings are monthly at Hedley Road, St. Albans, where visitors



Affiliated Societies Contest last year. Logging G3LXP, on the key G3JDG. Gear, "LXP" 10 watt Tx, s.w.r. bridge, Z match, 888A.



Two hours to go and the coax on the Cubical Quad comes adrift, one of the many incidents on NFD.

are always welcome and a quick word with the Secretary G3PAO, 6, Leggatts Wood Avenue, Watford, Herts. (WATford 25526) will bring full details.

Club finances are under the watchful eye of our lady treasurer Miss P. Connelly who incidentally is also licensed. Her "stirling" efforts include creeping across a dark meadow last year at three in the morning to operate in V.H.F. Field Day.

The Club's "newspaper" consists of a monthly news sheet sent to all members, edited by G3LXP and dispatched piping hot from the press by our "printer" Wilf Whitehouse G3SKB.

A regular feature is the Club "Owls Net" on 1980kc/s, Saturdays. This usually starts up about 10.30 p.m. with everybody "having to cut it short tonight", and finishing with a final ragchew around 2.0 a.m.

Most contests are entered including N.F.D. V.H.F.N.F.D., M.C.C., etc. Last year a small group of keen types went on safari to nearby Salisbury Hall to rig up a station and take part in the Top

Continued on page 66

OSCILLATOR CIRCUITRY

R. Leyland

3—A.F. OSCILLATOR NETWORKS

THE only kind of waves that can pass through phase-shifting networks without distortion are sine waves. However, changes do take place in their amplitude and phase. The output wave is usually smaller in amplitude and shifted out of synchronism by a fraction of a cycle, or so many degrees.

It is convenient to represent a sine wave by an arrow called a complexor. The length of the arrow (see Fig. 1) is the peak amplitude of the wave, and by turning the arrow through the corresponding angle, the level at any other point of the wave is


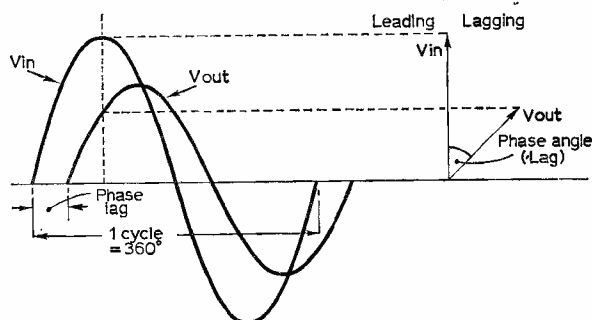


Fig. 1: Method of representing the attenuation and phase shift of a sine wave by means of a complexor diagram.

Fig. 2: The frequency responses of (a) high pass; (b) low pass networks.

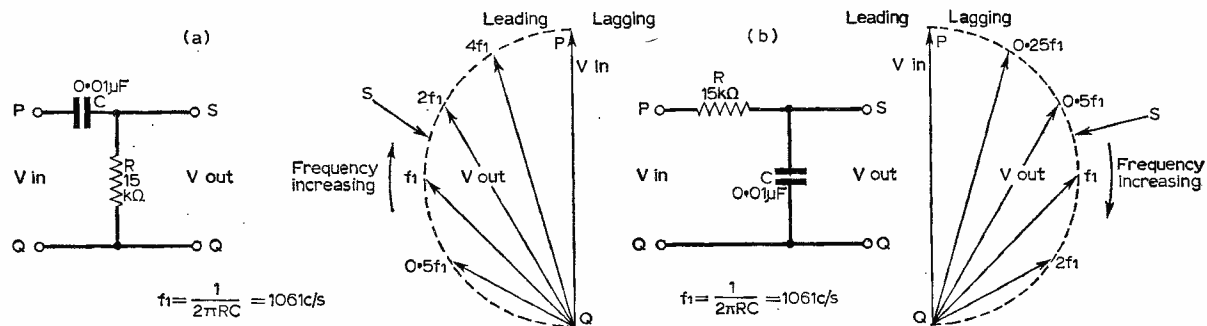

obtained. A vertical complexor represents the input to the network, and another tilted complexor, shorter in length, represents the output. The angle between them is the amount of phase shift.

There is no phase shift in a network containing only resistance, but a capacitor stores and releases

energy, and this causes its current to lead the voltage by 90°. When the current from a capacitor passes through a resistance, the voltage across the resistor will be 90° ahead of the voltage across the capacitor. If, as in Fig. 2(a), the output is from across the resistor, it will lead the input voltage, although by less than 90°. On the other hand, if the output is from across the capacitor, the output voltage will lag on the input.

Frequency Response

The actual amount by which the output voltage wave is shifted relative to the input depends upon the frequency and, in many types of network, phase shift is accompanied by attenuation; i.e. as the phase shift increases, the output becomes smaller. The vertical arrow or complexor representing the input remains the same, but as the frequency is varied, the other complexor representing the output swings to a new phase angle and also changes in length.

In so doing, it will trace out a path or locus depending upon the type of network. Quite often the locus is circular, although in the case of the simpler networks (Fig. 2), only a semi-circle.

In the diagrams, the locus curve, dotted, shows how the alternating voltage of the output terminal marked S changes as the frequency is varied. At the points on the locus corresponding to a series of frequencies, the complexor is drawn in, giving the magnitude and phase of the output at these frequencies.

It will be noticed that the frequencies are shown

as half, twice, etc., of a special frequency, f_1 , which can be calculated from the values chosen for R and C. The value of f_1 can be altered without changing the impedance of the circuit at f_1 by multiplying only the capacitance values, since this leaves the reactances unchanged. In the formula C is in farads,

SURBITON PARK RADIO

AMPLIFIERS · TUNERS Selection

ARMSTRONG 221 10-10 watts Stereo, Mag PU and Filter. Cash £33.15.0
 Or Dep. 133/- and 8 m. pymts. 49/6 (H.P. Price £36.9.0)
 ARMSTRONG 222 10-10 watts Stereo Amplifier. Cash £27.10.0
 Or Dep. 119/- and 12 m. pymts. 40/4 (H.P. Price £29.14.0)
 ARMSTRONG 224 F.M. Tuner Powered. Cash £22.10.0
 Or Dep. 90/- and 12 m. pymts. 33/- (H.P. Price £24.6.0)
 ARMSTRONG 223 AM/FM TUNER Powered. Cash £28.15.0
 Or Dep. 115/- and 12 m. pymts. 42/2 (H.P. Price £31.1.0)
 ARMSTRONG 127 MONO 5W with AM/FM. Cash £26.10.0
 Or Dep. 106/- and 12 m. pymts. 38/10 (H.P. Price £28.12.0)
 ARMSTRONG 127 STEREO as above Stereo amp. Cash £37.10.0
 Or Dep. 150/- and 12 m. pymts. 55/- (H.P. Price £40.10.0)
 ARMSTRONG 227 MONO 10W amp. with AM/FM. Cash £36.15.0
 Or Dep. 137/- and 12 m. pymts. 58/10 (H.P. Price £39.13.0)
 ARMSTRONG 227 STEREO as above with Stereo Amp. Cash £52.15.0
 Or Dep. 211/- and 12 m. pymts. 77/4 (H.P. Price £56.19.0)
 ARMSTRONG 226 STEREO as above, but Mag. P.U. Filter Cash £61.0.0
 Or Dep. 260/- and 12 m. pymts. 88/- (H.P. Price £65.16.0)
 Teak Cases for all Armstrong Units. £3.10.0

MOTORS · PICK-UPS Selection

GARRARD SRP10 Mono. Cash £5.10.0
 GARRARD Model 1000 Mono. Cash £7.10.0
 Or Dep. 34/- and 6 m. pymts. 26/- (H.P. Price £9.10.0)
 GARRARD Model 3000 Stereo Lightweight arm. Cash £11.11.0
 Or Dep. 47/- and 6 m. pymts. 25/6 (H.P. Price £12.11.0)
 GARRARD S125 Less cart.; Single player. Cash £12.10.0
 Or Dep. 50/- and 8 m. pymts. 27/6 (H.P. Price £13.10.0)
 GARRARD AT60 Less cart.; Heavy table. Cash £13.0.0
 Or Dep. 52/- and 12 m. pymts. 19/- (H.P. Price £14.0.0)
 GARRARD LAB80 Push button oper., less cart. Cash £27.10.0
 Or Dep. 110/- and 12 m. pymts. 40/4 (H.P. Price £29.14.0)
 GARRARD 401 Transcription Table. No arm. Cash £32.10.0
 Or Dep. 130/- and 12 m. pymts. 47/8 (H.P. Price £35.2.0)
 GOLDRING G66 Mono Single Player. Cash £11.11.0
 Or Dep. 47/- and 8 m. pymts. 25/6 (H.P. Price £12.11.0)
 GOLDRING GL68 Less cart.; Pickup lift. Cash £19.10.6
 Or Dep. 78/6 and 12 m. pymts. 28/7 (H.P. Price £21.1.6)
 GOLDRING GL70 Less cart.; PU lift. Heavy table. Cash £29.15.6
 Or Dep. 120/6 and 12 m. pymts. 43/9 (H.P. Price £32.5.6)
 TERMS: C.W.O. or C.O.D. ALL ITEMS CARRIAGE FREE
 Leaflets available upon receipt of 6d. stamp

48-50, Surbiton Road, Kingston-on-Thames, Surrey
 Phone KIN. 5549 Hours 9 a.m. to 6 p.m. daily (1 p.m. Weds.)

YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.R.E. Exam.; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronic subjects only. Fullest details will be gladly sent without any obligation.

To: British National Radio School, Reading, Berks.

Please send FREE BROCHURE to:


NAMEBlock
 ADDRESSCaps.
Please
 5.66

BRITISH NATIONAL RADIO SCHOOL

HERE'S VERSATILITY FOR YOU...

The **Brenell**


MONO/STEREO HI-FI TAPE LINK

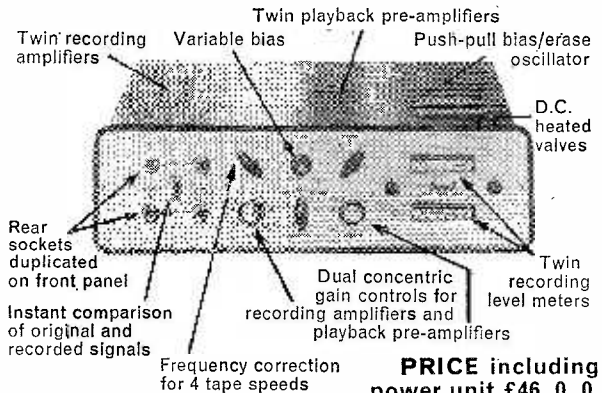

PRICE including power unit £46. 0. 0.

Designed for use with 2/2 or 2/4 track heads

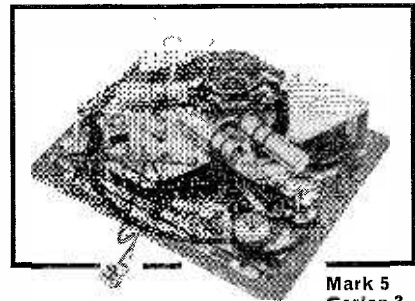Built to the same high standards as our tape recorders and decks this HI-FI TAPE LINK has been developed for use with your high fidelity equipment. It is capable of giving superb results when matched to one of our Mark 5 Series 3 decks fitted with the appropriate heads. Write for full details of this amplifier and deck and complete range of tape recorders.



Mark 5 Series 3 Deck

Brenell

BRENELL ENGINEERING CO. LTD.,
 231/5 Liverpool Road, London, N.1.
 Telephone: NORTH 8271 (5 lines)

GD378

IMPROVED

STANDARDS OF

ACCURACY AND RELIABILITY

Modern styling in light grey with legible black engraving.

Constructed to withstand adverse climatic conditions.

Ever ready case, including leads, prods and clips.

Improved internal assemblies.

Re-styled scale plate for easy, rapid reading. 2 basic scales, each 2.5 inches in length.

New standards of accuracy, using an individual calibrated scale plate: d.c. ranges 2.25% f.s.d. a.c. ranges 2.75% f.s.d.

Available accessories include a 2500V d.c. multiplier and 5, 10 and 25A shunts for d.c. current measurement.



Mk 4

MULTIMINOR

The Mk. 4 MULTIMINOR is an entirely new version of this famous Avo instrument and supersedes all previous models. It is styled on modern lines, with new high standards of accuracy, improved internal assemblies, and incorporating panclimatic properties.

The instrument is supplied in an attractive black carrying case, which also houses a pair of leads with interchangeable prods and clips, and an instruction booklet. It is packed in an attractive display carton. Robust real leather cases are available, if required, in two sizes, one to take the instrument with leads, clips and prods, and the other to house these and also a high voltage multiplier and a d.c. shunt.

D.C. Current: 100µA f.s.d.—1A f.s.d. in 5 ranges. Resistance: 0.2 MΩ in 2 ranges using 1.5V cell.
 A.C. Voltage: 10V f.s.d.—1,000 f.s.d. in 5 ranges. Sensitivity: 10,000Ω/V on d.c. Voltage ranges.
 D.C. Voltage: 2.5V f.s.d.—1,000 f.s.d. in 6 ranges. 1,000Ω/V on a.c. Voltage ranges.
 D.C. Millivolt range: 0—100 mV f.s.d.

● Write for leaflet

AVO LTD AVOCET HOUSE - 92-96 VAUXHALL BRIDGE ROAD - LONDON, S.W.1 - Phone: VICToria 3404



MM17

BROADWAY ELECTRONICS

92 MITCHAM ROAD, TOOTING, S.W.17

Phone: BALham 3984

(four minutes from Tooting Underground Station)

GARRARD 4 SPEED DECKS WITH CARTRIDGE: Auto-changers: AT60, £10.0.0; 3000, £8.8.8; 2000, £7.7.0; 1000, £6.6.0; Autoshim £5.5.0; De Luxe Autoshim with plug-in head, £5.15.0. P. & P. 6/ Single Players: SP25, £10.10.0; SRP12, £5.0.0; Garrard Plinth. W.B.A., £8.12.6. P. & P. 4/6 for plinth. Motor boards 6/6 each.

CARTRIDGES: Ronette Stereo 25/-; Acos GP67, 15/-; G.C.2 Garrard 15/-; AT6 shells 5/-, P. & P. 6d. HGP83/2 Stereo 20/-.

SPEAKER ENCLOSURES: "TONY" Corner Cabinet 20 x 10 x 7in., takes 10 x 6in. speaker, covered in grey Rexine and Vynair, 45/-, P. & P. 5/-. "BLAKE" Heavy Duty Cabinet with port, 24 x 18 x 9in. Baffle tin, thick. Covered Rexine and Vynair, £5. P. & P. 10/-. Extra baffle for 8 or 10in., 3/6. "BLAKE DE LUXE" veneered with wood-grain Formica and standing on smart 6in. legs, £6.5.0. P. & P. 10/-. "HAYDON" 16 x 15 x 7in., fabric covered, suitable 12in. speaker, 45/-, P. & P. 7/6. Crystal Mike 200C replaces BMS, 30/-, P. & P. 2/-. Stand for same, 9/6. P. & P. 1/6. Guitar Pick-up with Screened Lead, 12/6. P. & P. 6d. Crystal Lapel Mike, 7/6. Neon Panel Light Arcoelectric 240v. A.C., 2/6. P. & P. 6d. Tape Spools: 3in., 9d.; 4in., 1/-; 5in., 1/3; 5 1/2in., 1/9; 7in., 2/- each.

BARGAINS IN TRANSISTORS: AC127, AF 114, 115, 116, 117, 118, 119, OC169, 170, 171, 172, 5/6 each. OC72, 75, 82, 3/6. OC71, 81M, 3/-, BF Packs—1 OC44, 2 OC45 8/6. AF Packs—1 OC41, 2 OC41, 6/-, AF Pack—1 CBT118, 2 CBT119, 5/6. OC28, 28, 29, 7/6. ORP12 Light Cell, 7/6. Diodes OA81, 2/3, OA91, 1/6. P. & P. on all these 6d.

EARPIECES with cord and 3.5 mm plug, 8 ohm magnetic 3/-; 250 ohm, 4/-; 180 ohm Magnetic with clip, 6/6; Crystal, 4/-, P. & P. 6d.

SPEAKERS: ELAC Heavy duty Ceramic Magnet, 11,000 lines, 10in. round, 10 x 6, 15 or 3 ohm, 42/6. P. & P. 3/6. 8in. round 15 or 3 ohm, 38/6. P. & P. 3/6. EMI 13 1/2 x 8in. 15 or 3 ohm, 42/6. P. & P. 3/6.

Stockists for Eagle Products, Goodmans, W.B. Wharfedale, Bakers, Tripletons, Linear, all makes of amplifiers and speakers supplied. Let us quote for your requirements. S.A.E. please. NO C.O.D. Trade terms to bona fide dealers.

VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!

SETS		1R5, 1R5, 1T4, 384, 3V4, DAF91, DF91, DK91, DL92, DL94.	1R5, 1R5, 1T4, 384, 3V4, DAF96, DF96, DK96, DL96, 4 for 24/6.
1A7GT 7/6	10C3 11/6	DH76 8/6	EP85 5/-
1R5GT 7/3	10F1 9/9	DH77 4/-	EP86 6/9
1N5GT 7/9	12AT7 3/9	DH81 12/6	EP89 4/3
1R5 4/9	12AU6 4/9	DK32 7/9	EP91 2/9
1R4 4/9	12AU7 4/9	DK31 4/9	EP92 2/-
1R5 3/9	12AX7 4/9	DK91 3/-	EP93 6/9
1T4 2/3	12K7GT 3/6	DK96 6/6	EP184 6/9
8A5 6/9	12K8GT 3/6	DL33 6/9	EL33 6/6
8Q4 5/6	12Q7GT 3/6	DL35 5/-	EL38 11/9
3V4 4/9	20L1 11/9	DL92 4/9	EL41 7/9
3V4 5/6	20F8 10/9	DL94 5/9	EL84 4/9
3V4G 4/6	20P4 12/6	DL96 6/-	EL90 4/9
3V3GT 4/12	20P5 11/6	DY86 6/9	EM80 5/9
524G/GT/6/9	25U4GT11/6	DY87 6/9	EM81 7/3
630L2 8/9	30C18 8/-	EABCS0 6/-	EM84 5/9
6AL5 2/-	30E5 8/6	EAF42 7/6	EM87 6/6
6AM6 2/9	30FL1 9/6	EB41 4/-	EY31 6/3
6AQ5 4/9	30LL5 10/3	EB91 2/-	EY86 6/9
6AT6 4/-	30L17 12/-	EB93 6/-	EZ40 6/3
6BA6 4/6	30P4 13/6	EB41 6/6	EZ41 6/6
6BE6 4/3	30P12 7/6	EBF90 6/-	EZ80 4/-
6BJ6 5/6	30P19 13/6	EBF98 7/6	EZ81 4/6
6BW6 7/9	30PL1 9/6	EBF99 5/9	GZ23 12/6
6E13 3/6	30PL13 10/9	EC40 6/9	KR61 6/6
6E14 9/6	30PL14 11/-	EC61 3/9	KR63 4/-
6E23 9/6	35LAGT 6/3	EC93 4/9	N18 14/9
6K7G 1/8	35W4 4/6	EC98 7/-	N78 14/9
6K9G 4/3	35ZAGT 4/6	EC98 6/3	PC87 5/9
6K8GT 7/6	53KU 9/-	EC98 5/6	PC88 5/6
6P28 9/6	85A2 5/9	EPF80 7/6	PC89 9/9
6Q7G 5/9	6063 12/6	EC92 6/-	PC89 9/9
6L7GT 4/9	AZ31 3/6	EC98 10/9	PC89 9/9
6V6G 3/6	B36 4/6	EC98 10/9	PCF62 6/-
6V6GT 5/6	CL33 9/6	EC98 10/9	PCF62 6/-
6X4 3/6	CY1 12/6	EC98 10/9	PCF62 6/-
6X5GT 6/3	DAC32 7/6	EC98 10/9	PCF62 6/-
7B7 7/9	DAF91 3/9	EC98 10/9	PCF62 6/-
7C6 7/9	DAF96 6/-	EC98 10/9	PCF62 6/-
7C6 5/9	DCC90 6/9	EC98 10/9	PCF62 6/-
7E7 4/9	DF33 7/9	EP39 3/9	PCF62 6/-
7Y4 5/-	DF91 2/3	EP41 3/9	PCF62 6/-
9BW6 6/6	DF96 6/-	EP80 4/9	PCF62 6/-

READERS RADIO

24 COLBERG PLACE, STAMFORD HILL, LONDON, N.16. STA 4587
 85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. CRE 7441
 Postage on 1 valve 9d. extra. On 2-valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra.

R in ohms.

Alternatively, the impedance of any of these circuits can be altered without changing f_1 if the capacitances are multiplied by the same number used to divide the resistance values, e.g., to double the circuit impedance, leaving f_1 unaltered, double the resistances and halve the capacitances.

Resistors are made in preferred values, and will not give a required frequency exactly. This accounts for the frequencies 1061 c/s, 1160 c/s, 1181 c/s in the diagrams, which are the nearest to 1000 c/s using fixed resistors.

Once component values have been chosen, a locus diagram for the network will show how the output varies with frequency above and below f_1 . What this special frequency is can be seen from the diagram, e.g. in Fig. 2, f_1 is the frequency at which the output

to vary the phase over a very wide range while keeping the output constant in amplitude.

All that is needed is a centre-tapped input voltage. For this we can use two equal resistors, or a centre-tapped transformer, but the most useful arrangement is probably a "phase splitter" using a valve or transistor. The circuit is shown in Fig. 3. The phase of course varies with frequency as before, and f_1 is now the frequency of 90° phase shift. The output is constant and equal to the "input voltage" which is half the total applied voltage.

An important point is that the anode voltage of a valve is in antiphase to the grid voltage, while the cathode voltage is in phase with the grid. This reversal of phase means that for circuit (b) of Fig. 3, the locus diagram is turned through 180°, so that the output is lagging the input instead of leading as with

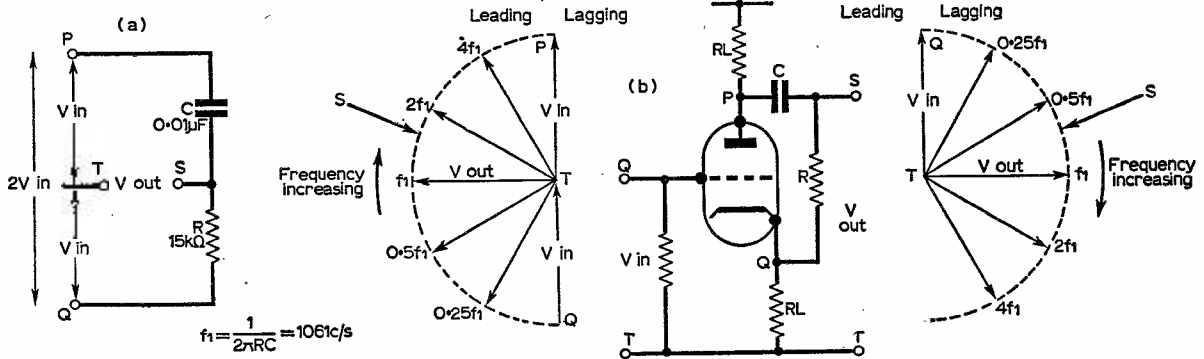


Fig. 3: Phase shifting arrangements with a constant output.

is 70% of the input, and the phase shift is 45°. Capacitive reactance decreases with frequency, so in (a) the phase shift and attenuation are greatest at low frequencies, while in (b) phase shift and attenuation are greatest at high frequencies.

Notice how as the phase shift increases to 90° the output decreases to zero. We thus have a complete picture of the response of the circuit for different frequencies.

Constant Output

It can be seen that although the circuits of Fig. 2 have a semi-circular locus, in both the output varies down to zero because the complexor radiates from the point Q. If the end of the complexor can be moved further up the diagram until the complexor becomes a radius as in Fig. 3, it will then be possible

circuit (a). Grid (or cathode) potential is in antiphase to anode potential (referred to point T as zero potential). Both are additive across the phase-shifting circuit.

In this arrangement the phase can be varied by changing the value of R and C, and the output will remain constant, providing the values of RL are low so that no appreciable change in loading occurs. Two such circuits in cascade can give an overall phase-shift of 180° and this can form the basis of a very satisfactory type of a.f. oscillator.

Ladder Networks

To produce this phase shift of 180° by means of a ladder network requires three sections. The locus diagrams (Fig. 4) of ladder networks consisting of equal resistances and equal capacitances are not quite

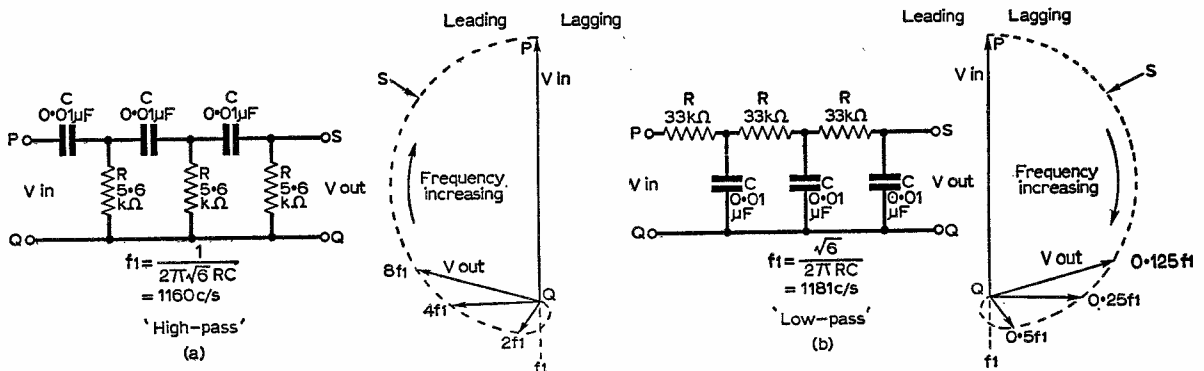


Fig. 4: Frequency responses of ladder networks having three equal sections.

circular in shape. Because the network has three sections, the locus curves into the third quadrant, reaching zero at 270°.

The output at f_1 , here the frequency of 180° phase shift, is almost too small to show on the diagrams since it is only 1/29th of the input voltage, but this does not prevent the network from being successfully used in an oscillator, providing there is a sufficient amplifier gain. Since a single valve or transistor gives a phase reversal in the usual arrangement, an oscillator using a single valve or transistor is possible with a ladder network.

The 180° phase shift of the network is cancelled out again by the phase reversal of the amplifying stage to give an overall phase shift of zero as is required for oscillation.

It should be noticed that with these ladder networks, the frequency is six times higher for shunt

shift, while a low-pass network produces a phase lag. If we combine the two we might expect that at some frequency the two phase shifts would exactly cancel, making the effective phase shift zero.

This is in fact what happens in the three networks of Fig. 5, and the output also passes through a maximum at f_1 , the frequency of zero phase shift, although this maximum is only one third of the input voltage. The output therefore is slightly peaked at f_1 which is at the top of the circular locus, this time a complete circle, but this peaking of the output is relatively unimportant.

What matters in a phase shift oscillator is the phase shift, which takes place with any variation of frequency about f_1 , since oscillation can only be maintained at a frequency where the overall phase shift is zero.

The third of these circuits, Fig. 5 (c) is the most

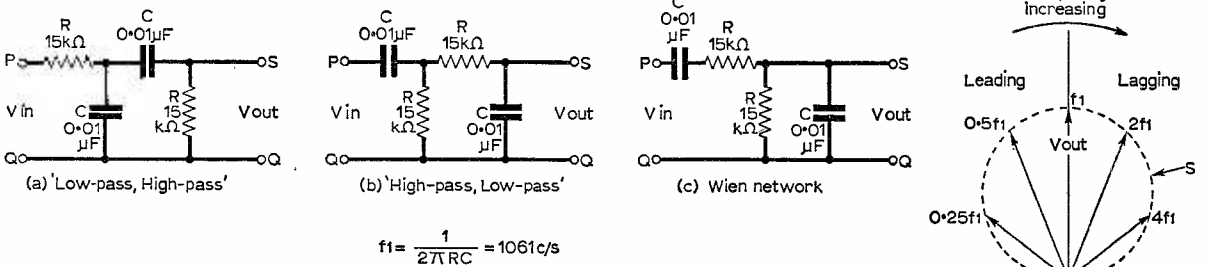


Fig. 5: Three networks having the same "peaked" frequency response.

capacitances and series resistances than vice versa, assuming that the component values are the same in both circuits. This is why in Fig. 4 the series resistances in (b) for a frequency of roughly 1kc/s are six times as high as the shunt resistances in (a).

Used in a transistor oscillator, the frequency would be somewhat different owing to the loading effect of the transistor.

Zero Phase Shift

It only makes sense to employ a phase shifting network to produce zero phase shift when this is obtained at one particular frequency, which in an oscillator determines the frequency of oscillation.

A high-pass network produces a leading phase

widely used. It is the Wien Network, but all three have the same frequency response, as shown in the locus diagram. At f_1 the phase shift is zero, so positive feedback applied through the network in an oscillator will produce oscillation at this frequency. Usually negative feedback is also applied, and this will alter the locus diagram, moving the end of the output complexor upwards from the point Q. This should increase the rate at which the phase angle changes with frequency variation, so making the circuit more effective.

The combination of positive and negative feedback forms a bridge circuit, and since there is zero phase shift at f_1 , a balance or null at f_1 would be possible, as in a Wien Bridge for measuring purposes, but in


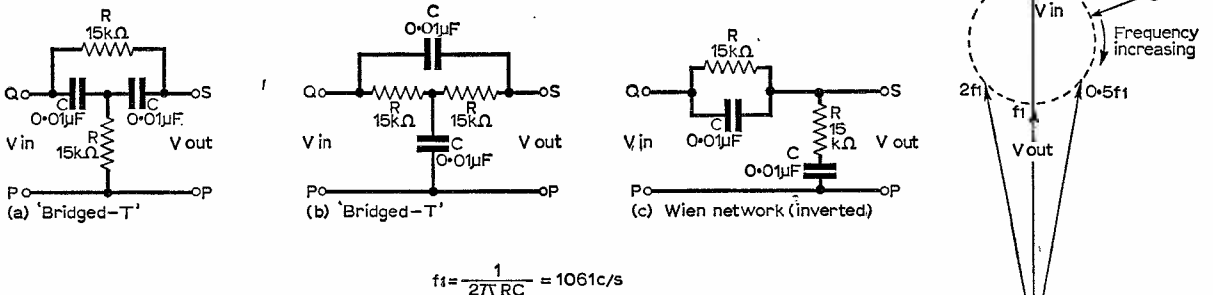


Fig. 6: Three networks with the same "valley" response.

ELECTRONIC TIMERS

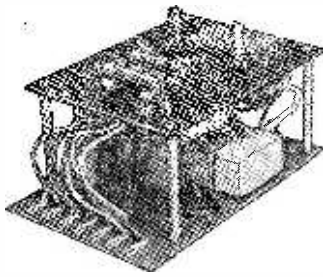

£3. 10. 0 each
(Cases extra at 16/- each)

TIMERS are supplied complete with socket and circuit diagram and provides a variable 'ON' variable 'OFF' control

TIME RANGE

3 - 8 seconds each channel continuously adjustable (Range can be altered by changing capacitor).

SUPPLY

240 - 250 Volts A.C.

RELAY CONTACTS

Single pole. Normally open. 5 amp 250 volts. None inductive.

CONSTANT VOLTAGE TRANSFORMERS

Input 190 - 260 volts 50 cycles. Output matched to Half Wave Rectifier to give 310/340 volts. 30 MA D.C. Transformer only. £3 each. (Ideal for front ends of power packs).

LIMITED OFFER ONLY — SEND CASH WITH ORDER TO:

E. G. I. LTD.

341a SOHO ROAD . HANDSWORTH . BIRMINGHAM 21

NEW FROM PITMAN

Telecommunication Principles

R. N. Renton

One might have thought that a book on principles could have remained unchanged and valid indefinitely, but such has been the pace of developments in telecommunication during the last decade or two that a revised edition of this standard work was thought necessary. The biggest single change is a new chapter dealing with semi-conductor devices (Theory and Application). In addition the book deals with properties of new magnetic and dielectric materials (including square-loop materials and ferrites). The revised City and Guilds Syllabuses are fully covered and recent questions have been added to ensure that this textbook retains its high reputation for easy comprehension and accuracy.

New third edition 50s. net

from all booksellers Pitman Parker St. London



for practical soldering



Bell Tip
for printed circuit de-soldering.



Split Bell Tip
for printed circuit de-soldering.



Printed Circuit Bar Tips
for de-soldering multiple straight line connections.



Smoothing Tip
for heat sealing.



Chisel point Tip
for all general purpose soldering.



Thermo-plastic tile cutting and putty removing tip.



Conical Tip
for spot soldering.



Needle Point Tip
for all delicate work.

NEW!

The Instant Heat Soldering Kit complete with tips, extension barrel, probe and solder. COMPLETE £3.19.6d. GUN ONLY £2.17.6d.



Some jobs can only be accomplished professionally by using the exclusive rigid single-pole construction of the Burgess SG 1225. Ask for a demonstration from your local dealer or fill in the coupon below for full details.

Please send details of NAME..... "PW/5/66"



SG 1225 KIT.

ADDRESS.....

BURGESS PRODUCTS CO. LTD.,
Electric Tools Division, Sapcote, Leics.
Tel: Sapcote 292 Telex 34549

DE LUXE PLAYER KITS FROM £10

4-Speed Players 2-tone Cabinets 17" x 15" x 8 1/2". High flux loudspeaker and 3 watt Famous Mike amplifier ready built. Quality output, Volume and Bass controls. All Items fit together perfectly. Special instructions enable assembly in 30 minutes, only 5 wires to join. 12 months' guarantee.



TO BUILD YOURSELF

SINGLE PLAYER KITS		AUTOCHANGE KITS	
BSR Junior	£10.00	BSR Monarch	£11.00
BSR GUY	£11.00	Garrard 1000	£12.10
Garrard SRP1	£11.00	Garrard Mod 50	£14.10
Garrard SP25	£17.00	Garrard A760	£16.10
OR SEPARATELY: De Luxe Player Cabinet		£8.10	
3 watt amplifier with speaker		£3.10	
AUTOCHANGE UNITS		SINGLE PLAY UNITS	
BSR Monarch	£5.10	BSR Junior	£3.10
Garrard 1000	£6.10	BSR GUY	£5.00
Garrard 2000	£7.10	Garrard SRP2	£5.00
Garrard 3000	£8.10	TRANSCRIPTION UNITS	
Garrard Mod 50	£9.00	Garrard SP25	£11.00
Garrard A760	£11.00	Garrard LAB80	£25.00
Garrard A70	£21.00	Garrard 401	£30.00

ALL POST FREE!

Q MAX CHASSIS CUTTER

Complete: a die, a punch, an Allen screw, and key.

1/4 in.	1/4 in.	1/8 in.	1 1/2 in.	22/6
1/4 in.	1/4 in.	1/8 in.	2 in.	34/3
1/4 in.	1/4 in.	1/8 in.	2 1/2 in.	37/9
1/4 in.	1/4 in.	20/-	2 1/2 in.	44/3
1/4 in.	1/8 in.	20/6	1 in. sq.	31/6

CRYSTAL MIKE INSERTS

1 1/2 x 1/2 in. 0/6; RM3 1 x 1/2 in. 7/8; AC08 1 1/2 x 1/2 in. 3/8
TANNY CARBON MIKE WITH SWITCH 5/6
BARGAIN XIAL PICK-UP ARM Complete with AC08 LP-78 Turnover Head and Sybil 90/-; Stereo 30/-
SPEAKER FEET Tyroner various colours, 62in. wide, from 10/-; 26in. wide from 5/-; 11. Samples S.A.E.
EXPANDED METAL Gold or Silver 12 x 12 in. 6/-.

RETURN OF POST DESPATCH

Post 1/6, List 1/-, C.O.D. 2/6 extra. (Export—Send remittance and extra postage, no C.O.D.)

CALLERS WELCOME

RADIO COMPONENT SPECIALISTS

337 WHITEHORSE ROAD, WEST CROYDON Tele: THO 1665

NEW ELECTROLYTICS FAMOUS MAKES

TUBULAR		TUBULAR		CAN TYPES	
2/350 v.	2/3	100/25 v.	2/-	8/600 v.	9/-
4/350 v.	2/3	250/25 v.	2/6	16/600 v.	12/-
8/450 v.	2/3	500/15 v.	3/-	16-16/500 v.	7/6
16/450 v.	3/-	8-8/450 v.	3/6	32-32/450 v.	6/-
32/450 v.	3/9	8-16/450 v.	3/9	50-50/350 v.	7/-
25/25 v.	1/9	16-16/450 v.	4/3	64-120/350 v.	11/6
50/50 v.	2/-	32-32/350 v.	4/8	100-200/275 v.	12/6

PAPER TUBULARS

350v.-0.1 9d. 0.5 1/9; 1 mid. 3/1; 2 mid. 150v. 3/-
 500v.-0.001 1/ 0.05 9d.; 0.1 1/-; 0.25 1/6; 0.5 3/3
 1.000v.-0.001, 0.0022, 0.0047 0.01, 0.02, 1/6; 0.047, 0.1 2/-;
 0.22, 0.47, 3/-; 2.000v.-0.005, 0.01, 0.02 2/6; 0.05 3/6.
E.H.T. CONDENSERS. 0.001mid., 7kV. 6/6; 20kV. 10/6.

SUB-MIN. ELECTROLYTICS. 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 500, 1,000 mfd. 15v. 2/6; 1,000 mid. 50v. 7/6; 2,000/50 11/6.
CERAMIC. 500 v. 1 pF. to 0.01 mid. 9d. **DISC CERAMICS** 1/-, **PULSE CERAMICS.** 10 to 180 pF., 12 v. 2/6.
SILVER MICA. Close tolerance (plus or minus % pF.). 5 to 47 pF. 1/-; ditto 1% 50 to 300 pF. 1/-; 1,000 to 5,000 pF. 2/-;
TWIN GANG. "0-0" 208 pF. +176 pF. 10/6; 365 pF. miniature 10/-; 500 pF. standard with trimmers, 9/-, midget 7/6; midget with trimmers, 9/-; 500 pF. slow motion, standard 9/-; small 8-gang 500 pF. 18/6. **Single "0" 365 pF. 7/6.**
SHORT WAVE. Single 10pF., 25pF., 50pF., 75pF., 100pF., 160 pF., 5/6 each. Can be ranged. **Couplers** 9d. each.
TUNING. Solid dielectric, 100 pF., 900 pF., 500 pF., 3/6 each.
TRIMMERS. Compression ceramic 30, 70 pF., 9d., 100 pF., 150 pF., 1/3; 250 pF., 1/6; 600 pF., 750 pF., 1/8.

MAINS TRANSFORMERS


	Post
250-0-250, 30 mA. 6.3 v. 3.5 a., or 4 v. 4 a. Rectifier 6.3 v. 1 a. or 5 v. or 4 v. 2 a., 25/-; Ditto 350-0-350, 29/6;	2/- each
300-0-300 v. 120 mA., 6.3 v. CT. 4 a., 0.5, 6.3 v. 2 a. 38/6	
MINIATURE 200 v. 20 mA., 6.3 v. 1 a.	10/6
MIDGET 230 v. 45 mA., 8.3 v. 2 a.	15/6
SMALL 300-0-300 v., 70 mA., 6.3 v. 4 a.	19/6
BREATHER TRANS. 6.3 v. 1 1/2 a., 7/6; 6.3 v. 4 a.	10/6
Ditto tapped sec. 1.4 v. 2, 3, 4, 5, 6.3 v. 1 1/2 amp.	10/6
GENERAL PURPOSE LOW VOLTAGE. Outputs 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. at 2 a.	25/-
Ditto 1 amp. 5, 10, 15, 20, 25, 30, 40, 45, 50, 55, 60 29/6	
Sub-Min. Mains to 9 v. 30 mA. 1 x 1 x 1 in.	7/6
AUTO. TRANS., 150 v. 0, 115 v., 230 v., 25/-; 500 v. 29/6.	

T.V. REMOTE CONTROLLER For Philips 19TG111A, 121A, 125A, 142A, 22TG111A, 118A, 121A, 131A, Stella ST1032A, 39A, 43A, 53A, Cosor CT1910A, 21A, CT2310A, 21A, 31A. Ready to plug in, with 111L 7 way cable, dual pot Volume and Brightness, GAB1 diode, etc. List 3/6s. **NEW, MAKERS BOXES, OUR PRICE 19/6 FREE.**

BAKER LOUDSPEAKERS

HIGH FIDELITY ALL POST MODELS FREE!

12in. STALWART	£5. 5.0
12in. STANDARD	£8. 0.0
12in. DE-LUXE	£9. 0.0
12in. BASS	£12.10.0
12in. SUPERS	£15. 0.0
15in. BASS	£18. 0.0

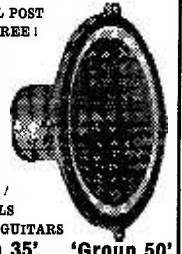

LABORATORY STANDARD MODELS

12in. D.W.I. Cone	£28.10.0
15in. D.W.I. Cone	£28.10.0

NEW CATALOGUE FREE!

GROUP MODELS FOR VOCALS

BASS, LEAD AND RHYTHM GUITARS

'Group 25'	'Group 35'	'Group 50'
12in. 5 gns.	12in. 8 1/2 gns.	15in. 18 gns.
25w.	35w.	50w.

LOUDSPEAKERS P.M. 3 OHMS, FAMOUS MAKES. 2 1/2in., 3in., 4in., 5in., 7in. x 4in., 15/6 each; 5in., 17/6; 6in., 18/6; 12in., 30/-; (15 ohms 35/-); 10in. x 6in., 22/6; 8in. x 6in., 21/-; 8in. x 8in., 21/-; E.M.I. Ceramic 13in. x 8in. x 8in. 15 ohm, 45/-; STENTORIAN 10in. HF1012, 99/6; 8in. HF812, 79/6; HORN TWEETERS 3-16 kc/s 10w. 29/6; 20w. 20 kc/s. 99/6.

WAVE-CHANGE SWITCHES WITH LONG SPINDLES: 2 p. 2-way or 2p.16-way or 3 p. 4-way or 1 p. 12-way each, 4/6
 4 p. 2-way or 4 p. 3-way, 4/6; 5 p. 4-way, 5/6; 6 p. 4-way
Wavechange "MAKITS" 1 p. 12-way, 2 p. 6-way, 3 p. 4-way
 4 p. 3-way, 6 p. 2-way. Prices include click spindles, adjustable stops, spacers, etc. 1 water 8/6; 2 water 12/6; 3 water 16/-
TOGGLE SWITCHES, s.p. 2/-; d.p. 3/6; d.p.d.t. 4/-.

HIGH GAIN TV. PRE-AMPLIFIER BAND I B.B.C. Tunable channels 1 to 5. Gain 18 dB. ECC84 valve. Kit price 32/6 or 55/- with power pack. Details 6d. (PCC84 valves if preferred for 0.3a heater chassis)
BAND III I.T.A.—same prices. Tunable channels 7 to 13. Gain 17 dB.
Band I or III. Coils and circuit only, 9/6. Chassis 4/9.

RADIO BOOKS (P. & P. 9d.)

Radio & T.V. Valves, Diodes & Transistors equivalents	10/6
"V.V." Radio Valve Data	7/6
High Fidelity Speaker Enclosures	5/-
Mullard Audio Amplifier Manual	8/6
Practical Radio Inside Out 4/8, T.V. Fault-Finding	6/6
Transistor Audio Amplifier Manual	6/-
Shortwave Transistor Receivers	5/-

4-STATION INTERCOM



Solve your communication problems with this new 4-Station Transistor Intercom (1 Master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires, each 6ft., and other accessories. P. & P. 4/6.



Modernize business or home with this new two-way Transistor Intercom, consisting of Master and Sub. In strong plastic cabinets, with chromium stands. Designed as a two-way instant communication system—call/talk/listen. Operates on one 9V battery. Complete with 60 ft. wire. Battery 2/6. P. & P. 2/6.



Telephone Amplifier with Rotary Calendar and Pen-Holder. Take down long telephone messages or converse without holding the handset. A status symbol? Yes, but very useful one. On/off switch. Volume Control. Operates on one 9V battery (supplied). P. & P. 3/6. Full money refunded if not satisfied in 7 days.
WEST LONDON DIRECT SUPPLIES (PW11)
 6 CHIGNELL PLACE, WEST EALING, LONDON W18

NEW 1966 Edition

WORLD RADIO TV HANDBOOK

28/- Postage 1/-

RADIO AMATEUR HANDBOOK, 1966, by A.R.R.L. 40/-. Postage 2/6.

UNDERSTANDING LASERS AND MASERS, by S. Leinwoil. 13/6. Postage 1/-.

TRANSISTOR POCKET BOOK, by R. G. Hibberd. 25/-. Postage 1/-.

ABC'S OF ELECTRONIC ORGANS, by N. H. Crowhurst. 16/-. Postage 1/-.

RADIO CONTROL MANUAL, by H. J. Nicholls and T. Dowdeswell. 16/-. Postage 1/-.

BASIC THEORY AND APPLICATION OF TRANSISTORS. 10/- Postage 1/-.

TROUBLESHOOTING WITH THE OSCILLOSCOPE, by R. G. Middleton. 20/-. Postage 1/-.

SERVICING AGC CIRCUITS, by H. E. Thomas. 28/-. Postage 1/-.


COMPLETE CATALOGUE, 1/-.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books
 19-21 PRAED STREET LONDON, W.2
 Phone: PADdington 4185
 Open 6 days 9-6 p.m.

FAMOUS FOR THIRTY YEARS for SHORT-WAVE EQUIPMENT of QUALITY

H.A.C. SHORT-WAVE KITS

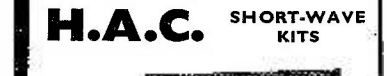


H.A.C. were the original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

IMPROVED 1966 RANGE
 1-Valve model "CX", complete kit, Price 34/6
 Customers say: "Definitely the best one-valve S.W. kit available at any price." This kit contains all genuine Short-Wave components, a drilled chassis, accessories and full instructions. Ready to assemble and of course, as all our products, fully guaranteed. **FULL RANGE** of other kits still available including the famous model "K", price 77/-. Before ordering call and inspect a demonstration receiver or send for a descriptive catalogue and order form to:—

"H.A.C." SHORT-WAVE PRODUCTS (Dept. P.W.), 44 Old Bond St., London W.1


FREE

INSIDE NEXT MONTH'S ISSUE!

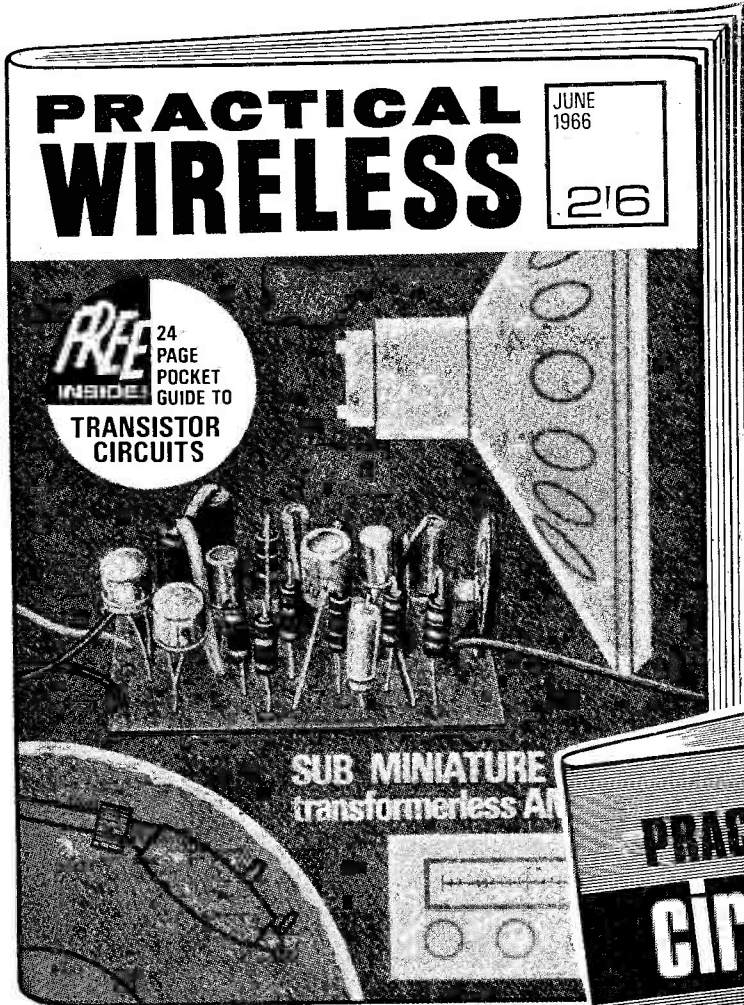

24-PAGE POCKET GUIDE TO TRANSISTOR CIRCUITS

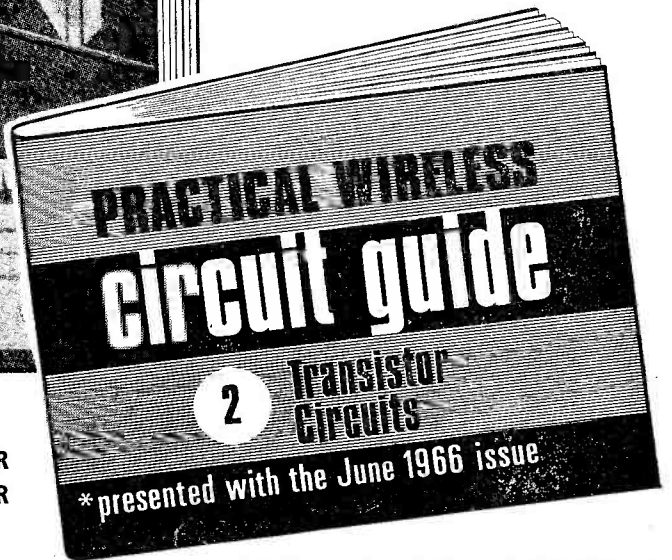Another in the 'PRACTICAL WIRELESS' circuit series. This second guide will deal with transistor circuit techniques, covering r.f., i.f., and a.f. amplifiers, and the many other circuit arrangements found in contemporary radio and electronic equipment.



ALSO IN THIS ISSUE

- HOW-TO-BUILD**
- SUB MINIATURE 300mW AMPLIFIER
 - "IMPERIAL" 3-BAND TRANSMITTER
 - TRANSISTOR SET BOOSTER

MAKE SURE OF YOUR COPY! Hand this Form to your Newsagent

TO (Name of Newsagent)

Please reserve/deliver the June issue of PRACTICAL WIRELESS (2/6) on sale May 5th and continue until further notice.

NAME

ADDRESS

an oscillator there must be an excess of positive feedback for oscillation, so the bridge must be unbalanced.

"Bridged-T" Networks

After mentioning the four-branch arrangements known as bridges, we now turn to circuits which are "bridged" in the more obvious sense of having one component connected like a bridge across two other components.

The output of the networks in Fig. 5 is from terminals SQ. If, instead, the output is taken from terminals SP, the three networks will re-arrange as shown in Fig. 6 where (a) and (b) are symmetrical "Bridged-T" arrangements. There is now a minimum at f_1 instead of a maximum, because the original "peaked" output has been subtracted from the input to produce a "valley" response.

The re-arranged circuits also can be used in an oscillator, but are placed in a negative feedback path. As before, a surplus of positive feedback at f_1 is needed to produce oscillation, and this has the effect of reversing the complexor in the locus diagram, so that conditions are virtually the same as when one of the original three networks of Fig. 5 is employed.

Many different types of a.f. oscillator are possible incorporating one or another of the phase-shifting networks described, as a substitute for an L-C tuned circuit. Tuned amplifiers and filters are also possible, and in these feedback is used to magnify the effect of the network, so that a more sharply peaked response to the signal input results than is depicted by the locus diagram.

Parallel-T Network

Another circuit of interest is the parallel-T network (Fig. 7). This can be described as a true null network because it is complete in itself and gives zero output at a particular frequency f_1 . In this circuit, unlike the previous ones, it is no longer possible to choose all the components alike in value, and

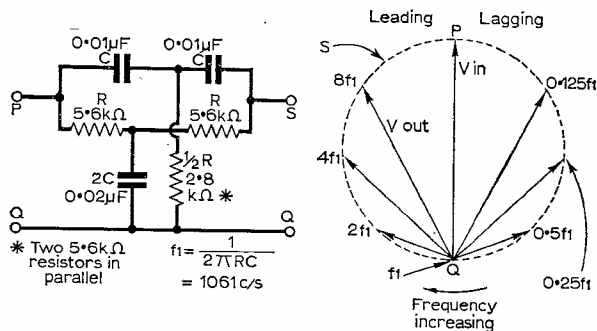


Fig. 7: Frequency response of parallel-T network.

certain ratios must be observed. The simplest arrangement makes the shunt impedances half of the series impedances.

The output follows a circular locus which has a diameter equal to the input. At the frequency f_1 the output decreases right down to zero, so the arrangement is applicable as a filter. An output taken from terminals PQ instead, will be maximum at f_1 , and equal and in phase with the input.

Used in an oscillator the circuit requires less amplification than other arrangements, but is restricted to fixed frequency applications, because tuning would require a triple-ganged potentiometer with one section half the resistance of the others.

The full capabilities of all versions of this network are not obvious without a more complete analysis, and it appears that with different ratios one variation of the parallel-T network can produce oscillation from a single transistor.

All of the networks described have been voltage-transfer networks, but the corresponding current transfer networks are easily derived from them, and are often preferred for use in transistorised oscillators.

CLUB SPOT

—continued from page 57

band Transatlantics. Armed with ten watts of s.s.b./c.w. and 300 feet of wire the net total for the night was some 50 cups of cocoa, 4lbs. of sausages and six contacts across the pond.

The club owns two 40ft. masts, both homebrew and a demonstration of the simple erecting of these (four men 10 minutes, and a bit of luck, from scratch) was demonstrated by "Verulam" at the Woburn Mobile Rally last year where the club also manned the talk-in stations.

A lecturer is in attendance most meetings either resident or visiting. A fortunate annual event is a visit from Mr. G. Turner of the GPO Engineering Dept., when TVI/BCI is the topic for the evening. Other lecturers in the past year have included Antennas (G3HRH), Working DX (G3AAZ), SSB (G3DZW), and Receiver alignment (J. Akim, Marconi Instruments).


Demonstrations have also proved very popular and have included some well-known names such as T. Withers (G3HGE), Vic Hartopp (J. Beams), and Green and Davis.

The Club has its own test equipment the more impressive of which is v.h.f./u.h.f. signal generators (Marconi), General Purpose Oscilloscope, and a 5-band home-brew transmitter.



Tuning the stubs on the Quad for max. front-to-back ratio. Note the novel method of keeping the ladder up. (Method not patented!)

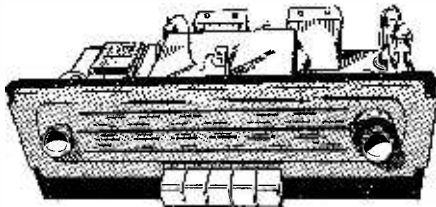BRAND NEW AM/FM (V.H.F.) RADIOGRAM CHASSIS AT £15.15.0 (Carriage Paid)



Chassis size 15 x 6½ x 5½in. high. New manufacture. Dial 14½ x 4in. in 2 colours, predominantly cream. 200-250v. A.C. only. Pick-up. Ext. Speaker. Ae., E., and Dipole Sockets. Five push-buttons— LW, MW, SW, FM and Gram. Aligned and tested. O.P. Transformer Tone control. 1000-1900 M.; 200-550 M.; 85-98 Mc/s. 6-17 mc/s. EZ80 rect.; ECH81, EF89, EABC80, EL84, ECC85, 8-ohm speaker required. 9 x 6in. ELLIPTICAL SPEAKER, 20/- to purchasers of this chassis. **TERMS:** (Chassis), £4.0.0 down and 5 monthly payments of £2.10.0. Cheap Room Dipole for V.H.F., 12/6. Feeder 6d per yard. Total H.P. price £16.10.0. Circuit diagram 2/6. Carriage to N. Ireland 20/- extra.


NEW 6 PUSH-BUTTON STEREOGRAM CHASSIS. M.W.; S.W.1; S.W.2; V.H.F.; Gram; Stereo Gram. Two separate channels for Stereogram with balance control. Also operates with two speakers on Radio. Chassis size: 15 x 7 x 6½in. high. Dial cream and red, 15 x 3in. Valves ECC85, ECH81, EF89, 2 x ECL86, EM84 and Silicon Rect. Price £17.17.0, carr. paid or £5.0.0, deposit and 5 monthly payments of 50/-. Total H.P. price £15.15.0. Cream moulded escutcheon for dial, 7/6 extra, 190-550M; 18-61M; 60-157M; VHF 86-100 mc/s.

TAPE AMPLIFIER FOR COLLARO OR MAGNA-VOX TAPE DECKS—2 TRACK


Chassis 12½ x 5½ x 4½in. high. Plastic front panel "gold" finish—12½ x 4½in. 200-250 A.C. Record/Playback amp. switch; OR/On-Tone; Vol/Mic; Vol/Gram; Mic. Input; Gram. Input; Monitor; Speaker Sockets. Valves 6BR7; 12AX7; EM85; EL84; 6X4. Separate power pack. Complete amp. and power pack £7.19.8. (6/- P. & F.).

SELF-POWERED VHF TUNER CHASSIS

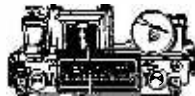Covering 88-95 Mc/s. Dims. 8 x 6 x 6in. high. Valves ECC85, EABC80 and 2-EF89's with metal rectifier. Mains transformer. Fully wired and tested ONLY £8.17.6 (carr. paid). Room dipole 12/6. Feeder 6d. per yard.



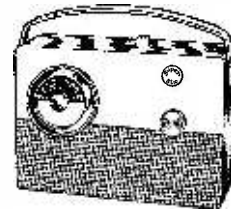The
SUPER 6
LONG & MEDIUM WAVE
TRANSISTOR RADIO



A quality radio available as a kit or ready-built. The sparkling performance and superb finish of the completed receiver give you value equivalent to a £12.12.0 commercial model.

★ All new parts. ★ 6 transistors and diode. ★ 350mW output. ★ Superhet circuit. ★ Ferrite rod aerial. ★ Weymouth Radio printed circuit board. ★ Component positions and references printed on back of board. ★ Nicely styled wooden cabinet, 11 x 7½ x 3½in. ★ Vinyl covered in various colours. ★ 6 x 4in. speaker giving good bass and treble response. ★ Full instruction booklet, 2/-. Free with kit. ★ I.f. frequency 470 kc/s. ★ Lining up service if required. ★ All parts supplied separately. Write for list, S.A.E. PLUS 5/- POST. **COMPLETE KIT ONLY £4.0.0**
OR FULLY BUILT £6.7.6. Tax & Carr. Paid.

8 WATT PUSH-PULL O.P. AMPLIFIER £5.5.0
(6/- Carr.)

200-240 A.C. mains. Bass, treble and vol. controls. EZ80, ECC83 and 2-EL84's. Chassis 12 x 2½ x 3½in. With o.p. trans. for 2-3 ohm speaker. Front panel (normally screwed to chassis) may be removed and used as flying panel. With Cream/Black control panel whole length of front chassis.




BATTERY ELIMINATOR

For 4 low consumption valves (96 range) 90v. 15mA and 1.4v. 125 mA, 42/6 (4/- post), 200-250v. A.C. Also for 250mA, 1.4v. and 90v. 15mA at same price. Two units each 3½ x 3½ x 1½in.

GLADSTONE RADIO
66 ELMS ROAD, ALDERSHOT, Hants.

(2 mins. from Station and Buses). Aldershot 22240
CLOSED WEDNESDAY AFTERNOON
CATALOGUE 6d.
Regret overseas orders cannot be executed

ADAMIN THERMAL STRIPPERS

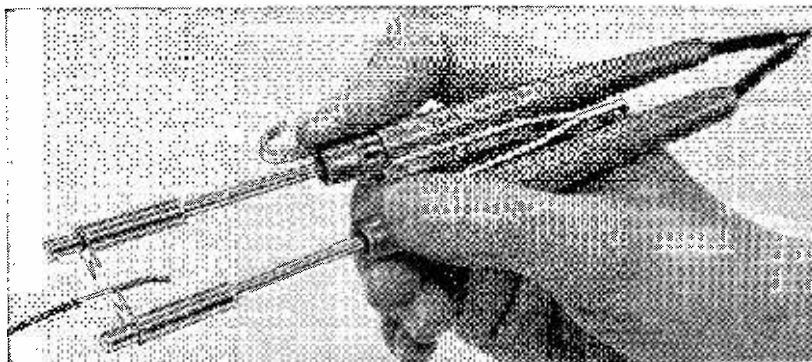

FOR **PTFE** INSULATION
FOR **PVC** INSULATION

The new ADAMIN thermal wire strippers allow one-handed operation, using a simple tweezer action.

They strip coverings of up to about 5/32 inch diameter with absolutely no risk of damaging the conductors.

use Model 2B24 (illustrated), available for 24 volts only. and similar low temperature materials, use Model 2B6, available for 12 or 24 volts.

LITESOLD TRANSFORMERS permit safe operation from any mains power point. Free details of the whole wide range of ADAMIN and LITESOLD soldering equipment in brochure SPI0.

LIGHT SOLDERING DEVELOPMENTS LTD., 28 Sydenham Road, Croydon, Surrey. Telephone: CRO 8589

THE SINCLAIR AUDIO-

Build a SINCLAIR Hi-Fi System

By building ALL three Sinclair designs featured this month, you can become the proud owner of a unique A.M-F.M/Stereo Hi-Fi system that will give complete satisfaction and save pounds compared with other systems. Each unit is complete in itself and you will have two radio units, each of which can be used separately as an independent self-contained personal receiver. These designs cover all aspects.

A.M

The Micro-6. It has amazing range and power and combines readily with the Z.12.

F.M

For quality, the Micro FM gives all you want both as a tuner and a pocket receiver for personal listening.

HI-FI

The Z.12 more than replaces larger conventional amplifiers for price, size and power. Two in stereo cannot be bettered.

A CONSTRUCTOR TELLS US


"I was determined to finish it (The Micro FM) at one sitting. Having completed, it, I am amazed at its quality of reproduction, and am spending far too much time listening to it; it even works on trains which is more than can be said of AM radios."
(Signed) D.V.B., Tunbridge Wells, Kent.

SINCLAIR MICRO FM

ALL YOU WANT FROM AN F.M. TUNER AND RECEIVER IN A SINGLE UNIT

When Sinclair Radionics decided to design an F.M receiver which could be carried in the pocket and yet satisfy the most stringent demands likely to be made of it, it was realised from the start that radical departures would have to be made from conventional F.M design techniques. The problems of alignment would have to be eliminated for constructors. Sensitivity had to be such that good reception could be enjoyed using no more than the telescopic aerial necessary to keep the set truly portable. Audio quality had to be at least as good as that from sets where size and price were not important considerations. Sinclair Radionics achieved this and much more in their Sinclair Micro FM. Today, it enjoys the unique distinction of being the only set of its kind in the world, it can be used as a tuner and as an independent pocket size personal F.M receiver. In appearance, this fully-fledged 7 transistor superhet F.M is as outstanding as it is in its performance. The brushed and polished aluminium front panel with spun aluminium tuning dial makes it the most elegant, professionally styled set ever made available to constructors. Yet with these and many other important features, the Micro F.M costs pounds less and enables constructors to enjoy F.M reception to the full at once.

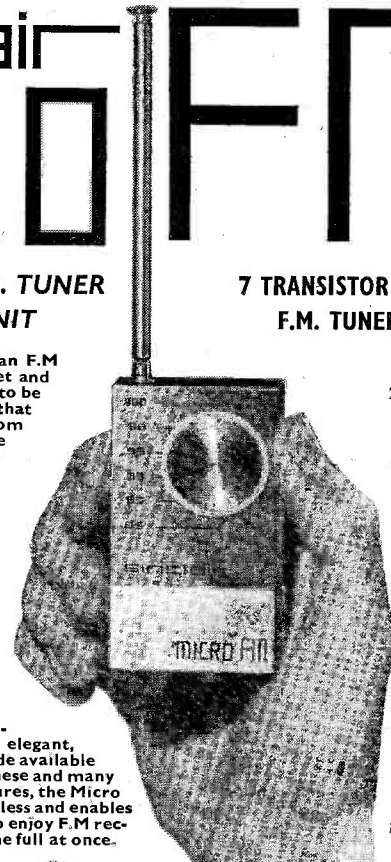7 TRANSISTOR COMBINED F.M. TUNER RECEIVER



- 2 1/2 x 1 1/2 x 3/4 in.
- Needs no Alignment
- One output for Hi-Fi
- One output for personal listening
- Tunes from 88-108 Mc/s

Complete kit of parts including transistors, aerial, case, front panel, dial, earpiece and instructions

£5.19.6




TECHNICAL DESCRIPTION

The Sinclair Micro FM is a completely self-contained double-purpose FM superhet housed within a case less than 3in. high x 1 1/2in. wide with a depth of 1/2in. It uses 7 transistors and 2 diodes in special superhet FM circuitry. The R.F. amplifier is followed by a self-oscillating mixer and 3 stages of I.F. amplification which dispense with I.F. transformer and all problems of alignment. The final I.F. amplifier produces a square wave of constant amplitude which is converted into uniform pulses so arranged that the original modulation is reproduced exactly. A pulse-counting detector ensures improved linearity and therefore better audio quality at the output stages. After equalisation the signal is channelled to one output for feeding to amplifier or recorder and to another in which the receiver's own audio amplifying stage enables the Micro and FM to be used as an independent self-contained pocket portable. A.F.C. is used to lock the programme tuned in; the telescopic aerial included with the kit will be found sufficient for all but the worst signal areas.

- Supply voltage—9v from self contained standard battery.
- Consumption—5mA.
- Sensitivity—Typically 3mV
- Signal to Noise Ratio—30dB at 30 microvolts.
- Audio frequency response —10-20,000 c/s.
- Two Audio Outputs—One for feeding to amplifier or tape recorder. One for feeding to earpiece to enable set to be used as a portable receiver.
- A.F.C. for automatically locking on to each station tuned in.
- Inserting plug of earpiece or tuner lead switches set ON.

the smallest set on earth

—it's the inimitable

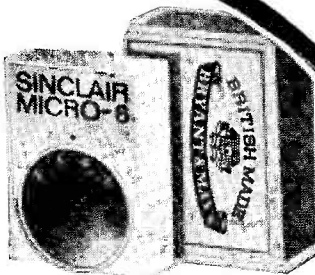

SINCLAIR MICRO-6

SIX STAGE A.M. RECEIVER

- 1 1/2 in. x 1 1/2 in. x 1/2 in.
- Weight—1 oz.
- Bandspread for Luxembourg
- Build it in an evening
- Plays anywhere

No transistor set in the world has ever yet compared with this six-stage marvel for power, range and size. It gives you the whole of Europe to listen to. The Micro-6 has 2 stages of R.F. amplification, double diode detection and 3 stage high gain A.F. amplifier. A.G.C. counteracts fading from distant stations. Tunes over medium wave-band. The whole set complete with ferrite rod aerial and batteries is contained in a case smaller than a matchbox, and is a delight to build.

All parts inc. transistors, case and dial assembly in white, gold, black, earpiece and instructions

59/6

MALLORY MERCURY CELL ZM312 (2 reqd.) each 1/11

FULL SERVICES FACILITIES AVAILABLE TO SINCLAIR CUSTOMERS



sinclair

sinclair radionics ltd.
22 newmarket road, cambridge
Telephone 52731

FIDELITY PROGRAMME

SINCLAIR Z.12 COMBINED AMPLIFIER AND PRE-AMP

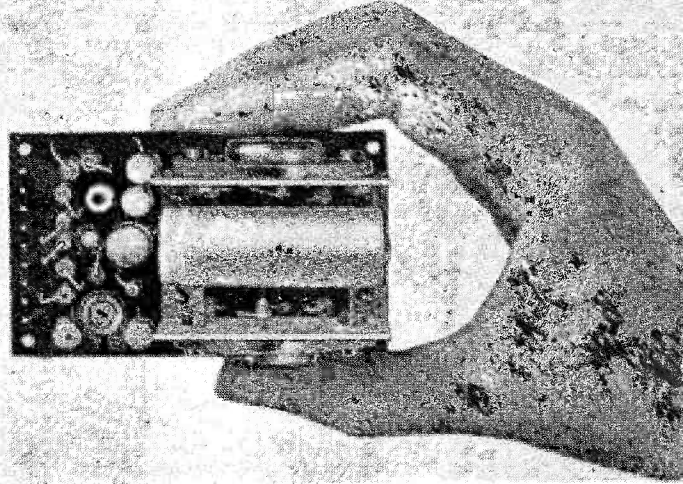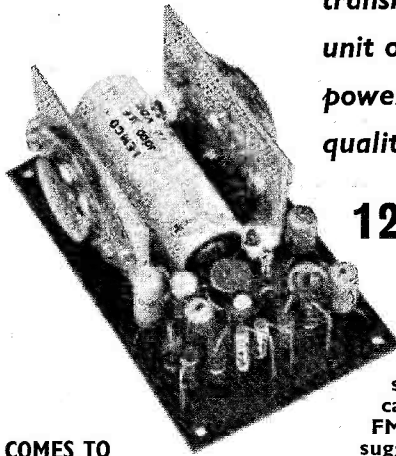An eight
transistor
unit of enormous
power and superb
quality giving



12 WATTS RMS OUTPUT

For size alone, the Z.12 marks another important advance in quality design, for its amazing compactness opens up exciting new vistas in amplifier housing and application. Combined with this are the fantastic power and superb quality of the Z.12 which can provide an effortless output of 12 watts R.M.S. continuous sine wave from its unique eight transistor circuit. Basically intended as the heart of any good mono or stereo hi-fi system, the size and efficiency of this Sinclair unit make it equally useful for a car radio (with the Micro-6 for example), a high quality radio with the Micro FM, in a guitar, P.A. or intercom system, etc. Other applications are sure to suggest themselves to constructors. The manual included with the Z.12 details many mono and stereo tone and volume control circuits by which inputs can be matched (and switched in) to the pre-amp. The size, performance and price of the Z.12 all favour the constructor seeking the finest in transistorised audio reproduction—it is in fact today's finest buy in top grade high fidelity.

COMES TO
YOU READY
FOR IMMEDIATE USE

Ready built, tested
and guaranteed
With Z.12 manual

89/6

- FOR 6-20V OPERATION
- SIZE 3in. x 1 3/4in. x 1 1/2in.
- IDEAL FOR 12 VOLT BATTERY OPERATION
- MAKES A SUPER STEREO ASSEMBLY

Technical Specification

- 8 special HF transistors.
- Ultra-linear class B output and generous neg. feedback.
- Response—15 to 50,000 c/s ± 1 dB.
- Output suitable for 3, 7.5 and 15 ohm loads. Two 3 ohm

speakers may be used in parallel.

- RMS Output—12 watts continuous sine wave (24w peak). 15 watts continuous music power (30w. peak).
- Input—2mV into 2K ohms
- Signal to noise ratio—better than 60dB.

THREE MONEY-SAVING OFFERS TO Z.12 PURCHASERS

PACK 'A'

Comprising Micro FM and Z.12 together. Normal price £10.19.0. Special 'Pack' price £9.10.0

Saves you
19/-

PACK 'B'

Comprising Micro-6 and Z.12 together. Normal price £7.9.0. Special 'Pack' price £7.0.0

Saves you
9/-

PACK 'C'

Comprising two Z.12 amplifiers. Normal price £8.19.0. Special 'Pack' price £8.8.0

Saves you
11/-

NEW PZ.3 MAINS POWER UNIT

An entirely new design by Sinclair using a unique transistorised smoothing system giving exceptionally smooth DC output. Will power two Z.12 units for stereo etc. For AC mains 200/250v. **79/6**

Guarantee

Should you not be completely satisfied with your purchase when you receive it from us, your money will be refunded in full and at once without question.

If you do not wish to cut this page, please quote PWS when writing your order.

● FULL SERVICE FACILITIES AVAILABLE TO SINCLAIR CUSTOMERS

To: SINCLAIR RADIONICS LTD., 22 NEWMARKET ROAD, CAMBRIDGE

Please send items detailed below:

NAME

ADDRESS

For which I enclose cash/cheque/money order.

PW.5

SINCLAIR

Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 1/6d. per word (minimum order 18/-), box number 1/6d. extra. Semi-displayed setting £4 12s. 6d. per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Advertisement Manager, PRACTICAL WIRELESS, George Newnes Ltd., Tower House, Southampton Street, London, WC2, for insertion in the next available issue.

SOUND RECORDINGS

A UNIQUE TAPE BUY! Top brand 7in., 2,400ft., 25/-; 5in., 1,200ft., 15/-. P. and p. 1 at 2/-, 2 at 2/9, 3-6 at 3/6. Bargains in all sizes. S.A.E. for list. E. C. KINGSLEY AND CO. LTD., 93 Tottenham Court Road, London, W.1, EUSton 6500.

TAPE RECORDERS, TAPES, Etc.

TAPES TO DISC — using finest professional equipment—45 rpm—18/-. S.A.E. leaflet. DEROY, 52 Hest Bank Lane, Lancaster.

SERVICE SHEETS

SERVICE SHEETS for all makes of Radio and TV, 1925-1966. Prices from 1/- with free fault-finding guide. S.A.E. inquiries. Catalogue of 6,000 models 1/6. Valves, modern and obsolete, Radio/TV Books. S.A.E. lists. HAMILTON RADIO, Western Road, St. Leonards, Sussex.

SERVICE SHEETS, Radio and Television, 4/-, post paid. VEST AND EMERY, 17 Hallgarth Street, Durham.

SERVICE SHEETS, Radio, TV, 5,000 models. List 1/-. S.A.E. inquiries, TELRAY, 11 Maudland Bank, Preston.

SERVICE SHEETS (75,000), 4/- each. Callers welcome. Always open. 5 South Street, Oakenshaw, Bradford.

SERVICE SHEETS

4/- each, plus postage

We have the largest display of Service Sheets for all makes and types of Radios and Televisions, etc., in the country. Speedy service. To obtain the Service Sheet you require please complete the attached coupon.

Name:

Address:

.....

.....

To: S.P. DISTRIBUTORS

44 Old Bond St., London, W.1

Please supply Service Sheets for the following:

Make:

Model No. Radio/TV

Make:

Model No. Radio/TV

Make:

Model No. Radio/TV

I require the new 1966 List of

Service Sheets at 1/6 each plus postage.

(please delete items not applicable). I

enclose remittance of.....

MAIL ORDERS ONLY May PW

RECEIVERS & COMPONENTS

TRANSISTORS, UNMARKED, UNTESTED. 40 for 10/-, p. and p. 1/-, 4 packets post free. Relays, thousands of types, special catalogue free. General catalogue of Mechanical and Electrical Gear, Tools, etc. (5,000 items), free. K. R. WHISTON (Dept. PRW), New Mills, Stockport.

SPEAKER REPAIRS. Cones fitted. Satisfaction guaranteed. L. S. REPAIRS, Pluckley, Ashford, Kent.

R & R RADIO & TV SERVICE

Dept. P.W.
MARKET STREET, BACUP, LANCs.
Telephone 465

SALVAGE VALVES	Tested before despatch	
6FL3 4/6	U229 5/-	PL26 6/-
6L18 4/6	10P14 5/-	PL22 3/6
EF80 1/6	20F5 6/6	U801 7/6
ECC82 3/-	30P 7/-	10P1 1/6
ECL80 3/6	6F15 5/-	20P2 5/3
30F5 5/-	EB91 1/-	30FL1 5/-
FL38 6/-	EF85 5/-	PY32 6/-
PCF80 4/-	6/30L2 4/-	GU4GT 5/-
PL81 5/-	20P3 6/-	6F1 2/6
PZ30 5/-	30PL1 4/-	BY86 4/-

Speakers. Ex-TV. 6in. round 6 x 4in., 3/6; 8in. round 6/-; post 2/-.

Line Output Transformers available. State set model No. Turret Tuners, 8/-, post 2/-.

Scan Coils, etc. Quote set model No. with all enquiries and S.A.E. for prompt reply. All goods subject to satisfaction or money refunded.

SILICON PLANAR Transistors. Matched complementary pairs 18V, 200mW, hFE 60 to 100 at 10/- pr. Power types 2N3402, NPN 25V 560mW at 8/6. High gain NPN, ZN3711 hFE 180 to 660 at 7/-. ELECTROVALUE, 6 Mansfield Place, Ascot, Berkshire.

TRANSISTORS & COMPONENTS

OC71, OC44, OC45, OC72, OC81, OC81D—3/- each. OC83—6/4 each. AF116, AF117, OC171—3/6 each. AF114, AF115—4/- each. BY100 Mullard Branded 250V 550 M/A—5/- each. AG128—8/- each. ASY28—8/6 each. AF186 cut of FREQ 800 Mc/s—27/6.

Byz 15 Silicon Rectifiers 200 P.I.V. 40 Amps 57/- ea.

M.A.T. TRANSISTORS MAT 100 7/9. MAT 120 7/9.

MAT 101 8/6. MAT 121 8/6.

Acos Record Player Cartridge Replacements for Collaro, Garrard, B.S.R., etc.—12/6 each.

TEXAS TRANSISTORS 2N1302—ASY28 6/6 each. 2G302—GET872 7/6.

GM290—AF189 13/6. 2G301—GET873 6/6.

Other types available on request.

NEWMARKET TRANSISTORS

NKT218 13/- NKT225 6/6 NKT271 8/-

NKT214 6/6 NKT301 30/- NKT272 8/-

NKT213 8/- 2A2P1 66/6 NKT273 8/-

NKT212 12/6 NKT219 8/- NKT274 8/-

NKT224 6/6 NKT223 5/- NKT275 6/6

NKT279A 3/4 NKT283 8/- NKT278 10/-

NKT212 8/- NKT264 8/- 3AN3 35/-

NKT224 6/6 NKT265 6/6 NKT677 9/6

Send S.A.E. for complete list of Transistors.

NEWMARKET TRANSISTOR POWER SUPPLIES

Type PC101, mains input D.C., output 9v. Max. load current, 150 M/A. Max. ripple voltage, 200mV, R.M.S., 37/6, P. Paid.

S.A.E. all enquiries. All above Post Paid.

Mail Order Only

J. ROBINSON

(Radio & T.V.)

4 Highlife Road, Blackley, MANCHESTER 9

RECEIVERS & COMPONENTS

(continued)

19 SETS (A sets complete) with Power Packs, Control Box and all Connectors, tested and working R and T, £6/10/- plus 35/- carriage and packing. Sets only, £4, 20/- c. and p. Head Sets £1. 46 SETS, new, unpacked, complete with 2 Head Sets, Connectors, Haversack, £6/10/-, carriage 17/6. WALDEN, Main Road Garage, South Green, Billericay, Essex.

TRANSISTORS AND DIODES

OC71, OC44, NKT213, OC81M, 3/-. Matched Sets: 2 OC81M, 1 OC81DM, 9/-; GET111, 5/-; 2N1225, 4/-; OC170, 3/6; OA70, OA79, OA95, 1/6; BY100, 5/-; OC26, 8/6; OC29, 8/-; OC36, 8/-. All post free.

THE RADIO CONSTRUCTOR'S CENTRE

363 WESTBOROUGH ROAD
WESTCLIFF-ON-SEA, ESSEX

"HEATHKITS" can now be seen in London and purchased on easy terms. Free brochure, DIRECT TV REPLACEMENTS LTD., Dept. PW7-9, 126 Hamilton Road, West Norwood, S.E.27. Gipsy Hill 6166.

Assorted High Stab Resistors, 7/6, 100.

Assorted Syflex P.F. Condensers, 7/6, 100.

Copper Laminate Board, 12in. x 12in., 5/-, single or double sided.

Paxolin Sheet, 1/16in. x 12in. x 12in., 3/-.

Thin Paxolin Sheet, approx. 1/64in. x 12in. x 12in. 6 sheets for 5/-.

White Plastic Sheet, approx. 1/32in. x 6in. x 24in., suitable dials, insulation, case fronts, etc. 4 sheets for 5/-.

Small E.M. Counters, 5 digit, 500 ohm, 6/6.

Buigin Extra Sensitive Micro Switch, 5/-.

P.O. Relay 2000 ohm, 1B, 5/-, 1M, 1B, 6/-.

Key Switches, 4 pole, 2 throw, 3/6. 3 position DP+DP centre off, 5/-, 3 c/o+4 c/o centre off, 6/-, DP+DP 2 for 5/-.

Plessey Plugs and Sockets, 12-way, 3/- pair. 6-way, 5/- pair.

6 or 12-way screened cable to match, 3/- yard.

Breast Mike, 6/-, Carbon Inserts, 1/6.

Power Pack and L.F. Amplifier for 38 Set, 15/-.

Battery Ever-Ready, 90v+7v, 4/6, 12 for 30/-, Small Component Boxes, 12/6, for 60 sample 6d.

Mp Metal Screen for 5pP7 with fittings 6/6. 250 m/A Fuses 14 x 4in., 5/-, 100.

100 volt Hand Generator, 7/6.

Valves New Boxed, 6V6, 4/6. EF91, 3/-, 6AL5 3/-.

Rheostat Ww Rotary, 15 ohms, 3.6 amp., 12/6.

Details of Instrument Case Assembly free. Send large addressed envelope.

Elac Speakers, 5in., 5/-, 7 x 4in., 7/-, 8in., 8/-.

Terms Cash with Order. Post 2/- on orders under 20/-.

E. R. NICHOLLS

Mail Order and Retail Shop

46 LOWFIELD ROAD

off SHAW HEATH, STOCKPORT

CHESHIRE

BUILD 24 INTERESTING DESIGNS

with your own components and transistors on a printed-circuit chassis.

"EXPERIMENTAL" PRINTED CIRCUIT KIT

Contents

- (1) 2 Copper Laminate Boards 4" x 2 1/2".
- (2) Resist. (3) Etchant. (4) Resist Solvent.
- (5) Cleanser/Degreaser.
- (6) 16-page illustrated booklet.

"PRINTED CIRCUITS FOR AMATEURS"

containing full etching instructions.

- (7) Attractive case 4 1/2" x 2 1/2" for a pocket Transistor Radio, Crystal Set, etc. Suits designs enclosed.
- (8) Miniature Radio Dial MW/LW.
- (9) Miniature Radio Dial SW/MW/LW.

Also free with every kit.

- (10) Essential Design Data and Constructional Details of easy-to-build.

24 SUGGESTED PROJECTS

which you can build on a P.C. chassis made from this kit. Part Layouts, Circuit Diagrams, P.C. Chassis plans, Assembly Drawings, Photographs. Many recently developed very efficient designs you probably haven't heard of yet. (1) Crystal set with biased detector. (2) Crystal set with voltage-dynamic loudspeaker. (3) Crystal set with audio amplifier. (4) Carrier Power Conversion Receiver uses the B.B.C. signal to bring in distant foreign stations. No battery. (5) Split-Load Neutralised Double Reflex Pocket Loudspeaker Receiver. Uses only 3 transistors in a very sensitive and economical circuit. (6) Matchbox or Photocell Radio. Small receiver powered by a single photocell or mercury battery. (7) "TRIFLEXON" Triple Reflex with self-adjusting regeneration, variable bandwidth, amplified A.G.C. Uses only 3 transistors in cascade. Each transistor amplifies 3 times. Terrific gain. Excellent selectivity. The best circuit yet invented (Patent Pending). Simplicity of the TRF with the performance of the superhet. Makes possible the construction of extremely low-consumption subminiature radios. (8) Solar Battery Loudspeaker Radio. Employs photocells to charge a small accumulator. Entirely practical design.

3 SUBMINIATURE RADIO RECEIVERS

The smallest 3 designs yet offered to the Home Constructor anywhere in the World. Based on the "Triflexon" circuit. Let us know if you know of a smaller design published anywhere. (10) Postage-Stamp Radio. Size only 1.62" x .95" x .25". (11) Wrist-watch Radio, 1.15" x .80" x .55". (12) Ring-Radio, .70" x .70" x .55". (13) Bacteria-powered Radio. Runs on sugar or bread. (14) Radio Control Receiver. (15) Transistor P/P amplifier. (16) Intercom. (17) 1-valve amplifier. (18) Photoelectric Burglar Alarm. (19) Light-Seeking Animal, Guided Missile. (20) "Perpetual Motion" Machine. Atmospheric Engine. (21) Metal Detector. (22) Simple Transistor Tester. (23) Human Body Radiation Detector. (24) Electronic Man/Woman Discriminator. Thermal Proximity Fuse, etc. P.C. Kit price 7/6. Post and pack. 1/-.

Extra copper laminate available.

OUR CUSTOMERS WRITE: ... "I have just received your P.C. kit and I would like to say how satisfied I am. (S.M.) ... I think it is very good value for money. (K.D.) ... I am very pleased. (J.L.) ... Thanks for the P.C. kit. Really wonderful value for money (W.T.) ... worth 7/6 for the circuit alone. (K.T.)."

"YORK ELECTRICS" 181a, York Road, LONDON S.W.II.

Send S.A.E. for full details


RECEIVERS & COMPONENTS (continued)

SILICON RECTIFIERS—800 P.I.V.—5.0 amp 5/3 each post paid. 11 valve R.A.F. Receivers R3582A—£1 plus 12/6 carriage. 112 Groby Road, Glenfield, Leicester.

RESISTORS Lab mixed 4/- per hundred. Postage 1/6d. 500 or more post free. C.W.O. Mail Orders only. 203 Long Lane, Finchley, N.3.

PADDED MOVING COIL head phones and moving coil mike with lead and plug, 12/6 post paid. G. WEBSTER (ELECTRICAL) 9a Greyfriars Road, Coleham, Shrewsbury, Shropshire.

6 TRANSISTOR PRINTED CIRCUIT RADIO

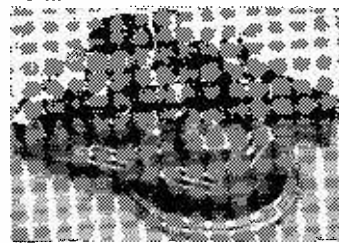

Components for the above as follows:—
6 transistor printed circuit 1/8. 2 1/2in. speaker 6/6.
Ferrite block 1/-. Edge volume control D.P.5K. 1/8.
IF and Osc. coils (set of 4) 6/8 set. Slide switch
D.P.D.T. 1/-. Ganged condenser 5/-. P.P. output
transformer 7/8. Driver transformer 7/8. Circuit 1/8.

37/6 All the above made specially and ready for assembly. Any item supplied separately. Add 1/6 P. & P. when order less than 10/-.

GLEVELEYS ELECTRICAL ENGINEERING CO.
Holmefield Av., Cleveleys, Nr. Blackpool

FOR SALE

MORSE MADE EASY!

The Famous RHYTHM RECORDED COURSE cuts the practise time down to an absolute minimum.

One student, aged 20, took only 13 DAYS, and another, aged 69, took under a week to read 18 wpm. If you wish to read Morse easily and naturally please enclose 8d. in stamps or two international reply coupons for full explanatory leaflet to

G3CHS, 45 Green Lane, Purley, Surrey.

SPECIAL OFFER

GEVAERT TAPE. New, Boxed, 5 1/2, 600ft. with Stop and Leader Tapes, 9/- or 6 for 50/-, post paid.

GRUNDIG MAL. 2 Transistor Pre-amps for Tape Monitoring or Microphone Boosters, 57/6, post paid.

LIST PRICE 4 GNS.
LEE ELECTRONICS
400 Edgware Road, Paddington 5521
Send for Free Lists and details of above

ELECTRIC SOLDERING-IRON



FANTASTIC BARGAIN PRICES

Lightweight Pistol Grip handle
40 watt. 240/250v. A.C. Solid
copper bit. Detachable handle
forms cover for iron when hot in
use. With 4ft. Safety 3-core
flex. Indispensable for
every home handy-
man. A boon to model
makers and a necessity
for every wireless en-
thusiast. Offered to
you at this new amaz-
ing price.

**ONLY
9/6**
P & P
1/-

C. H. SERVICE (Dept P.W.)
Lusted Hall Lane, Tatsfield, Kent.

FOR SALE (continued)

STROUD AUDIO 50 watt guitar amplifier with tremolo. £14. E. RILEY, 1 Boulton Square, West Bromwich, Staffs.

HAMMERITE HAMMER PATTERN BRUSH PAINT FOR PANELS AND BOXES

★ THE PATTERN IS IN THE TIN ★
ALL YOU DO IS BRUSH IT ON!

2 1/2 oz. tins 3/6 1/2 gallon 35/-**
1/2 pint 7/6 1 gallon 55/-**
1 pint 15/- (* sent by road)

Carriage: Orders up to 5/-, 9d.; up to 10/-, 1/9;
over 10/-, 2/9. Colours: Blue, Silver or Metallic
Black. Return of post service, Monday to Friday.
From your component shop or direct from the
manufacturer:

FINNIGAN SPECIALTY PAINTS (PW)
Mickley Square, Stocksfield, Northumberland
Tel. Stocksfield 2280

A CASE for that circuit

We have a quantity of Brand New MERCURY 'SIX' Transistor Radio Cabinets, which must be disposed of to make way for new stock. Attractively styled and solidly constructed rexine covered wood, size approx. 14 1/2" x 7 1/2" x 4", complete with plastic carrying handle and feet. An ideal cabinet for Radios, Amplifiers, and 101 other circuits. We are also offering a limited number of MERCURY 'SIX' printed-circuit boards FREE with each cabinet. Normal price 25/-.

Unrepeatable offer at 9/6, plus 2/- post and packing.

NORCOL LTD.,
147 London Road, Camberley, Surrey

SPECIAL OFFER

1 watt S.T.C. 300 mc/s N.P.N.
Silicon Planar, 100% Transistors
limited stocks. £1 for 6.

3/- each. OC44, OC45, OC70,
OC71, OC81, OC81D, OC200,
GET16, GET20.

4/- each. AF114, AF115, AF116,
AF117, OC170, OC171.

5/- each. OC139, OC140, GET7,
GET8, GET9, XCI141, BY100, OA211.

SUN SOLAR CELL KITS

24 page Booklet on Experiments
inc. 4 Sun Solar Cells, 11/- set.

G.P.O. DIAL TELEPHONES

20/- each 35/- pair.

Send 6d. for full lists:—
inc., S.C.R., Zeners

CURSONS

78 BROAD STREET
CANTERBURY, KENT

METAL WORK

METAL WORK: All types cabinets, chassis racks, etc., to your specifications. PHILPOTTS METAL WORKS LTD., Chapman St. Loughborough.

WANTED

WE BUY New Valves and Transistors. State price. A.D.A. MANUFACTURING CO., 116 Alfreton Road, Nottingham.

URGENTLY WANTED: New, Modern Valves, Transistors, Radios, Cameras, Tape Recorders and Tapes, Watches, Tools, any quantity. S. N. WILLETTS, 16 New Street, West Bromwich, Staffs. Tel. 2392.

DAMAGED AVO METERS wanted. Models 7 and 8. Any condition. Any quantity. HUGGETTS LTD., 2-4 Pawson's Road, West Croydon.

WANTED VALVES ONLY

Must be new and boxed
Payment by return

WILLIAM CARVIS LTD.
103 North Street, Leeds 7

WANTED: Popular Brand New Valves. R.H.S., Stamford House, 538 Great Horton Road, Bradford 7.

WE BUY New Valves for cash, large or small quantities, old types or the latest. Send details. Quotations by return. WALTON'S WIRELESS STORES, 15 Church Street, Wolverhampton.

URGENTLY WANTED: New Centre Spindle for Marconi ARG40A Auto Radiogram. WESTWOOD, 44 Sandringham Road, Wombourne, Nr. Wolverhampton.

MISCELLANEOUS

ELECTRONIC MUSIC?

Then how about making yourself an electric organ? Constructional data available—full circuits, drawings and notes! It has 5 octaves, 2 manuals and pedals with 24 stops—uses 41 valves. With its variable attack you can play Classics and Swing.

Write NOW for free leaflet and further details to C. & S., 20 Maude Street, Darlington, Durham. Send 3d. stamp.

CONVERT ANY TV SET into an Oscilloscope. Diagrams and instructions 12/6. REDMOND, 42 Dean Close, Portslade, Sussex.

EDUCATIONAL

RADIO OFFICERS see the world! Sea-going and shore appointments. Trainee vacancies during 1966-67. Grants available. Day and Boarding students. Stamp for prospectus. Wireless College, Colwyn Bay.

CITY AND GUILDS (Electrical, etc.) on "Satisfaction or refund of fee" terms. Thousands of passes. For details of modern courses in all branches of Electrical Engineering, Electronics, Radio, TV Automation, etc., send for 156-page handbook—FREE. B.I.E.T. (Dept. 168K), 29 Wright's Lane, London, W.8.

RADIO OFFICERS' Training Courses. Write Principal, Newport and Monmouthshire College of Technology.

"OCEAN LINERS and other ships require Radio Officers. State if Attendance or Postal Course desired. Approved Training Centre: Radio School, 91 Lancaster Rd., Preston, Lancs."

TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for I.E.R.E., City & Guilds (Telecoms and Radio Amateurs') R.T.E.B., etc. Many unique diploma courses incl. Colour TV, Electronics, Telemetry & Computers. Also self-build kit courses—valve and transistor.

Write for FREE prospectus and find out how ICS can help you in your career.

ICS, DEPT. 541 PARKGATE ROAD,
LONDON, S.W. 11.

BOOKS & PUBLICATIONS

AUDIO, America's foremost journal. Year's subscription 43/-, specimen copy 4/-. All American radio journals supplied—list free. WILLEN (Dept. 40), 61a Broadway, London, E.15.

BOOKS & PUBLICATIONS

(continued)

SURPLUS HANDBOOKS

19 Set Circuits and Notes	3/6 P.P. 6d.
1155 Instruction Handbook	4/6 P.P. 6d.
H.E.O. Instruction Handbook	3/6 P.P. 6d.
38 Set Instruction Handbook	3/6 P.P. 6d.
46 Set Walkie-talkie circuit and notes	3/6 P.P. 6d.
88 Set Walkie-talkie Instruction Handbook	5/- P.P. 6d.
Frequency Meter BC221 Instruction Handbook	3/6 P.P. 6d.
Wavemeter Class D Handbook Mk. I, II, III	3/6 P.P. 6d.
18 Set Circuit Details and Notes	3/6 P.P. 6d.
A.R.38D Instruction Manual	15/- P.P. 1/6d.
R.107 Instruction Handbook	5/- P.P. 6d.
CE.100/B.28 Receiver Handbook	3/6 P.P. 9d.
R116/A Circuit Diagram and Details	1/9 P.P. 6d.
R1224/A Circuit Diagram and Details	1/6 P.P. 6d.
R1355 Circuit Diagram and Details	1/6 P.P. 6d.
RF24, 26, 28 Circuit Diagrams and Details	1/6 P.P. 6d.
Amplifier A1184 Circuit Diagram and Details	1/9 P.P. 6d.
Transmitter T1154 Circuit Diagram and Details (all models)	2/- P.P. 6d.
Resistor Colour Code Indicators. Indicates the value of a resistor at a glance	1/6 P.P. 6d.

All mail orders to:

Instructional Handbook Supplies

Dept. PW, Talbot House, 28 Talbot Gardens,
Roundhay, Leeds 8

PLEASE MENTION

PRACTICAL WIRELESS

WHEN REPLYING TO

ADVERTISEMENTS

SITUATIONS VACANT

City and County of Bristol Education Committee

BRISTOL TECHNICAL COLLEGE

Applications invited for following new post, duties to commence 1st September, 1966.

DEPARTMENT OF NAVIGATION, MARINE RADIO & RADAR

ASSISTANT LECTURER, Grade B, in Marine Radio & Radar. Applicants must have P.M.G. Certificate in Radio Telegraphy (first class) and B.O.T. Radar Maintenance Certificate. Special consideration given to applicants with additional qualifications such as H.N.C. and O.N.C. in Electrical Engineering or Electronics.

Salary: £955—£1,625 p.a.

Starting salary dependent upon approved experience and qualifications.

Further particulars and application forms (to be returned within 14 days) from Registrar, Bristol Technical College, Ashley Down, Bristol, 7.

Please quote Ref. T66/19/1 in all communications.

TV AND RADIO: A.M.I.E.R.E., City and Guilds, R.T.E.B. Cert., etc., on "Satisfaction or refund of fee" terms. Thousands of passes. For details of Exams. and Home-training Courses (including practical apparatus) in all branches of Radio, TV and Electronics, write for 156-page handbook—FREE. B.I.E.T. (Dept. 137K), 29 Wright's Lane, London, W.8.


RADIO AND TV Exam. and Courses by Britain's finest Home-study School. Coaching for Brit.I.R.E., City and Guilds Amateur's Licence, R.T.E.B., P.M.G. Cert., etc. FREE brochure from BRITISH NATIONAL RADIO SCHOOL, Russell Street, Reading.

A FULL-TIME TECHNICAL EXPERIENCED SALESMAN required for Retail Sales. Write, giving full details of age, previous experience and salary required to the Manager, HENRY'S RADIO LTD., 38 Edgware Road, London, W.2.

A.M.I.Mech.E., **A.M.I.E.R.E.**, City and Guilds G.C.E., etc. Become a Technician or Technologist for high pay and security. Thousands of passes. For details of Exams and Courses in all branches of Engineering, Building, Electronics, etc., write for 156-page handbook—FREE. B.I.E.T. (Dept. 169K), London, W.8.

GET THIS GREAT NEW ROAD ATLAS ONLY 3'-

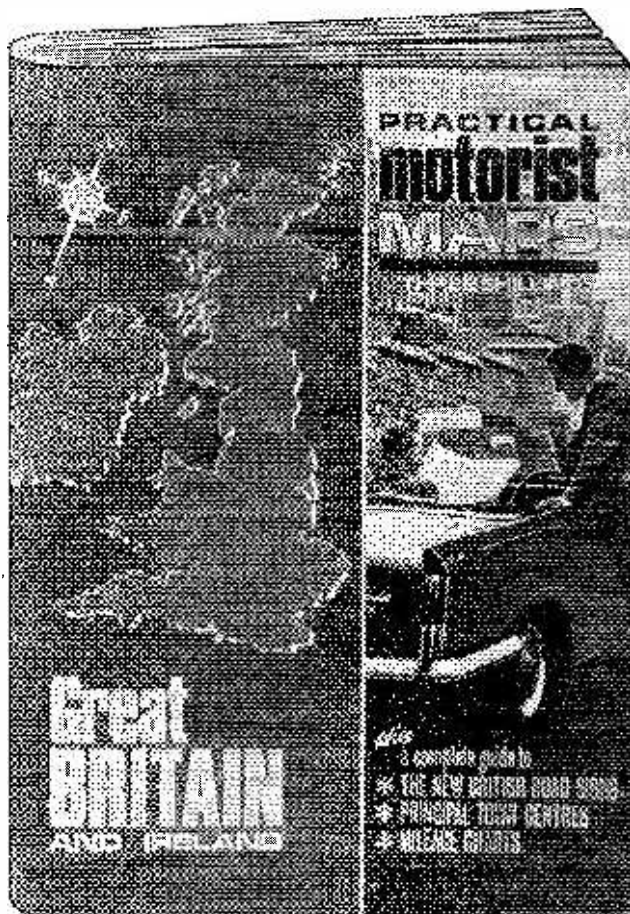- **LARGE SCALE-8 MILES TO 1"**
(Ireland 10 miles to 1")
- **A & B ROADS NUMBERED
WITH OFFICIAL CODES**
- **48 PAGES OF ROAD MAPS of Great Britain and Ireland**
- **MOTORWAYS, EXISTING AND UNDER CONSTRUCTION**
- **32 DETAILED MAPS OF PRINCIPAL TOWN CENTRES**
- **TOWN-TO-TOWN MILEAGE CHART**
- **FULL COLOUR GUIDE TO NEW BRITISH ROAD SIGNS**




PRACTICAL motorist MAPS

AT ALL NEWSAGENTS AND BOOKSTALLS

HOME RADIO (Mitcham) LTD., 187 London Road, Mitcham, Surrey. Phone: MIT 3282

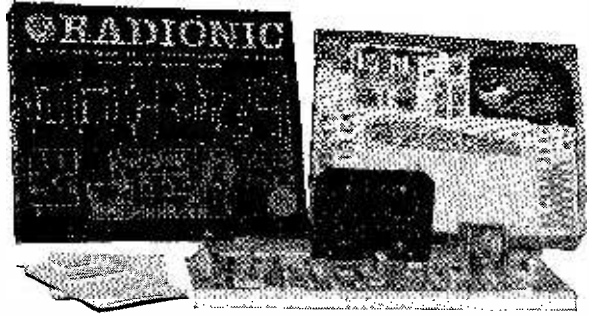One of the most interesting sections of our Components Catalogue is the **KITS SECTION**, which runs to 14 pages listing 169 different items. Here is an extract from the page dealing with **RADIONIC KITS** . . .



"Designed for both the beginner (aged 10 and upwards) and the expert in electronics. The only tools required are the spanner and a pair of scissors. Build and rebuild as often as you wish and check circuit at a glance through the transparent panel. Extra components can be purchased to expand sets as required. Adopted by Universities, Technical Colleges, Schools and the Armed Forces for electronics training."

- KT 46** Set No. 1. Fourteen different circuits can be made, including regenerative receivers for earphone operation **£5.18.6**
- KT 48** Set No. 2. Twenty different circuits. T.R.F. and Reflex receivers. **£6.19.6**
- KT 50** Set No. 3. Twenty-two different circuits, including microphone and pick-up amps. and receivers for loud speaker operation... **£10.19.6**
- KT 52** Set No. 4. Twenty-six different circuits, including a 6-transistor super-heterodyne receiver..... **£14.19.6**

Would you like to see the other 209 pages, listing 5,800 items, 900 of them illustrated, plus a 21-page supplement and a Semi-Conductor Centre brochure? Then post the coupon now with your cheque or P.O. for 9/- (7/6 plus 1/6 P. & P.). *Remember, every catalogue contains five coupons, each worth one shilling when used as directed.*

Please write your name and address in block capitals

NAME

ADDRESS

HOME RADIO LTD., Dept. PW, 187 LONDON ROAD, MITCHAM

SPECIAL OFFER

Mail Order Only

HIGH GRADE RECORDING TAPES

- | | | | |
|----------------|------|---------------------|------|
| 3in. Long Play | 2/6 | 5 1/2 in. Long Play | 16/6 |
| 5in. Long Play | 13/6 | 7in. Long Play | 19/6 |

POCKET TRANSISTOR RADIOS

- | | | |
|---|-----|---------|
| Golden Eagle Medium Wave 6 Transistors | ... | £2.7.6 |
| Golden Eagle Medium and Long Wave 7 Transistors | ... | £6.18.9 |

TRANS/CEIVER

- | | | |
|---|-----|----------|
| Raleigh 9 Transistor Trans/Ceiver 28.5 mc/s | ... | £28.10.0 |
|---|-----|----------|
- This is for the Licensed Amateur Radio Operator

MULTI-METERS

- | | | | | | |
|--|-----|----------|-------------|-----|----------|
| Eagle EP10K 10K OPV | ... | £4.0.0 | Eagle EP50K | ... | £8.19.6 |
| Eagle EP20K 20K OPV | ... | £4.15.0 | Eagle K140 | ... | £12.19.6 |
| Eagle EP30K 30K OPV | ... | £6.0.0 | Eagle K142 | ... | £15.19.6 |
| P.A. Column Speakers Five 8in. Units 10 watts 15Ω | ... | £10.10.0 | | | |
| Speaker Extension Cabinet 5in. 15/-, 8in. 22/6, 10in. 32/6, 12in. 42/6 | | | | | |

Send now for special offer list on components and audio equipment.

All goods sent by return. Post and Packing FREE.

SIGNHILD LTD., 4 GORSEY MOUNT ST., STOCKPORT, Ches

A book for every electronics engineer . . .

TRANSISTOR POCKET BOOK


by R. G. Hibberd, B.Sc., M.I.E.E., Sen.M.I.E.E.E.

A comprehensive guide to the characteristics and use of the various types of transistor now available. The manufacture of the various types of transistor, up to and including the latest epitaxial planar, field of effect and metal-oxide silicon transistors, is described in detail in order to make clear the different characteristics of each. Includes notes on the use and handling of transistors, and chapters on solid state circuit techniques and recent developments.

304 pages 250 illustrations 25s.

From your Bookseller, or in case of difficulty, 27s. from G. NEWNES LTD., SOUTHAMPTON STREET, W.C.2

NEWNES

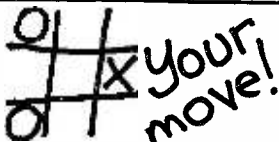

Unless you put your X between the two O's the machine will win at the next move. Even if you do, the machine puts the next O in the centre square, which not only stops you winning, but also guarantees the machine's win at the next move. Try it and see. Full circuit, wiring diagram and instructions for our unbeatable Noughts and Crosses Machine. 3/6d. post free

Wirewound Resistors 1 Watt 1%. 1Ω to 5kΩ. 3/8; to 20kΩ 4/8. 1% add 3d. Your value would to order. Special quotation for quantities, low value resistors down to 0.1Ω, multi-tapped universal shunts, etc. S.A.E. further details.
1% High Stability Resistors 2/- Full standard range plus special multimeter values. S.A.E. stock list.

PLANET INSTRUMENT CO.
25(w) DOMINION AVE., LEEDS 7

A.R.R.L. RADIO AMATEURS HANDBOOK 1966

New Edition 40/- Postage 3/-

- World Radio and T.V. Handbook 1966 by Johansen, 28/-, P. & P. 1/-.
- Transistor Pocket Book by Hibberd, 25/-, P. & P. 1/-.
- ABC's of Electronic Organs by Crowhurst, 16/- P. & P. 1/-.
- Electric Guitar Amplifier Handbook by Darr, 24/- P. & P. 1/-.
- New Radio Valve and T.V. Tube Equivalents by Babani, 6/- P. & P. 8d.
- Radio Amateur Examination Manual by B.S.G.B., 5/- P. & P. 8d.
- Practical Transistor Servicing new ed. by Caldwell, 24/- P. & P. 1/-.

Where possible 24 hours service guaranteed.

UNIVERSAL BOOK CO.
12 LITTLE NEWPORT STREET,
LONDON, W.C.2
(adjoining Lisie Street)


2 METRES 4

The thrills of VHF Amateur Radio! Complete Kit, 70-150 Mc/s, costs only 42/6 (by post, UK, 3/3 extra) also now available, new transistor Short-Wave kit model TR2 10-100 metres, ideal for beginners to Ham radio via simplified "Easy-Build" step-by-step instructions from 79/6. Write today enclosing a stamped addressed envelope for literature and full details. Overseas enthusiasts note we despatch to all parts of the world—local stamp OK for literature. "GLOBE-KING" (Regd.) precision standard products tried and trusted by Amateurs everywhere.

JOHNSONS (Radio)
St. Martins Gate, Worcester

TWO-YEAR GUARANTEED TUBES

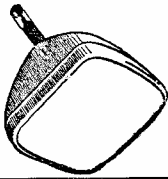14 in. 59/6
 17 in. 79/6
 21 in. 99/6
 and all Slimline Tubes



100% REGUNNED
 Add 10/- or old tube.
 110°—30/- on old tube.
 Carr. 10/6. 14in. Slim-
 line 17 and 19 in.—
 overseas postage 30/-.


EX-MAINTENANCE TESTED TUBES

17 in.—35/- Most makes and types available. 14 in.—15/-
 Guaranteed good picture. Carriage 5/- extra.

EX-RENTAL TELEVISIONS

14 in. 17 in.
 £7.10.0 £11.10.0

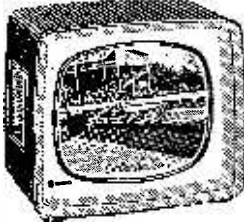12 months' 3 star Guarantee
 *Tube *Valves *Components
COLOURED FREE LIST
 Channels for all areas
 Demonstrations daily from Large
 Selection.
 Personal collection or Insured
 Carr. 14in. 20/-; 17in. 30/-.



TWO-YEAR GUARANTEE

On all our slimline TV's send for free list.

Record player cabinets 49/6.
 Latest design covered cabinet takes any modern autochanger.
 Single player cabinets 19/6.
 P. & P. 5/6.

VALVES £1 per 100. Assorted TV and Radio. Surplus ex-rental dismantled receivers. Post 4/6. Send for list.
 CONDENSERS, 10/- per 100. New Assorted Electrolytics and p.f.s. P. & P. 2/6.
 RESISTORS, 5/- per 100. New. Mostly High Stabs. Assorted. P. & P. 2/- Overseas 3/6.
 SPEAKERS, 7/9, 6in., 8in., 7 x 4in., 8 x 3in. Ex.-mfd. Salvage. P. & P. 2/3. Overseas, 4/-.

DUKE & CO. (LONDON) LTD.

621/3 Romford Road, Manor Park, E.12
 Liverpool St.—Manor Pk.—10 mins.
 Phone: ILFord 600-1-2-3. Stamp for Free List.

TECHNICAL TRAINING

in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- Institution of Electronics & Radio Engineers (Brit.I.R.E.)
- C. & G. Telecommunication Techns' Certs.
- C. & G. Supplementary Studies
- R.T.E.B. Radio/T.V. Servicing Certificate
- Radio Amateurs' Examination
- P.M.G. Certs in Radiotelegraphy
- General Certificate of Education, etc.

Examination Students coached until successful

NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, signal generator and multi-test meter—all under expert tuition. Transistor Portable available as separate course.

POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics.

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 171, Intertext House, Parkgate Road, London, S.W.11

Please send me the ICS prospectus—free and without obligation.

(state Subject or Exam.).....

NAME

ADDRESS.....

5.66

INTERNATIONAL CORRESPONDENCE SCHOOLS

SOUDOGAZ Blowlamp for the handyman



Baby "R" Heater 89/11
 Container Extra



Lumogaz "C" Lantern 69/11
 Cartridge Extra

Modern, Clean, Efficient

Ready for instant use at the strike of a match, operated by an expendable 200 Cartridge, gives instantaneous heat at 2,198°F. (1,200°C) for approx. 2½ hours. With the three accessories, solderings on lead, bronze, silver, zinc and aluminium, electrical installations, defrosting pipes, paint stripping, gutter repairs, etc., can be quickly completed.

SOUDOGAZ Blowlamp 45/- (complete with normal jet burner). Cartridge 3/9 extra. Paint Stripper, Fine Jet, Soldering Iron, each 9/- extra.

Available from hardware and ironmonger stores and all branches of Halfords.



CAMPING GAZ INTERNATIONAL DIV.
 PTC. SOUTH STREET, DORKING, SURREY.

D. & B. TELEVISION (WIMBLEDON) LTD.

131 KINGSTON ROAD · SOUTH WIMBLEDON · LONDON S.W. 19

Telephone: CHerrywood 3955

ALL BRAND NEW VALVES GUARANTEED 3 MONTHS

Postage and Packing on Valves 6d. each


AZ31	10/6	EF80	7/-	PCF80	8/4	UCH81	7/3	6F25	10/9
DAF91	7/10	EF85	7/-	PCF82	9/4	UCL82	8/8	6F28	9/8
DAF96	7/10	EF86	9/4	PCF86	10/6	UCL83	10/8	6L1	15/6
DF91	6/8	EF89	7/-	PCF801	10/-	UF41	7/6	6L18	12/6
DF92	6/8	EF91	11/-	PCF802	10/-	UF42	9/-	6/30L2	9/8
DF96	7/10	EF92	9/-	PCF806	10/-	UF80	7/6	10C2	12/-
DK91	7/10	EF183	9/8	PCF82	8/4	UF85	7/6	10F1	8/6
DK92	7/10	EL33	10/6	PCL83	9/8	UF89	7/6	10F9	8/-
DK96	7/10	EL34	9/9	PCL84	8/8	UL41	7/6	10F18	8/-
DL92	6/8	EL36	9/9	PCL85	8/8	UL46	10/6	10P13	12/6
DL94	6/8	EL41	8/-	PCL86	8/8	UL84	8/8	10P14	11/-
DL96	6/8	EL44	6/4	PL36	10/-	UY41	5/6	20P2	11/-
DY86	7/-	EM30	7/8	PL81	8/4	UY85	5/5	20L1	12/6
DY87	7/-	EM81	7/8	PL82	6/4	5Y3	5/5	20P3	15/-
EABC80	7/6	EM84	8/8	PL83	8/4	5Z4	7/6	20P4	13/-
EAF42	8/6	EM85	10/-	PL84	7/-	6V6	7/6	20P5	13/-
EB91	4/8	EY51	7/-	PL500	14/-	6X5	7/5	30C15	9/6
EBC36	11/2	EY66	7/-	PY33	9/6	R19	14/8	30C17	11/6
EBC41	7/8	EZ40	5/6	PY30	6/-	U25	10/3	30C18	10/-
ERC81	6/6	EZ41	5/6	PY81	7/-	U26	10/6	30P3	10/-
EBF80	7/-	EZ80	5/6	PY82	5/6	U191	9/9	30P11	10/3
EBF88	7/-	EZ81	5/6	PY83	9/6	U193	7/-	30L15	13/8
ECC31	7/4	EZ90	5/-	PY88	7/-	U251	11/8	30L17	11/6
ECC32	7/4	GZ32	11/-	PY800	7/-	U281	13/9	30P12	9/6
ECC33	7/4	GZ34	11/-	UY901	7/-	U282	13/9	30P24	12/-
ECC84	7/8	UBC90	6/4	UABC80	7/-	U301	13/9	30P19	12/-
ECC85	7/4	FABC80	7/6	UBC41	7/-	U801	13/9	30P1	12/6
ECF80	9/6	PC85	8/10	UBC81	7/-	U99	8/6	30PL13	12/6
ECH35	13/-	PCC38	8/10	UBF80	7/-	6F1	9/6	30PL14	11/8
ECH42	8/6	PC97	7/6	UBF89	7/-	6F13	12/8	30PL12	10/6
ECH81	7/-	PCC84	7/4	UC84	8/10	6F14	15/-	30PL14	10/6
ECL80	7/4	PCC85	7/4	UCC85	7/4	6F15	12/6	30FL12	10/6
ECL82	8/8	PCC88	12/6	UCF80	9/4	6F23	10/6	30FL18	10/6
ECL83	10/6	PCC89	10/6	UCH42	9/6	6F24	10/9		
ECL86	8/8	PCC189	10/6						

We are open 9 a.m. to 6 p.m. Monday, Tuesday, Thursday and Saturday; 9 a.m. to 7 p.m. Friday. Closed all day Wednesday

SERVICE SHEETS TELEVISION !! ALL MAKES AND MODELS 4/- P. & P. 4d.

GUITAR AMPLIFIERS with TREMOLO

12 months' guarantee (valves 3 months)

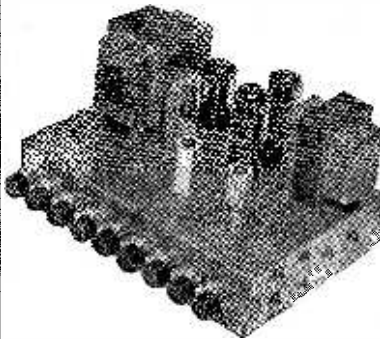

Five jack socket inputs with four separate mixing volume controls. High gain of 10 millivolts makes it suitable for all types of guitars and microphones. Separate Bass and Treble controls. Master gain control. Tremolo speed and depth controls. Remote tremolo switch socket, 7.5 and 15 ohms outputs. 30 and 50 watt valves ECC83, ECC83, EL34, EL34, GZ54. 15 watt valves ECC83, ECC83, EL34, EL34, EZ81. Two extra valves ECC83 used in the tremolo circuit. Tremolo operates on one input only. Black and gold front panel (fitted tremolo type only at present). Chassis finished silver grey hammer.

PRICES	
50 watt with tremolo	£21.17.6
50 watt less tremolo	£19.10.0
30 watt with tremolo	£16.17.6
30 watt less tremolo	£14.10.0
15 watt with tremolo	£13.17.6
15 watt less tremolo	£11.10.0

Add carriage 10/- any amplifier. Credit terms arranged. Descriptive leaflet free stamp appreciated. Suitable speakers, Bakers 12in. Guitar L.S., 5 gms. Bakers 15in. Group 50 L.S., 18 gms. Carriage free.

Cash with order only, regret no C.O.D.

"No trade or export"

STROUD AUDIO

CASHES GREEN ROAD, STROUD, GLOS.

Stroud 783

TRANSISTOR BARGAINS! FANTASTIC OFFER!

Mixed R.F./I.F./A.F. types. Untested. Only £1.0.0 per 100.

Switching Transistors. N.K.T. 124/5. Tremendous gain! 6 for 10/-.
Large Car Radio type Output Transistors. N.K.T. 405. 10/- each.

CONDENSERS

Silver Mica, Polystyrene, Ceramic. Mixed Types, values, only.
Very good selection from 3.3pf to 6,800 pf. 10/- per 100.
(Normal retail value approx. £6.0.0)
Paper 200V Condensers. .0001µf., .001µf., .002µf., .005µf., .04µf
Your choice. 7/6 per 100. £3.0.0 per 1,000.

RESISTORS

Low wattage. Mixed. 10/- per 100.
Mixed 1/2 watt to 3 watt. Close Tolerance. Very wide range of values. Polythene wrapped on cards of 10. MIXED VALUES ONLY.
Give-away price. 50/- per 1,000 plus 5/- post and packing.
(Normal retail value OVER £50.0.0!)

SIGNAL INJECTOR

R.F./I.F./A.F. Transistors, components and circuit to make.
ONLY 10/- COMPLETE

ACOS PICK-UP HEADS

Complete with needles.
This is the price that you would expect to pay for the needles only!
Monaural 14/-
Stereo 21/-
DIAMOND Stereo 28/9

Will fit most record changers. CAN BE PROFITABLE!


Many more bargains! We will send you a list with your order! You will not find better value for money ANYWHERE !!!

G. F. MILWARD

17 Peel Close, Drayton Bassett, Near Tamworth, Staffs.
Tamworth 2321 Post only


Hi-Fi

EQUIPMENT CABINETS OF DISTINCTION

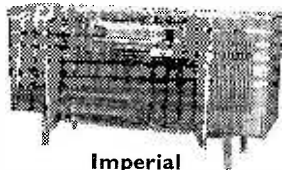

Imperial

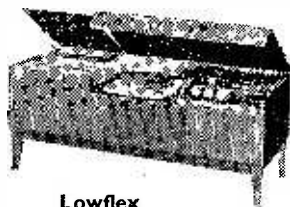- Illustrated in this advertisement are two fine cabinets from the Lewis Radio Range.
- These Cabinets are just two of a really extensive range.
- Each one carefully made by British Craftsmen and soundly constructed from the best materials available.
- Fill in coupon below to obtain FREE catalogue showing this wonderful range of cabinets.



Lowflex

FREE THE NEW LEWIS RADIO CATALOGUE

Designed to assist your choice of Cabinet
The New Lewis Radio Cabinet Catalogue—the most comprehensive ever prepared. Sent absolutely FREE!
Please send your FREE cabinet catalogue.

NAME

ADDRESS

..... (Dept. P47)
Capitals please

LEWIS radio

100 Chase Side, Southgate, London
Tel.: Palmers Green 3733/9666

LOOK! AT OUR PRICES

GERMANIUM RECTIFIERS

GJ7M 24V 1/2 Amp 24/-
or 2/6 each + 6d. postage Doz.
Postage 1/-

MINIATURE GERMANIUM DIODES

6/- doz. Postage 6d.

BY 100 SILICON RECTIFIERS

800v. P.I.V. 500mA 78/-
or 7/6 each + 4d. postage Doz.
Postage 1/-

TANK AERIALS

6 Section. Total length 10' 10".
Perfect for Vertical Aerial or Fishing
10/6 Rod.
each 1/6 P. & P.

VEROBOARD Now in Stock

2 1/4" x 5" 3/8 2 1/4" x 3 3/4" 3/-
3 1/2" x 5" 5/2 3 1/2" x 3 3/4" 3/8
Postage 6d. each extra.

TRANSISTOR HOLDERS

3 or 5 pin type 11/6
1/- each + 4d. postage Doz.
Postage 6d

PETHERICK'S RADIO SUPPLIES

Dept. P

22 HIGH STREET, BIDEFORD, N. DEVON
Tel.: Bideford 3217

KEY BOOK paper backs

HI-FI AND AUDIO

by A. T. Collins

Modern Designs for the Amateur Constructor. High Sensitivity Amplifier. Two-valve Pre-amp and Equaliser, Mains Gramophone Amplifier. Output Transformers and Loudspeakers, etc.

SIMPLE RADIO CIRCUITS

by A. T. Collins

A Complete 'Build Your Own Radio' Guide. Simple Mains Short Wave Receiver, Medium Wave Transistor Receiver, Dual Wave One-valve, etc.

3s. 6d. each from All Booksellers

or, in case of difficulty, 4s. each by post from George Newnes Ltd., Tower House, Southampton Street, London, W.C.2.

NEWNES

'PIRATE' SIGNAL BOOSTER

LUXEMBOURG CAROLINE LONDON

all for only 39/6 with the Fabulous DEWTRON Wave Trap

Just place NEAR your Transistor portable and BOOST all distant stations! Extend Battery life! NO CONNECTIONS! Use in car INSTEAD of aerial.

Send £2 (post free)
Money-back guarantee (7 days)
D.E.W. Ltd., Dept. P.W., Ringwood Road, FERNDOWN, DORSET

SWLs · SWLs · SWLs · SWLs

Hark! Hark!

—the DX is calling!



Special RX tuner
4 1/2" x 3 1/2" x 3 1/2"

JOYSTICK ANTENNA SYSTEM

Variable Frequency

This revolutionary and pat. pend aerial system possesses the unique property of an even response over all frequencies between 1.4-30 Mc/s.

Every JOYSTICK Aerial System is supplied complete with feeder and an aerial matching unit. Just connect your RX—it is ready to go and gives an unprecedented 'hit' to signal strength especially for 'chiff' and 'cave' dwellers—EVEN FROM UNDERGROUND! Naturally the advantages of using the 'JOYSTICK' 'up-in-the-clear' are even greater!

4,000 Joystick aerials all over the world have already shown that this is the first major breakthrough for 20 years in the field of aeriels. The performance for such a compact unit (7.6in. assembled) is staggering. Even the sceptics have been convinced once they have understood the basic principles and have followed the simple 'tune-up' procedure given in the detailed instructions.

New Joystick Range

There is now a whole new range of Joystick Aerial Systems—made to match your QTH, your rig and your pocket! The SYSTEMS cover SWL, TX/RX, indoor and outdoor, mobile and even a new JOYMAST! Made only in the finest materials the SYSTEMS are reliable and permanent! Read all about them in our new brochure—

GUARANTEE: Partridge operate a rigid, 100% Money Back Guarantee if you're not completely satisfied!

Read testimonials from all over the world! "Four different receivers showed improved performance over a dipole" reports the U.S.A. C.Q. Magazine.

"Excellent results, Australia, Ceylon, South Africa at good strength although lately reception conditions have been poor." W. Cummings, Lissiemouth, Scotland.

WASLEM—Henry Wilkins III of Houston, Texas, writes: "The Joystick really surprised me; it really works like you said it would... I took all my dipoles down."

L.G. Riden, Leighton Buzzard: "I cannot speak too highly of my internal Joystick which continues to give most excellent reception."

GSUGB—A. Woffenden, Bristol: "I have used the Joystick for some months now and am more than pleased with its performance... extremely good reports on 160M and 80M."

READ ALL ABOUT IT!

This ticket will bring you the new brochures by return of post!

PARTRIDGE ELECTRONICS LTD.

Caister House, Prospect Road,
Broadstairs, Kent Tel. THANET 62535


NAME

ADDRESS

P.W.5

1/2 PRICE SPECIAL RADIO CHASSIS OFFERS

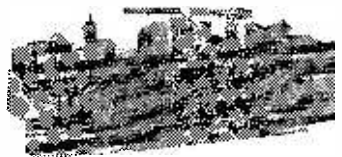HI-FI CONTINENTAL
STEREOPHONIC RADIOGRAM CHASSIS



Magnificent 'Continental' Stereophonic Radiogram Chassis with piano key switches, built-in ferrite rod aerial. Complete with two 10" elliptical loudspeakers, plus a mono/stereo 4-speed autochanger. Complete £29.19.6. Chassis only 19½ gns. Special terms available of £7.10.0 deposit followed by 18 monthly payments of £1.9.1 (total H.P. of £33.13.6) + 15/- P. & P. Send £8.5.0 now.


IMPERIAL HI-FI STEREOPHONIC RADIOGRAM CHASSIS



The Imperial Stereophonic 4 waveband chassis has the most advanced specifications yet offered in this country. There is a built-in ferrite rod aerial, seven piano key buttons. Long-Medium-Short and VHF bands. Complete with two 10" loudspeakers plus a mono-stereo 4 speed automatic record changer. Complete £41.9.6. Chassis only 29½ gns.

Special terms available of £10.7.6 deposit followed by 24 monthly payments of £1.11.8 (total H.P. £48.7.6) + 17/6 P. & P. Send £11.5.0 now.

HI-FI EMPRESS RADIOGRAM CHASSIS

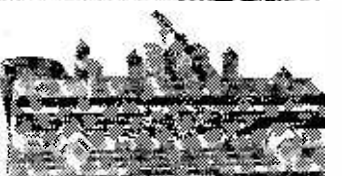

This fabulous 'Empress' Hi-Fi radiogram chassis is offered complete with 10" loud-speaker plus 4 speed autochanger. At only £24.3.0. This is the bargain of the year. Chassis only 15½ gns.

Special terms available of £6.3.0 deposit followed by 18 monthly payments of £1.3.4 (total H.P. £27.3.0) + 15/- P. & P. Send £6.18.0 now.

All Lewis Radio equipment including valves are fully guaranteed for one year. Send your cheque or P.O. today while stocks last to Dept. P.46.

LEWIS radio

LEWIS RADIO, 100, CHASE SIDE, SOUTHGATE
LONDON, N.14 - Telephones: PA1 3733 / 9666

I.F. TRANSFORMERS:—This month's snip! Brand new, small size, 2 different types Television I. F.'s and only 5/- PER PAIR! Limited quantities available.

CAPACITORS:—
100 x 300 x 100 x 16 MPD, 275v. } 7/6 each
100 x 400 x 16 275v. } + 1/- P. & P.

AERIAL WIRE:—Still some of this wonderful insulated wire left at old prices—25ft. coil, 1/8; 50ft. coil, 2/8. P. & P. 6d.

BATTERY ELIMINATORS:—For value for money you can't beat our "QUANTA" 9v. power supply. Complete and ready to use in place of a PP3 etc, it costs only 18/3 + P. & P. 1/-. For the connoisseur, the slightly more sophisticated Eagle Model LA-6P with a self-contained pilot lamp is still cheap at 23/6 + 1/- P. & P.

TEST METERS:—1. Model 200H—A wonderful buy for the discerning engineer with a limited budget. 20 K. ohms per volt makes this an extremely accurate instrument that measures voltages, current, resistance, capacitance and decibels. At £4.9.6, it is second to none!

2. Model Test 7—At last, an inexpensive multi-meter with a mirror included in the scale. Why pay over £20 when this will often do the trick for only £2.5.0.

3. Avo-Minor Mk. IV—Still one of the best and all British, £9.10.0.

4. Taylor 127A—Excellent value, £10.10.0. Full range of panel and multi-meters always in stock.

LOUDSPEAKERS:—At really keen prices—all 8 ohm, brand new. 2in. and 2½in., 7/6 each, 3in. and 3½in., 9/- each; 4in., 10/6; 5in. 12/-, All plus 1/-, P. & P.

AMPLIFIERS:—Veritone 60W, £26.19.6 complete; 30W, £19.15.0 complete; 4/5W 6 gns. complete but less cover; 3/4W Record Player amplifier—ready to plug in and use. Manufacturers surplus. Brand new, £2.19.6. Mullard OA81 Diodes, brand new, 2/3 post free. Mullard OA91 Diodes, brand new, 2/6 post free. Mullard OA95 Diodes, brand new, 2/6 post free.



**BOTHWELL ELECTRIC
SUPPLIES (Glasgow) LTD.**
54 EGLINTON STREET
GLASGOW, G.5

Member of the Lander Group

is at your disposal whether you are a personal or mail order customer. Use our FREE ADVISORY SERVICE by writing or phoning, SOUTH 2904—Trade enquiries welcomed.

PADGETTS RADIO STORE

OLD TOWN HALL,
LIVERSEDEGE, YORKS.

Telephone: Cleckheaton 2866

18 Set Receiver, 4 Valve Battery S/H 6-9 Mc/s. Clean condition, 12/6. Post 5/-.

68 Set Receiver, 4 Valve Short Wave Battery Set, New 15/6. P/P 5/-.

500 Micro-Amp Meter from 18 Set Tx., 7/6. P/P 1/3.

New 100 Micro-Amp Meter from 68 Set Tx. 12/6. P/P 1/3.

Muirhead Pattern Slow Motion Drives. Removed from units, 5/-, P/P 1/3.

Magic Eye with Holder, Ex Units Octal Base, 2/6. P/P 1/3.

New Boxed Tube Unit, CR.100. Complete with Two small CRT Tubes VCRX333 and VCRX286. Plus 21 small valves and 0-1ma. meter. Relays removed, 57/-, Carr. 10/-.

Reclaimed Tubes, Six months' guarantee. AW43/30, 30/-; MW43/80, 30/-; 2W 43/69, 30/-; CRM172, 30/-; CRM142, 17/-; 12" Tubes 10/-; 17" tubes perfect but without guarantee, 17/- each. Carriage on any tube in G.B., 10/-.

Specialty Selected Nearly New Valves with 6 months' guarantee. Single valves, Post. 7d.

EF90	6/-	807	5/-	EF91	2/-
PCC84	5/6	AP12	1/6	6K8	1/9
PCF80	5/6	ECL80	3/6	6K8	2/-
PL36	6/-	ECC83	5/-	6V6	1/9
PL81	5/6	ECC82	4/3		

VALVE LIST
Ex Equipment, 3 months' guarantee
Single Valves Post 7d.

EF90	1/6	KT36	5/-	6F14	5/-
ECL80	1/6	PCF80	2/-	10C2	5/-
EF91	9d.	PCC84	2/-	10P13	2/6
EB91	9d.	PCL82	4/-	10P14	5/-
EF90	3/-	PCL83	3/-	20D1	2/-
ECC81	3/-	PCL84	3/-	20L1	2/-
ECC82	3/-	PCL85	3/-	20P1	4/-
ECC83	4/-	PZ30	5/-	20P4	6/6
EL84	5/-	PY81	1/6	U801	8/6
EY51	2/6	PY82	1/6	U329	5/-
EF50	1/-	PL81	4/-	U301	5/-
EY96	5/-	PL36	5/-	U311	5/-
6K25	5/-	PY33	5/-	U281	5/-
6U4	5/-	6B8	1/6	U282	5/-
6P25	5/-	6F1	1/-	U25	5/-

Motors removed from Washing Machines 1/2 h.p. with pulley, 26/-; Carriage 10/-; Hoover M.K.L. 15/-; Carriage 7/6, 1/2 h.p. motor.


13 Amp. Double Sockets, Brown Surface Type, 3/-; Post 1/6, 6 for 18/-; Post paid.

New Jap. Earpieces complete with lead and plug, 8 ohms, 3 or 5mm., 1/11 or 20/- per dozen, Post Free.

Diodes. Top grade. No duds, 3/- per doz., Post Paid.


Perfect Speakers removed from T.V. sets. Round 6" 6/-; Roll 6 x 4, 3/-; Goodmans 7 x 4, 5/-; 6" Round, 3/-; Philips 5" Round, 2/-; Plus Post on any Speaker 2/9, 6 x 4, 6" and 5" Round Speakers, 6 for 20/-; Post Paid.

BBC2 (625 LINE) TV AERIALS

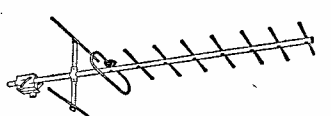

Mast Mounting Arrays, 9 element, 45/-; wide spaced high gain, 11 element, 55/-; 14 element, 62/6; Wall Mounting with Cranked Arm 9 element, 60/-; wide spaced high gain, 11 element, 67/6; 14 element, 75/-; Chimney Arrays Complete, 9 element, 72/-; wide spaced high gain, 11 element, 80/-; 14 element, 87/6. Loft Arrays, 7 element, 32/6; wide spaced high gain, 11 element, with Tilting Arm, 62/6; 14 element 70/-; All high gain units have special Multi-rod Reflector. Low loss co-axial cable, 1/6 per yard. UHF transistor pre-amps from 75/-.

BBC · ITV · F.M. AERIALS

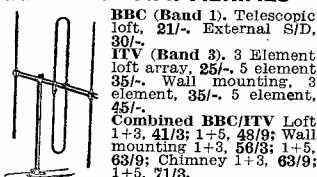

BBC (Band 1), Telescopic loft, 21/-; External S/D, 30/-
ITV (Band 3), 3 Element loft array, 25/-; 5 element 35/-; Wall mounting, 3 element, 35/-; 5 element, 45/-
Combined BBC/ITV Loft 1+3, 41/3; 1+5, 48/9; Wall mounting 1+3, 56/3; 1+5, 63/9; Chimney 1+3, 63/9; 1+5, 71/3.
VHF transistor pre-amps from 75/-.
F.M. (Band 2), Loft S/D, 12/6, "H", 30/- 3 element, 52/6. External units available. Co-ax cable 8d. yd. Co-ax plugs, 1/3. Outlet boxes, 4/6. Diplexer Crossover Boxes, 12/6. C.W.O. or C.O.D. P. & P. 4/6. Send 6d. stamps for illustrated lists.

K.V.A. ELECTRONICS (Dept. P.W.)
27 Central Parade, New Addington
Surrey
LOD 2266

NEW VALVES!

Guaranteed Set Tested
24 HOUR SERVICE

1R5	4/-	DL33	6/6	EF89	4/3	PY82	4/9
1R5	3/3	DL35	4/9	EF91	2/9	PY83	5/3
1T4	2/-	DL92	4/3	EL33	6/3	PY800	5/11
384	4/3	DL94	5/-	EL41	7/6	U25	8/-
3V4	5/-	DL96	5/11	EL84	4/6	U26	8/6
6K7G	1/3	DY86	8/3	EY81	5/11	U301	10/6
6K8G	3/3	DY87	6/9	EY86	5/6	U801	9/6
6Q7G	5/6	EABCO8	5/6	EZ40	5/6	U801	14/9
6V6G	3/-	EB91	1/9	EZ80	3/9	UABC80	5/3
10C2	11/-	EB041	8/3	EZ81	4/3	UAF42	6/11
20L1	11/-	EBF80	5/9	KT61	6/3	UBC41	6/6
20P3	10/6	EBF89	5/9	PCC84	5/6	UBF60	5/8
20P4	13/-	ECC81	3/3	PCC89	9/9	UBF69	5/9
20P5	11/6	ECC82	4/6	PCF80	6/6	UCC84	7/11
30FL1	9/3	ECC83	4/6	PCF82	5/9	UCC85	6/3
30L15	9/9	ECC85	5/3	PCF805	8/3	UCF80	8/3
30LL13	10/3	ECH85	9/9	PCL82	6/9	UCH42	7/9
CL83	8/6	ECH85	9/9	PCL83	8/9	UCH31	6/6
DAC32	6/9	ECH42	7/9	PCL84	7/6	UCL82	7/6
DAP91	3/3	ECH81	5/6	PL86	9/-	UCL83	9/-
DAP96	5/11	ECL80	5/11	PL81	6/9	UCL83	9/-
DF88	7/6	ECL82	6/6	PL82	5/-	UF41	6/6
DF91	9/-	ECL85	9/-	PL83	5/11	UF89	5/6
DF96	5/11	EF89	3/6	PL84	8/-	UL41	7/9
DK32	7/-	EF41	5/9	PY32	8/9	UL84	5/9
DK91	4/-	EF80	4/3	PY33	8/9	UY41	4/3
DK92	7/9	EF85	4/6	PY80	4/9	UY85	4/9
DK96	6/3	EF86	6/3	PY81	5/-	Z77	2/9

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any parcel insured against damage in transit 6d. extra. Office address, no callers.

GERALD BERNARD
83 OSBALDESTON ROAD
STOKE NEWINGTON LONDON N.16

Packed with concise servicing data
 . . . the "gen" at your fingertips in one
 authoritative volume for day-to-day use!

TAPE RECORDER SERVICING MANUAL

by **H. W. HELLYER**
 A.M.T.S., A.I.P.R.E., A.M.I.S.M.


Tape recorders present special problems to the service engineer. Many decks are quite complex mechanically, whilst high performance is required of the associated electronic circuitry. The best aid the service engineer can have in dealing with recorders is adequate information. This book provides concise

**A book to save
 you time and
 make you profit**

service data, including circuit diagrams and numerous layout diagrams and views of mechanisms and adjustments, for the majority of tape recorders and decks that have been released in this country. The notes are compiled partly from manufacturers' official data, from trade sources, and also from bench notes and observations made by the author in the course of a number of years' practical servicing. Also contains an authoritative introductory section on the principles and practice of tape recording, practical repair procedures, and microphones and matching.

**Covers 282 models
 in 344 pages
 supported by over
 345 drawings,
 exploded views and
 circuit diagrams
 63s.**

**Published by
 NEWNES**

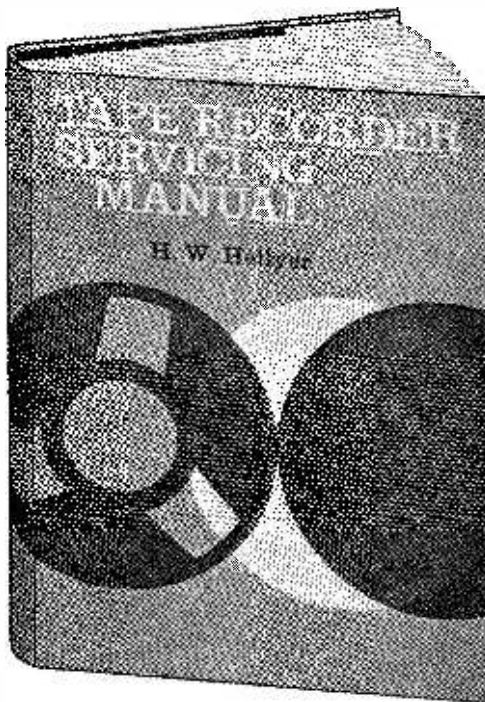

Alba, Allegro, Amplion, B.S.R., Baird, Brenell, Bush, Butoba, Collaro, Cossor, Dansette, Defiant, Dynatron, E.M.I., Editor, Ekco, Elizabethan, Elpico, Elpico-Geloso, Ferguson, Ferranti, Ferrograph, Ficord, Fidelity, G.B.C., G.E.C., Garrard, Geloso, Gramdeck, Grundig, H.M.V., Hagen, Kolster-Brandes, Korting, Magnavox, Motek, Murphy, Peto-Scott, Philco, Philips, Playtime, Portogram, R.G.D., Recording Devices, Regentone, Robuck, Simon, Sobell, Sonomag, Sony, Sound, Soundmirror, Steelman, Stuzzi, Telefunken, Thorn, Truvox, Ultra, Verdik, Volmar, Walter, Winston and Wyndsor.

**MAKE SURE
 OF YOUR
 COPY
 NOW!**

from your bookseller, or:—

Complete this form and post today

To George Newnes Ltd., Tower House, Southampton Street, London, W.C.2.

Please send me TAPE RECORDER SERVICING MANUAL for which I enclose remittance of 63s.

Name

Address

Head Office and Warehouse

44A WESTBOURNE GROVE

LONDON W2

Tel. PARK 5641/2/3

Please write for full catalogue

Z & AERO SERVICES LTD

Retail Shop

85 TOTTENHAM COURT ROAD

LONDON W1

Tel. LANGHAM 8403

Open all day Saturday

Please send all correspondence and Mail-Orders to the Head Office

When sending cash with order, please include 2/6 in £ for postage and handling
MINIMUM CHARGE 1/6. No C.O.D. orders accepted

0A2	6/-	8AF4	10/-	6CL6	9/-	6V6	9/-	
0A3	11/-	8AF6G	11/-	6CW4	12/-	6V6G	5/-	
0A4G	20/-	8AG5	2/8	6CY5	10/-	6V6GT	7/6	
0B2	6/-	8AG7	6/-	6CY7	11/-	6WC5	7/-	
0B3	6/-	8AH6	10/-	6D1	2/-	6X4	4/-	
0C2	14/-	8AJ5	9/-	6D3	2/8	6X5	7/-	
0C3	6/-	8AK5	5/0	6D4	15/-	6X6GT	6/-	
0D3	8/-	8AK6	7/-	6D6	2/8	6Y6G	10/-	
1A3	3/-	8AL5	3/-	6D0C	12/6	6Z4	6/-	
1A5GT	5/-	8AM5	2/8	6DK6	6/-	7A4	3/-	
1A7GT	3/-	8AM6	4/-	6DQ6	11/-	7A6	7/-	
1B3GT	7/-	8AN4	15/-	6RA8	11/-	7A7	6/-	
1C5GT	6/-	8AN5	15/-	6EV5	12/-	7A8	5/-	
1D5	17/6	8AR6	6/-	6E13	6/8	7A7	13/-	
1D6	8/-	8AQ4	5/-	6E4	30/-	7A7	7/-	
1G4GT	7/-	8AQ5	6/-	6E5	5/-	7B4	3/-	
1G6GT	7/-	8AQ5A	7/8	6E6	3/-	7B5	10/-	
1H5GT	7/-	8AQ6	8/-	6E8G	5/-	7B6	11/-	
1L4	17/6	8AR5	6/-	6E8G	5/-	7B7	7/-	
1L6	27/6	8AR6	6/-	6E13	6/8	7C4	4/6	
1N5GT	3/-	8ARS	17/6	6F14	15/-	7C5	10/-	
1R4	6/-	8AS9	5/-	6F15	11/-	7C6	7/-	
1R5	5/-	8AS8	5/-	6F17	6/-	7C7	5/-	
1R4	5/-	8ASTG	20/-	6F19	6/8	7D3	3/-	
1R5	4/6	8AT0	3/6	6F20	10/-	7D5	3/-	
1R4	3/6	8AUGT	6P23	4/6	7D8	7/-	7D9	7/-
1T5GT	6/-	8A15	15/-	6F25	10/8	7E5	5/-	
1U4	5/-	8A06	6/-	6F32	3/-	7E6	4/-	
1U5	6/-	8A06	6/-	6G6G	2/8	7E7	10/-	
1V	5/-	8AW8A	14/-	6H6	2/-	7E7	10/-	
1Y2	10/-	8AX4GT	8/-	6J4	9/-	7J7	14/-	
1X2B	3/6	8AX5GT	6/-	6J5G	4/6	7K7	10/-	
1Z2	35/-	8B12	12/8	6J5GT	4/6	7Q7	9/-	
2A3	5/-	8B4G	16/-	6J6	3/8	7K7	12/-	
2A4G	30/-	8B7	5/-	6J7	9/-	7S7	18/-	
2A6	6/-	8B8	7/-	6J7G	5/-	7Y4	8/-	
2A7	7/-	8BA6	5/-	6K6GT	8/6	7Z4	6/-	
2CW4	12/-	8B17	15/-	6K73	2/-	8B5W6	6/-	
2D21	6/-	8BC4	17/6	6K7G	5/-	9D2	3/6	
2E24	40/-	8BE6	5/6	6K8	3/-	10C2	13/-	
2E26	30/-	8BF6	6/-	6K23	7/6	10D1	7/-	
2G21	12/-	8BG6G	15/-	6K25	24/-	10F1	14/-	
2X2A	3/-	8BH6	7/8	6L1	10/-	10F8	8/-	
3A4	4/-	8B35	15/-	6K73	2/-	8B5W6	6/-	
3A5	3/-	8B38	8/-	8L6GC	3/-	10L1	7/6	
3A8GT	3/-	8BJ7	7/-	6L7	5/-	10P13	12/8	
3D6	4/-	8BK4	25/-	6L18	8/-	10P14	13/-	
3E29	60/-	8BL7GT	9/-	6N7	8/-	10Y	15/-	
3G4	8/-	8BN6	7/6	6P1	11/-	12A5	10/-	
3O5GT	6/8	8BQ6	11/-	6P25	12/8	12A6	3/-	
3R4	5/-	8BQ7A	8/-	6P28	12/6	12A7	10/-	
3V4	6/-	8BR7	12/-	6G07	6/-	12A8GT	5/-	
5E4GY	9/-	8BR8	5/-	6E7	6/-	12AC6	8/-	
5T4	8/-	8BS7	17/-	6E87	7/-	12AD6	8/-	
5U4G	9/-	8BW6	9/8	8A7	8/-	12AE6	7/6	
5U4GB	6/8	8BW7	10/-	8E7	9/-	12AL5	7/-	
5V4G	9/-	8BZ6	6/-	8D7GT	5/-	12B5	7/-	
5X4G	8/-	8BZ7	11/-	8E7	7/-	12AT6	5/-	
5Y8GT	5/-	8C4	2/6	68G7	6/-	12AT7	4/-	
5Y4G	9/-	8C5	3/-	8E7	7/-	12AU7	6/-	
6E3	7/6	8C6GT	4/-	8E7	7/-	12AU7	6/-	
6Z4G	8/-	8C6	4/-	8SL7GT	5/-	12AU7A	6/-	
6/80L2	11/-	8C8G	7/-	68N7GT	4/6	12AV6	6/-	
6A7	10/-	8C9	11/-	68Q7	7/-	12AV7	3/-	
6A8	3/-	8C31	12/-	68R7	8/-	12AV6	20/-	
6A8B	6/8	8C36	5/-	68S7	3/-	12AX7	7/-	
6AB7	4/-	8C6DA	6/-	68U7GT	10/-	12AY7	10/-	
6AC7	4/-	8C7	17/-	6T8	7/-	12BA4	9/-	
6AD4	18/-	8C6GT	10/-	6U4GT	10/8	12BA6	6/-	
6AD7G	10/-	8C6	6/-	6U8	7/8	12B6	5/8	

First Quality Fully Guaranteed



ELECTRONIC VALVES

12BH7A	7/-	30L1	6/6	8840	10/-	DL75	10/-
12BY7A10	7/-	30L15	12/6	6060	5/-	DM70	5/6
12C8	4/-	30L17	14/-	6080	25/-	DM160	10/-
12F5GT	8/-	30P12	10/-	6136	9/-	DY80	7/-
12H6	3/-	30P16	7/8	6146	27/6	DY86	8/-
12J5GT	3/-	30P18	7/-	7586	22/6	DY87	9/-
12J7GT	7/6	30P19	14/-	7895	22/6	EP183	8/-
12K7GT	7/-	30P1L	12/6	9001	4/-	EP184	8/-
12K8	8/-	30P1L3	12/6	9002	5/6	EP184	8/-
12Q7G	4/-	30P1L4	12/6	9003	9/-	EP184	8/-
12S7	7/-	35A3	12/-	9005	15/-	E180CC	8/-
12S7A	4/-	35A5	11/-	9006	2/8	E180F	20/-
12S7GT	4/-	35B5	12/-	A2293	16/-	E180G	7/6
12S7GT	4/-	35C3	6/8	AZ11	6/-	EAC91	4/-
12S7GT	4/-	35D5	12/-	AZ12	9/-	EAF42	9/8
12S7GT	4/-	35LACT	7/-	AZ31	9/-	EB41	5/-
12S7GT	4/-	35W4	5/-	AZ41	7/-	EB91	3/-
12S7GT	4/-	35Z3	10/-	C1C	12/-	EBE21	7/6
12S7GT	4/-	35Z4GT	8/6	CE3D	4/-	EBE33	7/6
12S7GT	4/-	35Z5GT	8/-	CL33	3/-	EBE41	8/6
12S7GT	4/-	35Z6	12/-	CF31	7/-	EBE48	6/8
12S7GT	4/-	50B5	7/-	DA1	5/-	EBE90	5/-
12S7GT	4/-	50C5	6/6	DA30	10/-	EBE91	6/-
12S7GT	4/-	50L6GT	6/6	DA41	40/-	EBF2	12/-
12S7GT	4/-	50Y6GT	10/-	DAC32	7/-	EBF80	7/6
12S7GT	4/-	75B1	5/6	DAP91	4/6	EBF83	9/-
12S7GT	4/-	75C1	12/-	DAP92	7/-	EBF89	7/-
12S7GT	4/-	80	6/-	DAP96	7/-	EBL1	14/-
12S7GT	4/-	85A1	25/-	DC70	12/-	EBL21	11/-
12S7GT	4/-	85A2	8/6	DF33	8/-	EBL31	20/-
12S7GT	4/-	85A3	5/6	DF72	7/-	EC86	12/-
12S7GT	4/-	90C1	12/-	DF73	7/-	EC88	12/-
12S7GT	4/-	135BTAL5	10/-	DF91	3/-	EC89	22/-
12S7GT	4/-	2524G	8/-	DF92	2/6	EBL21	11/-
12S7GT	4/-	2525	10/-	DF96	7/6	EBE13	20/-
12S7GT	4/-	2526GT	11/-	829	30/-	EH63	6/-
12S7GT	4/-	2527	7/-	822	20/-	DH76	5/6
12S7GT	4/-	30	4/-	854	8/-	KK40	11/-
12S7GT	4/-	30A5	7/-	955	9/-	DK91	5/-
12S7GT	4/-	30C1	7/6	956	2/-	DK92	9/-
12S7GT	4/-	30C15	11/-	957	5/-	EK96	8/6
12S7GT	4/-	30C17	13/-	958	4/-	DL33	6/6
12S7GT	4/-	30C18	11/-	959	8/-	DL35	5/-
12S7GT	4/-	30F8	11/-	954	8/-	DL63	3/-
12S7GT	4/-	30FL1	12/-	5670	10/-	DL68	10/-
12S7GT	4/-	30FL2	12/-	5763	10/-	DL70	8/-
12S7GT	4/-	30FL4	12/-	5814A	10/-	DL73	12/-

MULTIMETERS

Type 108-IT; 24 range precision portable meter, 5000 o.p.v.; DC Volts: 2.5-10-250-500-2500V. A.C. Volts: 10-50-100-250-500-2500V; D.C. current 0.5-5-50-500mA. Resistance 2000-20,000 ohms to 200 megohms. Power output calibration in A.C. for 600 ohms lvs. Complete with prods and batteries £55.0. P. & P. 7/6.

Type U-1; sensitivity 1000 o.p.v. A.C./D.C. voltage ranges 10-50-200-500-1000V; D.C. current ranges 100-500mA; Resistance ranges 2000-20,000 ohms. Complete with prods and battery, £22.0. P. & P. 7/6.

COUNTER TUBES

GR10A—10-way register-indicator tube, 45/-.
GC10/4B—bi-directional 10-way computing tube, double pulse, 50/-.
GC10B—scale-of-ten counter, 35/-.
GC10D—scale-of-ten counter for single pulse operation 55/-.
GS10D—Bi-directional 10-way selector tube, 55/-.
810H—as GS10D but physically small, 40/-.

SiC HALF WAVE RECTIFIERS.

HALF WAVE, 3 AMPS D.C.

RS310, 140 pIV 4/-	RS350, 700 pIV 7/6
RS320, 280 pIV 5/-	RS360, 340 pIV 9/-
RS330, 420 pIV 6/8	RS370, 380 pIV 9/-
RS340, 560 pIV 7/-	RS380, 1120 pIV 10/-

PHOTO CELLS GS18

Caesium Antimony, side-on window. HT 160V. sensitivity 160µA/Lumen 5/- P.P. 1/6

SILICON BRIDGE CONNECTED POWER RECTIFIERS, 100 P.I.V.

1B20K10, 2 amps DC (1.4"x1.4"x6")	25/-
1B40K10, 4 amps DC (1.4"x1.4"x6")	30/-
1B100K10, 10 amps DC (2.25"x2.25"x1")	35/-

GERMANIUM DIODES

OA5	4/6	OA81	2/-	CG4E	2/-
OA6	4/-	OA85	3/-	CG10E	1/6
OA10	8/-	OA86	3/6	CG12E	2/-
OA70	2/-	OA90	2/-	CG23	1/6
OA73	1/6	OA91	2/3	GEX44	1/8
OA79	2/3	OA95	3/-	GEX54	2/-

TRANSISTOR COMPLEMENTARY PAIRS:
2N697 (NPN) and 2N1132 (PNP) 60/- per pair

SEMICONDUCTORS

Transistors, Microwave diodes, Detector diodes, Rectifiers and silicon zone diodes and power rectifiers in silicon or germanium. Leader with prices and short specifications available on request.

CLEARANCE OFFER OF METERS

500µA D.C. MC 1in. round flush, ringnut mounting, calibrated 0 to 1	17/6
500µA D.C. MC 2in. round flush, ringnut mounting	17/6
500µA D.C. MC 2in. round flush, for clip fixing, undrilled flange	10/-
1mA D.C. MC 2in. round flange mounted, sealed, calibration 0-3/30/300	12/-
1mA D.C. MC 2in. round flange mounted	17/6
1mA D.C. MC 2in. square flange mounted	17/6
30mA D.C. MC 2in. round flange mounted	10/-
50mA D.C. MC 2in. square flange mounted	12/6
50mA D.C. MC 2in. round flange mounted	10/-
75mA D.C. MC 1in. round flush, clip mounted	12/6
100mA D.C. MC 1in. round flush, clip mounted	12/6
100mA D.C. MC 1in. round flange mounted	15/-
100mA D.C. MC 2in. round flange mounted	12/6
150mA D.C. MC 1in. round flush, clip mounted	12/6
500mA D.C. MC 2in. round flange mounted	12/6
25A D.C. MI 2in. round projecting	7/6
100A A.C. MI 2in. round flush, clip mounted	12/6
15 V. AC. MI 2in. round flange mounted	12/6

The following blueprints are available from stock. Descriptive text is not available but the date of issue is shown for each blueprint. Send, preferably a postal order to cover cost of the blueprint (stamps over 6d. unacceptable) to Blueprint Department, Practical Wireless, George Newnes Ltd., Tower House, Southampton Street, London, W.C.2.

The Strand Amplifier } (Oct. 1962)	5/-	The Celeste 7-transistor Portable Radio } (June 1963)	5/-
The PW Signal Generator }		The Spinette Record Player }	
The Berkeley Loudspeaker Enclosure... } (Dec. 1962)	5/-	Transistor Radio Mains Unit }	5/-
The Luxembourg Tuner }		7 Mc/s Transceiver }	
The PW Troubadour } (June 1962)	7/6	The Citizen (December 1961) }	5/-
The PW Everest Tuner }		The P.W. 35-watt Guitar Amplifier (May 1964) ... }	5/-
The PW Britannic Two } (May 1962)	6/-	The Mini-amp (November 1961) }	5/-
The PW Mercury Six }		The PT Multimeter (October 1961) P.T. }	5/-
Beginner's Short Wave Two } (Nov. 1963)	5/-	The Beginner's Short Wave Superhet (Dec. 1964) ... }	5/-
S.W. Listener's Guide }		The Empire 7 Three-band Receiver (May 1965) ... }	5/-
Beginner's 10-watt Transmitter }	5/-	Electronic Hawaiian Guitar (June 1965) }	5/-
Transmitting and Aerial Data }		Progressive S.W. Superhet (February 1966) }	5/-
P.W. "Sixteen" Multirange Meter }	5/-		
Test Meter Applications Chart }			

★ PLEASE NOTE THAT WE CAN SUPPLY NO BLUEPRINTS OTHER THAN THOSE SHOWN IN THE ABOVE LIST. NOR ARE WE ABLE TO SUPPLY SERVICE SHEETS FOR COMMERCIAL RADIO, TV OR AUDIO EQUIPMENT. ★

Before using the query service it is important to read the following notes:

The PW Query Service is designed primarily to answer queries on articles published in the magazine and to deal with problems which cannot easily be solved by reference to standard text books. In order to prevent unnecessary disappointment, prospective users of the service should note that:

- (a) We cannot undertake to design equipment or to supply wiring diagrams or circuits, to individual requirements.
- (b) We cannot undertake to supply detailed information for converting war surplus equipment, or to supply circuitry.
- (c) It is usually impossible to supply information on imported domestic equipment owing to the lack of details available.

(d) We regret we are unable to answer technical queries over the telephone.

(e) It helps us if queries are clear and concise.

(f) **We cannot guarantee to answer any query not accompanied by the current query coupon and a stamped addressed envelope.**

QUERY COUPON

This coupon is available until 4th May, 1966 and must accompany all queries in accordance with the rules of our Query Service.

PRACTICAL WIRELESS, MAY, 1966



16 PAGE TRANSISTOR LIST
Send 6d. stamp for new list
all types of semi-conductors.
Valves and Quartz Crystals.










1966 150-PAGE CATALOGUE

Fully detailed and illustrated components, equipment and Hi-Fi. All types and makes. 5000 Stock lines. 500 Transistors and Devices. 1000 Quartz Frequencies. 800 Valves and Tubes. The Finest and Largest Range available. A mine of information.

Price 6/- post paid.

FREE with Catalogue, 6/- Value Discount vouchers gives 2/- in pound discount on purchases.
(Vouchers must be returned with orders)

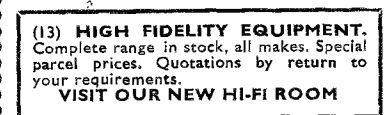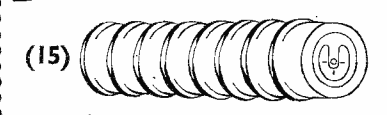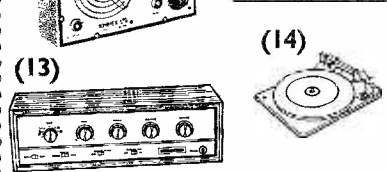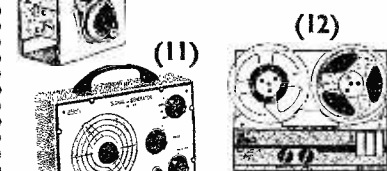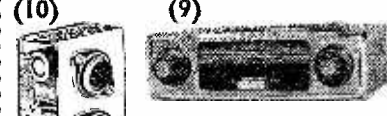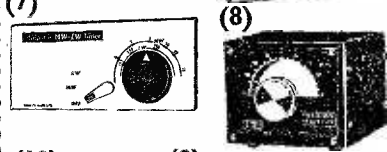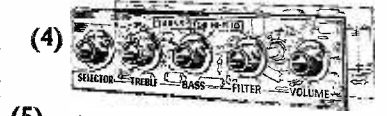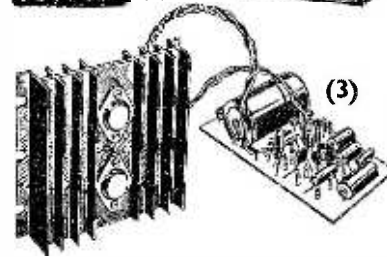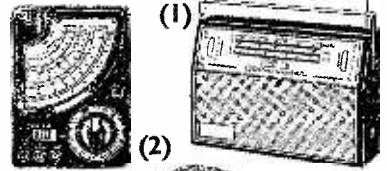CATALOGUE COSTS NOTHING AFTER USING VOUCHERS



(1) GLOBEMASTER MW/LW/SW PORTABLE

Full 3-waveband tuning. Pushbutton wave-change. Superhet printed circuit. Black-chromed cabinet 11 x 7 1/2 x 3 1/2 in. (SW 17-50 metres). Ear/Record sockets.

TOTAL COST TO BUILD £8.19.6 P.P. 3/6

(8) V.H.F. FM TUNER

87/105 Mc/s Transistor Superhet. Geared turning. Terrific quality and sensitivity. For valve or transistor amplifiers. 4 x 3 1/2 x 2 1/2 in.

TOTAL COST TO BUILD £6.19.6 P.P. 2/6
(Cabinet Assembly 20/- extra)

10 AND 20 WATT MONO AND STEREO HI-FI UNITS

(3) **POWER AMPLIFIERS.** 10 watts RMS output. 100mV input. 30 c/s to 20 kc/s ± 1dB. 6-Transistor Push-Pull. Panel size 4 x 2 1/2 x 1 in. H/S 4 x 4 in.

TPA10/3 3-5 ohm speaker. £5.10.0, p.p. 2/6
TPA10/15 12-16 ohm speaker., £5.19.6, p.p. 2/6
(Mains unit for 1 or 2 amplifiers, 59/6, p.p. 2/6)

(4) **PREAMPLIFIERS.** 8 input selector Treble, bass, volume, filter controls. 1.5mV to 300mV inputs. Battery operated or from Mains Unit. Output up to 150mV RMS.

For 10 or 25 Watt Amplifiers.
MP2 Mono 9 1/2 x 2 1/2 x 2 in. £5.10.0, p.p. 2/6 (brown and gold front panel 8/6).
SP4 Mono/Stereo, 9 x 3 1/2 x 1 1/2 in., £10.19.6, p.p. 3/6 (front panel plate 12/6).

The Finest High Fidelity at Unbeatable Prices

● ALL UNITS BUILT AND TESTED

(12) BUILD A QUALITY TAPE RECORDER

Three speeds—3 watts. Complete kits with new "363" decks. Supplied as preassembled sections. Complete with amplifiers, portable cabinets and Speaker—excellent quality. 1,200ft. tape and spool.
★ TWO TRACK P.P. £26 8/6
★ FOUR TRACK P.P. £30 8/6
Decks separately: 2-Track 10 gns. 4-track £13.10.0.

(10) 5 WATT AMPLIFIER

6-Transistor Push-pull, 3 ohms. 6mV into 1K. 12/18V supply. 2 1/2 x 2 x 1 1/2 in.

BUILT AND TESTED 79/6 P.P. 2/-
(optional mains units 54/- p.p. 2/-)

New matching Preamplifier, 6 inputs, treble/bass/selector/volume controls. 6-10mV o/p, 9-18V supply. 79/6, p.p. 2/- For use with any Transistor Amplifier.

(6) REGENT-6 MW/LW POCKET RADIO

6-Transistor superhet. Geared tuning. Push-pull output Moulded cabinet 5 x 3 x 1 1/2 in. Phone socket. Printed circuit design.
TOTAL COST TO BUILD 85/- P.P. 2/-

(11) NOMBREX SIGNAL GEN.

150 kc/s to 350 Mc/s. P.P. 2/6
10 c/s-100 kc/s AUDIO GEN. P.P. 2/6
£16.15.0 P.P. 2/6

(15) DEAC CELLS RECHARGEABLE BATTERIES

● 3.6 volt 500 mA/H. Size: 1 1/2" x 1 1/2" dia. 12/6, P.P. 1/6.
● 9.6 volt 225 mA/H. Size: 2 1/2" x 1" dia. 20/-, P.P. 1/6.
BRAND NEW — Offered at a fraction of normal retail price.

(13) 25 WATT AMPLIFIER

New 8-Transistor design. Push-pull output for 7 1/2 to 16 ohm speaker. 150mV input. 30 c/s to 20 kc/s ± 1dB. For use with valve or transistor preamplifiers as item (3) above. Size 2 1/2 x 2 1/2 x 6 1/2 in.
PRICE BUILT AND TESTED £8.19.6 P.P. 3/-
(Mains unit 79/6, p.p. 2/6)

(9) ROADSTER MW/LW TRANSISTOR CAR RADIO

Supplied as Preassembled Panels. Permeability tuned superhet. Push-button wave-changer. Push-pull output. Fits any car. 7 x 4 x 2 in. 12 volt (+) earth.
ASSEMBLY TOTAL COST £8.19.6 P.P. 3/6
(Speaker/Baffle/Car Fixing Kit, 20/-).

(14) GARRARD DECKS

(P.P. 5/- any type)
1000 mono £5.19.6 stereo £6.6.0
2000 mono £6.6.0 stereo £6.6.0
*SP25 mono £10.10.0 stereo £10.19.6
Autoslim mono £5.9.6 stereo £5.9.6
*AT6 mono £8.19.6 stereo £9.10.0
*AT60 mono £10.10.0 stereo £10.19.6
LAB80 £25.0.0 3000LM stereo £8.19.6
(*Deram cartridge add 60/- to mono price)
All autochange (except SP25), complete with cartridge. Brand new. Send for complete list.

(2) MULTI-METERS

PT34 1kV 39/6 TP55 20kV £5.19.6
M1 2kV 49/6 EP30k 30kV £6.10.0
TP10 2kV 75/- EP50k 50kV £8.15.0
EP10k 10kV 79/6 500 30kV £8.17.6
ITI-2 20kV 89/6 EP100k 100kV £10.10.0
EP20k 10kV 99/6
See Catalogue for complete range of test equipment in stock.

(5) VHF FM TUNER ALL TRANSISTOR

Supplied as 2 Preassembled Panels, plus metal work Superhet design, 88-108 Mc/s, 9 volt operated.
TOTAL COST £12.17.6 P.P. 2/6.

(7) MW/LW QUALITY SUPERHET RADIO TUNER

Fully tunable superhet with excellent sensitivity and selectivity. Output up to 1 volt peak. Complete with front panel, etc. 9 volt operated.
TOTAL COST TO BUILD £3.19.6 P.P. 2/6

(13) **HIGH FIDELITY EQUIPMENT.** Complete range in stock, all makes. Special parcel prices. Quotations by return to your requirements.
VISIT OUR NEW HI-FI ROOM

HENRY'S RADIO LTD.
303 EDGWARE ROAD, LONDON, W.2
PADdington 1008/9
Open Mon. to Sat. 9-6. Thurs. 1 p.m.
Open all day Saturday.

LET US QUOTE FOR COMPONENTS AND ACCESSORIES FOR YOUR CIRCUIT. SEND A LIST FOR QUICK REPLY. QUALITY COMPONENTS AT VALUE FOR MONEY PRICES. ALSO TEST EQUIPMENT AND HI-FI.