


# PRACTICAL WIRELESS

APRIL 1975  
30p

## REACTION TIMER



## QUIZ MONITOR

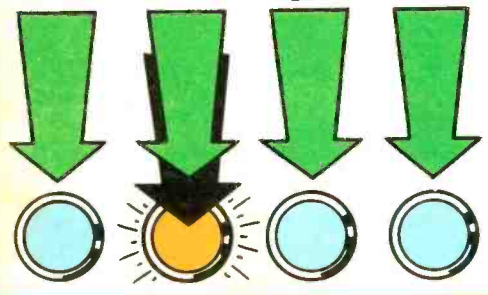

also:- The 'IC + 2' Receiver  
The 'EASYBUILD' Electronic Organ-Part 2

# NEW EDU-KIT MAJOR

Completely Solderless Electronic Construction Kit  
Build these projects without soldering iron or solder

- ★ 4 Transistor Earpiece Radio
- ★ Signal Tracer.
- ★ Signal Injector.
- ★ Transistor Tester NPN-PNP
- ★ 4 Transistor Push Pull Amplifier.
- ★ 5 Transistor Push Pull Amplifier.
- ★ 7 Transistor Loudspeaker Radio MW/LW.
- ★ 5 Transistor Short Wave Radio.
- ★ Electronic Metronome.
- ★ Electronic Noise Generator
- ★ Batteryless Crystal Radio.
- ★ One Transistor Radio.
- ★ 2 Transistor Regenerative Radio.
- ★ 3 Transistor Regenerative Radio.
- ★ Audible Continuity Tester.
- ★ Sensitive Pre-Amplifier.

**Total Building Costs**  
**£7-23** P P & Ins. 44p  
(Overseas Seamail P & P £2-35)  
(+ 8% VAT 57p)

Components Include: 24 Resistors • 21 Capacitors • 10 Transistors • 3 1/2" Loudspeaker • Earpiece • Mica Baseboard • 3 12-way connectors • 2 Volume controls • 2 Slider Switches • 1 Tuning Condenser • 3 Knobs • Ready Wound MW/LW/SW Coils • Ferrite Rod • 6 1/2 yards of wire • 1 Yard of sleeving etc. • Parts Price List and Plans 55p free with parts.

## NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT




Nine Transistors, 9 Tunable wavebands, V.H.F. Built in ferrite rod aerial for MW/LW. Retractable chrome-plated telescopic aerial for VHF and SW. Push Pull output using 600 mW transistors, 9 Transistors and 3 diodes, tuning condenser with V.H.F. section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavechange controls. Attractive all white case with red grille and carrying strap. Size 9 1/2" x 7" x 2 1/2" approx. Parts Price List and Plans free with parts.

**Total Building Costs** **£6-95** P P & Ins. 44p  
(Overseas Seamail P & P £2-35)  
(+ 8% VAT 56p)


## POCKET FIVE

NOW WITH 3" LOUD-SPEAKER

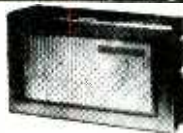

3 Tunable wavebands, M.W. L.W. and Trawler Band, 7 stages, 5 transistors and 2 diodes, super-sensitive ferrite rod aerial, attractive black and gold case. Size 5 1/2" x 3 1/2" x 3 1/4" approx. Plans and Parts Price List 20p free with parts.

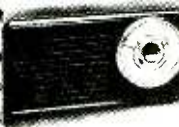**Total Building Costs** **£2-50** P P & Ins. 35p  
(Overseas Seamail P & P £1-70)  
(+ 8% VAT 20p)



**TRANSONA FIVE NOW WITH 3" LOUDSPEAKER**

Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and Parts Price List free with parts.

**Total Building Costs** **£2-75** P P & Ins. 36p  
(+ 8% VAT 21p)  
(Overseas Seamail P & P £1-70)

## TRANS EIGHT

8 TRANSISTORS and 3 DIODES

8 Tunable Wavebands: MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves, 3in. Speaker, 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2 in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans free with parts.

**Total building costs** **£4-48** P P & Ins. 40p  
(+ 8% VAT 36p)  
(Overseas Seamail P & P £2-00)

## ROAMER SIX

CASE AND LOOKS AS TRANS-EIGHT

6 Tunable Wavebands: MW, LW, SW1, SW2. Sensitive ferrite rod aerial and telescopic aerial for Short Waves, 3in. Speaker, 8 stages—6 transistors and 2 diodes. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9 x 5 1/2 x 2 1/2 in. approx. Plans and parts price list free with parts.

**Total building costs** **£3-98** P P & Ins. 40p  
(+ 8% VAT 32p) P & P £2-00

## NEW Everyday Series

Build this exciting New series of designs



E.V.5. 5 Transistors and 2 diodes. MW/LW. Powered by 4 1/2 volt Battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3" loudspeaker. Attractive case with red speaker grille. Size 9" x 5 1/2" x 2 1/2" approx. Parts Price List and Plans free with parts.

**Total Building Costs** **£2-95** P P & Ins. 36p  
(Overseas Seamail P & P £1-70)  
(+ 8% VAT 23p)

E.V.6. Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, 3" loudspeaker, etc. MW/LW coverage. Push Pull output. Parts Price List and Plans free with parts.

**Total Building Costs** **£3-60** P P & Ins. 36p  
(Overseas Seamail P & P £1-70)  
(+ 8% VAT 29p)

E.V.7. Case and looks as above. 7 Transistors and 3 diodes. Six wavebands. MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt battery. Push Pull output. Telescopic aerial for short waves. 3" Loudspeaker. Parts Price List and Easy Build Plans free with parts.

**Total Building Costs** **£4-08** P P & Ins. 39p  
(Overseas Seamail P & P £2-00)  
(+ 8% VAT 32p)

## ROAMER EIGHT Mk I

NOW WITH VARIABLE TONE CONTROL



7 Tunable Wavebands: MW1, MW2, LW, SW1, SW2, SW3 and Trawler Band. Built in Ferrite Rod Aerial for MW and LW. Chrome plated Telescopic aerial can be angled and rotated for peak short wave listening. Push pull output using 600mW transistors. Car aerial and Tape record sockets. Selectivity switch, 8 transistors plus 3 diodes. Latest 4" 2 watt ferrite magnet loudspeaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in. approx. Easy to follow instructions and diagrams. Parts price list and plans free with parts.

**Total building costs** **£6-98** P P & Ins. 47p  
(Overseas Seamail P & P £2-50)  
(+ 8% VAT 56p)

## ROAMER TEN Mk 2

WITH VHF INCLUDING AIRCRAFT



Now with free earpiece and switched socket.

10 Transistors. Latest 4" 2 watt Ferrite Magnet Loudspeaker. 9 Tunable Wavebands, MW1, MW2, LW, SW1, SW2, SW3, Trawler Band, VHF and Local Stations also Aircraft Band. Built in Ferrite Rod Aerial for MW/LW. Chrome plated 7 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mW Transistors. Car Aerial and Tape Record Sockets. 10 Transistors plus 3 Diodes. Ganged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off. Wave Change and tone Controls. Attractive Case in black with silver blocking. Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and plans 60p free with parts.

**Total building costs** **£9-50** P P & Ins. 52p  
(Overseas Seamail P & P £2-50)  
(+ 8% VAT 76p)



"EDU-KIT"

Build Radios, Amplifiers, etc. from easy stage diagrams.

Five units including master unit to construct.

Components include:

Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine Tone 3" Moving Coil Speaker: Terminal Strip: Ferrite Rod Aerial: Battery Clips: 4 Tag Boards: 10 Transistors: 4 1/2 Diodes: Resistors: Capacitors: Three 1/2" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans free with parts.

**Total building costs** **£5-50** P P & Ins. 40p  
(Overseas Seamail P & P £2-35)  
(+ 8% VAT 44p)

## RADIO EXCHANGE LTD

★ Callers side entrance "Lavelle's" shop.  
★ Open 10-1, 2.30-4.30, Mon.-Fri. 9-12 Sat.

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD, MK40 1SA  
Tel.: 0234 52967. Reg. No. 788372.

I enclose £..... for.....

Name .....

Address .....

(Dept. pw 04.)



# PRACTICAL WIRELESS

VOL. 50 NO. 12

ISSUE 818

APRIL 1975

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

## EDITOR

Lionel E. Howes, G3AYA

## ASSISTANT EDITOR

Eric Dowdeswell, G4AR

## TECHNICAL EDITOR

Sam Lewis B.Sc. (Eng.)

## PRODUCTION & NEWS EDITOR

Colin R. Riches

## TECHNICAL SUB-EDITOR

Bill Tull

## ART EDITOR

Peter Metall

## TECHNICAL ARTIST

Alan Martin

## SECRETARIAL

Jenny Maunder  
Susan King

## ADVERTS MANAGER

01-634 4293

Roy Smith

## CLASSIFIED ADVERTS

01-634 4301

Colin R. Brown

Published by IPC Magazines Ltd.,  
Fleetway House, Farringdon Street,  
London EC4A 4AD. Tel. 01-634 4444

## SUBSCRIPTIONS

Publisher's Subscription Rate for one year to the UK is £3.85 and to the rest of the world £4.95 (\$13.50 USA/CAN) including postage. Enquiries to Subscription Department, IPC Magazines Ltd., Carlton House, 68 Gt. Queen Street, London, WC2 5DD. Phone 01-242 4477. International Giro facilities Account No. 5122007. Please state reason for payment "message to payee".

Binders (£1.34) and indexes 30p (inc. VAT) can be supplied by the Binders Dept at the same address.

## BACK NUMBERS

We regret that we are unable to supply back numbers of Practical Wireless. Readers are recommended to enquire at a public library to see copies. Requests for specific back numbers of *Practical Wireless* and *Television* only can be published in our CQ Column.

## COPYRIGHT AND QUERIES

© IPC Magazines Limited 1975. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

We regret that we cannot answer technical queries by telephone nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.

## ● NEWS & COMMENT

- 1084 AIDING AND ABETTING—Leader article
- 1085 NEWS . . . NEWS . . . NEWS . . .
- 1094 HOTLINES on recent developments by *Ginsberg*
- 1101 ON THE AIR
- 1101 Amateur Bands—*Eric Dowdeswell, G4AR*
- 1102 Broadcast Bands—Short Wave—*Derek Bell*
- 1103 NEXT MONTH IN PRACTICAL WIRELESS
- 1116 PRODUCTION LINES by *Colin Riches*

## ● CONSTRUCTIONAL

- 1086 P.W. 'ASCOT' STEREO CASSETTE DECK—Part 3—  
*Keith Cummins & Tony Francis*
- 1097 REACTION TIMER—*A. Willcox*
- 1104 P.W. 'EASYBUILD' ELECTRONIC ORGAN—Part 2—  
*M. J. Hughes, M.A., C.Eng., MIERE*
- 1111 IC +2 RECEIVER—*R. H. Longden*
- 1120 QUIZ MONITOR—*A. Fowell*


## ● OTHER FEATURES

- 1125 THE UNITRON—Magnetic Field-Effect Technology—  
*Don Reschovsky*
- 1129 GOING BACK—Earlier days of Wireless—*Colin Riches*

LISTEN TO

**CODAR**® THE WORLD!

★ **CR70A**

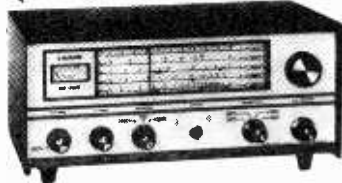

**COMMUNICATION RECEIVER**

The CODAR CR70A is an outstanding general coverage communication receiver, ideal for the keen S.W.L. It tunes from 540 metres medium through to 10 metres with no gaps. Covers shipping, coastguard and distress frequencies, all six amateur bands 160-10 metres, International broadcast, Met. stations etc. etc. giving world-wide reception. Exclusive features include Air-spaced CODAR-COIL Hi-"Q" Aerial input, illuminated Meter and Slide Rule Scale, Two Speed vernier tuning, Switched B.F.O. for CW/SSB signals. Separate output for Tape recorder. Ready to plug in to 200/240 volts A.C. it only needs your aerial and a 2/3 ohm loudspeaker to bring the world to your finger tips. 12 months full guarantee.

★ **IMPORTANT NOTE**

This fine receiver is not a mass produced item, but each set is hand built to your order, individually checked and air tested. Please allow for this when ordering—your delivery date will be shown on your receipt, sent by return.

★ **MADE TO ORDER!**

**£37-15!**

VAT PAID CARR. 85p



**P.R.40** ★



**£10-93!**

VAT PAID CARR. 32p

**R.F. PRESELECTOR**

The PR40 R.F. Preselector is the solid state version of the world famous PR30 which it now supersedes. It employs Silicon "N" Channel FET (Field Effect Transistor) front end followed by silicon NPN Broad Band R.F. Amp., and will substantially improve receiver performance over the range 1.5 to 35 MHz, providing a considerable increase in gain up to an overall average of 30dB, with improved image rejection and noise ratio. Supplied complete with co-ax plug (less standard 9 volt PP6 Battery). 12 months Guarantee . . .



**MULTIBAND-6** ★

**SHORT WAVE RECEIVER KIT**

**£16-90! CARR. 43p**

All transistor T.R.F. Receiver tunes 550 KHz to 30 MHz (540 to 10 metres) complete coverage—no gaps. Medium waves—Trawlers—Ship/Shore Telephone—All Six Amateur Bands 160-10 metres—International Broadcast from Australia, Far East, Russia, USA etc. using 4 miniature plug in Coils. Hi-Gain FET Regen. Det./AF/AF Module giving full loudspeaker output to any external 2/3 ohm speaker. Receives AM/CW/SSB. Separate Electrical Bandspread, Calibrated Main Tuning. A Quality CODAR-KIT with 12 months Guarantee. No technical knowledge required, simple to build, printed circuit and Pictorial Instruction Manual, fully detailed step by step. Complete Kit with 4 Coils (less standard PP6 battery).

ILLUSTRATED LEAFLETS FREE ON REQUEST

ON THE DESIGN STAFF—  
G3SZM G3IRE

**CODAR**

TO COPE WITH INCREASING DEMAND—PLEASE  
NOTE NEW SALES OFFICE TEL NO. BRIGHTON 38345  
MON-THURS-9.30 a.m.-4.30 p.m.

**VALCON WORKS · BURRELL BUILDINGS · CHURCHILL INDUSTRIAL ESTATE · LANCING · SUSSEX**  
WORLD-WIDE MAIL ORDER—EXPORT QUOTES FREE. **BN15 · 8TZ**



# YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the **CITY & GUILDS EXAMS** (Technicians' Certificates); the Grad. Brit. I.E.R. Exam.; the **RADIO AMATEUR'S LICENCE**; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have **OVER 20 YEARS'** experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Fullest details will be gladly sent without any obligation.

To: **British National Radio & Electronics School, Dept W.C.45, P.O. Box 156, Jersey, C.I.**

Please send **FREE BROCHURE** to

NAME ..... Block  
ADDRESS ..... Caps.  
..... Please

**BRITISH NATIONAL RADIO  
AND ELECTRONICS SCHOOL**

**12" LONG PERSISTENCE CRT.**  
Full spec. Price £8-50 to include V.A.T. and Carriage.

**MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED SOLID STATE SWITCH.** 2 Hz to 8 MHz. Hook up a 9 volt battery and connect to your scope and have two traces for **ONLY £8-25, P. & P. 25p.** (Not cased, not calibrated.)

**WIDE RANGE WOBBLATOR.** 5 MHz to 150 MHz up to 15 MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 10-7 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6 3V A.C. and use within minutes of receiving. All this for **ONLY £8-75, P.&P. 25p.** (Not cased, not calibrated.)

**20 Hz to 200 kHz WB. SINE and SQUARE GENERATOR.** Four ranges. Independent amplitude controls, thermistor stabilised. Ready to use. 9V supply required. £8-85 each, P. & P. 25p. (Not cased, not calibrated.)

**GRATICULES** 12cm x 14cm high quality plastic 15p each, P. & P. 5p.

Large quantity of good quality components — **NO PASSING TRADE** — so we offer 3lbs of **ELECTRONIC GOODIES** for £1-50. Post paid.

**ROTARY SWITCH PACK**—6 brand new switches (1 ceramic; 1 off 4pole 2 way etc.). 50p, P. & P. 20p.

**P.C.B. PACKS** S. & D. Quantity 2 sq ft—no tiny pieces. 50p plus P. & P. 20p.

**CAPACITOR PACK**—50 Brand new components, only 50p, P. & P. 20p.

**TRIMMER PACK.** 2 Twin 50/200pF ceramic 2 Twin 10/60pF ceramic; 2 min. strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. **ALL BRAND NEW.** 25p the lot, P. & P. 10p.

**PHOTOCELL** equ. OCP71, 13p each. **MULLARD OCP70**—10p each.

**DELIVERED TO YOUR DOOR** 1 cwt of Electronic Scrap chassis, boards, etc. No rubbish. **FOR ONLY £4-00.**

**MODERN TELEPHONES** type 706. Two-tone grey, £3-75 each. Two-tone green £3-75 each. Black £3-75 each. P. & P. 35p.

Ideal **EXTENSION TELEPHONES** with standard GPO type dial, bell and lead coding. £1-75 each, P. & P. 35p.

**HANDSETS** — complete with 2 inserts and lead 75p each, P. & P. 37p. **DIALS ONLY** 75p each, P. & P. 25p.

**HIGH VALUE—PRINTED BOARD PACK.** Hundreds of components, transistors, etc.—no 2 boards the same—no short leaded transistor computer boards £1-75 post paid.

**Beehive Trimmer 3/30 pf** Brand new. Qty. 1-9 15p ea. P. & P. 15p 10-99 10p ea. P. & P. 25p; 100-999 7p ea. P. & P. free.

**HF Crystal Drive Unit.** 19in. rack mount. Standard 240V input with superb crystal oven by Labgear (no crystals) £5 ea. Carr. £2-00

**1000pf FEED THRU CAPACITORS** only sold in packs of 10, 30p, P. & P. 10p.

**ALWAYS** some **CHEAP SCOPES AVAILABLE**—or build your own—send for our tube list with a S.A.E.

PLEASE ADD V.A.T. AT 8%  
OPEN 9 a.m. to 6.30 p.m. ANY DAY

**CHILTMead LTD**



7/9 ARTHUR ROAD, READING, BERKS.  
(near Tech. College) Tel.: Reading 582805/85916

# RSC 100 watt DISCO SYSTEM

50 WATT SPEAKER 50 WATT SPEAKER  
TWIN TURNTABLE WITH PRE-AMP. and POWER AMPLIFIER

Complete with lid HEADPHONES MICROPHONE

FANTASTIC LOW PRICES!

Units listed below  
(a) DISCOMASTER TWIN TURNTABLE CONSOLE with integral 100W amplifier  
(b) PAIR OF HI-FI HEADPHONES  
(c) MATCHING DYNAMIC 'MIKE' (attached to h'phone)  
(d) PAIR 50 WATT SPEAKERS Black/Redine covered Cabinets Size approx. 18" x 18" x 8"

**£159-95**

DEP. £19-95 & 18 fortnightly payments of £9-11 (Total £183-93).

STEREO VERSION OF ABOVE SYSTEM  
Or DEP £29-95 and 18 fortnightly pymts. £11-11 (Total £229-98) Carr. £3-50

# RSC TDI DISCO CONSOLE

Incorporating twin Garrard SP25 or BSR MP60 turntables and Sonotone or Acos Cartridges with diamond stylis. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate input for 'mike' with vol. control switch. Black/Vynide covered Cabinet with lid. See illustration on left. Or Dep. £29-00 and 18 fortnightly pymts. £4-81 (Total £91-98) Carr. £1-50

**£79-95**

TD2S STEREO VERSION OF ABOVE SYSTEM  
Terms. Dep. £15-00 and 18 fortnightly payments £2-51 (Total £132-18) Carr. £1-80

## DISCOMASTER TWIN TURNTABLE POWER CONSOLE £109-95 Carr. £2-50

Garrard SP25 or McDonald MP60 turntables. Sonotone or Acos cartridges with built-in 100 watt Power Amplifier, complete with lid. Or Deposit £12-95 and 18 fortnightly payments £6-31 (Total £126-58)

STEREO DISCOMASTER £145 (Total £186-70). Carr. £3

## R.S.C. COLUMN SPEAKERS IDEAL FOR VOCALISTS AND PUBLIC ADDRESS

All types 15 Ohms covered in Rexine and Vynair  
TYPE C38 40-50 WATTS Incorporating three exceptionally efficient 8" speaker units.  
Terms: Dep. £2-95 and 8 monthly payments £2-87 (Total £25-91) Carr. 65p.

TYPE C37/70 70 WATTS. Fitted three 12" 25 watt Highly sensitive high flux speakers with high power voice coils. Size approx. 54" x 14" x 11". Dep. £5-11 and 8 mthly pymts. £5-11 **£39-95** (Total £45-99) Carr. 85p

## FANE ULTRA HIGH POWER SPEAKERS & KITS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE High flux ceramic magnets. ALL CARRIAGE FREE.

'POP' 100	'POP' 60	'POP' 50
18" 100 Watt 14,000 gauss 8/15G <b>£29-95</b> Dep: £3-80 and 8 mthly payments £3-80 (Total £34-20)	15" 60 Watt 14,000 gauss 8/15G <b>£16-95</b> Dep. £2-17 and 8 monthly payments. £2-17 (Total £19-63)	12" 50 Watt 13,000 gauss 15G <b>£12-95</b> Terms for pairs Dep £3-90 & 8 mthly pymts £3-16 Total £29-18

FOR BASS GUITAR, ELECT. ORGAN, ETC.

## ALL RSC PRICES INCLUDE VAT

INTEREST on Credit Purchases REFUNDED settled in 3 months

### SUPER MINSTREL GUITAR AMP.

Incorporating Tremolo and 13" x 8" or 10" Speaker. Output 10 watts R.M.S. Continuous. 3 Jack Inputs for Microphone and Instrument. Mains Neon Controls: Volume, Tone, Tremolo Speed Tremolo Intensity.  
Terms: Deposit £6-73 and 8 monthly payments £3-00 (Total £50-73) Carr. Free

**£26-73**

## FANE CRESCENDO SPEAKERS

FULL RANGE AVAILABLE AT ALL BRANCHES

## 'POP' 25/T 12" 25W. PH50 HIGH POWER TWEETER

Dual cone. 15 ohm Imp. (Not for Bass Guitar use) **£8-95**

PH50 High Power Tweeter Rating 50 Watt Imp. 8Ω with 2 to 4 mfd. Non elect. filter available 55p **£5-95**

## MODEL D40 FULL RANGE 40 WATT SPEAKER KIT £19-99

Consisting of 12" 40 watt Bass Unit HPX1 200w Cross-over and PH50 Tweeter Rating 40w R.M.S. Imp. 8 ohms. Terms: Deposit £3-99 and 8 mthly payments £2-50. (Total £23-99).

## HIGH QUALITY LOUDSPEAKER UNITS

ALL TWO TONE VYNIDE AND VYNAIR FINISH  
L12/2 50 WATT Fitted pair of 12" 30 watt high flux speakers for conservative rating. Impedance 8-15 ohms. Carr. £1-50 Or deposit £5-11 and 8 monthly pymts. of £5-11. Total £45-99

L12/25G 12" 25 WATT 13,000 gauss 15 ohms Terms for Pairs. Approx. 14" x 14" x 9" **£12-95** Carr. 65p. Terms for Pairs. Dep. £2-05 & 8 mthly pymts £2-05 (Total £18-45).

## FAL MAESTRO COMBINED 30W AMP. AND 12" SPEAKER £47-88 Carr. Free

For Lead Guitar, Mic, Gram, Radio, Tape (Not for use with Bass instruments) Inc. 3 Inputs and 2 vol controls plus Treble & Bass. TREMOLO with associated controls. Attractively finished in black with silver-finished fascia. Compact size fitted carrying handle. Deposit £7-88 and 8 monthly payments £5-75 (Total £53-88)

RSC 'PHANTOM 50' Rating 50 watts. 3 inputs. 2 vol. controls. Bass, Treble, Presence **£55-00** Carr. £1-50  
Terms: Deposit £8-00 & 8 mthly. pymts. £6-76 (Total £62-08).

## FAL PHASE 50 Mk. III AMPLIFIER 50 WATT

Solid state. 4 Separately controlled inputs Plus master vol. control. Ind. Bass and Treble Controls. Protective Circuitry against serious output overloading. Output for Speakers 8 to 15 ohms. Size 17" x 7" x 7 1/2". 200-250v. A.C. mains. Output 50 watts. Inbuilt rating. Or deposit £7-88 & 8 monthly payments £5-76. Total £58-88. Carr. Free **£47-88**

## REGENT 50X 50 WATT AMP.

A powerful high quality unit for lead, rhythm guitar, vocalists, gram, radio, tape. 50w Peak O/P rating. Not for Bass Guitar.  
★ Two Fane heavy duty high flux 12in. spkrs.  
★ Four Jack inputs and two Volume Controls for instant use of up to four pick-ups or "mikes". Bass and Treble controls. Send S.A.E. for leaflet. Credit Terms: Deposit £9-95 & 18 fortnightly payments of £4-15 (Total £84-65). Carr. £2-50

REGENT 50B for Bass Guitar and general purposes. Or Dep. £10-95 & 18 fortnightly payments £4-78. (Total £98-09). Carr. £2-50 **£84-95**



speakers. Send SAE for leaflet. Terms: Dep. £5-58 & 8 mthly pymts £3-68 (Total £34-22) Carr. 75p

## GP30 AMPLIFIER

For Guitar, Vocal or Instr. Group, Gram, Radio or Tape. 4 inputs. 2 Vol. Controls. Current Valves. Peak o/p rating. Strong Vynide covered cabinet with carrying handles. Black/Silver Facia. Neon Indicator. For 200-250v A.C. For 3 or 16 1/2 mthly pymts. £3-89 **£12-95** Carr. 56p.

## REGENT '50' AMPLIFIER

As supplied with Regent 60x or 50B. Terms: Dep. £5-11 & 8 mthly pymts £5-11 (Total £45-99) **£39-95** Carr. £1



## FAL DISCO PRE-AMPLIFIER

T/Table mixing inputs. Headphone Monitoring. Mic. Jack & Tape inputs. Independent Vol. Control. Std. 200-250v A.C. Mains operation. **£18-50**

NEW BRANCHES AT  
**BOLTON, COVENTRY  
DONCASTER, PRESTON  
and STOCKPORT**



Barclaycard and Access accepted

All items subject to availability. Prices correct at 14.2.75 E. & O.E.

## HI-FI CENTRES LTD.

DONCASTER 3 Queensgate, Waterdale Centre.  
EDINBURGH (Closed Thurs). Tel. 63069  
101 Lothian Rd. (Closed Wed.). Tel. 229 9501  
GLASGOW 328 Argyle St. (Closed Tues.). Tel. 248 4158  
HULL 7 Whitefriargate (Closed Thurs.). Tel. 20505  
LEICESTER 32 High Street (Closed Thurs.). Tel. 56420  
LEEDS 5-7 County (Mecca) Arcade, Briggate (Closed Wed.). Tel. 28252  
LIVERPOOL 73 Dale St. (Closed Wed.). Tel. 236 3573  
LONDON 238 Edgware Road, W.2. (Closed Thurs.). Tel. 723 1629

MAIL ORDERS & EXPORT ENQUIRIES TO—  
AUDIO HOUSE, HENCONNER LANE, LEEDS. 18. Tel: Pudsey (09785) 77631.

MAIL ORDERS MUST NOT BE SENT TO SHOPS  
TERMS C.W.O. or O.O.D. No O.O.D. under £1.  
POSTAGE 40p PER ORDER OR AS QUOTED.  
TRADE SUPPLIER

S.A.E. PLEASE WITH ENQUIRIES.  
MANCHESTER 60A Oldham Street (Closed Wed.).  
MIDDELSBROUGH Tel. 238 2778  
106 Newport Road (Closed Wed.). Tel. 47096  
NEWCASTLE UPON TYNE 24 Newgate Shopping Centre (Closed Wed.). Tel. 21469  
NOTTINGHAM 19/19A Market Street  
PRESTON (Closed Thurs.). Tel. 48068  
41 Friargate Walk, St. Georges Shoppg Prec. Tel. 51979  
SHEFFIELD 13 Exchange Street (Castle Mkt. Bldg.)  
STOCKPORT (Closed Thurs.). Tel. 207116  
8 Little Underbank (Closed Thurs.). Tel. 480-0777  
SUNDERLAND 5 Market Sq. (Closed Wed.). Tel. 70573

OPEN ALL DAY SATURDAYS (5 Day Week)  
BRADFORD 10 North Parade (Closed Wed.). Tel. 25349  
BOLTON 23 Deansgate. (Closed Wed.). Tel. 33512  
BIRMINGHAM 30/31, Great Western Arcade. Tel. 021-236 1279 (Closed Wed.).  
COVENTRY 17 Shelton Square, The Precinct. Tel. 25983  
DERBY 97 St. Peter's Street. (Closed Wed.). Tel. 41361  
DARLINGTON 19 Northgate (Closed Wed.). Tel. 68043

# NEW MULLARD & MAZDA VALVES

All individually boxed and guaranteed. Full trade discounts to bona fide companies. Price and availability lists on application.

## EXPRESS POSTAGE

10p for 1 Valve.  
Each additional Valve add 2p.

DM70	0.61	ECL83	0.46	PC88	0.95	PL500	0.90	30C15/PCF80	1.01
DY51	0.80	ECL86	0.64	PC88	0.95	PL500	0.90	30C15/PCF80	1.01
DY86/7	0.41	EF80	0.42	PC97	0.47	PL504	0.90	30C17	1.01
DY802	0.46	EF83	0.98	PC900	0.52	PL508	1.24	30C18/PCF80	1.00
EABC80	1.03	EF85	0.42	PC834	0.54	PL509	1.56	PCF80	1.00
EB91	0.64	EF86	1.16	PC835	0.50	PL802	1.40	30F5/PCF818	0.84
EB081	0.79	EF89	1.14	PC838	0.56	PL803	1.04	30F5/PCF818	0.84
EBF80	0.68	EF91	1.00	PC839	0.64	PL804	0.98	30F5/PCF818	1.03
EBF83	0.69	EF92	1.37	PC189	0.80	PL805	0.92	30F5/PCF818	1.03
EBF89	0.53	EF95	1.47	PC180	0.64	PL806	0.98	30F5/PCF818	1.03
EC86	0.73	EF183	0.63	PCF82	1.22	PL807	1.56	30F5/PCF818	1.03
EC88	0.76	EF184	0.63	PCF86	1.04	PL808	1.56	30F5/PCF818	1.03
EC90	0.88	EH90	0.85	PCF200	1.00	PL809	1.56	30F5/PCF818	1.03
EC97	0.60	EL24	0.92	PCF201	1.00	PL810	1.56	30F5/PCF818	1.03
EC98	0.60	EL26	1.01	PCF801	0.64	PL811	1.56	30F5/PCF818	1.03
EC981	0.47	EL81	0.85	PCF802	0.70	PL812	1.56	30F5/PCF818	1.03
EC982	0.44	EL84	0.47	PCF806	0.64	PL813	1.56	30F5/PCF818	1.03
EC983	0.47	EL85	0.85	PCF800	1.15	PL814	1.56	30F5/PCF818	1.03
EC984	0.58	EL86	0.92	PCF82	0.58	PL815	1.56	30F5/PCF818	1.03
EC985	0.71	EL86	0.92	PCF82	0.58	PL816	1.56	30F5/PCF818	1.03
EC988	0.84	EL91	0.00	PCF83	0.64	PL817	1.56	30F5/PCF818	1.03
EC989	0.88	EL95	0.92	PCF85	0.64	PL818	1.56	30F5/PCF818	1.03
EC989	0.88	EL95	0.92	PCF85	0.64	PL819	1.56	30F5/PCF818	1.03
EC989	0.88	EL95	0.92	PCF85	0.64	PL820	1.56	30F5/PCF818	1.03
EC989	0.88	EL95	0.92	PCF85	0.64	PL900	1.56	30F5/PCF818	1.03

# NEW VALVES

Individually boxed and guaranteed but of European or other origin at greatly reduced prices. Quotations for any valve not listed. Send SAE for lists.

AZ1	0.75	EF39	1.25	MU14	1.00	PC88	0.95	PL500	0.90	30C15/PCF80	1.01
AZ31	0.60	EF80	0.35	N78	3.50	PC88	0.95	PL500	0.90	30C15/PCF80	1.01
CB131	1.40	EF85	0.45	OA2	0.45	PC88	0.95	PL500	0.90	30C15/PCF80	1.01
CL33	1.50	EF98	0.50	OB2	0.45	PC88	0.95	PL500	0.90	30C15/PCF80	1.01
CY31	0.60	EF99	0.35	PC86	0.65	PC88	0.95	PL500	0.90	30C15/PCF80	1.01
DAF91	0.40	EF91	0.40	PC88	0.65	PC88	0.95	PL500	0.90	30C15/PCF80	1.01
DAF95	0.40	EF92	0.40	PC88	0.65	PC88	0.95	PL500	0.90	30C15/PCF80	1.01
DDC90	1.35	EF95	0.45	PC97	0.55	PC88	0.95	PL500	0.90	30C15/PCF80	1.01
DF91	0.40	EF98	0.80	PC904	0.45	PC88	0.95	PL500	0.90	30C15/PCF80	1.01
DP96	0.60	EF183	0.40	PC88	0.82	PC88	0.95	PL500	0.90	30C15/PCF80	1.01
DK91	0.60	EF184	0.40	PC88	0.82	PC88	0.95	PL500	0.90	30C15/PCF80	1.01
DK92	1.00	EL32	0.90	PC189	0.65	PC88	0.95	PL500	0.90	30C15/PCF80	1.01
DK96	0.75	EL33	2.50	PCF80	0.40	PC88	0.95	PL500	0.90	30C15/PCF80	1.





### SINCLAIR DM2 DIGITAL MULTIMETER



Will measure AC and DC volts, AC and DC current, and resistance in a total of 20 ranges. The large light emitting diode display will read up to 1999 and automatically indicate polarity. Indication of positive and negative overload is also provided. The instrument is fitted with a combined carrying handle and bench stand and sockets are provided for the connection of an external power supply.

**RANGES:**  
DC VOLTS: 1v, 10, 100v, 1000v  
AC VOLTS: 1v, 10, 100v, 1000v.  
DC CURRENT: 1mA, 10mA, 100mA, 1000mA  
AC CURRENT: 1mA, 10mA, 100mA, 1000mA  
RESISTANCE: 1k, 10k, 100k, 1000k  
**OUR PRICE £59.95 P & P 50p**

### RUSSIAN C116 Double Beam OSCILLOSCOPE




5 MHz pass band. Separate Y1 and Y2 amplifiers. Rectangular 5" x 4" CRT. Calibrated triggered sweep from 0.2µsec. to 100 mill-sec/cm. Free running time base, 50Hz-1MHz. Built-in time base. Calibrator and amplitude calibrator. Supplied complete with all accessories and instruction manual.  
**OUR PRICE £87.00 Carr. paid**

### MODEL TE15 GRID DIP METER



Transistorised. Operates as Grid Dip Oscillator, Absorption Wave Meter and Oscillating Detector. Frequency range 440kHz-280MHz in six coils. 500µA meter. 9V battery operation. Size: 180 x 80 x 40mm.  
**OUR PRICE £17.50 P&P 30p**
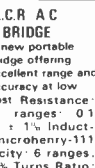
### TRANSISTORISED L.C.R. AC BR/B MEASURING BRIDGE



A new portable bridge offering excellent range and accuracy at low cost. Resistance: 6 ranges: 0.1 ohm-11.1 megohm; 1% inductance: 6 ranges: 1 microhenry-111 henries; 2% Capacity: 6 ranges: 10pF-1110 mfd ± 2%. Turns Ratio: 6 ranges: 1/11000-1/11000 ± 1%. Bridge Voltage at 1.000cps. Operated from 9-volt battery. 100 microamp meter indication. Size 7 1/2" x 5" x 2".  
**OUR PRICE £27.50 P&P 30p**

### TE16A TRANSISTORISED SIGNAL GENERATOR



5 ranges, 400kHz to 30 MHz. An inexpensive instrument for the handy-man. Operates on 9V battery. Wide easy to read scale. 800kHz modulation. Size: 149 x 149 x 92mm. Complete with instructions and leads.  
**OUR PRICE £8.97 P&P 30p**

### TE-200 RF SIGNAL GENERATOR



Accurate wide range signal generator covering 120 kHz-500 MHz on 6 bands. Directly calibrated. Variable R.F. attenuator audio output. Xtal socket for calibration 220 240V a.c. Brand new with instructions. Size 140mm x 215mm x 170mm.  
**OUR PRICE £19.95 P&P 50p**

### ARF 300 AF/RF SIGNAL GENERATOR



All transistorised compact fully portable. AF sine-wave 18Hz to 220 kHz. AF square wave 18Hz to 100kHz. Output Square/Sine wave 10V. P.P.F.F. 100kHz to 200MHz. Output 1V maximum. 220/240V AC operation. Complete with instructions and leads.  
**OUR PRICE £37.50 P&P 50p**

### MODEL TE20 RF SIGNAL GENERATOR



Six bands, 120kHz-260MHz. Dual output RF terminals. Separate variable audio output. Accuracy ± 2%. Audio output to 9V. Power requirements: 105-125V, 220-240V AC. Size: 193 x 265 x 150mm. Complete with test leads etc.  
**OUR PRICE £18.95 P&P 50p**

### TE22 SINE SQUARE WAVE AUDIO GENERATOR



Sine 20cps to 200kHz on 4 bands. Square 20 cps to 30 kHz. Output impedance 5000 Ohms. 200V AC. AC operation. Supplied brand new guaranteed, with instruction manual and leads.  
**OUR PRICE £24.95 P&P 50p**

### MODEL UA4311 Sub-standard Multi-range Volt-Ammeter



Sensitivity 330 Ohms/Volt AC and DC. Accuracy 0.5% DC. 1% AC. Scale length: 165mm. 0/300/750µA/1.5/3/7.5/15/30/75/150/300/750mA/1.5/3/7.5/15/30/75/150/300/750V/1.5/3/7.5/15/30/75/150/300/750V DC. 0/750mV/1.5/3/7.5/15/30/75/150/300/750V AC. Automatic cut out device. Supplied complete with test leads, manual and test certificates.  
**OUR PRICE £52.00 P&P 50p**

### DT 124 POWER UNIT




220 240V AC Input. Output: 6.75 or 9V DC 400 mA.  
**OUR PRICE £2.20 P&P 50p**

### PS200 Regulated POWER SUPPLY UNIT



Solid state. Variable output 5-20V DC up to 2 Amp. Independent meters to monitor voltage and current. Output 220/240V AC. Size: 190 x 136 x 98mm.  
**OUR PRICE £19.95 P&P 50p**

### BATTERY/LEVEL PANEL INDICATOR

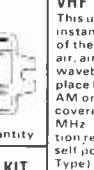

250µA 18mm 18mm Panel mounting.  
**OUR PRICE 75p P&P 15p Discounts for quantity**

### NEW GOLDRING G102 KIT




Belt-drive 2-speed turntable in kit form complete with pick up arm and head shell.  
**OUR PRICE £16.95 P&P 75p**

### VU METER TYPE 3



Size 33mm 20mm  
**£1.25 P&P 15p**

### SOH8V MONO/STEREO HEADPHONES

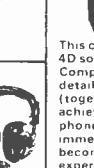

Volume control for each channel. 416 ohms impedance. Frequency response 20Hz-18kHz. Complete with 10ft. coiled lead and jack plug.  
**OUR PRICE £4.97 P&P 30p**

### BH001 HEADSET and Boom Microphone



Moving coil. Ideal for language teaching, communications etc. Headphone impedance 16 ohms. Microphone impedance 200 ohms.  
**OUR PRICE £5.95 P&P 30p**

### T.T.C. SPRITE STEREO HEADPHONES



Feather weight (15oz) Dynamic stereo headphones providing high quality reproduction at a budget price. Soft removable ear pads and adjustable headband. Speaker size 28mm Impedance 8 ohms. Frequency response 30 13000Hz.  
**OUR PRICE £1.95 P&P 30p**

### UNIPEX NT100A



The UniPEX NT100A is a compact portable transistorised PA amplifier. This versatile unit has a maximum output of 10 watts RMS and operates on any 10 16V DC source, negative or positive ground and uses only 1.5A at rated output. Supplied complete with mounting brackets etc. plus full installation and operating instructions.  
**OUR PRICE £21.75 P&P 50p**

### EA41 REVERBERATION AMPLIFIER




Self contained, transistorised, battery operated. Simply plug in microphone, guitar etc. and output to your amplifier. Volume control and depth of reverberation control. Beaulieu cabinet. 184 x 77 x 108mm.  
**OUR PRICE £7.50 P&P 30p**

### RANK AUDIO RA 2107 STEREO AMPLIFIER



7.7 watts rms Inputs for magnetic phono, tuner, tape and aux. Separate bass, treble, balance and volume controls. Headphone socket. Teak case. Unrepeatable offer.  
**OUR PRICE £17.50 P&P 50p**

### VHF 105

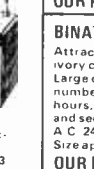


This unit will give instant reception of the ground-to-air, air-to-ground waveband. Simply place beside any AM or FM Radio, covering 35 1605 kHz. 88 10 MHz. No conversion or connection required. This converter is self powered by one 9-volt (PP3 Type) battery and comes complete with a full set of instructions and battery.  
**OUR PRICE £3.50 P&P 50p**

### Just arrived - the sensational! WIEN ET1008 CASSETTE RECORDER




A highly recommended cassette recorder at this really low Laszky's price.  
**FANTASTIC VALUE! ONLY £8.95 P&P 50p**
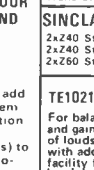
### SPECIAL OFFER! CONVERT YOUR STEREO SYSTEM TO 40 SOUND



This clever unit enables you to add 4D sound to your existing system. Complete with simple connection details. Use this converter (together with 2 extra speakers) to achieve the fantastic 4D quadrophonic sound! The effect of being immersed within the music becomes a thrilling new experience (2 year guarantee).  
**OUR PRICE £2.95 P&P 50p**

### FM TUNER CHASSIS

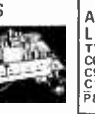

6 transistor high quality tuner. Size only 153 x 101 x 63mm. 3 IF stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Covers 88-108MHz. Ready built, ready for use. Fantastic value for money.  
**OUR PRICE £8.95 P&P 20p Stereo Multiplex Adaptor £9.95 extra**

### WALKIE TALKIES SKYFON NV7




Super low cost transistor receivers 100MW with call buzzer and on-off volume control. 7 transistors. Telescopic rod antenna.  
**OUR PRICE £31.50 per PAIR P & P 50p. NOT LICENSABLE IN THE U.K.**

### ELECTRONIC CALCULATORS



We carry a tremendous range of both pocket and desk calculators from as little as £8.90. Owing to the demand it is not possible to include them in this advertisement, so send for our latest price list or call into any branch.

### MINIATURE ORGAN MUSIC MASTER AM100

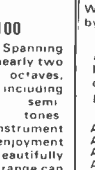


Spanning nearly two octaves, including semi tones. This instrument will give hours of enjoyment to all the family. Beautifully finished. The keyboard range can be adjusted to be in tune with any instrument. Operates from internal 9V battery. Fitted with on/off switch, vibrato switch, earphone socket and external 9V D.C. socket.  
**OUR PRICE £7.95 P&P 50p**

### BINATONE DIGITAL CLOCK




Attractive ivory case. Large clear numbers for hours, minutes and seconds. A.C. 240V operation. Size approx. 6 1/2 x 3 1/2 inches.  
**OUR PRICE £4.50 P&P 50p**
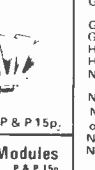
### SINCLAIR IC12 INTEGRATED CIRCUIT AMPLIFIER




complete with printed circuit mounting board.  
**OUR PRICE £1.50 P & P 15p**

### SINCLAIR Project 80 Modules

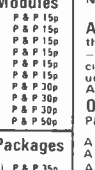


240 Power Amp £9.95 P & P 15p  
260 Power Amp £7.45 P & P 15p  
Stereo 80 Pre-Amp £13.95 P & P 15p  
Active Filter Unit £7.45 P & P 15p  
FM Tuner £13.95 P & P 15p  
Stereo Decoder £8.95 P & P 15p  
PZ5 Power Supply £5.95 P & P 30p  
PZ6 Power Supply £8.95 P & P 30p  
PZ7 Power Supply £8.45 P & P 30p  
Transformer for PZ8 £4.05 P & P 50p

### SINCLAIR Project 80 Packages

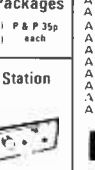

2x240 Stereo 80 PZ5 £25.44 P & P 35p  
2x240 Stereo 80 PZ6 £27.84 each  
2x260 Stereo 80 PZ8 £29.84

### TE1021 Stereo Listening Station

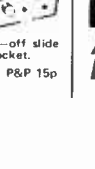

For balancing and gain selection of loudspeakers with additional facility for stereo headphones switching. Two gain controls, speakers on-off slide switch, stereo headphone socket.  
**OUR PRICE £2.25 P&P 15p**

### AUDIOTRONIC LOW NOISE CASSETTES

TYPE	5	10	25
C60	£1.57	£3.00	£7.08
C90	£1.24	£4.25	£10.00
C120	£2.73	£5.17	£12.24

P&P 3p each 10 and over Post Free

### MP7 MIXER-PREAMPLIFIER



5 Microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. Size: 235 x 127 x 76mm. Inputs: Mics. 3 x 3mV 50k; 2 x 3mV 600 ohms. Phono, Mag. 4mV 50k; Mono Ceramic 100mV 1Meg. Output 250mV 100k.  
**OUR PRICE £8.97 P&P 20p**

### AUDIOTRONIC AH4101 Stereo Headphone Amplifier



All silicon transistor amplifier operating on complete magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. INPUTS: 5mV and 100mV. OUTPUT: 50mV per channel.  
**OUR PRICE £8.50 P&P 30p**

### JUSTYKIT HIGH QUALITY CONSTRUCTION KITS



WE ARE STOCKISTS AT Oxford Street, 142 & 257 Tottenham Court Road, 34 Little Street, 152, Fleet Street, 311 Strand, London, W.1C 9YD. BIRMINGHAM KINGSTON LEICESTER NORTHAMPTON SOUTHEND TUNBRIDGE WELLS WOLVERHAMPTON branches, or by Mail Order.

All kits are complete with comprehensive easy to follow instructions and covered by full guarantee. Post and Packing 15p per kit.

AF20 Mono amplifier	£5.61
AF25 Mkr	£3.29
AF30 Mono pre amplifier	£3.20
AF35 Emter amplifier	£2.42
AF60 0.5W mkr. amplifier	£4.86
AF305 Intercom	£7.67
AF120 2 Mono Amplifier	£7.55
M160 Multi vibrator	£2.18
M130 Transistor tester	£8.33
M130 VU Meter	£5.37
M192 Stereo balance meter	£5.93
L F380 Quadraphonic device	£8.42
AT5 Automatic light control	£3.75
AT30 Photo cell switch unit	£6.68
AT50 400W trace light dimmer/speed control	£5.18
AT56 2,200W trace light dimmer/speed control	£6.75
AT60 1 channel light control	£10.82
AT65 3 channel light control	£16.52
GU300 Tremolo unit	£8.10
HF61 Diode detector	£3.87
HF65 FM transmitter	£3.21
HF75 FM receiver	£3.66
HF310 FM tuner	£16.32
HF325 Deluxe FM tuner	£26.33
HF330 Stereo Hi-Fi (10/325)	£10.55
GP310 Stereo pre amplifier for use with 2 x AF310	£22.98
GP312 Circuit board	£10.02
GP304 0.5W mkr. board	£5.33
HF380 iW/h aerial amplifier	£6.02
HF395 broadband aerial amp.	£2.10
NT10 Stabilised power supply 100mA, 9V	£6.27
NT300 Master p. supply	£13.16
NT310 Power Supply 240 V AC or 2 x 18V D.C. at 2amps	£5.64
NT305 Voltage converter	£5.64
NT135 Power supply 240V AC 104.5/15V DC, 500mA.	£11.06

Amateur Electronics with Justy-Kit, the professional book for the amateur - covers the subject from basic principals to advanced electronic techniques. Complete with circuit board for A to AE listed below.

**OUR PRICE £3.30 (No VAT) P&P 25p plus VAT**

A E1 100mA output stage	£1.55
A E2 Pre amplifier	£1.32
A E3 Diode receiver	£2.05
A E4 Flasher	£1.26
A E5 Astable multi vibrator	£1.14
A E6 Monostable multi vibrator	£1.11
A E7 RC generator	£1.08
A E8 Bass filter	£1.05
A E9 Treble filter	£1.05
A E10 CCIR filter	£1.05

Also see previous page  
**ALL PRICES EXCLUDE VAT**



# SEW PANEL METERS

SEW PANEL METERS ARE STOCKED AT OUR  
3 LISLE ST., 311 EDGWARE RD., & 152 FLEET  
ST., BRANCHES or order by post.

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES ETC.

Over 200 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.



CALL INTO YOUR NEAREST  
LASKYS BRANCH OR  
SEND COUPON BELOW  
FOR NEW 32 PAGE  
HI-FI PRICE LIST

## CENTRAL LONDON

481 OXFORD ST	01-493 8641
3 LISLE ST. WC2	01-437 8204
34 LISLE ST. WC2	01-437 9155
118 EDGWARE RD. W2	01-723 9789
193 EDGWARE RD. W2	01-723 6211
207 EDGWARE RD. W2	01-723 3271
311 EDGWARE RD. W2	01-262 0387
346 EDGWARE RD. W2	01-723 4453
382 EDGWARE RD. W2	01-723 4194
109 FLEET ST. EC4	01-353 5812
152 1/3 FLEET ST. EC4	01-353 2833
10 TOTTEHAM CT. RD.	01-637 2232
27 TOTTEHAM CT. RD.	01-636 3715
33 TOTTEHAM CT. RD.	01-636 2605
42/45 TOTTEHAM CT. RD.	01-636 0845
257/8 TOTTEHAM CT. RD.	01-580 0670

## ESSEX

86 SOUTH ST. ROMFORD 20218  
205/206 CHURCHILL WEST,  
VICTORIA CIRCUS, SOUTHEND 0702 612241

**GLOUCESTERSHIRE**  
16/20, PENN. ST. BRISTOL 0272-20421

## KENT

53/57 CAMDEN RD., TUNBRIDGE WELLS  
0892-23242

## LEICESTERSHIRE

45 MARKET PLACE, LEICESTER  
0533-537678

**NORTHAMPTONSHIRE**  
73 ABBINGTON STREET,  
NORTHAMPTON 0604-35753

**NOTTINGHAMSHIRE**  
5-7 LOWER PARLIAMENT STREET,  
NOTTINGHAM

## OXFORDSHIRE

16 WESTGATE SHOPPING CENTRE, OXFORD

## STAFFORDSHIRE

30 WULFRUM WAY, WOLVERHAMPTON  
0902-23384

## SURREY

1046 WHITTING CROFT, CROYDON  
01-481 3027  
38/40 EDEN ST., KINGSTON 01-546 1271  
32 HILL ST. RICHMOND 01-948 1441

## WARWICKSHIRE

116 CORPORATION ST., BIRMINGHAM  
021-236 3503

ALL BRANCHES OPEN FROM  
9am to 6pm MON. TO SAT

**OUR CUSTOMER SERVICES DIVISION** ahead of office  
will answer all your enquiries—  
just ring 01-200 1321

**EXPORT** Personal exports  
arranged for overseas visitors.  
Goods, specially packed,  
insured and despatched to all  
parts of the world at minimum  
cost exclusive of VAT.  
Payment by bank transfer,  
certified cheque, postal order  
or money order in any  
currency.

**BARCLAYCARD & ACCESS**  
Phone your order  
to 01-200 0937 or  
call into any branch

**NO DEPOSIT TERMS**  
available on most goods  
for personal callers

CHEQUES TO THE VALUE OF £30  
ACCEPTED FROM PERSONAL SHOPPERS  
WITH BANKERS CARD. IN OTHER CASES  
AND FOR AMOUNTS IN EXCESS OF £30,  
PLEASE ALLOW TIME FOR CLEARANCE.  
BANKERS DRAFTS ACCEPTED.

All prices correct at 13/1/75 but  
subject to change without notice E & O. E.

A member of the  
Austrotron Group of Companies

### CLEAR PLASTIC MODEL SD640

Size: 85 x 64mm

50uA	£3 90
100uA	£3 85
200uA	£3 80
500uA	£3 75
50-0-500uA	£3 85
100-0-1000uA	£3 80
1mA	£3 75
5mA	£3 75
10mA	£3 75
50mA	£3 75
100mA	£3 75
500mA	£3 75
1A DC	£3 75
5A DC	£3 75
10A DC	£3 75
5V DC	£3 75

10V DC .. £3 75  
20V DC .. £3 75  
50V DC .. £3 75  
300V DC .. £3 85  
15V AC .. £3 85  
300V AC .. £3 85  
VU Meter .. £4 00




### \*Items with asterisk are Moving Iron type, all others are Moving Coil

### CLEAR PLASTIC MODEL SD830

Size: 110 x 83mm

50uA	£4 40
100uA	£4 35
200uA	£4 30
500uA	£4 25
50-0-500uA	£4 35
100-0-1000uA	£4 30
1mA	£4 20
5mA	£4 20
10mA	£4 20
50mA	£4 20
100mA	£4 20
500mA	£4 20
1A DC	£4 20
5A DC	£4 20
10A DC	£4 20
5V DC	£4 20

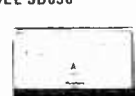10V DC .. £4 20  
20V DC .. £4 20  
50V DC .. £4 20  
300V DC .. £4 20  
15V AC .. £4 30  
300V AC .. £4 30  
VU Meter .. £4 50



### CLEAR PLASTIC MODEL MR 65P

Size: 86 x 78mm

50uA	£4 05
100uA	£3 95
200uA	£3 90
500uA	£3 85
50-0-500uA	£3 95
100-0-1000uA	£3 90
500-0-5000uA	£3 80
1mA	£3 80
1-0-1mA	£3 80
5mA	£3 80
10mA	£3 80
50mA	£3 80
100mA	£3 80
500mA	£3 80
1A DC	£3 80
5A DC	£3 80
10A DC	£3 80
15A DC	£3 80
20A DC	£3 90
50A DC	£3 95
500A DC	£4 15
5V DC	£3 80
10V DC	£3 80
15V DC	£3 85
20V DC	£3 80
50V DC	£3 80
150V DC	£3 80

300V DC .. £3 80  
15V AC .. £3 90  
50V AC .. £3 90  
150V AC .. £3 90  
300V AC .. £3 90  
500V AC .. £4 00  
S Meter 1mA .. £3 90  
VU Meter .. £4 20  
1A AC .. £3 80  
5A AC .. £3 80  
10A AC .. £3 80  
20A AC .. £3 80  
30A AC .. £3 80  
500mA AC .. £3 80



### CLEAR PLASTIC MODEL SW100

Size: 100 x 80mm

50uA	£4 70
100uA	£4 60
500uA	£4 40
50-0-500uA	£4 60
100-0-1000uA	£4 55
1mA	£4 40
1A DC	£4 40
5A DC	£4 40
20V DC	£4 40
50V DC	£4 40
300V DC	£4 40

150V AC .. £4 55  
300V AC .. £4 55  
VU Meter .. £5 00



### CLEAR PLASTIC MODEL MR 45P

Size: 50 x 50mm

50uA	£3 30
100uA	£3 20
200uA	£3 20
500uA	£3 10
50-0-500uA	£3 25
100-0-1000uA	£3 20
500-0-5000uA	£3 05
1mA	£3 05
5mA	£3 05
10mA	£3 05
50mA	£3 05
100mA	£3 05
500mA	£3 05
1A DC	£3 05
5A DC	£3 05
10V DC	£3 05
20V DC	£3 05
50V DC	£3 05
300V DC	£3 05
15V AC	£3 15

300V AC .. £3 15  
S Meter 1mA .. £3 15  
VU Meter .. £3 50  
1A AC .. £3 05  
5A AC .. £3 05  
10A AC .. £3 05  
20A AC .. £3 05  
30A AC .. £3 05



### BAKELITE MODEL S80 Enlarged Window

Size: 80 x 80mm

50uA	£4 60
100uA	£4 55
500uA	£4 30
50-0-500uA	£4 55
100-0-1000uA	£4 50
1mA	£4 30
1A DC	£4 30
5A DC	£4 30
20V DC	£4 30
50V DC	£4 30
300V DC	£4 30
15V AC	£4 40
VU Meter	£4 80



### EDGWISSE MODEL PE70

Size: 90 x 34mm

50uA	£4 25
100uA	£4 20
200uA	£4 15
500uA	£4 00
50-0-500uA	£4 25
100-0-1000uA	£4 15
1mA	£3 95
300V AC	£4 05
VU Meter	£4 40



### MODEL ED107 EDUCATIONAL METER

Size: 100 x 90 x 150mm including terminals

A range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is easily accessible to demonstrate internal working.

50uA	£8 70
100uA	£8 10
50-0-500uA	£8 10
1mA	£7 80
1-0-1mA	£7 80
1A DC	£7 80
5A DC	£7 80
5V DC	£7 80
10V DC	£7 80
15V DC	£7 80

20V DC .. £7 80  
50V DC .. £7 80  
300V DC .. £7 80  
500mA/5A DC .. £8 80  
5V/15V DC .. £8 80  
1/5A DC .. £8 80



### CLEAR PLASTIC MODEL MR 38P

Size: 42 x 42mm

50uA	£3 20
100uA	£3 15
200uA	£3 10
500uA	£3 05
50-0-500uA	£3 15
100-0-1000uA	£3 10
500-0-5000uA	£2 85
1mA	£2 85
1-0-1mA	£2 85
2mA	£2 85
5mA	£2 85
10mA	£2 85
20mA	£2 85
50mA	£2 85
100mA	£2 85
150mA	£2 85
200mA	£2 85
300mA	£2 85
500mA	£2 85
750mA	£2 85
1A DC	£2 85
2A DC	£2 85
5A DC	£2 85
10A DC	£2 85
3V DC	£2 85
10V DC	£2 85
15V DC	£2 85

300V AC .. £3 15  
S Meter 1mA .. £3 15  
VU Meter .. £3 50  
1A AC .. £3 05  
5A AC .. £3 05  
10A AC .. £3 05  
20A AC .. £3 05  
30A AC .. £3 05



### CLEAR PLASTIC MODEL MR 52P

Size: 60 x 60mm

50uA	£3 80
100uA	£3 75
500uA	£3 60
50-0-500uA	£3 80
100-0-1000uA	£3 75
1mA	£3 60
5mA	£3 60
10mA	£3 60
50mA	£3 60
100mA	£3 60
500mA	£3 60
1A DC	£3 60
5A DC	£3 60
10V DC	£3 60
50V DC	£3 60
300V DC	£3 60
15V AC	£3 50
300V AC	£3 50

S Meter 1mA .. £3 40  
VU Meter .. £3 90  
1A AC .. £3 40  
5A AC .. £3 40  
10A AC .. £3 40  
20A AC .. £3 40  
30A AC .. £3 40



### CLEAR PLASTIC MODEL MR 85P

Size: 120 x 110mm

50uA	£5 80
100uA	£5 55
200uA	£5 50
500uA	£5 40
50-0-500uA	£5 55
100-0-1000uA	£5 50
500-0-5000uA	£5 35
1mA	£5 35
1-0-1mA	£5 35
5mA	£5 35
10mA	£5 35
50mA	£5 35
100mA	£5 35
500mA	£5 35
1A DC	£5 35
5A DC	£5 35
15A DC	£5 35
30A DC	£5 35
10V DC	£5 35
20V DC	£5 35
50V DC	£5 35
150V DC	£5 35

300V DC .. £5 40  
15V AC .. £5 45  
300V AC .. £5 45  
S Meter 1mA .. £5 35  
VU Meter .. £5 70  
1A AC .. £5 35  
5A AC .. £5 35  
10A AC .. £5 35  
20A AC .. £5 35  
30A AC .. £5 35



### CLEAR PLASTIC MODEL SD460

Size: 58 x 46mm

50uA	£3 60
100uA	£3 55
200uA	£3 50
500uA	£3 45
50-0-500uA	£3 45
100-0-1000uA	£3 40
1mA	£3 40
5mA	£3 40
10mA	£3 40
50mA	£3 40
100mA	£3 40
500mA	£3 40
1A DC	£3 40
5A DC	£3 40
10A DC	£3 40
5V DC	£3 40

10V DC .. £3 40  
20V DC .. £3 40  
50V DC .. £3 40  
300V DC .. £3 40  
15V AC .. £3 55  
300V AC .. £3 55  
VU Meter .. £3 75



### BAKELITE MODEL MR 65

Size: 80 x 80mm

25uA	£5 40
50uA	£4 10
100uA	£4 05
500uA	£3 75
50-0-500uA	£4 05
100-0-1000uA	£4 00
500-0-5000uA	£3 70
1mA	£3 70
1-0-1mA	£3 70
5mA	£3 70
10mA	£3 70
50mA	£3 70
100mA	£3 70
500mA	£3 70
1A DC	£3 70
2A DC	£3 70
5A DC	£3 70
10A DC	£3 70
15A DC	£3 70
30A DC	£3 70
50A DC	£3 70
5V DC	£3 70
10V DC	£3 70
20V DC	£3 70
50V DC	£3 70
150V DC	£3 70

300V DC .. £3 90  
30V AC .. £3 70  
50V AC .. £3 70  
150V AC .. £3 70  
300V AC .. £3 70  
500V AC .. £3 70  
VU Meter .. £4 20  
1A AC .. £3 70  
5A AC .. £3 70  
10A AC .. £3 70  
20A AC .. £3 70  
30A AC .. £3 70  
50A AC .. £3 70  
500mA AC .. £3 70  
50mV DC .. £3 85  
100mV DC .. £3 85



POSTAGE & PACKING 15p

### 240° Wide Angle

1mA METERS  
MW1-6 60 x 60 mm  
£6.50 P & P 15p  
MW1-8 80 x 80 mm  
£6.90 P & P 15p



### YAMABISHI VARIABLE VOLTAGE TRANSFORMERS

Excellent quality at low cost. Input: 230V 50/60Hz. Output 0-260V.  
MODEL S260 BENCH MOUNTING

1A	£10.50
2.5A	£12.00
5A	£17.50
8A	£30.35
10A	£33.75
12A	£35.40
20A	£85.00
25A	£95.00
40A	£120.00



**ALL PRICES EXCLUDE VAT**

"I have used Rhombics, 4 half waves in phase, centre fed dipoles etc., but the success I have had with the Joystick (V.F.A.) has been amazing . . . only 20' high on 2" pipe in front of my mobile home, I never receive less than R7 and mostly R9 on CW DX working."— Bob Green, SU1KG/G3APH, W.B.E., W.A.C., Phone & C.W.

# ABOVE ALL

it's the antenna system that counts! However good your equipment, if a **PART-  
RIDGE SYSTEM** cannot improve your signals with the VFA at same height, return it (In re-saleable condition) for a cash refund.

**PARTRIDGE** have a complete **VFA SYSTEM**, correctly terminated for your equipment ranging from modern communications gear to a modest solid state radio. Don't be satisfied with anything less than the **PARTRIDGE WORLD RECORD ANTENNA SYSTEM!** Make your selection from the list below:-

- (Each **SYSTEM** consists of the elegant gold stove enamelled 7' 6" VFA and a matching finish **JOYMATCH A.T.U.**, despatched direct by parcel post—our risk). (All prices delivered—our risk)
- SYSTEM 'A'** for modern Communications Receivers ..... £28.43
  - SYSTEM 'D'** for other S.W. and M.W. receivers, all types ..... £20.84
  - SYSTEM 'J'** for TXs and TCVRs up to 500w PEP 160 thru 10m (pa inpt) ..... £33.59
  - JOYMATCH A.T.U.** kit (1.6 continuous to 30 mHz) ..... £8.24
  - JOYMATCH A.T.U.** kit (500 kHz continuous to 30 mHz) ..... £8.24
  - Either kit fully assembled ..... £7.55
  - JOYMATCH "Aerial Bandswitch"** tuned aerial. MW & SW ..... £8.24
  - SUPER SENSITIVE** general coverage DX-CRYSTAL SET that REALLY WORKS, not a toy, complete with Aerial and a sensitive matching Earpiece ..... £3.92
  - COMMUNICATIONS HEADPHONES**, 8 ohms, matches most modern Comm. Rxs. .... £3.99
  - VFA Stack Lashing (Massive VFA support on chimney stack) ..... £2.51
  - JOYMATCH Artificial Earth** (ground) switch tuned ..... £8.24
  - A.G.T.U. Artificial Earth D.I.Y. add on unit for your A.T.U. .... £0.80
  - Radials for the A.G.T.U. cut to required band, each ..... £0.60
  - "INVISIBLE AERIAL" wire, tough PVC covered tinned copper 22swg per 10m ..... £0.60
  - A.G.T.U. supplied fitted to **JOYMATCH A.T.U.'s** (less radials) ..... £0.80
  - AERIAL WIRE**, heavy duty 16swg enamelled aluminium, per 10 metres ..... £0.59
  - VALVES**, complete set for 9R59DS & 9R59DE, including OA2 stabiliser ..... £5.25

**PARTRIDGE SUPER PACKAGE COMPLETE RADIO STATION FOR ANY LOCATION** £157.58  
Comprising:—Trilo QR666 Gen. Cov. RX, Headphones, V.F.A., System 'A', all connecting cables, del. (our risk)

Send 4p stamp for details and expert advice.




Phone 0843 62535  
or 62839  
(after office hours)  
G3CED G3VFA


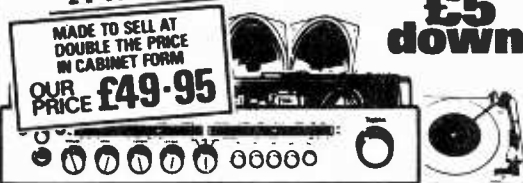
## QUALITY STEREO SOUND.

ALMOST 1/2 PRICE OFFER! SOLENT AUDIO SYSTEM



MADE TO SELL AT DOUBLE THE PRICE IN CABINET FORM  
OUR PRICE £49.95

£5 down

\*Stereo Tuner Amplifier chassis with AM,FM radio covering long medium short and Stereo FM wavebands. Separate Base and Treble controls. 30 watts total power output (frequency response 25-20,000 Hz) Tape record and playback facilities. Dimensions 18" x 8 1/2" x 3 1/4". The very latest BSR automatic record deck with cue and pause control. Two matching elliptical speaker units.

Order early limited stocks available cash price £49.95. Credit Sale £5.00 deposit 9 monthly payments of £5.75 (Total Credit price £56.75). P. & P. £3.00. Send £8.00 today.

Chassis only available for cash at £35.00.


Full 12 months Guarantee.

CALLERS WELCOME.

LEWIS radio PW/4/75 100 CHASE SIDE SOUTHGATE LONDON N14 5PL Telephones: 01-882-1644

NEW

ALL SILICON!

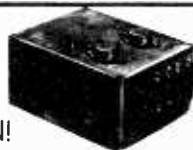

PRACTICAL WIRELESS

## ELECTRONIC IGNITION SYSTEM

This Capacitor-Discharge Electronic Ignition System was described in *Practical Wireless*, and has proved extremely popular.

The kit is supplied with a ready-drilled roller-tinned printed-circuit board and fully machined die-cast case with AMP Electrical Spade Connector Block together with a custom wound transformer, first grade components and full constructional details.

The original circuit employed Germanium Power Transistors for the negative earth version. WE OFFER SILICON P.N.P. POWER DEVICES AT NO EXTRA COST! All components are available separately. Case size 4 1/2" x 3 1/2" x 2". Complete assembly and construction manual free with kit, available separately 25p.

SUITABLE FOR 12V SYSTEMS WITH NEG. OR POS. EARTH.

PRICE: £9.50 U.K. ORDERS PLEASE ADD VAT

Quantity Discounts:

Trade and Overseas	1-5 Nett	6-9 less 10%
Enquiries Invited	10-49 less 15%	50-99 less 20%
Mail Order Only.	100-999 less 25%	1000 up less 30%

PLEASE STATE POS. OR NEG. EARTH WHEN ORDERING

## DABAR ELECTRONIC PRODUCTS




98 LICHFIELD STREET  
WALSALL, Staffs WS1 1UZ






I.L.P. (Electronics) Ltd

# SHEER SIMPLICITY!

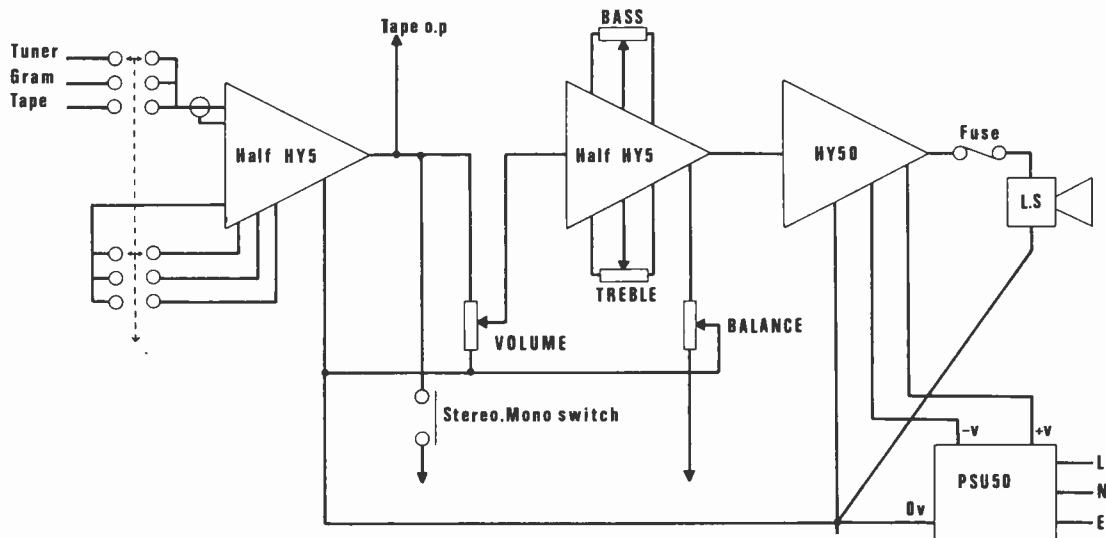

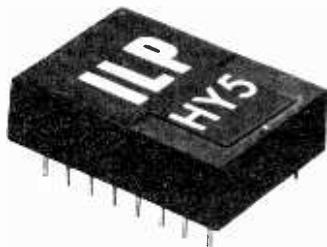MONO ELECTRICAL CIRCUIT DIAGRAM WITH INTERCONNECTIONS FOR STEREO SHOWN



The HY5 is a complete mono hybrid preamplifier, ideally suited for both mono and stereo applications. Internally the device consists of two high quality amplifiers—the first contains frequency equalisation and gain correction, while the second caters for tone control and balance.

#### TECHNICAL SPECIFICATION

Inputs: Magnetic Pick-up 3mV RIAA; Ceramic Pick-up 30mV; Microphone 10mV; Tuner 100mV; Auxillary 3-100mV; Input Impedance 47kΩ at 1kHz. Outputs: Tape 100mV; Main output 0db (0.775V RMS). Active Tone Controls: Treble ± 12db at 10kHz; Bass ± 12db at 100Hz. Distortion: 0.5% at 1kHz. Signal/Noise Ratio: 68db. Overload Capability: 40db on most sensitive input. Supply Voltage: ± 16-25V.

PRICE £4.50 + 36p VAT  
P. & P. free




The HY50 is a complete solid state hybrid HI-FI amplifier incorporating its own high conductivity heatsink hermetically sealed in black epoxy resin. Only five connections are provided, input, output, power lines and earth.

#### TECHNICAL SPECIFICATION

Output Power: 25W RMS into 8Ω. Load Impedance: 4-16Ω. Input Sensitivity 0db (0.775V RMS). Input Impedance: 47kΩ. Distortion: Less than 0.1% at 25V typically 0.05%. Signal/Noise Ratio: Better than 75db. Frequency Response: 10Hz-50kHz ± 3db. Supply Voltage: ± 25V. Size: 105 x 50 x 25mm.

PRICE £5.98 + 48p VAT  
P. & P. free

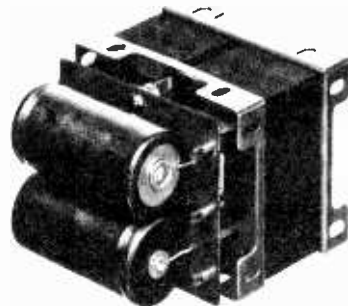

The PSU50 incorporates a specially designed transformer and can be used for either mono or stereo systems.

TECHNICAL SPECIFICATIONS  
Output voltage: 50V (25-0-25V). Input Voltage: 210-240V.  
Size: L.70. D.90. H.60mm.

PRICE £6 + 48p VAT  
P. & P. free

## TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd.  
Crossland House,  
Nackington, Canterbury  
Kent CT4 7AD  
Tel (0227) 63218

Please supply, .....  
Total Purchase price .....  
I Enclose, Cheque  Postal Orders  Money Order   
Please debit my Access account  Barclaycard account   
Account number .....  
Name & Address .....  
Signature .....



### POWER UNIT Type A126

Supplying 6, 7.5 or 9 Volt DC at 200 mA.

In moulded case forming a 2 pin 5A mains plug.

2 metre output lead with 4-way muting giving 2.1 and 2.5 mA sockets and 3.5 mA plugs.

Price £2.30. Post 10p.



### 2" and 4" PANEL METERS

2"		4"	
SIZE: 60mm Wide x 45mm High x 40mm Deep.	I.R. Movement Ohms	SIZE: 110mm Wide x 82mm High x 43mm Deep.	I.R. Movement Ohms
0-50 micro A.	1250	0-50 micro A.	1400
0-100 micro A.	580	0-100 micro A.	730
0-500 micro A.	170	0-500 micro A.	200
0-1 mA	170	0-1 mA	200
0-5 mA	170	0-5 mA	200
0-10 mA	6	0-10 mA	6
0-50 mA	0.5	0-50 mA	0.5
0-100 mA	0.5	0-100 mA	0.5
0-500 mA	0.5	0-500 mA	0.5
0-1 AMP	0.5	0-1 AMP	0.5
0-2 AMP	0.5	0-2 AMP	0.5
0-25 Volt	15K	0-25 Volt	15K
0-50 Volt	50K	0-50 Volt	50K
0-300 Volt	300K	0-300 Volt	300K
"x" Meter	170	"x" Meter	200
VU Meter	5250	VU Meter	5250

VU Meters are complete with detectors. Modern wide view. Price 2" £3.15 Post 10p. Price 4" £4.15 Post 10p. Lamps 75p per set.

### 1/2 watt CARBON FILM RESISTORS

1/2 watt at 70°C E 12 range 10Ω-1MΩ 5% tol above 470 KΩ 10% tol at 85p per 100.

### CI100 MULTIMETER

Special Offer Compact General Purpose Mini Multimeter Input Resistance 1000 ohms per volt



Ranges:  
AC Volts 0-15, 50, 250, 1000 V  
DC Volts 0-10, 50, 250, 1000 V  
DC Current 0-1 mA  
0-100mA  
Resistance 0-100K ohms  
Size 80 x 24 x 90 mm  
Complete with Batteries, Test Prods, Instructions. Special price £3.25 Post 20p.

### CI101 MULTIMETER

Input Resistance 20,000 ohms per volt Overload protection 150 μA movement, clear scale Ranges—AC Volts 0-10, 50, 250, 1000V DC Volts 0-5, 25, 125, 500, 2500V DC Current 0-50 mA Resistance 0-80 Kohms, 0-6 Mohms Decibels -20 to +22 dB. Carrying Case, Test Prods and Batteries Included. Size: 11.5 x 8.3 x 2.7 cm. Price £9.85. Post 20p.

# TRANSFORMERS

### CASED TRANSFORMERS

Housed in smart resin-coated steel cases, with 3-core power cable and outlet socket, fused primary winding. Isolation types are fitted with 3-pin outlet sockets, and are available with 110 volt or 240 volt output. (Please state). Auto types are fitted with 2-pin flat style sockets up to 500 VA. 3-pin sockets from 750 to 3000 VA. See Auto and Isolation sections for prices.

### SAFETY ISOLATING

Prim. 120/240V. Sec. 120/240V. Centre Tap with Screen.

VA	Ref. No.	Price Cased	Price Plugs 2 Pin 1 Earth	Price Open Post
60	149	7.35	0.80	4.00 0.38
100	150	8.22	0.80	4.60 0.52
200	151	10.20	0.80	7.40 0.52
250	152	11.88	0.80	8.88 0.65
300	153	14.10	0.80	10.80 0.80
500	154	15.88	0.80	12.38 1.00
750	155	24.83	1.00	18.72 1.20
1000	156	32.19	1.00	26.50 1.50
1500	157	38.18	1.00	30.34 0.20
2000	158	45.20	2.40	34.58 0.20
3000	159	68.50	2.40	53.35 0.20

### 12 & 24 Volts Prim. 200-240V.

Amps 12V	24V	Ref. No.	Price	Post
0.3	0.15	242	1.34	0.22
0.5	0.25	111	1.88	0.22
1	0.5	212	1.88	0.22
2	1	71	2.09	0.22
4	2	18	3.58	0.38
6	3	70	3.80	0.42
8	4	108	4.20	0.52
10	5	72	4.80	0.52
12	6	116	5.01	0.52
16	8	17	6.22	0.52
20	10	116	9.47	0.69
30	15	187	11.95	0.97
40	20	232	13.26	1.00
50	30	226	16.30	1.10

### 30 Volts

Prim. 200-240V. Amps	Ref. No.	Sec. 12, 15, 20, 24, 30V. Price	Post
0.5	112	1.72	0.22
1	79	2.31	0.38
2	3	3.26	0.38
3	20	4.10	0.42
4	21	4.88	0.52
5	51	5.80	0.52
6	117	6.50	0.52
8	88	8.50	0.67
10	89	9.97	0.67

### AUTO TRANSFORMERS

VA	Ref. No.	Price Cased	Price Plugs 2 & 3 pin	Price Open	Post
Tapped at 115, 220, 240 Volts	20	113	3.00	0.15	1.55 0.30
Tapped at 115, 200, 220, 240 Volts	180	4	5.80	0.15	3.98 0.30
	200	65	6.40	0.15	4.50 0.40
	300	66	7.27	0.15	5.28 0.52
	500	67	9.99	0.15	8.29 0.67
	750	83	12.58	0.75	9.76 0.82
	1000	84	15.70	0.75	12.40 0.82
	1500	93	19.88	0.75	16.58 1.30
	2000	95	30.10	1.44	25.05 1.60
	3000	73	43.58	1.90	37.00 1.90

### 50 Volts

Prim. 200-240V. Sec. 19, 25, 33, 40, 50V.

Amps	Ref. No.	Price	Post
0.5	102	2.33	0.30
1	103	3.00	0.38
2	104	4.57	0.42
3	105	5.20	0.52
4	106	5.89	0.52
6	107	11.17	0.67
8	116	14.19	0.97
10	119	15.47	0.97

### 60 Volts

Prim. 230-240V. Sec. 24, 30, 40, 48, 60V.

Amps	Ref. No.	Price	Post
0.5	124	2.08	0.38
1	126	2.95	0.38
2	127	4.53	0.42
3	125	6.84	0.52
4	123	7.94	0.67
5	40	8.86	0.67
6	120	10.15	0.82
8	121	13.58	1.00
10	122	18.16	1.00
12	189	16.00	1.10

### MINIATURE AND EQUIPMENT

Prim. 240V with screen.

Sec. 1 Volts	Sec. 2	Milliamps	Ref. No.	Price	Post
3-0-3		200	238	1.23	0.10
0-6	0-6	500	234	1.30	0.10
0-6	0-6	1000	212	1.88	0.22
9-0-9		100	13	1.23	0.10
0-9	0-9	330	330	2.35	1.48
0-8-9	0-8-9	500	500	2.07	1.75
0-8-9	0-8-9	1000	1000	2.08	2.30
15-0-15		40	240	1.23	0.10
0-15	0-15	200	200	2.36	1.30
20-0-20		30	241	1.33	0.10
0-20	0-20	150	150	2.37	1.30
0-15-20	0-15-20	500	500	2.05	2.47
0-20	0-20	300	300	2.14	1.72
0-20		3500	NO SCREEN	11.16	3.00
20-12-0-12-20		700 (D/C)	221	2.31	0.40
0-15-20	0-15-20	1000	1000	2.06	3.22
0-15-27	0-15-27	500	500	2.03	2.73
0-15-27	0-15-27	1000	1000	2.04	3.52

### PLASTIC CASED SILICON BRIDGE RECTIFIERS

One Amp	Two Amp	Four Amp	Six Amp
50 P.I.V. 25p	50 P.I.V. 35p	100 P.I.V. 55p	50 P.I.V. 45p
100 P.I.V. 25p	100 P.I.V. 40p	200 P.I.V. 55p	100 P.I.V. 70p
200 P.I.V. 28p	200 P.I.V. 45p	400 P.I.V. 65p	200 P.I.V. 80p
600 P.I.V. 30p	400 P.I.V. 50p	600 P.I.V. 75p	400 P.I.V. 90p

ADD 10p P & P PER ORDER

PLEASE ADD 8% FOR VAT

### POWER UNIT Type CC 12-05

Output switched 3, 4.5, 6, 7.5 and 9 and 12 volts at 500 mA D.C. Operates from 240 V mains, suitable for Radios, Tape Recorders, Record Players etc Size 7.5 x 5.0 x 14.0cm. Price £3.95. Post 25p.



### MINIATURE NEONS

6mm dia., 12mm length leads length approx. 20mm. Recommended ballast resistor 150K ohms for 240 Volt operation Price: Packet of 10 for 55p. Postage 10p.

# A.S.P. LTD.

DEPT PW2, SIMMONDS ROAD, WINCHEAP, CANTERBURY, KENT. Tel: (0227) 52436

### INVERTERS

240v-50Mz. from your 12v car battery.  
25 watt—£3.90 + 30p p & p.  
40 watt—£6.80 + 55p p & p.  
75 watt—£9.95 + 75p p & p.  
All above inverters are in kit form but may be purchased built up & ready for use. Price list sent on receipt of stamped addressed envelope.

### P.W. AUTOMATIC EMERGENCY SUPPLY

250v-50Hz-150 watt inverter with built in battery charger. In event of power failure switches over automatically from battery charging to inverter operation. Cct. as appeared in Dec. 73 P.W. Complete kit of parts (excluding meter) £22.50 + £1.10 p & p.

### COMPLETE FLUORESCENT LIGHT INVERTOR KIT

8 watt-12v-Fluorescent light, suitable for tents, caravans, houses, boats and secondary lighting for, factories, hotels etc. 12"-8 watt £2.90 + 25p p & p. 21"-13 watt. £3.30 + 30p p & p.

### TRANSFORMERS & COILS

Both high volume & small order capacity available for Mains, R.F., & I.F. Transformers. Before you buy elsewhere let us quote you and see what you save. V.A.T. at 8% included.

### TRADE & EXPORT ENQUIRIES WELCOMED

ASTRO ELECTRONICS, 10A SPRINGBANK RD., CHESTERFIELD, DERBYSHIRE

# ELECTRONI-KIT

... educational kits of exceptional quality! (AUDIO mag. Dec. 1974)

### BUILD AND REBUILD ANY NUMBER OF TIMES:

Radios, microphones, burglar alarms, inter-comms, ferrite detectors, solar cell, photoelectric cell, voice relay, electronic cats, birds, guns, organs, illuminometers, voltmeters, meters of all types, etc., etc., plus your own circuit designs.

COMPLETELY SAFE—suitable for all, from beginners on. 30 different projects £10-45, 100 different projects £20-45, over 150 £33-95. Add-on kits, spares, available too.

Prices include Manuals, Battery, p & p, VAT, etc. Cheque/PO (or 7p for catalogues) to DEPT. PW:

Satisfaction guaranteed.

ELECTRONI-KIT LTD, 408 St. John's Street, London, EC1. (01-278 4579)

# Crescent Quality Components

**BARGAIN CAPACITOR 2.200MFD at 63v. DC wkr.**  
Size = 2" x 1 1/2" diameter. Tag ended. All new and unused. Our price 85p.

**S. G. BROWN HEADSET**  
Finest quality British made Lightweight Headphones. Incorporates ceramic piezo electric transducers.  
Specification:-  
Frequency—20-17,500 CPS  
Impedance—Predominantly capacitive, at .001MFD per earpiece can be regarded as 150K at lka.  
Weight—3.5oz. (98 grams).  
A bargain at £1.25 each set

**JB11D STEREO JUNCTION BOX**  
The most popular stereo junction box. Facility for two pairs of headphones and two speakers. 3 position switch selects headphones, loud-speakers or both.  
A bargain at £2.50



**LIGHT EMITTING DIODES**  
TL1 208 (Red) With Clip 25p each  
TL1 208 (Green) With Clip 85p each  
TL1 208 (Yellow) With Clip 85p each  
Med 500 T092 Type 18p each

**LED HEADOUTS**  
Litronix  
DL707 3 Character 14 Pin Dtl. £2.90  
DL701 as above but ± 1 £2.00  
DL747 6 Character £2.82  
Minitron  
3015 7 Segment 16 Pin Dtl £1.18  
3015G as above but ± 1 £1.18  
Clock Chip  
CT7001 MOS/LSI Digital Clock/Calendar Chip Plus full Circuits and Information leaflet £5.95  
Circuits and Information Sheet 15p  
Lit 704 Led Display for above £1.35  
Or 4 for £5.25

**WAFER SWITCHES**  
1 Pole 12 Way £2.00  
2 Pole 2 Way £2.00  
2 Pole 3 Way £2.00  
2 Pole 4 Way £2.00  
2 Pole 6 Way £2.00  
3 Pole 4 Way £2.00  
4 Pole 3 Way £2.00  
25p each



**POTENTIOMETERS**  
All types 1" and less diameter  
Singles Dual  
5K Log or 5K  
10K Lin Less 10K  
25K Switch 25K Less  
50K 15p each 50K Switch  
100K 100K 45p each  
250K Double 250K  
500K Pole 500K  
1M Switch 1M  
2M 30p each 2M

**PRE SETS**  
Sub Miniature Skeleton Type 0-1 Watt Horizontal Mounting 100, 250 and 500 ohm, 1k, 2.5k, 5k, 10k, 25k, 50k, 100k, 250k, 500k, and 1M ohm 6p each

**MAINS TRANSFORMERS**  
Open Type Double Wound Continuously Rated, two hole fixing clamp with colour coded flying leads, varnish impregnated. Approx. size: 1 1/2" x 1 1/2" x 1 1/2" high  
Fixing centres: 2 1/2"/3"  
TR1 20-0-20v 100 m/a  
TR2 12-0-12 v 100 m/a All  
TR3 9-0-9 v 100 m/a 240 Volt  
TR4 6-0-6 v 100 m/a Primary  
TR5 3-0-3 v 100 m/a  
Our Price £1.23 each

**200/250v MAINS RELAY**  
Heavy duty relays 2-500 ohm coil. All new and unused P.F.T. mains relays 50p, Carr. Free. Special quantity £40 per 100 off.

**MINIATURE RELAYS**  
Brand new range of British made Relays, Size 1 1/2" x 1" x 1/2". All two changovers with 250v 1.5A contacts and suitable for fitting on 1m Veroboard.  
Type Volts Current Ohms All  
27/A 12v 17mA 700 £1.30  
21/A 12v 25mA/A 430 £1.30  
12/A 6v 33mA/A 185 each

**MONO/STEREO MICROPHONE MIXER**  
9 volt. High impedance input. Gold finish with four black plastic chrome tipped level control knobs. On/Off switch and stereo/mono switch. 4 Input sockets.  
**SPECIFICATIONS:-**  
Input Imp = For XTAL Mics etc.  
Gain = Approx 3.D.B.  
Max Input Sig = 1 volt  
Max Output Sig. = 1.3 volt  
Noise Ratio = -60DB  
Supply = 9 volt  
OUR PRICE = £5.95p

**POWER PACKS**  
PP1 Switched 3 - 6 - 7 1/2 - 9 volt 400M/A Transistor and Zener Stabilised On/Off Switch and Polarity Reversal Switch, in a black metal case £5.25 each.  
PP2 Switched 6 - 7 1/2 - 9 volt Battery Eliminator. Approx. size 2 1/2" x 2 1/2" x 3 1/2". Ideal for cassette recorders £3.25  
PP3 Car converter. From 12v Pos. or Neg. to = 6 - 7 1/2 - 9 volt. Easy to fit and transistor regulated £3.90



**VEROBOARD**

1	15	Plain 15
3 1/2 x 3 1/2	32p	15p
2 1/2 x 5	34p	15p
3 1/2 x 3 1/2	34p	15p
3 1/2 x 5	39p	45p
17 x 2 1/2	1.08p	77p
17 x 3 1/2	1.45p	1.16p
17 x 5	1.85p	1.10p

Pin insertion tool 75p  
Spot face cutter 52p  
Pkt. 36 pins (state 1 or 15) 25p

**LOUDSPEAKERS**

2 1/2" 8 ohm	50p
2 1/2" 40 ohm	50p
2 1/2" 80 ohm	50p
5" 8 ohm	ceramic £1.25
5 1/2" 8 ohm dual cone	ceramic £2.50
10" 8 ohm dual cone	ceramic £3.75
7" x 4" 8 ohm	ceramic £1.80
8" x 5" 8 ohm	Permanent Magnet £1.80
*EMI 13" x 8" 450 Kit	£4.10
3 - 8 - 15 ohm	£4.10
*EMI 13" x 8" 350 Kit 8 ohm	£7.50

**10 inch DUAL CONE L/S**  
Manufactured by "ELAC" to a very high standard these loudspeakers are a real bargain.  
SPEC:- Size = 10" Dual Cone.  
Power = 10 Watts  
Frequency = 40-12000Hz  
Our Price = £3.75p each

**MAINS KEYNECTOR**  
Keynector connects any Electrical Equipment to the mains supply in seconds. Ideal for bench, garage demonstrations, etc. Multi connections can be made (max. load 13A fused).  
£3.25p.


**ALUMINIUM BOXES**  
Metal project boxes give your work a professional finish

	L	W	H	
AB7	2 1/2	5 1/2	1 1/2	54p
AB8	4	4	1 1/2	62p
AB9	4	4	1 1/2	54p
AB10	4	2 1/2	1 1/2	62p
AB11	4	2 1/2	2	54p
AB12	3	2	1	45p
AB13	6	4	2	89p
AB14	7	5	2 1/2	89p
AB15	8	6	3	99p
AB16	10	7	3	£1.35
AB17	10	4 1/2	3	£1.02
AB18	12	5	3	£1.20
AB19	12	8	3	£1.50

**ABS PLASTIC BOXES**  
Handy boxes for construction projects. Moulded extrusion rails for P.C. or chassis panels. Fitted with 1mm front panels.  
1006 = 105mm x 73mm x 45mm = 51p  
1006 = 150mm x 73mm x 47mm = 66p  
1007 = 184mm x 124mm x 60mm = 98p  
1021 = 105mm x 74mm x 45mm (sloping front) = 50p

**BARGAIN BOARDS**  
Components galore for the experimenter Ex Computer boards with Resistors, Capacitors and useful Transistors—at least 4 transistors per board. Five boards £1.00.

**CLEAR PLASTIC PANEL METERS**  
Size 59mm x 46mm x 35mm these meters require a 35mm hole for mounting.  
ME6 = 0 to 50 micro amp Full Scale  
ME7 = 0 to 100 micro amp Full Scale  
ME8 = 0 to 500 micro amp Full Scale  
ME9 = 0 to 1 m/a Full Scale  
ME10 = 0 to 5 m/a Full Scale  
ME11 = 0 to 10 m/a Full Scale  
ME12 = 0 to 50 m/a Full Scale  
ME13 = 0 to 100 m/a Full Scale  
ME14 = 0 to 500 m/a Full Scale  
ME15 = 0 to 1 amp Full Scale  
ME16 = 0 to 50 volts  
ME17 = 0 to 300 volts A.C. Full Scale  
ME18 = "S" Meter  
ME19 = "VU" Meter  
OUR PRICE £3.90

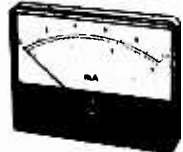

**ADD LUXURY TO YOUR CAR**  
with a motor driven car aerial  
SPEC:- ★ 5 section  
★ extended length 100cm  
★ Length under fender 40cm  
★ Cable length 120cm  
Supplied complete with fixing bracket and control switch £7.50

**DECON DALO 33PC ETCH RESIST PEN**  
The Decon Dalo 33PC is a unique instrument for the professional and amateur electronics engineer, enabling him to prepare in minutes a perfect printed circuit board.  
OUR PRICE 80p

**WIRE WOUND VOLUME CONTROL**  
250ohm Only 25p EACH.  
Approx 1" Diameter. Long standard spindle.

**CABLE LESS SOLDERING IRON**  
WAHL "ISO-TIP"  
★ Completely Portable  
★ Heats in 5 seconds  
★ Solders up to 150 joints or more per charge  
★ Recharges automatically in its own stand  
★ No AC leakage or induced current to damage delicate components  
★ Heats to 700 deg. F  
★ Fine Tip for delicate and general purpose soldering  
★ Only 8" long and weighs just 8 ozs.  
OUR PRICE £9.75 (spare bits are available)

**STOP PRESS**

BHA002	16 watt Amp Module	£2.50
NE555	Timer I.C.	78p
MC1310P	Stereo Decoder I.C.	£2.90
7805	Regulator	£1.49
TIP 29A		65p
TIP 30A		85p
BC107		10p
BC108		10p
BC109		10p

**L.C. SOCKETS**  
D.I.L.  
8 pin  
14 pin  
16 pin

**BARGAIN TRANSFORMERS**  
12-0-12 volt 500m/a  
240 volt primary transformer bargain.  
approx size = 60mm x 40mm x 50mm  
fixing centres = 75mm  
Our Price = £1.20.  
18 volt 500m/a  
240 volt primary  
approx size = 60mm x 40mm x 50mm  
fixing centres = 75mm  
Our Price = £1.00.

**LOW NOISE LOW PRICE CASSETTES**  
Good quality tape in well made screw type cassettes. Presented in single plastic cases.  
C80 = 81p  
C90 = 42p  
C120 = 55p  
10% Discount on ten or more cassettes of one type.

**U.K. POSTAGE 15p UNLESS OTHERWISE STATED**  
**V.A.T. Please add 8% to all Totals**


**CRESCENT RADIO LTD. P.W.**  
All mail to 11 MAYES ROAD,  
WOOD GREEN, LONDON N22 6TL  
Phone: 01-888 3206  
Callers Welcome at  
15 Mayes Road & 13 South Mall, Edmonton N9.

**If you construct You should own one.**  
**CRESCENT CATALOGUE**  
Price 30p.

# R T V C

# FOR AUDIO AT A BUDGET

## COMPLETE STEREO SYSTEM

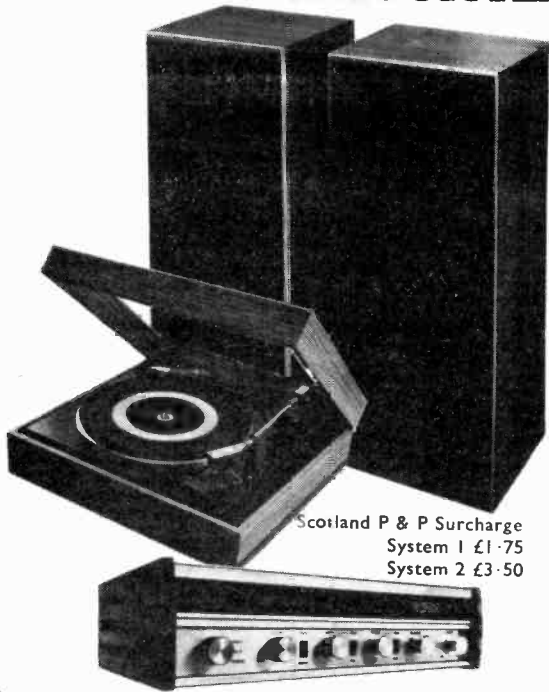

Scotland P & P Surcharge  
System 1 £1.75  
System 2 £3.50

### System 1. £59.00

40 Watt Amplifier. Viscount III - R102 now 20 watts per channel.  
\* System 1 includes:  
Viscount III amplifier - volume, bass, treble and balance controls, plus switches for mono/stereo on/off function and bass and treble filters. Plus headphone socket.  
**Specification**  
20 watts per channel into 8 ohms. Total distortion  $\alpha$  10W @ 1kHz 0.1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K. equalised within  $\pm$ 1dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power). Tape out facilities: headphone socket, power out 250mW per channel. **Tone controls and filter characteristics:** Bass:  $\pm$ 12dB to  $\pm$ 17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble  $\pm$ 12dB to  $\pm$ 12dB @ 15kHz. Treble filter: 12dB per octave. **Signal to noise ratio:** (all controls at max.) -58dB. Crosstalk better than 35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx. 13 $\frac{1}{2}$ " x 9" x 3 $\frac{1}{2}$ ".  
Garrard SP 25 Mk III deck with magnetic cartridge, de luxe plinth and hinged cover.  
Two Duo Type II matched speakers - Enclosure size approx. 17 $\frac{1}{2}$ " x 10 $\frac{1}{2}$ " x 6" in simulated teak. Drive unit 13" x 8" with parasitic tweeter. 10 watts handling.

### Complete System £59.00

### System 2. £82.00

Viscount III amplifier (As System 1)  
Garrard SP 25 Mk III deck (As System 1)  
Two Duo Type III matched speakers - Enclosure size approx. 27" x 13" x 11 $\frac{1}{2}$ "  
Finished in teak veneer. Drive units 13" x 8" bass driver, and two 3" (approx.) tweeters. 20 watts R.M.S., 8 ohms frequency range - 20 Hz to 18,000 Hz.

### Complete System £82.00

#### PRICES: SYSTEM 1

Viscount III R102 amplifier  
£27.00 + £1.60 p & p

2 Duo Type II speakers  
£14.00 + £3.50 p & p

Garrard SP25 with Mag. cartridge de luxe plinth and hinged cover  
£21.00 + £2.80 p & p

total: £62.00

Available complete for only:  
£59.00 + £5.50 p & p

#### PRICES: SYSTEM 2

Viscount III R102 amplifier  
£27.00 + £1.60 p & p

2 Duo Type III speakers  
£39.00 + £6.40 p & p

Garrard SP25 with Mag. cartridge de luxe plinth and hinged cover  
£21.00 + £2.80 p & p

total: £87.00

Available complete for only:  
£82.00 + £6.50 p & p

## STEREO 21 \* QUALITY SOUND FOR LESS THAN £20.00

Stereo 21, easy to assemble audio system kit. No soldering required. The unit is finished in white P.V.C. and the acrylic top presents an unusually interesting variation on the modern deck plinth.

Includes: - 1 BSR 3 speed deck, automatic, manual facilities together with stereo cartridge.

Two speakers with cabinets.


Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.

Specifications: For the technically minded: -

Input sensitivity 600mV. Aux. input sensitivity 120mV. Power output 2.7 watts per channel. Output impedance 8-15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs - radio, tape, etc., and outputs for taping discs. Overall Dimensions. Speakers approx. 15 $\frac{1}{2}$ " x 8" x 4". Complete deck and cover in closed position approx. 15 $\frac{1}{2}$ " x 12" x 6".

Complete only £19.95 + £1.00 p & p. Extras if required. Optional Diamond Stylus £1.37.

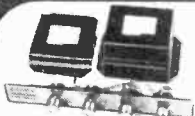Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance. £3.85.



## BUILD YOUR OWN \* STEREO AMPLIFIER

For the man who wants to design his own stereo - here's your chance to start, with Unisound - pre-amp, power amplifier and control panel. No soldering - just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency f.c. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only. £7.64 + 90p. p & p. Also available with 2 speakers (7" x 4") £9 + 75p p & p


## 8 TRACK HOME CARTRIDGE PLAYER \*



Elegant self selector push button player for use with your stereo system. Compatible with Viscount III system, Unisound module and the Stereo 21. Technical specification Mains input, 240V, Output sensitivity 125mV. Comparable unit sold elsewhere at £24.00 approx. Yours for only £11.95 + £1.45p. p & p.


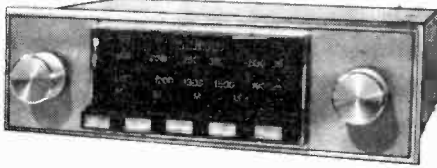
# PUSH BUTTON CAR RADIO KIT \* The Tourist II



**NO SOLDERING REQUIRED!**

**NOW BUILD YOUR OWN PUSH BUTTON CAR RADIO**  
Easy to assemble construction kit comprising fully completed and tested printed circuit board on which no soldering is required. All connections are simple push fit type making for easy assembly. Fine tuning push button mechanism is fully built and tested to mate with printed circuit board.

Technical specification: (1) **Output** 4 watts R.M.S. output. For 12 volt operation on negative or positive earth. (2) **Integrated circuit** output stage, pre-built three stage IF Module. **Controls** volume manual tuning and five push buttons for station selection, illuminated tuning scale covering full, medium and long wave bands.

Size chassis 7" wide, 2" high and 4 3/4" deep approx **£7.70**

**Speaker** including baffle and fixing strip **£1.65 + 37p p & p**

**Car Aerial** Recommended—fully retractable **£1.37 + 30p p & p**

**The Tourist I Kit** For the experienced constructor. If you can solder on a printed circuit board you can build this model. Same technical specification as Tourist II. **Price £6.60 + 90p p & p**

## EMI SPEAKERS AT FANTASTIC REDUCTIONS EASY BUILD SPEAKER KITS



These superb simulated teak-finished speaker kits have been specially designed by RT-VC for the cost-conscious hi-fi enthusiast who wants top quality speakers but doesn't want to spend the earth. Built to EMI's exacting specification, these new RT-VC speaker kits (350 type kit) incorporate 13" x 8" woofer, 3 1/2" tweeter and matching crossover. Easily put together with just a few basic tools.

Specification (each speaker) Impedance 8 ohms. Power handling 15 watts r.m.s. (30 watts peak). Response 20-20,000 Hz. Size 20" x 11" x 9 1/2". Comparable built units (EMI LE3) sold elsewhere for over £45 pair.

**£18.95 pair + £6.40 p & p Complete**

## 20 WATTS SPEAKER SYSTEM

System consists of a 13" x 8" (approx) elliptical woofer unit with a 8" x 5" (approx.) mid range unit incorporating parasitic tweeter and crossover components. Circuit Diagram

**Technical Specification:**


**Bass Unit**

Flux density—100 K, speech coil—1 1/2", Cone, Triple laminated paper with P.V.C. surround.

**Mid Range Unit**  
Flux density—33K, speech coil—1" with parasitic tweeter.

**Power Handling**  
20 watts R.M.S., impedance—8 ohms, frequency response—20 Hz to 18,000 Hz.

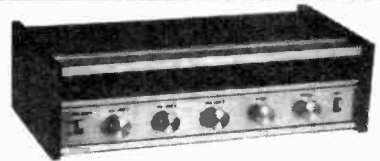**OUR PRICE**  
**£7.50. Complete**  
**+ 90p p & p.**



## DISCO AMPLIFIER\*



Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties. **Outputs** 20 watts R.M.S. into 8 ohms (suitable for 15 ohms). **Inputs** \*4 electrically mixed inputs. \*3 individual mixing controls.

\*Separate bass and treble controls common to all 4 inputs. \*Mixer employing F.E.T. (Field Effect Transistors) \*Solid State circuitry. \*Attractive styling.

**INPUT SENSITIVITIES** —Input — 1.) Crystal mic. guitar or moving coil mic, 2 and 10mV. (Selector switch for desired sensitivity).

—Inputs — 2), 3), 4). Medium output equipment — ceramic cartridge, tuner, tape recorder, organs, etc. — all 250mV sensitivity. AC Mains, 240V operation. Size approx: 12 1/2" x 6" x 3 1/2" **£17.00 — £1.15. p & p**

## PORTABLE DISCO CONSOLE\*

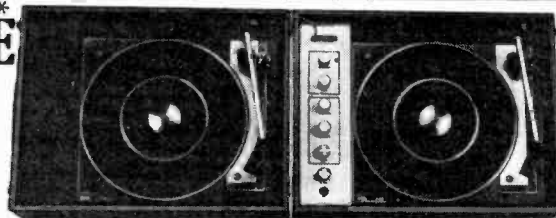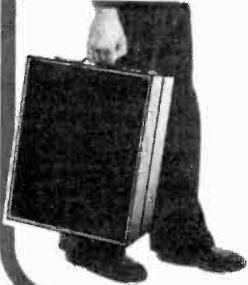

**INCORPORATES:** Pre-Amp with full mixing facilities, including switched input for mic with volume control, switched input for auxiliary with volume control, bass and treble controls, volume control and blend control for turntables.

Two B.S.R. single play professional series decks, fitted with crystal cartridges.

The turntables are designed and precision engineered. They combine clean modern styling with superb reproduction. Their many special features include square section aluminium tonearms, (high precision low mass design fully counterbalanced, with calibrated stylus pressure control for perfect tracking), and conveniently grouped easy to read linear controls. The turntables have viscous cueing devices which allows the tonearms to be placed or lifted at any point on the record.

The two lightweight cartridge shells have slide-in-holders to facilitate easy inspection of needles and cartridges.

### TECHNICAL SPECIFICATION:

**Pre-amp** — Output — 200mV.

Auxiliary inputs — 200mV and 750mV into 1 meg.

Mic input — 6mV into 100K. 240 volt operation.

**Turntables capacity** — 7", 10" or 12" records.

**Rumble, wow and flutter** —

Rumble Better than —35dB. Wow Better than 0.2%.

Flutter Better than 0.06% (Gauomont kaleo meter).

**Finish** — Satin black mainplate with black turntable mat inlaid with brushed aluminium trim. Tonearm and controls in black and brushed aluminium.

**Console size** —

Unit Closed — 17 1/2" x 13 1/2" x 8 1/2" (approx.)

Unit Open — 35 1/2" x 13 1/2" x 4 1/2" (approx.)

This disco console is ideally matched for the Reliant IV and Disco 50 or any other quality amplifier.

The unit is finished in black PVC with contrasting simulated teak edging diamond spun control knobs with matching control panel.

**Yours for only £45.00 + £5.60 p & p.**



**DO NOT SEND CARD**

Just write your order giving your credit card number

Mail orders to Acton. Terms C.W.O. All enquiries stamped addressed envelope. Goods not despatched outside U.K. Leaflets available for all items listed thus \* send stamped addressed envelope. All items subject to availability. Prices correct at 1st Feb. 1975 and subject to change without notice. All prices include V.A.T. at 8% rate.

**Personal Shoppers Edgware Rd 9a.m.-5.30p.m. Half day Thurs. Acton 9.30a.m.-5.30p.m. Closed Wed.**



Radio and TV  
Components  
(Acton) Ltd.

21c High Street, Acton, London W3 6NG  
323 Edgware Road, London W2


# How to order the cassette unit for your Kempton or Ascot player.

As a reader of Practical Wireless, you can get the cassette mechanism for your car stereo player direct from Goldring.

The units for both the PW Kempton and Ascot are made by Lenco and based on the famous STAAR design, with wow and flutter reduced to 0.3% max.


All you have to do is send the coupon to us, with a cheque or PO made out to Goldring Ltd. Be sure to state which unit you need. For the Kempton, it's Lenco FFR at £18.90; for the Ascot, it's Lenco CRV at £19.98. Prices include packing, carriage and VAT.

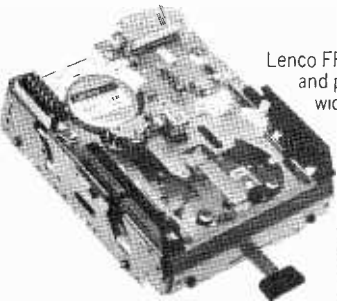The units are also available from selected distributors.



Lenco FFR for the Kempton. Robust and precision engineered, it's widely used in industry and by Europe's largest car stereo manufacturer.

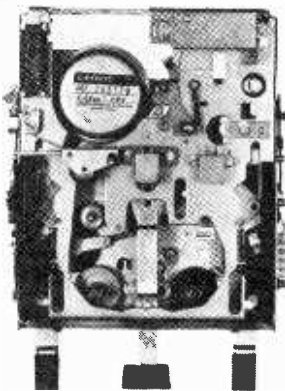Lenco CRV for the Ascot A record/replay unit made to hi-fi standards. Features of the Ascot Player include dynamic noise reduction, auto-stop and cassette ejection at end of play



## "I MADE IT MYSELF"

*Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.*

## Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn—and pave the way to a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio . . . a Burglar Alarm. You learn Radio and Electronics by doing actual projects you enjoy—making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

**No soldering—yet you learn faster than you ever dreamed possible.**

Yes! Faster than you can imagine, you pick up the technical know how you need. Specially prepared step-by-step lessons show you how to: read circuits—assemble components—build things—experiment. You enjoy every minute of it!

You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course. **AT NO EXTRA CHARGE!** And this is a course anyone can afford. (You can even pay for it by easy instalments).

**So fast, so easy, this personalised course will teach you even if you don't know a thing today!**

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics.

You become a man who makes things, not just another of the millions, who don't understand. And you could pave the way to a great new career, to add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own transistor radio. And after the course you can go on to acquire highpowered technical qualifications, because our famous courses go right up to City & Guilds levels.

**Send now for FREE 76 page book—see how easy it is—read what others say!**

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

To: Goldring Ltd, 10 Bayford Street, Hackney, London E8 3SE.

Please send me: Lenco FFR at £18.90

Lenco CRV at £19.98

I enclose PO, cheque for £ \_\_\_\_\_

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

**Goldring**

**POST TODAY FOR FREE BOOK**

To: ALDERMASTON COLLEGE  
DEPT. CPW04  
READING RG7 4PF

CPW04

Yes, I'd like to know more about your course. Please send me free details—plus your big, 76-page book that tells about all your courses.

Name \_\_\_\_\_

Address \_\_\_\_\_


POST CODE \_\_\_\_\_

**BIET**

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

# CHROMASONIC electronics

Dept 1 56, Fortis Green Road,  
Muswell Hill, London, N10 3HN.  
telephone: 01-883 3705

RECTIFIERS				BRIDGES			TRIACS		SOLDERING		
V	1A	3A	6A	V	1A	2A	6A	4A	Soldering		
50	IN4001	6p	IN5400	15p				25v	2N6068	52p	 <p>Desolder Braid Reel 64p</p> <p>Multicore 18 swg size 5 32p 22 swg size 15 36p carton size 1 50p " " 12E1.57</p> <p>Aiccala Invader 1.66 1.1 x 0.1 x 0.1 bit £2.80 1.66 23 watt 3/16" bit £3.13</p>
100	IN4002	7p	IN5401	16p				50v	2N6069	52p	
200	IN4003	9p	IN5402	17p	BYX61	50	£3.21	100v	2N6070	56p	
400	IN4004	9p	IN5404	22p	BYX61	100	£3.48	200v	2N6071	43p	
600	IN4005	11p	IN5406	26p	BYX61	200	£3.76	400v	2N6073	68p	
800	IN4006	13p	IN5407	28p	BYX62	400	£4.29	600v	2N6075	£1.49	
1000	IN4007	16p	IN5408	31p	BYX62	600	£4.29	1000v			

DIN CONNECTORS				HEAT SINKS	
Pins	Plugs	Sockets	Line Couplers	Transistor covers	
2	9p	7p	11p	TO 3	TO 3 (TO 3)
3	10p	7p	11p	TO 66	TO 66 (TO 66)
4	11p	7p	11p		
5 (180)	11p	8p	11p		
5 (240)	11p	8p	11p		
6	11p	9p	11p		
7	13p	9p	11p		

CO-AXIAL		I.C. SOCKETS	
Plugs	Sockets		
Plastic Moulded	7p	U1(TBAE10)	16p
Chrome Screened	12p	U1(TBAE10S)	16p
Coupler	15p	U2(TBAE10AS)	16p
		U2(TCA540)	16p
		U3(TDA1020)	35p

## AUDIO I.C.'S

A brand New Audio I.C. Leaflet with Circuits and pin connections for ALL the I.C.'s listed below FREE with orders over £1.00 or 10p without

POWER OUTPUT Watts	Supply Volts	Load Ohms	Style	Power I.C.	Amplifiers	Price	Pre-Amplifiers	Supply Volts	Style
0.25	9	16	C	MFC4000R	78p	Dual Low Noise	+24 A	LM381	£2.16
0.5	9	8	E	MC1306P	68p	Dual Low Noise	-14 A	LM382	£2.19
1	9	8	F	TAA300	£1.76	Dual Pre-Amp	+10 A	MC1303L	£1.59
2	12	8	G	TBA820	74p	Dual Low Noise	-12 A	MC1339P	£1.31
2	18	8	A	LM380	£1.08	Dual Low Noise	+15 U	TSA231	88p
2 1/2 + 2 1/2	18	8	A	LM377	£2.91	General			
3	18	8	J	SL434	£1.72	D.C. Controlled attenuator		MFC6040	83p
5	24	16	J	SL415	£2.24	3 stage G.P. amp.		TAA263	80p
5	24	8	H	TBA800	96p	Tape Pre-Amp		TAA310	£1.34
7	16	4	H	TBA810S	£1.07	Bi-Fet		TAA320	97p
7	16	4	K	TBA810AS	£1.07	Hear/Aid Amp 1.3v		TAA370	£5.05
10	20	4	M	TCA940	£1.94	PPL stereo decoder(i)		MC1310	£2.14
15	30	3	O	BHA0002	£2.60	4 channel SQ (ii)		MC1312	£2.42
35 driver	25	8	F	NE540L	£1.08	4 pre-amp (iii)		MC1314	£4.05
20	+15	4	N	TDA2020	TBA	CBS SQ Logic (ii)		MC1315	£5.37

SWITCHES		MAINS TRANSFORMERS	
High Quality	Rotary	Primary	Secondary
250v 1A	2A Mains	6-0-6v, 100mA 97p	20-0-20v 1A £4.55
S.P.S.T. 25p	Switches	9-0-9v, 100mA 97p	24-0-24v 3A £2.48
D.P.D.T. 45p		12-0-12v, 100mA 97p	28-0-28 1A £6.18
	Bulgin	18-0-18v, 200mA plus	0-24v 40mA 97p
	push-to-make		
	25p		
	Erg Dil Switches		
	1 pole 8 way 99p		
	2 pole 4 way 85p		
	4 pole 2 way £1.24		
	Latin water switches 27p		
	1 pole 12 way, 4 pole 2 way		
	3 pole 4 way, 4 pole 3 way		

## VAT INCLUSIVE PRICES AT 8%

OVERSEAS CUSTOMERS DEDUCT 27% VAT INVOICES ON REQUEST P&P On UK Orders 15p Overseas Orders at Cost



ERSIN

**Multicore**

5 CORE SOLDER

**for fast easy reliable soldering**  
**EASY TO USE DISPENSERS AND REELS**  
**IDEAL FOR HOME CONSTRUCTORS**

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

**SAVBIT** handy solder dispenser



A coil of Ersin Multicore Savbit Solder in a dispenser 7 1/2 in of 18 s.w.g. (2.2 metres of 1.22mm). The Solder that reduces the wear of soldering iron bits.

Size 5 32p

**SAVBIT** solder for general purpose work

A handy plastic reel of SAVBIT alloy. 63ft of 18 s.w.g. (19.2 metres of 1.22mm)

Size 12 £1.72



**ALU-SOL** for soldering aluminium

New Multicore Alu-sol flux-cored solder in 16 s.w.g. No extra flux needed. Plastic reel holds 36ft. Supplied with full instructions. Also available in solder dispenser.

Size 4 £2.32



**Fine gauge solder** for soldering small components

Fine gauge solder for soldering small components 138ft of 22 s.w.g. (42.0 metres of 0.71mm) Ersin Multicore 5 core solder wound on a plastic reel. Suitable for intricate work and small components.

Size 10 £1.44



**For soldering fine joints**



Dispensers of Ersin Multicore Solder make those small jobs easier. 21ft of 22 s.w.g. (6.4 metres of 0.71mm) solder, specially suitable for soldering fine wires, small components and for repairing printed circuits.

Size 15 36p

Or size 19A for kit wiring or Radio and T.V. repairs 7ft. (2.1 metres) of 18 s.w.g. (1.22mm) Ersin Multicore Solder.

Size 19A 34p

**NEW BIB WIRE STRIPPER & CUTTER**



Fitted with unique 8 gauge selector with handle locking device and easy grip handles. Spring incorporated for automatic opening. Strips insulation from flex and cables in seconds and can also be used as a cutter.

Model 8B-80p

**NEW SOLDER WICK**



Absorbs solder instantly, from tags and printed circuits. Only needs 40 to 50 Watt soldering iron. Quick and easy to use. Does not need flux and is non-corrosive.

Size 18 90p

**Bib Hi-Fi Accessories Limited,**

Sole U.K. Sales Concessionaires, P.O. Box 78 Hemel Hempstead, Herts. HP2 7EP

Prices shown are recommended retail excluding V.A.T. From Electrical and Hardware Shops. If obtainable, send 15p P&P. Prices and specifications subject to change without notice.

**MAINS UNITS for all types of TRANSISTOR EQUIPMENT**

**RUN YOUR TRANSISTOR RADIO OR CASSETTE RECORDER FROM YOUR CAR BATTERY** (Similar to illustration)

This unit enables you to run your cassette tape recorder from the car whilst travelling. It is easily fitted and comes complete with fitting instructions. Please state make of cassette, voltage and type of plug required.



ONLY £2.86

**RUN YOUR TAPE RECORDER OFF AC MAINS**

Mains unit supplied complete and ready to plug into your cassette recorder. (State voltage, make and type of plug required, if in doubt send diagram of recorder socket.)



ONLY £3.40



**RUN YOUR TRANSISTOR RADIO OFF AC MAINS**

For single outputs, 6v, 9v £2.86


For two separate outputs, 6v + 6v, 9v + 9v £3.52 per unit. (Please state outputs required.)

All units are completely isolated from mains by double wound transformer ensuring 100% safety. All British Made. All Prices inc. V.A.T. and P. & P. R.C.S. PRODUCTS (RADIO) LTD. (Dept. PWA)

31 Oliver Road, Walthamstow, London, E17

Full refund if not completely satisfied.

**verobox**

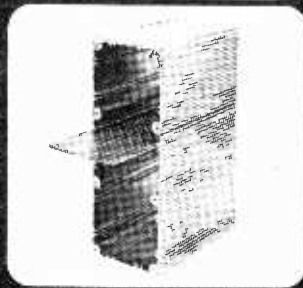

**ALUMINIUM ENCLOSURES**

- 6 standard sizes available from your local retailer.
- Made from precision extrusions with integral board guide slots.
- Finned sides improve appearance and radiate heat.
- Parallel sides for ease of component mounting.



**VERO ELECTRONICS LTD.**


Eastleigh, Hants. SO5 3ZR  
 Tel: Chandler's Ford 2952 Telex: 47551

Subsidiaries and Agents throughout the World

NEW IMPROVED

**MAINS INTERCOM**

NO BATTERIES  
 NO WIRES

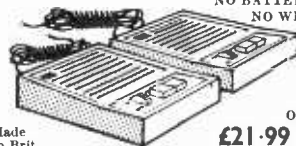

Made to Brit. Safety &

ONLY £21.99 per pair + VAT £1.76

Telecom. Standards, Supplied with 3-core wire. Just plug into power socket. Ready for use. Crystal-clear communication from room to room. Operates over a 3-mile range. On/Off switch, Vol. control. Useful as office intercom, baby alarm, invalids. No G.P.O. licence reqd. Full price ref. if returned in 10 days. 12 months service guarantee. P. & P. 60p.

**NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER**



ONLY £11.95 + VAT 96p

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/Off switch, volume. Direct tape recording model at £12.95 + VAT £1.04 P. & P. 48p. 10-day price refund guarantee.

WEST LONDON DIRECT SUPPLIES (PW11)  
 169 KENSINGTON HIGH STREET, LONDON, W.8

# ELECTROVALUE

Present

a price-stabilizing policy for 1975

new revised catalogue · attractive discounts · free postage & packing (U.K.)

## A 100 OF THE BEST out of our latest catalogue

2N1307	47p	AF200U	70p	BD135	37p
2N2646	51p	AF239	60p	BD136	30p
2N3053	30p	B1906	35p	BDY20	83p
2N3054	60p	BA138	31p	BF154	15p
2N3055	70p	BB103	24p	BFR39	23p
2N3702	11p	BB105	34p	BFR79	23p
2N3703	10p	BB109	18p	BFX29	33p
2N3704	11p	BC10/A	16p	BFX84	27p
2N3705	10p	BC107B	16p	BFY51	23p
2N3794	18p	BC108B	15p	BRY39	50p
2N3619	23p	BC108C	15p	BY154	51p
2N4062	11p	BC109B	18p	C106B1	42p
2N4443	93p	BC109C	18p	C106D1	47p
2N5052	42p	BC147A	12p	C1406	78p
2N5163	20p	BC147B	13p	MJ481	£1 28
2N5459	32p	BC148B	12p	MJ491	£1 35
40361	48p	BC149C	14p	MJ2955	80p
40362	44p	BC158B	15p	MJ371	89p
40602	46p	BC159	15p	MJ521	81p
40636	£1 36	BC167B	13p	MJ5255	£1 12
40689	£1 10	BC168B	12p	MJ5355	68p
AC128	17p	BC169B	12p	OA91	6p
AC151R	35p	BC169C	13p	SD4	8p
AC153	27p	BC179B	28p	TIP31A	70p
AC153K	37p	BC182L	12p	TIP32A	80p
AC176	24p	BC184L	10p	TIP41A	80p
AC176K	38p	BC212L	12p	TIP42A	£1 00
AC187K	31p	BC214L	14p	W02	30p
AC188K	29p	BC257A	14p	ZTX300	14p
AD133	£1 92	BC259B	14p	ZTX304	23p
AD136	£1 11	BCY58	30p	ZTX500	14p
AD149SL	65p	BD130	70p	ZTX504	45p
AD161	42p	BD131	43p		
AD162	40p	BD132	52p		

## ELECTROLYTIC CAPACITORS

Axial Lead	3V	6-3V	10V	16V	25V	40V	63V	100V
qf								
0-47	—	—	—	—	—	11p	11p	3p
1-0	—	—	—	—	11p	—	—	8p
2-2	—	—	—	—	—	—	—	8p
4-7	—	—	—	11p	—	—	—	8p
10	—	11	—	—	8p	8p	8p	8p
22	—	—	8p	—	8p	8p	8p	10p
47	8p	—	8p	8p	8p	8p	10p	13p
100	9p	8p	8p	8p	8p	10p	12p	15p
220	8p	8p	10p	10p	11p	17p	23p	—
470	8p	10p	10p	11p	13p	17p	24p	45p
1,000	11p	13p	13p	17p	20p	25p	41p	—
2,200	15p	—	—	26p	37p	41p	—	—
4,700	—	—	39p	44p	58p	—	—	—
10,000	42p	46p	—	—	—	—	—	—

## RESISTORS

Code	Watts	Ohms	1 to 9	10 to 99	100 up
C	1/3	4.7-470K	1-3	1-1	0-9 nett
C	1/2	4.7-10M	1-3	1-1	0-9 nett
C	3/4	4.7-10M	1-5	1-2	0-87 nett
C	1	4.7-10M	3-2	2-5	1-92 nett
MO	1/2	10-1M	4	3-3	2-3 nett
WW	1	0-22-0-47 16	14	11	nett
WW	1	0-56-3-9 Ω	12	10	nett
WW	3	1-10K	9	8	nett
WW	7	1-10K	11	10	nett

**Codes:**  
 C = carbon film, high stability, low noise.  
 MO = metal oxide. Electrofil TR5 ultra low noise.  
 WW = wire wound, Plessey.  
**Values:** All E12 except C 1/3, C 1/2 and MO 1/2.  
 E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82, and their decades.  
 E24: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.  
**Tolerances:**  
 5% except WW 10% = 0.05 Ω below 10 Ω and 1/2 W MO 2%  
**Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order.) Prices for 100 up in units of 100 only.**

1975 is the year of challenge. Rather than sit back and wait for things to happen, we have produced our own policy to help stabilize price structure and maintain the services for which ELECTROVALUE are pre-eminent.

**PRICES**  
 as shown in our latest catalogue (No. 7, issue 3) will be maintained at least until March 31st next (except in cases of severe market fluctuation) and then held after review for further three-month periods instead of making day to day price change.

**CATALOGUE 7 ISSUE 3**  
 is now ready with 108 pages of bargains and information. Price—30p post paid including 25p refund voucher for use on orders list value for £5 or more

**DISCOUNTS**  
 apply on all items except the few where prices are shown NETT. 5% on orders from £5 to £14.99; 10% on orders value £15 or more.

**FREE POSTAGE & PACKING**  
 in U.K. for pre-paid mail orders over £2 (except Baxandall cabinets). If under, there is an additional handling charge of 10p.

**QUALITY GUARANTEE**  
 All goods are sold on the understanding that they conform to makers specifications. No rejects, seconds or sub-standard merchandise.

**V.A.T. @ 8% must be added to total value of orders. Every effort is made to ensure correctness of information at time of preparing and putting this advertisement to press.**

## WAYCHANGE SWITCHES

1 pole 12 way; 2 pole 6 way; 3 pole 4 way; 4 pole 3 way each 33p  
 TAG STRIP 28 way 11p

## NUTS, SCREWS, etc.

In lots of 100 each  
 4BA NUTS 31p; 6BA NUTS 28p  
 1" 4B Screws 30p; 1" 6BA Screws 24p  
 Threaded pillars 6BA, 1" hexagonal £1-35  
 Plain spacers 1" round £1-32  
 Other sizes available

## CAPACITORS

**DALY ELECTROLYTIC** in cans, plastic sleeved  
 1000mF/25V 34p; 2200/100 £1-91  
 5000/100 £3 56; 1000/50 50p  
 5000/25V 75p; 2000/50 70p  
 2000/50 70p; 5000/50 £1-44  
 1000/100 £1-00

**POLYESTER TYPE C.280**, Radial leads for P.C.B. mounting. Working voltage 250V d.c.  
 0-01; 0-015; 0-022; 0-033; 0-047 ea. 3p  
 0-068; 0-1; 0-15 ea. 4p  
 0-22 5p; 0-33 7p; 0-47 8p; 0-68 11p; 1-0 14p; 1-5 21p; 2-2 24p

**SILVERED MICA**. Working voltage 500V d.c. Tolerance 1% or 0.5p  
 Values in PPs—2.2 to 250 in 26, stages ea. 6p  
 270-320 in 9 stages, ea. 7p  
 1000, 1500, 1800 9p; 2200 10p; 2700, 3600, 4700, 5000 10p; 6800, 8200, 10,000 25p

**TANTALUM BEAD**  
 0-1, 0-22, 0-47, 1-0 mF/35V, 1-5/20V, 3-5/16V ea. 16p  
 2-2/16V, 2-2/35V, 4-7/16V, 10-6-3V ea. 15p  
 4-7/35V, 10/16V, 22/6-3V ea. 21p  
 10/25V, 22/16V, 27/6-3V, 100/3V, 6-8/25V, 15/25V ea. 23p

**POLYCARBONATE**  
 Type B42540 Working Voltage—250V Values in mF:  
 0-0047; 0-0068; 0-01; 0-15; 0-22 ea. 4p  
 0-018; 0-027; 0-033; 0-039; 0-047; 0-068; 0-082; 0-1; 100V/0.1 ea. 5p  
 0-18; 0-22 7p; 0-27 8p; 0-33 9p; 0-39, 0-47 11p; 0-56, 0-68 16p

**CERAMIC PLATE**  
 Working voltage 50V d.c.  
 In 26 values from 22pf to 6800pF ea. 2p

**POTENTIOMETERS**  
**ROTARY, CARBON TRACK.**  
 Double wipers for good contact and long working life  
 P.20 SINGLE linear 100 ohms to 4.7 meg ohms, each 14p  
 P.20 SINGLE log. 4-7 Kohms to 2.2 megohms, each 14p  
 J.P.20 DUAL GANG 1in. 4-7 Kohms to 2.2 megohms, each 48p  
 J.P.20 DUAL GANG log. 4-7 Kohms to 2.2 megohms, each 48p  
 J.P.20 DUAL GANG Log/antilog 10K, 22K, 47K, 1 megohm only, each 48p  
 J.P.20 DUAL GANG antilog 10K only 48p  
 2A DP mains switch for any of above 14p extra.  
 Decades of 10, 22 and 47 only available in ranges above.  
 Skeleton Carbon Presets, Type PR, horizontal or vertical 6p each.

**SLIDER**  
 Linear or log mono 4-7K to 1 meg. in all popular values each 30p  
 STEREO, matched tracks, lin. or log in all popular values from 4-7K to 1 meg. each 60p  
 Escutcheon plates, mono, black or grey, each 10p  
 Control knobs, blk/wht/red/yel/grn/blue/dk. grey/lt. grey, each 7p

**MINITRON DIGITAL INDICATORS**  
 3015F Seven segment filament compatible with standard logic modules; 0-9 and decimal point; 9mm characters in 16 lead DIL £1 26  
 Sullite BCD decoder driver 7447 £1-15  
 3015G showing + or — & 1 & dec. pt. £1-20  
**LEDS** (Light Emitting Diodes) 25p  
 Photo Cells, cadmium sulphide each 40p

**ANTEX Soldering Irons**  
 C240 £2-25 Spare bits 32p  
 CCN240 £2-65 Spare bits 42p

# ELECTROVALUE LTD

28, ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB  
 Telephone Egham 3603 Telex 264475 Shop hours 9-5.30 daily: Sat. 9-1 p.m.  
**NORTHERN BRANCH:** 680, Burnage Lane, Burnage, Manchester M19 1NA  
 Telephone (061) 432 4945 Shop hours 9-5.30 daily: Sat. 9-1 p.m.  
**U.S.A. CUSTOMERS** are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore PA 19081.

All postal communications, mail orders etc. to Head Office at Egham address, Dept. PW 4, S.A.E. with enquiries requiring answers.

# TRANSFORMERS

## SAFETY MAINS ISOLATING TRANSFORMERS Prr. 120/240 V Sec. 120/240 V Centre Tapped and Screened

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	P & P £ p
07	20	1 8	7.0 x 6.0 x 6.0	2.80 38
149	60	3 4	9.9 x 7.7 x 8.6	4.37 45
150	100	5 0	9.9 x 8.9 x 8.6	4.89 45
151	200	8 0	12.1 x 9.3 x 10.2	8.13 53
152	250	13 12	12.1 x 11.8 x 10.2	9.83 73
153	350	15 0	14.0 x 10.8 x 11.8	11.88 73
154	500	19 8	14.0 x 13.4 x 11.8	13.65 91
155	750	29 0	17.2 x 14.0 x 14.0	20.51
156	1000	38 0	17.2 x 16.6 x 14.0	29.15
157	1500	46 0	21.6 x 13.4 x 18.1	33.23
158	2000	60 0	21.6 x 15.3 x 18.1	37.07

## AUTO TRANSFORMERS

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	P & P £ p
113	20	1 0	5.8 x 5.1 x 4.5	0-115-210-240	1.67 30
64	75	2 4	7.4 x 6.7 x 6.1	0-115-210-240	2.90 38
4	150	3 4	8.9 x 7.7 x 7.7	0-115-200-220-240	4.12 45
66	300	6 4	9.9 x 9.6 x 8.6	"	5.82 53
67	500	12 8	12.1 x 11.2 x 10.2	"	8.82 67
84	1000	19 8	14.0 x 13.4 x 14.3	"	13.68 91
93	1500	30 4	14.0 x 15.9 x 14.3	"	18.31
95	2000	32 0	17.2 x 16.6 x 14.0	"	24.20
73	3000	40 0	21.6 x 13.4 x 18.1	"	35.09

## CASED AUTO TRANSFORMERS

115V mains lead input and U.S.A. 2-pin outlets. 20VA £3.23 pp 38p  
500VA £10.45 pp 80p 1000VA £17.51 via B.R.S.

## TRANSFORMERS

Ref. No.	12V 24V	Amps.	Weight lb oz	Size cm.	Secondary Windings	P & P £ p
111	0.5	0.25	1 8	4.8 x 2.9 x 3.5	0-12V at 0.25A x 2	1.47 23
213	1.0	0.5	1 4	6.1 x 5.8 x 4.8	0-12V at 0.5A x 2	1.74 30
71	2	1	1 12	7.0 x 6.4 x 6.1	0-12V at 1A x 2	2.29 38
18	4	2	2 12	8.3 x 7.7 x 7.0	0-12V at 2A x 2	2.86 38
70	6	3	3 8	8.9 x 8.0 x 7.7	0-12V at 3A x 2	4.12 45
108	8	4	5 8	9.9 x 8.9 x 8.6	0-12V at 4A x 2	4.56 45
72	10	5	6 4	9.9 x 9.6 x 8.6	0-12V at 5A x 2	5.14 53
116	12	6	6 12	9.9 x 10.2 x 8.6	0-12V at 5A x 2	5.52 53
17	16	8	8 12	12.1 x 9.9 x 10.2	0-12V at 8A x 2	7.28 60
115	20	10	11 8	14.0 x 9.6 x 11.8	0-12V at 10A x 2	10.39 73
187	30	15	15 8	14.0 x 12.1 x 14.0	0-12V at 15A x 2	13.59 85
226	60	30	32 0	17.2 x 15.3 x 14.0	0-12V at 30A x 2	16.83

## 30 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
112	0.5	1 4	6.1 x 5.8 x 4.8	0-12-15-20-24-30V	1.81 30
79	1.0	2 4	7.0 x 6.7 x 6.1	"	2.40 38
3	2.0	3 4	8.9 x 7.7 x 7.7	"	3.49 38
20	3.0	4 8	9.9 x 8.3 x 8.6	"	4.53 45
21	4.0	6 4	9.9 x 9.6 x 8.6	"	5.14 53
51	5.0	6 12	12.1 x 8.6 x 10.2	"	6.41 53
117	6.0	8 0	12.1 x 9.3 x 10.2	"	7.16 60
88	8.0	12 0	12.1 x 11.8 x 10.2	"	9.90 67
89	10.0	13 12	14.0 x 10.2 x 11.8	"	9.87 73

## 50 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
102	0.5	1 12	7.0 x 6.4 x 6.1	0-19-25-33-40-50V	2.58 30
103	1.0	2 12	8.3 x 7.4 x 7.0	"	3.38 38
104	2.0	5 8	9.9 x 8.9 x 8.6	"	4.68 45
105	3.0	6 12	9.9 x 10.2 x 8.6	"	5.81 53
106	4.0	10 0	12.1 x 10.5 x 10.2	"	7.60 67
107	6.0	12 0	14.0 x 10.2 x 11.8	"	12.09 85
118	8.0	18 0	14.0 x 12.7 x 11.8	"	12.98 87
119	10.0	25 0	17.2 x 12.7 x 14.0	"	16.99

## 60 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
124	0.5	2 4	7.0 x 6.7 x 6.1	0-24-30-40-48-60	2.33 38
126	1.0	3 4	8.9 x 7.7 x 7.7	"	3.41 38
127	2.0	6 4	9.9 x 9.6 x 8.6	"	5.08 45
125	3.0	8 12	12.1 x 9.9 x 10.2	"	7.52 60
123	4.0	13 12	12.1 x 11.8 x 10.2	"	8.75 67
40	5.0	12 0	14.0 x 10.2 x 11.8	"	9.75 73
120	6.0	15 8	14.0 x 12.1 x 11.8	"	11.30 85
121	8.0	25 0	14.0 x 14.7 x 11.8	"	15.00
122	10.0	25 0	17.2 x 12.7 x 14.0	"	17.52
189	12.0	29 0	17.2 x 14.0 x 14.0	"	19.98

## MINIATURE TRANSFORMERS WITH SCREENS P & P

Ref. No.	VA	Weight lb oz	Size cm.	VOLTS	P & P £ p
238	20A	1 2	2.8x2.6x2.0	3-0-3	1.54 10
212	1A 1A	1 4	6.1x5.8x4.8	0-6-0-6	1.84 30
13	100	4 4	3.9x2.6x2.9	9-0-9	1.41 13
235	330,330	4 4	4.8x2.9x3.5	0-9-0-9	1.56 19
207	500, 500	1 00	6.1x5.4x4.8	0-8-9-0-8-9	1.92 30
208	1A, 1A	1 12	7.0x6.4x6.1	0-8-9-0-8-9	3.30 38
236	300, 200	4 4	4.8x2.9x3.5	0-15-0-15	1.43 19
214	300, 300	1 4	6.1x5.8x4.8	0-20-0-20	1.93 30
221	700 (D.C.)	1 8	7.0x6.1x6.1	20-12.0-12.20	2.17 38
206	1A, 1A	2 12	8.3x7.7x7.0	0-15-20-0-15-20	3.46 38
203	500, 500	2 4	8.3x7.0x7.0	0-15-27-0-15-27	3.00 38
204	1A, 1A	3 4	8.9x7.7x7.7	0-15-27-0-15-27	3.85 38

\* Carriage via BRS

PLEASE ADD 8% FOR V.A.T.  
INCLUDING P. & P.

# BARRIE electronics

3, THE MINORIES, LONDON EC3N 1BJ

TELEPHONE: 01-488 3316/8

NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST.

# Loudspeakers at Manufacturers Prices

## £15.50 per pair

— as supplied by us to the trade  
— less than half retail price.  
Cabinets in teak size 18" x 11" x 7" deep 15 watts  
RMS (30 watts music power) output into 8 ohms.


GOODMANS/EMI

6½" bass plus 3½" tweeter. Frequency response 35 Hz. to 19,000 Hz. Leads connectors supplied — acoustically damped speakers.


HI FIDELITY  
QUALITY AT ONLY  
£15.50 per pair plus  
£1.00 post, packing and insurance.

Please send cash, cheque or Access order to Ben Ford (Hi Fi Cabinets) Limited, 58 Somers Road Industrial Estate, Rugby, Warwickshire. Telephone 78213.

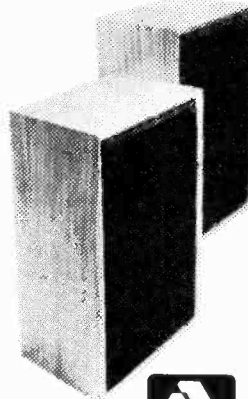For Access orders just quote Access number and address. Immediate despatch for all orders.



# CARBON SLIDE POTENTIOMETERS

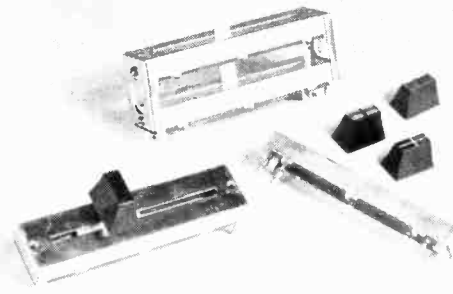

60mm Single Track including Black Knob 50p (inc. V.A.T.), 60mm Twin Track including Black Knob 60p (inc. V.A.T.), 60mm Quad Slide Potentiometers— Prices upon application. 1K, 5K, 10K, 25K, 50K, 100K, 500K ohms Log, Lin, Antilog. Metal Case. 3-2db Matched Track. 15mV Nominal Noise (B.S. 2122). Life Exceeds 20,000 cycles. Fixing Holes 2 x M3 on 80mm Centres.

Designed, Manufactured and Supplied by:—

# RIVLIN INSTRUMENTS LTD

DOMAN ROAD, CAMBERLEY, SURREY GU15 3DJ

Send cash with order to above address. Postage and packing 15p per order. Trade enquiries invited.

**no extras**  
all prices inc VAT  
FREE delivery



ALL ITEMS SUBJECT TO  
MANUFACTURERS INCREASE  
AND AVAILABILITY  
**Personal  
Callers are  
Welcome!**



**High Quality  
Construction  
Kits, stocked  
at all branches  
Send for  
catalogue!**

**AMPLIFIERS**

Rotel RA211	£43.95
RA311	£54.95
RA611	£86.95
Sansui AU101	£48.25
AU505	£74.95
Sinclair 2000	£34.95
Linton Mk. II	£59.95

Adastra 'Top 20' 12in 25 watt 8 or 15 ohm	£8.25
Adastra 'Hi-Ten' 10in 10 watt 8 or 15 ohm	£3.70
Also 5in 8 ohm speaker	£0.95
2 1/2in 8 or 64 ohm speaker	60p

G800	3.95	1.95
G800H	3.95	1.95
G800E	6.99	3.95
SHURE		
M44G	4.95	3.95
M55E	6.25	4.95
M75ED Type 2	11.75	8.25
MJ5EJ Type 2	9.75	6.25
VI5 Type 3	32.25	—

**CALCULATORS**

Sinclair Cambridge Build	£12.95
Scientific	£19.95

**TUNERS & RECEIVERS**

Leak Delta AM/FM	£69.95
Sinclair 2000/4000 Tuner	£34.95
Rotel RT222	£42.75
Pioneer SX434	£99.00
Rotel RX150A Tuner/ Amp.	£59.95
Rotel 152	£69.95
Sansui	
210 AM/FM/MPX	£75.50
310 AM/FM/MPX	£99.50
441 AM/FM/MPX	£91.95
Howland West DA 1000T AM/FM	£36.00

**WHARFEDALE SPEAKER  
BARGAINS**

Denton 1 pr.	£26.75
Denton 2 pr.	£32.00
Linton 2 pr.	£40.75
Glendale 3 pr.	£64.95
Kingsdale 3 ea.	£64.95
Dovedale 3 ea.	£44.95

**KITS**

Linton 2 pr.	£20.95
Glendale 3 pr.	£35.95
Dovedale	£55.50

**MICROPHONES**

UDI130 50K/600 ohm uni-dir. ball metal	£6.75
UDI47	£9.25
Condenser Mic. 600 ohm uni-dir	£9.50
Cassette Strick Mic. with R/Control	£1.60
Cass. Stiek Mic. with R. control (Philips type)	£2.00
Mic-Mixers Mono/stereo	£5.50
Akai ADM20	£7.50

**SINCLAIR PROJECT 80**

Stereo Pre-amp.	£12.95
Active Filter Unit	£7.25
Z40 15 watt Amp	£5.75
Z60 25 watt Amp	£7.25
P25 Power Supply for 240	£5.45
P26 Power Supply for 240	£8.45
P28 Power Supply for 260	£8.25
FM Tuner	£12.95
Stereo Decoder	£8.45
Q16 Speaker	£7.75
IC20 Stereo Amp. Kit	£7.45
PZ20 Power Kit	£5.25

**PORTABLE RADIOS**

Vega Jade	£5.75
Vega Zircon	£8.25
Vega Sapphire	£7.25
Vega VEF206	£13.95
Micado LM/MW/FM/SSW	£18.95
Murphy	
B833 MW/VHF	£9.95
BA838 LW/MW/VHF	
M/Batt	£18.50
MA5003 Head Set	
Radio LW	£7.95
Bush	
VTR165 LW/MW/VHF	£22.00
VTR127 LW/MW/VHF	£15.50
VTR 175 LW/MW/VHF	£13.95
VTR188 LW/MW/VHF/ 25W M/Batt	£31.95
BY5661 LW/MW/VHF	£14.95

**RECORD DECKS**

Garrard SP25 MkIV	£16.25
BSR MP60	£12.95
BSR Invicta P & C/SC7M	£9.95
Garrard	
SP25 MkIV P & C G/800	£25.95
Golding GL78 P & C/ G800E	£59.95
Rank Domus 13D 2000/ Rex 999 Cart.	£50.00
Connoisseur	
BDI Kit	£13.50
BD2 Chassis/SAU2	£32.50
SAU Arm	£14.25
SCUI Cartridge	£5.95
Pioneer PL12D	£43.50

**SPEAKER CABINETS IN  
KIT FORM (Teak Veneer)**

12in x 8in x 6in (8 x 5 or 7 x 4 cutout)	£2.90
14in x 12in x 9in (10", 6 x 5, 8", 6 1/2" & 3 1/2")	£3.95
18in x 11in x 9in (8" x 7" or 13 x 8)	£5.25
22in x 14in x 9in (12" & 7" or 13 x 8)	£6.75

**HEADPHONES**

RH430	£4.75
RH 630	£7.75
RH 700	£11.50
Koss	
K711	£11.50
KRO711	£10.95
K6	£13.00
K6LC	£14.95
KO727B	£16.75
KO747	£21.50
HV1	£21.95
PRO4AA	£29.25
PRO54	£29.95
K6LCQ	£26.00
Sansui SS10	£16.75

**CLOCK RADIOS**

Bush CR128 LW/MW	£13.60
Bush CR232 MW/VHF	£24.95
Murphy MV5600 MW/VHF	£22.95

**TAPE DECKS (Insurance 2.00)**

Akai	
4000DS Reel to Reel	£93.95
4000DB Reel to Reel	
Dolby	£149.50
GXC36D	£83.00
GXC38D	£103.95
CS33D	£79.95
Akai CR81D 8-track Rec. player	£73.95
GXC82D	£93.95

**TWEETERS & CROSSOVERS**

EMI 3 1/2" c/magnet in 3 or 8 ohm	£1.35
Cone Tweeter 10 watt 8 or 15 ohm (K2006)	£2.70
Cone Tweeter 3 watt 8 ohm (K2003)	£1.55
Horn Tweeter 8 ohm (K2007)	£6.50
Dome Tweeter 8 ohm (K2011)	£5.75
2-way Crossovers (CN23, CN28, CN216)	£1.40
3-way Crossover (CN38)	£2.85

\*Headphone adaptor  
(Junction box) £2.75  
extension lead 2ft curly £1.50

**CASSETTES**

C40	C60	C90	C120
Low Noise	—	35p	45p 55p
Philips	—	55p	75p 110p
Memorex	65p	79p	110p 155p
Amplex (360)	45p	55p	75p 99p
Amplex (20-20+)	59p	65p	99p 135p

**CARTRIDGES & STYLII**

ACOS			
GP91/2SC or 3CS (ster. comp)	1.10	1.25	
GP93/1 or 95/1 ster. cryst.	1.35	1.25	
GP94/1 or 96/1 ster. ceram.	1.75	1.25	
GP101 cryst. comp.	90	—	
GP104 ster. ceram.	1.75	1.25	
BSR			
X5M or X5H cryst. comp.	1.75	1.25	
SX6M or SX6H cryst. ster.	2.00	1.25	
SC5M ster. ceram.	2.75	1.25	
SONOTONE			
9TAHC or 9TAHC/G (Diam.)	1.85	1.25	
3509 Magnetic	1.90	1.25	
AUDIO TECNICA			
AT55	1.95	—	
EMPIRE 999 REX	3.95	—	
GOLDRING			
G850	2.95	1.95	

Chromium  
Dioxide — 99p 140p —  
Cassette Head Cleaner 45p  
Amplex Head Cleaner Demag £1.65  
BIB Stereo Test Cassette £2.15  
Cassette Racks (hold 6) £0.45  
Cassette Rotating Racks  
(hold 20) £3.50  
Cassette Carrying Case  
(hold 18) £1.95

**8-Track Cartridge Blanks**

C40	C64	C80
Amplex	80p	95p
8-track H/Cleaner Demagnetiser	£1.90	
8-track Carrying Cases (BIB)	£1.65	

Amplex (360) 45p 55p 75p 99p  
Amplex (20-20+) 59p 65p 99p 135p  
Chromium  
Dioxide — 99p 140p —  
Cassette Head Cleaner 45p  
Amplex Head Cleaner Demag £1.65  
BIB Stereo Test Cassette £2.15  
Cassette Racks (hold 6) £0.45  
Cassette Rotating Racks  
(hold 20) £3.50  
Cassette Carrying Case  
(hold 18) £1.95

**TAPES & CASSETTES**

Stnd	LP	DP	Cases
5"	55p	65p	1.00 20p
5 1/2"	65p	86p	1.35 25p
7"	80p	110p	1.85 30p
High frequency Amplex			
5"	—	1.40p	1.55p
7"	—	1.90p	2.95p
AKAI Metal Reel 7"			£1.99

**CASSETTE RECORDERS**

Murphy BA206	£16.95
Bush TP66 M/Batt	£25.75
Murphy BA200 M/Batt	£22.75
Bush BT8504 (miniature)	£25.50
Mains Battery Cass.	£15.50

**RADIO CASSETTES**

(Mains/Batt.)	
Murphy BA209 MW/VHF	£33.50

**STEREO RECORD PLAYER & SYSTEM**

Bush A1005	£56.50
Hanimex H101	£39.95
Hanimex HRC5060 8-track AM/FM/MPX + Speaker	£116.95

**CAR AUDIO**

Hitachi Car Radio WM702R LW/MW	£16.50
KM1510 LW/MW/VHF	£32.50
Hitachi Car Cassette CS114	£45.00
Hitachi AM/FM & Cassette CSW	£57.00
Battery Eliminators 240 in 6, 7.5 or 9 volt output	£2.95

ALL MERCHANDISE FULLY GUARANTEED

**NEWMART  
ELECTRONICS**

**Mail Order Dept** PW4  
**Belmont St, Monton,  
Eccles, Manchester.**  
**Tel: 061-789 5268**

**Manchester**  
30-32 Shudehill. tel 061-832 7710  
**Leeds**  
4 New Market St tel 0532 42708  
**Liverpool**  
15 Whitechapel tel 051-236 0738





# TRAMPUS

**Electronics Ltd.**  
WINDSOR, BERKS  
58/60 GROVE RD:  
SEND C.W.O. ADD VAT TO ALL PRICES IN U.K. P&P 15p. EXPORTS 60p.

MONEY BACK IF NOT SATISFIED.  
LARGE STOCKS. LOW PRICES.  
ALL BRAND NEW TOP GRADE FULL  
SPEC DEVICES. CALLERS WELCOME.  
CATALOGUE/LIST FREE SEND SAE.  
BARCLAYCARD & ACCESS X POST.

## Digital Displays



SLA7 RED LED 0.3"  
DIGIT 0-9DP 89p ea  
GREEN&YELLOW £1.40  
JUMBO LED 0.6" 747  
DISPLAY £2.25 ea.  
3015F 0-9DP £1 ea.  
ZENON FLASH TUBE  
£4. .Data 15p.

## LEDS red 13p

LEDS 209 STYLE ONLY 13p ea  
TIL 209 WITH CLIP RED 15p ea  
TIL 211 & CLIP GREEN 29p ea  
LARGE 0.2" & CLIP RED 17p ea  
LARGE 0.2" CLIP GREEN 30p ea  
209 STYLE OR .2"ORANGE 29p ea  
INFRA RED LED £1.2N5777 33p.

## PHOTO IC 81P

TEC12 PHOTO AMP/SCMITT/RELAY  
DRIVER OF LED TTL INTERFACE 81p



FLUORESCENT LIGHTS 12V MADE IN UK  
8 WATT 13" £3. 13W 22" £3.50

## DIGITAL CLOCK

IC AY51224 4 DIGIT CLOCK £3.75  
MMS311/4 6 DIGIT CLOCK £7

## CASSETTE mechanics £13.75

NEW 8tk CARTRIDGE MECHANISM £8  
STEREO CASSETTE MECHANISM £13.75  
Suitable for 'PW ASCOT' recorder  
with heads etc. SEND 15p for DATA

## INTEGRATED CIRCUITS

709 DIL 14 28p	LM377 2x2Wf2.87
555 TIMER 54p	LM380 2W AF 89p
703 RF/IF 28p	LM381 2xPre £2
709 DIL 14 28p	LM3900 4xOPA69p
710 DIL 14 28p	MC1303 £1.20
710 DIL 14 28p	MC1306 53p
723 Reg. 54p	MC1310&LEDc2.65
741 DIL 8 27p	MC1312 SQ £2.10
741 DIL 14 28p	MC1330 69p
741 T099 29p	MC1339 2xPre £1
748 2x741 70p	MC1350 55p
748 DIL 8 33p	NE536 fetOPA £2
7805 5V £1.40	NE540 DrVer £1
7812 & 15 £1.40	NE550 2xRef 79p
76013 8W AF £1	NE555 Timer 55p
8038 SIG GEN £3	NE559 2x" £1.20
CA3028 £1	NE560 PLL £3.15
CA3046 55p	NE561 PLL £3.15
CA3048 £2	NE562 PLL £3.19
CA3052 £1.50	NE565 PLL £2.69
CA3054 £1	SN72709 709 28p
LM300 2-20V £2	SN72741 741 26p
LM301 OPA 45p	SN72748 748 33p
LM304 0-40V £3	SN76660 IF £1
LM307 OPA 49p	SN76611 1F1.25
LM308 HIB 95p	TAD110 & IF £2
LM309K 5V £1.48	TB8810 7WAF 99p
LM372 IF £1.80	ZN414 RX £1.09

**SPECIAL OFFERS**  
2N3055 FULL HIGH SPEC 115W 37p  
741C 8PIN DIL 27p. MFC4000B 33p  
NE555 TIMER 55p. N414 RX £1.05  
BC109 9p. 2N3819e .16p. BFY51 15p

## 740 TTL

7400 GATES 13p	7473 74/76 29p
7404 INVERT 17p	7475 45p
7401/2/10etc14p	7480 52p
7413 SCMITT 31p	7491/2/3/1 59p
7410 BUFFER 14p	74100 74175 £1
7440 DRIVER 89p	74121 32p
7470 & 7472 29p	74123 32p
	74141 (&7441) 79p

## TRANSISTORS & DIODES

Price each	MATCHING 16p
AC127 & 128 16p	INS. BUSH SET10P
AC187 & 188 19p	TIP 41 70p
AD149 43p	TIP 42 88p
AD161 & 162 33p	TIP 2955 90p
BC107 & 108 9p	TIP 3055 55p
BC109 10p	TIS43 see 2N2448
BC147/8/9 10p	ZTX109&301 13p
BC157/8/9 12p	1N4001 14p
BC167/8/9 12p	1N4004 & 7 7p
BC177/8/9 18p	1N4148 14p
BC182/3/4/44L11p	2N697 14p
BCY70/1/2 17p	2N7068 11p
BD131 & 132 39p	2N2646 UJT 32p
BFR51 23p	2N2904 & 5 20p
BFR50/51 23p	2N2926 26p
BFR88 250V 29p	2N3053 17p
BFY50/1/2 15p	2N3055 115W 37p
BSX19/20/21 16p	2N3563 & 64 16p
MJE2955 90p	2N3614 49p
MJE3055 65p	2N3702 & 3 9p
MPU131 PUT 49p	2N3704 & 5 10p
OA91 OA81 6p	2N3706 & 7 9p
OA81 & OA91 6p	2N3708 & 9 8p
TIP 29 & 30 52p	2N3710 & 11 10p
TIP 31 & 32 69p	2N3819E FET 17p
	2N3823E FET 17p
	2N3904/5/6 15p

## NEW TRAMPUS FULL SPEC PAKS

PAK A 10 RED LEDS our choice £1
PAK B 7 741 OP £1
PAK C 4 2N3055 £1 D 12 BC109 £1
PAK E 10 BC182 £1 F 11 2N3704 £1
PAK G 8 BFY51 £1 H 9 2N3819e £1
PAK J 9 2N3053 £1 K 40 1N914 £1

BZ788 400mW	1A/50V SCR 36p
ZENER DIODES 9p	TAG1/400 55p
BRIDGE RECT	C106 & 7 SCR D1
1A 50V 20p	4A/400V 53p
BR100 DIAC 25p	SC146D TRIAC
	10A 400V 75p

## vero

VERO PINSx36 28p.  
COPPER CLAD VEROBOARD 0.1"  
2 1/2"x5" 29p 2 1/2"x3 1/2" 26p 3 1/2"x3 1/2" 31p.  
3 1/2"x5" 31p 3 1/2" 17" £1.50  
DIL IC's BOARDS 6x4 1/2" £1.50  
24 way edge connector 60p.  
36 way 90p. PLAIN 3 1/2"x17" £1.  
FACE CUTTER 45p. FEC ETCH PAK 50p

## DAOpen69p

PRINTED CIRCUIT BOARD KIT £1.69  
DECON NO MESS ETCH PAK £1.69  
DECON DESOLDER BRAID REEL 59p

## HEATSINKS

5F/T05 & 18F/T018 5p ea. TV4 15p.  
TV3/T03 16p. EXTRUDED 4" 4Y1 29p.  
TGS308 GAS DETECTOR £1.80 ea.  
LOGIC PROBE TTL TESTER PEN £5

## CAPACITORS

CERAMIC 22pF to 0.1uF 50v 5p.  
ELECTROLYTIC: 10/50/100 uF in  
10v 5p. 25v 6p. 50v 8p. 2uF/10v 5p.  
1000 uF/25v 18p. 200/500 25v 9p.

## POTENTIOMETERS (POTS) AB or EGIN

10K or LOG ROTARY 13p. SWITCH 11p  
DUAL 45p. SLIDERS 29p. STEREO 57p  
KNOBS 7p. PRESETS 6p. RESISTORS 13p  
SWITCHES: SPST 12p. DPDT 25p.

DIN PLUGS ALL 18p. SOCKETS 10p.  
ALI CASES AB5/AB7 50p. AB13 65p.  
TRANSFORMERS 1A 6v/6v or 12v/12v  
Only £1.34. 100mA type CT 75p.

## OIL sockets

TEXAS GOLD  
LOW PROFILE ea  
8, 14, & 16 PIN 13p  
SOLDERCON STRIPS:  
100 PINS 50p. 1K £3.

# THE NEW NELSON-JONES FM TUNER

**PUSH-BUTTON VARICAP DIODE TUNING (6 Position)**

(‘WW’ JUNE ‘73)

Exclusive Designer Approved Kits



What are the important features to look for in an FM tuner kit? Naturally it must have an attractive appearance when built, but it must also embody the latest and best in circuit design such as:-

- MOSFET** front end for excellent cross modulation performance and low noise.
- 3 GANG** tuning for high selectivity.
- VARICAP** tuning diodes in back to back configuration for low distortion.
- CERAMIC** filters for defined IF response.
- INTEGRATED** circuit IF amplifiers for reliability and excellent limiting/AM rejection.

The Nelson-Jones Tuner has all of these features and many more, and more importantly the design is fully proven not just with a few prototypes but with many thousands of working tuners spread across the world.

Typ. Specn: 20 dB quieting 0.75uV. Image rejection -70dB.I.F. Rejection -85 dB.

Basic tuner module prices start as low as £12.96, with complete kits starting at £26.95 (mono) + P.P. 65p, and of course all components are available separately.


Our low cost alignment service is available to customers without access to a signal generator. Please send large SAE for our latest price lists which details all of the many options and special low prices for complete kits. All our other products remain available.

**PORTRUS AND HAYWOOD PHASE LOCKED DECODER** (w.w. Sept. '70). Still the lowest distortion P.L. decoder available. THD typically 0.05% (at Nelson-Jones Tuner O/P level)! Supplied complete with Red LED.

Price £7.02 when bought with a complete N-J tuner kit or £8.29 if bought separately (P.P. 21p).

**PLEASE NOTE.** Existing tuners are readily convertible and kits/parts are available for this purpose.

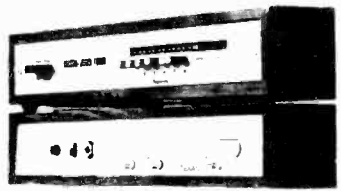**TEXAN AMPLIFIER.** We have designed the tuner case and metalwork to match the Texan amplifier (see photograph). Complete designer approved Texan kits are available at £33.48 plus P.P. 65p including Teak Sleeve.



## NEW LOW COST STEREO TUNER Available as basic or complete kits

Basic stereo tuner £15 post free.  
Basic mono tuner £12 post free.  
6 position push button units with  
Integral pots £3.24.



No alignment required. Mullard LPT186 front end module used with Ceramic IF and IC amplifier. Push button tuning (6 position) with Interstation Mute, restricted range AFC, single LED tuning indicator, phase locked IC decoder, and complete metalwork and veneered cabinet. Complete with IC regulated PSU and full assembly instructions. (Mechanically identical to N-J Tuner.)

**PRICE** Complete stereo kit £28.42  
Complete mono kit £24.19  
P. & P. 65p

**TYP. SPECIFICATION**  
2uV for 30dB S/N  
Image rejection 40dB  
IF rejection 65dB

VAT at 8% is included in all prices

**INTEGREX LIMITED, P.O. Box 45, Derby, DE1 1TW Phone Swadlincote (028387) 5432 Telex 377106**

## SOUND TO LIGHT UNIT

Add colour or white light to your amplifier. Will operate 1, 2 or 3 lamps (maximum 450W) Unit in Box all ready to work. **£7.95** plus 95p VAT and postage.



## PORTABLE CABINET OFFER

A nicely made portable cabinet, soft padded black finish intended for portable stereo system. Dimensions as sketch. With motor board cut out for Garrard SP 25. This was obviously a very costly cabinet originally made for a de-luxe record player. Offered at **£1.95** plus £1 carriage, free if bought with the Garrard or BSR record decks.



## LIGHT DIMMER KIT

For dimming up to 250W without heat sink or 750W with heat sink. This comprises, quadric variable control potentiometer, condenser, resistors, tag strip for mounting and data. Price **£1.80**. 5 amp Industrial Model **£3.30**.

## RELAY BARGAIN

Type 600 relay, 2 changeover one open and one closed contact. Twin 500 ohm coils make this suitable for closing off DC 6v, DC 12v, DC 24v or AC mains via resistor and rectifier, 33p each. Resistor and rectifier 20p extra.



## MAINS MOTOR

Precision made—as used in record decks and tape recorders—ideal also for extractor fans, blower, heaters, etc. New and perfect. Only at 75p. Postage 20p for first one then 10p for each one ordered. 1" stackmotor **£1.04**. 1 1/2" stackmotor **£1.20**.

## 15A ELECTRICAL PROGRAMMER

Learn in your sleep! Have radio playing and kettle boiling as you awake — switch on lights to ward off intruders — have a warm house to come home to. All these and many other things you can do if you invest in an electrical programmer. Clock by famous maker with 15 amp. on/off switch. Switch-on time can be set anywhere to stay on up to 6 hours. Independent 60 minute memory jogger. A beautiful unit. Price **£2.30** + 20p. p. & or with glass front, chrome bezel. **£1.00** extra.

## WINDSCREEN WIPER CONTROL

Vary speed of your wiper to suit conditions. All parts and instructions to make. **£2.75**.



## 6 DIGIT COUNTER

Resetttable. 440 ohm coil up to 25 impulses per second. Ex-equipment but guaranteed perfect. **£2.85** each. 4 digit counter as specified for telephone charge calculator **99p**.

## PRESSURE SWITCH

Containing a 15 amp change over switch operated by a diaphragm which in turn is operated by air pressure through a small metal tube. The operating pressure is adjustable but is set to operate in approx. 10 in. of water. These are quiet low pressure devices and can in fact be operated simply by blowing into the inlet tube. Original use was for washing machines to turn off water when tub has reached correct level but no doubt has many other applications **£1.72**, each.



## NUMICATOR TUBES

For digital instruments, counters, timers, clocks, etc. HI-vac XN.3. Price 99p each, 10 for **£9**.

## MULLARD AUDIO AMPLIFIERS

All in module form, each ready built complete with heat sinks and connection tags, data supplied. Model 1183 500mW power output 80p Model 1172 750mW power output **£1.07** Model EP9000 4 watt power output **£2.00** EP 9001 twin channel or stereo pre amp. **£1.41**

**TERMS:—**  
ADD 8% V.A.T.  
Send postage where quoted—other items, post free if order for these items is £6.00, otherwise add 30p.


## CENTRIFUGAL BLOWER

Miniature mains driven blower centrifugal type blower unit by Woods. Powerful but specially built for quick running—driven by cushioned induction motor with specially built low noise bearings. Overall size 4 1/4" x 4 1/4" x 4". When mounted by flange, air is blown into the equipment but to suck air out, mount it from centre using clamp. Ideal for cooling electrical equipment or fitting into a cooker hood, film drying cabinet or for removing flux smoke when soldering, etc. etc. A real bargain at **£2.50p**.



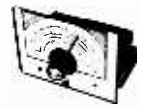
## TANGENTIAL HEATER UNIT

This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in Hoover and blower heaters. Comprises motor, impeller, 2kW element allowing switching 1, 2kW, and with thermal safety cut-out. Can be fitted into any metal lined case or cabinet. Only needs control switch. **£2.75**. Don't miss this. Control Switch, 55p. P. & P. 50p.


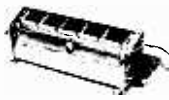
## SHORTWAVE CRYSTAL SET

Although this uses no battery it gives really amazing results. You will receive an amazing assortment of stations over the 19.25, 31.39 metre bands—Kit contains chassis front panel and all the parts. **£1.25**—crystal ear-phone 50p.



## DRILL CONTROLLER



### NEW IKW MODEL

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. **£2.25** plus 25p post and insurance. Made up model also available. **£3.25** plus 30p post & p.


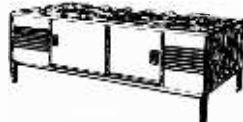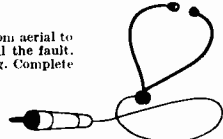
## RADIO STETHOSCOPE

Easiest way to fault find traces—signal from aerial to speaker, when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything. Complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. **£2.50** twin stetho-vent instead of earpiece 83p extra post and ins. 20p.



## STEREO RADIO CABINET

Long, Low and Modern. Teak veneered with sliding front and tapered legs. Speaker spaces each end. Size approx. 4ft. 2in x 15in x 15in. Probably cost over **£20** to make. Our Price **£8.10** each.

## TAPE DECK

In metal case with carrying handle, heavy fly wheel and capstan drive. Tape speed 3 1/2. Mains operated on metal platform with tape head and guide. Not new but guaranteed good working order. Price **£1.95** plus £1 post and insurance.



## GENERAL PURPOSE SWITCH

Responds to moisture, heat, light, touch, time delays, etc. etc. Basic kit comprising relay, transistors, diodes, condensers, resistors, etc. and data—only **£1.50** + 30p post.



## AMMETERS

—moving iron so AC/DC—ideal for chargers etc. 2" sq. full vision 0-8 amp 85p. 1 1/2" round 0-2 amp 55p. 0-3 amp 65p. 0-4 amp 75p.



## DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 6 feet of flex cable. Wired up ready to work. **£2.75** plus 25p P. & P.

## 7 WATT STEREO AMPLIFIER


Again made by the famous GEC company. This has exceptionally good tone quality and is complete with rectifiers and smoothing, so requires only a mains transformer. Treble, Bass, Volume and Balance controls. 15 ohm output. Inputs for tuner, ceramic pickup, etc. Price **£6** plus 30p post and insurance.

## SPIT MOTOR

200-250V induction motor, driving a Carter gearbox with a 1 1/2" output drive shaft running at 5 revs p.m. Intended for roasting chickens, also for driving models—windmills, coloured disc lighting effects, etc. **£2.50** plus 20p post and ins.
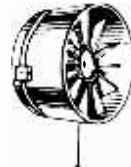
## EXTRACTOR FAN

Cleans the air at the rate of 10,000 cubic ft. per hour. Suitable for kitchens, bathrooms, factories, changing rooms, etc., it's so quiet it can hardly be heard. Compact, 5 1/2" casing with 5 1/2" fan blades. Kit comprises motor, fan blades, sheet steel casing, pull switch, mains connector, and fixing brackets. **£2.75** + 20p P. & P.



## NEW ITEMS THIS MONTH

The bargains in this column are just some of the items which appeared in the January supplement to our catalogue. You can receive the next 12 supplements and catalogue when published March or April.

**Room Thermostat.** Mercury Switch type with thermometer for hot voltage gas central heating systems etc. Made by a famous American Company, these are of very neat appearance, in plastic case, easily mounted but the most important feature is that they cut in and out quickly, thus maintaining a very steady temperature. Price **£1.85**

**Flexible heat.** You have probably from time to time wanted to warm something by actually winding the heater around it. You can do this now for we have in stock flexible elements comprising glassfibre tape approx. 1" wide, approx. 1/8" thick, 15 ft. long. The element is embedded into this, and fully insulated from the outside. The ends can be taken directly into a 13 amp plug or junction box which we can supply at 24p extra. These are rated at 100 watts but you can reduce this if you wish by joining two in series. Price of element is **£1.05**, no extra for postage if ordered with other items totalling **£5** or over.

**Self-adhesive paper discs 1"** Ideal for marking leads as you take them off, or for providing quick insulation of soldered or twisted joints. 50p per 1,000 or **£2** per box of 5,000.

**Pick-up cartridges.** We have two extra special bargains this month—"Sure" magnetic type number 77DB for **£3.50** and "Ronette" turnover mono cartridge standard replacement for DC400 series price **£1.50**.

Again available—two items which have been held up through supply difficulties: the domestic light dimmer kit at **£1.50** and the industrial 5 amp dimmer at **£3.50** are once again available for immediate despatch.

**Multi-core cable,** 7 cores each pvc insulated and covered, screened overall then with pvc outer covering. A miniature cable diameter approx. 1/2", price 20p per metre available in lengths up to 15 metres.

**Fluorescent control trays** made for Philips so therefore obviously firstclass. These are for two 4 watt 4 ft. tubes and contain quick start transformer, condensers all wired tube ends and provided with Terry clips to hold the tubes. A real bargain at **£2.75** each + 30p each post.

**Break before make water switch.** We are sometimes asked for these but we do not normally keep a range. However, we have some 2 pole 5 way with 1 1/2" water, a substantially well-made switch which we can offer for **45p** each.

**Universal switch** described in a recent edition of Everyday Electronics. This switch can be made to respond to many types of variables, for instance temperature changes through a thermometer, humidity changes through vapour sensing device, or just a piece of veribond put out to catch the rain or immersed in the flow—any light level changes through a photo-resistive cell and many others. This is basically a relay operated by a sensitive transistor circuit. We can supply relay, transistor and all the ancillary parts for **£1.50**.

**Foot switches.** We are producing a range of foot switches of robust construction and suitable for making and breaking circuits of up to 10 amps at mains voltage. Model A operates single changeover switch and the price is **£1.75**. Model B operates two changeover switches and is **£2.25**. Model C has three changeover switches and is **£2.75**. All are fully assembled ready for connection.

**A useful power pack** giving 250V DC and 6-3v AC mounted on chassis size 3 1/2" x 5" with 5 amp AC regulated double wound fully impregnated mains transformer and full wave rectifier with adequate smoothing condensers. Used but guaranteed in good order. Price only **£1.50** + 75p post.

**Mains Transformers.** We have a good range of mains transformers covering most requirements and we can still supply at reasonable prices, large or immersed in the flow—any light level changes through a photo-resistive cell and many others. This is basically a relay operated by a sensitive transistor circuit. We can supply relay, transistor and all the ancillary parts for **£1.50**.

V	A	Price	V	A	Price
1v	..	..	1 amp (special)	1.75	
2.4v	..	..	5 amp	..	85
6-3v	..	..	2 amp	..	1.00
6-3v	..	..	3 amp	..	1.50
9v	..	..	1 amp	..	95
9v	..	..	2.5 amp	..	1.95
12v	..	..	500mA	..	1.00
12v	..	..	1 amp	..	1.00
6-5v-0-6-5v	..	..	1 amp	..	1.35
18v	..	..	1 amp	..	1.25
20v	..	..	1 amp	..	1.50
24v	..	..	1 amp	..	1.50
12-0-12v	..	..	3 amp	..	3.50
6-0-6v	..	..	50mA	..	1.20
8-0-8v	..	..	50mA	..	1.20
18-0-18v	..	..	1 amp	..	1.25
25v	..	..	1 amp	..	3.50
60v 2 amp & 6-3v 1 amp	..	..	1 amp	..	1.95
80v 2 amp & 5v 1 amp	..	..	1 amp	..	1.50
27v	..	..	8 amp	..	4.50
30v	..	..	37 amp	..	28.00
80v tapped 75v & 70v	..	..	4 amp	..	5.80
230v-60mA & 6-3v	..	..	1-5 amp	..	1.75
275-0-275v at 90mA & 6-4v	..	..	3 amps	..	2.25
EHT Transformer 5000v at 23mA	..	..	(intermittent)	..	5.50
<b>Charger Transformers</b>					
6v and 12v	..	..	2 amps	..	1.25
6v and 12v	..	..	3 amps	..	2.25
6v and 12v	..	..	5 amps	..	3.50

## J. BULL (ELECTRICAL) LTD.

(Dept. PW), 102/3 TAMWORTH ROAD, CROYDON CR0 1XX

# The largest selection

## EX-COMPUTER STABILISED POWER MODULES

Complete with circuit diagrams etc. 99p each plus 22p p. & p.

## LOW COST CAPACITORS

01µF 400v. 8p. each  
500µF 50v. Elect. 10p each

## FIBRE-GLASS PRINTED CIRCUIT BOARDS

14 1/2 x 4" approx. 2 for 55p

## DECON-DALO 33PC Marker

Etch resistant printed circuit marker pen 99p each

## VEROBOARDS

Packs containing approx. 50sq. ins. various sizes, all 1 metric 55p

## REPANCO CHOKES & COILS

RF Chokes  
CH1. 2.5mH 20p CH2. 5.0mH 30p  
CH3. 7.5mH 31p CH4. 10mH 33p  
CH5. 1.5mH 25p

## COILS

DRX1 Crystal set 31p DRR2 Dual range 45p

## COIL FORMERS & CORES

NORMAN 1/2 Cores & Formers 5p  
1/2 Cores & Formers 10p

## SWITCHES

DP/DT Toggle 36p SP/ST Toggle 30p

## FUSES

1 1/2" and 20mm. 100mA, 200mA, 250mA, 500mA, 1A, 1.5A, 2A  
QUICK-BLOW 5p ea.

## EARPHONES

Crystal 2.5mm plug 42p  
Crystal 3.5mm plug 42p  
8 ohms 2.5mm plug 22p  
8 ohms 3.5mm plug 22p

## DYNAMIC MICROPHONES

B1223. 200 ohms plus on/off switch and 2.5mm and 3.5mm plugs £1.95

## 3-WAY STEREO HEADPHONE JUNCTION BOX

H1012 £1.87

## 2-WAY CROSSOVER NETWORK

K4007. 80 ohms Imp. Insertion loss 3dB @ 21.2

## CAR STEREO SPEAKERS

(Angled) £3.85 per pair.

## BI-PAK

CATALOGUE AND LISTS  
Send S.A.E. and 10p.

## INSTRUMENT CASES



(Black Vinyl covered)

No.	Length	Width	Height	Price
BV1	8"	4 1/2"	2"	£1.35
BV2	11"	6"	3"	£1.75

## ALUMINIUM BOXES

Box No.	Length	Width	Height	Price
BA1	5 1/2"	2 1/2"	1 1/2"	49p
BA2	4"	4"	1 1/2"	49p
BA3	4"	2 1/2"	1 1/2"	49p
BA4	5 1/2"	4"	1 1/2"	58p
BA5	4"	2 1/2"	2"	49p
BA6	3"	2"	1"	42p
BA7	7"	5"	2 1/2"	35p
BA8	8"	6"	3"	£1-10
BA9	6"	4"	2"	70p

P & P 15p on each box

## VISIT OUR COMPONENT SHOP

18 BALDOCK ST., WARE, Herts. (A10)

\*Open Mon.-Sat. 9-5.30 p.m. Tel. 61593

## BIB HI-FI ACCESSORIES

### De Luxe Groov-Kleen

Model 42 £1.95

Chrome Finish

Model 60 £1.50



Ref. B Stylus & Turntable Cleaning Kit 34p  
Ref. 38A. Record/Stylus Cleaning Kit 33p  
Ref. 43. Record Care Kit £2.42  
Ref. 31. Cassette Head Cleaner 58p  
Ref. 32. Tape editing Kit £1.68  
Model 9. Wire Stripper/Cutter 83p

Ref. 46. Spirit level 62p  
Ref. P. Hi-Fi Balance 31p  
Ref. 32A. Stylus Cleaner £1.87  
Ref. J. Tape Head Cleaning Kit 62p  
Ref. 58. Hi-Fi Stereo Hints & Tips 42p  
Ref. 45. Auto changer groove cleaner £1.08

## ANTEX SOLDERING IRONS

X25. 25 watt £2.05  
CCN 240. 15 watt £2.48  
Model G. 18 watt £2.28  
SK2. Soldering Kit £3.25  
STANDB: ST3, Suitable for all models £1  
SOLDER: 188WG Multicore 7oz £1.61  
228WG 7oz £1.61. 188WG 22ft 51p  
228WG Tube 33p

## ANTEX BITS and ELEMENTS

Bits No.  
102 For model CN240 3/32" 42p  
104 For model CN240 3/16" 42p  
1100 For model CCN240 2/32" 42p  
1101 For model CCN240 3/8" 42p  
1102 For model CCN240 1" 42p  
1020 For model G240 3/32" 42p  
1021 For model G240 1/8" 42p  
1022 For model G240 3/16" 42p  
50 For model X25 3/32" 48p  
51 For model X25 1/8" 48p  
52 For model X25 3/16" 48p

## ELEMENTS

ECN 240 £1.30 ECOCN 240 £1.82  
EG 240 £1.07 EX 25 £1.16

## ANTEX HEAT SINKS 10p

V.A.T. included in all prices. Please add 10p P. & P. (U.K. only). Overseas orders—please add extra for postage.

## NEW COMPONENT PAK BARGAINS

Pack No.	Qty.	Description	Price
C1	200	Resistors mixed values approx. count by weight	0.84
C2	150	Capacitors mixed values approx. count by weight	0.84
C3	50	Precision Resistors 1%, 2% mixed values	0.84
C4	75	1/4 W Resistors mixed preferred values	0.84
C5	5	Pieces assorted Ferrite Rods	0.84
C6	2	Tuning Gangs, MW/LW VHF	0.84
C7	1	Pack Wire 50 metres assorted colours	0.84
C 8	10	Reed Switches	0.84
C 9	3	Micro Switches	0.84
C10	15	Assorted Pots & Pre-Sets	0.84
C11	5	Jack Sockets 3 x 3.5m 2 Standard Switch Type	0.84
C12	30	Paper Condensers preferred types mixed values	0.84
C13	20	Electrolytics Trans. types	0.84
C14	1	Pack assorted Hardware Nuts/Bolts, Grommets etc.	0.84
C15	5	Mains Slide Switches	0.84
C16	20	Assorted Tag strips & Panels	0.84
C17	10	Assorted Control Knobs	0.84
C18	4	Rotary Wave Change Switches	0.84
C19	2	Relays 6-24V Operating	0.84
C20	1	Pack sheets of Copper Laminated 20 sq. ins	0.84

## PLUGS AND SOCKETS

PLUGS  
PB 1 D.I.N. 2 Pin (Speaker) 0.11  
PB 2 D.I.N. 3 Pin 0.12  
PB 3 D.I.N. 4 Pin 0.18  
PB 4 D.I.N. 5 Pin 180° 0.18  
PB 5 D.I.N. 5 Pin 240° 0.17  
PB 6 D.I.N. 6 Pin 0.18  
PB 7 B.I.N. 7 Pin 0.18  
PB 8 Jack 2.5mm Screened 0.12  
PB 9 Jack 3.5mm Plastic 0.12  
PB 10 Jack 3.5mm Screened 0.18  
PB 11 Jack 1/2" Plastic 0.15  
PB 12 Jack 1/2" Screened 0.22  
PB 13 Jack Stereo Screened 0.38  
PB 14 Phono 0.10  
PB 16 Car Aerial 0.22  
PB 16 Co-Axial 0.15

## INLINE SOCKETS

PS 21 D.I.N. 2 Pin (Speaker) 0.14  
PS 22 D.I.N. 3 Pin 0.20  
PS 23 D.I.N. 5 Pin 180° 0.20  
PS 24 D.I.N. 5 Pin 240° 0.20  
PS 25 Jack 2.5mm Plastic 0.18  
PS 26 Jack 3.5mm Plastic 0.18  
PS 27 Jack 1/2" Plastic 0.35  
PS 28 Jack 1/2" Screened 0.30  
PS 29 Jack Stereo Plastic 0.38  
PS 30 Jack Stereo Screened 0.18  
PS 31 Phono Screened 0.22  
PS 32 Car Aerial 0.22  
PS 33 Co-Axial 0.22

## SOCKETS

PS 35 D.I.N. 2 Pin (Speaker) 0.08  
PS 36 D.I.N. 3 Pin 0.11  
PS 37 D.I.N. 5 Pin 180° 0.11  
PS 38 D.I.N. 5 Pin 240° 0.11  
PS 39 Jack 2.5mm Switched 0.12  
PS 40 Jack 3.5mm Switched 0.12  
PS 41 Jack 1/2" Switched 0.20  
PS 42 Jack Stereo Switched 0.30  
PS 43 Phono Single 0.10  
PS 44 Phono Double 0.10  
PS 46 Co-Axial Surface 0.10  
PS 47 Co-Axial Flush 0.20

## LEADS

LS 1 Speaker lead 2 pin D.I.N. plug to open ends approx. 3 metres long (coded) 0.20

## CABLES

CP 1 Single Lapped Screen 0.07  
CP 2 Twin Common Screen 0.11  
CP 3 Stereo Screened 0.12  
CP 4 Four Core Common Screen 0.23  
CP 5 Four Core Individually Screened 0.30  
CP 6 Microphone Fully Braided Cable 0.10  
CP 7 Three Core Mains Cable 0.09  
CP 8 Twin Oval Mains Cable 0.07  
CP 9 Speaker Cable 0.05  
CP 10 Low Loss Co-Axial 0.18

## CARBON POTENTIOMETERS

Log and Lin  
4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M  
VC 1 Single less Switch 0.15  
VC 2 Single D.P. Switch 0.28  
VC 3 Tandem Less Switch 0.46  
VC 4 1K Lin Less Switch 0.15  
VC 5 100K Log anti-Log 0.48

## HORIZONTAL CARBON PRESETS

0.1 watt 0.06 each  
100, 220, 470, 1K, 2.2K, 4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 4.7M

## SOLVE THOSE STICKY PROBLEMS!



## CYANOACRYLATE C2 ADHESIVE

The wonder bond which works in seconds—bond plastic, rubber, metals, transistors, components permanently immediately!

OUR PRICE ONLY 54p for 2gm phial.

## BATTERY HOLDER

Takes 4, HP7's complete with terminal, clip and lead. 34p.

## WORLD SCOOP

JUMBO SEMICONDUCTOR PACK  
Transistors - Germ. and Silicon Rectifiers Diodes - Triacs - Thyristors - I.C.'s and Zeners ALL NEW AND CODED.

## APPROX 100 PIECES

Offering the amateur a fantastic bargain Pak and an enormous saving—identification and data sheet in every Pak.

Only £2 p. & p. 20p

## RECORD STORAGE/ CARRY CASES

7" EP. 18 1/2" x 7" x 8". (50 records) £2.10  
12" LP. 13 1/2" x 7 1/2" x 12 1/2". (50 records) £2.95

## CASSETTE CASES £1.80

Holds 12. 10" x 3 1/2" x 5". Lock & Handle

## 8-TRACK CARTRIDGE CASES

Holds 14. 13" x 6" x 6" £1.95  
Holds 24. 13 1/2" x 8" x 5 1/2" £2.70.  
Both with lock and handle.

## SPECIAL PURCHASE

2N2056. Silicon Power Transistors NPN. Famous manufacturers out-of-spec devices free from open and short defects—every one able 115v. T03. Metal Case.

OUR SPECIAL PRICE 8 for £1

## REPANCO TRANSFORMERS

240v. Primary. Secondary voltages available from selected tapings 4v, 7v, 8v, 10v, 14v, 15v, 17v, 19v, 21v, 25v, 31v, 33v, 40, 50 and 25v-0.25v.

Type	Amps.	Price	P & P
MT50/1	1	£1.98	45p
MT50/1	1	£2.49	45p
MT50/2	2	£3.50	60p

## CARTRIDGES

AC08  
GP91-18C 200mV at 1.2cm/sec £1.35  
GP93-1.280mV at 1cm/sec £1.35  
GP96-1.100mV at 1cm/sec £2.80  
TTC  
J-2005 Crystal/Hi Output £1.05  
J-2010C £1.20  
J-2008S Stereo/Hi Output Compatible £1.75  
J-2105 Ceramic/Med Output £1.95  
J-2203 Magnetic 5m/7cm/sec. including stylus £4.95  
J-2203B Replacement stylus for above £3.00  
AT-55 Audio-technica magnetic cartridge 4mV/5cm/sec £3.30

## CARBON FILM RESISTORS

The E12 Range of Carbon Film Resistors. 1/8th watt available in PAKS of 50 pieces. Assorted into the following groups:—  
R1 50 Mixed 100 ohms-820 ohms 50p  
R2 50 Mixed 1K ohms-8.2K ohms 50p  
R3 50 Mixed 10K ohms-82K ohms 50p  
R4 50 Mixed 100K ohms-1 Meg. ohms 50p  
THESE ARE UNREPEATABLE PRICES—JUST 1p EACH INCL. V.A.T.


## BI-PAK SUPERIOR QUALITY LOW - NOISE CASSETTES

C80. 86p C90. 48p C120. 60p

# -the lowest prices!

## BI-PAK QUALITY COMES TO AUDIO!
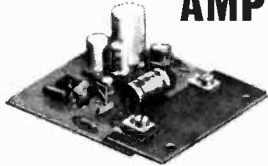
### AL10/AL20/AL30 AUDIO AMPLIFIER MODULES



The AL10, AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 3 to 10 watts R.M.S. The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the car and at home.

Parameter	Conditions	Performance
HARMONIC DISTORTION	Po = 3 WATTS f=1KHz	0-25%
LOAD IMPEDANCE	—	8-16 Ω
INPUT IMPEDANCE	f=1KHz	100 kΩ
FREQUENCY RESPONSE ± 3dB	Po = 2 WATTS	50 Hz - 25KHz
SENSITIVITY for RATED O/P	Vs=25V. Rl=8 Ω f=1KHz	75mV. RMS
DIMENSIONS	—	3" x 2 1/4" x 1"

The above table relates to the AL10, AL20 and AL30 modules. The following table outlines the differences in their working conditions.

Parameter	AL10	AL20	AL30
Maximum Supply Voltage	25	30	30
Power output for 2% T.H.D. (RL = 8 Ω f = 1 KHz)	3 watts RMS Min.	5 watts RMS Min.	10 watts RMS Min.

#### AUDIO AMPLIFIER MODULES

AL 10. 3 watts RMS	£2 50
AL 20. 5 watts RMS	£2 85
AL 30. 10 watts RMS	£3 20

#### POWER SUPPLIES

PS 12. (Use with AL10, AL20, AL30) 85p

SPM 80. (Use with AL60) £3 25

FRONT PANELS F.P. 12 with Knobs £1 10

#### PRE-AMPLIFIERS

PA 12. (Use with AL10, AL20 & AL30) £4 35

PA 100. (Use with AL60) £13 15

#### TRANSFORMERS

T461 (Use with AL10) £1 60 P & P 22p

T638 (Use with AL20, AL30) £2 30 P & P 22p

BMT80 (Use with AL60) £2 75 P & P 37p

#### PA 12. PRE-AMPLIFIER SPECIFICATION

The PA 12 pre-amplifier has been designed to match into most budget stereo systems. It is compatible with the AL 10, AL 20 and AL 30 audio power amplifiers and it can be supplied from their associated power supplies. There are two stereo inputs, one has been designed for use with \*Ceramic cartridges while the auxiliary input will suit most †Magnetic cartridges. Full details are given in the specification table. The four controls are, from left to right: Volume and on/off switch, balance, bass and treble. Size 152mm x 84mm x 36mm.

Frequency response—  
20Hz - 50KHz (-3dB)  
Bass control—  
± 12dB at 60Hz  
Treble control—  
± 14dB at 14KHz  
\*Input 1. Impedance  
1 Meg. ohm  
Sensitivity 300mV  
†Input 2. Impedance  
30 K ohms  
Sensitivity 4mV

Look for our


SEMICONDUCTOR ADVERTISEMENTS in

Practical Wireless Wireless World Radio Constructor

ALL PRICES INCLUDE V.A.T.
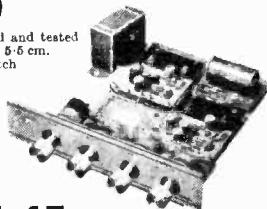
## The STEREO 20

The 'Stereo 20' amplifier is mounted, ready wired and tested on a one-piece chassis measuring 20 cm x 14 cm x 5.6 cm. This compact unit comes complete with on/off switch volume control, balance, bass and treble controls, Transformer, Power supply and Power amp. Attractively printed front panel and matching control knobs. The 'Stereo 20' has been designed to fit into most turntable plinths without interfering with the mechanism or alternatively, into a separate cabinet. Output power 20w peak. Input 1 (Cer.) 300mV into 1M. Freq. res. 25Hz-25kHz. Input 2 (Aux.) 4mV into 30K. Harmonic distortion: Bass control ±12dB at 60Hz typically 0.25% at 1 watt. Treble con. ±14dB at 14kHz.



£14.45 p. & p. 45p.

#### TC20 TEAK VENEERED CABINET

For Stereo 20 (front board undrilled) size 10 1/4" x 8 1/4" x 3". £8.95, plus 45p postage

#### SHP80 STEREO HEADPHONES

4-16 ohms impedance. Frequency response 20 to 20,000Hz Stereo/mono switch and volume controls £4 95

## NOW WE GIVE YOU 50w PEAK (25w R.M.S.) PLUS THERMAL PROTECTION! The NEW AL60 Hi-Fi Audio Amplifier FOR ONLY £4.25


- Max Heat Sink temp. 90°C.
- Frequency Response 20Hz to 100KHz
- Distortion better than 0.1% at 0-1KHz
- Supply voltage 15-50 volts

- Thermal Feedback
- Latest Design Improvements
- Load—3, 4, 8 or 16 ohms
- Signal to noise ratio 80dB
- Overall size 63mm x 105mm x 13mm

Especially designed to a strict specification. Only the finest components have been used and the latest solid state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.



## STABILISED POWER MODULE SPM80

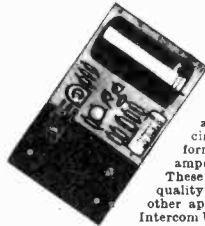

SPM80 is especially designed to power 2 of the AL60 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Main Transformer BMT80, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 63mm x 105mm x 30mm.

These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including:—Disc Systems, Public Address Intercom Units, etc. Handbook available 10p

PRICE £3.25

TRANSFORMER BMT80 £2.15 p. & p. 40p

## STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL60 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages.

Three switched stereo inputs, and rumble and scratch filters are features of the PA100 which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.

#### SPECIFICATION

Frequency Response 20Hz - 20KHz ± 1dB  
Harmonic Distortion better than 0.1%  
Inputs: 1. Tape Head 3.25 mV into 50K Ω  
2. Radio, Tuner 75 mV into 50K Ω  
3. Magnetic P.U. 3 mV into 50K Ω  
All input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within ± 1dB. from 20Hz to 20KHz.  
Bass Control ± 18dB at 20Hz  
Treble Control ± 15dB at 20 KHz  
Filters: Rumble (High Pass) 100Hz  
Scratch (Low Pass) 8KHz  
Signal/Noise Ratio better than -65dB  
Input overload + 26dB  
Supply + 35 volts at 20mA  
Dimensions 292mm x 82mm x 35mm

ONLY £14.25



#### MK 60 AUDIO KIT

Comprising: 2 x AL60, 1 x SPM80, 1 x BMT80, 1 x PA 100, 1 front panel, 1 kit of parts to include on-off switch, neon indicator, stereo headphone sockets plus instruction booklets. Complete Price: £29.75 plus 45p postage

#### TEAK 60 AUDIO KIT

Comprising: Teak veneered cabinet size 16 1/4" x 11 1/4" x 3 1/4", other parts include aluminum chassis, heatsink and front panel bracket, plus back panel and appropriate sockets etc. Kit price: £29.95 plus 45p postage

Giro No. 388-7006

Please send all orders direct to warehouse and despatch department

# BI-PAK

## P.O. BOX 6, WARE · HERTS

Postage and packing add 11p. Overseas add extra for airmail.

Minimum order 55p. Cash with order please.

Guaranteed Satisfaction or Money Back



# Aiding and Abetting

**A** PERSON who aids, abets, counsels or procures the commission by another person of a summary offence is guilty of that same offence and may be tried for that offence, whether or not he is charged as a principal . . .

As a follow-up to our comments last month on the reception of privileged transmissions, evidence exists which indicates that members of the public are quite openly being encouraged to break the law!

We refer of course, to advertisements that offer "walkie talkie radios" and "bugging devices" for which a licence is not available in the U.K.

These devices are currently being offered to members of the public and are often described for "fun and entertainment use". To invite members of the public to purchase these illegal devices is, in our opinion, a subliminal attempt to encourage the purchaser to break the law.

Purchasers of these devices could find themselves before the courts. Organisations or individuals that encourage others to break the law are aiding and abetting. Where does the responsibility lay? Is it the manufacturer, advertiser, publisher or retailer. Certainly, the purchaser will suffer if he breaks the law.

Heavy fines and the confiscation of equipment could result in conviction. What would the purchaser do then? Ask the supplier for his money back and reimbursement of fines and costs? Who is kidding who in these games that people are playing?

It is true that the small print invariably includes a statement to the effect that "a licence not available in the UK" or "a licence not generally available to members of the public".

Do not blame the Home Office if the equipment you purchase is not licensable in the UK—check first! Regulations exist on the allocation of frequencies to licensable equipment.

Our advice is simple: watch out for the small print in those advertisements. It could be the most important line in that advert! If in doubt, check with the Home Office Radio Regulatory Department, Waterloo House, Waterloo Road, London, SE1 8UA. You have been warned!

LIONEL E. HOWES—Editor.

We regret that due to pressure on Editorial space this month, Part 2 of "2 VHF Converters" has had to be held over. We hope to include this article in our May issue.

## NEWS...

### Eurovolts

**T**HE International Union of Producers and Distributors of electricity has agreed a 230V standard for electrical supplies throughout Europe. This standard has a  $\pm 10\%$  tolerance so the Continent can continue to operate on 220V and the U.K. on 240V.

This decision will now be made known to the International Electro-Technical Commission which hopes to produce a world standard voltage.

### U.S. calculators

**T**HE San Francisco based group National Semiconductors have launched a range of pocket calculators under the "Novus" brand-name. Prices range from £8 to £100.

### Conference

**T**HE Institute of Physics will hold a two day Conference on On-line Computers in Laboratory Use at Imperial College on 11-12 September, 1975. Residential accommodation will be available in Halls of Residence.

Papers will be presented under the following headings: General principals and techniques, Why use small computers?, Interfacing, Software, Systems Building and Data Presentation. Surveys of on-line computing applications in various branches of experimental physics. High energy physics, Plasma physics, crystallography, stress analysis, Space and atmospheric physics, Materials and Testing Atomic and Nuclear Physics, Low cost laboratory automation.

Specific examples of applications: Short contributions to come under the last heading are invited. Titles and short abstracts (200-300 words) should be sent to Dr. B. K. Penney, Department of Computing & Control, Imperial College, 48 Princess Gardens, London SW7 1LU by 21 June 1975.

Further details and application forms from *The Meetings Officer, The Institute of Physics, 47 Belgrave Square, London SW1X 8QX.*

### Good service

WHAT is believed to be a unique service has just been launched by SCS Components with the publication of two new catalogues. These catalogues, produced after a period of market research, list on the one hand the semiconductors of interest to the professional TV service sector and on the other hand those whose main interest will lie with the amateur small-order market.

The catalogues contain only a representative sample of the vast range of branded and guaranteed semiconductors offered by SCS Components at manufacturer's list prices. The only additional charge is 20p for post and packing and data sheets are free on request.

SCS Components is owned by one of the largest and most experienced distributors of semiconductors whose franchise agree-

ments include the leading manufacturers. Thus SCS Components are able to make available a broad and deep stocking level backed by technical expertise that has not hitherto been available.

The range includes all discrete and integrated semiconductors from Mullard, Motorola, Signetics, General Instrument (Microelectronics), G.I. (UK), Ferranti, RCA, Monsanto and Mostek. In the near future passive components from Mullard, Seatronics and Centralab will be added to the range.

David Jackson (previously of RS Components) has been brought in as sales manager and he reports to Albert Shipton, marketing manager of Semicomps Ltd.

The catalogue is available, free of charge, from *David Jackson, SCS Components, 5c Northfield Industrial Estate, Beresford Avenue, Wembley, Middlesex, HA0 1SD. Telephone 01-903-3168.*

### Lind-Air-Henry's

HENRY'S Home Entertainment Centres Ltd., a member of the Henry's Group of Companies, has now merged with Lind-Air Holdings Ltd. which trades as Lind-Air and Discount Audio. The new group has over 20 outlets in the United Kingdom and has recently opened its first European venture in Brussels with a 22,000 square foot showroom. The principal members of the board of the new group will be Henry French, chairman, David J. French, deputy chairman, Lionel G. Astor and Rafael Hyams, joint managing directors. The founder of Lind-Air, Mr. Bennie Linden still retains a material shareholding.

Henry's founded by Henry French over 30 years ago, and Lind-Air, both famous for their hi-fi centres which dominate the major London hi-fi areas of Tottenham Court Road and Edgware Road, now form a sizeable retail group of hi-fi specialised outlets.

### R.F. Power Meter

A NEW r.f. Power Meter, TF2512, from Marconi Instruments Limited is aimed directly at the mobile radio manufacturing and servicing industries, where a reasonable accuracy of measurement is sufficient. (The meter costs about half as much as MI's range of high-accuracy d.c. to 1GHz power meters.) It is a robust and light instrument (2.75kg), entirely self-contained, needing no mains/battery supply.

### High-power BBC

BBC Radio London's medium-wave service on 206 metres (1457kHz) is now transmitted from a new high-power transmitter at Brookmans Park, near Potters Bar.

Throughout the service area, reception should be improved and the area of good reception is expected to be extended southward to include Guildford, Godalming, Cranleigh, Horsham, Cuckfield, and Haywards Heath.

The v.h.f./f.m. transmissions of BBC Radio London on 94.9MHz continue unchanged.

### Audio-Visual Show

EXTENSIVE car parking facilities, expansive exhibition areas and potentially high attendance feature in the first Midland Audio/Visual Show to be held on 11th, 12th 13th April 1975. The exhibition is already attracting some of the largest manufacturers of audio and audio visual systems and will include one Press/Trade day and two weekend days to enable members of the public from the highly populated Midlands area to attend.

Site of this exhibition will be the conference and exhibition complex at the National Agricultural Centre, Kenilworth, Warwickshire. Over seven million people are said to live within easy reach of this area.

Exhibitors products at the Midland Audio/Visual Show will encompass video tape equipment, video lighting effects, educational aids for schools, sales training work and business aids. In addition there will be the consumer items including cassette, radio, cartridge and record equipment.

### South West transmitter

THE BBC brought a new transmitter into service at Redruth recently to broadcast the Radio 4 South West medium-wave service including 'Morning Sou' West', local news and weather reports. The new transmitter is located at the existing Redruth medium-wave transmitter site and transmits on 397 metres (755kHz). The daytime coverage extends to St Ives, Penzance, Helston, Falmouth, Truro, Newquay, Cambourne and Redruth.

The existing Radio 4 service from Redruth on 330 metres (908kHz) continues as will the v.h.f. service on Radio 4 South West.

Barnstaple, Plymouth and Torquay already have transmitters radiating the local Radio 4 programmes in the medium-wave band. Others are planned for Exeter and Taunton.

PW  
**'ASCOT'**  
**STEREO CASSETTE DECK**  
 PART 3

KEITH CUMMINS & TONY FRANCIS\*

**GENERAL CONSTRUCTION**

The machine is built into a wooden cabinet, designed as shown in Fig. 9. Once the cabinet has been built up the deck and electronics can be fitted. It should be stressed that accuracy in construction is essential if the parts are to fit together correctly and if the equipment is going to operate properly electronically.

The illustrations show the layout of every part but mistakes can still be made and every care should be taken to avoid errors in construction. It is always much simpler to take care initially and so eliminate time-consuming, and possibly expensive, trouble-shooting later.

The main sections of the machine can be listed as follows:— cabinet, deck mechanism, power supply, recording and playback amplifiers. The power supply and amplifiers are built and fitted into the cabinet, along with the deck mechanism. The parts are then



wired together as shown in Fig. 10. It is possible to lift out the circuit panels while the machine is operating. Wired connections are mostly made to the printed side of the panels so setting-up and service work is thereby simplified.

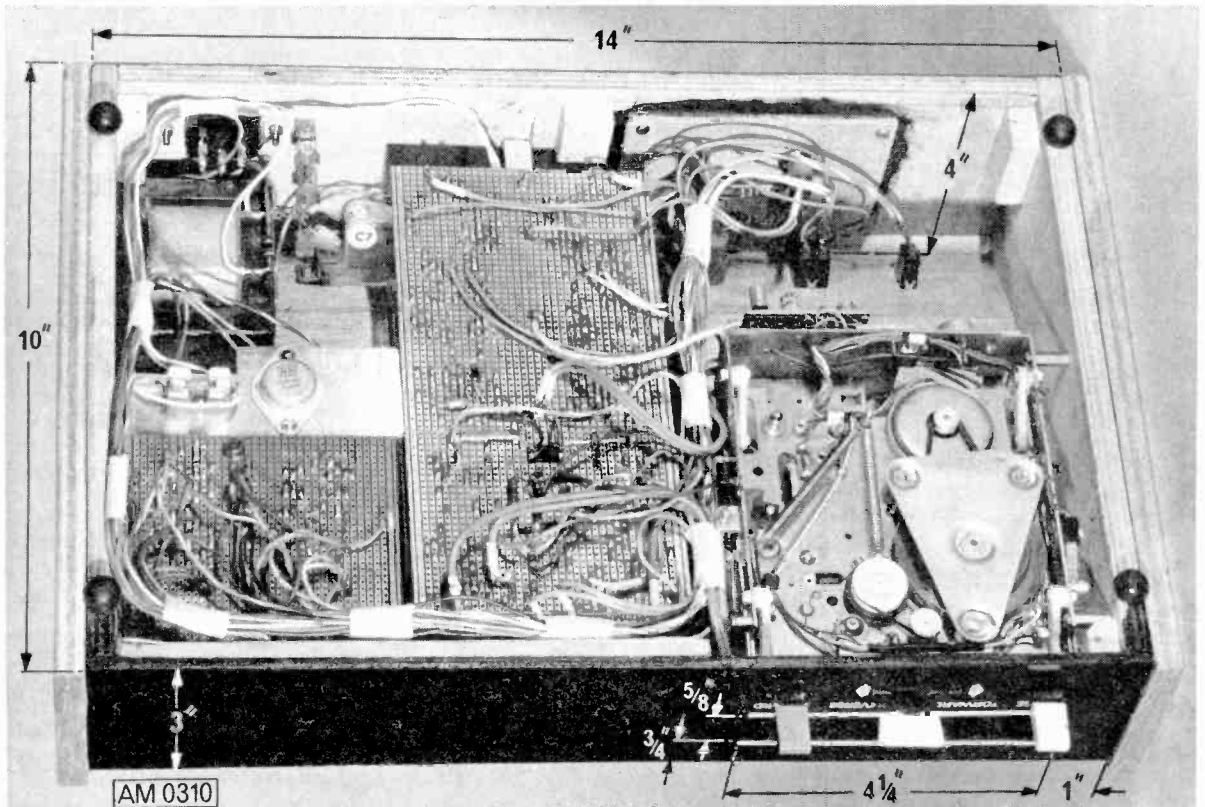


Fig. 9: Constructional information for the Ascot cabinet and cassette loading slot.

\* Hamilton Electronics Ltd.

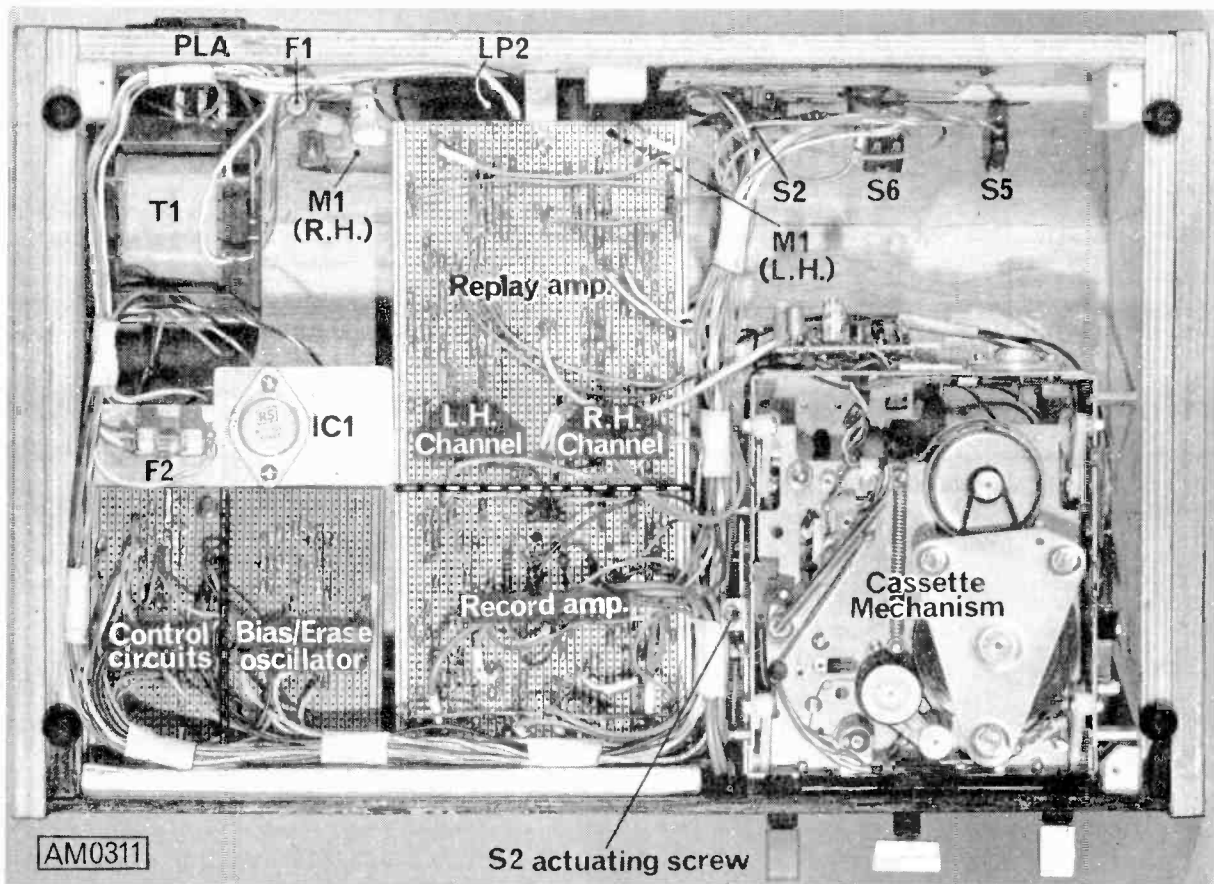


Fig. 10: Wiring guide between the circuit boards, deck mechanism and individual components.

We suggest that the following sequence of construction be followed, with careful reference to the diagrams at each stage:—

1. Build cabinet.
2. Fit slider controls, VU meters, lamps and switches.
3. Make up and fit supporting metalwork and transformer etc. to inside of cabinet.
4. Attach leads to heads, switch, control unit etc. of deck mechanism and mount deck mechanism in cabinet. The leads will be terminated later.
5. Build up electronic panels, Figs. 11 and 12, being particularly careful to check for accuracy of construction.
6. Fit panels to metalwork and observe that all parts fit accurately mechanically.
7. Connect panels to the remaining parts of the machine as shown in the wiring diagram, Fig. 10. Once the machine has been completely constructed, **RESIST THE TEMPTATION TO PLUG IN AND SWITCH ON STRAIGHT AWAY!**

## TESTING

Using a meter, check that no short-circuits are present on any of the supply rails A, B or C, Fig. 2. Likewise, check the supply line to the motor control circuit, which is taken off prior to the solid-state regulator. Having checked these points, fuses F1 and F2 may remain in while F3 is removed.

Power can now be applied to the deck mechanism. The motor should run when a cassette is inserted


and +12V should be available at the supply side of F3 fuseholder. This being so, F3 can be inserted. Using a cassette which does not have any important material recorded on it, the machine can be switched on when the cassette compartment lamp should light. On pressing the record button the record lamp should light and the relay will operate. Releasing the cassette and re-inserting it should restore the machine to the play mode. Voltages on the supply rail A, B and C may now be checked. In the play mode, rail A should read just under 11V. When pressing the "check record" button, rail B should assume +12V. When "record" button is pressed, rail A should move to zero, while rail C assumes nearly 12V with rail B at about 11.5V.

When all the supply rail switching has been proved to be operating correctly the machine may be connected to an amplifier, and a preliminary check made, using a recorded cassette, to prove that the playback amplifiers are working. The pots VR4 for left and right channels, should be set to the half-way position for this test. If everything is working out well, results on playback at this stage should be quite acceptable, although the threshold level of the noise-limiting circuit will need to be finally adjusted. As the dual sliders of the slide controls double up as record level and variable line out potentiometers, they will have to be set correctly to provide the appropriate input level for the amplifier used. This approach has obviated the need for special arrangements to cope with the DIN and phono standards.



RIGHT HAND CHANNEL

LEFT HAND CHANNEL

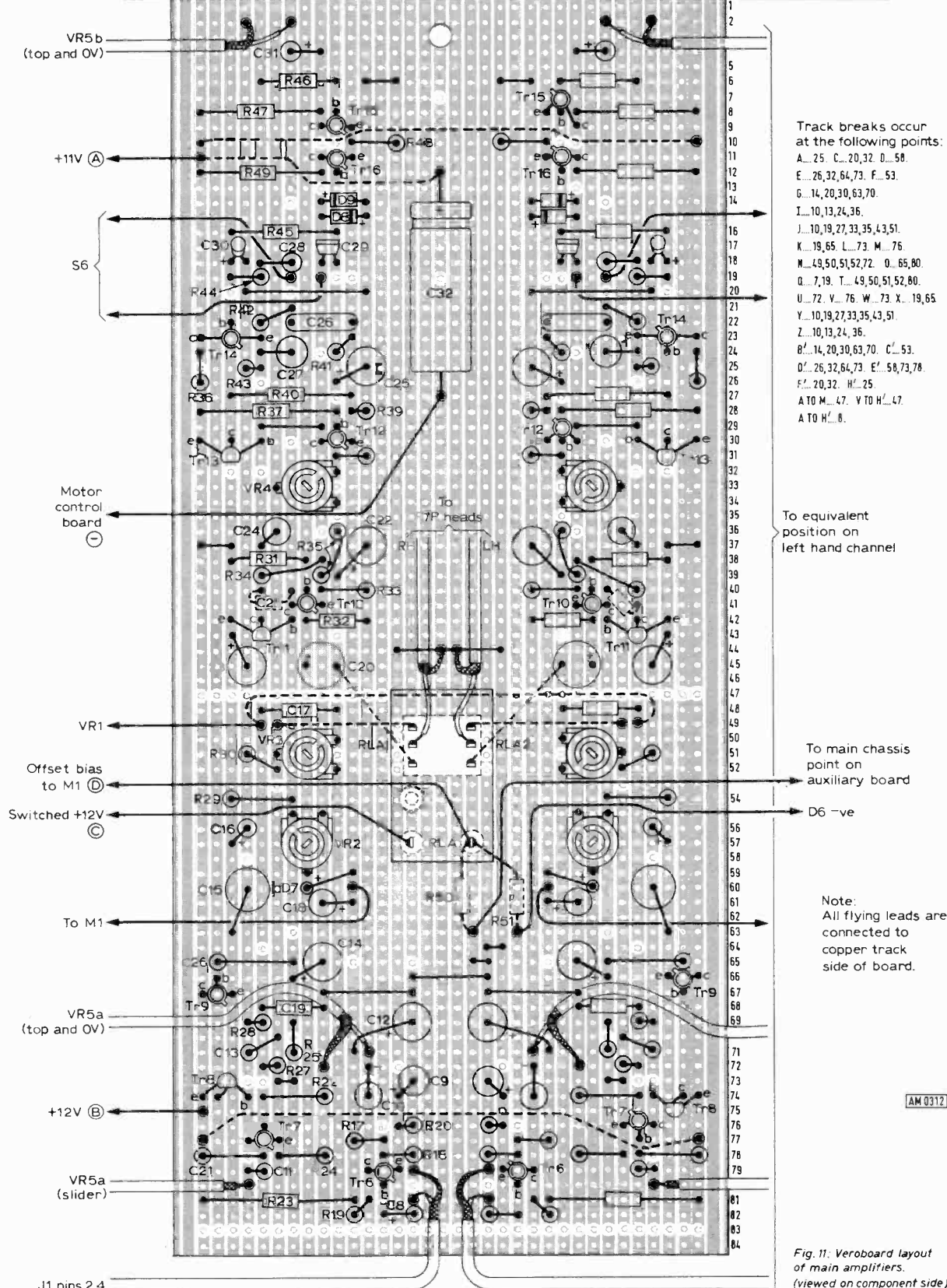

Track breaks occur at the following points:  
 A...25 C...20,32 D...58.  
 E...26,32,64,73 F...53.  
 G...14,20,30,63,70.  
 I...10,13,24,36.  
 J...10,19,27,33,35,43,51.  
 K...19,65 L...73 M...76.  
 N...49,50,51,52,72 O...65,80.  
 Q...7,19 T...49,50,51,52,80.  
 U...72 V...76 W...73 X...19,65.  
 Y...10,19,27,33,35,43,51.  
 Z...10,13,24,36.  
 B'...14,20,30,63,70 C'...53.  
 D'...26,32,64,73 E'...58,73,78.  
 F'...20,32 H'...25.  
 A TO M...47 V TO H'...47.  
 A TO H'...8.

To equivalent position on left hand channel


To main chassis point on auxiliary board

D6 -ve

Note: All flying leads are connected to copper track side of board.

AM 0312

Fig. 11: Veroboard layout of main amplifiers. (viewed on component side)

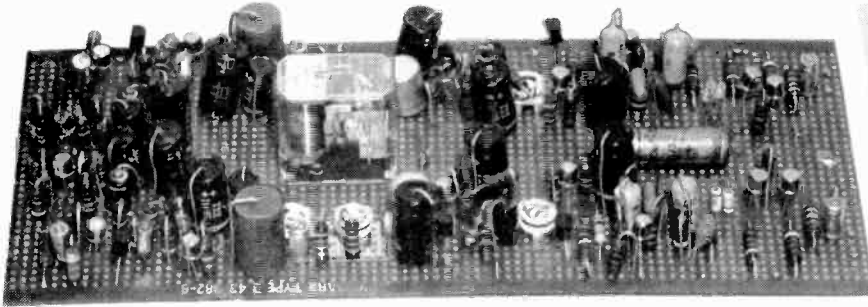

Main circuit board and relay, shown in detail at left. Note that connecting leads are taken from the printed rail side of the board.

AM 0313


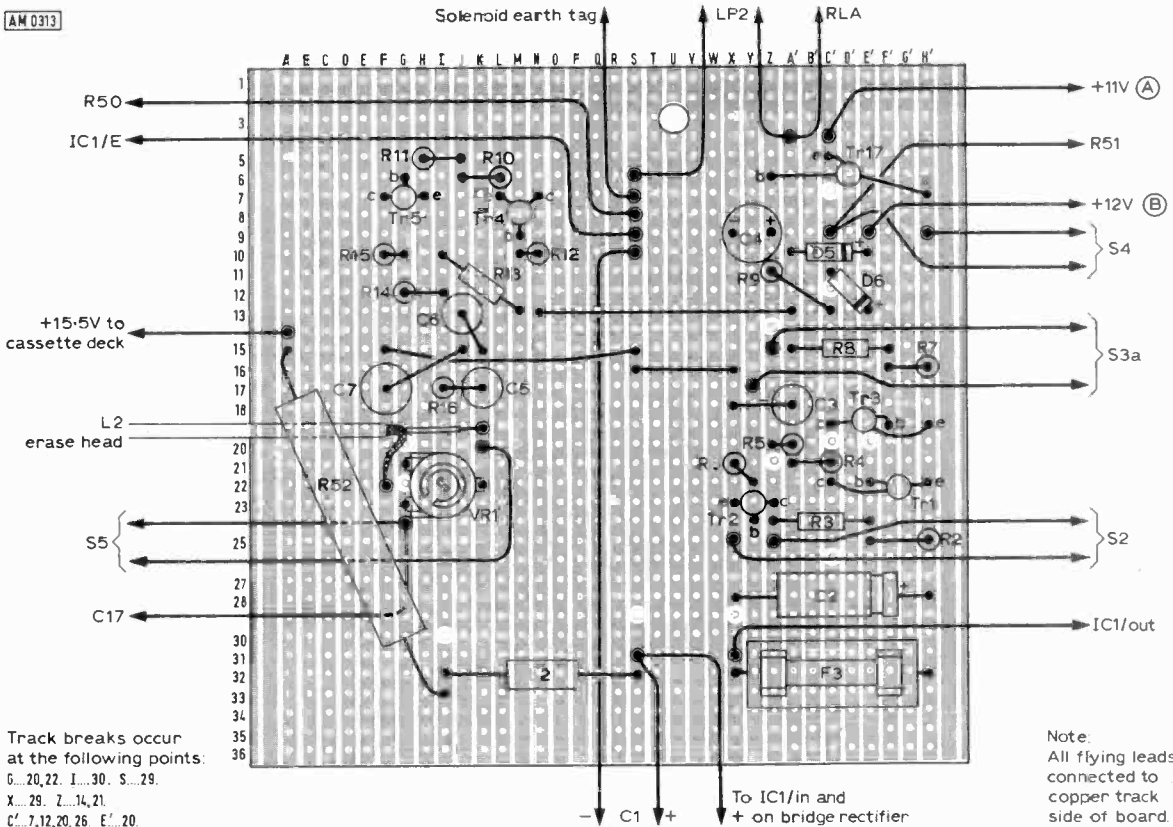


Fig. 12: Auxillary component board layout. The finished board is shown below. R52 and L1 are reversed for convenience, compared to Fig. 2, Part 1.

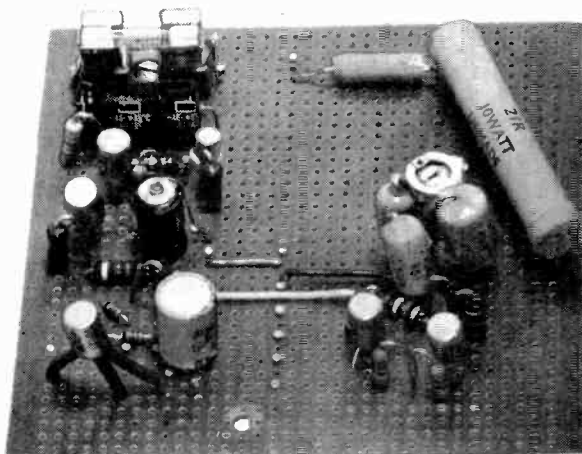

## FINAL ADJUSTMENTS

There now follows the complete setting-up procedure. If any part of the setting-up cannot be achieved correctly a fault must exist in the machine which should be rectified before going any further. The first paragraph of the setting-up procedure repeats instructions already given. It is included to ensure that the overall instructions are complete.

1. Playback check. Switch to play, use pre-recorded tape if test tape not available, and with noise limiter off, adjust VR4 to minimum position (i.e. all track in circuit) and VR5 (slider control) to set satisfactory LINE out level for amplifier.
2. Adjust head position with azimuth screw to provide crispest top response.
3. Switch on noise limiter and turn up VR4 on each channel until best top response, consistent with minimum distortion, is obtained. Too much gain will overload the output stages.

4. Switch to record, and with no signal input, check that machine erases a previously recorded tape. If an oscilloscope is available, a 50V peak-to-peak sinewave should appear across the erase head.
5. Insert chromium dioxide ( $\text{CrO}_2$ ) cassette, and by making repeated recordings at low input level, adjust pots VR3 for best quality of recording. If oscilloscope is available, adjust for 25V peak-to-peak signal (which corresponds to approximately 9V RMS).
6. Switch to standard tape (it does not matter if  $\text{CrO}_2$  cassette is left in at this stage) and adjust VR1 for a 20 per cent reduction of bias voltage across record/play head. The oscilloscope or a multimeter can be used for this test.
7. Check recording quality on standard tape. An improvement may be achieved by repeated tests using different settings of VR1.
8. Make recordings using progressively greater inputs until distortion sets in. Back off to satisfactory position, then adjust pots VR2 until meters show peak readings at level 10. If oscilloscope and signal generator are available, inject 1kHz signal, adjust for 3V peak-to-peak at emitter of Tr9, then adjust VR2 for level 10 reading on VU meter.

Having set up the machine according to the foregoing instructions, it should be possible to record and play back. It is important to realise however, that the machine can be overloaded by excessive input. Ideally, the input level at LINE should be such that the slider level controls need to be set half way in order to obtain a peak level indication.

It is possible for the input stage itself to be overloaded by excessive signal, so that the input to the level control potentiometers is itself distorted. Obviously, the only adjustment possible under these conditions is the setting of the optimum level of an already distorted signal!

## USING HEADPHONES

Should headphones be thought to be necessary then the circuit shown in Fig. 13 could be incorporated. This is one channel only, of course, but both channels could be built up on a small piece of veroboard and attached to the inside of the cabinet.

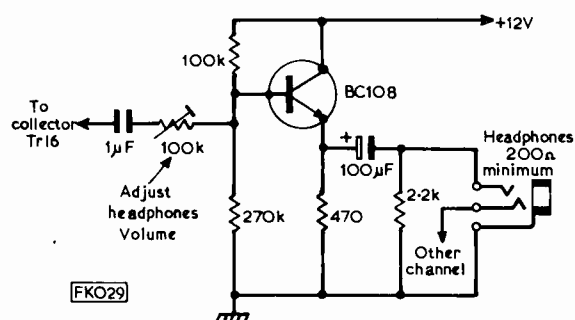


Fig. 13: Optional circuit to permit the use of headphones, one channel only being shown here.

The circuit as shown will operate on replay only although it might be possible to utilise the unused contacts on the relay to switch the input from the

replay to the record amplifier so that both functions can be monitored on headphones.

## MORE ON DISTORTION

After completing the setting-up procedure it was found that some distortion was evident on certain commercial pre-recorded tapes and this was traced to the noise limiter circuitry, Tr15/16. The circuit was modified by splitting R48 and adding a pre-set potentiometer as shown in Fig. 14. Adjustment of the pot allows additional emitter feedback to be applied without altering any DC condition.

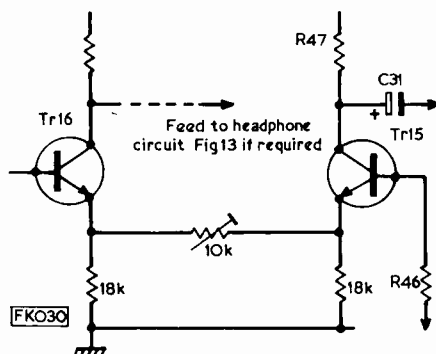


Fig. 14: Suggested modification to the noise limiter circuit, discussed in the text. Again, only one channel is shown.

Careful setting of the new pot and VR4 will enable optimum noise suppression to be obtained consistent with no overload condition. With the new pot set at mid position the gain of the stage approximates to unity while the noise should be down about 12dB, in theory.

## NOTES

It has been the purpose of this series to provide details for constructing a tape recorder which will compare favourably with commercial models. The design approach was made bearing in mind the requirements, capabilities and facilities of the home constructor. As a result the machine does not represent an attempt to mimic commercially available apparatus.

Again we stress that care is needed at all stages. Impetuosity invariably leads to regrets and construction should be undertaken steadily and methodically. A couple of extra days spent on construction could well avoid a week's effort to rectify mistakes, besides avoiding expensive "blow-ups".

Every effort has been made in the design to ensure "repeatability" of the circuits. The frequent use of complementary transistor stages with heavy negative feedback is the most significant factor which guarantees that all the circuits will yield the same performance. If the setting-up procedures are accurately followed the performance specification attained will be:— Overall response 50Hz to 9kHz on standard tape, 50Hz to 11kHz on chrome tape. Typical signal to noise ratio 46dB although these are all conservative figures.

Standard tape is, of course cheaper, but chrome dioxide ( $\text{CrO}_2$ ) tape will yield the best signal-to-noise ratio. It will be found that the top response of the chrome tape is higher than the standard tape,

# Complete the coupon and we'll send you our new catalogue. Completely free.



The new Heathkit catalogue is now out. Full as ever with exciting, new models. To make building a Heathkit even more interesting and satisfying.

And, naturally, being Heathkit, every kit is absolutely complete. Right down to the last nut and bolt. So you won't find yourself embarrassingly short of a vital component on a Saturday evening—when the shops are shut.

You'll also get a very easy to understand instruction manual that takes you step by step through the assembly.

Clip the coupon now and we'll send you your free copy to browse through.

With the world's largest range of electronic kits to choose from, there really is something for everyone.

Including our full range of test equipment, amateur radio gear, hi-fi equipment and many general interest kits.

So, when you receive your catalogue you should have hours of pleasant reading.


And, if you happen to be in London or Gloucester, call in and see us. The London Heathkit Centre is at 233 Tottenham Court Road. The Gloucester showroom is next to our factory in Bristol Road.

At either one you'll be able to see for yourself the one thing the catalogue can't show you.


Namely, how well a completed Heathkit performs.

Heath (Gloucester) Limited, Dept. PW-45, Bristol Road, Gloucester, GL2 6EE. Tel: Gloucester (0452) 29451.

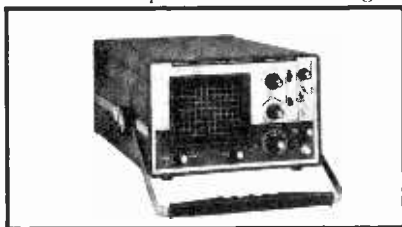A new oscilloscope from the Heathkit range.



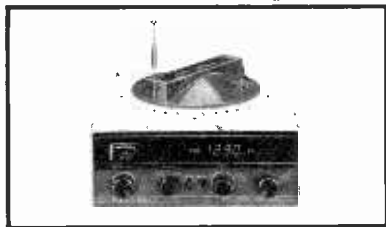Marine direction finder with digital read-out.



Stereo cassette deck with built-in Dolby.



## The new Heathkit catalogue. Out now. FREE.

To: Heath (Gloucester) Limited, Dept. PW-45, Gloucester, GL2 6EE. Please send me my free Heathkit catalogue.

Name \_\_\_\_\_ Address \_\_\_\_\_


Postcode \_\_\_\_\_

Remember easy terms are available with the Heathkit Monthly Budget Plan.





# BIG Discounts

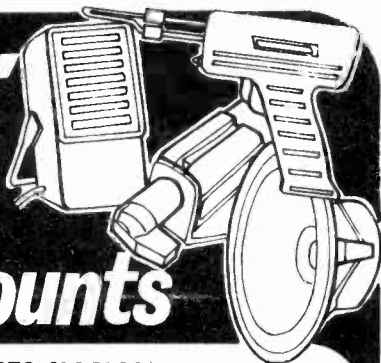

## ALL PRICES INCLUDE V.A.T.

SPEAKER BARGAINS		£	GOODMANS 6 1/2" 8 ohm		£
EMI 13" x 8" 3, 8 or 15 ohm	Plain	2.05	Dualcone	2.15	
With Co-Axial Tweeter	8 ohms only	2.20	ELAC 6 1/2" 8 ohm Dualcone	2.15	
Twin Tweeter 8 ohm only		3.95	ELAC 8" 8 ohm Dualcone	2.30	
Type 350 8 or 15 ohm.			ELAC 8 ohm Dualcone 10 watt	3.50	
20 watt		7.95	7" x 4" 3 or 8 ohm	1.00	
6 1/2" 8 ohm, 10 watt		2.60	ADAstra 10" 8 or 15 ohm,		3.55
8" 8 ohm, 10 watt		4.50	10 watt		
12" 8 ohm, 20 watt		6.70	BAKER GROUP 25 12" B or		7.95
8" x 5" C/Mag. 5 watt		1.40	15 ohm; 25 watt		
8" x 5" Dualcone		2.55	P. & P. 40p per speaker		
8 ohm, 10 watt			5" 8 ohm, C/Mag.		.85
			2 1/2" 8 ohm or 64 ohm		.55
			P. & P.		.15
TWEETER & CROSSOVER			Dome Tweeter 8 ohm, 30 watt		5.60
EMI 3 1/2" 3 or ohm C/Mag.		1.30	Crossovers CN23 (3 ohm),		
Cone Tweeter 8 or 15 ohm,			CN28 (8 ohm), CN216 (16		
10 watt		2.60	ohm)		1.30
Cone Tweeter 8 ohm, 3 watt		1.45	P. & P.		.10
Horn Tweeter 8 ohm, 20 watt		6.40			
KIT FORM CABINETS TEAK VENEER			18 x 12 x 9 with 13" x 8" cutout		4.75
12 x 12 x 6 with 8" x 5" or			for EMI 350		
6 1/2" and 3 1/2" cut out.		3.40	P. & P. ea.		.50
17 x 10 x 9 with 8" or 13" x 8"		4.25			
cutout					
MICROPHONES			TW209		5.75
CM70 Planet stick metal,			CONDENSER MIKE 600 ohm,		9.35
switch crystal		1.55	uni-dir		
DM160 Dynamic omni-dir.			Cassette Stick Mike with R.		
ball metal		4.90	Control on/off switch		1.50
UD130 50K/600 ohm, uni-dir			(2.5 & 3.5 mm J/Ply)		.30
ball metal		6.40	P. & P.		
SOLDERING IRONS			X25 25 watt (low		2.00
ANTEX CN240 15 watt		2.00	isakage)		.15
SK 1 Kit (15 watt Iron					
2 spare Bib etc.)		3.40			
CARTRIDGES & STYLII			SONOTONE		
ACOS GP91/25C or 35C ster.			9TAHC or 9TAHC/G Diam.		1.80
comp.		1.00	3509 Ster. ceram. Diam.		1.90
GP93/1 or 95/1 ster.			GOLDRING G850		2.95
cryst.		1.35	G800		3.95
GP94/1 or 96/1 ster.			G800E		6.90
ceram.		1.75	P. & P.		.15
GP101 cryst. comp.		0.80	D. Diamond Stylil for above.		1.25
GP104 ster. ceram.		1.65	G800/G850		1.95
BSR X5M or X5H cryst. comp.		1.70	G800E		3.95
SX6M or SX6H cryst.			P. & P.		.05
comp.		1.90			
SC5M ster. ceram.		2.60			
CALCULATORS SINCLAIR			Scientific		19.95
Cambridge		12.95			
BATTERY ELIMINATORS			12v d.c. Input (specify output)		2.30
240v Input 6, 7.5 or 9		2.95	at 300mA		.15
			P. & P.		
TAPES			PLASTIC LIBRARY CASES		
Std.	LP	DP	For 5" Reels		18p
5" 50p	65p	1.00p	5 1/2" Reels		22p
5 1/2" 65p	80p	1.40p	7" Reels		25p
7" 80p	1.10p	1.80p	P. & P. 1-3, 9p ea. 4 or more, lot 35p		
LOW NOISE CASSETTES			Cassette Cases		10p
C60	1-5	6-10	Cassette Head Cleaner		40p
C90	35p	33p	P. & P. 1-5, 5p ea. 6-10, 20p lot		11-20, Post Free.
C120	45p	43p			
	55p	52p			
BIB ACCESSORIES			WHARFEDALE SPEAKER BARGAINS		
Tape Editing Kit	Ref. 23	1.35	Linton 2 Kit (pr)		19.95 1.50
Recording Tape			Glendale 3 Kit (pr)		33.50 2.00
Splicer	Ref. 20	1.15	Dovedale 3 Kit (pr)		52.00 2.00
Cassette Tape, editing Ref. 24		1.50	Denton 2 Speaker (pr)		30.00 2.50
Cassette Salvage Kit Ref. 29		.45	Linton 2 Speaker (pr)		39.50 2.50
12's Cassette Case Ref. 34		£1.50	Dovedale 3 Speaker		(each) 42.00 2.50
Sylus Balance	Ref. 32A	1.20	Glendale 3 Speaker (pr)		57.00 3.50
Spiral Lever	Ref. 46	.50	Kingsdale 3 Speaker		(each) 59.95 4.00
Hi-Fi Stereo Test Cassette		2.10			
Groove-Kleen Record Cleaner		1.90			

Send 25p for COMPLETE CATALOGUE, refundable upon first order. ALL OUR MERCHANDISE IS FULLY GUARANTEED. Subject to manufacturer increase and availability.

# Riversdale Electronics

Mail Order Department **PW4**

P.O. Box 470, Manchester M60 4BU.

Make light work  
of wiring

with the **NEW**  
**SELF ADHESIVE**  
**WIRE STAPLES**



Countless uses in industry and offices

\*QUICK AND EASY TO APPLY -  
EVEN IN AWKWARD PLACES

\*SAVES DAMAGE TO WOOD AND PAINTWORK  
\*STICKS ON INSTANTLY: HOLDS WIRE FIRMLY

You'll save enormous time and trouble with the new Brandauer adhesive staple. Just peel off the backing strip and press staple into place. Then bend clips over to hold wire firmly in position. No messing with pins, tacks, soldering or drilling. No damage to woodwork, e.g. skirting boards. Use the Brandauer Staple for any wall, frame or cabinet wiring jobs — it's wonderfully easy for fitting in those awkward corners.

Send now for details to:

SPECIAL PRODUCTS DISTRIBUTORS LTD.  
81 Piccadilly, London W1V 0HL. Tel: 01-629 9556.

- ★ ELECTRONIC PIANO KIT
- ★ SYNTHESISER KIT
- ★ ELECTRONIC ORGAN KITS



There are five superb Electronic Organ kits specially designed for the D.I.Y. enthusiast. With the extreme flexibility allowed in design, you can build an organ to your requirements which will compare with an organ commercially built costing double the price.

Portable organ with 4 octave keyboard. £145.29. ★ Console organ with 5 octave keyboard. £250.93. ★ Console organ with 2 x 4 octave keyboards and 13 note pedal board. £470.65. ★ Console organ with 2 x 5 octave keyboards and 32 note pedal board. £680.00. ★ Console organ with 3 x 5 octave keyboards and 32 note pedal board. £960.00. ★ W/W Sound Synthesiser Kit. £130. ★ W/W Touch Sensitive Electronic Piano. £100. 2 speed Leslie type speaker units Hi-Fi Horn unit £70. Mid-range speaker unit £60. Base unit £50.

All components can be purchased separately, i.e., semiconductor devices, M.O.S. master oscillators, coils, keyboards, pedal boards, stop tabs, draw bars, key-contacts, etc.

Send 50p for catalogue which includes 5 x 10p vouchers or send your own parts list, enclosing S.A.E. for quotation.

## ELVINS ELECTRONIC MUSICAL INSTRUMENTS

12, Brett Rd., Hackney, London E8 1JP. Tel. 01-986-8455. 8, Putney Bridge Rd., London SW18 1HU. Tel. 01-870-4949. 40a/42a, Dalston Lane, Dalston Junction, London E8. Tel 01-249-5624.

Business Hours:— Open 10am-7pm Monday to Saturday  
Closed all day Thursday  
Open 10am-1pm Sunday

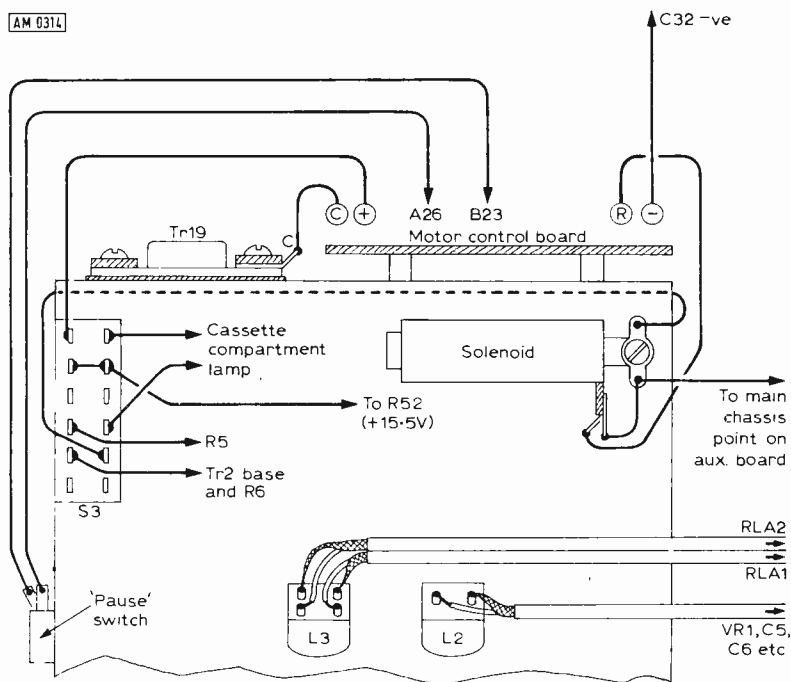


Fig. 15: The cassette deck mechanism used by the author was supplied to him complete with the motor control board etc. wired in. This diagram shows how the board of Fig. 8 and Tr19 are connected to the bare deck as now supplied. Microswitch S2 is mounted on a metal bracket fixed to the deck and cabinet. It is operated by the head of a 1¼ in. 6BA screw attached to the drilled bracket on the 'Record' switch slide mechanism.

so that an improvement in signal-to-noise ratio is achieved by turning down the treble control on the amplifier when chrome tape is being used. The difference in performance is generally very noticeable. Use of the noise limiter circuit will depend upon the discretion of the user at any time, and will obviously be affected by the type of tape in use and the recorded programme material.

## MAINTENANCE

No machine will run perfectly without occasional maintenance. The usual cause of trouble with cassette machines is dirty heads, which cause poor recording and playback, with weak top response. A non-uniform deposit on the heads will cause one channel to be affected more than the other. Once the head has suffered wear, it has to be replaced, so good quality tape should always be used as cheap tape usually has a rough surface which wears away the head besides depositing oxide on the heads, pinch roller and guides. Deposits are cleaned off using soft tissue paper soaked in methylated spirits.

Sometimes a defective cassette can cause difficulty. The take-up hub can jam, so allowing tape to spill over the pinch roller and capstan. A loop of tape can then wrap itself around the pinch roller or capstan shaft so that the tape winds off both parts of the cassette on to the roller or shaft until the machine jams completely. The only way to release the tape then is by careful removal and unwinding, cutting with a razor blade if necessary. The cassette itself is generally a write-off.

Jamming cassettes can sometimes be eased by giving them a healthy slap on one side against a fairly solid surface. This causes the tape to settle evenly. Uneven winding can cause the tape to jam against the sides of the cassette casing.

## MOTOR QUERIES

Goldring-Lenco report that some readers constructing the Kempton or Ascot projects have complained to them that the motor in the cassette deck mechanism is marked 3.5V believing that it ought to be 12V. Some readers have even returned decks to Goldring-Lenco demanding correct replacements.

The motor as supplied is CORRECT! The motor control board, fed from a 12V line, ensures that the correct voltage, nominally 4 to 4.1V, is applied to the motor.

This inconvenience to Goldring-Lenco could have been avoided if readers had directed their queries to *Practical Wireless* in the normal manner.

Note:—

Fig.4 Part 1. Resistor R23 should be shown between C12 and R21 and not between R21 and the collector of Tr8. The circuit board of Fig.11 is correct.

Fig.5 Part 2. Resistor R36 should be shown between collector of Tr13 and C32. The circuit board of Fig.11 is correct.

Fig. 5 Part 2. The noise reduction switch marked S5 should be marked S6.

In the components list S5 should be given as a SPST miniature toggle switch and not as DPDT. Add to the components list:—S6 DPST miniature toggle switch. Fig.7 Part 2. The 'Pause' switch is part of the cassette deck mechanism and is wired, via a 15kΩ resistor, between the left-hand contact of the commutating switch and the positive line. Connect the resistor between points A26 and C26, Fig.8, connect pause switch wires to A26 and positive line B1/B23.

# HOTLINES

ON RECENT DEVELOPMENTS

## DIGI-WATCH

READERS of this page will doubtless remember my urging them not to be too eager to buy a digital watch, but to wait a while because I thought prices would come tumbling. I note that already, one company in the UK is offering a digital wrist watch with liquid crystal display (LCD) for less than £60. I still think prices will be lower before the end of this year so don't burgle those piggy banks yet.

## MINI TV CAMERA

Fairchild has been kind enough to send me a photograph of the latest television camera. Difference is that it is entirely solid state (those charge-coupled devices again). Not only that, but it measures only 3in. in diameter and is just 1½in. deep. Power consumption is a miserly 1.5W. Whatever is coming next in tiny TV cameras?

Well, I'll tell you—there really is a smaller one, very much smaller! I've just heard of a TV device which can be safely slid along arteries and other internal organs allowing physicians to take a front seat look at the inside of humans. The lens part is a mere 4mm. in size and inside that is a tiny motor which drives a rotating mirror system. Information is scant at this time but more should be in by the time the next "Ginsberg" page comes round. Before departing, one thing that all this super-miniaturisation raises is; how on earth do you service it?

## 1A SOLAR CELL

I note with some satisfaction that North sea oil will be happily squelching ashore later this year—all part of beating the energy crisis. From the US comes news that one company has managed to manufacture a 3in. solar cell which can supply one amp (1A) of current. Could be interesting and I'll keep you posted as and when details are obtained.

## ULTRASONICS

I've often thought that more use could be made of ultrasonic control. It isn't all that new in the realms of television since one or two companies already have ultrasonic channel changing; others also

include volume, brightness, etc. control also.

ITT Semiconductors recently released details of two new ICs which are specifically intended for ultrasonics. Good thing is that ITT isn't doing things by halves, it's launched one chip which is a receiver and another for the transmitter. The first pair cater for fifteen channels. The transmitter chip requires only a fairly simple diode matrix, a few Rs and Cs plus, of course, the transducer and runs off 9V. The external crystal suggested is a 4.433MHz job and, obviously, these ICs have the TV market very much in mind. However, the Amateur constructor may well see a superb chance to do some ultrasonic control



Fairchild solid-state camera

for models which are, say, only used indoors or in a limited space where range isn't too great. Another pair (transmitter and receiver) of ultrasonic ICs from the same company caters for 30 channel usage.

For those still not enamoured with ultrasonics, let it be known that a great deal of research is being carried out in a number of areas. In the medical field alone a number of ideas are in the pipe line. One such application is to use ultrasonics to detect and measure hardened arteries but without puncturing the skin. The National Heart and Lung Institute of America recently gave publicity to this multi-million dollar idea and experimental ultrasonic scanners are well to the forefront in this scheme.

Nearer to home, the Plessey Company is known to be "getting its feet wet" in a scheme involving the Government to ultrasonically monitor

the flow of water in tidal basins and, of course, in rivers.

## BODY-END-SPOT

Remember those large 1W resistors where, instead of an all-band colour code it was body-tip-spot? Then came bands only for the vast majority. But resistors are always getting smaller. Ever tried to read the colour code on a ¼W or even a 1/16W in a hurry? Now take it a stage further and think of the poor old manufacturers of tiny "chip" capacitors. These are minute little blocks with a tiny conductive strip at each end by means of which they are bonded directly into the circuit. It's all very well you ordering 500 chip capacitors of a certain value, especially if they all come together in a small polythene pack. But can you imagine these little items getting mixed up?—after all, some of them measure barely 0.05in<sup>2</sup>.


Not so for chip capacitor manufacturer Vitramon Inc. This company actually prints a letter of the alphabet in one of several colours on the chip capacitor itself. The letter plus colour forms a unique code which tells the capacitance of the chip in question. Please note all school teachers—A no longer stands for apple, it can mean 40pF 3V wkg.

## FLOPPY DISCS!

I note that a number of US giants are now firmly into the CCD technology and not only at the drawing board stage either. Intel has just announced a 16,384-bit memory using this technique. It is thought by many that the CCD-type memories will replace the current "floppy disc" types. These are just what their name implies. A thin disc (about 0.005in. thick) is just under 8in. in diameter with a large (about 1.5in.) hole in the middle. The whole disc is housed in a plastic envelope, usually square and about ½-3/16in. thick. The plastic case is filled with some form of very soft material which permits the disc to revolve—at about 360 r.p.m. This disc might hold over 3 million bits of information.


*Ginsberg*

## SUPERSOUND 13 HI-FI MONO AMPLIFIER

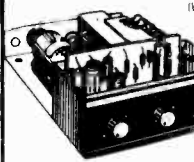

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohm. Frequency response 12Hz-30kHz  $\pm$  3dB. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/250V. PRICE £12.50. P. & P. 50p.

## DE LUXE STEREO AMPLIFIER

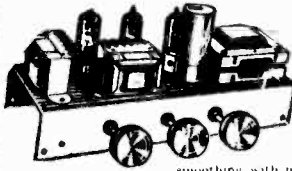

AC mains 200-240V. Using heavy duty fully insulated mains transformer. Full wave rectification giving adequate something with negligible hum as rectifier. 2 x ECL82 Triode Pentodes. £27.50 for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" w x 4" d. Overall height including valves 5". Ready built & tested to a high standard. £10.75. P.&P. 50p.

**POWER SUPPLY UNIT 200/240V.** A.C. input. Four switched fully smoothed D.C. outputs giving 6v. and 7.5v. and 8v. and 12v. at 1 amp on load. Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" x 3 1/2" x 2 1/2". Suitable for Transistor Radios, Tape Recorders, Amplifiers etc. etc. Ready built and tested. PRICE £5.20 P. & P. 35p.

**VYNAIR & REXINE SPEAKERS & CABINET FABRICS** ap. 54 in. wide. Our price £1.30 yd. length. P. & P. 15p per yd. (min. 1 yd.). S.A.E. for samples.

## HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 2.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240V. Supplied absolutely Brand New completely wired and tested with good quality output transformer. £4.20 P. & P. 40p BARGAIN PRICE

**FEW ONLY** High grade mains transformer with grain orientated lamination. Primary 200-240V. Secondary 18v. at 0.6 amps and 4.6 volts at 0.3 amps. Size 2" h x 2 1/2" w x 2" d overall. £1.35 plus 25p. P. & P.

**BRAND NEW MULTI-RATIO MAINS TRANSFORMERS.** Giving 13 alternatives. Primary: 0 210-240V. Secondary combinations 0.5-10-15-20-25-30-35-40-50v. half wave at 1 amp. or 10-0-10-20-0-20-30-0-30v. at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price £2.60 P. & P. 10p.

**MAINS TRANSFORMER** for transistor power supplies. Pri. 200/240V. Sec. 9 0 9 at 500 mA. £1.25 P. & P. 25p. Pri. 200/240V. Sec. 12-0-12 at 1 amp. £1.40 P. & P. 25p. Pri. 200/240V. Sec. 10-0-10 at 2 amp. £2.00 P. & P. 35p.

**3 VOLT RELAY** 100 mA single pole normally closed. 2 for 80p + 15p P. & P.

## GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 15Hz - 25kHz. Gain 20dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1 1/2". Brand new complete with instructions. Price £1.20p. P. & P. 15p.

## HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. Including many 1000's of British, U.S.A. European and Japanese transistors. ONLY 40p. Post 5p.

3 Reference Encyclopedias for Electronic Engineers and Designers, covering between them transistor characteristics, diode and transistor equivalents. Many thousands of up to date European types listed. Diode Equivalents, 90p. Transistor Equivalents, £1.00. Transistor Characteristics, £1.30. POST FREE. All three together, £3.00


## NEW ISSUE

Thyristor, Triac, Diac etc. encyclopedias £1.00. Post Free 8 pole 3 way 2 bank low loss Vaxley type switches 11" sections. Standard spindle, 2 switches 64p + 10p P. & P.

Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday Closed Wednesday.

All prices and specifications correct at time of press and subject to alteration without notice.
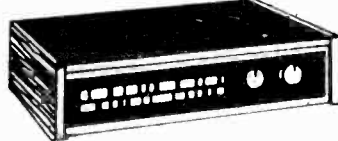
## HARVERSON MAINS OPERATED SOLID STATE STEREO FM TUNER



Enjoy fabulous stereo radio at this fabulous low introductory price!

Designed and styled to match our 10 + 10 amplifier but will suit any other standard stereo amplifier. The design incorporates the very latest circuitry techniques with high-gain, low noise IP stages. Automatic frequency control to 'lock-on' station and prevent drift. IC stereo decoder for maximum stereo separation. LED for stereo beacon indicator. Nominal output of tuner 100mV. Approximate size 12" wide x 8" deep by 2 1/2" high. Supplied ready built, fully tested and fully guaranteed (not available in kit form). Price £23.00 Post and Packing 50p.

## STEREO DECODER

SIZE 2" x 3" x 1 1/2" ready built. Pre-aligned and tested. Sens. 20-500 mV for 9-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £5.40 plus 10p. P. & P. Stereo beacon light if required 40p extra.



## SPECIAL BARGAIN OFFER!

Limited number of BSR IC23 Auto Changer De Luxe with light weight tubular arm and stereo cartridge. Brand new. ONLY £8.00 + P. & P. 60p.

**LATEST Hi Sensitivity Uni-directional slim-line condenser microphone** as used by many professionals. Very low acoustic feedback. Available hi impedance or low impedance. State which required. £13.50 plus 25p P. & P.

**LATEST ACOS GP11/18C mono compatible cartridge** with t/o stylus for LP/EP/78. Universal mounting bracket. £1.46. P. & P. 15p.

**CERAMIC STEREO CARTRIDGE.** Universal Mounting brackets and turnover stylus. 70mV per channel output. ONLY £1.75. P. & P. 10p.

**SCOTONE ST60 COMPATIBLE STEREO CARTRIDGE** T/O stylus Diamond Stereo LP and Sapphire 78. ONLY £2.27 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £2.78. P. & P. 15p.

**LATEST RONETTE T/O STEREO COMPATIBLE CARTRIDGE** for EP/LP/Stereo/78. £1.60 P. & P. 15p.

**LATEST T/O MONO COMPATIBLE CARTRIDGE** for playing EP/LP/78 mono or stereo records on mono equipment. Only £1.47. P. & P. 15p.

**QUALITY RECORD PLAYER AMPLIFIER MK. II** A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. PRICE £5.50. P. & P. 50p. ALSO AVAILABLE mounted on boards with output transformer and speaker. PRICE £6.70. P. & P. 60p.

## HI-FI LOUSPEAKER SYSTEM MK II

Beautifully made, simulated teal finish enclosure with attractive slatted front. Size 16 1/2" high x 10 1/2" wide x 9" deep (approx.). Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, H.F. tweeter unit and crossover. AVAILABLE IN NOMINAL 4 Ohm, 8 Ohm or 16 Ohm impedance (state which). OUR PRICE £9.50 (incl. Carr. 90p) Cabinet Available Separately £5.00, Carr. 90p. Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £8.00, Carr. 90p.

## LOUDSPEAKER BARGAINS

5in. 3 ohm £1.25, P. & P. 15p. 7 x 4in. 3 ohm £1.40, P. & P. 20p. 10 x 6in. 3 or 15 ohm £2.10, P. & P. 30p. E.M.I. 8" x 5in. 3 ohm with high flux magnet £1.70, P. & P. 20p. E.M.I. 13" x 8in. with high flux ceramic magnet with parasitic tweeter 3 or 15 ohm £8.50, P. & P. 30p. E.M.I. 13" x 8in. 3 or 15 ohm with inbuilt tweeter and crossover network £4.65, P. & P. 30p. E.M.I. tweeter. Approx. 3p. Available 3 or 8 or 15 ohms. £1.80 20p. P. & P.


**BRAND NEW.** Bakers Loudspeakers at substantial discounts. 12in. 15w. (H/D) Speakers, 3, 8 or 15 ohms. State which. Current production by well-known British maker. Now with 18Hz ceramic ferricobar magnet assembly £7.50. Guitar models: 25w £7.50, 35w £8.50, P. & P. 45p.

## "POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 1 1/2" x 1 1/2" x 1 1/2" deep. Weight 18oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20kHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £6.60 each. P. & P. 34p.

**NOW ALSO AVAILABLE:** 8" 10 watts r.m.s. 20 watt peak 40Hz-20,000Hz. Overall depth 1 1/2". Ideal for Hi-Fi or for use in cars. £4.32 + 25p P. & P.
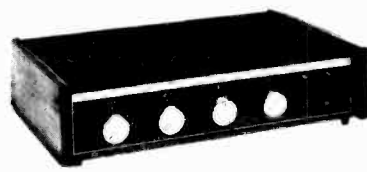
## HARVERSON SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohm. Compact design, all parts supplied including drilled metalwork high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response  $\pm$  60dB 12-30,000 Hz. Sensitivity:  $\pm$  3dB 12-15,000 Hz. Bass boost approx. to  $\pm$  12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall size 12" w x 8" d x 2 1/2" h.

Fully detailed 7 page construction manual and parts list free with kit or send 18p plus large S.A.E.

**AMPLIFIER KIT** £12.96 P. & P. 30p (Magnetic input components 33p extra)

**POWER PACK KIT** £4.32 P. & P. 40p  
**CABINET** £4.32 P. & P. 40p

(Post Free if all units purchased at same time) Full after sales service

Also available ready built and tested £28.08. Post Free.

Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc. and will then provide mixing and fading facilities for medium powered Hi-Fi Diatoneque use, etc.




## 3-VALVE AUDIO AMPLIFIER HA34 MK II

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" x 4 1/2" x 4 1/2". Incorporates ECC83, 1L84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc. wired and tested for only £25.50. P. & P. 45p.

**HSL "FOUR" AMPLIFIER KIT.** Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc £5.50 P. & P. 45p.
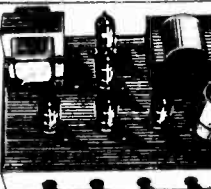
## 10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ohm speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 15p + SAE (Free with parts) All parts sold separately. ONLY £10.25 P. & P. 60p. Also available ready built and tested £14.00 P. & P. 70p.



## HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam ear-muffs. Wired and fitted with standard stereo 3/8 jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. PRICE £5.50. P. & P. 25p.

## PRICES INCLUDE VAT

# HARVERSON SURPLUS CO. LTD.

(Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

A few minutes from South Wimbledon Tube Station. SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. OF OVERSEAS ORDERS CHARGED EXTRA.





# REACTION

# TIMER



A. WILLCOX

**V**ARIOUS designs have been presented in the past for devices which measure the time taken for a person to react to a signal of some kind. Often a moving coil meter is used to display the individual's reaction time, usually by measuring the charge accumulated on a capacitor during the interval between the occurrence of the signal and the person's responding by pushing a switch.

## THE DISPLAY ARRANGEMENT

In the present circuit the display takes the form of a series of six light emitting diodes (LED's), the illumination of each representing some discrete interval of time after the signal has been given.

A pair of contacts is provided which, when touched, halts the passage of light along the LED display, leaving one LED illuminated to give the reaction time.

The signal is provided by the switching off of another LED which is normally on. The LED's in the display then come on one after another. If no reaction is made before the last light goes off the signal light comes on again, and the cycle repeats automatically.

If, however, the contacts are touched in time the cycle is suspended, and the LED which indicates the reaction time remains illuminated until contact is broken.

## ADVANTAGES

Obviously some accuracy is sacrificed by indicating time in discrete steps, but there are advantages in using this type of display.

First, the time interval measured by the display can be adjusted to cover the reaction times most likely to be encountered, whereas with a meter movement, if f.s.d. is arranged to indicate a suitable maximum time—say, 1/5 second—then the first half of the scale from zero to 1/10 second is redundant, because it would represent times which would not normally be achieved.

Also, with the LED display the light is stopped immediately contact is made. With a meter movement, however, there is a time lag before the meter pointer comes to rest. This is caused by the mass of the movement plus any damping, which prevents the meter from following faithfully the charge on the timing capacitor; a factor which would perhaps give the uninitiated a lack of confidence in the time indicated.

These points, together with the fact that a more robust and slimline construction was possible, seemed to justify the extra complications involved. The cost of a sensitive meter movement is certainly greater than that of the LED's and associated components, and so the choice is justified also on economic grounds.

## CIRCUIT DESCRIPTION

The complete circuit is given in Fig. 1. Upon switching Tr3 conducts forward bias being provided by R3. Resistors R2 and R5 limit the collector current to 20mA. This current flows through the signal light LED D3 which is therefore illuminated.

About 3.6 volts are developed across R5, biasing on Tr6, and so providing a path for current which would otherwise be charging C2.

It is the charge accumulated on this capacitor that is later monitored to indicate the time interval. R2 has 2.4 volts developed across it, forward biasing Tr7 which in turn removes the bias for Tr8. Thus, the supply to the LED display via Tr8 is removed.

Resistor R2 is also the emitter resistor for Tr1, and so the 2.4 volts developed across it keeps Tr1 cut off while C1 charges via R1.

The time constant here is long, and only after six or seven seconds does the base of Tr1 become sufficiently negative for it to start to conduct. As it does so some of the bias current to Tr3 now passes to Tr1, and so the collector current of Tr3 starts to fall, reducing the voltage across R2 as it does so.

This further assists conduction of Tr1, and the net result is that Tr1 is turned fully on and Tr3 is switched off rapidly.

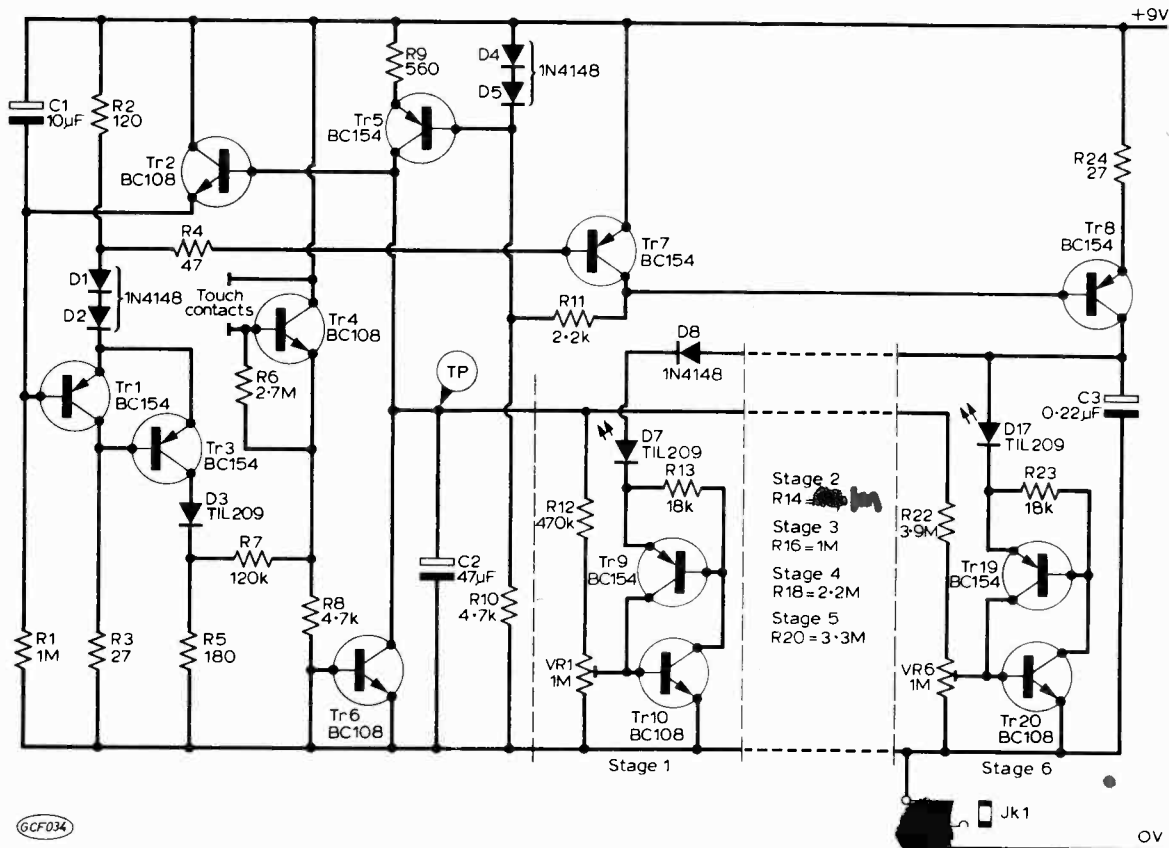


Fig. 1: Complete circuit diagram of the Reaction Timer. Only two stages of the display are shown, all being identical except for the resistor in series with the pre-set potentiometer. Values for the resistor are given.

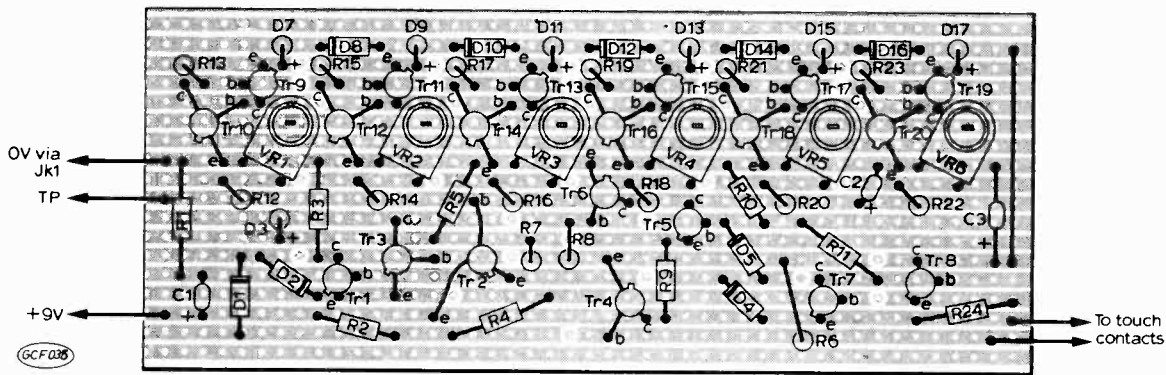


Fig. 2: Layout of the Veroboard with breaks in copper rails indicated. The cathode (+) of the TIL 209 is the longer lead.

LED D3 now extinguishes, providing the signal, and the bias for Tr6 is removed, so allowing the capacitor C2 to charge.


A constant charging current is provided by Tr5, its emitter voltage being fixed by the constant voltage (1.2V) across the diodes D4 and D5, and the value of R9 determining the current through the transistor; in this case 1mA.

By supplying the capacitor C2 with a constant current the voltage across it is a function of time, unaffected by any change in battery voltage. Also, the charge increases in a linear fashion, simplifying the calibration calculations.
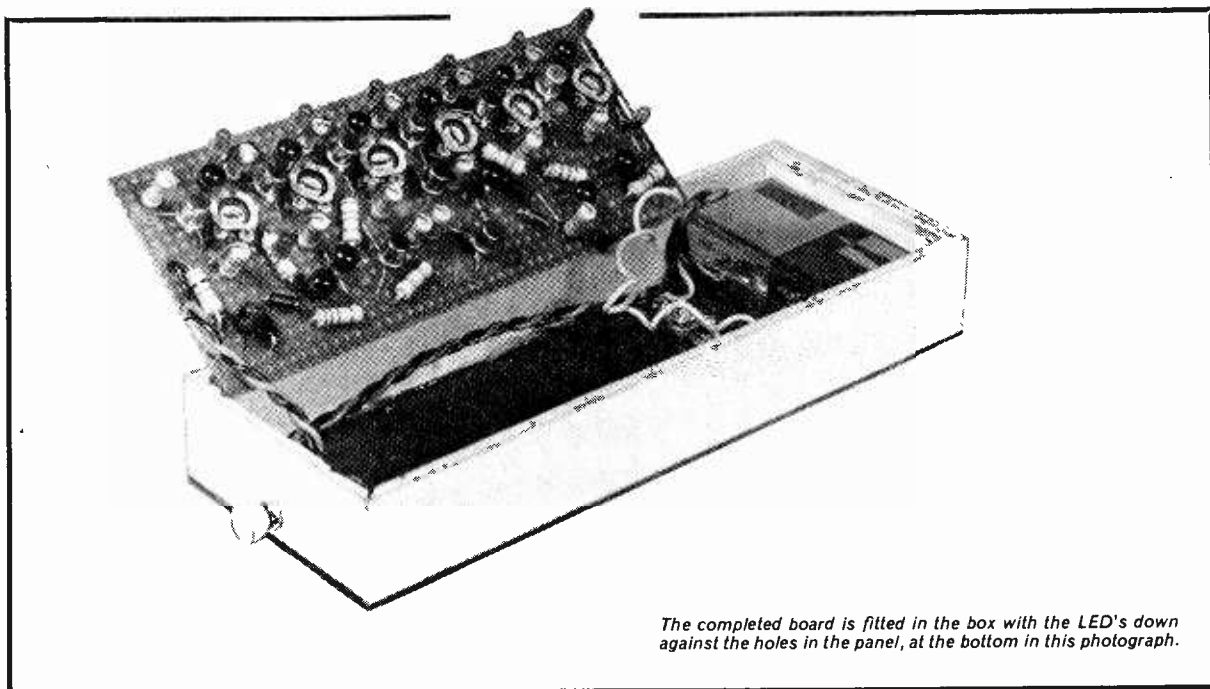
## DISPLAY DIODES

The voltage across R2 at this time is at a very low level because the current through it is now limited to 300 microamps by R3, and so Tr7 is turned off. Tr8, which supplies current to the display diodes, now receives bias from the forward voltage drop across D4 and D5 in common with Tr5. The current to the LED's is thus fixed by R24, whose value is chosen to provide 20mA.

Each LED in the display is driven by an n.p.n. and a p.n.p. transistor arranged so that they function as a sensitive thyristor. When the voltage on the base of the n.p.n. transistor exceeds 0.5V conduction starts. Each transistor then provides a bias path for the other, forming a rapid switch requiring only a minute current to activate it.



The completed board is fitted in the box with the LED's down against the holes in the panel, at the bottom in this photograph.

After a time interval of  $1/10$  second from LED D3 turning off, the voltage on C2 has reached 2.1 volts. If the slider of VR1 is in a position such that 0.5 volts appear on Tr1's base when 2.1 volts are present on C2, LED D7 will come on  $1/10$  second after D3 goes off, a path being provided through the diodes and Tr8.

When the time interval extends to  $1/9$  second the voltage on C2 has increased to 2.4 volts, and if the slider of VR2 is adjusted so that 0.5 volts appear on it when 2.4 volts are present at the top of R14, then LED D9 would come on and represent a time interval of  $1/9$  second. LED D7 is switched off in the process because the voltage at the junction of D8 and D9 is equal to the forward voltage of D9 only (typically 1.6 volts), and this is, of course, insufficient to cause D7 and D8 to conduct.

The process continues thus along the line, the illumination of each LED causing the cut-off of the one preceding it until the last LED, representing  $1/5$  second, is on.

## TOUCH SWITCH

If in the meantime the contacts are touched a small current flows into the base of Tr4, and is amplified sufficiently to turn on Tr6 again and short out the timing capacitor C2.

Although the voltage to all of the presets is in this way removed, whichever of the LED's was on at the time the contacts were touched remains on due to the self-maintaining action of the thyristor configuration of the lamp drivers.

The LED remaining illuminated represents the response time. For instance, the  $1/8$  lamp would indicate a response time between  $1/8$  and  $1/7$  second.

When contact is removed the capacitor is allowed to charge again, and once the voltage across it exceeds its previous value, the remaining LED's go through their normal sequence until the last LED comes on.

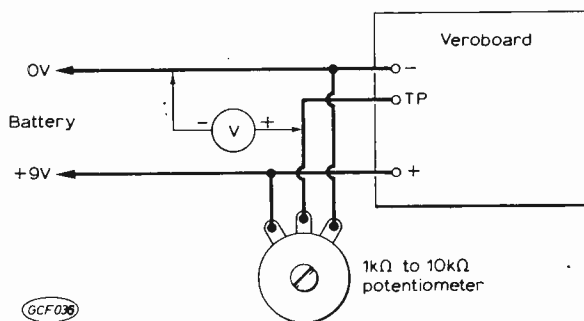


Fig. 3: Calibration circuit using a voltmeter and potentiometer.

## RESET

Once the last LED is on, some means must be provided to turn it off and switch the signal light back on. This is done in the following way: When the charge on C2 reaches the battery voltage minus 1.2 volts—corresponding to a duration of  $1/3$  second—Tr2 is brought into conduction (the emitter voltage is reduced by the forward voltage drop of D1 and D2 to achieve this) reducing the charge on C1 and thereby turning off Tr1, so allowing Tr3 to turn back on.

We are now back where we started with the signal light back on. So, as described above, the supply to the display LED's is now removed by the action of Tr7, and the last remaining lamp is extinguished.

## CONSTRUCTION

A suitable Veroboard layout is given in Fig. 2. The LEDs are best mounted last, as they are arranged

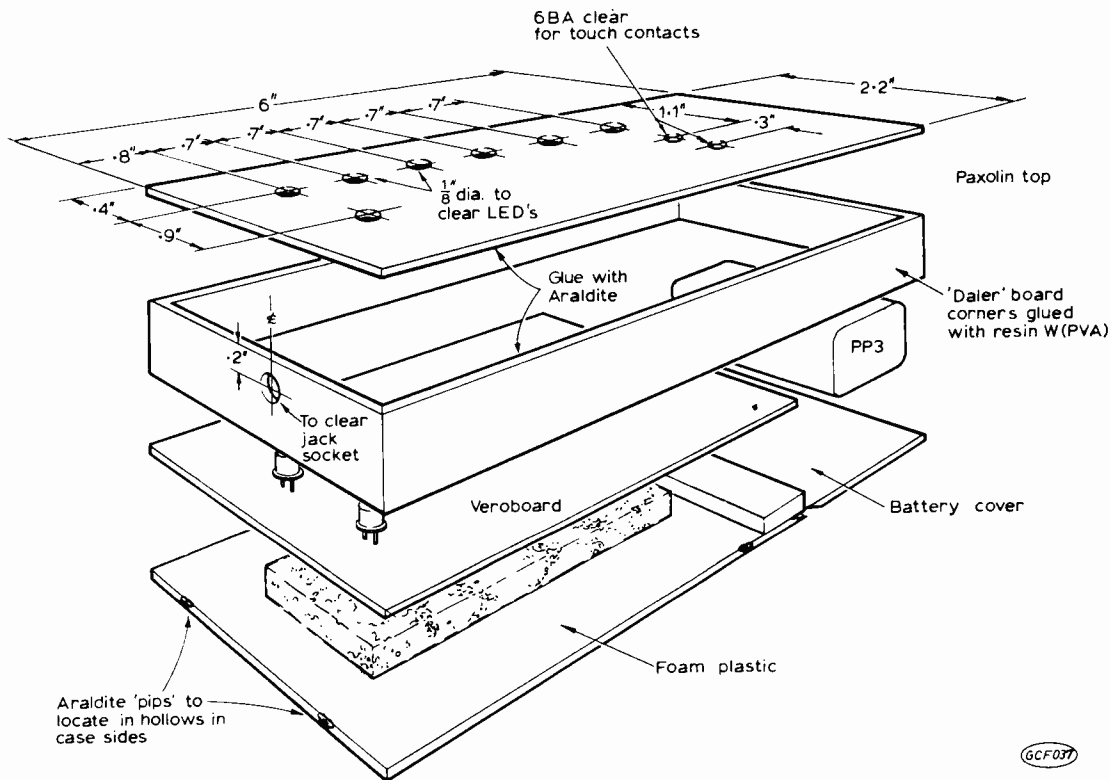


Fig. 4: Construction of the case, the sides and bottom being made from Daler board and the panel from paxolin.

## ★ components list

### Resistors

R1 1M $\Omega$	R13 18k $\Omega$	
R2 120 $\Omega$	R14 1M $\Omega$	
R3 27k $\Omega$	R15 18k $\Omega$	
R4 47k $\Omega$	R16 1M $\Omega$	
R5 180 $\Omega$	R17 18k $\Omega$	
R6 2.7M $\Omega$	R18 2.2M $\Omega$	(All $\frac{1}{2}$ or
R7 120k $\Omega$	R19 18k $\Omega$	$\frac{1}{3}$ W $\pm 10\%$ )
R8 4.7k $\Omega$	R20 3.3M $\Omega$	
R9 560 $\Omega$	R21 18k $\Omega$	
R10 4.7k $\Omega$	R22 3.9M $\Omega$	
R11 2.2k $\Omega$	R23 18k $\Omega$	
R12 470k $\Omega$	R24 27 $\Omega$	

VR1 to VR6 1M $\Omega$  miniature horizontal preset (6 off)

### Capacitors

C1 10 $\mu$ F 6.3V tantalum
C2 47 $\mu$ F 6.3V tantalum
C3 0.22 $\mu$ F 35V tantalum

### Semiconductors

Tr1, Tr3, Tr5, Tr7, Tr8, Tr9, Tr11, Tr13, Tr15, Tr17, Tr19 BC154 (11 off)  
 Tr2, Tr4, Tr6, Tr10, Tr12, Tr14, Tr16, Tr18, Tr20, BC108 (9 off)  
 D1, D2, D4, D5, D8, D10, D12, D14, D16 1N4148 (9 off)  
 D3, D7, D9, D11, D13, D15, D17 TIL209 (7 off)

### Miscellaneous

Jk1 Subminiature jack socket and plug  
 B1 PP3 9V battery  
 Paxolin for case top  
 Daler Board for case  
 1k to 10k potentiometer for calibration

to sit above the other components so that they protrude through the front panel.

The circuitry associated with each LED in the display is identical, with the exception of the value of the feed resistors to the presets. These are chosen to bring the presets to mid-range for the times allocated to them.

The sides and removable base of the case were constructed from "Daler Board," which is available from art dealers. This material has a good finish and is easily cut.

The top of the case was cut from paxolin and fixed with Araldite to the case sides. Two 6BA screws, with their heads filed flat, were used for the touch contacts. Fig. 3 gives details.

Because of its small size, a sub-miniature jack socket was used for an on/off switch, a jack plug being inserted to **switch the unit off**. This socket could also be used to plug in an external power supply, although the total current consumption of only 22 mA is easily supplied by a PP3 battery.

## CALIBRATION

Calibration is a simple matter, only a 1k $\Omega$  potentiometer and a voltmeter being required; the set-up is shown in Fig. 4.

All the presets are first turned fully anti-clockwise. The calibration potentiometer is also turned anti-clockwise. The unit is switched on and the signal light allowed to go off. It will now remain off because the voltage on C2 is kept down by the calibration potentiometer.

The next step is to turn up the calibration control until the voltmeter indicates 2:1 volts. VR1 is now advanced slowly until D7 switches on. Now the cali-

*continued on page 1130*



## AMATEUR BANDS

by Eric Dowdeswell G4AR

It is good to report that letters are still coming in on the subject of running a competition in this column. Unfortunately no-one has yet come up with a method of confirming the reception of a station other than by the virtually impossible method of getting a QSL card, difficult often for the transmitting amateur himself, let alone the SWL! A tape recording was frequently suggested but then not everyone has a recorder, although one must admit that they are remarkably cheap these days. However I have concluded that this is possibly the only way out and I am in the process of formulating some rules based on recordings.

It is a pity that the log itself cannot be accepted but it is a fact of life today that it is all too easy to log stations as worked by, say, a local DX'er. Looking at the pile of logs I get, I'm afraid that this does happen, the listener not having actually heard the DX station involved. As I have said before, it is no use running any competition unless the competitors can be assured that the winners have indeed heard the stations submitted in logs.

**John Porter** (Baslow, Derby) lost half his long wire in the gales but managed to copy VQ9HCS in the Seychelles on 15m for a fairly rare one. **C. P. Bennett** (Slough, Berks) joins our ranks with a Codar CR70A and ditto preselector fed from a 10ft vertical or 100ft long wire. He lacks signals on the 10m band which is not an unusual moan, only to be expected at the bottom of the sunspot cycle. Nevertheless some of our SWL's do quite well and so the receiving set-up ought to be suspect. Receiver alignment or rather, misalignment, can be a contributory factor and an aerial designed for the band will help no end, as will bringing any existing aerial to resonance on 10m.

**Roger Trett** (Norwich) swears he will try to get up much earlier in the mornings to get some of that exotic DX that the lie-a-beds never hear! More from **John Porter** who is all agog at hearing a W8 and a W0 on CW on TWO METRES! Yes, very likely, now that amateur satellite Oscar 7 is in orbit, following its launching on November 15 last. The 432MHz to 144MHz repeater has already provided many trans-Atlantic QSO's. Strong signals from telemetry beacons on 435.1 and 145.98MHz are being heard. A second repeater from the 2m to the 10m band is also opera-

tional plus a telemetry beacon on 29.5MHz. All this should be an incentive for some of you to try your hand at 2m and down. John uses a Microwave Modules converter into his FR50B and an indoor dipole on 2m.

Regular **Alan Doherty** (Portrush) wanted some QTH's for the stations he had heard but generally I am unable to help in this respect. Can only suggest keeping an eye on the DX news in Short Wave Magazine or Radio Communication where the QTH's of the rarer DX stations are generally given. **Stephen Lawrence** (Market Harborough) had some blush-making comments to make on the column plus ideas for a contest involving a short contest period so that logs could be checked against each other. This would penalise the really good operator who might hear the odd weak DX station that nobody else hears, and this does happen. This is where the tape recording would prove invaluable.

**Malcolm Sole** (Lancaster) would like times quoted on reception reports but I'm afraid that the delay before the information gets into print makes such information useless. All we can hope to do is to indicate the unusual stations that have been active in recent times and leave it to the SWL to deduce from experience when he is most likely to be able to hear them on the particular band indicated. Malcolm has an AR88 and 300ft of wire in the loft . . . some loft! or too many zeros! I've asked Malcolm to elucidate.

**Steve Cottis** and **Nick Hunt** of the same street in Harrogate have very sensibly combined their energies and borrowed a receiver in order to get started in our exciting hobby. The set is fairly good but nevertheless they would like to get a set of their own, but as they say 'money is very important as we have not got much of it', and since they are aged but 13 this is very understandable. Congratulations chaps, and let's hope your initiative will be rewarded.

**Tim Charles** (Colchester) was still waiting for his new CR70A when he wrote from hospital where he was visiting his Mum. He managed to note VP1FF on 40m SSB and VR6AF on the same band on CW plus KS6AZ on 20m CW all worthwhile goodies by any standards. **Gary Edge** (Warrington) must have been laying down the law to his 9R59DS which came up with HZ1TA, VU2BX and FP8SPM on 80m SSB. Following my February compliments to 16-year-old John Martin I received an unsigned letter from an unknown address in Plymouth pointing out that Phillip Askey of the Plymouth Radio Club had passed his RAE at 14 $\frac{1}{2}$ ! I gather that he is no less than G8JNN and I hope these startling revelations will not prove to be too much of an embarrassment! Outstanding entry from the log of **Max France** (Warrington) was VS6FB at



1543z towards the end of December on 80m. Round about our sunset I suppose, without looking up the tables, which would make the path ideal at the time.

**Eric Carling** (Lymington) persists with his request for a band/countries table each month but we again run into the problem of substantiating claims. **Alan Rae** (Glasgow) got money in lieu of goods at Christmas time and so is now looking for a receiver. Preference runs to Drake 2A, FR50 or 100 or the Trio series Jr310,500 or 160. Stanley Sharred's brother **David A8312** has decided to join the act by sharing the equipment and submitting his own log. David likes 160m where he has heard no less than 33 countries in little over a year. He, like several other readers, sent me info on ST2AY which is much appreciated but so far nil QSO! Hoped to make it in the CQ WW 160m contest but in spite of working 20 countries the ST2 eluded me.

On getting QSL cards, **Bernard Hughes BRS25901** (Worcester) reports a QSL card from Fiji as costing him 10p plus two IRC's plus an SAE! Which explains why we cannot demand cards as evidence in competitions! **John Burgess** (Birmingham) joins us with his Codar TRF receiver and 25ft outdoor wire and so far has concentrated on 20 and 80m. **Graham Wilson** (Blackpool) stuck with SSTV with his JR310 into a Spacemark monitor on 14230kHz to list nearly 100 stations. **Paul Barker** (Sunderland) is also happy on this mode plus some SSB catches. Paul comments on the excellent work done by **VK6WC** who acted as relay station in the first critical hours of the Darwin disaster.

Newcomer **Michael Adams A8520** (Gosport) has a CR70A and finds it a delight to use. The 132ft of wire, preselector and ATU must help quite a lot too. A Microwave Modules converter puts him on 2m as an additional interest.

**Keith Rawlings A8569** (Broxbourne, Herts) has begun his listening on 2m and 70cm, with converters into a PR40 fed from a 5 element job on 2m and a 46 element on 70cm rotated by an AR22. He has made up a preselector for the 70cm band which netted him F1AVG for a start. **Michael Green** (Northwich) has also been listening in to Oscar 7 with a converter into his HF arrangement of a QP166 front-end into a CR100 as an IF strip. As he says, further info on the Oscars can be heard on the RSGB broadcasts on about 3600kHz starting at 0930 on Sundays as well as on some VHF channels. The Oscar Net is on 3780kHz Sundays at 1015z. **John Martin A8781** (Kingsbridge, Devon) joins us with a general log but is very concerned at the general noise on 80m. We all learn to live with it, in time! An enlarged log from **Tim Charles**, previously mentioned above, confirms reception of his new CR70A at long last! **Andrew Darragh** (Wetherby) is also gloating, this time over a FR50B, which he actually had to buy!

### Log extracts

**B. Hughes:—80m** HZ1KE UA9VH/JT1 KG4DS XU1DX ZD7FT **20m** VQ9HCS VK8CE 4W1GM

**M. Bennett:—80m** HM5LV TG9YN **20m** FP8IZ VQ9B 5B4AV **15m** HC1AD 9Y5GA

**D. Sharred:—160m** EP2BQ OJOMA PY1RO VS6DO 9G1AR **80m** FM7AB OY7K VP1FF ZL2BT 8P6ES **40m** HP11W ZD7FT ZL2AMJ

**A. Rae:—80m** H18LC HK3KT JY9GR KZ5EQ W7AZG 6W8AF 9Y4CP

**E. Carling:—20m** A2CCV (Botswana) BV2B

ZS1ANT (Antarctica) **15m** CO2PZ HR3JJR TG9YN YN1GV **10m** A2CCY ZD7FT 9G1AR

**S. Budd:—80m** CP2BD H18HA HK4BTY JA8LQ KG4DS PJ2CW SU1MA TR8AC **20m** VP2AYL XU1DX 8R1X (POB 164 Georgetown)

**M. France:—80m** FG7GF KG4OS VP1FF ZF1RD 3E1KC (Panama) 9X5PT

**M. Sole:—40m** F2JD/P/5U7 **20m** BV2B HM1AQ KG6SW VP8NP YJ8CS

**J. Porter: 20m** HI3XMV MIC VP8NP **15m** FY7AS HS4AFD KZ5DK **2m** A W8 and W0 heard on CW via Oscar 7

**R. Trett:—20m** VP2VPK (Tortola) **15m** A2CCY CT3AA PJ2VD

**G. Wilson:—20m**(SSTV) CT1EQ EA5IO HA6VK HB9NL JA7FS K2ONE OD5HC SV1CG VE3FCN VU2AIC VQ9R

**M. Adams:—80m** FP8FU VE7EL VP5BT ZL3GS **15m** KP4DLA 5T5AC

**A. Doherty:—80m** EP2VJ HI8XRG YN2DX **40m** JA1DSL TG9PW VP9CW **20m** TJ1TAF 5U7BA

**M. Green:—80m** XE3LK VP2SG **10m** (from **2m** via Oscar 7) DC8BB G8AWS G8BCL **2m** (from **70cm** via Oscar 7) DJ9DL F6CH G8AWS HB9RG I0SVS LX1DB LX1SI VE2BYG

**T. Charles:—160m** K8CCV WB8AJH **80m** A4XVB HP1SW PZ5FB TTJX VP2EEB (Anguilla) **15m** JY9CR PJ8AJA PZ1DR VQ9FCS

**P. Barker:—20m** (SSTV) HB9IT I2LOV OE1SF OK3OZAS SVICD

**A. Darragh:—80m** FP8SPM HI8XRG **20m** DU1XKE HP1ZV 8R1X **15m** JY9CR PZ1DR TU2DV

All stations are SSB except those in bold which are CW.



## SHORT WAVE BROADCASTS

by Derek Bell

**I**N these days of the ever rising price it does my old bones good to be able to relate the story recently sent to me by **Andrew Toms** of Coventry. He wandered into a jumble sale in that neck of the woods and saw reposing there an old eight-band portable receiver, priced at ten pence. Bearing this home he found that it gave him:—

6055 at 2100 Radio Sweden from Horby

6065 at 1924 V.O.A. from Morocco

9540 at 1700 Radio Australia from Perth

All this when coupled to an ex W.D. tank aerial mounted ten feet in the air. Andrew asks for details of communications receivers suitable for general short wave listening. Well, OM, these would fill a book, but you seem well set up so I think it would be perhaps best to stay as you are.

CQ, CQ, **Rex Cooper**, you asked for details recently of FEBA from the Seychelles. In a recent band survey by the World DX Club (to whom my thanks for the gen) this station was reported on 11855 at 1800. While on the subject of band sweeping, acting on a recent letter reporting no traffic on 5MHz I did a bit of band surveying myself and came up with Ecos del Torbes, San Cristobal, Venezuela

—continued on page 1130




# IN NEXT MONTH'S PRACTICAL WIRELESS

## PW APOLLO-series


PART 1
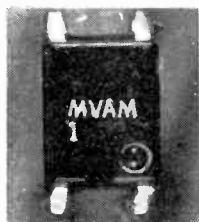
### TRIPLE VARICAP MEDIUM WAVE TUNER/RECEIVER



The very latest multiple Varicap is used in the Apollo series permitting the simultaneous tuning of several circuits at almost any distance by means of a simple potentiometer. The possibilities are tremendous! Protect your car radio by putting it in the boot and tuning it from the front seat! Comfortable armchair operation of your domestic radio . . . and remember, full tuning coverage is available in addition to the usual push-button facilities!

### also: CAR WIPER DELAY UNIT

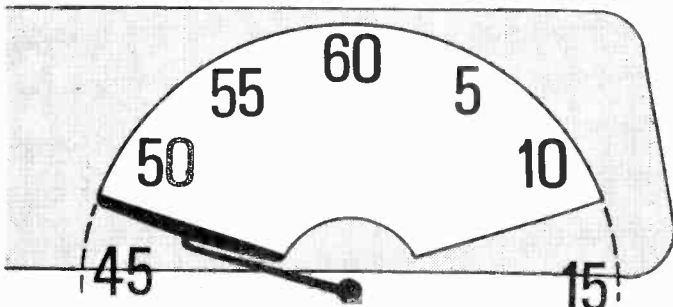

Clip this unit across your windscreen wiper switch and get single stroke operation at various controlled intervals to suit weather conditions.

### MODEL TRAIN CONTROLLER

Simulate precisely the movements of real trains! Based on the cheap 555 IC the unit includes a mains power supply.

MANY OTHER CONSTRUCTIONAL  
ARTICLES, SPECIAL FEATURES  
AND REGULAR COLUMNS.

ON SALE IN APRIL



M. J. HUGHES M.A., C. Eng

THE internal amplifier circuit shown in Fig. 5 uses the LM380 (IC17) in its simplest possible configuration. SK1 is a switched jack socket that allows a phono output to be taken before the internal amplifier and is so wired that the internal amplification system is disconnected when used with an outside amplifier. The output from IC17 is taken to both the internal speaker and to a headphone socket. This socket, when used, automatically cuts out the internal speaker. Should these jack sockets not be wanted the printed circuit board has two pairs of pins (A & A<sub>1</sub> and B & B<sub>1</sub>) which can be shorted together and the jack sockets omitted. Maximum output power from IC17 is developed across an 8Ω loudspeaker but in practice it has been found that sheer power is not too important from the internal unit, consequently any medium impedance loud-

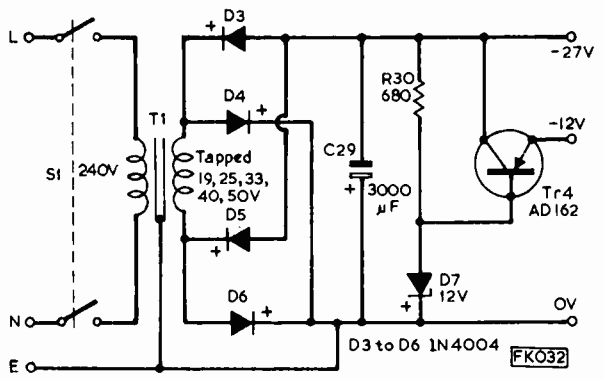


Fig. 6: Circuit of the power supply. Constructed on a PCB separately from the main organ PCB.

All smoothing and decoupling capacitors are mounted on the main board, with the exception of C29 which serves to provide a satisfactory -27V rail to feed the MOS devices.

NOTE

It is most important, before continuing any further, that the following points are read **before** even unwrapping the MOS integrated circuits (IC1 to IC13)!

In order to check the workings of the main board it is suggested that the power supply be assembled first. This board, Fig. 7, should be fabricated from fibreglass laminate as it will be used to support the mains transformer. Plenty of space has been allowed for transformers other than the MT50/1/2 but if using an unspecified transformer it is as well to check that it will fit before continuing. Using a pair of long-nose pliers form the component leads to exactly fit the hole spacing on the board, Fig. 8, ensuring that the diodes and the capacitor are inserted with correct polarity.

Theappings on the transformer should give an RMS output voltage of 18 or 19V, so if using the specified device it is suggested the supply be taken from the terminals marked 0V and 19V. On rectification this should give an off-load DC voltage of 26.6V across C29. Do not expect an exact voltage at this

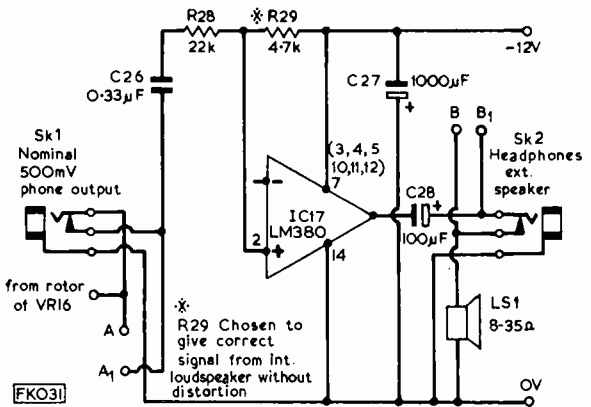


Fig. 5: Circuit of the simple audio amplifier incorporated in the organ-speaker (8Ω-35Ω) of suitable dimensions can be used.

Apart from the keyboard resistors and the power supply, all circuitry is housed on one board. This includes all the manual controls and thus greatly simplifies the normal problems of interconnections. The second board houses the power supply, Fig. 6, and, as with the rest of the organ, it contains only essential components. A fairly reliable -12V rail is required, hence the zener D7 and the series regulator transistor Tr4.



# PW 'Easubuild'

# ELECTRONIC ORGAN

## MIERE

## PART 2

point as it will be dependent on the loading of R30 and any eventual loading from the rest of the circuitry. Although the circuitry calls for a nominal -27V rail it has been found in practice that the circuits function adequately with this rail as low as -22V. On the other hand the -27V rail should not exceed -30V as damage to the IC's might result.

### POWER SUPPLY TESTING

When the power supply board is assembled, connect up a temporary mains lead to the primary of the transformer (not forgetting the earth wire to the board) and then wind a few layers of insulating tape around the terminals for protection.

It is suggested that a power supply test be carried out before any of the circuitry is assembled into the cabinet. Connect up to the mains, and check the off-load output voltages. Relative to the 0V (positive) rail should be something between -25 and -27V at the negative end of C30. If voltages wildly different from this are found check that the diodes are the right way round. If the voltage is just outside the above limits alter the output tapping of the mains transformer accordingly.

Having established a proper value for the nominal -27V rail go on to check that there is -12V at the emitter of Tr4. With the correct zener diode this should automatically fall within the range of 11.5 to 12.5V. If very different from this suspect the zener and replace it.

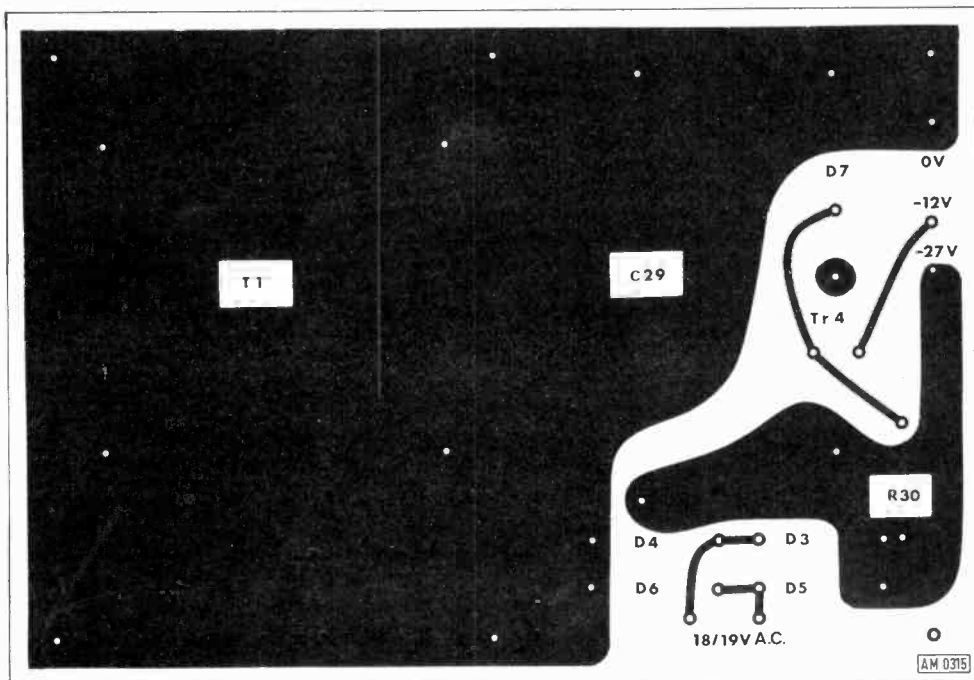


Fig. 7: Actual size layout for the PCB on which the power supply is built.

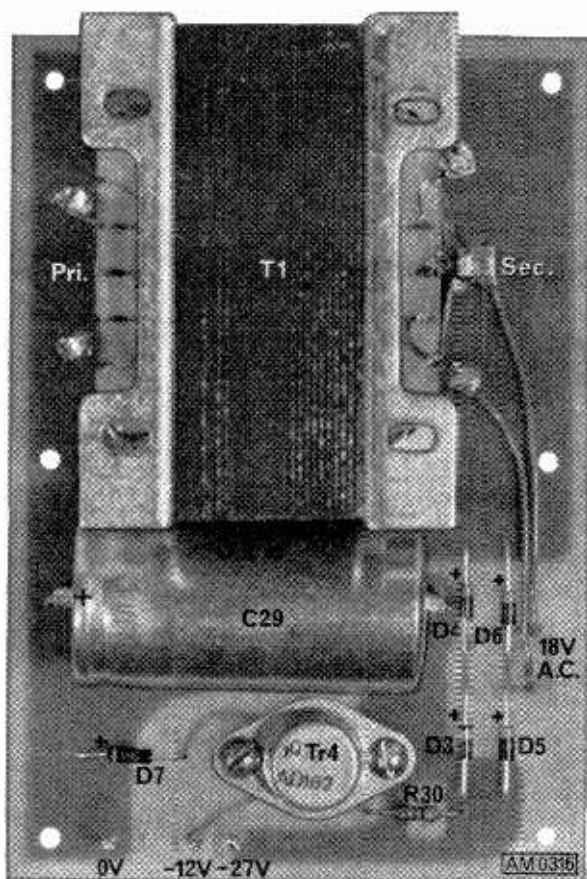


Fig. 8 : Location of components on power supply PCB. Observe correct polarity of diodes and capacitors.

## MAIN PCB

By any standards this is a large circuit board (Fig. 9) and it has to carry a number of manual controls which rely on their soldered connections for mechanical rigidity. For this reason fibreglass laminate must be used. It is large because we have removed most of a conventional organ's complexity from the hands of the constructor and put it into the board. Whether the board is home-made or bought it must be thoroughly checked for quality. Make a test for possible hair-line cracks in the very fine conductors that run between the tone generator IC's and the lead-out lands on the edge of the board. At the same time check that none of these fine conductors are shorting to their neighbours, either from under-etching or a "smear" from the roller tinning process.

If the board is ready-made there should, of course, be no problem but it saves an awful lot of bother later to devote five minutes to this test. Should any discontinuity be found in any of these conductors "home in" on the break with testmeter probes and then carefully solder a single strand of wire (taken from some fine flex) across the offending area. Do not try to bridge the gap with solder, at best it will make a messy job and at worst it will introduce a doubtful connection which could cause trouble later. Short circuits can easily be cleared by running a sharp knife between the conductors until the "bridge" is felt when it can then be scraped clear.

## MAIN BOARD ASSEMBLY

Start assembly with the nine slider potentiometers. The type specified will fit the lands on the circuit board exactly and will be self supporting. It is not recommended to use other types, but if it is unavoidable the contact positions may not coincide with those on the board. As a make-shift remedy carefully drill three holes in the correct position (without interfering with any of the printed wiring in that area) and attach the potentiometers in place on the top side of the board with Araldite. Connections to the lands can then be made on the underside of the board with insulated wire. This is an exceedingly messy job and should be avoided because it will be almost impossible to replace these components at a later date.

Make sure that all the tracks of the sliders are parallel with each other, a small latitude in positioning is afforded by the slight flexibility of their solder tags. When they are correctly positioned make sure that they are rigidly fixed with a generous amount of solder on each land.

Now insert and solder-in the inductor, L1 and L2, after which the board can be turned upside down for subsequent soldering. The components already in place will act as legs to hold the board clear of the working surface. Because of the high density of printed wiring, little metal is left on the board for soldering lands necessitating extreme care with the soldering iron. A miniature iron must be used for this and all subsequent operations, one with a 3/32in. diameter bit or, at most, 1/8in. diameter. Ideally, the iron should be equipped with an earthing lead, for reasons which will be explained later, but if it has no earth connection do not worry unduly; it is certainly not worth rushing out to buy one specially! Use the minimum amount of solder for each joint and make sure that each connection is clean and bright before moving on to the next. Dry joints can be a great headache in this project!


## OSCILLATOR AND VIBRATO STAGES

Now wire in all the topside conductor jumpers. These are cut from 22SWG tinned copper wire that has been work hardened to keep it straight. It is a useful tip to know how to harden wire for this, and other projects. First of all cut off about a yard of wire from the reel; it will, of course, have a tendency to curl. Firmly grip each end in a couple of pairs of pliers, a couple of twists around the jaws of the pliers helps maintain the grip, and then slightly stretch the wire by pulling apart on the pliers. Allow the wire to stretch for about 2 or 3 inches and when the pliers are removed the wire will remain straight.

Now cut off straight lengths; form the ends to fit the holes for the jumpers and solder them into position. Make absolutely sure that they are the right length so that there is no chance of them bowing and shorting together. Apart from the jumpers in the vicinity of IC2 to IC13 do not forget the two short links near IC15. Next insert and solder all the board pins into their correct locations.

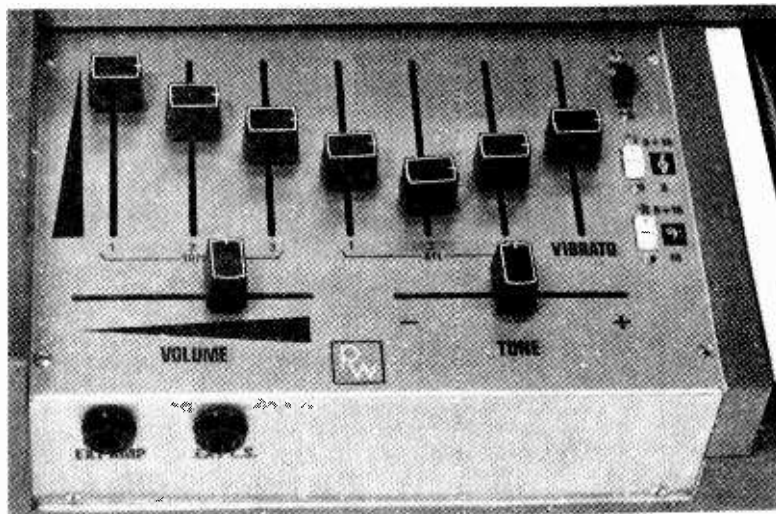Start assembly of the rest of the circuitry in the following sequence after which one can carry out a few tests to check progress. Begin with the master oscillator and vibrato stages by soldering in the resistors R1 to R11 (R5 and R6 are located near the slider pot VR2). Proceed with capacitors C1 to C7.





*Close-up of the organ control panel and outlets for external amplifier or speaker. The first three vertical sliders at the left control the 16ft. pitch, the next three controlling the 8ft. pitch.*

The latter is a compression type and should be mounted on the top side of the board; use tinned copper wire to connect its two terminals to the corresponding holes in the PCB. Make absolutely sure that C6 is in the right holes and that the polarity is correct.

Solder in the semiconductors D1, D2, Tr1, Tr2 and Tr3. Be careful not to damage the plastic casing of the diodes, form the leads and make sure they are inserted the right way round.

Now the oscillator can be tested with the help of a medium-wave transistor radio. Temporarily connect the 0V and -12V rails of the power supply to the corresponding circuit pins on the main board (near the location for IC13), hook a length of insulated flex to the end of R10 nearest Tr3 and set VR1 to minimum vibrato, i.e. the slider should be furthest away from the edge of the board). Set VR2 to the centre of its range and switch on the radio, tuned to about the middle of the medium waveband. Place the insulated wire from R10 very close to the radio and switch on the organ's supply. Using a screwdriver, adjust C7 until a signal is picked up by the radio. If there is a station nearby you should hear a clear heterodyne whistle. A signal indicates that the oscillator is functioning.

If no signal is picked up at any setting of C7 then it is almost certain that there is a missed connection, or Tr3 or the diodes are the wrong way round. Proceed to check the tune control by tuning C7 for a clear heterodyne whistle at some position on the waveband and then try sliding VR2 across its travel. It should have much the same effect as tuning C7 except that the degree of control is much finer.

Finally, check the vibrato by listening to the whistle while advancing VR1. The whistle should start to "wobble" in frequency and eventually, as the control is advanced further, break-up altogether into a series of low frequency pulses.

## TONE FORMING STAGES

However tempted one may be, **do not under any circumstances**, insert the MOS integrated circuits (ICs 1 to 13); this should be done at the very last stage in assembly. Instead, carry out assembly of the tone forming circuits and amplifiers.

Start with all the IC sockets as this will help in locating the positions of other components. Complete the installation of the remaining passive components, R12 to R29, the seven pre-set potentiometers and C8 to C28. At the same time put temporary shorting links across the board pins. A and A<sub>1</sub>, and B and B<sub>1</sub>. The board has been designed for use with Mullard C280 capacitors but ample room has been left to accommodate other types. When using the C280 devices widen the distance between the lead-outs slightly; this should be done very carefully and the leads should not be bent too close to the plastic covering as they can sometimes break away altogether. It is best to hold the lead with a pair of long-nose pliers, very close to the case, and carry out the bending operation on the side of the pliers furthest from the case.


Integrated circuits IC14 to IC17 can now be inserted into their sockets ensuring that they are correctly orientated. Be careful in deciding which way round they go because the orientation mark is a very small indent in one corner of the top side. This should not be confused with the larger moulding mark which appears on some devices. Before proceeding to the final stage of board assembly set all the pre-set potentiometers to the centre of their adjustment.

## MOS DEVICES

It only remains to insert the MOS devices. A reasonable amount of care is required for this operation because the devices, although protected to a degree, are subject to damage from high voltage static electricity, the type that can be induced on the body when one wears a pair of nylon overalls or a nylon sweater. To protect the devices in transit they are supplied with special packing. In the case of IC1 it will probably be sent in a plastic box, its pins pressed into a piece of black conducting foam rubber. It is quite safe to handle the device while its pins are thus protected but it would be a foolish man who did so immediately after combing his hair or stroking the cat, ideal ways of building up a high static charge on the body!!

Likewise, IC2 to IC13 are supplied with shorting devices, connected around the pins. Again the IC's

AM0317

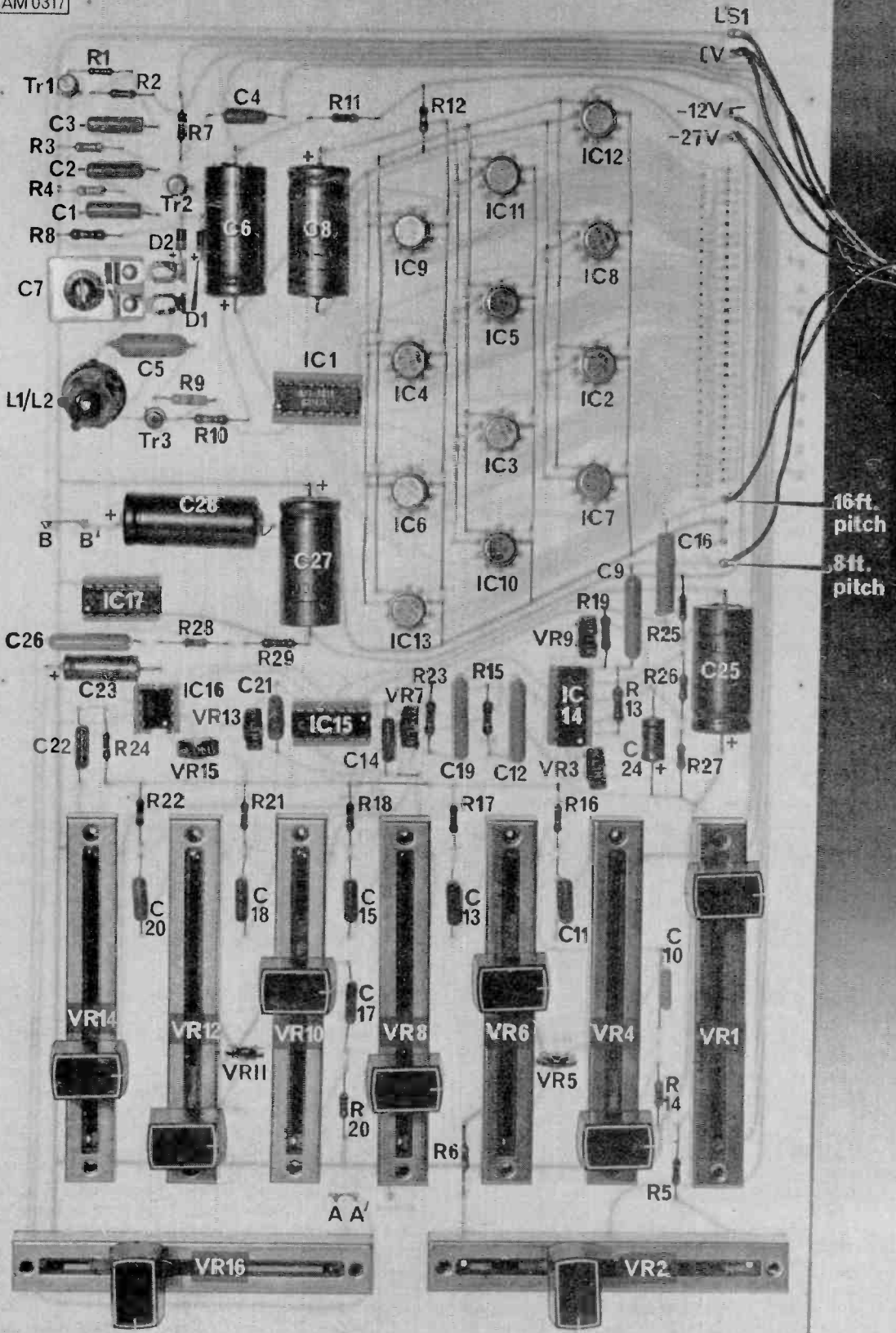

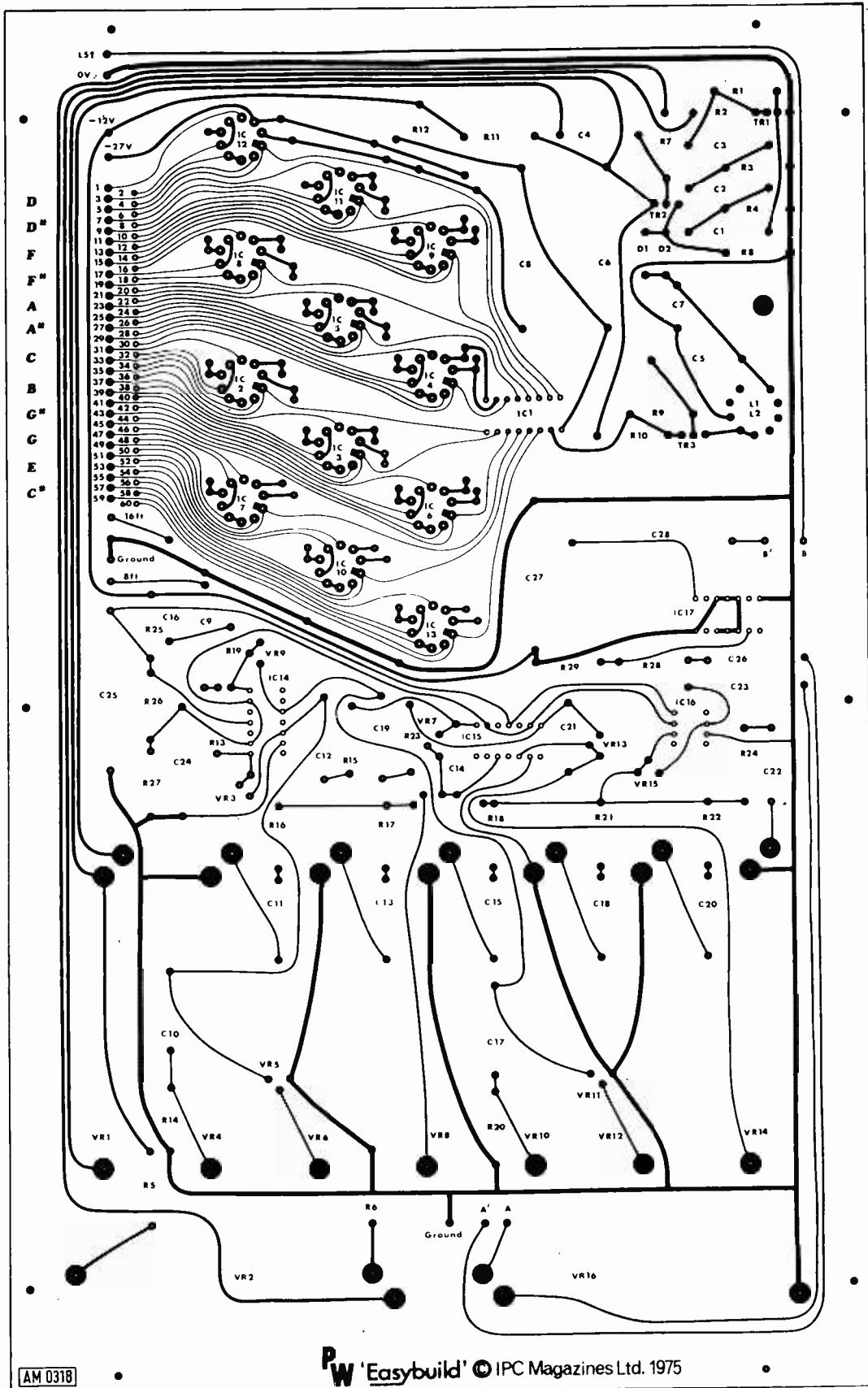


Fig. 9: Above, shows the main PCB layout, for reference purposes only. This is **NOT ACTUAL SIZE**. The board size is 330 x 205 mm (13 x 8in.). Details on obtaining a full-size paper drawing of the PCB can be found in Part 1. The annotated photograph, facing page, is of the finished board, which will assist constructors to locate the components. The copper side of the board is underneath.

AM 0318

PW 'Easybuild' © IPC Magazines Ltd. 1975

may be handled with these in place, but eventually these protective measures have to be removed so that one can solder the devices into place. IC1 is a dual-in-line package and hence a socket can be used for it and soldering is not required.

The ten-lead TO-5 packages of ICs 2 to 13, however, present a problem because sockets for this type of package are extremely expensive, making their use unjustifiable. Remember however, that soldering these devices straight to the board will probably invalidate any guarantee from the manufacturer for free replacement in the event of failure. As the sockets are very nearly as expensive as the devices themselves it was felt the extra insurance was hardly good value for money, and in any case provided these instructions are followed in every detail there should not be any problems.

The main worry is static electricity and every possible precaution must be taken to prevent introducing a static potential difference between the pins of the IC's which can be caused by a body charge induced by wearing synthetic fibre clothing while sitting on PVC chairs, wearing insulated soled shoes, a charge on a formica working surface that is insulated from the ground by rubber feet and from a charge induced on an unearthened soldering iron. Static is enhanced by dry, hot conditions.

From the above it might seem that we are suggesting that you strip off all your clothes and go barefooted into the garden to do your assembly on the lawn on a wet cold winter's day! Fortunately one need not go to these lengths but it is necessary to do one or two apparently strange things to ensure complete protection.

The object is to try and keep everything at a uniform potential and to avoid aggravating problems, i.e. work on a wooden table and avoid PVC covered chairs, a good old fashioned wooden chair is safer. Take off those beautiful synthetic soled shoes and put on your oldest slippers. Prepare your working surface by covering it with a generous sheet of aluminium cooking foil and make sure that it covers all the area on which you intend to work. Put all your tools and the PCB on this sheet together with the soldering iron stand and connect a lead of fine wire between a cool metal part of the iron's case and this sheet. If the soldering iron is properly earthed this means that anything that comes in contact with your work surface will automatically be earthed. While working on this part of the project, frequently touch the fingers on the foil. Alternatively roll up the sleeves so that the elbows frequently come into contact with the foil.

Tip out the IC's onto the aluminium foil and make sure that they have all come into contact with it. They can then be handled in the normal way without any further worries.

## DIVIDER IC's

Inserting ten-lead devices through a drilled circuit board can be a bit of a problem. It is therefore advisable to trim the leads to different lengths making the lead immediately under the locating lug the longest. Then, working round the leads, trim each one a little shorter than its predecessor but do not overdo the trimming because it must end up with between  $\frac{3}{8}$ in. and  $\frac{1}{2}$ in. for the shortest lead!

The lead immediately under the lug of each of the twelve IC's should be inserted first into the hole

which carries an identifying lug on the printed wiring side of the board. Then work round, carefully inserting each successively shorter lead in turn until the IC is in place. Push the circuit home making sure that the leads fan out gently without shorting against each other. Turn the board over and carefully solder the device into place with the maximum of care and the minimum of solder.

Proceed like this until all the TO-5 devices have been installed. Check that blobs of solder have not been dropped on the fine printed wiring and that there are no bridges between pads on the IC connection pattern. Finally insert IC1 into its socket, again making sure of its correct orientation, and the board is now complete and ready for testing.

Solder temporary leads, each about 12in. in length, to the board pins as follows: one wire to pin LS1, two wires to that marked 0V and one wire each to -12V, -27V, 16ft, and 8ft. Now dispense with the static protection paraphernalia as once the IC's are in circuit there is little chance of them being damaged.

## TESTING

Test the main board by connecting the leads 0V, -12V and -27V to the corresponding pins on the power supply PCB, and another lead from the 0V pin together with one marked LS1 to the loudspeaker (not yet in the cabinet). Set the knobs of all the sliders as follows: VR1 furthest away from the front of the board, VR2 mid-way, VR4, 6, 8, 10, 12 and 14 furthest away from the front of the board (i.e. to minimum signal) and VR16 to the furthest left position (minimum volume). Switch on the power when a "clunk" from the loudspeaker should be heard and nothing more. If nothing at all is heard check shorted points B and B<sub>1</sub> and similarly points A and A<sub>1</sub>. Advance the volume control (VR16) to about mid-way and you could hear a gentle "singing" from the loudspeaker. This may only be a faint signal but is a good sign that things are as they should be.

Now for the great moment: advance VR6, (the square wave control at 8ft pitch), to maximum and touch the flying lead from the 8ft pin on to any of the lands numbered 1 to 60. There should be a loud clear tone from the loudspeaker for every land that is touched. Pin 1 should be the lowest octave tone for the note D, pin 2 should be one octave up on this, pin 3 another octave higher, pin 4 one more octave higher and pin 5 the highest octave for D. Pin 6 should be the lowest octave for D and so on. Keep the wire on one mid-frequency tone and check that its loudness can be controlled by VR6 and the volume control VR16.

Now leave VR6 at minimum level and check the "spikey" signal by advancing VR4. It should sound much thinner and, probably, will be of much lower amplitude. Advance the volume control to maximum and turn VR15 (preset) down until the sound is at a comfortable level, approximately 25% up from its lowest position. If the sound is weak at this setting go to the busbar preamplifier gain control (pre-set) VR3 and adjust this to give a comfortable level.

**PART 3 NEXT MONTH CONTINUES WITH THE TESTING OF THE MAIN PCB, AND WIRING OF THE KEYBOARD.**

# IC+2 RECEIVER

R.H. LONGDEN



**T**HIS receiver uses an integrated circuit which provides mixer, oscillator, IF, detector and audio driver stages, with a ceramic filter in the IF position. A complementary push-pull audio output stage follows, to operate the speaker.

## CIRCUIT DESIGN

The switching and tuning arrangements adopted are of a somewhat simple nature and the way in which the three bands are obtained will be clear from Fig. 1. VC1/VC2 is the tuning capacitor with an integral ball drive. The band switch has three poles. On "M", for medium wave reception, L1 and L2 are in series and tuned by VC1. VC2 tunes the oscillator coil, with padder C4 in circuit. S1 also places C2 across VC2. In these circumstances, oscillator coverage is approximately 1165 to 2020kHz. As the receiver intermediate frequency is 455kHz, the oscillator operating HF of the signal frequency, coverage is approximately 710-1565kHz. No pre-set trimmer is required in the oscillator circuit because the panel trimmer VC3 allows for peaking of the aerial circuit throughout the band.

With the switch at "160" C2 remains in circuit, but the padder is changed to C3. Oscillator coverage is now approximately 2160 to 2600kHz. The oscillator is HF of the signal frequency as before so the receiver tunes about 1705-2145kHz which includes the 160m band (1800-2000kHz). L1 and L2 remain in series, but aerial tuning coverage is reduced by TC2 in series with VC1, to obtain a suitable band.

With the switch at "80" S1 shorts out the MW section L2 leaving only the short wave winding L1 in use. C2 is no longer across VC2 and TC3 is in series with C4. As a result, oscillator coverage is approximately 3045 to 3415kHz. The oscillator is now on the LF side of the signal frequency giving a band of about 3500-3870kHz for 80m reception. TC1 is in series with VC1 providing suitable coverage in the aerial circuit.

Alignment of these circuits is not particularly tricky as VC3 is present on all bands allowing manual trimming. It should be noted that there is not a great deal of latitude in capacitor values. Capacitor C4 is larger than the usual padder because the oscillator coil has to be set to a somewhat lower inductance than normal, which is easily within the core adjustment. The circuit allows effective bandspreading of 160m and 80m plus most of the usual MW coverage without the switching otherwise necessary to select alternative oscillator coils for the various bands.

## CIRCUIT DETAILS

The pins of IC1 are numbered as seen from below, Fig. 2. The aerial coil point 5 goes to the mixer base pin 1. Pin 3 is for the mixer emitter circuit with emitter bias components R2, R3 and C9. Pin 4 is the input of the audio amplifier, with pin 5 for negative feedback from the output transistors, via R16. Pin 6 is the audio section output, driving Tr1 and Tr2. Pin 7 is the IC earth line.

Pin 8 is the audio output going to volume control VR1, and AGC bias via R4 and R5 to control the gain of earlier stages. Pin 9 is the IC positive supply point. Pins 10 and 11 are the IF amplifier input, with by-pass capacitor C8 on pin 11.

Pins 12 and 13 are collector and emitter circuits of the IC oscillator, and go to the oscillator coil. Pin 14 is the mixer output in conjunction with pin 2, which is earthed via C7.

The IC is effectively 14 transistors, the end occupied by pins 1 and 14 being identified as shown in Fig. 2.

External connections only for the CFT455C filter are shown, pins are bridged and connected to place the ceramic filter in series with the coupling windings.

The output transistors employ emitter resistors R14 and R15 to stabilise working conditions the circuit being satisfactory for a loudspeaker of 8 ohms or over. A speaker of up to 75 ohms may be used, though output falls off a little, and a somewhat

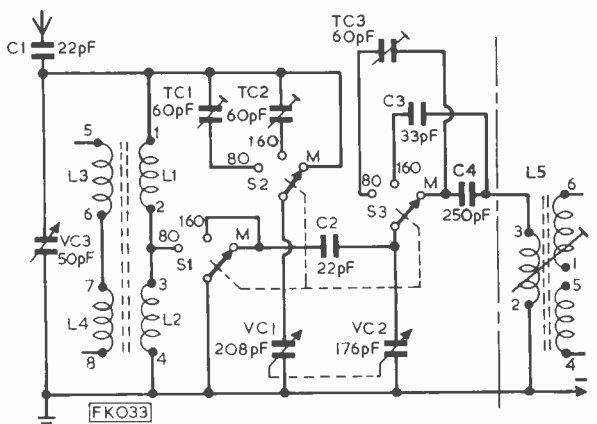


Fig. 1: Circuit diagram of the switching and tuning arrangements of the receiver. Connections to L3, L4 and L5 are shown in Fig. 2.



lower impedance (but not under 8 ohms) is more suitable. Low impedance phones may be plugged into the jack socket, for personal listening.

## CONSTRUCTION

The receiver, with speaker and battery, was constructed to fit a case  $6 \times 3\frac{1}{2} \times 1\frac{3}{4}$  in. internal dimensions, as a pocket set giving good 80m and 160m amateur band reception in addition to normal MW reception. The whole circuit of Fig. 2, with the exception of the aerial, VR1 and speaker, is assembled on 0.1in matrix plain Veroboard. In order that the components may be readily accommodated, it is most convenient to use the  $\frac{1}{4}$  watt resistors sometimes listed as "miniature". The capacitors are also of small size, and except for the electrolytics, are mostly low voltage disc ceramic.

The board is approximately  $4\frac{1}{4} \times 1\frac{5}{8}$  in, and components can be located from Fig. 3. Holes are first drilled to take the pins of the oscillator coil, IF filter and for bolts to secure the two angle brackets which attach the board to the receiver panel and which also form the earth return connecting points. Tags are fitted for this purpose. In most places the wire ends of resistors and capacitors can reach between the connecting points. Where other connections are required, these can be 24SWG tinned copper or similar wire. Insulating sleeving is necessary on many leads and different colours can be used to identify various connections.

When soldering to the IC, the same care to avoid overheating should be taken as when soldering the transistors. With the latter, short pieces of green sleeving were put on the emitter leads with white on the collector leads, to avoid possible short circuits and provide easy identification of connections. Flying leads are provided from R7, for VR1 centre tag and from R6/C12, also for VR1. The remaining VR1 tag is wired to chassis. Leads from C18 positive and the positive line run to the speaker. A red lead from C14 positive is fitted with a positive battery clip.

The bridging connections on the IF filter should not be overlooked and connections must not touch unused pins. C3 and C4 are soldered to pin 3 of the

## ★ components list

### Resistors

R1 22k $\Omega$	R8 27k $\Omega$	R15 2.2 $\Omega$
R2 150 $\Omega$	R9 470 $\Omega$	R16 15k $\Omega$
R3 820 $\Omega$	R10 10k $\Omega$	R17 10k $\Omega$
R4 8.2k $\Omega$	R11 100 $\Omega$	R18 220k $\Omega$
R5 8.2k $\Omega$	R12 680 $\Omega$	R19 2.7k $\Omega$
R6 390 $\Omega$	R13 47 $\Omega$	
R7 1k $\Omega$	R14 2.2 $\Omega$	

All resistors are 5%  $\frac{1}{4}$  watt

VR1 5k $\Omega$  log. potentiometer with switch S4

### Capacitors

C1 22pF	C8 0.047 $\mu$ F	C15 0.25 $\mu$ F
C2 22pF	C9 0.047 $\mu$ F	C16 0.01 $\mu$ F
C3 33pF	C10 0.047 $\mu$ F	C17 32 $\mu$ F 6.4V
C4 250pF	C11 10 $\mu$ F 6.4V	C18 320 $\mu$ F 6.4V
C5 0.047 $\mu$ F	C12 0.1 $\mu$ F	C19 100pF
C6 0.1 $\mu$ F	C13 320 $\mu$ F 6.4V	C20 880pF
C7 0.1 $\mu$ F	C14 220 $\mu$ F 10V	C21 0.047 $\mu$ F

VC1/VC2 208/176pF gang (Jackson Type 00 with slow motion)

VC3 50pF variable (Jackson Type C804)

VC4 20pF variable (Jackson Type C1804)

TC1/2/3 60pF compression pre-sets

### Semiconductors

IC1 TAD100 Tr1 AC141 Tr2 AC142 Tr3 ZTX108 or similar

### Miscellaneous

Ferrite rod aerial (Denco 5in. with MW winding only). Oscillator coil L5 (Denco TOC1). Filter F1 CTF455C (Ambit). Switch S1/2/3 3 pole 3 way rotary wafers. S5 slide switch. Speaker 8 ohm 2 $\frac{1}{2}$ in. but see text. Insulated jack socket 3.5mm. Veroboard, see text. Knobs.


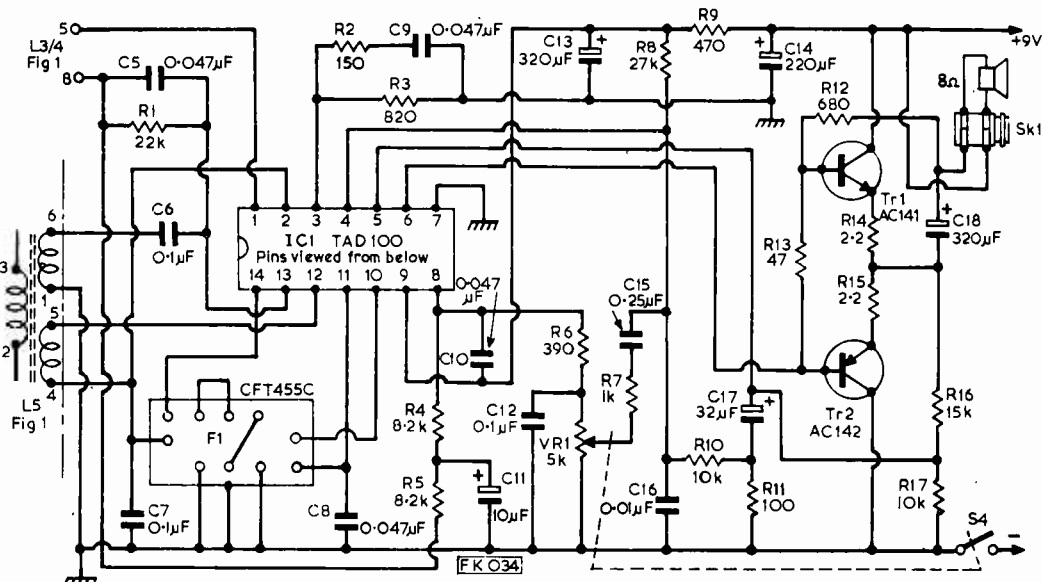


Fig. 2: Circuit diagram of the receiver and amplifier sections of the 'IC + 2'

oscillator coil and will go to S3. C10 has short leads to pins 8 and 9 of IC1.

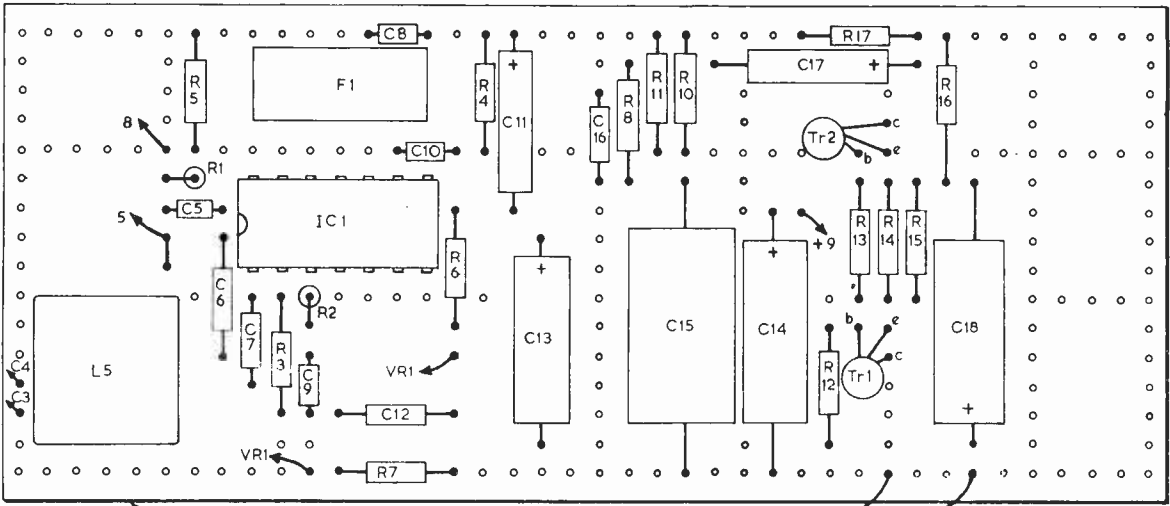A small soldering iron is necessary and care must be taken not to form very large joints or to bridge adjacent points with solder. The layout of components is quite compact though there is some free space.



FKO35  $4\frac{1}{4} \times 1\frac{5}{8}$  in. O-I in. matrix

Speaker via Sk1

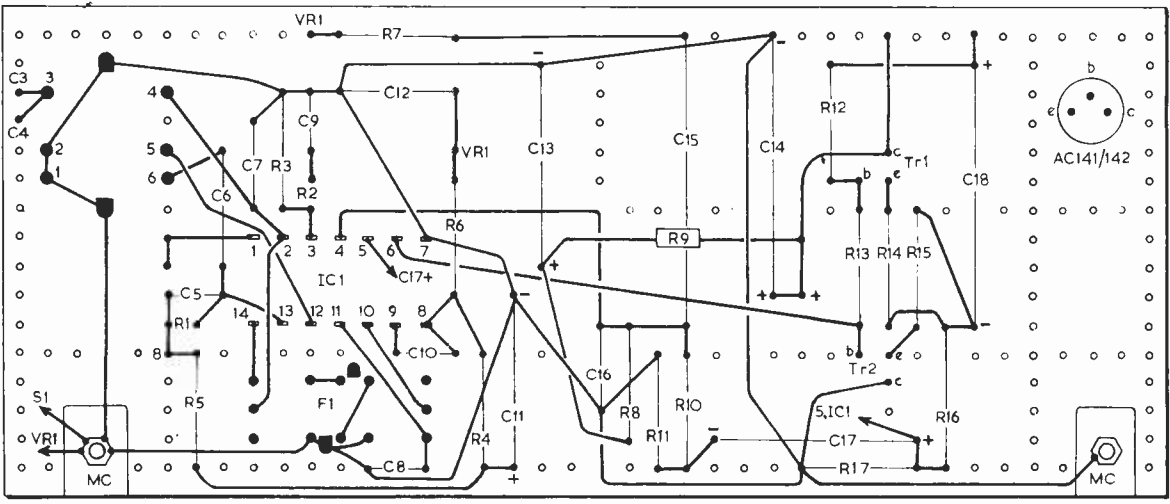


Fig. 3: Component layout on the perforated board. Use insulated wire for the underside wiring.

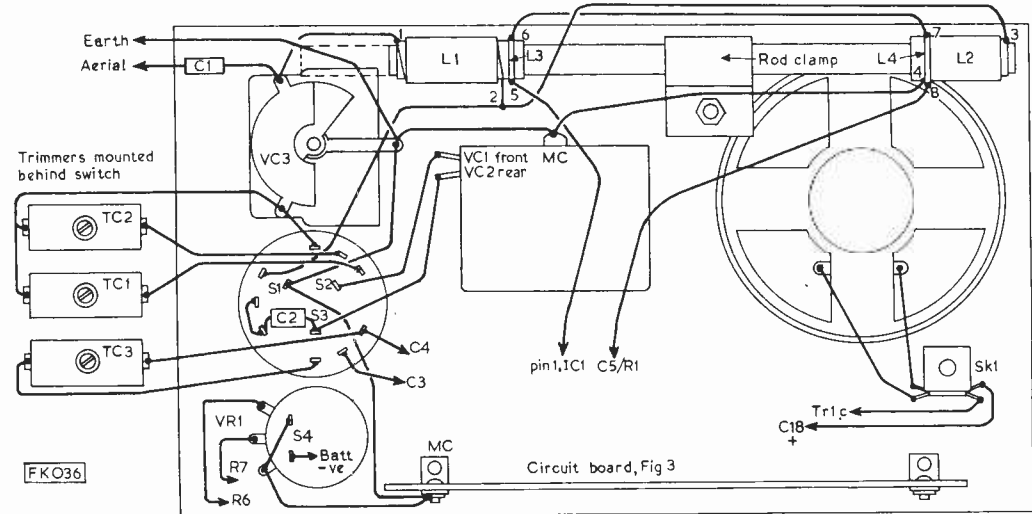


Fig. 4: Front panel component location and interwiring. Capacitors C3 and C4 are mounted between the board and the front panel.

The whole receiver is assembled on the panel of the case, so that it can be tested and adjusted easily. Connections here can be seen from Fig. 4.

VC1/VC2 is fixed with three 4BA countersunk bolts and is set back a little by placing extra nuts or washers between the capacitor and panel. If this is not done the control knob will project much more than necessary, since the spindle could, in any case, only be cut down very little, due to the integral reduction drive. VC1 is, the front section, having most plates, and VC2 the rear section.

The rotary switch is wired as shown except for the trimmers. These are then mounted by using 18 SWG or other stout wire directly to VC3 and the switch tags. These three trimmers are directly behind the switch.

## FERRITE AERIAL

A 1½in 6BA bolt passes through the panel and a spacer or extra nuts allows the rod to be clamped as in Fig. 4, by passing a strip of stout card round it.

A strip of paper about 1in to 1½in long is wound round the end of the rod, with a little adhesive, forming a tube which will allow L1/L2 to be slid along the rod. L1 begins at 1, and is 30 turns of 26SWG enamelled wire, close wound, ending at 2. L3 is two turns of any thin insulated wire, say 34 SWG, near L1.

As the MW section L2 is intended for use by itself 17 turns are unwound from its outer end. All the individual strands of the wire must be carefully cleaned and soldered together. This lead is 3, Figs. 1 and 4. L1 and L2 must be so phased that beginning at 1, continuing on to 2 and 3, and then to 4, all turns are in the same direction.

L4, already present with L2, is modified to leave only three turns. L3 and L4 must be in the same direction, as explained for L1 and L2. It is worth noting that the receiver can be tested on medium waves only by connecting L2, unmodified, to VC1 and chassis, and L4 to C5 and 1, IC1. Position the winding on the rod so that VC3 peaks up signal throughout the range.

## ALIGNMENT

This can be greatly simplified by using a signal generator or second receiver, but in any case efficiency is not lost provided VC3 can be rotated to peak up signals and is then not fully closed or fully open. However, band coverage does depend considerably on the trimmers and oscillator core setting.

If a calibrated receiver is available, place an insulated lead from its aerial socket near VC2. Switch to medium waves and close VC1/2. Unscrew the core of the oscillator coil until the oscillator frequency is 1165kHz, as shown by the receiver. If the receiver is not a type with a tuning indicator or BFO, the oscillator signal or carrier will be located only as a reduction in background noise, as when tuning in a station carrying no programme. The core can then be left in this position. Otherwise, unscrew the core a little, checking reception, until the MW band obtained is about 710-1565kHz. Any integral trimmers on the ganged capacitor should be left fully unscrewed.

Signals near the HF band end should peak up with VC3 about one-third closed. Position L2 on the rod so that VC3 is best in a similar position near the LF end of the band (VC1/2 nearly closed). With the

switch at 160, coverage depends on C3, and no other adjustment is provided. If 1.8 to 2MHz cannot be tuned, the oscillator coil core is probably wrongly set. There is some latitude, this range being about 1705 to 2145kHz. TC2 is adjusted so that the aerial circuit coverage is suitable, shown by VC3 not needing to be fully open for best volume.

When the switch is at 80, oscillator coil coverage is adjusted with TC3. There is not much latitude here, though a little over 3.5 to 3.8MHz can be tuned with the full swing of VC1/2. It is then necessary to set TC1 and if necessary also modify the position of L1 on the rod, until aerial coverage is similar, again as shown by VC3 peaking signals when rotated.


## NOTES

MW reception will usually be by means of the internal ferrite rod, through an external aerial naturally increases range. The ferrite rod will give sufficient pick-up of strong local signals on the 80m and 160m bands. It may be necessary to make use of the directional effects of the aerial by turning the whole receiver. However, normally an external aerial will be provided for 80m and 160m.

This aerial increases range and signal strength so that more transmissions can be heard, even if it is only a relatively short indoor wire. The aerial lead goes to C1. If a very long aerial is available, a further small capacitor or preset of about 50pF maximum can be put in this lead. For best reception an earthed connection should also be available, as this can increase signal strength to a worthwhile extent.

The aerial and earth sockets are on the side of the case with thin flexible leads running to them. The phones socket must be of fully insulated type, or separately insulated from the metal panel.

The dial is 2½ × 2¼in with a scale marked 0-100. It is covered with a piece of thin Perspex of the same size, fixed with the bolt holding the ferrite rod mount, and a second bolt near VC3. A transparent cursor with a line marked on it can be drilled to be a tight fit on a small grommet, which firmly grips the ¼in. spindle. Alternatively, a metal pointer could be soldered on. A piece of metal is shaped to hold the battery against the end of the case, and is bolted inside the case.

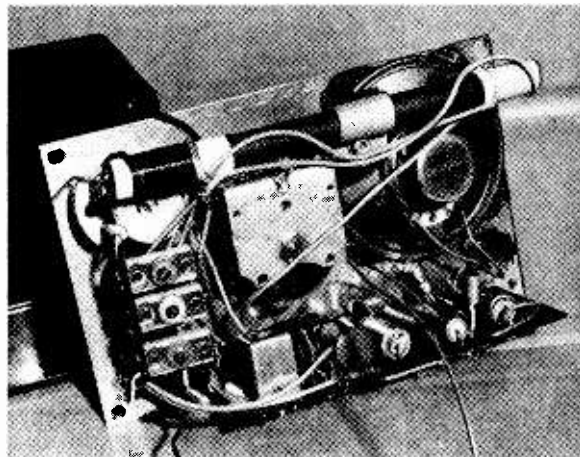

Internal view of the 'IC + 2' receiver (without BFO).

## OPTIONAL BFO

Broadcasts received on medium waves are AM or amplitude modulated and will be heard in the usual way. Some transmissions in the 160 and 80 metre bands are also AM. However, on the 80m amateur band in particular, a large number of single side-band and CW Morse transmissions will be present. A beat frequency oscillator is necessary to receive these and this can be assembled on the space provided at the end of the board, near the speaker. The BFO is not in use for the reception of AM signals, on any frequency.

Fig. 5 is the circuit of the BFO which is brought into operation by closing S5. The panel control VC4 allows fine adjustment of BFO frequency.

As the BFO pitch control now occupies the hole used for the phone socket, this has to be moved to the side of the case. It is also necessary to position the battery immediately against the speaker, and near the ferrite rod, so as to clear VC4 and the coil.

The coil is wound with 38SWG wire, Fig. 6. L6 has 165 turns and L7 has 40 turns. The former is approximately 7mm in diameter with an adjustable core. Begin winding near the base of the former, this being point C. Wind L6 in a pile occupying about 8mm winding length, ending at D. Leave a space of about 1mm and begin at A, winding L7 in a pile occupying about 4mm and terminating at B. The windings can be secured with a little adhesive and the ends are left long enough to reach the various connecting points.

Components for this stage are positioned and wired as in Fig. 6. S5 is a miniature slide switch, fitted in a slot near the speaker. VC4 is also a miniature component, secured with its bush nut. As the spindle of the specified VC4 is not  $\frac{1}{4}$ in in diameter, it is necessary to obtain a knob with a small hole, or to cut and shape a small piece of metal to pack out the spindle diameter. Or drill a  $\frac{1}{2}$ in length of plastic rod  $\frac{1}{4}$ in in diameter to fit the capacitor shaft.

No additional coupling into the receiver circuit was found necessary, other than that provided by stray capacitance and the unscreened coil.

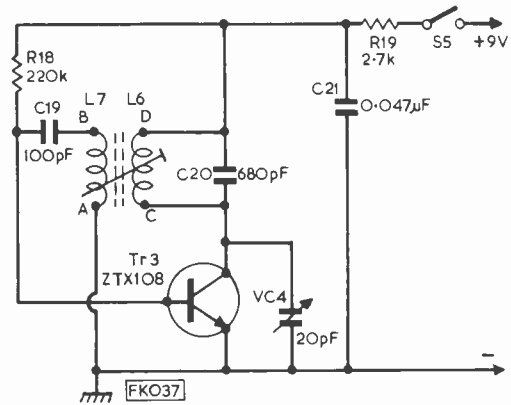


Fig. 5: Circuit diagram of the beat frequency oscillator.


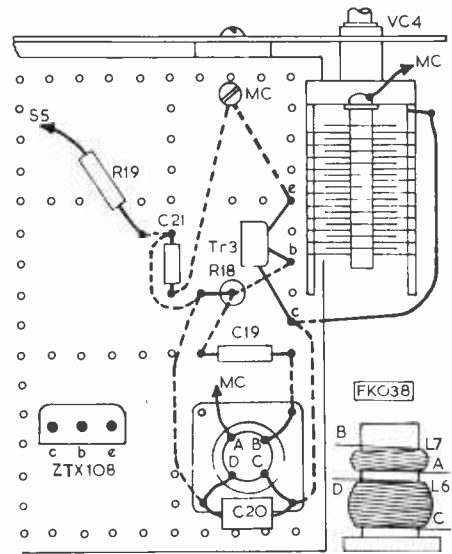


Fig. 6: Layout of the BFO components on the perforated board. The variable capacitor VC4 occupies the hole previously used for the jack socket.

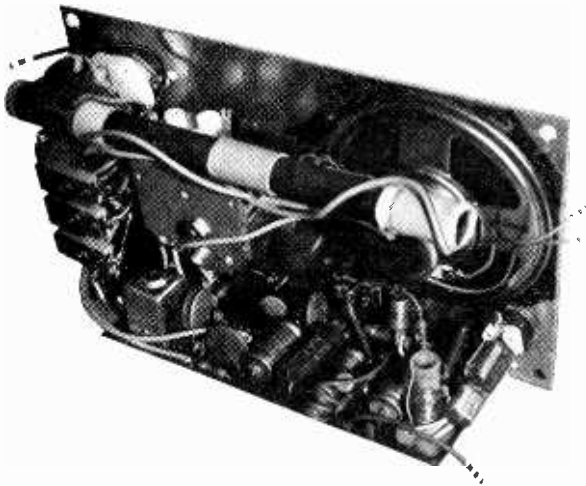

The 'IC + 2' receiver with the extra BFO components added.

## BFO ADJUSTMENT

The BFO can have no effect until it is adjusted to about the same frequency as the receiver intermediate frequency of 455kHz. To do this, half close VC4 and rotate the core of L6 until a strong heterodyne accompanies any AM signal tuned in. This is probably most easily done on the MW band. Check with more than one station to make sure the heterodyne is not a harmonic reaching the aerial circuit.

To receive CW, close S5 and adjust VC4 for the best note. For SSB reception, very careful adjustment of receiver tuning and VC4 are necessary. When CW or SSB signals are very strong, the aerial trimmer should be set to reduce them in power, so that VR1 can be near maximum gain. In this way the carrier of the BFO has sufficient strength to allow proper detection. A little use will soon show how the BFO control is adjusted.

Pw

# PRODUCTION LINES

colin riches

## LED DIGITAL WATCH DISPLAYS

Litronix, the optoelectronic and semiconductor manufacturer, has added four new low-power LED displays to its range of semiconductor devices for electronic digital watches. These 4-digit displays are mounted on small ceramic substrates measuring only 0.75in. long x 0.21in. high. To minimize area requirements, the packages are provided with solder bump contacts designed for reflow solder attachment to a watch module. Designated the DL-5175 Series, the displays are available in four different types, each with colon between second and third digits:

The DL-5175 is a 4-digit display of continuous-line monolithic digits 0.1 in. high.

The DL-5176 is a 3-1/2 digit hybrid display of characters 0.115in. high. The DL-5177 is a 4-digit display in a monolithic package with digits magnified to create 0.1in. high characters.

The DL-5178 is a 4-digit version of the DL-5176 for a 24-hour watch. Prices start at £3.66 in quantities of 1000.

All displays are manufactured from specially selected high-brightness materials which minimize drive current requirements, and enhance visibility in high ambient light. In the case of the DL-5177 the use of a



magnifying lens, which concentrates the emitted light into a narrow cone, makes it particularly suited to veiling in bright sunlight.

The pin-out configuration of the DL-5175 Series has been optimized to allow close spacing of associated integrated circuits, such as the Litronix LBC-1060 and LBC-1070 bipolar drivers.

For further information on these digital watch displays, contact *Bill Stott, Product Marketing Manager, Litronix, Bevan House, Bancroft Court, Hitchin, Herts, SG5 1LW.*

## BIB RECORD DUST-OFF

BIB announce a new BIB Record Dust-off, for removing dust and dirt quickly and simply from gramophone records to reduce record and stylus wear.



Normally it is recommended that the Dust-Off is used dry, but it has been designed so that it can be used in a moist condition if records are excessively dirty. The BIB Dust-Off comes complete with a clear protective cover in which is included a foam pad which can be moistened with BIB liquid cleaner so that when the Dust-Off is inserted into the cover the velvet surface and absorbs the moisture from the foam pad evenly.

The handle of the BIB Dust-Off is moulded in a simulated teak finish and the cleaning pad is covered in a smart, special purpose, high quality red velvet.

Recommended Retail Price of the Dust-Off is 66p each, excluding VAT. *BIB Hi-Fi Accessories Ltd., P.O. Box 78, Hemel Hempstead, Herts. HP2 7EP.*

## POCKET TEST METER

No bigger than a packet of cigarettes, the new ICE Microtest 80 test meter combines several unique features in one compact and accurate instrument.

Covering 8 fields of measurement and 40 ranges, the meter has a 20,000 ohm per volt sensitivity, with 2% accuracy on the a.c. and d.c. scales.

Design of the meter incorporates special automatic electronic regulation for zero ohms, and the movement is protected against an overload of 1,000 times in the ohmic ranges before automatic cut out. Protecting the low ohmic ranges is an internal fuse unit, easily repaired by winding on a fuse from a minute, internal bobbin.


The shockproof movement, with a compensated magnetic core provides a closed magnetic circuit screened against all external magnetic fields. The 20 components are housed on a printed circuit board, making replacement of components fairly easy.

Power is from a special 1.35V mercury battery which, in normal usage, will last up to 3 years. A complete range of accessories is available with the meter to extend its performance.

Incorporated into the design of the Microtest 80 are the latest-type manganese and metallic film resistors giving high stability and precision of 0.5%, while the mirror scale gives clear and accurate reading.

Each test meter is supplied with a comprehensive instruction manual, and a protective case incorporating the leads. Size is 90mm x 70mm x 18 mm.

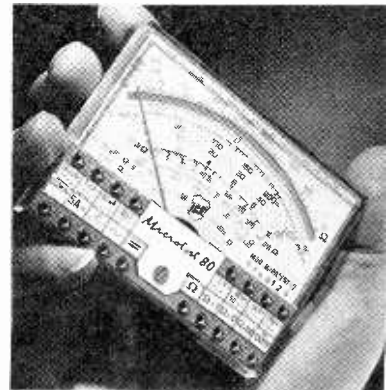Meters or further information available direct from the sole UK importers, *Electronic Brokers Ltd., of 49, Pancras Road, London NW1 2QB*, the Microtest 80 is priced at £11.95 ex VAT with special terms for quantity purchases.



*The Microtest 80 mini-meter.*



## HAM II ROTATOR

The Ham II rotator system, available from South Midlands Communications Ltd. is designed for Amateur aerial systems with a maximum of 7.5 sq. ft. It provides a full 360° range of rotation and aerial position is indicated on a meter scale.

The rotator motor, radial and thrust bearings, electrically-operated wedge brake, gear train and indicating sensing device are built into the bell-shaped aluminium housing.

The control unit utilises two transformers. One supplies 30V a.c. for releasing the brake and operating the motor when the control levers are operated. Transformer overheating is eliminated by a thermal cut-out switch in the primary winding.



The meter transformer is energised as the on/off control is switched to the "on" position (see diagram). Rotator size is 8in diameter and 20in high. Brake torque is 3,500in./lbs. and an 8-core cable is required between control unit and motor. Rotator weight is 12½lbs and power requirement 240V a.c.

These rotators are actually made in America but imported and retailed by *South Midlands Communications Limited* who will be pleased to supply details of prices etc. upon receipt of a stamped, addressed envelope. Their address is *S. M. House, Osborne Road, Totton, Southampton, SO4 4DM.*

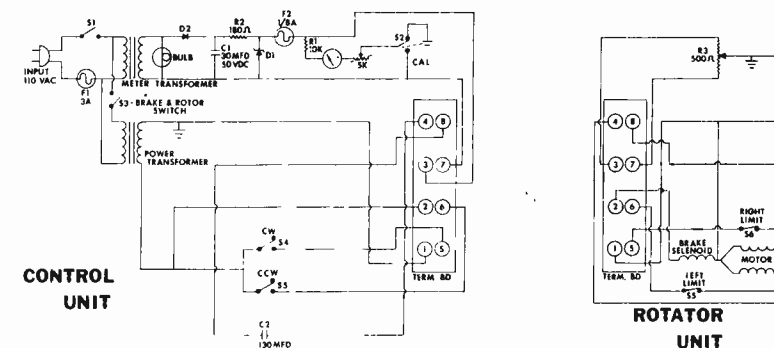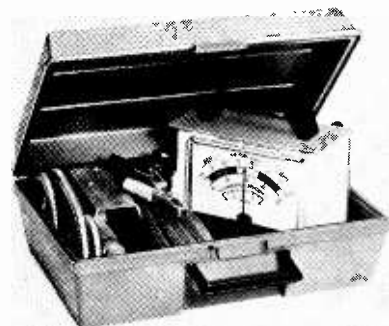
## EXHAUST GAS ANALYSER

With the new Heathkit CI-1080 Exhaust Gas Analyser, you can easily monitor exhaust output for minimum pollution and maximum efficiency. The CI-1080 will indicate relative combustion efficiency, air-fuel ratio and percentage of carbon monoxide from the exhaust emission of four cycle automotive engines. For best results, readings should be taken before and after an engine tune-up.

The CI-1080 consists of a large 4½in. meter and sensor which fit snugly inside the durable polystyrene carrying case. For operating power, the colour coded battery clips can be



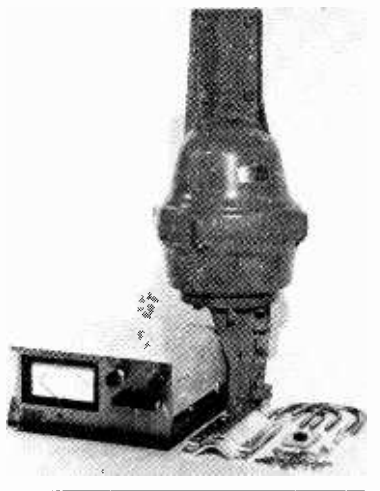(Above) circuits (110V version) of the control unit and rotator unit  
(Below) control unit and rotator.



attached to any 6 or 12 volt car battery. The meter is designed to hang on a partially open car door window or sit on any convenient flat surface. Flexible stainless steel tubing diverts exhaust gas from the engine exhaust pipe to the sensor where thermal conductivity of the gas is measured. A sensitive bridge circuit built into the instrument translates this measurement into units of air-fuel ratio, combustion efficiency (%) and carbon monoxide (%). These readings indicate the proper interaction of carburettor and ignition settings.

Operation of the CI-1080 is simple. After warming the engine to normal operating temperature and connecting the battery clips, the meter is adjusted to the balance point using the balance control. The flexible tubing is then connected to the sensor and the other end inserted into the exhaust pipe. After the meter stabilizes, readings can be taken. The kit K/CI-1080 costs £34.60 or Assembled: A/CI-1080 £49.90. (Including 8% VAT and delivery within the United Kingdom). *Heath (Gloucester) Ltd., Bristol Road, Gloucester GL1 6EE.*

## DIGITAL CAR CLOCK/TIMER KIT

On the Heathkit GC-1093 digital electronic car clock/timer, hours and minutes are displayed in bright orange on 7-segment Beckman planar gas discharge tubes—even visible in direct sunlight! When the sun goes in, the clock readout automatically dims so that the car driver won't be distracted while driving at night.

A quartz crystal time base and solid-state digital electronic circuitry combine to give the clock an accuracy of within one minute per month. The low-voltage clock memory is designed to maintain this accuracy even during battery-draining starting on cold mornings.

At the touch of a button on the front panel, the clock turns into a precise elapsed timer with a 20-hour capability. During the first ten minutes of elapsed timing, the digital readout is in minutes and seconds. Thereafter, readout is in hours and minutes for up to 20 hours. The clock readout can be recalled at any time without disturbing the memory of either the clock or the timer.

The GC-1093 kit is priced at £39.90 (this includes 8% VAT and delivery within the UK). *Heath (Gloucester) Ltd., Gloucester GL1 6EE.*



Please mention "Practical Wireless" when contacting manufacturers and suppliers whose addresses are given in "Production Lines".

# NEW LOW PRICES!

## Sinclair Scientific kit

(Was £19.95 - save £5!)

**£14.95**  
(INC. VAT)

### Britain's most original calculator now in kit form

The Sinclair Scientific is an altogether remarkable calculator.

It offers logs, trig, and true scientific notation over a 200-decade range - features normally found only on calculators costing around £100 or more.

Yet even ready-built, the Sinclair Scientific costs a mere £21.55 (including VAT).

And as a kit it costs under £15!

### Forget slide rules and four-figure tables!

With the functions available on the Scientific keyboard, you can handle directly

- sin and arcsin,
- cos and arccos,
- tan and arctan,
- automatic squaring and doubling,
- log<sub>10</sub>, antilog<sub>10</sub>, giving quick access to x<sup>Y</sup> (including square and other roots),
- plus, of course, addition, subtraction, multiplication, division, and any calculations based on them.

In fact, virtually all complex scientific or mathematical calculations can be handled with ease.

### So is the Scientific difficult to assemble?

No. Powerful though it is, the Sinclair Scientific is a model of tidy engineering.


All parts are supplied - all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our Service Department will back you throughout if you've any queries or problems.

Of course, we'll happily supply the Scientific or the Cambridge already built, if you prefer - they're still exceptional value. Use the order form.

Components for Scientific Kit (illustrated)

1. Coil
2. LSI chip
3. Interface chips
4. Case mouldings, with buttons, windows and light-up display in position
5. Printed circuit board
6. Keyboard panel
7. Electronic components pack (diodes, resistors, capacitors, etc)
8. Battery assembly and on/off switch
9. Soft carrying wallet
10. Comprehensive instructions for use

Assembly time is about 3 hours.

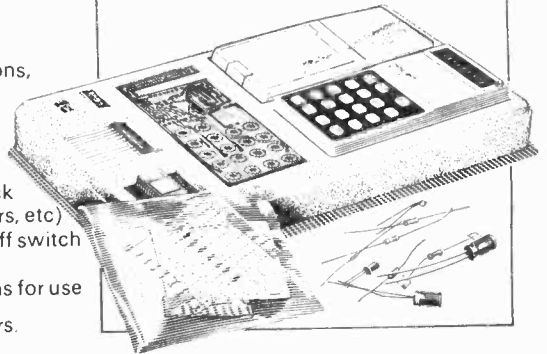

## Features of the Sinclair Scientific

- 12 functions on simple keyboard  
Basic logs and trig functions (and their inverses), all from a keyboard as simple as a normal arithmetic calculator's. 'Upper and lower case' operation means basic arithmetic keys each have two extra functions.

- Scientific notation  
Display shows 5-digit mantissa, 2-digit exponent, both signable.

- 200-decade range  
10<sup>-99</sup> to 10<sup>+99</sup>

- Reverse Polish logic  
Post-fixed operators allow chain calculations of unlimited length - eliminate need for an = button.

- 25-hour battery life  
4 AAA manganese alkaline batteries (e.g. MN2400) give 25 hours continuous use. Complete independence from external power.

- Genuinely pocketable  
4 1/3" x 2" x 11/16".  
Weight 4 oz. Attractively styled in grey, blue and white.



# NEW LOW PRICES!

## Sinclair Cambridge kit

(Was £14.95—save £5!)



At its new low price, the original Sinclair Cambridge kit remains unbeatable value.

In less than a year, the Cambridge has become Britain's most popular pocket calculator.

It's not surprising. Check the features below — then ask yourself what other pocket calculator offers such a powerful package at such a reasonable price.

### Components for Cambridge Kit

1. Coil
2. LSI chip
3. Interface chip
4. Thick film resistor pack
5. Case mouldings, with buttons, window and light-up display in position
6. Printed circuit board
7. Keyboard panel
8. Electronic components pack (diodes, resistors, capacitors, transistor)
9. Battery clips and on/off switch
10. Soft wallet

Assembly time is about 3 hours.

### Take advantage of this money-back, no-risk offer today

The Sinclair Cambridge and Scientific kits are fully guaranteed. Return either kit within 10 days, and we'll refund your money without question. All parts are tested and checked before despatch — and we guarantee any correctly-assembled calculator for one year. (This guarantee also applies to calculators supplied in built form.)

Simply fill in the preferential order form below and slip it in the post today.

### Scientific

Price in kit form £14.95 inc. VAT


Price built £21.55 inc. VAT.

### Cambridge

Price in kit form £9.95 inc. VAT.

Price built £13.99 inc. VAT.

## Features of the Sinclair Cambridge

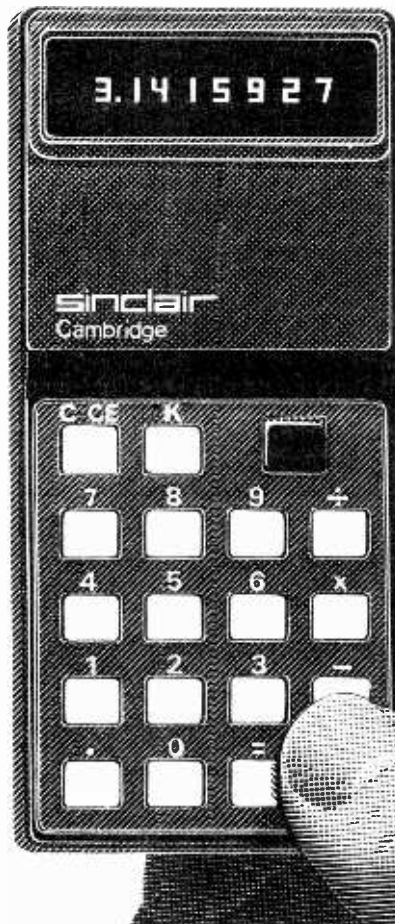

- Uniquely handy package. 4 1/3" x 2" x 1 1/16", weight 3 1/2 oz.
- Standard keyboard. All you need for complex calculations.
- Clear-last-entry feature.
- Fully-floating decimal point.
- Algebraic logic.
- Four operators ( +, -, ×, ÷ ), with constant on all four.
- Powerful constant with separate 'K' button.
- Constant and algebraic logic combine to act as a limited memory, allowing complex calculations on a calculator costing less than £10.
- Calculates to 8 significant digits.
- Clear, bright 8-digit display.
- Operates for weeks on four AAA batteries.

To: Sinclair Radionics Ltd,  
FREEPOST St Ives,  
Huntingdon, Cambs. PE17 4BR

Please send me

- Sinclair Scientific kit at £14.95
- Sinclair Scientific built at £21.55
- Sinclair Cambridge kit at £9.95
- Sinclair Cambridge built at £13.99

All prices include 8% VAT.

\*I enclose a cheque for £....., made out to Sinclair Radionics Ltd, and crossed.

\*Please debit my \*Barclaycard/ Access account. Account number

--	--	--	--	--	--	--	--	--	--	--	--

\*Delete as required.

Signed \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

Please print. FREEPOST — no stamp needed.

PW/4/75

# sinclair

Sinclair Radionics Ltd,  
FREEPOST St. Ives,  
Huntingdon, Cambs. PE17 4BR.

Reg. No: 699483 England. VAT Reg. No: 213 8170 88.

1119

# QUIZ MONITOR

A. FOWELL



ANYONE who has ever attempted to organise a quiz, either between friends or within the family, will no doubt have watched with envy the smooth running of such television programmes as University Challenge, Top of the Form, etc. In the home quiz, however, a free-for-all situation arises where a question is asked and whoever shouts first is allowed to answer! The difficulty here being in deciding who shouted first! In the TV programmes already mentioned the problem is solved using a buzzer system.

The quiz monitor described in this article was designed with a view to recreating a "University Challenge" atmosphere by providing each player with a button. The first button pressed turns on a corresponding light on the main console and sounds a buzzer. Once this has happened all other players are automatically excluded, and, although the buzzer stops upon releasing the button, the light remains on until cancelled by the quiz master.

## Circuit

The complete circuit of the quiz monitor for up to four players is shown in Fig. 1. At first sight the circuit looks rather complicated but its operation can

be readily understood by considering the action of a similar circuit, but for two players only, Fig. 2.

PB3 is a normally closed push button, whilst PB1 and PB2 are normally open. The values of R1, R2, R3 and R4 are chosen so that on closing PB1, sufficient gate current flows to trigger TH1 into conduction and LP1 therefore lights up. The voltage on TH1 anode falls to about 1V under these conditions, so the cathode of D2 is firmly fixed at a potential of 1V. The junction of R5 and R6 cannot therefore rise above about 1.6V, even if PB2 is pressed. R6 and R7 are chosen so that under this condition there is insufficient drive to the gate of TH2 to cause it to conduct. The same arguments apply if the other button is pressed first.

Due to normal thyristor action LP1 will remain illuminated even when PB1 is released, and it can only be extinguished by momentarily reducing the current through TH1 to zero. PB3 is included in the circuit for this purpose and is under the control of the quiz master. The thyristors specified are sensitive gate types which necessitate the use of R4 and R8. These prevent premature firing of the thyristor

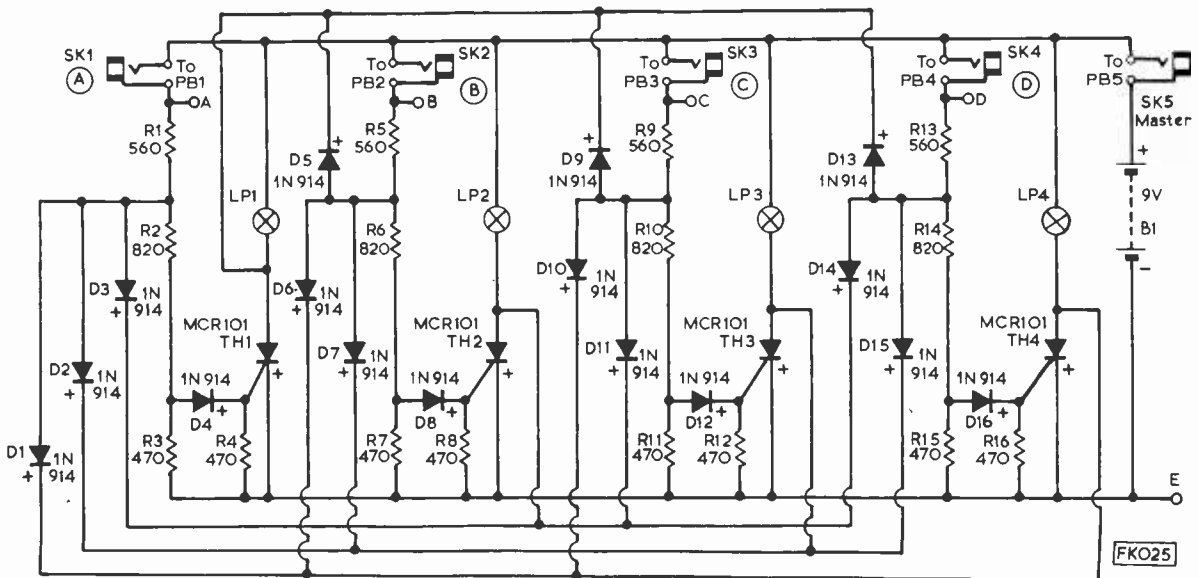


Fig. 1: Circuit diagram of the monitor proper the output being fed to the buzzer circuit of Fig. 3.

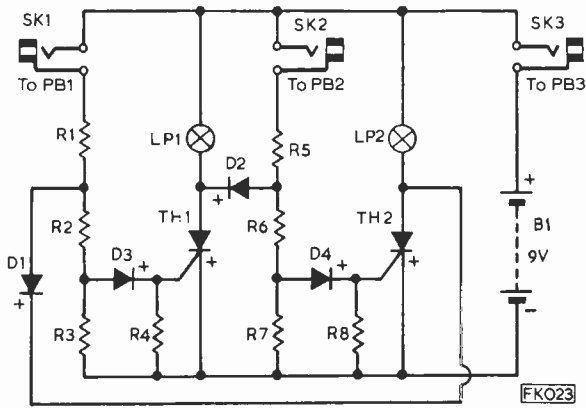


Fig. 2: A simplified circuit for two players only, to illustrate the operation of the monitor.


by providing a low impedance path to earth for any noise signals that may be present.

It is possible for the bulbs to light simultaneously if both buttons are pressed at precisely the same moment. In practice, however, this does not happen very often, but when it does it is reasonable to consider the situation as a draw. Diodes D3 and D4 are included in order to make the values of R2, R3, R6 and R7 relatively unimportant.

From this discussion it can be seen that from each stage of the circuit there must be one diode to every other stage. Thus for the four-channel circuit, Fig. 1, there are 12 diodes acting as feedback elements to other stages.

## Audible Warning

Fig. 3 shows the buzzer circuitry. Diodes D17 to D20 act in conjunction with Tr1, R17 and R18 as a logic 'OR' gate, i.e. if any of the four buttons are pressed then Tr1 is turned on and the buzzer sounds. Diode D21 is essential to prevent high voltage spikes,

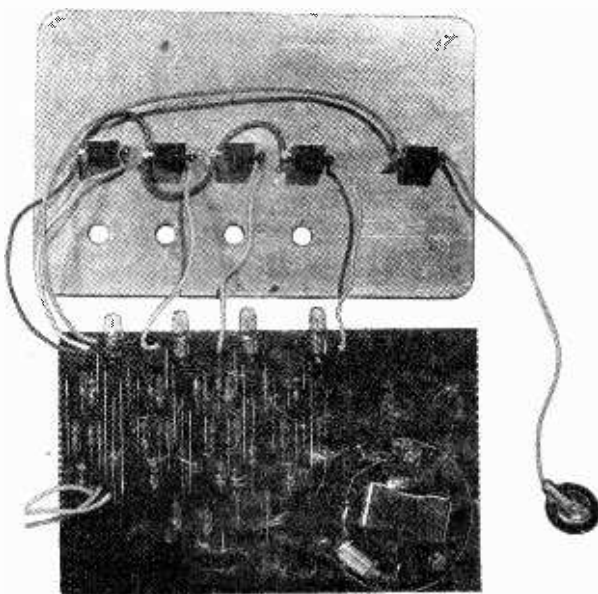

Finished circuit board wired to panel sockets. The lamps protrude through the holes in the panel.

due to the inductance of the buzzer coil, from damaging Tr1. C1 is included to minimise interference from the buzzers' contacts.

It will be noted that separate batteries are used for the main circuit and for the buzzer. The reason for this is twofold. First, the buzzer used only requires around 4.5V and it is difficult to design the rest of the circuit to work reliably off such a low voltage. Second, and more important, is the fact that the buzzer draws about 1A from a 9V supply. This causes a substantial voltage drop which can upset the operation of the main circuit.

## Construction

The prototype was built into a plastic instrument case measuring approximately 6 x 4 x 4in, although any case of about this size will suffice. All of the electronics, including the buzzer, are mounted on a piece of 0.1in pitch veroboard about 5<sup>3</sup>/<sub>4</sub>in x 3<sup>1</sup>/<sub>4</sub>in. The copper tracks need to be cut at several points, and these are indicated, with the corresponding component layout, in Fig. 4. The veroboard required is slightly longer than the standard 5in length, but if the buzzer can be accommodated elsewhere within

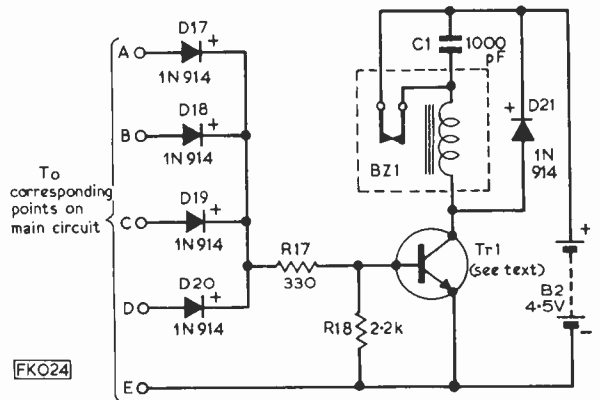


Fig. 3: Buzzer circuitry and input diodes fed from main circuit, Fig. 1.

the box, then the board dimensions can be reduced to 4 x 3<sup>1</sup>/<sub>4</sub>in.

The 21 diodes can be any general purpose signal type but D4, D8, D12 and D16 must be silicon since the forward voltage drop of germanium, about 0.2V, is too low for this part of the circuit. It is also recommended that the specified type of thyristor is used since its operating conditions are quite critical. The bulbs are 12V Lilliput types, which, with the 9V supply, only consume about 50mA. Bulb holders were dispensed with, for cheapness, and the bulbs soldered directly to the veroboard. Provided the soldering operation is carried out quickly the bulbs should not be damaged.

PB1 and PB4 can be ordinary bell pushes which are readily available very cheaply. PB5, on the other hand, must be a normally closed type, and may be a little more difficult to obtain. Tr1 can be any silicon NPN transistor with a collector current rating of at least 500mA. The buzzer is a standard domestic type which is easily obtainable at most electrical retailers.

The instrument case used for the prototype has two sets of slots moulded into it. These are used to secure the veroboard and an aluminium plate, the same size as the circuit board, which holds the two



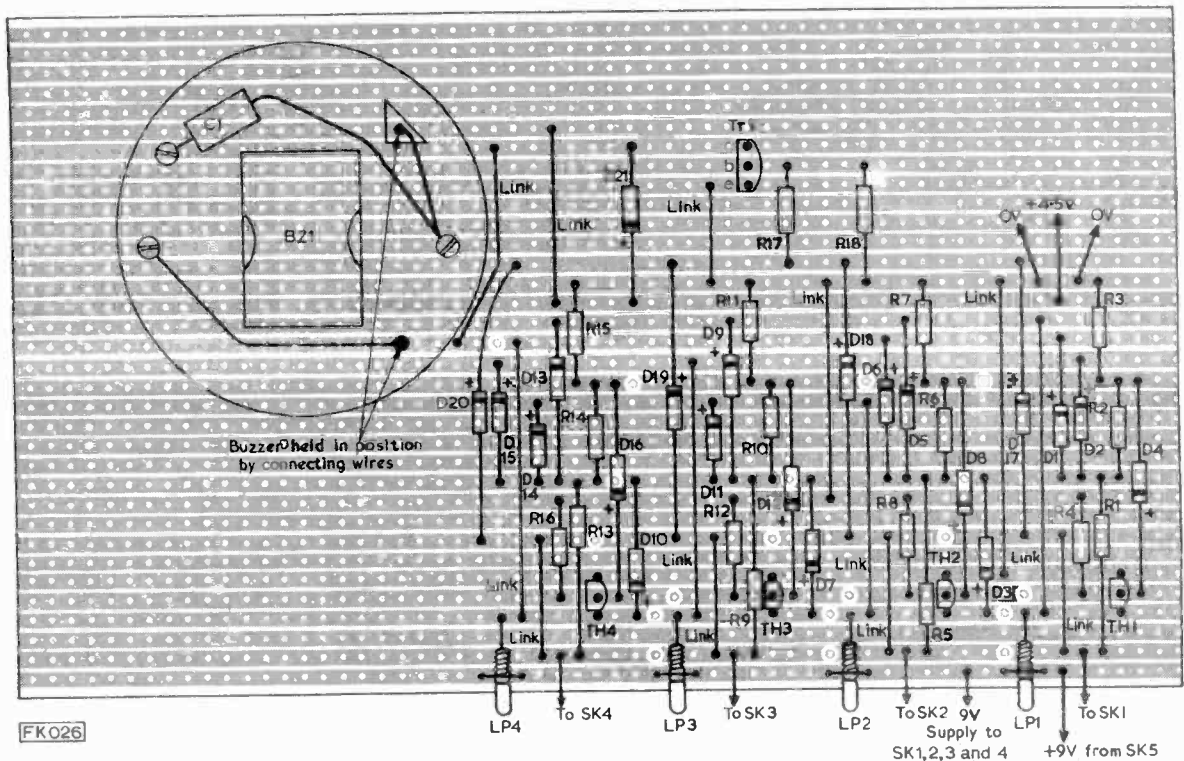


Fig. 4: Component layout on circuit board. Note carefully the breaks in the copper rails.

## ★ components list

### Resistors

R1 560Ω	R10 820Ω
R2 820Ω	R11 470Ω
R3 470Ω	R12 470Ω
R4 470Ω	R13 560Ω
R5 560Ω	R14 820Ω
R6 820Ω	R15 470Ω
R7 470Ω	R16 470Ω
R8 470Ω	R17 330Ω
R9 560Ω	R18 2·2kΩ

All  $\frac{1}{4}$  or  $\frac{1}{2}$ W 10%

### Capacitor

C1 1000pF 15V

### Semiconductors

TH1  
TH2  
TH3 } Motorola MCR 101 (0·5A)  
TH4

D1 to D20 1N914, 1N916 etc.

Tr1 2N3053 (Silicon NPN type with collector current rating of 500mA. min.)

### Miscellaneous

Four normally open push buttons. One normally closed push button. Five 2·5 or 3·5mm jack sockets and plugs. Four Lilliput 12V bulbs. Friedland 'Mini buzzer' or similar. PP7 (9V) and 1289 (4·5V) batteries.

Constructors of this monitor will be interested in the Reaction Timer also described in this issue.

batteries. The front panel, again of aluminium, completes the case and holds the circuit and chassis in position, see photographs.

The five push-buttons are connected to the circuit by means of panel-mounted jack sockets and plugs. It will be noted that no on/off switch is included since, with the bulbs and buzzer off, the current taken is only the leakage current of the thyristors and Tr1, which is negligible. If the unit is to be left for any length of time the batteries can be disconnected.

No great difficulty should be encountered in the construction of this project but the following points may be helpful. Make sure that adjacent tracks on the veroboard are not shorted out by blobs of solder. This is easily avoided by the use of a soldering iron with a bit diameter of no more than  $\frac{1}{16}$ in. Secondly, cut the veroboard track in accordance with Fig. 4 before mounting the components as it will be difficult to do so afterwards.

## Testing

Having completed the unit, connect the batteries and press any one button. The corresponding bulb should light and remain lit upon releasing the button. The buzzer should also sound during the time the button is pressed. Pressing PB5 should extinguish the light. Repeat this test with each of the other three buttons. Now, press one button, bringing on the corresponding light, and press each of the other three buttons. The buzzer should sound each time but the original light only should be lit. If any part of these two tests fails then it is likely that one or more of the diodes is either not connected or is connected the wrong way round.



GIRO NO. 331 7056. Access accepted.  
C.W.O. only. P. & P. 10p on orders below £5.  
Discount: 10-10%, £20-15% (except net items)  
Export Order enquiries welcome (VAT free)

Official Orders accepted from  
Educational & Government Departments  
ALL PRICES INCLUDE VAT AT 8%

**SPECIAL RESISTOR KITS** (Prices include post & packing)

10E12 1/2W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.58 net  
10E12 1/4W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), £3.77 net  
25E12 1/2W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £8.19 net  
25E12 1/4W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), £8.28 net  
5E12 1/2W KIT: 5 of each E12 value, 10 ohms—1M, a total of 305 (METAL FILM 5%), £2.80 net  
Due to current world shortages, resistor kits may contain some wattage and value substitutions.

**MULLARD POLYESTER CAPACITORS C280 SERIES**

250V P.C. Mounting: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 3.3p, 0.068µF, 0.1µF, 4.7p, 0.15µF, 4.7p, 0.22µF, 5.1p, 0.33µF, 8p, 0.47µF, 9p, 0.68µF, 12p, 1µF, 15p, 1.5µF, 23p, 2.2µF, 26p.

**MULLARD POLYESTER CAPACITORS C296 SERIES**

400V: 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 0.0047µF, 2.1p, 0.0068µF, 0.01µF, 0.015µF, 0.022µF, 0.033µF, 3.3p, 0.047µF, 0.068µF, 0.1µF, 4.7p, 0.15µF, 6.3p, 0.22µF, 8.1p, 0.33µF, 12p, 0.47µF, 14p.  
160V: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 0.068µF, 3.3p, 0.1µF, 4.7p, 0.15µF, 5p, 0.22µF, 5.1p, 0.33µF, 6.3p, 0.47µF, 8.1p, 0.68µF, 12p, 1µF, 14p.

**MINIATURE CERAMIC PLATE CAPACITORS**

50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8, (µF) 0.01, 0.015, 0.022, 0.033, 0.047, 2.1p, each 0.1, 30V, 5p.

**POLYSTYRENE CAPACITORS 160V 5%**

(pF) 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 6800, 10,000, 4.7p.

**RESISTORS**

CF—High Stab Carbon Film, 5% MF—High Stab Metal Film, 5%.

W. Type Range	1-99	100-499	500-999	1000+	Size mm
CF 22-1M	1	0.75	0.60	0.55	2.4x7.5
CF 22-2M2	1	0.75	0.60	0.55	3.9x10.5
CF 22-1M	1	0.75	0.60	0.55	5.5x16
MF 10-2M7	2	1.54	1.32	1.1	3x7
MF 10-2M2	2	1.43	1.21	0.99	4.2x10.8
MF 10-10M	3	1.98	1.81	1.65	6.6x13
MF 10-10M	4.5	3.52	3.08	2.75	8x17.5

For value mixing prices, please refer to our catalogue. (price in pence each).  
VALUES AVAILABLE—E12 Series only. (Net prices above 100)

**PRESET SKELETON POTENTIOMETERS**

MINIATURE 0.25W Vertical or horizontal 6p each 1K, 2K2, 4K7, 10K, etc. up to 1M Ω  
SUB-MIN 0.05W Vertical, 100 Ω to 220K Ω 5p each.



**B. H. COMPONENT FACTORS LTD.**

(P.W.) LEIGHTON ELECTRONICS CENTRE,  
59 NORTH ST., LEIGHTON BUZZARD, BEDS.  
Tel.: LEIGHTON BUZZARD 2316 (STD. Code 05253)  
CATALOGUE No. 3 20p

**Miniature Mullard Electrolytics**

1.0µF 63V	61p	68µF 63V	12p
1.5µF 63V	61p	100µF 10V	61p
2.2µF 63V	61p	100µF 25V	61p
3.3µF 63V	61p	100µF 63V	14p
4.0µF 40V	61p	150µF 16V	61p
4.7µF 63V	61p	150µF 63V	15p
6.8µF 63V	61p	220µF 16V	61p
8.2µF 40V	61p	220µF 10V	61p
10µF 25V	61p	220µF 63V	8p
10µF 63V	61p	220µF 63V	21p
15µF 16V	61p	330µF 16V	12p
15µF 63V	61p	330µF 63V	25p
16µF 40V	61p	470µF 6.4	9p
22µF 25V	61p	470µF 40V	20p
22µF 63V	61p	680µF 16V	15p
32µF 10V	61p	680µF 40V	25p
33µF 16V	61p	1000µF 16V	20p
33µF 40V	61p	1000µF 25V	25p
32µF 63V	61p	1500µF 6.4	15p
47µF 10V	61p	1500µF 16V	25p
47µF 25V	61p	2200µF 10V	25p
47µF 63V	8p	3300µF 6.4	26p
68µF 16V	61p		

**VEROBOARD 0.1 0.15**

2 1/2 x 5"	36p	36p
2 1/2 x 3 1/2"	33p	25p
3 1/2 x 5 1/2"	42p	46p
3 1/2 x 3 1/2"	36p	36p
2 1/2 x 1"	9p	9p
2 1/2 x 5" (Plain)	—	19p
2 1/2 x 3 1/2" (Plain)	—	19p
5 x 3 1/2" (Plain)	—	29p
Insertion tool	73p	73p
Track Cutter	56p	56p
Pins, Pkt. 25	22p	22p

**TRANSISTORS**

AC127	161p	BC212L	13p
AC128	23p	BC213L	12p
BC107	11p	BC214L	17p
BC108	12p	OC44	18p
BC109	13p	OC71	13p
BC148	12p	OC81	16p
BC149	12p	OC170	23p
BC182L	12p	T1S43	33p
BC183L	12p	2N2926	11p
BC184L	13p	2N3702	11p

**POTENTIOMETERS**

Carbon Track 5K Ω to 2M Ω, log or lin (and 1K lin). Single, 161p Dual Gang 46p. Log single with switch 26p. Slider Pots. 10K, 100K, 500K, semi log 30mm, 34p, 45mm, 47p, 60mm, 55p.

**DIODES**

IN4001	61p	DIN 2 Pin	12p
IN4002	71p	3 Pin	13p
IN4003	9p	5 Pin 180°	16p
IN4004	90p	Std. Jack	20p
IN4005	12p	2.5mm Jack	13p
IN4006	14p	Phono	6p
IN914	7p	<b>SOCKETS</b>	
IN916	7p	DIN 2 Pin	10p
BA100	10p	3 Pin	10p
OAS	42p	5 Pin 180°	12p
OAS7	9p	Std. Jack	15p
OAS8	11p	2.5mm Jack	13p
OAS20	8p	Phono	6p

**PLUGS**

1/25, 2/25, 4/25, 4/710, 5/25, 8/25, 10/10, 10/50, 16/25, 22/63, 25/25, 25/50, 32/25, 50/25, 100/10, 100/25, 61p, 50/50, 8p, 100/50, 200/25, 11p, 250/50, 10p, 500/10, 11p, 500/25, 15p, 500/50, 18p, 1000/10, 15p, 1000/25, 22p, 1000/50, 40p, 2000/10, 20p, 1000/100, 88p, 2000/25, 30p, 2000/100, 93p, 2500/25, 30p, 2500/50, 61p, 5000/25, 68p, 5000/50, £1.08.
---

**SOCKETS**

HI-VOLT: 4/350, 14p, 8/350, 19p, 100/100 20p, 16/350, 22p, 100/100, 20p, 100/25, 30p.
---

**METALLISED PAPER CAPACITORS**

250V: 0.05µF, 0.1µF, 6p, 0.25, 6p, 0.5µF, 7.1p, 1µF, 9p, 500V: 0.025, 0.05, 6p, 0.1, 6p, 0.25, 7.1p, 0.5, 9p, 1000V: 0.01, 11p, 0.022, 13p, 0.047, 0.1, 15p, 0.22, 23p, 0.47, 34p.

**PLEASE NOTE OUR NEW ADDRESS**

Our new Electronics Centre is now open in Leighton Buzzard and all callers are welcome. As well as our normal stock of over 2000 product lines, we have a large range of surplus equipment. Bargains, Calculators, etc. **OPEN 6 DAYS 9 to 5 (shut 12.30 to 1.30).**

**NEW KIT**

5E12 1/2W Metal Film, 5 each value 10Ω-1M, total of 305 £3.25

**MULTIMETER U4323**

22 Ranges plus AF/IF Oscillator 20,000Ω/Volt.  
Vdc—0.5—1000V in 7 ranges  
Vac—2.5—1000V in 6 ranges  
Idc—0.05—500mA in 5 ranges  
Resistance—5Ω—1MΩ in 4 ranges.  
Accuracy—5% of F.S.D.  
OSCILLATOR—1 KHz and 465 KHz (A, M) at approx. 1 Volt.  
Size—160 x 97 x 40mm.  
Supplied complete with carrying case, test leads and battery.  
PRICE £8.30 net p & p 25p.



U4323

**MULTIMETER U4341**

27 Ranges plus Transistor Tester. 16,700Ω/Volt. Overload protected.  
Vdc—0.3—900V in 8 ranges.  
Vac—1.5—750V in 6 ranges.  
Idc—0.06—600mA in 5 ranges.  
Iac—0.3—300mA in 4 ranges.  
Resistance—2KΩ—2MΩ in 4 ranges.  
Accuracy—dc—2 1/2%, ac—4% of F.S.D.  
Size—115 x 215 x 90mm.  
Complete with steel carrying case, test leads, and battery.  
PRICE £11.30 net p & p 30p.



U4341

**MULTIMETER U4324**

34 Ranges. High sensitivity. 20,000Ω/Volt. Overload protected.  
Vdc—0.6—1200V in 9 ranges.  
Vac—3—900V in 8 ranges.  
Idc—0.06—3A in 6 ranges.  
Iac—0.3—3A in 5 ranges.  
Resistance—25Ω—5MΩ in 5 ranges.  
Accuracy—dc and R—2 1/2% of F.S.D.  
ac and db—4% of F.S.D.  
Size—167 x 98 x 63mm.  
Supplied complete with storage case, test leads, spare diode, and battery.  
PRICE £9.95 net p & p 25p.



U4324

**MULTIMETER U4313**

33 ranges. Knife edge with mirror scale. 20,000Ω/Volt. High accuracy. mVdc—75mV.  
Vac—1.5—600V in 9 ranges.  
Vdc—1.5—600V in 9 ranges.  
Idc—60—120 microamps in 2 Idc—0.6—1500mA in 6 ranges.  
Iac—0.6—1500mA in 6 ranges.  
Resistance—1KΩ—1MΩ in 4 ranges.  
db scale—10 to +12db.  
Accuracy—dc—1 1/2%, ac—2 1/2%  
Size—115 x 215 x 90mm.  
Complete with steel carrying case, test leads, and battery.  
PRICE £13.40 net p & p 30p.



U4313

**NEW CAPACITOR KITS**

C280 Kit—PC Mounting polyester 250V. 5 of each value: 0.01 0.022, 0.047, 0.1, 0.22µF. 2 of 0.47, 1µF. £1.30 net.  
C296 Kit—Tubular polyester, 400V. 5 of each value: 0.01, 0.022, 0.047, 0.1, 0.22µF. 2 of 0.47µF. £1.30 net.  
Ceramic Kit—square plaquette 50V. 5 each value: 22, 33, 47, 100, 220, 330, 470, 1000pF, 2200, 4700pF, 0.01µF. £1.30 net.  
250V Paper Kit—Tubular metal case. 3 of each value: 0.05, 0.1, 0.25, 0.5, 1µF. 90p net.  
500V Paper Kit—Tubular metal case. 3 of each value: 0.025, 0.05, 0.1, 0.25, 0.5µF. 90p net.  
1000V Paper Kit—Tubular metal case. 3 each value: 0.01, 0.025, 0.05, 0.1µF. £1.10 net.

S-DeC	£2.14
S-DeC	£3.92
µDeC "A"	£4.30
µDeC "B"	£7.53
2 DeC	£4.72
MM6*	
Calculator	only £8.75
+ 30p P. & P.	

**MULTIMETER U435**

32 Ranges, High Sensitivity 20,000Ω/Volt.  
Vdc—75mV—1000V in 8 rgs.  
Vac—2.5—1000V in 7 rgs.  
Idc—0.001—2.5A in 6 rgs.  
Iac—0.005—2.5A in 5 rgs.  
Resistance—3-300K in 3 rgs.  
Capacitance scale 0-0.5µF Accuracy—  
dc and R—2 1/2% of F.S.D.  
ac and C—4% of F.S.D.  
Size—205 x 110 x 84mm  
COMPLETE WITH STEEL CARRYING CASE, TEST LEADS AND BATTERY  
PRICE £9.45 net p&p 25p



**SEND NOW!**

**YOUR SINGLE SOURCE FOR THE EASY-BUILD ORGAN**

**Studio Electronics**

LTD

PO BOX 18 HARLOW CM18 6SH ESSEX

Tel: HARLOW (STD 0279) 416771

New catalogue now available on receipt of S.A.E.




**ELECTRONIC KITS**

requires reliable firms well connected in own markets for handling exclusive sales in countries where no organisation yet exists.

Send enquiries to:

**AMTRON**

Casella Postale 4160, Milano, Italy

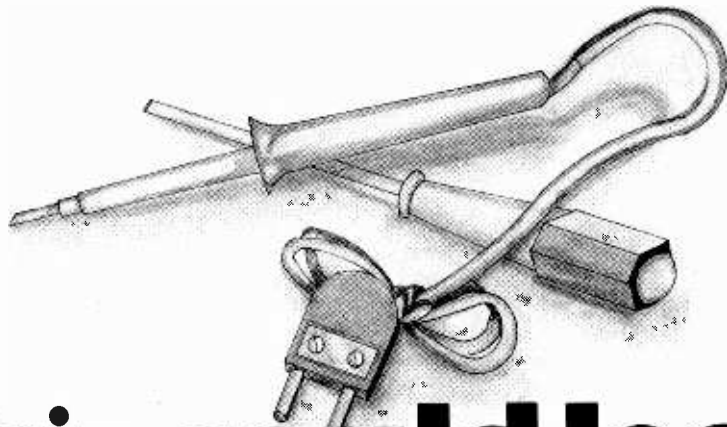

# This could lead to something big.

A soldering iron and a screw driver. If you know how to use them, or at least know one end from the other, you know enough to enrol in our unique home electronics course.

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.


You build, see and learn as, step by step, we take you through all the fundamentals of electronics and show you

how easily the subject can be mastered and add a new dimension not only to your hobby but also to your earning capacity.

This course is accepted by and used in a large number of schools and colleges and forms an invaluable grounding for professional training in the subject. All the training is planned to be carried out in the comfort of your own home and work in your own time. You send them in when you are ready and not before. These culminate in a final test and a certificate of success.

**1**


## Build an oscilloscope.

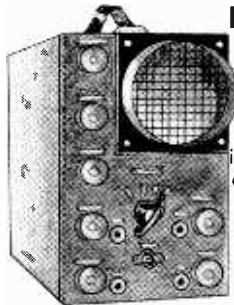

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a professional test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.

**2**

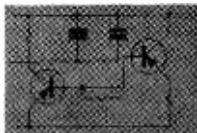
## Read, draw and understand circuit diagrams.



In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

**3**
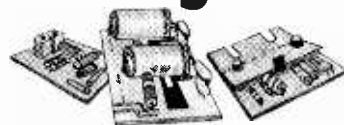
## Carry out over 40 experiments on basic circuits.



We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

**PLUS**



## FREE GIFT!

ALL STUDENTS ENROLLING IN OUR COURSES RECEIVE A FREE CIRCUIT BOARD ORIGINATING FROM A COMPUTER AND CONTAINING MANY DIFFERENT COMPONENTS THAT CAN BE USED IN EXPERIMENTS AND PROVIDE AN EXCELLENT EXAMPLE OF CURRENT ELECTRONIC PRACTICE

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

WAA

Brochure without obligation to:  
**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept WL/45**  
**P.O. Box 156, Jersey, Channel Islands.**

NAME .....

ADDRESS .....

(Block caps please)

# THE UNITRON

# A MAGNETIC FIELD-EFFECT TECHNOLOGY

DON RESCHEVSKY\*

EVERY once in a while, some major breakthrough in electronics changes the whole face of the industry. Now that world patents have been officially filed and registered, Solitronix Inc. has released details of a new device—in fact a new technology; the Unitron.

This component has such application potential that it is impossible to overstate its impact on the electronics scene both in industrial/professional and military applications plus, of course, consumer electronics. It works on an old, established principle but only now that there are newer materials available is it possible to exploit the full potential. Materials currently under investigation in the laboratories promise even better devices.

## The device

The Unitron is extremely simple, both in operation and manufacture—which means cheap devices. The heading shows simple magnets with north and south poles. Text books inform that *like* poles repel while *unlike* poles attract. Push two north poles together and they will oppose you, but make it one north and one south pole and they'll try to get together—you have to physically hold them apart.

Now let us come to the clever part. Let us lay down a large number of very tiny magnets close together such that the flux or magnetic field of each magnet couples with that of its neighbours. If we lay them so that they attract, then there will be a certain interaction between the poles of each adjacent magnet. Similarly, a certain repulsion will take place if adjacent magnets have like poles.

It is at this juncture that materials start to play an important role. Until recently, materials available would only allow a magnet structure such as that above which, in itself, is pretty useless. Research during the past two years has led us to a new magnetic material/substance which is synthetic (i.e. man made). The new substance is called Polyferrosamarium-bybutylcobalt. To the layman it is a bit of a mouthful but to us it spelt success. Abbreviated to PSB it has the strangest effect upon magnetism and it is this effect which gives rise to the Unitron which makes possible a whole new family of devices.

The material PSB takes the form of a soft, plastic ferrite with a crystalline structure. In its normal synthesised state it is not magnetised, i.e. it isn't a magnet and thus has no north or south poles and has no field surrounding it—it is magnetically inert. If we now bring another magnet close to the material it will suddenly magnetise forming a miniature magnet complete with poles. This effect may also be obtained by simply applying some form of voltage either a.c. or d.c. Taking away the source of power makes the material magnetically inert again. The rise and fall times of this induced magnetic effect can be less than a microsecond, however, the material stores some of the power which is released when the next "pulse" of power is applied. The

power appears to be stored within the material itself as a series of minute magnets which are themselves composed of smaller magnets. This tiny atomic magnet structure has the combined power of all the tiny magnets locked within it, but the poles are set up in such a fashion as to make the net magnetic effect across the whole structure add up to zero—until the next signal pulse is applied.

## Structure

A diagram of the device is shown in Fig. 1. The drawing is simplified to preserve clarity. For example, there are 100 tiny vertical magnets and in some devices the coupling magnets (the long ones top and bottom) are divided and cross-coupled. The sizes are given which shows just how tiny these structures are. The length of one magnet element is only  $2\mu$  wide by  $4\mu$  long.

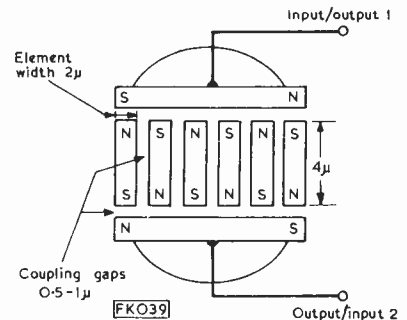


Fig. 1: Devices commonly have 100 elements on a  $300\mu \times 10\mu$  area. Only six are shown here for clarity. Note  $1\mu = 0.00003937$  in. or  $1/10000$  in =  $25\mu$ .

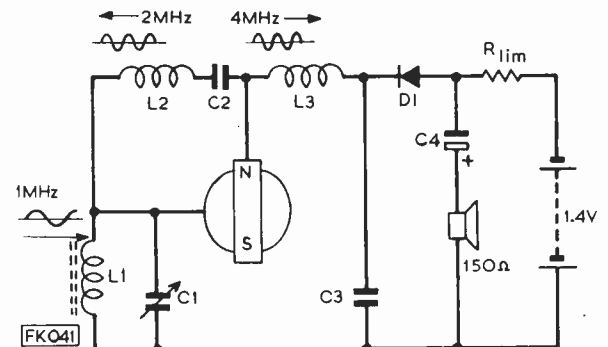


Fig. 2: M.W. receiver. The coil/capacitor combination L1/C1 tunes medium waves. (In example, we assume a 1MHz signal coming from the ferrite rod). L2/C2 tunes 2MHz and feeds signal back to input. L3/C3 tunes 4MHz and passes signal to D1, load R<sub>lim</sub> and speaker.

\* Chief Design Engineer, Solitronix Inc. Anaheim, California.

Device specifications in the semiconductor industry are commonly given in mils and to give some idea of the smallness of the elements in the Unitron it should be remembered that 1 mil is 1/1000in. which is equal to 25.4 microns. Thus even 25.4 microns (25.4 $\mu$ ) is only 0.001in. and thus 1 $\mu$  is 0.001 divided by 25.4.

The Unitron structure is manufactured using similar techniques to those for making integrated circuits except that an electron beam is employed to trim the magnetic pattern.

First, a solid layer (less than 0.05 $\mu$  for small signal devices and up to 7 $\mu$  for power components) is deposited on a ceramic substrate. Then, a computer-controlled programmed laser beam cuts the devices into separate areas. Lastly, another computer programmed electron beam divides the areas into a series of minute islands each forming an inert, potential magnet made of PSB.

### Operation

There is another peculiarity of PSB. The signal-induced magnetic field runs from input to output coupling magnets—a sort of magnetic ripple along the individual magnetic structures. However, immediately a signal is applied, a secondary magnetic surface wave streaks along the surface of the material, like a flat stone skimming across a millpond. Further, such a secondary field is exactly twice the speed, and therefore twice the frequency, of the induced field and lastly, it is very much larger. In other words, we have magnetic amplification. The degree of amplification is a function of two things—the type of field which caused it and the permittive index of the grade of PSB used.

Maximum gain obtained from a Unitron to date is 120dB. This is from an area less than 0.01in<sup>2</sup>. For power devices the same order of gain is obtainable but a larger area is required because dissipation is higher within the device itself.

Perhaps the most startling thing about seeing a Unitron for the first time is that it has only two leads (although power devices may have their cases bonded to a heat sink to improve heat dissipation).

The Unitron does, of course, require a battery or some source of power. Efficiency is extremely high for small signal applications. For example, Fig. 2 shows the circuitry required for a small medium wave receiver running from a 1.4V power source. The resistor, R<sub>lim</sub> is employed to act as a form of load, but also to limit the current taken by the device.

Thus if the output required (as shown in Fig. 2) is 250mW or 1/4W and the Unitron was a grade 1 device (efficiency 85%) then one simply allows d.c. power equal to 115% to be applied i.e., 85% plus the 15% to make up 100% plus 15% for the loss. In the case of Fig. 2 and assuming 250mW required, then R<sub>lim</sub> would be calculated for 0.1785A to flow. This is a

simple calculation using only Ohms law viz; Volts x Current = Power which means 1.4V x 0.1785A = 250mW.

That's all there is to the design. Unitrons are classified and marked according to their frequency handling capability and power ability. Providing the frequency rating is greater than that for which the device is to be used, there are no problems. Power is simply a matter of Ohms law as explained i.e., the applied voltage multiplied by the current drawn by the device must equal a number which is less than the specified power rating of the particular device. Thus a 3PSB2 is a Unitron for use up to 3MHz (first figure) and must not dissipate more than 2W (last figure). Devices needing a heat sink are signified by the addition of the letter S after the last figure. If there is no S, then the dissipation is for free air.

A Unitron 3PSB1 (as used in Fig. 2) currently costs about one dollar on the US market, that's about 40p in English money. Already the consumer industry has placed orders for some 100 million devices and production lines are running flat out. The devices should find their way onto the US Amateur market by the third quarter of this year. By then, even better Unitrons will be available.

Some practical circuits are given in the remaining diagrams just to whet your appetite and show what can be achieved. Before closing the theoretical side, it is worth mentioning a spin off from the Unitron research program. Figure 3 shows a structure using only 3 magnets for simplicity. The complex build up of power i.e. stored field, in the PSB structure made us think. Isn't that just what a capacitor does—even a coil?

To date, an electronic capacitor has been fabricated which could prove invaluable in the IC industry. There seems no reason why an electronic tuned circuit should not be manufactured using the Unitron technique. This would mean that complete receivers, transmitters, etc. could be manufactured on a single IC chip less than one hundredth of an inch square. The capacitor structure shown in Fig. 3 has allowed an electronic capacitance of 0.1 $\mu$ F at 3V working to be achieved in an area on 6 $\mu$  by 10 $\mu$  [1 $\mu$  = 0.0000393in.].

### Applications

Radio Amateurs will be interested in the circuit shown in Fig. 4. Here, a single field effect transistor feeds a single Unitron. Although the f.e.t. v.f.o. needs to tune only one section of half the lowest band of interest (remember, the induced reverse surface wave is twice the frequency which induced it) then any higher harmonic can be tuned by simple selective tuned circuits. A signal coming in at, say, 3.5MHz would come out of the Unitron at 7MHz. Here, a simple 7MHz acceptor LC combination would either accept the signal and pass it to the next stage for amplification or could feed it back to the input. Here it would go back through the Unitron and emerge as a

14MHz signal and so on. Input impedance of the Unitron varies with frequency but even at 20MHz this is still several hundred megohms so there is virtually zero damping of tuned circuits.

The Unitron may be a bit of a disappointment physically because it looks very much like an ordinary transistor.

Since the Unitron is bi-directional i.e., the signal can flow either way thus input and output are interchangeable, no pip or case marking is required and lead identification is unnecessary. What could be simpler!

It will be interesting to see just how far the Unitron has progressed by this time next year—who knows, transistors and ICs as we know them, may well be obsolete. Pw


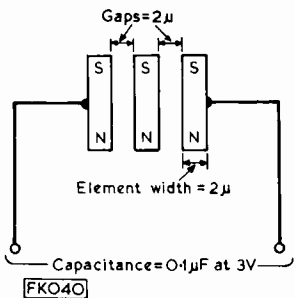


Fig. 3: (above) Electronic 0.1 $\mu$ F 3V wkg capacitor which takes up only 10 $\mu$  x 6 $\mu$ . An electronic coil can be fabricated (up to 86 $\mu$ H) but is more complex.  
Fig. 4: (right) Single f.e.t. v.f.o. providing only 1 $\mu$ W can drive a single Unitron to give 1/4W output on six bands, 1.8-30MHz.

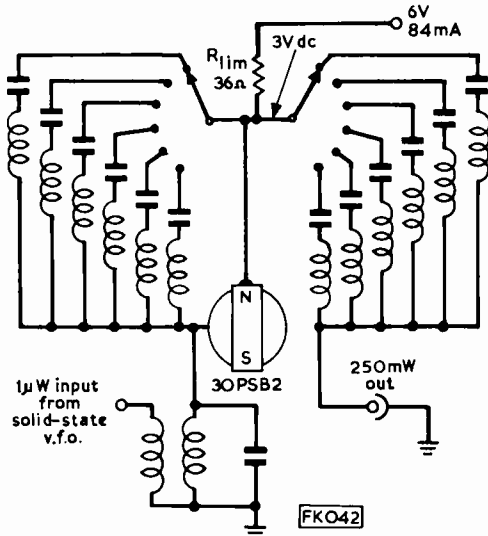



# BI-PRE-PAK

Bargains in Semi-Conductors, components, modules & equipment.

## Bargains from our FREE Catalogue

20 large pages, filled with real bargains in transistors, I.Cs, components, equipment, etc. Send large S.A.E. with 6p stamp for your FREE copy of 6th Edition by return. Meanwhile, for prompt delivery order from this month's ad. NOW.

### BPP TRANSISTOR PACKS ALL AT 50p EACH TESTED & GUARANTEED

- |  |  |
|--|--|
| <b>B79</b> 4 IN4007 Sil. Rec. diodes. 1,000PIV 1 amp. plastic            | <b>H39</b> 6 Integrated circuits 4 gates BMC 962, 2 flip flops BMC 945 BD131/BD132                   |
| <b>B81</b> 10 Reed Switches, 1" long 1/2" dia. High-speed P.O. type      | <b>H41</b> 2 Complementary Plastic Transistors 40361 Type NPN Sil. Transistors TO-5 can comp. to H66 |
| <b>H35</b> 100 Mixed Diodes. Germ. Gold bonded, etc. Marked and Unmarked | <b>H65</b> 4 40362. Type PNP Sil. Transistors TO-5 can comp. to H65                                  |
| <b>H38</b> 30 Short lead Transistors. NPN Silicon Planar types           |  |

### UNMARKED & UNTESTED

- |  |   |
|--|---|
| <b>B1</b> 50 Germanium Transistors PNP, AF and RF                          | <b>B86</b> 100 Sil. Diodes sub. min. IN914 and IN916 types                |
| <b>B66</b> 150 Germanium Diodes Min. glass type                            | <b>H20</b> 20 BY126/7 Type Silicon Rectifiers 1 amp. plastic. Mixed volts |
| <b>B83</b> 200 Transistors, manufacturers' rejects, AF, RF, Sil. and Germ. | <b>H34</b> 15 Power Transistors, PNP, Germ. NPN Silicon TO-3 Can          |
| <b>B84</b> 100 Silicon Diodes DO-7 glass equiv. to CA200, OA202            | <b>H67</b> 10 3819N Channel FET's plastic case type                       |

### PLASTIC POWER TRANSISTORS— 2 ranges

In NPN or PNP at shattering low prices sold to you under our Tested and Guaranteed terms.

Range 1. V.CE. Min 15. HFE Min 15 Range 2. V.CE. Min. 40. HFE Min 40  
 1-12 13-25 26-50 40 Watt 30p 25p 26p  
 90 Watt 24p 22p 20p 90 Watt 35p 33p 30p

### NEW X-HATCH GENERATOR Mk.2



Complete kit **£7-93**

Essential for Colour T.V. alignment of 4 patterns. Featuring plug in IC's and a more sensitive sync-pick-up circuit. The case is virtually unbreakable—ideal for the engineer's toolbox—only measures 3" x 5 1/2" x 3". Operates from 3 U.2 type batteries (extra).

Ready built unit only **£9-93**

### OVER 1,000,000 TRANSISTORS

of all most needed types in stocks including power, diode, rectifier, etc., etc., marked, tested and guaranteed. Hundreds of worthwhile bargains will be found in our FREE CATALOGUE (6th edition). Also Zener diodes, I.Cs, etc.

### SUNDRY

Metrication Pocket Charts 12p. 8 assorted relays £1.00. Rev. counter device (for cars) £1.00. U.H.F./TV Tuner Units £2.50. L.M.380 Audio I.C. £1.00 and technical books of all kinds.

### TERMS OF BUSINESS

V.A.T. Prices shown do not include V.A.T. Please add 8% to total value of your order including postage. No V.A.T. on overseas orders.

POSTAGE Except where stated, add 15p for postage & packing in U.K. Overseas—add £1, any difference being charged or refunded.

PAYMENT Cash with order, Cheque or money order. Minimum value—£1. You can also pay by ACCESS.

IMPORTANT—Every effort is made to ensure accuracy of prices and description at time of preparing this advertisement and going to press. Prices are subject to alteration without notice.

## BI-PRE-PAK LTD

Co. Reg. No R20319

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DF.

TELEPHONE: SOUTHEND (0702) 46344.

WRITE ORDER SEPARATELY AND ATTACH COUPON IF REQUIRED

challenging values!




# Stirling Sound


STIRLING SOUND AUDIO MODULES come to you as basic units assembled on P.C.Bs enabling you to add required components in layouts of your own choice. Modules are tested and boxed before despatched and include well printed instructions.
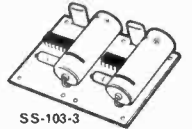
### AMPLIFIER MODULES

- Pre-amplifiers; tone control
- SS.100** Active tone control unit to provide bass, treble, balance and volume controls **£1.60**
- SS.101** Pre-amp for ceramic cartridge, tape and radio **£1.60**
- SS.102** Pre-amp for low output magnetic cartridge, tape and radio. With R.I.A.A. correction  $\pm 1\text{dB}$  at 1K **£2.25**




SS-103-3

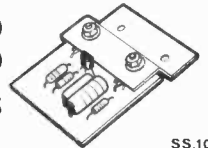


SS-105

### POWER AMPLIFIERS

- SS.103** Compact I.C. amp. with 3 watts R.M.S. output. Operating voltage 6 to 22. Size 3" x 2" **£1.75**
- SS.103-3** Stereo version of above using one I.C. on each channel **£3.25**
- SS.105** A compact and useful all-purpose amplifier which will run excellently on a 12V supply. With 5 watt output, two make a good stereo amp. Size 2 1/2" x 1 1/2" **£1.95**
- SS.110** Similar in size to SS.103 but with a 10 watt output. Ideal for many domestic and small size P.A. applications. Operates from 26 to 32V. **£2.40**
- SS.140** Excellently designed 40 watt R.M.S. (into 4 ohms) hi-fi amplifier. S/N ratio better than 75dB. THD better than 0.2%. Power requirements—45V. d.c. With 0.15" centre edge connections. Two can be bridged to give 80 watts R.M.S. into 4 ohms **£3.60**

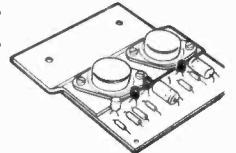


SS.140

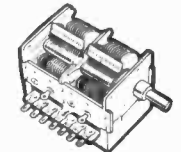


### TUNER MODULES

- SS.201** Ganged tuning condenser with accurately engineered slow-motion drive in rugged housing. Excellent sensitivity. Tunes 88-108MHz. With A.F.C. facility. Operates from 6V-16V **£6.25**
- SS.202** I.F. stage (with I.C.) Pre-tuned. A.F.C. connection. Operates from 4.5 to 14V **£5.25**
- SS.203** Stereo Decoder. Designed essentially for use with SS.201 and 2, this module can also be used in most mono FM tuners. A LED may be attached. Operating voltage 9-16V. d.c. **£5.62**

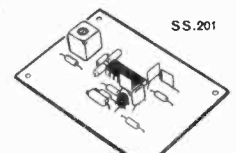

SS.201

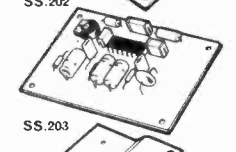

SS.202



SS.203

### POWER SUPPLY STABILIZER

- SS.300** Add this to an unregulated supply (say typically 45V output) to obtain a steady powerful working output adjustable from 12 to 60V. Essential or your audio and special systems. Money saving and very reliable **£2.25**

### ● ALL MODULES TESTED AND GUARANTEED

### ● WITH WELL PRINTED INSTRUCTIONS

### ● FULL RANGES OF ANCILLARY COMPONENTS AVAILABLE—SEE CATALOGUE

To BI-PRE-PAK, 222-224 WEST RD., WESTCLIFF-ON-SEA, ESSEX

Please send .....

for which I enclose.....Inc. V.A.T.

Name .....

Address .....

PW4

# And now the FANE 'SPECIALIST' RANGE

L'SPEAKERS OF OUTSTANDING QUALITY FOR THE DISCRIMINATING PROFESSIONAL

Features include ROBUST CAST ALUMINIUM CHASSIS and 2" EXTRA HIGH POWER VOICE COILS

All models available in impedances of 8 ohm or 15 ohm

Recommended Prices inc. VAT

Guarantee: 2 years



Illust.  
12"  
'DISCO 60'

12" 'DISCO 60' 60 watts R.M.S.

Linen Cone Surround. Fitted extra large Tweeter Cone. Frequency Range 50-15,000 Hz

£24.75

Rec. Retail Price

12" 'GUITAR 60L' 60 watts R.M.S.

Plastiflex Cone Surround. Aluminium Centre Dome. Frequency Range 50-9,000 Hz.

£23.50

Rec. Retail Price

DESIGNED FOR LEAD GUITAR

12" 'GUITAR 60B' 60 watts R.M.S.

Linen Cone Surround. Frequency Range 45-9,000 Hz.

£23.95

Rec. Retail Price

FOR USE IN MULTIPLES FOR BASS GUITAR

12" 'PA 60' 60 watts R.M.S.

Plastiflex Cone Surround. Fitted Tweeter Cone. Frequency Range 50-15,000 Hz.

£23.50

FOR GENERAL PURPOSE PUBLIC ADDRESS

15" 'BASS 70' 70 watts R.M.S.

Linen Cone Surround. Frequency Range 40-7,000 Hz. Can be used singly but ideally TWO UNITS IN A SINGLE CABINET.

£35.75

Rec. Retail Price

RECOMMENDED FOR ALL BASS INSTRUMENTS

OUR FAST SELLING  
and RELIABLE

'POP' RANGE  
IS STILL AVAILABLE AT  
REC. PRICES from

£6.30

AND for those who can afford the  
very best there is our range of  
'CRESCENDO'

MODELS

12" UNITS from £39.95

Rec. Retail

15" UNITS from £46.95

Rec. Retail



Please send S.A.E. for leaflets on any of above ranges

Distributors to Wholesale and Retail Traders—LINEAR PRODUCTS LTD., ELECTRON WORKS, ARMLEY, LEEDS.

Manufacturers enquiries to—FANE ACOUSTICS LTD., 286 BRADFORD ROAD, BATLEY, YORKS

Prices shown correct at 14 Jan, 1975

## HIGH FREQUENCY HORN UNITS

MODEL 910

Rating 50  
watts with  
recommended  
filter inc. VAT

£15.95

MODEL 920 Mk II (as illust)

SIGNIFICANTLY  
INCREASED SENSITIVITY.

UNCHANGED PRICE.

Rating with recommended  
filter 100 watts. Price inc. VAT

£39.95

HPXI HIGH POWER CROSS-OVER UNIT

Suitable for above Horn Units £2.50 inc. VAT.



## TECHNOMATIC LTD. 54 SANDHURST ROAD, LONDON NW9

Tel: 01-204 4333

AC126 7.8 11p	2N2926 8p	DIODES	SCR
AC176 12p	2N3053 18p	1N4001 5p	THYRISTORs
AC187/8 11p	2N3055 49p	1N4007 7p	1A/50V 2p
AD161/2 36p	2N3442 140p	1N914 4p	1A/400V 60p
AF114/5/7 12p	2N3702/3/4 11p	OA202 8p	3A/400V 75p
BC107/8 9p	2N4370/5 10p	AEY11 50p	CI06D 45p
BC109 10p	2N4373 220p	ZIJ 75p	2N3525 95p
BC109C 10p	2N3819 20p	TIL209 16p	TRIAC
BC154 13p	3N128 75p	ZENERS	3A/400V 95p
BC192/3 10p	3N140/1 85p	400mW 8p	6A/400V 120p
BC184 11p	40561 40p	1 3W 18p	16A/500V 180p
BC212/3 11p	43362 40p	1 5W 27p	DIAC 30p
BC214 13p	40503 58p	BR. RECT.	DIL SOCKETS
BCY71 16p	40573 38p	1A/50V 22p	(Low Profile
BFY501/2 15p		1A/600V 29p	Texas)
MPF103/5 31p		2A/100V 35p	8 Pin 12p
TIP41A 65p		2A/400V 45p	14 Pin 15p
TIP42A 70p		6A/100V 60p	16 Pin 14p
2N2646 35p	SCR		
	MCR101 25p		

TTL SERIES	Linear	1 AMP REG	MC1314	CMOS LOGIC
7400 14p	7473 34p	5V, 12V	360p	Gates (CD4001 AE,
7401/215p	7474 34p	555 192p	MC1315	CD4011 AE etc) 37p
7404 18p	7475 45p	555 50p	430p	CD4013AE 67p
7408 18p	7476 34p	555 110p	CA3046 55p	CD4016AE 90p
7410 15p	7486 41p	555 220p	ICL8038	CD4017AE 183p
7413 32p	7489 340p	567 250p	TBA800	CD4027AE 108p
7420 15p	7490 45p	709 28p	LM380 90p	CD4029AE 325p
7430 15p	7491 82p	723 55p	LM3900 70p	CD4024AE 148p
7441 70p	7492 52p	741 25p	MC1310	CD4030AE 82p
7442 56p	7493 45p	747 70p	225p	CD4046AE 220p
7447 90p	74107 45p	748 35p	DIL 8 or 14	CD4047AE 154p
7448 80p	74121 34p	DIL 8 or 14	MC1312	(SAE for full list please)
7472 27p	74141 75p		220p	


OPTO-ELECTRONICS	LIT747	210p	5001 12 Digit Calculator
7 SEGMENT READ	3 DIGIT READ OUTS		Chip 485p
OUTS	'BLISSDOR' LENS	250p	5314 Clock chip 650p
3015F	RED LENS	185p	Clock chip with Alarm (Similar MMS316)
MAN3M	LEDS		750p
MAN4	TIL209 (Red)	16p	PC Keyboard
LIT704	Green/Yellow	35p	2 36" x 3 76" x 0.45"
LIT707	LDR ORP12	50p	400p

FOR MORE SELECTION REFER TO OUR ADVERTS IN P.E. OR W.W.

Complete semiconductor kit for PW ASCOT STEREO CASSETTE DECK  
£5.70 + VAT.

MAIL ORDER ONLY  
MINIMUM ORDER £2.

P & P 15p.  
Add 8% VAT on total.

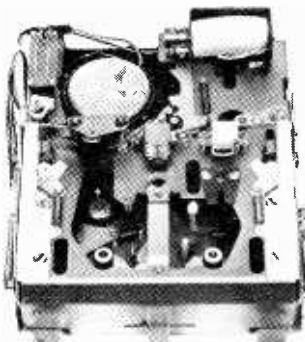

PAUSE CONTROL  
RELEASE & FASTWIND CONTROL  
RECORD CONTROL

## GARRARD CT4'S' MK III STEREO CASSETTE PLAYER & RECORDER

has full facilities for record, playback, pause, erase, rest, fast forward and reverse wind, automatic tape end stop and cassette release.

Robust, precision engineered mechanism based on the "STARR" patented design. Ideal for use in Car stereo cassette players, HI-FI stereo cassette recorders, industrial and many other applications.

Send cheque or Postal Orders for £19.98 (£18.50 + 8% VAT) (includes post and packing) to:

## BOTHWELL ELECTRIC SUPPLIES

(Glasgow) LIMITED


431 Sauchiehall Street

GLASGOW G2 3LG

Tel: 041-332 6184

Scotland's Leading Electronics Centre

# GOING BACK...

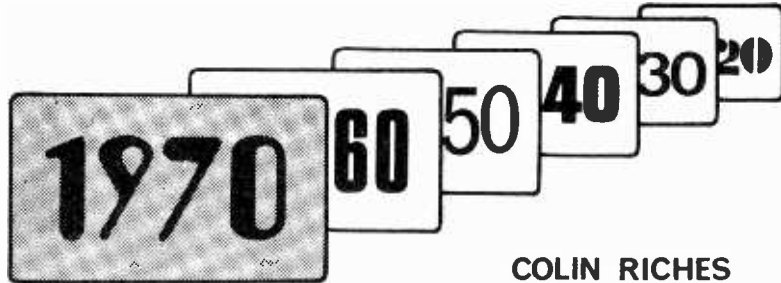

COLIN RICHES

**M**R. L. OWEN, 7 St. Richard's Road, Deal, Kent, writes to say that he used to have some small part in the manufacture of McMurdo Silver "15-17" receivers of about 1937-38. He says not many were made but, if anyone can help, he'd like to acquire one for old times' sake.

A photograph of the "R" type valves published a short while ago brought back two rather poignant memories to Mr. R. J. Hall of Penzance, Cornwall. He says that just after the First World War, he saw a shop window full of that type of valve for sale at 1d. each. Upon mentioning the fact to his elder brother who had been a radio operator in the R.N.A.S. on airships, he informed him that the "R" valves used by the Navy had filaments made of platinum wire—the filaments and lead-out wires being one single length of wire.

On hearing this, the young R.J.H. quickly returned to the shop to buy some but was promptly informed by the proprietor that he had disposed of the lot for a "a few shillings."

Mr. Hall's second recollection concerns an ex-Navy set which he had. It contained six "R" type valves all set in a row on the top of the set. Unfortunately a little accident occurred when H.T. and L.T. leads at the rear of the set were reversed. The valves lit up like arc lights for a few seconds, then were ruined forever.

Tempus fugit says W. J. Swift of 36 Pattenden Road, Catford, London SE6 4NQ, and this makes him less able to do the things he used to do. He has a book "Talks About Wireless" which contains some history of wireless pioneering. It is written by Sir Oliver Lodge and was published by Cassell in 1925. Another book in Mr. Swift's possession is "The Book

of Practical Radio," by John Scott-Taggart. It has 163 diagrams and 63 plates and was published by The Amalgamated Press in 1925. If anyone would like to make him an offer for these two books, please contact him direct.

Gilbert Davey of Harrow tells me that he has a "Hezzanith" horn loudspeaker which dates from about 1926 and which he uses in conjunction with his O-V-2 battery-operated receiver with which it was originally supplied. The maker's name, inscribed on the speaker is Heath and Co. of New Eltham, London. He wonders if there is any connection with the firm of scientific instrument makers of that name with an address in the same area.

Unlike the Brown "H" horn speaker shown in the October issue of P.W., Mr. Davey's speaker has a large diaphragm fixed around the edge and held over two magnets with the usual speech current windings round them. A knurled knob underneath operates a screw system

which brings the magnets nearer to or further away from the diaphragm. After 50 years, the magnets seem as powerful as they always were. The horn mounting is in the centre of the diaphragm just above the magnet system.

Operating the speaker from the O-V-2 receiver, the quality is similar to that of a small, cheap transistor set. Mr. Davey stresses that speech is far better than music although he always enjoyed its rendering of Jack Payne and Henry Hall in the earlier days.

Wiltshire reader George Southgate (Fourways Cottage, Chilmark, Salisbury) tells me he has many items of vintage equipment for disposal—valves, phones, condensers, transformers, mains-energised speakers, etc. If any readers are interested will they please send a stamped, addressed envelope to him for details.

## A million pirates

Even in January 1927 the Post Office were contemplating taking steps to discover unlicensed users of broadcast receivers so that disciplinary action could be taken against them. They stated that it was difficult to estimate even approximately the number of "pirates" in the country but a conservative figure would be a million!

## Anyone help?

S. J. McAlister, the manager of Bord Na Mona, Derrygreenagh Works, Rochfortbridge, Mullingar, Co. Westmeath, has sent me a photograph of an old crystal set and wonders if anyone can give him some more information on it.

The set was manufactured by Service Radio Co. Ltd., London N.16, and Mr. McAlister thinks it is dated c. 1925. It has two plug-in coils (see picture) numbered 50 and 60 and signed John Nicols.

On the left of the set there is a space for a "Service" amplifier powered by accumulators of 4V for L.T. and 45V H.T.

The set is on display in Mr. McAlister's V.H.T. Radio Communications Workshop and to enable visitors to listen to it, he has fitted an audio amplifier, the speaker of which can be seen to the left of the unit. The set is in perfect working condition.



Mr. McAlister's modified crystal set.

## ON THE AIR

—continued from page 1102

on 4980 at 0230! (I must have been mad!) so for all those night owls here's one for the log book.

Thirteen year old **David Lovatt** of Cheadle, Staffs, wonders if anyone knows of Radio Malaya in the 49 metre band. Radio Malaysia, as it is now known, still has a service on 6100 and 6175 called the Voice of Malaysia. It is a 100kW transmitter from Kuala Lumpur.

**Peter Kay** from Maghull, Liverpool, sends a comprehensive list of QSL times that must have taken hours to type. The star prize goes to Voice of Vietnam via Radio Havana, Cuba, that came after nearly two years! It seems that Peter has not been able to latch on to some of the broadcasts that I have featured in the column, and to this I can only say that if the DX isn't running then even the most expensive set won't find it.

The ionosphere I once heard described as "like a moving bowl of custard", and when you ask for SINPO lists, Peter, you would find that they would be out of date, in some extreme cases, after two hours. I can help with your other request though, and to do this let us call on **David Gordon** whose QTH is in Salford. David sends info on three DX shows:—

- R. Finland on 9500 at 1425 No Days given
- R. Prague on 9605 at 1545 No Days given
- R. Budapest on 9760 at 1615 Tues. and Fri.

Why not let me know of any DX shows you hear and then I will put together a week's list to ensure that you never miss any, thus keeping you glued to the set every spare minute.

When he has finished his days "collar feeling" policeman **James Walker** of Milton Keynes turns to feeling the tuning knob of his Heathkit SW717 with its 50ft long wire aerial. He has logged the following:—

- VOA Greenville Mass. on 15430 at 1530
- Vatican Radio on 11740 at 1500
- R. Ghana on 21720 at 1500

James then goes on to tell me that R. Peking's 1975 calendar has arrived and that it is the traditional aspects of China painted by Chinese artists. This came, along with a huge collection of magazines and pennants, so here's your chance, pennant collectors, QSL Peking, and try your luck.

From the horse's mouth comes an answer to the

recent query regarding a TV set that puts out the Deutsche Welle sign-on tune. **David Porter** is a BBC engineer at Sutton Coldfield and he explains that the sound carrier of a u.h.f. set is demodulated in an intercarrier sound detector and runs at 6MHz, this being the difference between the sound and vision carriers. Thus there are circuits in the set tuned to 6MHz followed by an a.f. amplification stage. Any local 6MHz signal tends to be picked up and amplified by these circuits. So there we are!

**David Blair** from Airdrie in Bonny Scotland logs WYFR on 11645 at 1700 and wonders what it is all about. This station used to be called Radio New York World Wide (WNYW) and it was sold a year or so ago to "Family Radio Ltd" a religious broadcasting company that owns many local US stations, particularly on v.h.f. The new company retained all the old WNYW frequencies but changed the programming from sweet music to general religious broadcasts.

From wild and woolie Wales, Holyhead to be exact, comes a plea from **John Higginbotham**. He would like to know the exact info that he should put on a QSL request. Many s.w. stations like the following, John:—

1. Date, time and frequency of broadcast heard.
2. Your type of radio and aerial.
3. SINPO of that particular broadcast.
4. Ten minutes of prog. content written out.

It always helps to comment on the type of programme and some stations require either IRCs or return postage, or both.

**Martin Daft** at his QTH in Mapperley, Notts, is bothered by interference from household electrical goods since buying an r.f. amplifier. This is purely a case of "amplify the signal, amplify the noise." Finally **Peter Roberts** of Pont Vaillant, Guernsey, very kindly says that it was this column that turned him on to DXing and that his Heathkit GR1 with its 35ft long wire has rewarded him with, among others:—

- Tema, Ghana on 9545 at 2110
- WINB Red Lion on 15185 at 2000
- V. of Nigeria on 15270 at 0610 (another early bird)

One final note while on the transmitter subject; R. Finland is to start a service on 9620 with a new 100 watt and is seriously considering a service on the MW. Thus we say farewell to this months column and wish 73s to you and yours.

## REACTION TIMER

—continued from page 1100

bration pot is turned up further until 2.4 volts is shown on the voltmeter, and VR2 is then slowly advanced until D9 comes on. At this point D7 will switch off.

The process is continued with the voltmeter indicating 2.7 volts for VR3 adjustment, 3 volts for VR4, 3.5 volts for VR5 and 4.3 volts for VR6. These voltages correspond to the charges that will be present on C2 after time intervals of 1/10, 1/9, 1/8, 1/7, 1/6 and 1/5 second from the signal light going off.

Calibration is now complete, and the meter and potentiometer can be removed.

For readers wishing to set the unit for intervals of time other than those given, the formula for the voltage on C2 is

$$V = \frac{It}{C_2}$$

where  $I$  is in microamps,  $C_2$  is in microfarads,  $t$  is in seconds and  $V$  is in volts. In this unit  $I=1,000$  microamps,  $C_2=47\mu F$ , and so  $V=21.3 \times t$ .

The current through the presets VR1 and VR6 is minute in comparison with the 1mA charging current to C2, and is ignored in the calculations.

The total accuracy of the unit is determined mainly by the actual capacitance of C2. A common tolerance value for tantalum capacitors is 10 or 20 per cent, but one would be unlucky indeed to pick a capacitor at the edge of its tolerance.

If it is desired to increase the length of time that the signal light remains on, this is best achieved by increasing the value of C1. If a light dependent resistor is wired in series with R1 and placed behind a small aperture in the case, a random element will be introduced into the duration of the signal, due to changes in the light entering when the unit is moved, or time of day, etc. D.W.

**ALL MAIL ORDER BY RETURN. C.O.D. SERVICE WELCOME**

# C. T. ELECTRONICS

V.A.T.  
Unless otherwise stated all prices are EXCLUSIVE of V.A.T. Please add 8% to all orders. Carriage: orders under £5 plus 20p. Over £5 post free.

All mail order and enquiries to 270 Acton Lane

Tel: 01-994 6275

## SEMICONDUCTORS

AC107	35p	BCY32	95p	MM1712	60p
AC125	25p	BCY34	60p	MPF102	45p
AC126	25p	BCY38	65p	MPF103	45p
AC127	27p	BCY39	£1.00	(2N5457)	35p
AC128	25p	BCY55	£1.50	MPF104	
AC176	25p	BCY70	22p	(2N5458)	35p
AC188	30p	BCY71	22p	(MPF105)	
ADY17	25p	BCY72	22p	(2N5459)	40p
ACY18	30p	BD121	75p	OA 70	10p
ACY19	30p	BD123	75p	OA 79	10p
ACY20	25p	BD124	65p	OA 79	10p
AD140	60p	BD131	40p	OA 81	10p
AD142	50p	BD153	75p	OA 90	10p
AD149	60p	BD156	75p	OA 91	10p
AD161	44p	BD156	75p	OA 200	10p
AD162	44p	BDY11	£1.40	OA 202	10p
AF114	25p	BDY19	£1.96	OA 211	35p
AF115	25p	BDY20	£1.40	OC16	95p
AF116	25p	BF152	20p	OC19	85p
AF117	25p	BF194	14p	OC22	55p
AF118	60p	BF195	15p	OC26	65p
AS221	60p	BF196	15p	OC28	60p
AS230	60p	BF197	20p	OC36	60p
BA102	33p	BF224J	30p	OC42	40p
BA112	50p	BFX29	30p	OC44	20p
BA114	16p	BFX29	30p	OC45	25p
BA156	12p	BFX34	30p	OC47	20p
BC107	12p	BFX85	30p	OC70	15p
BC108	12p	BFX86	30p	OC71	12p
BC109	14p	BFX88	30p	OC75	25p
BC113	15p	BFY44	50p	OC76	25p
BC115	15p	BFY51	25p	OC77	40p
BC117	12p	BFY52	25p	OC83	25p
BC147	11p	BFY53	25p	OC84	25p
BC148	11p	BFY90	65p	OC170	35p
BC149	12p	BSW63	80p	OC171	30p
BC153	15p	BY127	20p	OC200	60p
BC157	15p	BY164	65p	OC201	60p
BC158	15p	IS100	15p	OC202	75p
BC169	15p	IS103	15p	TIP29A	45p
BC182	12p	MJ340	50p	TIP30	55p
BC183	12p	MJ481	95p	TIP31A	57p
BC184	25p	MJ291	£1.25	TIP32A	69p
BC212	14p	MJ291	£1.95	TIP33A	£1.00
BC213	16p	MJE340	50p	TIP34A	£1.40
BC214	14p	MJE370	75p	TIP35A	£3.20
BC301	25p	MJE371	90p	TIP36A	£3.50
BC302	25p	MJE520	85p	TIP41A	70p
BC303	40p	MJE955	£1.70	TIP42	70p
BCY30	40p	MJE3055	75p	TIP92B	50p
BCY31	55p	MM1613	45p	TIP30B	60p

QTY. DISCOUNTS: 12+ 10%; 25+ 15%; 100+20%

## DIGITAL INTEGRATED CIRCUITS

SN7400	18p	SN7427	42p	SN7470	30p	SN74165	£2.00
SN7401	18p	SN7428	50p	SN7472	30p	SN74166	£4.00
SN7402	20p	SN7430	20p	SN7473	40p	SN74167	£4.25
SN7403	20p	SN7432	42p	SN7474	40p	SN74170	£4.10
SN7404	20p	SN7433	70p	SN7475	55p	SN74171	£2.00
SN7405	20p	SN7437	50p	SN7476	45p	SN74172	£1.50
SN7406	30p	SN7438	50p	SN7480	80p	SN74181	£6.00
SN7407	30p	SN7441	AN	SN7481	£1.75	SN74182	£2.00
SN7408	20p	SN7441	AN	SN7482	87p	SN74183	£2.45
SN7409	40p	SN7442	75p	SN7483	£1.00	SN74185A	£2.40
SN7410	18p	SN7443	£1.00	SN7484	90p	SN74190	£1.95
SN7411	23p	SN7445	£1.70	SN7486	45p	SN74191	£1.95
SN7412	22p	SN7446	£2.00	SN7490	75p	SN74192	£2.00
SN7413	40p	SN7447	£1.50	SN7491	AN	SN74193	£2.00
SN7416	30p	SN7448	£1.75	SN7492	75p	SN74194	£2.50
SN7417	30p	SN7450	20p	SN7493	75p	SN74195	£1.85
SN7420	30p	SN7451	20p	SN7494	80p	SN74196	£1.50
SN7422	38p	SN7453	20p	SN7495	80p	SN74197	£1.50
SN7423	38p	SN7454	20p	SN7496	£1.00	SN74198	£3.00
SN7425	38p	SN7460	20p	SN7497	£2.25	SN74199	£2.60

## ★ ★ SPECIAL OFFERS ★ ★

**MULTICORE CABLE.** 25-way, Individually screened, 14/0076. £1.00 per yard + V.A.T. Postage by weight.

**IMHOFF 19" RACKING CABINETS.** 13½" high, 22" wide, 13" deep. Brand new. £10.00 each + V.A.T. Carriage £1.00.

**SIEMENS CONTACTORS.** Over 1,000 in stock. All types. Phone or write for details.

**METAL OXIDE RESISTORS TR4/5/6** in stock. All values. 1-off price 3p each. Discount on quantity.

**10 TURN TRIMPOTS** by Bourns, Mec, Painton, etc. All values in stock. 50p each. Discount on quantity.

**9-WAY FULLY STABILISED BATTERY CHARGERS.** 24" L, 7½" H, 7" D. Price £14.00 each. Carriage £1.00 + V.A.T.

**DEAC RECHARGEABLE BATTERY CASSETTES.** 13.4V (nom.). Type B/SA 80351/108. Heavy duty encapsulated DEAC supply. Size 3½" x 2½" x 1½". Price £5.00 + V.A.T.

**8-WAY BATTERY CHARGER.** Type CC 999. Charges up to 8 of the above battery cassettes. Price £14.00 + V.A.T.

**12-WAY BATTERY CHARGER.** Type CC 999. Charges up to 12 of 13.4V DEAC batteries. Metered battery condition check. Price £25.00 + V.A.T.

We are open from 9.30 a.m.—6.00 p.m. Monday-Saturday.

We have the largest retail selection of components available. Phone or write if you are in difficulties obtaining a particular component.

C.O.D. service welcome. All mail order by return. Official orders welcome to Government establishments, Education Authorities, etc.

01-994-6275

## S.C.R.s

TIP31B	65p	2N2218	25p
TIP32B	77p	2N2219	25p
TIP33B	£1.00	2N2220	25p
TIP34B	£1.62	2N2222A	25p
TIP35B	£2.71	2N2306	20p
TIP36B	£3.50	2N2477	30p
TIP41B	78p	2N2640	50p
TIP42B	95p	2N2846	£1.50
TIP30C	72p	2N2804	25p
TIP31C	80p	2N2806	25p
TIP32C	£1.00	2N2926	12p
TIP33C	£1.20	2N3053	25p
TIP34C	£1.80	2N3054	65p
TIP35C	£3.00	2N3055	50p
TIP36C	£3.74	2N3232	70p
TIP41C	90p	2N3255	25p
TIP42C	£1.00	2N3643	30p
TI550	40p	2N3702	14p
ZTX107	15p	2N3703	12p
ZTX300	15p	2N3704	12p
ZTX500	18p	2N3705	12p
ZTX501	20p	2N3706	12p
ZTX504	30p	2N3707	12p
ZTX531	30p	2N3708	12p
ZTX550	25p	2N3709	12p
IN659	8p	2N3771	£1.70
IN914	8p	2N3772	£2.00
IN916	8p	2N3773	£2.50
IN4001	8p	2N3519	35p
IN4002	8p	2N3520	55p
IN4003	8p	2N3325	85p
IN4004	18p	2N3904	22p
IN4005	12p	2N3905	25p
IN4006	14p	2N4058	12p
IN4007	16p	2N4059	12p
IN4146	7p	2N4080	12p
2N695	25p	2N4081	12p
2N697	28p	2N4126	17p
2N698	25p	2N4286	15p
2N706	12p	2N4287	15p
2N606A	15p	2N4288	15p
2N708	15p	2N4289	15p
2N930	28p	2N4290	15p
2N132	25p	2N4444	£1.90
2N1302	16p	2N4871	35p
2N1303	16p	2N4903	£1.10
2N1304	25p	2N5069	£1.10
2N1305	25p	2N5191	96p
2N1306	25p	2N5194	£1.10
2N1307	25p	2N5195	30p
2N1308	25p	40361	50p
2N1309	25p	40362	50p
2N1613	25p	40669	90p
2N1711	25p	40673	70p
2N2147	70p	D5151	£1.00
2N2160	65p	Microwave Diode	
2N2217	25p		

## TRIACS

CRS1/05	40p	TXL228B	8A 400V
CRS1/10	50p	SC40D	£1.85
CRS1/20	60p	SC40E	£1.40
CRS1/40	80p	SC40F	£1.65
CRS1/60	90p	SC45D	£1.70
CRS1/80	100p	SC45E	£2.10
CRS3/20	62p	SC50D	£2.42
CRS3/40	90p	SC50E	£2.70
CRS7/400	£1.00	DIAC	25p
CRS16/100	85p		
CRS16/200	90p		
CRS16/600	£1.60		
C106B	45p		
C106D	70p		
40669	90p		
TIC44	35p		
2N4444	£1.90		
BT10/500A	90p		

## LINEAR I.C.s

LM309K	5V. 1A.		
LM723C	2-3TV.		
LM733C	150mA		
MFC4000	250mW		
TBA800	5 Watt		
709C	Op Amp		
D.I.L./TO99	45p		
741C	Op Amp		
D.I.L./TO99	35p		
748C	Op Amp		
D.I.L.	75p		
747C	Dual Op Amp		
ZN414	Radio I.C.		
TAD100	Radio I.C.		
inc. Filter	12-90		
CA3014	£1.55		
CA3018	£1.00		
CA3028	£1.20		
CA3036	£1.20		
CA3048	95p		
CA3048	£2.35		
CA3075	£1.60		
CA3090Q	£4.85		
MC1303L	£2.20		
MC1310P	£2.80		

## BRIDGE RECTIFIERS

W02 1A 200V	38p
BY164 1-4A 200V	57p
MDA952/2 6A 100V	80p

## ZENER DIODES

BZV78 Series	400mW
3-3V-33V, 5% 11p	1-5W range 25p
10W range	45p

## L.E.D.

TIL209	38p
HP5082	28p
MA2082R	20p

## L.D.R.

ORP12	60p
NE555 Timer	80p

## TO3 VOLTAGE REGULATORS

L005	5V 650mA
L036	12V 600mA
L037	15V 450mA

## VEROBOARD

24 x 34	32p	0-15	23p
24 x 35	35p	16-30	35p
32 x 32	35p	31-45	55p
32 x 5	40p	46-60	65p
17 x 24	£1.05	61-75	70p
17 x 32	£1.43	76-90	77p
17 x 5	£1.84	91-105	90p
PIN INS. TOOL	72p		
SP.F. CUTTER	52p		
100 PINS SS	30p		
100 PINS DS	30p		
500 PINS SS	£1.20		£1.20
500 PINS DS	£1.20		£1.20

## ALSO STOCKED

Electrolytic Capacitors, Mullard, Sprague, Lorlin, etc. Polyester, Polystyrene, Silver Mica Capacitors, etc. Resistors ¼W-10Watt. Potentiometers; carbon, wirewound, Preset, Rectilinear multitrn, Antex Soldering Irons, switches, rotary, slide, toggle, etc. Cable, veroboard.

## POTENTIOMETERS

Linear or Log	Single	Double
Rotary Pots	15p	42p
Rotary Switched	25p	

## ★★ SPECIAL OFFERS ★★

**MINIATURE MAINS TRANSFORMER.** PRI 240V. SEC. 12V, 100MA. Manuf.: Hinchley. Size: 36 x 45 x 40mm. F.C. 53mm. Price 1-85p. 100-50p ea. 1,000-50p ea. 10,000-40p ea.

**3 CORE PVC INSULATED MAINS CABLE.** GREY ML6650, 3x7/0.2mm. Price 100m-£4.50. 1000m-£35. 10,000m-£330.

**0-47 mfd. 50V MYLAR FILM CAPACITOR.** Size 1" x 0.35" x 0.65" P.C. Mount. Price 100-4p ea. 1000-3p ea.

**240V. A.C. SOLENOID.** Reversible operation; twin coil. Size approx. 2½ x 1½ x 1½in. 90p ea.

**30**



# YOU DESERVE A BIGGER SALARY

## "I learn more thanks to ICS"

Thousands of people have said it. Now it's your turn. ICS point the way to the better future you know you deserve.

### Personal Tuition

Whether you need a basic grounding or tuition to complete your technical qualifications, ICS offer expert guidance from fully qualified tutors. You take the road to a better life at your own pace, in your own home, with the backing of the world's most experienced home study school.

### Guaranteed success

ICS offer all examination students guaranteed tuition until successful. Plus expert advice on exam techniques. Make sure of your future with ICS. Choose the right course now.

### City and Guilds Certificate

Make sure you get your Certificate with ICS:  
Telecommunications Technicians  
Radio TV and Electronics Technicians  
Electrical Installations Technicians  
Electrical Installation Work  
Radio Amateurs  
Also MPT Radio Communications Certificate

### Technical Training

ICS offer a wide choice of non-exam courses designed to equip you for a better job in your particular branch of electronics, including:

Electronic Engineering & Maintenance  
Computer Engineering & Programming  
Radio TV & Audio Engineering & Servicing  
Electrical Engineering, Installations & Contracting  
Self Build Practical Radio Kits

### Colour TV Servicing

Technicians trained in TV servicing are in constant demand. Learn all the techniques you need to service Colour and Mono TV sets through new home study course approved by leading manufacturer.

### QUALIFY FOR A NEW CAREER

Home study courses also available for leading professional examinations and diploma courses for over 200 business and technical subjects including:

Accountancy	Engineering	Motor
Administration	Farming	Personnel
Advertising	Heating	Purchasing
Air Conditioning	Management	Sales
Building	Marketing	Storekeeping
Catering	Mechanical	Work Study

G.C.E. 60 subjects at 'O' and 'A' levels.

POST OR PHONE TODAY FOR FREE BOOKLET

I am interested in

Name

Address

# ICS

To: International Correspondence Schools,  
Dept. 530, Intertex House, LONDON SW8 4UJ  
or telephone: 01-622 9911 (all hours)

Accredited by CACC.

# Marshall's

A. Marshall & Son (London) Limited Dept. PW  
42 Cricklewood Broadway London NW2 3HD Tel: 01-452 0161  
& 85 West Regent Street Glasgow G22 QD Tel: 041-332 4133

Everything you need is in our new 1975  
catalogue. Available now price 25p

Trade and export enquiries welcome

## PW TELE TENNIS

As featured in PRACTICAL WIRELESS July - November 1974.  
Also on BBC Nationwide and in the Daily Mail October 2nd 1974.

This exciting new game is now available in kit form. Due to popular demand we are now able to offer a fantastic saving on list prices. Ideal game for whole family. No need to modify your TV set, just plugs in to aerial socket. Parts list as follows:

A Resistor Pack	£1.00 p.p. 20p
B Potentiometer Pack	£1.25 p.p. 20p
C Capacitor Pack	£3.10 p.p. 20p
D Semiconductor Pack	£14.50 p.p. 20p
E IC Sockets	£4.00 p.p. 20p
F Transformer	£1.15 p.p. 25p
G PCB's	£7.50 p.p. 20p
H Switches	£4.50 p.p. 20p
I I ChF Modulator Kit	£7.20 p.p. 20p

Special Prices—complete kit (excluding case) £42.00 p.p. 50p Sections A-F Incl.

£23.50 plus 30p. Assembly instructions with complete kit of 75p on request.			
SN7400 16p	SN7420 30p	SN7453 16p	SN7491 £1.10
SN7401 16p	SN7423 30p	SN7454 16p	SN7492 75p
SN7401AN 38p	SN7425 37p	SN7460 16p	SN7493 65p
SN7402 16p	SN7427 45p	SN7470 30p	SN7494 85p
SN7403 16p	SN7430 16p	SN7472 38p	SN7495 80p
SN7404 24p	SN7432 45p	SN7473 44p	SN7496 £1.00
SN7405 24p	SN7437 35p	SN7474 48p	SN74100 £2.16
SN7406 45p	SN7438 35p	SN7475 45p	SN74107 43p
SN7407 45p	SN7440 16p	SN7476 45p	SN74118 £1.00
SN7408 25p	SN7441 85p	SN7480 75p	SN74119 £1.92
SN7409 33p	SN7442 85p	SN7481 £1.25	SN74121 57p
SN7410 16p	SN7445 £1.59	SN7482 87p	SN74122 80p
SN7411 25p	SN7446 £2.00	SN7483 £1.20	SN74123 72p
SN7412 18p	SN7447 £1.30	SN7484 95p	SN74141 £1.00
SN7413 50p	SN7448 £1.50	SN7485 £1.58	SN74150 £1.44
SN7416 45p	SN7450 16p	SN7486 45p	SN74190 £1.95
SN7417 30p	SN7451 16p	SN7490 65p	

## TRY OUR NEW GLASGOW SHOP

Prices correct at March 1975, but all exclusive of V.A.T.  
Post and Package 20p postage and package charges

### Popular Semi-conductors

2N696 22p	2N3707 13p	AD142 59p	BC309 10p	LM709 48p
2N697 16p	2N3708 70p	AD143 45p	BC327 21p	TO99 38p
2N698 40p	2N3715 £1.50	AD161 50p	BC328 19p	8D1L 33p
2N699 45p	2N3716 £1.80	AD162 50p	BC770 17p	14D1L 40p
2N1302 19p	2N3721 £1.20	AD161 50p	BCV71 22p	LM723C 90p
2N1303 19p	2N3772 £1.80	AD162 £1.20	BCV72 13p	LM741 40p
2N1304 24p	2N3773 £3.20	AF109R 40p	BD123 82p	TO99 40p
2N1305 24p	2N3819 37p	AF115 24p	BD131 40p	8D1L 40p
2N1306 31p	2N3820 38p	AF124 30p	BD132 50p	14D1L 38p
2N1307 22p	2N3823 £1.42	AF125 30p	BD135 42p	LM747 £1.00
2N1308 25p	2N3904 27p	AF126 28p	BD136 49p	LM785 £2.00
2N1309 36p	2N3905 24p	AF127 28p	BD137 55p	MC1310 £2.92
2N1671 £1.44	2N4036 63p	AF139 39p	BD138 63p	MJ480 90p
2N1671A £1.54	2N4037 42p	AF178 55p	BD139 71p	MJ481 £1.14
2N1671B £1.72	2N4216 20p	AF179 65p	BD140 87p	MJ490 98p
2N1671C £4.32	2N4289 34p	AF180 58p	BF115 25p	MJ491 £1.38
2N2102 50p	2N4921 73p	AF239 51p	BF116 23p	MJ340 45p
2N2147 78p	2N4922 84p	AF240 27p	BF117 59p	MJE2955 £1.12
2N2148 94p	2N4923 83p	AF279 54p	BF154 16p	MJE3055 68p
2N2160 60p	2N5190 92p	AF280 54p	BF163 32p	MFC4000B 40p
2N2218A 22p	2N5191 95p	BC107 16p	BF180 35p	MFC4010A 49p
2N2219 24p	2N5192 £1.24	BC108 15p	BF181 34p	MFC4060 54p
2N2219A 26p	2N5195 £1.46	BC109 19p	BF184 30p	MFC6040 91p
2N2221 18p	2N5243 43p	BC147 13p	BF194 13p	NE355V 70p
2N2221A 21p	2N5457 49p	BC148 13p	BF195 12p	NE560D £4.48
2N2222 20p	2N5458 45p	BC149 12p	BF196 13p	NE531 £4.48
2N2222A 25p	2N5459 49p	BC167B 13p	BF197 15p	NE565A £4.48
2N2646 55p	40361 48p	BC168B 13p	BF198 18p	OC28 76p
2N2904 22p	40362 50p	BC168C 11p	BF200 40p	OC42 30p
2N2904A 24p	40411 £2.00	BC169B 84p	BF237 25p	OC71 20p
2N2905 24p	40406 44p	BC169C 13p	BF238 22p	OC72 25p
2N2905A 26p	40407 33p	BC182 12p	BFX29 30p	SL414A £1.80
2N2906 19p	40408 50p	BC182L 12p	BFX30 27p	TAA263 £1.00
2N2906A 21p	40409 52p	BC183 12p	BFX84 24p	TBA800 £1.50
2N2907 22p	40410 52p	BC183L 12p	BFX85 30p	TBA810 £1.50
2N2907A 24p	40411 £2.00	BC184 13p	BFX87 28p	TIP29A 49p
2N2926 11p	40602 46p	BC184L 13p	BF88 25p	TIP30A 78p
2N3053 25p	40604 56p	BC212K 16p	BF89 45p	TIP31A 62p
2N3054 60p	40669 £1.00	BC212L 16p	BFY19 62p	TIP328 74p
2N3055 75p	AC117 20p	BC214L 21p	BFY51 23p	TIP33A £1.01
2N3441 97p	AC126 20p	BC237 13p	BFY52 21p	TIP34A £1.51
2N3442 £1.65	AC127 20p	BC238 13p	BFY90 75p	TIP35A £2.90
2N341 10p	AC138 28p	BC339 13p	BFY39 48p	TIP36A £3.70
2N3416 15p	AC151V 25p	BC257 14p	C106D 65p	TIP10A 78p
2N3417 21p	AC152V 17p	BC258 13p	CA3020A 1.80	TIP42A 90p
2N3702 11p	AC153K 25p	BC259 14p	CA3046 70p	TIP2955 98p
2N3703 12p	AC176 18p	BC300 36p	CA3048 £2.11	TIP3055 60p
2N3704 14p	AC176S 25p	BC301 34p	CA3089E £1.96	ZTX300 13p
2N3705 12p	AC187K 23p	BC307 11p	CA30900 £4.23	ZTX302 20p
2N3706 9p	AC188K 34p	BC308 12p	LM301A 46p	ZTX500 15p

# SAXON

Money saving high performance audio equipment DIRECT FROM OUR OWN FACTORIES

## GUARANTEED TESTED HIGH PERFORMANCE MODULES—now better value than ever

- |                          |               |               |                                |
|--------------------------|---------------|---------------|--------------------------------|
| <b>SA35</b>              | <b>£5-45</b>  | Carriage free | ★ 25Hz-25kHz                   |
| 35W RMS 25-50V           |               |               | ★ 0-2% distortion              |
| 7 transistors, 7 diodes  |               |               | ★ Noise—80dB                   |
| <b>SA50</b>              | <b>£6-90</b>  | Carriage free | ★ 500mV into 20K               |
| 50W RMS 25-65V           |               |               | ★ 4-16 ohms                    |
| 7 transistors, 7 diodes  |               |               | ★ Simple wiring                |
| <b>SA100</b>             | <b>£12-50</b> | Carriage free | ★ Short and open circuit proof |
| 100W RMS 45-70V          |               |               | ★ Continuously rated           |
| 10 transistors, 7 diodes |               |               | ★ Top-grade components         |

**120 watt module complete with built-in supply—extra heavy duty £22-50** Carr. 60p



THE SA100 MODULE

## POWER SUPPLIES

### UNSTABILISED—READY WIRED

- |             |                                 |              |              |
|-------------|---------------------------------|--------------|--------------|
| <b>PU45</b> | Suits 2 SA35 or 1 SA50 (4 ohm)  | <b>£5-45</b> | Carriage 30p |
| <b>PU70</b> | Suits 2 SA50 (8 ohm) or 2 SA100 | <b>£8-45</b> | Carriage 40p |

### STABILISED

- |             |                                |              |               |
|-------------|--------------------------------|--------------|---------------|
| <b>PS45</b> | Suits 2 SA35 or 2 SA50 (4 ohm) | <b>£4-45</b> | Carriage free |
| <b>MT45</b> | Transformer for above          | <b>£3-50</b> | Carriage 30p  |
| <b>PS70</b> | Suits 2 SA100                  | <b>£5-45</b> | Carriage free |
| <b>MT70</b> | Transformer for above          | <b>£4-90</b> | Carriage 40p  |

N.B. PS70 is not suitable for the SA50

## Mk II STEREO DISCO MIXER £22-50

This well tried unit mixes two decks, handles any ceramic cartridge, and features mic over-ride plus separate full range bass and treble controls on both mic and deck inputs. Ample headphone power is available for P.F.L. May be used for mono and is mains operated. Fitted with sturdy screening case. Controls: Mic vol, base, treble. Left/Right fade, deck volume, bass, treble, headphone select, vol, Mains. Size 17 1/2in X 3in X 4in deep.



## DISCO MODULE £9-50

Thousands sold of this extremely popular mono version. A mic input may be fitted using the VA30 (see below). Low consumption from a 9V battery. Features the same high standards of reproduction as the Stereo version. Controls: H/phone select, vol, Left deck vol, Right deck vol, bass, treble, master vol. Size 12 1/2in X 3in X 2in deep.



## 3-CHANNEL SOUND-LITE £22-50

Only SAXON can supply such incredible value for money. This unit features 3kW power handling, full-wave control, bass, middle, treble AND master controls. Twin loudspeaker jacks for "through" connection as the Stereo version, or will panel mount next to either of the above. Also features unique CUT-BACK circuitry for extra wide range response. Size 12in X 3in X 2 1/2in deep. Professional standards at a price you can afford!




**SINGLE CHANNEL VERSION £7-50** Carr. free  
Recently reduced in price due to increasing sales, handles 1kW. Full wave operation.

ADD 8% VAT TO ALL ORDERS
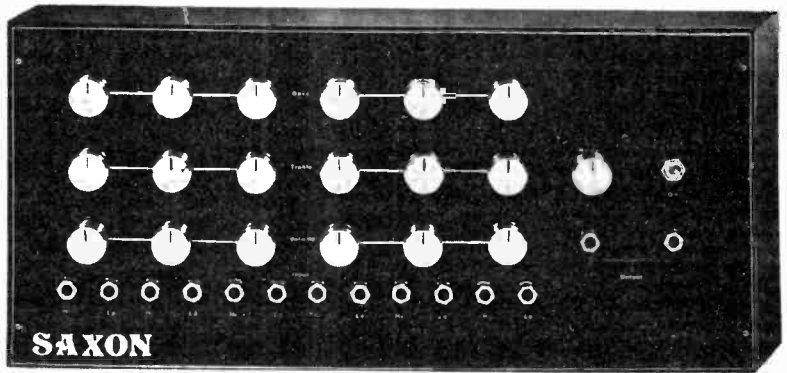
## MULTI-PURPOSE MIXERS

**M4HL £19-50** Carr. 50p  
**M6HL £29-50** Carr. 50p  
Featuring multiples of our VA30 module, the M4HL and M6HL fulfil the requirements of all clubs, groups, etc. where a high quality mixer is required. Each channel has one high and one low impedance input, plus volume, treble and bass controls. Input impedances may, if required, be easily changed. The M4HL has four channels, and one output, and the M6HL six channels (12 inputs) and a master control and two outputs. Either unit may be used free-standing or panel mounted. These mixers will feed all types of amplifier. Recommended for their versatility and high performance, and excellent value for money.




**VA30 CHANNEL MODULE £3-50** Carr. free  
This is the basic channel module in the above mixers and may also be used for extra inputs on either the mono or stereo mixers. Fitted with volume, bass and treble controls, requires just a jack and supply (9-100V)

## SAXON CSE 100
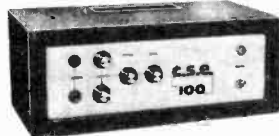
### COMPLETE AMPLIFIER

**£39-90** Carr. free

100W of speech and music—Two separately controlled inputs. Wide range bass and treble controls. Sturdy and attractive vinylite case. Twin outputs. Ideal for groups, discos, etc. Fully tested and guaranteed. 50W version identical in appearance.



**CSE50 £29-50** Carr. free

## NEW !!

### SAXON MULTIMIX 100 £57-00

100W rms four inputs slider controls plus master slider. Wide range bass and treble controls. Fantastic value, ideal for complete disco's, groups, clubs etc. SAXON MULTIMIX 50—Exactly as above but 50W rms. £45-00

## CALLERS AND MAIL ORDER

**SAXON ENTERTAINMENTS LIMITED**  
327-333 WHITEHORSE ROAD · CROYDON CR0 2HS

(Please quote magazine when ordering)  
SHOP HOURS: 9 a.m.-5 p.m. — LUNCH 12.30-1.30 p.m. MAIL ORDER DESK: 10 a.m.-3 p.m.  
24-HOUR ANSWER SERVICE. TEL. 01-684 6385. TECHNICAL ENQUIRIES: 01-684 0098.

SEND 10p FOR OUR 26 PAGE MANUAL—full circuits & details.  
TERMS OF BUSINESS: C.W.O., C.O.D. or ACCESS (just send in card number). Send 50p for C.O.D.  
Please send S.A.E. with all enquiries. VAT @ 8% must be added to all orders including carr. charges.



# WILMSLOW AUDIO

**THE Firm for speakers!**

## SPEAKERS

Baker Group 25 3, 8 or 15 ohm	£7-75
Baker Group 35 3, 8 or 15 ohm	£8-50
Baker Group 50/12 8 or 15 ohm	£12-50
Baker Deluxe 12" d/cone	£10-75
Baker Major " " "	£8-50
Baker Regent " " "	£7-75
Baker Superb " " "	£14-50
Baker Auditorium 12	£12-50
Celestion MH1000 horn	£10-95
Celestion PST8 for Unilux	£2-55
Celestion G12M 8 or 15 ohm	£12-00
Celestion G12H 8 or 15 ohm	£15-00
Celestion G12C 8 or 15 ohm	£24-00
Celestion G18C 3 or 15 ohm	£33-90
Coral 6 1/2" d/cone roll surr. 8 ohm	£2-50
Coral 8" d/cone roll surr. 8 ohm	£3-25
EMI 13 x 8 3, 8 or 15 ohm	£2-25
EMI 13 x 8 150 d/c 3, 8 or 15 ohm	£2-50
EMI 13 x 8 450 t/tw 8 ohm	£3-75
EMI 13 x 8 type 350 8 or 15 ohm	£2-25
EMI 13 x 8 20 watt base	£6-60
EMI 6 1/2" 98350 4 or 8 ohm	£3-00
EMI 5" 98132CP 8 ohm	£2-50
EMI 8 x 5 d/cone, roll surr 10 watt	£2-50
EMI 2 1/2" tweeter 97492AT	65
Eagle DT33 30 watt tweeter	£5-45
Eagle HT15 horn tweeter	£8-35
Eagle CT5 cone tweeter	£1-75
Eagle CT10 tweeter 8 or 16 ohm	£2-55
Eagle MHT10 horn tweeter	£3-80
Eagle crossover CN23, CN28, CN216	£1-50
Eagle FR4	£5-30
Eagle FR6	£8-35
Eagle FR8	£10-65
Elec 9 x 5, 59RM109 15 ohm, 59RM114 8 ohm	£2-80
Elec 6 1/2" 6RM171 d/c roll surr.	£3-50
Elec 6 1/2" 6RM220 d/cone	£2-85
Elec 4" tweeter TW4	£1-21
Elec 10" d/cone 10RM239 8 ohm	£2-65
Elec 8" 8CS175 3 ohm	£2-50
Fane Pop 15 watt 12"	£5-25
Fane Pop 25/2 25 watt 12"	£7-25
Fane Pop 40 watt 10"	£8-50
Fane Pop 50 watt 12"	£12-00
Fane Pop 55 12" 60 watt	£12-50
Fane Pop 60 watt 15"	£13-25
Fane Pop 100 watt 18"	£24-50
Fane Crescendo 12A 100 watt 12"	£29-00
Fane Crescendo 12B bass	£29-00
Fane Crescendo 15" 100 watt	£36-00
Fane Crescendo 18" 150 watt	£51-95
Fane 801T 8" d/c roll surr.	£7-00
Fane 807T 8" d/c roll surr.	£3-65
Fane 808T 8" d/c	£2-75
Fane 701 twin ribbon horn	£35-00
Fane 910 horn	£12-75
Fane 920 horn	£33-00

Goodmans 8P 8 or 15 ohm	£5-00
Goodmans 10P 8 or 15 ohm	£5-30
Goodmans 12P 8 or 15 ohm	£12-95
Goodmans 12P-D 8 or 15 ohm	£16-75
Goodmans 12P-G 8 or 15 ohm	£15-75
Goodmans Audiomax 12AX 100 watt	£37-50
Goodmans Audiomax 15AX	£40-25
Goodmans 15P 8 or 15 ohm	£21-00
Goodmans 18P 8 or 15 ohm	£36-00
Goodmans Midax 750	£16-00
Goodmans Axent 100 tweeter	£7-25
Goodmans Audiom 100 12"	£12-00
Goodmans Axlom 401 12"	£17-25
Goodmans Twinaxiom 8	£8-25
Goodmans Twinaxiom 10	£9-00
Kef T27	£5-25
Kef T15	£6-00
Kef B110	£7-25
Kef B200	£8-25
Kef B139	£14-25
Kef DN8	£2-00
Kef DN12	£4-95
Kef DN13	£3-30
STC4001 G super tweeter	£6-19
Richard Allan CG8T 8" d/c r/surr.	£8-35
2 1/2" 64 ohm, 70mm 80 ohm, 70mm 8 ohm	50
2 1/2" 75 ohm	50
7" x 4" 3 or 8 ohm	£1-40
8" x 5" 3 or 8 ohm	£1-50
10" x 6" 3, 8 or 15 ohm	£2-30

## SPEAKER KITS

Baker Major Module	each £10-75
Goodmans Mezzo	pair £45-00
Goodmans DIN 20	each £9-75
Helme XLK 25	pair £22-00
Helme XLK 30	pair £14-95
Helme XLK 50	pair £39-95
Keffit 1	each £20-95
Keffit 3	each £36-75
Richard Allan Twinkit	each £8-95
Richard Allan Triple 8	each £13-75
Richard Allan Triple 8	each £19-95
Richard Allan Super Triple	each £23-75
Wharfedale Linton 2 kit	pair £18-25
Wharfedale Glendale 3 kit	pair £34-50
Wharfedale Dovedale 3 kit	pair £52-50

## PA/DISCO AMPLIFIERS

(carr. and ins. £1)	
Baker Major 100 watt	£49-75
Linear 30/40	£30-00
Linear 40/60	£35-00
Linear 80/100	£58-95
Linear 100 watt slave	£44-00
Eagle PA range in stock—ask for catalogue.	

**Free with speaker orders over £7—**  
**"Hi-Fi Loudspeaker Enclosures"** book. All units guaranteed new and perfect. Prompt despatch. Carriage and packing: speakers 38p each, speaker kits 75p each (£1.50 pair) tweeters and crossovers 20p.

## ALL PRICES QUOTED INCLUDE VAT. WILMSLOW AUDIO (Dept. PW)

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire. SK9 1HF  
 Discount Radio, PA, Hi-Fi: 10 Swan St. Wilmslow  
 Send stamp for free booklet "Choosing a Speaker"



## Agfa Cassettes

**Agfa Low Noise Cassettes AT LESS THAN HALF PRICE!**

**AGFA HIGH DYNAMIC SUPER**

**AGFA STEREO-CHROM CHROMIUM DIOXIDE**

	1	5	10
C60	37p	£1-80	£3-50
C90	50p	£2-48	£4-95
C120	63p	£3-10	£6-20
C60+6	50p	£2-40	£4-70
C90+6	88p	£3-35	£6-80
C120	99p	£4-90	£9-80
C60	1	5	10
C90	85p	£4-20	£8-30
	£1-08	£5-35	£10-60

SAME DAY DESPATCH. P. & P. 15p per order

## WILMSLOW AUDIO

(DEPT. PW)  
 10 SWAN STREET, WILMSLOW, CHESHIRE, SK9 1HF

Cut-price prerecorded cassettes—send stamp for list

**Wire Wound Resistors.** Our selection of mixed values. 30 for £1 50. 100 for £4 00.

**Audio Amplifier Module.** Mullard LP1 73, output power, nominal 10 watt, supply voltage +24 volt, with data and circuit, £2 50.

**Ferguson Stereogram chassis** Mode 3357, all transistor, medium long, VHF/FM. 3 watts per channel S/M, with connection data, less tuning scale, £20. Post paid.

**Crystals HC6U:** 52-03333 MHz: 52-0250C: 52-01667: 51-56667: 51-58330: 37-7325C: 37-75000: 12-895-8: 12-891-6: 12-700-0: 9-458-33: 9-456-25: 9-455-55: 9-533-33: 9-531-64: 9-530-55: 9-090-62: 9-087-5 50p each.

**Electrolytics.** 32/32/32/µF, 325v. 2" x 1 1/2" 35p: 80µF 150vt 1 1/2" x 1" 20p; 2000µF 30v, 2 1/2" x 1" 25p; 2000µF 35v 3" x 2" 30p; 470µF 100v 3" x 1 1/2" 25p; 2000 2000µF 25v 2" x 1 1/2" 35p; 30 000µF 25v 4 1/2" x 2 1/2" 50p; 700µF 200v 3 1/2" x 1 1/2" 30p; 16 16µF 275v 1 1/2" x 1" 20p; 40 40µF 20v 275v 3" x 1" 20p; 4500 900 900µF 30v 2" x 1 1/2" 50p; 4000µF 35v 3" x 1 1/2" 40p; 4000µF 35vt 3" x 1 1/2" 35p; 2500µF 40vt 2 1/2" x 1 1/2" 40p; 4000µF 18v 2" x 1" 20p; 470µF 25v 1 1/2" x 1 1/2" 15p.

**Matched pair of bookshelf speakers.** Teak finish, size 12" x 8" x 5". 8 x 5 ohms ceramic, 5 watts RMS. Complete with cin leads. £11 00 pair.

**Thorn TV IF chassis,** 950 series (less valves), £1 75.

**UHF 625 transistor push button tuner** (NSF Telefunken) as used on Decca MS24C0. Brand new and boxed, £2 25. **Light Dependent Resistors** (RCA sq3536) 10p each, 4 for £1 00.

**P-C Boards** (not computer panels) 1 off 6 transistor single wave band. 1 off 4 transistor audio. 1 off 3 transistor £1 60. three boards.

**Rank EVR Teleplayer colour translator panels,** type and components on new panels listed as follows, £2 50, each panel. Z305—14 off BC148: 2 RCA ca3054 (ic): 1 crystal 4 433168 MHz—Z607—12 off BC148: 1 BC108: 1 BC158: 1 RCA ca3046 (ic), 1 RCA ca3045 (ic): Z608—23 off BC148: 2 BC158—Z612—12 off ME4103: 2 BC-251B: 1 BFY50.

**Mains Droppers,** 10 mixed values, £1 00.

**Edgewise Level meters,** 200µA, size 1 1/2" overall. 50p.

**Chrome Plastic knobs,** 3 types, 4 off each with spring clip, £1 25.

**Aluminium Chassis,** 7 1/2" x 5 1/2" x 2 1/2" 70p: 10" x 7 1/2" x 2 1/2" 85p. 11" x 7 1/2" x 2 1/2" 95p.

**BSR P128,** similar to HT70 single play, with heavy die cast turntable, less cartridge, £11 00.

**Transistorised FM tuner head,** with A.M. gang slow motion drive 88-108Mcs, with circuit diagram, £2 30.

**Ferguson Stereogram Chassis.** MW/LW VHF with tuning scale (5+5 watts sine wave) 15 ohms £28 50. Post paid

**15 ASSORTED SWITCHES** £2 00. 50—3 way to 7 way TAG STRIPS, £1 25. ALMA REED RELAY TYPE DRH. 3 VOLTS. 55p.

**REPAICO & DENCO COILS.** NEW/BOXED OUR SELECTION—5 FOR £1 25

**Goods not despatched outside UK** 15p handling charge on orders under £1 00. Please add 10% for post and packing on all items except gram chassis. All items include VAT.

## SURPLECTRONICS

216 LEAGRAVE ROAD, LUTON, LU1 1JD, BEDS.


# MAPLIN

# ELECTRONIC SUPPLIES

Get your 1975 CATALOGUE!

132 Big Pages

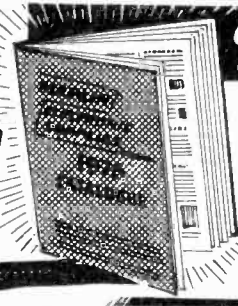Includes dozens of useful & interesting circuits you can build; data; hundreds of pictures, transistor equivalents list and hundreds of new lines. Packed with information. Only 35p.



## SUPERSONIC SAME-DAY-SERVICE - MEANS QUALITY COMPONENTS - FAST!

**● RESISTORS**  
**CARBON FILM**  
 1/4W 1Ω to 10M; 5%, IM2 to 10M: 10% E12  
 1/4W 1Ω to 10M; 5%, IM2 to 10M: 10%  
 E12 11Ω to 910k; 5% E12 & E24 1p each

**METAL OXIDE**  
 1/4W 10Ω to 1M: 2% E12 & E24 4p each

**WIREWOUND**  
 3W 0.22Ω, 0.27Ω, 0.33Ω, 0.47Ω:  
 10%, 1.15% 17p each  
 1.1Ω to 270Ω: 5% E12 13p each  
 Other ranges stocked. See our catalogue for details.  
 E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56,  
 68, 82 and decades.  
 E24: 11, 13, 16, 20, 24, 30, 36, 43, 51, 62,  
 75, 91 and decades.

**● POTENTIOMETERS**  
 Rotary miniature carbon track 1/4" spindle.  
 Values available: 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M, 2M.  
 Log. Single-gang 16p  
 Lin. Single-gang (+ 1K) 16p  
 Log. or Lin. Single-gang with switch 33p  
 Log. or Lin. Dual-gang without switch 49p  
 Slider 60mm track. Metal-cased; overall length 86-150mm (knob extra 7p).  
 Values available: 1k; 5k; 10k; 25k; 50k; 100k; 250k; 500k; 1M; 2M.  
 Lin. Single Gang 38p  
 Log Single Gang 38p  
 Lin or Log Dual Gang 49p  
 Presets: 0-1W Vertical or Horizontal.  
 100Ω, 220Ω, 470Ω, 1K, 2k, 4k7 10k, 22k, 47k, 100k, 220k, 470k, 1M 7p each

**● CAPACITORS**  
 Sub-miniature  
 Axial lead electrolytic  
 Mtd V Price Mtd V Price  
 1.5 63 6p 68 6.3 6p  
 2-2 63 6p 68 6.3 14p  
 3-3 63 6p 100 4 6p Mtd V Price  
 4-7 63 6p 100 10 6p 470 6.3 6p  
 6-8 40 6p 100 25 6p 470 10 14p  
 6-8 63 6p 100 40 6p 470 25 18p  
 10 25 6p 100 63 16p 470 40 25p  
 10 63 6p 150 6.3 6p 680 6.3 14p  
 15 16 6p 150 16 6p 680 16 16p  
 15 40 6p 150 25 6p 680 25 25p  
 15 63 6p 150 40 14p 680 40 28p  
 22 10 6p 150 63 18p 1000 4 14p  
 22 25 6p 220 4 6p 1000 10 16p  
 22 63 6p 220 10 6p 1000 16 25p  
 33 6-3 6p 220 16 6p 1000 25 28p  
 33 16 6p 220 25 14p 1500 6.3 16p  
 33 40 6p 33 40 6p 1500 10 25p  
 47 4 6p 220 63 25p 1500 16 28p  
 47 10 6p 330 4 8p 2200 6.3 25p  
 47 25 6p 330 10 6p 2200 10 25p  
 47 0 6p 330 16 14p 3300 6.3 28p  
 47 63 6p 330 63 28p 4700 4 28p

**● MAINS CONNECTORS**  
 P360 3-pin 1.5A Chassis Plug with Line Socket 33p  
 SA2190 3-pin 5A Chassis Plug 25p  
 SA1862 Line Socket for SA2190 28p  
 P437 3-pin 5A Chassis Socket with Line Plug 66p

**● TRANSISTORS & DIODES**

AC127	18p	BY126	13p
AC128	18p	BY127	13p
AC176	17p	BY164	49p
AD161/162 MP		BZY88 series	
BA100	9p	MPP102	38p
BA105	22p	OA91	6p
BC107	10p	OA200	7p
BA108	10p	OC71	20p
BC109	13p	SC146D	88p
BC109C	15p	T1843	28p
BC142	23p	W005	30p
BC143	26p	W04	33p
BC147	10p	IN914	4p
BC148	10p	IN4001	6p
BC149	12p	IN4002	6p
BC168C	12p	IN4003	7p
BC169C	12p	IN4004	7p
BC178	17p	IN4005	8p
BC182L	10p	IN4006	8p
BC183L	12p	IN4007	9p
BC184L	12p	IN4148	9p
BC212L	14p	2N1302	20p
BC213L	15p	2N1303	20p
BC214L	18p	2N1304	30p
BCY71	22p	2N1711	24p
BD131	45p	2N2219	25p
BD132	54p	2N2648	45p
BD131/BD132		2N2905	38p
MP	£1-20	2N2926or	10p
BD135	36p	Ye	12p
BD139	48p	Gn	13p
BD140	69p	2N3053	18p
BF258	35p	2N3055	45p
BF259	25p	2N3819	51p
BFX29	30p	2N5459	51p
BFX30	33p	7400	10p
BFX34	30p	7413	38p
BFX37	30p	7447	£1-10
BFX87	30p	7479	59p
BFX88	25p	7474	45p
BFY50	20p	7490	93p
BFY61	22p	7493	93p
BFY62	20p	74121	39p

L.E.D. RED  
 2med 1/2 only  
 Panel mtg. clip 15p  
 5p  
 (Other colours and 7-seg. displays in our catalogue)

**● INTEGRATED CIRCUITS**

CA8046 (14-pin DIL)	69p
LMC1492CH (TO99)	£4-25
MC1310P (14-pin DIL)	£2-50
MC1496 (UA796) (14-pin DIL)	59p
MFC4000R	59p
MFC6040	83p
NE555V (8-pin DIL)	85p
SC1485 (14-pin DIL)	£2-70
SG3402 (14-pin DIL)	£1-99
µA741C (8-pin DIL)	36p
µA741C (14-pin DIL)	45p
µA747C (14-pin DIL)	£1-05
µA748C (8-pin DIL)	38p
ZNA14 (TO18)	£1-20

**VOLTAGE REGULATORS**  
 µA7805 5V 1.5A (TO3) £1-75  
 µA7815 15V 1.5A (TO3) £1-75  
 MVR 5V, 12V, 15V, 500mA (TO3) £1-60  
 µA78M05 5V 500mA (Plastic power) £1-30  
 µA78M15 15V 500mA (Plastic power) £1-30  
 µA78L05 5V 100mA (TO92) 60p  
 µA78L15 15V 100mA (TO92) 60p  
 µA723C Variable 2 to 3V (TO99 or 14-pin DIL) 75p  
 Our catalogue contains application circuits and data for all the above I.C.'s and many more

**● DISCOUNTS**  
 Details in our catalogue. Start collecting MEB Discount Vouchers NOW!

**● SWITCHES**  
 Rotary adjustable stop. 1 pole, 2 to 12 way, 2 pole, 2 to 6 way; 3 pole, 2 to 4 way; 4 pole, 2 or 3 way 38p each  
 Slide Sub-min DPDT 9p  
 Slide Min. DPDT 13p  
 Push to make Non-locking SPST 14p  
 Push-on, Push-off Locking DPST 250V 4A 48p  
 Rocker White DPST 250V 10A 40p  
 Rotary Mains DPST 250V 2A 20p  
 Toggle with ON/OFF plate DPDT 250V 1.5A 25p

**BCD OUTPUT SLIDE SWITCH**  
 Marks the end of the old-fashioned thumb-wheel switch. With 7-segment type read-out. Full details in our catalogue. £1.38

**● PLUGS & SOCKETS**

DIN	PLUG	CHASSIS SOCKET
2-pin	8p	6p
3-pin	9p	7p
4-pin	10p	7p
5-pin A (180°)	10p	7p
5-pin B (240°)	10p	7p
6-pin	10p	8p

**JACK PLUGS**  
 1/2 Std. Mono Plastic Barrel 13p  
 1/2 Std. Mono Metal Barrel 24p  
 1/2 Std. Stereo Plastic Barrel 18p  
 1/2 Std. Stereo Metal Barrel 28p  
 2.5mm Plastic Barrel 9p  
 2.5mm Metal Barrel 15p  
 3.0mm Plastic Barrel 9p  
 3.5mm Metal Barrel 15p

**JACK CHASSIS SOCKETS**  
 2.5mm Open-type metal 8p  
 3.5mm Open-type metal 9p  
 1/2 Std. Mono Open-type metal 10p  
 1/2 Std. Mono Moulded with 2 break contacts 14p  
 1/2 Std. Stereo Open-type metal 15p  
 1/2 Std. Stereo Moulded with 3 break contacts 18p

**PHONO**  
 Plastic-topped Plug 5p  
 Screewed Plug Single 12p  
 Chassis Socket Single 4p  
 Chassis Socket Twin 6p

**● TRANSFORMERS**  
 LT700 min. output. Pri. 1k2; Sec. 5 Ω 200mVA 50p  
 Sub-min mains 6.0-6V 100mA 95p;  
 12.0-12V 50mA 95p  
 (Size both approx. 30 x 27 x 25mm) Min. mains  
 0-6V 500mA, 0-6V 500mA £1-36  
 0-12V 250mA, 0-12V 250mA £1-36  
 0-20V 150mA, 0-20V 150mA £1-36  
 0-24V 125mA, 0-24V 125mA £1-36  
 Mains MTRAT; Sec: 12-15, 20-24, 30V 2A £3-60  
 Mains MT206AT; Sec: 0-15, 20V 1A, 0-15-20V 1A £3-98

**● ORGAN CONSTRUCTION**  
 A Full Scale Electronic Organ that you can Build to Your Own Specification.  
**FULL CONSTRUCTIONAL DETAILS IN OUR LEAFLETS**  
 Leaflet MES 51: Price 15p, describes a fully polyphonic basic organ which can later be used as the basis of a large sophisticated instrument.  
 Leaflet MES 52: Price 5p continues the description of the MES 50 series organs and shows you how to add a second keyboard with lots more stops.



**● THE AMAZING DMO2**  
 A ready-built, tested and guaranteed digital master oscillator. Accurately generates the top 13 notes for your organ system and reduces the complete tuning of your organ to ONE SIMPLE adjustment. New design gives selectable C to C output ranges of (approx.) 4k to 8k (highest) or 2k to 4k or 1k to 2k, etc. right down to 16Hz to 39Hz! And this new compatible design is even smaller—only 3.5in x 3.7in including gold-plated edge connexion.  
 DMO2 includes built in variable depth and rate frequency shift tremulant.  
 DMO2 £12-25 DMO2T £14-25  
 SAJ 110: 7-stage frequency divider in 14-pin DIL package. 8ine or square wave input. Square wave output may be converted to saw-tooth, £1.80 each or 6 for £9.94 or 12 for £18-18.  
 Keyboards high quality, fully sprung.  
 Flat-front 48-note F to E £15-95  
 Sloping-front 49-note C to C £15-95  
 Sloping-front 61-note C to C £20-44  
 Swell pedal with 10k log. pot £6-33  
 \*Spring Line Unit (Short) £3-05  
 \*Spring Line Unit (Long) £8-29  
 \*Reverberation Driver Module £5-34  
 \*S.A.E. please for full details: leaflet MES 24. Gold-clad phosphor-bronze wire 30p per yd. Palladium earth bar 15p per octave length. Contact Blocks 2-make (GB2) 22p  
 Stop Tabs rocker type not engraved (white, red, grey or black) with DPDT switch 59p

**SPECIAL OFFER**  
**5W Audio Amp 1C TBA 810S**  
 with Data and Circuits Price £1.00.

**"ELECTRONICS TODAY INTERNATIONAL"**  
**4600 SYNTHESISER**  
 We stock all parts for this brilliantly designed synthesiser. This includes all the P.C.B.'s, metal-work and drilled and printed front panel giving a truly professional finish. Authoritative opinions agree the E.T.I. International Synthesiser is technically superior to most of today's models. Complete constructional details in our booklet, available shortly. S.A.E. please for price list and specification.  
 We also stock all parts for the P.E. Synthesiser and Minisonic.



P.O. BOX 3, RAYLEIGH, ESSEX. Tel.: Southend-on-Sea (0702)44101

VAT Please add 8% to the final total. Post and packing FREE in U.K. (15p handling charge on orders under £1).

First-class post pre-paid envelope supplied with every order.

# PE SCORPIO Mk 2 ignition system kit new from ELECTRO SPARES

\* 6 OR 12 VOLT  
\* + VE AND - VE GROUND

Here's the new, improved version of the original PE Scorpio Electronic Ignition System—with a big plus over all the other kits—the PE Scorpio Kit is designed for both positive and negative ground automotive electrical systems. Not just +ve ground. Nor just -ve ground. But both! So if you change cars, you can be almost certain that you can change over your PE Scorpio Mk. 2 as well. Containing all the components you need, this Electro Spares PE Scorpio Mk. 2 Kit is simply built, using our easy-to-follow instructions. Each component is a branded unit by a reputable manufacturer and carries the manufacturer's guarantee. Ready drilled for fast assembly. Quickly fitted to any car.

When your PE Scorpio Mk. 2 is installed, you instantly benefit from all these PE Scorpio Mk. 2 advantages.

- ★ Easier starting from cold ★ Firing even with wet or oiled-up plugs ★ Smoother running at high speed
- ★ Fuel saving ★ More power from your engine
- ★ Longer spark plug life ★ No more contact-breaker burn

Electro Spares prices:

De luxe Kit only £10.85 inc. VAT and p & p.  
Ready Made Unit £13.65 inc. VAT and p & p.  
State 6V or 12V system.

Send SAE now for details and free list.

## FM VARICAP STEREO TUNER

As featured in the May 1973 issue of 'Practical Electronics'. Superb Hi-Fi tuner Kit now available from Electro Spares. Including cabinet and all components - pre-set Mullard modules for R.F. and I.F. circuits. Motorola I.C. Phase Lock Loop Decoder for perfect stereo reception. No alignment needed. Guaranteed first time results - or send it back, and we'll return it in perfect order (for a nominal handling charge). Electro Spares price only £28.50 inc. VAT and p & p.

## 'GEMINI' STEREO AMPLIFIER

A superb unit with a guaranteed output of 30 watts RMS per channel into 8 ohms. Full power THD is a mere 0.02%, and frequency response is -3 dB from 20 Hz to 100 kHz into 8 or 15 ohms. Electro Spares have already sold 100s and 100s of these Kits. Get yours now! Depending on your choice of certain components, the price can vary from £50 to £60 inc. VAT and p & p.

- ★ All components as specified by original authors, and sold separately if you wish.
- ★ Full constructional data book with specification graphs, fault finding guides, etc. 55p plus 9p postage.
- ★ Price List only. Please send S.A.E. (preferably 9 x 4 minimum) for full details.

# ELECTRO SPARES



The Component Centre of the North  
288 ECCLESALL RD., SHEFFIELD S11 8PE (C)  
Tel: Sheffield (0742) 668888

## VALVE BARGAINS

Any 5 50p, 10 75p, 50 £3.30, 100 £6.40. Your choice from the following list:

ECC82, ECL80, EB91, EF80, EF183, EF184, PC86, PC88, PC97, PC900, PCC84, PCC89, PCC189, PCF80, PCF802, PCF805, PCL82, PCL84, PCL85, PCL805, PCL86, PFL200, PL36, PL504, PY33, PY81, PY800, PY8B, EH90, 30FL1, 30FL2, 30PL14.

Colour Valves 25p each  
PL508 PL509, PY500/A

Press 4 Button UHF  
Tuners £2.50.

## AERIAL BOOSTERS

We make three types of Aerial Boosters all for set top fitting, with Co-ax Plugs and Sockets.

**B11**—For Stereo and Standard VHF Radio

**B12**—For the older VHF Television, please state BBC1 and ITV Channels.

**B45**—For mon. or colour this covers the complete UHF band.

All Boosters are complete with Battery and take only minutes to fit.

Price £3.40 each

## BARGAIN PACKS

All Components in the Bargain Packs are unused and marked.

**Pack 1**—Polyester (C280) Axial Leads Capacitors—250V/W & 400V/W, very good mixed selection from 0.01 UF to 2.2 UF. Price 100 £1, 1000 £8 (our choice).

**Pack 2**—Electrolytic Capacitors—complete mix selection from 1 UF to 1000 UF, and from 10V/W to 63V/W. Price 100 £1.50, 500 £6 (our choice).

**Pack 3**—Transistors—any 10 80p, any 100 £7 (your choice). AC128 - AC176 - BC113 - BC115 - BC135 - BC153 - BC171 - BC172.

**Pack 4**—15 Mixed Plugs, mixed selection of co-ax, din2-3-5 pins, jack standard—3.5mm-2.5mm. Price £1.

Prices include V.A.T. P. & P. under £1/10p, £1 to £3/15p, above £3/20p. Overseas at cost. Money back guarantee on all orders.

ELECTRONIC MAIL ORDER LTD., 62 BRIDGE ST., RAMSBOTTOM, BURY, LANCS. Tel. Rams. 3036.

## CJL PRICES INCLUDE P&P AND V.A.T.

- AERIAL, telescopic, 15-120cm. . . . . £1.20
- AERIAL, telescopic, h and v swivel, 15-80cm. . . . . £1.78
- BIB HI-FI ACCESSORIES**
- CASSETTE TAPE RECORDER CARE KIT . . . . . £1.95
- CASSETTE SPLICING AND EDITING KIT . . . . . £1.50
- HI-FI STEREO TEST CASSETTE . . . . . £2.10
- 1/4" TAPE EDITING KIT . . . . . £1.35
- GROOV-KLEEN RECORD CLEANER . . . . . £1.85
- EARPHONE, stethoscope style, 8 ohm dynamic . . . . . £1.00
- HAND DRILL, (Leytout), compact precision drill, 5/16" chuck. Gears totally enclosed, S/L bearings. . . . . £2.99
- INTEGRATED CIRCUITS**
- AUDIO POWER AMPLIFIER (National) LM380 . . . . . £1.00
- A.M. RADIO RECEIVER (RCA) CA3123E . . . . . £1.40
- F.M. STEREO DECODER (Motorola) MC1310P . . . . . £2.80
- TIMER (Signetics) NE555V . . . . . £0.78
- VOLTAGE REGULATOR (Fairchild) uA7805 . . . . . £1.70
- VOLTAGE REGULATOR (Signetics) NE550A . . . . . £0.80
- D.I.L. SOCKETS (Pk of 3) 8 or 14 pin . . . . . £0.50
- KEYNECTOR, rapid connect to mains-single/multiple leads. Built-in piano switches neon & 13A fuse . . . . . £3.20
- LOCKFLEX RULE (Rabone Chesterman), 3m/10ft precision pocket rule. Easy to read, 13mm/1/2" wide steel tape. Blade length lockable-power return. . . . . £0.93
- A super rule . . . . . £0.93
- MICROPHONE, lightweight dynamic, remote start stop, 200 ohms, 100-10kHz, 6mV average output . . . . . £1.80
- MULTIMETER, attractive design, Vdc-10, 50, 250, 1,000. Vac-10, 50, 250, 1,000. Idc-100mA. R-150k . . . . . £4.95
- SIGNAL INJECTOR, audio through video signals, excellent for servicing amplifiers, radio & tv . . . . . £3.92
- SOLDERING IRON, 25 WATT, (Antex), X25, 240V, Very low leakage, 1/8" long 11fe bit (interchangeable) . . . . . £1.85
- 3/32" bit £0.45  3/16" bit £0.45  Element £0.95
- STAND, ST3, High grade base, chrome plated spring, sponges and accomodation for spare bits . . . . . £0.95
- SPEAKER, miniature, 75mm dia, 8 ohms. . . . . £0.80

**CJL** CJL LTD. P.O. BOX 34, CANTERBURY, CT1 1YT



# SPARKRITE MK 2

## CAPACITIVE DISCHARGE ELECTRONIC IGNITION KIT

"Sparkrite MK 2" is a high performance, high quality, capacitive discharge, electronic ignition system. Sparkrite completely eliminates problems of the contact breaker. Misfire due to contact breaker bounce is electronically eliminated, contact breaker burn is eliminated, the condition of the contacts is not relevant to the performance of the ignition, and the system is no longer dependent on the dwell period for recharging.

**Sparkrite will give you:** Up to 20% better fuel consumption, instant all weather starting, cleaner plugs, faster acceleration, higher top speed, longer coil and battery life, efficient fuel burning and less air pollution, smoother running, continual peak performance.

**The Kit comprises everything needed.** All ready drilled and guaranteed components and parts.

**Prices:** D.I.Y. assembly kit £10.93\*. Ready built unit £13.86\*. (Both to fit all vehicles with coil/distributor ignition up to 8 cylinders.) Switch for instant changeover from "Sparkrite" ignition to conventional ignition £2.79\*. R.P.M. limiting control £2.42\*. Details of more specialised units on request.

\*Inc. V.A.T., p & p. CALL IN AND SEE US FOR A DEMONSTRATION.

## ELECTRONICS DESIGN ASSOCIATES of WALSALL


### ALUMINIUM BOXES

Prices include lids, screws and V.A.T. (@8%). Add 18p to the total order value for postage and packing.

No. 7	5 1/2" x 2 1/2" x 1 1/2" high	47p
No. 8	4" x 4" x 1 1/2" high	48p
No. 9	4" x 2 1/2" x 1 1/2" high	46p
No. 10	5 1/2" x 4" x 1 1/2" high	49p
No. 11	4" x 2 1/2" x 2" high	46p
No. 12	3" x 2" x 1" high	38p
No. 13	6" x 4" x 2" high	58p
No. 14	7" x 5" x 2 1/2" high	75p
No. 15	8" x 6" x 3" high	93p
No. 16	10" x 7" x 3" high	£1.14
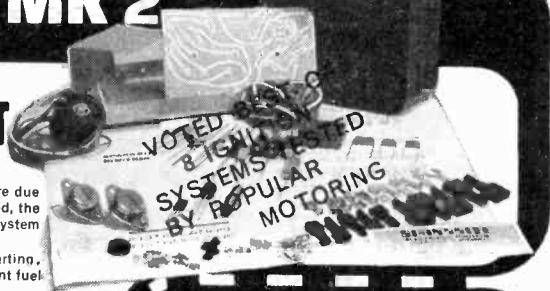
### FLUORESCENT LIGHT KIT

You can build this reverse polarity protected 12v, 8w, fluorescent light. Everything needed is supplied: white enamelled ready drilled metalwork, ready drilled heatsink, printed circuit board, high quality components and transformer, end caps, cable, the fluorescent tube, nuts bolts washers, and simple assembly and operating instructions. Prices: Assembly kit £3.19\*, Ready built £3.78\*. Diffuser £59p\*. \*inc. V.A.T. p. and p.



## ORDER NOW

**TO** Electronics Design Associates  
Dept PW4  
82 Bath Street, Walsall, WS1 3DE.  
Phone 33652.

**FROM** Name

Address

**QTY**

Please Supply  
SPARKRITE MK 2 DIY Assembly kits  
to build Neg. or Pos. @ £10.93  
SPARKRITE MK 2 Ready Built  
Negative earth @ £13.86  
SPARKRITE MK 2 Ready Built  
Positive earth @ £13.86  
Ignition changeover switches @ £2.79  
R.P.M. Limit systems in the above  
units @ £2.42  
Fluorescent light assembly kits  
@ £3.19  
Fluorescent light built units @ £3.78  
Diffusers for the above @ 59p  
of number alum. boxes @  
of number alum. boxes @  
of number alum. boxes @

I enclose cheque/P.O.s for £.....

Cheque No. ....

(Send SAE if brochure only required)

## FET & SEMICONDUCTORS AT LOWER PRICES! TTL DELIVERY PRICES INCLUDE VAT (AT 8%)

Type	1/24 25/99 100+	Type	1/14 25/99 100+	Type	1/24 25/99 100+		
7400	0-14 0-14 0-12	7437	0-31 0-29 0-27	7476	0-35 0-32 0-31		
7401	0-15 0-14 0-13	7440	0-15 0-14 0-13	7480	0-50 0-47 0-44		
7402	0-15 0-14 0-13	7442	0-73 0-68 0-64	7483	0-95 0-89 0-83		
7403	0-15 0-14 0-13	7445	0-99 0-92 0-86	7486	0-34 0-33 0-31		
7404	0-18 0-16 0-15	7447	0-98 0-96 0-87	7488	3-56 3-33 2-96		
7405	0-18 0-16 0-15	7450	0-15 0-14 0-13	7490	0-49 0-48 0-46		
7406	0-18 0-16 0-15	7451	0-15 0-14 0-13	7492	0-54 0-50 0-47		
7410	0-15 0-14 0-13	7453	0-15 0-14 0-13	7493	0-51 0-50 0-47		
7412	0-23 0-21 0-20	7454	0-15 0-14 0-13	7495	0-73 0-68 0-64		
7413	0-33 0-32 0-31	7460	0-15 0-14 0-13	7496	0-83 0-78 0-73		
7417	0-33 0-32 0-31	7472	0-29 0-27 0-25	74107	0-34 0-33 0-31		
7420	0-15 0-14 0-13	7473	0-33 0-32 0-31	74121	0-34 0-33 0-31		
7427	0-31 0-29 0-27	7474	0-33 0-32 0-31	74123	0-70 0-66 0-64		
7430	0-15 0-14 0-13	7475	0-51 0-49 0-47	74157	0-87 0-81 0-72		
7432	0-31 0-29 0-27	7476	0-35 0-32 0-31	74175	0-99 0-95 0-84		
1N4148 4p,	1N4001 4ip,	1N4002 5p,	1N4003 6p,	1N4004 6p,	ZTX107 10p,	ZTX108 8ip,	ZTX109 11ip.

All devices full spec. by famous manufacturers. TTL MAY BE MIXED FOR QUANTITY PRICES. S.A.E. for catalogue (includes TTL pin layout guide). 10p P. & P. on orders under £2, otherwise POST FREE.

J. C. JONES (Dept. PW3)

46 BURSTELLARS, ST. IVES, HUNTINGDON PE17 4XX  
(Mail Order only)

## FELSTEAD ELECTRONICS (PW90), LONGLEY LANE, GATLEY, CHEADLE, CHESHIRE SK8 4EE

**STYL** Replacements for virtually all ACOS, BSR, COLLARO, GARRARD, PHILIPS, RONETTE, SONOTONE. Single Tip: Sapphire 19p, Diamond 27p. Double Tip: Can be Stereo/LP + 78 or ST/LP Sapphire 37p. Double Tip: Diamond ST/LP + Sapphire 78 65p. Diamond ST/LP + Diamond ST/LP £1.25. For GOLDBRING Diamond G800, G800H and G850 at £2.10 each. G800E at £4.10. Charges 10p any quantity FREE LIST (FOR SAE) FULL DETAILS STYL AND CARTRIDGE EQUIVALENTS including SHURE, PICKERING, AUDIO-TECH, B & O, AND MANY MORE STYL FOR MAGNETIC AND CRYSTAL PICK-UPS.

**CARTRIDGES.** All with styl and fittings. Replacements for ACOS GP/91 8C (Stereo—mono compatible series) at £1.20, GP93 Stereo at £1.80, GP84 Stereo Ceramic at £2.20. Actual GP67-2, Front switch at £1.10. For BSR X3H, X5H and X5M at £1.50 each. SK5H and SK6M at £1.80 each. TC8H at £1.60. TCS Stereo, 3 pins £2.30; charges 10p any quantity.

**RECORDING TAPE.** ALL FINEST BRITISH MYLAR 5" 600ft. 40p; 5" 900ft. 60p; 3 1/2" 1200ft. 84p, 7" 1800ft. £1.10. Charges for 5" and 5 1/2". 1-4 13p each; 5 and over, 33p the oz. Charges for 7", 1-3 15p each, 4-5 35p the lot, 6 and over 40p the lot.

**CASSETTES** with screws. In library cases. C00—38p. C90—44p, C120—50p each. (Charges up to five, 5p each, six to ten, 25p the lot).

**SPEAKERS** 2 1/2", 3, 8 or 64 ohms (state which) 55p. (Charges 10p each.)

**CONNECTING WIRE.** Pkts of 5 coils, asstd. cols each 5yds. Solid core 19p Flexible 21p (Charges 10p per pack).

**EARPIECES.** Magnetic 2.5mm or 3.5mm plugs (state which) 15p. CRYSTAL (3.5mm only 35p. (Charges all 10p up to 6).

**VIBRATORS.** 7 pin SYNCH. (12SR7 type) 75p, 4-pin NON-synch (121HD4) 45p (Charges all 10p each).  
Send SAE for free styl, cartridge, accessories and components list. All prices include VAT.

## ENGINEERS

# FREE

YOURSELF FOR A

# BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This helpful guide to success should be read by every ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.



POST NOW

CUT OUT THIS COUPON  
CHOOSE A BRAND NEW FUTURE HERE!

Tick or state subject of interest. Post to the address below.

- |   |  |                          |  |                          |
|---|--|--------------------------|--|--------------------------|
| Build-As-You-Learn PRACTICAL RADIO AND ELECTRONICS (with kit) | Electronic Engineering                   | <input type="checkbox"/> | CITY AND GUILDS Installations and Wiring | <input type="checkbox"/> |
| Electrical Engineering  | Computer Electronics                     | <input type="checkbox"/> | CITY AND GUILDS Electrical Technicians   | <input type="checkbox"/> |
| Electrical Installations and Wiring                           | Computer Programming                     | <input type="checkbox"/> | CITY AND GUILDS Telecommunications       | <input type="checkbox"/> |
| Electrical Draughtsmanship                                    | General Radio and TV Engineering         | <input type="checkbox"/> | Radio Amateurs' Exam etc. etc.           | <input type="checkbox"/> |
| Electrical Mathematics  | Radio Servicing, Maintenance and Repairs | <input type="checkbox"/> |  |                          |
|   | Transistor Technology                    | <input type="checkbox"/> |  |                          |

To ALDERMASTON COLLEGE Dept. EPW-02, Reading RG7 4FP

EPW-02

NAME (Block Capitals Please)

ADDRESS

POST CODE

Other subjects

Age

Accredited by C.A.C.C.

Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

# ALL OUR PRICES INCLUDE V.A.T.

## BSR HI-FI AUTOCHANGER STEREO AND MONO

Plays 12", 10" or 7" records  
Auto or Manual. A BSR  
quality unit backed by BSR  
reliability with 12 months'  
guarantee. AC 800/250V.  
Size 12 1/2 x 11 in.



Above motor board 3 1/2 in.  
Below motor board 2 1/2 in.  
With STEREO/MONO CARTRIDGE £7-95 Post 45p.

## PORTABLE PLAYER CABINET

Modern design. Size 18" x 15" x 7" resin  
covered. Large front grille. Hinged lid. Chrome  
fittings. Motor board cut for Garrard deck.  
Few only, in red and black. £4-50 Post 45p.

## SOLID MAHOGANY PLINTH

With P.V.C. Cover. Cut out for most  
B.S.R. or Garrard decks.  
Size 12 1/2 x 14 1/2 x 7 in. £6-50 Post 45p.

## BSR JUNIOR SINGLE PLAYER

Heavy duty 4-speed motor with  
separate pick-up arm fitted  
LP/78 turnover mono. £4-95 Post 25p  
compatible cartridge.



## R.C.S. DISCO DECK SINGLE RECORD PLAYER

Fitted with auto stop, stereo/mono cartridge. Base-  
plate. Size 11 in x 8 1/2 in. Turntable. Size 7 in diameter. A/C  
mains. 220/250V motor has a separate winding 14 volt to  
power a small amplifier.  
3 speeds plays all size  
records. £5-50 Post 25p.

## COMPLETE STEREO SYSTEM

Two full size loudspeakers 13 1/2 x 10 x 8 1/2 in. Compact  
unit clips to loudspeakers making it extremely practical.  
Overall size only 18 1/2 x 10 x 8 1/2 in. 3 watts per  
channel, plays all records 33  
rpm 45 rpm.  
Separate vol-  
ume & tone  
controls 240V  
AC mains

Attractive  
Teak finish  
Weight 12 lbs. Bargain Price  
£25 85p carriage

## SPECIAL OFFER! SMITH'S CLOCKWORK 15 AMP TIME SWITCH 0-60 MINUTES



Single pole two-way surface mounting  
with fixing screws. Will replace existing  
wall switch to give light for return home,  
garage, automatic anti-burglar lights etc. Variable knob  
Turn on or off at full or intermediate settings.  
Fully insulated. Makers last list price £4-50. Brand new and  
fully guaranteed. OUR PRICE £2-20 Post 25p.

## CASSETTE RECORDER MOTOR ONLY. 6 Volt.

Will replace many types. Ideal for models. £1-25.

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2 in sides  
6 x 4 in 45p; 6 x 6 in 53p; 10 x 7 in 55p; 18 x 8 in 85p;  
14 x 9 in 90p; 16 x 9 in 90p; 12 x 8 in 50p; 16 x 10 in £1.

ALUMINIUM BOXES 3 x 3 x 3 in. 60p; 4 x 4 x 4 in. 70p.  
6 x 4 x 4 in. 80p. 9 x 4 x 4 in. £1. 12 x 4 x 4 in. £1-30.

ALUMINIUM PANELS 18 s.w.g. 8 x 4 in 12p; 8 x 6 in 19p;  
14 x 8 in 29p; 10 x 7 in 24p; 12 x 8 in 28p; 12 x 8 in 34p;  
16 x 6 in 24p; 14 x 9 in 40p; 12 x 12 in 47p; 16 x 10 in 60p.

1 1/2 inch DIAMETER WAVELENGTH SWITCHES 45p. EA.  
2 p. 2-way, or 2 p. 4-way, or 3 p. 4-way.,  
1 p. 1 2-way, or 4 p. 2-way, or 4 p. 3-way.

TOGGLE SWITCHES, sp. 20p; dp. 25p; dp. dt. 30p.

R.C.S. STABILISED POWER PACK KITS  
All parts and instructions with Zener Diode. Printed Circuit  
Bridge Rectifiers and Double Wound Mains Transformer.  
Input 200/240V a.c. Output voltages available 6 or 9 or 12  
or 15 or 18 or 20V d.c. at 100mA or less.  
PLEASE STATE VOLTAGES REQUIRED. £2-20 Post  
Details S.A.E. Size 3 1/2 x 1 1/2 in. 20p

## R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape P.U., Guitar, etc. Can be used with  
Battery 9-12v. or H.T. line 200-300V. D.C. operation. Size  
1 1/2" x 1 1/2" x 1/2". Response 25 c.p.s. to 25 Kc/s. 25 db gain.  
For use with valve or transistor equipment. £1-25 Post  
Full instructions supplied. Details S.A.E. 10p

NEW TUBULAR ELECTROLYTICS		CAN TYPES	
2/250V 14p	250/25V 14p	18+18+18/275V 45p	
4/250V 14p	500/25V 20p	60+50/800V 50p	
8/250V 18p	100+100/275V 65p	82+32/450V 60p	
16/250V 22p	150+200/275V 70p	100+50+50/350V 85p	
32/500V 50p	8+8/450V 25p	32+32+32/350 55p	
25/25V 10p	8+18/450V 25p	900MFD/350V 85p	
50/80V 10p	18+16/450V 40p	4700/63V 95p	
100/25V 10p	32+32/350V 40p		

LOW VOLTAGE ELECTROLYTICS.  
1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.  
500mF 15V 15p; 25V 15V; 25V 15V; 25V 15V.  
1000mF 12V 20p; 25V 35p; 50V 47p; 100V 70p.  
2000mF 6V 25p; 25V 42p; 50V 57p; 4700/63V 95p.  
2500mF 50V 62p; 3000mF 25V 47p; 50V 65p.  
5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p; 50V 95p.  
500V-0.001 to 0.05 4p; 0.1-10p; 0.25-12p; 0.47-25p.  
CERAMIC 1pF to 0.01mF, 4p. Silver Mica 1p to 5000pF, 4p.  
PAPER 250V-0.1 7p; 0.5 15p; 1mF or 2mF 150V 15p.  
MICRO SWITCH single pole changeover 20p  
MICRO SWITCH sub min 25p.  
TWIN GANG. "0-0" 208pF+176pF, £1-10.  
Slow motion drive 385pF+365pF with 25pF+25pF, 50p;  
500pF standard twin gang 75p. 120 PF twin gang 50p.  
SHORT WAVE SINGLE. 10pF, 80p; 25pF, 55p; 50pF, 65p.

ELAC 9 x 5 in. HI-FI SPEAKER. TYPE 69RM. THIS  
FAMOUS AND WIDELY USED UNIT NOW  
AVAILABLE AT BARGAIN PRICE £2-95  
10 WATT, 8 OHM. CERAMIC MAGNET.

NEON PANEL INDICATORS. 250V AC/DC Amber. 30p  
RESISTORS. 1/2 w., 1 w., 20%, 1p; 2 w. 5p. 10 Ohm to 10M.  
HIGH STABILITY. 1 w. 2%. 10 Ohms to 6 meg. 10p.  
Dials 5%. Preferred tolerance 10 Ohms to 10 meg. 4p.  
WIRE-WOUND RESISTORS. 5 Ohm, 10 watt, 16 watt,  
10 Ohms to 100K, 10p each; 2w 0.5 Ohm to 8.2 Ohms 10p.  
TAPE OSCILLATOR COIL. Valve type, 35p.  
FERRITE ROD 8" x 1/2"; 6" x 1/2"; 3" x 1/2" 10p.

## MAINS TRANSFORMERS ALL POST 25p each

250-0-250V 50MA. 6.3-2A £2-50.  
250-0-250 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. 24-00  
350-0-350 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a. 25-00  
300-0-300 v. 120 mA. 6.3 v. 4 a. C.T.; 6.3 v. 2 a. 28-00  
MINIATURE 200 v. 20 mA. 6.3 v. 1 a. 2 1/2 x 2 1/2 in. 75p  
MIDGET 220 v. 45 mA. 6.3 v. 2 a. 2 1/2 x 2 1/2 in. 90p  
HEATER TRANS. 6.3 v. 3 amps. £1-20 1/2 amp. 85p  
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs  
at 2 amp., 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. 24-00  
1 amp., 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 24-00  
2 amp., 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 24-00  
3 amp., 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 27-50  
5 amp., 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 29-75  
3, 5, 8, 10, 13 or 5-0-5 v. 5 amp. £1-70. 6-0-6 v. 500 mA  
90p. 9 v. 1 amp 95p. 12 v. 300 mA 75p. 12 v. 500 mA  
85p. 12 v. 750 mA 95p. 48 v. 2 amp. tapped 12 v. or 36 v.  
25-60. 20V 3 amp. £2. 40V 3 a. £2.50. 25V 0-25V 4 a. £3.  
AUTO TRANSFORMERS. 115v to 230v or 230v to 115v.  
150w. £4-00; 500w. £7-50; 750w. £15-00; 1000w. £18-00.  
CHARGER TRANSFORMERS. Input 200/250V.  
for 6 or 12v., 1 amp. £1-50; 2 amp. £1-80; 4 amp. £3  
BATTERY CHARGERS. Ready built with leads and clips  
1 1/2 amp. £2; 4 amp. £4; 5 amp. £4-50.  
FULL WAVE BRIDGE CHARGER RECTIFIERS:  
6 or 12v. outputs. 1 1/2 amp. 40p; 2 amp. 55p; 4 amp. 85p.

## MAINS ISOLATING TRANSFORMER

Primary 0-110-240V. Secondary 0-240V. 3 amps. 780  
watts. Insulated terminals. Varnish impregnated. Fully  
enclosed in steel case with fixing feet.  
Famous make. (Value £19) OUR PRICE £12 Carr.  
Suitable for outside use. 95p

## SET OF 3 MOTORS FOR COLLARO STUDIO 115 volt TAPE DECK £1-50 Post 50p.

## VOLUME CONTROLS 80 Ohm Coax 5p yd.

5 K. Ohms to 2 Meg. LOG or  
LIN. L/S 20p. D.P. 35p.  
STEREO L/S 55p. D.P. 75p.  
Edge 5K. S.P. Transistor 25p

BRITISH AERIALITE  
AERIAL-AIR SPACED  
40 yd. £2; 60 yd. £3.  
FRINGE LOW LOSS 10p yd  
Ideal 625 and colour.

Wirewound controls 1 1/2 in. diam. 3 watts. 10 Ohms to 100K  
British made with long spindles 2 in. dia 80p ea.

DUAL CENTRIC POT 500k LOG + 500k LIN D.P.  
switch. Inner spindle 3 1/2 in; outer spindle 2 1/2 in. 75p.

## E.M.I. 13 1/2 x 8 in. SPEAKER SALE!

With twin tweeters. £4-50  
And crossover. 10  
watt. State 3 or 8 or  
15 Ohm. As illustrated. Post 25p



With flared tweeter cone and ceramic  
magnet. 10 watt.  
Bass res. 45-80 cps.  
Flux 10,000 gauss.  
State 3 or 8 or 15 Ohm. Post 25p

## Bookshelf Cabinet £6-60

Finet wood front 18x10x7 in. Teak Veneer Post 45p


## GOODMANS 6 1/2 in. HI-FI WOOFER

8 Ohm, 10 watt. Large ceramic magnet  
Special Rubber cone surround.  
Frequency response 30-19,000  
cps. Ideal P.A. Columns,  
Hi-Fi Enclosure Systems, etc.  
Suitable cabinet 12 x 8 x 6 24-00.  
Suitable Tweeter £2-00.


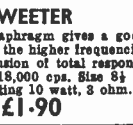
## ELAC CONE TWEETER

The moving coil diaphragm gives a good  
radiation pattern to the higher frequencies  
and a smooth extension of total response  
from 1,000 cps to 18,000 cps. Size 8 1/2  
x 3 1/2 x 2 in. deep. Rating 10 watt, 3 Ohm.  
Crossover £1-25 Post 20p £1-90



## GOODMANS 8 in. WOOFER

8 Ohm 12 watt. Deep cone.  
Heavy ceramic magnet. Bass  
resonance 35 cps. Frequency  
response 30-3,000 cps.  
Ideal bass unit for £3-75  
Hi-Fi systems



LOUDSPEAKERS P.M. 3 OHMS. 7 x 4 in. £1-25; 6 1/2 in. £1-60;  
8 x 6 in. £1-60; 8 in. £1-75; 10 x 6 in. £1-90; 10 in. £2-00.  
SPECIAL OFFER. LOUDSPEAKERS: All Brand New.  
3 Ohm, 2 1/2 in; 3 1/2 in; 5 Ohm, 2 1/2 in; 5 1/2 in; 5 in x 8 in;  
5 in. 15 Ohm, 3 1/2 in; 6 in; 6 x 4 in; 5 in x 8 in; 7 x 4 in; 8 x 5 in.  
25 Ohm, 2 1/2 in; 3 in; 6 x 3 in; 6 in. 35 Ohm, 3 in.  
80 Ohm, 2 1/2 in; 2 1/2 in. 120 Ohm, 3 in. £1 EACH.

LOUDSPEAKER VOLUME CONTROL 15 Ohm 10 watt  
with 1 in long threaded bush for wood panel mounting 65p.

RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 8 in.  
diameter 4W £2-50, 10 in. diameter 4W £2-95. Post 55p.  
12 in. diameter, 6W, £3-50; 3 or 8 or 15 Ohm models.  
SPEAKER COVERING MATERIALS. Sample Large S.A.H.  
Horn Tweeters 2-16Kc/s. 10W 8 Ohm or 16 Ohm £2-20.  
De Luxe Horn Tweeters 2-18 Kc/s. 15W, 8 Ohm 44-00.  
TWO-WAY 3,000 c.p.s. CROSS OVERS 3, 8 or 15 Ohm £1-25.  
3-WAY CROSSOVER 850 cps and 3000 cps (25 watt) £1-95.

## GOODMANS CONE TWEETER 18,000 cps. 25 watts. 8 Ohm. Price £3-30.

## ELECTRO MAGNETIC PENDULUM MECHANISM

1-6v d.c. operation over 250 hrs. continuous on SP2 battery.  
Fully adjustable swing and speed. Ideal displays teaching  
electro magnetism or for metronomes; strobe etc. 95p. Post 25p

## R.C.S. VALVE AMPLIFIER

2 Stage Triode Pentode valve. 3 watts 3 Ohm output. Volume  
on/off and tone controls AC mains. Complete and tested.  
With Loudspeaker. £4-50 Post 25p.

## WEYRAD COILS

P50/1AC-60p. RA2W 85p. Twin Gang £1-10.  
P50/2CC-40p. OP11 65p. Printed Circuit 35p.  
P50/3CC-40p. LFDT4. 65p. IN STOCK

## COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 18p

OUTLET BOXES, SURFACE MOUNTING 25p.  
BALANCED TWIN RIBBON FEEDER 300 Ohms, 7p yd.  
JACK SOCKET 8 1/2 in. open-circuit 15p, closed circuit 25p;  
Chrome Lead Socket 45p. Phone Plugs 10p. Phone Socket 5p  
JACK PLUGS 5 1/2 in. Chrome 20p; 3 1/2 in. Chrome 15p. DIN  
SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS  
Lead 3-pin 18p; 5-pin 15p. DIN PLUGS 3-pin 15p; 5-pin 25p.  
VALVE HOLDERS 5p; CERAMIC 10p; CANS 5p.

## FM/VHF AERIAL FEEDER CABLE

300 Ohm suitable for stereo 7p per yard.

## BRITISH FM/VHF TUNING HEART

88 to 108 Mc/s British made. 2 Transistors ready aligned—requires 10.7  
Kc/s IF. Complete with tuning gang.  
Connections supplied by some  
technical experience required.  
SUITABLE I.F. STRIP £2-95.  
Post 20p.

ALL PRICES INCLUDE VAT MINIMUM POST AND PACKING 20p. CALLERS WELCOME

# RADIO COMPONENT

Illustrated Brochure, Radio Books & Component Lists 10p. Written guarantee.

# ALL OUR PRICES INCLUDE V.A.T.

## E.M.I. WOOFER AND TWEETER KIT

THE PAIR, Post 45p.  
(Available separately.  
Woofer £4 25; Tweeter  
£1 90).

Comprising a fine example of a Woofer 10 1/2 x 6 1/2 in. with a massive Ceramic Magnet, 440s. Gauss 18,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3 1/2 in. square has a special lightweight paper cone and magnet flux 10,000 lines. Crossover condenser and full instructions supplied.

Impedance Standard 8 ohms  
Maximum power 12 watts  
Useful Response 25 to 18,000 cps  
Bass Resonance 45 cps

SUITABLE ENCLOSURE 20 x 18 x 9 in.  
MODERN DESIGN. TEAK WOOD FINISH.



£10-50  
Post 75p

## ELAC 8in. or 10 x 6in. HI-FI SPEAKER



Dual cone plasticized roll surround. Large ceramic magnet. 50-16,000 cps. Bass resonance 55 cps. 8 ohm impedance. 8in. 10 watts

£3-75

## TEAK VENEER HI-FI SPEAKER CABINETS Fluted Wood Fronts

MODEL "A". 20 x 13 x 9 in.  
For 12in. dia. Post  
10in. speaker. £10-50 75p

MODEL "B". 16 x 10 x 7 in.  
For 12 x 8in. or Post  
8in. speaker. £6-60 45p



LOUDSPEAKER CABINET  
WADDING 18in. wide, 20p ft.

BAKER RECOMMENDED 12 inch Enclosure 4 cubic ft.  
HI-FI CABINET £18-50 Carr. £2 each.  
Size 30 x 20 x 12in. Teak Finished Fluted Front.

TEAKWOOD LOUDSPEAKER FRONT GRILLS  
Modernise your cabinets with the Grooved look. Sizes—  
12 1/2" x 10 1/2"—75p. 10 1/2" x 7 1/2"—45p.

BARGAIN 4 CHANNEL  
TRANSISTOR MONO  
MIXER. Add musical  
highlights and sound effects  
to recordings. Will mix  
Microphone, records, tape  
and tuner and separate  
controls into single output.  
9 volt battery operated.



£4-50

STEREO VERSION OF ABOVE 25-95.

## R.C.S. STEREO FM TUNER BRITISH MADE



This completely cased mains powered Hi-Fi  
Tuner with brushed aluminium fascia is British  
made using the latest circuitry.

£23  
Post 45p.

BARGAIN 3 WATT AMPLIFIER. 4 Transistor  
Push-Pull Ready built with volume, treble and  
bass controls. 18 volt battery operated.

£3-50

## WAFER HEATING ELEMENTS THIN

OFFERING 1001 USES for every type of heating and  
drying applications in the home, garage, greenhouse,  
factory (available in manufacturing quantities). Approx.  
size 10 1/2 x 8 1/2 in. Operating voltage 200/250V, a.c.  
250 watts approx. Printed circuit element enclosed in  
asbestos fitted with connecting wires. Completely flexible  
providing safe Black heat. British-made for use in photo-  
copiers and print drying equipment.  
Ideal for home handymen and experimenters. Suitable  
for Heating Pads, Food Warmers, Convector Heaters, etc.  
Must be clamped between two sheets of metal or asbestos,  
etc., to make efficient clothes dryers, towel rails—ideal for  
airing cupboards. Ideal for anti-frost device for the garage  
—preventing frozen radiators or acting as oil sump heater.  
Use in the greenhouse for seed raising and plant protection.  
Invaluable aid for birds, hives, incubators, etc., etc. Can  
be used in series for lower heat. Or in parallel for higher  
heat applications.

ONLY 40p EACH (FOUR FOR £1-50)

ALL POST PAID—Discounts for quantity.

## BAKER MAJOR 12" £8-50



30-14,500 c/s. 12in. double  
cone, woofer and tweeter cone  
together with a BAKER  
ceramic magnet assembly  
having a flux density of  
14,000 gauss and a total flux  
of 145,000 Maxwells. Bass  
resonance 40 c/s Rated 20  
watts. NOTE: 8 or 8 or  
15 ohms must be stated.

Module kit, 30-17,000 c/s  
with tweeter, crossover, baffle  
and instructions. £10-95

Please state 8 or 8 or 15 ohms.

## "BIG SOUND" BAKER SPEAKERS

Robustly constructed to stand up to  
long periods of electronic power.  
As used by leading groups and discos

Useful response 30-13,000 cps.  
Bass Resonance 55 cps.

GROUP "25" £7-75  
12in. 25 watt  
8, 8 or 15 ohms.

GROUP "35" £8-50  
12in. 35 watt  
8, 8 or 15 ohms.

GROUP "50" £16-50  
15in. 50 watt  
8 or 15 ohms.

GROUP 50/12in. £12-95  
50 watt 8 or 15 ohms

Group + PA Cabinets in stock  
Send for Leaflet.



## MAJOR 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

All purpose transistorised.  
Ideal for Groups, Disco and P.A.  
4 inputs speech and music. 4 way  
mixing. Output 8/15 ohm. a.c. Mains.  
Separate treble and bass controls.  
Guaranteed. Details SAE.



£49 Carr.  
£1-00

NEW MODEL—MAJOR 50 WATT £39-95  
Carr. £1.

4 inputs 2-way mixing. 2 outputs separate treble and bass  
controls. Ideal disco or p.a. amp.

## DE LUXE 100 WATT VALVE AMPLIFIER CHASSIS

4 input 10 wide range controls. For Mikes, Discos, Organs  
Guitars, etc. 4, 8 & 15 ohm loudspeakers matching 869-00.

THE "INSTANT" BULK TAPE  
ERASER & HEAD DEMAGNETISER.  
Suitable for cassettes, and all sizes of  
tape reels. A.C. mains 200/250V.  
Leaflet S.A.E. £3-75 Post  
30p



## QUALITY LOUDSPEAKER ENCLOSURE

Teak veneered 3/4 in thick wood cabinet. Size  
18 1/2 in x 18 1/2 in x 8 1/2 in. Weight 23lbs. This  
cabinet features a wide mesh Silver Grill  
covering a separate compartment for mounting  
Tweeters or Mid-Range Horn. The fully  
sealed bass compartment is cut out for  
6 1/2 inch Woofer. £7-50 Carr. 85p.  
Rosewood Version £8-50 Carr. 85p.  
Baffle could be cut to take larger speaker.



SPECIAL OFFERS  
100 Ohm 20 watt Rheostat 2 1/2 in diam. Ceramic Former.  
Screw Terminals 1/2 in. diam. spindle. 95p. Post 25p.  
AC mains relay 3 pole change over 75p.

REVERSIBLE 4 POLE MOTOR  
1,400 r.p.m. Reversible 48 Watt. £2-25  
spindle 1 1/2" x 7/32", size 3 1/2" x 3".  
As illustrated, 240v. AC mains. Post 35p

E.M.I. TAPE MOTOR  
4 pole, 240 v. 135 mA. Size 3 1/2 x 2 1/2 x 2 1/2 in. £1-85  
1200 rpm. Spindle 1/2 in diameter. Post 30p

## BAKER HI-FI SPEAKERS HIGH QUALITY — BRITISH MADE

### REGENT 12in. 15 watts

An inexpensive unit for the  
beginner in high fidelity and  
for general purposes. May be  
used to improve any Radio,  
Amplifier, Hi-Fi or Television  
receiver.

Bass Resonance 45cps  
Flux Density 12,000gauss  
Useful response 45-13,000cps  
8 or 8 or 15 ohm models.

£7-75

### DE-LUXE Mk II 12in 15 watts

Especially designed to provide  
full range reproduction at an  
economical cost. Suitable for  
use with any high fidelity  
system. Built-in concentric  
tweeter cone.

Bass Resonance 30cps  
Flux Density 14,000gauss  
Useful response 25-16,000cps  
8 or 15 ohms models.

£9-75

### SUPERB 12in. 20 watts

A high quality loudspeaker,  
its remarkable low cone  
resonance ensures clear  
reproduction of the deepest  
bass. Fitted with a special  
copper drive and concoidal  
tweeter cone resulting in full  
range reproduction with  
remarkable efficiency in the  
upper register.

Bass Resonance 25cps  
Flux Density 16,500gauss  
Useful response 20-17,000cps  
8 or 15 ohms models.

£13-80

### AUDITORIUM 12in. 25 watts

A full range reproducer for  
high power, Electric Guitars,  
public address, multi-speaker  
systems, electric organs.  
Ideal for Hi-Fi and Disco-  
theques.

Bass Resonance 35cps  
Flux Density 15,000gauss  
Useful response 25-16,000cps  
8 or 15 ohms models.

£12-95



### AUDITORIUM 15in. 35 watts

A high wattage loudspeaker  
of exceptional quality with a  
level response to above  
8,000 cps. Ideal for Public  
Address, Discotheques, Elec-  
tronic instruments and the  
home Hi-Fi.

Bass Resonance 35cps  
Flux Density 15,000gauss  
Useful response 20-14,000cps  
8 or 15 ohms models.

£16-50

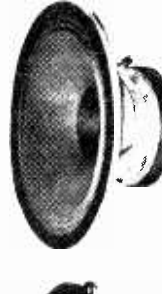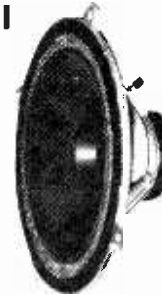Hi-Fi Enclosure Manual containing plans, designs, cross-  
over data and cubic tables. 60p. Post 3p.



CUSTOMERS FREE CAR PARK

# SPECIALISTS

(Exports Remit cash and extra postage.)

OPEN 9-6. WEDNESDAY 9-1. SATURDAY 9-5. Closed for lunch 1-15-2-30

## 337 WHITEHORSE ROAD . CROYDON

Buses 50, 68, 159. Rail Selhurst

Telephone 01-684-1665

**NEW SINCLAIR IC20** IC20 10+10 Watt stereo amplifier kit £8-95 (62p)  
**AMPLIFIER KITS** PZ20 power supply kit for above £4-10 (6p)

**SINCLAIR CALCULATORS**



Sinclair Scientific Assembled £16-95 (£1-70)  
 Cambridge Assembled £10-50 (£1-20)  
 Cambridge Memory Assembled £14-95 (£1-60)

**FERRANTI ZN414**

IC radio chip with data £1-20 (25p). Also available kit of extra parts to complete a radio £2-55 (47p). Send see for free leaflet.

**SINCLAIR PROJECT 80**

AFU £6-38 (78p)  
 Z40 £5-12 (88p)  
 Z50 £4-38 (78p)  
 Q16 £7-21 (95p)  
 P25 £5-11 (73p)  
 P26 £7-79 (94p)  
 P28 £7-36 (90p)  
 Decoder £7-75 (89p). Trans for P28 £3-85 (70p)  
 Tuner £11-62 (£1-42). Stereo 80 £11-62 (£1-42).  
 Project 80S £29-95 (£3-00).  
 Project 80SSQ £33-95 (£3-30)  
 Project 80 SQ Quad Decoder £15-95 (£1-28)



**ECONOMICAL QUADRAPHONICS**

Introducing the Napulex QA10 self contained matrix quadraphonic synthesizer. Just feed the output of any stereo system (including Project 80 or 80) into it and hook on 4 speakers to obtain the latest experience in sound. Send see for free leaflet. Only £10-15 (£1-10).



**SINCLAIR SUPER IC12**

6 Watt IC power amp and preamp. With 44 page booklet and printed circuit £1-80 (43p).



**DELUXE KIT FOR THE IC12**

Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1-80 (31p). Stereo model with balance control £3-90 (49p).

**IC12 POWER KIT**

Supplies 28V 0-5 Amps £3-07 (62p).

**LOUDSPEAKERS FOR THE IC12**

5" 8 ohm £1-40 (44p). 5" x 8" 8 ohm £1-75 (57p).

**PREAMP KITS FOR THE IC12**

Type 1 for magnetic pickups, mics and tuners. Mono model £1-50 (30p). Stereo model £2-70 (36p). Type 2 for ceramic or crystal pickups. Mono 88p (23p). Stereo £1-60 (30p).

SEND SAE FOR FREE LEAFLET ON KITS

**BATTERY ELIMINATOR BARGAINS**

The most versatile battery eliminator ever offered. Switched output of 3, 4, 6, 7, 9 and 12V at 500 mA £3-90 (80p).



Other eliminators stocked—  
 250mA:—3 way switched model giving 6, 7, and 9V £2-50 (65p).

50mA:— 4 1/2V £2-40 (40p). 6V £2-40 (40p). 9V £2-40 (40p). 7 1/2V cassette type £2-80 (50p). Double 4 1/2V + 4 1/2V £2-95 (50p). 8V + 6V £2-95 (50p). 9V + 9V £2-95 (50p).

500mA:— Heavy duty deluxe models 6V £2-78 (65p). 7 1/2V £2-78 (65p). 9V £2-78 (65p).

**S-DECS AND T-DECS**

S-DeC £1-88 (36p)  
 T-DeC £3-63 (52p)  
 μ-DeC A £3-99 (56p)  
 μ-DeC B £6-99 (86p)  
 IC carriers:—  
 16 dill: plain 81p (18p)  
 with socket £1-77 (28p)  
 10 TO5: plain 78p (18p). With socket £1-68 (27p).



**SWANLEY ELECTRONICS**  
 PO BOX 68, SWANLEY,  
 KENT BR8 8TQ.

Please add the sum shown in brackets after the price to cover the cost of post and new VAT. Official credit orders from schools etc. welcome. No VAT charged on overseas orders.

**TRANSISTORS (p. & p. 8p.)**  
 All new and full spec.  
 BC107/8/9, BC147/8/9, BC157/8/9 all 9p  
 BF180 25p, BF182/3 40p, BF184 17p,  
 BF187 13p, BFW10 55p, 741 8DIL 34p,  
 BF336 35p, 2N3771 £1-10, 2N3441 50p,  
 BD131 40p, 2N3055 45p, NE555 67p.


**EX COMPUTER PC PANELS**  
 4 x 2in packed with semiconductors and top quality resistors, capacitors, diodes etc. Guaranteed min. 35 transistors, plus data 25 boards £1 (30p)

**ELECTROLYTICS**  
 2,200μ 63v 35p (8p)  
 2,000μ 50v with clip 35p (8p)  
 4,700μ 63v 50p (12p)  
 15,000μ 30v, 68,000μ 16v 65p (22p)  
 30,000μ 25v 65p (22p)  
 4,000μ 70v, 3,600μ 40v 4 x 2" 55p (15p)  
 5,000μ 35v 40p (12p)  
 20A 100 piv Si recs 4 for £1 (12p)  
 3A 100 piv Si recs 4 for 50p (8p)  
 250 mixed resistors 60p (13p)  
 250 mixed capacitors 60p (11p)  
 150 mixed HI-STABS 60p (11p)  
 200 Si planar diodes 60p (8p)  
 QH bulbs 12v 55w 50p (7p)  
 2N3055 EQUIV 4 for £1 (10)

**SMALL ELECTROLYTICS**  
 2-2μ 10/16v, 10μ 35v, 50μ 40v, 100μ 40v,  
 100μ 6v, 150μ 10v, 64μ 10v 12 for 45p.

**PRESETS 100mW**  
 220Ω 470Ω 1k 4k7 10k 100k 12 for 50p.  
 Postage and packing shown in brackets  
 ADD 8% VAT to TOTAL

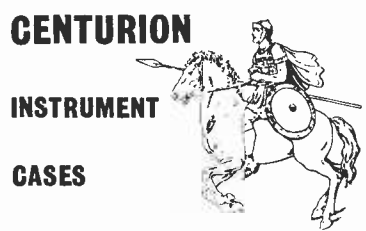**KEYTRONICS**  
 (Mail Order only)  
 44 EARLS COURT ROAD  
 LONDON W8. 01-478 8499



Model Nos. 119 and 121 two part aluminium construction base front and back unit finished in white gloss, hooded cover finished in blue hammer stove enamel.

Model D W H  
 119 152mm 127mm 89mm £1-60 ea  
 121 152mm 203mm 76mm £2-00 ea

Model Nos. 221F and 222F flat packs. Front & Rear panels aluminium case mild steel front panel finished in white gloss other parts finished in blue hammer stove enamel.

221F 152mm 203mm 152mm £2-80 ea  
 222F 197mm 254mm 159mm £3-40 ea

Prices include P & P U.K.  
 Add 8% V.A.T. U.K. only.  
 Send S.A.E. for full range brochure.

Manufactured by  
**Arbours Electronics Limited**  
 Unit 13 East Hanningfield Ind. Est.  
 Nr. Chelmsford, Essex CM3 5BG  
 Tel. Chelmsford (0245) 400700.  
 Sheet metal work wiring assembly service available

**8 PIN DIL 741's**  
 Full spec of course  
 10+ 26p 100+ 21p  
 25+ 23p 250+ 20p  
**555 TIMERS**  
 3+ 60p 25+ 46p  
 10+ 50p 100+ 43p

**PC ETCHING KIT**  
 Contains 1lb Ferric Chloride, 100 sq ins copper clad board, DALO etch resist pan, abrasive cleaner, etching dish and instructions, £3-30.

**FERRIC CHLORIDE**  
 Anhydrous to Mil-spec in 1lb double sealed packs. 1lb 90p, 3lbs £1-80; 10lbs £4-65.

**COMPUTER PANELS**  
 Large quantity always available. 3lbs assorted £1-60, 7lbs £2-85, 56lbs £35.  
 12 High quality panels with IC's, Trim pots, Power Transistors, etc. £2-65.  
 Pack with 50 14 pin DIL DTL IC's £1-20. Pack with 20 multi-turn trim pots + other parts £1-10. Pack with 51A 200V SCR's + 60 other parts 60p.

Price increases, which we regret, are due to higher postal, packaging and advertising costs. Prices include 8% VAT and inland postage. SAE list. Components, and equipment always wanted for cash.

**GREENWELD ELECTRONICS (PW4)**  
 Mail order dept., retail/wholesale shop  
 51 SHIRLEY PARK ROAD, SOUTHAMPTON SO1 4PX. Tel. (0783) 772501  
 Also callers welcome at 21 Deptford Broadway SE8. Tel. 01-692 2009 and 38 Lower Addiscombe Road, Croydon. Tel. 01-688 2950.

**VEROBOARD**  
 Approx. 8 pieces, total 100 sq. ins. assorted sizes and pitches £1-15.

**CAPACITORS**  
 200 Mica, ceramic, poly, etc. £1 15000 £42. 15 diff. trimmers, air-spaced and compression up to 1250pF. Only £1.

**71b BARGAIN PARCELS**  
 Hundreds of new components—resistors, capacitors, pots, switches + PC boards with transistors and diodes, also loads of odds and ends. Contents always changing as new stocks arrive £2-60.

**TRANSFORMERS**  
 All mains primary, 6-0-6V @ 100mA 85p; 9-0-9V @ 100mA 90p; 12-0-12V @ 100mA 95p; 24-0-24V @ 500mA £2. Ex-equip: 22j-0-22jV @ 1A £2-10; 12V @ 15A £3-75; 18V @ 5A £3-40; 55V @ 5A £4-50.

**HEAT SINKS**  
 6 x 5 x 3" finned aluminium, with 2xOC29 or 2xOC35. Only £1-20.

**POWER SUPPLIES**  
 G101: Mains transformer, 2A thermal cut-out, bridge rect. Will give 1-7V-10-5V output with 2 extra capacitors (provided). With data £1-30.  
 G102: Stabilised supply giving 7 1/2V @ 225mA (can be altered by changing zener). Not tested, probable minor fault. With circuit £1-10.  
 G104: Ex-LEO III. Contains 55V 5A transformer, 6 x 5 x 3" heat sink with 2xOC35, Stabiliser panel, 4x1000μF 63V caps, 1x4700μF 100V cap, etc. £12-50.

**MICROPHONES**  
 V996 Dynamic microphone, 50k Impedance, on/off switch, heavy desk stand. Very smart appearance £3-30. Crystal microphone insert 1 1/2" dia. 35p.

# ULTRON COMPONENTS

35 PARK AVENUE, POTTERS BAR, HERTS. 01-882 4355

MAIL ORDER ONLY

CASH WITH ORDER,  
OR PHONE US

DISCOUNTS:-15% off for 12 + 20% off for 50 + 25% off for 100 +

COMPARE THESE PRICES—  
ALL INCLUSIVE OF V.A.T.

Add 10p p & p for  
orders under £2.00

ALL TOP BRANDED MAKES, AND GUARANTEED

AC126	18p	BCY42	27p	MJE3055	85p	2N2907A	18p	OCP71	75p
AC127	18p	BCY43	25p	MPP102	30p	2N2925	14p	ZTX107	8p
AC128	18p	BCY58	16p	2N697	14p	2N2926	9p	PL4005	10p
AC164	19p	BCY59	16p	2N698	28p	2N3053	18p	R.C.A.	
AC187	12p	BF184	16p	2N699	30p	2N3054	42p	40309	30p
AC188	12p	BF177	27p	2N706A	11p	2N3055	44p	40310	48p
ACY17	25p	BF182	30p	2N708	13p	2N3056	25p	40311	32p
ACY20	18p	BF183	35p	2N914	18p	2N3440	50p	40312	50p
ACY21	20p	BF185	20p	2N916	24p	2N3625	80p	40314	32p
ACY22	16p	BF186	20p	2N918	30p	2N3614	60p	40315	32p
ACY40	21p	BF196	11p	2N920	45p	2N3615	68p	40316	48p
ACY41	26p	BF200	31p	2N929	18p	2N3663	12p	40317	32p
ACY44	30p	BF274	18p	2N961	55p	2N3702	10p	40319	38p
AD149	45p	BFX88	19p	2N1131	20p	2N3703	10p	40320	32p
AD161	35p	BFW89	18p	2N1132	20p	2N3704	11p	28926	80p
AD162	35p	BFW91	17p	2N1302	16p	2N3705	10p	TIP33C	
AF114	18p	BFX29	25p	2N1303	16p	2N3707	10p	TIP35	£2.00
AF117	13p	BFX28	30p	2N1304	15p	2N3708	6p	TIP36C	£3.80
AF125	24p	BFX85	25p	2N1305	23p	2N3709	7p	Stud diodes	
AF139	32p	BFX87	22p	2N1306	23p	2N3710	11p	6 Amp	28p
AF178	40p	BFX88	21p	2N1307	23p	2N3711	11p	18p Am	45p
BC107	10p	BFY11	20p	2N1308	27p	2N3730	90p	Bridges	
BC107B	10p	BFY18	47p	2N1309	27p	2N3771	£1.10	Rectifiers	
BC108	10p	BFY19	54p	2N1671	90p	2N3773	£2.25	1A, 50V	24p
BC109	10p	BFY59	19p	2N1671A	95p	2N3791	£2.25	2A, 600V	48p
BC109B	11p	BFY51	18p	2N1671B	£1.00	2N3819	25p	4A, 200V	55p
BC113	13p	BFY64	33p	2N2160	60p	2N3866	70p	6A, 100V	65p
BC114	14p	BFY99	72p	2N2217	21p	2N3903	14p	S.C.R.s	
BC115	13p	BSW70	15p	2N2218	20p	2N3904	14p	1/05	30p
BC116	13p	BSX28	22p	2N2220	18p	2N3905	15p	1/10	26p
BC116A	14p	BSX67	28p	2N2297	27p	2N3906	15p	1/20	40p
BC117	13p	BY127	11p	2N2303	75p	2N4061	12p	16/400	80p
BC118	10p	BU105	£1.00	2N2369	13p	2N4458	27p	16/600	£1.20
BC119	22p	MFP103	35p	2N2389A	15p	O A81	15p	Triacs	
BC134	12p	MJ480	75p	2N2411	50p	O A91	4p	8C40D	£1.05
BC136	16p	MJ481	85p	2N2646	44p	OC20	£1.08	8C45D	£1.30
BC137	16p	MJ490	85p	2N2846	70p	OC28	58p	8C45E	£1.45
BC138	16p	MJE371	60p	2N2884	35p	OC29	50p	8C50D	£1.50
BC153	17p	MJE2501		2N2904A	45p	OC35	48p	I.C.s	
BC154	17p	MFP103	£1.15	2N2905	22p	OC36	50p	741	30p
BC167B	12p	MJE2955		2N2906	14p	OC71	30p	1310	£2.40
BC183L	10p		£1.00	2N2906A	19p	OC83	20p		

AND MANY, MANY MORE

# SCIENTRONICS

## greet constructors with EXCLUSIVE INTRODUCTORY MONEY-SAVING OFFERS

SCIENTRONICS is a new company organised to develop and promote electronic designs of especial interest to constructors. We are privileged to offer, as our opening shot, a substantial quantity of selected items no longer part of the manufacturing programme of a famous manufacture. These include transistors by Ferranti, Texas, ITT and others made to stringent specifications, e.g., E 5401 with a guaranteed gain at 1 micro amp. All these transistors are brand new and guaranteed within the terms of our published specifications. S.A.E. brings full list by return. Leads on components are untrimmed.

### TRANSISTORS

GENERAL PURPOSE	NPN (N)	PNP (P)	ONE OFF PRICE in p	VCE	HFE Min.	mA
FRB 77	P	N	7.5	*50	100	1
E 5368A	N	N	7.5	25	100	1
E 5368B	N	N	7.5	25	150	1
E 5368C	N	N	8	25	250	1
E 5369	P	P	7.5	20	70	1
<b>LOW LEVEL</b>						
E 5401	P	P	7.5	*30	50	1µA
E 5403	P	P	7.5	*30	100	10µA
E 5404	P	P	7.5	*30	100	100µA
E 5405	P	P	7.5	*30	100	100µA

### DRIVERS & SWITCHING (tested for low Vce (sec))

FRB 772	P	N	8	40	40	
E 5370	N	N	5	20	15	500
E 5398	P	P	8	40	100	10
E 5397	P	P	8	20	100	100

### HIGH FREQUENCY (600 MHz FT)

E 5399	N	N	7.5	30	20	3
E 5400	N	N	8	10	10	1
XK 6116	N	N	8	20	10	1
<b>HIGH VOLTAGE</b>						
E 5407	P	P	9	65	50	10
E 5408	N	N	7.5	65	50	10

### QUANTITY DISCOUNTS (prices in pence per device)

Single	10	100	1000
5	4.5	3.6	3.0
7	7.0	5.5	4.5
7.5	7.2	5.6	4.6
8	7.4	5.7	4.9
9	7.8	6.5	5.5

\* Intended for 10V working guaranteed, but almost all would pass for higher voltage operation as indicated—most can be selected for higher voltage working at an extra charge of 1/2p per device.

### RESISTORS

Most values in E.12 series are available in 5% or 10% tolerances.

Miniature types (1/8 - 1/2 watt). Quantity rates apply for orders of same value.

0.8p each: 10 of same value 7p  
100 - 55p: 1000 £4.50

### CAPACITORS CERAMICS

1.1p to 2p each in a range of useful values. 10p to 18p for 10; 77p to £1.45 for 100; £6.25 to £11.75 for 1000

**ELECTROLYLIC** 10-50v; 1 to 220mF from 3p each; 27p for 10; £2.20 for 100; £17.25 for 1000.

NIXIE DISPLAYS/SWITCHES/TRANSFORMERS/KNOBS/NUTS/BOLTS, etc.—Send S.A.E. for full lists and prices—REAL MONEY SAVERS THESE.

**ENQUIRIES: TRADE & BULK BUYERS INVITED. SPECIAL QUANTITY DISCOUNTS.**

### ORDERING & GUARANTEE

All goods guaranteed within terms of specification and in stock at time of going to press. Send cheque or money order with order, or if cash, send reg. post. Please state requirements clearly. Satisfaction guaranteed or your money refunded. MIN. ORDER . . . . £1.00

All goods sent post paid in U.K. Overseas postage charged at cost. V.A.T.—Add 8% to total value of order in U.K.

## SCIENTRONICS

(Dept. P.W.4)  
40 HIGH STREET, SOMERSHAM,  
HUNTINGDON, CAMBS PE17 3JA.  
Telephone Somersham (04874) 321



## become a RADIO-AMATEUR!

learn how to become a radio-amateur  
in contact with the whole world. We give  
skilled preparation for the G.P.O. licence

**free!** Brochure, without obligation to:

**BRITISH NATIONAL RADIO & ELECTRONICS  
SCHOOL** Dept. w.b. 45, P.O. Box 156, JERSEY

NAME : \_\_\_\_\_  
ADDRESS : \_\_\_\_\_

BLOCK CAPS please



# Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 12p per word (minimum 12 words), box number 30p extra. Semi-displayed setting £10.00 per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd. Fleetway House, Farringdon Street, London, EC4A 4AD for insertion in the next available issue.

## Receivers and Components

**MULLARD 10W RMS AMPLIFIER MODULES.** Absolutely complete. £2.65 inclusive. LTE, 46 Minehead Road, South Harrow, Middx.

250mA. Cartridge Fuses 1½" 90p per 100. Unused Carbon Resistors. 100 different 50p. Unused W/W Resistors. 100 assorted £1.10. 100 Capacitor Mixture, 85p. 1lb. 8 to 2BA. Nut & Bolt mixture 28p. Brass 33p. 18 Assorted Potentiometers Unused £1.15 Ex Government Standard Jack Plugs 4 for 50p 6 volt 3s or 18 watt Bulbs. SBC, 70p per doz. Earphones Ex Govt. 85p per pair. New Meter or Cassette Cases, stiff imitation leather 6" x 3½" x 4". Only 55p. Ex T.V. Speakers. Perfect 3Ω elliptical 55p. 0-300mA Meters New. £1.75p. 7 Tape Spools 16p each. All postage in U.K. included in price

**SOUND SYSTEMS OF SUFFOLK**  
678 Foxhall Rd., Ipswich, Suffolk IP3 8NQ

**INFLATION? PRICE INCREASES?**  
ATES SGS 7 WATT IC TBA810AS only 99p. Send £1.98, post 20p, for two. Data included. PC Boards 55p each. Post 10p. Watson, c/o 131 Buxton Street, London E1.

## Precision Polycarbonate Capacitors

All High Stability—Extremely Low Leakage

440V AC (±10%)	63V Range	±1%	±2%	±5%
0.1µF (1½" x ½")	80p	0.47µF	50p	48p
0.22µF (1½" x ½")	80p	1.0µF	60p	56p
0.47µF (1½" x ½")	80p	2.2µF	80p	65p
0.8µF (1½" x ½")	80p	4.7µF	£1.30	£1.05
0.8µF (2" x ½")	80p	8.2µF	£1.94	£1.25
1.0µF (2" x ½")	80p	10.0µF	£2.00	£1.40
2.0µF (2" x ½")	80p	15.0µF	£2.75	£2.15

**TANTALUM BEAD CAPACITORS**—Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 15V/25V or 35V; 10.0µF at 15V/20V or 25V; 22.0µF at 6V/10V or 15V; 33.0µF at 6V or 10V; 47.0µF at 3V or 6V; 100.0µF at 3V. ALL at 10p each, 10 for 95p, 50 for £4.

**TRANSISTORS:** BC183/183L 11p BFX80 20p  
BC107/8/9 9p BC184/184L 18p BFY51 30p  
BC114 12p BC213/212L 14p BFX52 20p  
BC147/8/9 10p BC547/558A 12p AF178 80p  
BC125/7/8 15p BF194 15p OC71 15p  
BC182/182L 11p BF197 15p 2N3055 60p

**POPULAR DIODES**—1N914 6p, 8 for 45p, 18 for 80p; 1N916 8p, 6 for 45p, 14 for 80p; 1844 5p, 11 for 50p, 24 for £1.00. 1N4148 6p, 6 for 27p, 12 for 45p; 1N4001 8p; 002 6p; 003 6p; 004 7p; 005 7p; 006 8p; 007 8p.

**LOW PRICE ZENER DIODES**—400mW, Tol. ±5% at 5mA. Values available: 3V, 3.3V, 3.6V, 4.7V, 5.1V, 5.6V, 6.2V, 6.8V, 7.5V, 8.2V, 9.1V, 10V, 11V, 12V, 13V, 13.5V, 15V, 16V, 18V, 20V, 22V, 24V, 27V, 30V, 33V. All at 7p each, 6 for 89p, 14 for 84p. SPECIAL OFFER: 100 Zeners for £5.50.

**RESISTORS**—High stability, low noise carbon film 5%, ¼W at 40°C, ¼W at 70°C. E12 series only— from 2-2Ω to 2-2MΩ. ALL at 1p each, 8p for 10 of any one value, 70p for 100 of any one value. SPECIAL PACK: 10 of each value 2-2Ω to 2-2MΩ (730 resistors) 45p.

**SILICON PLASTIC RECTIFIERS**—1.5 amp, brand new winded DO27; 100 P.I.V. 7p (4 for 28p); 400 P.I.V. 8p (4 for 28p).

**BRIDGE RECTIFIERS**—2½ amp: 200V 40p; 350V 45p; 600V 55p.

**SUBMINIATURE VERTICAL PRESETS**—0.1W only: £1.1 at 5p each: 50Ω, 100Ω, 220Ω, 470Ω, 680Ω, 1kΩ, 2.2kΩ, 4.7kΩ, 8.2kΩ, 10kΩ, 15kΩ, 22kΩ, 47kΩ, 100kΩ, 250kΩ, 680kΩ, 1MΩ, 2.5MΩ, 5MΩ.

PLEASE ADD 10p POST AND PACKING ON ALL ORDERS BELOW £5. ALL EXPORT ORDERS ADD COST OF BR/MAIL.

PLEASE ADD 8% V.A.T. TO ORDERS. Send S.A.E. for lists of additional ex-stock items. Wholesale price lists available to bona fide companies.

**MARCO TRADING (Dept. W4)**  
The Old School, Edstaston, Nr. Wem, Shropshire.  
Tel: Whixall 464/465 (STD 094 878)  
(Proprs. Minicost Trading Ltd.)

**COMPONENTS GALORE.** Pack of 500 mixed components manufacturers surplus plus once used. Pack includes resistors, carbon and W.W., capacitors various, transistors, diodes, trimmers, potentiometers etc. Send £1+10p p&p. C.W.O. To: Caledonian Components, Strathore Road, Thornton, Fife.

**ALLARD ELECTRONICS**  
Branded Components—Full Specification

TRANSISTORS	T.T.L's	T.T.L's Price ea.
BC212/3/4 0-11	74001/1/2/3 0-14	7486 0-37
BC167/159 0-18	7404/5 0-18	7489 0-55
BC158 0-11	74017 0-38	7411AN 0-98
TIP29a 0-49	7408 0-20	74119 1-68
TIP30a 0-57	7409 0-24	74154 1-68
TIP31a 0-61	7416/7 0-37	74191/2/3 1-20
TIP32a 0-74	7423/5/7 0-37	74196/7 1-80
TIP41a 0-68	7428 0-38	
TIP42a 0-90	7429/33 0-38	
I.C.'s		
709C (DIL or TO)	7441/2 AN 0-75	
723C (DIL or TO)	7470/72 0-87	
741C TO 0-76	7473/74 0-86	
741C DIL 0-32	7475 0-54	
748C TO 0-44	7480 0-60	
748C DIL 0-40	7482 0-85	
LM309K 3-00	7483 1-10	
NE555 0-95	7484 0-95	
2N414 1-10		
TBA800 1-35		

**POTENTIOMETERS—CARBON TRACK**  
LIN. OR LOG. 1" BUSH—  
SPINDLE 2" F.M.F. 0-16 ea.  
5K to 2 Meg Single .. with D/P sw 0-16 ea.  
5K to 2 Meg .. with D/P sw 0-22 ea.  
5K to 2 Meg Dual .. D/P sw 0-22 ea.  
5K to 2 Meg .. D/P sw 0-22 ea.

**FREE LIST**  
Over 1,500 semi-conductor types plus other components. S.A.E. please.

**299/301 BALLARDS LANE**  
LONDON N12 8NP 01-445-5188  
MAIL ORDER ONLY. Cash with order  
Orders under £3 plus 15p P & P. Add VAT to total

**LEDs.** Red, green, yellow. Sizes: 0.1in, 0.125in, 0.16in, 0.2in. Mixed bags all sizes and colours. 50—£5, 100—£9 including postage, VAT, C.W.O. Individual types and larger quantities by negotiation. Industrial Electronic Supplies (Stockport) Ltd., 181a Bramhall Lane, Davenport, Stockport, Cheshire.

**BETA DEVICES**  
FOR BETTER PRICES

TRANSISTORS	DIODES & BEST	BRIDGE BEST
AC187/8 PR 0-40	1N914 0-04	1A 100v 0-20
BC107/8/9 0-09	1N4148 0-04	1A 200v 0-22
BC109C 0-11	BY127 0-14	1A 600v 0-80
BC147/8 0-10	1N4001/2 0-05	25A 200v £2.00
BCY70/71/72D 13	1N4003/4/5 0-06	ZENERS
BFX88 0-80	1N4006/7 0-08	BZY88e 3-3-
BFX50 0-18	1N5401 0-11	35p 5%, 0-09
BFX51/52 0-18		1 watt 6.8-
2N1132 0-25	7 SEG DISPLAYS	200V 5% 0-15
2N1711 0-25	3015F £1.00	L.E.D.
2N2646 0-30	DL707-LEDE1-70	209-RED 0-17
2N2906A 0-21	DL747-LEDE4-45	LED CLIP 0-02
2N3055 0-14		QB, AMP, 10%
2N3056 0-35		
TIP29A 0-49	D.I.L. SOCKETS	709C/7099 0-30
TIP30A 0-57	8 Pin 0-12	709C D.I.L. 0-30
TIP31A 0-61	14 Pin 0-12	741C TO99 0-36
TIP32A 0-74	16 Pin 0-14	741C D.I.L. 0-88
TIP41A 0-74		723C D.I.L. 0-88
TIP42A 0-90		747C D.I.L. 0-85
		748C D.I.L. 0-36

**V.A.T. INC.**

7400N 0-16	74 SERIES T.T.L.	7474N 0-87
7401N 0-18	7420N 0-18	7480N 0-88
7402N 0-18	7427N 0-28	7492N 0-63
7404N 0-19	7430N 0-18	7493N 0-82
7408N 0-23	7440N 0-18	7421N 0-50
7410N 0-18	7447N £1.00	74122N 0-70
7413N 0-39	7472N 0-32	74123N £1.25
		74141N £1.13

**C.W.O. PLUS P.P. 15p TO BETA DEVICES.**  
263 THE RIDGEWAY, ENFIELD, MIDDIX.

**NEW COMPONENTS** post free, 8% VAT included. 2N3702, 2N3704, 9p. Guest UPM 050 ½ W Carbon Film resistors 1p each. Seven segment common anode LED displays, 0.3in. DL707 £1.90, 0.6in DL747 £2.38. Siemens B32540 250V Polycarbonate 0.01, 0.015, 0.022, 0.033, 0.047, 4p; 0.068, 0.1µF, 5p. Triac TAG 250 400V/8A, 75p. D32 diac 25p. 300W Light Dimmer, £2.75. Delivery from stock or your money returned. Greenbank Electronics, 94 New Chester Road, Wirral, Merseyside L62 5AG.

**NEW MODEL V.H.F. KIT MK2**  
Our latest kit. Improved design and performance plus extra amplifier stage, receives aircraft, amateurs, mobile, radio 2, 3, 4, etc., this novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 volt battery, complete with easy to follow instruction and built in jack socket for use with earphones or amplifier.  
Only £4.50 + p&p 30p U.K. only.  
Illustrated catalogue of selected kits and components, 35p inc. VAT. P&P free.

**ALL PRICES PLUS 8% VAT**  
Galleon Trading Co.  
12, Burrs Way,  
Corringham,  
Stanford-Le-Hope,  
Essex. SS17 9DE

**BRAND NEW COMPONENTS** by return. Electrolytics, 15V, 25V, 50V 0.47, 1, 2, 4, 7, 10 Mfd.—4p. 22, 47—4½p (50V—5p). 100—5½p (50V—7p). 220—6p (50V—9p). Subminiature bead-type tantalums 0.1/35V, 0.22/35V, 0.47/35V, 1/35V, 2.2/35V, 4.7/35V, 10/16V, 22/16V, 47/6V, 100/3V—9p. Mylar Film 100V 0.001, 0.002, 0.005, 0.01, 0.02—2½p. 0.04, 0.05—3p. Mullard Tubular Polyester 40V E6 series, 0.001-0.022—3p. 0.033-0.1—4p. Mullard miniature C333 ceramics E.12 series 2% 1.8pf-47pf.—2½p. 56pf-330pf.—3p. Polystyrene 63V. E12 series 10pf-1,000pf.—2½p. 1,200pf-10,000pf.—3½p. Miniature Highstab Carbon Film Resistors ½ W E12 series 5% 1Ω-10MΩ (10% over 1 Megohm)—1p. Postage 8p. Prices VAT inclusive. The C.R. Supply Co., 127 Chesterfield Road, Sheffield S8.

**TAPE HEADS**  
Send stamp for lists.  
**R.D.I. Ltd.**  
Chilton Works,  
Garden Rd.,  
Richmond,  
Surrey,  
TW9 4NS

For valve and transistorized recorders from £2 ea.

**MULTI-BAND RADIOS.** Grundig Satellit, 13 band, £129; Koyo, marine, aircraft, PSB, FM, SW1, SW2, MW, LW, batt/mains, £44; 4-band, MW, FM, aircraft, PSB, £14. SAE lists. Langtons Radio, High Street, Rocester, Staffordshire. 088 923 388.

**Ladders**  
LADDERS, timber and aluminium. Tel: Telford 586644 for brochure.

## Situations Vacant

**MEN!  
£70p.w.  
can be yours**

Jobs galore? Tens of thousands of new computer personnel needed over the next few years alone. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £3500 + p.a.

London Computer Operators Training Centre subscribes to the British Government backed National Computing Centre code of practice for Computer Training Schools so you know your training will be second to none.

After training, our executive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or phone TODAY, without obligation.

**London Computer Operators  
Training Centre**

Y22, Oxford Hse.,

9-15 Oxford St. W1. Tel: 01-734 2874

## Service Sheets

**SERVICE SHEETS, Radio, TV etc.,** 8,000 models. Catalogue 20p. S.A.E. enquiries. Telray, 11 Maudland Bank, Preston.

## LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS,  
RECORD PLAYERS, TRANSISTORS,  
STEREOGRAMS, RADIOGRAMS,  
CAR RADIOS)  
ALL AT 50p EACH

**"PLEASE ENCLOSE LARGE S.A.E  
WITH ALL ENQUIRIES & ORDERS"**

Otherwise cannot be attended to  
(Uncrossed P.O.'s please, original  
returned if service sheets not available.)

### PLEASE NOTE

We operate a "by return of post" service. Any claims for non-delivery should be made within 7-days of posting your order.

## C. CARANNA

71 BEAUFORT PARK  
LONDON, N.W.11 6BX

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.

Free TV fault tracing chart or TV list on request with order.

Mail order or phone 01-458 4882

**BELL'S TELEVISION SERVICES** for Service Sheets, Manuals, Books on Radios, TVs, etc. Service Sheets 50p plus SAE. Free booklists on request. Back issues of PW, PE, EE, TV available 25p plus 9p post. SAE with enquiries.—BTS (Mail Order Dept.), 190 Kings Road, Harrogate, Yorks. Telephone (0423) 55885.

## Educational

**GO TO SEA** as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

## TELEVISION TRAINING

**16 MONTHS'** full-time practical and theoretical training course in Radio and TV Servicing (Mono and Colour) for beginners.

**13 WEEKS'** full-time Colour TV Servicing course. Includes 100 hours practical training. Mono revision if necessary. Good electronics background essential.

NEXT SESSION commences on April 21st.

Prospectus from: **London Electronics College, Department B4, 20 Penywern Road, London SW5 9SU. Tel. 01-373 8721.**

## C AND G EXAMS

Make sure you succeed with an ICS home study course for C and G Electrical Installation Work & Technicians Radio/TV/Electronics Technicians. Telecomms Technicians and Radio Amateurs.

## COLOUR TV SERVICING

Make the most of the current boom! Learn the techniques of servicing Colour and Mono TV sets through new home study courses, approved by leading manufacturers.

## TECHNICAL TRAINING

Home study courses in Electronics and Electrical Engineering, Maintenance, Radio, TV, Audio, Computer Engineering and Programming. Also self-build radio kits. Get the qualifications you need to succeed.

Free details from:

**INTERNATIONAL  
CORRESPONDENCE SCHOOLS,**  
Dept 732, Intertext House, London SW8 4UJ.  
Or Phone 01-622 9911 (All Hours)

## Aerials

### J. and A. TWEEDY (Electronic Supplies) Limited

Full range of Jaybeam Aerials available  
We supply High Gain Multibeam aerials. Carriage and VAT included in the quoted price.  
**MULTIBEAM UHF TV AERIALS** MBM 28 £25-00,  
MBM 48 £8-00, MBM 70 £11-00.  
**PARABEAM UHF TV AERIALS** PBM 12 £4-00,  
PBM 18 £5-00.  
**STEREOBEAMS FM AERIALS** SBM 2 £3-00,  
SBM 3 £4-00, SBM 5 £5-00, SBM 6 £8-00.  
SAE for full list of accessories available—Low Loss Co-ax 12p/m.  
78 Chatsworth Road, Chesterfield, Derbyshire  
Tel: 34982

## For Sale

PW, WW, HI-FI NEWS, Radio Constr., etc. 1950-70. 450 mags. Mostly complete volumes. Birmingham, Box No. 122.

**SELLING COMPLETE:** Volumes Practical Wireless between 1953 and 1969. Offers. SAE please. Box 123.

HRO-MX, twelve coils, power unit, "O" multiplier; £45. Mitchell, Tel: 0484 842777 (Yorkshire).

**SOUNDLIGHT CONVERTORS.** 3 channel 1.5 kW £17; 3kW £25; 1 channel 1kW £9. STROBES: from £21. SEQUENCERS (Chasers): £93, etc. Call or catalogue sent. Aarvak Electronics, 98A (P), West Green Road (side door), London N15 5NS. Tel. 01-800 8656.

**THYRISTORS,** BT106, branded products, 95p each. Tantalum Bead Capacitors IMFD 35V, 22MFD 16V 12p each. Prices are exclusive of VAT. CWO plus p.p. 10p. Pace Electronics Ltd., 138 Glebe Road, Deanshanger, Milton Keynes, MK19 6NB.

### COPPER CLAD LAMINATE FOR PRINTED CIRCUITS

Single sided 1/16" paper base—1.0p/sq. Inch. Single sided 1/16" glass-epoxy—1.5p/sq. Inch. Any rectangular sizes cut to your requirements. Please send cash with order. Price includes postage and packing. From: **SIMTECH ENGINEERING LTD VOLUNTARY PLACE WANSTEAD LONDON E.11. 01-530-4246.**

**MICROPHONES:** AKG D109, £12-65; AKG D202EI, £43-45; AKG D190C, £18-70; AKG D190E, £20; AKG D224 £55; Sennheiser MD211N, £49-50; Sennheiser MD413N, £29-70. All brand new and boxed. Send CWO to J. J. Francis, (Wood Green) Ltd., Manwood House, Matching Green, Harlow, Essex. Tel: Matching 476.

**GREENBANK ELECTRONICS.** New components. Digital Clock chip AY-5-1224 + data £3-66, data alone 16p (refundable on order). DL747 0-6in "Jumbo" LED display now only £2-04. 1/2 W Carbon Film Resistors 4.7 ohm to 4.7 Meg 1p each. Triac TAG 250-400 8A, 69p. D32 diac 23p. IN914/4148 3p. 2N3702/3704 9p. Post free, add standard VAT. 94 New Chester Road, Wirral, Merseyside L62 5AG.

## Wanted

AVO. 7 & 8 any condition. Any quantity. Huggett's, 2 Pawsons Road, W. Croydon.

**EARLY WIRELESS** receivers, components and magazines, details to Johnson Raffles, Haverbreaks, Lancaster.

### TOP PRICES PAID FOR NEW VALVES and TRANSISTORS

popular T.V. and Radio types.

**KENSINGTON SUPPLIES (C),**  
367 Kensington Street, Bradford 8,  
Yorkshire.

**WE BUY** New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S,** 55 Worcester Street, Wolverhampton.

**"RADIO & TV SERVICING"** books wanted from 1961 onwards. Any quantity. £2-00 paid per copy by return of post.—Bell's Television Services, 190 Kings Road, Harrogate, Yorkshire. Tel. (0423) 55885.

Books and Publications

# BOOKS ON ELECTRONICS

**Electronics** ..... £1.60  
—An elementary introduction for beginners (SI Units). The eagerly awaited step by step explanation for those meeting with the subject for the first time.

**Mullard Publications**

- Integrated Circuits ..... 50p
- Thyristors ..... 60p
- Magnetic Core Memories ..... 50p
- Simple Transistor Measurements ..... 30p
- Simple Valve Measurements ..... 30p
- Principles of X-Rays .. 30p
- Principles of Electrostatics ..... 30p
- A Simple Closed Circuit Television Camera ..... 90p (A Construction Manual)

(Prices include postage & packing)

**SELRAY BOOK COMPANY**  
60, Hayes Hill,  
Hayes, Bromley, BR2 7HP.

## Technical Books — Radio & Electronics

- World's Radio & TV Stations (International Edit).....£0.68
- Audio Amplifiers ..... £0.70
- Boys Book of Crystal Sets & Simple Circuits ..... £1.15
- Television Timebase Circuits ..... £0.68
- Radio TV and Industrial Tube & Valve Equip ..... £0.68
- How to get the best out of your Tape Recorder ..... £1.67
- Modern Electronic Troubleshooting ..... £1.55
- Jack Darr's Service Clinic ..... £1.55
- Transistor Circuits for Modern Test Equipment ..... £0.68
- Rad & Electr Colour Codes and Data Chart ..... £0.20
- Handbk of Transistor Equip and Substitutes ..... £0.48
- Hi Fi, PA & Disco Amplifier Design Hndbk ..... £0.87
- Radio Servicing Problems ..... £0.75
- Electronic Circuits for the Amet Photographer ..... £0.40
- Handbook of Simple Transistor Circuits ..... £1.10
- TV Fault Finding ..... £0.60
- Sound and Loudspeaker Manual ..... £2.80
- TV Technicians Bench Manual ..... £0.85
- Radio Amateur Operator's Handbook ..... £1.00
- Television Servicing Vol. No. 1 ..... £1.27
- Television Servicing Vol. No. 2 ..... £0.75
- Television Servicing Vol. No. 3 ..... £1.00
- Radio Technicians Bench Manual ..... £3.30
- Servicing Transistor Radio Receivers ..... £0.90
- 1st Book of Hi Fi Loudspeaker Enclosures ..... £0.68
- 2nd Book of Hi Fi Loudspeaker Enclosures ..... £0.60
- Manual of Electronic Circuits for the Home ..... £0.40
- Modern Crystal Set Circuits for Beginners ..... £0.58
- Electronic Novelties for the Motorist ..... £1.07
- 2nd Book of Transistor Equip & Substitutes ..... £0.58
- Handbook of Electronic Musical Novelties ..... £0.40
- Transistorised Novelties for Hi Fi Enthusiast ..... £0.95
- Fault Location Exercises in Rad. & TV Vol.1 ..... £1.55
- Fault Location Exercises in Rad. & TV Vol.2 ..... £2.70
- Colour TV Picture Faults ..... £0.48
- Practical Transistor Novelty Circuits ..... £0.68
- Boys Book of Practical Radio & Electronics ..... £0.68
- Radio Receiver Construction using ICs & Transis ..... £0.68
- ICs & Transistor Gadgets Construction Hndbk'k ..... £0.85
- Integrated Circuits Equip & Substitutes Hbk. .... £3.30
- Audio Technicians Bench Manual ..... £3.30
- Improving your Hi-Fi ..... £2.80
- Guide to Printed Circuits ..... £5.35
- Receiving Pal Colour Television ..... £3.80
- World Radio TV Handbook 1975 ..... £3.80

All prices include Postage & Packing


**RADIO BOOK SERVICE**  
40 Elwill Way, Beckenham BR3 2RZ

Miscellaneous

**HEADPHONES:** 8 ohms. Suitable communications receivers, £3-39. Partridge Electronics Ltd., Broadstairs, Kent.

**LOW COST I.C. MOUNTING.** Lengths of 100 I.C. pin sockets, 60p (p & p 5p). Quantity rates, SAE details & sample. L.E.D. (MLED500), 20p each. (post paid). P.K.G. Electronics, "Oak Lodge", Tansley, Derbyshire.

**MINI ACCUMULATORS**



2 volt MULTI-USE Sealed Lead Acid Rechargeable Cells.  
Size L46-1.4" x 1.1" x .44" 3 for £1.85 inc. P. & P.  
Size GA2-1.7" x 1.3" x .5" 3 for £2.35 inc. P. & P.  
**GARFIELDS, 289 Rye Lane, London, S.E.15**

**HAVE YOU HAD YOUR CHIPS?** AY-5-1224 Digital Clock chip now £3-95 inc. VAT, post free. Circuit and details s.a.e. **GREENBANK ELECTRONICS** (Dept. 322), 94 New Chester Road, Wirral, Merseyside L62 5AG.

SIMPLE TO FORM  
NON-MAGNETIC RUST PROOF  
MILL FINISH

## ALUMINIUM

FLAT MINI SHEETS  
10ins. x 14ins. 20 swg (0.90mm.)

6 sheets for £2 incl P&P

OTHER SIZES AVAILABLE

For general car repairs, trims, kick plates, etc.

**BAYKIN ENGINEERING LTD.**

(Dept. PW)  
GREVILLE ROAD, BEDMINSTER,  
BRISTOL, BS3 1LL

**EX-EQUIPMENT COMPONENTS.** Indicators modifiable to aerial direction monitors, chokes, relays, switches, instruments, fuse holders, push buttons, caps, etc. SAE for list. Eldun Electronics, 16 Raven Road, Timperley, Cheshire.

**SINTEL** Add 10p P. & P. for orders under £2. Data and circuits where appropriate, supplied with orders or available separately 4p. stamp each).

3 Digit DIP LED calculator High Quality 0.3in LED 7 seg. display 95p+VAT=£1.02  
MK50250N Alarm Clock IC. £8-90+VAT=£7.45  
Send for our new simple MK50250N circuit diagrams Soldercon IC socket pins — 300 pins for £1-54+VAT=£1.62  
1,000 pins for £4-00+VAT=£4.32  
MK50250N+4xDL704 0.3in LED's £10-20+VAT=£11.01  
Complete circuits and special prices for MK50250N with LED's, Minitrans or SP352's  
**SINTEL, 53n ASTON ST, OXFORD** Tel (0865) 43203

**SUPERB INSTRUMENT CASE** by Bazelli, manufactured from heavy duty PVC faced steel. Hundreds of Radio, Electronics and Hi-Fi enthusiasts are choosing the case they require from our range of over 200 models. Generous trade discount. Fast despatch. Free literature. Bazelli, Department No. 25, St. Wilfrids, Foundry Lane, Halton, Lancaster LA2 6LT.

# FANTASTIC NEW MICROTEST 80

MEASURES ONLY

90x70x18 mm

Amazing Value at **£11.95**

8 fields of measurement and 40 ranges

- Volts D.C. 6 ranges: 100mV - 2V. - 10V. - 50V. - 200V. - 1000V. (20kΩ/V)
- Volts A.C. 5 ranges: 1.5V. - 10V. - 50V. - 250V. - 1000V. (4kΩ/V)
- Amp. D.C. 6 ranges: 50μA - 500μA - 5mA - 50mA - 500mA - 5A
- Amp. A.C. 5 ranges: 250μA - 2.5mA - 25mA - 250mA - 2.5A
- Ohms 4 ranges: LowΩ - Ω x 1 - Ω x 10 - Ω x 100 (da 1/10 diΩ fino a 5 MegaΩ)
- V Output 5 ranges: 1.5V. - 10V. - 50V. - 250V. - 1000V.
- Decibels 5 ranges: + 6dB, +22dB, +36dB, +50dB, +62dB
- Capacity 4 ranges: 25μF - 250μF - 2500μF - 25,000μF



**SUPERTESTER 680R ICE**  
20,000 Ohm per Volt/sensitivity • Fully screened against external magnetic fields • Scale width and small case dimensions (128 x 95 x 32mm) • Accuracy and stability (1% in D.C., 2% in A.C.) of indicated reading • Simply and easily used • Full range of accessories • 1000 times overload • Printed circuit board is removable without de-soldering • More ranges than any other meter. Ask for free catalogue **£18.50**

Accessories (extra) available to convert Microtest 80 & SuperTester 680R into following: SIGNAL INJECTOR, GAUSS METER, ELECTRONIC VOLTMETER, AMPER LAMP, TRANSISTOR TESTER, TEMPERATURE PROBE, PHASE SEQUENCE INDICATOR—Send for details.

## MORE RANGES FOR LESS MONEY!

- AC/DC Multimeter type U4324
- A-DC 0-0.03A - 6 Ranges.
- A-A.C 0-3-3A - 5 Ranges.
- V-DC 0-0-1200V - 9 Ranges.
- V-A.C 3-900V - 8 Ranges.
- Freq.: In the range of 45 to 20kHz.
- Resistance: 500 Ohm to 5 MOhm.
- 5 Ranges, Decibel: -10 to +12dB
- Accuracy: ± 2.5% DC. ± 4% AC
- Dimensions: 167 x 98 x 63 mm.

Only **£8.85**



## ALPHANUMERIC NIXIE TUBES B7071

The Alphanumeric NIXIE tube has the ability to display all the letters of the alphabet, numerals 0 thru 9 and special characters in a single tube. From the standpoint of both readability and electrical characteristics, the Alphanumeric NIXIE tube provides many unique benefits including ★ 170v-21mA ★ All d.c. operation ★ Uniform, continuous line characters of equal height ★ Memory with simple solid state drive circuits ★ Readability in high ambient light, ... 200 footcandle brightness ★ Long life with no loss of brightness ★ Character height 23in.



Price only **99p** each plus 16p P/P. Bases for above 80p each.

## JUST ARRIVED !!

**NUMERIC INDICATOR TUBES**  
Ultra-long life, high quality, 0-9 and 2 independent decimal points. Supply voltage 200V D.C. Current 14mA, Pulse duration 100μs. Character height 0.51, overall size 1.4. Brand new, guaranteed. Surplus to manufacturers requirements. Type B5853at 1-25 £1-00 1000 - price on application 25+ 80p  
Add 8% VAT to all items + 35p P & P  
**ELECTRONIC BROKERS LTD.**  
49-53 Pancras Road, London NW1 2QB  
Tel: 01-837 7781

**VALVES, TRANSISTORS, STYLI.** Valves 1930 to 1975. 1,500 types in stock, many obsolete. List 15p. Transistors, list 15p. Diamond styli, 83p each, list 10p. 159 TV aerial chimney lashing. Heavy duty steel £250. Buyer collect. Cox Radio (Sussex) Ltd., The Parade, East Wittering, Sussex. West Wittering 2023.

## Synthesiser "Sounds Supreme" by Dewtron (VAT extra.)

Famous kits, e.g. waa-waa complete kit £3.50; Fuzz kit £5.50. P & P 25p under £10. Ring Modulator modules £9. "Mister Bassman" Bass Pedal Units and whole range of synthesiser modules, musical novelties, etc. Catalogue 15p from D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

**PRINTED CIRCUITS.** PCB for any Practical Wireless and Practical Electronics project, 50p per board. From individual patterns £1, plus 5p per sq in. Add VAT plus 5p P & P per board. Mail order only. TEC, 241 Burnt Oak Broadway, Middlesex.

### P.W. EASY-BUILD ORGAN

SET OF TWO P.C.B.'s £7.20  
SET OF THIRTEEN MOS I.C.'s £21.85  
SET OF ALL SEMICONDUCTORS £26.70  
SET OF ALL SEMICONDUCTORS PLUS THE P.C.B.'s £32.00

ALL INCLUDE P & P AND V.A.T.

**FORESIGHT ELECTRONICS**  
62 HIGH ST., CROYDON, SURREY

PCBs PRODUCED quickly. 5p/sq in, 50 minimum. FERRIC CHLORIDE, strong solution, 500ml bottle, £1.95. PCB INK (blue etch resistant) 175cc bottle, £1.25. P.W. easybuild organ keyboard, fitted gold contacts and resistors. One only, £22.00. Prices inclusive. Cheques, POs to J. F. Haggins, 8 Portnall House, Portnall Road, London W9 3BH.

## DON'T LOOK

unless you can resist the temptation to get these super 'attention-getters':

- ★ Pocket-sized **MAXI-VOLT** Big 1/2 inch Spark Generator (instant 15,000 volts!). Ready-made, needs no batteries. Carry it around anywhere. Only weighs about 3 oz. (89g.) send £1.90 for your Maxi-Volt now!
- ★ Unique **TRANSMITTER/RECEIVER** Kit. No licence examinations or tests required to operate this transistorised equipment. Easy to build. Get transmitting. Send £6.90 for yours now!
- ★ Psychedelic **MINI-STROBE** Kit. Take a pocket-sized lightning storm to Disco's & parties. 'Brain-freeze' 'em with vari-speed stop-motion flashes. Includes super case too. Send £2.90 now! (all prices include V.A.T., packing & postage.)

Send remittance to:

**BOFFIN PROJECTS,**  
4 CUNLIFFE ROAD,  
STONELEIGH, EWELL, SURREY  
(Mail order U.K. only)

Or for more details, send 20p for lists

**P.W. CRATA F.M. TUNER.** Set of five P.C. boards £3, p&p 20p. Other components available. S.A.E. for lists. Teleradio, 325 Fore Street, Edmonton, London N9 0PE.

**PRINTED CIRCUIT MANUFACTURERS OFFER,** PCBs for All PE and PW projects published after June '74, at one price, 70p each. Any 5, £2.85. PCB sets for: PW Tele-tennis, £3.50. Sandown Tuner with screens, £2.20. PE CCTV, £1.45, Power Slaves, £1.35; Scorpio Ignition, 'WW' Ferret Metal Locator, 65p each. CWO Prices inclusive. PRODUCTION SPACE AVAILABLE FOR: PCB production, PCB and electronic design, electroplating, silk-screening, roller tinning, photography and all artwork. Estimates by return post or phone. WKF Electronics Wellbeck Street, Whitwell, Worksop, Notts. Tel: 695.



### TREASURE TRACER MK III Metal Locator

- Varicap tuning
- Britain's best selling metal locator kit
- Weighs only 22oz.
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Thoroughly professional finish
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snips
- Five transistor circuit

Send s.a.e. for leaflet

Complete Kit	£9.80
Built, tested and guaranteed	£13.75
P & P 60p	78p
	P & P 60p, — £1.10 VAT

**MINIKITS ELECTRONICS,**  
54 CLEVELAND ROAD,  
LONDON, E18 3AN (Mail order only)

**ANTIQUE WIRELESS ENTHUSIASTS!** For all your requirements in obsolete radio, contact "Tudor Rees." 1975 Full catalogue now available, 40p post paid. Antique Wireless Service, 64 Broad Street, Staple Hill, Bristol, BS16 5NL. Tel. 0272 565472.

**LOWEST COST IC SOCKETS.** Use Soldercon IC socket pins for 8 to 40 pin DIL's. Make 8 pin sockets for 4p, 14 pin for 7p (at 300 pin price). 70p for strip of 100 pins, £1.50 for 3 x 100. £4 for 1000, 10p p&p for orders under £2. Add 8% VAT. Instructions supplied—send sae for sample. SINTEL, 53n Aston Street, Oxford. Tel: 0865 43203.

**12 VOLT 21" 13 Watt Fluorescent Lighting** (by Thorn/AEI) with diffuser & on/off switch. Ideal caravan, boat, emergency lighting, etc. Guaranteed.



£5.50 inc. VAT & Post. List price £7.02 inc. VAT  
**SALOP ELECTRONICS** 23 Wyle Cop,  
Shrewsbury, Shropshire Tel. 53296

**HARDWARE.** Comprehensive range of screws, nuts, washers, etc. in small quantities, and many useful Constructors' items. Sheet aluminium to individual requirements, punched, drilled, etc. Fascia panels, dials, nameplates in etched aluminium. Printed circuit boards for this magazine and other individual requirements, one-offs and small runs. Machine engraving in metals and plastics, contour milling. Send 2 x 4 1/2 p stamps for catalogue. Ramar Constructor Services, Masons Road, Stratford on Avon, Warwicks., CV37 9NF.

## AMBIT INTERNATIONAL

### INTEGRATED CIRCUITS

CA3053	40p
CA3089E	1.94
CA3090AQ	£3.75
CA3123E	£1.40
CT7001	£9.80
ICL8038	£3.10
LM309K	£1.90
LM380N	£1.00
LM381N	£1.85
LM1496	£1.02
LM3900	68p
NE550	80p
NE555v	78p
NE560B	£3.19
NE561B	£3.19
NE562B	£3.19
NE565A	£2.75
NE566v	£2.55
NE567v	£2.75
uA720	£1.40
uA723	80p
uA741	40p
uA753	99p
uA7805UC	£1.50
uA7805KC	£1.75
TBA120A	£1.00
TBA651	£1.81
TBA810s	£1.30
TD A1200	£1.94
SN76660N	£1.00
7400	20p
7413	38p
7446/7	£1.20
7448	£1.25
7490	71p
74121	38p
74192	£1.57
74S112	£2.30
78L12	45p
9368	£2.20
9582	£2.50
95H90	£9.90

### TRANSISTORS

BC318	14p
BF256L	34p
MEM614/5	38p
MEM616	50p
TIP2955	89p
TIP3055	60p

### 7 SEG LED DISPLAY

DL704 cc red	95p
SLA7 ca red	£1.50
SLA21 ca yellow	£1.75

### TOKO FILTERS, COILS

CFK10.7	60p
CFS10.7	40p
CFT455/470	45p
MFH41/71T	£1.75
BBR3125N	£1.30
BLR3107	£1.75
IF coils	each 27p
set of 3	60p

### FM RADIO

Larsen complete tunerset 7252	£20
Larsen head 8319	£7.74
TOKO head 5603	£8.40
TOKO head 703	£3.30
3089E quad coil	30p
3089E 22uH	15p
3090AQ 2mH	30p

### KITS

CA3090AQ built	£6.40
MCI3100 built	£5.40
FMR185 built	£4.35
TBA810s	£2.75

VAT 8%  
p/p 15p

### STAR ITEMS

**CT7001** Clock/Calendar chip with 24hr alarm and two auxiliary timers  
£9.80

**7252** Larsen tunerset. VHF-FM to audio. Voltage tuned with AFC £20

**8038** Sine, square and triangle waveform generator with voltage control  
£3.10

**CA3090AQ** PLL stereo decoder with stereo defeat. New low-noise version of this industry-standard RCA IC £3.75

**LM3801** 2 Watt four terminal audio power amplifier and low noise stereo preamplifier  
£1.00/£1.85

### DATA

1 page free on request with everything we sell. Data booklets free with ICL8038 CA3089E, LM380, EF5603

### CATALOGUE

Contains data and applications on our range of high technology IC'S.

Price 25p inc. VAT and postage.

**37a High Street, Brentwood,**  
**Essex CM14 4RH. (216029)**

# WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS, ENGLAND  
MAIL ORDER. CALLERS SATURDAYS ONLY

Send 10p postage for our comprehensive catalogue

## TRANSISTORS (less 10% for 25+ of one type)

AC125 15p	BC149C 8p	BF180 33p	OC81 24p	2N1131 20p	2N3773 240p
AC126 11p	BC154 18p	BF181 33p	OC82 15p	2N1132 20p	2N3819 24p
AC127 11p	BC157 13p	BF184 22p	OC83 20p	2N1301 20p	2N3820 38p
AC128 11p	BC158 11p	BF185 22p	OC140 100p	2N1302 20p	2N3823 60p
AC176 11p	BC179 15p	BF194 10p	OC201 70p	2N1303 20p	2N3824 50p
AC187 12p	BC167 12p	BF195 10p	OC202 80p	2N1304 20p	2N3904 15p
AC188 11p	BC168 12p	BF196 12p	TIP29 43p	2N1305 24p	2N3905 17p
AC177 35p	BC169 12p	BF197 15p	TIP29A 45p	2N1306 24p	2N3906 17p
AC190 25p	BC170 11p	BF257 32p	TIP30 48p	2N1307 24p	2N4037 35p
AC191 24p	BC171 11p	BF595 18p	TIP30A 54p	2N1893 30p	2N4547 30p
AC192 24p	BC172 11p	BFX86 21p	TIP31 48p	2N1900 45p	2N4548 30p
AD140 48p	BC178 16p	BFY88 22p	TIP32 64p	2N2217 23p	2N4549 30p
AD149 48p	BC179 16p	BFY90 15p	TIP33 95p	2N2926 9p	
AD161 78p	BC180 16p	BFY51 15p	TIP34 130p	2N2926G 9p	
AD162 78p	BC183 10p	BFY52 15p	TIP41A 68p	2N2926G 9p	
AD163 78p	BC184 11p	BFY53 17p	TIP42 70p	2N2926G 9p	
AF115 13p	BC212 12p	BSX20 16p	TIP42A 74p	2N2926G 9p	
AF116 13p	BC213 12p	MJE150 63p	TIP43 74p	2N2926G 9p	
AF117 13p	BC214 17p	MJE371 78p	TIP44 74p	2N2926G 9p	
AF118 40p	BCY42 28p	MJE520 62p	TIP45 74p	2N2926G 9p	
AF121 33p	BCY43 25p	MFP102 30p	TIP46 74p	2N2926G 9p	
AF124 30p	BCY58 18p	MFP103 30p	TIP47 74p	2N2926G 9p	
AF125 30p	BCY59 18p	MFP104 30p	TIP48 74p	2N2926G 9p	
AF126 30p	BCY70 15p	MFP105 30p	TIP49 74p	2N2926G 9p	
AF127 30p	BCY71 15p	OC2 40p	TIP50 74p	2N2926G 9p	
AF128 30p	BCY72 12p	OC28 48p	TIP51 74p	2N2926G 9p	
AF181 45p	BD131 40p	OC35 48p	TIP52 74p	2N2926G 9p	
AF186 48p	BD132 40p	OC36 52p	TIP53 74p	2N2926G 9p	
AF239 38p	BD137 45p	OC41 15p	TIP54 74p	2N2926G 9p	
BC107 8p	BD138 45p	OC42 15p	TIP55 74p	2N2926G 9p	
BC108 8p	BDY60 59p	OC44 11p	TIP56 74p	2N2926G 9p	
BC108B 11p	BDY61 53p	OC45 11p	TIP57 74p	2N2926G 9p	
BC109 10p	BF115 22p	OC70 11p	TIP58 74p	2N2926G 9p	
BC109B 11p	BF177 26p	OC71 11p	TIP59 74p	2N2926G 9p	
BC147 7p	BF178 28p	OC72 11p	TIP60 74p	2N2926G 9p	
BC148 7p	BF179 33p	OC74 28p	TIP61 74p	2N2926G 9p	

## TTL 74 DIGITAL ICs

Discounts Less 5% for 15+ mixed  
Less 10% for 25+ mixed  
Less 15% for 50+ mixed

7400 14p	7428 38p	7473 33p	74121 32p
7401 14p	7430 15p	7474 32p	74123 63p
7402 15p	7432 25p	7475 47p	74141 75p
7403 15p	7433 36p	7476 32p	74151 69p
7404 18p	7437 27p	7480 44p	74153 69p
7405 18p	7438 27p	7481 99p	74155 69p
7406 18p	7440 15p	7482 75p	74156 70p
7407 38p	7441 75p	7483 83p	74160 101p
7408 15p	7442 65p	7484 90p	74166 143p
7409 15p	7443 120p	7485 125p	74167 315p
7410 15p	7444 105p	7489 334p	74170 215p
7411 20p	7445 86p	7490 47p	74172 540p
7412 20p	7446 105p	7491 80p	74176 103p
7413 35p	7447 100p	7492 48p	74180 106p
7414 60p	7448 86p	7493 47p	74184 106p
7416 35p	7450 15p	7495 63p	74185 169p
7417 35p	7451 15p	7496 72p	74190 46p
7420 15p	7453 15p	74100 135p	74191 160p
7422 24p	7454 15p	74104 40p	74192 128p
7423 27p	7460 15p	74105 40p	74193 128p
7425 27p	7470 30p	74107 33p	74198 210p
7426 27p	4772 26p	74110 43p	74199 210p

## SPECIAL OFFER

White stocks last

709C 8 pin	27p
723C 14 pin	50p
741C 8 pin	26p
748C 8 pin	26p
TBA 300	95p
ZN 414	105p

## OPTO ELECTRONICS

Minitrons 3105F	110p
7 seg display	40p
OC70	40p
OC71	85p
ORP12	58p
ORP60	45p
ORP61	46p

## LED TIL 209 (Red)

(with socket)	18p
2N5777	40p

## LINEAR IC'S (less 5% 50+ mixed)

709C 27p	LM380 100p
723C 50p	MC724 60p
741C 26p	MC1303L 130p
747C 80p	MC1304P 360p
748C 26p	MC1310P 240p
7805 (T03) 160p	MC1710CG 60p
AY-1-0212 510p	MFC4000B 39p
AY-1-5051 45p	MLM309K 158p
CA3018 72p	MV12 170p
CA3035 135p	NE555 55p
CA3036 90p	PA263 195p
CA3046 55p	SL403D 150p
CA3048 210p	SL414A 150p
CA3075 150p	SN76033 250p
CA3081 150p	SN76115 250p
CA3089E 199p	TAD100 140p
CA3090C 310p	TBA820 95p
LM300 170p	TBA810 150p
	1E05 1-3W 17p

## BRIDGE RECTIFIER

(plastic case)	1A 50V 38p
	1A 100V 42p
	1A 200V 21p
	1A 600V 70p
	1A 600V 70p
	3A 100V 44p
	3A 400V 75p
	3A 600V 91p
	4x4x1 1/2" 45p
	4x2x1 1/2" 45p
	4x5x1 1/2" 48p
	4x2x2 1/2" 50p
	3x2x1 1/2" 38p
	7x5x2 1/2" 78p
	8x6x3 1/2" 99p
	10x7x3 1/2" 118p
	10x4 1/2"x3 1/2" 99p
	12x5x3 1/2" 120p
	12x8x3 1/2" 150p

## SCR (Thyristor)

200V 3A 91p
500V 3A 120p
400V 6A 120p
500V 6A 150p

## DIL SOCKETS

8 pin	14p
14 pin	14p
16 pin	15p
24 pin	75p

## ZENER DIODES

Range	3-3V
	3-33V
	400mW 9p
	1-3W 17p

## FUSES AND HOLDERS

20mm 150mA-5A	3p
1 1/2A-13A mains	4p
1 1/2 250mA-15A	3p
Panel Holder Single	6p
Chassis Holder 20mm	16p
Chassis Holder 1 1/2"	22p

## BUZZER

for 4.5V operation	39p
--------------------	-----

## ENAMEL COPPER WIRE (2oz reel)

16, 18, 20, 22 SWG	32p
24, 26, 28, 30 SWG	39p
32, 34, 36, 40 SWG	48p

## FERRITE RODS: 1/2" diam.

2" - 8p; 5 1/2" - 12p; 6 1/2" - 16p
-------------------------------------

## STEREO JUNCTION BOXES

Provides multiple output to your Amplifier.  
JB31: 4 outputs, 2 for two sets of stereo headphones and 2 for two speakers.  
Price: £1.48 only.  
JB11D: Has output for two sets of stereo headphones, 2 speakers and 3 position switch for headphones, loudspeakers or both.  
Price: £1.95 only.

## THERMISTORS 15p each

VA 1034; VA 1040; VA 1055; VA 1056;
VA 1058; VA 1066; VA 1067; VA 1077;
VA 1098; VA 1100.

ALL DEVICES BRAND NEW AND FULLY GUARANTEED.  
ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O.s OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P & P ADD 15p TO ORDERS UNDER £4 00. OVERSEAS ORDERS POSTAGE AT COST, AIR/SURFACE. PRICES EXCLUSIVE OF VAT.

## POLYESTER CAPACITORS: Axial lead type. (Values are in µF)

400V: 0.001, 0.0012, 0.0015, 0.0018, 0.0022, 0.0034, 0.0047, 0.0068, 0.01 3p; 0.015, 0.022, 0.033, 0.047, 0.068, 0.1 4p; 0.15, 0.22, 7p; 0.33, 10p; 0.47, 13p; 160V: 0.1, 0.15, 4p; 0.22 5p; 0.33 6p; 0.47 9p; 0.68 10p; 1.0 13p. 250V: 0.22 6p; 0.33 8p; 0.68 12p; 0.47 9p; 2.2 18p.

## RADIAL LEAD P.C. TYPE (Values are in µF)

250V: 0.01, 0.015, 0.022, 3p; 0.033, 0.047, 0.068, 3 1/2p; 0.1 4p; 0.15 4p; 0.22, 0.33 5p; 0.47 7p; 0.68 10p; 1.0 11p; 1.5 20p; 2.2 22p.

## ELECTROLYTIC CAPACITORS. Axial lead type (Values are in µF)

63V: 0.47, 1.0, 1.5, 2.2, 3.3, 4.7, 6.8, 10, 15, 20, 22, 47, 68, 100, 12p. 40V: 100, 6p 300V, 350V, 25V: 10, 68, 150, 6p; 220, 11p; 470, 13p; 680, 18p; 1000, 24p; 2200, 34p, 3000, 33p; 4700, 47p. 16V: 40, 125, 250, 6p. 16V: 1000, 1500, 16p. 10V: 4, 100, 5p; 540, 10p; 1000, 14p; 2200, 18p.

## POTENTIOMETERS (AB) Carbon

Track, 0-25W Log & 0-5W Linear values  
1K Ω-2M Ω single gang 14p  
5K Ω-2M Ω single gang D/P switch 28p  
2K Ω-2M Ω dual gang stereo 42p

## SLIDER POTENTIOMETERS

0-25W log and linear values  
5K Ω-500K Ω single gang 35p  
10K-500K ohm Dual gang 50p  
KNOBS for above Black or Silvered 8p

## PRESET POTENTIOMETERS

0-1W 50 Ω-1M Ω Vertical only 5p  
0-25W 100 Ω-2M Ω Horizontal 6p  
0-25W 1K Ω-2M Ω Vertical 6p

## QUALITY RESISTORS. ERIE MAKE

Small Size, High Stability, Low Noise	PRICE
Type Pw Tol. Range Val. 1-99	40-999 500+
Carbon 1W 5% 2-2 Ω-10M E24	1p 0-8p 0-7p
Carbon 1W 5% 2-2 Ω-10M E12	1p 0-8p 0-7p
Carbon 1W 5% 2-2 Ω-10M E12	2-5p 2p
VW 4W 10% 2-2 Ω-100 E12	2p

Quantity price applies to resistors of each value not mixed.

## JACK PLUGS SOCKETS PANEL METERS

Screened chrome	Plastic body	Open metal	Moulded with
2.5mm 10p	8p	8p	break
3.5mm 14p	10p	8p	contacts
Standard Mono 17p	13p	15p	17p
Standard Stereo 30p	18p	15p	25p

60mm x 46mm x 35mm requires 1 1/2" hole  
FULL SCALE  
ME 6 0-50µA  
ME 7 0-100µA  
ME 8 0-500µA  
ME 9 0-1mA  
ME 10 0-5mA  
ME 11 0-10mA  
ME 12 0-50mA  
ME 13 0-100mA  
ME 14 0-500mA  
ME 15 0-1 amp  
ME 16 0-50V AC  
ME 17 0-300V AC  
ME 18 "S" Meter

Price £2.48, p & p 10p

## DIN 2PIN LOUDSPEAKER

Type. 3, 4, 5 (180° & 240°) 6PIN	Plugs	Sockets	Couplers
	12p	8p	15p

## CO-AXIAL (TV)

10p	8p	15p (f.f.)
-----	----	------------

## PHONO assorted colours

6p	5p (sgl.) 7p (dbl.) 10p (trpl.)	9p
----	---------------------------------	----

## BANANA SWITCHES

TOGGLE: SPST 18p	PUSH BUTTON: Miniature push to make or break non locking 15p	R.F. CHOKES 1-5mH 18p 2-5mH 18p
DPDT 22p	ROCKER (white): 10A 250V SP changeover centre off 25p	HEAT SINKS Low Power To5 15p To18 15p To66 (TV2) 15p To1 (H13) 5p
SUB-MIN TOGGLE SP changeover 40p	ROCKER: Illuminated (white) incorporates neon, lights when on 3A 240V 45p	
SPST on/off 45p	ROTARY SWITCH: 1 pole/12way 2p/6w, 2p/2w, 2p/4w, 3p/3w/4w, 4p/2w, 4p/3w 24p	
DPDT 6 Tag 64p		

## TRANSFORMERS MAINS

Primary 220-240V	100mA 90p
6-6 (miniature) 100mA 90p	
9-9 (miniature) 100mA 90p	
12-12 (miniature) 100mA 9	

## "SLO-SYN" 3-LEAD SYNCHRONOUS STEPPING MOTOR



Type SS15. These fine motors are easily reversed, starting and stopping in less than 5° without electrical or mechanical braking. Simple relay circuit can

be applied to give D.C., to winding for a maximum holding torque of 300oz/in with 35v at 0.35 amps through winding. For A.C. (synchronous) operation at 120v., 50Hz. Speed 60 rpm at 60Hz., 72 rpm. STEPPING. Holding torque at 50 steps per second—100 oz/in. Can be wired to give 100 or 200 steps per revolution with accuracy of 0.1° per step non-cumulative. Torque characteristics can be modified by simple R.C. circuits. Dimensions: dia. 4", body length 4 1/2", spindle length 2 1/2" x 1/8" dia. Weight 6 1/2 lbs. BRAND NEW in maker's packing. Offered at less than 1/2 maker's price.

OUR PRICE ONLY £15 P & P £1-00

## UNISELECTORS

8 Bank 25 way double sweep 48v. D.C. ex-computer in 1st class condition. £4 plus 95p. P & P.

## SHADED POLE MAINS MOTOR

A quality shaded pole motor. Open frame, 3" high x 2 1/2" x 2" Spindle 1" x 1/8". 1,420 r.p.m. £1-95 P & P 20p

## CROUZET Open Frame

Shaded pole motor, 115/240 V.A.C. 1425 r.p.m. approx. size: 2 1/2 inches x 2 1/2 inches x 1 1/2 inches deep 1/8" dia. spindle 2" long £2-25 p. & p. 25p.

## "LABGEAR ELIMINAC"

P.S.U. 200-250v. 40/60Hz. Alternative outputs fully variable (varioc incorporated). Output 1. 12v at 5a D.C. fully smoothed. Output 2. 12v at 8a D.C., with ripple content. Output 3. 20v at 10a A.C. 2 1/2" x 2 1/2" flush 0-20v D.C. m/c meter. In attractive grey hammer finish case. In maker's carton £27-50. Carr. & Pkg. £1-50.

## SPECIAL OFFER LIGHT DEPENDENT RESISTORS

Matched pairs Pioneer Type 174 similar to ORP 12. Resistance 1K to 40K Dia 1/4" with 1/2" flange. £1-50 for two pairs (minimum) 10 or more pairs, 50p. per pair incl. P & P.

## MAINS SOLENOID

This little unit gives vertical lift of approximately 1" through hinged "elbow". Bracket incorporates 2 fixing screws. Length of arm, 2 1/2". 240V A.C. Pull at coil is approximately 1lb. £1. FREE P. & P. Special quotes for quantities.

## SOLENOIDS by WESTOOL

240AC type MM6. 3lb. pull, 2 3/4" x 1" x 1 1/2". Travel 1" £1 each. P. & P. 20p.  
240AC type MM4. 2lb. pull, 1 1/2" x 1 1/2" x 1". Travel 2" 80p each. P. & P. 20p. Quantity discounts: 10-50 10%, 50 upwards 25%.

## OPEN FRAME shaded pole GEARED MOTORS


240 AC., 110rpm. NEW HIGH TORQUE, approx. overall size: 3 1/2" x 3 1/2" x 2 1/2" + spindle 1/2" dia. £3. P. & P. 50p. 110rpm with pressed steel gear case (similar to above but slightly smaller). £2-70. P. & P. 30p.

## SILVANIA MAGNETIC SWITCH

Now complete with reference magnet!

A magnetically activated switch, vacuum sealed in a glass envelope. Silver contacts, normally closed. Rated 3amp at 120v., 1/2amp at 240v. Size: (approx.) 1 1/2" long x 1/2" dia. Ideal for burglar alarms, security systems etc., and wherever non-mechanical switching is required. 10 for £2-10; P. & P. 15p. 50 for £2-60; 100 for £15-50. FREE P. & P. over 10.

## AMPEX 7.5v. D.C. MOTOR

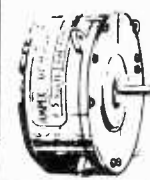

An ultra precision tape motor designed for use in the AG20 portable recorder. Torque 450GM/CM. Stall load at 500ma. Draws 60ma on run, 500rpm ± speed adjustment. Internal AF/RF suppression. 1/2" dia. x 1" spindle, motor 3". Dia. x 1 1/2". Original cost £16-50. OUR PRICE £4-25. P. & P. 25p. Quantity available. Mu-metal enclosure available 75p each. FREE P. & P.

## FAN/BLOWER



Precision-built in Germany. Dynamically balanced mains unit (200/240) continuous rated, reversible 60MA on run. Size: 5 1/2" dia. x 2 1/2" deep. Back plate is tapped for 4 fixing screws (supplied). Well under maker's price at £3. P. & P. 40p.

## ALL PRICES INCLUDE V.A.T.

Whilst we welcome official orders from established companies and Educational Departments, it is no longer practical to invoice goods under £5. Therefore, please remit cash with orders below this amount.

# ELECTRO-TECH COMPONENTS LTD.

315/317, EDGWARE ROAD, LONDON, W2.  
Tel: 01-723 5667 01-402 5580

## INDEX TO ADVERTISERS

Allard Electronics ... 1142  
Ambit International ... 1145  
Amtron Electronics ... 1123  
Arbour Electronics ... 1140  
A.S.P. Ltd. ... 1070  
Astro Electronics Ltd. ... 1070

Barrie Electronics ... 1078  
Baykin Engineering Ltd. ... 1144  
Benford Cabinets ... 1078  
Beta Devices ... 1142  
B.H. Component Factors Ltd. ... 1123  
Bi-Pak Semiconductors ... 1082-1083  
Bi-Pre-Pak Ltd. ... 1127  
Bib Hi-Fi Accessories Ltd. ... 1076  
Boffin Projects ... 1145  
Bothwell ... 1128  
British Institute of Engineering Technology ... 1074, 1137, cover iii  
British National Radio & Electronics School ... 1062, 1124, 1141  
J. Bull (Electrical) Ltd. ... 1081

C. Caranna ... 1143  
Chiltmead Ltd. ... 1062  
Chromasonic Electronics ... 1075  
C.J.L. Ltd. ... 1136  
Codar ... 1062  
Colomar (Electronics) Ltd. ... 1096  
Crescent Radio Ltd. ... 1070  
Crofton Electronics ... 1096  
C.T. Electronics ... 1131

Dabar Electronics Products ... 1068  
D.E.W. Ltd. ... 1145

Electronic Brokers ... 1144  
Electronic Design Associates ... 1137  
Electronic Mail Order Ltd. ... 1136  
Electroni-Kit ... 1070

Electrospares ... 1186  
Electro-Tech ... 1147  
Electrovalue Ltd. ... 1077  
Elvins Electronics ... 1092

Felstead Electronics ... 1137  
Foresight Electronics ... 1145

Galleon Trading ... 1142  
Garfields ... 1144  
Goldring Ltd. ... 1074  
Greenweld Electronics ... 1140

H.A.C. (Shortwave) Products ... 1096  
Harversons Surplus Co. Ltd. ... 1095  
Heath (Gloucester) Ltd. ... 1091  
Henry's Radio Ltd. ... cover iv

I.L.P. (Electronics) Ltd. ... 1069  
Intergrex Ltd. ... 1080  
Intertext (I.C.S.) ... 1132 & 1143

Jones, J. C. ... 1137

Kensington Supplies ... 1143  
Keytronics ... 1140

Lasky's ... 1065-1066-1067  
Lewis Radio ... 1068  
Linear Products Ltd. ... 1128  
London Computer Operators Training Centre ... 1143  
London Electronics College ... 1143

Maplin Electronic Supplies ... 1135  
Marco Trading ... 1142  
Marshall, A. ... 1132  
M and B. Components ... 1096  
Milward, G. F. ... 1148  
Minikits Electronics ... 1145

Newmart Electronics ... 1079

Partridge Electronics Ltd. ... 1068

Radio Book Services ... 1144  
Radio Components Specialists... 1138-1139  
Radio Exchange Ltd. ... cover ii  
R.C.S. Products Ltd. ... 1076  
R.D.I. Ltd. ... 1142  
R.S.C. (Hi-Fi) Centre Ltd. ... 1063  
R.S.T. Valve Mail Order Co. ... 1064  
R & TV Components Ltd. ... 1072-1073  
Riversdale Electronics ... 1092  
Rivlin Instruments ... 1078

Salop Electronics ... 1145  
Saxon Entertainments Ltd. ... 1133  
Scientronics ... 1141  
Selray Book Co. ... 1144  
Sinclair (Cambridge) Ltd. ... 1118-1119  
Simtech Engineering Ltd. ... 1143  
Sintel ... 1144  
Sound Systems of Suffolk ... 1142  
Special Products Distributors Ltd. ... 1092  
Studio Electronics ... 1123  
Surpltronics ... 1134  
Swanley Electronics ... 1140

Technomatic Ltd. ... 1128  
Trampus Electronics Ltd. ... 1080  
Tweedy (J. & A.)... 1143

Ultracomponents Ltd. ... 1141  
Vero Electronics... 1076

Watford Electronics ... 1146  
West London Direct Supplies ... 1076  
Wilmslow Audio ... 1134

Z & I Aero Services ... 1148



Head Office and Warehouse  
44A WESTBOURNE GROVE  
LONDON W2 5SF  
Tel: 727 5641/2/3

## Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to Head Office  
Our new 1975 Catalogue/Price list of valves, tubes, semiconductors, Test Equipment  
and passive components is now ready. Please send £0.20 for your copy.  
No C.O.D. orders accepted

Retail Shop  
85 TOTTENHAM COURT ROAD  
LONDON W1  
Tel: 580 8403  
Open all day Saturday

### AC/DC MULTIMETER TYPE U432A



33 ranges up to  
3 Amps AC/DC;  
1200V DC, 900V  
AC, 500kΩ, +12  
db.

Sensitivity:  
20kΩ/V DC;  
4kΩ/V AC

Accuracy:  
±2.5% DC;  
±4% AC


Movement is protected by silicon  
diodes.

Dimensions 167×98×63 mm. Weight:  
1.5lb.

PRICE: complete with test leads,  
instruction manual and fibre-board  
storage case £9.85. Packing & carr.  
£0.50.

### MULTIMETER TYPE U4323

Sensitivity: 20,000Ω/V.

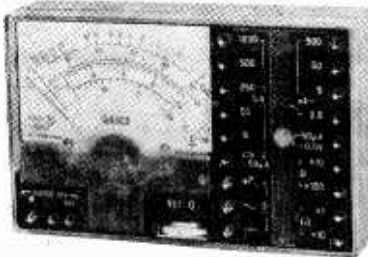


7 D.C. Voltage ranges 0.5-1000V  
6 A.C. Voltage ranges 2.5-1000V  
5 D.C. Current ranges 0.05-500mA  
4 Resistance ranges 1kΩ-1MΩ

Built-in oscillator providing AF output of  
1kHz and I.F. output of 465kHz with an ampli-  
tude of 1 volt minimum.

Dimensions: 140×87×40 mm. Weight 0.5kg

PRICE complete with leads and plastic  
storage case £8.00. Packing & postage £0.50

### AC/DC MULTIMETER TYPE U4313

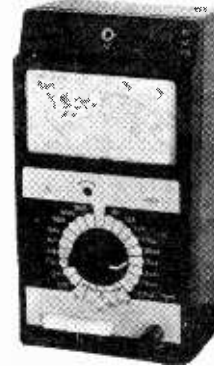

39 ranges:  
600μA to 1.5A  
AC  
60μA to 1.5A DC  
75mV to 600V  
DC

1.5V to 600V AC  
1MΩ, 0.5μF, 12db

Accuracy: 1.5%  
DC; 2.5% AC  
Sensitivity: 20k  
Ω/V DC; 2kΩ/V  
AC

Mirror scale 86mm long.

Dimensions: 115×215×90 mm, Weight 3.3lb.

PRICE, complete with test leads, service  
manual and steel carrying case £13.80.  
Packing & carriage £0.50.

**ALL THE ABOVE INSTRUMENTS FEATURE TAUT SUSPENSION MOVEMENTS  
PRICES ARE EXCLUSIVE OF V.A.T.**

**G. F. MILWARD, 369 Alum Rock Road, Birmingham B8 3DR.**  
Tel. 021-327 2339

We are glad to say that it is now possible to supply from stock the following integrated circuits.  
**ALL ARE BRANDED, FULL SPECIFICATION** devices offered at unbeatable prices

	1/99	100/499	500/1000		1/99	100/499	500/1000		1/99	100/499	500/1000
7400	£0.15	£0.125	£0.10	7442	£0.645	£0.537	£0.43	7494	£0.495	£0.412	£0.33
7401	£0.15	£0.125	£0.10	7443	£1.275	£1.062	£0.85	7495	£0.63	£0.525	£0.42
7402	£0.15	£0.125	£0.10	7445	£0.855	£0.712	£0.57	7496	£0.72	£0.60	£0.48
7403	£0.15	£0.125	£0.10	7446	£1.05	£0.875	£0.70	74104	£0.315	£0.262	£0.21
7404	£0.18	£0.15	£0.12	7446A	£1.05	£0.875	£0.70	74105	£0.315	£0.262	£0.21
7405	£0.18	£0.15	£0.12	7447	£1.05	£0.875	£0.70	74107	£0.315	£0.262	£0.21
7406	£0.375	£0.312	£0.25	7447A	£1.05	£0.875	£0.70	74121	£0.315	£0.262	£0.21
7407	£0.375	£0.312	£0.25	7448	£0.855	£0.712	£0.57	74122	£0.45	£0.375	£0.30
7408	£0.15	£0.125	£0.10	7450	£0.15	£0.125	£0.10	74123	£0.63	£0.525	£0.42
7409	£0.15	£0.125	£0.10	7451	£0.15	£0.125	£0.10	74141	£0.75	£0.625	£0.50
7410	£0.15	£0.125	£0.10	7453	£0.15	£0.125	£0.10	74151	£0.69	£0.575	£0.46
7412	£0.195	£0.162	£0.13	7454	£0.15	£0.125	£0.10	74153	£0.69	£0.575	£0.46
7413	£0.345	£0.287	£0.23	7450	£0.15	£0.125	£0.10	74155	£0.69	£0.575	£0.46
7416	£0.345	£0.287	£0.23	7472	£0.255	£0.212	£0.17	74156	£0.69	£0.575	£0.46
7417	£0.345	£0.287	£0.23	7473	£0.315	£0.262	£0.21	74160	£1.005	£0.837	£0.67
7420	£0.15	£0.125	£0.10	7474	£0.315	£0.262	£0.21	74161	£1.005	£0.837	£0.67
7423	£0.27	£0.225	£0.18	7475	£0.485	£0.387	£0.31	74162	£1.005	£0.837	£0.67
7425	£0.27	£0.225	£0.18	7476	£0.315	£0.262	£0.21	74163	£1.005	£0.837	£0.67
7426	£0.27	£0.225	£0.18	7480	£0.435	£0.362	£0.29	74166	£1.425	£1.167	£0.95
7427	£0.27	£0.225	£0.18	7482	£0.75	£0.625	£0.50	74174	£1.20	£1.00	£0.80
7430	£0.15	£0.125	£0.10	7483	£0.825	£0.687	£0.55	74175	£0.975	£0.812	£0.65
7432	£0.27	£0.225	£0.18	7485	£1.275	£1.062	£0.85	74192	£1.275	£1.062	£0.85
7437	£0.27	£0.225	£0.18	7486	£0.315	£0.262	£0.21	74193	£1.275	£1.062	£0.85
7438	£0.27	£0.225	£0.18	7490	£0.465	£0.387	£0.31	74198	£2.10	£1.75	£1.40
7440	£0.15	£0.125	£0.10	7492	£0.465	£0.387	£0.31	74199	£2.10	£1.75	£1.40
7441A	£0.825	£0.687	£0.55	7493	£0.465	£0.387	£0.31				

To secure the above prices, all orders for these devices must exceed £10 in total value. Price  
rating is established by TOTAL NUMBER OF DEVICES ORDERED. Any mix may be made.  
For special quotations for large orders ring 021-327 2339 NOW!

#### NEW! NEW! NEW! NEW!

An aerosol spray providing a convenient means of producing any  
number of copies of a printed circuit both simply and quickly.

Method: Spray copper laminate board with light sensitive spray.  
Cover with transparent film upon which circuit has been drawn. Expose  
to light. (No need to use ultra-violet.) Spray with developer, rinse and  
etch in normal manner.

Light sensitive aerosol spray .. .. . £1.00  
Developer and Etchant .. .. . 50p

PLUS POSTAGE

#### FIBRE-GLASS COPPER LAMINATE

Single-sided .. .. . 75p sq. ft.

Double-sided .. .. . £1 sq. ft.

Cut in any multiple of 6"

To a maximum size of 3' x 4'

### BRAN TUB !!!

- ★ Resistors, Wire-wound and Carbon
- ★ Capacitors, Silver-mica, Paper, Ceramic, Polyester and Electrolytic
- ★ Controls, Volume, Pre-set, Carbon, Wire
- ★ Diodes, Silicon, Germanium, Zener
- ★ Transistors, Silicon, Germanium

All the above are new and unused stock.

We have made up packs of 2lb gross weight, all are different in content, and contain a mixture of components from the above list. This is a fantastic unrepeatable offer that will enable you to get a good stock of spares at a tiny fraction of normal price!

To make things even more interesting - TWENTY OF THESE BAGS ALSO CONTAIN A POUND NOTE! TWENTY CUSTOMERS WILL BE VERY PLEASED INDEED!

Rush your order now! This offer is only made to reduce our surplus stock! It is unlikely that in these days of rising prices we shall ever be able to repeat!

And the price that we are asking? Only £1.50 including both postage and VAT!

POSTAGE 30p

NOTE: ALL GOODS PLUS 8% VAT (EXCEPT OVERSEAS)

POSTAGE 30p

# FREE!

## Over 150 ways to engineer a better future

HIGHER PAY

A BETTER JOB

SECURITY

### find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it today and we'll send you full details and a free book. We have successfully trained thousands of men at home—equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost home study course gets results fast—makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call in on you... but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained, a view echoed by two colleagues who recently commenced the course". Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects"—Student J.A.O. Dublin.

"My training quickly changed my earning capacity and, in the next few years, my earnings increased fourfold". Student C.C.P., Bucks.

### FIND OUT FOR YOURSELF

These letters and there are many more on file at Aldermaston College, speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to

## ALDERMASTON COLLEGE

Dept. RPW04, Reading RG7 4PF.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

This FREE 76 page book can put you on the road to success through a BIET Home Study Course. Choose your subject now!

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.**

Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.



**CUT OUT THIS COUPON**  
Tick or state subject of interest. Post to address below.

<b>MECHANICAL</b>	<b>DRAUGHTSMANSHIP</b>	Construction Surveyors Institute L.C.S.I. City & Guilds General Building (all branches) Heating & Vent. Inst. Clerk of Works Site Surveying Health Engineering Road Construction Quantities Estimates Hydraulics Structural Eng.
Society of Engineers—	Institute of Engineering Designers (A.M.I.E.D.)	<input type="checkbox"/>
A.M.S.E. (Mech)	General Draughtsmanship	<input type="checkbox"/>
Institute of Engineer & Technicians (A.M.I.E.)	Elec. Draughtsmanship	<input type="checkbox"/>
<b>CITY &amp; GUILDS</b>	Architectural Draughtsmanship	<input type="checkbox"/>
Gen. Mech. Eng. Maintenance Eng. Welding	Technical Drawing	<input type="checkbox"/>
Sheet Metal Work Eng. Inspection Eng. Metallurgy		<input type="checkbox"/>
<b>ELECTRICAL &amp; ELECTRONIC</b>	<b>RADIO &amp; TELECOMMUNICATIONS</b>	<b>GENERAL</b>
<b>CITY &amp; GUILDS</b>	City & Guilds Telecoms.	Agricultural Eng. Council of Eng. Institutions Farm Science Plastics
Gen. Electrical Engineering	Gen. Radio & TV Eng.	<input type="checkbox"/>
Electrical Installations	Radio Amateurs Exam	<input type="checkbox"/>
Electrical Maths	Radio Servicing	<input type="checkbox"/>
Computer Electronics		Supplementary courses for Nat. Certificates.
Electronic Eng. Practical Radio & Electronics (with kit)	<b>AUTOMOBILE &amp; AERONAUTICAL</b>	
<b>MANAGEMENT &amp; PRODUCTION</b>	Institute of the Motor Industry A.M.I.	
Institute of Cost & Management Accountants	MAA/IMI City & Guilds Auto Eng.	
Computer Programming	Gen. Auto Eng. Motor Mechanics	
Works M'nent Work Study	Auto Diesel Eng. Garage M'nent	
Gen. Production Eng.	AEC Aero Engineering Exams	
Estimating & Planning	Gen. Aero Eng.	
Storekeeping Management	<b>CONSTRUCTIONAL</b>	Coaching for many exams, including C & G
Skills Quality Control	Institute of Building L.I.O.B.	<input type="checkbox"/>
	A.B.T. Clerk of Works	<input type="checkbox"/>

**G.C.E.**  
—choose from 58 'O' & 'A' level subjects

## POST TODAY FOR A BETTER TOMORROW

To Aldermaston College, Dept. RPW04, Reading RG7 4PF.

NAME .....

Block capitals please

ADDRESS .....

POSTCODE .....

OTHER SUBJECTS .....


AGE .....

Accredited by C.A.C.C. Member of A.B.C.C.

130 LOVE

# Henry's Radio

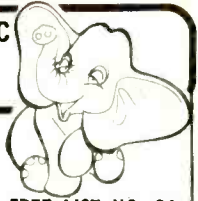**LARGEST SELECTION OF ELECTRONIC COMPONENTS AND EQUIPMENT. LOW PRICES- MEAN LESS VAT.**



## You can build the Texan and Stereo FM Tuner TEXAN 20 + 20 WATT IC STEREO AMPLIFIER

Features glass fibre PC board, Gardners low field transformer 6-IC's, 10-transistors plus diodes, etc. Designed by Texas Instruments engineers for Henry's and, P.V. 1972. Supplied with full chassis work, detailed construction handbook and all necessary parts. Full input and control facilities. Stabilised supply. Overall size 15 1/2" x 2 1/2" x 6 1/2" mains operated. Free teak sleeve with every kit. **£31.00 (Carriage 50p).** (also built and tested £37.50)



**HENELEC Stereo FM Tuner** Features capacity diode tuning, lead and tuning meter indicators, stabilised power supply—mains operated. High performance and sensitivity with unique station indication IC stereo decoder. Overall size in teak sleeve 8" x 2 1/2" x 6 1/2". Complete kit with teak sleeve **£21.00 (Carriage 50p).** (also built and tested £24.95)



## JOIN THE LARGE BAND OF HAPPY CONSTRUCTORS!

### NEW SPECIAL PURCHASE



**AM/FM tuner modules**  
Mullard type LP1179 and LP1171  
These two modules together form a high quality AM/FM tuner covering the long, medium and VHF broadcast bands. Requires only 16 resistors and capacitors and a switch to complete. Supplied with circuits and spec. data

FM Coverage	87-108 MHz
Bandwidth	300 KHz
Selectivity	36 dB
Signal to noise at limiting threshold	40 dB
Audio output	75 mV

**AM Bandwidth** 6.5 KHz  
**Sensitivity** 1 pV  
Built-in AGC  
Supply 6V negative earth  
LP1179 and LP1171 £7.50  
Suitable Ferrite aerial £0.75

**Amplifiers with controls**

E1210	12 volt 2 1/2 + 2 1/2 watts 8 ohms	8.25
SAC14	Mains 7 + 7 watts 8 ohms	11.75
SA C30	Mains 15 + 15 watts 8 ohms	14.95
CAO38	9 volt 1 1/2 + 1 1/2 watts 8 ohms	6.95
CAO68	12 volt 3 + 3 watts 8 ohms	10.50

**AM/FM Modules**  
Mullard LP 1186 FM tuner (front end) with data 10.7 MHz O/P **£ 4.85**  
LP1157 AM/Module **£2.50**  
LP1171 AM/FM Module **£4.50**  
Mullard LP 1185 10.7 MHz IF unit with data **4.50**  
Gorler Permeability FM tuner (front end) 10.7 MHz O/P **4.20**

**FM and AM Tuners and Decoders**  
FM5231 (tu 2) 6 volt fm tuner **7.95**  
TU3 12 volt version (FM use with Decoder) **7.95**  
SD4912 Stereo Decoder for Tu 3-12 volt **7.95**  
SP62H 6 volt stereo FM tuner **14.80**  
A1007 9 volt MW-AM **4.95**  
Sinclair 12/45 volt FM tuner stereo recorder for above **7.45**  
A1018 9 volt FM tuner in cabinet **13.95**  
A1005M (S) 9-12 volt Stereo decoder FM for above **7.50**  
106Z 12 volt Stereo decoder general purpose **6.50**

**Preamplifiers**  
Sinclair Stereo 60 Preamplifier **6.75**  
E1300 Cart/Tape Mic Inputs 9 volt **2.85**  
E1310 Stereo 3-30 mV mal cart 9 volt **4.75**  
FF3 Stereo 3 mV tape head 9 volt **4.95**  
3402 Stereo 5-20 mV Mag. cart. mains **5.95**  
EQ25 Mono 3-250 mV Tape/Cart/Flay 9 volt **1.95**

**Power Supplies Mains Input**  
(\*chassis-rest cased)  
470C6/7/9V 300 MA with ad'rs **2.25**  
P500 9 volt 500 MA **2.20**  
HC24R 3/6/7 1/2 amp. 400 MA stabilised **3.20**  
\*P11 2v. 1/2 amp. 3-30 **3.30**  
\*P15 28V. 1/2 amp. 12v **3.30**  
\*P1080 12V 1A 4.70 **4.70**  
\*P1081 45V 0.9A **7.80**  
P12 4 1/2-12V. 0.4-1 amp **7.15**  
SE101S 3/6/9/12V. 1 amp stabilised **12.75**  
P1076 3/4/6/7 1/2/9/12V. 1/2 amp **4.20**  
SE800A 1-1/5 VOLT 0-1/2 A stabilised **17.50**

### EMI SPEAKERS SPECIAL PURCHASE



13 in. x 8 in. chassis speakers (Carr./packing 30p ea. or 50p pr.)  
\*150 TC 10 watts 8 ohms twin cone **£2.20**  
EW 15 watt 8 ohms with tweeter **£5.25**  
350 20 watt 8. 15 ohm with tweeter **£7.80** each  
\*Polished wood cabinet **£4.80** carr., etc. 35p each or 50p pair.

### UHF TV TUNERS

625 line receiver UHF transistorised tuners UK operation. Brand new. (Post/packing 25p. each).  
TYPE C variable tuning **£2.50**  
TYPE B 4-button push-button (adjustable) **£3.50**

### PA-DISCOTHEQUE LIGHTING EQUIPMENT



Without doubt U.K.'s best range of modular and complete equipment. Lighting, mixing, microphones, accessories, speakers, amplifiers, lenses, etc., etc.  
FREE stock lists (Ref. No. 18) on request CALL IN AND SEE FOR YOURSELF at

**HENRY'S DISCO CENTRE, 309 EDGWARE ROAD. TEL. 01-723 6963**

EP27 Low Cost Seven Segment Led. Digit Height 1/2 inch. £1.35 pp 15p  
L450 RECHARGEABLE BATTERY 2v 400mA/HR 50p pp 15p.

**PHILIPS 12V FLUORESCENT INVERTOR** for 8w fluorescent tube. Supplies with instr. and tube **£3.50 p.o. 30p.**

**STC & ITT MINIATURE RELAYS**

5.50	150R	6v	2p	c.o.
3.30	180R	6/12v	2p	c.o.
3.30	185R	12v	2p	c.o.
4.70	1250R	12/55	2p	c.o.
7.80	1700R	18/24v	2p	c.o.
7.15	1800R	24v	4p	c.o.
12.75	2500R	18/24v	2p	c.o.
4.20	4000R	24v	2p	c.o.
17.50	BRAND NEW	60p	p.p.	15p

### TEST EQUIPMENT MULTIMETERS

Carr/packing 35p) £ p  
J4324 20kΩ/V with case 9.25  
J435 20kΩ/V with steel case 8.75  
J431 20kΩ/V with steel case 12.50  
J4317 20Ω/V with case 16.50  
J4341 33kΩ/V plus transistor steel case 10.50  
U4323 20kΩ/V plus 1kHz OSC with case 7.70  
IT2 20Ω/V slim type 5.95  
T.H.L33D (L33DX) 2kΩ/V Robust 7.50  
TP55N 20kΩ/V (Case £2) 8.25  
P105 20kΩ/V 6.25  
TW20S 20kΩ/V 10.00  
J431 20kΩ/V 11.25  
EP10KN 10kΩ/V 9.95  
S100TR 100kΩ/V plus transistor tester 22.50



### NEW REVOLUTIONARY SUPERTESTER 680R

£ p  
680R Multi-tester 18.50  
TTE10 AC Multivoltmeter 19.75  
TTE15 Grid dip meter 19.50  
440KHz-28MHz  
†TTE5 28 Range valve voltmeter 22.50  
†TTE20 RF Generator 120Hz-500kHz 18.95  
†TTE20 AF Generator 20Hz-200kHz 19.95  
\*HM350 in circuit transistor tester 19.50  
\*C3025 Deluxe meter 1-300MHz 6.95  
\*TT15 Compact transistor tester 14.75  
†G3-36 R/C osc. 20Hz-200kHz 19.75  
\*C3042 SWR Meter 5.75  
\*SE350A De-luxe signal tracer 12.95  
\*SE400 Mini-lab all in one tester 15.50  
CI-5 Scope 500,000KHz (carr. £1.00) 43.00  
\*C3043 5 CH F/A meter 1-300MHz 5.75  
R'stance sub box + P'st etc 2.40  
Capacitor 1/20p 2.10  
2 amp variable transformers (carr. £1) 6.55  
Radio actively counter 0-10r (carr. £1) 9.97  
Mains unit for above (carr. 50p) 3.75

### TAPE HEADS

Marriot XRPS/17 1/2 Track High **2.50**  
Marriot XRPS/18 1/2 Track Med **3.50**  
Marriot XRPS/36 1/2 Track Med. **5.00**  
Marriot XRPS/63 1/2 Track High **1.75**  
Marriot Erase Heads for XRSP 17/18/36 (XES11) **75p**  
Marriot BX12E 343 1/2 Track erase **75p**  
R/RPI Rec'd/Play 1/2 Track HR/ S'gle Trk Rec/Play **45p**  
Bogen Type UL290 Erase Miniature Stereo Cassette Rec/Play **35p**  
**2.25**

### EXCLUSIVE 5 WATT IC AMPLIFIERS

Special purchase 5 watt output 8-16 ohm load. 30 volt max. DC operation, complete with data. Price £1.50 each or 2 for £2.85.  
Printed Circuit Panels 50p.

### CALCULATORS

Sinclair Cambridge Kit £9.95 (inc VAT)  
Sinclair Cambridge (B1) £14.95 (inc VAT)  
Sinclair Memory £17.95 (inc VAT)  
Sinclair Scientific £19.95 (inc VAT)  
Sinclair Scientific Kit, £14.50 (inc VAT)

ALL PRICES SUBJECT TO 8% VAT

### SEND NOW FOR OUR FREE LIST NO. 36 FOR OUR COMPLETE RANGE OF OVER 10,000 SEMICONDUCTOR DEVICES AT NEW LOW PRICES.

TTL "7400 series" IC's from **16p** each  
Cosmos "4000 series" IC's from **27p** each  
Linear Op-Amps **40p** each  
Signonics Phase Lock IC's; RCA Linear IC's; TO3 Power Devices in PNP and NPN; BC107 and "BC range" **from 12p**  
Range of "OC" types  
Plastic Power Devices, Rectifiers, Zener Diodes up to 10 watts, Power Regulator IC's and many others.  
8 pin DIL Sockets **14p**  
14 pin DIL Sockets **15p**  
16 pin DIL Sockets **17p**  
705 IC Sockets **from 40p**  
24 pin DIL Sockets **£1-15**  
28 pin DIL Sockets **£1-25**

### NOMBREX TEST EQUIPMENT

**Model 35 Stabilised Power Supply**  
A short circuit proof power supply delivery up to 30 volts at 1 Amp. Built-in Volts and ammeters. **£23.60**

**Model 40 Wide Range Audio Signal Generator**  
A high stability signal generator using the low distortion Wien bridge principle. Covering 10Hz to 100 KHz in 4 ranges. Adjustable output from 1mV to 1V. Sine and Square wave output. **£25.90**

**Model 41 RF Signal Generator**  
Covering 150 KHz to 220 MHz in 8 ranges. Built in AF mod. Output up to 50mV. Crystal calibration facilities. Large linear scale with slow motion drive. **£35.00**

**Model 42 Wide Range RF Signal Generator**  
Covering 150 KHz to 300 MHz in 8 ranges. Highest range in harmonic. Built in AF mod. Output up to 50mV. Circular scale. **£17.50**

**Model 43 RC Bridge**  
Null indicating bridge for resistors and capacitors. Resistance range 10r to 10M ±2% at Centre Scale. Capacity range 10µF to 10µF ±2% Centre Scale except 1pF to 10pF Range ±5%. Power Factor Measurement 0-70% **£16.50**

**Model 44 Inductance Bridge**  
Measures 1pH to 100H in 4 ranges ±5% accuracy. Q measurement from 0.1-1,000 ±10%. **£27.50**

**Model 45 Direct Reading Frequency Meter**  
10Hz to 100 KHz in 4 ranges. Input from 10MV to 5V **£28.90**

All models except Model 35 are internally powered from 9V battery (extra). Carriage and packing all models 37p.

### NOW OPEN—SUPERMARKET

Come and browse round the new components supermarket at 404 Edgware Road. Bargains galore. Goodie Bags. Components, etc.

WATCH FOR FURTHER DEVELOPMENTS!

# Henry's Radio

Electronic Centres  
404-406 Electronic Components & Equipment 01 402 8381  
309 PA-Disco Lighting High Power Sound 01 723 6963  
303 Special offers and bargains store  
All mail to 303 Edgware Road, London W2 1BW  
Prices correct at time of preparation. Subject to change without notice. E. & O. E.  
Hi Fi and Electronics Centres Open 9 am - 6 pm