

PRACTICAL WIRELESS

NOVEMBER
1975

35p

extra
INSIDE

8-PAGE SUPPLEMENT No.2
SIMPLE HOME PROJECTS

TV

SOUND TUNER

for HI-FI SYSTEMS



fm tuner

DIGITAL READOUT



Also: UNIJUNCTION TESTER
TRIPLE RANGE WOBBULATOR

PRACTICAL WIRELESS

VOL. 51 NO. 7
ISSUE 825
NOVEMBER 1975

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

EDITOR

Lionel E. Howes, G3AYA

ASSISTANT EDITOR

Eric Dowdeswell, G4AR

ART EDITOR

Peter Metallii

TECHNICAL EDITOR

Sam Lewis B.Sc. (Eng.)

PRODUCTION & NEWS EDITOR

Colin R. Riches

TECHNICAL SUB-EDITOR

Bill Tull

TECHNICAL ARTIST

Alan Martin

SECRETARIAL

Susan King

ADVERTS MANAGER

01-634 4293 Roy Smith

CLASSIFIED ADVERTS

01-634 4301 Colin R. Brown

Published by IPC Magazines Ltd.,
Fleetway House, Farringdon Street,
London EC4A 4AD. Tel. 01-634 4444

Binders (£1.90) and indexes 30p (inc.
VAT) can be supplied by the Binders
Dept at Carlton House, 66-68 Great
Queen Street, London, WC2 5DD.

BACK NUMBERS

We regret that we are unable to supply
back numbers of Practical Wireless.
Readers are recommended to enquire
at a public library to see copies. Re-
quests for specific back numbers of
Practical Wireless and *Television* only
can be published in our CQ Column.

COPYRIGHT AND QUERIES

© IPC Magazines Limited 1975. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

We regret that we cannot answer technical queries by telephone nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.

Practical Wireless, November 1975

● NEWS & COMMENT

- 550 THE FUTURE OF AMATEUR RADIO—Editor's comments
- 551 NEWS . . . NEWS . . . NEWS . . .
- 561 HOTLINES on recent developments by *Ginsberg*
- 575 NEXT MONTH IN PRACTICAL WIRELESS
- 599 ON THE AIR—
- 599 Broadcast Bands, SW—*Derek Bell*
- 600 Amateur Bands—*Eric Dowdeswell, G4AR*
- 603 Broadcast Bands, MW—*Charles Molloy*
- 603 CQ! CQ! CQ! CQ! CQ!

● CONSTRUCTIONAL

- 552 DIGITAL READOUT SYSTEM FOR F.M. TUNERS,
Part 1—*Martin Oliver*
- 557 UNIJUNCTION TESTER—*R. Meredith*
- 565 AIDS TO IMPROVED RECEPTION, Part 2—*C. Heath*
- 570 IMPROVE YOUR BUDGET STEREO SYSTEM, Part 2—
B. Barnard
- 576 TV SOUND TUNER by *Alan C. Ainslie*
- 591 TTL WOBBLATOR—*J. G. Ransome*
- MINIATURE 2m EQUIPMENT—Part 3 of this article will be
published in the December issue

● OTHER FEATURES

- 562 GOING BACK, Equipment of yesteryear—*Colin Riches*
- 584 AUDIO 75—HARROGATE

**SPECIAL EXTRA! — 8-PAGE SUPPLEMENT —
SIMPLE HOME PROJECTS No. 2**

NOTE TO ADVERTISERS—If you wish to have advance information concerning components for P.W. projects, contact Dennis Brough on 01-634-4116 or Christine Dunn on 01-634-4293.

HUGE DISCOUNTS ON LEADING BRAND HI-FI

Full labour and material guarantees for 12 months

	LOW DEPOSIT CREDIT TERMS	Rec. Price	RSC Price
LINEAR 202 Amplifier		£45.40	£28.95
LINEAR 505 Amp 5 + 5w		£22.85	£19.95
AUDIO FIDELITY Model 60 Amp		£69.45	£53.95
WHARFEDALE LINTON Amp		£78.75	£57.95
LEAK 2100 Amplifier		£138.60	£107.95
LEAK 2002 Cassette		£161.46	£125.95
LEAK 2030 L/ Speakers		£109.38 Pr	£85.95
LEAK 2060 L/ Speakers		£96.95 Ea	£74.95
LEAK 2000 Tuner/ Amp		£223.96	£169.95
ROTEL RX152 Tun/ Amp		£109.39	£79.95
ROTEL RX202 Tun/ Amp		£124.43	£89.95
ROTEL RX402 Tun/ Amp		£169.93	£119.95
ROTEL RT224 Tuner		£72.50	£51.95
ROTEL RT324 Tuner		£92.50	£66.95
WHARFEDALE Denton I L/ Spkr		£39.10 Pr	£26.95
WHARFEDALE Denton 2XP L/ Spkr		£57.29 Pr	£41.95
WHARFEDALE Linton 3XP L/ Spkr		£79.69 Pr	£58.95
FANE Ambassador 35 L/ Spkr		£103.00 Pr	£79.95
FANE MARQUESS 30 L/ Spkr		£86.75 Pr	£57.50
FANE Mode One Spkr Kit		£29.90 Pr	£21.95
WHARFEDALE Linton II Kit		£33.45 Pr	£24.95

BASF CASSETTES


in Snap Pack CARR. FREE

LH CASSETTES		SUPER SM CASSETTES	
Rec. Price	RSC Price	Rec. Price	RSC Price
C60 98p	65p	3.00	4.99
C90 1.36	90p	3.99	6.99
C120 1.87	1.20	5.50	9.90
		1.94	1.46
		6.75	12.95

Also Shure Cartridges, Basf Tape, Koss H/Phones, etc. Prices of above correct at Sept. 1 1975

RSC G66 Mk II 6+6 WATT high quality STEREO AMPLIFIER

Controls: Bass, Treble, Vol. and Bal. 10 Transistors plus Diodes. Range 20-20,000 c.p.s. Bass Control ± 12db. Treble Control ± 13db. Selector switch for Crystal P.U. or Tape/Radio. 3—15 ohms. Attractive Black and Silver finished metal fascia plate. COMPLETE KIT INC FULLY WIRED PRINTED CIRCUIT and WIRING DIAGRAMS & INSTR OR FACTORY BUILT IN TEAK VENEERED CABINET as illustrated £18.50.



£14.99 Carr. 40p

AUDIOTRINE HIGH FIDELITY SPEAKERS

Plasticised Cone surround. "D" or "T" indicates Tweeter Cone providing extended frequency range up to 15,000 Hz. Impedance 3 or 8-15 ohms. PLEASE STATE CHOICE.

Exceptional performances at low cost.					
HF808T	8" 10W	£2.95	HF120D	12" 15W	£7.50
HF120	10" 10W	£2.95	HF126	12" 13W	£9.25
HF120	12" 15W	£8.95	HF128D	12" 15W	£9.95

AUDIOTRINE HI-FI SPEAKER SYSTEM

Consisting of matched 12in. 11,000 Gauss 15 Watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range. **£7.95** Carr. 45p. OR SENIOR IS WATT INCLUDING **£10.25** Carr. 50p. HF123 13,000 GAUSS SPEAKER



AUDIO FIDELITY FR1 SPKR KIT

Response 30 Hz-15 KHz. Rating 15 watts in sealed cabinet. Imp. 8-15 ohms. 8" Bass Unit with P.V.C. Cone surround for ultra low resonance. Pressure Tweeter. Printed Circuit. Inductive/Capacitive Cross-over. Damping Material, Screws. Terminal Panels.

£13.64 each Carr. Free **SPECIAL OFFER £18.50** Pair Carr. 50p



R.S.C. TRANSFORMERS, L.F. CHOKES & RECTIFIERS FULLY GUARANTEED.

Impregnated and Interleaved where necessary. Primaries 800-350v. 50c/a. Screened

ALL PRICES INCLUDE V.A.T.	TOP SHROUDED DROP-THROUGH TYPE	43.19
MIDGET CLAMPED TYPE	250-0-250v. 70mA 6.3v. 2a. 0.5-6.3v. 2a.	£2.60
250v. 60mA 6.3v. 2a.	250-0-250v. 100mA 6.3v. 3.5a.	£2.90
250-0-250v. 60mA 6.3v. 2a.	250-0-250v. 100mA 6.3v. 2a. 6.3v. 1a.	£3.20
FULLY SHROUDED UPRIGHT MOUNTING	350-0-350v. 80mA 6.3v. 2a. 0.5-6.3v. 2a.	£3.20
250-0-250v. 60mA 6.3v. 2a. 0.5-6.3v. 2a.	250-0-250v. 100mA 6.3v. 4a. 0.5-6.3v. 3a.	£4.35
250-0-250v. 100mA 6.3v. 4a. 0.5-6.3v. 3a.	300-0-300v. 100mA 6.3v. 4a. 0.5-6.3v. 3a.	£4.35
300-0-300v. 130mA 6.3v. 4a. C.T. 6.3v.	300-0-300v. 130mA 6.3v. 4a. 0.5-6.3v. 1a.	£4.35
1a. for Mullard 510 amplifier	suitable for Mullard 510 Amp	£5.20
350-0-350v. 100mA 6.3v. 4a. 0.5-6.3v. 3a.	350-0-350v. 100mA 6.3v. 4a. 0.5-6.3v. 3a.	£4.35
350-0-350v. 130mA 6.3v. 4a. 0.5-6.3v. 3a.	350-0-350v. 150mA 6.3v. 4a. 0.5-6.3v. 3a.	£5.20
425-0-425v. 200mA 6.3v. 4a. C.T. 5v. 3a.	FILAMENT OR TRANSISTOR POWER PACK	
425-0-425v. 200mA 6.3v. 4a. 6.3v. 4a. 5v. 3a.	Type: 12v. 1a. £1.10. 6.3v. 1.5a. £1.06. 6.3v. 2a. £1.10. 6.3v. 3a. £1.70. 6.3v. 6a. £2.60. 12v. 3a. or 24v. 1.5a. £2.60. 0.9-18v. 11a. £2.26. 0.12-25-42v. 2a.	
450-0-450v. 250mA 6.3v. 4a. C.T. 5v. 3a.		

AKAI TAPE UNITS

	Rec. Price	RSC Price
CS30D Spec. Price	£105.95	£69.95
CS34D	£137.50	£99.95
GXC39D	£186.50	£132.95
GXC39	£205.50	£144.95
GXC75D	£258.50	£181.95
GXC310D	£219.50	£154.95
CR81D	£113.00	£79.95
GXR82D	£162.50	£116.95
4000DS MK II	£169.50	£122.95

TURNTABLES

GOLDRING GL75 with G800 As above but with Plinth and Cover	£39.95	£51.95
PIONEER PL12D with Plinth and Cover	£49.95	£49.95
BSR MP60 with Plinth and Cover plus G850 Goldring Cartridge	£24.95	£24.95
GARRARD SP25 Mk. IV with Plinth and Cover plus G850 Cart.	£27.95	£27.95

PLINTH AND COVER



for Garrard SP25 or BSR MP60

£3.95 Carr. 50p

HI-FI SPEAKER ENCLOSURES

Simulated Teak finish. Sizes approx. Carr. 50p. per enc.

ME8 13 x 9 1/2 x 6 1/2 in.	£4.50
JEB 16 x 11 x 9 in.	£6.95

Both cut for 8in. speaker.




SE10 25 x 16 x 9 in.	£10.25
Cut for 10in. and Tweeter	
SE12 25 x 16 x 9 in.	£10.25
Cut for 12in. and Tweeter	

ALL R.S.C. PRICES INCLUDE VAT

TITAN GROUP/DISCO SPEAKERS


	Rec. Price	RSC Price
T12/35 12" 35w	£13.00	£10.95
T12/60 12" 60w	£20.00	£14.95
T12/100 12" 100w	£35.00	£27.95
T15/70 15" 70w	£27.00	£19.95
T15/100 15" 100w	£38.50	£27.95
T18/100 18" 100w	£42.50	£29.95



AUDIO FIDELITY MODEL 80 HIGH FIDELITY SPEAKER

A full range 8in. 10 watt unit for excellent sound quality, in suitable enclosure. Roll P.V.C. cone surround and long throw voice coil to achieve very low fundamental resonance of 30 c.p.s. Tweeter cone is fitted to extend high note response. Frequency range 25 Hz to 15 KHz. Gauss 10,000. Impedance 8-15 Ω. **£8.21** ea. **£9.25** pr.

MODEL 83 8" 15w. with parasitic Tweeter. **£7.99** ea. **£12.50** pr. Response 25 Hz to 15 KHz. Gauss 13,000 Imp 8-15 Ω.



DISCO SYSTEM 40 WATT



Consisting of Twin Turntable Console with Pre-amp and built-in Power Output. Sep. vol. controls for each Turntable. H/phone monitoring facilities. Sep. Bass and Treble controls. Mic. Vol. control. Neon Mains Indicator. Plus Pair 12" 25w Spkrs. in matching Rexine covered cabinets. **£99.99** carr. £3

Terms: Dep. £15.99 and 18 fortnightly paymts. £5.38. (Total £112.83)

AS ABOVE LESS SPEAKERS

Terms: Dep. £9.00 and 18 fortnightly payments £4.61 (Total £91.98) **£79.95**

MOBILE DISCO CONSOLE



MIC., JACK, PHONE JACK, MONITOR VOL. CONTROL, MONITOR SELECTOR DECK (1) Vol. Control, DECK (2) Vol. control, Mic. Vol. Control, Treble Control, Bass Control and ON/OFF Switch, Neon Indicator, Twin Turntables. **£59.95** Carr. £3

Terms: Dep. £7.95 and 18 fortnightly paymts. £3.33 Total £67.89.

POWER (SLAVE) AMPLIFIER 100 WATT



Suitable for use with above or other DISCO Consoles. **£39.95**

Also for increasing output of lower-powered Amplifiers. Terms: Dep. £5.11 and 8 mthly payments of £5-11 (Total £45-99) carr. £1

SELENIUM RECTIFIERS F. W. (Bridged)

All 6/12v. D.C. output. Max. A.C. input 18v.

1a. 45p. 2a. 57p. 3a. 65p. 4a. 85p. 5a. 11.15.	
--	--

L.F. CHOKES

160mA, 7-10H. 250 Ω	£1.25
100mA, 10H. 200 Ω	£1.10
60mA, 10H. 400 Ω	41p.

AUTO (STEP UP/STEP DOWN) TRANSFORMERS

0-110/120v. 200-230-250v. 50-80w.	£2.90
150watts	£5.20.
250watts	£6.37.
500watts	£9.84

CHARGER TRANSFORMERS

0-9-15v. 11a. £2.03. 21a. £2.26. 3a. £2.32. 5a. £2.84. 6a. £3.19. 8a. £3.48	
---	--

OUTPUT TRANSFORMERS

Standard Pentode 5000 to 3 ohm, or 7000 ohm to 3 ohm £1.12. Push Pull 8 watts EL84 to 3 ohm or 15 ohm £1.68; Push Pull 10-12 watts 6v. 6 to 3 ohm or 15 ohm £2.61; Push Pull 10-12 watts to match 6v. 6 to 3, 5, 8 or 15 ohm £2.72. Push Pull EL84 to 3 or 15 ohm 10-12 watts £2.61; Push Pull Ultra Linear for Mullard 510 etc. £4.35.

RSC 100 WATT DISCO SYSTEM

AT FANTASTIC LOW PRICES!

50 WATT SPEAKER

50 WATT SPEAKER

TWIN TURNTABLE WITH PRE-AMP. and POWER AMPLIFIER Complete with lid

HEADPHONES MICROPHONE

Units listed below

(a) DISCOMASTER TWIN TURNTABLE CONSOLE with integral 100W amplifier

(b) PAIR OF HI-FI HEAD PHONES

(c) MATCHING 'MIKE'

(d) PAIR 50 WATT SPEAKERS Black Rexine covered Cabinets Size approx. 18" x 18" x 8"

(a) (b) (c) & (d) Carr. £3-00

£169-99

RSC TDI DISCO CONSOLE

Incorporating twin BSR MP80 type turntables and Sonolone or Aco's Cartridges with diamond styl. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate input for 'mike' with vol. control. Black Vynide covered Cabinet with lid. Or DEP. £9-95 and 18 fortnightly pymts. £5-11 (Total £101-98) Carr. £1-60

£89-95

Carr. £1-60

DEP. £19-99 & 18 fortnightly payments of £9-75 (Total £195-49).

STEREO VERSION

Of Above System

Or DEPOSIT £24-95 and 18 fortnightly pymts. £11-19 (Total £228-87) Carr. £3-50

£209-95

TD25 STEREO VERSION OF ABOVE

Terms DEPOSIT £20 and 18 fortnightly payments £8-71 (Total £140-78) Carr. £1-60

£125-00

DISCOMASTER TWIN TURNTABLE POWER CONSOLE £119-95

Twin McDonald MP60 type turntables. Sonolone or Aco's cartridges with diamond styl. Facilities as TDI Console but with built-in 100 watt Power Amp. puffer, complete with lid. Or Dep. £18-95 and 18 fortnightly pymts £8-73 (Total £185-99)

STEREO VERSION £155 or DEPOSIT £25 and 18 fortnightly pymts £8-80 (Total £174-40) Carr. £3

R.S.C. COLUMN SPEAKERS IDEAL FOR VOCALISTS AND PUBLIC ADDRESS

All types 15 Ohms covered in Vynide & Vynair

TYPE C132 40-50 WATTS £27-95

Incorporating two exceptionally efficient 13" x 8" speaker units. Dep. £3-95 and 8 monthly payments £3-50 (Total £31-95) Carr. 65p

TYPE C8 70 70 WATTS Fitted three 12" 26 watt Highly sensitive high freq speakers with high power voice coils. Size approx. 54" x 14" x 11". Dep. £5-11 & 8 mthly pymts. £5-11 **£39-95** (Total £46-99) Carr. 85p

FANE ULTRA HIGH POWER SPEAKERS & KITS

All power ratings are R.M.S. continuous. 2 YEARS' GUARANTEE High flux ceramic magnets. ALL CARRIAGE FREE.

'POP' 100	'POP' 60	'POP' 50
18" 100Watt 14,000 gauss 8/15Ω	15" 60 Watt 14,000 gauss 8/15Ω	12" 50 Watt 13,000 gauss 8/15 ohm
£38-95	£22-95	£14-95
Dep. £8-95 and 8 monthly payments £4-60 (Total £43-75)	Dep. £3-95 and 8 monthly payments. £2-87 (Total £28-91)	Dual Cone. Terms for pairs Dep. £3-90 & 8 mthly pymts £4-24. Total £37-82 PAIR SUITABLE ALL PURPOSES

FOR BASS GUITAR, ELECT. ORGAN, ETC.

ALL RSC PRICES INCLUDE VAT

INTEREST on Credit Purchases REFUNDED settled in 3 months

SUPER MINSTREL 10 W GUITAR AMP.

Incorporating Tremolo and 10" Speaker. Output 10 watts R.M.S. Continuous. 3 Jack Inputs for Microphone and Instrument. Mains Neon Controls: Volume, Tone, Tremolo Speed, Tremolo Intensity.

Terms: DEPOSIT £7-73 and 8 monthly payments £3-40 (Total £34-93) Carr. free

£29-99

FANE CRESCENDO SPEAKERS

FULL RANGE AVAILABLE AT ALL BRANCHES



FAL MAESTRO COMBINED 80W AMP. AND 12" SPEAKER £55-95

For Lead Guitar, Mic, Gram, Radio, Tape (Not for use with Bass Instruments) Inc. 3 inputs and 2 vol controls plus Treble & Bass TREMOLO with associated controls. Attractively finished in black with all-ferrous fascia. Compact size Fitted carrying handle. Deposit £9-25 and 8 monthly payments £6-76 (Total £63-33)

PHANTOM 50 COMBINED AMPLIFIER AND SPEAKER £59-95

Rating 50 watts. 3 inputs, 2 vol. controls, Bass, Treble, Presence

Dep. £7-95 & 8 mthly. pymts. £7-48 (Total £67-79) Carr. £1-50



FAL PHASE 50-4 AMPLIFIER 50 WATT

Solid state. 4 Sep. controlled inputs Plus master vol. control. Ind. Bass and Treble Controls. Protection against serious o/p overloading. O/p for spkrs. 8 to 15 ohms. Size 17" x 7" x 7 1/2". 200-250v. A.C. mains. O/p 50w Music. Deposit £8-80 & 8 mthly. payments. £5-75. Total £54-60 Carr. Free. **£48-60**



REGENT 50X 50 WATT AMP.

A powerful high quality unit for lead, rhythm guitar, vocalists, gram, radio, tape. 50w Peak O/P rating. Not for Bass Guitar.

★ Two Fane heavy duty high flux 12in. spkrs.

★ Four Jack inputs and two Volume Controls for instant use of up to four pick-ups or "mikes". Bass and Treble controls.

Send S.A.E. for leaflet. Credit Terms: Deposit £9-95. & 18 fortnightly payments of £4-15 (Total £84-65) Carr. £2-50

REGENT 50B for Bass Guitar and general purposes. Or Dep. £9-00 & 18 fortnightly payments £4-81 (Total £81-98) Carr. £2-50

FAL DISCO PRE-AMPLIFIER

Monitoring, Mic, Jack & Tape inputs. Independent Vol. Control. Std. 200-250v A.C. Mains operation

£18-50

I.S.E. JINGLE MACHINES FS8000

Employing Standard 8 Track Cartridge Or Dep. **£37-95** £4-85 & 8 monthly pymts £4-85 (Total £43-65)

FAL HEAVY DUTY CABINETS

Black Vynide covered. Fitted Protective Corner Pieces. Cut for various Speaker Combinations. Carr. £1 each unit.

SE1 24" x 24" x 12"	£20-95
SE2 24" x 24" x 12"	£20-95
SE3 36" x 24" x 12"	£28-95
SE4 36" x 24" x 12"	£28-95
SE5 30 1/2" x 28 1/2" x 12"	£28-95
SC1 32" x 16" x 10"	£18-95
SC2 47" x 22 1/2" x 10 1/2"	£29-95



LIQUID WHEEL PROJECTORS £24-75

from

'SOUND TO LIFE' SYSTEM

PULSAR special price complete kit **£99-95**

Dep. £11-48 and 18 fortnightly pymts. £6-74. (Total £114-80). Super 8L Unit. 1000 watt per channel. Manual override buttons, 2 spotbanks with 8 bulbs (3 sep. colours) 5 yd. and 10 yd. leads, 11ft plug. Units sold sep.

FAL SOUND-TO-LITE UNIT £21-60

3-WAY SPOT BANK

Excluding Bulbs Each **£16-20**

COMPLETE SYSTEM Carr. **£55**

Incl. 2 Spotbanks and bulbs.

New Branches at YORK, BOLTON, DONCASTER, and PRESTON

OPEN ALL DAY SATURDAYS (5 Day Week)

BRADFORD 10 North Parade (Closed Wed.). Tel. 25349

BOLTON 23 Deansgate (Closed Wed.). Tel. 33512

BIRMINGHAM 30/31 Great Western Arcade. Tel. 021-236 1279 (Closed Wed.).

COVENTRY 17 Shelton Square, The Precinct. Tel. 25983

DERBY 97 St. Peter's Street. (Closed Wed.). Tel. 41361

DARLINGTON 19 Northgate (Closed Wed.). Tel. 68043

DONCASTER 3 Queensgate, Waterdale Centre. (Closed Thurs). Tel. 63069



Barclaycard and Access accepted

All items subject to availability. Prices correct at 1.9.75 E. & O.E.

EDINBURGH 101 Lothian Rd. (Closed Wed.). Tel. 229 9501

GLASGOW 326 Argyle St. (Cl'd Tues.). Tel. 248 4158

HULL 7 Whitfriargate (Closed Thurs.). Tel. 20505

LEICESTER 32 High Street (Closed Thurs.). Tel. 56420

LEEDS 5-7 County (Mecca) Arcade, Briggate (Closed Wed.). Tel. 458252

LIVERPOOL 73 Dale St. (Closed Wed.). Tel. 236 3573

LONDON 238 Edgware Road, W.2. (Closed Thurs.). Tel. 723 1629

MANCHESTER 60A Oldham Street (Closed Wed.). Tel. 236 2778

MIDDLESBROUGH 108 Newport Road (Closed Wed.). Tel. 47096

MAIL ORDERS & EXPORT ENQUIRIES TO: AUDIO HOUSE, HENCONNER LANE, LEEDS, 18. Tel: Pudsey (09785) 77681.

MAIL ORDERS MUST NOT BE SENT TO SHOPS

TERMS C.W.O. or O.D. No O.D. under £1. POSTAGE 40p PER ORDER OR AS QUOTED. TRADE SUPPLIED S.A.E. REQUIRED FOR LEAFLETS OR WITH ENQUIRIES.

NEWCASTLE UPON TYNE 24 Newgate Shopping Centre (Closed Wed.). Tel. 21469

NOTTINGHAM 19/19A Market Street. Tel. 40868

PRESTON 41 Friargate Walk, St. George's Shopping Prec. Tel. 51978

SHEFFIELD 13 Exchange Street (Castle Mkt. Bldg.) (Closed Thurs.). Tel. 20716

STOCKPORT 8 Little Underbank (Closed Thurs.). Tel. 480-0777

SUNDERLAND 5 Market Sq. (Closed Wed.). Tel. 70573

YORK 5 CHURCH ST. OPENS OCTOBER

TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious men to move up into higher paid more secure jobs in the field of electronics - now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

- Telecommunications Technicians
- Radio, T.V. Electronics Technicians
- Technical Communications
- Radio Servicing Theory
- Radio Amateurs
- Electrical Installation Work
- Also MPT Radio Communications Certificate

Diploma Courses

- Colour T.V. Servicing
- Electronic Engineering & Maintenance
- Computer Engineering and Programming
- Radio, T.V. and Audio, Engineering & Servicing
- Electrical Engineering, Installations & Contracting

Other Career Courses

A wide range of other technical and professional courses are available including GCE.

FREE BOOK

Post this coupon or 'phone today for free ICS careers guide.

Name _____
 Address _____

 Age _____

ICS

To ICS, Dept. S31, Intertext House,
 London SW8 4UJ
 or telephone 01-622 9911 (all hours)

GLOCK COMPONENTS

PW Clock Constructors—
 See starred ★ Items

- ★AY51224 4 digit clock IC £4.25
- ★DL704E 0.3" Red Common Cathode LED—Pin-for-pin direct replacement for MAN3640 **only 85p**
- MAN3M 0.13" Red CC LED 48p FND500 0.5 Red CC LED £1.50
- ★CRYSTAL TIMEBASE KIT: Will provide stable 50 cps for clock IC's, incl. AY51224, giving time accurate to a few seconds a month; contents: small PCB, 32,768 kHz Xtal, 3 CMOS IC's, trimmer, C's, R's, IC sockets £6.40
- 6 DIGIT ALARM CLOCK KIT—contains all components necessary, except for the case, to build a 6 digit alarm clock with bleep alarm, snooze function, intensity control, 0.3" LED's £19.86
- ★SOLDERCON IC PIN SOCKETS
 The sensible method for lowest cost sockets for IC's, displays, CMOS, TTL (nylon supports available if required. Samples encl. with any pin order) Strip of 100 for 50p 400 for £2. 1000 for £4. 3000 for £10.50.
- LSI Sockets (Soldercon Pins with nylon supports) 24, 28 & 40 pin: 30p ea. 20 way colour-coded Flexible Flat Cable £1 per metre; £8.50 per 10m.

RCA CMOS PRICES ARE DOWN

Widest stock range in UK—at the new manufacturers' 1 off prices.

CD4000 0.17	CD4021 0.83	CD4039 7.47	CD4057 20.35	CD4082 0.18
CD4001 0.17	CD4022 0.79	CD4040 0.88	CD4059 10.64	CD4085 0.57
CD4002 0.17	CD4023 0.17	CD4041 0.69	CD4060 0.92	CD4086 0.57
CD4006 0.97	CD4024 0.64	CD4042 0.69	CD4061 16.43	CD4093 0.66
CD4007 0.17	CD4025 0.17	CD4043 0.83	CD4062 7.33	CD4095 0.86
CD4008 0.79	CD4026 1.42	CD4044 0.77	CD4063 0.90	CD4099 1.50
CD4009 0.46	CD4027 0.46	CD4045 1.15	CD4066 0.58	MC14501 0.32
CD4010 0.46	CD4028 0.74	CD4046 1.10	CD4068 0.18	MC14502 0.65
CD4011 0.17	CD4029 0.94	CD4047 0.74	CD4069 0.18	MC14508 4.20
CD4012 0.17	CD4030 0.46	CD4048 0.46	CD4070 0.18	MC14510 1.26
CD4013 0.46	CD4031 1.81	CD4049 0.46	CD4071 0.18	MC14511 1.95
CD4014 0.83	CD4032 0.88	CD4050 0.46	CD4072 0.18	MC14518 1.03
CD4015 0.83	CD4033 1.14	CD4051 0.77	CD4073 0.18	MC14520 1.03
CD4016 0.46	CD4034 7.83	CD4052 0.77	CD4075 0.18	MC14528 0.87
CD4017 0.83	CD4035 0.97	CD4053 0.77	CD4076 1.27	MC14553 4.07
CD4018 0.83	CD4036 7.47	CD4054 0.95	CD4077 0.18	MC14566 1.21
CD4019 0.46	CD4037 0.78	CD4055 1.08	CD4078 0.18	MC14585 1.45
CD4020 0.92	CD4038 0.88	CD4056 1.08	CD4081 0.18	MM74C14 1.16


RCA 1975 CMOS Databook: Pin-Outs, 400 pages of data, 200 pages of circuits, applications and use £2.30 (No VAT) + 37p p & p.

ADD VAT at 8% (higher rate does not apply to any of above).
 15p p & p on orders under £3—Despatch is 1st Class Post BY RETURN!
 Price List sent FREE with any order, or on request (an see helps).
 Official orders welcomed (written or phoned)—Univs, Polys, Govt. Cos. etc.
 Export orders: No VAT, Add 35p (Europe) 70p (overseas) for Air Mail p & p.

SINTEL, 53n Aston Street, Oxford. Tel: 0865 43203

QUALITY STEREO SOUND

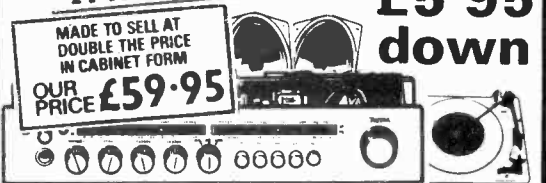ALMOST **1/2 PRICE OFFER!** SOLENT AUDIO SYSTEM
£5.95 down



*Stereo Tuner Amplifier chassis with AM/FM radio covering long medium short and Stereo FM wavebands. Separate Base and Treble controls. 30 watts total power output (frequency response 25-20,00 Hz) Tape record and playback facilities. Dimensions 18" x 8 1/2" x 3 1/2". The very latest BSR automatic record deck with cue and pause control. Two matching elliptical speaker units.

Order early limited stocks available cash price £59.95. Credit Sale £5.95 deposit 9 monthly payments of £7.00 (Total Credit price £68.95). P. & P. £3.00. Send £8.95 today.

Chassis only available for cash at £42.00.

Full 12 months Guarantee.

CALLERS WELCOME.

Stereo headphones supplied with every complete order.
LEWIS radio PW/11/75 100 CHASE SIDE SOUTHGATE
 LONDON N14 5PL Telephones: 01-882-1644

BI-PRE-PAK

The people for component bargains




Makers of
Stirling Sound
audio equipment

ORIGINATORS OF PRE-PACKED COMPONENTS IN BRITAIN—AND STILL LEADING!

AUDIO MODULES—today's most challenging values!

POWER AMPS

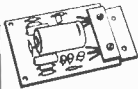

SS103
Compact I.C. amp. 3 watts R.M.S. Single channel (mono). On P.C.B. size 3½" x 2". Needs 10-20V supply. **£1.75**

SS103-3
Stereo version of above. (Two I.Cs.) **£3.25**

NEW! SS105 Mk. 2
A compact all-purpose power amp. Size 3½" x 2". Useful 5W output (mono) into 3Ω using 12V. Two in bridge formation give 20W from 12V, for P.A. etc. **£2.25**



SS110 Mk. 2
Similar in size to SS105 but will give 10W output into 4Ω using 24V (mono). Two in stereo give first-class results, suitable for many domestic applications. **£2.75**

NOW—SS120 20W r.m.s. into 4Ω using 34V. 3½" x 2" **£3.00**

SS140*
Beautifully designed. Will give up to 40W R.M.S. into 4Ω. Excellent S.N.R. and transient response. Fine for P.A., disco use, etc. Operates from 45V DC. Two in bridge formation will give 80W R.M.S. into 8Ω. **£3.75**

PRE-AMP/CONTROL MODULES

SS100
Active tone control unit to provide Bass and Treble cut and lift. With full instructions (stereo). **£1.60**

SS101
Pre-amp for stereo ceramic cartridges, radio and tape. **£1.60**

SS102
Pre-amp for low-output stereo magnetic cartridges, radio and tape. **£2.25**


BUILD A STEREO F.M. TUNER

SS201
Front End assembly. Ganged tuning with well engineered slow-motion geared drive in robust housing. A.F.C. facility. Requires 6-16V. Excellent sensitivity. 88-108MHz. **£6.25**

SS202
I.F. Stage (with I.C.). Designed to use with SS201 uses I.C. Carefully checked before despatch. **£5.25**

SS203
Stereo Decoder. Designed essentially for use with SS201 and SS202, this excellent decoder can also make a stereo tuner of almost any single channel FM tuner. Supplied ready aligned. A.L.E.D. can easily be fitted. **£5.62**

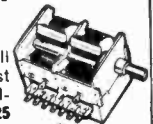Above 3 units together special price **£12.12**



SPECIAL OFFERS

LM 380 AUDIO IC
(Marked SL60745). Brand new and to spec. 3 watts R.M.S. out. With date. **£1.00**

2X SN7490. Brand new I.C. to spec. decade counters. **£1.00***

3XSN 7400 Quad 2 input Nan gate ICs. **50p***

SUNDRY

P.1 PAK—Approx. 170 short-lead semiconductor and components. PNP, NPN, diodes, rectifiers, etc. on PCBs. At least 30% factory marked. Some data supplied. **50p***

UHF 625 line tuner, rotary. **£2.50**
Rev Counter (for cars) (8%). **£1.00***
Books by Bernard's Publications. Newnes-Butterworth's etc. No VAT.

THE FREE CATALOGUE

New edition better than ever. It's your's for free and well worth getting—only please send large S.A.E. with 10p stamp if we have to post it to you.

TERMS OF BUSINESS:

VAT at 25% must be added to total value of order except for items marked * or (8%), when VAT is to be added at 8%. No VAT on overseas orders. POST & PACKING add 22p for UK orders unless marked otherwise. Minimum mail order acceptable—£1. Overseas orders, add £1 for postage. Any difference will be credited or charged. PRICES subject to alteration without notice. AVAILABILITY All items available at time of going to press when every effort is made to ensure correctness of information.

BI-PRE-PAK LTD

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DZ.
TELEPHONE: SOUTHEND (0702) 46344.

WRITE ORDER SEPARATELY AND ATTACH COUPON IF REQUIRED

NEW RANGE TRANSISTOR & COMPONENT PACKS

TP SELECTION

TP5 20 Transistors, PNP Germanium, Red Spot A.F.

TP6 20 Transistors, PNP Germanium, White spot RF.

TP7 1 2N174 150w 80Vce Power Transistor, with mounting assembly.

TP19 100 diodes, mixed Germanium, Gold-bonded, etc. Marked Uo.

TP23 Twenty NPN Silicon uncoded T05. Similar to BFY50/2, 2N696, 2N1613, etc. Complementary to TP24.

TP24 Twenty PNP Silicon, uncoded T05. Similar to BFY64, 2N2904/5.

TP26 8 power diodes 400V, 1.25A Silicon FST 3/4.

UT SELECTION

UT1 50 PNP's Germanium, AF & RF.

UT2 150 Germanium diodes, min. glass.

UT4 100 Silicon diodes, min. glass, similar to IN914, IN916.

UT5 40 250mW Zener diodes OAZ24 range; average 50% good.

UT7 30 Silicon rectifiers 750mA, mixed voltages, Top Mats, etc.

UT9 40 NPN Silicon planers. Similar to 2N3707-11 range. Low noise amps.

UT12 25 2N3702/3 Transistors, PNP Silicon, Plastic to 92.

CP SELECTION

CP1 Mixed bag of capacitors—Electrolytic, Paper, Silver Mica (Approx. 150—sold by weight).

CP2 200 (approx.) Resistors, various types, values, watts. (Sold by weight.)

CP3 40 Wire wound resistors, mixed.

CP4 12 pots—pre-set, w/wound, carbon, dual, with/without switches—all mixed.

CP7 Heat sinks, assorted. To fit SO-Z (OC72) TO-1 (AC128), etc.

ALL ABOVE PACKS—60p EACH. TP Tested & Guaranteed; UT Untested, unmarked; CP Components.

CAPACITOR DISCHARGE IGNITION KIT

Simple to assemble and fit. Improves car performance, saves on fuel. P&P 30p. **£7.50***

BI-PRE-PAK X-HATCH GENERATOR Mk.2

Four-pattern selector switch 3" x 5½" x 3"
Ready-built and tested
In kit form **£9.93**
£7.93

Please add 35p for postage and packing
Is invaluable to industrial and home user alike. Improved circuitry assures reliability and still better accuracy. Very compact, self-contained. Robustly built. Widely used by TV rental and other engineers. With reinforced fibreglass case, instructions, but less batteries. (Three U2 type required.)

TV SIGNAL STRENGTH METER

Complete kit as described in "Television" **£19.50** plus 40p* for P&P

SS300 POWER SUPPLY STABILISER

Add this to your un stabilised supply to obtain a steady working voltage from 12 to 50V for your audio system, workbench etc. Money saving and very reliable. **£3.25***

PLASTIC POWER TRANSISTORS

40 WATT SILICON*

Type	Polarity	Gain	VCE	Price
40N1	NPN	15	15	20p
40N2	NPN	40	40	30p
40P1	PNP	15	15	20p
40P2	PNP	40	40	30p

90 WATT SILICON

Type	Polarity	Gain	VCE	Price
90N1	NPN	15	15	25p
90N2	NPN	40	40	35p
90P1	PNP	15	15	25p
90P2	PNP	40	40	35p

If you prefer not to cut coupon out, please mention PW10 when writing

To BI-PRE-PAK, 224-226 WEST RD., WESTCLIFF-ON-SEA, ESSEX

Please send

for which I enclose Inc. V.A.T.

Name

Address

PW10

AERIALS

Telescopic, 15-120cm £1.50
 Telescopic, H & V Swivel, 15-80cm £2.25
 Indoor FM antenna, Compact design £2.45
 Loft mounting FM dipole antenna £2.45

CAPACITANCE SUBSTITUTION BOXES

Single control for easy selection
 0001, 001, 0022, 01, 022, 047, 0.01, 0.22 £2.35

KEYNECTORS

Rapid connect to mains. Built-in piano switches, neon & 13A fuse £3.50

MULTIMETERS

Vdc-10, 50, 250, 1,000. Vac-10, 50, 250, 1,000. Idc-100mA. R-150k £4.95

PRINTED CIRCUIT MTS

Contain all items necessary to produce printed circuits £3.95

SIGNAL INJECTORS

Audio through video signals, ideal -servicing amplifiers, radio & tv £4.25

TEST SWITCHES

5 miniature push to test switches £1.00

VERNIER DIALS

Positive logging to 1/10th of a degree, 8:1 ratio, clear scales £2.45

VU METERS

Callbrated -20 to +3, 0-100%, ideal -recording level or power output £3.40



AUDIO PRODUCTS

AUDIO LEADS

5p din plug to 5p din plug, 1.5m lead £1.20
 2p din plug to 2p din socket, 10m lead £1.45
 5 pin din plug to 2 phono plugs £1.20

BIB HI-FI ACCESSORIES

GROOV-KLEENS-Ref. 42 £1.95
 1/2" TAPE EDITING KITS-Ref. 23 £1.50
 CASSETTE EDITING KITS-Ref. 24 £1.65
 CASSETTE HEAD CLEANERS-Ref. 31 £0.65
 HI-FI STEREO TEST CASSETTES-Ref. 53 £2.15

CASSETTE WALLETS (HOLD 6)-Ref. 39

£0.90
CASSETTE HEAD DEMAGNETISERS
 Shaped pole piece-saves time £3.65

EARPHONES

Stethoscope style, 8 ohm dynamic £1.20
 Crystal earphone with lead & plug £0.65
 High resistance, 2000 ohm headphone £3.20

FOOT SWITCHES

Push on-push off. Anti skid base £2.70

INTERCOMS

2-station, ideal for the home-baby alarm, office, with cable & staples £6.35

Door-telephone 'Answer door before opening' Completely weatherproof £9.95

MICROPHONES

Dynamic, remote start/stop, 200 ohms, 100-10kHz, 6mV output £2.15

MINIATURE TRANSISTOR MODULES

Microphone pre-amplifier £2.45
 Power amplifier £2.70

(Each plug-in with mounting socket)

STEREO HEADPHONES

Supert stereo listening in comfort and privacy, 30-15kHz, 8 ohms £4.85

STEREO HEADPHONE JUNCTION BOXES

3 way switch unit selects phones only, speakers only or both £2.30

STEREO PRE-AMPLIFIERS

In: 3-30mV, Equilise: RIAA. Out: 200-800mV flat, 20-20kHz, Supply: PP3 £7.30

SPEAKERS

Miniature, 75mm dia, 8 ohms £0.95

TWEETERS & CROSSOVERS

Super Tweeters, 8 ohms, c/f 7kHz, For systems up to 30W RMS £4.60

Cone Tweeters, 8 ohms, c/f 3kHz, For systems up to 10W RMS £2.35

Crossovers, 8 ohms, c/f 800, 3kHz, 7kHz, For systems up to 40W RMS £5.85

Crossovers, 8 ohms, c/f 3kHz, For systems up to 15W RMS £2.10

BATTERY ELIMINATORS

Miniature AC adaptor-provides 9V at 50mA DC output from mains £4.35

POWER SUPPLY UNITS

P1 Switchable between 6 & 9V (200mA) Ideal-most small radios, etc. £4.85

P2 Switchable to provide 6, 7.5, 9V at 400mA £7.15

TRANSFORMERS

Mains (miniature), 2 secondaries 0-6V, 0-6V RMS, 280mA £2.70

p-12V, 0-12V RMS, 150mA £2.70

Mains (sub miniature) 6-0-6V RMS, 100mA £1.45

12-0-12V RMS, 50mA £1.45

PERSONAL RADIOS

Phillips RL077 with earphone & case £6.00
 Phillips RL020 with earphone & case £7.50



TOOLS

COMBINATION TRY & MITRE SQUARES

Cabinet/Chassis/P.C.B. work. One tool combining Try & Mitre Square, Depth, Height and Marking Gauges, 300mm/12in Rule, Spirit Level/Plumb & Steel Scriber £2.35

HAND DRILLS

Laytool compact, 5/16" chuck, 8oz totally enclosed, S/L bearings £3.99

SOLDERING IRONS

Antex 25W, X25, 240V, Low leakage, 1/8" interchangeable long life bit 3/32", 1/8", 3/16" spare bits-each £2.05

X25 Elements £1.10

Stands, ST3, High grade base, spring, sponges, accomodation-spare bits £1.00

SOLDER - in handy Bib dispenser £0.43

WIRE STRIPPERS & CUTTERS

Bib BB, 8 gauge selector, automatic opening, easy grip handles £0.85

PRICES INCLUDE VAT

KITS Hi-Fi Cabinets TEAK Veneer

P & P 75p
 17" x 10" x 7 1/2" cut for 8" & Tweeter £5.95
 12" x 8" x 4 1/2" cut for 6 1/2" or 7" x 4" £3.75
 18" x 12" x 7 1/2" cut for 10" or 8" & Tweeter £5.95
 Complete with Instr. & Hardware.

MICROPHONES P & P 20p

UD 130 Cardoid Dyn. 50-50,000 C/S Dual Imp. £7.40
 UD 147 Cardioid Dynamic £9.50

MULTIMETER Model ITI-2

20,000 O.P.V.
 AC 0-10, 50, 100, 500, 1000 DC 0-5, 25, 50, 250, 500, 2500 DC Current 0/50 uA 2.5, 250 Resistance 0/6k Ohms, 6 Meg Ohms DB -20 to +22 Capacitance 10pF, 0.1uF, 0.1uF £6.75 P & P 20p

PANEL METERS P & P 15p

The following 2" range measure 2 1/2" x 1 1/2" x 1 1/2" deep

1 1/2" diam. hole in panel read.
 ME0 0-50 uA, ME7 0-100 uA, ME8 0-500 uA, ME9 0-1 mA, ME10 0-5mA, ME11 0-10 mA, ME12 0-50 mA, ME13 0-100 mA, ME14 0-500 mA, ME15 0-1 amp, ME16 0-50 volts AC, ME17 0-300 volts AC, ME18 "S", ME19 "VU".
FULL SCALE AT £3.00 EACH

JACK PLUGS P & P 12p per 12

Screened Chrome Plastic Body
 2.5mm 13p
 3.5mm 19p
 Standard Mono 25p
 Standard Stereo 43p

SPEAKERS Chassis P & P 40p

(Tweeter 20p)
 ELAC 8" 8 watt HF Cone £2.85
 ELAC 8" 15 watt Long Throw £3.95
 ELAC 10" 10 watt £3.12
 ELAC 10" 10 watt HF Cone £3.95
 FANE 7" x 4" Cer. Mag. £1.75
 2 1/2" Tweeters £0.75

CARTRIDGES & STYLII P & P 20p

Goldring (inc Styl) (D/Diam)
 G800 £4.50 £1.95
 G850 £3.50 £1.95
 G800E £9.00 £4.95

SHURE M44/7 £5.50 £4.30

M55/E £6.50 £3.45
 M75/EJII £9.75 £6.85
 M75/ED £11.50 £8.90

CASSETTES & TAPES

EMI Sound Hog C60 C90 C120
 Compact Low 39p 48p 58p
 Noise 32p 41p 50p
 BASF LH 55p 75p 97p
 LH Super 72p 90p £1.00
 P & P 25p per order 10 or more P & P FREE

Reel to Reel Recording Tape

Std. Play Long Play
 5" 59p 74p
 5 1/2" 69p 90p
 7" 85p £1.20p

Up to 4 P & P 25p. Thereafter 10p
 Prices correct at time of going to Press.

Venusound Ltd Send 10p for Brochure!
 63 Whitworth Street Manchester 1
 Telephone 061-236 3921

YOUR CAREER in RADIO & ELECTRONICS ?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam.; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study College specialising in electronics subjects only. Fulltest details will be gladly sent without any obligation.

To: British National Radio & Electronics School, Dept W.C. 115 P.O. Box 156, Jersey, C.I.

Please send FREE BROCHURE to


NAME Block
 ADDRESS Caps.
 Please

BRITISH NATIONAL RADIO AND ELECTRONICS SCHOOL




I.L.P. (Electronics) Ltd

SHEER SIMPLICITY!

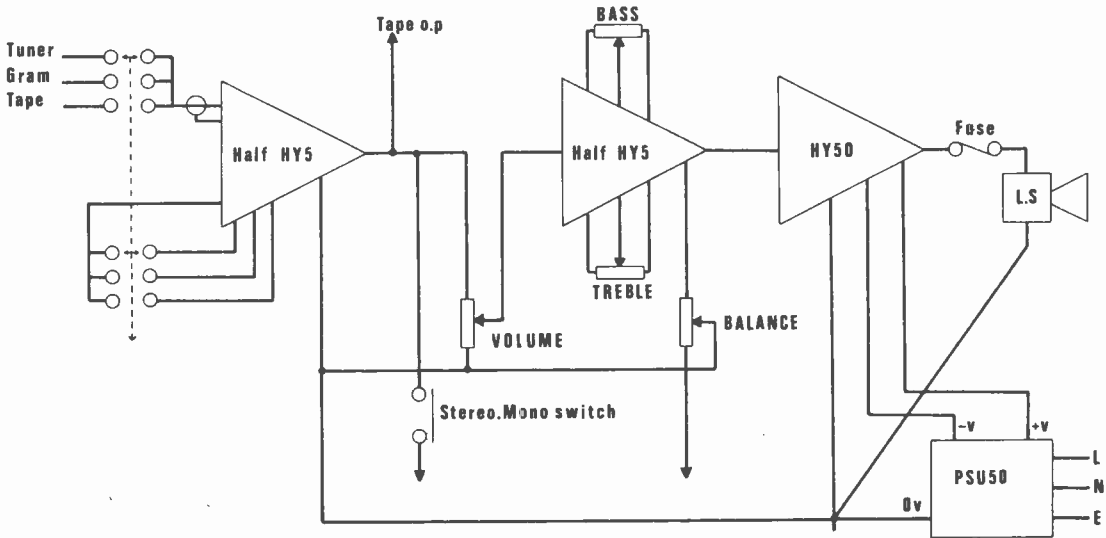

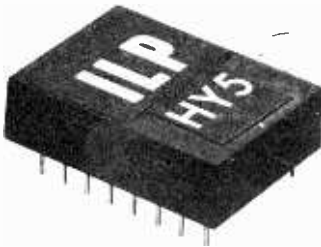MONO ELECTRICAL CIRCUIT DIAGRAM WITH INTERCONNECTIONS FOR STEREO SHOWN



The HY5 is a complete mono hybrid preamplifier, ideally suited for both mono and stereo applications. Internally the device consists of two high quality amplifiers—the first contains frequency equalisation and gain correction, while the second caters for tone control and balance.

TECHNICAL SPECIFICATION
Inputs: Magnetic Pick-up 3mV RIAA; Ceramic Pick-up 30mV; Microphone 10mV; Tuner 100mV; Auxiliary 3-100mV; Input Impedance 47kΩ at 1kHz. Outputs: Tape 100mV; Main output 0db (0.775V RMS). Active Tone Controls: Treble ± 12db at 10kHz; Bass ± 12db at 100Hz. Distortion: 0.5% at 1kHz. Signal/Noise Ratio: 68db. Overload Capability: 40db on most sensitive input. Supply Voltage: ± 16-25V.


PRICE £4.50 + 36p VAT
P. & P. free



The HY50 is a complete solid state hybrid HI-FI amplifier incorporating its own high conductivity heatsink hermetically sealed in black epoxy resin. Only five connections are provided, input, output, power lines and earth.

TECHNICAL SPECIFICATION
Output Power: 25W RMS into 8Ω. Load Impedance: 4-16Ω. Input Sensitivity 0db (0.775V RMS). Input Impedance: 47kΩ. Distortion: Less than 0.1% at 25W typically 0.05%. Signal/Noise Ratio: Better than 75db. Frequency Response: 10Hz-50kHz ± 3db. Supply Voltage: ± 25V. Size: 105 x 50 x 25mm.

PRICE £5.98 + 48p VAT
P. & P. free

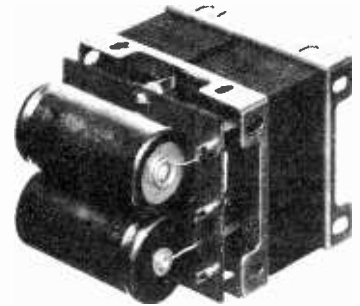

The PSU50 incorporates a specially designed transformer and can be used for either mono or stereo systems.

TECHNICAL SPECIFICATIONS
Output voltage: 50V (25-0-25V). Input Voltage: 210-240V. Size: L.70. D.90. H.60mm.

PRICE £6 + 48p VAT
P. & P. free

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd.
Crossland House,
Nackington, Canterbury
Kent CT4 7AD
Tel (0227) 63218

Please supply,
Total Purchase price
I Enclose, Cheque Postal Orders Money Order
Please debit my Access account Barclaycard account
Account number
Name & Address
Signature

Regd. V.A.T. No. 202141535

Signature

Greenbank Electronics

—Established 1970—

DIGITAL CLOCK COMPONENTS

FREE! DATA

Telephone or write for data on AY-5-1224 & MK 50253 digital clock chips, detail of P.C.B.s and component kits for AY-5-1224, data sheets for LED 8mm and 16mm displays, clock circuit diagrams.

NEW! CLOCK/'STOPWATCH' P.C.B.s

Glass fibre P.C.B.s to suit AY-5-1224 clock chip and display etc. (Easily modified to give additional 4 range 'stopwatch' facility, our brief application note AN-D1 free on request, explains how). Board size 112 x 89mm.
Type 1224-704E/PCB for 8mm high display 95p
Type 1224-747E/PCB for 16 mm high display 95p

SOON!

50 Hz clock timebase suggested circuit (single chip design using 3-2768 HMZ crystal)—details free.
1 Hz clock timebase suggested circuit (single chip design using 2-097152 MHz crystal)—details free.

CLOCK CHIPS

AY-5-1224 4 digit £3.66,
MK 50253 4/6 digit alarm £5.50
(CT 7001 discontinued)

4 DIGIT CLOCK KITS

Include: PCB, AY-5-1224 Chip, 4 LED digits, transistors, diodes, resistors, capacitors, mounting socket pins, 8 pages of instructions—extremely easy to

Greenbank Electronics, (Dept. W11P)
94 New Chester Road, New Ferry,
Wirral, Merseyside. L62 5AG England.
Telephone (Mon.-Sat.): 051-645 3391.

Terms: C.W.O. Add VAT to all prices at 8%, but where marked thus (*) add 25%. Post etc., U.K. 10p per order, Export 75p (no VAT). All orders processed on day of receipt. Callers welcome.

build—success guaranteed! Ref: 1224-704E /Kit (8mm high digits) . . . £9.95
Also, as above but using 16mm high digits (P.C.B. is same size) Ref: 1224-747E/
KIT . . . £3.44 extra.
(Either P.C.B. kit can be supplied assembled and tested for an additional 75p)

L.E.D.S.

DL-704E 8mm common cathode 7 seg. display (Economy Type) 85p
DL-747E 16mm common anode 7 seg. display (Economy Type) £1.70
DL-747 16mm common anode 7 seg. display ('Prime' quality) £2.45
DL-750 16mm common cathode 7 seg. display ('Prime' quality) £2.45
O.2" Single RED LED Indicator 12p

QUARTZ CRYSTALS FOR CLOCK TIME BASES

3-2768 MHz (=50Hz x 2¹⁴) } £3.90 each, including socket to suit.
2-097152 MHz (=1Hz x 2²¹) }
30pF parallel resonance tol ± 0.005 % (trimmable to 0%). Type MTC, approximate dimensions excluding pins 20 x 20 x 9mm. Oscillator circuit diagram available on request.

MINIATURE TRANSFORMERS

6VA Types with 240V primary, approximate dimensions W.45mm H. 38mm D. 40mm, fixing centres 53-5. Secondary voltages available: 2 x 4½V, 2 x 6v, 2 x 12V, 2 x 15V, 2 x 20V, all same price: £1.52.

TRANSISTORS

2N 3704 10p*, 2N3708 8p*, BC 213L (B) 11p*, BFR 39/41/79/81 23p*, MPS-A13 23p*


DIODES

IN 4148 3p*, IN 4002 5p, IN 4004 6p, IN 4007 8p.

CMOS

4001, 4011 gates 15p.

INVERTORS

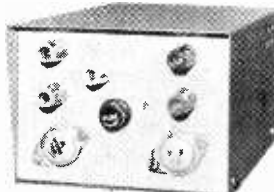

240v-50Hz from your 12v car battery.

25 watt—£4.20 150 watt—£19.10
40 watt—£7.35 300 watt (12v)—£29.95
75 watt—£10.71 300 watt (24v)—£23.75

All above Invertors are in kit form but may be purchased built up in metal case & ready for use. Price list sent on receipt of s.a.e. Prices include post & packing.

P.W. AUTOMATIC EMERGENCY SUPPLY

240v-50Hz-150 watt Inverter with built in battery charger. In event of power failure switches over automatically from battery charging to inverter operation. Cct. as appeared in Dec. 72 P.W. Complete kit of parts (excluding meter) £22.90+£1.10 p. & p.

FLUORESCENT LIGHT INVERTOR KIT
8 watt-12v-Fluorescent light, suitable for tents, caravans, houses, boats & secondary lighting for factories, hotels, etc.


12"-8 watt—£2.90+25p p. & p. Built up £4+25p.
21"-13 watt—£3.30+30p p. & p. Built up—£4.90+30p.

TRANSFORMERS & COILS

Both high volume & small order capacity available.
Special offer. Miniature mains transformer 12-0-12v-6V.A.—85p plus 10p p. & p.

TRADE & EXPORT ENQUIRIES WELCOMED

ORION STEREO AMPLIFIER

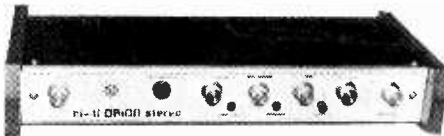

20 + 20 Watts r.m.s. into 8 ohm load. Distortion less than 0.01% 100Hz-10kHz. Frequency response ± 1dB 20 Hz to 20 kHz. Hum level virtually nil with vol. full on.

This is a power amplifier of superb quality incorporating the very latest design features. Professional hi-fi enthusiasts have classed it as fantastic and real value for money. The CCT incorporates a low flux transformer and inputs for disc, tape, tuner etc.

Complete kit of parts including slim line bookend case, silk screened front panel & knobs. £43 incl. VAT & p. & p.

The bookend case, I.C.s & semiconductors, P.C. board, Transformer, etc. may be purchased separately if desired. Send S.A.E. for further information

ASTRO IGNITION




ASTRO IGNITION SYSTEM

Complete kit of parts for this proven and tested system £9.50 incl VAT. Ready built with only two connections to alter £12.50 incl. VAT.

Thousands have used this system both home and abroad. Consider these advantages more power, faster acceleration, fuel economy, excellent cold starting, smoother running, no contact breaker burning. Also because of the high energy spark, the fuel mixture can be made weaker giving further economy and fewer plug problems. Fitting time when built 5 minutes approx. Please state whether positive or negative earth. Trade and export enquiries welcomed.

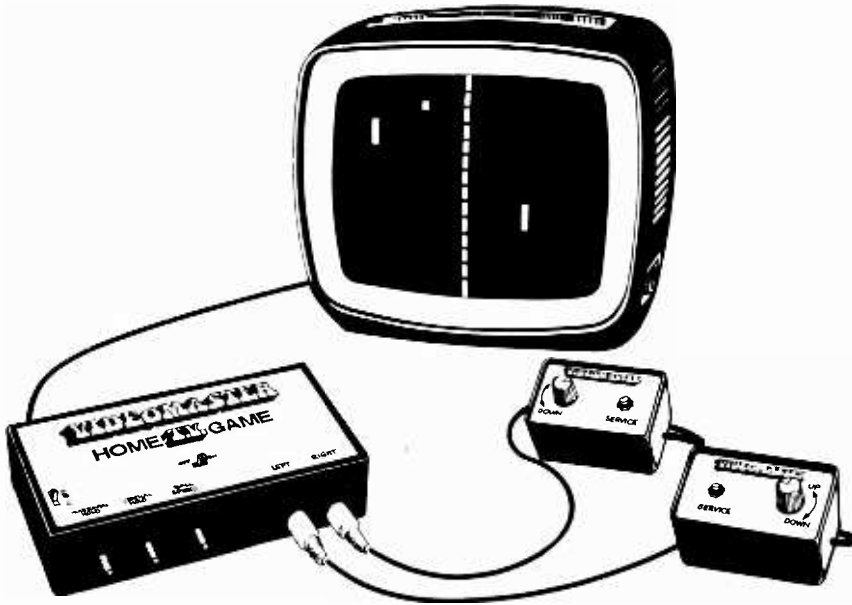ASTRO ELECTRONICS,
Spring Bank Rd., West Park,
Chesterfield.



Videomaster urge all good electronics enthusiasts to play the game

The best thing about the Videomaster Home T.V. Game Mk. III is that the sheer pleasure of building it is immediately followed by the excitement of playing three-fascinating games.

The famous Videomaster is now available for you to make. It plugs into any standard UHF 625 line TV set, and it shouldn't take you longer than a few hours to build.

In detail . . . The Videomaster Mk. III has eleven integrated circuits . . . four transistors . . . eleven diodes . . . is easy to build . . . with no alignment necessary because with ready-built and tested transistorized UHF modulator, is complete with all parts . . . including fully drilled and prepared p.c.b. . . . handsome plastic box . . . control leads . . . complete step by step assembly instructions . . . Runs on a PP79 volt battery . . . and has logic and analogue "state of the art" circuitry all with National Semiconductors CMOS devices . . . with full specification.

The cost? Only **£19.95** (+ VAT)

POST TODAY TO:

Videomaster Ltd

119/120 Chancery Lane, London WC2A 1QU

Please send me (insert no.) Videomaster Mk. III kits at £21.55 ea. inc. VAT. P & P

I enclose my cheque/money order for £

Tick if VHF Modulator required -£1 extra

NAME

ADDRESS

ALLOW 14 DAYS FOR DELIVERY



PW 2
Reg. No. 1115532

B-P-A-K

SEMICONDUCTORS

TRANSISTORS

BRAND NEW FULLY GUARANTEED

Type	Price	Type	Price	Type	Price	Type	Price
AC107	0-20	BBY40	0-58	AF118	0-36	ORP61	0-41*
AC113	0-19	BSY41	0-29	AF124	0-31	P20	0-51*
AC115	0-20	BSY95	0-13	AF125	0-31	P346A	0-20
AC117K	0-30	BSY95A	0-18	AF126	0-29	P397	0-48
AC122	0-12	BU105	22-04	AF127	0-29	ST140	0-18
AC125	0-18	CU11E	0-51	AF139	0-31	ST141	0-18
AC126	0-18	CA00	0-51	AF178	0-51	TIP29	0-44
AC127	0-19	CA07	0-88	AF179	0-51	TIP29	0-44
AC128	0-19	CA24	0-26	AF180	0-51	TIP81A	0-58
AC132	0-15	CA25	0-51	AF181	0-51	TIP32A	0-68
AC134	0-15	CA26	0-36	AF186	0-51	TIP41A	0-68
AC137	0-15	CA28	0-20	AF239	0-88	TIP42A	0-61
AC141	0-19	CA41	0-31	AL102	0-66	TI843	0-81*
AC141K	0-30	CA42	0-31	AL103	0-66	UT46	0-28*
AC142	0-19	CA44	0-36	AS726	0-58	ZN414	1-11
AC142K	0-30	CA50	0-22	ASV27	0-81	2G301	0-19
AC142K	0-30	CA50	0-22	ASV27	0-81	2G302	0-19
AC151	0-18	MAT100	0-19	ASV29	0-26	2G303	0-19
AC154	0-20	MAT101	0-20	ASV50	0-26	2G304	0-26
AC155	0-20	MAT120	0-19	ASV51	0-26	2G305	0-26
AC156	0-20	MAT121	0-20	ASV52	0-26	2G306	0-41
AC157	0-25	MJ2321	0-56	ASV53	0-26	2G309	0-36
AC165	0-25	MJE2955	0-57	ASV54	0-26	2N2928 G	1-18
AC166	0-20	MJE3055	0-57	ASV55	0-26	2N2928 Y	1-11
AC167	0-20	MJE3440	0-51	ASV56	0-26	2N2926 O	1-10
AC168	0-25	MPF102	0-48	ASV57	0-26	2N2928 R	1-10
AC189	0-15	MPF104	0-38	ASV58	0-26	2N2928 B	1-10
AC178	0-20	MPF105	0-38	ASV73	0-26	2N3010	0-71
AC177	0-25	OC19	0-41	ASV74	0-26	2N3011	0-15
AC178	0-29	OC20	0-65	BC107	0-08	2N3053	0-18
AC179	0-29	OC22	0-47	BC108	0-08	2N3054	0-17
AC180	0-20	OC23	0-49	BC109	0-08	2N3055	0-42
AC180K	0-30	OC24	0-57	BD136	0-41	2N3819	0-16
AC181	0-20	OC25	0-59	BD137	0-46	2N3819 A	0-17
AC181K	0-30	OC26	0-80	BD138	0-51	2N3892	0-16
AC187	0-22	OC28	0-51	BD139	0-58	2N3893	0-15
AC187K	0-22	OC29	0-51	BD140	0-61	2N3894	0-16
AC188	0-22	OC35	0-48	BD155	0-61	2N3895	0-18
AC188K	0-22	OC36	0-51	BD175	0-61	2N3402	0-21
ACY17	0-28	OC41	0-20	BD176	0-61	2N3403	0-21
ACY18	0-20	OC42	0-25	BD177	0-67	2N3404	0-29
ACY19	0-20	2N918	0-31	BD178	0-67	2N3405	0-48
ACY20	0-20	2N929	0-21	BD179	0-71	2N3414	0-18
ACY21	0-20	2N930	0-21	BD180	0-71	2N3415	0-18
ACY22	0-17	2N1131	0-20	BD185	0-67	2N3416	0-29
ACY27	0-19	2N1132	0-22	BD186	0-67	2N3417	0-29
ACY28	0-19	2N1302	0-16	BD187	0-71	2N3625	0-77*
ACY29	0-36	2N1303	0-16	BD188	0-71	2N3614	0-69
ACY30	0-36	2N1304	0-18	BD189	0-77	2N3615	0-76
ACY31	0-29	2N1305	0-18	BD190	0-77	2N3616	0-76
ACY34	0-21	2N1306	0-21	BD195	0-87	2N3646	0-09
BC173	0-15	2N1307	0-21	BD196	0-87	2N3702	0-12
BC174	0-15	2N1308	0-24	BD197	0-92	2N3703	0-12
BC175	0-22	2N1309	0-24	BD198	0-92	2N3704	0-18
BC177	0-19	2N1310	0-24	BD199	0-92	2N3705	0-12
BC178	0-19	2N1711	0-20	BD200	0-98	2N3706	0-12
BC179	0-19	2N1889	0-82	BD205	0-81	2N3707	0-18
BC180	0-26	2N1890	0-46	BD206	0-81	2N3708	0-08
BC181	0-25	2N1893	0-88	BD207	0-98	2N3709	0-09
BC182	0-16	2N2147	0-78	BD208	0-98	2N3710	0-09
BC182L	0-29	2N2148	0-80	BD209	0-98	2N3711	0-09
BC183	0-15	2N2192	0-88	BF115	0-25	2N3819	0-29
BC183L	0-16	2N2193	0-88	BF117	0-46	2N3820	0-51
BC184	0-20	2N2194	0-86	BF118	0-71	2N3821	0-68
BC184L	0-20	2N2217	0-22	BF119	0-71	2N3823	0-29
BC186	0-29	2N2218	0-22	BF121	0-46	2N3803	0-29
BC187	0-29	2N2219	0-22	BF122	0-51	2N3804	0-29
BC207	0-11	2N2220	0-22	BF125	0-58	2N3805	0-29
BC208	0-18	2N2221	0-20	BF127	0-51	2N3906	0-28
BC209	0-18	2N2222	0-20	BF132	0-58	2N4058	0-18
BC212L	0-12	2N2268	0-18	BF153	0-46	2N4069	0-10
BC213L	0-18	2N2369	0-15	BF164	0-46	2N4080	0-18
BC214L	0-17	2N2369A	0-15	BF165	0-47	2N4080	0-18
BC225	0-26	2N2411	0-24	BF175	0-58	2N709	0-18
BC226	0-26	2N2412	0-25	BF167	0-56	2N711	0-18
BC201	0-38	2N2646	0-46	BF168	0-56	BC115	0-18
BC302	0-25	2N2711	0-21	BF169	0-61	BC117	0-19
BC303	0-21	2N2712	0-21	BF160	0-41	BC118	0-10
BC304	0-37	2N2714	0-21	BF162	0-41	BC119	0-31
BC440	0-31	2N2904	0-18	BF163	0-41	BC120	0-31
BC460	0-37	2N2904A	0-21	BF164	0-41	BC122	0-19
BCY30	0-26	2N2905	0-21	BF165	0-41	BC126	0-19
BCY31	0-27	2N2905A	0-21	OC44	0-16	BC132	0-18
BCY32	0-21	2N2906	0-16	OC45	0-18	BC134	0-19
BCY33	0-22	2N2906A	0-19	OC70	0-10	BC135	0-19
BCY34	0-26	2N2907	0-20	OC71	0-10	BC136	0-18
BCY70	0-15	2N2907A	0-22	OC72	0-15	BC137	0-18
BCY71	0-20	2N2923	0-15	OC74	0-15	BC139	0-41
BCY72	0-16	2N2924	0-15	OC75	0-18	BC140	0-31
BCZ10	0-20	2N2925	0-15	OC76	0-16	BC141	0-31
BCZ11	0-26	ACY35	0-21	OC77	0-26	BC142	0-31
BCZ12	0-26	ACY36	0-22	OC81	0-18	BC143	0-31
BD115	0-30	AD140	0-18	OC81D	0-46	BC145	0-46
BD116	0-31	AD141	0-19	OC82	0-19	BC147	0-10
BD121	0-61	AD144	0-36	OC82D	0-16	BC148	0-10
BD123	0-67	AD130	0-39	OC83	0-20	BC149	0-12
BD124	0-70	AD140	0-49	OC139	0-20	BC150	0-19
BD131	0-61	AD142	0-49	OC140	0-20	BC151	0-30
BD132	0-61	AD148	0-39	OC141	0-20	BC152	0-18
BD135	0-61	AD149	0-39	OC170	0-28	BC153	0-39
BF753	0-41	AD161	0-36	OC171	0-28	BC154	0-31
BSX19	0-16	AD162	0-38	OC200	0-28	BC157	0-19
BSX20	0-16	AD161 & AD162(MP)	0-29	OC201	0-29	BC158	0-12
BSY26	0-16	ADT140	0-61	OC202	0-29	BC159	0-12
BSY27	0-16	AF114	0-25	OC203	0-28	BC160	0-48
BSY28	0-16	AF115	0-25	OC204	0-28	BC161	0-51
BSY29	0-16	AF116	0-25	OC309	0-41	BC162	0-51
BSY88	0-19	AF118	0-25	OCP71	0-44*	BC168	0-12
BSY89	0-19	AF117	0-25	ORP12	0-44*	BC169	0-12
				ORP80	0-41*	BC170	0-15
						BC171	0-15

* 74 SERIES T.T.L. I.C.'s

BI-PAK STILL LOWEST IN PRICE, FULL SPECIFICATION GUARANTEED. ALL FAMOUS MANUFACTURERS.

Type	Quantities	Type	Quantities	Type	Quantities
	1 25 100+		1 25 100+		1 25 100+
7400	0-14 0-13 0-12	7448	11-02 0-99 0-91	74122	0-65 0-63 0-60
7401	0-14 0-13 0-12	7450	0-14 0-13 0-12	74123	0-69 0-68 0-65
7402	0-14 0-13 0-12	7451	0-14 0-13 0-12	74141	0-79 0-78 0-78
7403	0-14 0-13 0-12	7453	0-14 0-13 0-12	74145	11-20 11-16 11-11
7404	0-14 0-13 0-12	7454	0-14 0-13 0-12	74150	11-20 11-16 11-11
7405	0-14 0-13 0-12	7460	0-14 0-13 0-12	74151	11-20 11-16 11-11
7406	0-38 0-31 0-29	7470	0-30 0-27 0-25	74153	0-98 0-98 0-98
7407	0-38 0-31 0-29	7472	0-30 0-27 0-25	74154	11-27 11-23 11-18
7408	0-38 0-31 0-29	7473	0-38 0-36 0-32	74155	11-11 11-08 11-02
7409	0-23 0-22 0-21	7474	0-38 0-36 0-32	74156	11-11 11-08 11-02
7410	0-14 0-13 0-12	7475	0-66 0-64 0-62	74157	0-98 0-98 0-98
7411	0-23 0-22 0-21	7476	0-61 0-40 0-39	74159	11-20 11-16 11-11
7412	0-38 0-36 0-32	7480	0-66 0-64 0-62	74161	11-20 11-16 11-11
7413	0-38 0-36 0-32	7481	1-02 0-97 0-93	74162	11-20 11-16 11-11
7414	0-38 0-36 0-32	7482	0-58 0-79 0-74	74163	11-20 11-16 11-11
7417	0-38 0-36 0-32	7483	11-11 11-08 11-02	74164	11-07 11-02 11-02
7420	0-14 0-13 0-12	7484	0-98 0-90 0-88	74165	11-07 11-02 11-02
7422	0-28 0-27 0-26	7485	11-48 11-44 11-39	74166	11-48 11-44 11-39
7423	0-37 0-36 0-35	7486	11-38 0-31 0-30	74174	11-48 11-44 11-39
7425	0-37 0-36 0-35	7489	23-70 23-47 23-24	74175	11-02 0-97 0-98
7426	0-37 0-36 0-35				

PO BOX 6 WARE HERTS

SUPER UNTESTED PAKS

Pak No.	Description	Sp	Price
U 1	120 Glass Sub-min. General purpose Germ. diodes	...	0-60
U 2	50 Mixed Germanium transistors AF/RF	...	0-60
U 3	75 Germanium gold bonded sub-min. like OA6, OA47	...	0-60
U 4	30 Germanium transistors like OC81, AC128	...	0-60
U 5	60 200mA sub-min. silicon diodes	...	0-60
U 6	30 Sil. Planar trans. NPN like BSY96A, 2N706	...	0-60
U 7	16 Sil. rect. TOP-HAT 750mA VLTG. RANGE up to 100	...	0-60
U 8	50 Sil. planar diodes DO-7 glass 250mA like OA200/202	...	0-60
U 9	20 Mixed voltages, 1 Watt Zener Diodes	...	0-60
U10	20 BA50 charge storage diodes DO-7 glass	...	0-60
U11	20 NPN Sil. planar trans. TO-5 like 2N1132, 2N2904	...	0-60
U13	30 PNP-NPN Sil. transistors OC200 & 2B104	...	0-60
U14	150 Mixed silicon and germanium diodes	...	0-60
U15	20 NPN Sil. planar trans. TO-5 like 2N696, 2N697	...	0-60
U16	10 3AMP sil. rectifiers stud type up to 1000 PIV	...	0-60
U17	30 Germanium PNP AF transistors TO-5 like ACY 17-22.	...	0-60
U18	8 6 Amp sil. rectifiers BYZ13 type up to 600 PIV	...	0-60
U19	20 Silicon NPN transistors like BC 108	...	0-60
U20	12 1.5 Amp sil. rectifiers top hat up to 1000 PIV	...	0-60
U21	30 AF. Germ. alloy transistors 2G300 series & OC71	...	0-60
U23	25 MADD's like MHz series PNP transistors	...	0-60
U24	20 Germ. 1 Amp rectifiers GJM series up to 300 PIV	...	0-60
U25	25 300 MHz NPN silicon transistors 2N708, BS727	...	0-60
U26	30 Fast switching silicon diodes like IN914 Micro-Min	...	0-60
U29	10 1 Amp SCR's TO-5 can. up to 600 PIV CR81/25-600	...	\$1.20*
U32	25 Zener diodes 400 mW DO-7 case 3-33 volts mixed	...	0-60
U33	15 Plastic case 1 Amp sil. rectifiers IN4000 series	...	0-60
U34	30 Silicon PNP alloy trans. TO-5 BCY26 2B302/4	...	0-60
U35	25 Silicon planar transistors PNP TO-18 2N2906	...	0-60
U36	20 Silicon planar NPN transistors TO-5 BFY50/51/52	...	0-60
U37	30 Silicon alloy transistors 80-2 PNP OC200, 82322	...	0-60
U38	20 Fast switching silicon trans. NPN 400 MHz 2N3011	...	0-60
U39	30 RF. Ger. PNP transistors 2N1303/5 TO-5	...	0-60
U40	10 Dual transistors 6 lead TO-5 2N2060	...	0-60
U43	25 Silicon trans. plastic TO-18 A.P. BC113/114	...	0-60
U44	20 Silicon trans. plastic TO-5 BC115	...	0-60
U45	7 3A SCR. TO66 up to 600 PIV	...	\$1.20*
U46	20 Unijunction transistors similar to T1843	...	0-60*
U47	10 TO220AB plastic triacs 60V 6A	...	\$1.20*
U49	9 NPN Sil. power transistors like 2N3055	...	\$1.20
U49	12 NPN Sil. plastic power trans. 60W like 2N5294/5296	...	\$1.20

Code No's mentioned above are given as a guide, to the type of device in the pak. The devices themselves are normally unmarked.

QUALITY TESTED PAKS

Pak No.	Quality Tested Paks	Price
Q 1	20 Red spot transistors PNP	0-60
Q 2	16 White spot R.F. transistors PNP	0-60
Q 3	4 OC 77 type transistors	0-60
Q 4	6 Matched transistors OC44/45/81/81D	0-60
Q 5	4 OC 75 transistors	0-60
Q 6	5 OC 79 transistors	0-60
Q 7	4 AC 128 transistors PNP high gain	0-60
Q 8	4 AC 126 transistors PNP	0-60
Q 9	7 OC 81 type transistors	0-60
Q10	7 OC 71 type transistors	0-60
Q11	2 AC 127/128 Complementary pairs PNP/NPN	0-60
Q12	3 AF 116 type transistors	0-60
Q13	3 AF 117 type transistors	0-60
Q14	3 OC 171 H.F. type transistors	0-60
Q15	7 2N2926 Sil. Epoxy transistors mixed colours	0-60
Q17	5 NPN 2 x ST.141. & 3 x ST.140	0-60
Q18	4 MADT'S 2 x MAT 100 & 2 x MAT 120	0-60
Q19	3 MADT'S 2 x MAT 101 & 1 x MAT 121	0-60
Q20	4 OC 44 Germanium transistors A.P.	0-60
Q21	4 AC 127 NPN Germanium transistors	0-60
Q22	20 NKT transistors A.P. R.F. coded	0-60
Q23	10 OA 202 Silicon diodes sub-min	0-60
Q24	8 OA 81 diodes	0-60
Q25	15 IN 914 Silicon diodes 75PIV 75mA	0-60
Q26	8 OA95 Germanium diodes sub-min-IN89	0-60
Q27	2 10A 600 PIV Silicon rectifiers 15A425B	0-60*
Q28	2 Silicon power rectifiers BYZ 13	0-60
Q29	4 Sil. transistors 2 x 2N696, 1 x 2N697, 1 x 2N698	0-60
Q30	7 Silicon switch transistors 2N708 NPN	0-60
Q31	6 Silicon switch transistors 2N708 NPN	0-60
Q32	3 PNP Sil. trans. 2 x 2N1131, 1 x 2N1132	0-60
Q33	3 Silicon NPN transistors 2N1711	0-60
Q34	7 Sil. NPN trans. 2N2369, 500MHz (code F587)	0-60
Q35	3 Silicon PNP TO-5 2 x 2N2904 & 1 x 2N2906	0-60
Q36	7 2N3646 TO-18 plastic 300 MHz NPN	0-60
Q37	3 2N3055 NPN Silicon transistors	0-60
Q38	5 PNP transistors 3 x 2N3703, 2 x 2N3702	0-60
Q39	6 NPN transistors 3 x 2N3704, 2 x 2N3705	0-60
Q40	5 NPN transistors 3 x 2N3707, 2 x 2N3708	0-60
Q41	3 Plastic NPN TO18 2N3904	0-60
Q43	5 BC 107 NPN transistors	0-60
Q44	5 NPN transistors 3 x BC108, 2 x BC109	0-60
Q45	3 BC 113 NPN TO-18 transistors	0-60
Q46	3 BC 115 NPN TO-5 transistors	0-60
Q47	4 NPN high gain transistors 2 x BC 157, 2 x BC 168	0-60
Q48	3 BCY 70 PNP transistors TO-18	0-60
Q49	3 NPN transistors 2 x BFY 51, 1 x BFY 52	0-60
Q50	7 BBY 28 NPN switch transistors TO-18	0-60
Q51	7 BBY 95A NPN transistors 300MHz	0-60
Q52	8 BY 100 type silicon rectifiers	\$1.20
Q53	25 Sil. & Germ. trans. mixed all marked new	\$1.50
Q54	6 TIL 209 Red LED	\$1.20*

MAMMOTH I.C. PAK

APPROX. 200 PIECES
Assorted fall-out integrated circuits, including: Logic, 74 series, Linear, Audio and D.T.L. Many coded devices but some unmarked—you to identify.
OUR SPECIAL PRICE £1.20p

WORLD SCOOP

JUMBO SEMICONDUCTOR PAK
Transistors—Germ. and Silicon. Rectifiers—Diodes—Triacs—Thyristors—I.C.'s and Zeners. ALL NEW AND CODED
APPROX 100 PIECES
Offering the amateur a fantastic bargain PAK and an enormous saving—identification and data sheet in every pak.
ONLY £1.85p

UNTESTED LIN PAKS

Manufacturers 'Fall Outs' which include Functional and part Functional Units. These are classed as 'out-of-spec'—by the makers' very rigid specifications, but are ideal for learning about I.C.'s and experimental work.
Pak No. Contents Price
ULIC709—10 x 709 0-60
ULIC710—7 x 710 0-60
ULIC741—7 x 741 0-60
ULIC747—5 x 747 0-60
ULIC748—7 x 748 0-60

C280 CAPACITOR PAK

Containing 75 of the C280 range of capacitors assorted in values ranging from -0.1uF to 2.2uF. Complete with identification chart.
PANTASTIC VALUE ONLY £1.20p.

SIL. G.P. DIODES

300 mW 40 PIV (min) SUB-MIN FULLY TESTED
Ideal for Organ builders
30 for 50p, 100 for £1.50, 500 for £5, 1000 for £9.

G.P. SWITCHING TRANS

TO18 SIM. TO 2N706/8 BSY27/28/95A
All usable devices. No open and shorts. ALSO AVAILABLE IN PNP similar to 2N2906, BCY 70 20 for 60p, 50 for £1, 100 for £1.80, 500 for £8, 1000 for £14.
When ordering please state NPN or PNP

G.P. 100

30 WATT GERMANIUM TO3 METAL CASE
Vcbo 80V, Vceo 50V, IC 10A, Ife 30-170 replaces the majority of Germanium power Transistors in the OC, AD NKT range.
1-24 25-99 100+
44p 41p 37p

G.P. 300

115 WATT SILICON TO3 METAL CASE
Vcbo 100V, Vceo 80V, IC 15A, Ife, 20-100 suitable replacement for 2N3055, BDY11 or BDY20
1-24 25-99 100+
50p 48p 46p

INDICATORS

3015F Minitron 7 Segment Indicator £1.11p*
MAN 3M L.E.D. 7 SEGMENT DISPLAY
O.127" High Characters £1.76p*

ZENER DIODES

FULL RANGE IN STOCK
VOLTAGE RANGE 2-33V
400 mw 8p 1-6 w 17p 10 w* 30p

VOLTAGE REGULATORS

TO.3 Plastic Encapsulation
uA.7905/L129 5V (Equiv. to MVR5V) £1.25p
uA.7812/L130 12V (Equiv. to MVR12V) £1.25p
uA.7815/L131 15V (Equiv. to MVR15V) £1.25p
uA.7818 18V (Equiv. to MVR18V) £1.25p

THYRISTORS

PIV	TO-6A	0-8A	1A	3A	5A	7A	10A	16A	30A
	T082	TO5	TO66	TO64	TO48	TO48	TO48	TO48	
10	0-18	0-15	—	—	—	—	—	—	—
20	0-15	0-18	—	—	—	—	—	—	—
30	0-19	0-22	—	—	—	—	—	—	—
50	0-22	0-28	0-20	0-25	0-38	0-48	0-51	0-54	\$1-13
100	0-25	0-30	0-25	0-25	0-48	0-48	0-51	0-57	\$1-43
150	0-31	0-33	—	—	—	—	—	—	—
200	0-38	0-44	0-25	0-30	0-50	0-50	0-57	0-62	\$1-78
400	—	—	0-30	0-39	0-55	0-57	0-62	0-71	\$1-69
600	—	—	0-39	0-48	0-69	0-69	0-78	0-99	0-90
800	—	—	0-58	0-65	0-81	0-81	0-92	\$1-23	\$1-39

DIODES

Type	Price	Type	Price	Type	Price	Type	Price
AA119	0-08	BY101	0-12	BYZ16	0-41	OA85	0-09
AA120	0-08	BY105	0-18	BYZ17	0-36	OA90	0-07
AA129	0-08	BY114	0-18	BYZ18	0-36	OA91	0-07
AA730	0-06	BY124	0-12	BYZ19	0-26	OA95	0-07
AAZ13	0-10	BY128	0-15	CG62	0-38	OA200	0-07
BA100	0-10	BY127	0-16	(OA91Eq)	0-26	OA202	0-07
BA116	0-21	BY128	0-16	CG651 (OA70)	0-07	8D10	0-06
BA128	0-02	BY130	0-17	OA79	0-07	8D19	0-06
BA143	0-15	BY133	0-21	OA5 Short	—	1N34	0-07
BA154	0-12	BY164	0-51	Leads	0-21	1N34A	0-07
BA155	0-15	BYX38/390-48	0A10	0-21	—	1N914	0-08
BA156	0-14	BYZ10	0-36	OA47	0-07	1N916	0-06
BA173	0-15	BYZ11	0-31	OA70	0-07	1N4148	0-06
BB104	0-15	BYZ12	0-31	OA79	0-07	18021	0-10
BY100	0-16	BYZ13	0-26	OA181	0-07	18951	0-70

UNTESTED T.L. PAKS

Manufacturers 'Fall Outs' which include Functional and part Functional Units. These are classed as 'out-of-spec'—by the makers' very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price
UIC09	-12 x 7400	0-60	UIC72	-8 x 7472	0-60
UIC01	-12 x 7401	0-60	UIC73	-8 x 7473	0-60
UIC02	-12 x 7402	0-60	UIC74	-8 x 7474	0-60
UIC03	-12 x 7403	0-60	UIC75	-8 x 7475	0-60
UIC04	-12 x 7404	0-60	UIC76	-8 x 7476	0-60
UIC05	-12 x 7405	0-60	UIC77	-8 x 7477	0-60
UIC06	-8 x 7406	0-60	UIC78	-8 x 7478	0-60
UIC07	-8 x 7407	0-60	UIC79	-8 x 7479	0-60
UIC10	-12 x 7410	0-60	UIC82	-5 x 7482	0-60
UIC11	-8 x 7411	0-60	UIC83	-5 x 7483	0-60
UIC13	-8 x 7413	0-60	UIC86	-5 x 7486	0-60
UIC20	-12 x 7420	0-60	UIC90	-5 x 7490	0-60
UIC30	-12 x 7430	0-60	UIC91	-5 x 7491	0-60
UIC40	-12 x 7440	0-60	UIC92	-5 x 7492	0-60
UIC41	-5 x 7441	0-60	UIC93	-5 x 7493	0-60
UIC42	-5 x 7442	0-60	UIC94	-5 x 7494	0-60
UIC43	-5 x 7443	0-60	UIC95	-5 x 7495	0-60
UIC44	-5 x 7444	0-60	UIC96	-5 x 7496	0-60
UIC45	-5 x 7445	0-60	UIC98	-5 x 7498	0-60
UIC46	-5 x 7446	0-60	UIC100	-5 x 74100	0-60
UIC47	-5 x 7447	0-60	UIC121	-5 x 74121	0-60
UIC48	-5 x 7448	0-60	UIC141	-5 x 74141	0-60
UIC51	-12 x 7451	0-60	UIC151	-5 x 74151	0-60
UIC53	-12 x 7453	0-60	UIC154	-5 x 74154	0-60
UIC54	-12 x 7454	0-60	UIC193	-5 x 74193	0-60
UIC60	-12 x 7460	0-60	UIC199	-5 x 74199	0-60
UIC70	-8 x 7470	0-60	UIC X125	Assorted 74's	\$1-50

FANE 'SPECIALIST' RANGE LOUDSPEAKERS

OF OUTSTANDING QUALITY FOR THE DISCRIMINATING PROFESSIONAL
Features include ROBUST CAST ALUMINIUM CHASSIS and 2" EXTRA HIGH POWER VOICE COILS
All models available in impedances of 8 ohm or 15 ohm. Guarantee: 2 years. Recommended Prices inc. VAT



Illust.
12"
DISCO 60'

12" 'DISCO 60' 60 watts R.M.S.

Linen Cone Surround. Fitted extra large Tweeter Cone. Frequency Range 50-15,000 Hz

Rec. Retail Price
£24.75

12" 'GUITAR 60L' 60 watts R.M.S.

Plastiflex Cone Surround. Aluminium Centre Dome. Frequency Range 50-9,000 Hz.

Rec. Retail Price
£23.50

DESIGNED FOR LEAD GUITAR

12" 'GUITAR 60B' 60 watts R.M.S.

Linen Cone Surround. Frequency Range 45-9,000 Hz. Rec. Retail Price

£23.95

FOR USE IN MULTIPLES FOR BASS GUITAR

12" 'PA 60' 60 watts R.M.S.

Plastiflex Cone Surround. Fitted Tweeter Cone. Frequency Range 50-15,000 Hz. Rec. Retail Price

£23.50

FOR GENERAL PURPOSE PUBLIC ADDRESS

15" 'BASS 70' 70 watts R.M.S.

Linen Cone Surround. Frequency Range 40-7,000 Hz. Can be used singly but ideally TWO UNITS IN A SINGLE CABINET.

Rec. Retail Price
£35.95

RECOMMENDED FOR ALL BASS INSTRUMENTS

HIGH FREQUENCY HORN UNITS

MODEL 910 Mk II

Rating 50 watts with recommended filter. Rec. Price

£16.95

MODEL 912 Rec. Price with even higher sensitivity **£19.50**

MODEL 920 Mk II (as illust) Rec. Price significantly increased sensitivity. Rating with recommended filter 100 watts **£47.50**

HPXI HIGH POWER CROSS-OVER UNIT Suitable for above Horn Units Rec. Price £2.50



Prices shown correct at Sept. 1, 1975

MODEL D40 50 WATT DISCO KIT

Consisting of 12" 13,000 Gauss BASS UNIT, HPXI HIGH POWER Cross-over and PH50 TWEETER. All purpose. Full range. Imp. 8-15 ohms.

£21.50


AND for those who can afford the very best there is our range of

'CRESCENDO'

MODELS Rec. Retail 12" UNITS from **£46.95**

Three models for specific purposes

15" UNITS Rec. Retail from **£60.95**

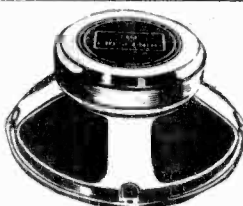

Distributors (Wholesale & Retail Trade): LINEAR PRODUCTS LTD., ELECTRON WORKS, ARMLEY, LEEDS. Manufacturers enquiries to: FANE ACOUSTICS LTD., 286 BRADFORD ROAD, BATLEY, YORKS.

'POP' RANGE

FAST SELLING and RELIABLE UNITS

POP 15 12" 15w **£7.70**

POP 33T 12" 33w **£10.99**

POP 50T 12" 50w **£14.95**

POP55/2 12" 60w **£19.99**


POP 60 15" 60w **£22.95**

POP 70 15" 70w **£24.50**

POP 100 18" 100w **£38.95**

Available in impedances of either 8Ω or 15Ω

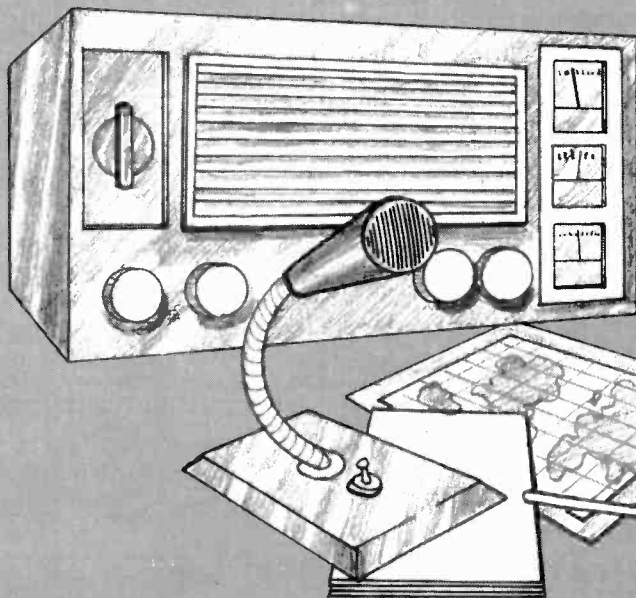Please send S.A.E. for leaflets any of above ranges



Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

Brochure, without obligation to:

To: BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept. WB115,
P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____


Block caps please

Free!

We don't miss anything out, so you won't miss out.

Our 1214 Series stereo equipment comes to you in kit form. And, as you would expect, coming from Heathkit, they are absolutely complete kits. With nothing left out.

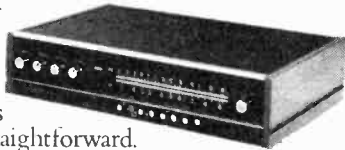So you'll have all you need to build our superb AR-1214 stereo receiver. Or, if you'd prefer, a separate amplifier and tuner (the AA-1214 and AJ-1214).



The easy to understand instruction manual you'll get makes assembly beautifully straightforward.

And very enjoyable.


And the high performance of the 1214 Series means you won't miss out on listening pleasure in any way either.

From the stereo receiver, or separate amplifier, you'll get 15 watts r.m.s. a channel, with reproduction so good it makes many ready-made systems really sit up and listen.

For full details of the 1214 Series, the rest of our audio range, including speakers, and our many other kits, just post the coupon now for your Heathkit catalogue.

Or call in at the London Heathkit Centre, 233 Tottenham Court Road.

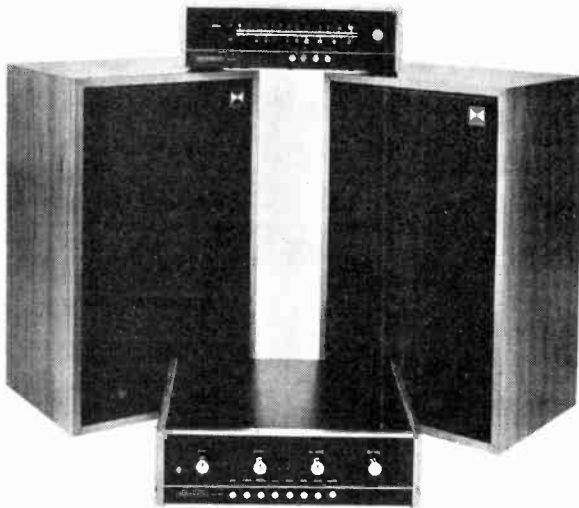Heath (Gloucester) Ltd., Dept. PW-115, Bristol Road, Gloucester GL2 6EE. Tel: (0452) 29451.



To: Heath (Gloucester) Limited, Dept. PW-115, Gloucester GL2 6EE. Please send me a Heathkit catalogue. I enclose a 10p stamp for postage.

HEATH
Schlumberger



Name _____

Address _____

Postcode _____

Monthly budget plan available

Look AT THESE PRICES AND BUY QUALITY

TOSHIBA VALVES

Type	Price (p)
DY87	30 0
DY802	30 0
ECC82	28 0
EF80	29 5
EF183	34 5
EF184	34 5
EH90	35 5
PC900	24 5
PCC89	40 0
PCC189	41 0
PCF80	31 5
PCF86	39 0
PCF801	42 0
PCF802	40 0
PCL82	39 0
PCL84	39 0
PCL85	44 5
PC185	41 0
PFL200	59 5
PL36	55 5
PL84	25 0
PL504	64 5
PL508	67 0
PL513	61 20
PY88	35 5
PY800	35 5
PY500A	85 0

Type Price

Each (p)	Type	Price Each (p)
15	BC125B	15
25	BC132	25
15	BC135	15
19	BC137	19
26	BC138	26
23	BC142	23
25	BC143	25
11	BC147	11
11	BC147A	11
10	BC148	10
10	BC149	10
15	BC153	15
15	BC154	15
14	BC157	14
10	BC158	10
11	BC159	11
18	BC173	18
20	BC178B	20
12	BC182L	12
12	BC183L	12
25	BC187	25
15	BC214L	15
28	BC328	28
19	BC337	19
75	BD124	75
45	BD131	45
39	BD132	39
139	BD160	139
49	BD235	49
52	BD237	52
42 40	BDX32	42 40
20	BF115	20
15	BF160	15
20	BF173	20
35	BF178	35
40	BF179	40
31	BF180	31
32	BF181	32
25	BF184	25
25	BF185	25
9	BF194	9
8	BF195	8
10	BF196	10
12	BF197	12
23	BF198	23
25	BF200	25
33	BF214	33
23	BF224	23
34	BF258	34
28	BF336	28
35	BF337	35
54	BF355	54
28	BFX86	28
19	BFY50	19
20	BFY52	20
75	BSY52	75
120	BT106	120
95	BU105/02	95
10	BU108	10
95	BU208	95
36	ET222	36
45	MJE340	45
45	OC71	45
16	OC72	16

Type Price

Each (p)	Type	Price Each (p)
22 00	R2008B	22 00
80	R2010B	80
80	RCA16334	80
80	RCA16335	80
57	TIP31A	57
67	TIP32A	67
67	TIP41A	67
80	TIP42A	80
55	2N3055	55
7	DIODES	7
14	BA115	14
19	BA145	19
19	BA148	19
11	BA154/201	11
11	BY126	11
12	BY127	12
27	BY199	27
21	BY206	21
25	BY238	25
5	OA30	5
7 5	OA202	7 5
5	IN60/OA91	5
5	IN914	5
5	IN4002	5

INTEGRATED CIRCUITS

Type	Price Each (p)
ETTR6018	42 00
MC1351P	70
SN76003N	42 35
SN76013N	41 50
SN76013ND	41 50
SN76023N	41 50
SN76023ND	41 45
SN76033N	42 35
SN76227N	41 45
SN76532N	41 45
SN76660N	58
SN76666N	87
TAA550	49
TAA700	42 95
TBA120AS	41 00
TBA120S	41 00
TBA480Q	41 40
TBA520Q	42 35
TBA530Q	41 75
TBA540Q	41 75
TBA550Q	42 90
TBA560CQ	42 40
TBA800	41 50
TBA920	42 90
TBA990Q	42 90
TCA2700	42 90
EHT MULTIPLIERS MONOCHROME (BRC) Price Each	
2HD 950MK1	960
2TQ 950MK2	1400
2DAK 1500	1 85
(17" & 19")	1 85
2TAK 1500	1 85
(23" & 24")	2 00

EHT MULTIPLIERS COLOUR

Type	Price Each
11TAQ IIT CVC 1 2 & 3	44 50
11TAZ GEC Sobell	44 50
11TAZ GEC 2110	44 85
11TAM Philips GB	44 50
11TBD Philips 550	44 50
3TCW Pye 691/693	43 50
1TH Decca 30 Series	44 50
11TAQ Decca Bradford	44 50
3TCU Thorn 3000/3500	45 00
11HAA Thorn 8000	41 90
11HAB Thorn 8500	42 25

PRICE QUALITY SERVICE



COMBINED PRECISION COMPONENTS (PRESTON) LTD
Department P.
194-200 North Rd.
Preston PR1 1YP
Tel: 55034
Telex: 677122.

New TOSHIBA TUBES

with 12 months in service guarantee

19" A49-191X equivalents	
A49-192 and A49-120X	48 95
20" 510JB22 equivalent	
A51-110X	50 75
22" A56/120X	54 25

PRICES SUBJECT TO 25% V.A.T.
All goods subject to settlement discount of 5% 7 days and 2% monthly.
No postage charges or minimum order values.
Write or phone for full details now.


IT MAKES SENSE TO

<p>HIKI 730X 30,000 opv. Overload protection. 6/30/60/300/600/1200V DC. 12/80/120/600/1200V AC. 60 μA. 30mA/300mA. 10 to 63dB. OUR PRICE £8.10 P/P & Ins 30p</p> 	<p>U4312 MULTIMETER extremely sturdy instrument for general electrical work. 657 opv. 0/0.3/1.5/5/30/60/150/300/600/900V DC & 75mV. 0/0.3/1.5/5/30/60/150/300/600/900V AC. 0/300uA/1.5/6/15/150/60/60mA/1/1.5/6A DC. 0/1.5/6/15/60/150/600mA/1.5/6A AC. 0/200/3k/30k ohms DC accuracy 1%. AC 1.5%. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions. OUR PRICE £11.60p P & Ins 60p</p> 	<p>MODEL 500 30,000 opv with overload protection. Mirror scale. 0/0.5/2.5/10/25A 100/250/500/1000V DC. 0/2.5/10/25/100/250/500/1000V AC. 0/50uA/0.5/5/50/500mA/10A DC. 0/0.6k/6 meg/60 megohms OUR PRICE £15.05p P & Ins 60p</p> 	<p>KAMODEN HM720B FET VOM Input impedance 10 Megohms. Ranges: 0/2.5/12.5/10/50/100V DC. 0/2.5/10/25/50/100V AC. 0/25uA/2.5/25/250 mA DC. 0/5k/50k/500k/5 M 500 Megohm DC. OUR PRICE £24.30 P/P & Ins 60p</p> 	<p>370WTR MULTIMETER Features: current ranges: 20,000 opv. 0/0.5/2.5/10/50/250/500/1000V DC. 0/2.5/10/50/250/500/1000V AC. 0/50uA/1/10/100 mA/1/10A DC. 0/100mA/1/10A AC. 0/5k/50k/500k/5 Meg/50 Meg. Decibels: -20 to +62dB. OUR PRICE £21.50p P & Ins 60p</p> 	
<p>U4323 MULTIMETER 20,000 opv. Simple unit with audio/F oscillator. Suitable for general receiver tuning. Ranges: 0.5/2.5/10/50/250/500/1000V DC. 2.5/10/15/250/500/1000V AC. 0.05/0.5/5/50/500mA DC. Resistance x10, x100, x1,000, x10,000 (50/2, 500/2, 5k/2 centre scale). Battery operated. Size: 160 x 97 x 40mm. Supplied in carrying case complete with test leads. OUR PRICE £8.60p P & Ins 60p</p> 	<p>U4315 MULTIMETER Sturdy 43-range multimeter for current and voltage in DC AC circuits with freq. 45-200kHz and DC resistance, capacitance etc. Ranges: DC 50 μA/100μA/0.5uA/1/5/25/100/500/2500. DC 75mV/1/1V/2.5/5/10/25/100/250/500/1000. AC 0.5 mA/1/6/25/100/500/2500. AC 1V. 2.5/5/10/25/100/250/500/1000. DC 300Ω. DC 6k/2/50/600/5000. -15dB +2dB. Complete with steel carrying case and leads, manual. OUR PRICE £10.80 p/p & Ins. 60p</p> 	<p>U4317 MULTIMETER High sensitivity instrument for field and laboratory work. Knife edge pointer. 95mm mirror scale. Overload protection. Ranges: 100mV/0.5/2.5/10/25/50/100/250/500/1000 V DC. 0.5/2.5/10/25/50/100/250/500/1000V AC. Current: 50uA/0.5/1/5/10/50/250mA/1/5A DC. Resistance: 0.5/10/100/200 ohms/1/3/30/300k ohms. Decibels: -5 to +10dB. Battery operated. Size: 210 x 115 x 90mm. Supplied in carrying case complete with leads. OUR PRICE £18.35p P & Ins 60p</p> 	<p>U91 Clamp VOLT AMMETER For measuring AC volt and current without breaking circuit. Ranges: 300/600V AC. Current: 10/25/100/250/500A. Accuracy 4%. Size 283 x 94 x 36mm. Complete with carrying case, leads and fuses. OUR PRICE £15.10p P & Ins 60p</p> 	<p>KAMODEN 72.200 Multitester High sensitivity tester. 200,000 opv. Overload protected. Mirror scale. Ranges: -0/0.6/3/30/120/600/1200V DC. 0/3/12/60/300/1200 V AC. 0/5uA/1.2mA/120mA/600mA/12A DC. 0/12A AC. 20 to +63dB. 0/2k/200k/2 Meg/200 Megohms. OUR PRICE £24.30p P/P & Ins 60p</p> 	
<p>TMK 200 MULTIMETER KIT Build yourself a quality 20000 opv multimeter and save money. Complete kit with meter scale, movement and rotary range selector ready mounted in cabinet. All parts, batteries, test prods and instructions. Ranges: 0.0.6/6/30/120/600/1200V DC. 0.6/6/30/120/600/1200V AC. Current: 0.0.5/5/60/600mA. Resistance: 0.10/100k/1/10 Meg ohms. Decibels: -20 to +63dB. Size: 90 x 150 x 35mm OUR PRICE £9.65p P/P & Ins 30p</p> 	<p>U4315 MULTIMETER Ranges: DC 50 μA/100μA/0.5uA/1/5/25/100/500/2500. DC 75mV/1/1V/2.5/5/10/25/100/250/500/1000. AC 0.5 mA/1/6/25/100/500/2500. AC 1V. 2.5/5/10/25/100/250/500/1000. DC 300Ω. DC 6k/2/50/600/5000. -15dB +2dB. Complete with steel carrying case and leads, manual. OUR PRICE £10.80 p/p & Ins. 60p</p> 	<p>MODEL AS.1000 VOM 100,000 opv. Mirror scale. Built-in meter protection. 0/3/12/60/120/300/600/1200V DC. 0.3/3/12/30/60/120/300/600V AC. 0/10uA/0.1/1A/300mA. 12 Amp. 0/2K 200K/2M/200 Meg Ohm. 20 to 17dB. OUR PRICE £18.90p P & Ins 60p</p> 	<p>SWR METER Model SWR3 Handy SWR meter for transmitter antenna alignment, with built-in field strength meter. Accuracy 5%. Impedance 52 Ohm. 100uA DC. Full scale 5 section collapsible antenna. Size 145 x 50 x 60mm. OUR PRICE £4.55p P/P & Ins 60p</p> 	<p>TE-200 RF SIGNAL GENERATOR Accurate wide range signal generator covering 120 kHz-500 MHz on 6 bands. Directly calibrated. Variable R.F. attenuator audio output. Xtal socket for calibration. 220V/240V a.c. Brand new with instructions. Size 140mm x 218mm x 170mm. OUR PRICE £24.30p P & Ins 60p</p> 	
<p>MODEL C7208FM 30,000 opv DC. 15,000 opv AC. 6/3/15/60/300/600/1200V DC. 6/30/120/600/1200V AC. DC Resistance x1, x10, x100, x1000 (50/2 centre scale). DC Current 30uA/3/30/600mA. -20 to +63dB. OUR PRICE £9.65p P/P & Ins 30p</p> 	<p>TMK Model TW50K 46 ranges, mirror scale. 50kV/V DC. 50kV/V AC. DC Volts: 0.125/0.25/1.25/2.5/5/10/25/50/125/250/500/1000. AC Volts: 1.5/3/5/10/25/50/125/250/500/1000. DC current: 25/50uA/2.5/5/25/50/250/500mA/5/10/100mA. Megohm: 10k/100k/1M. Meg: 10 Meg ohms. -20 to +81.5dB. OUR PRICE £13.50p P/P & Ins 60p</p> 	<p>KAMODEN 360 MULTIMETER High sensitivity. DC 100kOhm/V. AC 10kOhm/V. 5" mirror scale, overload protection. Ranges: 0.5/2.5/10/50/250/1000V DC. 0.5/10/50/250/1000V AC. Current: 0.01mA/0.5/5/50/600mA/10A. Resistance: 0.1/1/10/100 ohms/1/10/100k ohms/10/100k ohms/10/100k ohms. Decibels: -20 to +62dB. Battery operated. Size: 180 x 140 x 80mm. Supplied complete with test leads etc. OUR PRICE £18.90p P & Ins 60p</p> 	<p>KAMODEN TT35 TRANSISTOR TESTER High quality instrument to test reverse leak current and DC current. Amplification factor of NPN, PNP diodes, transistors, SCR's etc. 4" square clear scale meter. Operates from internal batteries. Complete with instructions, leads carrying handle. OUR PRICE £18.90 P/P & Ins 60p</p> 	<p>MODEL TE15 GRID DIP METER Transistorised. Operates as Grid Dip Oscillator, Absorption Wave Meter and Oscillating detector. Frequency range: 440kHz - 280MHz in six coils. 500uA meter. 9V battery operation. Size: 180 x 80 x 40mm. OUR PRICE £18.90 P/P & Ins 30p</p> 	
<p>U4324 MULTIMETER High sensitivity. 20,000 opv. Ranges: 0.6/1.2/3/12/30/60/120/600/1200V DC. 3/6/15/60/150/300/600/900V AC. Current: 0.06/0.6/6/60/600mA/3A DC. 0.3/3/30/300mA/3A AC. Resistance: 25/500 ohms/0.5/5/50/500k ohms/5 Megohms. Decibels: -10 to +12dB. Size: 167 x 98 x 63mm. Supplied complete with test leads, spare diode and instructions. OUR PRICE £10.60p P & Ins 60p</p> 	<p>MODEL AF.105 VOM 50,000 opv. Mirror scale. Meter protection. 0/3/3/12/60/120/300/600/1200V DC. 0/6/30/120/300/600/1200V DC. 0/30uA/6/60/300 mA/12 Amp. 0/10K/1m/10m/100 Meg Ohms. -20 to 17dB. OUR PRICE £13.50p P/P & Ins 60p</p> 	<p>Model HT100B4 MULTIMETER Overload protected, shock proof circuits. 9.5uA Meter with mirror scale. Sensitivity 100kV. Polarity change switch. Ranges: 0.5/2.5/10/50/250/1000V DC. 2.5/10/50/250/1000V AC. DC resistance: 0.2/20k/220 Meg. ohms. DC current: 10/100uA/2.5/25/250 mA/10A. AC current: -0.10A. -20 to +62dB. Operates from 2 x 1.5V batteries. Size: 180 x 134 x 79mm. OUR PRICE £21.50p P & Ins 60p</p> 	<p>100TR MULTIMETER TRANSISTOR TESTER 100,000 opv. Mirror scale. Overload protection. 0/0.12/0.6/3/12/30/120/600V DC. 0/6/30/120/600V AC. 0/1/2/60uA/1/12/300mA/6/12A DC. 0/10k/1 Meg/100 Meg. 20 to +50dB. 0.01 - 0.2 MFD. Transistor tester measures Alpha, Beta and Ico. Complete with instructions, batteries and leads. OUR PRICE £22.65p P/P & Ins 60p</p> 	<p>SINCLAIR DM2 DIGITAL MULTIMETER Will measure AC and DC volts, AC and DC current, and resistance in a total of 20 ranges. The large light emitting diode display will read up to 1999 and automatically indicate polarity. Indication of positive and negative overload is also provided. The instrument is fitted with a combined carrying handle and bench stand and sockets are provided for the connection of an external power supply. OUR PRICE £63.70p P & Ins 50p</p> 	
<p>HIKI 750X VOLT OHM-MILLIAMMETER 43 ranges: 0 - 0.3/0.6/1.5/3/15/30/60/150/300/600/1200V DC. 0 - 3/6/15/30/60/150/300/600/1200V AC. Current: 0 - 30/60uA/1.5/3/15/30/150/300 mA/6/12A. Resistance: 0 - 3/300k/30M ohms. Decibels: -10 to +17dB. Output: 0 - 3/6/15/30/60/120/300V. Accuracy ± 3% DC, ± 4% AC. Sensitivity: 50,000 opv DC, 5,000 opv AC. 4 inch meter. Built in protection. Size: 57 x 102 x 153mm. OUR PRICE £12.90p P & Ins 60p</p> 	<p>U4313 MULTIMETER High sensitivity DC and 2,000 opv on AC and accuracy of 1.5% on DC and 2.5% on AC. Ranges: DC and AC. Current: 0.6 mA/3/15/60/300/1.5A. DC and AC Voltage: 1.5V/3/7.5/15/30/60/150/300/600/3C resistance 1kOhm/10/100/1,000. -10 to +12dB. etc. Complete with manual carrying case and leads. manual. OUR PRICE £14.90 p/p & Ins. 60p</p> 	<p>MODEL C7080EN Giant 6" mirror scale. 20,000 opv. 0/0.25/1/2.5/10/50/250/1000V DC. 0/50uA/1/10/50/250/1000V AC. Sensitivity 100kV/500V DC. 0/2k/200k/20 Meg. -20 to +50dB. OUR PRICE £21.50p P & Ins 60p</p> 	<p>CIS PULSE OSCILLOSCOPE For display of pulsed and periodic wave forms in electronic circuits. VERT. AMP Bandwidth: 10MHz. Sensitivity at 100kHz: 10V/VRMS/mm. 0.1 - 25. HOR. AMP Bandwidth: 500kHz. Sensitivity at 100kHz: 0.3 - 25. Preset triggered sweep 1 - 300uses. Free running 20 - 200 kHz in nine ranges. Calibrator pips 220 x 360 x 430mm. 115 - 230V AC. OUR PRICE £47.50 P/P & Ins £1 50</p> 	<p>CUSTOMER SERVICES Our Customer Services Division at Head Office will answer all your enquiries just ring 01-200 1321</p>	
<p>ALL PRICES INCLUDE VAT</p>					<p>EXPORT Personal exports arranged for overseas visitors. Goods specially packed, insured and despatched to all parts of the world at minimum cost exclusive of VAT. Payment by bank transfer, certified cheque, postal order or money order in any currency.</p>

a service that makes sense!

BUY AT LASKYS

TRANSISTORISED L.C.R. A.C. BR/8 MEASURING BRIDGE




A new portable bridge offering excellent range and accuracy at low cost. Resistance: 6 ranges: 0.1 ohm-11.1 megohm ± 1% Inductance: 6 ranges: 1 microhenry-111 henries ± 2% Capacity: 6 ranges: 10pf-1110 mfd ± 2% Turns Ratio: 6 ranges: 1.1/1000-1.11100 ± 1% Bridge Voltage at 1,000cps. Operated from 9-volt battery 100 microamp meter indication. Size 7 1/2" x 5" x 2" **OUR PRICE £29.70** P/P & Ins 60p

TE22 SINE SQUARE WAVE AUDIO GENERATOR



Sine 20cps to 200kHz on 4 bands. Square 20 cps to 30 kHz. Output impedance 5000 Ohms. 200/250V AC operation. Supplied brand new guaranteed, with instruction manual and leads. **OUR PRICE £26.90** P/P & Ins 60p

ARF 300 AF/RF SIGNAL GENERATOR



All transistorised compact fully portable. AF sine wave 18Hz to 220 kHz. AF square wave 18Hz to 100kHz. Output Square/Sine wave 10V. P-P RF 100kHz to 200MHz. Output 1V maximum. 220/240V AC operation. Complete with instructions and leads. **OUR PRICE £40.50** P/P & Ins 60p

MODEL TE20 RF SIGNAL GENERATOR



Six bands. 120kHz-250MHz. Dual output RF terminals. Separate variable audio output. Accuracy ± 2%. Audio output to 0V. Power requirements: 105-125V, 220-240V AC. Size: 193 x 285 x 150mm. Complete with test leads etc. **OUR PRICE £20.45** P/P & Ins 60p

HANIMEX HOC 1900 DIGITAL ALARM CLOCK



240V operation with large clear numbers, night light and snooze switch. Attractively finished in white and silver. **OUR PRICE £8.10** P/P & Ins £1.00
ALL PRICES INCLUDE VAT

LASKYS make sense of Hi-Fi

AUDIOTRONIC HEADPHONES

LSH20 Individual volume controls. Mono/stereo switch. 40-19,000 Hz. 8 ohms. **OUR PRICE £6.25** P/P & Ins 50p




LSH30 Individual tone and volume controls. Mono/stereo switch. 30-20,000 Hz. 8 ohms. **OUR PRICE £8.95** P/P & Ins 30p



LSH40 Two-way speaker system. Individual volume controls. 20-20,000 Hz. 8 ohms. **OUR PRICE £10.75** P/P & Ins 30p



NEW GOLORING G102 KIT



Belt-drive 2-speed turntable in kit form complete with pick up arm and head shell. **OUR PRICE £21.15** Ins £1.00

AUDIOTRONIC AHA101 Stereo Headphone Amplifier



All silicon, transistor amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. INPUTS: 5mV and 100mV. OUTPUT: 50mV per channel. **OUR PRICE £10.65** P/P & Ins 30p

RANK AUDIO RA 210T STEREO AMPLIFIER



75 7 1/2 watts rms. Inputs for magnetic phono, tuner, tape and aux. Separate base, treble, balance and volume controls. Headphone socket. Teak case. Unrepeatable offer. **OUR PRICE £21.85** P/P & Ins £1.00

MINIATURE ORGAN MUSIC MASTER AM100



Spanning nearly two octaves, including semitones. This instrument will give hours of enjoyment to all the family. Beautifully finished. The Keyboard range can be adjusted to be in tune with any instrument. Operates from internal 9V battery. Fitted with on/off switch, vibrato switch, earphone socket and external 9V D.C. socket. [Size 228mm x 127mm x 64mm] **OUR PRICE £9.95** P/P & Ins 60p

SUPERB QUALITY LOW PRICES

AUDIOTRONIC DIGITAL CLOCK RADIO

AOC22 24-hour clock radio. covering MW/FM wavebands. 180-minute sleep timer. Choice of Grey or White cabinet. **OUR PRICE £17.50** P/P & Ins £1.00



WALKIE TALKIES SKYFON NV75



Super low cost transmitter/receivers. 100MW with call buzzer and on/off volume control. 7 transistors. Telescopic rod antenna. **OUR PRICE £43.60** per PAIR/P/P & Ins 50p. NOT LICENSABLE IN THE U.K.

SINCLAIR Project 80 Modules

Z60 Power Amp	£5.95 P/P & Ins 15p
Stereo 80 Pre-Amp	£13.10 P/P & Ins 15p
Active Filter Unit	£7.40 P/P & Ins 15p
F14 Tuner	£13.10 P/P & Ins 15p
Stereo Decoder	£8.40 P/P & Ins 15p
P25 Power Supply	£4.65 P/P & Ins 30p
P26 Power Supply	£8.40 P/P & Ins 30p
P28 Power Supply	£7.90 P/P & Ins 30p
Transformer for P28	£5.10 P/P & Ins 30p

AUDIOTRONIC LOW NOISE CASSETTES

MODEL	5	10	15
C80	£2.05	£3.80	£5.50
C90	£2.11	£3.34	£7.57
C120	£3.59	£6.80	£9.64

AUDIOTRONIC HIGH ENERGY LOW NOISE CASSETTES

MODEL	5	10	15
C60LN	£3.59	£6.80	£9.64
C90LN	£6.13	£9.72	£13.77
C120LN	£6.15	£11.66	£16.52

p/p & Ins. 15p per order

ELIZABETHAN DCR26 DIGITAL CLOCK RADIO



A smaller than usual digital clock AM/FM radio, measuring only 8 1/2" x 3 1/2" x 4 1/4". The DCR is finished in simulated teak veneer and is fitted with a pre-set sleep timer switch that will turn on the radio at the precise time chosen (Mains operated) List Price £24.25 **OUR PRICE £14.90** P/P & Ins. £1.35

ELIZABETHAN 8/LZ-1



8-Track Stereo Player. Home 8-Track player with automatic and manual programme change and illuminated channel indicators for use with your hi fi system. Size 7 1/2" x 12" x 2 1/2". List Price £28.90 **OUR PRICE £14.90** P/P & Ins. £1.35

FREE HI-FI CATALOGUE




LASKYS 32 PAGE CATALOGUE AND PRICE LIST - absolutely free and available from all stores or by post (see coupon below). This exciting catalogue provides a comprehensive selection from the largest Hi-Fi Retailer in Europe - a MUST for every Hi-Fi enthusiast

ELECTRONIC CALCULATORS



We carry a tremendous range of both pocket and desk calculators from as little as £8.20. Owing to the demand it is not possible to include them in this advertisement, so send for our latest price list or call into any branch.

SPECIAL OFFER! SINCLAIR 4000 AMPLIFIER AND FM TUNER



Streamline elegance and great performance from SINCLAIR - the 4000 amplifier gives 17W RMS per channel (both drives) into 8 ohms, phones jack, active switchable scratch filter, low noise and distortion, and much more. List Price £74.95 p/p & Ins. **OUR PRICE £33.95** £1.65

A perfect match for the 4000 amplifier is the 4000 FM tuner, which boasts a capture ratio of 3dB, sensitivity of 3µV for 30dB quieting, stereo compression, etc. List Price £62.43 p/p & Ins. **OUR PRICE £29.95** £1.65

BELTEK C6260 AM/FM 8-TRACK IN-CAR PLAYER

The BELTEK C6260 includes AM/FM radio, and stereo 8-track cartridge player, with volume-tone and balance control, cartridge program indicator, automatic head cleaning, comes complete with installation kit, suppressors, and instructions. 12w Neg (Speakers not included) p/p & Ins. **OUR PRICE £22.50** £1.35

HIGH QUALITY CONSTRUCTION KITS

JUSTY KIT

ALL PRICES REDUCED TO CLEAR

LIMITED STOCKS AT Oxford Street, 42 & 152, Fleet Street, 311 Edgware Road, CROYDON BIRMINGHAM KINGSTON LEICESTER NORTHAMPTON SOUTHEND TUNBRIDGE WELLS WOLVERHAMPTON branches.

your nearest store



CENTRAL LONDON	(01)	LEICESTER 45 Market Pl	537678
481 Oxford Street, W1	493 8641	NORTHAMPTON	
10 Tottenham Court Rd, W1	637 2232	78 Abington Street	35753
33 Tottenham Court Rd, W1	636 2605	NOTTINGHAM	
42/45 Tottenham Ct Rd, W1	636 0845	5-7 Lower Parliament St	48987
257/8 Tottenham Ct Rd, W1	580 0670	OXFORD 16 Westgate Centre	722870
3 Lisie Street, WC2	437 8204	READING	
118 Edgware Road, W2	723 9789	6 Friars Walk, Friar Street	0734 595459
193 Edgware Road, W2	723 6211	RICHMOND 32 Hill Street	948 1441
207 Edgware Road, W2	723 3271	ROMFORD 86 South Street	20218
311 Edgware Road, W2	262 0387	SOUTHEND	
346 Edgware Road, W2	723 4453	205/206 Churchill West	612241
382 Edgware Road, W2	723 4194	TUNBRIDGE WELLS	
109 Fleet Street, EC4	353 5812	53/57 Camden Road	23242
152/3 Fleet Street, EC4	353 2833	WOLVERHAMPTON	
BIRMINGHAM		30 Wilfrun Way	23384
116 Corporation Street	021-236 3503	Opening October in Slough & Lewisham	
BRISTOL		All prices correct at 20/8/75 but subject to change without notice E. & D. E.	
16-18-20 Penn Street	20421		
CROYDON			
1046 Whitgift Centre	681 3027		
KINGSTON 38/40 Eden St	546 1271		

TO LASKYS CUSTOMER SERVICES DIVISION

Audiotronic House, The Hyde, London NW9 6JJ. Tel: 01-200 1321

Please send me the following items

Name _____

Address _____

Signature _____

TOTAL PURCHASE PRICE _____ (inc. P/P & Ins.)

Please send me your Free 32-page Hi-Fi catalogue price list I enclose cheque postal order money order

I wish to pay by Barclaycard/Access and my number is _____

Registered in England No. 347947 at 12 Lower Grosvenor Place, London SW1 0EX **PW11**

TRANSFORMERS

ALL EX-STOCK—SAME DAY DESPATCH

MAINS ISOLATING

115V or 240V Sec. only
CENTRE TAPPED AND
SCREENED

Ref.	VA	£	p & p
07	20	2 80	38
149	60	4 37	45
150	100	4 89	45
151	200	8 13	53
152	250	9 83	73
153	350	11 88	73
154	500	13 65	91
155	750	20 51	BRS
156	1000	29 15	BRS
157	1500	33 23	BRS
158	2000	37 07	BRS

12 and or 24 Volt PRIMARY 240-250 VOLTS

Ref.	No.	12v	24v	£	p & p
		0-5	0-25	1-35	23
		1-0	0-5	1-74	30
		1-0	1-0	2-29	38
		1-0	2-0	2-86	38
		1-0	3-0	4-12	45
		1-0	4-0	4-56	45
		1-0	5-0	5-14	53
		1-0	6-0	5-52	53
		1-0	8-0	7-28	60
		1-0	10-0	10-39	67
		1-0	15-0	13-59	83
		1-0	20-0	16-83	BRS

30 VOLT RANGE SECONDARY TAPS

0-12-15-20-25-30

Ref.	No.	Ampts	£	p & p
		0-5	1-81	30
		1-0	2-40	38
		2-0	3-49	38
		3-0	4-35	45
		4-0	5-15	45
		5-0	6-41	53
		6-0	7-16	60
		8-0	9-87	67
		10-0	9-90	73

50 VOLT RANGE SECONDARY TAPS

0-19-25-33-40-50

Ref.	No.	Ampts	£	p & p
		0-5	2-58	30
		1-0	3-38	38
		2-0	4-68	45
		3-0	5-31	53
		4-0	7-60	67
		6-0	12-10	67
		8-0	12-98	85
		10-0	16-99	BRS

60 VOLT RANGE SECONDARY TAPS

0-24-30-40-48-60

Ref.	No.	Ampts	£	p & p
		0-5	2-33	38
		1-0	3-41	38
		2-0	5-08	45
		3-0	7-52	60
		4-0	8-75	67
		5-0	9-75	73
		6-0	11-30	85
		8-0	15-00	BRS
		10-0	17-52	BRS
		12-0	19-98	BRS

AUTO TRANSFORMERS

Ref VA	Auto Taps	£	p & p	
113	20	0-115-210-240	1-67	30
64	75	"	2-90	38
4	150	0-115-200-220-240	4-12	45
66	300	"	5-82	53
67	500	"	8-82	67
84	1000	"	13-68	91
93	1500	"	18-11	BRS
95	2000	"	24-20	BRS
73	3000	"	35-09	BRS

CASED AUTO TRANSFORMERS

240V mains lead input and USA 2 pin outlets.

Ref	VA	£	P&P	Ref
113W	20VA	£3-23	P&P 38p	Ref 113W
4W	150VA	£6-70	P&P 62p	Ref 4W
67W	500VA	£10-45	P&P 80p	Ref 67W
84W	1000VA	£17-51	P&P BRS	Ref 84W

SCREENED MINIATURES

Ref mA	Volts	£	p&p	
238	200	3-0-3	1-54	10
212	1A	0-6, 0-6	1-84	30
113	100	9-0-9	1-41	13
235	330	0-9, 0-9	1-56	19
207	500	0-8-9, 0-8-9	1-92	30
208	1A	0-8-9, 0-8-9	3-30	38
236	200	0-15, 0-15	1-43	19
214	300	0-20, 0-20	1-93	30
221	700(DC)	20-12, 0-12-20	2-17	38
206	1A	0-15-20, 0-15-20	3-46	38
203	500	0-15-27, 0-15-27	3-00	38
204	1A	0-15-27, 0-15-27	3-85	38
5112	500	12, 15, 20, 24, 30	1-88	37

HIGH VOLTAGE

Ref	VA	£	p & p	
	60	243	4-37	63
	350	247	10-41	95
	1000	350	27-06	BRS
	2000	252	41-07	BRS

PLUS

BRIDGE RECTIFIERS

50V	2A	35p
100V	2A	40p
200V	1A	45p
400V	4A	65p
600V	2A	50p
500V	10A(PM 7A6)	£2-35

TEST METERS

AVO 8 MK5	£50-80
AVO 72	£19-75
U4313*	£11-80
U4315*	£13-85

*(USSR) inc. steel carrying case
P & P 95p

ANTEX SOLDERING IRONS

15W	£2-68	18W	£2-45	25W	£2-26
-----	-------	-----	-------	-----	-------

SOLDERING IRON KIT £3-61
STAND FOR ABOVE £1-13
P & P 25p

MAGNETIC TO CERAMIC
CARTRIDGE CONVERTOR
OPERATING VOLTAGE 20-45V
ONLY £2-65 P & P 18p

PLEASE ADD VAT AFTER P. & P.
AUDIO ACCESSORIES & BARGAIN COMPONENT PAKS
ELECTROSIL & SEMICONDUCTOR STOCKIST
Callers Welcome (Mon.-Fri.) or send stamp for lists.

Barrie Electronics Ltd.
3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/8
NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST

TOROIDAL TRANSFORMERS FOR THE TEXAN II

Designed by S.I.G.A. ELECTRONICS in conjunction with Texas Instruments for uprating Texan 20+20 Amplifiers. Pri. 220-240V; 50Hz; Screen; Sec. 25-20-0-20-25V, 1-5A. Fully impregnated; flying lead connections.
Ref. T1295 Price £6-70 + 25% VAT post 50p.

Ref. T1295/F with resin filled centre, 2BA clear hole.
Price £7-10 + 25% VAT post 50p.

Toroidal transformers suitable for Audio Power Supplies
Pri. 240V 50Hz; Screen; fully impregnated; flying leads

REF SECONDARIES	O.D. (cms)	HT.	Price	Post
315 (a)	33-0-33V 2A	12-0 x 4-4	£8-50	£0-69
	(b) 25-0-25V 0-1A			
291 (a)	33-0-33V 4A	13-0 x 5-7	£10-69	£0-78
	(b) 25-0-25V 0-2A			
061	20-0-20V 1A	7-9 x 4-3	£4-87	£0-50
360	25-0-25V 1-5A	7-7 x 4-5	£6-26	£0-50
285	25-0-25V 2A	9-0 x 5-1	£6-37	£0-60
284	0-45V 1A	9-5 x 4-4	£5-15	£0-60
000	0-45V 2A	11-3 x 3-8	£6-64	£0-69

Terms: Cash with order, please add 25% VAT to goods only.
Quantity discounts available on request.

Dept. PW 05

S.I.G.A. (ELECTRONICS) LIMITED
Sunderland Road, Sandy, Beds
SG19 1QY

PA50



£11-00

CARR. PAID

50W RMS into 8 Ω
with PP50/2 or
100W into 16 Ω
with two PA50
bridged and PP50/3.

RP3



£8-50

CARR. FREE
S/C and THERMAL PROTECTION.
Ripple at 3A—1mV. Needs 30V 4A D.C. supply
PP30/4. Complete with controls and instructions.


ZENTAC STUDIO QUALITY MODULES

Noise 70db
Less than 2% T.H.D.
±38V D.C. max
S/C, O/C, thermal prot.
20HZ-20K HZ power b/wdth.
Continuously rated. 500mV
into 10K ohms. 5 easy con-
nections plus two for bridge/
normal operation. Complete
with heat sink and full
instructions. All ratings ±
5db.

COMING SOON!
Encapsulated version of
PA100 and 4 Ω version
of PA50

REGULATED
MODULE giving
3A at 24V falling
to 2A at 6V. Current
LIMIT AND VOLTAGE
CONTINUOUSLY VARIABLE.
S/C and THERMAL PROTECTION.

PA100

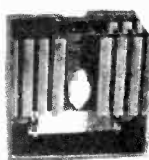

£14-25

CARR. PAID

100W RMS into 4 Ω
with PP50/3 or 75W
with PP50/2. Two
PA100 bridged give
150W into 8 Ω with
PP50/4 or 200W
with PP50/6.

POWER SUPPLIES

PP50/2	£9-00
PP50/3	£10-50
PP50/4	£12-00
PP50/6	£16-00
PP30/4	£7-00

50p Carriage

ALL
PRICES
FULLY INC

ZENTAC
265 PENTONVILLE ROAD
KING'S CROSS, LONDON
N1 01-837 2382

MAIL
ORDER
ONLY

AMTRON KITS

- UK105/C FM Microtransmitter **£8.07**
- UK220 Signal Injector **£3.53**
- UK230 AM/FM Antenna Amplifier **£4.16**
- UK285 UHF/VHF Antenna Amplifier **£8.87**
- UK302 4Ch. Radio Control Transmitter **£17.50**
- UK345/A Superhet R/C Receiver **£8.81**
- UK325 GXC 2Ch. R/C Splitter 1000Hz. & 2000Hz. **£8.34**
- UK330 GXC 2Ch. R/C Splitter 1500Hz. & 2500Hz. **£8.34**
- UK555 Radio Control Strength Meter **£9.65**
- UK780 Electronic Metal Detector **£11.65**
- UK875 Capacitive Discharge Electronic Ignition Kit Neg. Earth **£17.33**

723	FAIRCHILD 14 Pin DIL var. voltage Regulator 55p	ZN 414	FERRANTI Radio Chip £1.25
741	FAIRCHILD 8 Pin DIL Op-amp 30p	MFC 4000 B	MOTOROLA $\frac{1}{2}$ Watt Audio Amp 75p
NE 555v.	SIGNETICS 8 Pin DIL Timer 60p	MC 1310P	MOTOROLA 14 Pin DIL Coileless Stereo Decoder £2.10

MOTOROLA SMALL SIGNAL PLASTIC TRANSISTORS (TO 92)

Type No.	Polarity	Vceo Vdc	IcMAX mA dc	hFE @ Ic=2mA dc Vce=5Vdc	Price
BC237	NPN	45	200mA	120-460	15p
BC238	NPN	20	"	120-800	12p
BC239	NPN	20	"	120-800	15p
BC307	PNP	45	200mA	70-460	15p
BC308	PNP	25	"	70-460	13p
BC309	PNP	20	"	120-460	15p
BC317A	NPN	45	150mA cont.	110-220	18p
BC318B	NPN	30	cont.	200-450	18p
BC319C	NPN	20	300 Pk.	420-800	20p
BC320A	PNP	45	150mA cont.	110-220	20p
BC321A	PNP	30	200 Pk.	200-450	20p
BC322B	PNP	20	"	"	20p
BC327	PNP	45	1A Peak	40 Min. @ Ic=300mA Vce=1V	20p
BC328	PNP	25	"	"	18p
BC337	NPN	45	"	"	18p
BC338	NPN	25	"	"	16p
BC347	NPN	45	100mA	40-450	13p
BC348	NPN	30	"	"	12p
BC349	NPN	20	"	"	12p
BC350	PNP	45	"	"	15p
BC351	PNP	30	"	"	15p
BC352	PNP	20	"	"	15p

MACK'S ELECTRONICS for


MOTOROLA McMos®

- MC14001CP Quad 2 Input NOR **18p**
- MC14002CP Dual 4 Input NOR **20p**
- MC14011CP Quad 2 Input NAND **18p**
- MC14015CP Dual 4 Bit Static Shift Register **£1.26**
- MC14017CP Decade Counter **£1.22**
- MC14021CP 8 Bit Static Shift Register **26p**
- MC14023CP Triple 3 Input NAND **£1.26**
- MC14027CP Dual J-K Flip-Flop **86p**
- MC14042CP Quad Latch **£1.26**
- MC14046CP Phase Locked Loop **£1.85**
- MC14049CP Hex Inverter Buffer **61p**
- MC14510CP BCD Up-Down Counter **£1.40**
- MC14511CP BCD 7 Segment Latch Decoder Driver **£2.12**
- MC14528CP Dual Monostable **96p**

TTL TEXAS TTL TEXAS

- SN7400N Quad 2 Input NAND **16p**
- SN7402N Quad 2 Input NOR **16p**
- SN7404N Hex Inverter **19p**
- SN7413N Dual NAND Schmitt Triggers **32p**
- SN7447AN BCD To 7 Segment Decoder Drive **95p**
- SN7472N J-K Master-Slave Flip-Flops **26p**
- SN7473N Dual J-K Master-Slave Flip-Flop **30p**
- SN7475N 8 Bit & 4 Bit Bistable Latches **50p**
- SN7490N Decade Counter **50p**
- SN7493N 4 Bit Binary Counters **50p**
- SN7495N 4 Bit Right Shift Left Shift Registers **70p**
- SN74121N Monostable Multivibrators **35p**

SUPERTESTER 680 R ICE

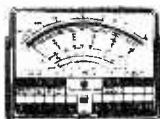

10 Fields-80 Ranges: Plus a lot of accessories for measurements of 500A-AC 100 A/DC - Temperature -50C to +200C- Magnetic fields up to 15 KGauss- Phase Indicator- EHT 25kV Electronic Volt Ohm-meter-Transistor Diode Tester, etc. Dimensions: 128 x 95 x 32 mm-300 grams 20kOhm/V-Accuracy 1% DC. Ask for free catalogue.

Accessories extra **£19.95**

NATIONAL SEMI-CONDUCTOR

LM 380 N

14 Pin DIL 2 watt Audio Amp
£1.20

NATIONAL SEMI-CONDUCTOR

MM 5314

24 Pin DIL Clock Chip
£4.35

NATIONAL SEMI-CONDUCTOR

LM 1303

14 Pin DIL Stereo Pre-Amp
£1.65

EUROSIL

E 1109

24 Pin DIL Clockchip
£7.78

NATIONAL SEMI-CONDUCTOR

LM 3900 N

14 Pin DIL Quad Amp
69p



I.C. INSERTION TOOL


Aligns pins for direct insertion

£1.45

EXTRACTION TOOL **45p**

LITRONIX

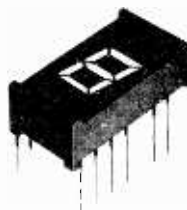7 SEGMENT LED DISPLAYS
DL707 common anode DP left
DL704 common cathode DP right



£1.80 each; 4 for **£7**; 6 for **£10**.
 14 pin DIL sockets **16p**

MACK'S ELECTRONICS

283 Edgware Road, London W2.

Tel. 01-262 8614

Hours of business 9.30 - 6.00

Monday to Saturday

Callers welcome

ALL PRICES INCLUDE VAT

PLEASE ADD 20p P & P

RTVC

FOR SPEAKERS AT FANTASTIC REDUCTIONS

NEW!



LE-4 SPEAKERS

Superb performance and beautifully finished in selected teak veneers. A professional standard four-way speaker system giving 25 watts RMS power handling. Bass unit is 14" x 9" with 8" x 5" unit for mid-range and twin 3" high frequency units to give monitor type quality and performance.

Specification — Size 33" x 14" x 16" approx. Impedance 8 ohms. Power handling 25W RMS. (Peak 50 watts.) Frequency range 35 Hz—20 KHz.


Our Price £34.00 each
(normally £66.00) + £5.80 p & p.
Scotland and the Orkneys
P & P Surcharge £3.50

THE 'COMPACT'

EASY BUILD SPEAKER KIT

A compact bookshelf speaker system giving a high electro acoustic efficiency for the low powered amplifier. The professional finish can be obtained with the minimum of tools, the infinite baffle type enclosures come ready mitred and professionally finished, simply apply glue, fold up around baffle board, and fix together with masking tape till glue dries.

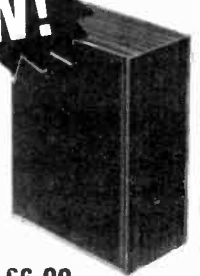The cabinet measures 12" x 9" x 5" deep approx finished in simulated teak, incorporating a quality 7" x 4" elliptical speaker, power handling 4 watts, flux density 30,000 maxwells, impedance 8-15 ohms nominal, voice coil dia 3" magnet size 2 7/8" approx.



£6.00
pair inclusive P & P £1.70

EASY TO BUILD SPEAKER KITS

These superb simulated teak-finished speaker kits have been specially designed by RT-VC for the cost-conscious hi-fi enthusiast who wants top quality speakers but doesn't want to spend the earth. Built to EMI's exacting specification, these new RT-VC speaker kits (350 type kit) incorporate 13" x 8" woofer, 3 1/2" tweeter and matching crossover.

Easily put together with just a few basic tools.
Specification (each speaker): Impedance 8 ohms. Power handling 15 watts RMS (30 watts peak). Response 20—20,000 Hz. Size 20" x 11" x 9 1/2" approx. Comparable built units (EMI LE3) sold elsewhere for over £45 pair.



£22.00 pair complete + £5.20 p & p.
Complete with crossover Components and circuit diagram



EMI 350 KIT

System consists of a 13" x 8" approx woofer with a 3" tweeter, crossover components and circuit diagram. Frequency response: 20 Hz to 20 KHz. Power handling 15 watts RMS into 8 ohms. (Peak 30 watts.)

£7.25 + £1.20 p & p.

Complete with crossover Components and circuit diagram

RTVC*

VISCOUNT IV STEREO SYSTEM

System 1a. £69.00

The new 20+20 watt Stereo Amplifier incorporating the latest silicon transistor solid state circuitry, the RT-VC VISCOUNT IV gives you a powerful 20 watts RMS per channel into 8 ohms. Superb teak-finished cabinet, with anodised fascia to harmonise with any decor. Polished trim and knobs.

The VISCOUNT IV has a comprehensive range of controls — volume, bass, treble, balance, mono/stereo, mode selector, and scratch filter.

Front panel socket for stereo headphones. And a host of sockets at the rear — for left and right speakers, tape recorder, auxiliary, tuner, disc and microphone.

SPECIFICATION: 20 watts RMS per channel 40 watts peak. Suitable 8-15 ohms speakers. Total distortion @ 10 watts better than 0.2%. Six switched inputs: 1. Magnetic P.U. — 3 millivolts @ 47 K ohms (R.I.A.A.); 2. Crystal/ceramic P.U. — 50 millivolts @ 50 K ohms (R.I.A.A.); 3, 4, 6. Tape Tuner/Aux. — 140 millivolts @ 50 K ohms (flat frequency response); 5. Microphone — 3 millivolts @ 50 K ohms (flat frequency response).

CONTROLS: Push button ON/OFF, stereo/mono, scratch filter, 6 position rotary selector. Individual rotary controls for treble, bass, balance and volume. Headphone socket, tape out socket. Aux. mains output. **Frequency response:** 25 Hz to 25 KHz @ full rated output. **Signal to noise ratio:** better than -50 dB on all inputs. **Tone control range:** Bass ± 15 dB @ 50 Hz; Treble ± 12 dB @ 10 KHz.

Power requirements: 200-250V A.C. mains @ 60 watts. **Approx. size:** 15 1/2" x 3" x 10".

MP60 type deck with magnetic cartridge, de luxe plinth and cover.

Two Duo Type IIIa matched speakers — Enclosure size approx. 19 1/2" x 10 1/2" x 7 1/2" in simulated teak. Drive unit 13" x 8" with 3" tweeter. 15 watts handling, 30 watts peak.

Complete System with these speakers £69.00 + £6.50 p & p.

System 2. £85.00

Viscount IV amplifier (As System 1a)
MP60 type deck (As System 1a)

Two Duo Type III matched speakers — Enclosure size approx. 27" x 13" x 11 1/2". Finished in teak simulate. Drive units 13" x 8" bass driver, and two 3" (approx.) tweeters, 20 watts RMS, 8 ohms frequency range — 20 Hz to 18,000 Hz.

Complete System with these speakers £85.00 + £7.60 p & p.

PRICES: SYSTEM 1a

Viscount IV R103 amplifier £27.50 + £1.90 p & p.

2 Duo Type IIIa speakers £30.00 + £8.50 p & p.

MP60 type deck with Mag. cartridge de luxe plinth and cover £22.00 + £3.30 p & p.

Total if purchased separately: £79.50

Available complete for only: **£69.00**

+ £6.50 p & p.

PRICES: SYSTEM 2

Viscount IV R103 amplifier £27.50 + £1.90 p & p.

2 Duo Type III speakers £46.00 + £7.50 p & p.

MP60 type deck with Mag. cartridge de luxe plinth and cover £22.00 + £3.30 p & p.

Total if purchased separately: £95.50

Available complete for only: **£85.00**

+ £7.60 p & p.

NEW!



20x20 SYSTEM

Scotland and the Orkneys P & P Surcharge
System 1a £1.70 System 2 £1.50

PUSH BUTTON CAR RADIO KIT— THE TOURIST TT*



NO SOLDERING REQUIRED

NOW BUILD YOUR OWN PUSH BUTTON CAR RADIO

Easy to assemble construction kit comprising fully completed and tested printed circuit board on which no soldering is required. All connections are simple push fit type making for easy assembly. Fine tuning push button mechanism is fully built and tested to mate with printed circuit board.


TECHNICAL SPECIFICATION: (1) Output 4 watts RMS output. For 12 volt operation on negative or positive earth. (2) Integrated circuit output stage, pre-built three stage IF Module.

Controls volume manual tuning and five push buttons for station selection, illuminated tuning scale covering full, medium and long wave bands.

Size—chassis 7" wide 2" high and 4 1/4" deep approx. **£9.50** +£1.05 p & p. Speaker including baffle and fixing strip **£2.00** +45p p & p. Car Aerial Recommended — fully retractable **£1.60** +40p p & p.

The Tourist 1 Kit For the experienced constructor. If you can solder on a printed circuit board you can build this model. Same technical specification as Tourist TT. **Price £8.20** +£1.05 p & p.

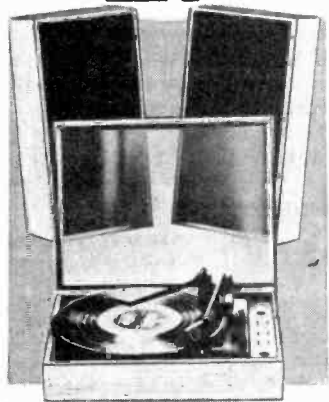*STEREO 21 QUALITY SOUND FOR LESS THAN £24.00



Stereo 21, easy to assemble audio system kit. No soldering required.

The unit is finished in white P.V.C. and the acrylic plinth presents an unusually interesting variation on the modern deck plinth.

Includes — BSR 3 speed deck, automatic, manual facilities together with stereo cartridge.

Two speakers with cabinets

Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.

Specifications — For the technically minded:

Input sensitivity 600mV Aux. input sensitivity 120mV Power output 2.7 watts per channel. Output impedance 8—15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs — radio, tape, etc., and outputs for taping discs.


Overall Dimensions. Speakers approx 15 1/2" x 8" x 4". Complete deck and cover in closed position approx. 15 1/2" x 12" x 6".

Complete only £23.20 +£3.00 p & p.

Extras if required. Optional Diamond Stylus **£1.60**.

Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance **£5.80**.

*DISCO AMPLIFIER

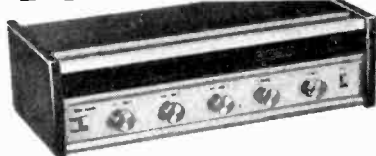

Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties. Output 20 watts RMS into 8 ohms (suitable for 15 ohms).

Inputs *4 electrically mixed inputs. *3 individual mixing controls. *Separate bass and treble controls common to all 4 inputs. *Mixer employing F.E.T. (Field Effect Transistors). *Solid State circuitry. *Attractive styling.

INPUT SENSITIVITIES — Input — 1). Crystal mic. guitar or moving coil mic, 2 and 10mV. (Selector switch for desired sensitivity.) — Inputs — 2), 3), 4). Medium output equipment — ceramic cartridge, tuner, tape recorder, organs, etc — all 250mV sensitivity. AC Mains, 240V operation. Size approx. 12 1/2" x 6" x 3 1/4".

£20.00 +£1.35 p & p.

8 TRACK HOME CARTRIDGE PLAYER



Elegant self selector push button player for use with your stereo system. Compatible with Viscount IV system. Unisound module and the Stereo 21. Technical specification Mains input, 240V, Output sensitivity 125mV.

Yours for only

£16.20 +£1.70 p & p.

BUILD YOUR OWN STEREO AMPLIFIER*




For the man who wants to design his own stereo — here's your chance to start, with Unisound — pre-amp, power amplifier and control panel. No soldering — just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only.

Also available with 2 speakers (7"x4") **£10** + £1.75 p & p. **£8.95** +£1.05 p & p.

Also available with the 'Compact' (see opposite page) easy build speaker kit **£13.50** +£2 p & p.

PORTABLE DISCO CONSOLE*

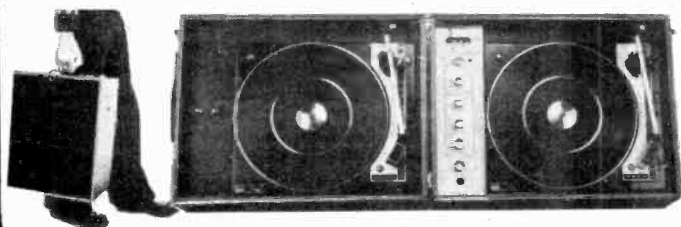

INCORPORATES: Pre-Amp with full mixing facilities, including switched input for mic with volume control, switched input for auxiliary with volume control, bass and treble controls, volume control and blend control for turntables. Two B.S.R. MP60 type single play professional series decks, fitted with crystal cartridges.

TECHNICAL SPECIFICATION:

Pre-amp — Output — 200mV. Auxiliary inputs — 200mV and 750mV into 1 meg. Mic input — 6mV into 100K. 240 volt operation. Turntables capacity — 7", 10" or 12" records. Rumble, wow and flutter Rumble Better than —35dB. Wow Better than 0.2%. Flutter Better than 0.06% (Gaugmont kalee meter).

Finish — Satin black mainplate with black turntable mat inlaid with brushed aluminium trim. Tonearm and controls in black and brushed aluminium.

Console size —

Unit Closed — 17 1/2" x 13 1/2" x 8 1/2" (app.)
Unit Open — 35 1/2" x 13 1/2" x 4 1/2" (app.)
This disco console is ideally matched for the Reliant IV and Disco 50 or any other quality amplifier.

The unit is finished in black PVC with contrasting simulated teak edging, diamond spun control knobs with matching control panel.

Yours for only

£49.00 +£6.50 p & p.



DO NOT SEND CARD

Just write your order giving your credit card number

Mail orders to Acton. Terms C.W.O. All enquiries stamped addressed envelope. Goods not despatched outside U.K.

*Leaflets available for all items listed thus * Send stamped addressed envelope. All items subject to availability. Prices correct at 1st Sept 1975 and subject to change without notice.

All prices include VAT at current rates



21C HIGH STREET, ACTON, LONDON W3 6NG
323 EDGWARE ROAD, LONDON W2

Personal Shoppers EDGWARE RD: 9 a.m.—5.30p.m. Half day Thurs
ACTON: 9.30a.m.—5p.m. Closed all day Wed.

The future of Amateur Radio

THE life blood of amateur radio is the spectrum space allocated to the amateur service between 1.8MHz and 25GHz. Without these precious frequencies, the radio amateur of today would become just another broadcast station listener. The regulation of the frequencies available to the various services, i.e. aeronautical, amateur, broadcasting, marine and so on, is governed by the conferences of the International Telecommunication Union which is the specialist agency of the United Nations for telecommunications. During the ITU conference the 144 member nations of the ITU vote on the proposals before them and in this way the future of frequency allocations is determined.

The last major ITU conference was in 1959 and there has been relatively little change in the spectrum allocation for amateurs since that time. The next major meeting is scheduled for October 1979 and the agenda will include a review of all frequencies comprising the usable spectrum. This means that each and every amateur service allocation will come under the scrutiny of the conference. On their decision alone will depend whether your present equipment will continue to be usable, or will be just another piece of surplus gear.

The possibilities and dangers arising from the 1979 World Administrative Radio Conference have been known and recognised by national societies and the International Amateur Radio Union for some considerable time. A great deal of preparatory work has already been undertaken and it is now clear that the amateur service will at this conference present a unified plan for its future modified only by minor regional differences. At the conferences of the ITU only the member nations are eligible to vote. However, the IARU is one of the few organisations recognised by the ITU and therefore entitled to attend its conferences as an observer where it may also speak and present papers.

Thus, while the IARU may participate actively in the conference its most essential work must take place in the co-ordination and advice offered to national societies throughout the world. It is the national societies only who can approach their own telecommunication administrations to seek their support for the future of the amateur service. It will be appreciated that in many countries this is a difficult task, never more difficult than in Africa. This is a challenge which has been accepted by the IARU and the national societies and the work of securing support for radio amateurs will continue without slackening until October 1979.

It would be unwise to give publicity to much of the work that has been, and will be done, and it is only the result that can prove its effectiveness or otherwise.

Now, as never before, the amateur service must be seen by all who come into contact with it to be something that is worth retaining and whose work and activity justify the present spectrum space allocated to it. Every radio club in every country has a part to play in this effort. It is the local radio clubs who bring together the individual radio amateurs and who form the backbone of the national societies. Those responsible for the conduct of a radio club should familiarise themselves with the position as it is today and with the steps that must be taken if the future is to be assured. Having done this they can then offer guidance to the individual members and initiate activity which will be of benefit not only to the amateur service but hopefully to the community at large.

continued on page 551

NEWS...

Practical Wireless P. C. Board Readers Service

IN the October issue of Practical Wireless we announced that this magazine will be introducing a 'new' readers service whereby our 'copyright' printed circuit boards for selected PW constructional projects will be offered to readers.

We are anxious this service shall represent good value and our boards to be of the highest standards, therefore we are taking a further month to finalise the details which we hope to publish in full in the near future.

Reprints

WE still have some copies of the Tele-Tennis reprints. If you would like one, send 82p to: Chief Cashier, (P.W. Tele-Tennis, IPC Magazines, Tower House, Southampton St., London, WC2E 4QX.

Special offer

HI-FI enthusiasts buying cassette decks which accept chromium dioxide cassettes will find there is a dearth of pre-recorded CrO₂ cassettes. To ensure that purchasers of BASF machines are able to use their machines to the full, BASF is giving them the opportunity to buy BASF pre-recorded CrO₂ cassettes at special low prices.

The repertoire contains 22 titles, four of which are double albums. The price of the cassettes is £3.90 for a single album and £5.80 for a double album, but BASF are offering them at £1.99 and £2.99 (inclusive of VAT) respectively. Six of the titles have been recorded in quadraphonic and these are available at no extra cost.

All the purchaser has to do is ask for a BASF Cassette Offer order form when he buys a BASF machine, tick the titles he wants and send the form with a cheque or postal order for the correct amount to BASF at its Knightsbridge, London, address. Customers may only send in one order form so they should ensure that they have all the titles they require.

Practical Wireless, November 1975

NEWS...

NEWS...

NEWS...

Heathkit Catalogue



MANY interesting new models are introduced in the latest Heathkit Catalogue: They are TM-1626 Stereo Microphone Mixer; TA-1620 Public Address Control Amplifier with optional Booster Amplifier, Speaker Column, or Distribution Transformer; ID-1590E Digital Electronic Wind Speed and Direction Indicator; IM-1212 Digital Multimeter; IO-4560 DC-5MHz, 100mV Oscilloscope; IO-4540 DC-5MHz, 20mV Oscilloscope; IG-4505 Oscilloscope Calibrator; IP-2700 Series of Digital and Analogue Power Supplies; IMA-18-1 Solid-state Conversion Kit for valve-type Heathkit VVm's; SR-205 Single Pen Chart Recorder; SR-206 Dual Pen Chart Recorder.

Heath also tell us that their electronic organ (shown in October "Production Lines") is on show at the Tottenham Court Road showroom.

The latest Heathkit Catalogue is now available: To postal enquiries, enclosing a 10p stamp for return postage, from: *Heath (Gloucester) Ltd., Bristol Road, Gloucester GL2 6EE.*

"Radio Exchange"


DUE to a printing error the above advertiser's full page advertisement in the September, 1975 issue was incorrectly priced. The magazine apologises for any inconvenience caused to readers.

Practical Wireless, November 1975

British 'Scope

THE only independent British oscilloscope manufacturers, Scopex Instruments, have just launched an addition to their range of low cost oscilloscope. The new 'scope, called the 4S-6, is intended for use in educational, service and amateur areas.

The new instrument follows the design philosophy of other machines in the range with emphasis on ease of use, with controls kept to a minimum and well labelled. Price is only £88 yet the specification is equivalent to similar units costing as much as twice that price. Main features are a maximum sensitivity of 10mV/cm and a bandwidth of 6MHz. The screen is a big 6×8cm for ease of viewing. The weight of the unit is only 4.5kg making it eminently suitable for field work. One feature of the 4S-6 only found on oscilloscopes

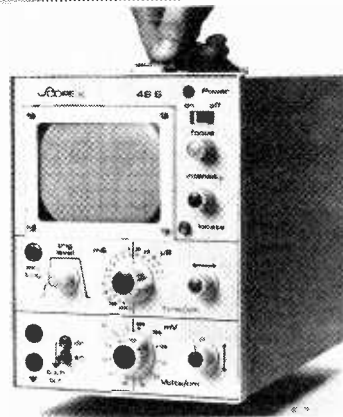

costing about £100 more is the beam locate facility which allows even the most inept operator to locate and return the trace to screen.

For further information contact *Scopex Instruments, Pixmore Industrial Estate, Pixmore Avenue, Letchworth, Herts.*

THE FUTURE OF AMATEUR RADIO

—continued from page 550

There are several forms of scientific activity in which the individual radio amateur can participate and play a valuable part. There is no other organisation in the world that can command the services of so many able technicians capable of carrying out specialist work at no cost to the community. As an example, we cite propagation research, possibly using the beacons already established in several parts of the world. Amateur progress in microwaves has astonished professional workers and this is a fertile field for experiment and development. The amateur satellite programme is another area where the skills of construction or mere observations can vitally assist research activity. In addition to participation in scientific activity the radio amateur must ensure that his transmissions are beyond reproach both in technical characteristics and in the messages conveyed. There are many listeners to amateur radio transmissions and the listener can only judge the quality by what he hears. Regrettably in many cases the quality leaves much to be desired.

The Radio Society of Great Britain* has always played a leading part in the representation of amateur radio at international levels. It is already heavily involved in the preparations for 1979 and will continue to make a maximum effort on behalf of all UK radio amateurs.

The future of amateur radio now depends upon the IARU, the national societies, the local clubs and, not least of all, the individual operator. Will you play an active and responsible part in the world wide activity intended to ensure the future of amateur radio?

LIONEL E. HOWES—Editor

* Radio Society of Great Britain, 35 Doughty Street, London, WC1N 2AE

DIGITAL READOUT SYSTEM

for FM tuners

PART 1 Martin Oliver*



WITH the increasing number of local radio stations occupying the VHF band, an accurate frequency indication is very desirable. The tuning scale provided on most FM tuners is rarely accurate enough to differentiate between two adjacent stations because it depends on the linearity of a variable capacitor, or a varicap diode for its accuracy. This problem is overcome in very expensive synthesiser tuners by generating the local oscillator digitally using a programmable frequency divider and a reference oscillator.

It is possible to provide the same digital display of frequency with a conventional tuner by counting the local oscillator frequency, and this method does not require much modification of the tuner.

The frequency counter described in this article gives an accurate tuning indication over the 88-108 MHz band, and can be easily modified to cover other ranges. It was designed to be used with a Heathkit model AJ1214, but it should work with most transistor tuners.

ISOLATION

It is important that the tuner chassis is fully isolated from the mains. Most modern tuners use a mains transformer to provide a low voltage supply for transistor circuits, and the chassis is connected to earth through the mains plug or is left floating. Check carefully that the chassis is not connected

directly to the line or neutral pin of the mains plug as it is then dangerous to connect external components to it and this circuit **must not** be used.

One problem which usually occurs, when building high frequency circuits is the need for special equipment, such as HF signal generators and oscilloscopes to set the circuit up. To get around this problem, broadband circuits are used in the HF sections of this design so there are no coils to be aligned, and the only equipment needed is a multimeter.

The unit is built on Veroboards contained in a separate metal case, and is connected to the tuner by coax cable. A metal box is needed as a screen between the tuner's sensitive front end and the logic ICs.

FM TUNER OPERATION

Before explaining how the circuit works, a brief description of the operation of an FM tuner may be useful. Fig. 1 shows a simplified block diagram of a

*Formerly with Texas Instruments.

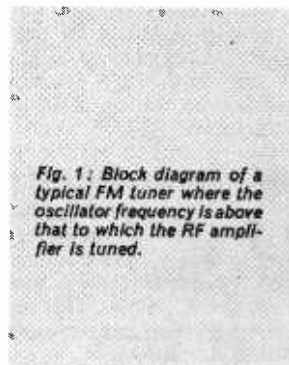
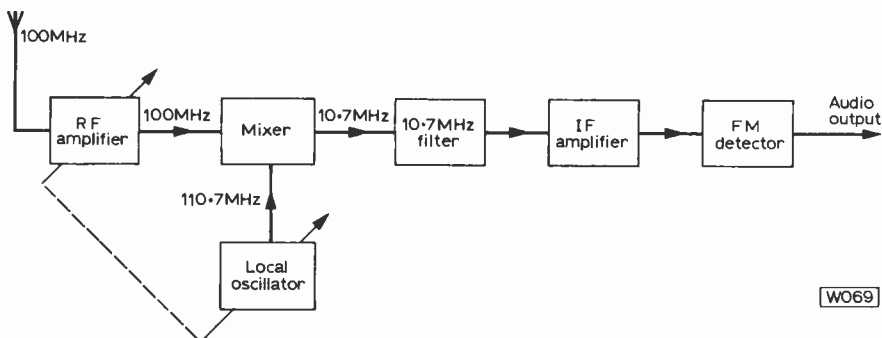


Fig. 1: Block diagram of a typical FM tuner where the oscillator frequency is above that to which the RF amplifier is tuned.

W069

"conventional" tuner. It is assumed to be tuned to a station on 100.0MHz. A signal picked up by the aerial is amplified by the RF amplifier to a level suitable for the mixer. The local oscillator runs at a frequency 10.7MHz above or below the frequency to which the RF amplifier is tuned. The output from the mixer is the IF frequency which is the difference between these two signals, i.e. 10.7MHz. The mixer feeds the IF amplifier via a bandpass filter which gives the tuner its selectivity.

It is not possible to measure directly the frequency of the signal from the aerial because this consists of many other stations apart from the one being received. Because of this the local oscillator is used, but as this is not the same frequency as the station being received, a correction must be made in the counting circuit. In the example of Fig.1, 10.7MHz must be subtracted from the measured frequency before it can be displayed.

Fig. 1 shows the local oscillator at a higher frequency than the RF amplifier. This is the more usual case, but if the oscillator was lower, i.e. 89.3MHz then 10.7 would have to be added to the count.

SYSTEM OPERATION

A block diagram of the complete system is shown in Fig. 2. The system operates by enabling a 'gate' for an accurately defined sampling period and counting the number of input cycles which occur during that time. TTL decade counters are used, but be-

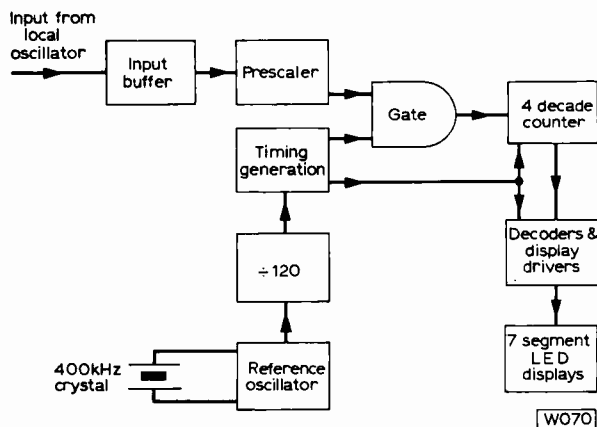


Fig. 2: Block diagram of the complete Digital Readout System.

cause the local oscillator frequency can be above 100MHz it must be divided to a frequency which TTL can handle. This is done in the prescaler, which divides the input frequency by three. So if the local oscillator varied over the range 99 to 119MHz the output of the prescaler would be between 33 and 40MHz which is low enough for the TTL counters.

It is important that the local oscillator is not loaded by the circuit connected to it as this would reduce the output or shift the frequency. To avoid this a high input impedance buffer is used. This is the only part of the circuit which is mounted inside the tuner.

To give the correct display for the number of digits used, a counting period of 300µs is needed. To get the required accuracy a crystal must be used, but to oscillate with a period of 300µs it would be

very large and expensive. In this design a 400kHz crystal is used followed by series of counters to divide the frequency by 120.

IF OFFSET COMPENSATION

The adding or subtracting of the IF frequency is accomplished by using presettable decade counters, (one for each displayed digit).

To add 10.7 to the displayed frequency the counters are loaded with this number before counting starts. The output from the counters is in binary coded decimal (BCD) and the decoders convert this to drive the seven segment LED displays. Because the most significant digit (hundreds) can only be 0 or 1, a separate decoder is not needed. The counting and display sequence takes 4.8ms as follows:

- 1) Load counters with IF offset frequency 300µs
- 2) Enable input gate to counters 300µs
- 3) Display result 4.2ms

During 1) and 2) the display is blanked, and this modulates the light output at about 200Hz, but the eye cannot follow this, and the display appears steady.

ELIMINATING JITTER

With counters of this type there is always an uncertainty of ±1 digit depending on the phase difference between the input and the sampling pulse. This normally causes the last digit to jitter, but when the last digit jitters between 9 and 0 the next digit is also affected. This is especially troublesome in this case as nearly all UK stations are on multiples of 100kHz, so the fifth digit (10kHz) would normally be zero and the jitter would pass on to the next digit.

The problem is overcome by adding 50kHz to the number which is loaded into the counter. Now, when a station is tuned in, the last digit reads five instead of zero, and the jitter is confined to this digit. Although it cannot be displayed as tens of kilohertz the last digit is used to indicate how accurately the station is tuned in. If the last digit is 3, 4, 5, 6 or 7 it is blanked. When it is 0, 1 or 2 a minus sign is displayed and for 8 or 9 a plus sign appears. This arrangement eliminates flicker when a station is tuned in, and still gives sufficient accuracy.

INPUT BUFFER

Fig. 3 shows the circuit of the input buffer, which is simply an emitter follower. This has the advantage of a low output impedance, which is needed to drive

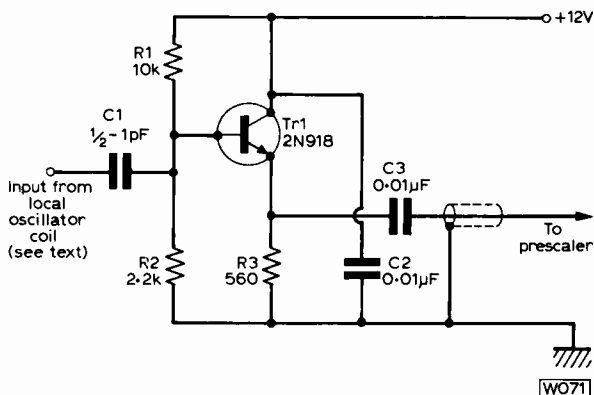


Fig. 3: Circuit diagram of the input buffer.

★ components list

INPUT BUFFER

Resistors

R1 10kΩ
R2 2.2kΩ
R3 560Ω } All ±5% ½W

Capacitors

C1 ½—1pF (see text)
C2, C3 0.01μF ceramic

Transistor

Tr1 2N918

PRESCALER

Resistors (All ±5% ½W)

R4 100Ω
R5 47Ω
R6 470Ω
R7 2.7kΩ
R8 82Ω
R9 180Ω
R10 180Ω
R11 68Ω
R12 68Ω
R13 2.7kΩ
R14 220Ω
R15 1.5kΩ
R16 12kΩ
R17 10kΩ
R18 2.2kΩ
R19 220Ω
VR1 220Ω miniature preset

Capacitors

C4—C8 0.01μF ceramic (5 off)
C9 20pF trimmer (DAU or similar)
C10 0.01μF ceramic

Semiconductors

Tr2—Tr4 2N918 (3 off)
IC1 SN72733N Texas

LOGIC BOARD AND DISPLAY

Resistors

R20, R21 820Ω (2 off)
R22—R30 330Ω (9 off)
R31 680Ω
R32—R45 330Ω (14 off)
R46 180Ω
All ½W ±5%

Capacitors

C11 0.1μF ceramic
C12 680pF polystyrene
C13 470pF polystyrene
C14—C20 0.1μF ceramic (7 off)

Semiconductors

IC2 SN7404N
IC3 SN7408N
IC4 SN7490AN
IC5 SN7493AN
IC6 SN7493AN
IC7 SN7420N
IC8 SN74196N
IC9 SN74176N
IC10 SN74176N
IC11 SN74176N
IC12 SN7410N
IC13 SN7447AN
IC14 SN7447AN
IC15 SN7447AN
LED1 TIL304
LED2—LED4 TIL302 (3 off)
LED5 TIL304 } Texas

Crystal

X1 400kHz (Channel 16, FT241—Interface Quartz Devices Ltd. 29 Market St., Crewkerne, Somerset. Tel. Crewkerne 2578).

the 75Ω coax lead connecting the tuner to the display circuit.

The input is taken from the local oscillator tuned circuit where the signal is about 1V peak-to-peak. A very low value coupling capacitor C1 is used to reduce the loading at this point.

The 12V supply can be taken from the tuner itself as the current drain is only 4mA. If there is no convenient 12V line in the tuner, then a separate wire can be taken from the 13V line in the main unit.

The coax cable couples the buffered local oscillator signal to the prescaler.

PRESCALER CIRCUIT

The basis of the prescaler is an SN72733 video amplifier (IC1 in Fig. 4). This is biased as a Schmitt trigger by connecting the output to the non-inverting input via R13. This is then made to oscillate by the feedback provided by R15, R14 and C9, where C9 sets the frequency.

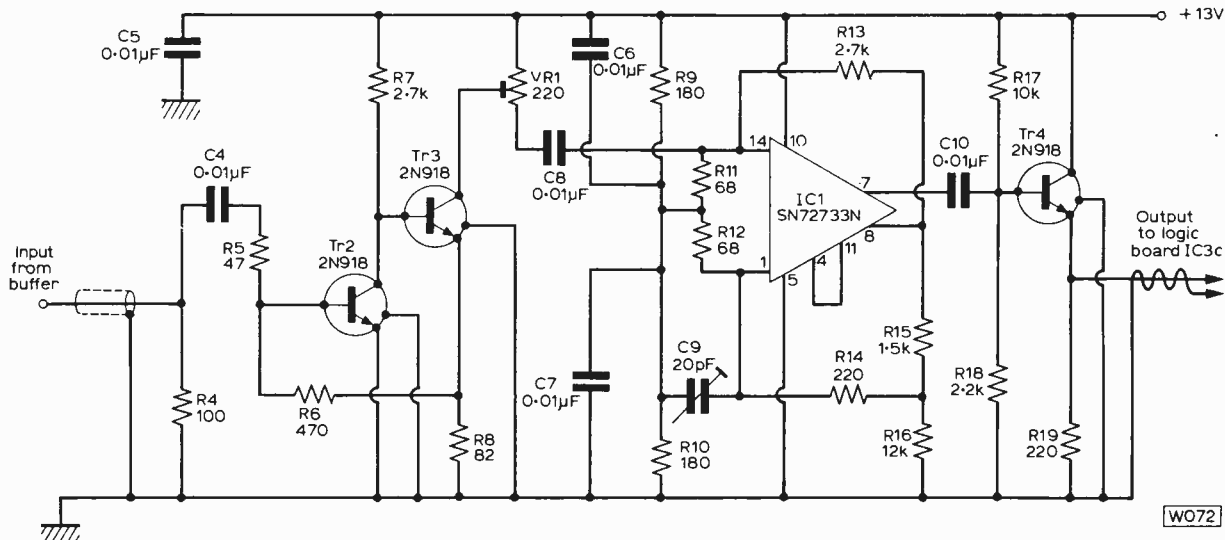


Fig. 4: Circuit diagram of the prescaler unit which uses the Texas SN72733N video amplifier IC.

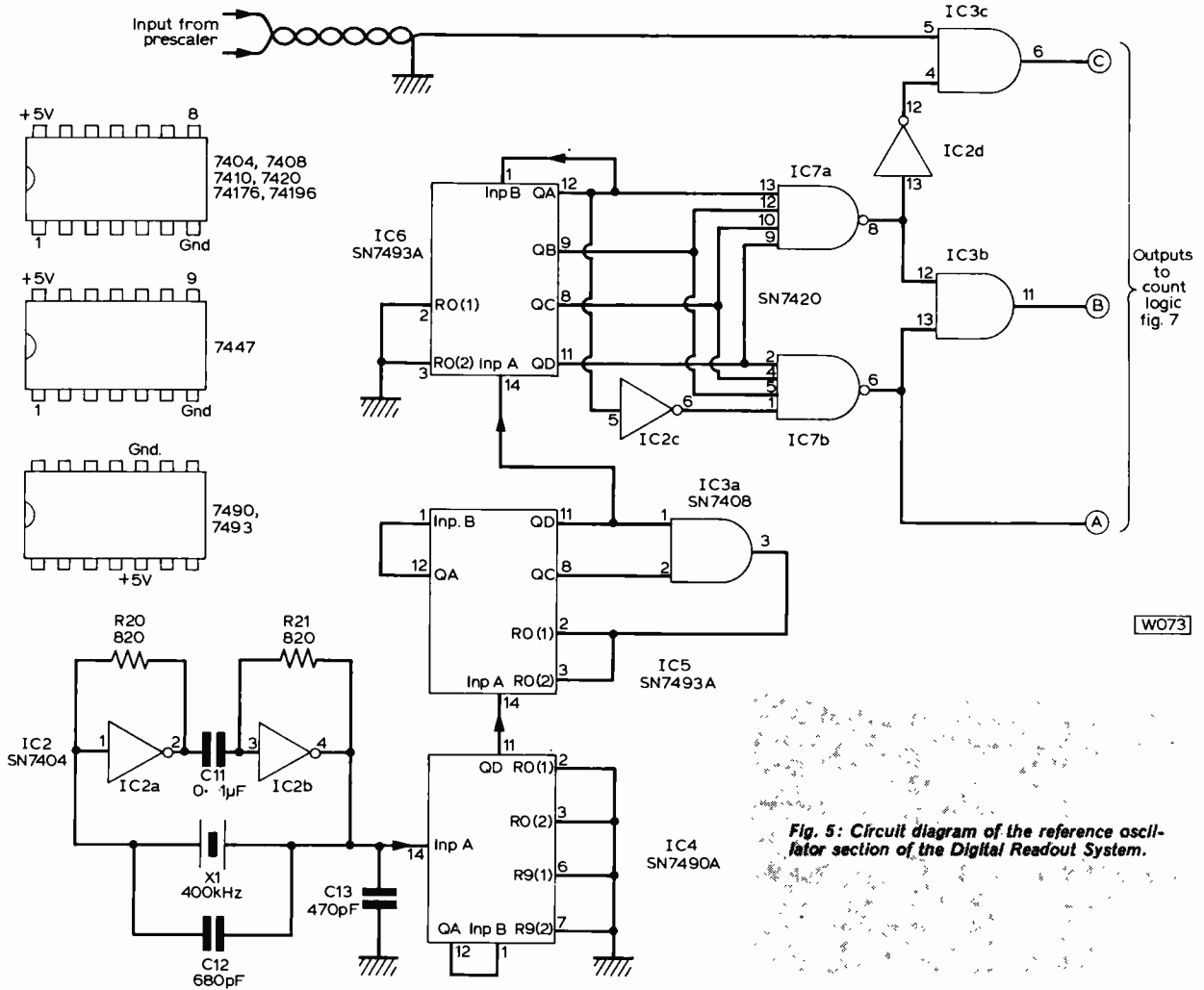


Fig. 5: Circuit diagram of the reference oscillator section of the Digital Readout System.

The signal from the buffer is amplified and coupled to the 733 oscillator which locks to one-third of the local oscillator frequency. The trimmer, C9, is used to adjust the free running frequency to the centre of the band so that the 733 can be pulled higher or lower in frequency.

Tr2 and Tr3 are connected as a DC feedback pair which gives reasonable gain over a wide frequency range. The gain is adjustable with VR1 to allow for variations in the amplitude of the local oscillator signal.

The other output of the 733 is fed to an emitter follower Tr4 which provides a low impedance drive at the correct level for the TTL circuit.

REFERENCE OSCILLATOR

Fig. 5 shows the circuit diagram of this section. The reference oscillator is made from SN7404 inverters which are biased into the linear region by resistors connected from output to input.

Two inverters are needed to give positive feedback. The frequency of 400kHz is determined by the crystal X1. Capacitors C12 and C13 are needed to prevent the circuit oscillating at one of the crystal's harmonic frequencies.

TTL counters are used to reduce the reference frequency. IC4 is an SN7490A which contains divide by two and divide by five circuits. By connecting output QA to input B it will divide the input frequency by 10. IC5 contains a divide by two and a divide by eight circuit. To give the necessary output frequency this must divide by twelve which is

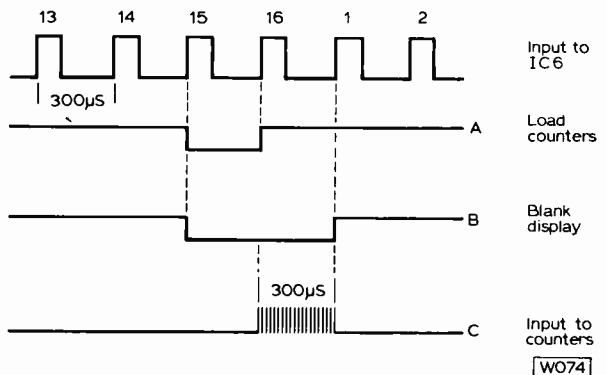


Fig. 6: Waveforms at various positions in Fig. 6.

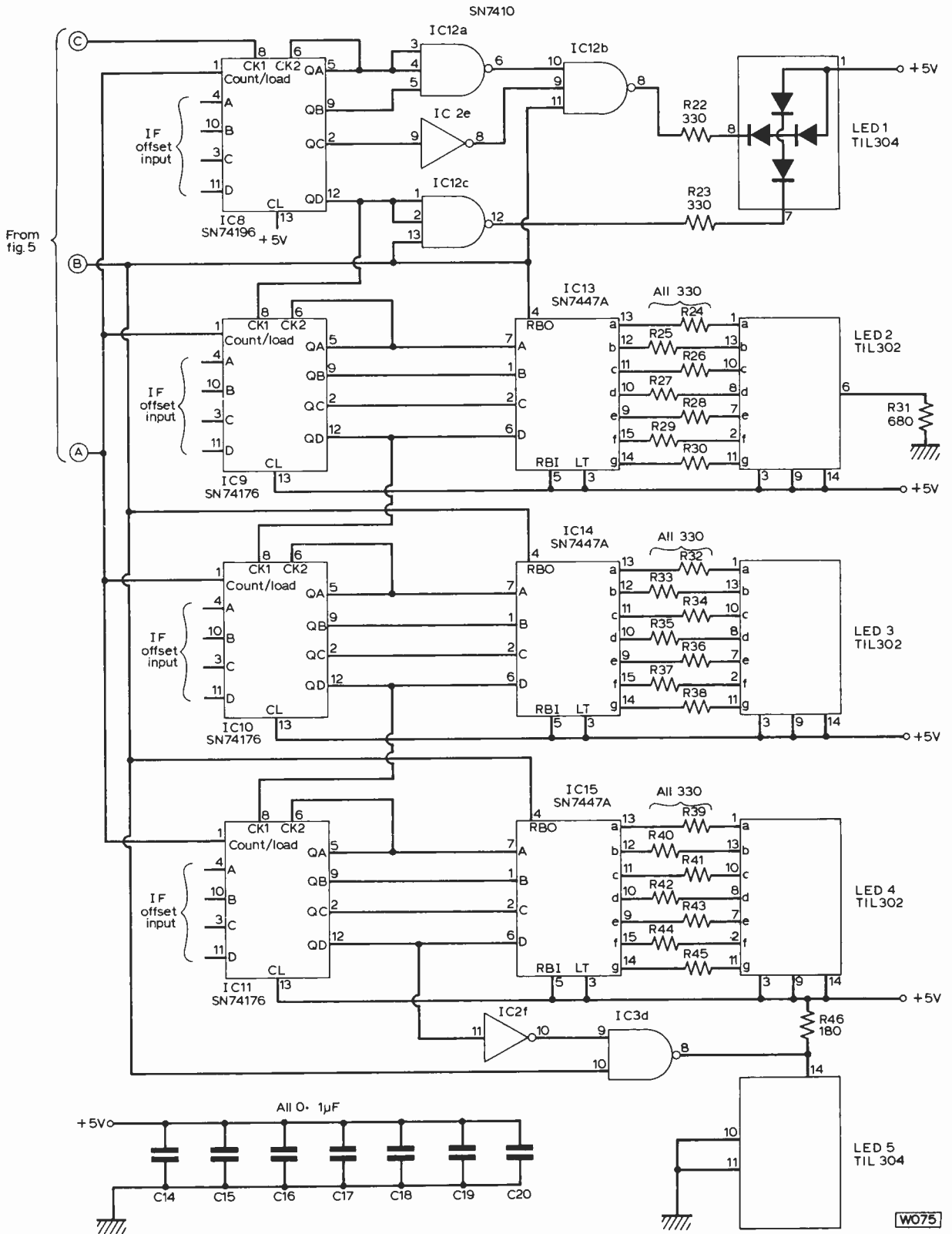


Fig. 7: Circuit diagram of the Counting and Display Logic.

continued on page 558

Practical Wireless, November 1975

UNIUNCTION TRANSISTOR TESTER

R. MEREDITH


THE unijunction transistor tester described here is basically a simple go/no-go tester, giving some indication of the intrinsic stand-off ratio. The total cost of components is about 80p, provided a multimeter with a suitable range is available.

discharged. The cycle now repeats.

Tr1 performs two functions. First, it increases the resistance of the meter by a factor equal to its h_{fe} , and secondly, it removes by reason of its base/emitter drop of 0.7V, the drop of the unijunction when it fires, giving true representation of the ISR.

Unijunction Theory


To understand the operation of this instrument, a certain basic knowledge of unijunction theory is necessary. A unijunction consists of a bar of N type silicon with contacts at each end. On this bar there is a P-N junction. When a voltage V is applied across the bar, a voltage which is less than V appears at A. The voltage at A is found by multiplying V by $\frac{d1}{d2}$. When the emitter voltage rises above that at A by about 0.7V, current begins to flow through the now forward-biased P-N junction. This reduces the voltage at A, so that the current continues until the voltage at the emitter falls below 0.7V. The ratio $\frac{d1}{d2}$ is the Intrinsic Stand-Off Ratio.

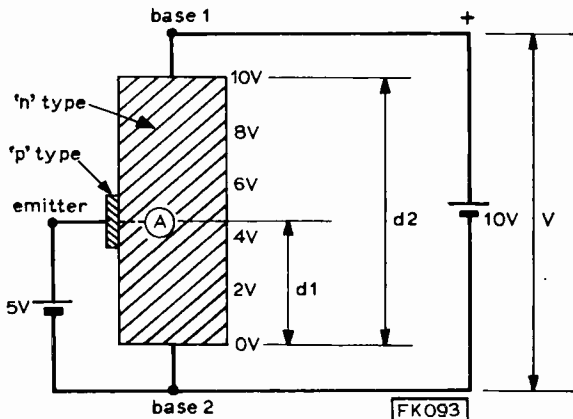

Theoretical circuit of a unijunction transistor with external biasing supplies. In this example, electrons will flow from the emitter, as the potential across base 1 and 2 is greater than that across the emitter and base 2.

Practical Circuit

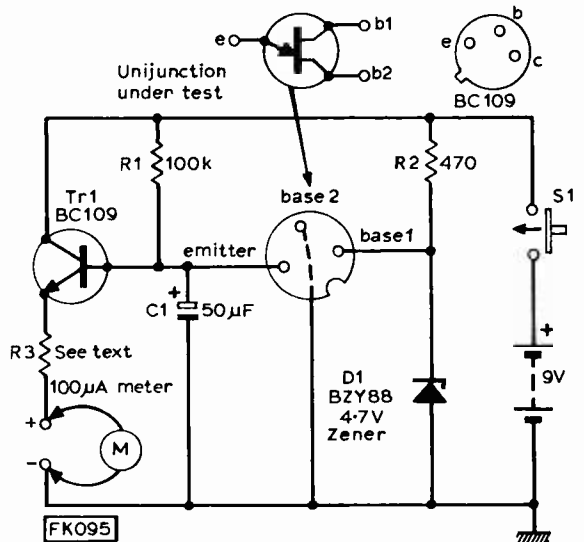The device described in this article works as follows: C1 charges through R1 until the voltage at the emitter rises 0.7V above the ISR x 4.7. This figure being the voltage between the bases, kept constant by the zener D1. At this moment the device starts to conduct and the capacitor C1 is rapidly



Circuit of the Unijunction tester, making use of an external meter. If the circuit is to be constructed with an integral meter, then one of about 100µA FSD should be chosen.

Construction

Although details are given for the PCB, layout is not at all critical and comprises only six components. A high gain transistor should be used for Tr1 such as the BC109, as the input impedance should be as high as possible. For the same reason, the meter should have a movement of around 100µA, or if

★ components list


Resistors	R1 100kΩ	R3 See text
	R2 470Ω	All 1/4W 10%
Capacitor	C1 50µF (8V)	
Semiconductors	Tr1 BC109	D1 BZY88 4.7V zener
Miscellaneous	S1, pushbutton switch, PP3 battery, Transistor socket, Two sockets for meter connection, Vero-board 80 x 40mm, Aluminium box 115 x 64 x 30mm.	

a suitable multimeter is available, then this could be used in place of a permanent meter. The value of R3 can be calculated as follows:

$$R3 = \frac{4.7}{\text{Sensitivity for fsd on meter}} - \text{Meter resistance}$$

A 5% resistor should be used here, as no advantage will be gained by the use of a more accurate one, especially as the diode itself is of 5% tolerance. The PCB was fixed inside a small aluminium box with sockets for the meter.

50x40mm (0.1inch veroboard)

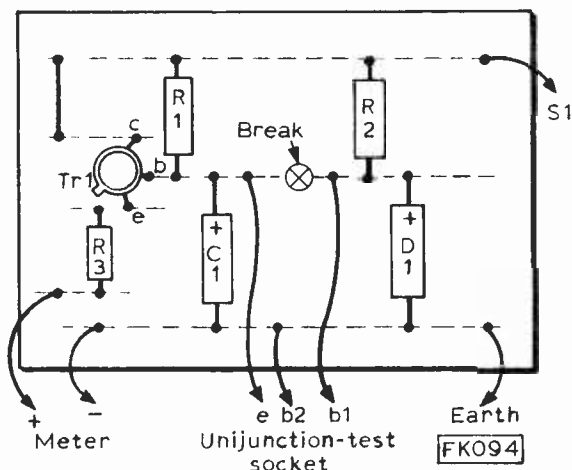

Component layout can be constructed on veroboard as shown above, or on a PCB. As components only number six, layout is not at all critical.

Use

Switch on and plug a unijunction transistor into the socket. The needle on the meter will move slowly across the scale, until at one point, the needle should flip back to near zero. If the meter is scaled 0 to 1 linearly, the ISR will be given by the maximum reading on the meter scale. If however, the voltage continues to rise, or does not rise at all, the unijunction is faulty. PW

STILL AVAILABLE!

REPRINTS OF PW's
TEXAN 20 + 20W
IC STEREO AMPLIFIER
May-August 72

Send 30p + 7p (post and packing) to:
Chief Cashier (PW Texan), IPC Magazines,
Tower House, Southampton Street,
London, WC2E 9QX

FM TUNER DIGITAL READOUT—contd from page 556

achieved by resetting to zero on the twelfth input pulse. IC3a does this by feeding a positive pulse to the reset inputs when outputs QC and QD go high. The output from QD has a period of 300µs which is the correct width for the sampling pulse.

IC6 is also an SN7493N and is used to generate timing pulses for the counting and display logic. It counts up to 16 and then resets to zero and outputs 15 and 16 are selected by the two NAND gates IC7a and b. The output at 15 (A in Fig. 5) loads the pre-settable counters with the IF offset, and the pulse at 16 gates the prescaler output into these counters. The output of IC3b is used to blank the displays. These pulses are shown in Fig. 6.

COUNTING AND DISPLAY LOGIC

The circuit is shown in Fig. 7. ICs 8 to 11 are the decade counters which are cascaded by feeding the QD output to next clock input. Also QA is connected to CK2 of each counter to cascade the two halves of each IC. The most significant digit (100MHz) can only be 0 or 1 so a decade counter is not needed.

The data inputs A-D are either connected to ground or +5V depending on the value of the IF offset. This is loaded into the counters when the count/load inputs are low. The counter outputs are in BCD form so decoder/driver ICs are used to drive the seven-segment LED displays (IC13, 14 and 15). These provide high current output to drive LEDs, and blanking can be achieved by putting a logic low on the RBO pins. The 330Ω resistors between the decoders and the displays determine the LED current, and R31 sets the current for the decimal point. For LED1 (+ or - indicator) a different circuit is used. The arrangement of IC12a, 12b and 2e illuminates the horizontal bar of LED1 when the output of IC8 is 0, 1, 2, 8 or 9. The vertical bar is also illuminated when the count is 8 or 9 due to IC12c. If the count is 3, 4, 5, 6 or 7 neither bar is on and the display is blanked. LED5 only displays 1 if QD of IC11 is low. If the count is 80 or 90MHz then QD is high and LED5 is blanked. The display blanking pulse B is also applied to IC12c and IC3d to blank LED1 and 5 during counting.

The capacitors C14-20 are to decouple the power supply. This is important because of the high edge speeds of the counting logic.

In Part 2 the power supply circuit is described and construction details and setting up procedure are given.

OUR "CQ" COLUMN

On page 603 of this issue, we have some CQ requests for back-numbers. **Please help us to help you**, if you want a "CQ" published, and you can do that by following the style on page 603 when you write to us. Please keep CQ's as short as possible.


CQ's should be sent to THE "CQ" COLUMN, Practical Wireless Editorial, Fleetway House, Farringdon Street, London, EC4A 4AD.

RADIO EXCHANGE LTD.

ALL PRICES INCLUDE VAT
We regret we cannot for the time being accept Overseas Orders. Open to U.K. and Ireland residents only.

NEW EDU-KIT MAJOR

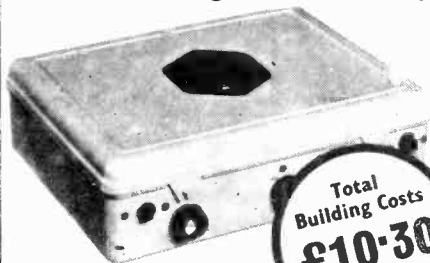Completely Solderless Electronic Construction Kit. Build these projects without soldering iron or solder



Total Building Costs
£10-30

P & P 65p

- ★ 4 Transistor Earpiece Radio.
- ★ Signal Tracer.
- ★ Signal Injector.
- ★ Transistor Tester NPN-PNP.
- ★ 4 Transistor Push Pull Amplifier.
- ★ 5 Transistor Push Pull Amplifier.
- ★ 7 Transistor Loudspeaker Radio MW/LW.
- ★ 5 Transistor Short Wave Radio.
- ★ Electronic Metronome.
- ★ Electronic Noise Generator
- ★ Batteryless Crystal Radio.
- ★ One Transistor Radio.
- ★ 2 Transistor Regenerative Radio.
- ★ 3 Transistor Regenerative Radio.
- ★ Audible Continuity Tester.
- ★ Sensitive Pre-Amplifier.


Components Include: 24 Resistors ● 21 Capacitors ● 10 Transistors ● 3 1/2" Loudspeaker ● Earpiece ● Mica Baseboard ● 3 12-watt connectors ● 2 Volume controls ● 2 Slider Switches ● 1 Tuning Condenser ● 3 Knobs ● Ready Wound MW/LW/SW Coils ● Ferrite Rod ● 6 1/2 yards of wire ● 1 Yard of sleeving etc. ● Parts Price List and Plans 55p free with parts.

ELECTRONIC CONSTRUCTION KITS

ECK 1

3 Transistor Easy Stage Earpiece Receiver Kit. Full Medium Wave Coverage. Complete with Ready Wound Ferrite Rod Aerial, High Efficiency Air Spaced Tuning Capacitor, Sensitive Crystal Earpiece and Gain Control. Operates from a 9 Volt P.P. 7 Battery (not supplied with kit). This Electronic Construction Kit is a good starter for those interested in kit building and soldering. Parts Price List and Plans free with kit.


Complete kit of Parts **£450** P.P. and Ins. 45p.

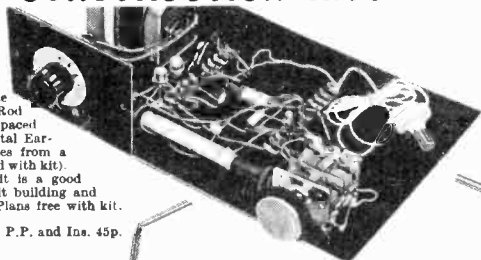

ECK 2

Self Contained Multi-Band V.H.F. Receiver Kit. 8 Transistors and 3 Diodes. Push/Pull Output. 3" Loudspeaker. Gain Control. Snub 9 section swivel ratchet and retractable chrome plated telescopic aerial, V.H.F. Tuning Capacitor, Resistors, Capacitors, Transistors, etc. Will receive (subject to local reception conditions) T.V. Sound, Public Service Band, Aircraft, V.H.F. Local Stations, etc. Operates from a 9 Volt P.P. 7 Battery (not supplied with kit)


Parts Price List and Plans supplied free with Kit. Complete kit of parts **£7-95** P.P. and Ins. 56p.

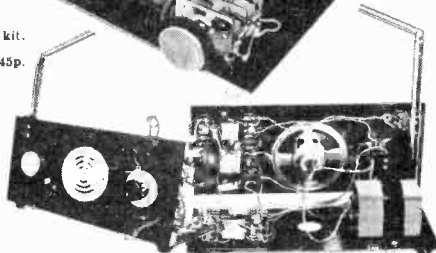

ECK 3

5 Transistor Medium Wave Receiver Kit. Class "A" Output with 3 1/2" Loudspeaker. Simple to operate with full Medium Wave Coverage. Ready Wound 8" Ferrite Rod Aerial. No external Aerial required. 7 stages, 5 Transistors and 2 Diodes. Tuning Capacitor, Gain Control, etc. Operates from a 4 1/2 Volt Battery (not supplied) Parts Price List and Plans free with kit. Complete

kit of parts. **£5-40** P.P. and Ins. 45p.

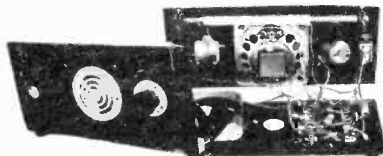

ECK 4

7 Transistors, 6 tuneable wavebands, MW, LW, Trawler Band, 3 Short Wave Bands, Receiver Kit. With 5" x 3" Loudspeaker. Push/Pull output stage, Gain Control, and Rotary Switch. 7 Transistors and 4 Diodes. 8" Sensitive Ready Wound Ferrite Rod Aerial, Tuning Capacitor, Resistors, Capacitors, etc. Operates from a 9 Volt P.P. 7 Battery (not supplied with kit). Parts Price List and Plans supplied free with kit. Complete

kit of parts. **£7-25** P.P. and Ins. 55p.




EDU-KIT JUNIOR

Completely Solderless Electronic Construction Kit. Build these projects without Soldering Iron or Solder.

- Crystal Radio Medium Wave Coverage:—No Battery necessary.
- One Transistor Radio.
- 2 Transistor Regenerative Radio.
- 3 Transistor Earpiece Radio Medium Wave Coverage.
- 4 Transistor Medium Wave Loudspeaker Radio.
- Electronic Noise Generator.
- Electronic Metronome.
- 4 Transistor Push/Pull Amplifier.

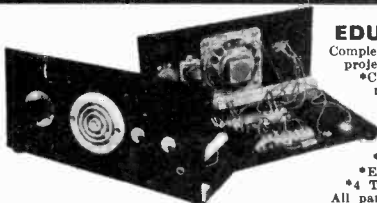All parts including Loudspeaker, Earpiece, MW Ferrite Rod Aerial, Capacitors, Resistors, Transistors, etc., plus Parts Price List and Plans free with kit. Complete kit of parts



£7-50 P.P. and Ins. 45p.

VHF AIR CONVERTER KIT

Build this Converter Kit and Receive the Aircraft Band by placing it by the side of a radio tuned to Medium Wave or the Long Wave Band and operating as shown in the instructions supplied free with all parts. Uses a Retractable Chrome plated Telescopic Aerial, Gain Control, V. H. F. Tuning Capacitor, Transistor, etc.




All Parts including Case and Plans. **£4-35** P.P. and Ins. 40p

ROAMER TEN MARK 2

With VHF including aircraft

Now with free earpiece and switched socket. 10 Transistors. Latest 4" 2 watt Ferrite Magnet Loudspeaker. 9 Tuneable Wavebands, MW1, NW2, LW, SW1, SW2, SW3, Trawler Band, VHF and Local Stations also Aircraft Band. Built in Ferrite Rod Aerial for MW/LW. Chrome plated 6 section Telescopic Aerial, can be angled and rotated for peak short wave and VHF listening. Push Pull output using 600mW Transistors. Car Aerial and Tape Record Sockets. 10 Transistors plus 3 Diodes. Ganged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off. Wave Change and tone Controls. Attractive Case in black with silver blocking Size 9" x 7" x 4". Easy to follow instructions and diagrams. Parts price list and plans 50p free with parts.

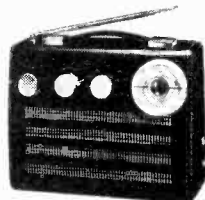

Total building costs **£11-87** P.P. and Ins. 65p.

RADIO EXCHANGE LTD.

TO RADIO EXCHANGE LTD., 61A HIGH STREET, BEDFORD MK40 1SA. Tel: 0234 52367, REG NO. 788372

- Callers side entrance "Lavella" Shop.
- Open 10-1, 2.30-4.30. Mon-Fri. 9-12 Sat.

I enclose £..... for

Name

Address

PW 11

HOTLINES

ON RECENT DEVELOPMENTS

POWER

ON reading past Ginsberg articles it seems that the small, minute marvels have hogged the limelight, probably because they really are remarkable achievements. However, to redress the balance let us take a look at something a shade bigger. It concerns power, and the laser. The generation of power is a problem. Solar cells, wind-driven generators, mirrors which focus the sun's rays have all featured in the news.

Now it just so happens that if you take a very small amount of a material and compress it sufficiently it may just be possible to arrange pressures and densities high enough to support fusion—when lighter atoms get together to form heavy ones and when they do, they give off energy which might be harnessed.

Experts claim that a tiny pellet of deuterium and tritium can, with the aid of a quick pulse from a 1MJ (one mega-joule) laser, be compressed by a factor of up to 10,000.

Another approach finds workers constructing a kind of ring arrangement in which electron beams are individually concentrated on a single pellet of material in the centre. Certainly on the drawing board stage (at least) is such a beastly which treats said pellet to a burst of electron beams whose total combined power amounts to some $2\frac{1}{2}$ trillion Watts (that's 2.5×10^{12} Watts).

Just to complete the story, capacitors are used as a means of storing energy for the system. Two banks are employed and each consists of 38, 60kV, 1.85 μ F capacitors. Oil dielectric transmission lines are employed and these are housed in a tank of transformer oil—40,000 gallons of it!

A final piece of news on the subject is that one particular machine under development produces a 10ns pulse of 40 trillion Watts.

27MHz

If you've ever tuned a radio receiver to around 27MHz you may well have picked up a weird cacophony of call-signs and titles not to mention some very strange conversations. Almost certainly you will have been listening in to conversations on the American "Citizens Band". Although power is (in theory) limited, no formal exams are required in order that one might

transmit. Note; this is in America and does NOT apply in the UK.

While the Citizens Band has been a source of debate for some time, a new idea has surfaced and looks like being a 'winner'. The thought is that a particular frequency or channel within the Citizens Band should be an emergency channel. This allows anybody and everybody to have a Citizens Band hand-held transceiver (walkie talkie) in, say, their car. Any accident could be immediately reported and a request for assistance would be almost instantaneous. One voluntary network has already sprouted up in Ohio and others could follow.

It occurs to me that old people living alone could easily have immediate access to help from the outside world. Mountain climbers etc. could also find the system of use. It is almost certain that the scheme would not be permitted in the UK due mainly to the stringent Post Office/Home Office regulations concerning the radiation of energy, a point on which they are quite fussy to say the least. Quick, check the radiation from the local oscillator of your broadcast receiver. And what about those TV timebases?

Speaking of TV reminds me that the central research laboratory of Japanese giant Hitachi has been working on a video disc player using the optical approach. Some half hour recording of colour pictures and sound has been recorded on a 12in. disc. Luminance, chrominance and sound are contained in the 54,000 holograms on the disc each hologram being only one millimetre in diameter. So densely is the information stored that the disc needs to rotate at only 6 r.p.m. It is interesting to note that in systems employed by two other major manufacturers, the discs rotate at 1,800 r.p.m.

BLIMPS ARE COMING

Look out—the Blimps are coming. They may sound like a second class limp but in reality they are huge balloons which are floated up to a certain altitude (around 10,000ft.) and then tethered. The Blimps have with them a large antenna and transceiving equipment. The idea is that it's cheaper to have a balloon that it is to have a satellite in order to transmit and receive information over greater

distances, particularly at the very high frequencies. No, it's not hot air, even the American military is increasing its interest in balloon borne radar. Makes you wonder about Amateur radio Hams' reaction. Perhaps Lisle Street will soon be selling Ex. Govt. barrage balloons. What better for portable stations—with a high wind it could get them off to a good start and raise them in the eyes of others!

RAZOR-SHARP TIME-KEEPING

News from abroad informs that there's a newcomer on the digital watch scene—Gillette, the company of razor fame. A research and development agreement has been signed between Gillette and some American electronics companies for carrying out investigations in the field of quartz modules for digital watches.

"MESFETS"

Another newcomer, this time to the semiconductor scene, is a device called the MESFET. Adding another S after the first would be a fair word for some early Ginsberg experiments with FETS! For the technically oriented, these devices are described as Schottky-barrier field-effect transistors. Efficiencies of 68% at 4GHz and over 40% at 8GHz have been claimed so clearly they're not just a pretty face. I hope to have more information shortly on these devices.


"SAWS"

When one talks about crystal oscillators it's usually about a bulk crystal—a chunk of crystal between two supports. Generally, the higher the frequency, the smaller (and often thinner) the piece of crystal is. There is a limit to how small and fragile one can make a crystal of this kind which is why fundamental frequencies are commonly no higher than 25MHz.

Marconi Research Laboratory has developed the SAW (surface acoustic wave) technology to a point where it can manufacture a compact and rugged crystal oscillator with a fundamental frequency of 1-2GHz.




GOING BACK...

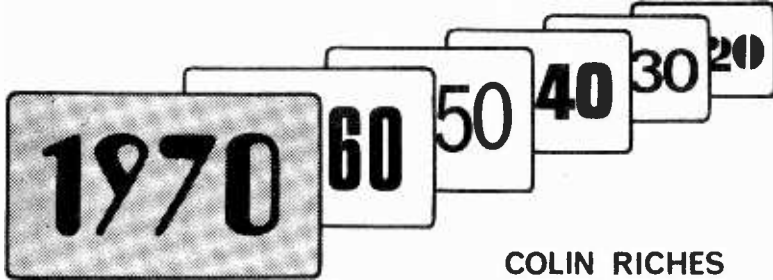

COLIN RICHES

Anyone help?

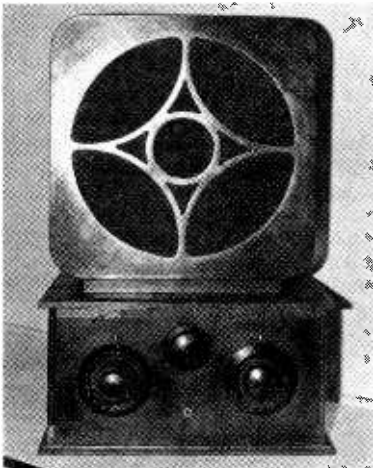MR. H. F. Mayman of 59 Delamere Street, Crewe, Cheshire has recently come across this interesting receiver, complete with speaker, and wonders if any other readers can help him with more information.



Apparently, the set was purchased in Crewe many years ago. It carries only a dealer's name and no details of a manufacturer. Valves are 2×PM2 and 1×PM1LF. The loudspeaker is simply marked "Blue Spot."

New books

ADAM Hilger Limited, publishers, 29 King Street, London, WC2E 8JH, have recently announced the first three volumes of a set of books entitled "The Story of Radio" by W. M. Dalton, Ch.Eng., M.I.E.R.E.

Volume 1 "How Radio Began" covers the basics from early experiments with electricity and magnetism. An interesting chapter on Wireless Telegraphy describes experiments and discoveries by such pioneers as Clark

Maxwell, Hertz and Marconi. A chapter headed The Thermionic Valve contains items on the Edison Effect, Audion Tube, and early valve circuits.

Vol. 2, "Everyone an Amateur" begins the story after World War 1; and contains sections on the British Broadcasting Company and the Rediscovery of Short Waves.

It tells how during the early years of peace after the First World War, the seepage of official information and the knowledge of wartime developments brought home by ex-service men led to an enthusiasm for radio fostered almost entirely by amateurs. They built their own transmitting stations and receivers, compelled Governments to provide public broadcasting services, and eventually astounded the world by their unaided achievements in long distance low-power short-wave communication. This second volume of Mr. Dalton's comprehensive history pays tribute to these devoted pioneers and, in recounting the birth-pangs of the British Broadcasting Company, tells how Everyman carried on building his own receiver in a craze from which, Mr. Dalton has said, 'a few of us never quite recovered.'

Vol. 3, "The World Starts to Listen" takes the story a little further: by the mid-twenties, the early amateurs were ready to turn professional, the world was ready to buy their sets. The B.B.C. had become a Corporation—and respectable—and people had started to listen to its programmes in preference to twiddling dials in a search for distant stations; and so the quality of broadcast sound improved. Valves were already being applied in many other fields, but they were still battery operated. Mr. Dalton

thus continues his step-by-step story of the development of radio.

These books are very interesting but also very expensive, for they are priced at £4.50 each volume. It's a pity because I feel that this is a text which has been needed for a long time now. Still, with inflation roaring ahead £4.50 will be the price of half a dozen resistors soon so . . .

Cassette History


SOME while ago I gave mention to the double LP set that the BBC issued to mark 50 years of broadcasting. Well, now they've issued the complete recording on cassette. It's entitled "BBC 1922-1972, 50 Years' of Broadcasting", and comes as a double-play cassette No. HRMC 050.

The tracks are produced by Alan Burgess and narrated by



Rene Cutforth and endeavour to recapture in a hundred minutes many great occasions at home and abroad and people whose voices became known through the medium of 50 years of BBC Radio. Broadcasting pioneers such as Lord Reith and Peter Eckersley can be heard as well as the first Christmas broadcast by King George V and historic broadcasts by famous wartime announcers. The tape also reflects musical events over the years from Twenties syncopation to The Beatles. Please don't try to obtain it from the BBC because they don't have a sales department for records and cassettes, but contact your local record shop. They're sure to be able to get one for you.

Practical Wireless, November 1975

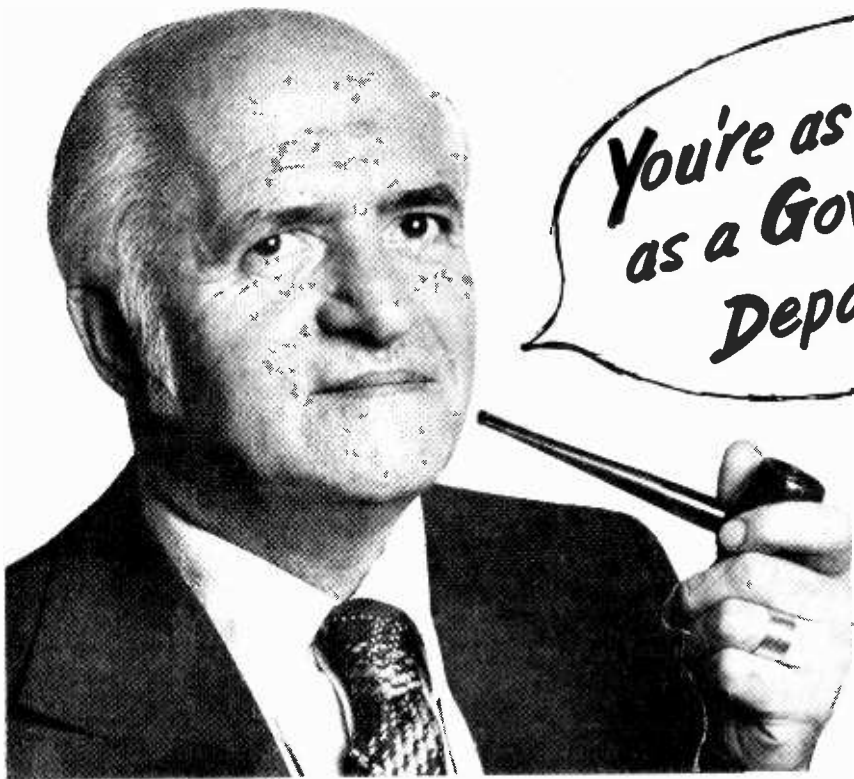

*You're as important
as a Government
Department!*



... at least, to Home Radio Components you are. I'm thinking of their Credit Account Service. They have of course always run accounts for supplying firms, colleges and Government Departments, but for years it was impractical to provide the same facilities for individuals. However, Home Radio Components have always looked upon their smallest customers just as important as their biggest, and after much thought and planning they devised a Deposit Credit Account matched to the needs of the small individual buyer.

The service is very convenient in many ways. For instance, thanks to their answerphone service exclusively for the use of Credit Account customers, you can take advantage of the cheap phone rates after 6pm week-nights and any time Saturday and Sunday. You not only save money, but you can often get your components much quicker. Briefly, the Credit Account Service works like this—you pay a deposit (you choose the amount) and you immediately get credit

for double that amount. Home Radio then send you special order forms and pre-paid envelopes, and advise you each month how much you have spent. You save quite a bit on postage costs, and having to draw only one cheque or P.O. a month makes quite a worthwhile additional saving. No wonder nearly 1000 customers are already using this service. Why not join them and save yourself money and frustration? First you will need the Home Radio Components catalogue. No constructor should be without one! For a book having 240 pages, listing about 6000 components, illustrating nearly 2000, the price of 85p is modest indeed. True, postage and packing adds another 33p, but every catalogue contains vouchers to the value of 70p when used against orders.

Full details of the Deposit Credit Account and an application form are included in the Catalogue. To take your first step to simpler, quicker component buying send the coupon with your cheque or P.O. for £1.18 today.

Today's finest Components
Catalogue **85p** plus 33p POST & PACKING

POST THIS COUPON
with cheque or P.O. for £1.18

The price of £1.18 applies only to customers in the U.K. and to BFPO Addresses.

Please write your Name and Address in block capitals

NAME.....

ADDRESS



HOME RADIO (Components) LTD., Dept. PW,
234-240 London Road, Mitcham, Surrey CR4 3HD

(Regn. No.
London 912966)

HOME RADIO (Components) LTD, Dept. PW, 234-240 London Road, Mitcham, CR4 3HD, Phone 01-648 8422

BI-PAK



BARGAIN BUNDLES

Send to: BI-PAK SEMICONDUCTORS, DEPT. P.W. P.O. BOX 6, WARE, HERTS

Bi-Pak bring you, for 2 months only a fantastic inflation beating offer FREE to help you, the customer. With every Pak comes a useful FREE GIFT. In addition to this, our star attraction is the D.I.Y. Printed Circuit Kit. With every kit sold during this offer comes a voucher to the value of £1.50 to be spent on any item from our Retail Catalogue.

PRINTED CIRCUIT KIT. Containing 6 sheets of 6" x 4" single sided laminate, a generous supply of etchant powder, etching dish, etchant measure, tweezers, etch resistant marking pen, high quality pump drill with spares, cutting knife with spare blades, 6" metal ruler, plus full easy-to-follow Instructions. £7.80p.

I.C. BUNDLE
 2 x 7400 2 x 7474
 2 x 74121 2 x 74141
 2 x 741

PLUS FREE
 2 x BPS8 and 2 x BPS16
 I.C. Sockets
ALL FOR ONLY £1.50
OFFER WORTH £3.27



3 for the PRICE of 2
 Buy 2 x C60 cassettes for 72p per pr. GET 1 x C60 absolutely FREE. Buy 2 x C90 cassettes for 96p per pr. GET 1 x C90 absolutely FREE.

DIODE + RECTIFIER BUNDLE
 20 GERM G.P. DIODES DIRECT REPLACEMENTS FOR (OA81-85 OA91-95)
 2 x BY100 4 x IN4004 4 x 1.5A 400V
 4 x IN4001 4 x 1.5A 50V 4 x IN4148

PLUS FREE BOOK
 No. BPS '38 PRACTICAL TESTED DIODE CIRCUITS FOR THE HOME CONSTRUCTOR"
ALL FOR ONLY £1.50 OFFER WORTH £3.00

TRANSISTOR BUNDLE
 2 x BC108C 2 x BC178
 2 x OC71 2 x BC107
 2 x BF115 2 x BC109
 2 x 2N3819 2 x BFX84
 2 x 2N3646 2 x BFX29

PLUS FREE
 ONE SHEET OF VEROBOARD
ALL FOR ONLY £1.50
OFFER WORTH £3.00

S.C.R. BUNDLE
 2 x 6A 100V 2 x 1A 400V
 2 x 1A 50V 2 x 3A 50V
 2 x 5A 400V

PLUS FREE
 2 METERS OF 18SWG MULTI-CORE SOLDER ALL FOR ONLY £1.50. OFFER WORTH £3.00

CAPACITOR + RESISTOR BUNDLE
 100 1W Resistors in assorted values ranging from 100 ohm to 1M ohm.
 50 C280 capacitors in assorted values ranging from .01uF to 2.2uF

PLUS FREE
 COLOUR CODE CHARTS
ALL FOR ONLY £1.50
OFFER WORTH £3.00

WATCH THIS SPACE FOR THE GREAT BI-PAK CHRISTMAS COMPETITION WITH A FIRST PRIZE OF A COLOUR T.V. PLUS 52 OTHER PRIZES

Fully guaranteed Individually packed VALVES

A1065	£1.25	ECL80	55p	G234	70p	PY81	40p
AR8	55p	ECL82	35p	G237	£1.00	PY82	40p
ATP4	50p	ECL83	70p	KT66	£2.50	PY83	40p
B12H	50p	ECL86	50p	KT88	£3.50	PY88	45p
CY31	50p	EF36	65p	MH4	75p	PY600	£1.00
DAF96	55p	EF37A	ML6	65p		PY600	45p
DF96	55p	EF40	£1.20	OA2	45p	PY801	50p
DK96	70p	EF40	75p	O82	45p	QQV05-10	
DL92	60p	EF41	65p	PABC80	40p	AD 149	£1.40
DL96	60p	EF80	30p	PC97	50p	AD 161	BC 172
DY86/87	40p	EF83	£1.25	PC900	50p	AD 162	BC 172A
		EF85	35p	PCC84	40p	ADZ 11	BC 172A
DY802	45p	EF86	35p	PCC85	40p	ADZ 12	BC 212A
E88CC/01	£1.00	EF89	30p	PCC89	50p	AF 114	BCY 31
		EF92	50p	PCC189	60p	AF 115	BCY 33
E180CC	70p	EF95	40p	PCF80	40p	AF 116	CA 5
E182CC		EF183	35p	PCF82	40p	AF 117	CA 5
		EF184	35p	PCF84	40p	AF 118	CA 5
EA50	40p	EF1200	75p	PCF86	50p	AF 124	CA 5
EAB30	40p	EL33	£2.50	PCF96	60p	AF 125	CA 5
EA42	75p	EL34	70p	PCF201	75p	AF 126	CA 5
EBF91	30p	EL36	60p	PCF801	55p	AF 127	CA 5
EBF93	40p	EL37	£1.80	PCF802	50p	AF 139	CA 5
EBF80	40p	EL41	80p	PCF805	90p	BSY 27	
EBF83	50p	EL81	60p	PCF808	90p		
EBF89	40p	EL82	55p	PCF808	90p		
EC52	85p	EL84	30p	PCF808	90p		
EC81	40p	EL85	60p	PCF808	90p		
EC82	85p	EL90	45p	PCF808	90p		
EC83	85p	EL94	45p	PCF808	90p		
EC84	35p	ELF04	80p	PCF808	90p		
EC85	60p	EM30	60p	PCF808	90p		
EC86	90p	EM80	55p	PLH200	70p		
EC88	50p	EM84	40p	PL36	60p		
ECC189	70p	EM87	£1.00	PL81	50p		
ECF80	40p	EY81	45p	PL82	45p		
ECF82	45p	EY81	45p	PL83	45p		
ECF801	75p	EY86	40p	PL86	45p		
ECH35		EY88	50p	PL904	80p		
		EZ40	70p	PL508	£1.00		
ECH42	80p	EZ41	75p	PL509	£1.35		
ECH81	35p	EZ80	80p	PL802	£1.75		
ECH83	45p	EZ81	80p	PY33	80p		
ECH84	45p	EY001	75p	PY80	40p		

TRANSISTORS, DIODES etc.

AC 113	AF 178	BSY 38	OAZ 200	OC 206	2N 3054
AC 126	AF 186	BSY 95A	OC 22	SX 754	2N 3055
AC 127	AFZ 12	BYZ 16	OC 25	ZR 11	2N 3391
AC 128	ASV 26	CRS 1/10	OC 26	ZR 21	2N 3391
AC 178	ASV 27	CRS 1/20	OC 28	2N 23A	2N 3819
AC 178	ASV 28	CRS 1/30	OC 29	1N 25	2N 4038
AC 19	BC 108	CRS 1/40	OC 35	1N 32A	2N 4058
AC 20	BC 118	CRS 3/10	OC 36	1N 38A	2N 4061
AC 39	BC 119	CRS 3/20	OC 42	1N 43	2N 4785
AC 40	BC 136	CRS 3/30	OC 44	1N 70	2N 5295
AC 149	BC 137	CRS 3/40	O 45	1N 277	3N 129
AD 161	BC 148A	CRS 25/C35	OC 70	1N 415C	3N 154
AD 162	BC 172	GET 115	OC 73	1N 4148	3N 159
ADZ 11	BC 172A	GET 116	OC 78	2N 456A	28 303
ADZ 12	BC 212A	GEX 66	OC 78D	2N 708	28 404
AF 114	BCY 31	NKT 222	OC 81	2N 918	2082
AF 115	BCY 33	CA 5	OC 82	2N 1304	40250
AF 116	CA 5	OA 47	OC 82D	40251	40251
AF 117	BF 115	OA 70	OC 82DM	2N 1307	40310
AF 118	BF 167	OA 71	OC 83	2N 1309	40608
AF 124	BF 185	OA 73	OC 139	2N 2062	
AF 125	BFY 51	OA 79	OC 140	2N 2147	
AF 126	BFY 52	OA 91	OC 170	2N 2411	
AF 127	BFY 90	OA 200	OC 172	2N 2989	
AF 139	BSY 27	OA 202	OC 200	2N 3053	

COLMOR All valves guaranteed

68C7G	40p	25L6GT	70p	6064	60p
68G7	50p	30C15	£1.00	6065	£1.00
68J7	55p	30C17	£1.00	6067	70p
68J7GT	35p	30C18	90p	6068	£2.30
68K7	55p	30F5	£1.00	6146	£3.95
68L7GT	50p	30FL1	£1.00	6148B	£3.85
68N7GT	50p	30PL12		8020	£5.00
68Q7	55p			9001	£5.00
6V8GT	55p	30FL14	90p	9002	£5.00
6X4	40p	30L15	85p	9003	70p
6X5G	40p	30L17	85p	9005	35p
6X5GT	50p	30P12	£1.00	9006	35p
6Y6G	90p	30P19	£1.00		
6Z4	85p	30PL1	95p		
6-30L2	80p	30PL13			
7B7	80p				
7Y4	80p	30P14	£1.10		
9D6	40p	35L6GT	75p		
11E2	£6.00	35W4	50p		
12A6	55p	35Z4GT	70p		
12A7G	45p	60C5	60p		
12A7T	40p	60CD6G			
12A7	35p				
12AV6	50p	75	£1.10		
12AX7	35p	75C1	75p		
12BA6	45p	76	75p		
12BE6	50p	76	75p		
12BH7	50p	80	75p		
12C6	55p	85A2	75p		
12E1	£3.50	723a/b	80p		
12K5	£1.10	803	£6.00		
12K7GT	50p	805	£14.00		
12K8GT	70p	807	85p		
12Q7GT	70p	813	£9.50		
12SA7GT		868A	£1.20		
12U7	35p	7031A	£6.00		
129G7	55p	954	50p		
129J7	55p	955	50p		
12Y4	40p	956	50p		
149T	£1.00	957	50p		
19A9G	85p	1305	£1.00		
19G3	£8.00	1829	70p		
19G6	£8.00	2051	£1.00		
19H5	£14.00	6933	£3.00		
20P3	80p	6067	75p		
20P4	£1.10	6060	70p		

-V.A.T.-
 Please add 25% to all orders

6BG6G	90p	6GH6	40p
6BJ6	85p	6J4WA	£1.25
6BQ7A	60p		
6BR7	£1.20	6J5	85p
6BW6	£1.00	6J5GT	50p
6BW7	£1.00	6J6	30p
6C4	40p	6J7	60p
6C6	50p	6J7G	40p
6CB6	50p	6KGGT	80p
6CH6	£1.45	6K7	55p
6CL6	75p	6K7G	50p
6D6	55p	6K8GT	50p
6EA8	85p	6K25	£1.00
6F7	£1.10	6L6	£1.90
6G6	75p	6L6GT	80p
6G8	90p	6L7G	40p
6F2	75p	6A7	50p
6F32	75p	6A7	50p
6F33	£3.50	6A7GT	40p

MINIMUM POSTAL ORDER £1. PERSONAL CALLERS WELCOME.
 MANY OTHERS IN STOCK include Cathode Ray Tubes and Special Valves, U.K.
 UK Postage £1-£2 17p, £2-£3 30p, £3-£4 40p, Over £5 free. C.O.D. 50p extra.



Colomor (Electronics) Ltd.
 170 GOLDHAWK ROAD, LONDON W12.
 Open 9-12.30, 1.30-5.30 p.m. Closed Saturdays

VALVES AND TRANSISTORS
 Telephone enquiries for valves, transistors, etc., retail 749 3934; trade and export 743 0899.


AIDS to IMPROVED RECEPTION

PART 2

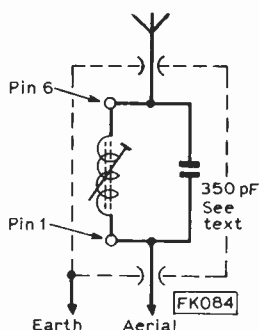C. HEATH

ANTI-BREAKTHROUGH TRAP

A parallel tuned wavetrapp can greatly reduce an interfering signal due to second channel or where intermediate frequency breakthrough is troublesome. The circuit uses a Denco Blue Range 3 coil and the trap is constructed in the maker's aluminium can provided. The 350pF capacitor is for 1.6MHz IF's, but the coil will tune 1500kHz to 6MHz with a trimmer capacitor of 500pF max. A Blue Range 2 is required for the MW band.



Adjustment of the core in the coil will also extend the range over which the trap will tune. For best rejection of an unwanted signal aim for minimum capacity and maximum inductance (core within the coil), provided the trap still shows a sharp point of rejection.

The trap must be connected as close as possible to the receiver's aerial and earth terminals if it is to be effective.


'Q'-MULTIPLIER

A circuit having a high "Q" tunes more sharply, and is thus more selective, than one with a lower "Q". The "Q"-multiplier uses a regenerative stage to enhance the "Q" of a coil tuned to the receiver's intermediate frequency.

Potentiometer VR1 controls regeneration but the circuit should not be allowed to oscillate. Variable capacitor VC1 allows the multiplier frequency to be moved across the receiver's IF passband. In use a "Q"-multiplier is sometimes considered difficult to adjust which probably explains why it is not used more often, but, properly set up, it affords a very economic way of providing a substantial increase in IF selectivity.

The output coupling capacitor is connected to the primary of the first IFT of the receiver, to the "hot"

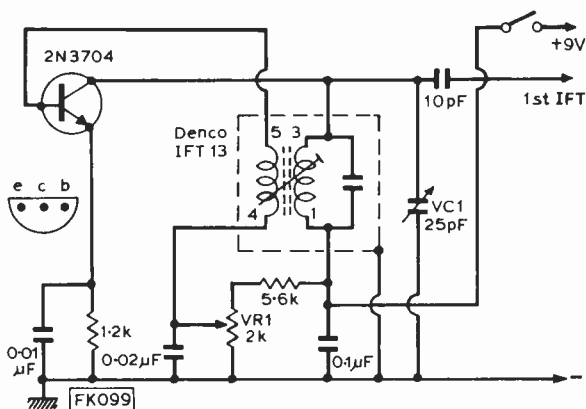end of the coil and not a tapping. The multiplier should be placed as near as possible to this IFT. The coil core is set so that it tunes to the receiver's IF, around 465kHz, with VC1 half way in. Realignment of the particular IFT may be needed on some sets. Potentiometer VR1 is set so that the multiplier is almost oscillating, equivalent to the point of maximum selectivity.



If a particular transistor does not oscillate smoothly reduce the battery voltage or include a resistor of between 100Ω and 1kΩ in series with the switch. The unit can be built in a metal box external to the receiver but the output lead must then be coaxial cable, as short as possible, with the outer screen earthed. The output capacitor should now be placed at the IFT in the receiver.


EXTERNAL AERIAL COUPLING

An external aerial will considerably increase the range of a portable type radio or allow it to be used in circumstances where the internal ferrite rod aerial is unsuitable, such as in a vehicle where the bodywork acts as a screen.

The external aerial is connected to a coupling coil added to the ferrite rod. The winding should be about 35 turns of 36SWG insulated copper wire but neither the number of turns nor the wire gauge are at all important. "Earth" in the circuit is the chassis of the receiver.

A short coaxial cable should be used to connect the external aerial to the receiver in a vehicle, to reduce electrical interference. But do not use screened cable as part of the aerial when the aerial is being added to increase range.

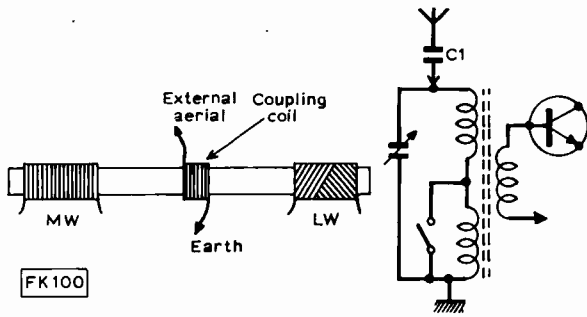
A capacitor C1 can be used as an alternative to



the coupling coil but its value must be kept low or it will detune the receiver's aerial circuit. A trimmer capacitor of a maximum value of about 15pF can be tried. If the receiver has an aerial circuit trimmer control this can be used to maintain correct tuning when an external aerial is connected via C1.

9V FROM 12V

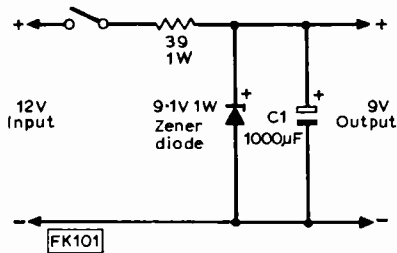If a 9V battery-operated receiver is frequently used in a vehicle it is more economical to use the vehicle's 12V battery than to replace the dry batteries. With the zener diode the output voltage is substantially constant despite the changes in current drawn by the radio.




Capacitor C1 should be as large a value as possible with 1000 μ F as a minimum. The 12V supply can be found at several places in a vehicle but choose one that gives a minimum of electrical noise in the receiver. If the parts are fitted in a box with dry battery terminals on the outside no changes need be made to the receiver which can be plugged in at any time. The terminals can be taken from the top of a defunct battery but be careful to observe the correct polarity.

HEADPHONE SOCKET

This simple modification involves fitting a suitable socket to a receiver to take a headset or earpiece. The circuit is arranged so that the speaker is cut out when the headset is plugged in to the socket. If the receiver's speaker is around 15 to 80 Ω the usual low impedance headset will function without any trouble. If the output impedance is low, 3 Ω or so, the load can be maintained by wiring a resistance or say 3.3 Ω across the headset. It can be fitted inside the headset plug in some cases.

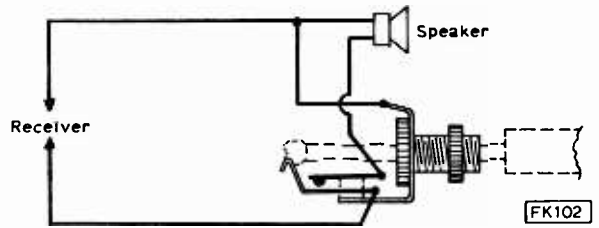The socket should be suitable for the headphone plug, normally 2.5mm or 3.5mm or 1/4in. in diameter,




but there is no reason why different sizes should not be connected in parallel to accommodate different headsets or earpieces.

This modification must **NOT** be made to TV equipment, where the chassis is generally alive.

NOISE LIMITER

This small unit prevents sudden and uncomfortable bursts of noise or signal reaching the speaker or headset. It is particularly effective when the receiver is being operated at maximum gain on a weak signal. The diodes, which must be germanium types, shunt strong signals but leave weak signals unaffected.

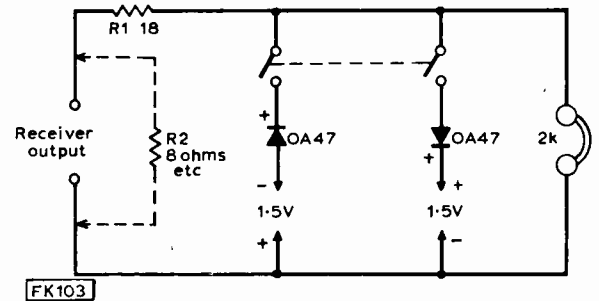Values shown are for output circuits of around 15 to 80 Ω , but for higher values increase R1 to suit. If a lower impedance load must be maintained, wire a suitable value resistor, such as 3 or 8 Ω , across the unit's input, shown dotted.



Headphones of 2k Ω impedance or higher are best for this particular circuit when the limiting voltage is comparatively low. The single cells can be replaced with resistors of about 5.6 Ω with only a slight loss of limiting action. In this case no switches are needed. The components can be fitted into a small box with a lead and plug at one end and socket at the other. Alternatively the limiter can be wired round the receiver's output socket or terminals.

TOP CUT TONE CONTROL

This simple circuit may seem hardly worth a mention but in fact it is very effective at reducing the level of whistles caused by adjacent or second channel interference. It will also help to compensate for the deficiencies of small speakers notorious for their effectiveness at the top of the audio range!

The capacitor should be 0.1 μ F or 0.25 μ F with a

More than just a catalogue!

PROJECTS FOR YOU TO BUILD

4-digit clock, 6-digit clock, 10W high quality power amp., High quality stereo pre-amp., Stereo Tuner, F.M. Stereo decoder, etc., etc.

CIRCUITS . . . Frequency Doublers, Oscillators, Timers, Voltmeters, Power Supplies, Amplifiers, Capacitance Multiplier, etc., etc. . . .

Full details and pictures of our wide range of components, e.g. capacitors, cases, knobs, veroboards, edge connectors, plugs and sockets, lamps and lampholders, audio leads, adaptor plugs, rotary and slide potentiometers, presets, relays, resistors (even 1% types!), switches, interlocking pushbutton switches, pot cores, transformers, cable and wire, panel meters, nuts and bolts, tools, organ components, keyboards, L.E.D.'s, 7-segment displays, heatsinks, transistors, diodes, integrated circuits, etc., etc. . . .


Really good value for money at just 40p.




The 3600 SYNTHESISER

The 3600 synthesiser includes the most popular features of the 4600 model, but is simpler. Faster to operate, it has a switch patching system rather than the matrix patchboard of the larger unit and is particularly suitable for live performance and portable use.

Please send S.A.E. for our price list.

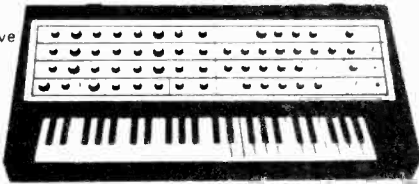


The 4600 SYNTHESISER

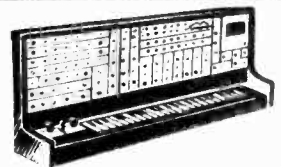

We stock all the parts for this brilliantly designed synthesiser, including all the PCB's, metalwork and a drilled and printed front panel, giving a superb professional finish. Opinions of authority agree the ETI International Synthesiser is technically superior to most of today's models. Complete construction details in our booklet now available price £1.50, or S.A.E. please for specification

GRAPHIC EQUALIZER

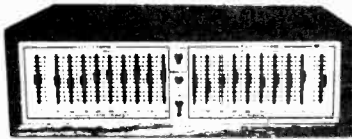A really superior high quality stereo graphic equaliser as described in Jan. 1975 issue of ETI. We stock all parts (except woodwork) including all the metal work drilled and printed as required to suit our components and PCB's. Complete reprint of article—price 15p.



ELECTRONIC ORGAN

Build yourself an exciting Electronic Organ. Our leaflet MES51, price 15p, deals with the basic theory of electronic organs and describes the construction of a simple 49-note instrument with a single keyboard and a limited number of stops. Leaflet MES52, price 15p, describes the extension of the organ to two keyboards each with five voices and the extension by an octave of the organ's range.

Solid-state switching and new footages along with a pedal board and a further extension of the organ's range are shown in leaflet MES53, priced at 35p (Pre-publication price 15p)



NO MORE DOUBTS ABOUT PRICES

Now our prices are GUARANTEED (changes in VAT excluded) for two month periods. We'll tell you about price changes in advance for just 30p a year (refunded on purchases). If you already have our catalogue send us an s.a.e. and we'll send you our latest list of GUARANTEED prices. Send us 30p and we'll put you on our mailing list — you'll receive immediately our latest price list then every two months from the starting date shown on that list you'll receive details of our prices for the next GUARANTEED period before the prices are implemented! — plus details of any new lines, special offers, interesting projects — and coupons to spend on components to repay your 30p

NOTE: The price list is based on the Order Codes shown in our catalogue so an investment in our super catalogue is an essential first step.

Call in at our shop, 284 London Road, Westcliff-on-Sea, Essex. Please address all mail to



MAPLIN ELECTRONIC SUPPLIES
P.O. Box 3 Rayleigh Essex SS6 8LR.

I enclose Cheque/P.O. value _____ PW
For _____ copy/copies of your Catalogue
Name _____
Address _____

MAPLIN ELECTRONIC SUPPLIES P.O. Box 3 Rayleigh Essex SS6 8LR.



WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 25 3, 8 or 15 ohm	£3-84
Baker Group 33 3, 8 or 15 ohm	£10-25
Baker Group 50/12 8 or 15 ohm	£14-00
Baker Deluxe 12" d/cone	£13-75
Baker Major " " "	£11-87
Baker Regent " " "	£10-90
Baker Superb " " "	£18-12
Baker Auditorium 12	£18-25
Celestion MH1000 horn, 8 or 15 ohm	£15-60
Celestion PS8 for Unilax	£3-75
Celestion G12M 8 or 15 ohm	£15-00
Celestion G12H 8 or 15 ohm	£18-45
Celestion G15C 8 or 15 ohm	£30-25
Celestion G18C 8 or 15 ohm	£39-85
EMI 13 x 8" 150 d/c 8 ohm	£2-94
EMI 13 x 8" type 350 8 or 15 ohm	£9-58
EMI 13 x 8" 20 watt base	£7-69
EMI 6 1/2" 93850 4 or 8 ohm	£4-37
EMI 8 x 5 d/cone, roll surr 10 watt	£3-44
EMI 2 1/2" tweeter 97492AT	£8-77
Eagle DT33 30 watt tweeter	£6-31
Eagle HT15 horn tweeter	£4-40
Eagle CT5 cone tweeter	£2-06
Eagle CT10 tweeter 8 or 16 ohm	£3-90
Eagle MHT10 horn tweeter	£4-44
Eagle crossover CN23, CN28, CN216	£1-75
Eagle FR4	£8-12
Eagle FR5	£8-12
Eagle FR8	£12-31
Elac 9 x 5, 59RM109 15 ohm, 59RM114 8 ohm	£3-44
Elac 6 1/2" 6RM171 d/c roll surr.	£4-06
Elac 6 1/2" 6RM220 d/cone	£3-12
Elac 4" tweeter T W4	£1-75
Elac 10" d/cone 10RM239 8 ohm	£3-12
Elac 8" 8CS175 3 ohm	£2-87
Fane Pop 15 watt 12"	£5-25
Fane Pop 25/25 watt 12"	£7-50
Fane Pop 50 watt 12"	£12-00
Fane Pop 55 60 watt 12"	£13-95
Fane Pop 60 watt 15"	£14-75
Fane Pop 100 watt 18"	£25-95
Fane Crescendo 12A 100 watt 12"	£34-50
Fane Crescendo 12B bass	£36-50
Fane Crescendo 100 watt 15"	£47-50
Fane Crescendo 150 watt 18"	£62-95
Fane 801T 8" d/c roll surr.	£8-12
Fane 801T 8" d/c roll surr.	£5-75
Fane 808T 8" d/c	£3-44
Fane 701 twin ribbon horn	£40-00
Fane 910 horn	£14-95
Fane 920 horn	£33-95
Goodmans 8P 8" or 15 ohm	£5-50
Goodmans 10P 8 or 15 ohm	£5-80
Goodmans 12P 8 or 15 ohm	£13-95
Goodmans 12P-D 8 or 15 ohm	£16-95

Goodmans 12P-G 8 or 15 ohm	£15-95
Goodmans Audlomag 12AX 100 watt	£36-50
Goodmans Audlomag 15AX	£40-25
Goodmans 15P 8 or 15 ohm	£21-00
Goodmans 18P 8 or 15 ohm	£36-00
Goodmans Hidas 750	£15-00
Goodmans Axent 100 tweeter	£8-44
Goodmans Audiom 100 12"	£13-90
Goodmans Axlom 402 12"	£20-00
Goodmans Twlnaxlom 8"	£10-14
Goodmans Twlnaxlom 10"	£10-75
Kef T27	£6-06
Kef T15	£6-94
Kef B110	£8-37
Kef B200	£9-50
Kef B139	£16-50
Kef DN8	£2-31
Kef DN12	£5-75
Kef DN13	£3-87
STC4001G super tweeter	£6-56
Richard Allan CGBT 8" d/c r/aurr.	£7-37
2 1/2" 64 ohm, 70mm 80 ohm, 70mm 8 ohm	77
2 1/2" 75 ohm	55
7" x 4" 3 or 8 ohm	£1-85
8" x 5" 3 or 8 ohm	£1-75
10" x 6" 3, 8 or 15 ohm	£2-69

SPEAKER KITS

Baker Major Module	each £13-44
Goodmans Mezzo Twlnkit	pair £47-10
Goodmans DIN 20	each £13-44
Helme XLK 25	pair £25-44
Helme XLK 30	pair £17-19
Helme XLK 50	pair £48-25
Keffit 1	each £48-44
Keffit 3	each £42-50
Richard Allan Twlnkit	each £10-37
Richard Allan Triple 8	each £15-94
Richard Allan Triple 12	each £23-15
Richard Allan Super Triple	each £27-50
Wharfedale Linton 2 kit	pair £23-12
Wharfedale Glendale 3 kit	pair £40-60
Wharfedale Dovedale 3 kit	pair £63-12

PA/DISCO AMPLIFIERS

(carr. and ins. £1)	
Baker Major 100 watt	£37-25
Linear 30/40	£30-00
Linear 40/50	£35-00
Linear 80/100	£58-95
Linear 100 watt slave	£44-00
Eagle PA range in stock—ask for catalogue.	

Free with speaker orders over £7—

"Hi-Fi Loudspeaker Enclosures" book. All units guaranteed new and perfect. Prompt despatch. Carriage and packing: speakers 38p each, 12" and up 50p each. Speaker kits 75p each (£1.50 pair) tweeters and crossovers 25p.

Including V.A.T. 25%

WILMSLOW AUDIO (Dept. PW)

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire. SK9 1HF
Discount Radio, PA, Hi-Fi: 10 Swan Street, Wilmslow
Send stamp for free booklet "Choosing a Speaker"



Cassettes

The best buy!

Agfa Low Noise Cassettes AT LESS THAN HALF PRICE!

	1	5	10
C60	40p	£2-00	£3-98
C90	54p	£2-70	£5-38
C120	75p	£3-70	£7-38

AGFA HIGH DYNAMIC SUPER

	1	5	10
C60+0	54p	£2-70	£5-35
C90+0	70p	£3-50	£6-75
C120	99p	£4-95	£9-95

AGFA STEREO-CHROM CHROMIUM DIOXIDE

	1	5	10
C60	90p	£4-50	£8-75
C90	£1-10	£5-50	£10-90

SAME DAY DESPATCH. P. & P. 15p per order

WILMSLOW AUDIO (DEPT. PW)

10 SWAN STREET, WILMSLOW, CHESHIRE, SK9 1HF

Cut-price prerecorded cassettes—send stamp for list

Wire Wound Resistors. Our selection of mixed values. 30 for £1.40. 100 for £3.50.

Audio Amplifier Module. Mullard LP1173, output power, nominal 10 watt, supply voltage +24 volt, with data and circuit, £2.30 + post.

Ferguson Stereogram chassis Model 3357, all transistor, medium long, VHF/FM, 3 watts per channel S/M, with connection data, less tuning scale, £18.00. Post paid.

Crystals HC6U: 52-03333 MHz: 52-02500: 52-01667: 51-55667: 51-58330: 37-78250: 37-75000: 12-895-8: 12-891-3: 12-700-0: 9-456-25: 9-455-55: 9-533-33: 9-531-94: 9-520-55: 9-090-62: 9-087-5 50p each.

Electrolytics. 32/32/32µF, 325v. 2" x 1 1/2" 35p: 80µF 150v 1 1/2" x 1" 20p: 2000µF 30v, 2 1/2" x 1" 25p 2000µF 35v 3" x 1" 30p 470µF 100v 3" x 1 1/2" 25p: 2000/2000µF 25v 2" x 1 1/2" 35p: 700µF 200v 3 1/2" x 1 1/2" 30p: 16/16µF 275v 1 1/2" x 1" 20p: 40/40/20µF 275v 3" x 1" 20p: 4500/900/900µF 30v 2 1/2" x 1 1/2" 50p: 2500µF 40v 2 1/2" x 1 1/2" 40p: 470µF 25v 1 1/2" x 1 1/2" 15p: 4,000µF 25v 3" x 1 1/2" 40p. 32µF 450v 1 1/2" x 1" 30p: 5µF/16µF 450v 1 1/2" x 1 1/2" 30p: 1000µF 12v 1 1/2" x 1 1/2" 15p. 5000µF 50v 2" x 1 1/2" 50p: 150/200/200µF 300v 3" x 1 1/2" 50p: 450µF 35v 2 1/2" x 1 1/2" 50p.

Try our parcel of small capacitors 20 mixed values £1.50 + post.

Matched pair of books self speakers. Teak finish, size 12" x 8" x 5", 8 x 5 8" ohms ceramic, 5 watts RMS. Complete with d.n leads. £10.00 pair + post.

Thorn TV IF chassis. 950 series (less valves). £1.60 + post.

UHF 625 transistor push button tuner (NSF Telefunken) as used on Decca MS2400. Brand new and boxed, circuit diagram supplied £3.00 + post.

P-C Boards (not computer panels) 1 off 6 transistor single wave band. 1 off 4 transistor audio. 1 off 3 transistor £1.40 + post, three boards.

Repanco Transformers AF1, AF2, LT45, 46, 47, 49, 53. 20p each + post.

M/M, W/W, VHF Tuner 5 transistor in kit form, complete with full assembly instructions. 9vt supply, positive earth. Output 100mw. Built-in A.M. aerial. 88-108 Mcs. £5.25 + post

Mains Droppers, 10 mixed values, £1.00 + post.

Edgewise Level meters, 200µA, size 1" overall. 50p + post.

Chrome Plastic knobs, 3 types, 4 off each with spring clip, £1.25 + post.

Aluminium Chassis, 7 1/2" x 5 1/2" x 2 1/2" 65p + post 10" x 7 1/2" x 2 1/2" 75p + post. 11" x 7 1/2" x 2 1/2" 85p + post.

Push Button Selector for varicap tuner—4 way £1.50 6 way £2.00 + post.

Portable Radio AFC FM, MB/SW/LW/MW. Battery only 12vt. £17.50 + post.


Ferguson Stereogram Chassis. MW/LW/VHF with tuning scale (5+5 watts sine wave) 15 ohms £26.25. Post paid 15 ASSORTED SWITCHES £1.90 + post. 50—3 way to 7 way TAG STRIPS, £1.15 + post. ALMA

REPANCO & DENCO COILS. NEW/BOXED OUR SELECTION—5 FOR £1.15 + post.

Please add 10% post and packing. Add 25% VAT to total order. Gram Chassis free postage. No goods despatched outside U.K.

SURPLECTRONICS


216 LEAGRAVE ROAD, LUTON, LU3 1JC, BEDS.

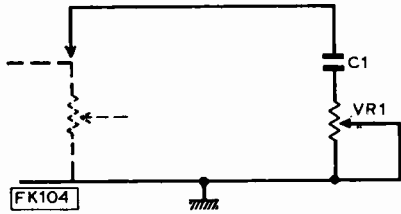

5kΩ potentiometer for VR1 in the case of transistorised receivers, and 0.02μF to 0.05μF with 25kΩ to 50kΩ for VR1 for high impedance circuits, such as are found in valved receivers. The connection is made to the top of the audio gain control but a tone control of this type must not be used in that part of a receiver in which negative feedback is already incorporated.

BANDSPREADING

BANDSPREADING is very effective at alleviating the critical tuning that is often experienced on the short wave bands. In a simple superhet receiver the aerial and oscillator circuits are tuned by a two-gang variable capacitor VC1/VC2. Simple bandspreading consists of adding a small value variable capacitor VC3 in parallel with the oscillator section VC2. VC3 is typically 5pF, mounted at a convenient point on the front panel and fitted with a slow-motion drive.

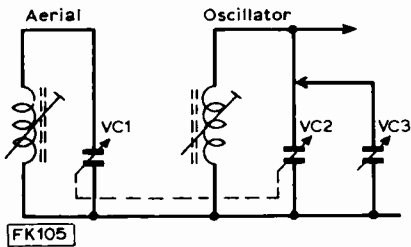

A capacitor similar to VC3, and ganged with it, can be connected in parallel with VC1 to maintain alignment of the aerial circuit but problems of tracking arise, especially if the receiver is bandswitched, so VC3 alone is advised.


The degree of bandspreading achieved by VC3 will depend on the frequency involved and the ratio of VC3 to the value of VC2 at any point on the dial. At low frequencies VC3 can be increased to 15 or 25pF.

9V DC MAINS UNIT

THIS circuit will provide 9V DC to replace the batteries in transistor radios and similar equipment. A transformer with a secondary of 9.0-9V at 100mA should be sufficient for most purposes. The silicon diodes should have a minimum PIV rating of 50V. Those in the 1N4000 range are suitable.

Output voltage will depend to some extent on the current drawn by the external load but small

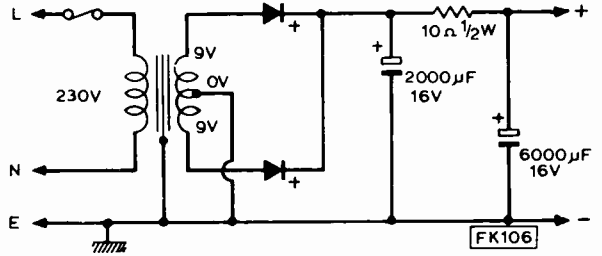variations are not usually of much importance with the average receiver. A zener diode could be added to stabilise the output voltage at a particular value.



The core of the transformer should be earthed, as well as the secondary centre tap, and a fuse in the mains supply is highly desirable. If the mains hum level is objectionable, in spite of the large value of smoothing capacitors used in this circuit, try fitting two capacitors, in parallel across the mains input, between fuse and transformer primary. The junction of these diodes should then be taken down to earth. The capacitors should be about 0.1μF each rated at NOT LESS than 750V working. Ensure the unit is disconnected from the mains before trying out this modification.

If an output of opposite polarity is required then reverse the diodes and the electrolytic capacitors.

BINDERS FOR PW

Keep your copies together
Keep them clean
with the
PW Easi-Binder

The Easi-Binder is attractively bound with the title blocked in gold on the spine with the current (or last) volume number and year. For any previous volume numbers please advise year and volume and a separate set of gold transfer figures will be supplied.

£1.90 inclusive of VAT, post and packing from:
Post Sales (Binders) IPC Magazines Ltd.,
Carlton House, 66 Great Queen Street,
London WC2

IMPROVE YOUR BUDGET STEREO SYSTEM

PART 2

B. BARNARD

READERS who have followed me so far will remember that we have replaced the ceramic pickup with a magnetic one (at the same time, of course, taking out any tone compensating components such as resistors in series or parallel with the pickup), constructed and fitted a pre-amplifier with its own power pack and have dealt with the problem of mains hum induced into the windings of the magnetic cartridge.

The result is very greatly improved reproduction of gramophone records over the treble range but distressingly "boomy" bass. This poor quality in the bass region is almost sure to be due to shortcomings in the design and construction of the loudspeakers but, before starting on this problem, it is probable that some tidying up is necessary on the work already done.

The first point is in the form of a warning; some makes of integrated circuit used in the preamp are very noisy in operation and for this reason I do not advise buying unknown makes over the counter on the assurance that they are "just as good"—they may be, but it is expensive to find out that they are not. Buy any of the well-known makes and be safe!

'TIZZY' SOUND

After playing several records on my own budget stereo after modification, I became aware of a "tizzy" sound whenever I touched the pickup arm, and, at the same time, I noticed an alarming increase in the pops and bangs whenever our refrigerator or central heating cut in or out. Since this followed the work I had done, it seemed very sensible to examine very closely the earthing arrangements on the input side of the new preamplifiers. In the original arrangement with the ceramic cartridge, the braided earth sleeve of the cartridge leads terminated on a tagboard on the underside of the Garrard deck and from this point another screened lead took over and fed the signal to the first stage of the main amplifier. This is the usual arrangement and is normally perfectly satisfactory. However when the additional amplifier is added with its high gain it may not be, and it certainly was not in the case of my own set-up!

I found it necessary to connect the braid at the tagboard direct to the record deck, which is itself connected direct to chassis by a separate lead from the motor terminal board. This, of course, gives a perfect "hum loop" situation but in this case it did not produce any hum. So that is how I have left it but I feel fairly sure that this will not be the solution in all cases and it may be found necessary to carry out a good deal of patient work on the earth-

ing arrangements before a satisfactory solution is found. However, in my case the live condition of the pickup arm was completely overcome and the pops and bangs reduced to minor proportions.

I had to do a lot more work to remove this annoying impulse interference altogether. This applies to a great deal of audio equipment and has been covered in many articles and books. I will not repeat it in this article but content myself by saying that you will probably use quite a few 0.01 μ F capacitors before you eliminate it completely!

IMPROVING THE LOUDSPEAKERS

The obvious and major criticism of the sound quality from the system so far is loud resonant one-note bass. Any hi-fi expert will tell you that anything on the price of a loudspeaker over £30 has been spent on improving the sound below 50Hz. As our purpose is to spend as little money as possible, it is quite obvious some compromise is essential.

When you remove the back from the budget loudspeaker, do not expect to find much sophistication, it is likely to be basic though fundamentally good value. In my own case, the speaker cabinets were approximately 18 x 13 $\frac{1}{2}$ x 7 $\frac{1}{4}$ in. deep. This is rather larger than the average and gives a cubic capacity of about 1760in.³, very suitable for an 8in. speaker when the cabinet is totally enclosed. Inside were two units, an 8in. general-purpose speaker and a cone tweeter. Neither unit was very robustly constructed. The tweeter was fed by a 4 μ F electrolytic capacitor, there being no crossover unit apart from this.

The inside of the cabinet was bare wood but the cabinet back was lined with a thick covering of foam plastic. The only surprise was a 2in. diameter hole in the front (in addition of course to those for the speakers) through which I assume the bass from inside the cabinet joined that from outside, hopefully in phase, thereby increasing the acoustic efficiency considerably in the lower region. With this arrangement it is not surprising that the modest rated 6W of audio was enough for the noisiest of teenage parties!

AIR TIGHT

The enclosures were constructed from chipboard and close examination of the edges at the back showed a lot of gaps which suggested to me that the quality of board left a good deal to be desired from a hi-fi point of view. Nevertheless, the general construction was solid enough and the backs fitted

Crescent Quality Components


BARGAIN CAPACITOR 2,000MFD at 50v. DC wkg. Size — 2" x 1" diameter. Tag ended. All new and unused. Our price **35p.** 25%.

BARGAIN PROJECT BOX

A plastic box with moulded extrusion rails for PC or Chassis panels with metal front plate fitted with four screws (all supplied).

An ideal box to give a small project a professional finish. SIZE (internal) 81mm x 31mm x 28mm.

OUR PRICE 40p. +8%

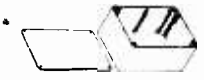

JB11D STEREO JUNCTION BOX

The most popular stereo junction box. Facility for two pairs of headphones and two speakers. 3 position switch selects headphones, loudspeakers or both.

A bargain at **£2.50** +25%

LIGHT EMITTING DIODES 5mm

	RED	GREEN	YELLOW	AMBER
0.2 inch	17p	27p	29p	27p
0.16 inch	24p	29p	30p	29p
0.125 inch	15p	25p	30p	25p

For orders of 10 and more LEDs 10% discount. (All LEDs supplied with free plastic mounting clip).

LOW COST SEVEN SEGMENT DISPLAYS 3-INCH +8%

Model	Color	Com. Anode	Left Dec.	Right Dec.	Price
CR72K	Red	Com. Anode	Left Dec.		£1.35
CR52G	Green	Com. Anode	Left Dec.		£1.35
CR82Y	Yellow	Com. Anode	Left Dec.		£1.35
CR74R	Red	Com. Cathode	Right Dec.		£1.35
CR54G	Green	Com. Cathode	Right Dec.		£1.35
CR84Y	Yellow	Com. Cathode	Right Dec.		£1.35

For full information on low cost displays please send 15p.

Clock Chip +8%

CT7001 MOS/LSI Digital Clock/Calendar Chip Plus full Circuits and Information leaflet **£4.95**
Circuits and Information Sheet **16p**
Lit 7001 Led Display for above **£1.10**
Or 4 for **£4.20**

WAFER SWITCHES

- 1 Pole 12 Way
 - 2 Pole 2 Way
 - 2 Pole 3 Way
 - 2 Pole 4 Way
 - 2 Pole 6 Way
 - 3 Pole 4 Way
 - 4 Pole 3 Way
- £7p each +8%**



POTENTIOMETERS

All types 1" and less diameter
Singles
5K Log or 5K Dual
10K Lin Less 10K
25K Switch 25K Less
50K 17p each 50K Switch
100K 100K 55p each
250K 250K +26%
500K Pole 500K
1M Switch 1M
2M 2M

FERRIC CHLORIDE

Anhydrous ferric chloride in double sealed one pound poly packs.
Our Price 50p + P/P + VAT @8% per lb.

MAINS TRANSFORMERS

Open Type Double Wound Continuously Rated, two hole fixing clamp with colour coded flying leads, varnish impregnated. Approx. size: 1 1/2" x 1 1/2" x 1 1/2" high
Fixing centres: 2 1/2"

- TR1 20-0-20v 100 m/a
 - TR2 12-0-12 v 100 m/a All
 - TR3 9-0-9 v 100 m/a 240 Volt
 - TR4 6-0-6 v 100 m/a Primary
 - TR5 3-0-3 v 100 m/a
- Our Price **£1.25 each +8%**

MONO/STEREO MICROPHONE MIXER

9 volt. High impedance input. Gold finish with four black plastic chrome tipped level control knobs. On/Off switch and stereo/mono switch. 4 Input sockets.

SPECIFICATIONS:

- Input Imp = For XTAL Mics etc.
- Gain = Approx 3.D.B.
- Max Input Sig = 1 volt
- Max Output Sig = 1.3 volt
- Noise Ratio = -60DB
- Supply = 9 volt

OUR PRICE = **£5.25p** +25%

POWER SUPPLY UNITS

PP1 switched 3, 4, 6, 7, 9 and 12 volts at 500 m/a, with on/off switch and pilot light. Size: 130mm x 55mm x 75mm. **ONLY £4.00.**
PP2 Switched 6-7-9 volt Battery Eliminator. Approx. size 2 1/2" x 2 1/2" x 3 1/2". Ideal for cassette recorders **£3.50**
PP3 Car converter. From 12v Pos. or Neg. to 6-7-9 v. Easy to fit and transistor regulated **£3.90** +8%



VEROBOARD +8%

Size	Price	Price	Price
2 1/2 x 3 1/2	35p	25p	15p
2 1/2 x 5	41p	41p	20p
3 1/2 x 3 1/2	41p	41p	
3 1/2 x 5	47p	49p	34p
1 7/8 x 2 1/2	1.24p	98p	69p
1 7/8 x 3 1/2	1.69p	1.32p	97p
1 7/8 x 5	2.16p		1.37p

Pin insertion tool **61p**
Spot face cutter **80p**
Pkt 36 pins (state -1 or -15) **30p**

LOUDSPEAKERS +25%

- 2 1/2" 8 ohm **50p**
 - 2 1/2" 16 ohm **50p**
 - 2 1/2" 80 ohm **50p**
 - 5" 8 ohm ceramic **£1.25**
 - 6 1/2" 8 ohm dual cone ceramic **£2.50**
 - 10" 8 ohm dual cone ceramic **£3.75**
 - 8" x 5" 8 ohm Permalt Magnet **£1.60**
- Pin insertion tool **61p**
Spot face cutter **80p**
Pkt 36 pins (state -1 or -15) **30p**



10-INCH 8 OHM DUAL CONE L.S.
Manufactured by "ELAC" to a very high standard these loudspeakers are a real bargain.
SPEC:—Size = 10" Dual Cone.
Power = 10 Watts
Frequency = 40-15000Hz
+25% Our Price = **£3.75p** each

MAINS KEYNECTOR

Keynector connects any Electrical Equipment to the mains supply in seconds. Ideal for bench, garage demonstrations, etc. Multi connections can be made (max. load 13A fused). **£2.25p.** +8%



ALUMINIUM BOXES +8%

Metal project boxes give your work a professional finish

Model	L	W	H	Price
AB7	2 1/2	4 1/2	1 1/2	54p
AB8	4	6	1 1/2	68p
AB9	4	2 1/2	1 1/2	64p
AB10	4	5 1/2	1 1/2	63p
AB11	4	2 1/2	2	64p
AB12	3	2	1	45p
AB13	6	4	2	69p
AB14	7	5	2 1/2	84p
AB15	8	6	3	99p
AB16	10	7	3	£1.25
AB17	10	4 1/2	3	£1.02
AB18	12	5	3	£1.20
AB19	12	8	3	£1.50

ABS PLASTIC BOXES +8%

Handy boxes for construction projects. Moulded extrusion rails for P.C. or chassis panels. Fitted with 1mm front panels.

- 1005 = 105mm x 73mm x 45mm = **55p**
- 1006 = 150mm x 75mm x 47mm = **72p**
- 1007 = 184mm x 124mm x 60mm = **£1.28**
- 1021 = 105mm x 74mm x 45mm (sloping front) = **55p**

TELESCOPIC AERIAL

Nine section fully swivelling telescopic aerial with 4BA single bolt fixing or two hole fixing bracket. Fully extended = 43"
Fully closed = 7"
Our Price **50p** + P/P + VAT @ 25%

CLEAR PLASTIC PANEL METERS

Size 69mm x 46mm x 35mm these meters require a 38mm hole for mounting.

- ME6 = 0 to 50 micro amp Full Scale
- ME7 = 0 to 100 micro amp Full Scale
- ME8 = 0 to 300 micro amp Full Scale
- ME9 = 0 to 1 m/a Full Scale
- ME10 = 0 to 5 m/a Full Scale
- ME11 = 0 to 10 m/a Full Scale
- ME12 = 0 to 50 m/a Full Scale
- ME13 = 0 to 100 m/a Full Scale
- ME14 = 0 to 500 m/a Full Scale
- ME15 = 0 to 1 amp Full Scale
- ME16 = 0 to 50 volts
- ME17 = 0 to 500 volts A.C. Full Scale
- ME18 = "8" Meter
- ME19 = "VU" Meter



OUR PRICE **£3.00** +8%

WIRE WOUND VOLUME CONTROL +8%

250 ohm Only **25p** EACH.
Approx. 1" Diameter.
Long standard spindle.

MINIATURE RELAYS

Brand new range of British made Relays. Size 1 1/2" x 1" x 1". All two changers with 250v 1.5A contacts and suitable for fitting on 1m Vero-board.

Type Volts Cur. Ohms
rent

- 27A 12v 17mA 700
 - 21A 12v 23mA 430
 - 12A 6v 33mA 185
- All **£1.30** each -

STEREO jack plug to two stereo line sockets complete with 110 mm of cable. For plugging two stereo inputs into one. A Bargain at **55p** + 25%

CABLE LESS SOLDERING IRON WAHL "ISO-TIP"

- ★ Completely Portable
 - ★ Heats in 5 seconds
 - ★ Solders up to 150 joints or more per charge
 - ★ Recharges automatically in its own stand
 - ★ No AC leakage or induced current to damage delicate components
 - ★ Heats to 700 deg. F
 - ★ Fine Tip for delicate and general purpose soldering
 - ★ Only 8" long and weighs just 6 ozs.
- OUR PRICE **£9.75** +8% (spare bits are available)

3 KILOWATTS PSYCHEDELIC LIGHT CONTROL UNIT

Three Channel Bass, Middle, Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 1000W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed).
£18.50 plus 75p P. & P. + 8%



BARGAIN TRANSFORMERS

12-0-12 volt 500m/a
240 volt primary transformer bargain.
approx size = 60mm x 40mm x 50mm
fixing centres = 75mm
Our Price = **£1.20** +8%

P.C. ETCHING KIT

This kit contains all that the constructor will need to etch the circuits of his own design.
Contents = Plastic etching dish.
Sample copper clad board.
Laminate Cutter.
1 lb Ferric Chloride.
Large Plastic Spoon.
Etch Resist Pen.
Full Etching Instructions.
Complete and Big Kit Value at **£3.75p** +8%

LOW NOISE LOW PRICE CASSETTES +8%

Good quality tape in well made screw type cassettes. Presented in single plastic cases.
C80 = 81p C90 = 42p C120 = 63p
10% Discount on ten or more cassettes of one type

U.K. POSTAGE 20p UNLESS OTHERWISE STATED
VAT—All prices are excluding VAT. Please add to each item the VAT rate indicated.

CRESCENT RADIO LTD. P.W.
All mail to No. 1 ST. MICHAELS TERRACE WOOD GREEN, LONDON N22 4SJ.
Phone: 01-888 4474
Callers Welcome at 15 Mayes Road & 13 South Mall, Edmonton N9.

If you construct You should own one.
CRESCENT CATALOGUE
Price 30p.

Marshall's

A. Marshall (London) Ltd Dept: PW
 42 Cricklewood Broadway London NW2 3ET Tel: 01-452 0161/2
 Telex: 21492
 & 85 West Regent St Glasgow G2 2QD Tel: 041-332 4133
 & 1 Straits Parade Fishponds Bristol BS16 2LX
 Tel: 0272 654201/2
 & 27 Rue Danton-Issy Les Moulineaux Paris 92 Tel: 642 2985
Catalogue price 25p Trade and export enquiries welcome

Our range covers over 7,000 items. The largest selection in Britain

Top 200 IC's TTL, CMOS & Linears

CA3018A	85p	CD4043	£1.80	NE565	£4.48	SN7448	90p	SN74157	95p
CA3020A	£1.80	CD4044	£1.80	SL414	£1.80	SN7450	16p	SN74160	£1.10
CA3028A	79p	CD4045	£2.65	SL610C	£1.70	SN7451	16p	SN74161	£1.10
CA3031S	£1.37	CD4046	£2.84	SL611C	£1.70	SN7453	16p	SN74162	£1.10
CA3046	70p	CD4047	£1.65	SL612C	£1.70	SN7454	16p	SN74163	£1.10
CA3048	£2.11	CD4049	81p	SK620C	£2.60	SN7460	16p	SN74164	£2.01
CA3052	£1.62	CD4050	66p	SL621C	£2.60	SN7470	33p	SN74165	£2.01
CA3089E	£1.96	LM301A	48p	SL622C	£4.59	SN7472	26p	SN74167	£4.10
CA3090Q	£4.23	LM308	£2.50	SL640C	£3.10	SN7473	36p	SN74174	£1.25
CD4000	36p	LM005T	£1.50	SN7400	16p	SN7474	36p	SN74175	90p
CD4001	36p	LM180	£1.10	SN7401	16p	SN7475	50p	SN74176	£1.44
CD4002	36p	LM381	£2.20	SN7401AN	38p	SN7476	35p	SN74180	£1.44
CD4006	£1.58	LM702C	75p	SN7402	16p	SN7480	50p	SN74181	£1.95
CD4007	36p	LM709	38p	SN7403	16p	SN7481	£1.25	SN74190	£2.30
CD4008	£1.63	8D1L	45p	SN7404	19p	SN7482	75p	SN74191	£2.30
CD4009	£1.18	8D1L	40p	SN7405	19p	SN7483	95p	SN74192	£1.15
CD4010	£1.18	LM710	60p	SN7406	45p	SN7484	95p	SN74193	£1.15
CD4011	36p	LM723C	90p	SN7407	40p	SN7485	£1.25	SN74196	£1.60
CD4012	36p	LM741C	40p	SN7408	19p	SN7486	32p	SN74197	£1.58
CD4013	66p	8D1L	40p	SN7409	22p	SN7490	45p	SN74198	£2.25
CD4014	£1.72	14D1L	38p	SN7410	16p	SN7491	85p	SN74199	£2.25
CD4015	£1.72	LM747	£1.09	SN7411	25p	SN7492	45p	SN76033N	£2.92
CD4016	66p	LM748	60p	SN7412	28p	SN7493	45p	TAA661B	£1.32
CD4017	£1.72	14D1L	73p	SN7413	35p	SN7494	82p	SN76031N	£1.95
CD4018	£2.55	LM3900	70p	SN7416	35p	SN7495	72p	SN76032N	£2.92
CD4019	86p	LM7805	£2.00	SN7417	35p	SN7496	75p	TAA621	£2.03
CD4020	£1.91	LM7812	£2.50	SN7420	16p	SN74100	£1.25	TAA636	£1.10
CD4021	£1.72	LM7815	£2.50	SN7423	29p	SN74107	36p	TAA300	£1.80
CD4022	£1.66	LM7824	£2.50	SN7425	29p	SN74118	£1.00	TAA350A	£1.10
CD4023	36p	MC1303L	£2.50	SN7427	29p	SN74119	£1.92	TAA550	60p
CD4024	£1.24	MC1318P	£2.59	SN7430	16p	SN74121	37p	TAA611C	£2.18
CD4025	32p	MC1330P	90p	SN7432	28p	SN74122	50p	TAA621	£2.03
CD4027	43p	MC1352P	80p	SN7437	35p	SN74123	60p	TAA618	£2.03
CD4028	£1.50	MC1355P	80p	SN7438	35p	SN74141	85p	TAA618	£2.03
CD4029	£3.50	MC1466L	£3.50	SN7440	16p	SN74145	90p	TBA641B	£1.69
CD4030	87p	MC1469R	£2.75	SN7441AN	85p	SN74150	£1.50	TBA800	£1.69
CD4031	£5.19	NE555V	70p	SN7442	65p	SN74151	85p	TBA810	£1.40
CD4037	£1.93	NE556	£1.30	SN7446	95p	SN74153	85p	TBA820	£1.15
CD4041	£1.86	NE560	£4.48	SN7447	95p	SN84154	£1.50		

BRISTOL 10% discount for callers at our new shop at 1 Straits Parade, Fishponds, Bristol, BS16 2LX producing a current issue of this mag. Tel: Bristol 654201/2

POPULAR SEMICONDUCTORS

2N696	22p	2N3906	27p	AF139	65p	BD139	71p	MPSA56	31p
2N697	16p	2N4037	42p	AF139	65p	BD140	87p	OC28	76p
2N698	82p	2N4036	67p	AF240	90p	BF115	36p	OC35	60p
2N699	59p	2N4058	18p	AF279	70p	BF117	55p	OC42	50p
2N706	14p	2N4062	15p	AF280	79p	BF154	20p	OC45	32p
2N708	17p	2N4289	34p	AL102	£1.00	BF159	27p	TIP29A	49p
2N916	28p	2N4920	£1.10	BC107	14p	BF180	35p	TIP29C	38p
2N918	32p	2N4921	83p	BC108	14p	BF181	36p	TIP31A	£2.00
2N1302	18p	2N5245	90p	BC109	14p	BF184	30p	TIP32A	24p
2N1304	21p	2N5245	47p	BC147B	14p	BF194	12p	TIP33A	£1.01
2N1306	31p	2N5294	48p	BC148B	15p	BF195	12p	TIP34A	£1.51
2N1308	47p	2N5296	48p	BC149B	15p	BF196	13p	TIP35A	£2.90
2N1711	45p	2N5457	49p	BC157A	16p	BF197	15p	TIP36A	£2.70
2N1702	60p	2N5458	46p	BC158A	16p	BF198	18p	TIP40	90p
2N12147	78p	2N5459	49p	BC167B	15p	BF244	17p	TIP295	98p
2N12148	94p	2N6027	45p	BC168B	15p	BF257	47p	TIP305S	50p
2N2218A	22p	3N128	73p	BC169B	15p	BF258	53p	TIS43	28p
2N2219A	26p	3N140	£1.00	BC182	12p	BF259	55p	ZTX300	13p
2N2220	25p	3N141	81p	BC182L	12p	BF261	27p	ZTX301	13p
2N2221	18p	3N200	£2.49	BC183	12p	BF262	27p	ZTX500	15p
2N2222	20p	40361	40p	BC183L	12p	BF299	24p	ZTX501	13p
2N2369	20p	40411	45p	BC184	13p	BF299	24p	ZTX502	18p
2N2646	55p	40406	44p	BC184L	13p	BFX29	30p	IN1914	7p
2N2904	22p	40407	35p	BC212A	16p	BFX30	27p	IN3754	15p
2N2905	25p	40408	50p	BC212LA	16p	BFX84	24p	IN4007	10p
2N2906	19p	40409	52p	BC213LA	15p	BFX85	24p	IN448	7p
2N2907	22p	40410	52p	BC214LB	18p	BFX88	25p	IN5404	22p
2N2924	20p	40411	£2.00	BC227B	18p	BFY50	22p	IN5408	30p
2N2926G	12p	40594	74p	BC238C	15p	BFY51	23p	AA119	8p
2N3053	25p	40595	84p	BC239C	15p	BFY52	20p	BA102	25p
2N3054	60p	40636	£1.10	BC257A	16p	BRY39	48p	BA145	18p
2N3055	75p	40673	73p	BC258B	16p	ME0402	20p	BA154	12p
2N3391	28p	AC162	20p	BC259B	16p	ME0412	18p	BA155	12p
2N3392	15p	AC127	20p	BC301	34p	ME4102	11p	BB103B	23p
2N3393	15p	AC128	20p	BC307B	17p	ME480	95p	BB104B	45p
2N3440	59p	AC151	27p	BC308A	15p	MI481	£1.20	BY126	12p
2N3442	£1.40	AC152	49p	BC309C	20p	MI490	£1.05	BY127	15p
2N3638	15p	AC153	35p	BC327	23p	MI491	1.45	BY211	51p
2N3702	12p	AC176	30p	BC328	22p	MI2955	£1.00	BY121	51p
2N3703	13p	AC187K	35p	BCY70	17p	ME340	48p	OA47	6p
2N3704	15p	AC188K	35p	BCY71	22p	ME370	65p	OA81	18p
2N3706	15p	AD143	68p	BCY72	15p	MIE371	75p	OA90	6p
2N3708	14p	AD161	50p	BD121	£1.00	MIE320	60p	OA91	6p
2N3714	£1.38	AD162	50p	BD123	82p	MIE521	70p	WOZ1A200	33p
2N3716	£1.80	AF106	40p	BD124	67p	MIE2955	£1.20	BY164	37p
2M3771	£2.20	AF109	40p	BD131	40p	MIE3055	75p	ST2diac	20p
2N3773	£2.65	AF115	35p	BD132	50p	MP8113	47p	ST2diac	51p
2N3809	£2.06	AF116	35p	BD135	43p	MPF102	39p	40669	£1.00
2N3819	37p	AF117	35p	BD136	47p	MPSA05	25p	TIC44	29p
2N3820	64p	AF118	35p	BD137	55p	MPSA06	31p	CI06D	65p
2N3904	27p	AF124	30p	BD138	63p	MPSA55	31p	ORP12	60p

Prices correct at October 1975, but all exclusive of VAT, P.&P. 25p.

J. BIRKETT

Radio Component Suppliers

25 The Strait, Lincoln, LN2 1JF
 Telephone: 20767

200 ASSORTED TUBULAR CERAMICS @ 57p.
 200 ASSORTED POLYSTYRENE CAPACITORS for 57p
 50 ASSORTED POTENTIOMETERS for £1.
 BF 180 or BF 181 R.F. TRANSISTORS 5 for £1.10.
 MULLARD LOCKFIT TRANSISTORS BC 147, BC 148, BC 149, BC 157, BC 158, BC 159, BF 194, BF 195, BF 196, BF 197, BF 332.
 All at 6 for 57p.
LARGE PACKET OF MICA WASHERS FOR TRANSISTORS @ 33p.
 100 ASSORTED SILVER MICA CAPACITORS @ 57p.
 X BAND GUNN DIODES with data @ £1.65 each.
 X BAND DETECTOR DIODES similar to SIM 2 @ 15p or IN 23 @ 25p.
 ERIE 1 to 12pf TUBULAR TRIMMERS @ 5p each.
 365pf 3 GANG TUNING CAPACITOR size 2 1/2 x 1 1/2 @ 66p.
 25 ASSORTED TRANSISTOR I.F. TRANSFORMERS for 40p.
 18 VOLT 1 AMP TRANSFORMER 240 VOLT AC INPUT @ 85p.
 UHF TRANSISTOR TV TUNERS. Brand New @ £1.10.
 I.C.'s SIMILAR TO TAA 57. Untested with data 5 for 57p.
 25 BC 107-8-9 METAL TO18 TRANSISTORS. Untested @ 57p.
 SUB-MINIATURE TRANSISTORS OC 57 @ 5p, OC 58 @ 10p, OC 59 @ 6p, OC 60 @ 10p.
 10 MINIATURE 10 AMP SILICON BRIDGES. Untested for £1.25
 CERAMIC FILTERS 10-7 MHz with data sheet @ 30p.
 COMPRESSION TRIMMERS 10pf, 30pf, 50pf, 1000pf. All @ 6p each.
 200 ASSORTED DISC CERAMICS for 57p.
 AF 279 NPN 800 MHz STRIPLINE TRANSISTOR @ 44p.
 HIGH SPEED DIODES BA 158 600 PIV 400mA 10 for 45p.
 240 VOLT MAINS NEONS Green @ 28p each.
 60 ASSORTED WIRE WOUND RESISTORS 3, 5, 10 Watt @ 57p.
 50 AC 128 TRANSISTORS. Untested @ 57p.
 50 RADIO AND TV KNOBS for 75p.
 TUNING CAPACITORS WITH SLOW MOTION DRIVE 250 + 250pf @ 38p, 500 + 500 + 17 + 17pf @ 38p.
 12 P CHANNEL MOS FET's with Circuits @ 75p.
 20 SUB-MINIATURE PRE-SET POTENTIOMETERS 3x300 ohm, 3x2.5K, 3x5K, 3x47K for 35p.
 50 PLASTIC NPN TRANSISTORS 85% GOOD @ 57p.
 50 PLASTIC PNP TRANSISTORS 85% GOOD @ 57p.
 CWO, VAT and Post Paid on Orders over £1.

ENGINEERS

FREE

YOURSELF FOR A
BETTER JOB WITH **MORE PAY!**



Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This helpful guide to success should be read by every ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.

POST NOW CUT OUT THIS COUPON
 CHOOSE A BRAND NEW FUTURE HERE!
 Tick or state subject of interest. Post to the address below.

- | | | |
|--|--|--|
| Build-As-You-Learn | Electronics Engineering | Transistor Technology |
| PRACTICAL RADIO AND ELECTRONICS (with kit) | Computer Electronics Computer | CITY AND GUILDS Installations and Wiring |
| Electrical Engineering | Colour TV Servicing | CITY AND GUILDS Electronic Technicians |
| Electrical Installations and wiring | C&G Radio, TV & Electronic Mechanics | CITY AND GUILDS Radio Communications etc. etc. |
| Electrical Draughtsmanship | General Radio and TV Engineering | |
| Electrical Mathematics | Radio Servicing, Maintenance and Repairs | |

To ALDERMASTON COLLEGE Dept. EPW09, Reading RG7 4PF
 Also at our London Advisory Office, 4 Fore Street Avenue, Moorgate-London, EC2Y 5EJ Tel: 01-628 2721

NAME (Block Capitals Please) _____
 ADDRESS _____
 POST CODE _____
 Other subjects _____
 Accredited by C.A.C.C. Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

tightly and securely. The result of all this examination immediately explained the loud and poor quality bass since the cones of the two 8in. speakers had no mechanical damping at all and, once set in motion by a low frequency signal, were free to carry on moving at their resonant frequency for an appreciable time after the signal had stopped.

The only and rather obvious answer to the problem was to set about making the cabinets *enclosures* in the proper meaning of the word, that is to say, make them as air-tight as possible so that the cone movements would be restricted by air pressure. This is, of course, the principle of the "infinite baffle" and most of the smaller good quality speakers are designed on this principle. The first job therefore was to block the unused hole in the cabinet front with a piece of good quality chipboard or 5-ply which was glued and screwed into position.

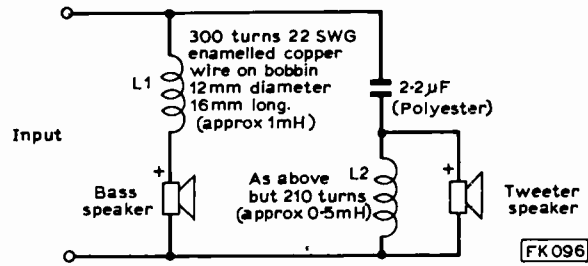


Fig. 1: Circuit details of the cross-over unit. Care should be taken in the winding of the coils, to ensure that the units for both channels are exactly the same.

CROSSOVER UNITS

The first major item of expenditure is a pair of crossover units which I believe are essential. The actual crossover frequency in this application is not critical and anything in the region of 3kHz will be suitable. Shopping around will most likely find a pair for less than £5 but for those who prefer to make their own, and do not mind tedious coil winding, Fig. 1 gives constructional and wiring details. Care must be exercised in connecting these to ensure that both follow the same wiring pattern so that problems do not arise later in getting both loud-speaker systems to operate in phase. Most speaker units have one tag marked with a red dot and if this is connected through the crossover unit to the live speaker lead in both cases, all will be well.

The next job was to line the interior of both cabinets with some soft sound-absorbing material. A good look around the household will usually reveal something suitable which will avoid dipping into the pocketbook. I found some surplus carpet underfelt of the rubberised variety and this is very suitable. Avoid very thick and heavy materials for, although they absorb sound, they also tend to reduce the effective cabinet volume which is undesirable. The material is fixed in place with small tacks and a little glue in strategic places. The photograph shows the interior of one cabinet after this treatment with the crossover unit in position. This photo also shows two other items not yet dealt with. Fixed to the back is a 50Ω wirewound potentiometer and the cone tweeter has been replaced by a superior dome type.

After completing the work and testing for several weeks, although the results were very pleasing, I

decided to extend the frequency response in an upward direction and to improve sound dispersion and thus the stereo effect. To do this I bought a pair of good quality dome tweeters (about £6 each). This certainly had the desired effect but I found that the new tweeters were very efficient and, since all the work I had done had tended to reduce the efficiency of the 8in. speakers, the overall effect was out of balance and the tweeters tended to predominate. For this reason, the 50Ω 3W potentiometers are fitted and they are, in effect, volume controls for the tweeters enabling the required balance to be obtained while playing programme material, Fig. 2.

VACANT SPACES

The last job in improving the speakers is to fill in the vacant spaces around the speaker units with more sound-absorbing material. For this, underfelt and similar material is not suitable as it is much too dense. The recommended material is BAF wadding which can be bought from most hi-fi shops for about 80p per sq. yd. I experimented with ordinary domestic cotton wool and found it very effective in this application, readily available in rolls about 12in. wide. It should be very carefully unrolled without teasing it out and then cut to suitable lengths. For my cabinets I inserted two pieces, 18in. long very loosely rolled, each side of the 8in. units. A shorter piece similarly rolled fills the spaces above the big speakers and behind the tweeters. The object is to replace some of the air in the enclosure with the wool but not to introduce a solid substance which would effectively reduce the enclosure capacity. For larger or smaller cabinets the actual quantity of BAF wadding or wool must be found by trial and error, too much will have the effect of killing the bass response but the correct amount removes all traces of any unpleasant "boxy" tone.

We are now at the stage where we can replace the backs on to the enclosures and our aim is to make them airtight so as to put a brake on those bouncing cones, so the backs must fit well and be screwed down tight. Pay particular attention: to the holes through which the leads are taken as it may be necessary to fill these with putty or some similar substance in order to avoid large air leaks.

By the way, when I say "airtight" I do not mean this too literally! There has to be some escape of pressure or the cones would never be able to move at all. So some leakage is essential and this is almost certain to take place through the gap between the speech coil and polepiece and it is also doubtful if the cone suspension is completely airtight in units of this quality. So in making the enclosure and its


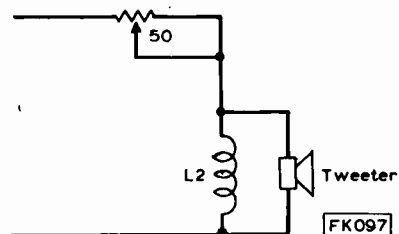


Fig. 2: 50Ω 3W potentiometer shown in-circuit, to provide some control over the tweeters.

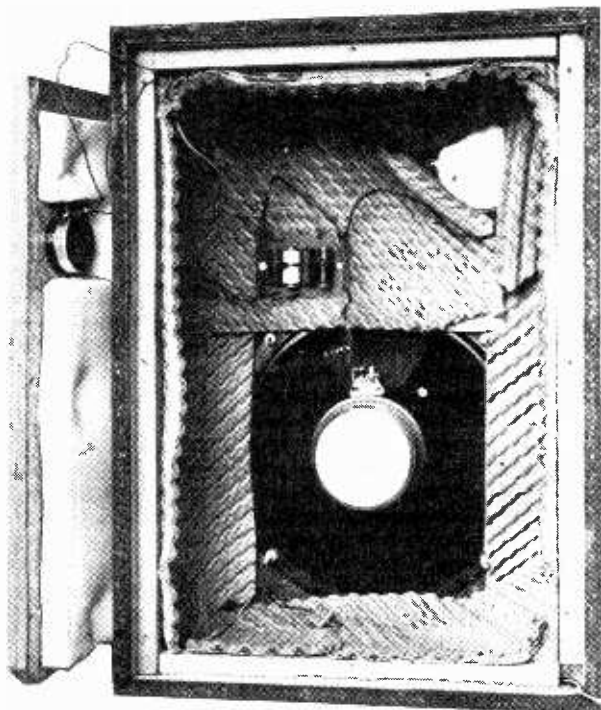

Interior view of the speaker enclosure, showing the rubberised carpet underlay fixed in position. The vacant space should now be filled with BAF wadding.

back as airtight as possible you are very unlikely to overdo it.

The two enclosures (we are fully entitled to call them that) can now be tested out on a signal. It will be obvious that the efficiency has been reduced in the middle and bass areas so the volume control will be further advanced than before this work was done. But the quality of sound should be immensely improved. The bass in particular will be "tight" and musical and it should be possible to advance the bass boost much further than before whilst still maintaining good tonal balance and really pleasant quality.

I believe the foregoing lines of attack will apply with great benefit to almost all budget loudspeakers. It is necessary before starting any work to assess very carefully the shortcomings of the speakers as supplied and to decide what improvements are required and then to examine the interior of the cabinets and the unit or units to decide what work is likely to be most beneficial. This will always reveal problems in the bass area no matter what else and the first answer to this is always cone damping. This inspection must also cover close examination of the cabinets themselves; if the construction seems weak and they sound hollow when tapped with a metal object, it may be necessary to fit wood struts in strategic places to make sure they will not rattle or resonate of their own accord.

FITTING A TUNING METER

Few budget stereos run to a tuning meter, but they nearly all have an AFC circuit which is intended automatically to adjust for any minor tuning errors and to correct any tendency to drift in the RF oscillator. A reliable tuning indicator which shows

when the tuning point of minimum distortion and minimum background noise is found is almost essential to anyone who takes his music seriously.

The circuit arrangements for a meter which peaks at the exact tuning point are very simple. A moving coil meter with FSD of about $100\mu\text{A}$ connected with about 30 to $40\text{k}\Omega$ in series is connected across the large electrolytic in the discriminator circuit. These meters are expensive to buy especially if you want to pick one that fits nicely with the styling of your system. I had a very elegant meter which exactly suited the styling of my unit audio but it required 1mA for FSD. We cannot use such a meter across the discriminator as it has an internal resistance of only 50Ω or so. The answer is to arrange the meter to be in circuit only when tuning and to remove it while we are listening.

One way is to fit a small press-button switch which brings the meter into circuit when made but disconnects it when open. This button is pressed when changing stations, the tuning adjusted until the meter peaks and the button then released, restoring the circuit to normal.

SPACE CONTACTS

Examination of the AFC switch revealed a pair of unused contacts. The usual arrangement is a simple make-and-break single pole switch which joins the AFC line to chassis when it is disabled but since manufacturers of budget stereo seldom design special switches for such a simple function it is very likely that you will find at least one pair of unused contacts which can be used to switch the meter in and out. The position then is that we disable the AFC when we want to tune and then tune for peak reading on the meter. After this we return to the AFC position, leaving the AFC diode to take care of any oscillator drift, the meter remaining out of circuit until we want to change stations.



The photograph above shows the meter fitted on my budget stereo alongside the AFC switch which controls it. It works extremely well and I get dead accurate tuning every time. I had to experiment with various values of resistance in series with the meter and finally fixed on $6.8\text{k}\Omega$ which gives between half and three-quarter scale reading on an $800\mu\text{V}$ signal at my aerial. By a slight circuit modifi-

continued on page 604

Get the party going!

IN NEXT MONTH'S
PRACTICAL WIRELESS

With our PW 'Easybuild'
STEREO DISCO SYSTEM
(100+100W)

This high-power stereo disco plus light show, has been designed for the home constructor who requires his equipment to be professional in both sound and looks. Specifications include a THD of 0.1% at 60W and the latest BSR belt drive turntable units. Mixing facilities provide crossfade and mic. plus aux. inputs. The light show, which comprises three colours, operates on the sound to light principle.



+ *yet another*
8-PAGE SUPPLEMENT

SIMPLE HOME PROJECTS No.3

also:
A STABILISED POWER SUPPLY

A simple to build power supply which has an output variable from 5 to 24V at 1A. The design features preset current limit, complete short circuit protection and a metered output. An ideal addition to your test equipment!

PLUS ALL THE REGULAR FEATURES
ON SALE IN NOVEMBER



TV SOUND T

THE transmitted sound quality of television is inherently very high, but due to severe limitations in the audio side of domestic TV receivers, it is rarely heard at its best. This article describes a high performance TV Sound Tuner for feeding into a hi-fi system or tape recorder, enabling full benefit to be gained from the broadcast.

Up-to-date techniques have been used to provide push button varicap tuning and high sensitivity. Three integrated circuits are used and a ceramic filter with quadrature detector ensures easy setting up without instruments.

TV SYSTEM


Television in Britain is transmitted on 625 lines with a line rate of 15.625kHz and 50Hz field rate. The video is transmitted as amplitude modulation of an RF carrier, while the sound channel is broadcast as frequency modulation of a sound carrier spaced 6MHz from the vision carrier. Fig. 1 shows a block diagram of the sound section of a TV receiver.

In all frequency changing operations in the receiver the sound carrier remains spaced 6MHz from the video. After final video detection the result at the output of the video detector is video and a 6MHz FM sound carrier, the vision carrier having been transferred to zero frequency. The audio is simply recovered from the FM carrier by frequency discrimination, using a conventional discriminator or the more recent "quadrature" detector.

CIRCUIT DESCRIPTION

The pre-assembled and aligned IF sub-assembly used in this project performs the function of IF amplifier, vision detector, 6MHz limiter amplifier and 6MHz quadrature discriminator.

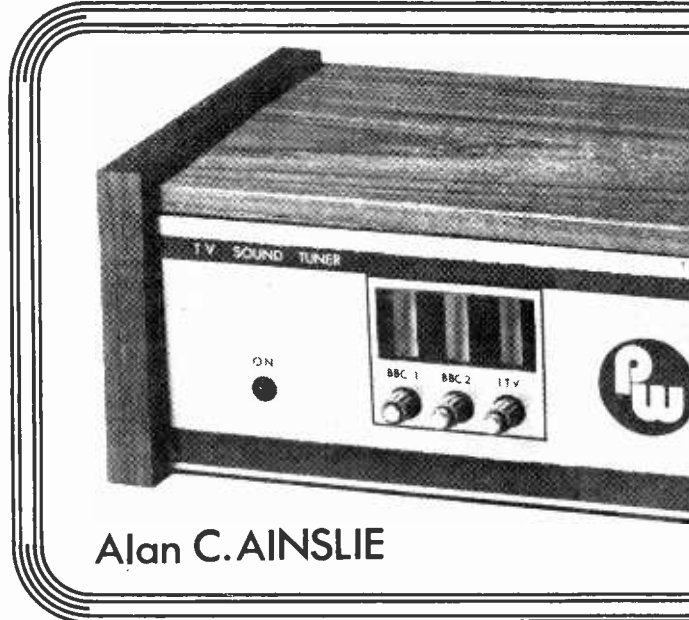The IF amplification and associated bandwidth shaping is performed in two Philips G8 colour receiver modules employing four transistors. The vision detector is included in the second module, giving video and 6MHz sound carrier at its output.



Alan C. AINSLIE

A 6MHz ceramic filter is used as a simple bandpass filter to remove the video and shape the characteristics of the following 6MHz amplifier.

Amplification at 6MHz is carried out in the TAA570 (or similar) IC, which also performs quadrature FM demodulation using only a single tuned circuit.

Fig. 2 shows the circuit diagram of the PW Sound Tuner.

The volume control is connected directly to the sub-assembly audio output and feeds Tr2, which is a simple emitter follower, to ensure that the TV Sound Tuner has a low output impedance. This enables long lengths of screened cable to be used on the output without any significant loss of treble.

The varicap tuner used in the prototype is the Mullard ELC1043, commonly used in contemporary


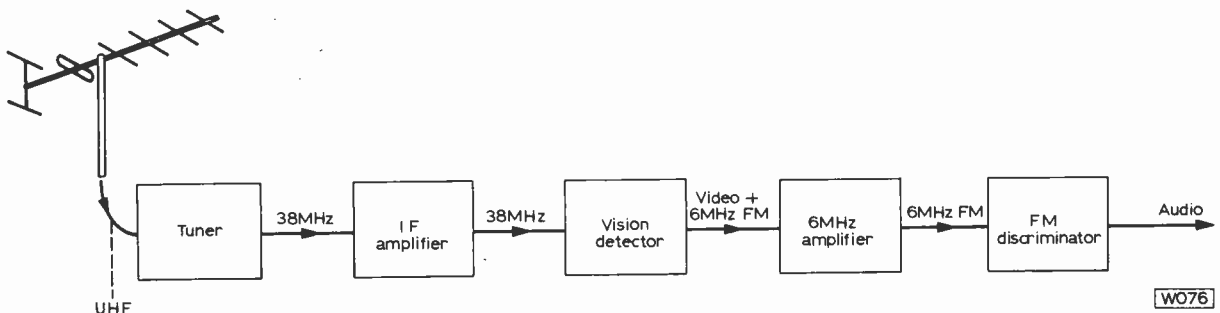


Fig. 1: Block diagram of the sound section of a TV receiver.

WO76

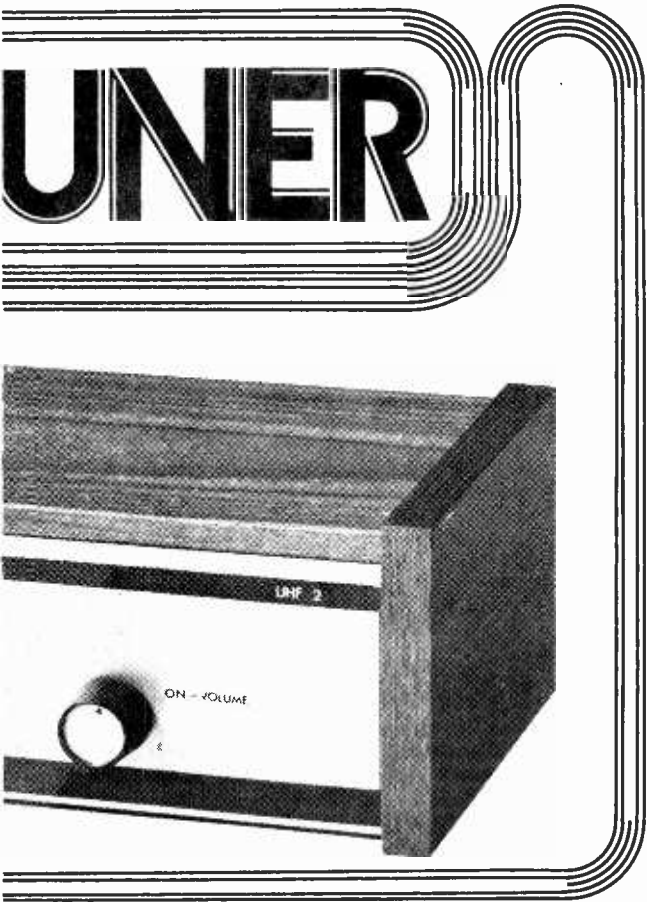

receivers and available at reasonable prices through surplus channels.

The ELC1043 has facilities for AGC but as it is not required in this unit, a potential divider, consisting of R10 and R9 connected across the supply, is used to bias the AGC terminal for optimum gain.

Power for the RF stages and oscillator is taken directly from the 12V supply to the sub-assembly.

To tune the ELC1043, a DC voltage variable between 0.3V and 30V is applied to the "tuning" terminal. This covers channels 21 to 68 for UHF reception. To achieve the necessary tuning resolution, multi-turn pots have to be used, in this case being neatly combined with the channel selection buttons in a commercial varicap push button control unit. These are available to give three, four, five or six preset channels and consist of the requisite number of preset pots connected across a stable 30V supply, with each wiper being selected by a push button and connected to the "tuning" terminal on the ELC1043. A small capacitor (C11) is used to remove any noise introduced by the tuning pots.

The IF output of the tuner feeds directly through a 1000pF capacitor into the first G8 module on the sub-assembly.

POWER SUPPLY

The mains transformer used in this project has two secondaries, one of 40V to feed the varicap diodes, and one of 12V for the IF sub-assembly, tuner and output emitter follower. The complete circuit of the power supply is shown in Fig. 2.

The 12V supply (actually adjusted to 11.5V) is obtained by full wave rectifying 12V AC from the transformer in a bridge made from D4 to D7, and smoothing with C4. Voltage regulation is necessary to prevent oscillator drift in the front end and is performed by IC2, a μ A550 regulator package.

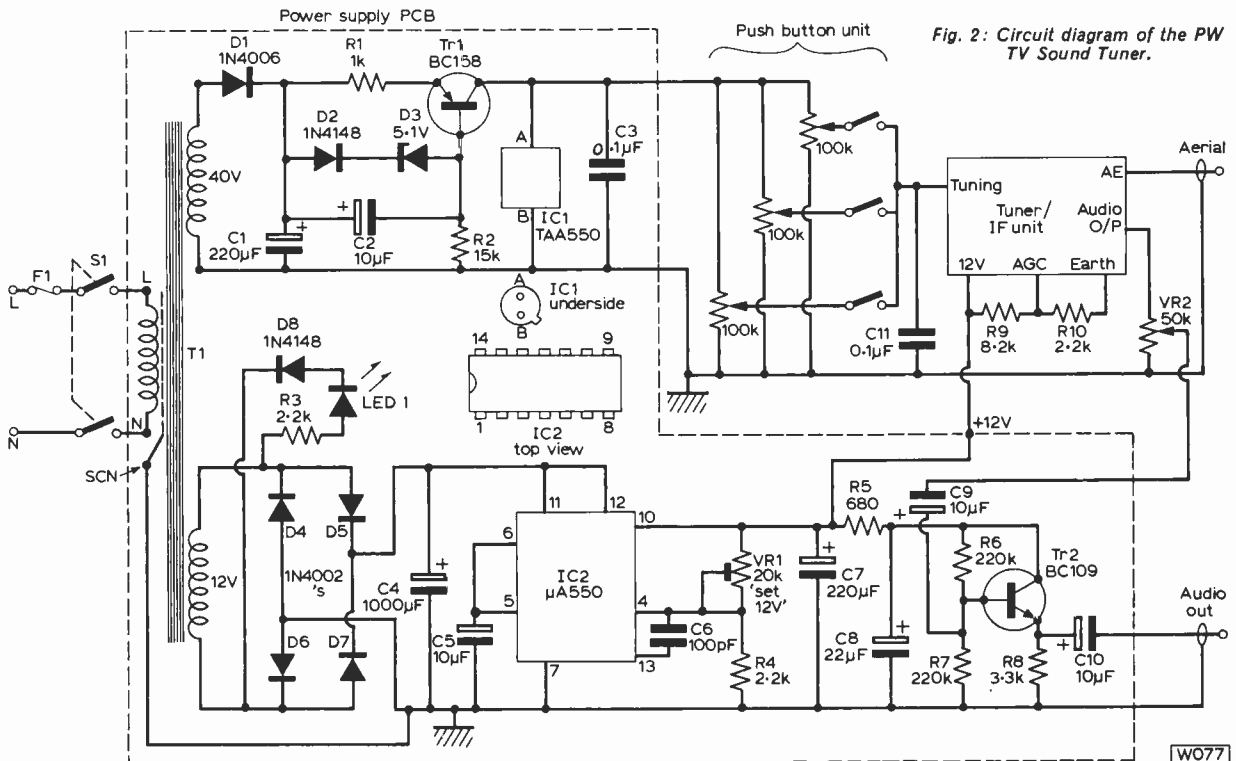


Fig. 2: Circuit diagram of the PW TV Sound Tuner.

This device works by comparing a reference of 1.63V produced at pin 6 with a fraction of the output voltage on pin 10, determined by R4 and VR1. Pin 4, connected to the junction of R4/VR1, is the inverting input to the comparison amplifier and pin 5 is the non-inverting input (connected directly to the reference).

The regulator acts to maintain the voltage on pins 4 and 5 equal, ensuring that the output is constant. VR1 is variable so that the required 11.5V output may be precisely set.

Capacitor C5 is included to smooth the reference while C6 is high frequency compensation, necessary for stability.

30V SUPPLY

A very high degree of stabilisation is required for the 30V supply as a few tens of millivolts change would cause appreciable detuning. Conventionally, a TAA550 IC regulator is used to stabilise the varicap diode supply in receivers. This is a two terminal device which is connected as a Zener diode, but which has very good temperature stability.

Continuing the analogy with a Zener diode, the dynamic resistance is quite low at around 10Ω but to make this resistance totally negligible compared to the source resistance a constant current source has been adopted in this design to ensure excellent tuning stability even with large mains voltage changes.


Transistor Tr1 in conjunction with Zener D3 and R1 forms a 5mA constant current source, with temperature compensation of Tr1 V_{be} provided by D2 (D3 with a Zener voltage of 5.1V would have a virtually zero temperature coefficient).

The varicap control unit is connected directly across the TAA550 and drains little current as each tuning pot is 100Ω. However, should a five or six button unit be used, R1 should be reduced to 820Ω to maintain an optimum 5mA in IC1.

On-Off indication of the tuner is provided by LED1 mounted on the front panel. R3 serves as a current limiting resistor while D8 is included as reverse voltage protection.

CONSTRUCTION

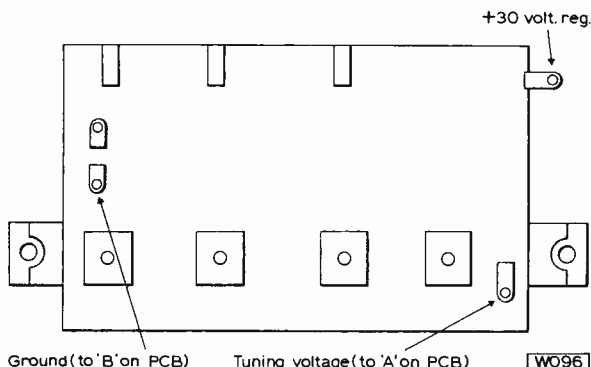The IF sub-assembly is purchased fully assembled and aligned so there is no work to do in this area. Both the ELC1043 and a three button unit will mount directly on one end of the PCB which has all the necessary printed wiring on the foil side.



The push button unit is supported by two 38mm 6BA bolts passing through the board and held captive between two units on each bolt. By adjusting these units, the buttons can be made to coincide with the cut-outs in the front panel.

A four station control unit can be accommodated on the PCB but an additional hole would have to be drilled. Larger units would have to be mounted directly on the chassis and the dimensions adjusted accordingly.

The connections for the push button units are shown in Fig. 3.

Before soldering the ELC1043 to the board, R10, R9 and C11, which mount under the tuner, must be soldered in place. R10 is on the copper side of the board and, to ensure that it does not short to the chassis, should be completely covered by a 25mm length of 5mm plastic sleeving.

POWER SUPPLY BOARD

Both the 12V and 30V supplies and the output emitter follower are constructed on a single PCB, the layout of which is shown in Fig. 4.

Constructors who prefer to make their own boards should have no difficulty, the only point to watch being the spacing of the pads for IC2 (0.1in apart, rows spaced 0.3in). As an alternative, fully prepared boards will be made available—details in the component list.

Five mounting holes are drilled in the board, one at each corner and one adjacent to the transformer to prevent the board sagging.

The transformer has two 6BA mounting lugs and when soldered in position, two corresponding holes should be drilled in the PCB and the transformer secured with a couple of short bolts.

Assembly of the board is quite straightforward, with particular care being taken with the orientation of electrolytics, diodes, ICs and transistors.

METALWORK

The complete TV Sound Tuner is mounted in a 'U' shaped aluminium chassis with holes for the mains lead, panel mounting mains fuse, output lead and aerial socket on the back panel. The front of the chassis is masked by a front panel, secured with the pot nut on the volume control.

Fig. 5 shows the metalwork for the chassis and front panel. To absorb any tolerances the PCB should be marked from the actual boards held in situ.

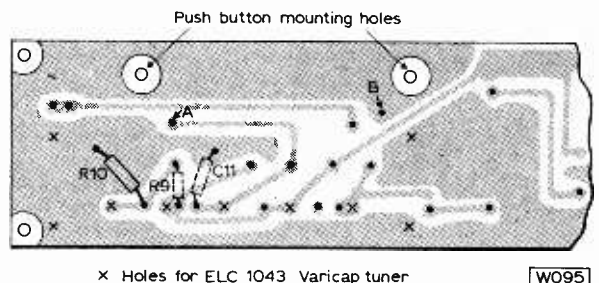


Fig. 3: Connections for the pushbutton tuner unit (left) and details of the mounting of the Mullard ELC1043 tuner on the PCB (above).

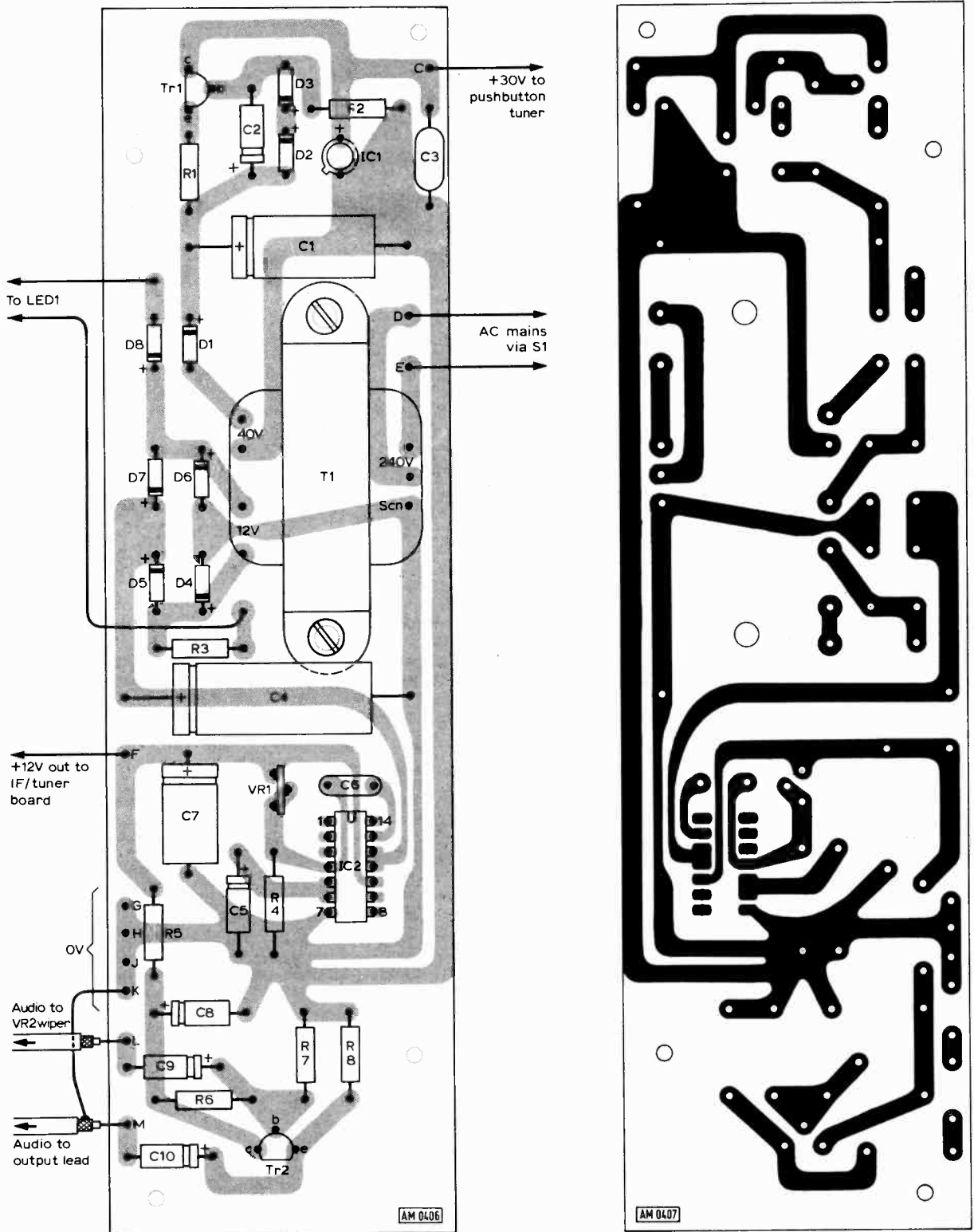


Fig. 4: Layout of the components on the power supply printed circuit board (left) and full size printed circuit master (right).

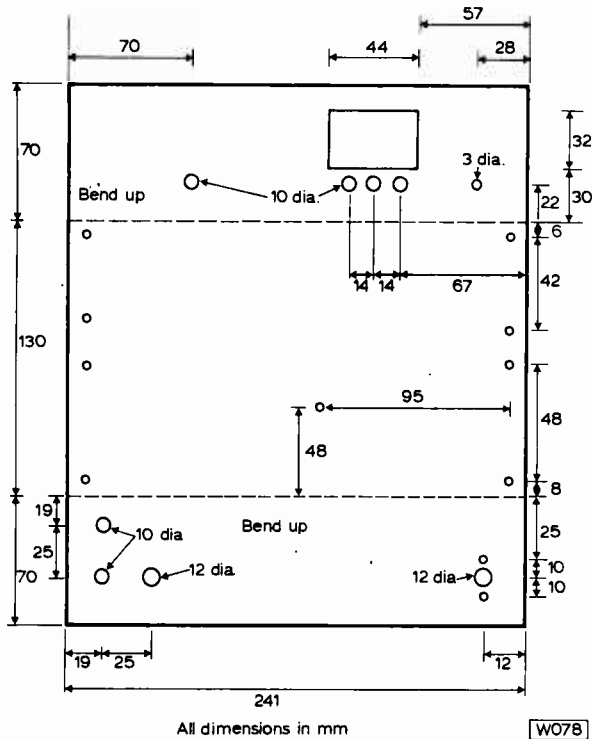


Fig. 5: Drilling details for the chassis (top) and front panel (bottom). Materials can be 18 s.w.g. aluminium.

The two PCB's are supported by 6mm stand-off collars on 6BA bolts. These collars make contact between the earth plane of the IF panel and the chassis, so the screws must be tight, with shakeproof washers used between the collars and the PCB.

VOLUME CONTROL MOUNTING

The ganged volume on-off control is mounted in the hole provided on the front panel which coincides with a clear area of the IF board. Providing that the control is physically small it will fit in without any trouble.

Mains wiring to the control will pass directly over the 6MHz ceramic filter which is very susceptible to RF pickup. To reduce the possibility of interference, a small tinfoil shield is soldered to the mounting clip of the second G8 module, to cover the filter and associated components. The photograph shows the details.

★ components list

Resistors (All 1/2W)

- R1 1k Ω (820 Ω if 5 or 6 button unit is used)
- R2 15k Ω
- R3 2.2k Ω
- R4 2.2k Ω
- R5 680 Ω
- R6 220k Ω
- R7 220k Ω
- R8 3.3k Ω
- R9 8.2k Ω
- R10 2.2k Ω
- VR1 20k Ω skeleton preset
- VR2 50k Ω log pot with d.p.d.f. switch (S1)

Capacitors

- C1 220 μ F 63V elect
- C2 10 μ F 25V elect
- C3 0.1 μ F polyester
- C4 1000 μ F 16V elect
- C5 10 μ F 25V elect
- C6 100pF ceramic
- C7 220 μ F 16V elect
- C8 22 μ F 25V elect
- C9 10 μ F 10V elect
- C10 10 μ F 10V elect
- C11 0.1 μ F polyester

Semiconductors

- T1 BC158
- T2 BC109
- D1 1N4006
- D2 1N4148
- D3 5.1V 400mW Zener
- D4-D7 1N4002 (4 off)
- D8 1N 4148
- IC1 TAA550
- IC2 μ A550 (NE550A)
- LED1 TIL209


Miscellaneous

- T1 Type M1103
- IF Sub-Assembly
- Mullard ELC1043 varicap tuner (or ELC1042 for VHF) *
- Pushbutton control unit (100k per section)
- S1 Double pole mains switch (ganged with VR2)
- F1 500mA fuse and panel mounting holder
- Sk1 Coaxial aerial socket
- Screened audio output lead, mains lead, PCB for PSU, chassis, cabinet, front panel, knob.

The transformer is available from Monty Enterprises, 2 Silver St., Doncaster, price £3.95 + VAT. A wooden box is available from Birch & Ridley, Watson Road, Worksop, price £2.25 + VAT + 50p postage and packing. The metal chassis and front panel can be obtained from Richard Friday Ltd., Old Coach House, Greystone Yd., Moorgate, Rotherham, Yorks, price £5.65 + VAT + 35p postage and packing. The IF Sub-assembly, ELC1043 tuner, and pushbutton unit are all available from Manor Supplies, 172 West End Lane, London NW6, price £6.80 + 45p, £4.20 + 30p and £1.20 + 25p respectively. If all three are purchased p & p is 50p.

WIRING


To avoid earth loops and the attendant difficulties it is important that the only ground connection between the PCB's is that made as part of the power supply wiring. Screened leads should be used for the signal wiring from the IF board to the volume control and from the volume control to the PSU board (input to emitter follower) but the screen of the lead should be cut short and not connected to the PSU panel.

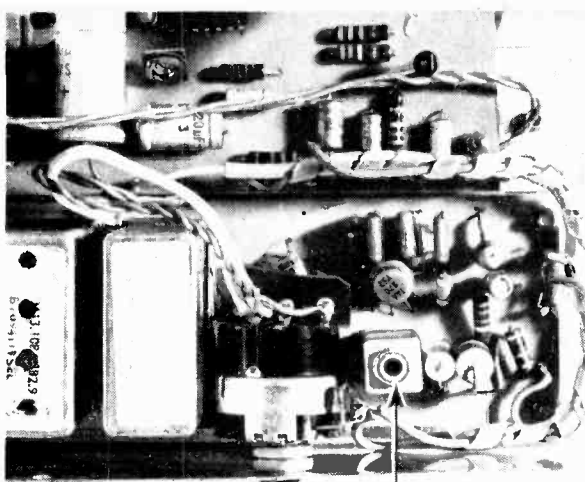

Quadrature Coil

AM0405

Fig. 6: Position of the quadrature coil which may need adjusting. A photograph of the completed unit is shown right. Note the small metal shield between the volume control and the board.

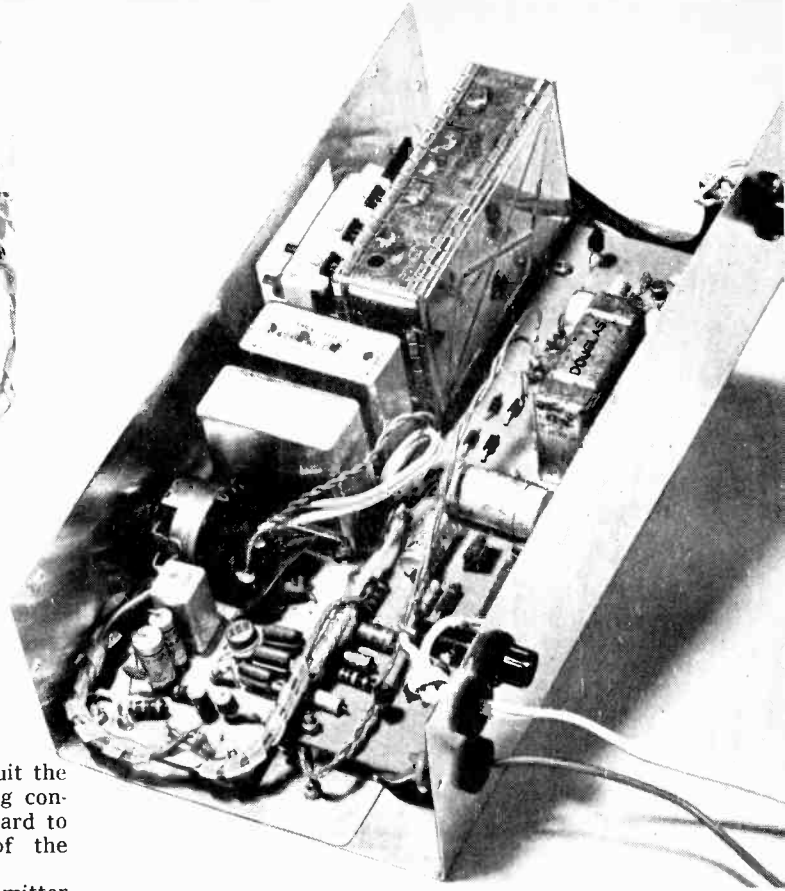

The screened output lead (with a plug to suit the hi-fi system on the other end) has its braiding connected to the ground terminal of the PSU board to maintain earth continuity with the rest of the equipment.

To keep the mains wiring away from the emitter follower, the switch leads pass between the two panels and under the PSU board near the mains transformer.

By using a transformer isolated supply, no 'live chassis' hazards exist and the aerial connection can be made directly to the aerial terminal on the end of the ELC1043. On most units an earth braiding connection has to be made by soldering directly to the tuner case adjacent to the 'aerial' connector.

FRONT PANEL

The front panel for the prototype was sprayed with car 'touch up' paint and lettering and lines applied using Letraset. A final spray of clear polyurethane protects the lettering from fingermarks and abrasions.

The window for the tuning indicators on the control unit was made from a piece of 6mm clear Perspex carefully filed to size and affixed with a couple of dabs of epoxy cement. A waterproof felt tip pen was then used to mark the window area for each button.

Assembly of a wooden case depends on the facilities available and the skill of the constructor. As a guide, the case for prototype is a simple 'hood' made from veneered plywood. The front panel, of course, covers any screws that may be used to hold the chassis in the cabinet.

SETTING UP

After a thorough check of all wiring, component values, etc., VRI is set to minimum resistance and power applied. By increasing VRI it should be possible to set the supply rail to exactly 11.5V.

No adjustment is possible on the tuning diode supply but it is as well to check that the voltage is of the right order.

Plugging the output lead into an amplifier and turning up the volume should give a high level of hiss, with possibly a couple of foreign radio stations as well. Plugging in an aerial and adjusting the tuning controls should give the local region TV stations loud and clear.

Channel numbers are not marked on the push button units but the pointer at the bottom indicates channels at the low end of the UHF band. The three regional stations are always grouped together with BBC1 being the lowest channel number, ITV next, then BBC2.

Tuning will be a little difficult at first without the picture to help. For each station, several tuning points will be apparent, close to each other. The correct one will be towards the higher channel number end of the group, just before a region of 'vision buzz'.

When tuning has been mastered any remaining buzz can be carefully taken out by tuning the quadrature coil (see Fig. 6) with the CORRECT TRIMMING TOOL. No more than one turn adjustment should be needed as it is merely to compensate for the capacitance of the metal chassis, etc. No other tuned circuits (i.e. those in the front end or G8 units) should be touched as specialist gear is needed to set them up again.

The Sound Tuner is very sensitive and, while it would be silly to expect good results from the proverbial "piece of wire", a weak signal (such as would produce a quite noisy black and white picture and very poor colour) would be sufficient. This means that a splitter in the main receiver TV co-ax will furnish plenty of signal or alternatively a second small aerial could be installed.

The Sinclair DM2 Multimeter.

Comprehensive. Accurate. Portable.

And really rugged.

Yet only £59. (PLUS VAT)



State-of-the-art circuit design, incorporating high-quality components, has resulted in a professional, $3\frac{1}{2}$ digit instrument of outstanding performance and reliability at a realistic price.

A custom-designed MOS LSI digital processing IC controls the auto-polarity dual-slope-integration A to D converter. The circuit built around this IC uses a MOSFET op-amp input buffer with 0.1% metal-film resistors. The result is excellent accuracy and stability with a very high basic input impedance.

The instrument reads to ± 1999 and has a basic accuracy on the 1 V DC range of $0.3\% \pm 1$ digit. Four 8 mm LED displays provide excellent legibility and angle of view. Battery operation allows complete independence of mains supply.

The Sinclair DM2 has all the capability you need. Just take a look at its features and compare them with higher-priced multimeters. You'll find the DM2 is their equal in virtually everything – except price!

Features of the Sinclair DM2

5 functions giving 22 ranges

DC volts – 1 mV to 1000 V
 AC volts – 1 mV to 500 V
 DC current – 0.1 μ A to 1 A
 AC current – 1 μ A to 1 A
 Resistance – 1 Ω to 20 M Ω

Easy to use

Automatic polarity, push-button selection for all ranges and modes from a single input terminal pair.

Easy to read

Big, bright 8 mm LED display gives a quick, clear reading.

$3\frac{1}{2}$ digit display

Display reads from 000 to 1999. Overload indicator.

Protected

Separate fuses for current and resistance circuits.

Accurate

Dual slope integration. High stability.

Rugged construction

Tough metal casing takes the roughest treatment – try standing on it!

Two power sources

Supplied with a 9 V battery, giving 60-hour typical life. Mains adaptor also available.


Portable

Weighs only 3 lb approx, including battery. Measures only 2 in x 9 in x 6 in approx.

Optional extras

Mains adaptor – £3.19 inc VAT.
 Carrying case – £5.40 inc VAT.
 12-month no-quibble guarantee

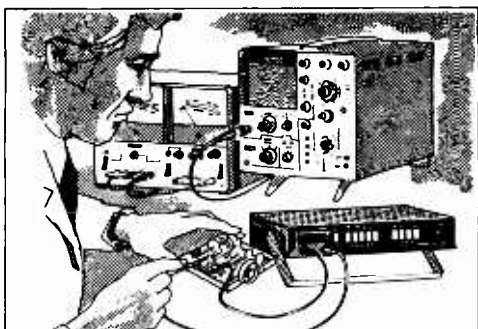
The Sinclair DM2 Multimeter: full technical story



Use it in your laboratory. The DM2 sits rigidly on its combined carrying handle/stand.



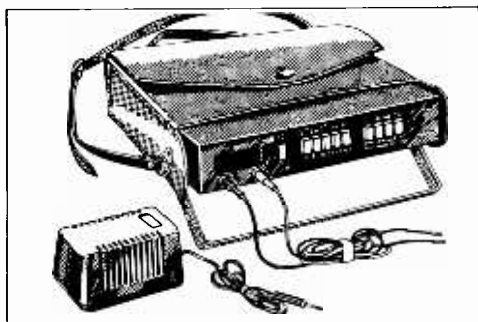Use it on the move. Keep the DM2 in its carrying case - it's always ready for use.



All you need to use the DM2... anywhere. Mains adaptor... carrying case... multimeter... you're ready for quick, efficient metering - whatever the situation.

Take advantage of this money-back, no-risk offer today

Test the Sinclair DM2 for yourself. Simply send us a cheque, your Access/Barclaycard number, or an official company order, with the coupon below. And in the unlikely event you find it's not what you need, return it to us within 10 days and we'll refund your money in full.

Interested in a quantity discount? Use the coupon to arrange a demonstration and get details of prices on 5 or more instruments.

Sinclair Radionics Ltd,
London Road, St Ives, Huntingdon,
Cambs., PE17 4HJ.

Tel: St Ives (0480) 64646.

VAT Registration No: 213 8170 88.

sinclair

Practical Wireless, November 1975

DC Volts Range	Accuracy	Input Impedance	Resolution
1 V	0.3% ± 1 Digit	> 100 MΩ	1 mV
10 V	0.5% ± 1 "	10 MΩ	10 mV
100 V	0.5% ± 1 "	10 MΩ	100 mV
1000 V	0.5% ± 1 "	10 MΩ	1 V

Maximum overload - 350 V on 1 V range
1000 V on all other ranges.

AC Volts Range	Accuracy	Input Impedance	Frequency Range
1 V	1.0% ± 2 Digits	10 MΩ/40 pF	20 Hz-3 KHz
10 V	1.0% ± 2 "	10 MΩ/40 pF	20 Hz-3 KHz
100 V	2.0% ± 2 "	10 MΩ/40 pF	20 Hz-3 KHz
1000 V	2.0% ± 2 "	10 MΩ/40 pF	20 Hz-1 KHz

Maximum overload - 300 V on 1 V range
500 V on all other ranges.

DC Current Range	Accuracy	Input Impedance	Resolution
100 μA	2.0% ± 1 Digit	10 KΩ	100 nA
1 mA	0.8% ± 1 "	1 KΩ	1 μA
10 mA	0.8% ± 1 "	100 Ω	10 μA
100 mA	0.8% ± 1 "	10 Ω	100 μA
1000 mA	2.0% ± 1 "	1 Ω	1 mA

Maximum overload - 1 A (fused).

AC Current Range	Accuracy	Frequency Range
1 mA	1.5% ± 2 Digits	20 Hz-1 KHz
10 mA	1.5% ± 2 "	20 Hz-1 KHz
100 mA	1.5% ± 2 "	20 Hz-1 KHz
1000 mA	2.0% ± 2 "	20 Hz-1 KHz

Maximum overload - 1 A (fused).

Resistance Range	Accuracy	Measuring Current
1 KΩ	1.0% ± 1 Digit	1 mA
10 KΩ	1.0% ± 1 "	100 μA
100 KΩ	1.0% ± 1 "	10 μA
1000 KΩ	1.0% ± 1 "	1 μA
10 MΩ	2.0% ± 1 "	100 nA

Overload protection - 50 mA (fused).

Readers outside the UK, please write for details of your local distributor to:

Sinclair Equipment International Ltd,
33 Beauchamp Place, London SW1 1NU.

To: Sinclair Radionics Ltd, FREEPOST, St Ives,
Huntingdon, Cambs., PE17 4BR.

Please send me:

..... Multimeters @ £63.72
inc VAT.
..... Mains adaptors @ £3.19
inc VAT.
..... Carrying cases @ £5.40
inc VAT.

*I enclose a cheque for £

*My Access/Barclaycard
number:

I am interested in 5 or more
multimeters.

..... Please arrange a
demonstration.
..... Please send details of
quantity discounts.

*I enclose an official company
order - signed and dated.

*Please complete or delete as
applicable.

Name

Address

Please print

FREEPOST - no stamp needed with address above. PW1 J

AUDIO '75 HARROGATE

MORE than 74 exhibiting firms with over 120 trade names filled the hotels Majestic and Cairn at Harrogate this year, when Audio 75 was held from August 29th to 31st.

To report on every item seen and to mention every firm would fill half-a-dozen issues of Practical Wireless, so we have chosen a few which we think will particularly interest our readers.

Alba

Alba exhibited a portable radiogram, Model 3200. It employs a 2-speed player and an a.m. radio and operates from 6×HP2 batteries or from the mains. Also on show was their UA 8080D teak-finished 3-piece suite with a 3-band tuner, stereo 3W per channel amplifier and a BSR autochanger.

Model UA 9070D is a music centre comprising a.m./f.m. tuner, 2×8W amplifier, BSR changer and a cassette recorder—all in a teak cabinet with matching speakers.

Bang & Olufsen UK Ltd

Beocentres 1400 and 1800 were shown along with an impressive range of assorted equipment styled in the unique B & O way.

The 1400 has a stereo, a.m./f.m. radio, 20W per channel amplifier and a built-in cassette recorder. Price in teak, £249·50. The 1800 model has a similar

specification but features an automatic record player instead of a recorder.

Amongst the range of Beogram record decks on show was the very sophisticated Beogram 6000 electronically controlled 4-channel deck with built-in CD4 decoder and MMC 6000 cartridge. Price is £387·90 but you do get a free copy of Mahler's 5th Symphony recorded in CD4 thrown in!

BASF UK Ltd

This firm was showing at Harrogate for the first time and exhibited their comprehensive range of reel-to-reel tapes and cassettes with a special display on the recently released 'LH Super Range'. With LH tape, the principle is as follows:

The magnetic particles of normal ferric oxide tape are comparatively large and irregularly shaped. Apart from increasing the noise level, this also reduces the sensitivity of cassettes at high frequencies, where the shorter wavelengths approach the length of the particles, because of the slow running speed.


A Low Noise tape overcomes this by using smaller particles. LH Tape (Low noise/High output, invented by BASF in 1967) also uses smaller particles, but at a much greater density, giving a higher output on playback. LH Super is a very recent breakthrough in ferric oxide tapes from BASF. It extends the LH principle by using a new high density coating process and the smaller and more evenly sized particles of Maghemite (the mineralogical name for specially processed gamma Fe_2O_3 oxide).

The result is a full 50 per cent increase in sound quality. This can be seen by recording at OVU level, where the harmonic distortion is just 2·5 per cent—half the figure set by the DIN standard.


Even compared to BASF LH tape, LH Super is said to give a 3dB increase in recording level and over 2dB less tape hiss. Also seen were the automatic switching CrO_2 cassette machines—the Compact CC9110 at £35, the CC902 (£65) and the CC9302 with mixing facilities and a four-band receiver, priced at £90. Cassette decks on show were the 8200 (£180) and the 8100 at £120. See details of the BASF special offer in our News . . . pages.

Bib Hi-Fi accessories

Bib, as is usual at this type of exhibition had their full range of Hi-Fi accessories on show. Of particular interest was the new cassette storage unit Ref 86 which holds 30 cassettes in their containers. Fitted with a tinted acrylic hinged lid, the base of the unit comes in a simulated teak effect and the whole cabinet measures 15in×4 $\frac{1}{4}$ ×10 $\frac{1}{2}$ in wide. Price is £6·60 excluding VAT.

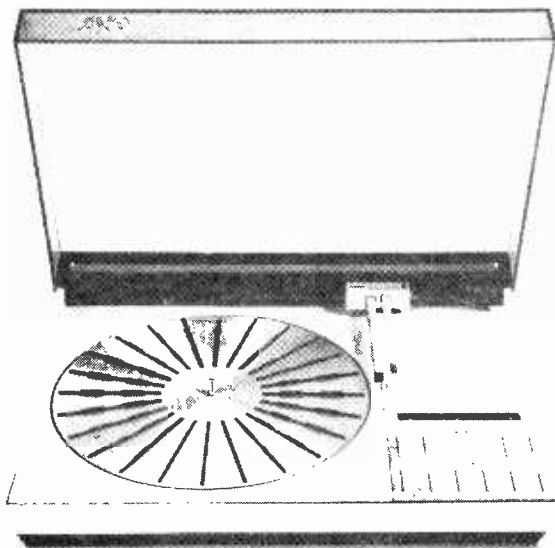

Bang and Olufsen's 6000 model.

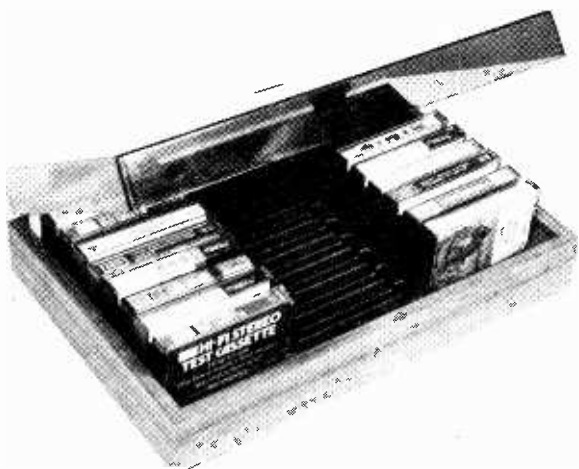

Bib's new cassette storage unit.



Some of the Eagle equipment on display.

The 2004 amplifier is rated at 20W per channel. It has a facility for two extra speakers to give simulated quad. The 2006 has a similar spec. with the addition of 'sound effects controllers'. The A2004 costs £65 and the A2006, £85.

Eagle were also exhibiting equipment under the Beltek name and had their M1150 Dolbyised stereo cassette deck priced at £158 on show. Also there was the M1130 deck which was very similar but did not have the Dolby feature.

Fidelity Radio Ltd

The Fidelity range included the UA4 budget stereo system priced at £48.60. Features are a two-speed record deck, 5W per channel amplifier and two white-finish speakers. The UA7 priced at £65.40 uses a BSR three speed record deck. The UA3 system is very similar in styling and priced at £87.96 with BSR changer, 2x4W sine wave amplifier and a.m./f.m. tuner.

One of the latest additions to the range is the UA6 system at £144.68. This comprises Garrard SP25 single play record deck with magnetic cartridge; 10W per channel amplifier, a.m./f.m. stereo radio tuner. A tape socket and a socket for stereo headphones are provided. Top of the range is the MC2 Music Centre with BSR record changer, a.m./f.m. stereo radio, stereo cassette recorder/player, 2x4W amplifier. Storage is provided for cassettes.

GEC (Radio & Television) Ltd

Music Centre Model 2917 has a.m./f.m. stereo radio, stereo cassette recorder/player and Garrard 6300 auto/manual 3-speed record player. The amplifier is rated at 10W per channel and provision is made for "ambio" sound. Price: £242.75. At £234.09 comes model 2919. It uses Garrard SP25 single play record deck; 4-band tuner with decoder fitted; and has a 15W per channel amplifier with provision for ambio sound. In teak, with matching speakers.

Top of the range is the model 2820, £271.21. Features include: 20W per channel amplifier with ambio facility; f.m. stereo radio tuner with electronic touch tuning, calibrated tuning meter, and interstation quieting; Garrard 86SB single play record deck with Shure magnetic cartridge.

Model 2821 is a combined 4-band stereo radio with BSR C141R record deck and 2x7W amplifier, two speakers, it is priced at £121.66. Model 2816. (£147.72) has 4-band radio with BSR P128R record deck and a 15W per channel amplifier.



The BDS 90 deck from BSR.

Eagle International Ltd

On show for the first time to the general public was the 2000 range, including the A2004 and A2006 amplifiers, turntables D2005 and D2006, headphones type H2008 and H2009, tuner T2008 and the S2002, 2003, 2004, 2005 and 2006 range of speakers.



The Goldring L65 deck.

Goldring

Model L65—the latest addition to the Goldring Lenco range was shown. Particular items of interest are the automatic functions of the tonearm, the viscously damped suspension and the anti-skating device which with separate scales is adjustable for elliptical and spherical styli.

Other items in the specification are:

Speed: 33 $\frac{1}{3}$ and 45 r.p.m. Wow and flutter weighted according to DIN 45507: <+/-0,12% Rumble unweighted according to DIN 45539: >38 dB Rumble weighted according to DIN 45539: >57 dB.

Turntable: Dia. 300 mm Weight 1.4 kg.

Tonearm: With a super light weight aluminium headshell suitable for use with all international standard cartridges. Stylus pressure adjustable 0.5 gm.

Mains voltage: 110V/60Hz, 220V/50Hz Power Consumption: Approximately 2.5 VA.

Measurements: Chassis 405 x 300 x 2 mm. Depth required below chassis 54 mm. With plinth and dust cover 426 x 321 x 148 mm.

Weight: With plinth and dust cover 6.75 kg, and packing 8.6 kg.

The Goldring Lenco ST800 compact stereo system was also on show. Incorporating the GL78 transcription unit, fitted with a G800E cartridge, it has an f.m. tuner fitted with three pre-set station buttons. Output is 40W per channel and slider controls are provided for volume, bass, treble and balance.

Also shown was the Goldring range of stereo magnetic cartridges—including the easily replaceable stylus system types 820 and 800 series.

JVC (UK) Ltd

JVC model 1845 shown on the stand features a 3-band a.m./f.m. tuner with 2 x 15W rms amplifier, front loading cassette deck with CrO₂ facility and noise suppressor. This comes with a belt-drive transcription turntable with magnetic cartridge. The tuner is fitted with tuning meter and loudness control. Price, including speakers, is £280 plus VAT.

Model MC-1820L features a stereo cassette deck of the same design as the company's more expensive ANRS decks, plus an a.m./f.m. stereo tuner 16W per channel amplifier all housed in low profile cabinet. Price, exclusive of speakers, is £145 plus VAT.

JVC have developed a new I.C. for their ANRS (Automatic Noise Reduction System). It is said to improve both performance and reliability and lower

the cost of incorporating ANRS in existing equipment.

Compactness is the keynote of the new ANRS circuit now and the relatively few external components used in the unit allows the whole p.c. assembly to occupy half the area previously taken up.

Philips Electrical Ltd

The Philips range on show was so vast that we can only mention a few items of their equipment.

Model RH734 tuner-amplifier covers a.m./f.m. bands and has a 30W per channel output. Price is £207.18. The RH732 tuner-amp has a similar radio specification but a 12W per channel output. It sells at £172.45. A matching record deck for either unit is the new GA427 belt-drive model fitted with a GP400 magnetic cartridge. Price is £62.50.

Another recent addition to the Philips range is the RH741 4-band tuner with a 15W per channel amplifier. An interesting feature of this model is the visual indication on scales for bass and treble response. Price is £167.83.

The GF907 record playing system is in a crackle black and silver finish (something different anyway!) The deck employs the GC007 belt-drive turntable fitted with a GP400 cartridge. The amplifier is rated at 15W per channel output and the price is quoted as £184.61.

Top of the range of music centres is the new RH832 priced at £781.25. The spec. includes: 4-channel pre-amplifier with built-in SQ decoder and connection for CD4 demodulator; 2-speed electronically controlled record playing deck with GP422 magneto-dynamic cartridge; a.m./f.m. tuner equipped for stereo f.m. and 4-channel (SQ) transmissions.

Pye Ltd

Pye's Sound Project ZU440 record player/f.m. radio/cassette recorder was on show. It features 'disc jockey' mixing. The cassette unit has DNL (Dynamic Noise Limiter) and the amplifier delivers 15W per channel. The tuner has decoder fitted. Price, including two 2-unit speakers and mono microphone, £364.88.

ZU540 combines f.m. tuner with stereo beacon and four station push buttons; transcription type 2-speed record deck; cassette recorder with Dolby system and CrO₂/Fe₂O₃ automatic sensing. The amplifier is rated at 2 x 20W. The speaker assemblies use a bass/mid range unit with a line tweeter. Price is £475.48.



Sound Project ZU540 from Pye/Ekco.

SUPERSOUND 13 HI-FI MONO AMPLIFIER

A superb solid state audio amplifier. Brand new component-throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz 30KHz \pm 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/2" deep. AC 200/250V. PRICE £16 00. P. & P. 65p.

DE LUXE STEREO AMPLIFIER

A.C. mains 200-240 v. 10" x 8 1/2" x 4 1/2" heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line-up: 2 x ECL86 Triode Pentodes, 1 x E240 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully controlled circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" x 4" d. Overall height including valves 5". Ready built & tested to a high standard. £12.50. P. & P. 85p.

ALL-PURPOSE POWER SUPPLY UNIT 200/240V. A.C. input. Four switched fully smoothed D.C. outputs giving 6v. and 7 1/2v. and 9v. and 12v. at 1 amp on load. Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case overall size 6" x 3 1/2" x 2 1/2". Ready built and tested. PRICE £6.35 P. & P. 55p.

VYNAIR & REXINE SPEAKERS & CABINET FABRICS per yd. 34 in. wide. Our price £1.30 yd. length. P. & P. 30p per yd. (min. 1 yd. S.E. for samples).

HARVERSON'S SUPER MONO AMPLIFIER
A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7 1/2" wide x 3 1/2" deep x 6 1/2" high overall. AC mains 200/240V. Supplied absolutely Brand New completely wired and tested with good quality output transformer. £5.00 P. & P. 60p BARGAIN PRICE

FEW ONLY!
High grade mains transformer with grain orientated lamination. Primary 200/240 Secondary 18.5 volts at 0.6 amps and 4.6 volts at 0.3 amps. Size 2 1/2" x 1 1/2" x 2 1/2" d overall. £1.40 plus 35p P. & P.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240v. Secondary combinations 0-5-10-15-20-25-30-35-40-50v. half wave at 1 amp. or 10-0-10. 20-0-20. 30-0-30v. at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 8in. deep. Price £2.75 P. & P. 65p.

MAINS TRANSFORMER. For power supplies. Pri. 200/240v. Sec. 9-0-9 at 500 mA. £1.35. P. & P. 30p. Pri. 200/240v. Sec. 12-0-12 at 1 amp. £1.50. P. & P. 30p. Pri. 200/240v. Sec. 10-0-10 at 2 amp. £2.20. P. & P. 40p.

3 VOLT RELAY
100 mA/4 single pole normally closed. 2 for 60p + 15p P. & P.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER
For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 26dB. 8-lead encapsulation size 1 1/2" x 1 1/2" x 1". Brand new complete with instructions. Price 1.86p. P. & P. 15p.

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES
A must for servicemen and home constructors. Including many 1000's of British, U.S.A. European and Japanese transistors. ONLY 40p. Post 7p.

Reference Encyclopedias for Electronic Engineers and Designers, covering between them many thousands of valves, diode and transistor equivalents. Many thousands of us to date European types listed.
Diode Equivalents. £1.00; Transistor Equivalents. £1.20; Transistor Characteristics. £1.40; POST FREE All three together. £3.20

NEW ISSUE
Thyristor, Triac, Diac etc. encyclopedias £1.70. Post Free 8 pole 3 way 2 bank low loss Vaxley type switches 11" sections. Standard spindle. 2 switches 75p + 15p P. & P.

Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday Closed Wednesday.
All prices and specifications correct at time of press and subject to alteration without notice.

HARVERSONIC MAINS OPERATED SOLID STATE STEREO FM TUNER



Enjoy fabulous stereo radio at this fabulous low introductory price!

Designed and styled to match our 10 + 10 amplifier but will suit any other standard stereo amplifier. The design incorporates the very latest circuitry techniques with high-gain, low noise IF stages. Automatic frequency control to "lock-on" station and prevent drift. IC stereo decoder for maximum stereo separation. I.E.D. for stereo beacon indicator. Nominal output of tuner 100mV. Approximate size 12 1/2" wide x 8" deep by 2 1/2" high. Supplied ready built, fully tested and fully guaranteed (not available in kit form). Price £27.50 Post and Packing £1.00.

STEREO-DECODER
SIZE 2" x 3" x 1" ready built. Pre-aligned and tested. Sens. 20-600 mV for 9-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £6.25 plus 15p. P. & P. Stereo beacon light if required 45p extra.

SPECIAL BARGAIN OFFER!
Limited number of BSR C129/123 Auto Changer De Luxe with lightweight tubular arm and stereo cartridge. Brand new. ONLY £11.00 + p. & P. 60p.

LATEST HI SENSITIVITY Uni-directional slim-line condenser microphone as used by many professionals. Very low acoustic feedback. Available in impedance or low impedance. State which required. £16.25 plus 25p P. & P.

LATEST ACOS GP91/19C mono compatible cartridge with t/o stylus for LP/EP/78. Universal mounting bracket. £1.75. P. & P. 15p.

CERAMIC STEREO CARTRIDGE. Universal Mounting brackets and turnover stylus. 70mV per channel output. ONLY £2.06 + 15p P. & P.

SONOTONE STAEIC COMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78. ONLY £2.62 P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £3.18. P. & P. 15p. **LATEST CRYSTAL T/O STEREO/COMPATIBLE CARTRIDGE** for EP/LP/Stereo/78. £1.98 P. & P. 15p. **LATEST T/O MONO COMPATIBLE CARTRIDGE** for recording EP/LP/78 mono or stereo records on mono equipment. Only £1.75. P. & P. 15p.

QUALITY RECORD PLAYER AMPLIFIER MR. II
A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. wide x 3in. deep x 6in. high. Ready built and tested. £27.50. P. & P. 75p. **ALSO AVAILABLE** mounted on board with output transformer and speaker. PRICE £7.75. P. & P. 75p.

HI-FI LOUSPEAKER SYSTEM MK II

Beautifully made, simulated teak finish enclosure with attractive slatted front. Size 16 1/2" high x 10 1/2" wide x 9" deep (approx.). Fitted with E.M.I. Ceramic Magnet 1 1/2" x 8 1/2" bass unit, H.F. tweeter unit and crossover. AVAILABLE IN NOMINAL 4 Ohm, 8 Ohm or 16 Ohm impedance (state which). **OUR PRICE £11.25** each Carr. £1.25. Cabinet Available Separately £6.25, Carr. £1.10. Also available in 8 ohms with EMI 13" x 8" bass speaker with parasitic tweeter £10.00, Carr. £1.25.

LOUSPEAKER BARGAINS
5in. 3 ohm £1.45. P. & P. 15p. 7 x 4in. 3 ohm £1.60. P. & P. 25p. 10 x 6in. 3 or 15 ohm £2.50. P. & P. 35p. E.M.I. 8 x 5in. 8 ohm with high flux magnet £2.06. P. & P. 25p. E.M.I. 13" x 8in. with high flux ceramic magnet with parasitic tweeter 3, 8 or 15 ohm £4.12. P. & P. 35p. E.M.I. 13 x 8in. 3, 8 or 15 ohm with inbuilt tweeter and crossover network £5.50. P. & P. 35p. E.M.I. tweeter. Approx. 3 1/2". Available 3 or 8 or 15 ohms. £2.00 + 25p. P. & P.

BRAND NEW Bakers Loudspeakers at substantial discounts. 12in. 15w. H/D Speakers, 3, 8 or 15 ohms. State which. Current production by well-known British maker. Now with HiFlux ceramic ferrobar magnet assembly £9.50. Guitar models: 30w £8.95. 35w £10.50. P. & P. 75p.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER
Size 11 1/2" x 14 1/2" x 1 1/2" deep. Weight 19oz. Power handling 20W r.m.a. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £7.98 each. P. & P. 60p. **NOW ALSO AVAILABLE:** 8", 10 watts, r.m.s. 20 watt peak 40Hz-20,000Hz. Overall depth 1". Ideal for Hi-Fi or for use in cars. £5.18 + 40p P. & P.

HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT
A really first-class HI-FI Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise, level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metalwork high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification; Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response \pm 3dB 12-30,000 Hz Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: \pm 3dB 12-15,000 Hz. Bass boost approx. to \pm 12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 25v. at 1.0 amp. Overall Size 12" w. x 8" d. x 2 1/2" h.
Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S.A.E.

HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



AMPLIFIER KIT ... £15.00 P. & P. 60p (Magnetic input components 33p extra)
POWER PACK KIT ... £5.35 P. & P. 55p
CABINET ... £5.35 P. & P. 55p
(Post Free if all units purchased at same time)
Full after sales service
Also available ready built and tested £32.50. Post Free.

AMPLIFIER KIT ... £15.00 P. & P. 60p (Magnetic input components 33p extra)
POWER PACK KIT ... £5.35 P. & P. 55p
CABINET ... £5.35 P. & P. 55p
(Post Free if all units purchased at same time)
Full after sales service

Also available ready built and tested £32.50. Post Free.
Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc. and will then provide mixing and fading facilities for medium powered Hi-Fi Discotheque use, etc.

8-VALVE AUDIO AMPLIFIER HA34 MK II
Designed for HI-FI reproduction of records. A.C. Mains operation. Ready built on slatted heavy gauge metal chassis, size 7 1/2" x 4 1/2" x 4 1/2" h. Incorporates ECC83, EL84, E240 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £7.75. P. & P. 70p.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc £6.50 P. & P. 70p.

10/14 WATT HI-FI AMPLIFIER KIT
A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EP95 and E240 rectifier. Simple instruction booklet ONLY £12.00 P. & P. £1.00. Also available ready built and tested £16.50 P. & P. £1.00.

HI-FI STEREO HEADPHONES
Adjustable headband with comfortable flexible ear-muffs. Wired and fitted with standard stereo ϕ in jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. PRICE £4.05, P. & P. 25p.

Prices include VAT at Current Rate
(Please write clearly)
PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

HARVERSONIC SURPLUS CO. LTD.

(Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985
A few minutes from South Wimbledon Tube Station.
SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

Model 1570 is a unit audio console in a teak cabinet having record storage facilities. The amplifier is rated at 15W per channel. The tuner is a.m./stereo f.m. and the record deck is a single play unit. Twin 2-unit speaker assemblies are included in the quoted price of £237·58.

Model SX0940 is priced at £199 with a tuner including s.w. band, cassette deck and GC014 single play record deck. The amplifier rating is 2×5W.

Priced at £230·91, which includes speakers and metal stand, is the model 5024 comprising 3-band radio/cassette recorder and 3-speed stereo record player.

Pyser Ltd

On show was the new Marantz 1040 integrated stereo amplifier. Rated at 20W per channel, it features professional type graphic tone controls and main/remote speaker switching with ambience and loudness compensation. Price: £132 plus VAT. Also shown was the new 1070 amplifier and the model 2325, 2×125W stereo receiver with Dolby.



Marantz 1040 stereo amplifier.

Rank Radio International

On view for the first time was the SP range of Wharfedale loudspeakers. Two models make up the range, the Dovedale SP and Airedale SP. Both are floor standing reflex enclosures.

The Dovedale SP is a 60 litre enclosure handling 60 watts DIN whilst the larger Airedale contains 100 litres and accepts 100 watts DIN. The Dovedale has two in-phase bass drivers, one mid-range and one high frequency unit. The Airedale has a bass driver, two mid-range units covering between them the range of frequencies between 300Hz and 5kHz and a high frequency unit.

The Airedale SP has a bass cut-off frequency of 27Hz (-3dB) which represents the lower limit of human audibility. The Dovedale SP is little higher with a bass cut-off of 35Hz (-3dB). Both respond to beyond the limits of audibility at high frequencies.

The Dovedale SP and Airedale SP are available in Teak with removeable speaker grilles at the respective recommended retail prices per pair of £182·71 and £274·10 including VAT.

Skantic (UK) Ltd

Skantic introduced their new model 17532 17W per channel stereo hi-fi music centre. This unit includes an f.m. stereo radio and there are push buttons for selection of five pre-set stations.

The Skantic turntable has a 16 pole synchronous motor, an anti-skating device and easily adjustable stylus pressure. The arm includes a Pickering V15



Rank Radio International's latest models.


AT2 magnetic cartridge. The cassette recorder is completely designed and manufactured by Skantic's own engineers. The tape deck also has a built-in DNL noise reduction system, an autostop and chrome dioxide switching system. A VU meter for recording and playback levels and a digital counter are also included.

The 17532 exceeds European standard DIN 45·500 and is ready for ambiophonic stereo. The unit is available in Rosewood, teak or walnut high grade veneer as well as white or black lacquer.

Skantic's newly designed speakers, which are included with the 17532, each have a power handling capacity of 30 watts. Each speaker has two units a 20cms unit for bass and middle range and a 2·5cms dome-tweeter.

Features of the unit include loudness compensation filter selector; switchable sockets for headphones and inputs for two microphones.

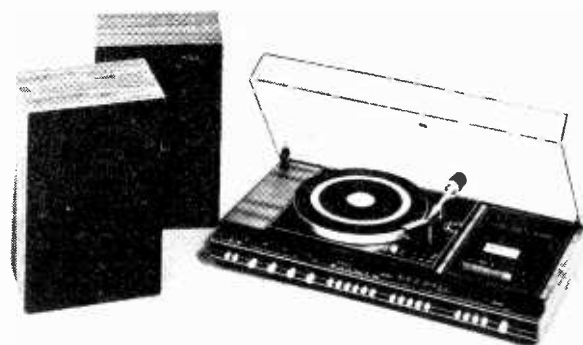Price including speakers: Rosewood—£308·78 + VAT; Teak—£288·75 + VAT; Walnut W/B—£302·33 + VAT.



The 17532 music centre from Skantic.

PW

RETURN OF POST MAIL-ORDER SERVICE

£6-95 Post 45p.



R.C.S. DISCO DECK SINGLE RECORD PLAYER

Fitted with auto stop complete with cartridge. Base-plate. Size 11in x 9in. Turntable. Size 7in. diameter. A/C mains. 200/250V motor has a separate winding 14 volt to power a small amplifier. Three speeds. Plays all records.

COMPLETE STEREO HI-FI

Two full size loudspeakers 13 1/2 x 10 x 8 1/2in. Player unit clips to loudspeakers making it extremely compact. Overall size only 13 1/2 x 10 x 8 1/2in. 8 watts per channel, plays all records 33 rpm, 45 rpm. Separate volume & tone controls. 240V AC mains.

Attractive Teak finish Weight 13lbs.



Bargain Price **£25** 85p carriage

SPECIAL OFFER

SMITH'S CLOCKWORK 15 AMP TIME SWITCH 0-60 MINUTES

Single pole two-way, surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Makers last list price £4-50. Brand new and fully guaranteed. Fully insulated. **OUR PRICE £2-50 Post 25p**



WEYRAD P50—TRANSISTOR COILS

RA2V Ferrite Aerial. 85p Printed Circuit, PCA1. 85p
 I.F. P50/2CC 470 kc/s. 40p J.E. Tuning Gang. \$1-80
 3rd I.F. P50/3CC. 40p OPTI. 65p
 Spare Cores. 8p Driver Trans. LFDT4. 65p
 P50/LIC. 80p
 Ferrite Rod 8 x 1/4in. 20p 6 x 1/4in. 20p 3 x 1/4in. 10p

VOLUME CONTROLS

5 K. ohms to 2 Meg. LOG or LIN. L/S 25p. D.P. 40p. STEREO L/S 55p. D.P. 75p. Edge 5K.S.P. Transistor 35p

80 Ohm Coax 5p. rd. BRITISH AERIALITE AERIAL-AIR SPACED 40 yd. £2. 60 yd. £3. FRINGE LOW LOSS. Ideal 625 & colour **10p yd.**

8in or 10 x 6in ELAC HI-FI SPEAKER

Dual cone plasticized roll surround. Large ceramic magnet. 50-15,000 c/s. Bass resonance 55 c/s. 8 ohm 10 watt. **£4-35** Each Post 40p



10 inch 18 watt Twin Cone, 8 ohm 25-20

E.M.I. 13 1/2 x 8in. SPEAKER SALE!

With tweeter and crossover. 10 watt. (8 or 8 or 15 ohm. Post 45p) (As illustrated) **£5-25**



With flared tweeter cone and ceramic magnet. 10 watt. Base res. 45-60 c/s. Flux 10,000 gauss. State 3 or 8 or 15 ohm. Post 45p (As illustrated) **£3-45**

BOOKSHELF CABINET Size 16 x 10 x 7in. teak finish **£6-95** Post 75p

E.M.I. 13 x 8in. BASS WOOFER. 20 WATTS RUBBER CONE SURROUND. £8-50 Post 40p.

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2in. sides 6 x 4in. 55p; 8 x 6in. 65p; 10 x 7in. 75p; 12 x 8in. £1-00; 14 x 9in. £1-20; 16 x 6in. £1-25; 18 x 8in. 55p; 16 x 10in. £1-40.

ALUMINIUM PANELS 18 s.w.g. 6 x 4in. 15p; 8 x 6in. 25p; 14 x 8in. 25p; 10 x 7in. 30p; 12 x 6in. 30p; 12 x 8in. 40p; 16 x 6in. 45p; 14 x 9in. 50p; 12 x 12in. 55p; 16 x 10in. 75p

SPECIAL OFFER

100 ohm 20W Rheostat 2 1/2in. diam. Ceramic Former, screw terminals, 1/4in. diam. spindle. 95p, post 25p.

RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, CROYDON

Minimum post 30p. Illustrated Radio Books & Components Lists 10p. Cash price includes VAT. Open 9-6 Wed. 9-1 Sat. 9-5 (Closed for lunch 1.15-2.30) Rail Selhurst. Tel. 01-684 1645

ANOTHER RCS BARGAIN!

ELAC 8 x 6in. HI-FI SPEAKER. TYPE 50RM. THIS FAMOUS AND WIDELY USED UNIT NOW AVAILABLE AT BARGAIN PRICE **£3.45** 10 WATT, 8 OHM. CERAMIC MAGNET.

4MFD 800V DC PAPER CAPACITOR
 Block Capacitor. Ideal as Filter Unit in 100 watt Loudspeaker Systems. 95p each, post 30. Also 2MFD 800v 90p.

GOODMANS CONE TWEETER
 18,000 cps. 25 watts. 8 ohm. Price **£3-75**
 8 inch Rubber surround woofer. **£5-75**

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12v. or H.T. 200-300V. d.c. operation. Size 10 x 1 1/2 x 1 1/2. Response 25 c/s. to 25 Kc/s. 26 dB gain. For use with valve or transistor equipment. **£1.45** Post Full instructions supplied. Details S.A.E. 30p

TEAKWOOD LOUDSPEAKER GRILLS. Will easily fit to baffle board. Size 18 1/2 x 10 1/2in—75p. 10 1/2 x 7 1/2in—45p.

RCS 100 watt Valve Amplifier Chassis

4 input master volume, treble and bass controls. This professional quality amplifier chassis is ideal for P.A. disco or groups where high power quality sound is required. 285. Carr. £2-50.

RCS "MINOR" 10 watt AMPLIFIER KIT

This kit is suitable for record players, guitars, tape playback, electronic instruments or small P.A. systems. Two versions available: Mono, £12-50; Stereo, £20. Post 45p. Specification 10W per channel; input 100mV; size 8 1/2 x 3 x 2in. approx. S.A.E. details. Full instructions supplied.

MAINS TRANSFORMERS. Postage Small 45p, Large 75p

250-0-250 80 mA. 6-3V 2amp. £2-80
 250-0-250 80 mA. 6-3V 3-5A 8-1V 1A or 5V 2A. £4-80
 350-0-350 80 mA. 6-3V 3-5A. 6-3V 1A or 5V 2A. £5-80
 300-0-300 120mA. 6-3V 4A C.T.; 6-3V 2A. £7-00
 MIDJET 220V 45mA. 6-3V 2A. £1-75
 HEATER TRANS. 6-3V 1 amp 85p. 8 amp £1-50

GENERAL PURPOSE LOW VOLTAGE. Trapped outputs at 2 amp, 8, 4, 5, 6, 8, 10, 12, 15, 18, 24 and 30V £4-80

1 amp, 6, 8, 10, 12, 15, 18, 24, 30, 36, 40, 48, 60 £4-80

2 amp, 6, 8, 10, 12, 15, 18, 24, 30, 36, 40, 48, 60 £7-00

3 amp, 6, 8, 10, 12, 15, 18, 24, 30, 36, 40, 48, 60 £8-70

4 amp, 6, 8, 10, 12, 15, 18, 24, 30, 36, 40, 48, 60 £11-25

6-0-6V 500mA 90p, 20V 1A £1-85

9V 1 amp 95p 18V 300mA 75p 12V 500mA 85p 12V 750mA 95p, 10, 30, 40V 2 amp £2-30V 3 amp £2-40V 2A £2-75.

22-0-22V 4A D.C. £3. 18V 1 amp. 95p. 12V 2 amp £1-85.

AUTO TRANSFORMERS. 115V to 250V or 230V to 115V 150W £5. 250W £6. 400W £7. 500W £8.

FULL WAVE BRIDGE CHARGER RECTIFIERS; 6 or 12V outputs. 1 amp 40p; 2 amp 55p; 4 amp 85p.

MAINS ISOLATING TRANSFORMER

Primary 0-110-240V. Secondary 0-240V. 8A. 780W. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. **OUR £13-50** Carr. Famous make. (Value £19) **PRICE £13-50** 95p

Can be used as 800W auto transformers 240-110V. **IDEAL FOR COLOUR T.V. OR GARDEN TOOLS.**

NEW ELECTROLYTIC CONDENSERS

2/250V .14p 100/25V .10p 50+50/500V .50p
 4/850V .14p 250/25V .14p 350+350/325 .85p
 3/850V .22p 500/25V .20p 32+32/850V .40p
 18/350V .35p 100+100/275V .65p 32+32/450V .60p
 22/350V .55p 150+150/275V .70p 32+32/32/850V .65p
 32/500V 50p 8+8/350V .25p 32+32+32/450V .85p
 25/25V .10p 8+16/350V .25p 900/850V .95p
 50/50V .10p 16+16/350V .40p 4700/85V .95p
 2000+2000/25V .95p


LOW VOLTAGE ELECTROLYTICS

1, 2, 4, 5, 8, 10, 25, 50, 100, 200mF. 15V. 10p.
 200mF. 15V. 15p; 25V. 20p; 50V. 30p; 100V. 40p.
 1000mF. 12V. 20p; 25V. 25p; 50V. 47p; 100V. 70p.
 2000mF. 6V. 25p; 25V. 45p; 50V. 57p.
 2500mF. 50V. 62p; 3000mF. 25V. 47p; 50V. 66p.
 5000mF. 6V. 25p; 12V. 42p; 25V. 75p; 50V. 85p; 50V. 96p.
 2000+2000/25V. 75p.

MICRO SWITCH. Single Pole Change Over. 20p.
MICRO SWITCH. Snap Min 25p.
CERAMIC 1/2p 0-01mF. 5p. Silver Mica 2 to 5000pF. 5p.
PAPER 850V-0 1 7/8. 0-5 1/2p; 1mF 15p; 2mF 150V 15p.
500V-0-001 to 0-05 4p; 0-1 10p; 0-25 15p; 0-47 25p.
TWIN GANG. "0-0" 208pF-170pF. £1-20; 500pF standard 75p; 855+855 with 25+25pF Blom motion drive 50p.
TWIN GANG. 120pF 50p. 385pF 50p.
SHORT WAVE, SINGLE. 10pF 50p; 25pF 55p; 50pF 55p.
WIRE WOUND. 1000pF. 250V AC/DC Amber 25p.
RESISTORS. 1/4W, 1/2W, 1W, 20% 2p; 5W, 5p, 10 10 to 10M. HIGH STABILITY. 1/4w. 2% 10 ohms to 6 meg., 12p. Dittie 5% Preferred values 10 ohms to 10 meg., 4p. WIRE-WOUND RESISTORS. 5 watt, 10 watt, 15 watt 10 ohms to 100K 10p each.
TAPE OSCILLATOR COIL. Valve Type 35p.

NEW MODEL "BAKER LOUDSPEAKER" 12in. 50 watt GROUP 50/12 8 or 15 ohm high power full range. Professional quality. **Post 80p £14-50**

BAKER MAJOR 12" £11-50 Post 60p



30-14,500 c/s, 12in. Double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwell. Bass resonance 40 c/s. Rated 30 watts. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£14-50** Post 50p
 Please state 3 or 8 or 15 ohms.

BAKER "BIG-SOUND" SPEAKERS

'Group 25' 12 inch £8-95
 25 watt 35 watt
 8 or 8 or 15 ohm 8 or 8 or 15 ohm


'Group 35' 18 inch £10-50
 35 watt 80 watt
 8 or 8 or 15 ohm 8 or 15 ohm

TEAK VENEERED HI-FI SPEAKER CABINETS

For 12in. or 10in. dia. speaker 20 x 18 x 12" £12-00 Post 95p
 For 18 x 8in. or 8in. speaker 16 x 10 x 7" £7-50 Post 75p
 For 8 x 6in. speaker 12 x 8 x 6" £4-60 Post 50p
LOUDSPEAKER CABINET WADDING 18in. wide, 20p 1/2

GOODMANS 6 1/2in. HI-FI SPEAKER

8 ohm, 10 watt. Large ceramic magnet. Special cone surround. Frequency response 30-15,000 c/s. Ideal P.A. Column, Hi-Fi Enclosure Systems, etc. Suitable cabinet 12 x 8 x 6 1/2. Suitable Tweeter £2-00.



£4-60 Post 30p

ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 c/s to 18,000 c/s. Size 8 1/2 x 3 1/2 x 2 1/2in. deep. Rating 10 watt, 8 ohm Suitable **£2-20** Post 30p

SPEAKER COVERING MATERIALS. Samples Large 8.5in Horn Tweeters 2-18kc/s, 10W 8 ohm or 15 ohm £2-50

CROSSOVERS TWO-WAY 3000cps 3 or 8 or 15 ohm £1-50

LOUDSPEAKERS 3 OHMS 7 x 4in. £1-25; 9in. £1-80; 12 x 8in. £1-75; 10 x 6in. £2-40; 10in. £2-85.

SPECIAL OFFER: 8 ohm, 8 1/2in., 8 1/2in. 5 ohm, 3in., 2 1/2in. dia., 5 x 3in. 6" x 4" **£1-25 EACH** 15 ohm, 3 1/2in. dia.; 6 x 4in.; 7 x 4in.; 5 x 3in. TYPE 8 ohm, 2 1/2in.; 3 1/2in.; 5in. dia. (6 x 4in. 8 ohm £1-80)

RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 8 in. diameter 4 watt £2-50. 10in. diameter 5 watt £2-95; 12 in. diameter, 6 watt £3-80.

VALVE OUTPUT TRANS. 40p; MIKE TRANS. 50-1 40p. MIKE trans. mu metal 100-1 £1-25.

MAJOR 100 WATT ALL PURPOSE GROUP OR DISCO AMPLIFIER



All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 8/15 ohm. a.c. Mains. Separate treble and bass controls. 8 WATT 4 INPUTS. 2-WAY MIXING. **IDEAL FOR DISCO OR PA. £49-95, Post £1**

£59 Carr. £1-00

3-WAY CROSSOVER 950 CPS and 3000 CPS £2-20 with leads ready assembled

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. **£5-20**

TWO CHANNEL STEREO VERSION £6-85

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume, treble and bass controls 18v. **MAINS POWER PACK £3-45.**

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 18p. COAXIAL OUTLET BOXES, surface, 85p. BALANCED TWIN FEEDER 300 ohms 7p yard. JACK SOCKET 8d. open-circuit 15p, closed-circuit 25p. Chrome Lead Socket 45p. Phone Plugs 5p. Phone Socket 8p. DIN PLUGS 8d. Chrome 20p; 3 6mm Chrome 12p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 18p; 5-pin 25p. DIN PLUGS 3-pin 18p; 5-pin 25p. VALVE HOLDERS. 5p; CERAMIC 10p; CANS 5p.

RCS SOUND TO LIGHT KIT

3 channel 1000 watts per channel. As featured in recent issue. £12-50 post 30p.

E.M.I. GRAM MOTOR £1-25
 120v. or 240v. A.C. 2,400 rpm. 2-pole 70mA. Size 2 1/2 x 2 1/2 in. Post 80p.

ENGINEERS

FREE

YOURSELF FOR A BETTER JOB WITH MORE PAY!



Do you want promotion, a better job, higher pay? "New opportunities" shows you how to get them through a low-cost, Home Study Course. There are no books to buy and you can pay as you learn.

This easy to follow GUIDE TO SUCCESS should be read by every ambitious engineer. Send for this helpful 76-page free book NOW! No obligation, nobody will call on you. It could be the best thing you ever did.

CHOOSE A BRAND NEW FUTURE HERE

CUT OUT THIS COUPON
Tick or state subject of interest. Post to address below.

- | | | |
|--|--|---|
| <input type="checkbox"/> ELECTRICAL & ELECTRONICS | <input type="checkbox"/> Radio, Servicing & Repairs | <input type="checkbox"/> Painting & Decorating |
| <input type="checkbox"/> Practical Radio & Electronics (with KIT) | <input type="checkbox"/> Radio Amateur's Exam. | <input type="checkbox"/> MECHANICAL |
| <input type="checkbox"/> Electronic Engineering Certificate | <input type="checkbox"/> AUTO & AERO | <input type="checkbox"/> A.M.S.E. (Mech.) |
| <input type="checkbox"/> General Elect. Eng. Certificate | <input type="checkbox"/> Motor Mechanics | <input type="checkbox"/> General Mech. Eng. |
| <input type="checkbox"/> C. & G. Elect. Installations | <input type="checkbox"/> C. & G. Motor V. Mechanics | <input type="checkbox"/> Inst. Engineers & Technicians |
| <input type="checkbox"/> Elect. Install. & Work | <input type="checkbox"/> General Auto Engineering | <input type="checkbox"/> Maintenance Engineering |
| <input type="checkbox"/> C. & G. Elect. Technicians | <input type="checkbox"/> A.M.I.M.I. | <input type="checkbox"/> Welding |
| <input type="checkbox"/> RADIO & TELECOMMUNICATIONS | <input type="checkbox"/> Air Registration Board Certs. | <input type="checkbox"/> MANAGEMENT & PRODUCTION |
| <input type="checkbox"/> Colour TV Servicing | <input type="checkbox"/> M.A.A./I.M.I. Dip. | <input type="checkbox"/> Computer Programming |
| <input type="checkbox"/> C. & G. Telecoms. Technician's Cert. | <input type="checkbox"/> CONSTRUCTIONAL | <input type="checkbox"/> Inst. of Cost & Managements Accts. |
| <input type="checkbox"/> C. & G. Radio, TV & Electronics Mech. Cert. | <input type="checkbox"/> Heating, Ventilating & Air Conditioning | <input type="checkbox"/> DRAUGHTS-MANSHIP & DESIGN |
| <input type="checkbox"/> Radio & TV Engineering Course | <input type="checkbox"/> Architectural Draughtsmanship & Design | <input type="checkbox"/> General Draughtsmanship |
| | <input type="checkbox"/> L.I.O.B. | <input type="checkbox"/> A.M.I.E.D. |
| | <input type="checkbox"/> Carpentry & Joinery | <input type="checkbox"/> Electrical Draughtsmanship |
| | <input type="checkbox"/> Plumbing Technology | |
| | <input type="checkbox"/> General Building | |



G.C.E.
—58 'O' & 'A' Level Subjects
—over 10,000 Group Passes!

Aldermaston College

Dept. TPW11, Reading RG7 4PF.

also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London EC2Y 5ET. Tel. 628 2721.

NAME (Block Capitals)

ADDRESS

..... Postcode.....

Other subjects of interest..... Age.....

Accredited by C.A.C.C. Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

AIRCRAFT H.F. Rx type R4187 and Control Box these are a crystal controlled Rx intended for remote control and will provide up to 24 channels in the range 2-8 to 18Mc/s the Rx is a dual conversion type with 2 RF stages, I.F. Filters, BFO, N.L. O/P stage etc. uses 16 type B7g valves Normal power I/P 24 and 19v DC (or 200v HT and 19v) crystals required Hc6/u type not supplied. Supplied complete with control box and manual. **£16.20. AERIAL SYSTEM** single dipole type for use on 100/150Mc/s band complete with 36ft of UR67 H.D. 50 ohm coax new in crate **£5.40. DISH AERIALS** 18" dia 4" deep at centre plain Ali finish new **£3.70. PYE VANGUARD R.T.** units set up for 70/85Mc/s range for use on 12v DC, RF O/P 20 watts, double conversion Rx with transis I.F. & O/P stage, Rx IFs 10.7 & 455Kc supplied less Tx & Rx crystals (2nd LO. crystal supplied) with circs and crystal data, less accs. **£10.60. FREQ METER** Marconi type TF1026/4 range 2 to 4KMc/s absorption type with meter ind, in case **£14. PYE RANGER R.T.** sub units Rx unit with 11 valves dual conversion 10.7 & 2Mc/s I.F.s needs 12v & 200v HT O/P for 3 ohm spk. for use in 70/80Mc/s range less Rx crystal (2nd Osc crystal supplied) **£3.75. Modulator & H.T. Inverter** section with all transis & heatsink about 15 watt mod, 200 or 400v HT at 150 Ma 12v I/P. both sub units supplied with circs. **£4.75. CONTAMINATION METERS** range .1 to 10 Mill/R per Hr meter indication with probe head and GM tube in carrying case with mains P.U. and manual new tested **£8.50. ROLLER COASTER** coll 5 x 1 1/2" dia 36 turns, silver plated fittings carbon brush **£3.40. CRYSTAL CALIBRATORS** for use on 240v gives O/Ps at 100Kc, 1 & 10 Mc/s from 3 separate crystals with harmonics up to 50th of fund fuller description on request **£19. CRYSTALS** FT243 type in range 5 to 8Mc/s supplied as they come 5 different for **£1.30. T.V. FILTER UNITS** made to fit in Ae lead fully screened Ali box 4 1/2 x 1 1/2 x 1 1/2" fitted standard coax plug & sk new 4 for **£1.25. HEAD & MIKE SETS** for use with 19 set MC type low res with lead & plug new **£2.60. CRYSTAL OVENS** with heater contains 12 type Hc6/u crystal holders these can be removed **95p. COAX LEADS** 25ft fitted N type plugs on 50 ohm H.D. cable new **£2.70. METER UNIT** dual scale as 270° 1 Ma & 100-0-100Ua meter in same case size 3 1/2" Sq ex aircraft **£4. HEADPHONE MATCHING TRANS & LEAD** as high to low res trans with 5ft lead and standard jack plug new **£1. METER UNIT X POINTER** for use with R1155 Rx as dual 115 Ua meters in same case **£2. R1155B Rx** units few of these well known Rx covers Long & Med wave plus 2 S.W. 3 to 18 Mc/s fitted N type drive, tuning Ind etc complete with DF section, reqs ext supply of 220v 60Ma H.T. & 6.3v 4a heaters, O/P for phones supplied tested with manual (fuller spec on request) **£30.**

List of Circs and Manuals available on request.

Above prices include carr/postage and VAT. S.A.E. for list 13 or enquiry, Goods ex equipment unless stated otherwise.

A. H. SUPPLIES

57 MAIN ROAD, SHEFFIELD S9 5HL
Phone 444278 (0742)

TRIPLE RANGE WOBBULATOR

J. G. RANSOME



FREE running oscillators designed around TTL ICs are notorious for poor frequency stability. The most significant factor contributing to frequency drift is variation of the supply voltage, and it is this apparent 'disadvantage' that is exploited in this circuit.

The FM Signal Generator (Wobbulator) is an essential piece of apparatus for setting up the HF circuits of FM receivers, and is extremely useful for the fast, accurate alignment of AM IF strips. In the conventional RF signal generator a continuous carrier is generated at constant frequency. A second signal at (usually) audio frequency is then applied to this RF signal varying the RF output voltage amplitude in direct relationship to the second, modulating frequency. In the FM signal generator the RF waveform is generated at constant amplitude and the modulating tone is used to vary the frequency of the RF signal.

The simple Wobbulator described here provides signals at three selected centre frequencies with provision for wide frequency deviation using external modulating sources. Although the RF signal is based on a square waveform rather than the more conventional sine wave, the effect of this difference is negligible in practice.

Basic circuit

The basic circuit of the free running TTL multi-vibrator is shown in block form in Fig. 1, and is probably the simplest circuit available to the

amateur constructor! If Ct is omitted the oscillator comprises three positive logic NAND gates in series. In this configuration the mode of operation is quite straightforward. If the input at gate 1 is 'low' the output will be 'high'. Gate 3 thus has a 'low' input and a 'high' output and since the output of gate 3 drives the input of gate 1 a self-oscillating loop is created.

The operating frequency of this oscillator is deter-

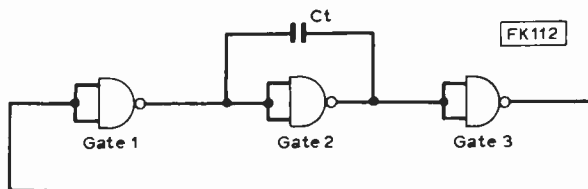


Fig. 1: Block diagram of a basic TTL oscillator.

mined by the signal propagation delays through the gates. For the SN7400 gate the propagation delay for the 'low' state is approximately 8.0ns and for the high state 18ns. As the oscillator alternates between two 'low' plus one 'high' state, and two 'high' and one 'low' state the total delay alternates between (8+18+8)ns and (18+8+18)ns. The typical average delay is thus: $\frac{34+44}{2}$ or 39ns, giving typical

free-running frequency of $\frac{1}{39 \times 10^{-9}}$ Hz or 25MHz.

As the two delays are not equal the output is not a 1:1 mark/space ratio squarewave and in practice stray capacitance and internal imbalances tend to emphasise the delay difference to give a ratio nearer 2:1.

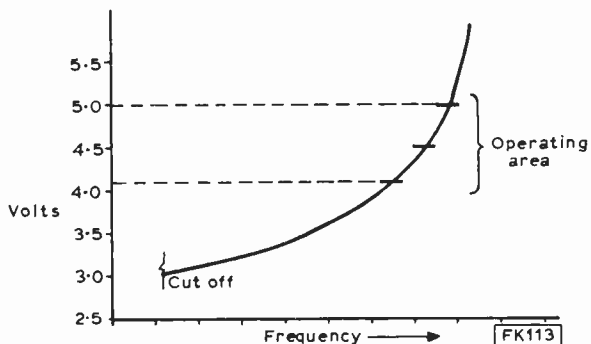


Fig. 2: Frequency plotted against voltage for a TTL oscillator. As can be seen, the relationship is non-linear.

Frequency variation

The oscillator frequency can be varied by altering the propagation delay time, by modifying the rise time of the transfer pulse. This is the function of C_t . It is possible to use a series of capacitors across one, two or all three of the gates to give a more stable arrangement but in practical circuits this complication is rarely justified. The effect of C_t is surprisingly linear and for the purpose of initial trials the oscillator frequency can be expressed as: If $C_t=22\text{pF}$ then $F=11\text{MHz}$ and if $C_t=500\text{pF}$, $F=500\text{kHz}$.

These values as calculated should be treated with some caution as tolerances can lead to quite significant modifications to C_t to obtain a given frequency of operation. The equation thus indicates an approximation for C_t , the actual value has to be found by experiment.

The oscillator frequency increases with increasing supply voltage, Fig. 2, and as can be seen the frequency/voltage relationship is non-linear. However, if we consider a relatively small voltage change ($\pm 0.5\text{V}$) the linearity is sufficiently good to make the control of frequency by means of varying the supply voltage a worthwhile proposition.

The simplest arrangement for varying the supply voltage is the series emitter follower shown in Fig. 3 in which the base of the transistor is biased by means of a potential divider and the collector taken to a suitable positive supply. In this arrangement the voltage appearing at the emitter is equal to the base voltage less the base/emitter voltage drop of the transistor (0.6V in the case of silicon). If a variable voltage is now applied to the base of the transistor the emitter voltage will rise and fall in

phase with the base voltage so that the emitter 'follows' the base voltage.

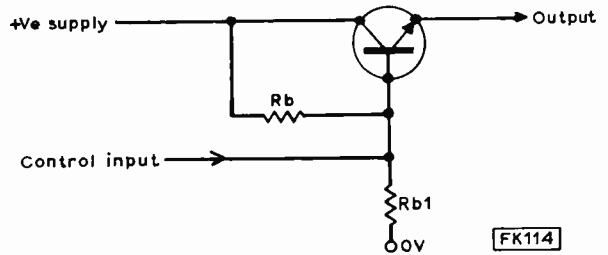


Fig. 3: The theoretical series emitter follower shown here, varies the voltage, and thereby the frequency of the oscillator to which it is connected.

Practical circuit

In the practical circuit Fig. 4, the timing capacitor (C_t of Fig. 1) is switched by means of S_{1c} to provide three spot frequencies, the values shown giving spot frequencies of 455kHz , 1.6MHz and 10.7MHz .

Variable resistors VR_{2-3-4} are incorporated to set the precise operating frequency. These resistors modify the current flows to the gate inputs and provide a small degree of frequency adjustment on each range. It is important that these resistors should be set to the highest possible value to minimise the gate bias, as overbiasing can lead to erratic running and poor stability. If it is found that the tuning resistor has to be set to a value of less than $2\text{k}\Omega$, then an alternative timing capacitor should be sought.

The SN7400 is a quadruple NAND gate, and since


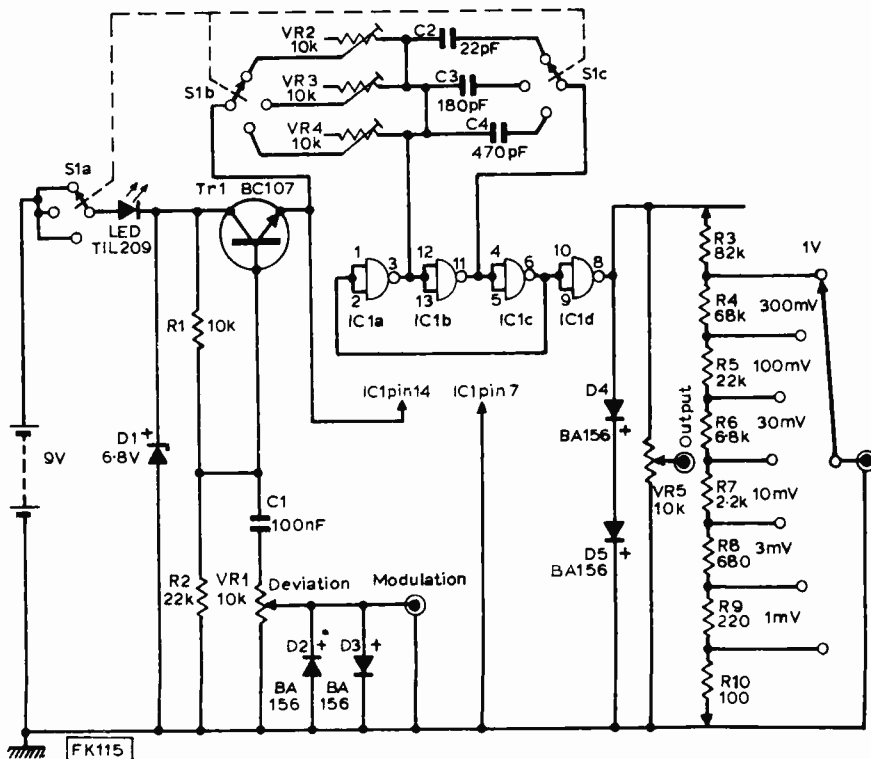


Fig. 4: Circuit diagram of the complete TTL Wobulator. The output may be taken from either the rotor of VR_5 , or alternatively from the attenuator network. However only one of these two, should be connected in circuit.

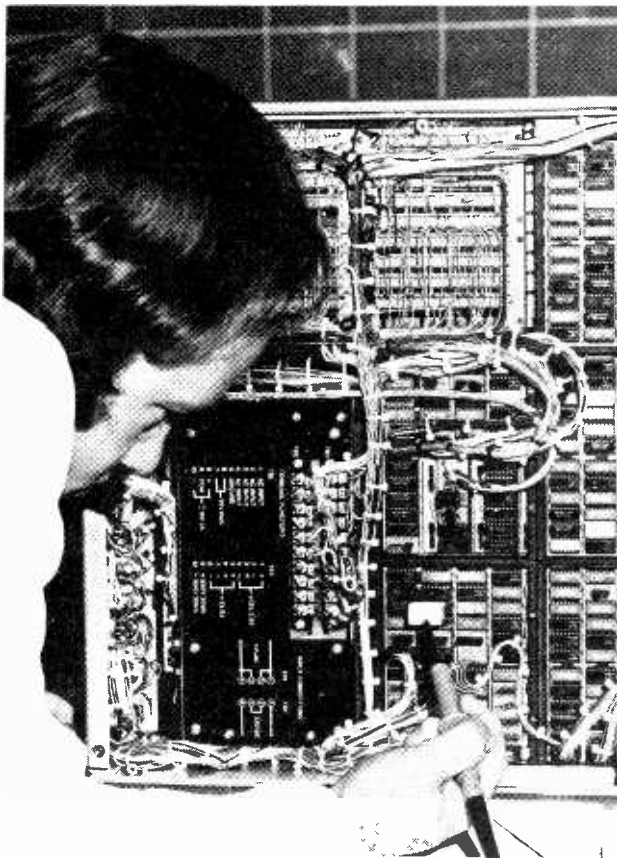

This hobby brings big rewards.

A soldering iron and a screwdriver. If you know how to use them, or at least know one end from the other, you know enough to enrol in our unique home electronics course.

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.


You build, see and learn as, step by step, we take you through all the fundamentals of electronics and show you how easily the subject can be mastered and add a new dimension not only to your hobby but also to your earning capacity.

All the training is planned to be carried out in the comfort of your own home and work in your own time. You send them in when you are ready and not before. These culminate in a final test and a certificate of success.


1

Build an oscilloscope.

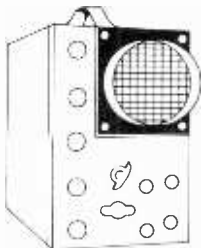As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.




2

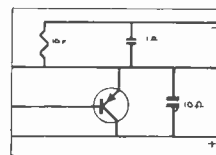

Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

3

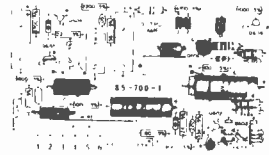


Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

PLUS

FREE GIFT!

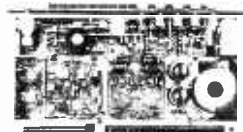

ALL STUDENTS ENROLLING IN OUR COURSES RECEIVE A FREE CIRCUIT BOARD ORIGINATING FROM A COMPUTER AND CONTAINING MANY DIFFERENT COMPONENTS THAT CAN BE USED IN EXPERIMENTS AND PROVIDE AN EXCELLENT EXAMPLE OF CURRENT ELECTRONIC PRACTICE

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.


Brochure without obligation to:
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept W.H.115
P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

(Block caps please)

KITS FOR THE CONNOISSEUR

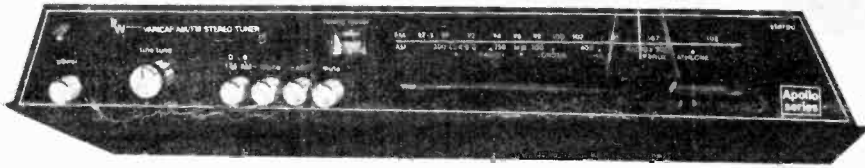

Apollo III Tuner

High Quality FM/AM Tuner as Featured in the July and August Issues of Practical Wireless

Complete Kit	Order as TTS/1000/S	£55-00	Circuit Board only	Order as TTS/1375/S	£5-00
Kit less Cabinet	Order as TTS/1001/S	£46-00	Built and Tested	Order as TTS/A/BT	£68-50
Complete Kit less Part I	Order as TTS/1003/S	£45-60			

Scorpio Tuner FM/AM Varicap Tuner

Similar in appearance to the Apollo III.

This more complex kit builds into a high performance tuner with special features such as the EC5603U tuner head, the 3089 IF IC, 1310 stereo decoder and BR2007N pilot tune notch filter. Also has remote tuning facilities and adjustable output.

Complete Kit	Order as TTS/1005/A	£48-50	Remote Control Unit	Order as RC/1005/A	£5-20
Built and Tested	Order as TTS/SC/BT	£60-50	Cabinet and Metal work only	Order as TTS/CM/O	£13-00

All prices quoted are exclusive of VAT—please add 25%.

Capricorn Amplifier, Aquarius Tape Unit, Taurus Quadraphonic Add-on Unit

Due to difficulties with certain components modifications are now being undertaken on these units and they will not now be available until early next year.

All kits include all parts necessary to complete the particular kit, together with full constructional information.

Please send a stamped self-addressed envelope with all enquiries.

WE DESIGN AND MANUFACTURE A COMPLETE RANGE OF DOMESTIC AUDIO EQUIPMENT INCLUDING MUSIC CENTRES, QUADRAPHONIC UNITS AND TUNER AMPLIFIERS

TRADE ENQUIRIES WELCOME.

TAPE TRAINING SERVICES LTD Rear of 7 West Road, Westcliff-on-Sea, Essex.

SPARKITE MK 2

CAPACITIVE DISCHARGE ELECTRONIC IGNITION KIT

Sparkite MK 2 is a high performance, high quality capacitive discharge, electronic ignition system. Sparkite completely eliminates problems of the contact breaker. Misfire due to contact breaker bounce is electronically eliminated, contact breaker burn is eliminated, the condition of the contacts is not relevant to the performance of the ignition, and the system is no longer dependent on the dwell period for recharging.

Sparkite will give you: Up to 20% better fuel consumption, instant all-weather starting, cleaner plugs—they last up to five times longer without attention, faster acceleration, higher top speed, longer coil and battery life, efficient fuel burning and less air pollution, smoother running, continual peak performance.


The Kit comprises everything needed: Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heatsink, top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.

WE SAY IT IS THE BEST SYSTEM AT ANY PRICE

Voted best of 8 Ignition systems tested by a leading Motoring Magazine

Price: D.I.Y. assembly kit £10-93 including VAT post and packing. Ready built unit £13-86 including VAT post and packing. (Both to fit all vehicles with coil distributor ignition up to 8 cylinders.) Switch for instant changeover from Sparkite ignition to conventional ignition £2-79 including VAT post and packing. (Fitted in case on ready built unit dashboard mounting on kit.) We can supply units for petrol-engined vehicle (boat, motorcycle, etc.) with coil/contact breaker ignition. Details on request.

CALL IN AND SEE US FOR A DEMONSTRATION

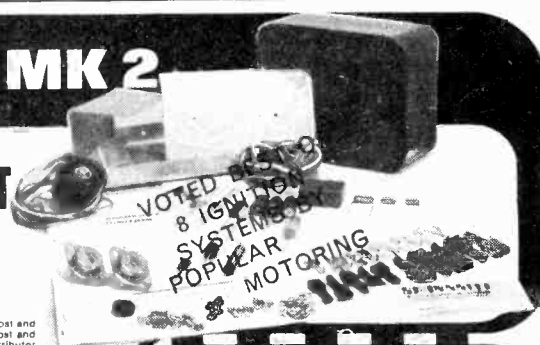

ORDER NOW

To: Electronics Design Associates Dept. PW 11
82 Bath Street, Walsall, WS1 3DE. Phone 33652

From: Name

Address

Quantity Please Supply

- Sparkite Mk. 2 D.I.Y. Assembly kits at £10-93
- Sparkite Mk. 2 Ready Built Negative earth at £13-86
- Sparkite Mk. 2 Ready Built Positive earth at £13-86
- Ignition changeover switches at £2-79
- R.P.M. Limit systems in the above units at £2-42
- Fluorescent light assembly kits at £3-46
- Fluorescent light built units at £4-10
- Diffusers for the above at 50p

of number aluminum boxes at
of number aluminum boxes at
of number aluminum boxes at

I enclose cheque/P.O. for £..... Cheque No.
(Send S.A.E. if brochure only required)

ELECTRONICS DESIGN ASSOCIATES of WALSALL

ALUMINIUM BOXES

Prices include lids, screws and VAT (at 8%). 18p should be added to the total order value for postage and packing.

No. 7	5 1/2" by 2 1/2"	by 1 1/2" high	47p
No. 8	4" by 4"	by 1 1/2" high	48p
No. 9	4" by 2 1/2"	by 1 1/2" high	48p
No. 10	5 1/2" by 2 1/2"	by 1 1/2" high	50p
No. 11	4" by 2 1/2"	by 2" high	48p
No. 12	3" by 2"	by 1" high	38p
No. 13	6" by 4"	by 2" high	58p
No. 14	7" by 5"	by 2 1/2" high	75p
No. 15	8" by 6"	by 3" high	83p
No. 16	10" by 7"	by 3" high	£1-14

FLUORESCENT LIGHT KIT

You can build this reverse polarity protected 12V 8W fluorescent light. Everything needed is supplied: white enamelled drilled metalwork, ready drilled heatsink, printed circuit board, high quality components and transformer, and caps, cable, the fluorescent tube, nuts, bolts, washers and simple assembly and operating instructions. When complete the light has many uses: workshop and workbench illumination, garage lighting, emergency lighting, lighting for camping, and boating as an inspection lamp and many more.

Price: Assembly kit £3-46 inc. VAT post and packing. Ready built £4-10 inc. VAT post and packing. Diffuser 50p inc. VAT post and packing.

only three gates are used for the oscillator, the fourth gate can be used as a buffer to prevent the output load from affecting the operation of the oscillator. The output from the buffer gate depends very much on the device used. The cheap, low-noise immunity gates give a swing of about 2V, while the more expensive can manage 3V or so. These output levels are too high for most purposes and the circuit of an optional attenuator circuit is shown in Fig. 4. As the output from the gate is a squarewave the simplest way of maintaining constant amplitude to the attenuator is to clip the signal at a predetermined level. This is the function of the diode network D4/D5 which limits the output to 1.8V. The clipped signal is then fed to VR5 or the resistive ladder network (R3-R10) which makes up the attenuator.

Modulation

The modulating signal is AC coupled to the base of Tr1 to prevent any residual DC component of the waveform from de-tuning the oscillator. The diodes D2 and D3 wired back-to-back limit the modulating signal. Silicon diodes are again used here with a forward voltage drop of 0.6V so that they need at least 0.6V across them before they conduct. If the input signal exceeds this value one or other of the diodes conduct shorting the excess signal to earth.

The potentiometer VR1 determines the level of modulating signal reaching Tr1 base and therefore controls the frequency variation of the oscillator with respect to input voltage. This potentiometer is thus the deviation control. The zener diode D1 limits the rail voltage to 6.8V. An alternative mains power unit is shown in Fig. 5.

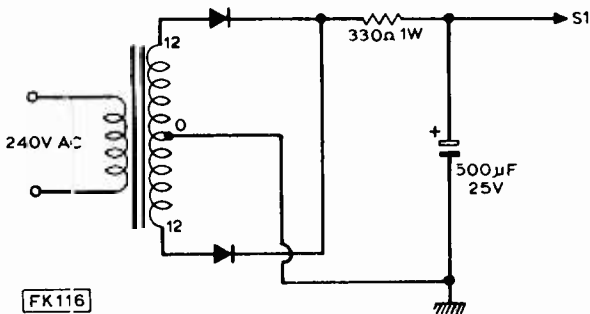


Fig. 5: Alternative mains power supply. This is recommended if prolonged use is to be made of the Wobbulator.

Construction

The oscillator and modulator are built on a piece of 0.1in. matrix veroboard, Fig. 6. The layout is not critical and may be built on any scrap piece of veroboard. The trimming capacitors and resistors are wired directly on the range switch while the resistors comprising the alternative attenuator chain are similarly mounted round the output range switch (not shown in photograph).

Using an aluminium box 130 x 100 x 50mm deep, the battery powered version can be neatly accommodated on the metal panel as shown in the photographs. The mains powered version can be built

into the same size box if the Doram transformer specified is used. However, as this involves some rather careful 'packing' of components, the less experienced would be well advised to opt for a larger box.

Calibration

Carefully check the wiring, switch on and check that Tr1 emitter voltage is 4.5V ($\pm 0.2V$). R1 should be adjusted if necessary to obtain this voltage. The spot frequencies must next be established. During this setting-up procedure the modulation input must be shorted to earth. Using an 'all-band' communications type receiver, feed the attenuated output from the wobbulator into the aerial socket. With the BFO switched on, the wobbulator output can be detected and VR2-3-4 adjusted until the required three spot frequencies are obtained. The attenuator function can also be checked against the 'S' meter.

In the absence of a suitable communications receiver the spot frequencies will have to be set up against known frequency IF strips. The output from the wobbulator should be injected into the first IF transformer, the most convenient point being at the mixer stage. A voltmeter should then be connected across the AGC line and the appropriate VR adjusted until maximum AGC voltage is detected. The spot frequency is then set to the centre frequency of the IF.

★ components list

Resistors

R1	10k Ω	R8	680 Ω
R2	22k Ω	R9	220 Ω
R3	82k Ω	R10	100 Ω
R4	68k Ω	VR1	10k Ω
R5	22k Ω	VR2	10k Ω
R6	6.8k Ω	VR3	10k Ω
R7	2.2k Ω	VR4	10k Ω
All 5% $\frac{1}{2}$ or $\frac{1}{4}$ W		VR5	10k Ω

Capacitors

C1	100nF	C3	180pF
C2	22pF	C4	470pF

Semiconductors


Tr1	BC107	D4	BA156
D1	BZY96 6.8V zener	D5	BA156
D2	BA156	IC1	SN7400
D3	BA156		

Miscellaneous

LED type TIL209. Two coaxial sockets. Four knobs. Four-way three-pole wafer switch. 0.1in. matrix veroboard 40 x 30mm. Metal box 130 x 100 x 50mm. Single pole, seven way wafer switch.

Optional power supply

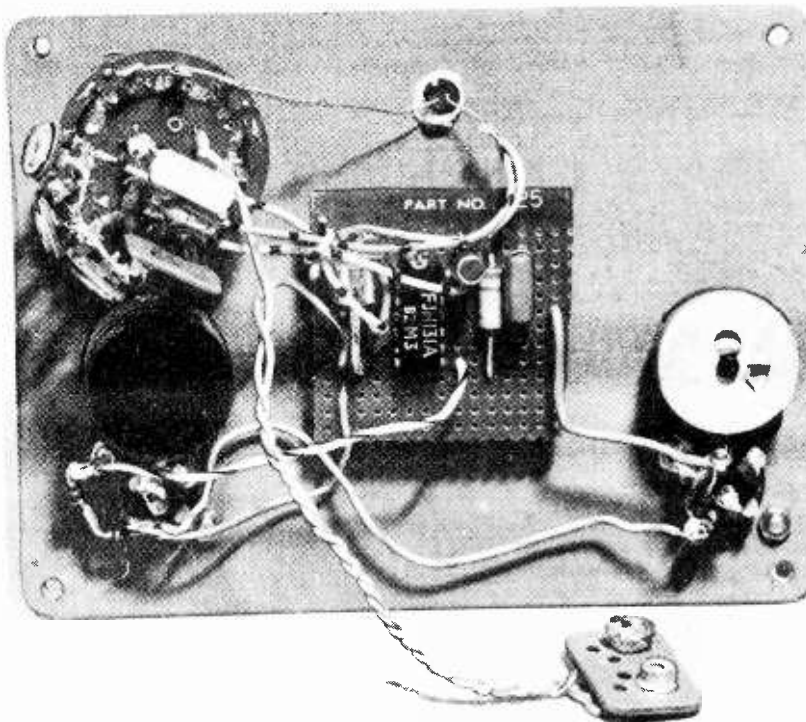Mains transformer, sub. miniature 12-0-12V, type 196-274 Doram Electronics. Two rectifier diodes type 1N4001. 330 Ω 1W resistor. 500 μ F 25V electrolytic capacitor.



Photograph showing the mounting of the components on the rear of the front fascia. Notice the variable resistors and timing capacitors mounted on the wafer switch.

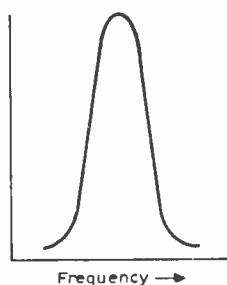


Fig. 7a: Ideal response curve.

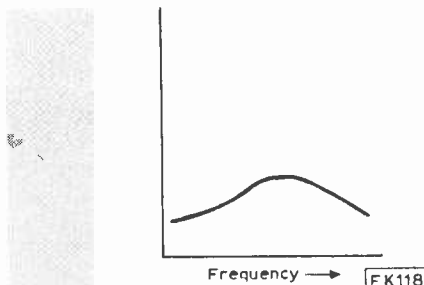


Fig. 7b: Poor selectivity.

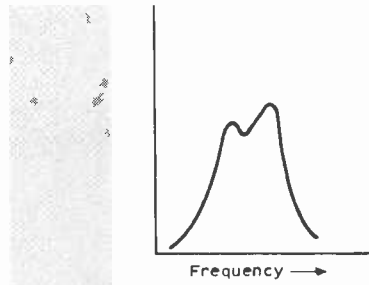


Fig. 7c: Detuning of one or more stages in the IF strip.

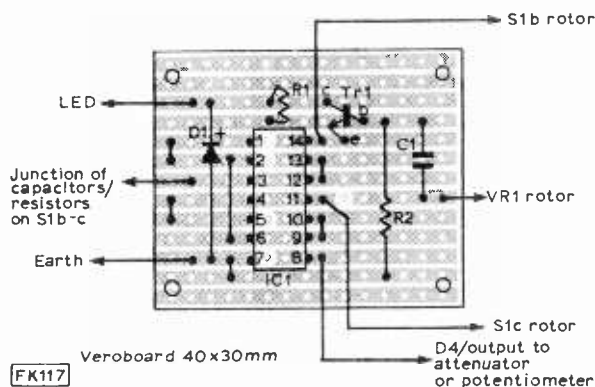


Fig. 6: The circuit should be laid out on 0.1in. matrix Veroboard as shown above.

Operation

To use the wobbulator effectively an oscilloscope with an X deflection output is required which is fed into the modulation socket of the wobbulator and the Y input (vertical deflection) is coupled to the detector of the intermediate frequency strip under test. The wobbulator output is then applied to the IF transformers in turn starting with the last IF and progressing to the first. The response shown on the cathode ray tube should be as Fig. 7a. Figs. 7b and 7c show poor selectivity and detuning of one or more stages respectively. With care it will be found that this technique will give up to 6dB more gain and greater selectivity than the usual method of amplitude modulated signal generator plus ear!

PW

RECORD PLAYBACK TAPE HEADS

Individual prices of these are:
 2 track record playback heads 75p each.
 4 track record playback heads £1-10 each.
 Erase heads are also available separately—
 2 track 60p—4 track 85p.
 MV metal mounting shields 60p each.
 2 track heads already fixed on heavy mounting plate with shield £1.85. ALL VPL 25% VAT

CONTROL DRILL SPEEDS

DRILL CONTROLLER

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £2-60 plus 45p post & VAT. Made up model also available.

NEED A SPECIAL SWITCH

Double Leaf Contact. Very slight pressure closes both contacts 12p each. Plastic pushrod suitable for operating. 10p each. 10 for 68p.

1 R.P.M. MOTOR + GEAR BOX

Made by the famous Chamberlain & Hookham Ltd. These could be made to drive clock or similar. Really robust reliable unit. Price £1-50 + 30p Post & VAT

MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole, 6 way—1 pole, 12 way. All at 38p + 15p post & VAT each.

MULTI-SPEED MOTOR

Six speeds available 500, 850 and 1,100 r.p.m. and 8,000, 12,000 and 15,500 r.p.m. Shaft is 1 in. diameter and approximately 1 in. long. 230/240v. Its speed may be further controlled with the use of our Thyristor controller. Very powerful and useful motor size approx. 2 in. dia x 5 in. long. Price £1-40 + 45p post & VAT.

SLIDE SWITCHES

Slide Switch, 2-pole changeover panel mounting by 2 x 6B.A. screws. Size approx. 1 1/2 in. x 1 in. rated 250V lamp. 15p + 7p post & VAT.
 Sub Miniature Slide Switch, DPDT 10mm (1 in. approx.) between fixing centres. 25p + 9p post & VAT each or 10 for £1-90. SP Change over spring return 250V 1 amp. 25p + 8p post & VAT.

6 DIGIT COUNTER

Resettable. 440 ohm coil up to 25 impulses per second. Ex-equipment but guaranteed perfect. £3-30 + 40p Post & VAT each.
 1 digit counter as specified for telephone charge calculator 93p.

PRESSURE SWITCH

Containing a 15 amp change over switch operated by a diaphragm which in turn is operated by air pressure through a small metal tube. The operating pressure is adjustable but is set to operate in approx. 10in. of water. These are quite low pressure devices and can in fact be operated simply by blowing into the inlet tube. Original use was for washing machine to turn off water when tub has reached correct level but no doubt has many other applications £2-10 each + 25p post & VAT.

TELESCOPIC AERIAL

for portable, car radio or transmitter. Chrome plated—six sections, extends from 7 1/2 to 47 in. 50p + 15p Post & VAT.

KNUCKLED MODEL FOR P.M. 80p + 17p Post & VAT.

LIGHT DIMMER KIT

For dimming up to 250w without heat sink or 750w with heat sink. This comprises quadric variable control potentiometer, condenser, resistors, tag strip for mounting and data. Price £1-95 + 30p Post & VAT.

RELAY BARGAIN

Type 600 relay, 2 changeover one open and one closed contact. Twin 500 ohm coils make this suitable for closing off DC 6v, DC 12v, DC 24v or AC mains using resistor and rectifier. 40p each. Resistor and rectifier 20p extra... and Post VAT 80p.

TERMS

CASH DISCOUNTS

25% on order over £500, 20% over £100, 15%, 10%, 5%.

SMALL ORDERS

Please add 30p if order under £25.

LARGE ORDERS

Deduct discounts as follows: £30-£50 deduct 10%; £60-£100 deduct 15%; £100-£499 deduct 20%; over £500 deduct 25%.

SWITCH TRIGGER MATS

So thin is undetectable under carpet but will switch on with slightest pressure. For burglar alarms, shop doors, etc. 24in x 18in £1-90. Post & VAT 30p.
 13in x 6in £1-50. Post & VAT 25p.



SMITHS CENTRAL HEATING CONTROLLER

Push button gives 10 variations as follows:—(1) continuous hot water and continuous central heating (2) continuous hot water but central heating off at night (3) continuous hot water but central heating only for 2 periods during the day (4) hot water and central heating both on but day time only (5) hot water all day but central heating only for 2 periods during the day (6) hot water and central heating on during the day time only—then for summer time use with central heating off (7) hot water continuous (8) hot water day time only (9) hot water twice daily (10) everything off. A handsome looking unit with 24 hour movement and the switches and other parts necessary to select the desired programme of heating. Supplied complete with wiring diagram. Originally sold, we believe, at over £15—we offer these, while stocks last, at £8-95 each, VAT & Postage 85p each.

WALL THERMOSTATS (SMITHS)

Wall mounting and in a handsome plastic case. (Cream and beige). Adjustable by slider (lockable) and may be set to control temperatures from around freezing through to 50°C. The slide panel is engraved and indicates (frost), (warm), (very warm), etc. The thermostat will control heaters, etc., up to 15 amp at normal mains voltage and is ideal for living room, bedroom and greenhouse, etc. Price £1-95. VAT & Postage 30p. Don't miss this.

AUDIO AMPLIFIER

Part of the famous Reditude background music system, secondhand, but believed in good order. However, no guarantee; we are selling for spare-value only. These are 6 valve amplifiers, the output valves are 2 x EL 84 in push/pull, complete with mains transformer, rectifier and simple smoothing equipment. The mains transformer alone, today would cost at least £4. Size is 9 1/2" x 5 1/2" x 4 1/2". Price only £2-00 + postage and VAT £1-50.

15A ELECTRICAL PROGRAMMER

Learn in your sleep! Have radio playing and kettle boiling as you awake—switch on lights to ward off intruders—have a warm house to come home to. All these and many other things you can do if you invest in an electrical programmer. Clock by famous maker with 15 amp, on/off switch. Switch-on time can be set anywhere to stay on up to 6 hours. Indispensable for family memory jogger. A beautiful unit. Price £2-95. VAT & Postage 60p, or with glass front, chrome bezel, £1-50 extra.

SHORTWAVE CRYSTAL SET

Although this uses no battery it gives really amazing results. You will receive an amazing assortment of stations over the 19, 25, 31, 39 metre bands—Kit contains chassis front panel and all the parts. £1-50—crystal ear-phone 55p. VAT & Postage 75p.

THIS MONTH'S SNIP

Smiths 24 hr. timer heart, really the "Autoset" without its plastic case. This is a 24 hr. twice on, twice off, clock switch which will repeat until re-programmed. Switches rated at 15 amps. Limited supplies—£3.95 VAT & post 55p. each.

12 VOLT 1 1/2 AMP POWER PACK

This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 mfd smoothing. Price £3-75 plus VAT and Post £1.

Heavy Duty Mains Power Pack. Output voltage adjustable from 15-40V in steps—maximum load 250W—that is from 6 amp at 40V to 15 amp at 15V. This really is a high power heavy duty unit with dozens of workshop uses. Output voltage adjustment is very quick—simply interchange push on leads. Silicon rectifiers and smoothing by 3-000uF. Price £10-50 plus £25 VAT & post.

TANGENTIAL HEATER UNIT

This heater unit is most efficient, and quiet running. Is as fitted in Hoover and blower heaters—costing £15 and more. Comprises motor, impeller, 2kW element and 1kW element allowing switching 1, 2 and 3kW and with thermal safety cut-out. Can be fitted into any metal cabinet. Only needs control switch. £5-82 plus VAT post £1. 2kW Model as above except 2kW £4-25 plus VAT & post 75p. Don't miss this. Control Switch 44p, P. & P. 40p.

INSTANT START FLUORESCENT LIGHTING BARGAINS

Starterless control gear, complete with tube ends and tube clips for window lighting, signs, fascias, etc. 4 ft. 40w. £1-90; 5 ft. 65w. £2-00; 6 ft. 80w. £2-20; 6 ft. 80w. £2-45; and for pairs as follows:—twin 2 ft. 20w. £2-55; twin 3 ft. 30w. £3-55; twin 4 ft. 40w. £3-25; twin 5 ft. 65w. £3-25; twin 5 ft. 80w. £3-95; twin 8 ft. 125w. £5-75. These are about one half of maker's current prices and can't be repeated once stocks are cleared. Please add 30p per piece to cover postage or carriage and 8% VAT.

MAINS TRANSFORMERS

All standard 230-250 volt primaries.	£ p
1v	1 amp (special) 1-75
2-4v	5 amp
6-8v	2 amp
6-3v	3 amp
9v	1 amp
9v	3-5 amp
12v	1 1/2 amp
12v	1 amp
6-5v-0-6 5v	1 amp
18v	1 amp
24v	2 amp
24v	3 amp
12-0-12v	50mA
6-0-6v	50mA
8-0-8v	1 amp
18v-0-18v	2 amps
25v	1 1/2 amp
50v 2 amp & 6-3v	1 amp
60v 5 amp & 5v	1 amp
27v	8 amp
30v	37 amp
80v tapped 75v & 70v	4 amp
230v-0-230v & 6-3v	15 amps
275-0-275v at 90mA & 6-4v	3 amps
EHT Transformer 5000v	23mA
.....	(intermittent) 5-50

Charger Transformers

6v and 12v

6v and 12v

6v and 12v

Add 30p per piece to cover postage and VAT 25%.

ONLY £1-50 FOR SEVEN ELECTRIC MOTORS



7 powerful batt. motors—used in racing cars & power models. Output & types vary for use in hundreds of different projects—Tools, toys, models, etc. All brand new reversible & for 1 1/2-12v. batts. Wiring diag. inc. VAT & Post 40p. FREE plan for min. power station.

BLACK LIGHT

As used in discotheques and for stage effects, etc. Virtually no white light appears until the rays impinge on luminescent paint or white shirts, etc. We offer 9" 6w tubes complete with starter, choke, lamp-holder and starter-holder. Price £2-75 + 30p post. Tubes only £2. Post & VAT 60p.

MULLARD AUDIO AMPLIFIERS

All in module form, each ready built complete with heat sink and connection tags, data supplied.
 Model 1153 500mW power output £1-10 + 40p post & VAT.
 Model 1172 1W power output £1-35 + 45p post & VAT.
 Model EP9000 4 watt power output £2-40 + 40p post & VAT.
 E1 9001 twin channel or stereo pre amp. £2-50 + 50p post & VAT.

LIGHT SWITCH

Automatically switches on lights at dusk and off at dawn. Can also be used where light and dark is a convenient way to start and stop an operation. Requires only a pair of wires to the normal switch. In bakelite box, normal switch-plate size. 1 amp model £3-75. VAT and Postage 50p.

MAINS TRANSISTOR PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v, 9v, 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP2, PP4, PP6, PP7, PP9 and others. Kit comprises: main transformer, rectifier, smoothing and load resistor condensers and Instructions. Real snip at only £1-50. VAT & Postage 80p.

SOUND TO LIGHT UNIT

Add colour or white light to your amplifier. Will operate 1, 2 or 3 lamps (maximum 450w). Unit in Box all ready to work. £7-95 plus 85p VAT and postage.

MAINS MOTOR

Precision made — used in record decks and tapes recorders—ideal also for extractor fans, blower, heaters, etc. New and perfect. Snip at 85p + VAT & Postage 20p. Postage 20p for first one then 10p for each one ordered.
 1 1/2" stackmotor £1-25 + VAT & Postage 25p.
 1 1/4" stackmotor £1-50 + VAT & Postage 30p.

EXTRACTOR FAN

Cleans the air at the rate of 10,000 cubic ft. per hour. Suitable for kitchens, bathrooms, factories, changing rooms, etc. It's so quiet it can hardly be heard. Compact, 3 1/2" casing with 5 1/2" fan blades. Kit comprises motor, fan blades, sheet steel casing, pull switch, mains connector and fixing brackets. £4-25 VAT & Postage £1-50.

J. BULL (ELECTRICAL) LTD.

(Dep. P.W.) 103 TAMWORTH ROAD, CROYDON CRO IXX

FULL SPEC. LED'S

Packs of 5—inc clips & data

	1/25" lens	1/8" lens	1/4" lens
RED	£0.75	£0.75	£0.75
GREEN	£1.20	£1.20	£1.20
YELLOW	£1.20	£1.20	£1.20
ORANGE	£1.20	£1.20	£1.20

ECONOMY QUALITY LED'S
MIXED BAGS ALL COLOURS OF ALL SIZES—
IDEAL FOR EXPERIMENTS

50—£5
100—£9

FULL SPEC LED SEVEN SEGMENT DISPLAYS

0.3" COMMON ANODE
L.H. DECIMAL
RED, GREEN, YELLOW
£1.35 ea inc data



ECONOMY QUALITY

0.3" COMMON ANODE—L.H. Dec. RED 73p ea.

PLASTIC BOXES— COLOUR GREY



ABS—Ribbed inside on 5mm centres for 1.5mm PCB. Brass Corner inserts for securing top with 3mm screws. 62mm x 112mm x 31mm 1-9 52p ea; 10+ 48p; 120mm x 65mm x 40mm 1-9 66p ea; 10+ 62p ea; 150mm x 80mm x 50mm 1-9 75p ea; 10+ 71p ea.

POLYSTYRENE—PLAIN INSIDE—TOP SECURED BY SELF TAPPING SCREWS
61mm x 112mm x 31mm 1-9 35p ea, 10+ 32p ea.

SPECIAL OFFER

SAMPLE PACK—4 BOXES—1 ea size £2.10

NEON INDICATORS

150mm lead out wires



Fit 8mm hole and include spire clip for fixing
RED, AMBER, CLEAR, OPAL —19p ea
GREEN —28p ea

TYPE MF

Fits 6.4mm hole—nut fixing
RED, AMBER, CLEAR, OPAL —22p ea

LAMPHOLDER DH



Takes either LES (with adaptor provided) or MIDGET FLANGE BULBS.
Fits 13mm hole—nut fixing
RED, BLUE, GREEN, AMBER, CLEAR, OPAL.
ORANGE 25p ea (bulbs not provided)

QUOTATIONS FOR LARGER QUANTITIES ON REQUEST. ALL PRICES INCLUDE VAT AT 8% ORDERS UNDER £5 please add 15p P & P ORDERS OVER £5 P & P free. TERMS—CWO

**MICHAEL WILLIAMS
ELECTRONICS**

47 Vicarage Avenue,
Cheshire Hulme, Cheshire SK8 6JP

ALL
6p/sqin

FREE
Brochure
on New
KITS

PCB'S

Whether professional, student, teacher or amateur, the field of electronics can open up a new world for you.



CROFTON don't just sell kits, we offer you a technical back up service to ensure your success


The following is a selection of some of the more popular kits

- ★ Mullard CCTV Camera
- ★ PE CCTV Camera
- ★ PE Rondo Quadraphonic Four Channel Sound (Designer Approved)
- ★ Electronic Ignition
- ★ Electronic Flash
- ★ P.W. Tele-Tennis Game
- ★ UHF Modulator
- ★ Bench Power Supply
- ★ Wobulator
- ★ All ETI Top Projects
- ★ Many of the Elektor Projects

NOTE PCBs for most published projects available to order

CROFTON ELECTRONICS LTD
Dept B 124 Colne Road Twickenham, Middx O1 898 1569

4-STATION INTERCOM

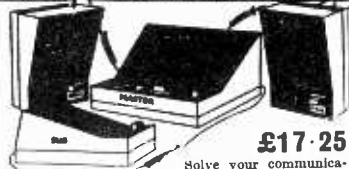

£17.25

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals and Office. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 6ft. and other accessories. P. & F. 70p.

MAINS INTERCOM NEW MODEL
No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £31.24 per pair P. & F. 70p.

NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



ONLY £12.95

VAT £1.04

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/Off switch, volume. Direct tape recording model at £13.95 + VAT £1.12 P. & F. 70p, 10-day price refund guarantee.

WEST LONDON DIRECT SUPPLIES (PW11)
169 KENSINGTON HIGH STREET, LONDON, W8

PRECISION PETITE LTD.


119A HIGH STREET,
TEDDINGTON TW11 8HG

Tel. 01-977-0878

INTRODUCING A
MINIATURE
PRECISION 12V. D.C.
DRILL DESIGNED FOR
THE ELECTRONIC
ENGINEER



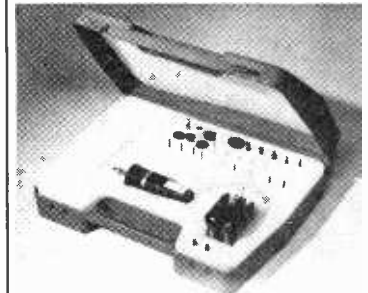Drill only £7.00 p.p. 35p
Stand £3.75 p.p. 58p



Complete kit as illustrated (less batts.) with a variety of 30 tools. Space for Stand and Transformer.

KIT 30 TOOLS £15.01 p.p. 75p
STAND £3.76 p.p. 58p
TRANSFORMER £5.50 p.p. 75p

**S.A.E. FOR
DETAILS**



BROADCAST BANDS

SHORT WAVE BROADCASTS

by Derek Bell

BEARING out my long-held view that the HAC one-valver is the ideal simple set for the beginner, **Andrew McIntee** from Craichie, by Forfar, in Scotland, opens this month's offering with the logging of New Zealand on 11780 at 0900. This is only a 7.5 kW station and to pull it on the HAC is worthy of a round of applause at least. Andrew does admit though that he has a 180ft long wire aerial and has fitted an ATU. Speaking of which, I hear that one of the advertisers in PW is testing a new aerial tuning unit and if it is a success it will be launched in the near future. I have no news on the price as yet but will keep you informed.

This month certainly seems to be rich in unusual loggings, it must be the revivification caused by the summer holidays! This is evidenced by **John Spinks** of Great Moulton, Norfolk who, using his Trio and the old faithful Joystick on the garage roof, he has pulled in the following:—

Radio Bolivar on 4770 at 0120
Radio Bucaramanga on 4845 at 0115
Kinshasa, Zaire on 4880 at 2150
Radio Yaounde, Cameroon on 4972 at 2140
Sibu, Sarawak on 5005 at 2215

In fact John's complete log contains a fistfull of very rarely reported stations and even had me trying for a few of them, nice work, John! **Robert Hill** of Crewe is off to Portugal for his holidays, a little late perhaps but he found time to drop us a line logging ELWA Liberia on 11895 at 0920. Aside from cramming for the dreaded 'A' levels Robert has fitted a reel-to-reel tape recorder to his Invicta 8027 and seems to be set fair to record some station ID's in order to refresh his memory, if need be.

Another old friend of ours is **John Higginbotham** of Holyhead and this worthy gentleman sent a long amusing letter regarding his domestic set-up. It seems that he has the same problem that many DXers face, namely, where to put all the bits and pieces! John says that his mother was "fed up with the bedroom looking like a workshop". Thus it is that he has moved into a garden shed. Fine on the shed John, but remember that radios in the main are precision instruments and do not take kindly to damp.

The best thing to do is to keep the sharpest of eyes on the humidity and try to beg, borrow or steal some form of heating. Thanks to this column John has pulled Radio Afghanistan on 15195 at 1130. He also QSL'd Pekin and the score to date on replies is as follows:— One calendar, two books, seventeen(!) magazines, two QSL cards, three skeds, three report forms and one notebook! Personally I can't see what they hope to achieve but they still keep sending out all this literature.

Two writers this month focus the spotlight on Radio Mexico. **Harold Emblem** from Mirfield, Yorks reports them testing on 15285 at 2205 while **Jonathan Marks** of Norwich writes that on 15125 they were asking in English and French for reports at 2258 while 2309 the language changed to Spanish. This indicates to me that they are trying to establish themselves in Europe in competition with Radio Nacional de Brazil. They asked for reports, without IRCs, to be sent to Radio Mexico, PO Box 20/620, Mexico City, Mexico and promise that accurate reports will get a Radio Mexico pennant.

Another address for QSLs comes from **Chris Clarke** of Shipdam who passes on the info that the American religious station WYFR asks for reception reports to be sent to Family Radio, Oakland, California, N 4621 U.S.A. Far across the Indian Ocean both India and Sri Lanka broadcast to their citizens in other lands. One person who reports them is **P. K. Gulati** of Guildford who sends the loggings of Air Delhi on 1110 and 7150 at 1900 plus Radio Sri Lanka on 1200 at 1730.

The popular question of QSL cards is raised by **Jeremy Hinton** who hails from Newcastle, Staffs. He asks what is the average time for a reply? Well Jeremy, this all depends on the station and its eagerness to maintain good relations with its audience. I will not deny that some stations lose reports or are plain lazy, and recently some American DXers got their replies back after ten years! You mentioned, Jeremy, that Radio Nederland refused you a QSL because you omitted to report the frequency. These details are important to the engineers in order that they can judge if their signal is reaching the target area.

A very welcome letter comes from Malta and asks if the writer is justified in sending reports to PW. I regret that I could not decipher the name but I believe it to be **Vincent Canabatt**. Well, Vincent your part of the world is very rich in transmitters and if you can hear them then there is a very good chance that we in the UK will. PW is read in a good many countries overseas and your tips will help them a lot. All that is needed is to write the station name, frequency, and time in GMT. It is also of interest



if you include any unusual details such as addresses or any news of future events that the station may broadcast.

There has been a very heavy post so inevitably many letters have to be left out, so to the writers I can only apologise and say 'keep trying' and to everyone wish best 73s and so close the column for this month.

AMATEUR BANDS

by Eric Dowdeswell G4AR

I am very glad to notice, in the various amateur radio magazines, an upsurge in operating using quite low power. As one would expect, those who try this very interesting work usually get quite a kick out of working stations thousands of miles away when using milliwatts of power and ordinary receiving type transistors. The work is virtually all on CW and the point in mentioning it is to ask those of you who are interested in copying code to have a look at the LF ends of the various bands for those chaps calling 'CQ QRP'.

Needless to say, one can spend a lot of time calling without getting a reply so, for a change, these stations would probably welcome reports from listeners. CQ Magazine runs a regular feature on QRP work which makes very intriguing reading! With the widespread abuse of licence power limitations in various countries it is good to hear of those who have gone in the opposite direction! Let us hope it will be a continuing trend.

The summer hang-up is really showing now with relatively few reports coming in. Readers are no doubt taking every advantage of the sub-tropical weather we have been enjoying for so long. Let's hope they are building up a great reserve of strength for the forthcoming DX season which will be quite tough with the bottom of the sunspot cycle not yet reached.

Fortunately, Paul Barker (Sunderland) has kept his nose to the grindstone possibly due to the added incentive of being able to watch slow-scan TV. 'Catch of the Month' for Paul was 9X5AV on 20m SSTV but for sheer excellent picture quality Paul gives full marks to DL7DE in Berlin. (Marks—oh dear!) Paul points out that prefix C9 is now being used in place of the old CR7 reporting C9MIC as active in this strife-torn country. He also notes YR as a special prefix for Rumania but if I went to my very ancient collection of QSL cards I could find one showing YR as the old prefix used by that country! I think someone once said something about "all is change but nothing changes".

Mike Bennett (Slough) didn't mention too many catches but all are very much worth while, such as C21NI on Nauru and FP0YY on St. Pierre and

Michelon and the Mount Athos DXpedition SV1GA/A. Jeremy Hinton A8962 (Newcastle, Staffs) had trouble with his Trio 9R59DS, which I hope I have been able to straighten out, so his log is very short this month. Back to Mike Bennett who sends some info on changes to licensing areas in PY land, too long to publish, but first suffix Z indicates a foreign operator such as PYIZAA while similar suffixes W, X or Y indicate a novice licence. Just in case you ever hear one operating car mobile, his call will add /MT!

Although Neil Whiteside has been on holiday with a 160m receiver in Dorset, away from his usual QTH in Hitchin, I am sorry to say he allowed local attractions to divert him from amateur radio! Let's hope he has got back on to the straight and narrow by now!

Ian Jay (Mansfield) has really got the knack now of only listing those stations of real interest including VP2 and ZL2 on 40m SSB. Tim Charles (Colchester) apologises for lack of a log last month but his excuse is 'great changes going on in the shack', which, I suppose, is fair enough! Main receiver is now a Heathkit GR64 plus a home-built Q multiplier. He tried to flog his CR70A at the Anglian Mobile Rally, without success, but I suspect he will be glad, in the long run, to keep it as a second receiver. Can't have too many of them around the place! Tim quotes latest UK calls issued as G8KMM and G4EHT in the middle of August but there will be many more with their hard-earned bits of paper 'ere you read this.

Stephen Budd A8713 (Worthing) has very wisely erected a Lazy-H beam which he thoroughly recommends. He doesn't mention its size but if it has 66ft centre-fed elements then it is a very good performer indeed, with open line feeder and an ATU, for 40m to 10m. The usual problem is getting enough height above earth for the lower elements to be really effective. The bi-directional beam obviously passes through the Pacific because he logs such interesting ones as KB6CU on Canton Is., four KG6's on Guam and KJ6CF on Johnston Is. all of which come into the 'rare' category. That was on 20m SSB but I hope Stephen will try that beam on the other bands in due course.

Log extracts

S. Budd:— 20m HS5AKW KB6CU K1MTJ/KG6 WB4LEE/KG6 KG6JBE KJ6CF KL7BJW KM6EA KS6FF KS6FK ST2SA VR1AT VS5DB ZD8LS

T. Charles:— 40m VK3XB 20m HC5PC JW5NM VR1PE ZL1EGM 2m DB0VR PI3VAD (repeater) SP3BUE

I. Jay:— 40m CO2GS OJ0MA VP2MCT ZL2AGY 80m HZ1AB TR8DG VU2GDG 20m H18MOG SV0WKK (Crete) TG5YN VP2LBR VP2SN VS5DB 5L2FW 7X2BK

N. Whiteside:— 80m 9X5SP 5Z4LW 20m XE1APA KZ5RS

J. Hinton:— 15m A4XFW JY5UNM HI6EA

M. Bennett:— 20m C21NI FB8ZG FP0YY FR7ZW PJ8MS SV1GA/A 15m CX2BE LU6EAU ZP5IL 10m LU5DBA OJ0MA

P. Barker:— 20m C9MIC JA0AXV YR2KBO 7X2BK 7X5AB PV0SH (Singapore) 9V0SN 9Y4HM 20m SSTV DJ9NG DL7DE F3RT 18WAM OH5RM OK2OI 9X5AV

All stations are SSB except those in bold which are CW.

Henry's Radio

LARGEST SELECTION OF ELECTRONIC COMPONENTS AND EQUIPMENT. LOW PRICES—MEAN LESS VAT.

ELECTRONIC COMPONENTS AND EQUIPMENT

More selection—Bigger Stocks for every purpose. Let us quote for your requirements. (Please enclose SAE with all enquiries).

Build the Texan and Stereo FM Tuner

TEXAN 20 + 20 WATTS IC STEREO FM AMPLIFIER

BUILT + TESTED STEREO FM TUNER

Features capacity diode tuning, led & tuning meter indicators, stabilized power supply—mains operated. High performance and sensitivity with unique station indication IC stereo decoder. Overall size in teak sleeve 8" x 2" x 6". Complete kit with sleeve

£26.25 Inc. VAT. BUILT & TESTED £31.20 C & P 50p

Join the large band of happy constructors



Features glass fibre PC board, Gardners low field transformer, 6-IC's 10-transistors plus diodes etc. Designed by Texas Instruments engineers for Henry's and P.W. 1972. Supplied with full chassis work, detailed construction handbook and all necessary parts. Full input & control facilities. Stabilised supply. Overall size 15 1/2" x 2" x 6" mains operated. Free teak sleeve with every kit. £29.95 Inc. VAT. BUILT & TESTED £39.95 C & P 50p



NEW LOW PRICES

SPECIAL OFFER

GARRARD CT4 STEREO CASSETTE TRANSPORT MECHANISM



Features * Stereo Heads * Built in Motor Stabiliser * Auto Stop & Eject * Pause Control * 12V DC Operation

Robust. Precision engineered mechanism based on the "STARR" patented design. Ideal for use in Car stereo cassette players, Hi-Fi stereo cassette recorders, industrial and many other applications. Suitable for the "PW" Ascot Stereo Cassette Deck.

£13.50 inc. VAT. P & P 35p

SINCLAIR MODULES AND KITS

ST80 stereo amplifier £14.05
Audio filter unit £8.17
Z40 15 watt amplifier £8.40
Z60 25 watt amplifier £8.17
PZ5 power supplies for 1 or 2 Z40 £5.73
PZ4 power supplies (STA3) for 1 or 2 Z40 £8.18
Transformer for PZ8 £4.86
FM tuner £14.05
Stereo Decoder £8.35
IC20 power amp kit £9.34
PZ20 power supply for 1 or 2 IC20 £55.88

PACKAGE DEALS

(carr./packg. 35p)
2 x Z40 ST80 PZ5 £29.32
2 x Z60 ST80 PZ6 £32.60
2 x Z60 ST80 PZ8-trans £40.42
805 Kit £42.25

SINCLAIR SPECIAL PURCHASES
* Project 80 stereo preamp £7.94 (p. 20p)
* Project 605 Kit £23.44 (p. 25p)

ALL HENRY'S PRICES ARE NOW INCLUSIVE OF VAT

TAPE HEADS P.P. 15p

Marrlot XRSP/17; Track High £3.50
Marrlot XRSP/18; Track Med. £3.75
Marrlot XRSP/38; Track Med. £7.50
Marrlot XRSP/83; Track High £1.89
Marrlot Erase Heads for XRSP 17/18/36 (XES11) 88p
Marrlot BXIZE34; track erase 81p
R/RPI Record/Play & Track 48p
H/RPI Single Track Rec/Play 48p
Bogen Type U90 Erase £2.50
Miniature Stereo Cassette Rec/Play £2.59

8 DIGIT POCKET ELECTRONIC CALCULATOR

Sinclair Cambridge Built £9.45
Cambridge Kit £4.00
Cambridge Memory £2.50
Built £16.50
Scientific Built £15.00
Scientific Kit £14.00



ELECTRONIC FOOTBALL & TENNIS WITH THE FABULOUS VIDEO SPORT

ON YOUR OWN TV

Play three exciting electronic ball games. FOOTBALL, TENNIS, HOLE IN THE WALL on your own TV! Just plug Video Sport into the aerial socket of your TV and away you go. Completely safe for you, your children and your TV. M's operated. OUR INCREDIBLE PRICE £29.50 Inc. VAT



DEMONSTRATIONS NOW IN ALL CENTRES!

STOP PRESS VIDEO SPORT NOW AVAILABLE AS A KIT. FULL KIT AS PARTS WITH INSTR. ONLY £19.50 C & P 50p

SPECIAL PURCHASE

MULLARD TYPE LP1179 AND LP1171 AM/FM TUNER MODULES

These two modules together form a high quality AM/FM tuner covering the long medium and VHF broadcast bands. Requires only 16 resistors and capacitors and a switch to complete.


Supplied with circuits and spec. data.

LP1179

FM Coverage 87-108 MHz
Bandwidth 300kHz
Selectivity 35dB
Signal to noise at limiting threshold 40dB
Audio output 75mV

LP1171

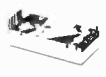AM Bandwidth 6-5kHz
Sensitivity 1mV
Built-in AGC
Supply 6V negative earth
LP1179 and LP1171 £4.80 each or £8.63 pair. C & P 30p. Suitable Ferrite Aerial 83p.



Mullard Modules
LP1157 AM/TYPE £2.88
LP1135 10-7 I.F. Unit £6.81
LP1186 10-7 F/M Tuner £7.31
Gorler Perm. F/M Tuner £5.03

TEST METERS AND TEST EQUIPMENT

THL33 Multimeter
16 Range Multimeter, 2K Ω /V Max current Range 250 mA Loads. Battery and Instr. £8.10

ITI-2 Multimeter
16 Range Multimeter, 20K Ω /V AC/DC volts Ranges to 1000V. Max DC current Range 250mA. Ideal as small testmeter £6.43

AF105 Multimeter
23 Range multimeter, 50K Ω /V. Mirrored scale, overload protection AC/DC Volts Ranges to 1-2KV DC current ranges to 12A Resistance to 100M Ω . Loads. Battery, Instr. & case. £15.75

C1000M Multitester
Compact Test for Batteries, Car Electrics, house wiring etc. 1K Ω /V. £5.08

ICE 680R
Compact Precision multimeter 20K Ω /V 10 fields of measurement and 80 Ranges 1% accuracy. Damped movement. Mirror Scale. Supplied with leads, Accessories and shatterproof case. £19.98

Accessories for 680R
ICE 6603 Electronic Adden Amp £22.68
ICE 682 Transistor & Diode Tester £12.90
HiVoltage Probe £8.42
Temperatures Probe £12.90
Gauss Meter £12.90
Current shunts 5-100A £4.86

Microtest 80
Pocket Precision Multimeter 20K Ω /V 2% Accuracy 40 Ranges, Shatter Proof Case, Mirror Scale Auto-zeroing ohms range £11.88

TE 22 AUDIO GENERATOR
20-200 KHz in 4 bands. Sine and Square output Max output 7V Varlor Dial £25.00

TE 22 AUDIO GENERATOR
SPEC as TE2 £26.50

TE-20D RF SIGNAL GENERATOR
120 KHz—600MHz in 6 bands Internal and External Mod Crystal Calibrator Socket Vernor Dial. Shape as TE22D £23.50

TE40 AC MILLIVOLTMETER
1mV-300V, 1-0Hz-2mHz \pm 1dB. Twin 0-10, 0-3-14 Scale with dB scaling Input Impedance 11M Ω Attenuator calibrated in 10dB steps. £24.30

TE 65 VACUUM TUBE VOLTMETER
6" scale, 1-5-1500V, Resistance Range to 100M Ω . Appearance similar to TE-40 RF22 RF Probe for TE-65 £3.18 HV20 30KV Probe for TE-65 £3.78

TE-15 GRID DIP OSCILLATOR
Absorption Wavemeter 400KHz—280MHz in 6 Ranges Battery operation £21.54

TWO NEW STORES NOW OPEN
If you live in the Midlands come and see our new components section at 94-95 UPPER PARLIAMENT STREET, NOTTINGHAM. Phone Nottingham 42688. Components are back in Tottenham Court Road. Try our new store at 231 TOTTENHAM COURT ROAD. Phone 01-580 3459

625 line receiver UHF transistorised tuners UK operation, Brand new. (Pst/packing 25p each); TYPE A variable tuning. Slow motion drive £3.50

TYPE B 4-button push-button (adjustable) £4.60
TYPE C variable tuning £2.90
TYPE D 6-button UHV/VHF £5.20

EMI SPEAKERS SPECIAL PURCHASE
13in x 8 in chassis speakers. (carr./packing 30p each or 50p pr.) *150 TC 10 watts 8 ohms twin cone £2.53

450A built-in tweeter 8 ohms £4.43
EW 15 watt 8 ohm with tweeter £6.61
350 20 watt 8-15 ohm with tweeter £10.06 each
*Polished wood cabinet £6.00 carr., etc. 35p each or 50p pair.

DMI DIGITAL MULTIMETER

3 1/2 Digit multimeter reading AC & DC Volts and current and Resistance Reads from 1 μ V to 1000V DC (10mA μ resistance) Polarity indicator 1mV to 1000V AC (100K μ to 10M Ω resistance) Resistance from 1 Ω to 10M Ω Working, but may go out of calibration £17.00

Also some not working, with circuits. No Guarantee £6.50

Don't miss your copy of Henry's new Catalogue

* 200 pages with over 5,000 items.
* Dozens of new lines and new ranges.
* A Discount Voucher with every copy, worth 50p.
Send for your copy enclosing 70p remittance.



Henry's Radio

EDGWARE ROAD, W2

Electronic Centres Edgware Road
404-406 Electronic Components & Equipment 01-402 8381
354 Disco, Lighting & High Power Sound 01-402 5854
303 Special Bargain Centre
Also at 94-96 Upper Parliament St., Nottingham.
Nottingham 40403
231 Tottenham Court Road W1 01-636 6688


Phone or call for Best prices Barclay and Access welcome.

LISTEN TO

CODAR®

THE WORLD!

★ **CR70A**

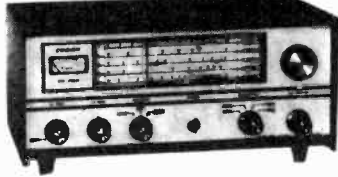

COMMUNICATION RECEIVER

The CODAR CR70A is an outstanding general coverage communication receiver, ideal for the keen S.W.L. It tunes from 540 metres medium through to 10 metres with no gaps. Covers shipping, coastguard and distress frequencies, all six amateur bands 160-10 metres, International broadcast, Met. stations etc. etc. giving world-wide reception. Exclusive features include Air-spaced CODAR-COIL Hi-"Q" Aerial input, illuminated Meter and Slide Rule Scale, Two Speed vernier tuning, Switched B.F.O. for CW/SSB signals. Separate output for Tape recorder. Ready to plug in to 200/240 volts A.C. it only needs your aerial and a 2/3 ohm loudspeaker to bring the world to your finger tips. 12 months full guarantee.

★ **IMPORTANT NOTE**

This fine receiver is not a mass produced item, but each set is hand built to your order, individually checked and air tested. Please allow for this when ordering—your delivery date will be shown on your receipt, sent by return.

• Special discounts for Educational Authorities and Senior Citizens.




"Free Gift!! Claim your Codar ball-point pen free with your next order!!"



★ **MADE TO ORDER!**

£39.00! (carr. free) + VAT **£9.75**

★ **P.R.40** ★

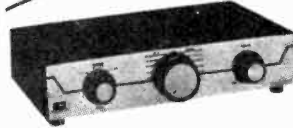


£11.00! (carr. free) + VAT **£2.75**

R.F. PRESELECTOR

The PR40 R.F. Preselector is the solid state version of the world famous PR30 which is now superseded. It employs Silicon "N" Channel FET (Field Effect Transistor) front end followed by silicon NPN Broad Band R.F. Amp., and will substantially improve receiver performance over the range 1.5 to 35 MHz, providing a considerable increase in gain up to an overall average of 30dB, with improved image rejection and noise ratio. Supplied complete with co-ax plug (less standard 9 volt PP6 Battery). 12 months Guarantee ...

MULTIBAND-6 ★

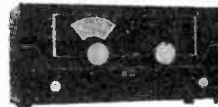

SHORT WAVE RECEIVER KIT

£16.56! (carr. free) + VAT **£4.14**

All transistor T.I.F. Receiver tunes 550 KHz to 30 MHz (540 to 10 metres) complete coverage—no gaps. Medium waves—Trawlers—Ship/Shore Telephone—All Six Amateur Bands, 160-10 metres—International Broadcast from Australia, Far East, Russia, USA etc. using 4 miniature plug in Coils. Hi-Gain FET Regen. Det./AF/AF Module giving full loudspeaker output to any external 2/3 ohm speaker. Receives AM/CW/SSB. Separate Electrical Bandspeed, Calibrated Main Tuning. A Quality CODAR-KIT with 12 months Guarantee. No technical knowledge required, simple to build, printed circuit and Pictorial Instruction Manual. Fully detailed step by step. Complete Kit with 4 Coils (less standard PP6 battery).

CODAR

NEW! AVAILABLE SOON!!
THE MINI-CLIPPER STARTER KIT. ALL SOLID STATE SHORT WAVE RECEIVER, ALSO SUPER HI-"Q" A.T.U.

VALCON WORKS · BURRELL BUILDINGS · CHURCHILL INDUSTRIAL ESTATE · LANCING · SUSSEX

WORLD-WIDE MAIL ORDER—EXPORT QUOTES FREE.

Tel: LANCING 61901


BN15 - 8TZ

TRAMPUS

Electronics Ltd.
WINDSOR, BERKS
58/60 GROVE RD.
SEND C.W.O. ADD VAT TO ALL PRICES IN U.K. P&P 15p. EXPORTS 60p.

MONEY BACK IF NOT SATISFIED.
LARGE STOCKS, LOW PRICES.
ALL BRAND NEW TOP GRADE FULL SPEC DEVICES. CALLERS WELCOME. CATALOGUE/LIST FREE SEND 80p. BARCLAYCARD & ACCESS * POST.

Digital Displays

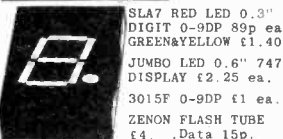

LEDS red 13p

LEDS 209 STYLE ONLY 13p ea
TTL 209 WITH CLIP RED 15p ea
TTL 211 & CLIP GREEN 29p ea
LARGE 0.2" CLIP RED 17p ea
LARGE 0.2" CLIP GREEN 30p ea
209 STYLE OR 2" ORANGE 29p ea
INFRA RED LED £1.2N5777 33p.

PHOTO IC 81p

TEC12 PHOTO AMP/SCMITT/RELAY DRIVER or LED TTL INTERFACE 81p

FLUORESCENT LIGHTS 12V MADE IN UK
8 WATT 13" £3. 13W 22" £3.50

DIGITAL CLOCK

IC AY51224 4 DIGIT CLOCK £3.75
MC5311/4 6 DIGIT CLOCK £7

CASSETTE mechanics £13.75

NEW 8tk CARTRIDGE MECHANISM £8
STEREO CASSETTE MECHANISM £13.75
Suitable for "PW ASCOT" recorder with heads etc. SEND 15p for DATA

INTEGRATED CIRCUITS

709 D114 29p	LM377 2x2W£2.87
555 TIMER 54p	LM380 2W AF 89p
703 RF/1F 28p	LM381 2kPre £2
709 T099 23p	LM3900 4xOPA69p
709 D1L 14 28p	MC1303 £1.20
710 D1L 14 34p	MC1306 49p
723 Reg. 54p	MC1310ALED£2.96
741 D1L 8 27p	MC1312 SQ £2.10
741 D1L 14 29p	MC1330 69p
741 T099 29p	MC1339 2kPre £1
747 2x741 70p	MC1350 55p
748 D1L 8 33p	NE536 fetOPA £2
7805 5V £1.40	NE540 Driver £1
7812 & 15 £1.40	NE550 2vRef 79p
76013 6W AF £1	NE555 Timer 55p
8038 SIG GEN £3	NE556 2x £1.20
CA3028 £1	NE560 PLL £3.15
CA3048 55p	NE561 PLL £3.15
CA3048 £2	NE562 PLL £3.19
CA3052 £1.50	NE565 PLL £2.69
CA3054 £1	SN72709 709 28p
LM300 2-20V £2	SN72741 741 26p
LM301 OPA 45p	SN72748 748 33p
LM304 0-40V £3	SN76660 IF £1.25
LM307 OPA 49p	SN76611 IF£1.25
LM308 HiBo 95p	TAD110 & IF £2
LM309 5V £1.48	TBA810 7WAF 99p
LM372 IF £1.80	ZN414 RX £1.08

SPECIAL OFFERS

2N3055 FULL HIGH SPEC 115W 37p
741C 8PIN DIL 27p. MFC4000B 33p
NE555 TIMER 55p. ZN414 RX £1.09
BC109 9p. 2N3819e 16p. BFY51 15p

740 TTL

7400 GATES 13p	7473/74/76 29p
7404 INVERT 17p	7475 45p
7401/2/10etc14p	7490 52p
7413 SCMITT 31p	7491 2/3/4 39p
7440 BUFFER 14p	74100 74175 £1
7447 DRIVER 89p	74121 32p
7470 & 7472 29p	74123 59p
	74141 (&7441) 73p

TRANSISTORS & DIODES

Price each	MATCHING	16p	
AC127 & 128 16p	INS. BUSH SET10p		
AC187 & 188 19p	TIP 41	70p	
AD149 43p	TIP 42	89p	
AD161 & 162 33p	TIP 2955	90p	
BC107 & 108 9p	TIP 3055	55p	
BC109 10p			
BC147/8/9 10p	TS1543 see 2N2866		
BC157/8/9 12p	ZTX109&301	13p	
BC167/8/9 12p	1N4001	4p	
BC177/8/9 18p	1N4004 & 7	7p	
BC182/3/4&4L10p	1N4148 & 914	4p	
BC212/3/4&4L11p	2N697	14p	
BCY70 1/2 17p	2N706&8	11p	
BD131 & 132 39p	2N2646 UJT	32p	
BFR51	2N2904 & 5	20p	
BFR50/51 23p	2N2926 POK	9p	
BFR88 250V 29p	2N3053	17p	
BFY50/1/2 15p	2N3055 115W	37p	
	2N3563 & 64	16p	
	2N3614	49p	
	2N3702 & 3	9p	
	2N3704 & 5	10p	
	MJE3055	65p	
	2N3708 & 9	8p	
	2N3710 & 11	10p	
	2N3819E FET	16p	
	TIP 29 & 30 52p	2N3823E FET	17p
	TIP 31 & 32 69p	2N3904/5/6	15p

FULL SELECTION IN OUR FREE LISTS.

NEW TRAMPUS FULL SPEC PAKS

PAK A 10 RED LEDS our choice	£1
PAK B 4 741 OP AMP	£1
PAK C 4 2N3055 I.D 12 BC109	£1
PAK E 10 BC182 I.F 11 2N3704	£1
PAK G 8 BFY51 I.K 9 2N3819e	£1
PAK J 9 2N3053 I.K 4 1N914	£1

BZY88 400mW	1A/50V SCR	36p
ZENER DIODES 9p	TAG1/400	55p
BRIDGE RECT	C106 & 7 SCR	D1
1A 50V	1A/400V	53p
BR100 DIAC	SC146D TRIAC	
	10A 400V	75p

VERO

VERO PINSx36 28p.
COPPER CLAD VEROBOARD 0.1"
24"x5" 29p 24x3" 26p. 31x3" 31p.
31"x5" 31p 31x 17" £1.50
DIL IC's BOARDS 6x4" £1.50
24 way edge connector 60p.
36 way 90p. PLAIN 31"x17" £1.
FACE CUTTER 45p, PEC ETCH PAK 50p

DALopen69p

PRINTED CIRCUIT BOARD KIT £1.69
DECON NO MESS ETCH PAK NEW 69p
DECON DESOLDER BRAID REEL 50p

HEATSINKS

5F/705 & 18F/7018 5p ea. TV4 15p.
TV3/703 16p. EXTRUDED 4" 4Y1 29p.
TG308 GAS DETECTOR £1.80 ea.
LOGIC PROBE TTL TESTER PEN £5

CAPACITORS

CERAMIC 22pf to 0.1uf 50v 5p.
ELECTROLYTIC: 10/50/100 uf in
10v 5p. 25v 6p. 50v 8p. 2uf/10v 5p.
100uf/25v 18p. 200/500 25v 9p.

POTENTIOMETERS (POTS) AB or EGIN

LIN or LOG ROTARY 13p. SWITCH 14p
DUAL 45p. SLIDERS 29p. STEREO 57p
KNOBS 7p. PRESETS 6p. RESISTORS 14p
SWITCHES: SPST 12p. DPDT 25p.

DIN PLUGS ALL 12p. SOCKETS 10p.
ALL CASES AB5/AB7 50p. AB13 65p.
TRANSFORMERS 1A 6v6v or 12v12v
Only £1.34. 100ma type CT 75p.

OIL sockets

TEXAS GOLD ea
LOW PROFILE
8, 14, & 16 PIN 13p
SOLDERCON STRIPS:
100 PINS 50p. 1K £3.



MEDIUM WAVE DX

by CHARLES MOLLOY

NORTH AMERICAN medium wave stations are often heard here in the UK. A path of darkness between transmitter and receiver is required for medium wave propagation and this occurs to North America some five to six hours after sunset in the UK. During the winter months Canadians can be heard as early as 2300, to be followed an hour later by outlets situated on the eastern seaboard of the United States. North Americans operate on channels spaced 10kHz apart and they are allocated call signs which are used frequently as a means of identification, followed by the city or town where the studios are located. Listen on 930kHz for CJON St. John's in Newfoundland. It is the most consistent North American, its time zone is 3½ hours behind GMT and it can be found on the low frequency side of AFN Berlin on 935kHz.

Other Canadians which are heard regularly when conditions are favourable are CBN St. John's on 640kHz; CHER Sydney, Nova Scotia on 950kHz; CBA Moncton, New Brunswick on 1070kHz. Broadcasts from the United States to look for are WABC on 770kHz, WINS on 1010kHz and WNEW on 1130kHz, all in New York City; WIIDH on 850kHz in Boston on 850kHz and WCAU in Philadelphia on 1210kHz.

Steve Whitt (London) reports "I can't wait for winter DX conditions to test my loop aerial and I'm looking forward to a batch of North American goodies". Steven is now using the PW medium wave loop aerial and balanced FET pre-amplifier (April 1973) with his Chapman SGBS communications receiver and he reckons this aerial is far better, more sensitive and more directional, than his 30ft longwire on the roof. Stations logged on this new set-up include Radio Andorra on 701kHz, Radio Dakar in Senegal on 764kHz and CJON St. John's Newfoundland on 930kHz, three continents!

Harold Emblem sends a really outstanding log of summer DX heard at his QTH in Mirfield, Yorkshire, on an Eddystone 730/4 communications receiver using a long wire and a medium wave loop. DX heard includes CBT Grand Falls, Newfoundland on 540kHz; CKVO Clarenville, Nfld on 710kHz; CBNM Marystown, Nfld on 740kHz; WABC New York City on 770kHz; CBH Halifax, Nova Scotia on 860kHz; CJCH in Halifax on 920kHz; CBM Montreal on 940kHz; CHNS Halifax on 960kHz; WINS New York City on 1010kHz; WNEW also in NYC on 1130kHz; WCAU Philadelphia 1210kHz; CKEC New Glasgow, N.S. 1320kHz; WLAC Nashville, Tennessee on 1510kHz and WKBW in Buffalo, N.Y. on 1520kHz.

Peter Bowyer (Kettering) uses a Murphy A168 for DXing on the medium waves and reports hearing AFN Augsburg and Radio Tirana, Albania both on 1394kHz and Trans World Radio, Montecarlo on 1466kHz. Fifteen-year-old Stephen Boyle of Auchterarder, Perthshire used a Philips 90RL210 with an externally mounted MW loop. Stations logged include Radio Norway on 1578kHz (in English at midnight GMT) and Radio Tirana, Albania on 1394kHz again.

Joseph Bite (Dublin) and Derek Vivian (Jersey C.I.) ask which type of receiver is the most suitable for MW DXing. Communications receivers such as the Trio 9R59DS, AR88, CR100 or the Heathkit GR78 (which operates from batteries or mains) have the sensitivity and selectivity that will bring optimum results. Simpler receivers when connected to a good aerial will, however, pull in a considerable amount of DX on the medium waves.

BROADCAST BANDS

Short Wave reports by the 15th of the month to Derek Bell c/o Practical Wireless, Fleetway House, Farringdon Street, London, EC4A 4AD.

Medium Wave Logs to Charles Molloy, 132 Segars Lane, Southport, PR8 3JG.

AMATEUR BANDS

Logs covering any amateur band/s in band/alphabetical order by the end of the month to Eric Dowdeswell G4AR, Silver Firs, Leatherhead Road, Ashted, Surrey, KT21 2TW.

CQ! CQ! CQ! CQ!

ISSUES WANTED

..Television for March, April, May, June 1974.—R. Mehrotra, F-114 D.D.A. Colony, Naraina, New Delhi-28, 110028, India.

..August 1973 Issue of P.W.—T. J. Flanagan, 17 Addison Crescent, Old Trafford, Manchester, M16 0WN.

..January to April 1973 P.W. Inclusive also June 1973 and March and April 1974 P.W.—K. Hunter, 31 Cwmbath Road, Morrision, Swansea, SA6 7BA.

..1950 March, November, December. 1952 January March, April, August, September. 1953 May—all Practical Wireless.—J. Luxton, Bergheim, Battery Hill, Fairlight, Hastings, TN35 4AP.

..P.W. for February 1974, February 1966, April 1969 and June 1969 plus any subsequent issues dealing with aerials, April 1970, June 1970 plus any subsequent issues dealing with the LF Bands Transceiver, April 1972. Also P.E. for

April 1965 and February 1966.—S. A. Rizvi, P.O. Box 2671 Tripoli, Libya.

..December 1970 and January 1971 issues of P.W.—J. M. Bell, 60 Wendover Road, Harlesden, London, NW10.

..all issues of P.W. including December 1971.—B. Disselmann, Skovlyporten 3-1, DK-2840, Holte, Denmark.

..issues of P.W. or the circuits of the P.W. Sound Effects Synthesiser first published in March 1971 (circuits 3-11 wanted).—D. Weeks, S.A.C., K8093975, GESF, R.A.F. Wildenrath, B.F.P.O. 42.

..any back issues of Practical Wireless, Television.—Craig Sellen, Box 853, Wayne, N.J. 07470, U.S.A.

..issues of P.W. containing instructions of the VHF Transistor Receiver with blueprint (around July 1965).—J. W. Cooling, 33 Flat Sorrel Court, 1 The Green, Mt. Sorrel, Leicestershire.

..P.W. May 1971—J. Rendall, 59 Hood Avenue, Southgate, London, N14 4QJ.

..P.W. January 1972 to October 1972 Inclusive, P.W. March 1973—June 1973 inclusive and P.W. October 1973.—G. F. McCarthy, Ballymodan Place, Bandon, Co. Cork, Ireland.

IMPROVE YOUR BUDGET STEREO SYSTEM

—continued from page 574

cation I arranged that the audio is completely muted when tuning. Fig. 3 shows the final arrangement.

Any circuit changes should only be done after reference to the manufacturers circuit diagram to make quite sure that no unpleasant or even disastrous effects will result. The AFC circuit shown is common to almost all budget stereos. The AFC and audio are fed from the discriminator output via a high value resistance (typically 150k Ω) to the AFC switch. The AFC line is decoupled after the switch

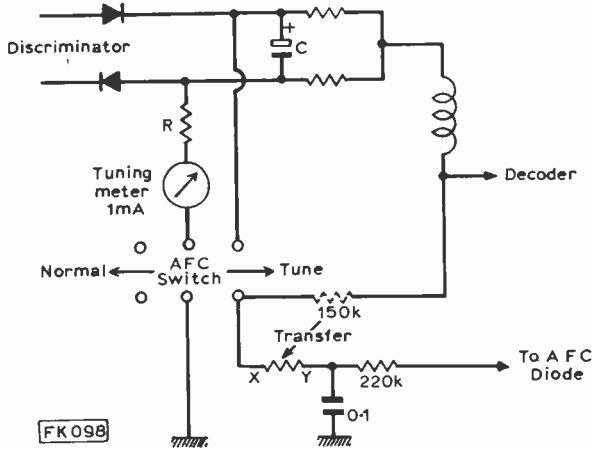


Fig. 3: Spare contacts on AFC switch are used to switch-in an insensitive meter (see text for value of R). Note that the 150k Ω resistor is moved to the new position XY.

(typically 220k Ω and 0.1 μ F). The 150k Ω prevents the audio from being shorted to chassis when the AFC is disabled. In the new circuit arrangement, however, we want to lose it so that muting takes place when tuning, done by moving the 150k Ω to the diode side of the switch. With printed circuit boards the easiest way of doing this is to short out the existing 150k Ω with a wire link and to carefully cut the foil on the other side of the switch, bridging the gap with a new 150k Ω resistor.

The end product is superior to that provided on more expensive systems. We tune for a peak on the meter in complete silence, selecting the wanted station by the position of the tuning scale and then switching in the AFC to take care of drift. The muting works quite smoothly and there are no loud noises when it is switched in and out.

TO BE CONTINUED

AVAILABLE NOW! REPRINT OF PW's TELE-TENNIS SERIES


July-November 74

Send 75p + 7p (post & packing) to: Chief Cashier
(PW Tele-Tennis), IPC Magazines, Tower House,
Southampton St., London, WC2E 9QX.



**BUILD THESE
VEROBOARD PROJECTS**

VERSATILE LIGHT ALARM

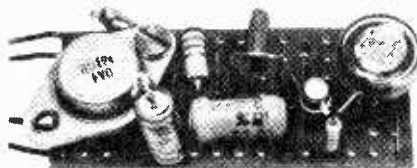


**PLUS MANY MORE ARTICLES
ON SALE 1st OCTOBER**

RADIO & ELECTRONICS CONSTRUCTOR

FREE VEROBOARD IN OCTOBER ISSUE

BROADCAST BAND RECEIVER

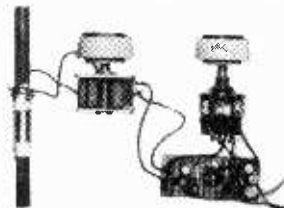

**BUY NOW AND BE SURE
OF YOUR COPY - PRICE 30p**

The All Elektrik Wireless.

Electronically tuned MW/LW tuners.

- MC720** 3 Stage tuned MW HiFi tuner module, with IC RF/IF system and ceramic filter. kit price £8; built version (MC9720) £9.95.
- MC722** 2 stage varicap tuned MW/LW tuner, with electronic MW/LW switching and ferrite rod antenna; terminations to .2" edge connector kit price £8; built (MC9722) £10.45.

FM tunerheads

- EF5600** 5 varicap cct., AFC, AGC, mos input £10.00
- EC3302** 3 varicap cct., AFC, FET input £5.00.
- 8319** 4 varicap cct., AFC, AGC, dual mosfet £9.
- NT3302** 3 mechanically tuned ccts. 366+366pF AM gang capacitor. FET FM input stage. £5.00.

Complete tuner systems/accessories and miscellaneous items

- 7252** Tunerset. 1uV for 26db S/N; .1% THD, with varicap tuning, full scan/lock facility. £24.
- 7253** Tunerset with PLL MPX decoder; 1.2uV for 26dB S/N; .7%THD (inc. decoder).£24.00.
- 7500** Teak cabinet and chassis/front panel for our various am/fm tuner modules and kits. With provision for 3 meters, long slider, 6 preset unit, 5 push button switches, LED etc. £10.00 (carriage £2.50 extra.)
- 7501** The International (see ETI Sept 75) FM tuner. Complete kit & cabinet. £40.00.
- Misc.** G3XGP 2m converter kit. (Complete excluding case) £7.50/WS150 150mm slider £3. MVAM1 £2.75; MVAM2 £1.05 Full list OA.

Ambit is the UK's most comprehensive source for wireless components. Delivery for items in stock is by return of post. Only first quality types are supplied. An SAE will bring you the current shortform price and information list. 40p will bring you the complete data information folder. Please remember to add VAT & PP.

ambit international

37 High Street
Brentwood
Essex CM14 4RH
tel:216029 tlx:995194

Terms: UK prices exclude vat.
UK postage and packing 20p
per order. Europe 40p/4 oz at
airmail rate. Min order £1.00.

RELAY UNIT

Smart steel case 12 x 7 x 4 1/2" with 22 PO Type relays, most with at least 3 sets c/o contacts; 4 reed relays+coils, 2 pots, resistors, capacitors, 12BH7 valve, various diodes, tag board etc. Only £3.75

PC ETCHING KIT MK II

Contains 1lb Ferric Chloride, 100 sq ins copper clad board, DALO etch resist pen, abrasive cleaner etching dish and instructions. Now also includes 2 miniature drill bits. £3.95

FERRIC CHLORIDE

Anhydrous technical quality in 1lb double sealed packs. 1lb 85p; 3lb £1.99; 10lb £4.99; 100lb £38.

COMPUTER PANELS

Large quantity always available. 3lb asstd £1.75; 7lb £3.99; 56lb £18. Pack with about 500 components inc. at least 50 transistors £1.

7lb BARGAIN PARCELS

Hundreds of new components—pots, resistors, capacitors, switches, + PC boards with transistors and diodes also loads of odds and ends. Contents always changing. Only £3.25.

POWER SUPPLY UNIT

G101: Mains transformer, 2A thermal cut-out, bridge rect., will give 17-10.5V output with 2 extra capacitors (provided). With data, only £1.39

TRANSFORMERS

All mains primaries. 6-0-6V @ 100mA 99p; 9-0-9V 100mA 95p; 12-0-12V 100mA £1.09. 24-0-24V 500mA £2.95 1A multi-tapped to give 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 or 30V, also 12-0-12 or 15-0-15 £3.15. 2A version £4.40. 6-5-0-6-5V 500mA £1.45; 17V 1A £2; 9V 10A £3.99; sub-miniature 12-0-12V @ 50mA 89p.

Send 10p Stamp for Illustrated Multimeter Catalogue (Free with orders over £3).

All prices include UK postage and VAT @ 8% or 25% as appropriate. SAE int. enquiries. Surplus components wanted for cash. PRICE INCREASES DUE TO NEW POSTAL RATES.

GREENWELD (PW11)

51 Shirley Park Rd. Southampton, SO1 4FX. Tel: (0703) 772591. Also callers welcome at 21 Dapford Bdy SE8 01-692 2000, & 38 Lower Addacomb Rd. Croydon 01-688 2950

BARGAIN PACKS

- | | |
|----------------|-----------------|
| 12 BC107 £1.20 | 25 1N4001 £1.20 |
| 14 BC108 £1.20 | 22 1N4002 £1.20 |
| 12 BC109 £1.20 | 20 1N4003 £1.20 |
| 15 BC148 £1.20 | 18 1N4004 £1.20 |
| 13 BC149 £1.20 | 16 1N4005 £1.20 |
| 12 BC157 £1.20 | 14 1N4006 £1.20 |
| 12 BC158 £1.20 | 12 1N4007 £1.20 |
| 12 BC159 £1.20 | 40 1N4148 £1.20 |
| 2 2N2646 £1.20 | 3 2N3055 £1.20 |
| 10 BC328 £1.20 | 12 BC548 £1.20 |
| 12 BF194 £1.20 | 12 BF195 £1.20 |
| 7 BF173 £1.20 | 5 BF181 £1.20 |
- All full spec marked components.

9 PIN DIL 741's

10+26p; 25+23p; 100+21p; 250+29p

555 TIMERS

3+ 55p; 10+ 45p; 25+ 40p; 100+ 38p

RESISTORS AND CAPACITORS

400 asstd carbon resistors £1.50
250 Hi-stabs 1, 2, 5%, 1/2, 1W £1.40
100 Wirewounds, 2W to 15W £2.00
200 ceramic, mica etc caps £1.10
100 C280 polyesters, .01-.47 £1.30
200 min electrolyt cs, but mainly unmarked, so only £1.45.
15 airspaced & compression trimmers up to 1250pF £1.10
200 min. resistors, 1/2, 1W, mostly carbon film £1.10

JUMBO PACK—1 each of the above.

£10.90 value for only £8.50!!!

VEROBOARD

100 sq ins, about 8 pieces asstd sizes and pitches £1-15

MISCELLANEOUS

SPCO microswitch, 5A 12p; 15 asstd pots 75p; plug in relay, 250012 4 c/o 25p; 4 x 80V 10A rectis on heat sink, ideal batt. charger, £1.20 SN76680N £1. Good range close tolerance resistors—SAE list 96kHz crystal £1.

CHESTER WAREHOUSE MUST BE CLEARED BY 1st NOV. TOWER WHARF, RAYMOND ST., CHESTER

TRANSISTOR PACKS

Large quantity of mainly unmarked out of spec. transistors just arrived. Sample tests show 75% OK. Sold in mixed packs with PMP, NPN, RF, AF, plastic, metal can, small signal and power devices. At least 200 for £1.99; 500 for £3.99; 1000+ for £8.99. Out-of-spec 2N3055's 10 for £1.99 25 untested BFY51 type transistors £1.00, 40 untested BC108 £1; 100 £2.00.

B. BAMBER ELECTRONICS

5 STATION ROAD, LITTLEPORT, CAMBS., CB6 1QE
Telephone: ELY (0353) 860185 (2 lines) Tuesday-Saturday

ALL BELOW—ADD 8% VAT

VARIABLE STABILISED PSU, solid-state 240V a.c. input, output 0-24V d.c. at 500mA, +32V d.c. at approx. 50mA. Voltage controlled by external 5kΩ pot. Size 7 1/2 x 4 x 2 1/2 in (less 5kΩ pot). £5 each

THREE-TURN WIRE-WOUND POTS, 5kΩ, for above, 75p each

MAINS TRANSFORMERS

All 240V input, voltages quoted approx RMS (Please quote type no. only when ordering.)

TYPE 10/2, 10-0-10V at 2A, £1.50 each

TYPE 18/2, 18V at 2A, £1.85 each

TYPE 28/4, 28V at 4A + 125V at 500mA £4.

TYPE 63/1, 6.3V at 1A, 85p each or 2 for £1.50

TYPE 129, 400V at 20mA + 200V at 10mA + 6.3V at 500mA, £1.25

TYPE 72/03, 400V at 10mA + 200V at 5mA + 6.3V at 400mA, £1.25

TYPE 70462, 250-0-250V at 80mA + 6.3V at 3A, £1.75

RADIOSPARES 500W AUTO TRANSFORMERS, 100-110-150-200-220-240-250V tapped input and output, step-up or step-down facility, ex-new equip £6

CURLY LEADS, 4 core telephone type, 2 for 20p

PC board with withdrawal handles, mixed coils 8 for 50p

Solder, 20SWG, 60/40 alloy, approx 8yds 25p

25-way ISEP PLUGS AND SOCKETS, 40p

(plug + 1 skt)

DIE CAST BOXES (approx size in inches)

4 1/2 x 2 1/2 x 5 75p

4 1/2 x 3 1/2 x 7 85p

4 1/2 x 3 1/2 x 7 11.00

4 1/2 x 3 1/2 x 7 11.85

4 1/2 x 3 1/2 x 7 11.85

4 1/2 x 3 1/2 x 7 12.25

1mA METERS 2in square, plastic fronts (these have a paper scale stuck over the original, marked 0-1mA, which is easily peeled off, and an internal 18kΩ resistor which is easily removed). £1.75 each, or 2 for £3.

TERMS OF BUSINESS: CASH WITH ORDER (minimum order £1) POST FREE (UK ONLY).

PLEASE ADD VAT AS SHOWN

Export enquiries welcome. Callers welcome. Tues. to Sat

Please enclose S.A.E. with ALL enquiries.

ALL BELOW—ADD 8% VAT

Black plastic knobs, 1/4 in dia., 1/4 in spindle, 1 for 50p

Ring magnets, 7mm inside dia., 20 for 50p

1 1/2 in polythene chassis mounting fuse-holders, 8 for 30p

LES Lamps, 24V, 2W, 10 for 40p

3 Switch Push Button Units (3 x 2 pole, 2 way), min. push-push switches, 1/4 in dia. buttons, mounted on one unit, 40p

Perspex coil formers, 1 1/2 x 1 in dia., 5 for 25p

Turret tags, 1/4 in dia., 25p pack

Rotary switches, min. 4 pole 2-way, 2 for 30p

Telephone type earpiece insert, 50p

Reeds (for reed relays) single-pole make, 5 for 30p

Mullard tubular ceramic trimmers, 1-18pF, 6 for 50p (as featured in Rad Comm, Jan. p. 25)

1 C s, some coded, 14DIL type, untested mixed, 20 for 25p

Miniature slider switches, 2 pole, 2-way, 5 for 50p

TRANSISTOR HEATSINKS, to take 2 x TO18 transistors, screw in clamps, block size 1 1/2 x 1/2 x 1/2 in, with holes for mounting, 3 for 50p

TO3 transistor insulator sets, 10 for 50p

ALL BELOW—ADD 25% VAT

TV plugs, metal type, 6 for 50p

TV sockets, metal type, 5 for 50p

TV line connectors (back-to-back socket) 5 for 50p

OC200 transistors, 6 for 50p

BSY95A transistors, 6 for 50p

BFY51 transistors, 4 for 60p


BCY72 transistors, 5 for 50p

PNP audio type TO5 transistors, 12 for 25p


IF cans 1/4 in square, suitable for rewinding, 6 for 30p

DIN SPEAKER SOCKETS (2-pin) 4 for 30p

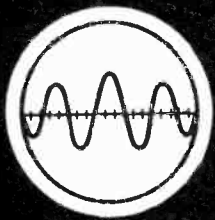HIGH QUALITY SPEAKERS, 8 1/2 x 6 1/2 in elliptical, only 2in deep, inverse magnet, 4 ohms, rated up to 10W, £1.50 each, or 2 for £2.75 (qty discount available)




TUAC

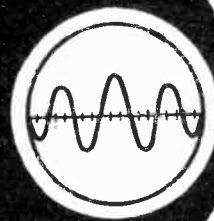

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.
163 MITCHAM RD. LONDON SW17 9PG 01-672 3137/9080

TUAC POWER MODULES offering more power and quality than ever before


- 125 watts RMS continuous sine wave output

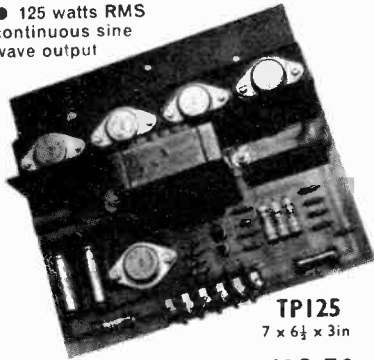


TP125
7 x 6½ x 3in
£19.50

- 4 R.C.A. 150 watt 15 amp output transistors
- Rugged layer wound driver transformer
- Short—Open—and Thermal overload protection
- Only 6 connections

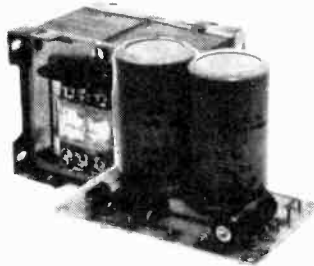Power supplies vacuum impregnated Transformers with supply board incorporating pre-amp supply.



PS 125 ± 45 volts for TP125 **£12.25**
PS 100 ± 43 volts for TL100 **£11.25**
PS 60 ± 38 volts for TL60 **£10.00**
PS 30 ± 25 volts for TL30 **£6.75**
PSU 2 for supplying disco mixer **£4.75**

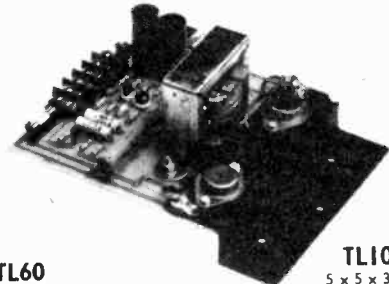

TL60
5 x 5 x 3in

- 60 watts R.M.S. continuous sine wave output
- 2 R.C.A. 110 watt 15 amp transistors

£12.50

TL100
5 x 5 x 3in

- 100 watts R.M.S. continuous sine wave output
- 2 R.C.A. 150 watt 15 amp transistors

£15.00

Specification on all power modules. All output power ratings ± 0.5dB; Output impedance 8-15 ohms; THD at full power 2% typically 1%; input sensitivity 60mV into 10kΩ; Frequency response 20Hz-20kHz ±2dB; Hum and noise better than -70dB.

TUAC DISCOTHEQUE MIXER WITH AUTO FADE



£31.50

Designed for the discerning D.J. of professional standard. Offering a vast variety of functions. Controls: Mic Vol; Tone, over-ride depth; auto/Manual Sw; Tape Vol; L & R Deck Faders; Deck Volume; Treble and Bass; H. Phon Vol Selector; Master Vol On/Off Sw. Max output 1V RMS.

Specification; Deck Inputs—50mV into 1MΩ; Deck Tone Controls—treble +20—10dB at 12kHz; Bass +22—15dB at 40Hz; Mic Input—200 ohms upwards, 2mV into 10kΩ; Mic Tone Control—Total Variation Treble 15dB. Total Variation Bass 10dB; Tape Input—30mV into 47kΩ; Power Requirements—30—50 volts at 50mA.

PANEL SIZE
18 x 4½ in.
DEPTH 3 in.

HOW TO ORDER BY POST

Make cheques/P.O.s payable to TUAC LTD (PW6)
or quote Access/Barclay Card No.
and post to TUAC LTD (PW/6)
163 Mitcham Road, London, SW17 9PG
We accept phone orders against
Access/Barclay Card Holders
Phone: 01-672 3137/9080

STOCKISTS—CALLERS ONLY

Arthur Sallis Ltd., 28 Gardner Street. Tel. Brighton 65806
Bristol Disco Centre, 86 Stokes Croft. Tel. Bristol 41666
Socodi, 9 The Friars. Tel. Canterbury 60948
Cookies, 132 West Street. Tel. Crewe 4739
Calbarrie Audio, 88 Wellington Street. Tel. Luton 411733
Al Music Centre, 88 Oxford Street. Tel. Manchester 236 0340
Damon Electronics, 99 Carrington Street. Tel. Nottingham 53880
Electra Centre, 58 Lancaster Road. Tel. Preston 58488
Mitchell Electronics, 64 Winchester Street. Tel. Salisbury 23689
Wec Lighting, 10 Commercial Road. Tel. Southampton 28102

ALL PRICES INCLUDE V.A.T. (8%) AND POSTAGE AND PACKING


ACCESS & BARCLAY CARDS ACCEPTED JUST SEND OR PHONE US YOUR NUMBER H.P. ENQUIRIES INVITED.



TUAC ANNOUNCES THE LATEST
1976 STEREO DISCO MIXER £75

Printing schedule precluded illustration. However send now for details and specification.

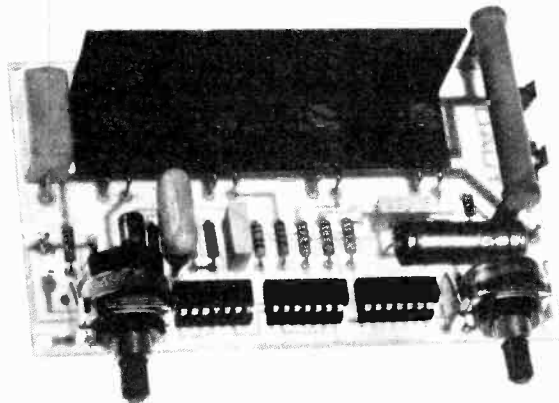NEW!!! 4 CHANNEL SOUND TO LIGHT SEQUENCER—4LSMI



Patents applied for

- R.C.A. 8 amp Triacs
- 1000W per channel
- Fully suppressed and fused
- Switched master control for sound operation from 1/2W to 125W
- Speed control for fixed rate sequence from 8 per minute to 50 per second
- Full logic integrated circuitry with optical isolation for amplifier protection
- Full wave control
- 13 easy connections


£22.00

3 CHANNEL LIGHT MODULATOR


- R.C.A. 8 amp Triacs
- 1000W per channel
- Each channel fully suppressed and fused
- Master control to operate from 1W to 100W
- Full wave control
- 12 easy connections.

Single Channel Version 1500 watts **£7.25**

£15.50

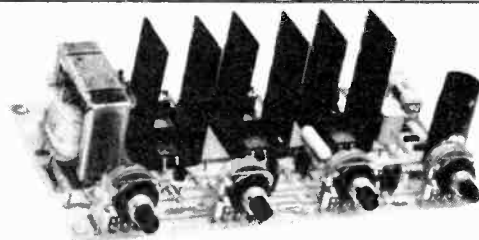

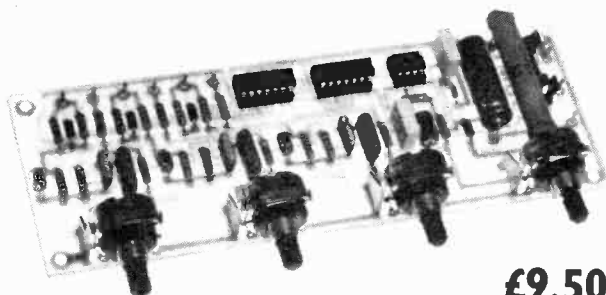
ADD SEQUENCE AND DIMMING EFFECTS TO YOUR TUAC 3 CHANNEL LIGHT MODULATOR



£9.50

SEQUENCE DIMMER MODULE—3SDMI

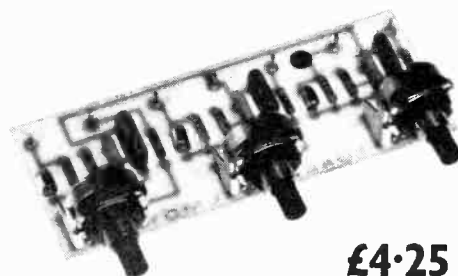Speed Control 3 per min. to 10 per sec. Dimmer control to each channel. Full logic integrated circuitry. 9 easy connections



£4.25

DIMMER MODULE—LMDI

Dimmer control for each channel
7 easy connections



TUAC

OPEN 6 DAYS A WEEK 9.30am - 6.00pm.
 163 MITCHAM RD · LONDON SW17 9PG 01-672 3137/9080



"I MADE IT MYSELF"

Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.

Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn—and pave the way to a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio . . . a Burglar Alarm. You learn Radio and Electronics by doing actual projects you enjoy—making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

No soldering—yet you learn faster than you ever dreamed possible.

Yes! Faster than you can imagine, you pick up the technical know how you need. Specially prepared step-by-step lessons show you how to: read circuits—assemble components—build things—experiment. You enjoy every minute of it!

You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course. **AT NO EXTRA CHARGE!** And this is a course anyone can afford. (You can even pay for it by easy instalments).

So fast, so easy, this personalised course will teach you even if you don't know a thing today!

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics.

You become a man who makes things, not just another of the millions, who don't understand. And you could pave the way to a great new career, to add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own transistor radio. And after the course you can go on to acquire highpowered technical qualifications, because our famous courses go right up to City & Guilds levels.

Send now for FREE 76 page book—see how easy it is—read what others say!

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

POST TODAY FOR FREE BOOK

To: ALDERMASTON COLLEGE
DEPT. CPW 11, READING RG7 4PF CPW11

Also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London, EC2Y 5EJ Tel. 01-428 2721
Yes, I'd like to know more about your course. Please send me free details—plus your big, 76-page book that tells about all your courses.

Name

Address

POST CODE



HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY



4 1/2" x 3 1/2" METER. 30μA, 50μA or 100μA, £3.85. P. & P. 13p.

TAPE RECORDER LEVEL METER
500μA, 80p
P. & P. 10p.



CARDIOID DYNAMIC MICROPHONE

Model UD-130. Frequency response 50–15,000c/s. Impedance Dual 50K and 600 ohms, £7.40. P. & P. 13p.



42 x 42mm METERS 1mA, 10mA, 100mA, 500mA, £2.76, 11p P. & P.

60 x 45mm METERS 50μA, 100μA, 500μA and 1mA VU METER £2.92, 11p P. & P.

EDGEWISE METERS, 90mm x 34mm, 1mA £3.40, 13p P. & P.

MULTI-METER

Model ITI-2
20,000 ohm/volt, £6.90.
P.&P. 16 1/2p.



3 WATT STEREO AMPLIFIER

1 1/2 W PER CHANNEL
£4.30. P. & P. 12 1/2p.



All above prices include V.A.T. LARGE S.A.E. for List No. 12. Special prices for quantity quoted on request.

M. DZIUBAS

158 Bradshawgate · Bolton · Lancs. BL2 1BA

VALVE BARGAINS

Any 5 64p, 10 99p, 50 £4. Your choice from the following list: ECH84, ECC82, ECL80, EF80, EF183, EF184, PC86, PC88, PCF80, PCF802, PCL82, PCL84, PCL85, PCL805, PCL86, PFL200, PL36, PL504, PY33, PY81, PY800, PY88, EH90, 30FL1, 30FL2, 30PL14. 6F28

Colour Valves 25p each
PL508 PL509, PY500/A

Press 4 Button Transistor UHF Tuners £2.50

AERIAL BOOSTERS

We make three types of Aerial Boosters all for set top fitting, with Co-ax Plugs and Sockets.

B11—For Stereo and Standard VHF Radio
B12—For the older VHF Television, please state BBC1 and ITV Channels.

B45—For mon. or colour this covers the complete UHF band.

All Boosters are complete with Battery and take only minutes to fit. **Price £3.90 each**

BARGAIN PACKS

All Components in the Bargain Packs are unused and marked.

Pack 1—Polyester (C280) Axial Leads Capacitors—250V/W & 400V/W, very good mixed selection from 0.01 UF to 2.2 UF. Price 100 £1.25, 1000 £10.00 (our choice).

Pack 2—Light Dimmers. 300 watt Light Dimmers complete with Plate (replaces existing switch. Takes only minutes to fit. Price £2.85.

Co-Ax Connectors 8p (70p).

Co-Ax Plug—8p (70p).

Jack Plugs—Standard 17p (£1.50), 2.5mm 10p (85p), 3.5mm 10p (85p).

Din Plugs—2 Pin 12p (£1.00), 3 Pin 14p (£1.20), 5 Pin 18p (£1.50). (Price in brackets for Ten).

Prices include V.A.T. P. & P. under £1/10p, £1 to £3/15p, above £3/20p. Overseas at cost. Money back guarantee on all orders.

ELECTRONIC MAILORDER LTD., 62 BRIDGE ST., RAMSBOTTOM, BURY, LANCS. Tel. Rams. 3036.

Everest Instruments Ltd.

34, Shakespeare St., Nottingham.
Tel. (0602) 45466

All prices quoted include p. & p., & VAT, min. order £1, CWO only.

Transformers		10 x 6 EMI	£ p
All 240v 50hz primaries		8 ohm 20 watt	7.36
		13 x 8 EMI	
		8 ohm 20 watt	6.75
		8 ohm 25 watt	7.84
Volts	Amps	£ p	
6-3	1.5	1.83	
6-3	3.0	2.09	
9-0	1.0	1.83	
12-0	0.5	1.83	
12-0	1.5	2.09	
12-0	3.0	3.02	
6-0-6	0.5	1.96	
9-0-9	0.5	1.96	
9-0-9	1.0	2.23	
10-0-10	2.0	3.60	
12-0-12	2.0	2.23	
12-0-12	2.0	3.13	
12-0-12	3.0	4.32	
15-0-15	1.0	2.88	
15-0-15	2.0	3.78	
15-0-15	4.0	6.32	
20-0-20	1.0	3.63	
20-0-20	2.0	4.32	
30-0-30	1.0	4.32	
0-10-12-14-			
16-18	4.0	4.58	
0-12-15-20-			
24-30	2.0	4.45	
0-5-20-30-			
40-60	2.0	6.54	
Bulk tape eraser		3.53	
15-8-3 ohm 12 watt matching		1.71	
Transistor driver 4:1-1		0.27	
P.C. Board			
Single sided fibre glass		0.70 sq ft	
Double sided fibre glass		1.00 sq ft	
Cut in multiples of 6" i.e. 6 x 6, 6 x 12, 12 x 12, 12 x 18, etc.			
Circuit etchant 250ml		0.55	
1 lb ferric chloride		0.50	
250ml plastic bottles		0.16	
Speakers		£ p	
3" Goodman tweeter			
8 ohm 51CD4		1.47	
3" Audax tweeter			
8 ohm 15 watt		1.60	
5" Audax bass			
8 ohm 10 watt		3.23	
6 1/2" Audax 8 ohm 15 watt		2.95	
6 1/2" EMI d/cone 8 ohm 10 watt		3.59	
8 x 5 EMI d/cone 8 ohm 10 watt		3.67	
8" Celestion d/cone 8 ohm 10 watt		2.76	
Electrolytics. Tubular with axial leads except where stated.			
Mfd.	Volts	Pence	
47	4	7	
330	4	7	
68	6.3	7	
470	6.3	9	
1000	6	11	single end p/c fitting
25	10	7	
47	10	7	
220	10	7	
330	10	9	
15	16	7	
33	16	7	
68	16	7	
220	16	9	
220	16	9	single end p/c fitting
330	16	12	
1000	16	20	
10	25	7	
22	25	7	
47	25	7	
100	25	7	
150	25	9	
200	25	11	
1250	25	24	single end can
5000	25	55	single end can
1000+1000	30	32	single end can
2500	30	40	single end can
6.8	40	7	
16	40	7	
100	40	7	
1000	50	35	single end can
1	63	7	
4.7	63	7	
10	63	7	
32	63	7	
800	63	32	single end can
2500	63	80	single end can
4700	63	140	single end can

DIGITAL CLOCK KITS

MHI—A modular approach to digital clock building. An MHI kit uses an MHI clock kit plus an MHI display kit. Any of the clock kits will interface with any of the display kits or with any other common-anode LED display. Each clock kit contains basic components plus a PCB—all you have to supply is a few resistors, transistors, etc.

MHI-5378. This kit has full car/boat clock facilities, quartz time source, brightness control, etc. Display is switchable with ignition for power saving.

Kit: MMS378, socket, CA3081, 2MHz XTAL and trimmers, PCB. £15.10

MHI-5024. The MHI-5024 kit will act as a 6 or 4 digit stop watch chip with readouts down to 1 sec. Clock will count up or down and can (with additional components) also act as a calculator.

Kit: MK5024, socket, CA3081, PCB £14.00

MHI-5314. Six digit basic clock, 12/24 hour, MMS314 chip. £8.60

MHI-5025. Six digit alarm clock, Snooze, MK5025 chip. £9.35

MHI-7001. Six digit Time/Date/Alarm/Timer, can be used as electronic time-switch in addn to other functions. £10.00

MHI-D707. Four or six digit display kit, 0.3" digits Supplied with PCB. 4 Dig—£8.60 6 Dig—£9.50

MHI-D727. Four or six digits, 0.5" high digits. Supplied with 6 digit PCB. 6 Dig—£12.00

MHI-D747. Four or six digits, 0.6" high digits. Supplied with PCB for 6 digits. 6 Dig—£14.70

TERMS: CWO. Access, Barclaycard (simply quote your number and sign). Credit facilities to Accredited account holders.

BYWOOD

66 Ebbwens Road, Hemel Hempstead, Herts HP3 9RDA. VAT: All prices exclude VAT (8%) P/P: 15p.

H.A.C. SHORT-WAVE KITS WORLD-WIDE RECEPTION



Famous for over 35 years for Short-Wave Equipment of quality. "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

1975 "DX" RECEIVER

Complete kit—Price £5.50 (incl. p. & p. & V.A.T.). Customer writes: "Australia, India and America at loud volume." "I have now heard over 300 stations including many Amateurs. I have received 32 Q.S.L. verified reports—from all continents. An amazing one-valver."

This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K Plus" (illustrated above). All orders despatched within 7 days. Send now for free descriptive catalogue of kits and components.

Send stamped envelope for details.

"H.A.C." SHORT-WAVE PRODUCTS
P.O. BOX No. 16, EAST GRINSTEAD, SUSSEX RH19 3SN

JC12 AMPLIFIER
6W IC audio amp with free data and printed circuit £2.95



DE LUXE KIT FOR THE JC12

Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £2.52. Stereo model with balance control £5.20.

JC12 POWER KIT

Supplies 28V 0.5 Amps £4.77.

PREAMP KITS FOR THE JC12

Type 1 for magnetic pickups mics and tuners. Mono model £2.15. Stereo model £3.70. Type 2 for ceramic or crystal pickups. Mono £1.27. Stereo £2.33.

SEND SAE FOR FREE LEAFLET ON KITS

SINCLAIR

IC20

AMPLIFIERS

SEND SAE FOR FREE DATA BOOKLET

IC20 10+10W stereo amp, kit with free booklet and printed circuit £8.50
PZ20 power supply kit for above £5.91
VP20 volume, tone control and preamp kit £6.79

JC40 AMPLIFIER

The big daddy of our range of IC audio amplifier kits. 20W output. With free booklet and printed circuit £8.

BATTERY ELIMINATOR BARGAINS

6-WAY SPECIAL

The most versatile battery eliminator ever offered. Switched output of 3, 4, 6, 7 1/2 and 12V at 500 mA £5.45.



3-WAY MODEL

Switched outputs of 6, 7 1/2 and 9V at 250mA with unique 4 way multi jack plug and socket output connector £3.55.

RADIO MODELS

50mA output with poppet battery connectors for transistor radios etc. 6V £4.65. 9V £4.65. Double 4+4V £4.43. 6+6V £4.43. 9+9V £4.43.

TAPE RECORDER MAINS UNITS

7 1/2V output complete with 5 pin DIN plug to run cassette tape recorders from the AC mains £4.81.

SINCLAIR CALCULATORS

Cambridge £9.95

Cam. Memory £14.10

Scientific £14.10

Oxford 100 £9.95

Oxford 200 £15.90

Oxford 300 £22.98

MAINS UNITS

For Oxford Series £3-19

For Cambridge, Cam.

Mem. and Scientific

£3-65

FERRANTI ZN414

IC radio chip with data £1.69. Also available kit of extra parts to complete a radio £3.38. Send sae for free leaflet.

SINCLAIR PROJECT 80

AFU £7.55

Z40 £5.75

Z60 £7.10

Q16 £8.87

PZ5 £6.21

PZ6 £8.70

PZ8 £8.29

FM Tuner £13.25

Stereo decoder for above £9.55

Transformer for PZ8 £5.10

Stereo 80 £13.25

Project 805 £38.22

Project 805SQ £46.65

Project 80 Quadraphonic decoder £26.97

S-DECS AND T-DECS

S-DeC £2.34

T-DeC £4.15

µ-DeC A £4.55


µ-DeC B £7.85

IC carriers:—

16 dit: plain £1.18

With socket £2.21

10 TOS: plain £1.09. With socket £2.08

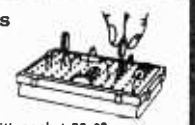


SWANLEY ELECTRONICS

PO BOX 68, SWANLEY, KENT BR8 8TQ.


Prices include post and VAT. Official credit orders from schools etc welcome. No VAT charged on overseas orders. All prices are special offers.

RADIO & TV SERVICING

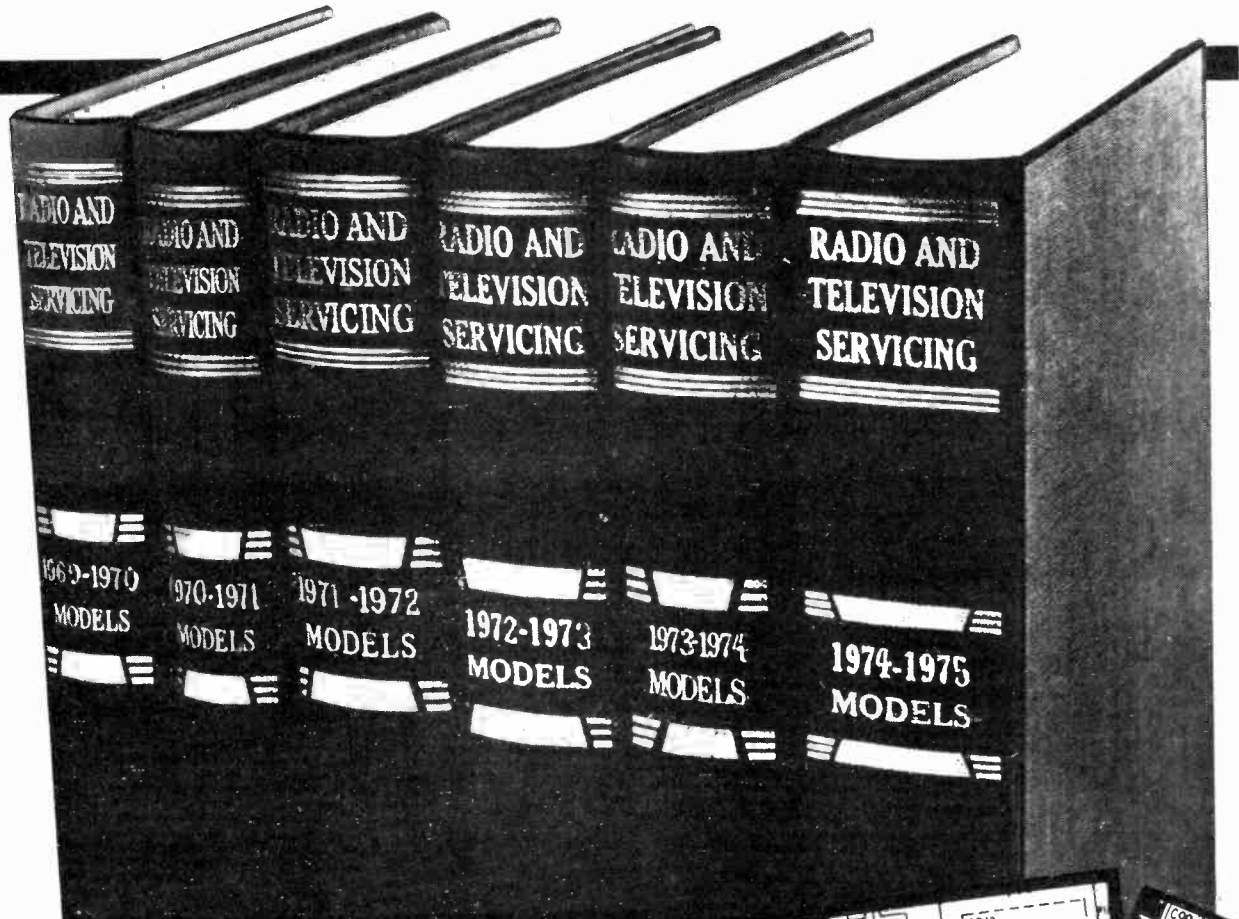

Essential data for over 1500 popular models

With this vast 6-volume library at your fingertips you have all the necessary servicing data you need covering almost every popular model from 1969 to the very latest on the market today. And not only radio and TV but stereograms, record players and tape recorders too. Much of the earlier information on this equipment is quite unobtainable elsewhere and *Radio & TV Servicing* is now the only available source of technical data. The 1975 edition, now ready, brings the library right up-to-date with abstracts from manufacturers' service bulletins issued during the past year. *Radio & TV Servicing* is the only work of its kind—a money-spinner that no service engineer should be without.

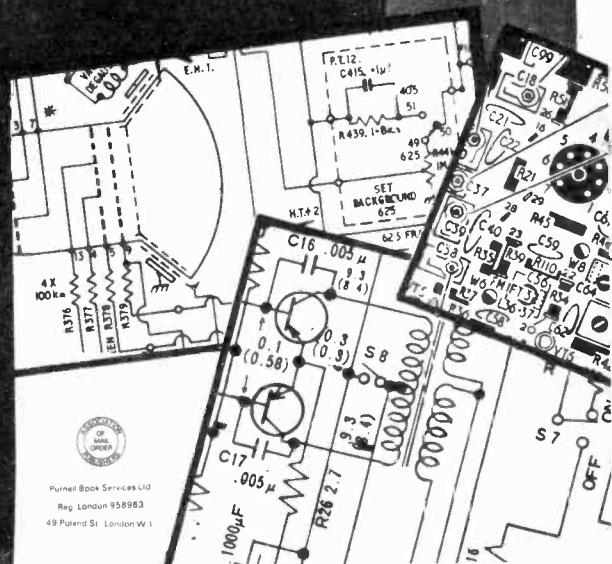

Purnell Book Services Ltd
Reg. London 958983
49 Putney St. London W1

6 Volume library '69-'75 is now ready

The
only work
of its kind
anywhere

Speedier, more efficient servicing means increased turnover . . .

This library is a gold-mine of technical information. Six hard-bound volumes giving vital data on more than 1500 models of Television (colour and mono), Radios, Car Radios, Stereograms, Record Players and Tape Recorders. More than 4000 pages clearly display thousands of circuits, printed panel diagrams, component layout diagrams, waveform graphs, block diagrams, etc. Over 800 pages, devoted entirely to Colour TV, include installation instructions, new term explanations, purity adjustments, colour balance, static convergence and a wealth of invaluable information. Here, in fact, is all the data you need for efficient and speedy repair work.

Your Guarantee

Sending for these valuable books, even though you also enclose your remittance, commits you to nothing. Unless you are absolutely satisfied you are perfectly free to return the set and if you do so within 10 days of receipt your money will be refunded in full and without question.

How to get your 6-volume set
Detach the Order Form below and send it, with the appropriate remittance to:
Purnell Book Services Ltd.
Box 20, Abingdon, Oxon, OX14 4HE

Makes of Colour TV include:

Alba, Baird, Bang and Olufsen, B.R.C., Bush, Decca, Dynatron, Ekco, Ferguson, Ferranti, G.E.C., Invicta, H.M.V., Marconiphone, I.T.T./K.B., Masteradio, Murphy, Philips, Pye, Sobell, Stella, Ultra, Hitachi, Thorn Consumer Electronics, Korting, R.G.D., Sony, Telefunken.

All these makes of Mono TV, Radios, Car Radios, Stereograms, Record Players, Tape Recorders:

Aiwa, Alba, Baird, Bang and Olufsen, Beogram, Beolit, Blaupunkt, B.R.C., Bush, Cossor, Crown, Dansette, Decca, Defiant, Dulci, Dynatron, Eddystone, Ekco, Elizabethan, Ferguson, Ferranti, Fidelity, G.E.C., Grundig, Hacker, Halcyon, H.M.V., Hitachi, Invicta, I.T.T./K.B., JugoElektra, Klinger, Loewe Opta, Marconiphone, Masteradio, Monogram, Murphy, National, Nivico, Perdio, Peto Scott, Philco, Philips, Portadyne, Pye, Radiomobile, Radionette, R.G.D., Roberts' Radio, Robux, Sanyo, Sharp, Sobell, Sony, Standard, S.T.C., Stella, Stereosound, Telefunken, Teletron, Ultra, Unitra, Van Der Molen, World Radio, Thorn Consumer Electronics, Elpico, Rigonda (USSR), Waltham.

Plus such developments as:

Stereo Multiplex Transmission - Phase Locked Loop Stereo Decoding - Dynamic Noise Limiting - Adoption of Integrated Circuits in Receiver Design - Thyristor Power Supplies - Silicon Controlled Switch Timebases - Sony Trinitron Systems - Modifications to Circuitry and Fault-Finding Tips.

To: Purnell Book Services, P.O. Box 20, Abingdon, Oxon OX14 4HE

Please send me the 6-volume set of RADIO & TV SERVICING for which I enclose cheque P.O. No. _____ crossed and made payable to Purnell Book Services Ltd for the full cash price of £31.75 tick for £9.25 deposit to be followed by 6 successive appropriate monthly payments of £4.00 (total £33.25) box

I understand that unless I am entirely satisfied I may return the volumes in good condition within 10 days and my money will be refunded in full
BLOCK LETTERS PLEASE

Name _____

Address _____

TRADE APPLICATION (To be accompanied by Trade Order)

Please supply _____ 6-volume set(s) of RADIO & TV SERVICING at £31.25 per set. (Credit 30 days) **BLOCK LETTERS PLEASE**

Name _____


Company _____

Signature _____

IMPORTANT: Individual volumes are available on application.

Please return entire form. Available U.K. only

057

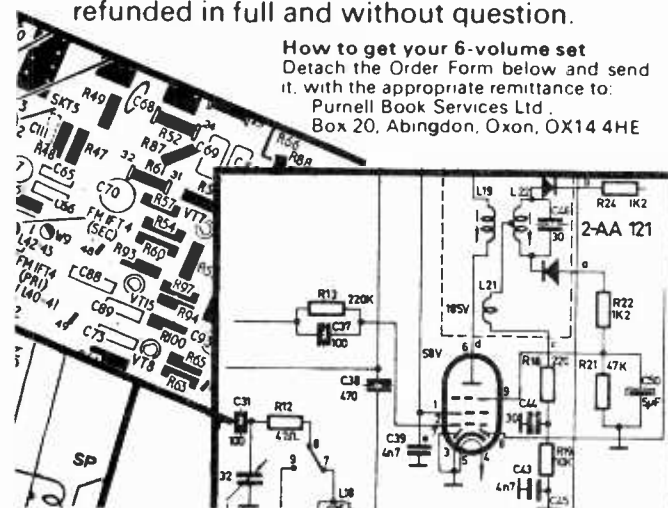

SAXON ENTERTAINMENT LTD.


NEW PROFESSIONAL MODULES TO SAVE YOU £££

THE NEW POWER AMPLIFIERS

New features—new performance standards

- ★ New 90°C overtemperature cutout (electronic not mechanical).
- ★ New Integral output capacitor, no external components required for normal operation.
- ★ Short circuit load line type protection with twin summing amplifiers.
- ★ Inherently open circuit proof.
- ★ Input sensitivity —10 dBm (240 mV into 50k) i.e. suitable for most mixers. Response 30Hz—40KHz ±2dB.
- ★ Typical distortion 0.4% Noise —80 dB (as graph in catalogue).
- ★ Compact: 15cm x 8 cm x 3 cm
- ★ Suitable for all public address, discotheque, and group applications.
- ★ Fused supply terminal.
- ★ Single supply line (split supply not required).

Three brilliant new power modules employing the same circuitry, using 10 transistors, three diodes and one zener diode with electronic over temperature cutout as well as normal thermal protection, load line short circuit and incorrect load protection, integrally mounted output capacitor. Fused D.C. supply terminal. May be solder or screw connected. The Input Impedance is high enough to accept all types of mixer having an output of 250 mV.

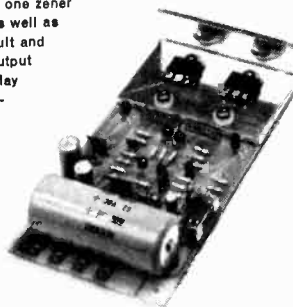

SA608

60 w.r.m.s. into 8Ω;
30 w.r.m.s. into 15Ω
Texas 15A output transistors.

£11.50

CONSTRUCTIONALLY & ELECTRONICALLY BETTER : MULTIPLE TESTED : GUARANTEED

SA1208

120 w.r.m.s. into 8Ω
60 w.r.m.s. into 15Ω
Glass fibre printed circuit board.
15A output transistors

£16.00

SA308

30 w.r.m.s. into 8Ω
15 w.r.m.s. into 15Ω
basic circuit identical to SA1208
10A 'Plastic Power' output transistors

£9.00

THE NEW POWER SUPPLIES

- ★ One piece, ready to wire assembly with integral glassfibre pcb. **PM1201** 95 volts for one SA1208 **£11.00**
- ★ Grain oriented laminated transformers for compactness. **PM1202** 95 volts for two SA1208 **£14.00**
- ★ Facilities for preamp supply. **PM602** 65 volts for one or two SA 608 **£9.00**
- ★ Fully fused.
- ★ Size of all models 10 x 8 x 13cm. **PM302** 45 volts for one or two SA 308 **£7.50**
(PM1202 16cm)

MODULAR PRE-AMPS

Mono & Stereo

Up to twenty IM7001 Input modules may be used with the IM7002 mixer module. Each Input module has various types of equalisation and monitor path outlets.


★ Equalisation to suit ceramic AND magnetic cartridges, low and high imp. mic. and all musical instruments. ★ Mono and stereo. ★ Mono module may be matrixed into stereo. ★ low noise circuitry with carbon film resistors. ★ 20 Hz—50 kHz + 1dB. ★ Wide range bass and treble controls—zero noise with vol. at min. ★ 18 volt supply. ★ Outputs for monitoring and echo send. * May be used in conjunction with the discotheque mixers and Minotaur amplifiers.

IM7001M **£5.50** (mono) IM7001S **£9.00** (stereo)

IM7002 Mixer module with output suitable for most amplifiers PLUS up to 1 Watt of monitoring power.

★ Accepts up to twenty IM7001 Input modules. ★ Mono or stereo. ★ Up to 3V output—will feed loads down to 600 ohms. ★ Up to 1 watt into 8Ω for monitoring (will feed higher impedance). ★ Accepts echo and other effects return signals.

IM7002M **£5.50** (mono) IM7002S **£9.00** (stereo)

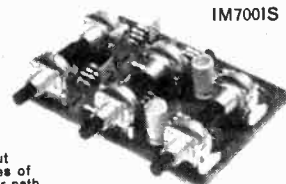


IM7001S

SAXON SUPERFECT

(Illustrated)

All these features in ONE UNIT:
No other commercially available module to our knowledge, offers all these facilities in one complete unit.

- ★ Sequential display with variable speed.
- ★ Frequency dependent channels—individually fused.
- ★ Continuously variable function control gives uninterrupted light display in absence of signal.
- ★ Electronic override on each channel.
- ★ RCA 8 Amp. triacs handling 1000 watts per channel.
- ★ Limiter circuitry to reduce 'flicker'.
- ★ Individually controlled bass middle and treble plus master audio control for ease of adjustment.

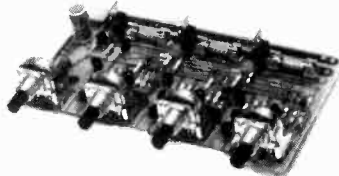

LIGHT UNIT

£19.75

SAXON SOUND-LITE

- Our ever popular 3000 watt unit is now available in module form at only
- ★ Individual control of bass middle and treble plus master control for ease of adjustment.
 - ★ 1000 watts per channel—individually fused.
 - ★ Negligible load on amplifier.
 - ★ RCA 8 AMP triacs for reliability.

£13.50

THE ULTIMATE IN MIXER MODULES

- ★ Inputs for two decks (ceramic cartridge) plus tape; overall bass and treble controls
- ★ Hi/lo imp. mic input with separate volume bass and treble controls.
- ★ Continuously variable autofade depth plus preset threshold control.
- ★ Low noise (—80dB) virtual earth mixing circuitry.
- ★ Up to 0.5W from low distortion push pull monitor amp.
- ★ Response 20Hz—50kHz ± 1dB.
- ★ Low power consumption (20mA at 18 volts).
- ★ Compact—mono version 40cm x 6cm x 3cm. stereo version 40cm x 10cm x 3cm.
- ★ Output —10dBm (240mV) to suit all Saxon amplifiers and most other makes.

MONO VERSION

£18.50

STEREO VERSION

£27.50



SAXON MONO & STEREO DISCOTHEQUE MIXER WITH AUTOFADE

SAXON ENTERTAINMENTS LTD.

WHITE HORSE ROAD
CROYDON, SURREY CR0 2HS

SYSTEM 7000

PROFESSIONAL STANDARD COMPLETE UNITS

A total range project to satisfy the most discerning.

- ★ STAINLESS STEEL ESCUTCHEONS*
- ★ TOTALLY COMPATIBLE WITH ALL SAXON MODULES
- ★ TOUGH EASILY READ FACIA
- ★ PLUG ISOLATED TERMINALS THROUGHOUT.




MINOTAUR 100

- ★ 100 W.r.m.s. into 8Ω.
- ★ Two mixed inputs, wide range bass & treble controls.
- ★ May be operated as a slave amplifier.

- ★ Extremely compact (27cm x 16cm x 10cm).
- ★ Fully protected against all incorrect loads and short circuits.
- * Except Minotaur (anodised aluminium).

£47.50

SYSTEM 7000 DISCO CONTROL UNIT

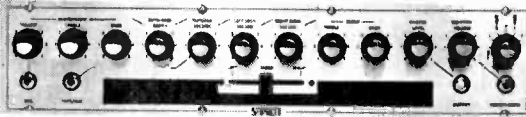

- ★ Mono or stereo.
- ★ 2 Deck and one tape inputs, individually controlled plus L/R deck fader (ineffective at central).
- ★ Wide range bass and treble controls plus separate MIC volume bass and treble controls. Overall master control.
- ★ Continuously variable autofade depth and threshold.

- ★ Five position monitoring switch with two mute positions—ample headphone power.
- ★ Complete, cased with all terminations by plug/socket etc.
- ★ Noise—80 dB Response 20Hz-50 kHz ± 1dB.

Mono £28.50

Stereo £45.00

SYSTEM 7000 MODULAR MIXING—UP TO 20 CHANNELS

Complete versions of the IM7001 and IM7002 modules shown in our advertisement make a professional quality versatile mixer to your requirements using these modules mono and stereo inputs may be combined.

- ★ The mixing modules split mono signals.
- ★ Each input module has own monitor switch.
- ★ Stainless steel panel on 15cm x 5cm matrix (approx.)
- ★ Input equalisation for all types of signal inc. magnetic cartridge.
- ★ Complete system may comprise twenty channels, mono or stereo with ample monitoring power.
- ★ May be patched in with disco mixers or minotaur amplifier.



Mono Input module £8.50

Mono Mixer Module £8.50

Stereo Input Module £12.00

Stereo Mixer Module £12.00

Power Supply Unit for up to 20 Modules £7.50

SYSTEM 7000 LIGHTING CONTROL UNIT

- ★ 1000 watts per channel. Sound light and SEQUENTIAL and OVERRIDE.
- ★ Individual control of bass middle and treble.
- ★ Master control for easy adjustment.
- ★ Plug/socket terminations throughout.
- ★ Slider control for function, allows sound/light, sequencing or combination of both.
- ★ Stainless steel front panel to match disc control unit.
- ★ Compact (17 cm x 10 cm x 10 cm approx.).
- ★ Electronic override eliminates clicks.
- ★ High sensitivity, negligible input power.

£35.00



ALL SAXON MODULES AND UNITS ARE GUARANTEED FOR TWO YEARS FROM DATE OF PURCHASE.

TO ORDER TELEPHONE 01 684 6385 NOW. FOR INFORMATION RING 01 684 0098 WE ACCEPT TELEPHONE ORDERS FOR COD AND ACCESS/BARCLAYCARD ACCOUNT HOLDERS.

IF ORDERING BY POST PLEASE SEND CHEQUE/CROSSED POSTAL ORDERS MADE PAYABLE TO SAXON ENTERTAINMENTS, OR ENCLOSE YOUR ACCESS/BARCLAYCARD NUMBER.

TRADE ENQUIRIES:

TO NORMAN ROSE ELECTRICAL LTD AT ANY BRANCH.
LONDON TEL: (01) 837 9111 BIRMINGHAM (021) 236 4718
MANCHESTER (061) 273 1408 BRADFORD (0274) 24006

ALL PRICES INCLUDE POST & PACKING BUT V.A.T. AT 8% MUST BE ADDED TO VALUE OF ORDER.

Shop Hours Monday to Saturday 9.00 a.m.—5.00 p.m.
Telephone as shown above.

The sound match maker

Every month Practical Hi-Fi & Audio carries an updated matching hi-fi guide. With this detailed knowledge, you can now choose your components and assemble a quality system with confidence.

There is also regular coverage of hi-fi developments and commonsense advice on hi-fi problems.


A sound match of practical hi-fi and audio

PRACTICAL HI-FI & AUDIO

Every month 30p

NEW Motorcycling Monthly takes to the road

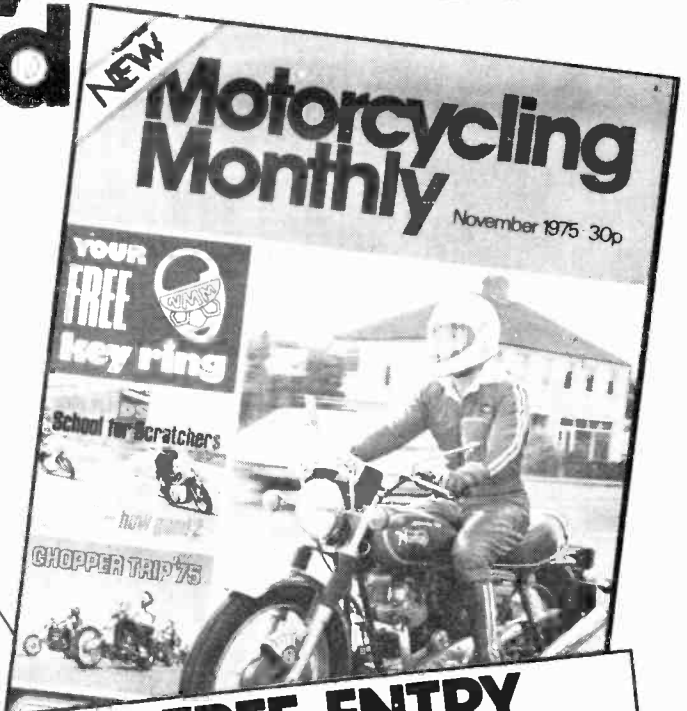
It's the exciting new-look mag that's tuned to today's biker... there'll be exhaustive 10,000 km road tests – the most comprehensive ever – as well as performance impressions of the newest machines... technical analyses and tuning... and features on customising. All this plus all the fun, colour and excitement of the fast-moving motorcycling scene. Give No. 1 a ride.



FREE

The New Motorcycling Monthly Key ring

(It's steel, so it's tough and durable)

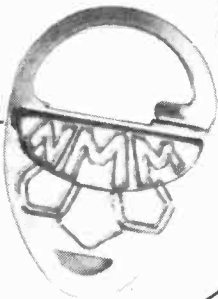

GREAT FREE-ENTRY COMPETITION-WIN A DREAM BIKE

– The winner takes his choice from 15 models each worth up to £1,300; with 150 runners-up prizes of Rivett's V.P. Touring gloves and Melton helmet visors.

... and there are lots more good reasons for shooting your bike down to the newsagent's right now!

NEW RIDE IN STYLE EVERY MONTH WITH
Motorcycling Monthly
No. 1 (NOVEMBER ISSUE)
OUT NOW 30p

POWER UNIT Type A126

Supplying 6, 7.5 or 9 Volt DC at 200 mA.

In moulded case forming a 2 pin 5A mains plug.

2 metre output lead with 4-way multiple giving 2.1 and 2.5 mm sockets and 3.5 mm plug.

Price £2.80. Post 10p.



2" and 4" PANEL METERS

SIZE: 60mm Wide x 45mm High x 40mm Deep.	SIZE: 110mm Wide x 82mm High x 43mm Deep.
Movement	I.R. Ohms
0-50 micro A.	1250
0-100 micro A.	580
0-500 micro A.	170
0-1 mA	170
0-5 mA	170
0-10 mA	6
0-50 mA	0.5
0-100 mA	0.5
0-500 mA	0.5
0-1 AMP	0.5
0-2 AMP	0.5
0-25 Volt	15K
0-50 Volt	50K
0-300 Volt	300K
"g" Meter	170
VU Meter	5250

VU Meters are complete with detectors. Modern wide view. Price 2" £3.20 Post 10p. Price 4" £4.00 Post 10p. Lamps 60p per set.

1/4 watt CARBON FILM RESISTORS

1/4 watt at 70°C E 12 range 10Ω-1M Ω 5% tol above 470 K Ω 10% tol at 95p per 100.

C1000 MULTIMETER

Special Offer
Compact General Purpose Mini Multimeter. Input Resistance 1000 ohms per volt.
Ranges:
AC Volts 0-15, 50, 250, 1000 V
DC Volts 0-10, 50, 250, 1000 V
DC Current 0-1 mA, 0-100mA
Resistance 0-150K ohms
Size 80 x 24 x 90 mm
Complete with Batteries, Test Prods, Instructions. Special price £3.35 Post 30p.



C1001 MULTIMETER

Input Resistance 20,000 ohms per volt
Overload Protection
150 μA movement, clear scale
Ranges—AC Volts 0-10, 50, 250, 1000V
DC Volts 0-5, 25, 125, 500, 2500V
DC Current 0-50 mA
Resistance 0-80 Kohms, 0-6 Mohms
Decibels -20 to +22 dB
Carrying Case, Test Prods and Batteries included.
Size: 115 x 83 x 27 cm.
Price £9.85. Post 20p.

TRANSFORMERS

CASED TRANSFORMERS

Housed in smart resin-coated steel cases, with 3-core power cable and outlet socket, fused primary winding. Isolation types are fitted with 3-pin outlet sockets, and are available with 110 volt or 240 volt output. (Please state). Auto types are fitted with 2-pin flat style sockets up to 500 VA. 3-pin sockets from 750 to 3000 VA. See Auto and Isolation sections for prices.

SAFETY ISOLATING

Prim. 120/240V. Sec. 120/240V. Centre Tap with Screen.

VA (watts)	Ref. No.	Price Cased £	Price Plugs 2 Pin + 1 Earth £	Price Open Post £
60	149	8-60	8-88	4-37
100	150	9-40	8-88	4-90
200	151	11-70	8-88	8-14
250	152	13-15	8-88	9-80
350	153	15-75	8-88	11-88
500	154	17-50	8-88	13-82
750	155	27-35	1-10	20-59
1000	156	35-65	1-10	29-15
1500	157	42-25	1-10	33-37
2000	158	49-95	2-84	37-10
3000	159	73-50	2-84	58-55

12 & 24 Volts Prim. 200-240V.

Amps	Ref. No.	Price £	Post £
12V	24V		
0-3	0-15	2-42	1-58
0-5	0-25	1-11	1-38
1	0-5	2-13	1-74
2	1	3-71	2-30
4	2	5-18	2-96
6	3	7-0	4-18
8	4	10-8	4-56
10	5	12-72	5-20
12	6	11-6	5-41
16	8	17	7-00
20	10	11-5	10-42
30	15	18-7	13-25
40	20	23-2	14-85
60	30	22-6	16-83

30 Volts

Prim. 200-240V. Amps	Ref. No.	Price £	Post £
0-5	112	1-90	0-47
1	79	2-40	0-66
2	3	3-50	0-66
3	20	4-50	0-64
4	21	5-15	0-72
5	51	6-40	0-72
6	117	7-16	0-88
8	88	9-55	0-95
10	89	9-87	0-95

AUTO TRANSFORMERS

VA Watts	Ref. No.	Price Cased £	Price Plugs 2 & 3 pin £	Price Open £	Post £
Tapped at 115, 220, 240 Volts	20	113	4-10	0-20	1-71
Tapped at 115, 200, 220, 240 Volts	150	4	6-45	0-20	4-12
	200	65	7-30	0-20	4-95
	300	66	8-25	0-20	5-81
	500	67	11-25	0-20	8-85
	750	83	14-10	0-85	10-80
	1000	84	17-50	0-85	13-85
	1500	93	22-15	0-85	18-81
	2000	95	33-40	1-80	24-25
	3000	73	48-20	2-10	35-10

50 Volts

Prim. 200-240V. Sec. 19, 25, 33, 40, 50V. Amps	Ref. No.	Price £	Post £
0-5	102	2-58	0-47
1	193	3-48	0-56
2	104	5-03	0-64
3	105	5-91	0-72
4	106	7-58	0-88
6	107	12-30	0-95
8	118	18-20	1-13
10	119	17-02	O.A.

60 Volts

Prim. 230-240V. Sec. 24, 30, 40, 45, 60V. Amps	Ref. No.	Price £	Post £
0-5	124	2-30	0-56
1	126	3-41	0-56
2	127	5-09	0-72
3	125	7-52	0-80
4	123	8-75	0-95
5	40	9-75	0-95
6	50	11-20	1-01
8	121	15-00	1-19
10	122	18-20	O.A.
12	189	18-50	O.A.

MINIATURE AND EQUIPMENT

Prim. 240V with screen.

Sec. 1 Volts	Sec. 2	Milliamps	Ref. No.	Price £	Post £
3-0-3	—	200	238	1-50	0-25
0-6	—	500	234	1-38	0-25
0-6	—	1000	212	1-90	0-47
9-0-9	—	100	13	1-40	0-25
0-9	—	330	235	1-50	0-25
0-8-9	—	500	207	1-83	0-34
0-8-9	—	1000	208	2-76	0-47
15-0-15	—	40	240	1-35	0-25
20-0-20	—	200	236	1-38	0-25
0-20	—	30	241	1-35	0-25
0-20	—	150	237	1-38	0-25
0-15-20	—	500	205	2-73	0-56
0-20	—	300	214	1-93	0-47
0-20	—	3500	NO SCREEN	1-16	0-64
20-12-0-12-20	—	700 (D/C)	221	2-50	0-47
0-15-20	—	1000	206	3-50	0-56
0-15-27	—	500	203	3-00	0-56
0-15-27	—	1000	204	3-85	0-56

PLASTIC CASED SILICON BRIDGE RECTIFIERS

One Amp	Two Amp	Four Amp	Six Amp
50 P.I.V. 20p	50 P.I.V. 35p	100 P.I.V. 55p	50 P.I.V. 65p
100 P.I.V. 25p	100 P.I.V. 40p	200 P.I.V. 59p	100 P.I.V. 70p
200 P.I.V. 23p	200 P.I.V. 45p	400 P.I.V. 65p	200 P.I.V. 80p
600 P.I.V. 30p	400 P.I.V. 60p	600 P.I.V. 75p	400 P.I.V. 90p

ADD 10p P & P PER ORDER

PLEASE
ADD
VAT

POWER UNIT Type CC 12-05

Output switched 3, 4.5, 6, 7.5 and 12 volts at 500 mA D.C. Operates from 240 V mains, suitable for Radios, Tape Recorders, Record Players etc. Size 7.5 x 5.0 x 14.0cm. Price £4.05. Post 30p.



MINIATURE NEONS

6mm dia., 12mm length leads length approx. 20mm. Recommended ballast resistor 150K ohms for 240 Volt operation. Price: Packet of 10 for 60p. Postage 15p.

A.S.P. LTD.

DEPT PW9, SIMMONDS ROAD, WINCHEAP, CANTERBURY, KENT. Tel: (0227) 52436

Send 25p for Catalogue

poly-planar

20-Watt Full Range Speaker

Completely replaces the conventional cone speaker
Super-thin construction permits new installation ideas.



Power capability: 40 watts peak. Frequency range: 40 Hz-20 KHz
Sensitivity: 85 dB/M for 1 watt electrical input. Input Impedance: 8 ohms. Operating temperature range: -20°F to +175°F. Size (WxDxL): 1-7/16" x 1-13/4" x 14-11/16". Weight: 19 ounces.

£8.50 each Stereo pair £16.50

INCLUSIVE OF VAT AND POSTAGE

web europa

P.O. Box 9, Ruthin Clwyd

TV SPARES AND COMPONENTS

IF Sub-Assembly (Philips G8) £6.80. P & P 45p.
Mullard ELC 1043 Varicap VHF Tuner £4.20. P & P 30p
3-way Station Control Unit £1.20. P & P 25p
(Post and packing if all 3 items ordered 50p)

And other parts available for The Practical Wireless T.V. Sound project.

Callers welcome at shop premises.

MANOR SUPPLIES

172 WEST END LANE, LONDON NW6

(Near W. Hampstead Tube Stn.) Tel. 01-794 8751

DIABOLICAL LIBERTIES!

With an antenna just 230 cm long!!—Only the **WORLD RECORD PARTRIDGE VFA** gets away with it—it works better in the clear **HONESTLY!!!**

**These are VFA USERS claims, and remember, SWL's, A GOOD TRANSMITTING AERIAL IS AN EQUALLY GOOD Receiving AERIAL—You sure can't work 'em if you can't hear 'em!*

ZLIASY worked GC3EML on the 20m. band with ***"JOYSTICK lying ON FLOOR OF SHACK!"**

G2BAH (ex G4CJN), Kendal, reports: "I happened to be listening on 80m. and heard someone in Manchester testing. We established a strength 8 qso each way. He had a ***VFA** laying on his kitchen table and was making tests to see if it would load up, etc. An old timer, a G2 and 2 letters, so he knew what he was doing."

G3ZDR worked a W3 on 20m. using a ***VFA** and a PM3A with 2 watts.

G3VFA worked WITW on 20m. using a ***VFA** and 750mW.

W6TYP worked WA6JPR over hundreds of miles on 40m. using ***VFA** and microwatts "equivalent to ONE MILLION!!! miles per watt of input power" (So says his **WORLD RECORD** achievement certificate).

P.W. "ON THE AIR" feature reports "Terry Gilbert sends a logging of a **VERY RARELY** reported station, Radio Afghanistan on 15195 at 1130. This goodie was pulled in via a Codar CR70A and **"JOYSTICK"**.

THE PARTRIDGE VFA SYSTEM to put YOU in the **WORLD RECORD** class is:—SYSTEM 'A' for modern Comm RX's **£32.76**: SYSTEM 'J' 500W P.E.P. 6 bands **£40.72**.

NEW! THE FLAT DWELLER'S ANSWER!! THE BIG BREAKTHROUGH—ENJOY THE ADVANTAGES OF OUTDOOR SPACE WITHOUT THE OUTDOOR SPACE!! SYSTEM RC1 (RX) £35.81; SYSTEM RC2 (TX/RX) £44.72: THIS IS ANOTHER PARTRIDGE FIRST—WRITE FOR DETAILS (7p).

(Each **SYSTEM** consists of the elegant gold stove enamelled 7' 6" VFA and a matching finish **JOYMATCH A.T.U.**, despatched direct by parcel post—our risk) (All prices delivered—our risk). Prices subject to alteration without notice. COMMUNICATIONS HEADPHONES 8 OHMS **£4.82**; R.F. Field Strength meter (Jap) **£2.10** 9R59DS-DE, replacement valves incl. OA2 **£6.12**; A.G.T.U. Art earth **70p** plus radials **72p** each.

PARTRIDGE SUPER PACKAGE

COMPLETE RADIO STATION FOR ANY LOCATION. Comprising: Trio QR666 Gen. Cov. RX, Headphones VFA., System 'A', all connecting cables, del. (our risk)

£185.18

Send stamp for details and expert advice.



Phone 0843 62535
or 62839
(after office hours)
G3CED G3VFA



CLEARANCE BARGAINS

Special Offer metallised Polyester Capacitors by Erie, Mullard, etc. Values include .01/160V, .01/250V, .015/160V, .022/160V, .033/160V, .047/160V, .068/160V, .1/160-250V, .22/160V, etc. This is a bargain not to be missed, 100 for **£2.00**.

Assorted Capacitors, Silver Mica, Tubular and Disc Ceramics, Polystyrene, tremendously good selection. 300 for **£1.70**

Mullard Ferrite Cores LA3, 54p, LA4, 81p, LA2100, 54p. Out of Spec. 2N3055. 5 for **£1.08**

Ceramic Formers L23mm, Dia 13mm bore, 1 end 8mm other 4mm. 100 for **£1.88**

Rotary Switches, very good quality IP x 18W x 3 BANK. 65p All prices include V.A.T. and U.K. postage.

Mail Order Only.

XEROZA RADIO,

1, EAST STREET, BISHOPS TAWTON, DEVON,

PLEASE MENTION
PRACTICAL WIRELESS
WHEN REPLYING TO
ADVERTISEMENTS

RECHARGEABLE BATTERIES

CAN SAVE YOU A FORTUNE!
Bush & Meissner's two purpose-built battery chargers for economy minded enthusiasts:

The "KESTREL-DOWN" Charger **£11.31** for Alkaline rechargeable batteries, no-load voltage of 1.5 volts per cell, for the following sizes ALKALINE (All prices ex-VAT)
Equivalent to

to	Type	Capacity	PRICE
U2 size	SA-13D	2Ah	£1.73
U11 size	SA-14C	1Ah	£1.13
U7 size (pencil)	SA-15AA	0.3Ah	£0.36p

NICKEL-CADMIUM (All prices ex-VAT)
The "DAIMON" Charger **£9.76** for Nickel-Cadmium batteries, no-load voltage of 1.25 volts per cell, for the following sizes

Type	Capacity	PRICE
NCC400	4Ah	£3.64
NCC200	2Ah	£2.48
NCC50	0.5Ah	£1.45

Charger designed to give optimum results with a specific type of cell. Never be without power, day or night.

*Note, under no circumstances must Alkaline batteries be used with the Daimon charger.

S.A.E. brings full details

Bush & Meissner

Importers & Distributors
Dept LS260
275 West End Lane,
London NW6 1QS
01-794-9611



Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 14p per word (minimum 12 words), box number 35p extra. Semi-displayed setting £12.00 per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd. Fleetway House, Farringdon Street, London, EC4A 4AD for insertion in the next available issue. (01-634 4451).

Receivers and Components

COMMUNICATIONS RECEIVER modules. Small superhet circuit boards requiring only controls and tuned circuits. 9 volt. Mosfet mixer, IC IF, BFO, Prod. Det. Excellent AM/CW/SSB results reported by delighted users. From £11.50. SAE details. PR Goldledge Electronics, Millend, Stonehouse, Glos.

UNBELIEVABLE SPEAKER BAR-GAINS! 8Ω Acoustic Suspension, teak/sculptured foam front, 6 watt £5.30; 12 watt £6.50; 16 watt (8in woofer, 3in tweeter) £7.90. (Lists 20p.) Satisfaction guaranteed (10% p&p). Gregg Electronics, 105 Grange Road, London SE25.

BRAND NEW COMPONENTS BY RETURN: Electrolytics—16V, 25V, 50V—0.47, 1.0, 2.2, 4.7, 10 mfd.—5p. 22, 47—5½p. (50V—6p) 100—7p. (50V—8p), 220—8p. (50V—10p), 500—11p. (50V—16p), 1000/25V—18p. Subminiature bead-type tantalums—0.1/35V, 0.22/35V, 0.47/35V, 1.0/35V, 2.2/35V, 4.7/35V, 10/20V, 22/16V, 47/6V, 100/3V.—11p. Mylar Film 100V—0.001, 0.002, 0.005, 0.01, 0.02.—3p. 0.04, 0.05—3½p. Mullard tubular polyester 400V E6 series 0.001-0.022—3½p. 0.033-0.1—4½p. Mullard miniature C333 ceramics 63V E12 series 2%, 1.8 pf.—47 pf.—5p. 56 pf.—330 pf.—3½p. Polystyrene 63V E12 series 10 pf.—1000 pf.—3p. 1200 pf.—10,000 pf.—4p. Miniature Highstab. carbon film resistors ½W E12 series 5% 1Ω-10MΩ. (10% over 1MΩ) 1.2p. Postage 10p. Prices VAT Inclusive. The C.R. Supply Co., 127, Chesterfield Road, Sheffield S8.

CLEARING DISTRIBUTOR STOCKS, transistors, diodes, components, etc. Sample pack 65p incl. postage or send stamp for list. Redhawk Sales Ltd., 10 Maple Lodge Close, Rickmansworth, Herts. Mail Order Only.

Bargain Relpak Tested Semiconductors
R1. 10NPN, SIL, T092—75p IN4001—6p
IN4006—13p R2. 10PNP, SIL, T092—75p
IN4002—7p IN4148—6p R3. 10NPN,
SIL, T018—75p Zeners—2 to 33V—9p
R4. 10PNP, SIL, T018—75p Philips Pots:
Lin: 1K to 2M2—16p. LISTS 25p.
Export enquiries welcomed. Deduct 8% VAT. Mail
Order only. Satisfaction guaranteed or money back.
P. & P. and VAT included.
RELTRON LIMITED
(Dept. P.W.), P.O. Box 18, Camberley,
Surrey

NICKEL CADMIUM Cylindrical Accumulators. Sealed. High power/weight ratio. All sizes: 1.2V, 1.2Ah (SP11 size approx.), weight 50gm, £1.94 each. Heavy duty (U2 size approx.), 150gm, 4Ah, 1.2V, £4.15 each. Others include 450mAh, 1.2V (HP7 size approx.), £1.56 each; 2.5Ah, 1.2V, £3.49 each. Ultra heavy duty, 6Ah, 1.2V (60 amp for 5 mins.), £5.71 each. Special 9V transistor radio battery (PP3 size approx.), £3.80 each. Current limiting chargers from £8.09. Further information and sales from Sandwell Plant Ltd., 1 Denholm Road, Sutton Coldfield, West Midlands. 021 354 9764.

BETA DEVICES			
MANUFACTURERS BRANDED PRODUCTS			
TRANSISTORS	DIODES & RECT.	BRIDGE RECT.	
AC187/8 PR 0.40	IN814	0.04	1A 100v W01.0.20
BC107/8/9 0.09	IN4148	0.04	1A 200v W02.0.22
BC109C 0.11	BY127	0.14	1A 600v W06.0.30
BC147/8/9 0.10	IN4001/2	0.05	25A 200v £2.00
BCY7071/720 18	IN4003/4/5	0.06	ZENERS
BFX88 0.20	IN4006/7	0.08	BZY88c 3.3.
BFY60 0.18	IN5401	0.11	33v 5% 0.09
BFY61/52 0.12			1 watt 6.8.
2N1132 0.25	3016F	1.00	200v 5% 0.16
2N1711 0.25	DL747	2.45	LED
2N2846 0.30	TR4800	0.90	209-RED 0.17
2N2905A 0.21	565 Timer	0.50	LED CLIP 0.02
2N3053 0.14			OP. AMP. IC's
2N3055 0.38	D.I.L. SOCKETS		709C T099 0.80
OC28 0.45	8 Pin	0.12	709C D.I.L. 0.80
OC35 0.35	14 Pin	0.12	741C T099 0.36
OC28 0.45	16 Pin	0.14	741C D.I.L. 0.38
OC36 0.35			728C D.I.L. 0.80
TIP41A 0.74			747C D.I.L. 0.85
TIP42A 0.90	ADD 17% V.A.T.		748C D.I.L. 0.36
7400N 0.16	74 SERIES TTL	74121N	0.60
7404N 0.18	7447N	1.00	74123N 1.28
7410N 0.18	7474N	0.87	74141N 1.13
ALUMINIUM ELECTROLYTIC CAPACITORS			
10µF	22µF	47µF	100µF 220µF 470µF 1,000µF
16v 0.07	0.07	0.10	0.12 0.14 0.22
25v 0.07	0.07	0.08	0.10 0.13 0.16 0.26
C.W. PLUS P.P. 15p TO BETA DEVICES, 4, Highbridge Street, Waltham Abbey, Essex.			

VALVES, RADIO-TV-TRANSMITTING-INDUSTRIAL 1930 to 1975. 2200 types stocked. Many obsolete. SAE for quotation. List 20p Postal Export Service. We purchase new and boxed valves. Cox Radio (Sussex) Ltd., The Parade, East Wittering, Sussex. West Wittering 9223.

ELECTROLYTIC 50V—0.47, 1.2, 2.2, 4.7, 10µF, 5p; Mylar Film 100V—0.001, 0.002, 0.005µF, 2p; Polyester 250V—0.01 to 0.047µF, 3p; 0.068, 0.1µF, 4p; 0.15, 0.22µF, 6p; 0.33µF, 7p; 0.47, 9p; Polystyrene 10pF—8,200pF, 3p. Bead-type Tantalums, 11p; Resistors—¼W, 1.5p; 1W, 2p; Zeners, 10p. Inclusive prices. P&P 10p. SAE list D. Coulam, Thimbleby, Horncastle, Lincs.

COMPONENTS GALORE, pack of 500 assorted Radio, TV and Electronic components, a real bargain at a realistic price. Send only £1.50 c.w.o. This applies only to United Kingdom and Ireland. Overseas prices by arrangement. Caledonian Components. PO Box 3, Glenrothes, Fife, Scotland.

Precision Polycarbonate Capacitors

All High Stability—Extremely Low Leakage
440V AC RANGE 63V DC RANGE
Value Dimen- Price Axial or Radial leads
(µF) (mm) each available: Value µF ±1% ±2% ±5%

0.1µF	27	12.7	51p	0.01µF	60p	49p	42p
0.15µF	27	12.7	7p	0.1µF	60p	49p	42p
0.22µF	33	16	64p	0.22µF	67p	50p	43p
0.25µF	33	16	67p	0.33µF	67p	50p	43p
0.33µF	33	16	75p	0.47µF	67p	50p	43p
0.47µF	33	19	80p	0.68µF	74p	53p	46p
0.5µF	33	19	87p	1.0µF	82p	62p	52p
0.55µF	50.8	19	86p	1.5µF	82p	62p	52p
1.0µF	50.8	19	1.03p	2.2µF	98p	75p	61p
1.5µF	50.8	25.4	1.21p	3.3µF	11.15	82p	68p
2.0µF	50.8	25.4	1.44p	4.7µF	11.02	11.13	94p
INTEGRATED Circuits				6.8µF	11.96	11.38	11.13
NE555 Timer	61p	10µF	22.40	11.95	21.64		
741C 8 Pin DIL	32p	15µF	23.22	22.79	23.24		
ZR414	1.15	22µF	24.28	23.68	23.08		

TANTALUM BEAD CAPACITORS—Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 15V/25V or 35V; 10.0µF at 16V/20V or 25V; 22.0µF at 6V/10V or 16V; 33.0µF at 6V or 10V; 47.0µF at 3V or 6V; 100.0µF at 3V. ALL at 10p each, 10 for 95p, 50 for 24.

TRANSISTORS: BC183/183L 11p BFV60 20p
BC107/8/9 9p BC184/184L 12p BFV61 20p
BC114 18p BC221/21L 14p BFV52 20p
BC147/8/9 10p BC347/308A 12p AF178 80p
BC183/7/8 12p BF194 18p OC71 18p
BC182/182L 11p BF197 18p 2N3055 50p

POPULAR DIODES—IN914 6p, 8 for 45p, 18 for 90p; IN916 5p, 8 for 45p, 14 for 90p; 1844 5p, 11 for 60p, 24 for 1.00. IN4148 5p, 8 for 27p, 12 for 48p; IN4001 6p; 009 6p; 009 81p; 004 7p; 006 7p; 006 8p; 007 81p. **LOW PRICE ZENER DIODES**—400mW, Tol. ±5%, at 5mA. Values available: 3V, 3.3V, 3.6V, 4.7V, 5.1V, 5.6V, 6.2V, 6.8V, 7.5V, 8.2V, 9.1V, 10V, 11V, 12V, 13V, 15.5V, 16V, 18V, 20V, 22V, 24V, 27V, 30V, 33V. All at 7p each, 5 for 33p, 10 for 65p. **SPECIAL OFFER:** 100 Zeners (may be mixed) for 28.00.

RESISTORS—High stability, low noise carbon film 5%, 1W at 40p, 1W at 70p. E12 series only from 2.2Ω to 2.2MΩ. ALL at 1p each, 8p for 10 of any one value, 70p for 100 of any one value. **SPECIAL PACK:** 10 of each value 2.2Ω to 2.2MΩ (730 resistors) 85.

SILICON PLASTIC RECTIFIERS—1.6 amp, brand new wirewound DO27: 100 P.I.V. 7p (4 for 28p); 400 P.I.V. 8p (4 for 30p).

BRIDGE RECTIFIERS—2½ amp: 200V 40p; 350V 45p; 600V 55p.

SUBMINIATURE VERTICAL PRESETS—0.1W only: ALL at 5p each: 60Ω, 100Ω, 220Ω, 470Ω, 680Ω, 1kΩ, 2.2kΩ, 4.7kΩ, 6.8kΩ, 10kΩ, 15kΩ, 22kΩ, 47kΩ, 100kΩ, 250kΩ, 500kΩ, 1MΩ, 2.5MΩ, 5MΩ. £.

PLEASE ADD 15p POST AND PACKING ON ALL ORDERS BELOW £5. ALL EXPORT ORDERS ADD COST OF 85p/AIRMAIL.

PLEASE ADD 25% V.A.T. TO ORDERS. Send S.A.E. for lists of additional ex-stock items. Wholesale price lists available to bona fide companies. **MARCO TRADING (Dept. W11),** The Old School, Edstaston, Nr. Wem, Shropshire. Tel: Whittall 464/465 (STD 094 872) (Propra. Minicost Trading Ltd.)

Aerials

GENUINE FULL SIZE 18 element TV aerial as used by leading TV companies

FOR ONLY £2.85 (incl. VAT) +77p car

Save ££s. We supply this genuine U.H.F. aerial for only £2.85 can be fitted outside or inside. Quality made technically advanced design. Precision grid reflector eliminates ghosting. Complete with clamp, instructions, advice. Money Back Refund. Wall/Caravan Bracket 25p. Best Cable 12p per yard. Plug TOP & FREE with order maps & channel reference of Radio & TV Transmitters. Send direct to Dept. PW11 219 Mansfield Rd. Nottingham

IMPERIAL TRADING (AERIALS) LTD.
The quality Aerial Specialists

NEW HIGH GAIN 4 ELEMENT VHF, FM Stereo or mono!

Increase volume, quality and sensitivity of any VHF/FM Radio or Hi-Fi stereo or mono with this genuine aerial. It is a necessity if you want the best out of your equipment whether a small radio or expensive stereo. Don't put up with poor reception any longer. Send now hear for yourself. Ideal for the do it yourself enthusiast. Supplied with clamp, instructions and advice. Use inside or out! FREE with order maps and channel reference of all Radio and TV Transmitters. Money Back Refund. Send Direct to Dept PW11 219 Mansfield Rd., Nottingham

ONLY £4.49 (incl. VAT) +86p P&P

Best cable 12p/yard

IMPERIAL TRADING (AERIALS) LTD.
The quality Aerial Specialists

SERVICE SHEETS. SERVICE MANUALS PRACTICAL AND TECHNICAL BOOKS

COVERING COLOUR & MONO TELEVISIONS, RADIOS, RECORD PLAYERS, TAPE RECORDERS, ETC.

SERVICE SHEETS 50p PLUS S.A.E. SERVICE SHEET CATALOGUE 25p

BOOKS

Prices include Postage U.K. only

TV FAULT FINDING BOOK by DATA PUBLICATIONS LTD.	£1-05
COLOUR TELEVISION SERVICING by KING	£4-90
COLOUR TELEVISION THEORY by HUTSON	£5-40
MAZDA BOOK OF PAL RECEIVER SERVICING by SEAL	£5-20
NEWNES COLOUR TV SERVICING MANUAL VOL. 1 by KING	£5-40
NEWNES COLOUR TV SERVICING MANUAL VOL. 2 by KING	£5-40
BEGINNERS GUIDE TO COLOUR TELEVISION by KING	£2-25
COLOUR TELEVISION (PAL SYSTEM) by PATCHETT	£5-25
BEGINNERS GUIDE TO TELEVISION by KING	£1-95
PAL-D COLOUR RECEIVER Q. & A. by BOHLMAN	£1-85
TELEVISION TIMEBASE CIRCUITS by BANTHORPE	£1-20
STEREO F.M. RADIO HANDBOOK by HARVEY & BOHLMAN	£2-70
UNDERSTANDING ELECTRONIC COMPONENTS by SINCLAIR	£3-50
CREATIVE TAPE RECORDING by CAPEL	£3-50

(Send large S.A.E. for free booklists)

COLOUR TV MANUALS

Covering following makes:

Alba, BRC, Decca, Defient, Dynatron, Ekco, Ferguson, GEC, HMV, ITT-KB, Pye, Invicta, Marconi, Philips, RGD, Sobell, Stella, Ultra.

Please send S.A.E. for quotation.

"COMPREHENSIVE TV REPAIR MANUALS"

by McCOURT. In 7 volumes

These unique books save time and money on repairs and cover most British & Foreign makes. Price £3-50 per volume plus 35p post or complete 7 Volumes for only £22-50.

We stock new and secondhand editions of "RADIO AND TELEVISION SERVICING" Books. From Volume One up to 1974-75 Edition
Prices on request.

Back issues of following magazines available. Cover price plus 10p postage:

P. WIRELESS, P. ELECTRONICS, E. ELECTRONICS, TELEVISION, R. CONSTRUCTOR, ELECTRONICS TODAY

BELL'S TELEVISION SERVICES

190 KINGS ROAD, HARROGATE, N. YORKSHIRE. TEL. HARROGATE (STD 0423) 55885

Open to callers daily 9.0 to 5.0 p.m. Please include an S.A.E. with enquiries.

SERVICE SHEETS for Radio, TV, Tape Recorders, Stereo, etc., with free fault-finding guide, 50p and SAE, Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)
ALL AT 50p EACH

"PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS"

Otherwise cannot be attended to

(Uncrossed P.O.s please, original returned if service sheets not available.)

PLEASE NOTE

We operate a "by return of post" service. Any claims for non-delivery should be made within 7-days of posting your order.

C. CARANNA

71 BEAUFORT PARK
LONDON, N.W.11 6BX

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative. Free TV fault tracing chart or TV list on request with order.

Mall order or phone 01-458 4882

NO OVERSEAS MAIL PLEASE

SERVICE SHEETS, radio, TV etc. 10,000 models. Catalogue 24p, plus SAE with orders, enquiries. Telfray, 154 Brook Street, Preston PR1 7HP.

Situations Vacant

**MEN!
£90 p.w.
can be yours**

Tens of thousands of new computer personnel needed over the next few years alone. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks!

It can pay around £35 p.w. as a starter and can reach over £90 p.w.

After training, our executive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or phone TODAY, without obligation.

London Computer Operators Training Centre

Y29, Oxford Hse.,
9-15 Oxford St. W1. Tel: 01-734 2874

OPPORTUNITY arises in North London company for Electronics Engineer to assist in design and development. Qualifications are 2 years or more commercial experience plus technical training in electronics. Age limit 25. Phone 808-3719 or write Box No. 127.

Ladders

LADDERS, timber and aluminium. Tel: Telford 586644 for brochure.

Educational

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

BE A SUCCESSFUL TV ENGINEER. Join our full-time Two-Year College Diploma Course, specially designed to cover the examinations of the City and Guild Radio, Television and Electronics Technicians' Certificate. Full theoretical and practical instruction on all types of modern receivers including the latest colour sets. Enrolments are now under way for January 1976. Minimum entrance requirements are Senior Cambridge or 'O' Level, or equivalent in Mathematics and English. Contact us for free prospectus. **THE PEMBRIDGE COLLEGE OF ELECTRONICS**, 34a Hereford Rd., London W2 5AJ. Tel: 01-229 9117.

Wanted

WE BUY New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S**, 55 Worcester Street, Wolverhampton.

TOP PRICES PAID for NEW VALVES and TRANSISTORS

popular T.V. and Radio types.

KENSINGTON SUPPLIES (C),
367 Kensington Street, Bradford 8,
Yorkshire.

WANTED A.F.U. and stereo F.M. tuner for Sinclair Stereo 60 system. M. Stanley, 9, Ormiston Gardens, Belfast BT5 6JD.

For Sale

MICROPHONES: AKG D202EI, £45.00; AKG D190C or E, £20.00; AKG D224, £60.00; Sennheiser MD211N, £45.00. All brand new and boxed. Please add 25% for VAT. All other AKG and Sennheiser mikes, SAE for quote. J. J. Francis (Wood Green), Ltd., Manwood House, Matching Green, Harlow, Essex. Tel: Matching 476.

For Sale in the Westcountry. Small, established radio-communication, rental company. Genuine reason for sale, yields on rental alone over £9,000 per annum, plus installations, sundries, etc. Easily run by one person. Offers of £19,000 and over to Box. No. 126.

DISCOLIGHTS. Best! Cheapest! Reliable! Bumper catalogue: Aarvak Electronics, 12a(P) Bruce Grove, N17 6RA. 01-800 8656.

LAMINATE OFF-CUTS FOR PRINTED CIRCUITS. Copper clad 1/16in single/double sided EPOXY GLASS IN ASSORTED SIZES (average 5in x 10in) £1.00 per lb (approx 200 sq.in) Minimum order £1.00. Cash with order please to:— Midland Circuits Limited, 76 Cato Street North, Birmingham B7 5AN.

COPPER CLAD LAMINATE FOR PRINTED CIRCUITS

Single sided 1/16" paper base—1.5p/sq. inch. Single sided 1/16" glass-epoxy—2.0p/sq. inch. Any rectangular sizes cut to your requirements. Please send cash with order. Price includes postage and packing. From: **SIMTECH ENGINEERING LTD** Dedham Road, Ardleigh, Colchester, Essex, CO7 7QA Telephone 0206 230133

Miscellaneous

LOW-COST IC MOUNTING for any size DIL package. 100 pin sockets, 50p. 7 and 8 hole plastic supports, 5p/pair. Quantity rates. SAE details and sample. Trial pack, 50p. (P&P 10p/order.) PKG Electronics, Oak Lodge, Tansley, Derbyshire DE4 5FE.

DON'T LOOK

unless you can resist the temptation to get these super 'attention-getters':

- ★ Pocket-sized **MAXI-VOLT** Big 1/2 inch Spark Generator (instant 15,000 volts!). Ready-made, needs no batteries. Carry it around anywhere. Only weighs about 3 oz. (89g.) send £2.45 for your Maxi-Volt now!
- ★ **Unique TRANSMITTER/RECEIVER Kit.** No licence examinations or tests required to operate this transistorised equipment. Easy to build. Get transmitting. Send £7.95 for yours now!
- ★ **Psychedelic MINI-STROBE Kit.** Take a pocket-sized lightning storm to Disco's & parties. 'Brain-freeze' 'em with vari-speed stop-motion flashes. Includes super case too. Send £3.50 now! (all prices include V.A.T., packing & postage.)

Send remittance to:

BOFFIN PROJECTS,
4 CUNLIFF ROAD,
STONELEIGH, EWELL, SURREY
(Mail order U.K. only)

Or for more details, send 20p for lists

ALUMINIUM PROJECT BOXES

Box No.	Length"	Width"	Height"	Price
7	5 1/2	2 1/2	1 1/2	47p
8	4	4	1 1/2	48p
9	4	2 1/2	1 1/2	48p
10	4 1/2	4	1 1/2	48p
11	4	2 1/2	2	48p
12	3	2	1	38p
13	6	4	2	58p
14	7	5	2 1/2	75p
15	8	6	3	93p
16	10	7	3	£1.14

Prices include VAT (at 8%) but 18p should be added to the total order value for postage and packing. **8 WATT 12 VOLT FLUORESCENT LIGHT KIT** Complete Kit including all components, heatsink, channel, tube, etc.

ONLY £3.49 inc. VAT p & p
Ready Built £4.10 inc. VAT, p & p
Diffuser 50p extra inc. VAT, p & p
Send Cheque or P.O.'s with your order direct to:—
ELECTRONICS DESIGN ASSOCIATES
(Dept. PW9), 82 Bath Street, Walsall WS1 3DE
Phone: Walsall 33652

SUPERB INSTRUMENT CASES by Bazelli, manufactured from heavy duty PVC faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range, competitive prices start at a low 75p. Examples: width, depth, height, 8in x 5in x 3in, £1.55; 10in x 6in x 3in, £2.20; 10in x 8in x 3in, £2.75; 12in x 10in x 3in, £3.60; 8in x 4in x 4in, £1.80; 10in x 6in x 4in, £2.70; 12in x 8in x 4in, £3.60; 7in x 7in x 5in, £2.65; 8in x 10in x 6in, £3.60; 12in x 8in x 7in, £4; 12in x 12in x 7in, £4.40. Plus 8% VAT & 50p postage. Over 200 models to choose from. Prompt despatch. Free literature (stamp would be appreciated), Bazelli, Dept. No. 25, St. Wilfrid's, Foundry Lane, Halton, Lancaster LA2 6LT.

GREENWELD ELECTRONICS AT

★ CHESTER ★

Our warehouse at Tower Wharf, Raymond St, Chester, containing 100 tons of surplus electronic equipment, components, tools, clothing, glassware, paper, adding machines, etc., must be cleared by 1st November.

BLUE PCB INK
ONLY (ETCH ~ RESIST)
75p USE WITH ANY PEN!
(30 cc)

In UK VAT & Post FREE
CWO Please to -
JFH SUPPLIES, 30 BAKER ST., LONDON W1M

ETCH YOUR OWN CIRCUIT BOARD. Printed circuit board, 10in x 5in, complete with etching compound and instructions, 85p. P&P 15p. Ferric Chloride etching compound in 1lb packs complete with instructions, 40p. P&P 25p. Lancashire Mail Order, 6 William Street, Stubbins, Ramsbottom, Bury, Lancs.


BUILD YOUR OWN

You are invited to send S.A.E. for lists of our very extensive range of high quality amplifier, pre-amps, F.M. tuners, instruments. Radiocontrol ignition units and many other kits. Please state requirements.

TELERADIO ELECTRONICS,
325 FORE STREET, EDMONTON,
LONDON N9

MINI ACCUMULATORS

2 volt MULTI-USE
Sealed Lead Acid Rechargeable Cells.
Size L450—1.4" x 1.1" x .44". 3 for £2.15
inc. P. & P.
Size GA2—1.7" x 1.3" x .5". 3 for £2.85
inc. P. & P.
Suits FI-Cord
GARFIELDS, 295 Rye Lane, London, S.E.15



ERNIE

PURLEY RANDOM NUMBERS

MINICOMP 100 6-IC's brilliant Nixie tubes, 3 transistors. Now 5 ranges 1-6 (DICE), 0-9, 0-36 (ROULETTE), 0-59 (POOLS DRAWS) and 0-99. Elegant white case. Built & tested £29.50 inclusive. C.W.O. Mail order only. 1-yr. guarantee.

MICROELECTRONICS

51 Mexfield Road, London SW15 2RG

GIEGER COUNTER TUBES CV2247, ex-equipment (unused) complete with socket £1.50p, 50 uA Moving Coil meter scaled .1-10 milli Rontgens per hour complete with mounting clip. Ex-equipment £1.00p (or one tube and one meter for £2.00p). Smiths Motaysyn Position Indicator and Transmitter, with or without modification will work as an aerial or wind direction monitor, £1.70p, 240° ex-aircraft moving coil meter 1mA FSD, scaled 0-110% with coloured sectors, 3in dia. (would make ideal wind speed indicator) £2.75p. Prices include P & P. Mail order only. SAE for list. Eldun Electronics, 16, Raven Road, Timperley, Cheshire.

THE SCIENTIFIC WIRE CO

Copper - Nickel Chrome - Eureka - Manganin Wires.
Enamelled - Silk - Cotton - Tinned Coverings.
No minimum charges or quantities.
Trade and Export enquiries welcome.

S.A.E. Brings List.

P.O. BOX 30, LONDON, E4 9BW

BUILD THE

TREASURE TRACER

MK III Metal Locator



- Varicap tuning
- Britain's best selling metal locator kit
- Weighs only 22oz. Fitted with Faraday shield.
- Speaker and earphone operation
- Knocks down to only 1 1/2in.
- Prebuilt search coil assembly
- Thoroughly professional finish
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snips
- Five transistor circuit

Send stamped, addressed envelope for leaflet

Complete Kit **£10.90** Built & tested **£15.25**
Post 60p (10p VAT 8%) Post 60p £1.27 VAT 8%

MINIKITS ELECTRONICS,
63 CLEVELAND ROAD,
LONDON, E18 2AN (Mail order only)

PRINTED CIRCUIT BOARDS, all prices inclusive of P&P etc. No extras. We offer: "P.W." Easybuild Organ (2 PCB's) £5.70. Tele-tennis (6 PCB's) £3.68—Add-on Sound Effects £1.20—Add-on Ball Speed £1.00—All eight PCB's £5.60. Electronic Clock (3 PCB's) £1.95. Tricolour £1.25. Ferret Locator 75p. Derby £1.00. Tone Control plus Scratch and Rumble (2 PCB's) £1.50. Telephone Exchange £1.50. "P.E." Joanna £1.30 each—all issues. Power Slaves (3 PCB's) £1.52. CCTV (2 PCB's) £2.15p. Ferret Locator 75p. I.C. Pulse Generator £1.30. Scorpio Mk2 £1.00. Many others available. S.A.E. for list. All orders C.W.O. Production space always available for PCB production, silk-screen printing, tinning, electroplating, plus all Art/graphic and Photographic services. We also sell direct Art/graphic aids and supplies. Cat: 45p. Production Estimates; By return or Phone: W.K.F. Electronics, Welbeck St., Whitwell, Work-sop, Notts, S80 4TW. Tel: Whitwell (Derbys) 695, STD 090974. Callers seen by appointment only at Station Rd.

Practical Wireless, November 1975

PCB SUPPLIES: Ferric Chloride available by the cwt., or ton, £350 per ton. Solid Carbide PCB drill bits for Epoxy/glass. Most sizes from 1mm up. £2.50 each. High speed steel quick spiral PCB drill bits for SRBP £3.75 per dozen. W.K.F. Electronics. Address above.

12 VOLT 21" 13 Watt Fluorescent Lighting
(by Thorn/AEI) with diffuser & on/off switch. Ideal caravan, boat, emergency lighting, etc. Guaranteed.



£5.50 inc. VAT & Post. List price £7.02 Inc. VAT
SALOP ELECTRONICS 23 Wyle Cop,
Shrewsbury, Shropshire Tel. 53206

GLASS FIBRE P.C.B.'s. Send master and 30p per board plus 7p per square inch tinned or plus 9p per square inch drilled and tinned. Proto Design, 4 Highcliffe Way, Wickford, Essex. Previously Electro Circuits, Wickford.

Synthesiser "Sounds Supreme"

by Dewtron (25% VAT extra.)

Famous kits, e.g. vaa-waa complete kit £4.50; Fuzz kit £6.50 P&P 25p under £10. Ring Modulator modules £11. "Mister Bassman" Bass Pedal Units and whole range of synthesiser modules, musical novelties, etc. Catalogue 20p from D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

E. WENMOUTH, Radio & Television, 50 South Street, Exeter. Tel: 76058. Due to popular demand we have pleasure in announcing that our stocks of radio, amateur and DIY spares are now being increased to meet your requirements.

TEXAN AMPLIFIER 20 + 20 Watt Complete Kit £32.00 (Tax extra)

Pack 1. Res. 80p. Pack 2/3. Capacitors £3.65. Pack 5. Switches £1.50. Pack 6. Pots. Pack 7. Semi Cond. £8.25. Pack 9 P.C.B. £3.00. Pack 10. Chassis £3.00 Case £3.50.

Toroidal Transf. £6.00 P.P. + Tax extra £2.
(Toroidal Transf. for 28W £6.10 + tax & post £2)

TELERADIO ELECTRONICS
325 Fore St., Edmonton, London N9

JAYBEE FOR KITS

AMTRON, JOSTYKIT, ETC.

Send S.A.E. for full information


JAYBEE ELECTRONICS, Sarum Farm Est.
SARUM ROAD, WINCHESTER, HANTS
Telephone 0962-41806

HARDWARE. Comprehensive range of screws, nuts, washers, etc. in small quantities, and many useful Constructors' items. Sheet aluminium to individual requirements, punched, drilled, etc. Fascia panels, dials, nameplates in etched aluminium. Printed circuit boards for this magazine and other individual requirements, one-offs and small runs. Machine engraving in metals and plastics, contour milling. Send 2 x 42p stamps for catalogue. Ramar Constructor Services, Masons Road, Stratford on Avon, Warwicks., CV37 9NF.

Practical Wireless, November 1975

FANTASTIC NEW MICROTEST 80

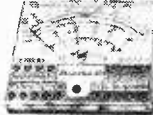MEASURES
ONLY
90 x 70 x 18 mm
ELECTRONIC ZERO Ω



Amazing Value at **£11.95**
8 fields of measurement
and 40 ranges

PRINTED CIRCUIT BOARD IS
REMOVABLE WITHOUT SOLDERING

Volts D.C. 6 ranges: 100mV - 2V - 10V - 50V - 200V - 1000V. (20k Ω/V) 2% precision on DC and AC
Volts A.C. 5 ranges: 1.5V - 10V - 50V - 250V - 1000V. (4k Ω/V)
Amp. D.C. 6 ranges: 50μA - 500μA - 5mA - 50mA - 500mA - 5A
Amp. A.C. 5 ranges: 250μA - 2.5mA - 25mA - 250mA - 2.5A
Ohms 4 ranges: Low Ω - Ω x 1 - Ω x 10 - Ω x 100 from 1/10 of Ω until 5 Mega Ω
V Output 5 ranges: 1.5V - 10V - 50V - 250V - 1000V
Decibels 5 ranges: + 6dB, +22dB, +36dB, +50dB, +62dB
Capacity 4 ranges: 25μF - 250μF - 2500μF - 25,000μF



SUPERTESTER 680R ICE
20,000 Ohm per Volt/sensitivity • Fully screened against external magnetic fields • Scale width and small case dimensions (128 x 95 x 32mm) • Accuracy and stability (1% in D.C., 2% in A.C.) of indicated reading • Simplicity and ease of use and readability • Full ranges of accessories • 1000 times overload • Printed circuit board is removable without de-soldering • More ranges than any other meter. Ask for free catalogue **£18.50**

Accessories (extra) available to convert Microtest 80 & Supertester 680R into following: LIGHT-METER, GAS-METER, ELECTRONIC VOLT-METER, AMPERCLAMP, TRANSISTOR TESTER, TEMPERATURE PROBE, PHASE SEQUENCE INDICATOR, Ω x 1000 Multiplier, SIGNAL INJECTOR—Send for details.

MORE RANGES FOR LESS MONEY!

AC/DC Multimeter type U4324

A-DC 0-0.3A - 6 Ranges.
A-AC 0-3A - 5 Ranges.
V-DC 0-6-1200V - 9 Ranges.
V-AC 3-300V - 8 Ranges.
Freq.: In the range of 45 to 20kHz.
Resistance: 500 Ohm to 5 MOhm - 5 Ranges. Decibel: -10 to +12dB.
Accuracy: ± 2.5% DC, ± 4% AC
Dimensions: 187 x 98 x 63 mm.



Only **£9.25**

ALPHANUMERIC NIXIE TUBES B7971

The Alphabetic NIXIE tube has the ability to display all the letters of the alphabet, numerals 0 thru 9 and special characters in a single tube. From the standpoint of both readability and electrical characteristics, the Alphabetic NIXIE tube provides many unique benefits including: ★ 170V-21mA ★ All d.c. operation ★ Uniform, continuous line characters of equal height ★ Memory with simple solid state drive circuits ★ Readability in high ambient light ★ 200 footlamberts brightness ★ Long life with no loss of brightness ★ Character height 2 1/2 in.

Price only **99p** each plus 16p P/P.
Bases for above 60p each.

JUST ARRIVED!!

NUMERIC INDICATOR TUBES

Ultra-long life, high quality, 0-9 and 2 Independent decimal points. Supply voltage 200V D.C. Current 14mA, Pulse duration 100μs. Character height 0.51, overall size 1.4 in.
Brand new, guaranteed. Surplus to manufacturers requirements. Type B5853cat
1-25 £1 25+ 80p 100+ 80p

1000+ price on application
8% VAT to all items + 35p P & P

ELECTRONIC BROKERS LTD.
49-53 Pancras Road, London NW1 2QB
Tel: 01-837 7781

GRUNDIG SATELLIT 2000
13 BAND COMMUNICATIONS RECEIVER
List Price **£209** SAVE **£50**
Our Special Price **£159.90** inc. VAT P/P
Large Stocks of Grundig equipment at Discount Prices.
Send S.A.E. for Catalogue
GORSE PHOTOGRAPHIC LTD.
42-44, Church St., Blackburn, Lancs.
Tel: Blackburn 51682
77, THE MALL, BURNLEY, Lancs.
Tel: Burnley 35229

Books and Publications

UFO CHARTS: Wave Prediction 56p; Daily Flight Pattern 50p; TV Detection 66p; Propulsion Theory 57p; "Anti-Gravity" 57p; Map 52p; Circuits: Transistor Optical Detector 68p; Radiation/Optical 46p; Crystal Radiation Counter 85p; Sighting Recorder 55p; 22-Range Multimeter Digital 95p. R & E, Highlands, Needham Market, Suffolk.

Technical Books - Radio & Electronics

World's Radio & TV Stations (International Edit)... £0.68
Audio Amplifiers £0.70
Boys Book of Crystal Sets £0.33
Television Timebase Circuits £1.15
Radio TV and Industrial Tube & Valve Equip. £0.68
How to get the best out of your Tape Recorder ... £1.67
Practical Electronic Science Projects £0.85
Jack Darr's Service Clinic £1.55
Transistor Circuits for Modern Test Equipment... £0.68
Modern Tape Recording Handbook £0.80
1st Book of Transistor Equip. and Substitutes ... £0.48
Hi Fi, PA & Disco Amplifier Design Hndbk. £0.87
Radio Servicing Problems £0.75
Electronic Circuits for the Amat Photographer ... £0.68
Handbook of Simple Transistor Circuits £0.40
TV Fault Finding £1.10
Sound and Loudspeaker Manual £0.60
Practical Stereo & Quadrophony Handbook £0.85
Radio Amateur Operator's Handbook £0.85
Coil Design & Construction Manual £0.58
Radio TV & Electronics Data Book £0.68
79 Electronic Novelties Circuits £0.80
The Complete Car Radio Manual £0.80
Radio Technicians Bench Manual £3.30
Servicing Transistor Radio Receivers £0.90
1st Book of Hi Fi Loudspeaker Enclosures £0.68
2nd Book of Hi Fi Loudspeaker Enclosures £0.68
Manual of Electronic Circuits for the Home. £0.60
Modern Crystal Set Circuits for Beginners. £0.40
Electronic Novelties for the Motorist. £0.58
2nd Book of Transistor Equip. & Substitutes. £1.07
Handbook of Electronic Musical Novelties. £0.58
Transistorised Novelties for Hi Fi Enthusiasts. ... £0.40
Fault Location Exercises in Rad. & TV Vol.1. £0.95
Fault Location Exercises in Rad. & TV Vol.2. £1.55
Colour TV Picture Faults. £2.70
Practical Transistor Novelty Circuits £0.48
Boys Book of Practical Radio & Electronics ... £0.68
Radio Receiver Construction using ICs & Trans. ... £0.68
ICs & Transistor Gadgets Construction Hndbk'k ... £0.68
Integrated Circuits Equip. & Substitutes Hbk. ... £0.85
Audio Technicians Bench Manual £3.30
Improving your Hi-Fi £3.30
Guide to Printed Circuits £2.80
Diode Characteristics Equip. & Substitutes £1.05
WORLD RADIO TV HANDBOOK 1975 £3.80

All prices include Postage & Packing
RADIO BOOK SERVICE
40 Elwill Way, Beckenham BR3 2RZ

T.V. REPAIRS MADE EASY
Send your make/model/chassis no. & £3.50; by return you receive the repair manual containing simple to follow instructions including your set (no circuit diagrams included). British sets covered in 4 mono manuals & 3 colour manuals (some foreign). Write/phone now for trade terms.
Instructions to make a signal injector for £1.20. Ask about the giant Circuit Diagram Manuals.
TV TECHNIC (PW1),
76 CHURCH STREET, LARKHALL,
LANARKS, ML9 1HE. (0698 883334),

WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS, ENGLAND
MAIL ORDER CALLERS SATURDAYS ONLY

TRANSISTORS (less 10% for 25+ of one type)			
AC125 13p	BC154 13p	BF181 33p	OC140 100p
AC126 13p	BC157 13p	BF184 22p	OC201 70p
AC127 12p	BC158 12p	BF185 22p	OC202 80p
AC128 12p	BC159 13p	BF194 10p	TIC44 30p
AC141 20p	BC167 12p	BF195 10p	TIP29 45p
AC142 15p	BC168 12p	BF196 12p	TIP29A 45p
AC176 12p	BC169 12p	BF197 12p	TIP29C 70p
AC187 12p	BC170 11p	BF198 12p	TIP30 48p
AC188 12p	BC172 11p	BF199 12p	TIP30A 64p
AD161 34p	BC177 18p	BF252 15p	TIP30B 64p
AD162 34p	BC178 18p	BF253 17p	TIP30C 76p
AD163 34p	BC179 18p	BF254 15p	TIP31 54p
AD164 34p	BC180 18p	BF255 15p	TIP32 60p
AD165 34p	BC181 18p	BF256 15p	TIP32A 60p
AD166 34p	BC182 18p	BF257 15p	TIP32B 60p
AD167 34p	BC183 18p	BF258 15p	TIP32C 60p
AD168 34p	BC184 18p	BF259 15p	TIP33 95p
AD169 34p	BC185 18p	BF260 15p	TIP33B 112p
AD170 34p	BC186 18p	BF261 15p	TIP33C 130p
AD171 34p	BC187 18p	BF262 15p	TIP34 130p
AD172 34p	BC188 18p	BF263 15p	TIP35 259p
AD173 34p	BC189 18p	BF264 15p	TIP36A 330p
AD174 34p	BC190 18p	BF265 15p	TIP41A 68p
AD175 34p	BC191 18p	BF266 15p	TIP42 74p
AD176 34p	BC192 18p	BF267 15p	TIS43 28p
AD177 34p	BC193 18p	BF268 15p	TIS44 17p
AD178 34p	BC194 18p	BF269 15p	ZTX107 10p
AD179 34p	BC195 18p	BF270 15p	ZTX108 8p
AD180 34p	BC196 18p	BF271 15p	ZTX109 12p
AD181 34p	BC197 18p	BF272 15p	ZTX110 12p
AD182 34p	BC198 18p	BF273 15p	ZTX111 14p
AD183 34p	BC199 18p	BF274 15p	ZTX112 14p
AD184 34p	BC200 18p	BF275 15p	ZTX113 14p
AD369 34p	BC385 18p	BF460 15p	ZTX298 14p
AD370 3			

PLEASE ADD APPROPRIATE V.A.T.



PERSONAL CALLERS ARE WELCOME!

all items subject to manufacturers increase and availability



High Quality Construction Kits, stocked at all branches. Send for catalogue!

AMPLIFIERS P&P 95p Ins. £1	
Sansul AU2200	£50.96
AU4400	£78.00
Sinclair 4000	£50.00
Pioneer SA5300	£45.60

RECORD DECKS P&P 85p Ins. 50p	
Garrard SP25 Mk. IV	£16.20
Garrard SP25 Mk. IV/G800	£27.50
Plinth & Cover	
BSR MP60	£12.75
Connoisseur BD1 Kit	£13.25
BD2 Chassis/SAU2	£34.15
SAU2 Pick-up Arm	£14.25
SCU1 Cartridge	£5.95
Pioneer PL12D	£46.59
Sansul SR212P	£44.80

SPEAKERS P&P 45p	
EMI 13" x 8", 3, 8 ohm plain	£2.50
with co-axial tweeter	
8 ohm only	£2.75
with Tweeter & Crossover	
15 ohm only	£4.25
Type 350 8 ohm, 20 watt	£8.25
13" x 8" Bass unit, 15 watt	£5.45
6 1/2" 8 ohm, 10 watt	£2.95
6 1/2" 8 ohm, 10 watt	£4.50
8" x 5" C. Mag. 5 watt 3, 8 or 15 ohm	£1.70
8" x 5" Dualcone 8 ohm, 10 watt	£2.95
Elac 6 1/2" 8 ohm Dualcone	£2.45
8" x 8 ohm Dualcone	£2.70
Baker Group 25 12", 8 or 15 ohm	£12.00
Adastra 10" 10 watt, 8 or 15 ohm	£3.75
Goodmans 8" x 5" 8 ohm	£1.70
Global 8 ohm 5 watt (pair)	£7.95

WHARFEDALE SPEAKER BARGAINS	
P&P 85p Ins. £1	
Chevin (pair)	£25.50
Denton 2 (pair)	£32.00
Linton 3 (pair)	£47.60
Linton 2 (kits)	£20.95
Glendale 3 (kits)	£35.95

KIT FORM CABINETS	
Teak Veneer P&P 85p Ins. 50p	
12" x 8" x 4 1/2" (8 x 5 or 7 x 4 cutout)	£3.75
12" x 12" x 7 1/2" (10", 8 x 5, 8", 6 1/2" and 3 1/2")	£5.25
18" x 11" x 7 1/2" (8" x 3 1/2" or 13 x 8)	£6.56
22" x 14" x 7 1/2" (12" x 3 1/2" or 13 x 8)	£7.96

TWEETERS & CROSSOVERS	
P&P 25p	
Cone Tweeter 8 or 15 ohm, 10 watt	£2.95
Cone Tweeter 8 ohm, 3 watt	£1.55
Horn Tweeter 8 ohm, 20 watt	£6.50
Dome Tweeter 8 ohm, 30 watt	£5.75
Crossovers CN23 (3 ohm) CN28 (8 ohm), CN126 (16 ohm)	£1.40

CARTRIDGES & STYLII	
P&P 25p	
Acos GP91/2SC or 3SC (ster. com.)	£1.10
GP93/1 or 95/1 ster. crystal	£1.35
GP94/1 or 96/1 ster. ceram.	£1.75
GP101 cryst. comp.	£0.90
GP104 ster. ceram.	£1.95
BSR X5M or H5X cryst. comp.	£1.95
SX6M or SX6H cryst. ster.	£2.10

SC5M ster. ceram.	£2.85	£1.25
Sonotone 9TAHC or 9TAHC G (Diam)	£1.95	£1.25
3509 ster. ceram.	£1.95	£1.25
Audio Tecnica AT55	£1.95	—
Empire 999 REX	£3.95	—
Golding G850	£3.10	£1.95
G800	£4.25	£1.95
G800H	£4.25	£1.95
G800E	£7.25	£3.95
Shure Carls & Styli M44G	£4.95	£3.95
M55E	£6.25	£4.95
M75ED Type 2	£11.75	£8.25
M75EJ Type 2	£9.75	£6.25
V15 Type 3	£32.25	—

MICROPHONES P&P 25p	
CM70 Planet stick metal, switch crystal	£1.70
DM160 Dynamic omni-dir. ball metal	£4.95
UD130 50K 600 ohm, uni-dir, ball metal	£6.75
TW209	£5.90
CONDENSER MIKE 600 ohm, uni-dir.	£9.50
Cassette STICK MIKE with R Control on/off switch (2-5 & 3.5 mm) J/Ply)	£1.65
Cassette STICK MIKE with R/Control (Philips Type)	£2.80

BATTERY ELIMINATORS	
P&P 25p	
240v input 6, 7.5 or 9 volt output	£3.10
12v d.c. input (specify output 6, 7.5 or 9 d.c.) at 300mA	£2.95

CASSETTES P&P25p				
Type	Low noise	Philips	Memorex	Ampex
C45			65p	45p
C60	35p	55p	75p	55p
C90	45p	75p	£1.10	75p
C120	55p	£1.10	£1.55	99p

CASSETTE CASES	
Cassette Head Cleaner	£0.12
BIB Stereo Test Cassette	£2.15
AMPEX Head Cleaner Demag	£1.65

TAPES P&P 25p			
Std	LP	DP	Cases
55p	65p	£1.00	20p
65p	86p	£1.35	25p
80p	£1.10	£1.85	30p

SINCLAIR PROJECT 80	P&P 25p
Stereo Pre-amp	£12.95
Active Filter Unit	£7.95
Z40 15 watt Amp	£5.75
Z60 25 watt Amp.	£7.25
Power Supply for 240	£5.45
Power Supply for 240	£8.45
Power Supply for 260	£8.25
FM Tuner	£12.95
Stereo Decoder	£8.45
Q16 Speaker	£7.75
IC20 stereo amp. kit	£7.45
PZ20 Power kit	£5.25

Send 25p for catalogue.
PLEASE BRING THIS ADVERTISEMENT TO OBTAIN THE BENEFIT OF THESE SPECIAL PRICES

ALL MERCHANDISE FULLY GUARANTEED

NEWMART ELECTRONICS

Mail Order Dept PW11
Belmont St, Monton,
Eccles, Manchester.
Tel: 061-789 5268

Manchester
30-32 Shudehill. tel 061-832 7710
Leeds
4 New Market St tel 0532 42708
Liverpool
15 Whitechapel tel 051-236 0738

INDEX TO ADVERTISERS

Adcola Products cover iii	Electroni-Kit 560	Partridge Electronics Ltd. 617
A. H. Supplies 590	Electronic Brokers 621	Pembridge College of Electronics 619
Ambit International 605	Electronics Design Associates 594 & 620	Peter Styles Electronics 560
A.S.P. Ltd. 616	Electronic Mail Order Ltd. 608	Precision Petite 598
Astro Electronics Ltd. 536	Electrovalue Ltd. 614	Purnell Books 610, 611
Bamber, B. 605	Everest Instruments Ltd. 609	Radio Book Services 621
Barrie Electronics 546	Flairline Supplies 614	Radio Component Specialists 589
Bell's Television Service 619	Garfields 620	Radio Exchange Ltd. 559
Bentley Acoustic Ltd. 614	Gorse's Photographic Ltd. 621	Reltran Ltd. 618
Beta Devices 618	Greenbank Electronics 536	R.S.C. (Hi-Fi) Centres Ltd. 530-531
B. H. Component Factors Ltd. 560	Greenweld Electronics 605 & 620	R.S.T. Valve Mail Order Co. 541
Bi-Pak Ltd. 538-539, 564	H.A.C. Short-wave Supplies 609	Radio & T.V. Components Ltd. 548, 549
Bi-Pre-Pak Ltd. 533	Harversons 587	Salop Electronics 621
Birkett, J. 572	Heath (Gloucester) Ltd. 542	Sales Team, The 537
Boffin Projects 620	Henry's Radio Ltd. 601	Saxon Entertainments Ltd. 612, 613
British Institute of Engineering Technology 572, 590, 608	Home Radio 563	Scientific Wire Company, The 620
British National Radio & Electronics School 534, 540, 593	I.L.P. Electronics Ltd. 535	S.I.G.A. Electronics Ltd. 546
J. Bull (Electrical) Ltd. 597	Imperial Trading 618	Simtech Engineering Ltd. 620
Bush & Meissner 617	Intertext—I.C.S. 532	Sinclair Radionics Ltd. 582, 583
Bywood Electronics 609	J. F. H. Supplies 620	Sintel 532
C. Caranna 619	Jaybee Electronics 621	Studio Electronics 613
Central Imports & Exports 614	Kensington Supplies 619	Surplronics 568
Chromasonic Electronics cover iv	Lasky's Ltd. 543, 544, 545	Swanley Electronics 609
C. J. L. 534	Lewis Radio 532	T.V. Technical Publications 621
Codar Radio Co. 602	Linear Products 540	Technomatic Ltd. 624
Colomar (Electronics) Ltd. 564	London Computer Operators Training Centre 619	Teleradio Electronics 620 & 621
Combined Precision Components 542	Manor Supplies 616	Trampus Electronics Ltd. 602
Crescent Radio Ltd. 571	Macks Electronics 547	T. T. Service 594
Crofton Electronics 598	Maplin Electronic Supplies 567	Tuac Ltd. 606, 607
C. T. Electronics cover ii	Marco Trading 618	Venusound 534
Date Publications 604	Microelectronics 620	Watford Electronics 622
D. E. W. Ltd. 621	Marshall, A. & Son 572	Web Europa 616
Dzudas, M. 608	Michael Williams Electronics 598	West London Direct Supplies 598
	Minikits Electronics 620	Wilmslow Audio 568
	Newmart Electronics 623	Xeroza Radio 617
		Z. & I. Aero Services 624
		Zentac 546

ADCOLA Special offer


A FABULOUS SOLDERING GUN
PLUS THE RENOWN INVADER
SOLDERING IRON

DESOLDERING MADE SIMPLE

- ONE HAND OPERATION
- NO ELECTRICS
- NO CABLES
- TROUBLE FREE



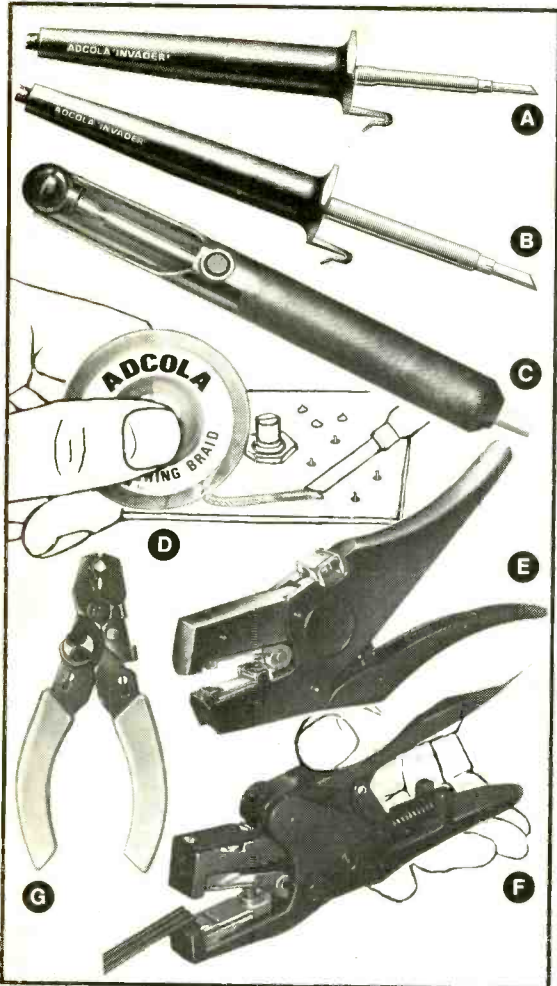De-Soldering is no longer a problem when you use the de-soldering gun and Adcola Invader soldering iron.
NORMAL PRICE £9.43 SPECIAL OFFER PRICE £6.97
 If you order the L646 Soldering Iron and de-soldering gun, this offer saves you 25% off the manufacturer's recommended list price for these top quality tools.



- A L646. One of the most famous soldering irons in the world, 23 watt, $\frac{3}{16}$ " diameter bit. Efficient, reliable and above all, trouble free. The general purpose soldering tool at only £3.55.
- B L706. As the above described tool but 17 watt, $\frac{1}{8}$ " diameter bit. The best iron for small electronic work priced at £3.43.
- C FM22. Easy to use de-soldering gun. Simply press the plunger and place the nozzle over the molten solder as illustrated above. Solder is drawn up into the gun by pressing the release button. Pellets of hardened solder are ejected by depressing the plunger for further use, price £5.88.
- D DE-SOLDERING BRAID. Used in conjunction with a soldering iron and operates by capillary action. Supplied in 5½ft reels at £0.89 per reel.
- E FM28. Lightweight self-adjusting Wire Stripper. Fitted with the famous flexi-jaw consisting of a large number of independent leaf blades enabling the cutting edge when under pressure to surround each conductor. The blades therefore self adjust to wire diameter and cannot damage conductors. Also fitted with a wire cutter. Capacity 0.2mm – 2.75mm. Weight 127gms. The tool for the discerning user at £13.66.
- F FM27. A slightly heavier version of the FM28 stripper but without wire cutter. Capacity 0.2mm – 3.75mm. Weight 243gms. Price £13.66.
- G FM29. Wire Stripper/Cutter. An inexpensive quality tool for cutting and stripping wires. The tool has moulded handles, high grade steel blades and a capacity up to 6mm². Priced at £1.78.

All prices include 8% V.A.T.
 Please add 25p to all orders for postage and packing.

**BUY NOW AT THESE PRICES
 FOR TWO MONTHS ONLY!**

SEND CHEQUE OR POSTAL ORDER NOW TO: ADCOLA PRODUCTS LIMITED, GAUDEN ROAD, LONDON S.W.4. 6LH

130 Lovel

CHROMASONIC electronics

Dept 1 56 Fortis Green Road,
Muswell Hill, London, N10 3HN.
telephone: 01-883 3705

C-MOS

	1-24	25-99	100up
CD4000AE	23p	19p	15p
CD4001AE	23p	19p	15p
CD4002AE	23p	19p	15p
CD4003AE	£1.59	£1.33	£1.06
CD4007AE	23p	19p	15p
CD4008AE	£1.75	£1.46	£1.17
CD4009AE	Use	CD4049	
CD4010AE	Use	CD4050	
CD4011AE	23p	19p	15p
CD4012AE	23p	19p	15p
CD4013AE	69p	58p	46p
CD4014AE	£1.75	£1.46	£1.17
CD4015AE	£1.75	£1.46	£1.17
CD4016AE	69p	58p	46p
CD4017AE	£1.75	£1.46	£1.17
CD4018AE	£2.51	£2.09	£1.67
CD4019AE	80p	66p	53p
CD4020AE	£1.97	£1.64	£1.31
CD4021AE	£1.75	£1.46	£1.17
CD4022AE	£1.83	£1.53	£1.22
CD4023AE	23p	19p	15p
CD4024AE	£1.26	£1.05	84p
CD4025AE	23p	19p	15p
CD4026AE	£2.79	£2.33	£1.86
CD4027AE	99p	82p	65p
CD4028AE	£1.53	£1.28	£1.02
CD4029AE	£1.12	£1.76	£1.41
CD4030AE	71p	57p	47p
CD4035AE	£1.75	£1.46	£1.17
CD4040AE	£2.01	£1.68	£1.34
CD4042AE	£1.49	£1.24	99p
CD4049AE	69p	58p	46p
CD4050AE	69p	58p	46p
CD4051AE	£2.78	£2.32	£1.85
CD4052AE	£2.78	£2.32	£1.85
CD4056AE	£2.12	£1.76	£1.41
CD4060AE	£2.51	£2.09	£1.67
CD4066AE	£1.13	94p	75p
CD4068AE	28p	24p	19p
CD4069AE	28p	24p	19p
CD4070AE	28p	24p	19p
CD4071AE	28p	24p	19p
CD4072AE	71p	59p	47p
CD4081AE	28p	24p	19p
CD4082AE	28p	24p	19p
CD4085AE	£1.28	£1.06	85p
CD4086AE	£1.28	£1.06	85p
CD4093AE	£1.56	£1.20	£1.04
CD4099AE	£2.56	£2.46	£1.96

74 TTL

	1-24	25-99	100+
7400	14p	12p	10p
7401	14p	12p	10p
7402	14p	12p	10p
7403	15p	12p	10p
7404	16p	13p	11p
7408	16p	13p	11p
7409	16p	13p	11p
7410	16p	13p	11p
7411	27p	24p	20p
7417	27p	23p	20p
7420	16p	13p	11p
7427	27p	23p	18p
7430	16p	13p	11p
7432	27p	23p	18p
7437	27p	23p	18p
7441	75p	62p	50p
7442	65p	55p	45p
7445	85p	71p	57p
7447	95p	83p	67p
7448	85p	71p	57p
7449	95p	83p	67p
7448	85p	71p	57p
7470	30p	25p	20p
7472	25p	21p	17p
7473	30p	25p	20p
7474	30p	25p	20p
7475	47p	39p	31p
7476	30p	26p	21p
7482	75p	62p	50p
7485	£1.30	£1.09	87p
7486	32p	26p	21p
7489	£3.58	£2.80	£2.10
7490	47p	40p	32p
7491	65p	55p	45p
7492	57p	46p	36p
7493	49p	40p	32p
7495	67p	55p	45p
74100	£1.08	89p	72p
74107	35p	28p	22p
74121	34p	28p	23p
74122	47p	39p	31p
74141	78p	63p	53p
74145	68p	58p	48p
74154	£1.75	£1.48	86p
74174	£1.00	83p	67p
74180	£1.06	88p	71p
74181	£3.20	£2.50	£1.90
74192	£1.35	£1.14	90p
74193	£1.35	£1.14	90p
74196	£1.64	£1.34	99p

LINEAR I.C.'s

555 (8 pin dip) V 55p	7824UC (TO-220)	LM3900	69p	SN76001N (TA7611)	£1.12
555 (TO-99) T 81p	ICL8038	LM3909	66p	SN76003N	£3.30
556 (14 pin dip) £1.29	AY-1-0212	MC1303L	£1.84	SN76003N	£1.98
703 (RF/IF Amp) £1.59	AY-1-5051	MC1306P	80p	SN76023N	£1.98
709 (8 pin dip) 39p	AY-5-1224	MC1310P	£2.39	SN76227N (MC1327)	£1.89
709 (TO-99) 45p	AY-5-3500	MC1312	£2.42	SN76532N	£1.89
709 (14 pin dip) 39p	AY-5-3507	MC1315	£4.62	SN76544N	£1.81
	AY-5-4007	MC1327	£1.12	SN76550-2 (TA7651)	89p
	BHA0002	MC1330P	83p	SN76552-2	81p
	CA2111	MC1339P	£1.52	SN76660N (TA76120)	75p
	CA3045	MC1350	64p	SN76666N (CA3065)	£1.12
	CA3046	MC1351	88p	TAA263	£1.12
	CA3053	MC1352	88p	TAA300	£2.10
	CA3065	MC1357	£1.52	TAA310A	£1.87
	CA3075	MC1358 (CA3065)	£1.26	TAA320	£1.44
	CA3078	MC1375	£1.48	TAA350	£7.50
	CA3080	MC1456	£1.68	TAA370	£3.40
	CA3081	MC1455 (555T)	62p	TAA570	£2.74
	CA3082	MC1456CG	£1.68	TAA700	£5.03
	CA3089E (TDA1200)	MC1458CPI	84p	TBA1205	£1.25
	CA3130	MC1468G	£2.18	TBA231	£1.02
	CA3097E	MC1495L	£4.24	TBA281 (723)	£2.59
	CA3123E	MC1496G	96p	TBA500	£3.16
	CA3401E (LM3900)	MC3302P	£1.50	TBA520	£3.85
		MC3401P	74p	TBA530Q	£3.27
		MFC4000B	87p	TBA540Q	£3.72
	CA3600E	MFC4060A	79p	TGA550Q	£5.29
	CT7001	MFC6400	79p	TBA560EQ	£5.29
	LO05T (TO-3)	MFC6400	79p	TBA625A	£1.03
		MFC6070	£1.66	TBA625C	£1.03
	LM301T (TO-99)	MM5314	£4.80	TBA651	£1.87
		MM5316	£9.99	TBA720Q	£2.79
		MMV15V (TO-3)	£1.45	TBA750Q	£2.79
				TBA800	£1.11
				TBA810S	£1.24
				TBA810AS	£1.24
				TBA820	86p
				TBA920Q	£4.71
				TBA930Q	£4.71
				TCA270Q	£5.24
				TCA760	£2.16
				TCA800Q	£7.24
				TCA830S	£1.04
				TCA940	£2.25
				TDA1054	£1.50
				TDA1201	£2.43
				TDA1405	80p
				TDA1412	80p
				TDA1415	80p
				TDA2010	£3.00
				TDA2020	£3.75
				ULN2111A	£1.52
				ZN414	£1.26

SIEMENS LCD's

LINE-O-LIGHT

Full Range:
Denco Coils & I.F.T.'s, Jackson
Tuning Gangs, Transistors; Diodes;
Bridge's; Veroboard; Aluminium
Boxes; Mains Transformers;
Capacitors; Resistors; Mullard
LP1185, 1186 & LP1400.

NEW LED Linear Cursors
each device contains 10 light
emitting diodes in a 20pin dual-
in-line package. Ideal for solid
state analogue meters or dials.
Type 101 RED £2.26 ●



PHOTO-DARLINGTON

SPECIAL PURCHASE

SEVEN SEGMENT DISPLAYS

2N5777
V_{ceo}, V_{ceo} 25v, V_{ebo} 8v
V_{ceo}, V_{ceo} 25v, V_{ebo} 8v
h_{fe} 2500; I_c 250 mA **35p.**

enables
L17707 0.3" 90p; L17747 £1.99 ●

litronix
Xalitan
Monsanto

I.C. SOCKETS
Dual-in-line TOS
Pins 8 14 16 24 28 30 36 40 6 10
● Price 13p 15p 15p 26p 30p 39p 44p 31p 35p

NEW
Litronix Double Digit Displays
0.5", Common Anode - 2 R/H
D.S.,
DL721 gives 1-9
DL727 gives 0.0 to 9.9
Suitable for Clocks; Instruments;
T.V. Channel Indicator
Our Price £4.75 each ●

	COMMON ANODE R/H Dec. Pt.	COMMON ANODE L/H Dec. Pt.	COMMON ANODE T Dec. Pt.	COMMON CATHODE R/H Dec. Pt.	Our Price
RED	DL707P	DL707	DL701	DL704	£1.82 ●
GREEN	MAN51	MAN52	MAN53	MAN54	£1.82 ●
RED	MAN71	MAN72	MAN73	MAN74	£1.82 ●
YELLOW	MAN81	MAN82	MAN83	MAN84	£1.82 ●
ORANGE	MAN3610	MAN3620	MAN3630	MAN3640	£1.82 ●
GREEN	XAN51	XAN52	-	XAN54	£1.49 ●
RED	XAN71	XAN72	-	XAN84	£1.49 ●
YELLOW	XAN81	XAN82	-	-	-
GREEN	MAN4510	MAN4520	MAN4530	MAN4540	£2.32 ●
RED	MAN4710	MAN4720	MAN4730	MAN4740	£2.32 ●
YELLOW	MAN4810	MAN4820	MAN4830	MAN4840	£2.32 ●
ORANGE	MAN4610	MAN4620	MAN4630	MAN4640	£2.32 ●

L.E.D.'s
Free snap-on plastic retainer

0.125" dia. lens (TIL209)	0.16" dia. lens	0.2" dia. lens (MLED 550)
1+ 10+ 100+	1+ 10+ 100+	1+ 10+ 100+
Red 16p 15p 13p ●	27p 24p 22p ●	18p 16p 14p ●
Green 27p 24p 22p ●	33p 30p 27p ●	30p 27p 25p ●
Orange 27p 24p 22p ●	33p 30p 27p ●	30p 27p 25p ●
Yellow 34p 31p 29p ●	35p 32p 29p ●	35p 33p 30p ●

NOTICE
Postage & Packing Charges

With the recent increase in postal charges and a continuing increase in packaging cost we have been forced to review our policy. Henceforward:

- Orders valued at £5 or more will be post free.
- All U.K. 'small package' orders will go first class mail.
- Minimum postage & packing charge will increase to 20p.

	C/A L/H Dec. Pt.	C/A Dec. Pt.	C/C L/H Dec. Pt.	C/C Dec. Pt.
RED	DL747	DL746	DL750	DL749

Low Cost Red GoAsP Motorola MLED 500 in a T092 package. 15p ●

NEW Opto-isolators (LI 4N25 or TIL116) 6 pin industry standard package, 2 SKV isolation. £1.00 ●

NOTE: MAN4000 series pinouts are a 14 pin d.i. the same as MAN50,70 & 8C series.

VAT INCLUDED Items marked with a ● include 8% VAT Items unmarked include VAT at 25%
ADVERT. No.1 of Series B.
CALLERS WELCOME