

RADIO



BOOKS

Tape and Wire Recording. A selection of articles reprinted from the pages of *The Radio Constructor*, covering both the theory and practical applications. A really useful book on this latest development of the hobby. 2/6 post 3d.

Receivers, Preselectors and Converters. Practical articles, again reprinted from past issues of *The Radio Constructor*, which will prove of interest to many radio enthusiasts. 2/6 post 3d.

TV Fault Finding. Profusely illustrated with photographs taken from a television screen depicting the faults under discussion, and containing a wealth of technical information, with circuits, enabling those faults to be eradicated. 5/- post 4d.

F.M. Tuner Units for Fringe and Local Area Reception. Including optional Tuning Indicator and circuit of Osram 912 Amplifier. 2/- post 2d.

Radio Amateur Operator's Handbook. An indispensable aid to the amateur transmitter and listener, containing all details of information which are constantly required. Prefix Lists, Zone Boundaries, Call Areas, Codes, and Mileage Tables, together with Maps and much other useful operating data. 1956 edition 3/- post 3d.

Inexpensive Car Radio. In which two versions, one constructed from surplus and one from new components, are described. 1/6 post 2d.

Radio Control for Model Ships, Boats and Aircraft, by F. C. JUDD, G2BCX. A comprehensive work on this fascinating subject.
Standard edition, 8/6 post 5d.
Cloth bound edition, 11/6 post 7d.

All available from your local bookseller, or from

DATA PUBLICATIONS LTD

57 MAIDA VALE LONDON W9

Telegrams Databux London

Telephone CUNningham 6141 (2 lines)

Printed in Great Britain for the Proprietors and Publishers Data Publications Ltd., 57 Maida Vale, London, W.9, by A. Quick & Co. Ltd., Oxford House, Clacton-on-Sea, England. Is obtainable abroad through the following: Collets Subscription Service, Continental Publishers & Distributors, Ltd., William Dawson & Sons Ltd. Australia and New Zealand: Gordon & Gotch Ltd. South Africa: Central News Agency. U.S.A.: Gilfer Associates. Holland: "Radio Electronica." Registered for transmission by Magazine Post to Canada (including Newfoundland).



www.americanradiohistory.com

The **RADIO Constructor**



FOR THE RADIO AND TELEVISION ENTHUSIAST


VOLUME 9

NUMBER 10

MAY 1956

SIMPLE ALL- WAVE RECEIVER

by JAMES S. KENT

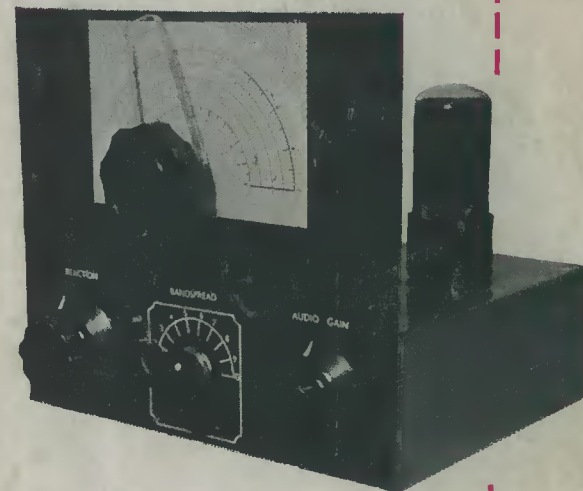

Also in this issue
PRACTICAL BAND III TUNERS
TRANSISTOR TEST BOARD
HANDY KITCHEN RADIO
THERMISTOR OPERATED THERMOMETER
TRANSISTORETTE RECEIVER, Part 4
and all the usual features

**DATA
Publications 1/6**

THE MODERN BOOK CO

The Radio Amateur's Handbook.
By A.R.R.L. 30s. 0d. Postage 1s. 3d.

The 3rd Audio Anthology. Published
by Radio Magazines Inc. 20s. 0d.
Postage 1s.

Radio Handbook. By W. I. Orr.
60s. 0d. Postage 1s.

**Sweep and Marker Generators for
Television and Radio.** By R. G.
Middleton. 20s. 0d. Postage 1s.

Basic Audio Course. By D. C. Hoefler.
22s. 0d. Postage 1s.

**The Practical Electrician's Pocket
Book 1956.** 5s. 0d. Postage 6d.

Making and Using a Telescope. By
H. P. Wilkins and P. Moore. 12s. 6d.
Postage 6d.

T.V. Fault Finding Data Book No. 5.
5s. 0d. Postage 4d.

The Services Textbook of Radio.
Vol. 3. "Electronics." 12s. 6d.
Postage 9d.

A Beginner's Guide to Radio. By
F. J. Camm. 7s. 6d. Postage 6d.

**Audio Handbook No. 5. The Quest
for Quality.** By N. H. Crowhurst.
6s. 0d. Postage 4d.

**Audio Handbook No. 4. Public
Address.** By N. H. Crowhurst.
4s. 6d. Postage 4d.

The Oscilloscope at Work. By
A. Haas and R. W. Hallows. 15s. 0d.
Postage 6d.

Radio Valve Data. Compiled by the
Wireless World. 3s. 6d. Postage 6d.

We have the Finest Selection of British and American Radio Books in the country

Complete list on application


19-23 PRAED STREET (Dept RC) LONDON W2

Telephone PADdington 4185

TELETRON Mk2 BAND III CONVERTER COIL KIT

The Teletron MK2 Converter

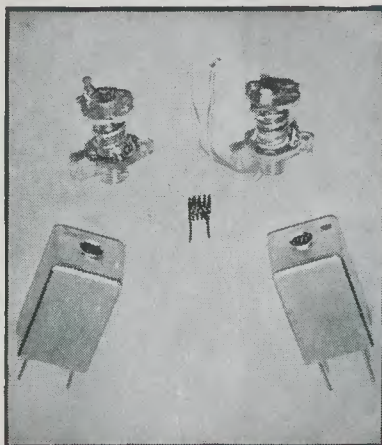uses a high gain cas-
codeconnected twin-
triode in a fully neu-
tralised circuit, which
is provided with a
high frequency com-
pensating inductor
and is coupled via a
special network to a
triode/pentode
mixer whose output
can be adjusted to
any channel in Band I



Simple
Construction.
Complete
Wiring
Diagram. High
Sensitivity,
Low Noise

Thousands of Mk. 2
converters are now
providing the I.T.A.
Channel 9 pro-
grammes at ranges
of up to 60 miles
from the Croydon
transmitter

COMPLETE PRECISION COIL KIT (CHANNELS 7-14) 17/6

Available from all leading stockists

Circuit and wiring diagram 3d.

THE TELETRON COMPANY LIMITED

266 NIGHTINGALE ROAD · LONDON N9 · Telephone HOW 2527


Trade enquiries to sole distributor **S. Mozer, 95 Kendal Ave N18** Telephone EDMonton 7707



Designed for



dependability

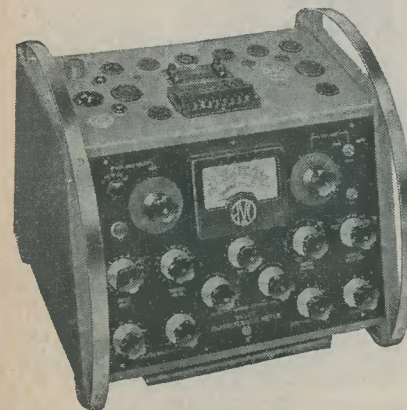

The "AVO" Valve Characteristic Meter, Mk. III is typical of the ingenuity of design and high standard of workmanship that exemplify all of the multi-range instruments in the wide "Avo" range.

It is a compact and comprehensive meter that will test quickly any standard receiving valve or small transmitting valve on any of its normal characteristics under conditions corresponding to a wide range of D.C. electrode voltages. The method of measuring mutual conductance ensures that the meter can deal adequately with modern T.V. receiver valves. It does many useful jobs too numerous to mention here, but a completely descriptive pamphlet is available on application.

List Price **£75** complete with Instruction Book and Valve Data Manual.

The AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO., LTD.

VICTORIA 3404
(9 lines)

AVOCET HOUSE · 92-96 VAUXHALL BRIDGE ROAD · LONDON · S.W.1.

The
AMATEUR'S
PARADISE

LANES (RADIO) LTD

11 GARDNER STREET
Telephone BRIGHTON 20773

LANES POWER PACK

220/230/250 Input A.C. 250V @
60 m/A Output D.C. Filament
6.3V @ 3 amps.

SUITABLE FOR DRIVING AUX-
ILIARY FM AND TUNING UNITS
ETC.

£3. 10. 0 POST FREE

★ ALL LEADING COMPONENTS ★
IN STOCK



LANE 4-WATT AMPLIFIERS

Illustrated in March issue


Independent treble, middle and bass controls. Valves 6BR7, 6BW6, 6X4. Output 4 watts matched to 2-3 ohms. Mains input tapped 200-250V a.c. **£6.12.6**

Why be swamped by BBC?

In areas with high signal strength the new B.B.C. high-powered Band I transmitter is likely to render the contrast control of your receiver almost inoperative. The OSMOR Variable Attenuator will reduce the signal to the required level. Easily fitted—just plug in. Reduction ratios variable 2-1 to 10-1. An ESSENTIAL with all types of Band III Converters.

Osmor New Dial Assembly

Calibrated
specially for
Osmor coils
and
Coilpacks

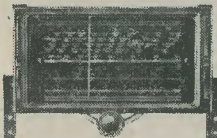

Type 5
Price
24/6
Scale
length 7"

This is a really attractive horizontal 3-colour slide rule, precision built assembly. Complete with 6-band Perspex scale 9" x 4 1/2", for chassis mounting. L, M and S. wavebands with station names; S.W.1, S.W.2 and trawler bands. The vernier drive has a ratio of 18-1 search, and 50-1 reverse. Positions for two dial bulbs.

ESCUTCHEON for above, bronze finish metal 4/-

ITA band III Converters

A simple but very efficient Band III Converter for all TV sets (including TRF). Approximately one hour to build! Guaranteed no breakthrough of Band I or re-radiation. Will convert any Band III Channel to any Band I Channel. AC or AC/DC. Excellent results assured. Kit £3. 5. 0 Ready wired £4. Postage and packing 3/-.

OSMOR RADIO PRODUCTS LTD
418 BRIGHTON ROAD SOUTH CROYDON
SURREY Telephone CROydon 5148-9

The Mullard 3-VALVE 3-WATT AMPLIFIER COMPONENTS

T.C.C. CAPACITORS		each
1	120pF 1015MP...	1/5
1	1,000pF 7015MP	1/8
1	0.02µF CP33N	1/9
2	0.1µF CP36H...	2/4
1	0.25µF CP48N	2/8
1	30µF CE88DE	3/-
1	50-50µF CE172LE	16/-

RESISTORS		each
8	1/2 watt	6d.
1	330 ohms	10d.
1	2.2 Mohms HS	1/9
1	680 ohms	2/-
3	Lab Type A Potentiometers	5/-

COMPONENTS		
1	Gilson WO767 Output Transformer	25/6
1	Gilson WO 839 Mains Transformer	35/-
2	Bulgin mains plug and socket	4/3
1	Bulgin red signal lamp	2/-
1	Bulgin d.p.s.t. mains switch	6/3
3	Bulgin T24 tag strips	1/-
1	Belling 1A fuse and holder	3/9
1	Belling coaxial socket	1/3
2	McMurdo B9A at 1/- each, 1 skirted	1/3
1	chassis 10" x 7" undrilled	7/-

VALVES		
1	Mullard EF86 (including p. tax)	24/4
1	Mullard EL84 (including p. tax)	18/1
1	Mullard EZ80 (including p. tax)	14/2

TERMS: C.W.O. or C.O.D. (minimum £1)


Orders over £1 post free

These are the specified Mullard TP283 components. Please send for our list MA3 which includes suitable alternative components at lower prices

J.T. FILMER MAYPOLE ESTATE
BEXLEY · KENT
Telephone BEXLEYHEATH 7267

THE ACOS MIC 36

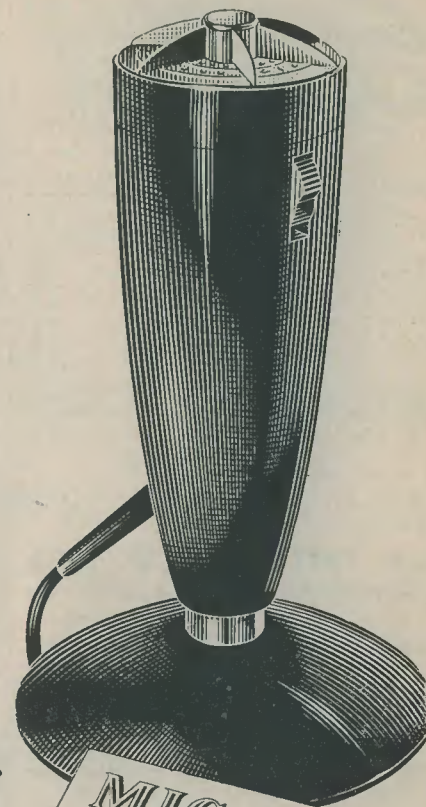The ACOS MIC 36 crystal microphone performs as well as it looks. It is omnidirectional, highly sensitive, and has a substantially flat response from 30 to 7,000 c/s. It retails at £3.3.0 without switch or £3.8.0 with one, and is widely chosen for tape and disc recording, P.A. and amateur radio.



STAND

TABLE



HAND

MIC 36
is just one popular example of
ACOS Microphones. The range
includes other models retailing
at prices from £1.5 to £12.12.

acos always well ahead

ACOS devices are protected by patents, patent applications
and registered designs in Great Britain and abroad.

COSMOCORD LTD · ENFIELD · MIDDLESEX · Tel: ENfield 4022

Smith's of EDGWARE ROAD

Component Specialists since broadcasting started

Can supply a full range of 4-sided Blank Chassis of 16 gauge half-hard aluminium of their own manufacture

Size (inches)	Price	Size (inches)	Price
6 x 4 x 2 ...	4/6	10 x 8 x 3 ...	8/6
7 x 5 x 2 ...	5/-	13 x 8 x 2 1/2 ...	8/9
8 1/2 x 5 1/2 x 2 ...	5/6	12 x 9 x 2 1/2 ...	8/11
10 x 4 x 2 1/2 ...	6/-	14 x 7 x 3 ...	9/-
9 x 7 x 2 ...	6/6	13 x 10 x 2 1/2 ...	9/9
12 x 4 x 2 ...	6/6	14 x 10 x 2 1/2 ...	10/-
9 x 8 x 2 1/2 ...	7/3	12 x 10 x 3 ...	10/3
10 x 8 x 2 1/2 ...	7/6	15 x 10 x 2 1/2 ...	10/6
12 x 5 x 3 ...	7/9	17 x 10 x 2 1/2 ...	11/3
12 x 7 x 2 1/2 ...	7/11	17 x 9 x 3 ...	11/9
11 x 8 x 2 1/2 ...	8/-	17 x 10 x 3 ...	12/6

Other sizes pro rata plus 2/6
Keep this list for reference

Panels cut to any size 4/- per sq. ft. and pro rata. Special discount for quantities of the above. Prices include post and packing (U.K. only).

H. L. SMITH & CO. LTD

287/289 EDGWARE ROAD LONDON W2
Telephone Paddington 5891

ARTHURS HAVE IT!

Large Stocks of Valves and C.R.T.s
Full Range of Meters available
Avo, Taylor, Cossor, Advance, etc.
Particulars on Request

FM Kit of Parts £5, less valves
(Ref. Radio Constructor July, 1954)

Amplifier Tape Recorders and
Loudspeakers

Jason FM Tuner Unit £15 17 0

Jason Power Pack £3 10 0

Radios and Television always in stock

VALVE MANUALS

Mullard, 10/6; Brimar No. 6, Osram, Part I,

5/-; Osram, Part II, 10/-

Postage 9d. each extra

Publications: "Lodestar" Tape Recorder, 3/6

Goods offered subject to price alteration and
being unsold

Arthurs first Est. 1919

Proprietors: ARTHUR GRAY LTD

OUR ONLY ADDRESS Gray House
150-52 Charing Cross Road
London WC2

TEmpLe Bar 5833/34 and 4765

AERIAL FITTINGS

FOR

Band III, Band I & Radio F/M

Our increased range of Diecast Alloy Fittings include Band III to Band I Mast Couplers, Reflector and Director Rod Holders, Insulators (both "Inline" and "H" types), Masthead Fittings, Masts and Elements, Chimney Brackets, etc., together with useful Formulae and Hints for constructing your own aerial quickly and cheaply.

Send 1/- P.O. to cover the cost of catalogue and postage to:

FRINGEVISION LTD
MARLBOROUGH WILTS

Telephone 657/8

THE ARGONAUT AM-FM RECEIVER

AUDIO LTD

All the components for
AM/FM Receiver available
from stock.

Mains transformer, Choke
and Output transformer,
as specified. Tested and
approved by Jason Motor &
Electronic Co.

37/6

Send for list of Radio
and Television components,
Post free.

AUDIO LTD

Tower Road London NW10
Telephone WILlesden 3905



**POST TODAY FOR OUR BROCHURE ON
THE LATEST METHODS OF HOME
TRAINING FOR OVER 150 CAREERS
& HOBBIES**

PRIVATE & INDIVIDUAL TUITION IN YOUR OWN HOME

City and Guilds Grouped Certificates in Telecommunications: A.M.Brit. I.R.E. Examinations, Radio Amateur's Licence, Radio and Television Servicing Certificates, General Radio and Television Courses, Radar, Sound Recording, etc. Also Courses in all other branches of Engineering and Commerce.

The advantages of E.M.I. training

★ The teaching methods are planned to meet modern industrial requirements. ★ A tutor is personally allotted by name to ensure private and individual tuition. ★ Free advice covering all aspects of training is given to students before and after enrolling with us.

NEW LEARN THE PRACTICAL WAY COURSES WITH EQUIPMENT

With many of our courses we supply actual equipment which is sent upon enrolment and remains your property. Courses include: Radio, Television, Electronics, Draughtsmanship, Carpentry, Photography, and Commercial Art, etc.

Courses
from 15/-
per month

POST THIS COUPON TODAY

Please send without obligation your FREE book,
E.M.I. INSTITUTES, Dept. 179K,
Grove Park Road, London, W.4. May


NAME

ADDRESS

SUBJECT(S) IC.38

EMI INSTITUTES

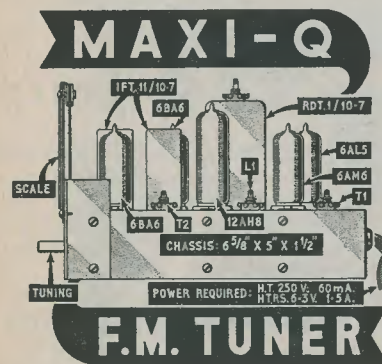The only Postal College which is
part of a world-wide Industrial Organisation.



The guaranteed components described below have been acclaimed by thousands as the finest obtainable.

Full constructional details, point-to-point wiring diagram and alignment instructions are given in our Technical Bulletin DTB.8, price 1/6.

F.M. SCALE. A bronze finished scale with yellow markings (0-20 Log) for use with all types of f.m. tuners or receivers. Consisting of metal scale, pointer, cord drive spindle, pulleys, 2 1/8" drum, cord and instructions for the assembly of the cord drive. The scale measures 5 1/2" x 3" and is for a cabinet aperture of 4" x 1 1/2", price 9/-.
RDT.1/10.7 Mc/s. A transformer for use in ratio discriminator type circuits. Can size 1 1/8" square x 2 1/2" high. Secondary winding of bifilar construction, iron dust core tuning, polystyrene formers and silver mica condensers, price 12/6.

PDT.1/10.7 Mc/s. A miniature phase discriminator transformer for use in frequency modulation detector circuits where the limiter/Foster-Seeley type of circuit is employed. Designed for carrier deviation of ±.75 Kc/s. Qk=1.5. Screening can 1 1/8" x 1 1/8" square, price 9/-.
IFT.11/10.7 Mc/s. A miniature i.f. transformer of nominal frequency 10.7 Mc/s. The transformer is primarily intended for the i.f. stages of frequency modulation receivers and converters. The Q of each winding is 90 and the coupling critical. Dimensions as PDT.1., price 6/-.


IFT.11/10.7/L. As IFT.11/10.7 but with secondary tap for limiter input circuits, price 6/-.
COILS Type L1, T1 and T2. These coils are specially designed for use in the "MAXI-Q" F.M. TUNER, price 3/11 each. Chassis and screens for the above unit, completely punched in aluminium, 7/6.
Obtainable from all reputable stockists or, in case of difficulty, direct from works. GENERAL CATALOGUE covering technical information on full range of components 1/- post free.

DENCO (Clacton) LTD 357/9 OLD ROAD CLACTON-ON-SEA ESSEX

STOP PRESS: MAXI-Q F.M. TUNER UNIT assembled and valved at £9 . 19 . 6 inc.
POWER PACK at £3
OSRAM F.M. TUNER completely assembled and valved at £30 . 16 . 0 inc.

HOME RADIO of MITCHAM

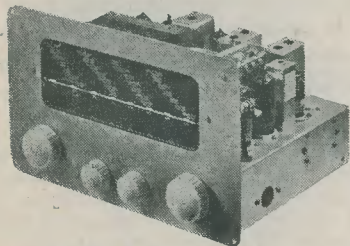JASON "ARGONAUT" ← HAVE ALL PARTS IN STOCK FOR THE → **MULLARD 3-Watt AMPLIFIER**



Dial, chassis, gang condenser ready assembled £3. 18. 0
 Complete set coils and I.F. transformers £2. 17. 9
 Special switch 9/6
 Silver mica and ceramics 9d. each; 8mfd 150V 2/6; 25mfd 25V 2/-
 Output transformer as specified 5/6

Ready punched chassis from 7/6. Specified output transformers from 21/-. Gilson and Elstone mains transformer. All resistors and condensers in stock. Valves: EL84 10/6, EZ80 10/6.

The ideal speaker for both these units is a WB high fidelity. We carry the full range including bass reflex cabinets, etc.

★ PLEASE SEND S.A.E. FOR COMPLETE DETAILED PRICE LISTS OF THESE KITS ★


HOME RADIO

187 LONDON ROAD MITCHAM SURREY Telephone MITcham 3282

REPANCO

MATCHED PAIR DUAL RANGE COILS

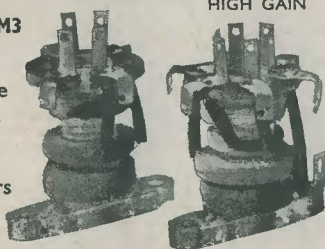Type DRM3 Super Selective coils for T.R.F. receivers




HIGH GAIN

A NEW RANGE OF HIGH GAIN R COILS

Iron Dust Cored

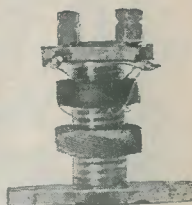This range of Coils has been carefully designed for maximum efficiency with small physical dimensions



Actual Size

Range	Aerial	H.F.	Osc.
800-2,000 metres ...	RA1	RHF1	RO1
190-550 metres ...	RA2	RHF2	RO2
70-230 metres ...	RA3	RHF3	RO3
15-50 metres ...	RA4	RHF4	RO4

I.F.T.s 455-475 Kc/s. 0.0005mfd Tuning Condenser. Complete with Circuits Each 3/3
 Send S.A.E. for Catalogue of complete range of Coils

IDEAL FOR RADIO FEEDER UNIT FOR THE MULLARD 3 WATT AMPLIFIER

Reaction winding on H.F. Coil. Range L.W. 900-2,000 metres; M.W. 190-550 metres. With two Mains, one battery, and high quality Feeder Unit Circuits 8/- Pair

RADIO EXPERIMENTAL PRODUCTS LTD

33 MUCH PARK STREET COVENTRY

Telephone 62572

NEW!

EXPERIMENTAL KITS in Radio, T.V etc.

LEARN THE PRACTICAL WAY

Specially prepared sets of radio parts from which we teach you, in your own home, the working of fundamental electronic circuits and bring you easily to the point when you can construct and service radio sets. Whether you are a student for an examination; starting a new hobby; intent upon a career in industry; or running your own business — these Practical Courses are intended for YOU — and may be yours at very moderate cost.

EASY TERMS FROM 15/- A MONTH


With these outfits, which you receive upon enrolment, you are instructed how to build basic Electronic Circuits (Amplifiers, Oscillators, Power Units, etc.) leading to complete Radio and Television Receiver Testing and Servicing.



BEGINNER'S RADIO OUTFIT

— For carrying out basic practical work in Radio and Electronics, from first principles and leading to the design and building of simple Receivers.

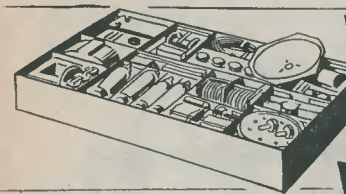
ALL EQUIPMENT SUPPLIED IMMEDIATELY AND REMAINS YOUR PROPERTY



ADVANCED RADIO OUTFIT

— With this equipment, you are instructed in the design, construction, testing and servicing of a complete modern T.R.F. Superhet Radio Receiver.

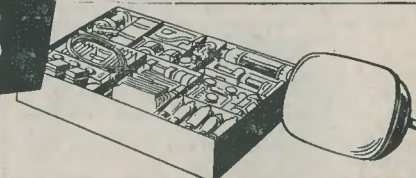TELEVISION — With this equipment you are instructed in the design, construction, servicing and testing of a modern high quality Television Receiver.



OTHER COURSES WITH EQUIPMENT INCLUDE:

MECHANICS · ELECTRICITY
 CHEMISTRY · PHOTOGRAPHY
 CARPENTRY

ALSO

DRAUGHTSMANSHIP · COMMERCIAL ART
 AMATEUR S.W. RADIO · LANGUAGES · ETC.

POST THIS COUPON TODAY

Please send me your FREE book on Practical Courses.

Subject(s) of interest
 To: E.M.I. INSTITUTES, Dept. 179x, Grove Park Road, London, W.4.

NAME


ADDRESS

E.M.I. INSTITUTES

The only Postal College which is part of a world-wide Industrial Organisation

WORLD-WIDE DX IS CERTAIN
with the
Labgear 150 Watt TRANSMITTER

MODEL LG300 MK II

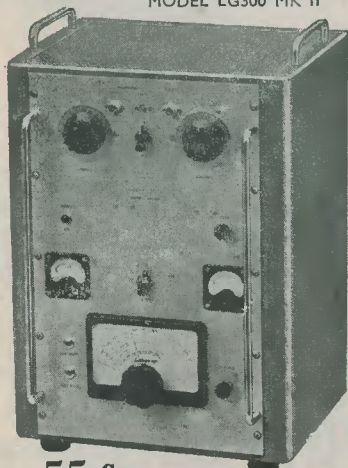

PRICE 55 Gns. (With all valves except 813)

Hire Purchase terms if required
Companion Power Unit/Modulator now available
Send S.A.E. leaflet RC5035

Labgear (Cambridge) Ltd
WILLOW PLACE . CAMBRIDGE . Telephone 2494

G2ACC offers you

DISC CERAMIC CAPACITORS

The very modern capacitor for decoupling purposes. Midget size, non-inductive, excellent dielectric insulation. Ideal for TV, short wave and VHF. 500 volt d.c. (300V a.c.) working; 470pF, 0.001µF, size 1/8" dia., 9d. each; 0.002µF, 0.003µF, size 1/4" dia., 9d. each; 0.005µF, size 3/8" dia., 9d. each.

HI-K TUBULAR CERAMIC CAPACITORS

Similar dielectric and insulation to above, of tubular construction and midget size, 500 volts d.c. working: 0.0005µF, 0.001µF, 0.0015µF, 0.002µF, 0.003µF, 10½d. each; 0.005µF, 0.01µF, 1/- each.

STANDARD TUBULAR CERAMIC CAPACITORS


Of lower K than the above and suitable for coupling in addition to decoupling, 500V d.c. working: 1, 1.5, 2, 3pF, 1/- each; 5, 7.5, 10, 15, 20, 25, 30, 40, 47, 50, 60, 75, 100pF, 10½d. each; 150, 200, 250, 300, 350, 400, 500pF, 1/2 each.

NEGATIVE TEMPERATURE COEFFICIENT CAPACITORS

For tuned circuits where compensation is required. 3, 4.7, 6.8, 10, 15, 30, 50, 75, 100pF, 1/- each.

Minimum postage 6d. on orders under £2

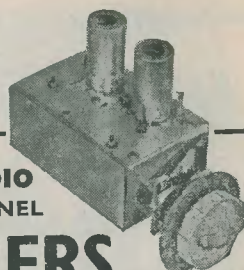SOUTHERN RADIO AND ELECTRICAL SUPPLIES
SORAD WORKS REDLYNCH SALISBURY
Telephone Downton 207



**VALRADIO
13 CHANNEL
TUNERS**


NOW AVAILABLE TO THE
HOME TV CONSTRUCTOR

Adapt your set to receive the Commercial TV programmes. Valradio tuners are suitable for home constructed receivers including "The Wireless World," "Magnaview," etc. I.F. outputs, 9-14 mcs; 16-20 mcs; 19-24 mcs; and 34-40 mcs. Complete with fitting instructions ... **£6**
Bracket for fixing tuner to cabinet ... 2/6



Valradio Limited, Feltham, Middlesex
Telephone Feltham 4242 & 4837

JACKSON

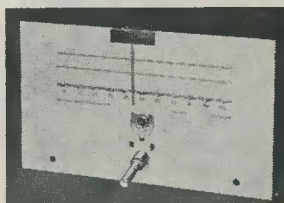

S.L.16 DRIVE

RETAIL PRICE 11/6

A general purpose slide rule drive for F.M./V.H.F. units, short-wave converters, etc. Printed in three colours on aluminium, with a 0-100 scale, and provision is made for individual calibrations. Travel of pointer 4 3/8". Scale plate 7" x 4 1/2". Scale aperture 5 1/2" x 1 1/2".

S.L.15 DRIVE


RETAIL PRICE 25/6

A complete kit of parts for the construction of the Jackson S.L.15 drive, calibrated for the F.M./V.H.F. band.

IT'S RELIABLE IF IT'S MADE BY JACKSONS

Write for our illustrated Price List

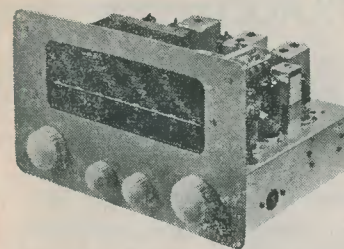JACKSON BROS. (London) LTD
KINGSWAY WADDON SURREY
Telephone CROYDON 2754-5



**BUILD THE
Jason "ARGONAUT"
A.F.-F.M. TUNER-RECEIVER**

Following the success of our F.M. Tuner Kit, we now introduce this super-sensitive M.W.-F.M. Tuner-Receiver. The switching and wiring are simple, but performance has not been sacrificed. There is space on the chassis for power pack and output stage. The building instructions are appearing in the March and April issues of this magazine, and will be available as a reprint.

Dial assembly, with chassis, flywheel tuning, Jackson Bros. 4-gang condenser, 500pF + 500pF, and 15pF + 15pF, glass scale calibrated in station names on both bands, and hammer finish front panel, price **£3. 18. 0**

All coils, including ratio detector, M.W. coils and 2 twin-i.ft.'s (472 kc/s and 10.7 Mc/s), price **£2. 17. 9**
Approximate total cost to build, as a receiver and with power supply, **£16. 0. 0**

Send S.A.E. for complete component price list

THE JASON MOTOR & ELECTRONIC CO
328 CRICKLEWOOD LANE LONDON NW2
Telephone SPeedwell 7050

RADIO CONTROL

FOR MODEL SHIPS, BOATS AND AIRCRAFT

by F. C. JUDD, G2BCX

To operate a model ship or aircraft is a most interesting hobby. But how much more fascinating it would be if one could emulate the skipper or pilot and remain in control after the model has been set off on its course. This, thanks to radio control, can now be done, and enthusiasm for it is steadily mounting. Radio Control for Model Ships, Boats and Aircraft has become a recognised handbook in this field.

144 pages 135 diagrams and illustrations

Standard Edition, art board cover, 8s. 6d. postage 5d.

Cloth bound, with gold lettering, 11s. 6d. postage 7d.

DATA PUBLICATIONS LTD
57 MAIDA VALE LONDON W9

HANNEY of BATH
OFFERS

ALL COMPONENTS FOR

Mullard


3 VALVE 3 WATT AMPLIFIER
510 HIGH QUALITY AMPLIFIER
TYPES 'A' & 'B' PRE-AMPS
FM TUNER UNIT

Osram

912 + H.Q. AMPLIFIER
PASSIVE UNIT
PRE-AMPLIFIER
FM TUNER UNIT

Send stamp for lists

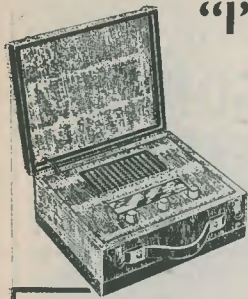L. F. HANNEY
77 LOWER BRISTOL ROAD BATH
Telephone 3811



"I'M SET TO GO PLACES with you"

The SUPEREX "55" BATTERY PORTABLE is a first-class receiver guaranteed to give good reception throughout the country. Equal in appearance and performance to any commercial model. Cabinet size 10 $\frac{1}{4}$ " x 8 $\frac{3}{4}$ " x 5".

- Four Valve Superhet
 - Long and Medium Wave
 - Large Elliptical Speaker
 - B7G 1.4V Miniature Valves
 - Simple Construction
- All parts available separately. Send 1/6 for Superex Construction Booklet.



ONLY £7.15.0
Plus 3/6 p.p.

QUALITY RECORD REPRODUCTION AT MODERATE COST

The S.R. 3-4 Watt Amplifier

High quality 3 valve 3 watt amplifier for a.c. mains 200/250 volts. Four engraved controls give a wide range of tone variation. Output transformer matched for any 3 ohm speaker. Chassis fully isolated. Valve line-up: 6SG7, 6V6, 6X5. Bronze crackle finished chassis. Overall size 8" long, 4" wide, 5" high. Supplied built and tested; guaranteed for 12 months (90 days valves).

PRICE £5.5.0 Plus 3/6 p.p.

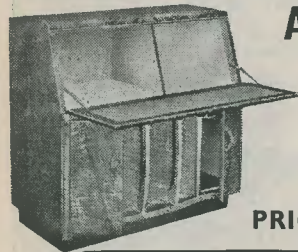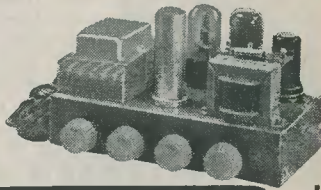

AN ELEGANT CABINET to suit your pocket!


Very elegant in highly figured walnut veneer with internal panels in sycamore. Sloping radio panel size 16" long x 10 $\frac{1}{2}$ " high. Uncut motor board size 15 $\frac{3}{4}$ " long x 13 $\frac{1}{4}$ " back to front. Lid panelled in beige leatherette. Two large storage cupboards. Speaker chamber large enough for 12" speaker. Overall cabinet size 35" high, 34" long, 16 $\frac{1}{2}$ " deep. Send for full details of this and other types in stock.

PRICE £17.0.0 Plus 25/- p.p.

FROM ALL CORNERS — Here's greatest value!

A craftsman-built corner type speaker cabinet designed for any good quality 12" speaker. Solidly constructed of 1" thick veneered board, expertly finished in high figured walnut veneer or in natural finish light oak veneer. Size 31" high, 28" wide, 19" back to front. Definitely a cabinet of distinctive design.

PRICE £12.10.0 Plus 17/6 Carr.

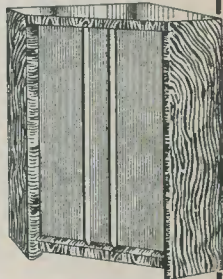

RADIO COMPONENTS

We carry a very wide range of radio and television components, also AM/FM radio chassis, tuners and h.f. amplifiers. Quality speakers always in stock. SEND FOR LISTS

TERMS

Cash with Order or C.O.D. (extra charge for C.O.D.) U.K. and N. IRELAND ONLY.

Superior

Radio supplies

37 HILLSIDE, (HARROW ROAD)
STONEBRIDGE, NW.10. Elgar 3644.

PRICE 15/6
Plus 2/6 p.p.

THIS MONTH'S SNIP

Attractive bakelite cabinet with long and medium wave two-colour glass dial and two cream knobs. Ideal for T.R.F. construction. Available in Walnut and Green. Size 12" long, 7" high, 5 $\frac{1}{4}$ " deep. Complete with handle and back.

The Radio Constructor

incorporating THE RADIO AMATEUR



CONTENTS FOR MAY

VOL. 9, NO. 10

MAY 1956

ANNUAL SUBSCRIPTION 20/-

Editorial and Advertising Offices

57 MAIDA VALE LONDON W9

Telephone CUNNINGHAM 6141 (2 lines)

Telegrams DATABUX, LONDON

Editor C. W. C. OVERLAND, G2ATV

Advertising Manager F. A. BALDWIN, A M I P R E

- 612 Suggested Circuits: A Voltage Regulated Power Pack, by G. A. French
- 615 In Your Workshop, by J. R. D.
- 621 Band III Television for the Home Constructor, Part 11, by S. Welburn
- 627 The "Transistorette," Part 4, by G. A. French
- 632 V.H.F. Feeder Losses, by H. E. Smith, G6UH
- 634 Handy Kitchen Radio, by E. Govier
- 636 Simple All-Wave Receiver, Part 1, by James S. Kent
- 642 Using Mains Transformers having Unconventional Voltage Tappings, by G. W. Short, M.A.
- 644 Transistor Test Board, by V. T. Rolfe
- 647 Right—From the Start; Part 5, L.F. Amplification, by A. P. Blackburn
- 651 Can Anyone Help?
- 652 Radio Miscellany, by Centre Tap
- 655 Transmitting with the EL34, by W. Oliver, G3XT
- 656 A Thermistor-Operated Thermometer, by J. W. Bagnall
- 658 The 1956 London Audio Fair
- 660 A Constructor Visits the R.E.C.M.F. Exhibition
- 662 The Moving Coil Meter, by David A. Morris

THE CONTENTS of this magazine are strictly copyright and may not be reproduced without obtaining prior permission from the Editor.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors


NOTICES

THE EDITOR invites original contributions on construction of radio subjects. All material used will be paid for. Articles should preferably be typewritten, and photographs should be clear and sharp. Diagrams need not be large or perfectly drawn, as our draughtsmen will redraw in most cases, but all relevant information should be included.

All MSS must be accompanied by a stamped addressed envelope for reply or return. Each item must bear the sender's name and address.

TRADE NEWS. Manufacturers, publishers, etc., are invited to submit samples or information of new products for review in this section.

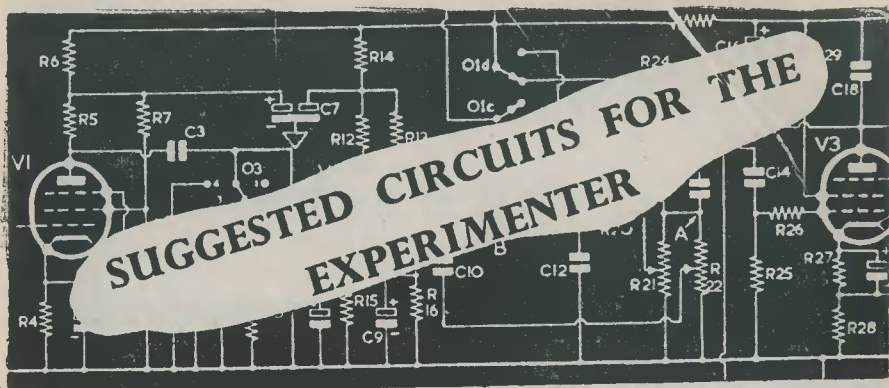ALL CORRESPONDENCE should be addressed to THE RADIO CONSTRUCTOR 57 Maida Vale London W9



The circuits presented in this series have been designed by G. A. FRENCH, specially for the enthusiast who needs only the circuit and essential relevant data

No. 66. A VOLTAGE REGULATED POWER PACK

DURING EXPERIMENTAL WORK THE NEED often arises for a power pack capable of supplying a well-regulated source of h.t. voltage. This power pack should be such that its output has a constant potential despite differing h.t. current consumptions or variations in the mains supply voltage. The power pack should, in addition, be capable of maintaining its steady voltage during very quick changes in load current.

Conventional rectifier h.t. power units employ either condenser or choke input filtering. Condenser input filtering is more economic than choke input filtering because it enables a higher h.t. voltage to be obtained from the same mains transformer. However, the regulation of a condenser input power pack is poor. Choke input filtering provides better regulation but necessitates the use of an expensive mains transformer if a reasonably high h.t. voltage is to be obtained. Even with choke input filtering, h.t. regulation for slow changes in current consumption can be no better than that permitted by the resistive elements of the circuit. In other words, the equivalent circuit of a power pack employing choke input filtering may consist of a source of steady potential in series with a resistance; this resistance representing the sum of the resistances of the transformer and choke windings, plus

transformer losses and the internal resistance in the rectifier. Neither a condenser input or choke input power pack will, of course, be able to prevent alterations in h.t. output voltage caused by variations in the mains supply.

The Circuit

This month's circuit illustrates a power pack which works on an entirely different principle. It employs a conventional condenser input filter arrangement which is followed by a valve whose effective resistance can be altered by varying its grid-cathode potential. This potential is varied by a second valve whose function is that of comparing the h.t. voltage output of the power unit with that appearing across a voltage regulator valve.

The h.t. output of the power unit shown in the circuit should be capable of adjustment from some 150 to 250 volts, its maximum output current being approximately 150mA. The 6.3 volt i.t. supply also provided by the power pack is not regulated. The resistor values shown in the diagram have been calculated from the curves of the particular valves employed, and should give rise to no trouble in practice. However, this point is discussed in more detail later. A type number for the rectifier, V₁, is not given,


since this may consist of any full-wave valve capable of passing the maximum h.t. current required.

Operation

The operation of the circuit is fairly simple. It works on the principle that the regulation of the h.t. voltage applied to the anode of V₂ is poor, and that, to ensure a constant voltage at the output terminals, the effective resistance of this valve is varied to compensate for the poorly regulated voltage.

It would be advisable to commence a more detailed explanation of the operation of the power unit by assuming that it is supplying an h.t. voltage at a particular current via

The cathode of V₃ is held at a constant potential by V₄ and is relatively undisturbed by the fall in h.t. voltage. On the other hand, the grid voltage of V₃ is proportional to the output voltage of the power pack and, in consequence, goes negative. The anode current of V₃ therefore falls. The drop in anode current of V₃ results in a lower voltage appearing across R₄. The voltage across R₄ is that which biases V₂ with the result that, when it decreases, so also does the effective series resistance provided by V₂. The ultimate effect is that the h.t. voltage appearing at the output terminals of the power pack then rises, reaching, or very closely approaching, its previous value.

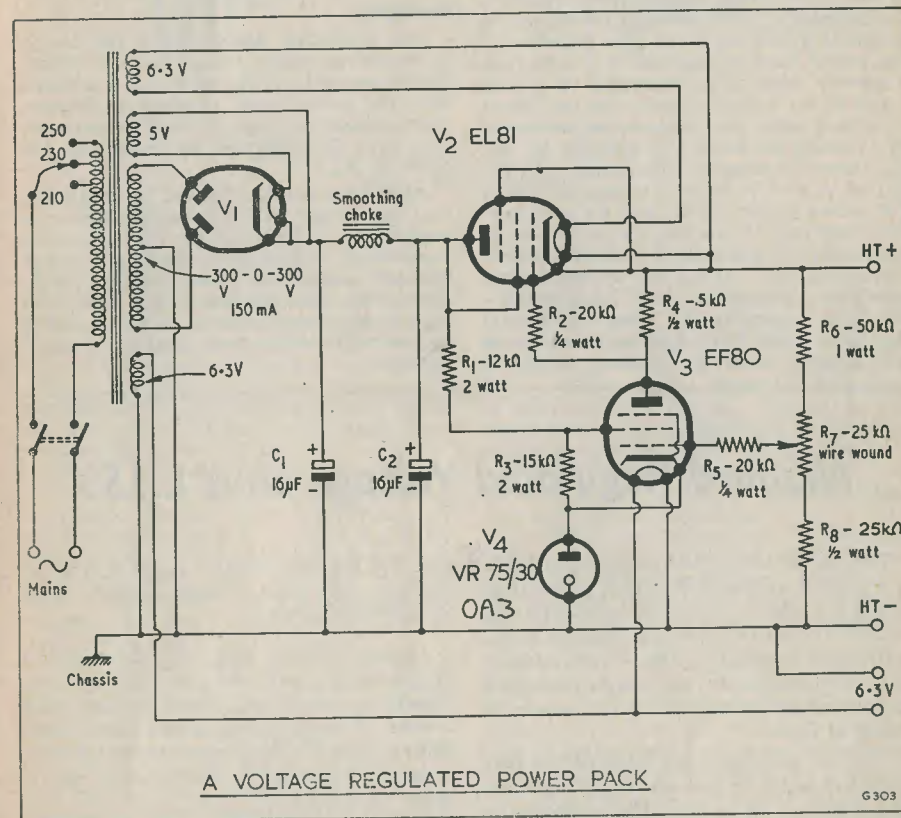

A VOLTAGE REGULATED POWER PACK

G303

its output terminals. For some reason, such as would be given by increased load current or by a drop in mains input voltage, the h.t. voltage at the output terminals commences to drop. This drop in voltage is then passed, via the tap into the potentiometer formed by R₆, R₇, and R₈ in series, to the grid of V₃.

Practical Points

It will be seen from the above that the output h.t. voltage always tends to revert to its original state, its reference voltage being provided by the regulator valve V₄. The purpose of the potentiometer R₇ is to apply the desired fraction of the total output h.t. voltage to the grid of V₃. Adjusting R₇

will, in practice, alter the stabilised voltage available from the power unit. The component values shown in the circuit should enable this control to provide regulated outputs between 150 and 250 volts. It should be pointed out, however, that regulation over a wide range of currents may be slightly lower when the output voltage approaches 150 or 250 volts than it is at the design centre of 200 volts.

If it is to be of practical use, a regulated power supply should be capable of accommodating changes in load current which occur at relatively high frequencies. This infers that the regulating circuit should function effectively during a small fraction of one cycle of the load current frequency. Unfortunately, if the action of the regulating circuit is made too quick it is possible for the power pack to oscillate at a very high frequency when it is connected to a load which is not purely resistive. In the circuit illustrated here this tendency is prevented by inserting the series grid resistors R_2 and R_5 , these operating in conjunction with the C_{gk} of V_2 and V_3 to form integrating filters. The values shown for R_2 and R_5 are somewhat high but, despite this, the circuit should still cope quite satisfactorily for load current frequencies up to 20 kc/s and above. Higher regulating frequencies could be accommodated by decreasing the values of R_2 and R_5 ; these being reduced, if necessary, to as low a value as several hundred ohms. If

such a course is followed the wiring between V_2 and V_3 should be kept short.

Due to the current passing through V_4 , a voltage regulator, and not a reference valve, has been chosen for this position. In consequence, the power pack reference voltage is liable to alter slightly as the current flowing through V_4 varies. The valve type given for V_4 has a shift of approximately 5 volts for a variation of current of 5 to 40mA. In this circuit V_4 should pass a current lying between the approximate limits of 10 to 22mA and should, in consequence, not cause any serious shift in reference voltage.

Sensitivity

The regulation sensitivity of the circuit is dependent mainly upon the value chosen for the anode load, R_4 , of V_3 . If it is found that the power pack provides inadequate regulation at very high or low load currents, this may be improved by increasing the value of R_4 .

As a final point, it should be mentioned that the heater of V_2 is supplied from a separate 6.3 volt winding on the mains transformer. The separate winding is recommended because the heater-cathode insulation of the valve specified is not sufficiently high to allow the heater to be connected to chassis whilst the cathode is at h.t. positive potential.

Mullard Regulated Voltage Unit L.153

The Mullard regulated voltage unit L.153 is a general purpose laboratory power unit, which provides a stable low impedance d.c. supply continuously variable between 0 and 300V at up to 300mA. Two 4A a.c. supplies of 6.3V, tapped at 4V, are also incorporated, as well as an unregulated e.h.t. supply of 1.2kV at 2mA.

The d.c. outputs of two units can be connected in series to give up to 600V positive and negative to earth. The variation in output voltage is less than 100mV for mains variations of +10% to -15%. Ripple voltage is less than 3mV, and output resistance is about 0.2 ohms.


The 1.2kV output can be either positive or negative with respect to the negative ter-

minal of the 300V supply. It can be used for cathode ray tubes, Geiger Muller tubes, photomultipliers, etc.

Output voltage and current meters are incorporated, and the unit is protected against overloads by a circuit breaker which breaks the supply connections and lights a warning lamp. This circuit breaker may be reset by operating a push-button on the front of the unit.

A new form of construction is used which enables the bench mounting case, in which the unit is supplied, to be very quickly removed for servicing and maintenance. The front panel and chassis are designed to fit any standard 19in rack.

IN
YOUR
WORKSHOP

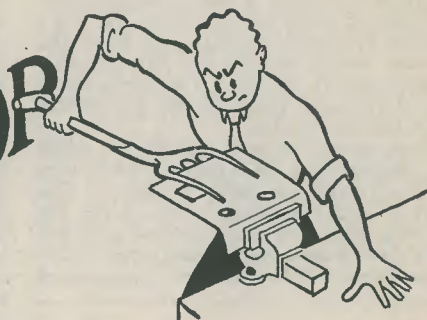

Once more, in these two experimental articles, J.R.D. hands over his space to old Smithy, the Serviceman.

WHEN DICK WANDERED INTO OLD Smithy's workshop just after nine o'clock one morning, the serviceman was in a very disgruntled mood. He had a television chassis lying on the bench but his customary array of test gear was absent. "You can't rely on anyone these days," grumbled Smithy, seeing Dick enter. "People just don't seem to be able to keep their promises like they used to."

"What's up?" asked Dick.

"I've got a faulty set on the bench," complained Smithy, "and I haven't even got a testmeter to help me find the fault. I was working late at a friend's house last night and, rather than take all my gear home, he promised to bring it in for me this morning. He hasn't turned up yet, so I'm stuck with a repair job I can't fix."

"Well, you've done repair jobs before now without gear," commented Dick, "perhaps you had better use your 'desert island technique' again this time!"

Smithy brightened a little. "Yes, I suppose I should," he said, "although I'm never very keen on using dodges or tricks in the workshop. That's because many supposed short-cuts often take longer than finding a fault in the text-book way. Nevertheless, I might be able to do something in this instance."

He reached into a drawer and pulled out a small home-made device. It had a short body covered with sleeving, from either end of which protruded two flexible insulated leads about nine inches long. One lead was

terminated in a crocodile clip, the other in a test prod.

"Now this," he said proudly, "is an extremely clever little device, designed especially for checking television receivers. With this I can locate faults anywhere in the a.f. stages, in the frame timebase, and in the decoupling circuits. The set on the bench has no frame deflection so this little gadget should prove ideal for the job."

Dick was suitably impressed.

"What is it?" he asked, "a midjet transistor oscillator or something?"

"Nothing so complicated," chuckled Smithy. "All it consists of is a common-organ garden 0.01 μ F paper condenser! The sleeving just helps to insulate and anchor its leads. See?" And he gave the simple arrangement to Dick to examine. (Fig. 1).

"Now for a demonstration," continued Smithy. "I start off by clipping the croc clip on to the grid of the a.f. output valve. Then, when I touch the test prod with my finger I get a slight hum from the speaker of the set, which is just what you'd expect. Now let's see if we can chase the missing frame timebase waveform. The frame oscillator is a blocking oscillator, so let's see what happens when I touch the test prod on its anode."

As he applied the test prod to the anode a 50-cycle buzz became audible from the speaker of the televisor.

"That's fair enough, then," said Smithy. "The blocking oscillator seems to be O.K. Now, let's try the anode of the frame output

valve. A quick touch of the prod is all we want here, because, if it's working properly, there will be a fairly high amplitude at this point. Ah, silence. That shows there is no frame waveform there. The next step is to check the frame output grid. There's a coupling condenser to this grid from the oscillator anode and it's just possible that it's gone o/c. It has, too! There's no frame buzz at the grid, even though it's present at the previous anode.

"Now, before we start making too many rash assumptions, let's make doubly sure that that condenser really is faulty. This I can do with the device again. I put the croc clip on to the frame output grid and touch the test prod on the oscillator anode. Before I started I'd set the brilliance control

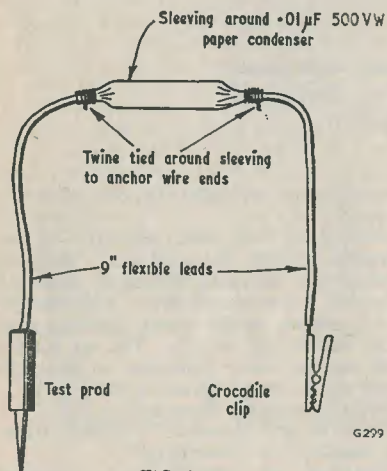


FIG. 1.

right back to avoid damaging the tube, so we'll turn it up again. And, as you can see, we get a picture!

"What's happening now is that the 0.01 μ F condenser is bridging the open-circuit condenser in the set. The frame linearity is incorrect but that's only because the temporary condenser has the wrong value. When I put in a new condenser with the correct value everything should be as right as rain again."

"That's certainly a useful dodge," said Dick. "How else can you use the condenser?"

"It's always useful for checking a.f. stages," replied Smithy, "because you can use it in the reverse direction. This time you put the clip on the frame output grid, whereupon you have a 50 cycle buzz on the test prod. You then trace back along the a.f. chain until you find the place where the

buzz disappears. Apart from the frame oscillator there is another source of a.f. in the set which you can use if you like as well, this being given by putting the clip on to one of the heater pins of a valve which is very near the earthy end of the heater chain. This time you get a 50 cycle note. Pure 50 cycles—as reproduced through a high fidelity amplifier—is practically inaudible, but most t.v. a.f. systems are so 'low-fi' that you can hear its harmonics.

"If you get instability in a set you can fix the croc clip to chassis and prod all the decoupling points to see if any decoupling circuit has gone o/c. It's rather 'naughty', expecting nine-inch leads to provide a suitably short decoupling path when checking an i.f. strip working at 30-odd Mc/s, but even at these frequencies the idea seems to work quite well. And, of course, the gadget has its uses with a radio chassis, too."

"Well," said Dick, "when I get home I am going to augment my test equipment with one 'Smithy Patent Test Probe'! It'll be the cheapest piece of gear I've got."

In the meantime Smithy had commenced to solder in a replacement condenser. He handed Dick a book whilst he concentrated on his work.

"Have a look at that," he said. "It concerns what we discussed the last time you called in."

"Oh, yes, I remember," said Dick. "We were talking about wires and the wave-winding of coils. I was just about to ask you how the wire on wave-wound coils was actually placed on the former."

"That's right," said Smithy, putting the iron back on its rest and pulling up a stool. "Now, this booklet will help you to understand how it is done. In my factory days, before I set up for myself, I used to have quite a lot to do with coil-winding. Anyway, let's return to the book. Now, this is a manual for a 'Douglas' wave-winding machine. 'Douglas' wave-winders are used more commonly than any other machine in British radio factories, so we're on good ground here. Have you heard the name of the manufacturers before: The Automatic Coil Winder and Electrical Equipment Co.?"

"Why, yes. They're the people who make the 'Avo' test equipment, aren't they?"

"Correct! Now, let's have a look in this manual. Here's a layout of the complete machine, and this should enable us to split it down into its various parts. Now, the main purpose of the machine is to lay the coil wire on the former such that it travels from side to side. This particular job is carried out by means of the wire guide. The wire guide consists of the wire guide arm, the pulley, and the button. (Fig. 2).

"First of all, therefore, let's examine the

wire guide arm. This is fitted to a horizontal spindle in such a manner that the wire guide arm is free to move on the spindle as axis. However, the arm cannot move in a lateral direction. I think this sketch I'm drawing makes that fairly clear. At the top of the wire guide arm there are the pulley and button. The pulley guides the wire on to the button, which rests flat against the surface of the coil. The groove in the surface of the button then guides the wire on to the exact point on the former it is intended to go. (Fig. 3). Now you can see why the wire guide arm is pivoted on the spindle. Since the diameter of the coil will be increasing all the time that it is

builds up. This is done by making the wire guide spindle move from side to side laterally whilst the coil is being wound. (Fig. 4). The lateral oscillation of the spindle is then transmitted directly to the guide arm and its button, with the result that the wire falls into the correct position on the former as the latter rotates."

"How do you move the spindle, and how do you know that it will travel over the right distance?"

"That brings in another piece of mechanism. To begin with, the lateral oscillation of the spindle is obtained by coupling it up to a special cam. This cam (Fig. 5) has a groove in its surface in which a roller

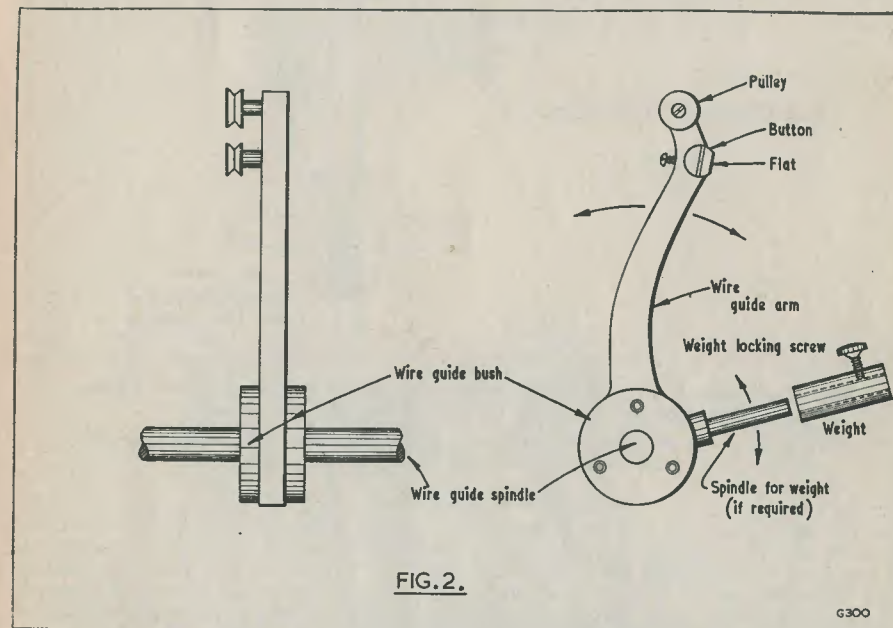


FIG. 2.

Fig. 2. Simplified view of the wire guide arm of a "Douglas" wave-winder. (This and subsequent diagrams are simplified and are not necessarily to scale, and may omit many of the various adjustments available on the "Douglas" wave-winder)

being wound the button must be free to move away from the former. To keep the button pressed firmly against the coil, provision is made for mounting a weight on the wire guide arm. (Fig. 2). The position of this weight then regulates the pressure of the button on the surface of the coil. Sometimes the weight is not needed, as the weight of the guide arm itself is quite sufficient.

"Whilst the button is guiding the wire on to the coil, it is necessary to ensure that the wire forms the right pattern as the coil

engages tightly. When the cam revolves, the roller is forced to follow the contour of the groove. The sideways motion of the roller is then transmitted to the wire guide spindle via the actuating spindle and a pivot. (Fig. 6). An interesting point in this particular assembly is that, by moving the pivot towards the cam roller, you can increase the distance over which the wire guide spindle oscillates; and vice versa. The net result of this is that, whilst the cam movement is transmitted to the wire guide spindle via the pivot, the position of the latter also provides an adjust-

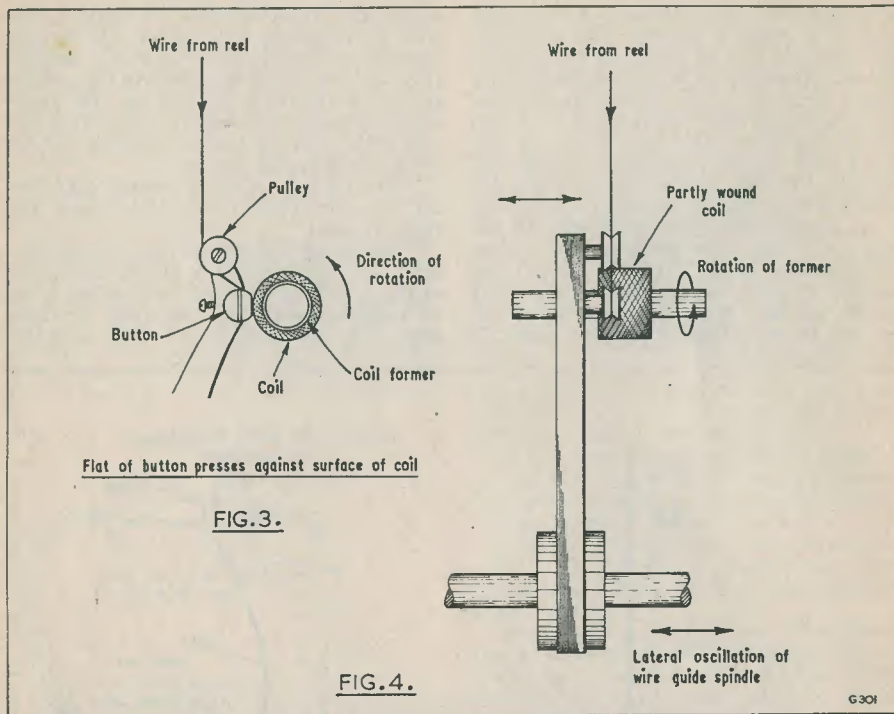


Fig. 3. Showing how the flat of the button rests against the surface of a coil being wound, thereby laying the wire in the position required

Fig. 4. To cause the wire to move from side to side as the coil is wound the wire guide spindle oscillates laterally, as shown here


ment of the width of the coil being wound. Thus, to obtain a coil of a certain width, all you have to do is to set the pivot to the right position. In the 'Douglas' machine the pivot is mounted on a 'throw adjusting block' and a screw thread adjustment enables you to set this block just exactly where you want it."

"Well, that's the basic mechanics of the cam and wire guide system. However, although the cam system may look quite simple in its bare bones, a lot of hard work has to be put into making it a really practicable proposition. Probably the most important thing to ensure is that no lateral 'play' exists in the whole system from the cam to the wire guide button. It takes good engineering to make certain of that."

"Well, I think that seems pretty clear," said Dick. "What I can't understand yet, though, is how the machine can wind different gauges of wire. Is there some ratio between the revolutions of the cam and the coil former?"

"There is, indeed," replied Smithy. "The two are coupled up by means of an adjustable gear train rather like the gear train used on a lathe for screw thread cutting. Adjustment of the gear ratio is given by fitting different gear wheels, as required. To wind a particular coil you work out the gear train from the diameter of the wire you intend using and the width of the coil. The wire diameter enables you to substitute in a special formula, after which you find the particular gear train you require with the aid of a table. The width of the coil is a factor in determining whether a complete wire guide cycle—from side to side and back again—occurs for approximately one, or a multiple or fraction of approximately one, complete revolution of the former. There is an adjustable train of gears to satisfy this second requirement as well."

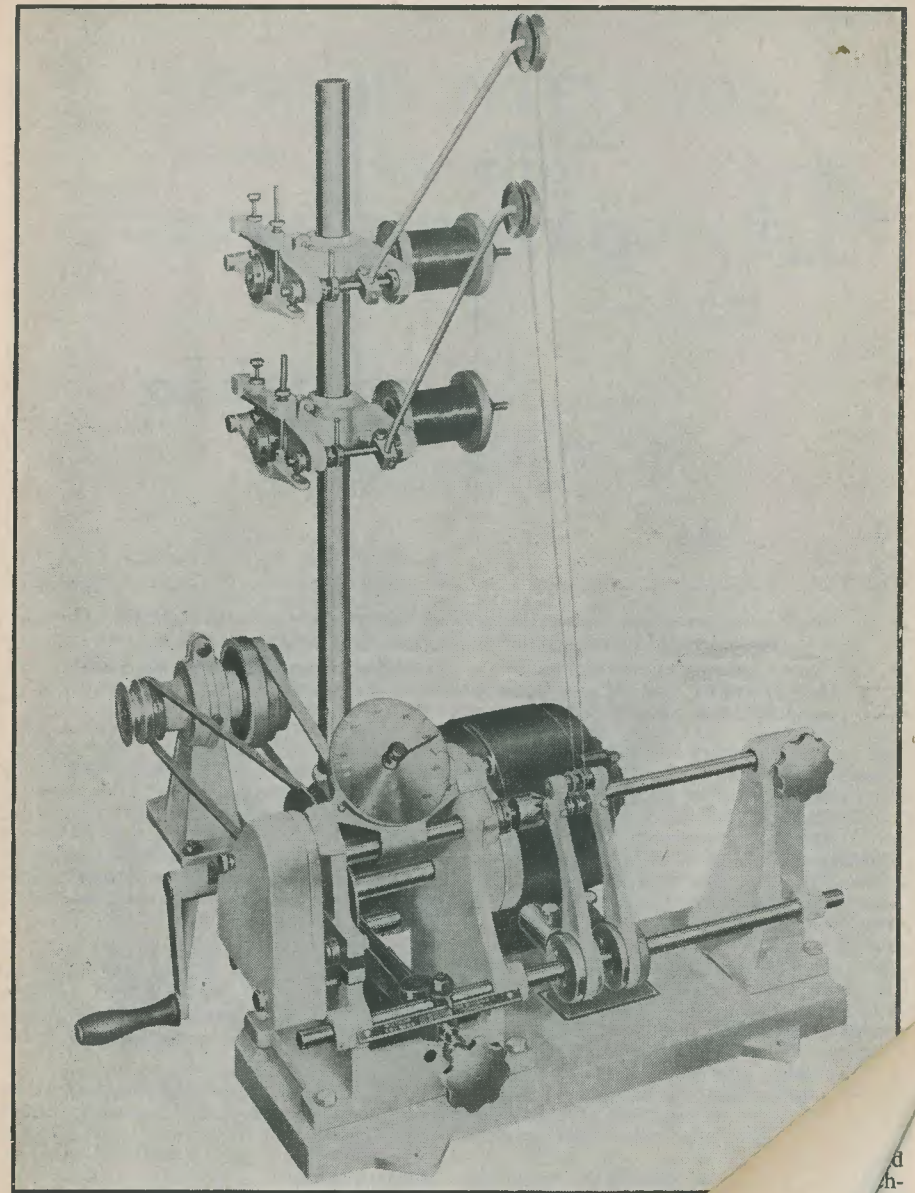"Phew!" said Dick, after a few thoughtful moments. "As I said last time, with radio you always find something new whenever you begin to examine any part of it in real



The complete "Douglas" wave-winding machine. The "clock" machine counts the number of turns wound on the coil. The bottom adjusts the position of the throw adjusting block. The gears (as shown here) are clearly visible on the wire guide spindle. The view, is to the rear of the machine, beneath the clock.

As a
Feltham
acquired
620

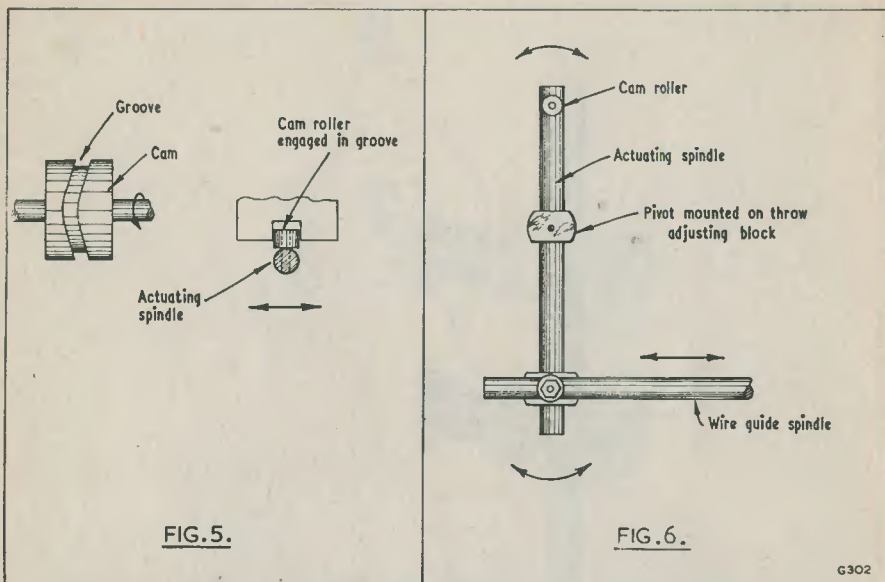


Fig. 5. The cam which causes the oscillatory motion of the wire guide spindle. The cam is coupled via a gear train to the head stock holding the coil former

Fig. 6. Showing how the cam roller is coupled to the wire guide spindle. The oscillation, or "throw," of the wire guide spindle can be adjusted by moving the throw adjusting block nearer to, or further away from, the cam roller

detail. Sometimes I wonder if it is possible to know even half of all there is in radio."

Smithy sighed a little.

"That's truer than you think," he said quietly. "There is so much to electronics these days that you are almost forced to specialise in a particular branch if you really want to keep abreast of things. I'm one of the old school, I suppose, and am liable to get rather nostalgic about the old times. In those days everybody in radio was an enthusiast. To a lot of people nowadays, radio is just a job. I suppose I've got old-fashioned ideas, Dick, but my advice to anyone who, like yourself, is considering making electronics his career is to tackle it always from the viewpoint of the enthusiast. You'll get a lot more fun from your work that way."

A car horn tooted outside the workshop. "Anyway," said Smithy, brightening up, "that's enough of senile philosophy for

to-day! Unless I'm mistaken my missing test gear has turned up; and I've got my living to earn. So, after we've put this set back in its box we'll tackle that other one on the shelf there. The brilliance is uncontrollable, and I'm keeping my fingers crossed for my customer's sake that the tube doesn't have a cathode-heater short . . ."

Grateful acknowledgments are made to The Automatic Coil Winder and Electrical Equipment Co Ltd. for assistance rendered with regard to drawings and mechanical details of wave-winder operation used in this article.

The "progressive" wave-wind operation described in last month's article should not be confused with progressive wave-winding wherein the wire-guide arm travels progressively laterally in addition to its oscillatory motion, and for which a separate "Douglas" machine is available.

Change of Address

As a result of a serious fire at their Feltham Works, Valradio Limited have acquired new premises, which are consider-

ably larger in Browells Lane, Feltham, Middlesex. The telephone numbers will remain as Feltham 4242 and 4837.

BAND III TELEVISION for the HOME CONSTRUCTOR

PART 11

by S. WELBURN

This month S. Welburn continues his popular Band III series by reviewing the possibilities of channel selection. He discusses various techniques, looking at these from the point of view of the amateur constructor.

SINCE THE CHANCELLOR OF THE EXCHEQUER seems to have the impression that it is far more sinful for a retailer to sell a television set than it is for a Ministry to re-sell £26,000 worth of goods it didn't want for £13,000, the prospects of having a third Band III service do not appear to be particularly bright at the time being.

However, the situation is not too dismal, because there is the possibility that quite a few viewers already have a choice of three programmes. These programmes are given by existing B.B.C. transmissions, plus the two I.T.A. stations operating on Channels 8 and 9. Whilst the two I.T.A. transmitters sometimes carry the same programme there are frequent differences, and viewers in certain localities could, in consequence, take advantage of whatever of the three programmes they care to choose. A similar choice of programmes may be available to other viewers when Channel 10 comes on the air.

Because of this state of affairs it might be of value to examine the possibilities of channel selection in home-constructed Band III equipment.

Channel Selection

For the constructor who is prepared to experiment, the provision of Band III channel selection to a converter is a fairly simple operation. A certain amount of mechanical ingenuity is needed, but amateurs have not in the past shown themselves to be lacking in this respect.

There are four main ways in which channel selection can be carried out in Band III converters. These are by variations in

tuning capacity; by variations in tuning inductance due to the physical movement of slugs in and out of coils; by variations in tuning inductance provided by switching in incremental inductance; and, finally, by taking advantage of turret tuners. Let us now consider these different methods of channel selection in more detail.

The first method of channel selection mentioned in the last paragraph is by variations in tuning capacity, these being possibly provided with the aid of a switch. As most readers will be aware, this scheme is not very attractive on technical grounds owing to the fact that, at Band III frequencies, it is necessary to keep the L/C ratio of all tuned circuits as high as is feasible. Indeed, normal Band III practice tries to ensure that, wherever possible, all resonant circuits are tuned by little more than the stray capacities appearing across each coil, plus the inevitable valve capacities which must exist in the circuit to which each coil is connected.

Despite this, tuning by variations in capacity is still fairly attractive if the channels being selected are not too far apart in frequency. To take an example, tuning by variable capacity between Channels 10 and 8 would not constitute too heinous a technical offence so long as it was appreciated that the converter gain on Channel 8 (where the extra tuning capacity would have to be introduced) could be noticeably lower than on Channel 10. The shift from Channel 10 to Channel 8 constitutes a change in operating frequency of 10 Mc/s, and this would probably be the largest shift which should be attempted by capacity variation alone.

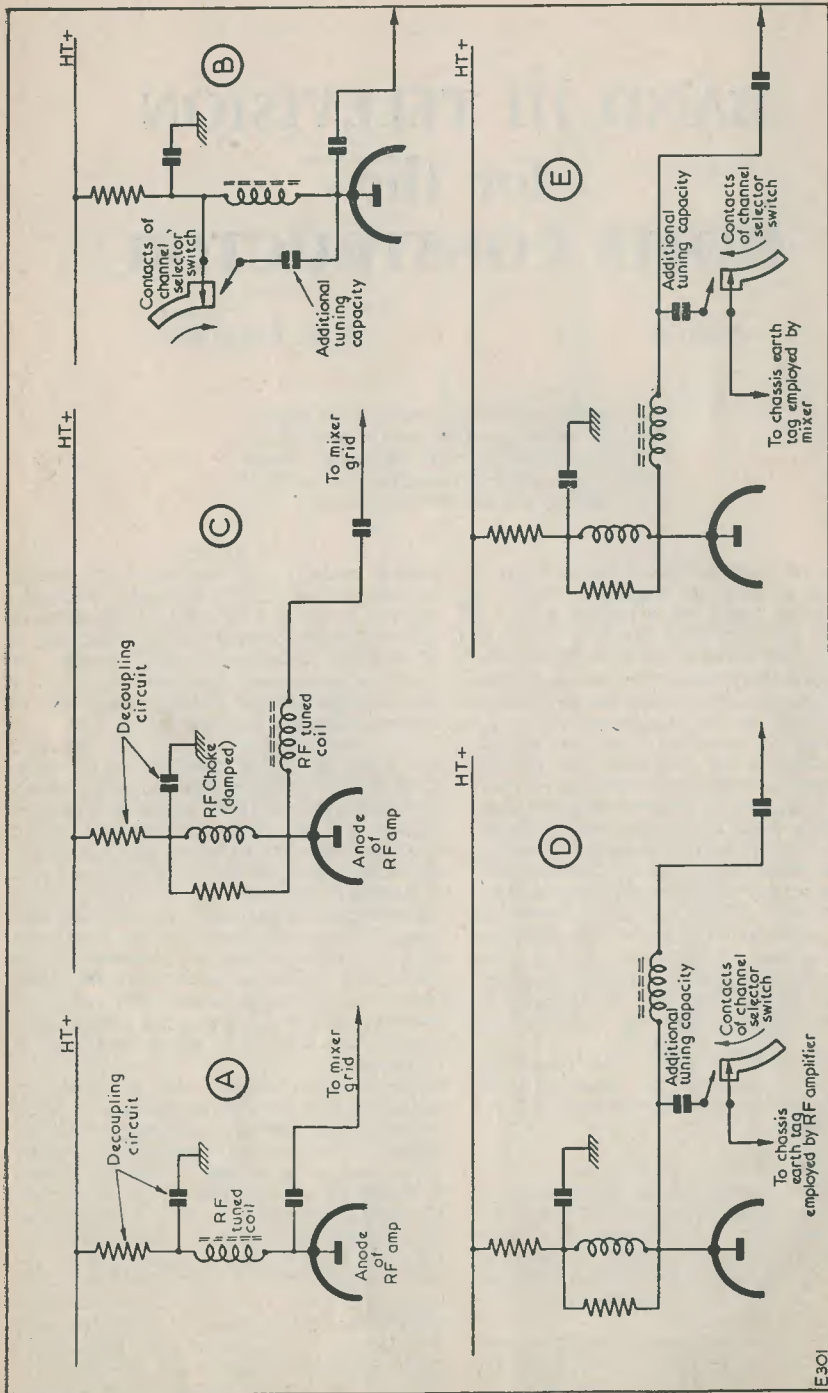


Fig. 1(a). A typical shunt-tuned circuit Band III coupling circuit. (b) For low frequency changes the channel selection arrangement shown here would be simple and effective. (c) A series-tuned coupling circuit. (d) and (e) Two methods, discussed in the text, of providing incremental tuning of the circuit of (c). Note the chassis returns recommended

The situation where the two required channels are adjacent to each other should normally be capable of solution with the aid of a "fine tuner" in the oscillator circuit alone. This fine tuner would need to have a capacity swing adequate enough to cover the two adjacent channels; whereupon the aerial and r.f. coupling coils could be peaked to a point midway between the two channels, or to the channel which provides the weaker signal. This process may result in a slightly lopsided converter frequency response curve on one (or both) of the channels. However, the normally low Q given by most Band III coils results in such a flat response that it is doubtful if any very deleterious effect would be noticeable in the picture itself.

To revert to the case where it is intended to capacity-tune the converter over 10 Mc/s, or so, a slightly more complicated situation arises. This is due to the necessity of tuning not only the oscillator but the aerial and r.f. circuits as well.

So far as the oscillator is concerned it would definitely be advisable to retain a variable fine tuning condenser, this being given a capacity swing sufficient to cover the larger range now required. The reason for this choice is that, if additional capacity were introduced into the oscillator tuned circuit by means of a switch, the reset accuracy of the latter would not be sufficiently high to ensure correct oscillator frequency each time it was operated. A fine tuning condenser would still be required; whereupon the fitting of a switch as well becomes pointless.

A high switch reset accuracy is not required at the r.f. coupling coil. If this employs a shunt tuned circuit, as shown in Fig. 1 (a), the switching circuit used could be that illustrated in Fig. 1 (b). It should be noted that the additional tuning capacity is returned via the switch to the "dead" end of the coil and not to chassis. If a series-fed coupling circuit (or pi-network), of the type shown in Fig. 1 (c) is used in the converter, the additional capacity may be switched in between either end of the coil and the applicable chassis point, as illustrated in Fig. 1 (d) or (e). The end of the coil which causes greater frequency shift for similar capacity change is that to which the switch circuit should be connected. It is probable that this will normally be at the anode end of the coil. It should be noted that, in Fig. 1, the actual switch contacts have been shown. This has been done to emphasise the necessity of keeping the capacity to chassis as low as possible.

The aerial coil may be treated similarly to the r.f. coil of Figs. 1 (a) and (b). In some converters, however, the aerial coil may have such a flat response that little advantage

would be given by using capacity variation at all, the coil being set to the best compromise position between the two channels.

In Fig. 1, the additional tuning condensers switched in for the shift in channel frequency are shown as fixed components. The value of these condensers could normally be found empirically, checking tuning by means of the coil slug after fitting each particular experimental value. Ceramic condensers would be essential. Air-spaced or ceramic trimmers could, of course, be employed instead of fixed condensers, but they are liable to be bulky and may not have a sufficiently low minimum capacity. Normally, the additional tuning condensers would have a value of a few pF only.

The switch employed for adding the additional capacity need not necessarily have ceramic insulation, but it must be of reliable construction and should have silver-plated contacts. The switch contacts must be positioned very close to the appropriate coil, and the circuit through the metal-work of the switch itself must be kept as short as possible.

Variable Inductance Tuning

Variable inductance tuning is, from the technical point of view, much better than variable capacity tuning. The reason for this is that it maintains a high L/C ratio. The second method of channel selection for the home constructor mentioned earlier referred to tuning by means of the physical movement of slugs in and out of coils. As some constructors may be aware, this system is used in at least two commercial converters, and is also employed in a standard "front-end" by a television receiver manufacturer. In some of the commercial units the insertion of slugs into the aerial, r.f., and oscillator coils is carried out by means of a ganged mechanical assembly. An assembly of this type requires a great deal of design skill and development time if it is required to track accurately over a large number of channels, and would probably prove to be an unprofitable venture for the amateur whose equipment is limited. However, a ganged assembly which is intended to track accurately over two or three channels only should not be too difficult.

Some care has to be exercised in the choice of slug material which would be employed for a channel selection arrangement of this type. Normal iron-dust cores, as used in such things as 465 kc/s i.f. transformers, etc., are liable to cause severe losses at Band III frequencies. At such frequencies manufacturers employ iron-dust cores made especially for v.h.f. work. In these cores the particles of iron are very widely separated in the plastic insulating material which forms the body of the core, with the result that

losses at Band III frequencies are considerably reduced. The reduced iron content of the v.h.f. type iron-dust core results, incidentally, in a lower permeability in the material, and reduced inductance change. For the amateur who still wishes to use normal broadcast-frequency iron-dust cores, probably the best solution would consist of allowing these to enter the coil no more than, say, quarter-way. This would give a fairly useful frequency range without introducing too many losses.

At v.h.f. the losses introduced by brass slugs are normally lower than those given

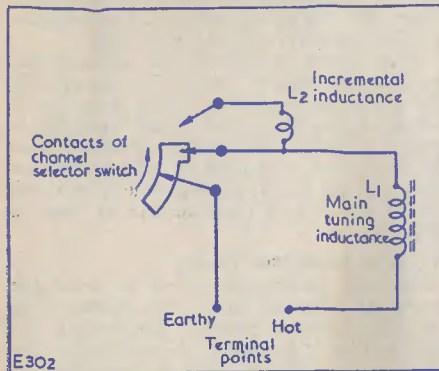


Fig. 2. The basic incremental inductance switching circuit

by broadcast-frequency iron-dust cores. The effect of a brass slug as it enters a coil is that of reducing inductance. Unfortunately, the tuning range given by a brass slug is usually noticeably lower than that given even by a low-permeability v.h.f. type iron-dust core of the same size. However, a relatively large brass core should give a tuning range of some 20 Mc/s or so at Band III frequencies if its outside diameter is permitted to closely approach the internal diameter of the coil it tunes.

Incremental Inductance

Probably the most attractive method of channel selection available to the amateur is provided by the switching of incremental inductance. This is fairly simple to accomplish technically, and the only mechanical design considerations involved are those of ensuring that the switch contacts employed are positioned very close to the circuits concerned. Once again a reliable switch (not necessarily with ceramic insulation) is required, and silver-plated contacts are essential.

The basic switching circuit required for incremental inductance channel selection is illustrated in Fig. 2. In this diagram the main tuning inductance is provided by the coil L_1 . Since we are speaking in terms of Band III frequencies it would be more realistic to state that the real tuning inductance is that provided by the coil plus the inductance of the metal path, including the switch contacts and wiring, between the terminal points. (The terminal points would be those which connect to the appropriate valve electrodes or chassis decoupling circuits). When the switch of Fig. 2 is turned in the anti-clockwise direction an extra coil, L_2 , is connected in circuit; this causing the total inductance to increase. It is important to remember once again that the real inductance of the arrangement is given by the total metal path between the terminal points with the result that, when the switch is turned to the anti-clockwise position the length of this path is increased in the switch itself as well as in the external inductance. The necessity for keeping this point continually in mind will be appreciated when it is realised that the coil L_2 may, in practice, consist of a straight piece of wire, or even two straight pieces of wire in parallel!

The attraction of the incremental inductance method of channel selection for amateur use is given by its extreme simplicity, its cheapness, and its reasonably high efficiency. It is also fairly easy to set up and align.

An example, in which the arrangement is used with a converter oscillator, is illustrated in Fig. 3. In this case, the incremental inductance is added at the grid end of the coil, it being assumed that this has the lower impedance to chassis. As may be seen, a fine tuning condenser is still retained, this being necessary to finally trim the oscillator tuned circuit. The reset accuracy of the switch could not normally be relied upon to give sufficient accuracy of inductance at the oscillator position. If the arrangement of Fig. 3 were used in the oscillator circuit of a converter, the arrangement shown in Fig. 2 could be employed for the r.f. and aerial tuned circuits. The total switching facilities would then be given by a 3-wafer switch traversing the length of the converter chassis, each wafer being positioned close to the tuned circuit it switches.

Practical examples of the incremental inductance "coils" brought into circuit by the switch are illustrated in Fig. 4. Fig. 4 (a) shows a coil having a single turn, this being probably sufficient to cause a frequency shift of 4 or more channels at Band III frequencies. The "coil" shown in Fig. 4 (b) would cause a possible shift of some 2 to 3 channels, and that illustrated in Fig. 4 (c) a shift of approximately 1 channel. In

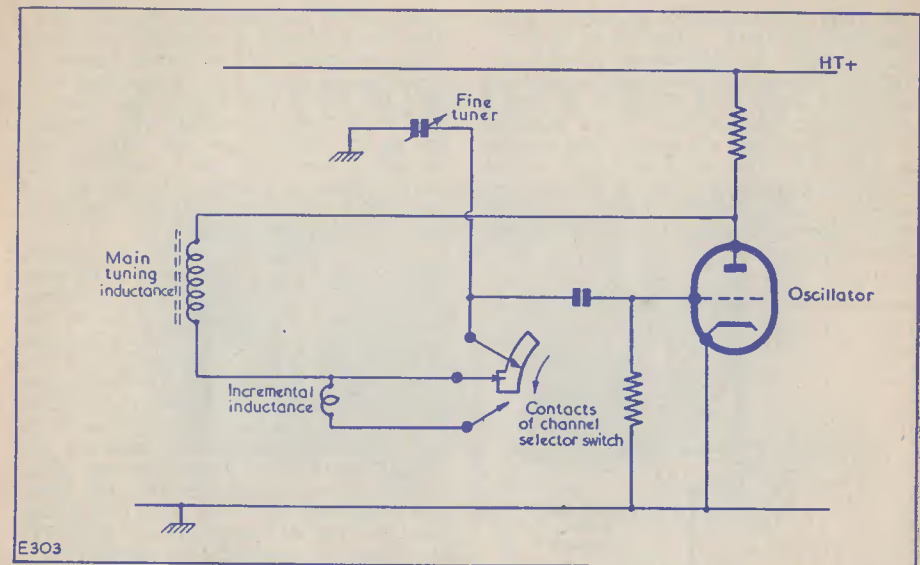


Fig. 3. Applying incremental inductance switching to the oscillator of a converter

Fig. 4 (b) inductance can be increased by increasing the length of the wire between the two switch contacts; whilst, in Fig. 4 (c), inductance can be adjusted by altering the length of either one or both of the wires.

cope quite adequately for the additional inductors. It is worth pointing out, also, that the inductance of the incremental coils will decrease slightly as wire diameter increases, and vice versa.

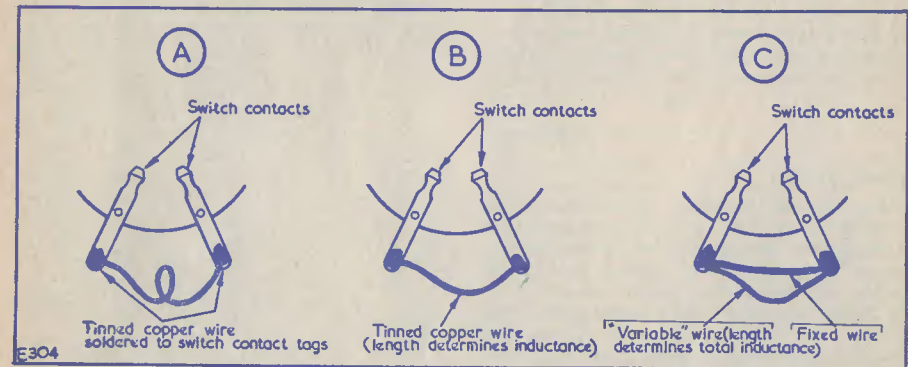


Fig. 4. Some practical incremental inductance "coils." The possible frequency shift given by these "coils" is discussed in the text

The preparation of the incremental inductances required is entirely empirical, experimental "coils" being soldered across the switch contacts and the resultant total inductance checked by adjusting the slug of the main coil. Bare tinned copper wire of any gauge thicker than 24 s.w.g. should

For those who wish to try something a little more ambitious, the circuit shown in Fig 5 may be of interest. This shows an incremental inductance arrangement capable of switching to two Band III frequencies and one Band I frequency. The Band I frequency is selected when the switch is in

the fully anti-clockwise position, thereby switching in coil L₃. The circuit of Fig. 5 is, in reality, a scaled-down version of a normal commercial incremental inductance switching circuit, and is not at all outside the range of the amateur who is prepared to experiment with the simple coils required at Band III. The circuit of Fig. 5 should, of course, be employed with the conventional cascode, triode-pentode line-up which has now become established practice in television front-ends.

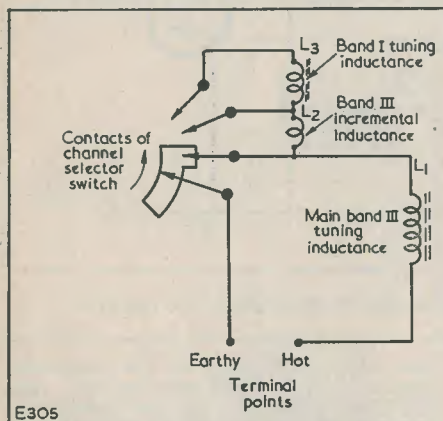


Fig. 5. A more ambitious arrangement, providing selection of one Band I and two Band III channels. The Band I coil will need to have slightly less inductance than it would normally have if employed on its own

Turret Tuners

For several reasons, turret tuners may present rather more difficulty to the amateur than is given by the simpler type of converter which employs fixed coils. This is due to the fact that turret tuners are not quite so readily available on the home constructor market as are other types of tuners, and because technical information on some units may be difficult to obtain. There is the further point that many turret tuners employ band-pass coupling between the r.f. stage and the mixer grid, and are consequently rather difficult to align without the aid of a wobulator and oscilloscope. However, despite these points, the presence of turret tuners on the home constructor market cannot be ignored, and the following notes may consequently be of interest and value.

Practically all turret tuners consist of a self-contained chassis holding the r.f. and

mixer stages, together with the coil turret. The turret chassis is normally capable of being connected into a receiver merely by the coupling up of h.t., heater, and a.v.c. lines, etc. The turret tuner will have its own aerial input terminals, with provision for an i.f. output from the mixer anode. Usually, a tuned i.f. coil is fitted into the turret chassis, a coupling winding on this coil supplying a low-impedance output to the i.f. strip of the receiver.


From the point of view of the amateur who is considering employing a turret tuner as the front-end of a receiver, the first thing to ascertain is the frequency of its i.f. coil. If the frequency of this coil differs from that of the set with which it will be used, a new coil will have to be wound. Unfortunately, changing the turret i.f. will upset the oscillator tuning of the individual turret coils. If the new oscillator frequencies required are outside the range of slug adjustment of the appropriate oscillator coils, the coils themselves will have to be adjusted. Coil adjustment at Band III frequencies may frequently be effected by squeezing the turns together (to increase inductance) or opening them out, as required, but it should be pointed out that this process is only recommended to those who feel competent to tackle it.

Winding new coils for a turret tuner is a fairly skilled business, but is not outside the scope of the reasonably experienced amateur. If spare coil formers and "biscuits" are not available for a new channel, those for an existing channel which is not in use could have their windings removed and new coils fitted to their formers. The new coils should be wound primarily to resemble any existing coils in the turret which are close to the desired frequency. Thus, a Channel 8 coil would provide a good "model" for an experimental Channel 7 coil. After winding, a little adjustment in turn spacing and dressing may then yield quite satisfactory results. So far as band-pass coils are concerned, the best plan would consist of trying to make the spacing between the new coils equal to that of any existing coils which are close in frequency to the channel concerned.

Before concluding, the writer would like to stress once more that it would be unwise for the amateur to experiment too widely with turret coil assemblies unless he is confident of success. In the case of turret tuners fitted to commercial receivers, new coils should be obtained from the manufacturers of the receiver.

If the writer is able to obtain sufficient practical information in time, he hopes to deal with Band III alignment using a wobulator and oscilloscope in next month's contribution.

The "TRANSISTORETTE"

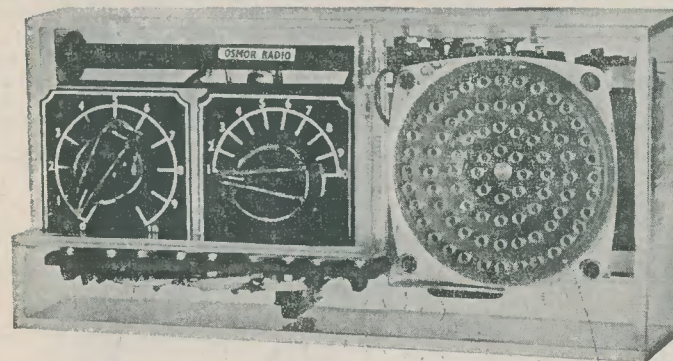

PART 4.

by G. A. FRENCH

In this article, the fourth in the series describing the Transistorette, G. A. French gives details of the Perspex cabinet in which this transistor receiver was presented in the 1955 Radio Show at Earl's Court. Our contributor also discusses one or two small points concerned with operation.

IN THE LAST THREE ISSUES OF *The Radio Constructor* full details of the chassis of this modern transistor receiver were given. In this concluding article we pass on to the construction of a suitable cabinet.

When the Transistorette was exhibited at the 1955 Radio Show it was housed in a cabinet made of Perspex. As may be imagined, the effect given by this method of presentation was most striking, since the cabinet was very attractive and it also enabled the public to obtain an excellent idea of the internal construction of the receiver. It is possible that many constructors may wish to employ this type of cabinet in their own versions.

Alternatively, it might be found preferable to build the cabinet with an opaque material. In such a case the dimensions given in this article will still apply, so long as provision is made for any differences given by varying thicknesses of material. The Perspex employed for the Exhibition cabinet had a thickness of $\frac{1}{8}$ -inch, and joints were made with the aid of an adhesive, it being sufficient to have all corners butt-jointed. A similar technique is, of course, quite possible with other materials. A typical choice for such a

material would be plywood. An attractive finish could be given also by covering the completed cabinet with rexine, skyver, or a similar type of cloth.

Dimensions

The appearance and general layout of the completed cabinet will already have been learned from the photographs accompanying these articles. As will have been seen, a particularly compact assembly is given by means of sinking the two control knobs. The tops of these knobs then lie slightly above the surface of the remainder of the cabinet.


Apart from their being applicable to materials of $\frac{1}{8}$ -inch thickness, it should be pointed out also that the dimensions given in this article apply to the receiver when it is used with the Ever Ready B.122 hearing-aid battery. If a B.110 battery, which is slightly larger, is used it will be necessary to extend the dimensions of the top, bottom and two sides by $\frac{1}{8}$ -inch at the loudspeaker end.

As we mentioned above, butt jointing is used for the corners of the cabinet. The adhesive employed for the prototype was

Durafix, and this enabled a cabinet of more than adequate mechanical strength to be constructed.

The dimensions of the top piece of the cabinet are illustrated in Fig. 22. It will be noted that a centre is shown in this diagram for the loudspeaker cut-out. The cut-out may be obtained either by making a clean hole of $1\frac{1}{2}$ inch radius on this centre (the hole being later covered on the underside by loudspeaker fabric), or by drilling a series of holes in the material. If the latter device is adopted, a suitable drilling layout is given in Fig. 21.

Fig. 26 (a) and (b) show the two side pieces. That illustrated in Fig. 26 (a) is purely rectangular in form and requires no further discussion. The side piece shown in Fig. 26 (b) will butt against the control panel, and it has four holes drilled in it for the aerial-earth panel. This latter should be a standard item available from an advertiser, but the reader is advised to check the dimensions of the particular panel obtained before finally drilling the holes for it. The aerial-earth panel will be mounted behind the cabinet material, the aerial and earth plugs passing through the two $\frac{1}{4}$ -inch holes

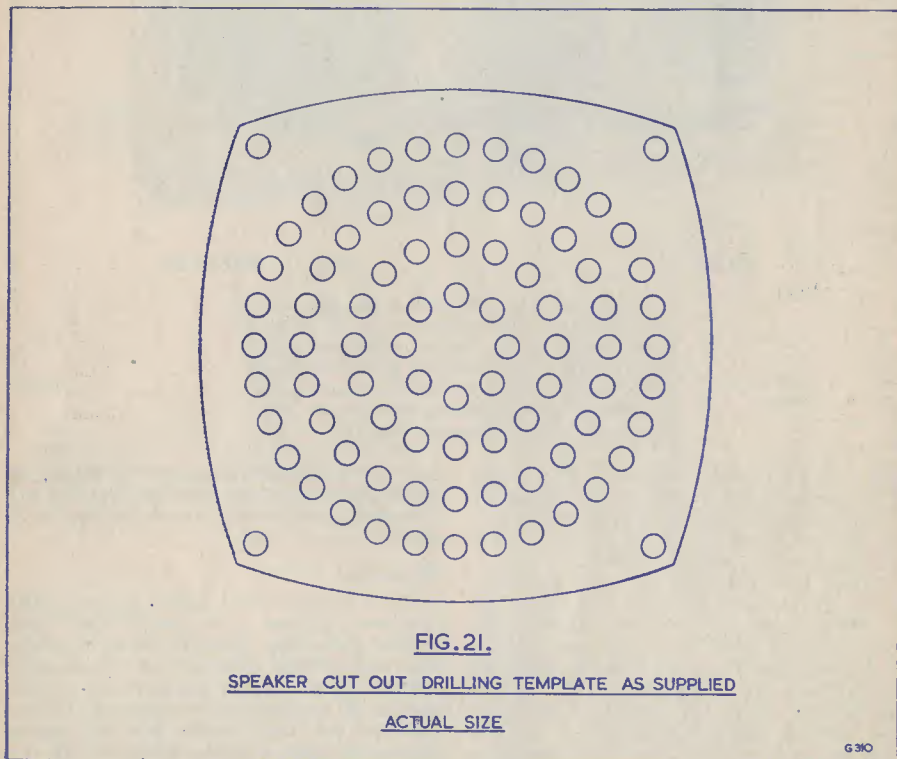

The two ends of the cabinet come next. These are illustrated in Fig. 23 (a) and (b). Fig 24 (a) and (b) illustrate the two pieces which form the recess for the sunken control panel.

The panel itself is illustrated in Fig. 25. There is little that requires comment here, apart from emphasising the necessity of marking out and drilling the two $\frac{3}{8}$ -inch diameter holes accurately. The chassis will later be mounted by fitting the bushes of the volume control and tuning condenser through these holes.

illustrated in Fig. 26 (b) before making contact with the appropriate sockets.

The bottom of the cabinet is shown in Fig. 27. This diagram, together with those showing the side end dimensions, does not include any details for fixing the bottom to the remainder of the cabinet. This omission is due to the difficulty of specifying standard parts for such a fixture, in addition to the fact that readers' individual ideas may vary on this point according to their tastes and the workability of the material employed. In the prototype, the cabinet bottom was

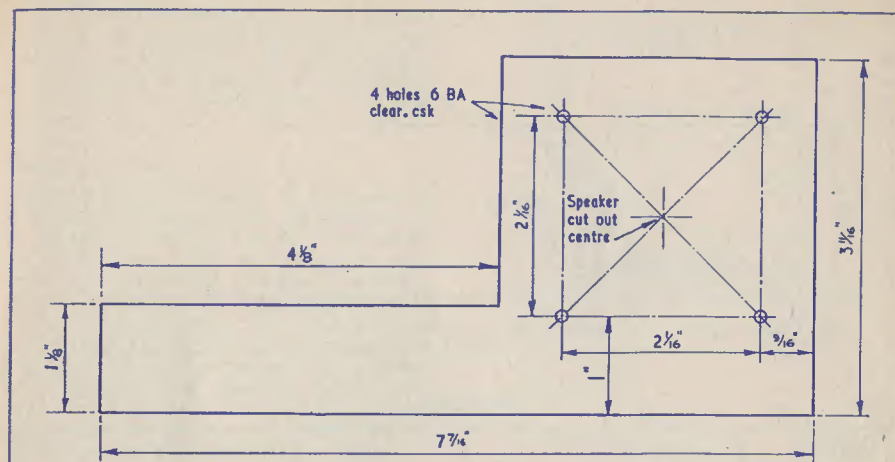


FIG. 22.

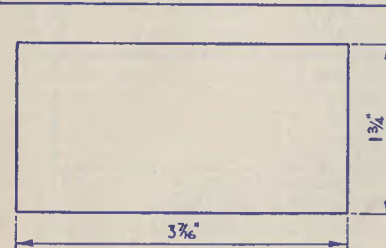


FIG. 23 (a)

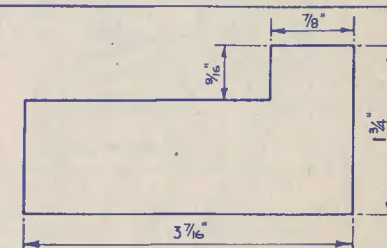


FIG. 23 (b)

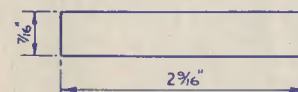


FIG. 24 (a)

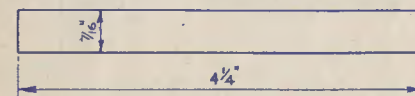


FIG. 24 (b)

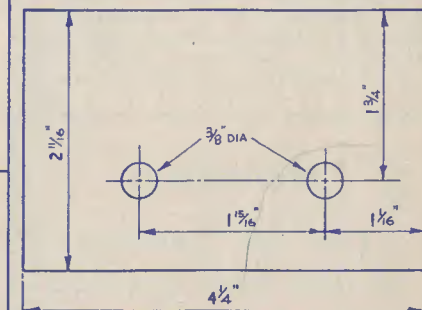


FIG. 25.

Fig. 22. The top section of the Transistorette cabinet. Fig. 23 (a) and (b). The end sections of the cabinet. Fig. 24 (a) and (b). The two pieces which form the sides of the sunken control panel. Fig. 25. The control panel.

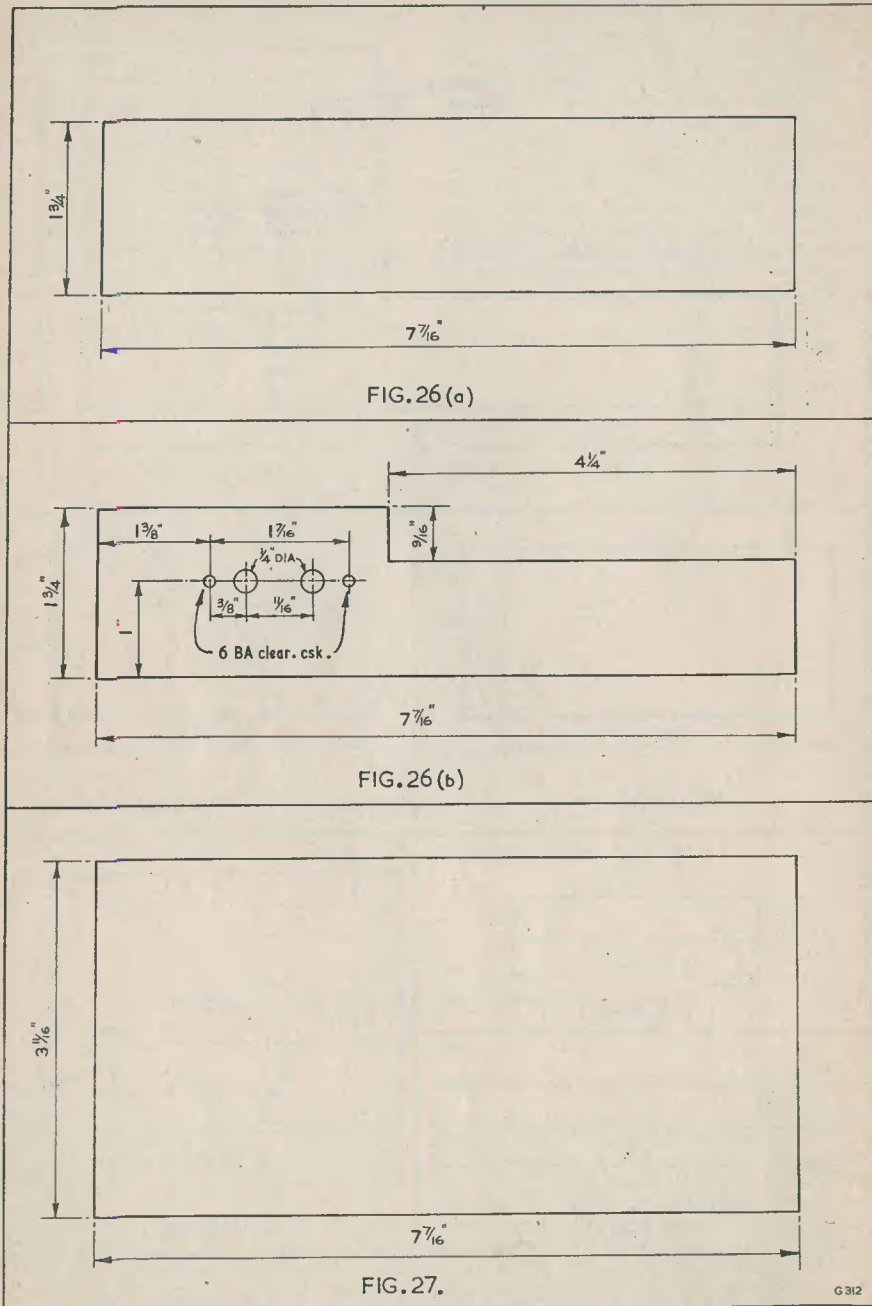


Fig. 26 (a) and (b). The side sections. Fig. 27. The dimensions of the cabinet bottom

fixed by small rectangular pieces of Perspex stuck to the inside of the bottom, these locating with the inside walls of the cabinet. An alternative arrangement would be provided by the use of small hinges, or similar fixtures.

Fitting the Chassis

Before fitting the chassis to the cabinet it is necessary to mount the loudspeaker. It is possible to employ two of its mounting screws to hold a battery housing as well, and a typical example of such a housing is shown in Fig. 28. No fixed dimensions are given in this diagram, since the available tolerances are quite wide and the constructor may wish to take advantage of what materials he may happen to have on hand. Also shown in Fig. 28 is the loudspeaker itself; and this should be fitted so that its tags lie below those of the aerial-earth panel.

The output transformer can be mounted by bolting it to the side panel—that shown in Fig. 26 (a) of the cabinet. In the photographs, this component is shown mounted to a small bracket integral with the chassis. It is felt that the construction of this bracket is more complicated than the simple overall design of the receiver warrants, and that the alternative method of mounting suggested here is preferable. The transformer will occupy the same position as that shown in the photographs, although its axis will now be turned through 90 degrees.

All that remains is to fit the chassis in the cabinet. As was mentioned above, this is done by passing the bushes of the volume control and tuning condenser through the $\frac{3}{8}$ -inch holes of the control panel. To ensure a snug fit, it is advisable to remove the locking nuts and washers from the bushes before passing the latter through the holes. They may then be fitted and tightened down again on the outside of the panel. It is recommended that the appropriate Panel-Sign transfers be fitted to this panel, as these give an extremely neat finish to the whole assembly. For best results, the transfers should be affixed to the front panel and allowed to dry firmly before finally tightening the bush nuts.

Warning

As it is possible that the h.t. battery may be replaced by non-technical persons, it is important to ensure that the battery compartment is adequately marked with the polarity of the appropriate terminals. A dab of red paint could be used on the positive contact spring. An effective warning notice is given in Fig. 29. This notice can be cut out and stuck in a prominent place in the cabinet.

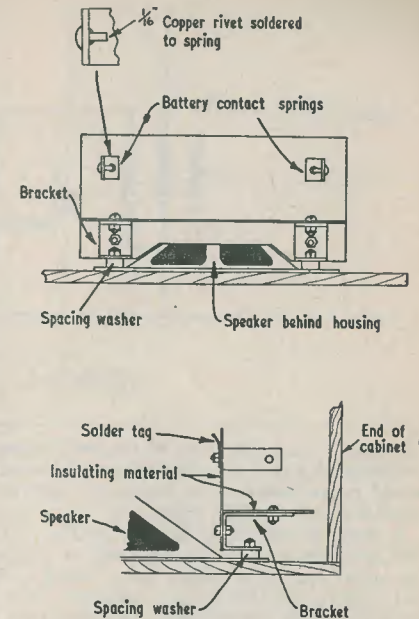


FIG. 28.

Fig. 28. A suggested housing for the h.t. battery

Selectivity

Due to the simple tuning circuit employed, it is possible that sufficient selectivity may not be available in one or two parts of the British Isles where medium-wave interference levels are very high. Although this fact was not considered detrimental to per-

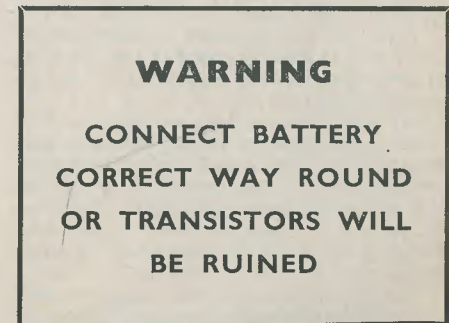


Fig. 29. Warning Label. This label may be cut out and fixed in a prominent place in the cabinet

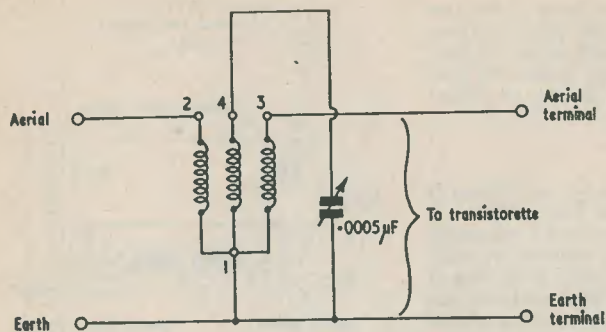


FIG. 30.

G34

Fig. 30. The circuit of a medium wave trap. This should be required only in areas of heavy medium-wave interference

formance during the tests of the prototype, it was decided that a simple wave trap circuit would prove beneficial to those who experienced difficulty in this respect.

A suitable circuit is shown in Fig. 30. This employs a triple-wound coil, in which the aerial energy is passed to a tuned coil and, thence, to the tertiary winding. This tertiary winding then connects to the receiver. A suitable coil for this application is the

Teletron type HAX, and the numbers shown in the diagram apply to the tags of this coil. The tuning condenser shown in Fig. 30 may be a bakelite dielectric model similar to that used in the receiver itself; in which case the external wave trap can be built into a very compact little unit indeed. As was just stated, such a wave trap will only be required for districts which suffer from heavy medium-wave interference.

VHF FEEDER LOSSES

by H. E. SMITH, G6UH

SATISFACTORY RECEPTION OF BAND III stations in fringe areas will only be achieved by making full use of the available signal. The most important thing to remember in connection with weak signal reception is that as much as possible of the signal must be conveyed to the actual aerial input of the receiver.

Those not familiar with operation above 100-Mc/s may be surprised at the following comparisons between Band I and Band III reception conditions.

We will assume a location, say 50 to 60 miles from Alexandra Palace, where the field strength of the signal is approximately 200 M/vM. Standing waves plus feeder loss will reduce this figure to something far less by the time the signal reaches the input to the receiver. This will be due to the following factors:

At 45 Mc/s, 50 ft of good quality coaxial feeder will have an attenuation figure of something like 1.5 db. 1.5 db represents approximately 30% power loss.

Aerial to feeder mismatch will probably introduce a standing wave ratio of at least


2 : 1 which corresponds to a power loss ratio of 1.2 : 1. The final loss is, therefore, something like 36%, or more than one-third of the available signal lost before it reaches the input to the receiver.

There are probably many thousands of Band I installations where this state of affairs exists, but as the sound and picture are considered to be reasonable, nobody seems to worry.

Now supposing we apply the same conditions to Band III. We can assume that something less than half of the Band I signal will be available at the location referred to above. Even if the transmitter were radiating the same effective power as on Band I, the attenuation and "shadow" effect of surrounding buildings and trees will reduce the local field strength to an extent far greater than on Band I.

Using 50 ft of the same good quality coaxial feeder for the Band III aerial, and paying particular attention to the matching at both ends, we are still faced with an overall power loss of at least 65%!

One important fact emerges from the

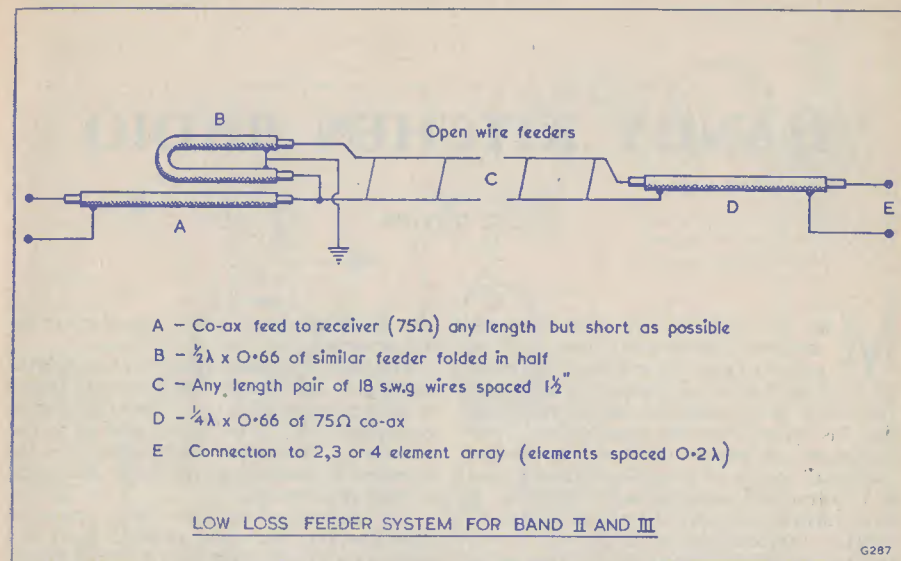

above, and it doesn't take much mental effort to see it. It is that even the best of the coaxial feeders generally available for domestic use are not suitable for efficient fringe area reception of Band III stations. Let us make another interesting comparison with two types of feeder, relating to local interference.

Feeder Loss v. Local Interference

It may not be generally appreciated that the use of low loss feeder results in a higher signal-to-noise ratio. The following example, calculated for Band III operation, will show how this comes about. Assuming that Feeder "A" consists of 100 ft of 300 ohm ribbon and Feeder "B" is 100 ft of high quality semi-air spaced coaxial cable, we find the attenuation figures for 28 Mc/s to be 0.82 db and 1.8 db respectively. (28 Mc/s is chosen for calculation purposes because many forms of local interference peak up between 26 and 32 Mc/s.) This means that interference voltage peaks will be attenuated by 17% on Feeder "A" and 35% on Feeder "B."

For 200 Mc/s operation, the attenuation figures for the two feeders are 4.5 db "A," and 8 db "B," or 64% and 85% respectively. (These figures assume perfect matching to aerial and input to receiver.)

Simple calculations will show that if both the signal and the interfering pulse have an amplitude of 200μ/V, the result is as follows:

Feeder "A" will deliver 72μ/V of signal to the receiver input, plus about 42μ/V of interference pulse.

Feeder "B" will deliver 30μ/V of signal plus about 33μ/V of interference.

As it is usually much easier to obtain a lower standing wave ratio on the higher impedance feeder it can be assumed that the figures given for Feeder "B" are somewhat optimistic.

Spaced Feeder Lines

High impedance air spaced feeders seem to be the logical answer to this loss problem. A pair of 18 s.w.g. tinned copper wires spaced at 1 1/2 in and operating on 200 Mc/s have an attenuation figure of 0.25 db per 100 ft (5% power loss).

Even if the feeder to aerial mismatch is so poor that a standing wave ratio of 4.5 : 1 is introduced, the overall power loss will be no greater than approximately 12%.

With spaced feeders, difficulties arise in the matter of connection to the aerial, bringing them into the house, and connecting into the coaxial socket of the receiver. These difficulties can be overcome by using simple "baluns," made up from lengths of coaxial cable, or by using linear transformers, utilising lengths of lower impedance balanced feeder.

Fig. 1 shows one method of using spaced feeders with a typical Band III installation. The improvement in signal will be well worth the additional trouble taken over the installation.

An identical installation can be constructed for Band II (f.m.) remembering that the

(continued on page 635)

HANDY KITCHEN RADIO

by E. GOVIER

MOST OF US HAVE, AT SOME TIME OR another, wanted that cheap, easy to construct and efficient receiver for use either in the kitchen or, perhaps, a bedroom. The writer is no exception to the rule, and cast his mind over the possibilities. For cheapness the answer obviously lay in the "straight" variety of receivers, while for ease of construction, together with efficiency, a three valve circuit seemed to be the complete answer. Accordingly, a circuit was drawn and the prototype constructed, using parts and component values already to hand. Following several modifications in the light of experience, the circuit shown in Fig. 1 was finally evolved.

Circuit

The circuit consists of a detector stage built around the 6SL7 octal base high-mu double triode, one half of which is utilised as the first audio amplifier stage. The output circuit uses the well-known 6V6G/GT beam tetrode, while the rectifier is a 5Y3GT type valve. These octal base valves are all obtainable at "surplus" prices.

A short "throw out" aerial, some ten to fifteen feet in length, is connected to an Osborn type QR11 coil. Reaction is provided in the normal manner by varying C_1 , the other end of the winding being connected to anode 1 of the 6SL7. C_2 , together with R_1 , is connected to the grid, one end of R_1 being wired directly to the cathode and thence to chassis. Tuning is carried out with C_3 , a 500pF paxolin type variable condenser. Anode 1 is taken to the h.t.+ line via the resistors R_2 and R_3 , the former being of the one watt rating type. C_4 is the decoupling component and this should be of good quality if efficient operation and reaction control are to be achieved.

It will thus be seen that the first half of the 6SL7 acts as a leaky grid detector.

The resulting audio signal is fed, via C_5 , into the grid of the second part of the valve, R_6 being the grid leak. R_5 and C_6 provide the necessary bias, and note should be taken of the polarity of C_6 and the other electrolytic condensers shown in the circuit diagram.

The amplified signal is now passed on to the following stage via C_7 .

The variable potentiometer R_7 controls the audio gain and also the on/off switch shown in the a.c. mains input line. The output stage is conventional, C_9 being included as a tone corrector. The output transformer is of the standard 6V6 matching type easily obtainable at most radio stores.


The full-wave rectifier valve provides adequate h.t. for this receiver, and the smoothing components, an old 10H 60mA choke already to hand, together with the associated condensers C_{10} and C_{11} , ensure that the resultant power is well smoothed.

Little else need be said about the circuit as shown; it can be made up on a $5" \times 7" \times 2\frac{1}{2}"$ chassis in a couple of hours or so. When completed, it may either be enclosed within an existing cabinet or one made for the purpose. The writer did neither of these, but included the whole chassis and speaker in an unused drawer of the kitchen cabinet, a speaker fret being first cut out in the drawer front.

Variations

Several variations may, of course, be made to the circuit as shown, according to the individual preferences of the reader. A tone control could easily be added by removing C_9 , and connecting a 0.1 μ F tubular condenser, of 350V working, from the anode of the 6V6 and thence via a 50k Ω variable to chassis. A further alternative would be the replacement of the smoothing choke by a 10k Ω 5 watt resistor, this being much cheaper than a choke where the latter is not already to hand. A further point to remember is that the 6SL7 may be replaced, without any base alterations, by the 6SN7 double triode. The effect of this replacement is that somewhat less audio gain is available.

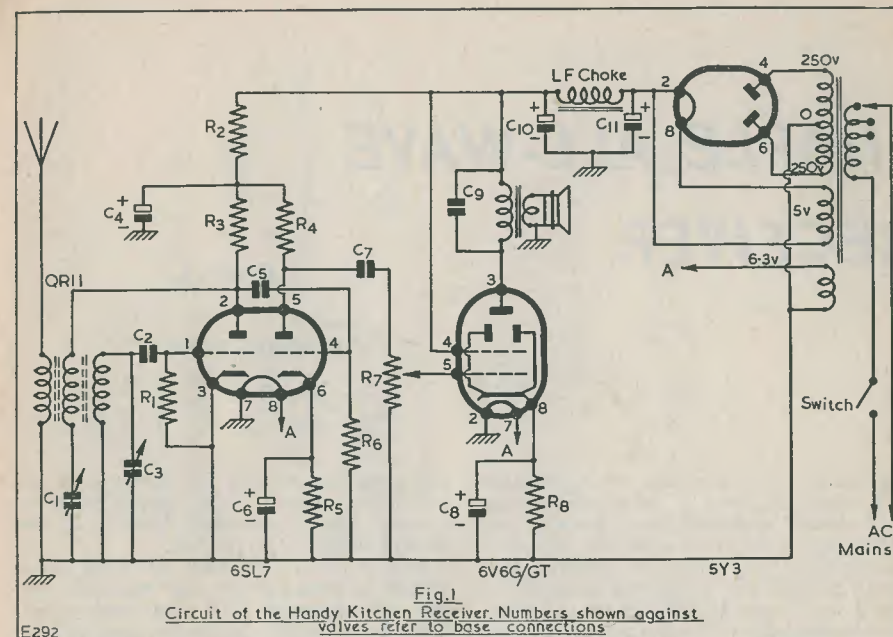A glance at the component list will show that all the values used are standard and all are easily available. Once completed, the receiver will prove well worth the time and trouble taken to construct. Cheap and simple to build, it will provide excellent service to the owner.



COMPONENT LIST

Resistors

R_1	2M Ω $\frac{1}{2}$ watt
R_2	150k Ω 1 watt
R_3	47k Ω $\frac{1}{2}$ watt
R_4	47k Ω $\frac{1}{2}$ watt
R_5	1k Ω $\frac{1}{2}$ watt
R_6	470k Ω $\frac{1}{2}$ watt
R_7	1M Ω pot with switch
R_8	300 Ω $\frac{1}{2}$ watt

Condensers

C_1	500pF variable, mica
C_2	200pF mica
C_3	500pF variable, mica
C_4	8 μ F, 350V wkg., electrolytic
C_5	0.01 μ F, 350V wkg.
C_6	25 μ F, 12V wkg., electrolytic
C_7	0.01 μ F, 350V wkg.
C_8	25 μ F, 25V wkg., electrolytic
C_9	0.002 μ F, mica
C_{10}	16 μ F, 350V wkg., electrolytic
C_{11}	8 μ F, 350V wkg., electrolytic

Valves

V_1	6SL7 (see text)
V_2	6V6G/GT
V_3	5Y3

Coil

Osborn, type QR11

Mains Transformer
Ellison type
MT162

Speaker

5" Rola

Choke

10H, 60mA (see text)

Speaker Transformer

6V6 matching or multi-ratio type

Other items

Chassis (see text), valveholders, nuts and bolts, wire, etc.

V.H.F. FEEDER LOSSES—continued from page 633

electrical lengths of coaxial and balanced feeders are determined by the velocity factor, which is approximately 0.66 for coaxial and 0.85 for 100 ohm balanced and 300 ohm ribbon. A quarter wave section of coaxial

will, therefore, be 0.66 of a quarter wavelength, and the balanced feeder of 100-300 ohm types will need to be cut to 0.85 of a quarter wavelength wherever these are used in "baluns" or matching transformers.

SIMPLE ALL-WAVE RECEIVER

Part I

by JAMES S. KENT

A SIMPLE RECEIVER DESIGNED TO OPERATE efficiently over a fairly wide range always maintains its popularity and adherents. Although the receiver about to be described was designed primarily as a simple standby job, it occurred to the writer that it was in fact an ideal set for the beginner to construct. Following on this thought, it was decided to go one further and to construct a similar receiver for the more advanced, using the modern miniature valves, in a parallel design. Thus, with the present set, offered herewith, an octal based double triode feeding into an octal output tetrode, will be followed in Part 2 with the self-same arrangement but with the difference that two valves of the Noval range will be featured. The same remarks also apply to the power supply unit.

Receiver designs specifically intended for the beginner are, unfortunately, not very plentiful—although several excellent designs have appeared in the past within this magazine. However, as these newcomers are constantly arriving within the hobby, so to speak, it is felt that a further design would most certainly be of advantage to them as a whole—not to mention the new reader picking up the magazine for the very first time!

Circuit Description

With this receiver, the minimum of components has been used consistent with reasonable efficiency. The power supply has been constructed as a separate unit, partly for the reason that it is required for other apparatus at times, and partly for the fact that most beginners prefer to build a power supply as an individual item of equipment.

In the first stage of the receiver, a 6SL7GT high-mu double triode acts as detector and first audio amplifier, the resultant audio

being fed directly into the output stage via a volume control. The output stage is entirely conventional and consists of the 6V6GT output beam tetrode.

Plug-in coils are used as these have several advantages for the beginner over the manufactured coil assembly types. They are available separately, and may be thus purchased one at a time if required; also the use of these coils obviates the need for a switching system with its attendant losses and, to the beginner, its complex wiring. Those used are the miniature Eddystone coils (see component list). Coverage of the complete set, as listed, is from 32 Mc/s to 730 kc/s.

As the above coils have a common earthing point for all three windings, the reaction condenser is inserted between the anode and the "hot" end of the appropriate winding.

A series aerial condenser is incorporated in order to avoid "dead spots" with the reaction control. In the prototype shown herewith, this is mounted on the chassis, but if preferred, this could easily be mounted on the front panel thus allowing instant variation without recourse to screwdriver adjustments for each coil inserted.

The output transformer is of the midget variety enabling this to be mounted under the chassis and on the chassis backdrop.

Circuit

This is shown in Fig. 1, the aerial being fed into the primary winding of the coil via C_1 , the variable condensers C_2 and C_3 being the bandset and bandspread controls respectively. R_1 and C_4 form the grid components of the leaky grid detector. Reaction is obtained by varying the condenser C_5 . As this is in series with the anode it therefore has an r.f. potential across it.

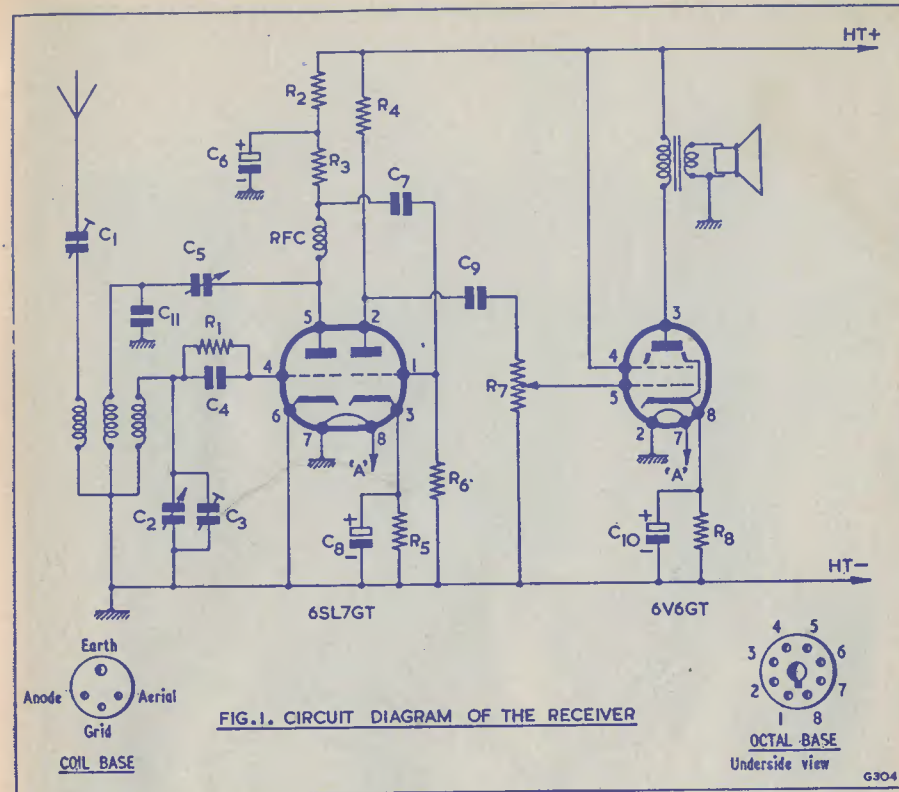


FIG. 1. CIRCUIT DIAGRAM OF THE RECEIVER

This being so, the actual condenser must *NOT* be earthed to the chassis at any point. As mounted in the prototype, two insulating washers and a short length of paxolin tube have been used in securing the component to the front panel—effectively isolating the metal parts from the chassis and panel. The same object may be achieved by cutting out a small square from the panel and bolting into position a slightly larger square of paxolin, through which a hole has been drilled enabling the condenser to be mounted. If adopting this method, however, ensure that the condenser fixing nut does not itself come into contact with the panel or chassis.

The resistors R_2 and R_3 form the anode load components which, together with the associated by-pass condensers C_6 and C_{11} , ensure that smooth reaction is obtained, in association with the other detector circuit components, over the range of the receiver.

The audio output of the detector stage is fed, via C_7 , into the grid of the following triode portion of the 6SL7GT, where R_6 acts as the grid leak component. Cathode bias is supplied via the resistor R_5 and the


electrolytic condenser C_8 . R_4 is the anode load and the output of this first audio amplifying stage is taken, via C_9 , into the volume control R_7 .

The output stage is entirely conventional and one with which the beginner soon becomes conversant, the 6V6GT being a very popular output valve with home constructors. R_8 and C_{10} are the bias components.


Constructional Notes

Providing the circuit as shown in Fig. 1 and the illustrations are studied carefully from time to time as construction advances, no difficulty should be experienced by the beginner. The layout is straightforward and, commencing with the detector portion of the wiring follows thus: 1st audio stage followed by the output stage.

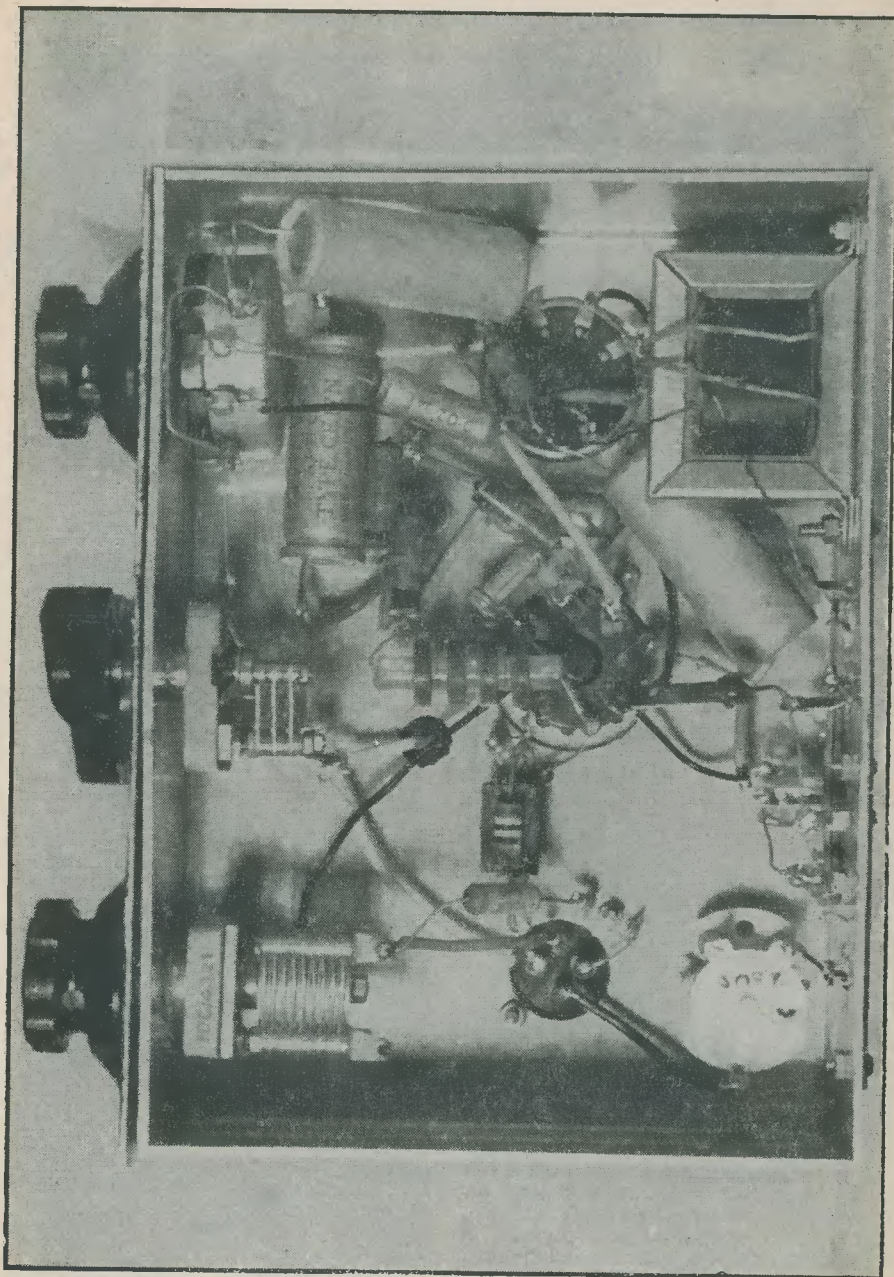All the resistors are $\frac{1}{2}$ watt and the ratings and types of the various condensers are given in the component list. All of the specified parts are currently obtainable on the market—suppliers of the various items used being stated where applicable.



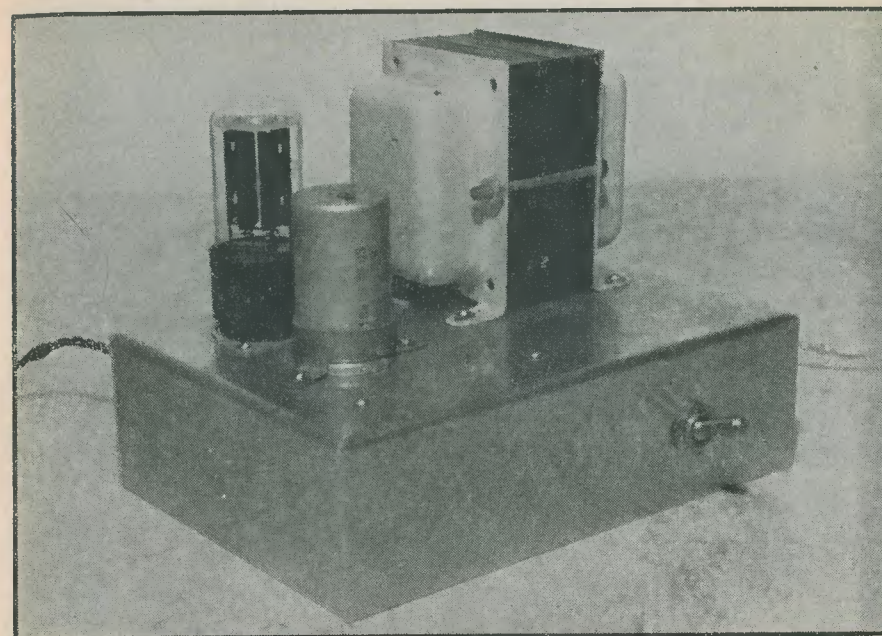Underchassis layout of the original "Simple All-wave Receiver." Most important points are that grid and anode leads should be kept well apart, and should be kept as short as possible



The original power supply unit. If built separately, it is always available for use with other equipment—but there is, of course, no objection to the power pack being built on the same chassis as the receiver, provided that it is sited on the end furthest away from the detector stage. A larger chassis will obviously be required

Drilling details of the front panel, chassis and chassis backdrop are given in Part II of this series and will be featured next month. For the moment, beginners are advised to first obtain the components and also a chassis size 7in by 5in by 2in together with an aluminium panel size 7in by 6in. A slightly larger panel and chassis will, of course, do no harm; one does not necessarily have to conform strictly to either the sizes stated or the drilling details given next month. Provided the panel and chassis are of sufficient size, the remaining point of importance is to ensure that the layout of the components, as shown herewith, are followed reasonably closely.

Fig. 1, in addition to showing the circuit of the receiver, also features two small insets. One of these is the octal valve base as seen from the underside, and this, in turn, refers to the numbers shown on the circuit around each valve. Thus, in the detector stage pin 6 is the cathode and must therefore be wired to an earth tag.

When mounting the actual valveholders, one earth tag should be bolted to each holder, using one of the self-same bolts which secure the valveholder to the chassis.

In this way, each valve has its own earth return.

The speaker is separate from the receiver, a small 5in type being sufficient for the purpose, it being fed from a paxolin strip mounted on the receiver chassis backdrop.

Power Supply

This is shown in Fig. 2. It is generally conceded that the power pack is the item of equipment which frightens the beginner most of all. Having perhaps had some experience of battery supplies with 90 or 120 volts of h.t., the—to the beginner—"high voltages" of mains equipment, in this case 200 volts or so on load, is apt to be somewhat of a problem. This being so, it is proposed to clearly itemise the construction of the power pack.

The chassis size is the same as that for the receiver—5in by 7in by 2in. Provided the same mains transformer and rectifier as specified are used, the following instructions, if carefully carried out, will result in a power supply which will cause no worry at all.

Before commencing, however, a few words about power supplies and the very obvious precautions to be taken AT ALL

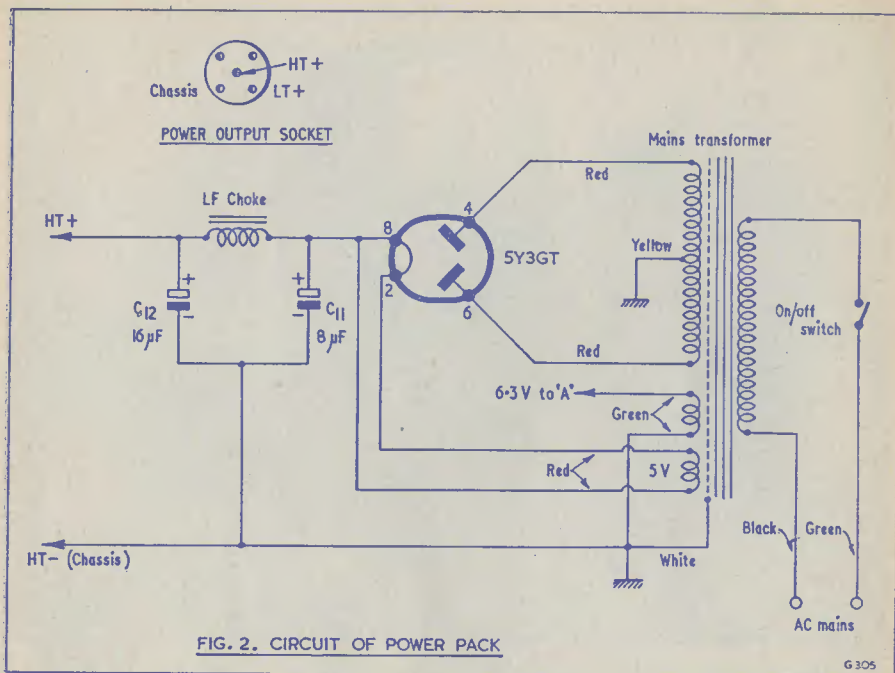


FIG. 2. CIRCUIT OF POWER PACK

TIMES will not come amiss. With the unit completed, and connected to the receiver, NEVER make any adjustment or alterations to the circuit with the power supply either switched on or connected to the mains. If you insist on making any alteration while the set is working, then place one hand behind your back—or better still—put one hand in your pocket.

With the components mounted on the chassis as shown in the photographs, not forgetting the use of rubber grommets for ALL leads going through the chassis deck, commence wiring as follows.

Mains transformer.—White, yellow and one green lead (one of the thick enamel covered ones) should be connected to chassis. In the photo this is shown wired to the earthed tag of the tag strip mounted on the chassis wall. The other thick green lead is connected to pin 3 of the valveholder, and from there a short length of wire is taken to the appropriate tag of the power output socket (see Fig. 2). NOTE: In case you are mystified with the use of pin 3 of the valveholder, this is used solely as a holding tag—no connection is made to the actual valve, by virtue of the fact that the 5Y3GT has no pin 3 at all. The thin red and blue wires should have their open ends taped with insulation tape and then be tucked away under the paxolin strip. Ensure

that the taping is done efficiently, that neither open end is in contact with each other and that no accidental connection is made with the chassis.

The thin black wire should next be soldered to a free tag, i.e. not an earthed one, of the tag strip. The thin green wire should be similarly treated.

A length of twisted mains lead should now be fed through a rubber grommet affixed to the wall at the rear of the chassis. Baring both wire ends, solder one each to either side of the on/off switch. At a point near the tag strip, cut one wire only. Bare both ends of these cut lengths and solder one to the same tag already holding the thin black wire. Solder the other end of the cut length to the tag to which the thin green wire has previously been soldered.

On the other side of the mains transformer there are four red wires. Select the two thick wires (these are enamel covered), solder one to pin 8 and the other to pin 2 of the valveholder. Before attempting to solder, however, ensure that the enamel is removed, otherwise a bad connection will result. One way of removing this enamel is to scrape away the covering with either an old knife or a single-edged razor blade.

The two thin red wires should now be soldered to pins 4 and 6 of the valveholder—one wire to each pin of course.

From either pin 2 or 8, it does not matter which, solder a length of covered wire, the other end of which is secured to the 8µF tag of the smoothing condenser, and from there to the tag of the smoothing choke—it does not matter which tag.

From the other tag of the smoothing choke, solder a length of covered wire to the 16µF tag of the condenser and from there to the power output socket (see Fig. 2).

The power supply is taken from the power pack to the receiver via a short length of 3-way cable. This cable is terminated at each end with a miniature plug arrangement which inserts into an appropriate socket forming part of a paxolin assembly mounted on both the receiver and power pack chassis backdrop.

Having completed the wiring as described, next check that the above instructions have been carried out, check with the circuit diagram, then insert the valve. Connect

to the mains supply socket via a suitable plug and switch on. The valve filaments should glow red, switch off. Do not allow the power pack to run for a long period when not connected to the receiver as this will eventually damage the valve.

Conclusion

With the information given in this issue, together with the circuit diagrams and the illustrations, the beginner, and those requiring a small standby receiver, may go ahead and construct the power pack while at the same time gathering the components for the receiver. Next month, a comparable design using the miniature valves 12AT7, 6BW6 and EZ41 will be featured. The instructions for the dial cursor and the panel fittings will be dealt with in the next issue.

Those then that are attracted to the circuit design may care to adopt next month's offering in preference to the one featured here.

COMPONENT LIST

Resistors

- R₁ 1MΩ ½ watt
- R₂ 10kΩ ½ watt
- R₃ 100kΩ ½ watt
- R₄ 100kΩ ½ watt
- R₅ 1kΩ ½ watt
- R₆ 470kΩ ½ watt
- R₇ 500kΩ Pot
- R₈ 270Ω ½ watt

Valves

- 6SL7GT Brimar
- 6V6GT Brimar

Chassis and Panel

H. L. Smith & Co. Ltd.

Output Transformer

Miniature type—H. L. Smith & Co. Ltd.

Coils

Eddystone types 707/LB, 706Y, 706/R, 706/W and 706/P

Coil Base type 707.

Home Radio or Southern Radio and Electrical Supplies.

Condensers

- C₁* 25pF variable
- C₂ 140pF variable, Eddystone, 586
- C₃* 25pF variable
- C₄ 100pF, mica
- C₅* 75pF, variable
- C₆ 2µF, 350V wkg, TCC type CE17N
- C₇ 0.02µF, 350V wkg, TCC type CP33N
- C₈ 25µF, 25V wkg, electrolytic
- C₉ 0.02µF, 350V wkg, TCC type CP33N
- C₁₀ 25µF, 25V wkg, electrolytic
- C₁₁ 100pF, ceramic

* Available from R.C.S. Products (Radio) Ltd.

RF Choke

The Teletron Co.

Valveholders

McMurdo

Paxolin Strips etc.

H. L. Smith & Co. Ltd.

Power Pack Component List

Chassis

H. L. Smith & Co. Ltd.

Mains Transformer

Ellison type MT162

Tag Strips, Plugs and Sockets etc.

H. L. Smith & Son, Ltd.

LF Choke

10H, 60mA—H. L. Smith & Co. Ltd.

C₁₁ and C₁₂

8×16µF, 350V wkg, electrolytic—H. L. Smith & Co. Ltd.

Valve

5Y3GT Brimar

Using Mains Transformers Having Unconventional Voltage Tappings

by G. W. SHORT, M.A.

Introduction

A MAINS TRANSFORMER IS OFTEN THE most expensive item in a piece of equipment. From time to time, non-standard mains transformers appear on the market at give-away prices. Often, these apparently useless items can, with a little ingenuity, be made to yield quite standard voltages. This article describes how one typical transformer was utilised. The general principles can, however, be applied by constructors to adapt other cheap non-standard transformers to their particular needs.

The transformer used in the power pack described here had normal a.c. mains primary windings, and the following secondary voltages:—

120V	350mA
9V	1A
12V	2A

Probably because none of the above voltages is of direct use for general radio work, it cost only 7s. 6d., although it is a well-constructed component. Nevertheless, without resorting to any drastic measures such as re-winding, it was made to provide the following supplies:—

- H.T.₁ 250V 100mA
- H.T.₂ 250V 50mA
- L.T.₁ 12.6V a.c., 2A (for 12V a.c. mains valves)
- L.T.₂ 0-10V d.c., 10MA. This can be used for bias supplies, transistor collector voltage, etc.

The circuit of the power pack is shown in Fig. 1. The primary is mis-volted by 10 volts, the 230V a.c. mains being connected to the 220V primary tapping. This is a negligible voltage overload, but it has the useful effect of raising the voltage of the 12V secondary to 12.6V, so that it can be used for supplying valve heaters. Valves with 12.6V heaters are supplied direct, while pairs of valves with 6.3V heaters and

similar current ratings can be connected in series across the supply. The h.t. secondary, which now gives 126 volts, supplies two full-wave voltage doubler circuits. Metal rectifiers such as the RM series can be used, or centre-tapped 250V rectifiers.

The exact arrangement of the h.t. supply is a matter of convenience. In the writer's case, two separate supplies were provided so that several pieces of equipment could be operated at the same time. If only one supply were provided, instability might result from stray couplings in the power pack. If, for instance, a radio tuner feeding a high gain audio pre-amplifier, in turn feeding a power amplifier, were all connected to one h.t. source, motor-boating would probably occur. With two h.t. supplies, the feeder and pre-amp can be connected to one and the power amplifier to the other. This greatly reduces the risk of motor-boating.

Low Voltage D.C. Supply

A half-wave metal rectifier was used here. It is not normally considered good practice to employ half-wave rectification in conjunction with transformers not specially rated for it, because d.c. flowing through a transformer winding can cause saturation of the core, and this results in a damaging increase of primary current. However, in the present case only a few milliamperes are drawn. The supply is designed to operate with the positive side earthed, for grid bias and transistor collector voltage supply. There is no reason why it should not be used with earthed negative, however.

Construction

This was quite straightforward, the unit being built on a wooden "bread board." This type of construction is to be recommended where no valves are used, and where, as in the present case, electrolytic condensers are employed in circuits where the negative

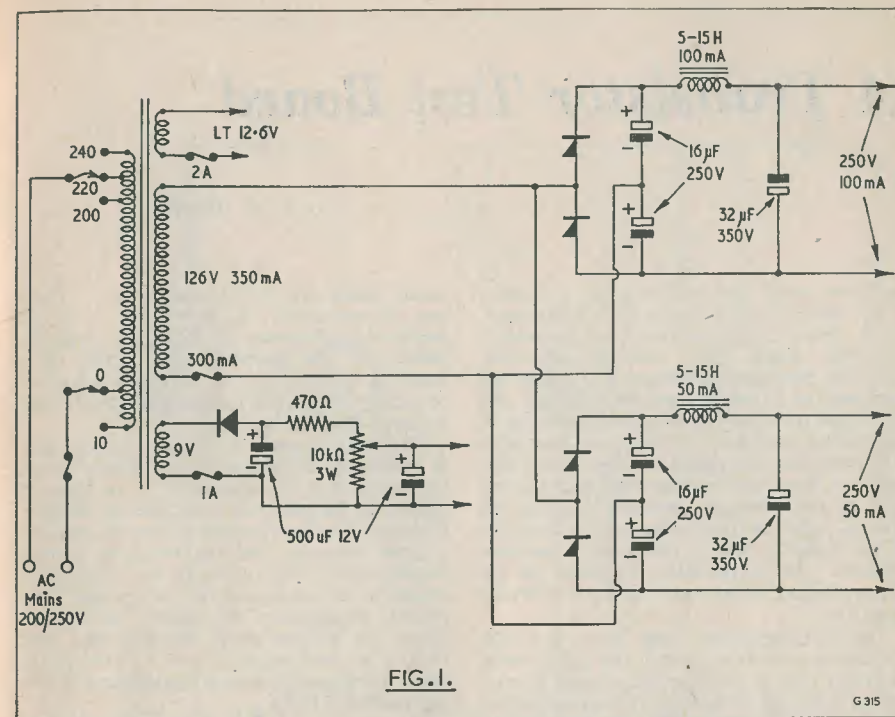


FIG. 1.

Circuit of the writer's power supply using a surplus mains transformer. Several other ways of using the same transformer are possible, and these are discussed in the text

side is not earthy. (If the chassis was a metal one, precautions would have to be taken to insulate the cans of some types of electrolytic from the chassis).

Alternative Circuits

Taking the same transformer as an example, several other ways of using it are possible:

- Battery Eliminators**
H.T. Supply. A half-wave rectifier fed from the 120V winding will yield enough voltage for any normal battery set (i.e. 70-125V). R.C. smoothing can be used, the series resistor being chosen to drop the h.t. voltage to the required value.
L.T. Supply. 7.5V, from the 9V or 12V winding, with either half-wave or bridge rectifier, and R.C. smoothing. 1.5V or 2V, by connecting the 12V and 9V windings in series, opposing one another. This gives 3V for a small bridge rectifier. Excess voltage can be dropped in the smoothing circuit.
- Step-down Mains Transformer**
 The 120V winding could be used to

supply American-type 115V a.c.-d.c. receivers. Power available is 42W.

3. Unusual L.T. Voltages

The 9V and 12V tappings in series give 21V. This voltage is correct for certain a.c./d.c. valves such as the UF42 high slope h.f. pentode. A current of 1A is available, enough for 10 such valves.

Alternatively, by feeding the 230V mains supply into the 250V primary windings, 19V l.t. is available. This would be suitable for an amplifier having, say, two PL33 output valves (heaters 19V, 0.3A). Three amplifying valves having heaters of 6.3V, 0.3A, could be connected in series across the l.t. ($3 \times 6.3V = 18.9V$).

It is hoped that enough has been said to encourage constructors to keep a sharp lookout for genuine bargains in the way of unusual mains transformers. Before making a purchase, however, it is advisable to do a little rapid mental arithmetic to make sure that the item in question is really useful and not just another white elephant.

A Transistor Test Board

by V. T. ROLFE

Now that transistors are becoming increasingly popular with home constructors, the need for some method of checking them has become apparent. Probably the simplest method is to regard the transistor as a double germanium diode, and check the forward and reverse resistances of the emitter-to-base and collector-to-base with a low voltage ohmmeter. When doing this test, it is important to remember that the red lead of the meter is normally *negative* on "ohms," and that the low resistance direction of the collector-base circuit is with the base negative. (It is normally operated in the high-resistance connection, with the collector negative.)

The test described only gives a rough indication of whether or not the transistor is working, and is useful only when it is suspected that the transistor is non-operative, either due to overloading, or overheating when soldering into circuit. With transistor circuits still in the experimental stage, it is not unknown for a constructor to build up a piece of equipment, only to find it doesn't work. In such cases it may be desirable to check the transistor characteristics. Apart from any circuit faults, non-operation may be due either to a faulty transistor, a low current gain, or high leakage current.

The test-board to be described will reveal any of these shortcomings. It is primarily intended for checking junction transistors such as the Mullard OC70 and OC71, although it could be used for other types with certain modifications, and probably with point contact types as well providing suitable batteries were employed.

The transistor is tested in the grounded emitter connection, since this is the arrangement which gives the greatest current gain, and is most likely to be encountered in practice. First of all the leakage current (I_{co}) is to be checked. This is the current which flows in the collector circuit when there is no input to the base. The basic circuit for checking this is shown in Fig. 1. The lower the value of I_{co} , the better the transistor, in some applications. Average values for the OC70 and OC71 are $110\mu A$ and $150\mu A$ respectively, whereas the maxi-

imum values are $225\mu A$ and $325\mu A$. These are measured at $V_c = -4.5V$, with an ambient temperature of $25^\circ C$. In practice, owing to the pentode like curves of a junction transistor, I_{co} is independent of collector voltage, but increases markedly with a rise in temperature.

The method used to measure current gain is to supply a certain base current to the transistor and by means of a backing-off circuit to balance out the collector current flowing. The base current is then changed by a given amount, and the resultant current measured by the meter is the change in collector current caused by this change. The circuit arrangement is shown in Fig. 2. Since the voltage drop between base and emitter is very small (approx. $100mV$), the resistor required to give a base current I_b can be calculated from $R = \frac{V}{I_b}$. Thus with a

1.5V battery, and a base current of $10\mu A$, a resistor of $150k\Omega$ is required. The resultant collector current is balanced out by adjustment of R_3 . Changing the value of the base bias resistor will change the base current. A resistor of $25k\Omega$ will give a base current of $60\mu A$, an increase of $50\mu A$.

The current gain a' is given by

$$\frac{\text{Meter reading (in mA)}}{50} \times 10^3 = 20 \times \text{Meter reading.}$$

In the practical circuit, the meter is shunted in this position to give a full scale deflection of $5mA$, and this corresponds to a current gain of 100. Thus the meter scale can be directly calibrated. The value of the shunting resistor R_4 will depend on the meter resistance, and will be given by $R_4 = 0.25R_m$.

The limits of current gain to be expected with the two transistors mentioned are 20 to 40 for the OC70, and 30 to 80 for the OC71.

Practical Details

The full circuit is given in Fig. 3. A switch and pilot lamp are incorporated to indicate when the unit is on, as it is not desirable to connect a transistor to the test terminals with the supplies already connected. A three-pole three-way switch is required for the main

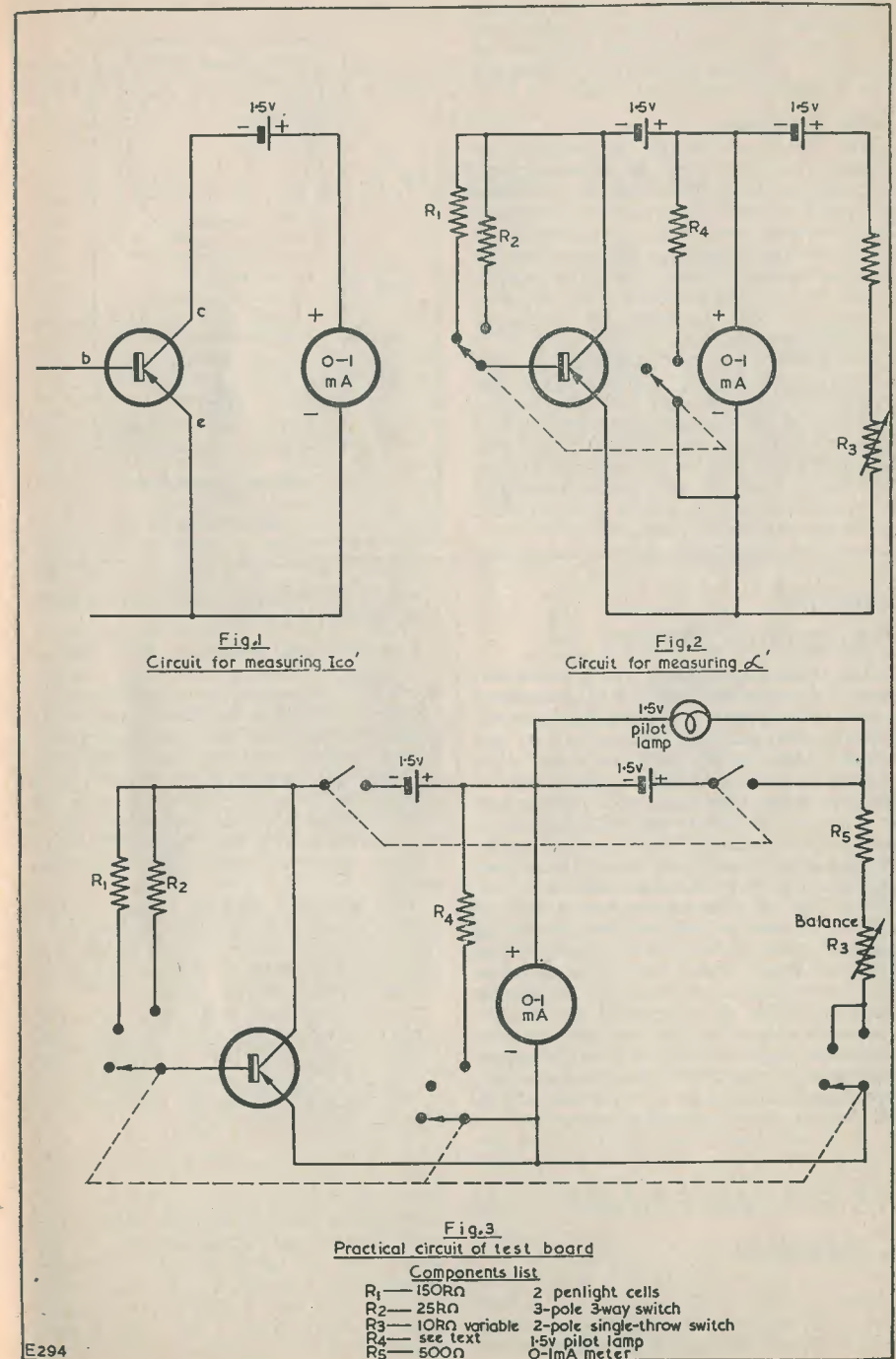


Fig. 3
Practical circuit of test board


- Components list
- R_1 —150 Ω 2 penlight cells
 - R_2 —25k Ω 3-pole 3-way switch
 - R_3 —10k Ω variable 2-pole single-throw switch
 - R_4 —see text 1.5V pilot lamp
 - R_5 —500 Ω 0-1mA meter

selector; this should be a good quality component with low contact resistance. Small pen-light cells can be used for the batteries. A typical panel layout is shown in Fig. 4, although this is not critical.

Safety Precautions

The test-board should be switched off before a transistor is either connected to or disconnected from the terminals. It is also advisable to check that the connections have been correctly made before switching on, as a reversal of polarity, particularly in the collector circuit, may permanently damage the transistor. For this reason it is important to ensure that the batteries are connected correctly when building the unit.

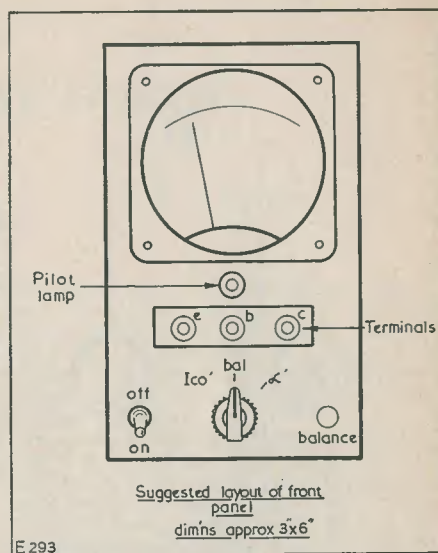Transistors may also be damaged by surge currents, such as may occur from the discharge of a condenser, or over-heating. Although these two points are not likely to arise in connection with this test-board, they are mentioned here to remind constructors that care is essential when using transistors. A heat shunt should always be used when soldering them into circuit.



Mullard Educational Service

"The White Paper (Cmd. 9703), which was issued in connection with the Government's recent announcement of plans for increased facilities for technical education, is well worth careful study, not only by those responsible for higher technological training, but also by head teachers and science masters in grammar, secondary technical and secondary modern schools, for whom the section (paragraphs 13 to 22) headed "The School Background" is of especial interest.

"The Mullard Educational Service will do all in its power to assist schools in carrying out the policy outlined in these paragraphs. "In this connection, it has occurred to us that while much of the material we already make available is acceptable for science specialists in grammar schools, we may have somewhat neglected the needs of the secondary modern school. We therefore cordially invite suggestions as to how we may help to fill the gap if, indeed, such a gap exists."

A NEW FILMSTRIP FOR TELEVISION SERVICING CLASSES

The Mullard Filmstrip No. E60 on "Servicing Projection Television" is now available. It covers the principles of the Mullard projection television system and gives comprehensive information concerning the maintenance and servicing of the optical unit and such features of the circuitry as are peculiar to projection television. The filmstrip has been prepared particularly for use in connection with the City and Guilds of London diploma course in television servicing.

Very complete teaching notes have been prepared and contain reproductions of all the illustrations in the filmstrip. These notes will also be available in bulk for distribution to the members of the class.

The filmstrip, with one copy of the teaching notes, can be obtained from Unicorn Head Visual Aids Ltd., 184 Aldersgate Street, London, E.C.1, price 12s. 6d. Further copies of the booklet of notes are available at the nominal price of 6d. each.

R.S.G.B. V.H.F./U.H.F. Convention

The R.S.G.B. and the London U.H.F. Group are holding a one-day convention for V.H.F./U.H.F. enthusiasts at the Bonnington

Hotel, Southampton Way, London, W.C.1, on Saturday, 26th May, from 10 a.m. to 11 p.m. Tickets and full information are available from F. G. Lambeth, G2AIW, 21 Bridge Way, Whitton, Twickenham, Middlesex, or from the R.S.G.B. Headquarters, N.w Ruskin House, Little Russell Street, London, W.C.1, telephone Holborn 7373,

RIGHT—From the Start

PART 5. LF AMPLIFICATION

by A. P. BLACKBURN

WE SAW LAST MONTH THAT THE VALVE could be used as an amplifier of electrical disturbances. Although we only spoke of one-valve amplifiers, we did mention that requirements do exist where a greater number of valve stages are necessary.

In these cases we are faced with the problem of coupling the stages together, and we shall now consider how this may be done. Many methods have been used in audio amplifiers, but most of them have been discarded in favour of the modern practice of "resistance capacity" coupling. We shall, therefore, concentrate on this type but a brief glance at some of the other methods would be useful, and can be saved for later on.

R.C. Coupling

At first sight, one may wonder what all the fuss is about. It seems simple enough; if the anode is the output of the valve and the grid is the input, surely the anode of valve No. 1 merely has to be connected to the grid of valve No. 2? True, this sounds perfectly logical, but take a look at Fig. 1.

Now the anode voltage of V_1 is, say, +100 volts, but the correct grid bias voltage for V_2 is -2V. Clearly then, we cannot connect points A and B together, because the grid (point B) would become positive with respect to its cathode and excessive grid current would flow and overheat the grid.

The voltages at A and B are both d.c. voltages; they are supplied by h.t. and grid bias batteries. Now, if we apply a signal to the grid of V_1 , an enlarged or amplified version of this signal will appear at the anode of the valve. You will remember, however, that this signal is necessarily of an alternating character, as we pointed out in a previous article. At the anode of V_1 , then, we have an alternating voltage superimposed on a d.c. voltage. So what we want is a component that will pass the a.c. voltage to the grid of V_2 , but will *not* pass the d.c. Fortunately, someone has already thought about this, and such a component is readily available: the capacitor. Incidentally, the

capacitor is often called a "condenser," but the former term is becoming more common nowadays.

The circuit of Fig. 1 may be connected as shown in Fig. 2. Any number of stages, may be now "cascaded" in this way. This is the most common way of coupling audio stages together: by "resistance capacity" coupling.

Transformer Coupling

Another type of component which will pass a.c. but not d.c. is the transformer. Fig. 3 shows one method of connecting a transformer between two valve stages. Very briefly, the current in V_1 flows through the primary winding of the transformer. This current sets up a magnetic field which interacts with the secondary and induces a voltage into it, which is applied to the grid of V_2 as shown. The important thing is that a d.c. current in the primary produces no voltage across the secondary, but an alternating current in the primary does produce a secondary voltage.

One advantage of the transformer is that more volts may be obtained at the secondary than are applied at the primary. If, for example, there are five times as many turns of wire on the secondary as there are on the primary, then 5 volts will appear across the secondary for every one applied to the primary.

This means that a stage of valve amplification might be saved by using a transformer instead of R.C. coupling.

Another way of connecting a transformer is shown in Fig. 4. This has the advantage that the standing current in the valve does not flow through the transformer as it is blocked off by the capacitor. The a.c. or signal will, however, still be fed to the transformer via the coupling capacitor.

Choke Capacity

A method of coupling rarely used nowadays, but still worthy of mention, is shown in Fig. 5. An iron cored choke takes the place of the usual anode load resistor. The advantage is that a lower h.t. voltage may

be used because the choke has a low d.c. resistance and few volts are dropped across it by the flow of standing anode current.

If the choke has a high inductance, say 20 henrys, or so, it will have a high reactance down to relatively low frequencies, and the gain of the stage could be as high as with a normal resistor. The capacitor C couples the anode to the next grid in the same manner as R.C. coupling.

Advantages

The advantages and otherwise of the methods of coupling illustrated are as follows:

1. R.C. coupling provides a system where the gain of the whole amplifier is constant over the widest band of frequencies. That is, the distortion is low.

2. Transformer coupling does not give such low distortion as R.C. coupling unless the transformer is elaborate, bulky and expensive. It does have the advantage of voltage "gain" from primary to secondary if required.

3. Choke coupling does not give low

distortion either. If the distortion can be tolerated, the efficiency of the stage may be higher than for R.C. coupling.

So much for the moment on the matter of interstage couplings. However, later we will return to the R.C. method and examine its "frequency response"; that is, whether all frequencies are treated as equals in that circuit.

Grid Bias

In all the circuits in this article so far, this grid bias has been indicated by a vague arrow marked "G.B." This, of course, indicates that a battery is connected there. Grid bias batteries have been in use for years, but most modern designs make use of other ways of obtaining the operating bias for the valves.

Fig. 6 shows how an ordinary grid bias battery might be connected to an amplifier. The positive end of the battery is connected to earth and the grids are connected to the appropriate negative voltages. In early battery-driven receivers, this system was widely used, but in some later types

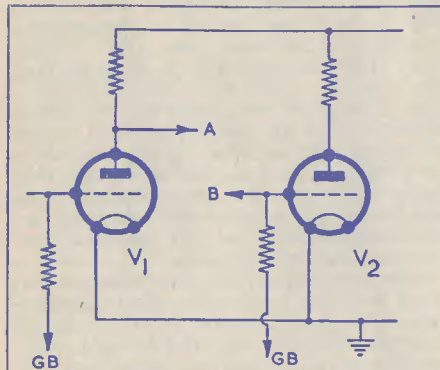


FIG. 1.

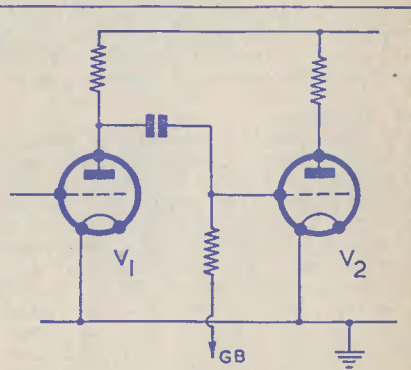


FIG. 2.

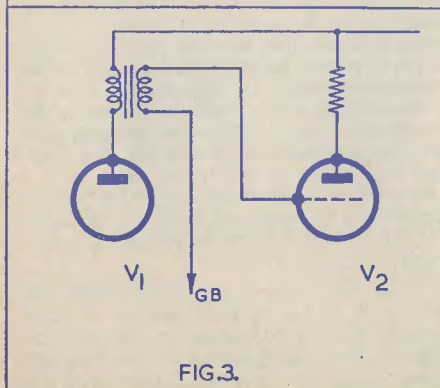


FIG. 3.

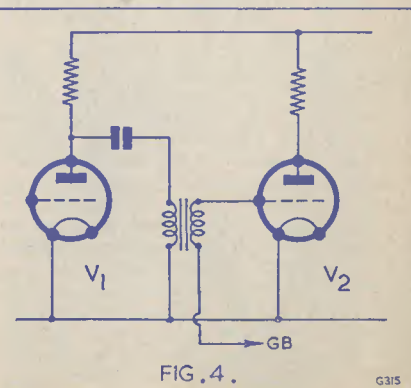


FIG. 4.

G315

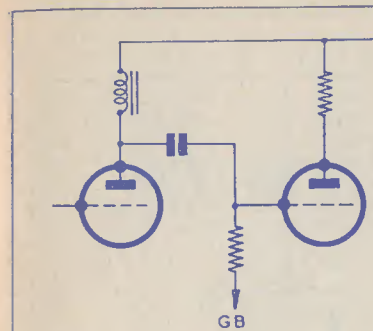


FIG. 5.

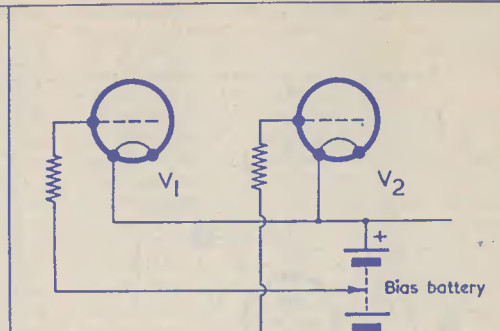


FIG. 6.

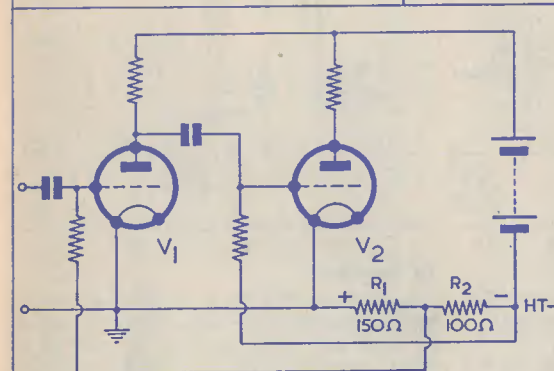


FIG. 7.

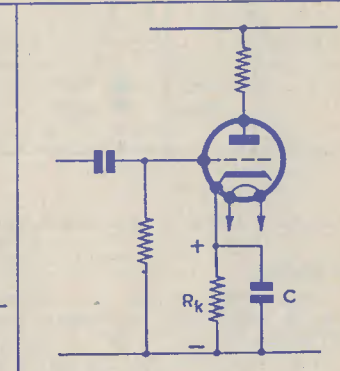


FIG. 8.

G316

an "auto bias" circuit appeared. The total valve h.t. current is caused to flow through a series of resistors as shown in Fig. 7. This means that the filaments are *positive* with respect to h.t.—, due to the valve current producing a voltage across R_1 and R_2 . The grids can now be connected to the points shown which are *negative* with respect to the filaments.

Say, for example, that the total valve current were 20mA and V_2 required a grid bias of 5 volts. Then the total resistance (R_1+R_2) would be by Ohms Law:

$$R = \frac{E}{I} = \frac{5}{0.02} = 250\Omega;$$

but if V_1 only required a bias of 3 volts, a resistance of

$$R = \frac{3}{0.02} = 150\Omega$$

would be required.

Therefore R_1 would be 150 Ω and R_2 100 Ω , thus making the total of 250 Ω for

the bias of V_2 . The arrival of indirectly heated valves produced another "automatic" biasing system. First, however, it should be explained that the indirectly heated valve is so called because the surface emitting the electrons is a tubular cathode placed around the filament. This enables an a.c. voltage to be used for the filament, as the cathode is electrically insulated from the filament. If a.c. were applied to the filament of a directly heated valve, some of the a.c. would be superimposed on the signal, resulting in an objectionable hum.

The method of automatic bias mostly used with indirectly heated valves to-day is shown in Fig. 8. The principle of operation is rather similar to that of Fig. 7. Here, however, only the current in individual valves is used to produce the bias voltage. The current flowing in R_K produces a voltage which is positive at the cathode. The grid, which is returned via its grid lead to the other end of R_K , is therefore negative with respect to the cathode.

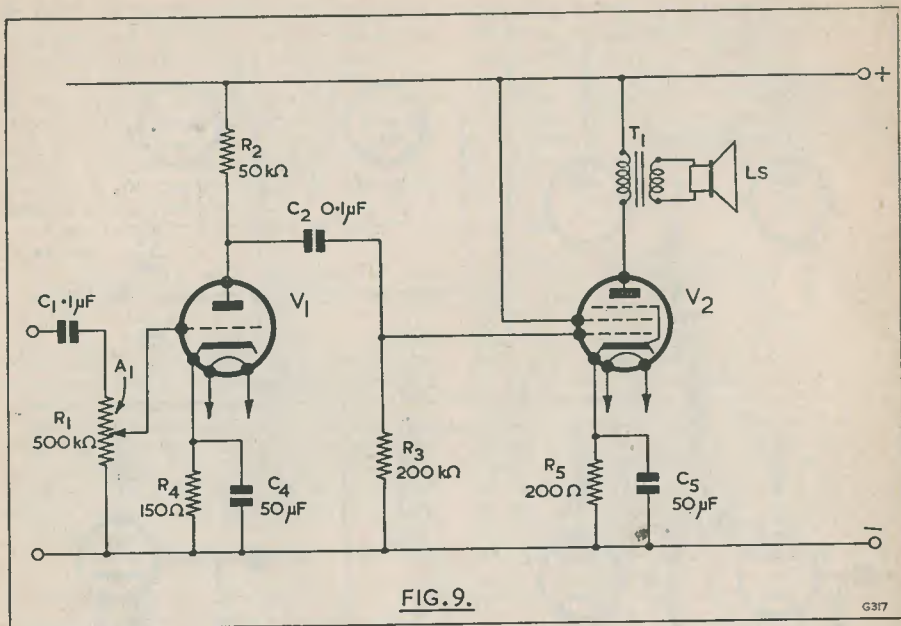


FIG. 9.

Decoupling

There still remains one component in Fig. 8 which has not been mentioned—the capacitor, C.

If we recall that the current in the valve varies with the applied signal, then the bias voltage will vary also. For example, if the grid signal momentarily became more positive, the current in the valve would increase. The voltage drop across R_K would therefore increase also, thus increasing the bias on the valve, i.e. making the grid more negative and decreasing the current in the valve. The result is a loss of gain in the stage because the change in current in the valve, and therefore the output voltage, are partially cancelled by the changing bias voltage.

The remedy is to “bypass” the cathode resistor with a capacitor, as shown in Fig. 8. If we remember that the reactance of a capacitor decreases with increasing frequency, a large value of C in the figure will effectively short out the cathode resistor, but only to a.c. As no d.c. flows in a capacitor, placing C across the cathode resistor will have no effect upon the voltage developed across it, but any rapid changes of voltage, such as those caused by a signal, will not occur because the capacitor will bypass them to earth.

There are many other uses for bypassing components as we shall see. The technique is often called “decoupling.”

An Amplifier

As we are now in a position to couple stages together and derive bias for them, the next step is to see how all this looks when combined in a simple amplifier. Fig. 9 shows a low power output amplifier which might find typical application as a gramophone amplifier.

The R.C. coupling circuit and biasing arrangements are exactly as already described, but there are one or two features not touched upon so far.

The first is R_1 , the volume control. The action is simple enough. The signal is applied across the two ends of the potentiometer R_1 and the position of the “wiper” connected to the grid of V_1 fixes the amount of resistance between the grid and earth. Now, the signal will cause a current to flow in R_1 so the signal reaching the grid will be the current multiplied by the resistance between the wiper and earth. When the wiper is at position A_1 all the signal will be fed to the grid. As the wiper is moved toward earth, less and less signal will be transferred.

The “output” stage V_2 is a pentode. The pentode is a higher gain valve than the triode, but the distortion it introduces is a little higher than the triode.

In the anode of V_2 a transformer is used to couple the valve to the loudspeaker. There is very little choice about this. In moving coil loudspeakers the impedance

of the coil is of the order of 2 to 15 ohms. This is so because it is necessary to have as little wire on the coil as possible in order that it may be light enough to move easily.

Now every valve has a recommended “load” to work into for maximum power output. It may have values anywhere from 2,000Ω to 20,000Ω or higher, dependent upon type. If the speech coil of the speaker were connected direct to the anode of the valve, very low power output would result. It is a property of the transformer that it can “match” one impedance to another. Therefore the transformer is connected as shown. Unfortunately, the transformer is one of the weakest parts of amplifier circuits, unless they are very well designed. Their weakness is the distortion they produce.

Voltage and Power

The two stages in Fig. 9, although providing gain, have in one respect different roles to play. V_1 is purely a voltage ampli-

fier, taking the input voltage and amplifying it as we have seen earlier. V_2 , however, has to produce power into the loudspeaker. For this reason the output stage is often called the power amplifier.

The output of amplifiers is usually specified in watts. This forms a measure of the loudness of the sound produced. For ordinary domestic purposes, the minimum required is about 1 watt, but larger powers are usually provided, up to 10 watts in some cases. In the interests of quality of reproduction it is advisable to have a little in hand; that is to say, if the amplifier is to produce 3 watts for comfortable listening, a 5 watt amplifier is required.

This article, of course, leaves a lot still unsaid about amplifiers. What would happen, for example, if C_3 in Fig. 9 were changed to 0.01μF, and why has 200kΩ been chosen for R_3 ? But these questions bring us closer to the question of the design, rather than the mere operation of the circuit.

Can Anyone Help?

Requests for information are inserted in this section free of charge; subject to space being available

L. J. POYNER, 7 Love Lane, Weymouth, Dorset, wishes to buy or borrow the circuit of the American G.E. radio GE L-643, range 540 kc/s to 1720 kc/s.

R. MULLINS, 72 St. Mary's Road, Tonbridge, Kent, requires manufacturer's circuit and details of Murphy V114 9in t.v. receiver (1947?) and is willing to pay for information.

S. C. ROBERTS, 24 Sutherland Avenue, Welling, Kent, wants the circuit or any information on the RT34/APS.13, 430 Mc/s transmitter/receiver, and is willing to purchase or borrow.

D. KENNEDY, 33 Greystoke House, Peckham Park Road, London, S.E.15, wishes to buy or borrow the circuit and alignment details of the Ferguson model 204XL receiver.

J. BALDWIN, The Dingle, Habberley Road, Bewdley, Worcs, requires the circuit and information on the v.h.f. receiver type R1392A; any expense will be gladly refunded.

J. ALLEN, 7 Chaucer House, Tabard Gardens, London, S.E.1, would like to obtain information on the v.h.f. transceiver X78A. It is spot tuned and only the receiver information is required.

B. PAGE, 7 Queen's Gardens, Eaton Socon, Hunts, would gladly pay any expenses for manual, circuit or data on the CR100 receiver and also the Siera 3-waveband receiver type SA1010U—valve line-up believed to be UY42, UL41, UBC41, UF41 and UCH42.

N. V. DINSDALE, Crayke, York, would be grateful for information on the ex-A.M. 1448 receiver, especially the circuit. Has any reader succeeded in adapting this set for higher frequencies?

R. REYNOLDS, G3IDW, 136 Beech Avenue, Swindon, Wilts, requires information in respect of a pre-war RME70 receiver. Circuit diagram or manual, buy or loan—your price.

P. DALY, 12 Stella Avenue, Glasnevin, Dublin, would like to buy or borrow the manual of the Hallicrafters Sky Challenger SX18 receiver. Any information on this set would be much appreciated.

D. CLOSS, 41 Culverden Road, London, S.W.12, urgently needs a replacement dial, reference number 70,307 for a 5 valve Pye receiver, and is willing to pay for same.

B. PHILLIPS, 24 Ombersley Road, Bedford, Beds, wishes to buy or borrow the handbook for the Eddystone 358X receiver.

C. W. FALKNER, “Thames Mead,” Abbey Drive, Laleham-on-Thames, requires details and operation data for the receiver type 78, A.M. reference No. 10D/1307.

W. EVANS, 109 Tansley Road, Kingstanding, Birmingham, wishes to tender his sincerest thanks to all those readers who kindly offered to supply him with back numbers of the magazine. The response to his appeal was enormous, and it will take some time to reply to each one individually.

M. WRIGHT, 54 New Hall Lane, Bolton, Lancs, has just purchased an indicator unit type 6L, reference number 10QB/299 and wishes to convert to a t.v. receiver. Any information on this conversion would be appreciated; alternatively, he is willing to pay for conversion work.

B. HAYES, G3JBU, 7 Western Terrace, Northampton, would like some information on fitting a noise limiter and “S” meter, together with any other improvements, to the Marconi CR100 receiver. He would also like to thank all those readers who replied to his previous appeal for information on the German RL12P35 valve. Having found it impossible to reply to all who wrote, owing to the very large number of replies received, he hopes that this short acknowledgment will suffice.

Radio Miscellany

ON A RECENT SUNDAY MORNING I HAD occasion to pass the Crystal Palace T.V. site and was very surprised at the number of people there sightseeing. More surprisingly they seemed to stop and stare for a long time although there is nothing much to see. The main aerial tower, which is to be 640 ft when complete, will not be ready for about another 15 months. It will, of course, also carry the I.T.A. aeri-als. Close by stands the 250 ft temporary mast (B.B.C.) at present in use; the I.T.A. mast being nearly a mile away. Both look puny affairs compared to the uncompleted tower. From the road nothing much else is visible as the buildings have been sunk under the terrace to leave the ground available for public use.

corresponding reduction in reception strength. Viewers will be warned by pre-recorded apologies which can be radiated at the touch of a switch!

Finishing Touches

A month or two ago I wrote on paint spraying. Since then I have been impressed by the interest evinced by many readers on this subject. At first I thought the topic would be of close interest only to transmitting amateurs who use large metal areas in their racks, etc., but I am beginning to think that almost every reader has something enclosed in metal work, chiefly instrument cases and test gear. Quite a lot of them have something to say on the subject. The vast majority used the cheap spraying heads, now

CENTRE TAP

talks about

T.V. AERIALS
PAINT SPRAYING
THE BEAUFORT SCALE

An absurd idea suddenly came to me. Suppose an enterprising spiv had been around the Alexandra Palace area buying up their superfluous attenuators, he would probably find a good market disposing of them half-price to the South Londoners now finding themselves swamped with the increased power right on their doorstep. Even those they might have left over will find a brisk sale next year when the permanent tower is finished and the maximum power, 200 kilowatts, brought into use. Why wasn't I born a business-man?

One innovation at Crystal Palace is that both the vision and sound transmitters are in duplicate, working simultaneously in parallel. Thus the continuity of the programme can be preserved in case of break-down although there will naturally be a

widely marketed, in conjunction with a hand bulb or foot pump, and the results obtained vary considerably. While many managed to make a good job of it at the first effort, a greater number seem to have met with varying degrees of disappointment. So much so that I am approaching an expert with a summary of their difficulties, and hope to find space in this column next month to pass on any advice he has to offer.

One thing rather pleased me. Among those readers who prefer external crackle finishes such as Panl, several mentioned that they have sprayed the insides of their cases with cellulose enamels. It is pleasing to know that even in these days of mass production, there is still pride in good workmanship, and a feeling that the inside should look as good as the outside.

Ill Winds

For several months now the B.B.C. have, in the weather reports and forecasts, used the Beaufort Scale to describe wind forces. Yet it is astonishing to find how few people are familiar with this scale. In fact the index numbers seem to be completely meaningless to the vast majority of people. My own interest in wind was greatly heightened when my very first v.h.f. aerial took off in a gale and landed in the garden of an already hostile neighbour. Incidentally, when re-erected, I made provision to lower it whenever gales were threatened—a precaution which, strangely enough, is still far from usual. Many nervous people are alarmed at the possibility of lightning striking the aerial, yet the danger of it sustaining damage and consequently doing further damage to person or property when it, or one of the elements, comes down, is many hundreds of times greater.

In my school days, we had no electric mains within some hundreds of yards, and my first interest in the wind was to harness it for the generation of electrical power. It would save hauling accumulators for re-charging and the prospect of getting something for nothing strongly appealed to the faint streak of Scot in me. I also built up a simple anemometer of the Robinson type. It consisted of four metal cups mounted on cross-bars geared to an indicator which moved across a scale relating the number of revolutions to m.p.h. There is another type,

the Dines, in which a recorder floating on water is used.

The Beaufort Scale, of course, has long been used for the more detailed type of weather reporting. It was devised by Sir Francis Beaufort in 1805 and the numbers 0 to 12 are used to indicate wind velocities in m.p.h.

During the power cuts of 1946-47 I wrote an article for *Short Wave News* on home-made power by wind-driven generators. Quite a number of amateurs have used them, especially when ex-W.D. generators of various patterns were cheaply available.

The more weather-conscious reader will have noted that wind forces of from 3 to 8 are common in the British Isles, so with reasonably sized storage cells, power for many uses could be available during the rare periods when wind pressures fall below 3. Writing, at that time, of the Beaufort Scale, I gave the generally accepted effects of the various wind forces to enable those without access to detailed reports, to judge wind speeds. Now that the Beaufort index numbers are regularly broadcast the velocity figures can be put to use the other way round—visualising the wind force by knowing the scale number. At least, you will be able to know just how much your aerial is likely to sway! As the "effect" details are likely to be of use to readers who missed the original article, no apology is needed for repeating them below.

Force	M.p.h.	Description	Effect
0		Calm	Smoke rises vertically
1	1 to 3	Light air	Direction discernible by smoke drift but not by wind vanes
2	4 to 7	Slight breeze	Felt on face, leaves rustle. Vanes moved by wind
3	8 to 12	Gentle breeze	Leaves and small twigs in gentle motion
4	13 to 18	Moderate breeze	Raises dust and loose leaves and small branches are moved
5	19 to 24	Fresh breeze	Small trees begin to sway
6	25 to 31	Strong breeze	Large branches moving, telegraph wires whistle
7	32 to 38	Moderate gale	Whole trees in motion. Hard to walk against it
8	39 to 46	Gale	Breaks twigs off trees
9	47 to 54	Strong gale	Liable to bring down occasional chimney pots, slates and tiles
10	55 to 63	Whole gale	Trees may be uprooted, structural damage
11	64 to 75	Storm	Widespread damage
12	Over 75	Hurricane	—

Stroke P

Following my last month's references to holiday-making I am reminded that last year many amateurs enjoyed their holiday part of that wonderful summer on the Norfolk Broads. This is an ideal way of spending a holiday for those who have a highly developed sense of freedom to satisfy—especially the freedom to carry on with one's hobby. Thus during the season there were quite a number of transmitting amateurs on the Broads operating portable on top band. Unfortunately the QSO's were fewer than they would have been had schedules been planned.


To make the most of such opportunities this year it is suggested that those who intend to operate /P should make previous contact with either the R.S.G.B. Territorial Rep. or with Dr. Arthur Gee, G2UK, "East Keal," Romany Road, Oulton Broad, Suffolk. The certainty of a greatly increased

number of contacts will then be assured.

I am not sure whether /P on the Broads ought not to count as "another county." Top Band County Logging is quite an idea for listeners eager to test set performance and operating skill. How many counties have you heard on 160 metres? If you haven't tried you will find it a harder test than you might at first think. The maximum is over a hundred (counting Eire, Isle of Man, etc.) but unless you are pretty good, or very well sited, it will take you months to get a third of that score!

A certain amount depends on luck. If you are able to put in a good spell of band searching during a contest for instance, you might get off to a magnificent start. But even that will only bring you to the tantalising state of looking for the rare counties a few weeks earlier. From that point the adding of a new county makes the event something of a red-letter day!

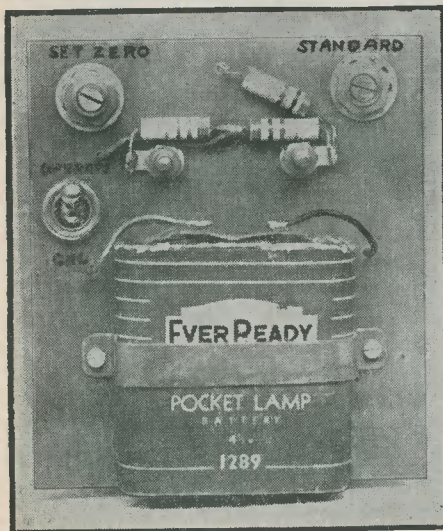Thermistor-operated Thermometer—continued from page 657



switched off and VR₁ adjusted to give full scale deflection on the meter. The switch is now changed to the "Calibrate" position and VR₂ is also adjusted to give a full scale reading. This control will need no further adjustment and should be sealed with wax to prevent further movement.

As the thermistor cools, readings should be taken every 5 degrees on the thermometer to enable the calibration to be completed. The use of ice may be found necessary to carry the calibration curve to zero, should the ambient temperature be too high. If ice is unobtainable the last part of the scale could be calibrated by interpolation. That is, a graph is drawn from the figures obtainable and the curve carried on in a natural line over the desired range. Although this may not sound very precise, in practice the results obtained will be found to be reasonably accurate. After the short across SW₁ has been removed, the "Thermistor Thermometer" is ready for use.

Exhibition at Bexleyheath

The North Kent Radio Society, in co-operation with three other local clubs, is holding an exhibition, open to the public, at the Bexleyheath Congregational Hall on Saturday 12th May. The North Kent Radio Society will be showing working equipment, and the club station—call sign G3ENT—will

be in operation. The other clubs exhibiting cater for the model aircraft, yachting and engineering enthusiasts.

The North Kent Radio Society holds its meetings at 8 p.m. on the second and fourth Thursdays of the month at the Congregational Hall, and the Hon. Sec., F. C. Beadle, G3KLI, of 56 Balliol Road, Welling, Kent, will be pleased to see prospective members at these meetings or at the exhibition.

TRANSMITTING WITH THE EL43

by G3XT

"FB FR QRP, OM!"—THAT'S THE SORT OF comment on your signals that you want to hear if you are keen on low-power transmitting; and I have heard it a good many times recently while trying out the EL34, a comparatively new Mullard pentode.

Although of course it is primarily intended for use in the output stage of an audio amplifier, the EL34 seems to be quite a promising valve for QRP transmitting purposes. It has been tried out at G3XT during the past few weeks, under very adverse conditions, and has given encouraging results in a single-stage Colpitts oscillator running at about 5 watts on the 7 Mc/s band.

As G3XT had been off the air as far as transmitting is concerned for the past two years (since moving to a new QTH), a temporary transmitter had to be rigged up in order to try out this new valve. Impatience to get on the air again resulted in the construction of a rather makeshift transmitter hooked together with ex-Government surplus junk; and a hastily-erected aerial of very doubtful efficiency, only about 20ft in height and rather badly screened.

Despite these handicaps, the whole thing worked from the word "go," and a QSO resulted from the very first call. Exceptionally poor conditions prevailed on the band throughout the greater part of the period during which I have been trying out the EL34, and no doubt it would have given a much better account of itself in more favourable circumstances.

Over 30 QSO's were obtained, however, with 7 countries, including EI, F, HB, ON, and SM, as well as with a number of British stations in places ranging from Edinburgh, Kirkcaldy and Glasgow in the north to Southampton and Plymouth in the south; and from Liverpool and Bristol in the west to Southend-on-Sea in the east. Due to

poor conditions, no doubt, the average strength reported was not high—only S5—but when conditions improved now and again for a brief spell, the reports rose to S7 or S8.

With a properly designed and carefully constructed transmitter, an efficient aerial and normal conditions on the band, this valve can reasonably be expected to yield reports averaging RST 579, with probably a fair number of 589's and a few 599 reports. That prediction is based on my experience with other valves which have given considerably poorer results when used under adverse conditions comparable with those in the test of the EL34.

QRP enthusiasts should find this valve worth a trial, either in a single-stage VFO or CO; or as the PA valve in a more ambitious type of low-power transmitter.

In designing a transmitter around the EL34, you should bear in mind that it radiates quite a lot of heat, so you should give it plenty of space above the "deck," and see that the cabinet is adequately ventilated. See, too, that the screen-grid feed resistor is of adequate wattage rating, otherwise this will run hot too! A potentiometer would probably be better.

Owing, probably, to the somewhat hazy construction of the temporary transmitter at G3XT, it was found advisable to run the grid circuit on 80 metres and extract the signal on 40 metres by tuning the anode circuit to that band. This frequency-doubling arrangement gave less RF output, but the valve was much "tamer" than when used with both tuned circuits on the same frequency.

Stability was excellent, the tone consistently T9 (except on one solitary occasion when a temporary fault in the power pack resulted in a T8 report), and the keying was free from chirp.

Catalogue Received

We have received from Messrs. R. Fagelston, 46 Hardwicke Road, London, N.13, a copy of their current catalogue, together with inserts. Readers may obtain their copies by sending 3d. along to the address quoted; periodic supplements will also be issued.

The catalogue, which is duplicated and well produced, consists of 18 pages listing the usual range of components, plus other

items not so usual, such as Scratch Remover. Also included are kits for various items which have been described in this magazine, such as the Transistorette, the Mullard 3 Watt Amplifier, a Modern Pre-amplifier, and so on. There is also a range of Band III converters, and a number of simple receiver kits. A number of bargain lines are being currently offered.

The prices quoted throughout are, we consider, very reasonable, and we suggest readers should obtain a copy.

A THERMISTOR-OPERATED THERMOMETER

by J. W. BAGNALL

IT IS OFTEN DESIRED TO MEASURE THE temperature of an object which is so positioned that the use of a mercury thermometer is most inconvenient. A machine bearing, or even a domestic hot water tank situated in some inaccessible corner, are but two examples that spring to mind.

The instrument about to be described is a temperature indicating device which makes use of a block type thermistor to deflect a meter which is calibrated from 0 to 40 degrees centigrade. A thermistor is a semi-conductor whose resistance drops rapidly with an increase in temperature. It consists of a pressed, sintered block of thermistor material soldered to a metal plate.


The instrument itself is made in two sections, one being a small case containing the meter, battery and bridge resistors; this being connected by a length of twin flex to the thermistor, which is placed in close contact with

the object of which the temperature is to be monitored. Should the ambient temperature be required, say, of the air outside the house, a U-shaped cover should be placed over the thermistor. This will shield it from direct sunlight and inclement weather, but still allow the air to circulate freely around the semi-conductor.

The Circuit

It will be seen that a bridge circuit has been employed, powered by a 4.5 volt battery, with the thermistor forming one arm of the bridge. The current flow through R_3 and R_4 is constant, therefore a constant potential will exist at point "B." Assuming that the same potential exists at point "A," then the deflection of the meter will remain at zero.

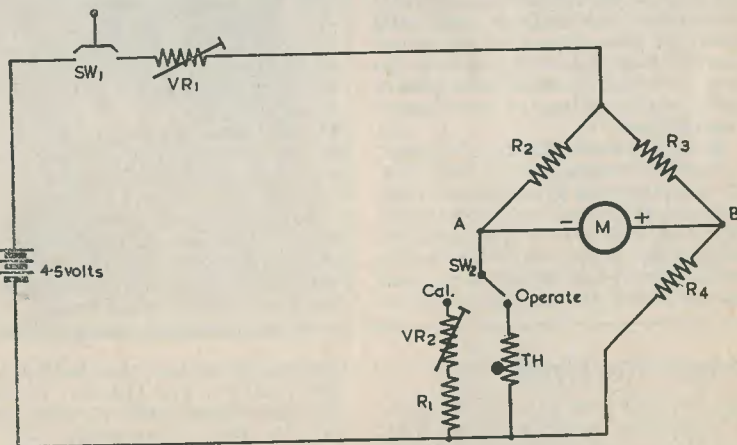When the thermistor is heated its resistance will fall, and current will flow from point "B" through the meter to point "A" and via



R_1 220 Ω	VR_1 500 Ω (set zero)
R_2 2.7K Ω	VR_2 500 Ω (standard)
R_3 100 Ω	SW_1 "press-to-make" switch
R_4 100 Ω	M 1mA F.S.D. meter
	TH Kb 1391/80 STC thermistor

6217

THE RADIO CONSTRUCTOR

the thermistor to ground. From this it will be realised that as the temperature of the thermistor is further increased, the greater will be the current flow giving a larger deflection on the meter. To allow for deterioration of the battery over a period of time, the bridge network is fed via a variable resistance VR_1 , the value of which is decreased as the battery voltage falls. To increase the voltage across the bridge willy-


The thermistor in this instance is mounted on a small block of paxolin, and is coupled to the bridge by a length of twin plastic flex. The use of shielded wire is not necessary.

Calibration

When construction is completed, it remains to calibrate the meter. In the original meter the scale was replaced with a thin card on which the new scale was drawn, using indian

Right: Front view of the thermometer.

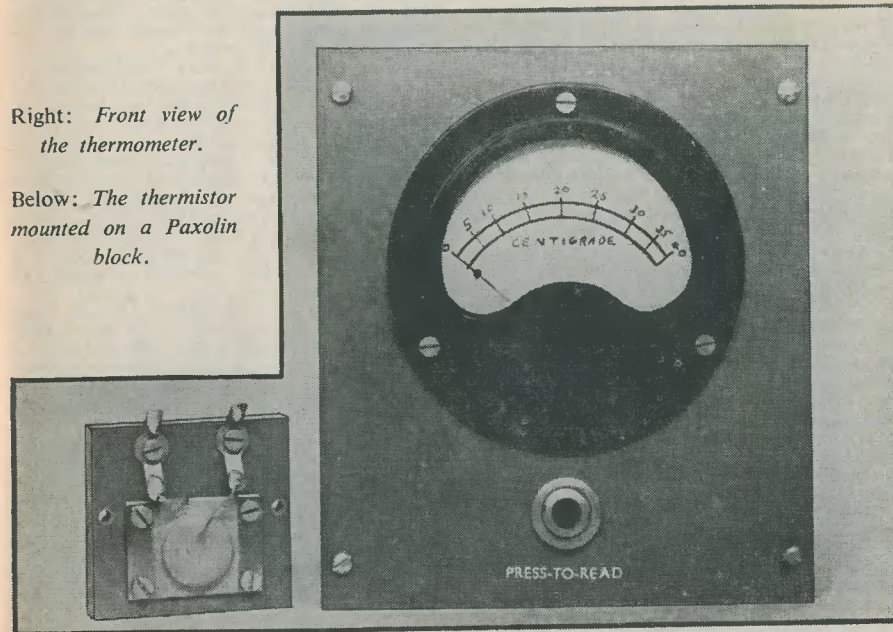Below: The thermistor mounted on a Paxolin block.



nilly would cause the calibration of the instrument to be incorrect. To obviate this, a switch is provided to remove the thermistor and insert a pre-set value resistor in its place. This is VR_2 plus R_1 . The resistor VR_1 is then adjusted for full scale deflection of the meter and the calibration is unaffected.

A push-to-read switch is mounted on the front panel so that current from the battery flows only when a temperature reading is being taken. The current drain from the battery is of the order of 10mA.

Construction

Although the reader will no doubt wish to use his own layout, some idea of the prototype will be gained from the illustrations. The resistors, battery, etc., are mounted on a paxolin panel, which in turn is held by the meter terminals. This makes for a compact arrangement which is easy to remove from the case.

ink and a fine mapping pen. Should the constructor prefer not to dismantle the meter to fit another scale, an alternative would be to draw a graph which could be referred to the original meter calibration.

To calibrate the instrument as a whole, a thermometer is placed in close contact with the thermistor and embedded in a ball of plasticine; this is done to ensure an even temperature rise. The assembly is now placed inside a suitable container, such as a metal box, together with a 100-watt electric light bulb, this being a convenient means to raise the temperature.

For the purpose of calibration, the press-to-read button should be shorted out and the switch SW_2 set in the "Operate" position. VR_1 is turned to maximum resistance.

When the temperature inside the "hot-box" reaches the desired maximum, in this case 40 degrees centigrade, the bulb is

(continued on page 654)

MAY 1956

The First London Audio Fair

IT IS A DEFINITE FACT THAT, SO FAR AS HIGH-fidelity reproduction is concerned, British audio equipment stands amongst the finest obtainable in any country to-day. This statement is supported by the fact that one of our most flourishing export markets is in hi-fi sound reproduction products, these continuing to be sold in large quantities all over the world. Frequently, British audio equipment has to compete against tough local opposition, yet, despite shipping costs and import tariffs, the British goods still sell in large quantities.

For a long time it has been apparent that British firms have needed a high-fidelity "shop-window." In America, audio shows and "fairs" have evolved an ingenious and highly effective technique to demonstrate the exhibits which have been entered. Instead of using a large hall, as is done for most normal exhibitions, several floors of a hotel are taken over, the individual rooms thereby giving just the right conditions for high volume demonstrations without mutual interference between exhibitors, as well as providing listening rooms of the same size as would be used by most prospective purchasers. The London Audio Fair Committee have now employed this device very effectively themselves, with the result that the first British Audio Fair occupied all the rooms in the first three floors of the Washington Hotel in Curzon Street. In addition, the front hall and main hall of the hotel were employed for exhibitors' stands. Practically all the firms at the fair had a stand on the ground floor, plus one or two demonstration rooms.

The popularity of the London Fair was well exemplified by the very large number of people who attended. Indeed, on the Saturday afternoon (the fair was held on Friday, 13th April to Sunday, 15th April) it was necessary to keep some people outside the hotel until a sufficient number inside had left. This was a wise move on the part of the organisers because, despite the inconvenience to those waiting outside, it prevented too heavy a crush in the show itself.

The Exhibits

It would be difficult to try and categorise the various exhibits demonstrated, as all were in more or less the same field. It would also be fruitless to comment on the standards of workmanship, design and performance obtained, as comparisons here would be out of place. Suffice it to say that everything shown was very good, and that some things were excellent indeed. So far as this report is concerned, it would be best to deal with exhibitors in alphabetical order. If some firms have been omitted, this is only due to the lack of space available here.

Acoustical

The Acoustical Manufacturing Co. make a good "first" on any audio list, as this is the firm which has produced the well-known Quad II amplifier. The Quad has been the subject of considerable discussion in audio circles, and was used in recent comparisons of live and recorded music at Carnegie Hall. For the Fair, Acoustical exhibited an electrostatic loudspeaker employing the principles recently discussed in *Wireless*

World. This speaker incorporates its own polarising supply.

Armstrong Wireless and Television, who specialise in custom-built chassis, were exhibiting their A.10 amplifier; this having been originally introduced a year or so ago. The A.10 is a fully tropicalised job which, amongst other things, can work in conjunction with the firm's f.m. tuner type 56. Armstrong also supply the "Sonixgram," a complete cabinet-housed high-fidelity system with chairside control.

Dynatron Radio Ltd. have a high reputation for individual and well-engineered designs. At the show they exhibited their f.m. tuner type FM1. This is a seven-valve receiver which has the attractive feature of pre-set tuning. The station selector switch spindle passes through the surface of the chassis at right angles. Dynatron also make a hi-fi amplifier (LF10) together with a tone control unit (TC10) and an a.m./f.m. tuner (T10). The f.m. tuner, amplifier and tone control unit can be obtained in a complete radiogram assembly called the "Windsor."

E.M.I. need no introduction here, as their contributions to the hi-fi world have been appreciated for many years. In addition to their normal 78 and 33 $\frac{1}{2}$ r.p.m. records, this company is making single channel tape records and twin-channel "Stereophonic" tape records (both 7 $\frac{1}{2}$ in/sec.). The Stereophonic tapes pass through a twin head, and the two separate recordings are reproduced via two separate loudspeakers spaced some distance away from each other. The two recordings on the tape were originally recorded, of course, with separate microphones similarly positioned. E.M.I. have also introduced a new tape (type 99) on a PVC backing. The thinness of this backing enables more tape to be stored on a standard reel.

The Garrard Engineering and Manufacturing Co. specialise in high-fidelity pick-ups, gramophone motors and changers. One of their products, the BA1.45 r.p.m. Single Record Player is intended to be powered from batteries for use in transistor record players. Consumption from the battery is only $\frac{1}{2}$ watt. In addition to a wide range of electric motors, Garrard also showed their Model 24 motor, this meeting a particular need insofar as it is spring-wound. The Model 24 has three speeds.

The "Presence Unit" type BCS 1852 is a high frequency unit which has now been introduced by G.E.C. especially for use with their metal cone loudspeakers. The unit has been designed to screw into the centre of the BCS 1851 metal cone loudspeaker, the Bakelite insert in the latter being removed for this purpose. This ingenious combination of two speakers is further simplified by careful design, the impedance of the presence unit being such that a cross-over network requires only a series 10 μ F condenser. Also shown were the home-constructor "912" amplifier, plus manufactured amplifiers for 12 and 25 watts output.

"Axiom" and "Audiom" are the names employed by Goodmans Industries for their loudspeakers. Goodmans Industries also make

an exclusive Acoustical Resistance Unit. This provides a means of reducing the overall size of an enclosure whilst retaining the same bass response.

Gramplan

Gramplan Reproducers are manufacturers of loudspeakers, amplifiers, microphones and recording equipment; a large proportion of their output being placed on the export market. Gramplan cutter-heads are used by the B.B.C. and by broadcast and recording companies throughout the world. Their 1255/15 speaker was exhibited at the Fair, this having a duralumin voice coil former, and a voice coil wound by special methods.

One of the engineers in the Grundig demonstration rooms went especially out of his way to assist the writer in preparing his copy. Grundig were exhibiting their TK820/3D "Specialist" recorder, this having a response of 40-14,000 c/s at 7 $\frac{1}{2}$ in/sec. The TK820/3D is a high fidelity instrument, and was demonstrated as such with its own internal speaker. One of the secrets behind the Grundig performance is the gap width of the head, this being quoted as 7 microns only.

His Master's Voice attracted large crowds with demonstrations of their "Stereosonic" reproducer. This employs the E.M.I. twin-track tapes mentioned previously.

Mr. H. J. Leak is now back from America and Canada where his equipment has been selling very well against strong local competition. The Leak "Point-One" series needs no further description here, although some readers may be unfamiliar with the new Leak "Trough-Line" f.m. tuner. This employs a Seeley-Foster, instead of a ratio, discriminator, and the oscillator is tuned by a "trough-line" arrangement, rather similar to Lecher wires. Tuning drift is kept, by this device, to less than 10 kc/s from the instant of switching on. The tuning indicator functions from the d.c. voltage on the discriminator load. H. J. Leak and Co. will shortly be marketing an electrostatic speaker.

The Lowther Manufacturing Co. exhibited their loudspeaker units and amplifiers, and Lustraphone demonstrated their microphones, transformers and accessories. A full transistorised power amplifier is a new Lustraphone product.

Mullard high-fidelity amplifiers for the home constructor have been built by many amateurs, and this magazine has assisted in providing constructional details of Mullard laboratory designs. Mullard showed, in addition to their amplifiers, many of their products in the valve and semi-conductor fields.

Pamphonic have introduced a quote-worthy term to the amplifier sphere, this being "Ab-Fi" (Absolute Fidelity). Pamphonic now have available a compact 10 watt amplifier designed for domestic use which is housed in a very stylish cabinet (type 1003). Their 1002/1002A 25 watt amplifier is claimed to be flat from 2 to over 100,000 c/s, with hum and noise 90dB down, and a total harmonic distortion of 0.05% at 15 watts (1,000 c/s).

Plessey

Plessey are in the high-fidelity market and, in addition to a conventional range of audio

equipment, have now introduced an Ionophone loudspeaker. The Ionophone principle has been discussed for quite a few years in audio circles, and has been the subject of much imaginative development work. The basic principle consists of ionising air in a cylinder, closed at one end, by means of r.f. at a high voltage. This r.f. is modulated by audio, whereupon the glow discharge in the cylinder varies at a.f. Sympathetic air pressures are then set up which may be applied to a loading horn. The device has attracted engineers owing to its inherent simplicity: there are no moving parts whatever and the loading applied to the drive circuit is constant, irrespective of audio frequency. Indeed, the only limitation to the audio range available is that imposed by the horn itself; and the dimensions of this can be calculated from well-established formulae. The Plessey Ionophone should be in production by the time of the Radio Show.

The Pye "Black Box" is, nowadays, a familiar piece of equipment, but it represents only a small proportion of Pye high-fidelity products. This company has now introduced a wide range of amplifiers and loudspeaker systems. Some of these are capable of being fitted into existing radiogram cabinets by "do-it-yourself" enthusiasts.

R.C.A. Photophone have been making hi-fi news with their new products over the last few years. In addition to good performance, R.C.A. Photophone believes also in good cabinet design, and seems to pay much more attention to attractive styling than do some other firms. This company has introduced a new 8-pole variable reluctance pick-up head, in which all electrical connections are encapsulated in polystyrene.

Another stereophonic reproducer, designed for the E.M.I. twin-track records, is made by Specto Ltd. This reproducer, for which sample export orders have already been met, is now in full production. Truvox demonstrated their new tape recorder to advantage (cf. the R.E.C.M.F. report in this issue); the speaker system being that housed in the recorder itself.

Wharfedale Wireless Works are well known, not only for their products but also for their association with Mr. G. A. Briggs, who has helped so much to introduce hi-fi equipment to the general public. Wharfedale were exhibiting their Super 3 Two-Speaker system, which enables a full frequency response to be obtained in a remarkably small enclosure.

Wright and Weaire have specialised in tape recording for many years. Their Tape Deck has, indeed, become a "standard." Wright and Weaire "Ferroglyph" products shown at the Fair included two tape recorders designed especially for portable use.

The Future

Thus was introduced the first London Audio Fair. Its organisers are to be congratulated for their imaginative outlook; and there is little reason to doubt that both home and export high-fidelity markets will have benefited accordingly. The London Audio Fair now becomes an exhibition to be anticipated eagerly each year by all who appreciate high quality reproduction.

A Constructor at the 1956 R.E.C.M.F. EXHIBITION

FOR SOME YEARS NOW IT HAS BEEN POSSIBLE to direct strangers to the R.E.C.M.F. Exhibition by the simple device of telling them to start at Marble Arch and walk against the stream of people carrying Ersin Multicore wallets. This year proved to be no exception, and the prominent red Multicore folders added their colour to the cheerful spring scene in Park Lane during the three days on which the R.E.C.M.F. Exhibition was held.

The 13th private exhibition of the Radio and Electronic Component Manufacturers' Federation took place in the Great Hall of Grosvenor House on April 10th, 11th and 12th, and was once more a scene of bustling activity. The necessity of moving the exhibition to a larger hall becomes more evident every year, and one cannot help but sympathise with the staff on the stands who have to deal with a continual barrage of questions under very cramped and crowded conditions.

Despite this, the Radio Component Show—to give it its short title—was up to its usual standard, and gave evidence once more of the high quality to be found in British components and radio equipment.

Export figures for British components reflect this quality. To take an example, direct exports of components and sound reproduction products in 1955 had a monetary value greater than £13 million, this being an increase on 1954 of 23%. One large market was provided by the U.S.A. (£900,000), who were also the largest purchasers of sound reproduction products.

Trends

So far as new developments were concerned, this was a fairly quiet show. The changes introduced by such things as Band III and FM have now become established, and manufacturers appeared to be concentrating more strongly on increasing and improving the reliability and performance of their existing products. If there was a significant trend at the exhibition, it was probably that towards miniaturisation.

In this particular field the battery manufacturers showed some new and interesting developments. Ever-Ready were well to the fore with a comprehensive range of dry batteries, this extending from large batteries for radio and photoflash equipment to tiny miniatures for valve and transistor hearing aids. Mallory exhibited their mercury cells, these having the advantages of low cubic capacity and weight. A 1.34 volt Mallory mercury cell, shortly to be introduced, has a diameter of 0.45in and a height of 0.125in only. This is the type R.M. 400, and its weight will be 0.04oz.

Batteries as small as this deserve equally small components and circuit assemblies. Typical of these were the components and amplifiers shown by Fortiphone, the former including several miniature transistor a.f. coupling transformers, and the latter a complete encapsulated a.f. amplifier using transistors. Lustraphone, who manufacture microphones and accessories, are

in the miniature field with a tiny electromagnetic microphone (type E.M. 6.2). This has been designed for deaf-aid and similar applications and employs a new principle of operation.

Transistors were well in evidence elsewhere, being exhibited by Mullard, Standard Telephones and G.E.C. Mullard showed also the photo-transistor type OCP71; this component changing from a partially conducting to a fully conducting state whenever light falls upon it. With this photo-transistor it is possible to operate a relay directly, without the necessity for amplifying valves or similar devices; and the consequent circuitry involved is extremely simple. The OCP71 may be featured shortly in this magazine. Included in the Standard Telephone transistors, incidentally, were the TS1, TS2 and TS3 range, as specified for the "Transistorette" receiver.

Other transistor amplifier applications were also to be seen. Lustraphone showed a fully transistorised power amplifier suitable for a record player, and Fortiphone a four-transistor hearing-aid amplifier fitted into the side arms of a pair of spectacles. The problem of obtaining maximum audio output from transistor a.f. stages is eased considerably by the introduction of a specially designed loudspeaker by Plessey. This has a centre-tapped voice coil, thus enabling push-pull transistor output stages to be connected directly to the speaker without the necessity of an output transformer at all.

Printed Circuits

Printed circuits are now, of course, here to stay, and development appears to be following two parallel paths; these consisting of work on the circuit boards themselves and on the components designed to be mounted on them.

T.C.C. exhibited a large range of printed circuit assemblies, these including a complete television "front end" (incorporating a tuner for Band I and Band III reception), an f.m. tuner, and transistor panel units for use in electronic computers.

Valveholders for printed circuit work were available from McMurdo. These were in B7G, B8A and B9A sizes, had "pen-nib" contacts for ease of dip-soldering, and could be supplied with skirts, if desired, for screening cans. Egen Electric showed resistors especially designed for printed circuit panels, whilst an extensive range of printed circuit components of all types was to be seen on the Plessey stand.

In the printed circuit sphere it would appear that steady progress over the last year is evident, but that no startlingly new techniques have been evolved.

Tools and "Hardware"

A firm which has gone to considerable lengths to make the lot of the service and production engineer easier is the Spear Engineering Co. (Worlingham, Surrey). In addition to the manufacture of components, this company makes tools which are especially applicable to the radio industry. These tools include screen-

ing can and valve extracting tools for valves of varying sizes, a complete set of trimming tools (capable, incidentally, of tackling those "awkward" trimmers used by some manufacturers), a control knob remover which enables spring-mounted knobs to be pulled safely without scratching the cabinet, and what is described as "The Trigga-Snip." This latter tool not only cuts wires, it holds them afterwards as well. It appears to work on a nibbling principle. The device has a pistol grip from which protrudes a rod some six inches long, the cutting action being incorporated in the end. The rod can pass through a quarter-inch hole and should be ideal for nosing into a crowded chassis. The really imaginative design and manufacture of tools of this type for the use of radio engineers is a trend that deserves to be warmly commended.

The "Bib" wire cutter is by now a well-known radio and electrical worker's tool, and it affords a good introduction to its manufacturer, Multicore Solders. Also exhibited by this firm were their established "Bib" recording tape slicer, together with an extensive range of solders. A new solder displayed at the Show is the Ersin "Savbit" alloy. This is a five-core solder and contains a small percentage of copper. It is claimed that the new solder can increase the useful life of a soldering bit by 10 times. "Savbit" alloy is covered by patent, and is already being made in 14, 16 and 18 s.w.g. Its melting point is approximately equal to that of conventional 60/40 solder, and its cost appears to be less.

Enthoven Solders exhibited an interesting new development, this being a solder which can be applied to aluminium. The tinning of a sample strip of aluminium was effectively demonstrated on the stand, the writer being given to understand verbally that the solder functioned best with commercial-grade aluminium, i.e. with metal that has slight impurities. The solder had a special flux, and this flux could be obtained separately, if desired, in paste or liquid form. For the stand demonstration a conventional soldering iron was employed. The core aluminium solder has the type number AS20.

Other exhibits in the "hardware" line were represented by the very large number of metal, ferrite and plastic parts to be seen. Magnets and laminations fall into the "metal" category, but there was little here that was new. In the ferrite department, Salford Electrical Instruments (associated with G.E.C.) showed a range of cores made with "Gecalloy." One of the Plessey core materials is "Caslam," and this was employed in many applications, these ranging from coil cores to deflector coil rings. Mullard "Ferroxcube" was also in evidence, the new "Ferroxcube" beads being of particular interest. These beads, threaded on to a straight piece of wire, increase its inductance by a sufficient amount to make it act as a choke at v.h.f. The beads may, therefore, be threaded on to the heater and h.t. wiring of v.h.f. equipment to replace more costly wound chokes.

The plastics side of radio is now assuming such large proportions that the two sciences are practically inseparable. Here again, no startlingly new developments were to be seen, but the sure and steady progress over the last few years is very evident. An interesting departure was shown on the Belling Lee stand, this consisting

of the flexible terminal blocks made by this firm. The insulating material is PVC, and the terminal blocks can be bent around any desired contour. This particular development well illustrates the wide field and variety now evident in radio plastics.

Encapsulating techniques were also shown, these mainly employing the epoxy resin, "Araldite," manufactured by Aero Research Ltd. Encapsulated assemblies enclose an entire circuit in a block of resin or similar material, the only connections being given by lead-out wires from the block. Once encapsulated, all components are virtually immune from physical damage and humidity.

Television

There was not a great deal new this year in the field of television. However, a number of 90 degree picture tubes were of interest; and it is probable that they will make their appearance in manufactured television sets before the next six months are out. A reflection on the present Government policy of hitting home-market TV is illustrated by a new Edison-Swan tube. This is the CRM93, and it has a nine-inch screen, plus all the latest developments to be found in larger tubes. Originally developed for portable TV, it is thought that it might now also be welcomed in receivers designed to reduce the hire-purchase deposit. (No comment from this writer.)

A smart-looking little "Table-top" Band III aerial was shown by Wolsey. This is their "Hi-Q" model, and is intended for use within a range of 10-15 miles from the Band III transmitter. The aerial is mounted on a rotatable base, with a cross-over network to take the existing Band I aerial, should this be desired. A lead from the "Hi-Q" may then be used to connect to the receiver aerial socket. The design is rather like that of a single loop, and a front-to-back ratio of 6 db is quoted.

Assemblies

Complete assemblies and instruments seemed to be rather more numerous this year than has previously been the case.

As an example of what was to be seen, Truvox were announcing a new tape-recorder, type R1; this being scheduled for release in mid-July. The R1 is a complete unit. Also to be seen on the Truvox stand was an adaptor for recording telephone messages.

Advance Components exhibited their range of test equipment, this including a.m./f.m. signal generators especially designed to meet the new requirements of servicing sound and television v.h.f. receivers. Advance also showed their new "Q" meter. The writer understands that this instrument represents an improvement on existing "Q" meter practice, insofar as the r.f. injected into the coil under test is modulated. It is the modulation, and not the r.f., which is then read by the "Q" meter valve voltmeter. Avo also have new equipment available to meet present-day requirements. A particularly interesting item is their a.m./f.m. signal generator type TFM, this being especially useful for television and f.m. work. A new, moderately priced, Avo instrument is the a.m. signal generator type III, this covering 150 kc/s to 220 Mc/s on fundamentals.

(continued on page 664)

The Moving Coil Meter

by DAVID A. MORRIS

THE MOVING COIL METER IS THE MOST common type of meter in use for measuring d.c., and at some time or another every radio experimenter will have found it necessary to use one. But I wonder how many readers have ever bothered to look up the theory of operation of such a meter? Very few, I'm sure! The purpose of this article is to give readers a brief account of the construction, design, theory and modifications of the moving coil meter.

Form

Briefly, the instrument consists of a small rectangular coil having a large number of turns of fine wire, uniformly wound upon a light aluminium former. This former is pivoted on jewelled bearings, and swings between the pole pieces of a strong permanent magnet. The pole pieces are cut so that they form a hollow cylinder around the coil. There is also a fixed cylinder of soft iron within the coil.

Attached to the pivots are two flat springs which exert a couple which acts against that of the deflecting current. When the current is switched off these springs return the coil to its original position. The springs have an additional function of carrying the current from the terminals to the two ends of the coil.

A light aluminium scale-pointer, a uniformly divided scale, and an outer protective case complete the meter (see Fig. 1).

Theory of the Instrument

Imagine our coil to consist of n turns on a former 1 cms. long and b cms. wide.

If the field strength of the magnet is H oersteds, and the current to be measured is i amperes, then there will be a turning force of $Hiln$ on each side of the coil, holding it an angle of θ° to its original position (see Fig. 2).

Thus the moments of the forces about the axis of the pivot

$$= Hiln \cdot \cos \theta$$

$$= HiAn \cdot \cos \theta \quad (\text{where } A = l \times b = \text{area of coil}).$$

In practice, however, the presence of a soft iron core and the shape of the pole pieces ensures that the field is radial, and so, whatever the angle of deflection, the plane of the coil is always parallel to the field.

Thus, our expression becomes: $HiAn$. The coil comes to rest when the above turning couple is equal to the opposing couple due to the springs (or $c\theta$, where c is the controlling couple per unit deflection).

Thus,

$$c\theta = HiAn$$

$$\text{or } i = \frac{c}{HAN} \theta$$

i is therefore equal to $K\theta$, where θ is the scale deflection and K is a constant depending upon the dimensions of the coil, field strength of the magnet and the torque supplied by the springs. The current is therefore proportional to the angle of deflection, and when a meter is calibrated against a standard, it will have a uniform scale.

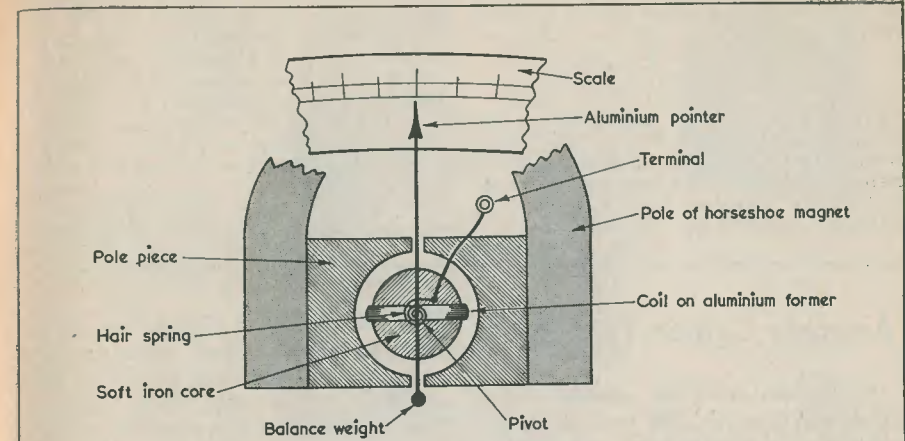


FIG.1. DIAGRAMATIC ARRANGEMENT OF METER

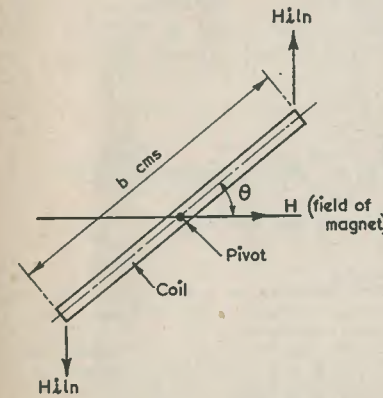


FIG.2. THEORETICAL DIAGRAM SHOWING DIRECTION OF FORCES (plan view)

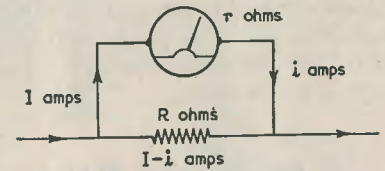


FIG.3(a). AMMETER (for theory see text)


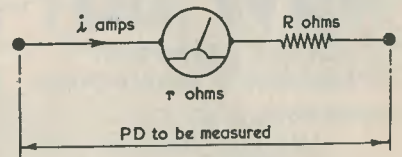


FIG.3(b) VOLTMETER

G166

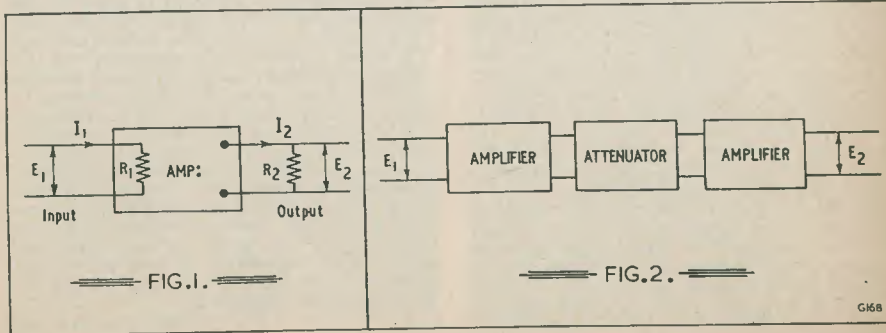

G168

Design of a Moving Coil Meter

A number of points must be considered when designing a meter. A meter for general use must be sensitive, easy to read, accurate and robust. A well designed meter provides all these points to a certain degree, hence its popularity for measuring d.c.

The sensitivity is given by θ/i , in other words, the angle of deflection for unit current. As $\theta/i = HAn/c$, the field strength of the magnet and the size of the coil have to be made as large as possible, without becoming too cumbersome.

The meter also has to be "damped" so that the coil comes to rest quickly, without oscillating across the required reading before it does finally stop moving. Electrical damping is usually provided by the eddy-currents induced in the metal coil former.

Finally, here are a few points of interest concerning the various ways in which the meter is used.

As an ammeter, the m.c. meter has to be wired in parallel with a resistance. The value of this resistance will depend upon the maximum current to be measured. If

you know the internal resistance of a meter, it can be used for different ranges by "shunting" with a resistance whose value is obtained from the equation

$$R = \frac{r \times i}{I - i}$$

where R is the required resistance, r is the resistance of the meter, I is the new maximum current, and i is the original maximum current for which the meter was designed. Multi-range ammeters have a number of switched resistances (see Fig. 3a).

As a voltmeter, the moving coil meter is used in series with a high value resistance. In this case the formula is $V = i (r + R)$. V is the p.d. to be measured, i is the current required to give a full-scale deflection, r and R are the resistances of the meter and the required resistor respectively (see Fig. 3b).

A last word of advice—remember that your meter is a valuable friend and should be treasured as such! With careful handling it will remain accurate for years; however, if it is given rough treatment the meter will soon become insensitive.

Amateur Colour Television

On Saturday April 8th, amateur colour t.v. signals were sent and received for the first time. G3CVO/T, near Chelmsford, received very clear colour bars and patterns from G2WJ/T at Dunmow. The colour equipment was built by Mr. C. G. Dixon of Ross-on-Wye, and runs at 150 lines, 100 fields per sec sequentially scanned, giving

33½ complete colour pictures per second. Both monochrome and colour receivers were used, and at the flick of a switch either colour bars or the G2WJ "studio" was seen. This is the first time that colour t.v. has been transmitted by amateurs anywhere.

Vision frequency 436 Mc/s, sound 145.7 Mc/s. Distance 13 miles.

There are now 21 /T stations in the U.K., and the DX record is 38 miles between G2DUS/T (Baldoock) and G3KKD/T (Ely).

New Revised Edition NOW OUT

RADIO AMATEUR OPERATOR'S HANDBOOK

INDISPENSABLE TO THE
AMATEUR TRANSMITTER
AND LISTENER

1956 Edition

It contains all those details of information which the transmitter and SWL constantly require.

Right up-to-the-minute Amateur Band Prefix lists, both alphabetically and by Country, Zone Boundaries, Call Areas, Mileage Tables, QSL Bureaux, "Q" and "Z" Codes, WWV Skeds, and much other information, as well as a selection of maps of DX areas.

Price 3/-, postage 2d.

DATA PUBLICATIONS LTD
57 Maida Vale London W9

R.E.C.M.F. Exhibition

(continued from page 661)

Gadgets

An exhibition is not a real show without working "gadgets," but these were rather disappointingly absent this year. Nevertheless, Plannair, manufacturers of blowers, gave a convincing and eye-catching demonstration of weights being blown up glass cylinders under the pressure of normal air blowers.


Probably the most interesting working model was exhibited by the United Insulator Co. Ltd., who, amongst other things, make ceramics and piezo-electric devices. Their exhibit incorporated a miniature "water-wheel," the outer edges of whose vanes just entered the surface of apparently placid water in a glass bowl. Despite this, the "water-wheel" rotated. The "drive" for the wheel was given by a small piezo-electric transducer immersed in the water about a foot or so away. This transducer agitated the water at a frequency of 3 Mc/s with a power of 30 watts. Whilst the writer discussed the device with an engineer on the stand, the engineer put his hand into the water to dispel a few small bubbles that had formed on the surface. Bubbles apparently reduce the efficiency of water as a supersonic power-conducting medium quite noticeably, since, without them, the "water-wheel" rotated nearly twice as quickly!

TRANSFORMER SNIP

11/6

Post 2/-

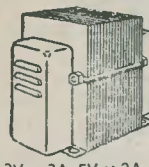
Fully shrouded—standard 200-250V primary. 280-0-280 at 80mA, 6.3V at 3A, 5V at 2A



CONNECTING WIRE
P.V.C. covered in 100ft coils—2/9 a coil or four coils different colours, 10/- post free

FINE TUNERS
Ceramic trimmers all with ¼" spindles of fair length. 5, 10, 15, 30pF, all 2/3 each or 24/- per doz.


BAND III AERIAL

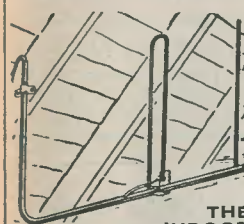

THE
INDOOR

This is a ¼ wave, 3 element array. Of all-alloy construction, the aerial is completely assembled and ready for instant mounting in loft, bedroom cupboard, window frame, etc. Price 12/6 plus 2/-

THE "ESTRONIC" BAND III CONVERTER

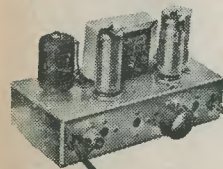


To-day's best value in Band III converters suitable for your TV or money refunded. Complete ready to operate, 59/6 non-mains, or 85/- mains post and insurance 3/6

THE CRISPIAN BATTERY PORTABLE



A 4-valve truly portable set with very many good features as follows: Ferrite rod aerials, low consumption valves, superhet circuit with AVC, ready built and aligned chassis if required, beautiful two-tone cabinet covered with I.C.I. Rexine and Tygan, guaranteed results on long and medium waves anywhere. All parts, including speaker and cabinet, are available separately, or if all ordered together the price is £7.15.0 complete, ready built chassis 30/- extra. Instruction booklet free with parts or available separately price 1/6.

AM/FM RADIOGRAM CHASSIS

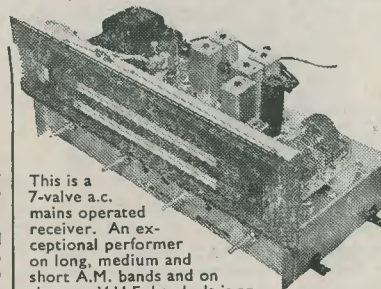

This is a 7-valve a.c. mains operated receiver. An exceptional performer on long, medium and short A.M. bands and on the new V.H.F. band. It is an ideal unit for a quality radiogram. Special features include magic eye tuning indicator, extra long scale and pointer travel—latest circuitry employing full a.v.c. feedback, etc., etc. Undoubtedly one of the finest AM/FM chassis available to-day. Chassis size 17½" x 6½" x 7½". Price £23.17.6, carriage, packing and insurance 20/- extra

GRAMOPHONE AUTO-CHANGERS


The latest models by very famous manufacturers. 3-speed with crystal turn-over pick-up, brand new and perfect, in original cartons. Prices from £7.19.6, carriage, ins., etc., 7/6



MULLARD
AMPLIFIER
"510"

A high quality Amplifier designed by Mullard engineers with a power output exceeding 10 watts. The price of the unit completely made up and ready to work is £12.10.0 plus 10/- carriage and insurance.


OFFICE INTERCOM

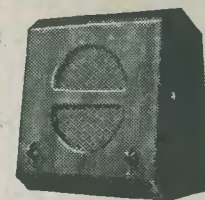


This is a very special offer of a master (two-station) unit using push-pull circuitry, operated from A.C. mains, and is complete in polished cabinet. Price only £4.19.6. Sub-stations 17/6 each

BAND III PRE-AMP

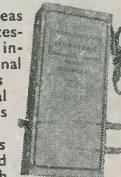In difficult areas it will be necessary to increase the signal level and this is the ideal unit for this purpose. It is A.C. mains operated and is fitted with input and output coax. plug. Price £4, post and packing 3/6




THE ARGONAUT AM/FM

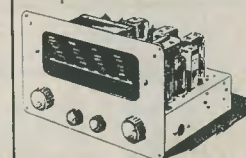

All parts are available and total cost is only £14.10.0 which includes drilled metal chassis and nine valves

THIS MONTH'S SNIP

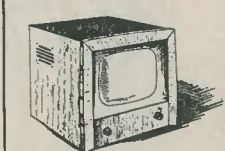

14" TV cabinet of the latest styling made for one of our most famous firms—beautifully veneered and polished—limited quantity. 19/6 each. Carriage and packing 3/6 extra

ELECTRONIC PRECISION EQUIPMENT LTD

Post Orders should be addressed to Dept. 34, 123 Terminus Road, Eastbourne

Personal shoppers, however, can call at

42-46 Windmill Hill
Ruislip, Middx.
Telephone RU1slip 5780
Half-day Wednesday

152-3 Fleet Street
E.C.4
Telephone FLEet 2833
Half-day Saturday

29 Stroud Green Road
Finsbury Park, N.4
Telephone ARChway
1049. Half-day Thurs.

249 High Rd., Kilburn
Telephone
MAIda Vale 4921
Half-day Thursday

G2AK THIS MONTH'S BARGAINS G2AK

THERE IS NO EXCUSE NOW

or not being on phone or for not having a nice clean signal

CRYSTAL HAND MICROPHONES

As illustrated, in silver hammer case with polished grille, handle and 4 feet screened lead. Only 21/- p. p.



COPPER WIRE: 14G, H/D 140ft, 15/-; 70ft, 7/6, post and packing 2/-. Other lengths pro rata.

KNOB AND DIAL with engraved scale 2" dia. New and boxed. White figures on black, complete with cursor, 1/9 each, post 6d. Ideal for portables and mobiles.

For the New MOBILE

12V miniature rotary transformers. Output 360/310V, 30mA c.s. or 70mA, I.C.A.S. Only 4 1/2" x 2 1/2" overall. ONLY 17/6 each, or 30/- for 2, post and packing 1/6

Carriage paid on all orders over £1 except where stated

POWER UNITS in black metal case. With input and output sockets. For 200/260V 50c input. Output 200/250V 60/80mA fully smoothed and fused. Also gives 31V 0.3A d.c. and 6.3V 3A a.c. fitted with 6X5 rectifier. 50/- each, carriage paid

FSK SOLARISCOPEs. Complete with charts, give world time, light and dark paths. Invaluable to the DX man. List 21/-. Our price 7/6 post free

PANL HOME CRACKLE. Black, 3/- tin, postage and packing 8d.

TWIN FEEDER: 300 ohm, twin ribbon feeder, similar K25, 6d. per yard. K35B Telcon (round), 1/6 per yard. Post on above feeder and cable, 1/6 any length

CERAMIC FORMERS, 2 1/2" x 1 1/2". Ideal for V.F.O. or turrets, 1/9 each or 17/6 doz.

CERAMIC SWITCHES. 2 bank, 2 pole, 4-way each bank, 5/- each, post and packing 9d.

PI CIRCUIT OUTPUT TUNING CONDENSERS. Made by E. F. Johnson Co., U.S.A. Max. cap. 500pF 1,500V rating. Ceramic insulation, size 5" long x 2 1/2" wide x 2 1/2" high, excluding spindle projection. Our price only 15/- post free

CONDENSERS 8µF, 600V trop, 750V normal. New ex-W.D. stock, 5/6 each, p. & p. 2/-

SHADED POLE MOTORS. Heavy duty type. Totally enclosed. Made for professional tape deck. Very limited quantity. Only 35/- each, p. and p. 2/-

RACK MOUNTING PANELS: 19" x 5 1/2", 7", 8 1/2" or 10 1/2", black crackle finish, 5/9, 6/6, 7/6, 9/- respectively, postage and packing 2/-

ABSORPTION WAVEMETERS: 3.00 to 35.00Mc/s in 3 switched banos. 3.5, 7, 14, 21 and 28Mc/s. Ham bands marked on scale. Complete with indicator bulb. A must for any Ham Shack. Only 15/- each, post and packing 1/-

Special Offers

CONDENSERS

8µF, 600V trop, 750V normal. New ex-W.D. stock, 5/6 each, p. & p. 2/-

SHADED POLE MOTORS. Heavy duty type. Totally enclosed. Made for professional tape deck. Very limited quantity. Only 35/- each, p. and p. 2/-

Please include small amount for orders under £1

CHAS. H. YOUNG LTD

ALL ORDERS TO 110 DALE END, BIRMINGHAM PLEASE PRINT YOUR NAME AND ADDRESS

MAIL ORDERS TO Dept. 'R,' 102 HOLLOWAY HEAD, BIRMINGHAM Midland 3254 Central 1635

VALVES

NEW TESTED AND GUARANTEED

1R5	7/6	6J5G	5/6	AZ31	10/6	EF37A	14/6
1S5	7/6	6J5GT	6/6	BL63	10/6	EF39	5/6
1T4	7/6	6K7G	6/-	DF91	7/6	EF55	9/6
354	7/6	6K8	8/6	DK91	7/6	EF80	10/-
3V4	7/6	6K8B	8/-	DAF91	7/6	EF85	10/6
5U4G	8/6	6K8GT	8/6	DL92	7/6	EF91	7/6
5Z4G	8/6	6L6G	9/6	DL94	7/6	EF92	4/9
6AG5	6/9	6Q7GT	8/6	DK92	7/6	EK32	8/6
6AM6	7/6	6SN7GT	8/6	DK96	9/-	EL32	7/6
6AL5	6/6	6SL7GT	8/-	EA50	1/6	EL84	11/-
6AT6	8/-	6S57	6/6	EB34	5/6	EM34	12/6
6BE6	8/-	6V6G	7/6	EB91	6/6	EY51	11/6
6BV6	8/-	6V6GT	7/6	EBC33	8/6	EZ35	8/-
6B8	7/6	6X4	8/-	EBF80	10/6	KT33C	9/6
6B8G	7/6	6X5GT	7/6	ECC81	10/6	KT66	11/6
6BA6	8/6	12AT7	9/-	ECH35	9/6	PL81	10/6
6BR7	8/6	12AU7	9/-	ECH81	10/6	PL82	10/6
6SA7	8/-	12AX7	8/6	ECH42	11/6	UCH42	11/6
6F6G	8/-	58	7/6	ECL80	10/6	PCC84	11/6
6F8G	8/6	807	6/9	EF22	7/6	X41	12/6
6G6G	4/9	5763	7/6	EF36	7/6	X65	10/6

Matched Pairs. EL84, 23/-; 6V6G and GT, 17/-; 6BV6, 18/-; KT33C, 19/6; 807, 14/6 per pair

Volume Controls. All valves, long spindle. L/S 3/-, SP 4/-, DP 4/6, ext. spkr. control, 3/-

W.W. Pots. Preset 3/-; 3W, long spindle 5/6, SP 6/6

Band III Converter Kits for Midland Litchfield Transmitter. Complete kit of parts, including ready wound coils, two EF80 valves, drilled chassis and wiring diagram. For a.c. mains 200-250V. £3 10s. 0d., p. and p. 1/6

As above less power pack components. Power required, 200V 20mA, 6.3V 0.6A. £2 5s. 0d., p. and p. 1/-

Teletron Band III Coil Set. Mk I 15/-; Mk II 17/6; Osmor Coil Set 17/6


Aerials. Band I from 13/6; Band II 17/6; Band III 6/6

Spare for Philips Radio and TV Receivers and most other makes supplied

P. and P. 6d. Over £1 post paid except where stated


R. COOPER G8BX 32 SOUTH END CROYDON SURREY CROYDON 9186

COMPLETELY BUILT SIGNAL GENERATOR

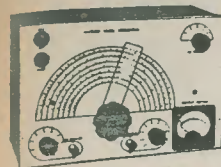

Coverage 120 Kc/s-320 Kc/s, 300 Kc/s-900 Kc/s, 900 Kc/s-2.75 Mc/s, 2.75 Mc/s-8.5 Mc/s, 8 Mc/s-28 Mc/s, 16 Mc/s-56 Mc/s, 24 Mc/s-84 Mc/s. Metal case 10" x 6 1/2" x 4 1/2". Size of scale 6 1/2" x 3 1/2". 2 valves and rectifier. AC mains 230-250V. Internal modulation of 400 c.p.s. to a depth of 30 per cent, modulated or unmodulated RF output continuously variable 100 milli-volts. CW and mod. switch, variable AF output and moving coil output meter. Black crackle-finished case and white panel. Accuracy ±2%. £4 19 6 or 34/- deposit and 3 monthly payments 25/- P. and p. 4/6 extra

PATTERN GENERATOR

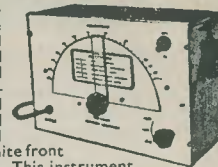

40-70 Mc/s direct calibration, checks frame and line timebase, frequency and linearity, vision channel alignment, sound channel and sound rejection circuits and vision channel band width. Silver-plated coils, black crackle-finished case 10" x 6 1/2" x 4 1/2" and white front panel. AC mains 200/250V. This instrument will align any TV receiver, accuracy ±1%. Cash price, £3 19 6 or 29/- deposit and 3 monthly payments of £1. P. and p. 4/6 extra

←Both generators guaranteed for 12 months ↑

COMPLETELY BUILT TV CONVERTER

for the new commercial stations, complete with 2 valves. Frequency can be set to any channel within the 186-196 Mc/s band. IF will work into any existing TV receiver between 42-68 Mc/s. Input arranged for 80 ohm feeder. EF80 as RF amplifier, ECC81 as local oscillator and mixer. The gain of the first stage RF amplifier 10db. Required power supply of 200 DC at 25mA, 6.3V AC at 0.6 amp. Input filter ensuring freedom from unwanted signals. Simple adjustments only, no instruments required for trimming. Will work into any TRF or superhet. Incorporating band switch and wire-wound gain control. Fully screened in black crackle-finished case, size 5 1/2" long, 3 1/2" wide, max. overall height 4 1/2". £2 19 6, p. & p. 2/6. As above with built-in power supply, £3 19 6, p. & p. 2/6. AC mains 200/250V

BAND III CONVERTER KIT

comprising 5 channel tuner, mains transformer, metal rectifier, electrolytic, 2 valves, 12AT7 and EF80, and all necessary components for a.c. mains operation. Complete with conversion data

£2.5.0 Post and Packing 2/6

Three-speed automatic changer B.S.R. Monarch, current model. Will take 7", 10" or 12" records mixed. Turnover crystal head. Brand new. A.C. mains, 200/250. £7 15 0, p. and p. 3/-

16" TUBE by famous manufacturer, brand new, guaranteed 3 months, EHT 14kV, heater 6.3V at 0.6A, £9 19 6, p. and p. and insurance, 22/6. H. P. terms arranged.

LINE EHT TRANSFORMER with built-in line and width controls, scan coil and frame output transformer, £2 19 6, p. and p. 3/- Focus unit to suit, 15/-

Used Metal Rectifier, 230V 50mA, 4/-, gang with trimmers, 6/6; M. & L. T.R.F. coils, 5/-; 3 Govt. valves, 3 v/h and circuit, 4/6; heater trans., 6/-; volume control with switch, 3/6; wave-change switch, 2/-; 32 x 32mfd., 4/-; bias condenser, 1/-; resistor kit, 2/-; condenser kit, 4/-

Line and EHT Transformer, 9kV, Ferrocast core, EY51 heater winding, complete with scan coils and frame output transformer and line and width control. P. and p. 3/-, 35/-

As above but complete with line and frame blocking transformers, 4 henry 250mA choke, 100 mfd and 150 mfd 350 wkg 380mA AC ripple. P. and p. 3/- £2 9 6

Standard Wave-change Switches. 4-pole 3-way, 5-pole 3-way, 3-pole 3-way, 1/9 each. 9-pole 3-way 3/6. Miniature type, long spindle 4-pole 3-way and 4-pole 2-way, 2/6 each. 2-pole 11-way twin water, 5/-; 1-pole 12-way, 5/- P. and p. 3d.

USED Metal Rectifier, 250V 150mA, 6/6

Combined 12" Mask and Escutcheon Perspex. New aspect, edged in brown. Fits on front of cabinet, 12/6 As above for 15" tubes, 17/6

Polishing Attachment for electric drills. 1/2" spindle, chromium-plated 5" brush, 3 polishing cloths and one sheepskin mop mounted on a 3" rubber cup. Post and pkg. 1/6. 12/6. Spare sheepskin mops, 2/6 each

Line or Frame Oscillator Blocking Transformers, 4/6 each. Smoothing Choke, 250mA, 5 henry, 8/6; 250mA, 10 henry, 10/6; Wide Angle PM Focus Unit vernier adj., state tube, 15/- PM Focus Unit for Mullard tubes with vernier adjustment, 15/-

Ion Traps for Mullard or English Electric tubes, 5/-, post paid

R. & TV COMPONENTS (ACTON) LTD

23 HIGH STREET ACTON LONDON W3

Where cost and packing charge is not stated, please add 1/6 up to 10/-, 2/- up to £1 and 2/6 up to £2. All enquiries SAE. Lists 5d. each

BAND III CONVERTER UNIT

Complete kit of parts for "Teletron" Converter. Including 2-EF80 and chassis and wiring diagram. Voltage required 200V 30mA, 6.3V 0.6A ... 48/6 plus 2/- p.p.
 Or assembled and tested... .. 67/6 plus 2/- p.p.
 Power supply components 22/-
 The Unit complete with power supply. Tested and ready to plug in 97/6

HIGH GAIN MODEL TELETRON Mk 2

Teletron Mk 2 coil set 17/6
 Additional resistors each 3d.
 Additional condensers each 9d.
 Valves, type PCF80 (tax paid) 12/6
 Valves, type PCC84 (tax paid) 12/6

Or the complete Mk 2 Kit at 59/6



QUARTZ CRYSTALS

TYPE FT243 fundamental frequencies 2 pin $\frac{1}{4}$ " spacing. 200 types in the following frequencies: 5675 Kc/s to 8650 Kc/s (in steps of 25 Kc/s); 5706 Kc/s to 8340 Kc/s (in steps of 33.333 Kc/s.) All brand new 10/- each. Special price for complete sets of 80 or 120. Above are suitable for regrinding.

TYPE FT241A 54th harmonic Crystals. 2 pin $\frac{1}{4}$ " spacing. 21.1 Mc/s, 21.2 Mc/s, 21.4 Mc/s, 21.5 Mc/s, 22.0 Mc/s, 22.8 Mc/s, 22.9 Mc/s, 23.2 Mc/s, 23.4 Mc/s, 26.0 Mc/s, 26.1 Mc/s, 26.4 Mc/s, 27 Mc/s. All brand new 7/6 each. FT241A 200 Kc/s 10/- each. FT241A 465 Kc/s 10/- each. Crystal Holders for both types 1/3 each



INDICATOR UNIT TYPE 182A

Unit contains VCR517 Cathode Ray 6" tube, complete with Mu-metal screen, 3 EF50, 4 SP61 and 1 5U4G valves, 9 wire-wound volume controls and quantity of resistors and condensers. Offered BRAND NEW (less relay) at 67/6 plus 7/6 carr. Radio Constructor scope circuit included.

CATHODE RAY TUBES

VCR139A. 2 1/2" C/R Tube. Brand new in original cartons (carr. free) £1 15 0
 VCR97. Guaranteed full T/V picture (carr. 2/-) £2 0 0
 VCR517C. Guaranteed full T/V picture MU-METAL SCREENS for VCR97 or 517 (P.P. 1/6) 10 0
 6" ENLARGER for VCR97 or 517 (P.P. 1/6) 17 6
 VCR97. Slight cut-off (carr. 2/-) 15 0
 3BP1 brand new £1 10 0

TRANSMITTER/RECEIVER "38" WALKIE TALKIE SETS

Complete with 5 valves, four VP23 and ATP4. These sets are not guaranteed but are serviceable. Circuit supplied. Freq. range 7.4 to 9 Mc/s. Range approx. 5 miles. 25/- Junction Box 2/6 extra

AN/APA.1 CATHODE RAY INDICATOR AMPLIFIER UNIT

Complete, comprising 3BP1 C.R.T., 7-6SM7gts, 1-6H6, 1-6G6, 1-2X2, 1-6X5 valves. Brand new. £4 19 6 plus carriage 7/6

RECORD CHANGERS

B.S.R. "Monarch," plays mixed records. 3-speed. Listed £16 10 0. Brand new £7 19 6

Post Free unless otherwise stated

SEND STAMPS FOR 28-PAGE CATALOGUE

62A INDICATOR UNIT

Containing VCR97 with Mu-metal screen, 21 valves: 12-EF50, 4-SP61, 3-EA50, 2-EB34. Plus pots., switches, H.V. cond., resistors, Muirhead S/M dial, double deck chassis and crystal. BRAND NEW ORIGINAL CASES, 67/6, carriage 7/6

U.S.A. INDICATOR UNIT Type BC929A

In black crackled cabinet 14 1/2" x 9" x 9". Complete with 3BP1 C/R Tube, shield and holder, 2 6SN7GT, 2 6H6GT, 1 6X5GT, 1 2X2, 1 6G6, V/controls, condensers, etc. Ideal for scope. Brand new, 65/-, carriage paid

PYE 45 Mc/s STRIP TYPE 3583 UNITS

Size 15" x 8" x 2". Complete with 45 Mc/s Pye Strip, 12 valves: 10 EF50, EB34 and EA50, volume controls, and hosts of resistors and condensers. New condition. Modification data supplied. Price 69/6, carriage paid

CRYSTAL MICROPHONE INSERTS

5/- POST FREE
 Ideal for tape recording and amplifiers. No matching transformer required

HENRY'S

(RADIO LTD)

SHOP HOURS

Mon.-Sat. 9 a.m.-6 p.m. Thursday 1 p.m.
 Telephone Paddington 1008/9 & 0401

5 HARROW ROAD LONDON W2

SMALL ADVERTISEMENTS

Readers' small advertisements will be accepted at 3d. per word, including address, minimum charge 2/-. Trade advertisements will be accepted at 9d. per word, minimum charge 6/-. If a Box Number is required, an additional charge of 1/- will be made. Terms: Cash with order. All copy must be in hand by the 8th of the month for insertion in the following month's issue.

PRIVATE

FOR SALE 1154B Transmitter and R109 receiver, 2 to 12 Mc/s, £4. Wakefield, 26 Lancaster Road, Basingstoke, Hants.

FOR SALE Quantity of radio and t.v. spares, over 50 new valves, £15 the lot. Quantity of radio and t.v. service manuals, £3. J. Lovewell, 15 Warrington Square, Dagenham, Essex.

FOR SALE R1155 receiver, power pack, output stage, speaker and circuit, £9. Phone Ewell 7257 evenings.

FOR SALE Meters 1.5mA, 15/-; 1 Megohm pots, 2/3; jack plugs G.P.O. type, 2/3; screened Mic transformers, 3/6. Box No. E111.

FOR SALE BC348R new and converted for Ham use. A.C. operation, S-meter, noise limiter, additional audio stage. Some spare valves, HS33 phones, circuit diagram and issue QST covering mods. £20 o.n.o. After 7 p.m. King, 233 Whittington Road, London, N.22.

FOR SALE Eddystone "750" perfect. Wanted, CR100. 41 Appleton Street, Northwich, Cheshire.

FOR SALE Experimenters surplus. Truvox Tape Deck in carrying case with speaker, amplifier, less power pack and valves, £15. R1155 with internal power supply etc., £6. Model D wavemeter, £6. VCR517, perfect, £1 or £25 the lot. 15 Dorian Road, Hornchurch, Essex.

FOR SALE CR100 coil pack (2 r.f. and f.c.) 4 gang capacitor and b.f.o. unit, 465 kc/s. Full Marconi manual, £2. Caxtons Practical Radio and Television, 4 vols., mint, 30/-. Robinson, 2 Kimberley Road, Cambridge.

FOR SALE Real "hot" communication receiver, rebuilt BC342N, with converters for Medium wave, 28 Mc/s, 21 Mc/s, amazing performance. Enquiries to F. W. Hardstone, 43 Shrubbery Road, Streatham, London, S.W. 16.

FOR SALE 18 inch 20 watt super power Bakers speaker, 15 ohms, cost £12 10s. 0d., almost new, £6. Moving coil microphone head 15 ohm, ideal middle frequencies, cost £6 15s. 0d., only £4. 6 Wetherby Close, Northolt, Middx.

WANTED The Radio Constructor, copies for January to December 1955, or bound volume required. Offers please to Box No. E112.

YOU GET FINE VALUE AT The Walk-around Shop

Admiralty Responder Unit W.4790. This receiver tunes from 160-182 Mc/s. Valve line-up VRI36 R.F., VR92 Mixer, VRI37 Osc., VR65's in 5 i.f. stages. Price 12/6. Each full valued. Post and packing 7/6

Miniature I.F. Strips. Size 10 1/2" x 10 1/2" x 3", frequency 9.72 Mc/s. Line-up 2 EF92's and 1 EF91 i.f. amps., EB91 DET/AGC, EF91 AGC amp and EF91 Limiter. Circuit supplied. Price, less valves, 8/- each, post paid.

62A Indicators. Ideal for conversion to oscilloscopes, TV units, etc. Containing VCR97, 12VR91 (EF50), 2 VR54 (EB34), 3 VR92 (EF50), 4 CV118 (SF61), slow motion dial, 13 pots, and scores of useful components. Size 8 1/2" x 11 1/2" x 18". Price £3.0.0 each plus 7/6 post and packing

Type 234 Power Units. Double smoothed 200-250V 505 input 240V 100mA 6.3 at 6 amps with voltmeter reading input and output voltages. Size 19" x 10" x 6 1/2". Standard rack mounting. Price £4.10.0 each plus 7/6 post and packing

Bendix I.F. Transformers. 1.63 Megs. Complete in cans, set of 2 new and boxed. Size 2" x 1 1/2" x 3 1/2". Price 5/- each, post and packing 1/6

Bendix Potted Audio Output Transformers. Complete with integral smoothing choke rating 4 1/2 watt 9,000 ohms primary, 600 and 4,000 ohms secondary. Size 4" x 1 1/2" x 2", new and boxed. Price 4/6 each, post and packing 1/6


Insulating Tape. Perfect condition, 1/2" wide, 25 yd reels. Foiled in tins. Price 1/3 each, post and packing 8d.

NOTE.—Orders and Enquiries to Dept. "R"

PROOPS BROS. LTD. Open all day Saturday
 52 Tottenham Court Road W1
 Hours 9-6 p.m. Thursday to 1 p.m. LAngham 0141

RADIO 39/6 CHASSIS

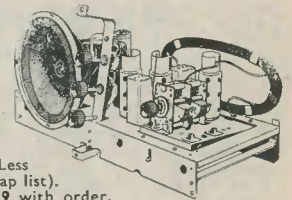3 w/band & gram. Extra speaker sockets, 5 valves international octal. Built-in portable aerial, 4 knob control. A.C. or universal optional. Less valves (see our cheap list). 8" P.M. speaker 7/9 with order. Set of knobs 2/-. Chassis 15 1/2" x 7" x 9" (when speaker is fitted). Carr. 4/6.



12" T.V. CHASSIS 97/6

Easily adapted to Band 3 (I.T.V.). Drawing 2/6 or FREE with order. Complete chassis by famous manfr. R.F. E.H.T. unit included. Owing to this chassis being in 3 separate units (power, t/base and s/vision inter-connected), it is easily fitted to table or console model. This chassis is less valves and tube. Ins. and carr: London 5/-, state B.B.C. channel—Provinces 10/-
RADIOGRAM CHASSIS, 29/9. Including 8" speaker, dial and knobs. 5 valve s/het. 3 w/band. A.C. mains. Complete. Guar. tested. Less valves. Ins. and carr. 4/6
POWER TRANSFORMERS, 15/9. 325-0-325V mains. 6V at 5A, 4V at 5A, 4V at 5A. Extra isolated winding for 2 or 4V tubes. Also similar trans. with 6V at 5A, 6V at 5A, 22V at 1 1/2A. Both are 250 mA. Plus post 2/-
MAINS TRANSFORMERS, 5/9. Heaters 6V and 5V. 350-0-350V, primary 200-250V. Post 2/-
MAINS POWER PACK UNIT, 29/9. 5kV E.H.T. 325V, 250mA. Smoothed h.t. heaters, 6V at 5A, 4V at 5A, 4V at 5A. Carr. 4/6.

DUKE & CO

621 ROMFORD ROAD LONDON E12
 Send 2 1/2d. stamp for FREE Catalogue Telephone GRA 6677

(continued on page 671)

CABINETS & HI-FI EQUIPMENT . .

We can supply any cabinet to your own specification


- The cabinet illustrated can be supplied in any shade of walnut, oak or mahogany for . . 19 gns.

We can supply and fit into any cabinet all the latest hi-fi amplifiers, tuners, transcription units, record changers, speakers, etc.

Send for free illustrated catalogue of cabinets, chassis, autochangers and speakers, etc. H.P. can be arranged

LEWIS RADIO COMPANY

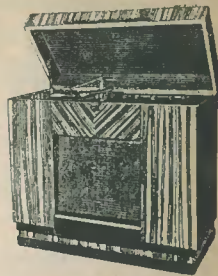120 GREEN LANES . PALMERS GREEN . LONDON N13



Telephone BOWes Park 6064

Build the Kitchen Receiver } £6-9-6
All components

£4-15-0 } All components (less valves)
Chassis undrilled

Our catalogue (price 3d) is reviewed in this issue

R. F. AGELSTON
46 Hardwicke Rd. London N13

GUARANTEED VALVES — Over 3,000 in Stock

6AM6, 6C4, EF92, 6AL5, EAC91, 6J6 ... 5/-
12AT7, 12AX7, 6AK5, 6F33, EC91, EL91, 6SN7, 6SL7,
6SK7, 6SJ7, R10, 6BA6, 6F17, 6CH6, 6BW6 ... 7/6
12AU7, 2D21 ... 9/-

A. A. W. SKILLMAN
74 FRANCHISE STREET : WEYMOUTH

17" TV TUBES 14"

★ 6 MONTHS GUARANTEE ★

17" £7.10.0 RECTANGULAR. Tetrodes and Triodes. All popular makes and types. Ins. & carr. 15/6
14" £5.10.0 RECTANGULAR. Latest types on all makes available. Ins. and carr. 15/6
12" £5 ROUND. State make and type required. If possible state equivalent second choice. Due to very heavy demand for some makes. Ins. and carr. 15/6
6 months Mullard, 3 months other types

SPRING CLEARANCE OF GUARANTEED BARGAINS

9" 16/6 Type 22/18 with slight burn. FREE post
12" 50/- Types, T12/72, T12/44. Tested, guaranteed 3 months. Ins. and carr. 15/6
12" 12/6 Types 121K, 12XP4, 31/14C. Slight burn. Ins. and carr. 15/6
14" £5 Types 141, 142. Round Mazda's, 3 month guarantee. Ins. and carr. 15/6
15" £5 Types 151, 152A or B. Round, 3 month guarantee. Ins. and carr. 15/6
16" £5 Type 41/1. 3 month guarantee. Ins. and carr 15/6

As we have been selling for the past 5 years All enquiries welcomed. Please send cash with order

Send 2½d. stamp for FREE Catalogue

MONEY BACK GUARANTEE **DUKE & CO** CWO OR COD
621 ROMFORD RD. LONDON, E.12. Tele: GRA 6677

H.A.C. SHORT-WAVE EQUIPMENT
Suppliers for over 18 years of Radio S.W. Receivers of Quality One-valve Kit, price 25/- . Two-valve Kit, price 50/- . Improved designs with Denco coils. All kits complete with all components, accessories and full instructions. Before ordering, call and inspect a demonstration receiver, or send stamped addressed envelope for descriptive catalogue.
H.A.C. SHORT-WAVE PRODUCTS (DEPT. R)
11 OLD BOND STREET LONDON W1

BRASS, COPPER, DURAL ALUMINIUM, BRONZE
ROD, BAR, SHEET, TUBE, STRIP, WIRE
3,000 STANDARD STOCK SIZES
No Quantity too Small List on application
H. ROLLET & CO. LTD.
6 Chesham Place SW1 Telephone SLOane 3463
also at Liverpool Birmingham Manchester Leeds

"FM TUNER UNITS

for Fringe and Local Area Reception"

This booklet, now in its Second Edition, includes a description of a **Suitable Tuning Indicator** and of **The Osram 912 High Fidelity Amplifier**.
32 pages with art board cover, price 2s. 2d., post paid

DATA PUBLICATIONS LTD
57 Maida Vale London W9
Telephone CUNningham 6141 (2 lines)

SMALL ADVERTISEMENTS

(continued from page 669)

PRIVATE

WANTED *The Radio Constructor*, Volume 7. Offers to Box No. E110.

WANTED Wearite Tape Deck, two or three heads, also 20,000 ohms/volt multimeter. Fg. Off. D. W. Hopper, Officer's Mess, Royal Air Force, Binbrook, Lincs.

JERSEY HOLIDAY. Near sea, town centre. Ham shack. Photo darkroom. SAE please for brochure. GC3KPO. "The Lincoln," 3 Saviours Road, Jersey.

TRADE

TAPE RECORDINGS transferred to disc. 78's and L.P.'s. Queensway Recording Studios, 123 Queensway, London, W.2. Telephone BAY 4992.

I.P.R.E. PUBLICATIONS. 5,500 alignment peaks for superhets, 5/9. Sample copy *The Practical Radio Engineer*, 2/-. Membership examination particulars, 1/-. Syllabus of TV and Radio Courses free and post free. Secretary, I.P.R.E., 20 Fairfield Road, London, N.8.

GOVERNMENT SURPLUS ILLUSTRATED CATALOGUE No. 12, containing over 400 items of electrical, mechanical and radio equipment for experiments, etc., price 1/6 post free. Arthur Sallis, 93 North Road, Brighton, Sussex.

JOIN THE INTERNATIONAL S.W. LEAGUE. Free Services to members including Q.S.L. Bureau, Translation, Technical and Identification Depts.—both Broadcast and Fixed stations, DX Certificates, contests and activities for the SWL and Transmitting members. Monthly magazine, "MONITOR" containing articles of general interest to Broadcast and Amateur SWL's, Transmitter page and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership, including monthly magazine, etc., 12/6 per annum. Secretary, ISWL, 86 Barrenger Road, London, N.10.

BUILD YOUR OWN TV and learn about its operation, maintenance and servicing. Qualified engineer-tutor available whilst you are learning and building. Free brochure from E.M.I. Institutes, Department R.C. 58, London, W.4 (associated with H.M.V.).

LEARN AS YOU DO IT—we provide practical equipment combined with instruction in radio, television, electricity, mechanics, chemistry, photography, etc. Write for full details to E.M.I. Institutes Department R.C. 47, London, W.4.

OSMOR—for efficient coils, coilpacks, etc. Send 5d. stamp for FREE circuits and lists. Dept. R.C.C., Osmor Radio Products Ltd. 418 Brighton Road, South Croydon, Surrey. Telephone Croydon 5148/9.

NEW SURPLUS . . .

0Z4A	6/-	6K7G	5/-	813	60/-	EM80	9/6
1A3	4/6	6K7GT	6/6	832	30/-	EY51	11/6
1C2	8/6	6K7M	6/6	CV286	7/6	EZ40	8/6
1L4	4/6	6K8M	9/6	CV287	7/6	EZ80	7/6
1LN5	4/6	6L7M	7/6	DL33	9/6	PCC84	11/6
1R5	8/6	6Q7GT	8/6	DAF96	9/6	PCF80	12/6
1S5	7/6	6SA7M	7/6	DF96	9/6	PCF82	12/6
1T4	7/6	6SG7M	6/6	DK96	9/6	PL81	11/6
2A3	7/6	6SK7M	6/6	DK92	8/6	PL82	9/6
3A4	6/6	6SL7GT	7/6	EAS0	2/-	PL83	11/6
3D6	5/-	6SN7GT	6/6	EABC80		PLC83	12/6
3Q5GT	9/6	6SQ7M	8/6		10/-	PY80	10/-
3S4	7/6	6V6GT	7/6	EAF42	10/6	PY81	10/-
3V4	8/6	6V6M	9/6	EBC33	6/6	PY82	9/6
5R4GY	12/6	6X4	7/6	EBF80	10/6	R19	12/6
5U4G	8/6	6X5GT	7/6	EB91	6/-	TT11	4/-
5Y4G	6/6	7B7	9/-	EBC41	10/6	UAF20	25/-
5Z4G	8/6	7C5	9/-	ECC81	10/6	SP61	3/-
6AC7M	6/-	7C6	9/-	ECC82	10/6	UAF42	10/6
6AG7M	9/-	7Y4	8/6	ECC83	9/6	UBC41	10/6
6AK5	6/6	12A6M	7/6	ECC84	13/6	UL41	10/6
6AL5	6/-	12AU6	9/-	ECC8Z	13/6	UCH42	10/6
6AM6	6/-	12AH8	12/6	ECH35	9/6	UY41	8/6
6AQ5	8/6	12BE6	8/6	ECH42	10/6	VR105/30	
6AT6	8/-	12J7GT	9/-	ECH81	10/6		7/6
6AU6	8/6	12K7GT	9/-	ECL80	10/6	VR150/30	
6B8G	5/-	12K8GT	9/-	EF50	4/-		7/6
6BA6	8/6	12Q7GT	9/-	EF50(S)	6/-	VS110A	4/6
6BE6	7/6	12SC7M	6/6	EF36	4/-	VT62	10/-
6BJ6	7/6	15D2	4/6	EF39	5/-	W77	5/-
6BS7	7/6	20L1	10/6	EF41	10/6	X66	7/6
6BW6	7/6	35L6GT	9/6	EF80	10/-	XPI.5	3/-
6C4	5/-	35Z4GT	9/6	EF86	12/6	Z77	6/-
6CH6	6/6	50L6GT	8/6	EF91	6/-	DL96	9/6
6F8G	4/6	80	9/6	EF92	5/-	12AU7	8/6
6G6G	3/6	220P	3/-	EL32	4/-	866A	12/6
6J5M	5/-	807	7/6	EL41	10/6	5763	9/6
6J6	5/-	808	25/-	EL84	10/6	HK24G	25/-

Moulded Valveholders. B7G, B9A, B8A, 9d. each. B7G, B9A with screening cans, 1/6 each. Int. octal 9d. B9A pack. 6d.
"PANL" Crackle Paint. Black, brown, green, 3/- tin
Midget Mains Trans. (same size as std. spkr. o/p). Input 230/250V, o/p 250V 20mA, 6.3V 0.6A, 10/6 each, post 1/3
Midget 465 kc/s I.F.s. Iron dust cored, high 'Q'. 1½" x ¾" sq., 9/6 pair
Chokes. 50H, 20mA, res. 1,200 ohms, 6/- each
M.C. Speakers. 6½", 3 ohm, 19/6 each, post 1/3
Electrolytics. Can 100 mfd 450V wkg, 5/-; 60+100 mfd 275V wkg, 6/-; 32+32 mfd 450V wkg, 6/-; 32+32 mfd 350V wkg, 5/-; 16+16 mfd 350V wkg 4/-; wire end 8 mfd 450V wkg, 2/-; 16 mfd 450V wkg, 2/9; 20 mfd 500V, 2/9; 25 mfd 25V wkg, 1/6

SPECIAL
Triplet Multi-range Foundation Meters
Scaled for volts, ohms and mA. 2½" rectangular dial. FSD 400 microamps. Int. res. 500 ohms. Complete with engraved top plate. Brand new, only 27/6 each, post paid

M.C. Meters. Flush round plug-in type, 2", 0-500 microamps (scaled 0-10V), 17/6. Ditto 2½", 0-250 microamps, 22/6. 2" round flush 0-25V 0-30mA (both 5mA basic), 6/6 each. 2" sq. fl., 0-50mA, 0-150mA, 0-500mA (RF T/C), 7/6 each; 0-300V, 9/6; 50-0-50A, 10/6. 3½" rd. fl. (2½" dial), 0-30mA, 0-200mA, 0-500mA, 0-15V (MI cal. at 50 cps), 0-2A, 12/6 each
Metal Rects. FW Bridge. 12V 1A, 7/6; 2A, 10/6; 4A, 17/6; 6A, 25/-; 2mA FW instrument type, 5/6; 6V ½A half-wave, 2/6

We regret we cannot accept orders from Eire or Overseas Post/Packing Under 10/- (9d.), 20/- (1/3), 40/- (2/-). Free over 40/-

JOHN ANGLIN
160 CLEETHORPE ROAD GRIMSBY LINC'S
Telephone 56315

(continued on page 672)

CRACKLE

Panel air-drying crackle has been used for many years by constructors, and most radio component dealers stock this popular finish as a regular line. Under air-drying conditions Panel is slow in hardening, but the hardening time can be considerably speeded up with the aid of an ordinary domestic gas oven. We feel this information will be of interest to manufacturers for prototype and test instrument finishing.

The work should be left to crackle according to the instructions printed on the label, OR place in the gas oven with the gas turned as low as possible and the door left wide open. When the crackle is complete and surface dry, proceed as follows:

Bake at 90 deg. F. approx. (Regulo 3) for one hour, or 150 deg. F. approx. (Regulo 5) for half-hour, with the oven door closed. (The times and temperatures are not critical.) Allow to cool, when the surface will be rock hard and ready for working on.

Panel is available in black in 1/8th pint cans at 3/-. Other sizes to special order. Trade and wholesalers' terms available.

If unable to obtain locally send 3/6 to:

G. A. MILLER 8 Kenton Park Crescent
Kenton Middlesex

PANL

SMALL ADVERTISEMENTS

(continued from page 671)

TRADE

TELEVISION INTERFERENCE. Receiver filters: High-Pass E.5037, 30/-; Low-Pass E.5031, 30/-; Composite Band 1/III, 49/6. Transmitter filter: E.5034 80dB 1kW. £6. Labgear (Cambridge) Ltd., Willow Place, Cambridge.

TV AERIALS Lashing sets, J. & U. bolts; Pole clamps, etc. SAE for list. BCM/SILEC, London, W.C.1.

MAINS TRANSFORMERS, 3/9. 350-0-350V, heaters 12 and 4V, primary 100-250V. Ideal auto-trans. Post 2/- Duke & Co., 621 Romford Road, London, E12.

MAINS TRANSFORMERS, 5/9. 350-0-350V, heaters 4 and 4V, primary 200-250V. Post 2/- Duke & Co., 621 Romford Road, London, E12.

BLUEPRINTS. High Gain 10 metre converter, with a de luxe circuit comprising EF91 r.f. stage, ECC91 double triode mixer and oscillator, EF92 i.f. amplifier, with stabilised voltage supply via a 7475. 1/8 post free with full instructions. Data Publications, 57 Maida Vale, London, W.9.

MULLARD 3 valve, 3 watt, high fidelity audio amplifier, featured in April issue, full sized blue print, 2/8 post paid. Data Publications, Ltd., 57 Maida Vale, London, W.9.

COILS, COILS, COILS. We can supply coils for all frequencies, r.f. chokes, etc. Send SAE for circuits and data. The Teletron Co., 266 Nightingale Road, London, N.9.


CONSTRUCTORS build these at low cost!

PERSONAL PORTABLE RADIO

30/-

Post Free

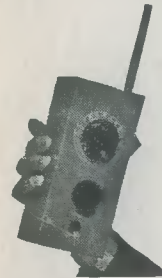This little set was designed to give you a real personal portable radio that you can enjoy anywhere without disturbing others. Ideal for the holiday, hiking, fishing, camping, cycling, etc. Use it at home, at the office, in bed, or just anywhere.



Send 2/- for layout, wiring diagram and components price list.

PRESELECTOR

Component parts for this unit, specially designed to suit the ALL-WAVE RADIO, are available as follows:

Panel and Chassis	3/6
Coil Holder	9d.
Coil to cover reqd. range 10-23, 20-43, 40-100 and MW range	each 3/6
954 Valve	3/-
Valveholder	2/-
0.00016µF Condenser	4/-
RF Choke	2/-
Variable potentiometer	3/-
Suitable resistors	2/6
Suitable condensers	2/6

POWER UNIT TYPE PUI


An ideal power supply for both these receivers and the Pre-selector. Also for inclusion in Test Equipment. 120V at 25mA. 6.3V at 1.5A.

32/6

ALL-WAVE RADIO


30/-

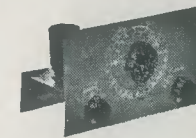Ideal for the beginner or for those requiring a simple standby receiver.



This 1 valve S.W. receiver can be built for 30/- from our list of components, which can be purchased separately. It includes valve and 1 coil covering 20-40 metres. Provision is made to increase to 2 or 3 valves if required, and all components are colour-coded so that the beginner can build this set quite easily. Send 2/- for specification, wiring diagram, layout and price list.

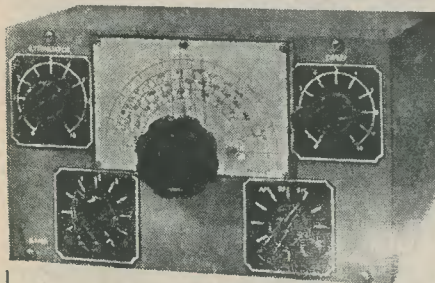R.C.S. PRODUCTS (RADIO) LTD
11 OLIVER ROAD (Mail order only) LONDON E17



For a really professional finish use . . .

PANEL-SIGNS TRANSFERS

Set No. 1: Receivers and Amplifiers
Five sheets 8½" × 5½" containing one large scale, twelve control panels and wording. 3s. 6d. Postage 2d.

Set No. 2: Test Instruments
Five sheets 8½" × 5½" containing two medium scales, twelve control panels and wording. 3s. 6d. Postage 2d.

Set No. 3: Wording
Wording for Receivers, Amplifiers, Transmitters, Test Equipment and other Radio Apparatus.
4 Sheets, Approx. 400 words, 2s. 6d. Postage 2d.

Panel-Signs Transfers Fixing Varnish
1s. per bottle. Postage 4d.

Trade Enquiries Invited

Published by **DATA PUBLICATIONS LTD**
57 MAIDA VALE · LONDON W9

Telephone CUNningham 6141 (2 lines)

Telegrams Databux London

YOU CAN RELY ON US

We specialise ONLY in radio and electronic components, a comprehensive stock of which are held by us, to supply Government, educational and commercial laboratories. Can we be of some help to you, the experimenter and constructor? ?

QUALITY AMPLIFIER KITS

IN STOCK

ALL SPECIFIED PARTS FOR

MULLARD 3 WATT QUALITY AMPLIFIER
INCLUDING WYNALL TRANSFORMERS
MULLARD 510, F.M. UNIT, PRE-AMP
20 WATT AMPLIFIER

OSRAM 912, PASSIVE UNIT, PRE-AMP, F.M. UNIT

TRANSFORMERS FROM STOCK—
WYNALL, PARTRIDGE, GILSON, W.B., ELLISON

Detailed Price List Available on Request New Catalogue No. 14 on Request

Next to South Ealing Tube Station 65 Bus

82 SOUTH EALING ROAD
LONDON W5 Telephone EAL 5737

RADIO SERVICING CO