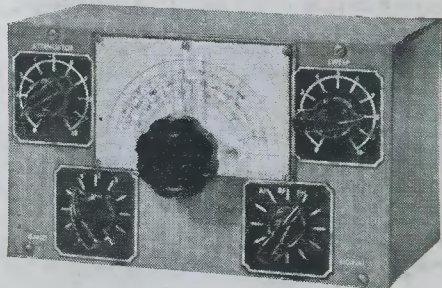


23

PUBLISHED IN CONJUNCTION WITH
THE
RADIO CONSTRUCTOR

Panel-Signs

Transfers



Set No. 1—RECEIVERS AND AMPLIFIERS

Five sheets $8\frac{1}{2}$ in x $5\frac{1}{2}$ in, including one large scale 6in x 4in (0-100 graduations in 4 bands), twelve control panels $1\frac{1}{8}$ in x $1\frac{1}{8}$ in, and two sheets of white wording, figures and symbols.

Set No. 2—TEST EQUIPMENT

Five sheets $8\frac{1}{2}$ in x $5\frac{1}{2}$ in, containing two medium scales 4in x $2\frac{3}{4}$ in approx. (may be "married" for R-C Bridges), twelve control panels $1\frac{1}{8}$ in x $1\frac{1}{8}$ in, and two sheets of white wording, figures and symbols.

Set No. 3—WORDING

Five sheets, including four of appropriate wording, for Receivers, Amplifiers, Transmitters, Test Equipment, and other Radio Apparatus. Also included are Transistor symbols, six alphabetic sets A-Z, and six sets of figures 0-9. One sheet of Station Names. Over 750 words and symbols in all. White, no background.

Set No. 4—WORDING

As Set No. 3, but wording in black.

(Each Set is contained in a strong envelope giving full instructions for fixing)
All Panel-Signs Transfers 3/6 per Set. Postage 2d.

DATA PUBLICATIONS LTD

57 MAIDA VALE LONDON W9

Telegrams Databux London

Telephone CUNningham 6141/2

Published in Great Britain by the Proprietors and Publishers
Data Publications Ltd 57 Maida Vale London W9

Printed by A. Quick & Co. (Printers) Ltd 125 High Holborn London WC1 England also at Clacton-on-Sea
Obtainable abroad through the following Collets Subscription Service Continental Publishers & Distributors Ltd
William Dawson & Sons Ltd Australia and New Zealand Gordon & Gotch Ltd South Africa Central News Agency
Holland "Radio Electronica"
Registered for transmission by Magazine Post to Canada (including Newfoundland)

THE JASON OG.10 GENERAL PURPOSE 'SCOPE, Part 2

VOLUME 13
NUMBER 2
SEPTEMBER
1959

The
**RADIO
Constructor**



RADIO · TELEVISION · AUDIO · ELECTRONICS

The **TOURIST**
Portable Receiver



The **MAJOR THREE**
Personal Transistor
Receiver

Included in this issue

TESTMETERS AND THEIR CIRCUITS
SIMPLE BURGLAR ALARM
RECEIVER OUTPUT MATCHING BOX
LINE OUTPUT FAULTS
UNDERSTANDING TELEVISION, contd.

DATA
Publications **1'9**

THE MODERN BOOK CO

The Radio Amateur's Handbook. 1959. By A.R.R.L. 32s. 6d. Postage 1s. 9d.

TV Fault Finding. A Data Publication. 5s. Postage 6d.

How to Get the Best out of Your Tape Recorder. By P. J. Guy. 8s. 6d. Postage 8d.

The Practical Hi-Fi Handbook. By G. J. King. 25s. Postage 1s.

Radio Handbook. 15th ed. 1959. 58s. 3d. Postage 1s. 9d.

An Electronic Organ for the Home Constructor. By A. Douglas. 15s. Postage 1s.

Practical Robot Circuits. By A. H. Bruinsma. 17s. 6d. Postage 6d.

Model Radio Control. By E. L. Safford, Jr. 21s. Postage 9d.

British Transistor Manual. By E. N. Bradley. 12s. 6d. Postage 9d.

Stereo: How it Works. By H. Burstein. 23s. Postage 1s.

Building the Amateur Radio Station. By J. Berens. W2PIK. 22s. Postage 1s.

Brimar Valve and Teletube Manual. No. 8. 6s. Postage 9d.

Television Engineers' Pocket Book. By J. P. Hawker. 12s. 6d. Postage 8d.

Radio Valve Data. 6th Ed. Compiled by "WW". 5s. Postage 9d.

We have the Finest Selection of British and American Radio Books in the Country
Complete catalogue 6d.

19-23 PRAED STREET (Dept RC) LONDON W2

Telephone PADdington 4185



ETCH-YOUR-OWN **21/-**
PRINTED CIRCUITS post free

First All British Kit for Home or Laboratory use


PROOPS BROS. LTD. Open all day Saturday
Dept R, 52 Tottenham Ct. Rd. W1
Hours 9-6 p.m. Thursdays 9-1 p.m. Telephone LANgham 0141

● Make printed circuits to suit any wiring arrangement simply and speedily at home or in the laboratory. Etch-Your-Own kits provide the complete answer to chassis and wiring problems in transistor and other miniature layouts. Losses and stray capacities are cut to a minimum. Exact duplication of prototypes can be ensured.

● Each kit contains more than sixty square inches of laminated board and sufficient chemicals to make dozens of printed circuits: additional laminated board can be supplied to order. All materials are of high quality, completely safe to handle, and are carefully prepared to ensure fine definition and consistently satisfactory results without laboratory technique or precision control.

● Etch-Your-Own kits do not require special skills or additional equipment. Errors can be corrected at any stage prior to etching and the entire process can be completed in less than one hour.

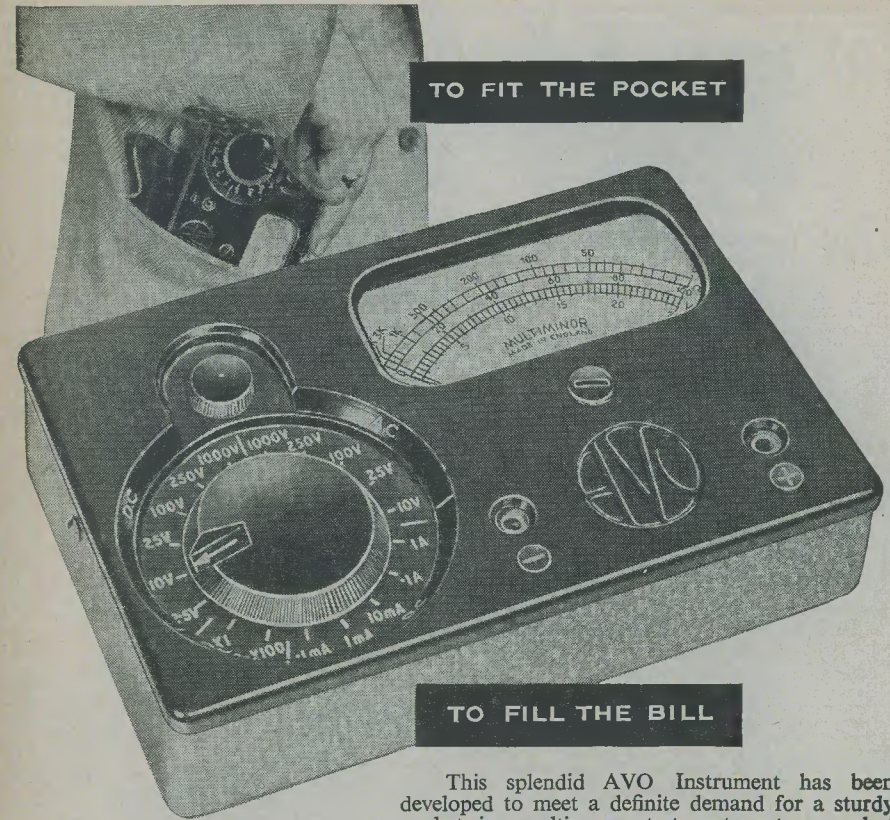● Supplied complete with comprehensive instruction book containing advice and illustrated examples on translating schematics into printed circuit layouts, soldering techniques, etc. Fully guaranteed.



TO FIT THE POCKET

TO FILL THE BILL

19 Ranges

D.C. Voltage	A.C. Voltage
0-100mV	0-10V
0-2.5V	0-25V
0-10V	0-100V
0-25V	0-250V
0-100V	0-1000V
0-250V	
0-1000V	

Resistance	D.C. Current
0-20,000Ω	0-100μA
0-2MΩ	0-1mA
	0-10mA
	0-100mA
	0-1A

Sensitivity
10,000 Ω/V on D.C. voltage ranges
1,000 Ω/V on A.C. voltage ranges

Accuracy
3% of full scale value on D.C.
4% of full scale value on A.C.

To meet special requirements, instruments can be supplied to a higher degree of accuracy for a small additional charge.



AVO Ltd. AVOCET HOUSE · 92-96 VAUXHALL BRIDGE ROAD · LONDON · SW1

Telephone VICtoria 3404 (12 lines)

This splendid AVO Instrument has been developed to meet a definite demand for a sturdy pocket-size multi-range test meter at a modest price, suitable for use on modern electronic apparatus as well as for radio and television receivers, motor vehicles, and all kinds of domestic appliances and workshop equipment. Readings are obtainable quickly and easily on a very open scale, and range selection is by means of a robust clearly marked rotary switch of the characteristic AvoMeter type. Measurements of A.C. and D.C. Voltage, D.C. Current and Resistance are made by means of only two connection sockets.


THE MULTIMINOR

List Price: **£9 : 10s.**

complete with Test Leads and Clips
Leather Case if required 32/6

Size: 5½ x 3½ x 1½ inches
Weight: 1lb approx.

Write for fully illustrated pamphlet

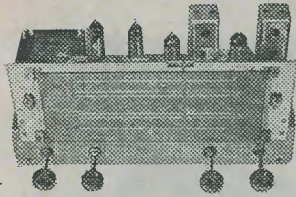

1959 RADIOGRAM CHASSIS

THREE WAVEBANDS
S.W. 16 m.-50 m.
M.W. 200 m.-550 m.
L.V. 800 m.-2,000 m.
12 month Guarantee. A.C. 200/250V, 4-way switch. Short-Medium-Long-Gram, A.V.C. and negative feedback. 4.2 watts. Chassis 13 1/2" x 5 1/2" x 2 1/2". Glass dial, horizontal or vertical, size 10" x 4 1/2". 2 pilot lamps. Four knobs, walnut or ivory, aligned and calibrated. Chassis isolated from mains. Immediate delivery.

BRAND NEW £9.10.0 Carr. 4/6

TERMS: Deposit £5.5.0 and 5 monthly payments of £1
MATCHED SPEAKERS: 8" 17/6. 10" 25/-, 12" 30/-

LATEST "E.M.I." 4 SPEED SINGLE RECORD PLAYER

Acos 73 Hi-Fi Stereo and Normal Xtal Pick-up
Silent Motor, Heavy Turntable

Special offer **£6.19.6** post 3/6

BUILD THIS REPRODUCER BARGAIN SPECIAL SINGLE PLAYER KIT

COLLARO 4-speed Gram-Pick-up Unit £4.10.0
Handsome portable case 17 1/2" x 13 1/2" x 7" with room to play 12" records £2.5.0
Ready built 3-watt amplifier with two valves and 7" ellip speaker, printed circuit £3.12.6

or **£9.15.0** complete kit post free

I.F. TRANSFORMERS 7/6 pair

465 kc/s slug tuning miniature can 2 1/2" x 1" x 1". High Q and good band width. By Pye Radio. Data sheet supplied.
Wearite M800 Midget I.F.S. 465 kc/s 12/6 pair
Wearite 550 Standard I.F.S. 465 kc/s 12/6 pair

New boxed Valves 95-day Guarantee

1R5	8/6	6K8G	8/6	EA50	1/6	EZ80	8/6
1S5	8/6	6L6G	10/6	EABC8010/6		E1148	1/6
1T4	8/6	6N7M	7/6	EB91	6/6	HABC80	12/6
2X2	2/6	6Q7G	10/6	EBC33	8/6	HVR2A	7/6
354	8/6	6SA7	10/6	EBC41	10/6	MU14	10/6
3V4	8/6	6SI7M	10/6	EBCF80	10/6	P61	6/6
5Y4	8/6	6SN7	7/6	ECC84	12/6	PCC84	12/6
5U3	8/6	6V6G	7/6	ECCF80	11/6	PCF80	11/6
5Z4	10/6	6X4	7/6	ECH42	10/6	PCF82	11/6
6AM6	8/6	6X5	7/6	ECL80	12/6	PCL82	11/6
6B6	5/6	7S7	10/6	ECL82	12/6	PLN25	6/6
6BE6	7/6	12AT7	10/6	EF39	7/9	PL82	10/6
6BH6	10/6	12AU7	9/6	EF41	10/6	PY80	8/6
6BW6	10/6	12AX7	9/6	EF50	5/6	PY81	10/6
6D6	7/6	12BE6	9/6	EF50	8/6	PY82	8/6
6F6	7/6	12K7	8/6	Sylv.		SP61	5/6
6H6	3/6	12Q7	8/6	EF80	10/6	UBC41	10/6
6I5	6/6	35L6	9/6	EF92	5/6	UCH42	10/6
6J6	7/6	35Z4	9/6	EL32	5/6	UF41	10/6
6J7G	8/6	80	10/6	EL84	10/6	UL41	10/6
6K6GT	6/6	807	6/6	EY51	12/6	UY41	8/6
6K7G	5/6	954	1/6	EZ40	8/6	U22	10/6

STOP PRESS B.B.C. TV Pocket Transistor. M.W. & L.W. Radio Kit 32/6.
'Phones 7/6. Ardent deaf aid earpiece 12/6. Special lead and plug 2/6. Continental OC71 7/6.

Our written guarantee with every purchase

C.R.T. ISOLATION TRANSFORMERS

For Cathode Ray Tubes having heater cathode short circuit and for C.R. Tubes with falling emission, full instructions supplied. Type A. Low leakage windings. Optional 25% and 50% boost on secondary; 2V, or 4V, or 6.3V, or 10.3V, or 13.3V, with mains primaries, 12/6. Our Latest Superior Product. Mains Input Type A2. High quality low capacity 10-15pF. Optional boost 25%, 50%, 75%, 16/6 each. Type B. Mains input. Low capacity. Multi output 2, 4, 6.3, 7.3, 10 and 13V. Boost 25% and 50%. This transformer is suitable for all TV tubes. 21/- each.

RESISTORS. Preferred values. 20% 10 ohms to 10 meg. 1/2W 4d., 1W 4d., 1W 6d., 1 1/2W 8d., 2W 1/-.
HIGH STABILITY. 1/2W 1%, 2/- All preferred values 100Ω-10MΩ. Ditto 5% 100Ω-5MΩ 9d. each.

WIRE-WOUND RESISTORS
5 watt } 1/3
10 watt } 1/6
15 watt } 2/-
25 ohms-10,000 ohms

15,000 ohms-50,000 ohms, 5W, 1/9; 10W, 2/3.
WIRE-WOUND POTS 3W Lab. Colvern, etc. Pre-set min. TV type. Standard size Pots, 2 1/2". Knurled slotted knob. Spindle, high grade. All values 25 ohms to 25k, 3/- each, 30k, 50k, 4/-; 6/6; 100k, 7/6. Ditto 1/2W Carbon Track 30kto 2 Meg, 3/-; W/W EXT. SPEAKER CONTROL 10Ω, 3/-

MAINS TRANSFORMERS—200/250 AC
STANDARD 250-0-250, 80mA, 6.3V tapped 4V 4A, Rectifier 6.3V 1A tapped 5V 2A and 4V 2A 22/6
Ditto 350-0-350 22/6
MINIATURE. 200V 20mA, 6.3V 1A 10/6
MIDGET. 250V 45mA, 6.3V 2A 15/6
SMALL. 250-0-250V 100mA, 6.3V 3.5A 19/6
STANDARD. 250-0-250, 65mA, 6.3V 3.5A 17/6
HEATER TRANS. 6.3V 1 1/2A 7/6
Ditto tapped sec. 2, 4, 6.3V 1 1/2A 8/6
Ditto, sec. 6.3V 3A 10/6
Mullard "510" Osram "912" 300-0-300, 120mA, 6.3V 4A c.t., 6.3V 2A tapped 5V 38/6

O/P TRANSFORMERS. Heavy duty 50mA, 4/6. Multi-ratio push-pull, 7/6. Miniature 3V4, etc., 4/6. Small pentode, 4/6. Hygrade push-pull 7 watts, 15/6. Heavy duty 10/20V 6k or 8k c.t., 30/-.
L.F. CHOKES 15/10H 60/65mA, 5/-; 10H, 85mA, 10/6; 10H 150mA, 12/6; 15H, 250mA, 16/6.

CRYSTAL MIKE INSERT by Acos 6/6
Precision engineered. Size only 7/8" x 3/8"
ACOS CRYSTAL HAND or DESK MIKE, 35/-

ALADDIN FORMERS and cores. 3/8" 8d., 3/8" 10d. 0.3" FORMERS 5937 or 8 and cans TV1 or 2. 3/8" sq. x 2 1/2" or 3/8" sq. x 1 1/2", 2/- with cores.

SLOW MOTION DRIVES. Epicyclic ratio 6-1, 2/3.
TYANA. Midget Soldering Iron. 230V 40W, 16/9.
REMPLOY INSTRUMENT IRON, 230V 25W, 17/6.

MAINS DROPPERS. 3" x 1 1/2". Three adj. sliders, 0.3A, 750 ohms, 4/3; 0.2A 1,000 ohms, 4/3.
LINE CORD. 0.3A 60 ohms per foot, 0.2A 100 ohms per foot, 2-way, 6d. per foot; 3-way, 7d. per foot.
MIKE TRANS. 50:1, 3/9; 100:1, potted, 10/6.
LOUDSPEAKERS. P.M. 3 ohm. 5", Rola 17/6; 6" x 4" Rola, 18/-; 4" Hi-Fi Tweeter, 25/-; 8" Plessey, 19/6; 6 1/2" Goodmans, 18/6; 10" R.A., 30/-; 12" Plessey, 30/-; 10" x 6" R.A., 27/6; 12" Baker 15W 3 ohm or 15 ohm models, 105/-; Stentorian HF1012 10", 95/-.

CRYSTAL DIODES. G.E.C., 2/-; GEX34, 4/-.
40 CIRCUITS FOR GERMANIUM DIODES, 3/-.
H.R. HEADPHONES 4,000 ohms, brand new, 16/6 pr.
SWITCH CLEANER FLUID, squirt spout, 4/3 tin.
TWIN GANG CONDENSERS. 365pF, miniature. 1 1/2" x 1 1/2" x 1 1/2", 10/-; 0.0005 standard with trimmers, 9/-; less trimmers, 8/-; Midget, 7/6; 50pF single, 2/6.
SHORT WAVE SINGLE 75pF, 100pF, 160pF, 7/- each.
TUNING AND REACTION CONDENSERS. 100pF, 300pF, 500pF, 3/6 each, solid dielectric.

HIGH GAIN TV PRE-AMPLIFIERS BAND I B.B.C.—See page 852 June issue

Tuneable channels 1 to 5 Gain 18dB. ECC84 valve. Kit price 29/6 or 49/6 with power pack. Details 6d.

BAND III I.T.A.

Tuneable channels 8 to 13. Gain 17 dB ECC84 valve. Kit price 29/6 or 49/6 with power pack. Details 6d.

Volume Controls 80Ω Coaxial Cable

Midget size. Long spindles. Semi-air spaced Polythene Guaranteed 1 year. All insulated 3/8" dia. stranded values 5,000 ohms to 2 Meg. Core. Ideal Band III 9d yd. No Switch D.P. Switch Losses cut 50% FRINGE QUALITY 3/- 4/9 Air spaced Coaxial 1/6 yd.

Coaxial Plugs 1/- Lead Socket 2/-
Panel Sockets 1/- Outlet Boxes 4/6
Balanced Twin Feeder, per yd 6d., 80Ω or 300Ω.
Twin Screened Balanced Feeder, 1/6 yd, 80 ohms.
Trimmmers. Ceramic 30, 50, 70pF, 9d.; 100pF, 150pF, 1/3; 250pF, 1/6; 600pF, 750pF, 1/9; Philips, 1/- each.
BLACK CRACKLE PAINT. Air drying, 3/- tin.
P.V.C. CONN. WIRE, 8 colours, single or stranded, 2d. yd. Sleeving 1, 2mm, 2d., 2, 3 mm, 3d., 6 mm, 5d. yd.
NEON MAINS TESTER SCREWDRIVERS, 5/3.
SOLDER RADIOGRADE, 3 yds 9d., 1lb 2/6.

Aluminium Chassis. 18 s.w.g. Plain, undrilled, with 4 sides, riveted corners and lattice fixing holes, with 1 1/2" sides. 7" x 4", 4/6; 9" x 7", 5/9; 11" x 7", 6/9; 13" x 9", 8/6; 14" x 11", 10/6; 15" x 14", 12/6; 18" x 16" x 3", 16/6.

Miniature Contact Cooled Rectifiers. 250V 50mA 7/6; 250V 85mA, 9/6. Selenium Rect. 300V 85mA, 7/6. Coils. Wearite "P" type, 3/- each. Osrom Midget "O" type, adj. dust core, from 4/- each. All ranges. **Telatron A.H.F. L. & Med. T.R.F.** with reaction, 3/6. **Ferrite Rod Aerials.** M.W., 8/9; M. & L., 12/6. **T.R.F. Coils A/HF, 7/- pair.** H.F. Chokes, 2/6. **Speaker Fret.** Gold cloth, 17" x 25", 5/-; 25" x 35", 10/-; **Tygan,** 4" 6" wide, 10/- ft; 2" 3" wide, 5/- ft. Samples, S.A.E.

Condensers. 0.001μF 7kV T.C.C., 5/6; ditto 20kV, 9/6; 0.1μF 7kV, 9/6; 100pF to 500pF Micas, 6d.; Tubular 500V 0.001 to 0.01μF, 9d.; 0.05, 0.1, 1/-; 0.25, 1/6; 0.1/350V, 9d.; 0.5, 1/9; 0.01/2,000V, 1/9; 0.1/2,000V, 3/6. **Ceramic Condensers.** 500V 0.3pF to 0.01μF, 9d. **Silver Mica.** 10% 5pF to 500pF, 1/-; 600pF to 3,000pF, 1/3; close tolerance (plus or minus 1pF), 1.5pF to 47pF, 1/6; ditto 1%, 50pF to 815pF, 1/9; 1,000pF to 5,000pF, 2/-.

NEW ELECTROLYTICS FAMOUS MAKES

TUBULAR	TUBULAR	CAN TYPES			
1/350V	2/-	64/350V	5/6	8/500V	3/-
2/450V	2/3	100/25V	2/-	16/500V	4/-
4/450V	2/3	250/25V	2/6	32/350V	4/-
8/450V	2/3	500/12V	3/-	100/270V	4/-
8/500V	2/9	8+8/450V	4/6	2,500/3V	5/6
16/450V	3/6	8+8/500V	5/-	6,000/6V	4/-
16/500V	4/-	8+16/450V	5/-	32+32/350V	5/-
32/450V	5/6	8+16/500V	5/6	50+50/350V	4/6
25/25V	1/9	16+16/450V	5/6	64+120/275V	7/6
50/25V	2/-	32+32/350V	4/6	64+120/350V	11/6
50/50V	2/-	32+32/500V	7/6	100+200/275V	12/6

Full Wave Bridge Selenium Rectifiers. 2, 6 or 12V 1 1/2A, 8/9; 2A, 11/3; 4A, 17/6. Free charger circuit. **Charger Transformers.** Tapped input 200/250V for charging at 2, 6 or 12V 1 1/2A, 15/6; 2A, 17/6; 4A, 22/6.

LONG PLAY "GEVAERT GEVASONOR" Plastic tape 50% extra 1,700ft 7" reel, 35/-; 850ft 5" reel, 21/-; Spare plastic reels 7" and 5 1/2" 3/- each. **SUPERIOR** 1,200ft plastic tape, 24/-; 7" plastic reel. 600ft plastic tape on 5" plastic reel, 15/-.
INSTANT bulk tape eraser, 200/250V a.c., 27/6.

BRAND NEW AND BOXED Model UA8
OUR PRICE £6.19.6
STEREO MODELS
UA8 £8.19.6
UA12 £10.10.0

★ COLLARO ★
HI-FI ATUOCHANGER £7.19.6
4 SPEEDS—10 RECORDS
or with Cabinet, Amplifier and Speaker
OUR PRICE £11.19.6 Carr. 5/6

★ GARRARD 4-SPEED RECORD CHANGERS RC121/D MK II MODELS ★
With Plug-in Normal Head **£10.10.0**
Stereo Head £2 extra

★ GARRARD 4-SPEED SINGLE RECORD PLAYER 4SP ★
£7.10s. AUDIO PERFECTION POST FREE
MODEL TA MK 11 £8.10.0 { Stereo Heads £2 extra
MODEL 4 HF £18

Wavechange Switches. 2 p. 2-way, 3p. 2-way, short spindle, 2/6; 5p. 4-way 2 wafer, long spindle, 6/6; 2 p. 6-way, 4 p. 2-way, 4 p. 3-way, long spindle, 3/6; 4 p. 4-way, 1 p. 2-way, long spindle, 3/6; wavechange "MAKITS," 1 wafer, 8/6; 2 wafer, 12/6; 3 wafer, 16/-; 4 wafer, 19/6; 5 wafer, 23/-; 6 wafer, 26/6.
Toggle Switches, s.p., 2/-; d.p., 3/6; d.p.d.t., 4/-.

JASON FM TUNER COIL SET, 26/-. H.F. coil, aerial coil, oscillator coil, two i.f. transformers 10.7 Mc/s, detector transformer and heater choke. Circuit and component book using four 6AM6, 2/6. **Complete Jason FM Kit,** with valves and Jason Chassis with calibrated dial, £6.15.0, post free.
Mullard 3-3. Quality amplifier ready built, with power socket for tuner, £7.17.6.

Valveholders. Pax. int. oct., 4d. EA50, E150, 6d. B12A, CRT 1/3. Eng. and Amer. 4, 5, 6 and 7 pin, 1/-, MOULDED Mazda and int. oct., 6d., B7G, B8A, B8G, B9A, 9d. B7G with can, 1/6. B9A with can, 1/9. Ceramic, EF50, B7G, B9A int. oct., 1/-; B7G, B9A Cans, 1/-; each.

TV Fault Finding, 5/-. Quality Amplifiers, 4/6. **Radio Valve Guide,** Books 1, 2 or 3 5/- each. **TRANSISTORS.** Ediswan Audio XB102, 10/-; R.F. XA103, 15/-; XA104, 18/-; Sub-miniature Electrolytics (15V), 1μF, 2μF, 4μF, 5μF, 8μF, 25μF, 50μF, 3/-.

Telatron Transistor Pocket Radios

Designers Specified Kits
COMPANION PRINTED CIRCUIT THREE
Local station receiver kit, 4 1/2" x 3" x 1 1/2" **£4.19.6**
3 Ediswan or Mullard transistors, plans 6d.

Transidyne Superhet Six 6" x 4" x 1 1/2"
T.C.C. Printed Circuit, internal Ferrite aerial, Rola loudspeaker push-pull output. All parts, cabinet, 6 Ediswan or Mullard transistors.
£11.19.6 Plans, etc., 9d.

RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD WEST CROYDON Catalogue 1/6 Telephone THO 1665

48 hour postal service 1/-, over £2 post free. C.O.D. 1/6 (Export welcome. Send remittance and extra postage)


MAKING A SOLDER GUN



A 7-second solder gun of the type costing £3-£4.

Only two essential parts are required—(a) the transformer and (b) the push switch. These we can supply at 11/6, plus 2/- post. The rest of the parts you will have in your own "junk" box. Copy of the article concerned given free with the kit.

SUPPRESSOR CONDENSER

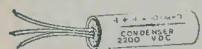

Stop your drill or other appliances interfering with your or your neighbours' radio or television. Simple instructions given. 1/6 each. 12/- dozen.

T.V. SERVICE SHEETS

200 sheets covering most popular post-war televisions by leading makers—Cossor, Ekco, Ferguson, Pye, etc., £2 post free. PREVIOUS PURCHASERS OF THESE SHEETS PLEASE NOTE: WE CAN SUPPLY SHEETS Nos. 100-200, £1, or 150-200, 10/-.

THIS MONTH'S SNIP

Car Starter Battery Charger—due to a fortunate purchase we are able to offer you a fine ready-made high output battery charger in stove-enamelled sheet steel louvered case. New, complete and ready to work, this charger is rated at 12V, 4 Amps. and has a variable rate selector for trickle charging, also a meter to show charging rate. Suitable for 230/250 A.C. mains. Made to sell at 85/-, but offered this month at special snip price of 55/-, plus 3/6 post and insurance.




MEDRESCO HEARING AID

As supplied by National Health completely overhauled and in good working order with six months' guarantee. Only £3.15.0 plus 2/6 post and ins. Complete with ear-phone and new ear plug but not batteries, these can be supplied as an extra for 5/- per set. Ardent models, as new, higher gain and self-contained batteries £7.10.0 or 10/- deposit and 16 fortnightly payments of 10/-




PULLIN SERIES 100 TEST SET

Undoubtedly a most useful instrument by a firm long famous for fine instruments, entirely re-designed, it has a square movement with diacon plastic cover, this makes for a brighter, more readable scale, extra scale length and wider angle of vision. With the test set is included a pair of combined test prods and crocodile clips also a stand for inclining the meter at the best reading positions. Ranges A.C. Volts: 0-10, 0-25, 0-100, 0-250, 0-500, 0-1,000, ditto D.C. A.C. Current 0-100mA. D.C. Current 0-2.5, 0-10, 0-100, 0-500mA. Resistance: 0-1M and 0-10K. All at 10,000 ohms per volt—Price £12.7.6 or £1 deposit and 24 Fortnightly payments of 10/-, non-callers add 5/- carriage and insurance.

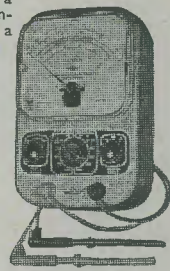

HI-FI SNIP Infinite Wall Baffle

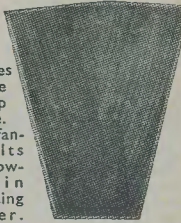Nicely veneered and polished. Corner fitting (attaches to picture rail). Takes up no floor space. Gives really fantastic results with only low-priced 8in speaker. Fitting for tweeter. Only 45/- each. Carriage and insurance 3/6.



SPEAKER BARGAIN




12in fidelity Loud-speaker. High flux. Permanent magnet type with standard 3 ohm speech coil. Will handle up to 12 watts. Brand new by famous maker. Price 32/6, plus 3/6 post and insurance.

"DIM AND FULL" SWITCH

Particularly useful for controlling photo-flood lamps which have only a short life at full brilliance. This toggle switch has three positions, the first position puts two lamps in series at half brilliance for setting up, the second position is off and the third position full brilliance for the operational shots. Also useful for controlling night lights, heaters, etc., etc. Price 2/6 each. Post 9d. Circuit diagram included.

MORGANITE POTENTIOMETERS

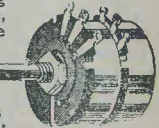Single and 2-gang types available, standard size with good length spindle, all new and boxed Single types 1/- each. Values available: 5kΩ, 10kΩ, 25kΩ, 50kΩ, 100kΩ, 250kΩ, 1MΩ, 2MΩ. Gang type, 3/- each. Values available: 5kΩ+5kΩ, 100kΩ+100kΩ, 500kΩ+500kΩ, 2MΩ+2MΩ.



DON'T STUMBLE IN THE DARK

Install 2-way switches. Our outfit comprises: 30 yds. Multicore cable, two 2-way switches, two wood blocks. Full instructions, 9/6 each, post and insurance 2/6.

SUPER SENSITIVE (2,000 O.P.V.) MULTIMETER KIT


17 ranges including D.C. volts to 1,000 volts, A.C. to 1,000 volts, D.C. milliamps to 500 ohms to 2 meg., capacity and inductance. All the essential parts including metal case, selected resistors, wire for shunts, selected switches, calibrated scale and instructions, 32/6, plus 2/6 post and insurance.

BUILD THE OG.10 OSCILLOSCOPE

with an authentic

Jason *kit*

Britain's Finest kits

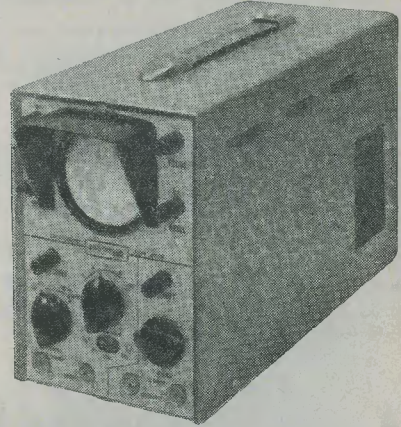

For absolute assured results, build this excellent Oscilloscope with an authentic Jason kit. All parts exact to author's specification. Amongst the many uses to which this instrument may be put, TV servicing and audio amplifier checking are important examples. Sensitivity—10mV/cm with a bandwidth of 2 c/s to 1.5 Mc/s. Complete with case, Mullard C.R.T. and all valves as specified.

£22.10.0 with tube

OTHER KITS IN THE JASON PROGRAMME

AUDIO GENERATOR AG.10

Excellent stability with output held constant over entire band. Tunes from 10 c/s to 100 kc/s over four switched stages and two scales. Switch for square or sine wave. Square wave rise time less than 2 microseconds at all frequencies. Min. calibrated output 100mV. With case, valves and calibrated scale £12.10.0 (Built £15.2.6.)

JTV. FM/TV SOUND TUNER

Provides switched reception of Home, Light and Third programmes on F.M., also sound transmission of both B.B.C. and I.T.A. TV as required. TV sound programmes may be safely recorded if so desired and for regular listening, full advantage of the very high quality from TV transmitters may be enjoyed. Self powered. The kit, less valves may be built for £12.19.0.

EVEREST ALL-TRANSISTOR PORTABLE

Two versions—"Everest 6" and "Everest 7". Both include high-quality 13K gauss speaker and class B output. Everest 7 has additional R.F. stage for extra power and sensitivity. Everest 6 may be built for £13.19.9. Everest 7 may be built for £15.18.9.

FMT.3 FM TUNER


A finely designed FM tuner with variable A.F.C. and dual limiters. Self powered. Normal working range at least 80 miles. The kit, less valves, may be built for £8.5.0.

Details of the above models in the Jason range, gladly sent on request. Please quote this journal when writing.

THE JASON MOTOR & ELECTRONIC COMPANY

3-4(E) GREAT CHAPEL ST. OXFORD ST. LONDON W1 Telephone GERrard 0273/4


<p>Electronics (Manor Park) Ltd. 520 High Street North Manor Park E12</p>	<p>If ordering by post, address to the Company nearest to you</p>	<p>Electronics (Finsbury Park) Ltd. 29 Stroud Green Road Finsbury Park N4 Telephone ARCHway 1049 Half-day Thursday</p>
<p>Electronics (Ruislip) Ltd. 42/46 Windmill Hill Ruislip Middlesex Telephone RUIslip 5780 Half-day Wednesday</p>	<p>Electronics (Croydon) Ltd. 266 London Road Croydon Telephone CROydon 6558 Half-day Wednesday</p>	<p>Electronics (Finsbury Park) Ltd. 29 Stroud Green Road Finsbury Park N4 Telephone ARCHway 1049 Half-day Thursday</p>

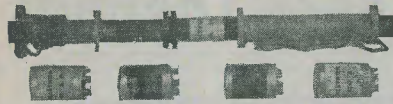

TELETRON MINIATURE TRANSISTOR 42/-
Superhet coil kit (as illustrated)

470 kc/s I.F. Transformers and Oscillator coil in screening cans $\frac{3}{4}$ " x $\frac{1}{2}$ " dia. Dual wave Ferrite rod aerial $5\frac{1}{2}$ " x $\frac{5}{16}$ " dia. Designed for the TRANSIDYNE miniature superhet receiver.

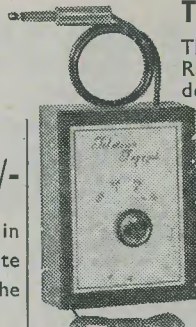Descriptive folder with circuit and assembly instructions Price 9d.



TELETRON TAPEJAK

The first Transistorised Radio Tuner, specially designed for use with Tape Recorders. Converts your Recorder to a high quality Radio receiver. Direct recording on Tape. 5 " x $3\frac{1}{2}$ " x $1\frac{1}{8}$ "

- High Sensitivity
- Twin tuned circuits
- Pre-setting for MW Programmes
- Fxd. tuned for 1500 M

● Switched prog. selector. ● Self Powered
Tested and ready for use Battery extra
£5-9-0

FERRITE ROD AERIALS Wound on high permeability Ferroxcube rod. Medium wave, FRM 4 " x $\frac{5}{16}$ ".
8/9. Dual wave FRD, 8 " x $\frac{5}{16}$ ", 12/9.



Send 5d. in stamps for complete data and circuits. All types available from advertisers in this Magazine and local component stockists

THE TELETRON COMPANY LIMITED

112b Station Road . Chingford . London E4 Telephone SIL 0836

A television course for you to study at home

*Entirely new! Practical!
Bang up to date!*

**THE FAMOUS BENNETT COLLEGE
OFFERS YOU THIS**

An entirely new course of study based upon up-to-date techniques has now been prepared by The Bennett College.

The course is non-mathematical, and contains numerous clear diagrams, starting from the very beginning (even including the basic principles of sound radio receivers, if desired) and covering all the relevant knowledge that you need to know!

This is what you've been looking for! You can now gain thorough knowledge of this vast subject in your spare time at home. The course includes: production

of the signal, scanning and reproduction of picture from signal. Aerials, types and purpose. The cathode ray tube. Time-base oscillators, and output circuits. Synchronisation. Video frequency amplifiers. The TV tuner, turret, incremental, etc. Television test gear. Television faults.

For more details, fill in the coupon below. Your studies cost you very little, the book you need is included in the cost.

To THE BENNETT COLLEGE
(DEPARTMENT J162TV) SHEFFIELD
Please send me details of the new
Television Servicing Course

NAME.....
ADDRESS.....
.....AGE.....




NOW OPEN!
LASKY'S
NEW
SHOWROOMS
207 EDGWARE RD., W2

Lasky's go still further ahead! Come and see the astonishing variety of leading makes of Electronic, Radio and TV Components, Accessories, Units, Tape Recorders, Constructor Kits, Cabinets, Cases, etc. Undoubtedly the largest and most comprehensive stocks for all constructors and high fidelity enthusiasts!

NOW READY!
THE FINEST
COMPONENTS
CATALOGUE

Never before has such a comprehensive and useful catalogue been made available to the constructor. Over 100 pages, size $8\frac{1}{2}$ " x $5\frac{1}{2}$ ", with hundreds of illustrations! Puts you abreast of all the latest developments and our prices save you pounds. A "must" for every constructor. The demand is certain to be enormous, so send for your copy NOW!

PRICE 2/- POST 6d.

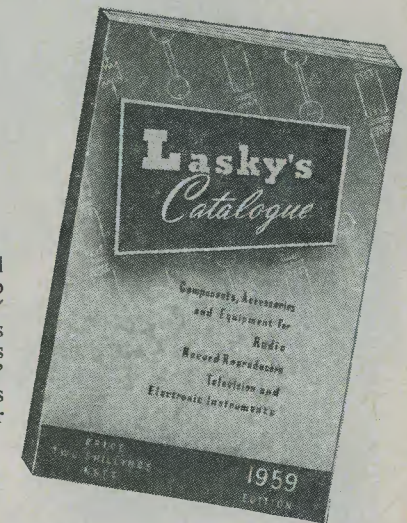

TWO ADDRESSES FOR PERSONAL SHOPPERS




207 EDGWARE ROAD, LONDON, W2
Few yards from Praed Street
LADbroke 4075 and CUNningham 1979

42 TOTTENHAM COURT ROAD, LONDON, W1
Nearest station Goodge Street MUSeum 2605


Both addresses open all day Saturday, close 1 p.m. Thursday

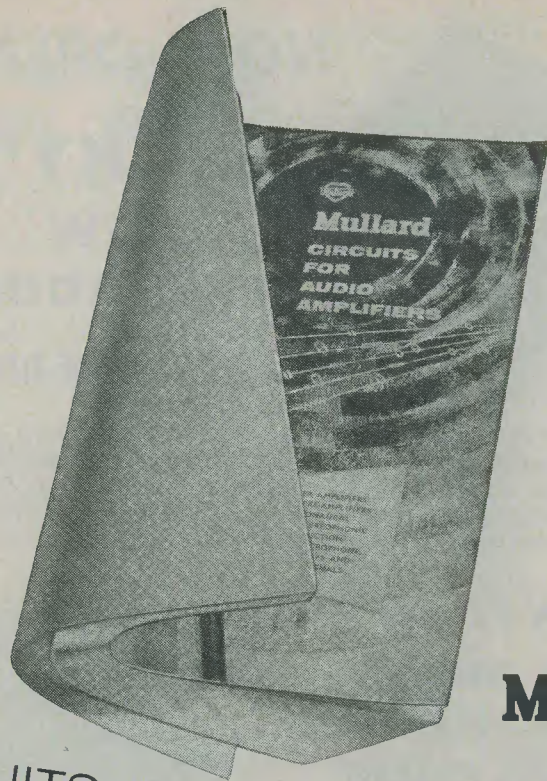Please address Mail Orders and enquiries to Lasky's (Harrow Rd) Ltd, 207 Edgware Road, London W2



Mullard

CIRCUITS FOR AUDIO AMPLIFIERS

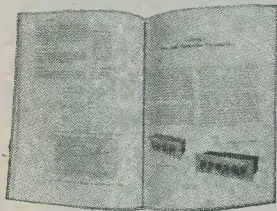

- a book every enthusiast will want!

This new Mullard publication is a practical manual for the audio enthusiast. In addition to describing twelve of the most popular Mullard circuits, it has introductory chapters on many of the theoretical and practical aspects of high quality sound reproduction.

Whether your customers are interested in disc or tape, monaural or stereo, they will find that "Circuits for Audio Amplifiers" gives just the sort of information they need.

This informative book costs only 8/6d. less the usual discounts. The demand for it is certain to be high, so order your stock now through your usual wholesaler.



MULLARD LTD • MULLARD HOUSE • TORRINGTON PLACE • LONDON • W.C.1
MVM 422A

NEW! **DO-IT-YOURSELF TRAINING TECHNIQUE**
in RADIO & ELECTRONICS

You LEARN while you BUILD...

SIMPLE...PRACTICAL...FASCINATING...

ANNOUNCING—after many years of highly successful operation in the U.S.A. and in Europe—the latest system in home training in electronics is now introduced by an entirely new British training organisation.

AT LAST—a comprehensive and simple way of learning—by practical means—the basic principles of radio and electronics, with a minimum of theory.

YOU LEARN BY BUILDING actual equipment with the components and parts which we send you. You advance by simple steps using high quality equipment and performing a whole series of interesting and instructive experiments. No mathematics!

INSTRUCTION MANUALS and our teaching staff employ the latest techniques for showing clearly how radio works in a practical and interesting manner. You really have fun whilst learning! And you end by possessing a first rate piece of home equipment with the full knowledge of how it operates and—very important—how to service and maintain it afterwards. A full library of magnificent illustrated textbooks is included with the courses.

IN FACT for the "Do-it-Yourself" enthusiast, the hobbyist or those wanting help with their radio career training, or to set up their own full or part-time servicing business—then this new and exciting instructional system is exactly what is needed and it can all be provided at very moderate cost. Easy payments available. Post the coupon now, for full details. There is no obligation of any kind.

BUILD YOUR OWN: • RADIO EQUIPMENT • HI-FI INSTALLATION • TEST GEAR—AND LEARN AS YOU DO IT.



RADIOSTRUCTOR

BRITAIN'S LEADING RADIO TRAINING ORGANISATION.

LOTS OF INSTRUCTIVE EXPERIMENTS AT HOME!

Power supply circuits

Test equipment supplied

Amplifier, oscillator and detector circuits

Basic 1st stage receiver

Servicing of commercial receivers



No Mathematics!

To: RADIOSTRUCTOR (Dept. G31)
46 Market Place, Reading, Berks.

Please send full details of your Radio Equipment Courses without any obligation to:

Name.....


Address.....

BLOCK CAPS PLEASE

(802) We do not employ representatives 9:59

Look at the NEW MOTEK K10

TAPE DECK

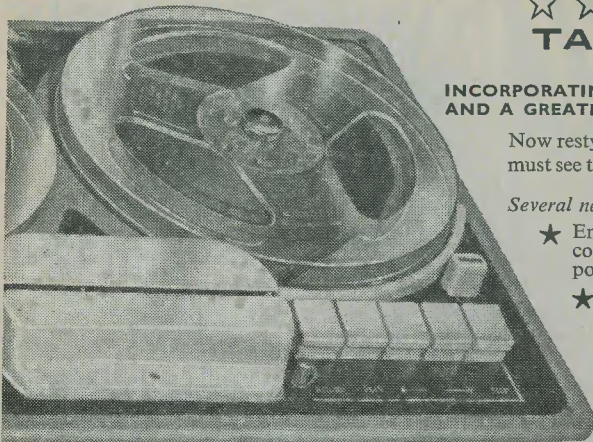

INCORPORATING MANY NEW FEATURES AND A GREATER FREQUENCY RESPONSE

Now restyled in two tones of grey—you must see the new, attractive Motek K.10

Several new features include:

- ★ Enlarged drive wheel on the rev. counter ensures accurate tape positioning.
- ★ Non-slip push buttons.
- ★ Frequency response better than 40 c/s—
- ★ 12,000 c/s at 7.5" per sec. with extremely low hum pick-up.

Patents pending

More and more manufacturers are installing Motek Tape Decks in their recorders.

MODERN TECHNIQUES
Wedmore Street, London, N.19. Tel: ARCHway 3114

Please send for brochure of K.10

21GNS

Now... in your own home, LEARN RADIO - TELEVISION - ELECTRONICS

No previous technical experience needed!

PRACTICAL EQUIPMENT
(INCLUDING TOOLS)

GIVES YOU A REAL LABORATORY TRAINING

"The trained electronics engineer has a great career ahead of him."

Valuable FREE book shows how E.M.I. Institutes School of Electronics can train you for today's wonderful opportunities.

Radio, Television and Electronics provide an exciting field for the qualified man—high pay, a prosperous future, or independence in your own business. You train at home with E.M.I. Institute's specialists who know the quickest way to prepare you for one of the fine jobs open to trained electronics-men. Whether you are a beginner or an advanced student with an examination in mind, E.M.I. Institutes School of Electronics has a Course exactly suited to your needs—with or without practical equipment—from electricity and magnetism to automation techniques.

We definitely Guarantee "NO PASS - NO FEE"
Full details of the Courses, practical equipment, convenient monthly payments, our Employment and Advisory Depts. and much other helpful information is given in our Guide to Careers in Electronics. Write for your copy today. The book will be sent to you without obligation and free of charge.

FREE BOOK - POST NOW!

Please send me a free copy of your Guide to Careers in Electronics.

NAME _____
ADDRESS _____

Subject or Exam _____

OPPORTUNITIES
IN RADIO
TELEVISION
& ELECTRONICS

Practical Radio
Radio & Television Servicing
Practical Electronics
Electronics Engineering
Automation
City & Guilds
R.A. Examination
R.T.E.B. Certificate
P.M.G. Certificate

E.M.I. INSTITUTES


SCHOOL OF ELECTRONICS

The Specialist Electronics Division of the British Institute of Engineering Technology
(DEPT. SE/23) COLLEGE HOUSE 29-31 WRIGHT'S LANE KENSINGTON LONDON W8




NEW MODELS NOT LISTED INCLUDE
FM TUNER (with valves) £13.12.6
DX-100 TRANSMITTER £78.10.0

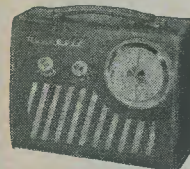
YOU can build these models easily and SAVE POUNDS




TRANSISTOR PORTABLE Model UXR-1

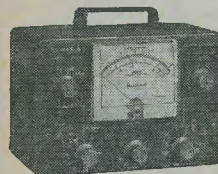

AUDIO GENERATOR Model AG-9U

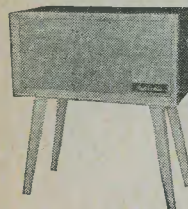

HI-FI SPEAKER SYSTEM Model SSU-1

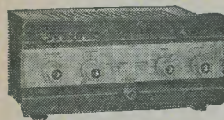

HI-FI STEREO AMPLIFIER S-33

CAPACITANCE/RESISTANCE BRIDGE C-3U. Measures capacity, 10pF to 1,000µF; Resistance, 100Ω to 5MΩ; Pwr. Fctr. £7.19.6 (Not illustrated)

AUDIO GENERATOR: AG-9U. 10 volts, 10 c/s to 100 kc/s pure sine-wave. Switch-selected frequencies/attenuation. £19.3.0

HI-FI SPEAKER SYSTEM: SSU-1. Ideal twin speaker/ducted-reflex cabinet for stereo/mono. in average room (left "in the white") Legs £1.7.0 extra. £10.5.6

HI-FI STEREO 6 WATT AMPLIFIER: S-33. Low priced but high quality; less than 0.3% distn at 2½ watts per channel. £11.8.0

TRANSISTOR PORTABLE: UXR-1. In elegant solid hide case, with golden relief. Six transistors, dual-wave, fine reproduction, very easy to build. £16.18.6

HI-FI STEREO BOOSTER: USP-1. Input of 2 to 20mV gives output adjustable from 20mV to 2V. Negligible distn. £5.19.6

HI-FI STEREO 16 WATT AMPLIFIER: S-88. Superb reproduction for the man who wants the best in Hi-Fi. Only 0.1% distortion at 6 W/chnl. Many special features. £25.5.6

5" OSCILLOSCOPE: O-12U. "Y" sensitivity 10mV/cm., 3 c/s to over 5 Mc/s. Rise time, 0.08 µsecs. or less. Sweep, 10 c/s to 500 kc/s. Electronically stabilised. £34.15.0

VALVE VOLTMETER: V-7A. The World's largest-selling VVM. Measures Volts to 1500 (DC & RMS) and 4000 pk. to pk.; Resistance 0.1Ω to 1000MΩ. Sensitivity: 7,333,333 Ohms per volt. £13.0.0

(Following models not illustrated)

"HAM" TRANSMITTER: DX-40U. 75 W. CW; 60 W. pk. c/c phone; 40 W. into Aerial. £29.10.0

VARIABLE FREQUENCY OSCILLATOR: VF-1U. 10V. output; covers 10 to 160 metres. £10.12.0

AUDIO WATTMETER: AW-1U. Up to 25 W. continuous, 50 W. intermittent. £13.18.6


AUDIO VALVE-MILLIVOLTMETER: AV-3U. 1mV to 300V AC. 10 c/s to 400 kc/s. £13.18.6

Model RP-1U TRANSCRIPTION RECORD PLAYER. Collar 4 spd; Ronette Stereo/Mono pick-up. Complete on plinth. £12.10.0

AT LAST! COMPLETE MATCHED STEREO OUTFIT comprising record player, amplifier and twin speaker systems. £42.10.0




VALVE VOLTMETER Model V-7A

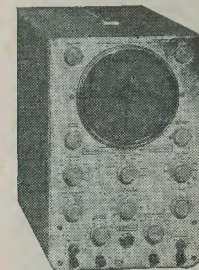

5" OSCILLOSCOPE Model O-12U



HI-FI STEREO AMPLIFIER S-88

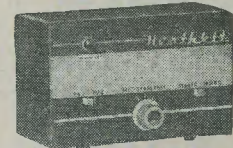

HI-FI STEREO BOOSTER Model USP-1

★ The range is growing fast!
SEND THIS COUPON NOW FOR FREE CATALOGUE

(Please write in BLOCK CAPITALS)

NAME _____

ADDRESS _____

ALL PRICES INCLUDE FREE DELIVERY IN U.K. AND ANY P.T. (Deferred terms are available)

Without obligation please send (Tick here)

BRITISH HEATHKIT CATALOGUE _____

FULL DETAILS OF MODEL(S) _____

DAYSTROM LTD. DEPT. RC9 GLOUCESTER, ENGLAND


A member of the Daystrom Group, manufacturers of the WORLD'S LARGEST-SELLING ELECTRONIC KITS

HOME RADIO OF MITCHAM

Dept. AC 187 LONDON ROAD MITCHAM SURREY
Shop hours: 9-6.30 (Weds. 1.0 p.m.) MIT 3282


We are main distributors for:
BRIBOND PRINTED CIRCUIT
Mullard '3-3' and '510' Amplifiers
Trade and overseas enquiries invited

COMPLETE "JUNIOR STEREO" HI-FI SYSTEM

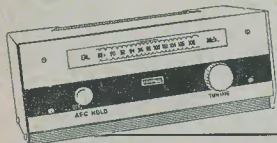


JASON FMT2 TUNER

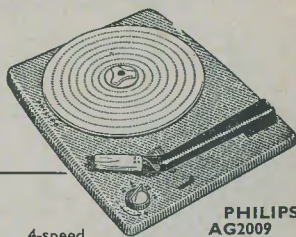Crystal clear Hi-Fi reception at all times. Modern slide rule scale, easy tuning, neat case. Full data in DB12 price 2/9 post paid. Complete kit with power unit £9.8.0.




**PHILIPS
AG2009**

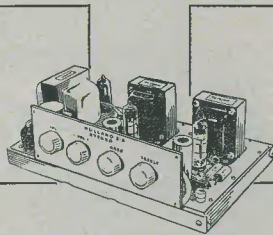
4-speed transcription player unit. Accurately machined turntable with variable control. Hi-Fi crystal pick-up for 78 and LP records. Leaflet on request. Price £10.10.0 post 2/-. Extra for stereo plug-in head £1.10.0



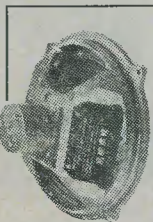New Mullard '3-3' Printed Circuit Stereo Amplifier. Easy to build and perfect results every time. Full constructional drawings and price list 1/9 post paid. Complete kit £16.0.0. All parts sold separately.



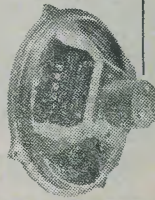Two WB Stentorian 10" High Fidelity HF1012 speaker units. Die cast chassis. Response 30 to 14,000 cycles. Universal speech coil. Price now reduced to £4.15.0 each plus 2/- post. Leaflet available.




R.C.S. "PERSONAL TWO" PORTABLE



2-valve dry battery personal portable with rod aerial. Ideal for bedroom or camping, etc. Smart metal case. Easy to build from data sheets. Price 2/- post paid. Parts cost 41/-. Also all parts for SW1 short waver in stock, price 35/-.

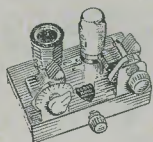We are appointed stockists for: "GLOBE KING" SHORT WAVE RADIO KITS



Real, long distance radio at minimum cost. This is a scientifically designed equipment for the real short wave enthusiast who desires the best results and efficiency. Produced up to a standard—not down to a price. Every item brand new and best quality. As easy to build as a Meccano model. Complete kit for 1 valver with three matched coils covering 10 to 100 metres, 79/6. May we send you full details and price list. Please enclose stamped addressed envelope.

BARGAIN LIST

Stocktaking clearance lines. Dozens of bargains. Send s.a.e. today for this list which can save you £ £ £s.

LUXEMBOURG PRE-AMP.

Complete kit of parts, including switch and chassis, to build the Luxembourg pre-amplifier as featured in this issue. PRICE 35/-. All parts available separately.

THE TRECOSCOPE

A high performance 3" oscilloscope built to highest standards and suitable for students, engineers and industry. Full specification on request. Immediate delivery. PRICE £17.17.0.

MULLARD DESIGNS



All parts stocked for the Mullard Tape Amplifier Tape Pre-amplifier, 4 Channel Mixer, Stereo Pre-amplifier and Amplifiers. Ready punched chassis and printed front panels available for most circuits. Full constructional data for all these in the new Mullard amplifier design book price 8/6, plus 1/3 post.

JASON KITS

We carry full range of parts for all JASON KITS including tuners, pre-amplifiers, amplifiers and test gear. JASON approved dealer.

TRANSISTOR SETS

Repanco **MINI-3**. Three-transistor pocket portable. Data 1/6. Complete kit £6.19.6. Repanco **MINI-7**. Seven-transistor pocket portable. Data 1/6. Complete kit £8.17.6. Repanco **THREE DEE**. Three-transistor bedroom set with 5" speaker. Data 1/-. Complete kit £4.10.0. Teletron **TRANSIDYNE**. Six-transistor pocket portable with printed circuit. Excellent results. Data 9d. Complete kit £12.10.0. R.C.S. One-transistor **Head-Phone** set. Complete kit of parts 30/-.

EDDYSTONE



Leaflet on request

PRICE
58/-

A high grade dial assembly for short wave receivers, converters, test gear, etc. Gear driven with 110 to 1 reduction and vernier scale. Cat. No. 898, delivery from stock. Full range of EDDYSTONE short wave components always in stock. Send 6d. stamp for full list.

The Radio Constructor

Incorporating THE RADIO AMATEUR



Vol. 13 No. 2 SEPTEMBER 1959 ANNUAL SUBSCRIPTION 25/- (including postage)

CONTENTS

- 86 Suggested Circuits: A Simple Burglar Alarm, by G. A. French
- 89 Can Anyone Help?
- 90 In Your Workshop
- 97 Understanding Television, Part 20, by W. G. Morley
- 102 The Jason OG.10 General Purpose Oscilloscope, Part 2, by G. Blundell and M. Smutny
- 109 Technical Forum
- 112 The "Major-Three" Personal Transistor Receiver, designed by D. J. French, Grad.I.E.E.
- 116 The "Tourist" Portable Receiver, described by Alan G. Hepworth
- 126 Radio Miscellany, by Centre Tap
- 130 Testmeters and Their Circuits, by W. Cleland
- 133 A Receiver Output Matching Box, by G5UJ
- 134 A Simple Chassis Punch, by M. J. Morley
- 136 Book Reviews

Editor

C. W. C. OVERLAND, G2ATV

Associate Editor

A. C. GEE, G2UK

Business Manager

J. H. BURROWS, A C A

Advertising Manager

F. A. BALDWIN, A M I P R E

Offices

57 MAIDA VALE LONDON W9

Telephone

CUNNINGHAM 6141
(2 lines)

Telegrams

DATA BUX, LONDON

NOTICES

THE CONTENTS of this magazine are strictly copyright and may not be reproduced without obtaining prior permission from the Editor.

ARTICLES appearing in this magazine which describe kits are inserted only on condition that such kits, or special components thereof, are freely available at a trade discount to all retail advertisers.

OPINIONS expressed by contributors are not necessarily those of the Editor or proprietors.

THE EDITOR invites original contributions on construction of radio subjects. All material used will be paid for. Articles should preferably be typewritten, and photographs should be clear and sharp. Diagrams need not be large or perfectly drawn, as our draughtsmen will redraw in most cases, but all relevant information should be included.

ALL MSS must be accompanied by a stamped addressed envelope for reply or return. Each item must bear the sender's name and address.

TRADE NEWS. Manufacturers, publishers, etc., are invited to submit samples or information of new products for review in this section.

TECHNICAL QUERIES should be submitted in writing. We regret that we are unable to answer queries, other than those arising from articles appearing in this magazine; nor can we advise on modifications to the equipment described in these articles.

ALL CORRESPONDENCE should be addressed to THE RADIO CONSTRUCTOR 57 Maida Vale London W9. REMITTANCES should be made payable to "DATA PUBLICATIONS LTD."

suggested circuits

The circuits presented in this series have been designed by G. A. FRENCH, specially for the enthusiast who needs only the circuit and essential relevant data

RATHER TO HIS SURPRISE, THE WRITER HAS received several requests recently to give details of a simple and reliable burglar alarm. The writer remarks on his surprise because he does not visualise a burglar alarm system as falling quite into the same category as have previous circuits in

this series. It may be that his correspondents have been thinking of an alarm system in terms of a rather elaborate electronic device; whereas, in reality, the most suitable alarm circuit employs very few components and works on simple electrical principles only. At any event it seems to be an established

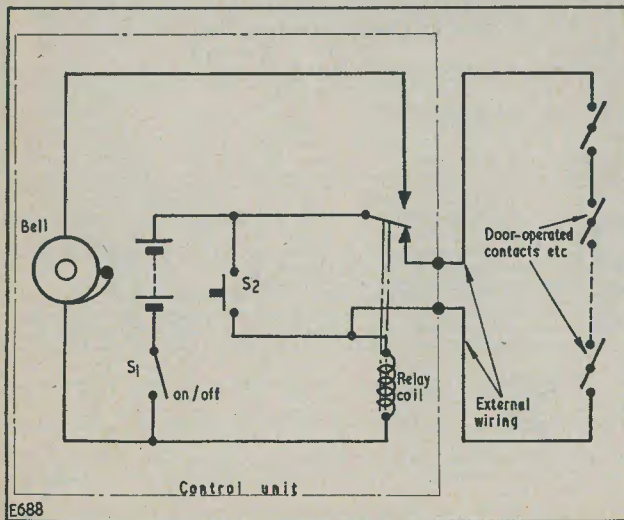


Fig. 1. The circuit of the burglar alarm

fact that petty pilfering, especially from small business premises, is on the increase these days, and it is this point, combined with the evident interest shown by some readers, that has finally prompted the writer to produce the *Suggested Circuit* which is published in this month's issue.

Circuit Operation

The circuit of the burglar alarm is illustrated in Fig. 1. As may be seen, it is extremely straightforward in operation, and it employs no electronic techniques whatsoever. The design of the circuit is based on the assumption that only the equipment immediately adjacent to the alarm bell may be considered as being vulnerable, the remainder—wiring, contacts, etc.—constituting the "sensitive" part of the device. If desired, the components around the alarm bell may be housed in a protective control box fitted with key-operated switches.

because the initial circuit via the change-over contact of the relay has now become broken.

It will be noted that the whole principle of alarm operation revolves around the fact that it is a *break* in the external circuit which sets it off, and that this break need be of a momentary nature only. Because of this basic principle it is not possible to put the alarm out of action by cutting any of the external wiring; such an act would, in fact, set off the alarm.

External Wiring

The fact that the alarm functions when a circuit is broken makes the design of contacts in the external wiring look a fairly simple process. As an example, Fig. 2 shows a suggested method for connecting a door into the loop. In Fig. 2 one contact is fitted to the door post and the other to the door itself, the wire to the latter travelling across the width of the door. Opening a door

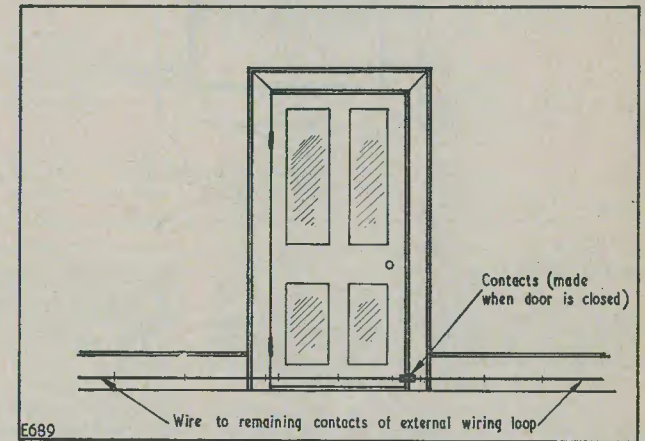


Fig. 2. A set of contacts fitted to a door

In Fig. 1 the alarm is shown switched on and in the "guard" condition. In this state a circuit is completed from the upper terminal of the battery, through the change-over contact (energised) of the relay, the external wiring loop, the coil of the relay and the on/off switch to the lower terminal of the battery. Due to the presence of this circuit current flows through the coil of the relay which continues to be energised. If, due to the ingress of an intruder, any of the external circuit is broken, the energising current to the relay immediately ceases. The relay de-energises and its change-over contact connects the battery to the bell, which then commences to ring. The alarm bell will continue to ring even if the external circuit is completed again shortly afterwards,

wired up in this manner would very obviously break the circuit and set off the alarm. Fig. 3 shows a similar idea applied to a sash window. Two sets of contacts are used here, the wire joining these travelling the width of the window.

It will be noted in Figs. 2 and 3 that the external wiring is routed in such a manner that the two wires to an individual set of contacts approach it from opposite directions. Such a wiring layout is desirable since it reduces the possibility of deliberate short-circuits before a set of contacts is broken. If it were intended to protect, say, a garage removed from a house, this would be preferably carried out by running two well-spaced separate wires to the garage, rather than by using a single length of twin cable between the garage and the house.

Alternative methods of providing protection readily suggest themselves. For instance, thin enamelled wire could be very conveniently stretched across points where entry may be attempted. If this wire were broken the external circuit would be interrupted, and the alarm would sound.

able the associated components can be mounted in a locked case, key-operated switches being employed for S_1 and S_2 .* Only the two leads from the external wiring loop need enter such a case.

Components

Due to the extreme simplicity of the

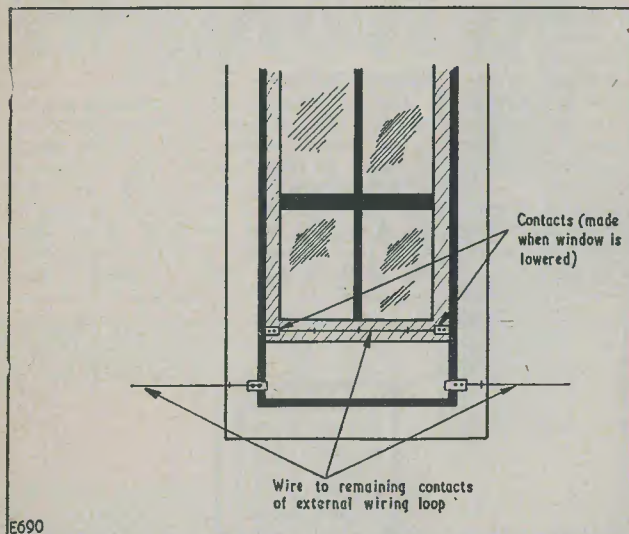


Fig. 3. A set of contacts fitted to a sash window. The contacts here, and in Fig. 2, may be made from any suitable springy metal bent to the required shape

The Control Unit

Apart from the fact that it houses the relay, battery and bell, the control unit shown in Fig. 1 also includes the switches needed to switch the alarm on and off, and to set up the relay.

The alarm is switched by S_1 , this coupling the lower battery terminal to the complete circuit. When depressed, push-button S_2 connects the battery direct to the relay coil, thereby energising it. When the alarm is initially switched on it is necessary to press S_2 to energise the relay, after which it may be released. Provided that the external circuit is complete, the relay will then remain energised.

It is presumed that the control unit will be kept in a secure place close to the owner of the premises. A typical instance would be the siting of the control unit in the owner's bedroom. In such a case there may be little point in making the unit itself "burglar-proof," with the result that ordinary switches can be employed in the S_1 and S_2 positions, and the small number of components required can be mounted in any convenient manner. If, however, it is decided to make the control unit less vulner-

circuit little difficulty should be encountered in obtaining the components needed for its manufacture.

The relay may be of any reliable type which is capable of being energised by the battery. There is no point in employing a relay having heavy contacts, as the currents involved should be quite small.

A disadvantage of the circuit is that a current is continually drawn from the battery when the alarm is switched on. However, such a disadvantage is inevitable if the essential feature of the device (wherein alarm indication is given when a circuit is broken) is to be achieved. The use of a battery, as opposed to operation from the mains, is also unavoidable, since it is necessary to be independent of power failures and the like. An economic method of running the alarm would consist of employing an accumulator in the battery position, this

*Suitable key-operated switches are manufactured by A. F. Bulgin & Co. Ltd. That employed in the S_1 position should be capable of having its key removed in either the "on" or the "off" position. A spring-loaded key switch is not available for exact replacement of the push-button S_2 , but a reasonable alternative should be provided by a switch whose key may only be removed when it is in the "off" position.

being charged when the alarm is not in use. Alternatively, the battery may be on continual trickle charge from the mains. It should be remembered that, in the case of a completely enclosed control unit, care should be taken to prevent corrosion due to any fumes which may be given off by the battery during charging. It is important, also, to

note that no charging circuit should be connected to the battery which may cause either terminal to be at earth potential when the alarm is switched on. Due to the possibility of random earth connections in the external wiring loop, such a charging circuit might cause unreliable operation of the alarm.

Can anyone help?

R.C.P. Valve Tester Model 314 and Signal Generator 52X2 Ref. No: 10SB/165.—D. W. Robson, 125 Atkinson Road, Benwell, Newcastle-on-Tyne 4, requires any information on these two items of test equipment, willing to purchase or refund expenses. He is able to supply numerous service sheets on t.v.'s, radios and tape recorders and one or two items of ex-government equipment, mostly U.S.A. types. S.a.e. for information required.

Panda Cub Transmitter.—F. Allan Herridge, G3IDG, 95 Ramsden Road, London, S.W.12, would like to hear from any reader who owns, and has carried out any modifications to, the above transmitter.

Marconi "Transatlantic" Receiver type 993.—J. R. Gomer, 150 Layer Road, Colchester, Essex, would like to obtain a service sheet on this receiver. Expenses met or exchange valves, odd meters, etc.

RI124C Receiver.—G. Gallamore, Spring Grove, Loch Lane, Partington, Urmston, Manchester, would like to communicate with anyone who has modified this receiver, particularly with reference to frequency coverage, alterations and the valve line-up etc.

W/S No: 19 Mk II.—F. K. Hanna, 57 Hatherly Road, Cheltenham, Glos., would be grateful for any information about this receiver, and especially data of the "B" set and wiring of the bottom plug.

UHF Calibration Receiver type TE564 with Preselector and Frequency Changer TM2578.—This receiver covers 10-150 Mc/s; and any information from readers will be gratefully acknowledged and costs defrayed by A. Melhuish, 31 Shepherds Bush Green, London, W.12.

Recording Unit 10D/16188.—H. C. Murfitt, 97 The Avenue, Nunthorpe, Middlesbrough, Yorks., would like to hear from anyone who has information on this unit, has used one, or knows where the film cassettes or a complete unit can be obtained. The unit consists of a 16 mm. camera with 1 inch Kinic Anastigmat which photographs the trace on a 3½ inch CRT, VCR-529. Valves used are: 7 x EF50, 2 x EF55, 5U4G, VU120 and VR92.

BC 929A Indicator Unit.—H. Harris, 12 Eastfield Road, Cotham, Bristol 6, requires the original circuit together with details and circuit of the conversion to a t.v. scope. All expenses met and postage paid.

Ekco Receiver type AW98 [1939].—C. M. Chapman, 12 Belgrave Road, London, E.11, requires the service data sheet or circuit of this receiver. Expenses reimbursed.

R1147B Receiver.—L. Lumb, 25 Moorville Street, Leeds 11, would like to receive information of the types of valves used in this receiver, their positions, and the frequency coverage. Also details of conversion to 2 metre operation. All letters answered and any expenses gladly refunded.

P40 Receiver.—J. Allen, 35 Damask House, Flower House Estate, London S.E.6, would much appreciate any information, circuit and frequency of xtal.

Murphy TV Model V114-116.—R. W. Sheppard, "Spring House", Hadlow, Kent, would like the loan of a service sheet for this televisor. All costs met.

Radio Section of Marconi Consul VRC74DA.—J. Harvey, 2a The Avenue, Rubery, Nr. Birmingham, requires service data, all expenses refunded.

Circuit required.—G. E. Smith, 39 Princes Road, Teddington, Middx, has an Osrom coil pack, type MTS, and requires a good circuit, using miniature valves, to suit this pack.

R1392.—N. A. Watson, 1 Strathearn Road, London S.W.19, has just acquired this ex-service VHF receiver and would like any information, circuit, manual etc.; all expenses met.


Acoustical Amplifier type QA12/P.—P. Harper, 59 Kingsway, Staines, Middx, would like to buy or borrow service sheet. Expenses gladly repaid.

R.A.F. Receiver Unit 153A. Ref. No: 8465.—681751 LAC, Lea-Jones, Electronics Centre, R.A.F., Finningley, Doncaster, wishes to borrow, beg or buy the circuit of this receiver.

Pye Communication Receiver PCR2 and W/S 19 Mk II.—D. Ransom, 33 Wellington Gardens, Charlton, S.E.7. Would like a circuit diagram of the former receiver and conversion of the latter to amateur band coverage with added bandspread details.

Ex-WD Indicator Unit 277.—W. A. Bone, 3 Audley Gardens, Seven Kings, Ilford, Essex, wishes to borrow or purchase any information on this unit as he wishes to construct a portable 'scope. All expenses gladly paid.

In your Workshop

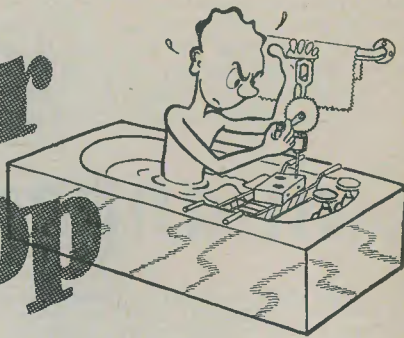

This month Smithy and Dick discuss ideas sent in by readers

"**B**UT that I am forbid," said Dick, entering the Workshop,
 "To tell the secrets of my prison house,
 I could a tale unfold, whose lightest word
 Would harrow up thy soul; freeze thy young blood;
 Make thy two eyes, like stars, start from their spheres."

Dick stopped, and shuddered violently.
 "Cor," he remarked to Smithy. "Fair gives you the creeps, don't it?"
 Smithy the Serviceman recognised the signs and chuckled.
 "I see," he said, "that the Thankful Thespians have once more condescended to include you in their company."

"If, laddie," replied Dick, "you are referring to the local Dramatic Society, I can inform you that they have, as is usual, called in my services for one of the more exacting parts in a forthcoming production. We shall shortly be presenting," he added grandiloquently, "the play *Hamlet, Prince of Denmark*."

"By William Shakespeare?"
 "Who else?"
 "And what part do you take?"
 "I," said Dick, with a gesture, "am the Ghost of Hamlet's Father."
 Smithy suppressed a smile.
 "Well, I hope your fan-mail is sent to the right address," he remarked.

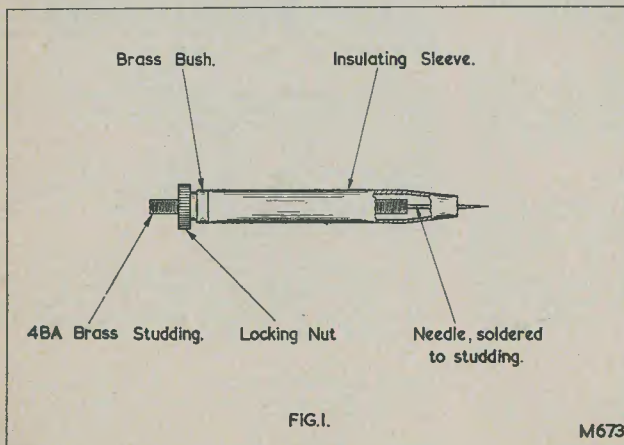


Fig. 1. A simple test prod capable of piercing rubber or p.v.c. insulation

Tips and Wrinkles

Dick forgot his histrionic career for the moment as Smithy's remark jogged a memory in his mind.

"Talking of fan-mail," he said, "haven't we in the Workshop got a few letters outstanding which are due for airing?"

"We have indeed," said the Serviceman. "Quite a number of people have sent us tips and wrinkles over the last few months, and I think we ought to have a look at some of these right now."

"We have, for instance, been given details of a very neat little test prod which is intended for piercing the insulation of rubber or p.v.c. wire so that readings may be taken from the conductor inside.¹ The thing which does the piercing is the business end of a sewing needle, and the hole it leaves in the insulation closes up almost completely after it has been removed. The hole should certainly close up well enough for any normal radio or t.v. application."

"As you may see (Fig. 1), the construction of the prod is quite simple, and the parts should be found in most junk-boxes. In the prototype, the insulating sleeve consisted of the lower half of a ball-pen, and the 4BA brass studding was found holding the heater dropper in an old receiver. I don't know where the brass bush came from but I should imagine that it was a fitting on the ball-pen, and that the designer tapped it out 4BA. All in all, I feel that the most important part of the device is the sewing needle itself, together with its ability to pierce insulating coverings. I'm quite certain that the average constructor will have no difficulty whatsoever in providing suitable insulated mountings basically similar to that used in the prototype."

"The idea of piercing insulated coverings is rather smart," commented Dick, "and it should certainly prove useful. To take the opposite extreme, I often feel that I need a prod which, instead of piercing through insulation, clips on to wires and stays there."

"Well, we have an extremely neat idea for that application," said the Serviceman, "and it is known as the 'Slim-Grip'.² The 'Slim-Grip' consists of three specially-shaped blades pivoted near one end, the whole being covered by a rubber sleeve. (Fig. 2.) The centre blade has a hole, behind the pivot, to enable a wire to be soldered to it. The insulation on such a wire passes inside the rubber sleeve so that there need be no break in the continuity of the insulation. When the working end of the device is pushed on to

an insulated wire the two outer blades open out in one direction, while the centre blade opens out in the other direction; with the result that the blades clip firmly on to the wire. The beauty of the design is that the rubber sleeve provides insulation all the way up to the wire the clip is attached to, so that there is no risk of shorts to adjacent conductors. It is, in fact, possible to run screening braiding over the outside of the clip, should this be desired, so that only a very small section, at the business end, is un-screened. An ingenious feature of the clip is that, apart from providing insulation, the rubber sleeve also provides the tension which pulls the blades inwards. If I add that the dimensions of the clip with sleeve are approximately 1½ inches long by ⅜ by ¼ inch you may begin to appreciate the 'Slim' part of its name. This slimmness, together with its excellent grip and the rubber sleeve insulation make the 'Slim-Grip' more useful in this particular application than anything else I've seen."

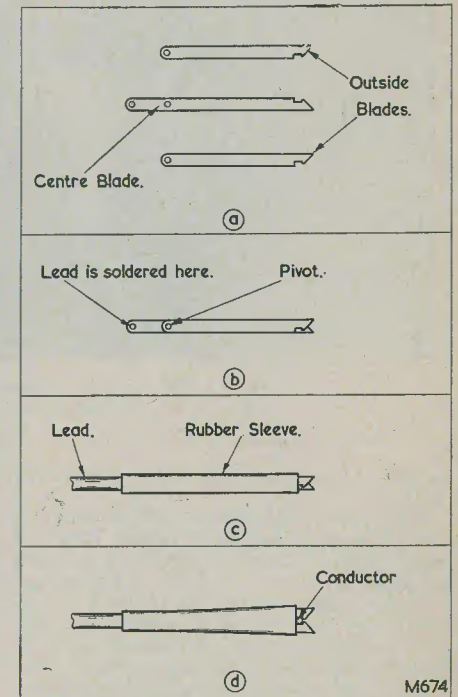


Fig. 2 (a) The three blades which make up the "Slim-Grip." (b) The blades riveted together. (c) A rubber sleeve fitted over the assembly provides insulation. (d) The clip fitted to a conductor. The blades open out against the tension of the sleeve

¹ Submitted by Mr. R. Bloomer, Shildon, Co. Durham.

² A provisional patent has been granted for the "Slim-Grip" described in this article. Trade enquiries should be addressed to Mr. W. O. Root, 44 Grange Drive, Glen Mills, Leicester.

"It's certainly a knobby idea," agreed Dick.

Valve Caddy

"And here," said Smithy, "is another knobby idea: what the Americans sometimes call a valve caddy. It's a smart, compact case suitable for carrying valves on either bench or field work.³ I've got a photograph of it here."



Photograph. A view showing the interior layout of the "Valve Caddy"

"Hmm, it looks quite neat," commented Dick.

"It is neat," said Smithy. "The caddy in the photograph carries fifty-eight B9A and eight B7G valves, and the case, which originally housed an old mains/battery portable, measures 11½ by 7½ by 4 inches. Any other case of similar proportions could be used instead. The individual valves fit into Mullard pin protectors screwed to the bottom and to the lid, and a large yellow label alongside each position indicates the valve type. You can see at a glance what valve is what and whether any 'refills' are needed."

³ Contributed by Mr. Gerald Dittrich, Dundee, Scotland.

"One thing I've noticed," remarked Dick, "is that the valves on the lid interleave with the valves fitted to the bottom when the lid is closed. With the intention, I presume, of giving you a case which is chock-full of valves when it's closed and which has them well spaced-out for ease of removal when it's open."

"That's right," confirmed Smithy. "By the way, I had better add that you've got the job

of knocking up a case like this for the Workshop as soon as you have a little spare time."

"I thought there'd be a catch in it somewhere," grinned Dick. "Still, it won't take very long. Have any more bright ideas come in?"

"Yes, I've got another one here," replied Smithy. "This one is quite a useful gadget for the chappie who does a little servicing now and again on the kitchen table.⁴ The main idea of the device is that it enables you to get light, soldering iron and mains socket for the set being repaired and for test gear all at one point, instead of having lots of wires trailing around all over the floor. I've got some photographs of the gadget and you

⁴ Contributed by Mr. H. A. Keable, Selby, Yorks.

can see that it consists fundamentally of a base with a pole sticking up. (Fig. 3.) The base is some nine to twelve inches square and the pole appears to be six feet high or thereabouts. A light, complete with shade, is fitted to a bracket on the pole, as also is a large 'Terry clip' for the soldering iron. There is, in addition, a smaller clip for holding bits of solder and such-like. The smaller clip can alternatively be used for holding bits of wire steady for tinning, and it is liable to stop drops of solder falling onto the sort of highly polished table-tops you find in desirable residences such as my own."

"We have cloths on ours," interjected Dick.

"You'll notice," continued Smithy, ignoring his assistant, "that the bracket carrying the light has a clamp which enables its height on the pole to be adjusted. On the base of the device are as many mains sockets as you care to fit, together with a switch which knocks them all off. The light and soldering iron can have separate switches, if desired. Also on the pole are two bollards for coiling up the lead which couples up the whole arrangement to the mains whenever it is in use."

"Fair enough," said Dick. "Yet another useful and simple idea gets the publicity it deserves! Any more tips?"

"No," said Smithy, "that's the lot. There were one or two others, for which I am very grateful indeed, but I am afraid that they have fallen by the wayside. So far as the future is concerned we would quite definitely be interested in some more tips and wrinkles including, especially, any which deal with out-of-the-way techniques. To give an idea of the sort of thing we like to see, how about a gubbins for magnetising and demagnetising screwdrivers."

"I don't follow you."

"Well," said Smithy, "if you had something which enabled you to quickly magnetise a screwdriver you could then use that screwdriver to pick up odds and ends which fell into awkward corners."

"That shouldn't be too difficult," commented Dick. "All you need is a coil which could be quite easily energised from the mains. For demagnetising you would apply raw a.c. to the coil and put your screwdriver into the middle. For magnetising you would rectify the a.c. before you applied it to the coil. It's certainly easy enough in theory."

"And it shouldn't be too difficult in practice," commented Smithy, "but I must point out that I only mentioned this idea to give people an instance of the type of thing we want."

"Some weeks ago I bumped into another idea which falls into the same category," Dick said. "I wandered into a friend's house

and found him sitting at the back of his t.v. set with a length of ¼-inch polythene tubing held up against his ear."

"I suppose," remarked Smithy, drily, "that that's as good a way as any, these days, of enjoying a t.v. programme."

"What had happened," continued Dick, doggedly, "was that his set had developed corona and he was trying to locate its source. He moved the free end of the tubing over all the e.h.t. parts of the receiver until he located the place where the sizzling sounded loudest."

"Hmm," said the Serviceman reflectively. "It's a new one on me. I can't see why it shouldn't work, though."

"It worked very well in this case," said Dick. "I tried it myself."

"O.K.," remarked Smithy. "Then I think we can count that technique as a second example of the sort of thing we like to hear about."

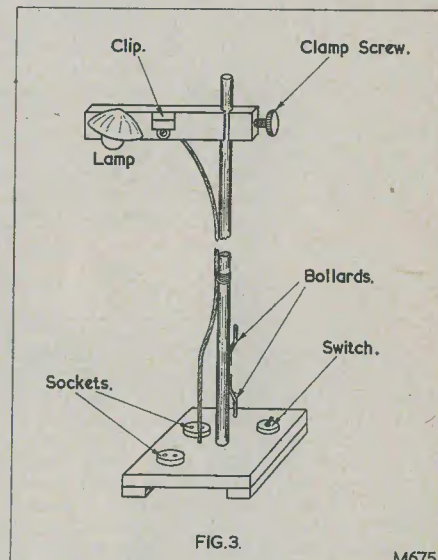


Fig. 3. A novel, but useful, device which brings mains voltages, etc., to a single location for occasional servicing sessions

More Hamlet

With this remark Smithy indicated that a little work would not now come amiss, whereupon his assistant obediently turned to his bench. The normal bustle of the Workshop soon made itself evident. With the difference, on this particular morning, that Dick broke the silence with intermittent and impassioned bursts of oratory as he practised for the local Dramatic Society's next presentation. Smithy suffered this state of affairs

for as long as he could, but his patience finally broke when, for the fifth time in succession, the words "slings and arrows of outrageous fortune," uttered very sonorously indeed, penetrated his consciousness.

"For the love of Mike," he called out irritably, "give it a rest! It's bad enough your practising the part of the Ghost, but I'm damned if I see why I should have to put up with your practising Hamlet's part as well. Isn't one part good enough for you?"

The long-suffering Serviceman jumped, and turned round peevishly.

"I do wish you wouldn't suddenly shout out like that," he complained irascibly. "I'm certain I secrete at least half a pint of adrenalin each time."

Deflector Yokes

"Sorry, Smithy," apologised Dick. "What happened was that the frame timebase suddenly cut out and I switched off quickly

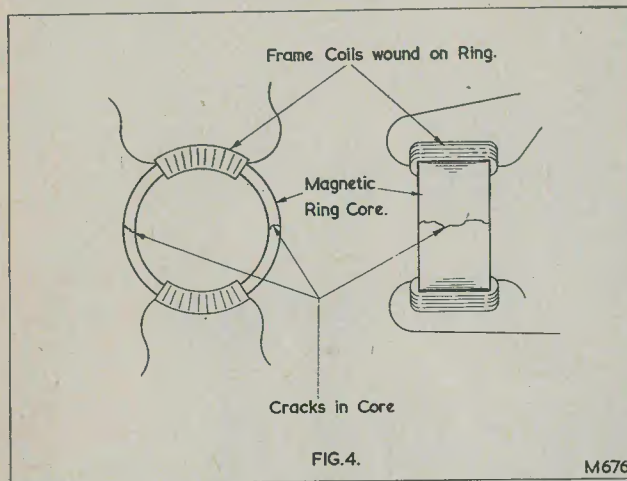


Fig. 4. In 110-degree deflector yokes the frame coils are wound directly on the magnetic cores

"Sorry, Smithy," said Dick contritely. "It's just that I'm so completely fascinated by Hamlet's soliloquy that I can't help trying it out myself. You know the bit I mean: it starts off 'To be or not to be.' Somehow," (here Dick struck a pose which he obviously intended to be indicative of great compassion), "I really *feel* for Hamlet when he makes that speech. Just think of that poor kid standing all by himself in the middle of the stage and bitching away quietly to himself because his Ma's shackled up with his old man's brother."

Smithy was horrified.

"Please, please, don't go any further," he protested. "With your peculiar genius for explaining things, you'd get even Noddy banned from the public libraries."

Dick looked hurt, but he turned back to his bench without comment. The Workshop grew quiet once more as he became immersed in the faulty 110 degree television receiver in front of him. However, Dick was not a person to keep silent for long.

"Whoops, Gertie!" he called out suddenly, as he very hastily switched off the set he was repairing.

to avoid striping the tube."

"Well, that's fair enough," said the Serviceman, somewhat mollified. "Even with present-day aluminised tubes it's still advisable to be on the safe side if you want to prevent the very bright horizontal line which is left when the frame timebase collapses from burning the screen phosphors."

Dick turned the brilliance control of his receiver fully back and switched on again. After a short while the line output stage commenced working and Dick cautiously advanced the brilliance control until the central horizontal line achieved an average brightness level.

"I think there's a broken connection in the deflector yoke," he remarked, "it was when I happened to waggle one of the lead-out wires that the picture lost its vertical scan."

Cautiously he moved the wire in question, whereupon the picture opened out momentarily and then collapsed once more.

"Yes," continued Dick, "there definitely seems to be a bad joint inside the works. Well, there's nothing for it but to get the yoke off."

Dick commenced to remove the scanning yoke. Finding that its leads were rather short, he unsoldered these at their chassis terminations. Smithy, despite himself, had been watching his assistant's actions with some interest.

"I've been meaning," he remarked, in explanation of this interest, "to have a look at the yoke of any 110 degree set that passes through our hands whenever the opportunity presents itself. So far as I'm concerned, 110 degree deflection is still new enough for me to be interested in the methods manufacturers use for making their yokes."

"Well, this particular example certainly seems to be a fairly intricate bit of work," commented Dick, surveying the yoke which now lay on his bench. "There are several sections fitting inside each other—rather like those Chinese boxes which hold smaller boxes and so on."

"That's true," agreed Smithy, "but the basic construction seems to follow the usual lines. You have a ring of magnetic material, just like we had in 90 degree yokes. With all the 110 degree yokes I've seen, however, the frame coils are wound directly on the magnetic material itself (Fig. 4) instead of on formers."

"How do they manage to wind through the hole in the ring?"

"I didn't know that," confessed Dick. "I suppose that, after cracking, the two halves have to be kept together in pairs until they join up again in the completed yoke."

"That's right. The cracked surfaces are bound to be irregular and so it is possible only to mate up the two halves of an original ring. If, by the way, you should ever cause the two halves of a deflector yoke ring core to come apart during servicing, you must always make certain that they mate up to each other perfectly when you re-clamp the assembly. Otherwise you'll get a distorted picture shape. You'll also get a distorted picture shape if there's a slight gap at either or both junctions of the two halves—even if that gap is of the order of a few 'thou' only."


"I see," remarked Dick. "I presume that the two coils which come out in a flare at the front of the assembly are the line coils."

"Correct."

"I notice that they have the stiff feeling such coils normally have. Are they what are known as bonded coils?"

"That's right," said Smithy. "The wire these coils are wound with is called self-bonding wire, and it consists of copper wire coated with synthetic enamel and an outside covering of glue. Immediately after the coil has been wound a heavy current is passed through it. This causes the coil to heat up

Fig. 5. One of the most useful items of equipment when servicing television receivers is a mirror fitted to a stand, as shown here. This enables adjustments to be made at the rear of the receiver whilst the screen is observed via the mirror. The sides of the mirror may be some 1 to 2 feet long

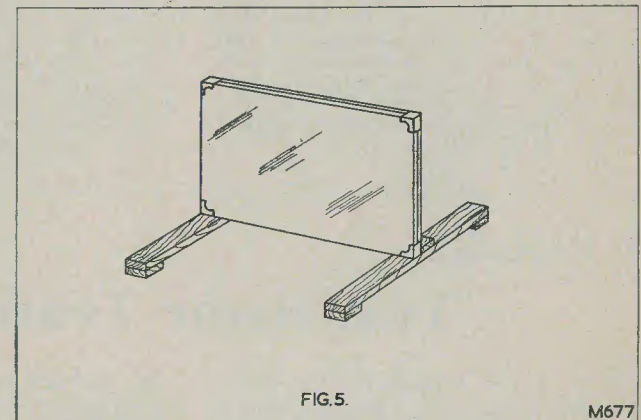

"They don't. The rings come in two halves and the coils are wound on these. After winding, the two halves are brought together, with a bit of Stickite between the surfaces which join, and then held with a clamp. I should mention, though, that the magnetic material is originally made in one complete ring because it's easier to do it that way. The complete ring is then cracked on opposite sides to give you the two halves."

and activates the glue covering, after which the current is switched off again. As soon as the wire has cooled off and the glue has set, the coil becomes self-supporting and retains the shape in which it was wound."

"Doesn't the cooking process damage the enamel insulation underneath the glue?"

"Not if the heating is carefully controlled," replied the Serviceman.

"Fair enough," said Dick, who was care-

fully examining the yoke he had just removed. "In the meantime I think I've found my bad connection."

He quickly applied a soldering iron to the offending yoke and, after a few exploratory tugs at the wire which had caused all the trouble, pronounced himself satisfied with his work. He then fitted the yoke over the neck of the tube, re-applied the tube socket and switched on.

As soon as the set had warmed up the picture re-appeared, with full vertical scan. Pleased, Dick positioned the receiver so that he could adjust the yoke whilst examining the picture with the aid of one of the mirrors which were stock equipment in the Workshop. (Fig. 5.) He first of all squared the raster with the edges of the mask by rotating the yoke assembly, after which he centred the picture.

"That's not too bad," remarked Smithy, whose interest in the yoke had caused him to remain and watch its re-installation in the chassis. "You may notice, if you look closely at the individual corners of the raster, that you get the impression of very slight pincushioning. This is all to the good with these 110 degree tubes because, with their extra screen curvature, very slight pincushioning gives the effect of a nice rectangular raster when the picture is viewed from a distance."

Smithy suddenly looked more closely at the screen.

"The only thing I don't like about your picture," he remarked, severely, "is that you've got your line coils connected back-to-front. The letter 'C' in the Test Card is right way round in the mirror only!"

Dick switched off the receiver and reversed the line coil connections.

"Dear, dear," continued the Serviceman, "you'll never learn! Why on earth don't you do what I and almost every other service engineer in the country does? That is: just jot down on a scrap of paper the connections to an unfamiliar component before you remove it. There's nothing clever in trying to remember connections, because you're bound to make a mistake at some time or another. And a mistake in wiring could quite easily have disastrous results."

More Hamlet

"In this case, for instance," grinned Dick, "I might have had to 'shuffle off this mortal coil' again."

The Serviceman groaned.

"Cracks of your own making are bad enough," he complained, "but when you borrow them from Shakespeare they become terrible."

But Smithy's reference to Shakespeare and to borrowing had caused Dick, once more, to transplant himself into his own private world of the footlights.

"Neither a borrower nor a lender be," he intoned.

"For loan oft loses both itself and friend;
And borrowing dulls the edge of husbandry."

Dick paused for a moment.

"That's part of Polonius's speech in Act I," he remarked, in a patronising manner.

"If you don't look out," replied Smithy, threateningly, "you'll come to the same end as Polonius did in Act III."

"We haven't got as far as that yet," exclaimed Dick, alarmed. "What happened to Polonius?"

"Hamlet stabbed him," said the wrathful Smithy, "through the arras."

FORREST

Transistor Transformers

H. W. Forrest (Transformers) Ltd., 349 Haslucks Green Road, Shirley, Solihull, Warks, have submitted samples of two types of Transistor Transformers newly added to their well-known range of such components.

The windings are wound on a new type of core on which the company are able to produce a wide range of ratios for either single-ended or push-pull stages. These two new types make a total of six different core sizes now manufactured for this type of transformer.

The first of the types submitted measures some $1\frac{1}{2}$ in. x $1\frac{1}{10}$ in. x $\frac{3}{8}$ in. and the second $\frac{3}{8}$ in. x $\frac{1}{2}$ in. x $\frac{1}{2}$ in.

The company specialise in manufacturing transformers of all types, singly for use by constructors or in production runs for manufacturers. Most types can be produced extremely quickly and a large stock of transformers is held. A stock range of transistor transformers to suit the majority of requirements called for in transistor circuits is available by return.

UNDERSTANDING

TELEVISION

PART 20

By W. G. MORLEY

The twentieth in a series of articles which, starting from first principles, describes the basic theory and practice of television

IN THE LAST ARTICLE IN THIS SERIES WE continued with the video amplifier stage, and we discussed the various circuit devices which may be employed to ensure that a suitable frequency response is obtained from this stage. We then commenced to examine the coupling between the video amplifier and the cathode ray tube, pointing out that it is usual in modern receivers to apply the video signal to the cathode of the cathode ray tube rather than to the grid.

Brilliance and Contrast

In order that a cathode ray tube may adequately handle the signal passed to its modulating electrode by the video amplifier, it is necessary for two basic requirements to be satisfied. Firstly, the video signal must have an amplitude which enables the range of intermediate shades in the picture between black to white to be reproduced correctly, and secondly, the cathode ray tube must operate under correct bias conditions. These two points will now be considered separately.

To help in illustrating the first requirement, Fig. 112 (a) shows an instance where the video signal applied to the cathode ray tube

is too small in amplitude. It will be seen from the diagram that, whilst black level appears at approximately the correct point on the grid voltage/brightness characteristic, peak white corresponds to a markedly low brightness level. In Fig. 112 (b) we see a signal which, this time, is too large in amplitude. Whilst black level is, once again, applied to approximately the correct part of the characteristic, peak white level now appears at a point well outside the range of input voltages which the tube can handle. As a result almost all signal levels above that which corresponds to zero grid voltage are reproduced on the screen at maximum brightness. Fig. 112 (c) indicates the state of affairs which results when the video signal has correct amplitude. In this case both black and peak white levels appear at their correct points on the characteristic, intermediate levels corresponding, as they should do, to intermediate brightness levels.

In practice, it is necessary to fit a control to the television receiver which is capable of varying the amplitude of the signal applied to the cathode ray tube. This control is known as the *contrast* control. The contrast

control is actually a gain control; and it varies the overall gain, between aerial and cathode ray tube, of the receiver. If the contrast control is set to too low a level the gain of the receiver becomes reduced and the signal applied to the cathode ray tube may have the appearance of that shown in Fig. 112 (a). Such a picture would be described as having low, or insufficient, contrast. If the contrast control is set too high the gain of the receiver becomes excessive, with the result that the signal applied to the cathode ray tube may resemble that of Fig. 112 (b).¹ In this case the resultant picture would be described as having excessive contrast. When the contrast control is set to its proper level the gain of the receiver becomes such that a signal of correct amplitude, as in Fig. 112 (c), is applied to the cathode ray tube.

the contrast control alter the grid bias of one or more valves in the i.f. strip or tuner unit, thereby varying the gain provided in this part of the circuit and, hence, the overall gain of the receiver. An occasionally met variant consists of making the anode load of the video amplifier a variable potentiometer; whereupon this potentiometer becomes the contrast control. The slider of the potentiometer couples to the modulating electrode of the cathode ray tube in much the same manner as the slider of a volume control connects to the grid of an a.f. amplifier valve. Contrast control circuits of this type require especial care in design to ensure that stray capacities do not cause alterations in frequency response at different contrast levels.

The second of the requirements for correct handling of the video signal (that of ensuring

voltage does not appear on the screen at all. In Fig. 113 (b) the cathode ray tube is under-biased. In this instance half the video signal becomes reproduced at a single level—that of maximum brightness. Also, the sync pulses now become fully visible in the picture. It is only when the tube is correctly biased that we can obtain the state of affairs which we saw in Fig. 112 (c), wherein the peak white and black levels took up their correct positions on the characteristic.

To ensure that the cathode ray tube is correctly biased it is necessary for the television receiver to be provided with a control which varies the voltage on either its grid or its cathode. Such a control is known as the *brightness* or *brilliance* control. It is usual, when the cathode ray tube is cathode-modulated, to apply the variable bias provided by the brightness control to the grid and vice versa.² The circuit arrangements employed for providing the variable bias voltage are basically very simple, a typical example being illustrated in Fig. 114 (a). In this diagram the cathode ray tube is cathode-modulated and the variable bias voltage is obtained from a potentiometer connected in series with two fixed resistors across the receiver h.t. supply. It is assumed that the cathode has a potential which lies between chassis and the h.t. positive line. When the brightness control varies grid voltage, as it does in Fig. 114 (a), the combined resistance of the variable and fixed resistors in series normally lies between 200k Ω and 1M Ω . The use of relatively high resistance values of this order is desirable because, apart from keeping h.t. current consumption and heat dissipation in the three resistors to a low value, it also prevents the flow of excessive grid current if the brightness control is set to too high a level. At normal settings of the control, grid current is negligible. The condenser bypassing the slider of the brightness control to chassis ensures that the grid of the cathode ray tube stays at a steady potential (from the point of view of video frequencies) relative to cathode. In Fig. 114 (b) we see a brightness control circuit applied to the cathode of a grid-modulated tube. The method of operation here is similar to that of Fig. 114 (a) with the exception that the cathode current of the cathode ray tube now flows through that part of the brightness control network which appears between the slider and chassis. The cathode current of a cathode ray tube is normally of the order of 100 to 200 μ A only, but this is still sufficiently high to make it desirable to use slightly lower resistance values in the brightness control

² In American receivers, however, it is frequent practice to apply the variable bias to the cathode of cathode-modulated tubes. In this case the video signal is applied via a series condenser.

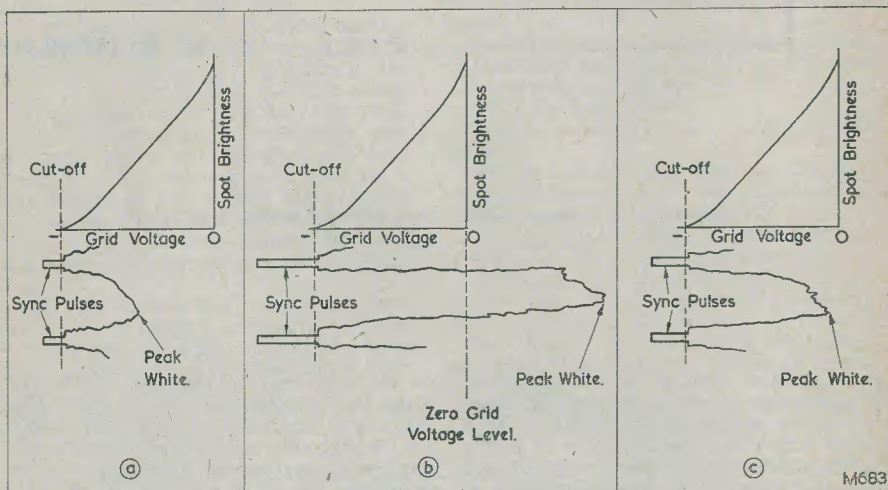


Fig. 112 (a) The effects of applying a video signal of low amplitude to the cathode ray tube. In this instance black level appears at approximately the correct point on the grid voltage/brightness characteristic, but peak white corresponds to a very low brightness level. (b) In this diagram a signal of excessive amplitude is applied to the cathode ray tube. Once again it is assumed that black level appears at approximately the correct point on the characteristic. However, most of that part of the signal to the right of zero grid voltage level will be reproduced at maximum brightness. (c) When a signal of correct amplitude is applied to the cathode ray tube, both black and white levels appear at their correct points on the characteristic

The manner in which the contrast control varies the gain of the receiver is liable to vary somewhat between receivers of different manufacture and design. Generally, the basic method of operation consists of having

¹ This assumes that overloading does not take place in the video amplifier stage. Such overloading would result in compression of that part of the signal which approaches peak white.

correct cathode ray tube grid bias) is demonstrated in Fig. 113. In Fig. 113 (a) a video signal of correct contrast level is applied to the cathode ray tube, but an acceptable picture is not reproduced because the tube is over-biased. The result is that only half of the video signal becomes applied to the grid voltage/brightness curve, and that that part of the signal which falls outside cut-off

network. In Fig. 114 (b) the combined resistance of the variable and fixed resistors in series would normally be in the region of 100 to 200 k Ω . Again a bypass condenser connects between the brightness control slider and chassis. In both Figs. 114 (a) and (b) this bypass condenser would have a value of 0.01 to 0.1 μ F.

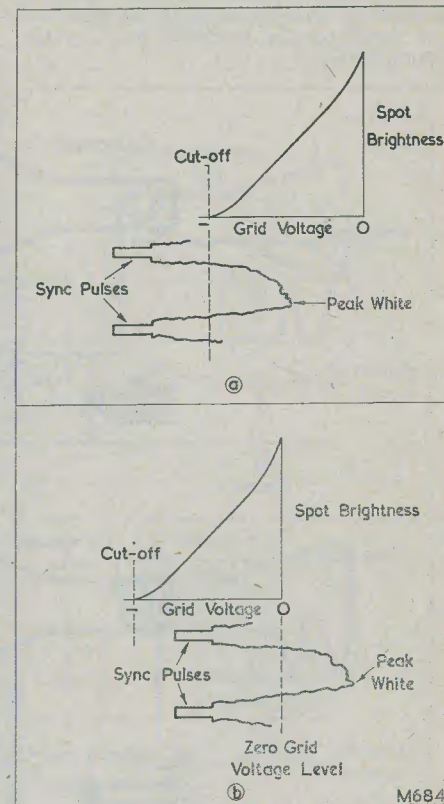


Fig. 113 (a) In this diagram a signal of correct amplitude is applied to an over-biased cathode ray tube. In consequence, only that part of the signal to the right of cut-off level is reproduced. (b) The effect given when the cathode ray tube is under-biased. All parts of the signal are reproduced at an elevated brightness level, most of that part to the right of zero grid voltage level giving maximum brightness. It should be noted that signal amplitudes in this diagram and in (a) are correct and that combinations of incorrect biasing and incorrect amplitude would give further variations on the examples illustrated

It frequently happens that, in practical receivers, a relatively low value resistor is connected between the slider of the brightness control and the controlled electrode. Such a resistor would be fitted at the points marked with a cross in Figs. 114 (a) and (b). The purpose of this resistor is to prevent the occurrence of excessive grid current during certain transitory conditions, such as occur immediately after switching off the receiver.³ The series resistor normally has a value around 30k Ω

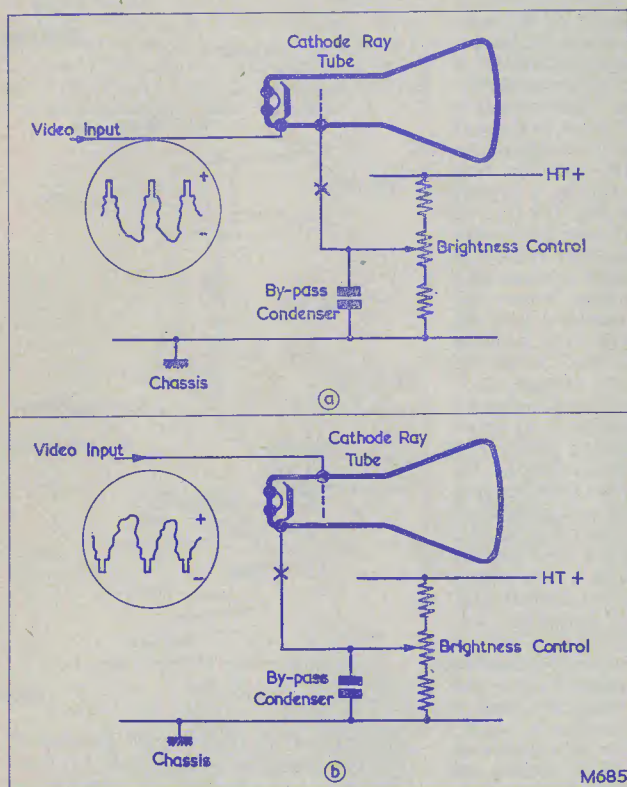


Fig. 114 (a) A simple brightness control circuit for a cathode-modulated tube. It is assumed that the cathode has a potential lying between chassis and the h.t. positive line. (b) A brightness control circuit for a grid-modulated tube. It is assumed in this case that the grid has a potential lying between chassis and the h.t. positive line.

Cathode-Heater Voltage

Due, mainly, to the necessity of keeping

³ With some circuit arrangements it is possible, immediately after switching off, for the potential on the cathode ray tube cathode to fall at a greater rate than the potential on the grid. This effect could occur, for instance, if the potential on the cathode of Fig. 114 (a) were proportional to the main h.t. voltage. The voltage across the main h.t. smoothing condenser (and hence the potential on the cathode) might then fall, immediately after switching off, at a greater rate than the voltage across the brightness control bypass condenser, this being due to different rates of discharge in the two condensers.

the voltage between heater and cathode of the cathode ray tube to a safe level (in order to prevent breakdown between these two electrodes) it is necessary to take special precautions in the circuit arrangements which couple the video amplifier anode to the modulating electrode of the cathode ray tube.

Fig. 115 (a) illustrates the case in which the video amplifier anode connects directly to the cathode ray tube. Under these conditions the cathode is liable to rise almost to full h.t. potential during the period when the video

amplifier is near cut-off. The cathode may rise to an even higher potential during warm-up time if the full h.t. voltage appears before the video amplifier valve draws its full working current. It should not be forgotten also that the heater of the cathode ray tube may attain a negative potential with respect to chassis and that when cathode heater voltages are being evaluated, this negative voltage should be added to the positive potential above chassis held by the cathode. In the example shown in Fig. 115 (a) two

valve heaters appear in the series heater supply "chain" between the cathode ray tube heater and chassis; with the result that the heater of the cathode ray tube will go negative of chassis by a potential equal to the peak voltage dropped across the three heaters once during every cycle of the mains supply.

much simpler to reduce the potential on the cathode of the cathode ray tube by other means whilst still maintaining a satisfactory coupling for the video signal.

Fig. 115 (b) shows that much the same cathode-heater voltage problem exists when a direct connection is provided between the video amplifier anode and the cathode ray

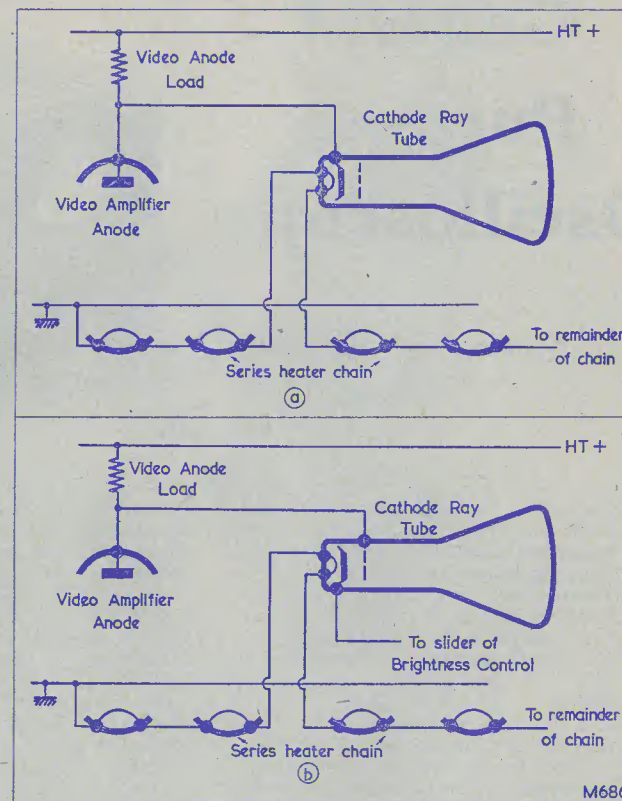


Fig. 115 (a) Whilst a direct connection between video amplifier anode and tube cathode is very desirable, it introduces high cathode-heater potential differences which could cause breakdown between these two electrodes. (b) High cathode-heater potential differences still exist when the cathode ray tube is grid-modulated by a direct connection to the video amplifier anode. This is because, for correct operation, it is necessary for the brightness control to provide a potential for the cathode which is higher than that held by the grid

The limiting safe voltage permissible between cathode and heater of a typical cathode ray tube is normally 200 volts only.⁴ In consequence, the h.t. voltage applied to the video amplifier anode of Fig. 115 (a) would need to be markedly lower than this figure if cathode-heater breakdown in the cathode ray tube were to be avoided. Whilst it would not be impossible to design a video amplifier stage capable of working at an h.t. voltage considerably lower than 200, it is

tube grid. To obtain a correct brightness level in this case it is necessary for the cathode of the cathode ray tube to be positive of the grid, whereupon this electrode must obviously take up a potential at least as high as that given by the cathode-modulated circuit of Fig. 115 (a) under normal operating conditions.

Next month


In next month's article we shall see how the cathode-heater voltage problem is solved in modern receivers and shall carry on to consider a.c. and d.c. couplings.

⁴ This figure applies when the heater is negative of the cathode and is quoted by Mullard for most cathode ray tubes in their range.

The JASON OG.10

General Purpose Oscilloscope

by G. Blundell and M. Smutny

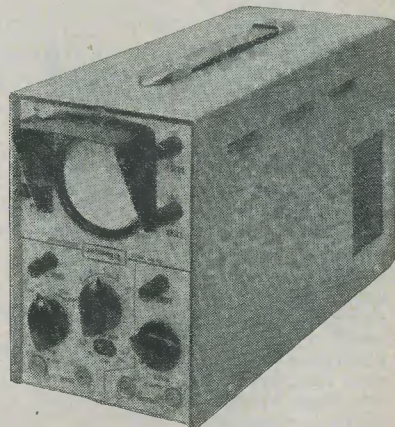

Part Two

SINCE PART 1 OF THIS ARTICLE APPEARED, improved accuracy on the voltage calibrator has been achieved by substituting the following values for those given in the Components List: R_{23} $220k\Omega$ 5% hi-stab; R_{24} $39k\Omega$ 5% hi-stab; R_{25} $10k\Omega$ 5% hi-stab. An error occurred in the Components List— C_{13} should have read $0.05\mu F$ 750V wkg.

X Amplifier


The X amplifier consists of V_6 (ECC82), a double triode connected as a "long-tailed pair." When the signal applied to the input grid is such that the anode current in the first triode increases, the anode potential falls and the voltage appearing across R_{45} and R_{46} increases making the grid of the second triode more negative in relation to the cathode, and so decreasing the current and raising the potential at the second anode. In other words, the signals appearing at the anodes are in push-pull, the component values being so chosen that they are substantially equal. The grid of the second triode is held at a steady potential which can be varied by means of VR_8 to provide a horizontal shift of approximately 6cms (1 screen diameter). The horizontal deflection plates of V_7 (DH7-91) are directly coupled to the anodes of V_6 . Although the shift voltage is applied to one grid only, as explained previously, the

current in both halves of the valve is shifted, and therefore a push-pull shift voltage is obtained without an expensive twin potentiometer.

Y Amplifier

The Y amplifier built into the oscilloscope makes use of three valves V_1 and V_3 (ECF80) and V_2 (EF80).

The triode portion of V_1 is connected as a cathode follower, its grid being connected to two panel sockets, one giving a ten-to-one reduction in sensitivity by means of the attenuator formed by R_1 and R_2 . C_1 is connected across R_1 to provide a flat frequency response. The output of the cathode follower is coupled via an electrolytic capacitor (C_3) to a potentiometer (VR_1) which provides a continuously variable gain control. The slider of the potentiometer is connected to the grid of the pentode portion of V_1 . High frequency response correction is applied to this stage in two ways. Firstly the bias resistor (R_8) is bypassed by a small capacitor (C_4) of $1,000pF$ which begins to be effective at about 1 Mc/s. Secondly the anode load is made up of an inductor (L_{42}) and a resistor (R_6) in series. As the operating frequency increases, the impedance of L_{42} increases to offset losses caused by stray capacitance to earth and the input capacitance

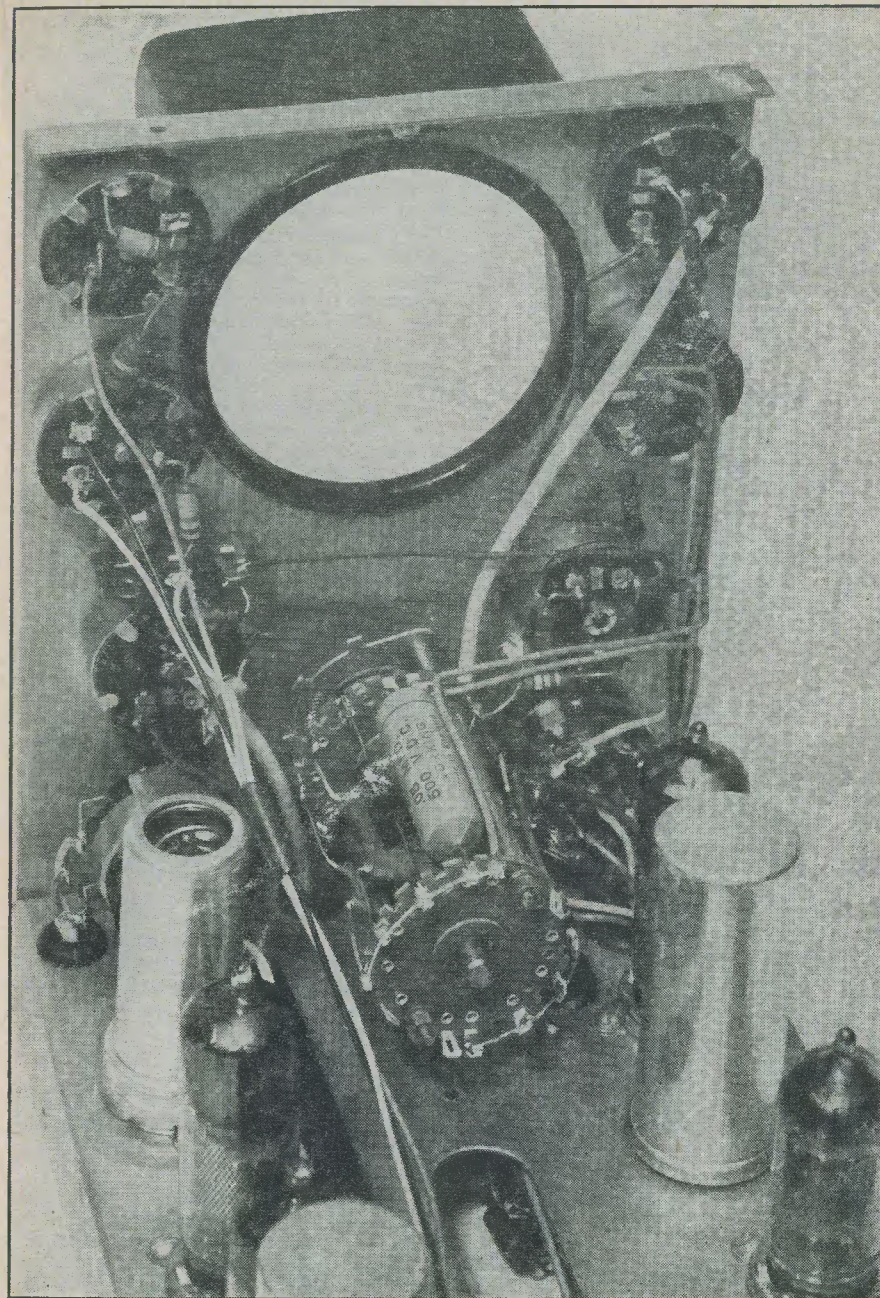

This illustration shows the switch, detailed in Fig. 5, mounted on the front panel detailed in Fig. 3

of the following stage. These stray capacitances shunt the resistive portion R_6 of the anode load. V_2 (EF80) and the pentode portion of V_3 (ECF80) are again connected as a "long-tailed pair." Frequency compensation is again obtained by means of inductors L_{43} in the anode circuits. A vertical shift of about 6cms (1 screen diameter) is provided by VR₂. The vertical deflection plates of V_7 (DH7-91) are directly coupled to the anodes of V_2 and V_3 by means of leads running through thick walled p.v.c. sleeving to reduce anode-to-anode capacitance by ensuring that the leads are adequately spaced. A frequency response within 1dB from 10 c/s to 1 Mc/s and within 3dB to 2 Mc/s, together with a sensitivity of 6mV r.m.s./cm, are obtained.

Notes on Assembly

The assembly follows normal practice for fixing valveholders, tagstrips, etc., details showing the disposition of parts being shown in Figs. 2 to 4, and only a few points require explanation.

(a) *Mains Transformers.*—The mains transformers must be mounted exactly as shown in Fig. 2, i.e. not turned through 180°. otherwise the magnetic fields will be adding instead of cancelling. The white lead coded red on transformer MT55 must be connected to chassis.

(b) *Front Panel.*—The front panel is secured to the chassis by eight 6BA x 1/4 in screws which also hold the four co-axial sockets in position. It will be found easier to fit all components to the front panel before it is screwed to the chassis.

The 3/16 in long 6BA screws provided must be used for fixing the preset type potentiometers, as longer screws will lock the centres. The condensers together with flying leads as shown on Fig. 5 should be soldered to switch S_1 before it is fixed to the panel. Flying leads should also be soldered to the "CAL" socket before this is screwed to the panel. The two switches and the Y gain control (VR₁) are each provided with two nuts. These should be located one in front and one behind the panel and set so that the end of the fixing bush is just level with the front nut.

(c) Condensers C_6 and C_9 are mounted so that the three lugs pass through the appropriate slots in the chassis. These are then twisted with a pair of flat nosed pliers to anchor the component firmly. Only a small twist is required as there is danger of breaking these tags.

(d) *Cathode Ray Tube.*—One length of the plastic foam tape provided should be stuck around the neck of the tube near the metal end and a second length around the conical portion just where it joins the neck. These will hold the tube firmly in place when it is

slid inside the mu metal shield. The mu metal shield is screwed to the chassis by 4BA self-tapping screws. The tube is placed in the shield before it is fixed to the chassis.

(e) The black p.v.c. extrusion is fitted round the edge of the large front panel hole to provide a mask for the cathode ray tube. The upturned flange on the light shield is pushed through the slot at the top of the front panel and screwed in place.

(f) The cover and base are fixed to the chassis with the same four 4BA self-tapping screws. The foam rubber feet are first inserted in the four holes in the corners of the base. This is then placed in position inside the chassis so that the four fixing holes line up with the corresponding holes in the chassis. The cover can then be slipped over the instrument and fixed in place by means of two 4BA self-tapping screws on each side screwing into the flange on the base. To hold the front panel firmly in place, two 4BA self-tapping screws are used which pass through the top of the cover and screw into the horizontal flange on the panel.

Wiring Notes

(a) The components shown on the wiring diagram Fig. 2 and front panel diagram Fig. 3 are not drawn to scale, but indicate the connection and appropriate position taken up by each component.

(b) The wiring diagram should be followed during assembly, but to gain familiarity with the instrument it should at every stage of the assembly be compared with the circuit diagram.

(c) Wires and component leads should be pushed through and wrapped around tags and valveholder pins to ensure a firm mechanical connection. No tag or valveholder pin should be soldered until all the leads and components on that particular tag or pin are in place and have been checked.


(d) Connecting wires should be straight with sharp distinct bends and be run flat touching the chassis.


Wiring Procedure

(a) Earth the centre spigot and appropriate pins on each valveholder to a soldering tag as shown in Fig. 2. In general, this can be done with bare wire.

(b) Run the wire connections as shown in the wiring diagrams Figs. 2 and 3. It is easier to do this before the components are wired in. Connections running from the underside to the top of the chassis are lettered to facilitate tracing on the drawings. Leads running to the cathode ray tube should be of flexible wire.

(c) Connect up the remaining components.

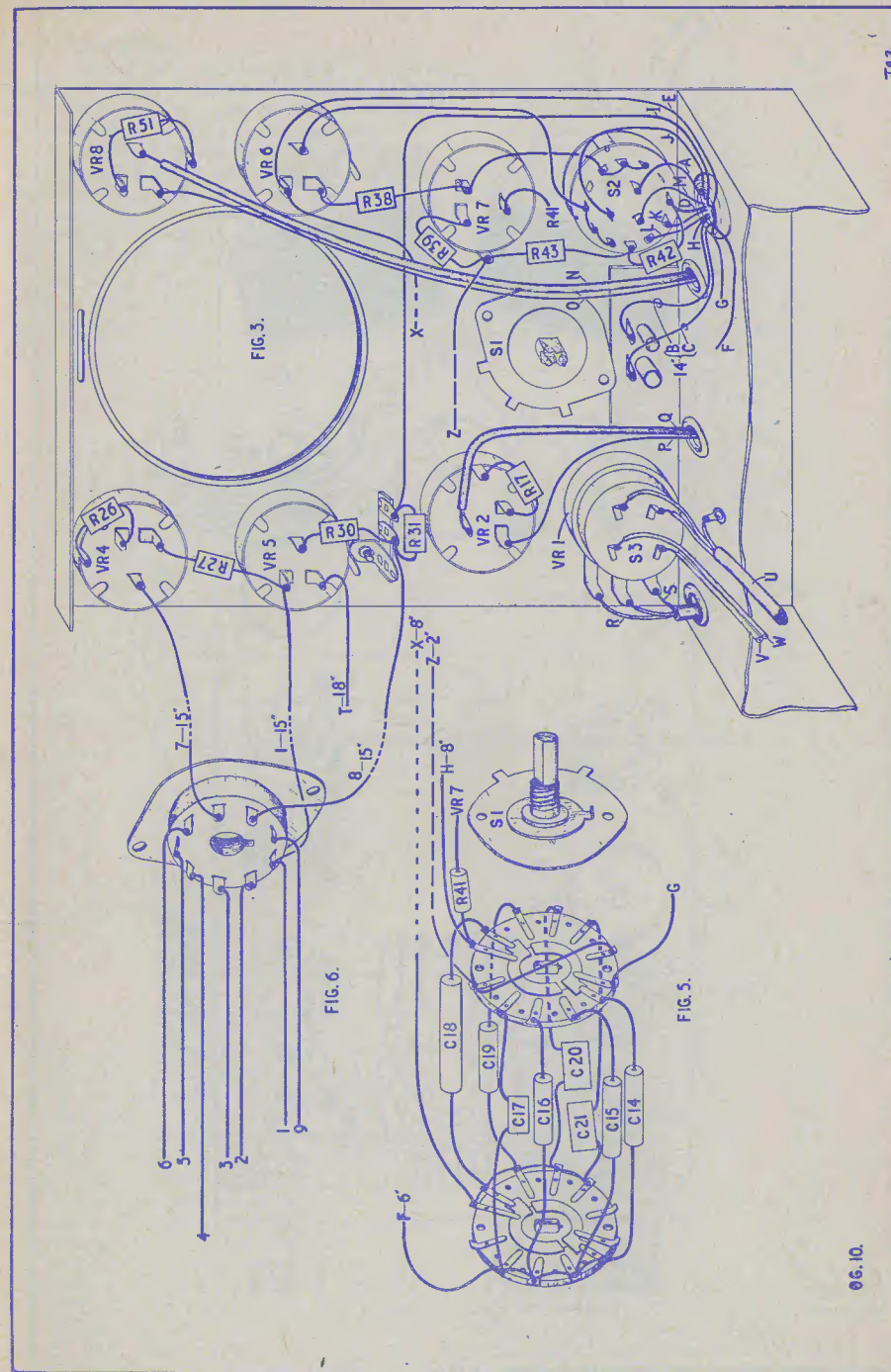

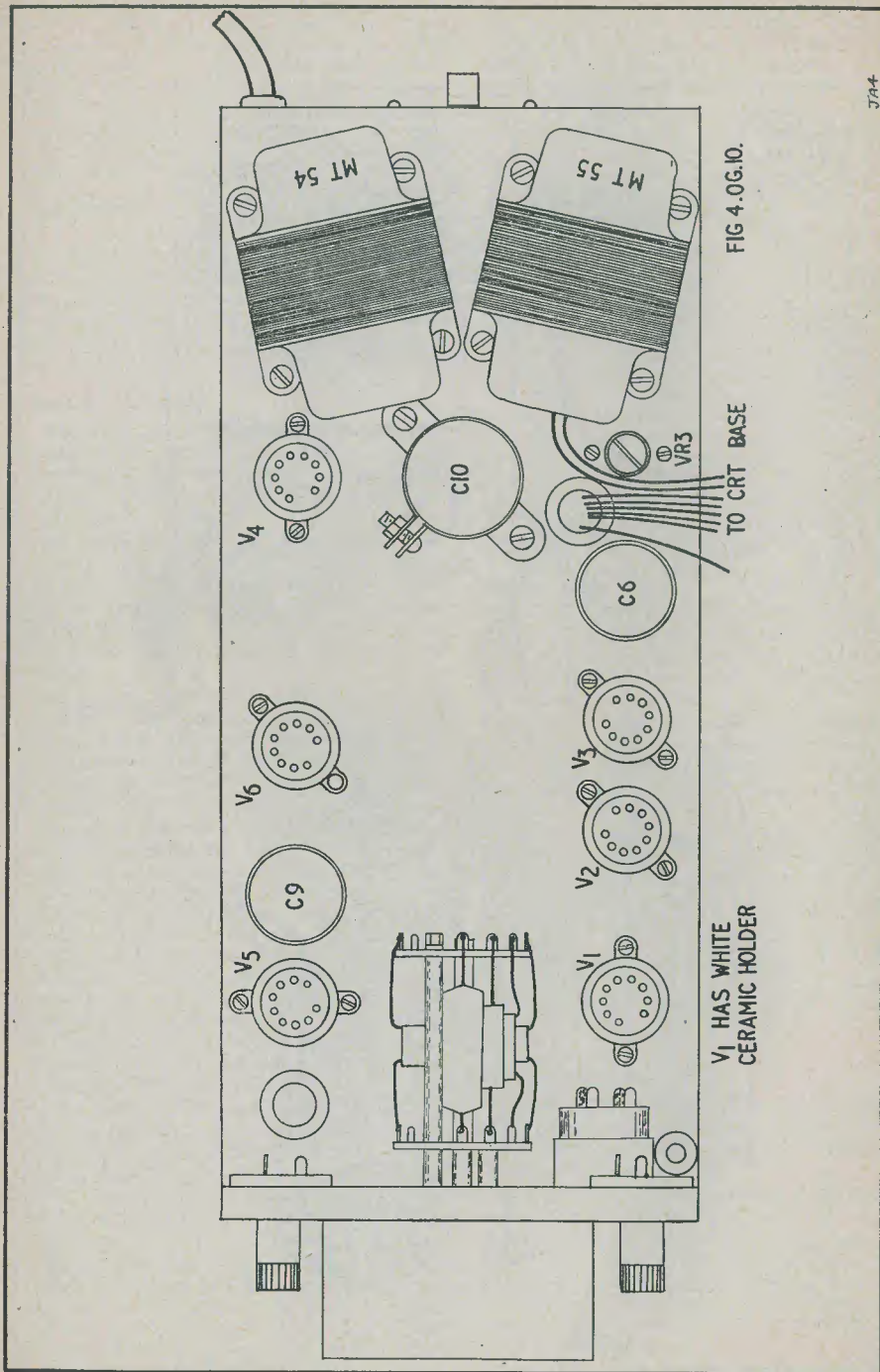


THE RADIO CONSTRUCTOR

Testing Procedure

(a) Check all wiring carefully. Time spent in careful checking of wiring is always well spent, as any mistakes can be rectified without any damage to components.

(b) With the valves and cathode ray tube in place, the X and Y shift controls and width and focus controls set about half-way, and the brilliance control set fully clockwise, a blurred horizontal line should be visible on the screen. Centre the line on the tube by means of the X and Y shift controls and reduce the brilliance to a normal level.

C _{6a}	190V
C _{6b}	90V
C _{9b}	100V
Pin 8, V ₁	40V
Pin 7, V ₁	1V
Pin 3, V ₁	80V
Pin 6, V ₁	50V
Pins 1 & 3, V ₂	30V
Pin 7, V ₃	150V
Pin 8, V ₂	
Pin 3, V ₃	150V
Pin 7, V ₂	
Pin 6, V ₃	150V

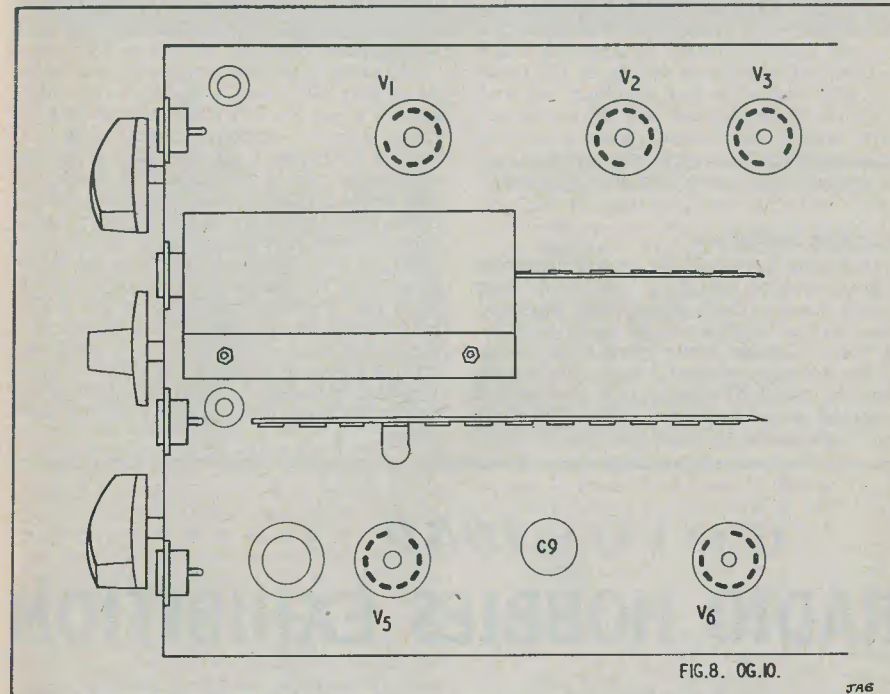

Measure the voltages appearing on the anodes of V₆. If they are not equal, turn the X shift control slightly until they are. Carry out the same procedure at the anodes of V₂ and V_{3a}. The two voltages should be almost the same (150V). Next connect the meter to the slider of the astigmatism control (VR₃) and turn the spindle until the voltage obtained is the mean of the previous two. It will now be possible to obtain a perfect focus.

The following voltages, which were measured with a 10,000 ohm V/meter, should be obtained. Due to variations in components, the actual voltages measured will differ slightly from those given.

Pin 3, V ₄	310V
Junction R ₁₉ -R ₂₀	250V

Pin 1, V ₃	20V
Slider VR ₃	150V
Pin 8, V ₅	75V
Junction R ₃₂ -R ₃₄	70V
Pin 7, V ₅	63V
Pins 8 & 3, V ₆	20V
Pins 6 & 1, V ₆	150V
Junction R ₂₆ -VR ₄ *	-320V
Junction VR ₄ -R ₂₇ *	-440V
Junction R ₂₇ -VR ₅ *	-620V
Junction VR ₅ -C ₁₂ *	-680V


* Note.—These are negative voltages and must be measured with the positive terminal of the meter connected to chassis.

If no meter is available, the following procedure should be followed. Turn the coarse speed control clockwise to the position

it is operating. It is usually possible to observe the arcing within the valve by viewing it under darkened conditions where an occasional flashover may be visible, usually at either the top or bottom of the electrode assembly.

A similar effect which may be less severe but which is nevertheless most puzzling when encountered for the first time is that which causes the random displacement of the lines as shown in Fig. 1. Although in the majority of modern receivers the vertical sides of the raster are not visible this horizontal shift of some of the scanning lines will cause the vertical edges in a picture to become ragged. This effect has been investigated at great length by both circuit and valve engineers, and it was generally tracked down to a leakage of the high potential which appears at the anode top cap travelling down the glass bulb to the base. This charge will go to earth via the valve pins, and that which leaks on to the grid pin will cause a small change in the grid voltage thus causing the spurious signal in the line deflection coils.

has the effect of producing a fairly well defined narrow white band from top to bottom of the picture and is usually in the left half section. Some readers will no doubt remember this form of oscillation being described in some of the introductory books on radio theory where it was shown to be produced by electrons oscillating at high velocity about the control grid; a condition which can occur when either the screen grid or anode falls below the potential of the control grid. During the line flyback period, the negative overshoot on the anode of a line output valve is often in the region of 1,000V, which is more than sufficient to produce Barkhausen oscillation. The oscillation occurs at an exceptionally high frequency and the tuned circuits associated with it can be formed by the leads to the anode, control grid or cathode of the valve. The cathode is usually earthed, and the effect of Barkhausen oscillation on the picture can often be eliminated by reducing the length of the cathode lead and making sure that it is well bonded down to the chassis. In many

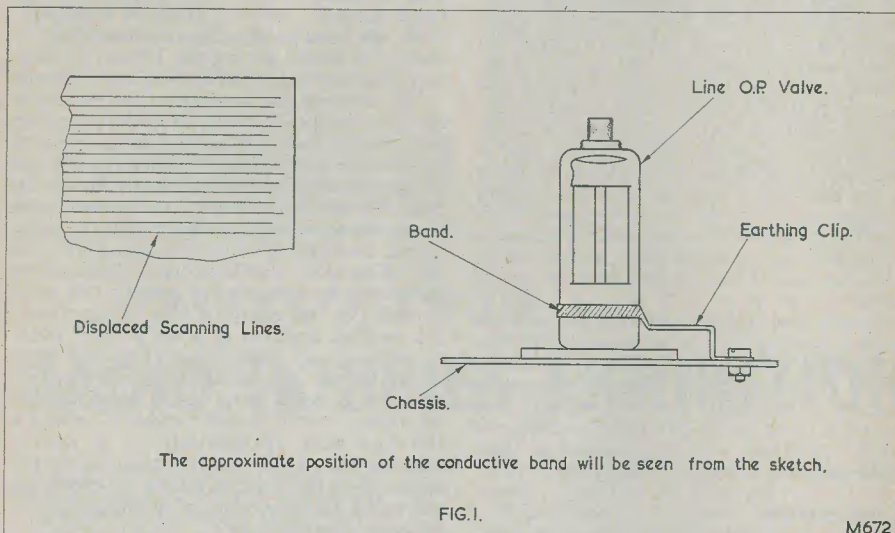

The leakage can be prevented from reaching the grid pin by painting a thin band of conductive paint around the bulb about $\frac{1}{8}$ in above the pins and earthing it by means of a thin spring clip which is screwed down to the chassis. Aluminium paint is suitable for the band but care should be taken to ensure that there is no paint on the bulb above the level of the bottom mica which is used to support the main electrode assembly.

Another fault which is associated with line output valves is Barkhausen oscillation. This

receivers this lead is reduced to $\frac{1}{4}$ in in length. If this does not improve the position, the use of an anode stopper (22Ω) or a grid stopper ($1k\Omega$) should be tried out as an alternative cure.

Thermal Effects

We classify under this heading all those effects which become apparent after the valve has been in use for a short period, and has attained its full operating temperature. Usually these defects manifest themselves as

either a reduction in scan, or a reduction in e.h.t. voltage, and become apparent after the receiver has been operating for some minutes after being switched on from cold. The cause of the trouble is usually either primary or secondary emission from the control grid, screen grid or anode. Anode emission will usually only have the effect of damping the negative overswing on the anode during the flyback period, because during this time electrons will leave the anode and travel to the screen grid. Unless very severe, this fault will not show up on the picture but will simply result in a small loss of e.h.t. Emission from the screen grid can, however, be rather more serious as in this case the electrons will leave the screen and flow towards the anode during the part of the flyback period when the anode is highly positive. This will reduce the amount of energy fed into both the scanning coils and the e.h.t. circuit, causing a reduction in both width and e.h.t. potential. As a reduction in e.h.t. will increase the deflection sensitivity of the picture tube, these two effects are partially self-cancelling as regards the width of the picture, but there will be a tendency for the height to increase. As the screen emission becomes worse, the e.h.t. voltage will decrease still more with a further increase in height and a deterioration in picture brightness. Emission from the control grid of the valve is least likely to occur, but when it does it will manifest itself

as a reduction in width and worsening of the line linearity which will become apparent some minutes after the receiver has warmed up. As with the other faults listed under this heading, the only cure is to renew the valve.

Insulation

The majority of line output valves run at fairly high temperatures, the bulb temperature often being in the region of 200°C , and under these conditions there is always a tendency for metallic deposits to be formed on the insulating parts within the valve. These insulating parts are normally for the purpose of either supporting or spacing the electrodes correctly, and the deposits as they build up will become apparent as a darkening of these parts of the valve. Such metallic deposits are conductive, so that after many thousands of hours use they may impair the inter-electrode insulation of the valve. This will in time become apparent by either producing internal sparking within the valve or by a reduction in the control grid insulation. This latter will show up first because of its adverse effect upon both the line linearity and width of the scan. Once again the only cure is to renew the valve.

We hope that this short survey of the faults which may occur in line output valves will assist readers in diagnosing the causes for one or more of the defects which have been described.

Courses for Radio Amateurs Examinations


Bradford Technical College

A course in preparation for the City & Guilds of London Institute's Radio Amateurs Examination will be held at Bradford Technical College on Thursday evenings from 7 to 9 p.m. Registration takes place on September 16, 17 and 18, 1959. Prospective students should contact the College for further details. Telephone 21748.

Grafton Radio Society

Grafton Radio Society announce that they have again made arrangements with the Holloway L.C.C. Evening Institutes for official courses in the Radio Amateurs Examination and Morse (both for beginners) to be held this winter at the Montem School, Hornsey Road, Holloway, London, N.7. The

classes will meet on Mondays, with a repeat lecture on Tuesdays and Wednesdays, commencing Monday, 28th September, for the Radio Amateurs course at 7-9 p.m. (Instructors: S. H. Iles, G3BWQ; P. F. Bernal, G3KQZ; R. C. Hills, G3HRH); followed by the Morse at 9-10 p.m. (Instructors: L. Barber and A. Ralph). The fee for either course is 20s., or 22s. 6d. for the two, and application in the first instance should be made to the Hon. Secretary of the Grafton Radio Society: A. W. H. Wennell (G2CJN) 145 Uxendon Hill, Wembley Park, Middlesex, so that a place may be assured. In the City & Guilds examination held last May another 26 passes were obtained, making the grand total of 111 in the six years this course has run. In addition to the above, the club meets on Friday evenings commencing 4th September for the usual club activity and new members and visitors are especially welcome.

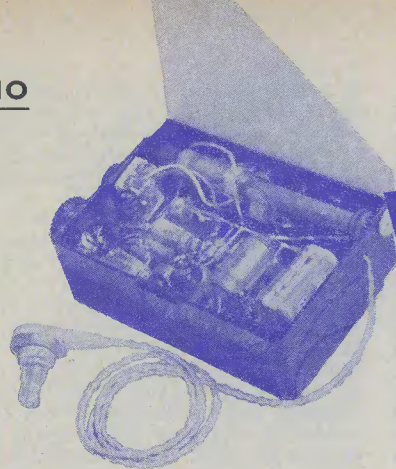

The MAJOR THREE Personal Transistor Receiver

Designed by D. J. French, GRAD.I.E.E.
of Henry's Radio Ltd.

THE POCKET PORTABLE TRANSISTOR RE-ceiver about to be described here is in logical sequence to the two earlier designs which were described in previous issues of this magazine. ("The Minor-One" and "The Major-Two"—see page 204, October 1958 issue.—Ed.) These were one- and two-transistor receivers respectively, which proved very popular with the home constructor fraternity. In the present design, three transistors—all Ediswan types—have been included, the circuit being that of a five-stage reflex receiver.

The "Major-Three" is fully tunable over the Medium wave range, and portability is ensured by the use of a Ferrite rod aerial together with the usual battery h.t. supply. Some three to six months of life may be expected from the battery specified—subject, of course, to the amount of usage. The whole receiver weighs only some 4 ounces and the "pocketability" may be judged by the overall size of 4½ in. x 3 in. x 1¼ in. It is contained in an attractive black and white moulded plastic case. The protruding controls are on/off switch and volume control combined, and tuning knob.

Circuit

This is shown in Fig. 1, from which it will be seen that it is a three-transistor five-stage reflex design. The transistor TR₁ functions primarily as an r.f. amplifier, the resultant r.f. signal being fed, via C₇, to the crystal diode. The signal is rectified here and then fed back, via the volume control and C₄, into the ferrite secondary winding and from thence into the base of the same transistor. The audio signal applied to the base of TR₁ is now amplified by the transistor and fed, from the collector and via the r.f. choke and C₅, into the base of TR₂. The amplified signal obtained from this second stage is now

passed, from the collector and via the inter-stage transformer, to the base of TR₃. From here, the audio output is taken via the collector to the deaf-aid insert. All three transistors operate in the earthed emitter mode.

Constructing the "Major-Three"

Constructors should note particularly the colour coding of both the ferrite rod aerial windings and the inter-stage transformer and ensure that these are correct—as given in the circuit diagram—when wiring these components into position. The correct polarity of both the electrolytic condensers and the battery should also be noted. As received, both the cabinet and the chassis are ready drilled and riveted.

With the exception of the volume control and the tuning condenser, the chassis should be wired up outside of the cabinet, the whole being assembled together when the chassis is wired, except for the two aforementioned components.

(1) Solder the bare wire to those solder tags forming the positive bar. Deal similarly with those tags forming the negative bar.

(2) Solder into position TR₁ holder (centre pin to one end of double solder tag).

(3) Connect C₂ (red to positive bar) and R₂ (black/brown/red) into circuit.

(4) Ensuring that the leads of RFC₁ are approximately 1 in. in length, solder this component into circuit, together with R₄ (yellow/mauve/red) and C₅ (0.1µF).

(5) Solder into position C₇ (47pF), and RFC₂.

(6) Connect the plain end of the diode to one end of C₇. Leave the red or dot end unconnected at this stage.

(7) Solder into position both R₅ (grey/yellow/blue) and R₆ (brown/black/orange).

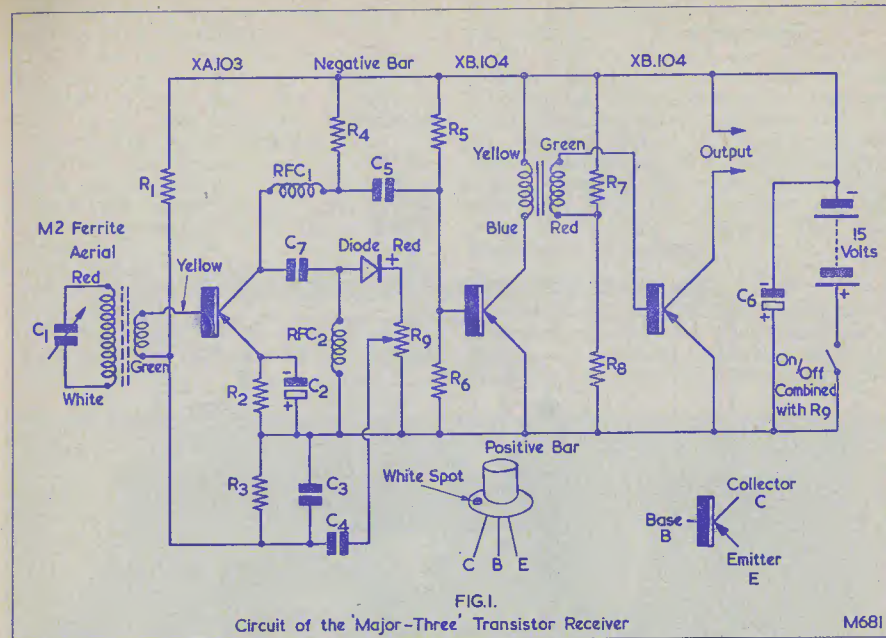


FIG. 1.
Circuit of the 'Major-Three' Transistor Receiver

M681

Components List

Resistors

- R₁ 100kΩ
- R₂ 1kΩ
- R₃ 10kΩ
- R₄ 4.7kΩ
- R₅ 680kΩ
- R₆ 10kΩ
- R₇ 100kΩ
- R₈ 4.7kΩ
- R₉ 10kΩ potentiometer w/switch

Capacitors

- C₁ 500pF trimmer
- C₂ 25µF electrolytic
- C₃ 0.005µF
- C₄ 0.1µF
- C₅ 0.1µF
- C₆ 100µF 18V wkg, electrolytic
- C₇ 47pF

Transistors

- TR₁ Ediswan XA103
- TR₂, TR₃ Ediswan XB104

Miscellaneous

- RFC₁, RFC₂ Henry's Radio Ltd.
- Ferrite Aerial, Type M2. Henry's Radio Ltd.
- Transformer type D240. Henry's Radio Ltd.
- 15V battery—Ever-Ready type B121
- Crystal diode
- Transistor holders
- Drilled cabinet and chassis. Henry's Radio Ltd.
- Deaf-Aid Insert. Henry's Radio Ltd.

To the junction of these two components, connect the other end of C₅ (0.1µF).

(8) Secure R₁ (brown/black/yellow) in position (one end only), and follow this by soldering R₃ (brown/black/orange) into circuit.

(9) On top of R₃ mount C₃ (0.005µF) and solder. Connect one end of C₄ (0.1µF) to the junction of R₃, C₃, leaving the remaining wire for the time being.

(10) Connect into circuit and join R₇ (brown/black/yellow) and R₈ (yellow/mauve/red).

(11) Solder into position the holder of TR₃ (third transistor).

(12) Secure into position the type D240 transformer and the holder of TR₂. Observe here the lead colour code of the transformer.

(13) Solder the deaf-aid insert leads but

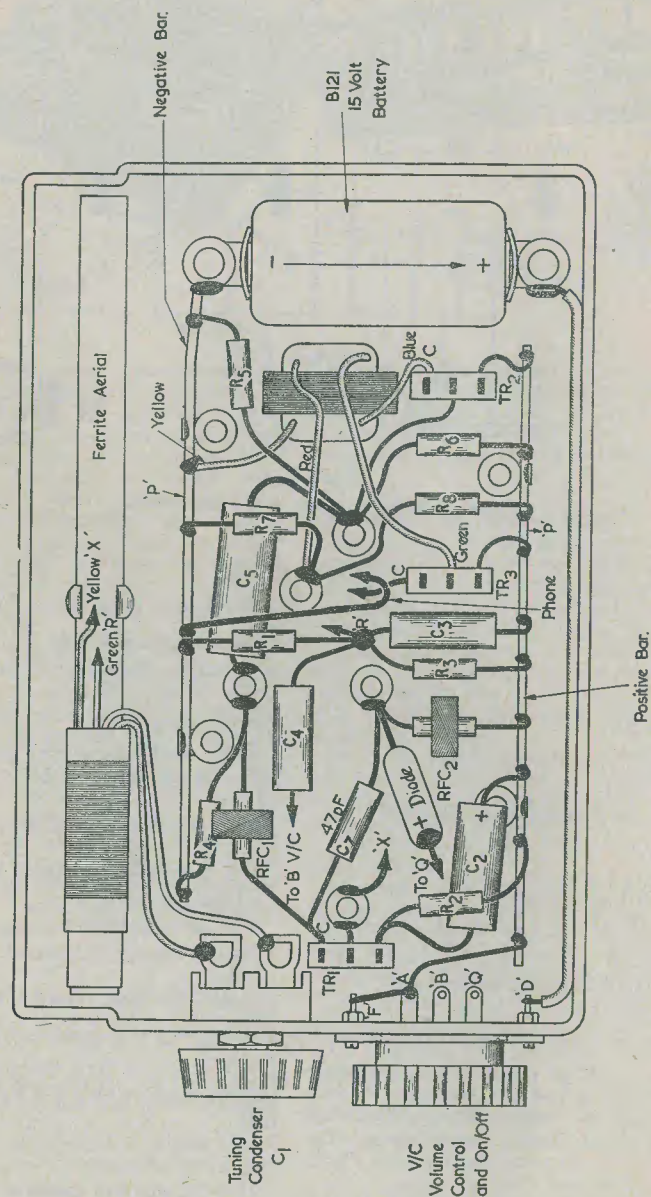


FIG. 2

leave the actual earpiece unconnected in order to prevent heat damage.

(14) Place the ferrite rod aerial assembly into the mounting clip and connect the secondary winding leads into position as shown on the circuit diagram. Leave these leads somewhat on the long side.

(15) Bolt the volume control and the tuning condenser to the side of the cabinet. Connect the remaining two leads of the ferrite rod primary winding to the tuning condenser.

(16) Connect C_6 (100 μ F) between points "PP" on negative and positive bars. (Black end to positive bar.)


(17) Solder the red or dot end of the crystal diode to "Q" tag of the volume control.

sistors are placed the correct way round, i.e. white dot at "C" on each holder.

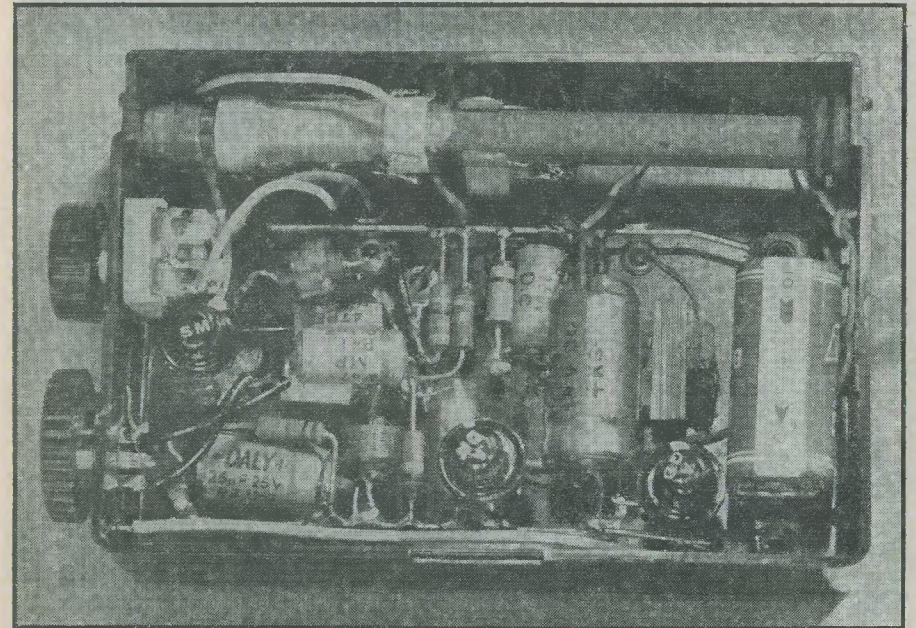(21) Thoroughly check the wiring before inserting the battery into position. Look especially for component wires touching each other where they should not be in contact at all. Ascertain that no "dry" joints have been made. Carefully check with the circuit diagram that the receiver has been correctly wired and with the illustration that the components occupy roughly the same positions as those shown.

Getting the Best Results

Once the receiver has been completed and is in working order, one small adjustment is capable of greatly increasing both the selectivity and sensitivity of the circuit. This



Inside view of the "Major-Three". Compare with Fig. 2

(18) Solder the remaining end of C_4 to tag "B" of the volume control and connect tags "A" and "F" of the volume control to the positive bar.


(19) Connect a lead from the positive battery connection to tag "D" of the volume control.

(20) Cut the transistor leads to about half an inch in length and plug these into the transistor holders thus: TR_1 , XA103; TR_2 and TR_3 , XB104. Ensure that these tran-

is achieved by the careful positioning of the choke RFC_1 in relation to the aerial winding on the ferrite rod assembly. This positioning of RFC_1 for optimum performance should be carried out with the tuning condenser set to the wavelength of strongest station receivable according to the location of the constructor. Should RFC_1 be positioned too near the aerial winding, a "bubbling" will be heard in the deaf-aid insert, in which case the r.f. choke will have to be spaced a greater distance from the winding.

The TOURIST

Portable Receiver

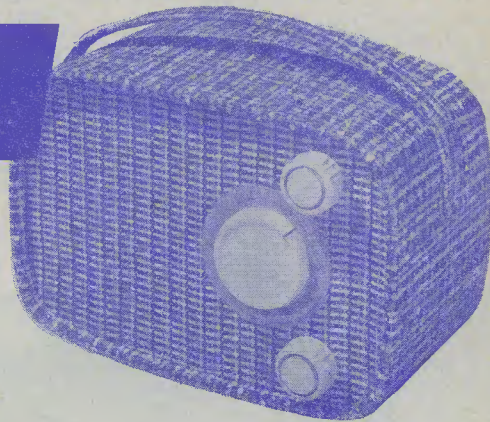

Described by
Alan G. Hepworth

AMID HOME CONSTRUCTOR CIRCLES, interest in the small portable receiver grows apace, evidence of this being the number and variety of such designs appearing in the radio press over the past few years. The portable receiver, as its title implies, must be one hundred per cent portable—which in turn suggests that it must be light in weight, be compact and efficient, and have convenience in shape. In addition to these factors, it must also be attractive in the sense of "eye appeal."

Such a receiver is the "Tourist"—a very apt name since the above conditions have been fully met on all counts. Utilising the latest type of circuitry, and giving an excellent performance combined with a low battery consumption, this really small and compact portable receiver has a high sensitivity combined with an excellent frequency response.

The completed receiver, including the battery, is housed within a cabinet measuring only some 8in x 5½in x 4in, and the total overall carrying weight is only 3½ pounds. It is apparent that a good deal of forethought and planning by the designers have gone into the production of this little receiver. The metal sub-chassis, as supplied, is completely pre-punched, with the valveholders already fitted into position. Likewise, the earthing metal tags and rubber grommets are already *in situ* as received. This means that the constructor is not only saved a great deal of time and trouble but the valveholder orienta-

tion of the prototype is exactly adhered to on every production model. The receiver controls protrude through the *underside* of the chassis, and this method of layout greatly assists short and direct wiring, with consequent stability of performance. A study of the illustrations showing the above- and below-chassis layouts will clarify the method of component assembly upon the sub-chassis.

The "Tourist" is a two-waveband receiver, uses the well-known 96 series of low consumption valves and incorporates a ferrite rod aerial. The speaker is a 5-inch circular extra high flux permanent magnet type, the excellent audio response being assured by the type of output transformer incorporated in the design. This latter component has been specially wound to match the circuit requirements.

The receiver, as may be seen from the front cover illustration, is housed in an attractive cabinet in modern styling, covered with contemporary leather cloth and contrasting Tygan speaker fret material, calibrated scale and ivory gold-filled knobs which, together with a neat carrying handle, completes the very smart appearance.

Circuit


This is shown in Fig. 1. The frequency changer V_1 , a DK96 heptode, has the grid connected, via S_1 portion of the wavechange switch, to a ferrite rod aerial assembly containing both long and medium wave windings. Each winding, when in circuit,

is tuned by the variable condenser C_2 and the trimmer condenser C_3 , the fixed value of C_1 being brought into circuit only on the long wave position. The oscillator section of the frequency changer is tuned by the variable condenser C_{16} , this being one half of a two-gang component comprising C_{16} and C_2 . The oscillator trimmer condenser is C_{15} , the switch S_2 being the requisite wave-change switch, which in the long wave position brings into circuit C_5 across the tuned winding. C_6 is the padder condenser. The oscillator coil is the well-known Osamor Radio Products Ltd type QO8. The oscillator "anode" h.t. potential is applied via the resistor R_2 , the condenser C_7 being the bypass component. The i.f. is 470 kc/s and the i.f. transformers are supplied pre-aligned to this frequency. The i.f. stage V_2 is constructed around the DF96 vari-mu pentode, the resultant output from this stage being taken, via IFT₂ and R_3 into the volume control R_5 .

frequency changer stages respectively. The diode pentode shown is the DAF96 type. The output from the diode pentode is taken into the output stage via the coupling condenser C_{13} . Automatic bias for the grid of this stage is developed across R_{11} , and applied via the grid leak R_{10} . The resistor R_9 provides a certain amount of negative feedback. Audio output to the speaker is fed via the transformer connected into the anode circuit. The output stage is constructed around the DL96 output pentode.

Assembling the Receiver

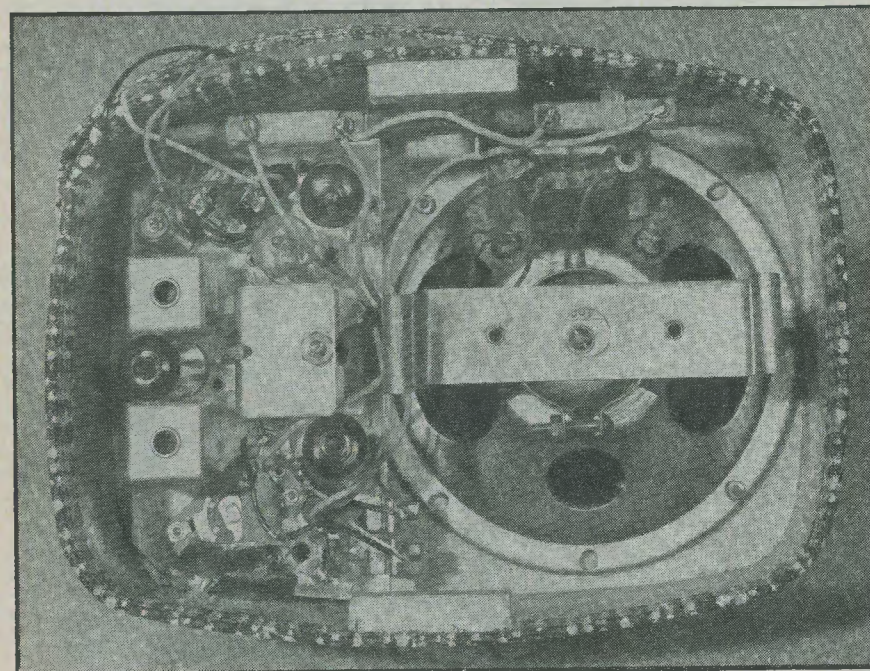First assemble on the ready-drilled chassis the volume control R_5 , and the two i.f. transformers IFT₁ and IFT₂. Radio beginners should note that the on/off switch S_3 and S_4 of Fig. 1 is also contained within the volume control. Secure each i.f. transformer to the chassis by means of two 6BA screws, but ensure from Fig. 2 that these are



Showing arrangement of units in cabinet

From that point, the signal is fed, via C_{10} , into the grid of the following stage. Rectification, of course, takes place at the diode, the load for which is R_3 in series with R_5 . An a.v.c. voltage is fed, via time constant components R_4 , C_9 and C_4 into the i.f. and

correctly located with respect to pin numbers. Looking at Fig. 2, you will note that this is the side of the chassis on which the valveholders have the soldering pins exposed. It is also on this same side of the chassis that the control spindles of the volume control

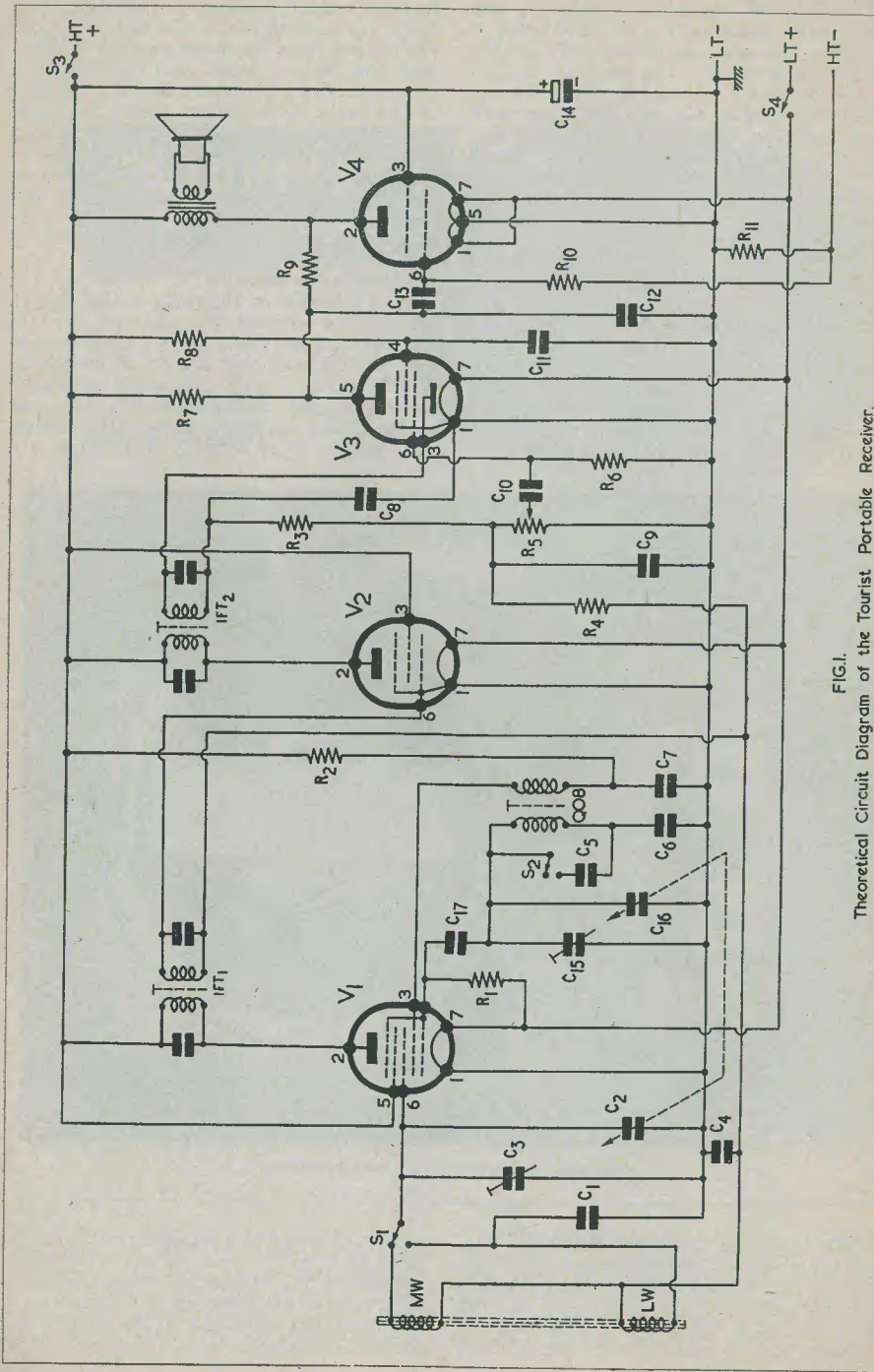


FIG. 1.
Theoretical Circuit Diagram of the Tourist Portable Receiver.

M67B

THE TOURIST COMPONENTS LIST

Condensers

- C₁ 130pF silver mica
- C₂ 365pF variable 2-gang
- C₃ 35pF trimmer
- C₄ 0.04 μ F
- C₅ 450pF silver mica
- C₆ 450pF silver mica
- C₇ 100pF silver mica
- C₈ 100pF silver mica
- C₉ 100pF silver mica
- C₁₀ 0.005 μ F
- C₁₁ 0.04 μ F
- C₁₂ 100pF silver mica
- C₁₃ 0.04 μ F
- C₁₄ 8 μ F electrolytic, 150V wkg.
- C₁₅ 35pF trimmer
- C₁₇ 100pF silver mica

Resistors

- R₁ 100k Ω $\frac{1}{2}$ watt
- R₂ 15k Ω $\frac{1}{2}$ watt
- R₃ 47k Ω $\frac{1}{2}$ watt
- R₄ 2M Ω $\frac{1}{2}$ watt
- R₅ 500k Ω potentiometer with switch
- R₆ 10M Ω $\frac{1}{2}$ watt
- R₇ 500k Ω $\frac{1}{2}$ watt
- R₈ 4.7M Ω $\frac{1}{2}$ watt
- R₉ 22M Ω $\frac{1}{2}$ watt
- R₁₀ 2M Ω $\frac{1}{2}$ watt
- R₁₁ 560 Ω $\frac{1}{2}$ watt

Valves

- V₁ DK96
- V₂ DF96
- V₃ DAF96
- V₄ DL96

Set out for easy reference to Fig. 1.

Miscellaneous

- Chassis with valveholders and grommets
- TRS Radio
- 5in P.M. speaker with O/P transformer
- TRS Radio
- Battery clip, ferrite clip, ferrite aerial—
- TRS Radio
- Wavechange switch, etc., TRS Radio
- I.F. transformers—TRS Radio
- QO8 oscillator coil—Osrom Radio Ltd.
- Battery plug, cabinet, dial and 3 knobs
- TRS Radio
- Nuts, screws, wire, etc.

Wiring the Circuit

The following instructions are intended for those who have had little or no experience of receiver construction but who are assumed to have mastered the art of soldering. It is also assumed that the intending constructor has a small electric soldering iron and a pair of pliers.

The more experienced constructor will, of course, work direct from the circuit diagram or possibly from Fig. 2 and 3.

Frequent glances at the accompanying illustrations will greatly assist the beginner with respect to the "real" position of components; both Figs. 2 and 3 being "approximate" drawings for purposes of clarity.

All the resistors used in the receiver, except, of course, for the volume control, are contained on a clearly marked card, each being designated both by the R number in the circuit diagram of Fig. 1, and its respective nominal ohmic value. The condensers are likewise clearly marked and are mounted on two separate cards. Beginners should remove each component as mentioned below and in that order. Do not remove the components from the card until they are mentioned,

and wavechange switch protrude. The outline shape of the chassis will greatly assist with respect to correct locations of components in both Figs. 2 and 3.

Next, secure in position the wavechange switch S₁ and S₂; again, this is a combined component. A glance at Fig. 3 will show the approximate locations of these components. Follow this by fixing the variable tuning condenser C₂ and C₁₆ into position (Fig. 3), using the three 4BA x $\frac{1}{4}$ inch screws. (Fig. 2.) Having completed this, the two trimmers C₃ and C₁₅ may be held in position (Fig. 3) by means of a 6BA screw and nut each. From Fig. 3 ascertain the position of the oscillator coil QO8 and firmly press this into the aperture provided, ensuring that the straight side of the tag ring is towards the two trimmers previously mounted.

Laying the chassis to one side for the moment, fit the battery retaining clip to the speaker magnet and tighten the 4BA screw and nut already fitted. Ensure that the clip is horizontal when the output transformer (already fitted to the speaker) is positioned at the top. Next, secure the ferrite rod aerial clip to the output transformer by means of a 6BA screw and nut through the left-hand aperture (looking at the rear of the speaker) on the top of the transformer. Fix the speaker, complete with the clip now mounted, into the cabinet by the two long screws already in position and secure with two 6BA nuts provided. Ensure that the output transformer is sited at the top of the receiver cabinet. This completes the assembly details.


otherwise identification will be impossible unless the colour code is known.

We commence by first soldering in the wires necessary to carry the h.t. and l.t. currents. Take two lengths of p.v.c. covered wire, about 4½ inches in length, and bare the four ends. Solder the end of one to the top left-hand tag at the rear of the volume control (see Fig. 3). Connect the other end of this wire to the appropriate pin of the four-pin plug, also shown in Fig. 3. To correctly solder this latter connection, pass the bare wire through the pin until it extends from the end furthest from the paxolin shoulder. Solder at this latter point and remove any surplus wire with the aid of a pair of cutters. Dealing with the second wire, solder one end to the top right-hand tag of the volume control and the other end to the

Connect into circuit the wires marked C and D shown in Figs. 2 and 3. Bare and connect the end of each to the 4-pin plug, as shown, and then pass these through the rubber grommet and solder the end of C to pin 4 of V₄; the end of D to pin 5 of the same valve.

To the lower left-hand tag at the rear of the volume control, solder one end of a short length of p.v.c. wire (A), the other end of which should now be connected to pin 1 of V₄. To the lower right-hand tag of the volume control connect a similar length of wire (B) and solder the other end to pin 3 of V₄. This completes the h.t. and l.t. inputs to the receiver. We must now connect into circuit other h.t. and l.t. points within the receiver.

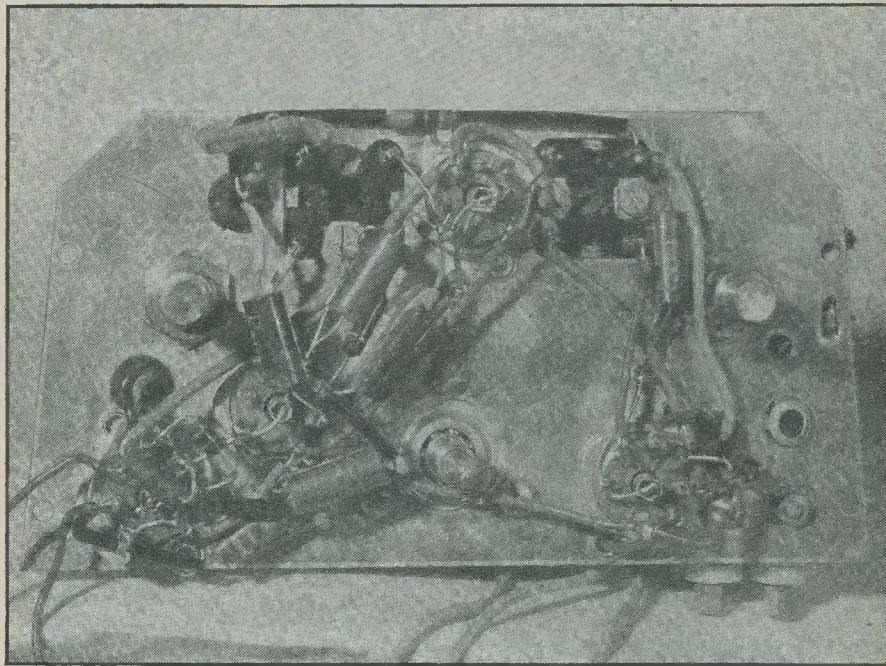Take a short length of p.v.c. wire and bare



Underside of chassis. Compare with Fig. 2 opposite

top left-hand pin of the four-pin plug. Note here that the view of the plug shown in Fig. 3 is that shown looking at the rear of the component with the pins pointing away from the reader. The position of the pins can be ascertained by the fact that the two top pins are set further apart than the remainder.

one end sufficiently so that pins 1 and 7 of V₄ may be connected together. Solder these connections and join the other end of this wire to pin 7 of V₃. From this latter pin connect a further length of p.v.c. wire to pin 7 of V₂. Returning to pin 7 of V₃, connect a further length of p.v.c. wire to this

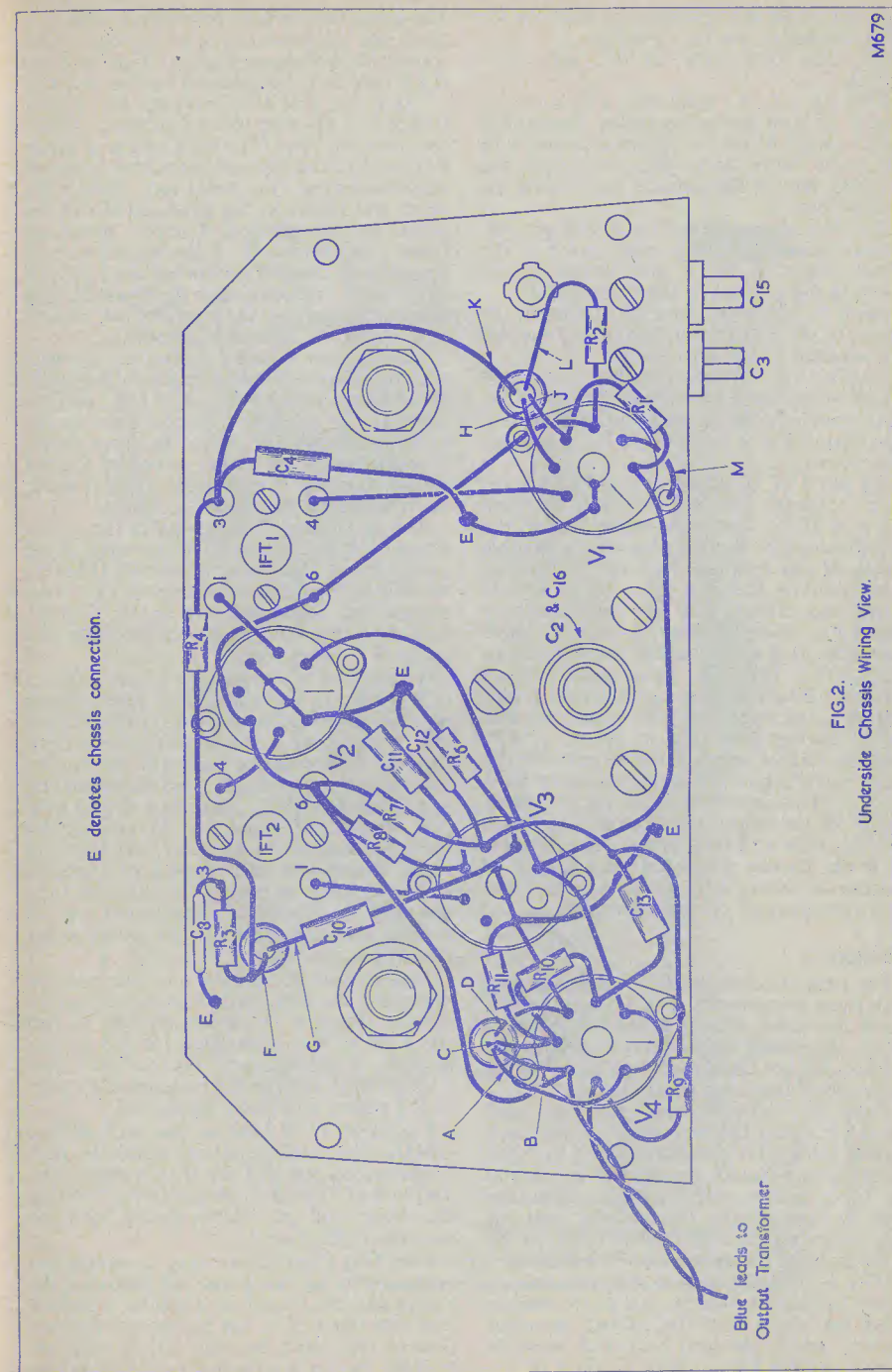


FIG. 2. Underside Chassis Wiring View.

M679

pin and solder the other end to pin 7 of V_1 . This completes the l.t.+ wiring.

We next deal with the h.t. and l.t.- wiring.

Dealing with V_1 first, with a bared short length of wire connect together the central metal spigot of the valveholder to pin 1 of the same valve and from thence to the earthing tag on the chassis just above the valveholder.

For V_2 , again with a bare length of wire, connect together, in this order, pin 5 to the metal spigot to pin 1 and thence to the earthing tag just below the valveholder.

With V_3 , using the bare wire, connect the spigot to pin 1 and from there to the earthed tag adjacent to the valveholder.

Lastly, V_4 , connect together the metal spigot to pin 5 and from there to pin 1 of V_3 . This completes the minus (-) return wiring. The next step is to bring in the h.t.+ connection points.

To pin 3 of V_4 solder one end of a short length of bare wire just sufficient to reach pin 6 of IFT_2 . Having soldered this to the valveholder pin, slip over the wire a suitable length of red systoflex material. Solder the other end to the i.f.t. connection already mentioned. To pin 6 of IFT_2 , and similarly covered as above, solder one end of a short wire, the other end of which is connected to pin 3 of V_2 . From this latter point, connect a further length of wire, again covered with systoflex, and solder the other end to pin 6 of IFT_1 . Having done this, to pin 6 of IFT_1 solder a further length, suitably covered, the other end of which is now connected to pin 5 of V_1 . This completes the h.t.+ wiring except for the output transformer, which will be dealt with at a later stage. The next job of work, having proceeded thus far, is to commence wiring into circuit all the components contained on the three cards.

Resistors

For ease of construction, it is best to deal with these components first, leaving the two condenser cards strictly alone for the time being. Beginners are advised to follow this method and not cause confusion by removing components from two cards at once.

Take R_1 (100k Ω) from the card and suitably shorten the wire ends so that each may be soldered to the valve pins of V_1 . (See illustrations.) Solder one end to pin 4 and the other end to pin 7 of V_1 . Note the position occupied by this resistor, and for that matter all the other components, in the photograph of the underside of the chassis.

With R_2 (15k Ω), cut one wire end only in such a manner that the far end of the resistor is resting up against the rubber grommet through which the long wire end must be passed. Solder the cut wire to pin 5 of V_1 .

The other wire end of this resistor will now reach the appropriate tag of the coil which should be bent down slightly. This wire end (L) should now be soldered to this coil tag.

From pin 3 of IFT_2 , connect R_3 (47k Ω), this end of the wire being shortened. Cover the other wire end (F) with a length of systoflex and feed this through the rubber grommet adjacent to the i.f.t. metal can. Solder the other end of R_3 to the left-hand tag of the actual volume control. (NOTE: There are three tags connected to the actual volume control and these are mounted on a paxolin strip; these are quite separate from the four tags contained on the rear of the control with which we have already dealt.)

Dealing now with R_4 , do not cut the wire ends but place over them lengths of systoflex, and solder one end to pin 3 of IFT_1 and the other end to the bare wire contained on the rubber grommet end of R_3 . In other words, connect one end of R_4 to one end of R_3 , but ensure that the correct end of R_3 is used, i.e. that nearest the rubber grommet.

The remainder of the wiring to the potentiometer R_5 will be left till a later stage in the proceedings. Dealing now with R_6 (10M Ω), suitably shorten the wire ends of this component and solder one end to pin 6 of V_3 and the other end to the earthed tag just below V_2 valveholder.

To pin 5 of V_3 valveholder solder one end of R_7 (500k Ω), the other end of which should now be connected to pin 6 of IFT_2 . Follow this by removing R_8 (4.7M Ω) from the card, suitably shortening the wire ends and soldering one end to pin 4 of V_3 and the remaining end to pin 6 of IFT_2 . Beginners should note here that R_6 , R_7 and R_8 do not require systoflex material to be fitted over the wire ends. These wire ends should be made as short and direct as possible, at the same time ensuring that none of these wires are in contact with any other metallic points other than those specified.

The resistor R_9 (22M Ω) should now be taken and the wire ends shortened in such a manner that they will reach pin 5 of V_3 and pin 2 of V_4 (see illustration for the correct location of this resistor). Fit over each wire a short length of systoflex material and solder to the points previously mentioned.

To pin 6 of V_4 solder one end of R_{10} (2M Ω), the other end of which is next connected to pin 4 of the same valveholder. To pin 4 of V_4 solder one end of R_{11} (560 Ω), the other end of which should now be secured to pin 5 of V_4 .

This latter instruction may be somewhat confusing to beginners who are following the circuit diagram, therefore it will be explained here that pin 4 of V_4 has no internal connection to the valve, but the pin is used externally as an anchoring and connection

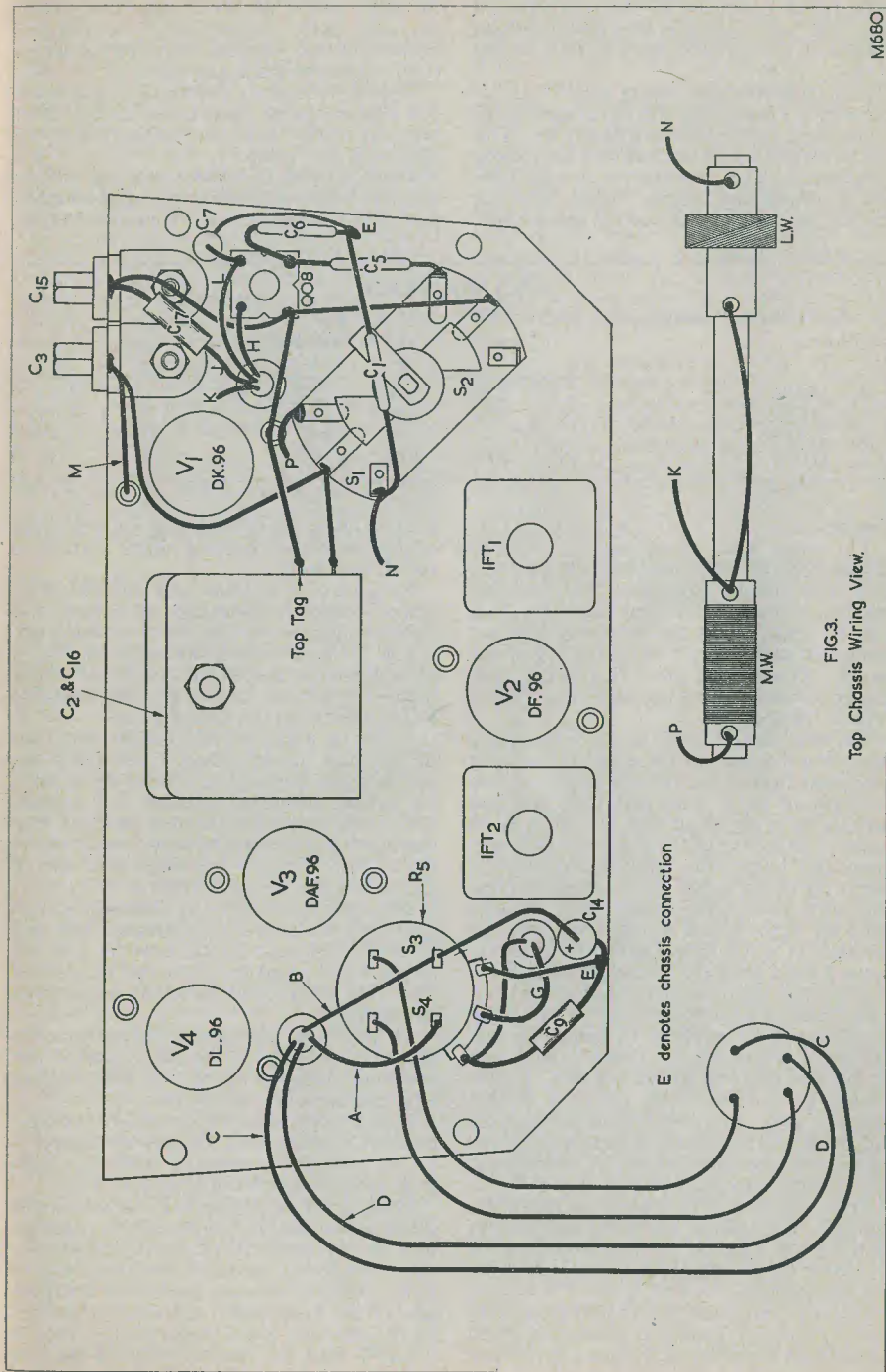


FIG. 3.
Top Chassis Wiring View.

M660

point for components; in this case R₁₀ and R₁₁. Pin 5 of V₄ has, in this instance, been utilised as the earth connection for one end of R₁₁.

This completes the wiring into circuit of the resistors except for the remainder of the connections to the volume control R₅. This will be carried out as we deal with the various condensers. The constructor should now, before proceeding further, check that all resistors are correctly connected and located.

the other end to the lower right-hand tag of the coil QO8. Again, note the physical position of this—and the following condenser (C₆),—from the photographs.

Similarly prepare C₆ (450pF) and connect one wire end to the same tag of the coil QO8 and the other end to that earthing tag alongside the switch.

The condenser C₇ (0.04μF) should now be soldered between the earthing tag connection just mentioned and the top right-hand tag of

VOLTAGE TABLE

All voltages measured with an AVO "8"—chassis negative.

Valve	Pin Numbers						
	1	2	3	4	5	6	7
V ₁ DK96	—	62V	33V	1.2V	62V	—	1.4V
V ₂ DF96	—	62V	62V	—	—	—	1.4V
V ₃ DAF96	—	—	18V	30V	—	—	1.4V
V ₄ DL96	1.4V	57V	62V	-5V	—	—	1.4V

Condensers

The silver mica condenser C₁ (130pF) should now be removed from the card, its wire ends suitably shortened and one end soldered to the top left-hand tag of S₁. (See Fig. 3.) Ensure that this wire end does not come into contact with any other tag of the switch. Connect the other end of this condenser to the earthing tag near the adjacent edge of the chassis.

We now deal with the connections to C₂, this being that part of the variable two-gang condenser nearest the metal chassis. Obtain a length of p.v.c. wire and bare one end sufficiently in length so that the end may be soldered to the tag of C₂, and some little way along this bared wire, also soldered to the centre tag of the switch S₂. In order that this wire does NOT make contact with the left-hand tag of the switch to which we have just connected C₁, this latter tag should be gently pressed away from the bare wire towards the chassis ensuring, of course, that it does not make contact with the chassis. Only slight pressure will be required to bend this tag. The other end of the p.v.c. wire should now be cut and soldered to the tag of C₃ (35pF trimmer). To this latter point, a further length of p.v.c. wire (M) should be soldered, the other end of which is fed through the aperture in the chassis near V₁ valveholder and connected to pin 6 of V₁.

From pin 3 of IFT₁ solder one end of C₄ (0.04μF) and connect the other end to that earthing tag adjacent to the valveholder of V₁. Note the position of this condenser from the illustrations.

Dealing next with C₅ (450pF), suitably shorten the wire ends and connect one end to the right-hand tag of S₂ (see Fig. 3), and

the coil QO8. Note from Fig. 3 the position of this condenser, it being placed vertical to the chassis deck.

To pin 3 of IFT₂ solder one wire end of C₈ (100pF), suitably shortened, of course, and the remaining end to the nearby earthing tag.

Fig. 3 shows the position of C₉ (100pF), and this should be soldered from the left-hand tag of the volume control R₅ with the other end connected to the earthing tag.

Take C₁₀ (0.005μF) and cut one wire end (G) to such a length that it will reach the centre tag of the volume control R₅ through the rubber grommet alongside this control. Cover this wire with systoflex material, feed through the grommet and solder to the centre tag of R₅. Connect the other wire end of C₁₀ to pin 6 of V₃ valveholder.

The next condenser C₁₁ (0.04μF) should now have the wire ends shortened; one end of this component should now be soldered to pin 4 of V₃ and the other end to pin 1 of V₂. This latter point serves as an earthing connection.

To pin 5 of V₃ valveholder connect one end of C₁₂ (100pF), the other end of this condenser connecting to the earthing tag adjacent to the V₂ valveholder.

Solder to pin 6 of V₄ one end of the condenser C₁₃ and the other wire end to pin 5 of V₃, having first covered both wire ends with suitable lengths of systoflex.

Dealing next with C₁₄ (8μF), note from the illustrations that this component is mounted in such a manner that it finally occupies a vertical position alongside the metal can of IFT₂. Suitably shorten the wire at the black end of the component and solder this wire to the earthing tag adjacent to the volume control. The red wire end should now be

connected to the lower right-hand tag on the rear of the volume control.

The remaining half of the two-gang variable condenser, C₁₆ (365pF), must now be wired into circuit. Solder a length of p.v.c. wire to the tag of this condenser and connect the other end to the bottom left-hand tag of the coil QO8. To this latter point also solder two other lengths of p.v.c. wire. The other end of one of these lengths must now be secured to the tag of the trimmer C₁₅. The remaining end should next be soldered to the centre tag of the wavechange switch S₂.

The last condenser should now be removed from the card and soldered into circuit. C₁₇ (100pF) should first have one wire end only shortened, and this should be soldered to the tag of the trimmer condenser C₁₅ (35pF). The remaining wire end (J) should now be covered with systoflex, fed through the adjacent rubber grommet, and be soldered to pin 3 of V₁.

This completes the wiring-in of the condensers, but the receiver is still not complete with all its wiring, and it is these final details that we must deal with next.

Final Details

Returning to the volume control R₅, and using a bare length of wire, connect one end to the lower right-hand tag of the actual control itself, i.e. *not* to any of the four tags contained on the rear of the potentiometer. Solder the other end of this wire to the adjacent earthing tag.

Using a suitable length of p.v.c. wire, bare both ends and connect one to the top left-hand tag of the coil QO8. Feed the other end of this wire (H) through the rubber grommet and solder the end to pin 3 of V₁.

The output transformer leads should now be shortened somewhat and bared at each end. One wire, it does not matter which, should now be soldered to pin 2 of V₄, and the other wire to pin 3 of the same valveholder.

We next deal with the ferrite rod aerial connections. Firstly, with a short length of p.v.c. wire (K), connect the two windings to each other by soldering each end of the wire to the two innermost studs. (See Fig. 3).

Mount the ferrite rod aerial to the metal fixture in such a manner that the fitted large rubber grommet positions securely into the metal bracket.

Obtain a suitable length of p.v.c. wire, bare both ends and solder one to the right-hand stud of the aerial assembly (N of Fig. 3). The other end of this wire should now be connected to the left-hand tag of the wavechange switch S₁.

The Medium wave winding connection (P) should now be completed by using p.v.c. wire and connecting one end to the stud

provided on the winding and the other end to the right-hand tag of the switch S₁. Ensure that both windings are positioned at the ends of the ferrite rod material.

The actual wiring of the receiver is now complete. Beginners should now check that all is correct, both with regard to the foregoing instructions and with regard to Figs. 2 and 3.

Fit the battery plug to the B114 battery (69V+1.5V) and switch on the receiver by rotating the volume control spindle in a clockwise direction. For those in possession of a meter, check the voltages between pins 1 and 7 of each valveholder. This should be 1.5V. (See voltage table for other information.)

Insert the respective valves into the appropriate holders. (See Fig. 3.) Fit the spindle extension to the spindle of the wavechange switch. Mount the chassis into the cabinet and secure into position by means of the four wood-screws provided. These should be driven into the wood blocks fixed to the receiver casing. Finally, fit the knobs to their respective spindles.

STATION GUIDE FOR CALIBRATION PURPOSES

Station	kc/s	Metres
Moscow	173	1734
BBC Light	200	1500
Luxembourg	233	1286
BBC Third	647	464
BBC Scottish	809	371
BBC London	908	330
BBC Midland	1108	276
BBC Light	1214	247
Luxembourg	1439	208

Aligning the Receiver

The i.f. transformers are already pre-aligned to 470 kc/s. Ensure that the wavechange switch is turned anti-clockwise (Medium Wave), and turn the volume control to the maximum position (clockwise).

Adjust the core of the oscillator coil (QO8) from the inside of the receiver cabinet until the core is level with the tag ring. Tune for the Home Service by rotating the tuning control. Move the medium wave coil on the ferrite rod until a position of maximum volume is obtained.

Rotate the tuning control anti-clockwise for another signal, around 200-220 metres, preferably a weak station, and adjust the trimmer C₃ for maximum volume. Retune clockwise to about 450 metres for Brussels, etc., or a similar station, and re-adjust the core of the oscillator coil QO8, rocking the tuning condenser slightly whilst obtaining peak output. Readjust the medium wave winding on the ferrite rod for maximum volume.

continued on page 129

radio

miscellany

SINCE THIS COLUMN FIRST TOOK AN interest in the garden-shed workshop I have been greatly surprised at the very high proportion of hobbyists who, either by force of circumstances or choice, have a self-built workshop. They vary from lean-to's, erected against a blank wall, and annexes tacked on behind the garage, to full-blown independent structures standing proudly in their own grounds. A few years ago garden shedders were few and far between, although many handymen had some sort of out-building used for storage, keeping the firewood dry, and rough or dirty work. Today's garden-shedders are in an altogether different category, and sturdy modern buildings with space heating, strip lighting and curtained windows are apparently becoming commonplace.

With t.v., f.m., etc., our hobby has become more and more complicated. The days have long since gone when one could get by with a soldering iron and a universal meter with the kitchen table as a workbench. Nowadays the keen types think nothing of carrying a comprehensive range of special tools and test equipment which would fill two sides of a medium-sized room. Pre-war, too, one could practically build a set in a single evening, but a modern f.m. or t.v. receiver may well be several weeks in the making. Hence it is nice to have a place where everything can be left undisturbed with tools and test gear right to hand. Even those who in the past have been content with a spare corner in the house are beginning to turn to specially designed garden buildings. While a brick and concrete workshop is a mighty expensive proposition if a builder has to be called in, it is neither too costly nor beyond the capability of a versatile radio enthusiast (and most of us are that) especially if one can get the advice and assistance of someone in the building line. In fact, I have more than once been greatly surprised how economically it has been done.

A Cosy Retreat




Our Editor has recently become the possessor of a handsome self-built workshop which was designed and erected by himself and brother-in-law—the latter experienced in the building trade. The centre photograph on the next page shows the start of the 9in front and side walls (rear wall 4½in). The damp course can be seen, and the missing brick on the side wall is to provide space for a switched power socket. Three more are fitted to the front wall. The concrete foundation, laid on hard core, is approximately 10in thick and the interior floor dimensions 14ft x 7ft.

The lower picture shows the building nearing completion, while the top one is of one corner viewed from the doorway. The interior is finished with hardboard fitted to the underside of the roof beams and held to the walls by 1in battening, giving it the effect of "cavity walls." The lathe, incidentally, is 3½in centre height and the bench drill is ½in capacity. Unfortunately the rest of the interior cannot be seen, but it includes a workbench, anglepoise lighting, 4in vice, steel shelving, etc., and also a 2ft rule (which is to wipe your feet when you go in!).

As might be expected from such a "professional type" job, no trouble has arisen from dampness, the only precaution necessary being the light greasing of stored tools, etc. The electric power is drawn from the house using Pyroténax cable travelling underground.

Your Say

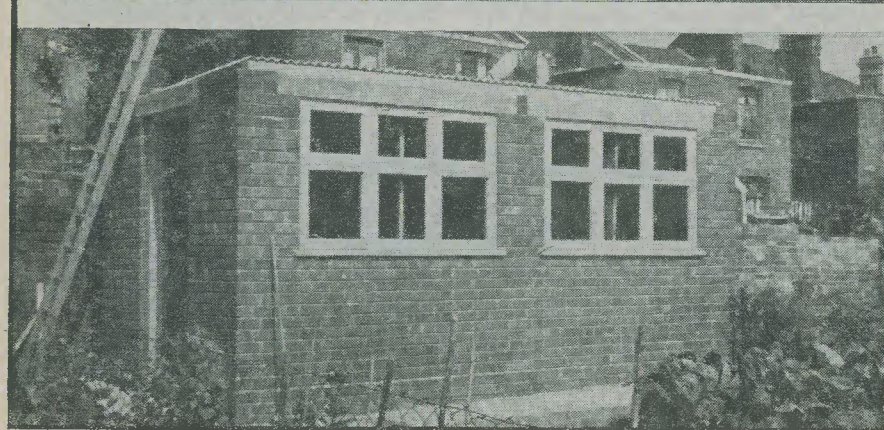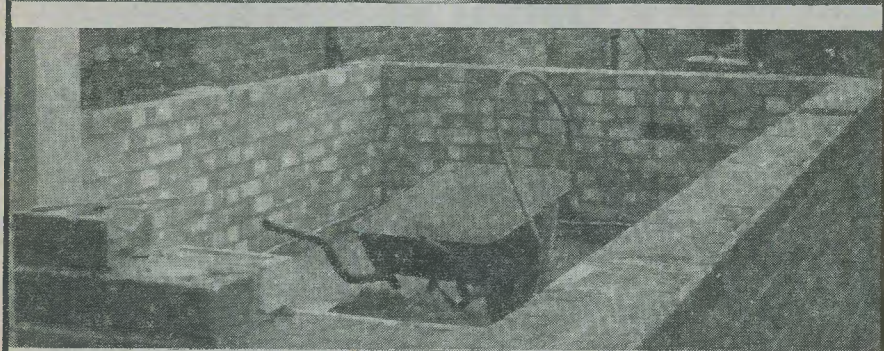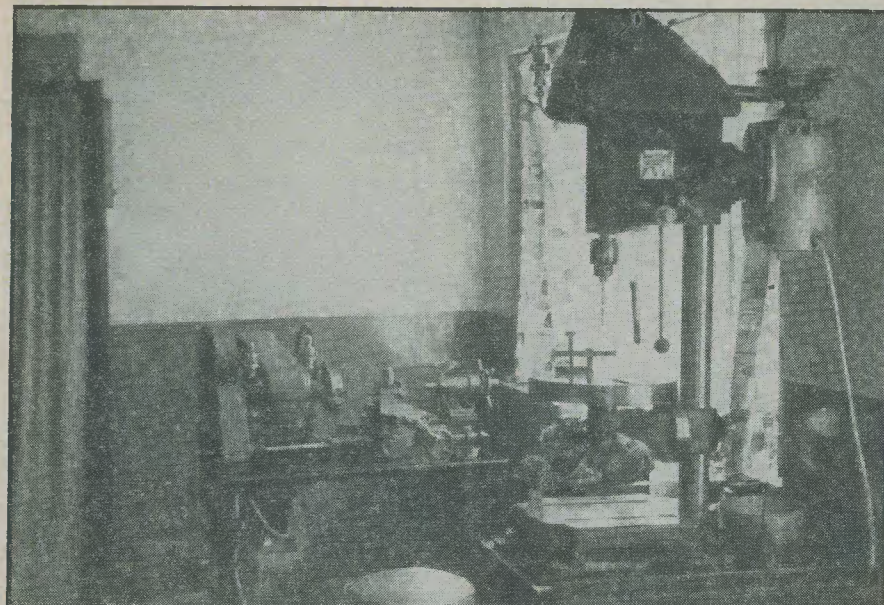While on the subject of outdoor workshops, an interesting letter comes from P.H.P. (South Norwood) who expresses surprise that when the question of ventilation was under discussion no one mentioned the Humex Ventmaster. This device, primarily designed for greenhouses, consists of a chemically filled cylinder which is fitted to the window frame. As the temperature



varies the fluid contracts or expands, automatically closing or opening the vent, thus needing neither power nor attention. From reports I have had from users, I gather that they are eminently satisfactory and will operate quite heavy ventilators or window frames with certainty. P.H.P. also mentions another device by the same firm, a fan ventilator controlled by a thermostat of which home-made versions might well be contrived by the average reader.

Another interesting letter from A.M.P. (Culcheth) on the subject of "disappearing" valve type numbers. He feels the manufacturers have given the question of more permanent markings much thought but have retained the practice of hand stencilling on safety grounds. Hydrofluoric acid etching is dangerous and likely to remove the operator's hands. Perhaps some reader can suggest a less risky etchant with which readers can treat their own valves. This should not be difficult as the time factor is not important, as it would be in a factory process. On the same subject a Mitcham reader (anonymous) cynically writes that manufacturers deliberately delay the marking until the last thing so they can leave their names off if the tubes fail to come up to standard on their final test!

childlike, collected them up with his magnet. From then on, of course, every time she picked up her scissors she found scores of pins clinging and dangling all over them! Which only goes to prove we needn't have worried about the permanence of those magnets after all.

Money for Old Rope

Although no one has written specifically on the subject, most correspondents in recent weeks have mentioned their complete agreement with my comments on many of the I.T.V. programmes which spell utter boredom to the intelligent viewer. Whenever I seem to have a little time to spare for casual viewing the screen is filled with interminably dreary Westerns, American quickies and stale films. It is amazing that we should spend dollars on such stuff, and to make it worse I.T.V. are asking the Government for another 21 hours a week—an example followed less eagerly by the B.B.C. Both authorities, especially I.T.V. would be better concerned with putting out improved programmes in their existing hours. It would be nice to have a few "sensible" programmes. I shudder to think what is going to happen during those extra hours and can only imagine that it will be more programmes

Centre Tap talks about items of general interest

Finally, more old-time memories, this time from W.G. (Bradford 3), were revived by my reference to early loudspeakers. His father-in-law, who was bedfast, was adept at making pleated paper cones which he scored lightly with a darning needle, gluing cork to the centre (instead of the sealing wax I mentioned). Also, instead of using stiff wire between the reed and cork, he used a matchstick. He considers (as did many others) that these were the best thing of their time. Later he bought one of the earliest moving coil speakers from Mr. Briggs, whose newly-started business was then in a city centre Bradford basement. This enterprise has now grown into the world-famous Wharfedale business. Incidentally, that speaker gave sterling service right up to the end of the war and after.

Old Timers will recall how we were apt to regard the early permanent magnet m.c. speakers with some suspicion, and wondered just how "permanent" the magnets would prove to be. Well, just recently I gave the magnet of a very old one to a youngster as a plaything. Later, when he knocked over a boxful of his mother's dressmaking pins he,

suitable for backward adolescents just merely to fill out time in order to justify still more advertising.

Many readers feel it would be better, too, if I.T.V. put the money spent on bubble cars, stole wraps, washing machines, bedroom suites, etc., into the programmes. Is it to attract the lower types of mentality that such prizes are lavishly distributed for answering questions which should present no difficulty to school-children?

With the B.B.C. sometimes even outdoing I.T.V. in finding some of the worst of the American bookings, many people, besides myself, are humbly grateful that "steam" radio nowadays still carries a satisfying proportion of worthwhile programmes during peak listening hours. And the pleasure is doubled when one listens to them on F.M.!

Incidentally, three of the I.T.V. programme contractors are increasing their advertising rates by 10% in the autumn, and a fourth on 1st January, but they will charge 20% more during peak hours (7.30 to 10.30 p.m.). The increases are made on the grounds that the audiences are now much larger. With this swelling of revenue no

doubt we shall see really big quiz prizes (if you can only answer such questions as "Where does Jamaican rum come from?") instead of such trifles as refrigerators and t.v. sets!

Lucky For Us

It is curious when you come to think of it that the additional t.v. hours now asked for exceed the total t.v. hours of a number of European countries. In Austria, for instance, they have three hours each evening except Tuesday, when there is no programme at all. A far higher proportion of their programmes are (if only for this reason) worth while sitting down to watch—instead of merely forming a background of time-filling trivialities which are allowed to drone on while various members of the family carry on doing something else and spare only an occasional glance at the screen.

It is nice, however, to think that we don't have to pay at the same rate for our t.v. Their licences, which are renewable every

month, cost fifty Austrian shillings (Exchange rate approx. 72 to the £1). Nor must it be overlooked that wages and salaries are considerably lower than they are here. Small wonder no one is expected to pay a year in advance at that rate, but even if one has got the cash a month is the longest period you can take.

Talking about money reminds me—suppose the B.B.C. get the extra hours, where is the additional expenditure coming from? Surely the next move will be to put our licences up to a fiver!

I note also that the House of Commons Public Accounts Committee have turned their attention to I.T.A.'s huge profits and consider that future rentals should represent the contractor's full capacity to pay. At this, the Chairman of Associated-Rediffusion is reported as suggesting that if the commercial t.v. companies have to pay more rent, viewers will get inferior programmes. Which makes me wonder where they are going to find 'em.

The TOURIST Portable Receiver

continued from page 125

Re-tune to Luxembourg (208 metres) and adjust C₁₅ trimmer for the correct calibration of the scale.

The above should be repeated to ensure maximum output with accurate calibration.

Turn the wavechange switch clockwise to the long wave position. Tune to the Light Programme (1500 metres) and adjust the long

wave ferrite aerial winding along the rod to obtain maximum output.

Having completed the lining-up process, it is advisable to seal the windings to the ferrite rod with a fixative material such as polystyrene cement, etc. The trimmers C₃ and C₁₅ should also be treated in a like manner.

PHILIPS

Continuous Tape Cassette

Philips Electrical Ltd. are now marketing a Continuous Tape Cassette, type EL3963/00, which is intended for use primarily with their AG8108G Tape Recorder and with certain other models which have a left to right tape sense and facilities for locking the tape turntable in a stationary position during recording/playback.

Of clear plastic, the cassette has a diameter of 3½ in. and contains low friction magnetic

tape coated on both sides. Playing time is 20 mins. at 1½ i.p.s., 10 mins. at 3¼ i.p.s. and 5 mins. at 7½ i.p.s. These times may be doubled by the formation of a "mobius loop" as described in the operating instructions.

The EL3963/00, which sells at £5.0s.0d., is suitable for application in all situations requiring a continuous operation of directions, messages or signals.

TESTMETERS and their circuits

By W. Cleland

In this article, methods are analysed which enable a meter scale to serve for a number of ranges

THE SUBSTITUTION OF AN EQUIVALENT generator for a network is quite revealing when applied to testmeter problems. For example, in a circuit under test there is a certain maximum amount of power "available" between any two given points, and a meter when connected must absorb only a small fraction of this. For radio work, we require a sensitive meter, and for some purposes may even have to increase its sensitivity by using valves or transistors.

disturb the circuit as little as possible. A voltmeter with a resistance n times that of the circuit across which it is placed will read low by $1/n$ th part. The same is true of an ammeter or milliammeter inserted at some point where the meter resistance is $1/n$ th of the network resistance. If, however, we can estimate the equivalent resistance of the circuit in terms of the d.c. resistances of its linear components and the slope resistances of its non-linear components (such as valves), we can apply a correction; but a high resistance voltmeter is much more convenient.

Current measurements are less common, and a drop of a fraction of a volt across the meter is usually of little importance. In a.c. measurement, however, the potential drop is often rather large.

Resistance Measurement

The facilities offered by a testmeter for resistance measurement are among its most useful, and it is always a simple matter to check the calibration by using a number of accurate resistors. Circuit details are given in Fig. 2. On each range the circuit reduces to an equivalent generator with a short-circuit current which corresponds to meter f.s.d. We need only multiply the generator e.m.f. and resistance by ten to multiply the scale readings by the same factor. A potential divider can be used to change the generator e.m.f. by the tenfold steps, and the circuit resistance need only be adjusted on each range to give short-circuit f.s.d.

It may only be possible to secure the further reduction in circuit resistance to give the lowest range by placing a shunt across the meter, and this will probably require a heavier current to be supplied by the battery than would suffice for the higher ranges. Another method often used for low resistance readings is to connect the unknown resistances as shunts across the meter, but the scale then becomes backward-reading, which is rather confusing. A better method is shown in Fig. 3, which will allow the equiva-

lent generator resistance to be reduced ten times without altering the e.m.f. It requires an auxiliary network of three resistances on the bottom range; the circuit taking the form of a bridge which is unbalanced by the unknown resistance.

A single forward-reading scale can thus serve all ranges. It is non-linear since it obeys the formula:

$$\frac{I_x}{I} = \frac{R_0}{R_0 + R_x}$$

where R_x is the resistance being measured, and I_x the corresponding meter current, R_0 the internal resistance which the ohmmeter

of the meter, i.e. its current for $R_x=0$.

Changes of current in the ohmmeter, however complicated the circuit, are always inversely proportional to $R_0 + R_x$. This is not difficult to prove and leads directly to the above formula.

In simpler types of ohmmeter, the means of readjusting to short-circuit f.s.d. as the battery deteriorates, over a long period, produces errors in measurement. The internal resistance of the battery may eventually reach hundreds of times its original value of a few ohms, while the e.m.f. may have dropped by 10%, so the method of readjustment ought to be effective against

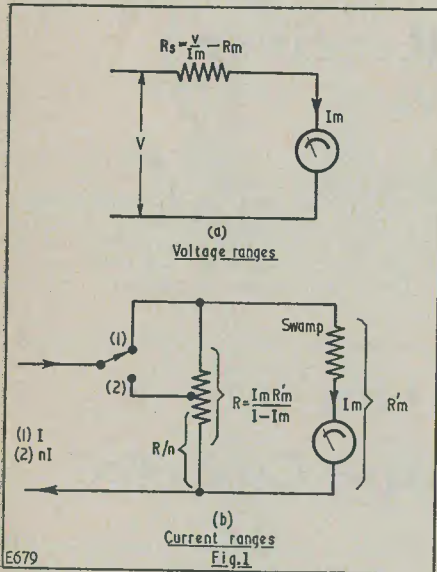


Fig. 1. D.C. multipliers. The values to be inserted in the formulae are those for full-scale deflection

Strictly speaking, the meter reading applies when the meter resistance is present. If it is to apply in the absence of the meter, the temporary addition of the meter must

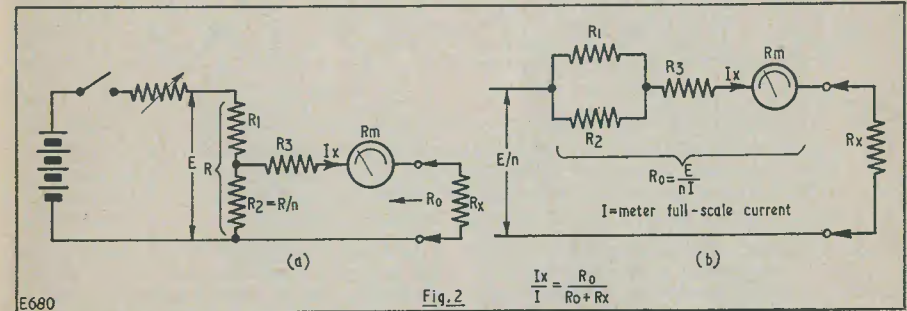


Fig. 2. Resistance ranges (a) with equivalent circuit (b). R_3 may be absent, but if temperature errors are to be avoided on the lowest range it is desirable to have enough series resistance to act as a swamp. For the lowest range a shunt may have to be placed across the meter to obtain the required reduction in the value of R_0

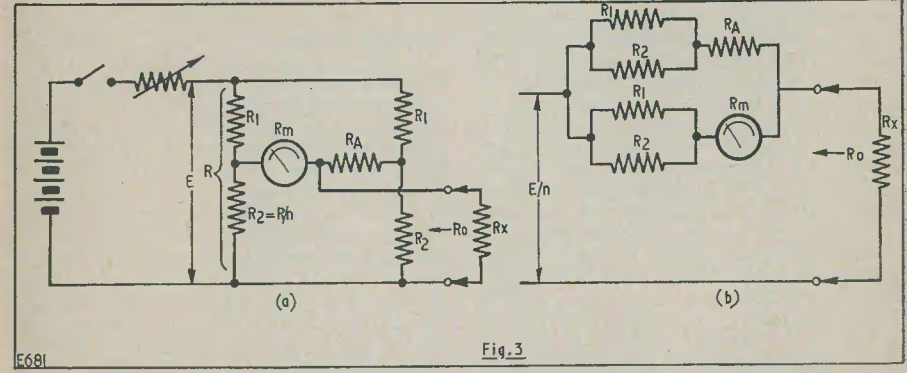


Fig. 3. Modified circuit of low resistance range. The value of R_2 might be $1/9$ th of the meter resistance, assuming a microammeter with a resistance of several hundred ohms. The value of R_A is only a fraction of R_2 , and it is included to enable the ohmmeter equivalent resistance R_0 to be adjusted to the exact value required

presents between its terminals on that particular range, and I the full-scale current

both these changes. The variable resistance in series with the battery of Fig. 2 can be used

to keep the voltage E constant, while on the top range it will be necessary to be able to adjust part of the resistance R_3 on that range to keep the generator resistance at its correct value.

Alternating Currents

When we turn to a.c. measurement we have to introduce a bridge-type meter rectifier,

under precisely the same conditions on all the voltage ranges. The universal shunt ensures this for the current ranges.

If a universal shunt of total value $1k\Omega$ is used for the current ranges, then replacing it by a series resistance of $1k\Omega$ will convert readings of milliamps into volts. This is the well-known transformation of a current source into an equivalent voltage source, and

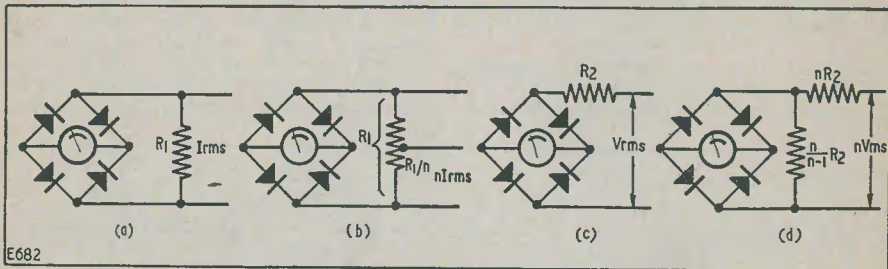


Fig. 4. A.C. multipliers with the corresponding input currents and voltages for f.s.d. Diagrams (a) and (b) represent current ranges using a common scale, (c) and (d) are voltage ranges. Note that if we make $R_1=R_2$, then $V_{r.m.s.} = R_1 I_{r.m.s.}$

whose resistance varies at different points of the scale. Nevertheless a nearly-linear scale can be obtained except at low readings, provided that no low-value series resistance or shunt is used. If, however, a comprehensive series of ranges is to be provided, this condition cannot be met, and the scale will depart considerably from linearity, with scale divisions crowded at low readings; and temperature errors will become appreciable, because the rectifier will constitute a large part of the resistance in series with the meter.

An instrument transformer is normally used for the current ranges, but a universal shunt can be used instead, although this will have rather a large power consumption on the higher ranges of current. The method is applicable because the current-multiplying factors of a universal shunt do not depend upon the meter resistance, so that any given value of rectified current through the meter will correspond on the different ranges to alternating current inputs to the testmeter bearing the fixed ratios to each other set by the universal shunt.

For alternating voltages, a number of ranges can be fitted to a common scale by using combinations of series and shunt resistances, each pair giving the same value when connected in parallel. On the lowest range a single resistance having this value can be used in series, without any shunt resistance. These arrangements constitute a type of attenuator which enables the attenuation to be changed by factors which are independent of the meter resistance as a load, and ensure that the rectifier works

would make it possible to use a single scale for alternating current and voltage ranges. However, better characteristics can be obtained if there are separate scales.

The calibration of an a.c. scale with sinusoidal current, in r.m.s. values, will only hold accurately for a sinusoidal waveform, because although the use of a shunt will cause a departure from linearity, it will not be easy to ensure that the rectifier meter closely follows a square law of deflection.

Practical Details

It will be seen that a system of networks can be made which, connected to any suitable type of meter, would convert it into a multi-range testmeter. A multiplicity of scales, of course, requires a pointer of the knife-edge type, but there is the alternative of using conversion tables with an existing d.c. scale.


The series and parallel elements for range extension should be stable accurate resistances of low temperature coefficient, and of the required current or voltage rating. Because of the low resistance of a shunt, it has to be provided with double leads, one pair to the input and the other to the meter. A double-pole switch is required, but a universal shunt is simpler in a number of respects, and could be used with sockets instead of a switch. The shunt is matched to the meter by adjusting a swamp resistance in series with the meter. This has to be of several times the meter resistance in order to avoid errors arising from the different temperature coefficients of the external resistance and the moving coil.

A Receiver Output Matching Box

by G 5 U J

THE UNIT HERE DESCRIBED IS BOTH HANDY and cheap, and has proved itself in use at a friend's station. As the schematic diagram (Fig. 1) shows, it consists of one of the well-known ex-Service FL8 Filter Units, a high/low impedance matching transformer, and three standard jacks. Built inside an Oxo tin, or similar metal box, it can be placed alongside the Rx, where it will provide the answer to the impedance matching problem. The circuitry is quite straightforward as a

Operation is quite simple, and needs little explanation—on plugging a pair of high-resistance 'phones into J_1 , output is obtained from the 3-position filter—enabling CW to be copied even through quite heavy QRM. J_2 , of course, gives normal receiver output, whilst J_3 is employed in the case of low-resistance 'phones. Several other applications may occur to the reader, which have not been mentioned. The total cost of the parts needed should not exceed £1 or so, as the

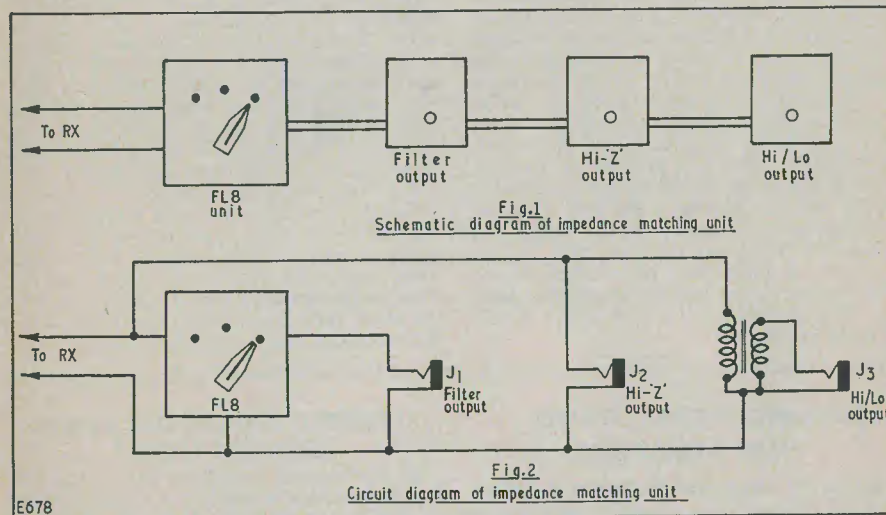

glance at Fig. 2 will show, and little time should be needed to assemble this handy little unit.

Few snags are likely to arise in construction providing care be exercised regarding insulation between the three jack sockets and the metal box. No specific design has been put forward, as it is assumed the reader may have ideas of his own as to layout, etc.

FL8 units are available on the surplus market for as little as 7s. 6d. to 8s. 6d.,* whilst in the same market the matching transformer should cost no more than a few shillings. The small outlay and time spent in building this useful piece of apparatus will be well repaid by the results obtained.

* The FL8 unit may be obtained from Messrs. N. R. Bardwell, 81 Sellars Street, Sheffield 8.

A SIMPLE CHASSIS PUNCH

by M. J. MORLEY

THIS LITTLE MACHINE WAS BUILT TO REDUCE the labour involved in piercing a large number of holes in a chassis before bending to shape. The size chosen was $\frac{3}{8}$ in as holes up to $\frac{1}{4}$ in can easily be drilled using an ordinary hand drill, and because both potentiometers, etc., and valvebase chassis cutters require a $\frac{3}{8}$ in hole.

Construction is simple and most of the materials can probably be found in the average junk box. The base is a flat steel plate, the size of which determines the available throat depth. Failing this a strong wooden base with a steel insert could be used. A $\frac{3}{8}$ in hole must be drilled in this plate, this being filed out underneath to allow clearance for the blank. The main arm is the next part, the strength of this determining the thickness of the material which may be handled. In the original version an arm of $\frac{3}{8}$ in x $1\frac{1}{2}$ in (from an old car tyre lever) enabled 18 s.w.g. aluminium to be handled at a throat depth of 3 in, while 22 s.w.g. could be cut at 6 in throat depth. The arm is fixed to the base by four $\frac{3}{8}$ in bolts using a $\frac{1}{2}$ in packing piece. At the end of the arm a $\frac{3}{8}$ in hole must be drilled to act as a bearing for the cutter; this hole must, of course, coincide with that in the base. A bush around the bearing length to at least $\frac{3}{8}$ in. If a $\frac{3}{8}$ in thick bar is available it would be ideal for the job.

The operating lever is fixed to the arm by a simple double linkage as shown in the diagram. A steel strip of about 1 in x $\frac{3}{8}$ in would be suitable. The cutter is from a piece of $\frac{3}{8}$ in diameter steel rod. One end is slotted and drilled to attach it to the operating lever; the cutting end is shaped as shown to make the cutting action easier. For work on aluminium the cutter does not need to be very hard; mild steel is quite suitable. Should it be desired to employ a hardened cutter, this is quite a simple thing to make. A length of $\frac{3}{8}$ in silver steel should be shaped as just described. To harden, it should be heated over a gas ring until the rod becomes "cherry red," when it should be immediately quenched by plunging into a pail of cold water. The silver steel will now be dead hard, and will need to be "let down." To do this, clean the cutting end with emery cloth until it is bright, and then heat again—but this time slowly. As the steel gets hotter, its colour will change. When it reaches a "dark straw," it should again be quenched in cold water. It is now ready for use.

For positioning of the work a grid may be marked on the base; in practice it was found easier to mark the hole and then position the work by sighting through the cutter bearing. The machine has now repaid many times over the short time spent on its construction by the increased ease of "chassis bashing."

JOBLING METAL OXIDE FILM RESISTORS

Extension of Range and Reduction in Prices


As a result of improved manufacturing techniques it has been found possible to extend considerably the ohmic range of the Jobling Metal Oxide Film Resistor (makers of "Pyrex"). These highly stable resistors are now available in values up to 2 megohms.

Economies resulting from increased sales allows substantial price reductions, effective immediately. These resistors will, in future, be marketed under the registered trade name "Electrosil".


"SIMPLE NOTES ON LEAD AND ITS USES"

It has become necessary to reprint this 4-page brochure which has, for over 4 years, enjoyed a steady demand among students not requiring an extensive or detailed knowledge of the mining, smelting and refining of lead, and who seek a brief account of its manifold uses.

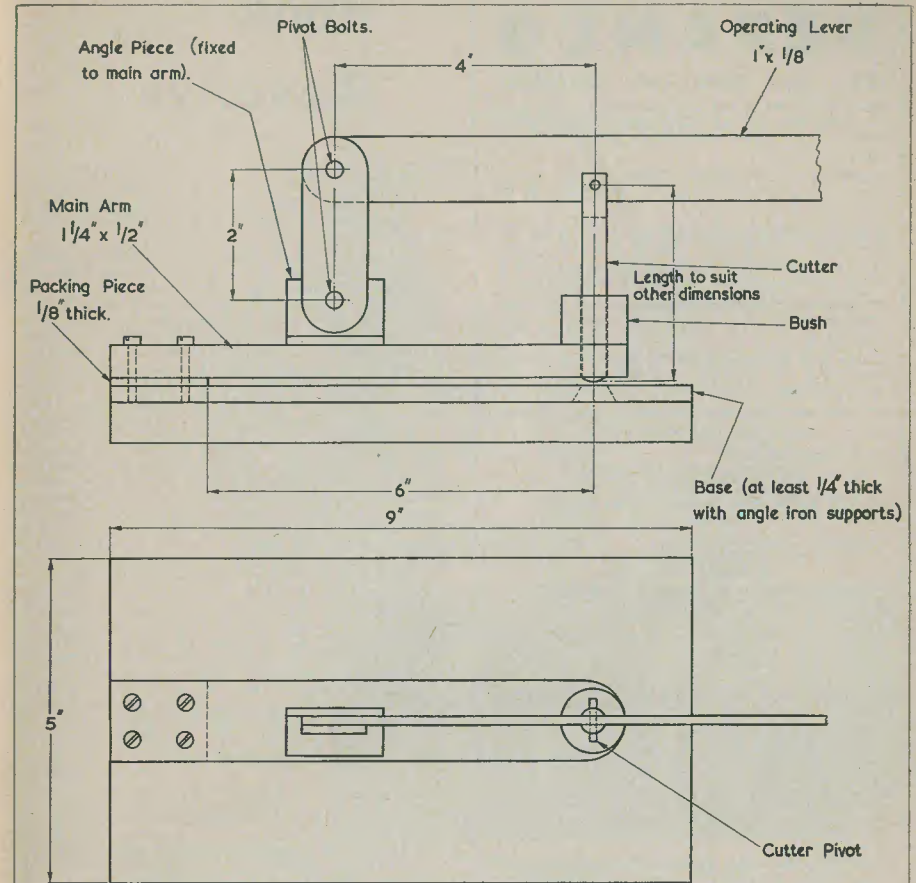The opportunity has been taken to re-write most of the text and to bring the factual information up to date. The Lead Development Association, 18 Adam Street, London, W.C.2 will be happy to meet demands from readers who are able to put them to good use.



Dimensions given are for guidance only.

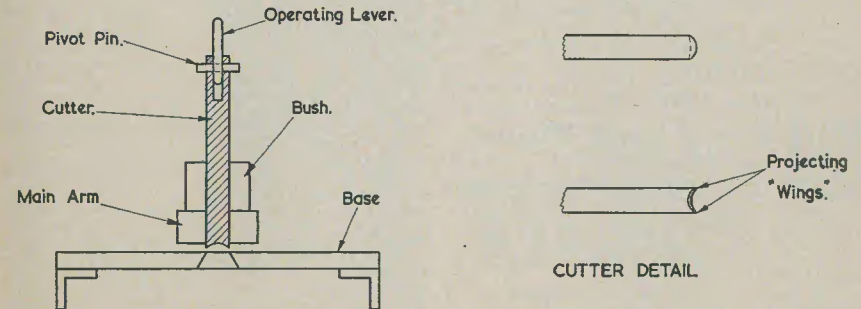

M671

REPANCO

HIGH GAIN TRANSISTOR COMPONENTS

MINIATURE RANGE—For pocket receivers. Ferrite Slab Aerial Type FS3. Medium Wave only. With fixing grommets. Size 3" x 3/4" x 3/8", 7/6.

Oscillator Coil Type XO8. Medium Wave only. Overall size 1/2" dia. x 1". Enclosed in Ferrite pots, 5/-.

I.F. Transformer Type XT6. Suitable for 1st and 2nd I.F. 455 Kc/s. Size 1/2" sq. x 1 1/4", 10/-.

I.F. Transformer Type XT7. Designed for 3rd I.F.T. or detector I.F.T. 455 Kc/s. Size as XT6, 10/-.

Push-Pull Interstage Transformer Type TT9. Ratio 1:1 C.T. radiometal core. Size 3/4" x 3/8" x 1 1/2", 12/6.

Push-Pull Output Transformer Type TT10. Ratio 8:1 C.T. matched to 3 ohm speaker. Size as TT9, 12/6.

Practical and theoretical circuits enclosed with each Repanco transistor component.

Mail Order and Trade

RADIO EXPERIMENTAL PRODUCTS LTD.

33 Much Park Street COVENTRY

Telephone 62572

Wholesale Enquiries and Export

REPANCO LTD.,

O'Brien's Buildings

203-269 Foleshill Road COVENTRY

Telephone 40594

NEW HI-FI PUBLICATIONS

MULLARD AMPLIFIER MANUAL	8/6
MULLARD TAPE PRE-AMP "C"	2/6
QUALITY AMPLIFIERS 7 designs	4/6
JASON FM TUNERS	2/6
MERCURY SWITCHED FM TUNER	2/-

Quality components and popular alternatives always in stock

Circuits for the Mullard 3-valve 3-watt amplifier, 2-valve pre-amp, tape amplifier free on request

J. T. FILMER 82 DARTFORD ROAD DARTFORD KENT
Telephone Dartford 4057

RADIO AMATEURS . . .

get your Licence in

Half The Usual Time!

You must be a good Morse operator! A "slap-dash" 12 w.p.m. neither satisfies the authorities, yourself, nor your operator friends. Morse operating is an exacting art unless your training is made simple and is based on sound fundamentals. For this reason, the Candler System was invented to take the "grind" out of Code tuition, turning a tricky subject into a pleasurable pursuit.

★ Send 3d. stamp for the "Book of Facts"

CANDLER SYSTEM CO
(Dept. 55 RC) 52b Abingdon Rd London W8
Candler System Company Denver Colorado U.S.A.

Book Reviews

RADIO ENGINEER'S POCKET BOOK (12th Edition). Edited by F. J. Camm. 180 pages. Published by George Newnes Ltd., Tower House, Southampton Street, Strand, London, W.C.2. Price 6s.

For a book which is small enough to be carried without discomfort in one's vest pocket, this well-established Newnes' publication contains a wealth of information in handy reference form. *Multum in parvo* could very well be used as a sub-title.

In addition to often-needed information on matters entirely "radio" in their application, many tables and formulae are given, such as those frequently required in arithmetic, geometry, mensuration and trigonometry, decimal equivalents, slide rule gauge points, powers and roots, and properties of metallic elements—to mention a mere few. This latest edition of the booklet contains several items of additional material, and the opportunity has been taken to revise the contents. In this latter connection the revision is stated to be a full one, but it would seem that the data on amateur wavebands, page 76, has somehow escaped the eagle eye of the publishers. The 5-metre band is no longer a permitted band for British amateurs due to its falling within television channel allocation, and the 15-metre and 160-metre bands are not mentioned.

The manner in which Kirchoff's Laws and their application are dealt with is certainly deserving of praise. It is surprising to find such a clear exposition tucked away in a small book like this one. On the other hand, crystal combinations found on page 46 seem to have nostalgic value only, particularly for grey-haired totterers like the writer of these notes. However, the omission of the zincite-bornite combination seems inexcusable if only for the sake of history!

On the whole, a very useful compendium, well produced and good value for money.

W. E. THOMPSON

TELEVISION ENGINEERS' POCKET BOOK (2nd Edition). Edited by J. P. Hawker. 264 pages, 140 diagrams, tables and illustrations. Published by George Newnes Ltd., Tower House, Southampton Street, Strand, London, W.C.2. Price 12s. 6d.

Servicing engineers will no doubt find this book to be useful in many aspects of their work. The treatment in terms of the number of pages devoted to any particular subject is not lengthy, but this does not mean that essentials are glossed over. Brevity is due to information being given briefly yet factually; verbosity finds no place in a book which has obviously taken account of the fact that those who need to consult it will have no time to waste on reading unnecessary padding. One of the most useful features is to be found in the list of intermediate frequencies contained in fifteen pages near the end of the book. Nearly fifty makes of television receivers are mentioned, and the number of models listed runs into about 1,500.

The chapters on fault-finding and aligning receivers contain many useful tips. Alignment procedure is simplified considerably by using the tables which show, step by step, in what order the tuning circuits should be brought into resonance, and the method of setting up test equipment to achieve the desired results.

Other chapters deal with standards and waveforms, a survey of the British television network, basic circuitry, projection television, Band III conversions, installing receivers, receiving aerials, interference, etc. The diagrams are clear and adequately illustrate the matters discussed in the text. The tables giving brief details of cathode ray tubes and valves, and equivalents, are a useful reference.

W. E. THOMPSON

Technical training in radio television and electronics engineering with




The decision is YOURS. To be a success in your chosen career; to qualify for the highest paid job . . . to control a profitable business of your own. ICS home-study courses put your plans on a practical basis; teach you theory and practice; give you the knowledge and experience to take you, at your own pace, to the top.

Choose the RIGHT course, RADIO AND TELEVISION ENGINEERING . RADIO AND TV SERVICING . RADIO SERVICE AND SALES . ELECTRONICS . VHF/FM ENGINEERING

ICS provides thorough coaching for professional examinations: A M B R I T . I R E , City and Guilds Telecommunications, Radio Servicing; Radio Amateurs P M G C E R T . (M A R I N E) .

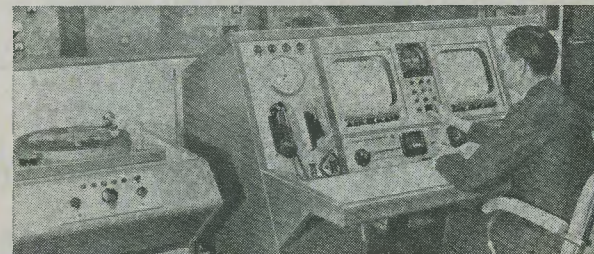THERE ARE ICS COURSES TO MEET YOUR NEEDS AT EVERY STAGE OF YOUR CAREER.



The first step towards success is to fill in and post this coupon today:

In return you will receive the FREE 60-page ICS Prospectus listing technical examinations and their appropriate ICS courses PLUS details of over 150 specialised subjects.

AN EYE-OPENING SURVEY OF THE ICS WAY TO COMPLETE TECHNICAL TRAINING

LEARN AS YOU BUILD
Practical Radio Course

Gain a sound up-to-professional-standards knowledge of Radio and Television as you build YOUR OWN 4 valve T R F and 5 valve superhet radio receivers, signal generator and high-quality multi-tester. At the end of the course you have three pieces of permanent and practical equipment and a fund of personal knowledge and skill . . . ICS Practical Radio courses open a new world to the keen radio amateur.

Other ICS courses include:

MECHANICAL, MOTOR, FIRE, CHEMICAL AND ELECTRICAL ENGINEERING, ETC., ETC. FARMING, GARDENING, ARCHITECTURE, WOODWORKING, SELLING AND MANAGEMENT, ART, PHOTOGRAPHY.

A whole world of skill and knowledge for the keen student.

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 248C Intertext House Parkgate Road London SW11

NAME..... AGE.....

ADDRESS

OCCUPATION..... 9.59

Premier RADIO CO

NOW UNDER ENTIRELY NEW MANAGEMENT




The "Petite" PORTABLE
MAY BE BUILT FOR **£7.7.0** plus 3/- P. & P

Batteries extra.
HT 10/- (Type B126) or equivalent.
LT 1/6 (Type AD35) or equivalent.

★ Size only 8" x 8" x 4 1/2"
★ Instruction book 1/6

Battery Eliminator, available in component form price 37/6 plus 2/- p. & p.

THE BEREC

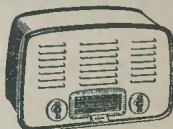

Battery Receiver for only **£4.19.6** plus 5/- p. & p., or **£1** deposit and 5 monthly payments of 19/-. This receiver is ideally suitable for use in the home or where normal electricity supply is not available, remarkable reception on both medium and short wave-bands, incorporating the following latest type miniature battery valves: DK92, DF96, DAF96, DL96, and operates on an external B103 battery or equivalent. It is housed in an attractive two-tone metal case. Size 11 1/2" x 7 1/2" x 5 1/4". Battery EXTRA, 18/6.

The "MID-FI"

A NEW DESIGN

4 1/2 WATT AMPLIFIER KIT


MAY BE BUILT FOR **95/-** plus 3/- P. & P.



A new circuit for the home constructor requiring a good quality medium powered amplifier for reproduction of records or f.m. broadcasts. Technical specifications: separate bass and treble controls Valve line-up EF86, EL84, EZ80 Voltage adjustment for a.c. mains from 200/250 volts, 3 or 15 ohms impedance. Negative feedback. Size 7" x 5" x 2", overall height 5". Silver hammered finished chassis. Instruction book available 1/-

MUSIC in your pocket

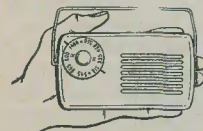With the pocket-sized transistor Superhet Receiver. Yours for an unrepeatable price of **£8.19.6**, p. & p. 2/6, or 25/- deposit and 8 monthly repayments of **£1.1.10**. Battery 2/-.




This receiver incorporates 6 selected transistors and the latest type printed circuit. It is extremely sensitive on medium waveband only, incorporating an internal Ferrite aerial, and operates on a 9-volt type PP4 battery. Fully constructed and housed in an attractive plastic cabinet in red, cream or blue.

PREMIER RADIO CO. 23 TOTTENHAM COURT ROAD LONDON W1 Telephone MUSeum 3451/2

MODERNISE YOUR RADIOGRAM

WITH AN *Armstrong* CHASSIS

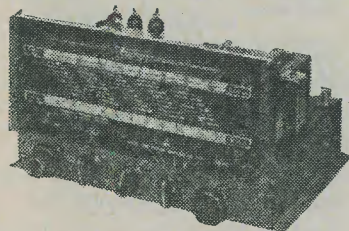

STEREO 44 CHASSIS 27 GNS

(illustrated)

8 watts output, 4 watts each channel ● 20dB negative feedback each channel ● Full FM band (87-108 Mc/s) and medium wave ● Stereo and monaural inputs for all crystal pick-ups, tape record and playback ● Separate bass and treble controls.

STEREO-TWELVE CHASSIS 36 GNS

12 watts push-pull output, 6 watts each channel ● Full FM band, medium and long waves ● Stereo and monaural inputs for all pick-ups, radio, tape record and playback ● Separate bass and treble controls ● AFC on FM band, ferrite aerial and magic eye.

JUBILEE CHASSIS 28 GNS

6 watts push-pull output, monaural ● Full FM band, medium and long waves ● Inputs for all pick-ups, tape record and playback ● Separate bass and treble controls ● AFC on FM band, ferrite aerial and magic eye.

Post this coupon or write for descriptive literature and details of Home Trial facilities, Hire Purchase Terms and Guarantee. Demonstrations at our Holloway Showroom 9 a.m.-6 p.m. Sats. 9-5 p.m.


NAME _____
ADDRESS _____

CSC

ARMSTRONG WIRELESS & TELEVISION CO. LTD

Walters Road · London N7 · NORth 321

KOFFEREMPFFÄNGER STERN 1

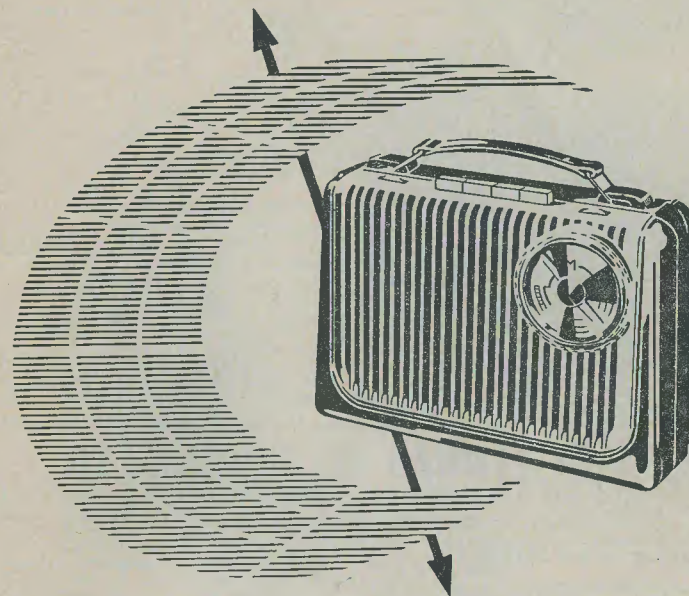

Portable Radio Stern 1 for battery or mains, approx. 2.9 kg (6 1/2 lb.) including the 10-hour accumulator (i.e. battery). Battery can be re-charged by owner himself. Dry-battery lasts about 100 hours.

Comfortable and elegant, with the technical perfection of a full-size apparatus: 2 Valves, 5 Transistors, Three wave band change by push button arrangement.



Further details and information may be obtained from:

Kurt Wolf, White's Hotel, Lancaster Gate, London, W.2

Information regarding Export:

Deutscher Inner & Aussenhandel
Elektrotechnik,
Berlin, N4, Chaussee. 111/113

SUMMER TIME IS AERIAL TIME

HEADPHONES. H.R. type, 4,000 ohms, very sensitive. Only 12/6 pair. P. & P. 1/6. C.L.R. (low res.) 8/6, P. & P. 1/6.

RECORD CHANGERS. Latest B.S.R. Monarch UA8 with manual and auto control, latest Ful-Fi Cartridge. List £9.15.0. OUR PRICE £6.19.6, carr. paid.

MULTI-WAY CABLE. $\frac{3}{8}$ " diam. 7 colour coded wires. Ideal for mobile or inter-chassis connection. Any lengths cut, 1/3 per yard. P. & P. 1/6 min.

10-WAY CABLE (5 pairs). Screened and plastic covered. Any length cut, 2/- per yard. P. & P. 1/6 min. 7-way (unscreened), 1/3 yard.

DUAL RANGE VOLTMETERS. Dual range 0-5V and 0-100 M.C. 1,000 Ω /V. Ranges easily extended. With test prods and leads. Complete in solid leather carrying case $6\frac{1}{2}$ " x 5" x 2 $\frac{1}{4}$ ". A GIFT at 25/-. Post free.

ABSORPTION WAVEMETERS. 3.00 to 35.00 Mc/s in 3 switched bands, marked on scale. Complete with indicator bulb. A MUST for any ham shack. ONLY 19/6 post free.

SPECIAL OFFER ROTARY CONVERTERS

6V input, 250V, 125mA output. Only 5 $\frac{1}{2}$ " x 3" x 3" 17/6 each. P. & P. 3/-.
12V MINIATURE ROTARIES

Only 4 $\frac{1}{2}$ " x 2 $\frac{1}{2}$ " overall. Output 360V, 30mA or 310V, 70mA. NEW LOW PRICE £2/6 each or 22/6 for 2. P. & P. 1/6.

100 KC/S CRYSTALS. American 3 pin based crystals. New condition. Worth £3.10.0. Only 25/-. Post free.

R.F. CHOKES. 2.5mH, 120mA. Pie wound, 2/- each. Three or more post free.

NATIONAL TYPE R-300 μ . Type R-300 μ pillar mounting choke, 1mH, 300mA, 3/- each or 6 for 15/-.

SHADED POLE MOTORS. For tape decks or gram units. 3-hole fixing, twin coil, closed field type, 200/240V, 50 c/s, 15/- each or 27/6 for two. P. & P. 2/-.

RACK MOUNTING PANELS. 9" x 5 $\frac{1}{2}$ ", 7", 8 $\frac{1}{2}$ ", or 10 $\frac{1}{2}$ " black crackle finish, 5/9, 6/6, 7/6 respectively, postage and packing 2/-.

AERIAL EQUIPMENT

COPPER WIRE. 14g. h.d.: 140' 17/-; 70' 8/6; 7/25 stranded; 140' 10/-; 70' 5/- plus 2/- P. & P.

RIBBED GLASS INSULATORS. 3" 1/6 each or 6 for 7/6. P. & P. 1/6.

TWIN FEEDER. 300 ohm twin ribbon feeder, similar K25, 6d. per yard. K358 Telcon (round) 1/6 per yard. Post on above feeder and cable 1/6 any length.

SUPER AERAXIAL CABLE 1/6 a yard. P. & P. 1/6.

CERAMIC FEEDER SPREADERS. Type F.S. 6" 9d. each or 8/- doz. P. & P. 2/-.

CERAMIC "T" PIECES. Type AT for centre of dipoles, 1/5 each or 3 for 4/-. P. & P. 1/6.

MOSLEY TRI-BAND BEAMS T33, JR, 3 EL ... £25
TA32 JR, 2 EL ... £18
V3 JR, Vertical 3 Band ... £18
PLACE YOUR ORDER EARLY

NEW MOSLEY POWER BEAMS. Write for details. 300 watt, 50 ohm COAX, $\frac{5}{16}$ " dia., very low loss, 1/6 yard or 20 yds. 25/-. P. & P. 1/9

CHAS H. YOUNG LTD (Dept. R)

110 DALE END BIRMINGHAM 4 (Tel. all departments) CEN 1635

★ VALVES NEW TESTED AND GUARANTEED ★

1R5	7/6	6X4	7/6	DK91	7/6	EF92	5/6
1S5	7/6	6X5G	6/-	DK92	9/-	EL41	10/-
1T4	6/-	12A8	8/-	DK96	9/-	EL84	9/-
3S4	7/6	12A7	7/6	DL92	7/6	EL91	7/6
3V4	8/-	12A7	7/6	DL94	8/-	EY51	10/6
5U4G	6/-	12AX7	9/-	DL96	9/-	E135	8/-
5Z4G	9/-	12K8GT13	6/-	EB91	5/6	EZ40	8/-
6AM6	6/9	12K7GT	8/6	EB41	8/-	EZ80	8/-
6AL5	5/9	12Q7GT	7/-	EF80	9/6	EZ81	8/6
6AT6	7/6	25A6G	10/6	ECC81	7/6	PCF82	11/-
6BA6	8/6	25L6GT	7/6	ECC82	7/6	PL81	13/6
6BE6	7/6	35Z5GT	8/6	ECC83	7/6	PL82	13/6
6BR7	10/6	35L6GT	9/6	ECC84	8/6	PY81	8/-
6BW6	8/6	53KU	11/6	ECF82	11/-	PCC84	9/-
6J5G	5/6	807	6/9	ECH81	10/6	PCF80	9/6
6J7GT	8/6	5763	10/6	ECH42	10/-	U76	8/6
6K7G	2/6	DAF91	7/6	ECL80	12/6	UBC41	10/-
6K8G	7/6	DAF96	9/-	EF36	7/6	UCH42	9/-
6Q7GT	8/6	DF91	7/6	EF39	5/6	UY41	10/-
6SL7GT	8/-	DG96	9/-	EF41	9/-	UL41	9/6
6SN7GT	8/6	DH76	8/6	EF80	8/-	UY41	8/-
6V6G	7/6	DH77	7/6	EF91	6/9	W76	8/6

Matched Pairs. EL84, 23/-; 6V6G, 17/-; 6BW6, 18/-; KT33C, 19/6; KT66, 27/6; 807 14/6 pair

1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DK92, DL92, DL94, any four, 27/6 per set
P.P. Op. Transformers. MR 3-15 ohms for EL84, 6V6, 6BW6, etc., 18/6; Op. Pen. 50mA, 5/6; 30mA, 4/6
Volume Controls. All values, long spindle. L/S 3/-, s.p. 4/-, d.p. 4/9, ext. spkr. control 3/-
W.W. Pots. Pre-set 3/-; 3W long spindle 5/6, s.p. 6/6
P.M. Speakers. 3 ohm. 5" 16/6, 6 $\frac{1}{2}$ " 17/6, 8" 21/-, 10" 25/-, 12" 30/-, Bakers 12" 15 ohm 15V, 90/-
Coaxial Cable. 75 ohm $\frac{1}{4}$ " stranded, 8d. yd; semi-air spaced, 9d. yd; screen cable single and twin, 9d. yd
Coaxial Plugs 1/- each; Sockets 1/- each
P. and P. 9d. to £1; 1/6 to £2; over £2 post free. C.O.D. 2/6

R. COOPER G8BX 32 SOUTH END CROYDON SURREY CROYDON 9186

★ C.R.T. Isolation Transformers with nil, 25% and 50% boost, low capacity a.c. mains 200/250V for 2V 4V, 6.3V and 13V tubes. All 10/6 each

Valveholders. 4, 5, 7 pin English and U.S.A. B7G, B9A, 10, M0, B8G, 9d. each; B7G, B9A with screening can, 1/6; B12A, 1/3. Aladdin formers $\frac{1}{4}$ " with core, 8d. each
Scotch Boy Recording Tape, 1,200ft reels, 27/-
Jack Plugs, miniature standard, 3/-; Sockets 3/-
2-Gang Condensers, 0.0005 μ F small size, 7/6
I.F. Transformers, 465 kc/s, small size, 7/6 pair
Capacitors, small mica, 5% 1pF to 100pF, 8d.; 120pF to 1,000pF, 9d.; 1,000V wkg. .01, .0015, .0025, .004, .005 μ F, 1/- each
Crystal Diodes, G.E.C., 1/6 each
Headphones, lightweight, 4,000 ohm, 16/6 pair
Ceramic Capacitors, close tol. 500V for V.H.F., 9d.
Paper Capacitors, tubular, 0.01 μ F 1,000V, 1/-; 0.1 to 0.5 μ F 500V, 10d.
Paper Blocks, 4 μ F, 1,000 wkg., 3/6
Rectifiers, contact cooled, 250V 50mA, 7/6; 85mA, 9/6
Reaction Condensers, .0001, .0003, .0005 μ F, 4/6 each
Heater Trans. 200/240V, 6.3V, 1.5A, 7/6
Resistors, $\frac{1}{2}$ and $\frac{1}{4}$ W, insulated, 4d. and 6d.; 1W, 8d. 6V W.V., 1/-; 10V, 2/-
Electrolytics. Wire ends. 25/25V, 1/6; 50/50V, 2/-; 12/50V, 9d.; 8/450V, 2/-; 16/450V, 2/9; 16/500V, 3/6; 32/450V, 4/-; 8+8/450V, 4/6; 8+16/450V, 4/6; can types: 16/450V, 3/6; 16+16/500V, 6/-; 32/500V, 6/6; 32/450V, 6/6; 20+20/450V, 4/6; 64+120/275V, 7/6
Wavechange Switches, midjet: 1p 12W, 2p 6W, 3p 4W, 4p 3W, 4p 2W, long spindles, 4/6
Toggle Switches. QMB, s.p.s.t., 2/-; s.p.d.t., 3/3; d.p.s.t., 3/6; d.p.d.t., 4/-
Chokes, 80mA, 15H, 8/6; 100mA 10H, 10/6; 150mA 10H, 14/6

★ Solder, Multicore, 4d. yd; Sleeving 2mm, 3d. yd

Build your own HI-FI!

At last! A specially selected and designed HI-FI Sound installation for your home at really reasonable cost!

You save because you assemble every-thing yourself following our step by step instructions. You gain because you learn about the equipment as you build and are able to service and maintain it afterwards.

Best of all—you'll have fun building it and be thrilled with the finished instrument, which will bring you an entirely new experience in the enjoyment of sound.

No previous skill or experience is needed. Post coupon now for full details, without any obligation. Easy terms available.

Equipment includes:
Luxury Cabinets · Top quality Amplifier for stereo or non-stereo reproduction
VHF/FM Radio Units · Record Player
Tape Recorder · Hi-Fi Speaker system

RADIOSTRUCTOR

Britain's Leading Radio Training Organisation



FREE BROCHURE - POST TODAY

Radiostructor, Dept. H35, 46 Market Place, Reading, Berks
Please send Brochure without obligation to:

Name BLOCK
Address CAPS
(301) PLEASE
9/59

Television Tubes

Replacement TV tubes as supplied to the trade. Every tube is guaranteed opened, repaired and resealed by craftsmen. Orders received and accepted are dispatched within 7 days. Failing satisfaction, money refunded immediately.


MULLARD AND MAZDA
12", 14", 15", 17" ... £6.5.0
21" ... £8.0.0

Full 12-month guarantee. Registration card enclosed with every tube. Carriage and insurance 10/- extra. Trade enquiries invited.

HAMILTON & HORSMAN DISTRIBUTORS LIMITED

199 Becontree Avenue Dagenham
Essex Telephone SEVen Kings 2306

RADIOSETTE

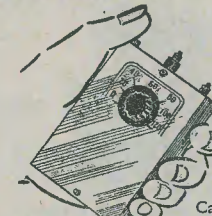


The ideal low cost transistor pocket radio for the beginner. The circuit utilises the new R.C.S. VARILoop-STICK transistor coil. A specially designed miniature .0004 tuning condenser permits the set to be in a case which fits the palm of your hand.

Can be built in 30 minutes **30/-**

All components are sold separately, full construction data including plan of parts, 2/-

ALL-WAVE RADIO 35/-

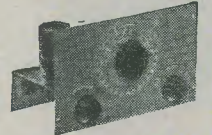Ideal for the beginner or for those requiring a simple stand-by receiver



This 1 valve S.W. receiver can be built for 35/- from our list of components, which can be purchased separately. It includes valve and 1 coil covering 20-40 metres. Provision is made to increase to 2

or 3 valves if required, and all components are colour-coded so that the beginner can build this set quite easily. Send 2/- for specification, wiring diagram, layout and price list.

Postage: Under 10/-, 9d.. Under 40/-, 1/6
Over 40/-, post free

R.C.S. PRODUCTS (RADIO) LTD

11 Oliver Road London E17 Mail Order only

SMITH'S of Edgware Road

ELECTRONIC COMPONENTS
DISTRIBUTORS FOR OVER 25 YEARS

BLANK CHASSIS

Precision made in our own works from commercial quality half-hard aluminium of 16 s.w.g. (1/16" thickness, these chassis go all over the world (and off it—in rockets!).

Same day service for ANY SIZE, to nearest 1/16" and up to 17" of straightforward two, three or four-sided chassis. Specials dealt with promptly.

SOLDERED CORNERS

While these chassis, owing to their thickness, hardness and efficient folding, will carry components of considerable weight and normally require no corner strengthening, we can do this by a special soldering technique at 6d. extra for each corner.

FLANGES

1/4", 3/8" or 1/2" flanges (inside or outside) 6d. extra for each bend.

PRICE GUIDE (normal chassis only)

Work out total area of material required, including waste, and refer to table below:

48 sq. in.	4/-	176 sq. in.	8/-	304 sq. in.	12/-
80 sq. in.	5/-	208 sq. in.	9/-	336 sq. in.	13/-
112 sq. in.	6/-	240 sq. in.	10/-	368 sq. in.	14/-
144 sq. in.	7/-	272 sq. in.	11/-	and pro rata	

Post 1/3 Post 1/6 Post 1/9
Discount for quantities. Trade enquiries invited. Spray finished arranged for quantities of 25 or over.

PANELS

The same material can be supplied for panels, screens, etc. Any size up to 3ft x 4/6 sq. ft. (sq. in. x 3/4) Post, up to 72 sq. in. 9d., 108 sq. in. 1/3, 144 sq. in. 1/6, 432 sq. in. 1/9, 576 sq. in. 2/-.

287/289 EDGWARE ROAD LONDON W2
Telephone PAD 5891/7595

REPANCO

HIGH GAIN COILS

Dual Range Crystal Set Coil, Type DRX1	2/6
Dual Range Coil with Reaction, Type DRR2	4/-
Matched Pair Dual Range T.R.F. Coils, Type DRM3	8/-
Pair Dual Range Superhet Coils, Type SH4	8/-
Miniature Iron Dust Cored Coils, Type "R"	each 3/3
Range	Aerial H.F. Osc.
800 2,000 m.	RA1 RHF1 RO1
190 550 m.	RA2 RHF2 RO2
70 230 m.	RA3 RHF3 RO3
15 50 m.	RA4 RHF4 RO4

Ferrite Rod Aerial, Dual Range Type FR1	12/6
Miniature I.F. Transformers, Type MSE (465 kc/s)	pair 12/6
Standard I.F. Transformers, Type TCG (465 kc/s)	pair 13/6

Send S.A.E. for latest Repanco Component Catalogue

Radio Experimental Products Ltd.


33 Much Park Street, COVENTRY
Telephone 62572

17" TV 19 GNS

WHILE STOCKS LAST

FEATURES

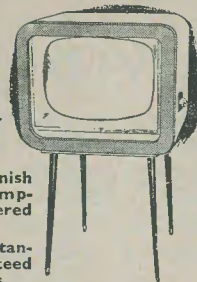- ★ Beautiful latest finish cabinet in contemporary style, covered and washable.
- ★ 17" BRITISH Rectangular Tube. Guaranteed fully for 12 months.
- ★ 13 channels "Turret Tuned" - ITV/BBC. Extra coils at only 7/6 a pair (with order).
- ★ Chassis. 14 B.V.A. Valves. - Salvaged but re-conditioned and guaranteed 3 months. Carr. and Ins. 30/-.



SUPER SUPERIOR RADIO 89/6


4 waveband. 5 valve superhet radio. 2-tone covered metal cabinet size 24 1/2 x 12 x 10". 4 control knobs. Postions for gram. p.u. and extension speaker. A.C. only. Ins. carr. 8/6. DEFERRED TERMS TO SUIT ALL POCKETS Monthly credit terms or weekly easy payments -Details on request.

DUKE & CO

621/3 Romford Road
Manor Park E12
Telephone 1LF 6001/3

Catalogue FREE upon request

Fully Guaranteed
Components

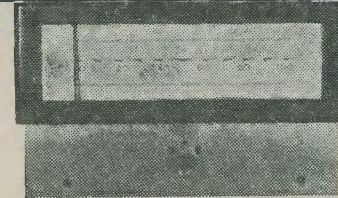

S. L. 16 DRIVE

A general purpose slide rule drive for FM/VHF units, short-wave converters, etc. Printed in two colours on aluminium, with a 0-100 scale, and provision is made for individual calibrations. Complete with bronze escutcheon and glass.

PRICE 13/9

It's reliable if it's made by Jacksons

JACKSON BROS
(LONDON) LTD.

Kingsway · Waddon · Surrey
Telephone CROydon 2754/5



Broadway
ELECTRONICS

92 MITCHAM ROAD . LONDON . SW17

Telephone BALham 3984
(near Tooting Broadway)

VALVES

3 months guarantee from Invoice Date

1R5	7/-	*DF96	8/6	ECC81	7/6	MU14	7/6
1S5	7/-	*or 31/- set		ECC82	7/6	5Z4	9/-
1T4	6/6			ECC83	8/6	UL41	8/6
3S4	8/-	EL41	8/6	ECC84	10/-	UY41	7/6
3V4	8/-	EZ40	7/6	ECC85	7/6	PL81	11/6
*DK96	8/6	EL84	9/-	EY51	12/-	PL82	8/6
*DAF96	8/6	EZ80	7/6	ECL80	10/-	PL83	8/6
*DL96	8/6	PY81	8/6	PY82	7/6	PY80	7/6

PERDIO TRANSISTOR RECEIVERS. All the parts and comprehensive instructions for making this superb 6 transistor receiver. Ivory, Red or Blue cabinets. A bargain at **£8.15.0.** POST FREE.

B.S.R. MONARCHS. 4 speed autochangers. **£6.15.0.** + 5/- p.p. Collaro Conquest 4 speed changer **£7.10.0.** + 5/- p.p.

PLESSEY 12" Speakers Cloth Suspension, 15 ohms—handle 5 watts. Only **50/-** plus 2/6 p.p.

ELAC 8" (Re-Coned) 12/6 + 1/6 p.p.

RICHARD ALLEN 7X4—17/6.

BUILD YOUR OWN



MAYKIT TRANSISTORISED CAR RADIO

- ★ HYBRID DESIGN—5 VALVE SUPERHET, TRANSISTOR AND PRINTED CIRCUIT
- ★ STANDARD SIZE 7" x 2"—12V BATTERY
- ★ ALL NEW COMPONENTS—AVAILABLE SEPARATELY OR IN COMPLETE PACK

First and best DO-IT-YOURSELF Car Radio. Uses new Brimar low volt valves, no vibrator. Printed circuit and power transistor. Negligible "fade" and no "buzz." Only 1.5 amp. consumption. Complete with chassis assembly, filter box and output stage including elliptical loudspeaker and detailed instructions. Also Jason Car Radios. Send 3/6 for Car Radio booklet.

Service facilities available

Can be built for **£13.10.0** plus 5/- p. & p.

(See page 673 March issue)

Cash with order

or write for BUY-AS-YOU-BUILD details

Dept. D **MAYRA ELECTRONICS LTD**
118 BRIGHTON ROAD, PURLEY
Telephone Bywood 1263

Ask "ARTHURS" First

NOTE NEW ADDRESS AT

125 Tottenham Court Road
London WC1

Close to Warren Street Station

You will have the same service and obtain all your requirements in Radio Components, Electrical Goods, Accessories and Television as previously

Test Instruments in stock include Avo, Advance, Cossor and Taylor. List on request

VALVE MANUALS AVAILABLE
Mullard 10/6 Brimar No. 7 6/-
Osram Part 1, 2nd Edition 7/6
Post and packing 9d. each extra


Arthurs first
Est. 1919

Proprietors ARTHUR GRAY LTD

Gray House
125 Tottenham Court Road
London WC1

Telephone EUSton 5802/3/4

DALY MINIATURE ELECTROLYTICS

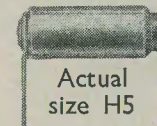

Actual size H5

Send for descriptive leaflet giving full details of complete new range

DALY (CONDENSERS) LTD

West Lodge Works The Green
Ealing London W5

Telephone EALing 3127/8/9

EDDY'S (NOTTM) LTD

172 ALFRETON ROAD • NOTTINGHAM

SURPLUS NEW AND GUARANTEED VALVES BY RETURN

AZ31	9/-	EF91	4/-	Z63	5/-	6SG7M	5/6
DAF96	8/6	EF92	5/-	Z66	8/-	6SJ7M	6/6
DH63	8/6	EL84	9/-	Z77	4/-	6SN7GT	4/9
DH77	7/6	EL85	9/6	1DS	9/6	6V6G	5/11
DK92	9/-	EL91	4/-	1L4	3/9	6V6GT	6/-
DK96	8/6	EY86	10/6	1R5	7/-	6X5GT	4/6
DL96	8/6	EZ80	7/11	1T4	5/3	7B7	8/-
DF96	8/6	GT1C	7/6	1S5	6/6	7C5	7/6
DM70	7/6	KT33C	8/6	3S4	7/-	7C6	7/6
EB34	1/6	KT36	9/6	3V4	7/9	7H7	7/6
EB91	4/6	L63	4/-	3Q4	7/6	7S7	9/6
EBC41	9/-	KTW61	7/6	5U4G	6/6	7Y4	7/6
EBF80	9/-	MU14	8/6	5Z4G	9/-	10F1	9/6
ECC81	6/-	OZ4	5/6	6AG5	5/-	10F9	9/6
ECC82	7/-	P61	2/6	6AT6	7/-	12A7	9/-
ECC83	8/-	PCC84	8/6	6AM6	4/-	12A7	6/-
ECC84	9/-	PCF80	9/-	6AL5	4/6	12AU7	7/-
ECC85	9/-	PCL82	12/-	6B8G	2/11	12AX7	7/6
EFC80	11/6	PEN36C	9/6	6BA6	6/6	25L6GT	9/6
ECH42	9/-	PL33	9/6	6B16	6/6	25Z4G	8/6
ECL80	10/6	PL81	13/6	6C4	4/-	35L6GT	9/6
EF36	2/6	PL83	9/-	6F1	9/-	35W4	7/6
EF37	4/6	PY31	8/6	6F6M	7/6	80	8/-
EF40	13/6	PY81	8/6	6F13	9/-	90AV	4/6
EF41	9/-	PY82	8/6	6F33	5/6	807(B)	3/9
EF42	9/6	PZ30	9/6	6H6M	2/6	807 (USA)	5/6
EF50	2/9	U31	8/6	6J5G	2/6	954	1/6
EF50(R)	4/-	U35	9/6	6J5GT	3/6	955	3/11
EF55	3/6	UBC41	8/-	6J5M	4/6	956	2/11
EF80	7/6	UCH42	9/-	6K7G	2/6	9001	4/6
EF85	7/-	UF41	9/-	6K8G	6/6	9003	4/-
EF86	13/6	UL41	8/6	6Q7G	8/3	9006	4/-

LUXEMBOURG EXPANDING AERIALS. Compact and easy to fit. No technical knowledge required. Greatly improve reception. 3/11, post 6d.
ACOS CRYSTAL PICK-UPS. Turnover head (two sapphire styli), 29/11, post 2/6.
NEON MAINSTESTER/SCREWDRIVERS 4/6, post 4d.

JACK PLUGS. Standard type, 1/11, post 6d.
DIMMER SWITCHES. Ideal for train speed regulator, 1/11, post 6d.
DYNAMOTORS. 200V d.c. to 12V d.c. Ideal for train sets. 19/11, post 2/6.
GERMANIUM DIODES 1/- each, 10/- doz, post 4d.
MORSE TAPPERS. Plated contacts, adjustable gaps, heavy duty, good quality. 3/6 each, post 9d.

CONDENSERS. Tubular wire end (not ex-Govt.). 8µF 450V 1/9; 8+8µF 450V 2/9; 16µF 450V 2/9; 16+16µF 450V 3/9; 32µF 450V 3/9; 32+32µF 350V 4/-; 16+8µF 450V 3/11, post 1/-.

RECTIFIERS. Contact cooled, 250V 60mA 8/6, RM1 4/9, RM2 7/-, RM3 7/6, RM4 15/6, RM5 19/6, post 1/-.
NIFE ACCUMULATORS. Midget single unit, size 3" x 2 3/8" x 3/8", 1/11 each, post 1/6.

THROAT MIKES 1/- each, post 6d. Could be used for electrifying musical instruments

GUITAR PICK-UP "THE PLECTRO." Super hi-fi non-acoustical universal fitting, 3" x 1 1/2" x 1/2". High quality output. Complete with lead and plug. Full and easy instructions. 39/11, post 1/-.

VIBRATORS. 12 volts 4-pin, 4/11, post 1/-.
PLASTIC CASES suitable for transistor portables. Size 6" x 3 1/2" x 1 1/2". Attractive black and white, 3/11, post 1/-.

ALL ABOVE ARE NEW AND GUARANTEED

Any parcel insured against damage in transit for only 6d, extra per order. All uninsured parcels at customer's risk. C.W.O. or C.O.D. only. Postage and packing 6d, extra per valve. Over £3 FREE.

It pays to go— to VIDIO

For value in Rebuilt Cathode Ray Tubes try Vidio. Each tube fully guaranteed for twelve months and fitted with a BRAND NEW Electron Gun Unit. Free Delivery in the U.K. with an immediate, off-the-shelf service.

TRADE ENQUIRIES INVITED

Write direct to the VIDIO REPLACEMENT COMPANY

(THEY'RE TRADE ASSOC. APPROVED)

Hales Street
Deptford High Street
London SE 8

Telephone TIDeway 4506

Member of the Association of
Tube Rebuilders



The Teletron TRANSIDYNE

Portable 6-Transistor Superhet
Receiver with printed circuit

Circuit diagram with
instructions available
from most advertisers
in this magazine, 1/-
post free

SAM MOZER LTD

288 Hedge Lane London N13

Telephone PALmers Green 1748

Sole Distributors to the Trade


Featured on the Front Cover of this issue!

See page 116 for full details



THE TOURIST PORTABLE

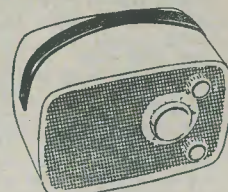light-weight Battery Radio. Size only 8" x 5 1/2" x 4", weight 3 1/2 lb. Uses B.114 Battery, 8/- extra.
2 WAVEBAND—4 LOW CONSUMPTION VALVES "96" SERIES—FERRITE ROD AERIAL
 Receiver Components Kit 57/6 P. & P. 1/6
 5" Speaker and o/p Trans. 21/- P. & P. 1/6
 Set of 4 Miniature Valves 35/- P. & P. 9d.
 Cabinet, Dial and Knobs, etc. 22/6 P. & P. 2/-



**MAINS
UNIT KIT**
45/- P. & P. 1/6

TERRIFIC PERFORMANCE—REMARKABLE SIZE—STAGGERING VALUE
COMPLETE KIT ONLY £6.10.0
 Post Free Latest circuitry, A.V.C. and neg. feedback. Instruction Booklet 1/6 (Free with Kit)

RECORD PLAYER BARGAINS
 All Brand New and Latest 4-sp. Models
SINGLE PLAYERS. B.S.R. (TU9) 90/-; Collaro (4/564) 6 gns.; Garrard (4SP) £7.10.0; Garrard (TA Mk 2) £8.19.6. Carr. and ins. 3/6.
AUTO CHANGERS. B.S.R. (UA12) £6.19.6; Collaro (Conquest) £7.19.6; B.S.R. (UA12) with stereo and monaural cartridge, 10 gns. Garrard (RC121/4D/Mk 2) plug in head and stereo adapted, 10 gns.; Carr. and ins. 4/6. Garrard GCS/10 stereo head £2 extra. Replacement Sapphire Styli available all units.

RE-GUNNED TV TUBES new budget prices

... and now 12 months guarantee!

All tubes rebuilt with new heater, cathode and gun assembly-reconditioned virtually as new:

12"-£6, 14"-£7, 17"-£8.10.0 etc
 10/- part exchange allowance on old tube
 Carr. and ins. 10/- Comprehensive Stocks—quick delivery

BAND III TV CONVERTER 180 Mc/s-205 Mc/s (Channels 6-13)

Suitable London, Birmingham, Northern, Scottish, Welsh and I.O.W. ITA transmissions.
Mk. 2 Model. Latest cascade circuit using ECC84 and EF80 valves giving improved sensitivity (18 dB) over standard circuits, built-in power supply a.c. 200-250V. Dimensions only 6 1/2" x 3" x 4". Simple and easy to fit—only external plug-in connections. Wired, aligned and tested ready for use. State channel required. Guaranteed. Bargain offer—good results or full refund. **ONLY £3.19.6** Carr. and pkg. 2/6
 Recommended Addition — Band I/ Band III changeover switch and B.B.C. aerial socket fitted and wired internal with converter 8/- extra.

7 VALVE AM/FM RADIOGRAM CHASSIS BARGAIN OFFER MANUFACTURERS SURPLUS
 Latest type ECC85 series valves with 3 watt EL84 Output Med., Long and V.H.F. Wavebands with Switched Gram Position. Magic Eye Tuning. Illuminated glass dial 1 1/2" x 3 3/8". 4 controls Chassis size 13 1/2" x 6 3/8" x 7 1/2" ht. A.C. 200/250V. Aligned and tested ready for use. Carr. **£13.10.0** and ins. 5/- Complete with 4 knobs—Walnut or Ivory to choice. P.M. Speakers only required, 8" 20/-, 10" 25/-.

TRANSISTORS—BVA 1st Grade
 Mazda XB102, XB104, each 10/-, XA103, 15/-, XA104, 18/-, G.E.C. GET3, 10/6, etc. OA81, 3/6, GEX34, 4/-, Mfrs. surplus (recommended and tested perfect). OC71, OC72, each 7/6. OC45 12/6, OA70 3/-.



RADIO COMPONENT SPECIALISTS

70 Brigstock Road Thornton Heath Surrey

Telephone THO 2188

Terms: C.W.O. or C.O.D. Post and packing up to 1/2 lb 7d., 1 lb 1/1, 3 lb 1/6, 5 lb 2/-, 10 lb 2/9

COAX 80 ohm CABLE—Stand. 1/4" diam.
 Low Loss Semi-Air Spaced AERAXIAL, polythene ins.
SPECIAL REDUCED PRICES
 20 yds 12/6, P. & P. 1/6; 40 yds 22/6, P. & P. 2/-;
 60 yds 32/6, P. & P. 3/- All other lengths 8d. yd.
 Coax Plugs 1/-, Coax Sockets 1/-, Couplers 1/3,
 Cable End Sockets 1/6, Outlet Boxes 4/6.

C.R.T. Heater Isolation Transformers

New improved types—mains prim. 200/250V
 tapped
 All isolation transformers now supplied with alternative no boost, plus 25%, and plus 50% boost taps, at no extra charge. All standard individual voltages available: 2V 2A-13V 0.3A (as previously advertised).

each **12/6** P. & P. 1/6.
 Small size and tag terminated for easy fitting.

LOUDSPEAKERS. P.M. 3 ohm, 2 1/2" Plessey, 17/6; 3 1/2" Goodmans, 18/6; 5" R. & A., 17/6; 6" Celes., 18/6; 7" x 4" Goodmans, 18/6; 8" Rola, 20/-; 10" R. & A., 25/-, 12" Plessey 30/-, etc.

SPEAKER FRET. Expanded bronze anodised metal: 8" x 8", 2/3; 12" x 8", 3/-; 12" x 12", 4/6; 12" x 16", 6/-; 24" x 12", 9/-, etc. TYGAN FRET (Contemp. pattern) 12" x 12", 2/-; 12" x 18", 3/-; 12" x 24", 4/-, etc.

VOLUME CONTROLS

Log. or lin. ratios, 10,000 ohms-2 Megohms. Long spindles. 1 year guarantee. Midget Ediswan type, 1 1/2" dia. No sw. 3/-, d.p. sw. 4/6.
TWIN GANGED CONTROLS. 1/2 Meg. 1/2 Meg. 1 Meg less sw., each 8/9.

PERDIO POCKET TRANSISTOR "6"

2 W/band Midget Portable. Printed circuit, 6 transistors and one xtal diode and stage by stage instruction manual. Complete Kit incl. **ONLY £9.19.6** P. & P. 2/6
 Cabinet and 2 1/2" Speaker.

CAR RADIO KIT. This popular Hybrid printed circuit 12V Car Radio as recently featured in The Radio Constructor is now available. **ONLY £12.19.6** P. & P. Complete Kit incl. Speaker 3/6
 Comprehensive Instruction Booklet, 3/6, (free with kit)

VALVES—NEW REDUCED PRICES. 1R5, 1T4, 7/6; 1S5, 7/6; 3S4, 3V4, 8/-; 5Z4, 9/6; DAF96, 9/-; DF96, 9/-; DK96, 9/-; DL96, 9/-; ECL80, 10/6; ECL82, 11/6; EF80, 9/6; EF86, 13/6; EF91, 8/6; EL84, 9/6; EY51, 10/-; EY86, 10/-; EZ80, 7/6; MU14, 9/6; PCC84, 10/6; PCF80, 10/6; PCF82, 10/6; PCL83, 12/6; PL81, 12/6; PL82, 9/6; PL83, 11/6; PY80, 7/6; PY81, 9/6; PY82, 7/6; U25 12/6, etc. send for list.

SPECIAL 1R5, 1T4, 1S5, 3S4 or 3V4 per set, 27/6, DK96, DF96, DAF96, DL96, 35/-, 6K8, 6K7, 6Q7, 6V6, 5Z4 or 6X5, 35/-.

Hours 9 a.m.-6 p.m., 1 p.m. Wed.

POCKET MULTIMETER

MODEL A10: 500 Micro-amp Movement.
 * AC/DC voltages, 2000 ohms per volt; 10, 50, 250, 500 and 1000 volts. * Resistance 10k ohms and 1 Megohm. * D.C. current 0.5 mA; 25 mA; 250 mA. * Decibel range. * DC \pm 2% accuracy; AC \pm 3%.
INCLUSIVE OF TEST PRODS, ILLUSTRATION BOOK AND BATTERIES £4-17-6
 Size $5\frac{1}{2} \times 3\frac{1}{2} \times 1\frac{1}{4}$ in. Weight 17 ozs. P.P. 1/6
BRAND NEW AND GUARANTEED
 Free Leaflet by Return

Bargain Offer 90 VOLT BATTERIES

Brand new 90 volt American Forces batteries tapped at 67 $\frac{1}{2}$; 45 and 22 $\frac{1}{2}$ volts.
IDEAL FOR VALVE PORTABLES 5/- P.P. 2/-
 Size $7\frac{1}{2} \times 4\frac{1}{2} \times 2\frac{1}{4}$ inch

373 MINIATURE I.F. STRIPS 9.72 MC/S



The ideal f.m. conversion unit as described in P.W., April/May 1957. Complete with 6 valves, three EF91s, two EF92s and one EB91. I.F.T.s, etc., in absolutely new condition. With circuit and conversion data.

12/6 (less valves) 37/6 (with valves)
 Postage and packing 2/6 (either type)

MARCONI CRYSTAL CALIBRATOR

For No. 19 Set
 10 kc/s, 100 kc/s and 1 mc/s xtal controlled osc. on/off modulator: 5-12SC7 valves: quartz crystal.
FULL HANDBOOK 79/6 P.P. 2/6

GLIDE PATH RECEIVER

Type AN/ARN-5D. 3-channel crystal controlled. Operating on 333.8; 332.6 and 335 mc/s. Input 24/28 volts D.C. Valves 28D7; 2-12SN7; 7-6AJ5; 12SR7 Relays, I.F.s, etc.
BRAND NEW 59/6 P.P. 5/-

Bargain Offer 8-DAY SMITHS CLOCKS

BRAND NEW IN SEALED CARTONS; 6-inch dial 8-day clocks with detachable adjustable time switch;
LIMITED QUANTITY ONLY 95/- P.P. 5/-

NEW FREE LISTS

- * Over 700 Different Valves and Tubes including Special Purpose Types and Metal Rectifiers.
- * 6 Pages of Transistors, Transistor Components and Data.
- * Over 500 Types of Quartz Crystals from 6 kc/s to 47 mc/s for all purposes.
- * New List of Surplus Units from Radar to Fuses, Transmitters to Condensers.
- * Descriptive Booklet on Do-It-Yourself Radios and Units.

ALL THESE LISTS ARE POST FREE

HENRY'S RADIO LTD · 5 HARROW ROAD · LONDON W2

Opposite Edgware Road Tube Station

(DEPT. RCSP)

Telephone PADDington 1008/9

RECORD CHANGERS

GARRARD 4-SPEED SINGLE PLAYER
 * GC2 Turnover Crystal Head. £6-19-6 P.P. 2/6
 * Brand New.
B.S.R. UA8 4-SPEED AUTO-CHANGER
 * Turnover Crystal Head. £6-19-6 P.P. 3/-
 * Plays Mixed Sizes.
 * Brand New.
B.S.R. UA8 4-SPEED AUTO-CHANGER
 * Turnover Crystal Head
 * Wired for Stereo
 * Up to 12 Records: Mixed Sizes £8-19-6 P.P. 3/-
 * Brand New
COLLARO Conquest 4-Speed AUTO-CHANGER
 * Turnover Crystal Pickup
 * Plays Mixed Sizes £7-19-6 P.P. 3/6
 * Brand New

Portable Gram Amplifier

* For use with crystal pickups. * Mounted on baffle board $12\frac{1}{2} \times 4\frac{1}{2}$. * Includes 7×4 inch LAC Speaker.
 * 2 Mullard valves: Output 2 watts. * Full volume and tone control.
JUST PLUG INTO MAINS AND 67/6 P.P. 2/6
 CONNECT PICKUP.

PACKARD-BELL PRE-AMP. Complete in screened case with 6SL7GT; 28D7 relay; leads, jack plug, etc. Handbook. Sealed in carton. ONLY **12/6 P.P. 2/-**

CRYSTAL CALIBRATOR NO. 10

Crystal controlled, coverage 500 kc/s to 10 mc/s: 1 c/s mod.; battery valves 2-IT4; IRS. **59/6 P.P. 3/6**
FULL HANDBOOK.

TRANSMITTER/RECEIVER

Army Type 17 Mk. II. Complete with Valves, High Resistance Headphones, Handmike and Instruction Book and circuit. Frequency Range 44.0 to 61 Mc/s. Range approximately 3 to 8 miles. Power requirements: Standard 120V h.t. and 2V I.t. Ideal for Civil Defence and communications.
BRAND NEW 45/- P.P. 5/-
 44-61 Mc/s calibrated wavemeter for same, 10/- extra

WALKIE/TALKIE

Type 38 Transmitter/Receiver. Complete with 5 valves. In new condition. These sets are sold without guarantee, but are serviceable. **22/6 P.P. 2/6**
 Headphones 7/6 pair, Junction Box, 2/6, Throat Mike 4/6, Canvas Bag 4/-, Aerial Rod 2/6.

To The Manager

HENRY'S RADIO LTD 5, HARROW ROAD, LONDON, W2

Please add my name to your list to receive all FREE lists available now and in the future, without obligation. Block capitals please

NAME

ADDRESS

RC1

MAJOR-3 (See page 112 this issue)

* 3 Ediswan Transistors. * 5-Stage Reflex Circuit.
 * Medium Wave Tuning. * No Aerial or Earth.
 * Size $4\frac{1}{2} \times 3 \times 1\frac{1}{2}$ in. * Min. Volume Control.
 Complete set of components including Ediswan Transistors and all items required. All parts available separately.
90/- post free

PRICES DOWN!! "THE TRANSISTOR-8" Combined Portable/Car Radio Push-Pull Portable Superhet

- * Tunable over medium and long wavebands
- * 250mW output push-pull
- * Internal Ferrite aerial
- * Highly sensitive and selective
- * 7" x 4" high flux speaker
- * All components identified and carded
- * EDISWAN transistors throughout
- * Easy-to-follow layout diagrams

Car radio components 8/-; A.V.C. 4/3; 325mW version now £11.11.6. P. & P. 2/6.

Size 9" x 7" x 3 $\frac{1}{2}$ ". Weight 4 lb.

NEW! SUPER-6 Six Transistor Medium & Long Wave Superhet

- * Plessey Printed Circuit
- * Mullard Transistors
- * 3-inch Speaker
- * Full Medium and Long Waves

* Size 7 x 4 $\frac{1}{2}$ x 2 in.

Recommended by us as being the easiest to build 6-Transistor printed circuit superhet receiver ever offered.
FREE LIST ON REQUEST

Complete set of parts including Rexine Covered Cabinet and all Components. ONLY **£9.19.6 P.P. 2/6**
 All parts sold separately

BARGAIN PARCEL

- * Perdio style moulded cabinet with gold trimmings (red, blue or cream) 12/6
- * J.B. 208+176pF screened gang 10/6
- * Miniature 2 $\frac{1}{2}$ " 3 ohm speaker 21/6
- * 20:1 output transformer to match 10/-
- * 5-transistor printed circuit 5/6
- * 5-transistor circuit diagram 1/-
- * Cabinet size 5 $\frac{1}{2}$ " x 3 $\frac{1}{2}$ " x 1 $\frac{1}{4}$ "

SPECIAL INCLUSIVE PRICE 55/- P.P. 2/-

All the above components are made to fit the cabinet and printed circuit. Other components for the radio available

AUDIO GENERATOR

Check audio circuits easily and quickly

- * Ediswan Transistor
- * Morse Practice Unit
- * Ideal Modulator
- * Size 2 $\frac{1}{4}$ " x 1 $\frac{3}{8}$ " x 1"

Ideal for morse practice unit (See August Issue)

P.P. 1/-

FREE DIAGRAM AND PRICE LIST


TRANSISTORS

FROM **5/- EACH**

Ediswan and Mullard Standard Range Transistor Prices Almost Halved.—SEND FOR NEW LISTS AND DATA

PRICES DOWN!! "THE TRANSISTOR-8" Combined Portable/Car Radio Push-Pull Portable Superhet

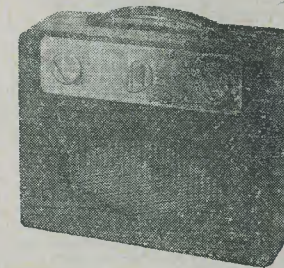Complete set of parts including cabinet and all components **Now £10.19.6 P. & P. 2/6**
 All parts sold separately.
FREE BOOKLET



MAJOR-2 (two-transistor pocket radio)

- * 4-stage reflex circuit
- * Tunable over medium waves
- * No aerial or earth
- * Over 6 months on one battery
- * Size 4 $\frac{1}{2}$ " x 3" x 1 $\frac{1}{4}$ "
- * Weight under 4 oz.
- * Layout diagrams

Complete set of components including 2 EDISWAN transistors, 72/6 post free. All components sold separately. **FREE NEW BOOKLET ON REQUEST**

CAR RADIO 2-watt Amplifier

A permanent power transistor stage complete with 7" x 4" speaker. May be used with any battery portable using a 3 ohm speaker. Use it with the "8"

Complete set of parts 65/- P.P. 2/6
 Unit built up and tested 77/7 P.P. 2/6
 All components available separately. Free diagrams and list

SIGNAL TRACER

RF, IF AND AUDIO TRACING

- * 2-Ediswan Transistors
- * New Chassis; Improved Design
- * Easy to Use; Small Size

A must for the Amateur and the Professional

Complete set of parts including headphones, transistors, etc. **37/6 P.P. 1/6**
FREE DIAGRAM ON REQUEST

HENRY'S RADIO LTD · 5 HARROW ROAD · LONDON W2

At junction of Edgware Road and Harrow Road

(DEPT. RCSP)

Telephone PADDington 1008/9

Heavy duty 500pF differential condensers 3/-. Small solid dielectric variables, 0.0001µF 3/-; 0.0003µF 3/9; 0.0005µF 4/-; Resistors from 3d. each. Assd. carbon (many 5%) for 3/11, 50 for 7/6 Hi-Stabs 10% 1/2 watt 6d.; 10% 1 watt 9d.; 1% 1/2 watt 2/-. Many odd values. Send requirements for quotation Ajax Crystal Set complete, 14/6; L.W. 15/-. Case and chassis 5/9. **Teleton HAX Coil 3/-. REP Dual Wave Xtal Coil 2/6. Germanium Diodes 1/-. Headphones, lightweight, 14/- and 16/-.** Nuts, bolts, washers, tags. Well assorted: 25 1/-, 72 2/9, 144 5/-. **Miniature Neons 1/10.** "Litesold" Miniature Soldering Iron, battery or mains, 21/6. Multicore Solder 4d. yd, 19ft reel 2/6, 1lb reel 14/9. Fine gauge for printed circuits, 40ft reel, 2/6. **Switches, s/p from 2/3, d/p from 3/6. Ferrite Rods 8" 2/-. 4" 1/6.** Mains neon indicators with built-in resistor. Domed top, chrome bezel, 1" long 1/2" diam. Opal, red, amber, 3/10; green 4/7. **Sub-miniature Electrolytics 8µF 6V, 16µF 12.5V, 32µF 3V, 5µF 12.5V 5µF 40V, 2.5µF 40V, 1.6µF 6V, 25µF 6V.** All 3/- each, 100µF 6V, 3/- Paper 0.01, 0.001, 0.002, 0.005µF, all 8d. each. **Transistor holders 1/- each, 6 for 5/9, 11/- doz.** **Ardente T.1065 transformers (page 911-**

July), 12/-.

Sub-miniature Speakers 1 1/2" round, 25/6; 2" x 3" elliptical, 30/6. **Sub-miniature Output Transformers, single-ended or p/p, 12/6.** **Subminiature Germanium Diodes 1/10.** **Volume Controls, button type (totally enclosed), 47k and 1MΩ, 2/6; preset skeleton type 5k, 2/6; spindle type 1/2M, 1M, 2M, 4/3 (page 705—May, '58)** **Ardente Deaf Aid Earpieces E.R.100, with cord and earpip. Limited number at 13/9.** **Ardente Catalogue 6d.**

Transistors: White Spot 14/-; Yellow/Green 7/6; Red Spot 7/-. Ediswan Transistors: XA104 R.F., 18/-; XA103 I.F., 15/-; XB104 A.F., XB102 A.F., 10/-. **Pye Goltp Transistors of all types stocked.**

THE TRANSIDYNE RECEIVER

Just right for holidays
This proved 6-transistor circuit now supplied with

NEW EDISWAN TRANSISTORS

(as specified by Teleton)

Complete Kit £11.15.6,
or less transistors £8.15.6
FREE—Special printed circuit solder with each kit

Only genuine Teleton parts. Full details and price list 1/- post free

Teleton "Tapejak" Price £5.9.0 (plus 1/6 post). **RF/AF Signal Tracer (Page 831 June issue).** Complete kit, with sub-miniature components and latest 2 1/2" plastic speaker (W.B.) £3.13.6. (S.A.E. for list) **COAXIAL OFFER.** High quality lead 6d. yd., 6yds 2/9, 12yds 5/-. **Sockets 1/-.** **Solderless plugs 1/3.** **Outlet Boxes, single 4/6, double 13/6.** **TRANSMITTING KEYS.** With lead and heavy duty jack plug 1/6 (1/3 post). **AMPLIFONE KIT.** All Telephone amplifier (R.C. March). All parts with 2 1/2" speaker £4.17.6. (S.A.E. list). **SENSITIVE TRANSISTOR RECEIVER (R.C. Nov. 1958).** Complete kit £4.18.9. (S.A.E. list). **VOLUME CONTROLS.** Long spindle, no switch 2/9; s/p 3/9; d/p 4/6. Most values. **MIDGET W/W PRESETS:** 1k, 2k, 3k, 3.5k, 5k, 10k, 20k, 25k. All at 2/9.

Alfa Multimeters—as reviewed on page 862 of June issue, 17 ranges, a.c./d.c., volts to 1,200; d.c. current to 300mA; resistance 0-2 Megohms. Price £6.19.6 plus 2/- post and packing. (Inclusive of batteries and test prods).

Microphone Cable: Black p.v.c. single screened: 3 yds 1/9, 6 yds, 3/- 12 yds 5/3. **Amplifone Kit:** Transistor Telephone Amplifier (R.C. March). All parts with 2 1/2" speaker (S.A.E. list).

QUOTATIONS gladly given (S.A.E. please)

R. FAGELSTON (MAIL ORDER)

Please add Postage to above prices

46 HARDWICKE ROAD · LONDON N13

SMALL ADVERTISEMENTS

Readers' small advertisements will be accepted at 3d. per word, including address, minimum charge 2/-. Trade advertisements will be accepted at 9d. per word, minimum charge 6/-. If a Box Number is required, an additional charge of 2/- will be made. Terms: Cash with order. All copy must be in hand by the 12th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the bona fides of advertisers.

PRIVATE

COSSOR double beam oscilloscope, £17; single beam oscilloscope, £8 10s.; Mullard R/C bridge, £5 10s o.n.o. All can be seen working.—Collier, 23 Dukas Avenue, Muswell Hill, London, N.10. Telephone TUDor 2552.

FOR SALE. 6-Transistor superhet portable, single-ended driving 5in. speaker, m/wave, £6 5s., post free.—Folds, "Maidwin", Lye Hill, Breachwood Green, Hitchin, Herts.

CLEARANCE. 100's electrically perfect bargains, carriage paid, s.a.e. queries. Examples, valves 1s. 6d. to 7s. 6d. Complete range Mullard 2V (new), scores Red "E", U.S.A., old British types. PM/MC speakers 6in. 12s. 6d., 8in. 15s. Higrade Williamson parts, exact specification. Pentode O/P transformers, 5s. and 2s. 6d. Exchanges, offers. Want *The Radio Constructor* prior January 1955, what have you?—48 Victoria Road, Torquay.

I.T.V. CONVERTERS Aerialite, Sterling, 50s. G.E.C., Philips, etc. 40s. Tubes, 9in. C9B 25s.; 12in. MW31/74 30s.; 14in. MW3624 30s. L.O.transformers, VT59DA, etc. Cossor 925 40s. Microamp meters 10, 250/250, 500/500, 15s. each, post paid.—O. D. Busscher, 25 Ramshead Approach, Leeds 14.

TAYLOR 77A MULTIMETER 50µA movement, new and unused. £9. 350 magazines, *The Radio Constructor*, *Wireless World*, *Practical Television*, *Practical Wireless*, offers for all or part.—94 Blenheim Road, Deal, Kent.

AMATEUR SELLING UP Components, testgear, hi-fi, etc. s.a.e. for lists.—36 Farleigh Road, Newhaw, Weybridge, Surrey

FOR SALE. Cossor 1044K valve voltmeter, complete. Perfect order on all ranges, nearly new, £14.—G. Badman, Long Crendon School, Sheringham, Norfolk. Telephone 502.

JUNK SALE. 6d. upwards, callers only. Dumont 'scope, AVO valve tester, perfect, offers? Consider exchanges model railways.—Peuleve, 17 Mount Road, New Malden, Surrey.

MORSE CODE TAPE RECORDER (undulator) type UG9, 230V a.c. variable speed, unused, £10. Ditto but without tape pulling mechanism, £2. Morse code keyboard perforator for perforating paper tape and sending morse, typewriter keyboard, £10. Would suit Radio School or Club. Transmitting unit for above, £5. Type 3A teleprinter, £5. All plus carriage.—Box No. E 214.

NEW SURPLUS . . . BY RETURN

1L4	5/-	6SA7M	7/6	1616	5/-	EZ80	7/6
1R5	6/6	6SG7M	6/6	1629	4/-	EZ81	8/-
1S5	6/6	6SH7M	5/-	5763	10/6	GT1C	7/6
1T4	5/-	6SJ7M	7/6	DC70	7/6	GK32	12/6
2A3	8/6	6SK7M	6/6	DL70	7/6	HK24G	25/-
2X2	3/6	6SN7GT	4/6	EA50	1/6	KT33C	8/6
3A4	4/6	6SQ7M	7/6	EABC80	1/6	OAC2	10/-
3A5	12/6	6ST7	8/6	EAC91	4/6	PCA84	9/6
3Q4	6/6	6V6G	7/6	EAF42	9/-	PCC85	9/-
3S4	8/6	6X4	6/-	EB34	2/-	PCF80	9/-
3V4	8/6	6X5GT	6/6	EB91	4/-	PCF82	9/6
5R4GY	9/6	7B7	8/6	EBC33	7/6	PLB82	11/-
5Y3GT	7/6	7C5	8/-	EBC41	8/6	PL81	13/6
6AC7M	5/-	7C6	8/-	EBF80	9/-	PL82	9/6
6AG5	3/6	7S7	9/6	EBF89	9/6	PL83	9/6
6AK5	5/-	7Y4	8/-	EC80	12/6	PY80	8/6
6AL5	4/-	12A6M	6/6	ECC82	8/6	PY81	8/6
6AM6	4/-	12AT6	8/6	ECC83	8/6	PY82	8/6
6AQ5	8/6	12AT7	8/6	ECC84	9/6	PY83	8/6
6AT6	7/6	12AU7	8/6	ECC85	9/-	TT11	4/-
6AU6	7/6	12AX7	8/6	ECCF80	12/6	U25	12/6
6B8G	3/6	12AU6	9/6	ECH42	9/-	UAF41	9/6
6BA6	7/6	12BE6	8/6	ECH41	10/-	UBC41	9/6
6BE6	7/6	12C8M	7/6	ECH81	10/-	UBF89	9/6
6BH6	7/6	12K7GT	6/6	ECL80	10/6	UCC85	9/6
6B3E	7/6	12K8M	12/6	ECL82	12/6	UCH42	9/6
6BR7	11/6	12Q7GT	6/6	EF36	4/-	UCH81	9/6
6BW6	9/-	12SC7M	2/6	EF39	4/6	UF41	9/6
6C4	4/-	12SJ7M	5/-	EF41	9/6	UF42	8/6
6F32	6/6	12SK7M	5/-	EF50	2/6	UF89	9/6
6F3T	5/6	12SQ7M	8/6	EF50(S)	4/-	UL41	9/6
6J5GT	4/6	35L6GT	9/6	EF80	7/6	UL84	9/6
6J5M	5/-	35Z5GT	8/6	EF85	9/6	UY41	8/-
6J6	4/-	35Z4GT	7/6	EF86	13/6	UY85	8/6
6J7G	7/6	42	7/6	EF89	9/-	UABC80	10/6
6K7G	3/6	50L6GT	9/6	EF91	4/-	VLS631	12/6
6K8G	6/6	80	6/6	EL32	4/-	VR150/30	10/6
6K8M	10/6	446A	10/6	EL41	9/6	VLS631	12/6
6H6M	2/6	801A	7/6	EL84	9/-	VR150/30	10/6
6L6G	8/-	803	2/6	EM80	9/6	VS70	3/-
6L6M	10/6	830B	15/-	EY51	12/6	Z77	4/-
6Q7G	7/6	866A	15/-	EY86	11/6		
6Q7GT	9/6	959	5/-	EZ40	7/6		

M.C. Meters. 2 1/2" rd. fl. (2" dial), 0-1mA, 21/- Ditto but scaled 0-30V, 13/6. 0-500µA, 17/6. 2 1/2" rd. plug in electrostatic 0-1,500V, 16/6. 2" sq. fl. 0-300V, 50-0-50A, 11/6. 0-50mA, 9/6.

Parmeko Mains Trans. Input tapped 200/250V, O/p. 750-630-0-630-750V. 96mA (ok for 140mA), 6.3V 2A, 4V ct. 3A. Wt. 9lb., 32/6 each, post paid.

Acos Stick Mikes. MIC39-1. List price £5.5.0. Few only new boxed less stand, 55/- MIC33-1 (list 50/-), our price 32/6.

Transistors. Audio, yellow/green, 6/6; yellow red r.f. to 8 Mc/s, 12/6.

Resistors 1/2 watt ins. Ass. pkts. of 50. Minimum 15 values mostly 10% between 100Ω and 820k, 5/6. Pkts. of 100 (min. 30 values), 10/6.

Valveholders, moulded. B7G, B8A, B9A, I.O., 9d. each, 7/6 doz; B7G Pffe, B9A Micalex, 1/- each, 10/6 doz; screened B7G, B9A, 1/6 each, 15/- doz; B9A Micalex, 1/9 each, 18/- doz. B9A Cer. 2/6 each, 24/- doz. Special prices large quantities.

SPECIAL OFFER OF VALVES IN £1 PARCELS
(plus 2/6 p/p per parcel irrespective of total value of order)

1A3, EA50, 12SC7M, 16 for £1.
2X2, 6AG5, 6B8G, 6H6M, EB34, EF50, 1626, 12J5GT, 6K7G, EL32, TT11, 12 for £1.

6ACT, 6I6, 1616, 1629 EF50(S), EAC91, 12SJ7, 12SK7, 8 for £1.

801A, 1625, 6SN7GT, 6F32, 5 for £1.
6K8G, 12A6, 12K7GT, 12Q7GT, 35Z4GT, 3Q4, 6BH6, 4 for £1.

Fully shrouded Chokes (U.S.A.) 10H 100mA 9/6. Post 9d. to £1, 1/6 to £2. S.A.E. enquiries

JOHN ANGLIN
385 CLEETHORPE ROAD GRIMSBY Lincs
Telephone 56315

continued on page 151

Get these
FREE
CIRCUITS
&
WIRING DIAGRAMS

T.R.F. Circuits Mains Circuits Send
Battery Circuits Filter Circuits 1/-
Portable Circuits TV Converter Circuits (stamps)
Sheet Circuits etc. etc.

OSMOR COILS are regularly used and recommended by designers writing in "Practical Wireless," "Wireless World" and "Radio Constructor." Why not follow the experts?

"Q COILS" All ranges • POTTED COILS • FM COILS
SPEAKER CROSS-OVER COILS
TAPE COILS • ROD AERIALS
SUB-MINIATURE COILS

COILS and I.F.s for Transistor Circuits • MIDGET I.F. TRANS With ferrite cores

OSMOR
418 Brighton Road
South Croydon
Telephone CRO 5148/9

Radio Control Mechanisms

by
RAYMOND F. STOCK

The first publication devoted entirely to the subject of radio control linkage mechanisms. Complementary to *Radio Control for Model Ships, Boats and Aircraft* and to other books on radio control.

64 PAGES PLASTIC ART BOARD COVER
70 ILLUSTRATIONS

2nd Printing 4s. 6d. plus 4d. postage

DATA PUBLICATIONS LTD
57 MAIDA VALE LONDON W9




Specialists in Equipment for Home Construction (Send stamp for complete list)

ALL POST ORDERS AND CORRESPONDENCE TO
162 HOLLOWAY ROAD · LONDON N7
NOR 6295/6/7

18 TOTTENHAM COURT RD. LONDON W1
MUS 5929/0095
Callers welcome at both branches

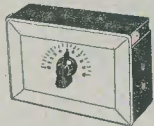OUR NEW SUPER TRANSISTOR CRYSTAL RECEIVER



Employing special NEW SUPER SENSITIVE circuit and incorporating built-in Ferrite Aerial. For use with headphones or deaf-aid type earpiece. Housed in attractive ivory and black plastic case measuring only 4½" x 2½" x 1½". Very simple to construct. Most economical to run. (Pen torch type battery lasts for months.) Completely safe. No external Aerial or Earth required. Excellent quality reception on Medium Waveband. Fully comprehensive, easy to follow, practical and theoretical instructions provided. **Special Price for all required components (inc. battery) only 30/- plus 2/- P. & P.**


Deaf-aid type earpiece available separately complete with lead at 12/6, or DLR5 headphones at 7/6 per pair.

Full details and assembly instructions can be supplied separately if required at 1/- post free.

E.M.I. 4-SPEED STEREO SINGLE RECORD UNIT, complete with Stereo Head and Sapphire Stylus. Brand New and Full G'teed. ONLY £6.19.6 plus 3/6 P. & P. whilst stocks last.

EXTRA SPECIAL OFFER!!

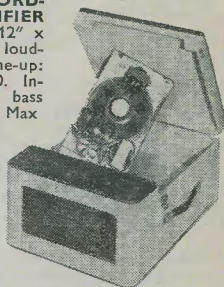A small three-valve **PORTABLE RECORD-PLAYER AMPLIFIER** mounted on baffle 12" x 7" with high flux 6½" loud-speaker. Valve line-up: ECC83, EL84, EZ80. Incorporates separate bass and treble controls. Max output 3 watts. Will match all types of high impedance pick-ups. Ready to use, £5.12.6 plus 3/6 P. & P.



NEW STYLE CABINET finished in two-tone Leatherette. Will accommodate above Amplifier and Baffle without modification, also most types of Ancillary Equipment. Overall size 18" x 13½" x 8½". Fitted with carrying handle. £3.9.6 plus 5/- P. & P. **NOTE.** If both items purchased together they will be supplied at a special inclusive price of £8.7.6 plus 6/6 P. & P.

SMALL ADVERTISEMENTS

continued from page 149

PRIVATE—continued

PORTABLE RECEIVER. Medium and long wave, battery/mains—just plug in, new battery, perfect working order, just over 12 months old, ferrite aerial, recently re-aligned. commercial model, red plastic case, ideal car radio etc., £8 carriage paid, guaranteed.—S. J. Hinckley, 29 Bradfields Avenue, Chatham, Kent

WANTED. Manuals, Service Instructions, etc, British or American teleprinters and associated equipments. State price required.—Hon. Secretary, British Amateur Radio Teletype Group, "East Keal", Romany Road, Oulton Broad, Lowestoft, Suffolk.

WANTED. Circuit and operating manual for Eddy-stone 358X receiver. Will offer four brand new television valves of your own choice in exchange.—M. Higgs, 33 Velsheda Road, Shirley, Solihull, Warks.

WANTED. Back numbers of *The Radio Constructor*, will exchange copies of *Short Wave Magazine*.—31 Franklin Road, Birmingham 30.

TRADE

CATALOGUE No. 14. Government surplus and model radio control, over 500 illustrated items. Price 1s. 8d., postage 4d.—Arthur Sallis Radio Control Ltd., 93E North Road, Brighton.

JOIN THE INTERNATIONAL S.W. LEAGUE. Free Services to members including Q.S.L. Bureau, Amateur and Broadcast Translation. Technical and Identification Dept.—both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, "MONITOR" containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes. QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership, including monthly magazine, etc., 21s. per annum.—Secretary, ISWL, 86 Barrenger Road, London, N.10.

AT LAST—at a reasonable cost—quality Hi-Fi in your home by building it yourself under our new system. **FREE** Brochure from: Dept. RC21, Radiostructor, 46 Market Place, Reading, Berks.

LEARN RADIO AND ELECTRONICS the NEW Practical Way. Very latest system of experimenting with and building radio apparatus—"as you learn." **FREE** Brochure from: Dept. RC10 Radiostructor, 46 Market Place, Reading, Berks.

SERVICE SHEETS from 1/- each, 100 TV Sheets, 18/6. Cheap Valves, Components, lists free. Hamilton Radio, 237 Sedlescombe Road North, Hastings, Sussex.

THOUSANDS OF SPARES, transformers, coils, valves, tubes, cheap from dismantled Radio, Television sets, 1938-1958. 9in-10in projection tubes, 30s.; 12in-14in, £3 10s.; 17in, £5. All guaranteed Picture Tested! EF80, EF91, EB91, 3s. 6d., EF50, 2s. 6d. Obsolete sets our speciality. Write, 'phone, call—"St. John's Radio," 156 St. John's Hill, S.W.11. BATtersea 9838.

MORSE CODE TRAINING. Special course for Beginners. Full details from (Dept. R.C.) Candle System Company, 52 Abingdon Road, London, W. 8.

PANL, recognised for many years as the unique one-coat black crackle finish. Brush applied, no baking. Available by post in ¼th pint cans at 3s. 9d. from G. A. Miller, 255 Nether Street, London, N.3.

"WORLD RADIO HANDBOOK." Copies available. 15s. 6d. inc. post and packing, from ISWL, 86 Barrenger Road, London, N.10.

1,000 INTERESTING ITEMS. List 3d.—Rogers, 31/33 Nelson Street, Southport, Lancs.

TECHNICAL WRITING IN ELECTRONICS, Radio and TV Instruction Books, Service Manuals, Brochures, Technical Drawings etc.—F. C. Judd, A.Inst.E., Rotech, 152 Maybank Road, London, E.18. Telephone BUCKhurst 9315.

HIGH CLASS DUPLICATING, Electronic Stencil Illustrations, circuits, etc. Sheets or booklets.—Rotech, 152 Maybank Road, London E.18. Telephone BUCKhurst 9315.

ALUMINIUM CHASSIS, brackets, accessories, component potting and circuit printing. Send for catalogue.—25 Leach Street, Prestwich, Manchester.

INCORPORATED Practical Radio Engineers home study courses of radio and TV engineering are recognised by the trade as outstanding and authoritative. Moderate fees to a limited number of students only. Syllabus of Instructional Text is free. *The Practical Radio Engineer*, journal, sample copy 2s. 6,000 Alignment Peaks for Superhets, 5s. 9d. Membership and Entry Conditions booklet, 1s., all post free from the Secretary, I.P.R.E., 20 Fairfield Road, London, N.8.

SMALL ADVERTISEMENTS

Readers' small advertisements will be accepted at 3d. per word, including address, minimum charge 2/-. Trade advertisements will be accepted at 9d. per word, minimum charge 6/-. If a Box Number is required, an additional charge of 2/- will be made. Terms: Cash with order. All copy must be in hand by the 12th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the bona fides of advertisers.

PP COMPONENTS LTD.

219 ILFORD LANE
ILFORD ESSEX Telephone ILFord 0295
Stamp for Catalogue—FREE

AUTUMN ATTRACTIONS

- ★ **BATTERY RECORD PLAYER 99/6.** 6 or 9V, 4 speed, P. & P. 4/6.
 - ★ **VALVE BATTERY AMPLIFIER 39/6.** 1.5V l.t. 60 or 90V h.t. Suitable for above. P. & P. 3/6.
 - ★ **3-TRANSISTOR AMPLIFIER 79/6.** Ideal for use with above player. 9V. P. & P. 3/6.
 - ★ **SPEAKERS 12/6.** Round 6½in. std. matching. 2-5 ohms. P. & P. 2/6.
 - ★ **ELLIPTICAL SPEAKERS 19/6.** 2 sizes. 7in x 4in or Bin x 5in. P. & P. 2/6.
- 8in P.M. SPEAKERS 5/9. Limited quantity Tested and guaranteed, Have a slight cone repair. Not affecting the quality. P. & P. 2/9; on 2, 3/6.

FOR THE RADIO ENTHUSIAST

- FOCUS MAGNETS 9/9.** Brand new 38mm. Incorporating picture shift control. P. & P. 1/3.
- ELAC FOCUS MAGNET 12/9.** New. 35/38mm. P. & P. 1/3.
- 17in TV MASKS 7/9.** White plastic. P. & P. 2/3.
- TUNING CONDENSERS 2/6.** New 2-gang. Std. size. P. & P. 1/3.
- INSULATING TAPE 1/6.** Good quality. 75ft x ½in wide, in sealed metal tin. P. & P. 9d.

TV AERIALS 7/9. Fitted with 9ft co-ax cable. For door rod or loft P. & P. 1/3.

TV AERIALS 15/6. Indoor type. Folded dipole with 12ft co-ax fitted. P. & P. 1/9.

CAR AERIAL 6/9. Cadmium plated whip antenna 50in long, collapsing to 11in. One-hole fixing. P. & P. 1/- (not telescopic).

MAINS TRANS 0/0. 300-0-300V 80mA. 4V at 5A, 4V at 2A. Drop thro' type, half-shrouded. Prim. 200/250V. P. & P. 3/9.

MAINS TRANS. 3/9. 350-0-350V 80mA. 4V at 5A, 4V at 5A. Prim. 200/250V. P. & P. 3/-.

HEATER TRANS. 1/9. 4V to 6V at 3A. Ideal auto trans. P. & P. 1/-.

O.P. TRANS. 1/3. Std. size 2-5 ohms. P. & P. 1/- 20 for £1, P. & P. 3/6.

VOLUME CONTROLS 2/6 doz. Mixed parcel of volume and tone controls from working chassis. P. & P. 2/-.

CO-AX CABLE 6d. yd. Good quality, cut to any length. P. & P. on 20 yds 1/6. 45/- per 100 yds. P. & P. 3/6.

COIL PACK SETS 3/9. Including pair 465 i.fs. 2-gang cond. 3 w/band. P. & P. 2/3.

PRESS BUTTON COIL PACK 10/6. 3 w/band. F.M. and gram. P. & P. 1/6.

S/VISION STRIP 2/9. S/het. Takes 6 EF91, 6D2 and 6F14. P. & P. 2/6. less valves.

PLESSEY S/V 4/9. P. & P. 2/6.

TIMEBASE 2/9. Including line trans., scanning coils and focus unit. P. & P. 3/6

TV SLIDER CONTROLS 5/-. 5 on a panel. Complete with knobs. P. & P. 1/-.

TRANSFORMERS

Suppliers to B.B.C., I.T.A. and leading radio manufacturers, single or long runs, prompt delivery, home and export,

rewinds to all makes

H. W. FORREST (TRANSFORMERS) LTD.,
Shirley, Solihull, Warwickshire.
Telephone: Shirley 2483

**BRASS, COPPER, DURAL,
ALUMINIUM, BRONZE**
ROD BAR SHEET TUBE STRIP WIRE
3,000 STANDARD STOCK SIZES
No quantity too small List an application

H. ROLLET & CO LTD
6 Chesham Place SW1 SLOane 3463
Also at Liverpool Birmingham
Manchester Leeds

Teleprinters, Perforators, Reperforators, Tape Readers, Terminals and V.F. Telegraph multi-channel units: Testing Equipment; Telephone Carriers and Repeaters; Signalling Rectifiers and Relays, Transformers, Transmit and Receive, Filters; Repeating and Retardation Coils; Racks, Relay Bases, Remote control transmitters; British, American, Italian and German Equipment.

BATEY & CO.,
Gaiety Works Akeman Street Tring Herts
Telephone Tring 2183 and 2310

B. B. C. - I. T. V. - F. M. AERIALS

B.B.C. (BAND 1). Telescopic loft, 19/6. External, S/D, 26/3.
I.T.V. (BAND 3). 3 Element loft array, 24/-, 5 Element, 32/6. Wall mounting, 3 Element, 33/9. 5 Element, 41/3.

COMBINED B.B.C. + I.T.V.
Loft 1+3 Element, 41/3. 1+5 Element, 48/9. Wall mounting, 1+3 Element, 56/3. 1+5 Element 63/9. Chimney and mast mounting units also available.

F.M. (BAND 2). Loft "H", 28/-. 3 Element loft, 52/6. S/D loft, 12/6. External S/D, 26/3. State channel when ordering. C.W.O. or C.O.D. P.P. 2/6. Coaxial cable, 8d. yd. Coaxial plugs, 1/3.

K. V. A. ELECTRONICS (Dept. RC)
38 Godstone Road Kenley Surrey

H.A.C. THE ORIGINAL SUPPLIERS OF SHORT-WAVE KITS

One valve Super Sensitive All-dry Short-wave Receiver Model "K" Complete kit including valve and chassis 77/- (Other S.W. kits from 25/-) Before ordering call and inspect a demonstration receiver, or send stamped envelope for full specification, catalogue and order form

H.A.C. SHORT-WAVE PRODUCTS (DEPT. R)
11 OLD BOND STREET LONDON W1

"GLOBE-KING"

WORLD-FAMOUS KITS AND RECEIVERS for the Radio Amateur and S.W. Listener. Catalogue Free, enclose stamp for postage. Kits from 79/6 obtainable at your dealers or direct from sole manufacturers

JOHNSONS (Radio)
ST. MARTINS GATE - WORCESTER

Sub-Miniature Soldering Instruments

New Ultra Lightweight Design. Only 1/2 oz. 6 volt 9 watt. 10/9 post free, or complete with transformer for a.c. mains 14/6 plus 1/9 p. & p.

KENNETT AND COMPANY
23 Leylands Grove · Bradford 9 · Yorkshire
Trade enquiries invited

PETHERICK'S RADIO SUPPLIES

Dept. R.C.
22 HIGH STREET BIDEFORD N. DEVON

Transistors Red Spot 6/9, Yellow/Green 6/9, White Spot 10/6, Red/Yellow 14/-, Practical Transistor Receivers, Book 1, 5/-, Crystal Diodes 1/- each, 10/- doz.; GEX 34s 4/- each. DRR2 Coils for BBC Transistor set, etc., with Circuits 4/-, Crystal Set Coils with Circuits M.L. 2/6. Vari-Loopstick Coils MW with Transistor Circuit 4/6. Reaction Condensers 0.0003 and 0.0005µF 4/- each. Headphones Lightweight for Crystal sets, etc., 14/- pr. Type CLR Headphones 8/6 pr. Metal Rectifiers 280 volt 80mA 5/6 each. Contact Cooled Rectifiers 240 volt 50mA 7/6. T.R.F. Coils M.L. with Circuits, 8/- pr. ALL SENT POST FREE IN U.K. Let us quote you for your requirements. S.A.E. Please.

THE RADIO CONSTRUCTOR BOUND VOLUMES

Attractively bound in blue cloth, with gold-blocked spine

Vol. 11, August 57 to July 58 £1.5.0, postage 1/9

Vol. 12, August 58 to July 59 £1.5.0, postage 1/9
(available October)

Where readers return all issues of a volume for exchange, the price is 12/6, plus postage 1/9

Please note:—we regret that we can no longer undertake to bind readers' own copies. (Many newsagents can arrange for books to be bound, and/or sell self-binding kits.)

DATA PUBLICATIONS LTD 57 MAIDA VALE LONDON W9

**INTEREST
is at 3 3/4%
per annum**

(There is no deduction for income tax, as this is paid by the Society)



ESTABLISHED 1865

Savings in this old established Building Society combine sound investment with an attractive return

The Duchess of Kent Permanent Building Society

Shares are in units of £25 each (maximum investment £5,000) . . . BUT, for the smaller saver, Subscription Share accounts may be opened with any sum from 1/- upwards. Interest is payable half-yearly on Fully Paid Shares—credited annually on Subscription Shares—all interest accrues monthly.

To Mr. A. Neville Gillman, F.C.A.
Duchess of Kent Permanent Building Society 103 Cannon Street London EC4

Please send to me, without obligation, free brochure and a copy of the audited statement of accounts. (I understand that I shall not be troubled with circulars or calls by representatives)

Name

(If lady, please state Mrs. or Miss)

Address..... R.C.

(Please use Block Capitals for both name and address)

SELRAY PUBLISHING & DISTRIBUTING CO

specialists in RADIO AND ALLIED PUBLICATIONS

- Foundations of Wireless. By M. G. Scroggie. 15s. Postage 1s. 3d.
- The Grundig Book. By F. Purvis. 12s. 6d. Postage 9d.
- All In One Tape Recorder. By J. M. Lloyd. 12s. 6d. Postage 9d.
- Television Servicing. By G. N. Patchett. Vol. 1, 5s. Vol. 2, 6s. Vol. 3, 5s. Vol. 4, 7s. 6d. Postage 5d. each.
- Radio Servicing. 4 vols. 5s. each. Postage 4d. each
Vol. 1: Basic Electrotechnology. By G. N. Patchett
Vol. 2: Intermediate Radio Theory. By G. N. Patchett
Vol. 3: Final Year Radio Theory. By B. Fozard
Vol. 4: Fault Finding. By G. N. Patchett
- Transistor and Crystal Diodes. By B. R. Bettridge. 5s. Postage 4d.
- Electronic Novelties for the Constructor. By E. N. Bradley. 5s. Postage 4d.
- Radio Control of Models. By G. Sommerhoff. 5s. Postage 4d.
- Practical Hi-Fi Handbook. Gordon J. King. 224 pages. 200 illustrations. 25s. Postage 1s. 6d.
- Radio Circuits. W. E. Miller. Revised by E. A. W. Spreadbury. 4th Edition. 15s. Postage 10d.
- British Transistor Manual. E. N. Bradley. 224 pages. 200 diagrams. 12s. 6d. Postage 9d.
- Transistor Circuits for the Constructor. Nos. 1 and 2. E. N. Bradley. 3s. 6d. each. Postage 4d.

Over 25 Years of Knowledge and Experience in Technical Publications at your disposal
60 HAYES HILL · HAYES · BROMLEY · KENT · Telephone HURstway 1818