

PUBLISHED IN CONJUNCTION WITH  
THE  
**RADIO CONSTRUCTOR**

★ *Data Book Series*

★ *Radio Reprint Series*

★ *Panel Signs Transfers*

Send stamped addressed envelope for  
latest

**BROCHURE**

giving details of ALL PUBLICATIONS

**DATA PUBLICATIONS LTD**

57 MAIDA VALE LONDON W9

Telegrams Databux London

Telephone CUNningham 6141/2

Published in Great Britain by the Proprietors and Publishers  
Data Publications Ltd 57 Maida Vale London W9

Printed by A. Quick & Co. (Printers) Ltd 125 High Holborn London WC1 England also at Clacton-on-Sea  
Obtainable abroad through the following Collets Subscription Service Continental Publishers & Distributors Ltd  
William Dawson & Sons Ltd Australia and New Zealand Gordon & Gotch Ltd South Africa Central News Agency  
Holland "Radio Electronica"

Registered for transmission by Magazine Post to Canada (including Newfoundland)

152  
LOW-POWER TRANSMITTER MODULATOR

The  
**RADIO  
Constructor**




VOLUME 14  
NUMBER 1  
AUGUST  
1960

RADIO · TELEVISION · AUDIO · ELECTRONICS

A PORTABLE  
OSCILLOSCOPE

The  
HEATHKIT  
0 S.1

by  
G. J. Stone

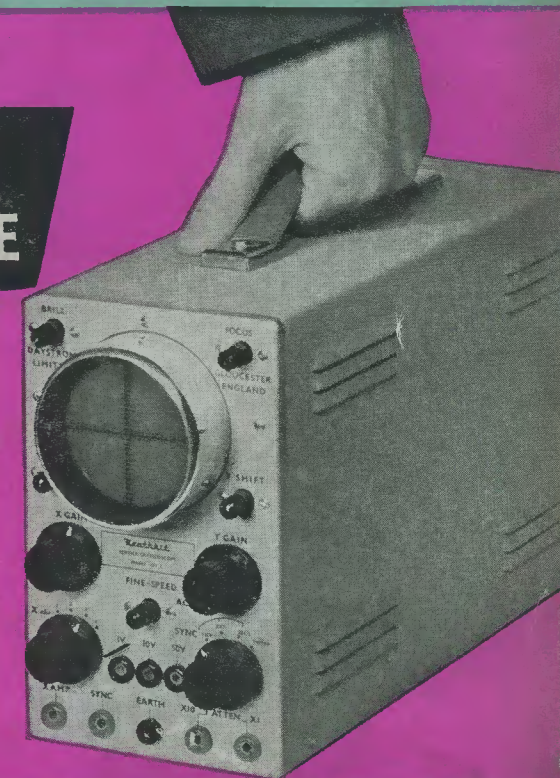

Included in this issue


TOUCH-PLATE OR PROXIMITY DETECTOR  
HIGH SENSITIVITY SHORTED TURNS TESTER  
ALTERNATIVE BAND III PRE-AMPLIFIER  
A PHOTO-TRANSISTOR SWITCH  
WINDING COILS AND SMALL CHOKES

**DATA  
Publications 19**



**Mullard**

## CIRCUITS FOR AUDIO AMPLIFIERS

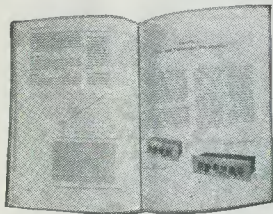

**-a book every enthusiast will want!**

This new Mullard publication is a practical manual for every audio enthusiast. In addition to describing twelve of the most popular Mullard circuits, it has introductory chapters on many of the theoretical and

aspects of high quality sound reproduction.

Whether you are interested in disc or tape, monaural or stereo, you will find that "Circuits for Audio Amplifiers" gives just the sort of information you need.

This informative book costs only 8/6d. The demand for it is high, so get your copy now from your local radio dealer.



MULLARD LTD · MULLARD HOUSE · TORRINGTON PLACE · LONDON · W.C.1  
MVM 422A

*Technical  
training  
in radio  
television  
and  
electronics  
engineering  
with*

The decision is YOURS. To be a success in your chosen career; to qualify for the highest paid job . . . to control a profitable business of your own. ICS home-study courses put your plans on a practical basis; teach you theory and practice; give you the knowledge and experience to take you, at your own pace, to the top.

Choose the **RIGHT** course,


RADIO AND TELEVISION ENGINEERING · INDUSTRIAL TELEVISION · RADIO AND TV SERVICING · RADIO SERVICE AND SALES · ELECTRONICS · VHF/FM ENGINEERING · COMPUTERS AND PROGRAMMING

ICS provides thorough coaching for professional examinations: A M BRIT. I R E, City and Guilds Telecommunications, C. & G. Radio and TV Servicing, C. & G. Radio Amateurs.
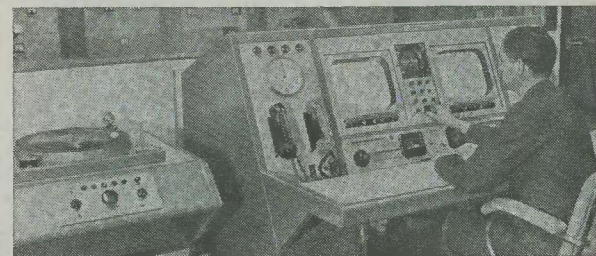
### LEARN AS YOU BUILD

*Practical Radio Course*

Gain a sound up-to-professional-standards knowledge of Radio and Television as you build your own 4 valve T R F and 5 valve superhet radio receivers, signal generator and high-quality multi-tester. At the end of the course you have three pieces of permanent and practical equipment and a fund of personal knowledge and skill . . . ICS Practical Radio courses open a new world to the keen radio amateur.



**THERE ARE ICS COURSES TO MEET YOUR NEEDS AT EVERY STAGE OF YOUR CAREER.**

Post this coupon today: In return you will receive the FREE 60-page ICS Prospectus listing technical examinations and their appropriate ICS courses PLUS details of over 150 specialised subjects.

Other ICS courses include: MECHANICAL, MOTOR, FIRE, CHEMICAL, ELECTRICAL AND CIVIL ENGINEERING, ETC. SELLING AND MANAGEMENT, ARCHITECTURE, WOODWORKING, FARMING, GARDENING, ART, PHOTOGRAPHY.

Please state subject on coupon

# ICS

#### INTERNATIONAL CORRESPONDENCE SCHOOL

(Dept. 248) Intertext House Parkgate Road London SW11

NAME ..... AGE .....

ADDRESS .....

OCCUPATION .....

SUBJECT .....

SUBJECT ..... 8.60

AUGUST 1960

See the whole



range at **STAND 112**  
**RADIO SHOW**


For the Discerning who require  
the Best Performance at Minimum Price

**HI-FI FM TUNER**



This model is available as two units which, for your convenience, are sold separately. They comprise a Tuner Unit, Model FMT-4U (£32.0 including Purchase Tax) with I.F. output of 10.7 mc/s and an Amplifier Unit complete with attractively styled cabinet, power supply and valves. Model FMA-4U (£10.10.6) making a total cost for the equipment of £13.12.6.

**AMATEUR TRANSMITTER Model DX-100U**

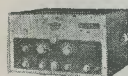


This is the most popular Amateur transmitter in the world and requires no introduction to "Hams" the world over. Covers all bands from 160-10 metres. Self-contained, including power supply, Modulator and V.F.O. £78.10.0

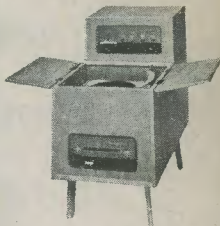
**THE "CHEPSTOW".**

This cabinet has specially been developed for those who require to house their equipment in as small a floor area as possible. Overall dimensions are 35" x 18" x 33" high.

It will accommodate Record Player, FM Tuner, Stereo Amplifier and where a Stereo Control Unit is used, one or more power amplifiers as well. An upper deck is available for the self-powered stereo amplifiers to ensure maximum heat dissipation. Left in the white, veneered for finishing to personal taste. £10.10.0



**TRANSCRIPTION RECORD PLAYER**

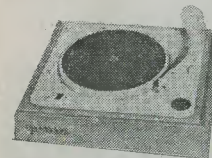

**TRANSCRIPTION RECORD PLAYER, Model RP-1U.** This new RP594 Collaro Transcription Unit has a Ronette Stereo Pick-up, giving excellent results on stereo or mono (33, 45, or 78 r.p.m.) discs. Complete with furniture-grade wooden plinth. £12.10.0

The "GLOUCESTER". It will house Tape Deck and/or Record Player—as well as FM Tuner and Stereo Amplifier, and storage space is provided for records, tapes and power amplifiers. Furthermore to meet the needs of those with whom room-space is an overriding consideration, provision is made in the cabinet ends for matched Hi-Fi Stereo Speaker Systems.


- Mk. 1. Tape Deck or Record Player. £15.18.6
- Mk. 2. Tape Deck and Record Player. £17.8.6



THE "COTSWOLD"


**THE "COTSWOLD".** This is an acoustically designed enclosure 26" x 23" x 15½" housing a 12" bass speaker with 2" speech coil, elliptical middle speaker together with a pressure unit to cover the full frequency range of 32-20,000 c/s. capable of doing justice to the finest programme source, its polar distribution makes it ideal for really Hi-Fi Stereo. Delivered complete with speakers, crossover unit, level control, Tygan grille cloth, etc. All parts pre-cut and drilled for ease of assembly and left "in the white" for finish to personal taste. £19.18.6

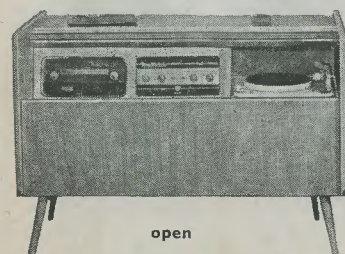BUY YOUR HI-FI EQUIPMENT ALL TOGETHER AS ONE OF OUR  
"PACKAGED DEALS" AND SAVE YOURSELF MORE MONEY!



open

THE  
"GLOUCESTER"

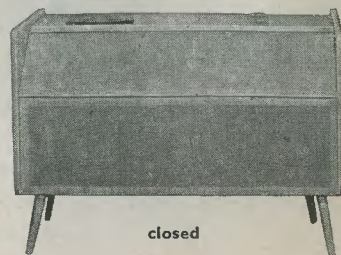

closed

**DAYSTROM LTD** DEPT. RC7 GLOUCESTER ENGLAND

Easily-built  
Equipment




of excellent  
quality

at much lower cost



O-12U

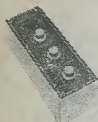

DC-1U



S-33



DX-40U



AG-9U



UJR-1



MA-12



OS-1




V-7A



S-88



SSU-1

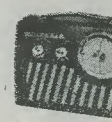

UXR-1



"STUDIO"

5" OSCILLOSCOPE: O-12U. "Y" sensitivity 10mV/cm., 3 c/s to over 5 Mc/s. Rise time, 0.08 µsecs. or less. Sweep, 10 c/s to 500 kc/s. Electronically stabilised. £34.15.0

2½" PORTABLE SERVICE OSCILLOSCOPE: OS-1. Ideal instrument for service and portable use. Size 5" x 8" x 14". Wt. 10½lb. £18.19.6

DECADE CAPACITANCE BOX: DC-1U. Provides capacity values from 100 mmf to 0.11 mfd. in 100 mmf. steps. Ideal for experimental, development and design work. £5.18.6

VALVE VOLTMETER: V-7A. The World's largest-selling VVM. Measures Volts to 1,500 (DC & RMS) and 4,000 pk. to pk.; Resistance 0.1Ω to 1,000MΩ D.C. Sensitivity: 7,333,333 ohms per volt. £13.0.0

HI-FI STEREO 6 WATT AMPLIFIER: S-33. Low-priced but high quality; less than 0.3% distn at 2½ watts per channel. £11.8.0

HI-FI STEREO 16 WATT AMPLIFIER: S-88. Superb reproduction for the man who wants the best in Hi-Fi. Only 0.1% distortion at 6 W/chnl. Many special features. £25.5.6

"HAM" TRANSMITTER: DX-40U. 75 W. CW; 60 W. pk. c/s phone; 40 W. into Aerial. £29.10.0

HI-FI SPEAKER SYSTEM: SSU 1. Ideal twin speaker/ducted-reflex cabinet for stereo/mono, in average room (left "in the white"). Legs £1.7.0 extra. £10.5.6

AUDIO GENERATOR: AG-9U. 10 volts, 10 c/s to 100 kc/s pure sine-wave. Switch-selected frequencies attenuation. £19.3.0

JUNIOR PERSONAL TRANSISTOR RADIO: UJR-1. Youngsters are not excluded from our kit programme. This special single transistor set is an excellent introduction to radio and an instructive present. £2.16.6

TRANSISTOR PORTABLE RADIO: UXR-1. In elegant solid hide case, with golden relief. Six transistors, dual-wave, fine reproduction, very easy to build. £15.18.6

SINGLE CHANNEL 12 WATT HI-FI AMPLIFIER: MA-12. Ideal for stereo conversions, etc. Generous auxiliary power provided. £9.19.6

COLLARO "STUDIO" TAPE DECK. This extremely attractive and compact 3-speed monaural tape deck features digital counter, pause control and piano-key switches. £17.10.0

(Following models not illustrated)

CAPACITANCE/RESISTANCE BRIDGE: C-3U. Measures capacity, 10pF to 1,000µF. Resistance 100Ω to 5MΩ; Pwr. Factor. £7.19.6

VARIABLE FREQUENCY OSCILLATOR: VF-1U. 10V output; covers 10 to 160 metres. £10.12.0

AUDIO WATTMETER: AW-1U. Up to 25 W. continuous, 50 W. intermittent. £13.18.6

AUDIO VALVE-MILLIVOLTMETER: AV-3U. 1mV to 300V A.C. 10 c/s to 400 kc/s. £13.18.6

ELECTRONIC SWITCH: S-3U. This extremely useful device extends your single-beam "scope" for double-beam uses. £9.18.6

DIRECT READING CAPACITANCE METER: CM-1U. Full-scale ranges of 0-100 mmf., 1,000 mmf., 0.01 mfd. and 0.1 mfd. £14.10.0

Money Saving "Packaged Deals"  
of Complete Stereo Equipment  
from £42.10.0

All prices include free delivery in U.K.  
Deferred terms available on orders above £10

★ SEND THIS COUPON NOW  
FOR FURTHER INFORMATION

Without obligation please send me  (Tick here)

(Please write in BLOCK CAPITALS)

BRITISH HEATHKIT CATALOGUE   
FULL DETAILS OF MODEL(S)

NAME

ADDRESS

**DAYSTROM LTD** DEPT. RC7  
GLOUCESTER · ENGLAND

A member of the Daystrom Group, manufacturers of the  
WORLD'S LARGEST-SELLING ELECTRONIC KITS


# BUILD THE OG.10 OSCILLOSCOPE

with an  
authentic

## Jason *kit*
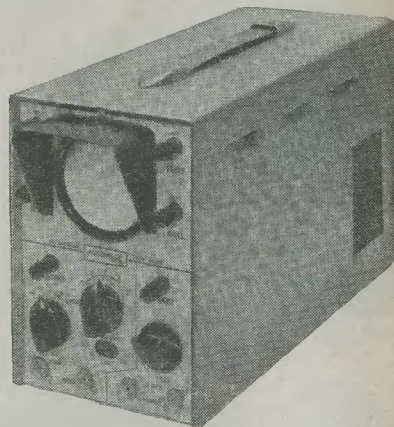
### Britain's Finest kits

For absolute assured results, build this excellent Oscilloscope with an authentic Jason kit. All parts exact to author's specification. Amongst the many uses to which this instrument may be put, TV servicing and audio amplifier checking are important examples. Sensitivity—10mV/cm with a bandwidth of 2 c/s to 1.5 Mc/s. Complete with case, Mullard C.R.T. and all valves as specified.



**£22.10.0** with tube

### OTHER KITS IN THE JASON PROGRAMME

#### AUDIO GENERATOR AG.10

Excellent stability with output held constant over entire band. Tunes from 10 c/s to 100 kc/s over four switched stages and two scales. Switch for square or sine wave. Square wave rise time less than 2 microseconds, at all frequencies. Min. calibrated output 100mV. With case, valves and calibrated scale **£14.5.0** (Built £17.10.0)

#### WOBBULATOR W.11

Enables FM signals, IF signals for AM sets and TV sound and vision channels to be correctly aligned. RF circuits may also be aligned from the 40-70 Mc/s output, the second and third harmonics of which serve for Bands II and III respectively. Return trace is blanked when using a 50 c/s sine wave sweep frequency to provide a reference base line not found on most commercial instruments. **£14.19.0** (Built £19.19.0)

#### CRYSTAL CALIBRATOR CC.10

Enables the exact frequency of a generator to be found between 10 kc/s and 250 Mc/s. A basic accuracy of 0.01% is achieved from a 1 Mc/s crystal. Self-powered unit complete with valves, crystal oscillator, speaker and case. **£16.19.0** (Built £21.0.0)

#### STABILISED POWER PACK PP.10M


175mA at 300V mains variation of  $\pm 10\%$  produces output change of less than 0.15%. Ripple less than one millivolt. Available with or without meter. Polarity change switch. With valves, meter and case. **£19.0.0**

Details of the above instruments and others in the Jason range, including audio and radio units gladly sent on request. Please quote this journal when writing.

## THE JASON MOTOR & ELECTRONIC COMPANY

3-4(E) GREAT CHAPEL ST. OXFORD ST. LONDON W1 Telephone GERrard 0273/4

# FANTASTIC UNREPEATABLE OFFER!

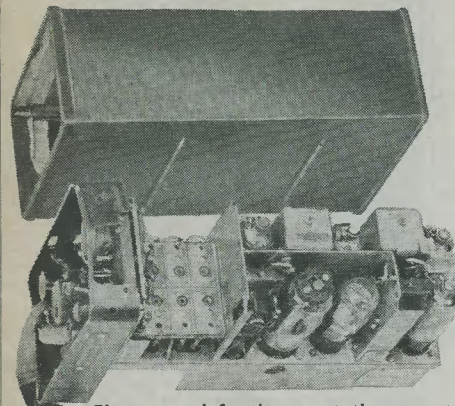

No. 46 TRANSCEIVER CHASSIS AND 2 PAIRS DLR 5 MOVING COIL HEAD- PHONES AND 2 THROAT MIKES. ALL NEW AND UNUSED. WORTH AT LEAST £4.10.0.

OUR PRICE **35/-** THE LOT  
CARRIAGE PAID G.B.


We challenge you to beat this this offer for price!

Cheap enough for the expert, the youngster or anybody to play with. Note Gentlemen. The No. 46 transceiver chassis contains 6 valves. Two VP23, ATP25, HL23, DD., QP25, A.T.P.4. Two 3-pole 2-way Yaxley switches, one 3-pole 3-way Yaxley switch, output and mic. transformers, 50 p.F. tuning capacitors and numerous useful resistors and capacitors. Build up this superhet circuit I.F. 470 kc/s, 3 channel switching, crystal controlled. One switch, removed to comply with Ministry regulations, no crystals.

BUSHELL'S 46-52 Brearley Street Birmingham 19 Aston Cross 3556-7
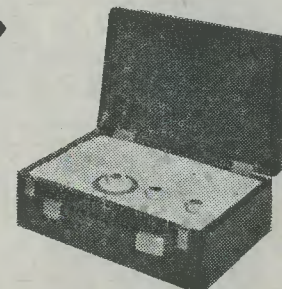
## RCS "REGENT" 4-Valve Portable Superhet

Plans 9d. or details S.A.E.  
(as featured in June issue)



- ★ Economy "96" Range Valves
- ★ Medium and Long Waves
- ★ 6" High Flux Speaker
- ★ T.C.C. Printed Circuit and Condensers
- ★ Osmor Ferrite Aerial and Coils
- ★ Attache Case Cabinet 12"x 8"x 4" Rexine-covered
- ★ Ready-made Mains Unit available. Price 39/6
- ★ All components identified and of finest quality

Special Reduced Price (for limited period) if all components are purchased at one time.

**£6.6.0**

Carriage 4/-  
Batteries extra 10/- set

CHAMPION VHF (FM) TUNER 88 to 96 Mc/s. any radio, radiogram or amplifier. Brand new. Ready 5 Mullard valves and superhet tuning heart. for use. 12 months guarantee. List price 16 gns.


Features: This is a self-powered 200/250V a.c. VHF (FM) adaptor with operating and servicing data and a screened lead for connection to pick-up sockets of 20/- extra.

Our price **£9 10.** carr. 4/6

Maroon and cream receiver styled cabinet 6" x 12" x 6".
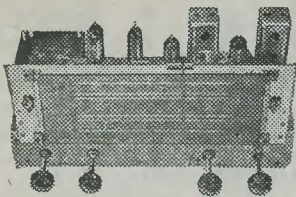
## RADIO COMPONENT SPECIALISTS

337 WHITEHORSE ROAD  
WEST CROYDON  
Telephone THO 1665



1960 RADIOGRAM CHASSIS

THREE WAVEBANDS S.W. 16 m.-50 m. M.W. 200 m.-550 m. L.W. 800 m.-2,000 m. FIVE VALVES LATEST MULLARD ECH81, EF89, EBC81, EL84, EZ80 12 month Guarantee. A.C. 200/250V, 4-way switch. Short-Medium-Long-Gram. A.V.C. and negative feedback. 4.2 watts. Chassis 13 1/2" x 5 1/2" x 2 1/2". Glass dial, horizontal or vertical, size 10" x 4 1/2". 2 pilot lamps. Four knobs, walnut or ivory, aligned and calibrated. Chassis isolated from mains. Leaflet S.A.E.

**BRAND NEW £9.10.0** Carr. 4/6  
TERMS: Deposit £5.5.0 and 5 monthly payments of £1  
MATCHED SPEAKERS: 8" 17/6, 10" 25/-, 12" 30/-

**LATEST "E.M.I." 4 SPEED SINGLE RECORD PLAYER**

Acos 73 Hi-Fi Pick-up for LP, 78 and Stereo 7", 10" and 12" records. Silent motor, heavy turntable, auto stop. Special offer **£6.19.6** post free

**BUILD THIS REPRODUCER BARGAIN SPECIAL SINGLE PLAYER KIT**

COLLARO 4-speed Gram-Pick-up Unit £3.15.0  
Handsome portable case 17 1/2" x 13 1/2" x 7" with room to play 12" records £2. 5.0  
Ready built 3-watt amplifier with two valves and 7" elip. speaker, printed circuit £3.12.6  
or **£9.9.0** complete kit post free

**I.F. TRANSFORMERS 7/6 pair**

465 kc/s slug tuning miniature can 2 1/2" x 1" x 1". High Q and good band width. By Pye Radio. Data sheet supplied.  
Wearite M800 Midget 465 kc/s 1 1/2" x 1/2" sq. 12/6 pair  
Weyrad Standard Size 465 kc/s 3 1/2" x 1 1/2" sq. 12/6 pair

**New boxed VALVES 90-day Guarantee**

1R5	7/6	6K8G	7/6	EA50	1/6	EZ80	7/6
1S5	7/6	6L6G	10/6	EABC80	8/6	E1148	1/6
1T4	6/-	6N7M	6/6	EB91	6/-	HABC80	12/6
2X2	3/6	6Q7G	8/6	EBC33	8/6	HVR2A	6/6
3S4	7/6	6SA7	6/-	EBC41	8/6	MU14	9/-
3V4	7/6	6SJ7M	6/6	EBF80	10/-	P61	3/6
5U4	7/6	6SN7	6/6	ECC84	9/6	PC84	9/6
5Y3	7/6	6V6G	6/6	ECF80	9/6	PCC80	9/6
5Z4	9/6	6X4	7/6	ECH42	10/6	PCL82	11/6
6AM6	5/-	6X5	6/6	ECL80	10/6	PEN25	6/6
6B8	5/-	12A6	7/6	ECL82	10/6	PL81	12/6
6BE6	7/6	12AT7	8/-	EF39	5/6	PL82	10/6
6BH6	9/6	12AU7	8/-	EF41	9/6	PY80	7/6
6BW6	9/6	12AX7	8/-	EF50	5/6	PY81	9/6
6D6	6/-	12BE6	6/6	EF80	8/-	PY82	7/6
6F6	7/6	12K7	8/6	EF86	12/6	SP61	3/6
6H6	3/6	12Q7	6/6	EF92	5/6	UBC41	9/6
6J5	5/6	35L6	9/6	EL32	5/6	UCH42	9/6
6J6	5/6	35Z4	7/6	EL41	9/6	UF41	9/6
6J7G	6/6	80	9/6	EL84	8/6	UL41	9/6
6K6GT	6/6	807	5/6	EY51	9/6	UY41	8/-
6K7G	5/-	954	1/6	EZ40	7/6	U22	8/-

DK96, DF96, DAF96, DL96, 8/6 ea. or 30/- set.

B.B.C. Pocket Transistor, M.W. and L.W. Radio Kit 32/6. Phones 7/6, or deaf aid earpiece 15/-.

Our written guarantee with every purchase

**C.R.T. ISOLATION TRANSFORMERS**

For Cathode Ray Tubes having heater cathode short circuit and for C.R. Tubes with falling emission, full instructions supplied. Type A. Low leakage windings. Optional 25% and 50% boost on secondary: 2V, or 4V, or 6.3V, or 10.3V, or 13.3V, with mains primaries, 12/6. Our Latest Superior Product. Mains Input Type A2. High quality low capacity 10-15pF. Optional boost 25%, 50%, 75%, 16/6 each. Type B. Mains input. Low capacity. Multi output 2, 4, 6.3, 10 and 13V. Boost 25% and 50%. This transformer is suitable for all TV tubes. 21/- each.

**RESISTORS.** Preferred values. 20% 10 ohms to 10 meg, 1/2W 4d., 1W 4d., 1W 6d., 1 1/2W 8d., 2W 1/-, **HIGH STABILITY.** 1/2W 1%, 2/-, All preferred values 100Ω-10MΩ. Ditto 5% 100Ω-5MΩ 9d. each.

**WIRE-WOUND RESISTORS** 1/3 25 ohms-10,000 ohms 2/6 1/2

**WIRE-WOUND POTS** Pre-set min. TV type. Knurled slotted knob. All values 25 ohms to 25k, 3/- each, 30k, 50k, 4/-, Ditto 1/2W Carbon Track 30k to 2 Meg, 3/-.

**3W Lab. Colvern, etc.** Standard size Pots, 2 1/2 Spindle, high grade. All values, 100 ohms to 50k, 6/6; 100k, 7/6. W/W EXT. SPEAKER CONTROL 10Ω, 3/-.

**MAINS TRANSFORMERS-200/250 AC**

STANDARD 250-0-250, 80mA, 6.3V tapped 4V 4A, Rectifier 6.3V 1A tapped 5V 2A and 4V 2A 22/6  
Ditto 350-0-350 22/6  
MINIATURE. 200V 20mA, 6.3V 1A 10/6  
MIDGET. 220V 45mA, 6.3V 2A 15/6  
SMALL. 220-0-220V 50mA, 6.3V 2A 17/6  
STANDARD. 250-0-250, 65mA, 6.3V 3.5A 17/6  
HEATER TRANS. 6.3V 1 1/2A 7/6. Ditto, sec. 6.3V 3A 10/6. Ditto, tapped sec. 2, 4, 6.3V 1 1/2A, 8/6.  
Mullard "510" Osram "912" 300-0-300, 120mA, 6.3V 4A ct., 6.3V 2A tapped 5V 38/6  
General Purpose Low Voltage. Outputs 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V. at 2A 22/6

**O/P TRANSFORMERS.** Heavy duty 50mA, 4/6. Multi-ratio push-pull, 7/6. Miniature 3V4, etc., 4/6. Small pentode, 4/6. Hygrade push-pull 7 watts, 15/6. Goodmans heavy duty 10/20V 6k or 8k ct., 30/-.  
**L.F. CHOKES** 15/10H 60/65mA, 5/-; 10H, 85mA, 10/6; 10H 150mA, 14/-.

**CRYSTAL MIKE INSERT** by Acos 6/6  
Precision engineered. Size only 3/8" x 1/8"  
**ACOS CRYSTAL HAND OR DESK MIKE, 27/6**

**ALADDIN FORMERS** and cores. 1/2" 8d., 3/8" 10d. 0.3" FORMERS 5937 or 8 and cans TV1 or 2. 3/8" sq. x 2 1/2" sq. x 1 1/2". 2/- with cores.

**LOW MOTION DRIVES.** Epicyclic ratio 6-1, 2/3. REMPLY INSTRUMENT IRON, 230V 25W, 17/6.

**MAINS DROPPERS.** 3" x 1 1/2". With adj. sliders, 0.3A, 1,000 ohms, 4/3; 0.2A, 1,000 ohms, 4/3.

**LINE CORD.** 0.3A 60 ohms per foot, 0.2A 100 ohms per foot, 2-way, 6d. per foot; 3-way, 7d. per foot.

**MIKE TRANS.** 50-1, 3/9; 100-1, 5/6.  
**LOUDSPEAKERS.** P.M. 3 ohm, 5", Rola, 17/6; 6" x 4" Rola, 18/-; 4" Hi-Fi Tweeter, 25/-; 8" Plessey, 19/6; 6 1/2" Goodmans, 18/6; 10" R.A., 30/-; 12" Plessey, 30/-; 10" x 6" R.A., 27/6; 12" Baker 15W 3 ohm or 15 ohm models, 90/-; Scentorian HF012 10", 95/-.

**CRYSTAL DIODES.** G.E.C., 2/-; GEX34, 4/-.  
**40 CIRCUITS FOR GERMANIUM DIODES, 3/-.**  
**H.R. HEADPHONES** 4,000 ohms, brand new, 15/- pr. **SWITCH CLEANER FLUID,** squirt spout, 4/3 tin.

**TWIN GANG CONDENSERS.** 365pF, miniature, 1 1/2" x 1 1/2" x 1 1/2", 10/-; 0.0005 standard with trimmers, 9/6; less trimmers, 8/-; midget, 7/6; 50pF single, 2/6.

**SHORT WAVE SINGLE 75pF, 100pF, 160pF, 7/- each.**  
**TUNING AND REACTION CONDENSERS.** 100pF, 300pF, 500pF, 3/6 each, solid dielectric.  
**RADIO & TV SERVICE SHEETS** 2/6 plus S.A.E.

**HIGH GAIN TV PRE-AMPLIFIERS BAND I B.B.C.**

Tunable channels 1 to 5. Gain 18dB. ECC84 valve. Kit price 29/6 or 49/6 with power pack. Details 6d. (PCC84 valves if preferred.)

**BAND III I.T.A.**—Same prices  
Tunable channels 8 to 13. Gain 17dB. ECC84 valve

**Volume Controls**

Midget size. Long spindles. Guaranteed 1 year. All values 5,000 ohms to 2 Meg. No Switch D.P. Switch 3/- 4/9 Linear or Log Tracks

**80Ω Coaxial Cable**

Post 1d. per yard extra Semi-air spaced Polythene Ideal Band III 6d. yd. Losses cut 50% FRINGE QUALITY 1/- yd. Air spaced Coaxial

**Coaxial Plugs** 1/- **Lead Socket** 2/-  
**Panel Sockets** 1/- **Outlet Boxes** 4/6  
**Balanced Twin Feeder,** per yd 6d., 80Ω or 300Ω.  
**Twin Screened Balanced Feeder,** 1/6 yd, 80 ohms.  
**Trimmers.** Ceramic 30, 50, 70pF, 9/-; 100pF, 150pF, 1/3; 250pF, 1/6; 600pF 750pF, 1/9; Phillips, 1/- each.  
**BLACK CRACKLE PAINT.** Air drying, 3/- tin.  
**P.V.C. CONN. WIRE,** 8 colours, single or stranded, 2d. yd. Sleeving 1, 2mm, 2d. 2, 3mm, 3d., 6mm, 5d. yd.  
**NEON MAINS TESTER SCREWDRIVERS,** 5/-.  
**SOLDER RADIOGRADE,** 4d. yd, 1lb 2/6.

**Aluminium Chassis.** 18 s.w.g. Plain, undrilled, 4 sides, riveted corners, lattice fixing holes, 2 1/2" sides. 7" x 4", 4/6; 9" x 7", 5/9; 11" x 7", 6/9; 13" x 9", 8/6; 14" x 11", 10/6; 15" x 14", 12/6; 18" x 16" x 3", 16/6.

**Miniature Contact Cooled Rectifiers.** 250V 50mA, 7/6; 250V 85mA, 9/6. Selenium Rect. 300V 85mA, 7/6. Coils. Wearite "P" type, 3/- each. Osmor Midget "Q" type, adj. dust core, from 4/- each. All ranges. **Teletron D.W.R. L. & Med. T.R.F.** with reaction, 3/6. **Ferrite Rod Aerials,** M.W., 8/9; M. & L., 12/6. **Ferrite Rods** 8" x 3/8"-2/6

**T.R.F. Coils A/HF,** 7/- pair. **H.F. Chokes,** 2/6. **Speaker Fret.** Gold cloth, 17" x 25", 5/-; 25" x 35", 10/-; Tygan, 4" 6" wide, 10/-; 2" 3" wide, 5/- ft. Samples, S.A.E.

**Condensers.** 0.001μF 7kV T.C.C., 5/6; ditto 20kV, 9/6; 0.1μF 7kV, 9/6; 100pF to 500pF Micas, 6d.; Tubular 500V 0.001 to 0.05, 9d.; 0.1, 1/-; 0.25, 1/6; 0.1/350V, 9d.; 0.5/350V, 1/9; 0.01/2,000V, 1/9; 0.1/2,000V, 3/6.

**Ceramic Condensers.** 500V 0.3pF to 0.01μF, 9d. **Silver Mica.** 10% 5pF to 500pF, 1/-; 600pF to 3,000pF, 1/3; close tolerance (plus or minus 1pF), 1.5pF to 47pF, 1/6; ditto 1% 50pF to 815pF, 1/9; 1,000pF to 5,000pF, 2/-.

**NEW ELECTROLYTICS FAMOUS MAKES**

TUBULAR	TUBULAR	CAN TYPES
1/350V 2/-	50/350V 5/6	8/500V 3/-
2/350V 2/3	100/25V 3/6	16/500V 4/-
4/450V 2/3	250/25V 3/-	32/350V 4/-
8/450V 2/3	500/12V 3/6	100/270V 5/6
8/500V 2/9	8+8/450V 4/6	2,500/3V 5/6
16/450V 3/6	8+8/500V 5/-	5,000/6V 5/6
16/500V 4/-	8+16/450V 5/-	32+32/450V 6/6
32/450V 5/6	8+16/500V 5/6	32+32+32/350V 7/6
25/25V 1/9	16+16/450V 5/6	50+50/350V 7/6
50/25V 2/-	16+16/500V 6/-	64+120/350V 11/6
50/50V 2/-	32+32/350V 4/6	100+200/275V 12/6

**Full Wave Bridge Selenium Rectifiers.** 2, 6 or 12V 1 1/2A, 8/9; 2A, 11/3; 4A, 17/6. Free charger circuit. **Charger Transformers.** Tapped input 200/250V for charging at 2, 6 or 12V 1 1/2A, 15/6; 2A, 17/6; 4A, 22/6.

**P.V.C. PLASTIC RECORDING TAPE**  
Long Play 7" reel, 1,700ft 32/6 Standard Play 5 1/2" reel, 1,200ft 22/6 7" reel, 1,200ft 21/- 5" reel, 850ft 19/6 5 1/2" reel 850ft 17/6 3" reel, 225ft 7/6 5" reel, 600ft 15/-  
Spare Plastic Reels all sizes 3/-. Metal Reels 7" only 2/- "Instant" Bulk Tape Eraser and Head Defluxer, 200/250V A.C., 27/6. Leaflet, S.A.E.



**BRAND NEW AND BOXED Model UA8 OUR PRICE £6.15.0**  
The Brilliantly Successful **Monarch** Stereo Heads £7.19.6  
Stereo Models UA8 £7.19.6 UA14 £10.10.0

★ **COLLARO HI-FI AUTOCHANGER** ★  
4 SPEEDS—10 RECORDS  
or with Cabinet, Amplifier and Speaker  
**OUR PRICE £11.19.6** Carr. 5/6

★ **GARRARD 4-SPEED RECORD CHANGERS MODEL 210** ★  
With Plug-in Head for Monaural Stereo Heads £2 extra **£10.10.0**

**AUTOCHANGER ACCESSORIES**  
Suitable player cabinets (uncut boards) 49/6  
Amplifier player cabinets with cut boards 63/-  
2-valve amplifier and 6 1/2" speaker for above 79/6  
3-valve amplifier and 6 1/2" speaker for above 95/-  
Wired and tested ready for use

★ **GARRARD 4-SPEED SINGLE RECORD PLAYER TA MK II** ★  
**£8.8.0** **AUDIO PERFECTION** Stereo wired  
with Plug-in GC8 Normal Heads **MODEL 4 HF £18** Stereo Heads £2 extra

**Wavechange Switches.** 2 p. 2-way, 3p. 2-way, short spindle, 2/6; 5p. 4-way 2 wafer, long spindle, 6/6; 2 p. 6-way, 4 p. 2-way, 4 p. 3-way, long spindle, 3/6; 3 p. 4-way, 1 p. 2-way, long spindle, 3/6; wavechange "MAKITS." 1 wafer, 8/6; 2 wafer, 12/6; 3 wafer, 16/-; 4 wafer, 19/6; 5 wafer, 23/-; 6 wafer, 26/6.  
**Toggle Switches, s.p., 2/-; 3/6; d.p.d.t., 4/-.**

**JASON FM TUNER COIL SET, 26/-.** H.F. coil, aerial coil, oscillator coil, two i.f. transformers 10.7 Mc/s, detector transformer and heater choke. Circuit and component book using four 6AM6, 2/6. **Complete Jason FMT-1.** Kit, and Jason chassis with calibrated dial, 5gns. 4 valves 20/-

**Valveholders.** Pax. int. oct., 4d. EA50, EF50, 6d. B12A, CRT 1/3. Eng. and Amer. 4, 5, 6 and 7 pin, 1/-.  
**MOULDED Mazda** and int. oct., 6d., B7G, B8A, B8G, B9A, 9d. B7G with can, 1/6. B9A with can, 1/9.  
**Ceramic, EF50, B7G, B9A, int. oct., 1/-.** B7G, B9A cans, 1/- each. **Valve and TV Tube equivalents 9/6**  
**TV Fault Finding, 5/-.** **Quality Amplifiers, 4/6.**  
**Radio Valve Guide.** Books 1, 2 or 3, 5/- each.  
**TRANSISTORS.** Ediswan Audio XB112, 10/-, R.F. 2 Mc/s XA103, 15/-; R.F. 4 Mc/s XA104, 18/-, Red Spot 5/-; White Spot 7/6.  
**Sub-miniature Electrolytics (15V) 1μF, 2μF, 4μF, 5μF, 8μF, 25μF, 50μF, 100μF, 3/-.**

**TELETRON POCKET RADIO KIT**  
**Transidyne Superhet Six** 6" x 4" x 1 1/2"  
T.C.C. Printed Circuit, internal Ferrite aerial, Rola loudspeaker push-pull output. All parts, cabinet, 6 Ediswan transistors, GEX34 diode, **£9.9.0** Details 9d.

**RADIO COMPONENT SPECIALISTS**

Buses 133 or 68 pass door. S.R. Stn. Selhurst.

THE RADIO CONSTRUCTOR

**337 WHITEHORSE ROAD WEST CROYDON**

Telephone THO 1665

Post and packing charge 1/-, over £2 post free.C.O.D. 1/6

(Export welcome. Send remittance and extra postage)

AUGUST 1960

**FREE** THIS BOOK WILL INTEREST YOU!

LEARNING the PRACTICAL WAY

**RADIOSTRUCTOR**  
EQUIPMENT-COURSES

**A NEW-PRACTICAL WAY of UNDERSTANDING**

## RADIO · TELEVISION · ELECTRONICS

Including: Transistors; VHF/FM; Hi-Fi equipment; Computers; Servo-mechs; Test Instruments; Photo-electrics; Nucleonics, etc.

FOR... Your Career... Your Own Business... An Absorbing Hobby...

Radiostructor—an organisation specialising in electronic training systems—offers a new self-instructional method using specially designed equipment on a “do-it-yourself” basis. You learn by building actual equipment with the big kits of components which we send you. You advance by simple steps, performing a whole series of interesting and instructive experiments—with no complicated mathematics! Instructional manuals employ the latest techniques for showing the full story of electronics in a practical and interesting way—in fact, you really have fun whilst learning! Fill in the coupon below, for full particulars—

**RADIOSTRUCTOR**  
LEADS THE WORLD  
IN ELECTRONICS TRAINING

### POST NOW

To RADIOSTRUCTOR (Dept. G.31)  
READING, BERKS.

Please send brochure, without obligation, to:

\* NAME .....

\* ADDRESS .....

\* BLOCK CAPS PLEASE  
(We do not employ representatives)

# CHASSIS CHASSIS CHASSIS CHASSIS CHASSIS

## A ★ COMPLETE ★ SERVICE

Stock sizes in 18 g. Aluminium 2" deep. All corners wrapped and rivetted-lattice fixing holes.

6" x 4" x 2"	4/3	10" x 7" x 2"	7/-	12" x 8" x 2"	8/-
8" x 6" x 2"	5/9	12" x 6" x 2"	7/6	14" x 10" x 2"	11/6

As above but in tin plate 6" x 4" x 2" 3/6 8" x 6" x 2" 4/6

Sectional tin plate chassis—two ends—two sides—one top—A boon for easy cutting and direct soldering. 7" x 5" x 2" 4/9 10" x 7" x 2" 6/- 14" x 10" x 2" 8/9 10" x 5" x 2" 5/3 14" x 5" x 2" 7/3.

**SPECIAL CHASSIS - ANY SHAPE -** ½ d sq. inch of blank plus 6d per bend - corner wrapping included

All the above post free or plus 2/- C.O.D.

PUNCHING and DRILLING TO YOUR REQUIREMENTS

**P.J. PRODUCTS** . 34 HIGH STREET . ERITH . KENT  
S.A.E. for full details  
TRADE ENQUIRIES WELCOMED

# FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?

ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

We definitely Guarantee  
“NO PASS—NO FEE”

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £20 a week, send for your copy of “ENGINEERING OPPORTUNITIES” today—FREE.

BRITISH INSTITUTE OF ENGINEERING  
TECHNOLOGY (Incorporating E.M.I. Institutes)  
(Dept. SE/23), 29 Wright's Lane, London, W.8

### WHICH IS YOUR PET SUBJECT?

Mechanical Eng.,  
Electrical Eng.,  
Civil Engineering,  
Radio Engineering,  
Automobile Eng.,  
Aeronautical Eng.,  
Production Eng.,  
Building, Plastics,  
Draughtsmanship,  
Television, etc.

GET SOME LETTERS AFTER YOUR NAME!

A.M.I.Mech.E.  
A.M.I.C.E.  
A.M.I.Prod.E.  
A.M.I.M.I.  
L.I.O.B.  
A.F.R.Ae.S.  
B.Sc.  
A.M.Brit.I.R.E.  
City & Guilds  
Gen. Cert. of Education  
Etc., etc.

### PRACTICAL EQUIPMENT

Basic Practical and Theoretical Courses for beginners in Radio, T.V. Electronics, Etc., A.M.Brit.I.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio

Radio & Television Servicing Practical Electronics Electronics Engineering Automation

### INCLUDING TOOLS!

The Specialist Electronics Division of B.I.E.T. (Incorporating E.M.I. Institutes) NOW offers you a real laboratory training at home with practical equipment. Ask for details.

B.I.E.T. SCHOOL OF ELECTRONICS

### POST COUPON NOW!

Please send me your FREE 156-page “ENGINEERING OPPORTUNITIES” (Write if you prefer not to cut page)

NAME .....

ADDRESS .....

SUBJECT OR EXAM THAT INTERESTS ME .....

THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD



Safety first every time with these patented spring-loaded AVO Prodclips.

Cleverly designed for use as insulated prods, they are invaluable for reaching and holding test points which are difficult of access.

Suitable for use with AvoMeter, Multiminor and Avo Electronic Test Meter Leads Post Free 15/- per pair

**AVO LTD** AVOCET HOUSE  
92-96 VAUXHALL BRIDGE RD., LONDON, SW1  
VICtoria 3404 (12 lines)

A Member of the Metal Industries Group of Companies  
2PC

## ERSIN MULTICORE SOLDERS

Wherever precision soldering is essential, manufacturers, engineers and handymen rely on MULTICORE. There's a MULTICORE SOLDER just made for the job you have in hand. Here are some of them.

### SAVBIT TYPE 1 ALLOY

A specially formulated alloy to reduce the wear of soldering iron bits. Contains 5 cores of non-corrosive Ersin Flux and is ideal for all soldering purposes.



### SIZE 1 CARTON 5/-

Available in three specifications.

### BIB WIRE STRIPPER AND CUTTER

Strips insulation without nicking wire, cuts wire cleanly, splits extruded flex 3/16 each



**ERSIN MULTICORE**  
Contains 5 cores of extra-active non-corrosive Ersin Flux. Prevents oxidation and cleans surface oxides.  
**SIZE 1 CARTON 5/-**

The Home Constructors Pack, containing 19 ft. of 18 s.w.g. 60/40 alloy is available at 2/6d.

**MULTICORE SOLDERS LTD.,**  
MULTICORE WORKS, HEMEL HEMPSTEAD, HERTS.  
(BOXMOOR 3636)

★ VALVES		NEW TESTED AND GUARANTEED	
1R5	6/6	6X4	7/6
1S5	6/6	6X5GT	6/6
1T4	4/6	12AH8	10/6
354	6/9	12AT7	7/6
3V4	7/6	12AU7	7/6
5U4G	6/-	12AX7	9/-
5Y3GT	7/6	12BH7	10/6
5Z4G	9/-	12K7GT	8/6
6AK6	6/6	12K8GT	13/6
6AL5	4/6	12Q7GT	6/6
6AM6	4/-	25A6G	10/6
6AT6	7/6	25L6GT	9/-
6BA6	8/6	35Z4GT	8/6
6BE6	7/6	35L6GT	9/6
6BR7	10/6	5763	10/6
6BW6	8/6	DAF91	6/6
6J7GT	8/6	DAF96	8/-
6K7G	7/6	DF91	4/6
6Q7G	7/6	DF96	8/-
6SL7GT	8/-	DH76	8/6
6SN7GT	8/6	DH77	7/6
6V6G	7/6	DK91	6/6
		EL84	10/6
		EL91	7/6
		EY51	9/6
		EZ40	6/6
		EZ80	6/6
		EZ81	7/-
		PL81	13/6
		PL82	10/6
		PY81	8/-
		PY82	7/-
		PCC84	9/6
		PCF80	9/-
		PCF82	11/-
		PCL82	7/6
		R19	12/6
		U76	8/6
		UBC41	10/-
		UCH42	10/6
		UF41	10/-
		UL41	8/-
		UY41	8/-
		UV76	8/6

Matched Pairs. EL84, 23/-; EL85, 25/-; 6V6G, 17/-; 6BW6, 13/-; KT33C, 19/6; 807 14/6 pair

SETS OF VALVES	
DK96, DF96, DAF96, DL96, "REGENT"	29/6 per set
DK91, DF91, DAF91, DL92, or DL94	21/- per set
1R5, 1T4, 1S5, 354, or 3V4	21/- per set
6K8, 6K7, 6Q7, 6V6, 5Z4, "G" Types	27/6 per set
12K8, 12K7, 12Q7, 35L6, 35Z4, GT Types	35/- per set
ECH42, EF41, EBC41, EL41, EZ40	37/6 per set
UCH42, UF41, UBC41, UL41, UY41	35/- per set

P.P. Op. Transformers. MR 3-15 ohms for EL84, 6V6, 6BW6, etc., 13/6; Op. Pen. 50mA, 5/6; 30mA, 4/6

P. & P. 6d., over £1 post paid. C.O.D. 2/6

**R. COOPER G8BX** 32 SOUTH END CROYDON SURREY CROYDON 9186

## CLYNE RADIO LTD.




Specialists in Equipment for Home Construction (Send stamp for complete list)

ALL POST ORDERS AND CORRESPONDENCE TO  
162 HOLLOWAY ROAD · LONDON N7  
NOR 6295/6/7

18 TOTTENHAM COURT RD. LONDON W1  
MUS 5929/0095  
99 CHEAPSIDE · LONDON EC2  
MON 6860

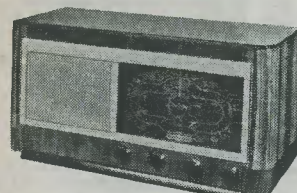FRUSTRATED EXPORT—Not Repeatable!  
LONG, MEDIUM AND SHORT WAVES  
**SUPERHET RECEIVER**



Manufactured by McCarthy for export. At present for operation on 6 volts, but conversion details supplied free. Valve line-up: 6K8G, 6K7G, 6Q7G, 6F6G, 6X5G and 6 volt 4-pin non-synchronous vibrator. 8" P.M. speaker, 4 watts output, p.u. socket, ext. i.s. socket, etc. Tone control. Fitted in polished wood cabinet, size 21 3/4" x 10 1/2" x 10 1/2". These cabinets are slightly soiled owing to storage, but each is guaranteed unused, in serviceable condition, tested prior to despatch. Price £5.19.6 only plus P. & P. 7/6, plus 27/6 for A.C. Mains Conversion Components if required. **OUTSTANDING BUY!**

NEW! NEW!  
The "Wavemaster"

7-Transistor 400 mW  
Luxury Portable output

To build yourself! Medium and Long Waves Push-Pull Superhet A.V.C. Perfect Car Radio reception. Size 10" x 6 1/2" x 4 1/2" at base tapering to 4" at top. Very attractive two-tone Vynide covered cabinet with cream and gold printed escutcheon plate, cream and gold knobs, handle and cabinet fittings.



Weight complete with long-life 7 1/2 volt battery—4 1/2 lb. Mazda high-grade transistors throughout, high-flux 7" x 4" elliptical speaker, slow motion tuning, co-axial socket at rear for direct connection to car radio aerial. Improved reception by use of seven-section plated telescopic aerial disappearing into cabinet when closed, 34" above cabinet when fully extended. Construction simplified by bakelite chassis board with the following components already mounted: i.f. transformers (3), oscillator coil, trimmer bank, output transformer, interstage transformer, aerial brackets and earth bar. **SPECIAL INCLUSIVE PRICE** for all required components, full assembly instructions—nothing more to buy—is £10.19.6 plus 3/6 P. & P. Alignment service available. Full assembly instructions and individually priced parts list, all of which are available separately 2/6 post free.

# Premier RADIO

23 TOTTENHAM COURT ROAD LONDON W1 Telephone MUSeum 3451/2  
and 309 EDGWARE ROAD LONDON W2 Telephone PADdington 6963

## Dramatic Price Reductions

AVANTIC SPA11 10 watt (per channel) combined Stereophonic Amplifier and Pre-amplifier. Dimensions: 14 1/2" x 8 3/4" x 4".  
Original Price 28 gns. **OUR PRICE 19 gns.** P. & P. 7/6.

AVANTIC SP21 Stereophonic Pre-Amp. Control Unit designed for use with the DL7-35 Power Amplifier. Power requirements 6.3V at 1.3A A.C., 250V at 5mA D.C. Dimensions 14 1/2" x 9" x 4".  
Original Price £28.10.0 **OUR PRICE 18 gns.** P. & P. 5/-

AVANTIC PL621 20 watt monaural Amplifier, frequency response 10 c/s-30 Kc/s 1dB. L.S. impedance, 4, 8, or 16 ohms. Dimensions 14" x 8 1/2" x 7 3/8".  
Original Price 29 gns. **OUR PRICE 19 gns.** P. & P. 7/6.

AVANTIC DL7-35 Power Amplifier, power output 54 watts peak, Valve line-up: GZ34, 2—EL34, ECC83, EF86. L.S. impedance 4, 8, or 16 ohms switch selected.  
Original Price 30 gns. **OUR PRICE £24.0.0.** P. & P. 7/6.

AVANTIC SL12-21 Speaker System employing 12" dia. P.M. L.S. and high frequency pressure unit in an acoustically designed enclosure. Dimensions 38" x 18 3/4" x 15 1/2". Finish matt medium walnut with front and sides covered with fawn fabric, standing on small contemporary legs.  
Original Price 22 gns. **OUR PRICE £21.0.0.** P. & P. 20/-

All this Equipment is Brand New and in Manufacturers' Original Sealed Cartons Full Descriptive Literature Available

## THE EASY-SIX 6-Transistor Battery Portable

May be built for **£9.15.0** plus Ever-Ready PP7 3/- p.p. Battery extra 3/3

**STAR FEATURES:** six 1st grade Mullard Transistors, internal Ferrite Rod Aerial, provision for Car Radio Aerial, 5" Loudspeaker printed circuit, with component positions indicated, pre-assembled Dial Assembly, 500 milliwatts output, full medium and long waveband coverage, attractive two-tone Blue/Cream Vynide covered Cabinet dimensions 8 1/2" x 6 1/2" x 3", full point-to-point instructions supplied, weight—3. lb. with Battery.

**The "MID-FI"**  
A NEW DESIGN 4 1/2 WATT AMPLIFIER kit  
**95/-** plus 3/- P. & P.


Technical specifications: separate bass and treble controls. Valve line-up EF86, EL84, EZ80. Voltage adjustment for a.c. mains from 200/250 volts, 3 or 15 ohms impedance. Negative feedback. Size 7" x 5" x 2", overall height 5". Silver hammered finished chassis.



# HOME RADIO OF MITCHAM

Dept. AC . 187 LONDON ROAD . MITCHAM . SURREY  
 Shop Hours: 9-6.30 (Weds. 1 p.m.) Telephone MIT 3282

## THE "CENTURION"

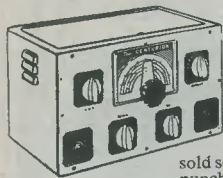

All-wave battery receiver. Can be constructed as one valver and audio and RF stages added later. All parts are standard, and sold separately. Ready punched chassis and cabinet. Full constructional details in *Short Wave Receivers for the Beginner*. Price 6/-, post 6d.

Price 6/-, post 6d.

## Circuits for Audio Amplifiers

This exciting new book by MULLARDS covers all aspects of high quality sound reproduction design and practice. Includes full constructional data for 12 different amplifiers, pre-amps, tape amplifiers, stereo amplifiers and pre-amps, mixers, etc. Price 8/6, post 1/- . We stock all the components for these designs, including punched chassis, front panels, Bulgin parts, ganged pots, etc. Price Lists 6d.

## EQUIPMENT CABINETS

Brand new grey hammer-finish steel cabinets with detachable lid and undrilled front panel and chassis. Size 12" x 7" x 7", and ideal for testgear, tuners, transmitters, power units, short wave receivers, etc. Louvered sides for ventilation. Similar to "Centurion" set above. Price £2.0.0, post 3/6.

## OUTPUT METER KIT

An essential piece of test gear for all serious engineers and Hi-Fi enthusiasts. An accurate audio-power output-meter by Labgear. Ranges, 25mW to 1 watt and 1 watt to 10 watts. Impedance 3, 15 and 600 ohms. Easily assembled from detailed instructions using printed circuit. Complete kit £3.15.0, or ready made £4.10.0.



## GOODMANS SPEAKERS




Superb new full-range 10" high-fidelity loudspeaker by Goodmans. Smooth response 40 to 15,000 cycles. Die-cast chassis and 12,000 gauss magnet. Aluminium speech coil. These features outclass all competition. Available from stock. 15 ohm only.

MODEL AXIOM 110 £5.0.0, plus 2/- post.
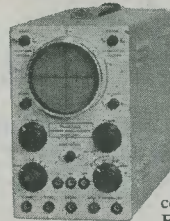
## SPECIAL OFFER

Very high-grade 3-core screened lead 1/8" dia. Black PVC covering, 1/- yd. Two-colour connecting wire. Ideal for radio work. Brand new. 25-yd. coils, 1/- each. S.A.E. for samples. Please add 6d. postage to all orders.




## HEATHKIT OS1 SERVICE OSCILLOSCOPE

Ideal light and compact portable scope for the service engineer and constructor. Dimensions 5" x 8" x 14 1/4"; weight 10 1/2 lb. Easily built from detailed instructions, and consistency of performance assured by printed circuit construction. Price £18.19.6, carriage paid. Full details of this excellent kit appears in this issue. We also stock most of the other HEATHKIT models of amplifiers, tuners, and test-gear.

Price £18.19.6, carriage paid.

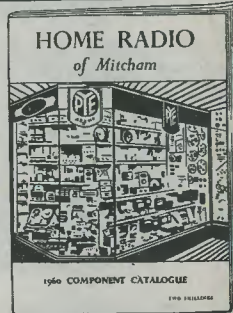
## STILL AVAILABLE . . . LATEST COMPONENT CATALOGUE

This fine component catalogue is a MUST for every keen constructor and engineer. 128 pages printed on high-grade paper with hundreds of illustrations, and listing over 4,000 items from our actual stock. Will save you endless time and money. SEND FOR YOUR COPY TODAY. Price 2/-, plus 9d. post.


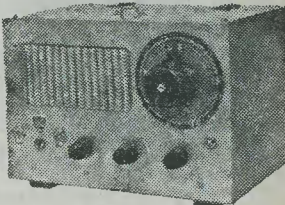
## JOHNSONS GLOBE-KING RECEIVERS

"The finest hobby of all." Explore the world on short-waves from your own armchair. Real long distance reception at minimum cost. Kit No. 100/A, One-valve battery set, £3.19.6, post 1/- . Kit No. 200/A, Two-valve battery, and Kit No. 300/A for A.C. mains, also available from stock. S.A.E. for details.



Model 300/A

## RECORDING TAPE -

Brand new boxed American "Brand Five" Ferrodynamic recording tape. One of America's top sellers. Super high-fidelity recording and replay. Give them a try NOW.

Standard	Long Play
5", 600 ft. . . . . 16/-	5", 900 ft. . . . . 18/6
7", 1,200 ft. . . . . 25/-	5 1/2", 1,200 ft. . . . . 23/6
Please add 1/- post to orders.	7", 1,800 ft. . . . . 35/-

## HEADPHONES

Lightweight 4,000 ohms headphones for crystal sets, transistor sets, short-wavers, etc. Boxed and new 15/- . Siemens-Ediswan type (usually 45/-) 22/6. Brown's popular type "F" 37/6. Ericsons as recommended by Eddy-stone £2.15.0. Add 1/- post to all orders.



# The Radio Constructor

Incorporating THE RADIO AMATEUR



AUGUST 1960

- 14 Suggested Circuits No. 117: A Touch-Plate or Proximity Detector, by G. A. French
- 18 In Your Workshop
- 24 Can Anyone Help ?
- 25 Understanding Television, Part 31, by W. G. Morley
- 34 Choosing a Valve, by J. B. Dance, M.Sc.
- 38 Comparing A.C. and D.C. Voltages for Meter Calibration, by P. G. Wright
- 40 A Portable Service Oscilloscope, Model OS-1, by G. J. Stone
- 49 Low-Power Transmitter Modulator, by D. Noble, G3MAW, and D. Pratt, G3KEP
- 51 A Console Recorder for Musique Concrète and Electronic Music, by F. C. Judd, A.Inst.E., G2BCX
- 54 RTTY—In Theory and Practice, Part 4, by J. B. Tuke, G3BST
- 58 A High Sensitivity Shorted Turns Tester, designed by M. G. Roberts
- 62 Radio Topics, by Recorder
- 65 Winding Coils and Small Chokes, by "Quench Coil"
- 66 Alternative Band III Pre-Amplifier, by A. S. Carpenter
- 68 A Photo-Transistor Switch, by K. Berry

Vol. 14, No. 1  
 Published Monthly

Annual Subscription 25/-  
 (including postage)

Editorial and Advertising Offices  
 57 MAIDA VALE LONDON W9

Telephone  
 CUNningham 6141  
 (2 lines)

Telegrams  
 Databux, London

© Data Publications Ltd

CONTENTS may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgment of source is given.

CONTRIBUTIONS on constructional matters are invited, especially when they describe the construction of particular items of equipment. Articles should be written on one side of the sheet only and should preferably be typewritten, diagrams being on separate sheets. Whether hand-written or typewritten, lines should be double spaced. Diagrams need not be large or perfectly drawn, as our draughtsmen will redraw in most cases, but all relevant information should be included. Photographs should be clear and sharp. Details of topical ideas and techniques are also welcomed and, if the contributor so wishes, will be re-written by our staff into article form. All contributions must be accompanied by a stamped addressed envelope for reply or return, and should bear the sender's name and address. Payment is made for all material published.

OPINIONS expressed by contributors are not necessarily those of the Editor or the proprietors.

TRADE NEWS. Manufacturers, publishers, etc., are invited to submit samples or information of new products for review in this section.

TECHNICAL QUERIES must be submitted in writing. We regret that we are unable to answer queries, other than those arising from articles appearing in this magazine; nor can we advise on modifications to the equipment described in these articles.

CORRESPONDENCE should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers, as appropriate.

REMITTANCES should be made payable to "DATA PUBLICATIONS LTD."

AUGUST 1960

13





feeds the anode load of  $V_{1(a)}$ , the section bypassed by  $C_8$  which supplies the anode loads of  $V_{1(b)}$  and  $V_{2(a)}$ , and the section (providing an unsmoothed voltage immediately after h.t. rectification) which feeds the anode circuit of  $V_{2(b)}$ . In addition to providing adequate decoupling, it has been felt necessary to detect the signal voltage present on the anode of  $V_{2(a)}$  with the aid of the separate diode,  $D_1$ , rather than to attempt leaky grid detection on the grid of  $V_{2(b)}$  itself. In the circuit given here whatever detected signal is present on the anode of  $V_{2(a)}$  is applied as a relatively steady direct voltage to the grid of  $V_{2(b)}$ , with the result that little a.f. voltage appears across the relay coil. If leaky grid detection on the grid of  $V_{2(b)}$  were attempted, a high a.f. voltage would appear on its anode, with consequent risk of feedback. Such feedback could, of course, occur (and would be more likely to occur) for the condition when the touch-plate was not touched or approached, the signal on  $V_{2(a)}$  anode consisting only of amplified noise generated in the early stages of the circuit.

In a device of this nature, self-generated noise can be troublesome because it may achieve sufficient amplitude at the anode of  $V_{2(a)}$  for a constant and relatively high negative voltage to be permanently present on the grid of  $V_{2(b)}$ . This constant voltage would reduce the effectiveness of the circuit and might make relay operation unreliable. Much of the noise generated in the earlier stages is reduced in amplitude by the two 500pF condensers  $C_5$  and  $C_9$ . Self-generated hum may also be a problem, and a "hum-dinger",  $R_{15}$ , is included in the design in order that hum level may be reduced to a minimum. The "humdinger" slider connects to the junction of  $R_{16}$  and  $R_{17}$ , at which point there is a positive potential of approximately 17 volts above chassis.

A final point concerns the crystal diode employed in the  $D_1$  position. It is possible for this component to have high inverse voltages applied to it and it is necessary to specify a diode having a high maximum inverse voltage rating, such as the OA91.

### Practical Points

The circuit should not cause any difficulties in construction provided that care is taken with layout. The stages should be positioned "in-line"; that is, the grid components of  $V_{1(a)}$  should be at one end of the chassis and the mains transformer at the other, with the anode circuit of  $V_{2(b)}$  next to it. Intermediate components in the circuit then take up intermediate positions on the chassis. Protection against hum pick-up from the heater wiring should be necessary in the  $V_1$

stages only, and it would be very desirable to employ twisted wiring dressed close to the chassis in feeding the heater of this valve. Twisted heater wiring to  $V_2$  and the "hum-dinger" should not be essential; but its use would be an added safeguard. All cathode bypass condensers should be mounted close to the valveholder tags to which they connect. The two electrolytic condensers,  $C_8$  and  $C_{13}$ , may consist of a dual component mounted at the power unit end of the chassis.  $C_2$ , however, would preferably be a separate component mounted close to  $V_{1(a)}$ .

It will be noted that  $V_1$  is screened as, also, is  $V_{1(a)}$  grid circuit. It is especially important to keep heater wiring well away from  $V_{1(a)}$  grid wiring. Provided care is taken in this respect it is probable that it will not be necessary to provide any screening around the sensitivity control,  $R_1$ , other than that given by connecting the metal work of this control to chassis, with its tags projecting outside the screening thereby provided. If a conventional coaxial socket is employed for the input connection it may be possible, here also, to dispense with any screening of the centre tag which projects back into the chassis. The series condenser,  $C_1$ , will, on the other hand, need to be completely screened, this being done either by putting it into a metal or foil tube or by using a metal cased component and connecting the case to chassis. The screening on the leads connecting together the components in the  $V_{1(a)}$  grid circuit should extend close to the points to which their inner conductors connect. The grid circuit of  $V_{1(b)}$  is liable also (but to a lesser extent) to pick up hum. In this case wiring should be short and kept well away from heater leads.

The diode  $D_1$  has a maximum inverse voltage rating which increases as the ambient temperature around it reduces. It should, in consequence, be mounted in a relatively cool part of the chassis.

The relay in the anode circuit of  $V_{2(b)}$  may be any conventional type capable of energising at the maximum anode current of  $V_{2(b)}$ . As calculated under the circuit conditions shown here (and assuming zero signal due to noise at the anode of  $V_{2(a)}$ ) this current is of the order of 10mA. Such a current, for an anode voltage of 200, approaches the maximum rated dissipation of the valve; and it would be advisable to employ a relay capable of energising at some 7 to 8mA, rather than at 10mA, so that energising current is "in hand" without the risk of over-running  $V_{2(b)}$ .

For most reliable operation, the chassis of the unit should be connected to earth.

### Setting Up

After the device has been constructed it is necessary to test and set it up. The process

of testing is carried out initially with no connection made to the input socket. A loudspeaker, connected via a conventional step down speaker transformer, is then coupled across  $R_9$  so that initial performance may be checked aurally. The test loudspeaker should be fitted in a cabinet or on a baffle so that it gives adequate response at the lower frequencies.

The unit should be switched on and the sliders of  $R_1$  and  $R_8$  set to the tops of their tracks. Under this condition, background hiss with, perhaps, a trace of hum should be audible from the speaker. The slider of  $R_{15}$  should then be adjusted for minimum hum. Especial care should be taken to listen for hum at the fundamental frequency of 50 c/s. Some people find this frequency difficult to hear even when its presence can be felt by lightly resting the fingertips on the cone of the loudspeaker.

The centre contact of the input socket should now be approached by the finger. It should be possible, as the finger closely approaches the centre contact, to hear an obvious increase in hum. When the finger touches the contact, there should be a very obvious increase in hum level.

When the device has been checked in this manner and appears to be satisfactory, the test loudspeaker should be disconnected. It next becomes necessary to ensure that  $V_{2(b)}$  is working under satisfactory conditions. This may be done by measuring its anode current, either by inserting a milliammeter in its anode circuit or by measuring the voltage dropped across its cathode resistor or the relay coil and evaluating current by means of Ohms Law. With  $R_{12}$  short circuited the current drawn by  $V_{2(b)}$  should be of the order of 10mA (differences from this figure being given by valve spread, and variations in h.t. voltage, coil resistance of the relay and, within the tolerance specified, value in  $R_{14}$ ). The short circuit across  $R_{12}$  should next be removed whereupon the self generated noise and hum in the amplifier will be passed, in rectified form, to the grid of  $V_{2(b)}$ . Anode current in  $V_{2(b)}$  may, in consequence, drop slightly.  $R_{15}$  should next be finally adjusted for maximum anode current in  $V_{2(b)}$  (corresponding to minimum self-generated hum in the amplifying stages). If the drop in anode current after removing the short circuit from  $R_{12}$  is sufficiently high to prevent satisfactory relay energising,  $R_{14}$  should be reduced in value (to a minimum of 82Ω) until the desired anode current is obtained. If it is considered that noise (evident as hiss in the previous loudspeaker test) is being especially troublesome in reducing anode current in  $V_{2(b)}$ , its effectiveness may be reduced by fitting an additional condenser (having a value between 500pF and 0.01μF)

between  $V_{2(a)}$  anode and chassis. If, on the other hand, it is considered that self generated hum (again aurally evident in the previous loudspeaker test) is causing excessive reduction in  $V_{2(b)}$  anode current, the efficiency of the screening in the input grid circuit, and other possible causes of hum, should be checked. It is possible to reduce the effect of hum and noise by adjustment of the pre-set sensitivity control  $R_8$ , but this step should only be taken when it is felt that no improvement can be effected elsewhere. Adjustment of  $R_8$  at this stage causes a reduction in overall sensitivity. If  $R_8$  is adjusted, it should be set to the position which causes the output valve to pass a satisfactory relay energising current with  $R_{14}$  reduced to 82Ω.


### The Touch-Plate

The touch-plate is connected to the input terminal of the device via good quality screened cable kept well away from un-screened mains wiring. It is difficult to specify a maximum length for the screened cable but it would be advisable to set a limit, during initial experiments, of some 10ft, this being increased later, if desired, in the light of experience. Some of the more inexpensive types of television coaxial cable may, incidentally, be unsatisfactory for this application due to coarse mesh in the outer braiding. A useful check of the efficiency of a particular type of cable consists of re-connecting the loudspeaker across  $R_9$  and checking whether hum level increases when the outside insulation of the cable is firmly grasped by the hands. (The hands should not be allowed to make electrical contact to the screening during this test, as they will then become "earthed" and unable to pass any hum pick-up signal to the inner conductor.) A satisfactory cable will allow no increase in hum level to occur.

Provided that the touch-plate is kept well away from mains fields, and a satisfactory screened coupling cable is employed, their connection to the input socket of the detector should cause negligible increase in hum pick-up. Slight increases may be taken up by re-adjustment of  $R_8$ .

The touch-plate itself may consist of any metal plate having an area between 1 and 6 sq. ins. A touch-plate with too large an area will tend to pick up hum of its own accord. It should be well insulated from earth. (An alternative to a plate, which may be worthy of experiment, would be provided by a foot or two of thin gauge wire.) When the touch-plate has been connected the sensitivity control,  $R_1$ , is adjusted to give the desired degree of sensitivity according to whether the relay is to operate on touch or close proximity.

*continued on page 24*

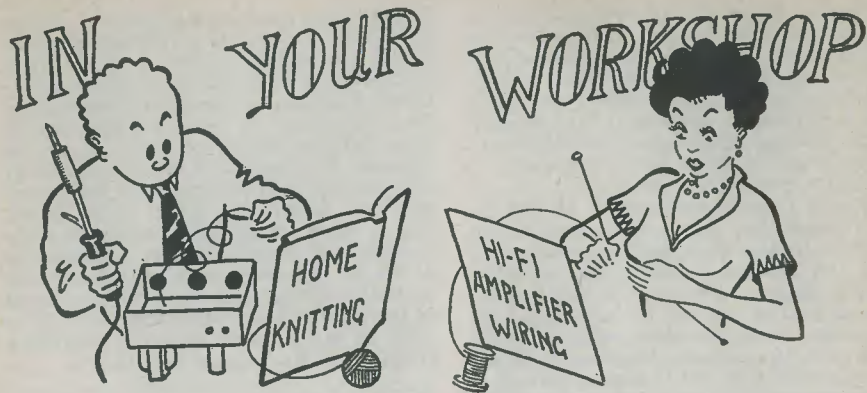

This month Smithy the Serviceman and his able assistant, Dick, go through a complete servicing exercise clearing a fault in the flywheel sync circuits of a television receiver

"THERE ARE TIMES", SAID SMITHY, AS HE walked over to Dick's bench, "when I feel that sets with flywheel line sync circuits are something of a bore."

Dick looked a little startled. The greatest condemnation that Smithy ever expressed on any aspect of servicing was to call it a "bore".

"I'm awfully sorry, Smithy," he said meekly, "but I've done everything I can think of to do the repair myself."

"Not to worry, lad," said Smithy comfortably. "I don't blame you at all. It's just that line flywheel sync circuits tend to have more obscure faults than do any other parts of a television set."

He looked with disfavour at the screen of the 17in receiver on Dick's bench. It presented an excellent picture which was marred only by a random horizontal jitter. For several seconds at a time the picture remained reasonably steady, after which it would suddenly jump sideways for half an inch or so and continue jittering horizontally with varying degrees of displacement until, after some further moments, the movement ceased and the picture again became reasonably steady.

"Irritating, isn't it?" said Dick.

"Well, at least", remarked Smithy philosophically, "it's an intermittent which seems to be present more or less all the time!"

#### Recapitulation

The Serviceman sat down heavily alongside his assistant.

"Right," he said. "Before going any further, let's recap on what has happened already. That'll help to get our minds clear."

"Okey-doke," replied Dick. "Here's the story up to date. The set came in with a customer complaint, which I thought very apt, of a 'flickering picture'. I hitched it on to the mains and found it gave exactly the same effect as we're seeing now. I recognised the set as a fairly recent model having flywheel sync and, before taking the chassis out of the cabinet, I substituted the valves in the flywheel sync and sync separator circuits for known good ones. There was no improvement so I put the old valves back. I wasn't going to lug out the chassis when it might have been a valve elsewhere, so I next tried swapping the line output valve and booster diode. But this gave no joy and I put the old ones back there, too."

"I think that's a very fair procedure," commented Smithy. "Any of the valves you mention could conceivably cause the jitter, and it would be silly to go to all the trouble of removing the chassis without exhausting the possibilities in that line."

"The story continues," said Dick, pleased with Smithy's approval, "and we next see the mad professor sitting quietly in his laboratory, pondering over the intricate equipment ranged about him."

Smithy cocked a suspicious eyebrow.

"I mean", continued Dick hastily, "that I was pondering. Now, although the set was giving this jitter all the time there were no flashes or changes of contrast, and no

crackles or alterations in volume from the loudspeaker. So I ruled out, fairly confidently, that the power supply was O.K., and I didn't worry my head over the rectifier and its associated components. I did feel, though, that there was a faint risk that there might be a dicky connection to the deflection coils, and so I next waggled the leads which connected to these; but with no success. I finally bunged a yard or so of flexible wire into the centre connector of the coaxial aerial socket and held it near the chassis. I still got a picture capable of being recognised with this apology for an aerial, but I got no splashes on the screen which would indicate sparking in the line output stage. Including, especially, sparking in the line output transformer or deflector coils."

"Very good," commented Smithy. "You're really inspired this morning."

"This is one of my better days," said Dick, modestly, "when I am able to slough off the heavy domestic burdens and responsibilities which continually clatter about my slim and youthful shoulders, and am able to concentrate with undiminished power upon my work."

"The only domestic burden you've ever had", exploded the Serviceman, "has been the choice between green suede shoes with one inch or with one-and-a-half inch crepe soles."

"The one-and-a-half inch soles", Dick pointed out, "give better insulation. Anyway, having found that there were no splashes on the screen with my makeshift aerial—and having noticed incidentally that, even with such an aerial, the jitter was still present—I made my big decision of the day and, as the Americans put it, pulled the chassis."

Smithy nodded approvingly.

"I next", continued Dick, "lightly waggled the leads of the chassis components in the flywheel sync circuit to see if I could stumble on a cold joint type of fault but, once again, I had no luck." He paused, scratching his head. "Now what did I do next?"

"You called out for me," chuckled Smithy.

"So I did! Your first remark was to see whether the jitter existed on the other channel. Which it did. But I didn't understand why you asked me to make that particular check."

"Never mind," said Smithy, "Carry on."

"You next told me to do two things. First of all, to check any h.t. electrolytic which decoupled the line output stages or flywheel sync circuits or both. And this I did; but the jitter still remained."

"I heard you," interjected Smithy disapprovingly. "One of these days I'm going to impound that 100 $\mu$ F test-condenser-cum-detector you so dearly love to splash across

h.t. circuits. You know, 16 $\mu$ F or so is quite enough for that sort of thing."

"Secondly", Dick sailed on, "you suggested checking the line hold potentiometer for bad contact between the slider and the track, or for a worn track."

"Yes, that's right," confirmed Smithy. "Both bad decoupling electrolytics and crackly line hold pots have given me this sort of jitter in the past. How did you check the pot?"

"Well," said Dick, "I didn't go to the trouble of wiring in another as it was much easier to open up the existing one and examine its innards. Both the slider and track looked O.K. and I decided to put a spot of Electrolube on the latter just to make sure. I reasoned that if the connection between the slider and the track were poor the Electrolube mightn't effect a permanent repair, but it would at least give such an obvious immediate improvement that I could at once condemn the pot."

"That's a good idea," approved Smithy. "You are on form today!"

#### Logical Search

But, this time, Dick did not respond to the Serviceman's praise.

"Not really," he remarked disconsolately, "because I've come to the end of the story. I've tried all my own ideas, and I've tried your suggestions, and now we're up to the present time. And we've still got horizontal picture jitter."

He glared malevolently at the set.

"Don't take it too much to heart," said Smithy. "I said earlier that flywheel sync circuits became a bit of a bore every now and again, but that's only because it's so much more difficult to localise awkward faults in them than it is in other television circuits. There are two approaches now open to us. One consists of going mad and replacing every component in the whole circuit until we find the one which is causing the trouble. The other consists of putting our thinking caps on and attempting to track it down logically. I think we'll try the second approach. Hand me the service manual."

For once, Dick actually had the service manual for the receiver he was repairing in front of him; and he handed it over to Smithy without comment. Smithy studied it for a few moments.

"Well, it's not so bad," he remarked. "It uses a basic circuit arrangement common to practically all flywheel sync circuits which employ reactance valves, and it's of a type which was especially popular up to a year or two ago. The fundamentals of the circuit can, in fact, be drawn out quite easily in block form. (Fig. 1.) We have first of all a

tuned circuit sine wave oscillator which, when all is working correctly, runs at line frequency. The output of this oscillator goes through a shaping circuit which gives it enough of a square wave or sawtooth characteristic to enable it to be fed to the grid of the line output valve. You will remember that the average line output valve only needs to become conductive about a third of the way along the scan so, provided the waveform allows this to happen and goes sharply negative at the end of the scan, it can have any old shape within reason you like. The shaping circuit, incidentally, can be in the oscillator valve itself: if you make the cathode and grid of a pentode act as an electron coupled oscillator and have a low-value anode load, limiting action will give you a square wave of sorts at that anode."

"Right!" continued Smithy. "Another output from the oscillator goes to a block which we'll call the 'comparator'. Also applied to the comparator are line sync pulses from the sync separator. The comparator compares the frequencies of the sync pulses and the sine wave oscillator, and generates a control voltage accordingly. If the sine wave oscillator is running at a higher frequency than the sync pulses, the comparator provides, say, a positive going control voltage, and if it is running at a lower frequency, a negative going control voltage."

"Or vice-versa?"

"Or vice-versa. Which way the control voltage goes depends on overall design and doesn't concern us here. Also fed into the comparator is a variable d.c. voltage from the line hold control. Adjusting the line hold control varies the centre control voltage from the comparator, and enables you to get the whole system on its correct operating point."

"It's getting a bit complicated now," complained Dick.

"Stay with it a little longer", grinned Smithy, "it gets easier from now on! I had better quickly add, before going any further, that I described the comparator as such since this part of the circuit is liable to vary in principle and design from set to set. Because of this, I used the blanket term 'comparator'."

"Well, I can understand that!" said Dick.

"Fair enough," chuckled Smithy. "Now we next apply the control voltage to a reactance valve. A reactance valve is one which has been made to function as a capacity or inductance by connecting a 90° phase-shift coupling between its anode and grid. Voltage and current in the anode circuit then flow 90° out of phase, just as they would do in a condenser or an inductance. A simple and cheap phase-shift coupling can be provided by connecting a condenser between anode and grid, where-

upon the anode and cathode of the valve appear to an external circuit as a capacity. And you can vary that capacity by varying the bias on the grid."

A light of understanding was beginning to shine in Dick's eyes.

"You next", continued Smithy, "couple the variable capacity provided by the reactance valve across the sine wave oscillator tuned circuit, and you apply the control voltage from the comparator to its grid . . ."

"With the result", broke in Dick quickly, "that the whole thing becomes similar to an automatic frequency control system. If the sine wave oscillator runs faster than the sync pulse frequency, a control voltage is generated which varies the capacity provided by the reactance valve, and slows the oscillator down again. And if the sine wave oscillator runs slower than the sync pulses the control voltage brings it up again."

"You've got it," said Smithy. "And you set the whole business up initially by putting the line hold control in the middle of its travel and tuning the sine wave oscillator, with the aid of a slug in its coil, so that it's running exactly at line frequency. Minor deviations, caused by ageing and so on, can then be taken up by the line hold control potentiometer."

Dick's gleam of comprehension was replaced by a frown.

"But where does the flywheel business come in?"

"Ah," grinned Smithy. "The flywheel is provided by a resistor and a condenser! I've put them in my sketch but haven't drawn attention to them yet. The control voltage from the comparator passes through the filter given by the resistor and condenser with the result that there is a time delay, dictated by the time constant of the filter, before changes in control voltage affect the reactance valve. The filter provides the essential flywheel action because, if a spurious pulse caused by interference is passed to the comparator the resulting change in control voltage is not fed to the reactance valve immediately, and the sine wave oscillator runs on at the same speed. With direct sync the line time base would have been triggered by the spurious pulse and would have taken a line or two more to settle down again. With flywheel sync the sine wave oscillator presses serenely on at its own frequency, being capable of alteration at slow rates only."

Dick grimaced at the receiver on the bench which, during Smithy's explanation, had not ceased to exhibit its random line jitter.

"I wish", he remarked, "that the line

oscillator in that set was pressing serenely on!"

"We'll get down to the set in a jiffy," remarked Smith. "There are just two more points I want to deal with. Firstly, in many practical circuits you may find more than one resistance-capacity filter delaying the application of the control voltage to the reactance

### Fault-Finding

Smithy lit a cigarette.

"O.K.," he continued. "Having sorted the circuit out and spent a little time in explaining it, let's now get down to trouble shooting the line jitter in this particular set. I can think of no tool more useful to us at the present moment than a nice fat 0.5µF paper con-

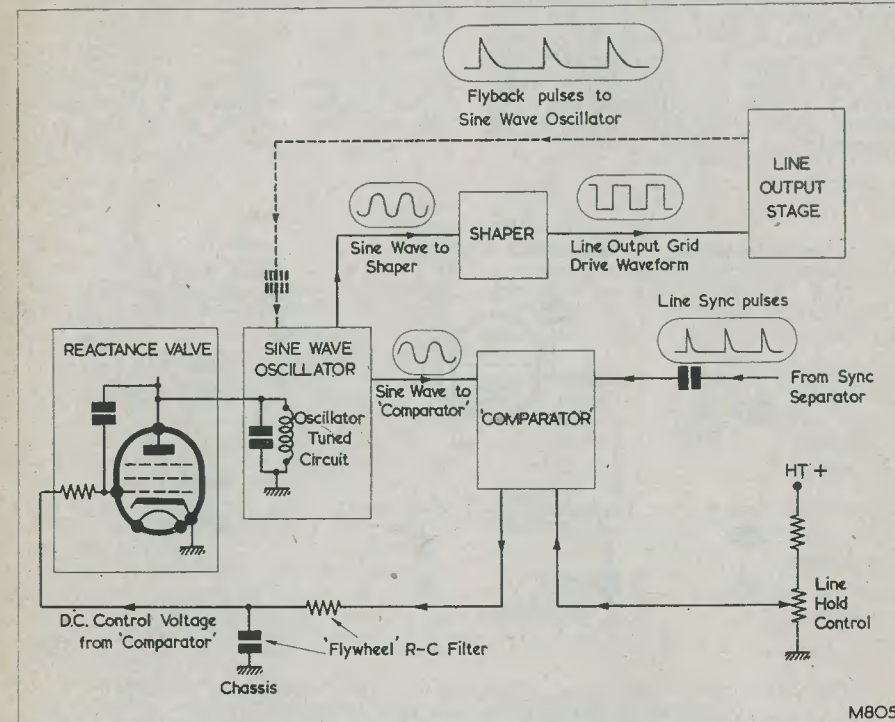


Fig. 1. A block diagram illustrating the operation of line flywheel sync circuits employing reactance valves. The flyback pulses from the line output stage to the oscillator are applied regeneratively to sharpen the line output grid waveform, the coupling being shown in dotted line since feedback of this type is not used in all receivers. Usually, the sine wave oscillator and shaper operations are carried out in one valve. In practice the anode of the reactance valve will carry an h.t. voltage, whereupon its connection to the oscillator tuned circuit will be via a blocking condenser. Alternatively, the earthy end of the oscillator tuned circuit may be connected to h.t. positive, being by-passed to chassis by a decoupling condenser

valve. However, the overall effect is just the same. The second point is that, in some circuits, a small flyback pulse from the line output stage is fed back, in a regenerative manner, to the grid or anode circuit of the sine wave oscillator in order to sharpen up the flyback pulse passed to the line output grid. Such a circuit is employed in the receiver we have here, and have I shown it in my sketch."

denser with no leaks in it. Sort one out, Dicky boy!"

Smithy's assistant rummaged in the spares cupboard and produced a brand new component.

"That's what I like to see," approved the Serviceman. "A condenser with a nice clean wax overcoat which has been sullied only by your own grubby fingerprints!"

Now that he was actively coming to grips with the line jitter, Smyth's previous disgruntled mood had vanished as if by magic: he had become, indeed, positively jubilant.

"We must first assume", he announced, "that the jitter is being caused by an intermittent connection which may quite probably be in a component. Now, this intermittent connection could be in the sync separator circuits, whereupon it could cause such widely varying control voltages to be given by the comparator that even the time delay filter can't smooth them out. So, let us kill the sync! This we do by popping our 0.5 $\mu$ F condenser across the sync input to the comparator and chassis."

"No luck there," said Smyth. "The jitter isn't coming in from the sync separator. Incidentally, in some sets the application of my 0.5 $\mu$ F condenser might have so affected the sine wave oscillator that you wouldn't be able to get back on line frequency within the range of the line hold control. In such an instance you'd have had to open the circuit from the sync separator in order to kill the sync."

"What's the next step?"  
 "Well, we now know that the sync separator's above suspicion, so let's carry on to the comparator section. If there were a bad intermittent in this section this could also cause horizontal jitter despite the

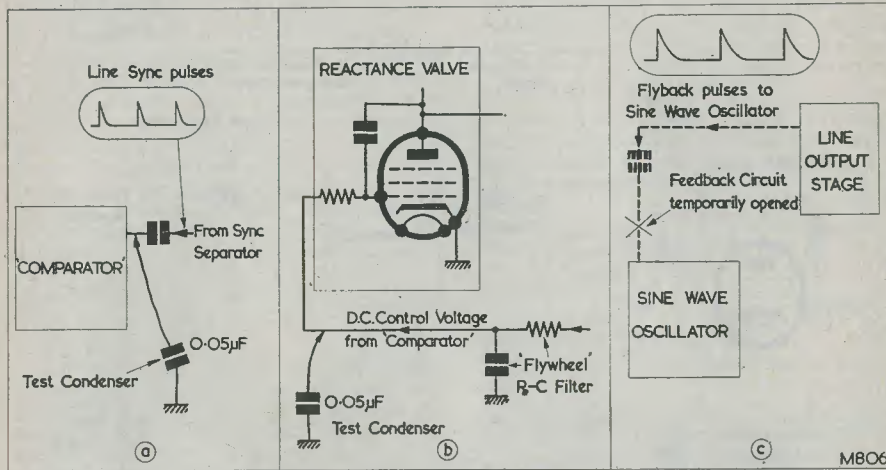


Fig. 2 (a) Smyth's first check, in clearing line jitter, consisted of temporarily by-passing to chassis the line sync input to the comparator  
 (b) Connecting the test condenser between chassis and the d.c. control voltage line checked for intermits in the comparator circuits and the R-C filter  
 (c) Opening the flyback pulse feedback circuit ensured that jitter was not being fed back from the line output stage

Smyth applied his condenser (Fig. 2 (a)), whereupon the picture on the screen went immediately out of lock.

"If you carefully turn the line hold control a little", Smyth told his assistant, "you'll be able to get the sine wave oscillator running at line frequency."

Dick carefully adjusted the control and was able to resolve the unsynchronised picture fairly satisfactorily on the screen. Despite the fact that it was continually passing slightly in and out of true horizontal synchronism, both he and Smyth could see that the line jitter remained. Smyth removed his condenser, whereupon the picture jumped back to its previous condition.

smoothing action of the resistance-capacity filter. Alternatively, there might be a fault in the filter itself, with the result that it wasn't smoothing things out as well as it should do. We can check both of these eventualities by slapping our 0.5 $\mu$ F condenser between the smoothed control voltage and chassis."

Smyth re-applied his condenser, (Fig. 2 (b)), causing the picture to jump momentarily as the condenser charged to the control voltage. The picture reverted almost instantaneously to its original condition, and it still had the jitter.

"Well, that's not too bad," commented Smyth. "If the jitter had stopped or reduced

when I connected the condenser I would have started looking in the comparator circuits or in the resistance-capacity filter for intermittent connections. But as no change occurred we can continue to look elsewhere."

"What about the pulse fed back from the line output stage?"

"You know, that's not entirely above suspicion, either," remarked Smyth. "Unfortunately, I'd probably gum up the oscillator works if I tried to eliminate it with the 0.5 $\mu$ F condenser. In this case we'll have to open the circuit coupling the pulse back to the oscillator. Don't forget that this operation will cause us to lose the sharp flyback pulse on the line output grid."

Smyth switched off the receiver and disconnected one end of the condenser, coupling back the pulse from the line output stage. (Fig. 2 (c).) He switched on again, keeping his hand on the switch in case there was evidence of line output transformer overload. After a few moments a dim picture, indicative of low e.h.t., appeared on the screen. It was still accompanied by the line jitter. Smyth switched off quickly.

"Well, that didn't stop the jitter," he remarked as he re-soldered the coupling condenser into circuit. "By the way, I switched off quickly just to be on the safe side. I don't know what condition this particular line output stage operates in without proper drive, and I didn't want to take any risks."

Smyth switched the receiver on again and, as its screen displayed the same jittering picture as had appeared before his last experiment, he and Dick returned to the service manual.

"It's a pretty safe bet", said Smyth, "that due to our process of elimination we have now narrowed our search down to an intermittent in the reactance valve circuit or the sine wave oscillator circuit. There aren't all that many components to play about with here, and after a quick check for poor connections, we can start by substitution of components in order of unreliability. Rough check, this would put resistors of 1M $\Omega$  and up first, condensers second, and anything you like to follow."

"Well, the wiring seems O.K.," said Dick, making a careful visual check, "so perhaps we'd better start on components. To begin with, there's a 1M $\Omega$  grid leak to the oscillator."

"Fair enough," said Smyth. "Swop it."  
 Dick replaced the resistor and switched on again. The jitter remained.

"O.K.," commented Smyth. "What's next?"

"There are no more resistors of 1M $\Omega$  and up," said Dick. "So I suppose we'd better have a bash at the condensers."

"Righty-ho," said the Serviceman. "Swap the easy ones first!"

"This one looks easiest," commented Dick, peering into the chassis. "It's a 50pF silvermica connected between the anode and grid of the reactance valve. Which will, of course, be the phase-shift coupling for that valve."

"Take a stab at it then, boy," remarked Smyth grandiosely.

Dick wasted no time in removing the condenser.

"Will a ceramic 50pF do as a replacement?" he called out from the spares cupboard. "Otherwise it means two 25pF silver-micas in parallel."

"Use the silver-micas," replied Smyth. "They'll have a very low temperature coefficient and that's important in this particular circuit position."

Dick carefully connected the two 25pF condensers in parallel preparatory to inserting them in the chassis.

"What's the next component to try?" he remarked, as he soldered the condensers into circuit.

"The condenser across the oscillator tuned circuit would be worth trying," said Smyth. "It's a 0.003 $\mu$ F paper. You hunt one out while the set's warming up."

Smyth switched on and Dick returned to the spares cupboard.

"This means three condensers in parallel now!" he hailed after a moment. "We've only got 0.001's in stock."

"Forget it," grinned Smyth.

Dick rushed back to the bench and looked at his receiver. The picture it displayed was now as steady as a rock.

#### Transmitted Jitter?

"Well, thank goodness for that," remarked Smyth's assistant, as he gazed happily at the set. "If you'd let me press on with that set on my own, it would still be there tomorrow! By the way, why did you ask me to check whether jitter was present on both channels?"

Smyth chuckled.

"You certainly never forget your questions," he laughed. "The point is that a lot of receivers with flywheel sync have long time constants in the flywheel filters, these extending to at least a frame or so. This set is one of them. I have a theory that, whilst such sets give perfectly steady pictures on camera and film programmes, they tend to suffer from jitter rather like that we've just seen when reproducing programmes which have been recorded on tape."

"I think I see what you're getting at," said Dick. "If the programmes are recorded on tape complete with sync pulses then mechanical shortcomings similar to 'wow' and

'flutter' in an audio tape deck will cause some of the sync pulses, together with the lines on either side of them, to be displaced out of their correct position in time."

"That's right," said Smithy. "If the receiver reproducing the picture has flywheel sync with a short time constant, say, twenty to forty lines or so, the discrepancies won't show up as badly as if the time constant is long. And, of course, they won't show up at all on receivers with direct sync."

Smithy paused.

"As I said," he concluded, "it's just a theory. Anyway, I think enough of it to suggest that if you ever start looking for line jitter on flywheel sync sets with long time constants it is a profitable exercise to ensure that it occurs with all programmes received instead of with some only. In your own particular case I assumed that the risk of having a taped programme on both channels at the same time was low."

**Next Receiver**

"I must remember that," said Dick, as he

walked over to the rack and selected another television receiver for repair.

"This one's got flywheel sync as well," he added, as he plugged it into the bench socket and switched on. After some moments the set warmed up and exhibited a picture which was perfect except for one thing.

It had line jitter.

"Try the other channel," said Smithy, wearily. "You know, Dick, these sets with flywheel sync are *really* something of a bore."

#### In Your Workshop—June Issue

In the June issue, Smithy the Serviceman was incorrect in his calculations for resistance and capacity values for a three-section phase shift oscillator. These values should

be found by:  $f = \frac{1}{2\sqrt{6\pi CR}}$ . Smithy's treat-

ment would have been correct if the individual sections were isolated (say by valves); but in the circuit given each section is affected by the next.

## Can Anyone Help?

*Requests for information are inserted in this feature free of charge, subject to space being available. Users of this service undertake to acknowledge all letters, etc., received and to reimburse all reasonable expenses incurred by correspondents. Circuits, manuals service sheets, etc., lent by readers must be returned in good condition within a reasonable period of time.*

Radio Receiver Unit type 5019; Ref. 110D/147.—G. M. King, 126a Portsmouth Road, Woolston, Southampton, Hants, would like to receive information, together with a circuit diagram, showing how this equipment may be converted into a Short wave communications receiver.

Hallcrafters Sky Buddy Receiver.—J. Parsons, 31 Cootes Lane, Middleton-on-Sea, Nr. Bognor Regis, Sussex, is urgently in need of the manual or circuit diagram of this receiver.

Signal Generator TF390G.—H. Lunson, 17 Tongdean Rise, Brighton, Sussex, would like to buy or borrow instruction manual and circuit diagram for this Marconi instrument.

Manuals and Circuits.—C. E. Woodrow, Haxted Mill-Edenbridge, Kent, would like to buy or borrow these for the following equipment—Bendix MN26 Radio Compass, RCA receiver CRV46151, a unit of aircraft radio equipment ARB. Mr. Woodrow has available manuals and circuits of the larger Bendix radio compass BC433 (SCR269) and of the DF circuits of the R1155—he would be pleased to lend these to any interested reader.


Ekco TV Model TU141 and TU142.—J. E. V. Henty, 24 Edward Way, Ashford, Middlesex, would be very grateful to receive, on loan or purchase, service sheets of these t.v. receivers to help solve problems which have arisen with both sets.

### SUGGESTED CIRCUITS

(continued from page 17)

In some locations it may be found that the random radiated hum level due to mains wiring is low and that a low signal is, in

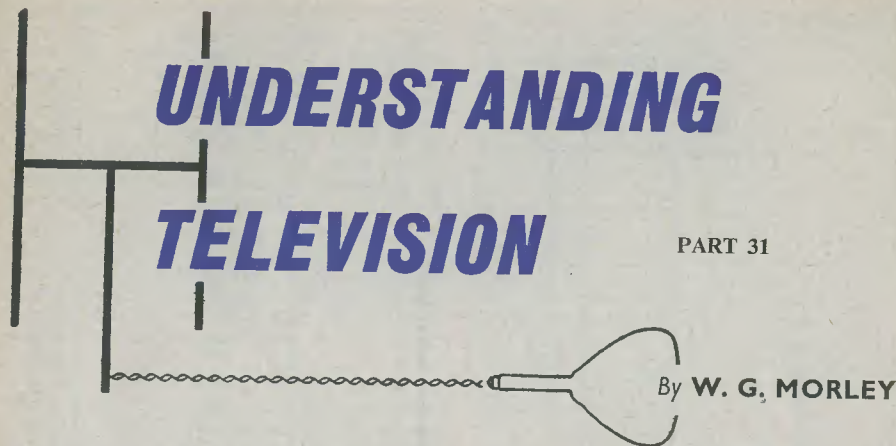consequence, passed to the detector when the touch-plate is approached or touched. The radiated hum level in such instances may be markedly increased by fitting an insulated wire connected to the live side of the mains some five feet or so away from the touch-plate.



*The thirty-first in a series of articles which, starting from first principles, describes the basic theory and practice of television*

IN LAST MONTH'S ISSUE WE COMPLETED OUR examination of the deflection arrangements employed in television receivers. We shall now carry on to discuss the sync separator.

#### The Function of the Sync Separator

In order that the line and frame sawtooth generators of the television receiver may be kept in step with those employed at the transmitter it is necessary for the transmitted signal to carry synchronising information. This information is provided in the form of synchronising, or sync, pulses. It is the function of the sync separator in the receiver to remove the sync pulses from the transmitted signal, so treating them that line synchronising information is passed separately to the line sawtooth generator, the frame synchronising information being passed separately to the frame sawtooth generator. In *directly synchronised* receivers the line and frame synchronising information from the sync separator is presented to the sawtooth generators in the form of pulses and these initiate flyback. In receivers employing *flywheel sync* circuits the frame sawtooth generator, as in *directly synchronised* receivers, has its flyback initiated by the pulses passed to it by the sync separator; but the line sawtooth generator is synchronised in a different manner. Flywheel sync circuits are discussed later.

Fig. 13<sup>1</sup> illustrates the manner in which synchronising information is added to the transmitted signal employed in the British 405 line system. It will be seen that the

synchronising pulses take up a position below blanking level. Picture information appears between white level and black level (the latter being 5% of full amplitude above blanking level). In consequence, all sync pulse information is at a lower level than black level and does not, therefore, enter the range of signal amplitudes which modulates the cathode ray tube beam.<sup>2</sup>

Fig. 13 is concerned mainly with the frame blanking period at the end of each frame, and the synchronising waveform occurring therein. The purpose of the latter is that of initiating flyback in the frame sawtooth generator. Fig. 13 also illustrates several line sync pulses before and after the frame blanking periods. Line sync pulses appear, between the frame blanking periods, at the end of each line of transmitted picture information, and a series of such pulses is shown in Fig. 186.<sup>3</sup>

#### Sync Clipping

Fig. 187 (a) illustrates a pentode to the grid of which a signal containing positive going sync pulses is applied by way of a series condenser and grid leak. The cathode of the pentode is connected to chassis and leaky-grid action takes place, the series

<sup>1</sup> Originally published in "Understanding Television", part 3, March 1958 issue.

<sup>2</sup> This assumes an "ideal" receiver. The possibility of sync pulse information interfering with the picture presented by practical receivers is discussed in a later article.

<sup>3</sup> A fully dimensioned waveform for the 405 line system sync pulse was given in Fig. 15 of "Understanding Television", part 3, March 1958 issue.

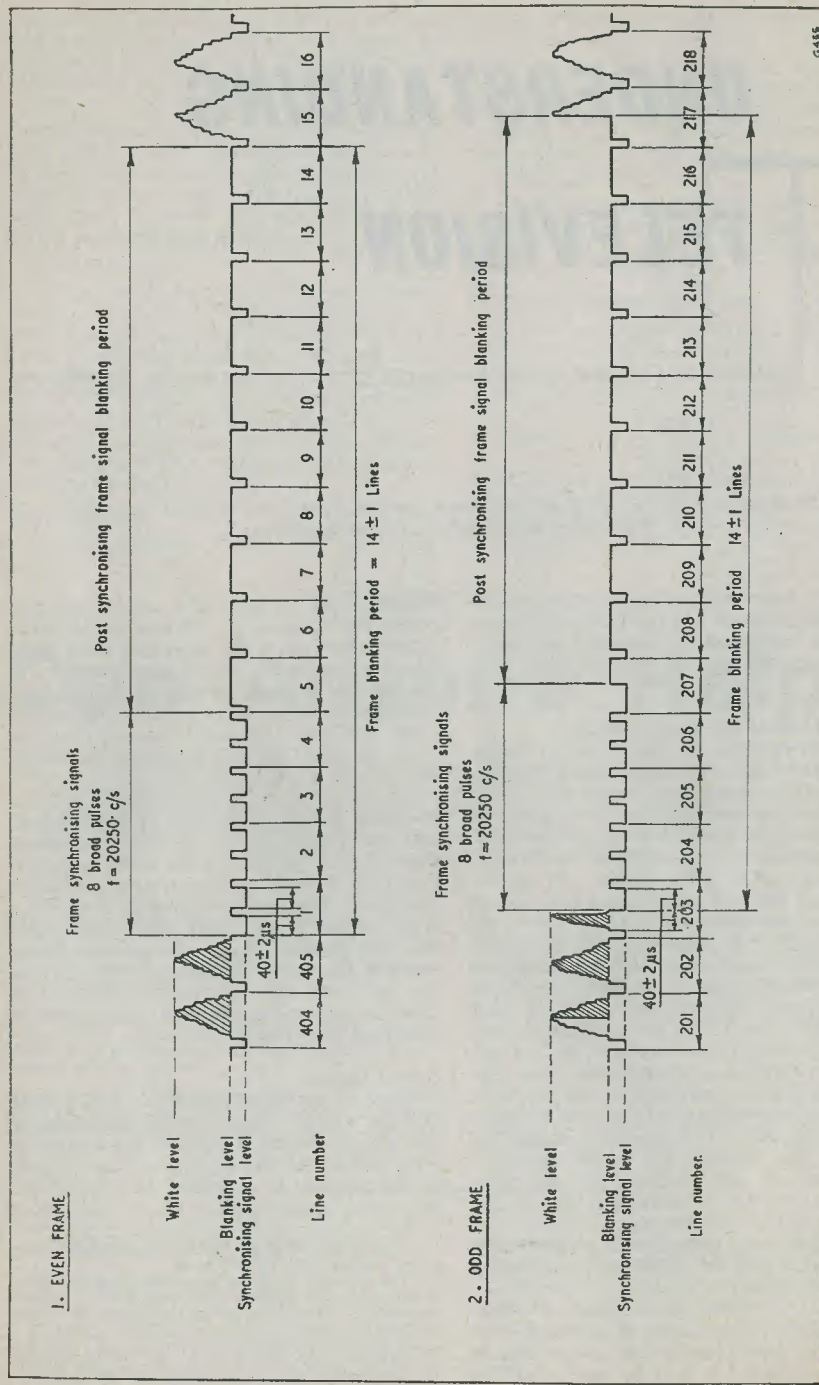


Fig. 13. Synchronising waveform of the 405 line system. The shaded part of the signal may consist either of picture information, as shown, or it may be occupied by a blanking period up to 2 lines in length

condenser taking up a charge such that the most positive parts of the input waveform (the sync pulse tips) assume a potential slightly positive of the pentode cathode. The pentode cuts off at a point approaching, but not exceeding, blanking level in the input signal, with the result that it handles no picture information. Inverted sync pulses then appear, on their own, at the anode of the pentode.

The clipping action is shown in more detail in Fig. 187 (b), wherein we see the video signal applied to the  $I_a V_g$  characteristic of the pentode. Since the picture information appears beyond cut-off point, the pentode anode current is varied only by the sync pulses.

A circuit arrangement of this nature is known as a *clipper*, the name being derived from the fact that it "clips" off, at a predetermined level, part of the signal applied to it. In Fig. 187 (b) the grid cut-off point for the pentode is identified as *clipping level*, because it is at this point that clipping of the signal takes place.

It should be noted that, to obtain pulses at the anode of the clipper, clipping level need not necessarily extend right up to the blanking level of the input signal. Indeed, it might appear at first sight, that satisfactory sync pulses would be given at the clipper anode if clipping level were as close to the sync pulse tips as, say, point X in Fig. 187 (b). In practice, however, the sync pulses passed to the sync separator tend to be rounded, as in Fig. 187 (c), and it is desirable to clip reasonably close to blanking level in order that full advantage may be taken of the vertical edges of the pulses. Another complicating factor is that, in a practical receiver, the amplitude of the sync pulses applied to the clipper may vary; due to the fact that weak video signals will, naturally, carry pulses of lower amplitude than those given by strong video signals. If clipping level were, therefore, positioned close to blanking level for the sync pulses carried by strong signals it would extend beyond blanking level and into picture information for the sync pulses given by weak signals. Under normal working conditions, the weakest video signal likely to be encountered in the receiver is that which is capable of just resolving a picture of minimum entertainment value on the cathode ray tube screen; whilst the strongest video signal likely to be encountered is that resulting from mal-adjustment of the receiver contrast control whereby an over contrasted picture (one having excessive amplitude) is fed to the cathode ray tube modulating electrode. The best compromise to cover these conditions would consist of choosing a clipping level which closely approached blanking level for

the weakest signal likely to be encountered, accepting the fact that only part of the sync pulse vertical edges would be handled for the strongest signal.

The circuit arrangement shown in Fig. 187 (a), wherein leaky-grid action with a pentode causes sync pulse information to be clipped from the composite video signal, is that which is most frequently employed in current television receivers. It has the advantage that few components are required and that sync pulses of good amplitude are available at the anode for further manipulation. The voltage at which grid cut-off occurs, i.e. the clipping level, is obviously important, and this is capable of being controlled (after the initial selection of a valve having suitable characteristics) by varying the potentials at the anode and screen-grid.

We have observed earlier<sup>4</sup> that it is desirable to feed a video signal with positive

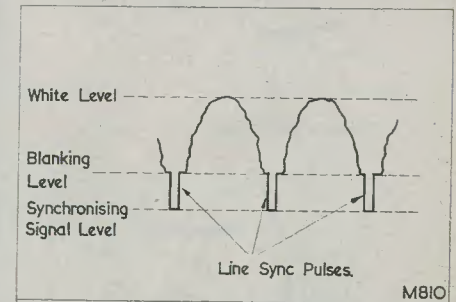


Fig. 186. Between frame blanking periods the line sync pulses appear at the end of each line as shown here

going sync pulses to the cathode ray tube modulating electrode, because this enables the associated sync separator circuit to be particularly simple and inexpensive. We may now see more clearly what that statement inferred: that feeding such a video signal to the cathode ray tube enables the simple clipping circuit of Fig. 187 (a) to be employed. If we combine the video amplifier anode circuit and the sync clipper input circuit we obtain the arrangement shown in Fig. 187 (d). This circuit arrangement is typical of current receiver practice. In Fig. 187 (d) the video signal on the anode of the video amplifier valve is applied to the cathode of the cathode ray tube and to the series grid condenser of the clipper, the negative going picture information in the signal having the polarity required for cathode modulation of the tube, and the positive going sync pulses having the

<sup>4</sup> In "Understanding Television", part 18, July 1959 issue.

polarity required for correct operation of the clipper. The series resistor shown in Fig. 187 (d) is almost always employed in practical applications, and it prevents the input capacity of the clipper valve from being

applied directly across the video output load (whereupon video response at the higher frequencies might be reduced). The value of the series resistor is normally of the order of 5 to 10kΩ.

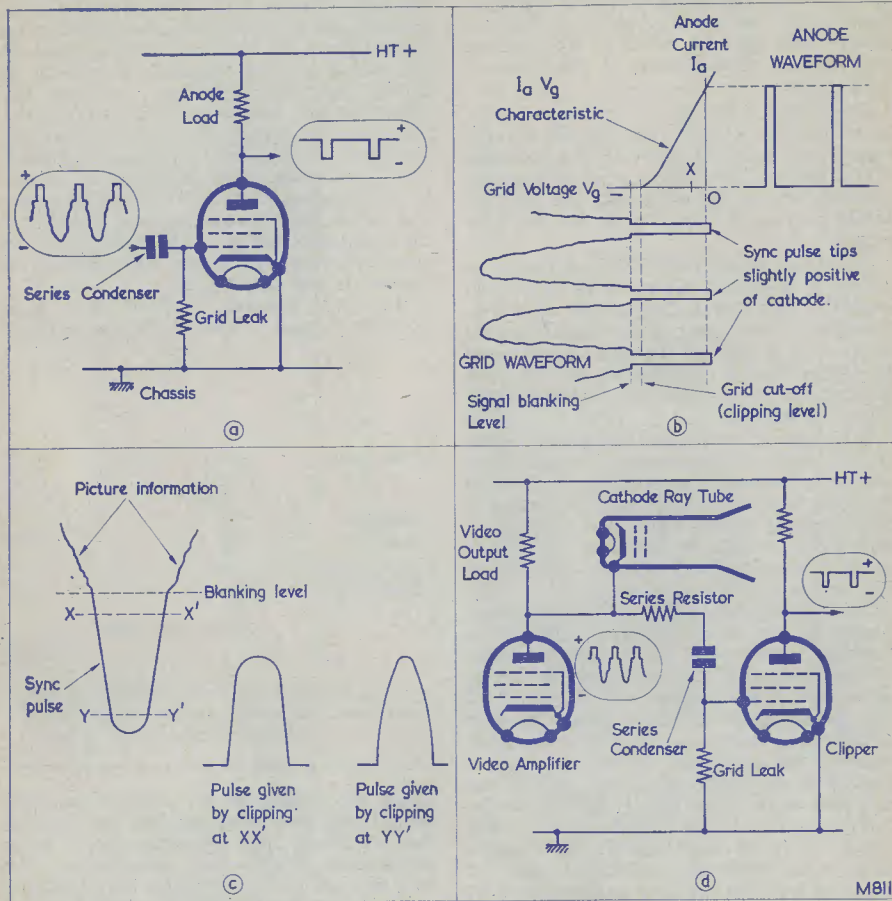


Fig. 187 (a) A sync clipping circuit. Due to the series condenser and grid leak the tips of the sync pulses take up a position on the pentode grid which is slightly positive of cathode. If the valve cuts off above blanking level the anode current is varied by sync pulses only

(b) Illustrating, with the aid of its  $I_a V_g$  characteristic, the action of the clipper valve. It may be seen that anode current is at maximum when sync pulses are present at the grid, and at zero when sync pulses are absent

(c) In practice, the sync pulses applied to the grid of the clipper tend to be rounded (as shown here in somewhat exaggerated form). It is desirable, therefore, to clip close to blanking level in order that a high proportion of the vertical edges appear at the anode of the clipper. The two pulses on the right represent those given at the clipper anode for different clipping levels

(d) When the video amplifier feeds negative going picture information to the cathode of the cathode ray tube, positive going sync pulses with good amplitude become available for the sync clipper

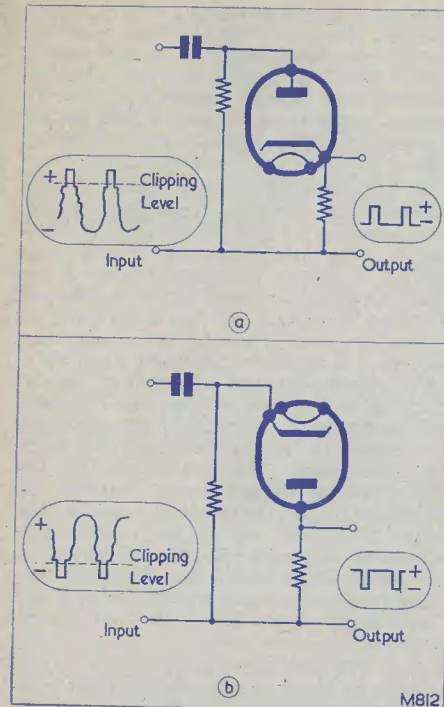


Fig. 188 (a) A simple diode clipper. If suitable values are provided for the condenser and resistors, the diode conducts in the presence of sync pulses only

(b) In this clipper circuit the polarity of the input signal and the diode of (a) are reversed

It is possible to provide clipping action by means of circuits other than that shown in Fig. 187 (a), and some of these may occasionally be encountered in practice. Fig. 188 illustrates two fairly typical examples. In Fig. 188 (a) we have a diode to whose anode is fed video information containing positive going sync pulses. In the same manner as occurred with the leaky-grid clipper, the series condenser becomes charged such that the most positive points of the waveform take up a position slightly positive of the diode cathode. In this case, however, the cathode is connected to chassis via a resistor instead of a direct connection. The result is that the cathode follows the more positive parts of the waveform applied to the anode. By judicious selection of component values in the circuit it is possible to cause the series condenser to take up a charge which allows the diode to conduct only when the input waveform is at a predetermined level above

blanking level. In consequence only the sync pulses appear across the cathode resistor, and the function of a clipper is achieved. The circuit of Fig. 188 (b) functions in the same manner as that of Fig. 188 (a), the diode and the polarity of the input waveform being reversed. In both cases, the thermionic diodes shown may be replaced by germanium or silicon diodes.

It was stated above that the sync-separation clipper is usually fed from the anode of the video amplifier valve. The main advantage of this arrangement is that, under normal conditions, the sync pulses have greater amplitude at the video amplifier anode than anywhere else in the receiver; with the result that clipper stage design and component tolerances become eased accordingly. Nevertheless, instances wherein the sync separator circuits fed from points other than the video

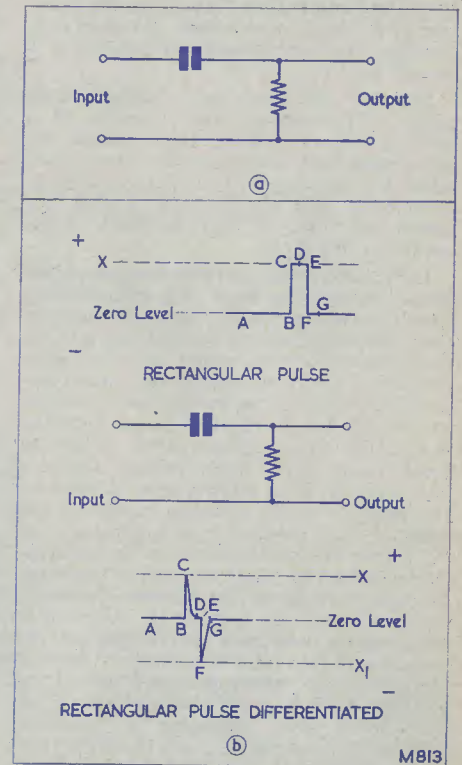


Fig. 189 (a) A differentiating circuit. The values of the condenser and the resistor are discussed in the text

(b) Differentiated pulses are given when a single rectangular pulse is applied to the input terminals of the circuit



amplifier anode may occasionally be encountered, a typical instance being where the sync clipper is fed from the video detector stage.

### Differentiation

The transmitted synchronising information in the 405 line system has the waveform shown in Figs. 13 and 186, and it appears, divorced from the picture information, on the anode of the sync clipper. As it stands, this waveform cannot be passed directly to the line sawtooth generator because the latter would fall out of synchronism during the period when the broad frame synchronising pulses are being transmitted, with the result that a number of lines in the succeeding frame would be out of position until the line sawtooth generator fell into synchronism again. It is necessary, therefore, to so process the sync waveform that the line sawtooth generator receives suitable synchronising information throughout the duration of the frame sync pulses. We shall now consider how such waveform processing is carried out.

Fig. 189 (a) illustrates a *differentiating circuit*. This consists, quite simply, of a series condenser followed by a resistor, the two components being given values which allow the condenser to discharge partly or completely into the resistor during the length, in time, of any particular pulse applied to the input.

In Fig. 189 (b) we apply a simple rectangular pulse to the input of a differentiating circuit whose component values are such that the condenser discharges completely into the resistor within the period of the pulse. Observing the input waveform, and commencing at point A, we see the input potential at a steady zero level. The output potential is similarly steady at zero level. When we reach point B the input voltage suddenly rises to point C, at positive level X. Due to the presence of the coupling condenser the output voltage similarly rises to positive level X. However, the condenser in the differentiating circuit at once commences to charge to pulse voltage via the resistor, becoming completely charged at point D. At point D the output is once more at zero level and the pulse has not yet come to an end. At point E the pulse ceases, whereupon the input voltage suddenly falls from positive level X to F, at zero level. The condenser is, however, charged to pulse voltage, with the result that, as its left hand plate drops suddenly to zero level, its right hand plate drops to negative level X<sub>1</sub>. The condenser at once begins to discharge into the resistor with the consequence that, at point G, the output voltage is at zero level again. Summing up it may be seen that, by applying the rectangular

pulse to the differentiating circuit we have obtained two spike shaped pulses, the first having the same polarity as the rectangular pulse and the second having opposite polarity. The leading edges of both spike shaped pulses have the same form as the leading and trailing edges of the rectangular pulse.

In the explanation just given it was assumed that, between rectangular pulses, both input and output voltages are at "zero level". The differentiating circuit will operate in exactly the same manner if the "zero level" of the input pulse is removed from the "zero level" of the output pulse by a fixed voltage. The only difference then occurring is that the condenser acquires a fixed charge between rectangular pulses, charging to the fixed voltage plus the pulse voltage during the duration of the pulse and discharging to the fixed voltage again after its termination. The condenser of the differentiating circuit could therefore be connected to, say, the anode of a sync clipper whilst the lower end of the resistor was connected to chassis. Rectangular pulses on the clipper anode would then cause differentiated pulses to appear across the resistor, the "zero level" of the latter being at chassis potential.

Fig. 189 (b) showed a positive going rectangular pulse. A negative going rectangular pulse would be differentiated by the circuit in just the same manner, the only dissimilarity being that the first spike shaped pulse would now be negative going and the second positive going.

### Synchronising with Differentiated Pulses

Let us now examine the sequence of events when we apply differentiated line sync pulses to the line sawtooth generator of the receiver.

In Fig. 190 (a) we see a grid waveform typical of any unsynchronised line sawtooth generator. When, in Fig. 190 (a), the grid voltage reaches cut-off potential the scan period of the associated oscillator ceases and flyback commences. In Fig. 190 (b) we apply our differentiated line pulse to the oscillator such that the first spike shaped pulse is positive going. This pulse causes the grid to rise above cut-off level with the result that flyback is initiated. The second, negative going, spike shaped pulse arrives slightly before, or shortly after, the end of the flyback

<sup>5</sup> This is true for a blocking oscillator. If the second spike shaped pulse of a differentiated rectangular pulse is fed to a multivibrator, before the end of the flyback period, it may initiate the scan period. If it is fed to a multivibrator after the flyback period, it has no effect. In consequence, it is desirable to design the multivibrator such that its flyback period is shorter than the length of the sync pulse. Occasionally, the second spike shaped pulses are clipped from the differentiated waveform.

period and it has, generally, no effect on sawtooth generator performance.<sup>5</sup> Thus, the flyback period of the line sawtooth generator oscillator is initiated by the leading edge of the first differentiated pulse, this leading edge corresponding exactly, in shape and time, to the leading edge of the original rectangular line sync pulse accompanying the picture information. The differentiated pulse may, in consequence, be used for synchronising the line sawtooth generator.<sup>6</sup>

ing signals shown in Fig. 13. Fig. 191 (a) illustrates the result of differentiation for even frames, and Fig. 191 (b) the result for odd frames. Commencing, in Fig. 191 (a), with the lines before the frame synchronising signals, we see that we obtain differentiated line sync pulses in the manner we have already discussed. In the diagram the leading edges of the line sync pulses are downward going, with the result that the first spike shaped pulse in each differentiated pair

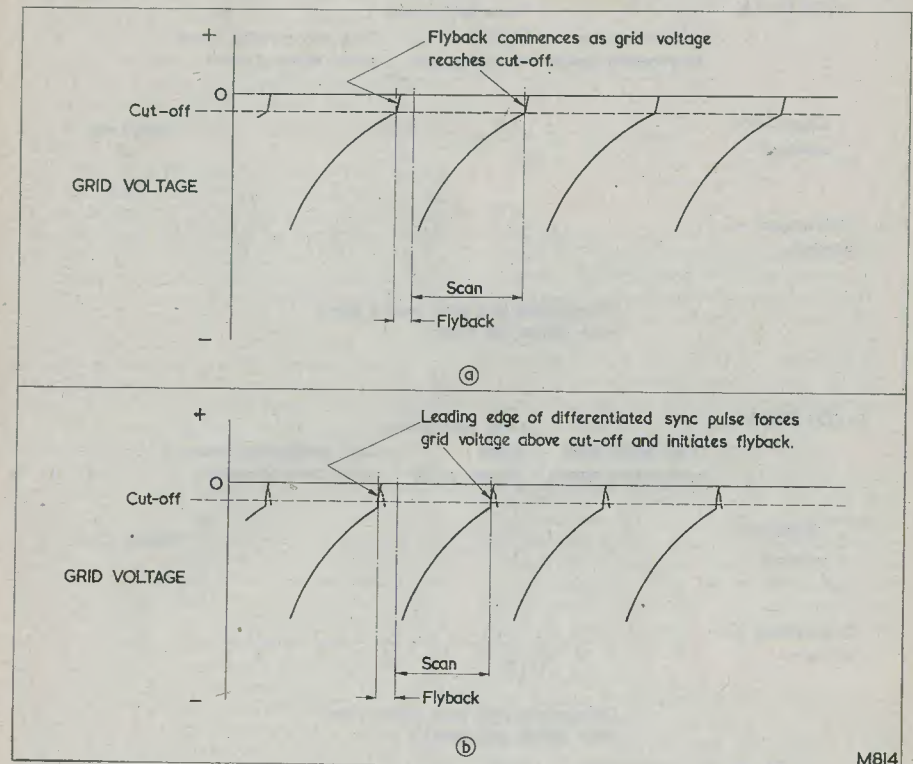


Fig. 190 (a) Typical grid waveform for the oscillator of a sawtooth generator. The flyback section is omitted in the diagram as this varies for different types of oscillator

(b) Illustrating how the leading edge of a differentiated sync pulse carries grid voltage above cut-off level, thereby initiating flyback

### Differentiating the Frame Sync Pulses

Let us now differentiate the waveforms associated with the 405 line frame synchronis-

<sup>6</sup> If the line sync pulse happens to be negative going, the first spike shaped pulse from the differentiating circuit will be similarly negative going. The line sawtooth generator may be synchronised by this negative going pulse if it is applied to a suitable point in its circuit. Synchronising with positive going and negative going pulses was discussed in "Understanding Television", parts 23 and 24, December 1959 and January 1960 issues.

is also downward going. It is the downward going spike shaped pulses which will be used to initiate flyback in the line sawtooth generator, and the upward going spike shaped pulses can be ignored.

When, at A in Fig. 191 (a), we reach the first broad frame sync pulse we have a downward going leading edge, and we obtain a differentiated pulse which is similarly downward going. The transmitted frame

sync pulse continues until we reach point B, whereupon the pulse ceases. At once, at this point, an upward going differentiated spike shaped pulse appears. At point C we have the leading edge of the next downward going frame sync pulse, with the formation of another downward going differentiated pulse. At point D, the end of the second frame sync pulse provides a further upward going differentiated pulse. This procedure is

At point P in this diagram we have the downward-going leading edge of the last line sync pulse before the frame sync pulses commence. A period equal to half a line follows point P, whereupon we have the leading edge, at Q, of the first frame sync pulse. A corresponding downward going differentiated pulse appears below. The end of the first frame pulse at R causes the next upward going differentiated pulse; to be

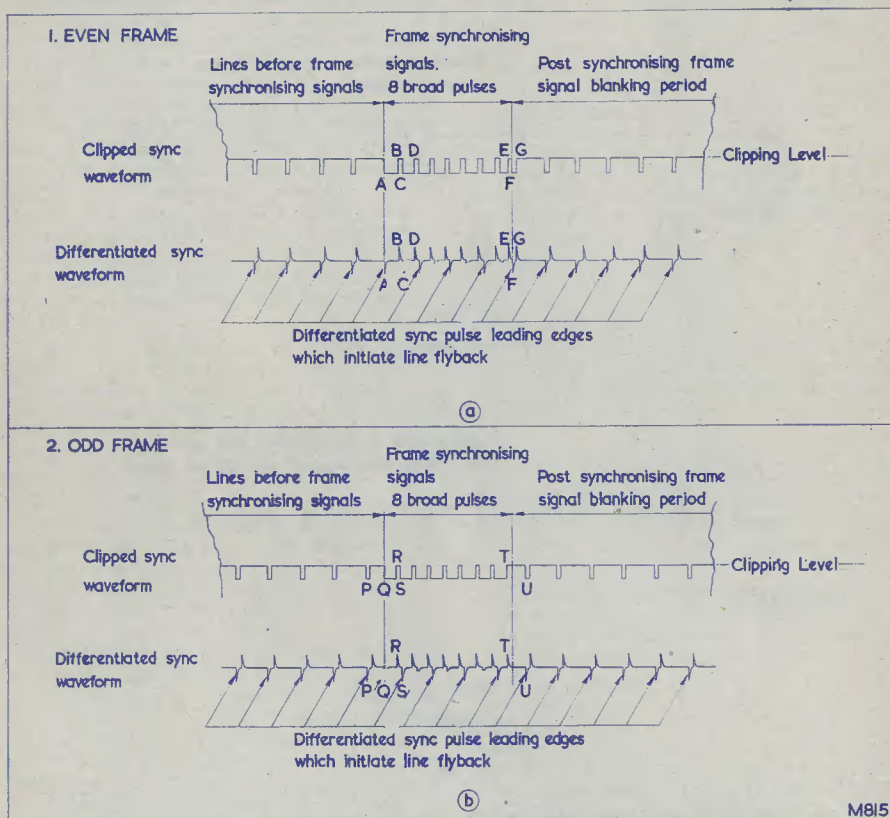


Fig. 191 (a) The result of differentiating the waveform around the even frame synchronising signals of Fig. 13  
(b) Differentiating the waveform around the odd frame synchronising signals

repeated for each frame sync pulse until, at point E, the last frame pulse ceases, to be followed by a conventional line sync pulse, FG. The resulting differentiated pulses are shown below. After point G we have a blanking period in which line sync pulses appear at normal line intervals just as they did before point A.

A slightly different state of affairs occurs for the odd frame waveform of Fig. 191 (b).

followed, at S, by the next downward going differentiated pulse. The process continues until we reach point T, where the end of the last frame pulse causes the formation of an upward going differentiated pulse. At point U we have the leading edge of a normal line sync pulse, this pulse being followed by further line sync pulses with normal spacing.

We can now see the differentiated pulses occurring around the frame sync pulses for

both even and odd frames. Commencing with an examination of the even frame pulses first (Fig. 191 (a)) we have an example where, before the commencement of the frame sync pulses, the line sawtooth generator is synchronised by downward going differentiated sync pulses spaced at intervals of one line. After point A, however, the downward going pulses are spaced at half-line intervals. What happens then is that the line sawtooth generator has its flyback initiated by the first downward going differentiated pulse, is unaffected by the second, has its flyback initiated by the third, is unaffected by the fourth, has its flyback initiated by the fifth, is unaffected by the sixth, and so on; until, after point F, the downward going differentiated pulses revert to normal line spacing. The pulses which initiate flyback are indicated in Fig. 191 (a).

In Fig. 191 (b) the last downward going differentiated pulse at regular line spacing occurs at point P. The first downward going differentiated pulse given by the frame pulses appears at Q. The line sawtooth generator is unaffected by this first pulse, has its flyback initiated by the second, is unaffected by the third, has its flyback initiated by the fourth, and so on, until it reaches point T, after which downward going pulses spaced at normal line intervals commence once more. Again, the pulses which cause the initiation of flyback are indicated in the diagram.

Considering the two waveforms generally, it may now be seen that, although the frame sync pulses have exactly the same shape and number for both odd and even frames, they still allow the line sawtooth generator to remain in a synchronised condition. In Fig. 191 (a) the line sawtooth generator has its flyback initiated, during the frame sync pulses, by the first, third, fifth, seventh and ninth differentiated pulses; and, in Fig. 191 (b), the line sawtooth generator has its flyback initiated by the second, fourth, sixth and eighth differentiated pulses.

The fact that the line sawtooth generator may be synchronised by alternate half line pulses becomes readily evident if Fig. 192 is examined. In this diagram the grid waveform of Fig. 190 (b) is repeated, with intermediate half line pulses added. Since the grid voltage, when the intermediate pulse appears, is markedly more negative than when the second flyback-initiating pulse appears, the intermediate pulse does not raise grid voltage above cut-off level and does not, in conse-

quence, affect the running of the sawtooth generator.

It should be pointed out that, under certain circumstances, and particularly if the differentiated sync pulses have large ampli-

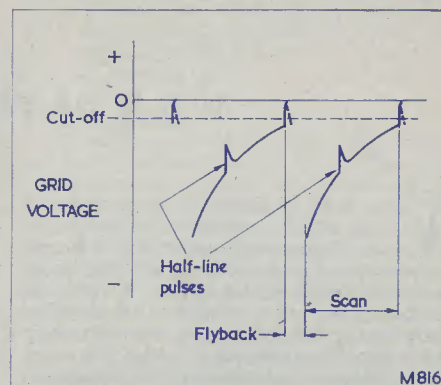


Fig. 192. During the frame synchronising period, differentiated half line pulses are fed to the line sawtooth generator. Since the oscillator grid voltage is considerably more negative, when these pulses appear, than it is near the end of the scan period, they do not raise grid voltage above cut-off level and do not, therefore, initiate the flyback period. This diagram should be compared with Fig. 190 (b)

tude, it may be possible to find a setting of the line hold control whereby the line sawtooth generator has its flyback period initiated by the half line pulses. Such a line hold control setting will cause an obvious loss of line synchronisation at the top of the picture (i.e. immediately after the end of the frame blanking period) and would automatically be avoided.

#### Next Month

In next month's article we shall carry on to frame synchronising circuits. This article will refer to Fig. 13, and this month's issue should in consequence be retained.

#### Reference

The information given in Fig. 13 is taken from Report No. 83, Television Systems; Extract from the documents of the C.C.I.R. VIIIth Plenary Assembly, Warsaw, 1956. The term "field", where it appears in extracts from the report, has been changed to "frame".

## QUIZ RIGGING LEGISLATION

The U.S. House of Representatives recently (28th June) approved a Bill against those engaging in deceptive programmes of the type exposed by a Congressional investigation of television quiz programmes and "payola".

The Bill, which now goes to the Senate, is designed

to provide a maximum penalty of one year's imprisonment and a fine of \$10,000 (approximately £3,600) for those failing to disclose that payment has been made for broadcast material or if they engage in rigged programmes. The penalty applies to both broadcasting stations and members of their staff.

# Choosing a Valve

By J. B. DANCE, M.Sc.

THE NUMBER OF DIFFERENT TYPES OF VALVE from which a constructor can choose has now become so great that it is only possible to discuss some of the more important points in this article. A valve has to be chosen not only for its electrical performance but also for the ease with which it fits into the apparatus in which it is to be used. Obsolete and replacement types should be avoided in new equipment as difficulty may be experienced in obtaining replacements at some future date.

## General Remarks

One of the most important characteristics of a valve is its heater voltage, or, in the case of a.c./d.c. equipment, its heater current. In equipment using a mains transformer, all of the valves are connected with their heaters in parallel and therefore the heater voltage of each valve must be the same; the most common value is 6.3 volts. When this type of heater connection is used the current taken by each valve may be different. Power valves, for example, require more heater power because they have a larger cathode which must be kept hot; this extra power is obtained by taking more current than the other valves. Directly heated valves with 1.4 volt heaters are made for operation from dry batteries; the heater power required is usually very small. In equipment for a.c./d.c. operation a mains transformer is not used, the valve heaters being connected in series. In this case the heater current for each valve must be the same (often 0.3 or 0.15 amp). Valves which require more power than the others have a heater with a higher working resistance and therefore a higher voltage is developed across the heaters of these valves. Thus the PL82 has a 16.5 volt, 0.3 amp heater. The heater voltage supply to any valve should be correct to within 5%.

Care must be taken that the maximum heater-cathode voltage rating of a valve, as indicated in the appropriate data, is not exceeded. Many rectifiers have high heater-cathode voltage ratings. Twin triodes which have a high heater-cathode voltage rating are useful in certain phase splitters.

Miniature valves may have advantages over the larger types at high frequencies because of the shorter lead lengths to the electrodes. Physical size, availability and cost are other considerations when deciding between miniature and other valves. Miniature valves are now used by almost all commercial manufacturers except possibly for power valves and rectifiers. The fairly new sub-miniature valves (having lengths of 28 mm and diameters of 5.4 mm) may become very popular in the future, but at present they are mainly used in large commercial equipment.

The choice of valves for the various stages of radio receiver will now be considered.

## R.F. Amplifiers

If it is likely that an r.f. amplifier will be required to handle a large signal at any time, a variable- $\mu$  valve with appropriate automatic (a.g.c.) or manual biasing should be used in order to avoid overloading. On the other hand, if it is desired that an r.f. pentode amplifier should generate the minimum possible amount of noise, a sharp cut-off pentode should be used. Sharp cut-off pentodes can normally be made with a higher mutual conductance than variable- $\mu$  valves and therefore tend to generate less noise and to give a higher gain. Even less noise is obtained from grounded grid triodes, but the amplification is much smaller. Other special low noise circuits such as cascode amplifiers are also available. Pentodes such as the 6AK5 (EF95) and the 6AG5 have been designed for use in low noise r.f. stages operating at high frequencies. They have a fairly high mutual conductance and a very high input impedance—the two most important qualities for a very high frequency amplifier. In the two types mentioned, two separate cathode pins are used so that the input and output circuits can be kept entirely separate.

## Converters

The main considerations concerning the design of a converter stage are (a) the amount of noise generated by the valve, (b) the means

to be employed in avoiding pulling of the oscillator frequency and, possibly, (c) what gain will be obtained. The gain is determined by the conversion conductance of the valve. The multigrad mixers such as the 6K8 triode-hexode, the 6BE6 and 6SA7 heptodes are usually used as self-oscillating converters in broadcast receivers and generate a relatively large amount of noise. Very little pulling of the oscillator frequency occurs with a well designed multi-grid valve; this type of mixer is also the most economical with respect to components used in the circuit.

Multi-grid valve converters have a conversion conductance of about 0.3 to 0.4mA per volt. A conversion conductance of about 2.5mA per volt can be obtained by feeding the oscillator voltage to the cathode of a pentode mixer, or alternatively, to the same grid of the mixer that the signal is fed. This method gives much higher gain and much lower noise than when multi-grid converters are used, but an extra buffer amplifier should be used between the oscillator and mixer or pulling will almost certainly occur. Three separate valves (oscillator, buffer amplifier and mixer) are therefore needed in this type of converter; this may be well worthwhile in a good communication receiver. (In television and f.m. tuners a buffer amplifier is not, however, employed.—*Ed.*)

## I.F. Amplifiers

Variable- $\mu$  pentodes are almost always used in the i.f. stages of a radio receiver because the receiver gain as a whole is controlled almost entirely by the i.f. gain. If the i.f. valves have a high value of anode resistance, the tuned circuits will be only slightly damped and the selectivity may be made as great as possible. The higher the mutual conductance of an i.f. valve, the higher the gain of the stage. If a valve is chosen so that its screen grid is designed to operate at the same voltage as its anode, fewer decoupling components will be required. Sharp cut off pentodes (i.e. not variable- $\mu$ ), are often used in broad band i.f. amplifiers for use in radar, television and f.m. receivers.

## Detectors

Most small diodes give very similar results as detectors. Any small triodes, or triode connected pentodes, are suitable for use as cathode follower detectors. Diode detectors load the previous tuned circuit and thus reduce its selectivity, but the load imposed by cathode follower detectors is very small (hence the name "infinite impedance detector"). Cathode follower detectors should be operated at a fairly high signal level. The choice of valves for these two types of detector may be made solely on

physical size, preferred base, etc. The leaky grid detector virtually consists of a diode combined with an a.f. amplifier although no separate diode is employed. Leaky grid detectors are very sensitive to small signals, but the quality of reproduction obtained is poor and considerable loading is applied to the previous tuned circuit. A triode or pentode may be used.

## Radio Amplifiers

Valves for use as very low level audio amplifiers should generate the smallest possible amount of noise, as any noise in the low level stages is amplified enormously. It is also desirable that low level audio amplifiers should have a bifilar heater construction to minimise hum. The valve holder should be made of a good electrical insulator such as P.T.F.E. or hum will be introduced by capacitive coupling through it. It is most important that microphonic valves are avoided in low level stages and good screening is essential. The 6BR7 and the EF86 have been specially designed for use in low level audio amplifiers. For the very best results it is advisable to pick out one valve from several of the same type. A valve with a very small reverse grid current should be chosen.

Audio amplifiers for use in stages at higher signal levels should have very linear characteristics or distortion will occur. Triodes tend to give much less distortion than pentodes at the higher voltage levels; negative feedback is essential for reasonably good reproduction when pentodes are used. If a high gain is required, an audio amplifier should have a large amplification factor. Pentodes give much higher gain than triodes.

## Power Amplifiers

Valves required to give an appreciable power output have a lower anode resistance, a much greater maximum value of anode dissipation, and a greater anode current, than valves intended for use as voltage amplifiers. The valve chosen for the power amplifier must be capable of giving the amount of power required at a certain permissible distortion level. Small amounts of power may be obtained by using valves which are normally only used as voltage amplifiers. The impedance of the device (speaker transformer, etc.), into which the power is fed must match the optimum load impedance of the valve fairly closely. When deciding on the power output required from a high quality audio amplifier, it should not be forgotten that the peak power is much greater than the average power. The amplifier must be able to handle the peak transient power or distortion will occur. A valve with a high slope (mutual conductance), will give a large voltage amplification; that is, the

voltage input to the amplifier for a certain power output will be smaller than if a low slope valve were used.

Beam tetrodes and pentodes can usually be made more efficient in operation than triodes, but triodes give less distortion for the same amount of negative feedback. At high power levels triodes need a higher h.t. voltage than tetrodes. Tetrodes may, of course, be triode connected if desired. The method of operation known as "ultra-linear" is popular. In this method, the valves are effectively operated somewhere between triode and tetrodes by connecting the screen of the valve to a tapping on the primary of the output transformer. Ultra-linear amplifiers are almost always of high fidelity standards and are therefore push-pull.

A power amplifier often takes as much current from the h.t. line as all of the other valves put together. When the amount of h.t. is limited (as when battery supplies are used), it is important to choose a power valve which is economical on h.t. current and which does not give much more power than is likely to be required.

#### H.T. Rectifiers

A heater supply of the correct voltage must be available for the rectifier (except in a.c./d.c. equipment); the heater power required by rectifiers is usually comparatively large. The 6X5 (octal), and 6X4 (miniature B7G) valves are sometimes useful because the 6.3 volt supply for their heaters can normally be taken from the commonly used 6.3 volt heater line feeding the other equipment. These two types of valve are limited to a maximum d.c. output of 70mA, however. In most other types of rectifiers the cathode is connected to the heater and a separate winding on the mains transformer is necessary for the rectifier heater.

It is usually advisable to choose an indirectly heated rectifier where possible so that, after switching on, the h.t. voltage is not applied to other valves until they have warmed up. This also prevents many of the capacitors in the equipment from having to withstand a higher voltage than normal just after the apparatus has been switched on.

## SOUTHERN TELEVISION GRANTS TO THE ARTS AND SCIENCES

Southern Television, the company serving central-southern and south-east England, recently announced that they are to make several grants to the arts and sciences. Repertory theatres, universities, music festivals and orchestras will receive sums totalling some £8,000. Of the repertory theatres, the following will each receive a sum of £500—Margate, Chichester, Canterbury, Guildford and Salisbury.

The rectifier must have a peak inverse voltage rating which is larger than any inverse voltage which will appear across the valve. In the usual type of full wave rectifier circuit, the peak inverse voltage is 1.41 times the r.m.s. voltage appearing across the whole of the secondary h.t. winding of the transformer providing that condenser input is used. This is equal to double the h.t. output voltage at no load.

In condenser input filters there is a limit to the maximum size of reservoir condenser which can be used. In choke input filters there is a limit to the minimum size of choke which can be used. These values are normally given in the valve data for the rectifier concerned. If they are not observed the peak cathode current rating of the rectifier may be momentarily exceeded during each cycle.

#### Combined Valves

It is often possible to reduce the size of equipment by employing two or more valves in the same envelope. Triode-hexodes are often used as oscillator-mixers and double diode triodes as combined audio detectors, a.g.c. detectors and audio amplifiers in broadcast receivers. Choice of these valves depends on the electrical characteristics of each separate part of the valve. Care should be taken to avoid undesired feedback from one section of the valve to another. Double triodes are particularly useful for a wide variety of applications, but the uses of some double triodes (e.g. 6J6 and 6SC7), are limited because there is only one common cathode for the two triodes.

#### Voltage Stabilisers

A simple gas filled voltage stabiliser tube must be chosen for adequate stability, the current ratings being suitable for the circuit concerned. Stabilisers should not be connected in parallel in order to increase the maximum permissible current for the reason that one of the tubes would probably then take all of the current. Stabilisers may be connected in series, however, in order to increase the voltage of the stabilised supply. The VS110 and VR105/30 are quite suitable for stabilising the h.t. supply to an oscillator.

A grant of £1,250 will be used at Southampton University to fund a research studentship in a branch of electronics and a similar sum will be used for the endowment funds of the new university college at Brighton.

The Central School of Speech and Drama has been offered £700 for a lectureship on aspects of television, this to encourage a better knowledge of the action and production techniques of this medium.

## New Valves for Small-Boat Radar

THE INSTALLATION OF RADAR IN A GROWING number of fishing boats, yachts, and the like, has led to radar equipments designed specifically for use in small craft. Apart from the general demands of high performance and reliability, the essential requirements of such equipments are low cost, small size and weight, and low power consumption.

To meet these requirements the radar manufacturer needs valves that are also designed for the purpose. Mullard have already made available a "line-up" of valves for 3kW small-boat sets, and they have now introduced a new series of three types—a magnetron, klystron and pulse modulator—intended for 6kW installations. Details of these three types, which were shown for the first time at the Instruments Electronics and Automation exhibition, are given below.

#### 6kW X-band Magnetron: type JP9-5

The JP9-5 is an inexpensive, low-voltage packaged magnetron giving a nominal peak output power of 6kW (minimum 5kW) at a fixed frequency in the band 9.345 Gc/s to 9.475 Gc/s. It requires an anode voltage of only 4.5kV and has a peak current rating of 5A. Its overall physical dimensions are small—11.4cm x 10.1cm x 5.1cm—and it weighs only 2½lb including the magnet system.

#### Pulse Modulator Valve: type QV12-P10

The QV12-P10 is a hard valve pulse modulator capable of a peak pulse output power exceeding 100kW with a d.c. hold-off voltage of 12kV. These ratings ensure that

the valve is only lightly loaded when used in service with the JP9-5 magnetron.

The QV12-P10 is octal-based, and measures 13.3cm x 5.5cm.

#### X-band Local Oscillator Klystron: type KS9-40

Despite its low cost the KS9-40 provides a very high standard of performance and has several features hitherto confined to valves costing much more.

An important feature is its high frequency stability, due largely to the construction of the tuning cavity. Although an integral part of the valve, the cavity is external and thus is isolated from the effects of variations in beam current. The warm-up frequency drift is less than 3 Mc/s, 5 minutes after switching on. Rugged construction enables the valve to withstand accelerations of 10g with no more than 2 Mc/s shift in frequency.

The noise performance is very good, the typical a.m. signal-noise ratio being greater than 160db per cycle of i.f. bandwidth for receiver intermediate frequencies above 25 Mc/s.

The valve is fitted with a WG16 waveguide output to take a plain flange coupling. A matching screw is incorporated to ensure close tolerance of output power, eliminating the need for a waveguide attenuator to control crystal current.

Mechanical tuning is provided over the range 9.3 Gc/s to 9.5 Gc/s, with an electronic tuning range between half-power points of ±20 Mc/s. The output power is 40mW at resonator voltage and current ratings of 300V and 35mA.

Overall dimensions of the KS9/40 are 8.6cm x 4.1cm x 5.1cm.

## ADHESIVE VENEER TAPES AND STRIPS

For the home constructor who carries out his own cabinet making a new product which edges chipboard, plywood or blockboard, etc., to obtain a "solid wood" appearance is currently available from Flexible Veneers Ltd., Cobbs Court Buildings, Carter Lane, London, E.C.4. The product consists of wood veneer fixed to a paper backing, this being stuck to the surface being covered by Agastik latex base adhesive (also available from Flexible Veneers). The paper backed veneer may be obtained in the form of Agastrips, these consisting of 4 or 10yd rolls having a width of ¾in, with the grain of the wood running across the width. Agastrips are also available with long grained veneer in individual lengths of 36in maximum. An alternative finish is offered by Agatapes, these being self adhesive and consisting of long grain veneer lengths of 19½in maximum. Width is again ¾in. Being real wood, the strips and tapes can, if desired, be stained, varnished or French polished. Colour grainings available are light oak, mahogany and walnut.

## BULGIN INTRODUCE ROCKER-CONTACT SWITCHES


Following considerable research, Bulgin have now added eight rocker-contact switches to their well-known and already extensive range. These switches have the dolly, bush and milled circular panel mounting nut familiar with normal panel mounting switches, and they are capable of switching (depending on circuit conditions) 6 to 10A at 250V a.c. and (in non-reactive circuits) 10A at 125V a.c. and 10A at 28V d.c. Screw terminals are provided. Three of the eight switches have central "off" positions, wherein all circuits are broken. Throwing the switch to either side of central then completes one set of change-over contacts. All switches are two-pole, five (including the three with central positions) being change-over, and three single-throw. Both biased and non-biased types are available. Biased switches spring back to a previous setting when released, and this setting may be at central or to one side. The finish is brilliant chrome. List numbers for the switches are S780 to S787, full details being available from A. F. Bulgin and Co., Barking, Essex.

# Comparing A.C. and D.C. Voltages for Meter Calibration

by P. G. WRIGHT

IN THE PAST THERE HAVE BEEN MANY circuits published for the construction of multimeters. The lower a.c. ranges on these meters are, however, dogged with non-linearity, and, since standard a.c. voltages are not generally available to the home constructor, calibration becomes extremely difficult. A method of comparing a.c. and d.c. voltages would be useful to have, since the latter can usually be measured accurately with the d.c. ranges of the multimeter in question if no other instrument is available.

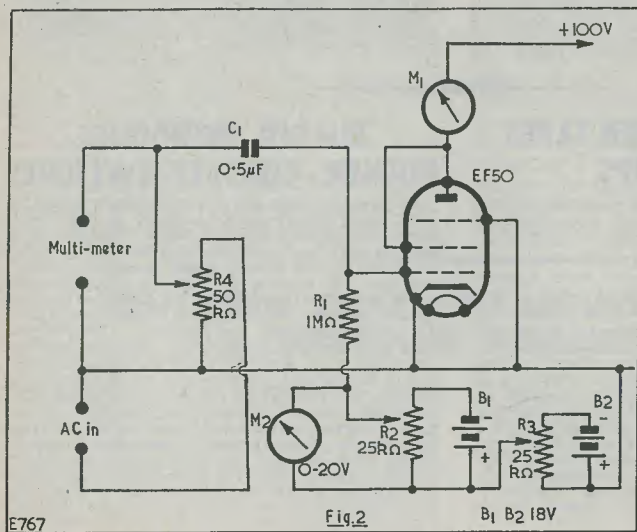A simple method of comparison is possible with the aid of a slide-back valve voltmeter. The basic circuit of such a voltmeter is shown in Fig. 1 (a). Fig. 1 (b) shows the variation of anode current with grid voltage for a normal sharp cut-off valve.



Consider the valve biased back by a d.c. voltage until it is just at the cut-off point; if now an alternating waveform is superimposed on the d.c. voltage, the positive peaks will cause anode current to flow. The valve may now be biased back still further, until the peaks cease to have any effect and the valve is at cut-off point again. The extra grid bias needed for the second operation will then be equal to the peak value of the superimposed a.c.

## The Circuit

The valve used in the writer's circuit (shown in Fig. 2) was an EF50 strapped as a triode; this combination was found to give quite a sharp cut-off with an anode voltage of 100. The meter in the anode circuit should be as sensitive as possible in order that reliable indications are given as the valve approaches the cut-off point.


The meter which measures the negative voltage at the lower end of  $R_1$  must be accurate, but need not be sensitive. If desired it may be calibrated by comparison with the multimeter itself. The calibration may be in volts, or in 0.707 times the actual applied volts, thus giving direct r.m.s. readings of the applied a.c. without recourse to the "guessing stick".

$C_1$  should have a low reactance compared to the resistance of  $R_1$  at the frequency used. Layout is unimportant at

low frequencies.

Calibration is carried out in the following manner. The instrument is switched on and allowed to warm up. The meter  $M_2$  is set to zero reading by adjustment of  $R_2$  and  $M_1$  set to zero by manipulating  $R_3$ . An a.c. supply is connected across  $R_4$ , and a convenient fraction tapped off and applied at the same time to the input terminals of the comparator.  $R_2$  is then rotated to cause a zero reading on  $M_1$ , thereupon the reading in  $M_2$  is equal to the peak (or r.m.s., according to the calibration) value of the a.c. voltage applied.

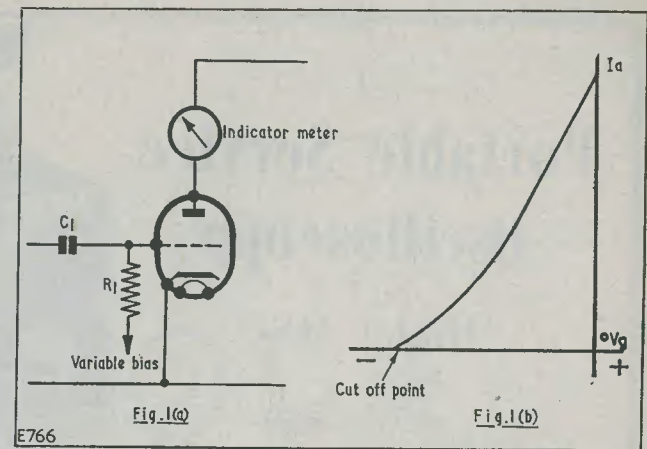The circuit shown in Fig. 2 gives accurate



results, the component values specified for  $C_1$  and  $R_1$  being suitable for inputs at 50 c/s.

## Brazil TV Station Opens Shortly

Marconi's Wireless Telegraph Co. Ltd. have supplied the complete studio and transmission equipment for a new television station at Recife, Brazil, which is expected to begin programme transmissions shortly. Scheduled test transmissions are now in progress at the station, which is owned by Empresa Jornal do Comercio S.A., Recife.

The luxurious, contemporary-style building contains a suite of three studios, completely equipped by Marconi's with the most up-to-date units, including seven Marconi 4½ in Image Orthicon cameras, master control equipment, two vidicon telecine units and lighting, sound, test and ancillary equipment. A three-camera outside broadcast vehicle and micro-wave link equipment are provided.

The transmission equipment consists of Band I 18kW vision and 9kW sound transmitters feeding into a 6-stack quadrant aerial, providing an effective radiated power of 110kW. The equipment operates on 625-line standards; it is capable of handling a compatible colour service should this be required.

## A.R.M.S. at U.S.A.F. Transmitter Site

On 19th June the Amateur Mobile Radio Society (Sec. G. E. Storey, G3HTC) held a memorable and extremely successful mobile meeting at U.S.A.F. Transmitter Site, Barford St. John, Oxon. It is estimated that more than 500 people were present, including over 30 American amateurs, some of whom travelled 200 miles just for the day. The majority of the 150 cars present were fitted with mobile radio. Whilst their families enjoyed baseball, a display of precision marching, go-cart and model flying demonstrations, OMs made frequent shuttle-service visits to the transmitter hall. The U.S.A.F. side of the organising was largely handled by Major Peter Kravchonok, K7LKS, who was, at a special emergency committee meeting, unanimously elected as the first honorary member of the A.R.M.S.

## Seven New Silicon R.G.A. Rectifiers

R.C.A. is pleased to announce 7 new silicon rectifiers of the diffused-junction type 1N2858, 1N2859, 1N2860, 1N2861, 1N2862, 1N2863 and 1N2864.

These types, which are designed for use in both industrial equipment and consumer-type products, have a maximum d.c. forward-current rating of 750 milliamperes (for resistive or inductive loads), and 500 milliamperes for capacitive loads up to 75°C ambient temperature. They offer the equipment designer a wide choice of peak inverse-voltage ratings — from 50 volts to 600 volts, respectively.

Special features of these silicon rectifiers are:

- (1) Rugged internal mount structure.
- (2) Diffused silicon junctions of extremely high uniformity produced by a special precisely controlled diffusion process.


- (3) Hermetically sealed, industry-preferred cases.
  - (4) Axial leads for flexibility of installation in either hand-wired or printed-circuit equipment designs.
- Long life and stability of electrical characteristics are assured by conservative ratings and the following stringent quality-control procedures and tests:

- (1) Thorough baking at high temperatures to assure stable performance.
- (2) Pressure tests to assure a hermetic seal against moisture and contamination.
- (3) Forward-and-reverse current characteristics tests at 25°C.
- (4) High-temperature dynamic tests under full-load conditions.

# A Portable Service Oscilloscope

## Model OS-1

By G. J. Stone

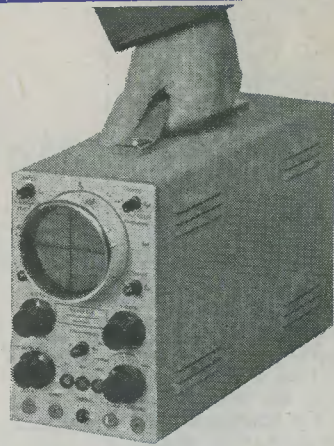

WITH MANY RADIO AND T.V. FAULTS THE 'scope is as essential as the test meter and, with the additional servicing required by f.m. receivers, the demand on the use of the 'scope is continually increasing. To provide an efficient service, the engineer must employ efficient methods, this only being achieved if he has available the correct instruments for the particular job in hand.

It is probable that the average workshop has only one oscilloscope, this being shared by a number of engineers, and its weight may be anything up to 1 cwt.—hardly portable! There is, therefore, a need for a small portable inexpensive oscilloscope to overcome this problem and also fulfil the requirements of servicing in the field. The oscilloscope must not be complicated but must be simple and easy to use. Apart from its use by the service engineer for radio and t.v. work it should also prove ideal for the radio and audio enthusiast and the radio amateur. Portable oscilloscopes are produced by Jason Motor & Electronic Co. and Cossor Instruments Ltd., as well as by Daystrom Ltd., but for the purposes of this article we shall be considering the Daystrom Heathkit model OS-1.

### CIRCUIT DETAILS

#### Y Amplifier

See Fig. 1. Two input sockets are available at the front panel, one being a direct input (X1) while the other introduces an attenuation of 10:1 (X10). The X10 input is frequency compensated by  $C_1$  in order that the attenuator will be independent of frequency and therefore produce a frequency response which is substantially flat. Also, the attenuator circuit is such that distortion of the input

signal is negligible. The first valve is connected as a cathode follower and has a continuously variable gain control VR<sub>1</sub> (Y Gain) in the cathode circuit. The slider of this control is connected to the grid of the pentode section of V<sub>1</sub> and this valve is compensated by L<sub>1</sub> and partly by C<sub>4</sub>. Without the use of the compensating coil L<sub>1</sub>, the frequency response would be reduced considerably at high frequencies due to the stray capacitance (formed by the wiring capacitance and input capacitance of the following valve) shunting the anode load R<sub>6</sub>. The use of L<sub>1</sub> in series with R<sub>6</sub> compensates for this effect since its inductive reactance is increased with frequency. The total anode impedance consequently increases with frequency and the normal loss at high frequencies is therefore compensated. Also, at low frequencies, the effect of C<sub>4</sub> across the bias resistor R<sub>7</sub> is negligible and a measure of negative feedback exists. At the higher frequencies, C<sub>4</sub> effectively decouples R<sub>7</sub>, reducing the feedback and hence the gain increases. The net effect, therefore, of L<sub>1</sub> and C<sub>4</sub> is to extend and maintain a reasonably flat response characteristic. Output from the pentode section of V<sub>1</sub> is coupled to V<sub>2</sub> where V<sub>2</sub> and V<sub>3</sub> are connected as a cathode coupled or "long-tailed" pair.

The operation is as follows: consider a positive going signal at the grid of V<sub>2</sub>. This will cause the anode potential to decrease and its cathode potential to increase. As V<sub>2</sub> and V<sub>3</sub> are cathode coupled, the increase in cathode potential will in effect make the grid of V<sub>3</sub>A more negative with respect to the cathode, therefore the anode potential of V<sub>3</sub>A will increase. We now have a state of

affairs where the single ended input signal produces a balanced push-pull output, i.e. the anode potential of V<sub>2</sub> is driven a certain amount in one direction, while the anode potential of V<sub>3</sub>A is driven an equal amount

in the other direction. Frequency compensation is achieved by L<sub>2</sub> and L<sub>3</sub> in the respective anode circuits. Vertical positioning of the c.r.t. trace is adjusted by VR<sub>2</sub> (Y Shift) and has a range of approximately  $\pm 2\frac{1}{2}$  cm. Its

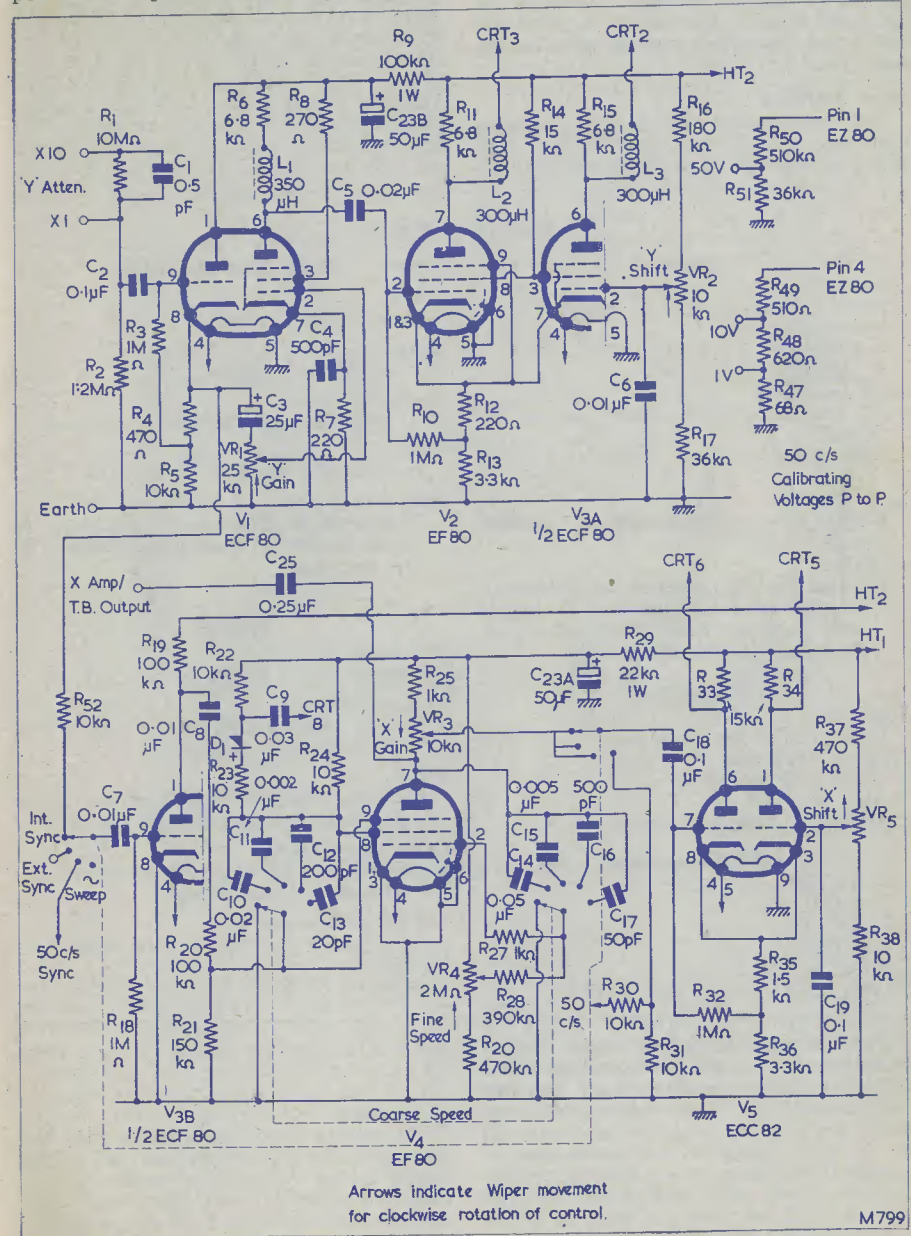


Fig. 1. Circuit diagram of the Portable Oscilloscope Model OS-1

operation depends upon the d.c. voltage produced by the potential divider R<sub>16</sub>, VR<sub>2</sub>, R<sub>17</sub> and this voltage is applied to the grid of V<sub>3A</sub>. The effect is similar to that already described except that this is a d.c. condition, i.e. the Y shift will adjust the static or quiescent anode potentials of V<sub>2</sub> and V<sub>3A</sub> and hence the position of the trace on the face of the c.r.t.

#### Sync. Amplifier

The triode section of V<sub>3</sub> is used as a sync. amplifier. The valve is operated with zero bias and produces at its anode an amplified

#### Time Base Generator

The time base generator uses V<sub>4</sub> in the well-known Miller transitron circuit. Coarse frequency control is obtained by the switch SB, and fine speed control by VR<sub>4</sub>. An output is taken from the anode of V<sub>4</sub> through an isolating condenser to a socket on the front panel, X AMP. While the time base is operating, a sawtooth waveform will be available at this socket. A switch position on SB allows the time base to be switched off and an external signal or time base can be fed into this socket. The amplitude of this

### SPECIFICATIONS

#### Y Amplifier

##### Sensitivity

10mV (r.m.s.) per cm (XI input)

##### Frequency Response

±1dB, 10 c/s–1.5 Mc/s  
±3dB, 10 c/s–2.5 Mc/s

##### Input Impedance

X1 attenuator input—1MΩ shunted by 20pF  
X10 attenuator input—10MΩ shunted by 10pF

##### Input Circuit

Built-in blocking condenser rated at 600V d.c.

##### Y Shift

DC type permits placement of undeflected trace at any horizontal level on usable area ±2½ cm from centre of screen. Positioning is instantaneous

#### X Amplifier

##### Sensitivity

1 volt (r.m.s.) per cm at 1kc

##### Frequency Response

±3dB, 150 c/s–500 kc/s

##### X Shift

Approx. ±3 cm from centre

#### Valve Complement

2—ECF80  
2—EF80  
1—ECC82  
1—EZ80

#### Cathode Ray Tube

High sensitivity 2¼in type 3AFP1

#### Time Base Generator

##### Circuit

Miller transitron type

##### Range

15 c/s–150 kc/s approx.

##### Sinusoidal Sweep

50 c/s fixed amplitude 4 cm.

##### Sync.

Int, Ext, and 50 c/s

##### Time Base Output

20 volt pk-to-pk nominal available at X amp socket on front panel when T/B is operating

#### General

##### Retrace Blanking

Operates on all ranges

##### Voltage Calibrator

Built-in source 1 volt, 10 volt and 50 volt  
50 c/s pk-to-pk nominal

##### Finish

Polychromatic silver front panel with black printing. Ash grey wrinkle cabinet

##### Power Requirements

200–250 volt (3 tappings) 40–60 c/s a.c.  
35 watts. Fused 500mA

##### Cabinet Dimensions

4½in wide x 7⅞in high x 12½in long

##### Net Weight

10½lbs.

signal is adjusted by means of the control VR<sub>3</sub> (X GAIN).

#### X Amplifier

The output from V<sub>4</sub> is taken from the slider of VR<sub>3</sub> (X GAIN) and fed to the double triode V<sub>5</sub> which is connected as a cathode coupled or "long tailed" pair. The operation of this valve is similar to that of V<sub>2</sub>, V<sub>3A</sub>. Horizontal positioning of the c.r.t. trace is adjusted by VR<sub>5</sub> (X SHIFT)

and has a range of approximately ±3cm. A switch position on SA allows the time base to be switched out and connects V<sub>5</sub> to a source of 50 c/s. This provides a 50 c/s sinusoidal time base and has a fixed amplitude of approximately 4cm. This feature is useful where Lissajou's figures are required for frequency comparison, phase shift, etc. It will be noted in the specifications that the frequency response is falling below 150 c/s, this being due to C<sub>25</sub>. At the low frequencies the capacitive reactance of C<sub>25</sub> becomes comparable to VR<sub>3</sub>, R<sub>25</sub> and hence the falling response. This can be improved by using a larger condenser but, due to the increase in physical size, it will be necessary to choose one having a lower voltage rating—C<sub>25</sub> is a 0.25μF 400-volt working condenser.

V<sub>4</sub>. This pulse is limited by D<sub>1</sub> and the resulting flat topped waveform is fed to the grid of the c.r.t. to blank the retrace or fly-back of the time base sweep. C<sub>26</sub> is included to reduce intensity modulation but its inclusion is a compromise between retrace blanking and intensity modulation. In general, the latter is the lesser of the two evils, the author personally preferring the improved retrace blanking by omitting C<sub>26</sub>.

#### Power Supplies

A single copper banded transformer provides all supplies (see Fig. 2). For h.t. supplies a full wave rectifier V<sub>6</sub> is used and two h.t. supplies are obtained using resistance, capacitance smoothing. An e.h.t. winding on the transformer and a half wave

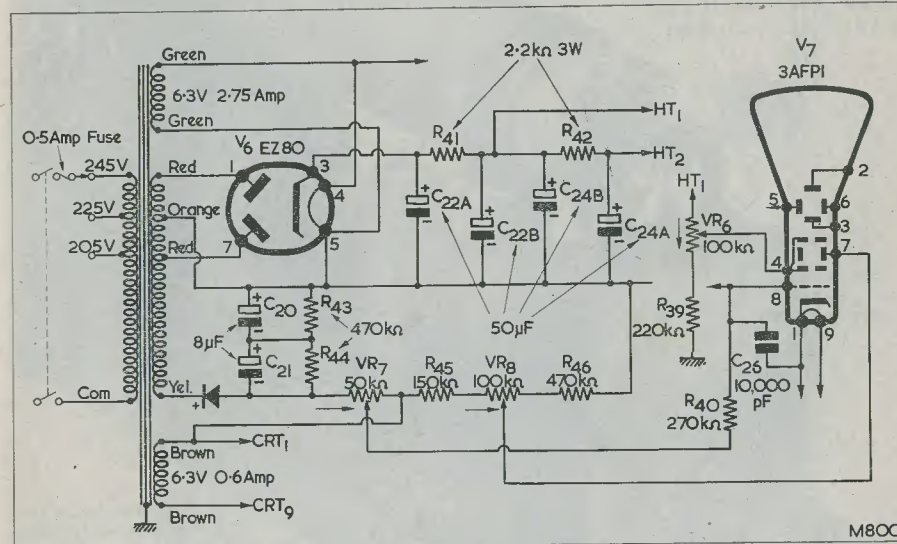


Fig. 2. Power supply and c.r.t. circuit

#### Calibration

50 c/s calibration voltages of 1, 10 and 50 volts peak-to-peak (nominal) are available at the front panel sockets. These enable the Y amplifier to be set to a specific gain.

#### Cathode Ray Tube (see Fig. 2)

Supplies for the c.r.t. are derived from the resistor chain across the e.h.t. supply. VR<sub>6</sub> is a spot shape or astigmatism control and is a pre-set potentiometer mounted on the chassis. This control is adjusted initially, in conjunction with the BRILLIANCE and FOCUS controls, to produce a well-defined trace. Flyback suppression is achieved by taking a negative pulse from the screen of

tubular rectifier provide a negative e.h.t. supply for the c.r.t. The e.h.t. supply is smoothed by two condensers connected in series across the supply, the two resistors R<sub>43</sub> and R<sub>44</sub> being used to ensure that equal voltages appear across each condenser.

The oscilloscope is protected by a 0.5 amp cartridge fuse which is integral with the mains voltage selector plug.


#### Anti-magnetic Shield for C.R.T.

The cathode ray tube is fitted with a treated mild steel shield in order to reduce the 50 c/s hum, produced by the stray field from the mains transformer, on the trace. The magnitude of the hum is of the order of

0.2 cm peak-to-peak and the only way this can be reduced still further is by the use of a mumetal shield fitted over the c.r.t. Mumetal shields are, of course, extremely expensive, but are available as an optional extra.

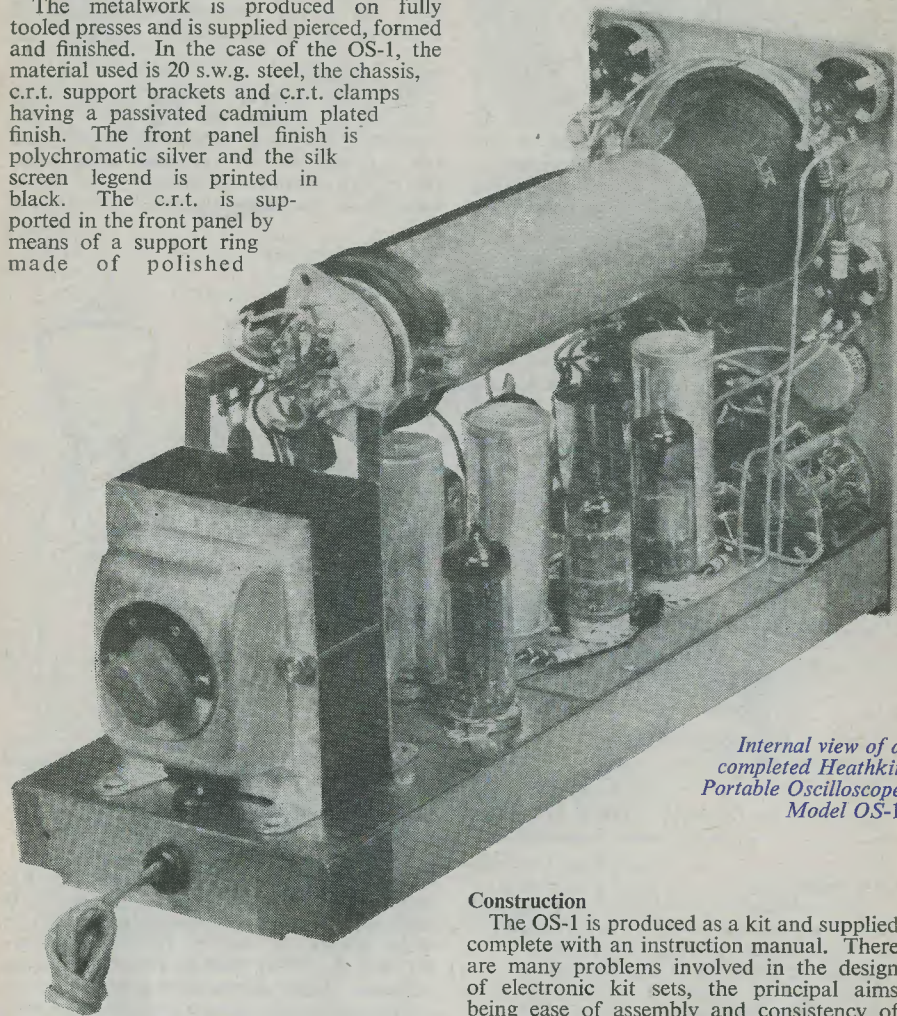**Metalwork**

The metalwork is produced on fully tooled presses and is supplied pierced, formed and finished. In the case of the OS-1, the material used is 20 s.w.g. steel, the chassis, c.r.t. support brackets and c.r.t. clamps having a passivated cadmium plated finish. The front panel finish is polychromatic silver and the silk screen legend is printed in black. The c.r.t. is supported in the front panel by means of a support ring made of polished



*Internal view of a completed Heathkit Portable Oscilloscope Model OS-1*


supplied with the OS-1 is a calibrated green plastic graticule which fits snugly within the plastic lined vizor.

The cabinet is finished in ash grey wrinkle paint which contrasts with the front panel. To ensure adequate ventilation the cabinet has four sets of louvres in each side panel and one set at the rear.

**Construction**

The OS-1 is produced as a kit and supplied complete with an instruction manual. There are many problems involved in the design of electronic kit sets, the principal aims being ease of assembly and consistency of performance. The assembly can be broken down into three sub-assemblies, (1) front panel (Fig. 3 showing component assembly and wiring), (2) chassis, and (3) the printed circuit board. Construction and assembly is greatly simplified by the use of a printed circuit board, the Y amplifier and time base circuits being contained thereon. The majority of the components associated with

aluminium. The ring, which is lined with a 1/4 in wide strip of black self-adhesive foam plastic material, also serves another useful purpose—that of a vizor. This reduces the amount of direct light falling on the face of the c.r.t. and therefore allows the tube to be operated at lower brilliancy and improved focus, etc. Also

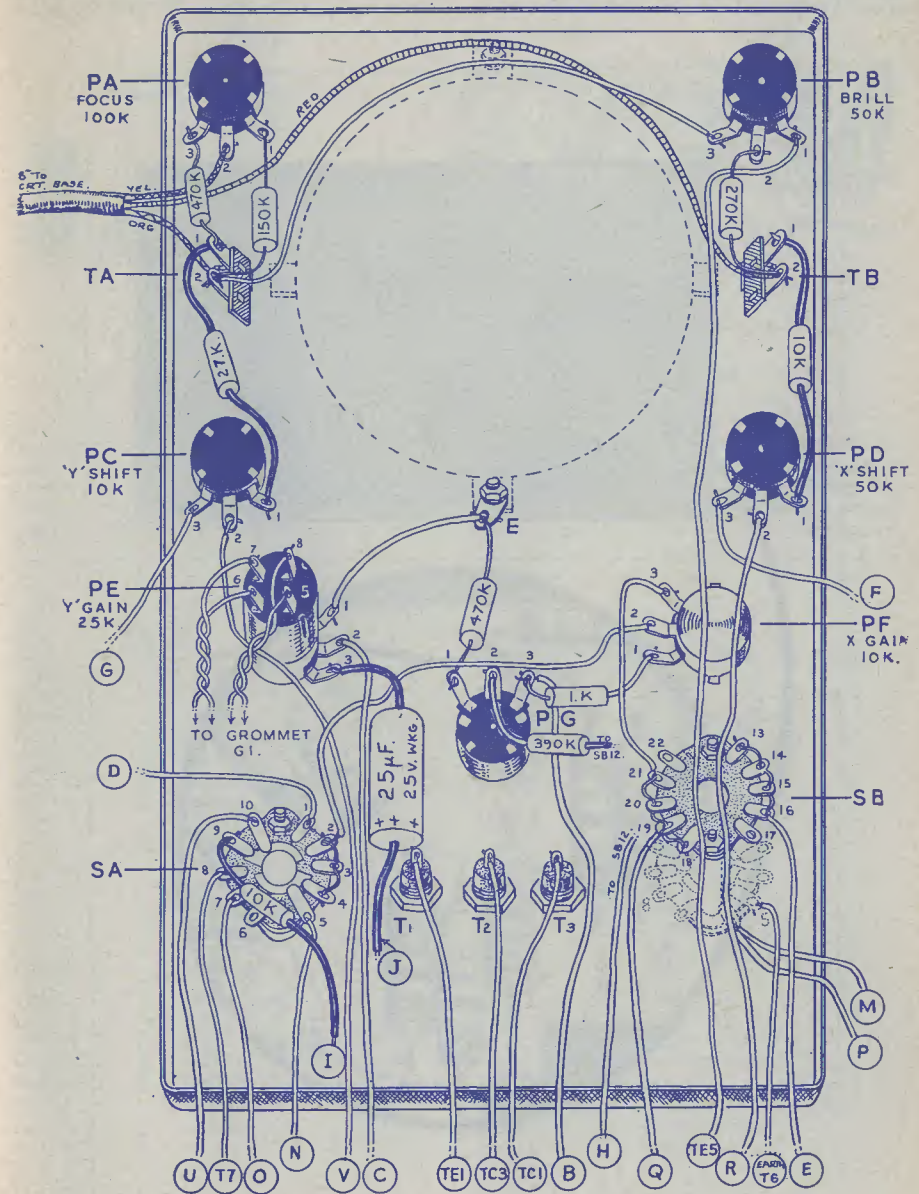


*Fig. 3. Front panel sub-assembly showing component layout and wiring. This diagram is reproduced from the comprehensive Instruction Manual supplied with the kit. Note the component and wire references as an aid to assembly*

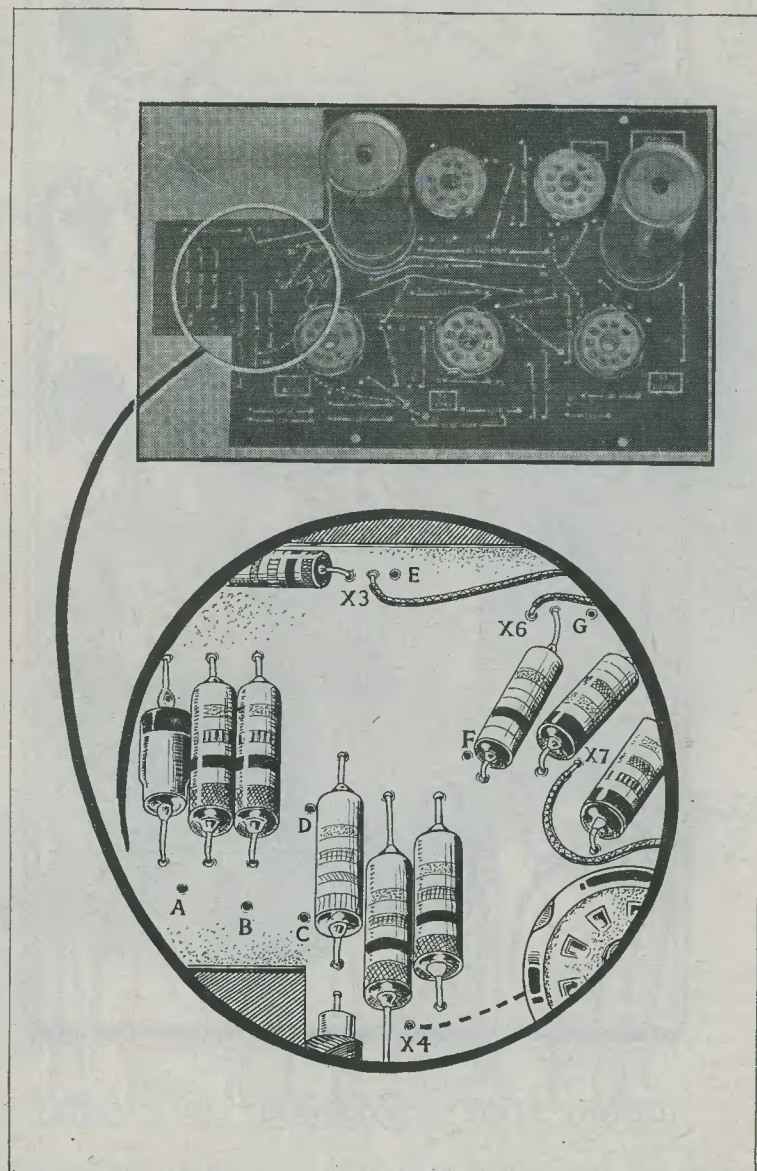

these circuits are mounted on the printed circuit board and permit a consistent and high degree of circuit stability. The phenolic side of the printed circuit board is silk screen

printed showing the exact location and value of each component to be mounted and this, in no small way, reduces the risk of wiring errors compared to the old point-to-point



View of the component side of a partly assembled OS-1 printed circuit board.  
Note the printed component locations and hole references for ease of assembly

wiring methods. The technique of component assembly and soldering to printed circuit boards is quite simple and full instructions are included in the manual. Methods

mounted to the board and the above chassis view of the completed oscilloscope.

#### Instruction Manual

As was mentioned previously, the OS-1 is

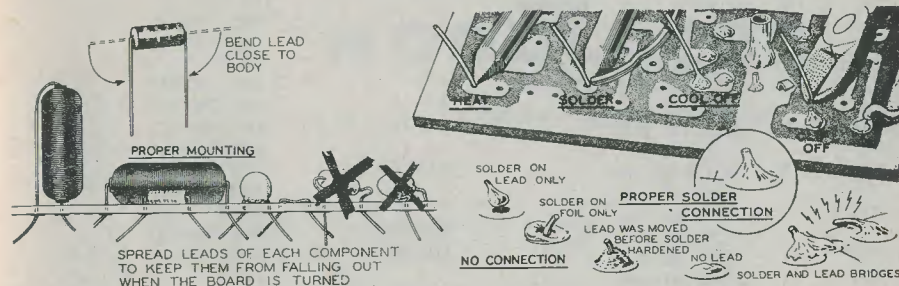


Fig. 4. Showing the component mounting and circuit board soldering procedure—right and wrong methods

of component mounting and soldering procedure are shown in Fig. 4. The photographs show a partly assembled OS-1 printed circuit board with the valveholders

supplied complete with an instruction manual, featuring a circuit diagram, circuit description, pictorial diagrams, step-by-step assembly and wiring instructions, voltage chart, operation, and other useful information.

#### Components List

Part No.	Per Kit	Description	Supplier	Part No.	Per Kit	Description	Supplier
<i>Resistors ±5% ½ watt</i>				<i>Resistors ±5% 3 watt</i>			
H-680C5	1	68Ω	Erie	3-222W5	2	2.2kΩ	Plessey
H-621C5	1	620Ω	"	<i>Condensers (ceramic and silver mica)</i>			
H-511C5	1	510Ω	"	21-527	1	½pF ±½pF ceramic tube	L.E.M.
H-363C5	1	36kΩ	"	20-527	1	20pF ±5% silver mica	"
H-514C5	1	510kΩ	"	20-528	1	50pF ±5% silver mica	"
H-134C5	1	130kΩ	"	20-501	1	200pF ±5% silver mica	"
H-273C5	1	27kΩ	"	20-529	1	500pF ±5% silver mica	"
<i>Resistors ±10% ½ watt</i>				21-508	1	500pF ceramic disc	Hunts
H-221C10	2	220Ω	"	21-511	4	10,000pF ceramic disc	"
H-271C10	1	270Ω	"	21-525	1	0.03μF 1,500V ceramic disc	"
H-471C10	1	470Ω	"	<i>Condensers (paper)</i>			
H-102C10	2	1kΩ	"	23-513	1	0.002μF 600V	Hunts
H-152C10	1	1.5kΩ	"	23-517	1	0.005μF 600V	"
H-332C10	2	3.3kΩ	"	23-511	2	0.02μF 400V	"
H-682C10	3	6.8kΩ	"	23-504	1	0.05μF 250V	"
H-103C10	7	10kΩ	"	23-505	2	0.1μF 250V	"
H-153C10	3	15kΩ	"	23-11	1	0.1μF 600V	"
H-104C10	2	100kΩ	"	23-63	1	0.25μF 400V	"
H-154C10	2	150kΩ	"	<i>Condensers (electrolytic)</i>			
H-224C10	1	220kΩ	"	25-512	2	8μF 500V	Dubilier
H-274C10	1	270kΩ	"	25-501	1	25μF 25V	Plessey
H-394C10	2	390kΩ	"				
H-474C10	4	470kΩ	"				
H-105C10	4	1MΩ	"				
H-125C10	1	1.2MΩ	"				
H-106C10	1	10MΩ	"				
<i>Resistors ±10% 1 watt</i>							
1-103C10	1	10kΩ	"				
1-223C10	1	22kΩ	"				

Part No.	Per Kit	Description	Supplier	Part No.	No. Kit	Description	Supplier
25-502	2	50+50 $\mu$ F 300V	T.C.C.	<i>Tagstrips-Knobs</i>			
25-523	1	50+50 $\mu$ F 350V	Hunts	431-14	1	1 way+earth tagstrip (R.H.)	Ariel Pressings
<i>Coils</i>				431-511	1	1 way+earth tagstrip (L.H.)	"
45-512	1	350 $\mu$ H	Kayblex	431-2	2	2 way tagstrip	"
45-513	2	300 $\mu$ H	"	431-10	1	3 way tagstrip (centre-tag earth)	"
<i>Potentiometers-Switches</i>				431-509	2	5 way tagstrip (centre-tag earth)	"
10-524	1	10k $\Omega$ lin. pot. pre-set	Dubilier	431-502	1	4 way tagstrip	"
10-525	2	50k $\Omega$ lin. pot. pre-set	"	462-506	4	Knob, with skirt	B. & G. Plastics
10-526	2	100k $\Omega$ lin. pot. pre-set	"	<i>Valves-Rectifier</i>			
10-527	1	2M $\Omega$ lin. pot. pre-set	"	411-502	2	ECF80	Mullard
10-528	1	10k $\Omega$ lin. pot.	"	411-521	2	EF80	"
19-505	1	25k $\Omega$ lin. pot. with switch	"	411-25	1	ECC82 (12AU7)	"
63-520	1	4 position switch	Plessey	411-522	1	EZ80	"
63-521	1	5 position switch 2-wafer	"	411-524	1	Cathode ray tube, type 3AFP1	E.T.E.L.
<i>Valveholders-Sockets</i>				57-505	1	Selenium rectifier K8/40	S.T.C.
434-528	5	9 pin valveholder (printed circuit type)	Plessey	56-502	1	Diode	G.E.C.
434-502	1	9 pin valveholder	"	<i>Miscellaneous</i>			
434-526	1	9 pin valveholder for C.R.T.	Cinch	54-516	1	Power transformer	H.G. Brown
436-503	3	Black socket	Belling-Lee	85-508	1	Printed circuit board	Mills & Rockleys
436-2	1	Black socket (non-insulated type)	Francois	211-501	1	Handle with 2 end plates	Taylor
436-504	4	Red socket	Belling-Lee	260-1	2	Crocodile clip	Bulgín
206-514	1	Valve screening sleeve	Plessey	414-503	1	Graticule	Priestleys Studios
258-506	3	Spring, valve retainers (large)	"	481-504	1	Mounting plate, for electrolytic capacitor	Plessey
258-507	3	Spring, ditto (small)	"	206-512	1	C.R.T. shield	"
				595-523	1	Instruction manual	"

## IMAGE ORTHICONS AT HOME AND ABROAD

The flexibility of operation provided by the wide range of English Electric Valve Co. 4.5in Image Orthicons is reflected in the recent announcements concerning installations using the new Marconi Mark IV television cameras. The Ampex Corporation, U.S.A., has taken delivery of ten of these cameras, three have been supplied to Poland and two to Tyne Tees Television in Great Britain—all fitted with E.E.V. Co. tubes.

Eleven Marconi cameras using 4.5in E.E.V. Co. camera tubes have been supplied

to Brazil for use in the new television station at Recife which is owned by Empresa Jornal do Comercio S.A. A suite of three studios and an o.b. van have been equipped with the most up-to-date units and scheduled test transmissions are now in progress.

3in and 4.5in Image Orthicon camera tubes manufactured by E.E.V. Co. are now marketed for many applications including studio and outside broadcast use under differing lighting conditions, colour television and general industrial, medical and scientific use.

## Low-Power

# TRANSMITTER MODULATOR


by David Noble, G3MAW, and David Pratt, G3KEP

*A low power modulator designed especially for the 160 metre transmitter described in our August 1959 issue.—Editor.*

SINCE THE PUBLICATION OF THE WRITERS' "Transmitter Circuit for 160 Metres" in the August 1959 issue of *The Radio Constructor*, there have been several requests from readers for a suitable modulator design. As the transmitter in question was

designed for the 160 metre band, and this larger modulator will be described at a later date.

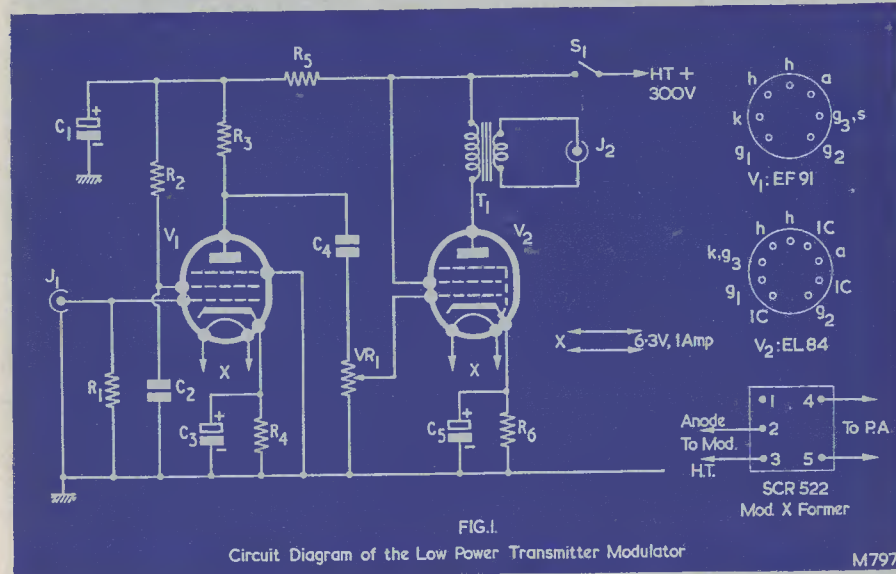The small modulator described herein has been used with much success on the 160 metre transmitter, and also on a low power experimental transmitter for 10 metres.\*




designed for the 160 metre band, it is, therefore, only used on low power, and a single-ended modulator using a 6V6 or similar valve may be used. The writers' present modulator design used with the TT11 p.a. stage is a push-pull circuit with high power ratings. This was made principally for the reason that it could be used, if desired, for a rather more higher powered transmitter for the other

**Circuit**  
The circuit consists of a very simple straightforward and orthodox two stage amplifier using the EF91-EL84 valve types. Although the EF91 is designed as an r.f. pentode, it functions very well in this a.f.

\*"QRP Transmitter for Ten" — Noble & Pratt, January 1959. *Short Wave Magazine*.

application. The input is intended for a crystal microphone, a coaxial socket being provided for this on the left-hand side of the chassis. The modulator gain control is a standard broadcast receiving type potentiometer with the switch  $S_1$  being inserted into

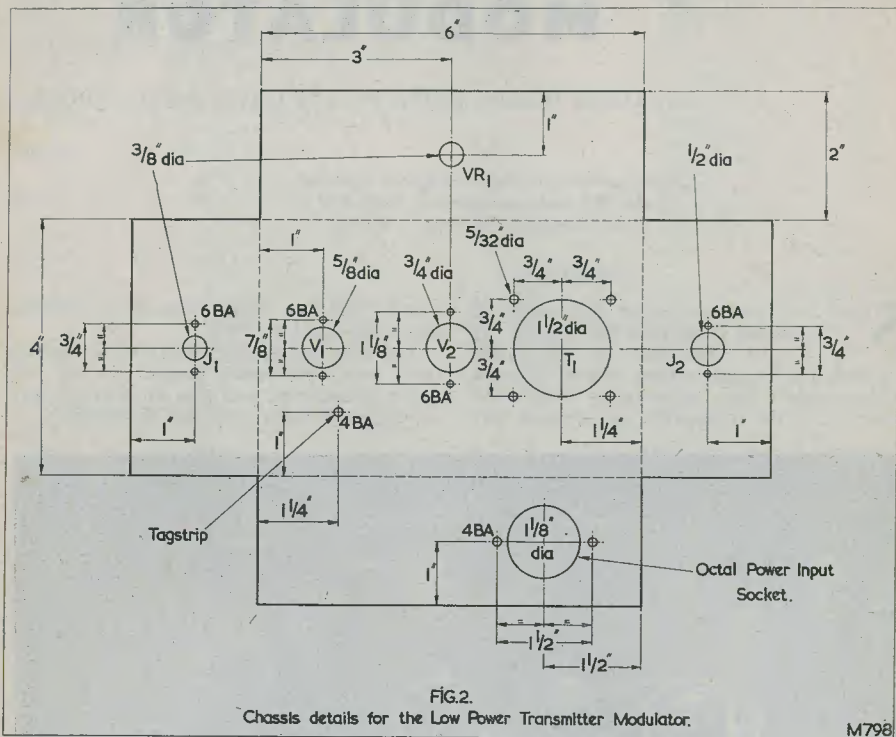transformer was that type used in the SCR522 transmitter. This transformer (A103018), connections for which are given in Fig. 1, is available quite cheaply on the surplus market. Other modulation transformers of a similar type may, however, be



the h.t. line as shown in Fig. 1. The output is taken via an insulated coaxial socket, the secondary of the modulation transformer being connected to h.t. potential at the transmitter. The modulation is fed to the transmitter via a coaxial lead fitted with insulated plugs; this merely for neatness and insulation. Jack plugs and sockets have been tried in this position but have been found to break down due to the high peak voltages involved.

In the prototype modulator, the modulation

used, but slight changes in the chassis dimensions will, of course, be necessary.

#### Power Requirements

An h.t. supply of 300 volts at approximately 40 milliamps is required for the modulator, and the 6.3 volt heater consumption is just over one amp. Unless the mains transformer in the transmitter has a h.t. current rating of, at least, 120 milliamps, it is recommended that the modulator be run from a separate power pack.

#### Components List

<b>Resistors</b>	
$R_1, R_2$	2.2M $\Omega$ 10% $\frac{1}{4}$ watt
$R_3$	1M $\Omega$ 2% $\frac{1}{4}$ watt
$R_4$	4.7k $\Omega$ 20% $\frac{1}{4}$ watt
$R_5$	22k $\Omega$ 10% $\frac{1}{4}$ watt
$R_6$	150 $\Omega$ 20% $\frac{1}{4}$ watt
<b>Condensers</b>	
$C_1$	8 $\mu$ F 350V wkg. electrolytic
$C_2$	0.1 $\mu$ F 400V wkg. paper
$C_3, C_5$	25 $\mu$ F 25V wkg. electrolytic

$C_4$	0.01 $\mu$ F 400V wkg. paper
<b>Miscellaneous</b>	
$VR_1$	500k $\Omega$ carbon potentiometer, log. with switch
$V_1$	Valve type EF91, 6AM6, Z77, etc.
$V_2$	Valve type EL84, 6BQ5, etc.
$T_1$	SCR522 modulation transformer or similar
1	Co-axial socket
1	Insulated co-axial socket
2	Valveholders
	Chassis and front panel

## A CONSOLE RECORDER FOR Musique Concrète\* AND ELECTRONIC MUSIC

By F. C. JUDD, A.Inst.E., G2BCX

*Our contributor, well known to readers of The Radio Constructor, gives details of a very comprehensive tape recording installation and its special uses, introducing his subject with several examples of musique concrète composition*

THE MOST STRIKING DIFFERENCE BETWEEN electronic and traditional music composition is that the former cannot be performed in public by a musician. The process of transforming sounds by cutting, splicing, retarding, accelerating or reversing magnetic tape excludes this possibility and leads to a different procedure in both composition and reproduction.

As there are no musicians to play *concrète* or electronic music and equally few able to compose, there is ample opportunity for original and interpretative re-creation. The composer of the "new music" has little need to offer a justification of his work, he can regard this as an experiment in an unexplored field and can supply musical motive by pointing to the fascination of creating new sounds.†

The following two examples of this new vogue in music were carried out with the aid of equipment designed and constructed with little more than the facilities available to many amateur recording enthusiasts. These and similar compositions are well within the scope of those willing to construct equipment on similar lines, or modify an existing recorder and build a few additional circuits for the creation of special effects and sounds.

The first example is one of an amusing composition based on the well-known melody *The Three Blind Mice*. The recording was made with the aid of the console recorder shown in the photographs and a multi-vibrator which, together with tone shaping

circuits and an electric plectrum guitar, were used to produce the musical tones for both the introduction and the main theme. The guitar was used mainly for a background of chords and the production of special musical sounds and effects. Since the title of the finished composition was *Three Mice on a Blind* little imagination was needed to create a theme applicable to three inebriated mice. Echos and the stereophonic effect were introduced so that some of the sound, like the three boisterous rodents, was made to move somewhat unsteadily along a path between two loudspeakers positioned for conventional stereo reproduction.

Another example of original composition, this time monophonic and also descriptive, was called *The Butterfly*. It was based on a rhythmic background from a series of endless tape loops with a flight sequence realistically simulated by arpeggios on relative diminished and minor chords from the electric guitar. Extensive use was made of artificial reverberation (echo) and speed control, conventional tape cutting and splicing being used for the final assembly of the sequences and for removing the "attack" and/or "decay" of certain sounds. Concrete sound sources were a deep set drum and a 24in cymbal, which were of course recorded via a microphone. The final composition lasted two minutes but took three days to record, and won the writer a first award for originality in composition and technique.

#### The Console Recorder

The popular domestic tape recorder does

\* When first employed, *musique concrète* referred to music which was entirely synthesised by such devices as the drawing of sound waveforms for subsequent reproduction by electronic means. Currently the term also embraces the production of sounds given by electronic oscillations, shaping circuits and the like.  
—Editor.

† Electronic Music and Musique Concrète. By F. C. Judd, A.Inst.E. (published by Neville Spearman Limited).

not readily permit special recording techniques, although simple *musique concrète* composition can be created with it. Two tape recorders, however, may be used most effectively and the procedure is to make a recording on one machine and transfer it, with added material, to a tape on a second machine. A more flexible method is to use both tracks of a standard tape, recording from one track to the other as required. By this method three or four recordings can be finally dubbed on to a single track. One or more extra playback heads may be used for controlled artificial reverberation, this being an extremely potent effect and widely used in the production of electronic music and *musique concrète*.

The very versatile equipment used by the writer incorporates all these features. It was entirely home constructed, including the deck, and may therefore be of interest to the more ambitious recording enthusiast. Stereophonic or monophonic recording approaching professional standards with a level frequency response (record to playback) of 20 to 15,000 c.p.s. and a very low percentage


of harmonic and intermodulation distortion was the primary design requirement for first class reproduction. No less than nine "pitch related" speeds as well as gradual speed variation are available. Two pairs of record and erase heads, one pair for each tape track, and a Truvox "in line" stereo head make provision for a flexible track-to-track recording system including the facility of direct monitoring during recording and the production of artificial echoes.

Two playback amplifiers, each with an output of 10 watts, two recording amplifiers, three bias oscillators, one for erase and two for recording, cater for most requirements since the amplifier units may be interconnected by a standardised system of screened patch cords and jacks. The recorder includes a built-in oscilloscope to which the output of any amplifier may be directly switched for the analysis of new sounds and a single frequency audio generator which provides a line up tone for stereo balancing and recording level.

All this equipment is housed in the console shown in the photographs. A built-in f.m.

receiver as well as a turntable and hi-fi pick-up are also included. Auxiliary equipment comprises two three-channel microphone and signal mixers, a tape head pre-amplifier for re-recording and echo work, a vibrato unit, several tone shaping networks

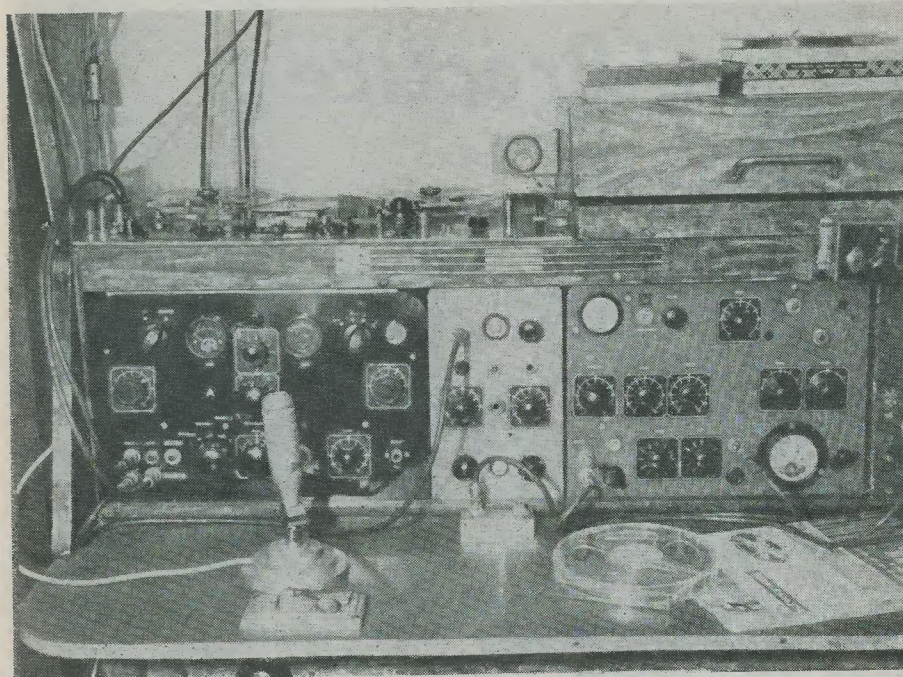recordings of "new music" that have been made with it. This departure from recording and conventional music may be frowned upon by some, but justification lies in the fascination of achieving something new and in exploring new territory.



General view of the console recorder

and special gating devices for automatic removal of the attack or decay of sounds.

The work involved in designing and constructing this seemingly complex equipment has been more than justified, not only by its flexibility and the excellent quality of reproduction but by the very satisfying

Most of the amplifiers were designed around circuits recently published by Mullard Limited.

The control scales and lettering used on the equipment are "Panel Signs" by Data Publications Limited.

## Northwood Evening Institute

Potter Street Northwood Middlesex

Classes for the R.A.E., G.P.O. Morse Test, Elementary Radio Theory and a more advanced course, will be held at Northwood again, beginning on 19th September; enrolments on Monday to Wednesday, 12th to 14th September, 6.30 to 8.30 p.m.

## The RADIO CONSTRUCTOR INDEX

The index for Volume 13, August 1959 to July 1960 inclusive, is now available. Direct subscribers to the magazine will already have received their copy enclosed with this issue. For non-subscribers, copies of the index are available from us at 6d. each plus s.a.e., preferably 9in x 6in.



"Creating new sound" with the recording equipment described in the article. The writer frequently uses a special Ormston Burns Electric Guitar as well as an Audio Signal Generator and *Concrète Sounds* (sounds picked up by a microphone) for producing short film and TV backing tracks of abstract music and sound effects

# RTTY In Theory and Practice

by J. B. Tuke, G3BST


PART 4

AFTER DISCUSSING THE RELATIVE ADVANTAGES and disadvantages of the various methods of achieving r.t.t.y. signalling, we now come to the point of how to get these signals actually "on the air".

It was explained earlier how the only practical system—as far as the normal h.f. bands are concerned—is that employing frequency shift keying (f.s.k.), and we will at this point consider the various methods of generating these signals. The object of this article is not so much to give circuit diagrams with values which can be slavishly copied, but rather to discuss the relative merits of the various methods which exist for producing f.s.k. signals, leaving the enthusiast to make his own choice.

The methods of producing f.s.k. can be subdivided immediately under two main headings (a) Direct shift of the oscillator frequency, and (b) the s.s.b. system.

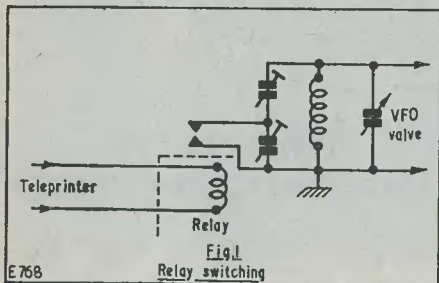Method (a) is, of course, the simpler of the two, and consists of circuitry which will change the oscillator frequency by the required amount upon the application of a changing d.c. voltage from the teleprinter.



The simplest possible way of doing this would be to have a relay, operated by the teleprinter signals, which would switch in (or out) a small condenser connected directly

across the v.f.o. tuned circuit. Although this system is not recommended for amateur use, it should not be considered as unworkable—it is in fact used on certain commercial transmitters mostly in the low frequency range. Its main snag, as far as amateurs are concerned, is obtaining the right type of relay, since this must be of the high speed type having, at the same time, very low self capacity (particularly to the body and coils). These are two conflicting requirements, high speed relays tending to be small, and low capacity types tending to be on the large side. If it is decided to use this circuit, better isolation and control can be achieved by having two condensers in series across the tuned circuit and arranging for the relay to short circuit one of them (see Fig. 1). Either or both of these condensers may be made variable thereby providing fine control of the frequency shift.

An improvement on this system is to use a diode (or diodes) in place of a mechanical relay. The diodes may be semiconductor or conventional valve types, though the former are more common. The *modus operandi* is really the same as that of the relay circuit, except that the relay is electronic and therefore the speed of operation is, for all practical purposes, instantaneous. The diode may be considered as conducting or non-conducting according to the polarity of the applied voltage, the capacitor therefore being effectively switched in and out of circuit. Isolation between the d.c. supply and the r.f. circuits is achieved by the use of r.f. chokes (see Fig. 2).


A further improvement on this method is to use one of the special variable capacity diodes. These devices have a self capacity which changes with the applied d.c. voltage, and they provide a simple method of achieving f.s.k. with the minimum number of components. It must be noted that in this case the frequency shift is dependent directly on

the applied voltage from the printer which must therefore be stabilised within close limits. This is unlike the two previous circuits where, providing more than a certain minimum voltage is applied, the full shift takes place.


An alternative way of changing the frequency of an oscillator is to use a reactance modulator. In this circuit arrangement, a second valve is connected in a phase shift network so that it behaves either as a condenser or an inductor, and it is then joined across the oscillator tank circuit (see Fig. 3). The value of the "capacity" or "inductance" is dependent upon the current drawn by the reactance valve, so that if its grid voltage is changed the "C" or "L" changes accordingly. The d.c. signals from the teleprinter are therefore applied to the grid, and are reproduced as reactance changes across the oscillator tank circuit, thereby producing f.s.k. It must be remembered that, although the deliberate voltage changes are applied to the grid, a change of any of the electrode voltages will produce a change in anode current and a consequent change of reactance. A stabilised h.t. supply may therefore be considered essential with this circuit. Despite this additional complication, it is an easy circuit to get going and is confidently recommended. It has the further advantage that it can be constructed out of parts which will be found in any amateur's junk box, and that it invariably works first time!

The amount of frequency shift produced may be altered in two ways. Either the value of the d.c. from the printer may be altered, or, what is often easier, the value of the

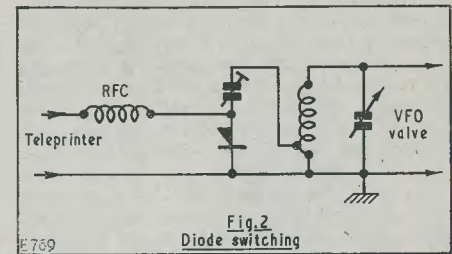of frequency shift produced will be greater or smaller according to whether the changing voltage is a large or small percentage of the total bias. The shift control, therefore, can be a variable resistor in the cathode of the reactance valve.



All the above systems suffer from one big disadvantage—if the operating frequency of the oscillator is changed, so also is the amount of frequency shift. Since, no matter which circuit is used, the frequency shift is produced by varying capacity (or inductance) relative to the oscillator tank constants, it follows that if these constants are altered, so is the amount of shift. This is not noticeable when "moving about" in one band, but if the oscillator tank components are changed, then the amount of frequency shift will require resetting. The large majority of amateurs do not, of course, change their oscillator tank constants when changing from one band to another—they simply use doublers and treblers. Unfortunately this does nothing to ease the problem, but only

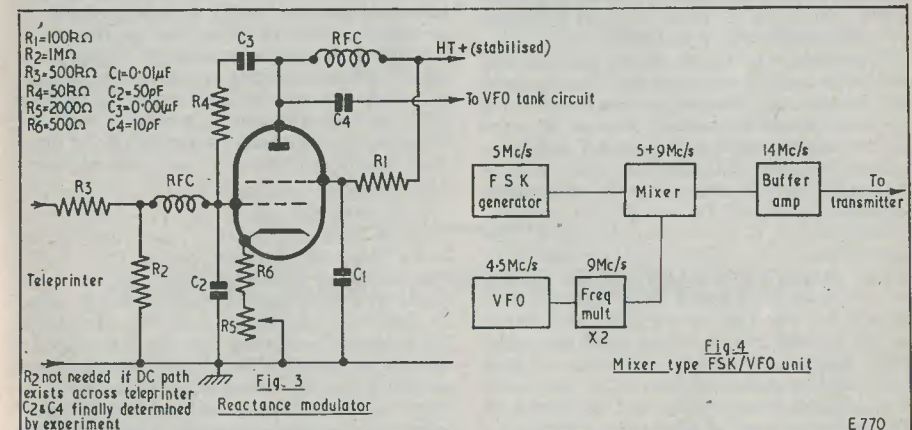

fixed bias applied to the reactance valve may be altered instead. Since the changing voltage from the teleprinter is applied on top of the steady bias, it follows that the amount

puts it in a different light. If an f.s.k. signal with a shift of 800 c/s is generated on, say, 3.5 Mc/s, and this is doubled to 7 Mc/s, the shift will also be doubled to 1,600 kc/s, and

if the frequency is again doubled to 14Mc/s, the shift will become 3,200 c/s! Consequently, resetting of the shift will be required whenever the band is changed—whether the oscillator frequency itself is altered, or whether frequency multipliers are used.

One way of overcoming this difficulty is to use the mixing technique, where the f.s.k. device is not associated directly with the v.f.o., but with another oscillator operating on a completely different (and usually fixed) frequency which has its output mixed with that of the v.f.o. to provide the final frequency (see Fig. 4). For example, the f.s.k. generator might operate on, say, 5 Mc/s. This could be mixed with a v.f.o. running on 1.2 to 1.5 Mc/s to give an output in the 80m. band, and with a v.f.o. on 2 to 2.15 Mc/s for output in the 40m. band, and so on. The amount of shift is obviously unchanged and independent on the final frequency. Although a perfectly sound system, this design involves a great deal of work simply to add r.t.t.y. to a transmitter, while there are the other much simpler methods; it may, however, appeal to those who already use a "mixing" system to provide their v.f.o. frequencies.

It is pertinent at this point to mention f.s.k. as applied to crystal oscillators. Any of the aforementioned shift circuits can be used, but their success is likely to depend upon the characteristics of the individual crystal, and would be difficult to forecast. It is unlikely that the required amount of frequency shift can be produced straight away, so that a crystal f.s.k. oscillator normally operates on a fairly low frequency and is followed by a number of frequency multipliers. Attempts to produce large shifts on a crystal often lead to instability.

The alternative to producing f.s.k. in the oscillator itself is to use an s.s.b. transmitter (or at any rate, the exciter portion). It is obvious that if a constant tone is fed into the modulator of an s.s.b. exciter, a definite carrier frequency is produced, and that if the audio tone is changed, then the carrier frequency is shifted by exactly this amount. Consequently, if two alternate tones, one corresponding to Mark, and the other to Space, separated from each other by 800 c/s (or whatever the desired value of shift may be) are fed into the s.s.b. exciter, the output is f.s.k. by 800 c/s, no matter what the actual radio frequency may be. It does not matter what the frequency of the audio tones are (providing they are within the band-pass of the audio section of the s.s.b. exciter) so long as they differ by the required amount of frequency shift.

The requirements for this system (apart from an s.s.b. transmitter!) are no more than an audio oscillator which will vary its fre-

quency by the required amount on being fed with teleprinter voltages. This is not difficult to arrange and, since it is at audio frequency, direct connection may often be made between the oscillator and teleprinter contacts—as for example when extra capacity is added across a phase shift oscillator working in the a.f. range.

It is not seriously suggested that any would-be r.t.t.y. enthusiast should sit down and build an s.s.b. transmitter in order to use this mode of transmission, but it may encourage some "s.s.b. merchants" who are becoming interested in r.t.t.y. to know that they already possess the most sophisticated type of r.t.t.y. transmitter and that the only additional item required is a small audio oscillator.

It is interesting to note that when using an s.s.b. transmitter for r.t.t.y., the amplifier stages may be run in class C, since amplitude linearity between input and output no longer matters. This is important, since some amateur s.s.b. transmitters are not designed to operate continuously in the linear mode without overloading—so that when using r.t.t.y., the operating conditions of the final should be changed to class C in order to take full advantage of the increased efficiency and reduced anode dissipation.

From the foregoing it will be agreed that the modifications to any transmitter to produce f.s.k. are extremely simple and can be applied with little difficulty. Certainly the transmission side of r.t.t.y. should dismay no one. Whatever system is used, it is emphasised that some sort of filter should be interposed between the teleprinter contacts and the shift device (unless the latter is a mechanical relay). This filter need only be a simple R-C device as outlined earlier. The values are not critical and the filter should progressively attenuate frequencies above 125 c/s—although a sharp cut-off is better if this can be arranged. Omission of the filter may possibly produce the most objectionable "key clicks".

Regarding the use of an f.s.k. transmitter, there is little to mention, the adjustments being those which are employed for normal c.w. working. There is no doubt that any faults in the transmitter will certainly come to light very quickly due to the continuous "key down" operation. This is not so likely with transmitters which have been designed primarily for telephone work, but the "c.w. only" enthusiasts may be surprised how the scent of cooking insulation permeates the shack after a long r.t.t.y. contact. This is not a problem peculiar to amateurs—commercial c.w. transmitters are "de-rated" when used for r.t.t.y. In fact the commercial problem is more acute as transmission may

continue unbroken throughout several days or weeks!

The simplest possible solution does not lie in replacing all over-run resistors, etc., but in the installation of a small air blower. It is surprising how the overheating problem disappears (or should one say is wafted away) when a comparatively small air draught is fed into the lower regions of the transmitter. We are not discussing forced-air-cooled p.a.'s or anything like that—simply the introduction of cool air, which is left to find its own way out, into the transmitter. Small motor blowers can be obtained on the surplus market and a little bit of elementary pneumatics with small bore plastic pipe will save the transmitter from disappearing in a cloud of smoke. The blower should only operate when the h.t. is applied.

Using r.t.t.y. should not cause t.v.i. problems—in fact in some cases this mode may free the amateur from trouble, where the transmission produces either shock excitation, or an overall brightening (or darkening) of the received picture. This is objectionable when c.w. keying is employed, but when "switch on" and "switch off" are separated by several minutes, as with r.t.t.y., it may well pass unnoticed. If f.s.k. produces t.v.i. particularly where it was not troublesome before, then there is something radically wrong with the transmitter, or excessive sidebands are being radiated due to omission of the filter. The aerial current should not change due to alteration from Mark to Space, since the r.f. circuits are usually sufficiently wide-band to consider the two signals as one.

The aerial for an r.t.t.y. transmitter is like any other aerial, directivity always being an advantage. Commercial systems favour rhombics, but this is impracticable for most amateurs, and it is also open to question whether the average amateur requires the high directivity produced by a correctly operated rhombic.

Some form of a.f. standard is required for

adjusting the amount of shift of any type of transmitter, and a calibrated audio oscillator is extremely useful. If an accurately calibrated one is not available, all is not lost, providing a stable variable a.f. oscillator can be produced. In the absence of a calibrated oscillator, the following method may be adopted. Listen on the station receiver to a commercial station using r.t.t.y. which is known to be using the correct value of shift. Zero-beat the audio oscillator with the alternate Mark and Space tones, and note these settings. Now switch on the f.s.k. generator, and arrange that it produces the same pair of tones in the receiver for Mark and Space as were produced by the commercial station—this being indicated by the oscillator zero beating on the same two settings. Providing the a.f. oscillator does not drift during this setting up procedure, the shift will be remarkably accurate.

One final point must be made before leaving f.s.k. devices—stability is of the utmost importance. If it is decided to use a system where the amount of shift is dependent upon the voltage produced from the printer, it is advisable to use batteries for this purpose, since if power supplies are used (and only a few volts are required to cause stabilisation problems) mains fluctuations will play havoc with the shift. H.T. supplies to the reactance modulator, its associated oscillator, and the v.f.o. (if separate) must be stabilised. The frequency of the v.f.o. must not shift even minutely when subsequent stages are switched on. Amateurs must operate highly selective r.t.t.y., and although this is primarily a job for the receiving end, a stable transmission is a first essential.

The final instalment of this article will deal similarly with receiving circuitry—discussing their relative merits, and leaving the amateur to take his choice. In transmitting as with receiving, the difference between simple and sophisticated circuitry is not so much in the actual results, but in ease of operation.

## A NEW HIGH POWER MAGNETRON

*Designed for high power long range radar applications, the M566 is the latest addition to the range of magnetrons marketed by the English Electric Valve Co. Ltd. This water and forced-air cooled, multi-resonator, pulse operated valve has a peak input power rating of 6mW and operates at a fixed frequency within the limits of 2,750 and 2,860 Mc/s.*

*The M566 is designed for use with a separate water cooled electro-magnet and a launching*

*section for coupling the valve to wave-guide No. 10 (2.84 x 1.34in internal dimensions). The wave-guide may be pressurised to 65lb/sq in absolute; the minimum wave-guide pressure being 35lb/sq. in absolute.*

*Water cooling of the anode is incorporated with the electro-magnet and the window is cooled by air at high pressure in the wave-guide. Low pressure air cooling may be used on the cathode terminal.*

# A High Sensitivity Shorted Turns Tester

Designed by M. D. ROBERTS

AN ITEM OF TEST EQUIPMENT WHICH IS always of considerable use, whether in the hands of the amateur home-constructor or the professional service engineer, is a shorted turns tester. Such a tester may be readily brought into service to discover faults which are quite impossible to diagnose by normal visual or resistance tests, these faults including such frequently occurring examples as adjacent turns short-circuiting in wave-wound coils, and in line output and mains transformer windings, provided that the latter are removed from their cores.

The shorted turns tester described in this article has been developed to provide a considerably high degree of sensitivity. Due

to the low frequency at which it operates (2.5 kc/s) it is, also, capable of detecting, without misleading readings due to excessive oscillator loading, shorted turns in windings having a large number of turns. A further attractive feature, again the result of the low operating frequency, is that it will not normally be affected by absorption due to resonance in the coil being tested. It is extremely unlikely that the self-resonant frequency of any coil presented to the tester will be as low as 2.5 kc/s.

## Circuit Diagram

The circuit of the tester appears in Fig. 1. The oscillator coil assembly shown in this diagram consists of a coil fitted to one end

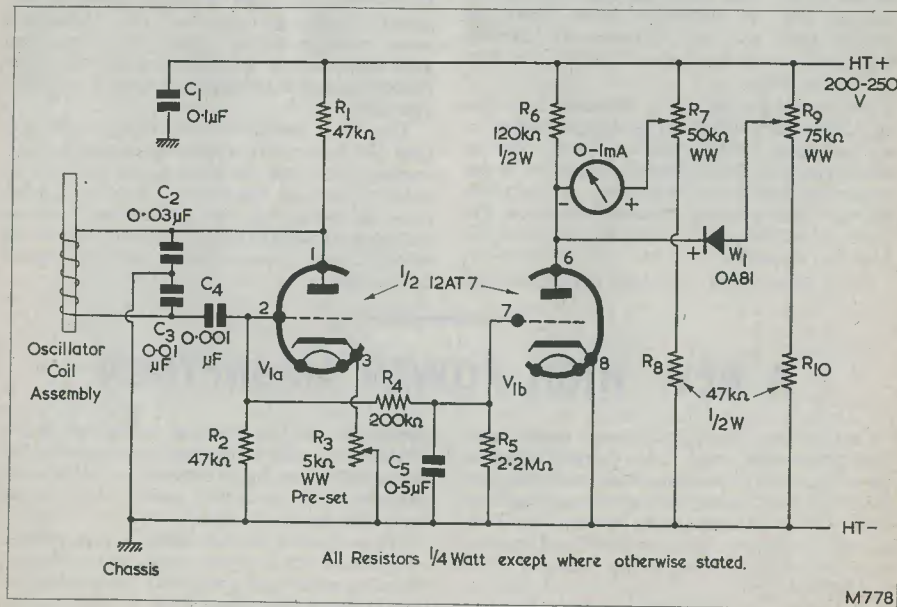


Fig. 1. The circuit of the high-sensitivity shorted turns tester

of a relatively long core made up of a number of lengths of insulated soft iron wire. Part of the core projects from the oscillator coil, and suspect windings are tested by being passed over this projection.

short-circuited turns is placed over the core, energy is drawn from the oscillator circuit and oscillator efficiency drops accordingly. This results in a drop in the negative voltage on the oscillator grid.

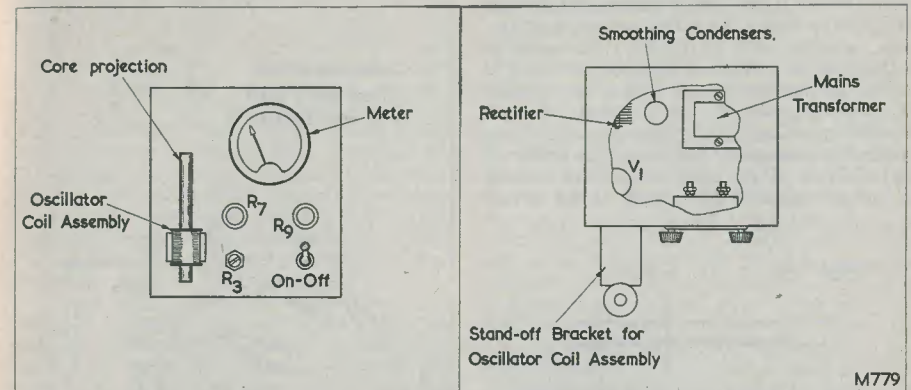


Fig. 2. A suitable front panel and parts layout for the tester. In the lower view, part of the cabinet top is cut away to show the main chassis components. The stand-off bracket for the oscillator coil assembly should be made of insulating material

The oscillator coil forms the inductive section of a Colpitts oscillator tuned circuit. The capacity tuning the coil is provided by  $C_2$  and  $C_3$  in series, the "earthy tap" into the tuned circuit appearing at the junction of these two condensers.  $R_2$  and  $C_4$  are oscillator grid leak and condenser respectively. A pre-set variable resistor,  $R_3$ , is inserted in series with the cathode of the oscillator triode,  $V_{1(a)}$ , in order to provide a sensitivity control.

A negative voltage, with respect to chassis, appears on the grid of  $V_{1(a)}$  due to leaky-grid action, and this voltage is passed, via the filter  $R_4$ ,  $C_5$ , to the grid of the amplifier triode  $V_{1(b)}$ . In the anode circuit of  $V_{1(b)}$  is connected an indicating meter, together with a zero-adjust potentiometer and an overload protection circuit.

## Tester Operation

The purpose of the circuit is to show visually, with the aid of the meter, the effects on oscillator efficiency caused by passing suspect coils over the projecting soft iron wire core. When no coil is fitted over the core, the oscillator functions at maximum efficiency, with the consequence that maximum negative voltage appears on the grid of  $V_{1(a)}$ . If a winding which has no short-circuited turns is placed over the core, oscillator efficiency remains unaltered and the negative voltage on  $V_{1(a)}$  grid maintains its maximum value. If, however, a coil having

The amplifier triode  $V_{1(b)}$  is connected in such a manner, that changes in negative voltage on the grid of  $V_{1(a)}$  are shown visually as changes of current flow through the meter in its anode circuit.  $R_7$  is set up such that, when the voltage on  $V_{1(a)}$  grid—and, hence, that on  $V_{1(b)}$  grid—is at its most negative, the meter indicates zero current. When, due to a coil with a short-circuited turn having been fitted over the oscillator coil core, the negative voltage on  $V_{1(a)}$  grid drops,  $V_{1(b)}$  draws increased anode current and the meter reading increases.

It is possible to set up the circuit to offer a high level of sensitivity, with the result that unless suitable precautions are taken, currents in excess of 1mA may be passed through the meter when a faulty coil is presented to the tester. This eventually is avoided by the overload protection circuit given by the diode  $W_1$ , in combination with resistors  $R_9$  and  $R_{10}$ .  $R_9$  is adjusted such that, for anode voltages in  $V_{1(b)}$  which allow less than 1mA current to flow through the meter, the diode does not conduct. As soon as the anode voltage drops sufficiently far to cause a current of 1mA to flow through the meter, the diode conducts. In consequence, anode voltage is prevented from falling to any markedly lower value, and currents significantly in excess of 1mA cannot flow through the meter.

## The Power Supply

A mains power supply is required for the

tester. Provided that it incorporates a transformer giving isolation from the mains, the power unit may be of any conventional type, employing a valve, metal, or contact-cooled h.t. rectifier, as desired. The heater requirement for the tester circuit proper is 6.3 volts at 0.3A (or, using the series heater combination possible with a 12AT7, 12.6 volts at 0.15A). H.T. voltage should be 200 to 250 volts, and the power unit should be capable of providing 40mA h.t. current. Under normal working conditions, however, h.t. current consumption will be of the order of 10 to 20mA. There is no necessity to provide a voltage-regulated h.t. supply as the circuit

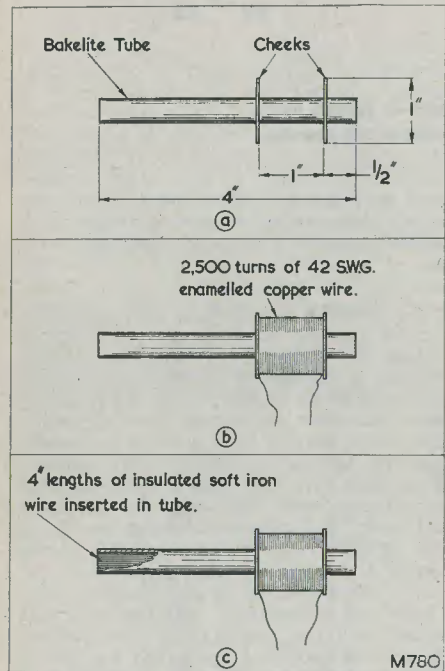


Fig. 3. The prototype oscillator coil assembly was constructed as shown here. (a) Two cheeks having a diameter of 1in were fitted to a Bakelite tube. (b) The coil, consisting of 2,500 turns of 42 s.w.g. enamelled wire, was then random-wound between the cheeks. (c) Finally, 4in lengths of 22 s.w.g. insulated soft iron wire were inserted in the tube and glued into position

is, to a certain extent, self-compensatory for changes in h.t. potential (an increase in h.t. potential causes a compensatory increase in negative grid voltage in  $V_{1(a)}$ ). Another

reason for not requiring a regulated h.t. supply is that the tester is a qualitative rather than a quantitative instrument. It is intended

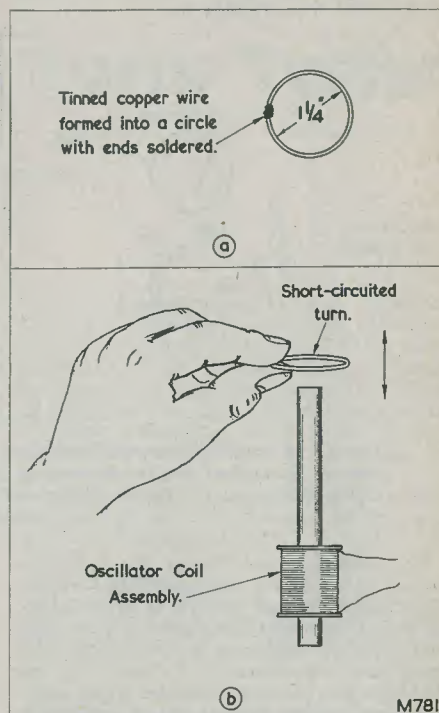


Fig. 4 (a) A simple short-circuited turn, made up as shown here, is necessary for checking and setting up the tester. (b) When the short-circuited turn is passed completely over the projecting oscillator coil core the tester meter current will rise. A measure of sensitivity may be obtained by loosening the coupling between the short-circuited turn and the core, as shown here. Maximum sensitivity corresponds to a given meter deflection with minimum coupling

to indicate that changes in oscillator grid voltage have taken place without defining such changes in terms of magnitude.

#### Construction

Few difficulties should be experienced with the construction of the tester for the reason that, due to the low operating frequency employed, component layout is not excessively critical. It would, nevertheless, be preferable to position the double-triode, and the components immediately connected to  $V_{1(a)}$ , reasonably close to the oscillator coil

connections. The circuitry around  $V_{1(b)}$  is of a "d.c." character, and any convenient positioning of components may be adopted here.

A suitable layout, including that for the front panel, is illustrated in Fig. 2. It will be noted in this diagram that all components, with the exception of the oscillator coil assembly, are intended to be fitted in a case. The oscillator coil assembly is mounted outside the case so that it becomes available for the testing of coils. In order to reduce losses in the oscillator coil it would be advisable to make the case, or at least that side of the case to which the coil assembly is fitted, of insulating material. The coil assembly should not approach any large metal area, including metal areas behind an insulated panel, by less than 3ins.

There will, obviously, be some heat dissipation inside the cabinet in which the tester, together with its power unit, is fitted. A simple means of ventilation should be provided to prevent excessive temperature rise.

#### The Oscillator Coil Assembly

The oscillator coil assembly is completely home constructed. Fig. 3 illustrates graphically the manner in which the prototype assembly was made up. A 4in length of Bakelite tube having an internal diameter of 1 1/8in and an outside diameter slightly in excess of 1 1/2in was obtained and fitted with 1in diameter cheeks, as shown in Fig. 3 (a). Approximately 2,500 turns of 42 s.w.g. normal enamel (or synthetic enamel type F) copper wire were then random-wound in the space between the cheeks, care being taken to keep the winding depth uniform as the winding operation proceeded. The total number of turns employed only requires to be held within an accuracy of 10%, and so approximate turn counting techniques will suffice.

The lengths of wire which constitute the core were then prepared. These consist of 4in lengths of 22 s.w.g. (0.028in diameter) soft iron wire, and they were primarily insulated by being dipped in an insulating varnish, such as shellac. When dry they are packed into the 4in Bakelite tube side by side and glued into position. Some 60 to 80

pieces of wire are required. It should be pointed out that it is essential to insulate the lengths of iron wire before inserting them into the tube otherwise excessive oscillator losses will occur with a consequent degradation in tester sensitivity.

#### Setting Up

After the tester has been completed it must be set up before it is ready for use. For this purpose it is necessary to have available a specially prepared single short-circuited turn which can be used to check circuit operation. Such a turn is illustrated in Fig. 4 (a). Before switching on,  $R_3$  should be set to its minimum resistance position. Also, the slider of  $R_9$  should be temporarily left at the bottom end of its track, in which condition no overload protection is provided for the meter. The tester may now be switched on. As the double-triode warms up,  $R_7$  should be adjusted to maintain the meter reading at any point near mid-scale. When the double-triode reaches full operating temperature,  $R_7$  is set to give zero reading on the meter.

It is next necessary to adjust  $R_3$  such that the negative voltage on the grid of  $V_{1(a)}$  is just within the grid base of  $V_{1(b)}$ . The amount of resistance inserted by  $R_3$  is experimentally increased until a reading of approximately 1mA is indicated on the meter, after which  $R_7$  is adjusted to bring the meter reading back to zero again. The short-circuited turn is then brought up to the oscillator coil core (as in Fig. 4 (b)) whereupon the meter reading should increase. The short-circuited turn should be advanced until the meter indication is slightly in excess of full scale deflection, whereupon  $R_9$  should be adjusted until the meter reading falls just below full-scale deflection.

The tester is now in a condition in which it may be used. However, it is advisable to make several further experimental adjustments to  $R_3$ , following up with adjustments to  $R_7$  and  $R_9$ , until a condition of maximum sensitivity is obtained, as indicated by the short-circuited turn. An increase of sensitivity will be evident when it is possible to obtain a given meter deflection with the short-circuited turn further away from the core.

Next Month . . .

## SIMPLE REFLEX SUPERHET THE PHONE - GUARD BEGINNER'S S.W. RECEIVER





# RADIO topics

BY RECORDER

IF THE MATTER WERE NOT OF SUCH A serious nature, the recent pother over "bugs" could be described as providing a wryly amusing combination of science-fantasy and Ruritanian comic opera. "Bugs" are transistorised listening devices which, secreted in Embassies and the like, transmit whatever speech they pick up to nearby receivers. So far as can be judged from newspaper reports, "bugs" are powered by an external transmitter. Presumably, this transmitter is sited at the receiving post and a sufficient amount of its energy is picked up by the "bug" to provide, after rectification, a source of h.t. for its own transmitting circuits, which then radiate on another frequency.

As some readers may have noticed, a "bug" (and rather an old one at that) was visible during a television newsreel recently when the American representative at U.N.O. demonstrated how it had been hidden inside a plaque. So far as could be seen from the television picture, the body of the "bug" consisted of a cylindrical housing about an inch to an inch and a half in diameter and an inch in length, with an aerial some eight inches long protruding radially from the diameter. Such an aerial (assuming it were a quarter-wave) would set the operating frequency of the "bug" around 300 Mc/s.

The Russian delegate pooh-poohed the American evidence and asked, in effect, when "the play would be produced". In a later reply the American representative stated that the "bug" would be operated with the aid of a "technical" device elsewhere.

Falling back on the term "technical" instead of describing a little more fully what seems to be a relatively simple electronic process, highlights, to my mind, the fact that

it may well be necessary for future diplomatic staff to be instructed in elementary electronics in addition to the complex subjects of their own calling. They would then be able to understand more readily the manner in which "bugs" operate and would not have to relegate them to a black magic pigeonhole labelled "technical devices". A general understanding of the functioning of "bugs" would, surely, assist in their earlier detection.

Present day "bugs" (again relying on newspaper reports) appear to be very tiny things indeed; so tiny that they may remain hidden in clothing without the wearer being even aware of their presence. One can sympathise with the security officers whose job it is to detect them. Some technically minded people might suggest that the best protection against such devices would be provided by holding secret conversations in rooms which were electrically screened. This screening would then act both to prevent the ingress of energising signals and to prevent the radiation from the room of transmissions from "bugs". In practice, however, the screening required would need to be extremely efficient. As most people who have worked at such frequencies will agree, it is impossible to get 100% screening at v.h.f. and higher frequencies by simply shrouding the screened object with wire netting or something of that order; it is necessary to shroud the object with unbroken copper sheet (or sheet made of a similarly good conductor) having all joins soldered or soundly connected together every few inches. And, even then, conductors carrying services such as telephone and lighting into the screened area would need to be fitted with filters!

Protection against "bugs" is not simple, and it is a sad comment on the rather lunatic

world in which we live that such things should exist.

## Film Dates

Turning to a lighter subject, some friends of mine complained recently that old films are presented on television without the viewer being advised of the year of their issue. I sympathised with this point of view: it is quite often desirable to know the year of issue, this enabling its dialogue to be followed with greater discernment. My friends were surprised when I next told them that the year of issue is shown on nearly all films televised, and that it is possible to see it on any receiver having reasonably good definition.

All films carry a copyright claim (which usually appears in the credits, before the start of the film, around the same time as the references to the sound recording system, etc.) this claim consisting of the word "copyright" followed by the year of issue. Simple, isn't it? The reason why most people fail to discern the copyright notice is that it is usually presented in small characters amongst credits which are not of interest to the average filmgoer or viewer. Also, the year is given in Roman instead of Arabic numerals. In recent films the word "copyright" may be replaced by the international copyright symbol, ©.

The following will help any readers who are a little rusty on their Roman numerals. The first three characters in the date of issue of any film are always MCM, these standing for 1900. MCM may be followed by XXX, signifying 30; by XL, signifying 40; by L, signifying 50; or by LX, signifying 60. These latter symbols will then be followed by the characters which stand for the last digit of the expression: V for 5; IX for 9; and so on. If the last digit is zero, no symbol follows that which defines the "tens". To take some complete examples, the Roman numerals MCMXXXIX stand for 1939, the numerals MCMXLIV stand for 1944, and the numerals MCML stand for 1950.

The next time you see a film on television look out for the copyright notice. Then you will know exactly the year in which it was issued.

## Music While You Drive

I have often thought that, during long periods at the wheel, a car radio can sometimes be nearly as much of a nuisance as a blessing. My reason for thinking this is that one normally wants relaxing entertainment whilst driving, and it just isn't possible for suitable programme material to be always available at all times of the day. There is, also, the particularly annoying feature of car

radio listening which is occasioned by programmes having orchestral music interspersed with dialogue. The music in such programmes tends to be annoyingly loud, with the result that one has to reduce volume; and the dialogue tends to be infuriatingly quiet, whereupon one has to turn the volume up again! This last effect is especially troublesome in a car because it is normally desirable to keep the output level of the radio sufficiently high to overcome ambient noise, but not so high as to distract attention from the road. Yet another shortcoming becomes evident when one is confronted with a long drive in the very early hours of the morning. One cannot normally use the car radio because hardly any stations are on the air!

All these snags are overcome by a car record player which has been introduced by Philips Electrical Ltd. This record player, the Philips' Auto-Mignon, accepts seven-inch 45 r.p.m. discs and is especially designed for permanent installation in a car. Amplification is provided by the radio already fitted, whereupon the whole installation becomes a car radiogram. The Auto-Mignon is capable of functioning from either a 6 volt or a 12 volt supply with the choice of positive or negative polarity.

Operation of the Auto-Mignon is simplicity itself. It has two controls, one being a gram/radio switch and the other being the record reject button. Records are played by inserting them into a slot; when they have finished playing they are automatically ejected. The record reject button is used only if it is desired to stop and eject a record before it has come to an end. The pick-up in the Auto-Mignon employs a crystal element with diamond stylus, and needle pressure is 10-12 grams. Output is quoted as 300mV. All the problems of possible disturbance by bumpy roads have been overcome by coupling the turntable assembly to a balancing system, and by fitting steadying weights to the underside of the turntable. Extensive tests, on the roughest roads and on the most difficult hills, and at any speed and with the sharpest turns, have demonstrated the stability of the player. At all times the stylus remains in the groove and reproduction quality is fully maintained.

If you want music while you drive—without the snags attendant upon broadcast entertainment—the Auto-Mignon provides the answer.

## Soldering Techniques and Problems

Smithy the Serviceman has several pet aversions, but I think that the hobby-horse he mounts most frequently and vituperatively is concerned with "solder tags which won't

solder". And who can blame him? There can be few things so infuriating as finding, when one has to make a connection in a crowded corner of a chassis, that the appropriate solder tag absolutely refuses to take any solder whatsoever. One scratches away at the tag with the iron (whose barrel, meanwhile, is melting great gouges out of adjacent wax-covered condensers) and all that results is the solder running off the tag like mercury.\*

It may give readers who have suffered from this trouble, when carrying out constructional or servicing work, a certain grim satisfaction to learn that electronics manufacturers have also torn their hair out on this very same point. I think it is fairly safe to say that manufacturers' troubles rose to a peak with the introduction of printed circuit assemblies and the subsequent dip-soldering and wave-soldering operations which were evolved for their mass production techniques.

An ordinary soldering operation consists of wrapping a wire around a tag and of applying a soldering iron and resin-cored solder. Without thinking about it, the person using the iron automatically rubs the bit against the wire and the tag, thereby, by abrasive action, removing oxide film and getting good thermal contact to the members of the joint. A quickly made joint results. If the members of the joint have a relatively tough oxide film on the outside it is still possible for the solder to "wet" the surface which has been rubbed clean, thereby providing a better thermal contact than is given via the bit alone. The resulting speedy temperature rise of the joint members then provides the resin in the solder with a chance to break down the remaining oxides, and a good joint results once more.

With dip-soldering and wave-soldering techniques there is no abrasive action to initially "start" the soldering of the joint. In the dip-soldering process all components are inserted into the board with their wires, or tags, protruding underneath; whereupon the board is lowered so that its underside is in contact with molten solder contained in a bath. The solder should then bridge over the protruding wires and tags to the sections of copper pattern through which they pass. In the wave-soldering process the components are mounted as for dip-soldering and the whole assembly is passed slowly over a stationary wave of continually replenished molten solder. Again, the solder should connect the protruding wires and tags to the

sections of copper pattern through which they pass. It should be noted that in neither of these two processes is there any abrasive action: the component leads and tags, and the copper of the pattern, must solder instantly.

At the introduction of the new soldering techniques it was found that instant soldering did *not* occur in many instances, and much research was put into this problem. Many of the faults discovered were obvious enough, but the fact that they are being corrected to satisfy printed circuit requirements means that standards throughout the industry will inevitably become higher. Thus, a frequent snag in the past with condenser and resistor wire ends has been that they have been soiled with grease or with the moulding resin used in the manufacture of the component. Special attention during manufacture and post-moulding cleaning operations have done a great deal to clear this trouble. Again and, perhaps, a little surprisingly, it has been found that tinned copper wire isn't always an ideal choice for making solder joints without abrasion. Because of this, some manufacturers have changed component wires from tinned copper to solder coated copper in order to meet printed circuit requirements. The solder coating has approximately the same thickness as the tin plating and it solders almost instantaneously.

Solder tags have been the subject of research in recent years, this being due to the general requirements of mass production and to the peculiar needs of printed circuits. Overall experience is worth quoting here, even though the facts may not surprise the older hands. Speaking generally, and keeping to the more economic tag finishes, it can be stated that electro-tinned solder tags are frequently a source of trouble, that hot tin dipped tags are almost perfect, and that silver plated tags are de-luxe! (Smithy will have to install a silver plating plant in his Workshop!)

Turning to a slightly different aspect of soldering, with which to conclude, some constructors and service engineers find themselves a little nonplussed when they encounter manufactured chassis having a yellow, brassy, appearance. Such chassis consist of mild steel, cadmium plated and "passivated". Passivation is a protective process which affects the outside molecules of the cadmium only; and it is quite simple to solder to a chassis having such a finish as the solder "wets" to the cadmium. A passivated chassis should *not* be heavily scraped before soldering as this may reveal the mild steel surface, to which it is much more difficult to solder.


# Winding

## COILS AND SMALL CHOKES

By "Quench Coil"

MANY CONSTRUCTORS OF RADIO EQUIPMENT, and other similar apparatus which require small chokes and random-wound coils, fight shy of trying to make these up themselves—often going to great trouble trying to locate something suitable from a dealer or from war surplus disposal stocks. If care is taken and the job is tackled in the right manner, excellent components of this type can, however, be

supporting iron wires, coil formers may be made very simply by winding gummed paper around a dowel of suitable diameter, as shown in Fig. 1. Care should be taken to ensure that the first few layers of paper do not stick to the dowel or it will be impossible to remove the former afterwards. By means of a nut and a bolt passing through the former, it now becomes possible to secure two Paxolin cheeks at either end, fibre

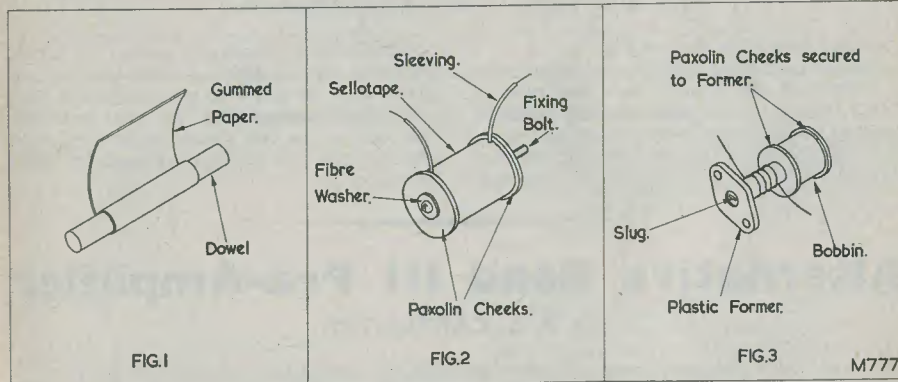

made quite easily in the home workshop. A small hand drill should be mounted as illustrated in the photograph, together with a shaft to carry the spool of winding wire. Two light springs, are fitted to the spool shaft, as shown, together with a brass bush whose position on the shaft can be easily adjusted. Varying degrees of spring tension may, in consequence, be applied to the spool. In this way the wire tension can be adjusted to suit differing winding conditions, and the spool can be prevented from unwinding too freely.

For chokes which do not require self-


washers being fitted under the bolt head and the nut. This assembly should next be painted with polystyrene dope, after which the threaded end of the bolt, with suitable packing to prevent damage to the threads, is held in the drill chuck. Winding then proceeds in the manner shown in the photograph. When complete, the choke has the appearance illustrated in Fig. 2, whereupon the protruding end of the bolt is at once available for mounting to the chassis.

Alternatively, cheeks may be fitted to an internally threaded polystyrene or Bakelite former, together with a nut and bolt to

\*I am indebted to Mr. A. D. Besford, G3NHU, for referring to soldering problems in a recent letter, and for raising some of the points mentioned here.

enable the assembly to be secured in the drill chuck. When the winding of this type of assembly is complete the bolt is removed and the requisite slug inserted, giving a complete

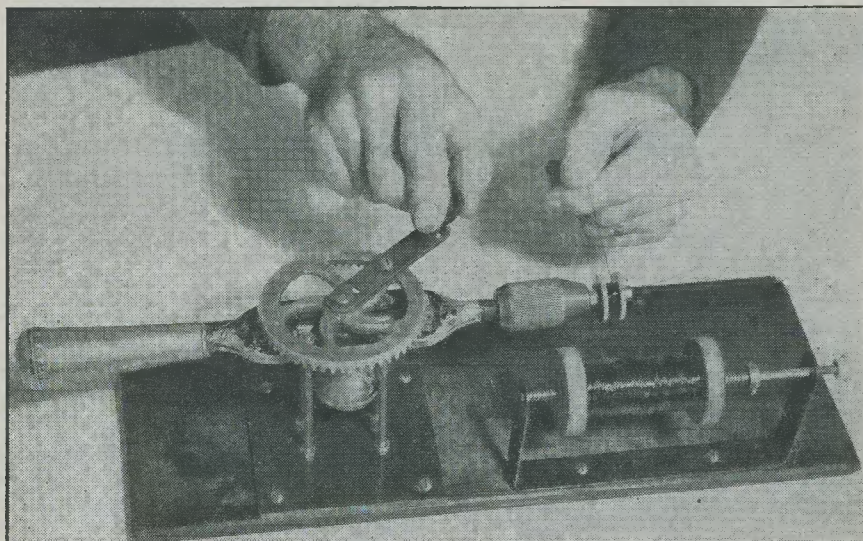working it from side to side in order to keep the turns even. Do not turn the drill too fast or the wire will tend to build up at one place.



The author winding a coil as described in the text

assembly similar to that of Fig. 3.

The ratio of hand drills varies from make to make. In the writer's case, the ratio is 4 to 1, which means that every 100 turns of the drill handle winds 400 turns of wire on to the coil former. The wire should be run through the thumb and finger during winding,

After a little practice it is easy to tell if the turns are too light or loose by the feel of the wire. It is a wise plan to have a trial run before commencing the final winding. The ends of the coil should be covered with sleeving and the bobbin finished off with Sellotape.

## Alternative Band III Pre-Amplifier

by A. S. CARPENTER

*In which our contributor describes modifications successfully carried out to a popular pre-amplifier design*


THE PRE-AMPLIFIER CIRCUIT PRESENTED here is suggested as an alternative to one described in an earlier issue of this journal.\* Its general appearance is identical with that of the previous pre-amplifier and, as similar components are used, the above and below chassis layouts may be similarly adopted. Both versions have been tested under stringent conditions and, of the two,

the arrangement depicted here is preferred by the writer. Where the original pre-amplifier is in use and already providing a good picture, no re-arrangement is required except where results are not sufficiently good.

No criticism of the previous pre-amplifier is made; the unit is a highly efficient one if properly constructed and used, and it has produced a tolerably satisfactory picture. Results, however, were only claimed on Channels 8, 9 and 10, and the importance of connecting impedances of the correct value to its input and output sockets was adequately

stressed. To receive Channel 11 transmissions, therefore, over a distance of 60 miles on a 6-element Yagi array was expecting

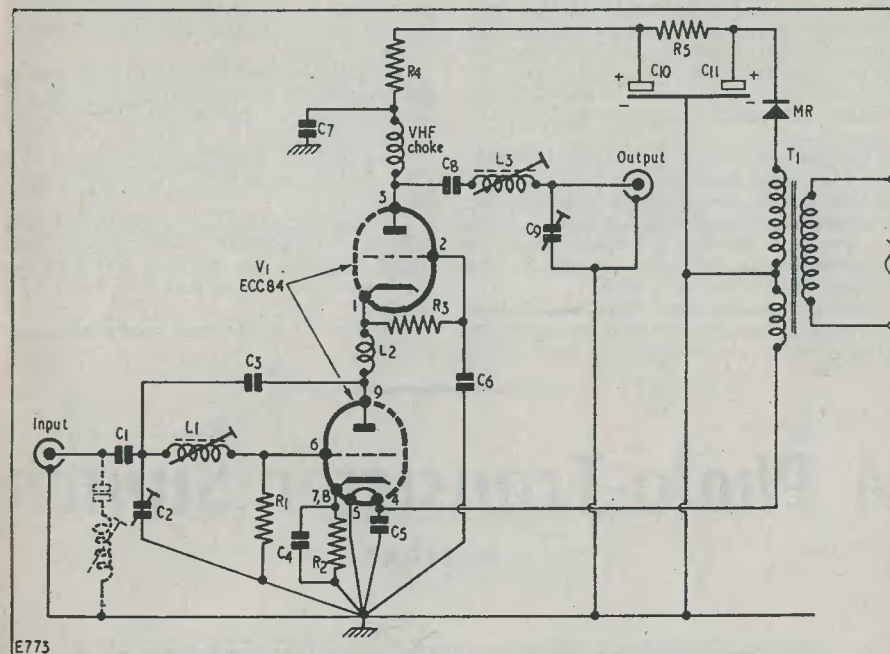maximum efficiency of all equipment preceding the television was vital. The aerial was very carefully positioned and oriented,



### Components List For the Modified Pre-amplifier

#### Resistors

- R<sub>1</sub> 220kΩ ¼ watt
- R<sub>2</sub> 100Ω ¼W
- R<sub>3</sub> 47kΩ ¼W
- R<sub>4</sub> 1.2kΩ ¼W
- R<sub>5</sub> 1kΩ ¼W

- V<sub>1</sub> ECC84. MR Miniature contact-cooled rectifier, 250V, 30mA

- T<sub>1</sub> Mains transformer, input 230V, output 200V at 30mA, 6.3V at 0.6 amp

#### Condensers

- C<sub>1</sub> 47pF, ceramic
- C<sub>2</sub>, C<sub>9</sub> 30pF, trimmers, ceramic
- C<sub>3</sub> 2pF, ceramic
- C<sub>4</sub>, C<sub>5</sub>, C<sub>6</sub>, C<sub>7</sub> 1,000pF, ceramic
- C<sub>8</sub> 500pF, ceramic
- C<sub>10</sub> 8μF, electrolytic
- C<sub>11</sub> 16μF, electrolytic

#### Inductors

- L<sub>1</sub> Teletron type 20T (modified)
- L<sub>2</sub> Teletron type 21T (or see text)
- L<sub>3</sub> Teletron type 22T (modified)
- V.H.F. choke—Teletron RFC2

#### Chassis

- Teletron Converter Chassis, modified

#### Miscellaneous

- 2 Coaxial sockets
- 1 B9A ceramic valveholder
- 1 3-way tagstrip, end tag earthed, wire, etc.

rather a lot of the pre-amplifier, and was certainly a most stringent test. Nevertheless, an attempt was made and reception proved possible. The receiver used was a five year old commercial model and, in view of this, it was realised right from the start that

care being taken with respect to matching. The resultant picture was passable but a fair amount of "snow" was present and, when steps were taken to lessen this, it was soon discovered that the pre-amplifier itself was not at fault but that impedances of unsuitable

\* "The HI-GAIN Band III Pre-Amplifier" by Derek Winters, *The Radio Constructor*, March 1958. Subsequently issued as Radio Reprint No. 8.

value were connected to its input and output sockets.

It was then decided to use pi-tuned circuits throughout instead of input and output transformers. The inductors in the pre-amplifier were simply modified by removing the single turn coupling windings, only the main windings being required. The re-arrangement proved most successful and "snow" disappeared completely from the screen.

The revised circuit is shown herewith. Band I or other breakthrough does not occur at this address due to opposing transmitter locations but should spurious signals cause patterning, a series tuned circuit could be incorporated at the point shown by the broken lines on the input side.

Inductor  $L_2$  is an extremely critical component upon it depending most of the gain; spacing, or closing, the turns, even

slightly, can cause large gain variations. Optimum results were obtained by winding four turns of 30 s.w.g. enamelled copper wire obtaining a diameter of  $\frac{1}{8}$  in, slight spacing of the turns being carried out whilst watching the picture, and using a long plastic knitting needle as a prod.

A slightly different method to that used in the original pre-amplifier circuit is employed for obtaining the potential for the grid of the second triode.

Note that the output circuit consists of a v.h.f. choke feeding the output inductor via  $C_8$ .

Capacitors  $C_2$  and  $C_9$  should be carefully adjusted for optimum operating conditions whilst watching the picture. For Channel 11, brass cores are needed in inductors  $L_1$  and  $L_3$ .

A full list of components accompanies this article.

# A Photo-Transistor Switch

By K. BERRY

*An article describing three different versions of a basic light operated relay circuit in which especial care has been paid to switching transistor stabilisation*

THE CIRCUIT DESCRIBED HEREWITH WAS developed to produce a general purpose light operated switch. The main requirements were reliability of operation, small size, and low power consumption. Several circuits were tried, but the one presented here gave by far the best results.

## Circuit Description

The preferred circuit, shown in Fig. 1, uses one photo-transistor, one transistor, one variable resistor, one fixed resistor, one relay and a silicon diode. It is powered from a six-volt supply.

The photo-transistor (OCP71) forms one arm of a potential divider supplying base bias to a transistor (OC72), the other arm being a 5k $\Omega$  variable resistor. When the photo-transistor is exposed to light, its effective collector-emitter resistance falls, i.e. it conducts. This has the effect of making the base of the OC72 more negative than when the OCP71 is in darkness.

The emitter of the OC72 is connected to the positive supply via a silicon diode

(OAZ208 or similar) which is supplied with a current of about 5mA by a 1k $\Omega$  resistor connected from the negative supply to the emitter of the OC72. A typical silicon diode characteristic is shown in Fig. 2 and it will be seen that when the diode is conducting, the voltage drop across it is substantially constant at 0.8 volts. Thus the emitter of the OC72 is stabilised at -0.8 volts (approx.) and, in order to switch the transistor on and off, the base voltage must therefore be varied about this given voltage. When the OCP71 is illuminated, the base of the OC72 becomes more negative than the emitter and the OC72 conducts, which causes the relay in its collector circuit to operate. When the OCP71 is in darkness, the base of the OC72 becomes positive with regard to the emitter and the OC72 is switched off (only  $I_{co}$  flows) causing the relay to fall out.

Measurements made on this circuit show that when the OCP71 is illuminated, the OC72 base is 0.25 volts negative with respect to the emitter, and, when the OCP71 is in darkness, the OC72 base is 0.28 volts positive

with respect to the emitter. Thus the transistor is well and truly off or on.


## Modified Circuits

The use of a silicon diode to stabilise the emitter voltage of the OC72 may be avoided as shown in the two alternative circuits.

The first alternative circuit (Fig. 3) completely omits emitter bias and relies on the fact that the base of a transistor must be about 0.15 volts negative with respect to the emitter before the transistor conducts. The circuit is quite reliable at room temperatures but may prove somewhat troublesome at higher temperatures due to increasing  $I_{co}$  in

relays are *not* capable of switching large powers, and if it is desired to break more than about 15 watts then this relay should be used to switch a second relay which has heavy duty contacts. A less sensitive relay can be used with a higher supply voltage but great care must be taken to ensure that the collector dissipation of the OC72 is not exceeded.

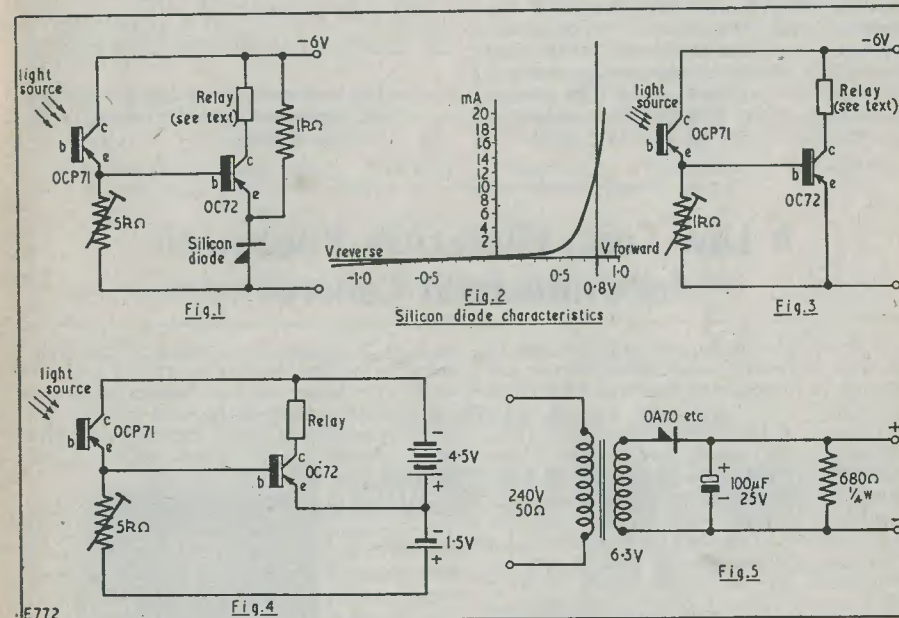Although a Mullard OCP71 photo-transistor was used for the prototype circuits, there is no need for the lack of same to prevent construction, an ordinary OC71 with the protective black paint covering removed working just as well. These circuits were in



the OCP71.

The second alternative circuit (Fig. 4) uses a tap on the battery to stabilise the OC72 emitter voltage. This circuit gives a better overall performance than that of the preferred circuit, the disadvantage being that two batteries, or one tapped battery, must be used. It should be noted that a 6 volt accumulator tapped at -2.0 volts could be used in place of dry cells.

## Choice of Components

The most critical component in any of these circuits is the relay. This should operate from a voltage of between 1 and 4.5 at a current of less than 25mA. The relay used by the author had a resistance of 140 $\Omega$  and operated from a 1.5 volt cell. Such

fact tested with an OC71 (paint removed!) and perfect operation resulted.

## Power Supply Unit

If it is desired to operate this unit from the a.c. mains, a suitable power supply may be obtained by using a 6 volt filament transformer, a germanium diode (Mullard OA70, OA10, or similar), a fixed resistor, and an electrolytic condenser in the circuit of Fig. 5.

## Typical Uses

This light-operated switch can be put to a great many uses. Since photo-transistors are very sensitive to red light, the circuit could be used as a fire detector. Operating in conjunction with a beam of infra-red or

white light it could act as a burglar alarm or count passing objects such as vehicles, or articles on a conveyor belt. More mundane uses include switching of lights at home, outdoors, or in shop windows when daylight falls below a certain brightness. No doubt other uses will suggest themselves.

#### Setting Up Procedure

Having wired any of the given circuits, the setting up procedure is as follows:

First set the variable resistor to its minimum value, then connect the supply (preferably via a milliammeter), whilst shielding the photo-transistor from full light. Adjust the variable resistor until the relay operates, then reduce the setting of the rheostat until the relay "drops out". Exposing the photo-transistor to full light should now result in the relay operating, with subsequent removal of the light causing it to "drop out". The optimum setting of the variable resistor will be found in use.

#### Circuit Performance

Measurements of OC72 base-emitter potential for each circuit are tabled here, and the "factor of reliable operation" as denoted by the difference in "light" and "dark" potentials may be compared.

Circuit	V <sub>b-e</sub> Light	V <sub>b-e</sub> Dark	Comments
Fig. 1	+0.25	-0.28	Good
Fig. 3	+0.35	+0.1	Fair
Fig. 4	+0.3	-0.78	Excellent

Note: The base-emitter voltages listed above are dependent upon the setting of the variable resistor.

## A Low Cost, Miniature Photo-cell for Industrial Control

A new photo-conductive cell, thought to cost less than any other photo-electric cell available in this country, has been introduced by Mullard.

The cell, of the cadmium sulphide type, is physically very small, and yet has a high sensitivity. It is housed in a standard transistor-type glass envelope measuring only 15mm long by 6mm diameter, which enables large numbers of the cell to be stacked in a small space. Its sensitivity is such that an illumination of 5ft candles, with a lamp colour temperature of 2700°K, will produce an average cell current of 500 microamps.

Applications of the cell include industrial counting and control systems where space is at a premium, and flame failure detection in oil-fired burners. Its tiny sensitive area of

only 0.25 square mm makes it especially suitable for fine positional control systems. Unlike the larger types of Mullard cadmium sulphide devices it is intended not for the direct operation of relays, but rather to drive cold-cathode trigger tubes such as the Mullard type Z803U.

The cell has a dark current of less than 1.5 microamps at the maximum cell voltage of 350V (d.c. or peak), and a maximum dissipation of 70mW at 25°C. The ambient temperature range is -40°C to +70°C.

Two versions are available—type ORP60 for end-on incidence of illumination, and type ORP61 for side illumination. Both types have flying leads for wiring-in to the circuit and are suitable for dip soldering.

## MARCONI'S POLDHU SITE GIVEN TO NATIONAL TRUST

On 6th July, at a private ceremony at Marconi House, London, Lord Nelson of Stafford, Chairman of the English Electric Group, presented to the National Trust the title deeds of 40 acres of land at Poldhu, Cornwall, the site of Marconi's historic transmitting station. The gift was accepted by Earl De La Warr, Chairman of the Trust's Estates Committee. Among those present was Mr. C. S. Franklin, who joined the Marconi Company in 1899 and was closely associated with Marconi in the Poldhu station project.

It was on 12th December, 1901, Marconi announced that signals from Poldhu had bridged the Atlantic and were being received by him at St. John's, Newfound-

land. This dramatic news at once took wireless telegraphy out of the laboratory, not only demonstrating its capabilities as a practical communication medium, but also confounding the learned critics of the day who stated that wireless waves would never reach beyond the horizon. The achievement underlined Marconi's great faith in his apparatus and theories, and his courage in proceeding against "informed" opinion.

Poldhu continued in use as a commercial wireless station until its dismantling in 1937. All that now remains at the site is a granite column overlooking Mounts Bay, this serving as a reminder of the momentous events which took place nearly sixty years ago.

# THE SELRAY BOOK CO

BOOKS FOR THE CONSTRUCTOR

**Basic Electricity.** 5 parts, 12s. 6d. per part. Postage 6d. 55s. per set. Post free.

**Basic Electronics.** 6 parts, 12s. 6d. per part. Postage 6d. 66s. per set. Post free.

Completely revolutionary in their methods of training with startling success. Send for detailed prospectus.

**Realistic High Fidelity.** Hartley. 5s. Postage 6d.

**High Fidelity Stereo Gramophone.** For the Home Constructor. Easterling. 5s. Postage 6d.

**Transistor Circuits No. 2.** Sinclair. 2s. 6d. Postage 4d.

**High Fidelity Tape Recorder.** For the Home Constructor. Sinclair. 2s. 6d. Postage 4d.

**High Fidelity Loudspeaker Enclosed.** Babani. 5s. Postage 6d.

**Transistor Superhet Receivers.** Sinclair. 7s. 6d. Postage 6d.

**Boys' Book of Crystal Sets and Simple Circuits.** 2s. 6d. Postage 4d.

**Practical Transistor Receivers.** Sinclair. 5s. Postage 6d.

**Transistor Circuits Manual.** Gregory. 2s. 6d. Postage 4d.

**Beginners' Guide to Radio.** Camm. 7s. 6d. Postage 6d.

**Servicing Transistor Receivers.** Pettit. 6s. Postage 6d.

SEND STAMP FOR LISTS (150 Titles)

When ordering kindly add postage up to a total of 1s. only

Dpt. RC • 60 HAYES HILL • HAYES • BROMLEY • KENT •

Telephone  
HURstway 1818

Another in our Data Book Series

## MODERN CAR RADIO RECEIVERS

by Richard Myers  
and H. R. Major of the Jason Motor and Electronic Co.



This Data Book (DB13) contains three up-to-the-minute designs, each being fully described with point-to-point wiring. Of those featured, the "Maykit" uses the new 12V valves with output transistor stage while the Jason-designed "Everest 6" and "Everest 7" employ transistors throughout.

All the receivers cover the Medium and Long Waves. The Jason sets are contained in compact cases and are easily removable from the car for use as ordinary portables, operating from internal batteries and ferrite rod aerials. The "Maykit" car radio is, of course, a permanent fixture within the car.

Fully illustrated with photographs and circuit diagrams, this Data Book should prove of interest to all car owners requiring a car radio.

40 pages, with varnished board cover

PRICE 3/6 POSTAGE 4d.

DATA PUBLICATIONS LTD 57 MAIDA VALE LONDON W9

**Better get the best —  
it costs less**

**VIDIO**

Offers you the finest rebuilding service available today! Each tube is completely rescreened, aluminised and fitted with a new Gun Unit! Available now—for IMMEDIATE DELIVERY!

**ALL TUBES ARE GUARANTEED FOR ONE YEAR**

Get full details now from

**VIDIO REPLACEMENTS LIMITED**




Hales St. Deptford High St.  
London SE8  
Telephone TID 4506

**Powerful! Personal! Portable!**

- ★ Sturdy metal case
- ★ No holes to drill
- ★ Detachable rod aerial
- ★ All batteries self-contained
- ★ Can be built in 1 hour
- ★ Covers medium waves
- ★ Loud clear tone
- ★ Selective tuning
- ★ All parts are sold separately

ONLY FOR **35/-**

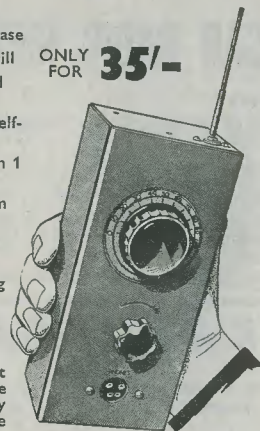

This delightful set is designed to give you a completely personal portable radio.

Bronze-finished case. Ideal for the beach, the bedroom, the office—in fact, anywhere.

Send 2/- for wiring diagram and component price list

**R.C.S. PRODUCTS (RADIO) LTD**  
11 Oliver Road London E17 Mail Order Only

**SMITH'S of Edgware Road**

1910 **GOLDEN JUBILEE YEAR** 1960

**BLANK CHASSIS**

Precision made in our own works from commercial quality half-hard aluminium of 16 s.w.g. (1/16" thickness. These chassis go all over the world (and off it—in rockets!). Same day service for ANY SIZE, to nearest 1/16" and up to 17" of straightforward two, three or four-sided chassis. Orders for specials dealt with promptly if sent with clear instructions.

**SOLDERED CORNERS.** While these chassis, owing to their thickness, hardness and efficient folding, will carry components of considerable weight and normally require no corner strengthening, we can do this, if required, by a special soldering technique at 6d. extra for each corner.

**FLANGES.** 1/4", 3/8" or 1/2" flanges (inside or outside) 6d. extra for each bend.

**PRICE GUIDE (normal chassis only)**

Work out total area of material required, including waste, and refer to table below:

48 sq. in.	4/-	176 sq. in.	8/-	304 sq. in.	12/-
80 sq. in.	5/-	208 sq. in.	9/-	336 sq. in.	13/-
112 sq. in.	6/-	240 sq. in.	10/-	368 sq. in.	14/-
144 sq. in.	7/-	272 sq. in.	11/-	and pro rata	
	Post 1/3		Post 1/6		Post 1/9

Discount for quantities. Trade enquiries invited. Spray finish arranged for quantities of 25 or over.

**PANELS.** The same material can be supplied for panels, screens, etc. Any size up to 3ft at 4/6 sq. ft. (sq. in. x 3/4). Post, up to 72 sq. in. 9d., 108 sq. in. 1/3, 144 sq. in. 1/6, 432 sq. in. 1/3, 576 sq. in. 2/-.

287/289 EDGWARE ROAD LONDON W2  
Telephone PAD 5891/7595

**HI-FI NEWS**

The Magazine for ...  
... The Sound Enthusiast

● HI-FI NEWS carries regular Constructors' features, reviews of all high fidelity and good quality audio equipment, and articles for both beginners and experienced readers. It is well produced and illustrated. We think you will like it—but sample it at our expense. Send 6d. for a specimen copy. Annual subscriptions are 27/6, or 30/- with annual index.

Price 2/- Monthly

**HI-FI NEWS**

99 MORTIMER ST LONDON W1


**PORTABLE TRANSISTOR RECORD PLAYER**

—BARGAIN OFFER ★ 6V operation (2 E/R Type 800 Batts. 1/4d each.)



- ★ 1 watt Push-Pull Output.
- ★ 4 Latest G.E.C. Transistors.
- ★ Garrard Fidelity Gram. Unit.

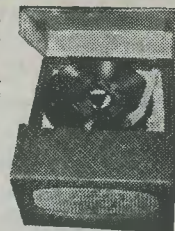Size 11" x 8 1/2" x 5"  
**COLOUR:** 2 Tone Red/White with Polka Dot relief. Alternative Blue/Fawn with Polka Dot relief.



**CABINET** incl. Motor Board and 7" x 4" Speaker £1.19.6 carr. 2/6.

**COMPLETE RECORD PLAYER KIT**  
Bargain Price £7.19.6 carr. 4/6.

**GARRARD BA1 Gram Unit.** £2.19.6. Carr. 2/6

**SEND FOR FULL DETAILS NOW LIMITED BARGAIN OFFER**

**RECORD PLAYER BARGAINS**

All brand new latest 4-speed Models—fully guar.  
**Single Players**—B.S.R. (TU9) with "FUL-FI" P.U. 90/- Garrard 4 S.P. with GC8 Crystal £6.17.6. Garrard TA Mk. 2 with Plug-in GC8 Head £7.19.6. Garrard 4HF Transcription Unit £18. Carr. 3/6.  
**Auto Changers**—B.S.R. (UA8) £6.19.6 UA8 Stereo £7.19.6 UA14 £7.19.6. Collaro Conquest £7.19.6. Garrard RC121/4D Mk. 2 9 1/2 gns. Carr. 4/6.

**SPECIAL—NEW RELEASE**

Garrard RC210, New 4-speed Autochanger Model with all the latest features and GC8 Plug-in Head, wired for Stereo, Bargain 10 gns. Carr. 4/6.  
**EMI** 4-speed Single, Player with Auto Stop/Start Dual Turnover Cartridge for Stereo and Monaural L.P. and 78—Bargain Buy at £6.19.6. Carr. 3/6.

**THE TOURIST PORTABLE**

4 valve, Med & L.W., lightweight battery Radio. Size only 8" x 5 1/2" x 4". Weight 3 1/2 lb with battery B114. Complete receiver component kit ... 57/6 P. & P. 1/6. Set 4 miniature valves (96 series) ... 35/- P. & P. 9d. 5" Speaker and O/put Trans. ... 21/- P. & P. 1/6. Cabinet, Dial and Knobs, etc. ... 22/6 P. & P. 2/- Latest superhet circuitry, dual ferrite aerial, delayed AVC and A.F. Neg. feedback. A remarkable little receiver with lots of punch and quality results.  
Complete Kit—BARGAIN £6.10.0 post free

**MAINS UNIT.** Size as B114. Battery Complete Kit 45/- P. & P. 1/6. Send for booklet now, 1/6 post free

**RECORD PLAYER CABINETS**

Contemporary styled, rexine covered cabinet in two-tone wine and cream, or mottled red with white polka dot. Size 18 1/2" x 13 1/2" x ht. 8 1/2", fitted with all accessories, including baffle board and anodised metal fret. Space available for all modern amplifiers and autochangers, as above, etc. Uncut record player mounting board 14" x 13" supplied.  
Cabinet Price £3.3.0. Carr. and Ins. 3/6.

**2-VALVE 2-WATT AMPLIFIER** With vol. and tone controls. Neg. feedback. A.C. 200/250V. Complete, ready wired to fit above cabinet. £2.17.6. P. & P. 1/- 6" Speaker and matching trans., 22/- P. & P. 1/6

**VALVES—New Reduced Prices—All Guaranteed**

1T4	6/-	DK96	9/-	ECL82	10/6	EY86	10/-
1R5, 1S5	7/6	DL96	9/-	EF80	8/-	EZ80	7/6
354, 3V4	7/6	EABC80	8/6	EF86	12/6	EZ81	7/6
5Z4	9/-	ECF80	9/6	EF91	5/-	MU14	9/6
DAF96	9/-	ECH42	10/6	EL41	9/6	PCC84	9/6
DF96	9/-	ECL80	10/6	EL84	8/6	PCF80	9/6
				EY51	9/6	PCL83	12/6

**TRANSISTORS—BYA 1st Grade—ex Mfrs.** Mazda XA102, 16/6; XA101, 14/6; XC101, 10/6; OC70, 9/6; XB102, 10/-; XA103, 15/-; XA104, 18/-; OA70, 2/9. Hours 9 a.m.—6 p.m., 1 p.m. Wed.



**RADIO COMPONENT SPECIALISTS**

70 Brigstock Road Thornton Heath Surrey Telephone THO 2188.  
Terms: C.W.O. or C.O.D. Post and packing up to 1/2 lb, 7d., 1 lb 1/1, 3 lb, 1/6, 5 lb, 2/-, 10 lb, 2/9.

**CRT HTR ISOLATION TRANSFORMERS**

New improved types, low capacity, small size and tag terminated, AC 200/250V. Secondaries Nil, +25%, +50% BOOST for 2V, 4V, 6.3V, 10.5V, 12V or 13V Tubes. Each type 12/6 each. P. & P. 1/6.

**JASON FM TUNER UNIT KITS (87-105 Mc/s)**

Standard Model (FMT1)—as previously extensively Tuner Coil Set, IFs, and Ratio Detector, etc., 26/-, advertised. Complete Kit—5 gns. Post free. Set of 4 spec. valves now only 20/-.  
**Model (FMT2)**—attractively presented shelf mounting unit in enclosed Metal Cabinet with Built-in Power Supply. Complete Kit, £7. P. & P. 3/6. Set of 5 spec. valves, 37/6.  
**Latest Model—JTV2**—Switched Band 1-2-3 AM/FM Unit with A.F.C. Kit £12.19.6. P. & P. 2/6  
**New Jason Comprehensive FM Handbook**, 2/6, post free. 48-hr. Alignment Service, 7/6. P. & P. 2/6.

**CONDENSERS**—Silver Mica. All pref. values, 2pF to 1,000pF, 6d. each. Ditto ceramics, 9d. each. Tubulars 450V T.C.C., etc., 0.001 mfd.—0.01 and 0.1/350V, 9d. each, 0.02—1/500V, 1/- each, 0.25 Hunts 1/6, 0.5 T.C.C. 1/9. 0.001 6kV 5/6. 0.001kV, 9/6.

**RESISTORS**—Full range 10 ohms—10 megohms 20%, 1/2W and 1W, 3d., 1/2W, 5d. (Midget type modern rating), 1W, 6d. 2W, 9d. 10% Hi-Stab. 1/2W, 5d. 1/2W, 7d. 5% 1/2W 9d. 1% HI-STAB, 1/2W 1/6 (10—100 ohms 2/-)

**LOUDSPEAKERS**—P.M. 3 ohm, 2 1/2" Plessey, 17/6; 3 1/2" Goodmans, 18/6; 5" R. & A., 17/6; 6" Celes., 18/6; 7 1/2" x 4" Goodmans, 18/6; 8" Rola, 20/-; 10" R. & A., 25/-; 12" Plessey, 30/-; etc.

**SPEAKER FRET**—Expanded Bronze anodised make 8 x 8 in., 2/3; 12 x 8 in., 3/-; 12 x 12 in., 4/6; 12 x 15 in., 6/-; 24 x 12 in., 9/- etc.


**TYGAN FRET** (Murphy pattern) 12 x 12 in., 2/-; 12 x 18 in., 3/-; 12 x 24 in., 4/- etc.

**COAX 80-OHM CABLE.** Now only 6d. per yd. High grade Low loss. Aeraxial Air spaced Polythene Coax—famous Manufacturer—Standard 1/4" diameter approx. 20 yds., 9/-, P. & P. 1/6; 40 yds. 17/6, P. & P. 2/-; 60 yds. 25/-, P. & P. 3/- Bargain prices. Special lengths. Coax Plugs 1/-. Coax Sockets 1/-. Couplers 1/3. Cable end sockets 1/6. Outlet Box 4/6.

**VOLUME CONTROLS**—5k-2 Megohm. ALL LONG SPINDLES, MIDGET TYPE, 1 1/2" diam. Guar. 1 yr. LOG OR LIN Ratios less SW, 3/- D.P. Sw., 4/6. Twin gang stereo controls log. or linear less SW 6/6. With D.P. SW 8/-.


★★ NO EXTERNAL AERIAL OR EARTH—NO REACTION CONTROLS ★★  
—EASY AS ABC TO BUILD AND A THRILL TO USE—  
**MAJOR-2** (Two-Transistor Pocket Radio) **MAJOR-3** (Three-Transistor Pocket Radio)

**IDEAL FOR BEGINNERS**

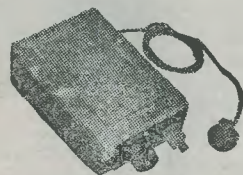

All components sold separately

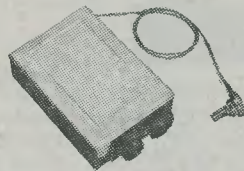- ★ 4-stage reflex Medium wave; tunable
- ★ Very sensitive
- ★ No aerial or earth
- ★ Complete layout
- ★ Over 6 months on one battery
- ★ 4½ x 3 x 1½"
- ★ Weight only 4 oz.
- ★ Personal phone included.



(As described in R.C., Sept. '59)

- ★ 5-stage Reflex Circuit
- ★ No Aerial or Earth
- ★ Miniature Volume Control
- ★ 3 Ediswan Transistors.
- ★ Medium Wave Tuning
- ★ Size 4½ x 3 x 1½"
- ★ Personal phone included.

TOTAL COST **69/6** P.P. 1/6 NEW BOOKLET FREE  
RECEPTION GUARANTEED ANYWHERE!

TOTAL COST **87/6** P.P. 1/6 NEW BOOKLET FREE  
FANTASTIC OUTPUT, TERRIFIC RECEPTION. GUARANTEED ANYWHERE

★★ NOT TOYS BUT REAL WORKING RADIOS! ★★

**TRANSISTORS**

**BRAND NEW AND GUARANTEED**

XB102, 10/-; XA104, 18/-; XA103, 15/-; XC101 matched pairs, 32/- pr.; XA131, 35/-; OC44, 19/6; OC45, 18/6; OC71, 10/-; OC72 pairs, 30/- pr.; OC170, 35/-; V15/10P, 15/-; V15/20IP, 25/-; XC141, 30/-; OC76, 15/-; SBO78, 10/-; SB305, 15/-; Red Spot, 3/6; White Spot, 5/-;  
SEND FOR LIST OF 50 TYPES WITH DATA AND PRICES

**"STEREO 3-D"**

New high-gain circuit with full tone, balance and volume controls. Can be used with all types of records as well as stereo.

- ★ 2 WATTS PEAK PER CHANNEL.
- ★ ECC83: 2-ECL82 VALVES.
- ★ MAINS 110/250V A.C.

**BUILT AND TESTED**  
**£5.7.6**  
P.P. 2/-

Complete with speaker sockets, calibrated dials, etc.

- ★ Collaro 4-speed stereo auto-changer, ideal for use with above amplifier, **£7.10.0**, P.P. 3/6.
- ★ 9" x 6" large magnet Elac speaker, for use with STEREO 3-D. 37/- pair. P.P. 1/6.

**ALL TRANSISTOR BABY ALARM**

**THE "BABY-SITTER"**



- ★ 100% Safe—Guaranteed
- ★ Fully Portable
- ★ No Mains—Battery Operated
- ★ Can be used over ANY Distance

USE IT AT HOME, TAKE IT ON HOLIDAY

Every Sound can be heard on large 5 inch Speaker

COMPLETELY ASSEMBLED WITH BATTERY **£5.10.0** P.P. 2/6

— BE WITH YOUR CHILDREN ALL THE TIME —

(Illustrated leaflet free on request)

**Our Specialities** Transistors, Quartz Crystals  
Valves, Miniature Components

Trade enquiries invited. Catalogues free. Compare our prices. WE ARE ABLE TO SUPPLY MOST OF THE COMPONENTS USED ON CIRCUITS PUBLISHED IN THIS AND OTHER MAGAZINES AND BOOKLETS. WHERE THE EXACT ITEM IS NOT AVAILABLE WE CAN RECOMMEND A SUITABLE SUBSTITUTE WHERE POSSIBLE.

**HENRY'S RADIO LTD • 5 HARROW ROAD • LONDON W2**

Opposite Edgware Road Tube Station. PADDINGTON 1008/9 OPEN MONDAY to SAT. 9-6, THURS. 1 o'clock

**TRANSMITTER/RECEIVER**  
**Army Type 17, Mark II**

Complete with Valves, High Resistance Headphones, Handmike and Instruction Book and circuit. Frequency Range 44.0 to 61 Mc/s. Range approximately 3 to 8 miles. Power requirements: Standard 120V H.T. and 2V L.T. Ideal for Civil Defence and communications.

BRAND NEW **45/-** P.P. 5/-

**VALVE REDUCTIONS**

(WHEN PURCHASED IN SETS)

- TP25, VP23, HL23/DD, PEN25 (or QP25) ... 25/-
  - 1A7GT, 1N5GT, 1HFGT, 1CSGT (or 3QSGT) ... 35/-
  - X66, KTW61, DH63, KT63, U50 30/-
  - 6K8G, 6K7G, 6Q7G, 5Z4G, 6V6G ... 32/6
  - 1R5, 1S5, 1T4, 1S4 (or 3S4 or 3V4) ... 25/-
  - DK96, DF96, DAF96, DL96 ... 35/-
  - 6K8G, 6K7G, 6Q7G, 25L6GT, 25Z5 (or 25Z6G) ... 35/-
  - 12K8GT, 12K7GT, 12Q7GT, 35Z4GT, 35L6GT (or 50LGT) 40/-
  - 12SA7GT, 12SK7GT, 12SQ7GT, 35Z4GT, 35L6GT (or 50L6GT) 32/6
- P.P. 1/- per set of valves

**Type 38 Transmitter/Receiver**

Complete with 5 valves. In new condition. These sets are sold without guarantee, but are serviceable.

7 to 9 Mc/s **22/6** P.P. 2/6

Headphones 7/6 pair. Junction Box 2/6. Throat Mike 4/6. Aerial Rod 2/6.

**"Practical Transistors Circuits"**

14 Circuits for the Home Constructor, including date, prices and information. 1st Edition, 2/-, post free.

**COMBINED PORTABLE/CAR RADIO**

Medium and Long Wave Full Tuning

- ★ New Printed Circuit
- ★ 6 "Top Grade" Ediswan Transistors
- ★ 5" High Fidelity Speaker
- ★ 400mW Push-Pull Output
- ★ Internal Ferrite Aerial
- ★ Slow Motion Tuning
- ★ Full Illustrated Building Instructions
- ★ Printed Circuit marked out.
- ★ Car Radio aerial socket and A.V.C.
- ★ ALL COMPONENTS GUARANTEED
- ★ Double Tuned IFs for selectivity
- ★ Size 9½ x 7 x 3½" Weight 4 lb.

**Continental Transistors**  
Direct Equivalent OC44 15/-  
Direct Equivalent OC45 12/6  
BRAND NEW GUARANTEED  
LIMITED QUANTITY ONLY


**Crystal Microphones**

ACOS 39-1 Stick Microphone with screened cable and Stand (List 5 gns.). 39/6. P.P. 1/6.  
ACOS 40 Desk Microphone with screened cable and built-in stand (List 50/-). 25/- P.P. 1/6.

**RED-SPOT TRANSISTORS**  
**3/6 each**

**WHITE-SPOT**  
**5/- each**

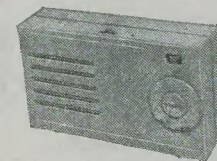NEW FREE LIST ON REQUEST Fully Guaranteed



6½" x 3½" x 1½"

**SPECIAL OFFER—LIMITED PERIOD**

**The Teletron "TRANSIDYNE" 6-Transistor Superhet**

- ★ Medium and Long Waves includes cabinet, battery, transistors, etc.
  - ★ 2½" Rola Speaker
  - ★ All Ediswan transistors
  - ★ Marked printed circuit
  - ★ Illustrated instructions
- FREE LEAFLET,  
BOOKLET 1/- POST FREE  
NOW ONLY **£9.10.0**  
P.P. 2/-

★ **RF AND IF GENERATOR**

Ideal for aligning TRF or Superhets. 470 Kc/s up to 3 Mc/s output. All components 25/- P.P. 1/-.

★ **3-TRANSISTOR HEARING AID**

High-gain circuit with built-in crystal microphone and amplifier. Includes miniature earphone. 3-Transformers. Size 3" x 2" x ¾". All components, 89/6. P.P. 1/-.

★ **2 WATT OUTPUT TRANSISTOR AMPLIFIER**

For connection to any battery portable to give up to 2W output. Works from 12V battery. Ideal for car radio use. Size 4½" x 3" x 2½", uses power transistor. All components (less speaker) 52/6. P.P. 2/-  
Ideal for use with Continental 6, etc.

★ **TRANSISTOR TRANSMITTER**

1.8 to Mc/s coverage. 3 transistors unit size 4½" x 3" x 1½". Range of 3-section rod aerial up to 300 yards. Includes built-in microphone, battery and 3-section rod aerial. All components, 57/6. P.P. 1/6.

★ **SQUARE WAVE GENERATOR**

2-Transistor. Chassis size 2" x 1½". 15V supply. All components, 20/- P.P. 1/-.

★ **RF, IF AND AUDIO SIGNAL TRACER**

Ideal signal peaker or quick fault-finder for receivers, amplifiers, etc. Size 4½" x 3" x 1½". All components, with 'phones, 37/6. P.P. 1/6. Less 'phones, 32/6. P.P. 1/6

★ **250mW PUSH-PULL OUTPUT AMPLIFIER**

For use with any 2, 3 or 4 transistor, earpiece or headphone radio to give room-filling volume on 3" speaker. All components including 2 Ediswan transistors, speaker, battery, special input socket to take earpiece plug, cabinet, etc., 59/6. P.P. 1/6.  
Ideal for use with Major-2 or Major-3.

★ **27 Mc/s RADIO CONTROL RECEIVER**

3-Transistor regen. circuit. Size 2" x 1½" x 1½". Weight with batteries, 1½ oz. Uses SB305 transistor. Multi-channel read operated. All components (less read), 50/- P.P. 1/-.

SEE PAGE 919 LAST ISSUE  
**JUST RIGHT FOR A DAY'S OUTING**  
**"CONTINENTAL-6"**

For Style, Quality Performance and Value for Money

Total Cost of all Components

**£11.10.0** P.P. 3/6

including Cabinet, Battery, Transistors, Car Radio, AVC and all necessary items.

A highly sensitive and selective portable fully tunable on medium and long waves. Performs equally well as a car radio. Low running costs, good looks and ease of construction combine to produce a radio equal to any commercial receiver in the 20 gns. class.

ALL COMPONENTS AVAILABLE SEPARATELY



SEND FOR DESCRIPTIVE LEAFLET AND PRICES

CALL FOR DEMONSTRATION

**Telescopic Chrome Aerial**

7-Sections, 3' 6" open; 6" closed. Ideal for Portable Receivers. Walkie-talkies, Radio Control, etc.

With Clips 12/6. P.P. 1/-.

**Crystal Microphone Inserts**

Latest ACOS 43-1, 2½ inch Round Hi-Fi Insert. 14/- P.P. 6d.  
¾" square (ex-units) 3/6 ea. P.P. 6d.

# Get these **FREE** CIRCUITS & WIRING DIAGRAMS

T.R.F. Circuits Single Valve FM Tuner, 2 Valve FM  
Battery Circuits Complete Set. Same on Printed  
Portable Circuits Circuit, etc., etc.  
S'het Circuits Postage 1/- (Stamps)

**OSMOR COILS** are regularly used and recommended  
by designers writing in *Practical Wireless*, *Wireless World*  
and *The Radio Constructor*. Why not follow the experts?

"Q COILS" • POTTED COILS • FM COILS  
All ranges

**SPEAKER CROSS-OVER COILS**

TAPE COILS • ROD AERIALS

SUB MINIATURE COILS

COILS and I.F.s for MIDGET I.F. TRANS  
Transistor Circuits With ferrite cores



418 Brighton Road  
South Croydon  
Telephone CRO 5148/9

## TRANSISTORISED "DO-IT-YOURSELF" CAR RADIO



REDUCED PRICE  
**£12.15.0**

Insist on this genuine quality radio you can build your-  
self, buy direct and save £'s. 5 valve superhet, standard  
size, 12 volt. Assembled and tested £16. P. & p. 5/-

## MAYKLITE £4.0.0 AUTOMATIC LIGHT SWITCH

Single unit fixed to windscreen switches car lights on  
when dark. Easy to fit. Complete. P. & p. 2/-

## MAYDEX £3.5.0 CARAVAN EXTENSION SPEAKER

Quality loudspeaker controls volume and on/off.  
Complete, plus cable at 2/6d. per yard. P. & p. 3/-

Write for details. Available ONLY from

**MAYRA ELECTRONICS LIMITED**  
DEPT. D 551 HOLLOWAY ROAD LONDON N19

12" Speaker and 5" Tweeter with coupling conden-  
ser by leading maker, 75/- (£8.15.0 list price.)  
Mains Transformers. Input 200/250V. Output  
tapped 3 to 30V 2A or 5, 11, 17V 5A. Each 24/6.  
F.W. Metal Rectifiers. 12/6 volt 1A, 7/6; 3A, 13/-;  
4A, 17/6; 6A, 27/6; 24V 2A, 23/6.  
Mains Transformer and Rectifier, giving 12V 1A  
d.c. output, 19/6; 30V 2A, 33/6.  
Relays. We hold large stocks. Any contact com-  
bination and operating coil voltage supplied from 3/-.  
Special Offer. 12V relays with 2 or 4-make con-  
tacts, 6/-; 2 for 11/6; 3 for 16/6; 4 for 21/-.  
Key Switches from 3/-.  
Toggle Switches d.p.d.t., 3/6. Micro Switches,  
M. & B., 5/6.  
Nickel Nife Batteries. 1.2V 2.5A. Size 3" x 2 3/4"  
x 1". Practically everlasting, 6/-; or 3 for 16/-; 4, 21/-.  
Army Morse Keys, 3/6, 6/- and 8/6.  
Lightweight Soldering Irons 17/9  
H.S. Twist Drills. Set 7, 1/4", 1/2", 3/4", 4/-; also Full Size  
in Plastic Wallet, 6/- Set of 13, 9/6 and 17-15/6, 1/8" to  
3/8". Tubular Hack Saws (Eclipse Type) 11/6.  
5" Side Cutters, 5/6. 5" Plated Round Nose Tapered  
Pliers, 5/- Pocket Neon Testers with retractable  
Screwdriver, 5/6. 7" Flat Nosed Tapered Pliers, 8/6.  
Celestion Speakers 8" x 5" 21/-  
Very Powerful Geared Small 12V d.c. Motor.  
Instant stop. 3" x 1 1/2", 16/6.  
New 12" Speakers. 3 ohm, 32/6.  
Paxolin Panels, 12" x 6" x 1/8", 3/6.  
Paxolin Tubing, 1 1/2" x 3/8" x 72", 17/6. Ideal for masts.  
Studio "O" Cartridges, 21/-

All items post paid, new and guaranteed

LISTS SENT ON REQUEST

Post orders only to

**THE RADIO & ELECTRICAL MART**  
29 STATION APPROACH SUBBURY TOWN  
WEMBLEY MIDDXX

## REPANCO Easy-to-build Receivers

	Envelopes
R.E.P. One Valve Radio ... ..	9d.
The Hiwayman. A 4 valve portable Radio	1/6
F.M. Tuner Unit. 5 valves plus tuning indicator ... ..	1/6
Twinette. A 2 transistor portable Radio ...	1/3
Three Dee. 3 transistor radio ... ..	9d.
Mini-7. 7 transistor pocket radio ... ..	1/6
Mini-3. 3 transistor pocket radio ... ..	1/3
Transeven. 7 transistor portable. (Preset stations) ... ..	1/6
Major-7. 7 transistor portable (Tunable) ...	1/6
Transistor Car Radio Receiver ... ..	2/-
Transistor Amplifier and Feeder Unit circuits ... ..	1/6

Please add towards postage

For details of our components send 6d. in stamps for  
1960 catalogue

**Radio Experimental Products Ltd**  
33 Much Park Street Coventry

Telephone 27114

## SMALL ADVERTISEMENTS

Readers' small advertisements will be accepted  
at 3d. per word, including address, minimum  
charge 2/-. Trade advertisements will be  
accepted at 9d. per word, minimum charge 6/-.  
If a Box Number is required, an additional  
charge of 2/- will be made. Terms: Cash with  
order. All copy must be in hand by the 12th  
of the month for insertion in the following  
month's issue. The Publishers cannot be held  
liable in any way for printing errors or  
omissions, nor can they accept responsibility  
for the bona fides of advertisers.

### PRIVATE

FOR SALE. Premier 4-valve portable and mains  
p.u. less valves and batteries £2. 5s.—Blainciffan,  
Beulah, Newcastle Emllyn, Carmar.

WANTED. Mains transformers for G.E.C. Miniscope.  
—Lunson, 17 Tongdean Rise, Brighton, Sussex.

FOR SALE. 9 volumes *Radio and Television Servicing*  
Vols. 1-5, 1955/56, 1956/57, 1957/58, 1958/59.  
New condition. £13 o.n.o.—Abraham, 1 Bassaleg  
Road, Newport, Mon.

FOR SALE. 30 copies *Wireless World* 15s. 18 copies  
*Aero Modeller* 9s. Varley dry accumulators Type  
VPT 9/17, 7s. 6d. Morse Code recorder. a.c.  
Motor variable speed. Marconi type UG9, £7.  
Top band portable Tx/Rx, 12 volt input, mic.,  
etc. £7. Erskine Laboratory oscilloscope 1 1/2 in.  
tube £8. Rotary, 12V in, 285V 60mA out, 12s. 6d.  
Rotary, 12V in, 480V 40mA out, 12s. 6d. Ext.  
speaker, wood cabinet 14 x 14 x 7 in., 10s. Gyro  
demonstration model with 12V rotary 15s. Fractional  
HP a.c. Motors £1. Speed control resistors for  
same 10s. E.D. Radio control transmitter £3.  
Postage and packing extra.—"East Keal", Romany  
Road, Oulton Broad, Suffolk.

FOR SALE. Mullard 5-10 and pre-amp. Perfect.  
TSL FM Tuner needs adjusting. Studio "O" Acos  
67/1 cartridges, new. 15 ohms speaker and tweeter.  
Lot £15. Box No. F111.

FOR SALE. Teletron "Companion", as new, £4.—  
R. Holland, 16 Beacon Avenue, Loughborough.

FOR SALE. Supreme 581 Generator, 135 kc/s to  
60 Mc/s, modulated r.f., a.f., and f.m. for scope  
alignment. Audio Generator 50-10,000 c/s, calibration  
charts, in excellent condition, £18. AVO model 7,  
£12. AVO Bridge, £8. AVO Valve Tester, 3 panels,  
£10. Weston 772, £10. Band III pre-amp, 50s.  
Offers to—C. Kemp, 6 West Park, Minehead, Som.

FOR SALE. Bush 12 in., ITV/B.B.C.; £6 post paid,  
Ultra, Bush, Sobel, etc., complete with converter,  
£5 Few only, sent at buyers risk, complete with  
converter, £4 plus postage. MW 31/74, CRM123,  
etc. 25s. post paid. Converters, Stirling, Aerialite,  
etc., 55s. post paid.—O.D.B., 25 Ramshead Ap-  
proach, Leeds, 14.

### TRADE

**BOUND VOLUMES** *The Radio Constructor*. Attractively  
bound in blue cloth, with gold-blocked spine.  
The following only are available: Vol. 12, Aug. '58  
to July '59 inc.; £1 5s., postage 1s. 9d. each. Where  
all issues of a volume are returned for exchange,  
12s. 6d., postage 1s. 9d. "Easibinders" for temporary  
or permanent binding, 12s. 6d., postage 9d. each.  
Indexes are available for Volume 12, price 6d.,  
postage 2d.—Data Publications Ltd., 57 Maida Vale,  
London, W.9. Telephone CUN 6141/2.

**LEARN RADIO AND ELECTRONICS** the NEW  
Practical way. Very latest system of experimenting  
with and building radio apparatus—"as you learn".  
FREE Brochure from: Dept. RC10 Radiostructor,  
40 Russell Street, Reading, Berks.

**MORSE CODE TRAINING.** Special courses for  
Beginners. Full details from (Dept. R.C.) Candler  
System Company, 52 Abingdon Road, London, W.8.

continued on page 79

## EDDY'S (NOTTM) LTD

172 Alfreton Road Nottingham Dept. RC

**NIFE ACCUMULATORS** 1.25 volt 7 amp hours.  
Weight 13 ozs. Size 3" x 2 3/4" x 7/8", 1/11 each. Post 1/6  
one only, add 9d. each cell.

**HANDMIKES** Carbon 3/11. Post 1/9.

**THROAT MIKES** 1/-. Post 6d. Could be used for  
electrifying musical instruments.

**HEADPHONE CORDS** High Quality. 6 ft. lengths  
1/11 per pair. Post 6d.

**TRANSISTORS** Red Spot 3/11. White Spot 4/11.  
Post and packing 6d.

**VARIABLE CONDENSERS** 0-0005uF Small twin gang  
built in slow motion drive 8/11. Post 1/6.


**DIMMER SWITCHES** Ideal for train Regulators 1/11.  
Post 9d.

**TUMBLER SWITCHES** 250 volts 5 amp 1/- each.  
Post 6d.

**GERMANIUM DIODES** 8d. each, 7/- doz. Post 6d.

All above are new and guaranteed

## BUILD YOUR OWN CAR RADIO

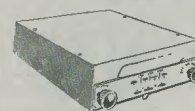

7 Transistors  
Long and Med-  
ium Waves. Two  
watts output.  
RF stage and  
automatic gain control.

(6 or 12 volts, please  
state.) Supplied with full instructions at  
**10 1/2 gns.** Size: 7 3/4" x 7 1/4" x 2 1/2"

Speaker 17/11 extra (7 x 4 ellipt.) if required.  
Postage and packing 5/- per kit


## NEW OR SURPLUS VALVES

Guaranteed and Tested by Return Post

DAF96 6/11	GT1C 6/11	UY41 6/3	6V6GT 6/-
DF96 6/11	P61 2/-	1A7GT 11/9	6BJ6 5/11
DK96 6/11	PCC84 7/3	1C5GT 10/6	6H6 1/11
DL96 6/11	PCF80 7/-	1D5 7/6	6X4 5/11
EB41 6/11	PCL82 7/6	1H5GT 9/6	6X5G 4/11
EB91 3/6	PCL83 11/3	1L4 3/6	12K7 5/6
ECC81 5/3	PL36 11/6	1N5GT 9/6	12Q7 12/6
ECC82 5/11	PL81 9/-	1R5 6/-	12K8 11/-
ECC83 6/6	PL82 7/3	1S5 6/-	25A6G 6/11
ECL80 7/6	PL83 7/3	1T4 3/11	25L6GT 8/11
EF36 3/-	PY80 6/11	3Q5GT 8/6	25Z4G 7/11
EF40 13/3	PY81 6/-	354 6/3	35L6GT 8/11
EF42 7/3	PY82 7/-	3V4 7/-	35Z4G 5/3
EF86 10/-	PY83 7/3	6AG5 4/-	90AV 3/6
EF91 3/6	PY31 8/3	6B8G 2/11	6I7G 5/-
EL41 7/3	PY32 10/11	6BA6 5/11	6SG7M 4/9
EL42 9/3	PEN36C 8/-	6BE6 5/11	12AT6 7/6
EL84 6/6	MU14 8/-	6C4 4/3	95A 1/6
EY51 8/6	UBC41 7/6	6C9 9/3	955 3/6
EY86 7/11	UCH42 7/6	6K7G 1/11	9001 3/11
EZ40 6/6	UF41 8/-	6K8G 5/6	9004 3/11
EZ80 6/-	UF42 7/-	6SN7GT 4/3	9006 3/11
EZ81 7/-	UY1N 10/11	6V6G 4/11	956 2/6

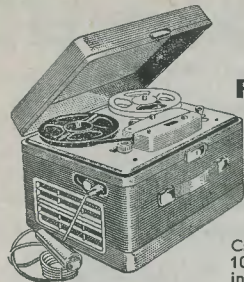Any parcel, insured against damage in transit for only  
6d. extra per order. All uninsured parcels at customers  
risk. Postage and Packing 6d. per valve extra. C.O.D.  
or C.W.O. only C.O.D. charge 3/-, S.A.E. with enquiries





## DE LUXE TAPE RECORDER CABINET

only **29/9**

Beautifully made Tape Recording Cabinet, Size 13" x 10½" x 7". Covered in two-tone coloured rexine cloth. Stylish design. Carrying handle with detachable lid, lock and key. Easily adapted to Record Player Cabinet. Exceptional value at this very low price. P. & P. 4/6

### TAPE RECORDER AMPLIFIER

Compact, well designed 5-valve amplifier. Output 3.5 watts. Valve line up—ECC83. Double triode first audio amplifiers. ECL82 Triode pentode further audio amplifier and output valve. 6BW6 Diode and eraser oscillator. EM84 record level indicator. EZ80 H.T. rectifier. Input for mike, radio and gram. controls: Record Playback volume and On/Off Playback tone. Dia: 8½" x 3" x 4½". Carr & Ins 4/6. £7.19.6 or terms. Knobs 2/6 per set. Beautiful perspex dial plate, 3/6. Completed with sockets for mike. Radio and superimpose switch.

**DUKE & CO.** (London) Ltd.  
621/3 ROMFORD RD.,  
MANOR PARK E12  
Telephone ILF 6001/3

### NEW SURPLUS . . . BY RETURN

1L4	3/6	6K8G	5/-	12SC7M	2/6	ECC83	6/6
1R5	6/-	6K8M	9/-	12SJ7M	5/-	ECH42	8/-
1S5	6/-	6H6M	2/-	12SK7M	5/-	EF36	2/6
2A3	8/6	6L6G	7/-	12SQ7M	8/6	EF39	3/6
2X2	2/6	6L6M	9/-	3SZ5GT	8/6	EF50	1/6
3A5	9/-	6Q7G	5/6	3SZ4G	5/-	EF50(S)	2/6
3Q4	5/6	6Q7GT	9/-	42	7/6	EF86	10/-
5R4GY	8/6	6SA7M	6/-	50L6GT	9/6	EF91	3/-
6AC7M	4/-	6SJ7M	5/6	80	6/6	EL32	3/-
6AG5	3/6	6SL7GT	5/6	446A	10/6	EL41	8/-
6AK5	5/-	6SN7GT	4/-	830B	8/6	EM80	9/6
6AL5	3/6	6ST7M	5/-	959	5/-	GT1C	6/6
6AM6	3/-	6V6G	7/6	1629	4/-	GZ32	10/-
6AU6	6/-	6X4	5/6	5763	10/6	KT33C	6/6
6BB8	2/6	12A6M	5/-	ARP12	3/-	PCC85	9/-
6BA6	6/-	12A7	7/-	DC70	4/-	PCF82	7/6
6BE6	6/-	12AU6	7/6	DET24	10/-	PEN25	4/-
6BH6	5/6	12AU7	5/6	DF73	4/-	PY80	6/6
6BJ6	5/6	12AX7	6/6	DL70	4/-	PY83	7/6
6F32	2/6	12BE6	7/6	EAS0	1/6	TT11	3/-
6F6M	5/6	12C8M	7/6	EAC91	3/-	VLS631	10/-
6J6	3/6	12K7G	5/-	EB91	3/-	VP23	3/-
6J7G	5/-	12K8M	10/-	EB33	4/6	VR150/30	7/6
6K7G	2/-	12Q7G	5/-	ECC82	5/6		

Post and Packing 6d. per valve. Free over £2

**A BARGAIN FOR STRIPPERS.** Modulator Unit 236 and Transmitter Unit 130, containing 5 first grade Gardner's 50 c/s mains transformers, 200-250V tapped, 1 of 6.3V 4A, 6.3V 1A, 2 of 320V 20mA, 6.3V 1A, 1 of 1,840V 4mA, 1 of 4V 14A, 6.3V 1A. 1 triple choke. Valves: 2 CV15, 1 807, 2 6J5GT, 1 GT1C. 10 Dubilier Nitrogen paper blocks 600V 2-4µF, plus hosts of small parts, switches, knobs, jack sockets, fuse-holders, etc. 30 sets only available brand new at 55/- pair, carr. paid U.K. mainland.

### JOHN ANGLIN

S.A.E. enquiries  
385 CLEETHORPE ROAD GRIMSBY LINCS.  
Telephone 56315

## REPANCO HIGH GAIN COILS

Dual Range Crystal Set Coil, Type DRX1	2/6		
Dual Range Coil with Reaction, Type DRR2	4/-		
Matched Pair Dual Range, T.R.F. Coils, Type DRM3	8/-		
Pair Dual Range Superhet Coils, Type SH4	8/-		
Miniature Iron Dust Cored Coils, Type "R"	3/3		
Range	Aerial	H.F.	Ocs.
800 2,000 m.	RA2	RHF1	RO1
190 550 m.	RA2	RHF2	RO2
70 230 m.	RA3	RHF3	RO3
15 50 m.	RA4	RHF4	RO4
Ferrite Rod Aerial, Dual Range Type FR1	12/6		
Miniature I.F. Transformers, Type MSE (465 kc/s)	12/6		
Standard I.F. Transformers, Type TCG (465 kc/s)	13/6		

Send S.A.E. for latest Repanco Component Catalogue Telephone 62572

### Radio Experimental Products Ltd

33 Much Park Street COVENTRY  
Telephone 62572

## Ask "ARTHURS" First

NOTE NEW ADDRESS AT

125 Tottenham Court Road  
London WC1

Close to Warren Street Station

You will have the same service and obtain all your requirements in Radio Components, Electrical Goods, Accessories and Television as previously.

Test Instruments in stock include Avro, Advance, Cossor and Taylor. List on request

VALVE MANUALS AVAILABLE

Mullard 10/6 Brimar No. 8 6/-  
Osram Part 1, 2nd Edition 7/6  
Post and packing 9d. each extra

## Arthurs first

Est. 1919

Proprietors ARTHUR GRAY LTD

Gray House

125 Tottenham Court Road  
London WC1

Telephone EUSton 5802/3/4

### SMALL ADVERTISEMENTS

Readers' small advertisements will be accepted at 3d. per word, including address, minimum charge 2/- . Trade advertisements will be accepted at 9d. per word, minimum charge 6/- . If a Box Number is required, an additional charge of 2/- will be made. Terms: Cash with order. All copy must be in hand by the 12th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the bona fides of advertisers.

TRADE continued from page 77

PANL, recognised for many years as the unique one-coat black crackle finish. Brush applied, no baking. Available by post in eighth pint cans at 3s. 9d. from G. A. Miller, 255 Nether Street, London, N.3. "WORLD RADIO HANDBOOK." Copies available, 1960 Edition, 16s. 6d., inc. post and packing from ISWL, 12 Gladwell Road, London, N.8.

1,000 INTERESTING ITEMS. List 3d.—Rogers, 31/33 Nelson Street, Southport, Lancs. TECHNICAL WRITING IN ELECTRONICS. Radio and TV Instruction Books, Service Manuals, Brochures, Technical Drawings, etc.—F. C. Judd, A.Inst.E., Rotech, 152 Maybank Road, London, E.18. Telephone BUCKHURST 9315.

HIGH CLASS DUPLICATING. Electronic Stencil Illustrations, circuits, etc. Sheets or booklets.—Rotech, 152 Maybank Road, London, E.18. Telephone BUCKHURST 9315.

INCORPORATED Practical Radio Engineers home study courses of radio and TV engineering are recognised by the trade as outstanding and authoritative. Moderate fees to a limited number of students only. Syllabus of Instructional Text is free. The Practical Radio Engineer, journal, sample copy 2s. 6,000 Alignment Peaks for Superhets, 5s. 9d. Membership and Entry Conditions booklet, 1s., all post free from the Secretary, I.P.R.E., 20 Fairfield Road, London, N.8.

THE INTERNATIONAL HAM HOP CLUB is a non-profit making organisation open to RADIO AMATEURS and SHORT WAVE LISTENERS. OBJECT: To improve international relationships through an organised system of hospitality. MEMBERS offer overnight hospitality to visiting members, entrance fee 2s. 6d. ASSOCIATE MEMBERS invite radio amateurs to visit their stations. S.A.E. for FREE Associate membership. FAMILY EXCHANGE holidays arranged, also FRIENDSHIP LINKS between radio clubs. H.H.C.'s official journal, Ham Hop News, 5s. per annum. Hon. Gen. Secretary: G. A. Partridge, G3CED, 17 Ethel Road, Broadstairs, Kent.

CATALOGUE No. 14. Government surplus and model radio control, over 500 illustrated items, 2s. (refunded on purchase), p.p. 6d.—Arthur Sallis Radio Control Ltd., 93 (E) North Road, Brighton.

## TELEKIT SUPPLY

104 High St.  
Beckenham Kent  
Phone: Beckenham 3720

30 Catford Hill  
London SE6  
Phone: Forest Hill 9658

SPECIAL OFFER!!!

## STEREO 19 gns.


Complete & Working

Consisting: Collaro Auto Changer with "Acos 73" Cartridge Quality Amplifier 2 x 2 watts, two Hi-Flex 8" Speakers. We stock and advise on: Kits, Amplifiers, Transistors, TV Tubes, Valves, Tapes and Tape Decks and Record Players, etc.

ALL OUR GOODS ARE GUARANTEED
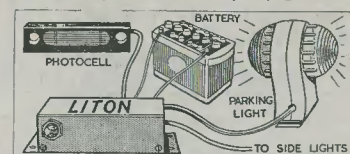
## "LITON" PHOTO-ELECTRIC PARKING LIGHT SWITCH

will switch your lights on at dusk—off at dawn, automatically. Controlled by daylight. Transistorised.



6 or 12 volts  
Kit of Parts  
52/6  
Built 57/6  
Photocells  
7/6, 12/6  
& 25/-

BURGLAR ALARM—GARAGE DOOR OPENER—LIGHT SAVER. Kit, £4.12.6. Built £5.10.0. Send 6d. stamp for full details and circuit of each device.

"ST. JOHN'S RADIO" 156 St. John's Hill SW11

Make your own world-wide range, Short wave radio receiver—you'll find it's much easier than you think when you use the latest totally-enclosed "Globe-king" coils! No complex switching or superhet circuitry, no alignment or service problems. Set of three coils covering 10 to 100 metres in special storage carton-container with circuits enclosed for battery, mains and transistor, SW receivers, RF tuner, etc., also special "Easy-Build" diagrams for beginner's single-valve receiver, model 100/A. Complete, 17s. 6d. Trade and wholesale inquiries welcomed.

## JOHNSONS (RADIO) ST. MARTINS GATE WORCESTER

### TRANSISTOR COMPONENTS

REPANCO . . . FS2 13/6; OT1 11/6; TT2 5/-; TT3 5/-; TT4 8/6; TT5 8/-; F53 7/6; X11 3/6; X08 5/-; XT2 10/-; XT7 10/-; also Cools . . . DRX1 2/6; DRR2 4/-; DRM3 8/-; SH4 8/-; MSE IP's 12/6 pr; "R" coils 3/3 each. FR1 aerial 12/6. Miniature resistors 10% 6d.; Miniature condensers 1, 2, 5, 8, 25, 50, 100 mid 3/- . . . SELECTED Transistors . . . Red spots 5/-; White spot 6/- . . . All Mullard and Ediswan Transistors in stock. SELECTED Germanium diodes 1/6; GEX34 4/-; OA70, OA79 and OA81 4/- each. Shopping List available for Mullards "Circuits for Audio Amplifiers."

### L. F. HANNEY

77 Lower Bristol Rd. Bath S.A.E. for LIST please

### TO CLEAR "ALL" AT 9d. P. & P. 6d.

1D6	2050	ARP18	VR21
3D6	2151	KTZ41	VT510
4D1	7193	ML4	VT61A
6AC7	2C22	NGT2	VW48
6B7	AR6	PM202	W21
6B8	ARP36	PP225	7B6
6SA7	EF36	QP21	7B7
6SG7	CV73	VR35	8D2
6SH7	CV188	SP41	9D2
12SC7	D1	SP61	6
12Y4	EA50	T41	And more,
78	EB34	RL37	Stamp for
210VP	GT1C	CV66	FREE
1203A	KT24	TT11	Catalogue

P. & P. COMPONENTS LIMITED  
219 ILFORD LANE ILFORD ESSEX

## TRANSFORMERS

Suppliers to B.B.C., I.T.A. and leading radio manufacturers, single or long runs, prompt delivery, home and export.

rewinds to all makes

**H. W. FORREST (TRANSFORMERS) LTD.,**  
Shirley, Solihull, Warwickshire  
Telephone SH1rley 2483

## BRASS, COPPER, DURAL, ALUMINIUM, BRONZE

ROD, BAR, SHEET, TUBE, STRIP, WIRE  
3,000 STANDARD STOCK SIZES  
No Quantity too small. List on Application.

**H. ROLLET & CO LTD**  
6 Chesham Place SW1 BELGRAVIA 4300  
Also at Liverpool, Birmingham, Manchester, Leeds

**Teleprinters, Perforators, Reperforators  
Tape Readers, Pen Recorders, Terminals and  
V.F. Telegraph multi-channel units, Test Frames and  
Testing Equipment, Telephone Carriers and Repeaters,  
Signalling Rectifiers and Relays, Transformers, Transmit  
and Receive Filters, Repeating and Retardation Coils,  
Uniselectors, Racks, Relay Bases, Remote Control Trans-  
mitters: British, American and German Equipment.**  
**BATEY & CO., Gaiety Works, Akeman Street,  
Tring, Herts.** Telephone Tring 2183 and 2310

## SERVICE SHEETS. 14 Days Free Hire

Line Output Transformer Specialists. All Makes/  
Models from 65/- Volume Controls 3/- Switched  
4/9. Resistors 1/2 watt, 1/2 watt 6d each. Hystab 10%  
1/2 watt 10d. Wirewound 10% 5 watt 1/3. 10 watt  
1/6. Sub-Miniature Electrolytics 1µF, 2µF, 4µF,  
5µF, 25µF, 50µF, 100µF, 15V, 3/- each. Coax. Cable  
6d. per yd. Crystal Diodes 2/- GEX34 4/- Hax.  
Coils 3/- each. R.E.P. DRR2 4/- All Repanco and  
Teletron components in stock. All transistors  
stocked.

Service sheet free hire on all orders over 25/- Deposit  
5/- extra returnable. P. & P. 1/-, over £2 free. S.A.E.  
all enquiries.

**WYNSOR TELEVISION SERVICE**  
ST. ALBANS ROAD BARNET HERTS.  
Telephone BAR 1769

## QUALITY COMPONENTS FOR CONSTRUCTORS

capacitors, resistors, coils, valves, diodes, controls,  
chassis, transformers, speakers, pick-ups, cart-  
ridges, stylis and all types of components in stock.

### CONSTRUCTIONAL PUBLICATIONS

Mullard Circuits for Audio Amplifiers	...	8/6
Mullard Tape Pre-amp "C"	...	2/6
Quality Amplifiers, 7 designs	...	4/6
Jason F.M. Variable Tuners	...	2/6
Jason F.M. and T.V. Mercury 2	...	3/6
Jason F.M. and T.V. JTV2	...	3/6

Price lists available on request

**J. T. FILMER** 82 DARTFORD ROAD  
DARTFORD KENT  
Telephone Dartford 24057

## H.A.C. THE ORIGINAL SUPPLIERS OF SHORT-WAVE KITS

One valve Super Sensitive All-dry Short-wave Receiver  
Model "K". Complete kit including valve and chassis  
77/- (Other S.W. kits from 25/-) Before ordering  
call and inspect a demonstration receiver, or send  
stamped envelope for full specification, catalogue and  
order form.

**H.A.C. SHORT-WAVE PRODUCTS (DEPT. R)**  
11 OLD BOND STREET LONDON W1

## SPECIAL AMATEUR LICENCE MORSE COURSE

**COMPLETELY NEW METHOD** takes all the  
drudgery out of learning Morse. Passes secured in all  
cases, even after previous failures.

By using specially prepared recordings (3 speed L.P.  
player required) students learn automatically and  
without effort, perfect Morse in half the time required  
by any other method. S.A.E. full details.

**G3HSC 45 GREEN LANE PURLEY SURREY**

## "GLOBE-KING"

WORLD-FAMOUS KITS AND RECEIVERS

for the Radio Amateur and S.W. Listener. Catalogue  
Free, enclose stamp for postage. Kits from 79/6  
obtainable at your dealers or direct from sole manu-  
facturers

**JOHNSONS (Radio)**  
ST. MARTINS GATE — WORCESTER

## RADIO AMATEURS ...

get your Licence in

## Half The Usual Time!

You must be a good Morse operator!  
A "slap-dash" 12 w.p.m. neither satisfies the authorities,  
yourself, nor your operator friends. Morse operating  
is an exacting art unless your training is made simple  
and is based on sound fundamentals. For this reason  
the Candler System was invented to take the "grind"  
out of Code tuition, turning a tricky subject into a  
pleasurable pursuit.

★ Send 3d. stamp for the "Book of Facts"

**CANDLER SYSTEM CO**  
(Dept. 55 RC) 25b Abingdon Rd., London, W8  
Candler System Company, Denver, Colorado, U.S.A.

3000 and 600 type relays brand new boxed and  
surplus, 4, 50, 100, 492, 500, 1000, 2000, 6500,  
Ohms. contacts etc. Resistors Capacitors,  
Valves, Meters, etc. SV-4X/450A eqvt £10 each.  
832 £1 each, 807 7/6 each, CV36 (klystron).  
Large quantity of enamelled and silk-covered wire  
to be sold as a lot. Discount for quantity. Prompt  
reply to postal inquiries.

★ ★ ★

## ABEL RADIO LTD

283 EDGWARE ROAD LONDON W2  
Telephone AMB 8614

## SCOTTISH INSURANCE CORPORATION LTD



62-63 Cheapside  
London EC2

## TELEVISION SETS, RECEIVERS AND TRANSMITTERS

Television Sets, Receivers and Short Wave Transmitters are expensive to acquire and you no  
doubt highly prize your installation. Apart from the value of your Set, you might be held responsible  
should injury be caused by a fault in the Set, or injury or damage by your Aerial collapsing.

A "Scottish" special policy for Television Sets, Receivers and Short Wave Transmitters provides  
the following cover:

- Loss or damage to installation (including in the case of Television Sets the Cathode Ray  
Tube) by Fire, Explosion, Lightning, Theft or Accidental External Means at any private  
dwelling-house.
- (i) Legal Liability for bodily injury to Third Parties or damage to their property arising  
out of the breakage or collapse of the Aerial Fittings or Mast, or through any defect  
in the Set. Indemnity £10,000 any one accident.
- (ii) Damage to your property or that of your landlord arising out of the breakage or collapse  
of the Aerial Fittings or Mast, but not exceeding £500.

The cost of Cover (a) is 5/- a year for Sets worth £50 or less, and for Sets valued at more than  
£50 the cost is in proportion. Cover (b) and (ii) costs only 2/6 a year if taken with Cover (a)  
or 5/- if taken alone.

Why not BE PRUDENT AND INSURE your installation—it is well worth while AT THE  
VERY LOW COST INVOLVED. If you will complete and return this form to the Corporation's  
Office at the above address, a proposal will be submitted for completion.

NAME (Block Letters).....

If Lady, state Mrs. or Miss

ADDRESS (Block Letters).....

/JB

## THE MODERN BOOK CO

**The Radio Amateur's Handbook.**  
1960 Ed. 32s. 6d. Postage 2s.

**Radio Servicing. Specimen Answers**  
to City and Guilds Questions. 1955/  
1959 (Intermediate). By A. R. Bailey  
and E. C. Bell. 8s. 6d. Postage 6d.

**Short Wave Receivers for the  
Beginner.** A Data Publication. 6s.  
Postage 6d.

**Marine Radio for Pleasure Craft.**  
By H. McKay. 23s. Postage 9d.

**A Beginner's Guide to Radio.** By  
F. J. Camm. 7s. 6d. Postage 6d.

**Radio Valve Data.** 6th Ed. Compiled  
by "WW". 5s. Postage 9d.

**TV Fault Finding, B.B.C. and I.T.A.**  
A Data Publication. 5s. Postage 6d.

**Rapid Radio Repair.** By G. Warren  
Heath. 23s. Postage 1s.

**Rapid TV Repairs.** By G. Warren  
Heath. 23s. Postage 1s.

**Basic Mathematics for Radio and  
Electronics.** By F. M. Colebrook and  
J. W. Head. 17s 6d. Postage 1s.

**Radio Servicing.** By G. N. Patchett  
and B. Fozard. 21s. 1 Volume Ed.  
Postage 1s.

**World Radio Handbook for  
Listeners.** Broadcasting & Television.  
1960. 15s. 6d. Postage 1s.

**G.E.C. Nine-One-Two Plus.** 4s.  
Postage 9d.

**FM Simplified.** 3rd. Ed. By M. River.  
45s. Postage 1s. 6d.

We have the Finest Selection of British and American Radio Books in the Country  
Complete catalogue 1/-

19-23 PRAED STREET (Dept RC) LONDON W2

Telephone PADdington 4185