

1520



# The RADIO Constructor

RADIO · TELEVISION · AUDIO · ELECTRONICS

## CONTENTS

TRANSISTORISED CAPACITY METER

HIGH IMPEDANCE TRANSISTORISED VOLTMETER

STEREO/MONO MICROPHONE MIXER UNIT


EXTERNAL LOUDSPEAKER WITH AUTOMATIC SWITCHING

"TWINETTE" TWO-TRANSISTOR RECEIVER

2-METER AERIAL SYSTEMS

GROUPBOARD TECHNIQUES

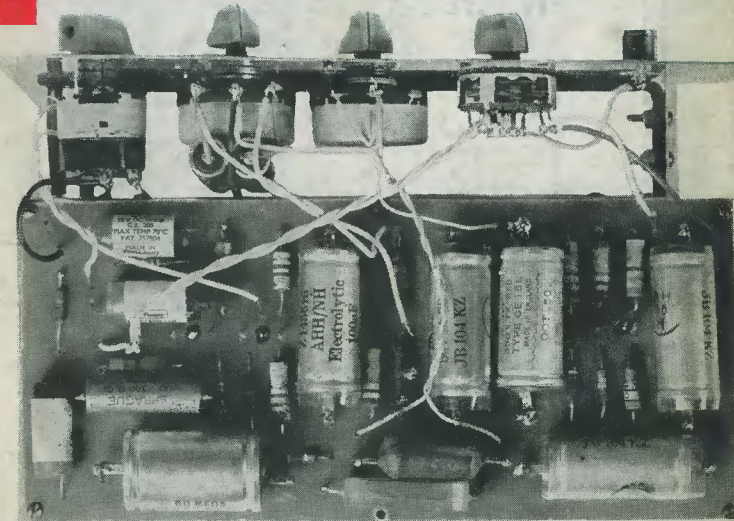ELECTRONIC VIBRATO FOR AMPLIFIED MUSICAL INSTRUMENTS, ETC., ETC.



A PRINTED CIRCUIT PRE-AMPLIFIER

## DATA Publications

ONE SHILLING AND NINEPENCE

### Transistor 750mW Push-Pull Amplifier

(Over 1 watt peak output)

● 1st Grade Mullard Transistors OC71, OC81D, 2-OC81.

● Printed Circuit 4" x 2 1/2" with Metal Heat Sink.

Ideal for Record Player, Intercomm. Baby Alarm for Tuners, etc., etc.

● BUILT AND TESTED

● Fully Guaranteed 79/6

● 9V battery operated p.p.1/6

● Output to 3 ohms speaker

Supplied with Diagrams Showing Uses—Free on Request.

Kit of parts for above complete in every detail 69/6 p.p.1/6

### CONTESSA Combined Portable and Car Radio

6 TRANSISTOR MEDIUM AND LONG WAVE SUPERHET  
TERRIFIC SENSITIVITY  
UNBEATABLE IN PERFORMANCE AND APPEARANCE



#### SPECIFICATION

- 425mW Push-Pull Output
- 6 "Top-Grade" Ediswan Transistors
- New Type Printed Circuit with all Components marked
- Full Medium & Long Wave Tuning
- High "Q" Internal Ferrite Aerial
- Car Radio Adaption and AVC
- Slow Motion Fingertip Tuning with Station Names
- "Hi-Fi" Quality Speaker
- Attractive Rexine Covered Cabinet. RED/WHITE or BLUE/WHITE

TOTAL COST OF ALL PARTS £11.10.0 P.P. 3/6

★ NO EXTRAS TO BUY ★

Call for demonstration. No technical knowledge necessary. All parts sold separately. New Descriptive Leaflet and Prices on request. Easy to build

### RANGER 3

● No External Aerial or Earth



Size 4 1/2 x 3 x 1 1/4

3-TRANSISTOR and 2-DIODES PERSONAL POCKET RADIO with 3 stages giving clear reception on medium wave, amateur top band and shipping. Only first grade components used throughout. Amazing results.

ALL COMPONENTS 79/6 P.P. 1/6

NO EXTRAS TO BUY Everything Supplied

● Easy to follow instructions with pictorial layouts


● Reception of Radio Luxembourg guaranteed (most areas).

Free Instrs. & Price List on request. Easy to build

● After Sales Service, Guaranteed Success ●
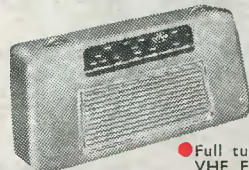
### 'PW' ROADFARER

(as described in April edition of Practical Wireless)



Parts as specified

£17 P.P. 3/6

All components sold separately. List on request

A.M. and F.M. 7-transistor mains/battery portable in attractive moulded case. Slow motion tuning; telescopic aerial; 7" x 4" speaker; Ferrite aerial, etc.

● Full tuning medium wave and VHF F.M. for clear reception of all programmes anywhere in the country

● 500mW push-pull output with Mains or Battery supply built in. Printed Circuit—SEVEN TRANSISTORS

● FULLY ILLUSTRATED BUILDING INSTRUCTIONS

### All Transistor Units

★ BUILT AND READY FOR USE ★

● LEAFLETS ON REQUEST

● Office or Home 2-way intercom system, 4 Mullard transistors. 2-5" speakers, unique call system. Battery operated. 2 portable rexine cabinets. Built and tested £6.19.6. P.P. 2/6.

● Portable 4-transistor Baby-Alarm as previously advertised. But now with 400mW output on 5" speaker. Can be used up to 200 yards. £5.10.0. P.P. 2/6. Including battery and microphone. Battery life 3 to 4 months used every day.


● 1 watt 4-Mullard Transistor Amplifier, printed circuit. Ideal for portable record players, tape recorders, radio tuners, etc. 6V 3Ω output 92/6 P.P. 1/6

● Telephone Pick-up Amplifier with induction coil. 4 transistor. Ideal for busy office, no more "holding on." £5.10.0. P.P. 2/6. Use 400mW Mullard Amplifier

ALL UNITS ARE PRE-TESTED AND FULLY GUARANTEED OTHER UNITS AVAILABLE

### 'PW' 6-Transistor

MEDIUM AND LONG WAVE POCKET SUPERHET

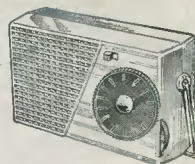

Size 5 1/2" x 3" x 1 1/4"

(as described Nov. P.W.)

● A sensitive pocket superhet with 150mW push-pull output on 2 1/2" speaker. Uses 6 first grade Mullard transistors and printed circuit. Moulded cabinet

● All parts sold separately. Send for list. Illustrated Building Plans, 1/6 plus post. £8.19.6

● ALL PARTS REQUIRED

★ No Extras To Buy—Everything Supplied ★

Practical Transistor Circuits

3/6 POST FREE

Contains easy to follow plans of 40 all-transistor units, including light operated switches, amplifiers, transmitters, receivers, test oscillators, signal tracers, hearing aids, radio control, etc. All parts available separately.

DESIGNED FOR THE HOME CONSTRUCTOR

Henry's Radio Ltd 5 HARROW RD. LONDON W2


Opposite Edgware Road Tube Station. PADDINGTON 1008/9. Open Monday to Sat. 9-6. Thurs. 1 o'clock

● COMPLETE LIST OF DO-IT-YOURSELF UNITS ON REQUEST ●

PLEASE TURN PAGE



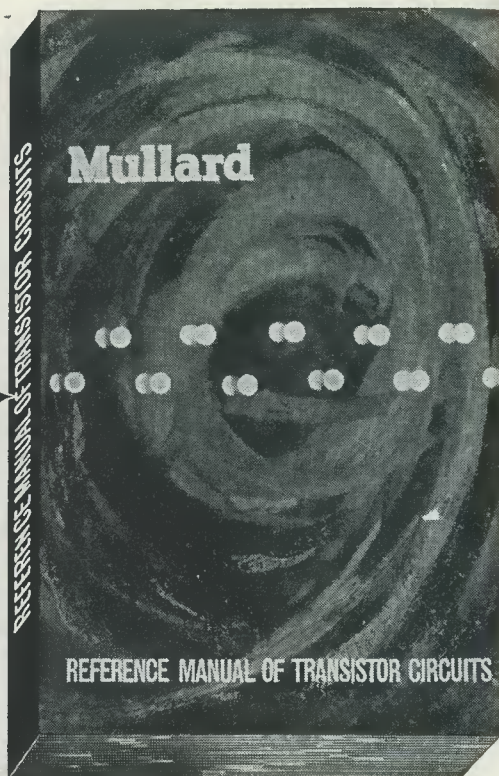over 30  
new  
circuits  
are in  
the  
**Mullard**  
REFERENCE  
MANUAL  
OF  
TRANSISTOR  
CIRCUITS



This new manual of transistor circuitry has been prepared by Mullard engineers, as an up-to-date and readable volume which will be of use and interest to technicians, service engineers, junior designers and electronics students.

It has a page size of 8½" x 5½" and describes more than 60 circuits—over 30 are made generally available for the first time—including both domestic and industrial applications.

**308 PAGES • 241 DIAGRAMS • U.K. PRICE 12s. 6d.**

**PUBLISHED BY MULLARD LTD.**

Get your copy of the Mullard "Reference Manual of Transistor Circuits" today from your radio dealer, or order direct from Mullard Ltd. (postage and packing 1s. Od. extra in U.K.).


**MULLARD LIMITED • MULLARD HOUSE • TORRINGTON PLACE • LONDON • W.C.1.**

*Overseas readers should enquire of their local Mullard Agents.*

MVM17

# BUILD A **Jason** TUNER

*Many models  
Well-presented  
designs*

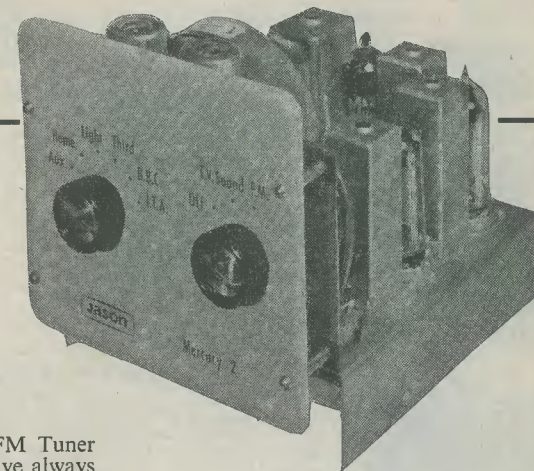

## Tuner Kits

*(Valves extra except on Mercury II and JTV/2K Kits with which 2 valves are included)*

- FMT/1**—The original Jason chassis tuner **£5.19.0**
- FMT/2**—As above but in shelf mounting case **£8.15.0**
- FMT/3**—Variable FM with AFC control (in case) **£9.19.0**
- JTV/2K**—Self-powered switched FM/TV sound **£14.19.0**
- Mercury II**—Switched FM/TV sound chassis **£10.14.0**
- Everest 7** Transistor Portable **£15.18.9**

### JASON TEST EQUIPMENT IN KIT FORM

*These highly dependable instruments are supplied in kit form for building oscillators, audio-generators, crystal-controlled calibrators, wobblers, etc. Excellent instructional literature is included with each model. Details on request.*

## JASON ELECTRONIC DESIGNS LIMITED

3-4(E) GREAT CHAPEL ST. OXFORD ST. LONDON W1 Telephone GERrard 0273/4

The World-famous



range of equipment

## For the Discerning who require the Best Performance at Minimum Price

### HI-FI FM TUNER

This model is available as two units which, for your convenience, are sold separately. They comprise an R.F. Tuner Unit, Model FMT-4U (£32.0 including Purchase Tax) with I.F. output of 10.7 Mc/s, and an Amplifier Unit complete with attractively styled cabinet, also power supply and valves. Model FMA-4U (£10.10.6) making a total cost for the equipment of £13.12.6.

### AMATEUR TRANSMITTER Model DX-100U

This is the most popular Amateur transmitter in the world and requires no introduction to "Hams" the world over. Covers all bands from 160-10 metres. Self-contained, including power supply, Modulator and V.F.O. £78.10.0


### 4-WAVE TRANSISTORISED PORTABLE RECEIVER, Model RSW-1

This possesses Medium, Trawler and two Short-wave bands and is mid-way between the domestic broadcasting and professional general communications receiver. Ideal and inexpensive for those who wish to listen to world broadcasts, shipping and aviation communications, etc. It is not the set to buy if you wish only to enjoy domestic broadcasting. In a handsome solid leather case, it has retractable whip aerial and socket for car radio use. £20.18.6



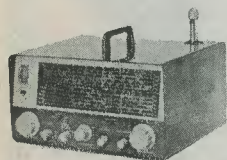
### THE "MOHICAN" GENERAL COVERAGE RECEIVER Model GC-1U

In the forefront of design with 4 piezo-electric transmitters, variable tuned B.F.O. and Zener diode stabiliser, this is an excellent fully transistorised portable or fixed station receiver for both "Ham" and Short wave listeners. Other features include printed circuit boards, telescopic whip antenna, tuning meter and large slide-rule dial of approximately 70". £38.15.0



**THE "COTSWOLD".** This is an acoustically designed enclosure 26" x 23" x 15 1/2" housing a 12" bass speaker with 2" speech coil, elliptical middle speaker together with a pressure unit to cover the full frequency range of 32-20,000 c/s. Capable of doing justice to the finest programme source, its polar distribution makes it ideal for really Hi-Fi Stereo. Delivered complete with speakers, cross-over unit, level control, Tygan grille cloth, etc. All parts pre-cut and drilled for ease of assembly and left "in the white" for finish to personal taste. £19.18.6

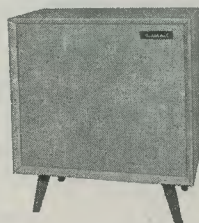

THE "COTSWOLD"

### HI-FI EQUIPMENT CABINETS

Range now available to suit vastly differing needs and all left in white for finishing to personal taste. Will house Record Player, F.M. Tuner, Amplifier and, in some models, also your Tape Deck. The "GLOUCESTER" cabinet is illustrated below.

Send for details of whole range. Prices from £10.10.0 to £17.8.0.



The "GLOUCESTER" (open)

All prices include free delivery U.K. Deferred terms available over £10.

### RECENT ADDITIONS TO THE RANGE

**TAPE RECORDING/REPLAY AMPLIFIERS.** Stereo (TA-S) £22.4.0. Mono (TA-M) £16.14.0

**R.F. SIGNAL GENERATOR, Model RF-1U.** Up to 100 Mc/s fundamental and 200 Mc/s on harmonics and up to 100mV output on all bands. £11.11.0

**GRID DIP METER, Model GD-1U.** £9.19.6. Transistorised version, Model XGD-1. £9.18.6

★ In THE FOREFRONT OF GENERAL COVERAGE RECEIVER DESIGN. The fully transistorised Model GC-1U, with 4 piezo-electric transmitters will be available shortly £38.15.0

**DAYSTROM LTD** DEPT. RC4 GLOUCESTER ENGLAND

Easily-built Equipment




of excellent quality

## at much lower cost



O-12U

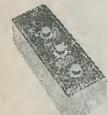

DC-1U



S-33



DX-40U



AG-9U



UJR-1



MA-12

**5" OSCILLOSCOPE: O-12U.** "Y" sensitivity 10mV/cm. 3 c/s to over 5 Mc/s. Rise time, 0.08 μsec or less. Sweep, 10 c/s to 500 kc/s. Electronically stabilised. £34.15.0

**2 1/2" PORTABLE SERVICE OSCILLOSCOPE: OS-1.** Ideal instrument for service and portable use. Size 5" x 8" x 1 1/4". Wt. 10 1/2 lb. £18.19.6

**DECADE CAPACITANCE BOX: DC 1U.** Provides capacity values from 100 mmf to 0.111 mfd in 100 mmf steps. Ideal for experimental, development and design work. £5.18.6

**VALVE VOLTMETER: V-7A.** The world's largest-selling VVM. Measures volts to 1,500 (DC & RMS) and 4,000 pk. to pk.; resistance 0.1Ω to 1,000MΩ DC. Sensitivity: 7,333,333 ohms per volt. £13.0.0

**HI-FI STEREO 6 WATT AMPLIFIER: S-33.** Low-priced but high quality; less than 0.3% distn. at 2 1/2 watts per channel. £11.8.0

**HI-FI STEREO 16 WATT AMPLIFIER: S-88.** Superb reproduction for the man who wants the best in Hi-Fi. Only 0.1% distortion at 6 W/chnl. Many special features. £25.5.6

**"HAM" TRANSMITTER: DX-40U.** 75W CW; 60W pk. c/c phone; 40W into Aerial. £29.10.0

**HI-FI SPEAKER SYSTEM: SSU-1.** Ideal twin speaker/ducted-reflex cabinet for stereo/mono in average room (left "in the white"). Legs 0 £10.5.6

**AUDIO GENERATOR: AG-9U.** 10 volts, 10 c/s to 100 kc/s pure sine-wave. Switch-selected frequencies attenuation. £19.3.

**JUNIOR TRANSISTOR RADIO: UJR-1.** Youngsters are not excluded from our kit programme. This special single transistor set is an excellent introduction to radio and an instructive present. £2.16.6

**TRANSISTOR PORTABLE RADIO UXR-1.** In elegant solid hide case, with golden relief. Six transistors, dual-wave, fine reproduction very easy to build. £14.18.6

**SINGLE CHANNEL 12 WATT HI-FI AMPLIFIER: MA-12.** Ideal for stereo conversions, etc. Generous auxiliary power provided. £9.19.6

**COLLARO "STUDIO" TAPE DECK.** This extremely attractive and compact 3-speed monaural tape deck features digital counter, pause control and piano-key switches. £17.10.0

(Following models not illustrated)

**CAPACITANCE/RESISTANCE BRIDGE: C-3U.** Measures capacity 10pF to 1,000μF. Resistance 100Ω to 5MΩ; Pwr. factor. £7.19.6

**VARIABLE FREQUENCY OSCILLATOR: VF-1U.** 10V output; covers 10 to 160 metres. £10.12.0

**AUDIO WATTMETER: AW-1U.** Up to 25W continuous, 50W intermittent. £13.18.6

**AUDIO VALVE-MILLIVOLTMETER: AV-3U.** 1mV to 300V AC. 10 c/s to 400 kc/s. £13.18.6

**ELECTRONIC SWITCH: S-3U.** This extremely useful device extends your single-beam "scope" for double-beam uses. £9.18.6

**DIRECT READING CAPACITANCE METER: CM-1U.** Full-scale ranges of 0-100 mmf, 1,000 mmf, 0.01 mfd and 0.1 mfd. £14.10.0

## Money Saving "Packaged Deals" of Complete Stereo Equipment from £42.10.0

All prices include free delivery in U.K. Deferred terms available on orders above £10



OS-1



V-7A



S-88



SSU-1



UXR-1



"STUDIO"

★ SEND THIS COUPON NOW FOR FURTHER INFORMATION

(Please write in BLOCK CAPITALS)

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

Without obligation please send me (Tick here)

BRITISH HEATHKIT CATALOGUE

FULL DETAILS OF MODEL(S)

**DAYSTROM LTD** DEPT. RC4 GLOUCESTER, ENGLAND

A member of the Daystrom Group, manufacturers of the WORLD'S LARGEST-SELLING ELECTRONIC KITS

## Component Price List for Repanco TWINETTE

(featured in this issue)

	s.	d.
Repanco Ferrite Slab Aerial Type FS 3	7	6
Repanco Ferrite Slab Aerial Type FS 4	7	6
Repanco Chokes Type RF1 & RF2 (pair)	6	0
Group Board & Panel Assembly Type 6/T	5	0
Repanco Transformer Type TT14	12	6
Repanco Transformer Type TT5	8	0
Set of Dial Plates	2	3
Resistor Kit	2	0
Fixed Condenser Kit	8	3
300pf Variable Condenser	4	6
100pf Variable Condenser	4	6
Two Transistor-Holders & Clips	2	0
4 Pole 3 Way Switch	4	0
3 Pointer Knobs at 9d. each	2	3
7" x 4" Elliptical Speaker	19	6
Ediswan Transistor XA 104	18	0
Ediswan Transistor XB 102	10	0
Mullard OA 81 Diode	4	0
Hardware Kit with Reaction Wire & Cord	1	6
Battery Type PP4 and Studs	3	0

All Components available from:

**Radio Experimental Products Ltd**  
33 Much Park Street Coventry

## SPECIAL

### "Practical Wireless"

Transistor

### "POCKET SUPERHET"

TRANSISTORISED  
**A.M./F.M.**

INCLUDING  
SPECIALIST-DESIGNED CABINET

Send for A—Z information on printed  
board construction

**OSMOR RADIO PRODUCTS LTD**  
418 BRIGHTON ROAD SOUTH CROYDON  
SURREY Telephone CRO 5148/9

## Ask "ARTHURS" First

NOTE NEW ADDRESS AT  
125 Tottenham Court Road  
London WC1  
Close to Warren Street Station

You will have the same service and obtain  
all your requirements in Radio Components,  
Electrical Goods, Accessories and Television  
as previously.

Test Instruments in stock include **Avo**,  
**Advance**, **Cossor** and **Taylor**. List on request

VALVE MANUALS AVAILABLE  
Mullard 10/6 Brimar No. 8 6/-  
Osram Part 1, 2nd Edition 7/6  
Post and packing 9d. each extra

# Arthurs first

Proprietors ARTHUR GRAY LTD

Gray House  
125 Tottenham Court Road  
London WC1  
Telephone EUSton 5802/3/4

## ERSIN MULTICORE SOLDERS

Wherever precision soldering is essential, manufacturers, engineers and handymen rely on MULTICORE. There's a MULTICORE SOLDER just made for the job you have in hand. Here are some of them.

### SAVBIT TYPE 1 ALLOY

A specially formulated alloy to reduce the wear of soldering iron bits. Contains 5 cores of non-corrosive Ersin Flux and is ideal for all soldering purposes.



### SIZE 1 CARTON 5<sup>4</sup>

Available in three specifications.

### ERSIN MULTICORE

Contains 5 cores of extra-active non-corrosive Ersin Flux. Prevents oxidation and cleans surface oxides.

### SIZE 1 CARTON 5/-

### Bib WIRE STRIPPER AND CUTTER

Strips insulation without nicking wire, cuts wire cleanly, splits extruded flex 3/6 each



The Home Constructors Pack, containing 19 ft. of 18 s.w.g. 60/40 alloy is available at 2/6d.

**MULTICORE SOLDERS LTD.**  
MULTICORE WORKS, HEMEL HEMPSTEAD, HERTS.  
(BOXMOOR 3658)

**For Safety's Sake**  
use  
**AVO Prodclips**

Patent No. 748811  
... with Trigger-Action Spring-Loaded Clips

Safety first every time with these patented spring-loaded AVO Prodclips.

Cleverly designed for use as insulated prods, they are invaluable for reaching and holding test points which are difficult of access.

Suitable for use with AvoMeter, Multiminor and Avo Electronic Test Meter Leads. Post Free 15/- per pair.

**AVO LTD** AVOCET HOUSE  
92-96 VAUXHALL BRIDGE RD., LONDON, SW1  
Victoria 3404 (12 lines)  
A Member of the Metal Industries Group of Companies  
2PC



BRITISH MADE  
**MICROPHONES**

For TELECOMMUNICATION  
BROADCAST, RECORDING  
AND P. A. REQUIREMENTS

A wide range of types and  
models is available, details of  
which will be sent on request


**LUSTRAPHONE LTD**

ST. GEORGE'S WORKS, REGENTS PARK ROAD  
LONDON NW1 Telephone Primrose 8844
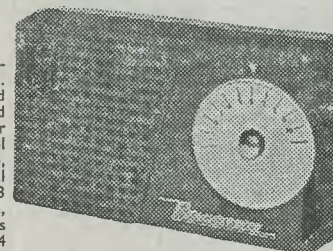
## TRANSISTOR POCKET RADIOS

MOST EFFICIENT  
R.F. CIRCUIT

Circuit comprises 2 h.f. transistors reflexed to equal 4 stages. Permanent germanium diode and high gain a.f. output stage, fitted with miniature speaker, proper tuning condenser, volume control and in case (less monogram), completely portable. No aerial or earth required. Pocket 3 uses 2 transistors and 1 diode, 3' /6. Pocket 4 uses 3 transistors and 1 diode, 42/6. Pocket 5 uses 4 transistors, diode and feedback, 5. 6 post & ins. 2/6



Transistors for R.F., F.M., T.V.  
and U.H.F.

Frequencies quoted are approx. cut-off.

SB 078 15-20 Mc/s	8/6
SB 305 20-30 Mc/s	9/-
SB 231R 40-50 Mc/s	15/-
AMERICAN 2N1727 100-150 Mc/s	15/-
AMERICAN 2N1728 100-150 Mc/s	12/6
AMERICAN T1832 1000-1300 Mc/s	25/-
AMERICAN T1833 1000-1300 Mc/s	25/-

★ Results proved in all areas.  
Components guaranteed for  
12 months.

★ Plans free with parts, or  
separately 1/6.

More details S.A.E.

### ELECTRONIC PRECISION EQUIPMENT LTD

★ Orders received by post are despatched from our warehouse, Dept. 34, 66 Grove Road, Eastbourne, and to save time, please post your order to this address. Please include enough for postage. Callers, however, should use one of the following addresses:

Electronics (M.P.) Ltd. 520 High Street North Manor Park, E.12	Electronics (Ruislip) Ltd. 42-46 Windmill Hill Ruislip, Mddx.	Electronics (Croydon) Ltd. 266 London Road Croydon	Electronics (Finsbury Park) Ltd. 29 Stroud Green Road Finsbury Park, N.4
--	---	--	--

Read these testimonials  
THE ORIGINALS MAY BE  
SEEN AT THIS OFFICE

Mr. S. Rigby-Jones, South Molton, N. Devon.—"I was delighted to receive my Pocket 4 Transistor set. After I assembled and tested it I was amazed such a small receiver had such good reception."

Mr. E. Balcombe, Manchester.—"I have constructed your Pocket 4 Loudspeaker radio and am delighted with its performance and appearance. For the cost I consider it excellent."

Mr. R. Belt, Newcastle-on-Tyne.—"I have built your Pocket 5 Transistor set. I am very pleased with it."

Mr. A. J. Simmonds, Welling, Kent.—"I purchased from you a week ago the Pocket 4 Transistor Kit. I put it together last night in 1½ hours. On switching on the set, I was right on Radio Luxemburg. I must say thank you, because not only has the set a very attractive appearance, it also behaves fantastically."



# Smith's

of  
EDGWARE ROAD

## THE COOPER-SMITH "MAGNUM" 20 WATT POWER AMPLIFIER

### COMPONENT PRICE LIST

Buy direct from the  
Designers to ensure  
100% results  
Guaranteed for 3 years

All enquiries promptly  
dealt with

Carriage free in U.K.

**H. L. SMITH & CO. LTD**  
287/9 EDGWARE ROAD  
LONDON W2

Telephone  
Paddington 5891 & 7595

V2 12AU7/ECC82	...	£	s.	d.
V3 EL34	...	1	0	0
V4 EL34	...	2	8	7
V5 GZ32	...	6	10	0
Input plug and socket, coaxial	...	4	2	0
Speaker plug and socket (2)...	...	2	7	0
Power socket, pre-amp., Int. Oct.	...	(inc. P.T.)	14	3
Power plug and socket, tuner, 5-pin	...	(incl. P.T.)	14	3
Mains plug and socket	...	...	15	0
Motor plug and socket, P360	...	...	15	0
Valve holders, B9A (2)	...	(inc. P.T.)	19	11
Valve holders, Int. Octal (3)	...	...	1	0
Speaker matching socket, 9-pin and	...	...	1	0
Speaker matching plug to fit (3Ω, 8Ω or 15Ω)	...	...	2	3
Mains selector and fuse, 2A	...	...	3	9
H.T. fuse and holder, 250mA	...	...	3	9
Group board and fixing screws	...	...	4	0
Chassis, cover and base	...	...	1	6
Nuts and screws, T.C. wire, sleeving, etc.	...	...	2	3
Instructions	...	...	5	0
Total	...	£24	2	6
Inclusive price for complete kit	...	£21	2	6
Laboratory built and tested	...	£23	12	6

## THE MODERN BOOK CO

The Radio Amateur's Handbook.  
1961. 32s. 6d. Postage 2/-.  
20 Suggested Circuits. A Data  
Publication. 3s. 6d. Postage 4d.

Short Wave Receivers For The  
Beginner. A Data Publication. 6s.  
Postage 6d.

Romping Through Mathematics. By  
R. W. Anderson. 5s. Postage 6d.

The Stereo Sound Book. A Focal  
Publication. 12s. 6d. Postage 9d.

Television Engineers' Pocket Book.  
By J. P. Hawker. 12s. 6d. Postage 6d.

A To Z In Audio. By G. A. Briggs.  
15s. 6d. Postage 9d.

World Radio TV Handbook, 1961  
ed. 16s. 6d. Postage 1s.

Model Radio Control. By E. L. Safford.  
21s. Postage 1s.

TV Fault Finding. A Data Publication.  
5s. Postage 6d.

Introduction To Wireless. By W. E.  
Pearce. 10s. 6d. Postage 9d.

Reference Manual Of Transistor  
Circuits. By Mullard. 12s. 6d.  
Postage 1s.

A Beginner's Guide To Radio.  
By F. J. Camm. 7s. 6d. Postage 6d.

Practical TV Trouble-Shooting. A  
Gernsback Lib. Publication. 18s. 6d.  
Postage 9d.

We have the Finest Selection of British and American Radio Books in the Country

Complete catalogue 1s.

19-21 PRAED STREET (Dept RC) LONDON W2

Telephone PADddington 4185

# Premier RADIO

23 TOTTENHAM COURT ROAD LONDON W1 Telephone MUSEum 3451/2  
and 309 EDGWARE ROAD LONDON W2 Telephone PADddington 6963



The "Petite" PORTABLE  
MAY BE BUILT FOR £7.7.0 plus 3/-  
P. & P.


Batteries extra  
HT 10/- (Type B126) or  
equivalent.  
LT 1/6 (Type AD35) or  
equivalent.  
★ Size only 8" x 8" x 4 1/2".  
★ Instruction book 1/6.  
Battery Eliminator, avail-  
able in component form  
price 37/6 plus 2/- P. & P.

### BATTERY ELIMINATOR


Housed in two containers  
which are to replace AD 35  
and B 126 Batteries.

MAY BE BUILT FOR 37/6  
Plus 2/- P. & P.

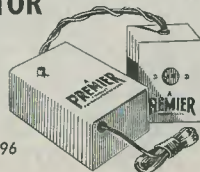Only suitable for use with DK96  
Series valves.



### THE SUPER 60

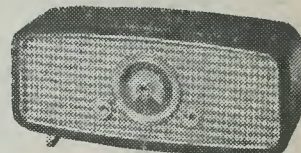

6-Transistor  
BATTERY  
RECEIVER  
MAY BE  
BUILT FOR  
£9. 15. 0  
plus 4/6 P. & P.  
Ever - Ready  
PP10 Battery  
Extra 11/-

**STAR FEATURES:**  
★ Six 1st grade Mullard Transistors and one Diode  
★ Internal Ferrite Rod Aerial  
★ 7" x 4" Elliptical Speaker  
★ Printed Circuit  
★ 500mW Push-pull Output  
★ Full Medium and Long wave-band coverage  
★ Calibrated Direct Drive Dial Drive Assembly  
★ Full point-to-point instructions supplied  
★ Dimensions 18" x 7 1/2" x 5 1/2"

The Receiver is housed in an attractive contemporary mahogany finished cabinet trimmed with gilt, supported by gilt stands.  
The Receiver will operate for months on one 9-volt long-life battery.  
Instruction Book separately at 2/6 p.p.

# FREE TO AMBITIOUS ENGINEERS

- THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?  
ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

We definitely Guarantee  
"NO PASS—NO FEE"

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £25 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

BRITISH INSTITUTE OF ENGINEERING  
TECHNOLOGY (Incorporating E.M.I. Institutes)  
(Dept. SE/23), 29 Wright's Lane, London, W.8

THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD

### WHICH IS YOUR PET SUBJECT?

Mechanical Eng.,  
Electrical Eng.,  
Civil Engineering,  
Radio Engineering,  
Automobile Eng.,  
Aeronautical Eng.,  
Production Eng.,  
Building, Plastics,  
Draughtsmanship,  
Television, etc.

GET SOME  
LETTERS AFTER  
YOUR NAME!

A.M.I. Mech. E.  
A.M.I.C.E.  
A.M.I. Prod. E.  
A.M.I.M.I.  
A.I.G.B.  
A.F.R. Ae. S.  
B.Sc.  
A.M. Brit. I.R.E.  
City & Guilds  
Gen. Cert. of Education  
Etc., etc.

### PRACTICAL EQUIPMENT

Basic Practical and Theoretic Courses for beginners in Radio, T.V., Electronics, Etc., A.M. Brit. I.R.E. City & Guilds Radio Amateurs Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

### INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T. (Incorporating E.M.I. Institutes) NOW offers you a real laboratory training at home with practical equipment. Ask for details.

B.I.E.T.  
SCHOOL OF  
ELECTRONICS

### POST COUPON NOW!

Please send me your FREE 156-page "ENGINEERING OPPORTUNITIES" (Name if you prefer not to cut page)

NAME.....

ADDRESS.....

.....

SUBJECT OR EXAM THAT INTERESTS ME.....

**★ VALVES NEW TESTED AND GUARANTEED ★**

1R5	6/6	6X4	7/6	DK92	7/6	EL84	8/-
1S5	6/6	6X5GT	6/6	DK96	8/-	EL91	7/6
1T4	4/6	12AH8	10/6	DL92	6/9	EY51	7/6
3S4	6/9	12AT7	6/-	DL94	7/6	EZ40	6/6
3V4	7/6	12AU7	6/-	DL96	8/-	EZ80	6/6
5U4G	6/-	12AX7	7/6	EB91	4/6	EZ81	7/-
5Y3GT	7/6	12BH7	10/6	EBC41	9/6	PL81	13/6
5Z4G	9/-	12K7GT	8/6	EBF80	10/6	PL82	10/6
6AK6	6/6	12K8GT	13/6	ECC81	6/-	PY81	8/-
6AL5	4/6	12Q7GT	6/6	ECC82	6/-	PY82	7/-
6AM6	4/-	25A6G	10/6	ECC83	7/6	PCC84	9/6
6AT6	7/6	25L6GT	9/-	ECC84	7/6	PCF80	9/-
6BA6	8/6	35Z4GT	8/6	ECC87	7/6	PCF82	11/-
6BE6	7/6	35L6GT	9/6	ECH81	10/6	PCL82	7/6
6BR7	10/6	5763	10/6	ECH42	8/6	R19	12/6
6BW6	8/6	DAF91	6/6	ECL80	9/6	U76	8/6
6J7GT	8/6	DAF96	8/-	EF41	8/6	UBC41	10/-
6K7G	7/6	DF91	4/6	EF80	8/-	UCH42	10/6
6Q7G	7/6	DF96	8/-	EF86	9/6	UF41	10/-
6SL7GT	8/6	DH76	8/6	EF91	4/6	UL41	8/-
6SN7GT	8/6	DH77	7/6	EF92	5/6	UY41	8/-
6V6G	7/6	DK91	6/6	EL41	9/-	W76	8/6

**Volume Controls.** All values, long spindle. L/S 2/9, s.p. 3/9, d.p. 4/3; ext. spkr. control 3/-.

**P.M. Speakers.** 3 ohms 5" 14/6, 6 1/2" 17/6, 8" 21/-, 10" 25/-, 12" 30/-; Bakers 12" 15 ohm 15W, 90/-.

**Coaxial Plugs 1/- each; Sockets 1/- each.**

**C.R.T. Isolation Transformers** with nil, 25% and 50% boost, low capacity a.c. mains 200/250V for 2V 4V, 6.3V and 13V tubes. All 10/6 each. P. & P. 1/6.

**Valveholders.** 4, 5, 7 pin English and U.S.A. B7G, 59A, 10, M0, B8G, 9d. each; B7G, B9A with screening can, 1/6; B12A, 1/3; Aladdin formers 1/4" with core, 8d. each.

**Jack Plugs.** Miniature standard 3/-; Sockets 3/-.

**Capacitors.** Small mica, 5% 1pF to 100pF, 8d.; 120pF to 1,000pF, 9d.; 1,000V wkg. .01, .0015, .0025, .004, .005µF, 1/- each.

**Crystal Diodes.** G.E.C., 1/6 each.

**Ceramic Capacitors.** Close tol. 500V for V.H.F., 9d.

**Paper Tubular.** .001-1.500V, 9d.; .25, 1/-; .5, 1/6; .01 1,000, 1/-.

**Paper Blocks.** 4µF, 1,000 wkg., 3/6; 4µF 250V, 2/6.

**Rectifiers.** Contact cooled, 250V 50mA, 7/6; 85mA, 9/6.

**Reaction Condensers.** .0001, .0003, .0005µF, 4/6 each.

**Heater Trans.** 200/240V, 6.3V, 1.5A, 7/6; 3A, 10/6.

**Resistors.** 1/4 and 1/2W, insulated, 4d. and 6d.; 1W, 8d.; 6W W.V., 1/-; 10W, 2/-.

**Electrolytics.** Wire ends. 25/25V, 1/6; 50/50V, 2/-; 12/50V, 9d.; 8/450V, 2/-; 16/450V, 2/9; 16/500V, 3/6; 32/450V, 4/-; 8+8/450V, 4/6; 8+16/450V, 4/6; can types; 16/450V, 3/6; 16+500V, 6/-; 32/500V, 6/6; 32/450V, 6/6; 20+20/450V, 4/6; 64+120/275V, 7/6.

**Wavechange Switches.** Midjet: 1p 12W, 2p 6W, 3p 4W, 4p 3W, 4p 2W, long spindles, 4/6.

**Toggle Switches.** QMB, s.p.s.t., 2/-; s.p.d.t., 3/3; d.p.s.t., 3/6; d.p.d.t., 4/-; rotary s.p., 3/-.

**Chokes.** 65mA 10H, 5/6; 80mA 15H, 8/6; 100mA, 10H 10/6; 150mA 10H, 14/6.

**Matched Pairs.** EL84, 17/-; EL85, 25/-; 6V6G, 17/-; 6BW6, 18/-; KT33C, 19/6; 807 14/6 pair. KT66, 32/6

**SETS OF VALVES**


DK96, DF96, DAF96, DL96 "REGENT"	29/6 per set
DK91, DF91, DAF91, DL92, or DL94	21/- per set
1R5, 1T4, 1S5, 3S4, or 3V4	21/- per set
6K8, 6K7, 6Q7, 6V6, 5Z4, "G" Types	27/6 per set
12K8, 12K7, 12Q7, 35L6, 35Z4, GT Types	35/- per set
ECH42, EF41, EBC41, EL41, EZ40	37/6 per set
UCH42, UF41, UBC41, UL41, UY41	35/- per set

P.P. Op. Transformers. MR 3-15 ohms for EL84, 6V6, 6BW6, etc., 18/6; Op. Pen. 50mA, 5/6; 30mA, 4/6. ★ P. & P. 6d., over £1 post paid. C.O.D. 2/6

**R. COOPER G8BX** 32 SOUTH END CROYDON SURREY CROYDON 9186

**Build the R.C.S. TAPE TUNER**  
AS DESCRIBED IN MARCH ISSUE

Put your FAVOURITE PROGRAMME on TAPE




**30/-**

All parts to Build

**The BIJOU**  
EASY TO BUILD TWO STAGE TRANSISTOR SET

As described in December issue  
The set that looks like a Radio Set.




- Attractive Case
- Mini 0.0005 µF Tuner
- High Q Litz Coil
- Works for months off No. 8 Battery
- Simple to construct in 15 minutes.

**TOTAL BUILDING COSTS 25/-** P.P. 1/6

You can't go wrong—We guarantee good results  
Components Price List. Layout Plans 1/6 free with order


**R.C.S. PRODUCTS (RADIO) LTD**  
11 Oliver Road London E17 Mail Order Only

**SOLO SOLDERING TOOL**  
ONLY 12/6

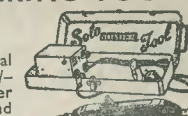

110V, 6V or 12V (special adaptor for 200/250V, 10/- extra). Automatic solder feed including reel solder and spare parts. It is a tool for electronic soldering or car wiring. Revolutionary in design. Instantly ready for use and cannot burn. In light metal case with full instructions for use. Post 3/6.

**EXTENSION SPEAKER** 19/9



8" P.M. Speakers fitted into polished cabinets. (Complete.) Switch and flex included. P. & P. 3/9.

**VALVES**

9d. each, 7/6 doz. 2D21, 4D1, 6AL5, 6C6, 6C9, 6D2K, 6J5, 6J7, 6SC7, 6SK7, AR6, EB91, EF36, EF39, T41, VR107, TT11, VT510, VT501, 2/9 each, 30/- doz. 6AM6, 6D6, 6F12, 6F13, 6F14, 6Z4, 7B7, 7Q7, 10F1, 25Z5, CL33, ECC34, ECC91, EY51, TH41, U24, U801, VP41, EF91, 5/9 each, 60/- doz. 5U4, 6Q7, 6V6, 6X5, 12AT7, 12AU7, 12K7, 12K8, 12Q7, EBC33, ECC31, ECC81, ECC82, ECC84, ECF80, ECL80, EL33, EL38, EL41, PY81, PL81, U76 and many others.  
Postage 1-7d. 6-1/6 12-2/6

**TO CLEAR 8/9**  
Ex manufacturers' salvag—5, 6, 8 and 7" x 4". P. & P. 2/9.  
Money back guaranteed.

**DUKE & CO (London) LTD**  
621/3 ROMFORD ROAD MANOR PARK E12  
Telephone ILF 6001/3 Latest FREE Catalogue

**SENSATIONAL NEW 1961 DESIGNS—BY CONCORD**  
LOW PRICES \* PICTORIAL STEP-BY-STEP PLANS \* EASY AS A.B.C.

**THE NEW "LISBON" TRANSISTOR SET**



Build the miniature highly sensitive "Lisbon" design. This is a pocket 2-stage transistor set not much larger than a matchbox. Excellent clear reception covering all medium waves and working for months and months off a tiny 1 1/2 or 3 volt battery costing only 3d. A very simple set to build and an excellent introduction to transistor circuitry. Everything can be supplied down to the last nut and bolt, including simple as A.B.C. pictorial step-by-step plans for only 19/6, plus post and packing 1/6 (C.O.D. 2/- extra). Parts sold separately, priced part list 1/-.

**OUR NEW 4-STAGE "MINUETTE"**



Build this newly-designed "MINUETTE" 4-STAGE transistor set in very strong ready drilled ultra-modern case, size only 6" x 3 1/2" x 1". Uses three transistors and diode and self-contained loudspeaker. Very sensitive, ideal for office, bedroom, holidays, etc. Months and months of listening off an 8d. battery. Can be built for only 39/6, including proper case, miniature speaker, etc. Simple as A.B.C. pictorial step-by-step plans, etc., plus post and packing 1/6 (C.O.D. 2/- extra). Parts sold separately, priced parts list 1/-.

**THE NEW 3-STAGE "RIO" only 29/6**




Don't be put off by the ridiculously low price, it is made possible by the bulk buying of transistors. This ALL-TRANSISTOR SPEAKER RADIO—THE "RIO"—covers all medium waves, etc. It is reliable and lightweight—slips easily into pocket or handbag—size only 4 1/2" x 2 1/2" x 1 1/4". Works for months and months off 8d. battery! Ideal for holidays, camping, bedroom, etc. Anyone can assemble it in an hour or two with simple-as-A.B.C. plan. Complete set of parts including miniature speaker—everything only 29/6, plus post and packing 1/6 (C.O.D. 2/- extra). Parts sold separately, priced parts list 1/-.

Cheques accepted. Cash on delivery 2/- extra. Please print name and address in block letters. Suppliers to schools, universities, Government and research establishments. Complete range of components and valves stocked. Regret no C.O.D. abroad. DEMONSTRATIONS DAILY AT WORKS

**CONCORD ELECTRONICS Dept R.C.1 210 Church Road Hove Sussex**

# THE ARGONAUT

## AM-FM, MW-VHF TUNER RECEIVER

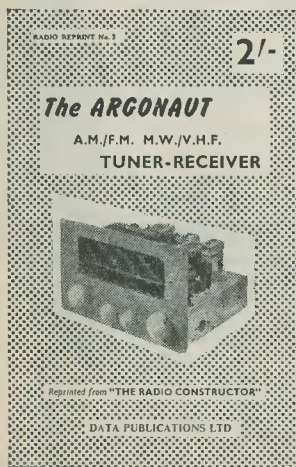

RADIO REPRINT No. 3

There is an increasing demand for A.M./F.M. receivers as the advantages of one cabinet housing a receiver covering both A.M. and F.M. reception are realised. Build this popular A.M./F.M. Tuner Receiver based on one of the proved attested Jason designs.

28 pp. plus stiff card cover 2s. postage 4d.

**DATA PUBLICATIONS LTD**  
57 MAIDA VALE · LONDON · W9


Telephone CUNningham 6141/2  
Telegrams Databux, London

# HOME RADIO OF MITCHAM

(Dept P), 187 London Road, Mitcham,  
SURREY. MIT 3282  
Shop hours 9 a.m. to 6.30 p.m. Wed. 9 a.m. to 1 p.m.

## NEW CRYSTAL

### MICROPHONES

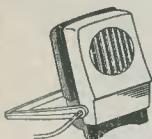

A high quality crystal hand microphone with built-in stand for desk use. Strong neat plastic case, and complete with 5 ft. screened lead.

Very sensitive and excellent response, ideal for tape recorders, transmitters, etc. Individually boxed and offered at a specially reduced price. **ONLY 21/- EACH**, plus 9d. post.

## ANTEX "PRECISION" SOLDERING IRON



A wonderful new miniature iron for the constructor. Five different sizes of interchangeable bits are available, also a practical bench stand and solder holder. All voltages from 6 to 240 volts in stock. Fully descriptive leaflet on request with s.a.e. Model as illustrated. **PRICE 29/6**, post paid. (Please state voltage).

## MULLARD BOOKS IN STOCK


### CIRCUITS FOR AUDIO AMPLIFIERS

Full constructional details for 12 exciting Hi-Fi designs. We stock all the parts. **PRICE 8/6**, plus 1/- post.

### TRANSISTOR MANUAL


The most up-to-date and comprehensive text book on transistor techniques, including 30 practical circuits, etc. **PRICE 12/6**, plus 1/- post.

## H.M.V. HIGH-FIDELITY EQUIPMENT

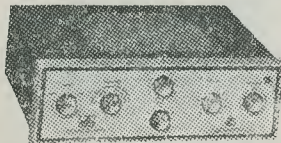

We are proud to announce that we are Appointed Agents for the range of H.M.V. Hi-Fidelity Sound Equipment. Illustrated is Model 544, the 4+4 watt stereo integrated amplifier at a moderate price, for those who demand the highest standards but whose loudspeaker requirements are not excessive. Elegant styling and power take-off for tuner. **PRICE 26 Gns.** Other models in stock, including the fabulous "Stereoscope" units.

## THIS WILL AMAZE YOU!

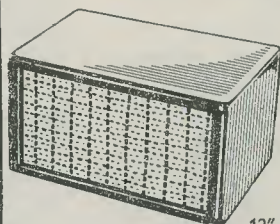


specially designed loudspeaker. **PRICE £5.19.3**, post paid. Please send for fully descriptive leaflet. Ideal for modern homes where space is at a premium.

The TSL "High-Q" Flexette Sound Reproducer is a giant in performance and a midget in size. Crisp, clear, natural, true reproduction without coloration gives a striking new experience in sound. Genuine high fidelity is achieved with minimum size. Frequency response 45 to 15,000 cycles. Power handling 4 watts continuous, 10 watts peak. **SIZE ONLY 12" x 6 1/2" x 7 1/2"**. Complete with

**PLEASE CALL AND HEAR IT**

## POCKET TRANSISTOR PORTABLE

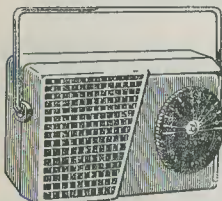

The OSMOR 6-Transistor Portable incorporates the latest design techniques and uses a printed-circuit panel to simplify construction. Performance equal to equivalent commercial receivers. All parts available separately, and fully detailed construction sheet and price list **PRICE 1/6**, post 6d. Covers Medium and Long wave and has built-in aerial and sensitive loudspeaker. Start building today ready for your holidays. We recommend that this

superhet circuit is only suitable for the experienced constructor. **TOTAL COST TO BUILD SET, £10.0.0.**

## HOLIDAYS AHEAD—GET A "UNIC" SHAVER



Precision engineered by a famous Swiss watch company the UNIC battery-operated Shaver will give you fast clean shaves anywhere, in the car, on the ship, in the train, on holiday, or at home. Uses single U2 cell and is fully suppressed against interference. Start this new modern easy way of shaving now. Ideal for camping, touring, sailing, or using at the office before important appointments. **PRICE £2.19.6**, complete, post paid.

## WE ARE ACTUAL STOCKISTS OF HEATHKITS



### HEADPHONES

Specialists in the supply of all types of headphones. Ex govt. low resistance 7/6. New "Royal" lightweight 4000 ohms high resistance 15/-. Popular S. G. Brown type "F" high resistance rugged construction 37/6. Ericssons professional pattern as recommended by Eddystone **£4.2.6**. PLEASE ADD 1/- post and packing to order.

### SPECIAL


Useful triple condenser 60+40+40 M.F.D 450 Volts. 12/6 each.

### COMPONENT CATALOGUE

2/- post 9d.

**NYLON DRIVECORD 4/6 25 yard reel**

## PULLIN SERIES 100 TESTMETER

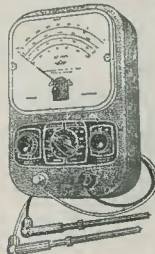

21 ranges and sensitivity of 10,000 ohms per volt. Printed circuit construction gives rugged, accurate instrument. New style diakon meter cover gives wide angle of vision and clear scales. Supplied complete with leads and prods. Full specification on request. **PRICE £12.7.6**, post paid. Terms **£2.7.6** deposit and 6 monthly payments of 35/-, or 12 monthly payments of 18/6.

# The Radio Constructor

Incorporating THE RADIO AMATEUR



APRIL 1961

Suggested Circuits No. 125: A Transistorised Capacity Meter, by G. A. French

654

In Your Workshop

658

Understanding Television, Part 39, by W. G. Morley

667

Can Anyone Help?

675

Designing a High Impedance Transistorised Voltmeter, by S. Smith

676

A Printed Circuit Pre-Amplifier, by G. N. Dale

679

Design for a Stereo/Mono Microphone Mixer Unit, by P. R. Travers

686

An External Loudspeaker with Automatic Switching, by M. J. Dunn

688

The "Twinette" Two-Transistor Receiver, described by R. J. Caborn

689

Getting Started on 2-Metres, Part 1, Aerial Systems, by J. N. Walker, G5JU

697

Radio Topics, by "Recorder"

700

Groupboard Techniques, by Ian Gardner

703

Electronic Vibrato for Amplified Musical Instruments, by Brian L. Phillips

706

Useful Transformer Tip, by S. G. Wood, G5UJ

710

© Data Publications Ltd, 1961

CONTENTS may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgment of source is given.

CONTRIBUTIONS on constructional matters are invited, especially when they describe the construction of particular items of equipment. Articles should be written on one side of the sheet only and should preferably be typewritten, diagrams being on separate sheets. Whether hand-written or typewritten, lines should be double spaced. Diagrams need not be large or perfectly drawn, as our draughtsmen will redraw in most cases, but all relevant information should be included. Photographs should be clear and sharp. Details of topical ideas and techniques are also welcomed and, if the contributor so wishes, will be re-written by our staff into article form. All contributions must be accompanied by a stamped addressed envelope for reply or return, and should bear the sender's name and address. Payment is made for all material published.

OPINIONS expressed by contributors are not necessarily those of the Editor or the proprietors.

TRADE NEWS. Manufacturers, publishers, etc., are invited to submit samples or information of new products for review in this section.

TECHNICAL QUERIES must be submitted in writing. We regret that we are unable to answer queries, other than those arising from articles appearing in this magazine; nor can we advise on modifications to the equipment described in these articles.

CORRESPONDENCE should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers, as appropriate.

REMITTANCES should be made payable to "DATA PUBLICATIONS LTD."



# Suggested Circuits

The Circuits presented in this series have been designed by G. A. FRENCH, specially for the enthusiast who needs only the circuit and essential data

No. 125. A Transistorised Capacity Meter

THIS MONTH'S SUGGESTED CIRCUIT is for a simple and relatively inexpensive capacity meter which employs two transistors and which can be powered by a 9 volt battery having a tap at 4.5 volts. The capacity meter has a useful overall range of 5 to 5000pF. It may be built up into a compact and self contained unit, a factor which makes it attractive for outside servicing work in addition to conventional applications in the workshop or laboratory. The capacity of the condenser under test is found by adjusting a calibrated two-gang tuning condenser with both sections paralleled, correct capacity being indicated by a sharp "dip" in the reading of a 0-1mA meter.

Making up the capacity meter should not raise many difficulties, especially for the more experienced constructor; but it must be pointed out that some component values are critical and may need adjustment from those shown in the diagram. Also, one of the coils required is not directly available through home constructor channels, since it consists of a conventional coil modified. A Medium wave broadcast receiver is needed during construction to carry out simple checks on the operation of part of the circuit.

## The Circuit

In the circuit, which accompanies this article, the condenser whose capacity is to be measured is connected to the two test terminals at the left hand side of the diagram. When  $S_1$  is set to Range 1 the test condenser is connected directly across coil  $L_1$ .  $L_1$  is the tuned winding in the oscillator circuit around  $TR_1$ , its coupling coil  $L_2$  connecting to the base of this transistor.  $C_4$  provides feedback from the collector of  $TR_1$ . The frequency of oscillation

is governed by the capacity of the test condenser, and component values in the circuit are such that reliable oscillations are obtained for a test capacity range, directly across  $L_1$ , from zero to 900pF. When  $S_1$  is set to Range 2 the test condenser is applied to  $L_1$  via the 1000pF condenser  $C_1$ , this enabling the range to extend beyond 900pF to some 5000pF. Condenser  $C_2$ , connected permanently across  $L_1$ , stabilises the oscillator circuit for test condensers having very low capacities.  $L_1L_2$  is a conventional Medium wave r.f. coupling coil.

The oscillatory voltage appearing across  $L_1$  is applied, via  $C_3$  and the tuned circuit  $C_8C_9$  and  $L_3$ , to the OA79 shunt detector. The OA79 rectifies, causing a negative voltage to appear on its upper terminal whose magnitude varies with the resonant frequency of the tuned circuit  $C_8C_9$  and  $L_3$ . When the tuned circuit is resonant at the same frequency as the oscillator it offers maximum impedance, and the negative voltage on the upper terminal of the OA79 is at a minimum.

The upper terminal of the diode connects, via  $R_6$ , to the base of transistor  $TR_2$ . A 0-1mA meter, together with variable resistor  $R_8$  and current limiting resistor  $R_7$ , is connected in the collector circuit of this transistor.  $TR_2$  functions as an amplifier, and the current flowing through the meter decreases as the negative voltage on the upper terminal of the OA79 decreases.

The overall operation of the circuit may be summed up in the following manner. The condenser under test is connected to the test terminals, causing  $TR_1$  to oscillate at a frequency which corresponds to the test capacity. Condenser  $C_8C_9$  is swung from minimum reading in the 0-1mA meter, this corresponding to minimum voltage on


the upper terminal of the OA79 and to resonance in  $C_8C_9$  and  $L_3$  at oscillator frequency. The value of the test condenser is then read from a scale fitted to  $C_8C_9$ .

## Points of Design

There are several points in the design of the capacity meter which need consideration.

To begin with, it is a requirement of the oscillator circuit around  $TR_1$  that reliable oscillations at fairly constant amplitude be generated when  $L_1$  is tuned by a parallel capacity ranging from slightly greater than 10pF ( $C_2$  plus circuit strays) to 900pF. This is a much wider range of tuning capacity

amplitude at the low frequency end of the band. Emitter resistor  $R_5$  is a normal stabilising component, but its parallel condenser  $C_7$  has a value which is low enough to permit a small level of negative feedback. In the prototype  $C_7$  was fairly critical (within plus or minus some 300pF) and its value may require adjustment in units built in conformity to the circuit. The question of component value adjustment is discussed later when constructional details are given. It should be pointed out that the values shown in the circuit were arrived at using an Osmor QHF8 coil in the  $L_1L_2$  position. Other coils will almost certainly require different component values around the

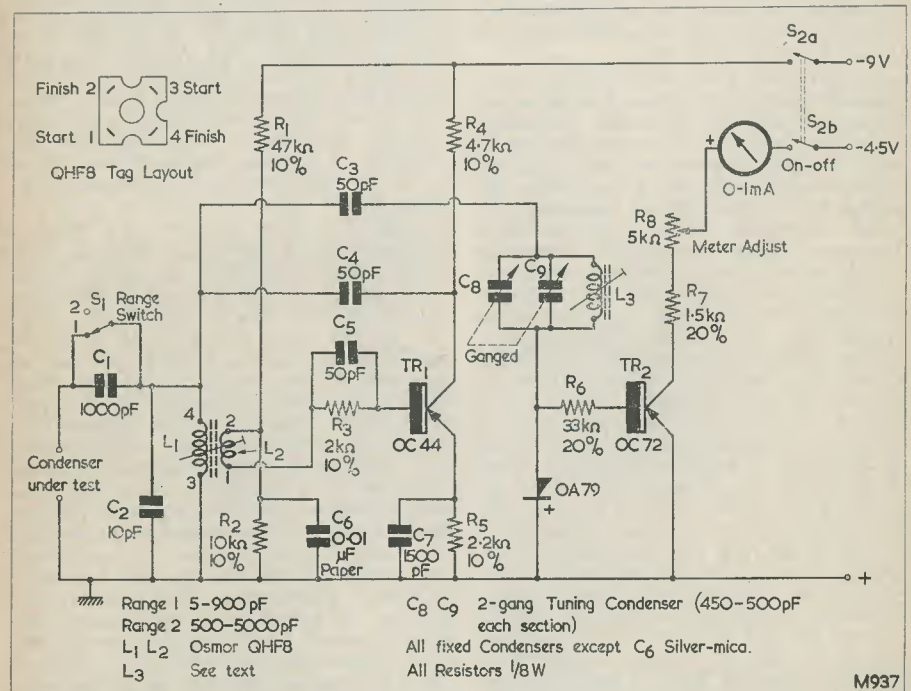

than is given in normal Medium wave oscillator circuits and it was found, with the prototype capacity meter, that the values of some components around  $TR_1$  tended to be critical in consequence. Condenser  $C_5$  and resistor  $R_3$  are inserted in the base circuit of  $TR_1$  to assist in obtaining reliable oscillations over the wide tuning range. The presence of  $R_3$  in series with the base limits base r.f. current and helps to keep oscillator amplitude reasonably level, particularly over the higher frequency end of the band of frequencies covered. Condenser  $C_5$ , across  $R_3$ , boosts oscillator

transistor.

When, in the prototype, component values had been finalised at those shown in the diagram, oscillator performance was checked by deleting  $C_2$  and connecting a two-gang condenser, with both sections (each 500pF) paralleled, across  $L_1$ . The oscillatory voltage across  $L_1$  was measured. Variations in oscillator voltage as the condenser was swung were smooth, and oscillator voltage was at no time less than 50% of maximum value. (The latter occurring around 300pF tuning capacity). It was considered that these results were adequate

for present purposes.

It was initially intended that the tuned circuit  $C_8C_9$  and  $L_3$  would be coupled to  $L_1$  such that it absorbed energy when it was at the resonant frequency of the latter. In practice, however, this scheme proved unsuccessful owing to the difficulty of obtaining a satisfactory fixed coupling between the two tuned circuits which could cater for the wide range of frequencies covered. The alternative device of connecting  $C_8C_9$  and  $L_3$  in series with the r.f. feed to the crystal diode was then tried out, and was found to be extremely successful. With the prototype, the dip achieved in the milliammeter for all values of test capacity checked was always less than 20% of full scale deflection, some values of test capacity (around 100pF) causing dips down to 10% of full scale deflection.

In a capacity meter of this nature it is possible to have the test condenser connected across  $L_1$  and the calibrated condenser,  $C_8C_9$ , across  $L_3$  (as is done here), or to have the test condenser across  $L_3$  and the calibrated condenser across  $L_1$ . Since the testing process consists of adjusting two tuned circuits to resonate at the same frequency, either method of connection would enable the calibrated condenser to indicate the value of the test condenser. Connecting the calibrated condenser across  $L_1$  has the disadvantage that oscillator amplitude (within the typical limits mentioned above) will vary as the condenser is swung, and dips in indicating meter current would not be so obviously discernible as they would be if meter current were constant on either side of the resonant point. When the test condenser is connected across  $L_1$  oscillator amplitude becomes fixed at the level corresponding to the resultant oscillator frequency, and the dip then becomes obviously apparent. To take up discrepancies for differing oscillator amplitudes, resistor  $R_8$  (which is a panel component) may be adjusted for full scale deflection on either side of the dip. In practice it was found with the prototype that for test capacities across  $L_1$  above 500pF or so, slight changes in meter reading occurred as  $C_8C_9$  was adjusted. However, the discrepancies were such that meter current changed smoothly as the calibrating condenser was swung, and they did not detract from the conspicuousness of the dip.

Connecting the calibrating condenser across  $L_3$  has the disadvantage that the condenser frame must be isolated from chassis in the capacity meter. On the other hand, one of the test terminals connected to  $L_1$  assumes chassis potential, with the result that condensers in equipment being serviced may be measured *in situ*.

It is desirable to have an inductance in  $L_3$  which causes the vanes of  $C_8C_9$  to be completely, or almost completely, disengaged for resonance when no condenser is connected across the test terminals. This is because the rate of change of capacity with spindle rotation in  $C_8C_9$  is at its lowest at the minimum capacity end, and the condenser has to be given the greatest amount of rotation to offer resonance with low value test condensers. The low capacity end of the scale for  $C_8C_9$  suffers, in consequence, the least amount of cramping. In practice, it is desirable to give  $L_3$  an inductance which is such that a dip for zero test capacity is just discernible as the condenser is adjusted about its minimum capacity position, since this allows a quick check of meter zero calibration to be made from the front panel. The resultant capacity in  $C_8C_9$  which corresponds to zero capacity would then be approximately that in which the moving vanes just commence to mesh with the fixed vanes. When the prototype was set up in this manner it was found to be capable of being calibrated down to some 5pF.

Since the tuned circuit  $C_8C_9$  and  $L_3$  has considerably less parallel stray capacity than is present across  $L_1$ , the desired inductance in  $L_3$  to meet the requirements just quoted is considerably higher than that in  $L_1$ . The writer cannot specify a readily available coil for the  $L_3$  position, but he can state that it should not prove too difficult to modify a conventional Medium wave coil. The procedure adopted in checking the prototype may prove helpful to constructors, the processes involved being relatively simple to carry out. The circuit was first of all checked by using a conventional air-cored single-winding Medium wave coil in the  $L_3$  position. The particular coil employed was wound with Litz wire in a single pie on a former having a diameter of  $\frac{1}{2}$ in. The inductance of this coil was then increased by the simple expedient of scramble-winding a further 35 turns of 30 s.w.g. rayon covered enamelled wire over the top of the existing winding, and by inserting an adjustable iron dust core. Modified in this manner the coil gave the desired inductance and was capable of being finally adjusted with the iron dust core. Despite the fact that the additional turns were of single strand wire, instead of Litz, the Q of the modified coil was sufficiently high to allow the dip figures at resonance mentioned above to be achieved. The added core, incidentally, offered a convenient "zero-set" adjustment for the meter as a whole.

Little else in the circuit requires comment except, perhaps, the components specified

for the crystal diode and  $TR_2$  positions. An OA79 was employed in the prototype, but the choice of diode here should not be very important. Most alternative types should give equivalent results. An OC72 was fitted in the  $TR_2$  position in the prototype, but the function it carries out is not of a critical nature. Most general purpose a.f. transistors should cope in place of the OC72, although they may require different values in  $R_6$ .

#### Constructional Points

The layout of the capacity meter is not critical provided that no inductive coupling exists between  $L_1L_2$  and  $L_3$ . These two coils should be mounted some distance from each other with their axes at right angles. A good plan consists of positioning  $C_8C_9$  between the two coils, whereupon its bulk provides a measure of isolation between them.

$C_8C_9$  should, of course, be insulated from chassis. The capacity to chassis of all components in either tuned circuit should be kept as low as possible. Of the two test terminals, that connected to  $C_1$  should be mounted on an insulated panel with at least  $\frac{3}{8}$ in clearance from chassis all round. Variable resistor  $R_8$  is mounted on the front panel.

Suitable batteries would consist of a 9-volt grid bias battery or two 4.5 volt flash-lamp batteries in series. However, current requirements are so small that much smaller batteries may be used, if desired. If, due to the use of miniature batteries, a high internal battery impedance is expected, a 0.01 $\mu$ F condenser should be connected between the 9 volt negative h.t. rail and chassis.

After a suitable layout has been determined, the capacity meter should be assembled with  $C_2$ ,  $L_3$  and  $C_8C_9$  omitted. Before these components are fitted, the oscillator circuit has to be checked; and this is done in the following manner.

Connect the right-hand plate of  $C_3$  to the upper terminal of the OA79. The 0-1mA meter will now monitor oscillation amplitude directly. Temporarily connect  $C_8C_9$ , with both sections paralleled, across the test terminals, and set  $S_1$  to Range 1. Adjust the dust core in  $L_1L_2$  such that it offers maximum coupling between the tuned and coupling windings. Switch on the unit and swing  $C_8C_9$  across its entire range. There should be a reading in the meter for all settings of  $C_8C_9$  and this should not drop to less than 40% of the maximum reading obtained. (The figure of 40%, 10% less than that given by the prototype,

should be adequate in practice). If the presence of oscillations is doubted, a positive indication is given by the fact that the meter reading will drop to a low level when tags 3 and 4 of  $L_1L_2$  are short-circuited. Couple the aerial of a broadcast receiver switched to Medium waves to the oscillator tuned circuit by holding a wire from the aerial socket close to  $L_1L_2$ . It should be possible to obtain clean heterodynes with stations spaced around the Medium wave band as  $C_8C_9$  is adjusted. If a loud hiss from the receiver is evident as the resonant frequency of the oscillator approaches that of the station being received the oscillator is squegging, and this is an undesirable condition. The whole purpose of the check with the receiver is to ensure that squegging does not occur.

If the oscillator fails to meet the requirements just given,  $C_7$ ,  $C_5$  or  $R_3$  may need adjustment. Too high a value in  $C_7$  causes squegging whilst too low a value causes amplitude at the low frequency end of the range to drop.  $C_5$  boosts response at the low frequency end of the range and may be increased or decreased accordingly. When  $R_3$  has too low a value there may be abrupt, instead of smooth, changes in oscillator amplitude as  $C_8C_9$  is swung.

When the oscillator has been checked and is giving satisfactory results,  $C_8C_9$  should be connected into the proper position in circuit, and  $C_2$  should be fitted. For the time being, a conventional Medium wave tuned winding may be fitted in the  $L_3$  position. The complete circuit may then be quickly checked for varying test capacities from 5 to some 900pF on Range 1, and for the appropriate values on Range 2. At each test capacity a pronounced dip should be given in the meter (after  $R_8$  has been adjusted) when  $C_8C_9$  is at the appropriate resonant setting. The coil in the  $L_3$  position may then be modified, or another fitted, following the suggestions given earlier.

The final process consists of calibrating  $C_8C_9$  against known values of capacity, the calibration including the overlap between Ranges 1 and 2. Range 2 will occupy only part of the 180° range of rotation in  $C_8C_9$ . There is no point in calibrating Range 1 above 900pF or Range 2 below 500pF.

#### Current Consumption

The current consumption from the 9 volt supply, as measured on the prototype, lay between 0.4 and 0.8mA, according to the value of the test condenser. The current drawn from the 4.5 volt supply is, of course, that indicated by the 0-1mA meter.

# IN YOUR WORKSHOP



This month Smithy the Serviceman, and his able assistant Dick, encounter some of the problems which beset many of us at this time of year.

LIKE ALL GREAT MEN, SMITHY THE SERVICEMAN had his little eccentricities. One of these exhibited itself in an almost fanatical desire to maintain order and uniformity in the permanent mains wiring which was installed in the Workshop. Under Smithy's eagle eye all additions and alterations to this wiring had been made to conform to a standard which he himself laid down; and he obtained great satisfaction whenever he looked at the neatly cleated wires which travelled exactly parallel to each other around the walls. In Smithy's scheme of things a permanently installed mains cable could only be horizontal or vertical, and the transition from one state to the other must be contained within a right angle having a corner as sharp as the insulation of the wire would allow.

All the mains wiring in the Workshop originated from a large wooden block near the door which was fitted with two rows of switches. At the end of each day Smithy would stand at this board and snap off each in turn. It gave him a feeling, he once confided to his assistant Dick, rather as though he were a captain on his bridge. When Dick passed this information on to his uncle (who was the Steward at Smithy's club) the latter remarked that it reminded him of the landlord of a pub at closing time.

## Switchboard Modification

Arriving at the Workshop before Smithy, it was to this switchboard that Dick turned one morning. Moving feverishly, he extracted

two switches from his mackintosh pocket, and quickly screwed them to the board at the left hand end of each row of switches. He had just completed this job when he heard Smithy's approach. With a sigh of satisfaction he left the switchboard and proceeded to leisurely remove his mackintosh.

"Morning, Smithy,"  
"Good morning, Dick," replied the Serviceman heartily. "You're bright and early this morning! Well, let's have a bit of light on the scene."

Subconsciously following his usual practice of counting over the switches, Smithy depressed two of them. The dial lamp of a receiver on Dick's bench at once lit up.

"Well, that's queer," commented the Serviceman.

The puzzled frown on Smithy's face grew even deeper as a television receiver on his own bench commenced to give a 10 kc/s line whistle. Perplexedly, Smithy watched a blank raster form on its screen.

Smithy tried several other switches, and his expression changed to complete bewilderment as he found that each switch controlled a service different to that he had expected.

"This is quite fantastic," he muttered. "The wiring behind the switchboard just couldn't have changed over like this on its own."

Suddenly a suspicious gleam came into his eye, and he slowly counted the switches in each row. He then turned round to his assistant who was, by now, almost doubled

up. Speechless, Dick pointed at the calendar on the wall, and a light of understanding dawned in Smithy's face.

"I should have known," he commented bitterly, "it's April the First!"

## Bottom-End Coupling

Some ten minutes later the Workshop had fallen into its normal busy routine, with both Smithy and Dick bent over their benches. The two offending switches had now been removed, and the only evidence of the preceding scene was given by an occasional

"I've tried everything in his set, and I still can't get at the fault."

Smithy put his test prods down on the bench, and walked over to look at Dick's receiver.

"What exactly is the trouble?"

"It's the aerial input circuit," replied Dick. "The set is a simple Medium and Long wave receiver and the stages are all O.K. from the frequency changer anode onwards. Also, the oscillator's working correctly. But when I try to trim the aerial tuned circuits I can't get any sense at all! Here's the circuit in the

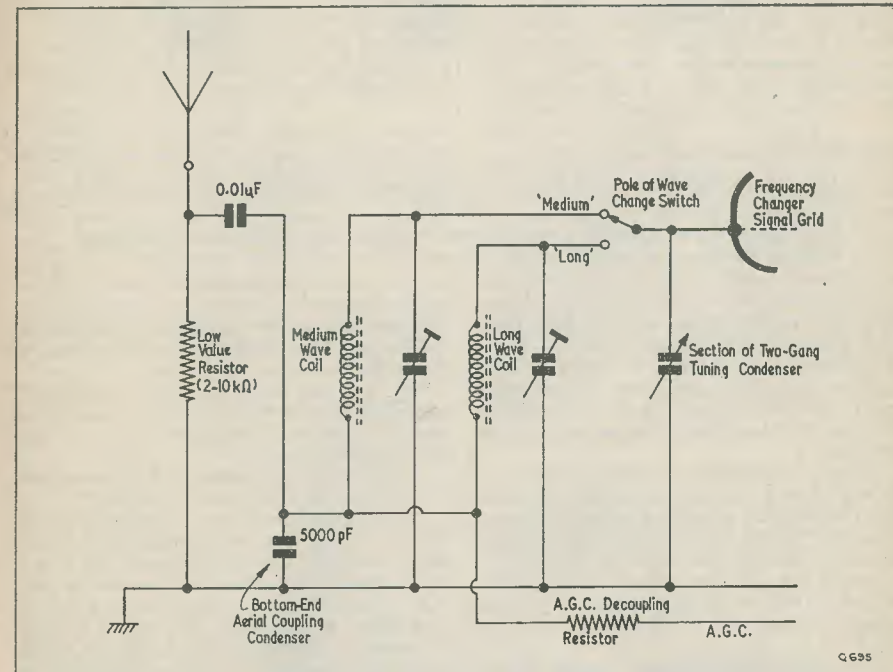


Fig. 1. A typical Medium and Long wave bottom-end coupled aerial circuit. The value given for the bottom-end coupling condenser (5,000pF) is typical of normal practice

retrospective chuckle from Dick, and a revengeful frown on Smithy's face. Dick was engaged in the repair of an a.m. Medium and Long wave sound receiver and, as he became more and more engrossed in his work, his chuckles gradually ceased.

"Smithy," he called out eventually. "Is it possible to have shorted turns in a coil wound with litz wire?"

"It's not impossible," commented Smithy over his shoulder, "but it doesn't happen very often. Hardly ever, in fact, if the litz wire is rayon covered."

"Then I give up," pronounced Dick.

service sheet. (Fig. 1.) I've checked the Medium and Long wave coils for resistance, and the Medium wave coil gives about an ohm or so and the Long wave coil about six ohms. Which shows there are at least no open circuits in the coils, but which doesn't confirm whether or not they have shorts between adjacent turns."

"Do you get the same trouble on both Medium and Long waves?"

"Yes. Neither aerial coil will trim."

"Then", remarked Smithy, "the fault lies more probably in a common component than in the coils. They would hardly both have

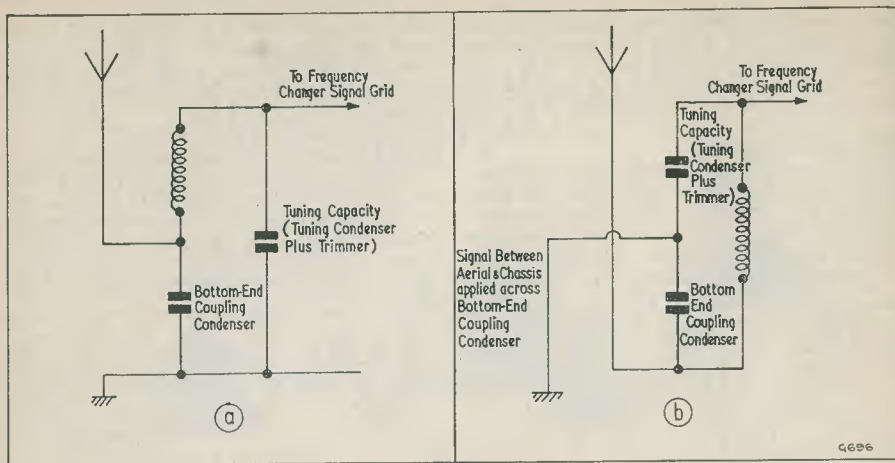


Fig. 2 (a). The bottom-end coupling circuit can be reduced to the simple form shown here

(b). This diagram, which is a rearrangement of (a), shows how the signal voltage between aerial and chassis is fed into the capacitive half of the tuned circuit

developed shorted turns at the same time. What's the set like with an aerial?"

"Fairish," said Dick. "I get the local stations reasonably well, and on the right part of the dial. There's a bit of a whistle with one of them which changes as you tune through."

"That," commented Smithy, "will be a second channel whistle, because the aerial tuned circuit isn't selecting the required signal properly. Have you checked the 5,000pF condenser between the coils and chassis?"

"Well, it's got no shorts in it," Dick replied, "because there's an a.g.c. voltage getting through to the frequency changer grid."

"Try changing it anyway," said Smithy shortly.

Obediently, Dick found a replacement condenser and soldered it into circuit.

"I had a shocking repair job to do last night," said Smithy chattily, as he watched Dick replacing the condenser.

"Oh, yes," remarked Dick. "What was it?"

"Just a record player," said Smithy carelessly. "And it didn't respond to any of the normal treatment. Ah, I see you've got that new condenser fitted in now. Let's see how the set behaves."

Dick switched it on. "Well, I'm dashed," he exclaimed after a moment. "The Medium and Long wave coils are trimming perfectly now!"

"And so they should," remarked Smithy. "But that condenser I replaced just now

was just an a.g.c. decoupler," protested Dick. "How on earth could it affect the tuning of the coils?"

"It was not only an a.g.c. decoupler," corrected Smithy. "It was also a bottom-end aerial coupling condenser. And it had undoubtedly gone o/c."

"A coupling condenser," Dick ejaculated, "with one side connected to chassis?"

"A coupling condenser," repeated Smithy firmly. "Now let's take a closer look at that input circuit. The arrangement used is a conventional bottom-end coupled aerial input circuit, and the aerial connects, via a 0.01μF condenser, to the upper plate of the 5,000pF component you've just replaced. Also connected to this condenser are the bottom ends of the Medium and Long wave coils, their top ends being selected by one pole of the wavechange switch. You will notice that there are no aerial coupling coils."

"Then how does the aerial signal get in?"

"Because of the bottom-end coupling condenser," Smithy picked up a pencil and started to scribble in Dick's notebook. "If you cut out the wavechange switch and some of the other components you will find that the circuit boils down to this. (Fig. 2 (a).) Which is exactly the same as this. (Fig. 2 (b).) Do you see how it works now?"

"It's coming a bit clearer," admitted Dick.

"The bottom-end coupling condenser is really part of the capacity tuning the coil. One way of feeding an aerial signal into a tuned circuit is to apply it to a tap in the coil. With bottom-end coupling you apply it to a tap in

the capacity! The fact that the aerial and earth inputs are upside-down doesn't matter, because you still have the same signal input voltage between these two points."

"That's exactly right," confirmed Smithy. "Also, you get a voltage step-up effect which is similar to that given by tapping into the coil. The step-up depends upon the ratio between the reactance of the overall tuning capacity—that is, the bottom-end condenser in series with the tuning and trimming capacity—and the reactance of the bottom-end condenser itself."

"Won't that ratio change as the tuning condenser is adjusted?"

"Definitely," replied Smithy, "and that's a snag with bottom-end coupling. Although it doesn't cause a lot of trouble in practice."

"What are the advantages of bottom-end coupling?"

"Well," said Smithy, "there are several important advantages. First of all you do away with a coupling winding on each coil, and this reduces coil manufacturing costs. Also, you only need one wavechange switch pole, as there are no coupling windings to switch."

"What about Short waves?"

"A bottom-end coupling condenser value suitable for Medium and Long waves," replied Smithy, "isn't much good for Short waves. But you can still add a Short wave

range easily enough. All you do is to put the Short wave coupling winding in series with the feed to the bottom-end condenser. (Fig. 3.) Since the Short wave coupling coil consists of a few turns of wire only, it doesn't have any effect worth writing home about on the Medium and Long wave circuits. Further, you can switch the grid coil and still retain your single wavechange switch pole."

"That's ingenious."

"It is a neat circuit," agreed Smithy. "And you will find it in most Long, Medium and Short wave receivers having bottom-end aerial inputs. Incidentally, a snag with bottom-end coupling is that the aerial input impedance is so low that you have to have an earth connection to the chassis to get any reasonable signal input. So, bottom-end aerial input circuits are used normally with mains receivers only."

"I don't get that," said Dick, puzzled. "Why only mains sets?"

"Because mains receivers are automatically connected to the earth provided by the mains wiring in the house or building. This wiring doesn't usually give a very good earth, admittedly, but it serves the purpose. If the receiver is an a.c./d.c. job the chassis will be connected directly to the mains wiring. If it's an a.c.-only job it will be connected to the mains wiring via the self-capacity in the

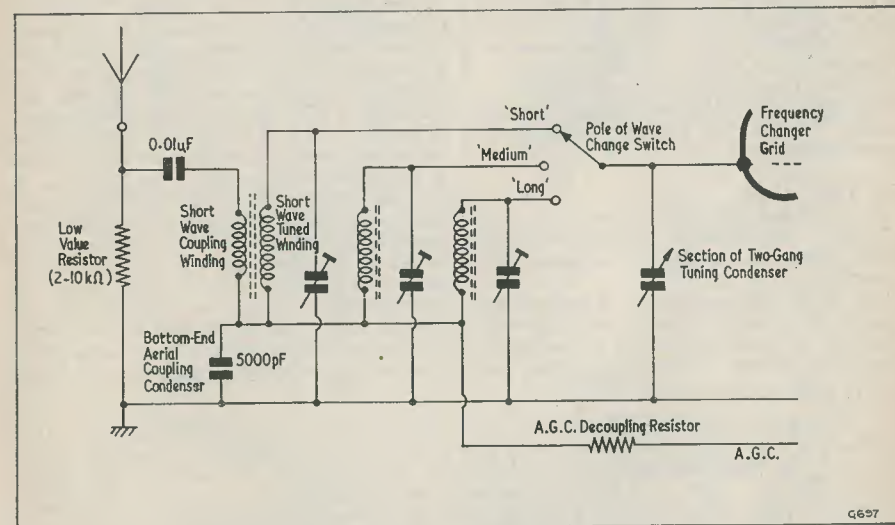


Fig. 3. Adding a Short wave range to the circuit of Fig. 1. The coupling winding of the Short wave coil is inserted in series with the aerial feed to the bottom-end coupling condenser, and its low inductance has little effect on Medium and Long wave performance. At the same time, the bottom-end coupling condenser provides a low reactance circuit to chassis for the lower ends of the Short wave coupling and tuned windings

mains tranny. In the latter instance the designer may, however, have added an anti-mains modulation condenser between one side of the mains and chassis, whereupon this condenser would also ensure that the chassis was effectively coupled to the mains wiring."

"There are one or two components in the circuit which puzzle me a little," confessed Dick. "What about the series 0.01 $\mu$ F condenser, for instance?"

"That's just an isolating condenser for use if the receiver is an a.c./d.c. job. It also prevents any voltages which appear accidentally on the aerial from finding their way on to the a.g.c. line."

"Fair enough," said Dick. "What's the low-value resistor between aerial and chassis for?"

"To prevent mains modulation of the input signal. The chassis may well have an a.c. mains voltage on it with respect to true earth and, if the aerial has a relatively large capacity to true earth, part of the a.c. voltage could appear across the bottom-end condenser. The low-value resistor very nearly short-circuits this a.c. voltage, whilst still offering a reasonably high impedance at r.f. It also very nearly short-circuits any hum voltages picked up by the aerial in the normal course of events. Unfortunately, it is difficult to give this resistor too low a value or you begin to lose aerial signal strength. Modulation hum is still possible, therefore, in the worst cases; as could occur if an aerial having a very large capacity to true earth were used with an a.c./d.c. receiver whose chassis happened to be connected to the live side of the mains."

"What's the solution to that problem?"

"Reverse the receiver mains plug," grinned Smithy, "so that the receiver chassis is at neutral potential."

#### T.V. Tuner Units

Dick digested this information.

"Aren't bottom-end coupling circuits getting rather old fashioned?" he asked after a moment.

"So far as the manufacture of a.m. sound receivers is concerned, yes," said Smithy. "Because it's more convenient nowadays to use ferrite frames. Nevertheless, there are

plenty of bottom-end aerial input receivers in use, and there are plenty which pass through the hands of service engineers. Don't forget, by the way, that bottom-end aerial coupling has been a fairly recent innovation on t.v. tuners."

"Come again?"


"You heard me. There are plenty of t.v. tuners knocking around these days with single-winding aerial coils. How do you think the aerial signal gets into them?"

"I've never really understood," confessed Dick. "When I look at the circuit diagrams of these tuners in the service manuals I see such a conglomeration of components around the aerial coil that I usually try and forget about them!"

"The circuits are quite simple really," said Smithy, "and they all start off with a basic bottom-end circuit like this (Fig. 4 (a).) Once again, you get a step-up effect like you had with the Medium and Long wave circuit, only in this case the total capacity across the coil is given by the bottom-end condenser in series with the input capacity of the r.f. amplifier valve. And, of course, you don't have a variable tuning condenser. You have, instead, a different coil presented to the circuit for each channel. Incidentally, the step-up given by the circuit is, in this case, that needed to match the 75 $\Omega$  impedance of the aerial to the input impedance of the valve."

"Normally," continued Smithy, "you want to apply a.g.c. to the valve, and so it's usual to put a blocking condenser and leak in the grid circuit. (Fig. 4 (b).) Compared with an input circuit using a coupling winding, the bottom-end input circuit has the disadvantage of leaving the grid rather wide open to the aerial, and so an i.f. rejector has to be added to prevent breakthrough. Here it is (Fig. 4 (c)), connected right across the input terminals. Oh, and there's neutralisation too, because the first valve in the tuner is almost bound to be a triode, this probably being part of a cascode. If you think about it you'll realise that the two ends of the coil are certain to be 180 degrees out of phase with each other at resonance, with the result that the neutralising condenser can be taken

Fig. 4 (a). The basic input circuit of a television tuner using a single winding aerial coil. The triode shown here is part of a double-triode cascode r.f. amplifier (b). In order that a.g.c. may be applied to the valve, it is necessary to add a blocking condenser and grid-leak (c). An i.f. rejector circuit is required also, to prevent breakthrough. (d). A further component is a neutralising condenser (e). The aerial isolating condensers. These appear between the "75 $\Omega$  input" of (d) and the actual aerial socket. The resistors across the condensers have high values (around 2M $\Omega$ ) and prevent the formation of static voltages on the aerial (f). The final component is a choke after the isolating condensers. This prevents Medium and Long wave breakthrough

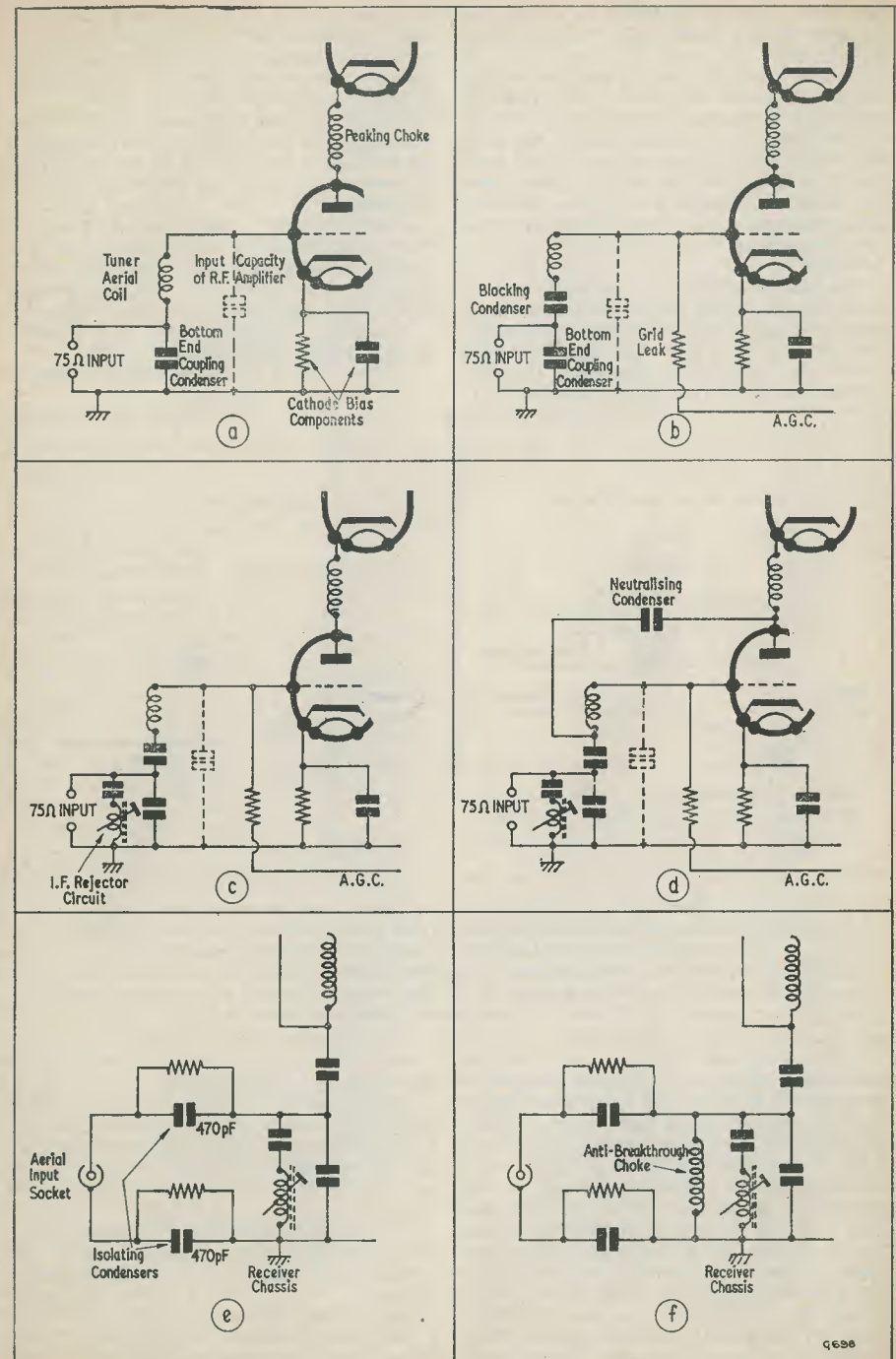

from the anode of the triode to the end of the coil remote from grid. (Fig. 4 (d).) O.K. so far?"

"I understand all the components you've added up to date," said Dick. "But I've still seen more in practical circuits!"

"I won't argue," replied Smithy, "so let's add the aerial isolating condensers and their parallel resistors. (Fig. 4 (e).) Now, you may find it surprising but the isolating condensers are liable to allow Medium or Long wave breakthrough to occur!"

"Hey?"

"Nothing less! Should you have a long co-ax download and live in an area of high signal strength, the download can pick up the local Medium or Long wave signal. If you assume, for the sake of argument, that the

condensers. (Fig. 4 (f).) This choke has a high impedance at t.v. frequencies, and a very low impedance at Medium and Long waves. The latter are, in consequence, shorted down to deck."

"Ah," said Dick with satisfaction. "Your final circuit is just about the sort of thing I see in Service manuals. And so that's how bottom-end coupling has found its way into t.v. tuners!"

"That's right," said the Serviceman. "Only this time it's usual to refer to the circuit immediately around the coil as a pi input circuit. The name's obvious enough if you draw the coil horizontally," (Fig. 6.)

A sudden thought crossed Dick's mind, and he changed the subject.

"What were you saying about a record

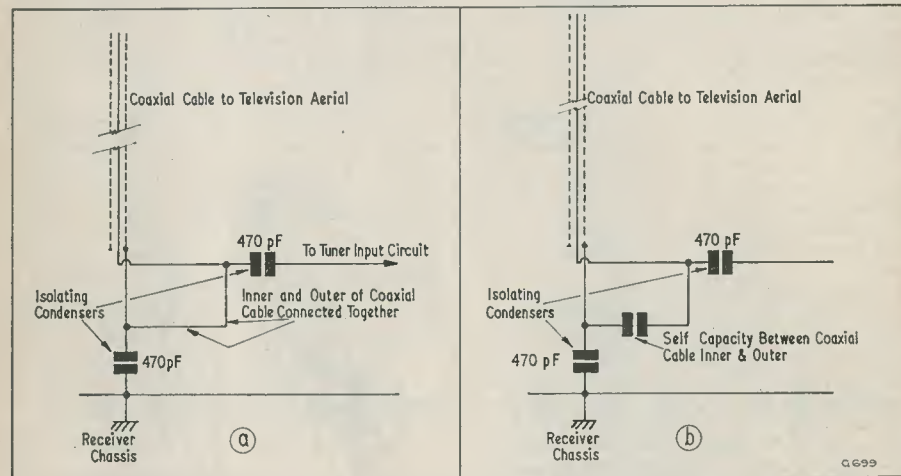


Fig. 5 (a). Showing how Medium and Long wave breakthrough is possible in a television tuner using a single aerial coil circuit. It is assumed here that the inner and outer conductors of the coaxial cable are connected together

(b). If the coaxial inner and outer conductors are not connected together they are still coupled by their self-capacity. In this instance the undesired signal would be largely picked up on the outer conductor

co-ax inner and outer conductors are short-circuited for Medium and Long waves then this signal is applied to the junction of the two 470pF isolating condensers. (Fig. 5 (a).) Quite a bit of the breakthrough signal will, obviously, find its way on to the grid of the first triode. In practice the co-ax inner and outer will only be connected together if you have a folded dipole sitting amongst the chimney pots but, even if the conductors aren't shorted together, their self-capacity will still be sufficiently high to allow the effect to occur. (Fig. 5 (b).) You overcome the trouble by adding a choke after the isolating

player you serviced last night?"

"I only said it was a shocker," replied Smithy. "As a matter of fact, the first snag I had with it was wow. You could almost see the variation in turntable speed. I had to clean up all the mechanical drive to the turntable."

"The synchronous motor," observed Dick. "Couldn't have been doing much good."

"This one didn't have a synchronous motor."

Dick looked interested.

"But don't you need a synchronous motor if you're running from the mains?"

"This one didn't get its power from the mains," said Smithy gravely. "It was a portable."

"Don't tell me it was one of those miniature battery jobs," said Dick excitedly. "Do you know, I've been trying to have a go at one of those for ages! How many speeds did it have?"

"Just the one."

"I know," enthused Dick. "It must be one of those 45 r.p.m. players. What did you do after you cleared the wow, Smithy?"

But the Serviceman was already moving back to his own bench.

"I can't stand here nattering all day," he complained. "We've got work to do."

And, deaf to his assistant's protests, he immersed himself in his work.

### Soldering Litz Wire

The Serviceman was to be left in peace for five minutes only.

"Smithy."

"Hello!"

"Can you just give me a bit of quick advice about this solder joint?"

The long-suffering Serviceman followed the well-trodden path to Dick's bench, where the a.m. sound receiver still lay.

"Dash it all," exploded Smithy, "haven't you finished that set yet?"

"I'm sorry, Smithy," said Dick contritely, "but when I worked on this set I removed some of the leads from the Medium wave coil. These were on the same tag that carried the litz wire from the winding. I'm a bit scared to solder the wires back now, in case I break any of the strands of the litz."

Smithy examined the tag.

"I don't blame your feeling worried about it," he remarked sympathetically. "What's happened here is a fairly common occurrence. When you first handle the connections to a tag of this nature, the litz wire is wrapped around it correctly and seems to be beautifully soldered. However, when subsequent soldering operations are carried out the litz joint suddenly starts to look unhealthily cold, and all the litz wire strands appear oxidised and brittle. Whenever I encounter a tag with litz wire soldered to it I try to leave it severely alone for exactly this reason. If I have to take away a wire which has been clenched on to the tag close to the litz I normally snip it. If I have to add a wire at the same point as the litz I do the soldering as quickly as possible."

"What exactly," asked Dick, "is the purpose of litz wire?"

Smithy sighed. Dick's fund of questions was like the widow's cruise.

"Well," he replied, "you have to remember that r.f. currents tend to travel on the surface of conductors. Litz wire has a lot of con-

ductors all interwoven together, with the result that you get a larger surface area for the r.f. to travel on than you would with a single round conductor of the same overall diameter. Also, the interweaving causes the strands in the litz wire to go in and out of the centre of the wire, and this forces some of the r.f. current to pass through the centre of the group of strands instead of on the outside ones only. The result is a further advantage over the round conductor. In actual fact, many of the multi-strand wires used for winding coils these days don't use the true litz formulation at all. Instead, they are what are called 'bunched' wires, this being a version which is cheaper to make and which gives, so far as I know, more or less the same results."

"Do all litz or bunched wires have a cotton or rayon outer covering?"

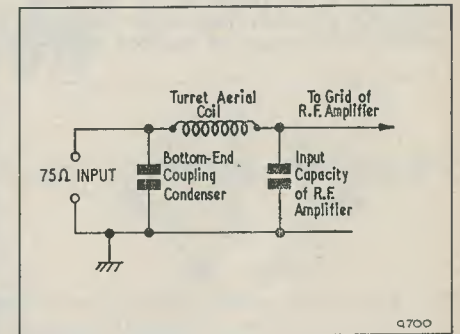


Fig. 6. When the tuned circuit components of Fig. 4 (a) are re-drawn as shown here they may be recognised as providing a pi coupling circuit

"Not necessarily," said Smithy. "It is essential, to start off with, that the strands in litz wire be insulated from each other, and this is normally done by using enamel insulation on the strands. The whole is then covered by a single, or double, rayon outside covering. Incidentally cotton, or natural silk for that matter, is rarely used nowadays for the outside covering of litz wire or any other enamelled winding wire. Rayon is cheaper. Some litz wires have no outer covering at all, the strands being held together sufficiently well for coil winding by passing them through an impregnating wax. Wire of this nature is known as 'waxed litz', and you occasionally encounter it in 465 kc/s i.f. transformers and the like."

"Talking of outside coverings," queried Dick, "I've sometimes heard people refer to 'art silk'."

"In this application," said Smithy, "art silk is rayon."

"How do they manage to solder all the strands of litz wire in the factory?"

"In the old days," said Smithy, "the enamel on the individual strands had to be burned off. The wire ends of a coil were pre-tinned before connection to the tags by initially passing them through a flame until the wire became red-hot. The red-hot wire was immediately doused in methylated spirits, and then just as quickly plunged into a heated pot full of molten solder. Once you got the knack of it, this process gave beautiful tinning."

"Didn't the meths ever catch fire?"

"Often! It was kept in a container with a hinged lid which could be flipped down if the meths caught alight, and thereby save ulcers in the insurance company. A funny thing about this process was that it was a once-only job. If you failed to tin the strands properly first go, you'd had it. The same length of wire would rarely tin on the second attempt. Modern litz, or bunched wire, has

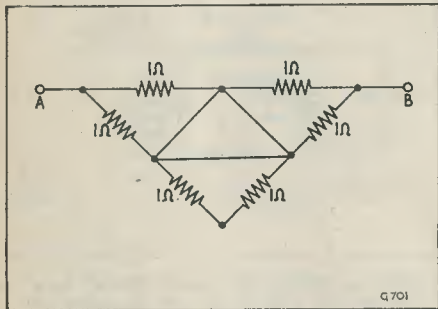


Fig. 7. Smithy's simple problem. What is the resistance between terminals A and B?

self-soldering enamel on the strands. This enamel melts at soldering temperatures, so you can either solder all strands on the tag itself or, preferably, pre-tin the wire end by dipping it in a pot full of molten solder."

"What frequencies is litz wire O.K. for?"

"Rough check," replied Smithy, "from some 200 kc/s or so up to 5 or 6 Mc/s. Outside these frequencies litz wire offers hardly any advantages over ordinary round conductors."

#### Smithy's Service Job

Dick was quiet for a moment.

"I hate to go back to that record player of yours," he remarked, "but I'm still completely fascinated by it. What else was wrong with it?"

"One thing I noticed", replied Smithy, "was that stylus wear was absolutely terrible.

You may not believe this, but I actually had to change over to a new stylus after playing only one side of a record."

Dick's eyes rounded.

"Phew, that was a *snag!*" he remarked. "Someone must have been cleaning up the pick-up with impact adhesive."

"Well, I didn't find anything like that," said Smithy, beginning to walk away. "And I must, for the second time this morning, remind you that I cannot stand here gassing all day long."

"Just satisfy a *little* more of my curiosity," pleaded Dick. "Was the output distorted?"

"It sounded pretty rough to me."

"At all volume levels?"

"There was only one volume level available," remarked Smithy soberly.

"Wasn't there even a volume control?"

"Nope."

"Then how did you control volume?"

"You didn't."

"Oh, come off it, Smithy," said Dick indignantly. "You can't *possibly* have a record player without a volume control!"

"This particular model", remarked Smithy, ignoring Dick's protests, "only comes on when the stylus is placed on the record."

"Well, that *is* a neat idea," said Dick enthusiastically, forgetting the lack of volume control for the moment. "I wonder what designers will think of next!"

But even Dick's fertile imagination was becoming unequal to the task of rationalising the picture conjured up by Smithy's words.

"You've just *got* to show me this gadget," he said eventually. "It sounds to me like the very *latest!*"

"Well, it was considered pretty modern when it was made," remarked Smithy.

"Around about 1930, I think it was."

Dick's mental image crashed about him in ruins.

"Why, you rotten devil," he cried, "you were talking all the time about an old-fashioned acoustic wind-up gramophone!"

"Of course I was," laughed Smithy. "It was you who made all the assumptions."

"But you said it only played one speed!"

"So it does. 78's."

Dick thought back for a moment.

"And there was I", he said remorsefully, "getting really worked up about it. What a mug!"

"Not to worry," chuckled Smithy. "That makes two of us today."

#### Smithy's Problem


A thought crossed Smithy's mind.

"Before I leave", he said, "I've just remembered that I've got one of my little problems for you. This time, it's a dead easy one too."

"I'll take your word for it," said Dick

cautiously. "Let's hear it."

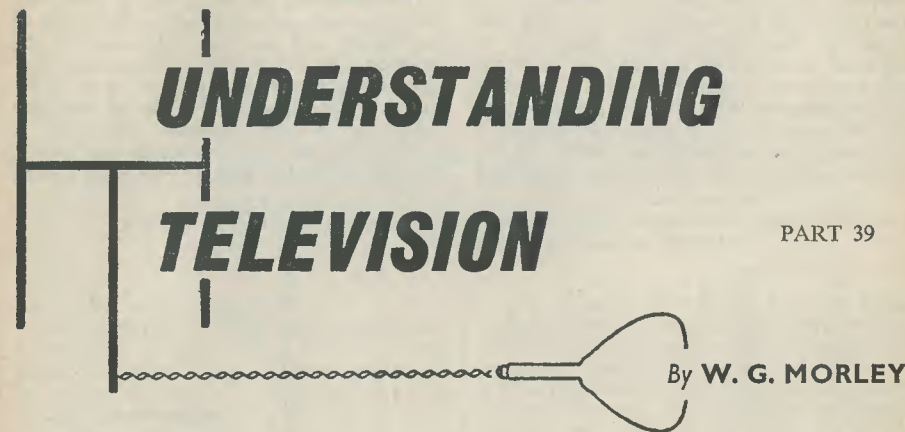"The problem goes like this," replied Smithy. "Between two terminals A and B you have six  $1\Omega$  resistors arranged in a triangular pattern with interconnecting wires. (Fig. 7.) What's the resistance between terminals A and B?"



The thirty-ninth in a series of articles which, starting from first principles, describes the basic theory and practice of television

IN LAST MONTH'S ARTICLE WE COMPLETED our discussion of power supply circuits. We shall now carry on to the last subject to be dealt with in this series: television receiver aerials.

#### The Television Receiver Aerial—the Dipole

The function of a receiver aerial is to pick up the signal radiated by the transmitter and cause it to be applied to the input terminals of the receiver. At the transmission frequencies encountered in television, it is readily possible for the receiver aerial to be given dimensions which allow it to be *tuned* to the frequency being received, thereby ensuring that a relatively high level of pick-up, at the desired frequency, is achieved.

Fig. 233 (a) illustrates a conductor whose length is approximately half that of a wavelength of the transmitted signal. The Greek letter  $\lambda$  (lambda) used in this diagram is that commonly employed to represent wavelength. When placed in the field of the transmitted signal the half-wavelength conductor exhibits the current and voltage distribution illustrated in the diagram. It

"Well, that shouldn't take long," said Dick, seizing paper and pencil. "I'm going to start on it right away."

"Oh no you're not," replied Smithy. "You've still got that set to clear up yet. I'll give you the answer next time we meet. And don't forget, this one's a piece of cake!"

circuit to present this impedance to the conductor if correct matching was to be achieved.

Fig. 233 (b) illustrates a working arrangement for picking up the signal to which the half-wavelength conductor is tuned, and we may now refer to the conductor as an aerial. An aerial of this type is known as a *dipole*, and it forms the basic element of a large number of television aerial designs.

In order that the manner in which a dipole becomes tuned can be more readily understood, it may prove helpful to consider it in the light of its own self-inductance and self-capacity. The dipole could, therefore, be depicted as shown in Fig. 233 (c), in which the conductor is represented by a series of coils representing its own self-inductance, and the self-capacity by a series of condensers between points on opposite sides of the centre. Fig. 233 (c) provides a simplified

picture of the self-inductance and self-capacity. Actually, the number of "coils" and "condensers" is infinite.

Fig. 233 (b) illustrates the dipole connected directly to the receiver input terminals. In practice the receiver has to be positioned some distance away from the dipole, whereupon it becomes necessary to provide a means of coupling the two together which will not upset the impedance matching between them. The coupling is provided by a two-conductor *feeder* having a *characteristic impedance* equal to that at the centre of the dipole and the input terminals of the receiver. See Fig. 233 (d). Under these conditions the feeder presents the same impedance to the dipole as is given by the input terminals of the receiver. Similarly, it presents the same impedance to the receiver as is given by the dipole. We shall discuss

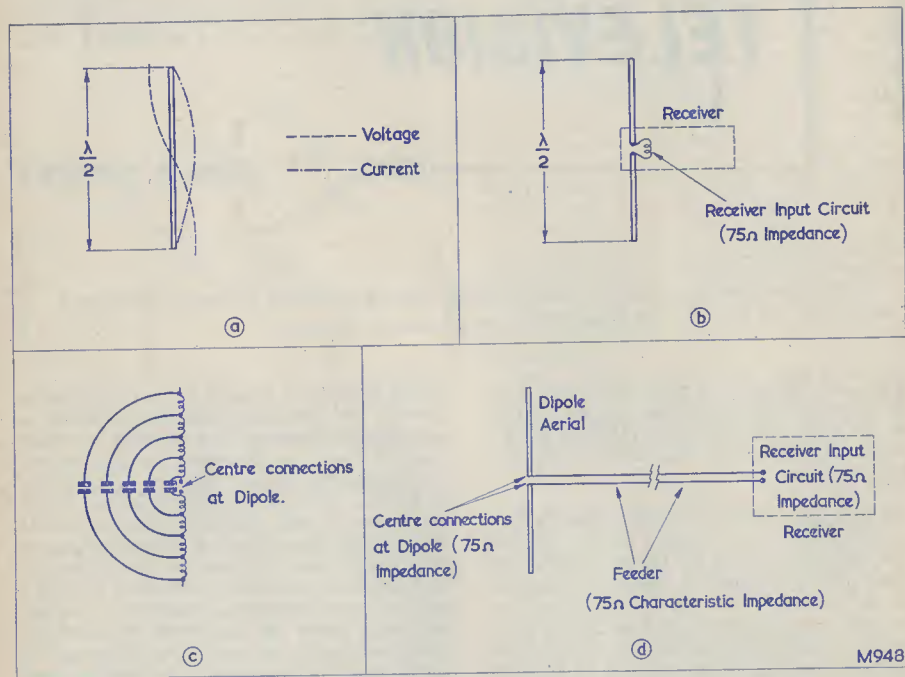


Fig. 233. (a) If a conductor in the field from a transmitter has a length approximately equal to half a wavelength of the transmitted signal the voltage and current distribution shown here is built up  
 (b) When the half wavelength conductor is broken at the centre it forms a dipole aerial. It is shown here connected directly to the input circuit of the receiver (depicted as a coupling coil)  
 (c) The dipole becomes tuned by reason of its own self-inductance and self-capacity  
 (d) It is normally impracticable to couple a dipole aerial direct to a receiver, as was illustrated in (b). The two are coupled together, therefore, by a two-conductor feeder having a characteristic impedance equal to that at the centre connections of the dipole and at the input circuit of the receiver

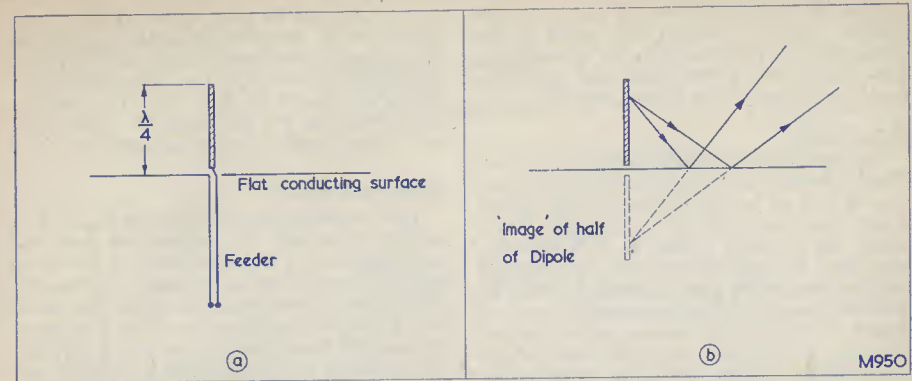


Fig. 234. (a) An aerial employing a quarter wavelength conductor mounted above a flat conducting surface. The feeder wire connecting to the conductor may conveniently be taken through a hole in the conducting surface  
 (b) Due to the reflecting properties of the flat conducting surface, an "image" of a dipole member is formed below it in the manner shown here

the feeder in more detail later.

The length of a dipole used at television frequencies is equal to a half-wavelength multiplied by a factor  $k$ . Since wavelength in metres multiplied by frequency in Mc/s equals 300, the dipole length may be conveniently expressed as follows:

$$\text{length (in metres)} = \frac{1}{2} \times \frac{300 \times k}{\text{Freq. (Mc/s)}}$$

Simplifying, and converting to inches (by multiplying metres by 39.37), this becomes:

$$\text{length (in inches)} = \frac{5906 \times k}{\text{Freq. (Mc/s)}}$$

The factor  $k$  varies according to the ratio between a half-wavelength and conductor thickness. It is always less than unity, and for most television receiving applications can be taken as being 0.94 to 0.95. The fact that the dipole is always shorter than an actual half-wavelength is due to "end-effect", this being an additional capacitive loading appearing at the ends of the dipole members.

The bandwidth of the dipole increases with the diameter of its conductors. Bandwidth may be expressed in terms of the frequency variation on either side of centre frequency which causes the signal voltage passed to the receiver to drop by 3dB. A television signal occupies a wide band of frequencies and the bandwidth of the aerial has, in consequence, to be sufficiently great to ensure that all frequencies in the signal are passed to the receiver without undue attenuation. To obtain the relatively wide bandwidth required, television dipoles usually employ metal tubing having diameters of the order of half an inch.

It is possible to dispense with the lower half of a dipole by mounting the upper section immediately above a flat conducting surface, as in Fig. 234 (a). The surface functions as a reflecting medium (not to be confused with reflector elements, which will be considered shortly) and "reflects" the upper half of the dipole, as shown in Fig. 234 (b). With this arrangement, the feeder connects to the lower end of the upper dipole section and to a point on the conducting surface immediately below, the impedance between these two points being roughly half that given by a dipole. This type of aerial is known as a *quarter-wave aerial* and it finds occasional application for television reception. It should be pointed out that the flat conducting surface need not be continuous; it may consist of wire mesh or of a number of metal rods radiating out from the centre. Normally, the feeder wire connecting to the conducting surface would connect to earth, or chassis, at the receiver end.

Since a tuned aerial designed to pick up signals at a particular frequency or band of frequencies offers the same characteristics when it is required to *transmit* such frequencies,<sup>1</sup> terms normally encountered in transmitting theory are frequently encountered when receiving aeriels are referred to. As we shall see, shortly, the simple dipole we have just referred to may have other tuned conductors placed close to it to modify its performance. In this instance the dipole may be referred to as the *driven element*, because it is the element to which the transmitter

<sup>1</sup> Providing, of course, that its conductors can carry the heavier currents which flow, and its insulation can stand up to the higher voltages.



output is applied and which is, in consequence, "driven". Again, the feeder to the dipole may be referred to as the *transmission line*, since it is via the feeder that the transmitter connects to the driven element.

### Polarisation

If a television transmitter employs a vertical dipole transmitting aerial the signal it transmits is said to be *vertically polarised*. If the transmitter employs a horizontal dipole aerial the signal it transmits is *horizontally polarised*. To receive a vertically polarised signal the receiving dipole should similarly be mounted vertically. A horizontally mounted dipole is required for horizontally polarised signals. In Britain, television signals are vertically polarised<sup>2</sup> whilst, in other countries, such as the U.S.A., horizontal polarisation is employed.

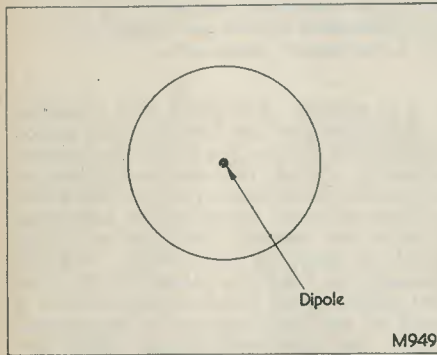


Fig. 235. The horizontal polar diagram of a vertical dipole is a circle, because the aerial has equal sensitivity in all directions in the horizontal plane

Unless otherwise stated, all the aerials discussed here are shown in the appropriate diagrams as being vertically polarised.

### Polar Diagrams

A polar diagram is employed to illustrate the efficiency of an aerial in a given plane. It consists of a circular chart on which is drawn a graph indicating signal strength at all points around the aerial, assuming that a transmitter of constant output is connected to it. (Conversely, the graph indicates the transmitted signal strength required at all points round the aerial to cause a constant signal strength to appear in a receiver connected to it.) The zero point for the graph is at the centre of the chart.

<sup>2</sup> With the exception of a few transmitters which radiate horizontally polarised signals.

We have, up to now, considered a single dipole aerial mounted vertically. Its polar diagram in a horizontal plane taken through the centre of the dipole would consist of a circle, as shown in Fig. 235, because the aerial receives (or transmits) at equal level in all directions in the horizontal plane.

### Adding a Reflector

The omnidirectional performance of a simple dipole may be considerably modified by positioning a reflector close to it. In its simplest application, a reflector consists of a conductor having approximately the same length as the dipole and mounted a quarter-wavelength away from it, as in Fig. 236 (a). The reflector is a continuous conductor and is not broken at the centre, as is the dipole.

Fig. 236 (b) shows the effect given by the dipole and reflector combination when the transmitter is on the opposite side of the dipole to the reflector. The signal from the transmitter causes currents to appear in both the dipole and the reflector. Since the reflector is a quarter-wavelength behind the dipole, it receives its signal one quarter of a cycle later. In consequence, the signal current in the reflector lags 90° behind that in the dipole. Due to the currents flowing in it the reflector re-radiates a signal which is 180° out of phase with that it receives from the transmitter. This re-radiated signal is picked up, after a further delay of a quarter of a cycle due to the quarter-wavelength spacing, by the dipole. The overall effect is as follows: the signal current in the reflector is firstly 90° behind that in the dipole, the re-radiated signal is 180° out of phase with that from the transmitter, and a further 90° delay takes place before the re-radiated signal is picked up by the dipole. The signal picked up by the dipole via the reflector has, therefore, been shifted through 360°; with the result that it is in phase with that picked up directly from the transmitter, and augments it.

If, as in Fig. 236 (c), the transmitter is on the same side of the dipole as the reflector a different effect takes place. To commence with, the signal current in the dipole is now 90° behind that in the reflector. As before, the reflector re-radiates a signal that is 180° out of phase with that it picks up from the transmitter. When this re-radiated signal arrives at the dipole it, also, is 90° behind that at the reflector and is, in consequence, 180° out of phase with that from the transmitter. Instead of augmenting the transmitter signal picked up by the dipole, the re-radiated signal now causes it to be diminished.

A typical horizontal polar diagram for a vertical dipole fitted with a reflector is shown in Fig. 237 (a). It will be noted that this differs considerably from that of the dipole


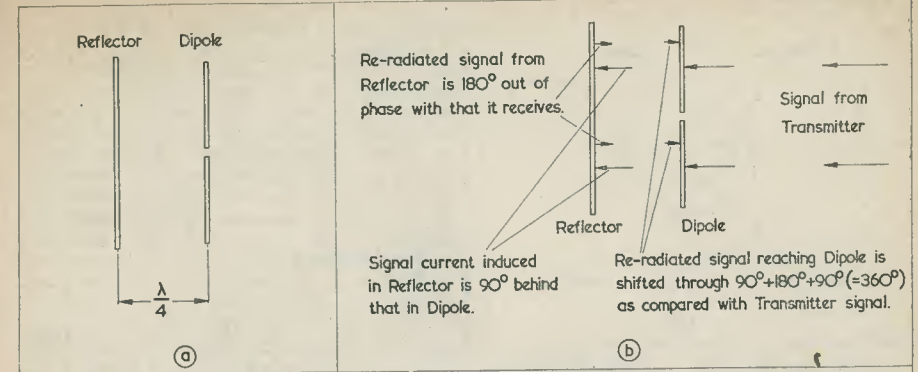


Fig. 236. (a) A simple reflector and dipole combination. The reflector is mounted in the same plane as the dipole and is a quarter wavelength behind it (b) When the transmitter is on the dipole side of the combination, the reflector augments signal strength in the dipole (c) When the transmitter is on the reflector side of the combination, signal strength in the dipole is diminished

on its own which was given in Fig. 235. Along the line OA—on the side opposite to the reflector—the curve indicates maximum sensitivity. Along the line OD—on the same side of the dipole as the reflector—the curve indicates minimum sensitivity. It should be noted, also, that the sensitivity along line OA is greater than that at any point around the single dipole because of the signal-augmenting effect of the reflector.

Two important advantages are provided by the reflector. The first of these is that sensitivity in the desired direction (along line OA in Fig. 237 (a)) is increased. The second is that sensitivity to signals from the reflector side of the dipole is considerably reduced. The aerial becomes directional in consequence. It will be seen from the polar diagram of Fig. 237 (a) that the angle over which minimum sensitivity is given is much sharper than that over which maximum sensitivity occurs. In areas where interference from a particular well-defined direction is troublesome, it is often possible to position the dipole and reflector combination such that the reflector is interposed between the dipole and the source of interference, as in Fig. 237 (b). In Fig. 237 (b) the dipole and reflector combination is not directed at the desired transmitter, but the signal strength picked up by the dipole is only slightly lower than that which would be given if it were so directed. At the same time, the signal from

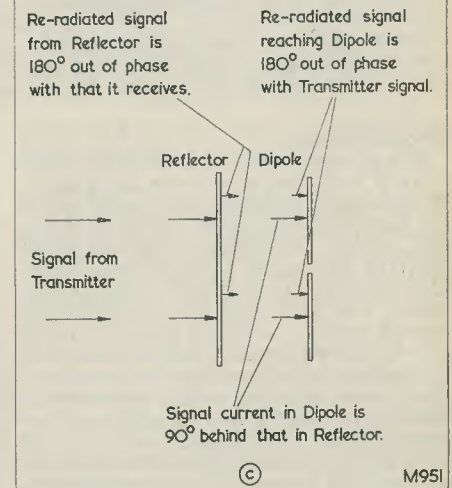

the interfering source is reduced to a minimum. In consequence, the highest signal-interference ratio which can be given by the dipole and reflector combination is achieved.

It is common practice to refer to the *front-to-back ratio* of a directional aerial. In Fig. 237 (a) this ratio would be expressed by the ratio between sensitivity along the line OA and the sensitivity along line OD, and would be equal to OB:OC.

It is conventional practice to make the reflector longer than the dipole, and the detuning which results causes a complex phase relationship between the reflector and dipole to come into effect over the frequencies for which the aerial is designed. This relationship enables the reflector to be positioned closer to the dipole than the quarter-wavelength illustrated in the simple examples of Fig. 236. In practical assemblies, the reflector may be as close as one-tenth of a wavelength away from the dipole.

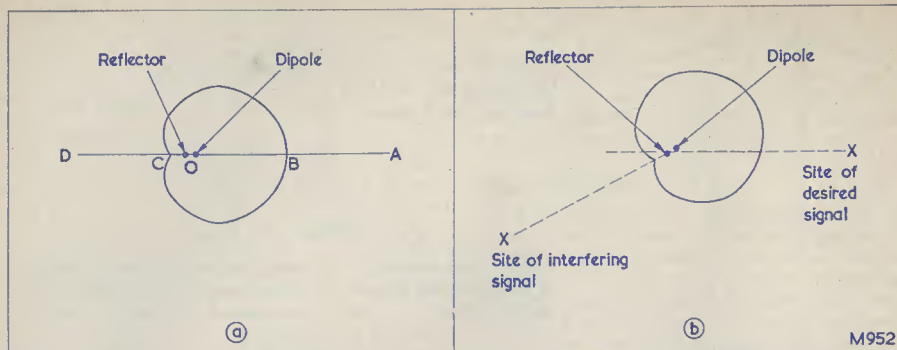


Fig. 237. (a) A typical horizontal polar diagram for a vertical dipole fitted with a reflector  
(b) When the direction from which an interfering signal appears is well defined it is sometimes possible to rotate a dipole and reflector combination such that the reflector is interposed between the interfering signal and the dipole

#### Adding a Director

It is possible to further increase the sensitivity of a dipole and reflector combination by adding one or more tuned conductors on the transmitter side of the dipole, as in Fig. 238. Unlike the reflector, which is longer than the dipole, the directors are shorter. The directors may be spaced away from the dipole, and from each other, by distances varying between one-tenth and one-quarter of a wavelength, a spacing of approximately 0.15 wavelength being fairly representative of common practice. Adding a director or directors to a dipole and reflector combination causes the polar diagram of Fig. 237 (a) to be modified to the typical example shown in Fig. 239. As may be seen, sensitivity in the desired direction is increased as, also, is the front-to-back ratio.

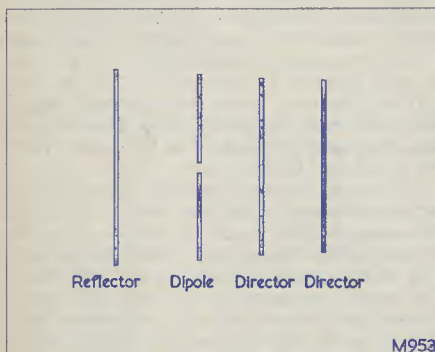


Fig. 238. One or more directors, which are shorter than the dipole, may be added on the opposite side to the reflector

#### Parasitic Elements—Impedance and Bandwidth

Because reflectors and directors are not directly connected to the receiver input feeder but modify, instead, the performance of the dipole, they are referred to as *parasitic elements*.

When parasitic elements are added to a dipole they cause the impedance at its two terminals to become reduced. A dipole fitted with a reflector can exhibit an impedance which may be as low as a half of that it would give on its own. If a director is added the impedance can be halved again. This effect is important, because it is desirable for television receiver aerials to match into standard feeder and receiver input impedances. In Britain the standard feeder and receiver input impedance is  $75\Omega$ , this enabling a good match to be made to a single dipole without parasitic elements. With careful design an adequate match to  $75\Omega$  feeder is still possible if a single parasitic element (either a reflector or a director) is added. If further parasitic elements are added to the dipole an accurate match to  $75\Omega$  feeder is difficult to achieve unless special matching arrangements are made at the dipole itself, or if the latter is changed to a folded dipole (shortly to be discussed).

The addition of parasitic elements also causes a reduction in bandwidth, and this factor necessitates especial care in aerial design for fringe areas wherein a relatively large number of directors, in addition to a reflector, may be required.

#### The Folded Dipole

Fig. 240 (a) illustrates a *folded dipole*. This, like the dipole we have already dis-

cussed, has an overall length which is equal to half a wavelength (less some 5 to 6% because of end effect). For television purposes the folded dipole has the advantage that the impedance at its terminals is four times that of a normal dipole. (Thus, the dipole of Fig. 240 (a) would exhibit an impedance of some  $300\Omega$ .) When a folded dipole is employed the impedance-lowering effect of parasitic elements can cause its relatively high impedance to drop such that a good match is provided to the standard British feeder and receiver input impedance of  $75\Omega$ . It is, in consequence, possible to add a relatively large number of parasitic elements to a folded dipole and still retain a good match to a  $75\Omega$  feeder.

The impedance of a folded dipole may be varied by employing a different thickness for the two conductors. If the unbroken conductor is thicker than the broken conductor (i.e. that to which the feeder connects) the impedance of the dipole increases. If the unbroken conductor is thinner than the broken conductor impedance decreases. When the two conductors have different thicknesses the impedance may be further altered by varying the distance between them. Increasing the distance between the conductors reduces the variation in impedance given by conductors of different thicknesses. Advantage may be taken of these points in the design of an aerial employing a large number of parasitic elements.

A *triple-folded dipole*, as shown in Fig. 240 (b), offers an impedance which is 9 times that of a normal dipole. This assumes that all conductor diameters are equal. Triple-folded dipoles are not normally employed in British television aerials, although they may have applications in countries where standard

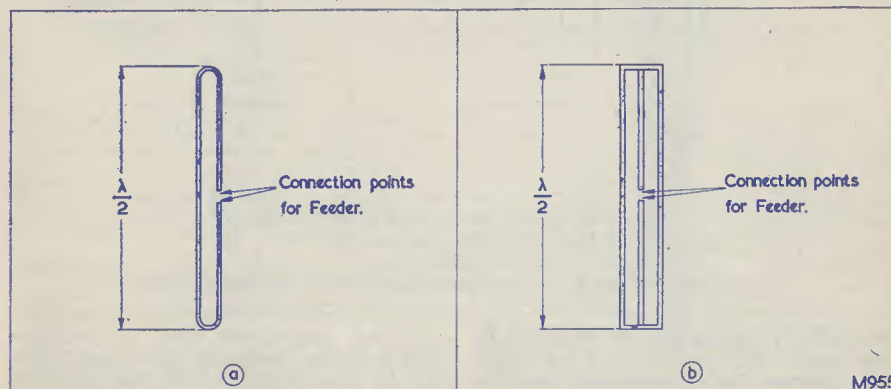


Fig. 240. (a) A folded dipole. This has an impedance four times that of a normal dipole  
(b) A triple-folded dipole offers an impedance nine times that of a normal dipole

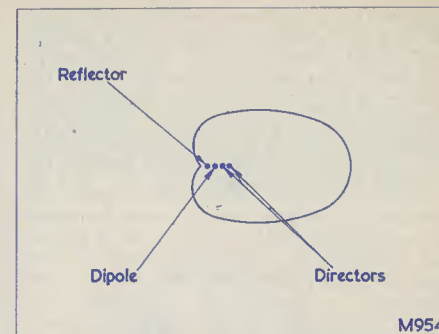


Fig. 239. Adding a director, or directors, to the dipole and reflector combination causes increased sensitivity in the desired direction, as is shown by this typical horizontal polar diagram

feeder and receiver input impedances are higher than  $75\Omega$ .

#### Aerial Gain

The performance of an aerial may be expressed in terms of *aerial gain*. This figure represents the increase in signal strength given by the aerial as compared with a normal dipole. The gain figure is a ratio and may be expressed in dB.

#### Practical "Outdoor" Aerials

Almost all "outdoor" television aerials employed in Britain are based on a dipole or folded dipole, with or without parasitic elements. In areas of good signal strength and low interference level a simple dipole is frequently all that is required for reception on Band I. Greater sensitivity on Band I is

provided by the use of an "H" aerial (Fig. 241 (a)), and this may consist of a normal dipole and reflector, both elements being mounted on a metal cross-arm. Since the voltage at the centre of the reflector is at a minimum (see the current and voltage distribution for a half-wavelength conductor in Fig. 233 (a)) there is no need to insulate the reflector from the metal cross-arm, and an

feeder unless special matching arrangements or a folded dipole are employed.

Band III aerials normally employ a folded dipole, a reflector and at least one director. (Fig. 241 (b).) The use of a folded dipole, with its initial high impedance, enables parasitic elements to be added far more readily than would be the case with a normal dipole. Once again a metal cross-arm is

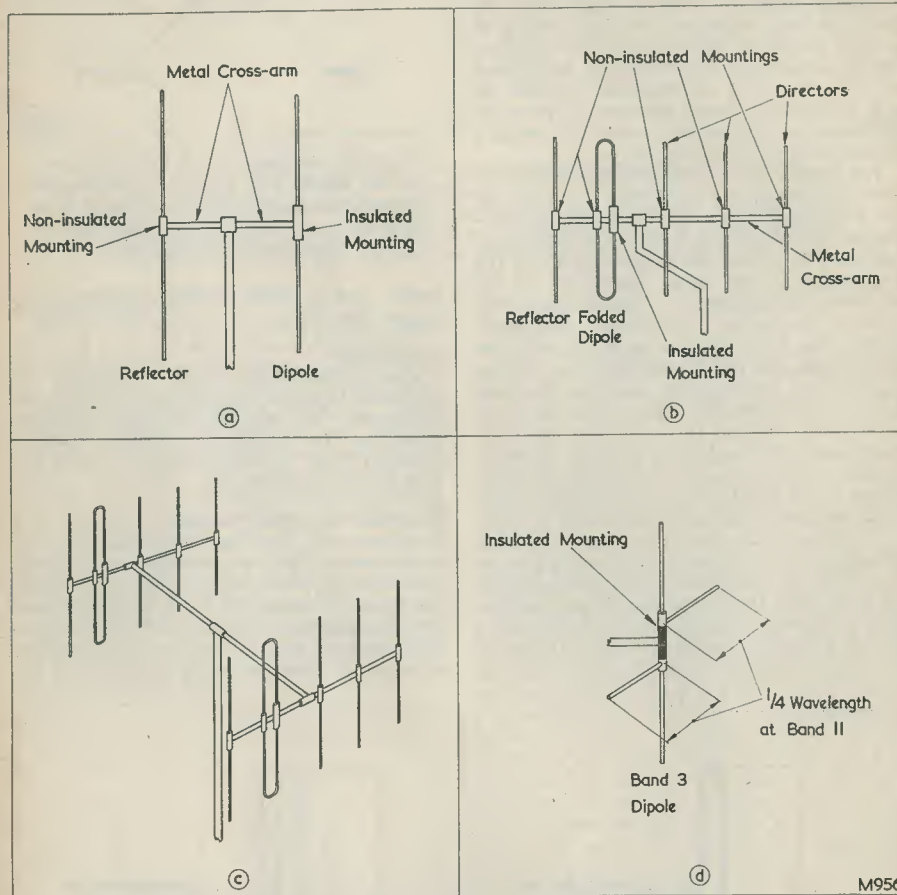


Fig. 241. (a) A typical Band I "H" aerial  
(b) A Band III aerial with three directors  
(c) A broadside array  
(d) A combined Band I vertical dipole and Band II horizontal dipole

inexpensive mounting can be employed in consequence. The inner ends of the dipole have, however, to be insulated from the cross-arm, so that the feeder connection is not short-circuited. It is possible to add a director in front of the simple "H" aerial, but this causes difficulties in matching to the

employed and, since there is minimum voltage at the centre of the reflector, the director (or directors) and the unbroken conductor of the folded dipole, none of these points needs to be insulated from the cross-arm. An insulated mounting is required only at the terminals of the folded dipole.

At Band III wavelengths element lengths are much shorter than at Band I, and it becomes possible to design aerials having a large number of parasitic elements which are still not excessively cumbersome or unwieldy.

Speaking in very general terms, reflectors in practical aerials are usually some 5 to 6% longer than the associated dipole. The director nearest to the dipole is usually some 4 to 5% shorter, further directors decreasing in length progressively. These figures are, however, very general: the design of a television aerial employing parasitic elements is a complex process in which the length, spacing and diameter of elements are all inter-related.

It is possible to employ two aerials, complete with parasitic elements, in a "broadside" array, as shown in Fig. 241 (c). The aerials are spaced by a half-wavelength and, for true "broadside" operation, the dipoles should be cross-connected such that the upper part of one dipole connects to the lower part of the other.

Sometimes, a means is provided for tilting a Band I or Band III aerial such that the directors are higher than the reflector. This allows optimum signal strength to be achieved when the incoming signal is down-ward-moving.

Combined Band I-Band III aerials are often employed, and designs vary considerably according to the manufacturer. A possible Band I-Band III aerial could employ a set of Band III elements with a Band I element at the rear, this functioning as a Band I dipole and as a Band III reflector. Alternatively, an "H" or "X" (to be dis-

cussed shortly) Band I aerial could appear after the Band III elements, the first Band I element—either a dipole or a director—functioning as a Band III reflector. Other combinations of Band I and Band III elements are feasible. An interesting combination of Band I and Band II aerials<sup>3</sup> is illustrated in Fig. 241 (d). In this diagram horizontal conductors are added at the centre of a conventional Band I dipole, causing a second horizontal dipole tuned to Band II to be effectively connected to the feeder. Such an arrangement can be used with combined television-f.m. receivers having a common aerial input circuit.

An alternative to the "H" aerial is the "X" aerial. In an aerial of this nature one-half of the "X" may consist of a dipole, and the other half of directors. Another variant is the "K" aerial, in which the vertical element may be the dipole and the two inclined members directors. "X" and "K" aerials are employed for Band I reception and offer an alternative to the conventional "H" aerial. Apart from any technical advantages such aerials may have over the "H" aerial, they have the mechanical advantage of deleting the cross-arm, thereby providing a lighter assembly.

#### Next Month

In next month's article we shall continue with our discussion of television aerials, carrying on to "indoor" aerials, and to feeders.

<sup>3</sup> Band II is employed for f.m. sound transmissions, and employs horizontal polarisation.

## CAN ANYONE HELP?

Requests for information are inserted in this feature free of charge, subject to space being available. Users of this service undertake to acknowledge all letters, etc., received and to reimburse all reasonable expenses incurred by correspondents. Circuits, manuals, service sheets, etc., lent by readers must be returned in good condition within a reasonable period of time

Jason F.M. Tuner.—E. Gale, 18 Tennal Grove, Birmingham 32, wishes to obtain details of modifications necessary to coils L<sub>1</sub>, L<sub>2</sub> and L<sub>3</sub> of the fringe area model in order to cover the frequencies 115 to 130 Mc/s.

Hammarlund Super-Pro Receiver.—G. Preston, 31D Hill Road, Arborfield, Reading, Berks, requires a copy of the circuit or the manual.

McMurdo Silver "15-17" (1938/9).—L. A. Brown, 23 Oxford Avenue, Cleethorpes, Lincs, urgently requires the manual or alignment details and any relevant information.

MCRI Receiver.—C. Robinson, 15 Lindley Street, Blackburn, Lancs, would like to obtain the circuit or manual of this receiver. Failing these, details of the valve line-up would be of great assistance.

Eddystone 358X Receiver.—P. G. Bell, 27 Churchill Avenue, Horsham, Sussex, would like to obtain circuitry of modifications to this receiver.

Communication Receiver Design.—J. Langford, 20 Eastlake Avenue, Parkstone, Dorset, would like to hire any copy of *The Short Wave Magazine* (since 1958) which has featured details of a home-constructed communications receiver.

Transistor Portable Receiver.—James M. Buchanan, Morningside Road, Annan, Dumfriesshire, is considering the purchase of such a receiver, in kit form, and would be pleased to receive from readers any information on the sensitivity of such sets. The receiver would be required for use in the western Highlands of Scotland where signal strengths are very low.

420 Mc/s Articles.—G. Allcock, G3QVO, South End, Beck Hill, Tealby, Lincoln, requires the texts and circuits of the 420 Mc/s articles published in *QST*, May 1951, page 39, and June 1948, page 52.

R1471 Receiver.—I. G. Morgan, 21 Pontey Mount, Waterloo, Huddersfield, Yorks, wishes to obtain the circuit diagram, servicing data and details of any modifications readers may have made in order to improve performance.

# Designing a High Impedance Transistorised Voltmeter

By S. SMITH

IDEALLY, A VOLTMETER SHOULD HAVE infinite impedance, so that it does not disturb the circuit being measured. This ideal is unattainable, but the high input impedance of thermionic valves (particularly "electrometer" valves) allows valve voltmeters to be designed with such high impedances that the resulting disturbance to the measured circuit is quite negligible.

Valves require a substantial power supply and are not very rugged, therefore a valve voltmeter is rather more delicate and inconvenient than one would like, as well as being too bulky and heavy to slip into the pocket for an outside servicing job.

Transistors are rugged, very small, and lend themselves very well to subminiature portable equipment, using small torch batteries as their power supply; but they have a low input impedance (1 to 2kΩ, compared with 1 to 10 MΩ for valves). In the circuit that follows, two transistors are given a very high input impedance by using 100% negative feedback, their very low output impedance under these conditions being used to drive a cheap meter (1mA full scale deflection, resistance 100Ω). Transistorised voltmeters have been described previously, but they usually require four transistors and a 100mA meter, this adding up to quite an expensive instrument.

## Obtaining a High Input Impedance

100% negative feedback (by putting the load in the emitter circuit) gives a high input impedance, and a low output impedance, in the following manner.

In Fig. 2,  $v_b$  (voltage at the base) is approximately equal to  $v_e$  (voltage at the emitter) by "emitter follower" action: i.e., if the emitter voltage goes down (or up) there is a heavy increase (or decrease) in collector current, and hence current through

"R", which restores the emitter voltage to its original value.

Since  $v_e = v_b$  approximately  
 $i_c = \alpha'' i_b$  (where  $\alpha''$  is the transistors' grounded collector current amplification factor) and  $v_e = R i_c$

Then change in  $v_b =$  change in  $v_e = R \times$   
change in  $i_c =$   
 $R \times \alpha'' \times$  change in  $i_b$   
change in  $v_b$   
i.e.  $\frac{\text{change in } v_b}{\text{change in } i_b}$  (= input resistance)  
 $= R \times \alpha''$

Thus the input resistance is  $\alpha''$  times the emitter load.

If this transistor is the emitter load of another transistor, the input resistance of whole assembly will be  $\alpha'' \times \alpha'' \times$  emitter load. In this way, vary large input impedances can be built up, because  $\alpha''$  is of the order of 20 to 100 (40 is a common value), and each additional transistor multiplies the input impedance by this factor.

The output impedance is low, because change in  $i_c = g_m \times$  change in  $v_b$  (using  $g_m$  in the "mutual conductance" concept already familiar from valve practice)  
 $= g_m \times$  change in  $v_e$  (by "emitter follower" action)

change in  $v_e$   
Thus  $\frac{\text{change in } v_e}{\text{change in } i_c}$  (= output impedance)  
 $= \frac{1}{g_m}$   
25Ω would be a common value.

## Adding a Second Transistor

In Fig. 3, the emitter load is two resistances in parallel, one of 100Ω (the meter), and one of 10kΩ: the net load is thus 100Ω, the 10kΩ is 100 times larger and could take only 1% of the available current. If we arrange matters as shown, with a base voltage of about 4.5V, and a 4.5V battery opposing the current through the meter, no current will flow through the meter. Any change in base voltage, however, will cause current to flow through the meter, with its 100Ω resistance, rather than the 10kΩ resistance. The input impedance of this arrangement is  $\alpha'' \times 100\Omega$ , i.e., about 4kΩ. This is not enough: we therefore use the circuit of Fig. 3 as the emitter load of another transistor, and obtain the circuit of Fig. 4.

The base of the second transistor (TR<sub>1</sub> in Fig. 4) is not connected into circuit, so the transistor passes its normal "leakage current", which is usually between 50 and 200μA. This current has to produce about 4.5V across the emitter load "r" to satisfy the second transistor. Thus, "r" is in the

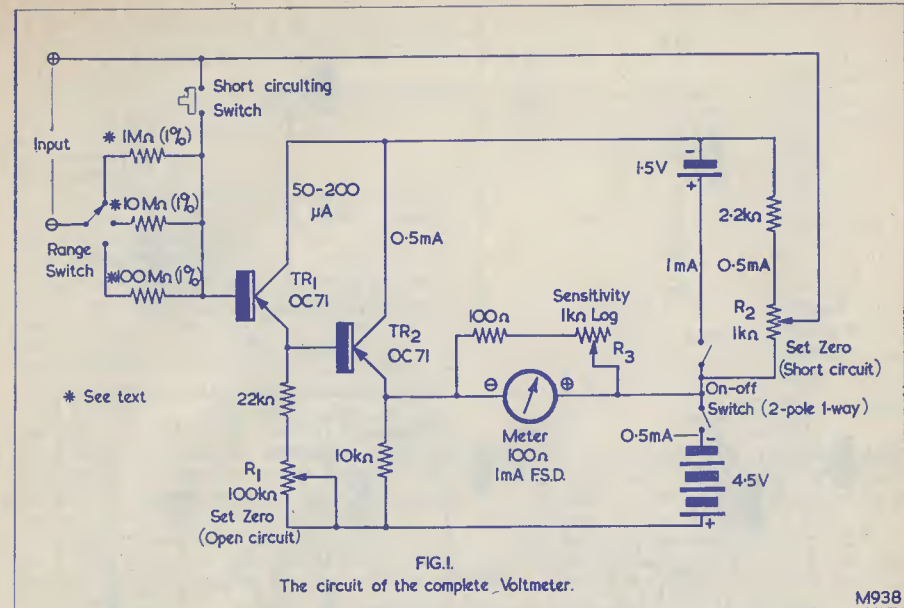


FIG.1  
The circuit of the complete Voltmeter.

M938

range 90kΩ to 22kΩ. We therefore make "r" 22kΩ+100kΩ variable in series. We have seen that the input resistance of the circuit of Fig. 3 is about 4kΩ, so connecting 22-90kΩ across it in parallel does not affect it a great deal. The input resistance of the whole circuit of Fig. 4 is now  $\alpha'' \times 4k\Omega$ . At low collector currents, like 50-200μA,  $\alpha''$  is lower than usual; 25 is fairly typical. So the nett input resistance is  $25 \times 4k\Omega = 100k\Omega$  approximately.

100mV across a 1mA meter of resistance 100Ω gives full scale deflection. So 100mV input to the circuit in Fig. 4 gives full scale deflection. We have, then, 100mV input into a resistance of 100kΩ, i.e., 1 megohm per volt input, which is of the same order as that of a valve voltmeter.


The base of the input transistor, TR<sub>1</sub>, is at 4.5V, plus a hundred millivolts or so, necessary to cause the second transistor to pass about 0.5mA and thereby cause the meter to give a zero reading. The input is therefore connected to the base of TR<sub>1</sub> and to a point in the circuit that is at an equal voltage; this giving rise to the arrangement shown in Fig. 5. Here we have added a 1.5V cell, to give a working potential of 1.5V between the collector and emitter of each transistor; and we use the same cell as the source of the 100-300mV above the emitter potential required to bring the other side of the input up to the potential of the base of TR<sub>1</sub>. The resistances employed must not be of the same order as the circuit's

input resistance or sensitivity to low voltages will suffer, so a value of 1kΩ (=1% of the input resistance) was chosen.
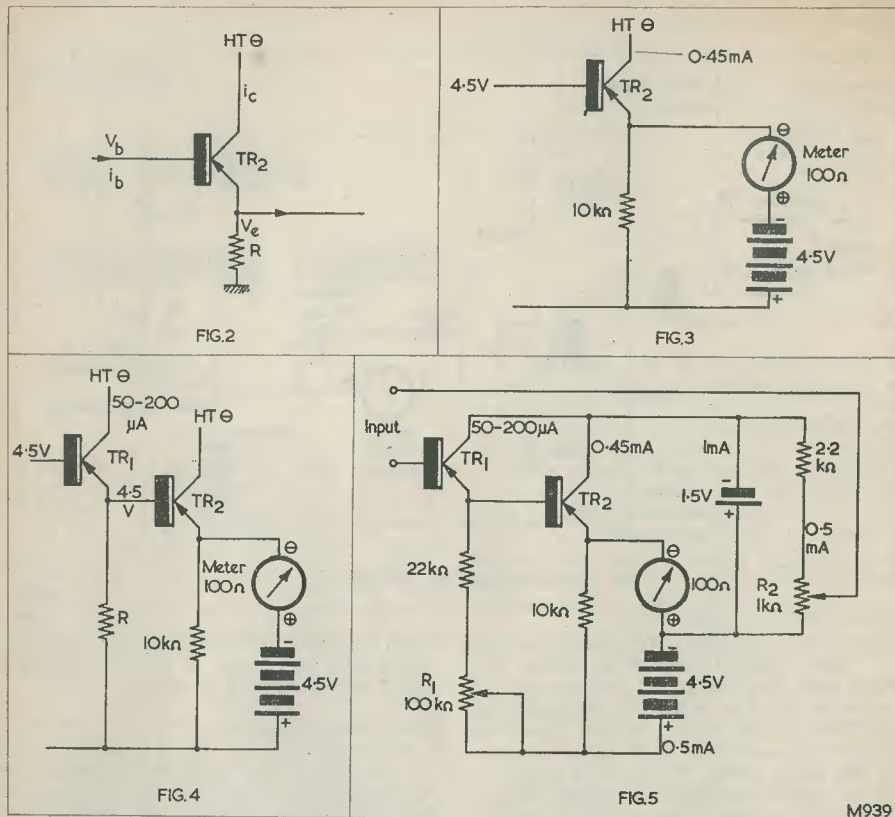
## The Complete Instrument

It is likely that the circuit parameters will be such that full scale deflection occurs at an input voltage that is not a round number: indeed it would be a sheer fluke if it were, say, exactly 100mV or exactly 200mV. For this reason, we must put a variable resistor in parallel with the meter to decrease the sensitivity of the circuit to a satisfactory round number. If the parallel resistance were the same as the meter's resistance, it could cause sensitivity to be reduced by as much as a half, if necessary. Thus if, say, the sensitivity were 143mV for full scale deflection, operation of the variable resistor could change it to 150mV, or 200mV, or 250mV, as required. In Fig. 1, which shows the circuit of the complete voltmeter, the variable resistor appears as R<sub>3</sub>, the 100Ω fixed resistor being included to restrict its range.

In Fig. 1 high-value resistors have been added in series with the input to change the range of the instrument: values of 1MΩ to 100MΩ are shown. These are nominal values, based on an input resistance of 100kΩ. In a practical instrument, the input resistance can differ from 100kΩ quite appreciably; it varies, for example, with the setting of the sensitivity control, R<sub>3</sub>. The correct values of the high-value



resistances are found by experiment in the following manner.

When the instrument has been set up, as detailed below, a source of known voltage equal to a volt or less is applied between the positive input terminal and the base of TR<sub>1</sub> via a 1MΩ 1% resistor. The sensitivity control R<sub>3</sub> is then adjusted. If input sensitivity is of the order of 100mV or better, it should be possible to obtain a reading on the meter which corresponds to 1 volt full scale deflection. If sensitivity is worse than 100mV then R<sub>3</sub> should be adjusted so that full scale deflection corresponds to the next convenient round number, say, 1.5 or 2 volts. The full scale reading obtained at this stage will then be multiplied by 10 when a 10MΩ series resistor is employed and by 100 when a 100MΩ series resistor is employed. Thus, if initial experiments with the 1MΩ resistor result in an f.s.d. figure of 1.5 volts being chosen, the three ranges switched in by the range switch of Fig. 1 would be 0-1.5 volts, 0-15 volts and 0-150 volts. Values of series resistor other than those shown in Fig. 1 could, of course,

be employed to obtain different multiplying factors.

A simple method of obtaining the source of potential just mentioned would consist of connecting a potentiometer having a value between 2 and 10kΩ across a single 1.5 volt cell, as shown in Fig. 6. An external voltmeter is connected between the slider of the potentiometer and one end of the cell in order to monitor the potential tapped off. By careful adjustment of the potentiometer it should be possible to obtain a potential equal to a round number, thus simplifying the procedure of initially selecting the figure for f.s.d.

#### Setting Up

- (i) With the input terminals open-circuited, adjust R<sub>1</sub> until the meter reads zero. This adjusts the emitter potential of TR<sub>1</sub>, caused by the TR<sub>1</sub> leakage current, to the value required to bring TR<sub>2</sub> emitter potential exactly to the 4.5V battery's potential.
- (ii) With the input terminals short-circuited, adjust R<sub>2</sub> until the meter


reads zero again. This brings both of the input terminals to the same potential.

- (iii) Set the sensitivity control and choose the high-value series resistances as described above.
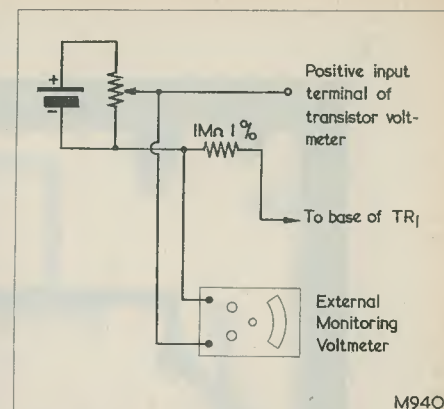
#### Operation

Use of the instrument is straightforward. It can be extended to a.c. measurements by using a diode probe in the usual way. For measuring very high voltage, it is recommended that a high resistance potentiometer be used to precede the instrument and reduce the voltage by a known factor, because very high value resistors tend to be unreliable. To measure, say, 1000V, a series resistor of 1000MΩ may be needed, and resistors of such high value are not reliable: it would be better to connect 100MΩ+10MΩ across the supply and to connect the instrument on its highest range across the 10MΩ resistor, thus measuring one eleventh of the input voltage.

Transistors are sensitive to heat, including the heat generated by their own power dissipation. So, unlike a valve voltmeter,



drift is a problem with this instrument. For greatest accuracy, R<sub>1</sub> and R<sub>2</sub> should be adjusted before every measurement as detailed in setting-up steps 1 and 2. It will be found in practice, however, that R<sub>1</sub> and R<sub>2</sub> rarely need adjustment more often than once at the beginning of each day.

## A Printed Circuit Transistor Pre-amplifier

by G. N. DALE

THE CONVENIENCE OF HAVING A CONTROL unit separated from the main amplifier is a well established principle in high fidelity audio work, although a certain number of composite pre-amp/amplifier units are commercially available in the middle price range. While thermionic


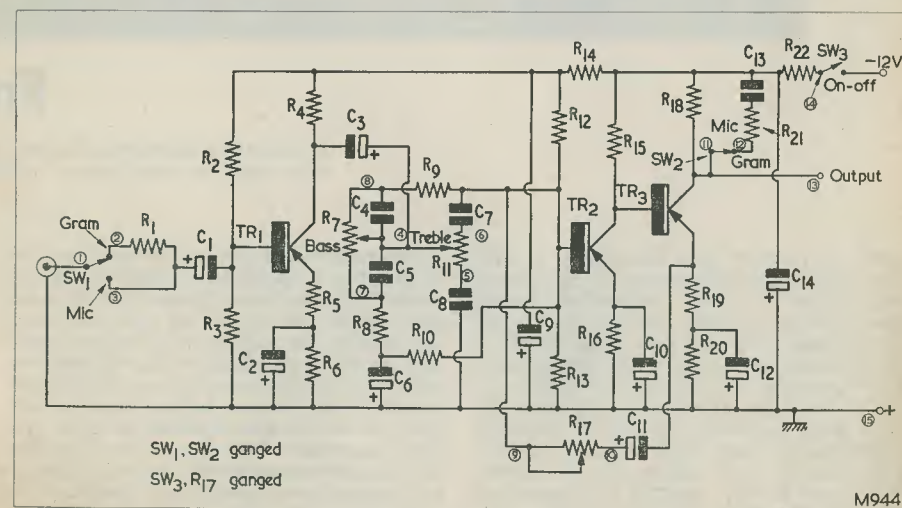


Fig. 1. The theoretical circuit of the pre-amplifier. The circled numbers correspond to the wired connections illustrated in Fig. 3.

Back

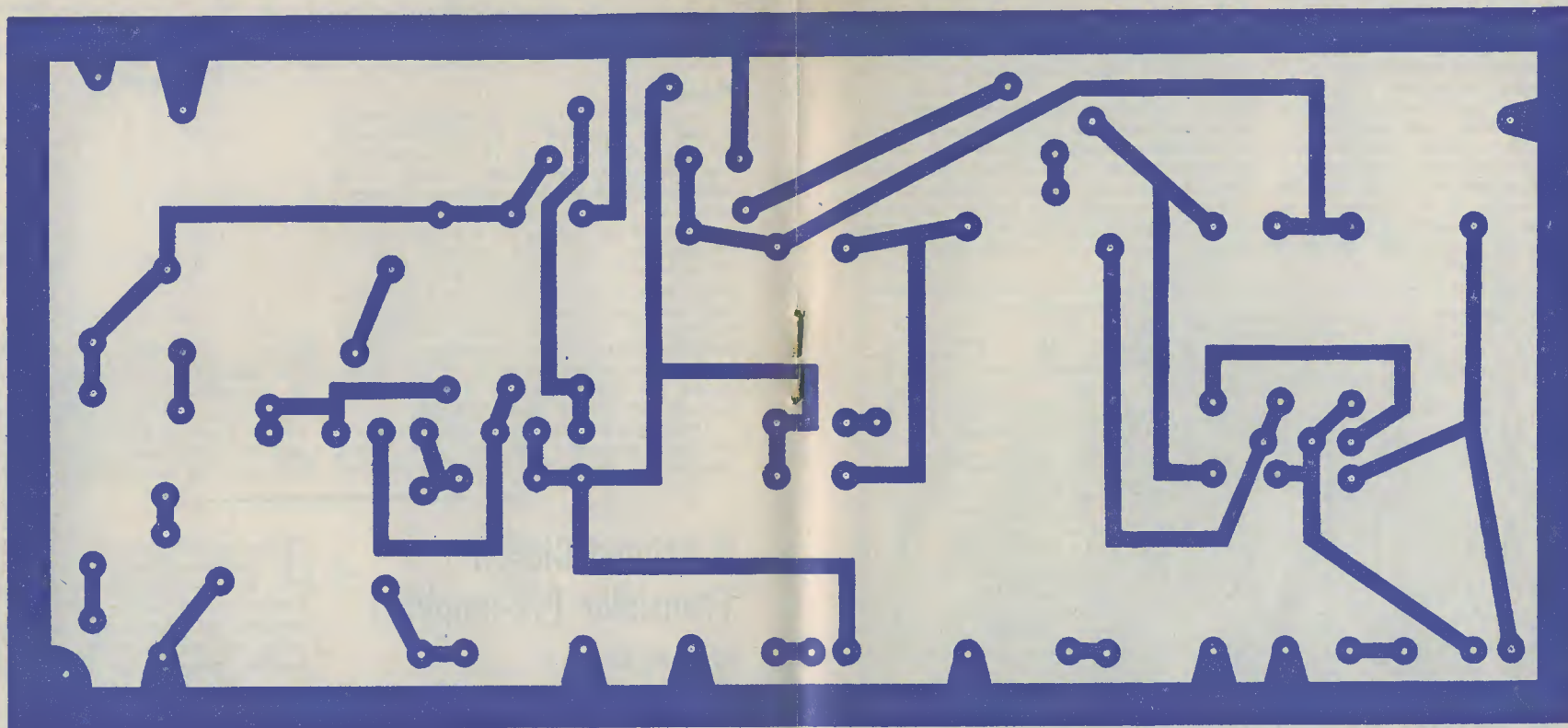

Front

Fig. 2. The printed circuit layout. This diagram has been reproduced here on a 1:1 basis and may therefore be traced direct. The copper side is uppermost

valves have been used exclusively in pre-amplifier design, the constructor has always been faced with the problem of finding the ideal layout and making the choice of components which kept noise levels to the absolute minimum. The arrangement and screening of connecting leads was critical and the high input impedance of valve grids called for the use of matching transformers when reproducing moving coil pickups and microphones, adding still more to the problem of screening. The need for high stability resistors for noise limiting added further to the expense of the unit.

Dismayed, no doubt by the poor quality of so many of the modern portable receivers, where transistors are operated too close to their limits, the enthusiast could at first be excused for saying that the transistor had no place in serious audio design. In a pre-amplifier, however, the source voltages are far from minute and a large overall gain is not always required to drive the main amplifier. This allows for a circuit in which transistors can be used at relatively low operating currents and feedback is employed to keep distortion to the absolute minimum.

The present design is based on a circuit

published some time ago in *Transistors for The Experimenter* (published by Mullard Ltd.). The low input impedance ( $5,000\Omega$ ) is one of its most useful features, making the unit very suitable for use in conjunction with moving-coil microphones or pickups, the maximum input voltage being only 30mV. The circuit is capable of a voltage gain of 220, and a current gain of 400, sufficient to drive a valve main amplifier. The tone controls should give more than 10dB of boost and cut at 50 c/s and 12 kc/s. At maximum gain 20dB of feedback is obtained, so that distortion is negligible.

All three transistors have a grounded

emitter circuit. Although in this configuration the maximum operating frequency is less than that for the grounded base arrangement, there is no effective limitation at audio levels and one has the advantage of a comparatively high current gain. This is very desirable in the first stage to allow for the attenuation which takes place in the tone control network ( $R_7$ ,  $R_{11}$ , etc.).

Full use is made of negative feedback in order to reduce distortion and improve the frequency response. As feedback which is applied over several stages may result in phase shift at upper frequencies, it is incorporated in the present design at two

points. The emitter resistor  $R_5$  is unbypassed producing some a.c. negative feedback, and the loop formed by  $R_{17}$ ,  $C_{11}$  applies voltage taken from the emitter resistance of  $TR_3$  to the base of  $TR_2$ .  $R_{17}$  being variable, the feedback is employed here to control gain over the second and third stages.

The circuit can be power or battery driven, although the latter is to be preferred so as to avoid hum and microphony, particularly as the current drain is only 4mA. An excellent source of voltage is a combination of a grid bias (9V) and flat pocket torch battery (4.5V) connected in series so that the tappings of the grid bias battery can be used to adjust for ageing.

$C_4$  and  $C_5$  are not included in the printed circuit but are mounted behind the potentiometer  $R_7$ . There is no significance in the fact that some of the 100 $\mu$ F condensers are shown physically larger than others. This results from the fact that available components were used wherever possible for the present unit. Values for  $R_1$ ,  $R_{21}$  and  $C_{13}$  will depend on the type of equipment being used with the pre-amplifier,  $R_1$  giving attenuation and the network  $R_{21}$ ,  $C_{13}$ , a constant treble cut required with some types of pickup. To make the unit more versatile a potentiometer may be substituted for  $R_1$ , connecting the ends to  $C_1$  and "earth" respectively and the slider to the

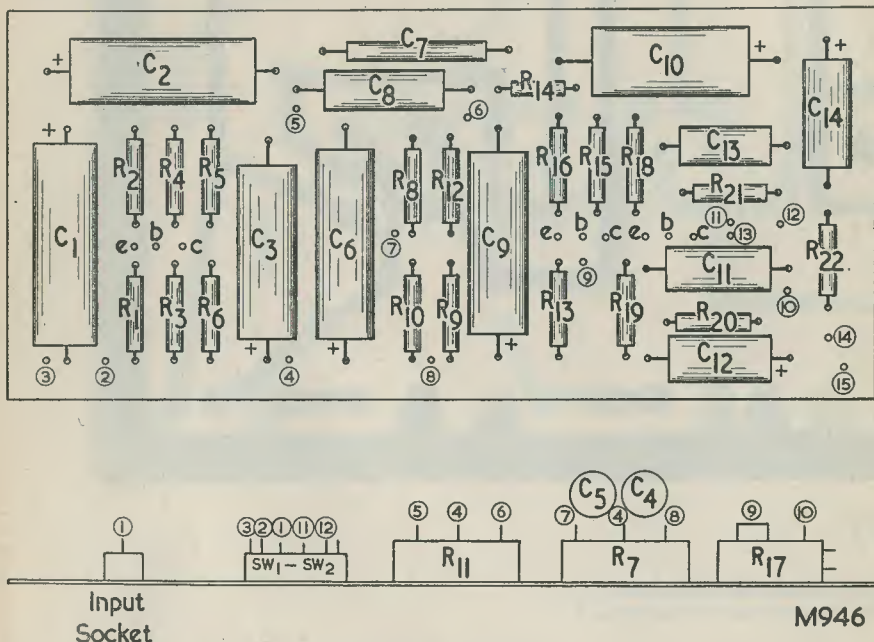


Fig. 3. Component layout as viewed from the top of the board. Wired connections are shown by pairs of circled numbers. On switches  $SW_1$ ,  $SW_2$ , contacts 2 and 12 are connected to their respective sliders in the "Gram" position. For clarity, the on/off switch of  $R_{17}$  is omitted. One contact of this switch should be taken to connection 14 and the other to the negative battery lead. Connection 13 is that of the output and connection 15 should be taken to the positive battery lead

No special printed circuit components are required in this design. Switches and potentiometers are conventional and wires are taken from these to appropriate connections on the printed circuit; this also results in a smaller board and more compact overall size. The wired connections are shown by the ringed numbers in Fig. 3.

input socket. A value of 100k $\Omega$  has been used successfully, but care should be exercised in using this as an impedance matching device, if distortion is to be kept to a minimum.<sup>1</sup>


<sup>1</sup> Recommended values for  $R_1$ ,  $R_{21}$  and  $C_{13}$ , for use with the Goldring Type 500 pick-up, are given in the components list.

The printed circuit may be made by any of the methods available to the home constructor. Fig. 2 is a "positive" of the circuit in which the black areas are conductors. Do not forget when comparing it with the top layout (Fig. 3) that the circuit as it appears here is the mirror image of the way it will look when viewed through the printed board.

Kits of materials for producing the etched circuit are available commercially, but the constructor who is beyond the stage of experimenting with this method and

paint (Belco is to be recommended); an aqueous solution of ferric chloride, about 20%; a flat dish or tray (porcelain, enamelled steel, or plastic) large enough to hold the largest board; an artist's small paint brush and a 1 or 2in paint brush.

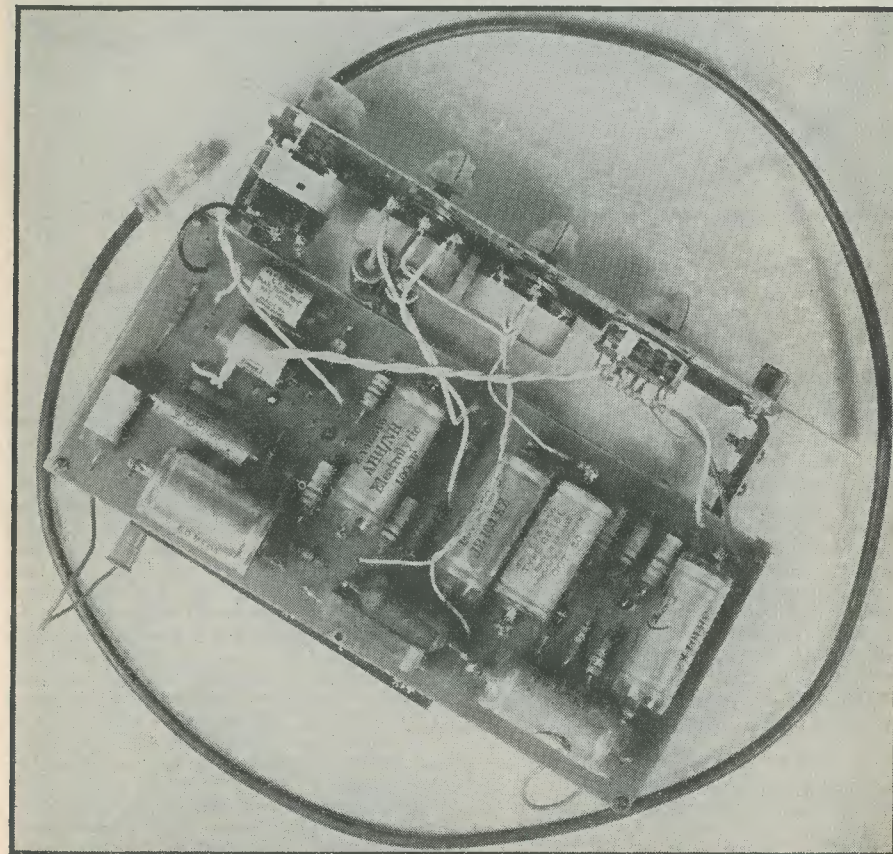
It is important to begin by thoroughly degreasing the copper surface so that good adhesion between it and the resist will result. The best method is to scrub with wire wool or a nylon dish cleaner and domestic scouring powder. After tracing the outlines of the circuit on to the copper,



Top view of the pre-amplifier showing the wiring between the printed board and the control panel components

plans to embark on a programme of several printed circuit units, will save money by obtaining the necessary items in quantity. The following will be required: Some copper-clad phenolic laminate; a suitable acid "resist" in the form of an oil or cellulose

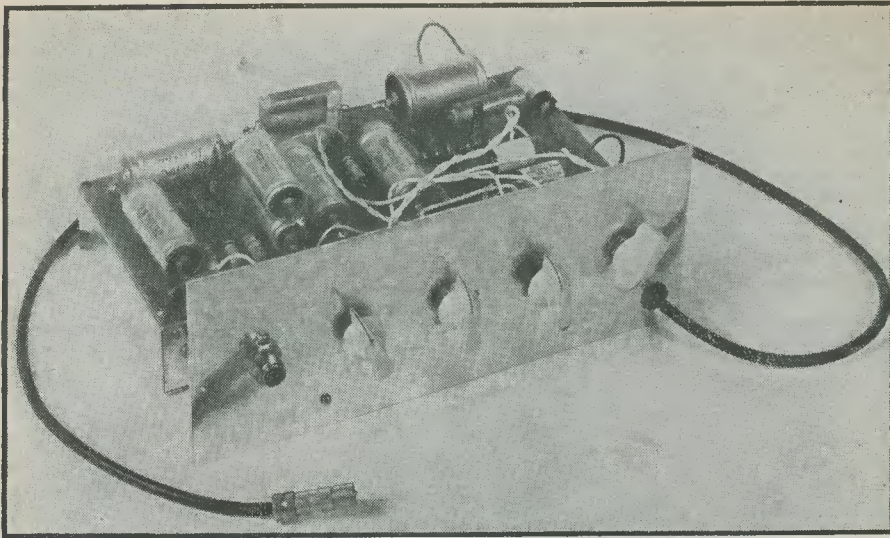the "conductors" are filled in by painting between the lines. When the resist is dry, the remaining copper is etched away in the ferric chloride solution. Etching progresses more rapidly if the solution is warm and may also be assisted by light brushing



Front view of the pre-amplifier. It will be noted that, in the prototype,  $C_3$  is made up of two condensers in parallel. In practice, a single component can be employed here


over the copper surface while immersed. The paint must then be removed with a suitable solvent from the conductors and the board thoroughly cleaned so that traces of paint do not prevent good soldered connections from being made.

The laminate usually has a tendency to warp, with the copper on the concave side. This is flattened again when screwed down to the chassis and is unlikely to result in any damage to the foil above. However, care should be taken to see that the board is held reasonably flat when soldering components to it, as subsequent forcible straightening may break the connection or pull part of the copper conductor away.<sup>2</sup>

After making the board, holes for component connections should be drilled out with a 1/16th or 5/64th bit. If the condensers being used have tag terminals rather than wire ends, a short length of wire must be soldered to the tag for connection to the board. None of the components used are large enough to warrant additional strapping to the chassis. Transistors are best connected in the following way (see Fig. 4): take three short pieces of 24 s.w.g. wire, about 1/2 in in length; form small loops at one end, pass the straight ends up through the board and solder the loops to the conductors; the top of each wire may now be bent over about 1/10 in and a "blob" of solder dropped on each wire. Remember always to hold the transistor connections with the pliers in order to provide a heat shunt while soldering.

The controls on the front panel are in the following order: Belling-Lee coaxial input socket, input selector switch, treble lift and cut, base lift and cut, gain plus on/off switch. Note that a d.c. blocking condenser is not shown in the output circuit. A 0.1  $\mu$ F paper condenser may be required in series with the output depending on the first stage of the main amplifier. Attention
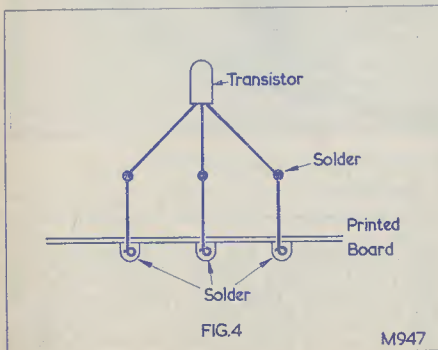
<sup>2</sup> The preparation of printed circuits was fully described in "Do-It-Yourself Printed Circuit Boards" by Squadron Leader S. W. Sarll, A.M. (Brit.), I.R.E., *The Radio Constructor*, November 1959.



should also be paid to the correct polarity of electrolytic condensers in the circuit.

The chassis is of simple construction, consisting of a shallow tray with flanges to which the printed board is held down by self-tapping screws at five points. Principal dimensions may be taken from Figs. 2 and 3 as these are reproduced to actual scale. The flanges should not be more than 1/4 in wide

and capable of making good contact with the "earth" conductor around the edges of the printed board. The front panel is a plain sheet of aluminium, bolted to the front of the chassis by means of a bracket at 1/4 in from each end. The whole unit may be mounted into a cabinet by screwing at the edges of the front panel (holes not shown).

### Components List

#### Transistors

TR<sub>1</sub>  
TR<sub>2</sub>  
TR<sub>3</sub> } OC71

#### Switches

SW<sub>1, 2</sub>. 2-pole, 2-way rotary.

#### Resistors (All 5% unless otherwise indicated)

R<sub>1</sub> (see text and note 1)  
R<sub>2</sub> 39k $\Omega$   
R<sub>3</sub> 10k $\Omega$   
R<sub>4</sub> 27k $\Omega$   
R<sub>5</sub> 100 $\Omega$   
R<sub>6</sub> 6.8k $\Omega$   
R<sub>8</sub> 1k $\Omega$   
R<sub>9</sub> 10k $\Omega$   
R<sub>10</sub> 10k $\Omega$  (10%)  
R<sub>12</sub> 15k $\Omega$   
R<sub>13</sub> 4.7k $\Omega$   
R<sub>14</sub> 470 $\Omega$  (10%)  
R<sub>15</sub> 15k $\Omega$   
R<sub>16</sub> 5.6k $\Omega$   
R<sub>18</sub> 2.7k $\Omega$   
R<sub>19</sub> 100 $\Omega$   
R<sub>20</sub> 1.5k $\Omega$   
R<sub>21</sub> (see text and Note 1)  
R<sub>22</sub> 220 $\Omega$  (10%)

#### Potentiometers

R<sub>7</sub>, R<sub>11</sub> 100k $\Omega$   
R<sub>17</sub> 25k $\Omega$  (with on/off switch)

#### Condensers (All electrolytic condensers 6w.v. unless otherwise indicated)

C<sub>1</sub> 100 $\mu$ F  
C<sub>2</sub> 100 $\mu$ F  
C<sub>3</sub> 30 $\mu$ F  
C<sub>4</sub> 0.05 $\mu$ F (10%) paper  
C<sub>5</sub> 0.5 $\mu$ F (10%) paper  
C<sub>6</sub> 100 $\mu$ F  
C<sub>7</sub> 8000pF (10%) silver mica  
C<sub>8</sub> 0.07 $\mu$ F (see Note 2)  
C<sub>9</sub> 100 $\mu$ F 12 w.v.  
C<sub>10</sub> 50 $\mu$ F  
C<sub>11</sub> 100 $\mu$ F  
C<sub>12</sub> 100 $\mu$ F  
C<sub>13</sub> (see text and Note 1)  
C<sub>14</sub> 100 $\mu$ F 12 w.v.

Note 1. The following values are suitable for use with the Goldring type 500 pickup. R<sub>1</sub>=3.3k $\Omega$ , R<sub>21</sub>=820 $\Omega$ , C<sub>13</sub>=0.5 $\mu$ F.

Note 2. C<sub>8</sub> may be made up with a 0.5 $\mu$ F and a 0.2 $\mu$ F condenser in parallel.

## NEW ELECTROLUMINESCENT DISCOVERIES

New discoveries have brought the industrial and equipment lighting of the future—electroluminescence—one step nearer reality.

This lighting illuminates whole metal sheets by the use of phosphorus, which lights up when an electric current is passed through it. No filaments or elements are needed.

Dr. Peter W. Ranby (Chief Chemist at the Lighting Laboratories of Thorn Electrical Industries Ltd.) and his research group, have developed a method that increases the brilliance of the plates more than three times.

This, says Dr. Ranby, gives Britain European leadership in the electroluminescent field and equal footing with the United States.

Some of the new plates were seen at the Tenth Electrical Engineers Exhibition at Earls Court in March, on the stand of a Thorn subsidiary, Atlas Lighting Ltd.

Hitherto the brilliance at 240 volts and 50 cycles was 1 foot-lambert. The new developments have raised this to 4 foot-lamberts at 2,000 cycles. The increased brilliance is due to general improvements in processing and the use of new enamels.

As far as it is known, this is the only British company developing the "ceramic on metal" type of electroluminescent product with a lamp built upon a steel sheet which forms the back electrode. The phosphorus is embodied in a vitreous enamel, fired at high temperatures. The lamp is completed with a conducting transparent layer of tin oxide to form the second electrode, and a protective clear overglaze.

It is claimed that, for ceramic lamps, they are more robust and versatile than the "organic on glass" lamps. The latter consist of a glass sheet on which a transparent conducting film of tin oxide is deposited, followed by the phosphorescent layer in an organic resin binder. The condenser is completed by a second electrode of evaporated metal and the assembly sealed with paraffin wax to exclude moisture. This type of lamp is supplied as cabin signs for many aircraft, including Comets and Caravelles.


For instance: luminous telephone dials, in which an electroluminescent strip is placed behind the dial and current consumption will be a matter of a few pence a year.

These lamps are suitable for aircraft instruments, car instruments panels and radio tuning dials; luminous clock faces and map readers are already in production.

Plans for the future include the use of electroluminescent road signs for the new motorways. Once installed, running costs will be negligible.



# Design for a Stereo/Mono

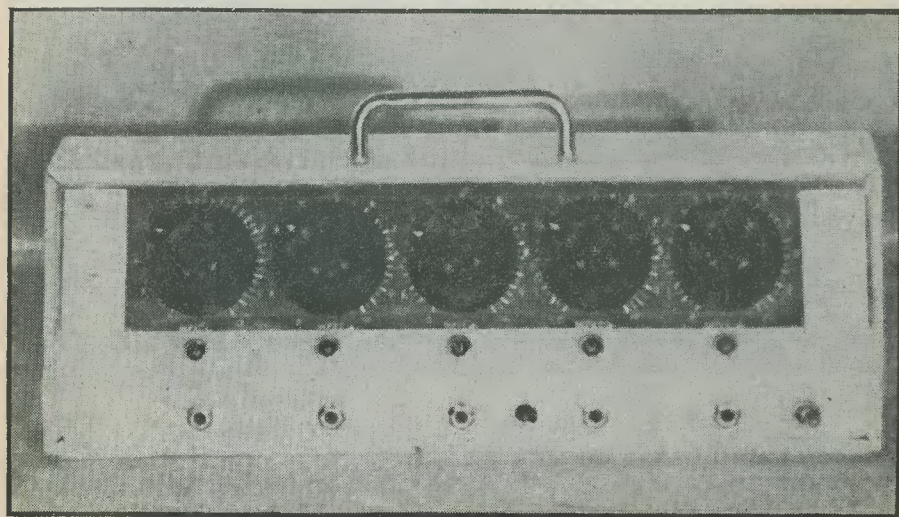

by P. R. TRAVERS

## Microphone Mixer Unit

SINCE THE WRITER'S ARTICLE ON DESIGNING a microphone mixer unit was published in 1959\* a requirement has arisen for a stereophonic mixer unit. In making stereo recordings of choral and orchestral works, or of theatrical productions, it is often essential to use more than one microphone in each channel. The first solution seemed to be to build two independent mixer units but, having already built a five-channel mixer with its own power supply, I was loath to discard it.

After a little thought it was found possible to convert the five-channel unit to a comprehensive mixer unit with the following specification.


1. To be a stereophonic mixer having three inputs for the left channel and two for the right.
2. Separate outputs to be available for left and right channels.

3. To be available also as a five channel monophonic mixer.

4. Two identical outputs to be available, each fed with the same mono signal but each completely independent of the other. This allows two recorders or a recorder and a separate amplifier to be fed with the identical signal.

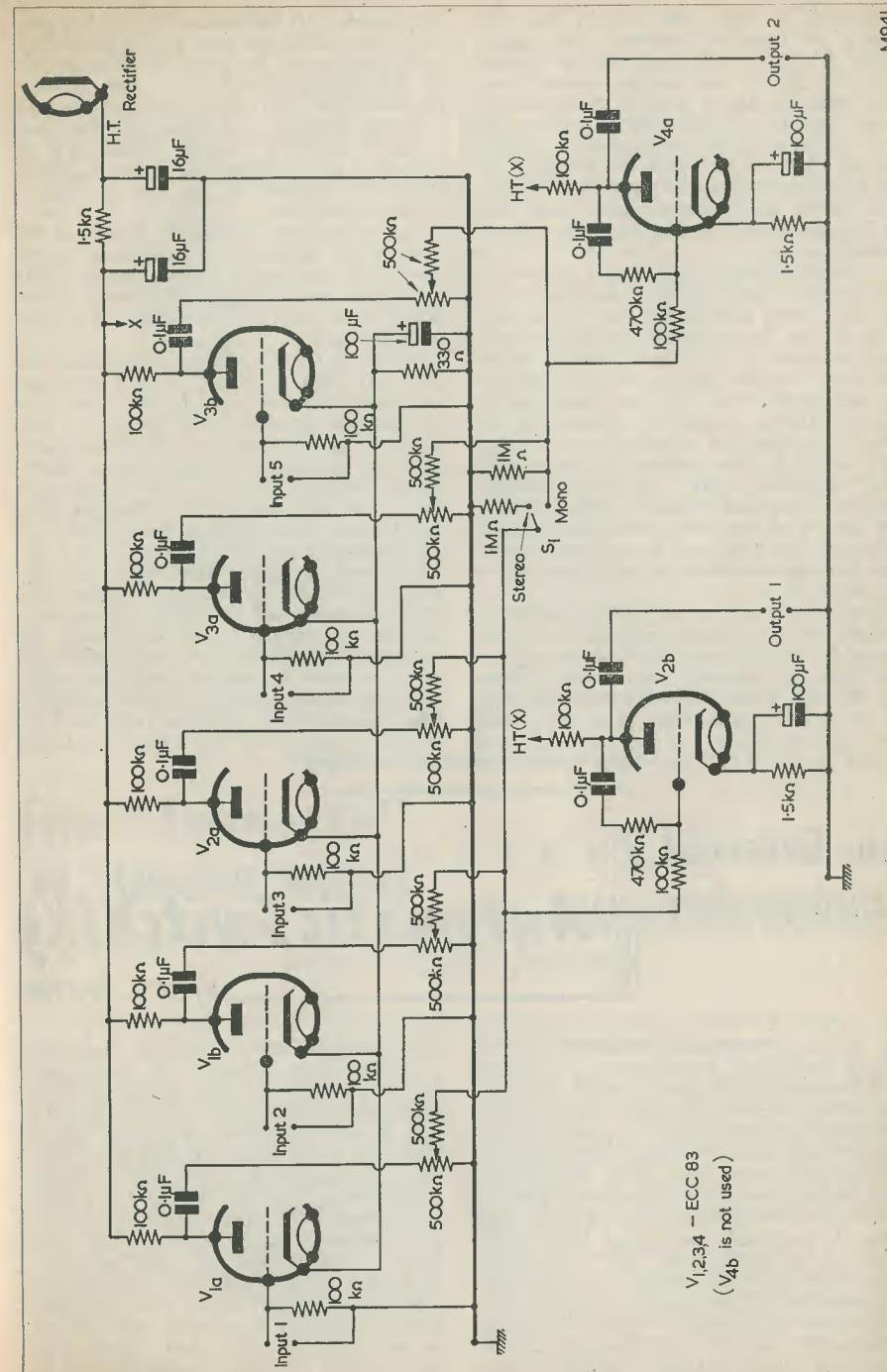5. The unit to be self-powered.
6. Figures for hum, noise and crosstalk to be kept to a minimum.
7. There should be immediate visual indication of the channels in use.

The circuit of the unit is shown in the accompanying diagram. It will be seen that each input channel is fed to a separate triode voltage amplifying stage. The signal at each triode anode is fed via a  $0.1\mu\text{F}$  condenser to a  $500\text{k}\Omega$  gain control. The  $500\text{k}\Omega$  resistors connected to the gain control sliders prevent interaction between the channels; without those resistors the volume level in one channel would be



V<sub>1,2,3,4</sub> - ECC 83  
(V<sub>4b</sub> is not used)

influenced by any alteration in the gain setting of another channel. The signals from the three left hand inputs (Inputs 1-3) are fed to the output triode  $V_{2(b)}$ . The amplified signal is then fed to Output 1 via the  $0.1 \mu\text{F}$  condenser. As the full gain of the stage is not required a portion of the signal is fed back to the grid via the  $0.1 \mu\text{F}$  condenser and the  $470\text{k}\Omega$  resistor. This serves to improve quality and also to keep hum and noise to negligible proportions.

A similar output stage ( $V_{4(a)}$ ) is provided for Inputs 4 & 5, which together form the right hand channel for the stereo pair.

$S_1$  is the Stereo/Mono function switch, and is shown in the Stereo position in the diagram. In this position a  $1\text{M}\Omega$  resistor is connected from the combined inputs of each stereo channel to chassis. In the Mono position the outputs from all five gain controls are connected in parallel with a single  $1\text{M}\Omega$  resistor connected between them and chassis. In this position the combined signal is fed to both output stages in parallel, and thus two identical but quite independent output channels are available.

The gain controls are  $500\text{k}\Omega$ : potentiometers with a single pole switch. The switch is wired so that a pilot light is switched on when the control is operated. Power for this light comes from the heater winding of the mains transformer. The pilot lights are situated below the gain controls and above the input sockets. Thus, even when

the equipment is operated in the half darkness that exists backstage in a theatre, immediate visual indication is given of the channels in use. A refinement is to use different coloured pilot lights for each stereo channel.

Power supplies are quite conventional, a valve full-wave rectifier being used to provide h.t. If desired, a saving in space could be achieved by the use of modern miniature rectifiers.

The photograph shows the layout of the unit. As it is invariably used close to the associated equipment, short output leads are fitted and cathode follower output stages were discarded in favour of triodes with feedback.

Within a few days of its completion the unit was used to record an extensive out of doors ceremony, and at the same time to feed an elaborate P.A. system. Three microphones were required for the ceremony with an additional commentator's microphone. It has also been used to record a large orchestral concert, a Passion Play with actors, choir, soloists and organ, and a "straight" play, all in stereo.

Crosstalk is better than  $60\text{db}$ . at  $1\text{kc}$  between any two channels and better than  $90\text{dB}$ . between left and right channels in the Stereo position. Hum and noise are inaudible with no inputs jacks inserted and all gain controls set at maximum (self-earthing sockets are used). With microphone plugs inserted, hum and noise vary with the length of cable and the care with which it is positioned.


## An External Loudspeaker with Automatic Switching

by M. J. DUNN

**M**ANY PEOPLE LIKE TO LISTEN TO SOUND broadcast programmes in rooms remote from that in which the radio set is kept. Normally this involves the purchase and installation of an extension speaker and cabinet—usually a boxy little affair placed on a shelf. Both the expense, and finding space for the extension speaker, can be avoided by making use of an existing item of equipment containing a loudspeaker (such as a radiogram). The latter may, also, offer the advantages of a superior loudspeaker and a larger cabinet. The circuit to be described shows how the loudspeaker in such equipment may be employed as an extension speaker without

the complications of manual switching, a simple relay causing the loudspeaker to be switched to the extension wiring whenever the equipment is switched off.

*It is most important to ensure that the equipment whose speaker is used as an extension loudspeaker has a chassis which is isolated from the a.c. supply by a mains transformer. The circuit must not be used with equipment having an a.c./d.c. power supply.* The reason for this warning is that, if it is not followed, the extension speaker wiring may be at mains potential. Suitable isolated equipment will normally be provided by radiograms, some of the older model television receivers, and the

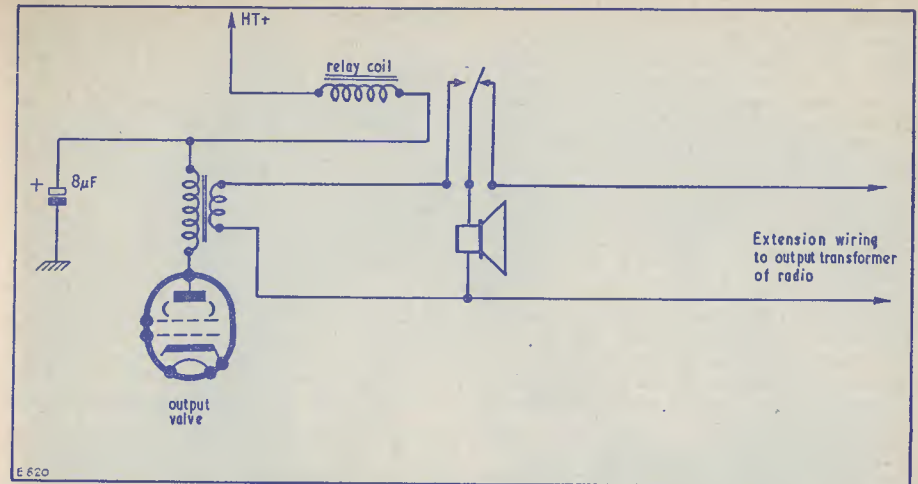

larger table model radios.

The switching circuit accompanies this article. The coil of a relay having changeover contacts is connected in series with the output transformer of the apparatus which houses the loudspeaker. The contacts are arranged so that when they are at rest, the loudspeaker is connected to the extension wiring. When it is required to use the apparatus itself the latter is switched on. As soon as the output valve has warmed

up current is drawn through the coil of the relay, whose contacts then switch the speech coil to the secondary of its own output transformer. From a constructional point of view the entire modification is conveniently centred round one (usually) accessible component—the output transformer. An  $8\mu\text{F}$  electrolytic condenser is included in the circuit to prevent the relay coil taking part in the a.c. load of the valve.

## The "Twinette" TWO TRANSISTOR RECEIVER

A SIMPLE EASY-TO-BUILD LOCAL STATION SET

Described by R. J. CABORN

*This article gives full details of a simple two-transistor receiver capable of being built both by the beginner and by the more experienced constructor*

**T**HERE IS ALWAYS A DEMAND AMONGST constructors for simple receivers which, whilst taking advantage of all the facilities offered by transistors, are still relatively inexpensive and easy to build. The "Twinette" meets this demand. It employs only two transistors, but these are used in a circuit which offers a very high degree of gain, such gain being realised by operating the first transistor in a reflex circuit wherein it carries out the double function of r.f. and a.f. amplifier, and by employing reaction. The latter further allows a satisfactory level of selectivity to be achieved. The output

transistor feeds into a  $7\text{in} \times 4\text{in}$  elliptical speaker, a speaker of this size being specified in order to take full advantage of the output power available. As may be seen from the photographs which accompany this article, the chassis dimensions are such that the speaker fits snugly into the component layout.

The "Twinette" is a local station receiver, and it employs separate ferrite slab aerials for Medium and Long wave reception. Facilities are provided for connecting a short external aerial in poor reception areas. The receiver is powered by a single battery.

## Circuit

The circuit of the "Twinette" appears in Fig. 1. At the left hand side of this diagram are the two ferrite slab aeri-als. Windings L<sub>1</sub>, L<sub>2</sub> and L<sub>3</sub> appear on the Medium wave ferrite slab aerial, and windings L<sub>4</sub>, L<sub>5</sub> and L<sub>6</sub> appear on the Long wave ferrite slab aerial. These windings are switched in and out of circuit by the three switches connected to their upper terminals. These three switches are combined with the on-off switch in a 4-pole 3-way unit providing "Off", "M.W.", and "L.W.". The numbers appended to the switch contacts in Fig. 1 correspond to those employed in the wiring layout diagrams which follow. Of the sets of windings on the ferrite slab aeri-als, L<sub>1</sub> and L<sub>4</sub> are tuned windings, L<sub>2</sub> and L<sub>5</sub> are coupling windings which provide a low impedance

match into the base circuit of transistor TR<sub>1</sub> and L<sub>3</sub> and L<sub>6</sub> are reaction windings. When an external aerial is employed this is connected, via C<sub>7</sub>, to the tuned windings.

The low impedance r.f. signal from L<sub>2</sub> or L<sub>5</sub> (according to whether "M.W." or "L.W." is selected by the switch) is fed directly to the base of transistor TR<sub>1</sub> and, via condenser C<sub>2</sub>, to its emitter. C<sub>2</sub> has a low reactance at r.f., with the result that almost all the r.f. signal from the ferrite slab aerial appears across the base and emitter of TR<sub>1</sub>. TR<sub>1</sub> functions as an r.f. amplifier, and the amplified signal appears at its collector, the r.f. choke L<sub>7</sub> functioning as a collector r.f. load. The amplified r.f. is then fed to the detector D<sub>1</sub>, via condenser C<sub>4</sub>. The r.f. choke L<sub>8</sub> provides a d.c. circuit for the detector, and a detected signal appears


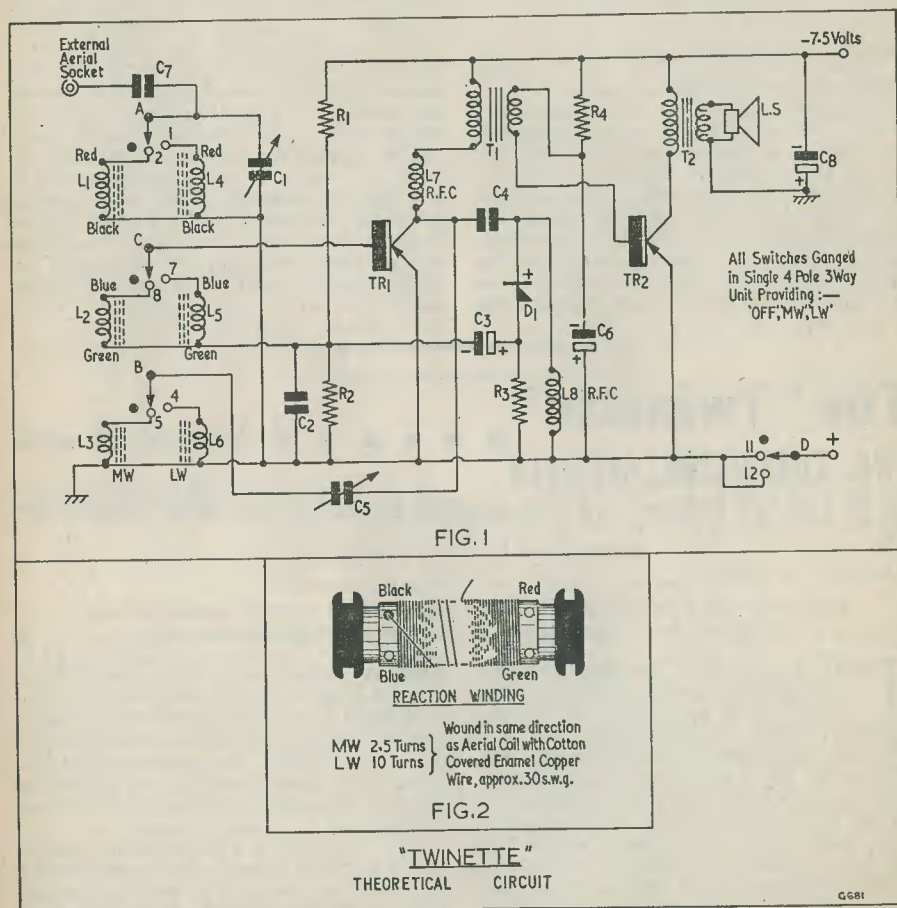


Fig. 1. The circuit of the "Twinette"

Fig. 2. How the reaction windings are added to the ferrite slab aeri-als

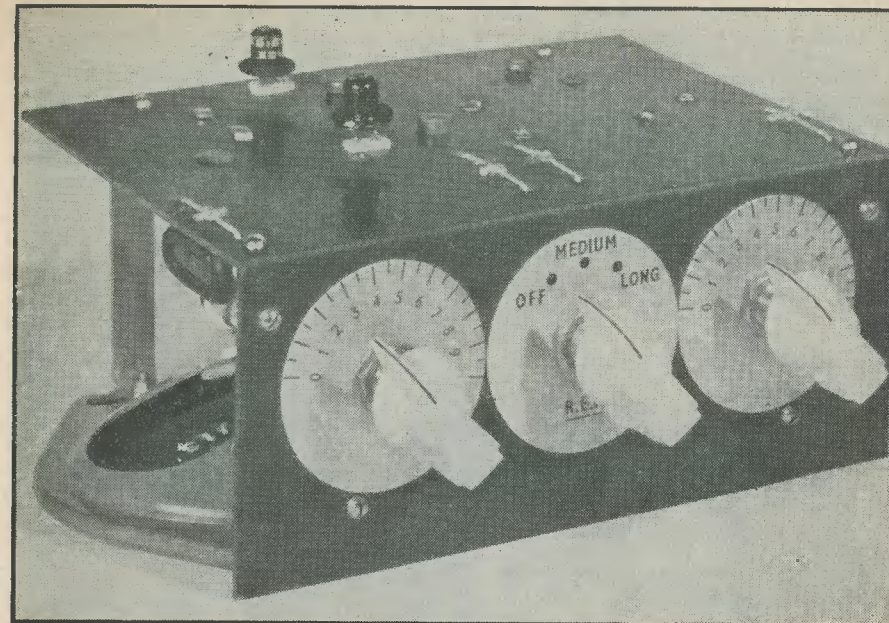

Front view of the completed "Twinette" Transistor Receiver

across R<sub>3</sub>. This signal is passed, via C<sub>3</sub>, to C<sub>2</sub> and the lower terminals of L<sub>2</sub> and L<sub>5</sub>. C<sub>2</sub> now carries out the secondary function of bypassing the r.f. component in the detected signal to chassis, its reactance at r.f. being sufficiently high to prevent any undue loss of detected audio signal. The detected audio signal is next applied, by way of L<sub>2</sub> or L<sub>5</sub> (according to which is selected by the switch) back to the base of TR<sub>1</sub>. This time TR<sub>1</sub> functions as an a.f. amplifier, the amplified a.f. signal appearing across the primary of transformer T<sub>1</sub>. Bias for TR<sub>1</sub> is provided by R<sub>1</sub> and R<sub>2</sub>.

The secondary of T<sub>1</sub> couples into the base and emitter circuit of the output transistor TR<sub>2</sub>, the emitter coupling being made via C<sub>6</sub>. Resistor R<sub>4</sub> biases TR<sub>2</sub>, causing it to operate at the desired point on its characteristic. The collector of TR<sub>2</sub> then feeds into the primary of the speaker transformer T<sub>2</sub>. Condenser C<sub>8</sub>, connected across the supply, ensures the existence of a low impedance between the positive and negative supply rails, thereby enabling the receiver to be used even when the internal resistance of the battery reaches a high value due to ageing.

## Construction

Construction proceeds in the following manner. The first steps are illustrated in

Fig. 4. It will be found helpful, throughout construction, to refer to Fig. 3, which illustrates hole layout in the top and back panels.

1. Wind 2½ turns of enamelled and silk or rayon covered wire (approximately 30 s.w.g.) on the Medium wave slab aerial (FS<sub>3</sub>) in the same direction as the aerial coil. (See Figs. 2 and 5.) Best results are obtained with the coupling coil close to the black and blue eyelets. Connect additional winding to black eyelet, as illustrated.

2. Wind 10 turns of enamelled and silk or rayon covered wire (approximately 30 s.w.g.) on the long wave slab aerial (FS<sub>4</sub>) in the same direction as the aerial coil, and over the centre of the existing winding. (See Figs. 2 and 5.) Connect additional winding to black eyelet, as illustrated.

3. Mount the Medium and Long wave slab aeri-als on the inside of the back panel, securing with a fine cord (such as dial drive cord) looped through holes T for the Medium wave aerial and holes F for the Long wave aerial, referring to Figs. 3 and 4.

4. Mount transformer T<sub>2</sub> on the rear panel using holes R and S. Secure with 4BA screws and nuts, with a 4BA solder tag at R. The transformer fly leads should be on the inside.


5. Mount transformer T<sub>1</sub> on the rear panel by pushing the lugs of its shroud through

holes P and Q and bending them towards each other. The primary winding (marked with a red spot) should face outwards.


6. Fit L<sub>7</sub> (green tags) in hole N with the tag ring in the position shown in Fig. 4, and glue into position.

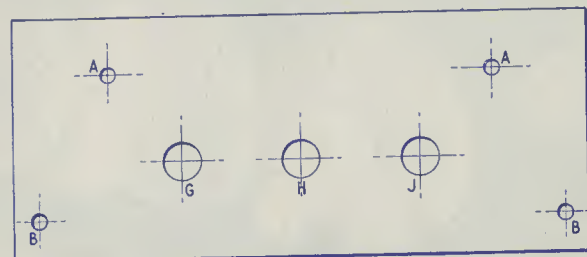7. Fit L<sub>8</sub> (yellow tags) in hole K with the tag ring in the position shown in Fig. 4. Glue into position.

emitter tag of TR<sub>1</sub> holder to eyelet 4. Connect eyelet 4 to the solder tag at R. Connect eyelet 4 to tag 4 of L<sub>8</sub>. Connect eyelet 6 to tag 1 of L<sub>8</sub>. Connect tag 4 of L<sub>7</sub> to collector tag of TR<sub>1</sub> holder. Connect tag 1 of L<sub>7</sub> to tag 1 of transformer T<sub>1</sub>. Connect tag 2 of T<sub>1</sub> to eyelet 3. Connect base tag of TR<sub>2</sub> holder to tag 4 of T<sub>1</sub>. Connect emitter tag of TR<sub>2</sub> holder to solder tag at R.



TOP PANEL  
Top View

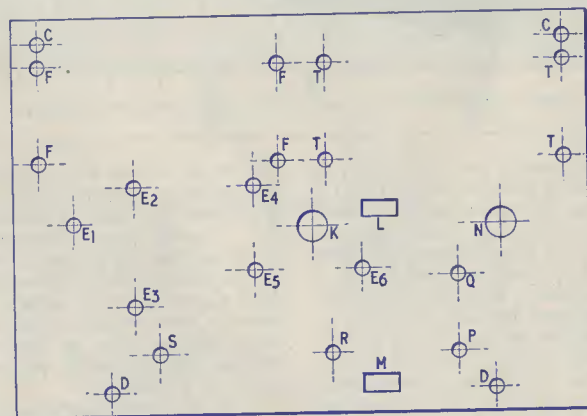

All holes marked 'E' are eyeleted

BACK PANEL  
Outside View

FIG.3

A top view of the top panel and an outside view of the back panel. This diagram will assist in the identification of holes referred to in the text

8. Fit the transistor holder for TR<sub>1</sub> in hole L with the tags in the position shown in Fig. 4.

9. Fit the transistor holder for TR<sub>2</sub> in hole M with the tags in the position shown in Fig. 4.

10. Connect the green eyelet of the Medium wave aerial to eyelet 2. Connect the green eyelet of the Long wave aerial to eyelet 2. Connect the black eyelet of the Long wave aerial to eyelet 4. Connect the

11. Connect the blue lead of T<sub>2</sub> to collector tag of TR<sub>2</sub> holder.

12. Connect the red lead of T<sub>2</sub> to eyelet 3.

13. Connect C<sub>6</sub> (2μF) from tag 3 of T<sub>1</sub> to the solder tag at R, with the positive end of C<sub>6</sub> at the solder tag.

14. Connect R<sub>4</sub> (47kΩ) from tag 3 of T<sub>1</sub> to eyelet 3.

15. Connect R<sub>1</sub> (220kΩ) from eyelet 2 to eyelet 3.

16. Connect R<sub>2</sub> (10kΩ) from eyelet 2 to

eyelet 4.

17. Connect C<sub>2</sub> (0.005μF) from eyelet 2 to eyelet 4.

18. Connect R<sub>3</sub> (10kΩ) from eyelet 5 to eyelet 4.

19. Connect C<sub>3</sub> (2μF) from eyelet 5 to eyelet 2, with the positive end at eyelet 5.

20. Connect diode D<sub>1</sub> from eyelet 5 to eyelet 6, with the cathode (red) end of the diode at eyelet 6.

21. Connect C<sub>4</sub> (100pF) from eyelet 6 to collector tag of TR<sub>1</sub> holder.

and nuts through holes C of the rear panel.

27. Connect tag A of the switch to tag "a" of C<sub>1</sub>.

28. Connect tag B of the switch to tag "b" of C<sub>5</sub>.

29. Connect tag C of the switch to base tag of TR<sub>1</sub> holder.

30. Connect tag D of the switch to the positive battery connector via a 1ft length of red flexible wire.

31. Connect tag 1 of the switch to the red eyelet of the Long wave aerial.

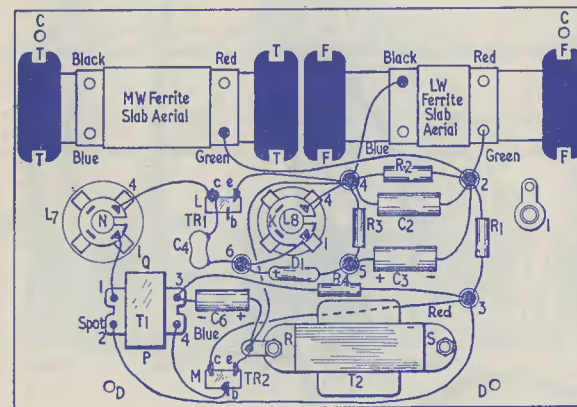


FIG.4

CG83

First steps in assembling the "Twinette"

### The Top Panel

The following steps are illustrated in Fig. 5.

22. Mount C<sub>1</sub> (300pF) through hole J of the top panel (with the body of the condenser under the panel) in the position shown in Fig. 5, fitting a 0-10 dial plate under the securing nut.

23. Mount C<sub>5</sub> (100pF) through hole G of the top panel (body underneath, as C<sub>1</sub>) fitting a 0-10 dial plate under the securing nut.

24. Mount the switch through hole H of the top panel (with its body under the panel) so that its tags are in the position shown in Fig. 5. Fit the switch plate under the securing nut as shown in the photograph of the top of the receiver.

25. Fit two angle brackets to holes B of the top panel with 6BA screws and nuts, the longer arms being those bolted to the top panel.

26. Join the top panel to the rear panel by securing the angle brackets with 6BA screws

32. Connect the free end of the Long wave aerial reaction winding (fitted in step 2) to tag 4 of the switch.

33. Connect the free end of the Medium wave aerial reaction winding (fitted in step 1) to tag 5 of the switch.

34. Connect tag "a" of C<sub>5</sub> to the collector tag of TR<sub>1</sub> holder.


35. Connect C<sub>7</sub> (100pF) from tag "a" of C<sub>1</sub> to the solder tag at R.

36. Connect C<sub>8</sub> (100μF) from eyelet 3 to solder tag at R, its positive end being at the solder tag.

### Final Wiring


The following steps are illustrated in Fig. 6. 37. Connect tags 10 and 11 of the switch together and then to tag "b" of C<sub>1</sub>, carrying on to the black eyelet of the Long wave aerial.

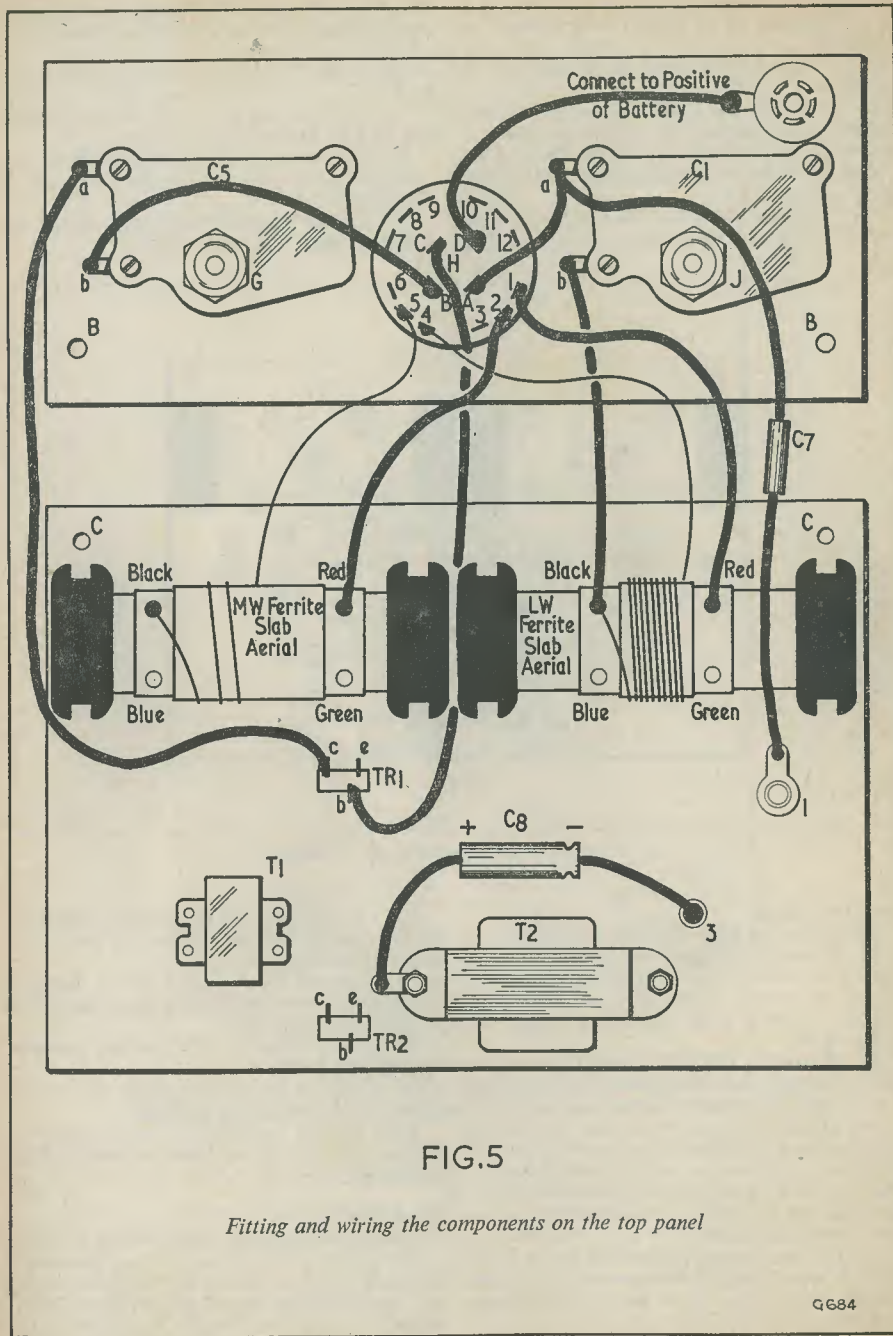38. Connect tag 8 of the switch to the blue eyelet of the Medium wave aerial.



39. Connect tag 7 of the switch to the blue eyelet of the Long wave aerial.
40. Connect together the black eyelets of the Medium and Long wave aerials.
41. Connect eyelet 3 to the negative battery connector via a 1ft length of flexible wire having a colour other than red.
42. Fit two angle brackets to the top panel

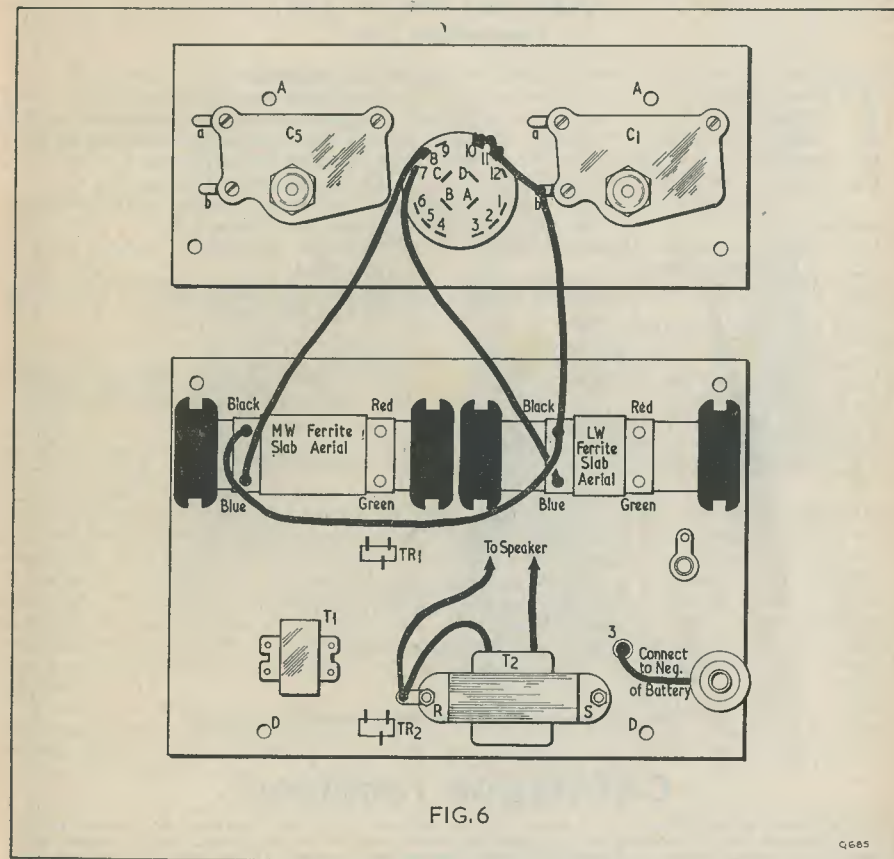47. Connect the red eyelet of the Medium wave aerial to tag 2 of the switch. (See Fig. 5.)
48. Fit a solder tag at either of the points D and connect to solder tag at R.
49. Bolt the speaker to the brackets fitted in steps 42 and 43, as shown in the photograph of the chassis. Use 6BA screws and



50. Insert TR<sub>1</sub> (OC44 or XA104) in the TR<sub>1</sub> holder, and TR<sub>2</sub> (OC71 or XB102) in the TR<sub>2</sub> holder.
51. Fit pointer knobs to the spindles of C<sub>1</sub>, C<sub>5</sub> and the switch.
52. Connect the positive battery connector (red lead) to the positive terminal of the battery, and the negative connector to the negative terminal of the battery, taking care to ensure correct polarity.

## Final Details

The "Twinette" is now complete and ready for operation. Tuning is carried out by adjustment of  $C_1$ ,  $C_5$  controlling reaction. Greatest sensitivity and selectivity will be given when the reaction setting is just below oscillation point. If an external aerial is

required this should be connected to the tag at eyelet 1. See Fig. 5. The eyelet at this position will accept a standard aerial plug.

The receiver will give adequate volume in its completed chassis state. To obtain optimum results the chassis should be fitted in a cabinet, the latter providing a baffle for the speaker.

## Components List

### Resistors

(All  $\frac{1}{4}$  watt, 20%)

- R<sub>1</sub> 220k $\Omega$
- R<sub>2</sub> 10k $\Omega$
- R<sub>3</sub> 10k $\Omega$
- R<sub>4</sub> 47k $\Omega$

### Condensers

- C<sub>1</sub> 300pF variable (Jackson Bros.).  
Dilicon dielectric
- C<sub>2</sub> 0.005 $\mu$ F, 250 w.v. (or less if available)
- C<sub>3</sub> 2 $\mu$ F, electrolytic, 12 w.v.
- C<sub>4</sub> 100pF, 250 w.v. (or less if available)
- C<sub>5</sub> 100pF variable (Jackson Bros.).  
Dilicon dielectric
- C<sub>6</sub> 2 $\mu$ F, electrolytic, 12 w.v.
- C<sub>7</sub> 100pF, 250 w.v. (or less if available)
- C<sub>8</sub> 100 $\mu$ F, electrolytic, 12 w.v.

### Miscellaneous

- 2 Transistor holders, Cinch type 81/001
- 2 Transistor holder clips, Cinch type 77/765
- 1 4-pole 3-way switch, miniature
- 1 7in x 4in elliptical speaker, Elac
- 3 Pointer knobs
- 1 Battery type PP4, Ever-Ready
- Nuts, bolts, washers, etc.

### Special Components

(All available from Repanco Ltd.)

- 1 Medium wave ferrite slab aerial type FS3
- 1 Long wave ferrite slab aerial type FS4
- 1 R.F. choke type RF<sub>1</sub> (L<sub>7</sub>)
- 1 R.F. choke type RF<sub>2</sub> (L<sub>8</sub>)
- Top and rear panels, with brackets.  
(Group board type 6/T)
- 1 Interstage transformer, ratio 4.5 to 1, type TT14
- 1 Output transformer, type TT5
- 1 Set of 3 dial plates.

### Transistors

- TR<sub>1</sub> Mullard OC44 or Ediswan XA104
- TR<sub>2</sub> Mullard OC71 or Ediswan XB102

### Diode

- D<sub>1</sub> Mullard OA81

## Catalogue received

Surplus Radio Supplies (Poldew Ltd.), 2 Laing's Corner, Mitcham, Surrey, have forwarded to us a copy of their Radio Component List. Comprising some 17 pages plus cover, this List includes a vast range of components at bargain prices, practically every item being well below current price ranges. Of the components offered, 90% are not Government surplus but brand new and unused, many being manufacturers' discontinued lines and warehouse "overs". Readers may obtain a copy of this list direct from Surplus Radio Supplies (Poldew Ltd.), at 1s. 6d. (including postage).

## Argosy Doppler Navigator uses EEV K350 Klystron

The new Argosy C. Mark I aircraft for R.A.F. Transport Command will be provided with a Marconi Doppler Navigator Type AD2300B which comprises a sensor, computer and display unit.

A K350 klystron, manufactured by the English Electric Valve Co. Ltd. is used in the transmitter/receiver (sensor) equipment as the transmitter source of power and by sampling at the mixer this klystron also provides the local oscillator signal. The K350 is a forced-air cooled, two resonator klystron with mechanical tuning covering the frequency range from 8,500 to 10,000 Mc/s. The output power is approximately 1W and this is obtained with low noise modulation and good frequency stability. Another feature of the K350 klystron is that it can be used at high altitudes without pressurising.

# Getting Started on 2-Metres

PART I—AERIAL SYSTEMS

by J. N. WALKER, G5JU

*This is the first of a series of articles written especially for the beginner interested in 2-metre operation. Our contributor, who has been active for many years in the 2-metre field, and who is associated with a well-known firm of Short wave component manufacturers, describes this month simple but effective aerial systems. Next month's article will describe a single valve converter and this will be followed by a description of the addition of an r.f. and i.f. stage to this basic design, these additional stages being fitted to the same chassis. A 2-metre transmitter will also be fully described in this series*

WHILST PERHAPS SOME SORT OF RESULTS can be achieved on two metres by, say, attaching an odd length of wire to the input socket of a two-metre converter, it is much more satisfactory to employ an aerial designed essentially to work on this one band and no other. Further, because the size of elements in an aerial for the 144 Mc/s band is relatively small, it becomes entirely practical to build up multi-element arrays without occupying a great deal of space. Such arrays naturally become highly directive both in the horizontal and vertical planes and, with the resulting concentration of power in a beam, very substantial gain is secured. The ability of a receiver to make weak signals intelligible is then greatly increased whilst, on the transmitting side, there is a considerable step-up in the effective radiated power.

However, to start with quite a simple aerial can be used—for example, a straight-forward dipole. The construction of such an aerial is illustrated in Fig. 1. It is preferable

to use tubing, made of any of the commonly obtainable metals, to give sufficient bandwidth to cover adequately the whole of the band,  $\frac{1}{4}$ in or  $\frac{3}{8}$ in diameter material being quite suitable. The use of wire instead of tubing will unduly narrow the bandwidth but, if one is in a hurry to get some sort of aerial erected, two or three lengths of 14 or 16 gauge wire in parallel will perform fairly well, especially if the ends are splayed out an inch or two.

The dipole is fed at the centre with either twin cable of 80 $\Omega$  impedance or 75 $\Omega$  coaxial cable, both providing a good match. A better balance is achieved with the twin cable. With coaxial cable there is almost certain to be some pick-up (or radiation) from the outer screen of the cable, this giving rise to omni-directional effects, partly in the vertically polarised mode. Incidentally most amateur work is carried out using horizontal polarisation and, accordingly, the aerial proper should be mounted horizontally.

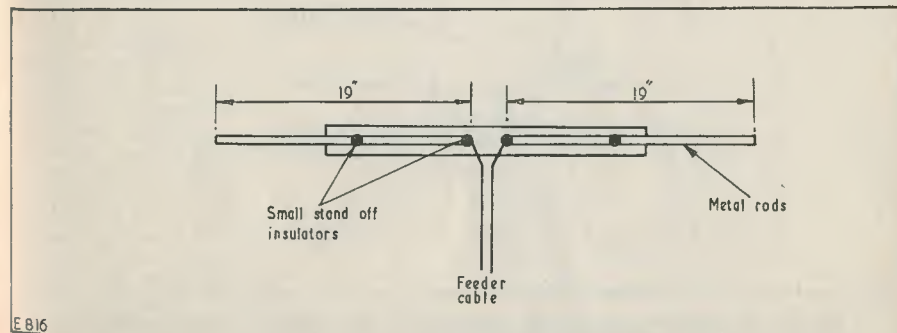


Fig. 1. A simple dipole aerial for the 2-metre band. Two lengths of metal tubing, four miniature stand-off insulators and a wooden support are all that are needed

To obtain the advantage of the figure-eight directional pattern given by a dipole, it is advisable to arrange for the dipole assembly to rotate through 90 degrees, or some signals may be missed.

#### Reflector and Director

Although the simple dipole gives some gain compared to an omni-directional aerial, this gain is not great. The addition of a reflector or director—or both—improves matters immediately by concentrating the beam mainly in one direction.

A complication arises here in that the centre impedance of the main element—the dipole itself—is reduced by the addition of further elements. However, with the addition of a single widely spaced reflector, as shown in Fig. 2, the mismatch with 80Ω or 75Ω cable is not serious and overall results will definitely be improved.

On making the array into a proper Yagi by adding also a director element, as illustrated in Fig. 3, the impedance at the centre of the dipole drops still more, to a value around 15Ω or 20Ω, whereupon something has to be done to correct the mismatch. The most satisfactory method, and the one generally adopted, is to convert the centre element into a folded dipole by adding another tube of the same length and diameter as the original but with no gap at the centre, as is shown also in Fig. 3. A transformation then results, stepping up the impedance by a factor of four, and so bringing the effective impedance back to near the 80Ω mark.

Still greater directivity and gain can be secured by adding a second director having

the same length and spacing as the first. Beyond this the advantage per director added is reduced, as the beam becomes exceedingly directional and covers only a small angle. In the majority of cases using more than two directors is hardly worth while. Little or no advantage is gained by trying to use more than one reflector.

As before, either balanced or coaxial feeder cable can be connected to the centre of the dipole. Since now the array is uni-directional it becomes necessary to arrange to rotate it through 360 degrees.

#### Quad Aerial

The Quad type of aerial is well known as a good performer on the lower frequency bands and it is also quite effective on two metres. A design which has proved successful in practice is shown in Fig. 4, and, although heavy gauge wire may be used at a pinch, it is better to fabricate the elements from light tubing, to give a wider bandwidth. A reflector is normally used as shown and some further benefit will be secured by adding a director, of a total length somewhat shorter than the main element.

The polarisation of the Quad depends on the point at which the feeder is connected—as shown, the aerial is horizontally polarised.

A more elaborate design of Quad aerial was described in the September 1960 issue of *The Radio Constructor*\* and the dimensions given there can be readily scaled down, using

\* "The Quad Plus", by A. S. Carpenter, *The Radio Constructor*, September, 1960.

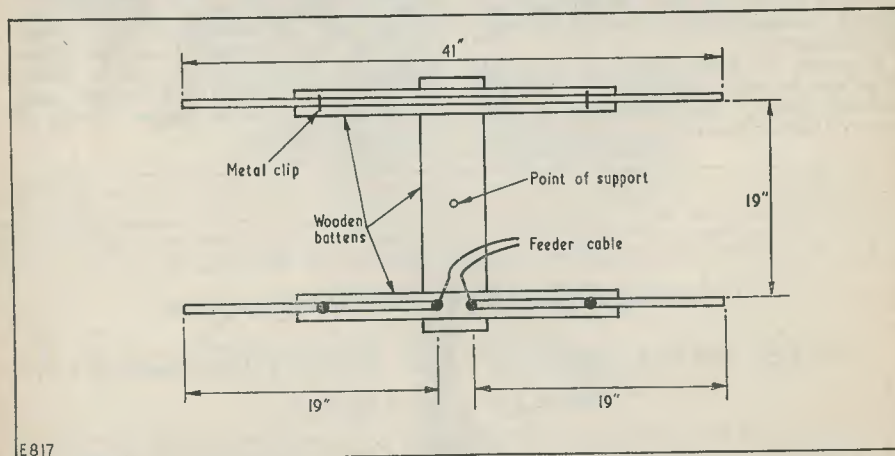


Fig. 2. An effective 2-metre wide spaced beam. The reflector is one continuous length of metal tubing, 41in long, whilst the radiator is split as in Fig.1. Any available wooden battens may be used and the reflector elements do not require to be insulated

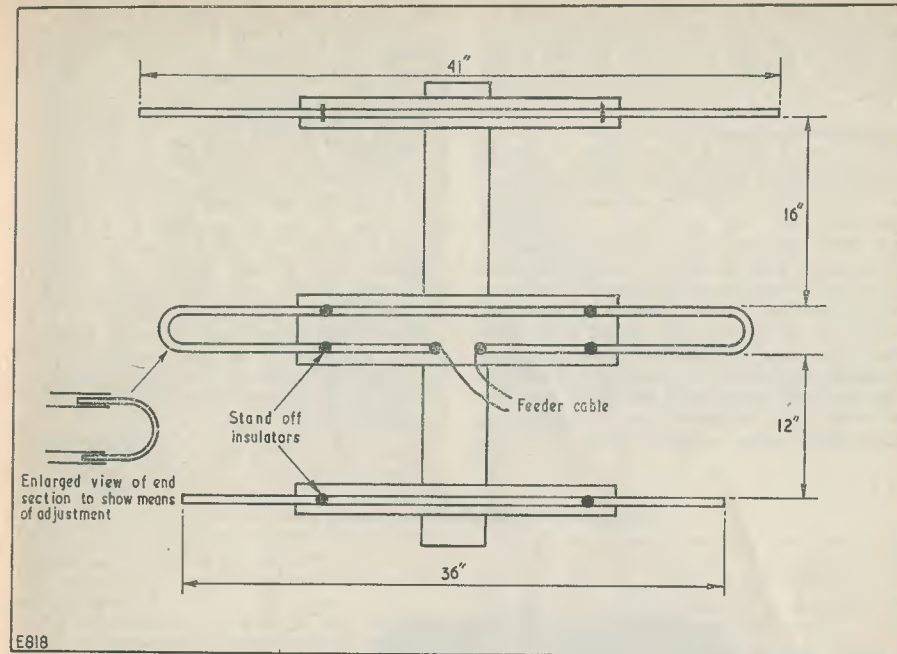


Fig. 3. A 3-element beam with folded dipole centre element. The metal tubing for the radiator should have a total length of 76in, including bends. To allow adjustments for resonance, make the ends a sliding fit inside the main tubes. These ends can be soldered when the aerial has been set up correctly


those given in Fig. 4 as a guide, to suit the two metre band.

#### Feeder Cable

Losses in feeder cable increase with frequency and the operator sometimes has to decide whether to erect his aerial array close to the station equipment where it may

not be in too good a position, or at a more distant point which is in the clear but which involves a longer run of cable. The latter situation, giving lower absorption losses and less screening, is likely to prove the better provided a good quality cable is employed. Ordinary 1/4in diameter t.v. coaxial cable and twin feeder is suitable only for comparatively

Fig. 4. Outline of a Quad aerial for 2-metre operation. The reflector is one continuous length of metal tubing with 21in sides. A suitable wooden framework should be constructed and the beam supported where insulators are indicated. The reflector is mounted directly behind the active loop

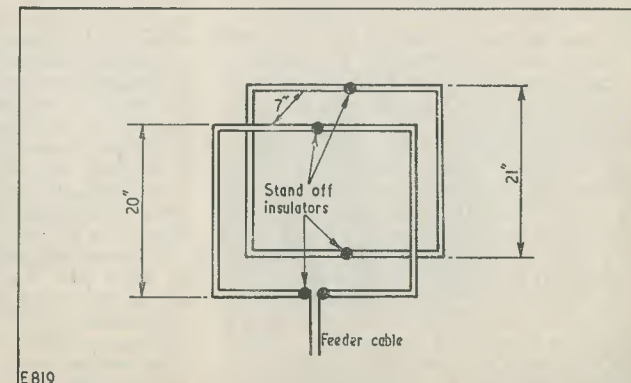

short runs (and for low power on the transmitting side). Where the cable length exceeds say 25ft, it is wise to employ heavier semi-air-spaced cable, with its much lower loss factor.

#### Testing for Resonance

Whilst the dimensions shown in the diagrams should bring the resonant frequency of the aerial inside the two-metre band variations can and do occur, these being due to the siting of the aerial, nearness of metal parts, and so on. In two recent cases where tests were made on aeriels assumed to be correctly resonant, one Yagi assembly was found to resonate at above 150 Mc/s, whilst the other, a Quad, showed resonance at about 142 Mc/s. It will be appreciated that results in such cases are likely to suffer on both the receiving and transmitting sides—gain will drop and directivity may

not quite follow the expected pattern.

For an easy and reliable method of testing, a calibrated grid dip oscillator should be used. A small loop of wire is formed and connected to the feeder termination. The coil of the grid dip oscillator is brought near to this loop and a pronounced dip should occur when the meter dial is swung over the correct frequency range. The frequency at which the dip is found should be as near as possible to the centre of the band i.e. 145 Mc/s., and this can be checked with a high degree of accuracy by tuning in the grid dip oscillator signal on the station receiving equipment.

Any small discrepancy can be ignored. If the discrepancy is considerable it will pay to adjust the length of the aerial radiator, shortening it if the observed frequency is too low, and *vice versa*.

(To be continued)

## radio topics

BY RECORDER

IN OUR NOVEMBER ISSUE LAST YEAR WE gave details of exceptional Dx television reception, as achieved by Mr. I. C. Beckett, of Twyford, near Buckingham. We have since had a lively correspondence with Mr. George Petersen, of Ayr, North Queensland, Australia. Mr. Petersen, a radio engineer, has been carrying out some extensive t.v. Dx work (and has been hitting the local headlines in consequence!) and I don't think I can do better than quote from one of his letters detailing his experiences during 1960. Don't forget, when reading this letter, that Mr. Petersen's receiver will be a 625-line job having intercarrier f.m. sound. That is why he needs a local oscillator, beating with the incoming sound carrier, to cause the

latter to be passed into his 5.5 Mc/s i.f. amplifier. (Sound-vision carrier spacing is 5.5 Mc/s in the Australian 625-line system, 4.5 Mc/s in the American 525-line system and 6.5 Mc/s in the Eastern European 625-line system; and all use f.m.) The footnotes in the letter are inserted by myself.

Mr. Petersen writes: "... Here in Australia I have put a considerable amount of effort into this same field. One of my main reasons was an unquenchable desire to come to grips with t.v. This was because the closest t.v. station to my location was 1,000 miles away.

"You will, of course, realise that conditions here are vastly different from those in Europe for Dx t.v. Firstly, the lowest

frequency channel in Australia is Channel 2 (63-70 Mc/s)<sup>1</sup> yet I have had some quite remarkable reception from four of our Eastern Australian stations, particularly Melbourne (1,400 miles) and Adelaide (1,700 miles). This, of course, via the Sporadic-E layer during our midsummer months mainly. Other more rare periods of reception have been possible even at mid-winter.

"Now on the more favourable lower frequencies I have to depend on t.v. stations 5,000 miles away to experiment with. Russian, Chinese, Korean, Hawaiian, as well as the 'local' Australian have been received.

"The receiver used is an Australian H.M.V. 23-valve 21-in, now almost three years old but recently modified by replacing the tuner with the latest type using frame grid valves. I give this all the help possible with good antennas. For the Australian Channel 2 I use a double-stack 10 element yagi. To cover the various Asiatic and Pacific t.v. signals and other v.h.f. transmissions a single big 10 element yagi is used, cut to favour our proposed Channel 1 (49-56 Mc/s).<sup>2</sup>

"Unfortunately, in spite of all this and even though signal strength from Russian and Chinese 49.75 Mc/s t.v. is quite remarkable at times, they are too often marred by a multitude of Japanese hams on 6 metres in contact with each other and also with some of the Australian 6 metre hams. Another Korean f.m. programme link on 48.3 Mc/s comes in with tremendous strength and quality for the greater part of the year.

"I should mention here that a 625-line 50 f.p.s.<sup>3</sup> receiver requires only minor adjustment to accommodate 525-line 60 f.p.s. signals.

"I use a small v.h.f. beat oscillator to extract the necessary 5.5 Mc/s sound of my Australian set from the 6.5 Mc/s Russian/Chinese signals and the 4.5 Mc/s of the American system. This same oscillator does a great job when receiving f.m. v.h.f. sound transmissions. Even a.m. transmissions are received with quite good quality by the same means; in this case, however, the resultant frequency should favour one side of the ratio detector, thus producing sufficient unbalance to produce sound.

"At the time of writing the most important of my photographs and tapes are in the hands of various Australian Government departments engaged in v.h.f. propagation research."

<sup>1</sup> 64.25 Mc/s vision carrier; 69.75 Mc/s sound carrier.

<sup>2</sup> 50.25 Mc/s vision carrier; 55.75 Mc/s sound carrier.

<sup>3</sup> Fields per second. (Frames per second in English terminology.)

The latest letter we have received from Mr. Petersen describes how he was able to receive a national event (namely the funeral of the Governor-General, Viscount Dunrossil), from Melbourne before the programme came generally on the air from Brisbane, Adelaide, Perth and Hobart. Lack of relay facilities prevented these cities from providing an instantaneous transmission of the event.

In this last letter Mr. Petersen states also that he is now photographing from the screen with an 8mm movie camera (16 frames per second) with results which are most gratifying.

We are much indebted to Mr. Petersen for his comments, and we would be interested to hear of any other instances of long distance t.v. reception. Where possible, details of such reception may be published in future issues.

#### Phonetic Alphabet

Another Australian reader (we seem to be getting very popular in that part of the world!), Mr. G. D. Clark, of Victoria, has passed on some comments concerning the joke alphabet I mentioned recently.

"I was very interested in the phonetic alphabet which you included in *The Radio Constructor* for December. I can remember learning this alphabet from a gramophone record about 35 to 40 years ago. There were certain topical references which would be lost on the younger generation; in my case there are some that I cannot remember but, for what they are worth, here are some variations and additions.

C for Highlanders	D for Ential
E for Adam	I for Novello
K for Ancis	N for a Dig
U for Films	W for a Bob

"Thank you for a very interesting column, and long may you continue to write it."

And I certainly agree with the last sentiment!

#### Build the "Malash" 5-Transistor T.R.F.

The monthly Soviet technical magazine *Radio* covers rather a wide range of subjects, these varying from articles (which may be fairly advanced) on general and topical electronic subjects to ham techniques and home-constructor projects. A recent issue features a receiver which appears to be simple and neat in design, and a few words about this may be of interest, especially if they reflect the Russian home-constructor scene.

The receiver (described by M. Romyantzi) is called the "Malash" (approximately "Tiny Tot") and it employs five p.n.p. transistors



in a simple t.r.f. circuit. All transistors are connected in the earthed emitter mode. The single-band aerial input stage employs a ferrite frame, one winding of which is tuned by a 10-450pF variable condenser. This is the only tuning control in the receiver. A coupling winding on the ferrite frame connects to chassis via a 6,800pF condenser and to the base of the first transistor via a 470Ω resistor. The collector of the first transistor then connects to the primary of an iron dust or ferrite cored transformer, the secondary of which couples into a conventional series diode circuit. This transformer is small in size and is not tuned in any obvious way, although it may well, I suppose, be self-resonant at some point in the frequency band covered. After the diode we have an a.f. transistor, followed by the third transistor. This drives the output transistors via an a.f. transformer with a centre-tapped secondary. The two output transistors work in conventional push-pull manner (emitters to chassis in this case, and bias via the a.f. transformer secondary), and their collectors connect direct to the two outside terminals of the centre-tapped speaker voice coil. The whole receiver is powered by a 4.5 volt battery.

Several components in the circuit provide top-cut. There is, for instance, a 6,800pF condenser between the base of the second transistor (that immediately following the diode) and chassis; although this may also provide an r.f. circuit for the diode. A 510pF condenser is connected between the collector and base of the driver transistor. Finally, a 3,000pF condenser is connected across each half of the speaker voice coil.

There is no stabilising in the receiver and circuitry is economic, there being eight resistors and eight condensers (including the tuning condenser). The whole receiver is mounted on a printed circuit board.

The receiver has one control only, the tuning condenser. This is operated by a large knurled disc which carries a projection at one point. When set to full capacity this projection operates a pair of contacts which switch off the receiver. The disc carries a set of numbers ranging from 344 to 1734, which are viewed through an aperture in the cabinet. If these are kc/s, the range of the receiver would be some 173 to 872 metres. Such a wide range is feasible, considering the lack of stray capacities across the tuned circuit.

It would seem that rechargeable batteries are used with the receiver, because a separate drawing illustrates a simple charging device. This consists of a two-rectifier circuit in series with an 0.01μF condenser. These components are mounted in a plug which connects to the 127 volt a.c. mains supply. The condenser

limits the a.c. current to the rectifiers, and the batteries receive their charge via two fly-leads.

#### News in Brief

The Royal Air Force has formed a Tape Recording Society, which is affiliated to the Federation of British Tape Recording Clubs. The Society will provide a link between recording clubs on R.A.F. stations at home and overseas. Events of interest, such as boxing, football, races, concerts, etc., will be taped and the recordings circulated. One of the declared aims of the Society is to provide a service for hospital patients, blind persons and other handicapped people. Membership is open to past and present members of the R.A.F., the W.R.A.F., Princess Mary's R.A.F. Nursing Service, and to personnel of N.A.T.O. and Commonwealth air forces. I haven't the address of the hon. secretary of the Society at the time of writing, but I hope to pass it on next month.

Electrolube, that very well known contact cleaning fluid, is now available in an "aerosol" dispenser. You press a button on the container and the fluid is released in a fine spray. The Electrolube "aerosol" dispenser has been developed in response to many requests from British users, and enables the fluid to be sprayed directly on to working commutators, switches, and contacts, whereupon it combines the actions of loosening tarnish, lubricating and spark inhibiting. The new dispenser was demonstrated for the first time at the *Salon International des Composants Electroniques* in Paris during 17th to 21st February.

*Radial*, the official journal of the Radio Amateur Invalid and Bedfast Club, has a lively February issue which includes details of a parallel American organisation. London members of the R.A.I.B.C. have now set up a very successful 2 metre Net.

"The transistor portable that just went on and on." That is what happened with a Philips "Philette" which was badly damaged in a fire in Grimsby. The receiver continued playing whilst firemen tackled the blaze, even though much of the case melted, the tuning indicator dial disappeared and the control knobs were lost. Three weeks later the set was still working. It could not be switched off because the on-off switch was also melted! The set was then sent, merrily playing away, 160 miles through the parcel post to Philips Electrical Ltd., at Century House, W.C.2, where it still continued working uninterruptedly. A photograph shows the receiver with most of the top half of the cabinet melted away and part of the speaker and chassis completely exposed.

# GROUPBOARD TECHNIQUES

by IAN GARDNER

*Our contributor offers useful advice on constructional techniques with the latest groupboard methods of assembly*

SINCE THE INTRODUCTION OF MINIATURE and subminiature components—especially those designed for use in transistor circuits—increasing use has been made of groupboards for the building of equipment. These groupboards are made of various insulating materials and may have the circuit connections etched in copper foil on one side or they may be wired. Such groupboards may be used in conjunction with more conventional chassis forms, as sub-assemblies, or they may be mounted parallel and close to a front panel which is used to support any required controls, thus providing a very compact assembly.

#### Printed Circuit Groupboards

The materials used for printed circuit groupboards are generally either resin bonded paper (Paxolin), fibreglass or laminated plastic to which is bonded a sheet of copper foil about 0.002in thick.

By various processes, including one which may be carried out by the home constructor and for which a kit is available, the copper foil may be etched in such a way that separate conductors are formed. These conductors are usually of the order of 0.04in wide, having connection spots about 0.10in dia. between which components are mounted. Components are mounted on the opposite

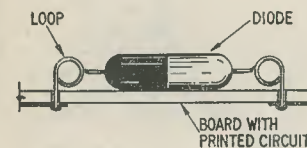


FIG. 1  
MOUNTING OF CRYSTAL DIODE ON PRINTED CIRCUIT BOARD

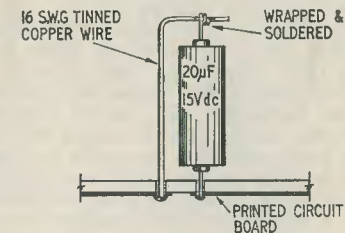


FIG. 2  
VERTICAL MOUNTING OF SMALL ELECTROLYTIC CONDENSERS

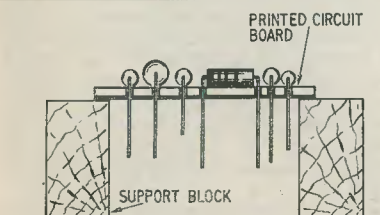


FIG. 3A  
PRINTED CIRCUIT BOARD ASSEMBLY — STAGE 1


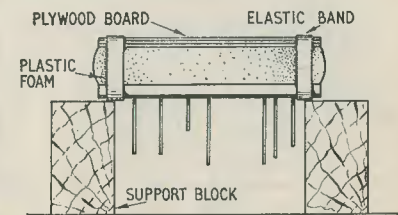



FIG. 3B  
PRINTED CIRCUIT BOARD ASSEMBLY — STAGE 2

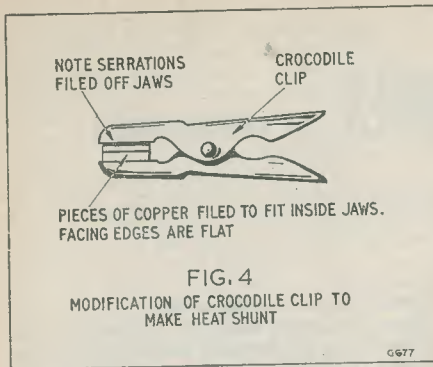

side of the board to the printed circuit. Resistors and condensers have their wire ends passed through holes drilled at the connection spots. With home-constructed boards, care should be taken to drill the holes through the centre of the spots (using a No. 52 drill, 0.0635in dia.) and to avoid tearing the copper foil from the board.

With commercially produced printed circuit boards, the hole spacing is normally such that the wire ends of resistors and condensers must be bent at 90° no closer than about  $\frac{1}{8}$ in from each end of the components. This arrangement should be maintained when designing printed circuit layouts.

Although special printed circuit valve bases are available, standard B7G and B9A valve bases may be modified easily by removing the fixing lugs and filing the connection spills to half their width. The valve base connection spots on the printed circuit board should then be drilled out to suit and a hole drilled in the centre to take the centre spigot of the valve base, which may then be connected to the nearest earth point.

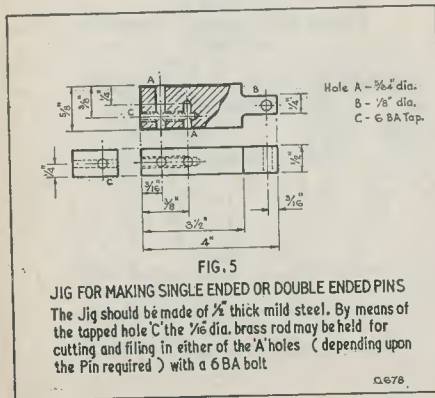


Crystal diodes should have their wire ends looped as shown in Fig. 1.

Transistors are best held in rubber or polythene sleeves which are glued to the board, the leads being insulated with coloured sleeving, this serving identification. The wire ends should be looped in the same manner as diodes.

In order to save space, small electrolytic condensers may be mounted vertically as shown in Fig. 2. It is advisable that such components should be mounted last.

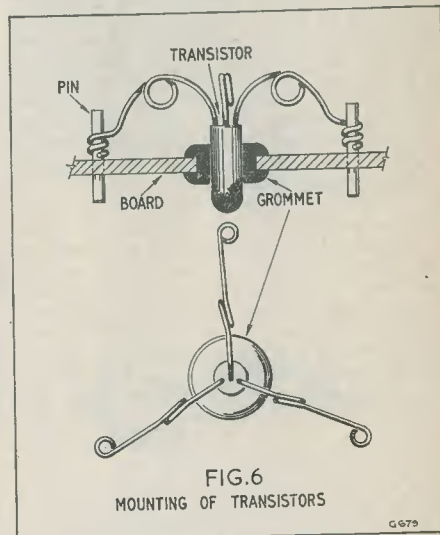Small transformers may be clamped or bolted to the board, their connections being made to the appropriate points with short wires. Large transformers are usually mounted on a metal chassis together with switches, potentiometers, etc., the printed circuit board being fitted as a sub-assembly.



### Soldering

It is convenient to do all the soldering at one and the same time. To support all the components neatly on the board, the following method has been successfully employed.

First clean up the printed circuit conductors by rubbing the board with a fine grade of wire wool.\* Tin all the wire ended components and bend the wires to 90° suiting the fixing hole positions. Assemble the components on the board, the latter being supported upon two blocks as shown in Fig. 3 (a).

When all the components are in place a piece of foam plastic about  $\frac{1}{8}$ in to 1in thick

\* Some commercially produced printed circuit boards have a coat of protective lacquer on the copper side which functions also as a flux. If such boards are in good condition, cleaning by abrasion should not be necessary.—Ed.

and a piece of  $\frac{1}{8}$ in thick plywood, which have been previously cut to the dimensions of the board, are placed as illustrated in Fig. 3 (b). Elastic bands are then slipped over the ends as shown so that the board may be turned over, the soldering completed, and the excess wire ends severed.

When soldering printed circuits, care should be taken to avoid overheating either the components or the copper conductors as the latter may tend to peel from the board. The minimum quantity of solder to effect a secure joint is required and a soldering iron having a small bit should be employed.

It is advisable to solder transistors separately in order to allow a heat shunt to be used. An easily made heat shunt using a crocodile clip and a spare soldering iron bit is shown in Fig. 4.

### Pin Type Groupboards

This type of assembly provides an inexpensive and neat method of building equipment in board form without the use of printed circuits. Materials used for these boards may be resin bonded paper, fibreglass or Perspex. Thicknesses may vary from  $\frac{1}{8}$ in to  $\frac{1}{4}$ in, a thickness of  $\frac{1}{8}$ in being generally used on account of its mechanical rigidity when heavy components are required to be mounted.

Large components are bolted or held by clips to the board, and resistors, condensers, etc., are supported between brass pins which may be of such a length that they protrude an equal length on each side of the board when in position, thus allowing components to be mounted on one side of the board and the wiring on the other. Shorter pins are also used when it is desired to have components and wiring on the same side, should an extremely shallow assembly be required.


Suitable pins for home constructed

boards may be cut from  $\frac{1}{8}$ in dia. brass rod using the jig illustrated in Fig. 5 to ensure uniform lengths. The pins are tapped lightly into holes which should be drilled with a No. 53 drill (0.0595in dia.) using the jig to support the board so that the hole "B" is directly below the hole drilled for the pin.

When designing a layout on this type of board pins should be spaced so that about  $\frac{1}{8}$ in of wire is left between the pins and the ends of components. Common pins may be used to link components in series or parallel but three wires should normally be the maximum for any pin. Adjacent pins should not be mounted closer than  $\frac{1}{4}$ in. A row of pins on one side of the board facilitates power supply and other connections.

Resistors and condensers should have their wire ends trinned and wrapped once round the pins before soldering.

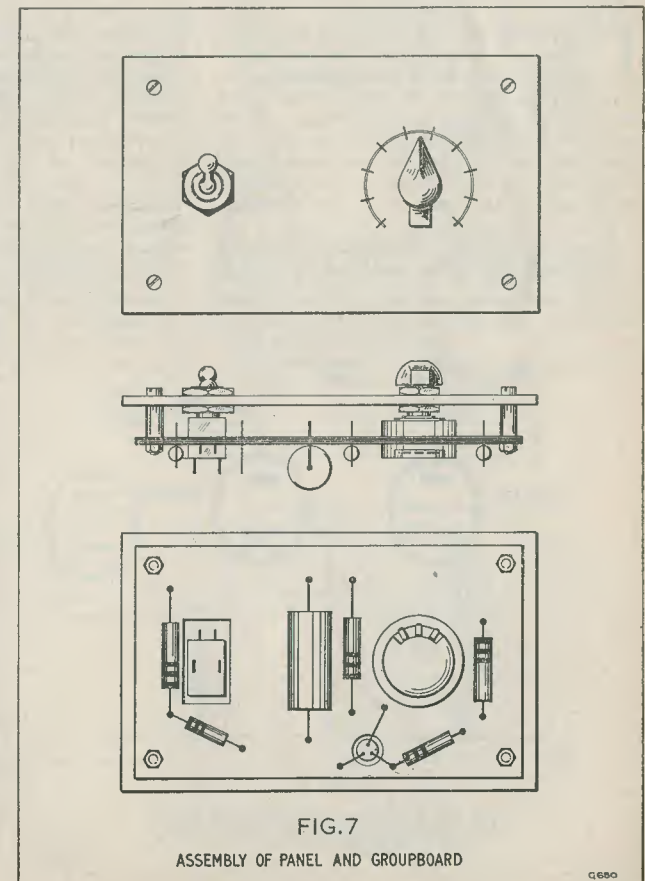Transistors should be mounted in rubber grommets with their leads sleeved and



brought out to pins as shown in Fig. 6. The leads should not be shortened but looped, and a heat shunt used when soldering.

Valveholders may be mounted as on a normal chassis or, by the use of suitable brackets, they may be mounted parallel to the board.

Before inserting pins into a drilled board, the component circuit references may be

marked or stenciled using black or white indian ink.

A typical groupboard assembly is illustrated in Fig. 7. The control panel supports a switch and a potentiometer and the groupboard is mounted upon spacers about  $\frac{1}{8}$  in behind the panel. The switch and potentiometer terminals are accessible through holes in the board.

## ELECTRONIC VIBRATO for Amplified Musical Instruments

by BRIAN L. PHILLIPS



THE READER WILL BE FAMILIAR WITH THE "vibrato" effect used on electronic organs, from the massive Hammond to the small Clavinoline, as well as with the present very popular electric guitar. There are various systems employed to give this effect, but they all produce the same desired result, namely, they modulate the incoming audio signal and give it a characteristic "beat".

In a large number of commercial designs a simple low frequency oscillator is used to

modulate the anode supply of an audio amplifying stage, thus varying the output of this stage at the rate of the oscillator frequency. Unfortunately there are one or two serious drawbacks to this system. The most important is that the oscillator is directly connected to the audio signal path (see Fig. 1); thus unless a high-pass filter is employed after this point, the oscillator signal will appear together with the audio signal at the amplifier output. This gives a most unpleasant "thumping" sound. Another drawback is that deep modulation of the signal is impossible without increasing the number of stages in the oscillator to obtain a large voltage change at its output.

Sometimes a multi-vibrator oscillator is employed and, under favourable conditions of operation, good results are possible; but invariably the early stages of the amplifier pick up the harmonics from the oscillator, which again appear in the output as "clicks".

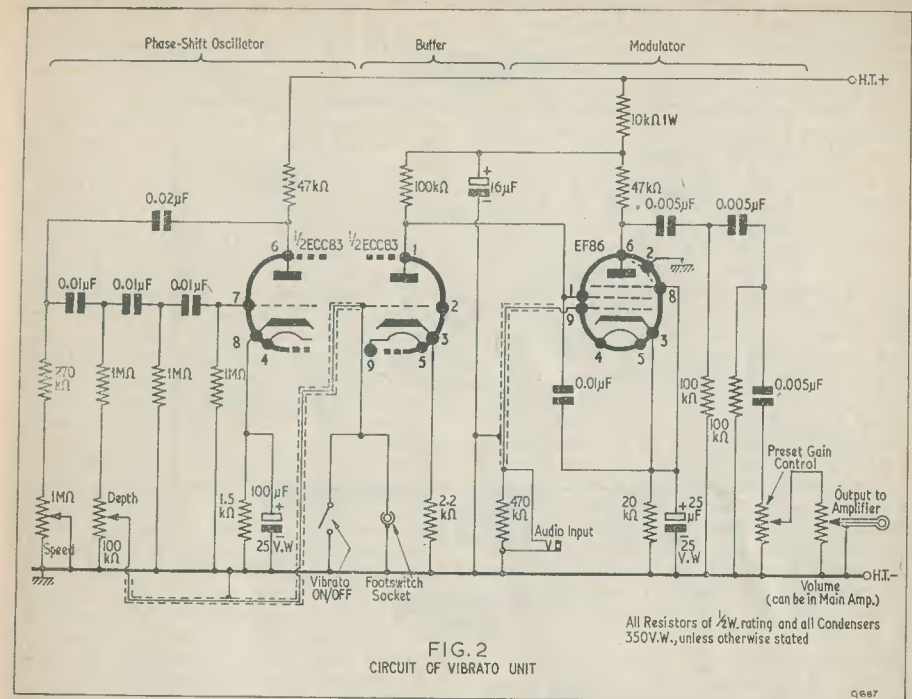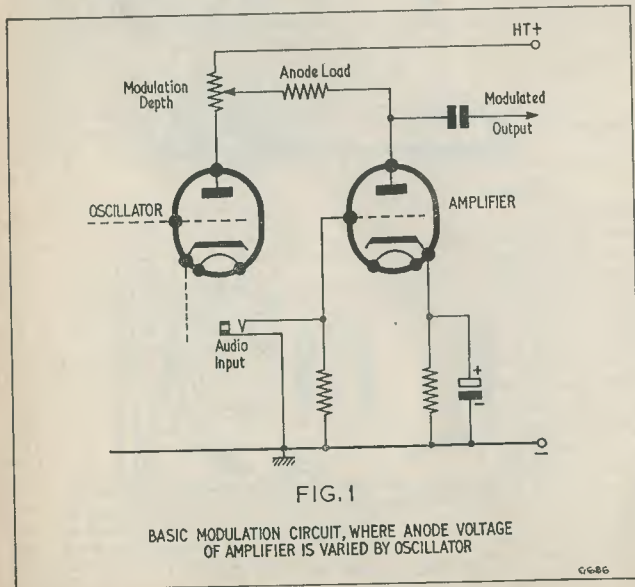The writer has, over the last three years, conducted extensive tests with electronic vibrato and the following circuits will be found to be free from undesirable traits.






### Circuit Operation

The unit, whose circuit is shown in Fig. 2, is connected between the input and the amplifier itself, since under low signal level conditions, it is very easy to modulate the audio before passing it on for normal amplification. No gain is given by the unit,

this being set up such that the output voltage is the same as the input, except for the modulation. It may be powered by the parent amplifier, or driven separately from the mains, whichever is required. Details are given for both methods.

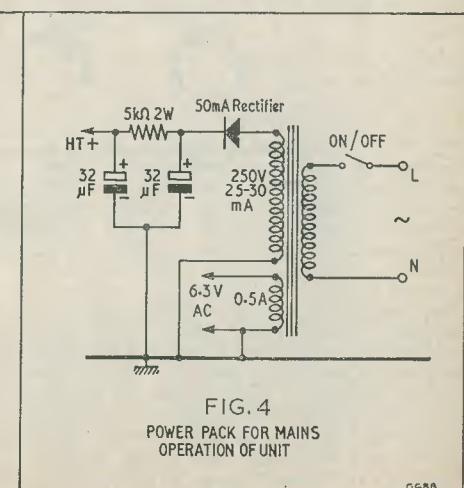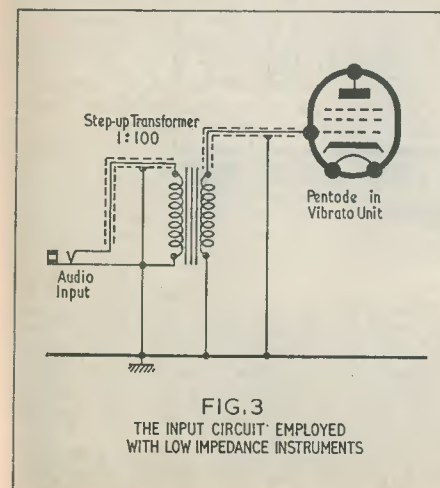The oscillator employed is the phase-shift



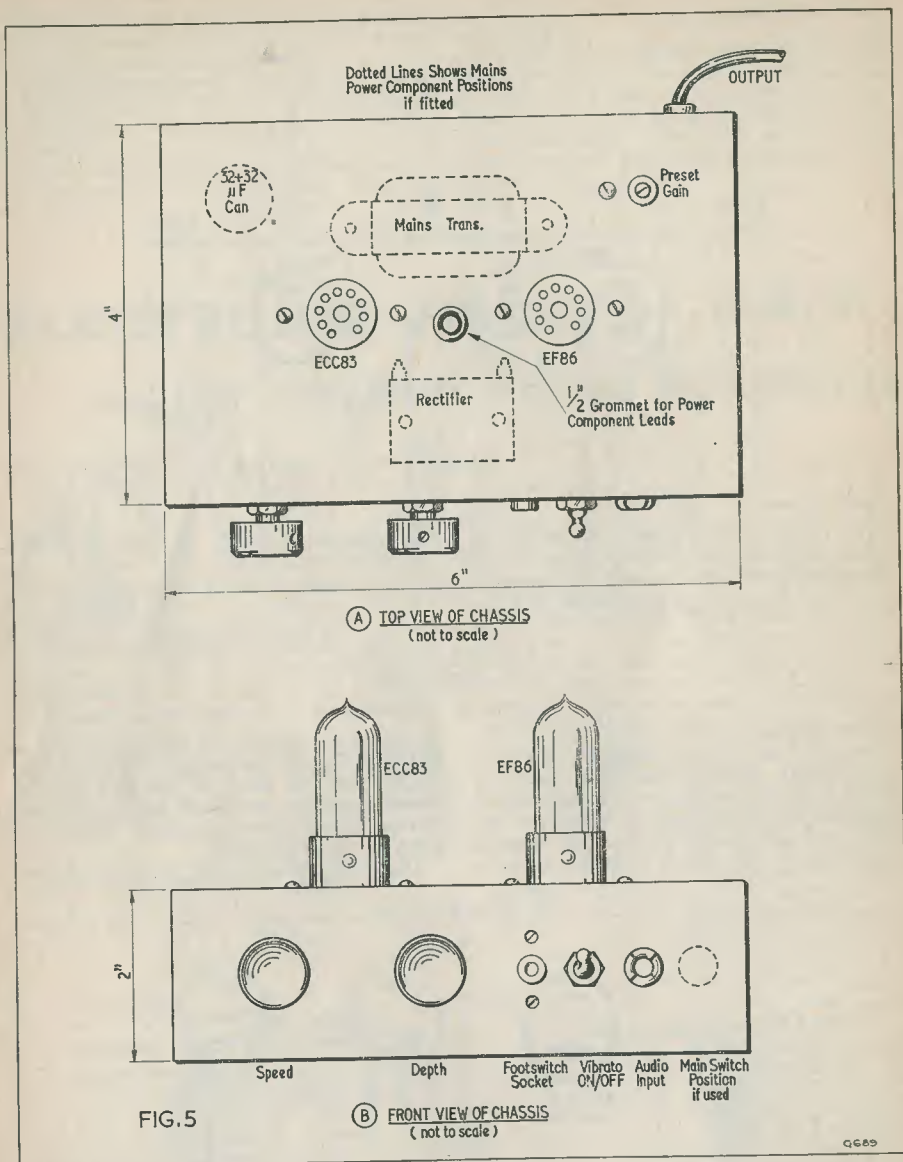

type, generating a very pure sine wave at between four and fifteen cycles per second. Oscillation is maintained by positive feedback between anode and grid via the phase changing network. The frequency of oscillation is controlled by the total time constant of this network, the variable element being one of the resistors, this giving a wide frequency or "speed" range. The output is

taken from a low potential point in the network by tapping into the "earthy" end of one of the other resistors. This avoids affecting the oscillator frequency; and, by making the lower portion of this resistor a potentiometer, a variable output or "depth" control is available.

This output is coupled to the control grid of a triode buffer stage which, apart from

isolating the oscillator from the rest of the unit, brings the oscillator output up to a level suitable for modulating the audio amplifier.

The modulated stage consists of a pentode, and the modulating voltage is injected into the screen-grid from the buffer anode circuit. As is well known, the gain of a pentode can be readily altered by varying the screen-grid voltage; and as this voltage is varying in sympathy with the oscillator frequency, the overall gain varies at this frequency. To improve this condition, a high level of bias is applied to the grid of the pentode by employing a high value of cathode resistor. Thus any audio signal applied to the pentode control grid will appear at the anode as a signal modulated at the same rate as the oscillator. To remove any oscillator fundamental from the output, a high pass filter is employed in the anode circuit. A pre-set gain control is also used at this point to set the overall gain at unity, so that the input to the parent amplifier is the same as if the unit were not in circuit. The gain control on the parent amplifier is used to alter the signal level. There is a coaxial socket for a foot-switch to operate the vibrato on and off, if required. Across this socket is a master on/off switch enabling the vibrato to be switched off from the unit itself if a foot switch is not available. The other socket is a closed circuit jack for the audio input. The output lead to the amplifier is permanently attached to the unit, the amplifier end of the lead terminating in a plug suitable for the input socket used, or, if the unit is made a permanent part of the amplifier, connected to the input within the amplifier.

#### Chassis

The layout of the unit is in no way critical, but screened lead *must* be used where indicated on the diagram to avoid hum pick-up. If the unit is to be used externally to an amplifier, it is best housed in a small box made either of sheet steel or, at least, 16 s.w.g. aluminium. Five ply-wood is also suitable. If it is to be mounted in the amplifier cabinet, then all that is required is a convenient corner where the chassis can be mounted and where the controls can be easily adjusted.

#### Safety Precautions

Some makes of amplifier used with musical instruments employ the a.c./d.c. technique of operation. To conform with safety standards the inputs to these amplifiers, and all external metalwork, have to be isolated from the mains supply. Some types employ isolating condensers, but the most frequently used method of isolation is to

couple the inputs to the first stage by 1:1 ratio transformers. As is well appreciated, "live" metalwork is not to be recommended on any mains operated equipment; least of all when the equipment will probably be used by somebody who knows little about mains polarity; so all external connections to an amplifier *must* be isolated.

If the vibrato unit is to be used with an a.c./d.c. amplifier it should be provided with its own power supply employing an isolating mains transformer. The only connection to the amplifier will then occur at the input terminals of the latter and, since these should be reliably isolated, there should be no direct connection between the mains and the chassis of the vibrato unit. If the amplifier employs an isolating mains transformer and its chassis is not connected directly to the mains, the vibrato unit may either draw h.t. and heater power from the parent amplifier, or be fitted with its own isolated power supply. When operated from the main amplifier, the h.t. positive connection is best taken from the h.t. rail just after the smoothing network, the negative side (chassis) being connected to the amplifier chassis near the input stages. A good thick earth connection between the two chassis is recommended to reduce hum effects.

When the input to the main amplifier is at low impedance it will be necessary to fit a step-up transformer (1:100) at the input to the vibrato unit, this employing the circuit shown in Fig. 3. This step-up transformer could be obtained from the main amplifier. The main amplifier will now require a 1:1 input transformer in place of the step-up transformer previously employed. Such a transformer *must* have insulation between primary and secondary, and between primary and core, which is fully suitable for mains isolation.

For separate mains operation, a suitable power pack is shown in Fig. 4, this consisting of an isolating transformer supplying 250 volts at about 25-30mA and 6.3 volts at 0.5 amp. A small pre-amplifier mains transformer is ideal. The rectifier is a contact-cooled type of 50mA rating. A conventional metal rectifier may, of course, be used if one is to hand. A suggested chassis layout is given in Fig. 5, and this can be employed in the "built in" version, or as the external unit; the only difference being that the latter will be mounted in a case or cabinet.


It is important to note that, if the vibrato unit chassis is fitted in the same cabinet as an a.c./d.c. amplifier, there must be no electrical connection whatsoever between the two chassis other than that between the vibrato unit output and the input terminals of the amplifier.

## USEFUL TRANSFORMER TIP

by S. G. Wood, G5UJ

FOR ANYONE NOT IN possession of a modulation transformer—often a not inexpensive item—the following tip may be of interest. Where a small modulation transformer is required, as in the case of a Top Band QRP transmitter, quite a useful alternative can be made up with two standard output transformers connected “back to back”. (See diagram.)

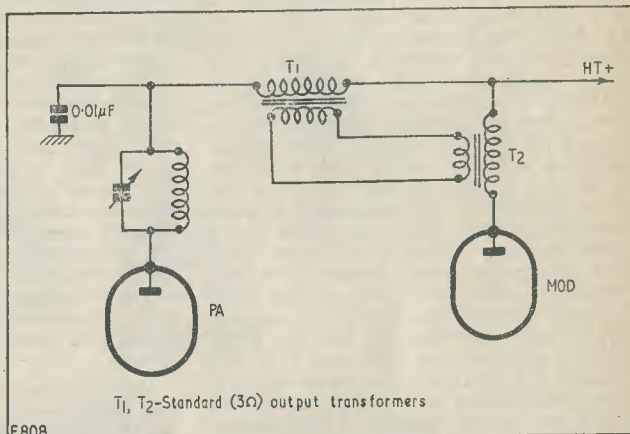These two transformers may conveniently be of the 3Ω variety. It will be appreciated that power in excess of 10 or 12 watts should not be used unless appropriate heavy duty components are employed (suitable transformers are often to be found in quality amplifiers and similar equipment).



Though by no means an original idea, a friend of the writer has used this particular system in a Top Band c.w./phone transmitter for several months, and has given results comparable in every way with an orthodox modulation transformer.

## BOOK REVIEW

**INTRODUCTION TO HI-FI.** By Clement Brown. 198 pages, 5½ x 8½ in. George Newnes Ltd. Price 21s.

In his preface to *Introduction to Hi-Fi* Clement Brown writes: “This book has been written by a music lover who hopes that his contribution to the cause of high quality sound reproduction will encourage others to take an interest in it.” This approach is maintained throughout the book, which deals in a very explanatory manner with all aspects of current high fidelity reproduction. The treatment is crisp and non-mathematical.

Mr. Brown commences with a chapter introducing high fidelity, and he ends with a look into the hi-fi world of the future. In between, the book covers records and pickups, amplifiers, radio tuners, loudspeakers, tape recording, stereo and listening room acoustics. Technical points in the text are clearly illustrated by diagrams and photographs. Also given is sound and practical advice on the purchase and installation of equipment. At the end of the book are several pages of useful data and a list of specially recommended recordings.

*Introduction to Hi-Fi* will be especially helpful to the novice, who will find that the subjects are covered clearly and carefully, without short cuts or any tendency towards “blinding with science”.

J.R.D.

# FREE

THIS BOOK WILL INTEREST YOU!

LEARNING  
the  
PRACTICAL  
WAY

**A NEW-PRACTICAL WAY  
of UNDERSTANDING**

## RADIO · TELEVISION · ELECTRONICS

Including: Transistors; VHF/FM; Hi-Fi equipment; Computers; Servo-mechs; Test Instruments; Photo-electrics; Nucleonics, etc.

**FOR ... Your Career ... Your Own Business ... An Absorbing Hobby ...**

Radiostructor—an organisation specialising in electronic training systems—offers a new self-instructional method using specially designed equipment on a “do-it-yourself” basis. You learn by building actual equipment with the big kits of components which we send you. You advance by simple steps, performing a whole series of interesting and instructive experiments—with no complicated mathematics! Instructional manuals employ the latest techniques for showing the full story of electronics in a practical and interesting way—in fact, you really have fun whilst learning! Fill in the coupon below, for full particulars—

# RADIOSTRUCTOR

**LEADS THE WORLD  
IN ELECTRONICS TRAINING**

## POST NOW

To RADIOSTRUCTOR (Dept. G.31)  
READING, BERKS.

Please send brochure, without obligation, to:

\* NAME .....

\* ADDRESS ..... 4.61

\*BLOCK CAPS PLEASE  
(We do not employ representatives)

# SCOTTISH INSURANCE CORPORATION LTD



38 Eastcheap  
London EC3

## TELEVISION SETS, RECEIVERS AND TRANSMITTERS

Television Sets, Receivers and Short Wave Transmitters are expensive to acquire and you no doubt highly prize your installation. Apart from the value of your Set, you might be held responsible should injury be caused by a fault in the Set, or injury or damage by your Aerial collapsing.

A "Scottish" special policy for Television Sets, Receivers and Short Wave Transmitters provides the following cover:

- (a) Loss or damage to installation (including in the case of Television Sets the Cathode Ray Tube) by Fire, Explosion, Lightning, Theft or Accidental External Means at any private dwelling-house.
- (b) (i) Legal Liability for bodily injury to Third Parties or damage to their property arising out of the breakage or collapse of the Aerial Fittings or Mast, or through any defect in the Set. Indemnity £10,000 any one accident.
- (ii) Damage to your property or that of your landlord arising out of the breakage or collapse of the Aerial Fittings or Mast, but not exceeding £500.

The cost of Cover (a) is 5/- a year for Sets worth £50 or less, and for Sets valued at more than £50 the cost is in proportion. Cover (b) and (ii) costs only 2/6 a year if taken with Cover (a) or 5/- if taken alone.

Why not BE PRUDENT AND INSURE your installation—it is well worth while AT THE VERY LOW COST INVOLVED. If you will complete and return this form to the Corporation's Office at the above address, a proposal will be submitted for completion.

NAME (Block Letters).....  
If Lady, state Mrs. or Miss  
ADDRESS (Block Letters).....

J/B

## Radio Control

FOR MODEL SHIPS, BOATS AND AIRCRAFT

by F. C. JUDD, G2BCX

To operate a model ship or aircraft is a most interesting hobby. But how much more fascinating it would be if one could emulate the skipper or pilot and remain in control after the model has been set off on its course. This, thanks to radio control, can now be done, and enthusiasm for it is steadily mounting. Radio Control for Model Ships, Boats and Aircraft has become a recognised handbook in this field.

144 pages 135 diagrams and illustrations

Standard Edition, art board cover, 8s. 6d. postage 6d.

## DATA PUBLICATIONS LTD

57 MAIDA VALE · LONDON W9

Telephone CUNningham 6141 (2 lines)

Telegrams Databux London

## Radio Control Mechanisms

by

RAYMOND F. STOCK

The first publication devoted entirely to the subject of radio control linkage mechanisms. Complementary to *Radio Control for Model Ships, Boats and Aircraft* and to other books on radio control.

64 PAGES ART BOARD COVER  
70 ILLUSTRATIONS

4/6 postage 4d.

ESTABLISHED



1865

Savings in this old established Building Society combine sound investment with an attractive return

# The Duchess of Kent Permanent Building Society

Members of the Building Societies Association

Shares are in units of £25 each (maximum Investment £5,000) . . . BUT, for the smaller saver, Subscription Share accounts may be opened with any sum from 1/- upwards. Interest is payable half-yearly on Fully Paid Shares—credited annually on Subscription Shares—all interest accrues monthly

Withdrawals at short notice

**INTEREST is at 3 $\frac{3}{4}$ % per annum**

(There is no deduction for income tax, as this is paid by the Society)

For further information apply to

MR. A. NEVILLE GILLMAN, F.C.A.  
DUCHESS OF KENT PERMANENT BUILDING SOCIETY  
103 Cannon Street London EC4  
Telephone MANSion House 8011

Please send to me, without obligation, free brochure and a copy of the audited statement of accounts. (I understand that I shall not be troubled with circulars or calls by representatives)

Name.....  
(If lady, please state Mrs. or Miss)

Address.....

R.C.

(Please use Block Capitals for both name and address)

"An essential piece of equipment..."

LOOK WHAT OWNERS WRITE OF THEIR INVESTMENT IN NEWNES RADIO AND TELEVISION SERVICING—  
 "More than repaid the cost in a short period," says E. J. S. (Wolvercote).  
 "One glance only was enough to convince me of its worth," writes J. F. B. (Leicester).  
 "The Free Technical Advisory Service is one more of many good reasons for having this set."—J. C. P. (Sutton).  
 "A boon and a must."—J. S. (Manchester).  
 "How fortunate I was in getting your servicing volumes."—I. K. (Leeds).  
 "More than pleased—will show these volumes to all my associates."—F. K. (St. Albans).

A—Fold along here

It costs you NOTHING to judge for yourself  
 Complete form at foot of page. Then fold at (A) and (B) and tuck (B) into (A) so that reply-paid portion with NEWNES address is shown. Final address is POST TO-DAY!

No Postage Stamp necessary if posted in Gt. Britain or Northern Ireland

Postage will be paid by George Newnes Ltd.

BUSINESS REPLY SERVICE  
 Licence No. W.C. 1129

GEORGE NEWNES, LIMITED  
 15-17 LONG ACRE,  
 LONDON, W.C. 99

B—Fold along here

Act-to-day for this certain money-maker

Send me Newnes RADIO AND TELEVISION SERVICING (in 7 Volumes) without obligation to purchase. I will return it in 8 days or send 15/- deposit 8 days after delivery, then fifteen monthly subscriptions of 20/-, paying £15. 15s. 0d. in all. Cash price in 8 days is £15.

For office use  
 RV

Name.....  
 Address.....  
 Occupation.....  
 Your Signature.....  
 (Or Your Parent's Signature if under 21) **RV. 139**  
 Free examination applies only in Gt. Britain and N. Ireland. Purchasers abroad should send the cash price plus 5/- for postage, packing and insurance.

Tick (✓) where applicable

House-OWNER	<input type="checkbox"/>
Householder	<input type="checkbox"/>
Living with Parents	<input type="checkbox"/>
Lodging Address	<input type="checkbox"/>

All the Servicing Data you need

- \* TELEVISION
- \* RADIO
- \* RADIOGRAMS
- \* CAR RADIOS
- \* TAPE RECORDERS
- \* RECORD REPRODUCERS

NEARLY  
**2,700**  
 POPULAR MODELS

**NEW**

**ALL THE CIRCUITS · DIAGRAMS  
SERVICING DATA · NEW REFERENCE  
DATA · YOU NEED FOR 1954-1961 POPULAR MODELS**

**IN NEWNES**

# Radio & Television Servicing

Here at call, any time, day or night, are the circuits and data you need for almost all the popular TV and Radio sets in use. In 7 volumes it is the only *complete library* of servicing data published, and worth its weight in gold! Never again will you look at a set and laboriously "work it out for yourself" or admit defeat. No more dealing with irate customers because, without data, you need to take their sets away for bench-work. You will be able in many cases now to do the job on the spot and keep customers happy . . . You'll find yourself doing two jobs where before you had time only for one! In these competitive days the time factor is all-important, as you know *to your cost*. If you've never seen previous editions, make sure of seeing this one—you pay nothing to prove its value for 7 days. Complete form on back NOW!

# 2,680 Popular Models

TELEVISION · RADIO · RADIOGRAMS · CAR RADIOS · TAPE RECORDERS · RECORD REPRODUCERS (Including Stereo)

Servicing Data for all these makes—  
Ace, Alba, Ambassador, Argosy, Armstrong, Baird, Banner, Beethoven, Berec, Brayhead, B.S.R., Bush, Capitol, Champion, Channel, Collaro, Cossor, Cydon, Danette, Decca, Defiant, Dynatron, E.A.R., Eddystone, Ekco, Elizabethan, E.M.I., Emerson, English Electric, Ever Ready, Ferguson, Ferranti, Ford Motor Co., Garrard, G.E.C., Gramdeck, Grundig, H.M.V., Invicta, K-B, McCarthy, McMichael, Marconiophone, Masteradio, Motorola, Murphy, Pageant, Pamperdio, Peto Scott, Philco, Philips, Pilot, Portadyne, Portogram, Pye, Telecommunications, Radiomobile, Rainbow, Raymond, Regentone, R.G.D., Roberts' Radio, Sobell, Sound, Spencer-West, Stella, Strad, Ultra, Valradio, Vidor, Walter, Webcor.

**PLUS 2 YEARS' FREE  
POSTAL ADVISORY  
SERVICE!**

**MORE THAN  
4,500  
CIRCUITS AND COMPONENT  
LAYOUT DIAGRAMS  
OVER  
4,425  
PAGES OF INFORMATION**

### LATEST DEVELOPMENTS

V.H.F. Transistors, A.M./F.M. Transistor Receivers, All-T-Transistor Car Radios, 4-track Tape Recorders, TV Push Button & remote controls, Automatic Contrast Controls, New Flywheel-sync. Circuit, Line Stabilization, 19in. and 23in. Tubes, Bright Spot Suppression, etc.


### TIME-SAVING HINTS

Printed circuit repairs, Chassis removal instructions, Data on picture tubes & replacement, Valve functions, Component values, Transistor data, Colour codes, Battery equivalents, Aerials, Interference, Valve & I.F. list for 800 older radios, Valve data and equivalents, BBC/ITVA stations, etc.

**IT'S YOURS ON 7 DAYS'**

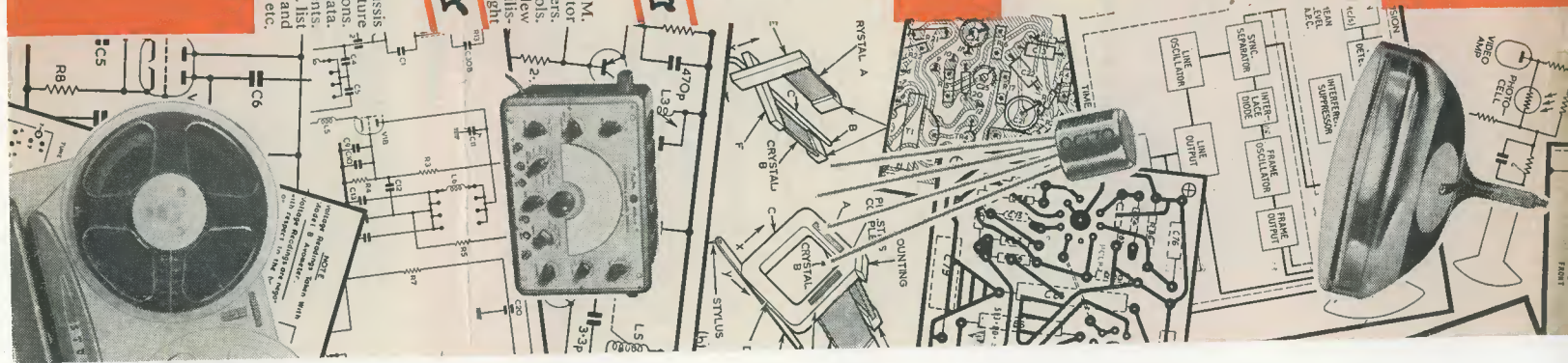**FREE TRIAL**

Send no money—simply fill up form overleaf and post leaflet to-day. The complete set is yours without cost or obligation to buy. The demand will be heavy so—**ACT NOW!**





# INTERNATIONAL SHORT WAVE LEAGUE

H.Q.—12 GLADWELL ROAD  
LONDON N8 ENGLAND

*THE LARGEST S.W.L. ORGANISATION IN THE WORLD*

Membership 21s. 0d. per annum (U.S.A. \$3.00) including 12 monthly issues of *Monitor*—the League journal. Including free use of all Services, QSL Bureau, etc.

Translation, Station Identification (Broadcast & Amateur), Technical Advice, Pen-Pal Bureau and other services. QSL Bureau service free for both directions. Certificates, Awards and Trophies. *Monitor* is a monthly magazine reviewing both Broadcast and Amateur activities. DX Contests held regularly.

League supplies include Badges, headed notepaper with matching envelopes, QSL cards overprinted with member's address and identification number, report pads, etc., etc.



## NEW SURPLUS ... BY RETURN

1L4	3/6	6K8M	9/-	12SK7M	5/-	ECC84	8/6
1R5	6/-	6H6M	2/-	12SQ7M	8/6	ECH42	10/6
1S5	6/-	6L6G	7/-	35Z4G	8/6	EF36	2/6
2A3	8/6	6L6M	9/-	35Z4G	5/-	EF39	3/6
2X2	2/6	6L7M	8/6	42	7/6	EF50	1/6
3A5	5/6	6Q7G	7/6	50L6GT	9/6	EF50(S)	2/6
3Q4	5/6	6Q7GT	9/-	80	6/6	EF91	3/-
5R4GY	9/6	6S17M	5/6	446A	10/6	EL32	3/-
6AC7M	4/-	6SL7GT	5/6	830B	8/6	EL41	9/6
6AK5	5/-	6SN7GT	4/-	959	5/-	EM80	9/6
6AL5	3/-	6ST7M	5/-	1629	4/-	GZ32	10/-
6AM6	3/-	6V6G	7/6	5763	10/6	KT33C	6/6
6AU6	6/-	6X4	5/6	AR8	3/-	PCC85	9/-
6B8G	2/6	12A6M	5/-	DET24	10/-	PCF82	7/6
6BA6	6/-	12AT6	7/-	DF73	4/-	PEN25	4/-
6BH6	5/6	12AU6	6/6	DL70	4/-	PY80	6/6
6B16	5/6	12AU7	6/6	EA50	1/6	PY83	6/6
6F32	2/6	12AX7	6/6	EAC91	3/-	TT11	3/-
6F6M	5/6	12BE6	7/6	EAF42	8/6	U25	12/6
6J5M	5/-	12CBM	7/6	EB91	3/-	UAF42	9/6
6J6	3/6	12K7G	5/-	EBG33	5/-	VLS631	10/-
6J7G	5/-	12Q7G	5/-	EBF80	7/6	VP23	3/-
6K7G	2/-	12SC7M	2/6	ECC82	6/6	VR150/30	7/6
6K8G	5/-	12SJ7M	5/-	ECC83	6/6		

Post and Packing 6d. per valve. Free over £2.

**TAPE DECKS**—BSR Monardeck. Brand new and boxed, only £8.0.0 each, plus 3/6 carr.

**BRAND NEW B9A MOULDED VALVE-HOLDERS**. Fully Screened, only 11/6 doz. Micalux ditto 13/6 doz.


**SPECIAL VALVE OFFER**. Any 12 for £1 (plus 2/6 p.p.). EF91, EB91, EL32, TT11, EF50(S), 6AM6, 6AL5, 6B8G, 6F32, 1626, 1629, 616, AR8, VP23, 2X2, 6K7G, S.A.E. ENQUIRIES

## JOHN ANGLIN

385 CLEETHORPE ROAD GRIMSBY LINCOLNSHIRE  
Telephone 56315

**12" Speaker and 5" Tweeter with coupling condenser** by leading maker, 75/-. Less than half list price.  
**Mains Transformers**. Input 200/250V. Output tapped 3 to 30V 2A or 5, 11, 17V 5A. Each 24/6.  
**F.W. Metal Rectifiers**. 12/6 volt 1A, 7/6; 3A, 13/-; 4A, 17/6; 6A, 27/6; 24V 2A, 23/6.  
**Mains Transformer and Rectifier**, giving 12V 1A d.c. output, 19/6; 30V 2A, 33/6.  
**Relays**. We hold large stocks. Any contact combination and operating coil voltage supplied from 5/-.  
**Special Offer**. 12V relays with 2-make contacts, 6/-; 2 for 11/6; 3 for 16/6; 4 for 21/-.  
**Key Switches** from 3/-.  
**Toggle Switches d.p.d.t.**, 3/6. **Micro Switches**, M. & B., 5/6.  
**Nickel NiFe Batteries**. 1.2V 2.5A. Size 3" x 2 1/2" x 1". Practically everlasting, 6/-; or 3 for 16/-; 4, 21/-.  
**Army Morse Keys**, 3/6, 6/- and 8/6.  
**H.S. Twist Drills**. Set 7, 1/4"-1/2", 4/-; also full size in Plastic Wallet, 6/-; Set of 13, 9/6, and 17, 15/6, 1/4"-3/8".  
**Tubular Hacksaws** (Eclipse type), 11/9.  
**5" Side Cutters**, 5/6. **5" Plated Round Nose Tapered Pliers**, 5/6. **Pocket Neon Testers** with retractable screwdriver, 5/-; **7" Flat Nosed Tapered Pliers**, 8/6.  
**New 12" Speakers** (list £12.12.0), £6.17.6.  
**Paxolin Panels**, 12" x 6" x 1/2", 3/6.  
**Hi-Fi Crystal Microphones**, 15/6.  
**Studio "O" Cartridges**, 18/-.  
**Finest Quality Recording Tape**. 5 1/2" spools, 850ft. 19/-.  
**Bench Hand Grinder**, 6" x 1" stone, 35/-; 5" x 1" 31/6.  
**Bench Vice** with clamp, 2 1/2" jaw, 15/6.  
**12V Miniature Relays**, 1 1/2" x 1 1/2" x 1". Wgt. 1 1/2oz. S.P.C.O., 8/6. S.P.C.O. and 3m. 9/6.  
*All items post paid, new and guaranteed*

**THE RADIO & ELECTRICAL MART**  
BOX 9 G.P.O. TUNBRIDGE WELLS KENT

Post orders only to  
  
**THE RADIO & ELECTRICAL MART**  
 BOX 9 G.P.O. TUNBRIDGE WELLS KENT

THE RADIO CONSTRUCTOR

# BARGAIN OFFERS

For the Constructor!

## TAPE RECORDER

Manufacturers' brand new, current production offer. Latest 5-valve circuit based on Mullard's famous design. Magic eye level indicator. Volume and tone controls. T.C.C. printed circuit already wired. Only power pack and controls to assemble and wire. Valves EF86, ECC83, EL84, EM84 and EZ80. A sensitive quality recorder at Special Unit Prices.



Wired printed circuit amp. control panel, knobs, etc. ... £4.15.0. P. & P. 2/-  
 4 valves ... £1.17.6 P. & P. 1/-  
 Power pack inc. EZ80 ... £1.18.6 P. & P. 2/6  
 B.S.R. Monardeck tape unit ... £8.10.0 P. & P. 4/6  
 Illust. handbook, circuit diag., etc. ... 2/6  
 Complete 4-unit kit ... Bargain £16.10.0 carr. 7/6  
**COLLARO KIT**—Modified kit version of above, for 3-speed Collaro Studio Transcription Deck, with freq. compensated switching, etc., now available for £5.10.0 extra. Send for Bargain Lists—Leaflet 3d. stamp. Contemp. cabinets available at bargain prices.

## RECORD PLAYER BARGAINS

All brand new latest 4-speed Models—fully guaranteed. **Single Players**—B.S.R. (TU9) with "FUL-FI" P.U. 90/- Garrard 4 S.P. with GC8 Crystal £6.17.6. Garrard TA Mk. 2 with Plug-in GC8 Head £7.19.6. Garrard 4HF Transcription Unit £17.19.6 Carr. 3/6 **Auto Changers**. New reduced prices.—B.S.R. (UA8) £6.15.0. UA8 Stereo £7.10.0. UA14 £7.19.6. Collaro Conquest £7.15.0. Carr. 4/6.

## SPECIAL—NEW RELEASE

**Garrard RC210**. New 4-speed Autochanger Model with all the latest features and GC8 Plug-in Head, wired for Stereo. Bargain 10 gns. Carr. 4/6.  
**EM1 4-speed Single Player** with Auto Stop/Start Dual Turnover Cartridge for Stereo and Monaural L.P. and 78—Bargain Buy at £6.19.6. Carr. 3/6.

## REGUNNED TV TUBES

Prices Reduced Again!

New Heater, Cathode and Gun Assembly fitted to all tubes, and now re-screened and aluminised at no extra cost!

12" £5 14" £5.50 17" £5.10.0

Mullard and Mazda types ex-stock carr. and ins. 10/- 10/- part exchange allowance on your old tube. 12" tube allowance 5/-

## RECORDING TAPE BARGAINS

**SPECIAL PURCHASE**. Famous American manufacturers. 1st grade tape in brand new sealed boxes.

Standard Long Play

5", 600ft ... 15/- 900ft ... 19/6  
 5 1/2", 900ft ... 16/6 1,200ft ... 22/6  
 7", 1,200ft ... 21/- 1,800ft ... 32/-

Plastic Tape Reels, special offer. Manufacturer's surplus. 3" 2/6, 5" 3/-, 5 1/2" 3/3, 7" 3/6.

## VALVES—New Reduced Prices—All Guaranteed

1T4	6/-	DK96	9/-	ECL82	10/6	EZ80/81	7/6
1R5, 1S5	7/6	DL96	9/-	EF80	8/-	MU14	9/-
3S4, 3V4	7/6	EABCB8	8/6	EF86	12/6	PCC84	9/6
5Z4	9/-	EF89	9/-	EF91	5/-	PCF80	9/6
DAF96	9/-	ECC85	11/6	EL84	8/6	PCL83	12/6
DF96	9/-	ECL80	10/6	EY51	9/6	PL81	12/6
				EY86	10/-	U25	12/6

**TRANSISTORS**—BVA 1st grade—ex Mfrs. Mazda XA102, 16/6; XA101, 14/6; XC101, 10/6; OC70, 9/6; XB102, 10/-; XA103, 15/-; XA104, 18/-; OA70, 2/9. Hours 9 a.m.—6 p.m., 1 p.m. Wed.

TRS

Est. 1946

## RADIO COMPONENT SPECIALISTS

70 Brigstock Road Thornton Heath Surrey Telephone THO 2188  
 Terms C.W.O. or C.O.D. Post and Packing up to 1/6. 7d., 11b, 1/1, 31b, 1/6, 51b, 2/-, 101b, 2/9

## "6 plus 1" TRANSISTOR RADIO KIT UNBEATABLE VALUE!

One of the season's outstanding bargains in Portable Transistor Radio Kits. A modern, sensitive Receiver Unit with latest features. 6 transistors and 1 diode, printed circuit, Med. and Long waves, ferrite aerial, car radio input, push-pull output into 3 ohm speaker, calibrated dial and slow motion tuning, etc. Size approx. 7" x 2 1/2". Kit (included printed circuit and all components) ... £5.5.0 P. & P. 2/6



Set of 6 transistors and 1 diode £2.5.0 P. & P. 6d.  
**Complete Kit—Bargain Offer**—  
 ONLY ... £6.19.6 P. & P. 2/6

3 ohm speaker only required ... From 17/6  
 Send for leaflet (3d. stamp) and judge for yourself!

**COAX 80-OHM CABLE**. Now only 6d. per yd. High grade low loss. Aeraxial air-spaced Polythene Coax—famous manufacturer—standard 1/2" diameter bargain prices. 20 yds. 9/-, P. & P. 1/6; 40 yds. 17/6, P. & P. 2/-; 60 yds. 25/-, P. & P. 3/-. Special lengths. Coax Plugs 1/-, Coax Sockets 1/-, Couplers 1/3. Cable end sockets 1/6. Outlet Box 4/6.

**VOLUME CONTROLS**—5k-2 Megohm. ALL LONG SPINDLES, MIDGET TYPE, 1 1/2" diam. Guar. 1 yr. LOG. OR LIN. ratios less sw. 3/-, D.P. sw. 4/6. Twin gang stereo controls log. or linear less sw., 1/6. With d.p. sw. 8/-.

**CRT. HTR. ISOLATION TRANSFORMERS**  
 New improved types, low capacity, small size and tag terminated, a.c. 200/250V. Secondaries nil, +25%, +50% BOOST for 2V, 4V, 6.3V, 10.5V, 12V or 13V tubes. Each type 12/6 each. P. & P. 1/6.

## JASON FM TUNER UNIT KITS (87-105 Mc/s)

**Standard Model (FMT1)**—as previously extensively advertised. Complete Kit—5 gns. P. & P. 2/6. Set of 4 spec. valves now only 20/-.

**Model FMT2**—attractively presented shelf mounting unit in enclosed metal cabinet with built-in power supply. Complete Kit £7. P. & P. 3/6. Set of 5 spec. valves, 37/6.

**Latest Model—JTV2**—Switched Band 1-2-3 AM/FM Unit with AFC. Kit £12.19.6. P. & P. 2/6.

**Tuner Coil Set, IFs and Ratio Detector, etc.**, 26/-.  
**New Jason Comprehensive FM Handbook 2/6**, post free. 48-hr. Alignment Service, 7/6. P. & P. 2/6.

**CONDENSERS**—Silver Mica. All pref. values, 2pF to 1,000pF, 6d. each. Ditto ceramics, 9d. each. Tubulars 450V T.C.C., etc., 0.001-0.01μF and 0.1 (350V), 9d. each, 0.02-0.1/500V, 1/- each, 0.25 Hunts 1/6, 0.5 T.C.C., 1/9, 0.001 6kV, 5/6, 0.001kV, 9/6.

**RESISTORS**—Full range 10 ohms—10 megohms 20% 1/4W and 1/2W 3d., 1/2W 5d. (Midget type modern rating). 1W 6d., 2W 9d., 10% Hi-Stab. 1/2W 5d., 1W 7d. 5% 1/2W 9d., 1% HI-STAB., 1/2W 1/6 (10-100 ohms 2/-).

**LOUDSPEAKERS**—P.M. 3 ohms, 2 1/2" E.M.I. 17/6, 3 1/2" Goodmans 18/6, 5" R. & A. 17/6, 6" Celestion 18/6, 7" x 4" Goodmans 18/6, 8" Rola 20/-, 10" R. & A. 25/-, 12" Plessey 30/-, etc.

**TYGAN FRET** (contemporary pattern)—12" x 12" 2/-, 12" x 18" 3/-, 12" x 24" 4/-, etc.

**SPEAKER FRET**—Expanded bronze anodised metal 8" x 8" 2/3, 12" x 18" 3/-, 12" x 12" 4/6, 12" x 15" 6/-, 24" x 12" 9/-, etc.

## SMITH'S of Edgware Road BLANK CHASSIS

Precision made in our own works from commercial quality half-hard Aluminium. Two, three or four sided.

### Same Day Service

of over 20 different forms made up to YOUR SIZE. Order EXACT size you require to nearest  $\frac{1}{16}$ " (maximum length 35", depth 4").

Specials dealt with promptly.

### SEND FOR ILLUSTRATED LEAFLET

Or order straight away, working out total area of material required and referring to table below, which is for four-sided chassis in 16 s.w.g.:

48 sq. in.	4/-	176 sq. in.	8/-	304 sq. in.	12/-
80 sq. in.	5/-	208 sq. in.	9/-	336 sq. in.	13/-
112 sq. in.	6/-	240 sq. in.	10/-	368 sq. in.	14/-
144 sq. in.	7/-	272 sq. in.	11/-	and pro rata	
Post 1/3		Post 1/6		Post 1/9	

Discount for quantities. Trade enquiries invited. Spray finish arranged for quantities of 25 or over.

**FLANGES** ( $\frac{1}{8}$ ",  $\frac{3}{8}$ " or  $\frac{1}{2}$ ") 6d. per bend.

**STRENGTHENED CORNERS**, 6d. each corner. **PANELS**. The same material can be supplied for panels, screens, etc. Any size up to 3 ft. at  $\frac{4}{6}$  sq. ft. (sq. in.  $\times$   $\frac{1}{4}$ d.). Post, up to 72 sq. in. 9d., 108 sq. in. 1/3, 144 sq. in. 1/6, 432 sq. in. 1/9, 576 sq. in. 2/-.

## H. L. SMITH & CO. LTD

287/289 EDGWARE ROAD LONDON W2

Telephone PAD 5891/7595

## REPANCO

## TRANSISTOR AMPLIFIER AND FEEDER UNIT CIRCUITS

Envelope of theoretical and practical layout diagrams for:

- 350/500 milliwatt Transistor Amplifier
- Simple TRF Band Pass Feeder Unit
- Medium wave TRF Feeder Unit with R.F. Stage
- Medium and Long wave Unit with R.F. Stage
- Medium and Long wave Superhet Feeder Unit
- Microphone Pre-amplifier

Send now 2/- (post free) for envelope

## Radio Experimental Products Ltd

33 Much Park Street Coventry

## LEARN RADIO and T.V. SERVICING for your own business/hobby

by a new exciting no maths system, using practical equipment recently introduced to this country

FREE BROCHURE FROM  
**RADIOSTRUCTOR**  
Dept. G103 Reading Berks. 4.61

### Transistor Components

Superhet AM Feeder Unit or Pocket Receiver only  $4\frac{1}{2}$ " x  $3\frac{3}{4}$ " x  $1\frac{1}{2}$ ". Total cost £5.10.0. Constructor's booklet and circuits 1/9.

"Weyrad" Transistor Receiver, Long and Medium wave. All components including Cabinet £8.17.6. Constructor's booklet 2/-.

"Mighty Atom" Single transistor, Long and Medium (Top-band also) as described in Bernard's No. 4 Transistor Circuit Manual. Circuit and Assembly Drawings 3d.

All components direct from manufacturers Send S.A.E. for shopping lists.

## WESTHAM RADIO SUPPLIES

Rear of 176 Abbotsbury Road,  
WEYMOUTH, Dorset.

## The Radio Constructor Bound Volumes

Attractively bound in blue cloth  
with gold-block spine

Vol. 12, Aug. 58 to July 59 £15.0, p. 1/9

Vol. 13, Aug. 59 to July 60 £15.0, p. 1/9

Where all issues of a volume are returned for exchange 12s. 6d., p. 1/9

"Easibinders" for temporary or permanent binding 12s. 6d., p. 9d.

Please note: Indexes are available for Volume 13, price 6d., postage 2d. A limited number of indexes are also available for volumes 4, 6, 11, and 12 at the same price.

## DATA PUBLICATIONS LTD

57 MAIDA VALE . LONDON . W9

## SMALL ADVERTISEMENTS

Readers' small advertisements will be accepted at 3d. per word, including address, minimum charge 2s. Trade advertisements will be accepted at 9d. per word, minimum charge 6s. If a Box Number is required, an additional charge of 2s. will be made. Terms: Cash with order. All copy must be in hand by the 12th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the bona fides of advertisers.

### PRIVATE

**FOR SALE:** Goodmans Stereophonic bowl loudspeaker. Only used for half-an-hour. It does not match the room in appearance! £5.—Rankin, 4 Arden Grove, Harpenden, Herts.

**FOR SALE:** R.C.A. AR88 Model D. Perfect condition. £35. Ring RIC 5773 evenings.

**FOR SALE:** PCR2 with internal power pack, excellent condition, £7 10s., plus carriage. Viewmaster and Simplex t.v. components, tubes, valves, etc. S.A.E. for list.—Channing, Empire House, Wembdon Hill, Bridgewater, Somerset.

**FOR SALE:** Emiscope t.v. tube TA/15. New and unused. £5.—48 Mote Avenue, Maidstone, Kent.

**FOR SALE:** Rogers Junior, walnut cabinet, record space, Collaro transcription motor, B.J. arm Decca head, Wharfedale W12C/S, sand filled baffle. £45.—1 Manor Court, Grange Park Road, Leyton, London, E.10.

**FOR SALE:** Really t.v.i. proof 35 watt transmitter for 7, 14, 21 and 28 Mc/s. 6 x 19 $\frac{1}{2}$ in (rack mounting), 8 $\frac{1}{2}$ in. deep. 10 metered positions. Relay controlled v.f.o. in die-cast box. Worked 120 countries. Separate p.s.u. £12 complete. Numerous transformers, valves, condensers, etc., at give away prices. Send S.A.E. for list.—G3KRC, 24 Galley Lane, Barnet, Herts.

**WANTED:** Cheap 160 metre band transmitter. —Tupman, 47 Pullman Road, Wigston, Leics.

**FOR SALE:** H.F. Transceiver Model UF1. 60 to 75 Mc/s. Telephone handset. Service Chart. £5. R107 a.c. mains or battery. 17.5 to 1.2 Mc/s. Headset. S-Meter service chart. £10.—Owen, 151 Firs Lane, Winchmore Hill, London, N.21.

**FOR SALE:** *The Radio Constructor*, Vols. 4-13; *Practical Wireless*, Vols. 31-35. Clean, unbound. Best offer.—Brown, 30 Judd Road, Tonbridge, Kent.

**FOR SALE:** Brush Acoustical microphone BA106 and stand, 25s. New R.C.A. Photocell 931A, mount, resistor chain, 30s. Zeiss crystals, 31 Mc/s, 10s.; 468 kc/s, 5s. Simmonds bandpass crystal filter 465/0, 3 kc/s, 25s. New uncalibrated Turner 200 microamp meter 4 $\frac{1}{2}$ in square, 30s. AR88 wavechange switch, 10s. New UCH21, UBC21, UY21, UF21, 5s. each. 4in P8 aircraft compass, 25s.—155 Upper Shoreham Road, Shoreham, Sussex.

**FOR SALE:** "Minimobile" amateur top band transmitter (206-140 metres) 4 transistor/mic., 95s. 5 transistor portable radio, 65s. 6d. Bendix TA12 40 watt transmitter, 95s. All working well.—41 Newfield, Sandbach, Cheshire.

**FOR SALE:** One Taylor Model 55A wobblulator and Taylor 65C signal generator. Price £9 for the two.—J. C. Snell, Central Garage, Stairfoot, Barnsley.

### TRADE

**LEARN RADIO AND ELECTRONICS** THE NEW Practical way. Very latest system of experimenting with and building radio apparatus—"as you learn". FREE Brochure from: Dept. RC10 Radiostructor, 40 Russell Street, Reading, Berks.

**FREE FROM THE I.P.R.E.** Syllabus of famous radio and t.v. courses. Membership conditions booklet, 1s. Sample copy *The Practical Radio Engineer*, 2s. post free.—Secretary, 20 Fairfield Road, London, N.8.

continued on page 719

## EDDY'S (NOTTM) LTD

172 Alfreton Road . Nottingham

### NEW AND SURPLUS VALVES

Guaranteed and Tested—by Return of Post

B36	8/6	EF86	9/6	UBC41	7/3	6F33	6/6
CTC	7/6	EF89	7/-	UCH42	7/6	6J5G	2/9
DAF91	4/9	EF91	3/6	UL41	7/3	6J5GT	3/9
DF91	3/11	EF92	4/6	UL84	7/6	6J7G	5/-
DF96	6/11	EL41	7/3	UY41	6/3	6K7G	1/11
DL94	6/9	EL84	6/6	UY85	6/3	6K7GT	3/9
DK96	6/11	EL91	4/6	VP23	6/6	6K7M	4/3
DM70	6/9	EY86	7/9	1A7GT	11/9	6K8G	5/3
EABC80	7/6	EZ40	6/3	1CSGT	9/9	6Q7G	5/9
EAF42	8/6	EZ41	7/3	1D5	7/6	6SA7M	5/9
EB41	6/11	EZ80	6/-	1HSGT	9/6	6SG7M	5/9
EB91	3/6	EZ81	6/9	1N5GT	9/9	6SL7GT	6/6
EBF80	8/-	GT1C	6/11	1S5	4/9	6U4GT	10/6
EBC41	7/6	KT33C	6/6	1T4	3/11	6V6G	4/9
EB34	4/3	MU14	7/-	1L4	3/6	6V6GT	6/-
EBC33	5/11	PC84	7/3	3Q4	7/3	6X4	5/9
EBF89	8/6	PCF80	7/3	3Q5GT	8/9	6X5G	6/11
ECC35	6/9	PCF82	7/6	354	5/11	10F1	6/11
ECC81	5/3	PCL82	7/6	3V4	6/9	12A6	5/3
ECC82	5/11	PCL83	12/6	5Y3G	5/9	12AT6	7/6
ECC83	6/6	PCL84	12/6	5Z4G	7/6	12AT7	5/3
ECC84	8/3	PEN44	12/6	5Z4M	11/-	12AU7	5/11
ECC85	7/11	PEN36C	8/-	5U4G	4/9	12K7	5/3
ECP80	9/-	PEN46	7/6	6A7	10/-	12Q7	5/3
ECF92	9/-	PL81	9/-	6AG5	4/-	25L6GT	7/6
ECH42	7/9	PL82	7/-	6BA6	5/11	25Z4G	7/1
ECH81	8/3	PL83	7/-	6BE6	5/11	35L6GT	8/19
ECL80	7/6	PL84	10/11	6B16	5/11	35W4	6/3
ECL82	10/-	PY80	7/-	6B8G	2/11	35Z4	5/6
EF41	7/6	PY81	6/6	6C4	3/6	954	1/6
EF42	7/6	PY82	6/9	6C6	4/9	955	2/6
EF50	1/9	PY83	7/3	6CH6	9/-	956	3/-
EF80	5/-	U25	12/6	6F6M	7/-	80	7/6
EF85	5/11	UAF42	8/9	6F13	11/6	30F5	8/6

Any parcel insured against damage in transit for only 6d. extra per order. All uninsured parcels at customers risk. Post and Packing 6d. per valve extra. C.V.O. or C.O.D. only. C.O.D. charge 3/- extra. S.A.E. with enquiries.

**CAR RADIO.** 7 transistors Long & Medium waves. 2 watts output. R.F. stage & Auto Gain control. Size 7 $\frac{3}{4}$ " x 7 $\frac{3}{4}$ " x 2 $\frac{1}{2}$ ". 6 or 12V (state which) supplied with full instructions, 10 $\frac{1}{2}$  gns. Speaker 17/11 extra. P. & P. 5/-.

**POCKET RADIO.** 2 transistor with miniature speaker. Complete with all parts, wiring diagram & full instructions, 27/6. Batteries 1/-, P. & P. 2/6.

**VIBRATORS.** 12V 4-pin, 4/11. Post 1/-.

**HAND MIKES.** Carbon, 3/11. Post 1/6.

**SPEAKER GOLD GRILL.** 6 $\frac{1}{2}$ " x 4", 1/-, Post 6d.

**THROAT MIKES.** 1/- each. Post 6d. Super quality model, 2/- each. Post 9d. Could be used for electrifying musical instruments, etc.

**V.H.F. EXPANDING AERIALS.** Complete and easy to fit. No technical knowledge required, 6/11. Post 10d.

**CRYSTAL SETS.** Complete 2 wave bands, high gain, good quality, 19/11. Also with transistor amplifier, extra 9/11. P. & P. 2/6.

**HEADPHONES.** High resistance to suit above crystal sets, good quality, 13/11 pair. P. & P. 1/6.

**MORSE TAPPERS.** Plated contacts, adjustable gaps. Heavy duty, good quality. Special price, 3/6. Post 9d.

ALL ABOVE ARE NEW AND GUARANTEED

**BRASS, COPPER, DURAL,  
ALUMINIUM, BRONZE**

ROD, BAR, SHEET, TUBE, STRIP, WIRE  
3,000 STANDARD STOCK SIZES

No Quantity too small List on Application

**H. ROLLET & CO LTD**

6 Chesham Place SW1 BELGRAVIA 4300  
Also at Liverpool, Birmingham, Manchester, Leeds

Red Spot Transistors, 3/-; White Spots, 3/-; Yell./Gr., 3/6  
Ediswan XA102, 10/-; XA104, 9/-; XA103, 9/-; XA101,  
9/-; XB103, 8/6; XB104, 7/6; XC101, 9/-. **Special Bar-  
gain set for P.V. Superhet 6 Transistors (1-XA102, 2-  
XA101, 1-XB103, 2-XC101), plus diode, 47/6; New-  
market V15/10 P, 15/-; Diodes, 1/-, 2/6, 4/-; Transistor  
holders, 1/-; Ardente Trans. D239, 8/6; D240, 8/6; D131,  
10/-; D132, 10/-; Sub. Min. Electrolytics (15V) 2, 4, 8, 10,  
25, 50, 100µF, 3/-; 32µF, 2/9; P.V. Superhet, complete  
kit, £9.7.6. M.C. Earpiece (used as speaker), 5/-;  
Balance Inserts (as earpiece or speaker), 2/6. Silicon Rec-  
tifier bargain 70 p.i.v. ½A, 3/3; Westalite Contact Recti-  
fier 250V, 60mA, 7/6; Transformer 250-0-250V, 6V and  
5V, 15/-; 6V Vibrator Pack, 120V, 60mA out., 12/6.  
**TERMS.**—Cash with order. Post extra, excess refunded.  
Morco Reflex Rx, best 2-transistor Receiver. Send 8d.  
stamps for notes.**

**MORCO EXPERIMENTAL SUPPLIES**

8 & 10 Granville Street Sheffield 2  
Telephone 27461

**SPARES, VALVES, TUBES—1930-1960**

Guaranteed perfect, set tested, ex-working equipment.  
LOTs from £1. FOTs, Osc. Tr. Def. Coils, etc., cheap.  
Tubes guaranteed 6 months, FITTED FREE. Picture  
shown to callers. 9" 30/-, 12" 50/-, 14" 60/-, 17" 70/-.  
VALVES—3,000 types stocked. EF50, SP61, 1/-; EF91,  
EB91, 6H6, 2/-; EF80, UF42, 6F1, 20D1, 3/-; 10F1, 6V6,  
B36, KT61, 4/-; PL81, PL82, PY81, ECL80, PCL83, 6K25,  
5/-; KT33C, 10P14, 10C1, UCH42, 6/-; EL38, KT36,  
U22, U35, U281, 7/6; PL38, PZ30, U24, 20P1, U25,  
185BT, 10/-; 27SU, U37, 12/6. Pre-war 4, 5 and 7 pin,  
5/- each. Postage 6d. Constructor's Parcel—2½lb  
assorted res., cond., pots., etc., from modern TVs, 7/6,  
postage 2/6. New Transistors—OC44, OC45, 15/- each.  
Send S.A.E. for list or with enquiries  
Photo-electric Burglar Alarm, Garage Door Opener,  
Light Saver. Main's kit £4.12.6; built £5.10.0. Send 6d.  
stamp for details and circuit.

**ST. JOHN'S RADIO**

156 ST. JOHN'S HILL SW11 Telephone BAT 9838

**UNREPEATABLE T.V. TUBE OFFER**

**GENUINE REBUILT**

**12" Mullard Tube**

**Only £2.10.0**

CARRIAGE 10/- Guaranteed 12 months  
Other types available

**S.T.S. LTD. 35 Pound Street**

Carshalton Surrey  
Telephone Wallington 9665

**"GLOBE-KING"**

WORLD-FAMOUS KITS AND RECEIVERS  
for the Radio Amateur and S.W. Listener. Catalogue  
free, enclose stamp for postage. Kits from 79/6  
obtainable at your dealers or direct from sole manu-  
facturers.

**JOHNSONS (Radio)**

ST. MARTINS GATE — WORCESTER

**SOLDERING TOOL 12/6**

A.C. mains or car battery, 110V or 6V and 12V. Adap-  
tor for 200-250V 10/- extra. Automatic solder feed.  
For electronic soldering or car wiring. Cannot burn.  
Fitted in a light metal carrying case with full instruc-  
tions. Brand new. Post 3/6.

**RECTIFIERS 2/9.** 250V 100mA half-wave. Salvage.  
P. & P. 1/3.

**V/TONE CONTROLS 2/6 doz.** Assorted and  
stripped from working chassis. P. & P. 2/-.

**SALVAGE STRIP 1/-.** With varied resistors,  
incl. slider resistors; varied condensers, incl. beehive  
trimmer; v/holders, H.F. choke & 8" x 4" alumin.  
chassis. P. & P. 1/9.

**SPEAKERS 8/9.** 5", 6", 8" and 7" x 4" mfd. Salvage.  
Good quality. P. & P. 2/6.

**P.P. COMPONENTS LTD.**  
219 Ilford Lane Ilford Essex

STAMP FOR  
FREE LIST

$$X = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

1st lesson  
and details  
**FREE**  
from

DON'T FUMBLE with Formulae.  
Master Mathematics quickly and  
easily the Understandable Way.

**UNDERSTANDABLE MATHEMATICS**

11k Dryden Chambers Oxford Street  
London W1

Name \_\_\_\_\_

Address \_\_\_\_\_

**SURPLUS RADIO SUPPLIES**

2 LAING'S CORNER MITCHAM  
SURREY Telephone MIT 8820

Specialists in manufacturers' and ex-Government  
surplus

Send for our booklet listing hundreds of exciting  
bargains. 1/6 post free

Name \_\_\_\_\_

Address \_\_\_\_\_

**SMALL ADVERTISEMENTS**

continued from page 117

**MORSE CODE TRAINING.** Special courses for  
Beginners. Full details from (Dept. R.C.) Candler  
System Company, 52 Abingdon Road, London, W.8.

**PANL,** recognised for many years as the unique one-  
coat black crackle finish. Brush applied, no baking.  
Available by post in eighth-pint cans at 3s. 9d.  
from G. A. Miller, 255 Nether Street, London, N.3.

**CATALOGUE No. 14.** Government surplus and  
model radio control, over 300 illustrated items, 2s.  
(refunded on purchase), p.p. 6d.—Arthur Sallis  
Radio Control Ltd., 93 (E) North Road, Brighton.

**FIND TV SET TROUBLES IN MINUTES** from that  
great book *The Principles of TV Receiver Servicing*,  
10s. 6d., all book houses and radio wholesalers. If  
not in stock, from Secretary I.P.R.E., 20 Fairfield  
Road, London, N.8.

**SERVICE SHEETS** from Is. Catalogue 6,000 models  
Is. Radio/TV spares, Valves, Transistor set kit,  
10s. S.W. kit, 22s. 6d. S.A.E. Lists/enquiries.—  
Hamilton Radio, 13 Western Road, St. Leonards,  
Sussex.

**ONE VALVE RECEIVER,** mains driven, fantastic  
sensitivity, only 15ft aerial required. Constructional  
booklet, *The First One*, Is. 3d. all booksellers;  
Is. 6d. direct.—High Fidelity Company, 18 Melville  
Road, Birmingham 16.

**"MEDIUM WAVE NEWS"**. Monthly during DX  
season.—Details from B. J. C. Brown, 196 Abbey  
Street, Derby.

**THE INTERNATIONAL HAM HOP CLUB** is a  
non-profit making organisation open to RADIO  
AMATEURS AND SHORT WAVE LISTENERS. OBJECT:  
To improve international relationships through an  
organised system of hospitality. MEMBERS offer over-  
night hospitality to visiting members, subscription  
10s. per annum. ASSOCIATE MEMBERS invite radio  
amateurs to visit their stations. Associate member-  
ship 5s. per annum. FAMILY EXCHANGE holidays  
arranged, also FRIENDSHIP LINKS between radio clubs.  
The Club's official journal is free to both Full and  
Associate members. Hon. Gen. Secretary: G. A.  
Partridge, G3CED, 17 Ethel Road, Broadstairs,  
Kent.

**"ELECTRONIC ORGAN"**. Building one this week?  
Nearly everything for construction. Switches—  
Springs—Sleeving—Vol. Controls—Condensers—  
Resistors, etc., etc. Price Lists sent.—Robert C.  
Tidwell, High Street, Gosberton, Spalding, Lincs.

**CLEARANCE SALE:** Components, electric tools, etc.  
Stamp for lists. Mail only.—98 Greenway Avenue,  
London, E.17.

**ORGAN MATERIALS.** Details S.A.E.—Cot, Tiptend,  
Wisbech.

**H.A.C. THE ORIGINAL SUPPLIERS  
OF SHORT-WAVE KITS**

One valve Super Sensitive All-dry Short-wave Receiver  
Model "K". Complete kit including valve and chassis  
77/-. (Other S.W. kits from 25/-) Before ordering  
call and inspect a demonstration receiver, or send  
stamped envelope for full specification, catalogue and  
order form.

**H.A.C. SHORT-WAVE PRODUCTS (DEPT. R)**  
44 OLD BOND STREET LONDON W1

**QUALITY COMPONENTS FOR CONSTRUCTORS**

capacitors, resistors, coils, valves, diodes, controls,  
chassis, transformers, speakers, pick-ups, cart-  
ridges, stylii and all types of components in stock.

**CONSTRUCTIONAL PUBLICATIONS**

Mullard Circuits for Audio Amplifiers ... 8/6  
Mullard Tape Pre-amp "C" ... 2/6  
Quality Amplifiers, 7 designs ... 4/6  
Jason F.M. Variable Tuners ... 2/6

Price lists available on request

**J. T. FILMER 82 DARTFORD ROAD  
DARTFORD KENT**

Telephone Dartford 24057

**RADIO AMATEURS...**

get your Licence in

**Half The Usual Time!**

You must be a good Morse operator!  
A "slap-dash" 12 w.p.m. neither satisfies the authorities,  
yourself, nor your operator friends. Morse operating  
is an exacting art unless your training is made simple  
and is based on sound fundamentals. For this reason  
the Candler System was invented to take the "grind"  
out of Code tuition, turning a tricky subject into a  
pleasurable pursuit.

★ Send 3d. stamp for the "Book of Facts"

**CANDLER SYSTEM CO**


(Dept. 55 RC) 25b Abingdon Rd., London, W8  
Candler System Company, Denver, Colorado, U.S.A.

**German Radio  
Television and Phono  
Exhibition**

August 25 to September 3 **Berlin 1961**

Exhibition ground at the W-Berlin radio tower  
Information:

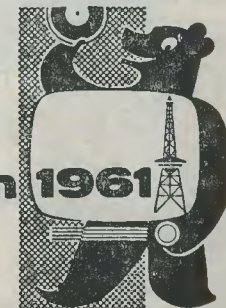
German Tourist Information Bureau  
61 Conduit Street, London W1


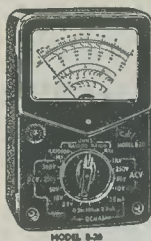
## Matched Sets of Transistors

- 6 Mullard Transistors and Diode
    - 1—OC44 ONLY
    - 2—OC45
    - 1—OC71 50/-
    - 2—OC72
 and PER SET  
 1—OA81  
 or with 2—OA81, 52/6
  - 6 Ediswan Transistors and two Diodes
    - 1—XA102
    - 2—XA101 ONLY
    - 1—XB103
    - 2—XC101 57/6
 and PER SET  
 2—Diodes
  - 6 Mullard Transistors and Diode—1 watt output
    - 1—OC44 ONLY
    - 2—OC45
    - 1—OC81D 62/6
    - 2—OC81
 and PER SET  
 1—OA81  
 or with 2—OA81, 65/-
  - 4 Mullard Transistors for 1 watt amplifier
    - 1—OC71 ONLY
    - 1—OC81D
    - 2—OC81 49/6
 with Cooling Clips  
 Capable of 1 watt Push-Pull
- ALL THE ABOVE TRANSISTORS ARE 1st GRADE AND SELECTED FOR PERFORMANCE

Excellent design and construction, very versatile



### RANGER-2

#### PERSONAL POCKET RADIO

★ Two High Gain Transistor Version of "Ranger-3"—See back page. Similar in appearance and performance.

ALL PARTS 59/6 P.P. 1/6. Everything supplied.

★ Pictorial plans and description  
FREE ON REQUEST



#### CRYSTAL MICROPHONES

ACOS 39-1 Stick Microphone with screened cable and Stand (list 5 gns.), 39/6, P.P.1/6.

ACOS 40 Desk Microphone with screened cable and built-in stand (list 50/-) 19/6 P.P. 1/6

ACOS 45 Hand Microphone with screened lead, very sensitive, 29/6, P.P. 1/6

MC 43 Stick Microphone with muting switch and screened cable 42/6, P.P. 1/6

● Brand New—Fully Guaranteed ●

## MULTIMETERS

● BRAND NEW—FULLY GUARANTEED ●

Model A-10 (500 Micro-amp. movement) (2K per volt) 0/10/50/250/500/1,000V A.C. (2K per volt) 0/10/50/250/500/1,000V D.C. current 0/0.5/25/250mA. Resistance: 0/10K/1 Meg. Size 5½" x 3½" x 1½". Weight 17 oz. inclusive of test prods, instruction book and batteries. £4.17.6 P.P. 1/6

Model B-20 (100 Micro-amp. movement) D.C. (10,000 ohms per volt) p/0.5/2.5V D.C. (4,000 ohms per volt) 0/10/50/250/500/1,000V A.C. (4,000 ohms per volt) 0/10/50/250/1,000V D.C. Current, 0/0.1/2.5/25/250mA. Size 5½" x 3½" x 2¼". Weight 24 oz. inclusive of test prods, instruction book and batteries. (Illustrated). £6.10.0 P.P. 1/6

### Type 38, Transmitter/Receiver

Complete with 5 valves. In new condition. These sets are sold without guarantee, but are serviceable.

7 to 9 Mc/s 22/6 P.P. 2/6  
Headphones 7/6 pair. Junction Box 2/6. Throat Mike 4/6. Aerial Rod 2/6

Complete range of TSL really sub-miniature superhet components in stock with circuits

## TRANSISTORS

POWER, RF, AUDIO, IF, FM, SHORT WAVE RADIO CONTROL, ETC.

from 3/6 each

SEND FOR NEW FREE LIST WITH DATA AND USES  
FULLY GUARANTEED  
We can supply a transistor for every need!

## SUPER-3

### PERSONAL POCKET RADIO

- Medium Wave Tuning
- Three Transistors and Diode
- 9 Months' Battery Life for 4½d.

Personal Earphone Output for Quality Listening

- Simple to Build
- After Sales Service
- Ideal for Beginners


BUILT-IN FERRITE ROD AERIAL

Total cost of all necessary items with earphone, battery and transistors, etc.

FREE Diagram on Request

37/6 P. & P. 1/6  
All parts sold separately

## REPANCO MINI-4

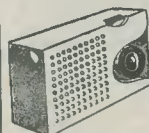

- 4-Mullard OC44/2-OC45/OC72 Transistor 5-stage Medium and Long wave pocket size superhet
- 2½" SPEAKER
- Easy to build and use
- Moulded Case Size: 5¼" x 3½" x 1½"

ALL PARTS £6.19.6 P.P. 1/6

● NEW EASY DIAGRAMS, 1/6 plus post  
PARTS LIST FREE ON REQUEST

★ TRANSISTOR FM PRE-BUILT UNITS FULLY TUNABLE ★  
● DETAILS ON REQUEST ●

We specialise in components for the Home Constructor. Valve or Transistorised; from Radio Control to Amplifiers, Test units to Transmitters.

Valves

Full catalogue of over 800 types for Domestic & Industrial uses with equivalents and data.

Quartz Crystals

Over 600 types in stock for all purposes. fundamental and overtones

Components

Large range of standard and miniature for all purposes—let us have your enquiries

VALUE FOR MONEY FROM **Henry's Radio Ltd**

See Back Cover for Address →

PUBLISHED IN CONJUNCTION WITH

THE

# RADIO CONSTRUCTOR

★ The Radio Reprint Series ★

	Price	Postage
RR3 The "Argonaut" AM/FM—MW/VHF Tuner Receiver—A Jason design	2/-	4d.
RR4 The "Eavesdropper". 3-Transistor local station pocket receiver	1/6	2d.
RR6 The Cooper-Smith B.P.I. High Fidelity 10-12 watt Amplifier and Control Unit	2/6	4d.
RR7 A Versatile 2-Valve Audio Pre-Amplifier—A Mullard design	1/-	2d.
RR8 High-Gain Band-3 Pre-Amplifier	1/-	2d.
RR10 The Cooper-Smith "Prodigy" 6-watt High Fidelity Amplifier	2/6	4d.
RR11 The Mullard Designed Type "C" Tape Pre-Amplifier	2/6	4d.

Send stamped addressed envelope for

# BROCHURE

giving details of ALL PUBLICATIONS

## DATA PUBLICATIONS LTD

57 MAIDA VALE LONDON W9

Telegrams Databux London

Telephone CUNningham 6141/2

Published in Great Britain by the Proprietors and Publishers  
Data Publications Ltd 57 Maida Vale London W9

Printed by A. Quick & Co. (Printers) Ltd Oxford Road Clacton-on-Sea England  
Obtainable abroad through the following Collets Subscription Service Continental Publishers & Distributors Ltd  
William Dawson & Sons Ltd Australia and New Zealand Gordon & Gotch Ltd Electronics Publications (Australia)  
South Africa Central News Agency Holland "Radio Electronica"  
Registered for transmission by Magazine Post to Canada (including Newfoundland)