

15 80.

THE Radio Constructor

RADIO
TELEVISION
AUDIO
ELECTRONICS

VOLUME 18 NUMBER 5
A DATA PUBLICATION
TWO SHILLINGS & THREEPENCE

December 1964

constructing
a solid bass
GUITAR



• • • Portable P.A. Amplifier • • •

• • • "Magic" Switching for Christmas Lights • • •

• • • Electronic Locks and Anti-Thief Devices • • •

THE **EDDYSTONE** MODEL "EC 10" TRANSISTORISED COMMUNICATIONS RECEIVER



**RUGGED, LIGHT AND COMPACT
FOR PROFESSIONAL AND AMATEUR USE**

A most efficient transistorised receiver giving an excellent and consistent performance over the whole range from 550 kc/s to 30 Mc/s. Thirteen transistors and diodes, including stabilising Zener diode. Ample audio output to internal speaker, and panel jack also fitted for telephone headset. Precision slow-motion drive with 110 to 1 reduction ratio ensures delightfully easy tuning.

Self-contained battery unit holds long-life cells. Alternative aerial inputs for dipole, long wire and short wire aerials. Selective audio filter improves c.w. reception. Robust construction, modern styling, attractive two-tone grey finish. Dimensions are $12\frac{1}{2}$ inches wide, $6\frac{3}{8}$ inches high, 8 inches deep. Weight with batteries 14 lb.

List Price (in U.K.) £48. 0s. 0d.

STRATTON & CO. LTD. BIRMINGHAM · England

LASKY'S RADIO

FOR THE FINEST RANGE OF TRANSISTOR RECEIVERS

We consider our construction parcels to be the finest value on the home constructor market. If on receipt you feel not competent to build the set, you may return it as received within 7 days, when the sum paid will be refunded, less postage.



THE SKYROVER Mk II

Now supplied with redesigned cabinet, edgewise controls, new colour tuning scale and cabinet in Sierra Tan. Controls: Waveband Selector, Volume Control with On/Off Switch, Tuning Control. In plastic cabinet, size 10" x 6 1/2" x 3 1/2", with metal trim and carrying handle. Can now be built for

£8.19.6

P. and P. 5/- extra
All components available separately. Four U2 batteries 3/4 extra. Data for each receiver 2/6 extra, refunded if you purchase the parcel.

★ LONG WAVEBAND COVERAGE IS NOW AVAILABLE FOR THESE WELL-KNOWN SETS. A simple additional circuit provides coverage of the 1,100-1,950 metre band (including 1,500 metre Light Programme). This is in addition to all existing medium and short wavebands. All necessary components with construction data. **Only 10/- extra** Post Free. This conversion is suitable for both models that have already been constructed.

The SKYROVER RANGE

GENERAL SPECIFICATION. 7 transistor plus 2 diode superhet, 6 waveband portable receiver. Operating from four 1.5V torch batteries. The SKYROVER and SKYROVER DE LUXE cover the full medium waveband and short waveband 31-94 M, and also 4 separate switched band-spread ranges, 13 M, 16 M, 19 M and 25 M, with band-spread tuning for accurate station selection. The coil pack and tuning head is completely factory assembled, wired and tested. The remaining assembly can be completed in under three hours from our easy to follow, stage by stage instructions. **SPECIFICATION:** Superhet, 470 kc/s. All Mullard transistors and diode. Uses 4 U2 batteries. 5" Ceramic Magnet P.M. Speaker. Easy to read Dial Scale. Band-spread Tuning. 500mW Output. Telescopic Aerial and Ferrite Rod Aerial.

THE SKYROVER DE LUXE

Tone Control circuit is incorporated, with separate Tone Control in addition to Volume Control, Tuning Control and Waveband Selector. In a wood cabinet, size 11 1/2" x 6 1/2" x 3", covered with a washable material, with plastic trim and carrying handle. Also car aerial socket fitted.

Can now be built for

£10.19.6

P. and P. 5/- extra



H.P. Terms:—25/- deposit and 11 months at 20/-

REALISTIC SEVEN

★ 7-transistor Superhet. ★ 350 milliwatt output into 4" high flux speaker. ★ All components mounted on a single printed circuit board, size 5 1/2" x 5 1/2" in one complete assembly.

★ Plastic cabinet with carrying handle, size 7" x 10" x 3 1/2", available in Blue/Grey, Full L. & M. coverage ★ Easy to read Dial. ★ External socket for car aerial.

★ I.F. frequency 470 kc/s. ★ Ferrite rod internal aerial. Operates from PP9 or similar battery. ★ Full comprehensive data supplied with each receiver. ★ All coils and I.F.s, etc., fully wound ready for immediate assembly.

An Outstanding Receiver. LASKY'S PRICE for the complete parcel including Transistors, Cabinet, Speaker, etc., and Full Construction Data. Can be built for: **£5.19.6**

P. and P. 4/6

PP9 Battery, 3/9. Data and instructions separately, 2/6. Refunded if you purchase the parcel. All parts sold separately.

REALISTIC 'Seven' De Luxe

With the same specification as standard model —PLUS a superior wood cabinet in contemporary styling. ALSO a full vision circular dial

FOR ONLY **£1** EXTRA
P. & P. as std. model

SINCLAIR SUPER MINIATURES

THE NEW SINCLAIR SLIMLINE

The new 2-transistor pocket radio, size only 2 3/4" x 1 3/8" x 1 1/2". Micro alloy transistors and printed circuit. Easy to assemble.

CAN BE BUILT FOR 49/6

THE SINCLAIR MICRO-6

Self-contained pocket radio. Size only 1 1/2" x 1 3/16" x 1 1/2". Truly amazing performance. Without doubt the most advanced transistor circuit ever offered to home constructors—yet may be built in an evening. Complete with earphone and detailed construction data. Mercury cell

CAN BE BUILT FOR 59/6

1/11 extra (2 required).

THE SINCLAIR X10

10 watt power amplifier fitted with integrated pre-amp. Requires only 1mV for an output of 10 watts undistorted. Frequency response is flat, ±dB from 5 c/s to 10 kc/s. Size only 6" x 3" x 2 1/2", weight 5 oz., built on printed circuit. Operates from 12V d.c. at 75mA quiescent. Circuit uses 7 MATs and 4 t.f. power transistors.

Kit price £5.19.6 READY TO BUILD £6.19.6

3 pots. for volume, bass & treble, 7/6 the 3 extra.

TRANSFILTERS by BRUSH CRYSTAL CO.

TO-01B 465 kc/s ± 2 kc/s	
TO-01D 470 kc/s ± 2 kc/s	6/6 each
TO-02B 465 kc/s ± 1 kc/s	P. & P. 6d.
TO-02D 470 kc/s ± 1 kc/s	
TF-01B 465 kc/s ± 2 kc/s	
TF-01D 470 kc/s ± 2 kc/s	

PICK-UP CARTRIDGES

Cystal P.U. Cartridges complete with stylus—at lowest prices ever!	
Mono C.T.I.	4/11
Collaro Type C, stereo, 2 sapphires.	15/-
Collol S.C.I. Stereo Diamond LP Sappi. std.	17/6
Sonotone BT, stereo, 2 sapphires	19/11
Sonotone 2TA, mono, 2 sapphires	15/-
Postage 1/- each extra.	

12" FANE HI-FI SPEAKER BARGAINS

Type 122/17. Power handling 25 watts—15 ohms imp. Flux density 17,000 gauss. Special anisotropic magnet. Listed at £11.17.6. Limited stock

LASKY'S PRICE £5.19.6 P. & P. 5/-

WHARFDALE WNA12. 12" 15Ω imp. Flux density 14,000 oer's. Max. input 15 watts RMS, 30 watts peak. Frequency range 25-4,000 c.p.s. Cone fitted with roll surround.

WHARFDALE SUPER 5. 5" mid-range and high frequency speaker. 15Ω imp. Frequency range 300-17,000 c.p.s. Aluminium voice coil. These two speakers provide an ideal matched pair for a full range hi-fi speaker system. Both brand new and individually boxed.

LASKY'S PRICE £12.19.6 the pair. P. & P. 10/-

Sub-Min. Transformerless Transistorised Amps. British made, these sub-min. amplifiers come to you fully built and ready for immediate use. Thousands of uses in all branches of electronics: sound and signal amplification—models—electro-medico equipment—pre-amps—radio tuners—tape head amps, etc. All use NPN-PNP circuit powered by 9V battery.

PC1, input 50mV, output 150mW at 40Ω, size 2" x 1" x 2". **LASKY'S PRICE 29/6 P. & P. 1/-**
PC2, input 1mV, output 400mW at 15Ω, size 2" x 2 1/2". **LASKY'S PRICE 37/6 P. & P. 1/-**
PC3, input 5mV, output 400mW at 15Ω, size 2 1/2" x 1 1/2". **LASKY'S PRICE 37/6 P. & P. 1/-**
PC4, input 150mV, output 400mW at 15Ω, size 2 1/2" x 1 1/2". **LASKY'S PRICE 37/6 P. & P. 1/-**

TAPE DECK MOTORS

Motors for the Collaro Studio Deck—new and unused. 200-250V A.C. Take-up and rewind. Listed at £2.5s. each. **LASKY'S PRICE 14/11 each.** P. & P. 2/6

State motor required when ordering.

High quality tape deck capstan motor made by E.M.I. Holland. Bi-directional. Size: 4" dia., x 2" high, 1" x 1/2" spindle. **LASKY'S PRICE 19/11. P. & P. 3/6.**

RECORDING TAPE SPLICER

By famous manufacturer—all metal construction. Listed at 18/6 **LASKY'S PRICE 14/6 Post Free**

LAFAYETTE TAPE

Famous American Brand—Fully Guaranteed at record low prices. In sealed cartons.

5in double play, 1,200ft. Mylar base ...	15/-
5in long play, 900ft. Acetate base ...	10/-
5in standard play, 600ft. PVC base ...	8/6
7in double play, 1,200ft. Mylar base ...	15/-
5 1/2in double play, 1,800ft. Mylar base ...	22/6
5 1/2in long play, 1,200ft. Acetate base ...	12/6
5 1/2in standard play, 850ft. PVC base ...	11/6
7in standard play, 1,200ft. Mylar base ...	12/6
7in long play, 1,800ft. Mylar base ...	19/6
7in double play, 2,400ft. Mylar base ...	28/-
7in long play, 1,800ft. Acetate base ...	15/-
3in message tape, 150ft ...	3/6
3in message tape, 225ft ...	4/11
3in message tape, 300ft ...	7/6
3in triple play, 450ft. Mylar base ...	12/6
4in triple play, 900ft. Mylar base ...	22/6
5in triple play, 1,800ft. Mylar base ...	42/6
5 1/2in triple play, 2,400ft. Mylar base ...	55/-
7in triple play, 3,600ft. Mylar base ...	75/-
P. & P. 1/- extra per reel; 4 reels and over Post Free.	

HI-FI TAPE RECORDER HEADS

High Impedance Record Play. Low impedance erase. Upper or lower track.

LASKY'S 29/6 Post free per pair. State track required.

MARRIOTT "X" Type 1/2 track heads. Record/Play and Erase.

LASKY'S PRICE 4 gns. pair

1/2-Track heads Record/Play and Erase 59/6 pair.

TAPE POSITION INDICATOR

Open type—as used by most makers. With re-set knob: **3 DIGIT 7/6; 4 DIGIT 10/6. P. & P. 9d. on each.**

TRANSISTORS

All New and Guaranteed
GET.51, GET.55, GET.56—2/6; 873A, 874P—3/6; OC.45, OC.71, OC.81D—4/6; OC.44, OC.70, OC.76, OC.81—5/6 (matched pair 10/6); AF.117, OC.75, OC.171, OC.200—6/6; OC.42, OC.43, OC.73, OC.82D—7/6; OCP.71—9/6; OC.28, OC.201, OC.204—15/-; OC.205, OC.206—19/6; OC.28—24/6.

33 TOTTENHAM COURT ROAD · W1 2 mins. Oxford St. Nearest Station: Goudge St. **MUSEUM 2605**
207 EDGWARE ROAD · W2 Few yards from Praed St. **PADDINGTON 3271/2**
152/3 FLEET STREET · EC4 (ELECTRONICS Fleet St. Ltd) FLEet 2833. Open all day Thurs. Closed 1 p.m. Sat.

HI-FI AMPLIFIERS TUNERS RECORD PLAYERS

S-33



S-99



AT-6



MA-12



HI-FI 6W STEREO AMPLIFIER. Model S-33. 3 watts per channel 0.3% distortion at 2.5W/chnl., 20dB N.F.B. Inputs for Radio (or Tape) and Gram, Stereo or Monaural, ganged controls. Kit **£13.76** Assembled **£18.18.0**

DE LUXE STEREO AMPLIFIER. Model S-33H. De luxe version of the S-33 with two-tone grey perspex panel, and higher sensitivity necessary to accept the Decca Deram pick-up. Kit **£15.17.6** Assembled **£21.7.6**

HI-FI STEREO AMPLIFIER. Model S-99. 18W output. Ganged controls. Stereo/Mono gram., radio and tape inputs. Push-button selection. Printed circuit construction. Kit **£27.19.6** Assembled **£37.19.6**

POWER SUPPLY UNIT. Model MGP-1. Input 100/120V, 200/250V. 40-60 c/s. Output 6.3V, 2.5A A.C. 200, 250, 270V, 120mA max. D.C. Kit **£5.2.6** Assembled **£6.12.6**

A wide range of American equipment available under direct mail order scheme. Full details and catalogue 1/- post paid.

GOLDRING LENCOR TRANSCRIPTION PLAYER. Model GL-58. With G-60 pick-up arm and Ronette 105 cartridge. **£20.1.3**

GARRARD AUTO/RECORD PLAYER. Model AT-6. With R 105 cartridge. **£13.12.1** With Decca Deram pick-up **£14.6.1**

HI-FI MONO AMPLIFIER. Model MA-5. A general purpose 5W Amplifier, with inputs for Gram., Radio. Presentation similar to S-33. Kit **£10.19.6** Assembled **£15.10.0**

HI-FI MONO AMPLIFIER. Model MA-12. 12W output, wide freq. range, low distortion. Kit **£11.18.0** Assembled **£15.18.0**

R.P.M. INDICATOR (Electronic Rev. Counter). A must for the motoring enthusiast. For 4 cylinders, pos. or neg. earth. 12V. Send for details. (Assembled only) **£8.19.0**



Make the most of the winter evenings...

FOR THE INSTRUMENTALIST



PA-1

PA AMPLIFIER PA-1. The ideal compact unit for VOCALISTS, INSTRUMENTALISTS, RECORDS, with 50 Watt output, 2 Heavy Duty Speakers. Variable TREMOLO. Elegant modern cabinet. Kit **£54.15.0** Assembled **£74.0.0**

Legs optional extra 17/6 set of 4

POWER AMPLIFIER MA-50 50W output. Kit **£19.18.0** Assembled **£27.18.0**

ELECTRONIC ORGAN

(Transistorised). Ideal for Soloists, Home use, Groups. FULL 20 WATTS VOLUME. **£187.10.0** Matching bench **£14.10.0** extra.

TRANSISTOR RADIOS

"OXFORD" LUXURY PORTABLE.

Model UXR-2. Specially designed for use as a domestic, car or personal portable receiver. Many features, including solid leather case. Kit **£14.18.0**



UXR-2

TRANSISTOR PORTABLE. Model UXR-1. Pre-aligned I.F. transformers, printed circuit. Covers L.W. and M.W. Has 7" x 4" loudspeaker. Real hide case. Kit **£12.11.0**



UXR-1

JUNIOR EXPERIMENTAL WORKSHOP. Model EW-1. More than a toy! Will make over 20 exciting electronic devices, incl: Radios, Burglar Alarms, etc. 72 page Manual. The ideal present! Kit **£7.13.6** incl. P.T.



UJR-1

JUNIOR TRANSISTOR RADIO. Model UJR-1. Single transistor set. Excellent introduction to radio. Kit **£2.7.6** incl. P.T.

Money-back Guarantee


Daysfrom Limited unconditionally guarantees that each Heathkit product assembled in accordance with our easy-to-understand instruction manual must meet our published specifications for performance or the purchase price will be cheerfully refunded.

TEST INSTRUMENTS

T.V. ALIGNMENT GENERATOR. Model HFV-1. Offers max performance at lowest cost. Covers 3.6 to 220 Mc/s fundamentals. Electronic sweep oscillators. Built in marker generators (5 Mc/s crystal) **£34.18.0** Kit **£44.10.0** Assembled



HFV-1

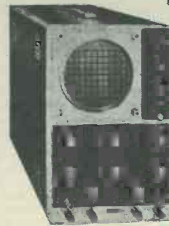

IO-12U

5" GENERAL-PURPOSE LABORATORY OSCILLOSCOPE. Model IO-12U. This outstanding oscilloscope, with its professional specification and styling, fulfills most laboratory and service requirements. Vertical frequency response 3 c/s to over 4.5Mc/s, sensitivity 10mV r.m.s. per cm. at 1 kc/s. T/B covers 10 c/s-500 kc/s. Kit **£32.12.6** Assembled **£41.10.0**

2 1/2" PORTABLE SERVICE 'SCOPE. Model OS-1. This is a light, compact oscilloscope, ideal for servicing, etc. Dimensions 5" x 8" x 1 1/4" long. Wt. 10 1/2 lb. Fitted metal CRT shield. Kit **£22.18.0** Assembled **£30.8.0**



S-3U

ELECTRONIC SWITCH. Model S-3U (Oscilloscope Trace Doubler). Enables a single beam oscilloscope to give simultaneous traces of two separate and independent signals. Switching rates approx. 150, 500, 1,500, 5,000 and 15,000 c/s. Sig. freq. response 0-100 kc/s. ±1dB. Separate gain controls and sync. output. Sig. input range 0.1-1.8V r.m.s. Kit **£12.18.0** Assembled **£18.10.0**

DE LUXE LARGE-SCALE VALVE VOLT-METER. Model IM-13U. Circuit and specification based on the well known model V-7A but with many worth-while refinements. 6" Ernest Turner meter. Unique gimbal bracket allows operation of instrument in many positions. Modern styling. Kit **£18.18.0** Assembled **£26.18.0**



IM-13U

AUDIO SIGNAL GENERATOR. Model AG-9U. 10 c/s to 100 kc/s, switch selected. Distortion less than 0.1%, 10V sine wave output metered in volts and dB's. Kit **£22.10.0** Assembled **£30.10.0**

VALVE VOLTMETER. Model V-7A. 7 voltage ranges d.c. volts to 1,500. A.c. to 1,500 r.m.s. and 4,000 peak to peak. Resistance 0.1Ω to 1,000MΩ with internal battery. D.c. input impedance 11MΩ. dB measurement, has centre-zero scale. Complete with test prods, lead and standardising battery. Kit **£13.18.6** Assembled **£19.18.6**



V-7A

MULTIMETER. Model MM-1U. Ranges 0-1.5V to 1,500V a.c. and d.c.; 150μA to 15A d.c.; 0.2Ω to 20MΩ. 4 1/2" 50μA meter. Kit **£12.18.0** Assembled **£18.11.6**



RF-1U

R.F. SIGNAL GENERATOR. Model RF-1U. Up to 100 Mc/s fundamental and 200 Mc/s on harmonics. Up to 100 mV output. Kit **£13.8.0** Assembled **£19.18.0**

A WIDE RANGE OF BOOKS ON ELECTRONICS AND RADIO AVAILABLE. SEND FOR LISTS OF PRICES

TAPE DECKS CONTROL UNITS TAPE AMPLIFIERS



MAGNAVOX



D-93



FM-4U



AM/FM

MAGNAVOX "STUDIO" TAPE DECK. The finest buy in its price range. Operating speeds: 1 $\frac{1}{2}$ ", 3 $\frac{1}{4}$ " and 7 $\frac{1}{2}$ " p.s. Two tracks, "wow" and "flutter" not greater than 0.15% at 7 $\frac{1}{2}$ " p.s. **£14.19.6**

TRUVOX D93 TAPE DECKS. High quality stereo/mono tape decks.

D93/2, $\frac{1}{2}$ track, **£36.15.0** D93/4, $\frac{1}{4}$ track, **£36.15.0**

HI-FI AM/FM TUNER. Model AFM-1. Available in two units which, for your convenience, are sold separately. Tuning heart (AFM-T1—£4.13.6 incl. P.T.) and I.F. amplifier (AFM-A1—£21.16.6). Printed circuit board, 8 valves. Covers L.W., M.W., S.W., and F.M. Built-in power supply. **Total Kit £26.10.0**

HI-FI FM TUNER. Model FM-4U. Also available in two units. R.F. tuning unit (£2.15.0 incl. P.T.) with I.F. output of 10.7 Mc/s, and amplifier unit, with power supply and valves (£13.3.0). **Total Kit £15.18.0**

TAPE RECORDING/PLAYBACK AMPLIFIER. Thermometer type recording indicators, press-button speed compensation and input selection. Mono Model TA-1M, Kit **£19.18.0** Assembled **£28.18.0**
Stereo Model TA-1S, Kit **£25.10.0** Assembled **£35.18.0**

MONO CONTROL UNIT. Model UMC-1. Designed to work with the MA-12 or similar amplifier requiring 0.25V or less for full output. 5 inputs. Baxandall type controls. **Kit £8.12.6** Assembled **£13.12.6**

STEREO CONTROL UNIT. Model USC-1. Push-button selection, accurately matched ganged controls to ± 1 dB. Rumble and variable low-pass filters. Printed circuit boards. **Kit £19.10.0** Assembled **£26.10.0**

Enjoy yourself building a Heathkit model



"AMATEUR" EQUIPMENT

AMATEUR BANDS RECEIVER. Model RA-1. To cover all the Amateur Bands from 160-10 metres. Many special features, including: half-lattice crystal filter; 8 valves; signal strength "S" meter; tuned R.F. Amp. stage.

Kit **£39.6.6** Assembled **£52.10.0**

THE "MOHICAN" GENERAL COVERAGE RECEIVER. Model GC-1U. With 4 piezo-electric transmitters, variable tuned B.F.O. and Zener diode stabiliser, this is an excellent fully transistorised general purpose receiver for Amateur and Short wave listeners. Printed circuits, telescopic aerials, tuning meter and large slide-rule dial.

Kit **£37.17.6** Assembled **£45.17.6**

160-10M TRANSMITTER. Model DX-100U. Careful design has achieved high performance and stability. Completely self-contained.

Kit **£79.10.0** Assembled **£104.15.0**



RA-1



RG-1



SB-10U

COMMUNICATIONS TYPE RECEIVER. Model RG-1. A high performance, low cost receiver for the discriminating listener. Frequency coverage: 600 kc/s-1.5 Mc/s and 1.7 Mc/s-32 Mc/s.

Kit **£39.16.0** Assembled **£53.0.0**

SINGLE SIDEBAND ADAPTOR. Model SB-10U. May be used with most A.M. transmitters. Less than 3W R.F. input power required for 10W output. Operation on 80, 40, 20, 15 and 10m bands on U.S.B., L.S.B. or D.S.B.

Kit **£39.5.0** Assembled **£54.18.0**

Many other British 'Amateur' models. Send for Catalogue.

SPEAKER SYSTEMS

COTSWOLD "MFS" SYSTEM. Specially developed to give best possible results in small rooms. This minimum floor space model is based on standard Cotswold. Size: 36" high x 16 $\frac{1}{2}$ " wide x 14" deep.

Kit **£23.4.0** Assembled **£30.15.0**

THE "COTSWOLD". This is an acoustically designed enclosure 26" x 23" x 15 $\frac{1}{2}$ " housing a 12" bass speaker with 2" speech coil, elliptical middle speaker together with a pressure unit to cover the full frequency range of 32-20,000 c/s. Capable of doing justice to the finest programme source, its polar distribution makes it ideal for really Hi-Fi Stereo.

Kit **£23.4.0** Assembled **£30.15.0**

HI-FI SPEAKER SYSTEM. Model SSU-1. Ducted-port bass reflex cabinet "in the white". Two speakers. Vertical or horizontal models with legs, Kit **£11.12.0**, without legs, Kit **£10.17.6** incl. P.T.



MFS



SSU-1

HI-FI CABINETS

A wide range of equipment cabinets are available to meet the differing needs of enthusiasts. Designed for max. operating convenience or for where room space is an overriding consideration, this range includes kits, ready assembled cabinets or fully finished cabinets, and has at least one model to suit your requirements. Send for full details.

Prices from **£7.7.0** to **£37.16.0**



MALVERN

AMERICAN HEATHKIT "AMATEUR" EQUIPMENT

(As stocks in U.K. are limited, order as early as possible to avoid disappointment)

80-10M RECEIVER. Model SB-300E.

This de luxe receiver offers unsurpassed value to the Radio Amateur. Of advanced design employing up-to-date construction techniques, its specification ensures unparalleled performance. Full details on request. Size 14 $\frac{1}{2}$ " x 6 $\frac{1}{2}$ " x 13 $\frac{1}{2}$ ". Kit **£133.14.0** (less speaker) plus import levy.



SB-300E

A fitting companion to this receiver is model **SB-400E TRANSMITTER:** Kit **£165.4.0** plus import levy.

SEND FOR AMERICAN CATALOGUE. 1/- Post Paid
Deferred Terms available in U.K. on all purchases over £10.
Extended Deferred Terms available in U.K. over £75.

SEND FOR FREE BRITISH HEATHKIT CATALOGUE

American catalogue also available 1/- post paid

Without obligation please send me **FREE BRITISH HEATHKIT CATALOGUE** (Tick here)

FULL DETAILS OF MODEL(S)
(Please write in BLOCK CAPITALS)

NAME

ADDRESS

DEPT. RC.12

DAYSTROM LTD


DEPT. RC. 12
GLOUCESTER

7 VALVE AM/FM RADIOGRAM CHASSIS

Three Waveband & Switched Gram positions. Med. 200-550m. Long 1,000-2,000m. VHF/FM 88-95 Mc/s. Phillips Continental Tuning insert with permanent tuning on FM & combined AM/FM IF transformers. 460 kc/s and 10.7 Mc/s. Dust core tuning all coils. Latest circuitry including AVC & Neg. Feedback. 3 watt output. Sensitivity and reproduction of a very high standard. Chassis size 13 1/2" x 6 1/2" x 7 1/2". Edge illuminated glass dial 11 1/2" x 3 1/2". Vert. pointer Horiz. station names. Gold on brown background. A.C. 200/250V operation. Magic-eye tuning. Circuit diag. now available.

Comp. with 4 knobs—walnut or ivory to choice. Indoor FM aerial 3/8 ex. 3Ω P.M. Speaker only required. Recommended Quality Speakers 10" Rola, 27/6. 13 1/2" x 8" E.M.I. Fidelity, 37/6. 12" R.A. with conc. Tweeter, 42/6. Carr. 2/6.

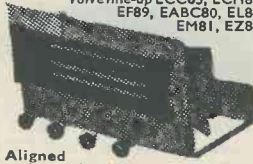Valve line-up ECC85, ECH81 EF89, EABC80, EL84 EM81, EZ80



Aligned and tested ready for use. **£13.10.0** Carr. & Ins. 7/6

ANOTHER TAPE RECORDER BARGAIN

Manufacturers' end of production Surplus Offer



A 24 gns. Tape Recorder offered at the bargain price of only 15 gns. plus 10/- carr. Supplied in 3 Units already wired and tested. A modern Circuit for quality recording from Mike Gram or Radio, using latest B.S.R. Twin Track Monardeck Type TD2. Valve line-up—EF86, ECL82, EM84, EZ80 and Silicon Diode. Send for detailed list—3d. stamp.

Completed Kit comprising items below

BARGAIN PRICE 15 Gns. + 10/- Carr.

2-tone Cabinet and 8" x 5" Speaker. Size 14" x 10 1/2" x 7 1/2" £3 10 0 + 5/- Carr.

Wired Amplifier complete with 4 Valves, front Panel, Knobs, etc. £5 12 6 + 3/6 Carr.

B.S.R. Monardeck Type TD2 £7 7 0 + 4/6 Carr.

Accessories: Mike, Tape, empty Reel, screened Lead and Plugs, Instructions, etc. £1 0 0 + 2/- Carr.

Jack Plugs. Standard 2 1/2 Igranic Type 2/6. Screened Ditto 3/3. Miniature scr. 1 1/2, 2/3. Sub-min. 1/3. Jack Sockets. Open Igranic Moulded Type, 3/6. Closed Ditto, 4/-. Miniature Closed Type, 1/6. Sub-min. (deaf aid) ditto, 1/6. Stereo Jack Sockets, 3/6. Stereo Jack Plugs, 3/6.

Phono Plugs, 9d. Phono Sockets (open), 9d. Ditto (closed), 1/-. Twin Phono Sockets (open), 1/3. Grundig Continental. 3 p. or 5 p. plug, 3/6. Sockets, 1/6.

Soldering Irons. Mains 200/220V or 230/250V. Solon 25 watt Inst., 22/6. Spare Elements, 4/6. Bits, 1/- 65 watt, 27/6 etc.

Alumin. Chassis. 18g. Plain Undrilled, folded 4 sides, 2" deep, 6" x 4", 4/6, 8" x 6", 5/9, 10" x 7". 6/9, 12" x 6", 7/6, 12" x 8", 8/- etc.

Alumin. Sheet. 18g. 6" x 6", 1/-. 6" x 9", 1/6, 6" x 12", 2/-. 12" x 12", 4/6 etc.

RECORDING TAPE

Quality tape at NEW REDUCED PRICES. A genuine recommended Quality Tape—TRY IT BRAND new, boxed and fully guaranteed. Fitted with leader and stop foils.

	Standard	Double Play	Long Play
5" 600'	13/-	1,200' 31/6	900' 17/6
5 1/2" 900'	16/-	1,800' 37/6	1,200' 19/6
7" 1,200'	21/-	2,400' 47/6	1,800' 28/6

SPECIAL OFFER. 3" Message tape 150', 3/9; 3" L.P. 225', 4/9; 3" D.P. 300', 6/6. P. & P. per reel 6d.

TAPE REELS. Mfrs., surplus 7", 2/3; 5 1/2", 2/-; 5", 2/-; 3", 1/3; Plastic spool containers, 5", 1/9; 5 1/2", 2/-; 7", 2/3.

New Boxed	VALVES	Reduced Bargain Prices	Electrolytics All Types New Stock
IT4	3/6 EF80	7/6 PCL83 10/6	25/25V 1/9
IR5	6/6 EF86	8/6 PCL84 10/-	50/12V 1/9
IS5	6/6 EL33 12/6	11/6 PCL95 11/6	50/50V 2/-
3S4	7/- EL34 12/6	10/6 PL36 10/6	100/25V 2/-
3V4	7/- EL84 7/-	9/6 PL81 9/6	8/450V 2/3
ECC81	7/- EY51 9/-	8/- PL83 8/-	4/350V 2/3
ECC82	7/- EY86 9/-	10/6 PY33 10/6	16 + 16/450V 5/6
ECC83	7/- EZ91 7/-	7/- PY82 7/-	32 + 32/450V 6/6
ECL80	9/- EZ32 9/6	10/6 UZ5 10/6	1000/25V 3/9
ECL82 10/-	PCC84 8/-	9/- UL84 9/-	Ersin Multicore Solder 60/40, 4d. per yard. Cartons 2/6, etc.
ECL86 10/6	PCF80 8/-		

DE LUXE R/PLAYER KIT

Incorporating 4 Speed Garrard Auto-Slim unit and Mullard latest 3 watt printed circuit amplifier (ECL 86 and EZ 80), volume, bass and treble controls, with 8" x 5" 10,000 line speaker. Superb quality reproduction.


Contemporary styled two-tone cabinet, charcoal grey and off-white with matching blue relief. Size: 17 1/2" x 16" x 8"

COMPLETE KIT £13.19.6 Carr. & ins. 10/-.

Illuminated Perspex escutcheon, 7/6 extra. Catalogue & construction details 2/6 (free with kit)

STANDARD RECORD PLAYER KIT

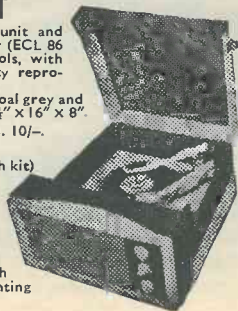Using BSR UA14 Unit, complete kit £11.10.0, carr. 7/6. Ready wired Amplifier, 7" x 4" quality Speaker and O/P trans. £3.19.6, carr. 2/6. BSR UA14 Unit, £6.10.0, carr. & ins. 5/-. Rexine covered cabinet in two-tone maroon and cream, size 15 1/2" x 14 1/2" x 8 1/2" with all accessories plus uncut record player mounting board 14" x 13", 59/6, carr. & ins. 5/-.



6 VALVE AM-FM TUNER UNIT

Med. and VHF 190m-550m, 86 Mc/s-103 Mc/s, 6 valves and metal rectifier. Self-contained power unit, A.C. 200/250V operation. Magic-eye indicator, 3 push-button controls, on/off, Med., VHF. Diodes and high output Sockets with gain control. Illuminated 2-colour perspex dial 11 1/2" x 4", chassis size 11 1/2" x 4" x 5 1/2". A recommended Fidelity Unit for use with Mullard "3-3" or "5-10" Amplifiers. Available only at present as built-up units, aligned and tested ready for use. **Bargain Price £12.10.0.** Carr. 5/-.

We hope to produce this popular unit in kit form very shortly.

Volume Controls—5K-2 Meg-ohms, 3" Spindles Morganite Midget Type. 1 1/2" diam. Guar. 1 year. LOG or LIN ratios less Sw. 3/-. D.P. Sw. 4/6. Twin Stereo less Sw. 6/6. D.P. Sw. 9/6 (100 k. to 2 Meg. only). 1/2 Meg. VOL Controls D.P. Sw. 1/4" flatted spindle. Famous Mfrs. 4 for 10/- post free.

ENAMELLED COPPER WIRE—1 1/2 reels, 14g-20g, 2/6; 22g-28g, 3/-; 36g-38g, 4/3; 39g-40g, 4/6, etc.

TINNED COPPER WIRE—14-22g, 2/6 + lb.

PVC CONNECTING WIRE—10 colours (for chassis wiring, etc.)—Single or stranded conductor, per yd., 2d. Sleeving, 1mm, and 2mm, 2d, yd., 2c.

KNOBs—Modern Continental types: Brown or Ivory with Gold Ring, 1" dia, 9d. each; 1 1/2", 1/- each; Brown or Ivory with Gold Centre, 1" dia, 10d. each; 1 1/2" 1/3 each. LARGE SELECTION AVAILABLE.

TRANSISTOR COMPONENTS

Midget I.F.'s—465 kc/s 1/2" diam. 5/6
Osc. Coil—1/2" diam. M/W. 5/3
Osc. coil M. & L.W. 5/9
Midget Driver Trans. 3.5:1 5/9
Ditto O/Put Push-pull 3 ohms 6/9

Elect. Condensers—Midget Type 15V 1mf-50mf, ea. 1/9. 100mf. 2/-.

Ferrite Aerial—M. & L. W. with car aerial coupling coil, 9/3.

Condensers—150V. wkg. .01 mfd. to .04 mfd., 9d. .05 mfd., 1 mfd., 1/- .25 mfd., 1/3. 5 mfd., 1/6, etc.

Tuning Condensers. J.B. "00" 208 + 176pF, 8/6. Ditto with trimmers, 9/6. 365pF single, 7/6. Sub-min. 2" DILEMIN 100pF, 300pF, 500pF, 7/-.

Midget Vol. Control with edge control knob, 5kΩ with switch, 4/9, ditto less switch, 3/9.

Speakers—2" P.M.—2" Plessey 75 ohms, 15/6. 2 1/2" P.M.—2" Plessey 85 ohms, 13/6. 7" x 4" Plessey 35 ohm, 23/6.


Ear Plug Phones—Min. Continental type, 3ft. lead, jack plug and socket. High Imp. 8/-, Low Imp., 7/6. High sensitivity M/coil 8-10 ohms, 12/6.

JASON FM TUNER UNITS

Designer-approved kit of parts:
FMT1, 5 gns. 4 valves, 20/-.
FMT2, 6 gns. 5 valves, 35/-.
JTV MERCURY 10 gns. 3 valves, 22/6.
JTV2 £13.19.6. 4 valves, 28/6.
NEW JASON FM HAND-BOOK 2/6. 18 hr. Alignment Service 7/6. P. & P. 2/6.

MULLARD "3-3" HI-FI AMPLIFIER

3 VALVES 3 WATT

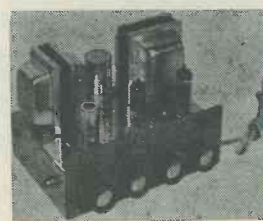

3 ohm and 15 ohm Output. Hi-Fi quality at reasonable cost. Bass Boost and Treble controls, quality sectional output transformer, 40 c/s-25 kc/s ± 1dB. 100mV for 3W, less than 1% distortion. Bronze escutcheon panel.

Complete Kit only £6.19.6. Carr. 5/- Wired and tested 8 gns.

MULLARD "5-10" AMPLIFIER 5 valves 10W, 3 and 15 ohms output.

Mullard's famous circuit with heavy duty ultra-linear quality output trf. Basic amplifier kit price £9.19.6. Carr. 7/6. Ready built 11 1/2 gns.

CONTROL PANEL KIT

Bass, Treble and Volume controls with 4-position selector switch for radio, tape and pick-up and 1 1/2" x 4" escutcheon panel.

Amplifier Kit and Control Panel Kit £11.19.6. Ditto ready wired £14.19.6.

2-VALVE PRE-AMP. UNIT

Based on Mullard's famous 2-valve (2 x EF86) circuit with full equalisation with volume, bass, treble, and 5-position selector switch. Size 9" x 6" x 2 1/2". Complete Kit £5.19.6. Carr. 3/6. Ready built £7.19.6.

Send for detailed bargain lists, 3d. stamp. We manufacture all types Radio Mains Trans. Chokes, Quality O/P Trans., etc. Enquiries invited for Specials, Prototypes for small production runs. Quotation by return.

RADIO COMPONENT SPECIALISTS

70 Brigstock Road, Thornton Heath, Surrey
TO 2188. Hours; 9 a.m.-6 m. 1 p.m. Wed. Terms
C.W.O. or C.O.D. Post and Packing up to 1 lb. 9d., 1 lb. 1/3, 3 lb. 2/3, 5 lb. 2/9, 8 lb. 3/6.



Est. 1946

Pioneers in build it yourself tuners and test equipment

Jason KITS

Jason were first to produce a stable switched f.m. tuner for reception of BBC transmissions and an outstanding success has been achieved with the introduction of simple-to-operate switched tuners to receive both f.m. and TV sound transmissions. Jason tuners and test equipment offer a wide choice of models designed to meet present-day requirements and are a delight to build.

OTHER JASON KITS

FMT1 F.M. Tuner, less valves	£5.19.0
MERCURY 11 Switched Tuner, less valves	£9.15.4
ARGUS Transistor M.W. Tuner, complete	£7.10.0
OG10 Oscilloscope, less c.r.t.	£18.10.0
W11 Wobbulator, complete	£14.19.0
EM10 Valve Voltmeter, complete	£23
SB26 Tape Deck (built only) ½-track mono	31 gns.
	4-track stereo 39 gns.



JTV2 SWITCHED TUNER for the reception of all BBC f.m. transmissions and BBC-I and ITV television sound channels at the turn of a switch. Foster-Seeley discriminator. Built-in power supply. Sensitivity 10µV for 40dB quieting. Audio output 0.4V approx. All components, including turret and coil plate but less four valves—£14.0.4.



FMT2 FM TUNER covering 88-108 Mc/s. Built-in power supply sensitivity better than 100µV for 40dB quieting. All components, less four valves, £9.9.0, less power supply components, £7.15.0.

FMT3 TUNER similar appearance to above, but for fringe area reception. All components, less valves, £10.9.0, less power supply components, £8.15.0.



JTL TAPE PREAMPLIFIER designed to suit any tape deck or head. Will simultaneously record and play back stereo or mono using two or four-track heads. Especially recommended for use with the Lorlin SB26 tape deck. (Send for details.) All components including valves, £22.1.0. Ready built and tested £30.9.0.



AG10 AUDIO GENERATOR. Excellent stability with constant output over entire range. Tunes from 10 c/s to 100 kc/s in four switched ranges. Square wave or sine wave outputs. Square wave rise time less than 2µsec. at all frequencies. Minimum calibrated output 100mV. Self-powered. All components, including valves, £15.19.0.


Write for descriptive leaflets and name of nearest stockist

Jason KITS

VISIT OUR
NEW WEST END
SHOWROOM

18 TUDOR PLACE, TOTTENHAM COURT ROAD, LONDON, W.1

Telephone: MUSEUM 4666/8

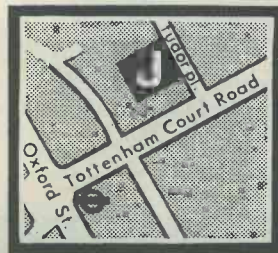

THE MOST OUTSTANDING

SINCLAIR


① MICRO-6 SIX-STAGE POCKET RECEIVER

*The smallest set in the world!
Easily built in an evening!*

THE 100% BRITISH DESIGNED SINCLAIR MICRO-6 continues unchallenged as the most remarkable receiver of its kind ever made available to the public anywhere in the world. It has special 6-stage circuitry and is, at the same time, the smallest set on earth. Everything except the lightweight earpiece is contained in the smart, minute white, gold and black case which is appreciably smaller than a matchbox, as the illustration shows. With vernier-type tuning control, bandspread over the higher frequency end of the medium waveband and powerful A.G.C. to ensure fade-free reception of the most distant stations, the Micro-6 provides remarkable standards of performance. Quality of reproduction is outstandingly good, and again and again the set is reported to give excellent results where other sets cannot be used at all. Order yours now and you will at once see why the Micro-6 cannot be too highly recommended, both as an intriguing design to build, and a most practical radio to use.



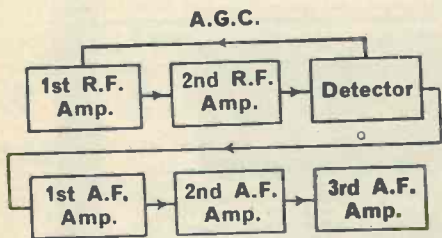- SIZE 1 1/5" x 1 3/10" x 1 1/2"
- WEIGHS UNDER 1 OZ
- BAND SPREAD TUNING FOR EASY RECEPTION FROM LUXEMBOURG
- VERNIER-TYPE TUNING OVER MEDIUM WAVE BAND
- CHOICE OF MANY STATIONS
- BATTERIES AND FERRITE ROD AERIAL CONTAINED IN CASE



SIX-STAGE POWER AND SELECTIVITY

The Micro-6 uses only three Micro-Alloy Transistors in a unique and very efficient circuit as follows: Two stages of R.F. amplification are followed by an efficient double-diode detector which drives a high-gain 3-stage A.F. amplifier. Powerful A.G.C. applied to the first R.F. stage ensures fade-free reception from the most distant stations tuned in. Everything including ferrite-rod aerial and batteries is contained within the elegant tiny case.

Building is simple. All parts including lightweight earpiece, case and dial, and 8-page instructions manual come to

59'6


Sinclair "Transista" well-styled, strong black nylon wrist strap Mally Mercury Cell Type ZM312 (2 required) each **7/6** **1/11** Pack of 6 **10/6**

②

SINCLAIR

TR750 POWER AMPLIFIER

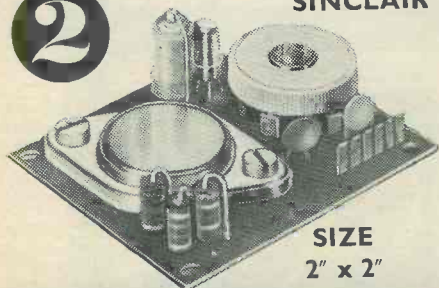Designed specially for use with the Micro-6



SIZE
2" x 2"

THE TR750 enables the Sinclair Micro-6 Receiver to be used as a powerful car, domestic or portable loud-speaker set. A connecting plug is provided for this. The TR750 also has many other applications such as a record reproducer, intercom or baby alarm. An output of 750 milliwatts for feeding into a standard 25-30Ω loudspeaker requires only a 10mV input into 2kΩ. Frequency response 30-20,000 c/s ±1dB. Power required—9 to 12 volts.

All parts with instructions come to

39/6

Ready built and tested with instructions

45/-


sinclair

SINCLAIR RADIONICS LTD
COMBERTON, CAMBRIDGE Telephone: COMBERTON 682

DESIGNS OF THE YEAR

3 SINCLAIR X-10

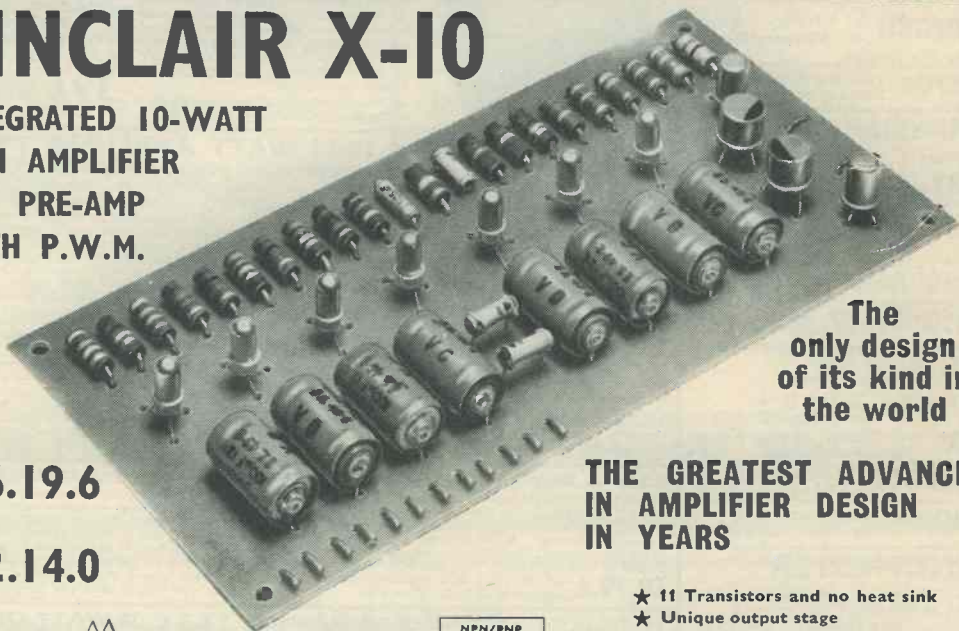INTEGRATED 10-WATT
HI-FI AMPLIFIER
AND PRE-AMP
WITH P.W.M.



The
only design
of its kind in
the world

Cost of all parts
together with In-
struction Manual

£5.19.6


Ready built and
tested together
with Instruction
Manual

£6.19.6

Mains power sub-
ply unit (A.C.
200-240 volt) to
drive one or two
X-10 amps.

£2.14.0

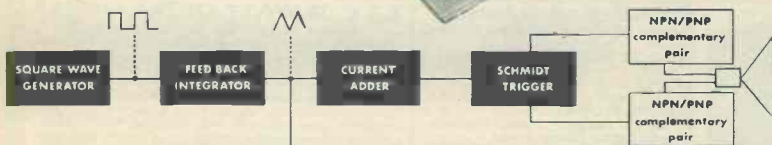THE GREATEST ADVANCE
IN AMPLIFIER DESIGN
IN YEARS



**Pulse-width modulation for
superb performance standards**

The principle of P.W.M., used in this remarkable amplifier which is complete with its own pre-amp stage and unique output stage, is briefly as follows: A square wave of constant voltage amplitude and with a frequency well above the highest audio-frequency to be reproduced, is applied to the terminals of the load. As the load has a high impedance at this frequency, negligible current flows through the voice coil of the speaker.

When an input signal is applied, the mark-space ratio changes with the result that there

is a net current flowing through the voice coil which deflects the cone. When the input signal is at any frequency up to 20 kc/s the net current is an exact replica of the input signal and is independent of the transfer characteristics of the output transistors, making the distortion figures incredibly low. The output transistors act as switches and so dissipate negligible power. This enables us to use 5 Mc/s transistors for this with great savings in space, current consumption and costs. No heat sink is required.

- ★ 11 Transistors and no heat sink
- ★ Unique output stage
- ★ Add your own choice of tone control circuit
- ★ Input sensitivity 1mV into 1k Ω
- ★ Can be used with all types of inputs including low-output pick-ups and microphones
- ★ Total harmonic distortion < 0.1%
- ★ Output power 10 watts
- ★ Frequency response 5-20,000 c/s ± 0.5 dB
- ★ Speaker impedance 15 Ω
- ★ Damping factor—greater than 100
- ★ Quiescent consumption 75mA
- ★ Supply voltage 12 volts from batteries or mains supply unit
- ★ Size 6" x 3"

SINCLAIR X-10 MANUAL

Explains how the amplifier functions and how you can add the correct tone and volume control system to suit your precise requirements. A variety of systems is shown, none of which will add more than a few shillings to the original cost of your Sinclair X-10, be it for MONO or STEREO.

TO SINCLAIR RADIONICS LTD., COMBERTON, CAMBRIDGE. Comberton 682

Please send items detailed below £ s d

NAME

ADDRESS

TOTAL £

For which I enclose cash/cheque/money order

RC12

sinclair

GUARANTEE

If you are not completely satisfied with your purchase (and we are confident that you will be) your money will be refunded in full at once and without question.

Full Service Facilities always available to Sinclair Customers.

R.S.C. (Manchester) Ltd.

MAIL ORDERS TO:
 13 POST HOUSE, WYND, DARLINGTON
 Terms C.W.O. or C.O.D. No C.O.D. under £1. Postage 2/9 extra under £2. 4/6 extra under £5. Trade Supplied. S.A.E. with all enquiries, please. Personal shoppers welcomed at any of the branches below. Open all day Saturday.

BRADFORD 54 Morley Street, Nr. Alhambra Theatre (Half-day Wednesday)

BRISTOL 14 Lower Castle Street Half-day Wednesday

BIRMINGHAM 30/31 Gt. Western Arcade, opp. Snow Hill Station (No half-day)

DERBY 26 Osmaston Rd., The Spot (Half-day Wednesday)

DARLINGTON 13 Post House Wynd (Half-day Wednesday)

EDINBURGH 133 Leith Street (Half-day Wed.)

GLASGOW 326 Argyle Street (Half-day Tuesday)

HULL 51 Savile Street (Half-day Thursday)

LEICESTER 32 High Street (Half-day Thursday)

LEEDS 5-7 County (Mecca) Arcade (No half-day closing)

LIVERPOOL 73 Dale Street (No half-day closing)

LONDON 238 Edgware Road (Half-day Thursday)

MANCHESTER
 Callers welcome at our extensive new premises at 60A/60B Oldham Street (No half-day)

MIDDLESBROUGH
 106 Newport Road (Half-day Wed.)

SHEFFIELD 13 Exchange Street, Castle Market Bldgs. (Half-day Thursday)

Fane Heavy Duty Hi-Fi Speakers

12" 15 ohms. Cast chassis. Exceptionally robust 2" diam. Voice Coil Assemblies. 122/10 20 watt, 5 gns.; 122/10A 20 watt, 6 gns.; 122/12 20 watt, 7 gns.; 122/12A 20 watt, 8 gns.; 122/14 22 watt, 9 gns.; 122/14A 22 watt, 10 gns.; 122/17 25 watt, £11.17.6.; 122/17A 25 watt, £12.17.6.
 15" 15 ohms. Cast chassis. Exceptionally robust 2" diam. Voice Coil Assemblies. 152/12 20 watt, 12 gns.; 152/12A 20 watt, 13 gns.; 152/14 27 watt, 14 gns.; 152/14A 27 watt, 15 gns.; 152/17 35 watt, 16 gns.; 152/17A 35 watt, 17 gns.
 "A" indicates dual cone type. 30-17,000 c.p.s. Send S.A.E. for leaflets. Terms available.
FANE EXTRA HEAVY DUTY LOUD-SPEAKER 15" TYPE 153. 40 watts. Total flux 375,000 lines. Extremely high sensitivity. 15 ohm voice coil. Only 18 gns. or Deposit 37/6 and 12 monthly payments of 31/6.

R.S.C. SENIOR 15 WATT LEAD or RHYTHM GUITAR AMPLIFIER

High-fidelity push-pull output. Separate bass and treble "cut" and "boost" controls. Twin separately controlled inputs so that two instruments or "mike" and pick-ups can be used at the same time. Loudspeaker is a heavy duty high flux 12" 20 watt model with cast chassis. Cabinet is well-made and finished as Junior Model. Size approx. 18" x 18" x 8".
 Carr. 10/-. Send S.A.E. for leaflet. Or DEPOSIT 19 Gns. and twelve monthly payments of 33/4.



BASS-MAJOR 30 WATT GUITAR AMPLIFIER


A MULTI-PURPOSE HIGH FIDELITY, HIGH OUTPUT UNIT FOR VOCAL AND INSTRUMENTALIST GROUPS
 Eminently suitable for bass, lead or rhythm guitar and all other musical instruments

- ★ Incorporating two 12" heavy duty 25-watt high flux (17,000 lines) loudspeakers with 2" diameter speech coils. Designed for efficiency handling full output of amplifier at frequencies down to 25 c.p.s.
- ★ Dual Cone in 2nd speaker reproduces frequencies up to 17,000 c.p.s.
- ★ Heavily made cabinet of convenient size 24" x 21" x 14" has an exceptionally attractive covering in two contrasting tones of Vynair.
- ★ For 200-250V, 50 c.p.s., A.C. Mains operation.
- ★ Four jack socket inputs and two independent volume controls for simultaneous connection of up to four instrument pick-ups or microphones.
- ★ Separate bass and treble controls providing more than adequate "Boost" or "Cut".
- ★ LEVEL frequency response throughout the audible range.
- ★ SUPERIOR TO UNITS AT TWICE THE COST.

Send S.A.E. for leaflet OR DEPOSIT of £4.3.0 and 12 monthly payments of £3.9.11 Carr. 17/6.

39 1/2 Gns.

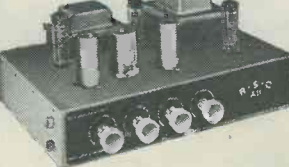HIGH FIDELITY 12-14 WATT AMPLIFIER TYPE A11 PUSH-PULL ULTRA LINEAR OUTPUT "BUILT-IN" TONE CONTROL PRE-AMP STAGES



Two input sockets with associated controls allow mixing of "mike" and gram, as in A10. High sensitivity. Includes 5 valves ECC83, ECC83, EL84, EL84, EZ81. High Quality sectionally wound output transformer specially designed for Ultra Linear operation and reliable small condensers of current manufacture. INDIVIDUAL CONTROLS FOR BASS AND TREBLE "Lift" and "Cut". Frequency response—3dB 30-30,000 c/s. Six negative feedback loops. Hum level 60dB down. Only 23 millivolts INPUT required for FULL OUTPUT. Suitable for use with all makes and types of pick-ups and microphones. Comparable with the very best designs for STANDARD or LONG PLAYING RECORDS. For MUSICAL INSTRUMENTS such as STRING BASS, LEAD OR RHYTHM GUITARS, etc.

OUTPUT SOCKET with plug provides 300V 30mA, and 6.3V 1.5A for supply of a Radio Feeder Unit. Size approx. 12" x 9" x 7". For A.C. mains 200-250V 50 c.p.s. Output for 3 & 15Ω speaker. Kit is complete to last nut. Chassis is fully punched. Full instructions and point-to-point wiring diagrams supplied. Carr. 10/- (Or factory built 51/- extra)

If required louvered metal cover with 2 carrying handles can be supplied for 18/9. **TERMS ON ASSEMBLED UNITS. DEPOSIT 24/9 and 9 monthly payments of 24/9.** Send S.A.E. for illustrated leaflet detailing Cabinets, Speakers, Microphones, etc., with cash and credit terms.

8 Gns.

R.S.C. G5 GUITAR AMPLIFIER

5-watt high quality output. Incorporating high flux 12" 10 watt 12,000 line loudspeaker. Sensitivity 50mV. High impedance jack input. Handsome strongly made cabinet (size 14" x 14" x 7" approx.) finished in complementary shades of Rexine/Tygan. 200-250 A.C. mains. Or DEPOSIT 22/3 and 9 monthly payments of 22/3. Carr. 7/6.

LINEAR TREMOLO/PRE-AMP UNIT

Designed for introducing the Tremolo effect to any amplifier which is fitted with a reserve power supply point for smoothed H.T. and 6.3V A.C. L.T. This applies to practically all amplifiers of our manufacture, and to those of several other manufacturers. The unit plugs into power supply point and any input socket or amplifier. Controls are Speed (frequency of interruptions), Depth (for heavy or light effect), Volume and Switch. Three sockets are for two inputs and Foot Switch. **ONLY 4 Gns.**

R.S.C. CORNER CONSOLE CABINETS

Polished walnut veneer finish. Pleasing design.
JUNIOR MODEL. Size 20" x 11" x 8" for 8" x 8" or 10" x 6" speakers, £2.9.9.
STANDARD MODEL. Size 27" x 18" x 12" for 8" or 10" speakers, £4.11.9.
SENIOR MODEL. Size 30" x 20" x 15" for 12" Speaker. Suitable Speaker systems below. Only 7 gns.
R.S.C. BASS REFLEX CABINETS, JUNIOR MODEL. Specially designed for W.B. HF1012 Speaker, but suitable for any good quality 10" speaker. Acoustically lined and ported. Polished walnut veneer finish. Size 18" x 12" x 10". Handsome appearance. Ensure superb reproduction for only £3.19.6.

STANDARD MODEL. As above but for 12" speakers. Size 20" x 15" x 13". For vertical or horizontal use. £5.19.6. Set of legs with brass ferrules, 19/6.

AUDIOTRINE HI-FI SPEAKER SYSTEMS. Consisting of matched 12" 12,000 line, 15 ohm high quality speaker, crossover unit (consisting of choke, condenser, etc.) and Tweeter. The smooth response and extended frequency range ensure surprisingly realistic reproduction. Standard 10 watt rating £4.19.9. Carr. 5/-. Or Senior 15 watt, £6.19.9. Carr. 7/6.
HEAVY DUTY LOUDSPEAKERS in substantial Rexine cov. Cabinets. Type BG1. Suitable for Bass Guitar. Speaker Unit 15", High Flux, 15Ω, 30W. Cabinet approx. 24" x 21" x 13". Only 19 1/2 gns. Or Deposit 43/- & 12 monthly payments of 34/-.

R.S.C. 30-WATT ULTRA LINEAR HIGH FIDELITY AMPLIFIER A10

A highly sensitive Push-Pull high output unit with self-contained Pre-amp. Tone Control Stages. Certified performance figures compare equally with most expensive amplifiers available. Hum level 70dB down. Frequency response ±3dB 30-20,000 c/s. A specially designed sectionally wound ultra linear output transformer is used with 807 output valves. All components are chosen for reliability. Six valves are used, EF86, EF86, ECC83, 807, 807, GZ34. Separate Bass and Treble Controls are provided. Minimum input required for full output is only 12 millivolts so that any kind of microphone or pick-up is suitable. The unit is designed for Clubs, Schools, Theatres, Dance Halls or Outdoor Functions, etc. For use with Electronic Organ, Guitar, String Bass, etc. For standard or long-playing records. Output Socket provides L.T. and H.T. for Radio Feeder Unit. An extra input with associated vol. control is provided so that two separate inputs such as Gram and "Mike" can be mixed. Amplifier operates on 200-250V 50 c/s. A.C. mains and has output for 3 and 15 ohm speakers. Complete Kit of parts with fully punched chassis and point-to-point wiring diagrams and instructions. If required, perforated cover with carrying handles can be supplied for 19/9. The amplifier can be supplied for 19/9. The amplifier can be supplied for 19/9. The amplifier can be supplied for 19/9.

11 Gns. Carr. 10/-
 Send S.A.E. for leaflet. **TERMS: DEPOSIT 33/9 and 9 monthly payments of 33/9.** Suitable mikes and speakers available at competitive prices.

R.S.C. B20 Bass Guitar Amp.

A highly efficient unit incorporating a massive 15" high flux loudspeaker specially constructed to withstand heaviest load conditions. Rating 25 watts. Individual bass and treble controls give ample "boost" and "cut". Two high impedance jack socket inputs are separately controlled. All controls are conveniently positioned in a recess on top of the cabinet. Cabinet is of substantial construction and attractively finished in two contrasting tones of Rexine and Vynair. Size approx. 24" x 21" x 13". Operation from 200-250V 50 c.p.s. A.C. mains.
 Send S.A.E. for leaflet. Or Deposit 39 1/2 Gns. £3.2.0 and 12 monthly payments of 51/8. Carr. 17/6.

12 in. 10-WATT HIGH QUALITY LOUDSPEAKER

In walnut veneered cabinet, Gauss 12,000 lines. Speech coil 3 ohms or 15 ohms. Only £4.19.6. Carr. 5/-.
 Terms: Deposit 11/3 and 9 monthly payments of 11/3. **12" 20 WATT HI-FI LOUDSPEAKERS IN CABINETS.** Size 18" x 13" x 10" Finish as above. Terms: Deposit 17/9 and 9 monthly payments of 17/9.
 Only **£7.19.6** Carriage 8/6

THE MODERN BOOK CO

Transistor Ignition Systems Handbook. By B. Ward. 20s. Postage 9d.

Know Your Oscilloscope. By P. C. Smith. 20s. Postage 9d.

Understanding Electronic Components. By F. J. Waters. 24s. Postage 1s.

Electronic Test Instrument Handbook. By J. A. Risse. 35s. Postage 1s.

ABC's of Boolean Algebra. By A. Lytel. 16s. Postage 9d.

How to Read Schematic Diagrams. By D. E. Herrington. 18s. Postage 9d.

Diode Circuits Handbook. By R. P. Turner. 18s. Postage 1s.

101 Ways to Use your VOM (Test-meter) and VTVM (Valve Voltmeter). By R. G. Middleton. 16s. Postage 9d.

The Transistor Radio Handbook. By D. L. Stoner and L. A. Earnshaw. 44s. Postage 1s.

Basic Electronic Circuits. Part 2. 18s. Postage 1s.

Organ Builder's Manual. By Artisan Organs. 35s. Postage 1s. 6d.

Hi Fi Year Book 1964. 10s. 6d. Postage 1s.

Aerial Handbook. By G. A. Briggs with R. S. Roberts. 8s. 6d. Postage 9d.

BBC2 Receiver Techniques. By E. A. W. Spreadbury. 7s. 6d. Postage 6d.

Radio Valve Data. 7th ed. Compiled by "W.W." 7s. 6d. Postage 10d.

The Amateur Radio Handbook. An R.S.G.B. Publication. 34s. Postage 2s.

Complete Catalogue 1s.

We have the Finest Selection of British and American Radio Books in the Country

19-21 PRAED STREET (Dept RC) LONDON W2

Telephone PADdington 4185

COMPONENTS FOR THE

"ALL BAND COMMUNICATION RECEIVER"

MAXI-Q

"BASIC SUPERHET FOR BEGINNERS"

as featured on page 699 in the May issue
Available end of December.

as featured on page 688 in the May issue

COIL TURRET CT.7/B

This turret is the basic portion of the CT.7. It comprises cadmium plated steel frame (5½" deep x 4½" high x 3½" wide), silver plated contacts, polystyrene insulation and rotary turret movement, incorporating Aerial, Mixer and Oscillator Coils for the three bands 1.5-4 Mc/s, 4-12 Mc/s and 10-30 Mc/s. Price 75/-

Coil strips for the long and medium wavebands may be purchased separately for incorporation in the turret. Price 10/6 each

The turret requires a 315pF tuning capacitor. A suitable 3-gang component with ceramic insulation is available. Price 19/-

Air spaced concentric trimmers 3-30pF Price 3/6 each

I.F. TRANSFORMER IFT.11/465 kc/s

A miniature I.F. Transformer for 465 kc/s giving excellent performance at low cost. Coils are litz wound and permeability tuned with high-grade iron-dust cores and silver mica capacitors. Screening Can 1½" x 1½" square. Price 6/6 each

Also available for 1.6 and 10.7 Mc/s.

BEAT FREQUENCY OSCILLATOR COIL BFO.2/465 kc/s

These compact coils are wound on a bakelite former complete with adjustable iron-dust cores enclosed in an aluminium screening can measuring 1½" x 1½" square. Price 5/- each

Also available for frequencies of 85 kc/s, 100 kc/s and 1.6 Mc/s.

COIL PACK CP.3/F

This 4-waveband coil pack is for use with a 500pF 2-gang condenser and covers the standard Long, Medium and Short Wavebands with the addition of the band 50-160 metres (1.85-6 Mc/s). It comprises of Aerial and Oscillator coils with iron-dust tuning cores, wavechange switch and mica compression trimmers mounted on an aluminium plate measuring 4½" x 2½" x 1" (not including spindle). Price 49/- plus 8/2 P.T.=Total 57/2

Two-gang 315pF Tuning Condenser Price 14/8

General Catalogue covering full range
of components, send 1/6 in stamps

STOP PRESS 3 Pole 3 way Bank Switch 7/6 each. 1 Pole 8 way 4/3 each.

PLEASE SEND S.A.E. WITH ALL ENQUIRIES

DENCO (Clacton) LTD

(DEPT. RC), 357/9 OLD ROAD
CLACTON-ON-SEA, ESSEX

HOME RADIO Ltd.

187 LONDON ROAD, MITCHAM, SURREY (MIT. 3282)


Shop hours:

9-5.30, including Saturday

Friday, 9-6.30

Closed all Wednesday

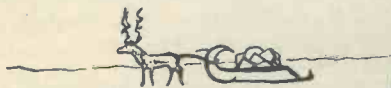*There's a hole in your baggage
Dear Santa!
Dear Santa!*



We trust that your HOME RADIO CATALOGUE is not among those giving Santa the slip! But just in case you haven't yet ordered one (dreadful thought) here is a gentle reminder. Fill in the Coupon and send it off today with cheque or P.O for 6/-.

**HOME RADIO LTD.
WISHES EVERYONE A
MERRY XMAS AND
A HAPPY NEW YEAR!**



Remember...

For every complete £1's worth of Components you order from us you can enclose one of the Coupons from our Catalogue and deduct a shilling from your remittance.

Enclose P.O. for 6/-

Name

Address

Home Radio Ltd., Dept. R.C., 187 London Road, Mitcham, Surrey

THE Radio Constructor

Incorporating THE RADIO AMATEUR



DECEMBER 1964

Vol. 18, No. 5
Published Monthly
(1st of month)

*Editorial and
Advertising Offices*

57 MAIDA VALE LONDON W9

Telephone
CUNningham 6141

Telegrams
Databux, London

First Published
1947

Portable P.A. Amplifier, <i>by V. E. Holley</i>	300
Can Anyone Help?	305
Hybrid A.F. Mixer Circuit for Valve Amplifiers (Suggested Circuit No. 169) <i>by G. A. French</i>	306
Electronic Locks and Anti-Thief Devices, Part 1, <i>by R. M. Marston</i>	309
News and Comment	314
Relay Binary Circuit—"Magic" Switching for your Christmas Lights, <i>by B. W. Osborn</i>	315
Understanding Radio (Introducing the Valve), <i>by W. G. Morley</i>	317
Economical Hybrid Amplifier and Portable Receiver Circuits, <i>by Sir Douglas Hall, K.C.M.G., B.A.(Oxon).</i>	322
Two-Way Home Telephone System, <i>by J. N. Price</i>	325
In Your Workshop	327
Constructing a Solid Bass Guitar, <i>by Angus Geddes</i>	334
Errors in Measurement, <i>by James Robert Squires</i>	337
Experiences of an Early Amateur, Part 5, <i>by C. H. Gardner</i>	340
The New Dual-Standard TV Sets, Part 8, <i>by Gordon J. King, Assoc.Brit.I.R.E., M.T.S., M.I.P.R.E.</i>	342
A Repeater Timer, <i>by A. P. Ainge</i>	345
500 kc/s Crystal Frequency Marker, <i>by Wallace Studley</i>	347
Trade News: The Sinclair "X-10" Integrated Amplifier	349
Radio Topics, <i>by Recorder</i>	350
1964 International Radio Communication Exhibition	352

© Data Publications Ltd., 1964. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription 33s. (U.S.A. and Canada \$5) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers please pay by cheque or International Money Order.

Published in Great Britain by the Proprietors and Publishers Data Publications Ltd. 57 Maida Vale London W9
Printed by A. Quick & Co. (Printers) Ltd. Oxford Road Clacton-on-Sea England



Portable

P.A.

Amplifier

V. E. HOLLEY

An inexpensive 10 watt design incorporating readily available components

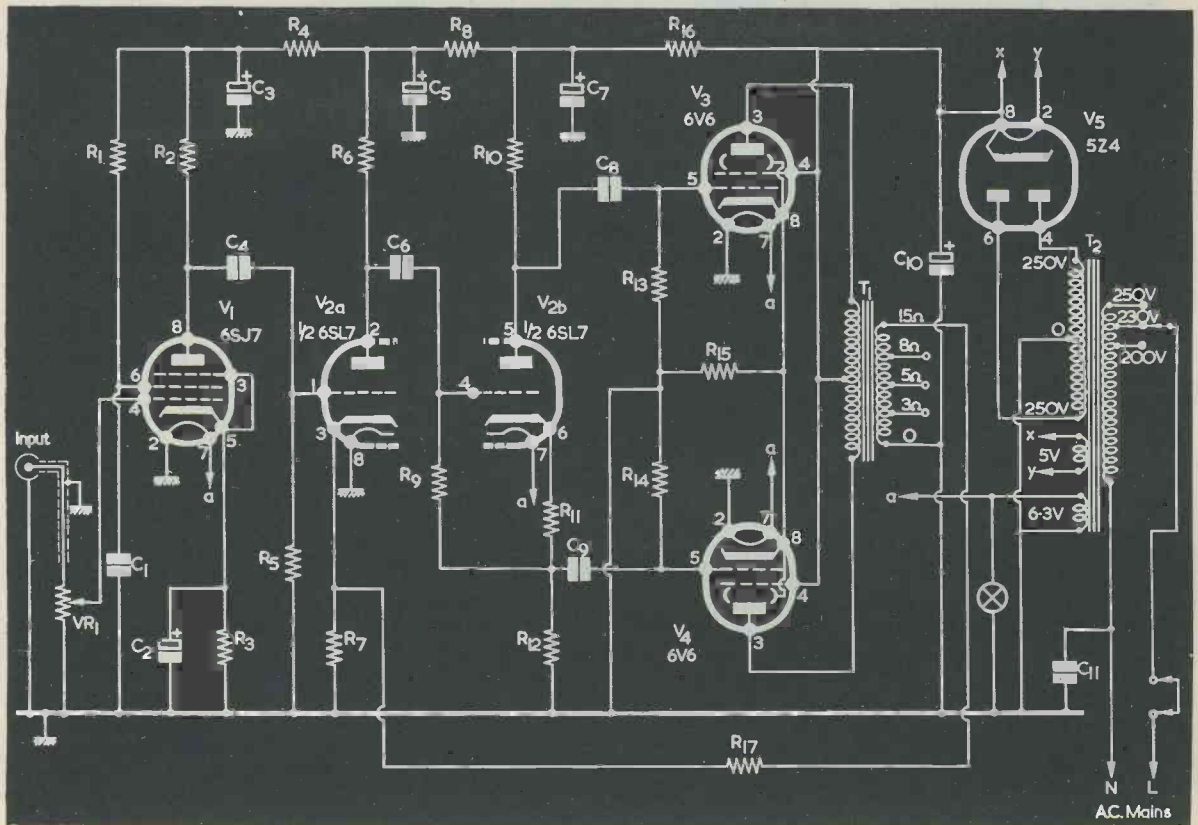


Fig. 1: The circuit of the 10 watt amplifier

THIS EQUIPMENT WAS DESIGNED AND BUILT FOR the use of a travelling lecturer who had, on occasion, to address large audiences. Though small in size and weight, it has an output of 10 watts and will give a good account of itself. The circuit is simple and the components few and inexpensive.

Design Considerations

Minimum size and weight are the primary considerations and the completed amplifier can be enclosed in a carrying case measuring only 10 x 7 x 5in, with a total weight of 7 lb. The requirement for clean, crisp reproduction of speech is met by introducing some attenuation of the lower audio frequencies, but this is done entirely at the input and output. The amplifier itself is suitable for any service and it will, in fact, reproduce music at a very acceptable standard of fidelity. Space does not permit the introduction of tone controls.

Circuit

The circuit is shown in Fig. 1. Surprise may

be felt at the use of octal valves, but these are more robust and less likely to be dislodged from their bases than are the more modern all-glass variety. Such considerations outweigh the disadvantage of size in portable equipment.

Power Supply

To keep the weight down, the power supply is obtained from a double wound mains transformer having a full wave h.t. secondary rated at only 250-0-250V, 80mA. Using a 5Z4 rectifier and a 32 μ F reservoir capacitor (C₁₀), a d.c. voltage of 300 is available at the reservoir under working conditions. This leaves no margin for voltage drop in smoothing components and so the output stage is fed direct from C₁₀. There is, of course, a large hum voltage at this point but since, with the push-pull connection, current flows through the two halves of the output transformer primary in opposite directions, it is largely cancelled out, leaving a satisfactorily low background level.

The mains transformer must have a 5V 2 amp. winding for the rectifier and a 6.3V winding for

Components List

Resistors

(All fixed resistors 10% $\frac{1}{2}$ watt unless otherwise stated)

R ₁	1.2M Ω , high-stability
R ₂	270k Ω , high-stability
R ₃	1.2k Ω
R ₄	47k Ω
R ₅	1.2M Ω
R ₆	100k Ω
R ₇	3.3k Ω
R ₈	22k Ω
R ₉	1.2M Ω
*R ₁₀	100k Ω
R ₁₁	3.9k Ω
*R ₁₂	100k Ω
*R ₁₃	470k Ω
*R ₁₄	470k Ω
R ₁₅	270 Ω , 2 watts
R ₁₆	4.7k Ω
R ₁₇	15k Ω
VR ₁	2M Ω potentiometer, log track

* Matched pairs.

Capacitors

(All capacitors 350V wkg. minimum unless otherwise stated—see text)

C ₁	0.01 μ F
C ₂	25 μ F electrolytic, 12V wkg.
†C ₃	8 μ F electrolytic
C ₄	0.01 μ F
†C ₅	8 μ F electrolytic
C ₆	0.01 μ F
†C ₇	16 μ F electrolytic
C ₈	0.01 μ F
C ₉	0.01 μ F
†C ₁₀	32 μ F electrolytic
C ₁₁	0.02 μ F paper, 250V a.c. wkg.

† C₃ and C₅ are in a single can as are C₇ and C₁₀.

Valves

V ₁	6SJ7
V ₂	6SL7
V ₃	6V6
V ₄	6V6
V ₅	5Z4

Transformers

T ₁	Mains transformer with tapped primary. Secondaries, 250-0-250V, 80mA; 6.3V, 2 amp; 5V, 2 amp. Upright mounting (see text)
T ₂	Output transformer. Push-Pull, 10-12 watts, 6V6 to 3, 5, 8 or 15 Ω . (R.S.C. (Manchester) Ltd., 54 Wellington Street, Leeds, 1)

Speakers

Re-entrant or cone units, as required

Microphone

Crystal microphone with floor stand

Lamp

M.E.S. indicator lamp, 6.3V, 0.3 amp.

Plugs and Sockets

1 octal plug
1 coaxial input plug
6 octal sockets
1 indicator lamp holder
1 coaxial input socket

Miscellaneous

Chassis, 16 s.w.g. aluminium (see Fig. 2)
1 2-way tagstrip
2 $\frac{1}{4}$ in grommets
Wire, etc.

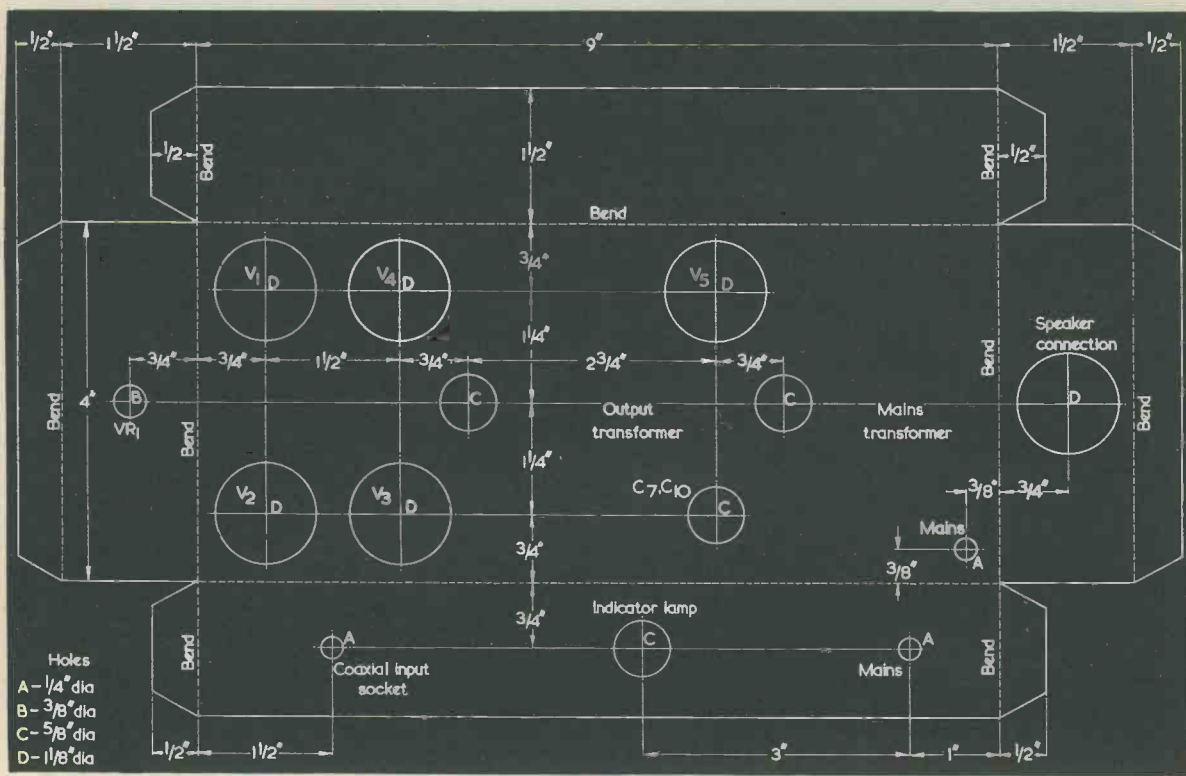


Fig. 2. The dimensions and principal holes in the chassis. The $\frac{5}{8}$ " hole for $C_{7,10}$ may need to be larger for some components. Before drilling mounting holes for the valveholders, check against Fig. 3 for orientation

the other valve heaters and indicator lamp, which together need 1.8 amp. No mains switch is provided but in order to avoid damage to the output valves should the amplifier be operated accidentally with no load, it is arranged that the withdrawal of the loudspeaker connecting plug shall interrupt the mains supply. It is convenient if the mains transformer has a mains voltage adjuster but if it has not, one can be fitted separately on the chassis in a position where it will be easily accessible in service.

Capacitor C_{11} , connected between the chassis and the neutral supply line, serves as an effective earth connection, as will be explained later. It may not always be needed.

Output Stage

The output stage employs a pair of valves type 6V6. The anodes and screen-grids are fed from the 300V h.t. line which, allowing for bias, provides about 280V, between these electrodes and the cathodes. The use of a common bias resistor, R_{15} , has two advantages. Firstly, because the signal currents through the valves cancel out at the cathodes, no bypass capacitor is required and, secondly, it tends to minimise differences between the valves so that exact matching is not necessary. It is well, though to check that the valves are not widely different. The value of R_{15} is a little on

the high side in order to keep the h.t. current within the capacity of the 80mA mains transformer secondary. The optimum anode-to-anode load is 8,000 ohms. The prototype uses one or two speakers (in series) of 7.5 Ω impedance and the ratios provided by the output transformer are therefore 33:1 and 24:1. If it is desired to use a 3 Ω speaker, a ratio of 50:1 will be needed.

Phase Inverter

For full loading, the output stage requires a signal of about 36V grid-to-grid and this is provided by $V_{2(b)}$ arranged as a phase inverter with equal anode and cathode loads of 100k Ω . These resistors, R_{10} and R_{12} , must be matched as closely as possible as also must the grid resistors of the output stage, R_{13} and R_{14} . The grid resistor for the inverter stage, R_9 , is returned to the junction of the bias and cathode load resistors, and since R_{11} is very small in relation to R_{12} , there is no point in bypassing it. The signal is applied to the stage between grid and earth so there is heavy negative current feedback and, as might be expected, the gain is low; it is in fact limited to 0.9 times each side or 1.8 times overall, so that an input of $\frac{36}{1.8}$ or 20V peak is needed. There will be no overloading with this large signal since most of it goes to counteract negative feedback in the cathode load. The

power supply to this stage needs some smoothing, which is provided by R_{16} and the associated $16\mu\text{F}$ capacitor, C_7 .

Voltage Amplification

The signal required by the inverter is supplied by $V_{2(a)}$ arranged as a resistance-capacitance amplifier with both current and voltage negative feedback. It will be noted that the cathode bias resistor consists effectively of R_7 and R_{17} in parallel, and that a negative voltage feedback derived from the secondary of the output transformer is applied by way of R_{17} . This improves the response of the amplifier and removes any hum not eliminated by the push-pull connection in the output stage. If the greatest gain is required, the value of R_{17} may be increased up to $33\text{k}\Omega$ without raising the residual hum level unduly whilst, if quality be the aim, it can be reduced to $6.8\text{k}\Omega$, when hum will be almost completely inaudible.

Pre-amplification is needed to raise the microphone signal to a suitable level for injection to the grid of $V_{2(a)}$. This is provided by a high gain pentode, 6SJ7 , again resistance-capacitance coupled, and having the volume control, VR_1 in its grid circuit.

The overall gain of the amplifier is fairly high, especially if a high value is assigned to R_{17} , and care is necessary in the selection of the resistors R_1 and R_2 which should be of the high stability noise-free type. The valve V_1 must be free from any tendency to microphony and its h.t. supply must be free from ripple. The latter point is taken care of by resistor R_4 and capacitor C_3 .

Frequency Response

The desired frequency response for speech is achieved by using re-entrant speakers which have only a limited low frequency range and by employing at the input a crystal microphone, for which the recommended load is $5\text{M}\Omega$ or more. Such an instrument may be regarded as an a.c. generator having in series with its output a small capacitance and it follows that, if the load resistance be reduced, so will be the output at the lower frequencies. VR_1 is therefore given a value of $2\text{M}\Omega$ only.

Components

All the resistors can be $\frac{1}{2}$ watt except R_{15} , which must be 2 watts, and all the capacitors except the electrolytics and C_{11} should be ceramic so that they can be accommodated easily in the rather restricted space available below chassis around the valveholders. Capacitors connected to the h.t. circuits must be at least 350V wkg., and it is a good idea to use 500V wkg. components so that if the amplifier should by mistake be connected to 240V mains with the voltage adjuster set for say, 200V , the overload will not be likely to cause a breakdown. Capacitor C_{11} should be rated for 250V a.c.

There is little room to spare on the deck of the chassis and unless the mains and output transformers are of the type shown in the illustration, it may be necessary to increase the size to accommodate them. The transformers should therefore be obtained before commencing construction.

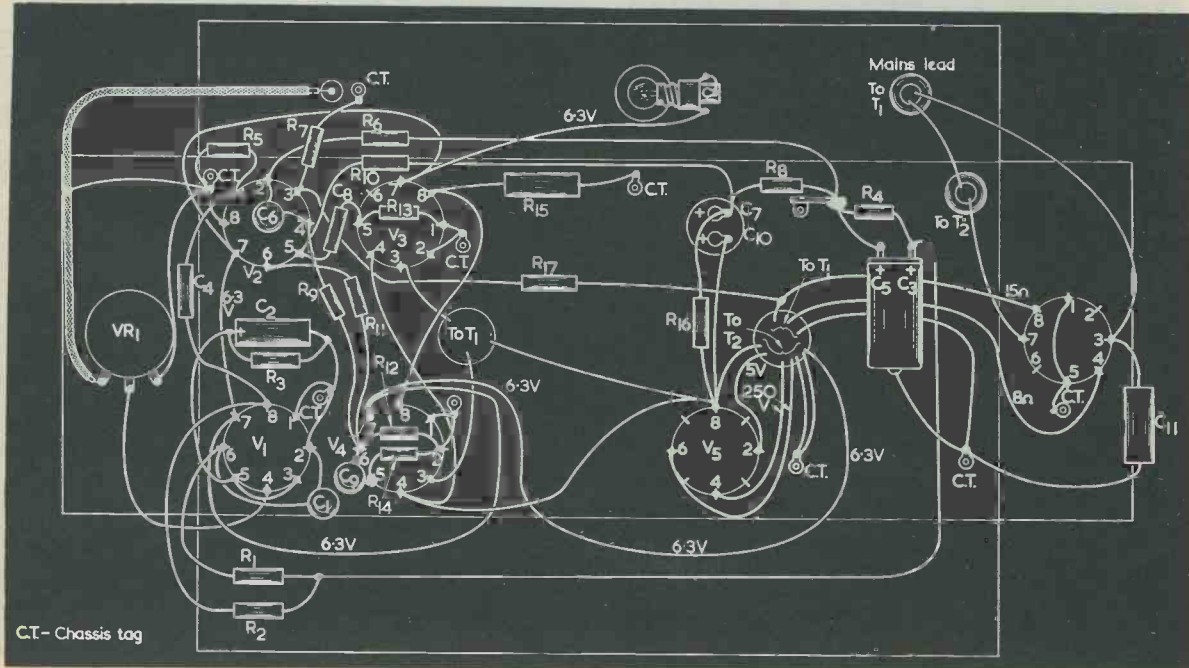


Fig. 3. The components and wiring below the chassis. Pin 6 of V_4 valveholder is employed as an anchor tag

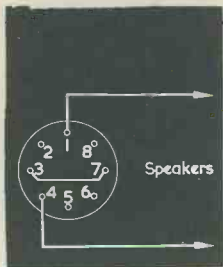


Fig. 4. Connections to the octal speaker plug. These enable one of two impedances to be selected

Construction

The amplifier is built on a chassis of 16 s.w.g. sheet aluminium measuring $9 \times 4 \times 1\frac{1}{2}$ in., a plan of which is given in Fig. 2. The work is quite straightforward and after the transformers and valveholders have been fitted, the wiring can proceed in any desired order. A wiring diagram is given in Fig. 3. The connections between the output transformer primary and the anodes of V_3 and V_4 should be sufficiently long to enable the leads to be changed over if, when the testing stage is reached, the feedback circuit is found to be positive. The speaker connection is made by way of an octal socket and this must be modified slightly by filing an additional keyway down the centre 180° opposite the existing one, i.e. between contacts 4 and 5. Check before fitting to the chassis that the modification permits the insertion of an octal plug in either of two positions, thus enabling the appropriate output transformer ratio to be selected according to the number of speakers in use. The wiring for the plug is shown in Fig. 4. The base of an un-serviceable octal valve makes a good plug and the impedance can be painted on opposite sides of it so that the correct figure is at the top when in position.

When metal valves are used, pin 1 of V_1 , V_3 and V_4 should be earthed, as shown in the wiring diagram.

Testing

When the wiring is complete and has been checked, connect a meter switched to a high resistance range between C_{10} and chassis to verify that there are no short-circuits in the h.t. wiring. If all is well, power can be applied and the operating voltages checked at the valve electrodes. As the valves warm up, there may be instability. If this occurs the mains supply should be switched off at once and the connections to the anodes of V_3 and V_4 interchanged to make the feedback negative. Residual hum should now be very low and, with VR_1 at minimum, should be inaudible at more than several feet from the speaker.

Carrying Case

Fig. 5 shows the construction of a simple carrying case made of $\frac{3}{8}$ in plywood. No skilled carpentry is needed here, and simple butt joints secured with panel pins and glue are adequate. If the cover is made a good fit round the amplifier chassis, the latter will be secured very firmly in position by its

flanges when the cover is screwed to the baseboard. Attention must be paid to ventilation and not less than three 1 in holes are required on each side and in the top and bottom of the case. These may be covered on the inside with perforated zinc secured with a reliable impact adhesive. Four rubber buffers should be fitted to the bottom of the baseboard so that it is raised a little from the surface on which it stands, thus permitting some under-chassis ventilation. The carrying handle is fitted at the point of balance.

Operation

The accessories for portable service should include lengths of mains, speaker and microphone cables sufficient to meet any likely contingency and a good assortment of various plugs and adaptors for making connection to the mains. A "neon mains tester" screwdriver is practically indispensable for detecting live outlets. Three-point outlets are by no means universal in many of the older buildings, so there is no point in using 3-core mains cable.

When an amplifier is operated with a high impedance input, it is often necessary to have an earth connection in order to avoid electrostatic hum pick-up. This is difficult with portable equip-

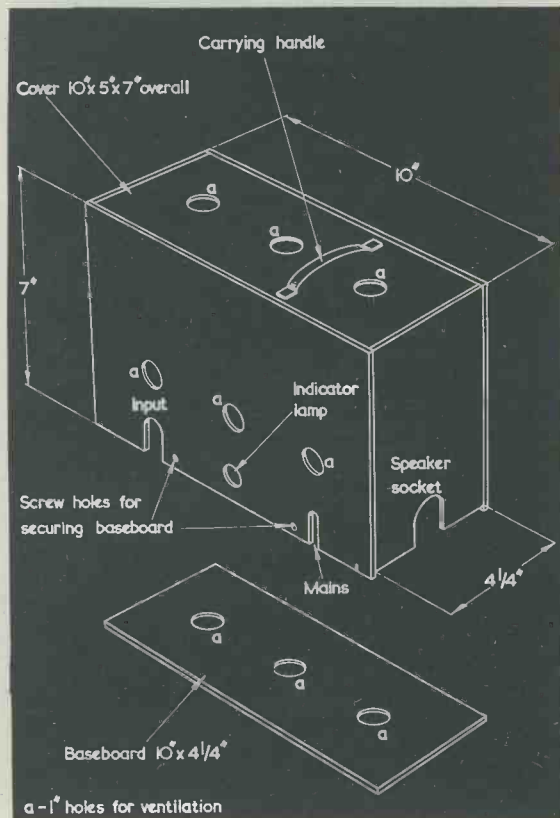


Fig. 5. Dimensions for a suitable carrying case. The handle is mounted at the point of balance. The material is 5 in plywood

ment but an equivalent result can be achieved by coupling the chassis to the neutral side of the mains through a capacitor (C_{11} in Fig. 1). Whether C_{11} becomes connected to the live or neutral main is a matter of chance at each connection but it can be checked by applying the mains tester to the chassis; if the tester glows, reverse the connection.* The most convenient operational arrangement is to site the amplifier near the foot of the microphone stand so that the mike cable is of no great length. Under these conditions, C_{11} may be found unnecessary and can be deleted. The re-entrant speakers have practically no output to the rear and may, if need be, be placed quite close to the microphone without fear of acoustic feedback.

Input

A cheap crystal microphone will provide a sufficient signal to load the amplifier fully. Alternatively, a moving-coil instrument may be used provided a suitable step-up transformer is interposed

* A capacitor such as C_{11} between one side of the mains and an amplifier chassis is employed with some commercial designs in order to prevent hum pick-up. If the connection to the mains supply is such that the live side connects to C_{11} , it is possible to experience a mild "tingling" type of shock when touching metal at chassis potential if the operator is standing on damp ground, a concrete floor, or a similar relatively low resistance substance. Because of this it is preferable to employ a capacitor in this circuit position only when entirely essential and to make quite certain that it connects to the neutral side of the mains. If the mains transformer has an electrostatic screen between primary and secondaries, this should be connected to chassis, whereupon it will probably be found that C_{11} is not needed. C_{11} should also not be needed if the amplifier chassis can be connected to a reliable earth. When C_{11} is fitted, it is essential that it be a completely reliable component with a minimum a.c. rating of 250V.—EDITOR.

before VR_1 . For reproducing music almost any high impedance pick-up is suitable and, as there is plenty of gain available, compensation for recording loss and a tone control may be added if desired. In designing such a network the aim should be to make the load on the pick-up at middle frequencies equal to that recommended by the manufacturer; VR_1 will of course be part of this load.

Output

The re-entrant type speakers recommended are very suitable for the reproduction of speech and have the advantage of small physical size but, if good fidelity is required for music, cone speakers should be used instead. Two 10in units will give excellent results. The re-entrants will, however, serve well enough for some purposes, such as background music at open-air functions. Speakers may be connected in series or in parallel according to their impedances, the series connection being preferable if there is a long run of cable. The recommended output transformer provides impedances of 3, 5, 8 and 15 Ω , any two of which can be made available at the speaker socket.

When two or more speakers are used, results will be inferior unless they are correctly phased. In other words, all the cones or diaphragms must be moving in the same direction at any instant. The terminals of re-entrant speakers often bear "+" and "-" signs for this reason. With cone units, the proper connections can be determined by connecting a 1.5V dry cell to the speaker line; place a finger lightly upon the cone and note the direction of movement as the circuit is made.

CAN ANYONE HELP?

Requests for information are inserted in this feature free of charge, subject to space being available. Users of this service undertake to acknowledge all letters, etc., received and to reimburse all reasonable expenses incurred by correspondents. Circuits, manuals, service sheets, etc., lent by readers must be returned in good condition within a reasonable period of time.

R109 Receiver.—A. R. Brackenborough, 41 Poets Corner, Margate, Kent, requires any information on this receiver, also details of a suitable power pack.

* * *

PCR2 Receiver.—W. Burke, GM3TQH, c/o 6 Belgrave Terrace, Glasgow, C.2, would like the circuit and any other data.

* * *

R1392.—W. J. Butt, 1 Harcourt Villas, London Road, Teynham, Sittingbourne, Kent, would be grateful for any information on this unit.


Ekco TV Model 155.—W. J. Robins, 7 Cedar Avenue, Birstall, Leicester, requires the circuit or any other information—particularly on the valve line-up.

* * *

CR100 Receiver.—B. Gordon, 72 Coldshott, Holland, Oxted, Surrey, requires loan or purchase of the manual for this receiver.

* * *

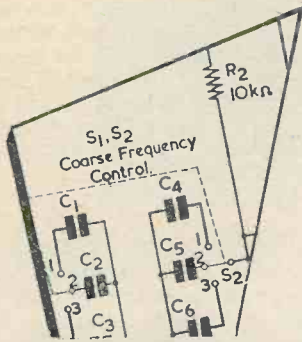BC620F and PSU.—D. W. Viton, 169 Worthing Road, Laindon, Basildon, Essex, would like to obtain any information, service manual or circuits of this ex-U.S. Army transmitter/receiver.



**SUGGESTED
CIRCUIT No. 169**



Hybrid A.F. Mixer Circuit

for

VALVE

AMPLIFIERS

By **G. A. FRENCH**

IT IS FREQUENTLY NECESSARY, WITH a.f. amplifiers, to cater for simultaneous amplification of two input channels. Gain controls are then required in each channel, and it is desirable for these to be completely independent of each other.

If cost is of importance the provision of separate independent controls is not always an easy matter, since the gain control circuits have to be completely isolated from each other. A typical solution, which assumes a valve amplifier, is shown in block

form in Fig. 1. In this diagram each gain control is followed by a buffer amplifier valve, the two valves sharing a common load across which the two signals are developed. The controls are completely independent of each other, but two valves are needed for a total overall gain equivalent to that offered by one. Independent gain control operation is achieved, therefore, at the cost of one valve.

An alternative and less expensive approach consists of using a circuit of the type shown in Fig. 2, in which

series isolating resistors are inserted after the sliders of the two gain controls. It is impossible to achieve complete isolation between the two controls here, because adjustment of one must inevitably alter the output level given by the other. The interdependence can be reduced to a fairly low level, however, by giving the series isolating resistors high values relative to the track resistance of the potentiometers, but limiting factors are imposed by the desirability (in most valve a.f. circuits) of having high values in the potentiometers and by the maximum external grid-cathode resistance specified for the following valve.

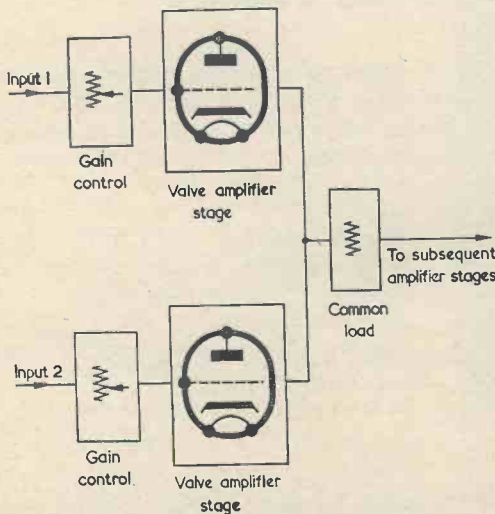


Fig. 1. One method of obtaining independent gain control in two a.f. channels consists of inserting buffer amplifier stages before a common load

The Hybrid Circuit

An unusual approach to this problem is offered in the hybrid mixer circuit shown in Fig. 3, which forms the basis of this month's Suggested Circuit. As may be seen, one input channel is applied to the grid of a triode voltage amplifier valve in normal manner, whilst the second input channel is fed to the base of a p.n.p. transistor. The latter functions as an emitter-follower, and causes the a.f. voltage on its base to be applied to the cathode of the triode. An amplified version of the signal then appears at the anode of the valve, in company with an amplified version of any a.f. signal fed to the grid.

Although the two input signals appear across the same anode load, R_4 , they are isolated at the input, and the operation of the two poten-

tiometers is completely independent.

The cathode bias voltage required by the triode is developed across the transistor, the actual voltage obtained being dependent upon the value of R_3 . Thus, the transistor and R_3 replace the normal cathode bias resistor and bypass capacitor, and may occupy approximately the same space on the chassis. Also, since the transistor need only be an inexpensive a.f. type, cost is kept at a low level. The valve will offer slightly less gain to the signal applied to its grid than would occur if it had a normal cathode bias circuit, this being due to the degeneration given by the absence of a cathode bypass capacitor.

Whilst the circuit of Fig. 3 has a number of advantages, it suffers from two restrictions. Firstly, the voltage amplifier employed should not appear in the early stages of a sensitive amplifier. This is due to the risk of hum pick-up from the heater because of the unbypassed cathode. The voltage amplifier could not, for instance, appear in a microphone pre-amplifier stage. Secondly, the input impedance for the second channel signal is low, being of the order (at the transistor base) of 10 to 30k Ω only.

In order to assist in explaining the operation of the circuit, Fig. 3 includes an input potentiometer in each channel. In practice, however, it would be possible to have the gain controls at earlier stages in either channel, whereupon the circuit reduces to that shown in Fig. 4. This circuit illustrates the fact that the transistor, together with R_3 and C_1 , could be incorporated in place of the cathode bias resistor and capacitor in an existing valve amplifier, thereby enabling a second channel to be injected without interfering with the functioning of the amplifier as it stands. The valve chosen for the modified cathode circuit could then be any voltage amplifier whose cathode may be left unbypassed without the onset of hum pick-up from the heater. As was mentioned earlier, there will be a slight reduction in gain due to the deletion of the cathode bypass capacitor. The relatively low input impedance offered by the transistor circuit would, incidentally, be no disadvantage if the equipment providing the second channel signal was, itself, transistorised.

The arrangement of Fig. 4 could be used for the injection of a vibrato voltage in a guitar amplifier.

In Figs. 3 and 4, the voltage amplifier is shown as a triode. The circuit would also function with a voltage amplifier pentode. However, the

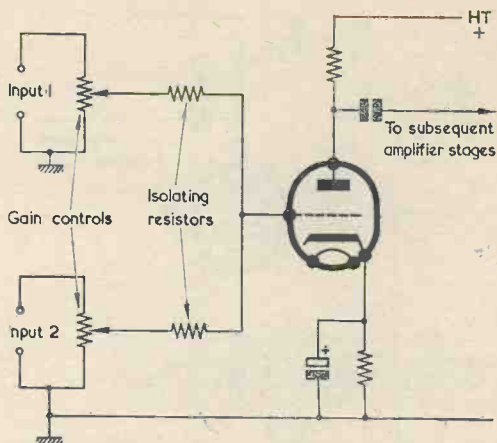


Fig. 2. A less costly method of providing gain controls for two channels. In this instance some interdependence between the settings of the two potentiometers is inevitable

checks carried out by the writer on the usefulness of the circuit were made with triodes only, these being a $\frac{1}{2}$ 12AX7 and a $\frac{1}{2}$ 12AU7.

Results with the Prototype

To check its usefulness, the circuit shown in Fig. 4 was made up in experimental form.

It was found that the transistor employed in the TR₁ position was in no way critical, and that satisfactory results were given by a variety of transistors ranging from an OC72 to an OC44. Each transistor required a different value in R_3 to enable the requisite cathode bias

voltage to be applied to the valve.

First tests were made using one triode of a 12AX7. The h.t. positive supply voltage was 250.

With a 100k Ω anode load at this voltage, the cathode bias potential for the 12AX7 should be approximately 2 volts. The value of R_3 was then experimentally adjusted until this voltage appeared between cathode and chassis. In the writer's set-up the required value was, typically, 82k Ω for the OC44. The circuit was then checked under static conditions to ensure that the cathode of the valve "followed" a varying potential applied to the base of the transistor.

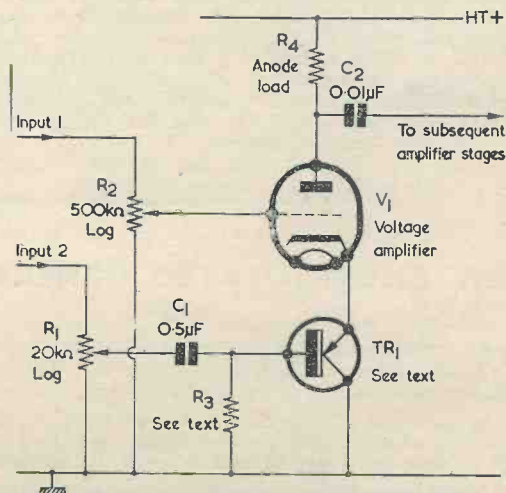


Fig. 3. A hybrid circuit which enables independent gain controls to be used. The cathode bias voltage for V_1 is dropped across TR₁. At the same time this transistor, operating as an emitter-follower, injects the second input into the cathode

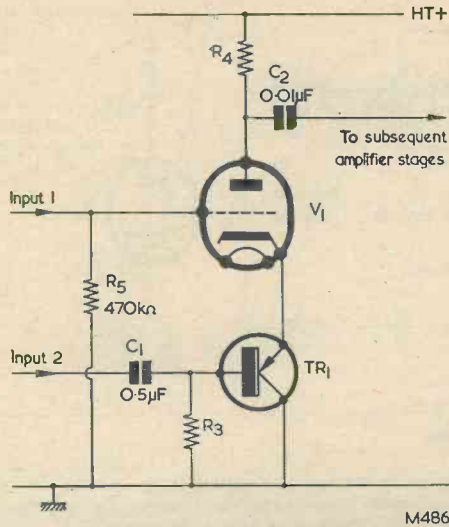


Fig. 4. It is not essential for the potentiometers of Fig. 3 to immediately precede the valve or the transistor. This diagram illustrates the fact that TR₁, C₁ and R₃ can be added to an existing valve amplifier in order that a second input channel may be handled

This occurred reliably over a swing from zero to +4 volts, relative to chassis. It could be assumed, therefore, that signals up to 4 volts peak-to-peak could be applied to the base of the transistor and be amplified satisfactorily. This is, of course, the maximum signal the valve can handle before the onset of grid current.

The $\frac{1}{2}$ 12AX7 was then replaced by a $\frac{1}{2}$ 12AU7. With a 250 volt h.t. supply and an anode load of 100k Ω , this valve requires 3.5 volts bias. Such a bias was obtained by adjusting R₃ to the typical value, for the OC44, of 91k Ω . A static voltage test then showed that the cathode "followed" the transistor base reliably for voltages from zero to +7

volts relative to chassis. A signal of 7 volts peak-to-peak could therefore be satisfactorily applied to the transistor circuit. Again, this is the maximum signal voltage the valve can handle without grid current.

Finally, music inputs were applied to both channels, the output across the anode load being fed to a subsequent amplifier. There was no evidence of distortion with either the 12AX7 or the 12AU7. It should be added that, although the value of R₃ was set up to give the correct bias voltage for each valve, no noticeable deterioration in quality was introduced when this value was shifted widely from its correct figure.

Practical voltage amplifier circuits

may employ different anode loads and h.t. voltages from those used by the writer for these checks. They will, in consequence, require different cathode bias voltages across TR₁. Such bias voltages may be obtained by adjustment of R₃. The value of this resistor is in any event experimental, as it depends upon the characteristics of the transistor employed. The transistor should not, of course, be used in a circuit which causes its maximum voltage or dissipation figures to be exceeded; but such a likelihood is remote so far as conventional voltage amplifier stages are concerned.

Further Points

It is possible to obtain a rough idea of the input impedance offered by the transistor by multiplying the cathode input impedance of the valve by α' . Assuming that input impedance is equal to the reciprocal of mutual conductance, the cathode input impedance of a 12AX7 is of the order of 800 Ω . If α' is 50, then transistor input impedance becomes 40k Ω . Shunted by the bias resistor, the final figure comes to some 25k Ω . The corresponding figure with a 12AU7 triode is around 14k Ω . These figures are intended to be a guide only, and it is not really advisable to attempt to increase them by the use of additional transistor circuitry, since the resulting complication would be of at least the same order as that resulting from introducing a second valve, as in Fig. 1. Some alleviation in this respect can, however, be given by employing a transistor having a high value of α' .

Since considerably less than half the supply voltage appears across the transistor in Figs. 3 and 4, there is no necessity to introduce d.c. stabilising components to prevent thermal runaway.

NEW ENCAPSULATED GENERAL PURPOSE RECTIFIERS

Pursuing the trend towards inexpensive encapsulation for semi-conductor devices, Mullard now introduce a plastic encapsulated silicon rectifier type BYX10 for general use. The hard plastic encapsulation is so successful that it readily fulfils the stringent requirements of the accelerated damp heat tests recommended by the I.E.C.

Designed to operate with an average forward operating current up to 200mA, the BYX10 will withstand a repetitive peak reverse voltage of up to 1.6kV and momentary "switching on" surge currents of up to 15A—both very important properties for an item which may be used in heavily inductive circuits.

Used in a single phase half wave circuit with resistive load, the rectifier can supply 200mA at 250V. These figures can be doubled to 400mA at 500V by using four rectifiers in a single-phase full-wave bridge circuit.

The wide range of possible applications include: power supplies for transistor and valve instrumentation, rectifiers for d.c./a.c. low power converters, logic elements in electro-mechanical systems and blocking diodes in mains equipment safety circuits.

Electronic Locks and Anti-Thief Devices

Part 1

by R. M. Marston

Protect Your Home By Electronics

THE ORDINARY TUMBLER LOCK IN GENERAL USE suffers from several disadvantages. Amongst these are the facts that skeleton keys can be made that will open any lock in a particular series, that most locks are easily picked by an expert, and that a wax impression of a key carelessly left about can easily and speedily be made; from which a replica of the original can be cut. All of these disadvantages stem from the fact that the "key" is a purely physical thing.

Electronic locks, on the other hand, suffer from none of these disadvantages. The "key" can be made a purely abstract thing, such as a series of numbers or letters carried around in one's mind. Or it can be some tangible but non-physical thing, such as a set of electronic signals, a combination of pre-determined voltages and currents, or a coded audio signal.

It must be pointed out at this stage that while ordinary locks usually combine both the lock and the latch mechanism, in the electronic device these two parts are considered as separate items, and it is only with the actual locks that this article is concerned. The latch itself may be a solenoid-operated unit that functions when the lock circuit is completed, or any other suitable device.

The only disadvantages of electronic locks are their cost and their vulnerability to electrical failure. By careful choice of components, cost can, however, be kept to a surprisingly low level, and the vulnerability to electrical failure can be eliminated by duplication of circuitry.

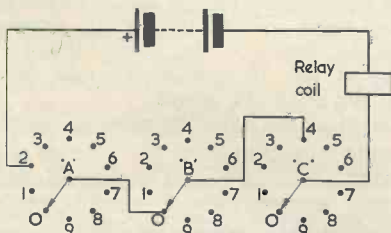


Fig. 1. The basics of a simple 3-decade electronic lock. There are 1,000 possible combinations ranging from 000 to 999

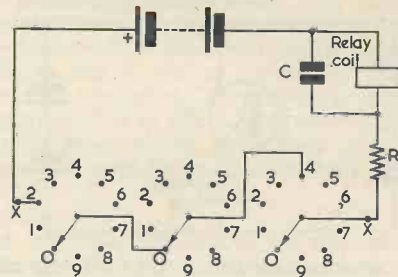


Fig. 2. Adding a simple delay circuit to the relay coil. This necessitates waiting for the relay to operate after the correct combination has been selected, and makes "searching" for the combination much more difficult and time-consuming

Decade Switch Lock

The simplest type of lock consists of a number of decade switches wired in series with the relay which controls the latch unit, as shown in Fig. 1. In order to complete the circuit and make the relay work it is necessary to put all three switches into the correct positions. Using only three decade switches there are a thousand possible sequences in which the switches can be arranged, while using a bank of six decades there are one million possible ways. We have, clearly, the basis of a combination lock.

The circuit shown in Fig. 1 has, however, a serious fault. In order to "crack" it, it is only necessary to "spin" the dials, first putting C and B at zero and running through the ten positions of A, and if the relay doesn't "click", setting B at 1 and spinning through A again, and so on, until the relay is heard to click over. This is because the relay operates so quickly that even the fraction of a second for which the circuit is completed by this method of "spinning" is sufficient to make it energise. Using this method, a three decade switch of the type shown can be broken in about one minute.

An effective way around this snag is to put a delay unit into the relay circuit. This can consist quite simply of a resistor in series with, and a capacitor wired across, the relay coils, as shown in Fig. 2. When the circuit is completed the current momen-

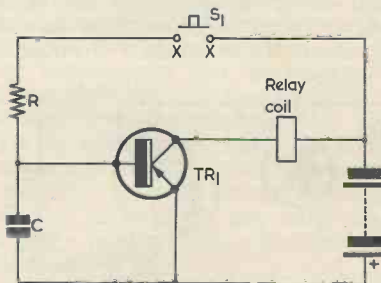


Fig. 3. An alternative type of delay circuit employing a transistor. Switch S1 may be assumed to replace the decade switches of Fig. 2

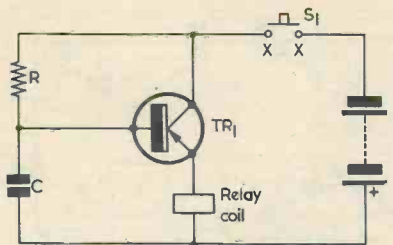


Fig. 4. A further delay unit, in which the relay coil is inserted in the emitter supply lead

tarily flows through the effective short-circuit of capacitor C and drops all of its voltage across R, so that the relay cannot operate. As C charges the voltage across it builds up until, after a pre-determined time which is dependent on the component values, sufficient voltage becomes available to operate the relay. The actual values of R and C will depend on the time delay required, the rating of the relay, and the battery voltage, and are best found by experiment. A delay of about five seconds will normally be the most useful.

A roughly approximate indication of the components required for a given time delay is given by the simple formula for time-constant: $T=RC$, where T=time in seconds, R=resistance in ohms, and C=capacitance in farads.

Using a capacitor of $200\mu\text{F}$, and a time delay of 5 seconds, it is found that a resistor of $25\text{k}\Omega$ will be required. The fact that this resistor is in series with the relay coil resistance introduces another snag in that the resistor and the coil form a voltage divider, necessitating an increase in the supply voltage. A 500Ω , 6 volt relay coil will require a supply of some 300 volts!

It is therefore essential to use expensive and very sensitive relays in this circuit. Surplus moving-coil relays are available, for example, that will work from as little as 140mV. These have a resistance of 350Ω and cost about 25 shillings. When used in the circuit of Fig. 2 with appropriate capacitance values, they could operate from a supply of 4.5 volts, and even as little as 1.5 volts.

Transistor Amplifier

Less sensitive and cheaper relays may be used in conjunction with a transistor amplifier, as shown in Fig. 3. S_1 , connected at points x-x would, in the

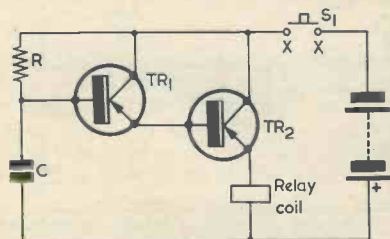


Fig. 5. A 2-transistor delay circuit which offers considerable advantages over those shown in Figs. 3 and 4

final circuit, be replaced by the decade switches. (See Fig. 2.) The input resistance of a transistor is generally in the order of about 100Ω , and the voltage divider effect still occurs. This may be considerably reduced by inserting the relay into the emitter line, as shown in Fig. 4, this giving an effective increase to the input resistance in a manner similar to the cathode follower principle. When S_1 is closed current will flow through R to charge C. The capacitor will be an effective short circuit at the instant of closing S_1 , and zero voltage will be presented to the base of the transistor. The voltage across C will slowly build up until, after a time determined by the component values, the relay will operate.

The actual component values used will depend on the transistor, the relay, the battery characteristics and the time delay required, and are best found by experiment. Almost any cheap transistor may be used, providing that its ratings are not exceeded.

The ultimate development along these lines is shown in the circuit of Fig. 5. Here a configuration known as a "super-alpha pair" is used. R and C form the time constant circuit. TR_2 is connected with the relay coil in its emitter circuit, thereby increasing the effective base or input resistance. This high input resistance is presented to the emitter of TR_1 , making the effective base resistance of this transistor so high that it has virtually no voltage divider effect with R at all. In an experimental set-up a relay with a resistance of 670Ω and operating current of 14mA was employed in conjunction with a pair of "red spot" transistors using this circuit. These transistors cost only a few shillings each, and the writer obtained the relay for about five shillings. The complete circuit was built for about ten shillings, which is less than half the cost of the more sensitive relay described earlier.

Any of the four time delay circuits shown in Figs. 2 to 5 may be fitted into the locks to be described, the type employed being a matter of individual choice. Also, they may be used with the decade switches of Fig. 2 to provide an elementary back system on its own.

Further Developments

To return to the development of electronic locks, an additional switch may be added in the battery circuit. This must be closed before the unit can function, and it can also be used to feed an alarm circuit as a precaution against unauthorised tampering. The alarm circuit utilises an arrangement similar to that shown in Fig. 5, but having a longer time delay of, say, 10 seconds. Its relay is used to operate a bell or similar alarm.¹

The circuit of the complete unit, as described so

¹ In the diagrams which follow, relays and their contacts are illustrated with the "detached" method of presentation. Relay coils are indicated by rectangles and are designated by a letter over a figure. The figure indicates the number of contacts possessed by the relay. The contacts may appear at any point in the diagram and are shown in the de-energised position. They are designated by a letter and a suffix number. Thus, A/2 refers to the winding of relay A; the designation also carries the information that there are two sets of contacts. These contacts will be found elsewhere in the diagram designated A1 and A2.—EDITOR.

far, is shown in Fig. 6. R_1 , C_1 , TR_1 , TR_2 and relay A2 form a 5 second delay circuit triggered by the combination switch chain, S_1 , S_2 and S_3 , these being connected to the battery via S_4 and S_5 . Relay A/2 has two sets of contacts, A1 and A2. A2 is used to operate the latch mechanism.

R_2 , C_2 , TR_3 , TR_4 , relay B/2, and contacts B1 and A1 form the anti-thief alarm circuit with, say, a 10 second delay. Connection to the battery is made via A1, S_4 and S_5 . Relay B/2 has two sets of contacts, B1 and B2. B2 is connected to the bell or alarm circuit.

The sequence of operations is as follows, S_5 is normally closed. In order to make the circuit work S_4 is also closed and voltage is applied to the anti-thief circuit via contact A1. Relay A/2, in the 5 second delay circuit, is de-energised, and will remain so for at least 5 seconds. Its contact A_1 is


button switch concealed inside the cabinet or protected enclosure, so that the correct combination must be found before the alarm can be stopped.

S_1 , S_2 , S_3 and S_4 are, of course, the only front panel mounted controls. The correct procedure for opening the lock is to first set the correct combination on the three switch dials, then close S_4 and wait 5 seconds until the latch slides back.

Precautions

Three important precautions are necessary when using the circuit of Fig. 6. First, the batteries must always be maintained at a satisfactory operating voltage. (As a safeguard, a pair of terminal points could be made available for the application of an external battery in parallel with that protected by the lock, a device such as a diode being incorporated to prevent connections of incorrect polarity from

Fig. 6. A comprehensive lock which sounds an alarm if the wrong switch combination is selected. The resistor and capacitor values shown in the diagram are those employed in the author's prototype, the two relays being 670Ω types energising at 14mA. The transistors can be OC72 or similar, the supply potential being 12 to 15 volts

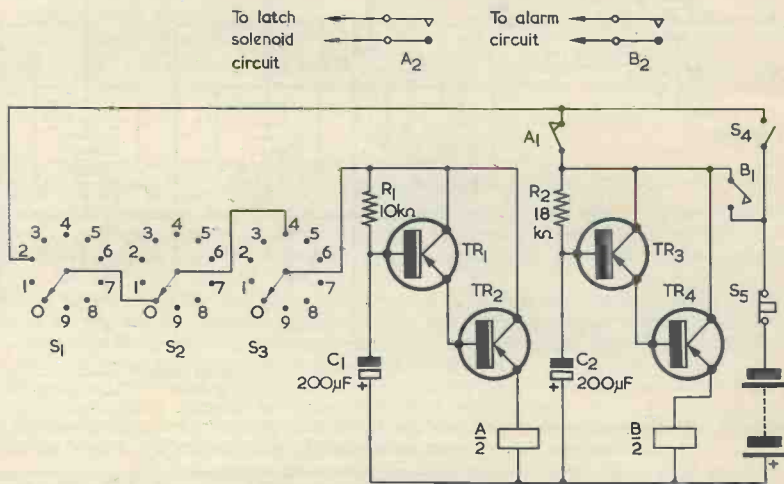

closed when the relay is de-energised, and *vice versa*. If the decade units are switched in the correct positions then the battery voltage will also be applied to the 5 second delay circuit and, at the end of this period, relay A/1 will energise. Contact A2 will close, operating the latch release solenoid, while at the same time A1 will open, cutting the battery supply to the alarm system and making it inoperative.

If, however, the decade unit is not switched to the correct combination within 5 seconds of closing S_4 , contact A1 will remain closed for the full 10 seconds required to operate relay B/2 and the alarm will sound. The thief could, if B1 were not in the circuit, switch off S_4 as soon as the alarm sounded, thus restarting the cycle and giving himself a further 10 seconds to break the lock; and so on until the lock was finally opened. To prevent this, contact B1 is used, when closed, to bypass S_4 and connect the alarm circuit directly to the battery. The alarm circuit is thus made self-latching, and will continue to sound once it has started, even if S_4 is made open-circuit. The only way the alarm can be stopped is by opening S_5 , which would be a press-

damaging the transistors.) Secondly, once the lock has been used it must be reset by opening S_4 . The third point is that, once the lock has been used and the door is shut again, all three dials must invariably be turned out of the contact positions, otherwise the thief will merely have to close S_4 to open the lock again.

It may be felt by some readers that an insufficient number of combinations are provided, or that the necessity of changing the dial positions after use is asking too much of their memories. In this case, a further development can be employed. It is possible to arrange things so that the after combination has been correctly dialled the relay is used not to operate the latch but to change the combination and make a second set of delay units available. It is then necessary to dial a second set of combinations, which, if correctly set, may either operate the latch or give a further change of combination and delay units; and so on.

Fig. 7 shows a circuit designed to offer this kind of operation. Here, it is necessary to dial, in the correct sequence, three sets of three digit combinations, using only three panel mounted dialing

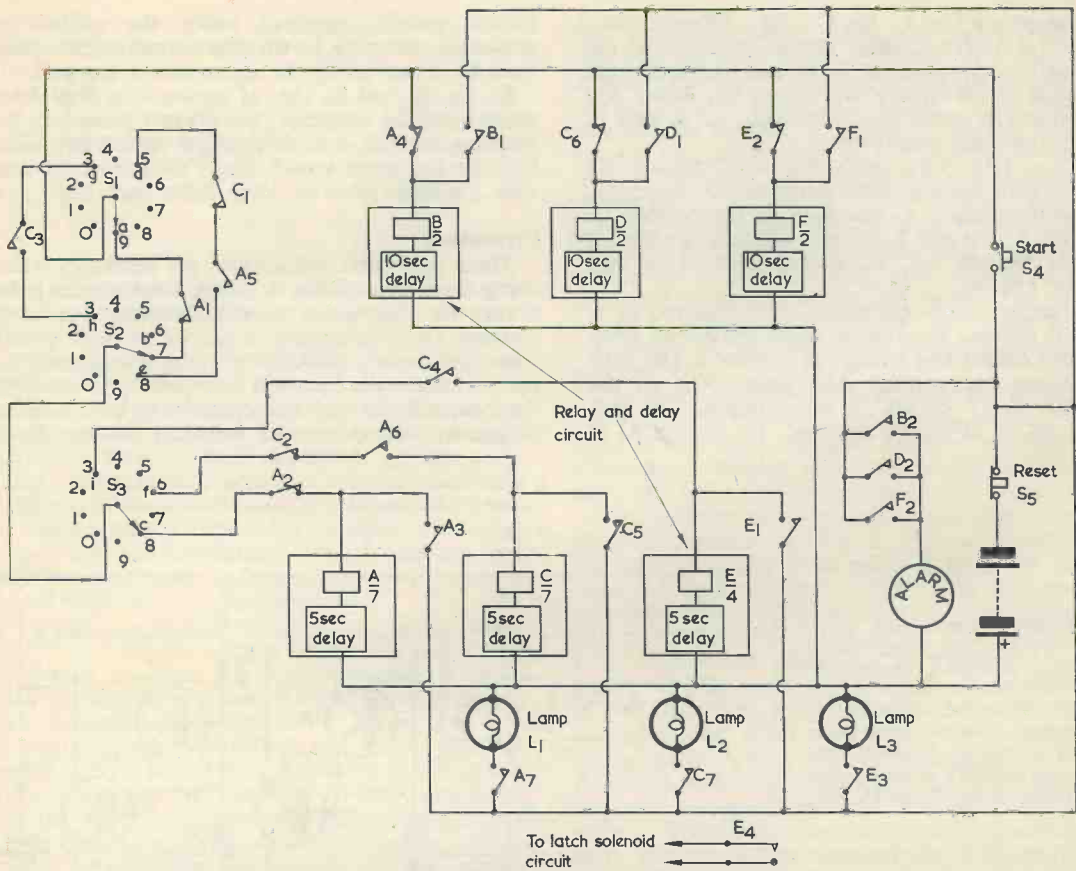


Fig. 7. A comprehensive circuit wherein three combinations have to be switched in successively. The combination changes automatically after the first and second selections

switches. There are thus one thousand possible combinations. It is possible to make only one attempt at opening the lock, after which either the latch will open or the alarm will sound. The odds against any unauthorised person opening the lock are therefore one thousand million to one. It should be noted that if the alarm is not fitted and any number of attempts can be made, it is possible to break the lock in, at most, three thousand attempts, it being necessary only to make up to one thousand systematic attempts at dialling to obtain the first three digits of the nine digit combination, and then, knowing this number, to make a further thousand attempts at finding the next three, and so on. It is therefore essential to the basic design of this and the earlier lock that the alarm system be fitted.

The operation of this lock, with reference to Fig. 7, is as follows. A three digit combination is selected via switches S₁, S₂ and S₃, and the start button, S₄, is pressed and held down. Voltage is applied, via contacts E₂, C₆ and A₄ to relays F/2, D/2, and B/2, together with their 10 second delay circuits. With reference to the decade unit it is necessary, for correct operation, that a voltage be

applied via the decade switches to one of the three relays A/7, C/7 or E/4 and their appropriate delay circuits. The path between contacts "d" and "e" of S₁ and S₂ has been made open-circuit by relay contact A₅, whilst "g" to "h" is open-circuit by C₃. Also, between S₃ and relays A/7, C/7 and E/4, "f" to C/7 is open-circuit by A₆, and "i" to E/4 is open-circuit by C₄. The only satisfactory positions for S₁, S₂ and S₃, therefore, are "a" via A₁ to "b", through S₃, and "c" via A₂ to relay A/7. If "a.b.c." has been dialled correctly, voltage will be applied to relay A/7 and its delay circuit, and after 5 seconds A/7 will energise. Contacts A₁, A₂, A₅ and A₆ will switch over and change the combination. Simultaneously, A₃ will close, locking relay A/7 on, regardless of the states of S₁, S₂, S₃ and the start button S₄. Contact A₇ will connect the supply to indicating lamp L₁, to indicate that the operation has occurred correctly, whilst A₄ disconnects the supply to relay B/2 and its 10 second delay circuit.

The start button should be released as soon as lamp L₁ comes on. If the button is not released, but remains depressed for a further five seconds, relay D/2 and F/2 will operate and lock themselves on

via their contacts D1 and F1, activating the alarm via contacts D2 and F2. If the correct combination has not been selected, relay A/7 will not operate, with the result that the supply will not be broken to relay B/2 before the 10 second period is up. The effect is the same as if the start button, S₄, were left depressed for too long and the alarm will sound.

If the first combination has been dialled correctly, the second one ("d.e.f.") can be set up and the start button depressed again, and a similar sequence will occur, only this time relays C/7 and D/2 will be used. If the combination is correct, lamp L₂ will come on and the combination will change again.

It is only after the third combination ("g.h.i.") has been dialled successfully that L₃ will come on and the latch will operate. If a mistake has been made at any time during the process and the alarm has sounded, the only way it can be stopped is by opening the lock and disconnecting the battery supply by pressing S₅, a push button reset switch concealed inside the safe or protected place. It will be necessary to reset the lock after use in any case, so it may be preferable to make S₅ a micro-switch which operates automatically when the door is opened.

It should be noted that with this circuit it is not essential to change the dial positions after use, as even if three of the nine digits in the combination are known, the odds are still one million to one against any unauthorised person finding the remaining six digits. The odds would in fact be even greater than this, as it is very unlikely that a thief would know how to operate the lock anyway, and even if he did, he would have no idea of the time delays involved. The time delays are, of course, a matter of individual choice, and need not even be the same between one relay and another, as long as the delay of the alarm relays is made appreciably longer than the longest delay given to the remaining circuits.²

To obtain the required number of contacts on relays A/7 and C/7, pairs of four pole relays may be coupled together.

² A possible economy, in Fig. 7, could be given by dispensing with relays B/2 and D/2, relying only on relay F/2 for the alarm function. Relay F/2 will then energise if S₄ is held down for too long during the first or second dialling operations, or if S₄ is held down for too long before relay E/3 energises during the third operation.—EDITOR.

(To be continued)

NEW PHOTOMULTIPLIER TUBE HAS FAST RISE TIME

First of a new range of fast photomultiplier tubes, suitable for use in nuclear physics and other applications where a fast rise time and high peak currents are required, is announced by EMI Electronics Ltd. The high-field focused dynode system of the Type 9594B tube employs antimony caesium secondary-emitting material to give maximum stability and minimum gain shift.

Fast rise time of 2½ nanoseconds is achieved by the use of an end-window with a concave inner surface, on which the semi-transparent photocathode is deposited, in conjunction with focus and deflector electrodes. These ensure good collection of photo-electrons into the first dynode and minimise the time spread of the output pulse. The fourteen-stage dynode structure gives an overall electron gain in excess of 100,000,000.

Flat external surface of the end-window facilitates coupling of scintillating crystals. The fast rise time, high gain and high peak currents make this tube particularly suitable for fast coincidence applications.

Variations of the basic type now in development include a tri-alkali cathode version for applications demanding an extended red response, and another with a quartz window for improved ultra-violet sensitivity.

The Heathkit Model SB-400 s.s.b. transmitter, illustrated herewith, covers all amateur bands from 3.5 to 30 Mc/s. Frequency stability is excellent, being less than 100 c/s drift per hour after 20 minutes warm-up under normal ambient conditions, and less than 100 c/s drift for ±10% line voltage variations. The types of emission are s.s.b. with selectable upper or lower sideband and c.w., the r.f. power output being 100 watts on 80 to 15 metres and 80 watts on 10 metres (50Ω non-reactive load). The visual dial accuracy is within 200 c/s on all bands and the electrical dial accuracy is within 400 c/s on all bands, after calibration at the nearest 100 kc/s point, backlash is no more than 50 c/s.

Carrier suppression is 55dB down from the rated output, harmonic radiation is 35dB below rated output, oscillator feedthrough or mixer products are 55dB below rated output (except at 3910 kc/s crossover which is 45dB). Unwanted sideband suppression is 55dB down from the rated output at 1,000 c/s and higher, third order distortion being 30dB down from rated p.e.p. output and noise level at least 40dB below rated carrier. The SB-400 s.s.b. transmitter is available at £165 4s., in easy-to-assemble kit form, carriage paid in U.K.

HEATHKIT MODEL SB-400 S.S.B. TRANSMITTER



NEWS

AND

COMMENT

60 Years Ago

The "Fleming Oscillation Valve", the forerunner of today's vast range of specialised valves, was discovered by Sir Ambrose Fleming just sixty years ago, in November 1904. Perhaps one of the most important electronic discoveries of the century, this invention heralded the birth of the electronics industry.

Today the transistor is fast replacing this early discovery, but it will be many years before the high power valves, handling many megawatts and using the same basic principle of cathodic emission as Fleming's valve, are replaced by solid state devices.

At the time of his discovery, Sir Ambrose was Professor of Electrical Engineering at University College, London, and since 1899 had been Scientific Adviser to The Marconi Company. He was very closely associated with Marconi himself and had played a leading part in the design of the powerful transmitting equipment at Poldhu in Cornwall, with which Marconi made his first successful wireless transmission across the Atlantic in 1901.

In his search for better methods of detecting electro-magnetic or wireless waves, Sir Ambrose, recalling the results of earlier research involving the passage of electric currents through rarefied gases, conducted a series of experiments utilizing some of his original apparatus. This new work led him to the discovery of the "Fleming Oscillation Valve", the first thermionic valve produced in the world. This was quickly recognised by The Marconi Company and the "valve" was soon put into full production.

During his years at University College, Sir Ambrose Fleming trained many hundreds of engineers who later made their names in the radio industry. He continued to lecture until ninety years of age!

Sir Ambrose died in his 96th year on 18th April, 1945.

100 Years Ago

From the issue dated 3rd November, 1863, of the *Lancet*, the famous medical journal:

"On Tuesday last the electric light was used in the operating

theatre of the Royal Ophthalmic Hospital, Moorfields. . . . The excellence of the light for operations on the eye was well demonstrated, and we have no doubt that it will be shortly in use in most hospitals for operations by night or on dark days."

Colour TV in 1967?

A report issued by the Heywood Electronics Information Centre expects colour television to take the air in a limited way during 1967. This belief is despite the high cost of receivers, expected to be four times that of black and white ones in the initial stages.

Further international discussion on colour television took place in London from 26th-29th October. Demonstrations were given by the B.B.C. and the British Radio Equipment Manufacturers' Association to the E.B.U. Colour Television Group.

These demonstrations mark a further step towards choosing a common colour system for Europe, the final decision on which is to be made at a meeting of the C.C.I.R. (International Radio Consultative Committee) in Vienna next March. The demonstrations compared colour pictures produced by the three systems, NTSC, SECAM and PAL, when transmitted over long international links, when recorded on video tape, and when transmitted direct to domestic receivers. They showed the effect of important improvements in colour television apparatus that have been made since the previous series of demonstrations in London last February.

Education of Amateurs

The Radio Society of Great Britain has recently, we understand, been devoting considerable thought to the education of the younger generation in Amateur Radio as a hobby and as a basis for a career in electronics generally.

One of the stands which interested us at their International Radio Communication Exhibition, reported elsewhere in this issue, was the Society's educational stand where a series of most interesting demonstrations were given. We would like to have seen this stand more prominently sited, instead of at

the far end of an annexe hall. Also badly sited, up in the balcony, was the stand of the British National Radio School. This was a pity as they were featuring a special Home Study Course covering the Radio Amateurs' Licence Examination.

We wonder whether the R.S.G.B. has considered holding the exhibition in London every other year, and in the alternate year holding a Hamfest with a small exhibition in centres of population other than London. The interest in the biennial exhibition in London would probably be greater and the provinces would feel that everything was not centred in London alone.

B.A.R.T.G.

On the final night of the foregoing Exhibition, the British Amateur Radio Teleprinter Group held its Annual General Meeting and got-together at the "Olive Branch".

This event was apparently very successful, some 50 people attending including 6 Dutch RTTY enthusiasts. One change of note was the retirement as Honorary Secretary, of Arthur C. Gee, G2UK, the founder of the group and a pioneer of RTTY in this country. His services will not be lost however as he undertook the position of Honorary Treasurer.

Mr. Eric Yeomanson, a member of the group, was in charge of the RTTY Radio Station at the previously mentioned exhibition. We would like to take this opportunity of congratulating Mr. Yeomanson on his appointment as the 1965 President of the Radio Society of Great Britain.

Phenomena

At some time or other, in connection with radio or television, most readers will have some across some example of freak reception or the like. In the writer's case, telephone conversations, which took place when a neighbour's radio was switched on, were clearly audible through its loudspeaker.

A most unusual cause of TV interference has been reported in the *Daily Express*. In this particular case interference was caused because the next door neighbour was building up static electricity—by stroking her cat!

Relay Binary Circuit

B. W. OSBORN



"MAGIC" Switching for your Christmas Tree Lights

THE CIRCUIT TO BE DESCRIBED was designed to operate in conjunction with a photocell and light beam system to control a set of Christmas tree lights, apparently by magic, for the amusement of friends' children.

The photocell and light units were placed in front of the tree in such a position that a person approaching the tree interrupted the beam momentarily and produced a pulse from TR₂ which energised relay X. See Fig. 1. Similarly, a further pulse was produced as the person moved away from the tree.

The associated binary circuit, shown in Fig. 2, was required to turn the tree lights on at the beginning of the first pulse and off at the end of the second.

Fig. 1 shows the phototransistor and power supply circuits, both of which are conventional and need not be described in detail. The relay binary, or "divide by two" circuit has two stable states, i.e. the output relay contacts are either open or closed, an input pulse changing the circuit from one state to the other. The relay circuit operates in the following manner.

Relay Operation

Contact XI of relay X changes over for the period during which the light beam is interrupted, and relay A is energised via contact A1 and resistor R₆. Contact A1 provides a hold-on circuit for relay A whilst contact A2 prepares

a path for the operation of relay B upon the subsequent release of relay X. The third contact of relay A connects the mains supply to the three lamps. When the person approaching the tree passes completely through the light beam relay X releases, causing the operation of relay B via contact A2. Contact B1 makes to provide a circuit which will short-circuit the coil of relay A when relay X re-operates (when the person moves away from the tree). When this occurs both sides of relay A coil are brought to the same potential and the relay releases. Relay B is maintained energised by a current flow through diode D₁, contact X1

(energised) and contact B1. The tree lamps stay alight due to the parallel mains supply path through contact B2. When the person has moved far enough back from the tree to clear the light beam, contact X1 returns to its original state and removes the supply from relay B coil. With relay B de-energised the circuit returns to the state shown in Fig. 2, and the tree lights are extinguished.

Installation

When in use both the phototransistor and light unit were hidden behind furniture and, as the phototransistor responded well into the infra-red region, a filter

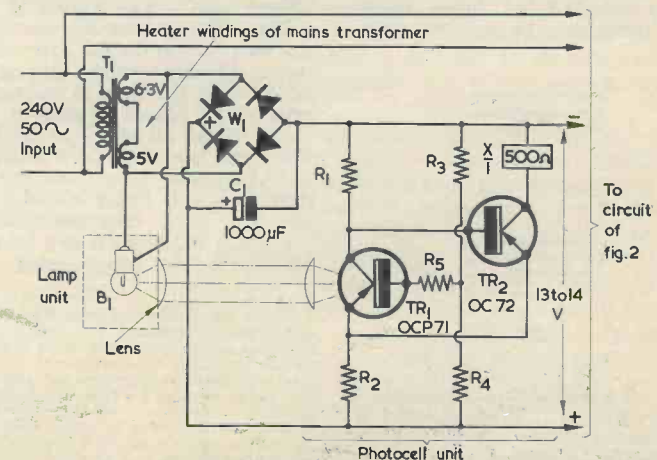


Fig. 1. The power supply and light-operated section of the circuit. The lenses may be inexpensive "magnifying glasses", or similar


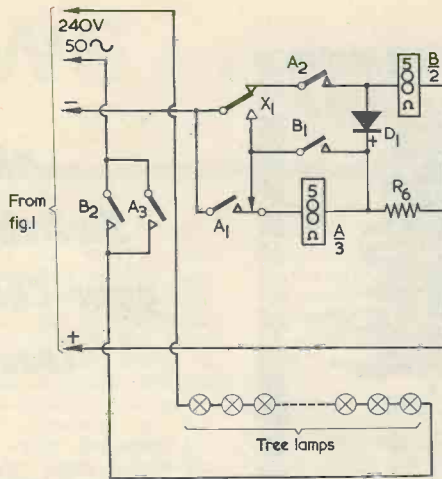


Fig. 2. The relay circuit. The relay contacts are shown with the "detached" presentation, i.e. separate from the corresponding relay coils, which have the same letter designation. All contacts are illustrated in the de-energised state. Contacts A1 are of the make-before-break type

was placed in front of the light source to remove visible light and avoid easy detection. The length of time for which relay X operates need be only a few milliseconds for satisfactory operation of the binary circuit, and the tree lights could be as easily operated by a wave of the hand through the light beam as by walking towards the tree.

Possible alternative uses of the system are.

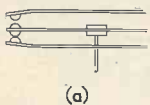- (1) The automatic switching of bedroom or stair lights by a child old enough to get out of bed to visit the toilet, etc., but not tall enough to reach the light switch.
- (2) Control of loft lights where access may be required when



(a)



(b)

Fig. 3. If a make-before-break contact set for A1 of Fig. 2 is not available, a changeover springset may be adapted. As shown in (a), the outer springs are bent inwards so that all springs connect together momentarily, as in (b), during the process of energising

the hands are not available for operating the light switch.

- (3) Operation of garage doors via a suitable actuator so that the doors open as the car approaches the garage and close as the driver leaves.

Mechanical Details

If a make-before-break springset is not available (for contact A1) a changeover set can be used if the outermost springs are bent slightly inwards so that all three springs are momentarily in contact as the relay operates. See Fig. 3.

The diode D₁ can be any general purpose type capable of passing 100mA with a p.i.v. rating of 150. The 100Ω resistor R₆ should be a 2 watt type as the full low voltage supply appears across it during the period when the beam is interrupted prior to the release of relay B.

The relays, all of which are P.O. 3000 type, were held on a length of $\frac{1}{2} \times \frac{1}{4}$ in thick aluminium bar by their 2BA coil fixing screws. The bar was bent into an inverted "U" form and screwed to a wooden baseboard, the relays being sus-

EDITOR'S NOTE

Whilst the contacts of P.O. 3000 relays, as normally encountered, will cope with the switching of Christmas tree lamps at mains voltage, it should be remembered that the insulation between springsets and armature may not be intended for such an application. From the point of view of safety, therefore, it would be preferable to ensure that bulb B₁ and the circuitry around TR₁ are reliably insulated from the tins in which they are fitted. For a similar reason, the remaining low voltage components should be mounted in an insulated case which prevents their being accidentally touched.

pended from the bar with their tags uppermost. Power supply components were also mounted on the board.

The light unit was contained in an old cocoa tin, the lampholder being fitted through the lid, with the lens pressed into an opening cut in the bottom of the tin. A similar tin housed the phototransistor and its associated circuitry, both units being held in "U" shaped cradles which permitted the light source and phototransistor to be easily aligned.

Components List (Figs. 1 and 2)

Resistors

(All resistors 10% $\frac{1}{4}$ watt unless otherwise stated)

- R₁ 10kΩ
- R₂ 470Ω
- R₃ 10kΩ
- R₄ 1.2kΩ
- R₅ 100kΩ
- R₆ 100Ω 2 watts

Capacitors

- C₁ 1,000μF electrolytic, 20V wkg.

Transformer

- T₁ Standard receiver mains transformer (h.t. windings not employed), with 6.3 and 5V secondaries connected in series

Transistors

- TR₁ OCP71
- TR₂ OC72

Relays

(All relays are P.O. 3000, with 500Ω coils)

- $\frac{X}{1}$ 1 changeover springset
- $\frac{A}{3}$ 1 make-before-break springset (see text), 2 make springsets
- $\frac{B}{2}$ 2 make springsets

Rectifiers


- W₁ 12V 1A selenium bridge rectifier (battery charger type would be suitable).
- D₁ General purpose (see text)

Bulbs

- B₁ 12V 6W Christmas tree lamps


Miscellaneous

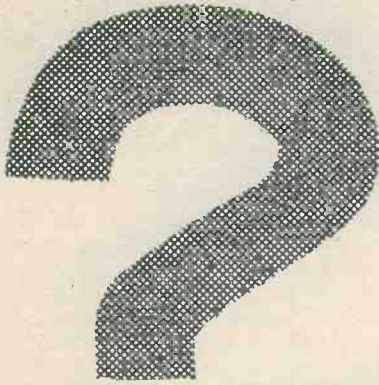- Bulb holder (for B₁)
- Convex lenses (for B₁ and TR₁)
- Lamp and phototransistor cases
- Baseboard, relay mounting bar, etc.



INTRODUCING THE VALVE

understanding radio

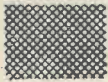

By W. G. MORLEY

After dealing with final details on loudspeakers, "Understanding Radio" turns its attention this month to the valve, which it introduces in the form of the diode

IN LAST MONTH'S ISSUE WE EXAMINED THE ELECTRO-static loudspeaker and the Ionophone. We have very nearly completed our discussion on loudspeakers and the only main aspects of this subject which are now left uncovered are the crystal loudspeaker and loudspeaker circuit symbols. After dealing with these, we shall introduce the valve.

The Crystal Loudspeaker

Certain crystalline substances, notably quartz and Rochelle salt, tend to exhibit deformation of shape if an e.m.f. is applied across two opposite surfaces. This effect, which is known as the *piezoelectric effect*, is most evident when sections having particular angles to the crystal axes are cut from the crystal.¹ By suitably clamping a crystal section, or a combination of two crystal sections, it becomes possible to impart a bending or twisting motion to the unclamped portion when an e.m.f. is applied. The bending or twisting motion may then be coupled, via an arm, to a cone or diaphragm.

If an alternating voltage at audio frequency is applied to the crystal section, the cone or diaphragm moves in sympathy with the frequency and amplitude of the applied voltage, whereupon the device becomes a loudspeaker. The source of alternating voltage is normally applied to conductive coatings, or metal foil, on opposing faces of each crystal section.

Due to the fragility of the crystal, it is not possible to apply alternating voltages of high amplitude to it, with the result that the *crystal*, or *piezoelectric loudspeaker* is only really useful for relatively low

power reproduction at the higher audio frequencies, i.e. as a tweeter. Because of its limitations, however, it is used very infrequently, even in this application. On the other hand, *crystal earphones* are quite often encountered, these having the same basic principle as for the loudspeaker.

Since the crystal sections exhibiting the piezoelectric effect are not conductors, no current flows through a crystal reproducer. Crystal reproducers present a relatively high impedance to the source of a.f. voltage, this being largely capacitive.

Transducers

The term *transducer* defines any device which converts power from one form to another. A loudspeaker is sometimes referred to as a transducer, because it converts electrical power into mechanical power.

Other types of transducer encountered in radio work are microphones, which convert mechanical power to electrical power, and gramophone pick-ups. The latter also convert mechanical power to electrical power, the mechanical power being imparted to the stylus by the groove of the gramophone record.

We have not dealt with either microphones or gramophone pick-ups at this stage but it is interesting to note, in passing, that these may employ the same basic principles, in reverse, that we have encountered in some of the loudspeakers we have considered. A moving-coil (or dynamic) microphone, for instance, has the same basic construction as the moving-coil loudspeaker. When sound impinges on its diaphragm, its coil moves in a magnetic field. A current which is proportional to the frequency and amplitude of the diaphragm movement is then

¹ The same crystal section will, conversely, cause a potential difference to appear across the faces if it is subjected to mechanical deformation. This is also a piezoelectric effect.

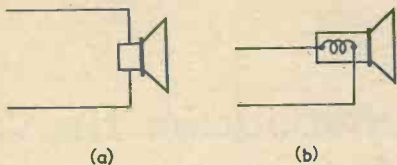


Fig. 246. Circuit symbols for loudspeakers are, usually, immediately recognisable. A general symbol is shown in (a), whilst that in (b) applies specifically to the moving-coil loudspeaker

induced in the turns of the coil, and may be amplified by a subsequent a.f. amplifier. Ribbon microphones, having the same basic assembly as the ribbon loudspeaker, may similarly operate in converse manner. So also may capacitor microphones (roughly equivalent to the two-electrode electrostatic loudspeaker) and crystal microphones. These microphones do not, of course, appear in the same physical form as the corresponding loudspeakers, because they are designed to do a different job.

Gramophone pick-ups commonly employ the piezoelectric effect to change the movement of the stylus to corresponding electrical voltages. An alternative design of pick-up employs the moving-coil principle.

Circuit Symbols

The generally employed circuit symbol for a loudspeaker is that illustrated in Fig. 246 (a). Other easily recognisable symbols may be encountered including, in particular, that shown in Fig. 246 (b). The symbol in Fig. 246 (b) refers to the moving-coil type only. Since the moving-coil loudspeaker is used much more frequently in practice than any other type it can generally be assumed that, unless specifically stated otherwise, the symbol of Fig. 246 (a) refers to the moving-coil version also.

The Valve

When, in the first article in this series², we examined the nature of electric current, we saw that the metals are good conductors because the electrons on the outer orbit shell of each metal atom are held insecurely to the nucleus. The result is that a number of *free electrons* move continually through

² Published in the August 1961 issue.


Fig. 247 (a). A thin filament of wire mounted inside an evacuated glass envelope

(b). Applying a battery to the ends of the filament in order to raise its temperature

(c). If the filament is sufficiently hot, free electrons leave the metal and appear in a cloud, the "space charge", around it

(d). Adding an anode which, by means of a second battery is caused to be positive with respect to the filament. Electrons emitted by the cathode are now drawn towards the anode

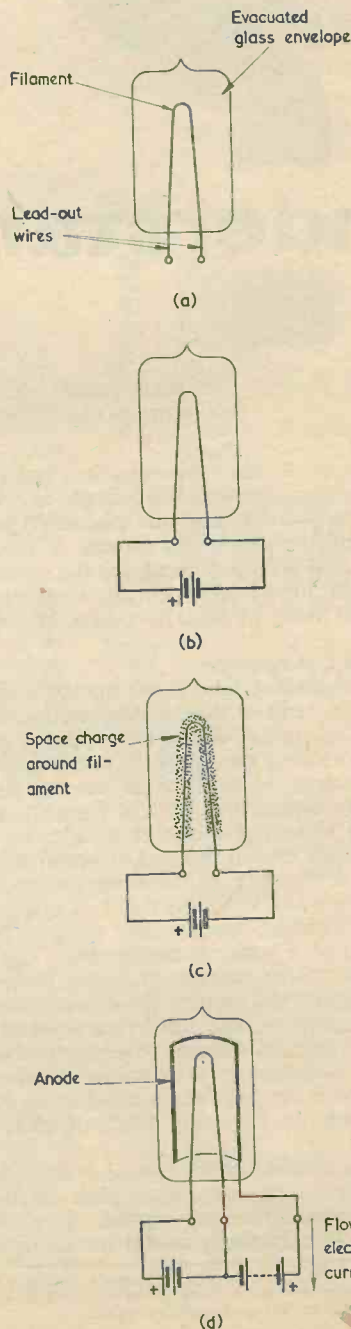the metal, joining first with one atom and then with another. The movement is random until a source of electromotive force is applied to two separate points on the metal, whereupon there is a general movement of the free electrons from the point of application of the negative pole towards the point of application of the positive pole. This flow of electrons constitutes an electric current.



In the type of *valve* we shall now consider, a current is similarly given by a flow of electrons, but in this case the electrons do not flow through a conductor. They pass, instead, through a vacuum or, in other words, through empty space.

In Fig. 247 (a) we introduce a length of wire into a glass envelope from which all the air and any other gases have been evacuated. We next apply, in Fig. 247 (b), an external battery to the ends of the wire, this causing it to increase in temperature in just the same manner as does the filament of an electric light bulb. We can, indeed, call the wire a *filament* in the present instance. As the temperature of the filament increases, so also does the velocity of movement of its free electrons until, at a temperature which varies from material to material, they acquire enough energy to fly out of the metal into the space immediately around it. A relatively high temperature is required for this phenomenon to occur and it is necessary, in consequence, to employ a material having a high melting point for the filament. A good practical choice is given by using tungsten wire.

The electrons emitted from the filament take up the form of a "cloud" around it, some of these electrons falling back into the filament to be replaced by others. See Fig. 247 (c). Once established, the "cloud" of electrons tends to repel most of the further emitted electrons, which similarly fall back into the filament. Thus, a state of equilibrium is set up, and the quantity of electrons in the "cloud" remains virtually constant. As we have seen when we discussed capacitors, an excess of electrons constitutes a charge. We call the "cloud" of electrons around the filament a *space charge*.

In Fig. 247 (d) we introduce a metal *plate*, or *anode*, into the evacuated envelope and connect up a second battery in such a manner that this anode is positive relative to the filament. The electrons emitted by the filament now become attracted by the positive anode and flow towards it. An electric current flows, therefore, from filament to anode, this being provided by the flow of electrons through the empty space inside the envelope. Also, an electric circuit is set up. Electrons leave the filament and pass into the anode, after which they carry on to the positive terminal of the anode-filament battery; at the same time electrons leave the negative terminal of the battery and flow into the filament to replace those which have been lost to the anode.

If the battery connected between anode and filament has a sufficiently high voltage, the anode will be capable of attracting *all* the electrons emitted by the filament. In consequence, there is no space charge, since all electrons leaving the filament travel immediately to the anode. If the battery has a lower voltage, the attraction exerted by the anode is not sufficiently great to draw *all* the electrons towards it. The result is that a space charge is retained. Electrons then leave the space charge to travel towards the anode, the space charge being replenished by new supplies of electrons from the filament.

Types of Cathode

We have referred to the plate of Fig. 247 (d) as an "anode", because this is the term normally applied to an electrode (i.e. a conductor which provides electrical connection into a device) which connects to the positive terminal of an actuating source of e.m.f. The opposing term is "cathode". We may, therefore, refer to our filament as a *cathode*.³

It is not necessary for the cathode of our assembly to consist of a filament of wire. It may, instead, consist of a sleeve of metal inside which is placed a *heater*, as in Fig. 248 (a). This heater is coupled to a source of e.m.f. which raises its temperature. The heater, in its turn, then raises the temperature of the metal sleeve, whose outer surface finally emits the electrons into the empty space of the evacuated envelope. The heater is insulated from the metal sleeve in which it is inserted, and its purpose is merely that of raising the cathode to emitting temperature. Insulation is normally provided by a layer of tough heat-resistant material, such as magnesium oxide, coated over the wire of the heater. Two types of heater construction are illustrated in Figs. 248 (b) and (c).

³ To be precise, the anode is the electrode via which "conventional current" flows into a device, and a cathode is the electrode via which "conventional current" flows out of the device. "Conventional current" is assumed to flow from positive to negative, even though this is opposite to the direction of electron flow.

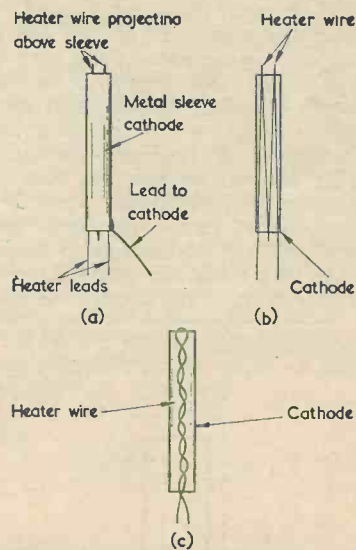


Fig. 248 (a). If a metal sleeve is raised to emitting temperature by an internal heater it may function as a cathode

(b). The heater wire inside the metal sleeve cathode of (a). The heater wire is coated with a tough, heat-resistant, insulating material which prevents it short-circuiting against itself and which provides insulation from the cathode

(c). An alternative heater construction, in which a loop of the heater wire is twisted

If both the cathode and heater are cold, as would occur if the source of e.m.f. for the heater had been disconnected or switched off for some time, a small period of time must elapse before the heater can raise the cathode to emitting temperature after its source of e.m.f. has been re-applied. This period is known as the "warm-up time" for the valve in which the heater and cathode are fitted. We are all familiar with the fact that a conventional valve radio receiver which draws its power from the mains supply takes a little time to come into operation after it has been switched on. The delay is due to cathode warm-up time in the valves employed in the receiver.

When we introduced the question of emission from the filament, it was stated that a good choice for the filament wire would be given by tungsten. Tungsten is, in fact, a perfectly practicable material for this purpose and was used extensively in the early days of radio. It needs, however, to be raised nearly to white heat (around 2,000°C or more) to provide an adequate emission of electrons. An alternative filament material is thoriated tungsten (tungsten with a small addition of thorium), and this offers improved emission at a somewhat lower temperature (of the order of 1,500°C). An alternative approach consists of coating the filament with a layer of rare-earth oxide⁴ such as calcium oxide, barium oxide or strontium oxide. These oxides offer a very high emission at much lower temperatures (around 800°C) than are required by the tungsten or thoriated tungsten filaments.

The metal sleeve cathode of Fig. 248 (a) would not be expected to operate at the very high temperatures needed by the tungsten or thoriated tungsten filaments. Because of this, such cathodes are given oxide coatings, whereupon they are able to offer high emission at relatively low temperatures.

With Fig. 247 (d) we saw the case where the anode potential was sufficiently high to draw all the electrons emitted by the filament towards it. In practice it is generally undesirable to arrange circuit conditions in such a manner that the total emission of the cathode flows to the anode, and this point is

⁴ An "earth", in this context, is an oxide of metal which is infusible and which is insoluble in water.

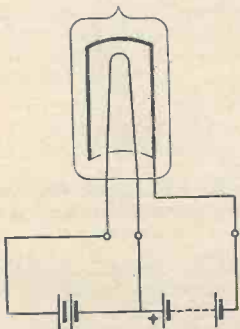


Fig. 249. Connecting the anode-cathode battery of Fig. 247 (d) with reverse polarity. In this case no current flows

especially important with the oxide-coated cathodes (whether these be filaments or separately heated) because such operation may cause permanent damage to the coating. When these cathodes are used, the electron flow to the anode has to be kept well below the possible maximum if the cathode is to have a long life. With the thoriated tungsten filament, electron flow to the anode has also to be maintained below the possible maximum if damage to the filament is not to occur. In this case, however, the maximum permissible electron flow may approach total emission much more closely than occurs with the oxide-coated cathode. With the tungsten filament, it is possible to allow all the electrons which are emitted to flow to the anode without risk of damage to the cathode.

It will be gathered from the preceding paragraph that the oxide-coated cathode must be operated such that it always has a space charge around it. The thoriated tungsten filament must similarly have a space charge, but this can be significantly smaller than that for the oxide-coated cathode.

Because of their high emission efficiency and low temperature requirements, oxide-coated cathodes are normally used in the valves found in domestic radio equipment. They are not suitable for use in applications where the associated anode has a very high voltage. High voltage applications arise mainly in radio transmitter circuits, and these use valves having tungsten or, preferably (because of their higher emission efficiency), thoriated tungsten filaments.

Reversing Anode Polarity

In Fig. 247 (d) we applied a battery between anode and cathode such that the anode was positive of the cathode. As a result, an electric circuit was set up, with electrons flowing from the cathode to the anode and then, via the battery, back into the cathode.

In Fig. 249 we connect up our anode-cathode battery once more but with reverse polarity, so that the anode is *negative* of the cathode. The result is that the electrons emitted by the cathode are now repelled by the anode, and they remain in the space charge. There is, therefore, no flow of electrons to the anode at all, and the valve behaves as though it were an insulator.

We learn, therefore, that a valve employing a cathode and an anode in an evacuated envelope is a "one-way" device. If a source of e.m.f. is applied to it so that the positive terminal connects to the anode, current flows. If the source of e.m.f. is applied to it so that the negative terminal connects to the anode, no current flows. Current can only flow in one direction.

Terminology

Before we proceed further, it now becomes necessary to introduce a number of terms applicable to the valve.

We have already, of course, inferred that the assembly of cathode and anode in an evacuated container constitutes a "valve". The term "valve" applies also, however, to assemblies which have one

or more further electrodes in addition to the cathode and anode; and it applies again to devices which manipulate electrons in other ways and whose electrodes are mounted in envelopes containing a gas. There is a very large family of "valves", in which the two-electrode device we have considered is just one member.

A valve having an evacuated envelope is referred to as a *vacuum tube* in American terminology. Alternatively, the term *tube* may be used to cover the same broad field as "valve".

A valve of the type we have discussed, with a cathode and an anode in an evacuated envelope, is known as a *diode*.

In Fig. 248 (a) the cathode is raised to emitting temperature by a separate heater, and it is described as an *indirectly-heated cathode*. On the other hand, the cathode of Fig. 247 (d) is also a filament through which passes the heating current, and it is referred to as a *directly-heated cathode*. The associated valve may be described as an *indirectly-heated valve*, or a *directly-heated valve*, according to the type of cathode it employs.

As we have seen, the cathode of Fig. 247 (a) may also be referred to as a *filament*, whilst the heating wire of Fig. 248 (a) is a *heater*. American terminology tends to favour "filament" for both cases.

The valve requires a source of e.m.f. to heat the cathode, and this is referred to as the *heater supply*, the *filament supply*, or the *l.t. supply*. A source of e.m.f. which causes the anode to go positive of the cathode is referred to as the *h.t. supply*. The letters "l.t." stand for "low tension", and the letters "h.t." for "high tension". American literature refers to the l.t. supply as the *A supply*, and the h.t. supply as the *B supply*.

Whilst we use the term "anode" almost invariably in this country, American usage favours the term *plate* for this electrode.

We have referred to the flow of electrons to the anode and, thence, into the h.t. battery. This flow of electrons constitutes the *anode current* of the valve. There is, also, a flow of electrons out of the h.t. battery into the cathode, and this forms the *cathode current* of the valve. In the case of the diode, the cathode current is equal to the anode current.

Circuit Symbols

The circuit symbol for a diode having a directly-heated cathode is given in Fig. 250 (a), whilst that

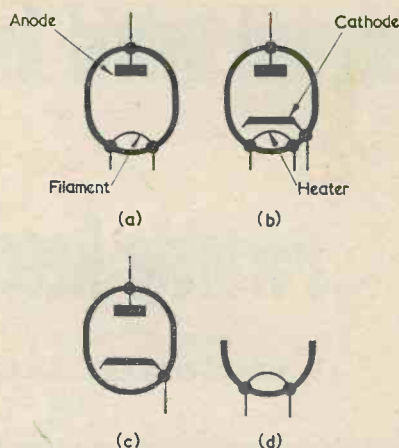


Fig. 250 (a). The circuit symbol for a directly-heated diode

(b). An indirectly-heated diode

(c). Sometimes the heater is not included in the circuit symbol for an indirectly-heated valve

(d). The heater, suitably identified, may appear in a different part of the circuit diagram, as shown here. Only part of the "envelope" around the heater is drawn in, to indicate that a section of the valve is being depicted

for a diode with an indirectly-heated cathode is shown in Fig. 250 (b). Frequently, the heater is omitted from the symbol for the indirectly-heated version, whereupon only the cathode and anode are shown, as in Fig. 250 (c). This symbol is employed either when the heater circuit is of no immediate interest or when, to avoid too many unnecessary lines crossing the circuit diagram, the heater is depicted elsewhere, as in Fig. 250 (d).

When there is more than one valve in a diagram, the individual valves may be identified by the letter "V" followed by a number, e.g. V_1 , V_2 , etc. In some cases more than one set of valve electrodes is enclosed in a single evacuated envelope, and the sections may then be referred to by an added suffix letter, such as $V_{1(a)}$, $V_{1(b)}$, etc.

Next Month

In next month's issue we shall examine further aspects of the diode valve, including its use as a rectifier.

We wish all our readers a very Happy Christmas and a
Prosperous New Year - Editor

Economical Hybrid Amplifier and Portable Receiver Circuits

By SIR DOUGLAS HALL, K.C.M.G., B.A.(Oxon)

IT IS, OF COURSE, TRUE THAT THE transistor is a more economical device than the valve. It is also true that, with modern transistor types, there is virtually nothing which can be done more effectively by valves. But the superior economy of the transistor can be exaggerated, and there is no question that most small Class B transistor amplifiers introduce a good deal more distortion than their Class A battery valve equivalents. This applies particularly when a miniature battery is used to power a device which, at peaks, draws up to 25mA or more.

Amplifier Costs

This article describes a small amplifier designed by the author which will give about 200 milliwatts

output through a Class A battery output valve. Circuitry is incorporated which reduces current consumption from a 90 volt h.t. battery to an average of about 2mA at low volume levels, 3mA at normal levels and about 4mA at maximum output. The overall average consumption over a long period will work out at about 3mA. An Ever Ready B103, or equivalent, 90 volt plus 1.5 volt battery is used which will last about 8 months at an average use of 2½ hours per day. A tuner is also described which will turn the amplifier into a very efficient and economical portable receiver of the larger, better quality, type, at virtually no increase in current consumption. Low tension consumption is about 50mA in the case of both amplifier

and receiver circuits and the low tension section of the B103 battery will outlast the h.t. section at the current values involved. At the time of writing, the B103 battery costs 19s. 6d.

An equivalent transistor amplifier would have to use Class B output and might be expected to take an overall average of 15mA from a 9 volt battery. For it to be economical it may be assumed that a PP9 type of battery would be used costing, at present, 3s. 9d.

The Ever Ready Co. (Great Britain) Ltd. have informed the author that the h.t. section of a B103 battery may be expected to last 600 hours at 3mA, taking 1.1 volts per cell as the end point. They have also said that the l.t. section may be expected to give 1,500 hours use at 50mA. They estimate that a PP9 battery would last 250 hours at 15mA for a similar end point of 1.1 volts per cell.

Simple arithmetic shows that the amplifier to be described costs 0.39 pence per hour to run, and the transistor equivalent 0.18 pence per hour. Putting it another way and assuming an average use of 2½ hours

Components List (Fig. 1)

Resistors

(All resistors ¼ watt 10%)

- R₁ 1kΩ
- R₂ 39kΩ (see text)
- R₃ 100kΩ

Capacitors

- C₁ 100μF electrolytic, 6V wkg.
- C₂ 50μF, electrolytic, 15V wkg.
- C₃ 0.1μF paper
- C₄ 0.01μF paper

Transformers

- T₁ Miniature transformer type D102 (Ardente)
- T₂ 1:4 intervalve transformer (Henry's Radio Ltd.)
- T₃ Standard pentode 65:1 output transformer (Henry's Radio Ltd.)

Valve
V₁ DL96

Transistor
TR₁ OC75

Diode
D₁ Westector type W6 (Henry's Radio Ltd.)

Switch
S₁ d.p.s.t. on-off switch

Speaker
3Ω impedance

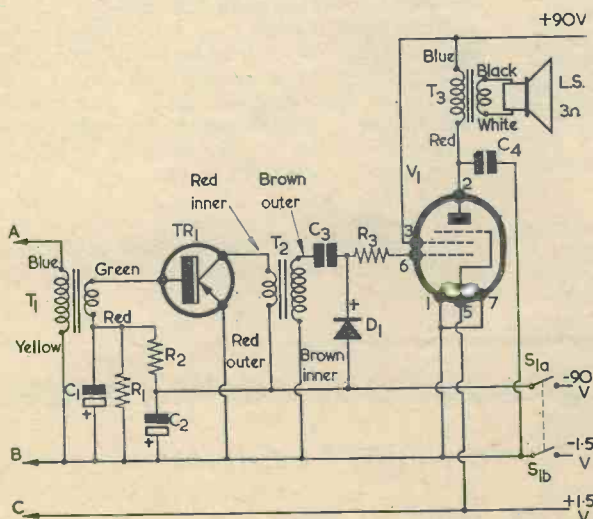


Fig. 1. The circuit of the hybrid amplifier

Components List

(Fig. 2)

(Additional components not common to Fig. 1)

Resistors

R₄ 1.8kΩ ½ watt 10%
R₅ 6.8kΩ ½ watt 10%
VR₁ 5kΩ potentiometer, linear track

Capacitors

C₅ 100μF electrolytic, 6V wkg.
C₆ 0.01μF paper
C₇ 0.001μF paper
VC₁ 150 or 160pF variable

Inductors

L_{1, 2} Medium wave ferrite aerial (see text)
L_{3, 4} Long wave, ferrite aerial (see text)

Transistor

TR₂ MAT101

Diode

D₂ OA81

Switch

S₂ d.p.s.t. wave-change switch

per day, the author's amplifier will cost just under one penny per day, or half a crown per month, as against a little under one halfpenny a day, or one shilling and twopence per month for the transistor equivalent.

For those who do not want miniature equipment but need better quality from a larger instrument, be it amplifier or portable receiver, the extra cost of one shilling and fourpence per month would seem to be reasonable. And it should be remembered that comparisons have been made with transistor apparatus using one of the larger transistor batteries. The author's portable receiver is a good deal more economical with at least equal sensitivity, and will give far better quality than a pocket sized transistor superhet using a miniature battery.

Amplifier Circuit

Fig. 1 shows the circuit of the amplifier, and it will be convenient to study this from the output backwards.

V₁ is the output valve. Its grid is over-biased so that, under no-signal and very low signal levels, a total of 1.75mA is passed by the valve. D₁ which must be a Westector type W6 metal rectifier and not a crystal diode, rectifies a portion of the incoming signal and thereby applies positive bias to the grid. This cancels out some of the standing negative bias so that the valve passes more current and can therefore deal

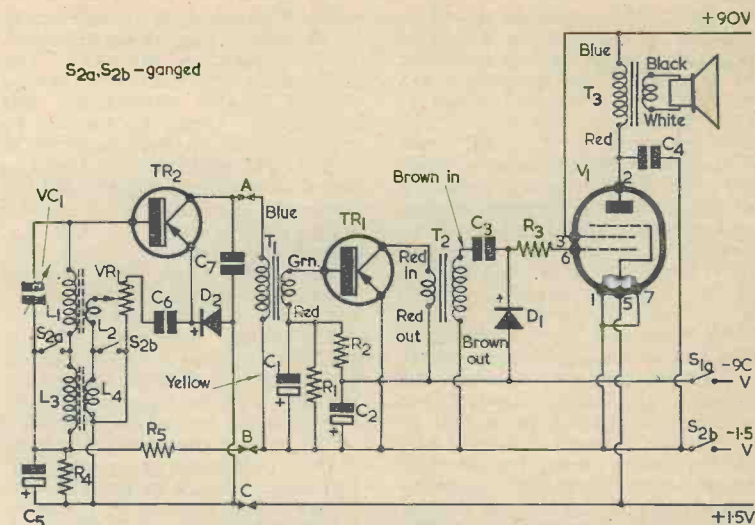


Fig. 2. The hybrid amplifier of Fig. 1 coupled to a single-transistor medium and long wave tuner to form a complete portable receiver. If it is intended to employ the tuner as a separate unit, it may be coupled to the amplifier at points A, B and C

with the signal. V₁ passes a total of 6mA at maximum output.

The provision of standing bias poses a problem which exists with Class B or quiescent push-pull arrangements as well as with the circuit being described. The easiest method of providing bias is to use a separate grid bias battery; but this is untidy, and there is the difficulty that the voltage would need constant adjustment as the high tension battery aged. The obvious alternative might appear to be the standard bias resistor connected between h.t. negative and i.t. negative. But the difficulty here is that if a resistor is chosen to give a consumption of 1.75mA under no-signal conditions, the voltage across it will be more than trebled when 6mA is passed. The reverse bias produced by D₁ will be unable to cope with the situation, whereupon the h.t. voltage available for V₁ will be drastically reduced and the output of the valve will be hopelessly curtailed. What is required is a resistor which decreases in value as the current passing through it increases. Fortunately a transistor, wired on the common emitter principle and without any d.c. negative feedback, such as is normally provided by means of a resistor between emitter and earth, is just such a device. And the transistor can be used to give both voltage and current amplification of the signal, thus performing a useful duty as a driver for V₁ in addition to its function as the valves bias resistor. The requirements of the

transistor are that it should have a good amplification factor and be capable of withstanding up to 8mA at 10 volts during momentary periods of overload. Normally the power handled will never exceed 6mA at about 9 volts. The OC75 has the characteristics needed.

Bias Circuit Operation

If Fig. 1 is examined it will be seen that the cathode current of V₁ passes through TR₁ and the primary of T₂. The value of R₂ is chosen to ensure a current of 1.75mA through V₁ and TR₁ when no signal is being received. When a signal arrives at

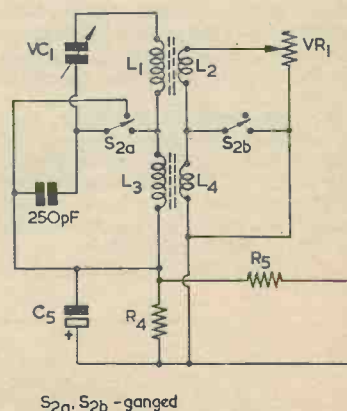


Fig. 3. A modified circuit which may be used if there is a tendency towards more treble on medium waves than on long waves. See "Additional Note"

the grid of V_1 a part of it will be rectified by D_1 , and this will be in opposition to the voltage occurring as a result of the transistor's d.c. resistance. The current through V_1 and TR_1 will increase and this will tend to cause a rise in voltage across TR_1 . But the rise in current through TR_1 will decrease its d.c. resistance so that the voltage between collector and emitter will tend to fall. Thus, the voltage across TR_1 will remain fairly constant and V_1 will be able to draw the extra current it needs to deal with a large input without being frustrated by an increase in standing negative grid bias voltage.

TR_1 will not be able to hold the voltage absolutely steady, but whereas an increase in current of three times through a normal bias resistor would result in a threefold increase in voltage across it, measurements with the prototype showed that when the current through TR_1 was trebled, the voltage across it only rose by less than one third. In practice it will be found that V_1 is able to receive the bias it needs for all circumstances.

Although TR_1 is deliberately arranged to be unstable as far as d.c. is concerned, there is no danger of damage due to thermal runaway as the current which can pass through V_1 is limited by the characteristics of the valve; and the current passing through V_1 is, of course, the current passing through TR_1 also.

The value of R_2 is fairly critical and if a milliammeter is available it is useful to insert it in one of the h.t. battery leads to check the current, which depends on the exact characteristics of TR_1 . If the current passing is less than about 1.5mA, R_2 may be decreased, slightly, in value; if the current is above about 2mA, R_2 should be increased. The author tried three different specimens of OC75, and in no case had to make any alteration to R_2 .

The requirements for T_2 are that it should provide a step-up of voltage from the collector of TR_1 to the input of V_1 , which is of very high impedance. Its primary should have a low resistance for d.c.—200Ω is ideal, 500Ω permissible—so as not to upset the voltage regulating

effect of TR_1 , and the winding should be capable of passing 6mA without the core becoming saturated. The transformer specified has proved suitable in all respects for this application. Connections to T_1 , T_2 and T_3 should be made as shown in Fig. 1. If, with the full portable circuit, there is instability on the long wave band, the long wave aerial rod, complete with L_3 and L_4 , should be turned through 180 degrees. This is only likely to prove necessary if the loudspeaker or T_3 are close to the long wave aerial rod.

The input impedance of the amplifier at points A and B is about 1MΩ, and it is therefore suitable for use after a crystal pick-up. If there is no volume control in the record player or other apparatus being used, a 1MΩ potentiometer can be used. Its slider connects to point A and its lower end to point B, the input being applied across the potentiometer. It will be seen that a third input point, C, is taken from the l.t. positive line. This makes it possible for the l.t. section of the battery to be used to power a tuner. The latter will need to have a high impedance output, as is given by a common base amplifier, in order to match into the primary of T_1 at the input of the amplifier.

Adding a Tuner

This amplifier lends itself very well to the construction of a portable receiver of the larger type, using a fair sized loudspeaker with which it will give excellent quality and good volume. To match the dimensions of the B103 battery, an 8 x 5in loudspeaker suggests itself. The prototype has been built into such a portable receiver, the tuning unit of which consists of a single MAT101 transistor wired on the "Spontaflex" principle which gives very sensitive results with a 1.5 volt power supply. The Spontaflex circuit has been described before by the author,* and it will suffice to say that it consists of a stage of common collector high frequency amplification with reaction, followed by demodulation

* See the article by Sir Douglas Hall in the June 1964 issue, and our note on page 56 of the August 1964 issue.

and a stage of common base low frequency amplification. The complete portable circuit is shown in Fig. 2. If, alternatively, the amplifier is to be built into a record player case and it is more convenient to have the radio tuner separate, the tuner circuit can be built into a small case of its own, coupling to the amplifier at points A, B and C.

The prototype uses two different ferrite rods for medium and long waves. L_1 and L_2 have 60 and 10 turns respectively of 32 s.w.g. enamelled wire close-wound on a $\frac{3}{8}$ in by 8in ferrite rod, the windings being separated by $\frac{1}{4}$ in. The long wave windings are on a large $9\frac{1}{2}$ in x $\frac{3}{8}$ in rod, as the portable receiver is used in a place where the long wave Light programme is badly screened. L_3 has 220 turns and L_4 35 turns of 38 s.w.g. enamelled wire. In many places a more normal $\frac{3}{8}$ x 8in rod will be found entirely satisfactory. An efficient arrangement with the smaller rod is to use 32 s.w.g. enamelled wire to give a long winding of 300 turns for L_3 , L_4 having 50 turns of the same wire separated from L_3 by about half an inch. All windings should be in the same direction.

The prototype of the portable receiver gives splendid results in S. Devon, many stations being available after dark at good volume, and a choice of four or five programmes during daylight.

Additional Note

Since the above was written, it has been found that there is a tendency towards more treble on the medium waveband than on long waves. This is because the relatively large impedance of L_3 provides negative feedback at high audio frequencies. Many constructors will prefer the deeper tone, and the effect can be obtained on the medium waveband by using a double pole, double throw switch for $S_2(a)$, (b). The junction of C_5 , R_4 , R_5 and L_3 is disconnected from the moving contact of $S_2(a)$ and taken to the new contact. A 250pF capacitor is shunted across these two contacts. The modified section of the circuit is shown in Fig. 3.

DENCO CT7B TURRET

In response to a continuing demand for these turrets, we are informed by Denco (Clacton) Ltd., that a further batch are being produced but that with material delays they will not be available until the end of this month.

The CT7B turret was featured in communication receiver designs in our November and December issues 1963, also in the May 1964 issue. It is also currently specified in our Data Book 14—*Short Wave Receivers for the Beginner*.

TWO-WAY HOME Telephone System

J. N. Price

THE AUTHOR WAS ASKED TO DESIGN AND BUILD a two-way telephone system by a neighbour who wished to be able to communicate between his house and garden shed-cum-workshop some 25 yards distant. The system described in this article was devised and the total cost was only just over £2. As the neighbour was non-technical (though, being a carpenter, he constructed the boxes) it was decided that the units should be identical and that operation should be as simple as possible. Unfortunately, this enables his two children to use the system!

Ex-G.P.O. Handsets

As readers will probably know, ex-G.P.O. handsets are available quite cheaply from surplus dealers. These handsets suffer from the disadvantage of a common connection between the microphone and earpiece. This leads to slight, though not unsurmountable, difficulties in design. Although

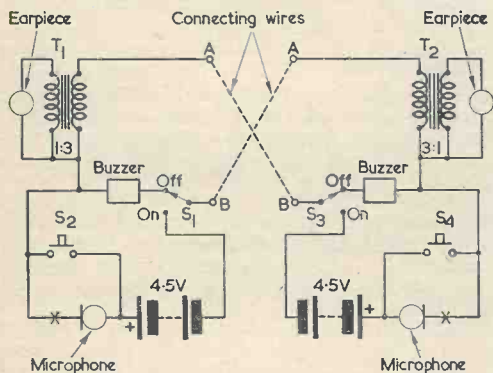


Fig. 1. The circuit of the telephone system

Components List (Fig. 1)

- 2 ex-G.P.O. Handsets (see text)
- 2 4.5V buzzers
- 2 Intervalve transformers, 3:1 (see text)
- 2 s.p.d.t. switches
- 2 Push button switches (1 make contact)
- 2 4.5V batteries (Ever-Ready type 1289)

experiments with one of these earpieces showed that they could operate satisfactorily with a direct current flowing in them, it was decided to use isolating transformers so that the d.c. necessary for the carbon microphone was kept away from the earpieces. The author tried an old intervalve transformer and, whilst it did not give the correct impedance match, operation was satisfactory.

Buzzers were used for signalling as the neighbour already had a door bell and a telephone. Buzzers are also smaller than bells. Two small 4.5V buzzers were procured together with two 3:1 intervalve transformers, two panel mounting push buttons and the remaining components. The author then decided that each unit could be accommodated in a box measuring about 6 x 4 x 2½ in deep, whereupon

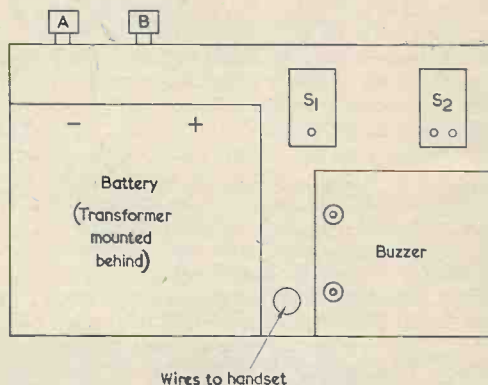



Fig. 2. The layout adopted by the author for each station

the neighbour provided two beautifully finished boxes with neat dovetail joints. It was only with much regret that the author drilled the necessary holes in them.

Circuit

The circuit of the system is shown in Fig. 1. The layout of components is not critical and any convenient mounting system can be used. A word of caution about the leads provided with the handsets is necessary. The pre-formed loops should not be disturbed as the wire will probably be of the tinsel variety which is almost impossible to solder properly.

The two line wires should be brought out to two terminals on the top of the case. It is important to

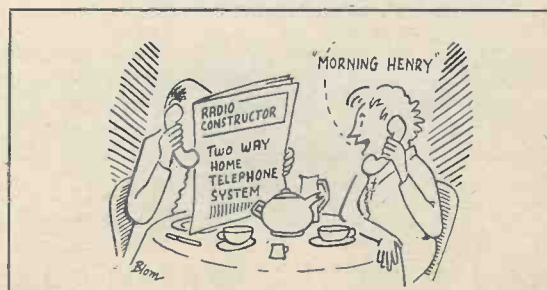

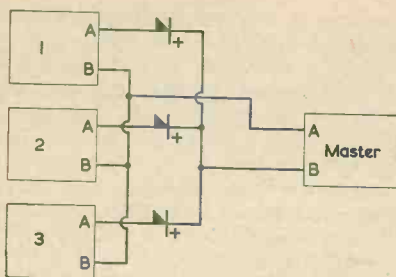


Fig. 3. A modification which allows multi-station operation to be achieved. Each station may, on its own, call the master station

identify these correctly, as A of one unit has to be connected to B of the other, and vice versa. The batteries can be fixed by small blocks of wood glued in position or by any other convenient method. With the author's units, contact was achieved by small brass strips screwed to the box, these being so positioned that the battery could not be reversed. If required, S_1 and S_3 may be operated by lifting the appropriate handset, but in the author's case ordinary toggle switches were used.

When the two units have been completed, it is suggested that they should be wired together on the bench for testing, as this saves much walking if any faults exist. If S_1 is operated, and then push button S_2 is pushed, the buzzer in the other station should operate. This can be silenced either by releasing S_2 or by operating S_3 . Whilst the buzzer is operating, the user of Station 1 will hear a tone in his earpiece due to the a.c. component of the current flowing in the primary of T_1 to the buzzer at Station 2. He should release S_2 before, or as soon as possible after, this tone ceases. After S_3 has been operated, the two users can speak to each other. When the conversation is over S_1 and S_3 must be returned to their Off positions. The method of calling from Station 2 is exactly the same. S_2 and S_4 should not be touched during the conversation as, apart from short-circuiting the microphones, pressing them together can cause an excessive current to flow through the transformers.

If, whilst the units are still on the bench, the handsets are placed together (microphone of one to earpiece of the other, and vice versa) a loud whistle will probably result. This can cause no damage, but indicates the carbon microphone's property of functioning as an amplifier.

Installation

The system may now be installed. Almost any insulated wire is suitable for wiring up, and the author used bell flex. It must be remembered that the wires must be identifiable, e.g. one black and one red.

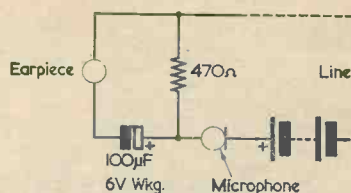


Fig. 4. An experimental circuit which obviates the necessity for the transformer

The units should be given a final test in their permanent positions. It may be found that some microphones cause a crackling noise to be produced in the earpiece. This is due to excessive d.c. in the microphone, and may be reduced by inserting a resistor and capacitor in parallel at point X. The resistor should be sufficient to reduce the current to about 5 to 8mA and the capacitor should have a low impedance compared with the resistance at the lowest frequency to be catered for.* (The commercial telephone system usually has a bandwidth of 300 c/s to 3.5 kc/s.)

Modifications

There are one or two modifications which the constructor may like to make. For instance, if a 4-wire cord is supplied with the handsets, the common connection between transformer primary and secondary may be omitted.

Two or more stations may be operated from the same master station by means of the simple modification shown in Fig. 3. The diodes can be of any small type sufficient to carry the current for the buzzer. Extensions cannot talk to extensions using this system, as this is difficult to arrange on a 2-wire basis.

Alternative Circuit

Since the installation described in this article was put into operation, the writer has been experimenting with a transformerless unit. This has been satisfactory for speech transmission and employs the circuit given in Fig. 4.

The transformerless circuit has not been checked with the full signalling facilities, but these should not offer too many difficulties. The switching arrangements will be the same as for the circuits previously described.

EDITOR'S NOTE

The ex-G.P.O. handsets employed by the author were obtained from Duke & Co. (Romford) Ltd., 621-3 Romford Road, Manor Park, London, E.12. The d.c. resistance of each earpiece was 60Ω . The transformers had a d.c. resistance of 30Ω in the winding connected to the earpiece and 225Ω in the winding connected in the microphone circuit.

* A capacitance of $25\mu\text{F}$ or more should be adequate in practice.
—EDITOR.

Next Month: THE "TRANSIVOX" MONOPHONIC ORGAN

IN YOUR WORKSHOP



Transistorised u.h.f. tuners for television receivers will be introduced in quantity in 1965. In this episode Smithy the Serviceman, aided as always by his able assistant Dick, takes time out before the Christmas holiday to describe the basic design features of this important new development

"I lift up my finger—"
"She loves you—"
"And I say: Tweet, Tweet—"
"Yeah, yeah, yeah—"
"Shush, Shush—"
"She loves you—"
"Now, Now—"
"Yeah, yeah, yeah!"
"Come, Come!"

Thus, respectively, sang Smithy and Dick as they clattered busily about their duties in the Workshop. For this was the afternoon of Christmas Eve and their hearts were full of joy and gladness, together with a stern determination to get the Christmas rush of faulty receivers cleared out of the way as soon as this could possibly be achieved.

Evidence of the festive scene was clearly visible about the Workshop. Dick's bench exhibited a magnificent array of Christmas Cards from his various aunts, whilst Smithy presented a more modest collection from his trade associates, these depicting in turn a robin perched on a television set, a robin perched on a radiogram, a robin perched on a transistor radio and a robin perched on a line output transformer. There was always a strange consistency in Smithy's Christmas Cards. Last year they had all been candles. This year they were all robins.

Transistors at U.H.F.

The singing of Dick and Smithy was continually interrupted by the sounds coming from the sets they were repairing. There was the wail of the signal generator, the whistle of the unstable i.f. amplifier and, after the triumphant fixing of the fault and the final test, the inevitable

sound of Christmas music.

All of a sudden the bustle ceased, and Dick and Smithy found themselves gazing at the now-empty "For Repair" racks.

"We've cleared them!" they exclaimed exultantly.

With one accord they sat down and allowed the feeling of pride in work well done to spread over them.

"And that," remarked Smithy with immense satisfaction, "is that. Another Christmas rush over!"

"It seems to have been easier this year," said Dick. "Either that, or I'm getting used to it."

"I think we've been luckier than usual," commented Smithy. "All the snags were nice easy ones. No intermittents or anything like that."

"Did you get any u.h.f. tuner faults?" asked Dick.

"Nary a one."

"Neither," said Dick, "did I. These u.h.f. tuners seem to be a lot more trouble-free than I thought they'd be when they first came in."

"They'll be even *more* trouble-free in the coming year and afterwards."

"How's that?"

"Because," replied Smithy, "they'll all be changing over from valves to transistors."

"That sounds interesting," said Dick enthusiastically. "What advantages do transistors give?"

"They give less noise at u.h.f. than valves do," replied Smithy. "And they also make it possible to design tuners which are simpler from the mechanical point of view."

"This is interesting," repeated Dick. "Have you got any gen on them?"

"Quite a bit," replied Smithy.

"It's pretty certain that the transistorised u.h.f. tuners in Britain will follow Continental practice in much the same manner as the valve types have done. What I've been doing, therefore, is to keep a close watch on Continental journals and publications, and to keep my ear down to the ground so far as things in this country are concerned. In consequence, I can give you some really reliable background gen on the form transistorised u.h.f. tuners will take up."

A thought occurred to the Serviceman, and he turned a suspicious gaze on his assistant.


"How is it," he asked, "that you're so enthusiastic about this new application for transistors? Last month you were screaming up the wall because British manufacturers have started introducing n.p.n. transistors into their radios!"

"That's different," replied Dick promptly. "In that case, I got the information *after* I'd tried to fix the sets which had the transistors in them. In this case, I'm getting the information before I have to tackle the sets."

"I suppose," said Smithy doubtfully, "that there is a certain amount of logic in what you say. Anyway, pop the kettle on and I'll collect my thoughts on this tuner business."

U.H.F. Oscillator

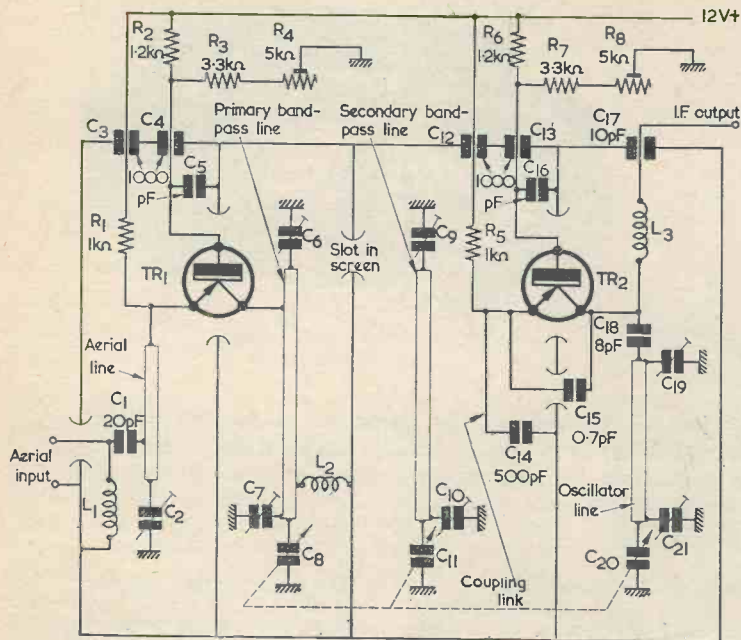Obediently, Dick walked over to the sink to fill the battered Workshop kettle and prepare the teapot, after which he returned to Smithy's bench. Smithy had, in the meanwhile, commenced to scribble out a circuit diagram, to which he was now putting



L_1, L_2, L_3 - UHF Chokes

Fig. 1. Basic circuit diagram for a transistorised u.h.f. tuner, following Continental practice. Component values are representative and half-wave lines are employed in the bandpass and oscillator tuned circuits. Trimmer values will be of the order of 0.4 to 4pF. TR_1 and TR_2 may be, typically, AF139s

the finishing touches. (Fig. 1.)

"Here we are," he announced triumphantly, as he put his pencil down on the bench. "This is the basic circuit for one of the two varieties of transistorised u.h.f. tuners which are knocking around these days. It's typical of Continental design approach and is, also, very similar to the valve tuners you find in current TV sets. It makes a good introduction, therefore, to the transistorised u.h.f. tuner. We've already nattered at quite some length about the valve u.h.f. tuner in the past, so I don't need to go over all that again. In any case there is an excellent description in 'Understanding Television'* which covers the ground completely."

Smithy cleared his throat, and prodded his finger at the circuit he had sketched out.

"In this circuit," he remarked, "you will note that there are two transistors. One of these, TR_1 , is the r.f. amplifier, whilst TR_2 is the oscillator-mixer."

"Just the same," remarked Dick,

"as you have with valves."

"That's right," confirmed Smithy. "Also, and in just the same manner as you have with the valve tuner, you have two bandpass tuned lines between the r.f. amplifier and the mixer-oscillator. There are, again as in the valve tuner, screened compartments. The aerial tuned circuit appears in one screened compartment, the primary bandpass line in the next screened compartment, the secondary bandpass line in the third, and the oscillator line in the fourth. (Fig. 2.) Valve u.h.f. tuners normally have a fifth compartment for the i.f. coil following the mixer, but this practice doesn't seem to be followed in the transistor versions. With these, the i.f. coil is normally mounted outside the case."

"What mode are the transistors connected in?"

"They're connected in grounded base," replied Smithy. "Transistors working in grounded base can amplify at much higher frequencies than when they are connected in the grounded emitter configuration. Another point to watch is that the supply to the tuner is positive of chassis, since it will normally be

taken, via a potential divider, from the television receiver h.t. line. A common type of transistor employed in u.h.f. tuners for both r.f. amplifier and mixer-oscillator is the AF139, although you may, of course, encounter other types which are similarly capable of working at these frequencies."

"Those supply circuits look a little complicated," commented Dick.

"They're quite easy when you get down to them," said Smithy, "as will shortly be revealed unto you. Before going further I should just spend a little time on the principle of operation of the tuned lines. The lines in the bandpass and oscillator compartments are of the order of half a wavelength long. They could thus become resonant at the frequency whose wavelength is twice their length, and you would have opposite voltage polarities at each end, as occurs with a tuned circuit. Actually, however, the lines are slightly shorter than a half wavelength at the highest frequency to be handled. This has the same effect as reducing their inductance, and so the lines can be made to resonate at frequencies lower than their natural resonant frequency by adding capacitance at both ends."

"Which is," commented Dick, "similar, once more, to what happens in the valve tuner."

"Exactly," agreed Smithy. "Let's now start off at the aerial input connection. In the tuner unit circuit I've drawn here the aerial goes into an aperiodic input circuit which is broadly tuned over the whole of Bands IV and V. Just so that we can keep in mind the frequencies we are dealing with I should add incidentally that, in the U.K., Band IV is 470 to 582 Mc/s and Band V is 614 to 854 Mc/s."

"Valve u.h.f. tuners," interrupted Dick, "don't have an aperiodic tuned circuit in the aerial input stage. It's tuned by the ganged variable capacitor."

"In this country it is," Smithy corrected him, "and that's because, due to the spacing between channels adopted for single transmitters over here, you need a high level of second channel rejection. The official quoted figure is, in fact, a minimum of 53dB. The second channel interference problem is not so acute on the Continent, and so they can get by with an aperiodic aerial stage. In the U.K., on the other hand, a tuned aerial stage is necessary to give the requisite second channel rejection. Or, at least, it is in valve tuners anyway."

"In the circuit you've just drawn,"

* *Understanding Television*, by J. R. Davies, Published by Data Publications Ltd.

Dick reminded Smithy, "the aerial stage is aperiodic."

"I know it is," replied Smithy, a little heatedly. "But as I said at the beginning I'm showing you a typical Continental design approach. British transistorised tuners will probably incorporate a tuned aerial input stage in just the same manner as current valve tuners do."

"Good," pronounced Dick with great satisfaction. "I'm glad we've got that little point settled."

"With all these interruptions of yours," complained Smithy, "I've forgotten where I'd got to!"

"We'd bunged the aerial signal," offered Dick helpfully, "into the input circuit. Presumably we next turn to the first transistor."

"Ah, yes," said Smithy. "The first transistor. Now this is connected, as I said just now, in grounded base, and we should next take a butcher's at the manner in which power is applied to it. We have a 12 volt positive point outside the tuner, this being taken from the receiver h.t. supply. The chassis of the tuner is, therefore, the negative supply rail. The r.f. amplifier transistor is a p.n.p., and so its collector wants to go to negative. This it does via the primary bandpass line and the u.h.f. choke L₂, the latter completing the circuit to chassis. The base of the transistor is grounded to chassis, from the point of view of r.f., via the 1,000pF capacitor C₅, which has to have a very low inductance. This component could, in practice, be a ceramic disc capacitor with one surface soldered direct to the screen between compartments. It would, also, be positioned very close to the transistor. The base needs a negative bias, and this is provided by the potential divider given by R₄, R₃ and R₂."

"R₄," interjected Dick, "is a preset pot. Why do you have a preset pot here?"

"It's intended to provide adjustment of base bias," explained Smithy. "It's set up at the factory for optimum transistor performance."

"Having preset pots," commented Dick, "is rather a new idea in tuners, isn't it?"

"The scheme seems to be quite common," replied Smithy, "so far as the present generation of transistor u.h.f. tuners is concerned. They all seem to have preset pots for getting the transistors on to the best operating points."

"Isn't this rather an expensive approach?"

"Not really," replied Smithy. "The tiny little preset potentiometers that are used these days don't

cost a great deal to produce. I should imagine, though, that when manufacturers have had a bit more experience of making u.h.f. tuners, the pots will disappear and be replaced by ordinary fixed resistors. For the time being, however, they seem to be used pretty universally."

"I see," said Dick. "What about the supply to the emitter?"

"That," replied Smithy, "comes from the 12 volt positive point via R₁. Once you've got used to the idea of chassis being negative, the whole supply business becomes very simple. The collector goes to negative via the primary bandpass line and L₂. The base receives bias from the negative chassis via R₃ and R₄, whilst the emitter goes to positive via R₁. You'll note, also, that this set-up gives you the standard stabilising circuit which is needed to prevent thermal runaway."

"Fair enough," commented Dick. "Let's carry on to the primary bandpass line."

Bandpass Circuits

But any reply that Smithy could have made was drowned by a piercing whistle from the kettle. Hastily, Dick got up and made his way to the sink, to undertake the ceremonial brewing of the Workshop tea. After briskly stirring the contents of the teapot with a hacksaw blade, he carefully poured out the precious fluid. He then returned, and placed a blue plastic beaker alongside the Serviceman.

"Dash it all," complained Smithy, "haven't we any cups?"

"Cups?" exclaimed Dick. "Cups?"

We haven't had a cup in the Workshop for the last three years!"

"What happened to that old tin mug of mine, then?"

Dick shuddered as a mental picture rose before him of Smithy's insanitary drinking vessel.

"That filthy object," he announced in a tone of revulsion, "is now reposing in our dustbin. It's sprung a leak."

"Sprung a leak? How come?"

"I accidentally," stated Dick, "drilled six ¼ in holes in the bottom of it."

"Well, that's a nice Christmassy action, I must say," grumbled Smithy. "Talk about the season of goodwill!"

"Blimey," said Dick, "I'd forgotten all about it's being Christmas. Just a minute!"

He hurried over to his bench, opened a drawer and extracted a limp brown paper parcel. Returning, he handed this over to the Serviceman with a flourish.

"Here we are, Smithy," he pronounced, "and a Merry Christmas, too!"

"Well, this is very good of you," said Smithy, unfastening the parcel. "Very good of you, indeed."

He removed the last piece of paper and gazed uncertainly at its contents.

"Ah yes," he remarked dubiously, "now this is just what I've always wanted!"

"I'm glad you like it," said Dick, pleased.

"I'm delighted with it," replied Smithy.

There was an awkward silence for

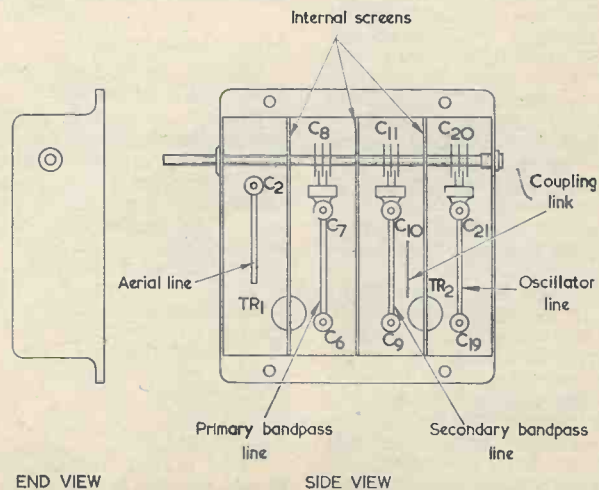


Fig. 2. Layout of the principal components of the tuner of Fig. 1. The trimmers are concentric types with internal adjusting screws, and are soldered to the chassis of the tuner. The transistors appear in slots in the screens, with their leads projecting upwards

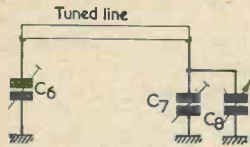


Fig. 3. The tuned lines, with capacitance at either end provided by the tuning capacitor and trimmers, enter pi tuned circuits. The components shown here apply to the primary bandpass line

a moment.

"Don't you want to try it on?"

"Try it on?"

"Yes," said Dick impatiently, "to see what it looks like."

"Where," asked Smyth doubtfully, "shall I put it?"

"Around your neck, of course."

"Oh," exclaimed Smyth, "it's a tie!"

"Of course it's a tie," replied Dick, reproachfully. "And I should add that I spent a lot of time choosing it for you, too."

"It seems to be very narrow."

"It's meant to be narrow," said Dick impatiently. "That's the modern idea. And the puce shade is just the thing right now. That tie, Smyth, is the snazziest one I've seen for ages."

"I'm certain it is," said Smyth.

"And I'm very grateful to you for giving it to me as well. Thank you very much, indeed."

"Aren't you," persisted Dick, "going to try it on?"

"Not for the moment," replied Smyth, carefully. "It'll mean undoing all my collar studs and things."

"As you like," said Dick, disappointedly. "Later on perhaps."

"Yes, of course," said Smyth hastily. "In the meantime, how about getting back to this transistorised tuner of ours?"

"Okeydoke," said Dick, forgetting the tie for the moment. "Let's carry on to the bandpass lines."

"Right," said Smyth, manifestly relieved at the change in subject. "As you will probably have noticed, the bandpass lines are pretty well the same as those you find in valve tuners. The collector of the first transistor couples directly into the primary bandpass line. Since this collector is at fairly low impedance, it taps into the line a little of the way from the end to get optimum matching. You may find other ways of coupling the collector into the primary bandpass line, but the method I've shown here is pretty

representative. The primary bandpass line has, in just the same manner as occurs with valve u.h.f. tuners, a trimmer at the tuning capacitor end, and a second trimmer at the other end."

"So making," chimed in Dick, "a pi circuit (Fig. 3). The trimmer at the tuning capacitor end is adjusted when the latter is at minimum capacitance, and the trimmer at the end remote from the tuning capacitor is adjusted when the latter is at maximum capacitance."

"That's the idea," agreed Smyth. "These adjustments are made at the factory and they enable all the lines in the tuner to be accurately tracked with each other over the swing of the variable gang capacitor. So there's nothing new there."

He paused and took a sip from his plastic beaker.

"We next," he continued, "carry on to the secondary bandpass line. The primary line is coupled to the secondary line in the same manner as you have with valve tuners. There may be a slot in the screen between the two compartments, or you may, for example, have an adjustable wire loop (Fig. 4). Also the same as in the valve tuner is the fact that the secondary line couples to the emitter of the mixer-oscillator via a coupling wire link."

"In the valve version," said Dick, "that link couples to the cathode of the mixer-oscillator valve."

"Exactly," replied Smyth. "And as you can see, things are very much the same here. The secondary bandpass line has, of course, the regulation pair of trimmers at each end."

Mixer-Oscillator Stage

"How," asked Dick, "does the mixer-oscillator oscillate?"

"That," commented Smyth, "is one of the delightful things about the transistorised u.h.f. tuner. Like the r.f. amplifier, the mixer-oscillator transistor is connected in grounded base. This means that the emitter and collector are in phase. When the emitter goes negative so, also, does the collector. To make the transistor oscillate, therefore, all you need to do is to couple its collector to a tuned line and, also, to the emitter via a capacitor of about 0.7pF. In my circuit this capacitor is C₁₅. And what could you have simpler than that?"

"That is neat," agreed Dick. "I should imagine that this also means that you've got to keep the stray capacitance between collector and emitter to an absolute minimum if you don't want oscillation to take place."

"You're dead right there," agreed Smyth. "Such feedback could cause instability with the r.f. amplifier transistor, and it's necessary to provide very adequate screening between emitter and collector in that stage. Returning to the mixer-oscillator transistor, you'll notice that the collector couples to the oscillator tuned line via the 8pF capacitor, C₁₈. The emitter is not at chassis potential so far as r.f. is concerned, because of the impedance offered by the coupling line."

"What about supplies to the mixer-oscillator transistor?" asked Dick. "There doesn't, for instance, seem to be any d.c. connection to the collector."

"What actually happens there," said Smyth, "is that the collector connects to chassis via an external i.f. coil which I haven't shown. L₃ is merely a u.h.f. choke which prevents the i.f. output feed-through capacitor, C₁₇, from affecting u.h.f. operation. In combination with that feed-through it will also, of course, prevent u.h.f. signals getting out into the i.f. circuits. The base receives its bias via the potential divider given by R₈, R₇ and R₆, R₈ being preset to enable the transistor to be set to optimum working conditions. And the emitter connects to the 12 volt positive point via R₅. This has a resistance of 1kΩ and doesn't affect u.h.f. signals. At the same time, in combination with R₈, R₇ and R₆, it provides stabilisation."

Smyth drained his beaker.

"And that," he remarked with an air of finality, "is that. More tea, please!"

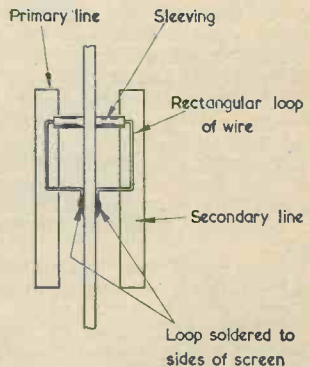


Fig. 4. A method of providing adjustable coupling between primary and secondary lines. The loop connects to the internal screen only at the points where it is soldered. Coupling is varied by bending the sides of the loop closer to, or further away from, the lines

"Do you mean to say," gasped Dick incredulously, "that that is all there is to transistorised u.h.f. tuners?"

"That's all there is so far as basic circuit operation is concerned," confirmed Smythy. "If you've followed what I've said up to now, you'll have a very good idea of how these tuners function."

"They're a piece of cake!" exclaimed Dick. "They're much simpler than valve u.h.f. tuners!"

"I wouldn't go so far as to say that," commented Smythy warily. "They may look a little simpler in circuit form, but that's mainly because they haven't got any heater wiring or heater chokes. More tea, please!"

"How do you get," persevered Dick, "the 12 volt supply?"

"A man," grunted Smythy, "could die of thirst in this Workshop!"

Hastily, Dick picked up Smythy's beaker and took it over to the sink to replenish it.

"But how do you," he persisted, over his shoulder, "get that supply?"

"There are several ways in which it can be done," replied Smythy. "One simple method would consist, for instance, of taking a dropping resistor from h.t. positive down to a 12 volt zener diode (Fig. 5). This would be economical of h.t. current, as the zener diode would only need a few milliamps to bring it on to the flat part of its characteristic. The remaining current in the dropping resistor would then be that used by the tuner itself. Which would be of the order of 10 to 20mA or so. At last!"

Smythy took the tea from his assistant and drank deeply.

"That's a point," remarked Dick impressed. "You're only working at 12 volts, and yet the current drawn is still just about the same as for a valve u.h.f. tuner."

"Exactly," said Smythy, smacking his lips. "And just think how much less heat is dissipated in the transistor tuner unit than in the valve version. One result of the reduced heat is that oscillator drift with warm-up is liable to be considerably lower."

Quarter-Wave Lines

Smythy took a further draught from the beaker and held it up in front of him.

"How," he asked, "did you come by this beaker?"

"I got it free," explained Dick, "with a large tube of Alka-Seltzers."

"Dash it all," said Smythy, glancing over at Dick's bench, "you've got one, too."

"I know," replied Dick. "But

don't forget that we're not only on the threshold of Christmas. There's New Year's Eve to come as well!"

Smythy chuckled.

"You seem to be stocking up well in advance," he grinned. "Which reminds me that I've got a present for you, too."

Smythy rummaged beneath his bench, and the second brown paper parcel of that afternoon made its appearance. Eagerly, Dick tore off the wrapping.

"They're very nice," he remarked with a puzzled frown as he surveyed Smythy's present. "Do you know, they're just what I wanted!"

"I thought you'd be pleased with them," commented Smythy with a benign smile. "Slip them on and see if they fit."

"Slip them on?"

"Yes, of course."

Once again, there was an embarrassed silence.

"How do you mean, slip them on?" queried Dick. "I can't think of any part of me that they'd fit."

"You put them on your shoes, you buffoon," exploded Smythy. "They're galoshes!"

"Galoshes?"

Smythy turned his eyes towards the ceiling.

"Haven't you ever heard," he snorted, "of galoshes?"

"I'm awfully sorry, Smythy," said Dick contritely, "but I honestly haven't."

"You put galoshes over your shoes to keep the wet out."

"Well, I'm blowed," exclaimed Dick. "What a knobby idea! And do people walk around with shoes on and galoshes?"

"Of course they do."

"Well, I'm blowed," repeated Dick. "Do you know, Smythy, I honestly didn't know that until now."

"Well, you do now," said Smythy, mollified.

"I think they're an excellent idea," said Dick enthusiastically. "I'll try them out on the way home. And thank you very much indeed."

"Not at all."


"They're a smashing present."

"Don't mention it."

"What an excellent Christmas Eve this is," remarked Dick, having satisfactorily discharged his obligations in the way of thanks. "Here we are, all the work is done, and we're just sitting around nattering with nothing else to do."

"It is pleasant," agreed Smythy. "Incidentally, I haven't finished giving you all the gen on this transistorised u.h.f. tuner unit business."

"Oh, of course you haven't," said

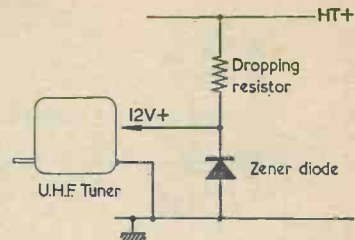

M479

Fig. 5. A simple method of providing the 12 volt supply for the u.h.f. tuner. The tuner chassis is at the same potential as the receiver chassis, and the zener diode stabilises at 12 volts

Dick, as a sudden thought occurred to him. "You said at the beginning that you were referring to one of the two varieties of Continental tuner. What's the second variety like?"

"Much the same as the first," replied Smythy, "except it doesn't use half-wave lines."

"What does it use, then?"

"Quarter-wave lines."


Dick looked bewildered.

"I don't get it," he said. "I can understand how a half-wave tuned line works, because I've got used to it with valve tuners and in the transistorised tuner we've considered up to now. How does this quarter-wave business fit in?"

"To explain that," said Smythy, pulling over his pad of papers, "I'll have to draw you another circuit."

There was silence for several minutes as Smythy sketched out a second tuner unit circuit (Fig. 6).

"There we are," he said, laying his pencil down. "And, once more, we'll start at the aerial input end. Again, we have an aperiodic aerial input circuit, only in this case the aerial goes straight into the emitter of the r.f. amplifier without any line at all. I must emphasise once more that this is Continental practice, and that the corresponding British versions may have a tuned aerial input stage to satisfy the second channel rejection requirement. You will note that the emitter of the r.f. amplifier, TR₁, connects to the 12 volt positive point via the 1kΩ resistor, R₁. The base is grounded to chassis via C₄, and bias can be applied by external components in the same manner as occurred with the previous tuner we discussed. The collector connects to the primary bandpass line, which terminates directly to chassis and thereby provides the negative supply. The primary line couples to the secondary bandpass line via a slot in the screen between them or by any other coupling device, and this sec-

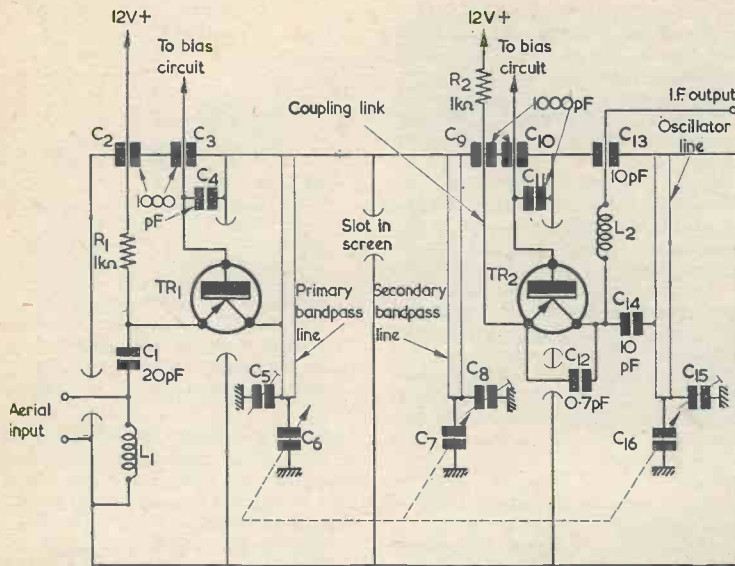

L_1, L_2 -UHF Chokes

Fig. 6. The basic circuit of a u.h.f. tuner employing quarter-wave resonant lines, with representative component values. The tuned lines terminate at the chassis

ondary line also terminates at the chassis."

"There's only one trimmer on those lines," objected Dick. "The lines in the previous tuner had a trimmer at both ends."

"I know," said Smyth. "But don't forget that, in this instance, the end of the line remote from the tuning capacitor connects to chassis, and so there's no point in putting a trimmer there in any case! Now, the secondary line couples to the mixer-oscillator transistor via a coupling link, as before. The earthy end of the coupling link passes through the bypass feed-through, C₉, and carries on to the 12 volt positive point via the 1kΩ resistor R₂. The base of TR₂ is grounded via C₁₁ and connects, externally, to the same sort of bias network as we had with the previous tuner. To obtain oscillation, the collector is coupled back to the emitter via a low-value capacitor, and it couples to the oscillator tuned line via the 10pF capacitor, C₁₄. It couldn't connect directly because, like the bandpass lines, the oscillator line is terminated at the chassis, and a direct connection would short-circuit the i.f. output. The collector connects to the u.h.f. choke L₂, and thence, via feed-through capacitor C₁₃, to an external i.f. coil. The latter provides the chassis connection, with the result that the mixer-oscillator collector has the negative

supply that it needs, as well."

"I'm still," said Dick, "not at all clear about those tuned lines."

"Well," replied Smyth, "as I said just now, they're quarter-wave lines. In just the same manner as the half-wave lines were slightly shorter than a half wavelength at the highest frequency to be covered, these are slightly shorter than a quarter wavelength at the highest frequency to be covered."

"In that case," Dick pointed out, "you must lose a fantastic amount of inductance. Do the variable capacitor sections or the trimmers have a higher capacitance than occurs in the half-wave tuner?"

"Those capacitances," said Smyth, "are about the same."

"Then how," asked Dick despairingly, "can you tune over the same band of frequencies with a line that's only half as long?"

"It's because," explained Smyth, "the line is terminated at a nodal point for voltage."

"That," snarled Dick, sarcastically, "answers all my questions! I'll now be able to go all through Christmas realising that a line of half the length resonates at the same frequency because it's terminated at a nodal point for voltage!"

"But that," protested Smyth, "is perfectly true."

"I don't even know," wailed Dick, "what a nodal point is!"

"Oh, I see," replied Smyth. "Perhaps that is something of a disadvantage."

He scribbled on his pad.

"I've just drawn," he continued, "a half-wave dipole. When this is resonant we have a voltage and current distribution along it in which voltage is highest at the ends and zero at the centre, and in which current is highest at the ends and lowest at the centre (Fig. 7). This corresponds to the condition under which the half-wave lines of the first tuner work. O.K.?"

"O.K. up to now," qualified Dick cautiously.

"Right," said Smyth. "Now, the term 'node' defines the position where an alternating quantity has zero amplitude. With the half-wave line, the voltage has zero amplitude at the centre. So this is the nodal point for voltage."

"That does at least," conceded Dick, "explain the nodal point business."

"Fair enough," said Smyth. "If, halfway along the line, we have zero voltage, the line at that point is at chassis potential. In consequence, there's no point in continuing the line any further and it can be terminated at the chassis itself."

Dick gazed at Smyth with agonised concentration.

"I'm sorry," he said eventually, "but I just don't get it. You can talk till you're blue in the face about nodal points and all that, but I'm right out of my depth here. So far as I can make out, we can cut a line in half and yet it's still resonant at the same frequency!"

"Have you ever heard," asked Smyth, "of a quarter-wave aerial?"

"Of course I have," replied Dick indignantly. "It's a quarter-wave rod stuck up over a flat metal plate. The plate provides a reflection of the rod, so that the whole thing functions in pretty well the same manner as a half-wave dipole."

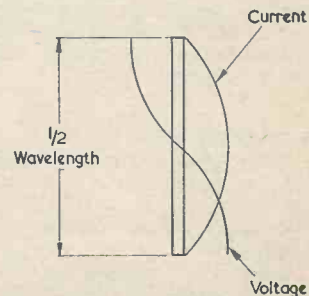


Fig. 7. The voltage and current distribution in a half-wave conductor at resonance

"Well?"

"I still don't see the connection," remarked Dick thoughtfully. "Wait a minute, though! The quarter-wave line in the tuner terminates at the chassis. Could you say that the chassis offers a reflection of the quarter-wave, so that the whole thing acts in the same way as a half-wave line?"

"What's good enough for aerials," pronounced Smithy, "is good enough for tuners! And your assumption is quite reasonable as a means towards understanding how the quarter-wave lines work. In practice, the quarter-wave lines of the tuner are soldered direct to the chassis side to which they are perpendicular (Fig. 8 (a)). You could say, therefore, that the metal side of the chassis offers reflections which make each line look like a half-wave line (Fig. 8 (b)). Which is all there is to it. By using the quarter-wave scheme, you get a lot of advantages. These include a simplified tuner assembly, shorter lines, a smaller chassis, and fewer components, all of which add up to a very sizeable saving in costs."

"There's one snag, though."

"What's that?"

"You've only got one trimmer for each line," said Dick. "The half-wave lines have two trimmers, which enable them to be easily tracked up. How can you make tracking adjustments with only one trimmer?"

"Tracking is more difficult with one trimmer," replied Smithy. "But don't forget that there are split end-vanes on the variable capacitor sections. With the quarter-wave tuner, tracking adjustments can be made by bending these out as required. You'll probably find much more evidence of factory adjustment of the end-vanes in a tuner using quarter-wave lines than in one using half-wave lines."

Final Ceremony

With an air of finality, Smithy pushed his pad of papers away from

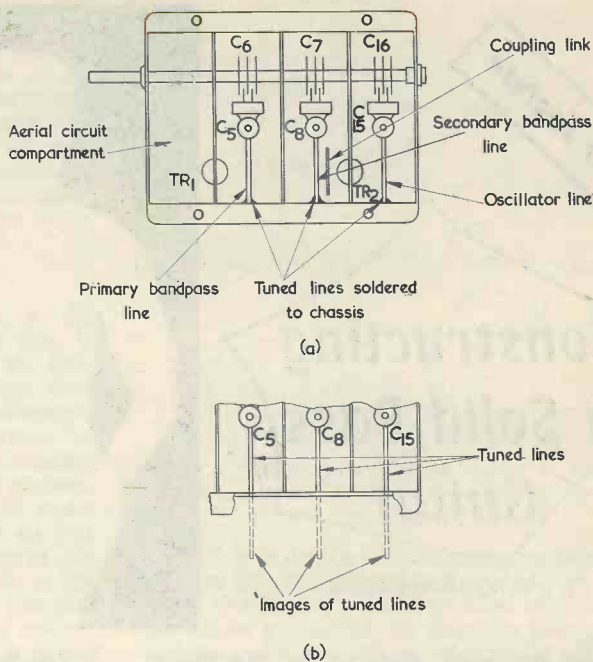


Fig. 8 (a). The layout of the principal components in the circuit of Fig. 6. The ends of the tuned lines are soldered direct to the lower side of the chassis

(b). Remembering that a quarter-wave aerial is "reflected" by the flat screen on which it is mounted, it can prove helpful to look upon the quarter-wave tuned lines as being "reflected" by the side of the chassis, so that they take up the appearance of half-wave lines

him and rose from his stool. He wandered thoughtfully to the cupboard in which the service manuals were kept.

"You'll be running out of hiding places, soon," chuckled Dick.

Ignoring his assistant's comment, Smithy returned with a bottle and two glasses.

"Here we are, my boy," he said, handing a charged glass to his assistant. "And all the very best!"

"The same to you," responded Dick, appreciatively, "and a Merry

Christmas, too."

Smithy held up his glass.

"A Merry Christmas to you as well."

The pair rose.

"We must also," continued Smithy, "wish a Merry Christmas to the readers who've put up with our antics over the past twelve months. A very Merry Christmas to you all!"

"And let us end," chimed in Dick, "as we have ended in all the previous years, by saying 'God. Bless Us, Every One!'"

Liverpool Airport has **EMI** Closed-Circuit TV

Visitors to Liverpool Airport can now see arrival and departure board information displayed on closed-circuit TV receivers at several points in lounges and restaurants throughout the main airport building. As subcontractor to Standard Telephones and Cables Limited, EMI Electronics Ltd. has installed three type 6 cameras, four monitors and a control console in a soundproofed studio.

One camera transmits picture of the arrival and departure boards. Another televises the girl announcers who make special announcements from time to time. The third camera transmits advertising slides.

Three monitors give preview pictures of the flight board, the announcer and the next advertising slide. The announcer, who sits at the control console, selects the picture to be transmitted and this appears on the fourth monitor.

Cover Feature

Constructing a Solid Bass Guitar

by Angus Geddes



ONE OF THE MOST POPULAR OF ELECTRONIC musical instruments is the solid bass guitar, in which the vibration of the strings is reproduced and amplified entirely by electronic means. In the traditional type of guitar the sound was magnified acoustically by resonance in the hollow body of the instrument. A later development was to fit a pick-up so that it picked up the tones from the resonant body and fed them to an electronic amplifier for subsequent playing at greatly increased intensity via a loudspeaker. The constructor of this type of instrument needed the woodworking skill of a professional musical instrument maker, but the assembly of the "solid" type is well within the capabilities of the average home constructor.

The bass guitar was originally designed to take the place of the double bass in jazz or pop groups, as the double bass is such an awkward instrument to carry about. Prices of commercially manufactured bass guitars can range from 40 to 160 guineas. As a reasonably efficient bass guitar of the solid type can be constructed comparatively easily, it is well worth considering the construction of such an instrument oneself. As can be seen from the illustrations and diagrams, construction of a presentable and efficient instrument can be carried out relatively easily and at the small cost of some £10 to £15 for materials and parts.

Materials

The materials required are as follows:

One piece of softwood, 12 x 18in in length and approximately 1½in thick. This is to form the body section and pine is a suitable wood for the purpose. One piece of oak, 30in long, 3in wide and 1in thick, for the arm. One piece of oak-faced ply, 22in long and 2½in wide, for the fretboard. One piece of Formica to cover part of the body, as shown in Fig. 1. One bass guitar pick-up, four bass guitar machine heads, one tail piece and bridge, four electric bass guitar strings and 4ft of fret wire. One jack socket.

Most of these items should be obtainable locally. The wood and Formica may be purchased from a good hobbies shop or, separately, from timber merchants and hardware stores. The pick-up, bass guitar machine heads, bridge and tail piece, strings, etc., can be purchased from a good music or record shop. The bridge and tail piece should be bought at the same time as the pick-up, so that the two match; i.e., the strings are held in such a position by the tailpiece and bridge that they come directly

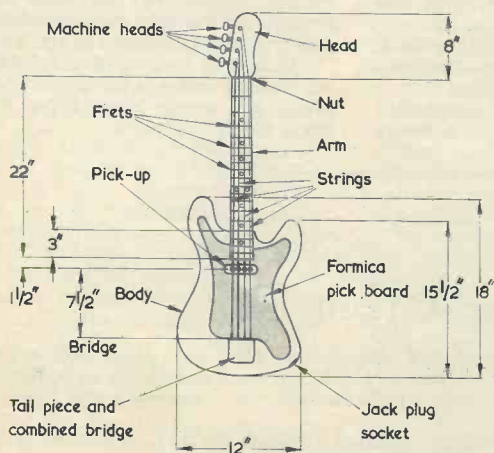


Fig. 1. The general appearance, with dimensions, of the completed guitar

over the centre of the pole pieces of the pick-up unit. There are various makes available, and the constructor is advised to seek the advice of his dealer, or advertisers in this magazine, for particulars of what is available. It should be noted, too, that the impedance of some pick-ups can be quite low, and that impedance varies from model to model. A pick-up should be obtained which offers a fairly reasonable match with the amplifier which is to be used.

Construction

First, with a fretsaw, cut the softwood to the rough shape of the body as indicated in Fig. 1. Then, with a coarse file, smooth down to the final desired shape. If desired, round off the edges, thus giving a better appearance to the finished instrument.

Next make up the arm. The section forming the fret board should be 22in long, with the remaining 8in shaped, with saw and file, into the head portion. Some constructors may feel it desirable to make the head section slope slightly backwards so that the strings are held reliably in the grooves of the "nut". This is not really necessary, however, as the "nut" shown in the model described here provides the necessary clearance, particularly if the surface of the head is well sanded down so that it slopes away slightly from the surface of the arm to which the fretboard is attached.

The fret board section of the arm should be 1½in wide at the "nut" and 2¼in wide at the join of the body. The strip of ply should be shaped to the fret board section and glued on.

The body and the arm now have to be *very firmly* joined together. This is done by dovetailing them together, gluing and screwing the joint. The details of this joint are shown in Fig. 2. Care must be taken in this operation not to make the body section dimensioned "A" too thin, when cutting out, or the joint will be weak. The actual thickness of the section shown at "A" in Fig. 2 depends on the thickness of the wood forming the body. In the author's instrument it is about ½in. Put the screws in from the underside of the body, and screw well home into the dovetail of the arm. Sink the screw heads just below the surface and cover their heads with plastic wood. When dry, sand the excess of the latter away, so that a smooth surface is available on the underside of the body for subsequent painting.

After this, the Formica is cut to the required shape for the pick board, which should be fairly large so as to cover the wires leading to the pick-up from the jack socket. The latter is mounted in a small cavity, gouged out of the rear of the body, as shown in Fig. 3. File a "flat" on the edge of the body near the cavity and drill through to take the mounting bush of the jack socket. Fill up the cavity with plastic wood and cover with a small piece of Formica, after having of course connected the pick-up wires to the connection tags on the socket.

The pick-up should be mounted after the top side of the body has been covered with Formica. Whilst the latter (shown in Fig. 1 as the "Formica pick

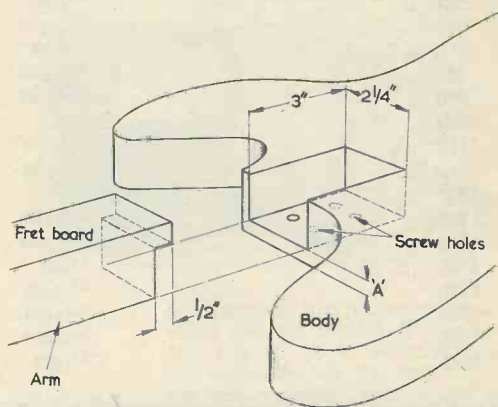


Fig. 2. Detail illustrating the manner in which the arm is secured to the body. For reasons of clarity, the arm is not shown rounded off

board") is primarily for decorative purposes, it also helps to give the pick-up unit a good, firm, foundation. The pick-up should be fitted after the strings have been positioned, so that the pole pieces are directly under the strings. It may be necessary to pad the pick-up unit up a little, so that there is a gap of not more than ¼in between the taut strings and the ends of the pole pieces. The pick-up is screwed, through holes in the Formica, into the wood of the body. Use screws long enough to give a good firm fixing.

Fitting the Frets

The next step is to fit the frets. These *must* be fitted accurately, so as to obtain a perfect note. The following dimensions are measured from the "nut" to the fret, then from the first fret to the second, and so on:

1st fret	113/16in
2nd "	15/8in
3rd "	19/16in
4th "	17/16in

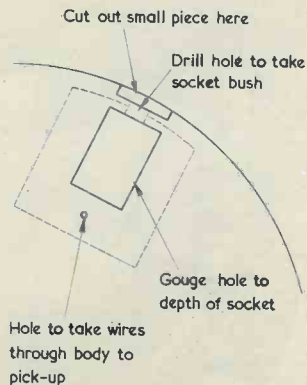


Fig. 3. View of the underside of the body, showing the fitting of the jack socket. The area within the dotted line is finally covered with Formica

5th	”	13/8in
6th	”	19/32in
7th	”	11/4in
8th	”	15/32in
9th	”	13/32in
10th	”	1in
11th	”	31/32in
12th	”	15/16in
13th	”	7/8in
14th	”	13/16in
15th	”	25/32in
16th	”	3/4in
17th	”	23/32in
18th	”	11/16in
19th	”	5/8in
20th	”	9/16in

It will be noted that there is a progressive decrease in the distance between successive frets from the outer to the inner end of the arm. At the lower end, this progressive decrease becomes very small and it is difficult to measure the position of these frets with accuracy. Fortunately, this end of the scale is very little used and discrepancies here are not of quite as much importance. The point is to make each fret just a little closer to its adjacent one than was the previous one. From about the 15th fret onwards, the decrease is in $\frac{1}{32}$ in steps, which are not easy to mark with accuracy. If the constructor finds difficulties in cutting and fixing the frets over this section of the scale, he should not worry too much and should attempt to mark to as high an accuracy as he can, bearing in mind the progressively decreasing spacings between frets.

To fit the frets, saw into the fret board with a fine

saw so making narrow grooves into which the fret wire, cut into suitable lengths, can be pressed. It is important to note that these fret dimensions are only for an instrument which has its *bridge 31in* from its “nut”


Finishing

Having completed the instrument up to this stage, the body should now be painted. When it is quite dry several coats of either clear varnish or plastic varnish should be applied.

Finally, fit the bass guitar machine heads, tail piece and bridge, bass pick-up and the four electric bass guitar strings. Tune the guitar to the notes E, A, D and G, and the instrument is complete.

Readers familiar with this type of musical instrument will know that, to get the best out of it, it must be used with an electronic amplifier suitable for the bass guitar. The instrument, as described, can be tested out on any amplifier with suitable input, the “Gram” input on some radiograms being suitable. But for the full capabilities of the bass guitar to be realised, an amplifier offering 20 to 50 watts is required, this being coupled to speakers capable of handling such an output. For those not already equipped with such an amplifier, one would mention that they can frequently be picked up secondhand and the writer would recommend the “Small Ads” columns of this magazine as a good place to advertise one’s requirements. Alternatively, several firms offer amplifiers of this type in kit form, and these are well within the capability of anyone who is able to make up the instrument itself. The reader is referred to the advertisement pages of this journal for details of such equipment.

LEARN TO PLAY THE GUITAR

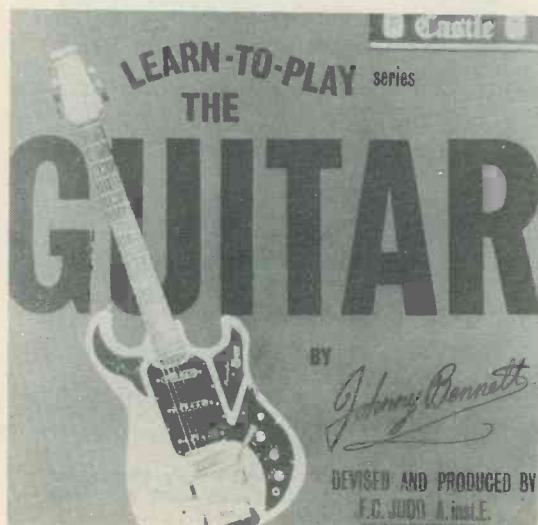

Having read how to make a guitar, it is most likely that many readers may now like to learn how to play it! Castle Records have just recently released the first of their “Learn to Play” series, the disc being entitled “The Guitar”.

This 10in LP disc has six complete lessons from tuning to modern beat rhythms and from this recording one can learn tuning, chords, plectrum technique, modern beat and blues rhythms. No musical knowledge is required—Johnny Bennett, top guitarist with many world famous vocal stars and orchestras, conducting the lessons. Electric guitar techniques have been used throughout the recording using a Burns guitar.

Each record is complete with modern chord guides, practice and tuning charts.

Record No: LPG.1, which also includes multi-track guitar recordings one can practice with, is available at 21s. (including tax), special packing and postage 3s. (applicable to U.K. only) direct from Recorded Tuition Ltd., 174/6 Maybank Road, South Woodford, London, E.18.

ERRORS IN MEASUREMENT

JAMES ROBERT SQUIRES



Whether we are interested in electronics from the amateur or the professional point of view, we must inevitably base much of our work on electrical measurements. Our contributor, resident in the United States, presents an overall view of the field of electrical measurement, and draws attention to sources of error which are often overlooked

THE MOST IMPORTANT ARGUMENT for considering errors in measurement is the time and money that can be saved through an understanding of their effects. In the shop or laboratory, measurements are a big time consumer each and every day. Which measurements are useless? Which cause more damage than good? Which measurements lead the operator down the wrong path? Answers to these questions and others may be supplied by an understanding of the mechanics of error. Those readings you feel you must take regardless of the instrument used will consume precious time. You will want to draw full value from those few readings. A wet finger in the lamp socket no longer completes the measurement tools, nor does the accompanying shock complete the analysis of that measurement.*

There are many reasons for false readings. For our purposes they can be divided into two classes. Errors over which we have little or no control fall into the first class. Errors that we can take steps to eliminate or circumvent are in the second class, and are of special interest to those who must make measurements every day.

* We must hasten to point out that, whilst a wet finger in the lamp socket may be an accepted approach with American 117 volt mains, we do not recommend the practice with British mains voltages!—EDITOR.

Limits Of Error

Each piece of test equipment will have its own limits or error. By knowing these limits of error, found either in the equipment handbook or stated on the equipment itself, we can evaluate a particular instrument for a particular job. Usually, the smaller the limit of error the more expensive the instrument. Often, money is wasted buying instruments too precise and too accurate for the measuring job at hand. Each person must decide his own measurement needs. Many instrument manufacturers often mark the accuracy of the equipment right on the meter face or instrument panel. It is possible that all of these precautions against gross errors might lead some into a false sense of security. There are, however, many steps in error reduction that can economise on indicator readings.

At the present state of the art, it is not possible to measure energy values without drawing some energy from them. This changes the original energy by the amount needed to operate meter movements, oscilloscope amplifiers, and so on. For example, it is not possible to find voltmeters that have infinite internal resistance. Nevertheless, there are some neat tricks that can be used to reduce errors or bypass them.

Suppose, for example, we wanted

to measure the voltage across a load, and the current in that load. See Fig. 1. Is it better to place the voltmeter on the load side or the power supply side of the ammeter? In this case it would depend on the limit of error of the instruments used. Generally the more accurate of the two instruments (that is, the instrument drawing the least circuit energy) would be placed nearer the load. A 1,000Ω per volt meter on the load side of the ammeter would draw appreciable current for its own meter movement and the ammeter would monitor load current plus voltmeter current. If the 1,000Ω per volt meter were replaced by the 5MΩ input of an oscilloscope, it should be connected nearer the load. The error in the ammeter reading would then be greatly reduced. This line of thought can be applied throughout much of the spectrum of instrument measurements.

Voltage Divider

If we had a voltage divider of series resistors of 20% tolerance and we wanted to know the voltage drops at the junctions with respect to ground, there are a number of ways in which those can be measured or calculated. First, let us measure the current in the divider line then, from the body of each resistor, read its resistance. By using Ohm's Law ($E=I \times R$), the voltage drop



ERRORS IN MEASUREMENT


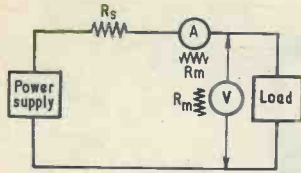


Fig. 1. Measuring the current and voltage applied to a load. On which side of the ammeter should the voltmeter be connected?

across each resistor can be determined. However, each voltage value may be in error by as much as 20%. This may or may not be a problem depending on the measurement goals. A second method of finding the voltage at each terminal of the divider would be to measure the actual voltage drop across each resistor and sum the drops. This technique accumulates the errors picked up at each voltage measurement. A third, and perhaps best, method would be to clip one lead of the voltmeter to ground and measure the voltage at each terminal. This method involves no calculations and it estimates the errors of the other two methods. This example may be over-simplified, yet it illustrates how both component tolerances and cumulative errors can be minimised. It is evident, then, that a measurement can be planned ahead of time to keep errors at a minimum.

Ideally, it is best to match the test instrument to the job. This is often impractical or too expensive, as we must make do with whatever test equipment we have. This approach will work fine as long as the error of the equipment being used is known and its effect on the circuit under measurement is understood. For example, let us take four 10kΩ resistors and apply 40 volts d.c. across this series string as illustrated in Fig. 2. The problem is to measure the voltage drop across the top resistor in the string. There will be 1mA flowing through the resistors.

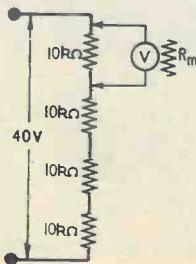If $\frac{1}{\text{ohms/volt}}$ = basic meter movement current on your voltmeter, and you know either the basic meter move-



ment current or its ohms per volt rating the other unknown can be found. Say that you know that your basic meter movement is 1mA. Then

$$\frac{1}{10^{-3}} = 1000 \text{ ohms/volt.}$$

Using the 50 volt range, the voltmeter resistance will be 50kΩ. When the meter is connected across the top 10kΩ resistor, the resistance changes from 10kΩ to

$$\frac{50k \times 10k}{50k + 10k} = 8.33k\Omega$$

The new current is 40/38.33k = 1.044mA. The voltage across the top resistor with the voltmeter connected is now

$$8.33 \times 1.044 = 8.7 \text{ volts}$$

and the percentage error is $\frac{10 \text{ Volts} - 8.7 \text{ Volts}}{10 \text{ Volts}} \times 100 = 13\%$ error.

If four 100Ω, 20%, resistors are connected as a series voltage divider, what would be the largest error in total resistance of the voltage divider? Each resistor may be as much as 20Ω in error. If all four resistors were off 20% in the same direction, the total error of the divider would not be 80% but still 20%. Here is how it works.

To find the total error in percentage, use the formula

$$\frac{\text{Marked Value} - \text{Measured Value}}{\text{Marked Value}} \times 100 = \text{Total percentage error in measured value.}$$

$$\frac{400 - (4 \times 80)}{400} \times 100 = \frac{8000}{400} = 20\%$$

This indicates that the total error is not the sum of the errors of the individual resistors.

Parallax

Equipment manufacturers have long been aware of parallax as a cause of error introduction in indicator readings. Parallax is the viewing angle error illustrated in Fig. 3. This viewing angle introduces either too high or too low an apparent reading. Meter manu-

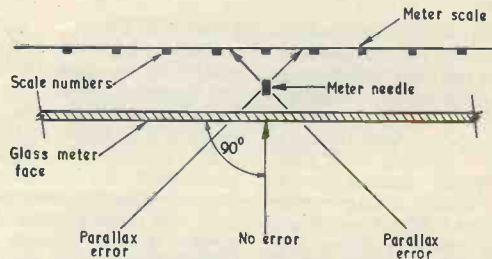


Fig. 3. Illustrating errors caused by parallax

A 13% error is very poor but is no reason to reach for the panic button. Herein is perhaps the message of the entire discussion on measurement errors. Once you know that this high error is present in the measurement, either mental or mathematical corrections can be taken. The point is that you can live with it. In this example the resistance of the voltmeter was only five times as large as the resistor developing the voltage of interest. Generally speaking, the voltmeter should, if possible, have at least ten times the resistance of the circuit across which it is connected.

Fig. 2. When a voltmeter is connected across part of a voltage divider, it may introduce a greater error than is generally realised

facturers have installed a mirror behind the needle to be used as a means of parallax correction. The needle is lined up in the mirror until the needle blade reflection disappears behind the needle, and this positions the operator perpendicular to the meter face. Also to overcome parallax errors, oscilloscope manufacturers are now imbedding the graticule in the c.r.t. face. Again, moving light indicators for galvanometers appear brightest when viewed perpendicular to the galvanometer face.

Let us look at some other oscilloscope errors that crop up. On the 20 volt per centimetre scale, the trace may be approximately 1 mm. thick (depending on the oscilloscope). This means that the oscilloscope trace is 2 volts thick. For a 50 volt per cm. scale, the trace would be 5 volts thick. Any attempt to measure values to better

than ± 5 volts on this scale becomes questionable, and this does not take into question the internal inaccuracies of the oscilloscope.

Trace thickness errors are also present when there is excessive noise on the signal. All trace thickness errors can be minimised by selecting a particular point of the thick beam (such as the uppermost part of the trace, for example) as the index level. Always use this same point, of course, to prevent the introduction of further reading errors.

How Many Readings?

There are times when all of us are sufficiently interested in the accuracy of a measurement to take a number of readings. How many readings are enough? If we took 10 readings of a value and then took 90 more, would the extra 90 readings be worth the time taken? The answer is no. From the statistics of probable error it can be shown that those extra 90 readings would only be twice as valuable as the original 10 readings. Time and therefore money can be saved by a working understanding of this fact alone.

Mechanical errors or calibration errors build up as the weeks wear on. Continued use of equipment often prevents us from noticing day-to-day slips in calibration or adjustment. There are errors that crop up in almost all types of instruments. Frequency errors occur when we attempt to use test gear above or below its frequency limits. There is a certain amount of estimat-

ing error always present when we have to read between the lines on any scale. We always live with errors introduced by temperature, with hour-to-hour changes during our data recording. When a reading is made more than once, there may repeatedly be error. This is the frictional error present where mechanisms are involved in measurement. Errors introduced due to signal dynamics are more involved. The effects of noise riding on a signal waveform (already mentioned) or of one wanted frequency and one unwanted frequency superimposed on each other all tend to give false or incorrect readings. These types of error strongly point to the need for every individual who has occasion to use test gear to know its limits and know its capabilities. For each of these measurement errors, it is up to the individual to cast out unimportant readings, decisions being based on experience or a past history of readings. In all cases the cast-outs are dropped on the basis of the things being measured and the overall goal of the measurements.

Human Factor

If all readings could be made by computers, much of the human factor of error could be eliminated. There has been a great deal done to improve readout instruments as these represent a weak link in the man-machine relationship. Often there is compromise between cost of equipment and its readability. It is known that certain panel layouts cause an increase in operator

error while others have a tendency to minimise these errors. Once the operator is aware of the problems that do exist, he is more tolerant of the shortcomings of the equipment. Included in the list of man-machine readout error causes are parallax (already mentioned), distance from readout to man, brilliance of indicator lamps, unwise use of colour, and other items too numerous for mention here. Often some emotional problem may upset us to the point that we misinterpret readings upon returning to the shop. Not too much can be said, however, in the area of errors arising out of emotional stress. We can only caution against them and watch for their influence on some measurement.

Another point is that the general professional appearance of an instrument may cause the operator to put more faith in its accuracy than the instrument warrants. Some instrument manufacturers are now including switches or push-buttons that allow selection of an exact value of frequency, voltage, etc., rather than continuously variable controls.

To sum up, errors will always be present in every measurement. We should always decide on two things. First, we should know how large the errors are, and second, we should determine if the errors are sufficiently significant to affect the reading materially. Today's instruments have forced a change in the outlook of 20 years ago, as is typified by currently available precision instruments which are low in error and high in readability.

HEATHKIT MODEL SB-300 S.S.B. RECEIVER

The Heathkit Model SB-300 s.s.b. receiver, shown here, is capable of receiving s.s.b., a.m. and c.w. signals on all amateur bands from 3.5 to 30 Mc/s. The pre-assembled and pre-aligned linear master oscillator and crystal-controlled heterodyne oscillators ensure highly accurate and stable operation, the use of circuit boards providing a clean chassis layout. A separate crystal filter may be obtained and is switch-selected from the front panel for each of the modes of operation to provide optimum selectivity. In the absence of the optional filters, a.m. stations are received using the exalted carrier method and c.w. may be received in either s.s.b. position.

Other features of this receiver are special aerial and power connections for v.h.f. converters, a 100 kc/s crystal calibrator, provision for transceiver operation with a compatible transmitter, and a smooth, virtually backlash free, dial tuning mechanism. The transformer-operated, silicon diode power supply is a long-life, low-heat power source. The SB-300 s.s.b. receiver is available at £133.14.0., in kit form, carriage paid in U.K.



Experiences of an




Early Amateur

The Concluding Article in this Series by C. H. Gardner

IN THESE ARTICLES AN ATTEMPT HAS BEEN MADE to give an impression of the atmosphere surrounding the activities of an enthusiastic amateur of the early days. Little has been said so far about transmitting activities because, although many of us operated our own transmitters, a great deal of our operations were confined to short distance transmissions of speech and gramophone records. The gramophone pick-up had not yet arrived, and the usual method of transmitting these records was by placing a microphone close to the trumpet of the gramophone. Some of these early transmissions must have been borderline cases for the P.M.G.'s licence conditions. One particular individual came on the air most Sunday afternoons and opened proceedings by calling up a long list of friends and relatives by name: Alf, Bert, Bill, Grandma, and others. His next announcement was "I am now going to put on some gramophone records for you." After half an hour's somewhat painful transmission of "music" he would sign off "Well, goodbye Grandma, Alf, Bert, Bill, (etc.). As we were restricted to working on a given frequency, performances of this nature interfered with the activities of many others in the vicinity. In general, though, most amateur transmitters co-operated enthusiastically in experimental work, this being of a rather more serious nature.

Erecting the Aerial

Severely limited by regulations as to the amount of power that we might use and restricted as to frequency, our attempts to improve range had to be largely confined to increasing efficiency, whereupon two major parts of the installation received attention: the aerial and the earth. As I mentioned in the first article in this series, one enthusiast even dug a trench down the middle of a rather lovely lawn and buried in it a 50 yard length of solid

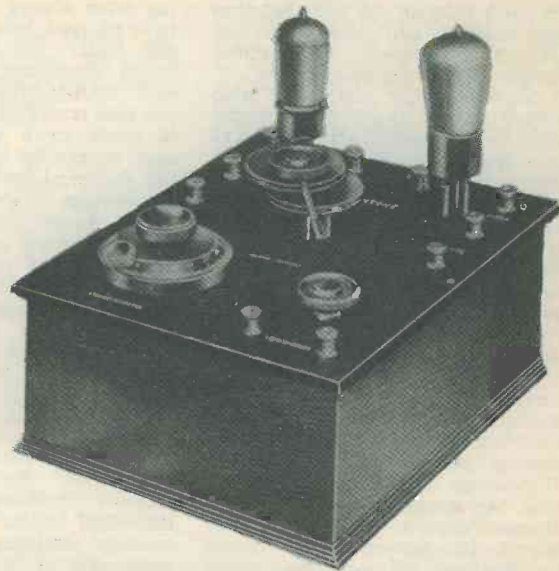

copper stick 1 in wide by $\frac{1}{2}$ in thick. This ran directly under his aerial. I must report that his results were so good that the Post Office sent an inspector, as they could not believe that he was restricting his power to the limit imposed. But the aerial problem was mainly concerned with height, and this brought forward the mast problem, with its attendant difficulties of expense and erection. The first 30 feet was not too difficult, but a 50-foot mast was quite another thing.

After due consideration of the expense and erection questions, my first personal choice fell upon a latticework wooden mast which was well advertised at that time. This duly arrived in three sections complete with jointing pieces, which had to be fastened together by short wooden strips and wood screws. It seemed fairly obvious that the mast could not be assembled in a vertical position and would have to be put together whilst lying on the ground. How to haul it into a vertical position was quite another problem. This was finally "solved" by calling in a number of friends to hold or pull on the stays. The first attempt was quite abortive, so one helper climbed a high tree and provided an upward pull to the top end. This worked well up to a point, but difficulty was encountered in keeping the foot of the mast on the ground. After some deliberations, an elderly and weighty relative finally agreed to sit astride the foot until the mast had become sufficiently vertical to enable this to be placed in position. All went well until a certain angle had been reached (a somewhat critical angle as we discovered) whereupon the foot of the mast, complete with elderly relative, suddenly rose twelve feet from the ground. With encouraging cries of "Ride him, cowboy" the writhing and snaking mast was gently and safely lowered once again to the ground.

The mast was eventually hoisted and the worst

twists and bends removed by adjustment of the guys but, alas, some structural damage must have occurred. A few months later the whole contraption blew down and was reduced to firewood in a gale, whereupon the cost and labour had to be written off as experience gained. It was finally replaced by a 40 foot steel mast erected by the manufacturers. This was still standing some years later when I left the district.

A Series of Broadcasts

In those days any real enthusiast with a few years of wireless experience behind him was labelled an "expert" and was often invited to talk to local budding radio societies and the like. Quite a proportion of B.B.C. listeners had a technical interest in their equipment and it thus came about that I was invited, over the years 1925 to 1927, to give a number of talks from the B.B.C. Birmingham Station on technical matters at the large fee of one guinea per half-hour's talk. The fee may not have been very attractive but there was the advantage that the talks enabled me to participate (without fee) in the "Children's Corner" and (again without fee) in the Studio Christmas parties, and also to make very many good friends amongst the grand people who appeared on both the technical and studio sides. The whole experience was thoroughly enjoyable and one which I shall never forget.

During these talks I dropped one real clanger. The Station Director, the late Mr. Percy Edgar, insisted upon one of the talks being concerned with the simple crystal receiver, since so many of these were still in use. The talk was not intended to tell the listener how the receiver worked or how to make it, but to tell him how to maintain it and get the best results from it. Crystal receivers have distinct limitations in this direction, and it may be remembered that the crystal detector of that period consisted of a copper cats whisker which had to be adjusted to make contact with a sensitive point of the crystal in use. In the course of time the cat's whisker point became oxidised, and this could cause a serious falling off in the sensitivity of the receiver. I felt therefore that it would be useful to suggest that clipping off the point of the cat's whisker in order to provide a fresh end might often improve results. Alas, part of my information was not up to date. I had not been aware of a considerable sale in the district of a number of expensive cat's whiskers with platinum tips which, as a result of my broadcast, were promptly snipped off.

Studio matters were not quite so formal as they are today. The engineer in control was able to view proceedings through a small glass window, through which he passed sign language "comments". These were apt at times to be a trial of one's self-control, because the engineer in question and myself both happened to have a similar sense of humour. It will take me a long time to forget the silent panic and activities of studio officials as they endeavoured to capture the station cat who had somehow strayed into the studio, and who had decided to accompany

a somewhat large and pompous tenor in his broadcast.

A "Portable" Receiver

Another series of talks, on "Reality in Broadcast Reception", was illustrated by demonstrations with gramophone records and a large bass drum. These were, perhaps, not too kind to makers of equipment whose normal range of reproduction was limited to the *very* middle frequencies but the only actual complaint came for an entirely different reason, from the maker of a "portable" receiver. This receiver, contained in a heavy wooden case and measuring approximately 2ft by 1ft by 1ft 6in, also required the use of another large wooden case holding a six volt accumulator and a hefty high tension battery. The illustrated advertisements showed the receiver being carried but omitted to show the battery case or loudspeaker.

In one of the talks in my series I dealt with the possibility of the future production of truly portable sets, and I warned listeners about illustrations showing portable receivers being carried but which omitted to show the elephant following behind to carry the ancillary equipment. As a result I was asked to attend an interview between the Station Director and the manufacturer, who claimed that I had undoubtedly described and criticised his portable receiver with consequent damage to his sales. At the interview I could not refrain from asking him if, as he said, my description was accurate, why he did *not* show the elephant carrying the ancillary equipment. It transpired that he felt that he was entitled to have a half-hour free of charge to broadcast an advertisement of his equipment. Needless to say, he did not get this.

In Conclusion

I mentioned, at the start of this article, that this series represents an attempt to give an impression of the atmosphere surrounding the activities of the early amateurs. In the space available I have only been able to give a few examples of this atmosphere, but it is hoped that these may have provided at least an impression of those early days.

At the beginning the attraction was purely technical. Later, many recruits appeared by reason of the fact that only by home construction could receiving equipment be obtained. In a still later phase, enthusiasts found that cheaper and, in some cases, better equipment could be constructed than was available from manufacturing sources. This situation fairly soon became reversed (some hi-fi enthusiasts may not entirely agree with this) and radio amateurs adopted the hobby either because they desired to undertake serious experimental work in communications or because of their love of constructional work.

Today, extensive research and experimental work by highly qualified graduates in the laboratories of manufacturers and universities has altered the picture. Television, u.h.f., long distance communications and hi-fi reproduction still provide plenty of scope for the enthusiast, but they require

a greater depth of pocket than was necessary for the early amateur. Nevertheless, the fascination of building one's own equipment, whether for special purposes or for the reception of broadcast sound or vision, will remain for a long time to come.

To the younger generation I can only say that

time spent on this work will be far from wasted, and that practical experience of this nature is very valuable. The radio and electronics industries require all the enthusiastic recruits they can obtain, and the well-being and future prosperity of our nation may well lie in their hands.

THE NEW DUAL-STANDARD TV SETS

By Gordon J. King, Assoc. Brit. I.R.E., M.T.S., M.I.P.R.E.

PART 8

This article, the eighth in our series on 405-625 line receivers, is devoted to the operation of the locked oscillator discriminator both on a.m. and f.m. A full description is given of the functioning of the discriminator with the frequency modulated intercarrier signal

LAST MONTH WE INVESTIGATED THE SOUND channel of a dual-standard set in which is used a ratio detector for the 625 f.m. sound and an ordinary diode for the 405 a.m. sound. We also looked briefly at a circuit in which a type EH90 heptode valve is employed as the f.m. detector on 625 lines and as an a.f. amplifier on 405 lines, a diode being used in the latter case as the detector.

This circuit was given in Fig. 25 of last month's article, to which reference should preferably be made now. One feature of this circuit is that only a single sound amplifier stage is used, as against the two stages in the circuit of Fig. 24 (also published last month). It will be recalled that the required sound channel gain is determined (a) by the sound take-off point in the vision i.f. channel on 405 lines and (b) by the intercarrier take-off point on 625 lines. Greater gain of the sound channel is required when (a) is from the output of the tuner direct and (b) is from the vision detector, while less gain is required when (a) is after the first vision i.f. stage and (b) is from the video amplifier output.

V₆ in Fig. 25 is the sound amplifier which receives either 38.15 Mc/s a.m. signals or 6 Mc/s f.m. signals. This amplifier is responsive to signals at either of these frequencies, as was explained last month. On 405 lines, transformer T₄ is operative, and it feeds the a.m. detector GR₂. The audio from this detector is coupled to the interference limiter diode GR₃ and its associated circuit through C₇₁.

The "limited" audio is redeveloped across R₆₃, from whence it is coupled to grid 1 of the heptode V₇, via C₇₃ and the low impedance (to audio) of the secondary of T₆. Note that, on "405 lines", SW₂₋₁ simply couples the top (dead to signal) end of the primary of T₄ to chassis via C₇₄. On "625 lines" it short-circuits the a.m. audio coupling circuit and, as we shall see later, brings the secondary of T₆ into action, so that V₇ can work as an f.m. detector instead of as an a.f. amplifier only.

Heptode as A.F. Amplifier

On the a.m. service, therefore, the audio is fed to grid 1 of V₇, and this valve operates as a reasonably conventional a.f. amplifier in spite of its multiple grids. The audio is developed across the anode load R₆₈, and is coupled to the volume control P₆, from whence the required level is tapped off and fed to the control grid of the output pentode in the ordinary way. Points to note here are firstly, that no a.f. triode is used, and that the triode section of V₈ is employed in another part of the circuit. This implies that the audio from the heptode is at a level similar to that which would be obtained from the conventional a.f. triode. The second point is that the volume control is interposed *after* the a.f. amplifier and not before it as is conventional when a triode-pentode valve is used.

On the f.m. service the heptode is arranged to serve not only as a detector but also, in effect, as an a.f. amplifier so that, on f.m. as well as on a.m., the audio at the anode is of a suitable level to drive an output pentode (via the volume control) without additional a.f. amplification. Switching is, therefore, eliminated subsequent to the heptode.

Switching is required at the front of the heptode, however, to change its action from that of a pure a.f. amplifier to that of an f.m. detector/amplifier, and we shall now consider this latter function of the stage.

Heptode as F.M. Detector

Fig. 26 shows the heptode arranged in the rôle of f.m. detector/amplifier, as when SW₂₋₁ of Fig. 25 is in the "625" position. The two electrodes fundamental to the operation of the valve as an f.m. detector are grids 1 and 3. These two grids can, in fact, be considered as control grids. That is, anode current is influenced by a potential change on either grid.

However, the valve is arranged so that anode

current flows only when both grids are biased positively with respect to cathode. If grid 1, for instance, is biased positively and grid 3 is biased negatively, then there is no anode current. Similarly, anode current is zero in the converse sense; that is, when grid 3 is biased positively and grid 1 biased negatively. This implies that the electrons from the cathode to the anode are blocked by either grid being negative. It needs both grids to be positive before the flow is restored.

Short Grid Base

Moreover, the valve possesses a short grid base at each grid. Let it be assumed that grid 3 is biased positively, then the excursion of signal at grid 1 is limited in terms of anode current. It requires only a small change in grid voltage to give an anode current swing from cut-off to saturation, which describes the term "short grid base".

The same characteristic is exhibited with grid 1 biased positively and the signal applied to grid 3. The valve has a large slope or gm.

Thus, whenever a signal which exceeds the grid base is applied to either grid (assuming that the one without a signal is positively biased), the resultant signal at the anode is limited on its positive half-cycles by anode current cut-off and on its negative half-cycles by anode current saturation. If the grid signal is a sine wave, then both the positive and negative peaks are clipped by the action of the valve and the signal at the anode has some of the characteristics of a square wave.

In Fig. 26 it will be seen that the 6 Mc/s f.m. intercarrier signal is applied to grid 1 via the coupling transformer T_1 . This transformer is tuned to the nominal 6 Mc/s "carrier". The amplitude of the intercarrier signal at grid 1 is such that it easily exceeds the grid base of the valve, meaning that in the event of grid 3 being positive, clipped pulses will appear at the anode, as has been described.

For the sake of simplicity of description, let it be supposed that the applied intercarrier signal is unmodulated. That is, it is a pure sine wave. The clipped or square wave pulses thus occurring at the anode simply charge the anode capacitor C_1 and a steady d.c. "signal-less" voltage is developed across it.

Even if the intercarrier signal were modulated under the existing conditions, there would still be no audio output at the anode, since the clipped pulses would simply change in frequency. More has to happen if the circuit is to work as an f.m. detector.

Grid 3 in Action

This is where grid 3 comes into action. Fig. 26 shows that this grid is connected to a tuned circuit L_1, C_2 . This circuit is also tuned accurately to 6 Mc/s and, because of the "space charge" coupling between grid 1 and grid 3, L_1, C_2 is also caused to oscillate at 6 Mc/s.

The situation due to the application of an unmodulated intercarrier signal at grid 1 is now that

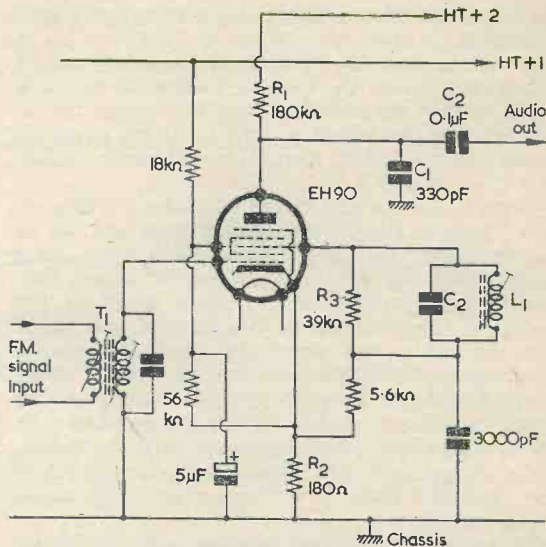


Fig. 26. Circuit of the heptode locked oscillator detector. This is fully described in the text

both grid 1 and grid 3 are in receipt of signal. The effective signal at grid 3 also exceeds the grid base so, if it were possible to "kill" the signal at grid 1 and bias that grid positively, clipped pulses would again occur at the anode, across C_1 .

Of course, signal at grid 3 cannot be present without the application of signal at grid 1, since the signal at grid 3 is caused by coupling in the electron

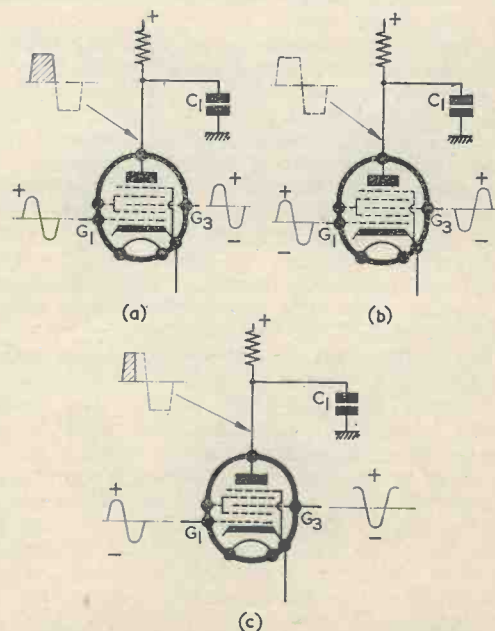


Fig. 27. The pulse width across the integrating capacitor C_1 is governed by the relative phase of the signals at grid 1 and grid 3 of the heptode valve

stream of the valve inciting L_1 , C_2 into sympathetic oscillation.

It will be understood that an oscillatory signal will appear across L_1 , C_2 only when that circuit is tuned, within its so-called "pull-in" range, to the frequency of the signal at grid 1. If the circuit is considerably detuned, then there will be no oscillatory effect at grid 3.

Now, if the rise and fall of oscillatory voltage at grid 1 were in exact phase with the rise and fall of the oscillatory voltage at grid 3 (both grids going positive and negative together—i.e. in phase), full-width squared pulses would again occur at the anode, as happened before when grid 1 had signal and the other was positively biased. Actually, assuming that the anode current is cut off completely as soon as the grids go from positive to zero signal and below (negative), only the positive half-cycles of signal would cause anode current response, as shown in Fig. 27 (a). When both grids fall below zero potential towards negative, then there is no anode output.

If one grid were to go negative while the other went positive, such as would occur if the signals on grids 1 and 3 were 180° out of phase with each other, there would be no anode output over the whole cycle, since one grid would always be at a negative potential. (Fig. 27 (b).)

If the signals were 90° out of phase with each other, as shown diagrammatically in Fig. 27 (c), both grids would be positive together only over a quarter of a cycle, and a half-width pulse of current would occur at the anode, as compared with the full-width pulse at (a). The active current pulses are shown shaded at both (a) and (c), with the dotted lines signifying the full cycle.

Actually, the space-charge or electron coupling within the valve gives rise to condition (c). That is, the oscillatory signal at grid 3 is 90° out of phase with the applied signal at grid 1. This is a natural characteristic of this mode of coupling between two tuned circuits resonated at the same frequency.

In effect, then, we get a "locked" oscillatory condition relative to the tuned circuit on grid 3, for which reason the circuit is often called the "locked oscillator f.m. detector or discriminator". The "oscillator" frequency "locks" to the frequency of the applied signal—but only over a limited range, called the "pull-in" or "deviation" range.

Thus, as the result of an unmodulated intercarrier signal at grid 1, there is an anode current consisting of a series of equal-width pulses. The anode current is constant and establishes itself at an average value, depending upon the exact width of the pulses in the chain. C_1 in Fig. 26 charges, as has been described, due to the anode current in the load resistor R_1 giving a voltage drop of constant value. It can be said that C_1 acts as an integrating capacitor, which is really what it is, since it adds or "integrates" the voltage pulses appearing across the load resistor.

Conditions of Modulation

We must now consider the action of the circuit

when the intercarrier signal applied to grid 1 is frequency modulated.

Let us suppose that the modulation causes the intercarrier signal to go *above* its nominal value of 6 Mc/s. Here we get the effect of a phase change between the two tuned circuits which causes the condition illustrated at Fig. 27 (c) going more towards that at (b). The voltage pulses across C_1 thus become narrower, depending upon the extent of the frequency deviation.

When the modulation causes the intercarrier signal to go *below* its nominal 6 Mc/s value, the effective phase change makes the nominal condition illustrated at Fig. 27 (c) go more towards that at (a). This, then, makes the voltage pulses across C_1 wider, again depending upon the extent of the frequency deviation.

It should be noted that the amplitude of the voltage pulses (resulting from the anode current pulses) remains the same from one deviation extreme to the other. The fundamental action of the circuit is that the pulses vary in width at a rate governed by the deviation frequency, while the extent of their width variation is governed by the "depth of modulation" (called "frequency deviation" f.m.-wise) of the intercarrier signal.

Since the voltage amplitude across C_1 is a function of the width of the pulses (i.e. a chain of narrow pulses will integrate to give a lower capacitor charge—or voltage—than a chain of wider pulses), it follows that the voltage across the capacitor will, in fact, vary in amplitude in sympathy with the modulation frequency.

Thus, produced across the capacitor is an audio signal corresponding in overall amplitude to the extent of frequency deviation of the inter-carrier signal and in frequency to the rate at which the pulses are varied in width.

This audio is fed through C_2 to the output pentode since, as we have already seen, its amplitude is large enough to drive such a valve without further voltage amplification. C_1 also serves as a de-emphasis component, which is a requirement of all f.m. receiving circuits where pre-emphasis is applied at the transmitter.

To provide the necessary high amplitude audio at the anode, the load R_1 is sometimes fed from the boosted h.t. line.

Amplitude Limiting

The circuit also provides automatic amplitude limiting, and in some sets using the circuit there may not be an amplitude limiter in the sound channel. Amplitude limiting occurs in three ways. One, owing to the "gating" action of the valve in terms of anode current which renders the detector somewhat insensitive to amplitude modulation. Two, at signal levels where the signal *amplitude* at the first grid exceeds the amplitude of the oscillator signal at the third grid there is a flow of grid current, and the resulting grid-to-cathode "diode" action of the valve tends to suppress amplitude disturbances in the normal "limiting" manner, without affecting the process of f.m. detection. Three, any a.m. on the

rectified voltage is also fed, via R_5 and VR_3 , to C_2 , which commences to charge at a slow rate. When the potential across C_2 reaches a sufficiently high level, Ne_1 strikes and illuminates the light dependent resistor. It should be noted that the time taken for the neon to strike is controlled by the values presented to the circuit by C_2 , VR_4 , R_4 , VR_3 and R_5 .

As soon as Ne_1 strikes, the l.d.r. offers a reduced resistance, thereby causing the collector current of the transistor to increase. The relay energises, and its contacts $A1$, $A2$ and $A3$ change over. Contacts $A2$ connect the fully-charged capacitor C_1 to the circuit offered by R_2 , VR_1 , VR_2 and R_3 . The values here are such that neon Ne_2 strikes and also illuminates the l.d.r. At the same time, contacts $A1$ disconnect the positive plate of C_2 from VR_3 and connect it to R_6 . C_2 discharges quickly into R_6 and Ne_1 becomes extinguished.

The relay still remains energised, however, because the l.d.r. is now illuminated by Ne_2 , the latter receiving its voltage from C_1 . After a period, C_1 discharges sufficiently to cause neon Ne_2 to extinguish. The l.d.r. now assumes its previous high resistance, and the relay de-energises. It should be noted that the time taken for Ne_2 to extinguish is controlled by the values presented to the circuit by C_1 , R_3 , VR_2 , VR_1 and R_2 .

When the relay de-energises, contacts $A1$, $A2$ and $A3$ take up their previous positions. Contacts $A2$ reconnect C_1 to the rectified voltage from MR_1 , whereupon it charges quickly once more. Similarly, contacts $A1$ connect C_2 to the same rectified voltage, whereupon this second capacitor commences to

charge at a rate dependent upon the values of the resistors in its immediate circuit. Thus, another cycle has commenced.

Summing up the operation of the circuit, it will be seen that the length of time during which the relay remains de-energised is controlled by the values presented to the circuit by C_2 , VR_4 , R_4 , VR_3 and R_5 . Similarly, the length of time during which the relay is energised is controlled by the values presented to the circuit by C_1 , R_3 , VR_2 , VR_1 and R_2 .

The relay has a third set of contacts, $A3$. These are used to control the external circuit.

Components

Components values in part of the circuit are experimental, but the following notes will help so far as their selection is concerned.

The fixed resistors in series with the variable resistors, i.e. R_2 , R_3 , R_4 and R_5 , could have a value of $20k\Omega$. R_3 and R_4 could be omitted if desired, as they merely limit the lowest resistance inserted by the combinations $R_3 VR_2$ and $R_4 VR_4$. Their omission reduces, however, the useful track range of the variable resistors. R_2 is necessary, since it prevents a direct connection between the fully-charged C_1 and neon Ne_2 . It is desirable to retain R_5 since it limits the initial charging current which can be passed by VR_3 when contacts $A1$ move to the de-energised position. The circuit could also be made to function with the combinations $R_3 VR_2$ and $R_4 VR_4$ completely omitted, although the range of control would then be reduced. Suitable values of VR_1 , VR_2 , VR_3 and VR_4 are between 1 and $10M\Omega$.

The capacitors C_2 and C_3 may

have values of the order of $200\mu F$ at 300V wkg.

By suitable choice of components it should be possible to obtain timing periods for both the "on" and "off" periods, which range from several seconds to greater than 5 minutes.

The two neons are inexpensive wire-ended types. They are mounted in very close proximity to the sensitive area of the l.d.r., the three components being housed in a light-proof case.

As with the resistors previously discussed, the value of R_7 is also experimental, in that it controls the transistor collector current and, hence, the relay operating current. The l.d.r. is an ORP12 and it would be preferable not to exceed its $50^\circ C$ dissipation rating of 100mW. This requirement will be met if R_7 has a value in excess of some 680Ω . The writer obtained satisfactory relay operation with values much higher than this.*

The transistor should be capable of passing sufficient current to energise the relay. An OC72 could be employed here with a relay capable of energising at some 10 to 20mA. When an OC72 is used, relay coil resistance should be 500Ω or higher.

The low voltage winding feeding MR_2 consists of two 6.3 volt windings in series. The value of R_9 is such that the rectified voltage across C_3 does not rise above the limiting collector potential for an OC72 of 16 volts when the relay is de-energised.

* More reliable operation of the circuit over long periods may be achieved by connecting a resistor between base and emitter of the transistor. The resistor should have as low a value as possible, commensurate with correct circuit functioning.
—EDITOR.



Valve Voltmeter with both RMS and Peak to Peak Scales

The PACO V.70 Valve Voltmeter is a versatile and rugged instrument that is a "must" in the workshop, school or electronics laboratory. Its balanced valve bridge circuit assures maximum sensitivity and stability for all measurements.

This instrument, which has 7 d.c. ranges from 0-1,500 volts and 7 a.c. ranges from 0-1,500 volts r.m.s. and 0-4,000 volts peak to peak plus an ohmmeter range of 0-1,000 Megohms and decibel range of -6dB to +66dB, comes complete with detachable 3-way probe to permit rapid, accurate tests on all types of equipment. Also available for use with the V.70 are the Model AV.1 High Frequency crystal probe and Model AV.2 High Voltage probe permitting direct reading of high voltages up to 60kW.

The PACO V.70 is priced at £22 12s., or may be purchased in kit form at £20 8s.

500 kc/s Crystal Frequency Marker

Wallace Studley



In this article the author describes an effective and simple transistor operated frequency marker complete with an audio modulator stage which should prove of interest to the s.w.l. and beginner alike

THE USEFULNESS OF A SIGNAL GENERATOR FOR receiver alignment and calibration is limited by its accuracy, and the simpler types often used by experimenters can rarely be relied upon when precise work needs to be done. Short wave listeners in particular are well aware of this and frequently make use of crystal controlled oscillators which confer a very high degree of accuracy indeed.

Components List (Fig. 1)

Resistors

(All resistors $\frac{1}{8}$ watt 10%)

- R₁ 15k Ω
- R₂ 3.3k Ω
- R₃ 1.5k Ω
- R₄ 1.2k Ω

Capacitors

- C₁ 100 μ F electrolytic 9V wkg.
- C₂ 3,000pF ceramic or paper
- C₃ 0.01 μ F ceramic or paper
- C₄ 100pF ceramic or silver mica

Transistor

TR₁ OC44 (or OC45—see text)

Transformer

T₁ I.F. transformer type P50/3CC (Weymouth)

Crystal

500 kc/s fundamental, type 10X (Henry's Radio Ltd.)

Miscellaneous

- s.p.s.t. on-off switch
- 6 volt battery
- Coaxial output socket
- Tagboard, case, etc.

In amateur circles crystal frequency markers are well-known, and they enable the user to check a transmission or calibrate a receiver scale very accurately.

A "marker" is really nothing more than a radio frequency generating device which operates at a single set frequency determined by the crystal it contains. By taking advantage of the harmonic content of a crystal marker signal, signals may be picked up at odd and even multiples of the funda-

mental frequency, these becoming progressively weaker as harmonic order increases. For example, if the crystal is a 1 kc/s type, this frequency, plus signals at 2 kc/s, 3 kc/s and so on, may be tuned in on a suitably coupled receiver. If the receiver is sensitive, harmonics may be heard up to around 30 Mc/s, and this range is usually adequate for s.w.l. requirements.

Marker points spaced at 1 kc/s intervals are hardly adequate though and, because of this, a 100 kc/s crystal is frequently preferred. On the 80 metre band, a 100 kc/s crystal gives indications at 3.5, 3.6, 3.7 and 3.8 Mc/s. On the 40 metre

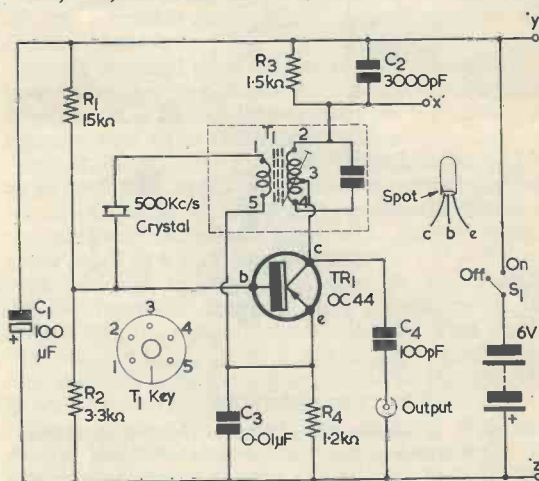


Fig. 1. The circuit of the crystal frequency marker. R₃ and C₂ can be omitted if the oscillator is not to be modulated, whereupon T₁ connects directly to the negative supply line

band there would be indications at 7.0 and 7.1 Mc/s, which offers an excellent state of affairs.

Many crystal markers employ valve circuits but benefits are conferred by transistorised versions, particularly since the physical size is reduced. Complete portability is also possible.

A Practical Circuit

The circuit of one model recently constructed by the writer is given in Fig. 1. Here TR₁ operates

in the common-emitter mode and oscillations are obtained at 500 kc/s. Due to T_1 and the crystal, energy is fed back from the collector to the base of TR_1 in the correct sense for oscillations to occur. An OC44 is specified for TR_1 , but an OC45 will probably work equally well.

Use of a fundamental frequency of 500 kc/s results in "markers" at 3.5 and 4 Mc/s on "80" and 7.0 and 7.5 Mc/s on "40" and this is often adequate for s.w.l. needs. The particular crystal frequency chosen also permits the use of a readily obtainable phase-shifting transformer. Care should be taken, if the circuit is duplicated, to ensure that a transformer of the type quoted is employed.

Resistors R_1 and R_2 form the base feed potentiometer which, in conjunction with R_4 , ensures temperature stability. Resistor R_3 and capacitor C_2 could be omitted if it is intended to employ the oscillator without modulation.

In use the marker circuit consumes some 2mA from a 6 volt d.c. supply. There is no warm-up time to worry about and the unit functions immediately it is switched on. Battery replacement is required only rarely.

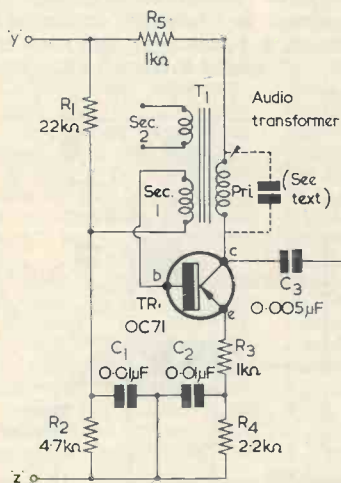


Fig. 2. A suitable a.f. oscillator. This is coupled into the circuit of Fig. 1 at points "x", "y" and "z"

Constructional and Setting-up

A small item of this kind can be easily built on a small piece of tagboard, and $2\frac{1}{2} \times 1\frac{1}{2}$ in is a suitable size for the present unit. The trial model used a 10X crystal obtained from Henry's Radio Ltd., and this, together with the transformer can, transistor body and switch, occupied the flat side of the board. The tags on the other side of the board retained the resistors and capacitors, etc. The complete assembly can be placed in a small plastic box and the only visible components need be the switch dolly and the output socket.

An oscilloscope is useful for setting up the unit. Alternatively a receiver of the communications type may be used, the presence and amplitude of oscillation being indicated with the aid of the b.f.o. and

S-meter. On the lower frequency bands coupling should be as loose as is possible compatible with adequate signal injection, and an insulated lead from the marker output socket twisted around another plugged into the receiver aerial socket is usually adequate. Alternatively, a 30pF concentric trimmer may be used. Very tight coupling might tend to damp transformer T_1 excessively.

It was found that the core setting of T_1 was moderately critical. The core should not need a great deal of adjustment, its final position being slightly out of the windings. In the test model the onset of oscillation was sudden as the core was rotated clockwise out of the windings. Oscillation was then apparent over two whole turns but further manipulation caused the non-oscillating condition to return.

Calibration of the marker can be made against MSF transmissions on either 2.5 or 5 Mc/s.

Signal Recognition

On the lower frequency bands it is easy to identify the marker harmonic signal but, as the receiver is tuned to higher frequency ranges, detection is not so simple because of harmonic tail-off and the

Components List (Fig. 2)

Resistors

(All resistors $\frac{1}{4}$ watt 10%)

R_1	22k Ω
R_2	4.7k Ω
R_3	1k Ω
R_4	2.2k Ω
R_5	1k Ω

Capacitors

C_1	0.01 μ F paper
C_2	0.01 μ F paper
C_3	0.005 μ F paper

Transistor

TR_1 OC71

Transformer

T_1 Class B driver transformer (see text)

fact that carriers are heard even when no aerial is connected. A signal due to the marker will of course fade out if S_1 is opened momentarily, but it is more helpful, for the purpose of identification, to add a modulator stage to make the signal audible. A simple circuit that may be tried is shown in Fig. 2 where TR_1 functions as a conventional a.f. feedback oscillator in conjunction with T_1 . The stability given by the bias components is excellent and the circuit is very easily set up.

The audio transformer, T_1 , may be a type used for Class B "driver" applications, such as the Weymouth LFD4. Transformers of this type have two separate low impedance windings and a ratio of about 4:1+1. One secondary winding is left disconnected. The windings used must be connected in the correct sense or the circuit

will not function. If no oscillations result when the unit is first switched on, reversal of the connections to the primary winding is usually sufficient to cure the trouble.

The frequency is controllable—within limits—in various ways, this being done either by altering the emitter or collector circuits. For example, a capacitor across T_1 primary winding lowers the operating frequency whilst a resistor of the order of $68k\Omega$ raises it. In the emitter circuit the frequency of operation is increased as R_4 is made larger and, although amplitude is adversely affected, a purer waveform results. The unbypassed resistor R_3 also contributes to waveform purity, due to the

TRADE NEWS . . .

The Sinclair "X-10" Integrated Amplifier

HAVING ESTABLISHED A NAME FOR THEMSELVES IN radio receiver design with the Micro-6 receiver, Sinclair Radionics Ltd., have now introduced a new type of transistor audio amplifier.

The Sinclair "X-10" is a high fidelity integrated power amplifier and pre-amp using 11 transistors and having a transformerless output of 10 watts for feeding into a 15Ω loudspeaker system. It requires only the addition of tone and volume controls plus a 12 to 15 volt d.c. power supply to make it a complete mono high fidelity assembly. Stereo is achieved by using two X-10 amplifiers, and ganged or separate controls. Input sensitivity is sufficient for crystal or magnetic pick-ups and the manual supplied with the "X-10" gives detailed instructions for connecting the controls and for using the amplifier in a wide variety of applications.

This radically new transistor amplifier (patents applied for) is claimed to be the first marketed anywhere in the world using the pulse width modulation principle (P.W.M.). This technique permits a considerable reduction in the power dissipation in the output transistors of an amplifier; and in the case of the Sinclair "X-10", the output efficiency is stated to be about 95% as compared with about 60% for conventional class B output stages. This immediately results in the following advantages:

(1) No heat sink is required for the output stage, and small high frequency transistors can be used in place of the conventional low frequency power transistors. Four transistors are used in the output stage of the Sinclair "X-10" and, as their cut-off frequencies are 5 Mc/s or more, the high frequency performance of the amplifier is exceptionally good and remains flat at high power levels.

a.c. feedback it introduces.

Adequate injection into the crystal controlled circuit results by completing the connections "x" of Figs. 1 and 2, but a high level audio signal can also be obtained—for Morse code practice perhaps—by extracting it from points "x" and "z". This means that points "x" and "z" may be used initially to check the circuit merely by connecting to them the leads from a pair of high-impedance phones. It should be noted however that, if this audio oscillator is used for Morse practice, it is impracticable to key the transistor supply voltage because the build-up time will not permit crispness. Usually it is convenient to key the output.

(2) The high efficiency of the Sinclair "X-10" means that less current is required from the power supply. Two ordinary lantern batteries costing 4s. each, for example, will power the amplifier for about three months in normal use. A mains power pack may also be used, and one is available from Sinclair at £2 14s.

(3) The absence of heat sinks and the use of small transistors makes the amplifier very light, compact and easy to fit.

(4) As none of the transistors in the Sinclair "X-10" has to dissipate excessive heat the reliability of the amplifier is excellent, and it should last indefinitely.

(5) It is stated that the use of P.W.M. assures a better transient response than is possible with other amplifiers and that it adds greatly to the quality of reproduction from the loudspeaker.

(6) Harmonic distortion is claimed to be so low as to be totally negligible and cross-over distortion, which can cause such marked unpleasant effects in conventional transistor amplifiers, simply cannot occur at all in a P.W.M. amplifier.

In addition to the use of P.W.M., the Sinclair "X-10" amplifier employs four transistors in the output stage in place of the usual two. This means that the amplifier, which is completely transformerless, requires no coupling capacitor to the speaker. It also halves the required supply voltage.

Sinclair Radionics Ltd. are making this new design available as a complete instrument, or separately in parts for the constructor to build and assemble for himself.

Principal Specifications of the Sinclair "X-10"

Number of transistors: 11.

Overall size: $6 \times 3 \times \frac{3}{4}$ in.

Input sensitivity: 1mV.

Total harmonic distortion: less than 0.1%.

Output power: 10 watts.

Frequency response: 5 c/s to 20 kc/s \pm 1dB.

Speaker impedance: 15Ω

Damping factor: greater than 100.

Quiescent consumption: 75mA

Supply voltage: 12 to 15 volts.

Price (post free): £5 19s. 6d., parts and instructions;

£6 19s. 6d. built and tested.

Mains power supply (for 1 or 2 amplifiers): £2 14s.

RADIO TOPICS . . .

by *Recorder*

WELL, HOW WOULD you LIKE to be painted gold all over?"

Any James Bond fan who, like myself, overhead this extraordinary question outside a cinema could at once assume, rightly, that the film being shown was "Goldfinger". I need hardly add that the Bond films represent, of course, a self-mocking send-up of all the spy stories ever written, and that they can offer quite a lot of fun if you're prepared to enter into the spirit of the thing.

Some of the minor points about these films which tickle my sense of humour are the delightful small electrical or electronic "devices" which the intrepid 007 employs in his war against the baddies of his world. Each gadget must be assembled by the prop-man with loving care, and nearly always incorporates a little battery clipped neatly into position and bearing a well known trade name such as "Ever Ready". This represents a touch of genius, because the familiar bright label links the everyday world of the shop battery counter to the fantasy scene being enacted on the screen.

Such an approach is to be expected from the electronically-minded makers of the Bond films. In "Goldfinger" a laser is used, very nearly, on the master-spy himself. Later, it is employed to burn out the doors of the U.S. gold repository at Fort Knox.

I had better cease on this subject now, however, because it is possible that some readers may look upon the Bond films with disfavour. To them, 007 is not a preferred number!

Hum on F.M.

A reader, R. G. Young of Peacehaven, Sussex, has sent us some interesting details of a possible cause of modulation hum in f.m. receivers.

The cause of the modulation hum is stated to be direct magnetic interaction between the mains transformer and the ratio discriminator coils. Mr. Young says that the hum, which has a rather high harmonic level, is liable to occur if the mains transformer is mounted close to the discriminator transformer and that it can be cleared by re-mounting the

transformer well away. Alternatively, our correspondent's "private cure" can be employed. This consists of fitting a hum-bucking coil around the discriminator transformer screening can and moving it around for minimum hum. The coil can have about 8 to 10 turns (in bad cases up to 20 turns may be needed) and is connected in series with one of the valve heaters. The turns of the hum-cancelling coil can be held in place by tying with cotton.

It seems feasible to me that a modulation hum effect of this type could occur if the dust core of the frequency-sensitive winding of the ratio discriminator transformer (e.g. the secondary in a conventional component having primary, secondary and tertiary windings) is acted upon by a strong magnetic field varying at 50 c/s. The incremental permeability of the core could then alter according to the strength and polarity of the field. Mr. Young hazards a guess that the field may have an effect on the performance of the diodes.

Micro-Soldering Irons

Light Soldering Developments Ltd., of 28 Sydenham Road, Croydon, Surrey, announce that their "Adamin" range of high performance micro-soldering instruments, which were introduced a few years ago, has just recently been re-styled and technically improved.

All "Adamin" instruments are now fitted with a completely new handle which is injection moulded in nylon type 66. This new handle has an attractive bright red colour, is extremely light (it weighs 5 grams) and comfortable to hold, and is stated to be so tough that it is absolutely unbreakable. Furthermore, it is unaffected by most chemicals and solvents, withstands considerable heat without softening and is self-extinguishing.

Modifications have been made to "Adamin" elements to improve performance and reliability, particularly in the case of the two mains voltage models in this range. One of these, the type CIOL is considered to be the smallest mains voltage instrument in the world.

"Adamin" copper bits are now

heavily chromium plated to prevent surface scaling and wetting of the sides by solder; preservation of the surface finish in service is an important factor in maintaining bit temperature.

The accompanying illustration shows an "Adamin" instrument with the new handle, and amply demonstrates its small size and ease of handling.

Thou Shalt Not . . .

Several readers have written in to tell me that my explanation of the "two equals one" calculation is not as accurate as I had fondly imagined it to be. I published the "proof" in the September and October issues, saying in the latter that it falls down on the third line because both sides are equal to zero.

Not so, declare my correspondents. The fallacy lies in going from the fourth to the fifth line, where both sides are divided by $(x-y)$. Since it is assumed that x is equal to y this is equivalent to dividing by zero whereupon, as one reader puts it, the fundamental rule that "thou shalt not divide by nought" is broken. It is after this particular step that the "proof" becomes nonsense.

I am indebted to the readers who have pointed this out, and so enabled me to get the matter straight.

My next trick, ladies and gentlemen, will be impossible . . .

Slightly Over-Run

I see that, elsewhere in this issue, Dick and Smithy are delving into the mysteries of transistorised u.h.f. television tuners. When I see new devices like this being accepted for everyday use, I sometimes wonder what would have been our reactions if they had suddenly been presented to us some 20 years or so ago. If at that time we had been shown a small unit having hardly any components, and certainly no valves, and had been told that it could amplify over the range of 470 to 854 Mc/s we would have raised, at the least, an unbelieving eyebrow. The added statement that only a 12 volt supply was needed would have finally brought forth our complete incredulity.

Looking back, though, we did some pretty incredible things with valves 20 years ago. Off duty, that is.

In that year of the war I was stationed in Italy, and I eventually managed to scrounge enough parts to knock up a short-wave receiver covering 5 to 18 Mc/s in order that we could pick up the B.B.C. Overseas broadcasts. Because I had come by a 6K8 frequency-changer (a great

prize) a superhet became feasible, and this used the line-up: 6K8, 6K7, 6Q7 and 6V6. I had also managed, by means of some rather weird and wonderful modifications to a component not intended for the job, to make up a mains auto-transformer which stepped the local 150 volt a.c. mains up to around 270 volts. There was, also, just sufficient room under the laminations to squeeze in a single 6.3 volt heater winding.

What was finally required was a half-wave h.t. rectifier. But this proved to be completely unobtainable, and I eventually decided to make do with a metal 6N7 Class-B double triode output valve having all grids and anodes strapped together to act as a single rectifier anode.


Believe it or not, but that shockingly maltreated 6N7 pressed on quite happily as a rectifier for at least 18 months. In common with the other valves, its heater was at chassis potential, whilst its cathode had a potential which lay anywhere between 200 to more than 300 volts positive of chassis according to the voltage provided by the highly unpredictable local mains. The cathode fed directly into the electrolytic reservoir capacitor and, as a precaution, I originally inserted a torch bulb in series to act as a fuse. The ripple current was sufficient to make this glow brightly when the mains voltage was high. But it burnt out so frequently that I put a short-circuit across it, and ran the circuit without a fuse.

At the end of the 18 month period I mentioned just now I was posted home, and I passed the set on to a friend, complete with its 6N7 with the mammoth performance and in full working order.

They certainly made valves tough in those days!

Ferroxcube Aerial Rods

In the September issue I referred

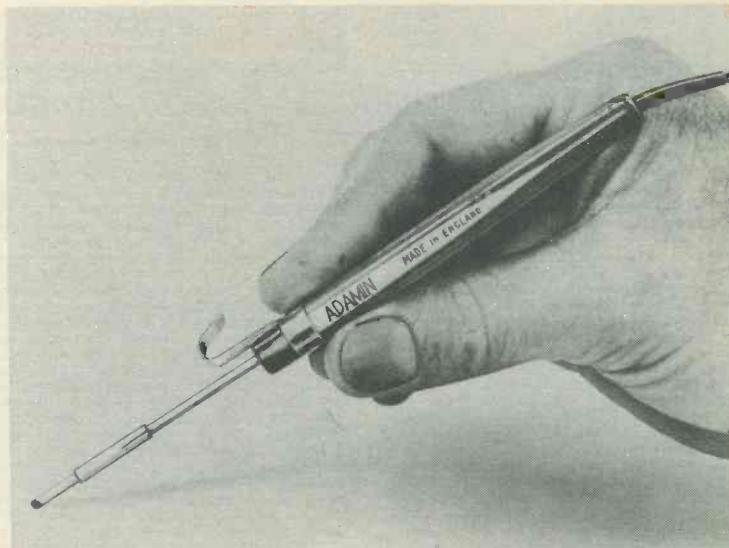

One of the micro-soldering instruments in the re-styled "Adamin" range manufactured by Light Soldering Developments

to my experiences in repairing the broken ferrite rod of a portable transistor receiver. Referring to an article in *Mullard Outlook*, I said that no adhesive requiring heat should be employed for joining the mating surfaces. I also said that the heat would impair the magnetic qualities of the rod.

I have since been informed by Mullard Ltd. that this is an incorrect reference to the effects of temperature on ferrite rods when using hot setting adhesives. Mullard pass on the further information:

"We feel that it should be made clear that ferrite properties are likely to be adversely affected by temperatures of 400°C or greater. As most hot setting adhesives do not require curing temperatures of anything greater than 120°C there will be no detrimental effects on the ferrite. If

rods exceed their Curie temperatures (greater than 130°C in the worst case, but for normal radio aerial material, greater than 250°C), the properties would return to normal upon cooling."

December Once More

And so we come to yet another December issue.

It has certainly been a lively year for us in the Editorial offices, and it looks as though next year is going to be even livelier. At the time of writing we have already started our planning for the earlier part of 1965, and I can assure you that there is plenty of really good stuff to come!

With which happy thought I must now add my sincere wish that you all have a really Happy and Merry Christmas.

See you in January!

MINIATURE TRANSISTOR AMPLIFIER FOR I.F. AND U.H.F. Applications

Introduced by Micro State Electronics Corporation, the new MTQ series of miniature transistor amplifiers provides many advantageous features. The series includes five models, designed for use as low noise i.f. and r.f. amplifiers covering all frequencies in the 30 Mc/s to 300 Mc/s range.

The features include: extra-small size; low noise figure; high gain; wide bandwidth; rugged construction and solid state reliability. Amplifiers are available also with built-in video detectors and a.g.c. circuitry.

The package size is a small 27mm x 19.1mm x 77.8mm (less connectors); r.f. connectors are Omni Spectra OSM; d.c. requirements: 20 volts at 35mA; the operating temperature range is from -50°C to +75°C.

For additional information contact Ad. Auriema Ltd., 125 Gunnersbury Lane, Acton, W.3, England.



International Radio Communications Exhibition

The 1964 International Communications Exhibition was again held this year at the Seymour Hall, W.1., and was opened by Mr. E. D. Whitehead, M.B.E., B.Sc., M.I.E.E., Director of Electrical Inspection at the Ministry of Aviation.

The writer, probably in common with many other enthusiasts, made a tour of the exhibition viewing the equipment on the various stands and, at the same time, meeting some old friends. Particularly of interest were those items of equipment that were new—at least as far as the writer was concerned.

The Radio Society of Great Britain stand, with its display of working and somewhat humorous models—including a much harassed treasurer and also a non-stop pedal cyclist complete with mobile radio equipment—was again complete this year with a fine array of home-constructed units. Those noted, amid many other fine examples, were a Communications Receiver prototype Mk. II by A. H. Shepherd, G3RKK; a Linear Amplifier by M. D. Mason, G6VX; a 1.8 and 144 Mc/s Transmitter by H. Rogers, G3NHR; a V.H.F. Multiband Receiver by P. J. Sterry, G3CBU and, last but not least, a 3-Band Crystal Mixer Transmitter by Members of the Basingstoke Amateur Radio Club. The writer was left with the distinct impression that items of home-constructed equipment improve year by year and that displayed in this exhibition in many instances measured up well with commercially produced units.

K. W. Electronics, Ltd., featured their well-known KW77 and KW707 Communications Receivers, the KW 500 Linear Amplifier and the KW One-Sixty Transmitter. The latter, as its name implies, has been specifically designed for the frequency range 1.78 to 2.1 Mc/s with a p.a. input of 10 watts (15 watts maximum) c.w. or phone. Break-in operation is permissible, the v.f.o. being keyed and a buffer between the v.f.o. and the p.a. assuring stable and "chirp-free" keying. The output impedance is 70–300Ω with pi output, the modulation is high level plate and screen, up to 100%. The transmitter is very compact (10 x 9 x 6in—panel 10 x 6in) and has a self-contained power supply. The valve line-up is EF80 oscillator, EF80 buffer, PL81 p.a., 6BR7 speech amplifier, 12AX7 audio amplifier and phase splitter, two 6BW6's modulator and an OA2 stabiliser. The controls are v.f.o. tune, p.a. tune, aerial coupling, off/phone/c.w. and net on/off. The KW2000C Transceiver was also in evidence and this is a complete unit providing transmission and reception of single sideband suppressed carrier, compatible amplitude modulation and continuous wave telegraphy on any four pre-selected channels in the range 1.6 to 30 Mc/s.

Daystrom Ltd, (Heathkit) presented a comprehensive display of their well-known excellent kits and showed many of them in completed form. The attractive appearance of their range has always impressed the writer and particular attention was paid (for personal reasons) to the Model MM-1U Multimeter and the R.F. Signal Generator Model RF-1U. The sensitivity of the former instrument is 20kΩ-per-volt d.c. and 5kΩ-per-volt a.c., and the function and range switches offer full-scale settings (a.c. and d.c.) of 0–1.5, 5, 15, 50, 150, 500 and 1,500 volts. Current ranges are 0–150μA, 15mA, 150mA, 500mA and 15A d.c. only. The resistance ranges are R x 1 (15kΩ centre scale), R x 100 (1,500Ω centre scale), and

R x 10kΩ (150,000Ω centre scale). This instrument will measure from 0.2Ω to 20MΩ. A large 4½in 50 micro-ampere meter, a dB range of –6 to +58dB, a polarity reversing switch and test leads are other features of the instrument. The R.F. Signal Generator provides a frequency coverage in 6 bands from 100 kc/s to 100 Mc/s on fundamentals and up to 200 Mc/s on calibrated harmonics. The dial has 6 large scales allowing precise frequency settings and a 2% accuracy is achieved through the entire coverage. Modulated or unmodulated r.f. output of at least 100 millivolts is available, this being controlled either by fixed step or by continuously variable output attenuators. A 400 c/s audio signal with 10 volts output is provided for audio tests. Many other test instruments, receivers, transmitters, audio equipment, etc., were also presented to make an enviable (at least to the writer) display.

The Hammarlund stand (K.W. Electronics Ltd) featured many of their world-famous receivers and transmitters. Those noted particularly were the dual-conversion HQ-145X 12 valve communications receiver covering the range 540 kc/s to 30 Mc/s. This receiver has an improved noise limiter; dual-conversion from 10 to 30 Mc/s, a directly calibrated electrical bandspread on the 80, 40, 20, 15 and 10 metre amateur bands; crystal filter with 6-position switch; adjustable slot filter with up to 60dB attenuation for elimination of adjacent channel interferences; S-Meter; temperature compensated b.f.o. for s.s.b. and c.w. reception and a high precision crystal controlled channel for any point within the entire frequency range. The triple-conversion HQ-170 was also in evidence and this receiver has so many excellent features that it is impossible to list them all here. Sufficient to say that it has a line-up of 17 valves, slot filter, separate vernier tuning, separate linear detector, tuned i.f. amplifier, selectable sideband, crystal calibrator, automatic noise limiter and a dial scale reset control. An optional extra is the telechron clock-timer, a combination clock and automatic timer fitted as an aid to meeting pre-arranged schedules.

Webbs Radio presented yet another very interesting display of the Eddystone receiver range. Of note here were two receivers of some interest, the first being the EC10 transistorised Communications Receiver. This has a frequency coverage of from 550 kc/s to 30 Mc/s in five bands and tuning is controlled by a gear drive having a reduction ratio of 110 to 1. The tuning scales have a length of 9in and are marked directly in frequency to an accuracy of within 1%. The transistor line-up for the following stages are all OC171's—r.f. amplifier, mixer, local oscillator, 1st i.f. amplifier, 2nd i.f. amplifier, b.f.o. and audio amplifier. The audio driver is an OC83, the push-pull audio output stage consisting of two OC83's. The a.g.c. attenuator diode is an OA70, and an OA90 acts as the detector and a.g.c. with an OAZ203 performing the function of a voltage stabiliser. The power supply is derived from six U2 type cells housed in a separate detachable compartment which is easily accessible from the rear of the cabinet. The 940, 830/2 and the EA12 Communications Receivers, among others, were also to be seen and inspected.

The Codar Radio Co., provided a range of equipment that was well worth inspection. A t.r.f. receiver having a coverage of from 10 to 2,000 metres was on view, this being a most useful design specifically offered to

the beginner or short wave listener. The CR66 Communications Receiver, the RQ10 "Q" Multiplier and the PR30 Pre-selector unit were to be seen. Of new interest here was the AT5 Miniature 12 watt Transmitter which, like the aforementioned equipments, was attractively styled. This transmitter operates on the 80 and 160 metre amateur bands and is designed for both mobile or fixed station operation. It is certainly miniature, being only some 8½ x 5 x 4in but it has a line-up of EF80, EF80, 6BW6, 12AX7 and 6BW6. A new modified Vackar type v.f.o. circuit, developed by Codar and providing extreme stability, is included in the design. A calibrated circular dial (1.8 to 2.0 Mc/s and 3.5 to 3.8 Mc/s) is fitted with a ball-bearing slow motion drive, free from backlash. A plug changeover for 6 or 12 volt heater supply is provided and this allows the heaters to be run from either a 6 volt transformer supply for fixed use or from a 12 volt battery supply for mobile operation. A matching stabilised power unit is available separately and a mobile 12V transistor power supply will be available shortly.

Electroniques (Felixstowe) Ltd., had many interesting items on show, including their range of coils, coilpicks, dials, complete a.m. and c.w. detector and a.g.c. units and i.f. transformers, etc. A brand new development on this stand was the combined pre-selector/converter fitted with a peak and notch i.f. filter. For the first time the functions of a converter and pre-amplifier have been combined and additionally, a "Q" multiplier and notch filter, of new design have also been incorporated. The unit is self-contained having its own regulated power supply. A 3-position push button unit selects either the pre-selector or the converter function and, when used as a converter, the other two buttons select either the peak or the notch functions. The i.f. output frequency is 1.620 Mc/s although an alternative output of 1.5 Mc/s can be supplied. An aerial tuning control, gain control and multiplier peak/notch control, plus the 6 waveband switch, are all contained on the front panel in addition, of course, to the main tuning control. Two models will be available (in date rotation from March onwards) these being the Model PC166HB (6 band spread amateur bands) and the PC166GC (6 band general coverage). Both models have a tunable i.f. whistle filter input circuit feeding into a high gain EF183 r.f. stage, this feeding an ECH81 combined mixer/oscillator.

The National Radio Co., presented a range of their latest designs among them being the NC-77X, NC-121, NC-140 and NC-90 communications receivers. Of note here however were two new designs, the NCX-5 All-Band-Transceiver and the HRO-500 receiver. The NCX-5 has been designed as an amateur station in one cabinet and covers the 10 to 80 metre bands. A separate power supply is required. The design incorporates a linear solid state v.f.o. and dial calibration is by means of a digital counter, the read-out being accurate to 1 kc on each band with additional counter calibration to 100 cycles. The transmit and receive selectivity is by means of a new 8-pole crystal lattice filter and filter bandwidth is 2.8 kc/s at 6dB with a 6–60dB shape factor of 1.7:1. Types of emission are s.s.b. (selectable upper or lower sideband) a.m. and c.w. The circuit contains 20 valves and 15 semiconductors. The National HRO500 Communications Receiver provides solid state circuitry and operates from 12V

d.c. batteries (current drain 200mA) or 115/230V a.c. 50-60 c/s sources. The receiver covers the entire v.l.f. and h.f. bands continuously from 5 kc/s to 30 Mc/s in 60 500 kc/s bands, the tuning rate, stability and dial calibration being 1 kc throughout. All facilities necessary for s.s.b., c.w., f.s.k. and a.m. reception are incorporated. The frequency is determined by a phase-locked crystal frequency synthesiser which eliminates multiple crystal oscillators for high frequency oscillator injection. All high frequency oscillator signals are synthesised from the output of a single 500 kc/s master crystal oscillator for maximum stability and the elimination of band-to-band recalibration. The line-up consists of 37 transistors and 20 semi-conductors.

Green and Davis Ltd., currently offered a 2 Metre Converter Mk. IV, this being a high sensitivity, low noise factor converter with internal mains supply. Frequency coverage is 144 to 146 Mc/s with i.f. outputs at 1.8-3.8, 4-6, 24-26 and 28-30 Mc/s with other frequencies available to order. The noise factor is better than 2.6dB. The size of the unit is 6 x 4 x 5in and the line-up is 6060 overtone oscillator/frequency multiplier, two 6CW4's cascode r.f. amplifiers and a 6CW4 mixer. Other items to be seen were a 70 cm Nuvistor Converter, the 2M1000 150 watt 2 Metre Transmitter having 70cm capabilities, the 2M15 20A (Falcon) 20 watt Mobile or Mains Transmitter for 144 Mc/s with 420 Mc/s facilities, the CTX2 18 watt Transmitter for 2 metres which may be also used as a driver for 70cm and the Green and Davis 500 watt Single Sideband Linear Amplifier PGLA1.

E. J. Philpott's Metalworks Ltd., presented a wide range of well designed modern styled metal cabinets finished in a selection of colours to suit most individual tastes. This firm specialises in producing metalwork to individual specifications and some examples of this were to be seen, together with cabinets having a two-tone colour scheme which was certainly most pleasing to the eye. The popular "S" line style of cabinet was predominantly evident.

Partridge Electronics Ltd., were showing their unique "Joystick" all-band aerial suitable for both receivers and transmitters. The "Joymast", specially produced for use with this aerial system, raises the "Joystick" to a height of some 31ft 6in when used as an aerial but the unit itself is designed primarily for mounting in a roof space or even within the "shack" itself. The "Joymatch" aerial tuning units were also to be

seen and these are of various types. Type 1 is a general purpose tuner whilst type 2 is specifically for use on the medium waveband with type 3 having a pi circuit and catering for the short wavebands. Type 6 is, in effect, a do-it-yourself tuner unit, having a tapped inductance with a shorting lead and two variable capacitors, these providing an individually chosen circuit within a few seconds.

Formica Ltd., provided a most interesting display of various copper-clad laminates showing the separate stages of production. Used extensively for printed circuit boards, especially with solid state devices, the static display showed two major methods of manufacture whilst a colour film ("Current Trends") was screened continuously showing in detail the production processes employed in the production of printed circuitry.

C & N (Electrical) Ltd., offered their Uniframe Modular Rack and Panel System based on a new approach to the construction and assembly principles. Consisting of strongly made vertical and horizontal members, capable of being easily and quickly bolted together to form the framework of a standard size instrument case, it may be extended to a height of 6ft and horizontally to any desired length in multiples of the original module. A basic kit of parts is available as a basic rack without side or back panels if desired and panels may be provided in a wide range of colours, being attached to the frame in relation to slide-on corner trims by alternative methods, thereby offering a choice of both style and colour in the completed assembly.

Ray Cross Electronic Co. Ltd., produced for inspection two communications receivers of great interest. The RCX505 is the first available British designed receiver to employ a linear balanced mixer system with no r.f. stage in order to give excellent protection against cross modulation. With conventional r.f. stages and non-linear mixers, trying to receive a weak signal some few kc/s adjacent to a powerful transmission often becomes impossible by virtue of the cross modulation that is apparent. Having no r.f. stage but with a linear balanced mixer provides excellent protection against this fault. The receiver features double conversion using 14 valves and 5 diodes and covers all the amateur bands from 10 to 160 metres in 9 bands. Switchable selectivity employs a Collins mechanical filter for s.s.b., crystal lattice filter for c.w., bandpass coupling for a.m. and a slot filter being tunable across the i.f. passband. The first oscillator is crystal controlled for

maximum stability. An internal 100 kc/s crystal calibrator; amplified a.g.c. with selection of fast, slow or off positions; product detector for s.s.b. reception and separate diode detector for a.m.; adjustable noise limiter; large illuminated 3 $\frac{1}{2}$ " "S" meter; a.f. filter for c.w.; an a.f. output of 2 watts and a precision geared tuning drive having no backlash and a 100-1 ratio are other features of this design. The dial provides an accuracy of frequency read-out, after standardising against the 100 kc/s calibrator, to the nearest kilocycle using the kilocycle counter facilities on the main tuning control. Due to the 1 kc calibration marks being $\frac{1}{2}$ in apart, frequency shifts of 250 c/s are easily read. The RCX-606, with direct digital frequency read-out, has identical specifications to that of the RCX505 but with the addition of electronic vernier tuning; tuneable a.f. filter for c.w.; precision geared tuning drive system with all rotating spindles being fitted with miniature ball-bearings driving a precision high speed digital counter; the calibration of this digital read-out being every 250 cycles with an accuracy of better than 1 kc. Both the RCX505 and the RCX606 have a 6:1 ratio reduction drive on the b.f.o. control, and slot filter and aerial trimmer controls are provided for ease of adjustment.

British National Radio School, the only privately run British home study Institute specialising in electronic subjects only, displayed some examples of their courses. Offering home study training for all subjects in TV, radio, etc., especially for the City and Guilds examinations, the Grad.Brit.I.R.E., the Radio Amateurs licence, P.G.M. Certificates and R.T.E.B. Servicing Certificates, etc., the Institute has over 20 years of experience in this type of tutorship.

It is impossible in a short review of this nature to mention all of the stands—least of all every, or even most, of the equipments on show. There were, as the above review shows, many new items to be seen and the overall trend towards miniaturisation continues apace. The increasing use of semi-conductors, either in whole or in part, of many of the circuits is also a sign of the times.

The stands of the respective services, the various societies devoted to specialist radio interests and those not specifically mentioned here, were all of interest and well worth a close inspection. Altogether an interesting exhibition and one that is an annual pilgrimage for all those interested in amateur radio in all its various aspects.

Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. Queries should be submitted in writing.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers, as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

Contributions on constructional matters are invited, especially when they describe the building of particular items of equipment. Articles should be written on one side of the sheet only and should preferably be typewritten, diagrams being on separate sheets. Typewritten articles should have maximum spacing between lines. In handwritten articles, lines should be double-spaced. Diagrams need not be large or perfectly drawn, as our draughtsmen will re-draw in most cases, but all relevant information should be included. Sharp and clear photographs are helpful, where applicable. If negatives are sent, we usually work from these rather than from prints. Colour transparencies normally reproduce badly—black and white photographs are very much better. Details of topical ideas and techniques are also welcomed and, if the contributor so wishes, will be re-written by our staff into article form. All contributions must be accompanied by a stamped addressed envelope for return, if necessary, and should bear the sender's name and address. Payment is made for all material published.

Production.—Letterpress/contact litho.

LEARN ELECTRONICS AS YOU BUILD 25 CIRCUITS ... EXPERIMENTS ... TEST GEAR ...

including

● CATHODE RAY OSCILLOSCOPE

- VALVE EXPERIMENTS
- SQUARE WAVE GENERATOR
- SIGNAL TRACER
- BASIC AMPLIFIER
- SIMPLE TRANSMITTER
- BASIC COMPUTER CIRCUIT
- BASIC RECTIFIER
- TRANSISTOR EXPERIMENTS
- BASIC RADIO RECEIVER
- PHOTO ELECTRIC CIRCUIT
- BASIC OSCILLATOR
- MORSE CODE OSCILLATOR
- TIME DELAY CIRCUIT
- ELECTRONIC SWITCH
- ETC. ETC.

This complete practical course will teach you all the basic facts of electronics by making experiments and building apparatus. You learn how to recognise and handle all types of components—their symbols and how to read a circuit diagram. You see how circuits are built and how they work **BY USING THE OSCILLOSCOPE PROVIDED.** Applications of all the main electronic circuits are

demonstrated—radio reception and transmission; photo-electrics; computer basics; timers; control circuits; etc.; including servicing techniques. **NO MATHS USED OR NEEDED. NO THEORY NEEDED. NO PREVIOUS KNOWLEDGE OR EXPERIENCE NEEDED.** Tutor service available. No extras needed—tools provided. Send now, for *Free Details* without obligation, to address below

POST NOW



To **RADIOSTRUCTOR**, Dept. K3, **READING, BERKS.** Please send free details of your electronics kit set to:

NAME

ADDRESS

SMALL ADVERTISEMENTS

Use this form for your small advertisement

To: The Advertisement Manager, Data Publications Ltd., 57 Maida Vale, London, W.9
Please insert the following advertisement in the issue of **THE RADIO CONSTRUCTOR**

16 words at 9d.
= 12/-

**ALL WORDING
IN
BLOCK LETTERS
PLEASE**

I enclose remittance of being payment at 9d. a word. **MINIMUM 12/-.**
Box Number, if required, 2/- extra.

NAME

ADDRESS

Copy to be received four weeks prior to publication. Published on the 1st of every month

SMALL ADVERTISEMENTS

Rate: 9d. per word.

Minimum charge 12/-.

Box No. 2/- extra.

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the *bona fides* of advertisers. (Replies to Box numbers should be addressed to: Box No. —, *The Radio Constructor*, 57 Maida Vale, London, W.9.)

DIRECT TV REPLACEMENTS LTD. Largest stockists of TV components in the U.K. Line output transformers, Frame output transformers, Deflector coils for most makes. Official sole suppliers for many set makers. Same day despatch service. Terms C.O.D. or C.W.O. Send S.A.E. for quotes. Day and night telephone: Gipsy Hill 6166.—126 Hamilton Road, West Norwood, London, S.E.27.

THE INCORPORATED PRACTITIONERS IN RADIO AND ELECTRONICS (I.P.R.E.) LTD. Membership conditions booklet 1s. Sample copy of I.P.R.E. Official Journal 2s. post free.—Dept. D, Secretary, 32 Kidmore Road, Caversham, Reading, Berkshire.

SERVICE SHEETS, 1925-1964. From 1s. Catalogue 6,000 models, 1s. 6d. S.A.E. enquiries.—Hamilton Radio, 13 Western Road, St. Leonards, Sussex.

S.E.S. SERVICE SHEETS for all Television, Radio, etc. Lists 1s. 6d. plus S.A.E.—Sun Electrical Services, 38 St. George's Road, Hastings, Sussex.

METALWORK. All types cabinets, chassis, racks, etc., to your specifications.—Philpott's Metalworks Ltd., Chapman Street, Loughborough.

HAMMER FINISH PAINT. The modern finish for electronics. Can be brushed or sprayed. Blue or silver. 2½ oz. tins 3s. 6d., ½ pint 7s. 6d., 1 pint 15s. Post 6d. on any order. Trade supplied.—Finnigan Speciality Paints, (RC), Mickley Square, Stocksfield, Northumberland.

CONVERT ANY TV SET INTO AN OSCILLOSCOPE. Instructions and diagrams, 12s. 6d.—Redmond, 26 St. John's Road, Hove, Sussex.

FOR SALE. Large amounts of aluminium sheet, tube and rod to be disposed of quickly. Send us your requirements and we will quote without obligation. Save £££'s.—Slater Metals (Non-Ferrous) Ltd., Non-Ferrous Metal Wholesalers, 17 Slater Street, Liverpool 1.

NAMEPLATES, Identification Panels in self-adhesive satin-finished aluminium to your own design or ours.—Aero-Engravers, Weston Lane, Bubbenhall, Coventry, Warwickshire. Telephone: Tollbar 3205.

FIND TV SET TROUBLES IN MINUTES from that great book *The Principles of TV Receiver Servicing*, 10s. 6d., all book houses and radio wholesalers. If not in stock, from—Dept. D, Secretary, 32 Kidmore Road, Caversham, Reading, Berkshire.

continued on page 357

BENTLEY ACOUSTIC CORPORATION LTD

38 CHALCOT ROAD CHALK FARM LONDON NW1
THE VALVE SPECIALISTS Telephone PRIMROSE 9090

IL4	2/3	9BV6	9/6	DK40	15/6	ECH84	9/6	EY88	8/9	PY88	7/9
IR5	4/-	10C1	8/9	DK92	8/-	ECL80	6/-	EZ40	5/3	PY800	6/-
IS4	5/-	10C2	12/3	DK96	6/3	ECL82	6/3	EZ41	6/-	PY801	6/3
IS5	3/6	10F1	10/-	DL96	5/9	ECL83	9/6	EZ80	3/9	TY86F	11/8
IT4	2/3	10F8	9/9	DM70	5/-	ECL86	8/9	EZ81	4/-	U24	12/6
2D21	5/6	10LD11	9/6	DY86	6/9	EF37A	6/-	HABC80	9/3	U25	8/6
3D6	3/9	10P13	8/3	DY87	8/-	EF40	8/9	KT61	6/9	U26	7/6
3Q4	5/3	10P14	11/6	E80F	24/-	EF41	6/9	KT66	12/3	U191	9/6
3Q5	7/-	12AH8	10/9	E83F	24/-	EF80	3/9	N339	15/-	U282	12/3
354	4/6	12AT6	4/6	E88CC	10/-	EF83	9/9	PABC80	6/9	U301	11/3
3V4	5/3	12AU6	5/9	E180F	19/6	EF85	4/6	PC85	10/3	U329	9/-
5Y3	4/9	12AV6	6/6	EABC80	5/6	EF86	6/-	PC88	9/6	U404	6/-
5Z4	7/-	12BA6	5/9	EAC91	3/3	EF89	4/-	PC95	11/8	U801	16/3
6AQ5	5/9	12BE6	4/9	EAF42	7/6	EF91	3/-	PC97	7/3	UABC80	5/-
6AT6	3/9	12BH7	6/-	EB91	2/3	EF92	2/6	PCC84	5/6	UAF42	7/6
6AU6	5/3	19AQ5	7/3	EBCC3	6/-	EF97	10/-	PCC85	6/9	UBC41	6/3
6AV6	5/6	20D1	10/-	EBCC41	6/6	EF98	10/6	PCC88	10/6	UBC81	6/3
6BA6	4/6	20F2	11/6	EBCC81	5/9	EF183	7/-	PCC89	7/9	UBF80	5/9
6BE6	4/9	20L1	12/6	EBF80	5/6	EF184	7/-	PCC189	10/6	UBF89	6/9
6BH6	5/3	20P1	12/6	EBF83	7/3	EL33	6/9	PCF80	6/-	UC92	6/3
6BJ6	5/6	20P3	12/-	EBF89	6/3	EL34	8/6	PCF82	6/3	UC84	8/9
6BQ7A	7/6	20P4	13/6	EBL21	10/6	EL36	8/9	PCF84	8/6	UC85	6/9
6BR7	8/3	20P5	12/3	EC70	4/9	EL41	7/-	PCF86	7/9	UCF80	8/9
6BR8	8/-	30C15	9/-	EC92	6/6	EL42	7/6	PCL82	5/3	UCH42	7/-
6BV6	6/9	30C18	10/6	ECC40	7/-	EL83	6/9	PCL83	7/9	UCH81	6/6
6CD6G	18/-	30F5	5/9	ECC81	3/6	EL84	4/6	PCL84	7/-	UCL82	7/9
6CH6	5/-	30L15	9/3	ECC82	4/6	EL85	7/6	PCL85	7/6	UCL83	8/6
6FI	9/6	30P4	12/3	ECC83	4/6	EL86	7/3	PCL86	8/9	UF41	6/9
6F13	3/9	30P12	7/6	ECC84	5/6	EL95	5/6	PL36	8/-	UF42	4/9
6J7G	4/6	30P19	12/3	ECC85	5/9	EM134	11/6	PL38	16/-	UF80	6/3
6K7G	1/3	30P11	8/6	ECC88	8/9	EM71	13/6	PL81	6/9	UF85	6/9
6K8G	3/3	30P13	9/6	ECC189	11/6	EM80	6/3	PL82	5/3	UF86	9/-
6L1	10/-	35W4	4/9	ECCF80	6/-	EM81	7/-	PL83	5/3	UF89	6/-
6L18	10/-	35A2	6/6	ECCF82	6/3	EM84	6/9	PL84	5/-	UL41	6/9
6LD20	5/6	3763	7/6	ECCF86	11/6	EM85	8/9	PNB4	9/3	UL46	8/6
6Q7G	4/-	AZ31	6/6	ECH21	9/-	EM87	7/6	PY33	8/9	UL84	6/-
6V6G	3/9	AZ41	6/6	ECH35	6/3	EY51	5/6	PY80	5/-	UM80	8/3
6X4	3/9	DAF96	5/9	ECH42	7/6	EY83	9/3	PY81	4/9	UY41	4/6
6X5	4/6	DF96	5/9	ECH81	5/9	EY84	9/6	PY82	4/9	UY85	5/-
6/30L2	8/3	DF97	10/-	ECH83	6/6	EY86	5/6	PY83	5/9	UX78	20/6

Terms of business: Cash with order or C.O.D. only. Post/packing 6d. per item. Orders over £3 post free. C.O.D. 3/6 extra. All orders despatched same day. Complete catalogue with terms of business 6d. Any parcel insured against damage in transit for 6d. extra. We are open for personal shoppers 8.30-5.30. Saturdays 8.30 a.m.-1 p.m.



**65 or 25
GIVE
A SOLON
FOR
CHRISTMAS**



Do-it-yourselfers of all ages will welcome a Solon Electric Soldering Iron. The 25-watt model above, or 65-watt below, are ideal for radio work or household jobs.



Obtainable from your usual electrical or radiodealer from 24/8.

SOLON Electric Soldering Irons

THE DUCHESS OF KENT PERMANENT BUILDING SOCIETY

Member of the Building Societies Association

Savings in this old established Building Society combine sound investment with an attractive return
Shares are in units of £25 each (maximum investment £5,000) . . . BUT, for the smaller
saver, Subscription Share accounts may be opened with any sum from 1/- upwards.
Interest is payable half-yearly on Fully Paid Shares—credited annually on Subscription
Shares—all interest accrues monthly


WITHDRAWALS AT SHORT NOTICE

INTEREST IS AT $3\frac{3}{4}\%$ PER ANNUM
(There is NO DEDUCTION FOR INCOME TAX, as
this is paid by the Society)

FOR FURTHER INFORMATION APPLY TO

**DUCHESS OF KENT
PERMANENT BUILDING SOCIETY**
103 Cannon Street London EC4
Telephone MANsion House 8011

ESTABLISHED

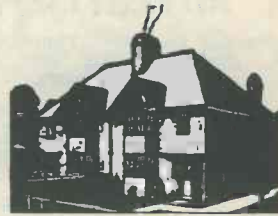

1865

Please send to me, without obligation, free brochure
and a copy of the audited statement of accounts. (I
understand that I shall not be troubled with calls by
representatives)

Name

(If lady, please state Mrs. or Miss)

Address

R.C.

(Please use Block Capitals for both name and address)

MAKE IT MARTIN



**ADD TAPE
TO YOUR HI-FI
WITH A RECORDAKIT**

**ALSO
AUDIOKITS FOR
HI-FI**

and now . . .

AUDIOKIT F.M. TUNER

All-Transistor. Available very
soon. Details on request.

With a Martin Recordakit you can either
build a complete tape recorder (with deck
and portable-type case if desired) or assemble
a pre-amp to connect your deck to existing
amplifier system. For two or four track. When
finished, you will enjoy performance and
quality that looks and sounds professional.
Building is very easy and prefabricated sections
are tested individually before despatch from
our factory.

KITS FROM 8 gns. TO 27½ gns.

MARTIN ELECTRONICS, 154 High St., Brentford, Middlesex

Details please of Recordakits and F.M. please

Name

Address

RC12

TAPE

RECORDING MAGAZINE

**Fullest, fastest, brightest and
most authoritative coverage of
all that is happening in the
world of tape recording**

Published on the third Wednesday of
each month

Price 2s

In case of difficulty write to "Tape Recording Magazine"
7 Tudor Street, London, E.C.4

FIRST AND FOREMOST IN THIS FIELD

SMALL ADVERTISEMENTS

continued from page 355

OFFERS for Philips 3-speed playing deck with auto change and 5 watt amplifier.—Box No. F216.

FOR SALE. New resistors. Assorted values, wattages and types. Mostly hi-stab. 1% and 5%. 10s. per 150.—B. Putland, 2 Poors Lane, Hadleigh, Benfleet, Essex.

FOR SALE. Quantity of new accumulators. Willard Radio-20-2, 2 volt. Size: 5in high x 3½in x 2½in., 5s. each plus carriage.—Box No. F224.

FOR SALE. New grey cabinet, length 12in, height 7in, back to front 7in, £2 post paid. Black crackle cabinet, length 16½in, height 7½in, back to front 7½in, £1 post paid. Crystal mic. in G.P.O. type desk stand, 15s. post paid.—Box No. F225.

FOR SALE. Complete 1958, 1959 & 1960 of *The Radio Constructor* £3.—101 London Road, Ipswich, Suffolk.

VALVES. 6J6, EB91 at 1s. 6d. 12AT7, CV51 at 2s. DAF91, 6AT6 at 3s. 6d. 5Y3GT, DL92, EF92, EL91, U14, 801A at 5s. 5R4GY, 6B4, 807, 6BR7, EF40, VT136 at 7s. 6d. KT66, RG1240A, 5B254M, 830B, T20 at 10s.—Box No. F226.

TO CLEAR BOOKSHELVES: *Fall Out* edited by A. Pirie, 7s. 6d.; *Radiation Monitoring in Atomic Defence* Gray & Martens, 7s. 6d.; *Radioactivity & Radioactive Substances* Sir James Chadwick, 10s.; *An Introduction to Radiation Counters & Detectors* C. Washtell, 10s.; *Elementary Nuclear Physics* W. K. Mansfield, 7s. 6d.; *Radio Aids to Air Navigation* J. Glover, 10s.; *Electric Clocks and how to make them* Hope-Jones, 7s. 6d.; *Radio Today* D. K. McCleery, 10s.; *Man in Space* Heinz Haber, 15s.; *Earth's Envelope* Theo Lobsack, 10s.; *The Atomic Submarine* Clay Blair, 7s. 6d.; *The Realities of Space Travel* L. J. Carter, 17s. 6d.; *Radio Astronomy* Graham Smith, (Pelican) 5s.; *Single Sideband for the Radio Amateur*, 7s. 6d.; *New Sideband Handbook* CQ Technical Series, 5s.; *Radio Control Handbook* Gernsback Library No. 53, 5s.; *Remote Control by Radio* Philips Technical Library, 5s.; *Radio-Controlled Models* R. H. Warring, 10s.; *Model Radio-Control* Gernsback Library No. 74, 7s. 6d.; *Model Boat Radio Control* A. R. Casebrook, 3s.; *Radio Control of Model Aircraft* Sommerhoff, 5s. All in good clean condition and offered at approximately half-price.—Box No. F227.

INTERESTED IN AMATEUR RADIO TELEPRINTING? Then join the British Amateur Radio Teletypewriter Group. Details from Hon. Sec., G2UK, East Keal, Romany Road, Oulton Broad, Suffolk.

continued on page 359

FOULSHAM-SAMS TECHNICAL BOOKS

- | | |
|--|----------|
| UNDERSTANDING ELECTRONIC COMPONENTS
F. J. Waters | 24s. net |
| ELECTRONIC TEST INSTRUMENT HANDBOOK
J. A. Risse | 35s. net |
| TRANSISTOR IGNITION SYSTEMS HANDBOOK
B. Ward | 20s. net |
| ELECTRONICS MADE EASY L. Stern | 30s. net |
| HOW TO READ SCHEMATIC DIAGRAMS
D. E. Herrington | 18s. net |
| TRANSISTOR CIRCUIT MANUAL A. Lytel | 35s. net |
| ELECTRONIC SERVICING FOR THE BEGINNER
J. A. Stanley | 24s. net |
| KNOW YOUR OSCILLOSCOPE P. C. Smith | 20s. net |
| TAPE RECORDERS: HOW THEY WORK
C. G. Westcott and R. F. Dubbe | 26s. net |
| HANDBOOK OF ELECTRONIC CHARTS AND NOMOGRAPHS A. Lytel | 35s. net |
| DIODE CIRCUITS HANDBOOK R. P. Turner | 18s. net |
| ELECTRONIC ENGINEERS AND TECHNICIANS REFERENCE HANDBOOK | 30s. net |
| ELECTRONIC COMPONENT TESTS AND MEASUREMENTS
R. G. Middleton | 24s. net |
| 101 WAYS TO USE YOUR VOM AND VTVM
R. G. Middleton | 16s. net |
| 101 WAYS TO USE YOUR SIGNAL GENERATOR
R. G. Middleton | 18s. net |
| COMPUTER CIRCUIT PROJECTS YOU CAN BUILD
L. Boschen | 21s. net |
| ELECTRONICS FOR THE BEGINNER J. A. Stanley | 25s. net |
| MODERN DICTIONARY OF ELECTRONICS | 45s. net |
| ELECTRONICS MATH SIMPLIFIED VOL. I
A. Andrews | 35s. net |
| ELECTRONICS MATH SIMPLIFIED VOL. II
A. Andrews | 35s. net |
| ELECTRONICS EXPERIMENTS AND PROJECTS
L. Buckwalter | 25s. net |
| INTRODUCTION TO LASERS AND MASERS
A. Lytel | 16s. net |
| ABC'S OF ELECTRONICS F. Waters | 16s. net |
| ABC'S OF COMPUTERS A. Lytel | 16s. net |
| ABC'S OF ELECTRICITY | 16s. net |
| ABC'S OF SHORT-WAVE LISTENING L. Buckwalter | 16s. net |
| ABC'S OF COMPUTER PROGRAMMING A. Lytel | 16s. net |
| ABC'S OF ELECTRIC MOTORS AND GENERATORS
A. Lytel | 16s. net |
| ABC'S OF BOOLEAN ALGEBRA A. Lytel | 16s. net |
| PRACTICE PROBLEMS IN ELECTRONICS CALCULATIONS
A. Andrews | 30s. net |
| BASIC ELECTRICITY/ELECTRONICS
Programmed Learning | |
| 1. BASIC PRINCIPLES AND APPLICATIONS | 35s. net |
| 2. HOW AC AND DC CIRCUITS WORK | 35s. net |
| 3. UNDERSTANDING TUBE AND TRANSISTOR CIRCUITS | 35s. net |
| 4. UNDERSTANDING AND USING TEST INSTRUMENTS | 35s. net |
| 5. MOTORS AND GENERATORS—HOW THEY WORK | 35s. net |
| BASIC ELECTRONICS SERIES
Thomas M. Adams | |
| 1. TRANSISTOR CIRCUITS | 24s. net |
| 2. OSCILLATOR CIRCUITS | 24s. net |
| 3. DETECTOR AND RECTIFIER CIRCUITS | 24s. net |
| 4. AMPLIFIER CIRCUITS | 24s. net |

Write for complete catalogue

Distributed by

W. FOULSHAM & CO. LTD.

ELECTRONICS DEPARTMENT

Yeovil Road, Slough, Bucks, England

ORDER FORM

TITLE	No.	£	s.	d.
<p>THE RADIO CONSTRUCTOR Price 2/3 each, postage 6d. Issue(s) required.....</p> <p>.....</p> <p>Annual subscription commencing with..... issue Price 33/-, post free</p> <p><i>Bound volumes:</i> Vol. 17. August 1963 to July 1964 Price 30/-, postage 3/-</p> <p>DATA BOOKS SERIES</p> <p>DB5 TV Fault Finding 96 pages. Price 6/-, postage 6d.</p> <p>DB6 The Radio Amateur Operator's Handbook 64 pages. Price 5/-, postage 5d.</p> <p>DB14 Short Wave Receivers for the Beginner 72 pages. Price 6/-, postage 5d.</p> <p>DB15 Twenty Suggested Circuits 48 pages. Price 3/6, postage 4d.</p> <p>DB16 Radio Control for Models 192 pages. Price 15/-, postage 9d.</p> <p>DB17 Understanding Television 512 pages. Price 37/6, postage 2/-</p> <p>PANEL-SIGNS TRANSFERS</p> <p>PS3: Wording — White</p> <p>PS4: Wording — Black</p> <p>PS5: Dials { In PS5 the control panels have a clear PS6: Dials { background; in PS6 the background is black.</p> <p>Price per set 4/6, postage 3d.</p>				
Total		£	:	:

*Please send cash with order, regret no C.O.D.
 Overseas customers please pay by International Money Order*

NAME

ADDRESS

(Please use Block Capitals for both name and address)

*All publications are obtainable from your local bookseller or direct from
 Data Publications Ltd 57 Maida Vale London W9*

SMALL ADVERTISEMENTS

continued from page 357

JOIN THE INTERNATIONAL S.W. LEAGUE. Free Services to members including Q.S.L. Bureau. Amateur and Broadcast Translation. Technical and Identification Dept.—both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes. QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazine, etc., 21s. per annum.—Secretary, ISWL, 12 Gladwell Road, London, N.8.

THE INTERNATIONAL HAM HOP CLUB is a non-profit-making organisation open to RADIO AMATEURS AND SHORT WAVE LISTENERS. OBJECT: to improve international relationships through an organised system of hospitality. MEMBERS offer overnight hospitality to visiting members, subscription 10s. per annum. ASSOCIATE MEMBERS invite radio amateurs to visit their stations. Associate membership 5s. per annum. FAMILY EXCHANGE holidays arranged, also FRIENDSHIP LINKS between radio clubs. The Club's official journal is free to both Full and Associate Members.—Hon. Gen. Secretary: G. A. Partridge, G3CED, 17 Ethel Road, Broadstairs, Kent.

SITUATIONS VACANT

ELECTRONIC/RADIO ENGINEER. For general work on electronic machine tool controls. Job would suit technically frustrated service engineer seeking wider interest.—Telephone RAV 6646 or write to Electronic Autosizing Metrology Ltd., 216 Homesdale Road, Bromley, Kent.

FISONS FERTILIZERS LIMITED require DRAUGHTSMEN at their works at Immingham, Lincolnshire.

1. SENIOR DRAUGHTSMEN. Applicants should preferably hold H.N.C. or equivalent in Mechanical Engineering and be experienced in plant layout, design and detail of mechanical and chemical plant. Experience with mechanical handling plant will be an advantage.

2. DRAUGHTSMEN. Applicants should hold O.N.C. in Mechanical Engineering and preferably be experienced in plant layout and detail of mechanical and chemical plant.

Salary will be according to qualifications and experience. Free daily transport is available from Grimsby and Cleethorpes. Please write for application form to—Personnel Officer, Fisons Fertilizers Limited, Immingham Dock, Immingham, Grimsby, Lincs.

TELEPHONE HANDSETS

G.P.O. pattern, house to workshop, garage, inter-office, etc. **15/6**
Works off any small battery. P.&P. 4/6. **per pair**

Stamp for FREE LIST

DUKE & COMPANY (London) LTD
621/3 Romford Road, Manor Park, E.12 ILF 6001/3

TO DESIGNERS & CHIEF ENGINEERS

OSMOR

SPECIALISE IN WINDING MINIATURE COILS, TRANSFORMERS, ETC. OF INTEREST TO BULK MANUFACTURERS IN THE INDUSTRIAL FIELD.

MANUFACTURERS USING UP TO 50 S.W.G. WOULD FIND OUR SERVICE ECONOMICAL AND RELIABLE. ENQUIRIES APPRECIATED.

LARGE CAPACITY AVAILABLE

PLEASE TELEPHONE CRO 5148
FOR SWIFT ACTION

OSMOR RADIO PRODUCTS LTD.

540 PURLEY WAY (PARKING FACILITIES)

(Nr. AIRPORT) CROYDON

CRO 5148/9

TESTED TRANSISTORS

1/- each Red or White Spots. OA81, OA202.

2/- each XA101, XA102, XA111, XA112, XB103, NKT122, OA90, OC430.

3/- each OC44, OC45, OC81, OC81D, OC200, GET16.

4/- each AF114, AF115, AF117, OC170, OC171, SX658, XV611.

5/- each OC72, OC139, OC140, OC204, GET8, ORP60, BY100.

10/- each OC35, OC26, OC28, AFY19, 2S013, ORP12, GET571.

ZENER DIODES 4.7 volt to 33 volt $\frac{1}{2}$ watt, 3/6 each, 1.5 watt, 5/- each, 7 watt, 6/- each.

Send 3d. stamp for Full Price List, and Free Equivalent Chart

B. W. CURSONS

78 BROAD STREET, CANTERBURY, KENT

CHASSIS and CASES by



287/9 Edgware Road
London W2
TELEPHONE
PADDDINGTON 5891/7595

BLANK CHASSIS—Same Day Service

Of over 20 different forms made up to YOUR SIZE.
Order EXACT SIZE you require to nearest 1/16th.
(Maximum length 35", depth 4")
Specials dealt with promptly.

SEND FOR ILLUSTRATED LEAFLETS

or order straight away, working out total area of material required and referring to table below which is for four-sided chassis in 18 s.w.g. (for 16 s.w.g. add 1/6th).
48 sq. in. 4/- 176 sq. in. 8/- 304 sq. in. 12/-
80 sq. in. 5/- 208 sq. in. 9/- 336 sq. in. 13/-
112 sq. in. 6/- 240 sq. in. 10/- 368 sq. in. 14/-
144 sq. in. 7/- 272 sq. in. 11/- and pro rata
P. & P. 2/6 P. & P. 2/9 P. & P. 3/-


Discounts for quantities. Finishes arranged for quantities of 25 or over.

FLANGES (1" or 1 1/2"), 6d. per bend.
STRENGTHENED CORNERS, 1/- each corner.
PANELS

Any size up to 3ft at 4/6 sq. ft. 18 s.w.g. (16 s.w.g. 5/3).
Plus postage and packing (orders over £2 Post Free).

CASES

ALUMINIUM, SILVER HAMMERED FINISH			Type W		
Type	Size	Price	Type	Size	Price
U	4 x 4 x 4"	9/6	Y	8 x 6 x 6"	25/-
U	5 1/2 x 4 1/2 x 4 1/2"	14/6	Y	12 x 7 x 7"	39/-
U	8 x 6 x 6"	20/-	Y	13 x 7 x 9"	44/-
U	15 x 9 x 9"	42/6	Y	15 x 9 x 7"	46/-
W	8 x 6 x 6"	19/6	Z	17 x 10 x 9"	63/-
W	12 x 7 x 7"	32/6	Z	19 x 10 x 8 1/2"	67/6
W	15 x 9 x 8"	42/-		* Height	

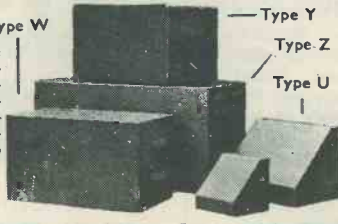

Type Z has removable back and front panels.
Type Y all-screwed construction.

BRASS · COPPER · LIGHT ALLOYS · ALUMINIUM BRONZE · STAINLESS STEEL

ROD, BAR, SHEET, TUBE, STRIP, WIRE. 3,000 STANDARD STOCK SIZES
No Quantity too small List on application

H. ROLLET & CO LTD
HOWIE ST. LONDON SW11 BATTERSEA 7872
Also at Liverpool, Birmingham, Manchester, Leeds, Glasgow

the unique **PANL** black crackle paint

4/-d. per 1/8 pt. Can
(We regret we can only supply on cash with order basis)

BRUCE MILLER LTD.,
249 Coastal Chambers,
Buckingham Palace Road, S.W.1.

AERIAL MATCHING TUNING UNITS

Latest American release bulk purchase of 3,000
These well made tuning units, made for the American 19. T.X.-R.X. are housed in a metal case size 4" x 4" x 10", using a large precision calibrated scale, are an essential piece of equipment for the serious T.X. or R.X. operator. This unit will match an untuned wire or whip aerial to almost any short wave receiver or transmitter, exceptionally good for mobile Top Band use. This American version being well noted as far superior to any other. **GUARANTEED BRAND NEW only 20/-, post 7/6.** Instructions supplied.

PYE OR INVICTA LOUDSPEAKER UNITS
Enclosed in a brown wooden cabinet with carrying handle, using a silver speaker mesh. Complete with 40ft. of lead and Jack Plug. A 10" heavy duty 3 ohms speaker is used, being very useful for Groups, Halls, P.A. work, etc. (made for Army entertainment use). **BRAND NEW & BOXED ONLY £2.15.0, carr. 5/-.** A fraction of cost.

88 T.X.-R.X. POWER UNIT
12V input to 90V, 7.5V, 1.4V stabilised output. Also contains L.F. amplifier. These are sold **BRAND NEW** with 4 B.7.G. valves only 50/-, P.P. 5/-.
J. T. SUPPLY, (Dept F) 38 MEADOW LANE, LEEDS 11

WE SPECIALISE

in Quality Transistors & Components
For Discerning Enthusiasts

British, American and Continental
semiconductor devices . . .
Miniature components for transistor circuit
applications . . .

Our Reference Catalogue, for which we ask only one shilling (stamps), contains very interesting gen and is a very useful guide to selecting components and semiconductors for special purposes. A coupon enables you to reclaim more than your shilling against an order.

J. WILLIAMS & CO. 208 HAGLEY ROAD
BIRMINGHAM 16

YOUR CAREER IN RADIO?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the **CITY & GUILDS EXAMS.** (Technicians' Certificates); the Grad. Brit. I.R.E. Exam.; the **RADIO AMATEUR'S LICENCE;** P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have **OVER 20 YEARS'** experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study Institute specialising in electronic subjects only. Fullest details will be gladly sent without any obligation.

SEND FOR **FREE BROCHURE TO:**
BRITISH NATIONAL RADIO SCHOOL
DEPT 4, RADIO HOUSE · READING · BERKSHIRE

THE RADIO CONSTRUCTOR — BOUND VOLUMES

Now available

Volume 17, August 1963 to July 1964 Price £1 10s 0d Postage 3s 0d

Where all issues are returned : Price £1 Postage 3s 0d

Limited number also available of:—

Volume 13, August 1959 to July 1960 Price £1 5s 0d Postage 2s 6d

Where all issues are returned : Price £1 Postage 2s 6d

We regret Volumes 14, 15 and 16 are now sold out

Send for latest brochure containing details of our other publications

DATA PUBLICATIONS LTD 57 MAIDA VALE LONDON W9



VALVE VOLTMETER

AC/DC (+ and -) Resistance.
AC/RMS and PK/PK.

Detailed leaflet on request.

- ★ AC RMS and DC Voltage 0/1½/5/15/50/150/500/1,500 volts. DC IMP. 11 meg. A.C SENS 7.33 meg/volt.
- ★ AC PK to PK 0/4.2/14/42/140/420/1,400/4,200 volts.
- ★ Resistance from 0.2 ohm to 1,000 Meg. In 4 ranges. AC/DC Probe, DC to 4 Mc/s, High Stability and Accuracy. Size 7¼" x 4¾" x 5". Mains operated. Fully guaranteed.
Price £13.19.6. P.P. 2/6
(Probe to extend to 100 Mc/s, 40/- extra)

BUILD A QUALITY TAPE RECORDER

- ★ Pre-Built Equipment—6 Valves—Collaro Studio Decks—Portable Cabinets with 8" x 5" Speakers



TWO TRACK Total Cost £26
P.P. 8/6

OR Deck 10 gns. P.P. 5/-; Amplifier 11 gns. P.P. 3/6. Cabinet with Speaker 5 gns. P.P. 3/6.

FOUR TRACK Total Cost £30
P.P. 8/6

OR Deck £13.19.6. P.P. 5/-; Amplifier 12 gns. P.P. 5/6. And Cabinet with Speaker 5 gns. P.P. 3/6.
All complete in every detail. Illustrated leaflets on request. Ideal for portable or domestic equipment.

GARRARD 2-TRACK BATTERY TAPE DECK



9V operated, 2 track, 2 speed. Brand new, fitted heads, etc. Supplied complete with cassette. Brand New. New Low Price
£10.10.0. P.P. 3/6.

FM VHF TUNING HEART

Printed circuit construction, fully tunable 85 to 105 Mc/s. Completely screened. Requires UCCB5 (8/6), R.F. stage and osc./mixer stage. With circuit.
Brand new in maker's cartons 15/- P.P. 1/-

TRANSISTOR SUPERHET TUNER



½ volt medium wave 3-transistor and diode superhet radio tuner. Ideal for all amplifiers. Price with circuit 67/6. P.P. 1/6.
Also mW/sW 4-transistor £7.9.6.

TRANSISTORS, CRYSTALS, VALVES AND COMPONENTS

THE LARGEST RANGE OF THE ABOVE ITEMS IN THE COUNTRY


We stock far too many types to list here. See our Catalogue for full range LET US QUOTE FOR PARTS FOR YOU RETURN OF POST SERVICE

A SELECTION FROM OUR STOCKS

See Catalogue for full details

- Sinclair X10 Amplifier (Kit) ... £5.19.6
- (Built) ... £6.19.6
- Sinclair Micro-6 (to build) ... 59/6
- Sinclair TR750 Amplifier (to build) ... 39/6
- Sinclair Micro Injector (to build) ... 27/6
- Sinclair X10 Amplifier Kit ... 119/6
- Sinclair X10 Amplifier Built ... 139/6
- Tape Jack Tuner (Full Med. Wave) ... 29/6
- 10-Watt Horn Tweeter ... 27/6
- 20-Watt Super Tweeter ... 69/6
- Two-channel Mixer for Mics/Pu's ... 15/-
- 1 to 200 Mc/s Field/str. Meter ... 59/6
- 5-hole Chassis Punch Kit ... 49/6
- Headphones 2kΩ 12/6; 4kΩ ... 14/6
- Stereo Stethoscope Headset, 8+8 arm ... 25/-
- Resistor Substitution Box ... 32/6
- Crystal Mono Stethoscope Headset ... 10/6
- Magnetic Mono Stethoscope Headset ... 12/6
- Transistor Signal Injector ... 35/-
- Fully Disappearing Car Aerial ... 35/-
- Test Lead Kit with Pouch ... 8/6
- Capacitor Substitution Box ... 22/6
- De Luxe Stereo Headsets with junction box ... 66
- PP3 9V Batt. Eliminator ... 18/6
- Transistor Telephone Amplifier ... 59/6
- 8+8Ω Stereo Headphones ... 62/6
- Crystal Contact Microphone ... 12/6
- MCI Crystal Mic. Insert ... 5/-
- Earphones, Crystal or Magnetic Complete with Jack and Socket. ... 5/-
- Telephone Recording Attachment ... 9/6
- 50-0-50μA Edgewise Meter ... 25/-
- 6/12V Min. 212w Relay ... 12/6
- Transistor Coil Set With Tuner, Ferrite Aerial and Circuit ... 20/-
- Complete Test Lead Kit ... 8/6
- 30W Pocket Mains Solder Iron ... 14/6
- 8" Hi-Fi 15/16 ohm Speaker ... 69/6
- 100 kc/s Quartz Crystal ... 15/-
- Twin Crystal 1 Mc/s and 100 kc/s ... 22/6

RECORD/REPLAY/ERASE TAPE HEADS

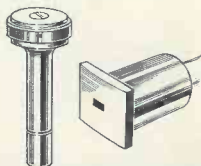

Marriot Type R/RP/3 ½ track record-replay head and Mullard type TS erase head with mounting post. Ideal for transistor circuits. Bargain Offer, 15/- Pair. P.P. 1/-

★ 700Ω IMPEDANCE ★

CRYSTAL MICROPHONES




(See Catalogue for details and for Dynamic Mics)

- Acos 39-1 Stick Microphone ... 32/6
- Acos 40 Desk Microphone ... 15/-
- Acos 45 Hand Microphone ... 19/6
- Lapel/Hand Microphone ... 12/6
- Acos Stick Microphone ... 15/-
- 100C Stick with Stand ... 32/6
- BM3 Stick with Stand ... 49/6
- Lapel/Hand Magnetic ... 8/6
- MM71 2k Mag. Mic ... 12/6
- MC70 Studio Mic ... 42/-

Trade and Export Enquiries Invited

NOMBREX TEST EQUIPMENT

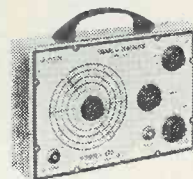

LEAFLETS ON REQUEST

FULLY GUARANTEED

All transistor portable units supplied with full instructions.

- ★ 150 kc/s to 350 Mc/s generator. RF Mod., AF, 8 ranges. Leads, batt., instructions, £9.10.0.
- ★ Resistance/Capacitance Bridge, £8.5.0.
- ★ Transistorised Power Supply, £6.10.0.
- ★ Audio Generator, £16.15.0.
- ★ Inductance Bridge, £18.

TRANSISTOR PORTABLE WALKIE-TALKIES

9-Transistor Portable Trans-receivers. Supplied complete with leather cases, batteries, aerials, etc., in presentation case. Range up to 5 miles in favourable conditions. Sizes 6½" x 3" x 1½". Superhet crystal controlled on transmit and receive.
Price £21 per pair. P.P. 3/6

- ★ DUAL IMPEDANCE (50 ohm-50k-ohm) or 600 ohm /50k-ohm dynamic professional quality microphone. Size 7½" long x 1½" diam. 40 c/s to 15 kc/s. Price 82/6.
P.P. 2/6



POCKET RADIOS

All complete with battery, earphone, carry case and fully guaranteed. 6 and 7 transistor superhet designs.

- ★ 6-Transistor Med. Wave, 69/6. P.P. 2/-
- ★ 7-Transistor Med. Wave, 79/6. P.P. 2/-
- ★ 6-Transistor Med./Long Wave, 5 gns. P.P. 2/6
- ★ 7-Transistor MW/LW/SW, £12. P.P. 3/6

MAINS AND BATTERY RECORD DECKS

ALL COMPLETE with ARM and CARTRIDGE

- ★ BSR UA14 4-speed ... £5.19.6
- ★ BSR UA15 4-speed ... £6.19.6
- ★ Garrard Autoslim 4-speed ... £6.10.0
- ★ Unpluggable Head Version ... £6.19.6
- ★ Stereo Version ... £7.19.6
- ★ 6-9 volt version ... £8.19.6
- ★ SRP10 4-speed or BSRGU7... £5. 0.0
- ★ Garrard AT6 with Stereo Cartridge, 4-speed ... £10.19.6
- ★ AT6 with Mono Head ... £10.10.0
- P. & P. 3/6 any type above
- ★ AT6 with EV26 or Sonotone ... £11.19.6
- ★ 9V Star, 45 r.p.m. ... £1.19.6
- ★ 45 and 33 r.p.m. Star, 9V ... £4.12.6
- ★ 45 r.p.m. Garrard 6V ... £1.15.0
- ★ 4-speed B.S.R., 9V or S.R.P.10 9V ... £5. 5.0
- P. & P. 2/6 any of above

HENRY'S RADIO LTD

303 EDGWARE ROAD LONDON W2

PADDINGTON 1008/9

Open Monday to Sat. 9-6. Thurs. 1 o'clock


PLEASE TURN TO BACK PAGE

FIRST AND BEST PROVED & TESTED DESIGNS, QUALITY COMPONENTS & UNITS

● TRANSISTOR HI-FI AMPLIFIERS

MONO or STEREO

10 WATTS and 20 WATTS

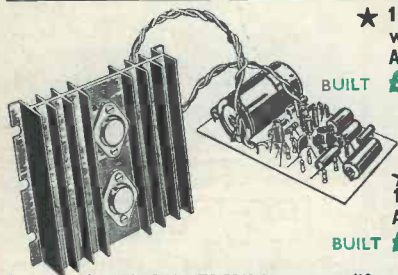

★ 15 to 16 ohm 10 watt Power Amplifier
BUILT £5-19-6 P.P. 2/6

(KIT £5-10-0 P.P. 2/6)


★ 3 to 4 ohm 10 watt Power Amplifier
BUILT £5-10-0 P.P. 2/6

★ MAINS UNITS 59/6 for one amplifier. (KIT 99/6 or 69/6 to power 2 amplifiers.)

★ Mono full function pre-amplifier with 8 input positions. Low noise, high quality and sensitivity. Gives 10 watts with one power amplifier or 20 watts with two amplifiers. Size: 9" x 2½" x 2".

BUILT £5-10-0 P.P. 2/-
(KIT 99/6 P.P. 2/-)

● PRE-AMPLIFIERS

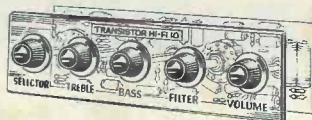

★ FRONT PANEL PLATE 8/6

● STEREO PRE-AMPLIFIER



Two Channel version of above For use with two power amplifiers for 10+10 watts. Size: 9" x 3½" x 1½".

PRICE BUILT £10-19-6 P.P. 3/6

★ Dark Brown with Gold Front Panel 12/6.

● MULTI-INPUT PRE-AMPLIFIER

Simplified pre-amplifier for use with one or two power amplifiers, 8 inputs.

PRICE BUILT 65/- P.P. 1/6

★ Front Panel Plate 6/6.


All the above pre-amplifiers can be used with any valve or transistor power amplifier requiring 250mV for full output. They can be operated with two 9 volt batteries in series or from the power amplifiers. High gain, low distortion, excellent quality designs, combined with value for money



CIRCUITS AND DETAILS ON REQUEST

Demonstrations of above equipment and VHF FM Tuner can be heard during normal shop hours. All units are fully guaranteed.

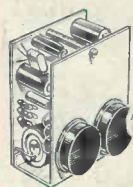NEW! TWO NEW PACKAGED TRANSISTOR QUALITY AMPLIFIERS



★ 6-Transistor printed circuit designs. Push-bully output for 3 to 5 ohm speakers. Can be battery operated. 6mV into 1 kΩ sensitivity. Response 40 c/s to 12 kc/s.

Can be used with above pre-amplifiers for mono or stereo in any amplification requiring a low distortion low cost amplifier. Overall sizes: 2½" x 2" x 1½".

★ 4 watt version operates PRICE BUILT 79/6 P.P. 1/6 from 12 to 18 volts.

★ 1½ watt version from 9 to 12 volts. PRICE BUILT 65/- P.P. 1/6

★ CIRCUITS AND DETAILS ON REQUEST ★

1½ watt and 4 watt

We can supply from stock most of the components and items specified on circuits published in this and other magazines. Quality parts at realistic prices Let us quote for your circuit.

300 TRANSISTORS TYPE DIODES AND RECTIFIERS
800 VALVES AND TUBES
500 QUARTZ CRYSTALS

All Transistor Car Radio NEW!

★ ONE HOUR TO BUILD WITH FACTORY ASSEMBLED CHASSIS AND PANELS

6-transistor 3 diode Med. and Long Wave Superhet Design. Features double tuned IFT's, AVC. Permeability tuning with geared drive, push-pull car filling volume. Full tuning of both wavebands. A high sensitivity design on printed circuits to fit any type of vehicle. 12 volt positive earth only. All parts available separately. After sales service and guarantee.



THE "ROADSTER"
★ Total Cost to Build £8-19-6 P.P. 3/6

★ 7 x 4 inch. hi-flux speaker with baffle and car fixing kit 20/-

★ Circuit and details on request.

VHF TRANSISTOR HI-FI FM TUNER

★ HIGH STABILITY — HIGH SENSITIVITY ★

Features 5-Mullard transistors with 4 diodes, compact printed circuit, high gain, low distortion, superhet design. Full tuning from 87/105 Mc/s with geared tuning, AVC and AFC. 9 volt 9mA operation. 50dB S/N. Output up to 1 volt audio. Easy to build and align. Overall size in cabinet 3½" x 2½" x 4". All parts sold separately and guaranteed.



Total Cost with Front Panel £6-19-6 P.P. 2/6

(Cabinet Assembly 20/- extra)

AFTER SALES SERVICE ★ CIRCUIT AND DETAILS ON REQUEST

"CONVAIR" PUSH BUTTON PORTABLE CAR RADIO

★ UNBEATABLE FOR PERFORMANCE AND DESIGN ★

Printed circuit 6-Transistor 2-Diode superhet radio with full tuning on medium and long wavebands. Push-pull output up to 1 watt. Attractive portable cabinet, size 10" x 7" x 3½" with horizontal slow motion tuning dial and push button wave change. Easy to build with superb performance. All parts sold separately. After Sales Service and Guarantee.




★ CIRCUIT AND DETAILS ON REQUEST

★ Total Cost of All Parts £7-19-6 P.P. 3/6

(Batteries 6/- extra) ★ The Finest Portable Available

4-CHANNEL TRANSISTOR MIXER UNIT

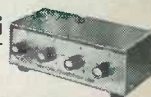Inputs suitable for microphones, pick-ups, tuners, guitars, etc.. Self-contained battery. Housed in attractive gold-finish cabinet. To feed valve or transistor amplifiers.



PRICE 49/6 P.P. 1/6

MULTI-METERS BRAND NEW FULLY GUARANTEED

PT34	1kΩ/volt sensitivity	...	39/6
CABYMI	2kΩ/volt sensitivity	...	49/6
THL33	2kΩ/volt sensitivity	...	75/-
(Illustrated)			
EP10K	10kΩ/volt sensitivity	...	79/6
IT12	20kΩ/volt sensitivity	...	82/6
TP55	20kΩ/volt sensitivity	...	£5.19.6
500	30kΩ/volt sensitivity	...	£8.19.6
EP30K	30kΩ/volt sensitivity	...	£5.10.0
EP50K	50kΩ/volt sensitivity	...	£8.10.0
EP100K	100kΩ/volt sensitivity	...	£9.19.6
POST AND PACKING 2/- ANY MODEL			



Sinclair Radionic, TSL and Martin Audio kits. All Transistor Equipment kits and built available from stock as advertised.

NEW 5th EDITION 90-PAGE CATALOGUE

Fully detailed and illustrated. Price 2/6 post paid.

HENRY'S RADIO LTD.,

303 EDGWARE ROAD LONDON W2
PADdington 100B/9

Open Mon to Sat. 9-6. Thurs. 1 p.m.