


THE

RADIO CONSTRUCTOR

Vol. 23 No. 2

SEPTEMBER 1969

THREE SHILLINGS

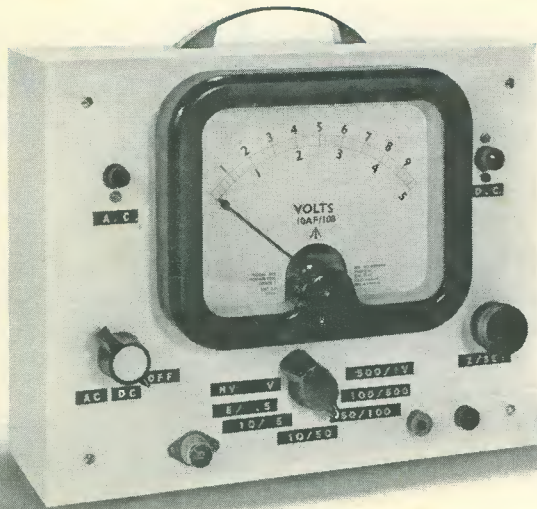

**Solid State
D.C. Voltmeter
and A.C.
Millivoltmeter**

Special
IN THIS ISSUE

Alarm for Mains Radios

Silicon Reflex T.R.F. Receiver

VALUE ALL THE WAY

INTEGRATED CIRCUITS

BI-PAK MONOLITHIC DIGITAL CIRCUITS
(10 lead TO-5)
BP305A, 8-input AND gate, 9/6 each.
BP314A, 7-input NOR gate, 9/6 each.
BP315A, Dual 3-Input NOR gate, 9/6 each.
BP316A, Dual 2-Input NOR gate (expandable), 9/6 each.
BP320A, J-K-Binary element, 11/6 each.
BP332A, Dual 3-Input OR gate, 9/6 each.

BI-PAK MONOLITHIC AMPLIFIERS (TO-5 8 lead)
BP709C, Operational amplifier, 15/6 each.
BP701C, Operational amplifier (with Zener output), 12/6 each.
BP702C, Operational amplifier (with direct output), 12/6 each.
BP501, Wide band amplifier, 18/- each.
BP521, Logarithmic wide band amp., 14/- each.
BP201C, General purpose amplifier (TO-5 8 lead), (voltage or current amp.), 12/6 each.
I.C. Operational Amplifier with Zener output. Type 701C, Ideal for P.E. Projects. Lead TO-5 case. Full data.

Our price 12/6 each 5 off 11/- each. Large Qty. Prices quoted for.

OTHER MONOLITHIC DEVICES

BP424, Zero voltage switch, 8/6 each.
This device is a monolithic I.C. that acts as combined threshold detector and trigger circuit for controlling a triac. It is designed to pulse the gate of a thyristor at the point of zero supply voltage, and thereby eliminate radio frequency interference when used with resistive loads.
D13D1 Silicon Unilateral switch 10/- each.
A Silicon Planar, monolithic integral circuit having thyristor electrical characteristics, but with an anode gate and a built-in "Zener" diode between gate and cathode.
Full data and application circuits available on request.
FAIRCHILD (U.S.A.) RTUL MICROLOGIC INTEGRATED CIRCUITS
Epoxy case T8-5 lead temp. range 15°C. to 55°C. UL900, Buffer, 10/6 each.
UL914, Dual two-input gate, 10/6 each.
UL923 J-K-flip-flop, 14/- each.
Complete data and circuits for the Fairchild I.C.'s available in booklet form priced 1/6.
MULLARD I.C. AMPLIFIERS
TA A243, Operational amplifier, 70/- each.
TA A263, 18 near AF amplifier, 18/6 each.
TA A293, General purpose amplifier, 21/- each.
CA3020 RCA (U.S.A.) LINEAR INTEGRATED CIRCUITS
Audio Power Amplifier, 30/- each.
Owing to the mass of I.C. printed matter often required by customers in connection with the I.C.'s themselves we ask you to help us in the cost of reproducing this literature by adding 2s. towards same. This is only necessary when a number of different sheets are required.

Sil. trans. suitable for P.E. Organ. Metal TO-18 Eqv. ZTX300 1/- each. Any Qty.

ADI161 NPN ADI162 PNP

MATCHED COMPLEMENTARY PAIRS OF G.E.R.M. POWER TRANSISTORS.
For mains driven output stages of Amplifiers and Radio receivers.
OUR LOWEST PRICE OF 12/6 PER PAIR.

HIGH POWER SILICON PLANAR TRANSISTORS.
TEXAS 25034 NPN TO-3.
VCB100 1c 4A FT. 15M/cs Pwr. 40W hfe(min.)
VEEB 60 Price 15/- each

FREE One 10/- Pack of your own choice free with orders valued £4 or over.

SEMI-CONDUCTOR HANDBOOK (VOLUME 2)
With introduction to basic circuits, registered transistor and diode types, full specification. Eleven languages including English, Dutch, French, German, Swedish, Spanish and Italian. 240 pages of semiconductor information.
Price 28/6. Money refunded if not fully satisfied.

NPN DIFFUSED SILICON PHOTO-DUODIODE TYPE IS701 (2N2175) for Tape Readout, high switching and measurement indicators. 50 V. 250mW. OUR PRICE 10/- EACH. 50 OR OVER 8/6. EACH. FULL DETAILS.

SIL. G.P. DIODES
300mV 30 10/-
25PIV (Min.) 100 25/-
Sub-Min. 500 45
Fully Tested 1,000 £9
Ideal for Organ Builders.

CADMIUM CELLS
ORP60 ORP61 8/- each
ORP12 8/6

FULL RANGE OF ZENER DIODES
VOLTAGE RANGE 2-16V.
400mW (DO-7 Case). 2/6 each
1-5W (Top-Hat) 3/6 each
10W (SO-10 Stud) 5/- each
All fully tested 5% tol. and marked state voltage required.

BRAND NEW TEXAS GERM. TRANSISTORS
Coded and Guaranteed
Pak 10
T1 8 2G3710 EQVT. .. 10/-
T2 8 2G374 OC75 .. 10/-
T3 8 2G3744A OC81 .. 10/-
T4 8 2G381A OC8D .. 10/-
T5 8 2G382T OC82 .. 10/-
T6 8 2G344A OC44 .. 10/-
T7 8 2G345A OC78 .. 10/-
T8 8 2G378 OC78 .. 10/-
T9 8 2G399A 2N1302 .. 10/-
T10 8 2G417 AFI17 .. 10/-

KING OF THE PAKS Unequaled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.	U1	120 Glass Sub-min. General Purpose Germanium Diodes	10/-
	U2	60 Mixed Germanium Transistors AF/RF	10/-
	U3	75 Germanium Gold Bonded Diodes sim. OA5, OA47	10/-
	U4	40 Germanium Transistors like OC81, AC128	10/-
	U5	60 200mA Sub-min. Sil. Diodes	10/-
	U6	40 Silicon Planar Transistors NPN sim. BSY95A, 2N706	10/-
	U7	16 Silicon Rectifiers Top-Hat 750mA up to 1,000V	10/-
	U8	50 Sil. Planar Diodes 250mA OA/200/202	10/-
	U9	20 Mixed Volts 1 watt Zener Diodes	10/-
	U11	30 PNP Silicon Planar Transistors TO-5 sim. 2N1132	10/-
	U13	30 PNP-NPN Sil. Transistors OG200 & 2S104	10/-
	U14	150 Mixed Silicon and Germanium Diodes	10/-
	U15	30 NPN Silicon Planar Transistors TO-5 sim. 2N697	10/-
	U16	10 3-Amp Silicon Rectifiers Stud Type up to 1000 PIV	10/-
	U17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	10/-
	U18	8 6-Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	10/-
	U19	30 Silicon NPN Transistors like BC108	10/-
	U20	12 1.5-amp Silicon Rectifiers Top-Hat up to 1,000 PIV	10/-
	U21	30 A.F. Germanium alloy Transistors 2G300 Series & OC71	10/-
	U22	10 1-amp Glass Min. Silicon Rectifiers High Volts	10/-
	U23	30 Mad's like MAT Series PNP Transistors	10/-
	U24	20 Germanium I-amp Rectifiers GJM up to 300 PIV	10/-
	U25	25 300 Mc/s NPN Silicon Transistors 2N708, BSY27	10/-
	U26	30 Fast Switching Silicon Diodes like IN914 Micro-min	10/-
	U28	Experimenters' Assortment of Integrated Circuits, untested. Gates, Flip Flops, Registers, etc., 8 Assorted Pieces	20/-
	U29	10 1 amp SCR's TO-5 can up to 600 PIV CRS1/25-600	20/-
	U30	15 Plastic Silicon Planar trans. NPN 2N2924-2N2926	10/-
	U31	20 Sil. Planar NPN trans. low noise Amp 2N3707	10/-
	U32	25 Zener diodes 400mW D07 case mixed Volts, 3-18	10/-
	U33	15 Plastic case I-amp Silicon Rectifiers IN-4000 series	10/-
	U34	30 Sil. PNP alloy trans. TO-5 BCY26, 2S302/4	10/-
	U35	25 Sil. Planar trans. PNP TO-18 2N2906	10/-
	U36	25 Sil. Planar NPN trans. TO-5 BFY50/51/52	10/-
	U37	30 Sil. alloy trans. SO-2 PNP, OC200 2S322	10/-
	U38	20 Fast Switching Sil. trans. NPN 400Mc/s 2N3011	10/-
	U39	30 RF Germ. PNP trans. 2N1303/5 TO-5	10/-
	U40	10 Dual trans. 6 lead TO-5 2N2060	10/-
	U41	30 RF Germ. trans. TO-I OC45 NK172	10/-
	U42	10 VHF Germ. PNP trans. TO-I NKT667 AFI17	10/-

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

QUALITY-TESTED PAKS

6 Matched Trans. OC44/45/81/181D	10/-
20 Red Spot AF Trans. PNP	10/-
16 White Spot RF Trans. PNP	10/-
5 Silicon Rects. 3 A 100-400 PIV	10/-
2 10 A Silicon Rects. 100 PIV	10/-
2 OC1 140 Trans. NPN Switching	10/-
1 12 A SCR 100 PIV	10/-
3 Sil. Trans. 25303 PNP	10/-
4 Zener Diodes 240mW 3-12V	10/-
3 200 Mc/s Sil. Trans. NPN BSY26/27	10/-
3 Zener Diodes 1W 33V 5% Tol.	10/-
4 High Current Trans. OC42 Eqv.	10/-
2 Power Transistors I OC26 1 OC35	10/-
5 Silicon Rects., 400 PIV 250mA	10/-
4 OC75 Transistors	10/-
1 Power Transistor OC20 100V	10/-
10 OA202 Sil. Diodes Sub-min.	10/-
2 Low Noise Trans. NPN 2N929/30	10/-
1 Sil. Trans. NPN VCB 100 ZT86	10/-
8 OA81 Diodes	10/-
4 OC72 Transistors	10/-
4 OC77 Transistors	10/-
4 Sil. Rects. 400 PIV 500mA	10/-
5 GET884 Trans. Eqv. OC44	10/-
5 GET883 Trans. Eqv. OC45	10/-
2 2N708 Sil. Trans. 300Mc/s NPN	10/-
3 GT31 LF Low Noise Germ Trans.	10/-
3 IN914 Sil. Diodes 75 PIV 75mA	10/-
8 OA95 Germ. Diodes Sub-min. IN65	10/-
3 NPN Germ. Trans. NK1773 Eqv.	10/-
2 OC22 Power Trans. Germ.	10/-
2 OC25 Power Trans. Germ.	10/-
4 AC128 Trans. PNP High Gain	10/-
4 AC127/128 Comp. pair PNP/NPN	10/-
2 2N1307 PNP Switching Trans.	10/-
7 CG62H Germ. Diodes Eqv. OA71	10/-
3 AF116 Type Trans.	10/-
12 Assorted Germ. Diodes Marked	10/-
4 AC126 Germ. PNP Trans.	10/-
3 Silicon Rects. 100 PIV 750mA	10/-
3 AF117 Trans.	10/-
7 OC81 Type Trans.	10/-
3 OC171 Trans.	10/-
5 2N2926 Sil. Epoxy Trans.	10/-
7 OC71 Type Trans.	10/-
2 2S701 Sil. Trans. Texas	10/-
3 12 Volt Zener 400mW	10/-
2 10 A 600 PIV Sil. Rects. IS45R	10/-
3 BC108 Sil. NPN High Gain Trans.	10/-
1 2N910 NPN Sil. Trans. VCB 100	10/-
2 1000 PIV Sil. Rect. 1.5 A R5310 AF	10/-
3 BSY95A Sil. Trans. NPN 200Mc/s	10/-
3 OC200 Sil. Trans.	10/-
2 GET880 Low Noise Germ. Trans.	10/-
1 AF139 PNP High Freq. Trans.	10/-
3 NPN Trans. 1 ST141 & 2 ST140	10/-
4 Mad's 2 MAT100 & 2 MAT120	10/-
3 Mad's 2 MAT101 & 1 MAT121	10/-
4 OC44 Germ. Trans. AF	10/-
3 AC127 NPN Germ. Trans.	10/-
1 2N3906 Sil. PNP Trans. Motorola	10/-
2 Sil. Power Rects. BYZ13	15/-
1 Sil. Power Trans. NPN 100Mc/s.	15/-
TK201A	15/-
6 Zener Diodes 3-15V Sub-min.	15/-
1 2N1132 PNP Epitaxial Planar Sil.	15/-
3 2N697 Epitaxial Planar Trans. Sil.	15/-
4 Germ. Power Trans. Eqv. OC16	15/-
1 Unijunction Trans. 2N2646	15/-
2 Sil. Trans. 200Mc/s 60Vcb ZT83/84	15/-
1 Tunnel Diode AEX11 1050 Mc/s	15/-
2 2N2712 Sil. Epoxy Planar HFE225	15/-
8 BY100 Type Sil. Rects.	20/-
25 Sil. and Germ. Trans. Mixed, all marked, New	30/-

PRINTED CIRCUITS

EX-COMPUTER
Packed with semiconductor components, 10 boards give a guaranteed 30 trans. and 30 diodes. Our price 10 boards 10/- Plus 2/- P. & P.

GERM. RECTIFIER SINGLE-PHASE BRIDGE. Mullard type. GEX541-B-P. Output Vlt. 48V. Output I.C. 5A. List Price 58/-. OUR PRICE 12/6 EACH.

2N2060 NPN SIL. DUAL TRANS. CODE D1699 TEXAS. OUR PRICE 5/- each.

120 VCB NIXIE DRIVER TRANSISTOR Sim. BSX21 & C407. 2N1892 FULLY TESTED AND CODED ND120. 1-24 3/6 each. TO-5 NPN 25 up 3/- each.

PLEASE NOTE. To avoid any further increased Postal Charges to our Customers and enable us to keep our "By Return Postal service" which is second to none, we have re-organized and streamlined our Despatch Order Department and we now request you to send all your orders together with your remittance, direct to our Warehouse and Despatch Department, postal address: **BI-PAK SEMICONDUCTORS, Despatch Dept., P. O. BOX 6, WARE, HANTS.** Postage and packing still 1/- per order. Minimum order 10/-.

FET'S

2N 3819 10/-
2N 3820 25/-
MPF105 8/-
OCPT1 Type. 8/6

UNIUNCTION

UT46. Eqv. 2N2646, Eqv. TIS43. BEN3000
7/6 EACH
25-99 5/- 100 UP 4/-

TESTED SCR'S

PIV 1A 7A 16A 30A	
25	7/6 30/-
50	7/6 8/6 10/6 35/-
100	8/6 10/- 15/- 45/-
200	12/6 15/- 20/- 55/-
300	15/- 20/- 25/-
400	17/6 25/- 35/- 80/-
500	30/- 40/- 45/- 95/-
600	40/- 50/-

SIL. RECTS. TESTED

PIV 750mA 3A 10A 30A	
50 1/- 2/9 4/3 9/6	
100 1/3 3/3 4/6 15/-	
200 1/9 4/- 4/9 20/-	
300 3/3 4/6 6/6 22/-	
400 2/6 5/6 7/6 25/-	
500 3/- 6/- 8/6 30/-	
600 3/3 6/9 9/- 37/-	
800 3/6 7/6 11/- 40/-	
1000 5/- 9/3 12/6 50/-	
1200 6/6 11/6 15/-	

BI-PAK

500, Chesham House,
150 Regent Street,
LONDON, W.1.

AMATRONIX LTD.

396 Selsdon Road,
South Croydon,
Surrey, CR2 0DE

Mail Order Only. Prompt Service.
Orders over 10/- UK post paid.

GUARANTEED TRANSISTORS

AD161-2	15/-	GET693	1/3	2N3055	16/6
AF239	10/-	HK041	2/6	2N3707	4/-
B5000G	11/3	HK101	2/-	2N3794	3/-
BD121	18/-	HK601	2/6	2N3983	5/8
BC107B	3/-	IS44	1/4	2N4058	4/6
BC168B	2/3	MEM554C	15/-	2N4285	3/-
BC168C	2/3	SF115	3/-	2N4289	3/-
BC169C	2/6	TIS18	7/-	2N4291	3/-
BF167	5/3	TIS60M	4/8	2N4292	3/-
BF178	9/-	TIS61M	4/11	2SB187	2/-
BF224	4/-	2N706	2/7	2SB405	5/-
BFY51	4/-	2N2926G	2/6	2SD72	5/-
		40468A	7/6		

RECTIFIERS:

1/- Submin. Selenium Bridge, 30Vrms, 150mA
800piv, 500mA Si, IS557, 3/-; 50piv, 100mA,
dc, 3/6; Contact-cooled Sel. Bridge, 30Vrms,
700mA dc, 6/-; Silicon Bridge, 80Vrms, 1Adc,
10/-.

INTEGRATED CIRCUITS

CA3011, 18/-; CA3020, 28/-; TAA263, 16/8;
TAA320, 15/-; TAB101, 21/-; PA234, 24/-.
ALL WITH DATA SHEETS.



MINI MAINS TRANSFORMERS

1 x 1 x 1 1/4 in., normal mains primaries.
Eagle MT6, 6-0-6V, 100mA, 13/6.
Eagle MT12, 12-0-12V, 50mA, 13/6.
Osmor MT9, 9-0-9V, 80mA, 12/6.
Supplied with Gen Sheet showing how 6-60V
may be obtained.

MINI MAINS PACK (as shown). All parts, 17/6

COMPONENT KITS

NEW! In response to many requests, we have designed an amplifier circuit for use with low-impedance speakers. The new AX5 delivers 3W to 3Ω and uses the well-tried arrangement of the AX4, plus one extra stage for higher sensitivity and input impedance.

- * 3W rms to 3Ω. Higher loads usable
- * -3dB at 50Hz and 20kHz
- * 30mV in 300k for full output

The AX5 needs a 12V, 500mA supply and will work from up to 15V. Component Kit with Data Sheet 39/-.

AND ALSO OUR REGULAR PACKS—RELIABLE AND EFFICIENT:

- AX2 Mini 9V Amplifier for any load. Still only 12/6.
- AX3 9V Amplifier, 800mW to 8Ω. Still only 22/6.
- AX4 18-24V Amplifier, up to 5W in 8Ω. 4W in 15Ω. Still only 30/-.
- AX9 TRF Receiver Kit (printed circuit). Still only 45/-.

CAPACITORS

Polystyrene, 160V, small, close tolerance.
6d. each: 12, 15, 39pF, ± 1pF
9d. each: 56, 82, 150, 270, 390, 560,
680pF, ± 2 1/2%
1/- each: 3300pF (.0033uF), 10,000pF
(.01uF), ± 2 1/2%
1/3 each: 22,000pF (.022uF, 22nF), ± 2 1/2%
Min. Metallised Polyester, 250V:
.01uF, 8d.; 0.1uF, 10d.; 0.22uF, 1/-.
J. B. Tuning Capacitors: 300pF Dilemin,
10/-; 4-gang 3-17pF FM type, built-in slow
motion drive, 17/-.

RESISTORS

Carbon Film, 1/4W, miniature, low noise.
10, 12, 15, 18, 22, 27, 33, 39, 47, 56,
68, 82Ω and so on to 10M. Tol. ± 5% to
1M, 10% above 1M. All 3d. each.
Carbon Skeleton Presets. Submin., vertical,
linear, 100mW. 50, 150, 500Ω and so on
to 1.5M. Egen Type 467, 1/6 each.
Volume Control, 10K log. with d.p. switch
and long aluminium spindle with flat.
Standard size, Egen. 5/6 each.

R. F. CHOKES. Repanco: CH1, 2.5mH, 2/6;
CH2, 5mH, 3/-; CH3, 7.5mH, 3/-; CH4,
10mH, 3/-; CH5, 1.5mH, 2/6. All small,
ferrite-cored.

FERRITE RODS: 4in. or 4 1/2in. x 1/2in., wound
for MW (300pF), 5/-; unwound, 2/-; oval,
unwound, 2 x 1/2 x 1/2in., with data, 2/6.

TRANSFORMERS, MINI. A.F.: Eagle
LT700, 1200Ω c.t. to 3Ω, 200mW, 5/-;
Repanco TT47 driver for single ended push-
pull, 4.5 to (1) + (1), 6/-.

TELESCOPIC AERIAL: 7 1/2in. opening to
47in., 9/-.

BATTERY HOLDER BH2 for two 1.5V pen
cells, with snap connector, 2/6.

EARPIECES, all 3.5mm plugged, crystal,
4/9; magnetic, 8Ω, 2/6; 50Ω, 3/-.

Fast Mail Order for the Amateur Radio Enthusiast!

AERIAL EQUIPMENT

TWIN FEEDER. 300 ohm twin ribbon
feeder similar K25, 8d. per yard. 75
ohm twin feeder, 6d. per yard. Post on
above feeders, 2/- any length.

COPPER WIRE. 14G, H/D, 140ft.
30/-; 70ft., 16/-; Post and packing 3/3.
Lengths are approx. only, actually sold
by weight.

FEEDER SPREADERS. 6" Ceramic type
F.S., 10d. each. Postage 2/6 up to 12.

CERAMIC CENTRE PIECE for dipoles
Type AT, 1/6 each. P. & P. 1/-.

AERIAL INSULATORS. Ribbed ceramic,
2/6 each. Short stick, 1/- each. Egg, 6d.
all plus postage.

2 METRE BEAM, 5 ELEMENT W.S.
YAGI. Complete in box with 1" to
2 1/2" masthead bracket. Price: £3 7s.
Carriage 5/-.


SUPER AERIAL, 70/80 ohm coax,
300 watt very low loss, 2/3 per yard. 50
ohm 300 watt 2/6 per yd. P. & P. 2/6.

TOUGH POLYTHENE LINE, type MLI
(100lb.), 2d. per yd. or 12/6 per 100
yds. Type ML2 (220lb.), 4d. per yd. or
25/- per 100 yds., ML4 (400lb.), 6d.
per yd. Ideal for Guys, L.W. Supports,
Halyards, etc. Postage 1/6 on all line.

"RAYMART" SUPER BANDCHECKER

This instrument is an adaptation of the simple Absorption type wavemeter and by utilising a diode and a sensitive meter its application is considerably widened. In addition to the familiar use of checking output frequency the increased sensitivity enables it to be used for many other applications such as:-

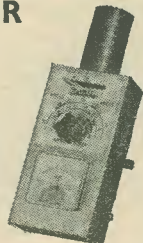- Checking of Multiplier stages in Multi Stage transmitters.
 - Neutralising R.F. Amplifiers.
 - Standing waves on coax Cables.
 - R.F. pick up in wiring.
 - R.F. pick up in microphone leads, etc.
- Price £4.4.0 (3.5-35 Mc/s)
or, including 160 Metre Band £4.10.0
p. & p. 3/-



AERIAL DIPOLE KITS

TYPE RD1 comprises:

- 2 x 70ft. 14G copper or 140ft. stranded (as preferred)
 - 1—AT Centre Piece
 - 2—Ribbed Insulators
 - 70ft. 300 ohm Ribbon Feeder
- 52/6 P. & P. 4/6

TYPE RD2 as above, but with:

- 12—FS 6in. Ceramic Spreaders
 - 140ft. Flexible Feedwire
- £3 10s. P. & P. 4/6

TYPE RE3 comprises:

- 70ft. Copper Wire (stranded or solid)
 - 1—T piece
 - 2—Ribbed Insulators
 - 50ft. of 75 ohm Balanced Twin
- 35s. P. & P. 3/6

The Widest Range of Components in the Midlands



★ HIRE PURCHASE
★ PART EXCHANGE

CHAS. H. **YOUNG** LTD.

At your service G2AK, G3LAY, G3VVF
Please print your address. No C.O.D. under £1.

'phone 021-236 1635

170-172 Corporation Street,
Birmingham 4

Now! A FAST EASY WAY TO LEARN BASIC RADIO AND ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—but you learn the *practical* way.

Now you can learn basic Radio and Electronics at home—the *fast*, modern way. You can give yourself the essential technical "know-how" sooner than you would have thought possible—read circuits, assemble standard components, experiment, build . . . and enjoy every moment of it. B.I.E.T.'s Simplified Study Method and the remarkable new **TECHNATRON** Self-Build Outfit take the mystery out of the subject—make learning *easy and interesting*.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

and what's more, **YOU'LL UNDERSTAND EXACTLY WHAT YOU ARE DOING.** The Technatron Outfit contains everything you need, from tools to transistors . . . even a versatile Multimeter which we teach you how to use. You need only a little of your spare time, the cost is surprisingly low and the fee may be paid by convenient monthly instalments. You can use the equipment again and again—and it remains your own property.

You **LEARN**—but it's as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build—and it's a good one—is really a bonus; this is first and last a *teaching* Course. But the training is as rewarding and interesting as any hobby. It could be the springboard for a career in Radio and Electronics or provide a great new, spare-time interest.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. Bite-size lessons—wonderfully clear and easy to understand, practical projects from a burglar-alarm to a sophisticated Radio set . . . here's your chance to master basic Radio and Electronics, even if you think you're a "non-technical" type. And, if you want to carry on to more advanced work, B.I.E.T. has a fine range of Courses up to A.M.I.E.R.E. and City and Guilds standards.

Send now for free 164-page book. Like to know more about this intriguing new way to learn Radio and Electronics? Fill in the coupon and post it today. We'll send you full details and a 164-page book —"ENGINEERING OPPORTUNITIES"—Free and without any obligation.



BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. 370B, Aldermaston Court, Aldermaston, Berkshire.

To: B.I.E.T., Dept. 370B, ALDERMASTON COURT, ALDERMASTON, BERKS.

I would like to know more about your Practical Radio & Electronics Course. Please send me full details and FREE 164-page book.

name

address

age

POST THIS COUPON NOW!


JACKSON

the big name in **PRECISION** components



The Latest Transmitter Capacitor Type TX 5

Variable Capacitor

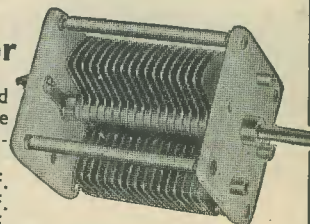

Ceramic insulation. End area $2\frac{1}{2} \times 2\frac{1}{2}$ ". Heavy gauge aluminium vanes with radiused edges.

.128" air gap up to 150pF.

.064" air gap up to 500pF.

.036" air gap up to 1000pF.

Designed for use in radio transmitting and power oscillators. Split stator models also available to order.

Write for details



JACKSON BROS. (London) LIMITED

Dept. RC, KINGSWAY-WADDON, CROYDON, CR9 4DG
Phone Croydon 2754-5 (01-688). Grams Walfilco, Croydon. U.S. Office: M. Swedgal, 258 Broadway, N. York. N.Y. 10007.



Hobbyists, Radio Technicians, here's the Valve Voltmeter and Transistor Tester for **YOU** — reliability, dependability, value! Also models for leisure entertainment, Hi-Fi, SW listening and all branches of Industry and Education.

SAVE TODAY — THE HEATHKIT WAY

Please show me how I can **SAVE MONEY** with the **HEATHKIT WAY**.
To: DAYSTROM LTD., Dept. RC-9
Gloucester, England
Name.....
Address.....

DENCO (CLACTON) LIMITED

355-7-9 OLD ROAD, CLACTON-ON-SEA, ESSEX

Our components are chosen by Technical Authors and Constructors throughout the World for their performance and reliability, every coil being inspected twice, plus a final test and near spot-on alignment as a final check.

Our General Catalogue showing full product range	2s. 6d.
DTB4 Transistor & Valve circuitry for D.P. Coils	2s. 6d.
DTB9 Valve Type Coil Pack Application circuitry	2s. 6d.
MD.1 Decoder Circuitry for Stereo Reception	4s. 0d.

All post paid, but please enclose S.A.E. with all other requests in the interests of retaining lowest possible prices to actual consumers.

THE MODERN BOOK CO

The Hi-Fi and Tape Recorder Handbook by G. J. King. 40s. *Postage 2s.*

Servicing With The Oscilloscope by G. J. King. 28s. *Postage 1s.*

Solid State Hobby Circuits Manual by R.C.A. 17s. 6d. *Postage 1s.*

Transistors For Technical Colleges by L. Barnes. 25s. *Postage 1s.*

Beginner's Guide to Radio Control by R. H. Warring. 18s. 6d. *Postage 1s.*

TV Fault Finding 405 625 Lines by J. R. Davies. 8s. 6d. *Postage 6d.*

Colour Television Pal System by G. N. Patchett. 40s. *Postage 1s.*

Electronics & Radio An Introduction by M. Nelkon & H. I. Humphreys. 30s. *Postage 1s. 6d.*

World Radio TV Handbook 1969. 42s. *Postage 1s.*

Radio Communication Handbook by R.S.G.B. 63s. *Postage 4s. 6d.*

Practical Integrated Circuits by A. J. McEvoy. 18s. *Postage 1s.*

Television Engineers' Pocket Book by J. P. Hawker. 21s. *Postage 1s.*

Electronics Made Simple by Henry Jacobowitz. 15s. *Postage 1s.*

Electronics in Photography by Byron G. Wels. 30s. *Postage 1s.*

Electronic Computers Made Simple by Henry Jacobowitz. 10s. *Postage 1s.*

Record Changers How They Work by Louis M. Dezettel. 28s. *Postage 1s.*

Novel Electronic Circuits by John Potter Shields. 28s. *Postage 1s.*

VHF-UHF Manual by G. R. Jessop. 21s. *Postage 1s.*

Rapid Servicing of Transistor Equipment by Gordon J. King. 30s. *Postage 1s.*


Hi-Fi in The Home by John Crabbe. 40s. *Postage 1s. 6d.*

We have the Finest Selection of English and American Radio Books in the Country

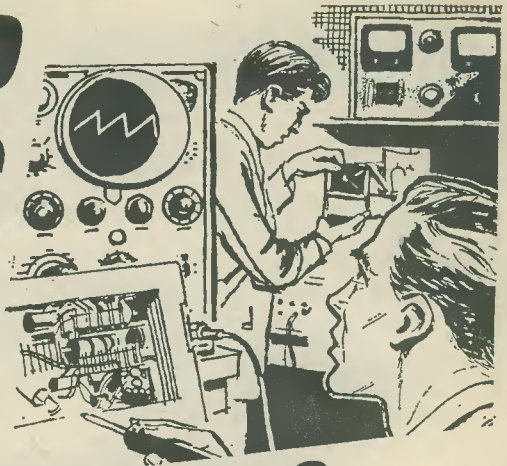19-21 PRAED STREET (Dept RC) LONDON W2

Telephone PADdington 4185

Speed up SERVICING -step up PROFITS with RADIO & TV SERVICING



This big RADIO & TELEVISION SERVICING repair library will help you speed up your repair work and increase your earnings. Packed with 2,657 circuits, component layout diagrams, printed panel diagrams, tables and waveform graphs, it covers all the popular 1965-1969 TV's, Radios, Radiograms, Car Radios, Record Players and Tape Recorders—including the latest data on COLOUR TV. Four volumes handsomely bound in maroon and gold. 2,180 pages written by a team of expert Research Engineers—there's no other publication like it! Speeds up repair work year after year. Examine this latest edition at home free for a week. Send no money—just post coupon today—there's absolutely no obligation to buy.

**1000 POPULAR MODELS
from 1969 right back to 1965**

Servicing data for all these makes

Aiwa, Alba, Baird, Beogram, Beolit, Blaupunkt, B.R.C., Bush, Carousel, Cossor, Dansette, Decca, Defiant, Dynaport, Dynatron, Eddystone, Ekco, Elizabethan, Ever Ready, Ferguson, Ferranti, Fidelity, G.E.C., Grundig, Hacker, H.M.V., Hitachi, Invicta, K.B., Klinger, Kolster-Brandes, Lowe-Opta, McMichael, Marconiphone, Master-Radio, Monogram, Motorola, Murphy, National, Newmatic, Pam, Perdio, Peto-Scott, Philco, Philips, Portadyne, Pye, Radiomobile, Radionette, R.G.D., Regentone, Roberts' Radio, Robux, Sanyo, Sharp, Smith's Radiomobile, Sobell, Sony, Standard, S.T.C., Stella, Stereosound, Telefunken, Teletron, Thorn, Trans Arena, Ultra, Unitra, Van Der Molen, World Radio

**RADIOS • RADIOGRAMS • CAR
RADIOS • RECORD PLAYERS
TAPE RECORDERS • TV'S**

including

COLOUR TV

All aspects of Colour TV are covered—from installation to static convergence. The vital information in this section makes this repair library invaluable to the Service Engineer.

**SENT TO YOU BY POST ON
7 DAYS FREE TRIAL**

To: Buckingham Press Ltd., P.O. Box 14, Gatehouse Rd., Aylesbury, Bucks. Please send RADIO & TV SERVICING—4 volumes, without obligation to buy if you accept my application. I will return the books in 8 days or post:

Tick Full cash price of £16, or
here 20/- dep. and 16 monthly payments of 20/-, paying £17 in all.
If under 21 your father must fill in coupon.

Full Name
(BLOCK LETTERS PLEASE)

Address

County

Occupation

Signature

{ Mr.
Mrs.
Miss

Please tick (✓) here

The address on left is

My/our property

Rented

unfurnished

Furnished accom

Temporary

address

If none of the above

please answer here

RV4/4088



From Pitman

Transistor Electronic Organs for the Amateur

Alan Douglas & S. Astley
Second Edition 20s. net

This second edition leaves the basic tonal design of the organ unaltered but the authors have exploited many of the changes in transistor circuitry that have taken place since the original organ was built and have corrected errors and omissions.

Radio Communication

J. H. Reyner & P. J. Reyner
Second Edition 60s. net Paperback 45s. net

Here is a book covering the work required for the City and Guilds Telecommunications Technicians Certificate (Radio Subjects) to final year.

Sir Isaac Pitman & Sons Ltd.
Pitman Publishing

Radio Upkeep and Repairs

A. T. Witts
Ninth Edition 20s. net

A practical handbook on servicing principles and receiver maintenance for the man who is training to be a radio mechanic, for the service man wanting a handy reference, and for the keen amateur. The book is full of valuable hints and tips on how to locate faults and how to correct them.

Worked Radio Calculations

A. T. Witts
Third Edition 16s. net


Graded practical examples for Radio Service Engineers, Wireless Operators, and students of radio.

build the

RM 'SINGLET'

SUPERHET RECEIVER

for RADIO CONTROL!

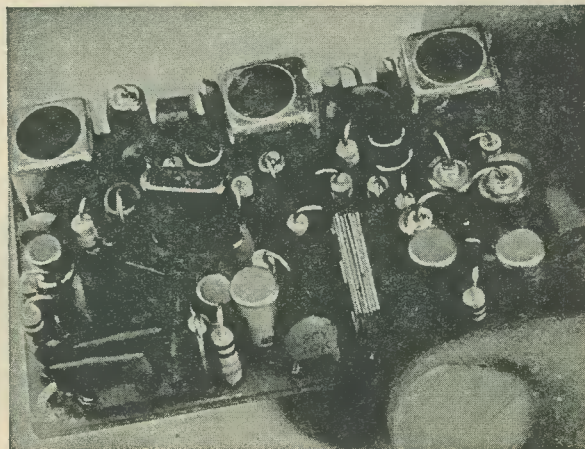

SPECIAL OFFER: Two issues of "RADIO MODELLER"
containing fully illustrated constructional features
both for ONLY 5/- (normally 3/6 each)

Also available: reprints of suitable transmitter - 1/- extra

Send P.O. to: "RADIO MODELLER" (Dept. SO),
64 WELLINGTON ROAD, HAMPTON HILL, MIDDLESEX

BI-PRE-PAK LIMITED

FULLY TESTED AND MARKED

AC107	3/-	OC170	3/-
AC126	2/6	OC171	4/-
AC127	2/6	OC200	3/6
AC128	2/6	OC201	7/-
AC176	5/-	2G301	2/6
ACY17	3/-	2G303	2/6
AF114	4/-	2N711	10/-
AF115	3/6	2N1302-3	4/-
AF116	3/6	2N1304-5	5/-
AC117	3/6	2N1306-7	6/-
AF186	10/-	2N1308-9	8/-
AF139	10/-	2N3844A	5/-
AF239	12/6	Power Transistors	
BFY50	4/-	OC20	10/-
BSY25	7/6	OC23	10/-
BSY26	3/-	OC25	8/-
BSY27	3/-	OC26	5/-
BSY28	3/-	OC28	7/6
BSY29	3/-	OC35	5/-
BSY95A	3/-	OC36	7/6
OC41	2/6	AD149	10/-
OC44	1/11	AUY10	30/-
OC45	1/9	2N3055	15/-
OC71	2/6	Diodes	
OC72	2/6	AAY42	2/-
OC73	3/6	OA95	2/-
OC81	2/6	OA70	1/9
OC81D	2/6	OA79	1/9
OC83	4/-	OA81	1/9
OC139	2/6	IN914	1/6
OC140	3/6		

FREE! Packs of your own choice up to the value of 10/- with orders over £4.

TRY OUR X PACKS FOR UNEQUALLED VALUE

XA PAK

Germanium PNP type transistors, equivalents to a large part of the OC range, i.e. 44, 45, 71, 72, 81, etc.

PRICE £5 PER 1,000
POST & PACKING 4/6 U.K.

XB PAK

Silicon TO-18 CAN type transistors NPN/PNP mixed lots, with equivalents to OC200-1, 2N706a, BSY27/29, BSY95A.

PRICE £4.5.0 PER 500 £8 PER 1,000
POST & PACKING 2/6 U.K.

XC PAK

Silicon diodes miniature glass types, finished black with polarity marked, equivalents to OA200, OA202, BAY31-39 and DK10, etc.

PRICE £4.10.0 PER 1,000
POST & PACKING 2/6 U.K.

ALL THE ABOVE UNTESTED PACKS HAVE AN AVERAGE OF 75% OR MORE GOOD SEMI-CONDUCTORS. FREE PACKS SUPPLIED WITH THESE ORDERS. ORDERS MUST NOT BE LESS THAN THE MINIMUM AMOUNTS QUOTED PER PACK.

NEW TESTED & GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries. Inc. book of instructions.	10/-
B77	2	AD161-AD162 NPN/PNP Trans. Comp. output. Pair	10/-
B79	4	1N4007 Sil. Rec. Diodes. 1000 Piv. 1 amp Miniature.	10/-
B81	10	Reed Switches. Mixed types large and small.	10/-
B89	2	5SP5 Light Sensitive Cells. Light res. 400Ω, Dark 1MΩ.	10/-
B91	8	NKT163/164 PNP Germ. to -5. Equiv. to OC44, OC45.	10/-
B92	4	NPN Sil. Trans. A06=BSX 20, 2N2369, 500 MHz, 360 mW.	10/-
B93	5	GET113 Trans. equivalent to ACY17-21 PNP Germ.	10/-
B94	6	NPN Sil. Planar Epitaxial Trans. CS4 similar to BSY38 or BC108.	10/-
B96	5	2N3136 PNP Sil. Trans. TO-18. HFE100-300. IC.600mA. 200 MHz.	10/-
B98	10	XB112 & XB102 equiv. to AC126, AC156, OC81/2, OC71/2, NKT271, etc.	10/-
B99	200	Capacitors, Electrolytics, Paper, Silver Mica, etc. Postage on this pak 2/6.	10/-
H4	250	Mixed Resistors. Post & packing 2/-.	10/-

HUGE CLEARANCE OF UHF/VHF TUNER UNITS REJECTS Stocks Almost Exhausted! Place Your Orders NOW!!! Fantastic Transistor Value!

TU.2. Containing 2 AF186's & 2 AF178's PRICE 10/- each Unit
TU.3. Containing 2 AF186's & 2 AF178's PLUS Waveband Slider Switch PRICE 12/6 each Unit

P & P 2/6 each Unit. All the Units have many other components, e.g. Capacitors, Resistors, Coils and Tuning Condensers, etc. Connection data supplied with all Tuner Units.

Return of the unbeatable P.I Pak.

Now greater value than ever

Full of short lead semiconductors and electronic components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP and NPN, and a host of diodes and rectifiers. Mounted on printed circuit panels. Identification chart supplied to give some information on the transistors.

P.I PLEASE ASK FOR PAK P.I ONLY 10/-
2/- P & P on this Pak.

MAKE A REV. COUNTER for your Car. The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a perfectly linear and accurate rev. counter for 20/- each any car. State 4 or 6 cylinder.

FREE CATALOGUE AND LISTS for:- ZENER DIODES TRANSISTORS, RECTIFIERS FULL PRE-PAK LISTS & SUBSTITUTION CHART

MINIMUM ORDER 10/-. CASH WITH ORDER PLEASE. Add 1/- post and packing per order. OVERSEAS ADD EXTRA FOR AIRMAIL.

MULLARD DATA BOOK

Semiconductor & Valve Data & equivalents. 3/6 EACH
Postage 6d.

NEW UNMARKED UNTESTED PAKS

B78	12	Integrated Circuits, Data & Circuits of types, supplied with orders.	10/-
B80	8	Dual Trans. Matched O/P pairs NPN. Sil. in TO-5 can.	10/-
B82	10	OC45, OC810 & OC81 Trans. Mullard glass type.	10/-
B83	200	Trans. Makers rejects. NPN/PNP. Sil. & Germ.	10/-
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202.	10/-
B66	150	High quality Germ. Diodes. Min. glass type.	10/-
B86	50	Sil. Diodes sub. min. IN914 & IN916 types.	10/-
B87	100	Germ. PNP Trans. equiv. to OC44, OC45, OC81, etc.	10/-
B88	50	Sil. Trans. NPN, PNP. equivalent to OC200/1, 2N706A, BSY95A, etc.	10/-
B60	10	7 Watt Zener Diodes. Mixed voltages.	10/-
H5	16	1 Amp. Plastic Diodes. 50-1000 Volts.	10/-
H6	40	250mW. Zener Diodes DO-7 min. Glass Type.	10/-



SPECIAL OFFER
Germanium Bridge Rectifiers
Mullard Type GEXS41-BP
48 volts, 5 amps
List Price 58/-
OUR PRICE 10/-

FREE! A WRITTEN GUARANTEE WITH ALL OUR TESTED SEMICONDUCTORS

BI-PRE-PAK LTD DEPT. C, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344

There are Catalogues AND Catalogues!

Ours is THIS kind...



... the kind that's

INDEXED THOROUGHLY For instance "Aerials Telescopic" under "A" and "Telescopic Aerials" under "T".

PLANNED LOGICALLY Having over 8,000 items it needs to be! Components are listed alphabetically in logical sections.

ILLUSTRATED PROFUSELY Over 1,800 pictures. Some are photos some are drawings, but all clearly show the features you look for.

PRINTED CLEARLY No eyestrain here. Large easy-to-read type, on 330 sensible-size pages—9½" x 7½" (ignore our artist's enthusiastic exaggeration!)

BOUND SECURELY This catalogue is bound to receive long and frequent use. Glossy laminated covers don't show fingerprints, don't tear easily.

PRICED REASONABLY Just 8/6d. plus 3/6d. for post, packing and insurance. Folk tell us it's worth twice the price! We quite agree.



Yes — the *Home Radio Catalogue* is a pleasure to buy and to use.

By the way, every Catalogue contains six Vouchers, each worth 1/- when used as directed, and we supply free a 30-page Price Supplement, a Bookmark giving electronic abbreviations and, of course, an Order Form.

POST THIS COUPON NOW
with cheque or P.O. for 12/-



Please write your Name and Address in block capitals

Name _____

Address _____



**WINGS
APPEAL**
SEPT. 15th-20th

GIVE FOR
THOSE WHO
GAVE

HOME RADIO (COMPONENTS) LTD., Dept. RC,
234-240 London Road, Mitcham, Surrey CR4 3HD.

The price of 12/- applies only to catalogues purchased by customers residing in the U.K.

THE Radio Constructor



Incorporating THE RADIO AMATEUR

SEPTEMBER 1969

Vol. 23 No. 2

CONTENTS

Published Monthly (1st of Month)
First Published 1947

Editorial and Advertising Offices
57 MAIDA VALE LONDON W9

Telephone
01-286 6141

Telegrams
Databux, London

© Data Publications Ltd., 1969. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription 42s. (U.S.A. and Canada \$5) including postage. Remittances should be made payable to "Data Publications Ltd.". Overseas readers please pay by cheque or International Money Order.

Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. Queries should be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

Production.—Letterpress.

Battery Saver for Bedside Radios (Suggested Circuit No. 226)	74
QSX	77
News and Comment	78
The Radio Constructor's 'Easy-View' Diary (Fourth Quarter 1969)	80
Suggestions for your 'Easy-View' Diary	81
'Milliwatt' Silicon Reflex T.R.F. Receiver	82
Double Speaker Unit for the SWL	87
Nomogram for Parallel Resistance or Series Capacitance	90
Alarm for Mains Radios	92
First World Dx Convention	94
Solid State D.C. Voltmeter and A.C. Millivoltmeter	96
Can Anyone Help?	104
Equipment Review — The Eddystone EC958 Receiver	106
The Q-Multiplier (Understanding Radio)	107
Courses of Instruction	111
In Your Workshop	112
Radio Topics	118
Radio Constructor's Data Sheet No. 30 (Square Roots of Numbers)	iii

OCTOBER ISSUE WILL BE PUBLISHED
ON OCTOBER 1st


Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London, W.9.

The Radio Constructor is printed by Kent Paper Company Ltd, London and Ashford, Kent.

SEPTEMBER 1969

BATTERY SAVER FOR BEDSIDE RADIOS

by G. A. FRENCH

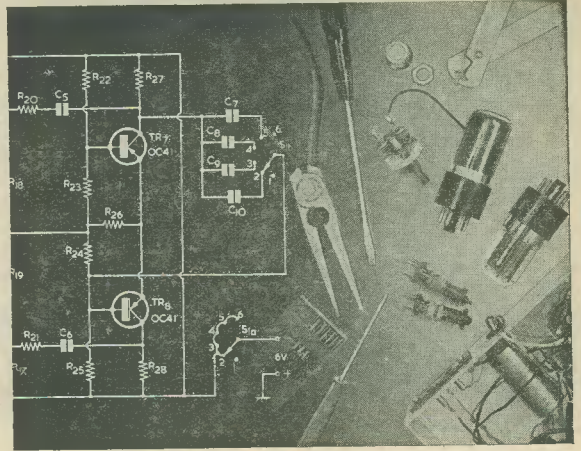

IT IS PLEASANT TO HAVE A TRANSISTOR radio in one's bedroom, since it is then possible to settle down to sleep against a background of radio music. How often does it happen, however, that one wakes up on the following morning to find that the transistor radio is still playing, having been left switched on all night!

This month's "Suggested Circuit" describes a simple delayed switching circuit which may be added to any standard 9-volt transistor radio. When switched in, the delay circuit allows the transistor radio to continue running for about three-quarters

of an hour, after which it turns the receiver off. It is possible, in consequence, to switch off the bedroom light and drift off into sleep whilst the radio is still playing, having the comforting knowledge that it will switch itself off automatically when the delay period has elapsed.

The delay circuit has the advantage that only a few components are required, but the disadvantage that one of these is a rather bulky electrolytic capacitor. As a result, it may not be possible to fit the circuit into very small receivers having compact internal layouts. If, never-

theless, a receiver of this type were adapted to run from an external battery when it is used in the bedroom, the delay circuit could easily be incorporated in a small unit with the external battery.

As a final introductory point it should be mentioned that the delay circuit does not employ a relay. The switching action is carried out by a transistor.

SWITCHING CIRCUIT

The switch-off delay circuit appears in Fig. 1, and it is intended for installation between the on-off switch of the receiver and the remainder of the receiver circuits. Transistors TR1 and TR2 are coupled together in a manner which allows a very high level of current gain to be achieved. The writer has used the same transistor combination in an earlier "Suggested Circuit"*, in which it was similarly employed for controlling the power supply to a transistor radio. An important feature of the circuit is the choice of a BC168C for TR2, this transistor having the extremely high gain figure of 450 to 900. (The BC168C is available from Amatronics, Ltd.). In the present instance it is merely necessary to point out that TR1 is held hard on for load currents of up to 50mA flowing between its emitter and collector when a current of slightly more than 1µA flows to the base of TR2. Thus, provided that the requisite base current flows in TR2, TR1 allows full battery voltage (less a fraction of a volt dropped in the transistor) to be applied to the circuits of the transistor radio.

In Fig. 1, switch S1(a) (b) will be normally in the "Out" position S1(a) then causes the positive supply

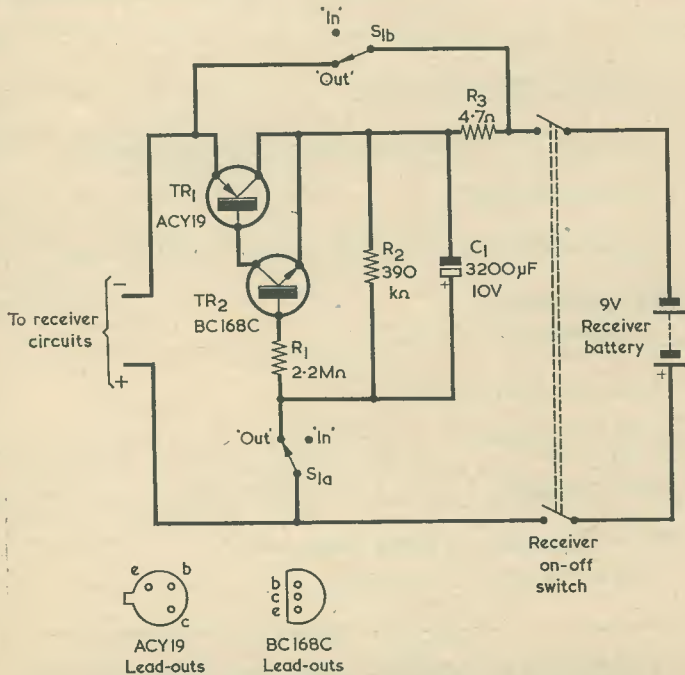


Fig. 1. The delayed switch-off circuit. This is incorporated immediately after the on-off switch of the associated receiver

* "Suggested Circuit No. 222 — Light Operated Radio Switch", *The Radio Constructor*, May, 1969.

line to be applied to the lower ends of R1 and R2, and to the positive terminal of C1. When the receiver is switched on C1 is, in consequence, charged to the full 9 volts provided by the battery. Also, S1(b) short-circuits TR1 and R3, thereby eliminating the small voltage drop in TR1 which occurs when it is conducting, plus that in R3. The receiver is operated in the usual fashion, and is switched on and off by its own on-off switch.

When it is desired to introduce the delayed switch-off facility the receiver on-off switch is left in the closed position and S1(a) (b) is thrown to "In". The short-circuit is taken off TR1 and R3, and the battery supply is now fed to the receiver circuits by way of these two components. A base current well in excess of $1\mu\text{A}$ flows to TR2 via R1, causing TR1 to be hard on. Since TR1 is conductive, the receiver continues to operate. At the same time the positive terminal of C1 is disconnected, by S1(a), from the positive supply rail. C1 now commences to discharge, the discharge currents flowing through R1 and the base-emitter junction of TR2, through R2, and through the internal leakage resistance of the capacitor itself. Due to the very high current gain in TR1 and TR2, the initial discharge current flowing to the base of TR2 via R1 is sufficient to maintain TR1 hard on, and the controlled receiver continues to play. After a period the voltage across C1 falls to a level at which the consequently reduced discharge current in R1 cannot maintain TR1 fully conductive, and the supply voltage applied to the receiver circuits commences to fall. When this supply voltage is insufficient to allow the receiver oscillator to function the set becomes silent. The supply voltage continues to fall until it reaches a negligibly low value. The current finally passed by TR1 is transistor leakage current only.

The receiver has therefore been initially silenced, after which the current drawn from the battery has further reduced, falling eventually to an insignificantly small level. The circuit has thus fulfilled its function and it remains in this state until S1(a) (b) is returned to the "Out" position. The set then proceeds to operate in normal manner. When desired, another delayed switch-off cycle can be initiated at any time by once more setting S1(a) (b) to the "In" position.

CAPACITOR DISCHARGE

As will have been gathered from the description of circuit operation just given, the delay circuit enables very nearly full supply voltage to be applied to the receiver circuits until the end of the delay period. The delay circuit does not then,

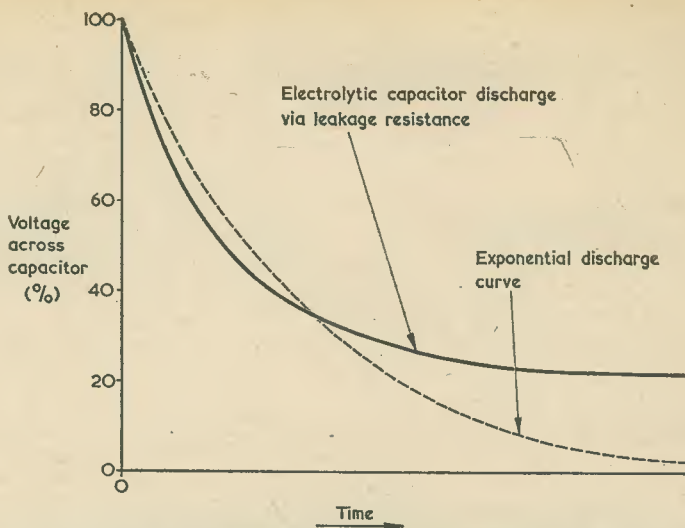


Fig. 2. The solid line shows a representative discharge curve for an electrolytic capacitor discharging into its own leakage resistance. The standard exponential discharge curve is given in dashed line

however, turn off the supply instantaneously but allows the current passed by TR1, and hence the voltage across the receiver supply rails, to fall gradually.

It is desirable that the time during which the current passed by TR1 is reducing gradually should be kept as short as possible, because this represents a period when battery current is wasted since it is not being used to provide an audible output from the receiver. A further factor, which has not been mentioned, is that it is preferable, in order to save cost and space, to keep the value of delay capacitor C1 as low as possible consistent with the achievement of a long delay period. These requirements are conflicting, as will next be explained.

The longest possible discharge time of which C1 is capable is provided when it is allowed to discharge through its own leakage resistance, with no external resistor connected across it. A large-value electrolytic capacitor can take a surprisingly long time to discharge completely under these conditions. Unfortunately, the leakage resistance of an electrolytic capacitor is not constant, but increases as the voltage across the plates reduces, resulting in a voltage/time discharge curve of the type shown in solid line in Fig. 2. As may be seen here, the voltage across the plates of the discharging capacitor drops relatively rapidly at first but then falls very much more slowly as, at the reduced voltage, the leakage resistance increases. Also shown in Fig. 2, in dashed line, is the normal exponential discharge curve for a capacitor and resistor in parallel. It will be seen that the electrolytic

capacitor discharging through its own leakage resistance "lingers" at the lower voltages for a much longer period than does a capacitor obeying the exponential discharge law.

Returning to Fig. 1, if R2 were omitted and C1 allowed to discharge mainly through its own leakage resistance, very long switch-off delays could be achieved with quite low values in C1. However, after the voltage across C1 had dropped to the level at which TR1 ceased to be fully conductive the subsequent fall in C1 voltage would be relatively very slow and the period during which TR1 remained partly conductive very much longer. The advantage of using a small value in C1 would be completely outweighed by excessive waste of battery current after the controlled receiver had been silenced.

A compromise is reached in the present circuit by using a somewhat large value for C1, and by shunting it with the fairly high value resistor R2. C1 then discharges mainly through R2 and only partly through its own leakage resistance, thereby approaching more closely the true exponential voltage/time discharge curve.

To assess the performance given by the combinations of C1 and R2, the output of the switching circuit (i.e. the two circuit points at the left of Fig. 1) was coupled to a 300Ω resistor instead of to the circuits of a transistor receiver. A 300Ω resistor draws a current of 30mA at 9 volts and is reasonably representative of a transistor receiver playing at a fairly high output level. Fig. 3 shows the results obtained with the prototype circuit, illustrating that the voltage across

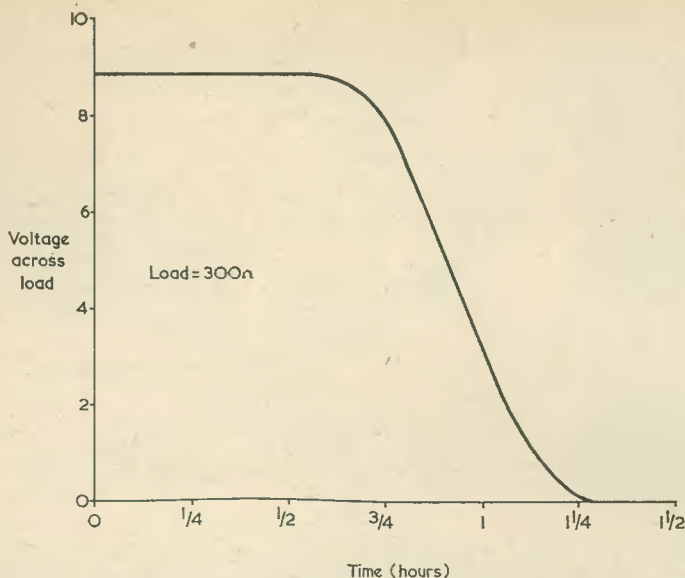


Fig. 3. The result given by the prototype switching circuit when coupled to a 300Ω load

the load remained constant at slightly less than 9 volts for nearly three-quarters of an hour after S1(a) (b) had been switched to the "In" position. The voltage then fell fairly quickly, dropping to a negligibly low value after slightly more than an hour and a quarter from the start. The current in the load resistor is, of course, proportional to the voltage across it. As may be seen from Fig. 3, the average current drawn during the half-hour after which the voltage commenced to fall is about one-half of the full current. It can be argued, in consequence, that the switching circuit has enabled full voltage and current to be applied to the load for nearly three-quarters of an hour, at a cost of a further quarter of an hour of wasted full current.

This performance seems to be more than acceptable for practical purposes, bearing in mind, in particular, the considerable simplicity of the delay switching circuit. The only disadvantage is that C1 requires the fairly high value of 3,200μF.

CAPACITOR PERFORMANCE

The manufacturers of electrolytic capacitors normally only quote the maximum leakage current which is to be expected in their products, and this is usually very much higher than the leakage current the capacitors actually exhibit. In consequence, the delay capacitor, C1, is used in an application which is not covered by manufacturers' specification, since it is expected to pass a leakage current (through its leakage

resistance) which is much lower than the manufacturer's maximum figure. Experience with high-value capacitors bears out, however, that the performance obtained in the writer's prototype circuit should be approximately duplicated in other circuits built up to Fig. 1, although there is no guarantee that an individual capacitor might not exhibit a higher leakage current whilst still being within manufacturer's specification. It can be anticipated that the delay offered with other capacitors may not be exactly equal to that illustrated by the curve of Fig. 3. Taking into account, also, variations in gain in TR1 and TR2 it would seem reasonable to expect that the switch-off delay in other circuits made up to Fig. 1 may range between about half-an-hour and an hour. The actual switch-off delay can only be ascertained by checking it in practice.

The capacitor employed in the prototype was a 3,200μF 10V component in the Mullard C431BR series. It has been the writer's experience that capacitors in this series offer consistently low leakage currents and are, as a result, particularly suitable for a circuit of the present type. It should be remembered that, when voltage is applied across a high value capacitor after it has been in store for a long period, quite an appreciable time is required for it to form and give its final performance. Several runs with the circuit should be undertaken before the usefulness of the capacitor is finally evaluated.

Turning to the other components

in the circuit, TR1 and TR2 have already been dealt with. The three resistors, R1, R2 and R3, may be 1/4 watt 10% components. R3 is merely a limiter resistor, and it limits switch-on surge currents in TR1. Its position in the circuit is such that it also limits switch-on surge currents in C1 as well.

Switch S1(a) (b) is a double-pole single-throw component and may have a toggle, slide or rotary action. If desired, S1(b) may be omitted, whereupon the battery supply to the receiver is fed via R3 and TR1 all the time. This alternative arrangement has the slight disadvantage that the small voltage drop across these two components is always present, and the slight advantage that the only switch required is the single-pole single-throw component shown in Fig. 1 as S1(a).

PRACTICAL PERFORMANCE

When S1(a) (b) is in the "Out" position, additional current is drawn from the receiver battery via R1, R2 and the leakage resistance of C1. The current in the two resistors is very small, being about 4μA and 23μA respectively. The leakage current at nine volts in the electrolytic capacitor employed in the prototype was about 25μA. All these currents are only drawn when the receiver is switched on and are extremely small when compared with the normal receiver current.

When describing the performance illustrated by Fig. 3, it was stated that the voltage dropped to a negligibly low level slightly later than one and a quarter hours after the start of the delay period. The current in the load at that time, as measured in the test circuit, was 0.3mA. This current continued to fall until, after a further quarter of an hour, it consisted of transistor leakage current only, and was actually less than 20μA.

When feeding into the 30mA load offered by the 300Ω resistor, the voltage dropped across R3 and the conducting TR1 was slightly in excess of 0.5 volts.

As a final point, Fig. 1 assumes that the receiver in which the delay circuit is incorporated has a double-pole on-off switch. The circuit may, of course, be similarly employed with a receiver having a single-pole on-off switch. When S1(a) (b) is in the "Out" position, the receiver will take a little longer to become silent after switching off due to the presence of C1. The receiver circuits will very probably have a high value electrolytic bypass capacitor across the positive and negative supply rails, and the delay circuit of Fig. 1 must appear between the on-off switch and this capacitor. If such a capacitor is not fitted in the receiver circuits, limiter resistor R3 could be omitted.



Q S X

by
FRANK A. BALDWIN
(All Times GMT)

● TOPIC

In a recent issue (June 1969) when writing under a pen name, I pointed out that many listeners found difficulty in obtaining information on publications providing some of the constant flow of information required by the keen Broadcast bands operator.

Very few books are published specifically for the interest of short wave listeners and it is quite an event when one appears on the bookstalls. Two such publications have, however, recently been released. The first is *How To Listen To The World*—published by World Radio-Television Handbook Co. Ltd., and available at 25/- plus 1/- postage from the Modern Book Co., 19 Praed Street, London W.2.

Between the covers of this publication is a veritable mine of information on all aspects of Dx-ing written by some of the world's foremost listener experts. Chapters on such subjects as — First Steps in Dx-ing; Selecting a Short Wave Receiver; Physics of the Ionosphere; Measuring Frequencies and Calibrating Receivers; How to Report to Stations; Tape Recording of Reports; Broadcasting in Peru and Languages in International Radio. Many other chapters — there are 45 in all — on other aspects of listening are included. Among the many well-known listeners who have contributed to this publication, the writer noted two British enthusiasts — Charles Molloy of Southport, an expert on Medium Wave Dx-ing and Alan Thompson of Neath, an experienced top-flight short wave Broadcast bands Dx operator. Much useful information is included even for the seasoned listener.

The second publication of the utmost importance to s.w. Broadcast bands listeners has recently been released — *World Radio-TV Handbook Summer Supplement*. A copy of this may be obtained from the bookshop mentioned earlier at 17/6 plus 1/- postage. This latest edition contains all the up-to-date information currently available on frequency and wavelength listings throughout the Long, Medium and Short Wave ranges and also the many TV channels.

This publication is a must for all who operate receivers over the

various bands, especially where a correct record of frequency listings is maintained. All the many changes are included and, where Short Wave Operation is the main interest, this book provides all the very latest information, in handy form, easily available to the short wave listener.

Also of interest to s.w.l.'s is the *World Radio Bulletin* published by World Publications. Lindorfsalle 1, Hellerup, Denmark. Published twice monthly, it contains information on all the latest news, frequency changes, schedules, new stations, addresses and programs, etc., of stations around the world. A sample copy is available on request and an annual subscription (26 issues) costs 36/-.

● AMATEUR BANDS

The past few weeks have provided plenty of Dx on these frequencies provided, as always, that one was prepared to spend some time 'digging' for it under the semi-local transmissions — this particularly applying to the c.w. portions of the various bands.

On 'Top Band' the usual summer conditions applied—plenty of heavy static varying reception conditions from the tolerable to the impossible!

1.8MHz

CW: GI3SLM, GM3UYF, GW3UMB, GW3XJC, OK1AFK, OK1JKR, OK1JMF, OK2SEX, OK3YAO, OL1AFO, OL1AKG, OL1ALM, OL2AIO, OL2AKS, OL2ALS, OL5ALY, OL9ADO.

7MHz

CW: CX7BY, HC2HMC, HK1BDE/4, PY1DMF, PY2DFR, PY3CFB, PY7AWW, PY7AZQ, ZL1AH.

14MHz

CW: CR6AL, CR6KB, CP4AB, FL8MB, HC2RT, HK7BDA, HS2AAF, JA3AOI/MM, (off ZF1), JA3GZN, JA3QQO, JA7TGO, JA8ZO, KZ5HC, LU1EC, VK2AMB, VK2QU, XE1RA, ZE2KL, ZL2CC, ZL3ADF, 9J2CL, 9J2MG, 9Y4DS.

SSB: EP2CB, FG7XL, HC2PC, HC2RZ, HKØBIS, HK3AUE, HK3MT, HK3SJ, HK4DF, HP1AS, HR1KS, JA2BTV, KG4DS, KZ5JW, PJ2CC, PJ3CA, TG9VD, TI2ES, VK3VK, VK4HA, VK7AZ, VP2VV, XE1AE, XE1OE, XE1KV, YN1RTS, YN2OM, YS1O, ZF1GC, ZL1ACP, ZL2BS, ZL2LA, ZS3BP, 5N2AAF, 6Y5GB, 9Y4LP.

21Mc/s

CW: CO2BB, CO2KG, CR6BX, CR6KB, CR6LK, HC3GG/1, JAØBYS, JA2CLI, JA3CNQ, KR8EA, KX6DQ, MP4TAF, PZ1CM, TJ1AJ, 6W8BM, 8P6BU.

● BROADCAST BANDS

This is the 'season' for best reception of the South American low-powered stations and listed here are some of the results of recent operating sessions on the lower frequencies.

3240kHz 0358 OBX4U Lima, Peru,

ending a programme of Latin American songs with the identification "Radio America".

3250kHz 0305 OCX7D Juliaca, Peru, with identification as "Radio Collasuyo" (also at 0257). Channel blotted out at 0310.

3265kHz 0247 ZFT Georgetown, Guyana, heard with identification in English and closing with their National Anthem.

3300kHz 0420 Belize, B. Honduras, with a talk in English. Tentative logging — QRM from strong unmodulated carrier on channel.

3330kHz 0350 OAX1M R. Progreso, Peru, with Andean type flute music. Signed off suddenly after announcement in Spanish at 0357, no National Anthem. Weak signal, tentative logging.

3350kHz 0254 OAX5J Ica, Peru, with a song programme. Identification as "Radio Independencia, Ica" at 2050. Signed off with slowly rendered choral song at 0254.

3380kHz 0250 TGCH Jocatan, Guatemala, featuring light music. This station often radiates organ music. 3 chimes between commercials. Identification and 5 chimes at 0334.

5045kHz 0425 CP38 La Paz, Bolivia, with Latin American music and identification "La Voz de Altiplano".

5180kHz 0331 OAX8F Lima, Peru, with light music and identification.

6040kHz 0243 HJLB Ibague, Colombia, with a programme of Latin American music and identification "La Voz del Tolima".

6075kHz 0315 HJCT Sutatenza, Colombia, with news in Spanish and identification.

6160kHz 0259 HJKJ Bogota, Colombia, with a commentary in Spanish and identification "Emisora Nueva Granada".

6250kHz 0305 OAX7A Cuzco, Peru, with 2 chimes and identification "Radio Cuzco". Cuzco is an ancient town situated in the Andes at an altitude of 11,400ft. in the valley of the Urabamba river. Cuzco was once the capital of the Incas, has an Incan temple and fortress and was besieged and sacked by Manco Inca in 1536. For those beginner Broadcast bands listeners who would like to try the higher frequencies and receive the more powerful stations, try these:—

17805kHz 0500 RSA, South Africa, with news commentary in English and identification.

17820kHz 0455 R. Australia, with news in English and identification.

21500kHz 0515 Brazzaville, Congo, with news in English and identification.

21540kHz 0510 R. Australia, with news in English. ■

AFRICA EXPEDITION RUNS INTO TROUBLE

The radio communications expedition to North, East and South Africa, led by 25-year-old Mr. David Dunn, of Cardiff, reported in our March issue, has run into difficulty with the Moroccan police.


The main objective of the four-man expedition is to study the reliability of low power short wave radio communications. Mr. Dunn, a senior draughtsman with the Powell Duffryn Group company Hydraulic Machinery (Great Britain) Limited, of Rhymney, Monmouthshire, did not have a transmitting licence for Morocco and, in accordance with Moroccan law, the radio equipment was confiscated.

Mr. F. J. Seller, secretary of the Amateur Radio Society at the University College, Cardiff, said the party were told the equipment would be returned when the expedition left the country, but this promise was not fulfilled.

Mr. Seller said, in a recent letter from Addis Ababa Mr. Dunn told him that he was beginning to despair of ever seeing the equipment again.

"If this is so it will, of course, mean the end of any short wave communication aspect of the expedition," said Mr. Seller. "This is most unfortunate since I understand Mr. Dunn has transmitting licences for almost all the countries he has yet to visit."

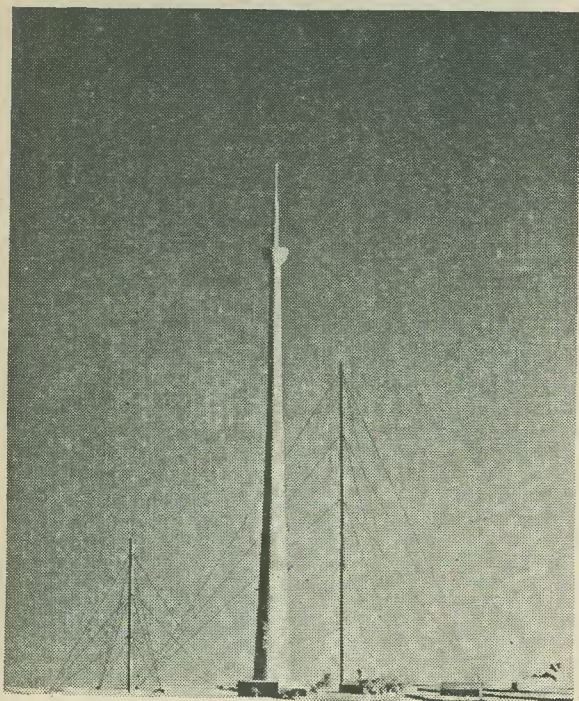Mr. Dunn hopes to rejoin the Cardiff office of Hydraulic Machinery at the end of the trip this September. His companions are Colin Such (24), and Richard White (22), both of Cardiff, and David Cocks (25) of Gloucester.



A model of the proposed new ITA reinforced concrete television tower which, by the end of 1970, will be broadcasting from Emley Moor the programmes of Yorkshire Television, BBC-1 and BBC-2 in UHF, 625-lines. It will also transmit the present 405-line VHF services for Yorkshire Television and BBC-1. For comparison purposes, a model of the present 675ft. "Swedish" mast is shown on the right, and of the temporary BBC-2 300ft. mast on the left.


NEW DIGITAL PRINTERS FROM KIENZLE

The entire range of Kienzle parallel entry digital printers has been superseded by a redesigned range offering all round improvements and several new features.

The new range of Kienzle printers have been re-housed in unbreakable plastic cases of advanced styling, complementary to modern electronic instruments and systems.

The redesigned mechanics permit an increase in the printing speed to four lines per second except on printers fitted with adding/subtracting register, where the speed remains at three lines per second.

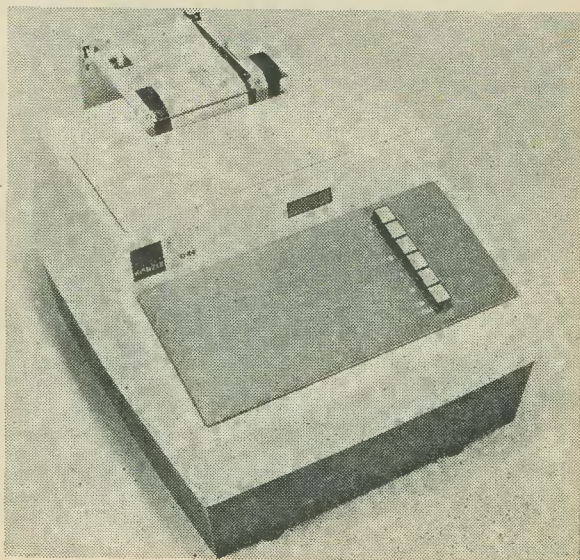Several other new features are incorporated, and the new printers are expected to find many applications in data logging, automatic test equipment, weighing systems, automation projects and instrumentation in the laboratory, industry and marine environment.



THE RADIO CONSTRUCTOR

COMMENT



Pat Otter, Divisional Manager of ITT Electronic Services, presents the prize of a box of chocolates to Miss Gill Harford, winner of a sales desk competition. Miss Harford averaged 9.95 seconds to look up any product in the new 1969 Stock Catalogue.

22% TIME SAVING WITH NEW CATALOGUE

Ten seconds is enough to find what you are looking for in the new 1969 Stock Catalogue issued by ITT Electronic Services.

A thumb index has been incorporated to produce what ITT Electronic Services claim to be the quickest reference catalogue published by any electronics distributor.

They put it to the test with a competition among staff on the sales desk. Using both the new catalogue and the previous one, expert salesmen and salesgirls looked up products pre-selected at random.

Winner was Gill Harford, who averaged 9.95 seconds to find any product in the new catalogue against 12.85 seconds in the 1968 edition.

ITT Electronic Services 1969 Stock Catalogue contains 1,076 pages, with full illustration and clearly-stated prices directly adjacent to product descriptions. Over sixteen thousand products are listed. Available free to buyers and engineers in industry from ITT Electronic Services, Edinburgh Way, Harlow, Essex (Harlow 26777).

SEPTEMBER 1969

G.E.C. RADIO FOR COVENTRY BUS CREWS

Within the next few months, 37 Corporation buses in Coventry will be fitted with GEC mobile radio communications systems which will provide crews with a permanent and instant radio contact with their new traffic control centre in the centre of Coventry.


The equipment consists of the GEC RC/600 high power v.h.f. frequency modulated transmitter/receiver which provides an extremely flexible communications system, capable of covering the whole area of operations of the Coventry bus service. The equipment is fully transistorised, except for the 20 watt power output and driving stages, which use 'quick-heat' valves of proven reliability and stability. The main transmitter unit with its power supplies is housed in a single unit, mounted under one of the seats. The receiver and system controls are in a small unit, mounted in the driver's cab. The receiver itself can be withdrawn from this mounting, and carried by the driver to keep him in touch with the base if he should have to leave his cab for any reason.

BIG DEMAND FOR OUR NEXT ISSUE

In our October issue, to be published on 1st October, we are including FREE with each copy Workshop Plans, containing a full scale point-to-point wiring diagram, drilling plans, tables, etc., for constructing the *Neophyte* amplifier. The plans are on special cartridge paper to allow for hard workshop use.

The *Neophyte* is a practical, easy to build, 5 watt amplifier, designed exclusively for our readers and will be very popular. We shall also be repeating our special offer, again exclusive to our readers, of motoring accessories such as roof racks, head rests, etc., and the issue will be packed with good articles and the usual features.

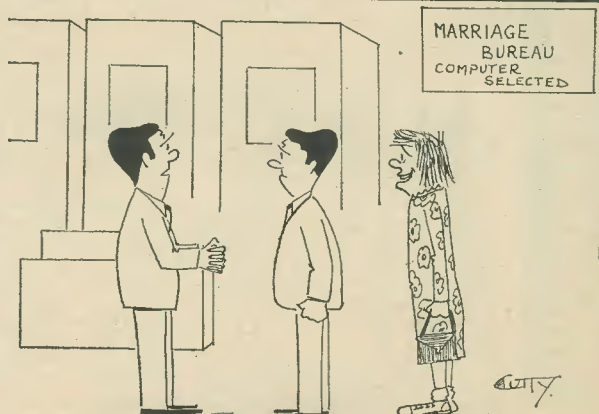We advise readers to place an order for the next issue with their newsagent, as soon as possible, as there will be a big demand.



"No, Sir, there's no mistake - it's just that the computer has such strange tastes!"

HOW TO MAKE FULL USE OF YOUR DIARY

Underline the dates of both personal and radio events in which you are interested or concerned, as shown in the illustration below, and enter brief details of these in the Diary Notes. A list of forthcoming events of radio interest taking place during the fourth quarter (October to December inclusive) is shown alongside. Detach your Diary from the magazine and affix to the workshop wall.

Tues	<u>2</u>					
Wed	<u>3</u>					
Thur	<u>4</u>	<u>11</u>				
Fri	<u>5</u>	<u>12</u>				
Sat	<u>6</u>	<u>13</u>	<u>20</u>			

3	<i>Go Birthday 21</i>
6	<i>R.S.G.B. July 24</i>
7	<i>Band to contest</i>
12	<i>Club A.G.M.</i>
14	<i>Mobate Kelly 28</i>

SUGGESTIONS FOR YOUR EASY-VIEW DIARY

OCTOBER

- 1-4 RSGB International Radio Engineering & Communications Exhibition, Royal Horticultural Society's New Hall, Greycoat Street, London, S.W.1 (10 a.m. to 9 p.m.)
- 4-5 VK/ZL/Oceania Phone Contest
- 5 RSGB Second 1296 Mc/s (Open) Contest
- 11-12 VK/ZL/Oceania CW Contest
- 11-12 RSGB 28 Mc/s Telephony Contest
- 18-19 Boy Scouts (USA) Jamboree
- 18-19 KR6 Dx Contest
- 25-26 CQ WW Dx Phone Contest
- 25-26 RSGB 7 Mc/s (CW) Contest

NOVEMBER

- 3 RSGB Eighth 144 Mc/s (SSB) Contest
- 8-9 RSGB 7 Mc/s (Phone) Contest
- 8-9 ARRL SS Phone Contest
- 15-16 RSGB Second 1.8 Mc/s Contest
- 15-16 ARRL SS CW Contest
- 29-30 CQ WW Dx CW Contest

DECEMBER

- 6-7 Tops CW Club 3.5 Mc/s Contest
- 7 RSGB Fifth 70 Mc/s (CW) Contest

"MILLIWATT" SILICON REFLEX T.R.F. RECEIVER

by

G. W. SHORT

Power consumption in this simple but effective receiver design is reduced to less than 2 milliwatts by operating the transistors at the lowest practicable current. The result is greatly enhanced battery life

THE STARTING POINT FOR THE DEVELOPMENT OF THE receiver described here was an enquiry from a friend whose daughter is at a boarding school. Illicit listening to pop music in bed, after 'lights out', is very much the done thing at this school—and perhaps at many others. The trouble is, as my friend explained, that the listener tends to fall asleep, leaving the set switched on all night. Rather bad for the batteries, this, so could I suggest a way round the problem?

My first idea was to modify an existing set by adding a sort of 'dead man's handle' in the form of a push-button switch which would turn off the set when the sleeper's hand relaxed. This was rejected on the ground that the user was more than likely to find some way of keeping the button pressed by lying on it.

The alternative was to reduce power consumption so much that an occasional overnight run became tolerable. This approach was adopted, and the resulting circuit is shown in Fig. 1.

CIRCUIT DESIGN

Readers may recognise the circuit as a development of one of the writer's earlier designs, the 'Silicon Reflex T.R.F.' described in the January, 1968, issue.* This proved to be a very reliable design, and it seemed better to stick to a good thing for the present purpose rather than start on something quite different and possibly less satisfactory.

For the benefit of readers unfamiliar with the original, this type of circuit maximises overall gain by making all two transistors contribute to both r.f. and a.f. amplification. TR2 acts as an emitter follower to r.f. and presents a high input impedance to TR1, thus maximising the r.f. gain of the first stage and providing a relatively low impedance drive to the detector diode. TR2 can thus be regarded as an impedance matching device which, while it produces no voltage amplification itself, nevertheless serves to increase the overall r.f. gain.

The a.f. output of the detector is passed to TR1 and thence to TR2 in the usual way. At audio frequencies, therefore, the circuit is a straight-forward two-stage amplifier.

LOW-CURRENT OPERATION

The original circuit was not at all fussy about transistor types. Practically any silicon n.p.n. transistors worked in it, though naturally some worked better than others. In the present 'Milliwatt' version, the choice of transistor types is much more restricted. The gain and, more especially, the cut-off frequency of transistors fall off as the collector current is reduced below the normal operating value, but in this circuit the transistors must provide high r.f. gain and low r.f. and a.f. noise at collector currents of $100\mu\text{A}$ or less. Very few transistor types meet all these requirements.

Fortunately, the new epoxy encapsulated planar transistor type SF115 has the necessary characteristics. In particular, it has low internal capacitances, a prime need in circuits with high-value resistance loads operated as wideband r.f. amplifiers, as occurs here. The SF115 is equivalent to the metal type BF115, but is much cheaper. Its one disadvantage is that it will not work well at very low collector voltages. This is why the detector diode specified is a silicon planar type instead of the usual germanium point-contact diode. The voltage drop across a silicon diode when just biased to conduction is 0.5V, whereas the corresponding voltage for a germanium diode of the OA70 class is only about 0.1V. In the present circuit, the drop across the diode forms part of the collector-emitter voltage of TR1. (This point may not be very obvious at first, but a study of Fig. 1 will show that the collector-emitter voltage of TR1 is the sum of the base-emitter voltages of the two transistors and the drop in D1). Using a silicon diode raises the total from about 1.3V to about 1.7V, and this provides a useful margin for reliable operation. It is important to use a high-speed planar diode for D1. An ordinary silicon rectifier type will not do because it will not work at radio frequencies. (The specified IS44 diode and the SF115 transistors are available from Amatronix, Ltd.)

The receiver consumes about $170\mu\text{A}$ at 9V, and is not unduly dependent on the battery voltage, which can fall to 6V or less without impairing the performance badly.

EARPHONE

The set was designed for use with a crystal earpiece

THE RADIO CONSTRUCTOR

*G. W. Short, 'Silicon Transistor Reflex T.R.F.', *The Radio Constructor*, January, 1968.

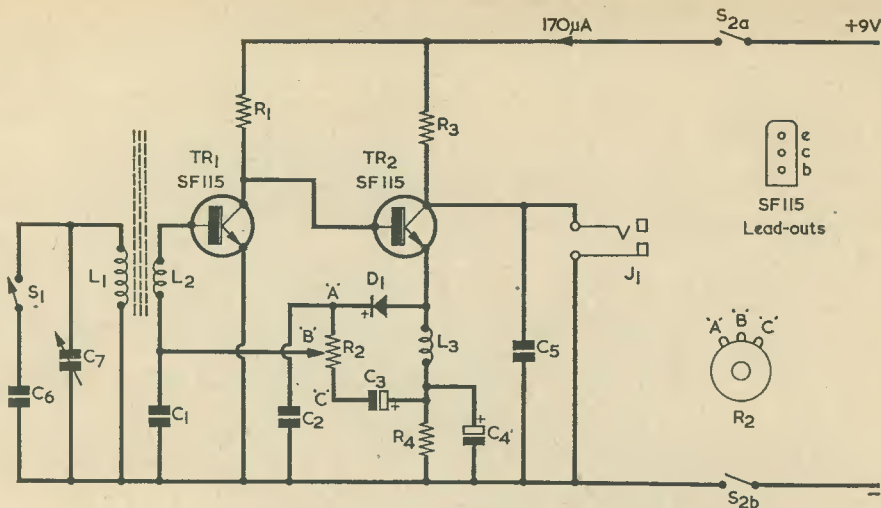


Fig. 1. Circuit diagram of the 'Milliwatt' Silicon reflex receiver

because these are suited to low-current high-voltage circuitry. It is, however, possible to use high-impedance magnetic earphones. The writer does not know of any miniature earpieces with the required impedance (4,000Ω or more), so for clandestine listening magnetic earpieces may be out. For normal purposes a good pair of magnetic phones, such as government surplus type CHR, with the earpieces connected in series can be connected in place of R3. It is also possible to use a step-down transformer to match low-impedance earpieces. For an 8Ω earpiece the turns ratio should be about 60 to 1. The primary inductance must be high (20H with 70µA d.c. flowing).

CONSTRUCTION

It is vital to keep the stray capacitance at the collector of TR1 and the base of TR2 as low as possible. This means that TR1, TR2, and R1 should be positioned close together so that leads can be kept short, and it also means that if a printed circuit or Vero-board base is used then the area of copper involved in joining the relevant three leads must be as small as possible. A pin-board base following the layout of Fig. 2 was used in the prototype, with all three leads on one small pin.

(For the benefit of readers who have not experienced the joys of this cheap and simple form of construction, here is a short description. The layout diagram is placed on a piece of dry wood. Ordinary domestic pins of the shiny plated type obtainable at office stationers are driven in at every junction point.

The heads are then cut off, leaving enough stem to act as solder tags for the leads. Perfectionists tin the stems first before attaching anything. The resulting wiring board is virtually self-checking and components are easily removed. Since everything is on one side of the board testing is easy, and the board can ultimately be made part of a case for the set.)

For reasons which are explained later, the lead-outs of choke L3 should be a little longer than is necessary for connection, in order that it may be orientated relative to the ferrite rod. Initially, its former should be at right angles to the rod.

In t.r.f. receivers, where the r.f. gain is always

COMPONENTS

(N.B.—Some of the components may have values differing from those listed here. Details are given in the text.)

Resistors

(All fixed values $\frac{1}{4}$ or $\frac{1}{8}$ watt 10%)

R1	68kΩ
R2	10kΩ potentiometer, log, with switch S2
R3	47kΩ
R4	10kΩ

Capacitors

C1	0.01µF
C2	1,000pF
C3	10µF electrolytic, 2V wkg.
C4	125µF electrolytic, 2V wkg.
C5	1,000pF
C6	see text
C7	see text

Inductors

L1, L2	see text
L3	1.5mH choke type CH5 (Repanco)

Semiconductors

TR1	SF115
TR2	SR115
D1	IS44

Switches

S1	s.p.s.t., rotary or toggle
S2	d.p.s.t., part of R2

Socket

J1	phone jack socket
----	-------------------

Miscellaneous

	Crystal earpiece with jack plug
	9-volt battery
	Knobs, as required

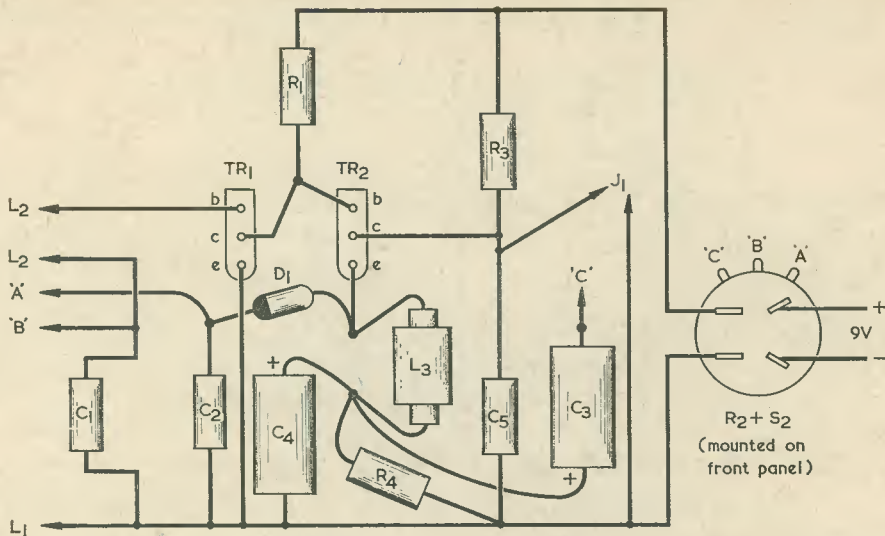


Fig. 2. Layout and wiring of the main components of the receiver. Identify the tags of S2 with a continuity tester before wiring to this component, as tag positioning with different switches may vary from that shown here

limited compared with superhets with their h.f., mixer, and i.f. stages, it is always advisable to keep the ferrite aerial rod well clear of everything else, in order to maximise signal pickup. In this design, the rod should also be kept at least $1\frac{1}{2}$ in. from L3. (See below under 'Reaction'.) The tuning capacitor and long-wave components S1 and C6 should be clear of the main circuitry, to reduce stray coupling which might cause instability. These considerations lead naturally to the sort of constructional layout sketched in Fig. 3.

The front panel and base dimensions are not critical, and the constructor may select these to suit the components he is employing. With the ferrite rod used in the prototype, the front panel may be some 5 in. wide by 3 in. to 4 in. high. The base can be about 3 in. deep, and could then accommodate a PP3 battery.

AERIAL CIRCUIT

The aerial tuned circuit should have a high Q, and a ferrite rod of reasonably large size should be used to provide a good input signal. In London, good results have been obtained with a $4\frac{1}{2}$ in. x $\frac{3}{8}$ in. round rod of Plessey NW25 ferrite (obtainable from Amatronix Ltd.).

The value of tuning capacitor C7 is not very critical and any standard air-space or solid dielectric variable capacitor offering a maximum value of about 200pF or more will be satisfactory. (A 300pF Jackson Bros. 'Dilemin' capacitor was employed in the prototype.) C7 tunes L1 over the medium wave band. Reception of one selected long wave station is provided by switching capacitor C6 across the tuning capacitor by means of S1. In the U.K., the long wave station is likely to be Radio 2 on 200kHz, and in this case C6 should normally be seven times the maximum capacitance of C7.

WINDING THE AERIAL ROD

Amateur constructors often have in their possession tuning capacitors salvaged from old sets. Unfortunately, the capacitance is not usually known, and even if it is the constructor is often discouraged from making his own ferrite aerial by the absence of information about the characteristics of the ferrite rod. Nevertheless, the winding of a rod for a set like the present design is not at all difficult if the constructor goes about it the right way. All that is needed is patience and a good supply of wire.

The method described here calls for no equipment other than the receiver itself, plus the usual tools, glue, and plastic sticky tape. To begin with, the rod is kept detached from the rest of the circuit, so that changes can easily be made. Only after the windings have been got nearly right is the rod installed and the final adjustment made.

First make up the rest of the circuit, providing in the process a pair of easily accessible tags for connections to L2 and one tag for making an 'earth' (i.e. supply negative) connection for L1 and C7. Check that the set is working by short-circuiting the L2 tags and listening in the earpiece with the volume control turned up. A gentle hiss should be audible. The constructor may then proceed with winding the coil for the rod.

First prepare the rod by wrapping a few turns of brown paper round the middle two inches or thereabout. Fix the paper with sticky tape or glue to prevent it unwinding, but if possible allow it to behave as a paper tube loose enough to be slid along the rod to provide fine adjustment of inductance. This paper tube is the coil former. Readers may have seen ferrite aeriels in which the windings are directly on the ferrite. This is not good practice for all grades of ferrite; and some work better if the coils are spaced away from the surface. (The spacing reduces

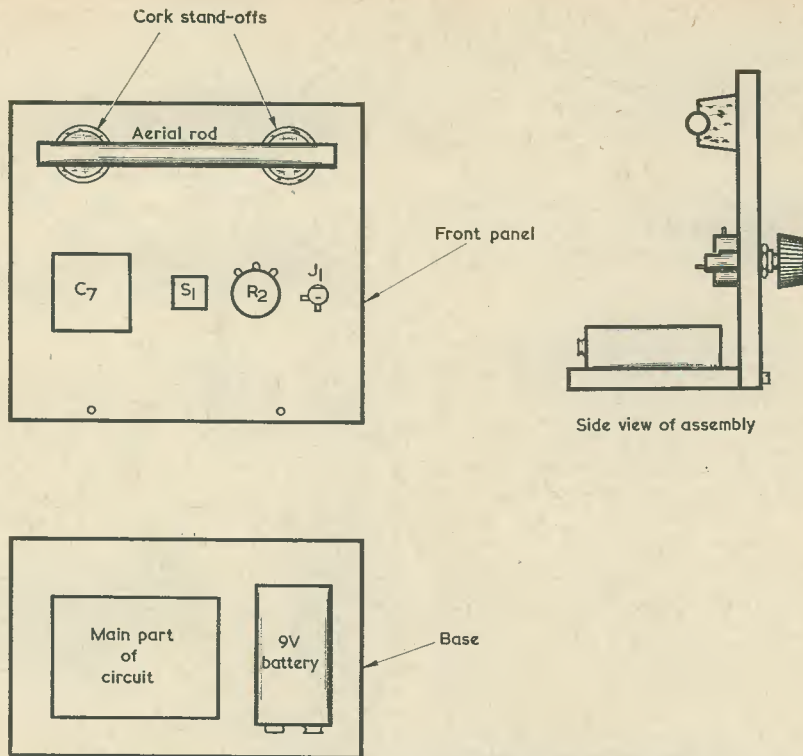


Fig. 3. A suitable layout for the front panel and base of the completed receiver. The rectangle designated 'main part of circuit' may enclose the components (apart from R2) shown in Fig. 2

certain r.f. losses.) L1 can be wound with any kind of litz wire (which can often be salvaged from old i.f. transformers) or with solid wire of around 30 s.w.g., silk or cotton covered. L2 can be wound with ordinary plastic covered hookup wire. Both coils are single-layer, close-wound. L2 can be wound on top of the earthy end of L1.

The number of turns needed depends on the capacitance and characteristics of the rod. As an indication, the rod just mentioned needs approximately 57 turns of 7/46 litz wire to tune over the medium wave band with a 300pF tuning capacitor. In finding the right number of turns by trial and error, it is best to begin with too many and then remove turns rather than to begin with too few and add them. If, on the other hand, plenty of wire is available, it may well be best to scrap the initial trial winding when the correct number of turns has been found, and then finally re-wind. In the latter case, it is a fairly safe bet that 50 turns will tune to some point in the medium wave band. If coverage down to the low frequency end at about 530kHz is not obtained, turns can be added. Should the set tune to lower frequencies than are needed, turns are removed. To make the initial trials, put on a temporary 3-turn winding for L2 with about 9in. of loose wire at each end. Twist the loose wire into flex and connect the ends up to the L2 tags on the circuit board, removing the short-circuit which was put on for the earlier test. The rod can now be kept well away from the circuit while L1 is adjusted. During adjustments, L1 and C7 may be connected with fairly long loose leads and

the ferrite rod and variable capacitor can be placed on a wooden table top or other insulating support. It is not necessary to 'earth' the moving vanes of C7 to the negative supply line of the receiver at this stage.

Using a trial coil of 50 to 100 turns for L1, tune in and identify stations, and add or remove turns as required to tune to the low frequency end of the medium wave band. When the correct number required is beginning to become clear, slide the coil along the rod so that L1 is central. Readjust the turns slightly if necessary.

The ferrite rod and C7 can now be mounted. The best position for the rod is behind the top of a front panel of Formica or similar insulating board. Keep it away from metal, including the volume control and C7. If possible, mount the rod on stand-offs (pieces of cork or dowel) so that the winding can be easily adjusted *in situ*. Trim off excess leads and connect up again to the circuit. Also complete the 'earth' connection to C7 and L1. There should be no marked change in performance. If there is, adjust L3 as described later under 'Reaction'. A slight final adjustment of inductance, if required, can be made by sliding the coil along the rod. If it has to be put right at the end of the rod, remove a couple of turns and start again.

So far, nothing has been said about the tuning at the high frequency end of the medium wave band. In general, if the low frequency end is all right, so also is the high frequency end. The only exceptions are, first, that if the tuning capacitor has a built-in

trimmer this may have to be set to minimum to obtain full coverage and, second, that if the tuning capacitance is too small the self-capacitance of the coil may be so large that it prevents full high frequency coverage. In the latter case there is nothing much to be done about it. As a guide, tuning capacitors of less than about 150pF maximum are in the 'danger area'.

The final job consists of fitting and wiring C6 and S1. If necessary, slightly alter the calculated value of C6 to bring in the Radio 2 transmission comfortably.

REACTION

Preset reaction is adequate to pep up the performance of this receiver. It is obtained in two simple ways, at no expense. Should L3 be near enough to L1 and L2 for there to be an appreciable amount of mutual coupling, then feedback is introduced between the input and output of the r.f. amplifier. If this feedback is negative, gain and selectivity both suffer. If it is positive, gain and selectivity are improved, and if the coupling is too high the circuit oscillates. The sense and magnitude of the coupling are adjusted by positioning L3. Initially, it should be placed so that it is approximately opposite the centre of L1 and at right angles to the rod; i.e. the former of L3 is pointing straight at a point near the middle of the rod. This is the position for minimum coupling. If L3 is now turned away from the right-angles position coupling with L1 is increased. There is no easy way of telling beforehand whether the result will be negative or positive feedback, but this becomes obvious when the receiver oscillates. L2 is finally positioned so that the set just fails to oscillate with a new battery.

The second method is to connect a short stiff insulated lead to the non-earthly side of L1 and place the free end near to or touching L2. If the sense of the windings on the rod is right, oscillation is obtainable. If not, reverse the connections to L2 and try again. Either or both of these methods of obtaining reaction may be used. There is some advantage in using both, since the L3 coupling method is usually most effective at the low frequency end of the band and the reaction wire method at the high frequency end. With both, the performance can be optimised over the band.

If necessary, an extra reaction wire can be connected to the non-earthly end of C6 to provide a separate adjustment of reaction for the selected long wave station.

GENERAL NOTES

The receiver is easily built, and a small battery lasts a long time. Apart from the tuning, there are no critical adjustments, and no critical component values. The volume control is a necessity in this low-consumption circuit, because it is essential to be able to turn down the volume on strong transmissions to avoid serious distortion caused by overloading on audio peaks; on the other hand its value is not critical and anything from 5k Ω to 100k Ω can be used. The electrolytic capacitors need not have the exact value specified. C3 can be 5 to 50 μ F and C4 50 to 500 μ F, both with any working voltage above the 2V specified.



IF YOU'RE BUYING A HOUSE

Mortgage Protection

is the best Policy for you

If you're buying your house with the help of a Building Society or a private loan, a "Yorkshire" Mortgage Protection Policy will take care of your outstanding payment in the event of your premature death. And, if you wish, you can arrange a Protection "Plus" Policy, which gives you a substantial cash return at the end of the mortgage term. It costs so little yet means so much to your dependants. Leave them a home not a mortgage!

Please send for further details, without any obligation, of course.

THE YORKSHIRE INSURANCE COMPANY LTD

Chief Offices: Rougier Street, YORK
and Becket House, 36-37 Old Jewry, LONDON E.C.2

Please send me further particulars of the
"Yorkshire" Mortgage Protection Policy

Name.....

Address.....

..... J/B

DOUBLE SPEAKER UNIT FOR THE SWL

by

FRANK A. BALDWIN

This simple double-speaker unit provides the short wave listener with two sources of audio output, each of which may be selected at the turn of a switch. The speakers differ with respect to audio response, and that best suited is brought into circuit according to the requirements prevailing. Additionally, an output is provided for tape recording facilities

WITH A COMMUNICATIONS RECEIVER SET TO ITS most selective state operating over the short wave Broadcast bands, the writer often found that the single speaker he previously used—a 7in. x 4in. elliptical type—was apt to offer an accentuated bass response. This state of affairs was largely a result of the sideband cutting given by the receiver in its most selective condition.

Requiring a higher pitched audio response, an inexpensive 3in. round speaker was experimentally connected into circuit and the elliptical speaker removed. The subjective improvement was surprising—the transmission being received having a much higher audio content with the smaller speaker. The former 'boomy' audio response vanished almost completely and the signal became perfectly intelligible. However, when the communications receiver was then set for wideband reception, audio quality (at least in communication terms) was sadly lacking.

Further checks with c.w. reception revealed that the smaller speaker produced a much better audio response than did the larger speaker, judicious use of the b.f.o. pitch control rendering morse signals much more intelligible. Indeed, the signal selected could be made to stand out with almost crystal clarity.

It occurred to the writer that a twin-speaker unit containing both speakers, together with a switch for selecting one or the other, would provide the best of both worlds. Since the writer also makes extensive use of a tape recorder, the opportunity was taken to provide an output for this instrument as well.

The end result is a simple twin-speaker unit which is comparatively inexpensive and easy to put together.

CIRCUIT

The simple circuit employed is shown in Fig. 1. The components are contained within a 12in. x 5in. x 3in.

COMPONENTS

Chassis

Aluminium 12in. x 5in. x 3in. (H. L. Smith & Co., Ltd.)

Speakers

3in. round
7in. x 4in. elliptical

Switch

Single-pole, two-way rotary

Knob

To suit switch

Mounting Feet

4 of rubber, grey (H. L. Smith & Co., Ltd.)

Miscellaneous

4BA nuts and bolts, speaker mesh, screened cable, p.v.c. covered wire, solder, etc.

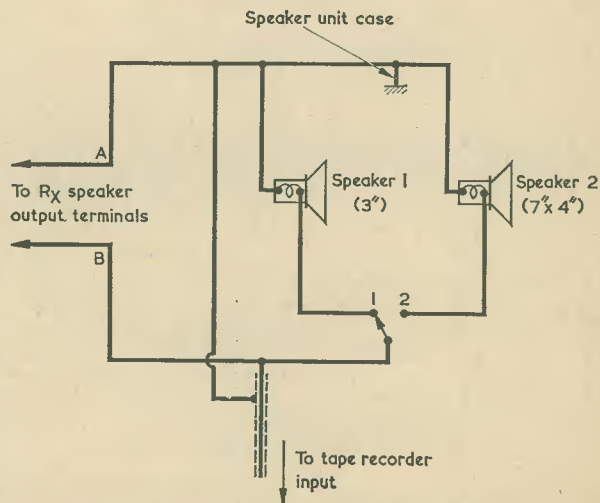


Fig. 1. The circuit of the twin-speaker unit with tape recording output facility


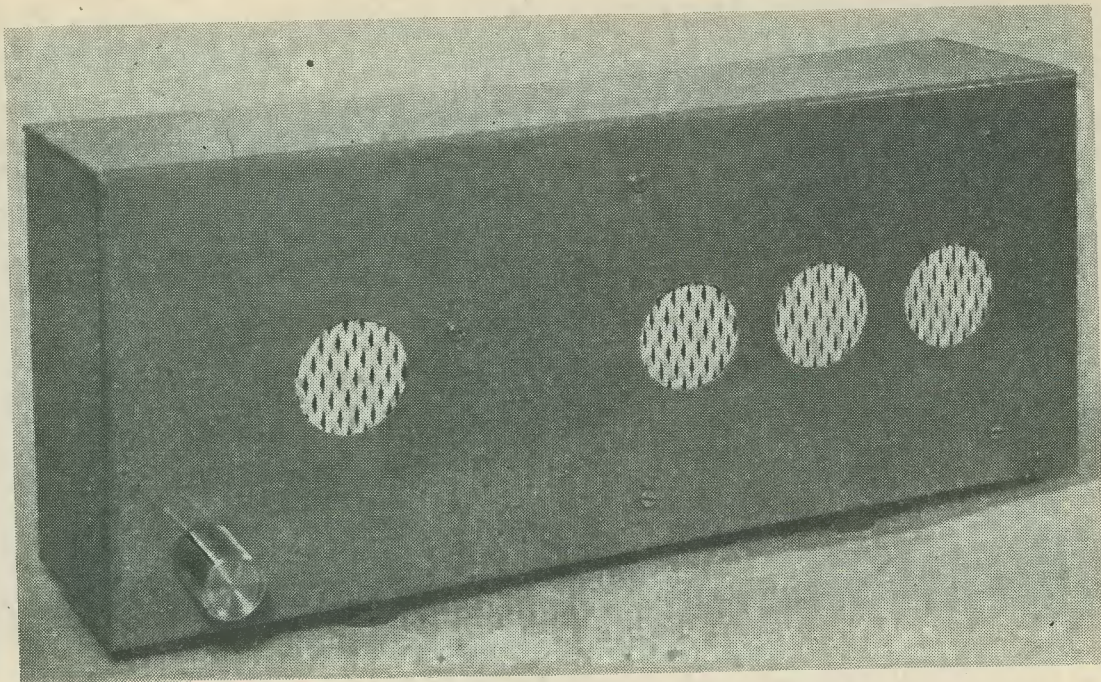


Fig. 2. Drilling details of the chassis deck — this being the speaker unit front panel when completed. Hole A is for the 3in. speaker and holes B, C and D are for the 7in. x 4in. speaker

aluminium chassis—see illustration—the input to the unit being taken from the receiver speaker output terminals on the rear of the receiver chassis.

The intending constructor of this unit should look at the circuit diagram of his communications receiver and ascertain whether or not one side of the output transformer secondary winding is connected to chassis. If this is the case, the receiver output terminal at chassis potential couples to input A of the unit (see Fig. 1) whilst the other output terminal connects to

input B. Should neither side of the output transformer secondary be connected to receiver chassis, and if no harm to or malfunctioning of receiver circuits would result if such a connection were made, then couple one of the receiver output terminals to the receiver chassis and wire input A to this point, as before. In the unlikely event that neither of the receiver output terminals can be connected to chassis the 2-speaker unit may still be used, but no connection is made to the unit case and the output facility for the tape recorder has

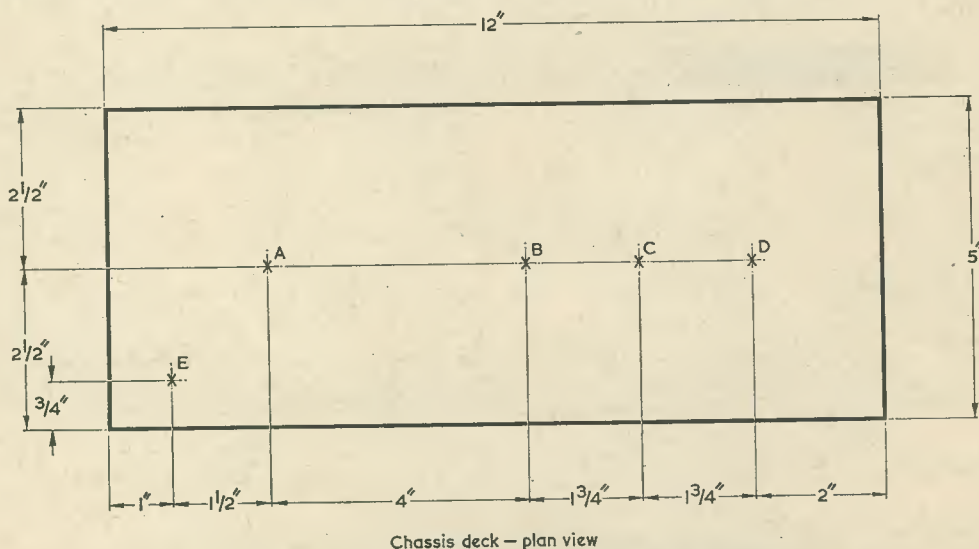

The completed twin-speaker unit. Speaker 1 is at the left and speaker 2 at the right. Note the rubber mounting feet and speaker aperture mesh

to be omitted. It is assumed in this last instance that there is no h.t. or otherwise dangerous potential on the output terminals.

The 2-speaker unit must *on no account* be used with a receiver having its chassis connected to one side of the mains. It may only be used with receivers having an isolating mains transformer and a reliably earthed chassis. It may also, of course, be used with battery operated transistorised receivers.

Inputs A and B may be connected via twin flex, lead A inside the unit connecting to a chassis tag secured under one of the speaker mounting nuts and thence to the two speakers, and lead B passing to the arm of the switch. The switch contacts then connect to the remaining speaker tags.

The tape recorder output is taken by screened cable, as shown, the screening connecting to the speaker unit chassis tag. Coaxial cable provides a satisfactory screened cable. Although this method of taking a tape recorder output from the receiver is not ideal—it would be preferable to take the output from an early point in the receiver a.f. amplifier stages—it has the advantage of simplicity and it ensures that no internal connections have to be made to the receiver. The writer found that recording quality was better with the small speaker switched into circuit.

Both speakers should have approximately the correct impedance specified for the particular receiver with which they are to be used.

CONSTRUCTION

Fig. 2 provides drilling details for the twin-speaker unit and from this, and the accompanying illustration, it will be seen that hole A is for the small 3in. round speaker whilst holes B, C and D are for the 7in. x 4in. elliptical speaker. Hole E is for the switch.

In the prototype, holes A, B, C and D are 1½in. diameter, being cut with an octal-sized chassis cutter. The two speakers are secured into position behind these holes on the chassis deck—which then becomes the 'front' panel—by means of 4BA nuts and bolts. The speaker apertures are covered with a white plastic mesh as shown, but any suitable material or metal mesh could, of course, be used. The rear of the speaker unit is left completely open.

Prior to mounting the switch, speakers and mesh, the chassis should be cleaned, and cellulose sprayed or painted to the colour choice of the individual constructor. When dry, four rubber mounting feet can be secured to the underside of the unit either by means of a suitable adhesive or by self-tapping screws or suitably sized nuts and bolts. The mesh, the two speakers and the switch are then secured into position and the circuit wired up. A suitable knob is fitted to the spindle of the switch.

The coaxial cable should be connected to the tape recorder radio input, the recorder handbook being consulted to ensure that correct connections are made.

Once in use, the short-wave enthusiast will soon wonder how on earth he ever managed previously with only a single speaker. ■


TRANSISTORISED G.D.O. FOR THE H.F. BANDS

We regret that, due to pressure on space, this article has been held over and will appear in the next issue—October—due to be published on 1st of October.

SEPTEMBER 1969

THE "RADIO CONSTRUCTOR'S" WINTER SEASON BEGINS WITH THE

NE PHYTE AUDIO AMPLIFIER

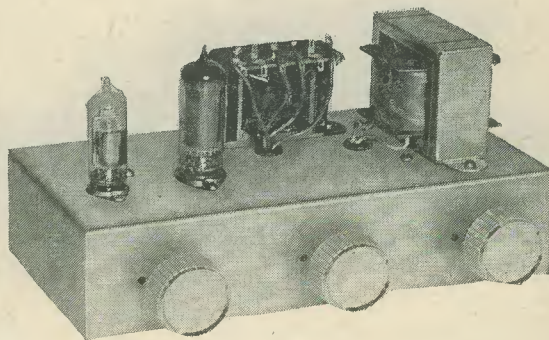

A practical easy-to-build project exclusively commissioned for our readers.

FREE INSIDE

Workshop Plans for the Neophyte 5 Watt Audio Amplifier on cartridge paper for hard wear, containing full scale point-to-point wiring diagram, drilling plans, tables, etc.

PLUS special motoring offer, many other constructional articles and all the usual features

IN OCTOBER ISSUE

On Sale 1st October

NOMOGRAM FOR PARALLEL RESISTANCE OR SERIES CAPACITANCE

by
R. H. DOUGHTY

This simple nomogram can be made to any convenient size with the aid of standard graph paper

WHEN ONE IS DEALING FREQUENTLY WITH THE practical solution of an equation containing more than two related variables, alignment charts or nomograms can often be used to advantage. This article describes a simple nomogram capable of providing solutions to the well known equation,

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2},$$

for two resistors in parallel. A similar equation exists for two capacitors in series.

BASIC NOMOGRAM

The basic nomogram is shown in Fig. 1. The two outer scales, OA and OC, are each inclined at 60° to the centre scale OB. The spacing between graduations on all three scales is the same.

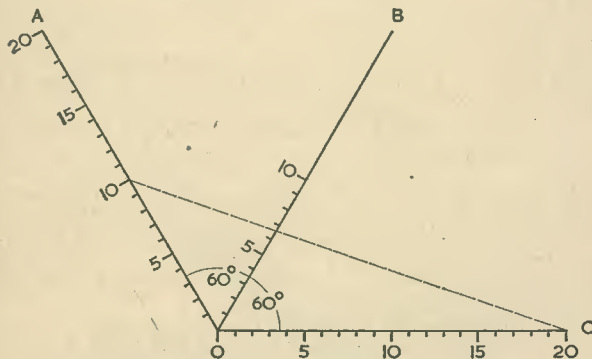


Fig. 1. The basic nomogram. As an example of its use, the dashed line indicates that a total resistance of 6.7Ω is given by resistances of 20Ω and 10Ω in parallel

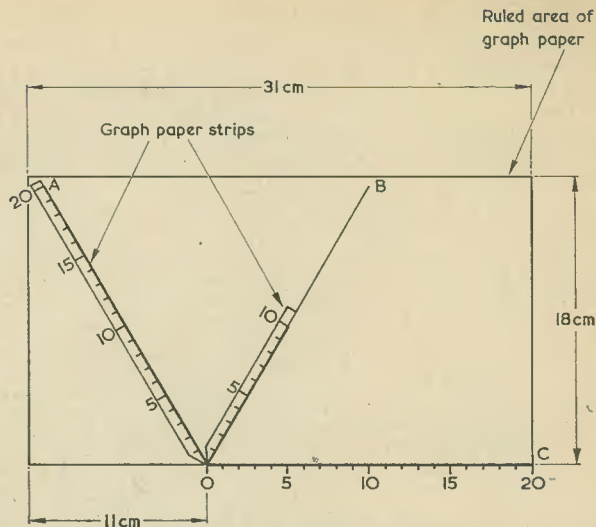


Fig. 2. Making up a large version of the nomogram on a sheet of centimetre graph paper

To determine the resultant of paralleling two resistors their values are set on the two outside scales with a straight edge and the resultant is read off at the point of intersection with the centre scale. The chart can, of course, be used in the reverse manner to determine what resistance must be placed in parallel with a given resistor to reduce it to a required new value.

Where the resultant of a number of resistances in parallel is required, the third resistance and the resultant of the first two are set on the outside scales and the result of combining three is read on the centre scale, and so on.

While the diagram shown in Fig. 1 could be used for approximate determinations, larger and more accurate nomograms may be constructed simply, using sheets of centimetre graph paper of foolscap or similar size. The squared area of these is usually about 31cm by 18cm.

Take a sheet of the graph paper with the 31cm dimension running from left to right, as in Fig. 2, and choose a point 11cm from the left hand border along the bottom edge of the ruled area as the centre from which the three scales radiate. This will enable each scale to be 20 units (each 1cm) long.

A line may be drawn along the bottom edge to give scale OC, after which lines can be drawn on the paper to give scales OB and OA. The requisite angles can be set with a protractor or a 60°/30° set-square if available. The scales are graduated along the lines in cm and mm. This may be done for OA and OB simply by cutting strips from a second sheet of graph paper and sticking them in position alongside the lines with transparent tape or gum. The scales can represent ohms or picofarads to any power of ten required, but the multiplier must be the same for each scale.

PROOF

The relationship between the lengths read on the three scales may be proved by similar triangles. If corresponding angles of two triangles are equal then

the lengths of each pair of corresponding sides are in the same ratio.

Fig. 3 shows the three graduated scales meeting at a point O with the straight edge cutting them at A , B and C , giving scale lengths of a , b and c . Add the perpendiculars AD and BF .

From the similar triangles ADC and BFC ,

$$\frac{AD}{BF} = \frac{DC}{FC}$$

$$= \frac{DO + OC}{OC - OF} \dots (1)$$

From the similar triangles ADO and BFO ,

$$\frac{AD}{BF} = \frac{AO}{BO}$$

also since these triangles have angles of 30° , 60° and 90° ,

$$\frac{DO}{OF} = \frac{\frac{1}{2} AO}{\frac{1}{2} OB}$$

Substituting in (1),

$$\frac{AO}{BO} = \frac{\frac{1}{2} AO + OC}{OC - \frac{1}{2} OB}$$

$$\therefore \frac{a}{b} = \frac{\frac{1}{2} a + c}{c - \frac{1}{2} b}$$

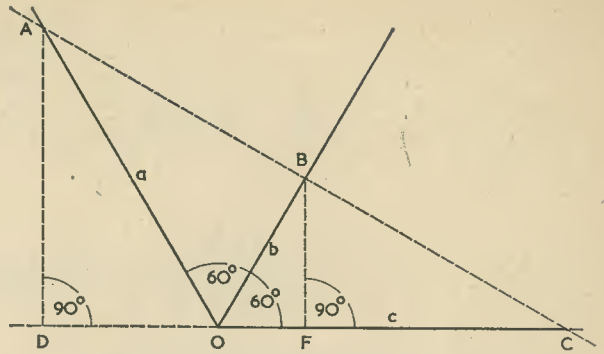


Fig. 3. Illustrating how the lengths of OB , OA and OC satisfy the equation for two resistances in parallel

$$\therefore ac - \frac{1}{2} ab = \frac{1}{2} ab + bc,$$

$$\therefore ac = ab + bc.$$

Dividing through by abc ,

$$\frac{1}{b} = \frac{1}{c} + \frac{1}{a}$$

The lengths read on the three scales thus obey the equation for parallel resistance or series capacitance. ■

QUEEN'S AWARD FOR BBC

Four years ago, a special Queen's Award to Industry was instituted to give public recognition to British industrial firms for outstanding achievement in the fields of export or technological innovation. This year, one of these highly coveted awards has gone to the BBC for its development of television standards converters, which make international exchanges of television programmes possible by changing the scanning standards and colour system of one country into those of another.

Through the inventions of its own engineers, the BBC was able to design and construct the first equipment capable of converting electronically both scanning standards and colour systems. The first electronic field-store standards converter, to give it its full name, was brought into use in 1967, when, for the first time, transatlantic colour television, transmitted via the Early Bird communications satellite, was broadcast in Britain. The converter provided colour pictures of very good quality, but the conversion process used resulted in the picture being somewhat reduced in size.

The second BBC converter, known as the advanced field-store television standards converter, brought a complete solution to the problem, the output pictures being of full size. This advanced unit has been described as the most intricate, complex and sophisticated piece of broadcasting equipment the BBC has ever used for television broadcasting. It was completed in time to provide Britain and other European countries with high quality live colour pictures of the Olympic Games from Mexico last year, and is now used regularly in the BBC television services. Nine countries used the output of the converter as a source of colour pictures from Mexico; and an additional eighteen countries, which were not yet ready to transmit colour, transmitted the pictures in monochrome.

The BBC has agreed that two British firms - Rank Precision Industries and Pye - can manufacture the BBC converter under licence and market it abroad. This will mean that high quality colour transmissions from America will be available to television audiences throughout the world. A Rank spokesman has estimated that there is a potential market for about a hundred of these converters, the first of which should be available next year.

ALARM FOR MAINS RADIOS

by

J. C. EADE, B.A.

This article describes successive steps in the design of a circuit which enables a modified alarm clock to switch on a mains-driven radio receiver. It must be pointed out that the circuits discussed here must only be employed with receivers having chassis which are isolated from the mains supply, and that the alarm clock wiring must be such that the clock frame connects to a reliable mains earth

TWO RECENT ARTICLES IN *THE RADIO CONSTRUCTOR* have described circuits which enable a transistor battery radio to be switched on in the morning by means of a modified alarm clock.* If a normal alarm clock is examined it will be seen that it has a metal disc concentric with the set alarm hand spindle, and that this disc moves forwards and releases the striker escapement at the preselected alarm time. In both the previous articles the clock was modified so that the disc, on moving forward, completed a circuit. This circuit was made via the clock chassis, the disc, and an additional contact mounted to the clock chassis by means of a small insulated block. In the first article the clock circuit connected a battery supply direct to a transistor radio. In the second circuit it triggered a thyristor which then switched on the receiver.

MAINS RECEIVERS

The author, having recently changed from a battery radio to a mains receiver, decided to see whether this could similarly be switched on by an adapted alarm

* A. G. Blewett, "Home Constructed Radio Alarm", August, 1967, issue; G. A. French, Suggested Circuit No. 217, "Thyristor Alarm Switch", December, 1968, issue.

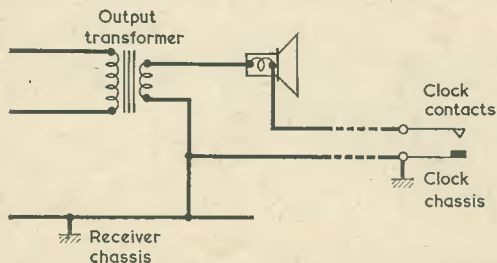


Fig. 1. A simple means of using alarm clock contacts to control a mains-driven radio

clock. Since it is essential that the clock switching circuit be isolated from the mains supply, it then becomes necessary to use a relay to switch on the set.

It must be emphasised at this stage that the circuits described in this article must only be used with a receiver whose chassis is reliably earthed and which is fully isolated from the mains by a mains transformer. On no account may the circuits be employed with a receiver whose chassis is connected to one side of the mains. The alarm clock must be wired so that its chassis connects to the receiver chassis. If a 2-way plug and socket is used between the receiver and the clock circuit, this must be of a non-reversible type.

The first circuit tried is that shown in Fig. 1, and it operates by simply inserting the clock contacts in series with the loudspeaker. This system works, of course, but it suffers from several disadvantages. First,

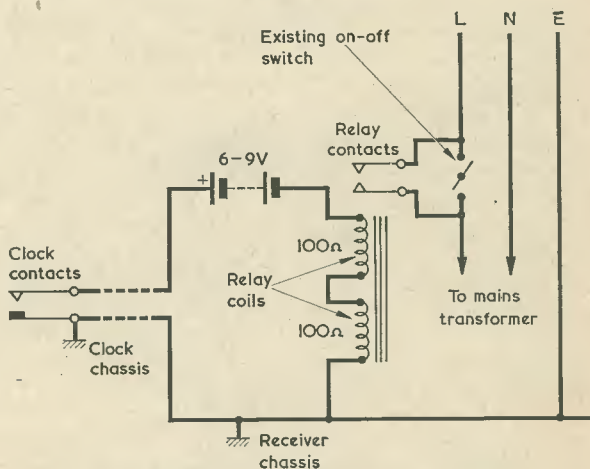


Fig. 2. Here, the contacts switch the receiver by way of a relay. The receiver should have a single-pole on-off switch inserted in the mains line input

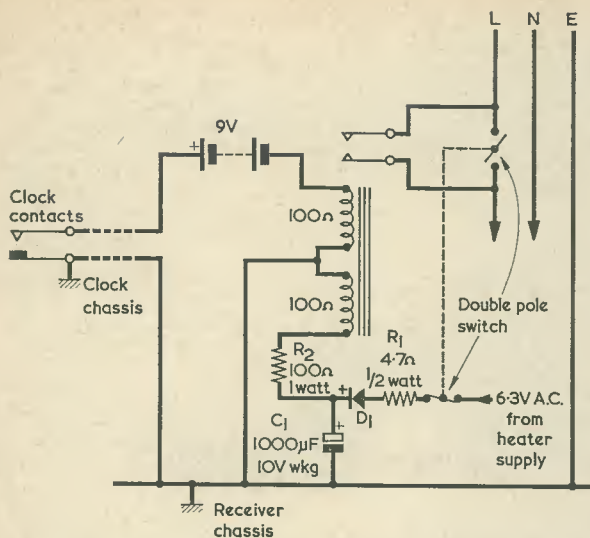


Fig. 3. A circuit in which the relay latches on when energised. A double-pole on-off switch is now required, the second pole being wired in the latching circuit

the receiver has to be left switched on. Second, damage can occur to the output transformer of some sets, due to high a.f. voltages in the primary, if the secondary does not have a load. (The author's set is a communications receiver and is so designed that the loudspeaker circuit is open-circuited for phones operation, anyway.) Third, the loudspeaker would only be connected for as long as the contacts in the clock remained closed. (However, in the author's case this occurred for about an hour and was not really a disadvantage.)

It was decided that something a little less crude was required, and this led to the circuit shown in Fig. 2, where a relay is used. The main disadvantage here (apart from the fact that the receiver is only switched on over the period when the clock contacts are closed) is that the relay continually draws current from the battery. The relay employed by the author had a double coil of 100Ω plus 100Ω and these two in series would draw 45mA from a 9-volt battery. Such a current is far too high for economic running.

To eliminate the heavy battery drain it was therefore decided to develop, first, a self-latching relay circuit and, second, a means of triggering the relay without causing a continuous battery drain. Fig. 3 shows the next circuit, which is self-latching. A double coil relay is necessary and also a double-pole mains switch to break the self-latching circuit. Otherwise there would be no way of switching the receiver off other than taking the mains plug out. There is no point in the circuit of Fig. 3 unless the battery voltage can be applied only momentarily. If an alarm clock can be adapted so that the contacts are closed for a short period only, then this circuit would be suitable.

FINAL CIRCUIT

As we have seen, Fig. 3 is only a partial solution since the heavy battery drain is still not eliminated. What was now required was some simple way of

obtaining a single pulse from the battery so as to just initially energise the relay.

Fig. 4 shows the final circuit. The charging current taken by C2 is sufficient to close the relay for a short moment, after which the current taken from the battery falls to a level depending largely on R3, and also on the capacitor leakage current. R3 is necessary in order that C2 may be sufficiently discharged, after the clock contacts open again, to enable a large enough current to flow to energise the relay when they next close.

Several values for R3 were tried. With R3 at 100kΩ the minimum time between operations was 10 minutes and the eventual current drain from the battery, with the clock contacts closed, was 100μA. A value of 1MΩ increased the minimum time between operations to 30 minutes, with an eventual current drain of 12μA. If R3 was omitted the minimum time between operations rose to several hours, with the eventual current drain depending on the condition of C2. In the writer's case the eventual current was less than 5μA. It was decided that, for reliability, the best value for R3 would be 1MΩ.

A high degree of smoothing is given to the rectified heater voltage by C1, this smoothing being introduced for two reasons. Firstly, if there were no smoothing the relay would act as a transformer, turning the pulsed d.c. into a.c. and causing alternating current to flow in the battery circuit. Secondly, C1 acts as a reservoir capacitor and prevents the relay unlatching due to momentary interruptions of the mains supply—which seem to be common in the author's area.

An important point is that the battery must be connected with correct polarity. The relay will not latch if the two voltages applied to its two coils are working in opposition.

In practice, the circuit of Fig. 4 worked well. The relay should be safely mounted in place inside the set, care being taken to ensure that wiring carrying

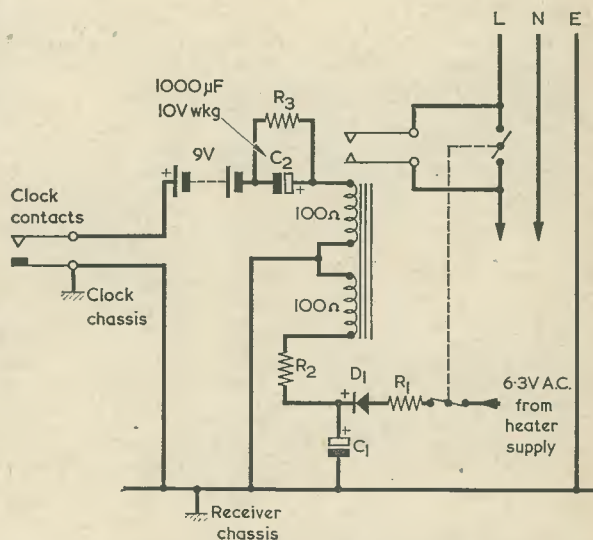


Fig. 4. The circuit finally devised. This requires only a short pulse of current from the battery to initially energise the relay. R1, R2 and C1 have the same values as in Fig. 3

high voltages cannot touch other wiring, including in particular the wiring to the clock. As already stated, the radio chassis *must* be connected to a reliable mains earth and the clock circuit *must* be connected so that its chassis is common to the receiver chassis. Do not work on the set unless the mains plug is out, don't rely on just switching off at the set itself.

Editor's Note

Post Office 3000 relays with 100Ω + 100Ω coils are

available from L. Wilkinson (Croydon) Limited, Longley House, Longley Road, West Croydon, Surrey, and for the present application should have twin platinum high voltage contacts. Only one make contact set is required. If a Post Office 3000 relay is employed, the relay metal-work should be insulated from the receiver chassis. R1 in Figs. 3 and 4 is a surge limiting resistor. Diode D1 may be a small silicon rectifier, such as the Lucas DD000.

First World Dx Club Convention

WORLD DX CLUB CELEBRATED the end of its first year of operations with a Convention held at the King Edward Hotel, Neath, in South Wales, over the weekend of June 20th/21st, 1969. A gathering of some 20 Dx'ers assembled there for a weekend of talks about the many problems which are currently concerning BC-band Dx'ers, and had a jam-packed programme of tapes and live items in the formal part of the programme.

WDXC President, Alan Thompson accompanied by his wife, Audrey, and son, David 'chaired' the informal Dinner which opened the proceedings on the Friday evening and read a list of greetings from overseas friends who were unable to be present: the greetings included kind wishes for the success of the proceedings from Anker Petersen, the President of the Danish Shortwave Club International, Gunhard Kock on behalf of Suomen Dx-Kuuntelijat r.y., Leo Van Der Walt of Radio South Africa, and many others.

The international assembly included many well-known British Dx'ers, amongst them being Charles Molloy (*Medium Wave News*), Noel Green (British Representative of the Danish SW Club International) and Martin Hall (who acted as co-chairman with the President throughout the weekend), whilst there was quite a sprinkling of well-known overseas guests present—they included Arthur Cushen and his wife, Ralda (from New Zealand); Maarten Van Delft (from Holland); Wolfgang Seyfried (from West Germany); Alan Roth (from the United States where he repre-

sents the Danish SW Club International), and Gerry Wood (one of the co-editors of *Contact*, the WDXC bulletin, who originates from Rhodesia). One of those with his feet in both camps—British and overseas—was Desmond Colling, the new Executive Editor of *Contact*, who now looks after the "Broadcast Bands" pages of *Monitor* for the I.S.W.L., and who is often heard over HCJB Quito, with contributions to "Dx Party Line" where he represents the American SW Listeners Club.

Following a delightful dinner, the drinks and the talk flowed freely until the small hours of Saturday morning whilst those present got to know one another and had an opportunity of poring—with avidity and, maybe, just a small touch of jealousy!—over the magnificent QSL albums which Arthur Cushen had brought with him from New Zealand. The Pacific Islands album, with its semi-nude maidens adorning numerous QSL's from "exotic" places and stations, was overwhelmingly voted (by the men present!) the high-light of Arthur's whole magnificent collection which now runs to something over 5,000 QSL's from 200-plus countries.

On Saturday morning, the Convention members were accorded a Civic Welcome at Neath's new Civic Centre by the Mayor and Mayoress of Neath (Councillor and Mrs. Leslie Morris) who showed much interest in the Club and the Dx hobby, whilst the visitors admired the superb views obtainable from the upper storeys of the fine building, and warmed to the cordial hospitality afforded them in the sumptuous Mayoral Parlour, and eagerly

accepted the Mayor's invitation to sign the official visitors' books.

The formal part of the proceedings started early on Saturday afternoon and were a mixed bag of live and taped talks on all aspects of the Dx hobby—discussion ranged fast and free! Arthur Cushen and Maarten Van Delft delivered short talks on the work of the Dx parliament (recently held in Sweden) and on the European Dx Council, immediately after the Club President, Alan Thompson, had spoken on the theme of "Dx Clubs and Bulletins—Now and in the Future". Many issues arising from this part of the agenda showed that there is much concern that EDXC should not proceed without some participation by Britain and Alan Thompson was able to announce that he had been invited to take part in the activities of a Working Committee of EDXC which is to look at the question of 'Club' versus 'Country' representation in that body.

On the real Dx side of the proceedings, Noel Green delivered a talk—with lots of excellent taped loggings—of his Afro-Asian Dx, whilst Charles Molloy enthralled his audience with some superb extracts from his tape library of medium-wave Dx. Nostalgia was the mood for 30 minutes whilst Clive Jenkins reviewed the 'pirate' scene, and from North America, Bill Matthews treated us to a round-up of the many types of North American stations as they are heard on his side of the water! A very interesting 15 minutes was spent, too, listening to Malcolm Peddar talking about the early days of the small Club which he started six years ago and which has now grown into World Dx Club—those present must have felt some surprise that the puny babe had grown into the healthy lad it is today!

Following a break for more refreshments, the Club President presented

THE RADIO CONSTRUCTOR

a "Dx Quiz" on tape from which ordeal, Noel Green emerged as the winner (see picture) – with the restoration of order (the President refusing to accept a motion that he was clearly sadistic to have concocted such an item!), the meeting passed into "Open Forum" and discussed a very wide range of subjects ranging from the technical to the organisational: from the humorous to the most serious! With such a widely drawn gathering it was inevitable that much was said "off the cuff" and it would, perhaps, not be wise to report this part of the proceedings in too much detail!

As 11 p.m. approached, the President brought the Convention to a close and the informality returned with the guests moving to the President's home where the discussion continued well into the night on many differing subjects—your reporter recalls barging through one group sitting on the stairs arguing the merits of various types of report letters: breaking up another argument about mini-skirts (what have they to do with Dx'ing?) in order to complete a taped record of an interview with every guest, whilst his shack was occupied by ten or 12 arguing whether he really had had Vatican Radio's interval signal on that 'Quiz' tape (no – he didn't!).

Throughout Sunday we said various 'goodbyes', and 'see you's' and finally it was all over! Was it a success? If you judge it in terms of what was achieved we shall not know the answer until we have had a chance to see what emerges from



Alan Thompson, President of World Dx Club (right) presents Noel Green with a bound volume of The Radio Constructor as the first prize in a "Dx Quiz", which was part of the First WDXC Convention held in Neath, on June 20th and 21st, 1969. Noel Green, who specialises in Afro-Asian Dx on the 60 metre broadcast band, is currently the British Representative of the Danish SW Club International, as well as being one of the 'Logbook' Editors of 'Contact', which is published by WDXC

it. However, in terms of helping to exchange ideas and views in free and frank argument there can be

no argument – it was a great success and we look forward to Convention 1970!

INTERNATIONAL RADIO ENGINEERING AND COMMUNICATIONS 1969 EXHIBITION

The 1969 Exhibition will again be held at the Royal Horticultural New Hall, Greycoat Street, Westminster, London, S.W.1, from 1st to 4th October.

Cable & Wireless Ltd. will be taking part for the first time, and we are pleased to announce that their Chairman, Colonel D. McMillan, C.B., O.B.E., has kindly consented to open the Exhibition on Wednesday, 1st October, at 12 noon.

An innovation last year was the display by the Diplomatic Wireless Service; as a follow-on this year the main stage feature will be presented by Cable & Wireless Ltd.

Of topical interest will be the large centre satellite set-piece and operations equipment shown by the Royal Air Force. The Royal Navy will have a greater display than before of radio and test gear, and the Royal Signals A.R.S., and the General Post Office will again be demonstrating various equipment and projects.

Manufacturers will have on show the world's latest radio receivers and transmitting equipment, test gear, hi-fi and components, as well as new developments in s.s.b. transceivers.

A feature which is always awaited with avid interest is the live transmitting station at the Exhibition. This will be in communication with stations throughout the world, using remote control and also a.m., s.s.b., phone, c.w., modes and teleprinter.

Another annual event is the Construction Contest. The winner will be awarded the annual Silver Plaque, and there will be many other awards and certificates.

Technical book sales at the 1968 Exhibition broke all records and the actual cash sales averaged over £1 per head of total attendance. Another record was the number of visitors from abroad.

International Day will be held on Friday, 3rd October, and this will end with a reception in the evening.

The Exhibition will be open from 10 a.m. to 9 p.m. from Wednesday, 1st October, until Saturday, 4th October, at an admission price of 3/6d.



Cover Feature

SOLID STATE D.C. VOLTMETER AND A.C. MILLIVOLTMETER

by

G. A. STANTON, G3SCV

This neat and ingenious design enables both a d.c. voltmeter and an a.c. millivoltmeter to be combined in a single unit sharing a common meter. Special features are f.e.t. input for both d.c. and a.c., and simplified construction on a single aluminium panel. Only one d.c. and one a.c. voltage, both monitored by an external meter, are required for calibration

TWO OF THE MOST USEFUL INSTRUMENTS FOR THE constructor's test bench are the electronic d.c. voltmeter and the a.c. millivoltmeter. The former enables d.c. voltages to be measured without loading the circuit under test, and the latter enables low voltage measurements to be made in a.c. circuitry. The millivoltmeter is particularly useful in testing audio equipment. In pre-semiconductor times both instruments tended to be bulky due to the valves used and to the related power supplies. In those days an attempt to combine the two units would have resulted in an even bulkier instrument and was generally considered impractical. Using semiconductors and modern components and circuitry both instruments can easily be miniaturised, and it is quite practical to combine the two as has been done in the unit to be described. This dual purpose unit not only saves space on the bench, but also saves expense, for one indicating meter serves for both functions.


The specification for the combined voltmeter and millivoltmeter is given in the accompanying Table.

D.C. VOLTMETER SECTION

The basic circuit of the d.c. voltmeter section of the instrument is given in Fig. 1(a) and it will be noted that this incorporates an inexpensive field effect transistor. If the circuit is redrawn as in Fig. 1(b) it will be seen that the f.e.t. forms one arm of a bridge circuit. With no input the circuit is balanced by means


of VR2 so that the indicating meter M1 reads zero. If a small d.c. voltage is applied to the gate of the f.e.t. the balance of the bridge is disturbed and an indication given on the meter, the indication being proportional to the voltage applied to the input. Experiments showed that using the components given, full-scale deflection could be obtained with an input of less than half a volt. By means of VR1 in series with the meter the sensitivity can be reduced and this enables the instrument to be adjusted for calibration purposes. With the lowest range set to read 0.5 volt full scale, the instrument is remarkably linear in operation.


The field effect transistor—unlike its bipolar cousin—has a very high input resistance, the input characteristics being very similar to those of a valve. Because of this, the input resistor network in Fig 1(a) totals 11M Ω , and gives a sensitivity of 22M Ω per volt on the lowest range and 22,000 Ω per volt on the highest range. This is similar to many of the valve voltmeters in current use, but is achieved at a much lower cost.

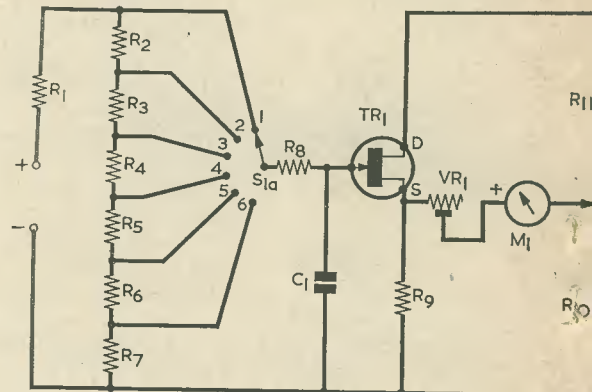

(a)

Fig. 1(a). The basic circuit
(b). The d.c. voltmeter m

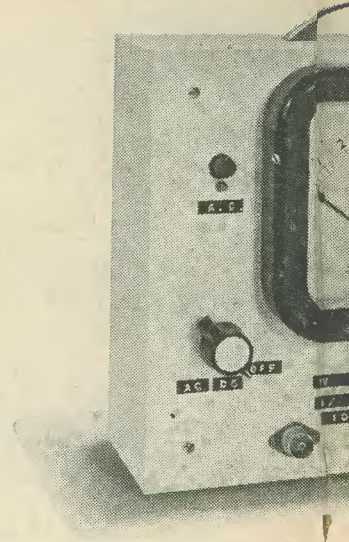

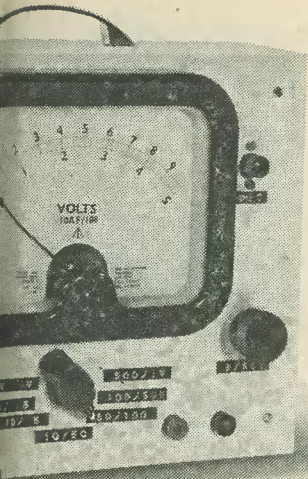

MILLIVOLTMETER SECTION

The circuit of the a.c. millivoltmeter section appears in Fig. 2. This, it will be seen, is basically a small signal amplifier the output of which is measured by a full wave rectifier and meter system. Input is fed via C2 and R28 to the gate of TR2, a field effect transistor connected in a "source follower" configuration. This is the f.e.t. equivalent of the familiar valve cathode follower and, like the cathode follower, it has an extremely high input impedance combined with a low output impedance. This stage gives no amplification but acts as a buffer between the circuit under test and the amplifier proper. Due to the high input impedance, measurements can be taken without undue loading effects.

The function of zener diode ZD1 is to prevent excessive voltages being applied to the gate of TR2, with consequent risk of gate-source breakdown. Without ZD1 such voltages could appear for a short period if the input were applied, with C2 discharged, to two


points having a high d.c. potential between them. The zener diode limits positive-going voltages by acting as a zener diode and negative-going voltages by acting as an ordinary diode. The diode used by the author was a Texas 1S7075A, this being a 7.5 volt 400mW type. However, any small zener diode having a zener voltage between seven and ten may be fitted in the ZD1 position.

Output from TR2 is taken from its source, the load being the attenuator network comprising R13 to R18. The values of the resistors in this network are chosen to give six ranges from 5mV full scale to 1 volt full scale.

The amplifier proper consists of TR3 and TR4. The main requirements here are threefold. There must be sufficient gain to enable an input of less than 5mV to give full-scale deflection on the meter; a flat frequency response over at least the audio range; and linearity of operation. These requirements are achieved with two direct coupled n.p.n. silicon transistors and ample negative feedback. The frequency response is flat from 40Hz to well over 20kHz; at 20 Hz, output is 3dB down. The gain of the amplifier can be controlled by means of VR3 and this provides for adjustment of calibration in use.

On low ranges meter and rectifier combinations are non-linear in operation, due to the characteristics of the rectifier diodes. In the present instrument non-linearity is reduced to acceptable proportions by means of R26 and R27. For extreme accuracy the meter scale would still have to be specially prepared and calibrated, but for ordinary test purposes the accuracy with the existing meter scale has been found adequate.

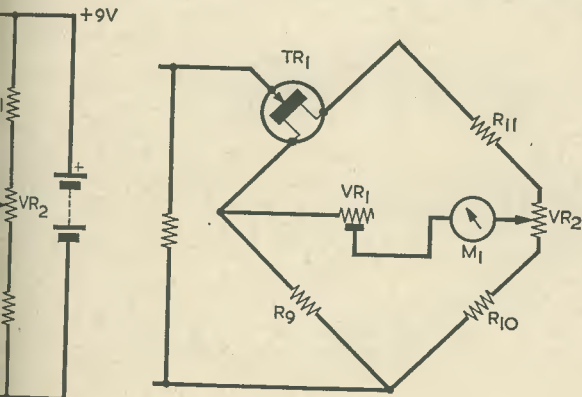The emitter of TR4 requires a high bypass capacitance to the negative supply line. This is provided here by connecting two electrolytic capacitors, C4 and C5, in parallel.



(b)

of the d.c. voltmeter section
y be presented as a bridge

SEPTEMBER 1969

TABLE

Solid State D.C. Voltmeter and A.C. Millivoltmeter
Specification.

D.C. Ranges: Input resistance 11M Ω

A.C. Ranges: Input impedance 6.8M Ω

Frequency response flat from 40 Hz to
20kHz (3dB down at 20Hz)

Range	D.C. (volts)	A.C. (mV r.m.s.)
1	0.5	5
2	5	10
3	10	50
4	50	100
5	100	500
6	500	1,000

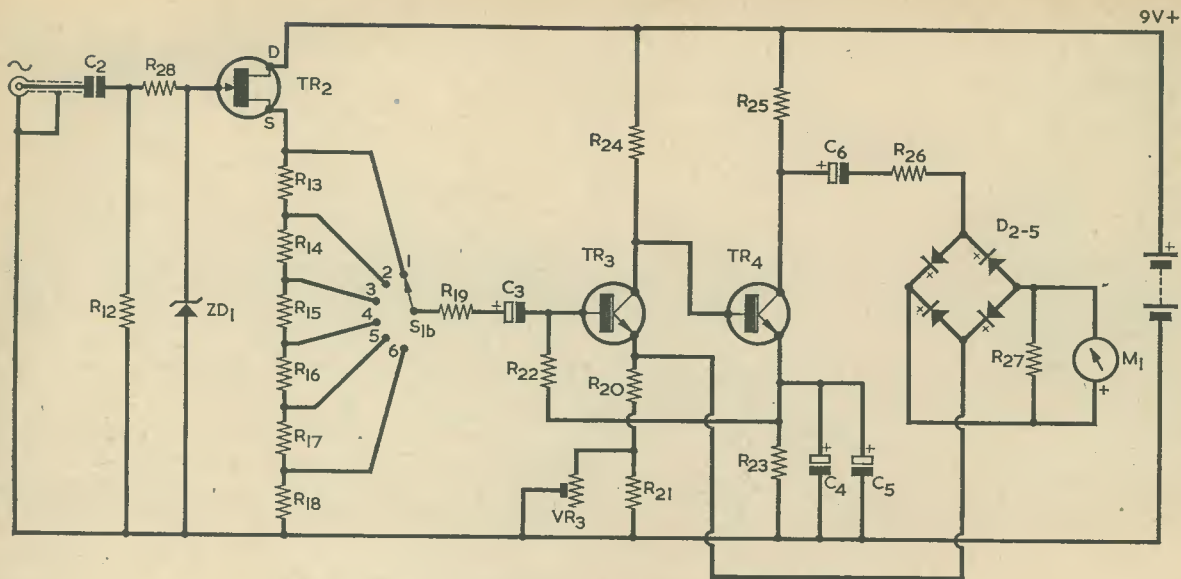


Fig. 2. The basic circuit of the a.c. millivoltmeter section

COMBINING THE SECTIONS

If desired the sections as described so far could be built as separate units, the only additional component needed being an on/off switch for each circuit. Separate units would, however, mean two indicating meters, two range switches, two batteries, two panels and two cabinets. A considerable saving can be made if the units are combined as in the full circuit, which is given in Fig. 3. In fact the only additional component needed to combine the two units is the four-pole three-way switch, S2. This is the function switch and, as

such, connects the meter to the d.c. and a.c. sections in turn and switches the instrument off. In the off position it short-circuits the meter and thus damps the movement, preventing any damage in transit. Additional protection is afforded to the meter by means of the silicon diode (D1) wired in parallel. The diode prevents damage should excessive current flow in the meter circuit.


The battery is connected to both sections of the instrument simultaneously, and this ensures that C6 is fully charged before the meter is connected to the millivoltmeter section, thereby preventing the sudden surge through the meter which would otherwise occur. It is thought that the protection to the meter given by this mode of operation is worth the extra drain on the battery. The total current consumption is still under 8mA.

It was found, with the prototype, that battery voltage could be reduced to 7.5 volts without unduly affecting the performance. In consequence, it was decided not to include a supply voltage stabilising circuit. The only critical factor, as supply voltage drops, is the "zeroing" of the d.c. section.

The meter may be any standard moving-coil instrument with an f.s.d. of $50\mu\text{A}$. That employed by the author was an ex-R.A.F. type with an internal resistance of $2,500\Omega$. Its scale was re-marked for the present application.

A minor point which needs to be mentioned with reference to Fig. 3 is that the inset showing the f.e.t. lead-outs indicates that the drain lead-out is in the centre, whereas some (but not all) Motorola literature shows the source as the centre lead-out. In practice, the source and drain of the MPP105 are interchangeable since this is a symmetrical transistor. TR1 and TR2 are connected to the printed circuit boards (described later) with the lead layout given in Fig. 3.

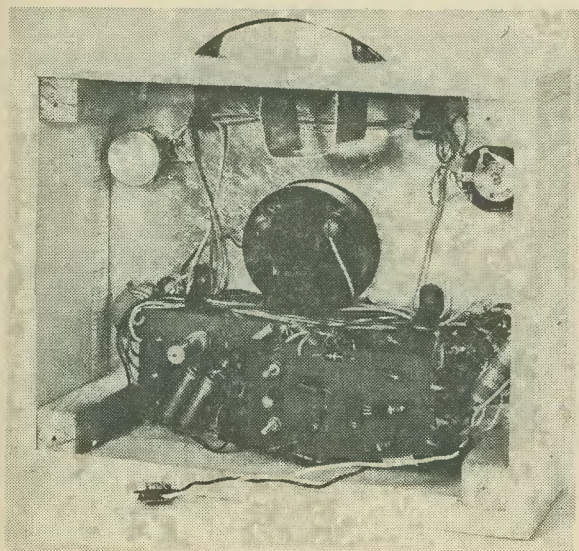The 2N2926 Yellow transistors specified for TR3 and TR4 are the basic 2N2926 with an hfe between 150 and 300. They are available from a number of



An inside view of the instrument. The clamp at the top secures the battery in position when this is fitted

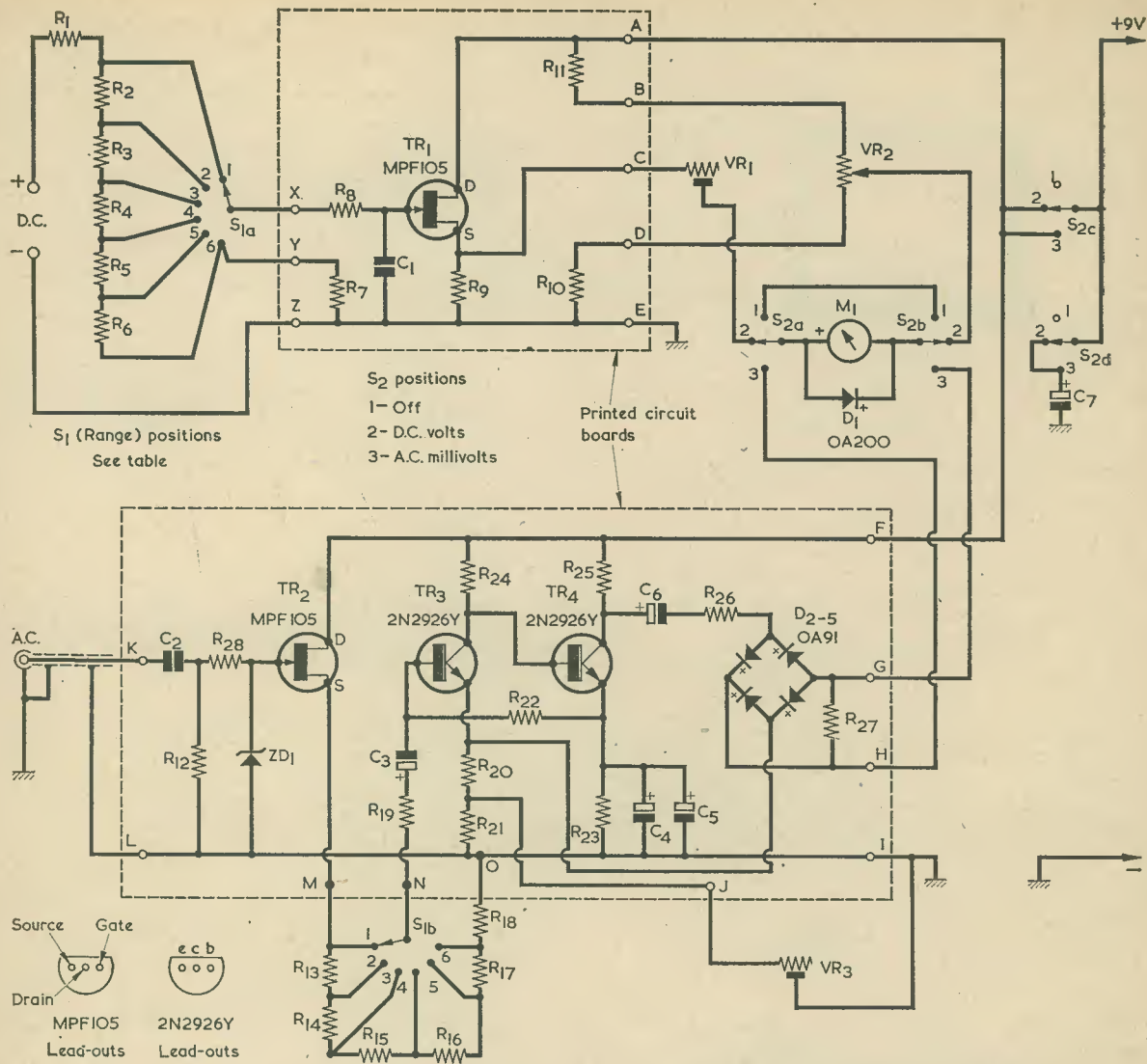


Fig. 3. The complete instrument, offering both d.c. voltmeter and a.c. millivoltmeter facilities

suppliers, including Electrovalue, 32a St. Judes Road, Englefield Green, Egham, Surrey.

CONSTRUCTION

Construction is quite straightforward and the general layout is given in Fig. 4. All the larger components are mounted direct to a 16 s.w.g. aluminium panel, there being no "chassis" in this instrument. The range switch is of the "Maka-Switch" type and two printed circuit boards carrying the smaller voltmeter and millivoltmeter components are mounted to the side-struts of this switch in a manner which is described in detail later. The exact dimensions of the panel will largely depend upon the meter employed. This in the author's case is a large type with a 5in. scale, but even so the whole instrument easily fits into a plywood cabinet 8in. high, 10in. wide and 3in. deep.

The two sections of the instrument are built on separate panels of printed circuit board, details of which are given in Figs. 5(a) and (b). In these two diagrams the copper side of the board is towards the reader. Assembly of the boards follows standard practice except for the input components of the millivoltmeter panel of Fig. 5(b). Because of the sensitivity of the circuit, TR2 and C2 are very prone to hum pick-up and require screening. In the prototype the f.e.t. is screened by having a coil of 22 s.w.g. insulated connecting wire slipped over it, with the end of the coil anchored and soldered to an earth point on the panel. The coil is formed by close-winding eight turns round a ¼in. rod, leaving a tail for the earth connection. See Fig. 6. This in practice forms an effective screen. Capacitor C2 is screened by wrapping a length of metal foil around it, this being secured by a few turns of bare 22 s.w.g. wire soldered together. This operation should be carried out before assembly


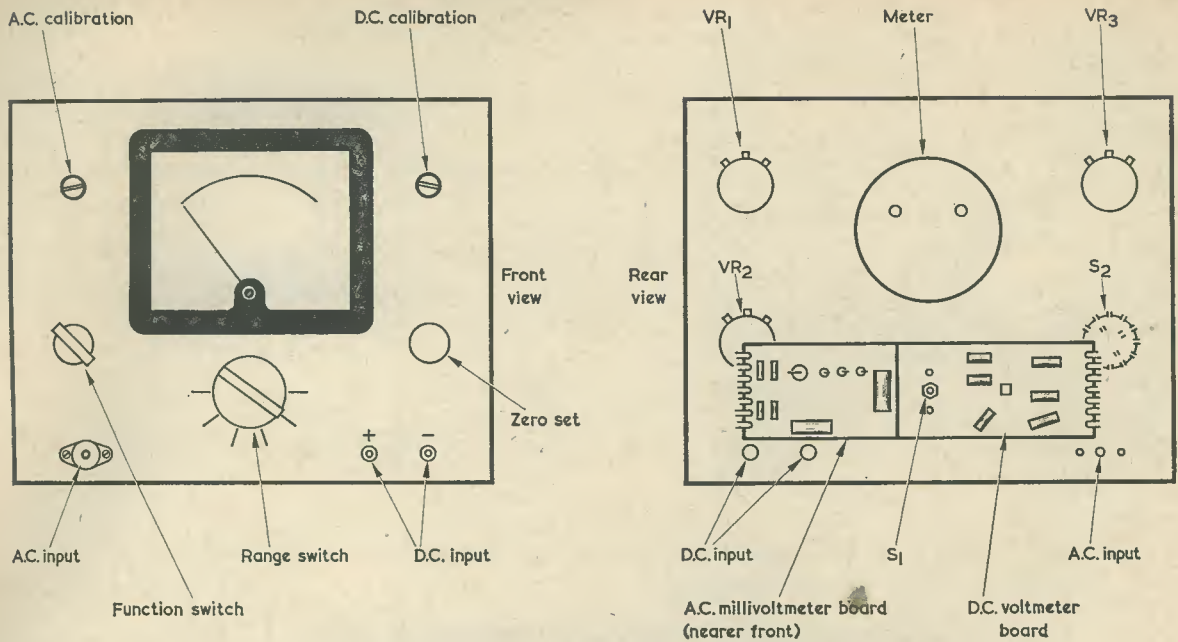


Fig. 4. Front and rear views of the panel, on which the larger components are mounted. The two printed circuit boards are affixed to the range switch

and care taken that the screen does not touch either of the capacitor's leads. When fitted, the screen should be connected to an earth point near the capacitor.

In the d.c. section (Fig. 5(a)) the value of R11 will depend upon the particular MPF105 used. Taking a number of these at random R11 was found to vary from 1k Ω to 5k Ω . In view of this a small skeleton type 5k Ω pre-set potentiometer could be substituted and adjusted accordingly. Alternatively R11 can be a 6.8k Ω fixed resistor plus a second resistor wired in parallel during the final setting up process.

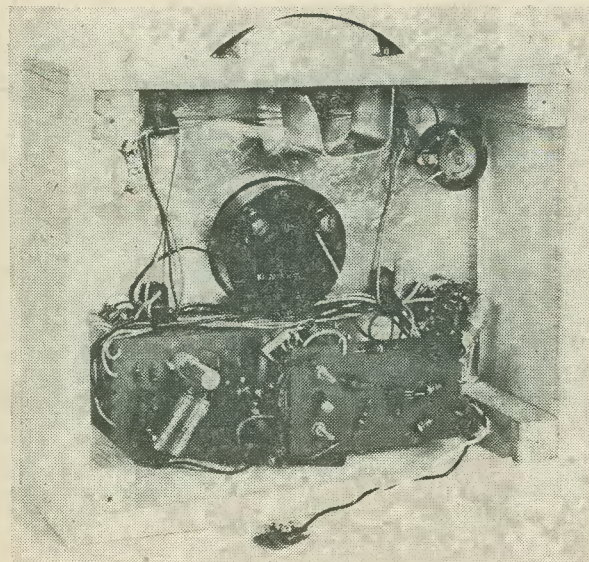


Another rear view. Note the two printed circuit boards secured to the range switch assembly

The printed circuit panels are completed by adding suitable lengths of connecting wire to the various terminal points, including those for connection to S1. If wires of different colour are available construction will be that much easier. In this respect it should be noted that interconnections between printed circuit boards, components mounted on the main panel and the range switch are all identified by letter in the circuit diagram of Fig. 3. The same letter coding is employed in Figs. 5(a), 5(b) and 7.


Assembly of the various sections is greatly facilitated if a definite sequence is followed. The first step is to mount the meter, controls and terminals to the front panel and, working from Fig. 3, complete all wiring which does not involve connections to the printed circuit boards or S1(a) and (b). The printed circuit boards appear inside the dashed line rectangles in Fig. 3.

The second step is to add the "Maka-Switch" mechanism. With this kit two side struts are included; the heads of these should be carefully removed and the "headless" struts screwed into position on the index mechanism. The struts are then locked into position by two 6BA nuts, care being taken not to foul the mechanism. Having done this the millivoltmeter panel is then slipped into position on the struts in the manner shown in Fig. 8, and the necessary connections made to other components on the panel. At this stage, the millivoltmeter panel will not be held down securely.

Before placing the switch wafer in position, this should be checked for correct functioning and resistors R2 to R6 and R13 to R17 wired into place as indicated in Fig. 7, which illustrates the wafer viewed from the rear. (R18 and R19, shown in Fig. 7, are already fitted to the millivoltmeter panel, as in Fig. 5(b).) In order to prevent any possibility of short-circuits during use a suitable length of sleeving should be

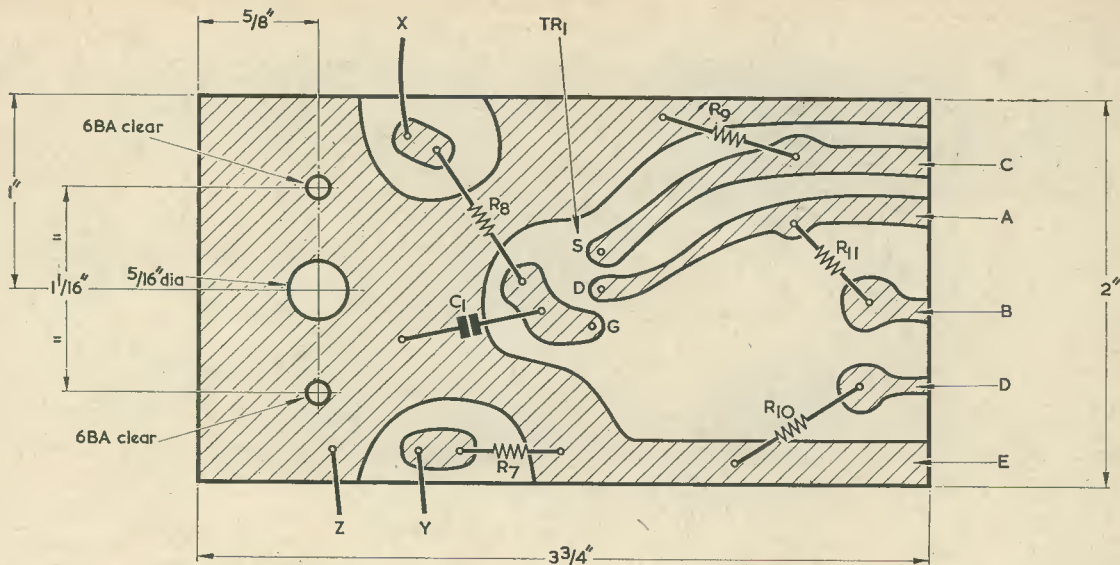

(a)

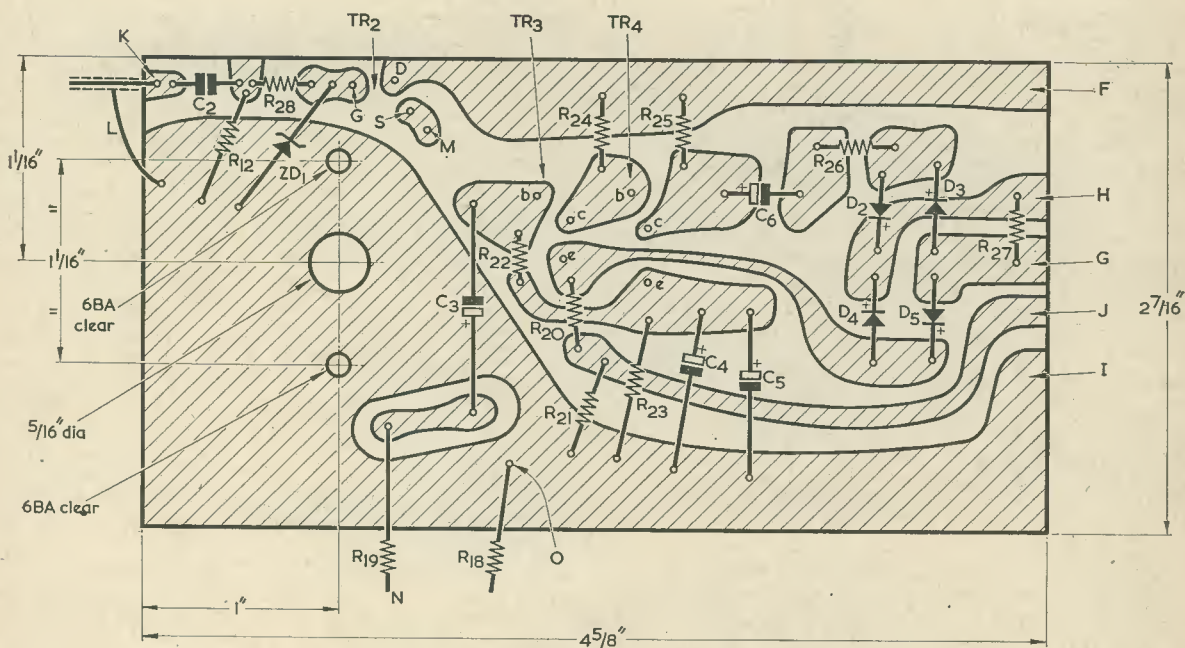

(b)

Fig. 5. The printed circuit boards for (a) the d.c. voltmeter section and (b) the a.c. millivoltmeter section, with copper side towards the reader. These are reproduced full size and may be traced, if desired

slipped over each resistor before mounting. The switch wafer is separated from the two panels by means of $\frac{1}{16}$ in. spacers, and is fitted so that the sides with R2 to R6 and R13 to R17 take up the positions indicated in Fig. 8. Complete the wiring between the wafer and the millivoltmeter panel and take a lead from the

wafer tag connected to the free end of R2 (see Fig. 7) to the d.c. positive terminal via R1. R1 is not mounted on the boards. Next add the voltmeter panel and secure the whole switch and circuit board assembly by the 6BA nuts of the side struts. The assembly should now appear as in Fig. 2. Connect all leads from

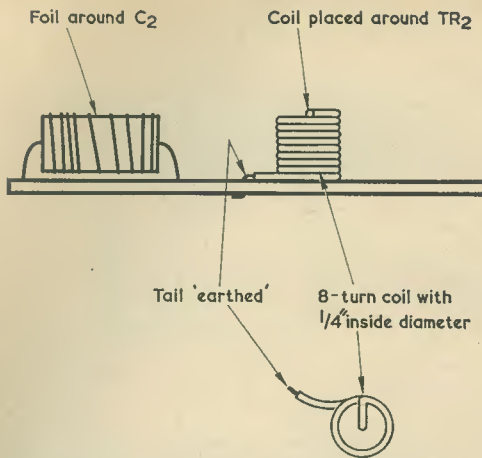


Fig. 6. Illustrating how TR₂ and C₂ are screened in order to reduce hum pick-up

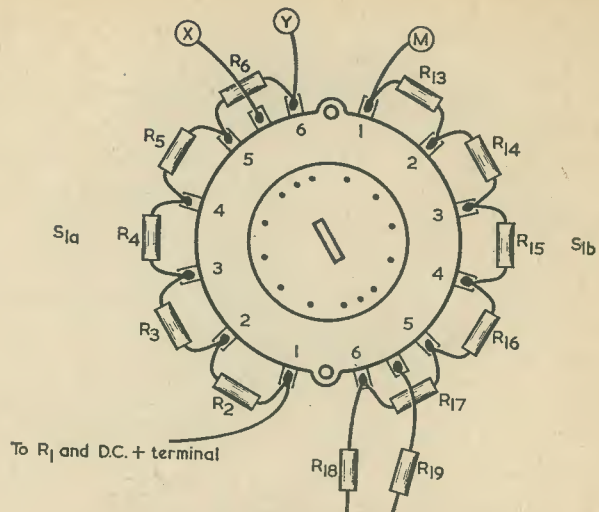


Fig. 7. Connecting the attenuator resistors to the switch wafer

the voltmeter panel and complete any other outstanding wiring.

This completes the construction of the instrument.

CALIBRATION

Before the instrument can be calibrated the value of R₁₁ in the voltmeter section must be determined. In order to do this VR₁ is set at maximum resistance and VR₂ at its mid-point position. If R₁₁ has been made a preset variable resistor this is adjusted until the meter reads zero and no further attention is required. If a 6.8kΩ fixed resistor has been wired in for R₁₁ then a 25kΩ variable resistor should be temporary clipped across it and adjusted for zero reading.

The variable resistor is then removed and its value measured; a second fixed resistor near this value is then soldered across R₁₁. The use of fixed resistors in this way is perhaps more trouble at this stage, but it is to be recommended for long term stability.

Calibrating the instrument is a simple process, and it is only necessary to provide one known direct voltage between 0.25 and 500 volts, and one known alternating voltage between 5mV and 1 volt. Figs. 9(a) and (b) show two suggested schemes. In Fig. 9(a) a 1kΩ potentiometer is connected across a 1.5 volt cell and adjusted to give a reading of 1 volt in any voltmeter known to have good accuracy. The instrument



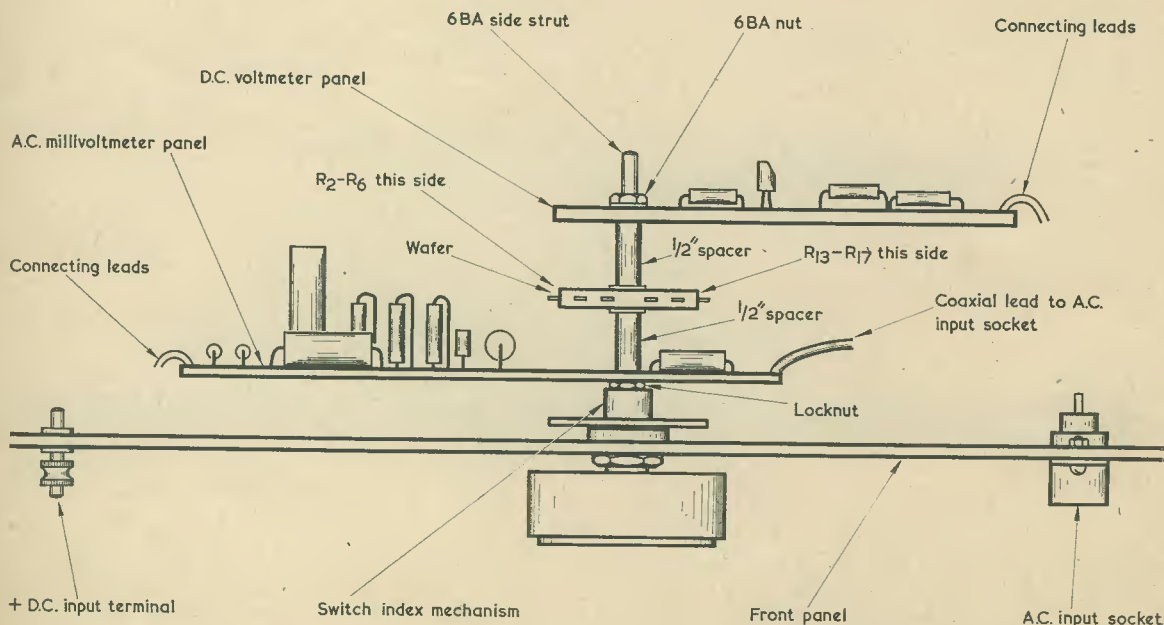


Fig. 8. The two printed circuit boards are affixed to the range switch in the manner shown here

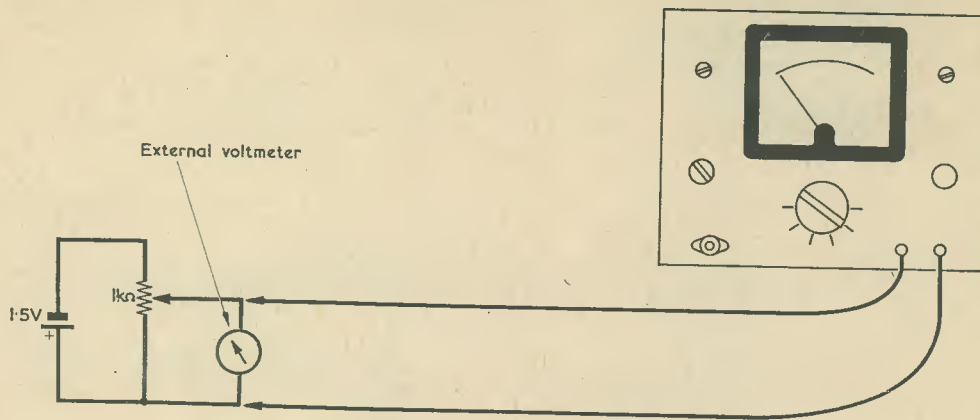

(a)

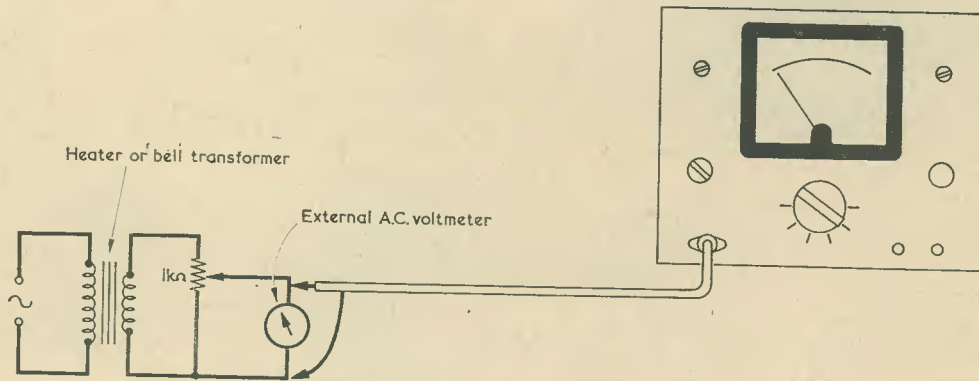

(b)

Fig. 9. Calibrating the d.c. and a.c. sections of the instrument. Each section requires only one calibration voltage

is first switched to read direct voltage and, without its test leads connected, set to zero by VR2. S1 is set to Range 2. The test leads are then connected across the external voltmeter and VR1 adjusted for a reading of 1 volt in the instrument.

In Fig. 9(b) a known alternating voltage of 1 volt (as monitored by an external meter known to have good accuracy) is selected by the $1k\Omega$ potentiometer. The instrument is switched to read alternating voltage, S1 is set to Range 6 and the test leads connected to the known source of voltage. VR3 is adjusted for a reading of 1 volt.

Both VR1 and VR3 are included on the front panel so that calibration can easily be checked and re-set during use.

The accuracy of the instrument will depend almost entirely on the two attenuator networks R2 to R7 and R13 to R18. For accurate work these should be

1% tolerance high stability types. Some of the values specified may be a little difficult to obtain from the usual mail order houses, in which case two resistors may be used in series or parallel. Thus, R2 could be $2.2M\Omega$ in series with $6.8M\Omega$. Similarly, R16 could be two 82Ω in parallel, and R17 and R18 each two 10Ω in parallel. If the experimenter requires indications rather than exact measurements, tolerances up to 5% could be substituted for R2 to R7 and R13 to R18. As already explained a degree of non-linearity is likely on the a.c. ranges and for extreme accuracy a graph could be plotted and used. A really keen constructor could of course calibrate the meter scale from this for accurate direct readings.

In use ordinary test leads are suitable for the d.c. ranges and a length of coaxial cable for the a.c. ranges. This should be kept as short as convenient in order to prevent losses on the higher frequencies.

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 5% unless otherwise stated.)

R1	1M Ω $\frac{1}{2}$ watt, hi-stab
R2	9M Ω 1%, $\frac{1}{2}$ watt, hi-stab (see text)
R3	500k Ω 1%, $\frac{1}{2}$ watt, hi-stab
R4	400k Ω 1%, $\frac{1}{2}$ watt, hi-stab
R5	50k Ω 1%, $\frac{1}{2}$ watt, hi-stab
R6	40k Ω 1%, $\frac{1}{2}$ watt, hi-stab
R7	10k Ω 1%, $\frac{1}{2}$ watt, hi-stab
R8	1M Ω
R9	4.7k Ω
R10	1k Ω
R11	See text
R12	6.8M Ω
R13	500 Ω 1%, $\frac{1}{4}$ or $\frac{1}{2}$ watt, hi-stab
R14	400 Ω 1%, $\frac{1}{4}$ or $\frac{1}{2}$ watt, hi-stab
R15	50 Ω %, $\frac{1}{4}$ or $\frac{1}{2}$ watt, hi-stab
R16	40 Ω 1%, $\frac{1}{4}$ or $\frac{1}{2}$ watt, hi-stab (see text)
R17	5 Ω 1%, $\frac{1}{4}$ or $\frac{1}{2}$ watt, hi-stab (see text)
R18	5 Ω 1%, $\frac{1}{4}$ or $\frac{1}{2}$ watt, hi-stab (see text)
R19	680 Ω
R20	10 Ω
R21	27 Ω
R22	6.8k Ω
R23	330 Ω
R24	6.8k Ω
R25	470 Ω
R26	1k Ω
R27	1k Ω
R28	1k Ω
VR1	10k Ω potentiometer, linear, preset (panel mounting)
VR2	1k Ω potentiometer, linear
VR3	100 Ω potentiometer, linear, preset (panel mounting)

Capacitors

C1	2,000pF ceramic
C2	0.33 μ F paper or plastic foil
C3	100 μ F electrolytic, 6V wkg.
C4	500 μ F electrolytic, 6V wkg.
C5	500 μ F electrolytic, 6V wkg.
C6	64 μ F electrolytic, 12V wkg.
C7	200 μ F electrolytic, 12V wkg.

Semiconductors

TR1	MPF105 (Motorola)
TR2	MPF105 (Motorola)
TR3	2N2926 Yellow spot (see text)
TR4	2N2926 Yellow spot (see text)
D1	OA200 (Mullard)
D2-D5	OA91 (Mullard)
ZDI	7.5 volt zener diode (see text)

Meter

M1	50 μ A moving-coil
----	------------------------

Switches

S1	Radiospares "Maka-Switch" kit, with one 2-pole 6-way wafer and four $\frac{1}{2}$ in. spacers*
S2	4-pole 3-way, rotary

Miscellaneous

Coaxial socket
2 terminals
3 knobs
Aluminium panel
Printed circuit board
9-volt battery

* Radiospares components may only be purchased through retailers.

CAN ANYONE HELP?

Requests for information are inserted in this feature free of charge, subject to space being available. Users of this service undertake to acknowledge all letters, etc., received and to reimburse all reasonable expenses incurred by correspondents. Circuits, manuals, service sheets, etc., lent by readers must be returned in good condition within a reasonable period of time.

Sobell TV T280 & Philips Radio 341A.—M. J. Levy, 19 Totternhoe Close, Kenton, Middlesex — manuals or data sheets, purchase or loan.

"Radio Constructor" July 1964. — G. Sawyer, St. Agnes, Elm Tree Road, Locking, Weston-super-Mare, Somerset — this issue of the magazine is required, particularly the article "Transistor Tape Recorder Circuits" Part 2. Loan or purchase.

Bush TV T99CB & HMV TV 6405S/T. — E. O. Odunfa, P.O. Box 1460, Ibadan, Nigeria — loan or purchase of service sheets for these models.

AVO Valve Tester No. 3. — Havering Technical College, Ardleigh Green Road, Romford, Essex — operating instructions required.


Taylor Valve Tester, Model 45B. — G. S. Ghataure, Box 10785, Nairobi, Kenya — would like to add noval base, can any reader suggest a circuit for this modification?

Hallicrafter SX71 Receiver. — G. W. Perkins, 35 Kingstown Road, Carlisle, Cumberland — loan or purchase of manual or circuit diagram — even information on the correct valve line-up would help!

RADIO CONSTRUCTOR

SPECIAL EXCLUSIVE OFFER

★ ROOF RACK

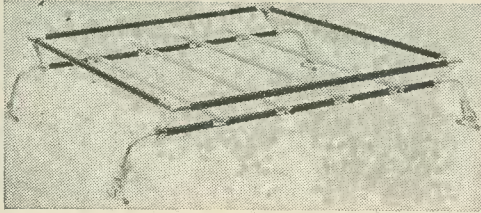


The Classic – a really new and handsomely designed roof rack. Made with high quality steel tubing and alloy castings. A fully collapsible model requiring only four bolts and four wing nuts supplied for its complete and rapid assembly. The framework is covered with a durable P.V.C. and the rack stands on the very latest type of gutter mountings. These mountings have very wide feet for maximum stability and are fixed to the car roof gutters via isolating polythene sleeves to prevent rusting. Carrying platform of 40" x 34" wide. List Price 99/6. **OUR PRICE 65/-** plus carriage 8/6

★ ESTATE CAR CONVERSION KIT


This converts the saloon kit into an estate car kit. Carrying platform becomes 75" x 34" wide.

List Price 99/6. **OUR PRICE 65/-** plus carriage 8/6

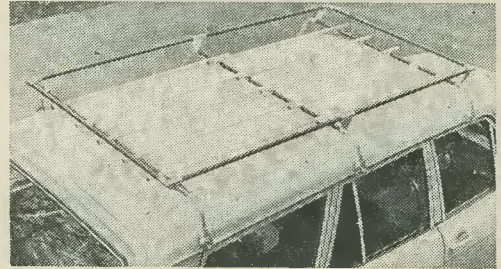If roof rack and conversion kit ordered together – carriage free




★ HEAD REST

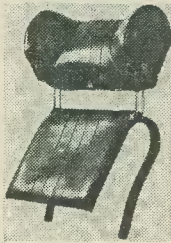

For comfort and safety! Latest Finish design. Suitable for all types of seating. Upholstered in first quality foam and covered in extremely durable P.V.C. Fully and easily adjustable for the widest range of height and angle. Available in black or red. List Price 59/6 **OUR PRICE 39/6** plus p. & p. 6/-

★ MASERATI AIR HORNS

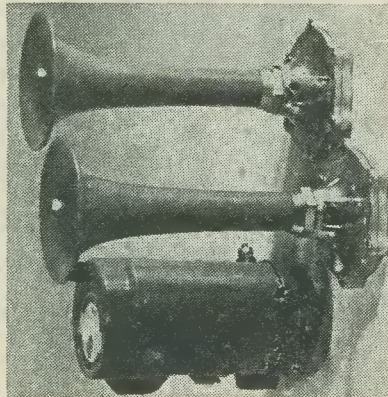

TS Sprint. Ideal for Motorway or Continental driving. Will fit under the bonnet of any car. Available in 6, 12 or 24 volts. This unit incorporates a new extra powerful compressor, which is only available with Maserati Air Horns. Extra tough red plastic trumpets, both 6½" long, base diameter of each 3". Compressor height 4½", diameter 2¼". Total weight, including box, 4¼ lbs. Complete with relay, tubing, securing nuts and bolts and fixing instructions. List Price 5 gns. **OUR PRICE 69/6** plus p. & p. 6/-

The above car accessories are first grade, high quality, and are covered by a **SEVEN-DAY MONEY BACK GUARANTEE**

Please send the following:—
(Please tick where applicable)

- Classic Roof Rack Head Rest
 Estate Car Conversion Kit Maserati Air Horns

Model and year of car..... Please state voltage required.....

I enclose cheque/crossed postal order for.....

Name

Address

BLOCK CAPITALS PLEASE

Please make remittances payable to our distributors:— **IVORYET LTD.** and send to:
RADIO CONSTRUCTOR SPECIAL OFFER, 57 MAIDA VALE, LONDON W.9

THE EDDYSTONE EC 958 RECEIVER

A NEW, SOLID-STATE RECEIVER, WHICH COVERS THE complete frequency range from the high frequency band down to the very low frequency band in a continuous sweep from 30MHz to 10kHz, and which provides facilities for high stability working, is announced by Eddystone Radio, Limited.

This new receiver, type EC 958, provides monitoring facilities over a wide range of frequencies which have previously required the use of two separate receivers, or elaborate 'add-on' units with a normal high frequency receiver. The low frequency band is still, of course, widely used for marine communications, broadcasting, and for a number of point-to-point services.

R.F. INPUT PROTECTION


The aerial input stage of the EC 958 receiver employs a junction MOSFET device with the high breakdown voltage of 25 volts. This circuit is further protected by four high-current silicon diodes, connected directly across the aerial input. These reduce on-tune signals to a maximum of about 2.4 volts peak-to-peak, while out-of-tune signals are further reduced by a high-Q bandpass input circuit which provides some 40 dB of attenuation at 10% off-tune. The input also has a trimming circuit incorporating capacitance diodes, which further protect the input circuits by de-tuning them when the r.f. potential exceeds some 5 volts.

This combination of circuit features provides a degree of protection to the completely solid-state r.f. circuits which compares favourably in this respect with a valve input. It also provides all the advantages of solid-state circuitry in terms of reliability and stability.

COMPLETE SPECTRUM IN TEN RANGES

Ten ranges cover the complete spectrum, from 30MHz down to 10kHz. The first four ranges cover the h.f. band. In these ranges, a triple conversion

(continued on page 111)


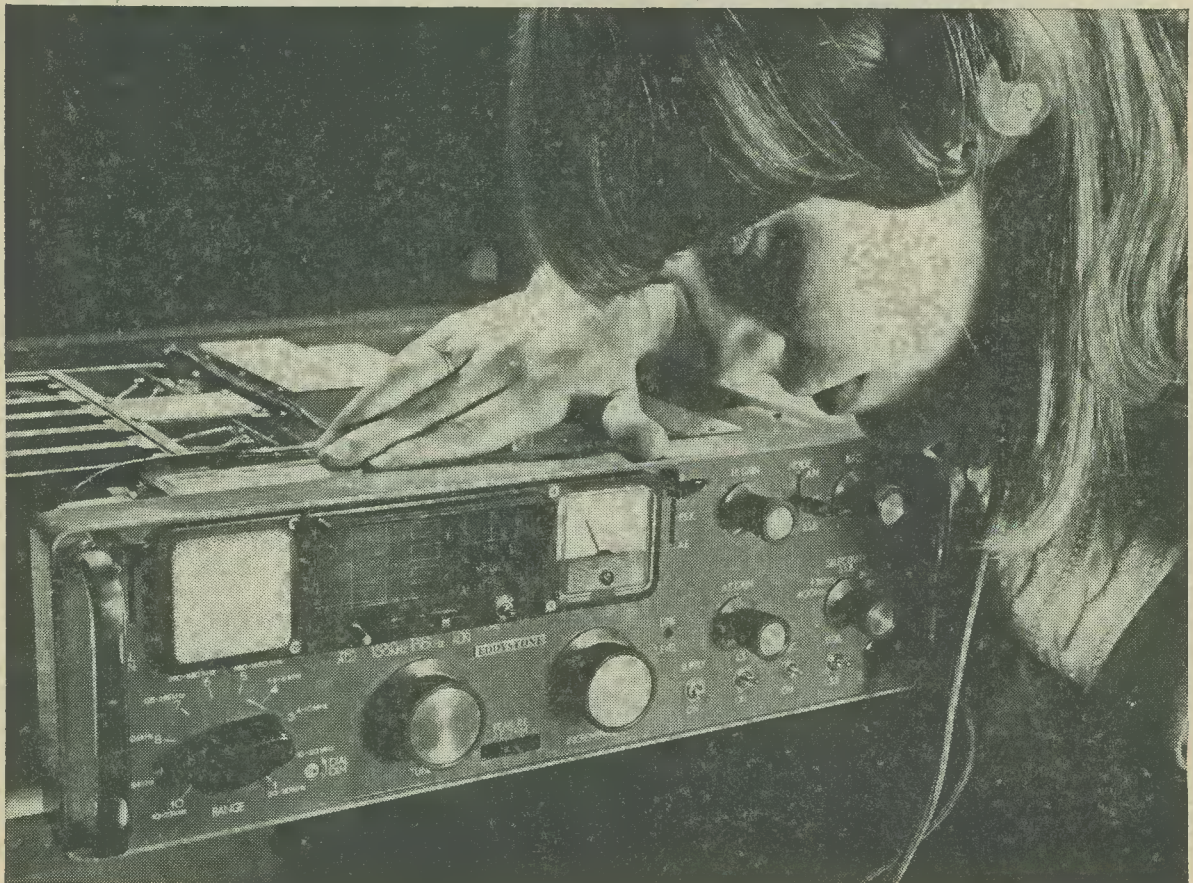


The EC 958 receiver is seen here with the main cover removed. The optical projection tuning scale is at the top of the front panel, beneath the operator's hand

UNDERSTANDING RADIO

THE Q-MULTIPLIER

$$f = \frac{1}{2\pi\sqrt{LC}}$$

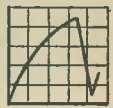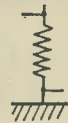

by W. G. Morley

IN LAST MONTH'S ISSUE WE EXAMINED THE MANNER IN which a quartz crystal may be employed to increase the selectivity offered by a superhet receiver. In this application the crystal appears in the i.f. amplifier of the receiver and it offers minimum attenuation to signals at its series resonant frequency. Since, in both its series resonance and parallel resonance modes, the crystal behaves like a tuned circuit having an extremely high value of Q , the crystal then functions as a sharply selective device for signals at or very close to its series resonance frequency.

As was also explained last month, a single crystal filter circuit incorporates a phasing control, this being a variable capacitor connected into the circuit such that it is capable of neutralising the capacitance of the crystal holder. Adjusting the phasing control effectively alters the parallel resonant frequency of the crystal, thereby allowing increased rejection to be offered to interfering signals close to the series resonant frequency of the crystal.

Crystal filters can employ two or more crystals when it is desired to pass a band of frequencies, as occurs when it is intended to receive amplitude modulated signals.

We turn next to another circuit device which is similarly capable of increasing the selectivity given by a superhet receiver.

INCREASING TUNED CIRCUIT Q

When, in earlier articles, we dealt with t.r.f. receivers (in which all the tuned circuits before the detector are resonant at the frequency of the aerial signal) we saw that the selectivity offered by a single tuned circuit may be considerably enhanced by the application of regeneration. Regeneration, in this context, is frequently referred to as "reaction". The regeneration is normally provided at the detector stage, and the usual practice consists of using the grid leak type of detector and of feeding back to the tuned circuit coupled to its grid a portion of the amplified r.f. signal appearing at its anode. The anode signal fed to the grid is arranged to be in phase with the grid signal, whereupon the feedback is positive. A feature of the circuit is that the amount of signal fed back can be controlled, this being done typically by means of a series variable capacitor. In consequence, it is possible to gradually increase the proportion of signal fed back until, eventually, the circuit breaks into oscillation. If the feedback control is adjusted so that the

circuit is just below the point at which oscillation occurs, the selectivity offered by the grid tuned circuit is considerably increased, because the positive feedback has very nearly cancelled out the inevitable "losses" in that tuned circuit.

Since the apparent efficiency of the grid tuned circuit is increased due to the regeneration, the sensitivity of the circuit is similarly increased.

It would appear attractive, at first sight, to employ a somewhat similar type of regenerative circuit in the i.f. amplifier of a superhet receiver, the regenerative circuit appearing either in one of the i.f. stages or at the detector. Indeed, superhet designs incorporating a regenerative i.f. stage or detector have been produced in the past, but the use of the technique is in no way general. A regenerative stage may occasionally be encountered in inexpensive commercially made receivers intended for short wave listening.

An alternative approach towards taking advantage of the very high Q offered by a tuned circuit to which regeneration is applied is given in the Q -multiplier, which forms the subject of this month's article. The Q -multiplier appears in the form of a separate unit which may be coupled to an existing superhet as an "add-on" device. Its use is almost entirely confined

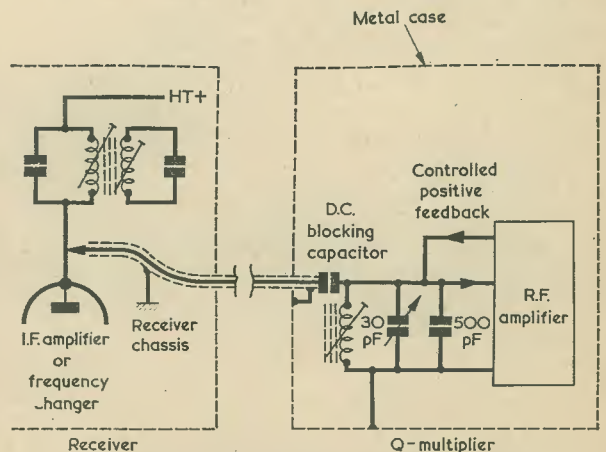


Fig. 1. The basic method of coupling a Q -multiplier to a receiver. The two capacitor values given are roughly representative of what may be encountered in a practical design

to receivers operated by amateur transmitting enthusiasts and short wave listeners, the function of the Q-multiplier being to improve the selectivity of an existing superhet receiver at relatively low cost.

There is no fixed circuit design for a Q-multiplier and a number of individual circuits have appeared in amateur and constructional publications. These all rely, for their operation, on the ability of a tuned circuit to offer a very high Q when regeneration is applied. Some Q-multipliers are designed to offer a sharp response curve for the *acceptance* of signals, whilst others are designed to offer a sharp response curve for the *rejection* of signals. Both these facilities are often available in a single design. It is usual, when discussing Q-multipliers, to initially think in terms of a device which provides a sharp response curve for signal acceptance, and we shall commence next by examining Q-multipliers of this type.

Basically, the Q-multiplier is coupled to an existing receiver in the manner shown in Fig. 1. A length of low-capacitance screened cable, such as aerial coaxial cable, is introduced inside the cabinet of the receiver. The inner conductor of the cable is connected to the anode of an i.f. amplifier, or to the anode of the frequency changer, and the braiding to any convenient chassis point close to the anode terminal. The self-capacitance of the screened cable is effectively in parallel with the primary of the associated i.f. amplifier and the alignment of this primary may then be readjusted so that it is resonant at the same frequency as before. Alternatively, and as will shortly be described, the detuning effect at the i.f. transformer primary can be removed by means of an additional coil in the Q-multiplier unit.

At the other end of the screened cable is the Q-multiplier unit, its components being fitted in a screened metal case which is positioned outside the receiver cabinet. The screened cable connects, via a d.c. blocking capacitor, to a tuned circuit consisting of a coil, a fixed capacitor and a variable capacitor, these components having values which allow the resonant frequency to be adjusted over the band of frequencies passed by the i.f. amplifier of the receiver. This tuned circuit is, in its turn, coupled to an r.f. amplifier which allows controlled regeneration to be fed back to it. If the regeneration level is adjusted such that the r.f. amplifier is just below the oscillation point, the tuned circuit effectively offers a very high level of Q.

In use, the associated receiver is tuned in to a signal in the normal way. Should the extra selectivity available from the Q-multiplier be required, this is next switched on and its variable capacitor adjusted so that the resonant frequency of the Q-multiplier tuned circuit is at the intermediate frequency given by the desired signal. Due to its high effective Q, the Q-multiplier tuned circuit exhibits a response curve having a very sharp peak at its resonant frequency. In consequence, the required signal suffers negligible attenuation due to the Q-multiplier tuned circuit, whereas signals close in frequency to the desired signal can be attenuated to a considerable degree.

It should be noted that the frequency of the Q-multiplier response peak is capable of being varied *within* the band of frequencies passed by the receiver i.f. amplifier. The Q-multiplier variable capacitor can be employed, therefore, to "peak" individual signals passing through the i.f. amplifier without making any adjustment to the tuning control of the receiver.

For best results the tuned circuit in the Q-multiplier unit must be designed so that it offers a high Q on its own before regeneration is applied to it, and this entails employing a highly efficient coil with very low "losses". The regeneration, if carefully applied and controlled, can increase the effective Q of such a tuned circuit until it approaches the performance offered by a crystal.

The fixed capacitor in the Q-multiplier tuned circuit ensures, in practice, that adjustments of the variable capacitor do not necessitate wide variations in regeneration control to keep the circuit just below oscillation point. The fixed capacitor also reduces drift of the resonant frequency due to shifting stray capacitances across the tuned circuit, as could for instance be given by inter-electrode capacitances in a valve r.f. amplifier as it warms up. The values given in Fig. 1 for these two components are, incidentally, merely intended as a rough indication of what is to be expected in a practical circuit.

CANCELLING CABLE CAPACITANCE

It was stated a little earlier that the self-capacitance of the screened cable coupling the Q-multiplier to the receiver i.f. amplifier or frequency changer anode detunes the primary of the i.f. transformer in that anode circuit, and that the detuning may be corrected by realigning the primary. An alternative and better approach consists of adding a coil at the Q-multiplier end of the screened cable, as illustrated in Fig. 2. This coil has an adjustable iron dust core, and its inductance is varied so that it becomes resonant, in company with the stray capacitance of the screened cable, at the centre of the receiver i.f. pass-band (i.e. the band of frequencies passed by the receiver i.f. amplifier). As will be apparent from Fig. 2 the coil and the self-capacitance of the screened cable form a parallel tuned circuit. Since the self-capacitance of the screened cable will be low – of the order of 20pF – the inductance in the coil of Fig. 2 needs to be greater than that of the Q-multiplier proper if it is to become resonant at the intermediate frequency of the receiver. According to Q-multiplier design, the inductance may be some 3 to 10 times greater. The existence of an added parallel tuned circuit across the i.f. transformer primary in the receiver does not significantly affect receiver performance in practice, but it is nevertheless desirable to ensure that the self-capacitance in the screened cable is kept low (by

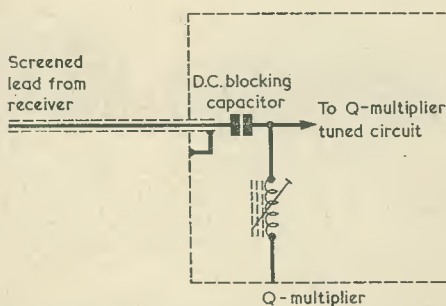


Fig. 2. If an additional coil is fitted in the Q-multiplier, as shown here, it may be made to resonate with the self-capacitance of the screened cable at the receiver intermediate frequency

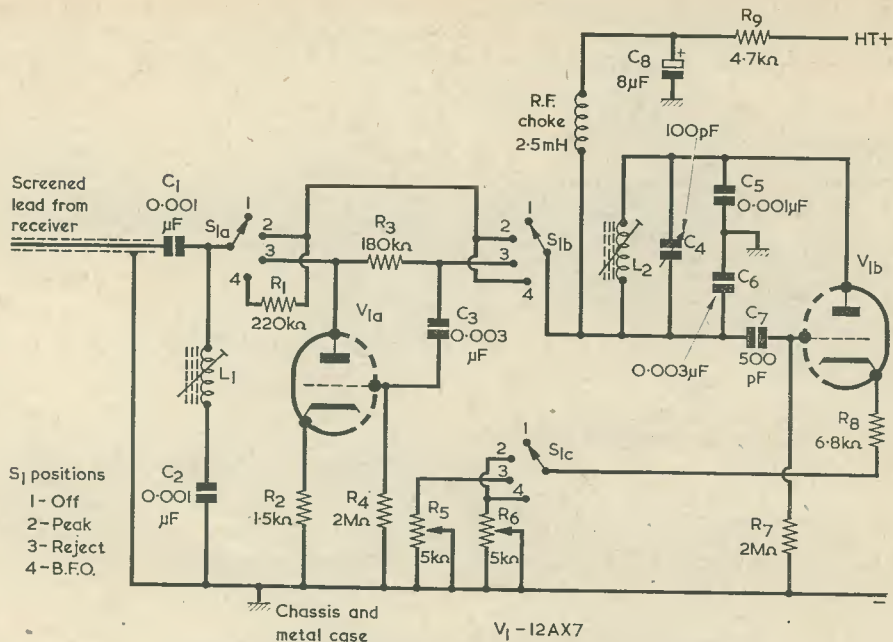


Fig. 3. The Q-multiplier circuit due to G2BVN. This can offer a sharp acceptance response or a sharp rejection response. It may also be switched to provide a b.f.o. signal

keeping the cable short) and to use an efficient coil at the Q-multiplier end. The Q-multiplier coil has the same effect on receiver performance regardless of whether the Q-multiplier is switched on or off. After the Q-multiplier has been coupled to the receiver, the coil of Fig. 2 is adjusted such that receiver i.f. performance is the same as was given previously. This is normally achieved by tuning in a steady signal, or applying a signal to the i.f. amplifier from a signal generator, after which the coil of Fig. 2 is adjusted for maximum signal level at the receiver detector.

It is almost inevitable that the receiver i.f. transformers will be aligned by means of adjustable iron dust cores, whereupon the use of the coil of Fig. 2 is to be preferred. This is because the fairly large core adjustment required by the Fig. 1 arrangement could also seriously upset the mutual inductance between the primary and secondary windings of the receiver i.f. transformer.

Q-MULTIPLIER REJECTION

As has already been mentioned, a Q-multiplier may, instead of providing signal acceptance, alternatively offer a sharp degree of rejection at a specific frequency. To see how this may be achieved we turn next to the practical Q-multiplier circuit shown in Fig. 3. The ingenious design illustrated here is due to R. F. Stevens, G2BVN.*

If, initially, we examine circuit operation with switch S1(a)(b)(c) in the "Peak" position, we may see that the screened cable from the receiver couples to the tuned circuit offered by L2, C4, C5 and C6. This is the Q-multiplier tuned circuit and it functions in the manner already discussed, the r.f. amplifier which provides regeneration being V1(b). Control of regeneration is given by the variable resistor, R6, switched in by S1(c). Coil L1, in Fig. 3, performs the same function as did the coil in Fig. 2.

When S1(a)(b)(c) is set to "Reject", valve V1(a) is introduced into circuit. Disregarding, for the moment, the tuned circuit incorporating L2, we may see that i.f. signals from the receiver are passed, in attenuated form, to the grid of V1(a) via R3 and C3. In consequence, amplified signals of opposite phase appear at V1(a) anode. Without L2, and due to the initial attenuation given by R3, these anode signals will not have a high amplitude and will not seriously affect receiver operation.

When, however, we introduce the L2 tuned circuit a different set of circumstances comes into being. If the correct amount of regeneration is applied to the tuned circuit around L2 this offers a very high Q, together with a similarly high impedance at its resonant frequency. In consequence, signals at this resonant frequency suffer much less attenuation due to R3 than do signals removed from the resonant frequency, and the anti-phase version of the resonant frequency signals at the anode of V1(a) is also correspondingly high. At resonant frequency, therefore, the V1(a) anode signals largely cancel out the original signals which produced them, and the circuit achieves a state of equilibrium where the original signals are allowed to have just sufficient amplitude

*Details of functioning, frequencies and coil inductances for the circuit of Fig. 3 are given in the Third and Fourth Editions of the R.S.G.B. Amateur Radio Handbook, published by the Radio Society of Great Britain, 35 Doughty Street, London, W.C.1. The circuit, with suitable recommendations for components, also appears in the sales literature of Electronics, Edinburgh Way, Harlow, Essex.

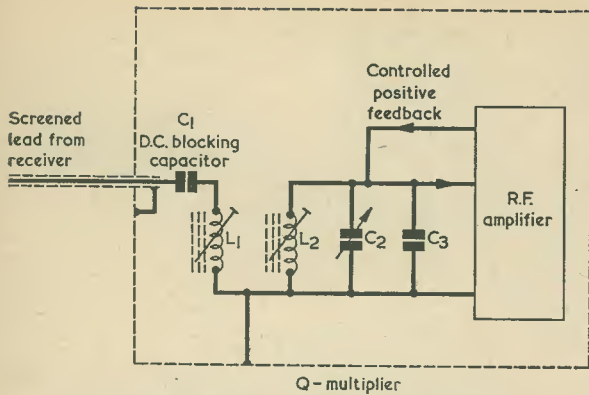


Fig. 4. A Q-multiplier offering sharp rejection. Coils L1 and L2 are coupled together inductively

to maintain the complementary cancelling signals.

The outcome, so far as receiver performance is concerned, is that a high degree of signal rejection occurs at the frequency at which this effect takes place, and it is possible to obtain a "notch" of similar type to that given by a crystal filter phasing control, the frequency at which the "notch" appears being controlled by C4.

Regeneration, when the "Reject" facility is selected, is controlled by R5.

For completeness, Fig. 3 also includes the "B.F.O." position of S1(a)(b)(c). When "B.F.O." is selected, R6 is advanced until V1(b) oscillates. The oscillator output is then fed into the receiver via R1, giving an audible beat note with received carriers according to the setting of C4. The facility provided here is similar to that provided by a conventional b.f.o. fitted normally in a communications receiver.

An alternative approach towards the use of a Q-multiplier for signal rejection is shown in Fig. 4. This version takes advantage of the *absorption effect* which occurs if the coil of a parallel tuned circuit is inductively coupled to the coil of another tuned circuit. If the second coil has a signal current flowing in its windings, and if the first tuned circuit is resonant at the frequency of that signal, the first tuned circuit will absorb energy from the second coil.

In Fig. 4, coil L1 is employed for cancelling out screened cable self-capacitance in the same manner as was the coil of Fig. 2. Coil L2 is in a parallel tuned circuit whose function is to extract energy by

absorption from L1. If the two coils are carefully positioned in relation to each other, and if the tuned circuit around L2 has a very high Q, the absorption effect appears over a very narrow band of frequencies, resulting in a "notch" in the i.f. pass-band of the associated receiver. The frequency at which the "notch" appears is controlled by C2, whereupon this capacitor has an effect which is similar to the phasing capacitor in a crystal filter. The requisite high Q in the tuned circuit around L2 is provided by a regenerative circuit, the regeneration being adjusted until the circuit is just below the oscillation point.

COMPARISON WITH CRYSTAL FILTERS

As will have been gathered, Q-multipliers in their various forms are comparable with crystal filters since, according to version, they can offer either a peak or a "notch" in receiver response. However, a Q-multiplier cannot offer both a peak and a "notch" at the same time, as can a crystal. The Q-multiplier does not, in general, offer quite as good an absolute performance as does the crystal. Also, the adjustment of the controls of a Q-multiplier tends to be critical as the oscillation point of its tuned circuit is approached.

On the other hand, the advantage of the Q-multiplier is that it may be added to a receiver which does not employ a crystal filter and that it introduces no significant losses in receiver sensitivity. A crystal filter, on the other hand, attenuates the signals which pass through it, and is normally fitted as an integral part in the original design of a receiver, the latter having sufficient gain elsewhere to accommodate the loss introduced by the crystal.

We have seen that a Q-multiplier incorporates an r.f. amplifier, and it follows that this will require some form of power supply. Such a supply may be obtained from the receiver itself, or suitable supply components may be fitted into the Q-multiplier unit.

As a final point it may be stated that a Q-multiplier is usually coupled to an early stage in the i.f. amplifier of the receiver. It is, in fact, common practice to couple the Q-multiplier to the frequency changer anode.

NEXT MONTH

In next month's issue we shall examine other selective devices employed in receiver i.f. amplifiers.



THE EDDYSTONE EC 958 RECEIVER

(continued from page 106)

superheterodyne system is employed, with intermediate frequencies of 1,335kHz (nominal), 250kHz and 100kHz. Below 1.6MHz, the conversion is direct to the second or third intermediate frequency, depending on the input frequency range in use.

HIGH SELECTIVITY

The main selectivity and gain of the receiver are provided at the final i.f. (100kHz). Selectivity is provided by a switched L-C filter, with bandwidths of 400Hz and 1.3kHz for c.w. and f.s.k. operation respectively. For d.s.b. operation, bandwidths of 3kHz and 8kHz are available. A further position is provided on the selectivity switch for s.s.b. operation, this introducing a multi-pole crystal filter.

The third signal mixer can be fed from crystal-controlled oscillators at either 150kHz or 350kHz. The final i.f. of 100kHz is then derived from the 250kHz stage input as a difference frequency, but the polarity of the sidebands can be reversed, depending on the oscillator selected. This enables the upper and lower sidebands to be filtered and amplified, using only one sideband filter arrangement.

PROJECTION TUNING SCALE

The tuning scales in the EC 958 receiver use an optical projection system to throw an image, derived from a 10in. circumference film disc, on to a ground glass screen in the front panel of the receiver. In this way, tuning scales with an effective length of 50in.

are provided, to enable the operator to set both the main and incremental tuning with an accuracy appropriate to the setting accuracy of the control circuits.

OUTPUT CIRCUITS

The output of the final i.f. amplifier is fed to either an a.m. detector, or to a c.w./s.s.b. detector incorporating a b.f.o. An output from the master oscillator provides carrier insertion for high stability s.s.b. operation. The a.f. output is fed to a Class-A audio amplifier providing an output of 1 watt which can be fed to an internal monitoring loudspeaker or to an external 3Ω speaker.

A separate a.f. amplifier is provided which gives an output of 10mW to a 600Ω line outlet. An additional drive, at 100kHz, is provided for an optional f.s.k. converter which can be mounted inside the unit.

SPECIFICATION

Some of the more important specification details are as follows.

Reception facilities consist of c.w., m.c.w., a.m. (d.s.b.) and s.s.b. in A3A, A3H and A3J modes, upper or lower sideband. F.S.K. facilities are available when an optional module (Type LP.3058) is fitted.

The power supply can consist of single-phase a.c. mains 100-125 and 200-250 volts (40-60Hz), or low voltage d.c. using an external d.c./a.c. converter.

The aerial input is 75Ω unbalanced throughout the entire range. An additional 600Ω input (balanced or unbalanced) is available below 1.6MHz.

The receiver incorporates 39 transistors (including f.e.t.'s), 43 diodes and seven integrated circuits. It may be bench mounted or fitted to a standard 19in. rack. The panel height is 5.25in. only.

The price of the EC 958 is £750 f.o.b.

COURSES OF INSTRUCTION

GRIMSBY

The Adult Education Institute, Grimsby, is offering a course of instruction in basic radio theory, entitled 'Radio for Amateurs'.

Intended primarily for those interested in Amateur Radio Transmitting, the course will cover the syllabus of the City and Guilds Radio Amateurs' Examination, but anyone interested in radio as a hobby will find much of interest in this course.

The course will be held at the Hereford Centre, Ely Road, Grimsby, on Monday evenings from 7 to 9 p.m. Enrolment will be on 16th, 17th and 18th September between 7 and 9 p.m. and fees are 22/6d. per term, or 10/- per term for persons under 18 and not in full-time employment.

An additional fee is payable for those who wish to take the examination.

LONDON BOROUGH OF HOUNSLOW

At Brentford Centre for Adult Education, Brentford Secondary Girls' School, Clifden Road, Brentford. Enrolments 11th, 12th, 15th and 16th September, 1969, 6.30 to 8.30 p.m. Fees 50/- for one subject, 20/- for each additional subject.

High Fidelity and Tape Recording

The course is designed to give an insight into the technique of high fidelity, tape reproduction and recording and to get the best out of existing apparatus and machines, including notes on construction and maintenance. Programming and special applications, both stereo and mono, will be dealt with, as will be sound on tape or film for cine work. Wednesday. Classes begin on 24th September, 1969.

Radio Amateurs' Course

This course is in preparation for the City & Guilds Examination which qualifies the successful candidate for recognition by the Postmaster-General for the purpose of Radio Transmission. The work includes: simple magnetism and electricity, principles of radio, valves and transistors and circuits, radio receivers, low-power transmitters, aerials, measurement of frequency meters. After the examination the course will include lectures on equipment design. Monday. Class starts week commencing 22nd September, 1969.

KNARESBOROUGH


At the Knaresborough Further Education Centre, Stockwell Road, Knaresborough. Evening Courses (7 to 9 p.m.) leading to the City & Guilds Radio Amateurs' Examination, including Morse Code. Timetable for the 1969-1970 Session as follows:-

RAE (1st year) Monday, Sept. 22nd, 1969 - Dec. 15th, 1969; January 5th, 1970 - March 16th, 1970.

RAE (2nd year) Thursday, Sept. 25th, 1969 - Dec. 18th, 1969; Jan. 8th, 1970 - March 19th, 1970.

Fees will be 30/- from September to March: a further fee of not more than 15/- will be charged for the Summer Term, 1970.

In your work-shop

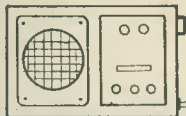

On the last day of work preceding what is euphemistically referred to as the Late Summer Bank Holiday, Dick and Smithy find that they have an unexpected period of spare time on their hands. But they are able, as always, to take full advantage of this situation, and they devote the time to discussing the latest hints received from readers.

up to take my Bank Holiday Monday at the beginning of August. But they've now gone and shifted it to the end of August".

"When you've got a moan", pronounced Smithy censoriously, "you certainly believe in sticking to it. Dash it all, Dick, you've been bitching away about the change in Bank Holiday date ever since it was introduced five years ago".

"And rightly so, too", snorted Dick. "Changing the date of a Bank Holiday is nothing less than flying in the face of Nature. Mark my words, Smithy, an alteration in the set order of things, such as this is, bodes ill for the future of mankind".

Smithy swallowed.

"You can always", he suggested sweetly, "come into work *during* the Bank Holiday if you like".

"There's no necessity for me to do that", answered Dick hastily. "In any case seeing that I was robbed, by *force majeure*, of my rightful holiday at the beginning of this month, I have no alternative but to

grudgingly accept next Monday as a day off in lieu".

READERS' HINTS

Smithy glanced over at his assistant as he sprawled gracelessly on the edge of the stool alongside his bench. It was the last Friday of August and there was half an hour left before the Workshop was locked up for the forthcoming week-end plus the subsequent Late Summer Bank Holiday Monday. All servicing work had been cleared up, and the pair had busied themselves during the previous hour in tidying and clearing up their benches. A process, it may be added, which had caused the suspension in the air of such a great volume of dust that the Workshop door had had to be vigorously swung open and shut from outside with all the windows open before the coughing Dick and Smithy could re-enter and take up their rightful positions beside their benches again.

After this display of energy they had decided to relax before official packing-up time, and had entered into a desultory conversation which had terminated in Dick's bitter tirade against those who alter our long-established customs.

A thought occurred to Smithy.

"Tell you what", he remarked brightly. "How about having a session on readers' hints?"

Dick straightened up.

"Now that", he remarked keenly, "really is a good idea. How many hints have you received since we last had a go at them?"

"Quite a few", replied Smithy, as he reached into a drawer under his bench and took out a bundle of letters. "And, as always, there are some very good ideas amongst them, too".

Eagerly, Dick carried his stool over to Smithy's bench and perched himself on it. He had completely forgotten his previous complaints about the forthcoming misplaced Bank Holiday.

Smithy selected a letter and read it carefully.

"Now here", he remarked, "is a good hint to start the ball rolling. As I'll explain to you in a minute, this idea is a wee bit in the experimental class. However, the experimental work is easy enough to carry out once you understand the basic operation".

Smithy indicated a circuit diagram drawn out in the letter. (Fig. 1(a)).

THE RADIO CONSTRUCTOR

"MESSING AROUND WITH THE calendar", complained Dick, "that's what it is".

Smithy heaved a sigh.

"What", he asked wearily, "are you dripping on about now?"

"This stupid Bank Holiday Monday business", retorted Dick aggrievedly. "I was always brought

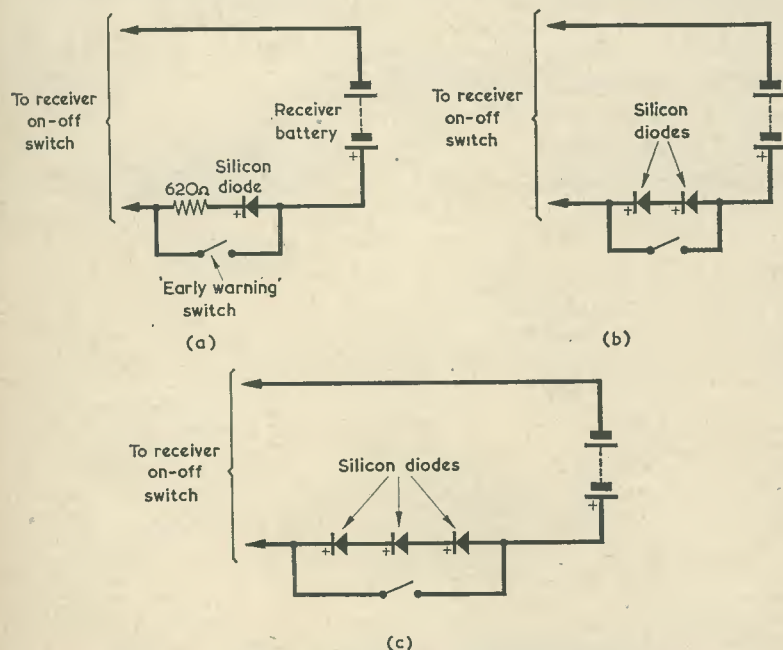


Fig. 1(a). A simple circuit which gives 'early warning' when a receiver battery is approaching exhaustion
 (b). As suggested by Smithy, silicon diodes without a resistor may alternatively be employed. The two shown here drop about 1 volt when the switch is opened
 (c). With three diodes, the voltage drop is approximately 1.5 volts

"The idea behind this circuit", he continued, "is to provide a simple 'early warning' of battery failure in a transistor radio. As you know, it's very annoying to have a transistor radio battery run out on you when you don't have a replacement immediately available. Normally, the switch in this 'early warning' circuit is closed, whereupon the radio operates in the usual manner. When the switch is opened, however, the silicon diode and 620Ω resistor are connected in series with the battery, whereupon a voltage is dropped across the conducting diode and the resistor. If the battery is near exhaustion and its voltage is correspondingly low, the receiver oscillator will cease to function when the switch is opened. This warns you that it's about time you got a new battery for the radio, because the present one won't last much longer".

"That's neat", commented Dick. "I suppose that, if the radio continues to operate with the switch opened, you then know that the battery has got a reasonable amount of life left in it".

"Exactly", agreed Smithy. "One of the advantages of this idea is that you can insert the switch and the voltage dropping components in series with the positive battery lead without having to alter any of the receiver circuits themselves. The switch and the components can be added quite easily to most transistor radios as a permanent feature".

"I wonder", said Dick thoughtfully, "why the resistor has to be 620Ω".

"Now that", replied Smithy, "is where the experimental bit comes in. The components in this circuit happen to be those which suited the particular transistor radio used by the reader who sent us the hint. What you have to do is to select voltage dropping components which will be applicable to your own radio. Speaking personally, I would prefer to use diodes only, rather than a diode and a resistor. Two conducting silicon diodes (Fig. 1(b)) will give a drop of about 1 volt when they're switched into circuit and three (Fig. 1(c)) will give a drop of about 1.5 volts. One or other of these two alternatives should be adequate to provide 'early warning' of battery failure with the majority of transistor radios. Incidentally, it's a good plan to find the dial setting at which the receiver oscillator first fails to operate as the supply voltage drops. If, for instance, this occurs at the low frequency end of the medium wave band, you can test the battery by opening the switch and tuning at that end of the band".

"I notice", said Dick, "that the test circuit is inserted in series with the positive connection to the battery. Couldn't it be connected in

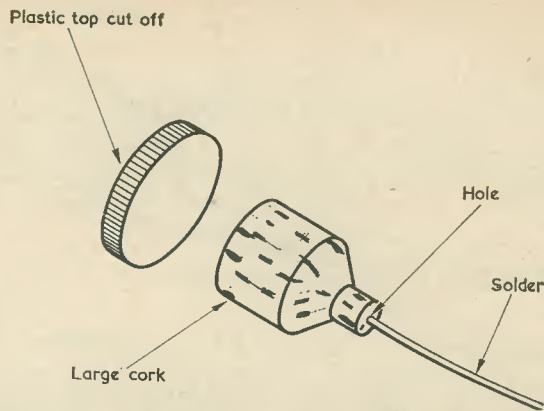


Fig. 2. A simple solder holder which enables odd bits of solder to be finally used up

series with the negative battery lead instead?"

"Oh definitely", stated Smithy. "Provided, of course, that you connect the silicon diodes the other way round".

"What sort of silicon diodes should be used?"

"Well", replied Smithy, "the diodes could pass a fairly heavy surge current if they are in circuit when the transistor radio is switched on, and this current might well be in excess of the maximum forward current rating of some of the smaller silicon diodes which are intended for signal circuits. The more knowledgeable experimenter who, say, buys his silicon diodes in bulk will know how to deal with this problem. So far as the less experienced home-constructor is concerned, however, I would suggest that he plays safe on this score by using small silicon power rectifier diodes. A good choice would be the popular Lucas DD000. This is quite a small diode and its forward current characteristics are more than adequate enough for the present application".

NO CHARGE FOR CORKAGE

Smithy turned to another letter in the pile.

"Ah", he chuckled. "Now here's a very smart little scheme for saving solder".

Smithy showed Dick a sketch attached to the letter. (Fig. 2).

"What you do", he continued, "is to take a large cork and cut it to the shape shown here. If it's got a plastic top which has a wider diameter than the body of the cork, you cut this top off. The next thing to do is to make a small hole in the tapered end of the cork, this hole being just large enough to take a piece of resin-cored solder. You now have a solder holder which, first of all, enables you to manipulate long lengths of solder more easily and which, secondly, protects your hand

from heat when you're using very short lengths of solder".

"That idea", said Dick, impressed, "would be just right for me. I'm always ending up with little bits of solder about an inch and a half long. I've got a tin full of them somewhere on the bench!"

"Then you can start using them up with this solder-saving gadget", pronounced Smithy. "The next time you order a bottle of Beaujolais with your egg and chips down at Joe's Caff, ask him to keep the cork for you".

"Fair enough", replied Dick equally. "But it won't be Beaujolais because Joe doesn't stock it. It'll probably be a hock like Liebfraumilch or something like that. The trouble with Joe is that he's rather fussy about the wines he serves with his chips".

Smithy cast a suspicious glance at Dick's patently innocent face.

"Oh well", he remarked uncertainly, "you'd better use whatever sort of cork you can lay your hands on".

The Serviceman hurriedly turned to the pile of letters on his bench and made a third selection.

"Now, this letter", he announced, after a moment's perusal, "describes a probe for an oscilloscope or millivoltmeter".

Smithy showed Dick the drawing of the probe. (Fig. 3).

"As you can see", went on Smithy, "this is built in the case of a fibre pen, the type employed by our correspondent being a Scripto 'Fibapen'. The outside insulation on the coaxial cable connecting to the probe is stripped back 1 inch from the end and the braiding removed over most of this length. A stranded earth lead is soldered to the braid which remains, and is passed through a hole in the case, as shown. A Veroboard terminal pin or any other plated pin suitable for a probe is, after being soldered to the inner wire of the coaxial cable, passed into the plastic case. The three entry

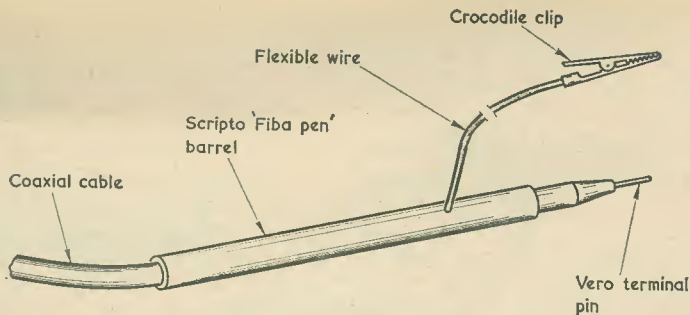


Fig. 3. Making up a screened oscilloscope or millivoltmeter probe in the case of a discarded fibre pen

points are then sealed with Araldite. When completed, the probe is capable of reaching into really awkward and inaccessible places. Also, it retains a high degree of screening due to the presence of the braiding inside the plastic case".

"That's a knobby scheme", remarked Dick approvingly. "It's amazing how many useful gadgets you can knock up for radio purposes out of quite simple basic materials".

"True enough", agreed Smithy. "Now let's take a look at the next hint. Ah now, this is another simple device but it can still be jolly useful during servicing work. The idea was conceived after encountering the difficulty of removing small silicon transistors of the BF173 variety from printed circuit boards in hybrid TV sets. The removal of these transistors can be particularly difficult when they're closely surrounded by other components, and the solution consists of making an extractor tool from a polystyrene or bakelite coil former of the type which accepts a 6 m.m. dust core. A piece of plastic sleeving is first slipped inside the former to give a good friction grip. The former is then passed over the transistor body, whereupon the grip is tight enough to allow the transistor to be drawn free of the printed panel once the solder is removed from the connections".

Dick looked at the sketch in the letter Smithy was holding. (Fig. 4).

"That's a useful idea", he commented. "Some of those little transistors can make life very frustrating when you want to unsolder them from a crowded circuit board".

"They can indeed", concurred Smithy. "An added bonus with this extractor tool is that you can use it to hold the transistor in position if you want to make ohmmeter checks to its lead-outs. Hold the base of the coil former in a vice, and the transistor is firmly positioned with its leads pointing conveniently upwards".

"Good point", approved Dick. "Transistors can be fiddling little components when you want to connect test leads to them".

"They can be irritating in that respect", agreed Smithy. "Well, let's see what the next letter has to tell us. Ah, this has to do with magnetising and demagnetising. As you know, Dick, we sometimes like to have screwdrivers and similar tools magnetised because they can then be used to pick up screws and things from awkward places. The trouble is that, once magnetised, the tools are difficult to demagnetise again afterwards, whereupon the magnetisation can occasionally become a nuisance. The present hint describes a simple and useful method of demagnetising such tools, this being done with the aid of an ordinary mains driven solder gun. You hold the tip of the iron near the object to be demagnetised

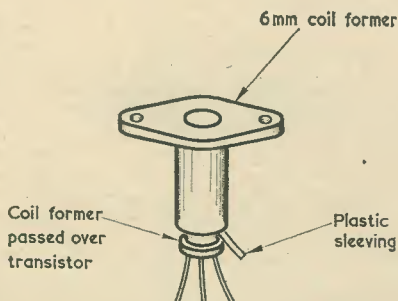


Fig. 4. Employing a coil former as an extractor for transistors fitted to crowded circuit boards

and pull the trigger. The field around the solder gun tip is usually strong enough to do the job very effectively".

TERMINAL STRIPS

"That's a new one on me", commented Dick. "I'd never looked upon a solder gun as being a degaussing tool before!"

But Smithy had already opened the next letter, and he passed over the sketches enclosed with this to his assistant.

"Have a shufti at these", he said, "whilst I tell you what's in the letter. This, incidentally, describes two separate hints. The first of these involves the use of what are known in the trade as 'barrier terminal strips'".

"I think I know what they are", said Dick. "Aren't they those polythene strips with individual metal connectors in them, each connector having two screw terminals?"

"That's right", agreed Smithy. "They're normally 12-way and are rated at mains voltages, and you can sub-divide them very easily with the aid of a knife. They're sold in Woolworth's as well as in shops dealing with electrical parts. Well now, if you like experimenting with different circuits, two of these terminal strips mounted parallel to each other can offer very convenient anchor points and are readily capable of taking temporary connections. (Fig. 5). You fit the components between the strips and simply secure their lead-outs under the terminal strip screws. The terminals should not be used for any r.f. wiring which needs to be particularly short, but they are extremely convenient for bias networks, decoupling components, and for circuits working at audio frequency. The most convenient terminal strips for this application are those rated at 2 amps".

"Next time I'm in Woolly's", said Dick, "I think I'll make a small purchase of two of those strips".

"Fair enough", said Smithy approvingly. "The second hint in this letter applies to constructors who prefer, perhaps due to lack of facilities, to avoid too much metal-bashing. You take two pieces of wood measuring 1 inch square and 6 inches long, and fix to them two further pieces measuring 1½ inch by ½ inch by about 10 inches long. (Fig. 6). You then add a front panel. Whereupon you have an almost complete chassis. The front panel can be of aluminium or plywood, as required. You can screw an aluminium sheet over the 1½ inch pieces if you like or, even, mount components directly to the wood. If the two 1½ inch pieces of wood are spaced by the requisite distance you can mount valveholders to them by having one piece of wood and the other on the

second piece of wood. The larger iron-cored transformers and chokes can be straddled across the two lengths of wood in a similar manner."

"That's certainly a novel idea", remarked Dick. "Do the 1½ inch pieces of wood have to be 10 inches long?"

"Oh no", said Smithy, consulting the letter in his hand. "The 10 inch dimension just happens to be a convenient one for most home-constructor projects. However, it can easily be increased or shortened to take any set of components you may require for a specific job."

Smithy put down the letter and turned to the next one in the pile on his bench.

"Now this", he said, studying the letter carefully, "is a really unusual one. Our correspondent likes to experiment with receivers and preselectors and he's evolved a knobby idea for mounting ferrite rod aeriels to these, this consisting of a rotatable ferrite rod assembly which can be plugged in to the unit with which it is to be used. The base of the assembly is provided by an electric light ceiling rose, the centre hole in this being opened out to accept a 'skeleton' jack socket of the type which is mounted by a single bush nut. A jack plug with a fairly long body plugs into this, the ferrite rod being mounted at its top. This is what it all looks like".

Smithy showed Dick a diagram in the letter he had been reading. (Fig. 7(a)).

"The type of jack plug used by our correspondent", continued the Serviceman, "was of the surplus variety and its body was made of an insulating material which melts with heat. In consequence, it was possible, with the aid of a soldering iron, to make a nice groove along the top of the body to take the centre of the ferrite rod. Individual constructors not having this type of jack plug can, of course, use other methods of mounting the rod. In our correspondent's case Paxolin discs were initially stuck to the body of the jack plug, a rectangular piece of Paxolin being secured over the ferrite rod at the top with the aid of two long bolts. (Fig. 7(b)). These bolts also provided the connections between the ferrite rod aerial winding and the plug contacts. Two wires from the latter were passed through holes in the side of the body".

"That is an unusual idea", agreed Dick. "You could do quite a bit of experimenting with different ferrite aeriels, just by plugging them in. And, of course, they're free to rotate".

"What catches my imagination here", stated Smithy, "is that this jack plug and socket idea has potential applications for quite a lot of gubbinses other than ferrite aeriels. Let's say that you want to knock up

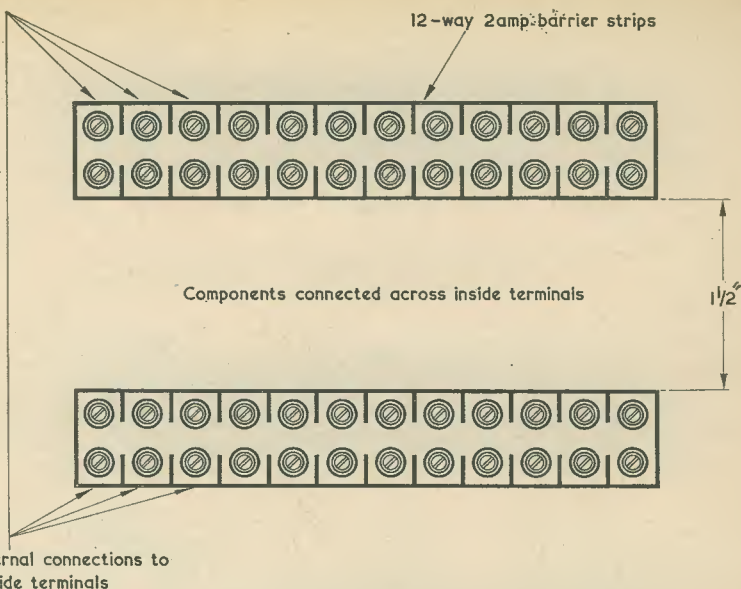


Fig. 5. Temporary and experimental circuits can be readily made up with the aid of standard electrician's barrier terminal strips

a gadget in which one part can be made to rotate around a centre whilst continual electrical connection is made to it. This jack plug and socket scheme provides an excellent solution to such a problem. First of all, it gives you a ready-made spindle and bush and, secondly, it gives you continual electrical contact to the rotating part via the contacts of the plug and socket".

"Just like a pair of slip-rings", said Dick. "I seem to remember that you can get jack plugs with three contacts. If you used one of these you'd have what is effectively three slip-rings".

"Three-pole jack plugs are available", confirmed Smithy, "And they're made by Bulgin. With a three-pole jack plug, both the tip and a short length of sleeve are in-

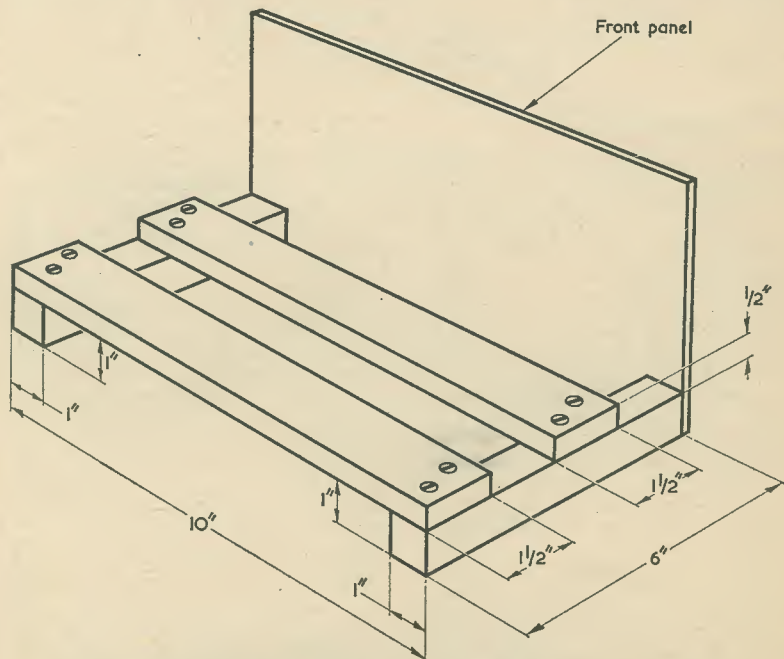


Fig. 6. A simple means of making up a chassis for the constructor whose metal-working facilities are limited

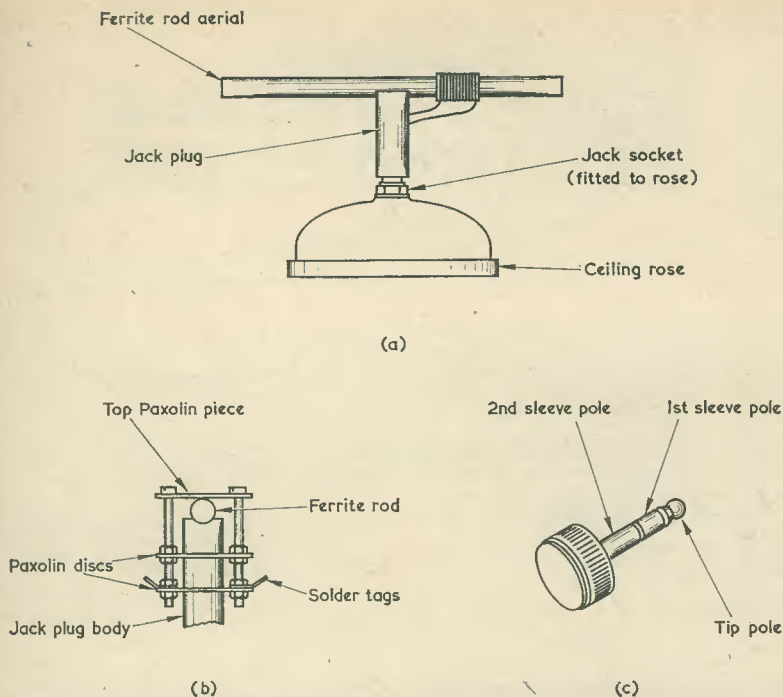


Fig. 7 (a). The basics of an unusual ferrite aerial mounting system (b). A suitable method of securing the ferrite rod to the jack plug. The two solder tags act as anchors for the coil lead-outs (c). The Bulgin 3-pole jack plug type P505. This, together with suitable sockets, is available from Home Radio (Components) Ltd.

ulated from the main part of the sleeve". (Fig. 7(c)).

"That would be just the job then", said Dick triumphantly. "It would give you *three* electrical connections continually made to the rotating part".

FLEXIBLE TORCH

"True enough", agreed Smithy absently, as he read a further letter. "Now, here's something which falls into quite a different category. It's a hint for making up what our correspondent describes as a 'flexible torch'. Actually it's a narrow diameter bulb holder which can be wired to coaxial cable, and it is very useful for illuminating inaccessible places. The other end of the cable connects to a suitable battery or heater transformer secondary."

Dick examined with interest the sketches accompanying the letter. (Fig. 8).

"These bits and pieces", he remarked, "look like parts of coaxial plugs".

"They are", confirmed Smithy. "Actually they're parts of standard Belling-Lee coaxial cable plugs and coaxial cable sockets. Do you know what I mean by 'coaxial cable sockets'?"

"I suppose", replied Dick, "that those will be the sockets which have

the same general appearance as coaxial plugs, and which can be wired up to coaxial cable in much the same way as the plugs are wired".

"That's right", agreed Smithy. "They're used for extending the length of a coaxial cable and for similar jobs. A more correct name for them, by the way, is 'free coaxial socket'. For the present application, the plug or socket which actually houses the bulb should be of the type having an insulated cap as opposed to the type with a metal cap. Also, the end of the plastic cap is cut off".

Smithy returned to the letter.

"Right!" he announced briskly.

"Now there are two ways of making up these bulbholders. The first is intended for ordinary flash-lamp bulbs. First, you take a coaxial plug and discard the inner parts. You next insert the bulb and, if necessary, wrap a sufficient length of tin or aluminium foil around its thread to ensure that it makes good contact to the outer part of the plug and fits in tightly. Then take a coaxial cable socket, and add to it a small spiral spring that just fits over the centre socket, allowing the spring to protrude by about $\frac{3}{8}$ inch. A suitable spring can be obtained from a discarded retractable ball point pen. You wire up a length of coaxial cable to the socket in normal

manner, push the socket into the modified plug and - hey presto! - you have a bulb-holder".

"Blow me", remarked Dick. "Well, *that* doesn't represent a great deal of work".

"It doesn't", said Smithy. "Now, there's a second approach. This doesn't require the spring and it's intended for lens-end bulbs. You fit the bulb into a cable socket, using tin or aluminium foil as before. In this instance, the bulb centre tip connects to the centre metal section of the socket. It may be necessary to cut away some of the insulation on this centre section to allow the bulb tip to make good contact. You next wire the coaxial cable to a coaxial plug, which is inserted into the other end of the socket. The result? Another bulb-holder!"

"These little 'bulb-holders'", commented Dick, "should be jolly useful for servicing work."

"That's their main purpose, of course", replied Smithy. "The coax running to the bulb-holder assembly can be any convenient length. You could, for instance, wire up one of these bulb-holders permanently on a work bench with, say, about two yards of coax coupling to a heater transformer. Another idea would be to fix the bulb-holder to the handle of a soldering iron. It could be held in place by a couple of springs, these being cut, say, from a length of curtain spring".

"I must", stated Dick, "have a dig in our box of coax plugs and sockets when I come back from holiday".

A frown creased his brow.

"Which reminds me", he continued, "that I still think it's a poor show that the Bank Holiday has been shifted to the end of August".

"Dear, oh dear", said Smithy. "Are you still moaning about *that*?"

"Too true I'm moaning", returned Dick hotly. "We're pushed around far too much these days by our administrators. If there's much more of it I'm darned well going to go Nationalist".

"You can't go Nationalist".

"Why not?"

"Because you're English", stated Smithy. "It's you the Nationalists *are against*".

Dick absorbed this information.

"Is it?"

"Of course".

"Hell's teeth", complained Dick. "There's just no avenue at all for keen young militants such as myself".

"And a good thing, too", snorted Smithy. "Anyway, there's five minutes left, so we'll make the next hint the last one for this particular session".

Dick forgot the injustices of the world for the moment.

"All these hints we get are very good, aren't they?"

"They always are", replied Smithy, "and they're all very much appreciated, too. Anyway, here's the last one for today, and it deals with a method of working out Veroboard component layouts. You take a piece of Veroboard, the largest you are likely to use, together with a piece of matt white Formica of the same size. With the white side of the Formica upwards, you place the Veroboard on top and, using a sharp scriber, pierce the Formica through every Veroboard hole in turn. (Fig. 9). You next take away the Veroboard, whereupon the Formica is ready for use. To work out a component layout you simply draw the components on the surface of the Formica with pencil, employing a red pencil at the places where the Veroboard copper strips have to be cut. The final job consists of preparing the Veroboard and wiring it up, copying the layout you've drawn on the Formica surface. You can use the piece of Formica over and over again, because the pencilled layout diagram can be easily cleaned off with a damp cloth, leaving just the scriber marks".

OFF AND AWAY

"Well, I'm dashed", said Dick enthusiastically. "What a crafty scheme!"

"Isn't it?" agreed Smithy, collecting the letters together and returning them to the drawer in his bench. "It's a very nice one to finish this hint sesh off with, too".

A thoughtful expression appeared on Dick's face.

"Do you know, Smithy", he remarked. "Despite what I said earlier on I've got half a mind to look upon next Monday as an ordinary working day after all and to come on in here".

"Blimey", said Smithy, impressed. "You really *must* be serious over this Bank Holiday business".

"I'm extremely serious about it", replied Dick fervently. "Don't forget that I'm an idealist, and that I believe in putting my ideals into practice".

"Well", said Smithy helpfully, "I can let you have the Workshop keys if you like".

"That would be fine", responded Dick enthusiastically. "By coming in I'll be making just the sort of passive demonstration that's needed to strike a blow for civil liberty".

Smithy decided to concentrate on the harder and more mundane facts of life.

"I presume", he commented, "that, since there are no sets to fix, you'll be carrying out work of a private nature".

"Actually", stated Dick guardedly, "I'd thought of trying some of the hints we've discussed today".

"Excellent", commented Smithy. "And I must compliment you on

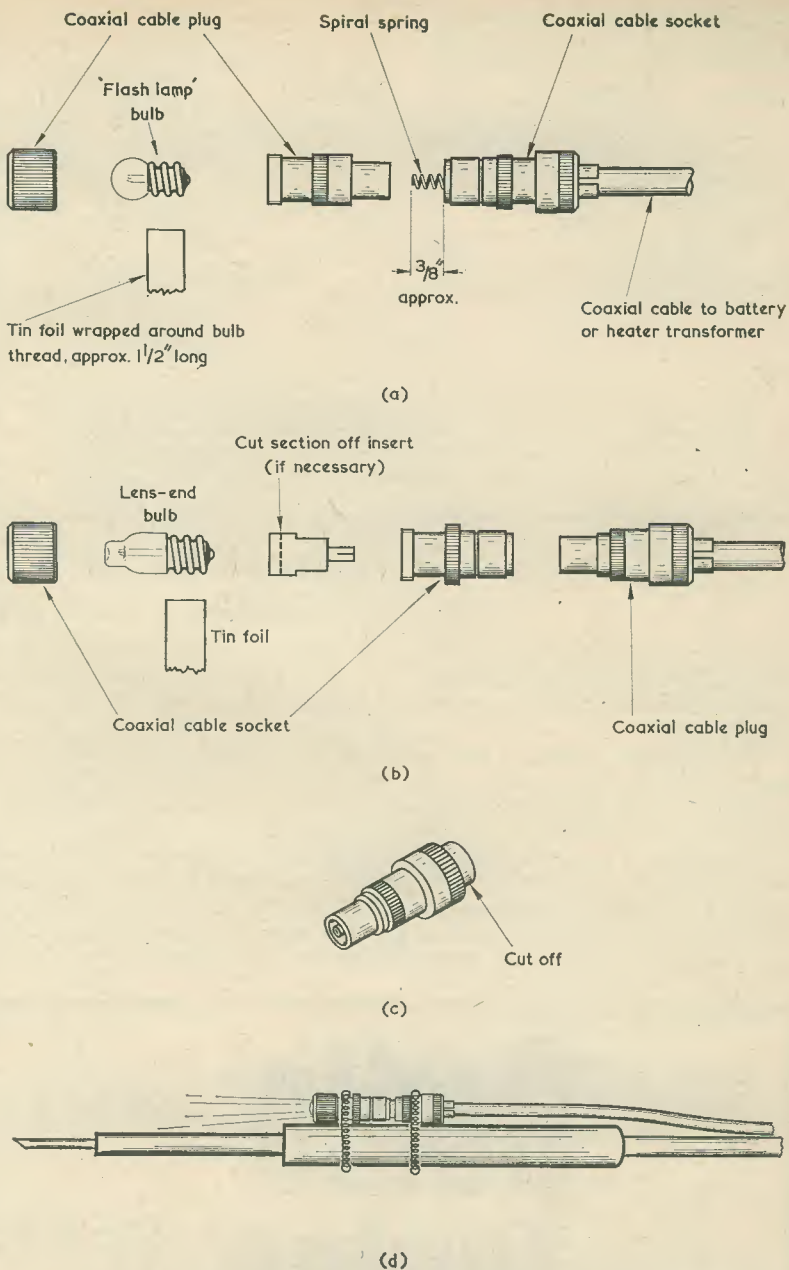


Fig. 8(a). Details of a simple bulb-holder having a narrow diameter
 (b). An alternative assembly incorporating a lens-end bulb
 (c). The end of the plastic cap at the bulb end should be cut off, as shown here
 (d). Mounting the bulb-holder assembly on a soldering iron

your enthusiasm. Seeing, though, that you won't be doing any official work on Monday you can't, of course, expect to be paid for coming in".

There was silence for a moment. "Can't I?" "Oh no".

The silence returned.

"I think", said Dick slowly, "that this will have to be another occasion when I have to bow my head to Authority".

"What do you mean?"

"Although it goes against the grain", explained Dick, "I'm going

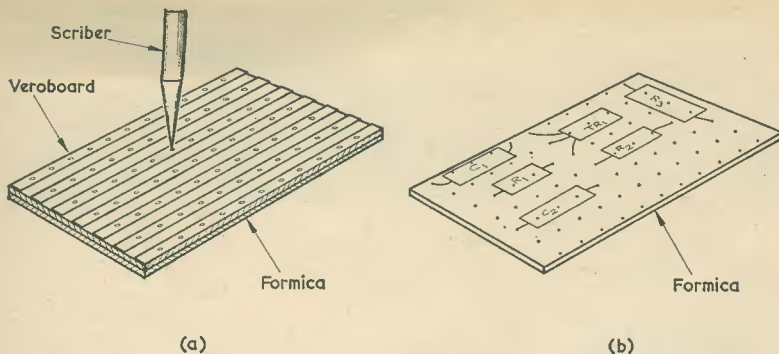


Fig. 9. Successive steps in planning a Veroboard component layout. In (a) the scribe is passed through the Veroboard holes in turn. In (b) the components are drawn on the Formica surface in pencil

to have this dratted Bank Holiday off. But I'll take jolly good care to see that I don't enjoy it!"

Which final statement on the part of Dick only serves to demonstrate, once more, the truth of the old and well proven dictum that the most successful idealist of them all is the one who keeps his eye fixed firmly on the loot.

EDITOR'S NOTE

The hints described in this episode of 'In Your Workshop' were submitted, in the order in which they appear, by D. Salmon, D. Fitzgerald, M. F. Docker, W. D. Graham, G. M. Watson, P. B. Moss, B. Richardson, A. J. Thorndyke and A. L. Dawson. Further hints for this feature are welcomed, and payment is made for all that are published.

DOMINICA ON THE AIR Marconi Transmitter in the West Indies

The people of Dominica are to increase the power of their radio service, with the construction of a new station to be equipped by the Marconi Company. This station, due to be on the air by October, is part of a general development plan drawn up by the Government of Dominica for the Island, and will be built near Roseau, the Island's capital.

The contract includes a Marconi 10 kW m.f. broadcasting transmitter together with studio facilities. The type B6029 transmitter is designed for use anywhere in the world and embodies the latest developments in solid-state technology. Being completely self-contained, it is easily installed and, since no rear access is needed, requires only minimal floor space.

Dominica, in associate statehood with Britain, is centrally placed in the islands of the Eastern Caribbean. The new radio station will cover not only Dominica, but also many of the surrounding islands. The station will broadcast a varied programme including local news, educational items and general entertainment, and a British news service. Also, because the islands are on the edge of a hurricane zone, the station will, when necessary, broadcast advance warning of bad weather conditions to the islanders.

Radio Topics

By Recorder

AFTER HAVING JUST READ Desmond Morris' *The Naked Ape* (now available in paper-back from Corgi Books—albeit with a front illustration that necessitates the cover being folded firmly back whilst reading in the train) I have been pondering a little on the processes of evolution. As you may recall, in his book Dr. Morris ex-

amines Man from the point of view of the zoologist, with results that are enlightening, entertaining and, in places, hilariously funny.

But it is the question of evolution, as treated in *The Naked Ape*, which is the most intriguing. A species dies out if it eventually becomes incompatible with its environment. At the same time, the

changes needed in a species to enable it to adapt and to advance are not consciously ordered. Instead, quite accidental deviations from the norm occur continually and, should any class of deviator be more successful in survival than the mean of the species, that class eventually dominates in status and in numbers. It is rather chastening to think that

Your Local Supplier

KENT

EMSAC BASIC ANTENNA SYSTEMS

GD1 All band dipole 1.8-30MHz. Length 102 ft. of 18 swg. 75 ohm feeder and 300 ohm matching stub total length 100 ft. Glass-fibre mouldings. 68/-.

GV1 General purpose vertical 1.8-30 MHz. Adjustable 7 ft. - 23 ft. 92/-.

TU2 Receiver antenna tuning unit. Amateur and SW broadcast bands 1.5-30MHz. 90/-.

TU4 Transmitter transmatch 5 band. 237/-.

Send SAE for details. Open weekends. Carriage extra.

G3IAR
**ELECTRONIC & MECHANICAL
 SUB-ASSEMBLY CO. LTD.**
 Highfield House, West Kingsdown, Kent.
 Tel: West Kingsdown 2344.

SURREY

Portable Transistor Amplifier plus Dynamic Microphone

A self-contained fully portable mini p.a. system. Many uses — ideal for Parties, or as a Baby Alarm, Intercom, Telephone or Record Player, Amplifier, etc. Attractive rexine covered cabinet, size 12 x 9 x 4 in., with powerful 7 x 4 in. speaker and four transistor one watt power amplifier plus dynamic microphone. Uses PP9 battery. Brand new in Makers' carton with full makers' guarantee. World famous make 90/- Post Free List 1/- Only 90/- Post Free

RADIO COMPONENT SPECIALISTS
 337 Whitehorse Road, West Croydon, Surrey. Phone 01-684-1665

SUSSEX

E. JEFFRIES

For your new television set, tape recorder, transistor radio, and hi-fi equipment.

PHILIPS, ULTRA, INVICTA, DANSETTE, MASTERADIO, PERDIO, MARCONI, PHILCO, FIDELITY.

6A Albert Parade, Victoria Drive, EASTBOURNE SUSSEX

EIRE

PEATS for PARTS

ELECTRONIC COMPONENTS RADIO & TELEVISION

For the convenience of IRISH enthusiasts we supply:

The Radio Constructor, Data Books and Panel-Signs Transfers

Also a postal service

Wm. B. PEAT & Co. Ltd.
 28 PARNELL STREET
 DUBLIN 1

as an experimental project only. As can be seen, the circuit of Fig. 2 fits in between the volume control slider of Fig. 1 and the control grid of the UL84. The 470kΩ resistor in Fig. 2 following the 2N4289 is merely a grid resistor for the UL84. The zener diode is shown as a 39 volt component but it can, in practice, be anywhere between some 36 and 40 volts. It should be capable of dissipating 80mW, which shouldn't be too difficult to arrange since most of the higher voltage zener diodes seem, in any case, to be in the 0.5 to 1.5 watt ranges.

Note that one side of the speaker transformer secondary connects to the positive side of the sub-amplifier supply and that negative feedback is provided via the 50kΩ preset potentiometer. When the amplifier is completed it will be best to initially leave this potentiometer out of circuit. Be careful to keep the volume control low when checking the amplifier in this condition because, if the record player has a small loudspeaker, excessive output might damage it. Then introduce the potentiometer set to insert full resistance, and gradually reduce this resistance until the desired overall gain is obtained. If, at any time, the amplifier goes into oscillation the feedback is positive. As soon as oscillation is heard, switch off quickly and reverse the feedback connections at the transformer secondary.

Mr. Owen's circuit does not take account of a tone control. The horrible top-cut affair using a 25kΩ variable resistor and 0.05μF capacitor across the speaker transformer primary which is shown in Fig. 1

could be retained. But this would be very naughty, as the tone control is inside the feedback loop. It would be better to either dispense with a tone control, or experiment with a circuit along the lines followed by Smithy.

The 2N4289 is available from Amatronix, Ltd. Alternatively, both transistors are available from Electrovalue, 32a St. Judes Road, Englefield Green, Egham, Surrey.

Mr. Owen states that he hasn't tried his circuit in a record player amplifier such as that in Fig. 1, because one wasn't available. But he says that the circuit gives good results under roughly similar conditions when fed with a ceramic cartridge.

SINGLE TRANSISTOR OUTPUT

Our popular contributor, Sir Douglas Hall, has sent us some thought-provoking notes on the subject of output stages using single transistors. These notes are not sufficiently long to constitute an article in their own right, and I gladly relinquish space here to allow their publication.

Single transistors (writes Sir Douglas Hall) are quite often used as Class A output devices in mains driven receivers or amplifiers, or in apparatus powered by car batteries. If a transformer is used the maximum undistorted output is confined by the dissipation capability, within reason, of the transistor employed. It is necessary for the transformer to have a suitable ratio, a large enough core, and a sufficiently low primary resistance. In these circumstances the greater the current

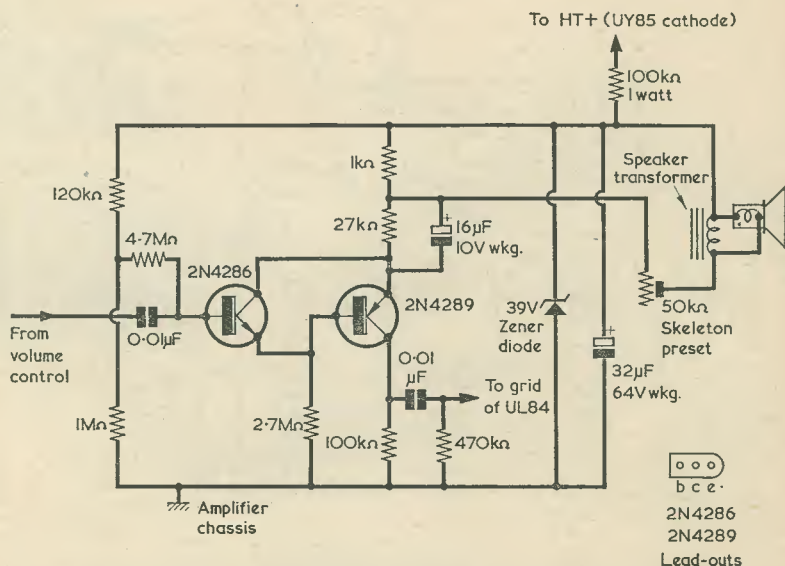


Fig. 2. A suggested amplifier circuit for improving the record player performance.

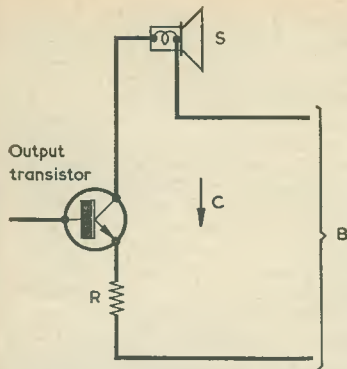


Fig. 3. Illustrating the conditions in a single transistor transformerless output stage

passed through the components the greater will be the output, and an efficiency not far short of 50% may be expected.

In recent years single transistor output stages have often used comparatively high impedance speakers so as to dispense with the output transformer. The impedance rating for these speakers is usually 15, 25 or 35Ω or, in the case of miniature battery receivers, 80Ω. The d.c. resistance of such speakers has about the same value as the nominal impedance. When a circuit of this sort is employed it is no longer possible to increase output indefinitely by increasing the current passed. There is an optimum current which, if exceeded, will result in a drop in output because of excessive drop of direct voltage across the speaker.

In order for maximum power to be passed by the transistor to the speaker, the impedance of the speaker should equal the impedance of the transistor. Then, as the impedance and resistance of the speaker are the same, the right conditions will occur when half the direct voltage available for the transistor and speaker combination appears across each. This will not be quite half the voltage of the power supply because of a small drop across the inevitable stabilising resistor. It follows that with a transformerless Class A output circuit rather less than 25% efficiency can be obtained because, first, half the direct voltage available is lost across the speaker and, second, only half the audio power given by the transistor can appear across the speaker.

In the diagram (Fig. 3) and the equations which follow, C=collector current in mA for maximum undistorted output, S=impedance and resistance of speaker in ohms, R=stabilising resistor in ohms, B=power supply in volts, O=maximum undistorted output in mW.

From Ohm's Law and the expression for power in a.c. circuits, it follows that

$$C = \frac{1,000B}{2S + R}, \text{ and}$$

$$O = \frac{CSB}{4S + 2R}$$

These equations apply whether the transistor is connected as shown, or as a common collector device with the speaker in the emitter circuit and the stabilising resistor either in series with the speaker or, in some cases, in the collector lead. However, if the common collector configuration is used, the losses due to mismatching will be smaller because of the effect of negative feedback.

The accompanying table shows optimum current and maximum output for various combinations of speakers and supply voltages. The figures for R have been chosen such as to drop about 5% of the supply voltage. In some cases it may be possible to reduce the resistance of R a little.

TABLE

Calculated output currents and powers for different values of S, R and B in a transformless single transistor output stage.

S	R	B	C	O
15	1.8	6	189	267
		9	283	601
		12	378	1,070
25	3.0	18	566	2,403
		6	113	160
		9	170	361
35	4.0	12	226	640
		18	340	1,443
		6	81	116
80	10.0	9	121	258
		12	162	464
		18	243	1,034
		3	18	12
		4.5	26	28
	6	35	49	
	9	53	112	

Some of the figures are rather surprising. For instance, about 260mW is the absolute maximum power that can be obtained from a 6 volt supply and a 15Ω speaker; and with a 35Ω speaker about 18 volts are required for supply before 1 watt output can be achieved.

The figures for power are slightly optimistic as they assume that 50% of the power given by the transistor will appear across the speaker, whereas there are certain losses which will reduce the efficiency somewhat.

Stella Nine Range Cases

Manufactured in Black, Grey, Lagoon or Blue Stelvetite and finished in Plastic-coated Steel, Morocco Finish with Aluminium end plates. Rubber feet are attached and there is a removable back plate. There is also a removable front panel in 18 s.w.g. Alloy.

Now all Aluminium surfaces are coated with a stripable plastic for protection during manufacture and transit. All edges are polished.

LIST OF PRICES AND SIZES

which are made to fit Standard Alloy Chassis

Width	Depth	4" Height		6" Height		7½" Height	
		£	s. d.	£	s. d.	£	s. d.
6½"	3¾"	12	6	15	0	18	0
6½"	4¾"	13	6	18	0	1	0
8½"	3¾"	15	0	1	0	1	0
8½"	6¾"	1	1	0	6	1	1
10½"	7¾"	1	8	6	1	15	6
12½"	3¾"	1	1	0	6	1	1
12½"	5¾"	1	8	0	1	14	0
12½"	8¾"	1	16	0	2	3	0
14½"	3¾"	1	5	0	1	11	6
14½"	9¾"	2	3	0	2	15	9
16½"	6¾"	1	18	6	2	6	3
16½"	10¾"	2	10	0	3	5	0

Cases—Post 4s. 6d. per Order.
Discounts available on quantities.

CHASSIS in Aluminium, Standard Sizes, with Gusset Plates

Sizes to fit Cases All 2½" Walls

s. d.	s. d.	s. d.
6"×3"	5 6	10"×7"
6"×4"	5 9	12"×3"
8"×3"	6 6	12"×5"
8"×6"	7 9	12"×8"
		14"×3"
		14"×9"
		16"×6"
		16"×10"

Chassis—Post 3s. 0d. per Order.
Discounts available on quantities.


E. R. NICHOLLS

MANUFACTURER OF ELECTRONIC INSTRUMENT CASES

(DEPT. R.C.) 46 LOWFIELD ROAD
STOCKPORT - CHESHIRE

Tel: 061-480 2179

DIMMASWITCH

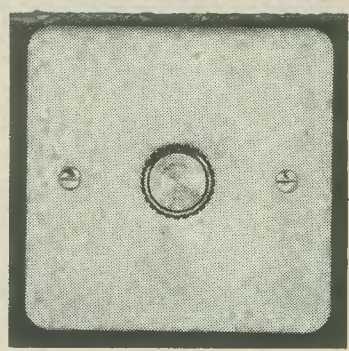

This is an attractive dimmer unit which fits in place of the normal wall light switch. The mounting plate is ivory to match modern fittings and the control knob is in bright chrome. An ON/OFF switch is incorporated to control up to 500 watts at mains voltages from 200-250 volts, 50HZ.

These are normally sold at £4 19s. 6d. —our price is £3 5s. We also offer at £2 15s. a complete kit of parts with simple instructions enabling you to build this dimmer yourself.

The circuit uses the latest miniature RCA triac and new diac triggering device to give complete reliability. Radio interference suppression is included.

DEXTER & COMPANY

14 Endsleigh Gardens, Chester CH2 1LT
Chester 26432

BENTLEY ACOUSTIC CORPORATION LTD.

38 Chalcot Road, Chalk Farm,
LONDON, N.W.1.
01 - 722 9090

The Old Police Station
Gloucester Road
LITTLEHAMPTON, Sussex
PHONE 6743

Please forward all mail orders to Littlehampton

5Z4G	6/9	ECC189	9/6	PC900	8/3	UABC80	5/9	ACY17	3/-	BYZ13	5/-
6A1T6	4/-	EFC80	6/6	PCC84	6/-	UBC81	7/-	ACY18	3/8	GET573	7/6
630L2	12/6	EFC82	6/6	PCC85	6/6	UBF80	5/9	ACY19	3/9	OA70	3/-
6BW6	12/9	EFC86	9/-	PCF88	9/9	UBF89	6/9	ACY20	3/6	OA79	1/9
6BW7	11/-	ECH42	10/-	PCC89	9/6	UC92	5/6	ACY21	3/9	OA81	1/9
6F23	13/3	ECH81	5/9	PCC189	9/6	UCC84	8/-	AD140	7/6	OA90	2/6
6L6GT	7/9	ECH83	8/-	PCF80	6/6	UCC85	6/6	AD149	8/-	OA91	1/9
10P13	13/-	ECH84	7/-	PCF82	6/6	UFC80	8/3	AD162	9/-	OA95	1/9
20P4	18/6	ECL80	6/6	PCF84	8/-	UCH21	9/-	AF14	4/-	OA182	2/-
30C15	13/6	ECL82	6/-	PCF86	9/-	UCH42	9/9	AF115	4/3	OA200	1/-
30C17	12/6	ECL83	9/-	PCF801	7/-	UCH81	6/6	AF119	3/-	OA202	2/-
30C18	8/9	ECL86	8/-	PCF802	9/-	UCL82	7/-	AF125	3/6	OC22	5/-
30F5	13/6	EF22	12/6	PCL82	7/-	UL83	10/-	AF139	13/-	OC23	5/-
30FL1	15/-	EF41	9/6	PCL83	9/-	UF41	9/6	AF180	9/6	OC24	5/-
30FL12	16/-	EF80	4/6	PCL84	7/6	UF80	6/9	BA102	9/-	OC25	5/-
30FL14	12/6	EF85	5/3	PCL85	8/3	UF85	6/9	BA115	2/8	OC26	5/-
30L17	13/9	EF86	6/9	PCF88	5/6	UF86	9/6	BA129	2/6	OC28	5/-
30L17	13/-	EF89	4/9	PE1A5DD	12/-	UF89	5/3	BA132	2/-	OC30	5/-
30P4	12/-	EF91	3/3	PFL200	12/-	UL41	9/6	BC107	4/-	OC35	5/-
30P4MR	17/6	EF183	6/3	PL36	9/6	UL84	6/6	BC108	3/6	OC36	7/6
30P12	13/-	EF184	6/6	PL81	7/3	UM80	5/-	BC113	5/6	OC38	11/6
30P19	12/-	EH90	6/6	PL82	6/6	UY41	6/9	BC118	4/6	OC41	10/-
30PL1	15/-	EL33	12/-	PL83	6/6	UY85	5/6	BCY10	5/6	OC44	2/-
30PL13	15/-	EL41	9/3	PL84	6/3	ZN404	6/-	BCY12	5/6	OC45	1/9
30PL14	15/-	EL84	4/6	PL500	12/-	ZN1756	10/-	BCY33	5/6	OC46	3/9
CL33	18/6	EL95	5/-	PL504	12/6	ZN2147	17/-	BCY34	4/6	OC70	2/3
DY87	5/9	EM80	5/9	PL509	28/9	ZN2297	4/6	BCY38	5/6	OC71	2/-
EB8CC	12/-	EM81	6/9	PL802	15/-	ZN2369	4/3	BCY39	4/6	OC72	2/-
EABC80	6/-	EM84	6/-	PY33	9/6	ZN2613	7/9	BCZ11	3/6	OC74	2/6
EAF42	6/-	EY81	11/9	PY31	5/3	ZN3053	6/6	BD19	9/-	OC75	2/-
EB91	2/3	EM87	7/3	PY82	5/-	ZN3121	50/-	BFY50	4/-	OC78	3/-
EB91	8/6	EY51	6/9	PY83	5/6	ZN3703	3/9	BFY51	4/-	OC78D	3/-
EB91	5/9	EY87	6/-	PY88	6/3	ZN3709	4/-	BFY52	4/6	OC81	2/-
EBF80	6/-	EZ40	7/3	PY800	6/6	ZN3866	20/-	BF159	5/6	OC81D	2/-
EBF83	8/-	EZ80	4/3	PY801	6/6	ZN3988	10/-	BF163	4/6	OC82	2/3
EBF89	6/3	EZ81	4/6	U19	34/6	25323	10/-	BF173	7/6	OC83	2/-
EC92	6/9	HV82	8/9	U25	13/-	AA119	3/-	BF180	6/-	OC84	3/-
ECC81	3/9	KTW62	10/-	U26	11/9	AA120	3/-	BY100	3/6	OC123	4/6
ECC82	4/6	PABC80	7/3	U37	34/11	AC113	5/6	BY126	5/6	OC169	3/6
ECC83	4/6	PC86	9/6	U191	12/6	AC127	2/-	BY127	5/6	OC172	4/-
ECC84	5/6	PC88	9/6	U301	11/-	AC154	5/6	BYZ10	5/6	OC200	4/4
ECC85	5/-	PC95	8/3	U404	7/6	AC156	4/6	BYZ11	5/6	OC202	4/6
ECC88	7/-	PC97	8/6	U801	18/-	AC157	5/-	BYZ12	5/6	OC203	4/6

Terms of business: Cash with order only. No C.O.D. Post/Packing 6d. per item. Orders over £5 post free. All orders despatched same day as received by first class mail. Complete catalogue including transistor section and components with terms of business 10d. Any parcel insured against damage in transit for 6d. extra. Business hours 9 a.m.-5.30 p.m. Saturdays 9 a.m.-1 p.m.

SMALL ADVERTISEMENTS

Rate: 9d. per word

Minimum charge 12/-

Box No. 2/- extra.

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the *bona fides* of advertisers. (Replies to Box Numbers should be addressed to: Box No. —, *The Radio Constructor*, 57 Maida Vale, London, W.9.)

BUILD IT in a **DEWBOX** robust quality plastic cabinet. 2in. x 2½in. x any length. S.A.E. for details. D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset. Write now—right now.

SERVICE SHEETS. Radio. Television. Transistors. Tape Recorders. Record Players (1925-1969). S.A.E. enquiries.—Hamilton Radio, 54 London Road, Bexhill, Sussex.

UFO DETECTOR CIRCUITS. Data, 10s. (refundable). Para-physical Laboratory (UFO Observatory), Downton, Wilts.

4 WATT GRAM AMPLIFIERS. Volume and tone controls. New and boxed. Fully guaranteed. Immediate delivery. Only 65/- post paid.—D. H. Electronics, 23 Wyle Cop, Shrewsbury, Shropshire.

"MEDIUM WAVE NEWS" Monthly during DX season.—Details from: K. Brownlee, 7 The Avenue, Clifton, York.

BOOKS FOR SALE: *Radio Astronomy*, Bernard Lovell & J. Clegg 12/6d. *Earth's Envelope*, Theo Lobsack 10/-, *Space Research & Exploration*, D. R. Bates 15/-, *Practical Yacht Racing*, Schiottz 15/-, *Yacht Racing*, Sturges £1, *Faster Sailing*, Bavier 10/-, *The Story of Atomic Energy*, Soddy 7/6d., *Radioisotope Laboratory Techniques*, Faires 7/6d., *Atomic Medicine*, Behrens 15/-, *Medical Radiation Biology*, Ellinger £1, *Sunday Times & Life World Library Volumes: Brazil, S.E. Asia, Israel, Italy, Russia, Mexico, Greece, Africa, Germany, France, India, Britain, Japan, Scandinavia*, 12/6d. each, *Life Science Library: Wheels, Mathematics, Man & Space, Planets, Energy*, 12/6d. each, *The Colour of Canada*, £1, *Science Survey 3*, Vista Books £1, *Science Today & Tomorrow* 10/-, Box No. F364.

MUSICAL MIRACLES. Send s.a.e. for details of Drum Sound Modules, versatile bass-pedal accompaniment unit, self-contained with unique effects. Kits for Waa-waa pedals 47/-, Also 50µA meters 25/- each. New. D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

FOR SALE: 77 copies *The Radio Constructor*, 1954-1963, complete volumes 8, 9, & 11. 17 copies *Practical Wireless*, 1962-1963. Offers? D. J. Norris, 7 Sawtry Close, Carshalton, Surrey.

FOR SALE: 110 used valves. 4-9 pins. £7 o.n.o. Telephone: 01-467-5091.

JOIN THE INTERNATIONAL S.W. LEAGUE. Free Services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept.—both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazine, etc., 35s. per annum. Secretary ISWL, 60 White Street, Derby.

continued on page 126

THE RADIO CONSTRUCTOR

TECHNICAL TRAINING by ICS IN RADIO, TELEVISION AND ELECTRONIC ENGINEERING

First class opportunities in Radio and Electronics await the ICS trained man. Let ICS train YOU for a well-paid post in this expanding field.

ICS courses offer the keen, ambitious man the opportunity to acquire, quickly and easily, the specialized training so essential to success.

Diploma courses in Radio TV Engineering and Servicing Electronics, Computers, etc. Expert coaching for:

- * C. & G. TELECOMMUNICATION TECHNICIANS CERTS.
- * C. & G. ELECTRONIC SERVICING
- * R.T.E.B. RADIO AND TV SERVICING CERTIFICATE
- * RADIO AMATEURS EXAMINATION
- * P.M.G. CERTIFICATES IN RADIO TELEGRAPHY

Examination Students Coached until Successful.

NEW SELF-BUILD RADIO COURSES

Build your own 5-valve receiver, transistor portable, signal generator, multi-test meter and professional-type valve voltmeter—all under expert guidance.

POST THIS COUPON TODAY and find out how ICS can help YOU in your career. Full details of ICS courses in Radio, Television and Electronics will be sent to you by return mail.

MEMBER OF ASSOC. OF BRITISH CORRESPONDENCE COLLEGES.

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 248, Intertext House, Stewarts Road, London, S.W.8.


NAME

Block Capitals Please


ADDRESS

9.69

SINCLAIR IC-10

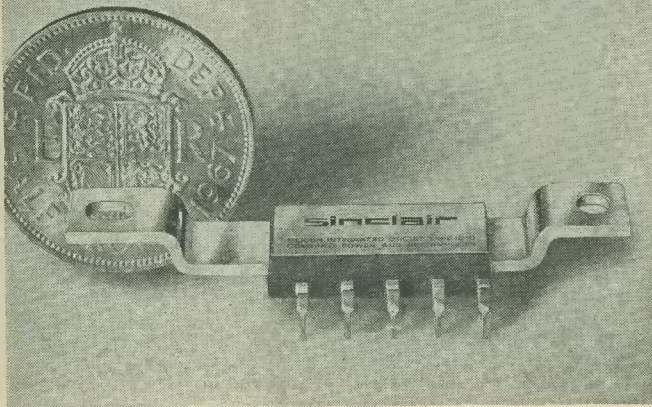

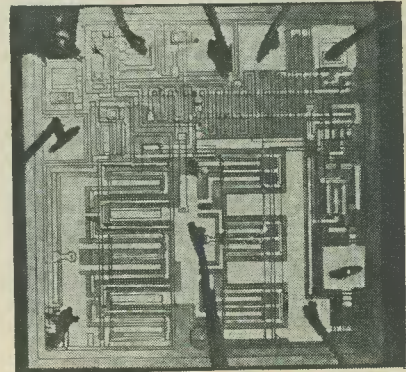10 WATT MONOLITHIC INTEGRATED CIRCUIT AMPLIFIER AND PRE-AMP



A 13 transistor circuit measuring only one twentieth of an inch square by one hundredth of an inch thick!

the world's most advanced high fidelity amplifier

The Sinclair IC-10 is the world's first monolithic integrated circuit high fidelity power amplifier and pre-amplifier. The circuit itself, a chip of silicon only a twentieth of an inch square by one hundredth of an inch thick, has an output power of 10 watts. It contains 13 transistors (including two power types), 2 diodes, 1 zenor diode and 18 resistors, formed simultaneously in the silicon by a series of diffusions. The chip is encapsulated in a solid plastic package which holds the metal heat sink and connecting pins. This exciting device is not only more rugged and reliable than any previous amplifier, it also has considerable performance advantages. The most important are complete freedom from thermal runaway due to the close thermal coupling between the output transistors and the bias diodes and very low level of distortion.

The IC-10 is primarily intended as a full performance high fidelity power and pre-amplifier, for which application it only requires the addition of the usual tone and volume controls and a battery or mains power supply. However, it is so designed that it may be used simply in many other applications including car radios, electronic organs, servo amplifiers (it is d.c. coupled throughout), etc. The photographic masks required for producing monolithic I.C.s are expensive but once made, the circuits can be produced with complete uniformity and at very low cost. It also enables us to give a 5-year guarantee on each IC-10, knowing that every unit will work as perfectly as the original and do so for a lifetime.

■ SPECIFICATIONS

Output: 10 Watts peak, 5 Watts R.M.S. continuous.
 Frequency response: 5 Hz to 100 KHz ± 1 dB.
 Total harmonic distortion: Less than 1% at full output.
 Load impedance: 3 to 15 ohms.
 Power gain: 110dB (100,000,000,000 times) total.
 Supply voltage: 8 to 18 volts.
 Size: 1 x 0.4 x 0.2 inches.
 Sensitivity: 5mV.
 Input impedance: Adjustable externally up to 2.5 M ohms.

■ CIRCUIT DESCRIPTION

The first three transistors are used in the pre-amp and the remaining 10 in the power amplifier. Class AB output is used with closely controlled quiescent current which is independent of temperature. Generous negative feedback is used round both sections and the amplifier is completely free from crossover distortion at all supply voltages, making battery operation eminently satisfactory.

■ APPLICATIONS

Each IC-10 is sold with a very comprehensive manual giving circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include stabilised power supplies, oscillators, etc. The pre-amp section can be used as an R.F. or I.F. amplifier without any additional transistors.

SINCLAIR

IC.10 with IC-10 manual and 5-year guarantee Post free

59'6

sinclair


SINCLAIR RADIONICS LIMITED

22 NEWMARKET RD, CAMBRIDGE Tel: 0223 52731

NEW

25 WATTS
(50 WATTS PEAK)

**HIGH-FIDELITY
POWER AMPLIFIER**

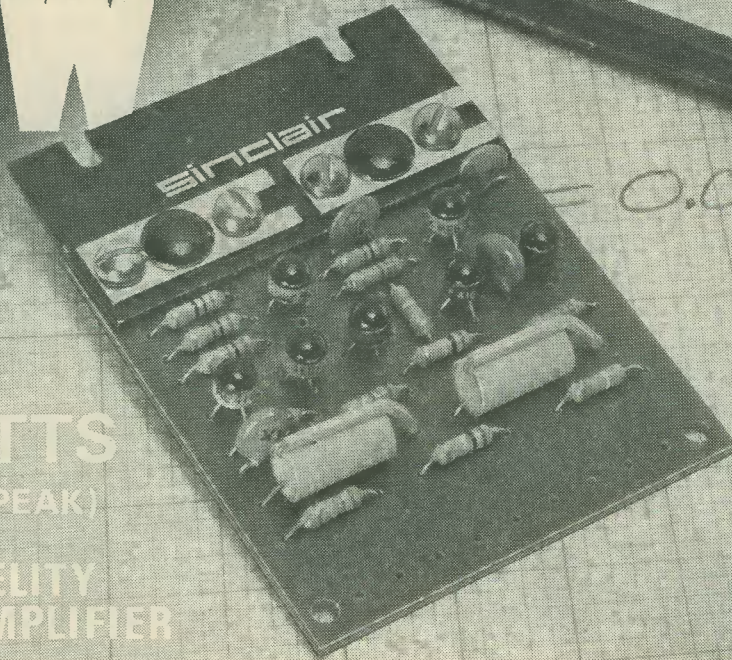

Z.30

**0.02% DISTORTION
AT FULL POWER**

■
**OPERATES IDEALLY
FROM 8 TO 35 VOLTS**

■
SIZE 3½ x 2¼ x ½ ins.

■
**FREQUENCY RESPONSE
FROM 20 Hz TO 30 kHz**

■
**USE IT FOR
HIGH FIDELITY, MUSIC
INSTRUMENTS, ECONOMY
RECORD PLAYER, P.A.,
INTERCOM, ETC.**


*Built, tested and
guaranteed, with
Z.30 manual*

89/6

THE WORLD'S LOWEST DISTORTION HIGH FIDELITY AMPLIFIER

For four years, the Sinclair Z.12 dominated the constructor world, being the best selling unit of its kind this side of the Atlantic. Excellent as it was, the new Sinclair Z.30 is still better. Half the size of the Z.12, it has more than twice the power, very much greater gain and a level of distortion 50 times lower. This incredible figure results from using over 60dB of negative feedback with a constant current load to the driver stage obtained by incorporating a two-transistor circuit in place of the more usual boot-strapping. 9 silicon epitaxial planar transistors are used to provide enormous power (up to 25 watts RMS continuous sine wave (50 watts peak)). The circuitry of this marvellous amplifier allows it to be operated from any voltage from 8 to 35 to perfection. At all output levels, distortion is only 0.02%. This puts true laboratory standards into the hands of every user of a Z.30. Two Z.30s and a new Stereo Sixty will make a stereo assembly of such perfection that it could not be bettered in its class no matter how much you spent. But the Z.30 has an enormous variety of applications, particularly where quality, precision and reliability are essential. Yet this brilliant new Sinclair design costs not a penny more than its famous predecessor.

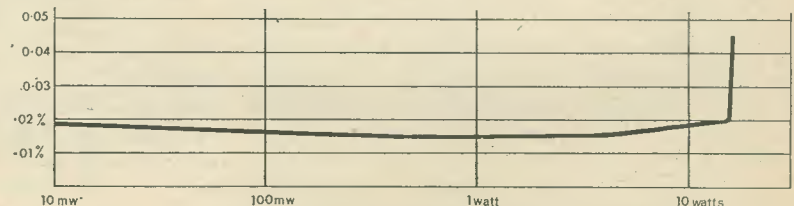- Input Sensitivity—250 mV into 100 Kohms
- Signal to noise ratio—better than 70dB unweighted
- Class AB output
- Power requirements 8–35 volts from batteries or PZ.5



sinclair

SINCLAIR RADIONICS LIMITED

22 NEWMARKET ROAD, CAMBRIDGE Tel: 0223 52731

THE RADIO CONSTRUCTOR

SENIOR RADIO TECHNICIAN

required for U.S. Middle East Oil Company familiar with LF, HF & VHF equipment. Must have C & G. or similar certificate plus experience in maintenance, installation and testing. Bachelor status. Good accommodation and pay. Low tax. 28 days annual leave, fare paid home. Sports and other facilities. Free medical treatment. Position can be permanent.

Details in confidence to:

P.M.C. Management Services,
160 High Street, Burton-on-Trent.

INTERNATIONAL SHORT WAVE LEAGUE



Membership 35s. 0d. per annum (U.S.A. \$5.00) including 12 monthly issues of *Monitor* — the League journal. Including free use of all Services, QSL Bureau, etc.

**THE LARGEST S.W.L. ORGANISATION
IN THE WORLD**

For full details write to:

**The Secretary,
I.S.W.L.,
60 WHITE STREET, DERBY**

SMALL ADVERTISEMENTS

Continued from page 122

LARGEST SUPPLIERS OF SERVICE SHEETS: TV, Radio, Tape, Recorders, Record Players, Transistors, Stereograms, Radiograms. Only 5/- each, plus s.a.e. Uncrossed P.O.'s please, returned if service sheets not available. We have the largest supplies of service sheets (strictly by return of post). Please state make and model number alternative. Mail order only. Please mention *The Radio Constructor* when answering this advert. Mr. C. Caranna, 71 Beaufort Park, London N.W.11.

FOR SALE: Disposing of small collection of 78 r.p.m. records. Classical, semi-classical and light music (some musicals). Many collector's items. S.A.E. for list. Box No. F369.

38 SET power supply. L.F. unit. Two 12 x 6 way connectors wanted. — P. Smithson, 1 Orlando Street, Bootle 20, Lancs.

MAGAZINES FOR SALE: *Wireless World* July to September 1965 inc., March, July and September 1966, 1967-January & February, May, June, August and September. *Radio Constructor* January 1966 to March 1968 inclusive. *Practical Wireless* 1964 February to April inc., June, 1965-March to September inc. plus November & December; 1966-January to April inc. *Practical Television* 1965-January, April, July & August; 1966-January to July inc., plus September & October. *Short Wave Magazine* 1965-March, July, September to December inc.; 1966-January to November inc. *R.S.G.B. Bulletin* 1965-January, March, June, August, September, November & December; 1966-January to September inc., plus November. *Hi-Fi News* 1965-May, August to October inc., November & December; 1966-January to October inc. *Amateur Tape Recording* 1965-May, August, September, October & December; 1966-January to April inc., June to August inc.; 1967-April, May, June to September inc. What offers? Will sell in lots or separately. Can be collected in London. Box No. F370.

POSTAL ADVERTISING? This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list.—The Holborn Direct Mail Company, Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407-1495.

FOR SALE: "Premier" Cine Film storage cases, grey hammer enamel finish, carrying handle, lock. Size 12in. x 7½in. x 7½in. to take 10 400ft. reels and cans at £1. Size 11in. x 6in. x 6in. to take 11 200ft. reels and cans at 15/-. Box No. F375.

WORLD DX CLUB covers all aspects of SWLing on Amateur and Broadcast Bands through its monthly bulletin "Contact". Membership costs 25s. a year. Enquiries to Secretary, WDXC, 17 Taunton Road, Bridgewater, Somerset.

CLEARING LABORATORY. Oscilloscopes, VTVM's, VOM's H.S. recorders, transcription turntables, electronic testmeters, calibrators, p.s.u.'s, pulse generators, d.c. null-potentiometers, bridges, spectrum analysers, voltage regulators, sig-gens, CCTV monitors, M/C relays, components, etc. Telephone: Lower Beeding 236.

FOR SALE: Revspeed revolution counter £3. Box No. F378.

FOR SALE: Metal Rectifier, Radiospares Type REC22, 30/-. Push-pull Interstage transformer, Repanco Type TT4, 7/6d. Pair Mullard OC36 transistors, unused 35/-. Heat sink to match, 10/-. 0-200mA meter, 2½in. diam., flush mounting, 10/-. 0-40mA meter, 2in. sq. f.m., 15/-. 50 assorted resistors, £1. 25 assorted capacitors, £1. Box No. F379.

continued on page 127
THE RADIO CONSTRUCTOR

SMALL ADVERTISEMENTS

Continued from page 126

PROFESSIONALLY MADE CONTROL PANELS from 4d. sq. inch. 16/18 gauge aluminium, cut, drilled, spray painted and legend. Send full size drawing for quotation. C. S. Conduit, 7 Millbrook, Salisbury, Wilts.

YOU CAN EARN EXTRA CASH in the comfort of your own home. Send now for free details to: Pittville Products, (RC51), 41 Canterbury Walk, Cheltenham, GL51 5HN.

ESSEX GARDENERS. Buy your bedding and rock plants, shrubs, etc., also cacti from May's Nurseries, 608 Rayleigh Road, Hutton, Brentwood, Essex. Callers only. Monday to Saturday.

FOR SALE: Four Mullard RG1-240A rectifier valves, with high voltage insulation filament transformer, suitable use in pairs. £5. Box No. G100.

BOOST! B.B.C.1-I.T.A. VHF Amplifier, Setside, battery powered. 50/-. Specify channels.

BOOST! UHF Amplifier, Setside, battery powered. 55/-. Covers all stations in area. Specify channels. B.K. Equipment, 7 St. George's Road, Belton, Gt. Yarmouth, Norfolk.

FOR SALE: 813 valve and socket. 50/-. Box No. G101.

INNOVATION IN DX CLUBS ANNOUNCED! Formed in October, 1965, the Radio New York Worldwide Listeners Club now has 3,600 members in 86 countries! A unique club offering shortwave listeners monthly magazines containing listening tips and technical features, numbered wallet-sized membership cards and gold 8½in. by 11in. membership certificates. Multi-lingual report forms available for cost of postage. "We must be doing something right!" Find out . . . join now!" Send 7s. 2d. (crossed domestic money order) for one year's membership to: The Radio New York Worldwide Listeners Club, 485 Madison Avenue, New York 10022, U.S.A.

ASSORTED LOTS OF USED COMPONENTS. Resistors 15/- for 50. Capacitors 10/- for 20. Box No. G102.

2.5kV SOLID STATE POWER SUPPLY for sale. As per description in *The Radio Constructor*, August 1966 issue. In cabinet 8in. wide x 11in. deep x 9½in. high. Matsunaga Variac and 0-3000V d.c. meter. £25 o.n.o. Box No. G103.

PROPERTIES for sale and to let in London and suburbs. Apply to Maggs & Stephens, Estate Agents, 229 Maida Vale, London, W.9. MAIDA VALE 8123.

TOROIDS FOR SALE: 550, 475, 500, 395, 480, 210, 185, 110, 92mH. 5/- each. Box No. G104.

IF YOU HAVE ENJOYED A HOLIDAY on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from:— The Hon. Membership Secretary, The Broads Society, "Icknield", Hilly Plantation, Thorpe St. Andrew, Norwich, NOR 85S.

GRAND CLEARANCE SALE everything must go

SUPER WHIP AERIALS. Brand new specially designed telescopic, chrome plated 25 in. sectional aerials. Consists of 6 sections and screw base. An ideal aerial for TX/RX use. Price only 6/6 each, p.p. 1/6. Two aerials for 12/6 post free. Four aerials £1 post free.

PRECISION METERS. Brand new and boxed, size 3½ in. sq. — Type 1, 0-500v. FSD; Type 2, 0-150 m/a. Moving coil movement. Fully guaranteed. List £3/10/-. Sale price 30/- each. Two for 50/- post free.

PRINTED CIRCUIT TOP BAND SUPERHET CHASSIS. Uses standard components. Complete with circuit. Only 15/- post free.

MINIATURE TRANSISTORISED B.F.O. UNIT. A compact B.F.O. unit that will enable your set to receive CW or SSB. Compact single hole fixing. The unit will fit anywhere. Ideal for all ex-Govt. and commercial receivers. Complete with fitting instructions. Only 39/6, p.p. 2/6.

HEAVY DUTY POWER SUPPLY UNITS. Famous manufacture. Input 200/250 volts A.C. Output 250 volts D.C. at 175 m.a. 6.3v./12v. at 4 amps. Robust rack mounting cabinet. List £42. Sale price 69/6 carr. 10/-.

GOVERNMENT SURPLUS WIRELESS EQUIPMENT HANDBOOK. Gives circuit details and notes on most British and American wireless equipment. Only 35/-, p.p. 5/-.

TELEPHONE SPARES. 600 TYPE RELAYS. Only 3/6 each p.p. 1/- Ten for £1 post free. **EYEBALL INDICATORS.** 6/- each. Four for £1 post free. **TELEPHONE DIALS** 4/6 each, p.p. 1/6. Four for £1 post free.

MEDIUM WAVE FERRITE SLAB AERIALS. Will fit most transistor radios. Only 3/6 each p.p. 6d. Two for 6/- post free. Four for 10/- post free.

HANDY PLASTIC CASES. Size 2½ in. by 1½ in. by ½ in. Ideal for building your transistorised equipment into. Only 1/- each p.p. 4d. 12 for 10/- post free. 24 for 15/- post free. 50 for 30/- post free. 100 for 50/- p.p. 5/- A very versatile little box.



GLOBE SCIENTIFIC LTD

All orders & callers to

DEPT. RC GLOBE SCIENTIFIC LTD, 38 BRIDGE END, LEEDS 1.

FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?

ENGINEERING OPPORTUNITIES is a highly informative 164 page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronic Courses administered by our Specialist Electronics Training Division — explains the benefits of our Appointments Dept. and shows you how to qualify for five years promotion in one year.

"Satisfaction or refund of fee" terms

Whatever your age or experience you cannot afford to miss reading this famous book. Send for your copy of "ENGINEERING OPPORTUNITIES" today — FREE.

Practical Equipment including Tools

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Basic Practice and Theoretical Courses for beginners in Radio, T.V., Electronics, etc. Ask for details.

Which is your pet subject

A.M.I.E.R.E. City & Guilds Radio Amateur's Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

The B.I.E.T. is the leading institute of its kind in the world.

WINGS APPEAL SEPT 15th-20th

**GIVE FOR
THOSE WHO
GAVE**



Please send
Free Books and
Full Information

**British Institute of
Engineering Technology**

NAME

ADDRESS



Subject
of interest..... Age.....

ALDERMASTON COURT, Dept. 480D. Aldermaston, Berks.

CHASSIS and CASES by



H. L. SMITH & CO. LTD.
287/9 Edgware Road
London W2
TEL: 01-723 5891


BLANK CHASSIS

FOUR-SIDED 16 SWG ALUMINIUM

Size	Price	Base	Size	Price	Base
6x4x2"	6/3	2/11	10x8x2 1/2"	12/-	5/6
7x4x1 1/2"	6/-	3/2	12x7x2 1/2"	12/-	5/11
7x5x2"	7/6	3/5	12x9x2 1/2"	13/9	7/-
8x4x2"	7/-	3/4	13x8x2 1/2"	13/9	6/11
8 1/2 x 5 1/2 x 2"	8/-	3/9	14x7x3"	14/6	6/6
9x7x2"	9/3	4/10	14x10x2 1/2"	16/-	8/7
10x4x2 1/2"	9/-	3/9	15x10x2 1/2"	16/6	9/1
12x4x2 1/2"	10/-	4/3	17x10x3"	19/6	10/1
12x5x3"	12/-	4/9			

CASES ALUMINIUM, SILVER HAMMERED FINISH

Type	Size	Price	Type	Size	Price
N	8x6x2"	18/-	W	12x7x7"	37/6
N	6x6x3"	17/6	W	15x9x8"	48/6
N	4x4x2"	11/-	Y	8x6x6"	29/-
U	4x4x4"	11/-	Y	12x7x7"	45/-
U	5 1/2 x 4 1/2 x 4 1/2"	17/-	Y	13x7x9"	50/6
U	8x6x6"	23/-	Y	15x9x7"	53/6
U	9 1/2 x 7 1/2 x 3 1/2"	24/-	Z	17x10x9"	72/6
U	15x9x9"	49/-	Z	19x10x8 1/2"	78/-
W	8x6x6"	23/-			

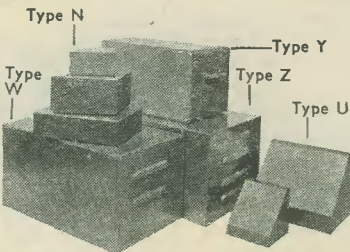

Type N has removable bottom, Type U removable bottom or back, Type W removable front, Type Y all screwed construction, Type Z removable back and front. Plus p. & p.

TO FIT OUR CASES

7x5 1/2 x 1 1/2"	7/-	3/9	12x6 1/2 x 2"	10/9	5/11
7x5 1/2 x 2"	7/9	3/9	14x8 1/2 x 2"	13/6	7/11
11x6 1/2 x 1 1/2"	10/-	5/6	15 1/2 x 9 1/2 x 2 1/2"	17/-	9/6
11x6 1/2 x 2"	10/-	5/6	17 1/2 x 9 1/2 x 2 1/2"	18/6	10/6

Plus post & packing


PANELS: Any size up to 3ft. at 6/- sq.ft. 16 s.w.g. (18 s.w.g. 5/3). Plus postage and packing.

THE WILSIC REVERBERATION UNIT KIT

Self-contained, 6 transistor, reverberation chamber to which microphones, instruments, tuners or tape recorders may be connected for added dimensional effect. The output is suitable for most amplifiers and the unit is especially suitable for use with electronic organs. A ready-built spring and transducer assembly is used (£8/11 if bought separately). Complete, easy-to-build kit with constructional notes and circuits: £7.10.0. Pre-drilled and printed case 34/- extra. All parts available separately. Send 1/- for circuit and construction details.

THE WILSIC SIGNAL INJECTOR

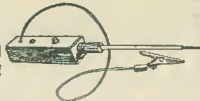Miniature transistorised square wave signal injector, ready for use, only 19/6 including battery. P. & P. 1/6.



Send 1/- for our catalogue of components, testmeters, musical electronics & more details of the above items. Callers welcome.

WILSIC ELECTRONICS LIMITED

6 Copley Road, Doncaster, Yorkshire

YUKAN SELF-SPRAY SO PROFESSIONAL THE YUKAN AEROSOL WAY-

Get these air drying GREY HAMMER NOW! OR BLACK WRINKLE (CRACKLE) finishes

Yukan Aerosol spraykit contains 16 ozs. fine quality, durable easy instant spray. No stove baking required. Hammers available in grey, blue, gold, bronze. Modern Eggshell Black Wrinkle (Crackle) all at 15/11 at our counter or 18/11, carriage paid, per push-button self-spray can. Also Durable, heat and water resistant Black Matt finish (12 ozs. self-spray cans only) 13/11 carriage paid.

SPECIAL OFFER: 1 can plus optional transferable snap-on trigger handle (value 5/3) for 18/11, carriage paid. Choice of 13 self-spray plain colours and primer (Motor car quality) also available.

Please enclose cheque or crossed P.O. for total amount direct to:

DEPT: N/5 YUKAN, 307A, EDGWARE ROAD, LONDON, W.2.

We supply many Government Departments, Municipal Authorities, Institutes and Leading Industrial Organisations - We can supply you too.

Open all day Saturday. Closed Thursday afternoons.



Other Yukan Air Drying Aerosols, 16 ozs. at 16/11 each, plus:

Includes:
Zinc Chromate Clear Lacquer
Metallics: Grey, Blue, Bronze and Gold.

NOW AVAILABLE

BOUND VOLUME No. 22

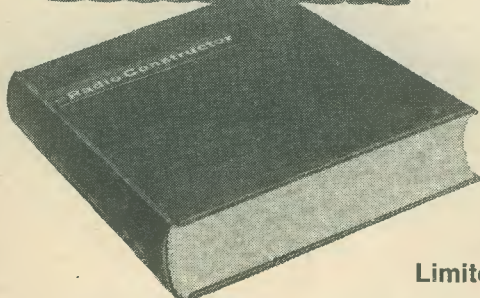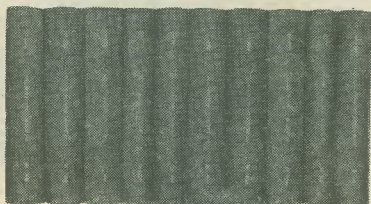of "The Radio Constructor" **FOR YOUR LIBRARY**



AUGUST 1968 to JULY 1969
Comprising 800 pages plus index

PRICE 35/- Postage 4/6

Special discount of 10/- for regular readers

Just cut the heading from each month's contents page, including title and month of issue, and this will be sufficient evidence of readership to qualify for the discount.

Thus regular readers will still retain their copies for workbench use, while having a splendid bound volume containing issues in mint condition.

PRICE 25/- Postage 4/6

Limited Number of Volume 21 - Price 35/- Postage 4/6

(August 1967 to July 1968) still available

We regret earlier volumes now completely sold out.

Available only from

DATA PUBLICATIONS LTD., 57 MAIDA VALE, LONDON, W.9

ENGLANDS LEADING COMPONENT & EQUIPMENT CENTRES

SOLID STATE-HIGH FIDELITY AUDIO EQUIPMENT


Mono or Stereo Audio. Equipment developed from Dinsdale Mk.II—each unit or system will compare favourably with other professional equipment selling at much higher prices.

COMPLETE SYSTEMS FROM **£15.5.0**

THE FINEST VALUE IN HIGH FIDELITY—CHOOSE A SYSTEM TO SUIT YOUR NEEDS AND SAVE POUNDS

All units available separately.

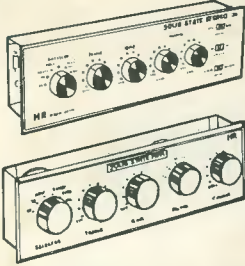SEND FOR FREE BROCHURE (No. 21) TODAY!
DEMONSTRATIONS DAILY AT '303' EDGWARE ROAD



ELECTRONIC ORGANS KITS TO BUILD YOURSELF AND COMPLETE UNITS

Acclaimed by everyone

The MAYFAIR

A completely new development in portable electronic musical instruments and a new field for the home constructor. The "MAYFAIR" produces a multitude of the most pleasing sounds with a wide range of tone colours, suitable for classic or popular music. The organ is fully polyphonic, that is full chords can be played over the entire keyboard. Includes 165 transistors, printed circuits panel, special fly spring and depth of touch adjusted keyboard, attractive vinyl covered cabinet with carry handle. A complete detailed and illustrated construction manual is provided with circuits and full parts list. All items may be purchased separately. All parts supplied are fully guaranteed. Full after sales service.

Deferred terms available
COMPLETE KIT
Deposit £29.19.0
12 monthly payments of
£7. Total £113.19.0
BUILT AND TESTED
Deposit £36.8.0 and
12 monthly payments of
£5. Total £164.8.0



THE MAYFAIR 99 GNS
BROCHURE 9

The GROSVENOR

is designed for the more ambitious musician and has a much wider range than most commercial organs. It comprises two four-octave (49 note) keyboards and a thirteen-note pedal board. It has four pitches (i.e. 8ft, 4ft, 2ft, 1ft) on the upper or solo keyboard, two pitches (i.e. 16ft, 8ft, 4ft) on the lower or accompaniment keyboard, two pitches (i.e. 16ft, 8ft) on the pedal board. Variable sustain on the solo keyboard and variable vibrato on both keyboards. It has 15 voices in the solo tone-forming unit, 10 voices in the accompaniment tone-forming unit and 4 voices in the pedal tone-forming unit. All components and kit sections are available separately including the Oak Console at £65.18.0.



THE GROSVENOR
KITS FROM £220 terms available
BROCHURE 9B

A complete detailed and illustrated construction manual is provided with circuits and full parts list. All items may be purchased separately. All parts supplied are fully guaranteed. Full after sales service and advice freely available. Once built the "MAYFAIR" or "GROSVENOR" will then provide years of enjoyable music. Call in—See them for yourself.

PRACTICAL ELECTRONICS—ELECTRONIC ORGAN KIT


We are able to supply Parts as described in this series. Details on request.

ORGAN COMPONENTS: COMPLETE RANGE IN STOCK - 49 AND 61 NOTE KEYBOARDS - 2 TO 5 AMP GOLD CONTACTS COILS AND CHOKES - REVERBERATION SPRINGS AND UNITS - STOP TABS AND ASSEMBLIES - PEDAL BOARDS - RHODIUM AND COPPER CLAD WIRE, ALSO PRINTED CIRCUITS ETC. COMPLETE RANGES FOR TRANSISTORISED ORGANS. ASK FOR NEW PRICE LISTS WITH DETAILS. LEAFLET 9B ALL ENQUIRIES TO: ORGAN DEPT.—MR. ELVINS

INTEGRATED TRANSISTOR AMPLIFIERS

MA66 12 WATTS STEREO

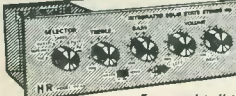We are pleased to offer two new designs with the choice of either mono or stereo systems. These BRITISH DESIGNED UNITS favour the user in so many ways—with fantastic power and quality with far greater adaptability, with freedom for battery or mains operation.



MAT MONO
£8.10.0

For complete listening satisfaction choose either—

OR THE STEREO
POST PACKING 6/-
EITHER MODEL


MA66

£16.10.0

OPTIONAL MAINS UNIT
PS20 62/6d. p.p. 4/-

Illustrated leaflets 12 and 14 FREE on request.

PORTABLE GEIGER COUNTERS

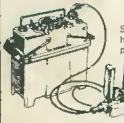


FOR MEASUREMENT OF RADIATION ACTIVITY.

Supplied complete with instructions, haversack, cables and probe. List price £70.

OUR PRICE, NEW, TESTED COMPLETE WITH BATTERIES
£7.10.0

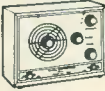POST 10/-
SPARE BATTERIES 15/- PAIR
POST 5/-



NEW MODELS NOMBREX

TRANSISTORISED Test Equipment

PRICE Leaflet

MODEL	£	s	d	No.
29a R.F. Gen.	21	0	0	35
29x Xtal R.F. Gen.	29	10	0	36
30 Audio Generator	19	10	0	24
31 R.F. Generator	12	10	0	25
32 C.R. Bridge	10	10	0	26
33 Inductance Bridge	20	0	0	29

The Detector Unit consists essentially of a highly sensitive 931A photo-electric cell combined with a firing circuit. Incorporates a single cold cathode electronic relay, capacitors and resistors designed to fail to safety if external wiring is open or short circuited. Encapsulated in a case which fully insulates the unit electrically and provides a high degree of mechanical and thermal shockproofing. Original price 77/4. OUR PRICE, BRAND NEW £6 each, with data sheet. Limited quantity available.

GRAVINER FIRE DETECTOR UNIT


SIZE 4 x 3 x 2 1/2 in.

SCOOP! STARR RECORD PLAYER

Deck, Plays 33, 45, 78 records, 9 volt operated. With mono cartridge. Brand new. As illustrated, 59/6 post 3/6. MULLARD 1 WATT AMPLIFIER 9 volt, 5 transistor unit complete with volume control. Output to 3 ohms. Ideal for use with Starr record Deck. 45/- post 3/6. Send for leaflet 2.

BUILD A QUALITY TAPE RECORDER

To get the best out of your MAGNAVOX DECK, you need a MARTIN RECORDKIT. This comprises a special high quality 6 valve amplifier and pre-amplifier which comes to you assembled on its printed circuit board—in fact everything needed down to the last screw FOR MAKING A SUPERB TAPE RECORDER, which, when built, will compare favourably with instruments costing twice as much, yet you need no experience or technical skill to bring this about. THE INSTRUCTIONS MANUAL MAKES BUILDING EASY AND SUCCESS ASSURED.

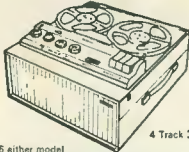

P.P. 22/6 either model

Kit comprises: Deck, Amplifier, Cabinet and speaker, with MICROPHONE 7 in 1, 2,000 Hz. tape, spare spool. ALL UNITS AVAILABLE SEPARATELY. Today's Value £80. ASK FOR BROCHURE 6.

VHF FM SUPERHERT TUNER MKII

*5 MULLARD TRANSISTORS & 4 DIODES - 300 Kcs/s BANDWIDTH - PRINTED CIRCUIT CONSTRUCTION - HIGH FIDELITY REPRODUCING MONO AND STEREO

A popular VHF FM Tuner now used throughout the country for quality reception of monophonic and, with the decoder stereophonic broadcasts. There is no doubt about it—VHF FM gives the real sound. Excellent stability economically priced. PARTS TOTAL COST £6.19.6. DECODER £5.19.6. (CABINET 20/- EXTRA) ASK FOR LEAFLET 3.

MANUFACTURERS—DISTRIBUTORS

We publish a QUANTITY, SEMI-CONDUCTOR BULLETIN listing over 500 different devices available FROM STOCK in medium to large quantities at KEEN PRICES coupled with PROMPT DELIVERIES. TO OBTAIN YOUR COPY, WRITE TO US (on Company Headed Newspaper please) requesting our SEMI-CONDUCTOR BULLETIN. For TELEPHONE QUOTATIONS, PHONE (01) 723 1008/9 Extn. 4 (01) 723 0401 Extn. 4.

We purchase medium to large quantities of Transistors and Devices excess to Manufacturers and Distributors requirements. Write or phone 723-0401 extn. 4.

NEW—MALLORY LONG LIFE MERCURY BATTERIES 50% OFF LIST PRICE

*RM12 1.35 volts 3600 mAh OUR PRICE 5/- each size 2 1/2 x 3 1/2 dia.

*RM625 10.35 volts 350 mAh Pack of 8. Size 2 1/2 x 4 1/2 dia.

OUR PRICE 10/- each

Easily split into eight 1.35v cells. These cells are ideal for any application where SMALL SIZE HIGH CAPACITY and LONG LIFE are required. QUANTITIES AVAILABLE.

GARRARD RECORDS

BRAND NEW All below list price £ s d
2025 Mono/Stereo GKS 25 8 8 0
3000LM Mono/Stereo 9 TAHC 9 16 6
SP25 Mk II 9 19 6
AT60 Mk II 13 0 0
APT5 19 0 0
SL55 11 19 6
SL65 14 14 0
SL75 29 0 0
SL85 35 0 0
A70 Mk II 12 12 0
B.S.R. UA25 Mono 5 19 6
MA65 9 19 6
MA70 12 12 0
MA75 15 5 0
401 Garrard 28 10 0

Carriage/Packing 7/6d. all models. Complete range of accessories available. Send for New 8 page brochure 16, 17.

TRANSISTORS—SEMICONDUCTORS

COMPLETELY NEW 1969 LIST OF 1000 types. Send for your FREE COPY TODAY. (list 36)

S.C.R.'s from 5/-
Field Effect Transistors from 7/6
Power Transistors from 5/-
Diodes and Rectifiers from 1/6


Hi-Fi equipment to suit EVERY POCKET

VISIT OUR NEW HI-FI CENTRE at 309 EDGWARE ROAD AND SAVE UP TO £40 ON SEPARATE UNITS OR THE SYSTEM OF YOUR CHOICE for all leading makes

- AMPLIFIERS
- TUNERS
- DECKS
- SPEAKERS
- MICROPHONES
- TEST EQUIPMENT
- HEADPHONES
- CARTRIDGES, etc.

All with Terrific Savings

It will PAY YOU to pay us a VISIT!

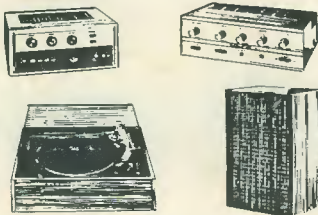


COMPLETE SYSTEMS from £46—Saves £12.10.0!
Send for new 8-page illustrated Hi-Fi list 16/17.

Fully Illustrated CATALOGUE

COMPLETELY NEW 9th EDITION (1969)
The most COMPREHENSIVE—CONCISE—CLEAR COMPONENTS CATALOGUE

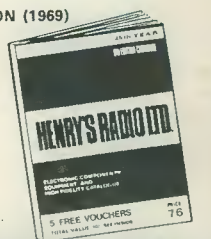Complete with 10/- worth discount vouchers
FREE WITH EVERY COPY
* 32 pages of transistors and semi-conductor devices, valves and crystals.
* 210 pages of components and equipment.
* 70 pages of microphones, decks and Hi-Fi equipment.



6,500 ITEMS
320 BIG PAGES
Send today 7'6 Post etc 2/-

HENRY'S RADIO LTD



OPEN MON.-SAT. 9 a.m.-6 p.m. THURS. 9 a.m.-1 p.m.

303 Edgware Road, London, W.2. Mail Order Dept. all types of Components, Organ Dept. (01) 723-1008/9
309 Edgware Road, London, W.2. High Fidelity Sales, P.A. and Test Equipment, Record Decks (01) 723-6963