

RADIO & ELECTRONICS CONSTRUCTOR

JANUARY 1977

35p



SIMPLE REGENERATIVE SW RADIO

CMOS
voltmeter




ALSO
FEATURED

THE '6-9' GAME

NOEL M. MORRIS

**SEMICONDUCTOR
DEVICES**

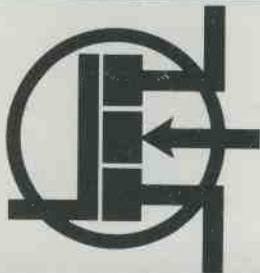

MACMILLAN BASIS BOOKS IN ELECTRONICS

**ANOTHER
SPECIAL
OFFER**

For a limited period

By arrangement with Messrs. MacMillan we are able to offer the above book at a special low price to readers of RADIO & ELECTRONICS CONSTRUCTOR.

Normal Price£4.35

SPECIAL OFFER PRICE £3.50

Saving 85p

Both prices include postage and packing

In this introduction to semiconductor devices, the author provides a comprehensive survey of modern active and non-active semiconductor technology. Without leaning too heavily on device physics, he explains device functions and then illustrates their use with typical circuits and applications.

Following a summary of the physical basis of semiconductor elements — in non-mathematical terms — a study of bipolar and field-effect transistors leads to considerations of monolithic integrated circuits. More advanced charge-coupled devices, semiconductor memories, and optoelectronic devices are studied in some detail.

CONTENTS

1. Semiconductors
2. Basic Semiconductor Devices
3. Semiconductor Diodes and the Unijunction Transistor
4. Bipolar Junction Transistors, Amplifiers & Logic Gates
5. Field-Effect Transistors, Amplifiers and Logic Gates
6. Monolithic Integrated Circuits
7. Charge-coupled Devices
8. Semiconductor Memories
9. Thyristors and other Multilayer Devices
10. Optoelectronics

To: Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please send me within 21 days copy/copies of

SEMICONDUCTOR DEVICES

I enclose Postal Order/Cheque for £.....

Name

Address

(Block Letters Please)

(We regret this offer is only available to readers in the U.K.)

RADIO & ELECTRONICS CONSTRUCTOR

JANUARY 1977
Volume 30 No. 6

Published Monthly (1st of Month)
First Published 1947

Incorporating The Radio Amateur

Editorial and Advertising Offices
57 MAIDA VALE LONDON W9 1SN

Telephone 01-286 6141 Telegrams
Databux, London

© Data Publications Ltd., 1977. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription: £5.50 (U.S.A. and Canada \$11.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers please pay by cheque or International Money Order.

Technical Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that such queries cannot be answered over the telephone; they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

Production.—Web Offset.

CMOS VOLTMETER by R. A. Penfold	334
T.T.L. SEQUENTIAL SWITCH (Suggested Circuit 314) by G. A. French	340
COURSE REVIEW	342
RELAY MULTIVIBRATOR by D. W. Savage	343
NEWS AND COMMENT	344
THE '6-9' GAME by R. J. Caborn	346
EXPERIMENTAL AERIAL TUNING UNIT by Henry Hatch	349
SIMPLE REGENERATIVE S.W. RADIO by A. P. Roberts	352
KIT REVIEW	358
SHORT WAVE NEWS — for DX Listeners by Frank A. Baldwin	359
THE OSCAR SATELLITE PROGRAMME The Future — by Arthur C. Gee	361
CURRENT MIRROR by M. G. Robertson	362
MEDIUM WAVE DX SUPERHET — Part 2 by R. A. Penfold	364
TRADE NEWS	369
IN YOUR WORKSHOP A.M. Mixer — Oscillator Stage	370
RADIO TOPICS by Recorder	375
ELECTRONICS DATA No. 18 (For the Beginner — Moving-Coil Voltmeters)	iii

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London W9 1SN

The *Radio & Electronics Constructor* is printed by Swale Press Ltd.

THE FEBRUARY ISSUE WILL BE
PUBLISHED ON 1st FEBRUARY



WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 25, 3, 8 or 15 ohms
 Baker Group 35, 3, 8 or 15 ohms
 Baker Group 50/12 8 or 15 ohms
 Baker Group 50/15 8 or 15 ohms
 Baker Deluxe 12" 8 or 15 ohms
 Baker Major 3, 8 or 15 ohms
 Baker Superb 8 or 15 ohms
 Baker Regent 12" 8 or 15 ohms
 Baker Auditorium 12" 8 or 15 ohms
 Baker Auditorium 15" 8 or 15 ohms

Castle BRS/DD 4/8 ohms
 Celestion G12M 8 or 15 ohms
 Celestion G12H 8 or 15 ohms
 Celestion G12/50 8 or 15 ohms
 Celestion G12/50TC 8 or 15 ohms
 Celestion G15C 8 or 15 ohms
 Celestion G18C 8 or 15 ohms
 Celestion HF1300 8 or 15 ohms
 Celestion HF2000 8 ohms
 Celestion MH1000 8 or 15 ohms
 Coles 4001 Gek
 Decca London ribbon horn
 Decca London CO/1000/8 Xover
 Decca DK30 ribbon horn
 Decca CO/1/8 Xover (DK30)

EMI 14 x 9 Bass 8 ohms 14A770
 EMI 8 x 5, 10 watt, d/cone, roll surr.
 EMI 6 1/2" d/cone, roll surr. 8 ohms
 Elac 59RM109 (15) 59RM114 (8)
 Elac 6 1/2" d/cone, roll surr. 8 ohms
 Elac 10" 10RM239 8 ohms
 Eagle FR4
 Eagle FR65
 Eagle FR8
 Eagle FR10
 Eagle HT15
 Eagle HT21
 Eagle MHT10
 Eagle FF28 multicell. horn

Fane Pop 15, 8 or 16 ohms
 Fane Pop 33T, 8 or 16 ohms
 Fane Pop 50, 8 or 16 ohms
 Fane Pop 55, 8 or 16 ohms
 Fane Pop 60, 8 or 16 ohms
 Fane Pop 70, 8 or 16 ohms
 Fane Pop 100, 8 or 16 ohms
 Fane Crescendo 12A, 8 or 16 ohms
 Fane Crescendo 12BL, 8 or 16 ohms
 Fane Crescendo 15/100A, 8 or 16 ohms
 Fane Crescendo 15/125, 8 or 16 ohms

SPEAKERS

£13.00 Fane Crescendo 18, 8 or 16 ohms
 £14.50 Fane 910 Mk.II horn
 £14.00 Fane 920 Mk.II horn
 £18.62 Fane HPX1 crossover 200 watt
 £17.50 Fane 13 x 8, 15 watt dual cone
 £15.00 Fane 801T 8" d/c, roll surr.
 £22.50 Goodmans Axent 100
 Goodmans Audiom 200 8 ohms
 Goodmans Axiom 402 8 or 15 ohms
 Goodmans Twinaxiom 8, 8 or 15 ohms
 Goodmans 8P 8 or 15 ohms
 Goodmans 10P 8 or 15 ohms
 Goodmans 12P 8 or 15 ohms
 Goodmans 12PG 8 or 15 ohms
 Goodmans 12PD 8 or 15 ohms
 Goodmans 12AX 8 or 15 ohms
 Goodmans 15AX 8 or 15 ohms
 Goodmans 15P 8 or 15 ohms
 Goodmans 18P 8 or 15 ohms
 Goodmans Hifax 750P
 Goodmans 5" midrange 8 ohms
 Gauss 12"
 Gauss 15"
 Gauss 18"

£9.28 Jordan Watts Module, 4, 8 or 15 ohms
 £12.95 Kef T27
 £15.95 Kef T15
 £18.00 Kef B110
 £20.00 Kef B200
 £26.95 Kef B139
 £39.95 Kef DN8
 £6.98 Kef DN12
 £8.55 Kef DN13 SP1015 or SP1017
 £13.50 Lowther PM6
 £5.90 Lowther PM6 Mk.I
 £29.95 Lowther PM7
 £6.95 Peerless KO10DT 4 or 8 ohms
 £19.95 Peerless DT10HFC 8 ohms
 £4.75 Peerless KO40MRF 8 ohms
 £19.95 Peerless MT225HFC 8 ohms
 £4.75 Richard Allan CA12 12" bass
 £5.11 Richard Allan HP8B
 £8.95 Richard Allan LP8B
 £11.95 Richard Allan DT20
 £14.06 Richard Allan CN8280
 £3.96 Richard Allan CN820
 £4.95 Richard Allan Super Disco 60W 12"
 £4.00 Coles 4001 G&K
 £5.95 Tannoy 10" Monitor HPD
 £4.95 Tannoy 12" Monitor HPD
 £5.95 Tannoy 15" Monitor HPD
 £6.95 Wharfedale Super 10 RS/DD 8 ohms

SPEAKER KITS

£75.95 Baker Major Module 3, 8 or 15 ohms each £13.50
 £15.75 Goodmans DIN 20 4 or 8 ohms each £15.75
 £45.95 Goodmans Mezzo Twin kit pair £51.95
 £2.50 Helme XLK 20 pair £17.50
 £5.50 Helme XLK 30 pair £21.95
 £8.96 Helme XLK 35 pair £26.75
 £8.50 Helme XLK 40 pair £38.50
 £14.95 KEFkit I pair £53.50
 £22.00 KEFkit III each £49.00
 £10.60 Peerless 1060 pair £54.00
 £6.50 Peerless 1070 each £46.50
 £6.95 Peerless 1120 each £54.00
 £16.50 Peerless 2050 pair £39.50
 £17.75 Peerless 2060 pair £53.00
 £18.75 Richard Allan Twin assembly each £13.95
 £44.00 Richard Allan Triple 8 each £20.75
 £49.00 Richard Allan Triple 12 each £25.95
 £24.00 Richard Allan Super Triple each £29.50
 £39.95 Richard Allan RAB Kit pair £37.80
 £16.00 Richard Allan RA82 Kit pair £59.40
 £4.05 Richard Allan RA82L Kit pair 85 70
 £95.00 Wharfedale Glendale 3XP Kit pair £49.50
 £110.00 Denton 2XP Kit pair £23.25
 £121.00 Wharfedale Linton 3XP Kit pair £34.25

HI-FI ON DEMONSTRATION

In our showrooms:
 Akai, Armstrong, Bowers & Wilkins, Castle, Celestion, Dual, Goodmans, Kef, Leak, Pioneer, Radford, Richard Allan, Rotel, Tandberg, Trio, Videotone, Wharfedale, etc.
 —Ask for our HiFi price list—

THIS MONTH'S SPECIALS (Carr. £2.00)

ROTEL RA 412 £77.95
 ROTEL RX 202 Mk. II £97.50
 VIDEOTONE MINIMAX II £43.00
 VIDEOTONE SAPHIR II £49.00
 PIONEER SX 450 £116.00
 SANSUI SC 2000/2002 £149.70

We stock the complete Radford range of amplifiers, preamplifiers, power amplifiers, tuners etc., and also Radford Audio Laboratory equipment, low distortion oscillator, distortion measuring set, audio noise meter etc.

ALL PRICES INCLUDE VAT

(Prices correct at 16/12/76)

Send stamp for free 38-page booklet "Choosing a Speaker"

All units guaranteed new and perfect

Carriage and insurance

Speakers up to 12" 60p; 12" £1.00; 15" £1.75; 18" £2.50; Kits £1.00 each (£2.00 per pair); Tweeters & Crossovers 33p each.

WILMSLOW AUDIO

DEPT REC

LOUDSPEAKERS, MAIL ORDER AND EXPORT;
 SWAN WORKS, BANK SQUARE, WILMSLOW
 HIFI, RADIO & TV: SWIFT OF WILMSLOW, 5
 SWAN STREET, WILMSLOW CHESHIRE
 PA, HIFI & ACCESSORIES: WILMSLOW
 AUDIO, 10 SWAN STREET, WILMSLOW
 CHESHIRE

TELEPHONE: LOUDSPEAKERS, MAIL ORDER
 AND EXPORT WILMSLOW 29599
 HIFI, RADIO ETC., WILMSLOW 26213

Access & Barclaycard Orders
 accepted by phone

COMPLETE KITS IN STOCK FOR

**RADFORD STUDIO 90, RADFORD MONITOR 180,
 RADFORD STUDIO 270, RADFORD STUDIO 360,
 HIFI ANSWERS MONITOR (Rogers), HIFI NEWS NO
 COMPROMISE (Frisby), HI FI NEWS STATE OF THE
 ART, WIRELESS WORLD TRANSMISSION LINE
 (Bailey), PRACTICAL HIFI & AUDIO MONITOR (Giles),
 PRACTICAL HIFI & AUDIO TRIANGLE (Giles),
 POPULAR HIFI (Colloms) ETC.**

**On Dem. Answers Monitor, State of Art, etc.
 Construction leaflets for Radford, Kef, Jordan Watts,
 Tannoy, HiFi Answers Monitor, Free on request**


**PA Amplifiers, microphones etc. by
 Linear, Shure, Eagle, Bayer, AKG etc.
 FREE with orders over £10**

"Hi-Fi Loudspeaker Enclosures" Book



Announcement

Electronic
Construction
Kits for 1976/77

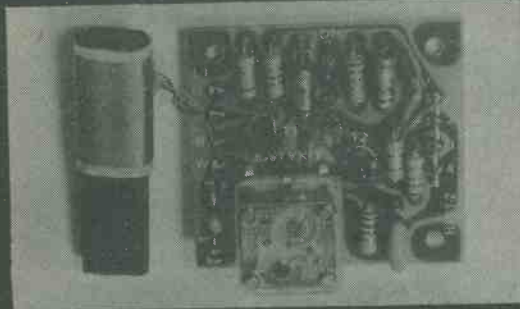

		£
AF 25	Mixer	2 50
AF 30	Pre-amplifier	2 30
AF 300	3 Watt audio amplifier	6 10
AF 310-3	Power amplifier	5 90
AF 340	40 watt AF power amplifier	8 95
AF 380	2 Watt IC universal amplifier	3 25
AT 5	Automatic light control	3 10
AT 30	Photo-cell amplifier	5 25
AT 50	Triac AC regulator up to 440W	3 70
AT 56	Triac AC regulator up to 2200W	5 55
AT 320	All-round AC/DC regulator	10 75
AT 325	Interval and flasher unit	7 20
AT 347	Electronic Roulette	8 75
AT 365	Light show	17 00
AT 405	Low-cost light/heat control	2 75
AT 460	Monolite	10 80
AT 465	Supersite	17 10
AT 466	Strobolite	20 45
AT 468	Quadrolite	19 45
GP 304	Main circuit unit	4 55
GP 310	Hi-Fi pre-amplifier	24 60
GP 340	Hi-Fi pre-amplifier	29 10
GU 330	Guitar tremolo	5 65
HF 61	Diode medium wave receiver	4 30
HF 65	FM transmitter/Signal Test Generator	2 50
HF 305	Amateur band 2 metre VHF 144 MHz converter	6 70
HF 310	FM tuner	11 50
HF 325 2	FM tuner module	19 85
HF 330	Stereo decoder	6 70
HF 375	Mini FM receiver	2 95
HF 385	VHF/UHF aerial amplifier	5 80
HF 395	Aerial amplifier AM-FM	1 50
LF 380	4d-stereo	8 45
MI 310	Stereo VU module	4 30
MI 350	S-meter module/amplifier	2 95
MI 360	Multivibrator/signal generator	1 40
MI 390	Dist module (meter not included)	2 55
MI 391	VU module (meter not included)	1 60
MI 392	Balance module (meter not included)	2 10
MI 393	Tuning module (meter not included)	2 60
MI 402	Semi-conductor tester for diodes/transistors	4 50
NT 300	Power pack (transformer not included)	10 15
NT 305	Voltage converter	4 40
NT 311	Voltage converter	2 80
NT 215	Power pack	8 75
NT 330	Power pack	4 70
NT 400	Power Supply (transformer not included)	17 15
NT 410	Power supply	4 50
NT 415	Power supply (transformer not included)	8 45

Please enclose 25p for p & p with order.

Send for free Catalogue to:
JOSTYKIT (UK) LTD., Mail Order Division
P.O. Box 68, Middlesbrough,
Cleveland, TS1 5DG

NAME.....

ADDRESS.....



"I MADE IT MYSELF"

Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.

Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn - and pave the way to a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio... a Burglar Alarm. You learn Radio and Electronics by doing actual projects you enjoy - making things, with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

No soldering - yet you learn faster than you ever dreamed possible.

Yes! Faster than you can imagine, you pick up the technical know how you need. Specially prepared step-by-step lessons show you how to read circuits - assemble components - build things - experiment. You enjoy every minute of it!

You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course. **AT NO EXTRA CHARGE!** And this is a course anyone can afford. (You can even pay for it by easy instalments).

So fast, so easy, this personalised course will teach you even if you don't know a thing today!

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics.

You become somebody who makes things, not just another of the millions, who don't understand. And you could pave the way to a great new career, to add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own transistor radio. And after the course you can go on to acquire highpowered technical qualifications, because our famous courses go right up to City & Guilds levels.

Send now for **FREE** 44-page book - see how easy it is - read what others say!

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

POST TODAY FOR FREE BOOK

To: ALDERMASTON COLLEGE
DEPT. Cr 25, READING RG7 4PF

CRE 25

Also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London, EC2Y 6EJ Tel: 01-628 2721. Yes, I'd like to know more about your course. Please send me free details - plus your big, 44-page book that tells about all your courses.

NAME.....

ADDRESS.....

POSTCODE.....



HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

BI-PAK

High quality modules
for stereo, mono and
other audio equipment




OUR PRICE
£20.45

The 450 Tuner provides instant program selection at the touch of a button ensuring accurate tuning of 4 pre-selected stations, any of which may be altered as often as you choose, by simply changing the settings of the pre-set controls.

Used with your existing audio equipment or with the BI-KITS STEREO 30 or the MK60 Kit etc. Alternatively the PS12 can be used if no suitable supply is available, together with the Transformer T461.

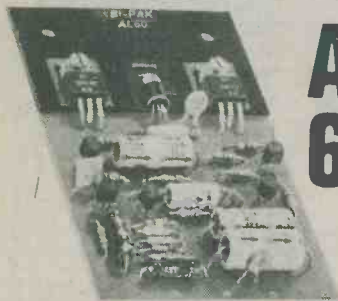The S450 is supplied fully built, tested and aligned. The unit is easily installed using the simple instructions supplied.



AL
60

VAT
ADD
12½%

25 Watts (RMS)

- Max Heat Sink temp 90C. ● Frequency response 20Hz to 100kHz ● Distortion better than 0.1 at 1kHz ● Supply voltage 15-50v. ● Thermal Feedback ● Latest Design Improvements
- Load - 3, 4, 5 or 16ohms. ● Signal to noise ratio 80db ● Overall size 63mm. 105mm. 13mm.

Especially designed to a strict specification. Only the finest components have been used and the latest solid-state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.

£4.35

Stabilised Power Supply Type SPM80

SPM80 is especially designed to power 2 of the AL60 Amplifiers, up to 15 watts (r.m.s.) per channel simultaneously. With the addition of the Mains Transformer BMT80, the unit will provide outputs of up to 1.5A at 35V. Size: 63mm. 105mm. 30mm. Incorporating short circuit protection.

Input Voltage: 33-40 V.A.C.

Output Voltage: 33V D.C. Nominal

Output Current: 10mA-1.5 amps

Overload Current: 1.7 amps approx.

Dimensions:

105mm x 63mm x 30mm

Transformer BMT80:

£2.60 + 62p postage

£3.75

NEW PUSH-BUTTON STEREO FM TUNER

Fitted with Phase Lock-loop Decoder

- ☆ FET Input Stage
- ☆ VARI-CAP diode tuning
- ☆ Switched AFC
- ☆ Multi turn pre-sets
- ☆ LED Stereo Indicator

Typical Specification:
Sensitivity 3µ volts
Stereo separation 30db
Supply required 20-30v
at 90 Ma max.

STEREO PRE-AMPLIFIER PA 100



3. Magnetic P.U. 3mV into 50K ohms
- P.U. Input equalises to R1AA curve within 1dB from 20Hz to 20KHz. Supply - 20 - 35V at 20mA.

Dimensions:
299mm x 89mm x 35mm

A top quality stereo pre-amplifier and tone control unit. The six push-button selector switch provides a choice of inputs together with two really effective filters for high and low frequencies, plus tape output.

Frequency response + \pm dB
20Hz-20KHz

Sensitivity of inputs:

1. Tape Input 100mV into 100K ohms
2. Radio Tuner 100mV into 100K ohms


£13.75

P.&P. 45p

MK60 AUDIO KIT: Comprising: 2 x AL60. 1 x SPM80. 1 x PA100. 1 front panel and knobs. 1 Kit of parts to include on/off switch, neon indicator, stereo headphone sockets plus instruction booklet. COMPLETE PRICE £29.55 plus 82p postage.

TEAK 60 AUDIO KIT: Comprising: Teak veneered cabinet size 16½" x 11½" x 3½", other parts include aluminium chassis, heatsink and front panel bracket plus back panel and appropriate sockets etc. KIT PRICE £10.70 plus 82p postage.

STEREO 30 COMPLETE AUDIO CHASSIS

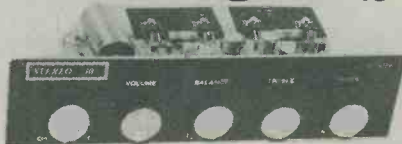

7+7 WATTS R.M.S.

The Stereo 30 comprises a complete stereo pre-amplifier, power amplifiers and power supply. This, with only the addition of a transformer wide range of inputs i.e. high quality ceramic pick-up, stereo tuner, stereo results, this unit is supplied with full instructions, black front panel, knobs, mains switch, fuse and fuse holder and universal mounting brackets struction or the cabinet available. Ideal for the beginner or the advanced constructor who requires Hi-Fi performance with a minimum of installation difficulty (can be installed in 30 minutes).

TRANSFORMER £2.45

plus 62p p&p

TEAK CASE £5.25 plus 62p p&p

£16.25

.p. & p. 45p

BI-PAK

PO BOX 6
WARE HERTS

SEMICONDUCTORS

POSTAGE & PACKAGE
Please add 25p. Overseas
add extra for airmail
Minimum order £1.

SECOND GREAT WINTER SALE!



VAT
Add 8%
Add 12% to
items
marked*

74 SERIES TTL IC's

Type	Quantity 1 100 £ p £ p	Type	Quantity 1 100 £ p £ p	Type	Quantity 1 100 £ p £ p
7400	0.09 0.08	7448	0.70 0.68	74122	0.45 0.42
7401	0.11 0.10	7450	0.12 0.10	74123	0.65 0.62
7402	0.11 0.10	7451	0.12 0.10	74141	0.68 0.65
7403	0.11 0.10	7453	0.12 0.10	74145	0.75 0.72
7404	0.11 0.10	7454	0.12 0.10	74150	1.10 1.05
7405	0.11 0.10	7460	0.12 0.10	74151	0.65 0.60
7406	0.28 0.25	7470	0.24 0.23	74153	0.70 0.68
7407	0.28 0.25	7472	0.20 0.19	74154	1.20 1.10
7408	0.12 0.11	7473	0.26 0.22	74155	0.70 0.68
7409	0.12 0.11	7474	0.24 0.23	74156	0.70 0.68
7410	0.09 0.08	7475	0.44 0.40	74157	0.70 0.68
7411	0.22 0.20	7476	0.26 0.25	74160	0.95 0.85
7412	0.22 0.20	7480	0.45 0.42	74161	0.95 0.85
7413	0.26 0.25	7481	0.90 0.88	74162	0.95 0.85
7416	0.28 0.25	7482	0.75 0.73	74163	0.95 0.85
7417	0.26 0.25	7483	0.88 0.82	74164	1.20 1.10
7420	0.11 0.10	7484	0.85 0.80	74165	1.20 1.10
7422	0.19 0.18	7485	1.10 1.00	74166	1.20 1.10
7423	0.21 0.20	7486	0.28 0.26	74174	1.10 1.00
7425	0.25 0.23	7489	2.70 2.50	74175	0.85 0.82
7426	0.25 0.23	7490	0.38 0.32	74176	1.10 1.00
7427	0.25 0.23	7491	0.65 0.62	74177	1.10 1.00
7428	0.36 0.34	7492	0.43 0.35	74180	1.10 1.00
7430	0.12 0.10	7493	0.38 0.35	74181	1.90 1.80
7432	0.20 0.19	7494	0.70 0.68	74182	0.80 0.78
7433	0.38 0.36	7495	0.60 0.58	74184	1.50 1.40
7437	0.26 0.25	7496	0.70 0.68	74190	1.40 1.30
7438	0.26 0.25	74100	0.95 0.90	74191	1.40 1.30
7440	0.12 0.10	74104	0.40 0.35	74192	1.10 1.00
7441	0.60 0.57	74105	0.30 0.25	74193	1.05 1.00
7442	0.60 0.52	74107	0.30 0.25	74194	1.05 1.00
7443	0.95 0.90	74110	0.48 0.45	74195	0.80 0.75
7444	0.95 0.90	74111	0.75 0.72	74196	0.90 0.85
7445	0.80 0.75	74118	0.85 0.82	74197	0.90 0.85
7446	0.80 0.75	74119	1.30 1.20	74198	1.90 1.80
7447	0.70 0.68	74121	0.28 0.26	74199	1.80 1.70

Devices may be mixed to qualify for quantity price. Data is available for the above series of IC's in booklet form
Price 35p

LINEAR IC's

TBA 800	*75p
72709 14 pin DIL	*20p
741P 8 pin DIL	*18p
72747 14 pin DIL	*36p
748P 8 pin DIL	*25p
NE 555 Timer	38p
NE 556 Dual Timer	78p

IC SOCKETS

BPS 8 8 pin	1611 9p
BPS 14 14 pin	161210p
BPS 16 16 pin	161311p

TRIACS

2A/400 T05	Price
Order No.	50p
TR12A/400	Price
10A/400 Plastic	80p
Order No.	80p
TR110A/400P	

ZENER PAKS

400mW	
PAK No:	
1 containing 20 3v-10v	
2 containing 20 11v-33v	
£1.00 PER PAK*	

DIACS

BR100	15p
D32	15p

CAPACITOR PAKS

16201 18 Electrolytics 47 µF-10 µF	
16202 18 Electrolytics 10 µF-100µF	
16203 18 Electrolytics 100µF-680µF	

BUY ONE OF EACH
Special Price £1.20* the 3

16160 24 Ceramic Caps 22pf-82pf	
16181 24 Ceramic Caps 100pf-390pf	
16162 24 Ceramic Caps 470pf-3300pf	
16163 21 Ceramic Caps 4700pf-0.047µF	

BUY OF OF EACH
Special Price £1.60* the 4

RESISTOR PAKS

16213 1/8th 100ohm-820ohm	
16214 1/8th 1K-8 2K	
16215 1/8th 10K-8 2K	
16216 1/8th 100L-1M	

BUY ONE OF EACH
Special Price £1.60* the 4

TRANSISTORS

AC128	10p	OC44	12p
AC153K	18p	OC45	12p
AC176	19p	OC71	9p
AC176K	22p	OC72	14p
AC187K	22p	OC81	14p
AC188	12p	ZTX107	* 6p
AC188K	22p	ZTX108	* 6p
BC107	6p	ZTX109	* 6p
BC108	6p	ZTX300	* 7p
BC109	6p	ZTX301	* 7p
BC118	*10p	ZTX302	* 9p
BC154	*16p	ZTX500	* 8p
BC147	* 8p	ZTX501	*10p
BC148	* 8p	ZTX502	*12p
BC149	* 8p	2N696	10p
BC157	*10p	2N697	11p
BC158	*10p	2N706	7p
BC159	*10p	2N706A	8p
BC169C	*10p	2N708	8p
BC170	* 6p	2N1613	15p
BC171	* 6p	2N1711	15p
BC172	* 6p	2N1893	18p
BC178	12p	2N2217	18p
BC179	12p	2N2218	15p
BC182L & K	* 9p	2N2218A	18p
BC183	* 9p	2N2219	15p
BC184	* 9p	2N2219A	18p
BC212L & K	* 9p	2N2221	15p
BC213	*10p	2N2221A	16p
BC214	*10p	2N2222	15p
BC251	* 6p	2N2222A	16p
BC327	*12p	2N2369	12p
BC328	*12p	2N2369A	12p
BC337	*11p	2N2904	14p
BC338	*11p	2N2904A	15p
BF115	10p	2N2905	14p
BF167	10p	2N2905A	15p
BF173	10p	2N2906	12p
BF194	* 9p	2N2906A	14p
BF195	* 9p	2N2907	12p
BF196	*12p	2N2907A	13p
BF197	*12p	2N2926G	
BF198	*12p		* 8p
BF199	*12p	2N2926Y	
BF258	29p		* 7p
BF259	34p	2N3053	14p
BFX29	18p	2N3055	38p
BFX84	15p	2N3702	* 7p
BFX85	20p	2N3703	* 7p
BFX86	20p	2N3704	* 6p
BFY50	12p	2N3705	* 6p
BFY51	12p	2N3706	* 7p
BFY52	12p	2N3903	*11p
BFY53	12p	2N3904	*11p
		2N3905	*11p
		2N3906	*11p
		2N5172	* 9p

DIODES

OA47	5p	IN4004	6p
OA81	5p	IN4005	6p
OA85	6p	IN4006	7p
OA91	5p	IN4007	8p
OA200/		IN5400	11p
BAX13	5p	IN5401	12p
OA202/		IN5402	13p
BAX16	5p	IN5403	14p
IN914	4p	IN5404	15p
IN4148	4p	IN5405	16p
IN4001	3p	IN5406	17p
IN4002	4p	IN5407	18p
IN4003	5p	IN5408	20p

VOLTAGE REGULATORS

MVR 7805	85p
MVR 7812	85p
MVR 7815	85p

OPTOELECTRONICS

LED DISPLAYS	Order No.	Price
DL707 0.3"	1510	0.70
DL747 0.6"	1511	1.50

LED's	Order No.
TIL209 RED .125"	1501
FLV117 RED .2"	1504
5 of either 50p	

PHOTO DEVICES

	Order No.	Price
ORP12	1515	38p
OC71 PAK of 5	1520	£1

THYRISTORS

T05	Order No.	Price
1A/50 PIV	THY 1A/50	18p
1A/400 PIV	THY 1A/400	32p
1A/600 PIV	THY 1A/600	38p
T066	Order No.	Price
5A/50 PIV	THY 5A/50	25p
5A/400 PIV	THY 5A/400	40p
5A/600 PIV	THY 5A/600	50p
T048		
16A/50 PIV	THY 16A/50	40p
16A/400 PIV	THY 16A/400	60p

UNIUNION

UT46/TIS 43	18p
-------------	-----

F.E.T.

2N3819	15p
--------	-----

ORDERING

Please word your orders exactly as printed not forgetting to include our part number



D.I.Y. PRINTED CIRCUIT KIT

Contains 6 pieces copper laminate, box of etchant powder and measure, tweezers, marker pen, high quality pump drill, Stanley knife & blades, 6" metal rule. FULL easy to follow instructions.

SALE £5.50

THE MODERN BOOK CO

JUST PUBLISHED

NEW FIFTH EDITION

RADIO COMMUNICATION HANDBOOK

VOL. 1 — R.S.G.B.

PRICE £8.10

ELECTRONIC CALCULATOR USERS HANDBOOK
by M. H. Babani PRICE: £1.20

PROJECT PLANNING & BUILDING
by M. A. Colwell PRICE: £2.25

SIMPLE CIRCUIT BUILDING
by P. C. Graham PRICE: £2.25

PRACTICAL ELECTRONIC PROJECT BUILDING
by A. C. Ainslie PRICE: £2.25

TRANSISTOR POCKET BOOK
by R. G. Hibberd PRICE: £4.40

110 OPERATIONAL AMPLIFIER PROJECTS FOR THE HOME CONSTRUCTOR
by R. M. Marston PRICE: £2.75

STEREO F.M. RADIO HANDBOOK
by P. Harvey PRICE: £3.00

RADIO SERVICING PROBLEMS
by W. A. L. Smith PRICE: 85p

THE HANDBOOK OF ELECTRONIC TABLES
by M. Clifford PRICE: £1.70

TEST INSTRUMENTS FOR ELECTRONICS
by M. Clifford PRICE: £2.10

110 ELECTRONIC ALARM PROJECTS FOR THE HOME CONSTRUCTOR
by R. M. Marston PRICE: £3.20

THE CATHODE-RAY OSCILLOSCOPE & ITS USE
by G. N. Patchett PRICE: £4.00

PRINCIPLES OF TRANSISTOR CIRCUITS
by S. W. Amos PRICE: £4.45

COLOUR T.V. WITH PART. REF. TO THE PAL SYSTEM
by G. N. Patchett PRICE: £5.40

COLOUR T.V. PICTURE FAULTS
by K. J. Bohlman PRICE: £2.75

PRINCIPLES OF PAL COLOUR T.V. & RELATED SYSTEMS
by H. V. Sims PRICE: £2.50

THE OSCILLOSCOPE IN USE
by L. R. Sinclair PRICE: £2.80

ELECTRONICS & RADIO
by M. Nelkon PRICE: £3.10

ELECTRONIC SYSTEMS FOR RADIO, T.V. & ELECTRONICS MECHANICS
by R. Lewis PRICE: £3.45

PRICES INCLUDE POSTAGE

We have the Finest Selection of English and American Radio Books in the Country
19-21 PRAED STREET (Dept RC) LONDON W2 1NP
Telephone 01-723 4185

LATEST BOUND VOLUME No. 29



of
"Radio & Electronics
Constructor"

FOR YOUR LIBRARY

NOW AVAILABLE

PRICE £3.10 P&P 75p

Comprising
776 pages
Inc. index

AUGUST 1975
to JULY 1976

BOUND VOLUME No. 27 (August 1973 to July 1974)
BOUND VOLUME No. 28 (August 1974 to July 1975)

PRICE £2.40 p. & p. 75p
PRICE £2.75 p. & p. 75p

Limited number of these volumes still available

We regret all other volumes are now completely sold out.
Available only from

DATA PUBLICATIONS LTD., 57 MAIDA VALE, LONDON, W9 1SN

Stirling Sound

Q.V. MODULES FOR COST-CONSCIOUS CONSTRUCTORS

SS.1100—A NEW 100w POWER AMP AT AN UNBEATABLE PRICE

£9.45*


Full size heat sink £1.00

This newest addition to the Stirling Sound range of power amps delivers 100 watts R.M.S. into 4 ohms, using 70 volt power supply. Ruggedly constructed and ideal for P.A. and disco use, etc. With heatsink mounting bracket. Approx. 5½" x 3" x 1¼" (140 x 76 x 32 mm).



SS.140 40 watts r.m.s. into 4 ohms using 45V supply such as SS345. Ideal for small disco and P.A. 101 x 76 x 19mm (4" x 3" x ¾")
£3.95*

PRE-AMP CONTROL MODULES UNIT ONE

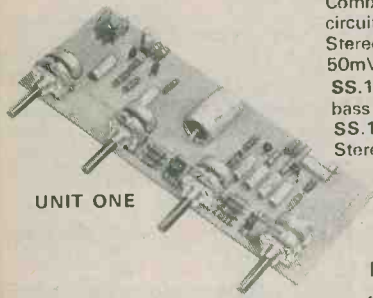

UNIT ONE

Combined pre-amp with active tone-control circuits. ±15dB at 10Khz treble and 30Hz bass. Stereo. Vol./balance/treble/bass. 200mV out for 50mV in. Takes 10-16V. **£7.80**

SS.100 Active tone control, stereo. ±15dB on bass and on treble **£1.60**

SS.101 Pre-amp for ceramic cartridges, etc. Stereo. Passive tone control details supplied. **£1.60**

SS.102 Stereo pre-amp for low output magnetic P.Us. R.I.A.A. corrected. **£2.65**

POWER AMPLIFIERS

SS.103 5 watt r.m.s. mono. I.C. short, **£1.75**

SS.103-3 Stereo version of above using two I.C.s **£3.75**

SS.105 5 watts r.m.s. into 4 ohms, using 12V **£2.25**

SS.110 10 watts r.m.s. using 24V and 4 ohm load **£2.75**

SS.120 20 watts r.m.s. into 4 ohms, using 34V **£3.25**


VAT on power units ordered with amplifiers SS.103-SS.120 becomes 12½%.

FM TUNING MODULES

SS.201 Front end tuner, slow geared drive, two gang. A.F.C. facility. Tunes 88-108 MHz **£5.00**

SS.202 I.F. amplifier. Metering and A.F.C. facilities **£2.65**

SS.203 Stereo Decoder for use with the above or other FM mono tuners. A LED may be fitted **£3.85**

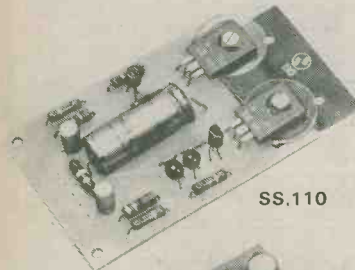

SS.110



SS.102

★ THE BUILT-IN QV FACTOR

means Stirling Sound's guarantee of **QUALITY AND VALUE** to give you today's best value all round.

Stirling Sound

A member of the Bi-Pre-Pak group


220-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SS0 9DF

Telephone Southend (0702) 46344

Personal callers welcome

TODAY'S BEST VALUE IN POWER SUPPLY UNITS

with 13-15V take-off points

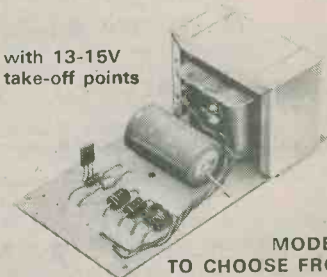

7 MODELS TO CHOOSE FROM

Complete with mains transformers and low volt take-off points (except SS.312). All at 8% V.A.T. rate. Add 50p for p/p any model.

SS.312	12V/1A	£3.75*
SS.318	18V/1A	£4.15*
SS.324	24V/1A	£4.60*
SS.334	34V/2A	£5.20*
SS.345	45V/2A	£6.25*
SS.350	50V/2A	£6.75*

SS.300 Power stabilising unit 10-50V adjustable for adding to unstabilised supplies. Built in protection against shorting (p/p 35p) **£3.25***



SS.300

Built-in protection against shorting

SS.310/50 Complete stabilised power supply with variable output from 10 to 50V/2A **£11.95***

WHEN ORDERING

add 35p for p/p unless stated otherwise. V.A.T. add 12½% to total value of order unless price is shown* when the rate is 8%. Make cheques, etc. payable to Bi-Pre-Pak Ltd. Every effort is made to ensure correctness of information at time of going to press. Prices subject to alteration without notice.

TRADE COMPONENTS

JUST A FEW BARGAINS ARE LISTED - SEND STAMPED ADDRESSED ENVELOPE FOR A QUOTE ON OTHER REQUIREMENTS. PAY A VISIT. OVER 90% OF STOCK BELOW QUANTITY WHOLESALE PRICE. RETURN POSTAL SERVICE UNLESS CHEQUE. ALL PRICES INCLUDE THE ADDITIONAL DISCOUNT IN LIEU OF GUARANTEE.

Goods sent at customer's risk, unless sufficient payment for registration (1st class letter post) or compensation fee (parcel post) included.

VALVE BASES

Printed circuit B9A-B7G	5p
Chassis B7-B7G	9p
Shrouded chassis B7G-B9A-B8A	10p
B12A tube	9p

Car type panel lock and key	40p
18 volt 4 amp charger, bridge rectifier	79p
GC10/4B	£3.00

Speaker 6" x 4" 5 ohm ideal for car radio £1.25

TAG STRIP - 6 way	3p	5 x 50pF or 2 x 220pF trimmers	20p
9 way	5p		

Telescopic aerial	
Closed 9½", open 38½"	
Fitted right angle TV plug,	50p

BOXES - Grey polystyrene 61 x 112 x 31mm, top secured by 4 self tapping screws 32½p

Clear perspex sliding lid, 46 x 39 x 24mm 10p

ABS, ribbed inside 5mm centres for P.C.B., brass corner inserts, screw down lid, 50 x 100 x 25mm orange 48p; 80 x 150 x 50mm black 70p; 109 x 185 x 60mm black £1.10

ALUMINIUM

3" x 2" x 1"	39p	4" x 2½" x 2"	44p	8" x 6" x 3"	£1.02
2½" x 5¼" x 1½"	45p	4" x 5¼" x 1½"	54p	10" x 4½" x 3"	£1.02
4" x 4" x 1½"	45p	6" x 4" x 2"	65p	12" x 5" x 3"	£1.20
4" x 2½" x 1½"	45p	7" x 5" x 2½"	79p	10" x 7" x 3"	£1.22
				12" x 8" x 3"	£1.50

SWITCHES

Pole	Way	Type	
4	2	Sub. Min. Slide	18p
6	2	Slide	20p
1	3	13 amp rotary	6p
2	2	Locking with 2 to 3 keys	£2.00

2 2 Amp 250V A.C. rotary 20p
Wafer Rotary, all types 30p

S.P.S.T. 10 amp 240v. white rocker switch with neon. 1" square flush panel fitting 20p
S.P.S.T. dot 13 amp, oblong, push-fit, rocker 15p

AUDIO LEADS

5 pin din plug 180° both ends 1½ Mtr.,	80p
3 pin din to open end, 1½ yd twin screened	35p
Phono to Phono plug, 6ft.	35p

COMPUTER AND AUDIO BOARDS

VARYING PANELS WITH ZENER, GOLD BOND, SILICON, GERMANIUM, LOW AND HIGH POWER TRANSISTORS AND DIODES, HI STAB RESISTORS, CAPACITORS, ELECTROLYTICS, TRIMPOTS, POT CORES, CHOKES ETC.

3lb for 85p + 85p post and packing
7lb for £1.95 + £1.20 post and packing

Skeleton Presets	3" Tape Spools	3p
Slider, horizontal or vertical standard or submin. 5p	1" Terry Clips	4p
	12 Volt Solenoid	30p

KNOBBS

SILVER METAL PUSH ON WITH POINTER, OR WHITE PLASTIC, GRUB SCREW WITH GOLD CENTRE 8p EACH

ENM Ltd. cased 7-digit counter 2½ x 1½ x 1¼" approx. 12V d.c. (48 a.c.) or mains 75p

ZM1162A INDICATOR TUBE

0-9 Inline End View. Rectangular Envelope 170V 2.5M/A £1

REGULATED TAPE MOTOR

9v d.c. nominal approx 1½" diameter 60p

12v 8 amp Transformer £2.50 (p&p 85p)
Ferric Chloride, Anhydrous mil. spec. 1lb bag 40p

RESISTORS

¼-¼ watt	1p
1 watt	2p
Up to 15 watt wire wound	6p
1 or 2% five times price.	

Cinch 8 way std 0.15 pitch edge connector 20p

Semiconductor Data Book 263 pages. Covers 2N21 through to 2N5558 plus some 3N's. Type/connection/parameter details £1.50
No VAT

POTS

Log or Lin carbon	16p
Switched	31p
Dual Pots	45p
Dual & switch	60p
Lin wirewound	25p
Slider Pot	35p
Dual Slider	50p
1.5m Edgetype	8p

THERMISTORS

VA1008, VA1034, VA1039, VA1040, VA1055, VA1066, VA1082, VA1100, VA1077, VA1005, VA1026	10p
	15p

RELAYS

12 volt S.P.C.O octal mercury wetted high speed	40p
P.O. 30J0 type, 1,000 OHM coil, 4 pole c/o	40p
Mains or 12v d.p.c.o heavy duty octal	50p

Boxed GEC KT88 valve £2

JAP 4 gang min. sealed tuning condensers New 20p

ELECTROLYTICS MFD/VOLT. Many others in stock

	70-	200-	300-	450-
Up to 10V	25V	50V	75V	100V
250V	350V	500V		
MFD				
10	4p	5p	6p	8p
12p	10p	12p	16p	20p
25	4p	5p	6p	8p
10p	15p	18p	20p	
50	4p	5p	6p	9p
13p	18p	25p		
100	5p	6p	10p	12p
19p	20p			
250	9p	10p	17p	28p
				85p
500	10p	11p	14p	45p
1000	13p	22p	40p	75p
				£1.50
2000	23p	37p	45p	

As total values are too numerous to list, use this price guide to work out your actual requirements

8/20, 10/20, 12/20 Tubular tantalum 20p each
16-32/275V, 100-100/150V, 100-100/275V 30p;
50-50/385V, 12,000/12V, 32-32-50/300V, 20-20-20/350V 60p; 700 mfd/200V £1.00; 100-100-100-150-150/320V £2.00.

RS 100-0-100 micro amp null indicator
Approx. 2" x ¾" x ¾" £1.50

INDICATORS

Bulgin D676 red, takes M.E.S. bulb	30p
12 volt or Mains neon, red pushfit	18p
R.S. Scale Print, pressure transfer sheet	5p

CAPACITOR GUIDE - maximum 500V

Up to .01 ceramic 3p. Up to .01 poly 4p.
.013 up to .1 poly etc. 5p. .12 up to .68 poly etc. 6p. Silver mica up to 360pF 8p, then to 2,200pF 11p, then to .01 mfd 18p.
8p. .1/600; 12p. .01/1000, 1/350, 8/20, .1/900, .22/900, 4/16, .25/250 AC (600VDC) 1/1500 .40p. 5/150, 9/275AC, 10/150, 40/150.

Many others and high voltage in stock.

FORDYCE DELAY UNIT

240 volt A.C./D.C. Will hold relay, etc., for approx. 15 secs after power off. Ideal for alarm circuits, etc. £1

CONNECTOR STRIP

Belling Lee L1469, 4 way polythene.	6p each
1½ glass fuses 250 mA or 3 amp (box of 12)	6p
Bulgin, 5mm Jack plug and switched socket (pair)	30p
Reed Switch 28mm. body length	5p

MAINS DROPPERS

36+79 ohm	5p
66+66+158 ohm, 66+66+137 ohm	
17+14+6 ohm, 266+14+193 ohm	5p
50+40+1k5 ohm	
285+575+148+35 ohm	5p
25+35+97+59+30 ohm	

5½" x 2½" Speaker, ex-equipment	3 ohm	30p
2 Amp Suppression Choke		8p
3 x 2½ x 1½"		4p
4½ x ½ x ½"		1p
PCV or metal clip on MES bulb Holder		4p
VALVE RETAINER CLIP, adjustable		2p

OUTPUT TRANSFORMERS

Sub-miniature Transistor Type	25p
Valve type,	40p

Transformers 6 volt ½A	25p
Whiteley Stentorian 3 ohm constant impedance volume control way below trade	80p
RS Yellow Wander Plug Box of 12	25p
18 SWG multicore solder	2½p foot

THE RADIO SHACK

161 ST. JOHNS HILL, BATTERSEA, LONDON S.W.11
Open 10 a.m. till 7 p.m. Tuesday to Saturday. VAT receipts on request.
Terms: Payment with order Telephone: 01-223 5016

SEMICONDUCTORS

Full spec. marked by Mullard, etc. Many other types in stock

AC107	16p	BC557/8/9	9p	BFW10/11 F.E.T.	40p
AC128/176	8p	BCX32 36	12p	BFW30	£1
ACY28	19p	BCY40	50p	BFW57/58	17p
AD149	40p	BCY70/1/2	12p	BFX12/29/30	20p
AF161/2	33p	BD112/3	50p	BFX84/88/89	17p
AF116	161p	BD115/6	31p	BFY51/52	13p
AF124/6/7	25p	BD131/2/3	35p	BFY90	50p
AF139	20p	BD135/7/9	30p	BR101	30p
AF178/80/81	30p	BD142	30p	BRV39/56	26p
AF239	30p	BD201/2/3/4	£0p	BSV64	30p
ASY27/73	30p	BD232/4/5	49p	BSV79/80 F.E.T.s	80p
BC107/B/9 + A/B/C	6p	BDX77	£1	BSV91 Mosfet	90p
BC147/8/9 + A/B/C/S	6p	BF115/167/173	15p	BSX20/21	14p
BC157/8/9 + A/B/C	6p	BF178/9	20p	BSY40	27p
BC178A/B, 179B	12p	BF180/1/2/3/4/5	15p	BSY95A	12p
BC184C/LC	9p	BF194/5/6/7	6p	BU105-01	50p
BC186/7	20p	BF194A, 195C	6p	CV7042 (OC41/44	5p
BC213L/214B	10p	BF200, 25B	20p	ASY63)	5p
BC261B	8p	BF202/3	30p	GET111	40p
BC327/8, 337/8	8p	BF336	27p	OC35	45p
BC547/8/8A	10p	BFS28 Dual Mosfet	£1	ON222	20p

2N2401	30p
2N2412	70p
2N2483	23p
2N2904/5/6/7/7A	15p
2N3053	14p
2N3055 R.C.A.	50p
2N3704	8p
2N3133	20p
2N4037	34p
2N5036 (Plastic 2N3055)	13p
2SA141/2/360	31p
2SB135/6/457	20p
40250 (2N3054)	30p

OTHER DIODES

1N916	6p
1N4148	2p
BA145	14p
Centercel	24p
BZY61/BA148	10p
BB103/110 Varicap	15p
BB113 Triple Varicap	37p
BA182	13p
OA57/710	15p
BZY88 Up to 33 volt	7p
BZX61 11 volt	15p
BR100 Diac	15p

BRIDGE RECTIFIERS

Amp	Volt		
1	1600	BYX10	30p
1	140	OSH01-200	26p
1.4	42	BY164	40p
0.6	110	EC433	6p
5	400	Texas	90p

OPTO ELECTRONICS

BPX40	50p	Photo transistor	
BPX42	80p	BPX29	80p
BPY10	80p	OCPT71	44p

(VOLIAC)

BPY68	80p	BIG L.E.D. 0.2"	
BPY69		2v 50mA max.	
BPY77		RED	10p
BPY79		ORANGE	17p
		GREEN	14p
		YELLOW	14p
		CLIP	2p

Diodes

TIL209 Red	10p
------------	-----

NEW B.V.A. VALVES

6B8W7	60p
EB91	34p
ECH81	34p
ECL80	36p
EF80	34p
EF183	34p
EY86/7	34p
PC86	53p
PC88	53p
PC97	36p
PCC84	34p
PCC89	45p
PCC189	45p
PCF80	34p
PCF82	34p
PCF801	46p
PCL82	34p
PL81	35p
PY500A	80p
PY81/800	38p
R20/U26	50p

INTEGRATED CIRCUITS

TAA700	£2.00
723 reg (TO99)	45p
741 8 pin d.i.l. op. Amp	20p
TAD100 AMRF	£1
CA3001 R.F. Amp	50p
CD4013 CMOS	36p
TAA300 1wt Amp	£1
NE555V Timer	35p
TAA550 Y or G	22p
TAA263 Amp	65p
7400/10	9p
7402/4/20/30	12p
7414	56p
7438/74/86	24p
7483	69p
LM300, 2-20 volt	£1
74154	90p

RECTIFIERS

Amp	Volt		
IN4004/5/6	1	4/6/800	5p
IN4007/BYX94	1	1250	5p
BY103	1	1,500	18½p
SR100	1.5	100	7p
SR400	1.5	400	8p
REC53A	1.5	1,250	14p
LT102	2	30	10p
BYX38-300R	2.5	300	40p
BYX38-600	2.5	600	45p
BYX38-900	2.5	900	60p
BYX38-1200	2.5	1,200	55p
BYX48-300R	2.5	300	26p
BYX49-600	2.5	600	35p
BYX49-900	2.5	900	40p
BYX49-1200	2.5	1,200	52p
BYX48-3U0R	6	300	40p
BYX48-600	6	600	50p
BYX48-900	6	900	60p
BYX48-1200R	6	1,200	80p
BYX72-150R	10	150	35p
BYX72-300R	10	300	45p
BYX72-500R	10	500	55p
BYX42-300	10	300	30p
BYX42-600	10	600	65p
BYX42-900	10	900	80p
BYX42-1200	10	1,200	95p
BYX46-300*	15	300	£1.00
BYX46-400*	15	400	£1.50
BYX46-500*	15	500	£1.75
BYX46-600*	15	600	£2.00
BYX20-200	25	200	60p
BYX52-300	40	300	£1.75
BYX52-1200	40	1,200	£2.50

PHOTO SILICON CONTROLLED SWITCH

BPX66 PNP	10 amp	£1.00
-----------	--------	-------

PAPER BLOCK CONDENSER

0.25MFD	800 volt	30p
1MFD	250 volt	15p
2MFD	250 volt	20p
4MFD	250 volt	20p

THRISTORS

1	240	BTX18-200	30p
1	400	BTX18-300	35p
1	240	BTX30-200	30p
15	500	BT107	£1
6.5	500	BT101-500R	90p
6.5	500	BT109-500R	£1.00
20	600	BTW92-600RM	£3.00
15	800	BTX95-800R Pulse Modulated	£8.00
30	1000	28T10 (Less Nut)	£3.00

*Avalanche type.

Amp	Volt	TRIACS	
6	800	Plastic RCA	£1.20
25	900	BTX94-900	£4.00
25	1200	BTX94-1200	£6.00

Mullard Data Book 40p

RS 2mm Terminals Blue & Black	5 for 40p
Chrome Car Radio fascia	15p
Rubber Car Radio gasket	5p
DLI Pal Delayline	50p
Relay socket	25p
Take miniature 2PCO relay	
B7G or B9A valve can	5p
0-30, or 0-15, black pvc, 360° dial, silver digits, self adhesive 4½" dia.	10p

COY11B L.E.D.

Infra red transmitter £1
One fifth of trade

I.C. extraction and insertion tool

3" red 7 segment L.E.D. 14
D.I.L. 0-9+D.P. display 1.9v
10mA segment, common anode 61p
DL747.6" £1.25
Minitron 3" 3015F filament £1.10

ENAM. COPPER WIRE SWG. PER YD.

20-24	3p
26-42	2.5p

TO3 HEATSINK

Europelec HP1 TO3B individual 'curly' power transistor type. Ready drilled 12p

CHASSIS SOCKETS

Car Aerial 9p, Coax 3p, 5 pin 180° 9p, 5 or 6 pin 240° din 6p, speaker din switched 5p, 3.5 mm switched 5p, stereo ½" jack enclosed 10p.

GARRARD

GCS23T Crystal Stereo Cartridge 66p
Mono (Stereo compatible), Ceramic or crystal 60p

Tested unmarked, or marked ample lead ex new equipment

ACY17-20	8p	OC71/2	5p
ASZ20	8p	OC200-5	8p
ASZ21	30p	TIC44	24p
BC186	11p	2G240	£1
BCY30-34	8p	2G302	5p
BCY70/1/2	8p	2G401	5p
BF115	10p	2N711	25p
BY126/7	4p	2N2926	4p
HG1005	10p	2N598/9	6p
HG5009	3p	2N1091	8p
HG5079	3p	2N1302	8p
L78/9	3p	2N1907	£1
M3	10p	Germ. diode 1p	
OA81	3p	GET120 (AC128 in 1" sq. heat sink)	15p
OA47	3p	GET872	12p
OA200-2	3p	2S3230	30p
OC23	20p		

CRAZY OFFERS

4700 mfd.	40v	35p
2500 mfd.	40v	3p
2200 mfd.	25v	30p
2200 mfd.	64v	40p
10000 mfd.	15v	12p
1250 mfd.	35v	10p
6800 mfd.	10v	6p
32+32 mfd.	275v	8p
16+32 mfd.	350v	12p
8+8 mfd.	350v	8p
150 mfd.	35v	4p
100 mfd.	70v	4½p
1 mfd. non-polar	350v	3p
680 mfd.	100v	10p
15 mfd.	160v	3p
4700 pf. sub min	500v	1½p
47 k. log stereo slide pot		12p
Philips electronic engineer kits add on series E1004		75p each

HANDLES

Rigid light blue nylon 6½" with secret fitting screws 5p

Belling Lee white plastic surface coax outlet box 20p

TIE CLIPS

Nylon self locking 7" or 3½" 2p

Geared Knob 8-1 ratio 1½" diam. black 70p

MINIATURE AXIAL LEAD FERRITE CHOKE FORMERS

RS 10 Turn Pot 1% 250, 500 Ω, 1K, 50K £1

Copper coated board 10" x 9" approx 25p

1lb Mixed bolts, nuts, washers etc.

45p


SMALL ORDERS, ENCLOSE SUITABLE STAMPED ADDRESSED ENVELOPE
LARGE ORDERS, ADD SUFFICIENT FOR POSTAGE, INSURANCE, ETC.
TOTAL GOODS PLUS CARRIAGE, ADD V.A.T.

MAIL ORDER CUSTOMERS ONLY ADD 8% VAT-I PAY BALANCE ON 12½% ITEMS.
ALL ENQUIRIES, ETC., MUST BE ACCOMPANIED BY A STAMPED ADDRESSED ENVELOPE



NEW STYLE SELF-BINDER

for
"Radio & Electronics
Constructor"

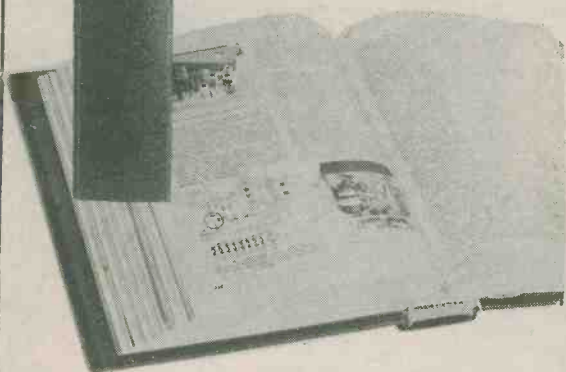

The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Rich maroon finish, gold lettering on spine.

Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

PRICE

£1.20

including V.A.T.

P. & P. 30p

Owing to heavy demand please allow 27 days for delivery.


Available only from:—

Data Publications Ltd.

57 Maida Vale London W9 1SN

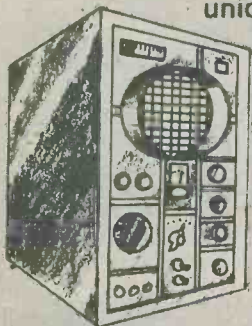1. Understand electronics.


Step by step, we take you through all the fundamentals of electronics and show you how easily the subject can be mastered using our unique Lerna-Kit course.



- (1) Build an oscilloscope.
- (2) Read, draw and understand circuit diagrams.
- (3) Carry out over 40 experiments on basic electronic circuits and see how they work.

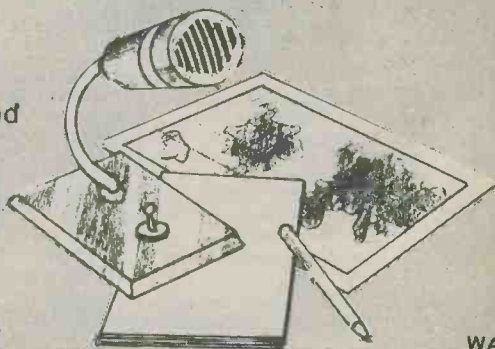2. Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.



Free!

Brochure, without obligation to:
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,
P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____

Block caps please

REK 17

WAA



Super 30 Kit shown with stand, flexible and transformer added

THE ABOVE KIT IS AVAILABLE AS SEPARATES

	£ p	p&p
● Kit Complete as above	33.48	1.15
● Mk.II Drill Stand	4.40	35
● Mk.II Drill Only	8.79	35
● Flexible Shaft.....	5.46	25
● Transformer	6.00	70
● S.30 Kit (Drill with 30 tools)	17.62	85

Postage for spares (any quantity) 15p

- Replacement accessories40p each
- Circular Saw Blade Sets (4)..... £2.00
- Spare Collets..... £0.40
- Spare Chuck & 3 Collets..... £2.50


ALL ABOVE PRICES INCLUDE V.A.T.

S.A.E. (9" x 4") FOR ILLUSTRATED LEAFLET & ORDER FORM

PRECISION PETITE LTD
119a High Street
Teddington, Middx.

Tel: 01-977 0878
(24hr. Tel: Enquiry Service)

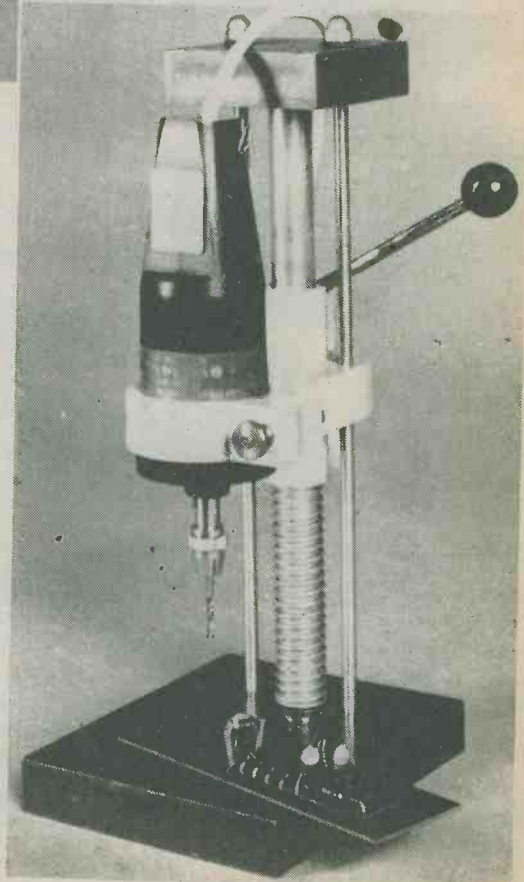Have pleasure in introducing their Precision Tools from France for all types of electronic design and development, professional or amateur.



RADIO & ELECTRONICS CONSTRUCTOR



UNDERSTAND DATA PROCESSING

DATA PROCESSING, by Oliver & Chapman, is now in its Third Edition — first published 1972.

200 pages 9 $\frac{3}{4}$ " x 6 $\frac{3}{4}$ " **PRICE £2.50**
Inclusive of postage

The primary aim of this outstanding manual is to provide a simplified approach to the understanding of data processing — (previous knowledge of the subject is not necessary).

The 40 chapters and appendices cover the following topics: Introduction to Data Processing; Organisation and Methods; Conventional Methods; Introduction to EDP and Computers; Hardware; Computer Files; Data Collection and Control; Programming and Software; Flowcharts and Decision Tables; Systems Analysis; Applications; Management of EDP, etc.

Available from:

D.P. PUBLICATIONS
 4 AMPORT CLOSE, WINCHESTER, HANTS SO22 6LP



Perhaps we can help you turn that old wish into reality

As all electronics constructors know, one of the secrets of happiness is to spend leisure time on work that is both interesting and constructive. Unfortunately, one's enjoyment of the hobby is soon spoilt if you can't

obtain the right components. That's where Home Radio Components come in, and if you're a regular reader of these advertisements you'll know exactly what we three 'typical customers' recommend. Here it is — the first step is to invest in a Home Radio Components catalogue. This will enable you to locate quickly and easily the parts you need for the project you have in mind. Then, to buy the components you have a choice of three methods. 1, You can visit Home Radio's shop in Mitcham, above Tesco's almost opposite Mitcham Baths. 2, You can send a cheque or P.O. for the items you need, in the normal Mail Order way. 3, You can join Home Radio's Credit Scheme and settle your account monthly. Full details of this popular scheme are given in the catalogue.

Whichever method you use, you will enjoy the prompt, personal service Home Radio always strive to give. So, back to the first step, send off the coupon with £1.40 for your copy of the catalogue — it's a superb production!

Please write your Name and Address in block capitals

NAME

ADDRESS

HOME RADIO (Components) LTD., Dept. RC
 234-240 London Road, Mitcham, Surrey CR4 3HD
 Regd No 912966 London



POST THIS COUPON
 with £1.40, cheque or P.O.

HOME RADIO (Components) LTD. Dept. RC, 234-240 London Road, Mitcham, CR4 3HD. Phone: 01-648 8422



CMOS

The introduction of the CMOS linear operational amplifier type CA3130T allows the construction of very simple circuits which take advantage of its extremely high input resistance. This article describes an electronic voltmeter incorporating the CA3130T and offering ranges of 0-1 volt, 0-5 volts, 0-10 volts and 0-50 volts.

There hardly seems to be an issue of an electronics magazine these days that does not give details of at least one project incorporating an operational amplifier i.e. of some sort or, at least, that is the author's impression. Operational amplifiers are certainly very versatile with their inverting and non-inverting inputs, ultra high gains, high input impedances and low output impedances.

Inexpensive devices such as the 741 and 748 do have limitations, however. Theoretically, an operational amplifier should have an infinite voltage gain, infinite input impedance and zero output impedance. No real operational amplifier achieves all these characteristics, of course, but most are suitable, with regard to gain and output impedance, for the majority of practical applications.

Devices such as the 741 and 748 have bipolar transistor input stages and, although very high input impedances can be attained, practical amplifiers tend to be well removed from the theoretical ideal in this respect. This is not a problem of academic importance, but is one that can complicate what would otherwise be a very simple circuit or can make a particular circuit completely impractical.

BASIC VOLTMETER

An example of a possible circuit which could not function adequately with an operational amplifier having a bipolar transistor input is shown in Fig. 1. This circuit is for an electronic voltmeter having a high input resistance. The output of the operational amplifier is returned to its inverting input, whereupon the amplifier acts as a voltage follower with its output voltage being equal to the input voltage. The meter and series resistor form a

voltmeter which can have a full-scale deflection of 1 volt. Voltages to be measured are applied to the test terminals, across which is an attenuator having four resistors. The switch taps into the attenuator to provide four voltage ranges.

A circuit of this type has several advantages over more conventional electronic voltmeters, such as those incorporating field-effect transistors. An electrical zero set adjustment for the meter is not required nor is there any need for thermal stabilization. Also, the linearity of the circuit is very nearly perfect,

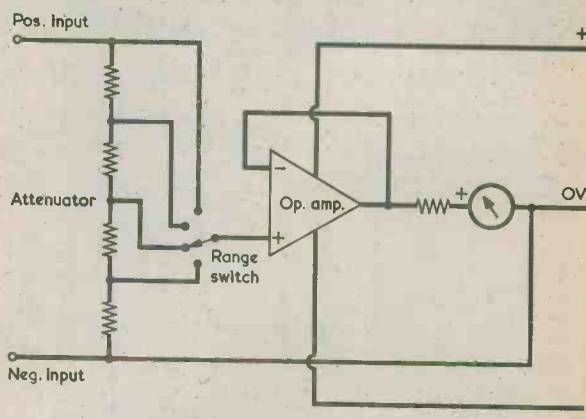


Fig. 1. Basic circuit for an electronic voltmeter. For satisfactory functioning the operational amplifier requires an extremely high input resistance

VOLT METER

By R. A. Penfold

and accuracy is virtually limited to the accuracy and resolution of the meter itself. The only obvious disadvantage is the necessity for a dual voltage power supply.

The circuit cannot be used successfully with an operational amplifier having a bipolar transistor input because the input resistance of such an amplifier, although high, is still too low to allow high value resistors to be employed in the attenuator. Satisfactory functioning calls for an operational amplifier having an input resistance of many hundreds, or preferably even thousands, of megohms. Suitable operational amplifiers have been available for some time but have been expensive. They incorporate a JUGFET input stage, but this is contained on a single chip separate from the main bipolar circuitry.

The situation has recently changed and it is now possible to obtain, at reasonable cost, an operational amplifier with a CMOS input, this being the RCA CA3130T. This i.c. has an extremely high input im-

pedance and readily lends itself to use in a circuit of the type shown in Fig. 1. This article describes an electronic voltmeter, incorporating the CA3130T, which has an input resistance of $15M\Omega$ on all ranges. There are four ranges, these being 0-1 volt, 0-5 volts, 0-10 volts and 0-50 volts. The unit can be assembled in very compact form.

The CA3130T is an 8-lead device contained in a TO-5 style package. Its lead connections and a block diagram showing its internal stages are illustrated in Fig. 2. The device has a typical voltage gain of 320,000 times, most of this being provided by the second stage, which incorporates a bipolar transistor. The input and output stages employ CMOS circuitry. Although of no consequence in the present application, the CA3130T has a gain-bandwidth product of 15MHz, a high slew rate of 30 volts per microsecond and is capable of a peak-to-peak output voltage swing which is only some millivolts inside the supply voltage.


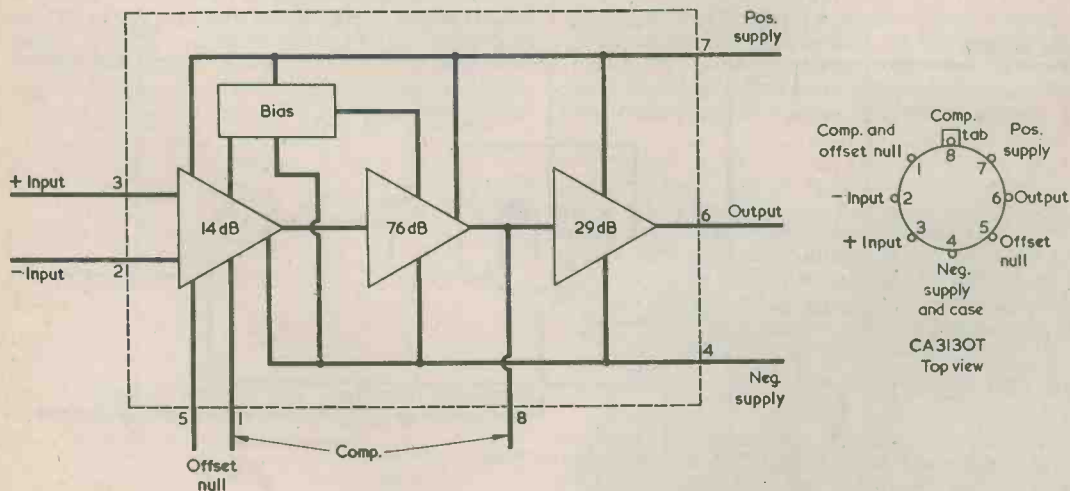


Fig. 2. Block diagram illustrating the internal stages of the CA3130T and a top view showing lead allocations

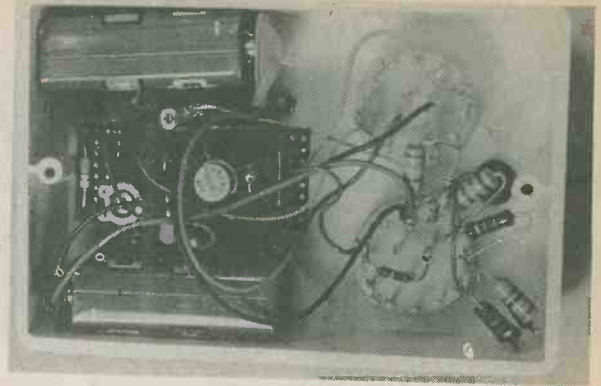The prototype has a simple layout, with the Veroboard panel located between the two meter terminals



THE CIRCUIT

The complete circuit of the CMOS voltmeter appears in Fig. 3. This is similar to the basic circuit of Fig. 1, with a few additions which are necessary for practical operation.

R1 to R7 form the input attenuator and the accuracy of the voltmeter depends upon the tolerance of the resistors employed here. The widest tolerance to be considered acceptable is 5%, and all the values listed are available in this tolerance from Electrovalue Limited. The first attenuator resistor requires a value of 12M Ω and it is unlikely that a suitable component will be available. The value is therefore made up by connecting four separate resistors in series. A 300k Ω resistor is needed for R7 and, in the prototype, this was made up of two 150k Ω resistors in series. S2 is the range switch.

The CA3130T has internal diodes to protect its input gates against breakdown voltages but it is still necessary to ensure that an excessive voltage cannot

be accidentally applied to the non-inverting input. In consequence current limiting resistor R8 is inserted in series with the non-inverting input, and it provides protection against overloads of up to 100 volts when the instrument is switched to 0-1 volt, on which range the i.c. is most vulnerable. The input resistance of the CA3130T is so high that R8 has no significant effect on normal circuit operation.

There is a 100% negative feedback loop from the output to the inverting input, causing the i.c. to have unity gain and thus act as a voltage follower. The i.c. does not have internal compensation, but only a single external compensating component is required. This is C1.

VR1 and R11 provide the series resistance for the meter. VR1 is set up so that the meter gives a full-scale reading at an output voltage, from the i.c., of 1 volt.

A supply voltage of between 3 and 16 volts can be used to power the CA3130T or, in the case of a dual

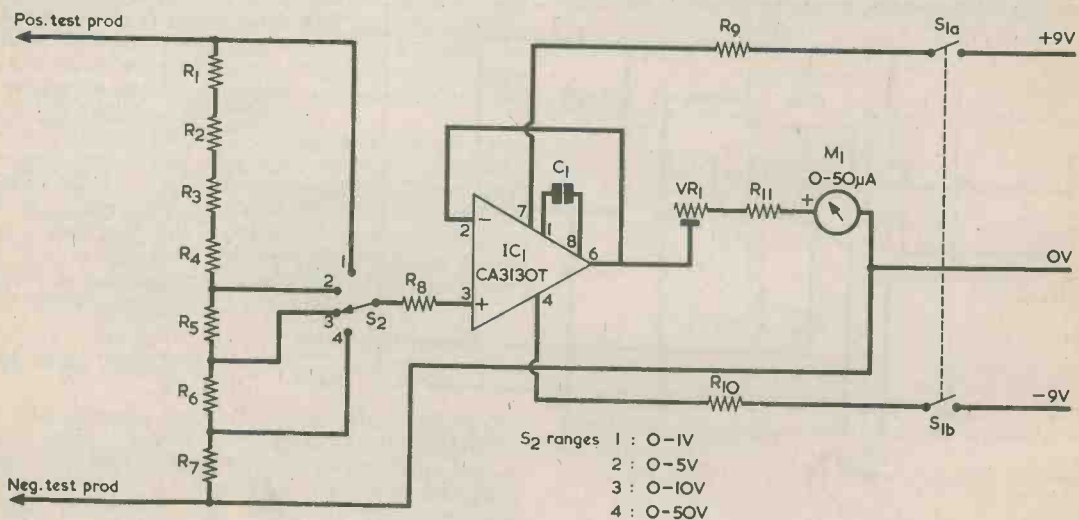


Fig. 3. The circuit of the CMOS voltmeter. This has two 9 volt supplies, one positive and the other negative of the central zero voltage rail

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ or $\frac{1}{2}$ watt. R1-R7 5% or less. R8-R11 10%.)

R1 2.7M Ω

R2 2.7M Ω

R3 3.3M Ω

R4 3.3M Ω

R5 1.5M Ω

R6 1.2M Ω

R7 300k Ω

R8 100k Ω

R9 3.3k Ω

R10 3.3k Ω

R11 15k Ω

VR1 10k Ω pre-set potentiometer, 0.1 watt skeleton, horizontal

Capacitor

C1 120pF ceramic plate or silvered mica

Integrated Circuit

IC1 CA3130T

Meter

M1 0-50 μ A moving-coil (see text)

Switches

S1 2-pole 2-way, rotary

S2 3-pole 4-way, rotary

Miscellaneous

2 batteries type PP9 (Ever Ready)

2 battery connectors

2 knobs

Veroboard, 0.1in. matrix

Plastic case (see text)

Test prod, red

Test prod, black

Wire, grommet, etc.

supply, voltages from 2.5 to 8 volts positive and negative. The i.c. cannot therefore be operated directly from two 9 volt batteries. A dual 4.5 plus 4.5 volt battery such as the PP11 could be used, but this is rather bulky for what is intended to be a miniature instrument. Also, since the current consumption of the unit is only 1.5mA, the use of a high capacity battery is not really justified.

The solution finally adopted is to employ two PP9 9 volt batteries, with series resistors R9 and R10 dropping the voltage which is actually applied to the CA3130T. This receives approximately 4.5 volts positive and negative, which is more than adequate for present requirements. No decoupling capacitors or supply stabilization are required.

Apart from the range switch the unit has only one other control, this being the on-off switch, S1(a)(b).

CONSTRUCTION

The author employed a 0-50 μ A meter from the Henelec 38 series having a square front measuring 42 by 42mm. With this meter it was possible to position the Veroboard panel between the terminals and to house all the components in a plastic case having internal dimensions of 110 by 75 by 33mm. Any plastic

case which is not smaller in any of these dimensions may be employed. The general layout is shown in the photographs. However, any other 0-50 μ A meter (or, as is explained later, 0-100 μ A meter) may be used, the layout and case being chosen to suit this. Using the author's layout the case stands vertically with the meter central and at the top. With the author's case there is just sufficient space for the batteries on either side of the meter.

The two switches are mounted below the meter, and a hole of about $\frac{1}{4}$ in. diameter is drilled below these and is fitted with a grommet. The test leads pass through this grommet.

Some of the components are assembled on a piece of Veroboard of 0.1in. matrix, and having 20 holes by 8 strips. Details of this board together with the remainder of the wiring are given in Fig. 4. To prevent possible damage to the CA3130T, all soldering must be carried out with an iron whose bit is reliably earthed.

Start by cutting out a panel of the required size and then make the five breaks in the copper strips by means of a Vero spot face cutter or a small twist drill held in the hand. Next solder in the components and the link wire. If a case and meter similar to those

A close-up view of the Veroboard assembly. There are two PP9 batteries, one on either side of the meter



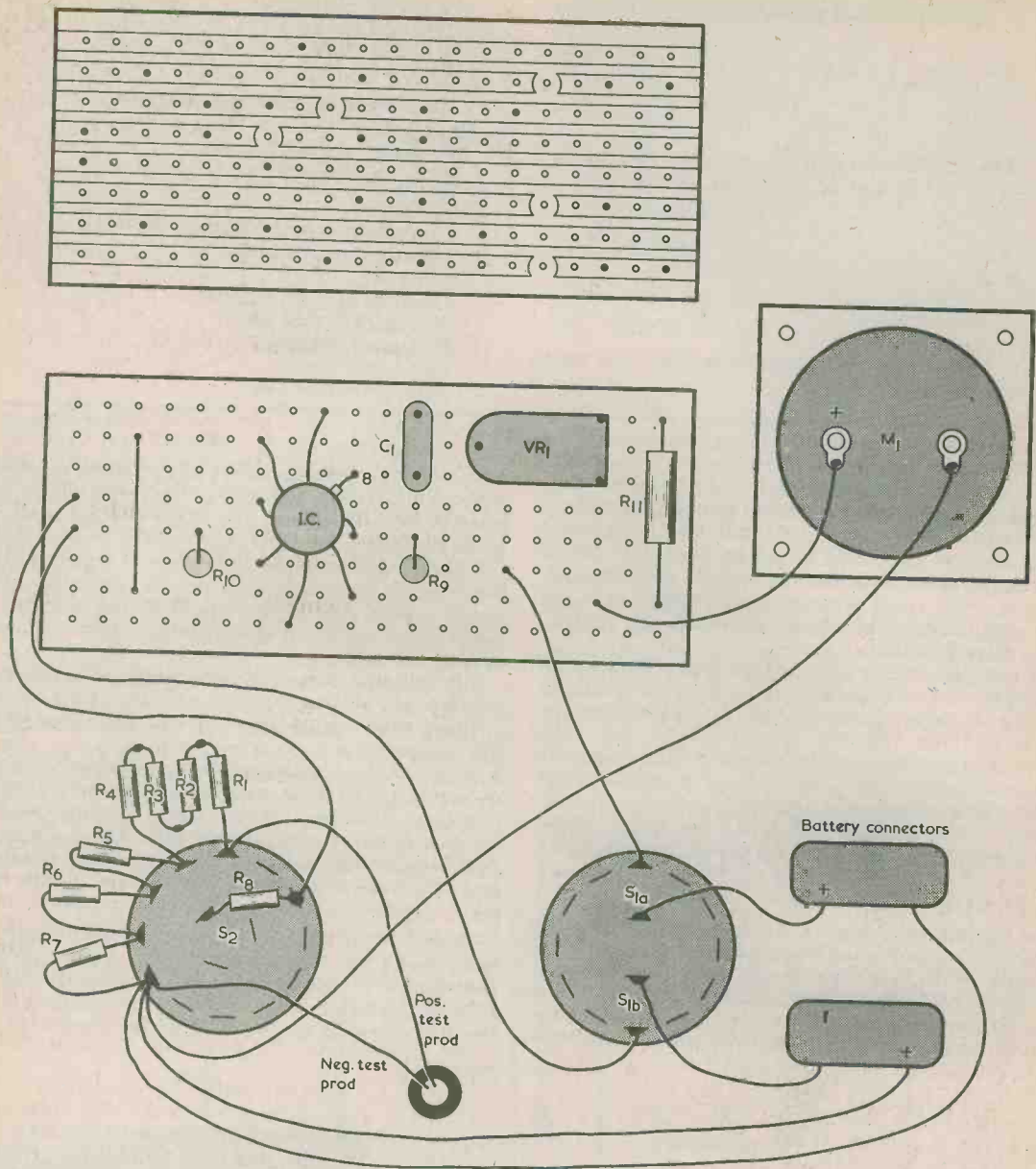



Fig. 4. Wiring details for the voltmeter, including the Verobard panel assembly

employed by the author are used, the Veroboard assembly should not be more than about 10mm. high or it will not fit the case; this requires that the components are kept close to the board.

R1 to R8 are soldered to switch S2, and it should be noted that two of the switch tags, on unused poles, are employed as anchor tags for one lead of R7 and one lead of R8. To avoid mistakes, first identify the four

outer tags corresponding to the inner switch arm tag by visual examination or with the aid of a continuity tester or an ohmmeter, then wire R1 to R6 inclusive to these. It should be noted that the relative positioning between the inner and outer tags may be different on some switches from that shown in Fig. 4. R7 and R8 may then next be wired in. S1(a)(b) is shown as a component having 12 outer tags, but any small 2-pole

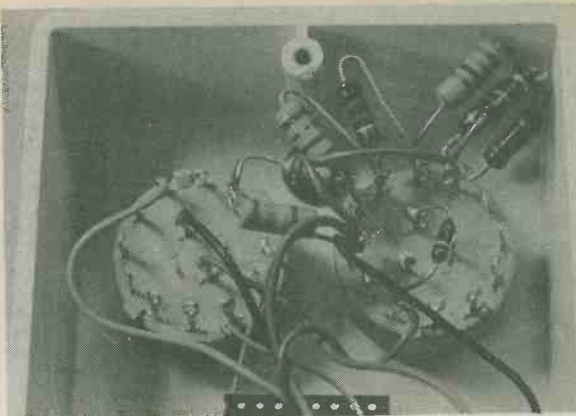The attenuator resistors are wired directly to the tags of the range switch



2-way rotary switch can be employed here.

The wiring between the switches, the board, the meter and the battery connectors is then completed. In the author's instance, the component board and batteries are held in place by the back of the case.

SETTING UP

Only one adjustment is required before the completed voltmeter can be used, and this consists of setting up VR1 to give the correct f.s.d. sensitivity.

This adjustment can be carried out in the following manner. Set VR1 to insert maximum resistance into circuit (slider fully anticlockwise), select the 0-10 volt

range and switch on. Then measure the voltage of the battery supplying the positive rail with a multimeter and note the reading. Remove the multimeter and apply the positive test prod of the voltmeter to the positive terminal of the battery which has just been checked. Adjust VR1 so that the meter gives a reading which is exactly the same as that obtained with the multimeter.

The CMOS voltmeter is then ready for use.


FINAL NOTES

Some final points need to be mentioned before concluding this article.


The author added the figures 0, 2, 4, 6, 8 and 10 to the scale of his 0-50 μ A meter to give a graduation from 0 to 10 in addition to the existing graduation from 0 to 50. Also added was the legend VOLTS. The figures and the legend were taken from Panel Signs Set No. 4, which is available from the publishers of this journal. Since the process of adding the figures and the legend involves removing the meter movement from its case, constructors who wish to do the same are advised to do so only if they feel confident to dismantle and reassemble the meter without damage. It should be borne in mind that a single speck of dirt can virtually ruin the operation of a meter if it finds its way into the moving parts. Legends on the front panel of the voltmeter were also taken from Panel Signs Set No. 4.

The output from the CA3130T will drive a 0-100 μ A meter, and a meter with this sensitivity may, in consequence, be employed instead of the 0-50 μ A meter listed in the Components List, should this be desired. With a 0-100 μ A meter, R11 requires a value of 7.5k Ω and VR1 a value of 5k Ω or 4.7k Ω .

The voltmeter circuit does not incorporate an offset null adjustment, with the consequence that the meter may possibly give an indication other than zero when no voltage is applied to the test prods. Judging from the data on the CA3130T the maximum offset voltage will be less than 10mV, and would not be discernible on a meter of the type employed by the author although it might just be visible with a large meter having a clearly graduated scale. Should such an offset voltage appear the meter needle may be returned to zero simply by adjusting the mechanical zero-set on the meter itself. The author has checked three CA3130T i.c.'s in the circuit and in each case the offset voltage was only about 1mV. ■

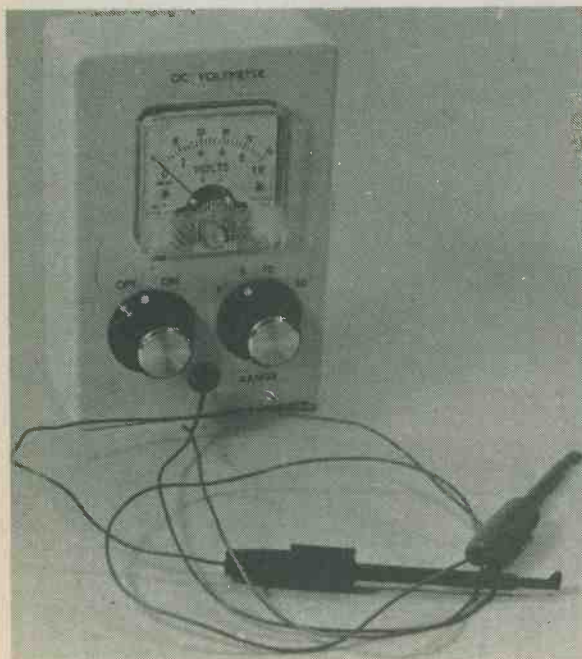

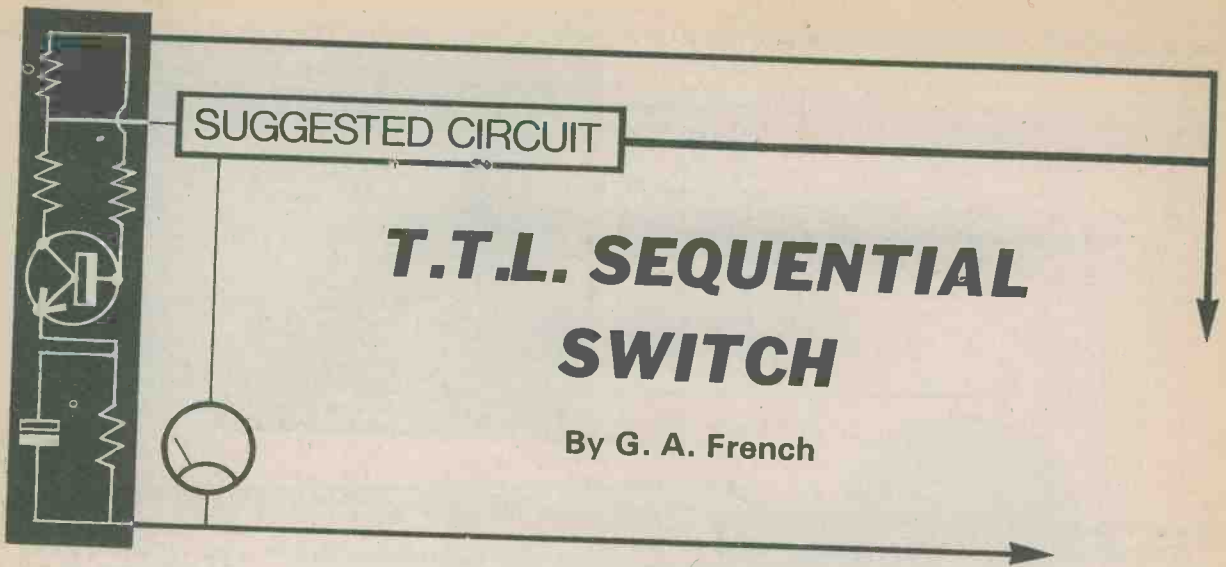Another view of the CMOS voltmeter, with its test prods all ready for use



T.T.L. SEQUENTIAL SWITCH

By G. A. French

Excusably, there is a tendency with modern electronics to look upon integrated circuits as enclosed "black boxes" with convenient terminal pins protruding for the connection of external components. In many cases, however, it is beneficial to be aware of at least part of the internal circuit of an i.c., especially if the i.c. is to be employed in an application other than that for which it was originally designed.

These remarks apply particularly to digital i.c.'s in the 74 t.t.l. series, and a knowledge of their input and output circuits reveals a capability for controlling surprisingly heavy loads.

74 SERIES CIRCUITRY

The input circuit for a standard 74 series digital i.c. has the basic form shown in Fig. 1(a), this applying to NAND gates, NOR gates, flip-flops and other devices. The input transistor has one or more emitters, each emitter coupling to an input pin. The input pins may be connected to the outputs of other i.c.'s of the 74 family. The base of the transistor couples to the positive supply rail via a resistor with a nominal value of $4k\Omega$. The positive supply rail is 5 volts stabilized, and should lie between 4.75 and 5.25 volts.

If a logic 0 is applied to the input terminal in Fig. 1(a) this terminal is drawn down very nearly to the zero volt rail. In consequence, a current flows through the emitter-base junction of the transistor and the $4k\Omega$ resistor. Assuming that the base-emitter junction of the transistor drops 0.6 volt, that the base resistor is exactly $4k\Omega$ and that the supply voltage is exactly 5, the maximum calculated current which can flow is 1.1mA (given by 4.4 volts divided by $4k\Omega$). In practice there are fairly wide

tolerances on the value of the resistor and other factors, and the maximum logic 0 input current quoted in the manufacturers' specifications is 1.6mA.

When the input is in the logic 1 state, it is raised above the zero volt rail by around 3.3 volts or more. Under this condition (and assuming that no other emitter is held at logic 0) the transistor base of Fig. 1(a) takes up a positive potential lower than that of the emitter due to the other circuitry in the i.c., and the emitter current which flows is proportionately very low, consisting of reverse bias leakage current. The maximum current figure quoted here by the

manufacturers is $40\mu A$. If, as in a NAND gate, one emitter moves to a logic 1 whilst a second emitter remains at logic 0, the second emitter holds down the transistor base to a low level and the junction of the first emitter and the base again become reverse biased. The only current which then flows in the first emitter is the leakage current in the reverse biased emitter-base junction.

These points explain, incidentally, why an unconnected input pin in 74 series logic automatically takes up the logic 1 state. The input has to be actively drawn down to a low voltage by an external circuit if it is to be in the logic 0 condition. It is in order, with

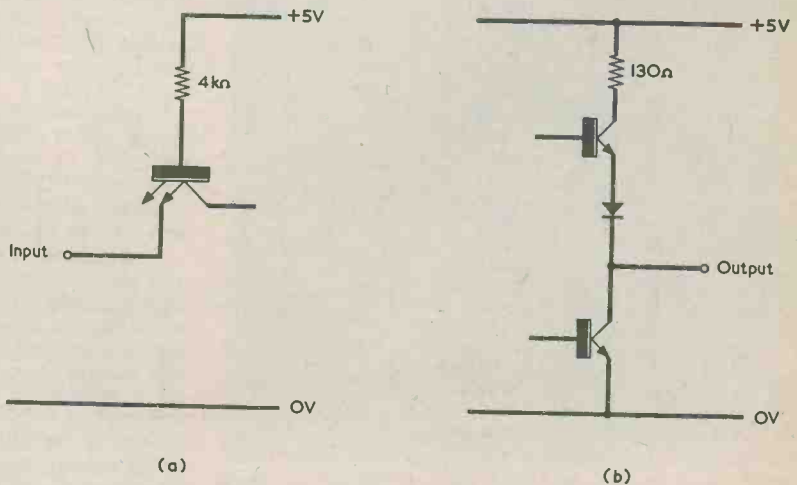


Fig. 1(a). The basic form of a 74 series gate input stage
 (b). A basic output stage

simple slow speed circuits, to leave a 74 series input open if it is desired that it take up a logic 1; but such an input should be taken to a suitable positive voltage or to the positive supply rail via a 1kΩ resistor if the i.c. is employed in a complex or high speed circuit.

The basic output stage for an i.c. gate in the 74 family appears in Fig. 1(b). When the output is in the logic 0 state the lower transistor is turned fully on and the upper transistor is cut off. Contrarily, when the output is at 1 it is the upper transistor which is turned on and the lower transistor which is off. There are several gates with open-collector outputs which omit the upper transistor and have the lower transistor only, but we can dismiss these for the time being.

The primary object of the output stage of Fig 1(b) is to drive one or more 74 series inputs. Since a considerably higher current is required to draw an input down to the logic 0 state, the lower transistor in the output stage has its emitter connected directly to the zero volt line and its collector connected directly to the output terminal so that the only voltage dropped in the circuit is that across the transistor itself. With a silicon transistor turned well on, this voltage will be of the order of 0.2 volt. The maximum voltage quoted by the manufacturer is 0.4 volt with 0.22 volt typical.

The current requirement for an output at logic 1 is very much smaller, and the output voltage can rise to an acceptably high value even though the upper transistor of Fig. 1(b) has in series with it a 130Ω resistor and a diode.

It is obvious that, if we wish to drive an external load from a 74 series output, we shall be able to draw a much larger current and have a higher voltage across the load if it is connected between the output and the positive rail rather than between the output and the negative rail. When the load is between the output and the positive rail the only item in series with it is the lower transistor of Fig. 1(b), and this is intentionally designed to pass a relatively high current.

The number of logic inputs to which a logic output can be connected is known as the output fan-out, and for 74 series logic the fan-out normally has a maximum value of 10. Thus, one output can draw ten inputs down to logic 0, each input having a maximum current rating of 1.6mA, whereupon the total output current has a maximum rating of 16mA. A 74 series output will, in consequence, drive any load connected between the output and the positive rail which does not consume more than 16mA.

The same remark applies to a gate having an open-collector output intended for coupling to the 5 volt positive rail. Driver gates with high voltage open-collector outputs have different criteria, and are in any case designed for relatively high output currents.

RELAY CIRCUIT

The fact that an ordinary 74 series gate can drive a load at currents up to 16mA opens up a number of interesting applications, of which the most obvious is that the load be a relay coil. An almost tailor-made component here is the "Miniature Open P.C. Relay" with 410Ω coil which is retailed by Doram Electronics Limited, P.O. Box TR8, Wellington Road Industrial Estate, Wellington Bridge, Leeds, LS12 2UF. The current drawn by this relay with 5 volts across the coil is 12.2mA, which fits comfortably inside the 16mA maximum output current figure.

The specified coil operate voltage range for this relay is 4.8 to 35 volts. The voltage across the relay coil will be 4.8 volts if the 74 series gate supply is exactly 5 volts and the voltage across the gate output transistor is 0.2 volt, and so the specifications just coincide. In practice, of course, the supply voltage may be a little lower than 5 volts and the voltage across the output transistor a little higher than 0.2 volt, whereupon the minimum specified voltage of 4.8 volts will not appear across the relay coil. However, the writer's experience with several samples of the Doram relay has shown that it just energises at voltages around 3.5 volts and operates reliably at a voltage of 4.35 volts. This is the minimum possible voltage if it is to be driven by a 74 series i.c. and is given

when the supply rail is at 4.75 volts and 0.4 volt is dropped across the output transistor in the 74 series gate. If it was desired to definitely ensure that the relay operating voltage was within specification the supply voltage could be stabilized at about 5.2 volts but, in the writer's opinion, there should be no necessity to work to such close limits.

A simple circuit in which a JK flip-flop type 7470 directly controls the Doram relay is given in Fig. 2. This is a sequential switch in which the relay energises when push-button S1 is pressed and then releases when it is pressed again. Pressing S1 a further time will cause the relay to be energised once more, and so on. The only discrete components are the relay, diode D1 and the push-button itself.

Pressing S1 results in a positive-going pulse edge being applied to the clock input of the flip-flop at pin 12, and this causes the Q output at pin 8 to change from its previous state. When the Q output is low the relay energises, and in the author's circuit the voltage at pin 8 was then only 0.15 volt positive of the zero volt rail, which is lower than the manufacturers' typical figure of 0.22 volt. The voltage at the not-Q output at pin 6 is opposite to that at the Q output, and the relay could alternatively be connected to this pin. The J and K inputs at pins 3, 4, 10 and 11 are all returned to the positive rail. The 7470 has inverting J

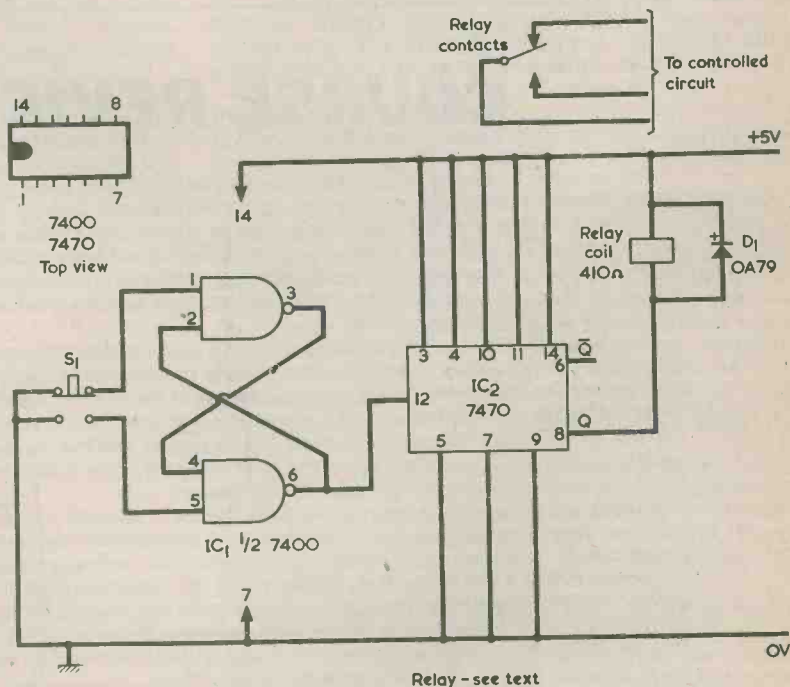


Fig. 2. A sequential switch circuit in which a t.t.l. flip-flop directly drives a relay coil

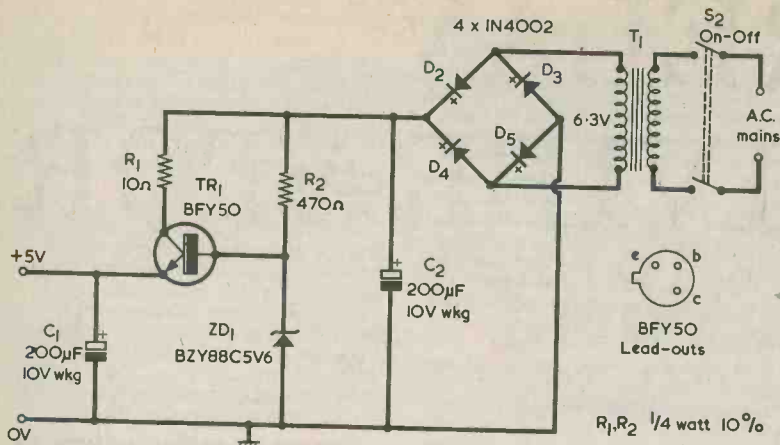


Fig. 3. A suitable power supply for the sequential switch

of the lower gate goes low, the output at pin 6 goes high and the output at pin 3 goes low. The circuit remains in this condition despite contact bounce in S1 and only reverts to its previous state when the switch is released and its upper contacts close again.

Turning to components, the push-button is an s.p.d.t. type, as indicated. The diode across the relay coil, D1, is included to prevent the formation of a high back-e.m.f. in the coil when the relay releases. A germanium type is chosen in order to limit the back-e.m.f. to around 0.2 volt positive of the positive rail. The relay specified has changeover contacts rated at 5 amps for 250 volts a.c. or 30 volts d.c. It is intended for soldering to a printed circuit board, but it can also be mounted in conventional fashion by means of two 8BA bolts and nuts. Its metal frame is common with its moving contact and this fact must be borne in mind if the relay is employed to switch mains voltages.

Constructors will probably have their own approaches towards obtaining the 5 volt stabilized supply. If it is intended to make up a power supply specifically for the sequential switch, a suitable circuit is given in Fig. 3. The mains transformer, T1, can be any small heater transformer with a secondary voltage of 6.3 volts.

A chassis symbol is shown in both Figs. 2 and 3. This may be ignored if the circuits are fitted in an insulated housing such as a plastic case.

and K inputs at pins 5 and 9 and these are returned to the zero volt rail.

A JK flip-flop cannot be controlled directly by a switch because of contact bounce when the switch closes. Two NAND gates of a 7400 are, in consequence, interposed between the push-button and the clock input of the 7470. Pin 14 of the 7400 is taken to the positive rail and pin 7 to the negative rail. No connections are made to any of the pins of either integrated circuit which do not appear in the diagram.

The two NAND gates form an RS

latch and the configuration is a standard one when a switch is coupled into a digital circuit. When S1 is not pressed the input at pin 1 of the upper NAND gate is low and so its output at pin 3 is high. As a result, both pins 4 and 5 of the lower NAND gate are high and the output at pin 6 is low. The circuit remains latched in this state when S1 is partially pressed and its upper contacts break because of the low input at pin 2, but it changes dramatically when the two lower contacts are connected together. Input 5

COURSE REVIEW

Of interest to beginners will be the series of books on "Basic Electronics" which has been produced by Project Technology, a body set up by the Schools Council at the College of Education, Loughborough. The aim of Project Technology is to promote a better understanding by pupils at all ability levels of the relevance of technology to society, and it has produced material which directly involves the pupil in the application of scientific knowledge to practical problems. The material on electronics is, of course, just as useful and helpful to those who have left school and are embarking on electronics as a hobby or a career.

The "Basic Electronics" course consists of five books which are intended to be read in numerical order. Book 1 (79 pages) is entitled "Introducing Electronics, Measuring Instruments", and shows how electronics is employed in all sections of modern life. It then deals with measuring instruments, these including the oscilloscope, the signal generator and the multimeter. "Resistors in Circuits, Capacitors in Circuits" is the title of Book 2 (112 pages), and the first section deals extensively with resistors, describing the various types and illustrating their functioning in circuits. The second part of the book deals with capacitors in a similar manner.

Book 3 (96 pages), "Inductors in Circuits, Diodes in Circuits", takes the reader further into the world of electronics and starts to demonstrate the properties of semiconductor devices. Book 4 (80 pages) covers "Meters, Voltage-dividers". The section on meters deals fully with meter shunts, series voltmeter resistors and ohmmeter circuits, whilst the remaining part of the book covers the field of voltage dividing circuits and their applications in such instruments as the Wheatstone bridge. "Transistors in Circuits, Transistors in Action, Post-transistor Projects" is the title of Book 5 (192 pages). This completes the course and takes the reader through transistors, transistor operation and transistor circuits, leading up to the operational amplifier.

The books are well illustrated with clear diagrams and include projects such as simple radio receivers, intercom amplifiers, intruder alarms, light operated devices and metal locators. Books 1 to 4 inclusive are priced at £1.25 each, and Book 5 at £2.00.

RELAY MULTIVIBRATOR

By D. W. Savage

The addition of a single capacitor allows two relays to function as a 50:50 multivibrator.

This useful little relay circuit appeared in the April 1976 issue of the Soviet journal *Radio*. When we tried it out in practice with two P.O. 3000 relays we found it worked so well that we felt it should be brought to the notice of readers of *Radio & Electronics Constructor*.

THE CIRCUIT

The circuit appears in the accompanying diagram, in which the blocks designated A/2 and B/2 are the coils of relays A and B respectively. Contact set B1 is a normally closed contact set of relay B, and contact set A1 is a normally closed contact set of relay A.

When the supply is applied both contact sets are closed. A charging current flows via the coil of relay A to the electrolytic capacitor C1 and relay A energises, causing its contact set A1 to open. The voltage across the capacitor increases as it charges. Relay B cannot energise as the circuit to its coil is broken by contact set A1.

After a period the voltage across C1 rises to a level at which the remaining voltage available for coil A/2 is too low to allow relay A to remain energised. Relay A releases and contact set A1 closes, connecting the charged capacitor across the coil of Relay B. Relay B

energises and its contact set B1 opens, breaking the circuit to the coil of relay A.

The capacitor now discharges into the coil of relay B, until the voltage across it falls to the level at which relay B releases. Contact set B1 closes and the voltage now available for coil A/2 is more than sufficient for relay A to energise. Contact set A1 opens and the capacitor starts to charge again via the coil of relay A. This continues until the voltage across the coil of relay A falls to the release level. Contact set A1 closes, the capacitor discharges into coil B/2, and the cycles continue.

External circuits can be switched by a second contact set on either relay A, or relay B, or both.

The two relays should be of the same type and have the same coil resistance. Relays having a release coil voltage which is considerably lower than the energise voltage are to be preferred. The supply voltage may be approximately twice the voltage normally employed to energise a single relay.


PRACTICAL RESULTS

The circuit was checked with two P.O. 3000 relays having 500 Ω coils. The supply was an 18 volt battery. Initially, C1 was 1,000 μ F.

The circuit functioned satisfactorily with a 50:50 cycle being completed in about 2.5 seconds. This is much longer than the time constant given by 1,000 μ F and 500 Ω would lead one to believe; doubtless the relay coil inductance, in opposing changes in current flow level, adds considerably to the length of each half-cycle. Changing the capacitor to 2,000 μ F roughly doubled the length of the cycle to approximately 5 seconds. Further increases in the value of the capacitor will result in roughly proportional increases in cycle length.

Rather surprisingly, the circuit operated well with quite low values of capacitance, and the minimum which gave good results was 50 μ F. With this value the relays completed a cycle in about 0.4 second. Relay operation was quite definite, with sharp energising and release actions.

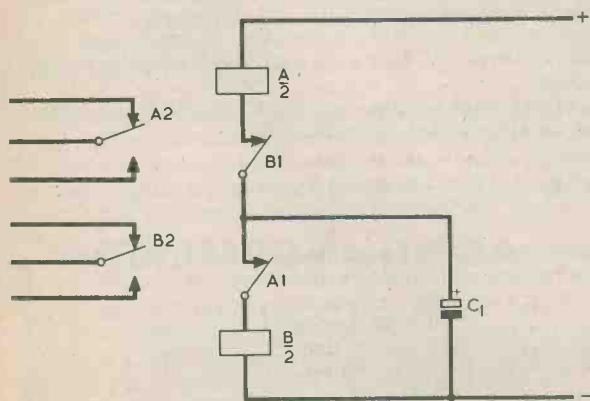
These notes should enable constructors to set up similar circuits. The relay coil resistances do not, of course, have to be 500 Ω provided that both resistances are the same. It is probable that best results will be given with relays having fairly high resistance coils, say above 300 Ω or so. The value of capacitance required for a particular cycle length can be found by experiment. ■



The circuit of the relay multivibrator. The relays energise alternately as the capacitor charges and discharges

NEWS . . . AND .

LABORATORY TWIN STABILISED POWER SUPPLY

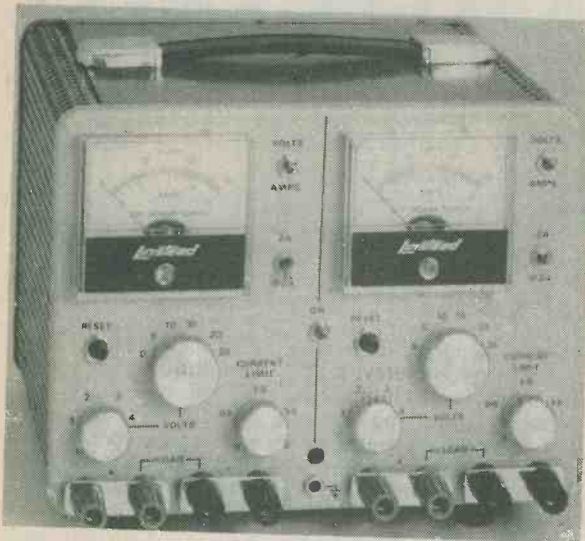

The new Twin Stabilised Power Supply from Linstead Electronic Instruments of Roslyn Road, London, N15 5JB is the S10. Intended for laboratory use it is a highly stable, completely isolated twin supply giving up to 2 amps over the range of 0 to 30

pedance is less than 0.2 ohms up to 1MHz.

The output voltage is controlled by a 5 volt step switch and a 0.5 volt fine control potentiometer. The ripple at all loads is less than 300 microvolts r.m.s. and the line regulation better than 0.01%. The output resistance is less than 0.005 ohms and the output impedance is less than 0.2 ohms up to 1MHz.

Over current protection is variable and calibrated over two ranges 0-200mA and 0-2 amps. It is easy, therefore, to set the maximum current very accurately. If this current is exceeded the volts automatically fall back to zero and a manual reset cutout operates.

Remote sensing is provided to compensate for voltage drop, where long leads are being used.

Both supplies are completely isolated with respect to each other and earth allowing series or parallel connections and \pm supplies to be constructed. It is, therefore, possible to obtain up to 60 volts at 2 amps or up to 30 volts at 4 amps.

Both outputs are metered and can be selected to monitor voltage or current.

The small size of the S10 (20.5 cm x 20 cm x 17.5 cm) means that it occupies a minimum amount of bench space and with its very high performance specification makes it an ideal piece of laboratory equipment.

Price: £137.

DESIGN CENTRE DISPLAY TO AID HI-FI UNDERSTANDING

Technical terms freely used by manufacturers can be baffling, but a display in The Design Centre, closing date 8th January 1977, will help all those who know little about hi-fi. As well as showing a selection of well-designed British hi-fi equipment, the display will show how hi-fi is achieved, and a specially prepared hi-fi guide will be available to help the non-specialist to understand what hi-fi is all about.

The centrepiece of the display will illustrate how the hi-fi system works while a commentary recorded by John Borwick, audio editor of the 'Gramophone', will explain in non-technical terms the various components needed for a successful hi-fi system. In conjunction with this exercise a 'Design Centre Guide to British Hi-Fi' has been compiled in association with the 'Gramophone'. An invaluable guide to prospective purchasers, it offers advice on selecting the right hi-fi equipment, illustrates some well-designed products take from Design Index, and explains how hi-fi is measured and the technical specifications used.

Several well-known manufacturers will be exhibiting their products in the display. The Acoustical Manufacturing Company's Quad 405 amplifier, which won a Design Council award earlier this year, will be on show and other amplifiers will be supplied from Armstrong Audio Ltd., Spendor Audio Systems Ltd. and Lecson Systems Ltd. A variety of

loudspeakers will be displayed by Gale Electronics, Jordan-Watts Ltd., Monitor Audio Ltd. and Rank Audio Visual Ltd.

Those who prefer more compact stereo systems and 'musiccentres' will be interested in the models from Rank Radio Ltd and ITT Ltd. Other equipment on display will include turntables, pick-up arms and headphones, together with record and cassette storage racks.

The Design Centre is situated near Picadilly Circus at 28 Haymarket, London SW1.

ANNOUNCEMENT

Owing to rising costs we regret that the cover price of this magazine will be 40p, commencing with the next issue. Annual Subscriptions will remain at £5.50.

We have a number of exciting projects lined up and our next issue will contain extra pages, thus enabling us to continue our policy of giving more space for articles than most of our contemporaries.

To make sure of your copy place a regular order with your newsagent.

COMMENT


UHF TV PATTERN GENERATOR INTRODUCED

Doram Electronics Limited, the Leeds based mail-order distributor of Electronic Construction Kits, audio and electronic components, have introduced a sophisticated yet simple to construct and operate UHF TV Pattern Generator.

As with all Doram construction Kits, this new and compact device has undergone extensive assembly and test trials with the result that graduate TV Service Engineers can build, with comparative ease, a really efficient test unit that will not only give long lasting service, but will be a very economical asset in the workshop or in field TV servicing.

The cleverly designed circuit with extensive use of integrated circuits does not require alignment and incorporates its own pulse generator to provide the added advantage of interlaced scan.

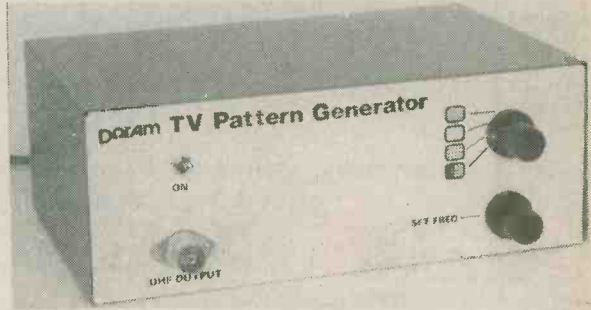A special feature is the inclusion of a visually adjusted frequency control which exactly locks its drift-free oscillator to both the TV line and frame sync. The four test patterns namely blank, dots, grey-scale and crosshatch have been carefully selected to provide



fast but accurate alignment of static and dynamic convergence, geometry, focus, beam limiting, grey scale and black level clamp.

For operation the device only requires connection to mains and the aerial socket of the TV.

The dimensions are 200 x 75 x 125 mm. Further details from Doram Electronics Ltd., P.O. Box TR8, Leeds 12 2UF.

BBC SEEKS GO-AHEAD FOR SPECIAL TRAFFIC REPORTS SERVICE

It is always encouraging to learn of the possible use of radio to ease our traffic problems.

A BBC scheme for road traffic information service direct to the motorist was recently put through its paces. Senior policemen, top Civil Servants, representatives of the AA, RAC, the Road Research Laboratories and the press went on a circular coach tour of London to hear how motorists could be given local traffic information over a small, cheap, fixed-tuner receiver in their car.

The scheme gives separate local traffic information via a network of low-power transmitters operating on the same frequency in the medium wave band. As the motorist travels, a receiver in his car automatically picks up the information being transmitted locally.

The receiver, could cost as little as £7 and could be so wired that it cuts into any programme the driver may choose to listen to on his car radio.


The key to the low-power system is that the information can be delivered in short messages repeated or updated at intervals, with longer periods of silence.

It was made clear the BBC was putting forward the scheme as an idea, and it was not proposed that the cost of the scheme should be a charge on the licence fee.

ELECTRONICS SUMMER SCHOOL FOR TEACHERS

The Department of Electrical Engineering Science at Essex University will be holding its annual Electronics Summer School for teachers during the week July 11-15 1977. Two courses will be run simultaneously. The Linear Circuit Design course is concerned with the use of transistors and operational amplifiers in analogue applications and the basic circuits of a hi-fi amplifier are investigated in detail. The Digital Circuit Design course concentrates on the use of the transistor as a switch and develops design using integrated logic circuits; a digital patchboard is used to introduce the concepts of combinational and sequential logic design.

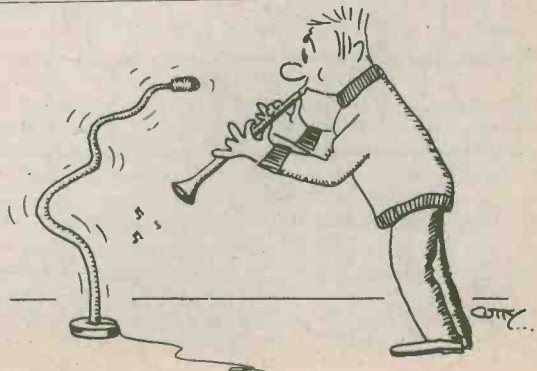Further information on the Summer School can be obtained from R. J. Mack at the Department of Electrical Engineering Science, University of Essex, Wivenhoe Park, Colchester CO4 3SQ.



THE '6-9' GAME

By R. J. Caborn

An amusing game for two contestants which can be programmed to offer a test of skill or provide a pure gamble.

This is a simple electronic game for two players, and it incorporates two inexpensive integrated circuits, a seven-segment digital l.e.d. display and a few other components. The seven-segment display alternately shows the figure 6 and the figure 9. The contestants each have a switch which causes the display to 'freeze' at the number which is showing when the switch is operated, whereupon one player endeavours to hold the display at the figure 6 and the other at the figure 9. If a player operates his switch at an incorrect time, the number shown is that of his adversary who thereby gains a point. The length of time in each cycle when the figure 6 is displayed is exactly equal to the time when the figure 9 is shown, with the result that


there is a complete lack of bias towards one number or the other.

A continuously variable speed control changes the length of the cycle over a range of 0.7 second to 0.1 second. At the slower cycle speeds operation of the switches is a test of the reaction time of the contestants. At the higher speeds the number displayed after operation of a switch is purely a matter of chance.

CIRCUIT OPERATION

The circuit of the '6-9' game appears in Fig. 1. This

Fig. 1. The circuit of the '6-9' game.

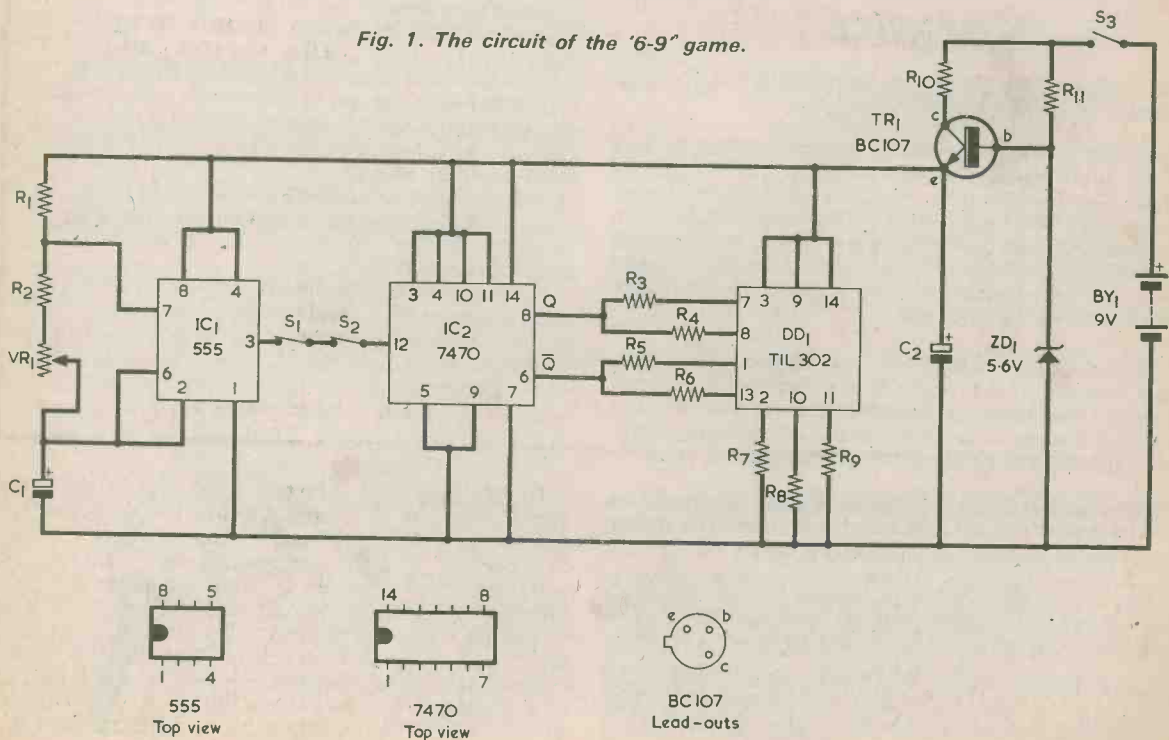

employs a 555 timer in conjunction with a J-K flip-flop type 7470. A device employing these two integrated circuits to produce a continually changing 50-50 output has been described earlier in this journal, and was used in a simpler application which demonstrated flip-flop operation in "In Your Workshop" in the June 1976 issue. Credit for the idea is therefore due to the erudite Smithy and his enthusiastic associate, Dick.

In the present circuit the 555 timer is employed in a standard astable multivibrator circuit in which C1 charges via R1, R2 and VR1, and discharges via R2 and VR1. The length of the cycle can be varied by adjusting VR1, which is a front panel control.

A series of regularly spaced pulses appear at the output, pin 3, of the timer and are passed via S1 and S2 to the clock input, pin 12, of IC2. S1 and S2 are the two switches operated by the contestants, and they are normally closed. IC2 is a t.t.l. J-K flip-flop with the J and K inputs at pins 3, 4, 10 and 11 taken to the positive rail. Pins 5 and 9 are inverting J and K inputs, and these are connected to the negative rail. Pins 14 and 7 are positive and negative supply pins.

The flip-flop outputs at pins 8 and 6 are Q and not-Q respectively. (Not-Q is represented by the letter Q with a bar over it.) These change state from the 1 to the 0, or from the 0 to the 1, condition with each pulse from the 555 timer. Since pin 8 is Q and pin 6 is not-Q, pin 8 is always at 1 when pin 6 is at 0, and vice versa. Both outputs are capable of drawing 16mA from the positive supply when they are in the 0 state. In the 0 condition, either output is about 0.2 volt positive of the negative supply rail.

The seven-segment display is a TIL302 or equivalent, and has the pin allocations shown in Fig. 2. Here, "D.P." refers to the decimal point, which is to

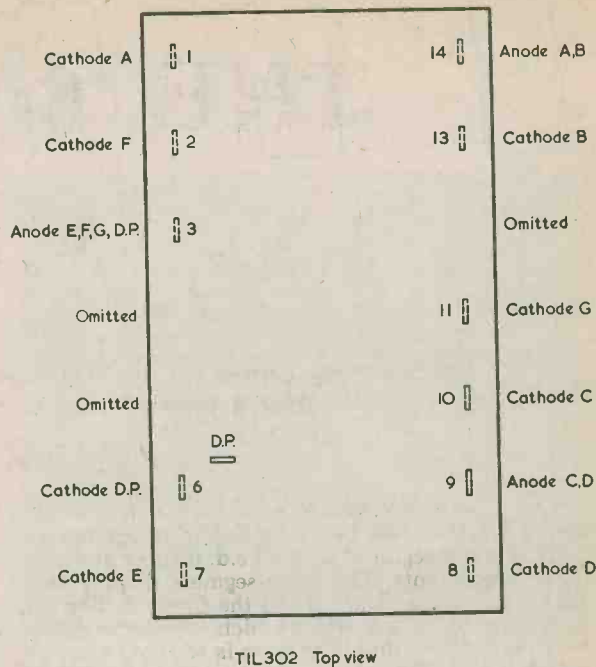


Fig. 2. Pin allocations for the seven-segment digital display type TIL302

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 5%)

- R1 4.7k Ω
- R2 1k Ω
- R3 1k Ω
- R4 1k Ω
- R5 1k Ω
- R6 1k Ω
- R7 1k Ω
- R8 1k Ω
- R9 1k Ω
- R10 39 Ω
- R11 1k Ω
- VR1 20k Ω potentiometer, linear

Capacitors

- C1 10 μ F electrolytic, 10 V. Wkg.
- C2 100 μ F electrolytic, 10 V. Wkg.

Semiconductors

- IC1 555
- IC2 7470
- TR1 BC107
- ZD1 BZY88C5V6
- DD1 TIL302 or equivalent (see text)

Switches

- S1 s.p.s.t. toggle
- S2 s.p.s.t. toggle
- S3 s.p.s.t. toggle

Battery

- BY1 9-volt battery (see text)

the left of the displayed figure and which acts as a convenient orientation marker for determining the pin numbers of the display. The pins are behind the body of the display, pointing away from the reader.

The seven segments of the display which make up the figures are identified by the letters A to G, as illustrated in Fig. 3(a). Figure 6 is formed by lighting up the segments shown in Fig. 3 (b), whilst 9 is formed in the manner illustrated in Fig. 3(c). It will be seen that segments F, G and C are illuminated for both numbers.

Returning to Fig. 1, the three common anodes of the display, at pins 3, 9 and 14, are connected to the positive rail. Pins 2, 11 and 10, for segments F, G and C, are returned to the negative rail via R7, R9 and R8, with the result that these three segments are continually illuminated. When the Q output of IC2 is at 0, segments E and D of the display are lit up via pins 7 and 8 and resistors R3 and R4. The figure 6 is consequently displayed. Similarly, when the not-Q output is at 0, segments A and B are illuminated, by way of pin. 1 and 13 and resistors R5 and R6, to form the

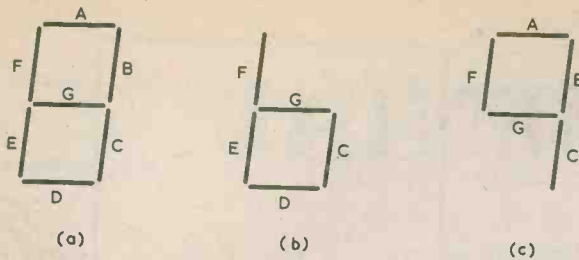


Fig. 3(a). The seven segments of the display are identified by letters, as shown here
 (b). The segments which are illuminated for figure 6
 (c). Here the segments light up to form figure 9

figure 9. Thus, the numbers 6 and 9 appear alternately in the display.

The values of R3 to R9 allow a current of approximately 3mA to flow in each segment when it is illuminated. This rather low current is chosen in the interests of battery life, but the resulting display is still more than adequately bright.

The 7470 requires a supply voltage of 5 volts for correct operation, and this is provided by the simple zener regulating circuit comprising ZD1, TR1 and R11. R10 is included to limit surge current on switching on as C2 charges. S3 is the on-off switch. The current drawn by the circuit is approximately 35mA and so a large battery, such as the PP9, is recommended. A better choice would be three 3-volt cycle lamp batteries (Every Ready No. 800) connected in series.

SWITCH OPERATION

As already mentioned, S1 and S2 are the contestants' switches, and are normally closed. If either switch is opened, the output of the 7470 remains in the condition it held at the instant of opening the switch, and the seven-segment display retains a 6 or a 9, as applicable. When one contestant's switch is opened the other switch has no control over circuit operation. S1 and S2 are toggle switches since this type gives a definite switching action. If simple push-buttons which open when pressed were employed it would be possible to cheat by pressing these lightly and "nudging" the output to the alternative number if the one selected happened to be incorrect. Push-button switches having a definite toggle action could, however, be employed.

One of the features of the game is that, so far as scoring is concerned, it does not matter which switch is opened. If the player favouring 6 inadvertently selects a 9 then the advantage accrues to his opponent. The switches can be operated at any time, although each contestant will naturally try to operate his own switch as many times as possible in order to score the highest number of points for the display of his figure. When a figure has been displayed and noted, the switch which has been opened is closed again and the game proceeds.

The total length for a complete cycle from the 555 timer depends upon the setting of VR1. When VR1 inserts maximum resistance into circuit the cycle time calculates at approximately 0.35 second, giving a total cycle period at the 7470 outputs of 0.7 second. If VR1 inserts zero resistance into circuit, the calculated time for a cycle from the 555 is approximately 0.05 second, whereupon that from the 7470 is 0.1 second. Because of component tolerances, the cycle times given in practice will vary somewhat from the calculated figures. With the cycle period at its longest it is a relatively easy matter to operate S1 or S2 to select a particular figure but, even at this slow speed, errors can be surprisingly frequent. About the best cycle length when skill is to be assessed is given with an overall cycle length of about 0.4 second. Each figure is then illuminated for 0.2 second, as opposed to the normal human reaction time of around 0.3 second. The game, incidentally, can offer a convincing demonstration that, contrary to the beliefs of some drivers, a few drinks do *not* speed reaction time!

VR1 is a normal carbon track potentiometer. If difficulty is experienced in obtaining a 20kΩ component, a 22kΩ or 25kΩ potentiometer may be employed instead, with a consequent increase of the longest cycle period available.

The TIL302 will plug into a 14 pin d.i.l. integrated circuit holder. There are a number of similar seven-segment displays available with a nominal display height of 0.3in. Notable amongst these is the SLA7, which has a single common anode for all segments connecting to pin 14. With this display, pins 3 and 9 are omitted. The other pins are the same as with the TIL302.


The components can be assembled in any small metal or plastic case large enough to accommodate them. The three switches and the seven-segment display are mounted on the front panel, with S1 and S2 near opposite edges. To avoid argument, it is of advantage to have one of these switches identified by the figure 6 marked on the front panel and the other similarly identified by the figure 9.



EXPERIMENTAL

AERIAL TUNING UNIT

By
Henry Hatch

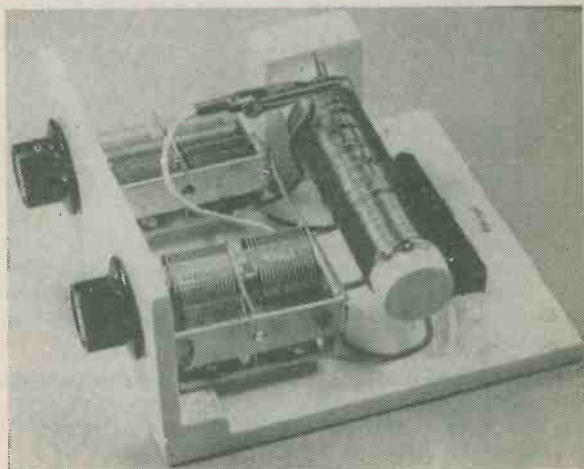

The tuning unit in its completed form. The two variable capacitors are mounted on the front panel with the coil positioned horizontally behind them. The tinned copper wires at the coil taps project upwards, and the crocodile clip connects to whichever of these is required

Intended for boosting signal strength on the short wave broadcast bands, this low-cost design takes advantage of homely materials in its construction.

This simple and inexpensive piece of home-constructed equipment is intended for connection between a short wave receiver and an aerial, and it should in almost every instance increase signal to noise ratio on the international short wave bands. Cost is low and only essential components have been used.

As can be seen from Fig. 1, the unit employs a pi matching circuit incorporating a series tapped coil with two variable capacitors at either end coupling to earth. Each tap in the coil corresponds to one of the short wave broadcast bands.

CONSTRUCTION

The first step in construction is to acquire a former for the coil. This is approximately 1 in. in diameter and can be very conveniently provided by about 5½ in. cut from a broom handle. (Almost all broom handles checked by the writer are 1 in. in diameter.) The wood should be perfectly dry and can, if desired, be painted.

About 80 turns of 20 s.w.g. enamelled wire are close-wound on this former, the ends being anchored

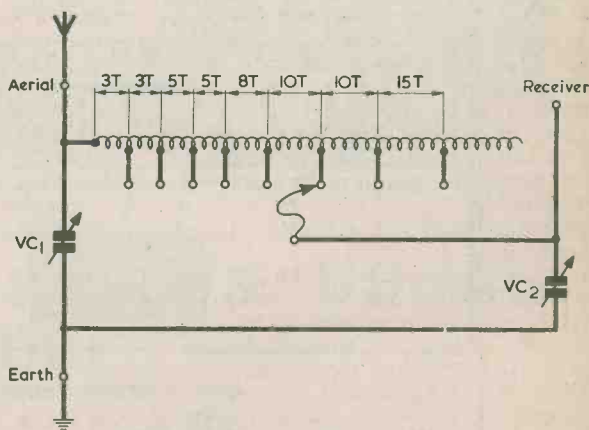


Fig. 1. The simple circuit employed in the aerial tuning unit

by soldering at two tags screwed into the wood. The start of the coil is about $1\frac{1}{4}$ in. from one end of the former. The coil has 8 taps, one for each of the main short wave broadcast bands of 11, 13, 16, 19, 25, 31, 41 and 49 metres.

The first tap, for 11 metres, is 3 turns from the start, and the second tap, for 13 metres is at 3 turns further on. The 16 metre tap is 5 more turns on, and the 19 metre tap another 5 turns after this. The 25 metre tap appears after 8 more turns, the 31 metre tap after 10 more turns and the 41 metre tap after another 10 more turns. The final tap, for 49 metres, follows a further 15 turns. There are about 20 turns of the coil remaining and these are available for experimental purposes later on.

Of these taps the only critical one is the first for 11 metres, and it may be found necessary to shift this tap by half a turn on one side or the other of the position specified. If taps are made every 5 turns after the 19 metre tap it would be possible for the unit to cover any frequency in the range. However, this requires some skill in soldering and the taps will all be rather close together.

The easiest way of making a tap consists of inserting a small thin screwdriver blade under the coil wire at the required tapping point and levering it up slightly. Then, leaving the screwdriver in place, about $\frac{1}{4}$ in. of the enamel is scraped off and a piece of 20 s.w.g. tinned copper wire $\frac{3}{8}$ in. long with $\frac{1}{4}$ in. bent at right angles at the bottom is soldered to the coil wire. The tinned copper wire projects upwards. The screwdriver is next removed and the coil wire pressed back into its original position.

PANEL AND BASEBOARD

A panel and baseboard are required, and these can be assembled as shown in Fig. 2 and the photograph. Two pieces of $\frac{3}{8}$ in. plywood are quite suitable. In the author's unit the coil former is passed through a 1 in. hole in a wooden block measuring $2\frac{1}{2}$ by $1\frac{1}{2}$ by $\frac{3}{8}$ in. thick. Any other means of mounting the former may be used provided that the material employed is mainly wood or another insulating material. VC1 and VC2 are mounted on the front panel. These two capacitors can have values of 350 to 500pF. The author used the rear sections of two 2-gang capacitors which happen-

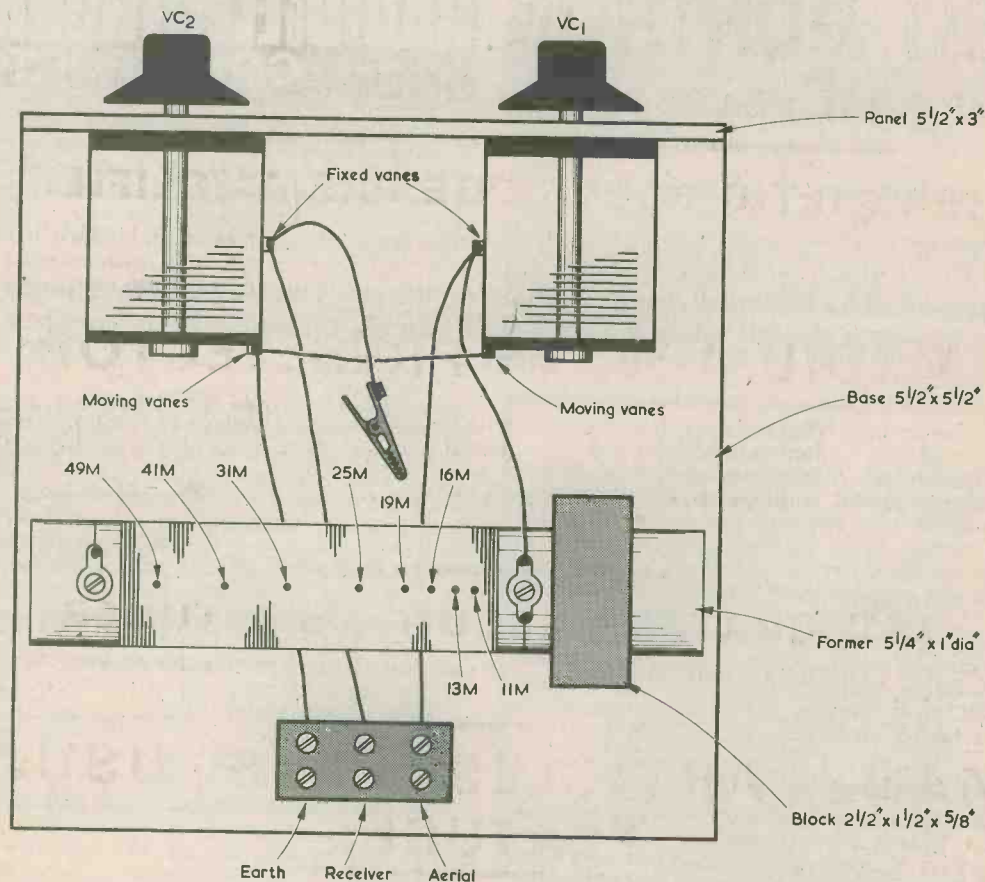


Fig. 2. Practical appearance of the unit. Dimensions are not critical provided that the general layout is observed

ed to be available, but single gang capacitors will normally be employed. The capacitors must be air-spaced types.

A 3-way terminal strip is fitted at the rear of the baseboard for connections to the aerial, earth and receiver, after which the unit is wired up as shown in Fig. 2. The crocodile clip lead from the fixed vanes tag of VC2 uses flexible wire and should be long enough to allow the clip to connect to any of the coil taps. All the remaining wiring uses single core tinned copper wire of around 20 s.w.g.

The unit is now ready to be tried out. First tune in a short wave signal with the aerial connected to the receiver in the normal manner, then connect the tuning unit between the aerial and the receiver. The aerial and earth connect to the appropriately identified terminals on the tuning unit, with the earth connection to the receiver being maintained. The 'Receiver' terminal connects to the aerial input of the receiver. Select the appropriate coil tap and adjust VC1 and VC2 for maximum signal level. If the receiver is fitted with an S-meter it is probable that

the tuning unit will increase meter deflection by some two S-points or more. There has always been disagreement amongst amateurs as to how many decibels are represented by an S-point, although most will agree to a minimum of 4dB, which corresponds to a voltage ratio of more than 1.5. Clearly, an improvement of several S-points in signal strength is really worth-while.

Beginners may ask how it is possible to achieve an increase in signal strength with the aerial tuning unit when it employs no amplifying device such as a transistor or a valve. The answer is that the unit ensures that as much as possible of the signal energy picked up on the aerial is passed to the receiver by providing optimum matching between the two.

As a final point, a warning must be given concerning mains operated receivers. The unit must not be used with a mains operated receiver unless the receiver chassis and earth terminal are fully isolated from the mains supply by way of a double-wound mains transformer. ■

NEXT MONTH IN

SPECIAL FEATURES

RADIO & ELECTRONICS CONSTRUCTOR

MAGNETIC CARTRIDGE PRE-AMPLIFIER

Many hi-fi amplifiers have an input which is suitable for a ceramic pick-up only. This article describes a stereo pre-amplifier which brings output of a magnetic cartridge up to the same level as that of a ceramic pick-up, and which also gives the necessary frequency response equalisation.

MEDIUM WAVE PRESELECTOR

A preselector design incorporating its own ferrite rod aerial and employing a dual gate MOSFET in the interests of low cross-modulation. It is primarily intended for use with the medium wave DX superhet as described in the previous two issues.



INTEGRATED CIRCUIT T.R.F. TUNER

This article describes a simple medium and long wave tuner incorporating the integrated circuit type ZN414.


MANY ARTICLES PLUS USUAL
FEATURES

EXTRA PAGES

Price 40p
ON SALE 1st FEBRUARY

SIMPLE REGENER

B
A. P. F

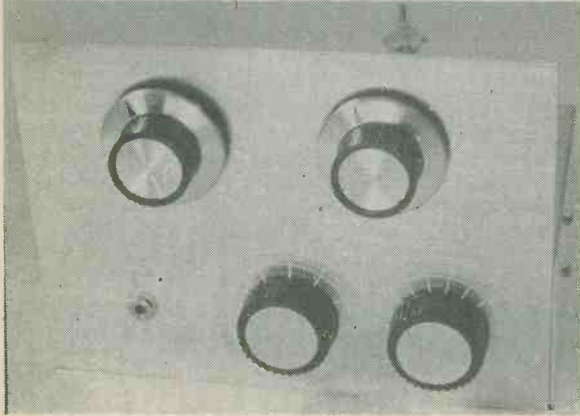

The front panel layout of the receiver

This little receiver employs an unus
and covers 1.5 to 36MHz by means o
headphone level, and it may alternativ
particular attraction is the low current
ly ba

CIRCUIT DETAILS

The circuit of the basic two transistor receiver is given in Fig. 1. TR1 is the regenerative detector with feedback, or regeneration, being controlled by VC2. Since the drain and source are in phase at signal frequencies the feedback is positive. VC2 functions as a coarse feedback control, with VR1 acting as a fine

This simple receiver covers what is virtually the complete short wave spectrum from approximately 1.5 to 36MHz. There are three ranges, these being selected by plugging in Denco Miniature Dual Purpose coils. Quoting the Denco range numbers, these are Range 3, 1.5 to 5.5MHz; Range 4, 5 to 17MHz; and Range 5, 10 to 36MHz. The use of plug-in coils makes construction much easier than would be the case if handswitching were employed. The coils are the Green type, and are normally associated with valve usage.

The basic receiver circuit employs two transistors, one of which is a field-effect type functioning as a regenerative detector whilst the other is a bipolar transistor providing a.f. amplification. The output is suitable for magnetic headphones having a resistance of 2kΩ per phone, or for any other load of 4kΩ or more. If desired, an optional untuned r.f. amplifier, which employs another f.e.t., can be added before the regenerative detector stage.

Excellent results have been obtained with the basic receiver using an indoor aerial only 6 metres long. A long outdoor aerial will provide better results, but an indoor aerial will suffice in locations where a proper outdoor type is not feasible. Current consumption of the basic receiver is about 2mA, this rising to about 3.5mA if the untuned r.f. amplifier is fitted. A 9 volt PP3 battery provides many hours of operation.

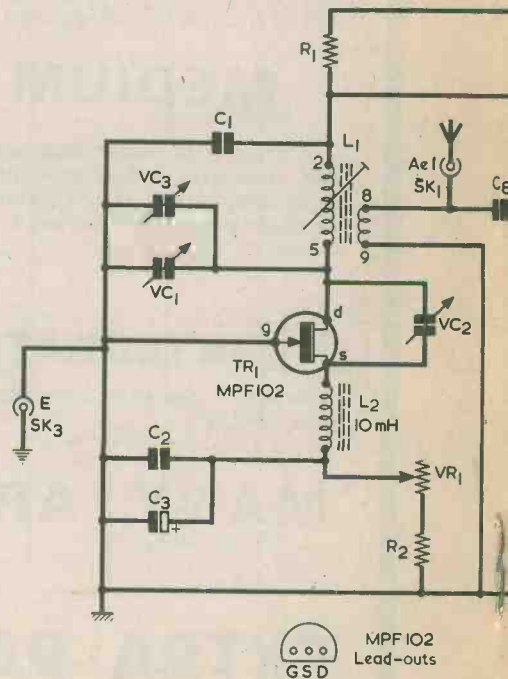


Fig. 1. Circuit of the two tran


REGENERATIVE S.W. RADIO

Roberts


ual regenerative f.e.t. detector circuit of three plug-in coils. The output is at vely be applied to an a.f. amplifier. A which is drawn from the 9 volt supp- ttery.

feedback control. For normal a.m. listening the feed- back is adjusted to a point just below that at which os- cillation commences.

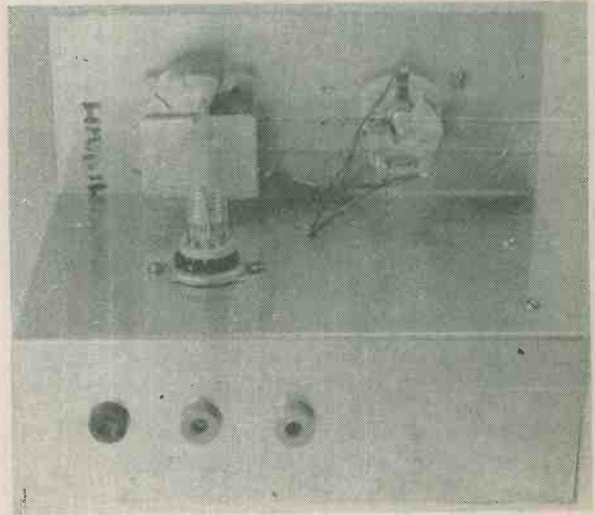A regenerative detector relies upon the fact that it distorts the r.f. signal by amplifying one set of half- cycles more than the other set. The result is a partial rectification which produces the required detection. The use of regeneration increases the distortion and



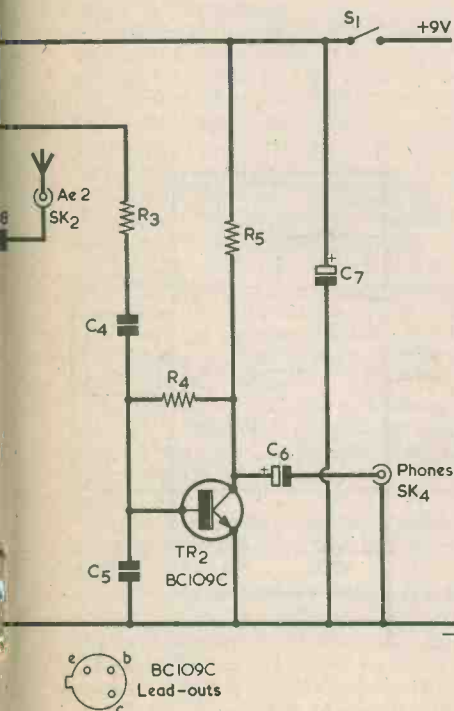The only components appearing above the chassis are the plug-in coil, the bandset tuning capacitor and the variable feedback capacitor



nsistor basic receiver

thus enhances detection efficiency. Regeneration also increases the gain of the amplifier to which it is applied and for these two reasons regenerative detectors are extremely sensitive. However, in order to obtain optimum results the detector regeneration level must be adjusted very carefully, as will be described more fully later.

The r.f. choke in the source circuit of TR1 provides a fairly high impedance at r.f., and also allows a ready path for the d.c. supply current for the transistor. The source resistance, given by VR1 and R2 in series, is bypassed at r.f. by C2 and at a.f. by C3. The circuit will in fact function without C3, but there is a slightly higher output when it is included. C2 is employed as well because some electrolytic capacitors do not provide an efficient bypass at high radio frequencies.

The tuned circuit which selects the required signal consists of the parallel combination of VC1 and VC3 and the winding of L1 between pins 2 and 5. VC1 is the main tuning or bandset capacitor whilst the lower value VC3 is the bandspread control. The aerial input is applied to the coupling winding between pins 8 and 9, with the aerial plugging into SK1 or SK2. The aerial is normally coupled to SK1, but if propagation conditions are good and the set is being swamped by strong signals the aerial is transferred to SK2. C8 then attenuates input signals to some degree and prevents the overloading. It should be noted that the coils

REGENERATIVE S.W.

By
A. P. Roberts

This little receiver employs an unusual regenerative f.e.t. detector circuit and covers 1.5 to 36MHz by means of three plug-in coils. The output is at headphone level, and it may alternatively be applied to an a.f. amplifier. A particular attraction is the low current which is drawn from the 9 volt supply battery.

CIRCUIT DETAILS

The circuit of the basic two transistor receiver is given in Fig. 1. TR1 is the regenerative detector with feedback, or regeneration, being controlled by VC2. Since the drain and source are in phase at signal frequencies the feedback is positive. VC2 functions as a coarse feedback control, with VR1 acting as a fine

feedback control. For normal a.m. listening the feedback is adjusted to a point just below that at which oscillation commences.

A regenerative detector relies upon the fact that it distorts the r.f. signal by amplifying one set of half-cycles more than the other set. The result is a partial rectification which produces the required detection. The use of regeneration increases the distortion and

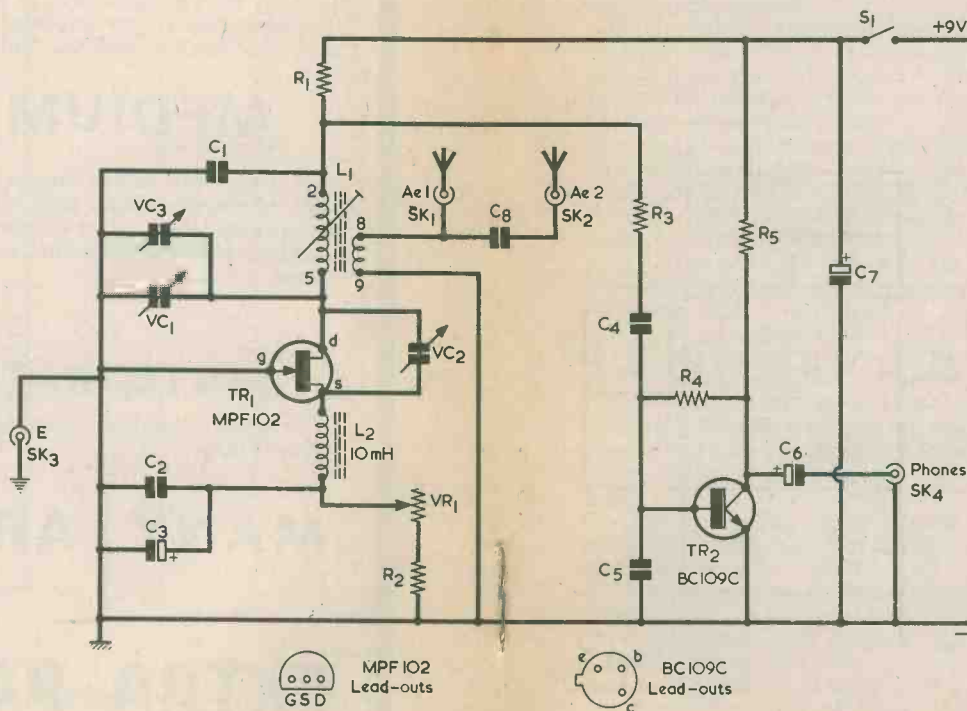


Fig. 1. Circuit of the two transistor basic receiver

specified for L1 have a third winding between pins 3 and 4. This winding is not employed in the present circuit and is not shown in Fig. 1.

TR2 is a high gain common emitter a.f. amplifier, with R5 as its collector load and R4 providing base bias. The detected signal from TR1 drain is applied via R3 and C4, the latter providing d.c. blocking. R3 and C5 function as a filter which prevents any r.f. signal from the detector reaching the base of TR2.

Such filtering is essential as the frequency response of the a.f. amplifier can extend well into the r.f. spectrum, and any r.f. entering this stage could cause instability. R3 and C5 also attenuate the higher audio frequencies, with a consequent improvement in signal-to-noise ratio.

The output signal is taken from SK4, C6 giving d.c. blocking. There is only one supply bypass capacitor, and this is C7. S1 is the on-off switch and is ganged with VR1.

COMPONENTS

Resistors

(All fixed values $\frac{1}{2}$ watt 5%)

- R1 3.3k Ω
- R2 390 Ω
- R3 680 Ω
- R4 3.3M Ω
- R5 5.6k Ω
- R6 3.9k Ω
- R7 680 Ω
- R8 680 Ω
- VR1 5k Ω potentiometer, linear, with switch S1.

Capacitors

- C1 0.01 μ F ceramic
- C2 6,800pF polystyrene
- C3 10 μ F electrolytic, 10 V. Wkg.
- C4 0.1 μ F type C280 (Mullard)
- C5 0.01 μ F type C280 (Mullard)
- C6 10 μ F electrolytic, 10 V. Wkg.
- C7 100 μ F electrolytic, 10 V. Wkg.
- C8 5.6pF ceramic or silvered mica
- C9 0.047 μ F type C280 (Mullard)
- C10 0.01 μ F type C280 (Mullard)
- VC1 365pF variable, type 01 (Jackson)
- VC2 50pF variable, type C804 (Jackson)
- VC3 15pF variable, type C804 (Jackson)

Inductors

- L1 Miniature Dual-Purpose Coils, Green, Ranges 3, 4 and 5 (Denco)
- L2 10mH r.f. choke, type CH4 (Repanco)

Transistors

- TR1 MPF102
- TR2 BC109C
- TR3 2N3819

Sockets

- SK1, 2, 3 wander plug insulated sockets
- SK4 3.5mm. jack socket (see text)

Switch

- S1 s.p.s.t. toggle (part of VR1)

Miscellaneous

- B9A valveholder
- 4 knobs (see text)
- Veroboard, 0.15. matrix
- Veropins, 0.15in.
- 9 volt battery type PP3 (Ever Ready)
- Battery connector
- 16 s.w.g. aluminium sheet
- Wire, nuts, bolts, etc.

CHASSIS AND PANEL

A home-made chassis and front panel are employed, these being constructed from 16 s.w.g. aluminium sheet. Fig. 2 gives the dimensions of the chassis and it is advised that this be made before the front panel is drilled.

A $\frac{3}{4}$ in. diameter hole is punched in the deck of the chassis and a B9A valveholder is mounted in this. This valveholder takes whichever coil is in use. If a suitable chassis punch is not available, an alternative method of making the hole is to drill a series of closely spaced small holes just inside the circumference of the cut-out and then break out the centre piece of aluminium. The rough edges are then removed and the hole filed out to the required diameter with the aid of a small half-round file. The valveholder is used as a template for marking out the positions of the two 6BA clear mounting holes. The valveholder is mounted with the orientation shown in Fig. 4, and there is a 6BA solder tag under one of its mounting nuts.

The remaining small hole in the chassis deck will allow the passage of several leads, and its precise positioning is not important. Also shown in Fig. 2 are the positions of the a.f. and r.f. panels. The mounting holes for these are drilled later.

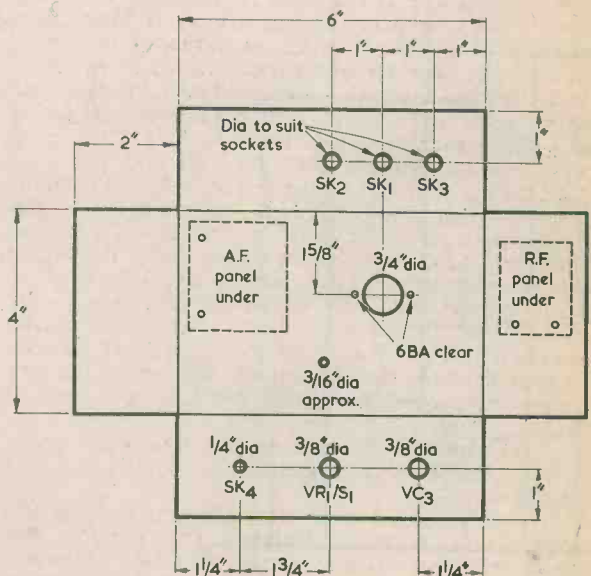


Fig. 2. Details of the chassis. The four flanges are bent down, away from the reader

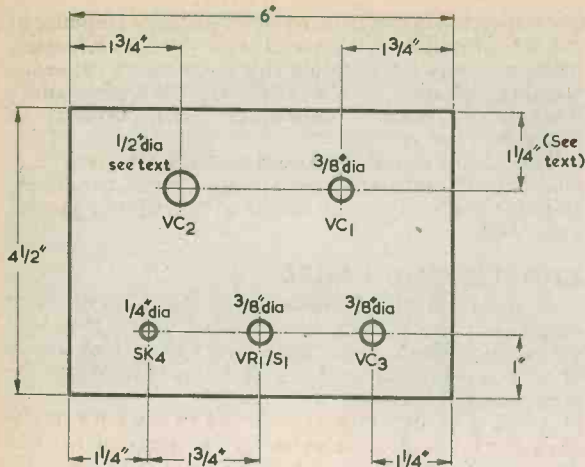


Fig. 3. The front panel is drilled out in the manner shown here

The front panel is illustrated in Fig. 3 and this should be cut out and the three lower holes only, those for SK4, VR1/S1 and VC3, drilled. The front panel is assembled to the chassis by the mounting bushes and nuts of these three components, and so the holes in the front panel must accurately match the corresponding holes in the chassis.

Temporarily assemble the chassis and panel together, then take up VC1 and check that the underside of its frame will be clear of the upper surface of the chassis when its spindle centre is $1\frac{1}{4}$ in. down from the top of the front panel, as indicated in Fig. 3. Working to manufacturer's specification there should be a little less than $\frac{1}{4}$ in. spacing between the capacitor frame and the chassis although in practice the spacing may be significantly greater than this. If there is adequate spacing, the holes for VC1 and VC2 may take up the positions shown in Fig. 3. If not, then the holes for these two components should be made slightly higher than is indicated in the diagram so that there will be no interference between VC1 frame and the chassis surface. There was no difficulty at all on this account with the prototype but, considering dimensional tolerances in home-constructed chassis and other factors, it is better to confirm that the position of the hole for VC1 spindle will be satisfactory rather than spoil the panel by drilling unwanted holes.

After confirming this point, the chassis and panel may be disassembled and the holes for VC1 and VC2 marked out.

VC1 is mounted by three 4BA bolts passing into tapped holes in the front plate of the capacitor, and three 4BA clear holes are required in the front panel. These holes are not shown in Fig. 3 and their positions may be marked out in the following manner. Cut out a $\frac{1}{4}$ in. hole in a piece of paper and pass it over the capacitor spindle. Mark the positions of the three 4BA tapped holes on the paper, then use this as a


template to mark out the corresponding holes in the panel. Drill these 4BA clear and lightly countersink them on the front. The three mounting bolts are short countersunk types and it is advisable to fit some washers or short spacers over them between the rear of the panel and the front plate of the capacitor. It is important to ensure that the ends of these bolts do not pass more than marginally beyond the capacitor front plate as they may then damage the fixed or moving vanes.

Since neither the fixed or moving vanes of VC2 are at chassis potential, this capacitor must have its mounting bush and nut insulated from the front panel. Fig. 3 shows the hole for VC2 as having a diameter of $\frac{1}{2}$ in. Insulating washers made of thin s.r.b.p. and having a $\frac{3}{8}$ in. hole can be fitted over the capacitor bush on either side of the front panel; the capacitor is then held so that its bush is approximately central in the panel hole as the mounting nut is tightened. After this process an electrical check is made with a continuity tester or ohmmeter to ensure that the capacitor bush is reliably insulated from the front panel. An additional measure which can be employed here is to initially affix one of the insulating washers to the front panel with adhesive, positioning it so that its hole is concentric with the $\frac{1}{2}$ in. hole in the panel. The capacitor bush will then be automatically centred in the panel hole.

WIRING

Fig. 4 shows the wiring for the basic receiver including that on the a.f. amplifier board. The latter employs a piece of Veroboard of 0.15 in. matrix having 15 holes by 10 copper strips. There are no breaks in the strips.

First drill the two 6BA clear holes in the Veroboard and then use it as a template for the marking out, and drilling, of the two corresponding 6BA clear holes in the chassis. The board takes up the approximate position, under the chassis, which is shown in Fig. 2. Next, assemble the components on the Veroboard, employing 0.15 in. Veropins for the external connections to S1, SK4 and the junction of R1 and C1. The board takes up its chassis connection from the sleeve contact

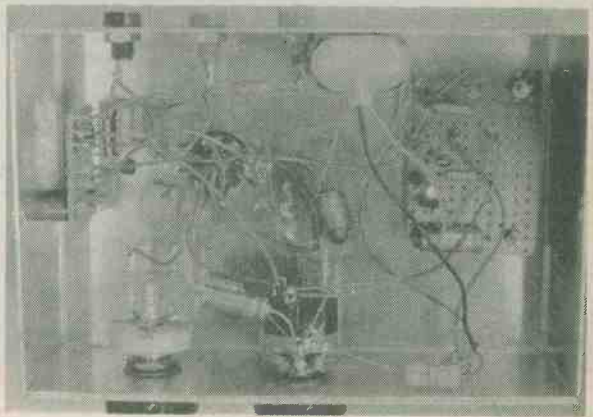

Layout of components and amplifier boards under the chassis

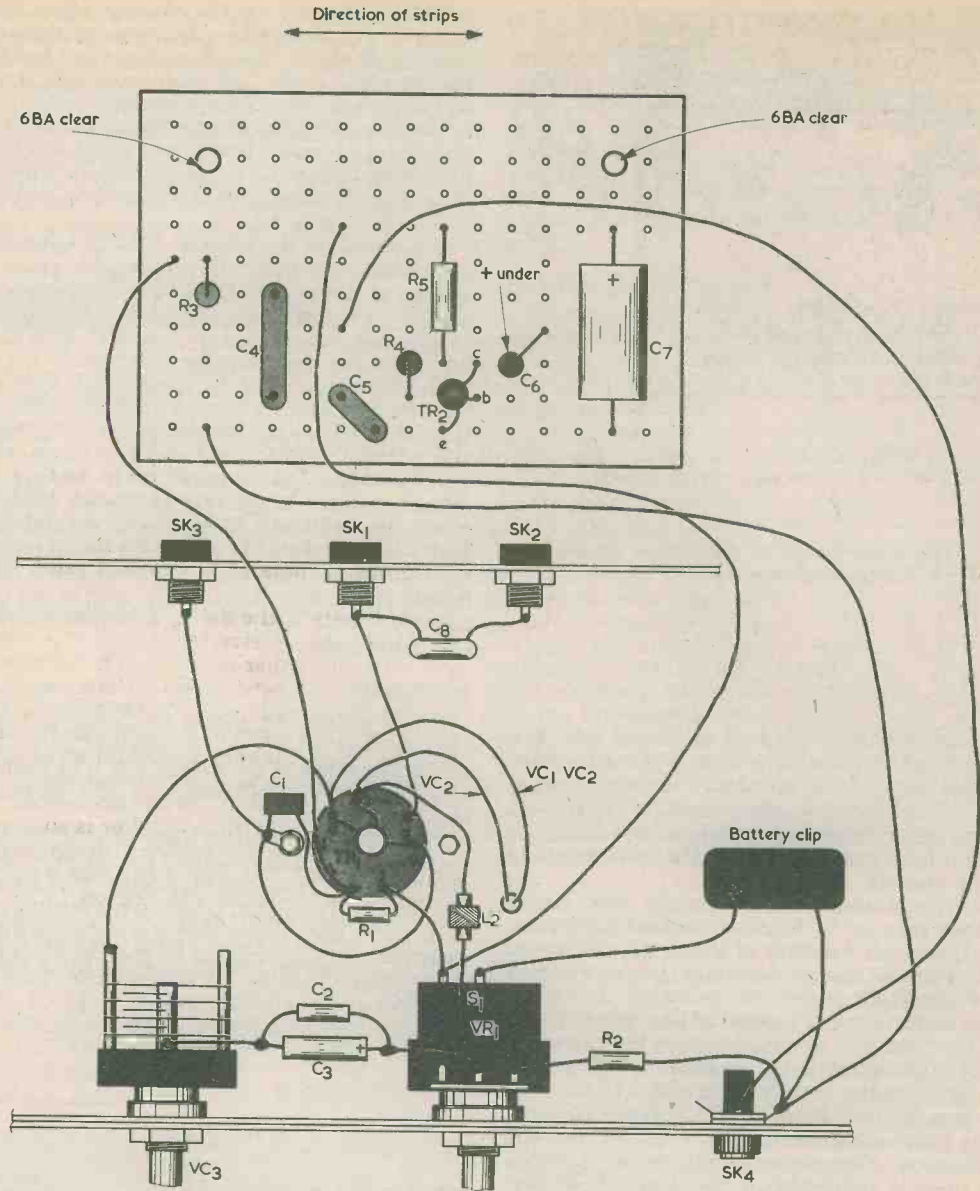


Fig. 4. Wiring diagram showing the connections around the B9A valveholder together with the component layout on the a.f. amplifier board


of SK4, and it is necessary for this socket to be of open construction (i.e. not insulated) so that this connection is automatically made by way of its mounting bush and nut.

The Veroboard is next mounted to the chassis, employing $\frac{1}{4}$ in. spacers on the mounting screws to keep the board underside clear of the chassis surface. All the remaining wiring shown in Fig. 4 is then completed.

Two wires pass through the chassis hole mentioned

when discussing Fig. 2. One wire, from the source of TR1, connects to the moving vanes of VC2. The other from TR1 drain, connects first to the fixed vanes of VC2, then to the fixed vanes of VC1.

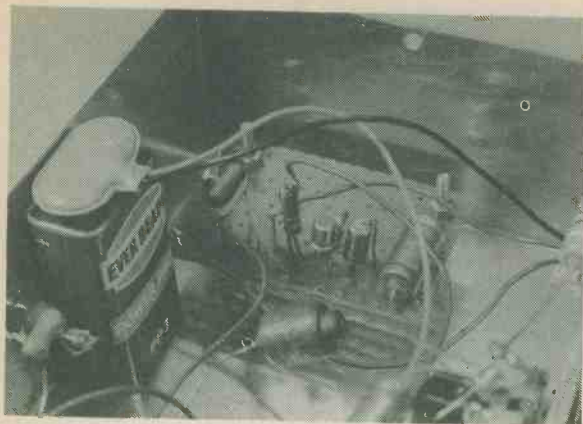There is plenty of space under the chassis for the battery, and it can be held in place by a simple clip or clamp. The four control knobs must be wholly or partly made of plastic. All-metal knobs cannot be used as they would allow the fingers to contact VC2 moving vanes when adjusting this capacitor.



A closer look at the a.f. amplifier board

USING THE RECEIVER

It is probably best to use the Range 4 coil when initially testing the receiver as there is usually a large number of strong signals present in this frequency range. The set operates most efficiently with VR1 turned back almost fully anticlockwise, with VC1 being advanced to a point that permits the detector to be brought to the threshold of oscillation when VR1 is slightly advanced. The receiver should always be adjusted to just below the point of oscillation by the use of VR1, as it is at this level that the receiver is most sensitive and has the highest degree of selectivity. If the regeneration is advanced beyond the threshold point proper reception of a.m. transmissions will not be possible, and heterodynes of varying pitch will be heard as the receiver is tuned across a.m. stations. Always carry out fine adjustment of regeneration by means of VR1, and not by VC2 which does not give such precise control.

Towards the low frequency end of each band it may be necessary to set VC2 at maximum capacitance and have VR1 well advanced in order to reach the threshold of oscillation. The circuit will still give good results, however, even though it will be operating at slightly less than optimum conditions. The regeneration controls are not like an ordinary volume control, and they will need resetting each time the tuning is significantly altered. It is well worthwhile spending some time experimenting with different settings of these controls in order to obtain the best possible results.

Do not try to accurately tune to stations by means of VC1. This is adjusted to the part of the band which is to be searched for stations, and then the tuning is carried out with VC3. As VC3 has a very low value it covers only a small part of each range, and tuning is much easier with this control.

It occasionally happens that a very strong signal blots out all the stations around it. If this happens, the aerial plug should be transferred from SK1 to SK2.

A suitable aerial for the set merely consists of a length of insulated wire set as high up as possible. A length of 10 metres or more is preferable, but as little as 3 metres will give reasonable results.

An earth connection will not be found necessary on Ranges 4 and 5, but it will considerably improve

results on Range 3. A simple earth connection can be made by attaching a length of wire to a piece of metal pipe which is then buried in moist soil. The free end of the wire connects to SK3, and this lead-in should be no longer than is necessary.

The Denco coils have adjustable iron-dust cores with threaded brass stems, and these are screwed fully down for packing purposes. If a signal generator is available the cores can be adjusted to give the approximate frequency ranges referred to at the start of this article. In the absence of a signal generator it will be in order to adjust each core so that about $\frac{1}{4}$ in. of the brass stem protrudes above the top of the former. This will give roughly correct frequency ranges and, as there is a large overlap between ranges, it is highly unlikely that there will be any gaps in the overall coverage.

R.F. AMPLIFIER

Satisfactory reception of s.s.b. and c.w. (morse) signals can be obtained by advancing VR1 to a point when the detector is just gently oscillating. VC3 is then carefully adjusted to resolve the s.s.b. signal or to obtain an a.f. note of the desired pitch with a c.w. signal.

Unfortunately, the detector oscillation will then be radiated by the receiver aerial and this can cause interference with other receivers. The solution is to add an r.f. amplifier between the detector and the aerial. The amplifier will prevent the detector oscillation from reaching the aerial, and will also give a small increase in gain which is very useful when only a short aerial is in use. It is essential that the r.f. amplifier be fitted if s.s.b. and c.w. reception is intended.

The circuit of the r.f. amplifier is shown in Fig. 5. This is a very simple untuned design employing a common source f.e.t. amplifier with its output connected to the coupling winding on L1. R7 and C9 provide supply decoupling.

The amplifier is assembled on a piece of Veroboard of 0.15in. matrix having 8 holes by 9 strips, as il-

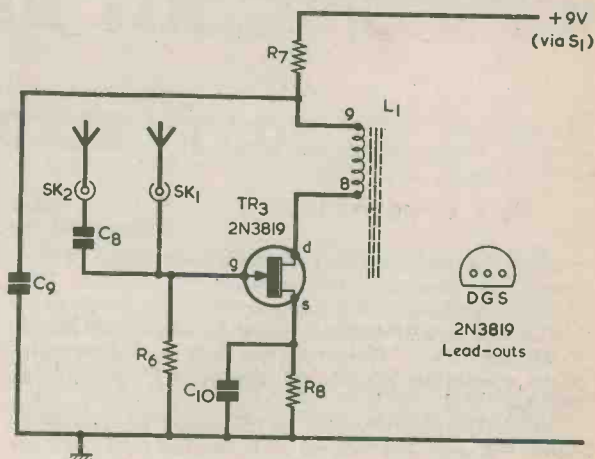


Fig. 5. The circuit of the untuned r.f. amplifier


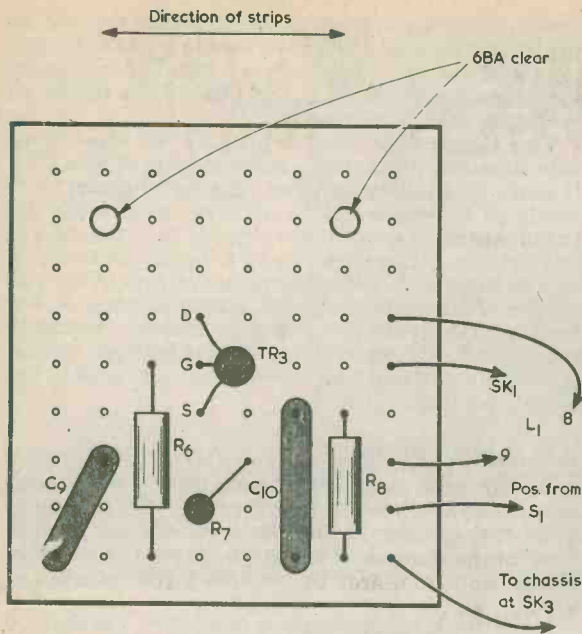


Fig. 6. The r.f. amplifier is assembled on a small piece of Veroboard as illustrated here

illustrated in Fig. 6. It is constructed, mounted and wired into circuit in the same manner as the a.f. panel, and it takes up the approximate position shown in Fig. 2.

Some small alterations are required in the wiring of

the basic receiver when the r.f. stage is added. The lead from SK1 to pin 8 of the coil is unsoldered from the valvholder and reconnected to the input of the r.f. amplifier board. TR1 gate lead-out and the chassis lead are disconnected from pin 9 of the coil and reconnected at pin 7. The board is then wired up as shown in Fig. 6, whereupon the receiver is once again ready for use, and the controls are operated exactly as before.

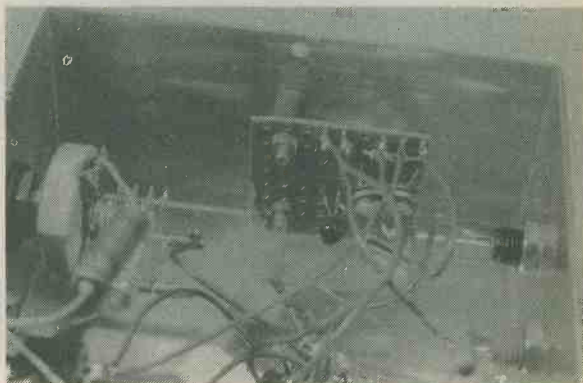

The optional r.f. amplifier board is mounted on one side of the chassis

The accompanying Components List gives details of the parts required for the complete receiver with the r.f. amplifier. If it is intended to build the basic two transistor receiver only there is no necessity to obtain R6, R7, R8, C9, C10 and TR3. ■

KIT REVIEW

JOSTY ELECTRONIC KITS

Now available in the U.K. is a wide range of electronic kits presented by Josty Kit (U.K.) Ltd., P.O. Box 68, Middlesbrough, Cleveland TS1 5DQ. Josty Kit is the largest manufacturer of electronic kits in Scandinavia and almost all the kits can be supplied with attractive "Module" cases of Scandinavian design.

There are over 50 kits in the range as well as 12 cases. The designs extend from simple t.r.f. medium wave receivers to a.f. amplifiers and disco equipment. Also included are f.m. tuners, stereo decoders, ambiphonic converters, electric guitar tremolo units and power supplies, as well as such items as photo cell

relay controllers, electronic roulette and a TV game.

Each kit is accompanied by an instruction book which discusses the components employed, deals with the assembly of the kit and then describes its technical functioning. In addition, the book gives notes on component handling, paying particular attention to the art of successful soldering.

Also available from Josty Kit is a book entitled "Applied Electronics", which has been especially produced for beginners and which includes a chapter describing 10 easily constructed projects. Nearly 200,000 copies of this book have been printed and it has appeared in 5 languages.

SHORT WAVE NEWS

FOR DX LISTENERS



By Frank A. Baldwin

Times = GMT

Frequencies = kHz

In addition to the broadcast bands, amateur frequencies can also provide much of interest to the all-rounder SWL. Listening to the local net 'ragchews' on the LF bands or Dx-chasing on the HF bands make a change from operating over the various broadcast bands. Recent forays on the amateur bands, using the CW mode, resulted in the following:

TOP BAND (1800-2000kHz)

DJ9LS, DL7CY, GD4BEG, GI3JEX, GM3YOR, HB0NL, HB9RM, K1PBW, KV4FZ, OK1ATP, OK1DUJ, OK2BPK, OL1AUQ, OL4ATY, OL5ATE, OL5AUZ, OL6AUE/P, OL8CGS, PA0HIP, W1BB/1, W1HGT, W8LRL, WA8IJI.

For the transatlantic signals, listen from around 0445 especially at weekends from 1800 to 1805kHz, 1802 and 1804 being the favourite "windows". For the signals of those from this side of the Atlantic trying to contact the U.S.A. etc., listen from 1830 to 1835kHz.

FORTY (7000-7100kHz)

CO2PY, HI8MOG, KP4EAJ, KP4CM, KP4WL, PY7DDA, UD6DII, VE3HUL, YV5BNR, ZL2ARN, ZL2UV, ZL3CC, ZL4CU.

These were all heard during late night or early morning sessions. At other times, "forty" is apt to be covered with CW signals from the USSR and Eastern Europe.

The writer does not find a great deal of time for amateur band operating but will from time to time report some of the Dx callsigns logged.

For those of my readers who aspire to collecting amateur QSL cards, equip yourselves to operate over the CW portions of the various bands — you will acquire a greater return reply ratio than reporting to SSB signals!

CURRENT SCHEDULES

● MONGOLIA

An External Service is radiated at various times throughout the period 1100 to 2125 from Ulan Bator. Probably the best times for listeners here in the U.K. would be as follows — from 1715 to 1745 (not Sundays) when in English to South East Asia and the Far East on 9574 and 11858 or from 1945 to 2015 (not Sundays, Mondays or Thursdays) when in French to the same areas on 17788 and 17860 or from 2100 to 2125 daily when in Standard Chinese on 7236 and on 7261. During these time periods the whole of the signal path is in darkness during this month.

● VIETNAM

The "Voice of Vietnam" operates a Domestic Ser-

vice from Ho Chi Minh City (formerly Saigon) from 2200 to 1605 on 6165 and 9620. The most favourable times for logging this transmitter would be from 2200 sign-on (at 2300 until 2330 the newcast is a relay of the Voice of Vietnam Domestic Service from Hanoi) and from around 1520 until 1605 sign-off.

● NIGERIA

The "Voice of Nigeria", Lagos, presents an External Service in English to Africa, the Middle East and Europe from 0655 to 0835, 1530 to 1700 and from 1800 to 1930 on 7275 and on 15120.

● CLANDESTINE

"Voice of the Eritrea Revolution" (in Arabic "Sawt ath-Thawrah al-Eritrea") is a pro-Eritrean Liberation Front transmitter operating on 9635 from 1500 to 1530 on Sundays, Tuesdays and Thursdays in Arabic. The location is thought to be Baghdad.

FOR THE SWL

● ALGERIA

Algiers on 11810 at 1850, a drama in Arabic in the "Voice of Palestine, Voice of the Palestine Revolution" programme, schedule from 1800 to 1900 and logged in parallel on 15150.

Algiers on 21565 at 1157, OM with song in Arabic, flute accompaniment, in an Arabic Network programme.

● PORTUGAL

Lisbon on 11925 at 1630, OM in Portuguese in a relay of the Domestic Service to the Azores, Madeira and Cape Verde Islands, scheduled from 0700 to 2400.

● ROMANIA

Bucharest on 15250 at 1309, OM and YL alternate with the news in English. English to Europe programme, schedule 1300 to 1330 and in parallel on 9690 and 11940.

● EGYPT

Cairo on 7050 at 1905, OM with the news in Arabic in the "Voice of the Arabs" programme. Also in parallel on 11630.

● ISRAEL

Jerusalem on 9355 at 2058, OM with a talk in Hebrew in a relay of the Domestic Service Network B to overseas listeners, schedule from 2000 to 2305. Also

in parallel on 12077.5 and 15512.5 (measured).

● **S. YEMEN**

Aden on 11770 at 1815, OM with a song in Arabic and some local-style music under QRM.

● **N. YEMEN**

Sana'a on 9780 at 1806, typical local music, songs in Arabic in the Domestic Service, also in parallel on 4853.

● **VIETNAM**

Hanoi on 6450 at 2249, YL with songs in Vietnamese, chorus and orchestra in the Domestic 1st Network and to the former South Vietnam. Schedule from 2055 to 1600 and in parallel on 7375.

● **ANDORRA**

Radio Andorra on 6230 at 0801, pop records (U.K. made) after identification by OM (Sunday morning).

● **AFGHANISTAN**

Kabul on 15195 at 1141, YL with listeners letters answered in the English to Europe programme, schedule from 1130 to 1200.

● **NORTH KOREA**

Pyongyang on 6600 at 2105, OM and YL alternate with the news in Korean in the Domestic Service, schedule from 2000 to 0830.

Also on a measured 6398 at 1958 when opening one of the daily transmissions with repeated chords on an organ as interval signal, identification in Korean by OM, 3 pips time-signal and National Anthem. This is the Domestic Service beamed to South Korea from 1500 to 1800, 2000 to 2130 and from 2200 to 1030.

● **KUWAIT**

Radio Kuwait on 15345 at 0530, YL with news of the Arab world in English to East and Southeast Asia, scheduled from 0500 to 0800.

● **EGYPT**

Cairo on 17625 at 0612, OM with chants and readings from the Holy Qur'an in the Palestine Service, scheduled from 0600 to 0800 and also in parallel on 15475 and 17745.

Cairo on 15135 at 1311, a programme of Arabic songs and music in the "Sudan Corner" transmission, schedule from 1200 to 1625.

● **SUDAN**

Omdurman on 11835 at 1339, OM with songs in Arabic, local-style music.

● **GREECE**

Athens on 9760 at 1139, OM in Arabic in a programme directed to Egypt and Libya, scheduled from 1130 to 1150.

FOR THE DX'ER

In which are listed some of the transmissions that may be of interest to the Dx'er.

● **BURMA**

Rangoon on 5039 at 1547, orchestral music Euro-style, hetro QRM. Rangoon is the capital city of Burma and is situated on the eastern arm of the Irrawaddy delta. The city has two cathedrals and many pagodas.

● **INDIA**

Lucknow on 3205 at 1550, OM in vernacular amid

very heavy commercial QRM. Generally speaking, if you can hear this one then the remainder of the Indian transmitters on the 90 metre band may be logged — QRM permitting of course! The power is 10kW, schedule from 0025 to 0215 and from 1130 to 1830.

● **SRI LANKA**

Colombo on 4902 at 1840, Buddhist chants on full moon day. This is Channel 1 of the Sinhala Service which is scheduled from 0015 to 0230, 1125 to 1730 and additionally on full moon days from 1030 to 0800. The power is 10kW.

● **NEPAL**

Katmandu on 5007 at 1543, OM in Nepali, local music and song by YL. The schedule is from 0020 to 0350 and from 1150 to 1720 and in parallel on 3425: the power is 5kW. Katmandu is the capital of Nepal and is sited on the Vishnumati River some 75 miles from the Indian frontier.

● **INDONESIA**

Jakarta on 4805 at 1550, YL with local song in Malindo through CW QRM. This is the Home Service of RRI with a schedule from 2155 to 0100 and from 1000 to 1600, the power is 20kW.

● **MALAYSIA**

Penang on 4985 at 1540, programme of classical music Euro-style. This is the English/Vernacular service of Radio Malaysia, the schedule here being from 2230 to 0130 (Sundays to 1630), from 0530 to 0630 (Saturdays till 1630) and from 0930 to 1630, the power is 10kW.

● **CHINA**

PLA Fuzhou on 3535 at 2015, YL in Standard Chinese under hetro QRM. This transmission, like that following, is directed to Taiwan and other offshore islands. The schedule on this channel is from 1413 to 2241.

PLA Fuzhou on 4045 at 2030, OM in Standard Chinese under unmodulated carrier. The schedule here is from 1000 to 0530.

Lanzhou on 4865 at 2327, YL in Standard Chinese. The schedule is from 2150 to 0600 and from 0950 to 1600.

● **RWANDA**

Radio Kigali on 3330 at 0519, African orchestra, YL's with chants. This is the Home Service, scheduled from 0300 to 0600 (Saturdays and Sundays until 0700), 0900 to 1200 (Saturdays and Sundays until 2100) and from 1330 to 2100, the power is 5kW.

● **COLOMBIA**


Emisora Nuevo Mundo, Bogota, on 4755 at 0525, OM with the local news in Spanish, many mentions of Bogota. This one has a 24-hour schedule and sometimes identifies as "Radio Caracol"; the power is just 1kW.

● **BRAZIL**

Radio Timbira, Sao Luiz, on 4976 at 2134, OM with announcements in Portuguese, local songs and music. The schedule is from 0700 to 0430 and the power is 5kW.

● **NOW HEAR THIS**

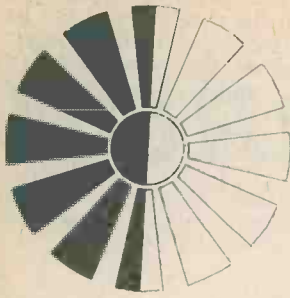Clandestine "Radio Iran Courier" on 11415 at 1802, OM with a harangue in Farsi. The schedule is from 1720 to 1810 and also in parallel on 11695. It is not Dx but it is interesting!



THE OSCAR SATELLITE PROGRAMME

THE FUTURE

By Arthur C. Gee

In the September 1976 AMSAT Newsletter, Vol. 7, No. 3, p.3 the following note appears: "In professional circles it is customary to call a spacecraft by one name prior to launch, and then give it its flight name after it leaves the ground. In the past we at AMSAT have also tried to keep to that custom. In the past when we were building one spacecraft at a time, it did not really matter if a spacecraft was called AMSAT-OSCAR B or AMSAT-OSCAR 7."

"Following the announcement of the Phase III satellite programme there has been a tendency to use OSCAR 8 and Phase III interchangeably. Again if only one spacecraft was in the works this would not really matter. But, now there are more than one spacecraft in the works. The launch of the FIRST Phase III spacecraft has slipped to about 1980. There is serious thought to a Phase II or AMSAT-OSCAR 6/7 follow on to replace AMSAT-OSCAR 6 and a lot of talk is coming from AMSAT-UK on the feasibility of a 21/28 MHz transponder communications satellite, also in the Phase II series."

"Thus at this time, no one is sure what AMSAT-OSCAR 8 will be, so let's refer to the spacecraft by the correct nomenclature."

The author has endeavoured to keep to the spirit of this note in the information given here. — Ed.

With OSCAR 6 and OSCAR 7 still "going strong" and with plans for the first Phase III OSCAR being somewhat uncertain, (see page 149, 'R. & E. C.' Oct. '76), it was interesting to receive from AMSAT-UK recently, a handout outlining the future possibilities for forthcoming OSCARs.

Quite apart from the Phase III OSCAR, there are a number of other amateur satellites, some only in the planning stage; others actually under construction, which might be launched in the near future.

AMSAT-USA A.O.D. is well advanced and could be launched in June 1977 from one of the ITOS Mission rockets, which may be launched around June '77. It is virtually identical to OSCAR 6, being a 2 to 10 metre repeater, but has more solar panels than 0.6, so that it could be used full time and would not need turning off from ground control to conserve batteries, as has to be done with 0.6. It would help to fill the gap until OSCAR Phase III is launched, particularly if 0.6 fails completely in the near future. OSCAR 6 has already outlived its expected life-span by many months!

JAMSAT 2—70. This is a Japanese planned amateur satellite with a 2 watt 70cm downlink and 2 metre uplink. The transponder unit has been built and is being tested on a mountain top by AMSAT-JA. The Japanese may launch this themselves or it could be launched along with the AMSAT-USA A.O.D. mentioned above, on the June ITOS Mission.

AMSAT-USA PHASE III OSCAR. This is the highly sophisticated satellite now under construction and described in this magazine in the issue for June 76, p.690. Not surprisingly, a satellite as sophisticated as this is taking rather longer than anticipated to progress and its possible launch date has been advanced to 1980.

"THE SHUTTLE". This spacecraft is being planned for ferrying personnel and equipment to manned orbital platforms. The first may be launched in 1979. They are planned for low orbits — around 300 miles, so the possibilities of satellites being launched from them are limited. However, the proposed AMSAT-UK 15-10 metre satellite might make use of them for propagation research and night-time path communication during low MUF years.

AMSAT-UK 10-15 METRE SATELLITE. A proposal has been put forward by some OSCAR enthusiasts in the U.K. for the design and construction of a satellite operating on the 10 and 15 metre bands. Suitable components, a qualified designer, and time and facilities to build it will all have to be found before this project can materialise. However, if these difficulties can be overcome, the project could be launched from The Shuttle.

THE "ARIANE" LAUNCHES. The European Space Agency are planning three launches from their Koror launching site in French Guiana, commencing 1979, upon which on-load space is available. The AMSAT-USA Phase III OSCAR might well be launched from one of these.

So we see that there are numerous possibilities for continuing the OSCAR Project and there is likely to be continued activity on an extensive scale in this field of amateur radio. Just what the next OSCAR will be, we shall have to wait and see. It will obviously depend on the progress made with the various projects and how this progress fits in with facilities for launching.

CURRENT MIRROR

By M. G. Robertson

Background details on a common integrated circuit constant current source.

A rather puzzling configuration which is often seen in the internal circuitry of linear i.c. operational amplifiers is shown in Fig. 1(a). Here, there are two n.p.n. transistors with their emitters connected to the negative supply rail for the amplifier. The two collectors are in the supply feeds to internal stages or components in the amplifier. The two bases are connected together, and the collector of one transistor is also taken to the common base connection.

A p.n.p. version of the configuration, with emitters connected to the positive rail, appears in Fig. 1(b).

CURRENT MIRROR

The configuration is a "current mirror" circuit, and its operation can be explained with the aid of Fig. 2. In this diagram the two transistors are silicon and have identical characteristics. This latter requirement can be very closely approached in two adjacent transistors on a silicon chip. It has to be remembered that the collector of a conductive silicon transistor can assume a potential with respect to its emitter which is lower than that at its base.

In Fig. 2 nearly all of the current I_1 flows into the collector and base of TR1. Most of the current flows into TR1 collector and the only current flowing into TR1 base is that which is required to maintain the

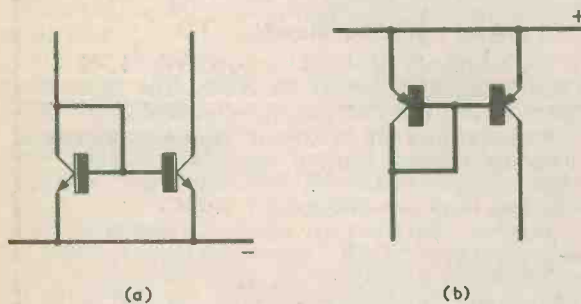


Fig. 1(a). This circuit detail is frequently encountered in i.c. operational amplifiers
(b). P.N.P. version of the configuration

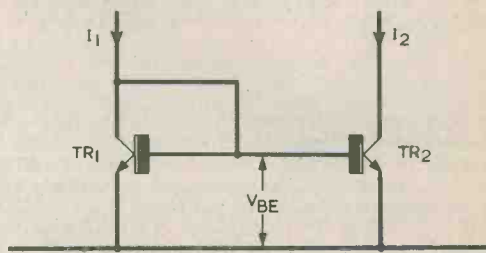


Fig. 2. The collector currents and base-emitter voltage at the two transistors

collector current. The collector and base assume a potential V_{BE} with respect to the negative rail which is of the order of 0.6 to 0.7 volt.

The base of TR2 takes up this potential also. A small current flows through the base-emitter junction of TR2, this adding to that flowing into the collector and base of TR1 to constitute the whole of I_1 . Since a current flows into the base of TR2 this transistor passes a collector current I_2 . The two transistors are identical and so, at a common value of V_{BE} , I_2 is equal to I_1 (less the small base currents).

If I_1 is increased the value of V_{BE} will rise slightly, causing I_2 to increase to the same level as I_1 . Similarly, if I_1 is decreased, V_{BE} drops slightly and I_2 falls to the same value as I_1 .

The functioning of the circuit can alternatively be described without referring to changes in V_{BE} . As the two transistors are identical each base-emitter junction presents the same forward resistance to current flow. In consequence the current available for the two base-emitter junctions divides equally between them.

TR2 functions as a constant current source, and the value of the constant current, I_2 , is controlled by the amplitude of I_1 . The constant current may be of the order of 1mA or less.

The p.n.p. version of Fig. 1(b) functions in the same manner as that described in Fig. 2 except that the potentials and directions of current flow are reversed.

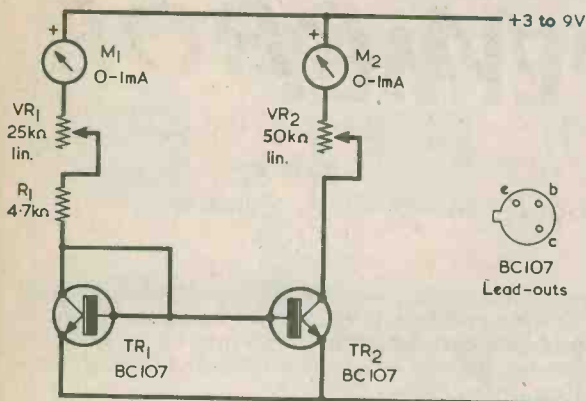


Fig. 3. A test set-up employed for evaluating the performance of discrete transistors in the circuit

PRACTICAL CIRCUIT

The configuration can be made to work quite well with two discrete transistors even when these have markedly different characteristics.

The author made up the test circuit shown in Fig. 3 employing BC107's. The current in TR1 could be varied by means of VR1, with R1 acting as a current limiting resistor to prevent the accidental flow of excessive current in meter M1. The current passed by TR2 was measured by M2, with VR2 being adjusted over the appropriate section of its track to assess constant current performance.


Half a dozen BC107's of varying make and age were tried in the TR2 position. In every case the current in TR2 increased and decreased in sympathy with the current in TR1, but with no transistor was TR2 collector current equal to TR1 collector current. The greatest discrepancies were given when TR2 collector current was about 40% of TR1 collector current and when TR2 collector current was about 120% of TR1 collector current. With one pair of transistors, TR2 collector current was approximately 90% of TR1 collector current.

All the transistors in the TR2 position gave good constant current performances at collector currents of 0.3mA and less, with two working well in this respect up to 0.45mA. At higher collector currents the constant current performance was poor or virtually non-existent with all transistors.

The discrete transistor circuit of Fig. 3 has the practical advantage that it is capable of providing a low constant current with a minimum voltage drop of 0.2 volt across TR2. There is no thermal coupling between the two transistors as is given in an integrated circuit but, at the low currents involved, the transistors should run virtually at room temperature. The current flowing in TR1 has to be pre-set to a value which takes up the different characteristics of the particular transistor employed for TR2.

BUY THIS BEST SELLER

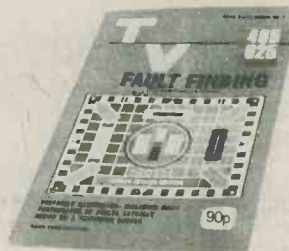NEW EDITION
OF
T.V. FAULT FINDING
405/625 LINES



REVISED & ENLARGED

Edited by J. R. Davies

132 pages

PRICE 90p

Over 100 illustrations, including 60 photographs of a television screen after the appropriate faults have been deliberately introduced.

Comprehensive Fault Finding Guide cross-referenced to methods of fault rectification described at greater length in the text.

Price 90p from your bookseller.

or post this Coupon together
with remittance for £1.08
(to include postage) to

DATA PUBLICATIONS LTD.
57 Maida Vale, London, W9 1SN

Please send me the 5th revised edition of TV Fault Finding. Data Book No. 5

I enclose cheque/crossed postal order for

NAME

ADDRESS

BLOCK LETTERS PLEASE

MEDIUM WAVE DX SUPERHET

The concluding article deals with the assembly of the mixer and oscillator stages, the i.f. amplifier, the a.f. amplifier and the S-meter circuit. The process of alignment is then described.

Part 2
By R. A. Penfold

In the article which appeared in last month's issue the circuit of this sensitive and selective receiver was discussed, after which constructional details were given for the case and chassis. Next to be dealt with is the mixer-oscillator wiring.

MIXER-OSCILLATOR

The mixer-oscillator wiring is carried out under the chassis, as illustrated in Fig. 4. The two trimmer capacitors are mounted by having one tag soldered to a chassis tag and the other to the appropriate valveholder tag.

For clarity the wiring is shown spread out in Fig. 4 but in practice component leads should be kept fairly short. All components and wiring should be within $\frac{3}{4}$ in. of the chassis underside, as they will otherwise

come into contact with the bottom cover of the case. All wiring other than component lead-outs should be insulated. Component lead-outs may be covered with sleeving if there is any risk of their touching other wires or the chassis.

Four wires pass through the chassis. Two of these connect to the fixed vane tags of VC1 and VC2. Of the remaining two, one carries the positive supply from the i.f. board whilst the other is the connection from TR1 drain to the mechanical filter, which is also on the i.f. board.

Although the 40673 is a MOSFET it can be wired into circuit in the same manner as an ordinary bipolar transistor, since internal protective diodes are connected to its gates. The manufacturer states that the soldering iron bit used for soldering it into circuit must be earthed.

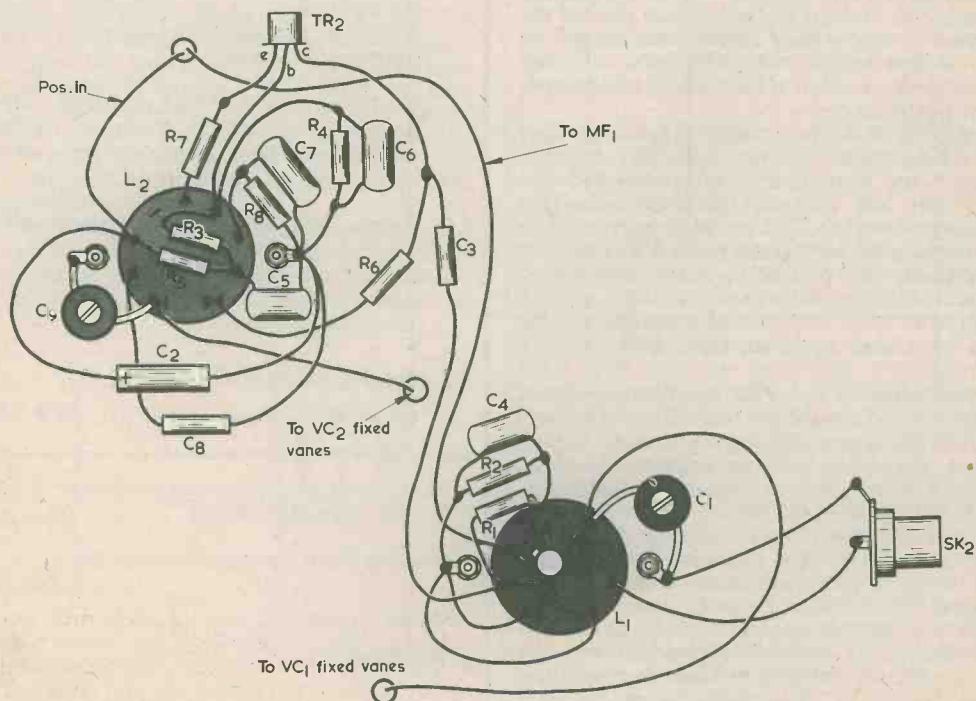


Fig. 4. Under-chassis wiring for the mixer and oscillator stages


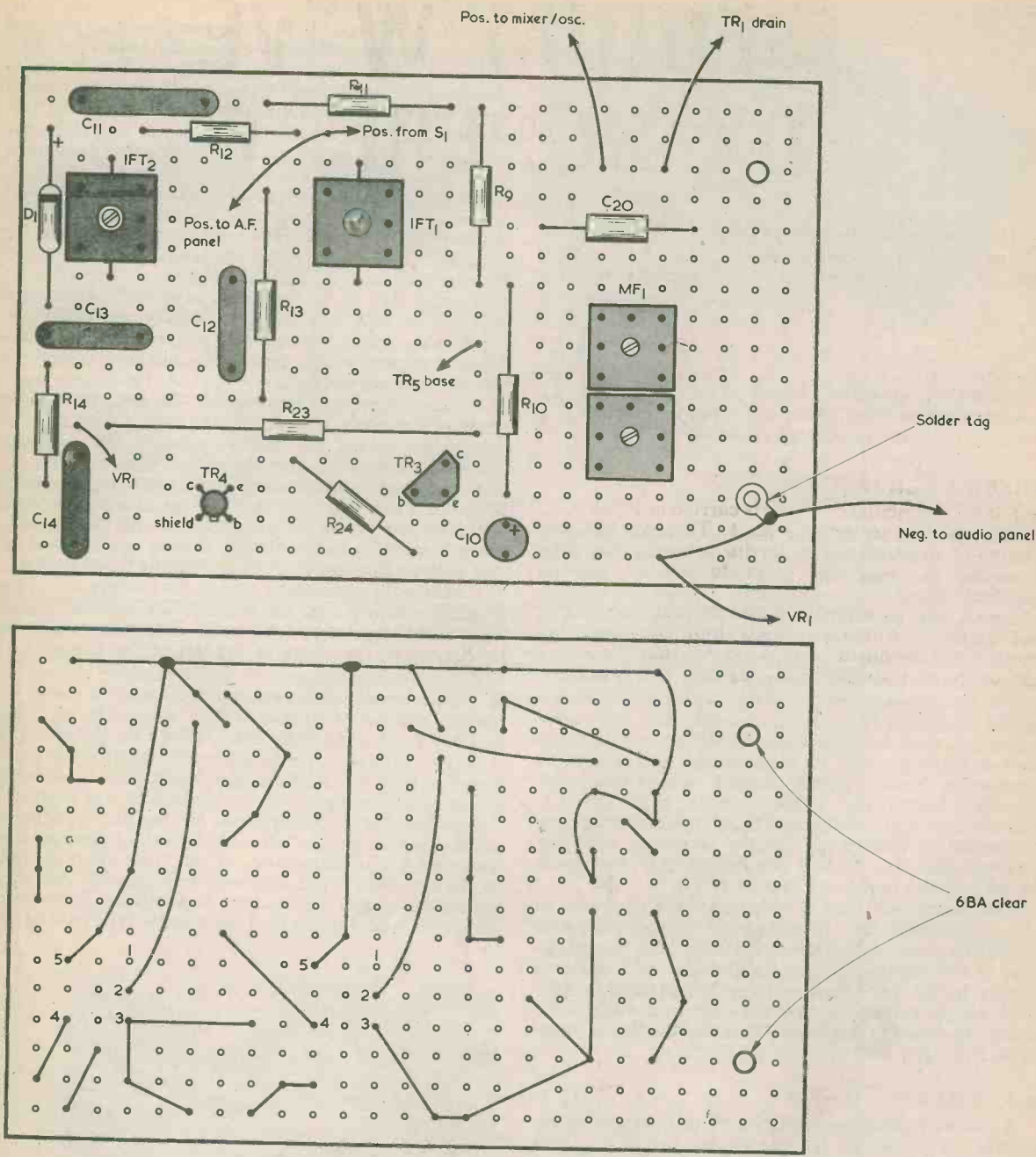


Fig. 5. The component and wiring sides of the i.f. amplifier board

I.F. BOARD

Fig. 5 shows the component and wiring sides of the i.f. board. The components are assembled on a plain Veroboard of 0.15in. matrix measuring 3 3/4 by 2 1/2 in. This is a standard size in which the board is sold. Veroboard of 0.15in. matrix is ideal for the present application as it can be easily adapted to accept both the Denco i.f. transformers and the mechanical filter.

Before fitting any components, drill out the two 6BA clear mounting holes. The board may then be used as a template to enable the corresponding holes in the chassis to be marked out and drilled. The board takes up the position shown in Fig. 3 (published last month). Some of the holes in the board next have to be enlarged to enable the i.f. transformers and mechanical filter to be fitted. A No. 42 drill, or

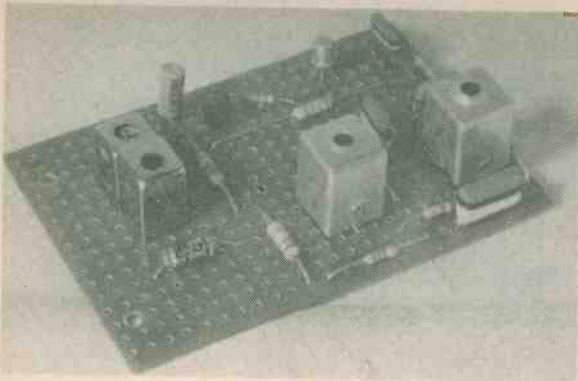

The i.f. amplifier board. This takes the mechanical filter, the two i.f. transformers and their associated components

similar, is used to do this. All seven holes for each Denco i.f. transformer must be enlarged but only those for the mounting lugs of the filter and its matching transformer need to be altered. As may be gathered, the mechanical filter actually consists of two parts, the filter proper and its matching transformer. 0.15in. Veropins are fitted at the points where external connections are made to the board.

The components are now fitted and wired as shown in the diagram. Sleeving is passed over any wires which run close to other wires. In some cases the component lead-outs will be long enough to reach their connecting points. Tinned copper wire is employed for the remaining wiring. Note that the i.f. transformer and mechanical filter mounting lugs are connected to chassis so that the screening cans are earthed. Also, the chassis connection to C11 is made by way of the mounting lugs of IFT2.

The completed panel is mounted to the chassis with $\frac{1}{2}$ in. spacers over each mounting bolt to keep the panel underside clear of the chassis surface. With the exception of the leads carrying the positive and negative supply to the a.f. board and that connecting to TR5 base, all the external connections are now made. VR1 should be fitted to the front panel and the two connections from the board are to its track.

A.F. BOARD

A piece of plain perforated s.r.b.p. board of 0.1in. matrix is employed for the audio amplifier. This board has 22 by 14 holes and it must be carefully cut down from a larger piece by means of a hacksaw. The two 6BA clear mounting holes are drilled out and the board is then used as a template to mark out and drill the corresponding holes in the chassis, with the board taking up the position shown in Fig. 3. The components are then mounted and wired as illustrated in Fig. 6. Veropins are fitted for external connections. If the board is of Vero manufacture the pins should be 0.1in. Veropins; if it is of different manufacture, 0.15in. Veropins will be found to give a better fit.

The board is then mounted on the chassis in the same way as was the i.f. board, and all the external wiring to it is completed.

S-METER BOARD

In the prototype the S-meter components are wired up on a piece of plain 0.15in. Veroboard having 14 by 10 holes. Details are given in Fig. 7. The board is mounted on the S-meter terminals themselves, two of the Veroboard holes being enlarged to take the terminal screws. If the meter employed has different spacing between its terminals than has that employed by the author the Veroboard layout is modified accordingly, and it may be necessary to use a larger piece of board. The same general layout may still be employed. 0.15in. Veropins are fitted to the board for external connections. After the board has been wired up and mounted, its external wiring is completed. At this stage R17 is set to insert maximum resistance into circuit, with its slider turned fully anticlockwise.

The two track tags of VR2 are connected to the positive supply at S1, and to the negative supply at the earthed tag of VR1.


As was mentioned last month, the S-meter can be omitted if desired, whereupon the meter, VR2 and the component panel are not required. This will not adversely affect the performance of the receiver.

A solder tag is fitted to one of the mounting screws of M1, and a lead from the earthed tag of VR1 connects to this to provide an earthing point for the front panel. If the S-meter is to be omitted, the tag can be fitted on one of the mounting bolts of the tuning drive instead.

It then only remains to wire in the battery clip. The negative battery lead connects to the earthed tag of VR1 and the positive lead to S1. The battery can be positioned in the space to the left of the chassis.

The current consumption of the receiver is about 9 to 10mA under quiescent conditions, this rising to peaks in excess of 100mA at high volume levels. The unit can be economically run from a PP3 battery if it is only to be used with headphones or with a modest power output to a loudspeaker. For higher volumes it would be advisable to use the larger PP6 size battery.

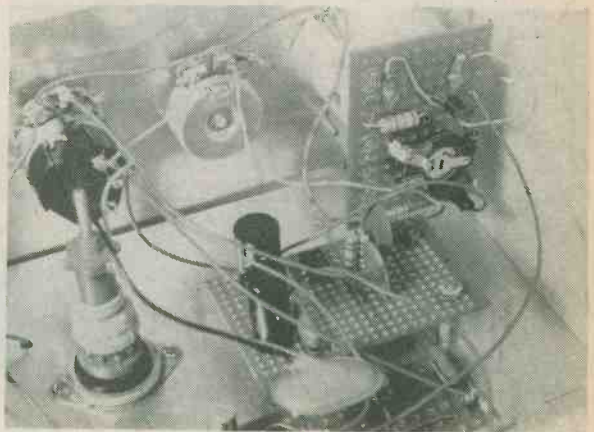Any speaker or headphones having an impedance of 8 Ω or more can be connected to the output of the receiver. A load impedance of less than 8 Ω must not be used as this could overload and possibly damage the output stage. The output is available from jack socket SK1, and if this is of the normal type having an



The S-meter and a.f. amplifier boards mounted in position. The S-meter board secures directly to the meter terminals

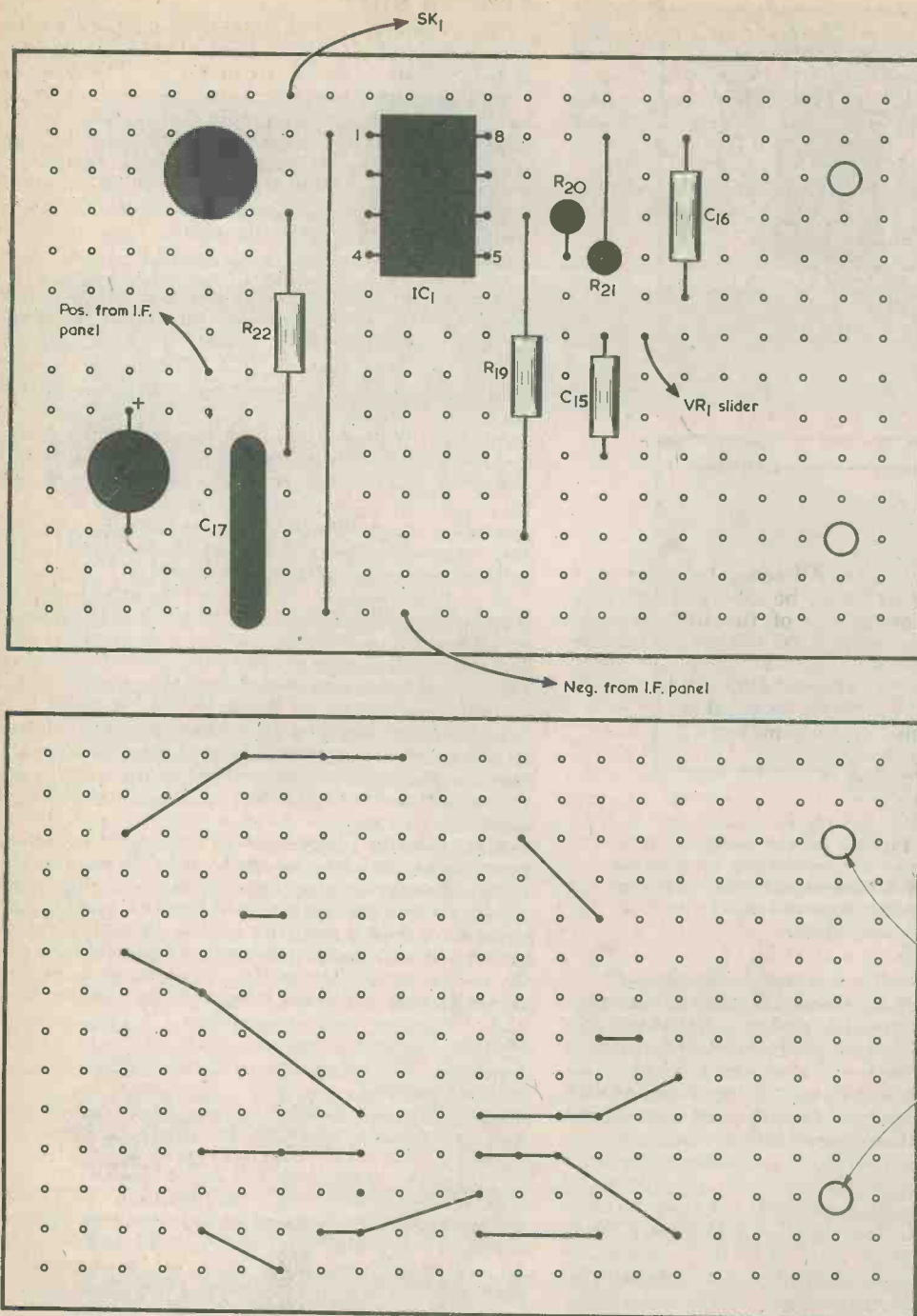


Fig. 6. Due to the use of an integrated circuit the a.f. amplifier board is quite simple to wire up and requires few discrete components

open construction the sleeve connection to chassis will be automatically provided by its mounting bush and nut. A slight disadvantage given by using a jack socket for the output connection is that the two con-

tacts can be momentarily short-circuited when a plug is inserted or withdrawn. In consequence, volume should be turned to a low level whenever a plug is fitted or removed.

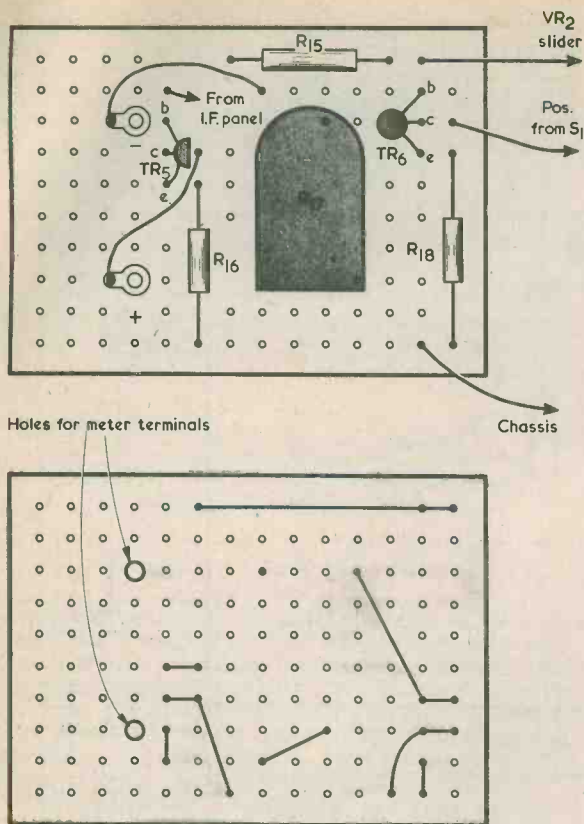


Fig. 7. Apart from VR2, all the components in the S-meter circuit are assembled on a board which is secured to the back of the meter by the meter terminals

ALIGNMENT

Testing and alignment can be carried out with the aid of a few feet of wire acting as an aerial. A suitable loudspeaker or pair of headphones should be plugged into the output socket.

For packing purposes, L1 and L2 are supplied with the brass threaded stems of the iron-dust cores screwed fully down. Adjust the core of L1 so that about $\frac{1}{2}$ in. of the threaded stem protrudes above the former, and adjust the core of L2 so that about $\frac{3}{4}$ in. protrudes. Set C1 to about half capacitance and C9 close to maximum capacitance. If 10-60pF trimmers are being employed, C1 is set to about a third of maximum capacitance and C2 to about two-thirds maximum capacitance. Set VR2 so that its slider is at chassis potential.

Switch on. M1 should immediately give a forward indication, whereupon VR2 is adjusted to zero the meter.

Adjusting the tuning capacitor should enable a few stations to be received although, even with VR1 nearly fully advanced, the volume may not be very high at this stage. Tune accurately to one of these stations, using the S-meter as a tuning indicator. If the S-meter is not fitted, a tuning indicator can be provided by an electronic voltmeter or a multimeter having a sen-

sitivity of 20k Ω per volt or more on its voltage ranges. The positive test lead of the meter is connected to the junction of R9 and R10 and the negative lead to chassis, and its reading reduces as signal strength increases.

The cores of the Denco i.f. transformers must be adjusted with a proper trimming tool and not with an ordinary screwdriver, which could easily damage them. A suitable trimming tool is the Denco type TT5. The cores of the mechanical filter and its matching i.f. transformer are very different in construction and a small screwdriver can be safely employed for their adjustment. Care must nevertheless be observed as the cores are made of ferrite and are rather brittle.

The cores of IFT1 and IFT2, and those of the mechanical filter and its matching transformer are now carefully adjusted for maximum signal strength. It will be found that the filter core adjustment is much less critical than is that of the transformers. Repeat the procedure several times until no further improvement in sensitivity can be obtained.

R.F. alignment commences by adjusting the core of L2 to give the correct coverage at the high frequency end of the band. Should a reasonably accurate signal generator be available, this can be used to set the limit of high frequency coverage at 1.6MHz.

If no signal generator is to hand the adjustment can be made after darkness has fallen, when the medium wave band is usually crammed with stations. With the tuning capacitor set for minimum capacitance, the core of L2 is unscrewed until short wave marine stations are heard in place of the medium wave broadcast stations. The core is then screwed back until a medium wave station is once again received. L2 then has the correct setting. If the receiver seems a little insensitive, the core of L1 can be adjusted to peak sensitivity.

Next tune the receiver to a station near, but not fully at, the high frequency end of the band. Choose a station that has a fairly constant signal strength, then adjust C1 for maximum signal. Find a station of fairly constant strength near the low frequency end of the range, with the tuning capacitor vanes almost fully enmeshed, and then adjust the core of L1 for optimum signal strength. Retune to the station at the high frequency end and readjust C1, then return to the low frequency end and readjust the core of L1. Continue this procedure until no further improvement is possible.

It will be noted that trimmer C9 is not adjusted during the alignment just described. If, however, it should be found that the coverage at the low frequency end of the range is obviously too small or too great, this can be corrected by a readjustment of L2 core at the low frequency end and an adjustment of C9 to set the limit at the high frequency end. C1 and the core of L1 will then have to be reset, in the manner just described, to take up the altered oscillator range.

R17 is adjusted with the receiver connected to a proper aerial. The strongest signal available is tuned in and R17 is then adjusted so that the meter reading is slightly above the S-9 point, or is at about 0.75mA if an ordinary 0-1mA meter movement is employed. Should it be subsequently found that another very strong signal causes the meter needle to overshoot the end of the scale, R17 is set to insert a little more series resistance.

This completes the alignment and adjustments needed in the receiver, which is now ready for use.

AERIALS

An ordinary long wire aerial can be used with the receiver, but better results will in many cases be obtained with some form of ferrite or frame aerial. These have the advantage of being directional.

The directional property is particularly useful, as it will frequently be found that two stations are received on virtually identical frequencies. The directivity of the aerial then often permits one of the stations to be nulled, producing intelligible reception of the other.

Employing a directional aerial that has to be tuned

has the disadvantage that it is necessary to adjust the aerial tuning every time the setting of the receiver tuning is significantly altered. This disadvantage is more than outweighed, however, by the freedom from breakthrough of spurious responses that a tuned aerial produces. It also reduces cross modulation by reducing the r.f. bandwidth.

A suitable preselector will be described in next month's issue, and this will feature an internal ferrite aerial and a dual gate MOSFET r.f. stage.

(Concluded)

Trade News . . .

BLOB BOARD

S-DeC manufacturer, P. B. Electronics, 57 High Street, Saffron Walden, Essex, has launched a new concept in prototype printed circuit boards.

Normally half the price of previously competitive boards, they allow the user to go direct from circuit diagram to completed board in a matter of minutes and without the use of messy chemicals.


Component layout can be drawn direct onto the Blob Board eliminating many of the errors which can occur in transferring from circuit diagram to ordinary PCBs.

Blob Board is extremely simple to use. Draw component layout on the Blob Board pattern using an ordinary felt pen. Lay components over their respective drawings and 'Blob' on some solder making the final soldered joint.

Components can be re-used and re-soldered making circuit prototype modifications and amendments both fast and easy.

All Blob Boards are roller-tinned to facilitate easy and reliable soldering.

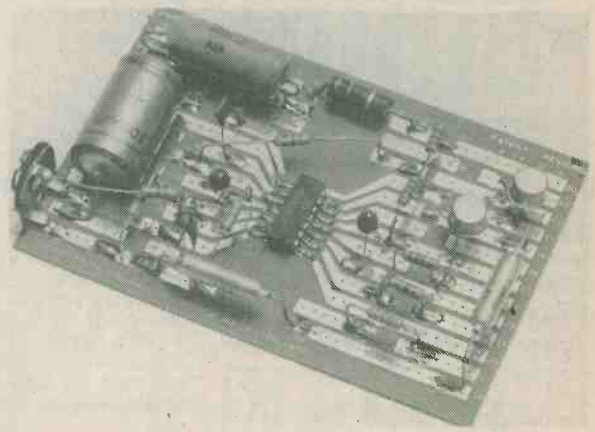Initially, there are twelve different Blob Boards available in a wide variety of patterns which, between them, will accommodate all components from discretes to ICs. One pattern for example, matches the S-DeC modular bread-board connections.



One of the twelve new Blob Boards launched by P. B. Electronics Ltd., showing a finished prototype.

The smallest discrete Blob Board (there are others for ICs) measures 3.6 x 2.4 in. and costs only 20p.

Blob Boards come in a range of standard sizes which match those already accepted by both professional prototype engineers and hobbyists. No drilling or special mounting of components is necessary and all Blob Boards are re-useable.

CLOSED CIRCUIT TV EXPORT ORDER

Crow of Reading Limited have received an export contract, valued at £40,000, for planning, design, installation and commissioning of a comprehensive close-circuit television system for the Kuwaiti stock exchange.

This system will enable dealers and members of the stock exchange to review central display boards and teleprint machines directly from their offices, and is expected to ease the load on local telephone systems, obviate delays and errors caused by indirect transfer of data and reduce the number of personnel required.

The Contract, which includes the supply of 40

professional television monitors, with cameras and associated video distribution equipment, was obtained as a result of an open tender to the Kuwaiti Ministry of Information in the face of international competition. Crow of Reading are recognised as one of the world's leaders in television broadcast engineering, and extend the same degree of professionalism to non-broadcast applications such as this closed circuit system. They are able to provide significantly higher standards of performance and reliability than those normally achieved by television engineers outside the broadcast field. This is believed to be an important factor in the selection of Crow as contractor.

In your work-shop

In this month's episode, Smithy the Serviceman, aided as always by his able assistant Dick, takes a look at a typical medium and long wave mixer-oscillator stage.

Dick walked happily towards the Workshop, swinging a medium sized a.m.-f.m. transistor radio from his left hand. It was a cold and misty New Year's Day morning, and Dick's breath condensed into small vaporous clouds that hovered around his head. As he approached the Workshop he was suddenly surprised to see all its lights come on, with their cheerful yellow rays streaming out of the windows.

Dick paused cautiously, edged to one of the windows and peered in. He gave a sigh of relief as he saw the familiar figure of Smithy divesting himself of his raincoat, then he went to the door and quietly let himself in.

"Happy New Year, Smithy!"

Smithy, who had his back to the door, jumped.

"Blimey, you gave me a shock. What are you doing here?"

"I could well," said Dick, as he walked over and placed the transistor radio on his bench, "ask the same question of you. After all, we did say we'd take New Year's Day off this year."

"I came in to get a few tools and a meter," explained Smithy. "One of our electric fires at home has started blowing fuses and I want to do a quick repair job on it. And now what brings you in?"

PRIVATE JOB

"A little private job," stated Dick, pointing to the transistor radio. "It's my Auntie Eff's and one of her darned cats knocked it off the table. I promised her I'd fix it up today if I could."

"Well," said Smithy, "let's hope the printed board hasn't got broken."

"I don't think it has," replied Dick, turning the receiver on and selecting medium waves. "It's quite all right on f.m., but it's weak on medium waves and even weaker on long waves."

He tuned in the local Radio 4 transmission. As he had said, this was weak. It was also accompanied by a whistle which changed in frequency as he tuned through the signal. He then switched to long waves, to demonstrate that the Radio 2 signal was, also as stated, even weaker.

"I've got a pretty good idea what's happened here," stated the Serviceman, grinning.

"Stap me," snorted Dick. "Don't tell me you're going to diagnose the trouble before I've even got the flipping back off."

"I'd hazard a guess, stated Smithy, "that the ferrite aerial rod is broken."

Dick glared at him then opened the rear of the radio case. The ferrite aerial rod was, indeed, broken. One half, with the medium wave coil on it, was still secured by a plastic clamp at what had been its centre. A small portion of the rod now protruded from the clamp on the side opposite to the medium wave coil, terminating at a jagged break. The remainder of the rod, with the long wave coil on it, lay forlornly on the bottom of the receiver case.

"You must," said Dick irritably, "have X-ray eyes or something. How the heck did you know that the ferrite rod was broken?"

"I only *guessed* that it was broken," replied Smithy soothingly, "but everything pointed towards it. For a

start the set had had a fall, and one of the first things to go in a case like that is the ferrite rod. Second, you said the set was working all right on f.m., and so it was unlikely that there'd be a fault in the common a.m. and f.m. stages. Third, you could tune in signals on medium and long waves and, since you didn't remark on the matter, presumably these were coming up at the proper points on the tuning scale. So the receiver oscillator was working correctly. Fourth, the local Radio 4 signal was weak and had what sounded like a second channel whistle on it when it would normally come belting in clear of interference, and the Radio 2 signal on long waves was also weak. The last three facts pointed to serious detuning of the aerial tuned circuits, and the first fact made it almost a hundred per cent certain that the circuits had become detuned because the ferrite aerial rod was broken."

Dick gazed at the Serviceman with reluctant admiration.

"Well," he remarked eventually, "you certainly used some logical reasoning there. I don't quite get the second channel whistle bit, though."

"That was a bit of luck," confessed Smithy. "But consider the situation. Say you've got an a.m. radio with an i.f. of 470kHz and you tune in a signal at 1,100kHz. The receiver oscillator will run at 470kHz above this frequency, which is 1,570kHz. But if there is a signal which is 470kHz above 1,570kHz, that is at 2,040kHz, and if it finds its way into the mixer, this signal will also pass into the i.f. amplifier. This is the second channel signal. What you normally hear with second channel interference is a whistle as the carriers of the two signals beat together. This whistle changes in pitch as you tune through the required signal because the difference frequencies from the mixer vary. If oscillator

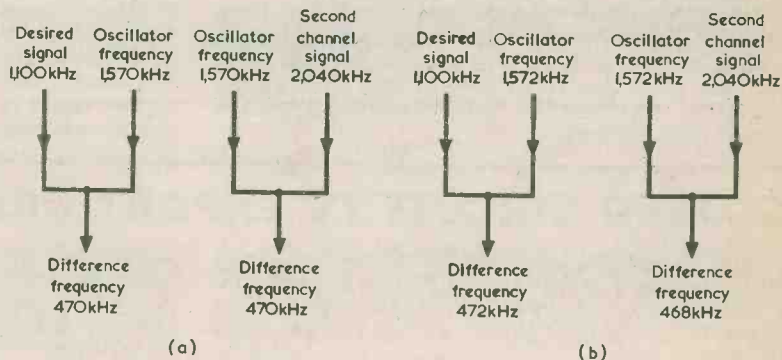


Fig. 1(a). If a second channel signal, which is higher than oscillator frequency by the intermediate frequency, finds its way into a receiver mixer stage input, an output is produced at intermediate frequency
 (b). Variations in oscillator frequency alter the pitch of the beat note given by the carriers of the desired signal and the second channel signal. Here, the oscillator frequency has been shifted upwards by 2kHz

frequency is increased a little the difference frequency given with the required signal goes up and the difference frequency given with the second channel signal goes down." (Figs. 1(a) and (b)).

"I know all about that," said Dick impatiently. "But why did the presence of that second channel whistle make you think that the aerial tuned circuit in the receiver was off-tune?"

"It's pretty obvious, isn't it?" retorted Smithy. "The job of the aerial tuned circuit of a superhet is to bring up the strength of the desired signal to as high a level as possible. This has two results. First, you get maximum sensitivity for the desired signal. Second, the desired signal is so much stronger than any second channel signal which may be knocking around that interference from the latter is either negligible or completely non-existent. You can expect a little second channel interference with a simple transistor a.m. superhet if you're tuned in to a weak signal and there happens to be a really strong signal at the second channel frequency, but not the other way round."

OSCILLATOR FREQUENCY

"Fair enough," conceded Dick. "Incidentally, there's something that's just occurred to me. Why is the oscillator frequency higher than signal frequency on these medium and long wave a.m. sets?"

"It has to be," replied Smithy. "One reason which comes immediately to mind is that if the oscillator frequency is below signal frequency and the set covers the long wave band of about 150 to 300kHz, the intermediate frequency would have to be lower than 150kHz. This would make the spacing between wanted and unwanted second channel signals too low and would increase the chances of second channel interference."

"All right then," said Dick. "How about having oscillator frequency lower than signal frequency on medium waves?"

"Okay, let's look at that next. Let's

say that the medium wave band is 600 to 1,600kHz and that we are still using our intermediate frequency of 470kHz. If the oscillator runs above signal frequency it will require a range of 1,070kHz to 2,070kHz. And if it runs below signal frequency it will require a range of, let me see now, 130 to 1,130kHz." (Fig. 2).

"What's wrong with that?"

"A very great deal," replied Smithy. "A frequency range of 1,070 to 2,070kHz represents a ratio between bottom and top frequencies of about 1 to 2 only. But a frequency range of 130 to 1,130kHz gives a ratio of about 1 to 8. The signal frequency range of 600 to 1,600kHz gives a ratio which is a little less than 1 to 3, and we consider this a sufficiently high ratio to be covered by a variable tuning capacitor. If we tried to cover an oscillator range with a ratio of 1 to 8 between the bottom and top frequencies we would need an absolutely enormous tuning capacitor!"

"Gosh," exclaimed Dick. "I can see it all now. Having the oscillator frequency above signal frequency means that the oscillator tuning capacitor has a shorter range to cover, and this in turn will mean that it can have a lower maximum value than that needed for the aerial tuned circuit."

"Exactly," confirmed Smithy. "What you normally find in practice these days with a.m. superhets is that both sections of the 2-gang tuning capacitor have the same value, but the effective value of the oscillator section is reduced by connecting a capacitor in series with it. Which is, by the way, known as a padding capacitor." (Fig. 3).

Smithy glanced at the receiver with the broken ferrite rod, then started.

"Dash it all," he complained irately, "you've done it again! In the very first half hour of our getting together in this New Year you've done it again!"

"Blimey, Smithy," protested Dick, "you don't half carry on. What have I done again?"

"Conned me into nattering about radio and electronics when there are other things to be done. You're *always*

Signal range	600kHz to 1,600kHz	600 : 1,600 \approx 1 : 3
Oscillator range (oscillator high)	1,070kHz to 2,070kHz	1,070 : 2,070 \approx 1 : 2
Oscillator range (oscillator low)	130kHz to 1,130kHz	130 : 1,130 \approx 1 : 8

Fig. 2. Medium wave signal and oscillator frequency ranges with oscillator frequency above and below signal frequency. An intermediate frequency of 470kHz is assumed

Your Local Supplier

LONDON

THE MODERN BOOK CO.

Largest selection of English & American radio and technical books in the country.

19-21 PRAED STREET,
LONDON, W2 1NP
Tel: 01-723 4185/2926

ESSEX

GLASS FIBRE P.C.B.'s

From your own tape, films or in master. Send S.A.E. for quotation.

RADIO ELECTRONICS AND CONSTRUCTOR P.C.B.'s

Send S.A.E. for details.

Dept. RE
PROTO DESIGN
4 Highcliffe Way,
Wickford,
Essex, SS11 8LA.

SUSSEX

JEFFRIES

For
Hi-Fi Equipment
Tape Recorders
Television
Transistor Radios

6A Albert Parade
Victoria Drive,
EASTBOURNE SUSSEX

EIRE

PEATS for PARTS

ELECTRONIC COMPONENTS RADIO & TELEVISION

For the convenience of Irish enthusiasts we supply:

Radio & Electronics
Constructor Data Books
Panel Signs
Transfers

Also a postal service

PEATS
the world of electronics
25 Parnell Street, Dublin 1. Telephone 749972

doing it. Let's get this set of your Auntie Eff's fixed up without any further messing around."

"I wonder," asked Dick dubiously, "if we could stick the two halves of the rod back together again? Say, with that new high-speed glue that people are using to stick their fingers together with?"

"Funnily enough," replied Smithy, "it is quite in order to stick the two halves of a broken ferrite rod together with adhesive. The adhesive can be any good cold setting type and the two parts must be nested together so that the interruption in the rod structure is as thin as possible. However, that rod in your aunt's set looks like a standard size to me, so we'll present her with a new one."

Smithy picked up a rule, held the two parts of the broken rod together and measured their length.

"Six inches," he announced. "No problem."

He walked over to the spares cupboard and, after a little searching, found a rod of the required length and diameter. He returned and handed it over to his assistant.

"Here you are, Dick" he announced. "I'll leave you to fit this. Don't forget to put the coils on the new rod the same way round as they are on the broken rod. Usually the two tuned coils are in series on long waves and if you put one the wrong way round they'll be out of phase with each other."

MIXER-OSCILLATOR

Dick loosened the plastic clamp which secured the broken rod, removed it and then fitted the new one. After this, he slipped the two coils, on their formers, over the ends of the rods. He switched on the receiver and turned its tuning control.

"Stap me, Smithy," he said, pleased, "there's no end of an improvement here. This set's as lively as anything now."

"Good show. Well, all you've got to do now is set the coils in their right positions on the rod. For a quick job we can assume that the aerial and oscillator trimming is all right whereupon the first thing to do is to tune in a station on medium waves that is near the low frequency end of the band and move the medium wave aerial coil along the rod for maximum signal strength. Then tune in to Radio 2 on long waves and adjust the long wave coil on the rod for optimum signal."

"That doesn't sound very technical to me," objected Dick.

"It isn't," confessed Smithy. "But it should be adequate if, as I say, we can assume that the trimming is correct. I hardly need to tell you that there's a trimmer across the aerial tuned circuit and another across the oscillator tuned circuit. The normal routine is to trim each tuned circuit with its trimmer at the high frequency end of the range and to adjust, or pad, each tuned circuit by changing the inductance at the

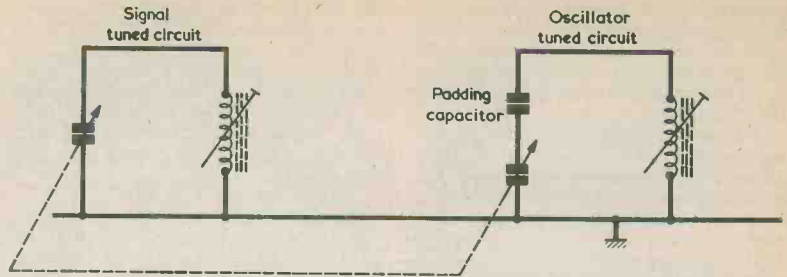


Fig. 3. Normally, the signal and oscillator sections of the 2-gang tuning capacitor have the same value, and a padding capacitor is connected in series with the oscillator section

low frequency end of the range. You change the inductance of the oscillator coil by adjusting its iron-dust core, and you change the inductance of the aerial coil by moving it along the ferrite rod." (Fig. 4).

"I've always understood why you trim at the high frequency end," commented Dick. "And that's because the tuning capacitor is then at minimum capacitance and the effect of the small trimming capacitor is at its greatest. But you don't have quite the same effect when you adjust coil inductance. Adjusting coil inductance seems to cause as much shift in resonant frequency at the high frequency end of the range as it does at the low frequency end."

"That's true," confirmed Smithy. "The two adjustments are interdependent, which means that you usually have to carry them out several times before you reach the final correct settings. Most of these transistor portables have rather involved medium and long wave trimming arrangements so, as a matter of interest, let's see if I can find the service sheet for this receiver of your Auntie Eff's."

As Smithy walked towards the filing cupboard, Dick grinned to himself. Smithy had already completely forgotten his complaint, a few minutes

earlier, that Dick had tricked him into spending his time talking about matters electronic. Once Smithy got into his stride on a particular subject there was no holding him back.

"Ah, here we are," said Smithy, returning with a service manual. "We happened to have this one in stock."

He opened the manual at its circuit diagram, placed it on the bench and indicated the circuitry around the a.m. mixer-oscillator transistor. (Fig. 5).

"Blow me," commented Dick. "There isn't much in the way of wave-band switching is there?"

"There isn't," said Smithy. "All the switching is carried out by a double-pole double-throw switch. The overall set-up is quite typical of the sort of thing you encounter in the medium and long wave sections of portable a.m.-f.m. receivers."

"Let's see," said Dick, "what happens when the switch is set to medium waves. The left hand switch section circuit is quite easy to follow. All the switch does is couple the transistor base via a $0.01\mu\text{F}$ capacitor to a coupling winding alongside the medium wave ferrite aerial coil. Now what does the right hand switching section do? Oh yes, it short-circuits the long wave ferrite aerial coil."

"There's not a direct short-circuit,"

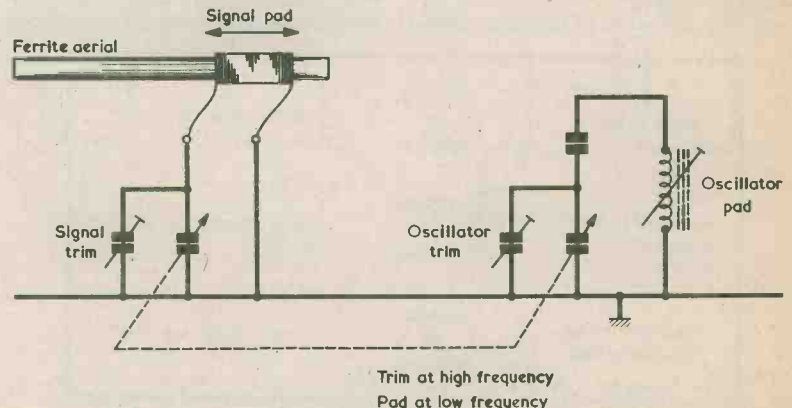


Fig. 4. Basic trimming and padding procedure for an a.m. broadcast band receiver

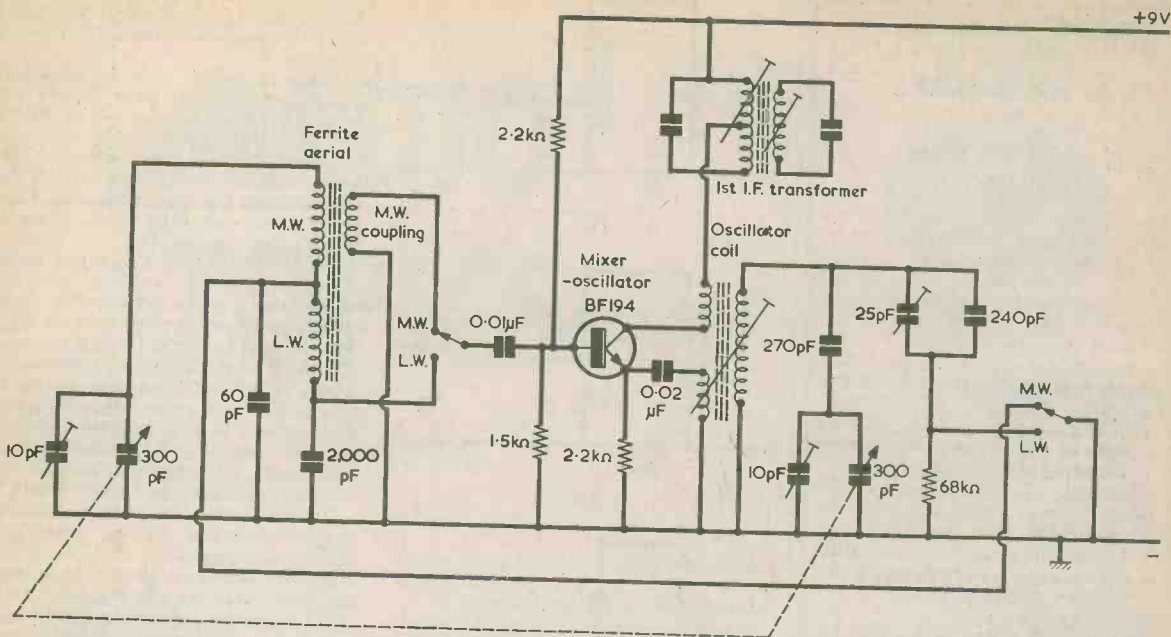


Fig. 5. Typical medium and long wave mixer-oscillator stage with representative component values and a d.p.d.t. wavechange switch. The bottom-end long wave signal coupling and medium wave oscillator damping circuits are encountered in some B.R.C. receivers

Smithy corrected him. "The right hand switch section connects the upper end of the long wave coil to the chassis, whilst the lower end of the long wave coil couples to chassis via a 2,000pF capacitor."

"That's as good as a short-circuit so far as I'm concerned."

"It's not, you know," persisted Smithy. "That 2,000pF capacitor has a reactance of around 250 to 500Ω at long wave frequencies. What happens is that the long wave coil becomes resonant at a very low frequency which is well below long wave frequencies. And this overcomes an ever-present problem which occurs whenever you have a medium and a long wave coil on the same ferrite aerial rod. If the long wave coil is open-circuit when medium waves is selected it may resonate with its own self-capacitance at a frequency in the medium wave band and cause awkward absorption effects. In some sets the long wave coil is directly short-circuited on medium waves. In this set it's tuned well away from the medium wave band."

OSCILLATOR SWITCHING

"As you like," said Dick carelessly. "Now let's have a look at the oscillator part. This seems simple enough, too, with the transistor emitter and collector connecting to coupling windings alongside the tuned coil. The oscillator section of the 2-gang tuning capacitor has a trimmer across it and it connects to the top end of the coil by way of a

270pF capacitor."

"It does," agreed Smithy, "and that 270pF capacitor is the padding capacitor. Both sections of the 2-gang tuning capacitor in this set have the same value."

"There's something funny here," stated Dick, frowning. "The top end of the coil also connects to a 240pF capacitor and 25pF trimmer in parallel and these connect to a 68kΩ resistor going to chassis."

"Forget about them for the moment," advised Smithy, "and see what happens when the two switch sections are set to long waves."

"All right," replied Dick agreeably. "On long waves the right hand switch section disconnects the upper end of the long wave ferrite rod winding from chassis, with the result that the medium and long wave windings are now in series. And the left hand switch section disconnects the transistor base from the medium wave coupling winding and connects it to that 2,000pF capacitor below the long wave winding. Hey, Smithy, that's crazy!"

"No, it isn't. What you've got there is what is known as a bottom-end coupling."

"Bottom-end coupling? That's new to me."

"It is a bit unusual," conceded Smithy. "The best way of explaining it is to start off by saying that one way of taking a low impedance output from a tuned circuit is to take it from a coil tap near the earthy end. Okay?" (Fig. 6(a).)

"Yes, I can visualise that."

"And another way," continued Smithy, "is to take the low impedance coupling from a tap in the capacitive side of the tuned circuit. You can't tap into a capacitor as you can into a coil, but you can do what is effectively the same thing and have two capacitors in series and take the coupling from their junction. If the capacitor connecting to chassis has a much higher value than the other capacitor then it has a much lower reactance, and the coupling is equivalent to a tap low down a coil." (Fig. 6(b).)

"That," remarked Dick, his brow furrowed in thought, "seems to be reasonable enough. But the high value capacitor in the receiver circuit is in series with the coil."

"No difference," responded Smithy. "All that has happened is that the chassis connection has shifted to the junction of the two capacitors and the coupling is taken from the junction of the high value capacitor and the coil." (Fig. 6(c).)

"Oh, I get it! But there's still one thing that doesn't seem to be quite right. Since the low value capacitor is actually the signal frequency tuning capacitor, won't the ratio between the two capacitors change as the tuning capacitor is adjusted?"

"It will," stated Smithy, "and the impedance at the coupling point will change, too. If the large value capacitor has a value which causes a sufficiently low impedance to be given when the tuning capacitor is at maximum value, all that will happen is that the impedance reduces as the

AN AUDIO SIGNAL GENERATOR for only £14.95!



STAR FEATURES:

- ★ 15Hz-150Khz
- ★ Sine/Square Wave Output
Variable 0-3V PkPk
- ★ Very Low Current Consumption,
9V Btty
- ★ One IC Plus 4 Transistor Circuit
- ★ Smart ABS Case, drilled and
screen printed
- ★ KIT includes All Components,
Drilled PCB, Controls, etc.
- ★ Unbeatable Value:
KIT.....ONLY £14.95 (pp 70p)
READY BUILT £19.70 (pp 70p)

CWO To:

WELLTEX MFG. CO.,
9 Sirdar Strand, Gravesend
DA12 4LP
(C.O.D. orders accepted)

GAREX

Modulation transformer

Valve type 747, for 30W Tx £2.60

Mains transformer (multitap primary)
250 0-250V 200mA, 6-3V 5A, 5V 2A,
fully shrouded, (suitable for 30W Tx - match-
ing style to mod. trans.) £5.95
Connection data supplied with transformers.

H.T. chokes 5H 80mA, 1.8H 125mA £1.25
Relays GPO type 2400, 12V coil, 8A contacts,
4PCO or 2P make 45p each; 5+ : 30p

Neons min. wire end, 55p/10; £4/100

Slide Switches min. DPDT 18p ea; 5+ : 13p
2 pole, 3 position 22p each; 5+ : 18p

PL259 UHF Plug & Reducer 68p; 5+ : 60p

SO239 UHF Socket panel mtd. 55p; 5+ : 45p

BNC cable mtg Socket 50 20p; 5+ : 15p

Resistor Kits E12 series, 22Ω to 1MΩ
57 values, 5% carbon film, 1/4W or 1/2W

Starter pack, 5 each value (285) £2.40

Mixed pack, 5 each 1/4W + 1/2W (570) £4.85

Standard pack, 10 each (570) £4.65

Giant pack, 25 each (1,425) £11.85

Numericators ZM1080 75p each; 5+ : 63p

I.C.'s (new, full spec.) CD4001AE 25p

SN76660 £1.12, 723 (TO5) 90p

NE555 Timer 65p

709 (TO5); 741 (DIL-8) Op. amps 30p each

5+ I.C.'s (any mix) at 20% discount

Nicad rechargeable cells HP7 size £1.05
each; 4+ : 95p; 10+ : 88p. Brand new.

We stock amateur V.H.F. equipment and
mobile aeriels, s.a.e. details.

Distributors for J. H. Associates Ltd.
(switches and lamps)

Prices include UK Post, Packing & VAT


Mail order only Sole Address:

GAREX ELECTRONICS


7 NORVIC ROAD, MARSWORTH,

TRING, HERTS HP23 4LS


Cheddington (STD 0296) 688684

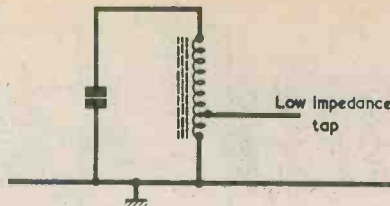

(a)

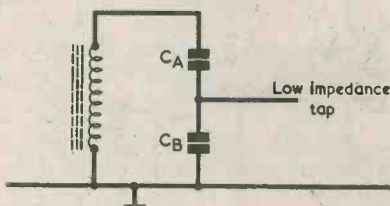

(b)

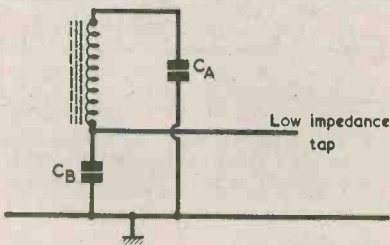

(c)

Fig. 6(a). Taking a low impedance tap from the inductive side of a tuned circuit

(b). The tap can alternatively be taken from the capacitive side of the tuned circuit. CB has a much higher value than CA

(c). An alternative version of the circuit, with the connections to CB reversed

tuning capacitance gets smaller."

"That seems to be all right then," yielded Dick. "Let's take a look at the oscillator section. The right hand switch section connects the 240pF capacitor and the parallel 25pF trimmer directly across the oscillator tuned coil."

"Whereupon," stated Smithy, "the oscillator frequency is much reduced and can now be tuned over the range required for long waves by the oscillator section of the 2-gang capacitor. Also, that 68kΩ resistor you were worrying about just now is short-circuited. The oscillator circuit is designed to run at correct level on long waves, when a relatively high capacitance is connected across the coil. But on medium waves, where there is much less tuning capacitance, the oscillator could run too violently unless some precaution were taken. The precaution consists of putting that 68kΩ resistor across the tuned circuit via the parallel 240pF capacitor and 25pF trimmer. The resistor damps the

oscillator tuned circuit so that the oscillator runs at just about the same level on medium waves as it does on long waves."

"That's crafty," commented Dick. "Well, we seem to have picked the bones of this wavechange switching circuit pretty thoroughly. No, we haven't! There's one capacitor we haven't looked at yet. That's the 60pF one between the top of the long wave ferrite rod winding and chassis. What's that do, Smithy?"

"It's effectively a long wave trimming capacitor," replied Smithy. "Since there are relatively few turns on the medium wave aerial coil, that 60pF capacitor can be looked upon as trimming all the aerial coil inductance which is in circuit on long waves. It only comes into use on long waves and it's purpose is to give good tracking between aerial and oscillator tuned circuits on this band. And that's the lot so far as this circuit is concerned."

"It isn't quite," said Dick quickly. "What does the service sheet say about alignment?"

Smithy leaned over and examined the instructions in the manual.

"It's pretty well what you'd expect," he announced. "Briefly, the medium wave band has to be adjusted first. The trimmer across the oscillator tuning capacitor is adjusted at the high frequency end for correct reception frequency as indicated by the tuning scale, and the aerial circuit trimmer is adjusted for maximum signal strength. Then the oscillator tuned circuit is padded at the low frequency end for correct reception frequency by adjusting the oscillator core, after which the aerial circuit is adjusted by moving the medium wave aerial coil along the ferrite rod. These two operations are repeated until there is no further improvement. Then you switch to long waves and make adjustments at a single frequency a little higher than that of the Radio 2 transmission. The 25pF trimmer in parallel with the 240pF capacitor is adjusted for correct frequency of reception, after which the long wave coil is moved along the ferrite rod for optimum signal strength. If you want the alignment instructions in greater detail, then I'll leave you to read them for yourself."

START OF THE YEAR

With which words, Smithy left his assistant, walked over to his own bench and proceeded to gather up some tools and a testmeter.

"Hey, Smithy," called out Dick. "You aren't going to leave just like that, are you?"

"I am," came Smithy's purposeful reply, as he put on his raincoat.

"But," wailed Dick, as Smithy opened the door, "haven't you forgotten something?"

"No, I haven't," said Smithy, half-way out of the door. "But this is the first chance I've had of saying it. And a Happy New Year to you, too!" ■

RADIO TOPICS

By Recorder

Up till now I had always looked upon the 741 as offering pretty well all that one could ask for in an operational amplifier working at d.c. or fairly low frequencies. It is extremely robust, has a typical voltage gain of 200,000 times and its input resistance is $0.3M\Omega$ minimum and $2M\Omega$ typical. Practical checks have shown that, if preceded by a silicon emitter follower transistor, the input resistance at the transistor base is well in excess of $1M\Omega$, with the proviso that this assumes leakage currents in the transistor that are lower than manufacturers' maximum specification figures. The combination of emitter follower and 741 was used, to effect, in G. A. French's 'Low Cost Electronic Voltmeter' in the July 1975 issue and, to even greater effect, in the resistance bridge described in 'In Your Workshop' in the October 1975 issue of this journal.

NEW DEVICE

But things never remain static in electronics and we now have a new operational amplifier, from RCA, which completely out-performs the 741 so far as input resistance is concerned. This is the CA3130 and the reason for its superior performance is that it is a CMOS device with a MOSFET input, whereupon the input resistance goes up to astronomical levels.

The internal circuitry of the CA3130 is a lot simpler than is that of the operational amplifiers we have become used to in recent years. Two p-channel MOSFET's appear in a differential amplifier in the first stage, with the inverting and non-inverting inputs connecting to their gates. Their drains couple to the collectors of two bipolar transistors in a modified current mirror configuration, a single-ended output being taken from one of the transistors. If desired, an offset null potentiometer may be connected to the emitters of the bipolar tran-

sistors, but even without this the input offset voltage is low.

The single-ended output connects to the base of another bipolar transistor. This is in the earthed emitter mode and has a constant current source as its collector load. The collector also connects directly to the gates of the output transistors, these being a p-channel and an n-channel MOSFET in a totem-pole complementary output stage. And that, apart from the input gate protecting diodes and a bias network, is the lot. Most of the voltage gain in the device is provided by the bipolar transistor which feeds the output MOSFET's.


A single external compensating capacitor is needed to prevent the i.c. from taking off. This couples effectively across the high gain bipolar transistor and requires a value of about $47pF$.

The input current to the CA3130 is typically 5 picoamps at 25 degrees Centigrade, rising to about 1,000 picoamps at 120 degrees. And 1,000 picoamps is, of course, one-thousandth of a microamp. This input current is mainly leakage current in the input gate protecting diodes. The typical input resistance at 25 degrees Centigrade is also quoted, as $1.5T\Omega$. I had to look up the reference books for 'T', which is short for 'tera'. $1.5T\Omega$ is the same as 1.5 million megohms!

As with all CMOS devices, some care is needed in handling the CA3130. The soldering iron bit used for connecting it into circuit should be reliably earthed, and if the input gate protecting diodes are made to conduct due to improper circuit operation the input current must not exceed 1mA. The CA3130 is normally supplied in an 8 lead TO-5 style package, whereupon it is referred to as the CA3130T.

The CA3130 will not be the op-amp to end all op-amps. But it certainly takes development towards that ideal a very considerable step forwards.

MORSE MADE EASY

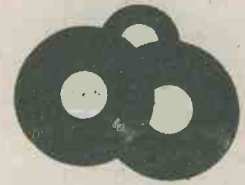

BY THE RHYTHM METHOD!

These courses, which have been sold for over 23 years, have been proved many times to be the fastest method of learning Morse. You start right away by learning the sounds of the various letters, numbers, etc., as you will in fact use them. Not a series of dots and dashes which later you will have to translate into letters and words.

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it. It's as easy as learning a tune. 18-W.P.M. in 4 weeks guaranteed.

The Complete Course consists of three records as well as instruction books.

For Complete Course send £5.00 including P.P.I. etc. (overseas surface mail £1 extra).

THE MORSE CENTRE

Box 8, 45 Green Lane, Purley, Surrey.
I enclose £5.00 or large s.a.e. for explanatory booklet.

Name.....

Address.....

PADEC COMPONENTS

(Dept. REC2)

STOCK UP NOW. QUANTITY PURCHASE OF QUALITY COMPONENTS

- 250 CARBON FILM RESISTORS 5% (at least 40 different values per pack).....£2
- 20 1 AMP/400 VOLT DIODES (1N4000 series).....£1
- 10 ZENER DIODES (all different values).....£1
- 40 metres PVC EQUIPMENT WIRE (2 amp. 7/0.2)
 - 10 metres of red
 - 10 metres of black
 - 10 metres of green
 - 10 metres of white.....£1
- 3 BRIDGE RECTIFIERS (mixed: 1-3 amp/50 volts).....£1
- 2 PLASTIC TRIACS 1.6 amp/400v (ideal for experiments, lead details given).....£1
- 10 GLASS WIRE ENDED NEONS (require a 220K resistor for mains operation).....70p


Also available:

Capacitor-Discharge (car) ignition transformers (FREE CIRCUIT)
Limited number of Stereo Headphones

S.A.E. with enquiries please
Quoted prices include post, etc.

P.O. BOX 71,
SOUTHEND-ON-SEA,
ESSEX SS2 5DZ.

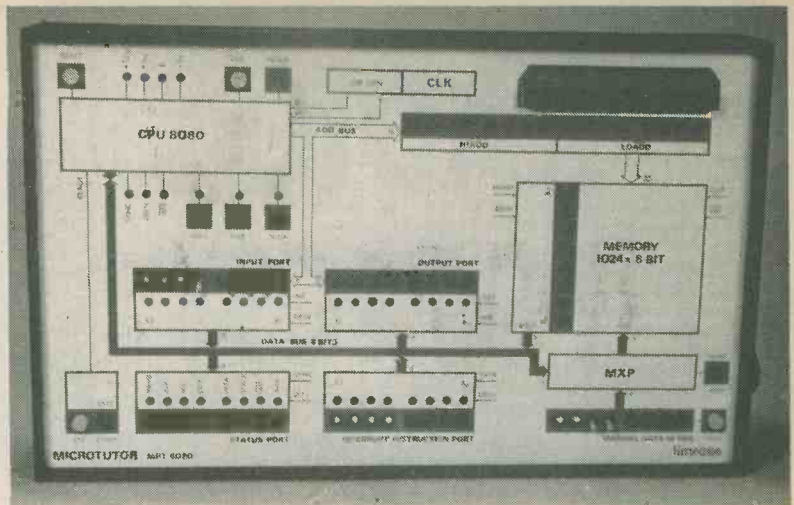The Limrose Microtutor 8080. This is a microcomputer in its own right and can be employed for developing an understanding of microprocessors and their software



PREFIXES

Since I had to look up 'T' for 'tera', it occurs to me that there are other prefixes denoting magnitude which are likely to crop up in the future, now that electronics deals more and more with very large and very small quantities. For the record, let's list them all here. Kilo (k) means a thousand, of course, whilst mega (M) stands for a million. The next one up is giga (G) which means a thousand million, followed by tera (T) which, as we've just seen, stands for a million million.

Going down in scale we have the familiar milli (m) which represents a thousandth part, micro (μ) a millionth, nano (n) a thousand millionth and pico (p) a million millionth. Now comes the unfamiliar ones. These are femto (f) a thousandth of a pico, and atto (a) a millionth of a pico.

And you can't get much smaller than that.

MICROTUTOR 8080

The accompanying photograph illustrates the Limrose Microtutor 8080, which is described as offering a fast, simple and inexpensive way of developing a fundamental understanding of microprocessors. It gives the 'hands on' experience needed to master and apply microprocessors.

The Microtutor 8080 is a full 8-bit microcomputer with an 8080 c.p.u., 1K x 8-bit random access memory, an input port, an output port, an interrupt instruction port and a status port. It has facilities for manual loading of the memory and for single stepping of the processor, and can therefore be used as a prototyping computer for development of applications software. It can also be expanded with additional memory and a teletype interface, using plug-in cards, for more advanced work.

All important signals, data bits and addresses are continuously displayed by means of over 40 l.e.d. indicators. Inputs are provided on several switch

registers and press-button switches. Data paths and the manner in which they relate to various registers are shown on the front panel.

By following the instruction book provided with the Microtutor, a person with limited technical knowledge can rapidly learn how microprocessors work. Trained electronic engineers can quickly bridge the gap between conventional hardware and microprocessor software by making a step-by-step progression from developing simple algorithms to complex programmes.

The Microtutor 8080 is available fully tested and assembled in a portable cabinet weighing only a few kilogrammes. It has merely to be plugged into the a.c. mains for the user to have a powerful microcomputer ready for use.

Further information is available from the manufacturers, Limrose Electronics Limited, 241-243 Manchester Road, Northwich, Cheshire.

GIM CATALOGUE

General Instrument Microelectronics Ltd., of 57-61 Mortimer St., London W1N 7TD, announce that, because of the large number of standard microcircuits now comprising their range of off-the-shelf MOS/LSI devices, they have published their latest product catalogue in a convenient, easy-to-use paper back form. The new catalogue is available at no charge to existing GIM customers or purchase managers and can be bought by first-time users from GIM distributors at a nominal cost.

The 320 page publication provides comprehensive data including functional descriptions, pinning, timing and peripheral circuit details for all MOS microcircuits in GIM's fast growing products range. This now comprises over 200 different MOS/LSI devices for the consumer, calculator, telecommunications and data management product areas.

General Instrument manufacturers MOS/LSI circuits for clocks, clock radios, TV tuners, remote control, appliance timers, radio and high fidelity systems.

GIM is also the leading supplier of LSI video game microcircuits. The AY-3-8500 was the first single chip LSI product to provide six different games with on-screen scoring and realistic sound.

SEEING HEAT

Presented by Marconi Space and Defence Systems Limited at the 1976 Farnborough International Air Show were details of a new lightweight thermal imaging night sight.

The new sight, probably the smallest and lightest of its type in Europe, is designed primarily to give a night-fighting capability to anti-armour guided weapon systems, but it has many applications in the fields of security and safety. Due to its ability to detect people in conditions of complete darkness it has considerable potential as an intruder detection device.

The sight has two magnifications, enabling a wide field of surveillance mode to be switched instantly to a narrow field of view at higher magnification whilst retaining the centre-field sight-line. Field-of-view, aspect ratio, spatial resolution and viewing optics can be provided to meet customer requirements. A graticule is fitted and a variable focus eyepiece is supplied which ensures that both graticule and scene are in focus.

Infra-red radiation from the scene is focused by a large aperture afocal lens system onto cadmium mercury telluride detector elements via an optic-mechanical scanner and a collimator. The detector output is fed via the processing electronics to a vertical multi-element light emitting diode array. The light from the l.e.d.'s is then directed via a collimator to the scanner, which reflects the output into the variable focus eyepiece.

LIGHT-EMITTING DIODES

Recently introduced by Litronix, 24 Sun Street, Hitchin, Herts, are two new red light-emitting diodes having a particularly high light output.

In these, the semiconductor material is gallium arsenide phosphide, and voltage drop is 2 volts at a forward current of 20mA. The lens is red diffused polypropylene and provides a large full flooded front radiating area with wide angle viewing.

Type numbers are RL-4403 and RL-4415. The RL-4403 is of conventional construction with its lead-outs extending backwards. As can be seen in the photograph, the RL-4415 has its lead-outs angled at 90 degrees to facilitate direct mounting to a printed circuit board. Snap-on clips are available for both types for panel mounting applications.

These rather unusual l.e.d.'s have their lead-outs at right angles for direct mounting to a printed board. They are high brightness types manufactured by Litronix


ternal screened compartment. This is a pretty standard practice with signal generators. It provides double screening of the tuned circuits, and it also ensures that they are well isolated from the outside world and are thereby more able to maintain their frequency accuracy in terms of the signal generator tuning scale.

Everything inside the tuned circuit compartment was as it should be, but I learned a little lesson about trimming capacitors. Each tuned circuit was trimmed by the capacitance between two twisted enamelled copper wires!

A thick enamelled wire, of around 12 s.w.g., protruded outward from the chassis, to which it was connected. Close-wound around it was a thin enamelled wire, around 26 s.w.g., this connecting to the non-earthly side of the appropriate tuned circuit. The number of turns of the thin wire on each of these assemblies varied from

on the thick wire, possibly by machine, and would intentionally have too many turns. When it became necessary to trim the tuned circuit concerned, the thin wire would then be carefully unwrapped from the thick wire until the resonant frequency was just at the correct level. This would be a one-way process, because it would be difficult to wind the thin wire back on tightly again if too much were removed.

The whole idea sounds rather primitive but, on reflection, is it? Two lengths of enamelled wire are cheaper than a physical trimmer having the long-term stability required in a signal generator, and the twisted wire assembly would certainly stand up to plenty of knocks and general maltreatment of the instrument. Patently, there should be no direct voltage between the two wires because of the thinness of the insulation between them but that seems to me to

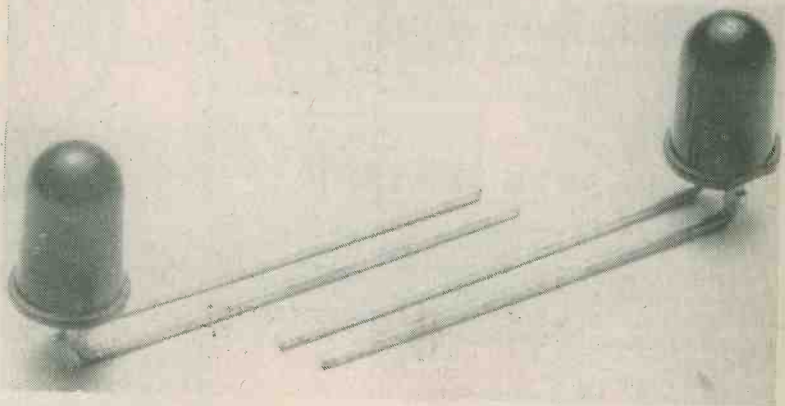

UNUSUAL TRIMMER

I was digging into a rather old valve signal generator the other day and had reason to take the screen off the coil and range switch department. Although the signal generator was housed in its own metal case the tuned circuits were contained in a further in-

ten to about thirty. The open end of each thin wire gave the appearance of having been removed and then cut off about half an inch from the thick wire.

The alignment procedure at the factory was quite obvious. Initially, the thin wire would be close-wound tightly

be the only serious disadvantage in the idea. So, the next time you require a stable low value trimmer, those two twisted enamelled wires may be just the job for you!

'Precedence Detector'

In the circuit description for this project it was stated, on page 232 of the November 1976 issue, that pin 3 of the 7400 is taken to 1 when S1 is pressed. It is, of course, pin 1 which is so taken.

BACK NUMBERS

For the benefit of new readers we would draw attention to our back number service.

We retain past issues for a period of two years and we can, occasionally, supply copies more than two years old. The cost is the cover price stated on the issue, plus 11p postage.

Before undertaking any constructional project described in a back issue, it must be borne in mind that components readily available at the time of publication may no longer be so.

We regret that we are unable to supply photo copies of articles where an issue is not available. Libraries and members of local radio clubs can often be very helpful where an issue is not available for sale.

Use the **NEW Strip-fix Plastic** **PANEL SIGNS**

★ **SET 3 - Wording - WHITE**

★ **SET 4 - Wording - BLACK**

Over 1,000 words and symbols, covering more than 300 terms, in each set

Illustration of actual size = RADIO

★ **SET 5 - DIALS**

6 sheets containing one Large and two Medium scales, Large Horizontal Tuning scale, Frequencies, 12 Control Panels

- Easy to fix
- Stapled in booklet form
- Designed to hang above workbench
- Pocket for loose cuttings
- Professional finish



PRICE

SET 3: 75p

SET 4: 50p

SET 5: 38p

(P. & P. 7p per set)

ALL PRICES INCLUDE V.A.T.

The Perfect Transfer for the Home Constructor

To Data Publications Ltd., 57 Maida Vale, London, W.9 1SN

Please supply Panel Signs as follows: Set 3 Set 4 Set 5

I enclose cheque / crossed postal order for (Tick which set is required)

NAME

ADDRESS

(BLOCK LETTERS PLEASE)

SMALL ADVERTISEMENTS

Rate: 8p per word. Minimum charge £1.00
Box No. 20p extra

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the *bona fides* of Advertisers. (Replies to Box Numbers should be addressed to: Box No. —, *Radio and Electronics Constructor*, 57 Maida Vale, London, W9 1SN.

WANTED TO PURCHASE: large and small quantities of transistors, diodes, I.C.s, etc. Immediate requirement for 10,000 BC109 transistors. Send samples/lists of any surplus components. Elekon Enterprises, 224a St. Paul's Road, Highbury Corner, London N1 2LJ. Telephone: 01-359 4224.

SERVICE SHEETS for Radios/TV's etc. 50p and s.a.e. Catalogue 20p and s.a.e. Hamilton Radio, 47 Bohemia Road, St. Leonards-on-Sea, Sussex.

WANTED TO PURCHASE: All early books on radio, preferably before 1925. Box No. 282.

THERS FIND MASSES MORE COINS/VALUABLES with latest auto-tuning 8 transistor variable acoustic professional detector. Save £100+ over comparable commercial machines. Complete easybuild plans/suppliers list £1.50. Detex Electronics, 20 Maldon Road, Acton, London W.3.

FAST SERVICE for resistors, capacitors, transistors, din plugs, jack plugs, audio leads. Special Offer: AC128 12p, post extra. S.A.E. list. Callers welcome. Torbay Electronic Components, 185 Higher Union Street, Torquay, Devon. Telephone: 211086.

BOOKS TO CLEAR. *Television Engineering* by Amos, Birkinshaw & Green, 1969, £2.00; *Radio & Line Transmission* by Danielson & Walker, 1969, £1.50; *Electric Model Car Racing* by D. J. Laidlaw-Dickson, 1965, 60p; *Radio Communication* by J. H. & P. J. Reyner, 1962, £2.00. All prices include Postage and Packing. Box No. G316.

MULLARD COMPONENTS. Send s.a.e. for free list to P.M.S., Dept REC4, P.O. Box 6, Crawley, Sussex, RH10 6LH.

ANTIQUA RADIO BOOKS. Newnes "Television & Short Wave Handbook" by F. J. Camm, 1935, £3.00. News Chronicle "Wireless Constructor's Encyclopaedia" by F. J. Camm, 3rd edition, circa 1930, £3.50. Prices include postage and packing. Box No. G318.

THE BRITISH AMATEUR ELECTRONICS CLUB for all interested in electronics. Four Newsletters a year, concessions for members and Major Projects sponsored by the B.A.E.C., currently the B.A.E.C. Computer. U.K. membership fee £2 a year from January 1st, overseas £3 surface, £4 airmail. S.A.E. for details to Hon. Sec., J. G. Margetts, 42 Old Vicarage Green, Keynsham, Bristol.

(Continued on page 381)



Random FLASHER UNIT
Wired ready for use Complete with three 100 watt coloured lamps that flash independently at random. **£18.95**



TWIN BANK 6 LIGHT UNIT (less lamps) LENGTH 14 1/2 inches **£9.55 EACH**
B.C. Fitting **£10.35 EACH**
E.S. Fitting



Sound to Light MASTER UNIT 600 WATTS PER CHANNEL **£30.95**
INCLUDING CHANNEL OUTPUT PLUGS AND MAINS INPUT SOCKET



TYPE A SPOT (less lamp) **£12.12 EACH**
E.S. Fitting



TYPE B 3 BANK UNIT (Less Lamps) **£6.90 EACH**
B.C. Fitting | **£7.26 EACH** E.S. Fitting



TWIN BANK 12 LIGHT UNIT Length 31 1/2" (less lamps) **£17.00 EACH**
B.C. Fitting | **£15.60 EACH** E.S. Fitting



100 WATT SPOT LAMPS RED, YELLOW, GREEN, BLUE, CLEAR **£1.30 each** or **£3.90** Minimum 3 lamps B.C. or E.S. Fitting

ALL PRICES INCLUDE V.A.T. AND POST & PACKING (These prices apply to the United Kingdom only)
Send 20p for illustrated leaflet & price list

ALBEN ENGINEERING CO LTD,
DEPT. RE THE CRESCENT, WORSTHORNE,
BURNLEY. LANCs. Tel: Burnley 20940



ETCHING KIT

All you need to make your own
PRINTED CIRCUITS

Full instructions, Copper Clad Board, Ferric Chloride, Dish and Pen

Price incl. VAT & Postage **£4.75**

Send cheque or P.O. today to:
HOME RADIO COMPONENTS LTD.

240 London Road, Mitcham,
Surrey, CR4 3HD

REVOR OPTICAL & TECHNICAL

42 TAVISTOCK STREET
LONDON W.C.2
Tel. 01-836 4536



4" dia. lens

£10.00

POST FREE

FLEXIBLE MAGNIFIER

WITH CAST IRON BASE, PRECISION GROUND AND POLISHED LENS, CHROME PLATED FRAME AND FLEXIBLE TUBE. IDEAL FOR HOBBIES, AND DETAILED WORK WHICH REQUIRES BOTH HANDS FREE.

CALLERS WELCOME

(Subject to price ruling at the time of issue)

RADIO MODELLER

ELECTRONIC BOOKS

● **MODEL RADIO CONTROL**
Detailing both Theory and Practice, this book, by leading authority Paul Newell, has become the standard reference work. A brief historical survey leads up to a detailed description of proportional systems, with over 100 illustrations, including theoretical circuits and p.c. layouts for an advanced digital system. 134 pages
Price £2.25

U.K. Packing & Postage 32p

theory and practice of

MODEL RADIO CONTROL

development of systems
proportional systems
digital system design
practical examples and
full circuit details

ON SALE NOW
at all leading shops
or direct from:-

RADIO MODELLER BOOKS DIVISION,
84 High Street,
teddington, TW11 8JD.

SMALL ADVERTISEMENTS

Use this form for your small advertisement

To: The Advertisement Manager, Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please insert the following advertisement in the issue of RADIO & ELECTRONICS CONSTRUCTOR

➔			

15 words at 8p
= £1.20

**ALL WORDING
IN
BLOCK LETTERS
PLEASE**

I enclose remittance of being payment at 8p a word. MINIMUM £1.00
Box Number, if required, 20p extra

NAME.....
ADDRESS.....

Copy to be received four weeks prior to publication. Published on the 1st of every month.

SMALL ADVERTISEMENTS

(Continued from page 379)

60kHz MSF RUGBY RECEIVERS BCD time-of-day output. High performance PLL 5V operation, pulsating LED. Kit or assembled instrument available. Prices £14.08-£23.47. Details: Toolex, Sherborne, Dorset.

COLLECTORS' ITEMS. Bound Volumes of "The Wireless World" (which was then published weekly) for 1929, 1930, 1931, 1932, 1933, 1934, 1935, 1936, 1937, 1938, and 1939 (nine months only for this year due to outbreak of war). Two volumes per year, total of 22 volumes. All in very good condition. Offers invited. Box No.G319.

TREASURE HUNTERS! Construct, inexpensively, metal detector giving £300 performance. 10 pages, illustrated plans, £1. C. H. Lucas, 241 Upminster Road South, Rainham, Essex.

THE RADIO AMATEUR INVALID & BEDFAST CLUB is a well established Society providing facilities for the physically handicapped to enjoy the hobby of Amateur Radio. Please become a supporter of this worthy cause. Details from the Hon. Secretary, Mrs. Rita Shepherd, 59 Paintain Road, Loughborough, Leics., LE11 3LZ.

HEATHKIT TEST GEAR, ETC. Most factory built. Generators: RF-1U £20. A.F. AG-9U £20. R/C bridge C-3U £15. Valve voltmeter with R/F probe V-7A £18. Oscilloscope 0-12-U £25. Electronic Switch S-3U £10. S.B.—101 case only £5. Collins mechanical filter 455-Z-5 with crystal £10. All items must be sold, i.e. o.n.o. Telephone: West Coker 2712.

COMPONENTS OBTAINED ON REQUEST for projects in this and other magazines for constructors in the Coventry area. Barras Electronics, 11 North Street, Coventry. Telephone 441141.


SPECIAL OFFER: Limited number of Bound Volume No. 25 "Radio Constructor" (1971/1972) which were only slightly damaged in a fire at our warehouse. Price £1.25 each plus 75p postage and packing. Data Publications Ltd., 57 Maida Vale, London W9 1SN.

FOR SALE: Avo electronic multimeter £10.00. Avo Minor £7.00. Super 8 projector £5.00. Stereo cassette mechanism £10.00. Closed circuit television camera, not working £40.00. Video recorder, not working £50.00. Box No. G322.

JOIN THE INTERNATIONAL S.W. LEAGUE. Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. — both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars, Membership including monthly magazines, etc., £3.75 per annum. (U.K. and British Commonwealth), overseas \$10.00 or £4.00. Secretary ISWL, 1 Grove Road, Lydney, Glos., GL15 5JE.

FOR SALE: Heathkit oscilloscope Model 10-18U, 4.5MHz bandwidth. Assembled and working but otherwise not used £15.00. Two c.r.t. 3BP1 for new transistorised oscilloscope, £5 each. L. Wade; Telephone: Epping 75899, office hours only.

(Continued on page 382)

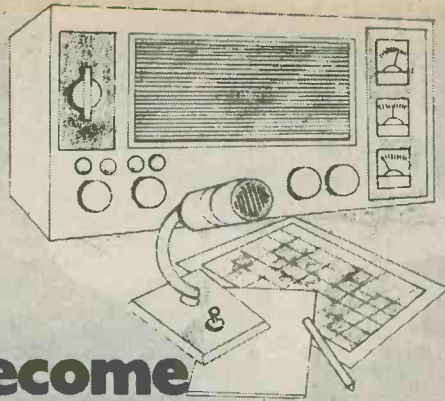

Become a radio amateur.

Learn how to become a radio amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

WAA
REK 17

Brochure, without obligation to:
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,
P.O.Box 156, Jersey, Channel Islands.

Free!

NAME _____

ADDRESS _____ (Block caps please)

PRECISION POLYCARBONATE CAPACITORS

ALL HIGH STABILITY - EXTREMELY LOW LEAKAGE

440V AC (+/-10%)	63V DC Range	+1%	+2%	+5%
0.1µF (1 1/2" x 1 1/2")	68p	0.47µF	£1.32	77p
0.22µF (1 1/2" x 1 1/2")	86p	1.0µF	£1.56	91p
0.25µF (1 1/2" x 1 1/2")	92p	2.2µF	£1.82	£1.32
0.47µF (1 1/2" x 1 1/2")	£1.10	4.7µF	£2.82	£1.88
0.5µF (1 1/2" x 1 1/2")	£1.16	6.8µF	£3.48	£1.23
0.68µF (2" x 1 1/2")	£1.25	10.0µF	£4.98	£2.32
1.0µF (2" x 1 1/2")	£1.37	15.0µF	£7.14	£3.32
2.0µF (2" x 1 1/2")	£1.95	22.0µF	£9.66	£4.78
			£6.44	£2.88
				£3.90

***TANTALUM BEAD CAPACITORS** - Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 15V/25V or 35V; 10.0µF at 16V/20V or 25V; 22.0µF at 6V/10V or 16V; 33.0µF at 6V or 10V; 47.0µF at 3V or 6V; 100.0µF at 3V. ALL AT 12p EACH: 10 for £1.10; 50 for £5.00.

TRANSISTORS:

BC107/8/9	9p	*BC183/183L	11p	*BF194	12p	BFY51	20p
BC114	12p	*BC184/184L	12p	*BF196	13p	BFY52	20p
BC147/8/9	10p	*BC212/212L	12p	*BF197	13p	OC71	20p
*BC157/8/9	12p	*BC547	12p	AF178	10p	2N3055	50p
*BC182/182L	11p	*BC558A	12p	BFY50	20p	*2N3702/411p	

1N914 6p; 8 for 45p; 18 for 90p. 1N916 8p; 6 for 45p; 14 for 90p. IS44 5p; 11 for 59p; 26 for £1.00. IN4148 5p; 6 for 27p; 12 for 48p.

LOW PRICE ZENER DIODES: 400mW; Tol. +5% at 5mA. Values available: 3V; 3.6V; 4.7V; 5.1V; 5.6V; 6.2V; 6.8V; 7.5V; 8.2V; 9.1V; 10V; 11V; 12V; 13V; 13.5V; 15V; 16V; 18V; 20V; 22V; 24V; 27V; 30V. All at 7p each; 5 for 33p; 10 for 65p. SPECIAL: 100 Zeners for £6.00.

***RESISTORS:** High stability low noise carbon film 5%, 1/2W at 40°C; 1/4W at 70°C. E12 series only - from 2.2Ω to 2.2MΩ ALL AT 1p EACH; 8p or 10 of any one value; 70p for 100 of any one value. SPECIAL PACK: 10 of each value 2.2Ω to 2.2MΩ (730 resistors) £5.00.

SILICON PLASTIC RECTIFIERS - 1.5 Amp - Brand new wire ended D027: 100 P.I.V. - 7p (4/26p); 400 P.I.V. - 8p (4/30p).

BRIDGE RECTIFIERS: 2 1/2 Amp. 200V - 40p; 350V - 45p; 600V - 55p.

SUBMINIATURE VERTICAL PRESETS - 0.1W only: ALL AT 5p each; 50Ω, 100Ω, 220Ω, 470Ω, 680Ω, 1K, 2.2K, 4.7K, 6.8K, 10K, 15K, 22K, 47K, 100K, 220K, 680K, 1M, 2.5M, & 5M.

PLEASE ADD 8% VAT TO ALL ITEMS EXCEPT THOSE MARKED WITH * WHICH ARE 12 1/2%. PLEASE ADD 20p POST AND PACKING ON ALL ORDERS.

Send S.A.E. for lists of additional ex-stock items. Wholesale price lists available to bona-fide companies. ALL EXPORT ORDERS PLEASE ADD COST OF SEA/AIR MAIL.

MARCO TRADING

Dept. P1, The Old School, Edstaston, WEM, Salop. Tel: WHIXALL (Salop) 464/5 (STD 094872) (Props: Minicost Trading Ltd.).

Sparkrite mk2

Capacitive discharge
electronic ignition kit

VOTED BEST
OF 8 SYSTEMS
TESTED BY
'POPULAR
MOTORING'
MAGAZINE



- * Smoother running
- * Instant all-weather starting
- * Continual peak performance
- * Longer coil/battery/plug life
- * Improved acceleration/top speeds
- * Up to 20% better fuel consumption

Sparkrite Mk. 2 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 15/30 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heat-sink, top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.

OPTIONAL EXTRAS

Electronic/conventional ignition switch. Gives instant changeover from "Sparkrite" ignition to conventional ignition for performance comparisons, static timing etc., and will also switch the ignition off completely as a security device, includes: switch connectors, mounting bracket and instructions. Cables excluded. Also available RPM limiting control for dashboard mounting (fitted in case on ready built unit).

CALLERS WELCOME. For Crypton tuning and fitting service — phone (0922) 33008.

PRICES INCLUDE VAT, POST AND PACKING.

Improve performance & economy NOW

POST TODAY!

Quick installation
No engine modification
required

Electronics Design Associates, Dept., REC/1
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 33652

Name

Address

Mk. 2 DIY Ass. Kit @ £11.80	Quantity	I enclose cheque/PO's for £
Mk. 2 Ready Built Negative Earth @ £14.97		
Mk. 2 Ready Built Positive Earth @ £14.97		Cheque No.
Ignition Changeover switches @ £4.30		
R.P.M. Limit systems in above units @ £2.42		Send SAE if brochure only required.

SMALL ADVERTISEMENTS

(Continued from page 381)

FOR SALE: 100 unmarked BZY88 50p. 25 unmarked 2W zeners 50p. 100 high wattage resistors 50p. S.A.E. for lists. Box No. G323.

FOR SALE: Telford Communications 2m. converter, G8AEV MK11. £10. G2UK, 21 Romany Road, Oulton Broad, Lowestoft, Suffolk.

ABS BOXES - Black with lids, brass corner inserts. 80 x 60 x 42mm. 35p. 100 x 75 x 42mm. 40p. 120 x 100 x 42mm. 45p. Please add 8% VAT and P&P. Nortek Engineering Ltd., 41a Harrowby Street, Farnworth, Lancs.

FOR SALE: Cassettes 10 - £10.00. S.A.E. for list. Box No. G324.

POSTAL ADVERTISING? This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list. - The Holborn Direct Mail Company Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407 6444.

FOR SALE: Books on Communications: Electronics: I.E.R.E. Journal Vol. 43: List. Transistor Checker. Transistor 2-Metre pre-amp. Wanted: "Microwave Journal" Hughes, 11 Henley Road, Ludlow, Salop.

FOR SALE: 4 1/2 in. reflector telescope, f/1900mm. Wooden tripod. 6mm. and 20mm. eyepieces. £50 o.n.o. Tony Weatherley, G3WDI, 16 Beverley Court, Carlton Colville, Lowestoft, Suffolk.

FREQUENCY LIST TRANSFERS. We have a limited supply of sheets of Dial Frequency Transfers in black. Short Wave frequencies 1.8Mc/s to 32Mc/s and 144Mc/s and 146Mc/s. Includes amateur band marker frequencies at 100kc/s points and other short wave frequencies from 2 to 32 Mc/s at every 500Kc/s points. Each frequency is repeated. Two sheets for 5p., five sheets for 10p., postage 7p. Data Publications Ltd., 57 Maida Vale, London, W9 1SN.

PERSONAL

JANE SCOTT FOR GENUINE FRIENDS. Introductions to opposite sex with sincerity and thoughtfulness. Details free. Stamp to: Jane Scott, 3/Con North St. Quadrant, Brighton, Sussex, BN1 3GJ.

ESSEX GARDENERS. Buy your Bedding and rock plants, shrubs, etc., also cacti from May's Nurseries, 608 Rayleigh Road, Hutton, Brentwood, Essex. Callers only. Monday to Saturday.

IF YOU HAVE ENJOYED A HOLIDAY on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from: — The Hon. Membership Secretary, The Broads Society, "Icknield," Hilly Plantation, Thorpe St. Andrew, Norwich, NOR 85S.

SPONSORS required for exciting scientific project. Norwich Astronomical Society are building a 30" telescope to be housed in a 20' dome of novel design. All labour being given by volunteers. Already supported by Industry and Commerce in Norfolk. Recreational, Educational. You can be involved. Write to: NAS Secretary, The Manse, Back Lane, Wymondham, Norfolk.

THE OPEN DOOR TO QUALITY



This catalogue — Electrovalue Catalogue No. 8 (Issue 2, updated) offers items from advanced opto electronic components to humble (but essential) washers. Many things listed are elsewhere very difficult to obtain. The company's computer is programmed to expedite delivery and maintain customer satisfaction. Attractive discounts are allowed on many purchases. Access and Barclaycard orders are accepted. **+FREE POSTAGE** on all C.W.O. mail orders over £2.00 list value (ex. V.A.T.) in U.K. If under, add 15p handling charge.

144 pages
Post paid
40p
inc. refund voucher worth **40p**

All communications to Dept. REC 1
28 St Judes Rd, Englefield Green, Egham, Surrey TW20 0HB
Phone: Egham 3603. Telex: 2644475. Shop hours 9-5.30, 9-1 pm Sats.
Northern Branch: 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone: (061) 432.4845. Shop hours 9-5.30, 9-1 Sats.

ELECTROVALUE LTD

MULLARD FERRITE CORES — LA3 100 to 500 kHz, 54p; LA5 30 to 100, kHz, 81p; LA7 < 10 kHz, 81p; LA13 for W.W. Oscilloscope, £1.50.

SPECIAL OFFER — Metallised Polyester Capacitors by Erie, Mullard, etc. Values include: .01/160V, .01/250V, .015/160V, .022/160V, .033/160V, .047/160V, .068/160V, .1/160-250V, .22/160V, etc. This is a bargain not to be missed. 100 for £2.00.

1N4148 **SWITCHING DIODES**, 10 for 30p; 50 for £1.25; 100 for £1.50; 1,000 for £12.50.

TRANSISTORS — All branded BC147, BC148, BC149, BC157, BC158, BC159, BF194, BF195, BF196, BF197, 8p each or 100 for £6.00.

Please note all prices include UK Postage and appropriate VAT @ 8% or 12½%

MAIL ORDER ONLY

XEROZA RADIO

1 EAST STREET, BISHOP'S TAWTON, DEVON

OVER 2,000 ELECTRONIC COMPONENTS IN A

BIG NEW FREE
100 PAGE CATALOGUE



YOURS BY POSTING TODAY

Please send me the 100 page Tandy catalogue

Name _____
Address _____
REC/6
Tandy Corporation (Branch UK), Bilsdon Road, Wednesbury, W Midlands WS10 7JN

TANDY

Nationwide supermarket of sound!

Denco Coils, Tuning Gangs, TTL C'MOS, Quartz Crystal, Vero, DVM Chips, Clock Chips, LED's, LCD's Displays, Transformers, Boxes, Cases, Knobs and millions of R's and C's, Transistors and Diodes. Oh, I forgot . . . Audio IC's.

It's all in our brand new illustrated catalogue. With every copy are 36p worth of vouchers absolutely FREE!

Send 35p inc. Free p&p to:

DEPT 6, CHROMASONIC ELECTRONICS
56 Fortis Green Road, London, N10 3HN
Telephone: 01-883 3705

BINOCULAR MAGNIFIER




FOR PRECISION CLOSE-UP WORK - LEAVES BOTH HANDS FREE
2, 2½ or 3x Model with Hinged Lens Mount

See close-up work with less eye strain. Lightweight adjustable headband. Powerful optically ground lenses. Can be worn over normal glasses. Essential Industry, Home Workshop, Collecting, Modelling, Jewellery, Watchmakers. Any fine work. DE LUXE model with superior quality lens. PLUS hinged lens mount. 2x model £9.95 + 75p p. & p., 2½x model £10.50 + 75p p. & p., 3x model £10.95 + 75p p. & p.

£9.95

MICROJET WELDER

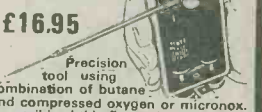A TINY FLAME UP TO 5000°F!
WELDS-BRAZES SOLDER
INC. FLAME TIPS



Precision tool using combination of butane and compressed oxygen or micronox. A pencil lead thin flame size, adjustable to 5000°F. Cuts metals, welds, brazes and solders gold, silver. Ideal electricians, opticians, dentists, silversmiths, modelling, jewellery, clockmakers, electronic and computer servicing. Up to 40 minutes use on fuel supplied. Replacement set of 2 micronox, 1 butane cylinder. £1.65 extra inc. post. Our price £16.95 + 90p p. & p.

£16.95

JOHN DUDLEY & CO. LTD., Dept RC8, 301 Cricklewood Lane, London NW2. Tel: 01-458 5917 Access accepted (Callers welcome)

H.M. ELECTRONICS

275a Fulwood Road, Broomhill SHEFFIELD S10 3BD Tel: 0742-669676

BEC CABINETS (Book End Chassis)

- Standard Cabinet GB2 14" x 7" x 3"
- GB1 14" x 6" x 2" GB3 14" x 9" x 4"
- GB1A 9" x 6" x 2" GB4 14" x 9" x 6"

Send 15p for wallet of leaflets.

A beautifully designed modern cabinet with simulated black leatherette top (PVC bonded to metal) solid wooden end cheeks, with room at the back for Output Sockets etc, felt pads are fitted on bottom of cheeks for non-scratch.

GOING DOWN?

LISTEN TO EXCITING 100-600KHz band with an L.F. CONVERTER. Includes 20dB gain antenna tuner and feeds 3.5-4MHz receiver. EASY to make, all parts, coils, printed circuit, case, etc., instructions, money back assurance. **ONLY £8.80 inc. post.**

CAMBRIDGE KITS 45 (EN) Old School Lane, Milton, Cambridge

RADIO & ELECTRONICS CONSTRUCTOR

Single Copies

Price **35p** each, postage 11p

Issue(s) required

Annual Subscription

Price **£5.00**, post free, commence withissue

Bound Volumes:

Vol. 27. August 1973 to July 1974	Price £2.40 , post & pkg 75p
Vol. 28. August 1974 to July 1975	Price £2.75 , post & pkg 75p
Vol. 29. August 1975 to July 1976	Price £3.10 , post & pkg 75p

CORDEX SELF-BINDERS

With title, 'RADIO & ELECTRONICS CONSTRUCTOR' on spine,
maroon only Price **£1.20**, post & pkg 30p

With no title on spine, maroon Price **£1.15**, post & pkg 30p

With no title on spine, green Price **£1.15**, post & pkg 30p

Prices include V.A.T.

DATA BOOK SERIES

DB5 TV Fault Finding, 132 pages	Price 90p , P. & P. 18p
DB6 Radio Amateur Operator's Handbook, 88 pages	Price 70p , P. & P. 12p
DB17 Understanding Television, 504 pages	Price £3.25 , P. & P. 60p
DB19 Simple Short Wave Receivers 140 pages	Price 80p , P. & P. 18p

STRIP-FIX PLASTIC PANEL SIGNS

Set 3: Wording — White Price **75p**, P. & P. 7p

Set 4: Wording — Black Price **50p**, P. & P. 7p

Set 5: Dials Price **38p**, P. & P. 7p

Prices include V.A.T. on Panel Signs

I enclose Postal Order/Cheque forin payment for

NAME

ADDRESS

(BLOCK LETTERS PLEASE)

Postal Orders should be crossed and made payable to Data Publications Ltd.

Overseas customers please pay by International Money Order.

All publications are obtainable through your local bookseller

Data Publications Ltd., 57 Maida Vale, London W9 1SN

PLEASE MENTION THIS MAGAZINE WHEN WRITING TO ADVERTISERS