

RADIO & ELECTRONICS CONSTRUCTOR

MAY 1979
Volume 32 No. 9

Published Monthly
(3rd of preceding Month)

First Published 1947

Incorporating The Radio Amateur

Editorial and Advertising Offices
57 MAIDA VALE LONDON W9 1SN

Telephone Telegrams
01-286 6141 Databux, London

© Data Publications Ltd., 1979. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription: £7.50, Overseas £8.50 (U.S.A. and Canada \$18.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers, please pay by cheque or International Money Order.

Technical Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that queries cannot be answered over the telephone, they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

Production— Web Offset.


WORKSHOP POWER SUPPLY — Part 1 by R. A. Penfold	534
NEWS AND COMMENT	540
ELECTROLYTIC CAPACITANCE METER — Suggested Circuit by G. A. French	542
NEW PRODUCT	544
SUSTAINED ALARM UNIT by Vincent S. Evans	545
IN NEXT MONTH'S ISSUE	546
DESIGNING REFLEX CIRCUITS — Part 1 by Sir Douglas Hall, Bt., K.C.M.G.	547
THE SNIPER — Part 1 by E. A. Parr	550
TUNE-IN TO PROGRAMS — No. 4 Take A Running Jump . . . by Ian Sinclair	554
ENLARGER METER by M. V. Hastings	558
VALVE HI-FI AMPLIFIERS — Class A Output Stages In Your Workshop	563
SHORT WAVE NEWS — For DX Listeners by Frank A. Baldwin	568
VHF MAINS TABLE RADIO — Part 2 (Conclusion) by R. A. Penfold	570
OPTO — ISOLATOR A.C. SWITCH TIL III Provides Control Voltage Isolation In A.C. Mains Switching Circuit by John Baker	573
NOR GATES — Electronics Data — No. 45 For The Beginner	iii

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London W9 1SN.

The *Radio & Electronics Constructor* is printed by Swale Press Ltd.

**THE JUNE ISSUE
WILL BE PUBLISHED
ON 4th MAY**

SUPERSOUND 13 HI-FI MONO AMPLIFIER

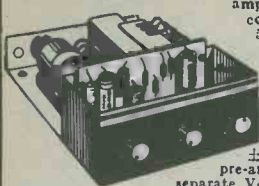

A superb solid state audio amplifier. Brand new components throughout.

5 Silicon transistors plus 2 power out-pull transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz. 30KHz \pm 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and

Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high \times 7" wide \times 7" deep. AC 200/250V. PRICE £16.00. P. & P. £12.00.

HARVERSONIC MODEL P.A. TWO ZERO


An advanced solid state general purpose mono amplifier suitable for Public Address system, Disco, Guitar, Gram., etc. Features 3 individually controlled inputs



(each input has a separate 2 stage pre-amp). Input 1, 15mv into 47k. Input 2, 15mv into 47k. (suitable for use with mic. or guitar etc.) Input 3 200mv into 1 meg Ω suitable for gram, tuner, or tape etc. Full mixing facilities with full range bass & treble controls. All inputs plug into standard jack sockets on front panel. Output socket on rear of chassis for an 8 ohm or 16 ohm speaker. Output in excess of 20 watts R.M.S. Very attractively finished purpose built cabinet made from black vinyl covered steel, with a brushed anodised aluminium front escutcheon. For ac mains operation 200/240v. Size approx. 12 1/2" w. x 5" h. x 7 1/2" d.

Special introductory price £28.00 + £2.50 carr. & pkg.

HARVERSONIC STEREO 44

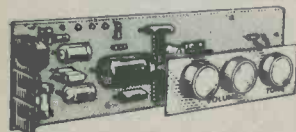

A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers. Using the latest high technology integrated circuit amplifiers with built in short term thermal overload protection. All components including rectifier smoothing capacitor, fuse, tone control, volume controls, 2 pin din speaker sockets and 5 pin din tape rec./play socket are mounted on the printed circuit panel, size approx. 9 1/2" \times 2 1/2" \times 1" max. depth. Supplied brand new and tested, with knobs, brushed anodised aluminium 2 way escutcheon (to allow the amplifier to be mounted horizontally or vertically), at only £10.00 plus 50p P. & P. Mains transformer with an output of 17V a/c at 500 m/a can be supplied at £2.00 plus 40p P. & P. if required. Full connection details supplied.

BEAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240v. Secondary combinations 0-5-10-15-20-25-30-35-40-60v. half wave at 1 amp, 0-10-0-10, 20-0-20, 30-0-30v. at 2 amps full wave. Size 3in. long \times 3 1/2in. wide \times 3in. deep. Price £3.20 P. & P. £1.20.

MAINS TRANSFORMER. For power supplies. Pri. 200/240v. Sec. 9-0-9 at 500 mA. £1.80 P. & P. 65p. Pri. 200/240v. Sec. 12-0-12 at 1 amp. £2.00 P. & P. 65p. Pri. 200/240v. Sec. 10-0-10 at 2 amp. £2.70 P. & P. 90p. Pri. 200/240v. Sec. 23v. at 1.5 amp, 6v at .6 amp, 8v. at 50 mA. £2.25 + 60p P. & P.


MAINS TRANSFORMER. Pri. 0,110 and 240 Sec. 28V at 1.8 amps. Also tapped at 12V -3 amp. Size 2 1/2in h x 3 1/2in w \times 2 1/2in d. £2.50 + £1 P. & P.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v battery or from H.T. line 200/300v. Frequency response 15Hz-25KHz. Gain 26dB. Size 1 1/2in \times 1 1/2in \times 1 1/2in. Brand new complete with instructions. Price £2.20. P. & P. 30p.


STEREO-DECODER SIZE, 2" \times 3" \times 1 1/2"

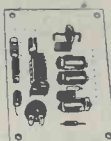Ready built. Pre-aligned and tested. Sens. 20-50mV for 9-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £6.00 plus 20p P. & P. Stereo beacon light if required 40p extra.



QUALITY RECORD PLAYER AMPLIFIER MK. II A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in wide \times 3in deep \times 6in high. Ready built and tested. PRICE £7.00. P. & P. £1.25 ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE £6.00. P. & P. £1.30.

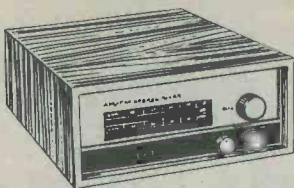MAINS OPERATED SOLID STATE AM/FM STEREO TUNER




200/240V Mains operated Solid State A/M F/M Stereo Tuner. Covering M.W. A.M. 540-1605 KHZ, VHF/FM 88-108 MHz. Built-in Ferrite rod aerial for M.W. Full AFC and AGC on AM and FM. Stereo Beacon Lamp Indicator. Built-in Pre-amps with variable output voltage adjustable by pre-set control. Max o/p Voltage 600 m/v RMS into 20K. Simulated teak finish cabinet. Will match almost any amplifier. Size 8 1/2" w. \times 4" h. \times 9 1/2" d. approx. LIMITED NUMBER ONLY at £28.00 + £1.50 P. & P.

SPECIAL OFFERS

Mullard LP1159 RF-IF Double Tuned Amplifier Module for nominal 470KHz. Size approx. 2 1/2" \times 1 1/2" \times 2" 7-6V + earth. Brand new pre-aligned. Full specification and connection details supplied. £2.25 + P. & P. 20p.

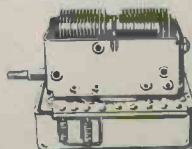Fye VHF/FM Tuner Head covering 88-108MHz. 10.7MHz IF output 7-8V + earth. Supplied pre-aligned, with full circuit diagram. Connection details supplied. Beautifully made with precision-grounded FM Gang and 323 Ft + 323 Ft AM Tuning Gang only £3-15 + P. & P. 35p.



PRECISION MADE

Push Button Switch bank. 8 Buttons giving 16 S/P C/O interlocked switches plus 1 Cancel Button Plus 3 d/p c/o. Overall size 5" \times 2 1/2" \times 1". Supplied complete with chrome finished switch buttons 2 for £1.80 + 20p, P. & P.

SPECIAL OFFER

Limited number only!

New but very slightly shop soiled transistor radios by well known manufacturer. Very smart and attractive vinyl covered with carrying handle.

AC mains or battery operated and covering VHF/FM and MW bands.

£10.00 + £1.30 p&p

Size 7in. H \times 9 1/2in. W \times 4in. D approx. Telescopic aerial for VHF/FM reception and internal ferrite aerial for AM bands, also earphone socket for personal listening. Uses four HP11 or SP11 batteries (not supplied).

LOUDSPEAKER BARGAINS

5in. 3 ohm £2.20, P. & P. 35p. 7 \times 4in. 3 ohm £2.80, P. & P. 45p. 10 \times 6in. 3 or 15 ohm £3.85, P. & P. 75p. 8 \times 5in. 3 ohm with high flux magnet £3.60, P. & P. 60p. Tweeter. Approx. 3 1/2". Available 3 or 8 or 15 ohms. £2.20, 30p P. & P.

VYNAIR & REXINE SPEAKERS & CABINET FABRICS app. 54 in. wide. Our price £2.00/yd. length. P. & P. 50p per yd. (min. 1 yd.). S.A.E. for samples.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 1 1/2" \times 1 1/2" \times 1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, etc. and used with or without baffle. Send S.A.E. for details. Only £2.40 each. P. & P. 90p for one, £1.10 for two. Now available in either 8" round version or 4" \times 8" rectangular. 10 watts R.M.S. 60Hz-20KHz £5.25 + P. & P. (one 65p, two 75p)

SONOTONE STANO COMPATIBLE STEREO CARTRIDGE

T/O stylus Diamond Stereo LP and Sapphire 78.


ONLY £2.50 P. & P. 20p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £3.00. P. & P. 20p.

LATEST CRYSTAL T/O STEREO/COMPATIBLE CARTRIDGE for EP/LP/Stereo 78. £2.00 P. & P. 20p

LATEST T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only £2.00 P. & P. 20p

STEREO MAGNETIC PRE-AMP sens. 3mV/in for 100m Volt 15 to 35V neg earth. Equ. \pm 1db. From 20 Hz to 20 KHz. Input impedance 47k. Size 1 1/2in \times 2 1/2in \times 5 1/2in. £2.60 + 20p P. & P.

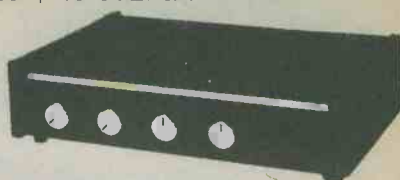HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT




A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Outputstage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specifications: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response \pm 3dB 12-30,000 Hz Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: \pm 3dB 12-15,000 Hz. Bass, boost approx. to \pm 12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall Size 12" w. \times 8" d. \times 2 1/2" h. Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S.A.E.

AMPLIFIER KIT £14.50 P. & P. 80p
(Magnetic input components 33p extra)
POWER PACK KIT £8.00 P. & P. 95p
CABINET £6.00 P. & P. 95p

Special offer — only £25.00 if all 3 units ordered at one time plus £1.25 P. & P.

Full after sales service

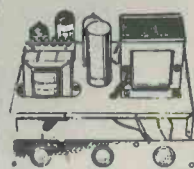Also available ready built and tested £31-25. P. & P. £1.50.



3-VALVE AUDIO AMPLIFIER HA34 MK II.

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" w. \times 4" d. \times 4 1/2" h. Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm


speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £8.50. P. & P. £1.40.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £8.00. P. & P. £1.40.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull.

Super reproduction of both music and speech, with negligible hum. Separate inputs for mlke and gram. Allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 25p \times S.A.E. (Free with parts). All parts sold separately. ONLY £16.50. P. & P. £1.40. Also available ready built and tested. £20.00. P. & P. £1.40.

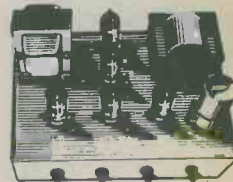

SPECIAL OFFER

Limited Number Only!

Goodmans Speakers, 6 1/2in.-8 OHM, long throw, ceramic magnet, full range rated 10 watts R.M.S. (when fitted in enclosure)

£4.00 + 80p p&p
(p&p on two £1.20)

OUR PRICES INCLUDE VAT AT CURRENT RATES

HARVERSON SURPLUS CO. LTD.

(Dept. REC) 170 MERTON HIGH ST., MERTON, LONDON, SW.18. Tel: 01-540 3985

A few minutes from South Wimbledon Tube Station

SEND SAE WITH ALL ENQUIRIES. FOR PERSONAL CALLERS ONLY: WE CAN NOW OFFER A FULL REPAIR SERVICE ON ALL HI-FI EQUIPMENT, DISCO, CASSETTES, CAR RADIO, ETC.

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday

Closed Wednesday.

Prices and specifications correct at time of press. Subject to alteration without notice

BUILD A PROJECT ON CSC

FREE

FILL IN COUPON & RECEIVE FREE COPY OF

ELECTRONICS BY NUMBERS PROJECT No 1 'TWO TRANSISTOR RADIO'


ELECTRONICS BY NUMBERS. TWO-TRANSISTOR RADIO.

Now using Experimentor Breadboards and following the instructions in "Electronics by Numbers" ANYBODY can build electronic projects.

Simply look at the diagram - this has exactly the same type of layout of all EXPERIMENTOR boards. Look at the component list and select the component Q1, this is an NPN transistor type 2N3904, this plugs into holes C10, D11, and B12.

Easy Isn't It?

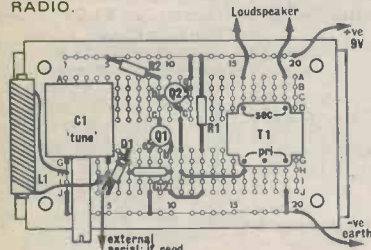Now take C2, which is a .1 uf capacitor, this plugs into holes H7 and H10. Do the same with all the components, connect a 9 volt battery and you have a perfect working TWO-TRANSISTOR RADIO.



YOU WILL NEED

- B1-9 VDC battery
- C1-365-pF variable capacitor
- C2-.1-uF capacitor
- D1-Diode, 1N914 or 4148 or equiv.
- L1-Standard broadcast loopstick antenna
- Q1-NPN transistor, 2N3904 or equiv.
- Q2-PNP transistor, 2N3906 or equiv.
- R1-100,000-ohm resistor, 1/4 watt
- R2-4700-ohm resistor, 1/4 watt
- S1-SPST switch
- T1-500:8-ohm matching transformer
- SPKR-8-ohm speaker

Building radios is lots of fun. Here's a loud-speaking crystal set. L1 and C1 form the circuit that tunes the radio. For better performance substitute a germanium diode such as IN34 or IN60.

These projects use components which are readily available from all suppliers and we've made a special effort to design the projects so that in many cases substituting close but wrong component values of different transistors will still result in a working circuit.

FILL IN THE COUPON AND WE WILL SEND YOU FREE OF CHARGE A COPY OF THE FULL PROJECT "TWO-TRANSISTOR RADIO".

PROTO-CLIP TEST CLIPS.

Brings IC leads up from crowded PC boards. Available plain or with cable with clips at one or both ends.



- PC - 16 pin. £2.75.
- PC - 16 pin with cable. £6.00.
- PC - 16 with cable and 16 pin clips at both ends. £10.25.



Europe, Africa, Mid-East: CSC UK LTD. Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ. Telephone: SAFFRON WALDEN 21682. Telex: 817477.

EXPERIMENTOR BREADBOARDS.

No soldering modular breadboards, simply plug components in and out of letter number identified nickel-silver contact holes. Start small and simply snap-lock boards together to build breadboard of any size.

All EXP Breadboards have two bus-bars as an integral part of the board, if you need more than 2 buses simply snap on 4 more bus-bars with the aid of an EXP.4B.

EXP.325. The ideal breadboard for 1 chip circuits. Accepts 8,14,16 and up to 22 pin IC's. **ONLY £1.60.**



EXP.350. £3.15. 270 contact points with two 20-point bus-bars.



EXP. 300. £5.75.



EXP. 650 for Micro-processors. £3.60.




EXP 4B. More bus-bars. £2.30.



ALL EXP.300 Breadboards mix and match with 600 series.

PROTO-BOARDS.

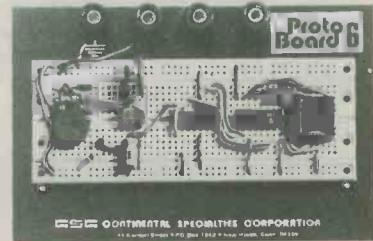THE ULTIMATE IN BREADBOARDS FOR THE MINIMUM COST. TWO EASILY ASSEMBLED KITS.



PB.6 Kit, 630 contacts, four 5-way binding posts accepts up to six 14-pin Dips.

PROTO-BOARD 6 KIT. £9.20.



PB.100 Kit complete with 760 contacts accepts up to ten 14-pin Dips, with two binding posts and sturdy base. Large capacity with Kit economy.

PROTO-BOARD 100 KIT £11.80.

HOW TO ORDER AND RECEIVE FREE COPY OF TWO-TRANSISTOR RADIO PROJECT.

It's easy. Give us your name and full postal address, in block capitals. Enclose cheque, postal order or credit card number and expiry date. OR telephone 0799 21682 and give us your Access, American Express or Barclaycard number and your order will be in the post that night.

EXPERIMENTOR BREADBOARDS.	CONTACT HOLES.	IC CAPACITY 14 PIN.DIP.	UNIT PRICE INCLUDING POSTAGE AND V.A.T.
EXP. 325	130	1	£ 2.53
EXP. 350	270	3	£ 4.21
EXP. 300	550	6	£ 7.29
EXP. 650	270	use with 0.6 pitch Dip's Bus-Bar Strip	£ 4.69
EXP. 4B.	Four 40 Point Bus-Bars		£ 3.29
TEST CLIPS			
PC. 16.			£ 3.78
PC. 16-18.			£ 7.56
PC. 16-18 Dual Clip.			£12.15
PROTO-BOARDS.			
PB. 6.	630	6	£11.01
PB. 100.	760	10	£13.82

NAME

ADDRESS

REC

<p>MOTORS 1-5 to 6VDC Model Motors, 20p. Sub. Min. 'Big Inch' Precision motors, 115VAC 3 rpm, 30p. 12VDC 5 Pole Model Motors 35p. 8 track 12VDC motors, new £1.25. Cassette Motors 6VDC ex. equip., 65p. Crouze geared motor, 115VAC 4 rpm new 95p. Smiths clock motor, synchronous 240VAC 1 rev per hour £1.75.</p>	<p>TRANSFORMERS All 240VAC Primary (postage per transformer is shown after price). MINIATURE RANGE: 6-0-6V 100mA, 9-0-9V 75mA and 12-0-12V 50mA all 73p each (15p). 12-0-12V 100mA 90p (15p). 0-6V, 0-6V, 280mA £1.10 (20p). 0-4-6-9V 200mA these have no mounting bracket, 65p (15p). 12V 2 amp 95p (22p). 12V 2 amp £2.25 (45p). 12V 4 amp £2.75 (45p). 15-0-15V 1 amp £2.10 (45p). 30-0-30V 1 amp £2.75 (54p). 20-0-20V 2 amp £3.50 (54p). 0-12-15-20-24-30V 2 amp £4.50 (54p). 20V 2.5 amp £2.20 (54p).</p>	<p>FETS Union carbide N channel FET similar to 2n3819 15p each. 3N140 or 8FW61 types 40p each. M203 dual matched pair of single gate mosfets in one can 40p. 2N5062 plastic (T092) SCR 100V 800mA 18p each. BX504 Opto isolators, 4 lead infra red led to photocell 25p each.</p>	<p>MISCELLANEOUS ITEMS MURATA 455KH Cer. Filters 35p each. PL259 Amphenol Plugs 43p. SO239 Chassis SKT for PL259 38p. PL259 Dummy Load - plug with 1 watt bulb and lens fitted - 52 ohms 1 watt 90p each.</p>	<p>TOOLS SOLDER SUCKER, plunger type, high suction, teflon nozzle, £4.75 (spare nozzles 65p each). Good Quality side cutters, insulated handles, 5" £1.35. Good Quality snub nosed pliers, insulated handles, 5" £1.35. Antex Model C 15 watt soldering irons, 240VAC £3.60. Antex Model CX 17 watt soldering irons, 240VAC £3.60. Antex Model X25 25 watt soldering irons, 240VAC £3.60. Antex ST3 iron stands, suits all above models £1.40. Antex heat shunts 12p each. Servisol Solder Mbp 45p each. Neon Tester Screwdrivers 8" long 40p each. Mlyama IC test clips 16 pin £1.75.</p>
<p>SEMICONDUCTORS All full spec. devices. 741 B pin 6 for £1. No. 555 Timers 22p each. TBA800 audio IC's 50p. 741S (wide bandwidth) 35p. LM380 80p. ZN414 Radio IC 75p. Mullard Orp61 30p. TIL305 alpha numerical displays £2.50. Miniature LDR's (same spec. as ORP12) 30p.</p>	<p>TRIAC/XENON PULSE TRANSFORMERS 1:1 (gpo style) 30p. 1:1 plus 1 sub. min. pcb mounting type 60p each.</p>	<p>DIODES IN4001 10 for 35p. IN4004 10 for 45p. IN4007 10 for 50p. BY127 10 for 75p. IN914 (numbered) 100 for £2.50. IN4148 (numbered) 100 for £2.25.</p>	<p>SURPLUS BOARDS No. 1, has 14 encapsulated 12V reed relays easily removable £1.95. No. 2, this has at least 11 C106 (50V 2.5A) plastic SCR's, one relay a unijunction transistor and tantalum capacitors £1.95. No. 3, I.F. Boards, these are a complete I.F. board assembly made for car radios, 465Khz, full set of IF's and oscillator coils, trimmers etc., 40p each. No. 4, Lamp flasher board, suitable for low load 240VAC applications, approx. 1 flash per second but can be varied via preset pot. 38p each.</p>	<p>SWITCHES Sub. miniature toggles; SPST (8 x 5 x 7mm) 45p. DPDT 8 x 7 x 7mm 50p. DPDT centre off 12 x 11 x 9mm 75p. PUSH SWITCHES, 16 x 6mm, red top, push to make 14p each, push to break version (black top) 16p each. SLIDE SWITCHES, all DPDT; 15 x 8 x 12mm 12p, 16 x 11 x 9mm 12p, 22 x 13 x 8mm 12p, 22 x 13 x 8mm centre off 13p. Multipole slider, double action 12 tags 29 x 9 x 11mm 24p.</p>
<p>PROJECT BOXES Sturdy ABS black plastic boxes with brass inserts and lid. 75 x 56 x 35mm 43p. 95 x 71 x 35mm 50p. 115 x 95 x 37mm 58p.</p>	<p>MICROPHONES ECM105 Condenser, Omni Directional, 600 ohms, on/off switch £2.95. EM506 Condenser Cardioid, Uni directional, 600 or 50K ohms 30-18Khz, heavy chromed copper case £12.95. DYNAMIC Stick mike, 5,000 ohms, on/off switch, fitted with std. jack £2.95. EM104 Sub. miniature tie pin condenser microphone, 1,000 ohms imp., 50-16Khz., uses deaf aid battery (supplied) £5.25. STANDARD CASSETTE MIKES, 200 ohms, fitted with 2.5/3.5mm jacks, on/off switch £1.25.</p>	<p>ZENERS BZY88 400mW 2V7 to 33V 6p each. BZX61 1.3 watt 7V5 to 33V 12p each.</p>	<p>POWER SUPPLIES 9 volt DC 120mA regulated supply, will replace PP9 etc., £2.25. SWITCHED TYPE, plugs into 13 amp socket, has 3-4.5-6-7.5 and 9 volt DC out at either 100 or 400mA, switchable £3.25. HC244R STABILISED SUPPLY, 3-6-7.5-9 volts DC out at 400mA max., with on/off switch, polarity reversing switch and voltage selector switch, fully regulated to supply exact voltage from no load to max. current £5.25.</p>	<p>MICRO SWITCHES Standard button operated 28 x 25 x 8mm make or break, new 15p each. Roller operated version of the latter, new 19p each. Light action micro, 3 amp make or break 35 x 20 x 7mm, 12p each. Cherry plunger operated micro, 2 normally open, 2 normally closed, plunger 20mm long (40 x 30 x 18mm) 25p each.</p>
<p>VERO POTTING BOXES 49 x 17 x 24mm, available in black or white with lid and 4 screws 39p each.</p>	<p>REPLACEMENT CRYSTAL INSERTS 35mm diam. x 10mm deep 45 each. DYNAMIC PA MICROPHONES, suitable for mobile use, hand held with thumb switch, curly lead. 50K imp. £3.40.</p>	<p>ELECTRICAL ITEMS Batien lampholders, Standard B.C. 25p. Angled version 28p. 13 amp rubber extension sockets, white 38p each. 13 amp plastic fused plugs (foreign) 25p each.</p>	<p>TOSHIBA LEDS TLG113 0.2" Green 13p. TLG115 0.2" Green diffused lens 14p. TLG1070 0.2" Green Flat top 14p. TLR120 0.2" Clear 17p. TOSHIBA TLR303 7 segment LED displays 0.3" Com. anode 65p. MAN3A min. (3MM) 7 segment LED displays Comm. anode 40p.</p>	<p>BUZZERS MINIATURE SOLID STATE BUZZERS, 33 x 17 x 15mm white plastic case, output at three feet 70db (approx), low consumption only 15mA, four voltage types available, 6-9-12 or 24VDC, 75p each. LOUD 12VDC BUZZER, Cream plastic case, 50mm diam. x 30mm high 60p. GPO OPEN TYPE BUZZER, adjustable, works 6-12VDC 25p each. SIREN, Rotary type, all metal, gives high pitched wail, adjustable bracket, 75 x 80 x 75 mm 12VDC £6.75.</p>
<p>VERO 'HAND HELD BOX' White ABS, 2.4" x 3.7" tapered, with screws 65p each.</p>	<p>RIBBON CABLE 8 way single strand miniature 20p per metre.</p>	<p>PUSH BUTTON TV TUNERS UHF, not varicap, transistorised new £2.25</p>	<p>RELAYS Clare Elliot sub. min. sealed relay 10 x 10mm 2 pole C/O, 1.250 ohm coil, new 75p. Miniature encapsulated reed relay 0.1 matrix mounting, single pole make, operates on 12VDC 50p each. Continental series, sealed plastic case relays, 24VDC 3pole change over 5 amp contacts, new 65p. 12VDC (130 ohm) 1 C/O, 3 make and 1 break contacts, new 65p each. Metal Cased Reed Relay, 50 x 45 x 17mm, has 4 heavy duty make reed inserts, operates on 12VDC 35p each.</p>	<p>ROCKER SWITCHES 2 amp SPST, single nut mounting, various colours (red, green, white, blue, yellow, black) 19p each. 250VAC 6amp rocker (all white) 21 x 15 x 13mm 17p each.</p>
<p>MULTIMETERS Big price reductions on pocket size testers. Model KRT100, 1,000 ohms per volt, mirror scale, range selector switch 1,000 volts AC/DC, 100K resistance, 150mA DC current £4.85. Model KRT101, same spec. as the KRT100, but range selection is via prod insertion £3.75.</p>	<p>SPECIAL OFFER SEMICONDUCTORS Plastic voltage regulators, 1 amp all now reduced in price, 7805, 7812, 7815, 7824 all 75p each. 7905, 7912, 7915, 7924 all 99p each. 3 types at give-away prices. LM309K T03 5V regulator only 75p each. LM340t 6 volt 1 amp regulator 40p each. 723 14 pin regulators 29p each.</p>	<p>TELEPHONE PICK UP COIL Sucker type with lead and 3.5mm plug 55p</p>	<p>DECON DALO ETCHING PEN With spare tip 72p.</p>	<p>TAPE HEADS Mono cassette £1.35. Stereo cassette £3.00. Standard 8 track stereo £1.75. BSR MNI330 1/4 track 50p. BSR SRP90 1/4 track £1.95. TD10 tape head assembly - 2 heads both 1/4 track R/P with built in erase, mounted on bracket £1.20.</p>
<p>CONTINUITY TESTERS Tubular with probe and croc. fly lead £1.35, with batts.</p>	<p>STOP PRESS New arrivals, 12 volt car stereo motors with pulley 55p. Car radio RF/IF and audio preamp boards 2 transistors, LM382 IC trimmers IF's etc., no info' 65p each.</p>	<p>TERMS: Cash with Order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive. S.a.o. for new illustrated lists.</p>	<p style="text-align: center;">PROGRESSIVE RADIO</p> <p style="text-align: center;">31 CHEAPSIDE, LIVERPOOL 2.</p>	
<p>MORSE KEYS Beginners practise key 95p. All metal fully adjustable type £2.45.</p>	<p>8 track stereo playback heads only 75p each. Car radio boards, complete with 6 transistors, IF's choke etc., these are new but no info available 75p each.</p>	<p>STOP PRESS New arrivals, 12 volt car stereo motors with pulley 55p. Car radio RF/IF and audio preamp boards 2 transistors, LM382 IC trimmers IF's etc., no info' 65p each.</p>		

SEMICONDUCTOR COMPONENTS

CERAMIC PAK

Containing a range of first quality miniature ceramic capacitors.

16160 - 24 - 3 of each value - 22p, 27p, 33p, 39p, 47p, 68p, 82p, 100p
 16161 - 24 - 3 of each value - 100p, 150p, 180p, 220p, 270p, 330p, 390p
 16162 - 24 - 3 of each value - 470p, 560p, 680p, 820p, 1000p, 15000p, 2200p, 2200p, 3300p
 16163 - 21 - 3 of each value - 4700p, 6800p, 0.01uf, 0.015uf, 0.022uf, 0.033uf, 0.47uf

ELECTROLYTIC PAKS

A range of paks each containing 18 first quality, mixed value miniature electrolytics.

16201 - values from 47mFD - 10mFD
 16202 - values from 10mFD - 100mFD
 16203 - values from 100mFD - 680mFD

CARBON RESISTOR PAKS

These paks contain a range of Carbon Resistors assorted into the following groups.

16213 - 60 mixed $\frac{1}{2}$ W 100ohms - 820ohms
 16214 - 60 mixed $\frac{1}{2}$ W 1K ohms - 8.2K ohms
 16215 - 60 mixed $\frac{1}{2}$ W 10K ohms - 83K ohms
 16216 - 60 mixed $\frac{1}{2}$ W 100K ohms - 820K ohms
 16217 - 40 mixed $\frac{1}{2}$ W 100 ohms - 820 ohms
 16218 - 40 mixed $\frac{1}{2}$ W 1K ohms - 8.2K ohms
 16219 - 40 mixed $\frac{1}{2}$ W 10K ohms - 82K ohms
 16220 - 40 mixed $\frac{1}{2}$ W 100K ohms - 820K ohms
 16230 - 60 mixed $\frac{1}{2}$ W 1 Meg - 10 Meg ohms
 16231 - 40 mixed $\frac{1}{2}$ W 1 Meg - 10 Meg ohms

COMPONENT PAKS

16164 - 200 Resistor mixed value approx (Count by weight) 60p
 16165 - 150 Capacitors mixed value approx (Count by weight) 60p
 16166 - 50 Precision resistors Mixed values 60p
 16167 - $\frac{1}{2}$ W resistors mixed values 80 60p
 16168 - 5 pieces assorted ferrite rods 60p
 16169 - 2 Tuning gangs MW/LV/VV 60p
 16170 - 1 Pak wire 50 meters assorted colours single strand 60p
 16171 - 10 Reed switches 60p
 16172 - 3 Micro switches 60p
 16173 - 15 Assorted pots 60p
 16174 - 5 Metal jack sockets 3 x 3.5 mm 2 x standard switch types 60p
 16175 - 30 Paper condensers - mixed values 60p
 16176 - 20 Electrolytics trans. types 60p
 16177 - 1 Pak assorted hardware - Nuts/bolts, connectors etc 60p
 16178 - 5 Mains slide switches assorted 60p
 16179 - 20 Assorted tag strips and panels 60p
 16180 - 15 Assorted control knobs 60p
 16181 - 3 Rotary wave change switches 60p
 16182 - 2 Relays 6-24V operating 60p
 16183 - 1 Pak copper laminate approx 200 sq inches 60p
 16184 - 15 Assorted fuses 100mA-5 amp 60p
 16185 - 50 metres PVC sleeving assorted size and colour 60p

METAL FOIL CAPACITOR PAK

Containing 50 metal foil Capacitor like Mullard C280 series. Mixed values ranging from .01uf - 2.2uf. Complete with identification sheet. O/N:16204 £1.20

SLIDER PAKS

16190 - 6 Slider potentiometers mixed values 60p
 16191 - 6 Slider potentiometers all 470 ohm 60p
 10k 1in 60p
 16193 - 6 Slider potentiometers all 22K 1in 60p
 16194 - 6 Slider potentiometers all 47K 1in 60p
 16195 - 6 Slider potentiometers all 47K log 60p

TRANSISTORS

BRAND NEW - FULLY GUARANTEED

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
AC126	£0.18	BC109A	£0.08	BC548	£0.10	BFY51	£0.16	TIP2955	£0.60	2N3708	£0.07
AC127	£0.18	BC109B	£0.09	BC549	£0.10	BFY52	£0.26	TIP3055	£0.50	2N3708A	£0.07
AC128	£0.16	BC109C	£0.10	BC550	£0.14	BP29	£0.38	TIS43	£0.22	2N3709	£0.07
AC128K	£0.26	BC147	£0.07	BC556	£0.14	BP20	£0.38	TIS90	£0.18	2N3710	£0.07
AC132	£0.20	BC148	£0.07	BC557	£0.13	BP19	£0.38	UT46	£0.20	2N3711	£0.07
AC134	£0.26	BC149	£0.07	BC558	£0.12	20MP	£0.80	ZTX107	£0.20	2N3819	£0.18
AC137	£0.20	BC157	£0.10	BC559	£0.14	BRY39	£0.45	ZTX108	£0.10	2N3820	£0.35
AC141	£0.22	BC158	£0.10	BD115	£0.50	BU105	£1.40	ZTX109	£0.10	2N3821	£0.60
AC141K	£0.30	BC159	£0.10	BD116	£0.80	BU105/	£0.80	ZTX300	£0.12	2N3823	£0.60
AC142	£0.20	BC167	£0.12	BD121	£0.85	02	£1.95	ZTX500	£0.13	2N4058	£0.12
AC176	£0.18	BC168	£0.12	BD124	£0.80	BU204	£1.40	2N1613	£0.20	2N4059	£0.14
AC176K	£0.28	BC169	£0.09	BD131	£0.35	BU205	£1.40	2N1711	£0.20	2N4060	£0.14
AC178	£0.25	BC169C	£0.10	BD132	£0.35	BU208/	£0.80	2N1889	£0.46	2N4061	£0.12
AC179	£0.25	BC170	£0.09	BD137/	£0.80	022	£2.25	2N1890	£0.45	2N4062	£0.12
AC187	£0.20	BC171	£0.09	BD138	£0.80	122	£0.38	2N1939	£0.38	2N4285	£0.18
AC187K	£0.28	BC172	£0.09	BD139	£0.40	MJE2955	£0.90	2N2147	£0.75	2N4285	£0.18
AC188K	£0.28	BC173	£0.09	BD135	£0.38	MJE3055	£0.60	2N2148	£0.70	2N4286	£0.18
AC181K	£0.28	BC177	£0.16	BD136	£0.35	MJE3440	£0.52	2N2160	£1.00	2N4287	£0.18
AC187	£0.18	BC178	£0.16	BD137	£0.35	MPF102	£0.28	2N2192	£0.38	2N4288	£0.18
AC187K	£0.28	BC179	£0.16	BD138	£0.35	MPF104	£0.35	2N2193	£0.38	2N4289	£0.18
AC188	£0.18	BC180	£0.25	BD139	£0.38	MPF105	£0.35	2N2194	£0.38	2N4290	£0.18
AC188K	£0.28	BC181	£0.25	BD140	£0.38	MPSA05	£0.20	2N2217	£0.22	2N4291	£0.18
AD140	£0.80	BC182L	£0.09	BD139/	£0.80	MPSA06	£0.20	2N2218	£0.22	2N4292	£0.18
AD142	£0.85	BC183	£0.09	140MP	£0.80	MPSA55	£0.20	2N2218A	£0.20	2N4293	£0.18
AD143	£0.75	BC183L	£0.09	BD155	£0.80	MPSA56	£0.20	2N2219	£0.20	2N4292	£0.55
AD149	£0.80	BC184	£0.09	BD176	£0.80	OC22	£1.50	2N2219A	£0.24	2N4293	£0.55
AD161	£0.35	BC207	£0.11	BD176	£0.80	OC23	£1.50	2N2904	£0.18	2N5135	£0.10
AD162	£0.35	BC208	£0.11	BD177	£0.68	OC24	£1.35	2N2904A	£0.21	2N5136	£0.10
AD162/	£0.70	BC209	£0.12	BD178	£0.68	OC25	£1.00	2N2905	£0.18	2N5138	£0.10
162MP	£0.70	BC212	£0.09	BD179	£0.75	OC26	£1.00	2N2905A	£0.20	2N5194	£0.55
AF114	£0.25	BC212L	£0.08	BD201/	£0.80	OC28	£0.38	2N2906	£0.18	2N5245	£0.40
AF115	£0.25	BC213	£0.09	202MP	£1.70	OC29	£0.95	2N2906A	£0.19	2N5294	£0.34
AF116	£0.25	BC213L	£0.09	BD203	£0.80	OC35	£0.95	2N2907	£0.20	2N5296	£0.34
AF117	£0.25	BC214	£0.09	BD204	£0.80	OC36	£0.90	2N2907A	£0.22	2N5457	£0.32
AF118	£0.40	BC214L	£0.09	BD203/	£0.80	OC70	£0.24	2N2926C	£0.09	2N5458	£0.32
AF124	£0.30	BC227	£0.18	204	£1.70	OC710	£0.15	2N2926V	£0.18	2N5459	£0.35
AF125	£0.30	BC238	£0.15	BOY20	£0.80	TIC44	£0.29	2N29280	£0.08	2N5551	£0.35
AF126	£0.30	BC251	£0.15	BOX77	£0.90	TIC45	£0.35	2N2928R	£0.08	2N6027	£0.34
AF127	£0.32	BC251A	£0.16	BF457	£0.37	TIP29A	£0.40	2N2928B	£0.08	2N6121	£0.70
AF139	£0.35	BC30A	£0.28	BF458	£0.37	TIP29B	£0.42	2N3052	£0.16	2N6122	£0.70
AF180	£0.80	BC302	£0.28	BF459	£0.38	TIP29C	£0.44	2N3054	£0.40	40311	£0.38
AF181	£0.85	BC303	£0.28	BF594	£0.30	TIP30A	£0.40	2N3055	£0.40	40313	£0.35
AF186	£0.80	BC304	£0.38	BF596	£0.28	TIP30B	£0.42	2N3414	£0.16	40316	£0.95
AF239	£0.38	BC327	£0.16	BF939	£0.24	TIP30C	£0.44	2N3415	£0.16	40317	£0.40
AL102	£1.20	BC328	£0.15	BF940	£0.25	TIP31A	£0.40	2N3416	£0.29	40326	£0.40
AL103	£1.18	BC337	£0.15	BF979	£0.28	TIP31B	£0.42	2N3417	£0.29	40327	£0.45
AL104	£1.40	BC338	£0.15	BF980	£0.28	TIP31C	£0.44	2N3614	£1.00	40345	£0.45
AU110	£1.40	BC440	£0.30	BFX29	£0.22	TIP32A	£0.40	2N3615	£1.05	40347	£0.55
AU113	£1.40	BC441	£0.30	BFX30	£0.30	TIP32B	£0.42	2N3616	£1.05	40348	£0.80
BC107A	£0.08	BC460	£0.38	BFX84	£0.22	TIP32C	£0.44	2N3646	£0.09	40380	£0.38
BC107B	£0.08	BC461	£0.38	BFX85	£0.24	TIP41A	£0.44	2N3702	£0.08	40361	£0.36
BC107C	£0.10	BC477	£0.20	BFX86	£0.25	TIP41B	£0.46	2N3703	£0.08	40362	£0.36
BC108A	£0.08	BC478	£0.20	BFX87	£0.22	TIP41C	£0.48	2N3704	£0.07	40405	£0.45
BC108B	£0.08	BC479	£0.20	BFX88	£0.22	TIP42A	£0.44	2N3705	£0.07	40407	£0.35
BC108C	£0.10	BC547	£0.10	BFX90	£0.56	TIP42B	£0.46	2N3706	£0.08	40408	£0.52
				BFY60	£0.16	TIP42C	£0.48	2N3707	£0.08	40409	£0.75

IC PAKS

Manufacturers "Fall-outs" which include functional and part numbers. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

16224 - 100 Gates assorted 7400 01 04: 10 50-60 etc £1.20
 16225 - 30 MIX Assortlet types 7441 47 90 154 etc £1.20
 16227 - 30 Assortlet Linear Types 709-741-747-748-710-588 etc £1.50
 16228 - 8 Assortlet types SL403 76013 7603 etc £1.00
 16233 - 5 I.C.'s ,6110 Egv. to MC1310P MA767 £1.50

JUMBO PAK SEMI CONDUCTOR

16222 Transistors Germ. and Silicon Rectifiers, Diodes, Triacs, Thyristors I.C.s and Zeners. ALL NEW & CODED. Approx 100 pieces. Offering the amateur a fantastic bargain PAK and an enormous saving £2.25

MAMMOTH I.C. PAK

16223 Approx 200 pieces assorted fall out integrated circuits including Logic, 74 series, Linear Audio and D.T.L. Many coded services but some unmarked - you to identify £1.20

UNTESTED SEMI-CONDUCTOR PAKS

16130 - 100 Germ. gold bonded OA47 diodes 60p
 16131 - 150 Germ point contact 100mA OA70/81 diode 60p
 16132 - 100 Silicon diodes 200mA OA200 60p
 16133 - 150 Silicon fast switch diode 75mA IN4148 60p
 16134 - 50 Silicon rectifiers top hat 750mA 60p
 16135 - 20 Silicon rectifiers stud type 3 amp 16136 - 50 400mW zeners D07 case 60p
 16137 - 30 NPN transistors BC107/8 plastic 60p
 16138 - 30 PNP transistors BC177/178 plastic 60p
 16139 - 25 NPN TO39 2N697/2N171 silicon 60p
 16140 - 25 PNP TO39 2N2905 silicon 60p
 16141 - 30 NPN TO18 2N706 silicon switching 60p
 16142 - 25 NPN BFY50/51 60p
 16143 - 30 NPN plastic 2N3904 silicon 60p
 16144 - 30 PNP plastic 2N3905 silicon 60p
 16145 - 30 400mW PNP 60p
 16146 - 15 plastic power 2N3055 NPN TO220 case £1.20
 16147 - 10 103 metal 2N3055 NPN £1.20
 16149 - 10 1 amp SCR TO39 £1.20
 16150 - 8 3 amp SCR TO66 case £1.20

74 SERIES TTL IC'S

BI-PAK STILL LOWEST IN PRICE. FULL SPECIFICATION GUARANTEED.

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
7400	£0.13	7409	£0.13	7441	£0.50	7481	£0.85	7492	£0.35	74122	£0.39
7401	£0.11	7410	£0.11	7442	£0.40	7482	£0.68	7493	£0.30	74123	£0.40
7402	£0.11	7411	£0.17	7445	£0.65	7483	£0.58	7494	£0.75	74141	£0.55
7403	£0.11	7412	£0.15	7446	£0.60	7484	£0.88	7495	£0.50	74154	£0.82
7404	£0.11	7413	£0.24	7447	£0.48	7485	£0.88	7496	£0.50	74180	£1.50
7405	£0.11	7414	£0.50	7448	£0.56	7486	£0.22	74100	£0.85	74181	

ambit international [®]

PARTS FOR CURRENT PW PROJECTS ... FROM AMBIT INTERNATIONAL

VHF FM monitor RX: A complete kit of parts for this project, which we firmly believe will be an established "standard" for years to come. The kit includes a 5 channel switched crystal oscillator added to the board end, using diode switching. Uses cheaper 3rd OT crystals, employing original oscillator as x3 stage. Price depends on filter selected (we have various types) and whether or not chip capacitors are required. More notes on the kit from our own lab. £25-£35 kit.

VMOS POWER TRANSISTORS FOR PW WINTON £9.95 pair * 2SK133/J48

FULL KITS FOR THE PW SANDBANKS METAL LOCATOR (should be ex stock)

FULL KITS FOR THE PW DORCHESTER

Radio ICs	
TDA1062	HF/VHF tunerhead 1.95
TDA1083	One chip AM/FM rx 1.95
TDA1090	One chip HiFi am/fm 3.35
TDA1220	One chip am/fm rx 1.75
HA1197W	HiFi AM tuner IC 1.40
CA3123E	AM tuner IC 1.40
TBA651	AM tuner IC 1.81
CA3089E	Famous FM IF system 1.94
CA3189E	As 3089+ deviation mute 2.75
	AF preamp, adj, agc 2.20
HA1137W	Improved S/N 3089 0.75
TBA120	limiting amp+detector 1.00
TBA120S	high gain 1.20
MC1350P	agc'd IF preamp 1.35
MC1330P	synch AM/video detector 0.65
KB406	Cascade IF preamp 1.95
uA753	limiting FM preamp 1.95
Communications circuits	
SD6000	DMOS RF/Mixer pair 3.75
KB4412	Bal mixers, IF+agc 2.55
KB4413	AM/SSB det, squelch, agc 2.75
KB4417	mic processor 2.85
MC3357	best thing in NBFM yet 3.12
MC1496P	popular double bal mixer 1.25
Multiplex decoders + noise blanker	
MC1310P	popular PLL decoder 2.20
uA758	buffered 1310 2.20
CA3090AQ	RCA PLL decoder 3.25
HA1196	improved PLL decoder with stereo preamps 3.95
HA11223	19kHz pilot cancel, low distortion, high S/N as HA11223 with remote 4.35
KB4437	VCO kill facility 4.55
KB4438	stereo MUTING preamp for post decoder mute 2.22
KB4423	impulse noise blanker 2.53

Discrete devices: more than ever:

BF960	800MHz/2.8dB nf mosfet	1.60*
BF961	200MHz/2.0dB nf	0.80*
40822	FM RF amp	0.43*
40823	FM mixer	0.51*
40673	Famous MOSFET	0.55*
2SJ49/2sK133	120v/100W MOSPOWER output devices	10.50*

LEDS: the best value today

	3mm	5mm	2.5x5mm
Red	0.14	0.14	0.17
Green	0.18	0.16	0.20
Yellow	0.18	0.15	0.20
Orange	0.22	0.29	0.24

100 off mix, 25% discount. All are AEG first grade types - absolutely no junk. 5mm clips for panel mounting 0.03 each

Misc. ICs for radio/audio applications

U237B	5 LED bargraph driver	0.80*
SAS6610	4 station touch tune IC	1.48*
SAS6710	adds 4 stations to 6610	1.48
MSM5523/4	LW,MW,SW and FM digital frequency readout plus clock, timers, stopwatch	£11*
MSM5526	LW/MW/FM DFM with direct drive for LCD	£11*
TCA730	DC volume control	3.50
TCA740	DC tone control	3.50
TDA1028	DC input switch	3.50
TDA1029	DC mode switch	3.50

Radio and Tuner modules

We cannot really list all the details we would like to here - but with advent of the new mark 3 tuner system, the Dorchester and matching AF units, Ambit offers you the widest choice ever, plus hardware and styling that matches the very high standards we have set in this new range.

At last, DIY Hi Fi which looks as if it isn't.

That's not to say it doesn't look like HiFi - just that it doesn't look like the usual sort of thing you have come to associate with DIY HiFi. The Mk3 outstrips and outperforms all British made HiFi tuners, and most imported ones too. Certainly at the price, there isn't one near it. But more than that, it looks superb. A small pic here would be an insult, so send an SAE for details on the kit that looks as if it isn't. It's something else.....


- * Exceptionally high performance - exceptionally straightforward assembly
- * Baseboard and plug-in construction. Future circuit developments will readily plug in, to keep the MkIII at the forefront of technical achievement
- * Various options and module line-ups possible to enable an installment approach to the system

and now previewing the matching 60W/channel VMOS amplifier:

- * Matching both the style and design concepts of the MkIII HiFi FM tuner
- * Hitachi VMOS power fets - characterized especially for HiFi applications
- * Power output readily multiplied by the addition of further MOSFETS
- * VU meters on the preamp - not simply dancing according to vol level
- * Backed with the usual Ambit expertise and technical capacity in audio

The PW Dorchester LW, MW, SW, & FM stereo tuner

THE DIGITAL DORCHESTER ALL BAND TUNER

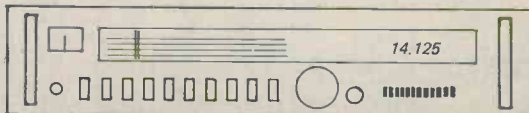

With styling and dimensions to fit in with the rest of AMBIT's new range of tuner & audio equipment.

When the new range of OKI digital frequency display ICs was announced, the original prototype of the Dorchester had been made - but since so many of you wanted to use the OKI frequency counterdisplay system with the Dorchester, we quickly designed a unit to incorporate the necessary facilities. The Digital Dorchester is designed in 19 inch form, and forms a perfect match for the other units in the range. If you don't want to go to the expense of the full Ambit DFM1 module, with AM/FM/Time/Timers, then the MA1023 clock module can be used instead.

The Dorchester has been described in PW Dec., Jan. and Feb. issues - but for those of you who may have missed it - it is an All Band broadcast tuner, covering LW/MW/SW and FM stereo in 6 switched ranges. Construction is very straightforward, with all the switching being PCB mounted - and the revolutionary TDA1090 IC used for AM/FM.

The electronics for the radio section of the Dorchester remain unchanged at £33.00, with 12.5% VAT. The hardware package, of case, meter, PSU now costs £33.00 + 8% with the MA1023 available for an extra £5 only.

For the fully digital version, with Ambit DFM1, the price is £56.50 + 8% VAT.

2 Gresham Road, Brentwood, Essex.



THIS is the Catalogue you need to solve your component buying problems!



- About 2,500 items clearly listed and indexed
- Profusely illustrated
- 128 A-4 size pages, bound in full-colour cover

- Bargain List of unrepeatabe offers included free
- Catalogue contains details of simple Credit Scheme
- Price includes packing and postage

Send the coupon today with cheque or P.O. for £1.25!

Please write your Name and Address in block capitals

NAME

ADDRESS



POST THIS COUPON WITH CHEQUE OR P.O. FOR £1.25

HOME RADIO (Components) LTD., Dept. RC
234-240 London Road, Mitcham, Surrey CR4 3HD
Regd. No. 912966, London

HOME RADIO (Components) LTD. Dept. RC, 234-240 London Road, Mitcham, CR4 3HD. Phone: 01-648 8422

OSTS

Since AMBIT introduced the "One Stop Technology Shop" to our service, we have been pleased to see just how many users of electronic components appreciate our guarantee to supply goods only from BS9000 approved sources. More than ever, professional and amateur electronics engineers cannot afford to waste time on anything less than perfect pedigree products.

SEE THE AMBIT AD TOO!

CD 4000 CMOS

4000	17p	4059	563p	4522	149p
4001	17p	4050	115p	4527	157p
4002	17p	4063	109p	4528	102p
4006	109p	4066	53p	4529	141p
4007	18p	4067	400p	4530	90p
4008	80p	4068	25p	4531	141p
4009	58p	4069	20p	4532	125p
4010	58p	4070	20p	4534	614p
4011	17p	4071	20p	4536	380p
4012	17p	4072	20p	4538	150p
4013	55p	4073	20p	4539	110p
4016	52p	4075	20p	4541	110p
4017	80p	4076	90p	4543	174p
4018	80p	4077	20p	4549	399p
4019	60p	4078	20p	4553	440p
4020	93p	4081	20p	4554	153p
4021	82p	4082	20p	4556	77p
4022	90p	4085	82p	4557	386p
4023	17p	4086	82p	4558	117p
4024	75p	4089	150p	4559	388p
4025	17p	4093	50p	4560	218p
4026	180p	4094	190p	4561	65p
4027	55p	4096	105p	4562	530p
4028	72p	4097	372p	4566	159p
4029	100p	4098	110p	4568	281p
4030	58p	4099	122p	4569	303p
4031	250p	4160	90p	4572	25p
4032	100p	4161	90p	4580	600p
4033	145p	4162	90p	4581	319p
4034	200p	4163	90p	4582	164p
4035	120p	4174	104p	4583	84p
4036	250p	4175	95p	4584	63p
4037	100p	4194	95p	4585	100p
4038	105p	4501	23p		
4039	250p	4502	91p		
4040	83p	4503	69p		
4041	90p	4506	51p		
4042	85p	4507	55p		
4043	85p	4508	248p		
4044	80p	4510	99p		
4045	150p	4511	149p		
4046	130p	4512	98p		
4047	99p	4513	206p		
4048	60p	4514	260p		
4049	55p	4515	300p		
4050	55p	4516	125p		
4051	65p	4517	382p		
4052	65p	4518	103p		
4053	65p	4519	57p		
4054	120p	4520	109p		
4055	135p	4521	236p		

Micromarket

6800 series	8216	1.95	2114	£10
	8224	3.50	2708	£10.55
6800P	6.50			
6820P	6.6			
6850P	2.75			
6810P	£4			
6852	3.65			
8080 series	2102	£1.70		
8080	6.30	2112	£3.40	
8212	2.30	2513	£7.54	
		4027	£5.78	

TTL: Standard AND LP Schottky

N'	LSN'	N'	LSN'	N'	LSN'	N'	LSN'	N'	LSN'				
7400	13	20	7455	35	24	74126	57	44	74185	134	74377	124	
7401	13	20	7460	17		74128	74		74188	275	74378	93	
7402	14	20	7463			74132	73	78	74190	115	74379	130	
7403	14	20	7470	28		74133		29	74191		74386	37	
7404	14	24	7472	28		74136		40	74192	105	180	74399	140
7405	18	26	7473	32		74138		60	74193	105	180	74395	139
7406	38		7474	27	38	74139			74194	105	187	74396	133
7407	38		7475	38	40	74141	56		74195	95	137	74398	180
7408	17	24	7476	37		74142	265		74196	99	110	74399	150
7409	17	24	7478	37		74143	312		74197	85	110	74445	92
7410	15	24	7480	48		74144	312		74198	150		74447	90
7411	20	24	7481	86		74145	65		74199	160		74668	110
7412	17	24	7482	69		74147	175		74248			74670	249
7413	30	52	7483A			74148	109		74249				
7414	51	130	7484	97		74150	99		74251				
7415		24	7485	104	99	74151	64	84	74252				
7416	30		7486		99	74153	64	54	74257				
7417	30		7489	205	40	74154	96		74258				
7420	16	24	7490	33	90	74155	54	110	74259				
7421	29	24	7491	76	110	74156	80	110	74260				
7422	24	24	7492	38	78	74157	67	55	74261				
7423	27	24	7493	32	99	74158			74266				
7425	27		7494	78		74159	210		74273				
7426	36	27	7495A	65	99	74160	82	130	74275				
7427	27	29	7496	58	120	74161	92	78	74279				
7428	35	32	7497	185		74162	92	130	74283				
7430	17	24	74100	119		74163	92	78	74290				
7432	25	24	74104	63		74164	104		74293				
7433	40	32	74105	62		74165	105		74295				
7437	40	24	74107	32	38	74166			74298				
7438	33	24	74109	63	38	74167	20		74324				
7440	17	24	74110	54		74168			74325				
7441	74		74111	68		74169		200	74326				
7442	70	99	74113	88		74170	230	200	74327				
7443	115		74112	68	38	74172	625		74352				
7444	112		74114		38	74173	170		74353				
7445	94		74116	198		74174	87	120	74362				
7446	94		74118	83		74175	87	110	74365				
7447	82		74119	119		74176	75		74366				
7448	56	99	74120	115		74177	78		74367				
7449		99	74121	25		74180	85		74368				
7450	17		74122	46		74181	165	350	74369				
7451	17	24	74123	48		74182	160		74373				
7453	17		74124			74183			74374				
7454	17	24	74125	38	44	74184	135	210	74375				

Voltage Regs

NEW LOW PRICES

7800 series UC TO220 package 1A all 95p
 7900 series UC TO220 package 1A all £1
 78MUC series TO220 package 1/2A all 90p
 78LCP series TO92 100mA all 35p

L200 up to 3A/adjustable V&A 195p
 78MGT2C 1/2amp adjustable volts 175p
 79MGT2C 1/2amp adjustable volts 175p
 723C precision controller 65p

MAINS FILTERS FOR NOISE/RFI etc
 1 amp in IEC connector £4.83
 5 amp in 'wire in' case £3.87
 NE550A 73p


TERMS: CWO psw, VAT to be added at 8% (inland), pp 25p per order. When ordering from the OSTs and Ambit - a single combined remittance and pp charge is sufficient. Account details OA.

2 Gresham Road, Brentwood, Essex.

The ICL7216BPI is still the cheapest way to make a full 8 digit 10MHz frequency counter/timer, and with 10 external components + display - it is also one of the simplest. For £19.82, it takes a lot of beating. The mains filters have been extended now to include a 6amp IEC version at £5.10, and with the amount of electronic noise on the average supply (next door's fridge, for instance) it is a really worthwhile addition to any sensitive equipment. LPSN TTL now includes many more of latest types, all - of course - are absolutely prime first quality types. And don't forget our range of OPTO displays includes Hewlett Package high efficiency 0.43" types in all colours - renowned as the finest quality in the market. For other types of component - discrete LEDs, radio and audio devices, tuner modules, kits etc, see our other advertisement for more details - or send for the AMBIT catalogue system. Part one (45p) includes details of our background 'standard' items, and the new part two includes all the latest introductions and developments, plus a rundown on OSTs.

Electronics. Make a job of it....

Enrol in the BNR & E School and you'll have an entertaining and fascinating hobby. Stick with it and the opportunities and the big money await you, if qualified, in every field of Electronics today. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY AND GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam successes. We are the only privately run British home study College specialising in electronics subjects only. Full details will be gladly sent without any obligation.

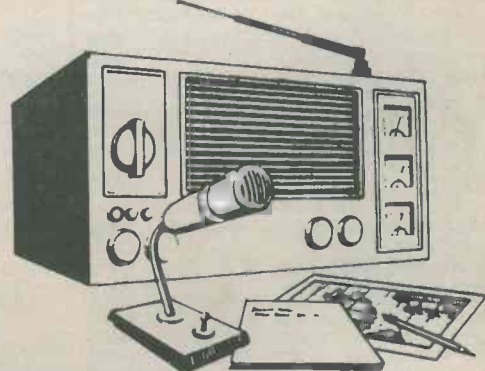

Become a Radio Amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

Brochure without obligation to:

British National Radio & Electronic School
 P.O. Box 156, Jersey, Channel Islands.

NAME _____
 ADDRESS _____

Block caps please

TRADE COMPONENTS

PAY A VISIT — THOUSANDS MORE ITEMS BELOW WHOLESALE PRICE. PRICE. CALLERS PAY LESS AS PRICES INCLUDE POSTAGE. PRICES INCLUDE VAT AND ADDITIONAL DISCOUNT ON MANY ITEMS IN LIEU OF GUARANTEE. GOODS SENT AT CUSTOMERS RISKS UNLESS SUFFICIENT ADDED FOR REGISTRATION OR COMPENSATION FEE POST.

OFFERS CORRECT AT 3/3/79 APPLICABLE TO ORDERS RECEIVED DURING APRIL

JAP 4 gang min. sealed tuning condensers 40p

VALVE BASES

Printed circuit B7G	7p
Chassis B7-B7G	11p
Shrouded Chassis B7G-B8A	13p
B12A tube. Chassis B9A	13p
Speaker 6" x 4" 5 ohm ideal for car radio	£1.55
4 1/2" diam. 30 Ω	£1.75
2 1/2" diam. 32 or 8 Ω	£1.07
TAG STRIP—6 way 4p	5 x 50pF or 1000 +
9 way 6p Single 1 1/2p	300pF trimmers 35p

Car type panel lock and key 65p

Transformer 9V 4A £3.78

Aluminium Knobs
for 1/4" shaft. Approx. 5/8" x 7/8" with indicator
Pack of 5 95p

ELECTROLYTICS Many others in stock

Up to 10V 25V 50V 75V 100V 250V 350V 500V MFD	63—	200—	300—	450—
10	6p	7p	7p	10p
25	6p	7p	7p	10p
50	6p	7p	7p	12p
100	7p	8p	13p	15p
250	12p	13p	15p	22p
500	13p	15p	22p	30p
1000	16p	27p	50p	60p
2000	28p	47p	55p	93p

As total values are too numerous to list, use this price guide to work out your actual requirements 8/20, 10/20, 12/20, 22/50, 47/25. Tub. Tant 24p each 16-32/275V, 100/150V, 100-100/275V 40p 50-50/385V, 2+2/200V non polar, 32-32-50/300V, 20-20-20/350V 0.1+0.1/500V AC 80p 200V, 100-200-60/300V £1.30 100-300-100-16/300V £1.85

RS 100-0-100 micro amp null indicator
Approx. 2" x 3/4" x 1/2" £1.85

INDICATORS

Bulgin D676 red, takes M.E.S. bulb 38p
12 volt, or Mains neon, red pushfit 23p
R.S. Scale Print, pressure transfer sheet 12p

CAPACITOR GUIDE — maximum 500V
Up to .01 ceramic 4 1/2p. Up to .01 poly 6p .013 up to .1 poly etc. 7p. .12 up to .68 poly etc. 8p. Silver mica up to 360pF 10p, then to 2,200pF 13p; then to .01 mfd 21p.
1/750 13p. .01/1000, 8/20, .1/900, .22/900, 4/16, 25/250 AC (600v/DC), 3/600 15p. 5/150, 10/150, 40/150 50p.

Many others and high voltage in stock.

SONNENSCHNEIN/POWERSONIC DRI-FIT RECHARGEABLE SEALED GEL (Lead Antimony) BATTERY, 6V 1 amp.hr. (3 1/2" x 2" x 1 1/2") £3.70.
6 amp. hr. (4 1/2" x 2" x 3") £7.60
Ex-equipment, little used.

CONNECTOR STRIP

Belling Lee L1469, 4 way polythene. 9p each

1 1/2 gass fuses 250 m/a or 3 amp (box of 12) 20p
Bulgin 5mm Jack plug and switched socket (pair) 40p
Reed Switch 28mm, body length 11p

Aluminium circuit tape, 1/8 x 36 yards—self adhesive. For window alarms, circuits, etc. 95p

TV MAINS DROPPERS

5 assorted multiple units for 75p

100pF air-spaced tuning capacitor 1.30
5 1/2" x 2 1/2" Speaker, ex-equipment 3 ohm 65p
2 Amp Suppression Choke 10p
3 x 2 1/2" x 1 1/2" } PAXOLINE 5 for 35p
4 1/2" x 1 1/2" x 1 1/2" } 10 for 15p
PVC or metal clip on MES bulb Holder 5 for 30p
VALVE RETAINER CLIP, adjustable 5 for 15p

Sub-miniature Transistor Transformer 35p
Valve type output transformer 90p

POT CORES with adjuster
LA2508-LA2519 43p per pair

16 Watt Power Amp. Module
35v 1A power required, giving 16 watt RMS into 8 Ω £3.45

REGULATED TAPE MOTOR
Grundig 6V approx., 3" x 1 1/2", inc. shock absorbing carrier; or Jap 9V, 1 1/2" diam. £1.05

3.5mm metal stereo plug 30p
Fane 8 ohm 3" sq. heavy duty communications speaker £1.60

RS neg. volt regulator 103, 306-099 (equiv. MPC900) 10A, 100 watt 4-30 volt. Adjustable short circuit protection. Normally £12.50+ £6.65

BOXES — Grey polystyrene 61 x 112 x 31mm, top secured by 4 self tapping screws 57p clear perspex sliding lid, 46 x 39 x 24 mm 15p.

ABS, ribbed inside 5mm centres for P.C.B., brass corner inserts, screw down lid, 50 x 100 x 25mm orange 65p; 80 x 150 x 50mm black 97p; 109 x 185 x 60mm black £1.52.

DIECAST ALI superior heavy gauge with sealing gasket, approx 6 1/2" x 2 3/8" x 1 3/8" £1.50; 3 3/4" x 2 3/8" x 1 3/8" £1.25.

VARIABLE CAMM PROGRAMMER 10, 12 or 15 pole 2 way, 50VAC motor — series with 1mfd, or 3k 10W or 15W pygmy bulb for mains operation. Ex equipment £4.32

SWITCHES

Pole	Way	Type	Price
1	2	Slide	15p
6	2	Slide	24p
2	1	Rotary Mains	28p
2	2	Rotary Mains	30p
2	3	Miniature Slide	20p
2	1	Toggle	42p
1	2	Sub-Min Toggle	75p
2	Alternating	2A Mains Push (1/2" hole)	43p
2	Alternating	Slide	15p

S.P.S.T. 10 amp 240v. white rocker switch with neon. 1" square flush panel fitting 60p; 1 pole 2 way 10 amp oblong clip in mains rocker appliance switch 38p

Standard thumb-wheel switch 0-9 in 1248N or B.C.D.. or Comp. 1242 also 2p co. £1.20
Standard Lever Key Switch, D.P.D.T. locking plus D.P.D.T. and S.P.S.T. Heavy Duty non latching 82p

AUDIO LEADS

3 pin din to open end, 1 1/2yd, twin screened 45p
5 pin din 180° to 2-phono 70p
3 pole Jack plug to tag ends, 4ft 75p

COMPUTER & AUDIO BOARDS/ASSEMBLIES
VARYING CONTENTS INCLUDE ZENER, GOLD BOND, SILICON, GERMANIUM, LOW AND HIGH POWER TRANSISTORS AND DIODES, HI STAB RESISTORS, CAPACITORS, ELECTROLYTICS, TRIMPOTS, POT CORES, CHOKES, INTEGRATED CIRCUITS, ETC.
3lb for £2 7lb for £3.70

1k horizontal preset with knob 10 for 40p
3" Tape Spools 5p
1" Terry Clips 5p
12 Volt Solenoid 40p

ENM Ltd. cased 7-digit counter 2 1/2 x 1 1/4 x 1 1/4 approx. 12V d.c. (48 a.c.) or mains £1.10

Auto charger for 12v Nicads, ex-new equipment £5.19

Miniature 0 to 5mA d.c. meter approx 1/8" diameter £1.25

RS Yellow Wander Plug Box of 12 40p

18 SWG multicore solder 3 1/2p foot

SAPHIRE STYLII. 15 different; dual and single point, current and hard to get types. My mix £2.

RESISTORS

1/4-1/2 watt 1 1/2p
1 watt 3p
Up to 15w w/wound 10p
1 or 2% 4 times price

Cinch 8 way std 0.15 pitch + edge connector 25p

RELAYS

RS/Alma reed relay, 3k Ω 18-30v d.c. coil, normally open 60p
12v d.p.c.o. heavy duty octal £1
700 Ω, 11-13v Min Sealed 2 p.c.o. £1
4 p.c.o. £1.20.

POTS

Wirewound 38p
Log. or Lin., carbon rotary or slide. Single 30p With switch 40p Dual 45p
Dual switch 55p 1.5m Edgetype 10 for 40p

Skeleton Presets

Slider, horizontal or vertical standard or submin 8p

THERMISTORS and V.D.R.'s

C21/2/6/11/14, KR22, KT150, VA1005/6/8/1010/1033/4/7/8/9 1040/1053/5 /1066/7/1074/6/7 / 1082/6/1091/6/7/8 / 1100/3/8/8602. Rod with spot blue/fawn/green.
E299DDP120 / 218 / 224 / 338 / 340 / 350 / 352 / YF020 E220ZZ/02 / KR150 All 22p
E23 glass bead 85p
YG150-S534 bead, KB13, E299 DHP230, 116-121 401 (TH7. VA1104. OD10) 35p. R53 Glass £1.20

BRIAN J. REED

161 ST. JOHNS HILL, BATTERSEA, LONDON SW11 1TO
Open 10 a.m. till 7 p.m. Tuesday to Saturday. VAT receipts on request.
Terms: Payment with order Telephone: 01-223 5016

Digital count unit. Counts in steps of 1, 2, 5 or 10 with total limit switch (2 x D.I.L. BCD), reed relay remote output. Mains power supply, relay and delay unit. UNUSED. Displays on 2 Minitron. 7 segments sold separately. £5.40

ACOS DUST JOCKEY Automatic record cleaner £1.30

Mail Order Over £50 deduct 10%. Over £100 deduct 20%

Burglar alarm, cord-operated for windows, doors, luggage and personal attack. Battery powered 86p

McMurdo 4 or 8 way plug and socket ex-equipment 50p

"Makaswitch" 1p 10-way water 15p Wood cased 8-12V buzzer £2.50

DEAC rechargeable NICAD 450K. Capacity 6V 450 m.a.h. at 10 hour rate. Ex-new equipment £4.11

Crouzet 30-minute timer-programmer, multi-variable contacts £7.56

ACOS DUST JOCKEY Automatic record cleaner £1.30

Mail Order Over £50 deduct 10%. Over £100 deduct 20%

Burglar alarm, cord-operated for windows, doors, luggage and personal attack. Battery powered 86p

McMurdo 4 or 8 way plug and socket ex-equipment 50p

DEAC rechargeable NICAD 450K. Capacity 6V 450 m.a.h. at 10 hour rate. Ex-new equipment £4.11

100 Electrolytics £3.00
 100 Resistors 1W £2.00
 100 Wirewound Resistors £4.50
 Well mixed values and voltages

100 Capacitors £2.50
 100 Resistors up to 1W £1.00
 100 Resistors 2-5W £3.00
 100 1% & 2% Resistors £3.50

Mullard + 12-0-12V 1A, 4A stabilized, regulated, power supply. £12.00
 27V 5A Double section bobbin transformer £4.32

UK & EIRE — Postal Orders for same day service. Cheques require 8 days from a Tuesday banking to ensure clearance. export — banker's draft (sterling) same day service. Foreign currency money orders etc. can lose value and take 4-6 weeks to clear.

C90 Cassette Tape 62p

50 ohm BNC plug, through connector or round or flanged chassis socket. TNC plug or N plug or through connector 65p each

250 Ω 50 watt + Resistor 40p

SEMICONDUCTORS Full spec. by Mullard etc. Many others in stock

AC126/12B/176 20p	BD113 57p	BFX84/88.89 20p
ADY29 22p	BD115 35p	8FY51 16p
AD161/2 match pr. 85p	BD116(BRC116T) £1.15	BFY90 57p
ADZ12 £4.00p	BD130Y £1.50	BR101 34p
AF116 20p	BD131/2/3 40p	BRV39/56 29p
AF124/6/7 28p	BD135/6/7/B/9 35p	BSV64 36p
AF139 23p	BD137/138 match pr. 82p	BSV79/80 F.E.T.s 90p
AF178/80/81 35p	BD140/142 35p	BSV81 Mosfet £1.00
AF239 35p	BD201/2/3/4 92p	BSX20/21 36p
ASU27/73 35p	BD232/3/4/5/8 55p	BSY40 30p
AY110/113 £2.50	BDX77 £1.15	BSY95A 14p
BC107/8/9 + A/B/C 8p	BD437 58p	BU204+Mount Kit £1.85
BC147/8/9 + A/B/C 8p	BF115/167/173 18p	BU208 £2.28
BC157/8/9 + A/B/C 8p	BF178/9 23p	CV7042 (OC41/44 ASY63) 12p
BC173 8p	BF180/1/2/3/4/5 18p	GET111/E112 45p
BC178A/B 179B 14p	BF194/5/6/7 8p	OC45(ME2) 13p
BC184C/LC 11p	BF194A, 195C 8p	ON222 23p
BC186/7 23p	BF200 258 324 23p	R2008B/20108 £2.30
BC213L/214B/238 13p	BF262/3 35p	TIP30 60p
BC327/8 337/8 10p	BF336/274 31p	TIS43 (2N2646) 39p
BC547/8+A/B/C 13p	BF528 Dual Mosfet £1.15	uA7805 £1.85
BC556/7/7B/8/9 11p	BF761 40p	ZT1486 £1.15
BCX32/36 15p	BFW10/11 F.E.T. 46p	ZTX300/341 9p
BCY31 90p	BFW30 £1.15	2N393 (MA393) 35p
BCY70/1/2 14p	BFW57/58 21p	2N456A 67p
BCZ11 32p	BFX12/29/30 23p	2N706A 18p

Amp	Volt	BRIDGE RECTIFIERS
1	1,600	BYX10 34p
1	140	OSH01-200 30p
5	100	Ex Equip 73p
0.6	110	EC433 20p
2 1/2	400	Texas £1.10
3 1/2	100	I.R. 48p
		B40C 3200 58p

RECTIFIERS		Amp	Volt
M1	1	68	5p
1N4005/6	1	6/800	8p
1N4007/BYX94	1	1250	8p
BY103	1	1,500	21p
SR100	1.5	100	9p
SR400	1.5	400	10p
REC53A	1.5	1,250	16p
LT102	2	30	16p
BYX22-200	1 1/2	300	26p
BYX38-300R	2.5	300	48p
BYX38-600	2.5	600	52p
BYX38-900	2.5	900	60p
BYX38-1200	2.5	1,200	65p
BYX49-300R	3	300	35p
BYX49-600	3	600	42p
BYX49-900	3	900	47p
BYX49-1200	3	1,200	60p
BYX48-300R	6	300	47p
BYX48-600	6	600	60p
BYX48-900	6	900	70p
BYX48-1200R	6	1,200	92p
BYX72-150R	10	150	42p
BYX72-300R	10	300	62p
BYX72-600R	10	600	65p
BYX42-300	10	300	36p
1N5401	3	100	16p
1N5402	3	200	18p
MR856	3	600	24p
BYX42-900	10	900	92p
BYX42-1200	10	1,200	£1.07
BYX46-300R*	15	300	£1.19
BYX46-400R*	15	400	£1.75
BYX46-500R*	15	500	£2.00
BYX46-600*	15	600	£2.30
BYX20-200	25	200	72p
BYX52-300	40	300	£2.05
BYX52-1200	40	1,200	£2.90
RAS310AF*	1.25	1,250	48p

*Avalanche type

Amp	Volt	TRIACS
25	900	BTX94-900 £4.50
25	1200	BTX49-1200 £6.75

Diode Characteristic, Equip., and Substitution Book 82p

Transistor equivalents and substitution Book 1 38p Book 2 82p

Chrome Car Radio fascia 28p

Rubber Car Radio gasket 10p

DLI Pal Delayline 90p

Relay Socket miniature 2PCO 20p

2B pin d.i.l. socket low profile 38p

Colour EHT Tray 3000/3500 £5.50

Nylon self-locking, 3 1/2" tie clips 1.5, 10, 22 or 750 μh choke 12p

0-30, or 0-15, black pvc, 360° dial, silver digits, self adhesive 4 1/2" dia. 13p

Mullard Semiconductor, Valve & Component Data Book 1976-78 60p

OPTO ELECTRONICS	
Diodes	Photo transistor
BPX40 57p	BPX29 92p
BPX42 92p	OCPT1 75p
BPY10 92p	
(VOLTAGE)	
BPY68 92p	L.E.D.'s
BPY69 92p	2" Red 16p
BPY77 92p	TIL209 .125" Red 14p
	Green 16p
Wire end neons 9p	

PHOTO SILICON CONTROLLED SWITCH
 BPX66 PNP 10 amp £1.15

3" red 7 segment L.E.D. 14 D.I.L. 0-9 + D.P. display 1.9v
 19m/a segment, common anode £2.25
 RS 0.6in. green £2.25
 Minित्रon 0.3in 3015F filament £1.25

CQY11B L.E.D. Infra red transmitter £1.15
 One fifth of trade

R.S. Battery Holder for 4 x HP/SP 11 30p

McMurdo PP108 8 way edge plug 12p
 Multicore Solder 1kg. 16 or 18 or 20 s.w.g. 60/40 £5.00
 3 inch 8 Ω speaker £1.15

New unmarked, or marked ample lead ex new equipment	
ACY17-20 10p	TIC44 28p
AS220 10p	G240 £1.17
AS221 35p	G2302 6p
BC186 13p	G2401 6p
BCY30-34 24p	2N711 28p
BCY70/1/2 10p	2N2926 6p
BY126/7 5p	2N598/9 8p
HG1005 12p	2N1091 10p
HG5009 4p	2N1302 10p
HG5079 4p	1N1907 £1.17
L78/9 4p	Germ. diode 2p
M3 12p	2N3055 5p
OA81 4p	Motorola 36p
OA47 4p	GET120 (AC128) 32p
OA200-2 4p	2N3055 5p
OC23 27p	GET872 16p
OC200-5 24p	2S3230 34p
C106 THY 38p	TIS43 25p

MINIATURE EDGE METERS
 100μA f.s.d., scaled 0.5. 12V illuminated blue perspex front, 35mm x 14mm £3.45
 200μA level meter, clear front. 10 x 18mm £1.20

2N21412 80p
2N2483 28p
2N2904/5/6/7/7A 18p
2N3053 16p
2N3055 R.C.A. 60p
2N3133/4062 56p
2N3553 24p
2N4037 39p
2N5484 FET 39p
2N5956 87p
2SA141/2/360 36p
2SB135/6/457 24p
2SC372/644/735 15p
2SC853 30p
40250 (2N3054) 35p

CATALOGUE
 30 A4 magazine size illustrated pages listing thousands of items, photo printed on day requested, from constantly updated masters, to ensure latest stock position. 75p plus large 16p s.a.e. (refundable with order).

TRANSFORMERS
 Ferromag C core. Screens 95-105-115-125-200-220-240v input output 17v 1/2 A, X, 2 + 24-0-24v 1.0A-2.0v. T.M.A. these current ratings can be safely exceeded by 50%. £4.90
 Cassette Dynamic Microphone with switch and twin plug £1.80
 Telephone Pickup, sucker with lead and 3.5 plug. 70p

THYRISTORS	
Amp	Volt
1	240
1	400
1	240
4	500
15	500
6.5	500
20	600
15	800

PAPER BLOCK CONDENSER
 0.25MFD 800 volt 87p
 1MFD 250 volt 54p
 1MFD 400 volt 65p

TV KNOB
 Dark grey plastic for recessed shaft (quarter inch) with free shaft extension 8p

CHASSIS SOCKETS
 Car Aerial 11p, Coax 8p, 5 pin 180° 11p, 5 or 6 pin 240° din 8p, speaker din switched 13p, 3.5 mm switched 7p, stereo 1/4" jack enclosed 20p.

SPECIAL OFFERS
 2500 mfd. 40v 56p
 0.1 mfd. 350/500v 10 for 50p
 10000 mfd. 15v 3 for £1.16
 6800 mfd. 10v 3 for 90p
 32+32/275v 3 for 90p
 16+32/275v 3 for 80p
 8+8 mfd. 375v4 for 90p
 1 mfd. non-polar 350v 10 for £1.19
 25000 mfd. 25v 65p
 12000/12v 3 for £1.16
 G.E.C. 5% Hi-stab capacitors 013, 061, 066, 069, 075, 08, AY5 B300 10 for 85p
 BC548B 500 for £28.50
 BC556 500 for £28.50
 BCY71 500 for £43.50
 BD437 50 for £13.75
 2N2906 500 for £43.50

TBA920 10 for £11.50
 Vero card handle 10 for 65p
 62 Ω 1/2W Resistor 2,000 for £6.75
 ON222 (superior matched BF181) 10 for £1.20
 68 Volt 10 Watt Zener Diodes.....5 for £2.50

OTHER DIODES	
1N916 8p	
1N4009 9p	
1N4148 4p	
8A145 17p	
Central 29p	
BZY61/BA148/OA81 12p	
BB103/110 Varicap 24p	
BB113 Triple Varicap 43p	
BA182 15p	
OA57/710 17p	
BZY88 up to 43 volt 10p	
BZK61 11 volt 17p	
AA133 10p	
BZY96C 10V 34p	
BZY95C 33V or 15V 34p	

RS Iravin high temperature wire, 19/0.16, minus 55° to 105°C, 600V 3A, white, black or red. Half trade price at 54p 10M coil.

PVC QUALITY TAPE
 Lasso 10m x 15mm grey 38p
 33m x 33mm green £1.13p

Trimmer: Post stamp type 3-30pF 16p
 10-80pF 19p
 30-140pF 23p

GARRARD
 GCS23T Crystal Stereo Cartridge £1.20
 Mono (Stereo compatible) Ceramic or crystal £1

INTEGRATED CIRCUITS	
TBA920 TCA720 £2.20	
TAA700 £2.40	
TBA800 £1.24	
741/7490/7473 28p	
uA702 op amp 53p	
(72) 709 52p	
74107/74122 38p	
SN76228N £2.03	
SN76131/75110 £1.55	
SN76013N/ND £1.40	
TAD100 AMRF £1.22	
CA3001 R.F. Amp £1.58	
CA3132 £2.22	
74151 45p	
CD4069 24p	
TAA300 1 wt Amp £1.15	
TAA550, Y or G 26p	
TAA263/74LS192 70p	
TAA320 £1.15	
7400/7401 18p	
7402/4/10/20/30 18p	
7414/74132N 6p	
7438/7474/7432 27p	
AY5 B300 £1.00	
7483/74520 79p	
7489/CD4013 41p	
LM3300 2/20V reg £1.15	
LM1303N £1.15	
74154/TBA810 £1.02	
TBA550Q/74S112 £1.80	
ZN414 £1	

HANDLES
 Rigid light blue nylon 6 1/2" with secret fitting screws 11p
 Beveling Lee white plastic surface coax outlet box 40p
 Miniature Axial Lead Ferrite Choke formers 5 for 13p
 RS 10 Turn pot 1% 250 500 Ω 1K, 50K £1.70
 Copper coated board 10" x 9" approx. 60p
 Geared Knob 8-1 ratio. 1 1/2" diam., black 95p
 KLIPPON 25A 440v TERMINAL BLOCKS
 Professional leaf spring clamp, twin with clip-over cover 11p
 Strip of 4, 40A 440V 18p

VAT & POST PAID

MINIMUM ORDER £3 OTHERWISE ADD 50%
 FOR SMALL ORDER HANDLING COSTS (UNDER £1.00 TOTAL ALSO INCLUDE 9p S.A.E.)

NO MORE TO ADD — Prices INCLUDE UK VAT and Post/Packing
 ALL ENQUIRIES, ETC., MUST BE ACCOMPANIED BY A STAMPED ADDRESSED ENVELOPE

THE MODERN BOOK CO

WORLD RADIO TV HANDBOOK 1979 £9.15

THE RADIO AMATEUR HANDBOOK 1979 by ARRL	Price £7.86	UNDERSTANDING DIGITAL ELECTRONICS by Texas Instruments	Price £3.90	ABC'S OF ELECTRONICS by F. J. Waters	Price £4.15
UNDERSTANDING AMATEUR RADIO by J. Rusgrove	Price £4.25	NEWNES RADIO & ELECTRONICS ENGINEER'S POCKET BOOK by Newnes	Price £2.80	BEGINNER'S GUIDE TO HOME COMPUTERS by M. Grosswirth	Price £3.20
SOLID STATE DESIGN FOR THE RADIO AMATEUR by ARRL	Price £6.00	BEGINNER'S GUIDE TO TAPE RECORDING by I. R. Sinclair	Price £3.20	ADVENTURES WITH ELECTRONICS by T. Duncan	Price £2.85
THE A.R.R.L. ANTENNA BOOK by ARRL	Price £4.25	BEGINNER'S GUIDE TO AUDIO by I. R. Sinclair	Price £3.00	PROJECT PLANNING & BUILDING by M. A. Colwell	Price £2.20
FM AND REPEATERS FOR THE RADIO AMATEUR by ARRL	Price £3.50	BEGINNER'S GUIDE TO INTEGRATED CIRCUITS by I. R. Sinclair	Price £3.00	110 COSMOS DIGITAL IC PROJECTS FOR THE HOME CONSTRUCTOR by R. M. Marston	Price £3.00
REPAIRING POCKET TRANSISTOR RADIOS by I. R. Sinclair	Price £2.50	BEGINNER'S GUIDE TO COLOUR TV by G. J. King	Price £2.50	110 OPERATIONAL AMPLIFIER PROJECTS FOR THE HOME CONSTRUCTOR by R. M. Marston	Price £2.75
BEGINNER'S GUIDE TO RADIO by G. J. King	Price £3.00	BEGINNER'S GUIDE TO ELECTRIC WIRING by F. Guillou	Price £2.50	TESTING METHODS AND RELIABILITY ELECTRONICS by A. Simpson	Price £4.30
BUILDING & DESIGNING TRANSISTOR RADIOS - A BEGINNER'S GUIDE by R. H. Warring	Price £3.30	THE OSCILLOSCOPE IN USE by I. R. Sinclair	Price £2.75	DIGITAL ELECTRONIC CIRCUITS AND SYSTEMS by N. M. Morris	Price £4.30
OP-AMPS - THEIR PRINCIPLES AND APPLICATIONS by J. B. Dance	Price £2.50	THE CATHODE-RAY OSCILLOSCOPE AND ITS USE by G. N. Patchett	Price £4.00	BEGINNER'S GUIDE TO MICROPROCESSORS by C. M. Gilmore	Price £4.75
ELECTRONICS FAULT DIAGNOSIS by I. R. Sinclair	Price £3.00	INTRODUCING AMATEUR ELECTRONICS by I. R. Sinclair	Price £1.50	GETTING ACQUAINTED WITH MICROCOMPUTERS by L. Frenzel	Price £7.00

* PRICES INCLUDE POSTAGE *

We have the Finest Selection of English and American Radio Books in the Country

19-21 PRAED STREET (Dept RC) LONDON W2 1NP

Telephone 01-723 4185

The action-packed show for the electronics enthusiast now includes the Midlands among its venues. If hobby electronics is your interest or your business, then Midlands Breadboard is tailor-made for you.

MIDLANDS

**BREAD
BOARD**

1979

**Bingley Hall, Birmingham,
23-26 May, 10am-6pm
Admission: £1 Adults
75p Students**

Crammed with the gear that constructors need. Circuit boards, components, audio kits, d.i.y. computer systems, electronic musical instruments - you'll find it all here. And you can buy it on the spot - or browse at your leisure. Demonstrations and competitions (exciting prizes!) keep the show humming with activity.

P.S. There's a London Breadboard too, December 4-8th, Royal Horticultural Halls - come to both!

I want to visit the show. Send me more details nearer the date.

Please send me details now of exhibition space.

Name

Position

Company

Address

Telephone Telex

Return to: Trident International Exhibitions Limited
Abbey Mead House, 23a Plymouth Road,
Tavistock, Devon. PL19 8AU

Telephone: 0822 4671 Telex: 45412 TRITAV

STEVENSON

Electronic Components

KNOBS

Ideal for use on mixers, etc. Push on type with coloured cap in red, black, green, blue, yellow and grey.

Position line marked 14p each.



POTENTIOMETERS

5K-2M2 single 26p ea. 100Ω-2M2 horizontal
5K-2M2 stereo (dual) 75p ea. or vertical preset 6p ea.
5K-2M2 DP switched 60p ea.

BRIDGE RECTIFIERS

Type	PIV	I	Type	PIV	I
W005	50	1A	2KBB10	100	2A 39p
W01	100	1A	2KBB20	200	2A 45p
W02	200	1A	2KBB40	400	2A 50p
W04	400	1A	BY225	200	4.2A 100p

METAL FILM RESISTORS

A range of high precision, very high stability, low noise resistors. Rated at 1/4W. 1% tolerance.

Available from 51 ohms to 330K in E24 series. Any mix


each	100+	1000+	
1/4W 1%	4p	3.5p	3.2p

Special development pack consisting of 10 of every value from 51 ohms to 330K (a total of 930 resistors) £23.75

MINIATURE TRANSFORMERS

240-Volt Primary

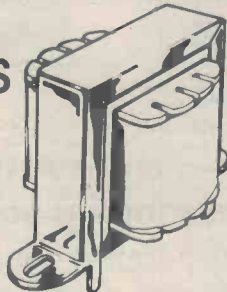Secondary rated at 100mA.
Available with secondaries of:
6-0-6, 9-0-9
and 12-0-12. 92p each



HEAT SINKS

T018 9p each T03 20p each T0220 20p each
T05 9p each T0126 20p each

Double T03 predrilled plain finish.
100mm x 124 x 27mm 90p each

Mounting kits: T03, T066 and T0220 all 4p per kit.

We now have an express telephone order service. We guarantee that all orders received before 5pm. are shipped first class on that day. Contact our Sales Office now! Telephone: 01-464 2951/5770.

ORDERS
DESPATCHED
BY RETURN
POST

Quantity discounts on any mix TTL, CMOS, 74LS and Linear circuits: 25+ 10%, 100+ 15%. Prices VAT inc. Please add 30p for carriage.

Official orders welcome.

BARCLAYCARD AND ACCESS WELCOME

Mail orders to: STEVENSON (Dept RE)

76 College Road, Bromley, Kent, England

TRANSISTORS

AC127 17p	BCY71 14p	ZTX109 14p
AC128 16p	BCY72 14p	ZTX300 16p
AC176 18p	BD131 35p	2N697 12p
AD161 38p	BD132 35p	3N1302 38p
AD162 38p	BD135 38p	2N2905 22p
BC107 8p	BD139 35p	2N3053 18p
BC108 8p	BD140 35p	2N3055 50p
BC109 8p	BF244B 36p	2N3442 135p
BC147 7p	BFY50 15p	2N3702 8p
BC148 7p	BFY51 15p	2N3704 8p
BC149 8p	BFY52 15p	2N3705 9p
BC158 9p	MJ2955 98p	2N3706 9p
BC177 14p	MPSA06 20p	2N3707 9p
BC177 ² 14p	MPSA56 20p	2N3708 8p
BC179 14p	TIP29C 60p	2N3819 22p
BC182 10p	TIP30C 70p	2N3904 8p
BC182L 10p	TIP31C 65p	2N3905 8p
BC184 10p	TIP32C 80p	2N3906 8p
BC184L 10p	ZTX107 14p	2N4058 12p
BC212 10p	ZTX108 14p	2N5457 32p
BC212L 10p		2N5458 30p
BC214 10p		2N5459 32p
BC214 10p		2N5777 50p
BC214 10p	1N914 4p	
BC477 19p	1N4001 4p	1N4148 3p
BC478 19p	1N4002 4p	1N5401 13p
BC479 19p	1N4004 5p	1N5402 15p
BC548 10p	1N4006 6p	1N5404 16p
BCY70 14p		1N5406 18p

DIODES

LINEAR

A SELECTION ONLY!
DETAILS IN CATALOGUE.

709 25p	LM324 50p	NE556 60p
741 22p	LM339 50p	NE565 120p
747 50p	LM380 75p	NE567 170p
748 30p	LM382 120p	SN76003 200p
CA3046 55p	LM1830 150p	SN76013 140p
CA3080 70p	LM3900 50p	SN76023 140p
CA3130 90p	LM3909 60p	SN76033 200p
CA3140 70p	MC1496 60p	TBA800 70p
LM301AN 28p	MC1458 35p	TDA1022 650p
LM318N 125p	NE555 25p	ZNA14 75p

OPTO

LEDs	0.125in.	0.2in.
Red	TIL209	TIL220 9p
Green	TIL211	TIL221 13p
Yellow	TIL213	TIL223 13p
Clips	3p	3p



DISPLAYS

DL704	0.3 in CC	130p
DL707	0.3 in CA	130p
FND500	0.5 in CC	100p

RESISTORS

Carbon film resistors.
High stability, low noise 5%.

E12 series. 4.7ohms to 10M. Any mix:

	each	100+	1000+
0.25W	1p	0.9p	0.8p
0.5W	1.5p	1.2p	1p

Special development packs consisting of 10 of each value from 4.7 ohms to 1 Megohm (650 res.)
0.5W £7.50. 0.25W £5.70

CAPACITORS

HERE ARE JUST A FEW OF THE CAPACITORS STOCKED

TANTALUM BEAD						
0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1 & 2.2uF @ 35V	each					
4.7, 6.8, 10uF @ 25V	9p					
22 @ 16V, 47 @ 6V, 100 @ 3V	13p					
	16p					
MYLAR FILM						
0.001, 0.01, 0.022, 0.033, 0.047	3p					
0.068, 0.1	4p					
RADIAL LEAD ELECTROLYTIC						
63V	0.47	1.0	2.2	4.7	10	5p
			22	33	47	7p
	100					13p
		220				20p
25V	10	22	33	47		5p
	100					8p
		220				10p
			470			15p
	1000					23p
10V		220				5p
			470			9p
	1000					13p
		2200				23p

74LS

LS00 16p	LS125 40p
LS01 16p	LS126 40p
LS02 16p	LS132 60p
LS03 16p	LS136 36p
LS04 16p	LS138 54p
LS08 16p	LS139 50p
LS10 16p	LS151 50p
LS13 30p	LS153 50p
LS14 70p	LS155 80p
LS16 16p	LS156 80p
LS17 30p	LS157 45p
LS20 16p	LS164 90p
LS30 16p	LS174 60p
LS32 24p	LS175 60p
LS37 26p	LS190 80p
LS40 22p	LS192 70p
LS42 53p	LS193 70p
LS47 70p	LS196 80p
LS48 48p	LS251 60p
LS54 16p	LS257 55p
LS73 29p	LS258 55p
LS74 29p	LS266 40p
LS75 44p	LS283 60p
LS76 35p	LS290 55p
LS78 35p	LS365 45p
LS83 60p	LS366 45p
LS85 70p	LS367 45p
LS86 33p	LS368. 45p
LS90 45p	LS386 35p
LS93 45p	LS670 180p

TTL

7400 12p	7493 34p
7401 12p	7494 52p
7402 12p	7495 52p
7404 12p	7496 50p
7408 14p	74121 25p
7410 12p	74122 33p
7413 25p	74123 40p
7414 48p	74125 35p
7420 12p	74126 35p
7427 24p	74132 50p
7430 12p	74141 56p
7442 43p	74148 90p
7447 55p	74150 70p
7448 58p	74151 50p
7454 14p	74156 52p
7473 25p	74157 52p
7474 25p	74164 70p
7475 32p	74165 70p
7476 28p	74170 125p
7485 70p	74174 68p
7489 145p	74177 58p
7490 32p	74190 72p
7492 35p	74191 72p
	74192 64p
	74193 64p
	74196 55p
	74197 55p

CMOS FULL DETAILS IN CATALOGUE

4001 15p	4029 60p
4002 15p	4040 68p
4007 15p	4042 54p
4011 15p	4046 100p
4013 35p	4049 28p
4015 60p	4050 28p
4016 35p	4066 40p
4017 55p	4068 20p
4018 65p	4069 16p
4023 15p	4071 16p
4024 45p	4075 16p
4026 95p	4093 48p
4027 35p	4510 70p
4028 52p	4511 70p
	4518 70p
	4520 65p

SKTS

8 pin	10p	24 pin	24p
14 pin	12p	28 pin	28p
16 pin	13p	40 pin	40p
Soldercon pins: 100: 50p			
1000: 370p			

AT LAST! OUR NEW 40 PAGE CATALOGUE OF COMPONENTS IS AVAILABLE. SEND S.A.E.



**SATISFACTION
OR YOUR MONEY
BACK IF GOODS
RETURNED
WITHIN
7 DAYS**

A BIG NEW DEAL

**STREAMLINED
RETURN-OF-POST
COMPONENT
ORDERS
SERVICE**

THYRISTOR

10 amp 100 p.i.v.
metal stud type
35p each

brand new

ELECTROLYTIC CAPACITORS

All brand new modern transistor types mostly, all values, voltages marked.

1uF/75v	6p
2uF/40v	5p
4uF/300v	5p
6.8uF/25v	6p
12uF/25v	5p
25uF/12v	5p
25uF/30v	4p
32uF/40v	5p
32uF/160v	6p
40uF/16v	5p
47uF/25v	6p
56uF/25v	5p
64uF/10v	4p
64uF/70v	5p
75uF/9v	4p
100uF/6.3v	4p
100uF/40v	5p
125uF/10v	5p
150uF/6.3v	4p
150uF/16v	5p
150uF/25v	5p
200uF/10v	5p
250uF/16v	5p
300uF/9v	5p
300uF/25v	5p
320uF/18v	5p
320uF/18v	5p
330uF/25v	5p
400uF/10v	5p
400uF/25v	5p
470uF/6.3v	5p
470uF/16v	5p

★ ★ ★ STAR PACK FOUR 2N3055 TRANSISTORS BRAND NEW ONLY £1.30

TRIMMERS

Compression types all brand new.
10pF, 30pF, 50pF, 1,000pF
all 15p each

Tubular solder-in types brand new.

3pF, 6pF, 8pF, 12pF
all 10p each

Dau semi-air spaced.
2 to 9pF 16p
6 to 45pF 18p
8 to 125pF 18p

★ ★ ★

STAR OFFER

Neon indicators to push in and fix with glue, brand new 240v w.kg.

Red 12p each
Amber 12p each

When fitted they look like normal panel indicators.

★ **BD187 TRANSISTORS**
Full spec. new. 4 for £1.00

SLIDER POTS

All brand new and plastic cased types marked values

470R Lin	15p
1K Lin	15p
1K8 Lin	15p
4.7K Log	15p
5K Lin	16p
10K Log	15p
25K Log	15p
50K Log	15p
100K Lin	16p
100K Log	16p

13 amp Rubber Plugs
Black, brand new, limited offer
28p each

ROTARY POTS

Modern carbon track types, 60% have long shafts, all brand new.

500R Log	12p
4.7K Log	12p
47K Lin	12p
50K Lin	13p
250K Lin (plastic)	10p
Dual 100K Lin	15p
Dual 100K Log	15p
Dual 22K Log	15p
Dual 500R Log + 500K Lin	15p
Dual 1K Lin + 500K Lin	15p

POLYSTYRENE CAPACITORS

47pF/400v	4p
60pF/350v	4p
163pF/125v	4p
390pF/160v	4p
395pF/350v	4p
1,000pF/350v	4p
3,070pF/125v	4p
4,000pF/125v	4p

All above are brand new transistor types with marked values.

★ **2N3054 TRANSISTORS**
Full spec. new. 4 for £1.20

SUPER PAKS

30 uncoded BC107	70p
30 uncoded BC108	70p
30 uncoded BC109	70p
6 uncoded photo trans	60p
30 asstd resistors	38p
6 FET's	80p
25 asstd capacitors	30p
25 ceramic capacitors	30p
25 C280 capacitors	30p
20 AC128 branded	40p
20 Vari-Cap diodes	35p
25 2W zeners uncoded	35p
40 asstd transistors	70p
6 asstd pre-sets	30p
20 w/w resistors	42p

13 amp Rubber Fly Lead
Sockets, black, new 35p each

★
TIP29 or
TIP33 Full
Spec transistors

only 29p each

WIRE-WOUND RESISTORS

All brand new modern types marked values.

1.5 ohm 5w	4p
2.7 ohm 2w	4p
30 ohm 5w	5p
51 ohm 5w	5p
56 ohm 5w	5p
500 ohm 5w	4p
560 ohm 5w	5p
1K 10w	5p
1K2 5w	5p
2.2K 5w	5p
2.7K 5w	5p
6.8K 5w	5p

FET's P-channel 16p
FET's N-channel 16p
FET 2N3819 equiv 17p

PHOTO TRANSISTORS

Uncoded but good and tested
18p each

This month's bargain

TEN POWER TRANSISTORS

All new and marked numbers, plastic and metal types, tested working.
Only £1.00

TBA120S FM DETECTOR
I.C.'s new with data but untested
18p each

WIDEBAND AMPLIFIER
I.C.'s new with data but untested
18p each

MULLARD TAA320
M.O.S.T. PRE-AMP I.C. with circuits brand new, tested
48p each

Mains Extension Leads
13 amp plug ready wired to 3 yds of 5 amp cable with 13 amp socket
£1.50

MAINS TRANSFORMERS

Please add 30p extra postage per transformer. All primaries 240v:

24v tapped 14v 1A	£1.80
12v 500ma	£1.80
22-0-22v 500ma	£2.00
16v 2 amp	£2.20
12v 1 amp	£1.70
24v ½ amp	£2.00
30v 1 amp	£2.20
13-0-13v 1 amp	£2.20
22v 500ma	£1.40
32-0-32v 500ma	£2.20

TUNING CAPACITORS

250 pf air spaced 40p
250 + 350 pf air spaced slow tune 60p
Both types are new

TQ3 TRANSISTOR COVERS

Nylon, black, new.
4 for 22p

POT PACK

SIX POTS

rotary types
all new, various
values, only 48p

TRANSISTORISED INVERTERS

Units listed are only on offer for this month.
All units ready assembled in blue rexine covered aluminium cases, plain bottoms, features include: on/off switch, output via 13A type rubber socket, silicon power transistors, all new components used throughout. 12v or 24v inputs as listed — output 240v AC off load, square wave, frequency between 45/54Hz approx.

12v in — 25 watts out. 6" x 5" x 4"	£7.50
12v in — 40 watts out. 6" x 5" x 4"	£10.80
12v in — 120 watts out. 11" x 8" x 5"	£21.00
24v in — 25 watts out. 6" x 5" x 4"	£8.80
24v in — 50 watts out. 6" x 5" x 4"	£12.80
24v in — 100 watts out. 11" x 6" x 5"	£21.00
24v in — 150 watts out. 11" x 6" x 5"	£26.00
24v in — 200 watts out. 11" x 6" x 5"	£34.00
24v in — 300 watts out. 11" x 6" x 5"	£42.00

Please add £1.50 p/p extra per unit. Delivery of these inverters can take up to 26 days as all are assembled to order.


PLEASE ADD 15p post/packing. Minimum order £1.50. Payment by cheques, postal orders etc. Overseas postage at cost. It is very helpful if you print your name and address clearly.
Goods ordered now sent by return of post except where indicated.

ELECTROVANCE
TEL: 01-736 0685 MAIL ORDER ONLY
P.O. BOX 191 LONDON SW6 2LS

APEL POWER SUPPLIES

STABILIZED POWER SUPPLIES WITH ELECTRONIC SHORT CIRCUIT PROTECTION

AL.212 P

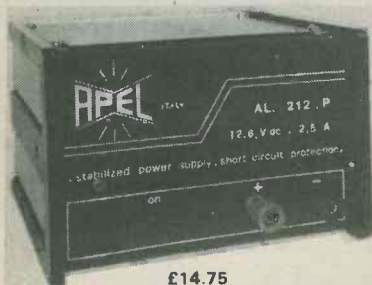

£14.75

INPUT VOLTAGE	220 V ac \pm 10% 50-60 Hz
OUTPUT VOLTAGE RANGE	12.6 V dc
OUTPUT CURRENT MAX	2.5 Amp
LOAD REGULATION	<0.3% 0-2.2 Amp
RIPPLE	<5mV 2.2 Amp
DIMENSIONS (mm)	W140 x H90 x D140
WEIGHT	1,490 Kg.

AL.315 P



£29.50

INPUT VOLTAGE	220 V ac \pm 10% 50-60 Hz
OUTPUT VOLTAGE RANGE	1.7-15 V dc
LOAD REGULATION	<0.2% 0-2.8 Amp
DIMENSIONS (mm)	W140 x H90 x D155
RIPPLE	3mV 2.8 Amp
WEIGHT	2,330 Kg.

AL.330 P



£46.50

INPUT VOLTAGE	220 V ac \pm 10% 50-60 Hz
OUTPUT VOLTAGE RANGE	3.4-30 V dc
OUTPUT CURRENT RANGE MAX	3 Amp
LOAD REGULATION	< 5% 0-2.8 Amp
RIPPLE	10mV 2.8 Amp
DIMENSIONS (mm)	W270 x H90 x D155
WEIGHT	4,250 Kg.

STOCKISTS

Alpha Sound Service,
50 Stuart Road, Waterloo, Liverpool L22 4QT,
England.

Anson Electronics,
1133 Hessle High Road, Hull, England.

Amateur Radio Shop,
13 Chapel Hill, Huddersfield, HD1 3ED,
England.

Brent Electronics,
Seaview Street, Cleethorpes,
Lincolnshire, England.

J. Birkett,
26 The Strait, Lincoln, England.

Bradford Consultants Limited,
25 Regent Parade, Harrogate,
Yorkshire, England.

F. Brown & Co. Ltd.,
44/46 George IV Bridge Street,
Edinburgh, Scotland.

N. R. Bardwell Limited,
Sellers Street, Sheffield, England.

Casey Brothers,
235 Boundary Road,
"Saint Helens",
Lancashire, England.

Electronic Services Limited,
33 City Arcade, Coventry CU11 HX, England.

A. Fanthorpe Limited,
6 Hepworth Arcade, Silver Street,
Hull, England.

G. W. M. Radio,
Portland Road, Worthing, Sussex.

Leeds Amateur Radio,
27 Cookridge Street,
Leeds LS2 3AG, England.

Target Electric Limited
16 Cherry Lane, Bristol, England.

New Cross Radio,
6 Oldham Road, Manchester,
England.

Progressive Radio,
93 Sale Street, Liverpool L2 2JD,
England.

R. E. Pitt Electrical Services Limited,
60/64 Bath Buildings, Mont Pelier,
Bristol, England.

Peats Electronics,
Parnell Street, Dublin.

R. F. Potts,
68 Bobbington Lane, Derby, England.

Brian A. Pearson Limited,
66 Moncur Street, Glasgow, Scotland.

R M E Supplies Limited,
143 Stockwell Street, Glasgow, Scotland.

Stephan James Limited,
Warrington Road, Leigh, Lancashire.

Stewarts Radio,
4 Chance Street, Blackpool, England.

The Radio Shop,
16 Cherry Lane, Bristol BS 3NG,
England.

Q. C. Trading,
1 St. Michaels Terrace, Woodgreen M22 4FT,
England.

AL.1 P5



£78.00

INPUT VOLTAGE	220 \pm 10% 50 Hz
OUTPUT VOLTAGE RANGE	\pm 15 V. dc
OUTPUT CURRENT MAX	5 Amp
LOAD REGULATION	< 0.1% 0-4.5 Amp
RIPPLE	< 2mV 4.5 Amp
DIMENSIONS (mm)	W210 x H185 x D250
WEIGHT	5,100 Kg.

AL.212 PS



£18.00

INPUT VOLTAGE	220 V ac \pm 10% 50-60 Hz
OUTPUT VOLTAGE RANGE	12.6 V dc
OUTPUT CURRENT MAX	2.5 Amp
LOAD REGULATION	<0.3% 0-2.2 Amp
RIPPLE	<5mV 2.2 Amp
DIMENSIONS (mm)	W140 x H90 x D140
WEIGHT	1,490 Kg.
AMPEROMETER	

AL.315 P2



£54.00

INPUT VOLTAGE	220 V ac \pm 10% 50-60 Hz
OUTPUT VOLTAGE RANGE	\pm 1.7-15 V dc
OUTPUT CURRENT RANGE MAX	3 Amp
LOAD REGULATION	< 0.2% 0-2.8 Amp
RIPPLE	< 3mV 2.8 Amp
DIMENSIONS (mm)	W270 x H90 x D155
WEIGHT	4,140 Kg.

Stan Willets Limited,
37 High Street, West Bromwich.

M/S Waltons,
55a Worcester Street,
Wolverhampton WV2 4LL, England.

Distributed in the U.K.
and Ireland by:

PEAT'S WHOLESALE LTD.

Chapel Lane, Parnell St., Dublin 1, Ireland.

PHONE 741746-740678-722845. TELEX 31787.

WORKSHOP POWER SUPPLY — Part 1

By R. A. Penfold


A VERSATILE INSTRUMENT

- *Continuously variable output from 7.5 to 42 volts*
- *Current limiting at 1 amp, 100mA or 10mA*
- *Dual supply rail option with independent positive and negative control*



An impressive front panel display. Outputs are available at the three terminals to the left of the meters. Immediately to the right of the meters are the voltmeter switch, the earth selector and the current limit switch. At the far right are the mains on-off switch, the positive output voltage control and the negative output voltage control

Fig 1. Simplified diagram illustrating the basic design of the power supply. There are two outputs, which can be employed on their own or in series. Alternatively, the unit may be used as a dual rail supply with a centre zero voltage rail

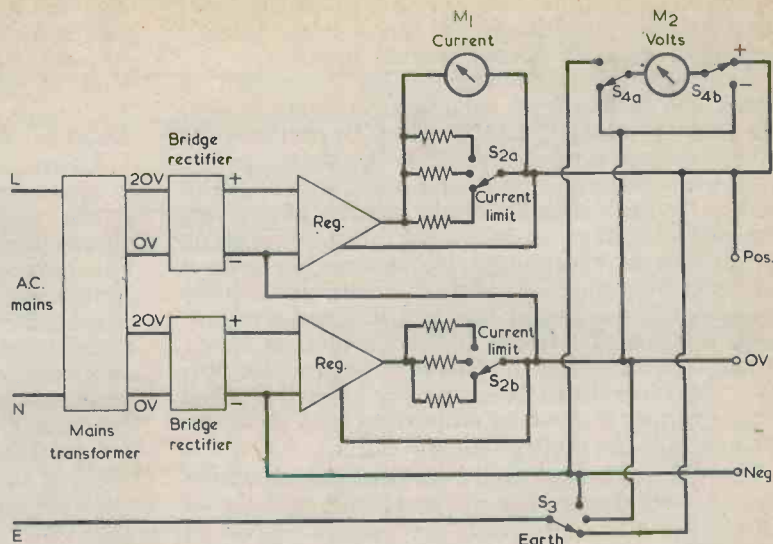

When building and servicing electronic equipment the need for some form of power supply frequently arises. Often it is possible to use batteries to power the equipment, but this is not always practical. How, for example, can a 25 watt audio amplifier be fully tested using ordinary dry batteries as a power source? It is mainly for supplying fairly high voltage and current requirements that a workshop supply is needed, and it is largely for applications of this type that the versatile instrument described in this article was developed.

CURRENT LIMITING

This unit can provide a single voltage rail which is continuously variable between about 7.5 volts and 42 volts at a maximum current of about 1 amp. A current limit of 1 amp is incorporated in the design in order to protect the instrument from accidental short-circuits and overloads at its output. This ensures that the power supply will not be damaged by excessive current, but it is also desirable that an output current limit be provided to protect the equipment being supplied as well. Since 1 amp may be too high a limit for some supplied equipment, two alternative current limits of 100mA and 10mA are provided. The three current limits of 1 amp, 100mA and 10mA are selected by a 3-way switch, this being set to suit the particular item which is supplied. A meter which monitors the output current is fitted in the supply, and its full-scale deflection sensitivity is equal to the selected current limit.

The supply can also be used to provide dual supply rails which are positive and negative of a common rail, the voltages being continuously variable from about 7.5 volts plus 7.5 volts to 21 volts plus 21 volts. The two supply rail voltages are independently variable, allowing the positive and negative rail voltages to be equal or unequal as desired. The unit can therefore supply nearly all operational amplifier circuits as well as power amplifiers having a direct coupled output. An output voltage meter is fitted.

The output is very well smoothed, with a noise level of approximately 1mV at any output voltage and current combination. Output voltage regula-

tion is excellent, and there is a drop of only about 40mV when the output current is changed from zero to full load. Of course, if the output current exceeds the selected limit level the output voltage falls, maintaining the output current at the limiting value.

BASIC OPERATION

As the design is a little unusual it would perhaps be advisable to consider the basic operation of the supply before proceeding to the circuit details. The general arrangement of the instrument is illustrated in Fig. 1.

The mains transformer has two secondary windings, each of which feeds a separate bridge rectifier and smoothing capacitor network. The two resultant d.c. outputs are then fed to conventional adjustable voltage regulator circuits. Each regulator has a current limit circuit which is actuated by the voltage dropped across a resistor in series with the output. The voltage across this resistor is applied to the base and emitter of an internal transistor in the integrated circuit regulator. The transistor has no effect on output voltage until its base-emitter voltage rises to a level which causes it to conduct, whereupon it then causes the output voltage to be reduced. The value of the series resistor in the power supply is such that about 0.66 volt is developed across it when the output current is at the chosen current limit level. Since the transistor in the regulator i.c. is, obviously, a silicon device, this voltage is approximately that needed to make it conductive. The difference between the base-emitter voltage needed to just make the transistor conduct and that which causes full saturation is extremely small, whereupon the regulator output voltage falls very rapidly to a safe level when any attempt is made to draw excessive current. This gives a very well defined current limit threshold.

A voltmeter with a full-scale deflection sensitivity of 0.66 volt is connected across the current limit resistor of one of the regulator circuits. Since each regulator actually has three switched series resistors to provide the three current limits, the voltmeter will indicate f.s.d. at the current limit irrespective of which resistor is selected. Thus, the f.s.d. sensitivity of the meter is automatically

switched to 1 amp, 100mA or 10mA at the same time as the output current limit is set and it thereby acts as an output current monitor.

The two regulator outputs are connected in series, the output from each being adjustable over the range of about 7.5 to 21 volts. In practice, the output voltage range provided by the prototype is a little wider than this, with the result that any unit built up to the design should be capable of covering the quoted voltage range, taking into consideration the effects of component tolerances. For output voltages between 7.5 and 21 volts it is only necessary to use one or other of the regulator outputs. Voltages of between 21 and 42 volts can be obtained by employing the two series-connected outputs, the central rail being simply ignored. A dual output supply is given by employing both regulator outputs and the central supply rail.

The current meter could be switched so that it can connect across the current limit resistor of either regulator, permitting the output current of the negative rail to be monitored when the unit is used in the dual rail mode. However, the author felt that the circuit complication involved was not worth-while, and this facility has not been incorporated into the prototype. (An indication of overload in the negative rail may, in any case, be provided by switching the internal voltmeter to that rail.)

A voltmeter with an f.s.d. of 25 volts can be

switched to monitor the output voltage from either regulator circuit. It is not possible to monitor the output voltage of the two regulators when these are used in series, but it is an easy matter to individually adjust the two output voltages to produce the required sum voltage.

A further 3-way switch enables the mains earth to be connected to the central rail, the negative rail or the positive rail, as appropriate for the conditions under which the power supply is being used. This may seem to be a minor point, but in fact it is an important one. Obviously, when the unit is used in the dual supply mode the central rail should be earthed, and in many instances it does not matter whether the positive or negative rail is earthed in the single supply mode, although it should not be the unused central rail which is earthed when the two outputs are employed in series. The importance of having the correct output earthed arises when the equipment being supplied is connected to some other item of mains powered equipment having an earthed input or output. For example, the equipment being supplied could be an amplifier which has a positive earth. If, say, a millivoltmeter having an earthed input terminal is connected to the amplifier no problems will arise if the power supply has its positive output earthed. On the other hand, a short-circuit through the earth wiring will be given if the power supply is incorrectly switched for a negative earth.

COMPONENTS

Resistors

(All fixed values $\frac{1}{2}$ watt 5% unless otherwise stated)

- R1 3.3k Ω
- R2 4.7k Ω pre-set potentiometer, 0.1 watt, horizontal
- R3 0.68 Ω 1 watt (see text)
- R4 6.8 Ω
- R5 68 Ω
- R6 12k
- R7 2.2k Ω
- R8 0.68 Ω 1 watt (see text)
- R9 6.8 Ω
- R10 68 Ω
- R11 12k
- R12 2.2k Ω
- R13 220k Ω
- R14 47k Ω pre-set potentiometer, 0.1 watt, horizontal
- VR1 22k Ω potentiometer, linear
- VR2 22k Ω potentiometer, linear

Capacitors

- C1 4,700 μ F electrolytic, 40V Wkg., single-ended with mounting clip
- C2 100pF ceramic plate
- C3 0.1 μ F type C280
- C4 100 μ F electrolytic, 25V Wkg.
- C5 4,700 μ F electrolytic, 40V Wkg., single-ended with mounting clip
- C6 100pF ceramic plate
- C7 0.1 μ F type C280
- C8 100 μ F electrolytic, 25V Wkg.

Transformer

- T1 mains transformer, secondaries 0-20V 1.2A, 0-20V 1.2A (see text)

Semiconductors

- IC1 723C in 14 pin d.i.l.
- IC2 723C in 14 pin d.i.l.
- TR1 2N3055
- TR2 2N3055
- D1-D8 1N4002

Switches

- S1 d.p.s.t., rotary toggle
- S2(a)(b) 2-pole 3-way rotary (see text)
- S3 1-pole 3-way rotary, break-before-make (see text)
- S4 (a) (b) 2-pole 2-way rotary, break-before-make (see text)

Meters

- M1 0-100 μ A moving coil (see text)
- M2 0-100 μ A moving-coil (see text)

Indicator

- PL1 neon indicator with integral series resistor, 240V A.C.

Terminals

- SK1, 2, 3 insulated terminals (see text)

Fuses

- FS1 1 amp cartridge fuse, 20mm.
- FS2 1 amp cartridge fuse, 20mm.

Miscellaneous

- Metal instrument case (see text)
- 6 control knobs
- 2 fuseholders, 20mm., chassis-mounting
- Finned aluminium heatsink (see text)
- 2 sets mica washers and insulating bushes (for TR1 and TR2)
- Materials for printed circuit board
- 3-core mains lead
- Nuts, bolts, wire, etc.

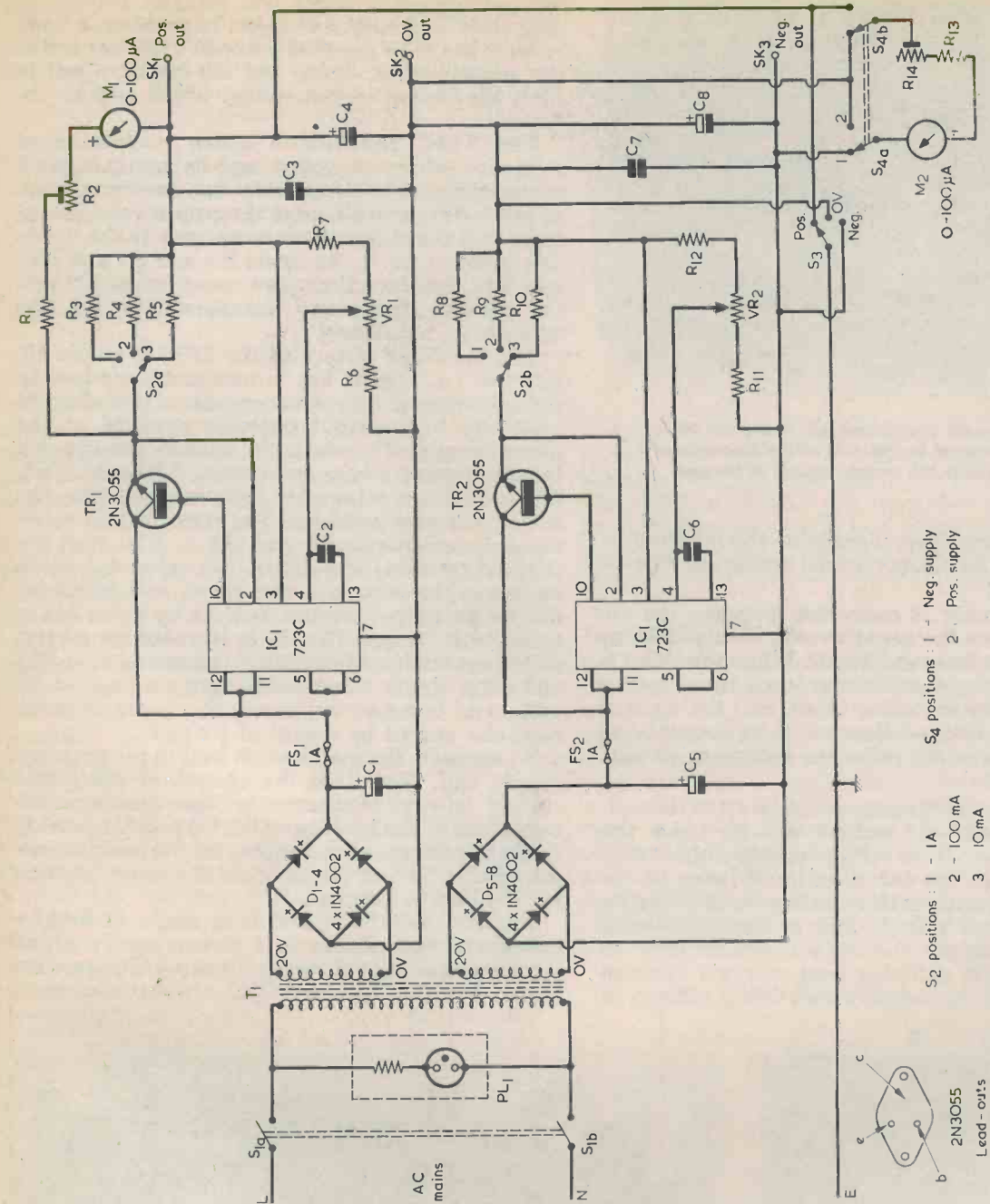


Fig. 2. Complete circuit of the workshop power supply. Output current limiting can be set for 1 amp, 100mA and 10mA. Output voltages for each rail are continuously variable from 7.5 to 21 volts, and the two outputs can be used in series to provide a maximum of 42 volts. Any output terminal may be connected to the mains earth

COMPLETE CIRCUIT

The complete circuit of the power supply is shown in Fig. 2. The a.c. mains input is applied to the primary of T1 via on-off switch S1(a)(b). PL1 is the mains indicator, this being a panel-mounting neon with integral series resistor intended for mains operation. The secondaries feed two bridge rectifiers, D1 to D4 and D5 to D8, and the rectified voltages are then smoothed by the large value electrolytic capacitors, C1 and C5.

A 723C integrated circuit voltage regulator appears in each voltage stabilizing circuit. As is shown in Fig. 3, the 723C consists basically of an operational amplifier having a reference voltage


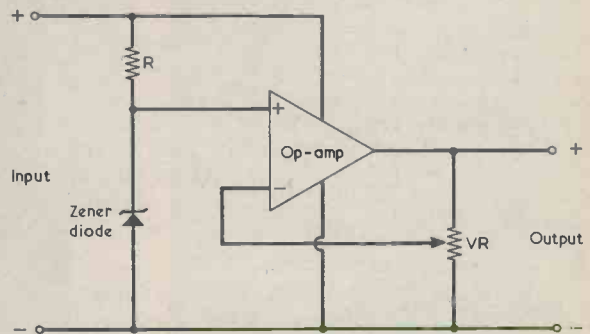


Fig. 3. A continuously variable stabilized output voltage can be obtained with the basic circuit shown here

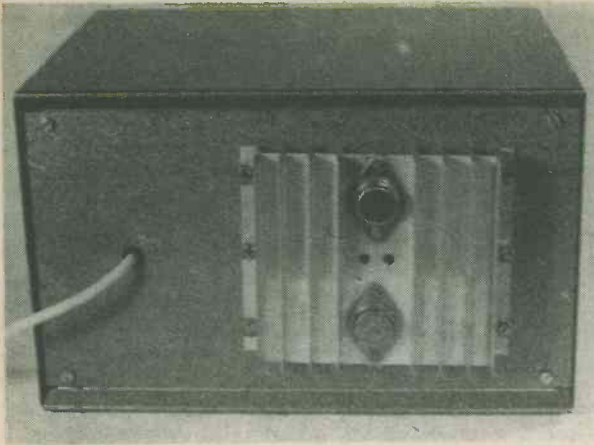

Two large pass transistors are mounted on a heatsink secured to the rear of the instrument case in which the power supply is housed

(depicted in simplified manner in the diagram as being provided by a zener diode) applied to its non-inverting input.

A potentiometer is connected between the op-amp output and the negative rail, its slider being returned to the inverting input. When the slider is at the top of the potentiometer track the output is connected to the inverting input, and the op-amp functions as a voltage follower with its output being virtually equal to the reference voltage at its non-inverting input.

Should the potentiometer slider be set to the centre of the track, the output will be twice the reference voltage. This voltage relationship is that which results in the inverting input being at the same potential as the non-inverting input. Because of the very high voltage gain of the operational amplifier the output voltage will remain fixed at this level despite differing load currents between the output and the negative rail. Other settings of


the potentiometer slider will produce corresponding stabilized output voltages. In practice, a fixed resistor has to be inserted between the lower end of the potentiometer track and the negative rail to limit the highest output voltage which may be obtained.

The 723C contains a quite sophisticated reference voltage generator, and its output at pin 6 connects direct to the op-amp non-inverting input at pin 5. VR1 and VR2 are the output voltage controls, and the slider of each connects to the inverting input at pin 4. Resistors R6 and R7 and R11 and R12, set the adjustment range limits. C2 and C6 provide frequency compensation for the operational amplifiers.


The stabilized output of the 723C is at pin 10, but the i.c., which has a maximum dissipation rating of 800mW only, is not capable of providing the relatively high output currents required of the power supply. Therefore, the outputs are coupled to two discrete power transistors, TR1 and TR2, which function as emitter followers and pass the output currents provided. The current limit series resistors are R3 to R5 and R8 to R10, and are selected by S2(a) and S2(b). The voltmeter which measures the voltage across them, and hence indicates the output current, is given by meter M1 in series with R1 and R2. R2 is adjusted for correct meter sensitivity. Meter M2, in company with R13 and R14, forms a voltmeter with an f.s.d. of 25 volts, and is connected across the upper or lower regulator output by means of S4(a)(b).

S3 connects the mains earth lead to the required supply rail. Note that the chassis of the power supply always connects to the mains earth regardless of the position of S3. C3 and C4 provide final smoothing and decoupling for the positive output, whilst C7 and C8 carry out the same function for the negative output.

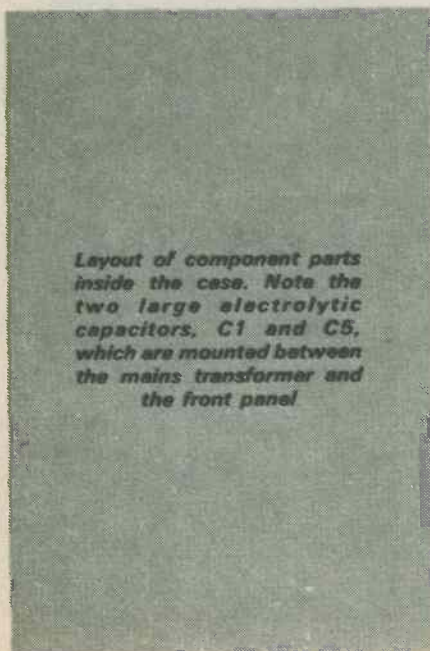The two fuses, FS1 and FS2, might at first be considered superfluous in a power supply which has automatic output current limiting. They are included because TR1 and TR2 are mounted on a



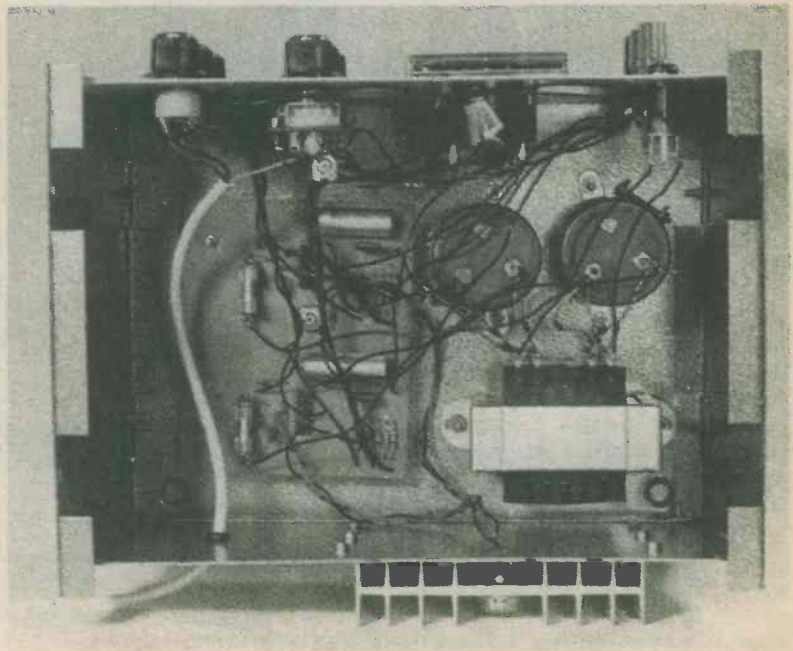Layout of component parts inside the case. Note the two large electrolytic capacitors, C1 and C5, which are mounted between the mains transformer and the front panel



Another view of the workshop power supply with its comprehensive control options. The legends on the front panel are taken from "Panel-Signs" Set No. 4.



heatsink which is at chassis potential, with the result that their bodies have to be insulated from the heatsink by mica washers and insulated bushes. If, for any reason, this insulation should fail, the unregulated section of the power supply could be short-circuited. The fuses thus protect this part of the supply. For optimum heat dissipation the transistors and the heatsink are positioned at the rear of the case, whereupon a short-circuit could also be given if a piece of wire or metal accidentally connected together one of the transistor bodies and the heatsink or if one of the transistor bodies came into contact with a conductor at earth potential.

COMPONENTS

The mains transformer employed for T1 is an R.S. Components part having two 20 volt 1.2 amp secondaries, and is described as a "50VA Transformer" with the type number 207-273. This is available through retailers who handle R.S. Components items. The two meters are both 0-100 μ A types, and are available from several suppliers, including Maplin Electronic Supplies and Home Radio. They have rectangular faces measuring 60 by 45mm. and an internal resistance of 580 Ω . S3 and S4 must be break-before-make rotary switches, and these can be obtained from Maplin Electronic Supplies. Break-before-make switches are essential here as otherwise the power supply outputs could be temporarily short-circuited when they are changed from one setting to the next. S2 may be a 4-pole 3-way rotary switch with only 2 poles used. S3 can be 4-pole 3-way with only 1 pole used. S4 can be, say, 2 poles of a 4-pole 3-way switch with adjustable end stop set for 2-way operation, or any other combination which gives 2-pole 2-way working.

The heatsink for the two transistors is a standard drilled type having dimensions of 124mm. wide and 102mm. high and can be seen in the photograph of the case rear. Two of the fixed resistors, R3 and R8, are specified in the Components List as 0.68 Ω . In practice, each consists of a 1.2 Ω $\frac{1}{2}$ watt 5% and a 1.5 Ω $\frac{1}{2}$ watt 5% resistor in parallel. The printed circuit board on which they are wired has provision for two resistors at both the R3 and R8 positions. The calculated value given by 1.2 Ω and 1.5 Ω in parallel is 0.667 Ω , which is sufficiently accurate for the present application.

The metal instrument case in which the power supply is built has dimensions of 254mm. wide by

159mm. high by 197mm. deep. This is a "Centurion" case model 222F, obtainable from Maplin Electronic Supplies. Finally, the three terminals, SK1, SK2 and SK3 are insulated types with a 4mm. top socket in addition to the usual terminal screw connection. They are available in various colours from which the constructor may make his own choice.

CONSTRUCTION

The layout and drilling dimensions for the front panel are shown in Fig. 4. The three terminals require a 7mm. hole, after which a small notch is made at the hole top to accommodate a locating pip in the insulated section of the terminal. The two large circular cut-outs for the meters may be made with a fretsaw. Once these cut-outs have been made, the meters themselves can be used to mark out the positions of the four small mounting holes around each. The remainder of the front panel drilling requires no comment apart from the hole for PL1. Some neon indicators may require a hole with a different size to that shown in Fig. 4.

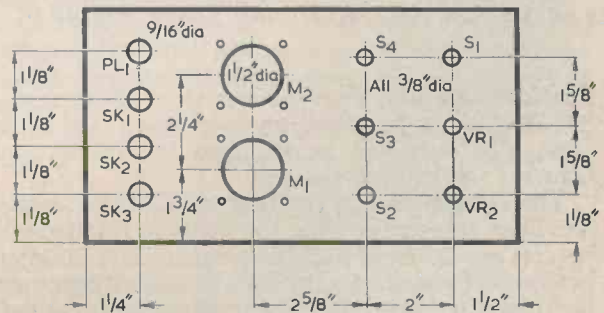


Fig 4. Drilling details for the front panel of the case

The mains transformer is mounted on the base of the cabinet at the left rear, with the primary and secondary tags facing towards the front. C1 and C5 are positioned side by side in front of the transformer, using suitable capacitor mounting clamps.

NEXT MONTH

In next month's concluding article we shall continue with constructional details and then carry on to the testing and setting up of this power supply.


(To be concluded)

CSC's EXPERIMENTOR BREADBOARDS

Continental Specialties Corporation, CSC, have announced three new advances in Breadboard design in their new Experimentor Breadboards.

Firstly, price — for as little as £1.60, CSC's Experimentor sockets let you design, assemble and modify circuits as fast as you can push-in — or pull-out — component leads. All Experimentor Breadboards have 0.1in. pitch which accepts all components, have letter/number system which identifies every hole and have built in bus-bars. They are precision-moulded out of durable, abrasion, temperature resistant material and pre-stressed nickel-silver contacts for positive connections and longer life.

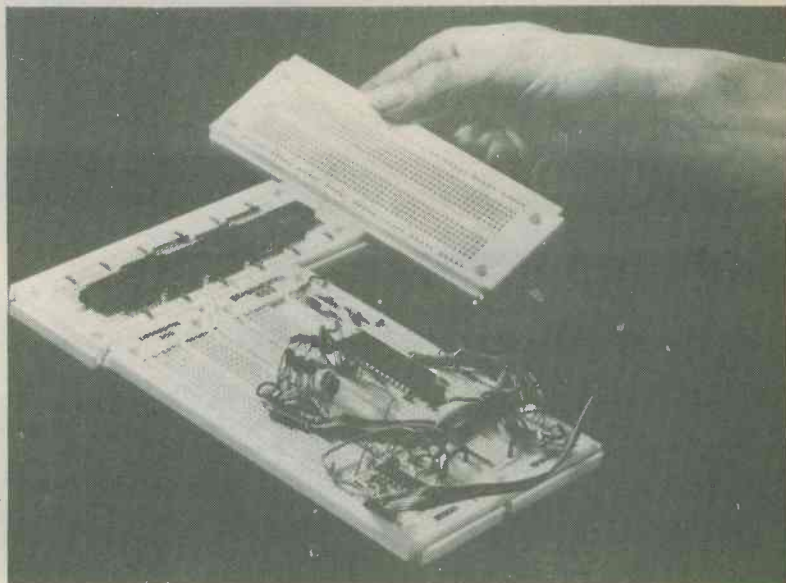Secondly, compatibility, Experimentor 600 Series 0.6in. centre is ideal for Microprocessors, clock chips, RAM's, ROM's, PROM's, etc. Whilst Experimentor 300 Series accept all DIP's on 0.3in. centres. Both units of course accept transistors, LED's, resistors, capacitors, pots, indeed almost any component and use ordinary solid core wire for jumper leads.



CSC Experimentor Breadboards are manufactured for development engineers, either professional or amateur

Finally, you can arrange your Breadboard to suit your circuit. Simply snap-lock together any size Experimentor Breadboard to any other vertically or horizontally.

THE VITAL VIDEO RACE RECORD

After a year's highly successful operation with two Fujinon semi-broadcast lenses. Racecourse Technical Services Ltd. — the firm that supplies officials with the vital video race-record which provides essential data for stewards' enquiries — has decided to purchase another lens of the same type. The lens will be supplied by Survey and General Instrument Co. Ltd.

The camera used is the Ikegami CTC 3X, and it has been adapted to take the Fujinon lens using a special mounting plate. The resulting combination is a powerful system with near broadcast standard but much lighter than the conventional broadcast camera with zoom lens.

This f 1.8 lens zooms from 29.5mm at wide angle to 413mm telephoto, and is particularly suitable for recording evening sporting events where the ambient light level is of low intensity. Every effort has been made to give this high power lens excellent light gathering properties: lens surfaces are all electron-beam coated to give especially good transmission ratios, and the iris is set electronically.



A Fujinon semi-broadcast lens in action on an RTS colour camera at Sandown Park

COMMENT

BRITAIN'S FIRST AMATEUR SPACECRAFT

The International Amateur Satellite Corporation (AMSAT) has to date, launched eight amateur satellites in the OSCAR series (Orbiting Satellites Carrying Amateur Radio). These have been built internationally by radio amateurs in the USA, Germany, Canada, Japan and Australia.

The University of Surrey's Telecommunications Research Group is to build Britain's first amateur spacecraft. It is working in conjunction with AMSAT and with the active support of Britain's electronics, telecommunications and aerospace industries.


The new satellite, to be built at Surrey University, will be Britain's first contribution in flight hardware to the Amateur Space Programme. The details of the special features and experiments that it will carry are still under discussion, but it is hoped to include a facility to enable radio amateurs all over the world to study the effects of the ionosphere on radio propagation.

The construction and testing of the satellite will take about two years and the cost is expected to be around £150,000 — a possible launch opportunity exists early in 1981. Support for the project is being provided by the Amateur Satellite Corporation (AMSAT) USA; the Amateur Satellite Organisation of the UK (AMSAT-UK); The Radio Society of Great Britain and a number of government agencies and commercial firms.

The University of Surrey's Telecommunications Research Group are certainly to be congratulated on their initiative and we are sure our readers will join with us in wishing the project every success.

Although we pride ourselves on being a practical magazine it is also part of our policy to stimulate interest in the scientific outreaches of our hobby and we shall continue, from time to time, to give news of this ambitious venture.

DESOLDERING STATION FOR INDUSTRY

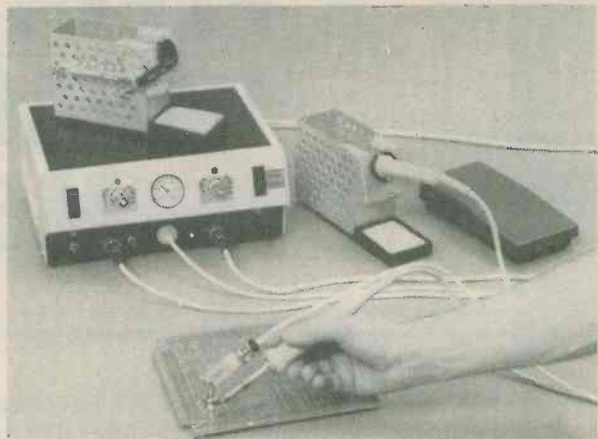

The Weller DS100 PEC Soldering/Desoldering Station with variable temperature control, from The Cooper Group

Cooper Tools Ltd., of Wear District 6, Washington, Tyne and Wear, has further developed its range of soldering and desoldering tools with the introduction of the soldering/desoldering station DS 100 PEC.

This new soldering/desoldering station has been specifically designed to meet the requirements of the electronic industry where highly sensitive components such as MOS and FETS are used.

The new DS 100 PEC can be operated either from factory compressed air systems or from a built-in vacuum pump. Both tools soldering and desoldering are operated at the safe low voltage of 24V, without earth connection. The vacuum for the desoldering action is controlled by a two-stage foot switch.

COMING CLUB EVENTS


●Royal Naval Amateur Radio Society Activity Period 0800 GNT 13th April 1979 to 1700 GMT 22nd April 1979. Location: HMS Belfast, Pool of London.


It is hoped to have at least three stations operational for twenty four hours per day during the above period using the call sign GB2RN. QSL's will be acknowledged on receipt only. The ship is open to the public from 1100 to 1800 daily and visitors are welcome.

Trio Corporation of Japan have kindly donated a complete HF installation to the special amateur demonstration station aboard the ship.

●The Northern Radio Societies' annual Radio & Electronics Exhibition NRSA 79 will be held at Belle Vue, Manchester on Sunday 22nd April 1979.

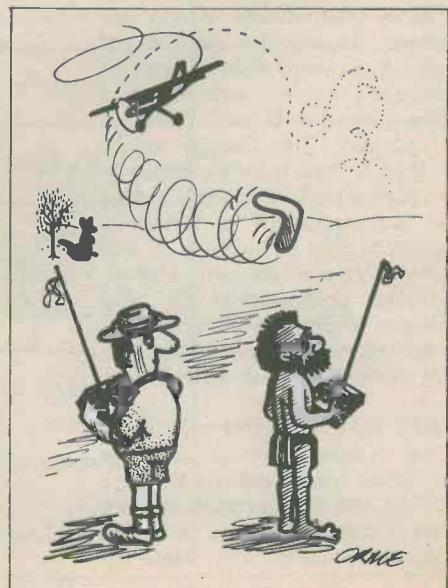The exhibition opens at 11.00 am, entrance fee is 20p which includes one raffle ticket, and the entrance is at the rear of Belle Vue opposite the main car park.



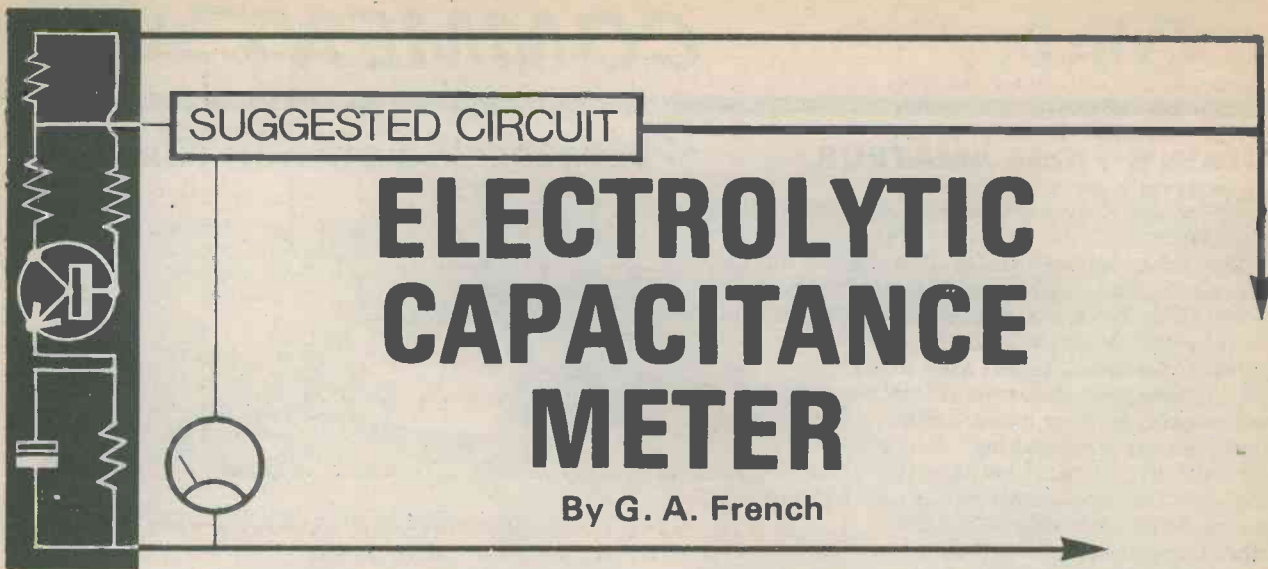

ELECTROLYTIC CAPACITANCE METER

By G. A. French

Many modern electrolytic capacitors have rather faint markings of value, and it quite often happens that these become partly or wholly erased particularly if the capacitors have been employed in a number of experimental circuits. Also, it is sometimes desirable to check electrolytic capacitors to ensure that they are offering their full nominal capacitance after having been held in stock for a considerable time.

Both these factors indicate that a useful item of test equipment can be a device which measures the capacitance of the capacitors concerned. However, the measuring device would not be employed very frequently and it would be uneconomic to make up permanently a unit which required a great deal of components or even, these days, a meter movement.

Fortunately, electrolytic capacitors are notoriously wide tolerance components which are employed in circuits capable of accepting a very wide spread in capacitance values, whereupon a precise indication of capacitance is not required. The design to be described in this month's article in the "Suggested Circuits" series takes advantage of a fortuitous operating feature of the 555 i.c. and requires only a small number of inexpensive components. It also employs a measuring instrument for the evaluation of capacitance, this being the user's wrist watch!

BASIC OPERATION

The basic circuit of the capacitance meter appears in Fig. 1 and, here, the 555 is connected in a standard circuit giving a one-shot monostable action. The value of

resistor R is known, whilst the value of the capacitor C is to be determined. A simple monitor circuit, which may be an arrangement of l.e.d.'s, can be connected to the output of the 555 to indicate whether this is in the high or low voltage state.

When the switch is closed the capacitor is discharged and the inputs at pins 2 and 6 of the 555 are low. The output at pin 3 of the 555 is then high. As soon as the switch is opened the capacitor commences to charge. When the voltage on the upper plate of the capacitor reaches two-thirds of the supply potential the internal comparator in the 555 becomes triggered and the 555 output goes abruptly low. The output remains low as C continues to charge until it reaches the full supply potential, and will only go high again when the switch is closed and the capacitor once more discharged.

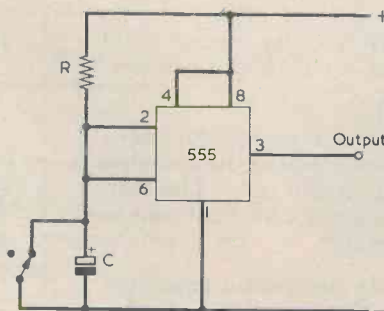


Fig. 1. The time taken for the capacitor to charge sufficiently to trigger the 555 is very nearly equal to the time constant of R and C. This enables the capacitance of C to be readily evaluated

In the circuit, the time taken for the capacitor to charge up to 63.2% of the supply voltage is known as the time constant of the capacitor and resistor. The time constant, in seconds, is equal to C times R, where C is in farads and R is in ohms or, more conveniently, where C is in microfarads and R is in megohms. The 555 triggers when the voltage across the capacitor is two-thirds, or 66.7% of the supply voltage. If we make the assumption that the 555 triggers after a time equal to the time constant of the capacitor and the resistor we shall be introducing only a relatively small error (acceptable with wide tolerance electrolytic capacitors) and shall have an extremely simple capacitance measuring device as a result. All we need to do is to find the time, in seconds, between the opening of the switch and the change in 555 output, and we can then use this time to calculate the value of C.

Before proceeding further, we have to consider the relationship between the capacitance, the resistance and the measured time constant. The time constant is equal to C multiplied by R. It follows from this that C is equal to the time constant divided by R.

FULL CIRCUIT

The full circuit of the electrolytic capacitance meter appears in Fig. 2. One addition here to the basic circuit of Fig. 1 is the 555 output monitor given by the two l.e.d.'s and their series resistors, R9 and R10. These indicate the output state of the 555: when the output is high LED1 is extinguished and LED2 is lit, and when the output is low LED1

is alight and LED2 is turned off. The short-circuiting switch of Fig. 1 appears as S1, with current limiting resistor R8 in series. R8 merely reduces possible sparking at the switch contacts if these close to short-circuit a charged test capacitor, and has no other effect in the circuit.

The single resistor of Fig. 1 is replaced by the seven resistors R1 to R7, these being selected by the range switch S2. When position 1 is selected the serious resistance is $1\text{M}\Omega$ whereupon the value of the test capacitance in microfarads is its time constant multiplied by 1. Position 2 of S2 switches in a $330\text{k}\Omega$ resistor and since this is (approximately) one-third of $1\text{M}\Omega$ the capacitance value is equal to the time constant multiplied by 3. If a $10\ \mu\text{F}$ capacitor is connected to the test terminals the time constant with the $330\text{k}\Omega$ resistor will be 3.3 seconds, giving a calculated capacitance value after multiplication by 3 of $9.9\ \mu\text{F}$. In practice, the timing will be to the nearest whole second, but this numerical example illustrates how the use of a $330\text{k}\Omega$ resistor causes the multiplying figure to be 3.

R3 has a value of $100\text{k}\Omega$, giving a multiplying figure of 10. The resistor values proceed in a similar manner up to R7, which has a value of $1\text{k}\Omega$ and gives a multiplying figure of 1,000. The accompanying Table lists the ranges and also shows nominal range limits, corresponding to time constants of 2 to 10 seconds. In use, it is almost certain that periods somewhat in excess of 10 seconds will be employed for measurement. Although such periods take up a little more time, they can yield a surprisingly high accuracy in results.

To take an example of how the meter may be used, let us imagine that we have an unknown electrolytic capacitor whose value we judge to be about $100\ \mu\text{F}$. Accordingly, we set S2 to range 4 and connect the capacitor to the test terminals. We then measure the time between the opening of switch S1 and the changeover of illumination in the two l.e.d.'s. We find this to be approximately 2 seconds, giving a calculated value of 30 times 2, or $60\ \mu\text{F}$. If we want a greater accuracy we can repeat the operation with S2 set to range 3. Should we find that the time constant then measures at 5 seconds we can say with more accuracy that the value of the capacitor is 10 times 5, or $50\ \mu\text{F}$. We could get an even

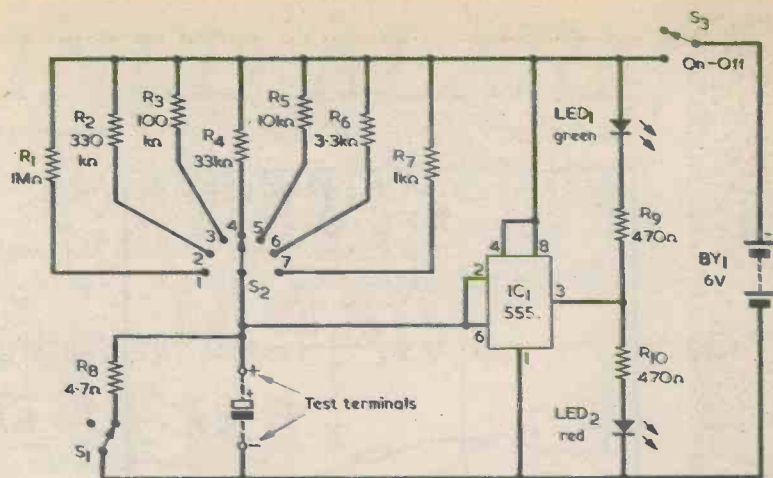


Fig. 2. The full circuit of the electrolytic capacitance meter. The ranges provided by S2 are listed in the table

higher level of accuracy by measuring the time constant with S2 switched to range 2, where the multiplier is 3, although the measurement will take longer than 10 seconds to carry out.

TIMING PROCEDURE

It might be considered that the measurement of the time constant could be rather difficult to carry out but the process is, in fact, quite easy. A front panel layout similar to that shown in Fig. 3 is helpful, the two l.e.d.'s being mounted fairly close together. Switch S1 should be a toggle type, which will have a quick snap action. When the meter is switched on with S1 closed the

red l.e.d. lights up. The test capacitor may then be connected to the test terminals.

If the wrist watch has a sweep second hand the switch may be put to the open position as the hand passes a 5-second division. With a digital watch the switch may be operated when the seconds figure reaches a multiple of 10. When the watch is held close to the panel of the meter it will be found possible to observe it whilst keeping the l.e.d.'s within the field of vision. The sudden change from the red l.e.d. to the green l.e.d. is very noticeable.

It will be seen that the positions of S2 in Fig. 3 are marked with the multiplier to which they correspond. All that then has to be remembered

TABLE

S2 Setting	Nominal Range	Multiply seconds by:
1	2-10 μF	1
2	6-30 μF	3
3	20-100 μF	10
4	60-300 μF	30
5	200-1,000 μF	100
6	600-3,000 μF	300
7	2,000-10,000 μF	1,000

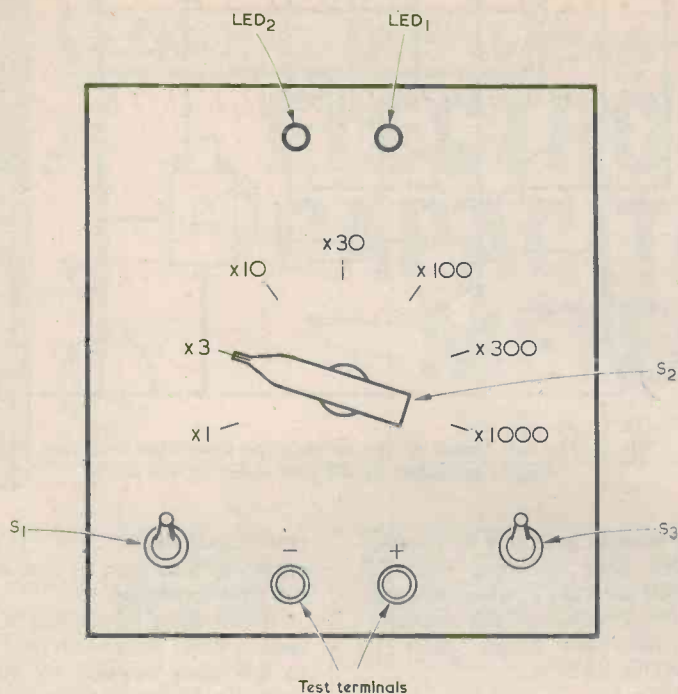


Fig. 3. A suitable panel layout. Mounting the two l.e.d.'s close together makes the changeover from LED2 to LED1 very noticeable visually

is that the test capacitance in microfarads is equal to seconds multiplied by the multiplier. A range of $2 \mu F$ to greater than $10,000 \mu F$ is available with the meter.

The current drawn from the 6 volt supply is of the order of 7mA plus charging current in the test capacitor. The latter will be initially 9mA when large value capacitors are being checked on range 7, and becomes progressively smaller on the lower ranges. A supply of 6 volts is employed since this will cater for nearly all electrolytic capacitors having low working voltages.

Apart from R8, all the resistors may be $\frac{1}{4}$ watt. R8 can pass some high momentary currents and it would be preferable to make this resistor $\frac{1}{2}$ watt. R1 to R7 can be 5% types and the remainder 10%. Switch S2 may be a 1-pole 12-way type with adjustable end-stop set for 7-way operation.

As a final point, if the capacitor being measured has been out of use for a considerable time it is advisable to allow it to charge by way of the meter for a short period before measuring its value. The initial charge will allow the capacitor electrolyte to "form" so that the capacitor then exhibits its true value. ■

New Product

THE 3rd HAND—NEW FROM THE U.S.A.

Tired of makeshift clamps or expensive, "in-the-way" pc board holders? "the 3rd Hand" gives you the answer. Simple, one-hand operation makes this sturdy tool a real helper. Leaves your bench top clear for working and the open-end construction allows it to hold boards of any size.

One year guarantee, recommended retail price £8.95. Special introductory offer £7.85 inclusive of post and packing.

Available from: Messrs Para Sales, 1 Hook Road, Kingsclere, Newbury Berks.



Clamp "3rd Hand" on edge of bench, table or workboard. Insert circuit board, position components — notice the convenient working angle

RADIO AND ELECTRONICS CONSTRUCTOR

SUSTAINED ALARM UNIT

By Vincent S. Evans

A neat circuit which allows a single 555 to do the job of two.


The 555 integrated circuit employed in this alarm project is a multivibrator designed to be used either in the astable mode or as a monostable. In the present application, however, the device has been made to offer both functions simultaneously. Published circuits which have come to the writer's notice use two 555's to achieve the same result, i.e. one to act as a timer and the other as an audio oscillator.

ACTIVE PERIOD

The astable mode is triggered by a momentary short-circuit at the input and continues for about 60 seconds. This period can be shortened, or extended to over ten minutes, by altering the value of the capacitor C1, according to the purpose for which the alarm is going to be used. R2 also influences the length of the period but is best kept within the limits of 33k Ω to 100k Ω .

In the circuit the resistor — capacitor chain R3, R4, C2 is the usual astable configuration for free running oscillation, producing a continuous audible frequency via the loudspeaker. The oscillation can only happen, however, if pin 4 of the i.c. is disconnected or held more than some 0.8 volt positive of the negative rail. (Pin 4 is the reset pin and is usually connected direct to the positive rail.) If pin 4 is held below 0.8 volt the astable function is cut off.

TR1 is normally turned off, with no voltage at its base. It passes negligible collector current and C1 is held discharged by R2, whereupon the voltage at pin 4 is below the critical 0.8 volt level. The astable multivibrator cannot then operate. If a positive pulse is applied to TR1 base by a temporary short-circuit of the input terminals the transistor turns on and causes C1 to charge to nearly the full supply

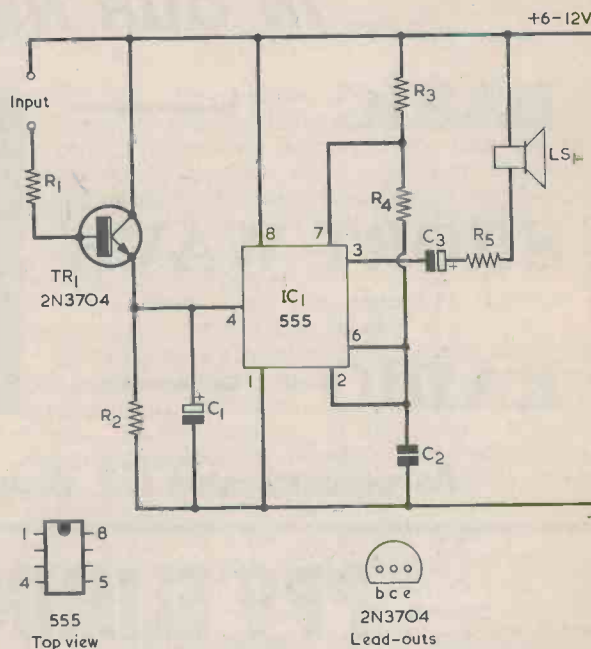

The circuit of the sustained alarm unit. In this, the 555 i.c. functions both as an astable multivibrator and as a controlling timer

ly voltage. The astable multivibrator will then start and will continue running until C1 has discharged sufficiently through R2. The period during which the multivibrator operates is much longer than the time constant of C1 and R2, because it ends when the voltage across C1 is a relatively small fraction of that it initially held when charged.

It is worth mentioning that if the input short-circuit is maintained the timing period cannot start and the alarm sounds continuously. This can be put to good effect in some applications. If the input is connected to a trigger mat the alarm will sound continuously if an intruder stands on the mat. What is more, it will continue to sound for the timing period after the intruder has left the mat, thereby adding to his confusion. Other means of operating and triggering the alarm circuit can be readily devised.

The output of the 555 is connected to the speaker via capacitor C3 and output current limiting resistor R5. The speaker may have any impedance between 3 Ω and 15 Ω . R5 could be omitted with an 80 Ω speaker, and this should give the loudest sound. Due to the inductive effect of the speaker voice coil it may still be necessary in some cases to insert a resistor of some 10 Ω in series with an 80 Ω speaker for best results. The musical pitch of the audio note can be changed by varying the value of C2.

COMPONENTS

Resistors

(All $\frac{1}{4}$ watt 10% unless otherwise stated)

- | | |
|------------------|-----------------------------------|
| R1 10k Ω | R4 33k Ω |
| R2 100k Ω | R5 82 Ω $\frac{1}{2}$ watt |
| R3 10k Ω | |

Capacitors

- C1 220 μ F electrolytic, 16V. Wkg.
 C2 0.1 μ F polyester
 C3 220 μ F electrolytic, 16V. Wkg.

Semiconductors

- IC1 555 TR1 2N3704

Speaker

- LS1 see text


RADIO & ELECTRONICS CONSTRUCTOR

IN OUR NEXT ISSUE —

BASIC —


SHORT WAVE

RADIO —

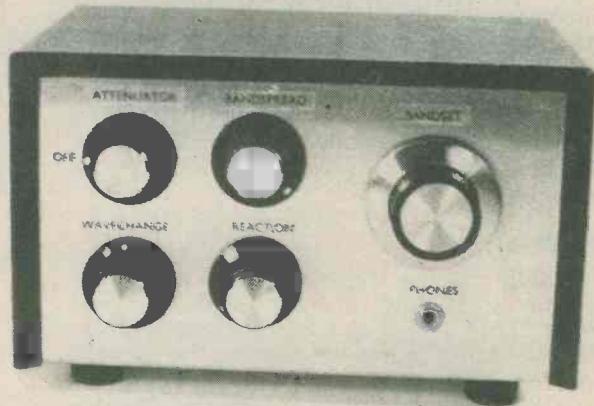

An uncomplicated t.r.f. design covering 1.2 to 24MHz

PP9 ELIMINATOR UNIT

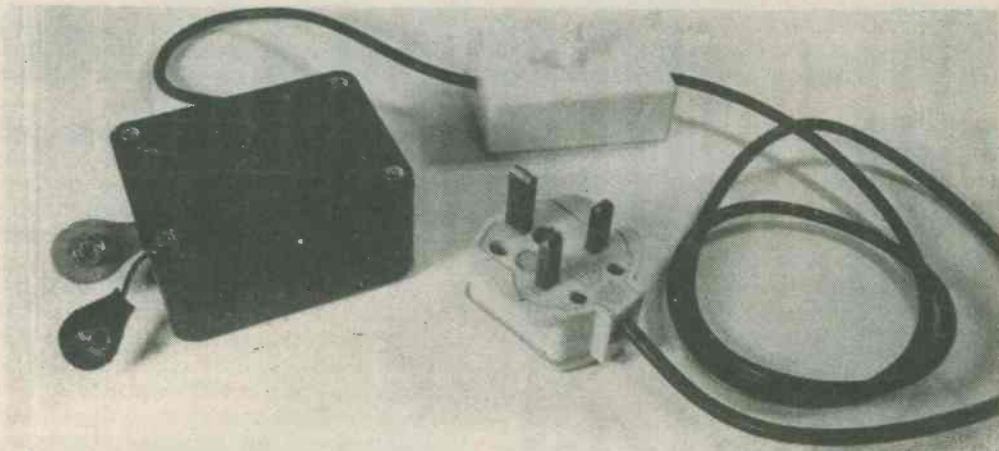

A simple and inexpensive unit designed to fit into battery compartment of a transistor radio

Supplies current up to 100mA: Fully Regulated: Fantastic Saving on Running Costs

*Remote Control Garage Light
Suggested Circuit*

*The "Slow Picture"
In Your Workshop*

MANY OTHER ARTICLES

ON SALE 4th MAY

Avoid disappointment. **ORDER NOW**

DESIGNING REFLEX CIRCUITS — Part 1

By Sir Douglas Hall, Bt., K.C.M.C.

Salient features in the design of reflex radio receivers

For anyone to be able to design his own circuits — perhaps the most exciting aspect of our hobby — he must have a basic knowledge of fundamental theory. That is to say, he must not only be able to recognise that a certain symbol represents, say, an audio frequency choke, he must also understand the total effects that this component will have on the circuit. With this yardstick in mind, readers will be able to judge whether the present article is likely to be helpful to them.

REFLEX RECEIVERS

A modern reflex receiver is one in which one or more active semiconductor devices is made to amplify more than once. Usually, one mode of amplification is at radio frequencies and the other is at audio frequencies, but in superhet designs the amplifications may be at intermediate frequencies and at audio frequencies. In the case of short wave superhets, the amplification can be at radio and intermediate frequencies or, even, at all three frequencies.

Reflex receivers were very popular in the early days of broadcasting since they allowed a single valve to amplify at the two separate frequencies, and the valves of the time were expensive and delicate. In addition, each valve drew 1 amp from a 4 volt accumulator as well as h.t. current from a high tension battery of 60 volts or more. There was obviously an advantage to be gained if one valve could effectively do the job of two. The popularity of the circuit fell away when dull emitter valves having lower filament current requirements were

introduced. The reflex circuit came back into favour when the first transistors capable of working at radio frequencies appeared as, like the early valves, these devices were expensive and rather fragile. There may seem less reason for using the reflex circuit today now that cheap transistors are available, but components generally are still expensive and a reflex receiver circuit uses far fewer of these than does the superhet. Design experiments are much less costly.

Fig. 1 shows a circuit in common use in the early 20's. John Scott-Taggart employed a similar arrangement, followed by a single amplifying triode, in his famous ST100 design which he described in *Modern Wireless* dated 9th January, 1923. It is known that at least 100,000 of these receivers were made, including one by the author some five years after the article appeared!

It will be seen that the valve amplifies as a tuned anode r.f. amplifier, the cat's whisker type crystal detects (after *very* careful adjustment!), the step-up transformer gives a voltage gain of about 5 times, after which the valve amplifies again, this time at audio frequency. The circuit was surprisingly efficient, and loudspeaker results were possible from the local station with one valve only. Reaction was obtained by inductively coupling the anode and grid coils together by means of a moving coil holder specially made for the purpose.

MODERN CONDITIONS

In designing reflex receivers for modern conditions, various points should be borne in mind.

Fig. 1. Reflex circuits were very popular in the early days of valves as they enabled one valve to carry out the functions of two. In this circuit, dating from the 1920's, the diode is a crystal detector with cat's whisker


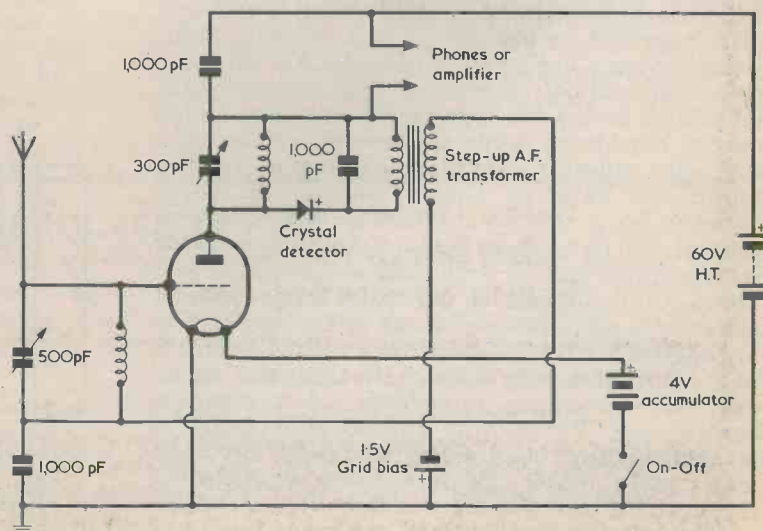


Fig. 2. A popular circuit from the days of low gain germanium transistors. Phasing problems preclude its use with modern transistors.

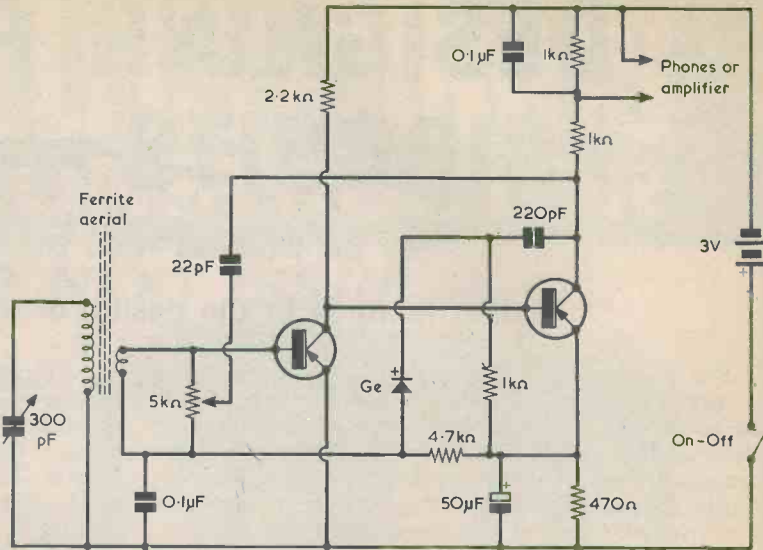


First, for maximum efficiency and economy the use of two reflexed transistors instead of one is suggested. Next, selectivity is nowadays more important than sensitivity which is, in any case, much easier to obtain. If the receiver is to employ only one tuned circuit, good selectivity requires careful design of circuitry. Should two or more tuned circuits be used, the only advantage of the reflex circuit over the more efficient superhet begins to fall away because of the consequent increased complication and expense. Thirdly, with modern high amplification transistors steps must be taken to avoid low frequency instability due to positive feedback. Precautions here are quite simple if the golden rule is observed that with medium and long wave designs any audio frequency at the output of the second transistor must be out of phase with any signal at the input of the first. In order that this state of affairs can be arranged, it should be remembered that the output of a common emitter amplifier is out of phase with its input, whereas in the cases of both common base and common collector amplifiers the output is in phase with the input.


It is also important to arrange that the output impedance of one transistor and the input impedance of the next should be similar. Much gain can be lost by damping the high output impedance of a transistor by coupling it to a following transistor having a low input impedance. For this purpose it should be remembered that common base amplifiers have a low input impedance and a high output impedance while the reverse applies with common collector amplifiers. Common emitter amplifiers have an output impedance which depends on a number of factors but which, in general, can be taken as medium. Input impedance with common emitter amplifiers also depends on a number of factors and in particular it rises with an increase in amplification factor or the application of negative feedback, and it falls with an increase in the current passing through the transistor. As an example, the input impedance of a common emitter amplifier with an amplification factor of 500 and passing $100\mu\text{A}$ might in a typical circuit be about $125\text{k}\Omega$, while a device with an amplification factor of 100 and passing a current of 1mA could, in the same circuit conditions, exhibit an input impedance of only about $2.5\text{k}\Omega$.

EARLY DESIGN

Fig. 2 shows a medium wave circuit which was very popular in the late 50's and early 60's. Applying the considerations which have just been dis-

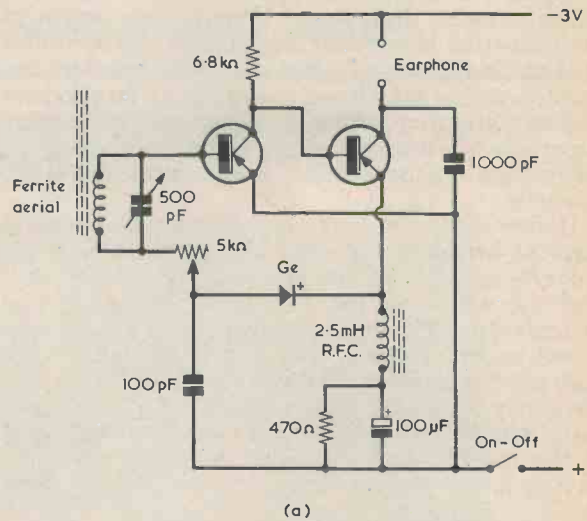

(a)

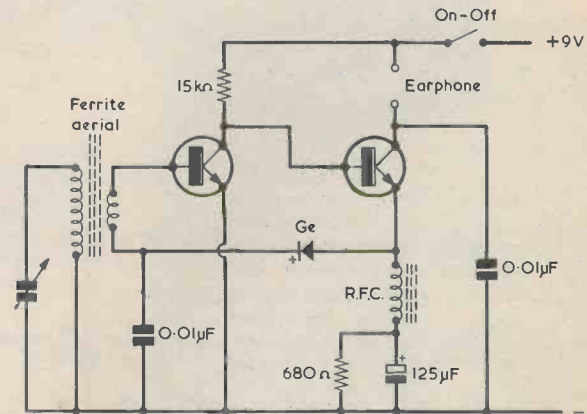

(b)

Fig. 5(a). A reflex circuit introduced by the author in 1964 (b). A circuit due to G. W. Short which was published in the January 1968 issue of this magazine


cussed it will be seen that TR2 output is in phase with TR1 input. With modern transistors there would be uncontrollable audio frequency instability. But the design used to be fitted with low amplification surface barrier germanium transistors so that stability was usually maintained. Selectivity was poor. In some versions employing more efficient transistors heavy negative feedback was applied to preserve stability.

In the April 1964 issue of this magazine the author introduced the circuit shown in Fig. 3(a). Here, in the reflex loop, a common emitter transistor is followed by a common collector amplifier, so that the output of the pair is out of phase with the input and no low frequency instability problem

arises. Also, because the impedance at the emitter of the first transistor is low there is good matching to the diode which does not damp the tuned circuit. The original circuit employed micro-alloy germanium transistors, but an article by the author in the November 1965 copy of this magazine described a modified circuit incorporating silicon transistors. In the January 1968 issue G. W. Short published an article showing his version of the circuit, which appears in Fig. 3(b). It will be seen that basically the two circuits are the same, although the one produced by G. W. Short has conventional coupling to the tuned circuit. Reaction with the circuit of Fig. 3(b) was pre-set by physically orienting the r.f. choke in relation to the tuned coil or by a small twisted wire capacitor from the collector of

"MINIFLEX"

TR1 back to the tuned coil; whereas the author's circuit offers variable reaction by means of the $5k\Omega$ potentiometer together with appropriate orientation of the r.f. choke. Either circuit will still give good results today, though selectivity will be a problem in areas where there is a powerful local transmitter. Indeed, these circuits give very similar results to those obtained with a ZN414 integrated circuit.

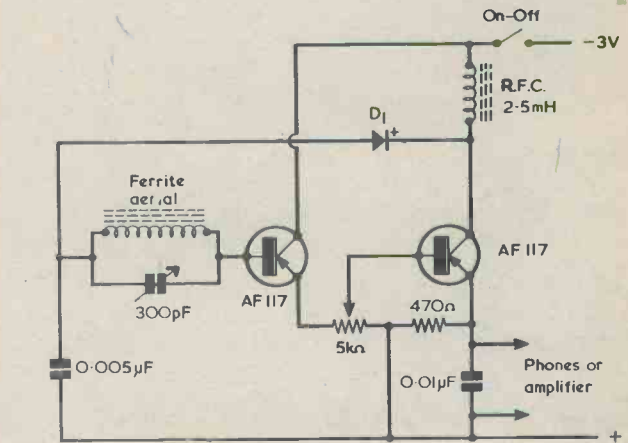

D₁ Selenium diode type M3

Fig. 4. The author's "Miniflex" circuit, which originally appeared in June 1968

copies for April and May 1977. The name "Miniflex" was given to the circuit. All recent versions have employed silicon transistors, and in the "M5" the selenium diode has been replaced by a silicon diode shunted by a 47pF capacitor.

In this circuit the first transistor is connected in the common collector mode and the second as a common emitter amplifier. Hence, as in the circuits shown in Fig. 3, the reflex output of the second transistor is out of phase with the input of the first transistor, and complete stability results. Here again, reaction is variably controlled by a potentiometer. The r.f. choke is oriented for proper reaction at the long wavelength end of the waveband. The circuit is sensitive and reasonably selective, and the author prefers it to that shown in Fig. 3(a).

(To be concluded)


MICROPROCESSOR HIRE

Emprise has started a new hire service for microprocessor evaluation and training systems. Intended for hands on training and experimentation the systems come complete with detailed instruction manuals and ready for immediate use. Types available include: National SCMP; Intel 8080; Motorola 6800; MOS Technology 6500; and Zilog Z80, with others available shortly. Rental is from £4.70 per week.

This inexpensive service enables users to gain 'hands on' experience with several systems for much less than the cost of a tuition course or evaluation kit.

As a further aid towards reducing costs, Emprise will help owners of unwanted or 'outgrown' evaluation kits and equipment sell their units to waiting buyers. Lists of secondhand equipment are available, which help put buyers and sellers in touch.

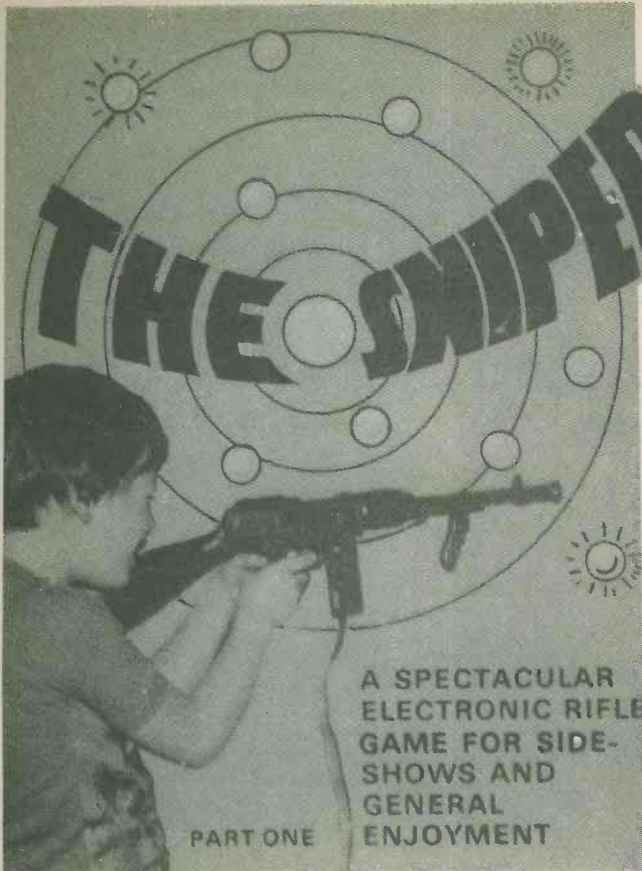For further details contact: Emprise 57, 25 Carlisle Close, Colchester, Essex CO1 2YT.



By E. A. Parr



**VERY
SUCCESSFUL
FUND RAISER**



**ENORMOUS FUN
TO PLAY**

This project was originally constructed as a fund raising side show for a Cheese and Wine party, but it is also great fun to play at home. The game consists of a machine gun and a target of ten lights, connected by an electronic control box. The lights come on one at a time, the machine gun "sees" the lights via a lens and photo-electric cell and the marksman tries to shoot the lights. The machine gun "fires" ten bullets per second, and hits and bullets are recorded on seven segment displays. The game ends after 80 hits or 800 bullets. In

its original use, a prize of a bottle of whisky was given for the least number of bullets for 80 hits, and it provoked quite a needle match to the benefit of our playgroup funds!

The gun is equipped with suitable sound and visual effects for added realism.

TARGET DESCRIPTION

As just mentioned, the target consists of ten light bulbs. These are 12 volt 2.2 watt m.e.s. types in batten lamp holders mounted in a random pattern on a board measuring about 4ft. by 3ft. Although the lights come on in a fixed sequence it is hard to memorise the pattern, and to the average marksman the display seems random.

The circuit to drive the lights is shown in Fig. 1. IC1 is the ubiquitous 555 connected as an oscillator with a period of about 4 seconds. The 555 output simply steps on a 7490 decade counter, IC3, via IC2 (a). The output of IC3 is decoded by IC4 and used to turn on one of the ten target lights via an open collector inverter and a simple output stage.

With a machine gun firing ten bullets per second, it would be a little bit too easy if the marksman were allowed to saturate the target. When a hit is given, the control logic sends a pulse to IC2 (a) pins 9 and 10 to step the counter. As we shall see, the control logic also inhibits the gun for 0.5 second which covers the slight possibility that the 555 was also pulsing the counter at the same time.

Switch S1 inhibits the stepping of the counter. This is used when the game is being set up in a new location. The stationary target simplifies the setting of the sensitivity of the gun photo-electric cell.


RADIO AND ELECTRONICS CONSTRUCTOR




There is no age limit in this electronic rifle game. It is ideal for amusing the young



By E. A. Parr

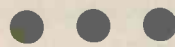

**VERY
SUCCESSFUL
FUND RAISER**

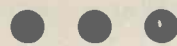

**ENORMOUS FUN
TO PLAY**

This project was originally constructed as a fund raising side show for a Cheese and Wine party, but it is also great fun to play at home. The game consists of a machine gun and a target of ten lights, connected by an electronic control box. The lights come on one at a time, the machine gun "sees" the lights via a lens and photo-electric cell and the marksman tries to shoot the lights. The machine gun "fires" ten bullets per second, and hits and bullets are recorded on seven segment displays. The game ends after 80 hits or 800 bullets. In

its original use, a prize of a bottle of whisky was given for the least number of bullets for 80 hits, and it provoked quite a needle match to the benefit of our playgroup funds!

The gun is equipped with suitable sound and visual effects for added realism.

TARGET DESCRIPTION

As just mentioned, the target consists of ten light bulbs. These are 12 volt 2.2 watt m.e.s. types in batten lamp holders mounted in a random pattern on a board measuring about 4ft. by 3ft. Although the lights come on in a fixed sequence it is hard to memorise the pattern, and to the average marksman the display seems random.

The circuit to drive the lights is shown in Fig. 1. IC1 is the ubiquitous 555 connected as an oscillator with a period of about 4 seconds. The 555 output simply steps on a 7490 decade counter, IC3, via IC2 (a). The output of IC3 is decoded by IC4 and used to turn on one of the ten target lights via an open collector inverter and a simple output stage.

With a machine gun firing ten bullets per second, it would be a little bit too easy if the marksman were allowed to saturate the target. When a hit is given, the control logic sends a pulse to IC2 (a) pins 9 and 10 to step the counter. As we shall see, the control logic also inhibits the gun for 0.5 second which covers the slight possibility that the 555 was also pulsing the counter at the same time.

Switch S1 inhibits the stepping of the counter. This is used when the game is being set up in a new location. The stationary target simplifies the setting of the sensitivity of the gun photo-electric cell.



There is no age limit in this electronic rifle game. It is ideal for amusing the young

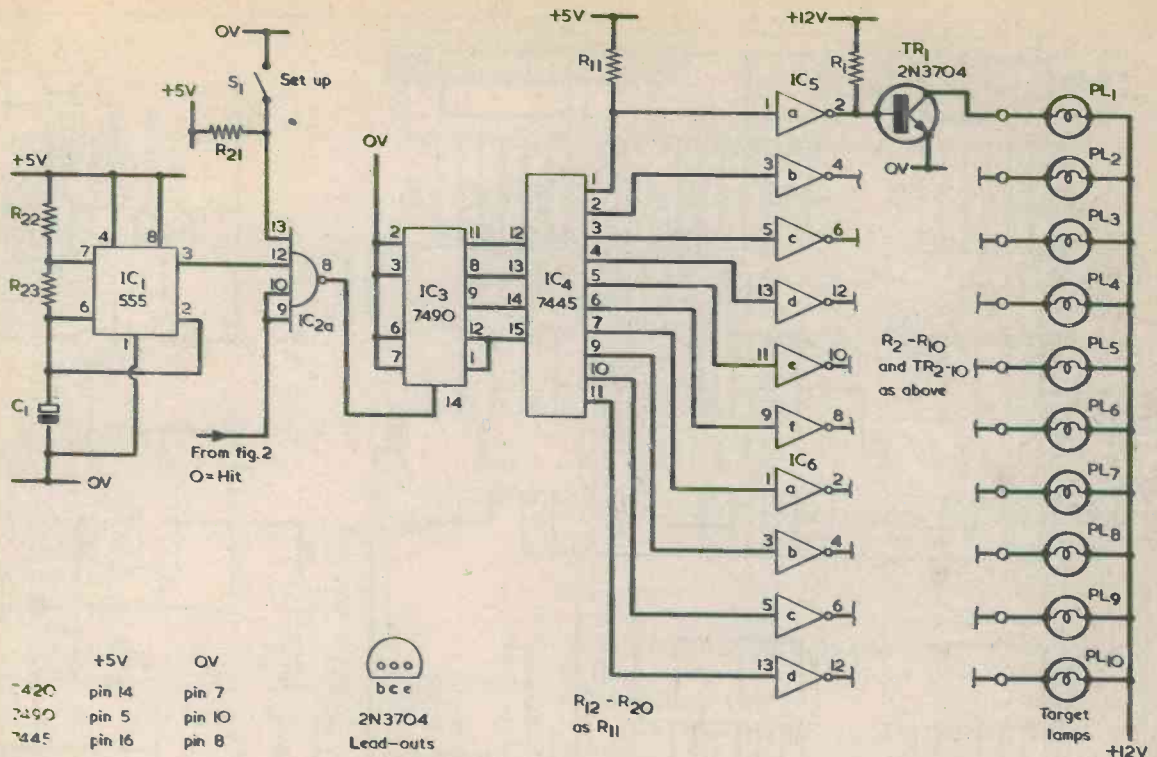


Fig. 1. The target logic

MAIN CONTROL LOGIC

The main logic is shown in Fig.2. Although the target logic and control logic are drawn separately they were, in fact constructed on one board.

The heart of the logic is the hits counter and display (IC12, IC13, IC17, IC18) and the shots counter and display (IC14 to IC16 and IC19 to IC21). These are text book circuits using 7490 counters, 7447 decoders and common anode seven-segment displays.

The machine gun rate is determined by IC1(a), arranged to be a 10Hz oscillator of approximately equal mark-space. The "bullets" produced are gated at IC2(b). IC2 pin 5 input comes from the bounce removing flip-flop IC9(a)(b), and is at a "1" when the trigger is pulled. IC2 pin 2 input inhibits the bullets for 0.5 second when there is a "hit" and IC2 pin 1 input inhibits the bullets when the game is over. These latter two signals will be described later.

The bullet pulses go straight to IC16 pin 14 to increment the shots counter.

The p.e.c. signal from the gun is nominally at 12 volts positive when the p.e.c. is on target. This is changed to a t.t.l. signal by TR11 and IC7(a). It is then gated with the bullets by IC9(c) to give a "0" pulse for a hit, which steps the hit counter IC13. The same signal also goes to IC2(a) pins 9 and 10 in Fig.1 to step on the lights after a hit.

At the same time the monostable IC10(b) is triggered. This has a period of 0.5 second and serves two purposes. The first is to sound the front panel hit buzzer via TR12. The second is to inhibit the bullets so the target can step on as described previously. The inhibit is done by IC7(d) onto pin 1 of IC2(b). The buzzer is any audible alarm which

can be operated by TR12, such as the RS Components audible warning device No. 248-808.

When the circuit was first built, it was found that a race could develop between IC2(b) and IC10(b). This had the effect of counting several hits for one bullet. The race was cured by the addition of C4.

When IC12 pin 11 goes to a "1" (for 80 hits) or IC14 pin 11 goes to a "1" (800 bullets) the output of IC8(a) goes to a "0", inhibiting further bullets, and TR13 lights the "game over" lamp.

The gun effects are produced by IC11. IC11(a) is a simple buffer, and drives a gun l.e.d. This is a large red l.e.d. in the gun body to simulate the gun flashes. IC11(b) is a 400Hz oscillator, swept up and



It can give the older ones plenty of fun too!

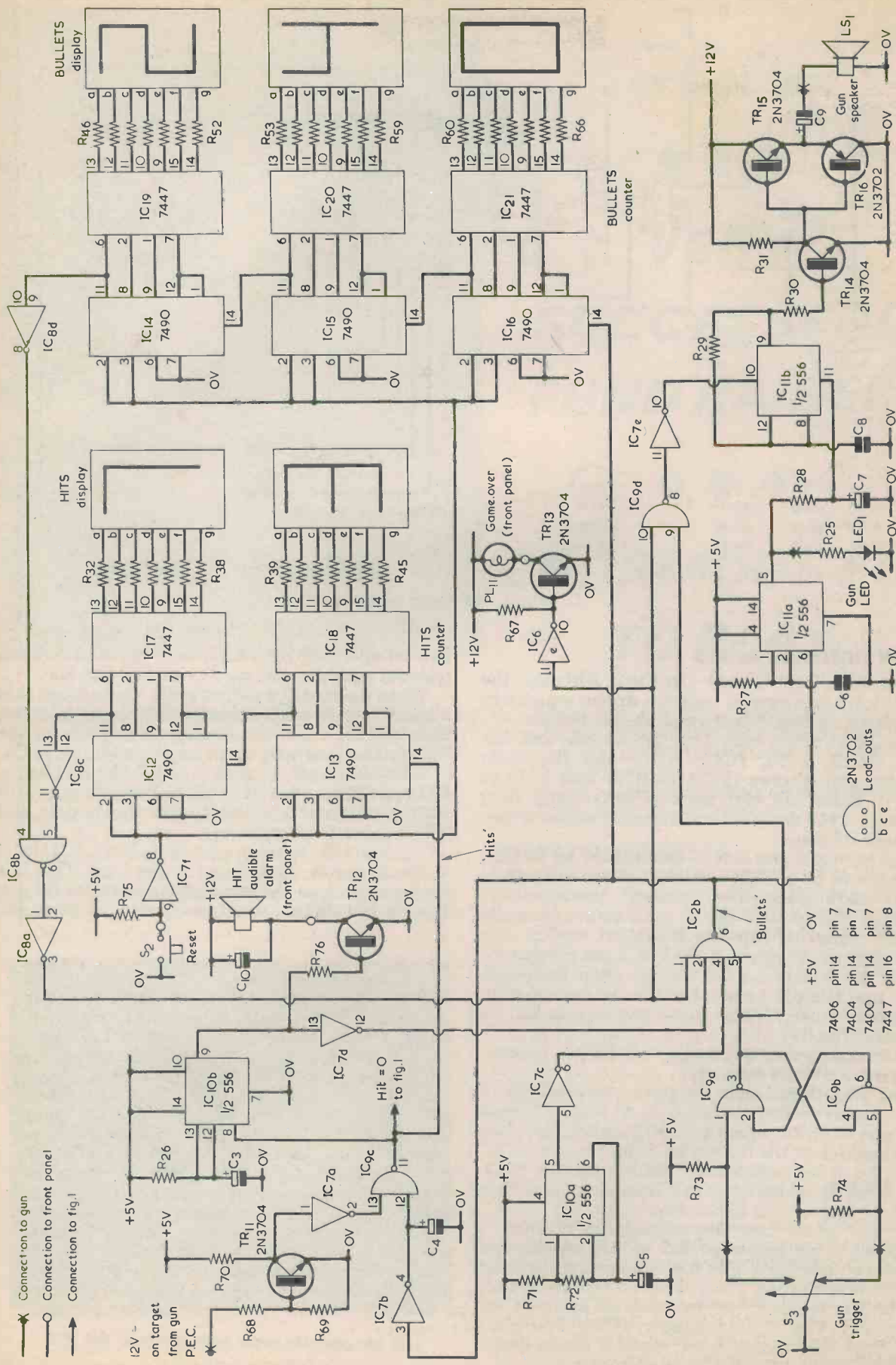


Fig. 2. The main logic. Pin connections to the five 7-segment displays depend on the particular displays employed

COMPONENTS

Resistors

(All fixed values $\frac{1}{2}$ watt 5%)

R1-R10 2.2k Ω
 R11-R21 4.7k Ω
 R22 100k Ω
 R23 1k Ω
 R24 10k Ω
 R25 120 Ω
 R26 100k Ω
 R27, R28 1k Ω
 R29 22k Ω
 R30 10k Ω
 R31 1k Ω
 R32-R66 270 Ω
 R67 2.2k Ω
 R68, R69 47k Ω
 R70 4.7k Ω
 R71 1k Ω
 R72 100k Ω
 R73-R75 4.7k Ω
 R76 270 Ω
 R77 2.2k Ω
 VR1 500k Ω or 470k Ω pre-set potentiometer,
 0.1 watt.

Capacitors

C1 47 μ F electrolytic, 10V. Wkg.
 C2 0.022 μ F polyester
 C3 4.7 μ F electrolytic, 10V Wkg.
 C4, C5 1 μ F tantalum, 16V. Wkg.
 C6 0.01 μ F polyester
 C7 100 μ F tantalum, 5V. Wkg.
 C8 0.1 μ F polyester
 C9 1,000 μ F electrolytic, 25V. Wkg.
 C10 22 μ F tantalum, 16V. Wkg.
 C11 5,000 μ F electrolytic, 25V. Wkg.
 C12 0.1 μ F polyester
 10-off 0.01 μ F polyester (see text)

Transformers

T1 Mains transformer, secondary 9V at 1A
 T2 Mains transformer, secondary 6V at 1A

Displays

5-off 7-segment common anode displays

Semiconductors

TR1-TR15 2N3704
 TR16 2N3702
 IC1 555
 IC2 7420
 IC3 7490
 IC4 7445
 IC5, IC6 7406
 IC7 7404
 IC8, IC9 7400
 IC10, IC11 556
 IC12-IC16 7490
 IC17-IC21 7447
 IC22 15V LAS
 IC23 7805
 REC1, REC2 silicon bridge rectifier, 1 amp.
 LED1, LED2 general purpose l.e.d. red

Switches

S1 s.p.s.t. toggle
 S2 push-button, press to make
 S3 s.p.d.t. microswitch
 S4 d.p.s.t. toggle

Speaker

LS1 miniature speaker, 75 Ω

Alarm

Audible warning device (see text)

Fuses

FS1 Cartridge fuse, 500mA
 FS2, FS3 Cartridge fuse, 2A

Lights

PL1-PL11 12v 2.2W m.e.s.

Miscellaneous

Gun (see text)
 12-core cable
 Lens
 Stripboard (see text)
 11-off m.e.s. batten bulbholders
 3-off fuse holders
 Interconnection plugs and sockets (see text)

down by the ramp generated by IC11(a), R28 and C7. The ramp is applied to the control voltage pin of IC11(b). The resulting warble is applied to a speaker in the gun by TR15 and 16. Having just seen "Star Wars", the author had a preference for a laser gun! The effects make the gun very satisfying to use.

The "reset" push button sets the bullet and hit counters to zero.

NEXT MONTH

Next month's concluding article will deal with the gun circuit and the gun construction, together with other relevant information.

The full Components List appears with the present article. It will be noted that ten 0.01 μ F capacitors are listed without C-numbers. These are distributed throughout the circuit as supply bypass capacitors at one per two 74 series i.c.'s. The

15V LAS photo-electric cell is available from RS Components. The prototype logic was assembled on an i.c. stripboard, RS Components No. 433-911. Alternative means of mounting and wiring the components can of course be used. IC23 is a 7805 5-volt regulator, also available from RS Components. It is rated at 1 amp and has an input voltage range of 7 to 25 volts. Switch S3 is a microswitch, such as the RS Components 337-879. (RS Components do not deal directly with individual constructors, and readers will need to order the appropriate parts through a retailer such as Ace Mailtronix Limited, Tootal Street, Wakefield, West Yorkshire, WF1 5JR.)

Details of the gun and lens, etc., will be given next month. Some of the parts in the Components List will also appear in circuits to be published next month.

(To be concluded)

EXCLUSIVE NEW SERIES

TUNE-IN TO PROGRAMS

Part 4

by

Ian Sinclair

Take a running jump

Normally, a program progresses smoothly from step 00 through steps 01, 02, 03, and so on to the last step, which is usually the [R/S] instruction. A jump is a step, backwards or forwards, which is out of sequence for some reason. The key on the Texas Instruments TI-57 marked [GTO] ([GOTO] on the PR-100) causes a program to jump in this way, and can also (see later) be used to locate a part of a program.


LABELLING KEY

When the [GTO] key is used in a program, it must be followed by a number, 0 to 9 on the TI-57, to indicate where the next step is. How does the number tie in with the program? The answer, as far as the TI-57 is concerned, is the labelling key, marked [Lb1], and activated by pressing [2nd] [R/S]. Suppose, for example, we want to find values of the reactance of a capacitor C at various frequencies. Just for the sake of an example, say we want to find the reactance of a $0.01\mu\text{F}$ capacitor at 1kHz and then at each 1kHz upwards. The formula for reactance of a capacitor is:

$$X_c = \frac{1}{2\pi fC}$$

which is $1/f \times 1/2\pi C$, with only the value of f changing from one calculation to the next.

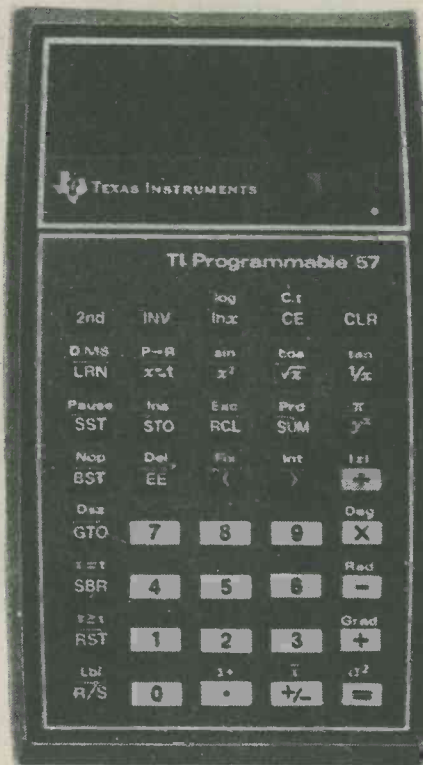The program of Fig. 1 does this. The first 7 steps



The keyboard of the Texas Instruments TI-57 programmable calculator. Most keys have a second function, whereupon facilities are nearly double the number of keys provided

are used to calculate the value of $1/2\pi C$, with the value of the capacitance C stored in memory 1. The value of $1/2\pi C$ is then stored in memory 1 ready for use, replacing the value of C in that memory. The

Program

```
LRN 2 X π X RCL 1
= 1/x STO 1 Lb1 0
(RCL 2 X 1 EE 3)
1/x X RCL1 =
Pause Pause Pause
1 SUM 2 GTO 0 LRN
```

Procedure

Enter value of C in μF , followed by EE 6 +/- STO 1 1 STO 2 Fix 2 CLR RST R/S Read answer on display at each pause. Test Data: C = $0.01\mu\text{F}$ gives first answer 1.59×10^4 which is displayed as 1.59 04.

Fig. 1

next step in the program is [LbI] [0] which doesn't cause anything to happen. As the name suggests, it's just a label, a way of marking a part of the program. The PR-100 uses the step number as a label rather than inserting a label into the program.

The program now goes on to [RCL] [2], taking out of memory 2 the value of frequency which, at the start, is 1kHz. The value of frequency is inverted (giving $1/f$), the value of $1/2\pi C$ recalled using [RCL] [1] and the two multiplied to give the value of X , the reactance. This is displayed, with three pauses to give you time to note it down, then 1 is added to the memory store by programming the instruction [1] [SUM] [2]. To calculate the reactance of the capacitor for the new frequency, we do not need to go over the whole program again, we only need the bit concerned with frequency. The next instruction is therefore [GTO] [0], meaning "go to the program step following label 0", which is the calculation of $1/f$. The complete program therefore starts by calculating $1/2\pi C$, then $1/f$, then multiplies and displays, but does not repeat the calculation of $1/2\pi C$, only the calculation of $1/f$ and the multiplication, display and increase of f value. Note that the steps [X] [1] [EE] [3] are used following the recall of the f value, so that the value in kHz is converted into values of frequency in Hz, as is needed in the formula. This, of course, could be tidied up by expressing the formula in kHz.

We can, of course, press [R/S] while the answer is being displayed (during the pause) and find out what frequency we've got to by pressing [RCL] [2]. Another press of [R/S] will start the program running again.

A jump made by using [GTO] and [Lb I] is very useful when part of a program has to be repeated. This type of jump is called an unconditional jump, because there's no choice about it: when the program gets to [GTO] [0] it just has to go to label 0. The [GTO] key followed by a two-digit number (such as 01, 07, 14, 26) can be used after the machine has been programmed (and after the [LRN] key has been pressed for the second time) to go to any part of a program, so that a program can be started at any point. More of this sort of thing later.

Even more useful than the unconditional [GTO] jump is the *conditional* jump, which enables decisions to be made. Suppose, in the program

we've just illustrated, we want to stop the calculations when $f=20\text{kHz}$. We can program so that the value of f is compared with 20, and when the two are equal, the action stops. The key which does this is $[x=t]$, activated by pressing [2nd] [SBR].

MEMORY 7

To be able to use the $[x=t]$ instruction in a program, we need to have a number stored in the "t" register, which is memory No. 7 of the TI-57. When the step $[x=t]$ occurs in a program, the number in the display is compared with the number stored in memory 7. If the two numbers are equal, so that $x=t$ (x is always taken as the number on the display) then the program goes on to the next step as if nothing had happened. If the two are not equal then the following step of the program is skipped, and it is the step *after that one* which is actually used. Suppose, for example, we had the sequence, a very common one, in our program:

$[x=t]$ [R/S] [GTO] [0]

If the number in the display equals the number in memory 7, then the program stops, displaying that number. If the number in the display is not equal to the number in memory 7, then the [R/S] step is skipped, and the next instruction is [GTO] [0], so that the program goes to label 0 and runs on from that point.

This step lets us program the calculator so that it will stop after it has done a pre-arranged amount of work. Let's go back to that program which calculated the reactance of a capacitor for values of frequency in 1kHz steps from 1kHz to 20kHz. A program is shown in Fig. 2, making use of the $[x=t]$ key. The early steps are pretty much the same as we used before, but we are now using a modified formula so that we don't need to change the units of frequency from kHz to Hz. On each run through, we check the value of frequency against the number stored in memory 7. We will enter 20 into memory 7 before we run the program, so that when the number in store 2 is less than 20, the next instruction will be to add 1 to the number in store 2 and then to go to label 0 to start another calculation. When the 20kHz value has been displayed, then the $[x=t]$ instruction ensures that there is no skip this time, and the [R/S] step stops the action of the

Program

```
LRN 1 STO 2 159 ÷
RCL 1
= STO 1 LbI 0 RCL 1 ÷
RCL 2 = Pause Pause
Pause
RCL 2  $x=t$  R/S 1 SUM
2 GTO 0 LRN
```

Procedure

```
Enter value of C in  $\mu$  F
STO 1 Fix 2 20 STO 7
CLR RST
R/S
When the run has finished, the figure 20 will be displayed indicating that 20 calculations have been completed.
```

Fig. 2

program. We can place the [x=t] step anywhere we like in the program — within limits. The limits are that we must be sure that it does what we want. If, for example, in the program of Fig. 2 we used [x=t] before the value of reactance had been calculated, then we would find that the program stopped before the last calculation.

A slight modification of Fig. 2 is given in the program of Fig. 3.

One of the very useful features of the TI-57 is that a total of four "questions" can be put for a decision. In each case, if the answer is NO, the program skips the next step; if the answer is YES, the program continues normally. The first of these conditional jumps, as they are called, is the [x=t] step which we've just met. We can also use the key sequence [INV] [2nd] [SBR], which is [INV] [x=t], asking the question "is x NOT equal to t?". Two more skips are available from the key [x≥t]. Used by itself (pressing [2nd] [RST]) the question is "is x greater than or equal to t?". When the [INV] key is used (before or after [2nd]) the question is then "is x less than t?"

The ability to test the number in the display in these four ways makes some quite interesting programming possible. PR-100 owners should note that their corresponding key is [SKIP] which will cause the program to skip a step (or two, depending on what the next step is) if the number in the display is negative. This avoids the use of a memory as a test register, but needs some thought in the programming stage. In our example, the frequency value in use would have to be subtracted from 20 before the [SKIP] step operated.

CALCULATING POWER

By now, you should be getting a flavour of the calculating power which the TI-57 and the PR-100 can deliver, so let's look at a program which makes a lot of use of conditional jumps.

Let's suppose that we are working on the resonant frequencies of coils and capacitors. What we want to find are the ranges of capacitors that we can use with given coils to resonate in the range 1MHz to 30MHz — we can, of course, alter the program to accommodate different frequency ranges. We want to be able to enter the coil inductance value, in μH , onto the display, to press [R/S], then see the display give the nearest preferred value of capacitor which will resonate around the upper limit (in this case around 30MHz). Pressing [R/S] again will result in a display of the preferred capacitor value which gives a resonant frequency closest to the lower limit, 1MHz in this case. A real bit of computing magic, this one, and quite a tall order. How do we go about it?

In fact, it would be quite easy if we knew right now what we shall soon know about sub-routines; it's not so easy at our present state of learning. The program (Fig. 4) starts by calculating what value of capacitance is needed to resonate with the amount of inductance at 30MHz. The formula here is $C = 28/L$, with C in pF. This quantity of capacitance is stored in memory 1, and a 1 is stored in memory 0. The division of [RCL] [1] by [RCL] [0] at this stage leaves the value of C unchanged, and the result is stored in memory 7, which is the test register.

The next steps are comparisons of the preferred values 1, 1.5, 2.2, 3.3, 4.7 and 6.8pF with the value of C which is stored in memory 7. Memories 2 to 6 inclusive are used for storing preferred values, the first value of 1 is used directly. If any one of these values in pF exceeds the value in memory 7, the [GTO] [2] instruction causes the value to be displayed. If the final value of 6.8pF is too small, the instruction [10] [Prd] [0] which follows the last [x≥t] step divides the capacitance value in memory 1 by 10, using [RCL] [1] [÷] [RCL] [0] when the program repeats. If the next run through produces a preferred value (now in the range of 10 to 68pF) greater than the value of capacitance stored in memory 7, the

This is a slight modification of Fig. 2. Instead of 20 being displayed at the end of the program, the display flashes to draw attention to the fact that this is the end of the program. This is done by using an impossible instruction; in this case GTO 1 should be GTO 1 with nothing entered under Lbl 1.

Program

```
LRN 1 STO 2 159 ÷
RCL 1
= STO 1 Lbl 0 RCL 1
÷ RCL 2
= Pause Pause Pause
RCL 2 x=t GTO 1
1 SUM 2 GTO 0 LRN
```

Procedure

As for Fig. 2.

Fig. 3

The program aims to find what range of capacitor preferred values will tune a given inductor (value in μ H) between 1MHz and 30MHz.

Program

```
LRN 1/x X 28 =
STO 1 1 STO 0
Lbl 1 RCL 1 ÷ RCL 0
= STO 7
1 x ≥ t GTO 2
RCL 2 x ≥ t GTO 2
RCL 3 x ≥ t GTO 2
RCL 4 x ≥ t GTO 2
RCL 5 x ≥ t GTO 2
RCL 6 x ≥ t GTO 2
10 Prd 0 GTO 1
Lbl 2 X RCL 0
= R/S 889 Prd 1
1 STO 0 GTO 1 LRN
```

Procedure

Enter as follows:
 1.5 STO 2
 2.2 STO 3
 3.3 STO 4
 4.7 STO 5
 6.8 STO 6
 CLR
 Enter inductance in μ H
 RST
 R/S
 Display shows C in pF
 for closest to 30MHz
 R/S
 Display shows C in pF
 for closest to 1MHz.
 All C values are nearest
 preferred values.

Fig. 4

preferred value is displayed by recalling the figure from memory and multiplying by the power of 10 stored in memory 0.

If the values are still too low, the number in store 0 is multiplied by 10 again (equivalent to using capacitors in the range 100 to 680pF) and so on. The final result will be the preferred value of capacitance which is the nearest (on the low side) to that needed for tuning to 30MHz. At the next press of the [R/S] key, the capacitance value in store 1 is multiplied by 889, since this gives the amount of capacitance needed to tune to 1MHz. Memory 0 is returned to 1

again, and the loop of operations starting at label 1 is started again. The same procedure is used, ending with the display showing the preferred values nearest (on the low side) to that needed to tune to 1MHz. The answer is, once again, in pF.

Take your time over this one, it's a much more elaborate program than anything we have done before. The idea is to show just what can be done with these remarkable machines. Next month we'll have a different type of jump operation which is already built into the machine in the form of the [Dsz] key.

Double Decker Series

We regret that No. 7 in this series, also written by Ian Sinclair, has been held over to next month due to pressure on space.

The article will be *Sound-Operated Light Switch*.

Mail Order Protection Scheme

The publishers of this magazine have given to the Director General of Fair Trading an undertaking to refund money sent by readers in response to mail order advertisements placed in this magazine by mail order traders who fail to supply goods or refund money and who have become the subject of liquidation or bankruptcy proceedings. These refunds are made voluntarily and are subject to proof that payment was made to the advertiser for goods ordered through an advertisement in this magazine. The arrangement does not apply to any failure to supply goods advertised in a catalogue or direct mail solicitation.

If a mail order trader fails, readers are advised to lodge a claim with the Advertisement Manager of this magazine within 3 months of the appearance of the advertisement.

For the purpose of this scheme mail order advertising is defined as:

"Direct response advertisements, display or postal bargains where cash has to be sent in advance of goods being delivered."

Classified and catalogue mail order advertising are excluded.

ENLARGER METER

By M. V. Hastings

Low cost indicator monitors light intensity

This simple enlarger exposure-meter can be built at comparatively low cost and, after initial checks for a particular box of paper, enables the correct exposure to be given without the need for test strips. The unit is actually a light level meter which, for the sake of cheapness, does not incorporate a meter movement. Instead, measurements are taken by adjusting a potentiometer for changeover of illumination in two light-emitting diodes and then reading the relative light intensity from a scale fitted to the potentiometer. The potentiometer is calibrated in arbitrary units from 0 to 100.

The instrument has a range of at least 5 stops. Power is obtained from an internal 9 volt PP3 battery, which should have an adequate life as current consumption is only of the order of 5 to 10mA (depending on the battery voltage itself). A facility for checking battery voltage is provided in the meter.

BASIC PRINCIPLE

The circuit is based on the comparator arrangement shown in Fig. 1. The non-inverting input of an operational amplifier couples to the potential divider consisting of the calibrated potentiometer, VR, and the photocell. The resistance of the photocell reduces as the light falling on it increases in intensity. The inverting input of the op-amp connects to the slider of the pre-set potentiometer, RA.

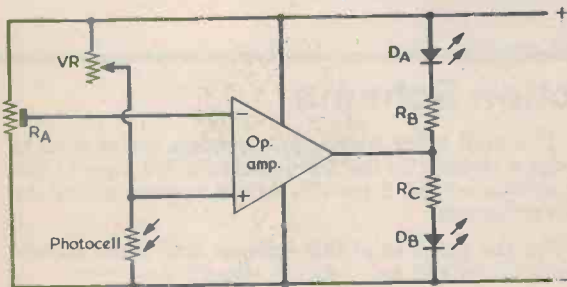


Fig. 1. Basically the meter functions as a comparator, VR being adjusted for equal input voltages to the operational amplifier. Light intensity in the photocell is then indicated by a scale fitted to VR

The output of the operational amplifier couples via RB to the l.e.d. DA and via RC to the second l.e.d., DB. If the voltage at the non-inverting input is negative of that at the inverting input, the op-amp output goes fully negative and diode DA lights up. When the non-inverting input is positive of the inverting input the output goes fully positive and diode DB becomes lit up.

When the photocell is illuminated at the maximum light level which will need to be measured, and with VR set to insert almost minimum resistance into circuit, RA can be adjusted so that the voltages at the two inputs of the operational amplifier are equal, as shown by the l.e.d.'s. If the light intensity falling on the photocell reduces the photocell resistance increases and it is necessary for VR to insert a higher resistance in order to bring the two op-amp inputs to the same voltage. The lower the light level on the photocell, the higher is the resistance which has to be inserted by VR to balance the circuit. As a result, measurements of light intensity can be obtained by first adjusting VR for equal voltages at the op-amp inputs and then reading off the intensity from the scale fitted to the potentiometer.

If the operational amplifier had a lower voltage gain it would be possible to adjust the potentiometer so that the output was at a voltage central between the positive and negative rails, with both l.e.d.'s alight at equal brightness. In practice, however, the op-amp has an extremely high gain level and it will be very difficult to adjust the potentiometer to give the precise resistance which results in an output at half-supply voltage level. As the potentiometer slider is adjusted to the balance setting it will reach a point where one l.e.d. abruptly extinguishes and the other lights up. The required balance setting is then that at which the l.e.d. changeover effect takes place.


WORKING CIRCUIT

The complete circuit appears in Fig. 2. This has some additional components, when compared with Fig. 1, to meet practical working requirements.

The main addition is a simple zener voltage stabilizing circuit, employing R3 and D1, which provides a regulated supply to the input networks for the op-amp. This is necessary because the photosensitive device which reacts to light intensity is a phototransistor, and this does not provide a true resistance as does, say, a cadmium sulphide cell because the current it passes does not vary greatly with changes in the applied voltage. However, its response to changes in light level is virtually instantaneous, whereas the decay time of a cadmium sulphide cell to reductions in light level can be as long as a few seconds, a factor which

RADIO AND ELECTRONICS CONSTRUCTOR

Fig. 2. The full circuit of the enlarger meter. The balance setting of VR1 is indicated by changeover of illumination in the two l.e.d.'s

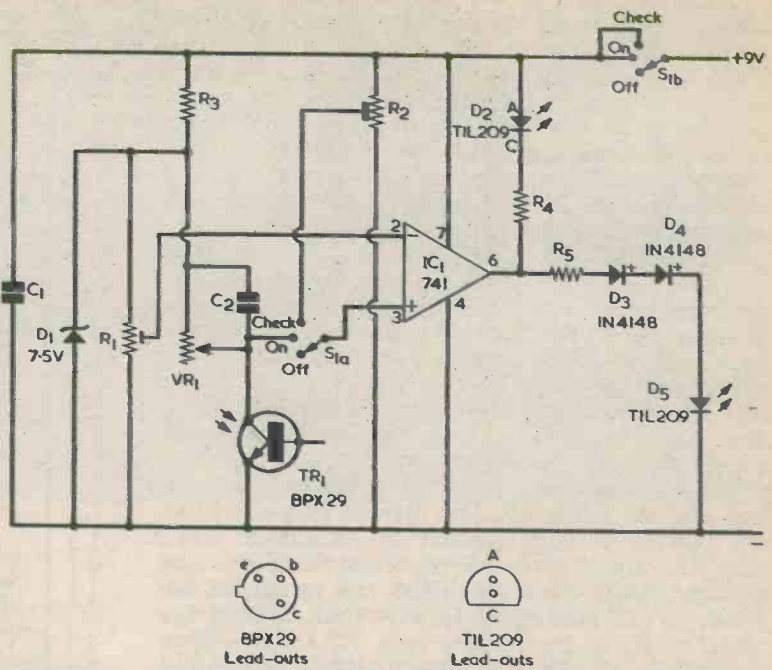

COMPONENTS

Resistors

(All fixed values $\frac{1}{2}$ watt 5%)

- R1 47k Ω pre-set potentiometer, 0.1 watt, horizontal
- R2 47k Ω pre-set potentiometer, 0.1 watt, horizontal
- R3 330 Ω
- R4 4.7k Ω
- R5 4.7k Ω
- VR1 2M Ω or 2.2M Ω potentiometer, log-

Capacitors

- C1 0.1 μ F type C280
- C2 0.1 μ F type C280

Switch

- S1(a)(b) 4-pole 3-way rotary (see text)

Semiconductors

- IC1 741 in 8-pin d.i.l.
- TR1 BPX29
- D1 BZY88C7V5
- D2 TIL209
- D3 1N4148
- D4 1N4148
- D5 TIL 209


Miscellaneous

- Plastic case (see text)
- 9-volt battery type PP3
- Battery connector
- 2 control knobs
- 2 l.e.d. panel-mounting bushes
- Wire, solder, etc.

would make an enlarger meter employing such a cell rather awkward to use.

No connection is made to the base of the phototransistor which functions purely by controlling the current which flows through its collector and emitter terminals.


If VR1 is adjusted to insert a fairly high resistance when the phototransistor has only a low level of illumination, the resulting high impedance at the non-inverting input of the op-amp could cause this input to be rather prone to stray pick-up of mains hum and similar electrical interference unless suitable precautions were taken. The noise, when amplified by the op-amp could cause both l.e.d.'s to be apparently switched on simultaneously, thereby masking the balance setting of the potentiometer. This trouble is overcome by adding the filter capacitor C2. The capacitor slows down the speed at which the circuit responds to changes in light intensity, but the delay is slight and is not significant.

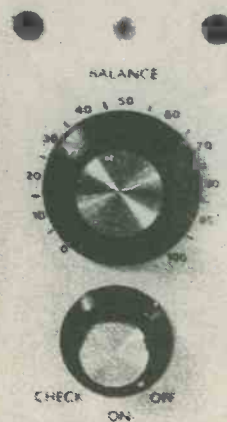

Front panel layout. The phototransistor is immediately above the balance control, with D2 to its left and D5 to its right

Two silicon diodes, D3 and D4, are connected in series with D5 and they are conductive when the output of the operational amplifier is positive. They are needed because the op-amp output voltage, when fully negative, is still about 2.5 volts positive of the negative rail. Approximately 1 volt is needed across the two diodes before they commence to pass forward current, and their presence ensures that D5 is fully extinguished when the op-amp output is negative.

Putting S1(a) to the "Check" position disconnects the non-inverting input from the phototransistor and VR1, and connects it instead to the slider of R2. This potentiometer is adjusted such that, when the battery voltage is at its lowest acceptable level, the voltages at the inverting and non-inverting inputs are equal and the circuit is at the l.e.d. changeover point. For battery voltages higher than the minimum level the non-inverting input of the op-amp is positive of the inverting input and D5 lights up. The reverse happens when the battery voltage is below the minimum level, and D2 then becomes illuminated. Since the voltage across R1 is stabilized, the voltage at the slider of R2 falls more rapidly than that at the slider of R1 as the battery ages. R2 slider will be negative of R1 slider if battery voltage should fall

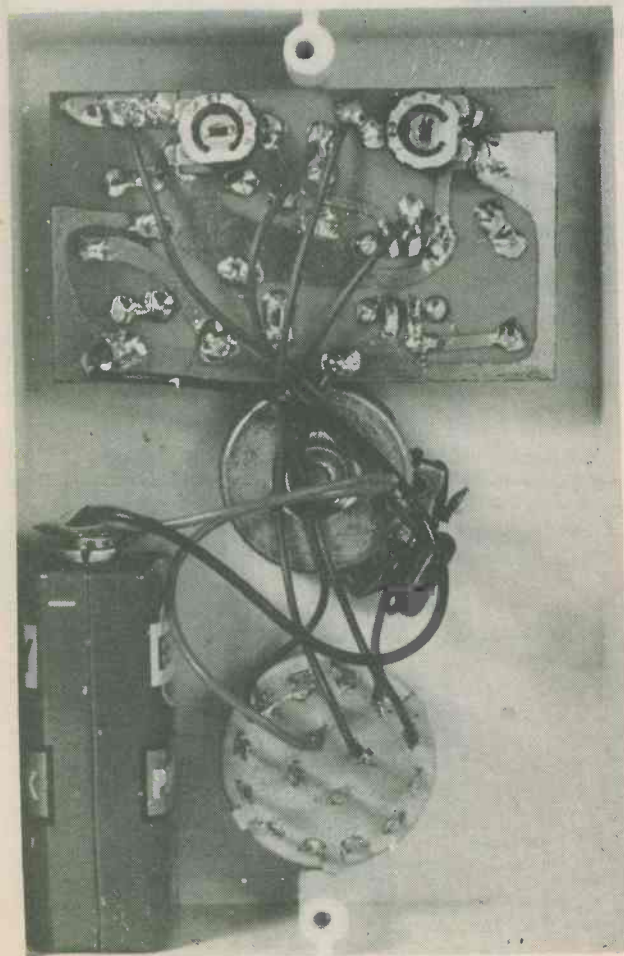

Assembly inside the enlarger meter case. R1 and R2 are mounted on the copper side of the printed board

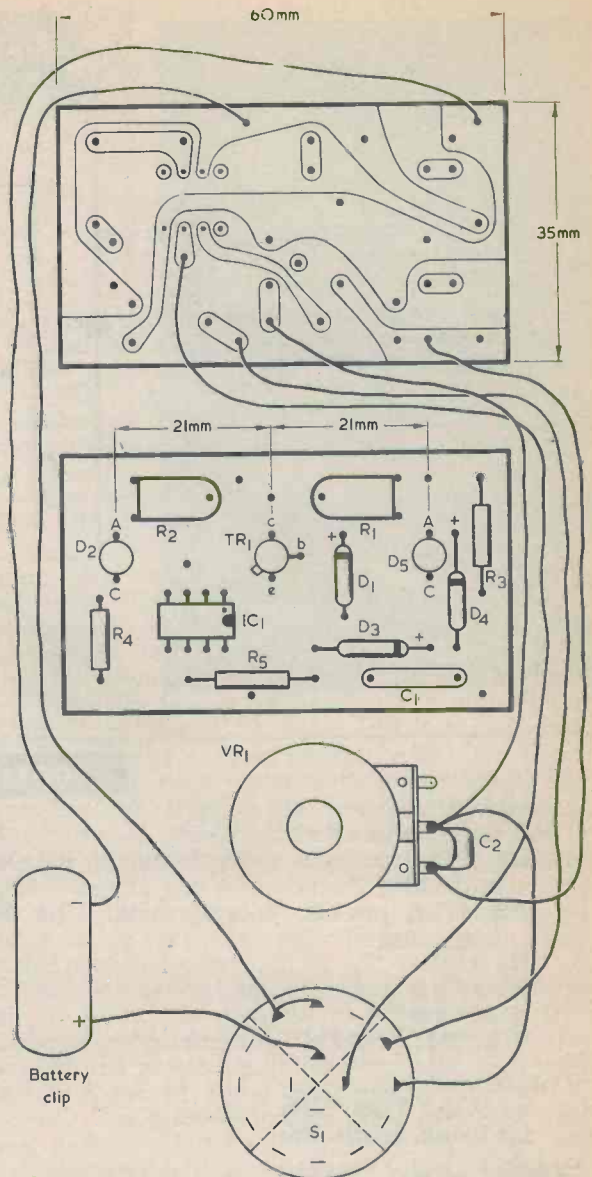


Fig. 3. The enlarger meter wiring. The printed board is reproduced full size for tracing. Note that R1 and R2 are mounted, in practice, on the copper side of the board. For reasons of clarity they are shown here on the component side


to the 7.5 volt stabilizing level provided by D1, and will continue to be negative for still lower battery voltages. R2 is, of course, set up after R1 has been adjusted to its final setting.

On-off switching is provided by S1(b), and C1 is the supply bypass capacitor. The BPX29 phototransistor is available from Brian J. Reed.

CONSTRUCTION

An inexpensive plastic box having approximate outside dimensions of 114 by 76 by 38mm. is used for the prototype, this being a box type PB1, as retailed by Maplin Electronic Supplies. Any similar plastic case capable of housing the components would also be suitable. As can be seen from the photograph of the front panel, VR1 is mounted centrally with S1(a) (b) below it. D2 and

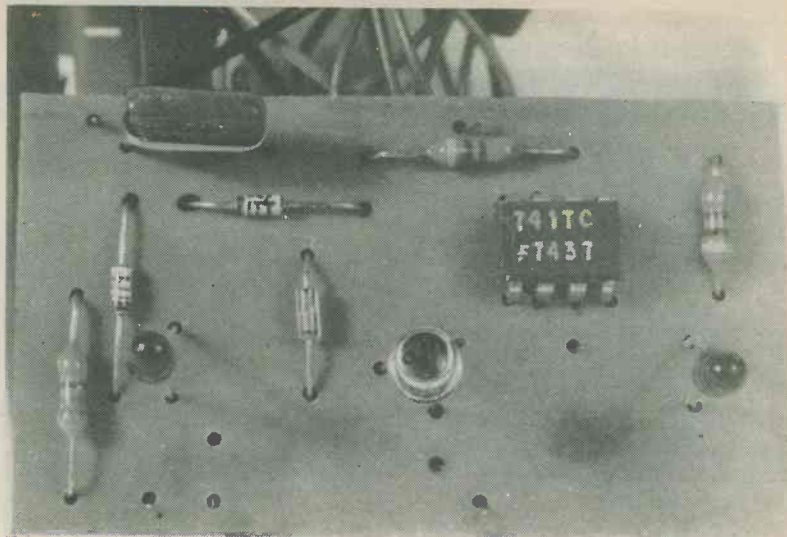The component side of the printed circuit board



D5 appear at the upper end of the panel, with TR1 between them.

TR1 has a standard TO18 encapsulation except for the transparent top which allows light to reach the internal semiconductor material. It requires a 5mm. (0.2in.) diameter hole in the panel. The holes for the two l.e.d.'s should have a diameter which accepts the l.e.d. panel-mounting bushes.

The printed circuit board is reproduced full size in Fig. 3, which also shows the other wiring in the meter. It is important to note that, for clarity, R1 and R2 are shown as being on the component side of the board. In practice, they are mounted on the copper side of the board as, otherwise, it would be impossible to adjust them after the board has been fitted in the case. External connections are also made to the copper side of the board.

After the board has been assembled, the l.e.d. centres should be 21mm. on either side of the centre of the phototransistor. The l.e.d.'s and the phototransistor then pass through appropriately positioned holes in the front panel of the case, the board being positioned right at the top of the case with R1 and R2 uppermost. It will probably be found easiest to assemble the board and then mark off the front panel holes with its aid before drilling these holes. The board is light and is quite securely held in place by the panel-mounting bushes of the l.e.d.'s. The holes for VR1 and S1(a) (b) should be drilled after the mounting arrangements for the printed board have been settled. The hole for VR1 should be positioned so that the potentiometer body is just slightly clear of the lower edge of the printed board when the latter is mounted in position. There is plenty of room below the potentiometer for S1(a) (b), and this should preferably be positioned with its body fairly close to the bottom of the case. Note, incidentally, that this component is a 4-pole 3-way switch with no connections made to two of its poles. Before wiring up to the switch, confirm with a continuity tester the outer tags which correspond to the inner tags. With some switches the tag positioning may differ from that shown in Fig. 3.

VR1 must be a potentiometer with a log and not a linear track and the positive stabilized voltage must be connected to the correct end of the track, as illustrated in Fig. 3. Otherwise only a very

restricted part of the scale will be available, making the meter difficult to use satisfactorily. C2 is mounted on the tags of VR1 and not on the printed board.

When the printed board assembly has been completed and finally fitted in the case, VR1 and S1(a)(b) may be mounted and the wiring from these components and the negative battery clip to the board completed. As already mentioned, the associated wires are soldered to the copper side of the board. The PP3 battery is placed to one side of S1(a)(b) and may be held in position by a home-made aluminium clamp. Alternatively, it can be secured by simply placing a piece of plastic foam between its rear edge and the inside surface of the case lid.

CALIBRATION AND USE

In use the meter monitors the light intensity of the enlarger by being placed on the enlarger baseboard with the phototransistor directed towards the enlarger lens.

It is first necessary to adjust R1 so that VR1 covers the required sensitivity range. Put a negative of average density in the enlarger and adjust it for a medium size print (8 to 10in. long). Place a diffuser, which should have a degree of translucency similar to greaseproof paper, under the enlarger lens and set the lens to minimum aperture. Find a setting for R1 which enables VR1 to balance the meter (i.e. reach the l.e.d. changeover point) when it is close to the anti-clockwise end of its range.

Open up the lens one stop at a time and note the new balance settings of VR1. These should be well spread out, although they will not form a linear scale. If cramping of the balance points occurs at one end of the scale, by experimentally setting R1 to either side of its present setting it should be possible to obtain a more equal spacing.

This exercise is merely to ensure that the potentiometer has the required range for measuring the light intensity of the enlarger. Its scale is not marked up with the balance points just found, but is given instead a purely arbitrary linear numbered scale. With the prototype this was from 0 to 100, using numbers taken from "Panel-Signs" Set No. 4 (available from the publishers of this magazine).

ELECTRONIC CONSTRUCTORS

SAVE MONEY!

With our BARGAIN PARCEL...

Contains:
10 x BC107, 10 x BC109, 10 x BC109, 3 x BFY51, 3 x 2N3819, 3 x 2N2926 and 10 Mixed Values - ELECTROLYTICS: 10 Mixed Values - CERAMIC CAPS: 20 Mixed Values - FIXED CAPS: 10 DIODES GERMANIUM - Sim. OA91; 10 DIODES SILICON - Sim. IN914; 2 x 741 IC's. 1 2gmm PHIAL CYANOACRYLATE ADHESIVE. VAT inc. in price (all items are brand new).

Plus a Free Gift worth 75p

Send £5 plus 50p p&p

(Cheque, Postal Order, Money Order) to

SIGTRONIC ELECTRONICS

27 Malvern Street, Stapenhill
Burton-on-Trent, Staffs. DE15 9DY
Tel: (0283) 46868 special orders

MORSE IMPROVEMENT

C90 Cassettes (A) 1-12 w.p.m. with simple exercises. Suitable for R.A.E. preparation. (B) 12-24 w.p.m. computer produced professional level operator material including international symbols.

Price each: complete with instruction and exercise booklets £4.50 including postage.

Morse Key and Buzzer Unit suitable for sending practice and DIY tape preparation.

Price £4.50 including postage.

Overseas Airmail £1 extra.

MHEL ELECTRONICS (Dept. R)

12 Longshore Way, Milton,
Portsmouth (UK), PO4 8LS

GAREX

V.H.F. Receivers New SR-9 for 2-metres F.M., fully tunable 144-146MHz, improved 2-speed slow-motion dial, also 11 xtal controlled channels. Compact, sensitive, ideal for fixed or mobile listening. Built-in L.S., 12v D.C. operation. INTRODUCTORY PRICE ONLY £54 inc. VAT. Crystals, if required: £2.50 each. All popular 2m. channels in stock. Marine band version (156-162MHz) £59.40 (xtals £2.79). Credit terms available, s.a.e. details.

Amplified Mobile Extension Speaker boosts audio from small receivers. Single compact unit, 12vDC operation, built-in 6W amplifier, with leads and jack plugs. £11.25 Neons min. wire end. 55p/10; £4/100

Slide Switches min DPDT 18p ea; 5+ : 14p

Resistor Kits E12 series, 22 Ω to 1M Ω

57 values, 5% carbon film, $\frac{1}{4}W$ or $\frac{1}{2}W$

Starter pack, 5 each value (285) £2.95

Mixed pack, 5 each $\frac{1}{4}W$ + $\frac{1}{2}W$ (570) £5.40

Standard pack, 10 each (570) £5.40

Giant pack, 25 each (1,425) £13.25

I.C.'s (new) 7410 25p CD4001AE 25p

SN76660 75p NE555 55p 723(T05) 75p

709 (T05), 741 (DIL-8) Op.amps 30p;

BNC Cable mtg socket 50 Ω 20p;

5+ : 15p PL259 UHF Plug & Reducer 68p;

5+ : 60p; SO239 UHF Socket panel mtd.

55p; 5+ : 45p Nicad rechargeables physically equiv. to zinc-carbon types: AAA

(U16) £1.64; AA(U7) £1.20, C(U11) £3.15;

D(U2) £4.94; PP3 £5.20 Any 5+ : less

10%, Any 10+ less 20%.

We stock amateur V.H.F. equipment and mobile aerials, s.a.e. details.

Distributors for J. H. Associates Ltd.

(switches and lamps)

PRICES INCLUDE UK POST, PACKING & VAT


Mail order only Sole Address:

GAREX ELECTRONICS

7 NORVIC ROAD, MARSWORTH.

TRING, HERTS HP23 4LS

Cheddington (STD 0296) 668684

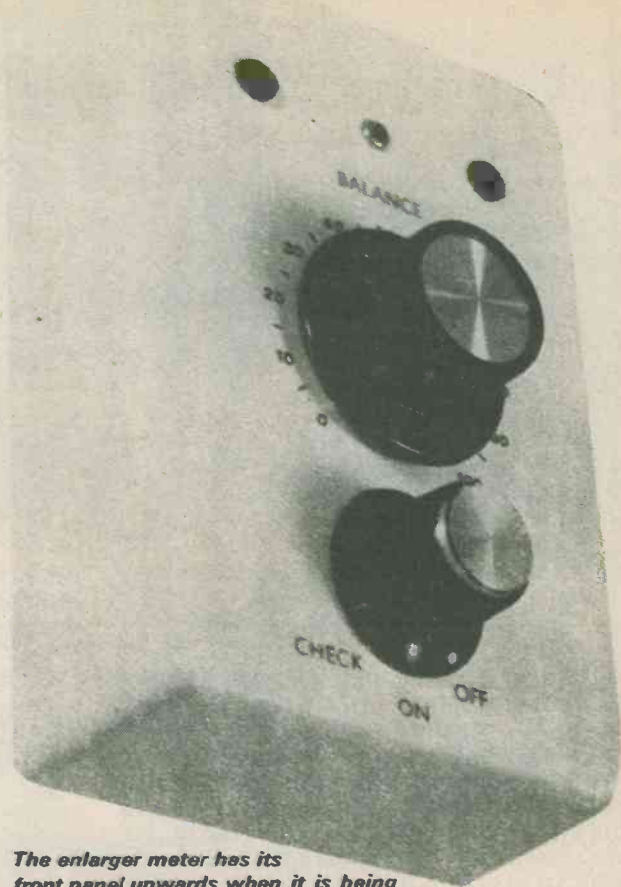

The enlarger meter has its front panel upwards when it is being used to assess enlarger light intensity

To find the scale setting for a particular box of paper, first find by test strips the exposure time and aperture required to give a good print from an average negative. With the negative and diffuser in place and the enlarger set to this aperture, place the meter on the baseboard and find the balance setting. Write the corresponding scale number and exposure time on the box for future reference.

In order to find the exposure required for new negatives the meter is put to this setting with the negative and diffuser in position, and the enlarger lens aperture is adjusted to balance the enlarger meter. The exposure time is not altered.

It is possible to use the meter as a spot meter, reading either a highlight or shadow tone as preferred, or as an integrating meter employing a diffuser under the enlarging lens whilst metering. These different methods of use will require different scale settings for any one box of paper. Therefore the scale setting must be determined using the method of metering to be employed to determine the exposure for new negatives.

The final adjustment is to set R2 so that i.e.d. changeover occurs with a supply potential just slightly below 8 volts. Ideally, a variable voltage power supply should be used to provide this voltage, but alternatively it may be given by a partly exhausted battery monitored by a testmeter set to an appropriate volts range. R2 is then adjusted to the i.e.d. changeover point. At battery voltages above the minimum level D5 will then turn on, whilst at lower voltages D2 will be lit up.

In your work-shop



VALVE HI-FI AMPLIFIERS

Class A Output Stages

With a sigh of relief Smithy switched off the music centre on his bench and closed its transparent lid. It had suffered from that most aggravating of all faults: an intermittent. Unexpectedly, the right hand channel would suddenly disappear on occasion, to reappear just as mysteriously several minutes later. It had taken the combined efforts of Smithy and his assistant Dick to finally run the fault, almost literally, down to earth. After determining that no voltage changes occurred anywhere when the fault was present they had embarked on a tiresome and time-consuming procedure of gently flexing the printed boards and tapping possible components until the trouble was finally located. It consisted of an occasional short-circuit between the centre conductor and the braiding of a screened lead connecting to the volume control.

"That," remarked Dick, as he commenced to carry the two speakers over to the "Repaired" rack, "represents at least two hours gone up the chute. And all for a lousy short!"

"I know," repeated Smithy dolefully, "but at least we did replace *something*, even if it was only a bit of screened wire. Sometimes you can spend ages on an intermittent, and you cure it in the end simply by resoldering a dry joint. It's a good thing that nearly everything we handle these days is solid-state. We used to get a lot more intermittents in the old valve days."

VALVE AMPLIFIERS

"Why was that?" asked Dick, as he returned for the music centre itself.

"Simply because valve equipment ran much warmer than semiconductor equipment does. The result was that all the components and wiring used to get good and hot when the equipment was switched on and would then cool down again after it was turned off. The resulting expansions and contractions all over the place meant that any connection which was liable to go intermittent was firmly encouraged to do so. I shudder to think what would have happened if they'd tried to make music centres like the one we've just fixed with valves!"

"I don't know about music centres," said Dick, returning to his stool and perching himself on it, "but the keener hi-fi buffs seem to be getting all het up these days about valves. I picked up a couple of audio mags recently and they both had articles about amplifiers with valve output stages."

Smithy pricked up his ears.

"I've noticed that preoccupation with valves, too," he remarked. "Whats more, I've seen ads for power output valves which are directed entirely at the hi-fi market. I find it an extremely interesting trend."

"What advantages," asked Dick, "do valves have over transistors?"

Smithy stroked his chin ruminatively.

"Well," he said slowly, "there are two obvious advantages which are

given by valves when they are used in the output stage of an audio amplifier. The first of these is that if a transistor output stage overloads it produces quite unpleasant distortion. This is simply the effect of clipping and it causes a sine wave to become partly changed to a square wave. When, on the other hand, a valve output stage is overloaded you don't go into an abrupt clipping process. You still get distortion, of course, but it comes on more gently and it doesn't sound so harsh. The second possible advantage with a valve output stage is a matter of fundamental design. A hi-fi valve output stage is run in Class A or Class AB whilst the semiconductor output stage is kept close to Class B. It's impossible to get crossover distortion with the valve output stage, but it's quite feasible, with a poorish design, to get it in the transistor output stage."

"But surely," protested Dick, "the better hi-fi designers would have got rid of transistor crossover distortion effects years ago."

"You're probably right there," admitted Smithy carelessly. "Anyway, another thing in favour of valve output stages is that they're fundamentally very simple in operation. What seems to be happening at the moment on the hi-fi scene is that there's a growing body of opinion which says that the performance of an audio amplifier cannot be judged entirely by laboratory tests, and that it should also be judged by subjective listening tests. You may then find that some hi-fi listeners will

state that they prefer a valve amplifier to a transistor amplifier having an identical laboratory specification just because the sound from the valve amplifier is 'rounder' or has a higher level of 'musicality'."

VALVE BIASING

"Blimey," snorted Dick, "that's pretty vague, isn't it? What do *you* think about it?"

"To be quite honest," replied Smithy, cautiously, "I haven't got a very firm opinion either for or against the value of subjective amplifier tests. I think that the best way to look upon a hi-fi installation is to say that it is a musical instrument in its own right. It is obviously impossible for a hi-fi system to exactly reproduce, say, a symphony orchestra spread over a large stage because all the hi-fi loudspeakers can do is reproduce composite signals made up from the sound-creating instruments in the orchestra. This doesn't, of course, prevent a hi-fi outfit from producing quite superb music. As there are no end of electronic, electrical and often mechanical links between the original orchestra and its loudspeaker reproduction, it would seem reasonable to judge the loudspeaker copy of the original sound by subjective checks as well as by electronic measurements. The argument is that since the hi-fi amplifier is one of the links in the chain then it should be given subjective listening tests."

"It's funny," said Dick, "why there's such a lot of controversy at present amongst hi-fi people."

Smithy chuckled.

"My dear Dick," he grinned, "there has *always* been controversy amongst hi-fi people! Even in the old days before the word 'hi-fi' started to be used there were still arguments raging about audio reproducing equipment."

Dick absorbed this information.

"Let's go back to valve output stages," he said after a moment. "I have to admit that I'm not entirely clear about this Class A and Class B business."

"All right," said Smithy equably. "Since there is an increasing interest at present in hi-fi output stages, it will do no harm at all to go into the old basics under which these stages operate."

He reached over and pulled his note-pad across the bench towards him. Picking up a pencil he quickly traced out a valve curve. (Fig.1(a).)

"Now here," he continued, "is a curve showing valve anode current plotted against grid voltage. To use

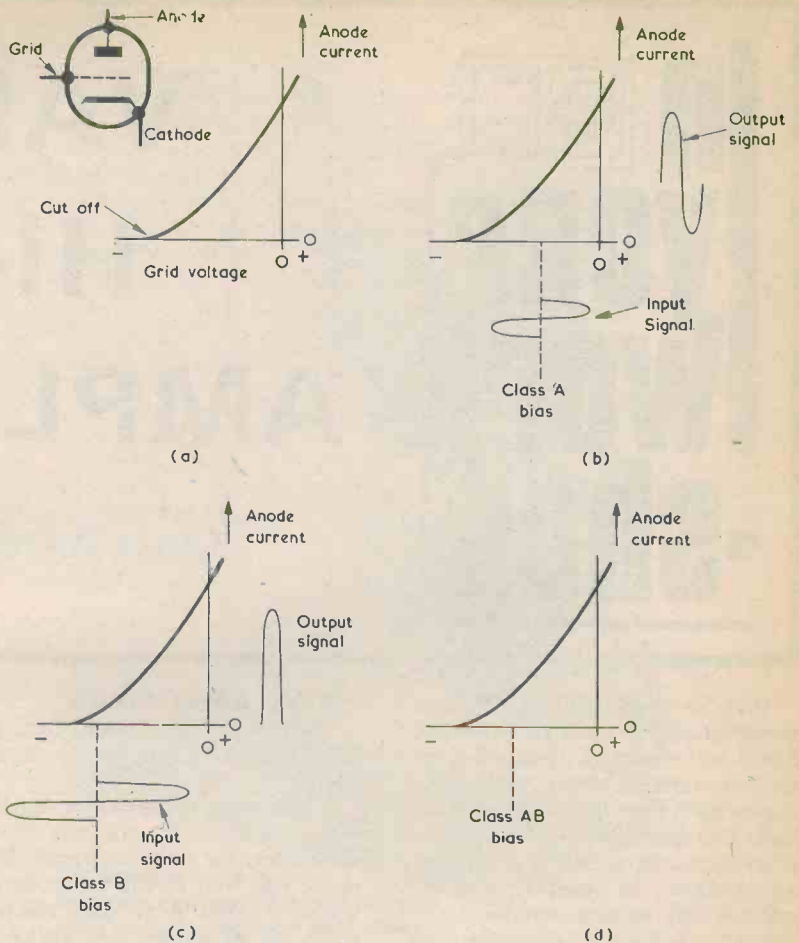


Fig. 1(a). An anode current-grid voltage curve for a valve
 (b). With Class A operation the grid bias is approximately at the centre of the linear section of the curve
 (c). The Class B bias point is at or very close to the cut-off point
 (d). Class AB bias is roughly mid-way between Class A and Class B

the proper terms we say that it is an Ia-Vg curve. The grid voltage is relative to cathode potential and I hardly need to tell you that anode current decreases as the grid goes more negative. The grid normally has a fixed bias which keeps it negative of the cathode and things are usually arranged such that the positive signal input half-cycle peaks do not take it positive of the cathode, although in some circuit designs this can happen. When the grid goes positive of the cathode it acts like the anode of a diode and a current flows just as it would in a diode. Now, here's the bias condition for Class A."

Smithy added a broken line, together with an input and output waveform. (Fig.1(b).)

"That bias," remarked Dick, "is just about mid-way between zero grid volts and the cut-off point."

"That's right," concurred Smithy.

"The input voltage waveform will normally not extend beyond the zero grid voltage or the cut-off voltage points, whereupon the resulting anode current waveform is a fairly undistorted version of the grid voltage waveform. I'll do Class B next."

Smithy rubbed out the waveforms on his sketch and added new ones. (Fig.1(c).)

"This time," he remarked, "the bias point is very near to cut-off. Nearly all the anode current waveform is then that which results from positive half-cycles at the grid."

"Gosh," remarked Dick. "That anode waveform is really distorted. What's this Class AB business you mentioned just now?"

"That's a bias setting which is roughly mid-way between Class A and Class B," stated Smithy. "Like this."

He busied himself again with his eraser and pencil. (Fig.1(d).)

"How," queried Dick, "does the valve work when it's in Class AB?"

"It gives Class A amplification for small signals," replied Smithy; "and a mixture of Class A and Class B amplification for strong signals. Just for the sake of completeness I should add that, with valves, Class AB operation can be subdivided into Class AB1 and Class AB2. Class AB1 is Class AB working in which grid current doesn't flow on positive half-cycle input peaks. Class AB2 is given when grid current *is* allowed to flow. A high power valve amplifier could use Class AB2, but it wouldn't be used in a high fidelity amplifier. Fair enough?"

PUSH-PULL OUTPUT

"I think so," said Dick doubtfully, "but nothing you've told me up to now has convinced me that valves can be better than transistors in an audio amplifier output stage."

"That's because you haven't got the complete picture yet," said Smithy. "Now, one disadvantage with valves of the type which are used in audio amplifier output stages is that they can only work with anode load impedances of the order of 2 to 8k Ω , depending upon the particular valve used. So they've got to have a step-down iron-cored transformer to match the anode to the speaker. Transistor output stages don't have this snag because they can work directly into the low impedance of the speaker. Also, for true high fidelity output, the valve

output transformer has to be carefully designed to give a very tight coupling between its primary and secondary at all audio frequencies and, preferably, for a fairly wide range of frequencies above the audio spectrum as well. Because of all this, a good hi-fi valve output transformer is a pretty heavy and hefty bit of work, and is correspondingly expensive."

"What you're saying," complained Dick, "seems to be aimed *against* valve output stages rather than towards them."

Smithy held up a finger.

"Ah," he remarked brightly, "but, having accepted the necessity for a valve output transformer we can next make a virtue out of that necessity by using it in a delightfully simple push-pull output stage. Like this."

Once again, Smithy's pencil moved busily across his note-pad, as he traced out the push-pull circuit. (Fig.2.)

"What's the first valve in this circuit of yours?" asked Dick, pointing to the triode at the left of Smithy's sketch.

"It's a phase-splitter," explained Smithy. "The input signal is applied to its grid and when this goes positive the triode passes increased anode and cathode current. The result is that its anode goes negative and its cathode goes positive. The opposite happens when the signal at its grid goes negative, and the overall effect is that the signals passed to the grids of the two output valves are in anti-

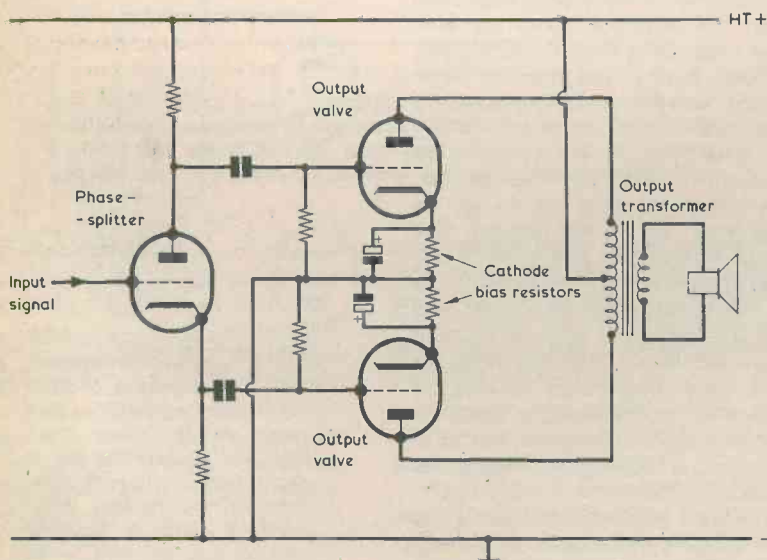


Fig. 2. A standard Class A or Class AB valve output stage. The valves are shown as triodes for simplicity, but in practice they would usually be tetrodes or pentodes

THE MODERN BOOK CO.

*Largest selection of English &
American radio and technical
books in the country*

**19-21 PRAED STREET
LONDON W2 1NP
Tel: 01-723 4185/2926**

PEATS for PARTS
ELECTRONIC COMPONENTS
RADIO & TELEVISION
*For the convenience of Irish
enthusiasts we supply:*

**Radio & Electronics
Constructor Data Books
Panel Signs
Transfers**

Also a postal service

PEATS
the world of electronics
25 Parnell Street, Dublin 1. Telephone 749972

MORSE MADE EASY



BY THE G3HSC RHYTHM METHOD!

These courses, which have been sold for over 23 years, have been proved many times to be the fastest method of learning Morse. You start right away by learning the sounds of the various letters, numbers, etc., as you will in fact use them. Not a series of dots and dashes which later you will have to translate into letters and words.

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it. It's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

The Complete Course consists of three records as well as instruction books.

For Complete Course send £5.00 plus part postage 50p (overseas surface mail £1 extra).

Now available Shrouded Morse Keys
£2.70 inc. UK postage

THE G3HSC MORSE CENTRE
Box 8, 45 Green Lane, Purley, Surrey.
I enclose £5.50 or s.a.e. for explanatory booklet.

Name

Address

phase. There are, incidentally, quite a few alternative phase-splitter circuits employing valves, but the one I've shown here is the easiest to understand. The anode and cathode load resistors for the phase-splitter have equal values, so that the out of phase signals passed to the output valve grids are equal in amplitude."

"The two output anode signals will also be out of phase, won't they?"

"They will," confirmed Smithy, "and the anodes are applied to the opposite ends of the centre-tapped primary of the output transformer. The output valves are biased by way of the resistors between their cathodes and chassis. These resistors drop a small voltage which makes each cathode positive of the grid, which is the same, of course, as biasing the grid negative of the cathode. This form of biasing is all right for Class A or Class AB operation, but it couldn't be used for Class B operation. With Class B operation the cathodes would connect direct to chassis and the grids would be biased negative by a specially produced fixed voltage."

"Could you use Class B with that push-pull circuit?"

"Oh yes," said Smithy. "One of the output valves then handles the positive-going signal half-cycles going to the phase-splitter grid and the other handles the negative half-cycles going to that grid. The two lots of anode half-cycles recombine in the output transformer and the complete signal then appears in the secondary for application to the speaker. The effect will be similar to a transistor output stage having an input driver transformer and an output speaker transformer, the only difference being that the driver transformer replaces the valve phase-splitter." (Fig.3.)

"Stap me," exclaimed Dick, "why, of course, the two circuits are the same! I should have seen it at once — I've handled enough transistor output stages in my time! what's the advantage of a valve Class B output stage, Smithy?"

"The same as it is with a transistor Class B output stage. You get maximum efficiency in terms of audio power output compared with the power supplied to the output stage. Also, there is minimum heat dissipation in the output valves. Even at maximum output power, each valve is only passing anode current for about half the time."

HI-FI OPERATION

"Would a Class B valve output stage be all right for a hi-fi

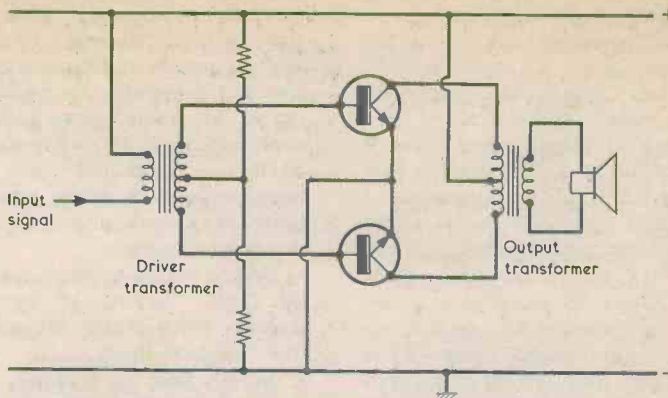


Fig. 3. A familiar Class B transistor output stage using transformers. The two resistors bias the transistors so that they pass a small quiescent current

amplifier?"

Smithy seemed almost shocked at the idea.

"Oh no", he replied. "Class B would be okay for a public address amplifier handling speech, but it would never do for a hi-fi valve amplifier. One reason is that you're liable to get crossover distortion, just as with a Class B transistor output stage, but the main reason is that Class A and Class AB valve operation offers specially good working conditions which are not given with Class B working. For a kick-off, let's suppose that the two output valves are nearly identical in characteristics and that they are biased in Class A. They will both draw a standing current from the positive h.t. supply, even in the absence of a signal. The combined anode current flows first from the h.t. positive rail to the output transformer primary centre-tap, and then the separate anode currents flow in opposite direction to the two anodes. Both valves draw the same anode current and the standing magnetic field produced by one half of the primary is exactly cancelled out by the standing magnetic field produced by the other half of the primary. The result is that the iron core of the transformer is not magnetised at all by the standing anode current, and the transformer is able to function more efficiently. The only time the core gets magnetised is when a signal comes along, and then the two anodes feed the outside ends of the primary with signals of opposite polarity." (Fig.4).

"I don't see how that gives any advantage over Class B operation," stated Dick, critically. "With Class B operation the standing anode current is quite small and the transformer is still called upon to

handle signal currents only."

Smithy threw a sharp glance at his assistant.

"That's a very good point," he remarked. "And you're quite right in what you say. With Class B working, though, you don't get the symmetry of operation that you get with Class A, where both output valves are handling the signal all the time. With Class A operation, too, non-linearity in one valve tends to be cancelled out by the similar non-linearity in the other, giving much less distortion than would be given if one valve were used in a single-ended output stage on its own. Indeed, when the valves are identical any even harmonics produced by them cancel out in the

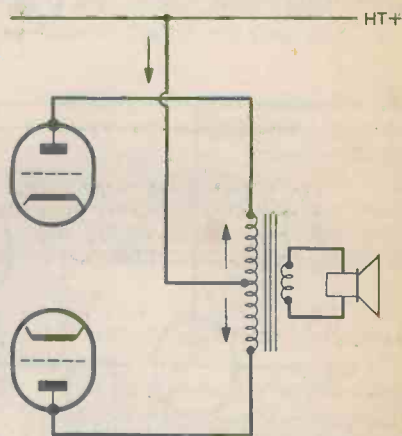


Fig. 4. In a class A or Class AB valve push-pull output stage, anode current flows from the h.t. positive rail to the output transformer primary centre-tap, after which it flows in opposite directions in the two halves of the primary. ("Conventional" current, flowing from positive to negative, is assumed here)

transformer primary. Unfortunately, the same cancellation effect is not given with odd harmonics."

"Are there any other cancellation effects?"

"There are two more. If there is any power supply ripple on the h.t. positive rail the ripple current flows through the two halves of the transformer primary in opposite directions, whereupon it cancels out in the primary. In the reverse direction there is a cancelling effect to the h.t. positive rail with the anode signal currents because the anode currents of the two output valves add up to what approaches a constant value even when they are handling a signal. This reduces power supply decoupling requirements."

put powers than triodes do. Unfortunately, they tend to give more distortion. And this is where a special circuit, which first saw the light of day in the early 1950's, comes into play. It's known as the 'ultra-linear' output circuit. Here it is."

Smithy picked up his pencil and drew a further circuit on his notepad. (Fig.5.)

"And that," he stated cheerfully, "is the last output stage circuit I'll draw for you today. The ultra-linear output stage uses tetrodes, and their screen-grids are connected to taps in the transformer primary which are roughly mid-way between the centre-tap and the outside ends, being slightly closer to the centre-tap than the ends. This very simple circuit alteration results

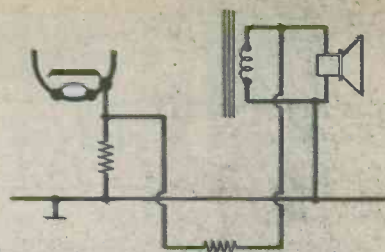


Fig. 6. A common method of obtaining negative feedback is to couple the output transformer secondary back to the cathode circuit of an early valve in the amplifier chain

variations on this theme." (Fig.6.)

"If valve hi-fi amplifiers are potentially so good," remarked Dick, "why did they become replaced by transistor hi-fi amplifiers?"

SNAGS WITH VALVES

"Because of the snags," said Smithy. "To start off with, there's that expensive output transformer which I've already mentioned. Then the output circuits are all in Class A, or in Class AB1 if a little more output power is required, which makes them very inefficient. For example, a 20 watt mono amplifier could require an h.t. supply of around 400 volts at 150mA, which means that there's 60 watts of h.t. power going in for 20 watts of audio coming out. The power consumed by the valve heaters could well add another 20 watts or so to the power input. So the mains transformer needed to power the amplifier will be pretty bulky and expensive, too. And we're only talking about a mono amplifier. The power supply requirements would be doubled if we wanted two amplifiers for a stereo system. Again, valves aren't like transistors because their characteristics vary with age. Add to all these points the fact that the valve amplifier is heavier and larger than its transistor equivalent and you can see why commercial production of hi-fi equipment had to change over to semiconductors. But it's nice to see that some of the true high fidelity enthusiasts are prepared to put up with all these difficulties with valves if they consider that the end result is a better sound. One thing is certain and that is that it will be well worthwhile keeping an eye on the future development of high fidelity valve amplifiers."

"They're certainly in a class of their own," agreed Dick. "Class A, in fact!"

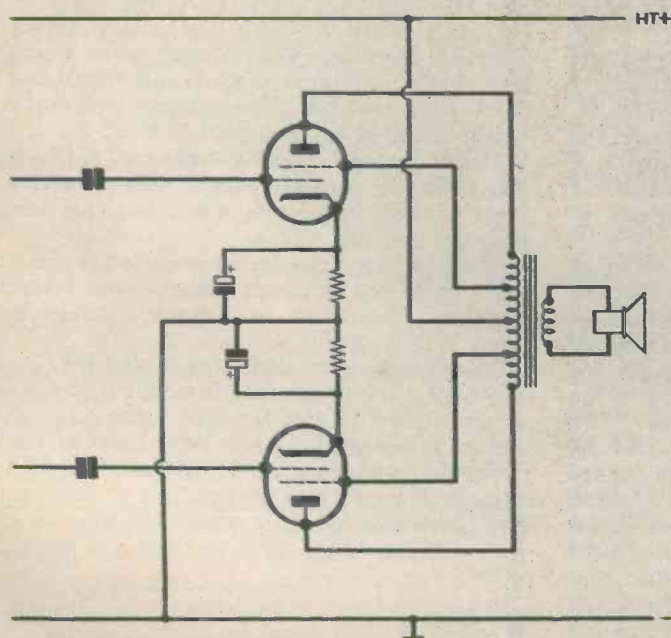


Fig. 5. The "ultra linear" output stage uses two tetrodes with their screen-grids connected to additional taps in the output transformer primary. The circuit has also been used with pentodes, the screen-grids of which are similarly connected to the transformer primary taps

ULTRA-LINEAR

"I'm beginning to see why these valve output stages are becoming more and more popular with hi-fi addicts," pronounced Dick. "They certainly have some features that you don't find with transistor output stages. You've shown triodes in your circuits up to now. Are these the only types of output valve which could be used?"

"I showed triodes purely for reasons of simplicity," replied Smithy. "In practice, the output circuits would use tetrodes or pentodes, which offer much higher out-

put powers than triodes do. Unfortunately, they tend to give more distortion. And this is where a special circuit, which first saw the light of day in the early 1950's, comes into play. It's known as the 'ultra-linear' output circuit. Here it is."

"I'll say," agreed Dick, looking at the circuit enthusiastically. "How about negative feedback?"

"That depends upon the amplifier design," said Smithy. "The standard approach here is to take feedback from the secondary of the output transformer and apply it to the cathode circuit of an early valve in the amplifier. But there can be many

SHORT WAVE NEWS

FOR DX LISTENERS



By Frank A. Baldwin

Times = GMT

Frequencies = kHz

● LAOTIAN QUEST

Signals from the Far East have been coming through quite well on the odd occasions over the past couple of months. Some of them — received at the tail end of the 'season' — are listed in this article, but the real search has been that for Laos on the LF bands. An account of that follows.

When deciding to 'listen out' for local or regional stations in any particular country, one must first collate the facts concerning such transmitters, secondly choose the most favourable time for reception here in the U.K., and then listen on a regular basis. The collated facts are listed below with the results achieved — or not achieved — mostly the latter!

Two stations in the Domestic Service open at 2230 (around the best time for reception of Laos here in the U.K. during the period October to February inclusive), these being Vientiane on 6130 and Udomsai on 6910. Both channels are hopeless, the former is in a broadcast band and the latter is covered by commercial QRM. The remainder open at 2300, these being Xieng Khouang on 4757 and 6675 (nothing but utility QRM although the former channel showed promise at times — but no Laos); Savannakhet on 7385 (surrounding QRM — no Laos); Pakse on 6600 (thought to be promising but military music and announcements in English, with time-check, at 2300 proved it was Moscow with the all-English programmed World Service — presumably an internal relay — it was using Russian some nights later); Luang Prabang on 4703 (no results after many attempts). Lastly there is Houa Phan on 4657 and 6198, the latter channel would be hopeless and was ignored but the former did produce very weak signals on two occasions in December when conditions were very good for reception of the area. At 2300 there were announcements, at 2305 YL with an Asian-type song, local-type music, the signal (such as it was) being lost under QRM at 2315. Was it Laos? I don't know, I didn't get any positive identification, so must list it as a tentative reception and try again.

● MEXICO

Radio Mexico on 15385 at 2315, OM with love song in Spanish, YL with announcements.

● SAUDI ARABIA

Riyadh on 11685 at 1855, OM with the Holy Qur'an Service (religious chants), scheduled here

from 1800 to 2100 (at the time of writing!). -

● NORTH KOREA

Radio Pyongyang on a measured 6401 at 1958, tuning signal repeated, identification in Korean and the National Anthem in the opening of the Korean Service to South Korea and Japan (in the External Service). This transmission is scheduled both here and on a logged and measured 6251 from 2000 to 1800. The former frequency is the better channel for listeners here in the U.K.

Radio Pyongyang on a measured 6338 at 1713, YL with the Arabic programme for Africa, the Near and Middle East, scheduled here from 1700 through to 1900.

Radio Pyongyang on a measured 6576 at 1720, OM with the French programme directed to Europe (discussion in French), scheduled here from 1700 to 1850.

Radio Pyongyang on a measured 9977 at 1536, YL with announcements in English in the English programme intended for Africa, the Near and Middle East, scheduled here from 1500 to 1650.

Radio Pyongyang on 11350 at 1532, OM with a song in Korean in a programme of local music in the Domestic Service, scheduled on this channel from 0400 to 0900, 1500 to 1800 and from 2000 to 0300.

● CHINA

Radio Peking on 11040 at 1410, YL with the Kazakh programme in the Domestic Minority Language Service, scheduled here from 1400 to 1455.

Radio Peking on 11455 at 1734, Chinese orchestral music in the Cantonese programme directed to S.E. Africa and S.E. Asia, scheduled here from 1700 to 1800.

Radio Peking on 9860 at 2310, OM with the Spanish programme to South America, scheduled from 2300 to 2400.

Radio Peking on 11980 at 2337, YL with the programme for Laos, scheduled here from 2330 to 2400.

Radio Peking on 7050 at 2232, YL and OM in Portuguese to Brazil, scheduled from 2200 to 2300.

Radio Peking on 17650 at 1143, YL in Thai to Thailand, the programme being scheduled here from 1130 to 1200.

PLA Fukien Front on 4380 at 1727, OM in Chinese with the programme for Taiwan in the Network 2 service, scheduled here from 0230 through to 1900.

CPBS Peking on **4460** at 2140, OM with a talk in Chinese in the Domestic Service 1 programme, scheduled here from 1103 to 1735 and from 2000 to 0020.

CPBS Peking on **7935** at 1423, Chinese opera in the Domestic Service 1 programme, scheduled from 1323 to 1735 and from 2000 to 2330.

CPBS Peking on **11000** at 2342, YL with programme for Tibet in the Domestic Minority Language Service, scheduled here from 2330 to 0025.

CPBS Peking on a measured **8007** at 2226, YL in Chinese in the Domestic Service 2 scheduled here from 0700 to 1600 and from 2100 to 2400.

● CHINA — REGIONALS

CPBS Lanzhou, Gansu, on **4865** at 1510, Chinese music, YL with a song, OM and YL announcers. The schedule is from 0320 to 0600, 1000 to 1600 and from 2120 to 0100 (Sunday to 0600).

CPBS Nanning, Kwangsi, on **4905** at 1517, OM in Chinese in a relay of Peking Domestic Service 1. The schedule is from 2000 to 2200 (from May to October from 2000 to 2300 and from 1100 to 1735).

CPBS Wuhan, Hupeh, on **3940** at 1534, YL and OM in a Chinese drama. The schedule is from 0850 to 1605, 2100 to 0100 and from 0300 to 0740.

S. KOREA

Seoul on **9870** at 1333, OM with a newscast in English followed by "News Highlights of the Past Week" in the English programme for Europe, scheduled from 1330 to 1400 on this channel.

● THAILAND

Radio Bangkok on a measured **4830.5** at 1549, OM's with a discussion in Thai. The schedule is from 2200 to 1600 and the power is 10kW but frequency can vary to **4833**.

● MONGOLIA

Ulan Bator on a measured **4763** at 2200, opening with the Mongolian National Anthem, OM and YL announcers in the Domestic Service 1st Programme, scheduled here from 1054 to 1500 and from 2200 to 0100. Also logged in parallel on **5055**.

● SAUDI ARABIA

Riyadh on **21505** at 1320, Arabic music in the Domestic Service scheduled here from 0730 to 1700.

● MADAGASCAR

Radio Nederland Relay on **21480** at 1402, OM with the Dutch programme to S.E. Asia, scheduled from 1330 to 1425.

● NEPAL

Radio Nepal, Khumaltar, on **3425** at 1518, local music (flute-like instrument and drum), YL with announcements at the end of the English programme "Thanks for listening and good night" followed by a trumpet fanfare. The schedule is from 0020 to 0350 (Sundays until 0450) and from 1150 to 1720. English programmes are radiated from 0220 to 0230 and from 1435 to 1520. The power is 100kW. Also logged in parallel on **5005**.

● INDIA

Radio Kashmir, Srinigar, on a measured **3277** at 1526, OM's with a discussion in vernacular in

the Domestic B Programme, scheduled from 0130 to 0200 and from 1130 to 1705. The power is 7.5kW.

AIR Lucknow on **3205** at 1528, YL with announcements in Hindi followed by the news in English at 1530. The schedule is from 0025 to 0215 and from 1140 to 1830, the power is 10kW.

AIR Bombay on **4840** at 1735, OM with local songs, Indian music in the Domestic B Programme, scheduled here from 0230 to 0400 and from 1230 to 1830, the power being 10kW.

AIR (All India Radio) Hyderabad on **4800** at 1740, OM with songs, local music in the Domestic A Programme, scheduled here from 1200 to 1830 with a power of 10kW.

AIR Delhi on **4860** at 1740, local songs and music in the Home Service, scheduled here from 0245 to 0400, 1030 to 1215, (Forces programme from 1235 to 1315), 1445 to 1830 with English newscasts at 1430 (Sunday), 1530, 1730 and at 1800.

AIR Hyderabad on **4800** at 1545, YL with a newscast in English followed by OM with a current affairs talk in English. The schedule is from 1200 to 1830 ('A' Programme Service) and the power is 10kW.

AIR Delhi on **3365** at 1550, OM with the news in English in the 'A' Programme, scheduled from 0025 to 0230 with a power of 10kW.

● VIETNAM

Hanoi on a measured **4944** at 1521, local music, OM with songs in Vietnamese in the Home Service 1, scheduled here from 2055 to 1630 (English programme from 2130 to 2145) but the frequency can vary up to **4950**.

Hanoi on **10040** at 1823, YL with the English programme to Europe, scheduled from 1800 to 1900.

● INDONESIA

RRI (Radio Republik Indonesia) Medan on a measured **4764** at 1502, OM in Indonesian (presumably a newscast). The schedule (a relay of Medan 1) is from 2300 to 2330 and from 0900 to 1700, the power being 50kW. The frequency of this one can vary from that shown to **4769**.

RRI Sorong on **4875** at 2120, Indonesian music, YL with songs, YL announcer. The schedule is from 2100 to 2330 and from 0800 to 1400 and the power is 10kW.

Yogyakarta on a measured **5046** at 1524, OM with a local newscast in Indonesian mentioning several place names "Vientiane" etc. The schedule is from 0100 to 0300, 0455 to 0800 and from 0955 to 1700. The power is 20kW.

● SARAWAK

Radio Malaysia, Kuching, on **4835** at 1550 typical local-style music, YL with songs. The schedule is from 2200 to 0130 and from 0830 to 1600, the power being 10kW.

● NOW HEAR THIS

RRI Tanjungkarang, Indonesia, on a measured **4002.5** at 1538, OM with announcements in Indonesian after a newscast (I presume) followed by a male chorus. Signal faded out by 1545. The schedule is from 2200 to 0130, 0455 to 0710 and from 0855 to 1600 and the power is 2.5kW.

VHF MAINS



TABLE RADIO Part 2 By R. A. Penfold

This concluding article completes constructional details and describes alignment.

In last month's article we discussed the circuit and components of this receiver, then dealt with initial constructional steps. We now continue with the remaining constructional details, concluding with the alignment of the trimmers, the i.f. transformer and the quadrature coil.

COMPONENT PANEL


Virtually all the components are mounted and wired up on the plain 0.1 in. matrix perforated board, which has 50 by 36 holes. Details are given in Fig. 4. The three mounting holes are drilled out 6BA clear. It is also necessary to slightly enlarge the holes which take the mounting lugs of IFT1 and L4, and these need to be about $\frac{1}{16}$ in. in diameter. IFT1 and L4 have pin spacing on a matrix of approximately 0.15 in., but they will fit into the 0.1 in. matrix board if they are mounted diagonally as shown in the diagram.

With this type of construction the components are fitted to the appropriate points on the board, and their lead-out wires or mounting lugs are bent flat against the board underside, being directly connected to each other as shown by the broken lines in Fig. 4. In the majority of cases the lead-out wires will be long enough for the connections to be made, but where necessary tinned copper wire of about 22 s.w.g. can be used to bridge any gaps. Tinned copper wire is also employed for the long


wiring run which is at chassis potential. Note that connection is made to both mounting lugs of IFT1 and to one of the mounting lugs of L4.

The centre tags of the ceramic filters are the common terminals and, since these devices are symmetrical, it does not matter which of the other tags is regarded as the input and which is regarded as the output. L1 and L3 are supplied with ferrite cores which are not required here and are removed. L2 consists of a short length of single strand insulated wire of around 22 s.w.g. One end of the wire is passed through the board and soldered at hole 18j in the board. It is then looped around the middle of L3 to form a single turn coupling coil and its free end, shortened as necessary, will be soldered to SK1 after the component board has been mounted in the case.

The completed board is secured to the base of the case with L1 and L3 to the rear, spacing washers about $\frac{3}{16}$ in. long being used to keep the underside wiring well clear of the metal case. Before the board is finally mounted, however, it must be connected, using multi-strand insulated hook-up wire, to the front panel components. T1, the mains lead, S1 and FS1 should also be connected into circuit at this stage. Fig. 5 shows the point-to-point wiring to VR1, S1 and VR2. Before connecting to S1 confirm with an ohmmeter the appropriate tags of this switch, as these may differ in positioning

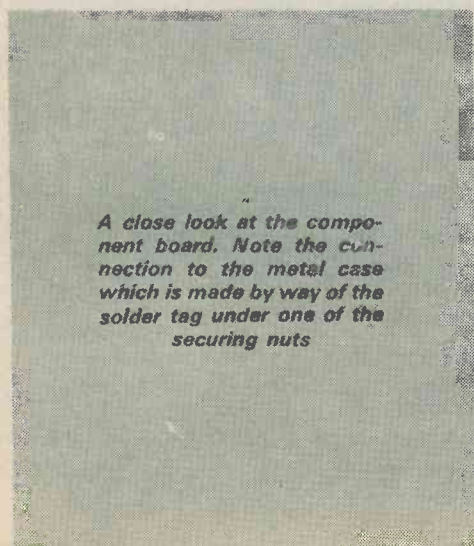

A close look at the component board. Note the connection to the metal case which is made by way of the solder tag under one of the securing nuts

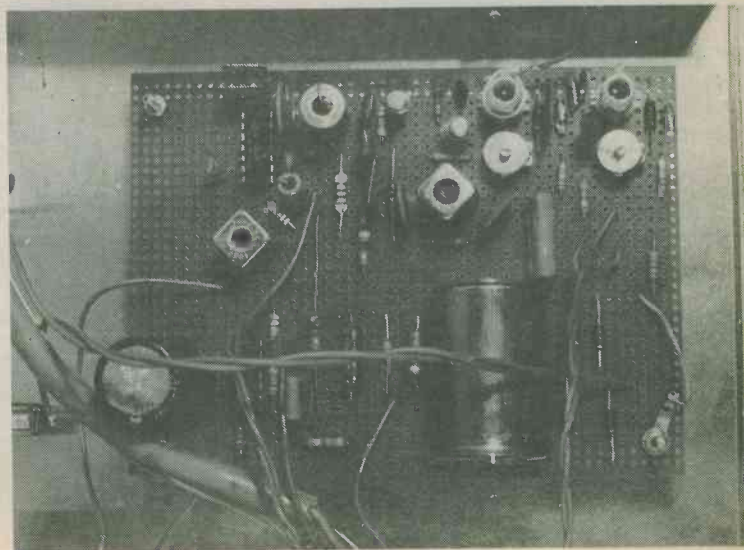


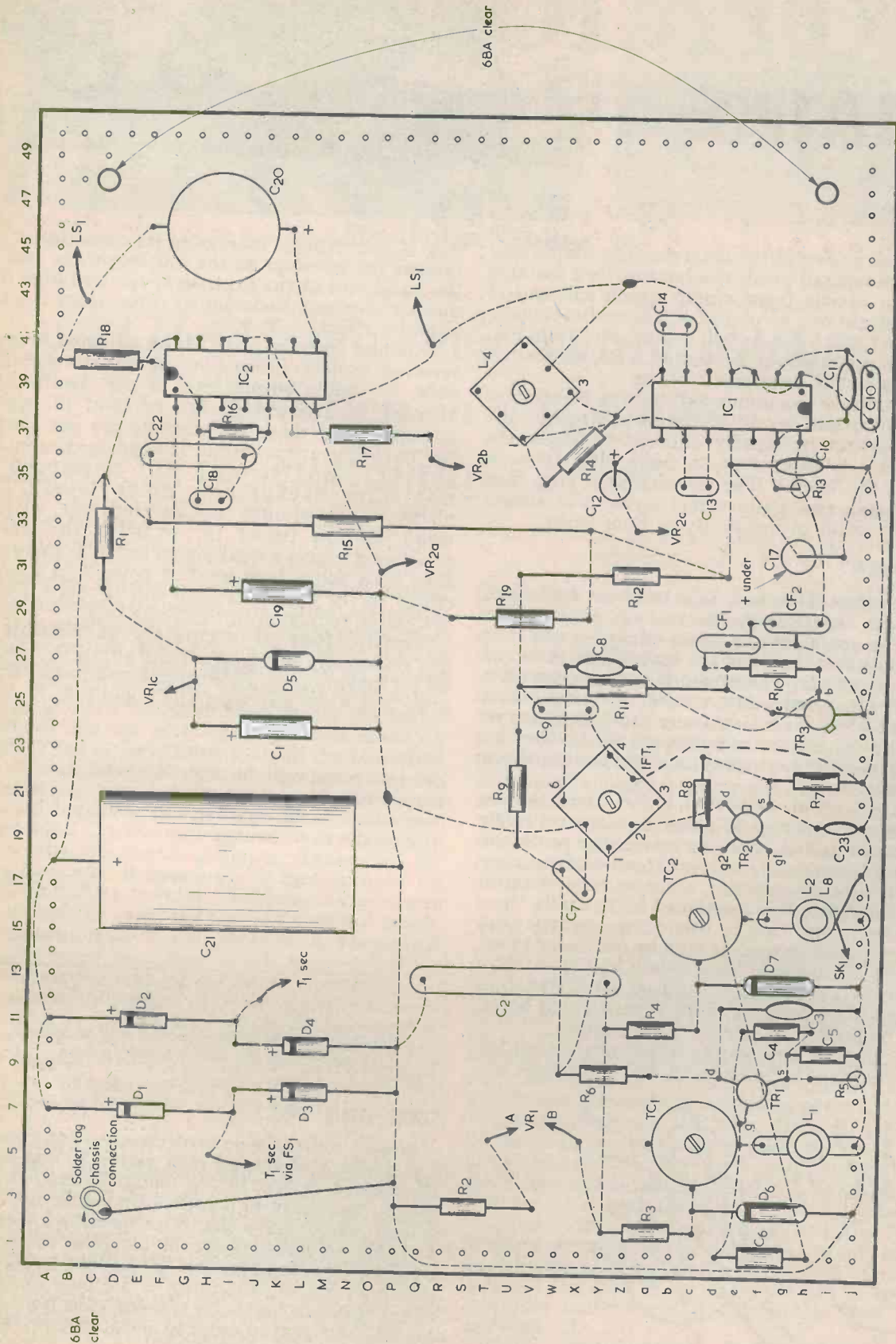


Fig. 4. Very nearly all the components are assembled on the plain perforated board shown here. Connections under the board are indicated by the broken lines

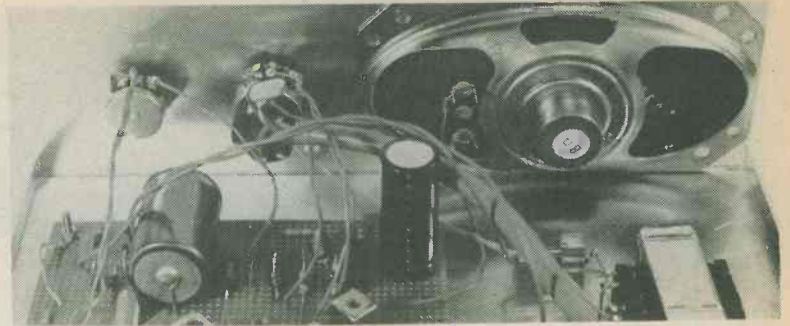A view from the rear. Capacitor C15 is not mounted on the component board and is soldered across the tags of the volume control



from those shown in the diagram. The mains lead should be secured inside the housing by a suitable plastic or plastic faced clamp which will ensure that no strain can be placed on the mains connections at S1 and VR2. As will be apparent from Fig. 5, C15 is mounted on the tags of VR2, and is not wired up on the component board.

It is strongly recommended that the component panel wiring and layout, the other wiring and the general layout be strictly adhered to unless the constructor is competent to make alterations or redesign the layout. The circuit has a very high level of gain and an incorrect layout will almost certainly result in instability or hum loops.

ALIGNMENT

First adjust TC1 and TC2 to about half their maximum capacitance. As yet, no adjustments should be made to the cores of IFT1 and L4. Remember that the lid of the case will be removed during alignment, whereupon it becomes possible to accidentally come into contact with the mains wiring at S1 and T1. Great care must be observed to ensure that the mains points are not touched by the fingers or by any metal tool, as a serious shock could then result.

With an aerial connected to SK1 and the set switched on it should be possible to receive a few stations but probably not very well. The prototype works well using just a couple of metres of ordinary hook-up wire as an aerial, and this type of aerial works best when it is positioned horizontally since very nearly all v.h.f. broadcast stations use horizontal polarisation. It may be necessary to experiment a little with the position and orientation of the aerial to obtain a really good aerial signal. In poor reception areas a more sophisticated aerial might be needed to provide good results.

TC1 is given any setting which enables all the desired stations to be received, and the precise set-

ting is not critical. Increasing its capacitance increases the coverage at the low frequency end of the band, but at the expense of reduced high frequency coverage. Reducing its capacitance has the opposite effect.

TC2 and the core of IFT1 are adjusted to peak received signals. Since f.m. signals are involved here, the audio output level is not significantly affected by changes in the r.f. and i.f. signal strengths, and these adjustments are not simply for maximum audio output. Instead, maximum r.f. and i.f. signal strength will correspond to minimum background noise level. The adjustments should be carried out with a weak station tuned in, or with the aerial positioned to give a weak signal input, as there will then be a fairly high level of noise, and any increase in the signal strength will produce a very noticeable reduction in this noise level.

Finally, tune as accurately as possible to any reasonably strong signal and adjust the core of L4 for maximum audio output. Use a proper trimming tool when adjusting IFT1 and L4.

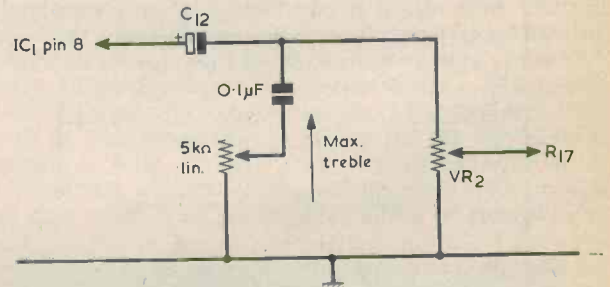


Fig. 6. If desired, a tone control may be added, employing the circuitry shown here

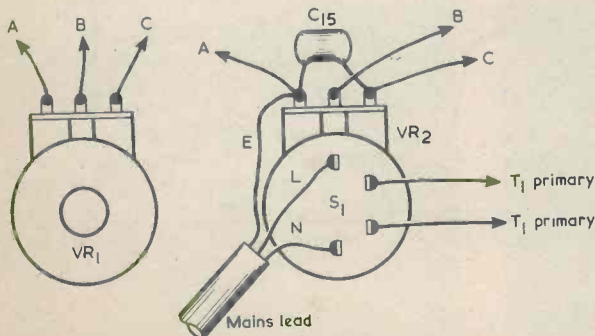


Fig. 5. The wiring behind the front panel to VR1, VR2 and S1

TONE CONTROL

Simple top-cut tone controls are often fitted to f.m. radios and it is an easy matter to add one to the present design, if this should be desired. It is merely necessary to decrease the value of C15 to $0.15\mu\text{F}$, and to add a $5\text{k}\Omega$ linear potentiometer and a $0.1\mu\text{F}$ polyester capacitor in series across the track of the volume control. The added circuitry is shown in Fig. 6. Of course, if the tone control is added it will be necessary to modify the front panel layout somewhat in order to accommodate the additional potentiometer.

(Concluded)

OPTO-ISOLATOR A.C. SWITCH

By John Baker

*TIL111 provides control voltage
isolation in a.c. mains
switching circuit*

When an electronic circuit is used to control mains powered equipment it is normal to employ either a relay or a triac as the switching device. A triac has certain advantages over a relay, such as ruggedness, high speed operation and no moving parts to wear out, with consequent almost unlimited life. On the other hand, it has the major drawback that one of its terminals (designated A1 or MT1) has to be common to both the controlled and the controlling circuit, which means that the controlling circuit has to be connected to the mains.

In some applications such a connection is at least undesirable and in others it can be quite definitely not permissible. As an example, thermostats for controlling the temperature of liquids used by photographers may have electronic temperature sensors and, to avoid the risk of dangerous shock, such sensors must be reliably earthed. They could not then be coupled directly to a triac controlling the heating element for the liquid concerned.

One possible method of isolating electronic control and triac circuits is to couple the two together by way of an isolating transformer. However, if the control signal were of a d.c. nature the drive circuit providing the a.c. input to the isolating transformer would be unnecessarily complicated.

OPTO-ISOLATOR

An alternative approach is to use some form of opto-isolator. An opto-isolator is a simple unit consisting of a light-emitting device positioned close to a photosensitive component in a light-proof box. A home-made opto-isolator was, for instance, described in the article "L.E.D.-L.D.R. Isolator" which appeared in the April 1975 issue of this magazine, and this employed a TIL209 light-emitting diode in conjunction with an ORP12 photoconductive cell. When the l.e.d. was extinguished the ORP12 exhibited a high resistance, this falling to a low value when the l.e.d. was alight.

There was no electrical connection between the l.e.d. and the photoconductive cell, and the latter, in its low resistance mode, could turn on a triac by way of an amplifier.

Nowadays, ready made opto-isolators are available on the home constructor market. These are completely self-contained, and have the advantages of small physical size, very high speed of operation and the ability to drive a triac directly without the need for any subsequent stages of amplification.

The unit described in this article is a slightly simplified version of the circuit featured in the earlier article and it employs the opto-isolator type TIL111.

THE CIRCUIT

The circuit diagram of the opto-isolator a.c. switch appears in Fig. 1. Here, the triac is connected in series with the neutral mains lead to the load to be switched, and the load will not be switched on until a current of some 20mA is passed through the gate and A1 terminals of the triac. The load will then be supplied with the full mains voltage less an insignificant voltage of the order of 1 volt dropped across the triac. Once it has been triggered to the conducting state, the triac stays conducting until the current flowing between its A2 and A1 terminals falls to a low level. Since the triac is in an a.c. circuit the current flowing through it falls to zero at the end of each half-cycle, so that it becomes re-triggered by the gate current at the start of the next half-cycle. If the gate current is removed the triac turns off at the end of the appropriate half-cycle and the load is then fully switched off.

A low voltage power supply, from which the gate current for the triac can be derived, is provided by step-down transformer T1, the bridge rectifier incorporating D1 to D4, and the smoothing com-

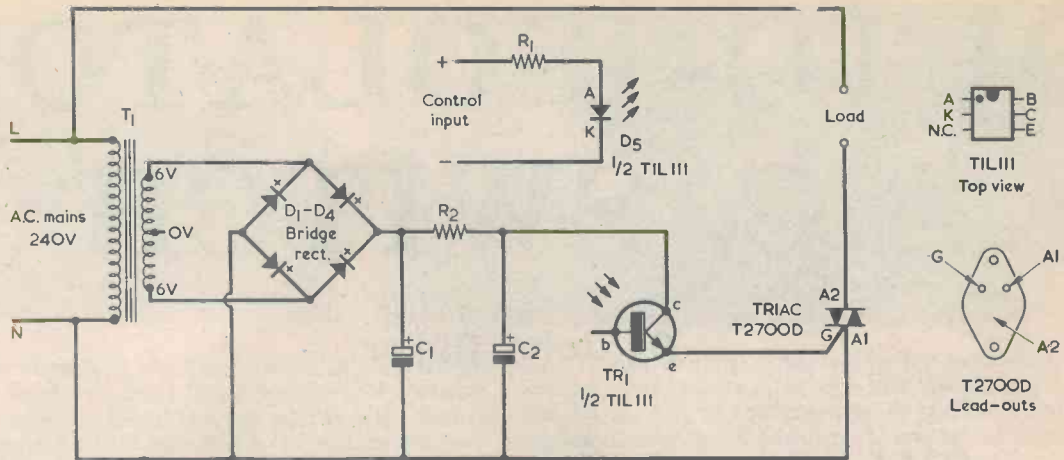


Fig. 1. The circuit of the opto-isolator a.c. switch. D5 and TR1 are combined in the single TIL111 package

COMPONENTS

Resistors

R1 180 Ω $\frac{1}{2}$ watt 5% (see text)
 R2 330 Ω $\frac{1}{2}$ watt 5%

Capacitors

C1 100 μ F electrolytic, 25V. Wkg.
 C2 100 μ F electrolytic, 25V. Wkg.

Transformer


T1 Sub-miniature mains transformer, secondary
 6-0-6V at 100mA (see text)

Semiconductors


Triac T2700D (see text)
 D1-D4 Silicon bridge rectifier,
 50V 1A or 2A
 TR1/D5 TIL111 (see text)

Miscellaneous

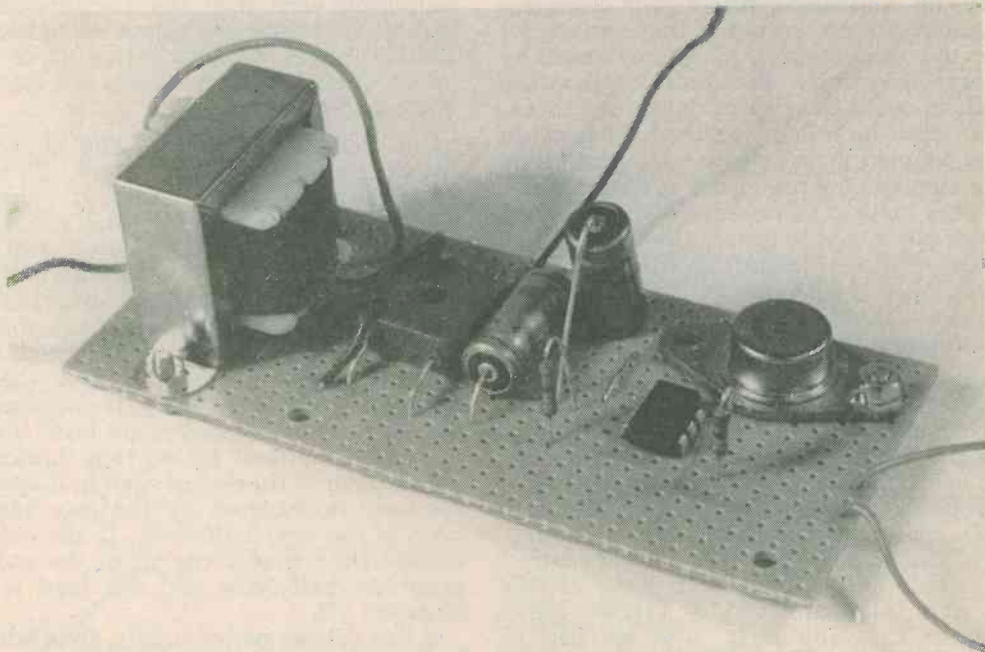Veroboard, 0.1in. matrix
 Veropins
 6BA mounting bolts, nuts, wire etc.



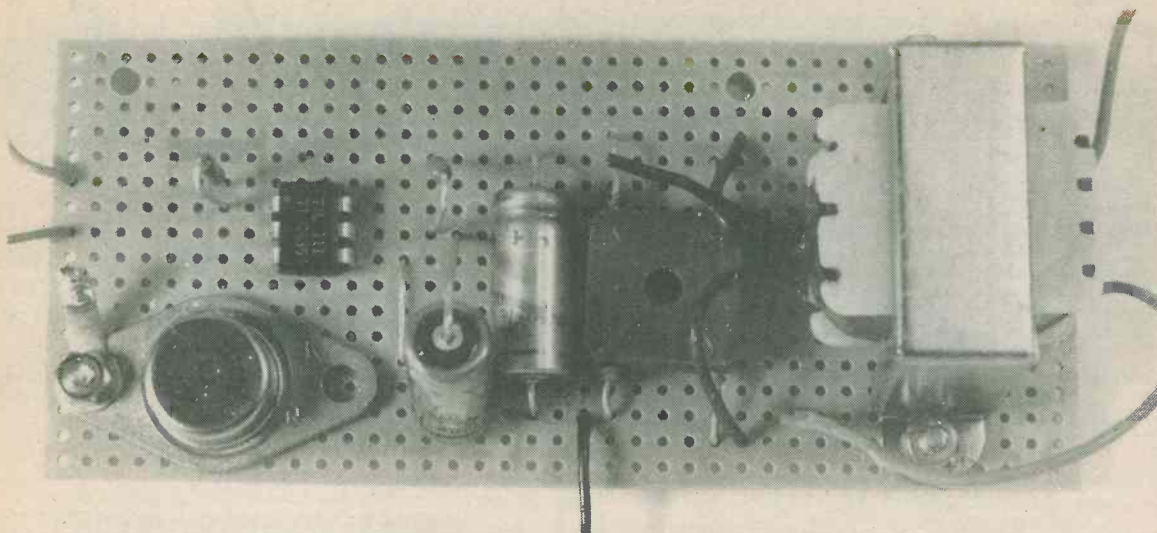A small Veroboard panel accommodates the opto-isolator components, including the mains transformer



The connection to the case of the triac, which provides the A2 terminal, is made by way of a solder tag and a 6BA nut and bolt, the bolt passing through the Veroboard

ponents C1, R2 and C2.

The TIL111 opto-isolator consists of an l.e.d. and an n.p.n. phototransistor. These are shown separately in the diagram as D5 and TR1, but in practice they are enclosed together in a small 6-pin d.i.l. package. In this circuit the phototransistor is used in the normal configuration with no connection made to the base of the transistor, and only minute leakage currents flow between the collector and the emitter when the l.e.d. is extinguished. Turning on the l.e.d. causes the collector-emitter current to be considerably increased and, provided sufficient current is fed to the l.e.d., the current through TR1 will be great enough to turn on the triac.

The input control voltage applied to R1 and D5 should be 6 volts with the polarity indicated, and R1 will then cause the l.e.d. current to be approximately 25mA. With the prototype circuit, an l.e.d. current of 20mA was sufficient to turn on the triac. However, due to component tolerances it may be found necessary to increase the l.e.d. current to turn the triac on fully, and this may be achieved by reducing the value of R1 and/or increasing the control voltage above 6 volts. With different control voltages and values of R1, the l.e.d. current in mA is equal to the voltage across R1 (i.e. the control voltage minus 1.4 volts dropped across the l.e.d.) multiplied by 1,000 and divided by the value of R1 in ohms. The l.e.d. current must not exceed the maximum rated value for the TIL111 of 60mA, and it should be possible to obtain satisfactory operation at currents comfortably below this level.

The loads controlled by the triac may have a current consumption of up to 1 amp, which corresponds to a maximum wattage of 240 watts with the U.K. 240 volt a.c. mains supply. It will be noted that, with the triac connected in the neutral line to the load, all the load wiring is at live potential when the triac is turned off. If correct wiring procedures are carried out this should not represent a hazard, and the alternative approach of inserting the triac in the live line would mean that T1 secondary cir-

cuit would be at live instead of neutral potential. Even with the method of switching employed, it is still essential that the switch unit to be housed in a robust insulated case which allows no access to any of the circuit points, and that either the negative or the positive side of the control voltage to the l.e.d. be reliably earthed. All other pertinent precautions against accidental shock must be fully observed.

CONSTRUCTION

The components can be assembled on a Veroboard of 0.1 in. matrix using the wiring layout illustrated in Fig. 2. This is perfectly straightforward, but make quite sure that none of the 14 breaks in the copper strips are omitted and that they are all effective. Two 6BA clear holes are drilled out at holes Q34 and B34 for mounting the mains transformer, and it is advisable to ensure that those two holes are correctly positioned by checking with the particular transformer to be employed before drilling them out. The mounting bolts for T1 must be isolated from the remainder of the circuit, and with the mounting bolt positions shown in Fig. 2 this isolation is achieved by the 6 breaks in the copper strips along vertical line 31.

When the gate and A1 lead-outs of the triac are passed through the holes indicated in Fig. 2, the left-hand hole in the metal case should appear over hole D2. This hole is also drilled out 6BA clear. A 6BA bolt is then passed through the hole, through a 6BA spacer to hold the body of the triac slightly clear of the board, and then through the hole in the triac case. A solder tag and 6BA nut are passed over the bolt and the nut is tightened up. The solder tag provides the connection to the triac A2, and the gate and A1 lead-outs are soldered to the copper strips at the holes through which they pass.

The remaining components are soldered to the board in normal fashion and care must be taken to ensure that no two adjacent strips are bridges together by blobs of solder. The "OV" secondary centre-tap lead of T1 does not connect into the circuit. The end of this lead should be covered with insulating tape and positioned well clear of com-

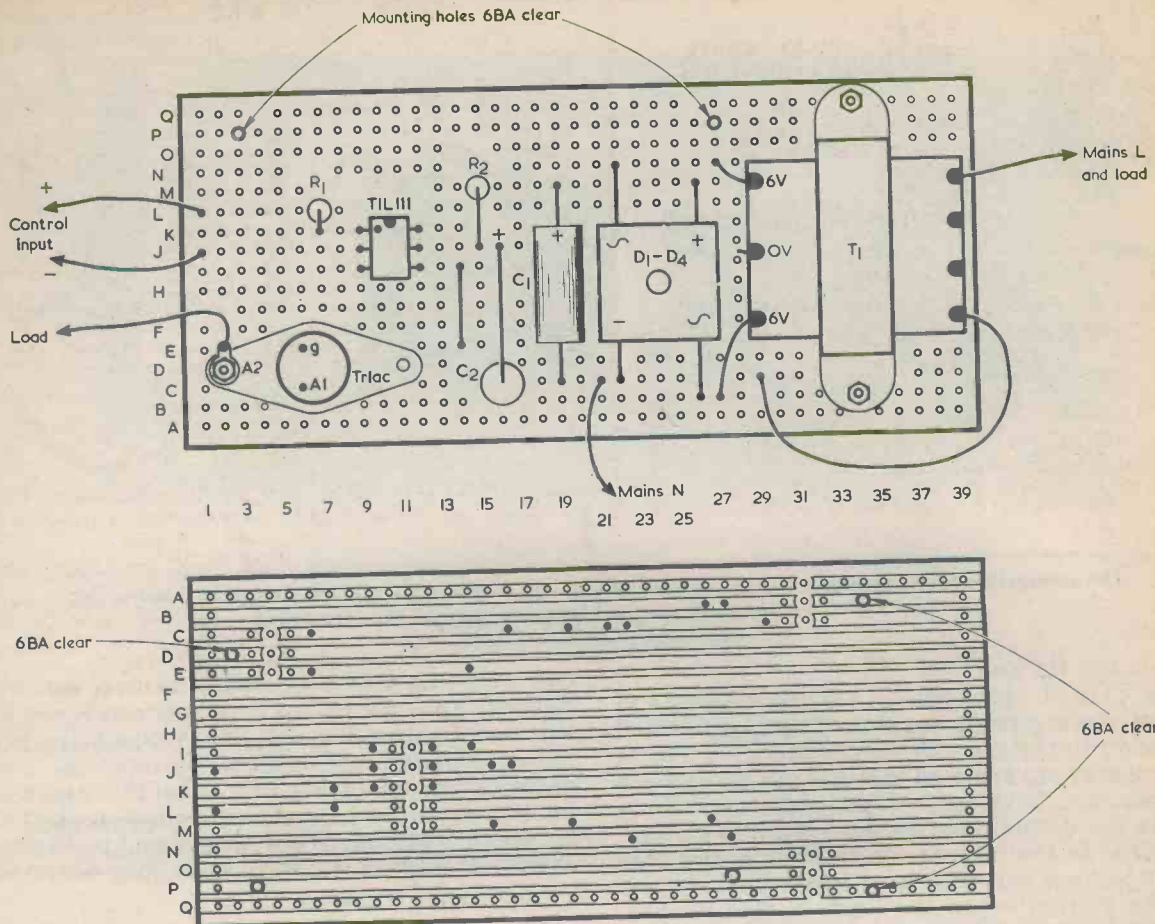


Fig. 2. The components of the opto-isolator switch may be assembled on a Veroboard panel. This has two mounting holes to enable it to be secured to a suitable surface

ponents and connections. For greatest reliability, Veropins suitable for 0.1 in. Veroboard should be soldered in place at the positions where external connections are made to the board, these being at the points where the control voltage and the neutral mains lead connect to the board. Since the mains transformer has flying leads an external terminal block suitable for mains voltages should be used for the connections to the mains supply and the load.

Before bringing the unit into use, thoroughly check all wiring for correctness. A continuity tester should be used to make certain that the input l.e.d. circuit is, in fact, isolated from the remaining cir-

cuitry. Also, make sure that the l.e.d. driving circuit is properly earthed.

COMPONENTS

A few of the components used in this switch unit are a little out of the ordinary and require some comment. The T2700D triac used in the prototype can be obtained from Electrovalue, and this has a voltage rating of 400 volts at a maximum current of 6 amps. The TIL111 opto-isolator is available from Greenbank Electronics, 94 New Chester Road, New Ferry, Wirral, Merseyside L62 5AG. A suitable component for transformer T1 is available from Maplin Electronic Supplies. ■

BACK NUMBERS

For the benefit of new readers we would draw attention to our back number service.

We retain past issues for a period of two years and we can, occasionally, supply copies more than two years old. The cost is 63p, inclusive of postage and packing.

Before undertaking any constructional project described in a back issue, it must be borne in mind that components readily available at the time of publication may no longer be so.



Wilmslow Audio

THE firm for speakers!

SEND 15p FOR THE WORLDS BEST CATALOGUE OF SPEAKERS, DRIVE UNITS KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST

AUDAX • AUDIOMASTER • BAKER • BOWERS & WILKINS • CASTLE • CELESTION • CHARTWELL • COLES • DALESFORD • DECCA • EMI • EAGLE • ELAC • FANE • GAUSS • GOODMANS • I.M.F. • ISOPON • JR • JORDAN WATTS • KEF • LEAK • LOWTHER • MCKENZIE • MONITOR AUDIO • PEERLESS • RADFORD • RAM • RICHARD ALLAN • SEAS • STAG • TANNON • VIDEOTONE • WARFEDALE • YAMAHA • SHACKMAN • TANGENT

WILMSLOW AUDIO DEPT REC

SWAN WORKS, BANK SQUARE, WILMSLOW CHESHIRE SK9 1HF
Discount HiFi Etc. at 5 Swan Street and 10 Swan Street
Tel: 0625-529599 for Speakers. 0625-526213 for HiFi

7400 10p	7432 20p	7482 75p	74126 35p	74155 45p	74181 130p
7401 10p	7433 20p	7483 75p	74128 60p	74156 45p	74182 50p
7402 10p	7437 20p	7484 70p	74130 120p	74157 45p	74184 120p
7403 10p	7438 20p	7485 60p	74131 90p	74160 85p	74185 100p
7404 12p	7440 12p	7486 25p	74132 45p	74161 85p	74188 320p
7405 12p	7441 45p	7489 130p	74135 90p	74162 65p	74190 70p
7406 25p	7442 40p	7490 25p	74138 80p	74163 85p	74191 70p
7407 25p	7443 60p	7491 40p	74137 90p	74164 80p	74192 60p
7408 12p	7444 60p	7492 35p	74138 100p	74165 60p	74193 60p
7409 12p	7445 65p	7493 30p	74141 50p	74166 75p	74194 55p
7410 12p	7446 50p	7494 70p	74142 180p	74167 180p	74185 50p
7411 15p	7447 80p	7495 45p	74143 270p	74170 100p	74196 50p
7412 15p	7448 80p	7496 45p	74144 270p	74173 80p	74197 50p
7413 25p	7450 12p	7497 120p	74145 85p	74174 80p	74198 100p
7414 45p	7451 12p	74100 80p	74147 100p	74175 60p	74199 100p
7415 25p	7453 12p	74104 40p	74148 90p	74178 60p	74293 90p
7416 25p	7454 12p	74105 40p	74150 65p	74177 60p	741500 18p
7417 12p	7460 12p	74107 25p	74151 45p	74178 75p	745112 80p
7421 20p	7470 25p	74108 100p	74153 45p	74179 120p	7423 20p
7422 15p	7472 20p	74109 25p	74154 70p	74180 80p	7425 20p
7426 22p	7473 25p	74118 75p	7476 25p	74122 35p	7430 12p
7427 22p	7474 25p	74120 80p	7480 40p	74123 40p	
7428 25p	7475 25p	74121 25p	7481 85p	74125 35p	

LINEAR	LM390 80p	SN76013ND 125p	TBA700 180p
AY38500 450p	LM381N 90p	SN76023N 110p	TBA7200 225p
CA3039 70p	LM382 90p	SN76023ND 125p	TBA7500 200p
CA3046 60p	LM391 180p	SN76033N 180p	TBA800 80p
CA3060 225p	LM555 25p	SN76227N 140p	TBA810 100p
CA3065 200p	LM709C 40p	SN/6228N 180p	TBA820 100p
CA3076 250p	LM71001L 85p	SN78660N 75p	TBA9200 280p
CA3080 75p	LM723105 40p	TAA350 100p	ICA2700 220p
CA3084 250p	LM733 120p	TAA550 35p	TCA2705 220p
CA3085 85p	LM741 20p	TAA570 220p	TCA760 200p
CA3086 80p	LM748 40p	TAA661B 140p	TCA4500A 450p
CA3088 190p	LM1303N 100p	TAA700 30p	TDA1008 380p
CA3089 160p	LM1458 100p	TAA790 350p	TDA1034 450p
CA3090A 380p	LM3080 75p	TAD100 150p	TDA2002 300p
CA3123E 130p	LM3900 55p	TAD110 130p	TLO84 120p
CA3130 100p	LM3908N 85p	TB4120S 60p	XR320 250p
CA3140 60p	LM3910 85p	TBA120T 85p	XR2206 450p
LF356 80p	MC1310P 140p	TBA4800 200p	XR2207 450p
LF357 80p	MC1312P 150p	TBA5200 200p	XR2208 800p
LM211H 250p	MC1314P 190p	TBA540 20p	XR2216 850p
LM3007RS 170p	MC1315P 230p	TBA5500 250p	XR2667 250p
LM301AN 30p	MC1310P 140p	TBA560C 250p	XR4136 150p
LM304 20p	MM5314 380p	TBA641A12 250p	XR4212 150p
LM307N 85p	MM5316 480p		XR4739 150p
LM308T05 100p	NE529K 150p		ZN414 100p
LM308DIL 100p	NE556 25p		95H90 700p
LM309K 100p	NE556 90p		
LM310T05 150p	NE6628 400p		
LM311T05 150p	SAD1024 1500p		
LM317K 325p	SL5178 850p		
LM324 70p	SN76003N 150p		
LM339 50p	SN76013N 110p		
LM348N 90p			

T. POWELL
306 ST. PAUL'S ROAD,
HIGHBURY CORNER, LONDON N.1
Telephone: 01-226 1489
ALL PRICES INCLUDE POST AND V.A.T.

CHESTER ELECTRONICS

CONVERGENCE POTS: 20R, 22R, 30R, 33R, 60R, 120R, 250R. All at 5p each or 100 mixed for £3.

AC128 16p	BC125 10p	BRY39 26p	1S44 4p
AC187K 25p	BC147B 7p	BU208 £2.00	1N914 2p
AD161 35p	BC184C 7p	BFY80 15p	1N4148 3p
AD162 35p	BD131 34p	BFY52 15p	OA47 10p
AD149 50p	BD132 34p	BFY63 15p	OA200 6p
AU110 £1.00	M/Pair 82p	TIP32C 50p	1N4001 4p
BC107 8p	BD238 45p	2N3055 35p	1N4004 5p
BC108 8p	BF262 30p	OC45 25p	1N4006 6p
BC109 8p	RFX89 20p	OC72 30p	1N4007 7p

Belling Lee Flush mounted 2-Gang Coaxial Outlets (Complete with screws) (Type L1481/R) SPECIAL CLEARANCE PRICE, 50p each

Belling Lee Flush Mounting Diplexer (UHF & VHF) (Complete with screws) (Type L1893) SPECIAL CLEARANCE PRICE, 75p each

Belling Lee Flush Mounting Twin Coaxial Outputs, Type L1704 (complete with screws) SPECIAL CLEARANCE PRICE 75p each

Zener Diodes 400mW: 4V7, 5V1, 11V, 13V5, 24V, 30V
8p each, 50 for £3.50, 100 for £5.00

Axial 25µ 24V 4p	Axial 200µ 6V 5p	Tantalum Beas Capacitors 1+ 100+
Axial 1.0µ 63V 5p	Axial 220µ 80V 15p	0.1µ 35V 10p
Axial 15µ 480V 20p	Axial 640µ 25V 20p	0.22µ 35V 10p
Axial 47µ 160V 10p	Tag 4700µ 16V 30p	0.47µ 35V 10p
Axial 100µ 80V 10p	Tag 3500µ 30V 20p	68µ 3V 10p
Radial 100µ 10V 5p	Tag 1000µ 25V 40p	

SMITH small clock motors. Mains 50Ω 2W (Brand new and unused) £1.00 each

Metal Rotary Pots 10 for £1.00 (Advise us of value preferred and we will send it or the nearest available)

SPECIAL OFFER: BFY50, BFY51, BFY52. (All new, full spec. marked etc) 10 for £1.45, 50 for £7.00, 100 for £12.50

WHITE IN LINE, CAR RADIO TYPE, FUSEHOLDERS, 5p each, 100 for £4.00
4 core Curly leads (unscreened) stretch from 3' to 8', 30p each

SPECIAL OFFER: 741 8 pin DIL, Brand New, marked, full spec. etc) 1-18p, 50 for £8.00, 100 for £15.00

Hunts Capacitor, Axial 0.0015µ 400V only 5p each

Tubular Ceramic Capacitors, 100 for £1.00 (Our mix but all low of values)

Do not add any VAT to the above prices. Only add 15p P&P to your total order. No callers please as we have no retail facilities.

Send your orders to:
DEPT. DP9 CHESTER ELECTRONICS
6 HUNTER STREET, CHESTER. CH1 2AU

MAGENTA ELECTRONICS LTD

REC4 98 CALAIS ROAD, BURTON-ON-TRENT, STAFFS DE13 0UL
PHONE 02 83 65435. 9 a.m.-12, 2 p.m.-5. MON.-FRI. Mail Order only

All prices include VAT & First Class Post. Add 25p to orders under £5

R.E.C. PROJECT KITS

Make us YOUR No. 1 SUPPLIER of KITS and COMPONENTS for REC Projects. We supply carefully selected sets of parts to enable you to construct REC projects. Appropriate hardware — nuts, screws, I.C. sockets are included. Each project kit comes complete with its own FREE COMPONENT IDENTIFICATION SHEET. We supply — You construct.
PRICES INCLUDE CASES UNLESS OTHERWISE STATED.
Project instructions only supplied as extra 39p each.

CONSTANT CURRENT TRANSISTOR TESTER, Mar. 79 £11.93.

I.C. MORSE PRACTICE OSCILLATOR, Mar. 79 £4.94.
Morse key extra £3.40.

2-TONE DOOR BUZZER, Feb. 79 £5.15.

3-BAND SHORT WAVE PREAMPLIFIER, Feb. 79 £13.33

ULTRA SENSITIVE ULTRASONIC REMOTE CONTROL, Feb. 79 £13.44. Doppler shift add-on unit, Mar 79 £3.61.

RADIO 4 CONVERTER, Jan 79, £5.99.

BRY39 METRONOME, Jan 79 £4.21.

BRY39 TOUCH SWITCH, Dec. 78 £1.31. Relay extra £1.83.

BRY39 PILOT LIGHT, Dec. 78 £1.15.

LIGHT CHANGE ALARM UNIT, Dec. 78 £9.31.

SWINGING METRONOME, Nov. 78 £11.38.

REMOTE READ-OUT THERMOMETER, Oct. 78 £13.60.

DIGITAL DICE, Sept. 78 £9.13.

VARIABLE — 'C' A.F. GENERATOR, Aug. Sept. 78 £14.59.

PHOTOCELL PROPERTY PROJECTOR, Aug. 78 £6.07. Bell extra £1.45.


1979 ELECTRONICS CONSTRUCTORS CATALOGUE


HAVE YOU GOT YOUR COPY YET? MAGENTA'S NEW CATALOGUE INCLUDES MANY NEW PRODUCTS — CAREFULLY CHOSEN FOR EVERYDAY ELECTRONICS READERS; PRODUCT DATA AND ILLUSTRATIONS MAKE THE MAGENTA CATALOGUE AN INDISPENSABLE GUIDE FOR CONSTRUCTORS; FULLY INCLUSIVE PRICES RIGHT NEXT TO THE PRODUCTS MAKE ORDERING EASY. NO MINIMUM ORDER — ALL PRODUCTS STOCK LINES. FIRST CLASS DELIVERY OF FIRST CLASS COMPONENTS. SEND FOR YOUR COPY AND SEE HOW EASY IT IS TO USE THE MAGENTA CATALOGUE!
WRITE TODAY ENCLOSING 4 x 9p STAMPS.


DIRECT SUPPLY SERVICE TO READERS

TOWERS INTERNATIONAL TRANSISTOR SELECTOR

(NEW REVISED EDITION)

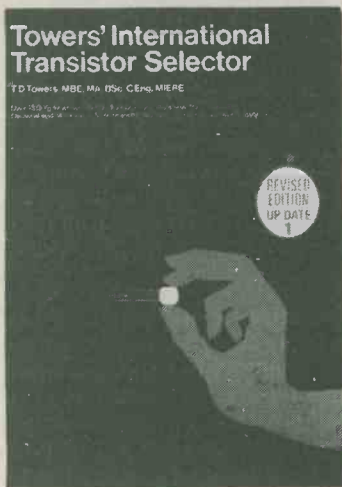

This is dead! 
Would this replace it?

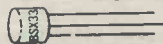

If it takes you longer than 1 minute to find out all about these transistors then you need a copy of TOWER'S INTERNATIONAL TRANSISTOR SELECTOR. Its one of the most useful working books you will be offered this year. And probably the cheapest!

In it you will find a really international selection of 13,000 transistor types — British, Continental European, American and Japanese. And we think that they will solve 90% of your transistor enquiries.

Current and widely used obsolete types were carefully selected and arranged in Numero-Alphabetical order by an author who was uniquely qualified to do the job. With his compendium, all you need to know is the type number and you can learn all about a transistor's specification; who made it and where to contact them; or what to use to replace it.

Price **£6.00** inc. P&P

(Please allow 21 days for delivery)

**Tower's
International
Transistor
Selector**

by **T. D. Towers**
MBE, MA, BSc, C Eng, MIERE
£6.00
inc. post and packing

To:—DATA PUBLICATIONS LTD.
57 MAIDA VALE
LONDON W9 1SN

Please send me copy/copies
to the address shown below

NAME


ADDRESS

.....
.....

.....(Block capitals)

TOWERS INTERNATIONAL FET SELECTOR

(JUST PUBLISHED)

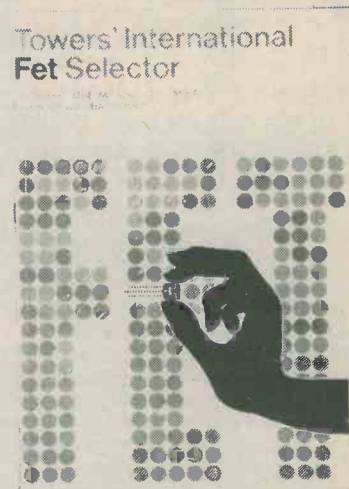

If you deal with field effect transistors, or fet's — whether as a student, a hobbyist, a circuit engineer, a buyer, a teacher or a serviceman — you often want data on a specific fet of which you know only the type number.

Specifications apart, you may be even more interested in where you can get the device in question. And perhaps more important still (particularly with obsolete devices), you may want guidance on a readily available possible substitute.

This fet compendium, a comprehensive tabulation of basic specification, offers information on:

1. Ratings
2. Characteristics
3. Case details
4. Terminal identifications
5. Applications use
6. Manufacturers
7. Substitution equivalents (both European and American)

The many fet's covered in this compendium are most of the more common current and widely-used obsolete types.

It is international in scope and covers fet's not only from the USA and Continental Europe, but also from the United Kingdom and the Far East (Japan).

Price **£4.00** inc P&P

(We regret this offer is only available to readers in the U.K.)

**Tower's
International
FET
Selector**

by **T. D. TOWERS**
MBE, MA, BSc, C Eng, MIERE
£4.00
inc. post and packing

To:—DATA PUBLICATIONS LTD.
57 MAIDA VALE
LONDON W9 1SN

Please send me copy/copies
to the address shown below

NAME

ADDRESS

.....
.....

.....(Block capitals)

SMALL ADVERTISEMENTS

Rate: 10p per word. Minimum charge £1.50

Box No. 25p extra

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the *bona fides* of Advertisers. Where advertisements offer any equipment of a transmitting nature, readers are reminded that a licence is normally required. (Replies to Box Numbers should be addressed to: Box No. —, *Radio and Electronics Constructor*, 57 Maida Vale, London, W9 1SN.

TIRRO'S NEW MAIL ORDER price list of electronic components now available on receipt of S.A.E. — TIRRO Electronics, Grenfell Place, Maidenhead, Berkshire.

WANTED: Large and small quantities of transistors, I.C.'s displays, etc., etc. Call any Saturday to: 306 St. Paul's Road, London N.1. Telephone: 01-359 4224.

A FAST INTRODUCTION TO COMPUTING £3.95. Introduction to Microprocessors and Computing £2.75. Both ordered together £6.20. S.A.E. for list of computing books. Dept. RC, Industrial Training Press, 3 Ringwood Way, Winchmore Hill, London N21 2RA.

FOR SALE: Inverter, 12V d.c. to 240V a.c. Suitable running electric shaver, camping, boating, etc. £5.50. Box No. G355.

SOLAR CELLS: Bits, books and bargains. Send 95p for Solar Cell booklet and Data Sheets or stamp for list. — Edencombe Ltd., 34 Nathans Road, North Wembley, Middlesex HA0 3RX.

SUPPLIERS OF ANY SERVICE SHEET or manual. S.A.E. with enquiries. Easy to follow repair instructions for any TV — send £5.00 and details of set. Circuit diagram £1 extra. AUSREC, 76 Church Street, Larkhall, Lanarkshire.

FOR SALE: Ex-A.M. rotary motor generator, 12V d.c. at 3.8 amps to 480V at 0.04 amps. £2.00 plus carriage. Box No. G356.

CAR BATTERY GIVING TROUBLE? Try our all electronic battery monitor. IC & PCB, £2.75 inc. S.A.E. for details. Tritsch Electronics, 190 Roding Road, Loughton, Essex.

NEW SHOP IN EAST KENT. Vast range of electronic components, equipment, hardware. Technocraft, 143 Tankerton Road, Whitstable, Kent. Telephone: 265097. Open Tuesday to Saturday. Easy parking.

THE RADIO AMATEUR INVALID & BEDFAST CLUB is a well established Society providing facilities for the physically handicapped to enjoy the hobby of Amateur Radio. Please become a supporter of this worthy cause. Details from the Hon. Secretary, Mr. H. R. Boutle, 14 Queens Drive, Bedford.

V.H.F./F.M. Miniature Transmitter Kit. Range 100 yards. 80-100MHz. Unlicenseable. £2.95 plus 25p postage. P. Faherty, 4 Angus Drive, South Ruislip, Middlesex.

FOR SALE: *Fundamentals of Radio Servicing* by B. W. Hicks, published by Hutchinsons Educational, £2.20 post paid. *Handbook of Satellites and Space Vehicles* by R. P. Haviland, £3.50 post paid. — Box No. G366.

(Continued on page 581)

ELECTROVALUE

FOR A GOOD DEAL BETTER THAN MOST

Catalogue 9

THE BEST EVER

- ★ *Completely revised*
- ★ *More items*
- ★ *More illustrations*
- ★ *120 pages*

FREE

SEND FOR YOUR COPY TODAY

*For all round satisfaction — Be Safe
Buy from ELECTROVALUE*

ELECTROVALUE LTD

Dept. R.C. 579, 28 St Judes Rd. Englefield Green, Egham, Surrey TW20 0HB
Phone: Egham 3603. Telex: 264475.
Northern Branch (Personal shoppers only) 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone: 061-432 4945.

A CAREER IN RADIO

Start training *today* and make sure you are qualified to take advantage of the many opportunities open to the trained person. ICS can further your technical knowledge and provide the specialist training so essential to success.

ICS, the world's most experienced home study college, has helped thousands of ambitious men to move up into higher paid jobs — they can do the same for you.

Fill in the coupon below and find out how!

There is a wide range of courses to choose from, including:

CITY & GUILDS CERTIFICATES

Telecommunications Technicians'
Radio TV Electronics Technicians'
Electrical Installations Technicians'
Electrical Installation Work
Radio Amateurs'

MPT Radio Communications Cert.

**EXAMINATION STUDENTS —
GUARANTEED COACHING
UNTIL SUCCESSFUL**

TECHNICAL TRAINING

ICS offer a wide choice of non-exam courses designed to equip you for a better job in your particular branch of electronics, including:
Electronic Engineering & Maintenance
Computer Engineering/Programming
Radio, TV & Audio Engineering & Servicing
Electrical Engineering, Installations & Contracting

COLOUR TV SERVICING

Technicians trained in TV Servicing are in constant demand. Learn all the techniques you need to service Colour and Mono TV sets through new home study course approved by leading manufacturer.

POST THIS COUPON OR TELEPHONE FOR FREE PROSPECTUS

I am interested in

Name

Age

Address

Occupation

ICS

Accredited
by CACC
Member of
ARCC

To
International Correspondence Schools
Dept G278, Intertext House, LONDON
SW8 4UJ or phone 01-622 9911 (anytime)

NEW FROM U.S.A.
THE 3rd HAND
 MAKES CIRCUIT ASSEMBLY A BREEZE

- Lets you work with both hands ●
- Sturdy aluminium construction ●
- Accepts boards of any size ●


STEP 1

Clamp "3rd Hand" on edge of bench, table or workboard. Insert circuit board, position components — Notice the convenient working angle.



STEP 2

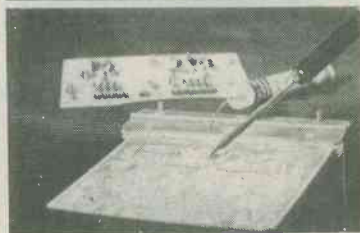Flip circuit board to flat position for soldering and clipping. Reverse procedure for double sided boards.



INTRODUCTORY OFFER £7.85 INC.

SOLE IMPORTERS · DEALER ENQUIRIES INVITED

PARA SALES

1 Hook Road, Kingsclere, Newbury, Berks

Strip-fix Plastic PANEL SIGNS



★ SET 3 - Wording - WHITE

★ SET 4 - Wording - BLACK

Over 1,000 words and symbols, covering more than 300 terms, in each set

Illustration of actual size = RADIO

★ SET 5 - DIALS

6 sheets containing one Large and two Medium scales, Large Horizontal Tuning scale, Frequencies, 12 Control Panels

6 SHEETS IN EACH SET

PRICE: £1 per set inc. VAT
 p. & p. 8p per set

To DATA PUBLICATIONS LTD.,
 57 Maida Vale, London, W9 1SN

Please supply Panel Signs as follows: Set 3..... Set 4..... Set 5.....

I enclose cheque/crossed postal order for.....
 (Tick which set is required)

NAME

ADDRESS

(BLOCK LETTERS PLEASE)

RADIO MODELLER

ELECTRONIC BOOKS

● **MODEL RADIO CONTROL**

Detailing both Theory and Practice, this book, by leading authority Paul Newell, has become the standard reference work. A brief historical survey leads up to a detailed description of proportional systems, with over 100 illustrations, including theoretical circuits and p.c. layouts for an advanced digital system.

134 pages

Price £3.35

U.K. Packing
 & Postage

32p

theory and
 practice of

**MODEL
 RADIO
 CONTROL**

development of systems
 proportional explaining
 digital system design
 practical examples and
 full circuit details

ON SALE NOW
 at all leading shops
 or direct from:-

**RADIO MODELLER
 BOOKS DIVISION,**
 High Street,
 Sunningdale,
 Berkshire SL5 0NF.

Now available . . .

LATEST BOUND VOLUME

No. 31

of

"Radio & Electronics Constructor"

NEW LARGER FORMAT



AUGUST 1977 to JULY 1978

Comprising
768 pages
inc. index

PRICE £5.20 P&P 90p

BOUND VOLUME No. 27
(August 1973 to July 1974)

Price £3.00 P&P 90p

BOUND VOLUME No. 28
(August 1974 to July 1975)

Price £3.20 P&P 90p

BOUND VOLUME No. 29
(August 1975 to July 1976)

Price £3.50 P&P 90p

BOUND VOLUME No. 30
(August 1976 to July 1977)

Price £3.70 P&P 90p

Limited number of these
volumes still available.

We regret all earlier volumes are now
completely sold out.

Available only from

**DATA PUBLICATIONS LTD.,
57 MAIDA VALE, LONDON, W9 1SN**

SMALL ADVERTISEMENTS

(Continued from page 581)

FOR SALE: Miniature hearing aid amplifiers £2; Red l.e.d.'s 10p; 1000 diodes £2.50; 100 transistors £1.00. — J. Fulton, Derrynaseer, Dromore, Co. Tyrone, N. Ireland.

FOR SALE: PARCELS — Caps., diodes, res., trans. items. Over 100 parts, £2.25; 200, £3.50. Mr. Sole, 377 Stanley Street, Ormskirk, Lancs., L39 2DH.

TRANSFORMERS. 5Va to 500Va designed and manufactured to specification for hobbyist or O.E.M. Fast service. Many popular types ex-stock. Competitive prices. Send details of requirements for quotations to Louth Transformer Company, Peppin Lane, Fotherby, Louth, Lincolnshire.

FOR SALE: "Experiments with Operational Amplifiers" — Learning by Doing. George B. Clayton £2.50. "Challenge of the Stars" by Patrick Moore and David A. Hardy £2.00. "Destroyers" by Antony Preston £4.00. Box No. G376.

RHYTHM GENERATOR. Samba, waltz, jazz, rock, cha cha, etc. Down beat led tempo volume stop-start. Slim case. Battery model £49.50. Mains model £59.50. Inclusion of VAT and post, etc. 2 year guarantee. P.E. Limited, Coed Aben Trading Estate, Wrexham, Clwyd.

POSTAL ADVERTISING? This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list. — The Holborn Direct Mail Company Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407 6444.

COLLECTORS' ITEMS. Nearly 50 copies of Radio Society of Great Britain's *Bulletins* covering period 1945 to 1949. In reasonable condition. Offers to: Box No. G377.

FOR SALE: Damaged Video Tape Recorder £75.00. Closed circuit television camera £50.00. — J. Fulton, Derrynaseer, Dromore, Co. Tyrone, N. Ireland.

TURN YOUR SURPLUS Capacitors, transistors, etc., into Cash. Contact COLES-HARDING & CO. 103 South Brink, Wisbech, Cambs. Telephone: 0945-4188. Immediate settlement. We also welcome the opportunity to quote for complete factory clearance.

FOR SALE: Dichromate hologram pendants, 3 dimensional effect or 2 dimensions £12.00. Voice control ladybird toy with, stop, go, turn or command £15.00. Light sensor shooting game £15.00. — J. Fulton, Derrynaseer, Dromore, Co. Tyrone, N. Ireland.

PERSONAL

JANE SCOTT FOR GENUINE FRIENDS. Introductions to opposite sex with sincerity and thoughtfulness. Details free. Stamp to: Jane Scott, 3/Con North St. Quadrant, Brighton, Sussex, BN1 3GJ.

BROADLANDS RESIDENTIAL CLUB for elderly people. Are you recently retired and looking for a home? We have a delightful top floor room overlooking Oulton Broad, facing south. Write to: The Warden, Broadlands Residential Club, Borrow Road, Oulton Broad, Lowestoft, Suffolk.

SPONSORS required for exciting scientific project. Norwich Astronomical Society are building a 30" telescope to be housed in a 20' dome of novel design. All labour being given by volunteers. Already supported by Industry and Commerce in Norfolk. Recreational. Educational. You can be involved. Write to: NAS, Secretary, 195 White Woman Lane, Old Catton, Norwich, Norfolk.

(Continued on page 583)

SMALL ADVERTISEMENTS

(Continued from page 582)

CAN YOU DESIGN PRINTED CIRCUITS, arrange layouts, and re-arrange? Engineer (Kent) requires help via post, to promote new designs. — Reply in complete confidence to Box No. G374.

IF YOU HAVE ENJOYED A HOLIDAY on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from: — The Hon. Membership Secretary, The Broads Society, "Icknield," Hilly Plantation, Thorpe St. Andrew, Norwich, NOR 85S.

UNIVERSAL AC TO DC CONVERTER



CHOICE OF
3-4½-6-7½-
9-12 VOLTS DC

£9.95

This ultra wide range power supply unit converts the usual domestic AC input 220/250 volts to a choice of DC outputs 3-4½-6-7½-9-12 volts DC, selected by a rotary switch. The output multi-plug is polarity reversing and combines a 3.5mm Jack plug with 2.1mm and 2.5mm power plugs PLUS 2.5mm Jack plug (slips over the 3.5mm plug). Suitable wide range of different units. Earthed, ventilated metal case with pilot light and switch. Exceptional value **£9.95 + 95p p&p**. Also single voltage 9V 150 MA model suitable for nearly all TV Games **£5.45 + 55p p&p**.

JOHN DUDLEY & CO LTD (Dept. RC10), Carolyn House, Water Road, Wembley, Middx. (Mail Order) Tel: 01-435 5456 (before noon). Access Accepted



£24.95

MICROJET WELDER
A TINY FLAME UP TO 5000°F!
WELDS-BRAZES SOLDERS

Precision tool using combination of butane and compressed oxygen or micronox. A pencil lead thin flame size, adjustable to 5,000°F. Cuts metals, welds, brazes and solders gold, silver. Ideal electricians, opticians, dentists, silversmiths, modelling, jewellery, clockmakers, electronic and computer servicing. Up to 30 minutes use on fuel supplied. Replacement set of 2 micronox, 1 butane cylinder **£2.30 + 25p p&p extra. £24.95 + £1.35 p&p**.

TRANSFORMERS

Primary 240V		
6-0-6V	100mA	£0.75
9-0-9V	75mA	£0.75
12-0-12V	50mA	£0.85
12-0-12V	100mA	£1.05
Post on above transformers 30p		
9-0-9V	1A	£1.80
12-0-12V	1A	£2.15
15-0-15V	1A	£2.36
6-3V	1½A	£1.80
6-0-6V	1½A	£2.20
Post on above transformers 45p		
9-0-9V	2A	£2.75
12V	2A	£2.40
Post on above transformers 86p		

MICROPHONES FOR TAPE RECORDERS

DM228R 200 ohm with 3.5 and 2.5mm jack plug	£1.66
DM229R 50K with 3.5 and 2.5mm jack plug	£2.20
DM18D 200 ohm with 5 and 3 pin DIN plug	£1.95
Postage on above microphones 13p	

CARDIOID DYNAMIC MICROPHONES

Model UD-130 frequency response 80-14,000Hz. Impedance dual 50K and 600 ohm	£8.02 post 36p
UD147 frequency response 50-15,000Hz. Impedance dual 50K and 200 ohm.	£13.85 post 36p
6V BUZZERS 50mm diameter, 30mm high. Very loud.	52p post 9p

PANEL METERS

42 x 42mm — and 500uA	£3.65 post 13p
60 x 45mm — 50uA, 100uA, 500uA, 1mA, 5mA, 10mA, 50mA, 100mA, 500mA, 1A, 2A, 25V DC, 50V DC, 300V AC, 'S' meters, VU meters, 50-0-50uA, 100-0-100uA, 500-0-500uA	£6.16 post 13p
4½ x 3½ — 30uA, 50uA, 100uA, 200uA or 500uA	£6.40 post 19p

MULTIMETER

Model ITI-2 20,000 ohm/volt	£12.32 post 33p
IT22 20,000 ohm/volt.	£12.48 post 33p

All above prices include V.A.T. Special prices for quantity quoted on request.

Send 40p for New Autumn 1978 Fully Illustrated Catalogue.

M. DZIUBAS

158 Bradshawgate · Bolton · Lancs. BL2 1BA

PRINTED CIRCUITS AND HARDWARE

Comprehensive range Constructors' hardware and accessories. Selected range of popular components. Printed circuit boards for individual designs. Drawing materials for printed circuits. Resist coated laminate, epoxy glass for the d.i.y. man. Full processing instructions, no unusual chemicals required.

Send 15p for catalogue

Ramar Constructor Services

Masons Road · Stratford-on-Avon · Warwks CV37 9NF

BUILD YOUR OWN

P.A. GROUP & DISCO SPEAKERS by R. F. C. Stephens

Save money with this practical guide. Plans for 17 different designs. Line source, I.B., Horn and Reflex types, for 8"-18" drive units. £3.95 post free (\$8 overseas).

THE INFRA-BASS LOUDSPEAKER by G. Holliman

(full constructional details for versions using 15", 12" and 10" drive units.) £2.95 post free (\$6 overseas).

THE DALESFORD SPEAKER BOOK by R. F. C. Stephens

This book is a must for the keen home constructor. Latest technology DIY designs. Plans for I.B., and Reflex designs for 10-100 watts. Also unusual centre-bass system. £2.20 post free (\$5 overseas).

VAN KAREN PUBLISHING

5 Swan Street, Wilmslow, Cheshire

REVOR OPTICAL & TECHNICAL

6 SICILIAN AVENUE
LONDON W.C.1
Tel. 01-836 4536

£14.91

POST FREE

4" dia. lens

FLEXIBLE MAGNIFIER

WITH CAST IRON BASE, PRECISION GROUND AND POLISHED LENS, CHROME PLATED FRAME AND FLEXIBLE TUBE. IDEAL FOR HOBBIES, AND DETAILED WORK WHICH REQUIRES BOTH HANDS FREE.

CALLERS WELCOME

(Subject to price ruling at the time of issue)



RADIO & ELECTRONICS CONSTRUCTOR

Single Copies

Price 50p each, p&p 13p

Issue(s) required

Annual Subscription

Price **£7.50 inland, £8.50 overseas**

post free, commence with issue

Bound Volumes:

Vol. 27. August 1973 to July 1974	Price £3.00 , post & pkg 90p
Vol. 28. August 1974 to July 1975	Price £3.20 , post & pkg 90p
Vol. 29. August 1975 to July 1976	Price £3.50 , post & pkg 90p
Vol. 30. August 1976 to July 1977	Price £3.70 , post & pkg 90p
Vol. 31. August 1977 to July 1978	Price £5.20 , post & pkg 90p

CORDEX SELF-BINDERS *NEW FORMAT*

With title, 'RADIO & ELECTRONICS CONSTRUCTOR' on spine,
maroon only

Price **£1.80**, post & pkg 40p

With no title on spine, maroon

Price **£1.80**, post & pkg 40p

With no title on spine, green

Price **£1.80**, post & pkg 40p

Prices include V.A.T.

DATA BOOK SERIES

DB5 TV Fault Finding, 132 pages Price **£1.20**, P. & P. 20p

DB6 Radio Amateur Operator's Handbook,
New edition in course of preparation

DB17 Understanding Television, 504 pages Price **£3.95**, P. & P. 70p

DB19 Simple Short Wave Receivers
140 pages Price **80p**, P. & P. 20p

STRIP-FIX PLASTIC PANEL SIGNS

Set 3: Wording — White — 6 sheets Price **£1.00**, P. & P. 8p

Set 4: Wording — Black — 6 sheets Price **£1.00**, P. & P. 8p

Set 5: Dials — 6 sheets Price **£1.00**, P. & P. 8p

Prices include V.A.T. on Panel Signs

I enclose Postal Order/Cheque for in payment for

NAME

ADDRESS

..... (BLOCK LETTERS PLEASE)

Postal Orders should be crossed and made payable to Data Publications Ltd.

*Overseas customers please pay by International Money Order.
All publications are obtainable through your local bookseller*

Data Publications Ltd., 57 Maida Vale, London W9 1SN

PLEASE MENTION THIS MAGAZINE WHEN WRITING TO ADVERTISERS