

# RADIO & ELECTRONICS CONSTRUCTOR

NOVEMBER 1980  
60p

## TREMOLO MODULATION UNIT



EASILY MADE CIRCUIT  
ADDS BRILLIANCE  
TO GUITARS, ORGANS  
AND ELECTRONIC MUSIC.



INDUCTIVE COUPLING TO  
M.W. RADIO - NO WIRES.


## COIL-COUPLED S-W- CONVERTER



19 TO 67 METRES

# DIRECT SUPPLY SERVICE TO READERS
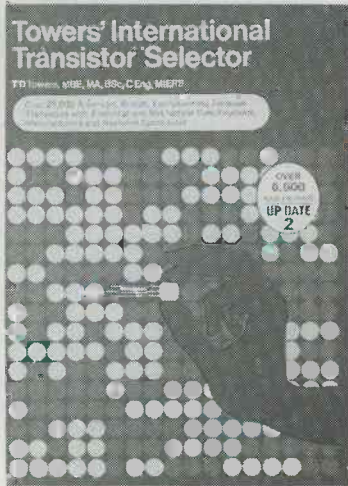
## TOWERS INTERNATIONAL TRANSISTOR SELECTOR (NEW REVISED EDITION)



This is dead!



Would this replace it?



If it takes you longer than 1 minute to find out all about these transistors then you need a copy of TOWER'S INTERNATIONAL TRANSISTOR SELECTOR. It's one of the most useful working books you will be offered this year. And probably the cheapest! In it, you will find a really international selection of 13,000 transistor types — British, Continental European, American and Japanese. And we think that they will solve 90% of your transistor enquiries.

Current and widely used obsolete types were carefully selected and arranged in Numero-Alphabetical order by an author who was uniquely qualified to do the job. With his compendium, all you need to know is the type number and you can learn all about a transistor's specification; who made it and where to contact them; or what to use to replace it.

Price £10.35 inc P&P

## TOWERS INTERNATIONAL FET SELECTOR



If you deal with field effect transistors, or fet's — whether as a student, a hobbyist, a circuit engineer, a buyer, a teacher or a serviceman — you often want data on a specific fet of which you know only the type number.

Specifications apart, you may be even more interested in where you can get the device in question. And perhaps more important still (particularly with obsolete devices), you may want guidance on a readily available possible substitute.

This fet compendium, a comprehensive tabulation of basic specification, offers information on:

1. Ratings
2. Characteristics
3. Case details
4. Terminal identifications
5. Applications use
6. Manufacturers
7. Substitution equivalents (both European and American)

The many fet's covered in this compendium are most of the more common current and widely-used obsolete types.

It is international in scope and covers fet's not only from the USA and Continental Europe, but also from the United Kingdom and the Far East (Japan).

Price £4.00 inc P&P

(Please allow 21 days for delivery)

**Tower's  
International  
Transistor  
Selector**

by **T. D. Towers**  
MBE, MA, BSc, C Eng, MIERE  
**£10.35**  
inc. post and packing

To:—DATA PUBLICATIONS LTD.  
57 MAIDA VALE  
LONDON W9 1SN

Please send me . . . . . copy/copies  
to the address shown below

NAME . . . . .

ADDRESS . . . . .

. . . . .

. . . . .

(Block capitals)

**Tower's  
International  
FET  
Selector**

by **T. D. TOWERS**  
MBE, MA, BSc, C Eng, MIERE  
**£4.00**  
inc. post and packing

To:—DATA PUBLICATIONS LTD.  
57 MAIDA VALE  
LONDON W9 1SN

Please send me . . . . . copy/copies  
to the address shown below

NAME . . . . .

ADDRESS . . . . .

. . . . .

. . . . .

(Block capitals)

# RADIO & ELECTRONICS CONSTRUCTOR

NOVEMBER 1980  
Volume 34 No. 3

Published Monthly

First published in 1947

Incorporating The Radio  
Amateur

Editorial and Advertising Offices  
57 MAIDA VALE LONDON W9 1SN

Telephone  
01-286 6141

Telegrams  
Databux, London

© Data Publications Ltd., 1980. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription: £9.50, Eire and Overseas £10.50 (U.S.A. and Canada \$25.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers, please pay by cheque or International Money Order.

**Technical Queries.** We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that queries cannot be answered over the telephone, they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

**Correspondence** should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

**Opinions** expressed by contributors are not necessarily those of the Editor or proprietors.

**Production** – Web Offset.

LINEAR SCALE OHMMETER – Suggested Circuit – by G. A. French	142
NEW CATALOGUE	144
RECENT PUBLICATIONS	145
NEWS AND COMMENT	146
CMOS COMBINATION SWITCH – Negligibly low stand-by current, Finger-tip operation by M. P. Horsey	148
TREMOLO MODULATION UNIT – Easily made circuit adds brilliance to guitars, organs and electronic music by I. M. Attrill	152
The INSTRUCTOR – A Practical Introduction to Microprocessors – Part 4 by Ian Sinclair	156
COIL-COUPLED S.W. CONVERTER by R. A. Penfold	161
SHORT WAVE NEWS – For DX Listeners by Frank A. Baldwin	166
TWO 20dB AMPLIFIERS – Part 2 by M. V. Hastings	168
NEW DEFENCE AID	171
RADIO DISTORTION FAULT – In Your Workshop	172
BOOK REVIEW	178
IN NEXT MONTH'S ISSUE	179
BASIC MEDIUM WAVE RADIO by T. F. Weatherley	180
TRADE NOTE – New Coils	182
SATISFACTORY SOLDERING – Notes for Newcomers by D. Snaith	184
BANDSPREADING Electronics Data No. 63	iii

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London W9 1SN.

The Radio & Electronics Constructor is printed by LSG Printers, Portland Street, Lincoln.

OUR NEXT ISSUE  
WILL BE PUBLISHED IN  
LATTER PART OF NOVEMBER

### MOTORS

1.5-6VDC Model Motors 22p. Sub. Min. 'Big Inch' 115VAC 3rpm Motors 32p. 6 volt standard cassette motors new £1.20. 8 track 12V Replacement Motors 55p. Cassette Motors 5-8VDC ex. equip. 70p. Geared Mains Motors (240V) 2.5 rpm 75p. 115VAC 4rpm Geared Motors 95p.

### SEMICONDUCTORS


LM340 80p. BY103 10p. 2N5062 100V 800mA SCR 18p. BX504 Opto Isolator 25p. CA3130 95p. TBA800 50p. 741 22p. 741S 35p. 723 35p. NE555 24p. 2N3773 £1.70. AD161/2 70p. ZN414 75p. BD238 28p. BD438 28p. IN4005 10 for 35p. TIL305 alpha numeric displays £2.50. TIL209 Red Leds 10 for 75p. Man3A 3mm Led Displays 40p.

### PROJECT BOXES

Sturdy ABS black plastic boxes with brass inserts and lid. 75 x 56 x 35mm 65p. 95 x 71 x 35mm 75p. 115 x 95 x 37mm 85p.

### MOTOROLA PIEZO CERAMIC TWEETERS

No crossover required

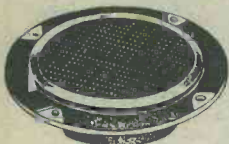

2.5" Direct Radiating Tweeter, maximum rating 25 volts R.M.S. 100 watts across 8 ohms. Freq. range 3.8kHz-28kHz, £3.65

### TOOL SALE

Small side cutters 5" insulated handles £1. Radiopliers, snipe nosed insulated handles £1. Heavy duty pliers insulated handles £1.10. Draper side cutters spring loaded £1.

### SWIVEL BASE VICES (with anvil)

With anvil, bench clamp, and plated parts, body smooth, lacquered finish. Jaw width 2", jaw opening 2 1/2" £5.55 D £1.20 P&P.

### MORSE KEYS

Beginners practice key £1.05. All metal full adjustable type. £2.60

### MINIATURE LEVEL METERS

1 Centre Zero 17 x 17mm 75p. 2 (scaled 0-10) 28 x 25mm 75p. 3 Grundig 40 x 27mm £1.25.

JVC NIVICO STEREO CASSETTE MECHANISM. Music centre type. Rev. counter, remote operation £13.50 and £1.00 p&p.

### JUMPER TEST LEAD SETS

10 pairs of leads with various coloured croc clips each end (20 clips) 90p per set.

### TRANSFORMERS

All 240VAC Primary (postage per transformer is shown after price). MINIATURE RANGE: 6-0-6V 100mA, 9-0-9V 75mA and 12-0-12V 50mA all 79p each (15p). 0-6, 0-6V, 280mA £1.20 (20p). 6V 500mA £1.20 (15p). 12V 2 amp £2.75 (45p). 15-0-15V 3 amp Transformer at £2.85 (54p). 30-0-30V 1 amp £2.85 (54p). 20-0-20V 2 amp £3.65 (54p). 0-12-15-20-24-30V 2 amp £4.75 (54p). 20V 2.5 amp £2.45 (54p).

### TRIAC/XENON PULSE TRANSFORMERS

1:1 (gpo style) 30p. 1:1 plus 1 sub. min. pcb mounting type 60p each.

### MICROPHONES

Min. tie pin. Omni, uses deaf aid battery (supplied), £4.95. ECM105 low cost condenser, Omni, 600 ohms, on/off switch, standard jack plug, £2.95. EM507 Condenser, uni, 600 ohms, 30-18kHz., highly polished metal body £7.92. DYNAMIC stick microphone dual imp., 600 ohms or 20K, 70-kHz., attractive black metal body £7.75. EM506 dual impedance condenser microphone 600 ohms or 50K, heavy chromed copper body, £12.95 CASSETTE replacement microphone with 2.5/3.5 plugs £1.35. INSERT Crystal replacement 35 x 10mm 40p. GRUNDIG electric inserts with FET pre-amp, 3-6VDC operation £1.00.

### LIGHT DIMMER

240VAC 800 watts max. wall mounting, has built in photo cell for automatic switch on when dark £4.50

### RIBBON CABLE

8 way single strand miniature 22p per metre.

### SPECIAL OFFER TAPE HEAD DEMAGNETIZER



240VAC with curved probe suitable for reel to reel or cassette machines, £1.95.

STEREO FM/GRAM TUNER AMPLIFIER CHASSIS, VHF and AM. Bass, treble and volume controls, Gram. 8-track inputs, headphone output jack, 3 watts per channel with power supply. £14.95 and £1.20 p&p (CCT supplied).

### MULTIMETER BARGAINS



Pocket Multimeter, 1,000 opv sensitivity. Ranges 1KV AC/DC Volts, 150ma DC current, resistance 0-2.5K, 0-100K, £4.50



20,000 opv., 1,000 volts AC/DC, DC current to 500ma, 5 ranges, resistance 4 ranges to 6 meg. Mirror scale, carrying handle, £9.75



2,000 OPV, 250 volts AC/DC, 0-100ma DC current, resistance to Meg in 2 ranges, mirror scale £5.75p.

40kHz Transducers. Rec/Sender £3.50 pair.

### TELEPHONE PICK UP COIL

Sucker type with lead and 3.5mm plug 62p.



Hand drill, double pinion with machine cut gears, 3/4", only £2.75p plus 50p p&p.

Dalo 33PC Etch Resist printed circuit maker pen, with spare tip, 79p.

### TERMS:

Cash with order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive.

S.A.E. for illustrated lists

### TMK500 MULTIMETER



TMK500 30,000 ohms per volt. 1KV AC/DC., D.C. Current to 12 amps. Resistance to 60 meg in 4 ranges, mirror scale, with built in buzzer for continuity testing £20.95

### YN360TR MULTIMETER



YN360 M/Meter. 20,000 ohms per volt. 1KV AC/DC volts, 250ma dc current, 4 resistance ranges to 20meg, also has built in transistor tester with leakage and gain ranges. £12.50

### CRIMPING TOOL

Combination type for crimping red blue and yellow terminations also incorporates a wire stripper (6 gauges) and wire cutter, with insulated handles only £2.30.

### POWER SUPPLIES

SWITCHED TYPE, plugs into 13 amp socket, has 3-4.5-6-7.5 and 9 volt DC out at either 100 or 40 0mA, switchable £3.45. HC244R STABILISED SUPPLY, 3-6-7.5-9 volts DC out at 400mA max., with on/off switch, polarity reversing switch and voltage selector switch, fully regulated to supply exact voltage from no load to max. current £4.95.

### AMPHENOL CONNECTORS

(PL259) PLUGS 47p. Chassis sockets 42p. Elbows PL259/SO239 90p. Double in line male connector (2XPL259) 65p. Plug reducers 13p. PL259 Dummy load, 52 ohms 1 watt with indicator bulb 95p.



Disco Strobe lights, adjustable speed, 80 joules, £22.50p.

### TOOLS

SOLDER SUCKER, plunger type, high suction, teflon nozzle, £4.99 (spare nozzles 69p each).

All Antex irons still at pre increase prices, order now as new stock will be going up next month.

Antex Model C 15 watt soldering irons, 240VAC £3.95

Antex Model CX 17 watt soldering irons, 240VAC £3.95

Antex Model X25 25 watt soldering irons, 240VAC £3.95

ANTEX ST3 iron stands, suits all above models £1.65

Antex heat shunts 12p each.

Servisol Solder Mop 50p each.

Neon Tester Screwdrivers 8" long 59p each.

Miyarna IC test clips 16 pin £1.95

### SWITCHES

Sub. miniature toggles: SPST (8 x 5 x 7mm) 42p.

DPDT (8 x 7 x 7mm) 55p.

DPDT centre off 12 x 11 x 9mm 77p. PUSH SWITCHES, 16mm x 6mm, red top, push to make 14p each, push to break version (black top) 16p each.

Mercury (Tilt) switches, 1" x 3/4" cylinder 35p each.

### RES. SUB BOX



Resistance Substitution Box. Swivelling disc provides close tolerance resistors of 36 values from 5 ohms to 4 meg. £3.95.



Signal Generator. Ranges 250Hz-100MHz in 6 Bands, 100MHz-300MHz (harmonics) internal modulator at 100Hz. R.F., output Max. 0.1vRMS. All transistorised unit with calibrating device. 220-240VAC operation, £48.95.

### TAPE HEADS

Mono cassette £1.75.

Stereo cassette £3.90.

Standard 8 track stereo £1.95 BSR MN1330 1/2 track 50p. BSR SRP90 1/2 track £1.95. TD10 tape head assembly - 2 heads both 1/2 track R/P with built in erase, mounted on bracket £1.20

# PROGRESSIVE RADIO

31 CHEAPSIDE, LIVERPOOL 2.  
ALL ORDERS DESPATCHED BY RETURN POST

# BI-PAK

**SEMICONDUCTORS**  
DEPT. RC11 PO Box, 6, WARE, HERTS.  
Visit our Shop at: 3 Baldock Street, Ware, Herts.

GIRO NO. 3887006  
TEL: 0920 3182  
TELEX: 817861

## EXPERIMENTOR BREADBOARDS

CONTINENTAL SPECIALITIES CORPORATION  
FROM 

No soldering breadboards. Simply plug components in and out of letter number identified, Nickel-alloy contact holes. Start small and simply snap-lock boards together to build a breadboard of any size.

All EXP Breadboards have two bus-bars as an integral part of the board. If you need more than two buses, simply snap on 4 more bus-bars with the aid of an EXP 48.

EXP 325 The ideal breadboard for 1 chip circuits. Accepts 8, 14, 16 and up to 22-pin IC's

ONLY £1.84  
48mm (1.9")

EXP 350 270 contact points with two 20-point bus-bars.  
ONLY £3.62  
91mm (3.6")

EXP 300 550 contacts with two 40-point bus-bars.  
ONLY £6.61  
152mm (6.0")

EXP 650 For Micro-processors.  
ONLY £4.14  
91mm (3.6")

EXP 48  
ONLY £2.65  
152mm (6.0")

EXP 600 As EXP 300 but accepts 24 pin DIL and over.  
ONLY £7.25  
152mm (6.0")

All EXP 300 Breadboards mix and match with 600 series.

## ANTEX IRONS

1943 15 watt quality soldering Iron with 3/32" bit £5.12

1944 Replacement element for 1943 £2.33

1944 Iron coated bit 3/32" for 1943 £0.58

1945 Iron coated bit 1/8" for 1943 £0.58

1946 Iron coated bit 3/16" for 1943 £0.58

1948 18 watt iron with iron coated bit £5.12

1952 Replacement element for 1948 £2.22

1949 Iron coated bit 3/32" for 1948 £0.58

1950 Iron coated bit 1/8" for 1948 £0.58

1951 Iron coated bit 3/16" for 1948 £0.58

1931 X25 25 watt iron, ceramic shaft and another shaft of stainless steel to ensure strength £6.12

1935 Replacement element for 1931 £2.05

1932 Iron coated bit 1/8" for 1931 £0.58

1933 Iron coated bit 2/16" for 1931 £0.58

1934 Iron coated bit 3/32" for 1931 £0.58

1953 SK1 soldering Kit - contains 15 watt soldering iron with 3/16" bit plus two spare bits, a reel of solder, heat-sink and a booklet 'How to Solder' £7.28

1939 ST3 Iron stand made from high grade bakelite chrome plated steel spring, suit all models - Includes accommodation for six bits and two sponges to keep the iron bits clean £1.89

1724 Model MLX as X25 iron but 12 volts £5.59

## CASES AND BOXES

VERO plastic case box. These boxes consist of top and bottom sections which include fixings points for horizontal mounting PC boards/chassis plates, the two sections are held together by four screws which enter through the base and are concealed by plastic feet.

No.	Length	Width	Height	Price
170	140mm	40mm	205mm	£4.35
171	140mm	75mm	205mm	£4.85
172	140mm	110mm	205mm	£6.30

INSTRUMENT CASES in two sections vinyl covered top and sides, aluminium bottom, front and back.

No.	Length	Width	Height	Price
155	9in	5 1/2in	2in	£2.01
156	11in	6in	3in	£2.10
157	6in	4 1/2in	1 1/2in	£1.93
158	9in	5 1/2in	2 1/2in	£2.59

ALUMINIUM BOXES made from bright anodized, folded construction each box complete with half inch deep lid and screws.

No.	Length	Width	Height	Price
159	5 1/2in	2 1/2in	1 1/2in	£0.98
160	4in	4in	1 1/2in	£0.98
161	4in	2 1/2in	1 1/2in	£0.98
162	5 1/2in	4in	1 1/2in	£1.10
163	4in	2 1/2in	2in	£0.98
164	4in	2in	1in	£0.67
165	7in	5in	2 1/2in	£1.54
166	8in	6in	3in	£1.98
167	6in	4in	2in	£1.32

SLOPE front aluminium boxes with black vinyl base and sides & aluminium back, top & front - strong construction easily accessible.

No.	2 1/2in	5 1/2in	2 1/2in	12in	3 1/2in	8in	Price
169							£5.45
168							£8.21

## AUDIO MODULES

### AMPLIFIERS

AL10	3 watt Audio Amplifier Module 22-32v supply	£1.63
AL20	5 watt Audio Amplifier Module 22-32v supply	£4.11
AL30A	7-10 watt Audio Amplifier Module 22-32v supply	£4.78
AL50	15-25 watt Audio Amplifier Module 30-50v supply	£5.92
AL80	35 watt Audio Amplifier Module 40-60v supply	£9.28
AL120	50 watt Audio Amplifier Module 50-70v supply	£15.11
AL250	125 watt Audio Amplifier Module 50-80v supply	£22.54

### STEREO PRE-AMPLIFIERS

PA12	Supply voltage 22-32v Input sensitivity 300mv suit AL10/AL20/AL30	£9.83
PA100	Supply voltage 24-36v Inputs - Tape, Tuner, Mag P.U., Suit AL60/AL80	£20.38
PA200	Supply voltage 35-70v Inputs - Tape, Tuner, Mag P.U., Suit: AL80/AL120/AL250	£20.98

### MONO PRE-AMPLIFIERS

MM100	Supply voltage 40-65v Inputs: Mag. P.U., Tape Microphone Max. output 600mv	£14.29
MM100G	Supply voltage 40-65v Inputs: 2 Gullars Microphones Max. output 600mv	£14.29

### POWER SUPPLIES

PS12	24v Supply suit 2 - AL10, 2 - AL20, 2 - AL30 & PA12/8-450	£1.90
SPM80	33v Stabilised supply - suit 2 - AL60, PA100 to 15 watts	£5.57
SPM120/45	45v Stabilised supply - suit 2 - AL60, PA100 to 25 watts	£7.34
SPM120/55	55v Stabilised supply - suit 2 - AL80, PA200	£7.34
SPM120/65	65v Stabilised supply - suit 2 - AL120, PA200, 1 - AL250, PA200	£7.34
SG30	150-15 Stabilised power supply for 2 - GE100MKII	£4.37

### MISCELLANEOUS

MPA30	Stereo Magnetic Cartridge Pre-Amplifier Input 3.5mv Output 100mv	£3.76
S.450	Stereo FM Tuner Supply Voltage 20-30v - Varicap tuned	£2.39
STEREO30	Complete 7 watt per Channel Stereo Amplifier Board - Includes amp, pre-amp, power supply, front panel, knobs etc. - requires 250 Transformer	£24.25
BP124	5 watt 12v max - Siran Alarm Module	£4.43
GE100MkII	10 channel mono-graphic equaliser complete with sliders and knobs	£25.45
VPS30	Variable regulated stabilised power supply 2-30v 0-2amps	£8.74

### TRANSFORMERS

No.	Rating	P&P	Price
2034	1.7 amp 35v suit SPM80	£8.21	£1.21
2035	2 amp 55v	£7.30	£1.47
2036	750mA 17v suit PS12	£3.68	
2040	1.5 amp 0-45v-65v suit SPM120/45, SPM120/55	£5.98	£1.21
2041	2 amp 0-55v-65v suit SPM120/55, SPM120/65	£7.82	£1.47
2050	1 amp 0-20v suit Stereo 30	£3.74	£0.75
1725	150mA 15-0-15v suit SG30	£2.04	

### ACCESSORIES

139	Teak Cabinet suit Stereo 30, 320 - 235 - 81mm	£8.06
140	Teak Cabinet suit STA 15 425 - 290 - 95mm	£9.78
FP100	Front Panel for PA100 & PA200	£2.07
BP100	Back Panel for PA100 & PA200	£2.05
GE100FP	Front Panel for one GE100MKII	£2.05
2240	Kit of parts including Teak Cabinet, chassis socket, knobs to build 15 watt stereo amplifier (Does not include modules)	£22.94

### SPECIAL OFFERS

MINIDRILL 12v hand held battery-operated mini drill, 7,500 r.p.m. Collet chuck. Ideal for drilling printed circuits or model making. No. 1402. Complete with 2 drills 1 and 15. £8.33

TRANSFORMER 240v Primary 0-20v at 2A Secondary. By removing 5 turns for each volt from the secondary winding, any voltage up to 20v at 2A is obtainable. Ideal for the experimenter. No. 2042. £15.0 + 50p P & P

ANTEX MLX Soldering Iron. Sturdy 25 watt iron complete with 44 metres of 2 core cable. Works off a 12 volt battery. Ideal for Car, Boat, Caravan. No. 1724. £5.29

### METAL FOIL CAPACITOR PAKS

16204 - Containing 50 metal foil capacitor like Mullard C280 series. Mixed values ranging for 01uf - 2.2uf. Complete with identification sheet £1.38

### TRIACS

2 amp	T05 case	10 amp	
100	TR12A/100	Price	TR110A/100
200	TR12A/200	£0.38	£0.88
400	TR12A/400	£0.59	£1.08
			TR110A/400
			£1.29
6 amp		10 amp	
100	TR16A/100	Price	TR110A/400P
200	TR16A/200	£0.59	£1.29
400	TR16A/400	£0.78	
			DIACS
			BR100 £0.23 D32 £0.23

## SILICON RECTIFIERS

200mA	IS820 50V	£0.07	3 Amp	IN5400 50V	£0.16
	IS921 100V	£0.05		IN5401 100V	£0.17
	IS922 150V	£0.08		IN5402 200V	£0.18
	IS923 200V	£0.10		IN5404 400V	£0.20
	IS924 300V	£0.12		IN5406 600V	£0.24
				IN5407 800V	£0.29
				IN5408 1000V	£0.35
1 Amp	IN4001 50V	£0.051	10 A.p	IS10/5 50V	£0.22
	IN4002 100V	£0.06		IS10/100 100V	£0.24
	IN4003 200V	£0.07		IS10/200 200V	£0.26
	IN4004 400V	£0.08		IS10/400 400V	£0.40
	IN4005 600V	£0.09		IS10/600 600V	£0.48
	IN4006 800V	£0.10		IS10/800 800V	£0.59
	IN4007 1000V	£0.12		IS10/1000 1000V	£0.68
				IS10/1200 1200V	£0.79

1.5 Amp	IS015 50V	£0.10	30 Amp	IS30/50 50V	£0.64
	IS020 100V	£0.12		IS30/100 100V	£0.79
	IS021 200V	£0.13		IS30/200 200V	£1.07
	IS023 400V	£0.15		IS30/400 400V	£1.44
	IS025 600V	£0.16		IS30/600 600V	£2.02
	IS027 800V	£0.18		IS30/800 800V	£2.33
	IS029 1000V	£0.23		IS30/1000 1000V	£2.66
	IS031 1200V	£0.29		IS30/1200 1200V	£3.31

60 Amp	IS70/50 50V	£0.86		IS70/400 400V	£2.59
	IS70/100 100V	£0.97		IS70/800 800V	£2.88
	IS70/200 200V	£1.38		IS70/1000 1000V	£3.45

## THYRISTORS

600ma	TO 18 Case	7 amp	TO 48 Case
Volts No.	Price	Volts No.	Price
10 THY600/10	£0.17	50 THY7A/50	£0.55
20 THY600/20	£0.18	100 THY7A/100	£0.58
30 THY600/30	£0.23	200 THY7A/200	£0.66
50 THY600/50	£0.25	400 THY7A/400	£0.71
100 THY600/100	£0.29	600 THY7A/600	£0.90
200 THY600/200	£0.44	800 THY7A/800	£1.06
400 THY600/400	£0.51		

1 amp	TO 66 Case	10 amp	TO 48 Case
Volts No.	Price	Volts No.	Price
50 THY1A/50	£0.30	50 THY10A/50	£0.59
100 THY1A/100	£0.32	100 THY10A/100	£0.66
200 THY1A/200	£0.37	200 THY10A/200	£0.71
400 THY1A/400	£0.44	400 THY10A/400	£0.81
600 THY1A/600	£0.52	600 THY10A/600	£1.14
800 THY1A/800	£0.67	800 THY10A/800	£1.40

3 amp	TO 66 Case	30 amp	TO 94 Case
Volts No.	Price	Volts No.	Price
50 THY3A/50	£0.32	50 THY30A/50	£1.38
100 THY3A/100	£0.35	100 THY30A/100	£1.64
200 THY3A/200	£0.38	200 THY30A/200	£1.87
400 THY3A/400	£0.48	400 THY30A/400	£2.06
600 THY3A/600	£0.58	600 THY30A/600	£4.03
800 THY3A/800	£0.75		

5 amp	TO 66 Case	No.	Price
Volts No.	Price		
50 THY5A/50	£0.41		
100 THY5A/100	£0.52	BT101/500R	£0.92
200 THY5A/200	£0.58	BT102/500R	£0.92
400 THY5A/400	£0.66	BT106	£1.44
600 THY5A/600	£0.78	BT107	£1.07
800 THY5A/800	£0.93	BT108	£1.13

5 amp	TO 220 Case	2N3228	Price
Volts No.	Price		
400 THY5A/400P	£0.86	2N3228	£0.81
600 THY5A/600P	£0.79	BTX30/50L	£0.98
800 THY5A/800P	£0.93	BTX30/400L	£0.53
		C106/4	£0.69
		BT116	£1.73

## ZENER DIODES

400 mw (Bzy88) D007. Glass encapsulated range of voltages available. 1.3v, 2.2v, 2.7


# DO YOU EVER WISH YOU HAD A FEW MORE HANDS?

ABSONGLEN LIMITED  
ANNOUNCE THE NEW
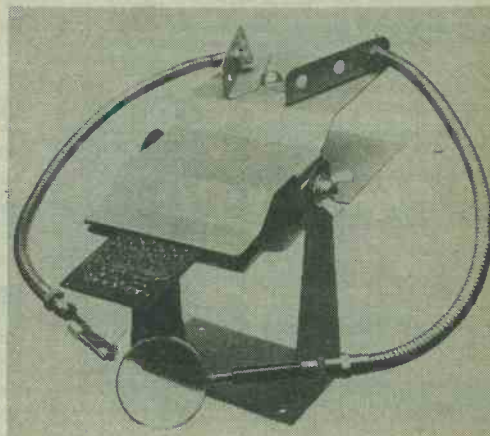
## MINIBENCH\* MK II SYSTEM



- Just a squeeze needed to clamp or release the circuit board.
- Adjustable minimum jaw aperture.
- Jaws flip over for work on either side of circuit board.
- Rubber lined jaws for circuit board protection and maximum grip.
- Single wing nut adjusts friction control of jaw setting.
- Crocodile clips mounted on flexi-arms hold components exactly where needed.
- Crocodile clip can be used as a heat shunt.
- Lens similarly mounted is ideal for close work and spotting those solder bridges.
- Flexi-arms are mounted on the jaw assembly to keep station with circuit board.
- 6 separate flexi-arm mounting positions.
- A typical configuration would include 2 flexi-arms with clips and one with lens.
- Attractive two tone stove enamelled finish.
- Built to last a lifetime.



PATENTED

SEE US ON STAND 21 at the ARRA Exhibition at the Granby Halls,  
LEICESTER, on the 6th, 7th, 8th NOVEMBER.

MINIBENCH MKII £12.95


FLEXI-ARMS WITH CLIPS £4.75 †

FLEXI-ARMS WITH LENS £5.75 † P. & P. £2.00

ABSONGLEN LTD. (Dept. REC) THE FORGE, STAPLOW, Nr. LEDBURY HEREFORDSHIRE HR8 1NP

\* TRADE MARK † PRICE APPLICABLE TO MINIBENCH PURCHASERS ONLY

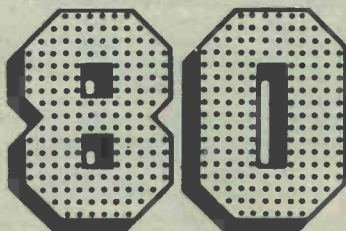COMPUTERS AUDIO RADIO MUSIC LOGIC TEST GEAR CB GAMES KITS



26th Nov — WEDNESDAY — 10am-6pm  
27th Nov — THURSDAY — 10am-8pm  
28th Nov — FRIDAY — 10am-6pm  
29th Nov — SATURDAY — 10am-6pm  
30th Nov — SUNDAY — 10am-4pm

COMPONENTS DEMONSTRATIONS SPECIAL OFFERS MAGAZINES BOOKS

### Royal Horticultural Halls Elverton Street

### Westminster London SW1

### November 26-30 1980

### It's all at Breadboard '80

This is **the** exhibition for the electronics enthusiast. From November 26-30 there is only one place in the universe for the electronics enthusiast to be — Breadboard '80, at the Royal Horticultural Hall in London. The majority of leading companies will be exhibiting, including all the top monthly magazines in the field. There will be demonstrations on most stands and many feature special offers that are EXCLUSIVE to Breadboard!

All aspects of this fascinating field are catered for, from CB to home computing, so whether you want to buy a soldering iron or a synthesiser — or just keep up to date with your hobby — don't miss Breadboard '80.

AVOID QUEUES — GET ADVANCE TICKETS

Send to: Advance Tickets, Modmags Ltd,  
145 Charing Cross Rd., London WC2H 0EE

Please send: ..... tickets @ £1.50

..... tickets @ £1.00 (Student/Child/OAP)

TO: .....

I enclose P.O./Cheque for £ .....

# PRIME COMPONENTS LOW PRICES

All our micro chips are at micro prices. Don't be fooled by low prices. We do not offer for sale sub-spec or rebranded devices. All our parts are guaranteed new, first quality, factory prime, full spec devices. It is also our policy to offer you the best of new devices that become available and these are featured regularly. Prices are exclusive of p&p and VAT - please refer to "Ordering Information" before ordering. Official orders from Schools, Colleges, Universities and Gov. Authorities accepted.

**DTL**

930	55p
935	65p
937	55p
944	65p
946	55p
957	55p
962	55p
9099	90p

**7400**

7400	11p
7401	12p
7402	12p
7403	13p
7404	17p
7409	18p
7410	40p
7412	18p
7413	28p
7420	16p
7430	18p
7432	25p
7440	16p
7448	75p
7473	32p
7474	32p
7475	40p
7476	40p
7490	35p
7492	50p
7493	40p
7496	45p
74121	35p
74123	45p
74154	80p
74157	55p
74122	45p
74125	50p
74135	100p
74196	100p
74283	140p
74290	120p
74365	90p
74366	90p

**74LS**

74LS00	12p
74LS01	12p
74LS04	15p
74LS06	20p
74LS10	19p
74LS11	30p
74LS12	30p
74LS14	60p
74LS15	38p
74LS20	19p
74LS30	19p
74LS32	25p
74LS40	25p
74LS42	56p
74LS47	78p
74LS48	85p
74LS49	99p
74LS73	30p
74LS74	30p
74LS75	39p
74LS86	39p
74LS90	40p
74LS107	40p
74LS123	69p
74LS125	50p
74LS132	78p
74LS138	69p
74LS151	75p
74LS153	75p
74LS155	65p
74LS161	78p
74LS163	90p
74LS164	90p
74LS168	180p
74LS174	99p
74LS175	99p
74LS195	87p
74LS221	110p
74LS244	175p
74LS245	32p
74LS251	120p
74LS257	110p
74LS280	95p
74LS293	120p
74LS366	57p
74LS373	170p
74LS374	170p
74LS377	180p
74LS377	180p
74LS393	135p
74LS490	140p
74LS570	260p

**74C**

74C20	30p
74C76	60p
74C85	145p
74C97	125p
74C98	125p
74C107	100p
74C180	110p
74C181	145p
74C182	145p
74C182	145p
74C183	175p
74C183	175p
74C194	175p
74C195	175p
74C903	45p

**CMOS**

4001	19p
4002	19p
4006	75p
4007	19p
4008	57p
4009	35p
4010	45p
4011	20p
4012	24p
4013	NE555
4014	NE565
4015	75p
4030	35p
4016	80p
4017	60p
4018	76p
4019	42p
4020	85p
4021	100p
4022	88p
4023	22p
4024	50p
4025	20p
4026	130p
4027	45p
4028	75p
4029	80p
4030	50p
4031	195p
4033	145p
4035	104p
4036	290p
4037	105p
4038	110p
4039	290p

**MEMORIES**

2114L 300 NS	250p
2114L 450 NS	225p
4116 150 NS	375p
4116 200 NS	275p
450 NS (1k x 4) CMOS RAM	550p
4315 (4k x 1) CMOS RAM	895p
450 NS	395p

**EPROMS**

1702A	450p
2708 450 NS	395p
2716 5V 450 NS	595p
2532 32K 450 NS	1995p

**UARTS**

AY-5-1013A	325p
AY-3-1015D	398p
IM6402 IPL	425p

**CHARACTER GENERATOR**

RO-3-2513 UC	450p
--------------	------

**KEYBOARD ENCODER**

AY-5-2376	795p
-----------	------

**FLOPPY DISK CONTROLLERS**

FD1771 B-01 S/D Inverted Bus	2995p
FD1791 B-01 D/D Inverted Bus	4995p
FD1792 B-01 S/D Inverted Bus	3495p
FD1793 B-01 D/D True Bus	5495p
FD1794 B-01 S/D True Bus	3495p
FD1795 B D/D Inverted Bus, side select	5995p
FD1797 B D/D True Bus, side select	5995p

**SUPPORT DEVICES**

6520	495p
6522	795p
6523	795p
6524	995p
6551	1095p
6810	375p
6820	425p
6821	425p
6860	425p
6862	425p
8212	395p
8214	450p
8216	395p
8253	375p
8255	495p
8257	1050p
8259	1325p
MC 144 12VL	350p
280 P10	595p
280 CTC	595p
280A P10	695p
280A CTC	695p
280 DMA	1995p
280 DMA	2495p
280 S10/0	2995p
280 S10/1	3495p
280 S10/1	2995p
280 S10/2	3495p

**74C**

74C20	30p
74C76	60p
74C85	145p
74C97	125p
74C98	125p
74C107	100p
74C180	110p
74C181	145p
74C182	145p
74C182	145p
74C183	175p
74C183	175p
74C194	175p
74C195	175p
74C903	45p

**LINEAR IC's**

AY-3-1350	695p
AY-3-8910	850p
709	30p
723	33p
741	71p
ICL7106	575p
ICL7107	695p
ICL7038	295p
ICM7236A	1875p
ICM7236	1675p
ICM7555	80p
LM301AM	50p
LM311	50p
LM318	75p
LM324	45p
LM339	45p
LM380	65p
LM1496	65p
LM1871	550p
LM1872	550p
LM3990	50p
LM3914	225p
LM3915	225p
LM13500	125p
NE555	18p
NE565	50p
RC4135	85p
SN76477N	175p
TBA810DAS	86p
TL071	55p
TL074	130p
TL082	75p
TL084	110p
TL490	175p
XR2206	325p
XR2207	375p

**DIL SWITCHES**

4 pole	89p
6 pole	115p
8 pole	140p
10 pole	175p

**LOW PROFILE SOCKETS BY TEXAS**

8 pin	7p	18 pin	15p	24 pin	22p
14 pin	9p	20 pin	18p	28 pin	25p
16 pin	10p	22 pin	22p	40 pin	28p

**CPU'S**

6502	795p
6505	795p
6505	795p
6800	695p
6802	995p
8080A	525p
8085A	1095p
Z80	795p
Z8001	1250p
Z8002	950p
WD9000B	1990p

**VOLTAGE REGULATORS**

7805/7812	55p
7905/7912	65p
7815/7805	575p
7812/7805	625p

**BIPOLAR PROMS**

93448 512 x 8 40 NS	p.o.a.
93453 1k x 4 40 NS p.o.a.	
93451 1k x 8 45 NS p.o.a.	
93511 2k x 8 50 NS p.o.a.	

**CHARACTER GENERATOR**

RO-3-2513 UC	450p
--------------	------

**KEYBOARD ENCODER**

AY-5-2376	795p
-----------	------

**FLOPPY DISK CONTROLLERS**

FD1771 B-01 S/D Inverted Bus	2995p
FD1791 B-01 D/D Inverted Bus	4995p
FD1792 B-01 S/D Inverted Bus	3495p
FD1793 B-01 D/D True Bus	5495p
FD1794 B-01 S/D True Bus	3495p
FD1795 B D/D Inverted Bus, side select	5995p
FD1797 B D/D True Bus, side select	5995p

**SUPPORT DEVICES**

6520	495p
6522	795p
6523	795p
6524	995p
6551	1095p
6810	375p
6820	425p
6821	425p
6860	425p
6862	425p
8212	395p
8214	450p
8216	395p
8253	375p
8255	495p
8257	1050p
8259	1325p
MC 144 12VL	350p
280 P10	595p
280 CTC	595p
280A P10	695p
280A CTC	695p
280 DMA	1995p
280 DMA	2495p
280 S10/0	2995p
280 S10/1	3495p
280 S10/1	2995p
280 S10/2	3495p

**74C**

74C20	30p
74C76	60p
74C85	145p
74C97	125p
74C98	125p
74C107	100p
74C180	110p
74C181	145p
74C182	145p
74C182	145p
74C183	175p
74C183	175p
74C194	175p
74C195	175p
74C903	45p

**INTERFACE LINEAR**

MC1488	90p
MC1489	90p
DM8123	125p
75150	125p
75154	125p
75182	195p
75322	250p
75324	325p
75325	325p
75351	350p
75355	295p
75451	50p
75491/2	75p
8726	175p
8728	175p
8795	175p
8797	175p

**ISOLATORS**

IL209	9p
TL121	13p
TL1212	15p
TL1220	12p
TL1222	15p
TL1224	18p

**MEMORIES**

2114 L 450 NS	225p
2114 L 300 NS	250p
4116 150 NS	375p
4116 200 NS	275p
450 NS (1k x 4) CMOS RAM	550p
4315 (4k x 1) CMOS RAM	895p
450 NS	395p

**EPROMS**

1702A	450p
2708 450 NS	395p
2716 5V 450 NS	595p
2532 32K 450 NS	1995p

**UARTS**

AY-5-1013A	325p
AY-3-1015D	398p
IM6402 IPL	425p

**CHARACTER GENERATOR**

RO-3-2513 UC	450p
--------------	------

**KEYBOARD ENCODER**

AY-5-2376	795p
-----------	------

**FLOPPY DISK CONTROLLERS**

FD1771 B-01 S/D Inverted Bus	2995p
FD1791 B-01 D/D Inverted Bus	4995p
FD1792 B-01 S/D Inverted Bus	3495p
FD1793 B-01 D/D True Bus	5495p
FD1794 B-01 S/D True Bus	3495p
FD1795 B D/D Inverted Bus, side select	5995p
FD1797 B D/D True Bus, side select	5995p

**SUPPORT DEVICES**

6520	495p
6522	795p
6523	795p
6524	995p
6551	1095p
6810	375p
6820	425p
6821	425p
6860	425p
6862	425p
8212	395p
8214	450p
8216	395p
8253	375p
8255	495p
8257	1050p
8259	1325p
MC 144 12VL	350p
280 P10	595p
280 CTC	595p
280A P10	695p
280A CTC	695p
280 DMA	1995p
280 DMA	2495p
280 S10/0	2995p
280 S10/1	3495p
280 S10/1	2995p
280 S10/2	3495p

**74C**

74C20	30p
74C76	60p
74C85	145p
74C97	125p
74C98	125p
74C107	100p
74C180	110p
74C181	145p
74C182	145p
74C182	145p
74C183	175p
74C183	175p
74C194	175p
74C195	175p
74C903	45p

**INTERFACE LINEAR**

MC1488	90p
MC1489	9

# AND THERE'S MORE WHERE THIS CAME FROM

It's a long time since one of our adverts was presented in 'list' form - but simply because we do not try to squeeze this lot in every time doesn't mean that it's not available. Our new style price list (now some 40 pages long) includes all this and more, including quantity prices and a brief description. The kits, modules and specialized RF components - such as TOKO coils, filters etc. are covered in the general price list - so send now for a free copy (with an SAE please). Part 4 of the catalogue is due out now (incorporating a revised version of pt.1).

LINEAR ICs - NUMERIC LISTINGS		TTL N and LSN		VARICAP		TRANSISTORS		CAPACITORS			
TBA120S	1.00	KB4413	1.95	7443N	1.15	74LS112	0.38	74LS169	2.00	AUDIO DEVICES	
L200	1.95	KB4417	1.80	7444N	1.12	74LS113	0.38	74170N	2.30	All 5mm or less spacing	
U237B	1.28	TD4420	2.25	7400N	0.13	74LS114	0.38	74LS170	2.00	CERAMIC 50V	
U247B	1.28	KB4420B	1.09	74LS00	0.20	7446N	0.94	74LS174	1.20	2P2, 3P3, 4P7, 6P6	
U257B	1.28	KB4423	2.30	7401N	0.13	74LS47	0.89	74120N	1.15	8P2, 10P, 15P, 18P...0.04	
U267B	1.28	KB4424	1.65	74LS01	0.20	7448N	0.56	74121N	0.42	22P, 27P, 33P, 47P	
LM301H	0.67	KB4431	1.95	7402N	0.14	74LS48	0.99	74122N	0.46	56P, 68P, 82P, 100P...0.05	
LM301N	0.30	KB4432	1.95	74LS02	0.20	74LS49	0.99	74123N	0.73	150P, 220P, 270P	
LM308H	0.96	KB4433	1.52	7403N	0.14	74LS51	0.24	74124N	1.75	330P, 390P, 470P...0.055	
LM308N	0.65	KB4436	2.53	74LS03	0.20	74LS52	0.24	74125N	0.38	1N0, 2N2, 3N3, 4N7...0.06	
LM339N	0.66	KB4437	1.75	7404N	0.14	74LS54	0.24	74LS125	0.44	10N (0.01uF)...0.005	
LM348N	1.86	KB4438	2.22	74LS04	0.24	74LS55	0.24	74LS126	0.44	BC416 0.07	
LF351N	0.38	KB4441	1.35	7405N	0.18	74LS56	0.24	74LS128	0.74	BC416 0.08	
LF353N	0.76	KB4445	1.29	74LS05	0.26	7406N	0.17	74128N	0.73	BC509 0.08	
LM374N	3.75	KB4446	2.75	7407N	0.38	74LS63	1.24	74129N	1.05	BC509 0.12	
LM380N-14	1.00	KB4448	1.65	7408N	0.17	7470N	0.28	74LS132	0.78	BC556 0.12	
LM380N-8	1.00	NE5044N	2.26	74LS08	0.24	7472N	0.28	74LS136	0.40	BC556 0.12	
LM381N	1.81	NE5532N	1.85	7409N	0.17	7473N	0.32	74LS138	0.60	BC556 0.12	
ZN419CE	1.95	SD6000	3.75	74LS09	0.24	74LS73	0.38	74141N	0.56	BC639 0.22	
NE544N	1.80	SL6270	2.03	74LS09	0.24	74LS73	0.38	74142N	2.65	BC640 0.22	
NE555N	0.30	SL6310	2.03	7410N	0.15	7474N	0.27	74143N	3.12	25C1775 0.18	
NE556N	0.50	SL6600	3.75	74LS10	0.24	74LS74	0.28	74LS139	1.10	25N872A 0.14	
NE556N	3.50	SL6640	2.75	7411N	0.20	7475N	0.38	74LS140	1.10	25P666A 0.30	
NE556N	4.05	SL6690	2.75	74LS11	0.24	7476N	0.37	74LS141	1.50	25S646A 0.40	
NE564N	4.29	SL6700	2.35	7412N	0.17	74LS76	0.38	74147N	1.75	25S648A 0.40	
NE565N	1.00	ICL8038CC	4.50	7413N	0.30	74LS78	0.38	74148N	1.09	25T076 0.45	
NE566N	1.60	MSL9362	1.75	7414N	0.51	7480N	0.48	74LS247	0.93	25T076 0.45	
NE570N	3.85	MSL9363	1.75	74LS15	0.24	7481N	0.86	74LS257	1.08	25T076 0.45	
SL624	3.28	HALL1211	1.95	7416N	0.30	7482N	0.69	74LS279	0.52	25Z546 0.19	
TBA651	1.81	HALL1223	2.15	7417N	0.30	7485N	1.04	74LS283	1.20	25Z546 0.19	
UA709HC	0.64	HALL1225	1.45	7420N	0.16	74LS85	0.99	74LS293	0.95	25Z547 0.19	
UA709PC	0.36	HALL2002	1.45	7420N	0.16	74LS85	0.99	74LS365	0.49	25Z547 0.19	
UA710HC	0.65	HALL2017	0.80	7420N	0.16	74LS85	0.99	74LS366	0.49	25Z547 0.19	
UA710PC	0.59	HALL2102	1.95	7420N	0.16	74LS85	0.99	74LS367	0.43	25Z547 0.19	
UA714HC	0.66	HALL2411	1.20	7420N	0.16	74LS85	0.99	74LS368	0.49	25Z547 0.19	
UA714CN	0.27	HALL2412	1.55	7420N	0.16	74LS85	0.99	74LS374	1.80	25Z547 0.19	
UA747CN	0.70	LF13741	0.33	7420N	0.16	74LS85	0.99	74LS377	1.95	25Z547 0.19	
UA748CN	0.36	SM76660N	0.80	7420N	0.16	74LS85	0.99	74LS379	1.30	25Z547 0.19	
UA753	2.44			7420N	0.16	74LS85	0.99	74LS393	1.40	25Z547 0.19	
UA758	2.35			7420N	0.16	74LS85	0.99			25Z547 0.19	
TBA810AS	1.09	SAAL1056	3.75	7420N	0.16	74LS85	0.99			25Z547 0.19	
TBA820M	0.75	SAAL1058	3.35	7420N	0.16	74LS85	0.99			25Z547 0.19	
TC9494	2.80	SAAL1059	3.35	7420N	0.16	74LS85	0.99			25Z547 0.19	
TD1102B	1.11	ICL8038CC	4.50	7420N	0.16	74LS85	0.99			25Z547 0.19	
TD1102N	2.11	ICL8038CC	4.50	7420N	0.16	74LS85	0.99			25Z547 0.19	
TD1105A	1.45	ICL8038CC	4.50	7420N	0.16	74LS85	0.99			25Z547 0.19	
TD11062	1.95	ICL8038CC	4.50	7420N	0.16	74LS85	0.99			25Z547 0.19	
TD11072	2.69	ICL8038CC	4.50	7420N	0.16	74LS85	0.99			25Z547 0.19	
TD11074A	5.04	ICL8038CC	4.50	7420N	0.16	74LS85	0.99			25Z547 0.19	
TD11083	1.95	ICL8038CC	4.50	7420N	0.16	74LS85	0.99			25Z547 0.19	
TD11090	3.05	ICL8038CC	4.50	7420N	0.16	74LS85	0.99			25Z547 0.19	
HALL137	1.20	ICL8038CC	4.50	7420N	0.16	74LS85	0.99			25Z547 0.19	
HALL196	2.00	ICL8038CC	4.50	7420N	0.16	74LS85	0.99			25Z547 0.19	
HALL197	1.00	ICL8038CC	4.50	7420N	0.16	74LS85	0.99			25Z547 0.19	
TD11220	1.40	ICL8038CC	4.50	7420N	0.16	74LS85	0.99			25Z547 0.19	
LM1303	0.99	ICM7106CP	9.55	7420N	0.16	74LS85	0.99			25Z547 0.19	
LM1307	1.55	ICM7107CP	9.55	7420N	0.16	74LS85	0.99			25Z547 0.19	
MCI1310P	1.90	ICM7216B	19.25	7420N	0.16	74LS85	0.99			25Z547 0.19	
MCI1330	1.20	ICM7217A	9.55	7420N	0.16	74LS85	0.99			25Z547 0.19	
MCI1350	1.20	SP8629	3.85	7420N	0.16	74LS85	0.99			25Z547 0.19	
HALL370	1.90	SP8647	6.00	7420N	0.16	74LS85	0.99			25Z547 0.19	
HALL388	2.75	95H90PC	6.00	7420N	0.16	74LS85	0.99			25Z547 0.19	
TD11490	1.86	HD10551	2.45	7420N	0.16	74LS85	0.99			25Z547 0.19	
MCI496P	1.25	HD44015	4.45	7420N	0.16	74LS85	0.99			25Z547 0.19	
SL1610P	1.60	HD12009	6.00	7420N	0.16	74LS85	0.99			25Z547 0.19	
SL1611P	1.60	HD4752	8.00	7420N	0.16	74LS85	0.99			25Z547 0.19	
SL1612P	1.60			7420N	0.16	74LS85	0.99			25Z547 0.19	
SL1613P	1.89			7420N	0.16	74LS85	0.99			25Z547 0.19	
SL1620P	2.17			7420N	0.16	74LS85	0.99			25Z547 0.19	
SL1621P	2.24			7420N	0.16	74LS85	0.99			25Z547 0.19	
SL1623P	3.28			7420N	0.16	74LS85	0.99			25Z547 0.19	
SL1624C	3.28			7420N	0.16	74LS85	0.99			25Z547 0.19	
SL1625P	3.17			7420N	0.16	74LS85	0.99			25Z547 0.19	
SL1626P	2.44			7420N	0.16	74LS85	0.99			25Z547 0.19	
SL1630P	1.62			7420N	0.16	74LS85	0.99			25Z547 0.19	
SL1640P	1.89			7420N	0.16	74LS85	0.99			25Z547 0.19	
SL1641P	1.89			7420N	0.16	74LS85	0.99			25Z547 0.19	
TD12002	1.25			7420N	0.16	74LS85	0.99			25Z547 0.19	
TD12020	3.00			7420N	0.16	74LS85	0.99			25Z547 0.19	
ULN2242A	3.05			7420N	0.16	74LS85	0.99			25Z547 0.19	
ULN2283B	1.00			7420N	0.16	74LS85	0.99			25Z547 0.19	
CA3380E	0.70			7420N	0.16	74LS85	0.99			25Z547 0.19	
CA3089E	1.84			7420N	0.16	74LS85	0.99			25Z547 0.19	
CA3090AQ	3.35			7420N	0.16	74LS85	0.99			25Z547 0.19	
CA1123E	1.40			7420N	0.16	74LS85	0.99			25Z547 0.19	
CA1130E	0.80			7420N	0.16	74LS85	0.99			25Z547 0.19	
CA1301T	0.90			7420N	0.16	74LS85	0.99			25Z547 0.19	
CA1340E	0.46			7420N	0.16	74LS85	0.99			25Z547 0.19	
CA1389E	2.20			7420N	0.16	74LS85	0.99			25Z547 0.19	
MCI357P	2.35			7420N	0.16	74LS85	0.99			25Z547 0.19	
LM3900N	0.60			7420N	0.16	74LS85	0.99			25Z547 0.19	
LM3909N	0.68			7420N	0.16	74LS85	0.99			25Z547 0.19	
LM3914N	2.80			7420N	0.16	74LS85	0.99			25Z547 0.19	
LM3915N	2.80			7420N	0.16	74LS85	0.99			25Z547 0.19	
KB4400	0.80			7420N	0.16	74LS85	0.99			25Z547 0.19	
KB4406	0.60			7420N	0.16	74LS85	0.99			25Z547 0.19	
KB4412	1.95			7420N	0.16	74LS85	0.99			25Z547 0.19	

### FREQUENCY DISPLAY & SYNTHESISER ICs

TC9494	2.80	SAAL1056	3.75
TD1102B	1.11	SAAL1058	3.35
TD1102N	2.11	SAAL1059	3.35
TD1105A	1.45	ICL8038CC	4.50
TD11062	1.95	ICL8038CC	4.50
TD11072	2.69	ICL8038CC	4.50
TD11074A	5.04	ICL8038CC	4.50
TD11083	1.95	ICL8038CC	4.50
TD11090	3.05	ICL8038CC	4.50
HALL1			



# THREE FOR FREE FROM CSC



See us on STAND 826,  
Green Hall at INTERNEPCON

Electronics by Numbers  
Projects No 7, No 8, No 9

Available from selected stockists  
**ELECTRONICS BY NUMBERS**

## No. 7 DIGITAL DICE

Roll the dice — the electronic way! The digital dice gives you an instant score randomly chosen from 1 to 6, every time you press the button. No losing this under the table!


## No. 8 QUIZ MASTER

Play your own 'Sale of the Century'! Up to four contestants pit their wits; the first one to get the answer lights up his 'win' light, and stops anybody else from having a go.
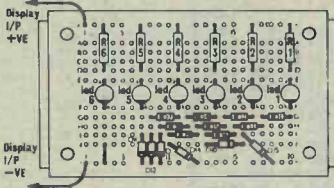
## No. 9 MOVING TARGET GAME

Test your reactions! A moving 'line of light' travels along from left to right, over and over again. You've got to 'fire' at just the right moment to score a hit. Fun for all the family!

Want to get started on building exciting projects, but don't know how? Now using EXPERIMENTOR BREADBOARDS and following the instructions in our FREE 'Electronics By Numbers' leaflets, ANYBODY can build electronic projects. For example, take one of our earlier projects, a L.E.D. Bar Graph;



You will need; One EXP 300 or EXP 350 breadboard, 15 silicon diodes, 6 resistors, 6 Light Emitting Diodes.

Just look at the diagram, Select R1, plug it into the lettered and numbered holes on the EXPERIMENTOR BREADBOARD, do the same with all the other components, connect to the battery, and your project's finished. All you have to do is follow the large, clear layouts on the 'Electronics by Numbers' leaflets, and ANYBODY can build a perfect working project.

## EXPERIMENTOR BREADBOARDS

No soldering modular breadboards, simply plug components in and out of letter number identified nickel-silver contact holes. Start small and simply snap-lock boards together to build a breadboard of any size.

All EXP Breadboards have two bus-bars as an integral part of the board, if you need more than 2 buses simply snap on 4 more bus-bars with the aid of an EXP 4B.

**EXP 325 £1.60** The ideal breadboard for 1 chip circuits. Accepts 8, 14, 16 and up to 22 pin ICs. Has 130 contact points including two 10 point bus-bars.



**EXP 350 £3.15** Specially designed for working with up to 40 pin ICs perfect for 3 & 14 pin ICs. Has 270 contact points including two 20 point bus-bars.



**EXP 300 £5.75** The most widely bought bread-board in the UK.

With 550 contact points, two 40 point bus-bars, the EXP 300 will accept any size IC and up to 6 x 14 pin DIPS. Use this breadboard with Adventures in Microelectronics.



**EXP 600 £6.30** Most MICROPROCESSOR projects in magazines and educational books are built on the EXP 600.



**EXP 650 £3.60** Has -6" centre spacing so is perfect for MICROPROCESSOR applications.



**EXP 4B £2.30** Four more bus-bars in "snap-on" unit.



The above prices are exclusive of P&P and 15% VAT.

## THE CSC 24 HOUR SERVICE TELEPHONE (0799) 21682

With your Access, American Express, Barclaycard number and your order will be in the post immediately

CONTINENTAL SPECIALTIES CORPORATION



C.S.C. (UK) LTD Dept. 16PP  
Unit 1, Shire Hill Industrial Estate,  
Saffron Walden, Essex CB11 3AQ.


Tel: Saffron Walden (0799) 21682 Telex: 817477

For full detailed instructions and layouts of Projects, 7, 8 and 9, simply take the coupon to your nearest CSC stockist, or send direct to us, and you will receive the latest 'ELECTRONICS BY NUMBERS' leaflet.

If you missed projects, 1, 2 and 3, or 4, 5 and 6, please tick the appropriate box in the coupon.
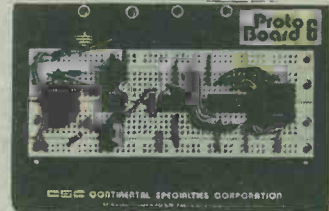
## PROTO-BOARDS

The ultimate in breadboards for the minimum of cost. Two easily assembled kits.



PB6 Kit, 630 contacts, four 5-way binding posts accepts up to six 14-pin Dips.

**PROTO-BOARD 6 KIT £9.20**



PB 100 Kit complete with 760 contacts accepts up to ten 14-pin Dips, with two binding posts and sturdy base. Large capacity with Kit economy.

**PROTO-BOARD 100 KIT £11.80**

## IT'S EASY WITH C.S.C. TO RECEIVE YOUR FREE COPY OF PROJECTS 7, 8 and 9

### Just clip the coupon

Give us your name and full postal address (in block capitals). Enclose cheque, postal order or credit card number and expiry date, indicating in the appropriate box(es) the breadboard(s) you require.

### For immediate action

The C.S.C. 24 hour, 5 day a week service. Telephone 0799 21682 and give us your Access, American Express or Barclaycard number and your order will be in the post immediately

EXPERIMENTOR BREADBOARDS	CONTACT	IC CAPACITY 14 PIN.DIP.	UNIT PRICE INC P&P & 15% VAT	Qty req.
EXP 325	130	1	£ 2.70	
EXP 350	270	3	£ 4.48	
EXP 300	550	6	£ 7.76	
EXP 600			£ 8.39	
EXP 650	270	use with 0.6 pitch Dip's Strip Bus-Bar	£ 5.00	
EXP 4B	Four 40 Point Bus-Bars		£ 3.50	

### PROTO-BOARDS

PB6	630	6	£11.73	
PB100	760	10	£14.72	

C.S.C. (UK) Ltd., Dept. 16PP, Unit 1, Shire Hill, Industrial Estate, Saffron Walden, Essex CB11 3AQ.

Tel: Saffron Walden (0799) 21682 Telex: 817477

NAME .....

ADDRESS .....

I enclose cheque/P.O. for £ .....

Debit my Barclaycard, Access,

American Express card No. ....

Expiry date .....

If you missed project No's

1, 2, 3, 4, 5, and 6, tick box.

For Free catalogue tick box



**PRICES SO LOW, THE POLICE INVESTIGATED ME TWICE**  
ALL ENQUIRIES, ETC. MUST BE ACCOMPANIED BY A STAMPED ADDRESSED ENVELOPE

**VAT & POST PAID**  
(2nd Class or Parcel)  
MINIMUM ORDER £3 (excluding catalogue) OTHERWISE ADD 50% FOR SMALL ORDER HANDLING COSTS (UNDER £1.00 TOTAL ALSO INCLUDE 12p S.A.E.)

UK - Postal Orders for same day service. Cheques require 8 days from a Monday banking to ensure clearance. Export - banker's draft (sterling) same day service. Foreign currency not accepted. VAT content becomes documentation charge.

**OPTO ELECTRONICS**

Photo Diodes: BPX40, BPX42, BPY10, CQY77, CQY17, BPY68, BPY69, BPY77 36p.  
Wire end neons 4p.  
Photo transistors: BPX43, BP103, 2N5777  
Darlington, 36p, OCP71 40p, LED's (Mullard Seimens) Red .2" 8p, .125" 9p; Green .2" 11p; .125" 12p; Micro Yellow LD481 7p.  
PHOTO SILICON CONTROLLED SWITCH BPX66 PNP 10 amp 36p  
CA3062 Photo Detector and power amp. £1

**7 SEGMENT L.E.D. DISPLAYS**  
.3" Red com. anode 81p  
.6" Green R.S.C.A. £1.77  
5082-7650 Red com. anode  
5082-7653 Red com. cath  
5082-7600 Yellow com. anode  
H.P. Highbrilliance .43" 72p

**HEWLETT PACKARD MULTIPLEXED .12" 7 SEGMENT LED DISPLAYS**  
3 Digit HP 5082 7413 45p  
4 Digit HP 5082 7414 45p  
5 Digit HP 5082 7415 45p  
Infra red transmit diodes CQY11B or LD27 High power 1.6-2v or 3-3.5v Pulse 32p LD242 36p  
H15B Photon coupled isolator I.R. diode and NPN Photo-Darlington amp 26p  
CNY17/1 opto coupler 70p  
Cold cathode tubes I.T.T. G517A or 5870L 60p

**SPECIAL OFFER**  
IN4004 or IN4006. Sealed manufacturers carton of 300.  
**£6.75**

**RESISTORS 1p**  
1/4 - 1 - 1/2 - 1 - 1 watt, mainly 5% 1, 2, 2.7, 3.3, 3.9, 4.7, 5, 5.6, 6.8, 8.2, 10, 12, 15, 18, 20, 22, 24, 27, 33, 36, 39, 43, 47, 51, 56, 62, 65, 68, 75, 82, 91, 100, 120, 130, 150, 160, 180, 200, 220, 270, 280, 290, 300, 330, 360, 390, 430, 470, 510, 560, 620, 680, 750, 820, 910, 1K, 1K1, 1K2, 1K5, 1K6, 1K8, 2K, 2K2, 2K7, 3K, 3K3, 3K9, 4K7, 5K6, 6K2, 6K8, 8K2, 9K1, 10K, 11K, 12K, 13K, 15K, 18K, 20K, 22K, 24K, 25K, 27K, 30K, 33K, 39K, 40K, 43K, 47K, 50K, 51K, 56K, 58K, 68K, 75K, 82K, 91K, 100K, 110K, 120K, 150K, 180K, 200K, 220K, 270K, 330K, 390K, 400K, 450K, 470K, 560K, 600K, 680K, 820K, 1M, 1M2, 1M5, 1M8, 2M, 2M2, 2M7, 3M, 3M3, 3M9, 4M7, 5M6, 6M8, 8M2, 10M.

**TUNING GANGS**  
AIRSPACED 100PF £1  
500 + 500PF £1.50  
900 + 500PF £1.50  
DIALECTRIC  
4 gang transistor radio type 40p  
250PF 82p  
265 + 108PF £1  
265 + 265PF £1

**DIODES**

AA119	7p	OA5	25p
AA133	9p	OA7	25p
AAZ15	15p	OA10	25p
B1	11p	OA47	7p
BA116	30p	OA70	10p
BA128	21p	OA75	11p
BA145	21p	OA79	11p
BA148	12p	OA81	31p
BA182 Varicap	6p	OA95	8p
BAX14	21p	OA200	21p
BAX54	8p	OA202	21p
BAY36P	21p	IGP7	11p
BB103 Varicap	6p	IGP10	11p
BB104 Varicap	16p	IN662	21p
BB109 Varicap	24p	IN914	11p
BB110B Varicap	24p	IN916	21p
BB113 Triple Varicap	43p	IN935B	71p
		IN936B	71p
BB139	£1	IN937B	71p
BY206	71p	IN941B	71p
BY207	23p	IN942B	71p
BY402	21p	IN943B	71p
BY403	21p	IN3064	21p
Centercell	3p	IN4009	21p
CG651	9p	IN4148	1p
CR HG/3	10p	IN4150	21p
CSD117YLZ	40p	IN4151	21p
CV7095	21p	IN4446	21p
CV7098	21p	IN4449	21p
D3202Y Diac.	11p	IN5456	15p
DC2845 Microwave	20p	5082 2900 RF Schotky Barrier	20p
DOG53	11p		
FSY28A	40p		
HG1012	10p		
HS2091	11p		
MPN3401	30p		

**RECTIFIERS**

Type	Volt	Amp	Price
BY212	EHT		6p
BY235	600	1 1/2	71p
BY236	900	1 1/2	71p
BY264	300	3	9p
BY265	600	3	11p
BY266	900	3	11p
BY274	300	5	14p
BY275	600	5	17p
BY277	1200	5	27p
BY299	800	2	4p
BY1202	2kV	10mA	6p
BYX20-200	200	25	72p
BYX22-200	300	1 1/2	25p
BYX38-300R	300	2 1/2	48p
BYX38-600	600	2 1/2	52p
BYX38-900	900	2 1/2	60p
BYX38-1200	1200	2 1/2	65p
BYX42-300	300	10	36p
BYX42-600	600	10	46p
BYX42-900	900	10	92p
BYX42-1200	1200	10	£1.07
BYX46-300R	300	15	£1.19
BYX46-400R	400	15	£1.75
BYX46-500R	500	15	£2.00
BYX46-600	600	15	£2.30
BYX48-300R	300	6	47p
BYX48-600	600	6	60p
BYX48-900	900	6	70p
BYX48-1200R	1200	6	92p
BYX49-300R	300	3	35p
BYX49-600	600	3	42p
BYX49-900R	900	3	47p
BYX49-1200	1200	3	60p
BYX52-300	300	40	£2.05
BYX52-1200	1200	40	£2.90
BYX72-150R	150	10	42p
BYX72-300R	300	10	52p
BYX72-500R	500	10	65p
BYX94	1250	1	6p
E250C50	250	1/2	14p
KS11394	800	3	23p
LT102	30	2	15p
M1	68	1	5p
MR856	600	3	24p
OA210	400	5	33p
RAS3 10AF	1250	1 1/2	48p
Avalanche			
RECS3A	1250	1 1/2	16p
SR10BR30	1000	30	£2.00
SKE4G	200	6	30p
SR100	100	1 1/2	9p
SR400	400	1 1/2	10p
IN3254	400	1	4p
IN4002	100	1	3p
IN4004	400	1	4p
IN4005	600	1	4p
IN4006	800	1	6p
IN4007	1250	1	6p
IN5059	200	1 1/2	10p
IN5401	100	3	10p
IS138	800	1 1/2	21p
IS921	100	1 1/2	8p
25G100	100	60	£4.35
3052	200	3	11p

**40 TURN CERMET TRIMPOT**  
1 1/2" track 100K LIN. with knob 11p

**BRIDGE RECTIFIERS**

1	60V	BC30 C350	23p
1	1,600	BYX10	34p
0.6	110	EC433	20p
1	50V	WO05	19p
1	140	OSH01-200	25p
1	200V	WO2 Ex Equip	15p
1	400V	WO4	28p
1	400V	MDA104	29p
1	800V	WO8	27p
1	1000	W10	36p
1 1/2	75V	IBIBY234	111p
1 1/2	150V	IBIBY235	15p
2 1/2	100	I.R.	40p
2 1/2	350V	9F2	70p
2 1/2	500V	9E4	85p
3	50	KBS005	30p
3	100	KB601	30p
3	200	KB502	30p
3	400	KB504	30p
3	600	KB506	30p
3 1/2	100	B40C 3200	58p
5	400	Texas	85p
		Miniature Meter Type	34p

**Thyristors**

Amp	Volt	Part No.	Price
1	240	BTX18-200	35p
1	240	BTX30-200	35p
1	400	BTX18-300	41p
4	500	40506 with heatsink	58p
4	600	2N3228	36p
6.5	500	BT109/SCR957	71p
2	400	SZ710D with heatsink	40p
8	100	S2800A	36p
4	600	C106M sensitive gate	36p
20	600	BTW92-600RM	£3.40
15	800	BTX95-800 Pulse Modulated	£1
4	50	S107F Sensitive Gate	36p
3	200	2N5064	18p
3	600	T3N06C00	53p
3	100	T3N1C00	36p
110	20	72R2CA	£3
75	800	71CG80	£6
150	1000	151RA100	£10
150	1200	151RA120	£11
12	1000	CR121103-RB	£8
10	200	S2800B	54p
5	600	S5800M	44p
8	600	S122M	54p
5	400	S3700D	44p
4	50	S2060F Sensitive gate	36p
7	400	S2620D	45p
7	600	S2620M	45p
4	400	S2061D Sensitive gate	38p
BT 106	70p	BT 107	£1
BT 121	70p		

**TRIACS**

Amp	Volt	Part No.	Price
0.1	40	7W84	3p
2.5	600	2N5757	44p
4	400	T2716D/40730	74p
6	200	T2500B/41014	54p
6	400	T2500D	72p
8	400	T2850D	72p
25	100	BTX94-100	£2.25
25	1200	BTX94-1200	£5

**ZENER DIODES**  
4/500MW. BZY88, BZX97, etc. 5p  
2v. 2v7. 3v. 3v3. 3v6. 3v9. 4v3. 4v7. 5v1. 5v6. 6v2. 6v8. 7v5. 8v2. 9v1. 10v. 11v. 12v. 13v. 13v5. 15v. 18v. 20v. 22v. 24v. 27v. 30v. 33v. 43v.  
BZY61 Laboratory Standard 400MW 7v5. Voltage Regulator Diode 12p  
1.3/1.5WT BZX61, BZY97, etc. 11p  
2v4. 2v7. 3v. 3v6. 3v9. 4v3. 4v7. 5v6. 6v2. 6v8. 8v2. 10v. 11v. 12v. 15v. 18v. 27v. 33v.  
2.5WT BZX70, etc. 13p  
v75. 1v. 2v4. 3v6. 3v9. 5v6. 6v2. 7v7. 7v5. 8v. 9v. 10v. 11v. 14v. 15v. (8p). 20v. 22v. 24v. 26v.  
5WT BZV40, etc. 15p  
3v3. 3v6. 3v9. 4v3. 4v7. 5v1. 5v6. 6v2. 6v8. 7v5. 8v2. 8v7. 9v1. 10v. 11v. 12v. 15v. 33v. 68v. 120v.  
10WT ZSD, ZX, etc. 20p  
4v3. 4v7. 5v1. 5v6. 6v2. 6v8. 7v5. 8v2. 11v. 12v. 13v. 16v. 18v. 21v. 22v. 33v. 36v. 39v. 68v. 150v.  
15WT BZV15C12R 12volt 37p  
20WT BZY93, etc. 44p  
8v2. 12v. 33v.

**1 WATT RESISTORS 1 1/2p**  
1, 1.5, 3, 5.6, 10, 12, 15, 18, 22, 25, 27, 30, 33, 39, 42, 45, 47, 50, 51, 55, 56, 58, 68, 82, 100, 120, 150, 180, 200, 220, 240, 250, 260, 270, 280, 300, 330, 350, 360, 390, 400, 450, 470, 510, 560, 600, 620, 680, 700, 750, 800, 820, 850, 1K, 1K2, 1K3, 1K5, 1K6, 1K8, 2K, 2K1, 2K2, 2K5, 2K7, 3K, 3K3, 3K5, 3K9, 4K5, 4K7, 5K1, 5K5, 6K2, 6K5, 6K8, 7K, 7K5, 7K6, 7K7, 8K, 8K2, 9K, 9K1, 10K, 11K, 12K, 15K, 15K, 18K, 20K, 22K, 24K, 25K, 27K, 30K, 33K, 36K, 39K, 40K, 42K, 43K, 45K, 47K, 50K, 51K, 56K, 60K, 61K, 62K, 68K, 70K, 75K, 80K, 82K, 91K, 100K, 110K, 120K, 130K, 150K, 180K, 200K, 220K, 240K, 250K, 270K, 330K, 390K, 400K, 450K, 470K, 500K, 510K, 550K, 560K, 680K, 800K, 820K, 1M, 1M2, 1M5, 1M8, 2M, 2M2, 2M7, 3M, 3M3, 3M9, 4M7, 5M6, 6M8, 7M5, 8M2, 9M1, 10M, 15M.



# TUNE IN to the new-look

FOR THE RADIO ENTHUSIAST ...

NOVEMBER 1980

## Practical wireless

65p

**FREE**

SURVEY OF 2m  
MULTI-MODES  
'SLIM JIM'  
FOR 28MHz

AND FEATURING

**PE HELFORD**  
PART 1

**FREE  
LEAD  
BENDING  
GAUGE**



**HF SSB TRANSCEIVER**

### ● PW 'HELFORD'

A new series giving full instructions on how to construct this Amateur Bands Transceiver.

### ● 'SLIM JIM' FOR 28 MHz


By popular request, Fred Judd, designer of the 'Slim Jim', has produced a version for the 10-metre amateur band.

November issue  
**OUT NOW 65p**


## Practical wireless

December issue out Friday November 7

**FREE**  
WORKSHOP  
TWEEZERS

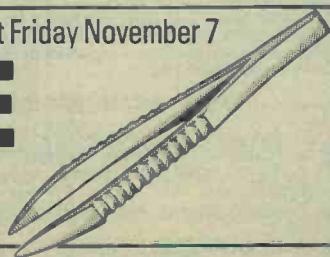
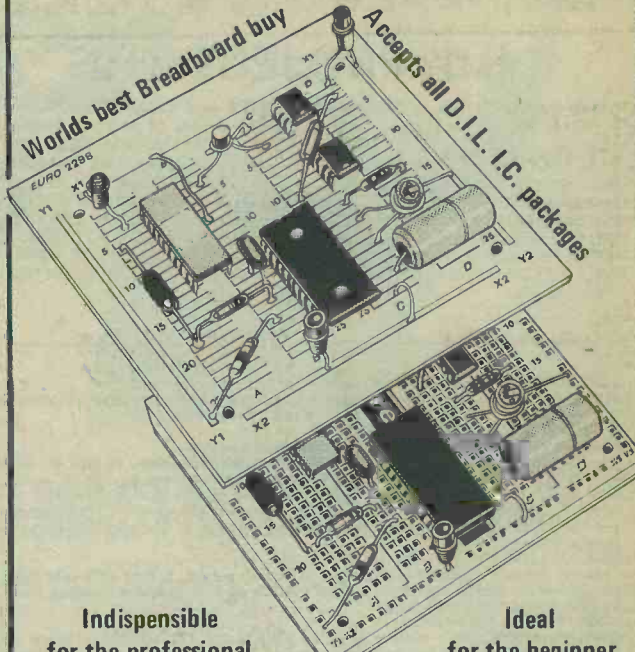
## First the EuroBreadBoard Now the EuroSolderBoard



World's best Breadboard buy

Accepts all D.I.L. I.C. packages

Indispensable  
for the professional

Ideal  
for the beginner

### Design on a EuroBreadBoard — Instal on a EuroSolderBoard

#### First the EuroBreadBoard

Will accept 0.3" and 0.6" pitch DIL IC's, Capacitors, Resistors, LED's, Transistors and components with up to .85mm dia leads. 500 individual connections PLUS 4 integral Power Bus Strips along all edges for minimum inter-connection lengths. All rows and columns numbered or lettered for exact location indexing (ideal for educational projects) Long life, low resistance (<10m ohms) nickel silver contacts £6.20 each or £11.70 for 2

#### Now the EuroSolderBoard

New 100mm square, 1.6mm thick printed circuit board with pre-tinned tracks identically laid out, numbered and lettered to EuroBreadBoard pattern. Four 2.5mm dia fixing holes. £2.00 for set of three ESB's

#### And don't forget the EuroSolderSucker

Ideal for tidying up messy solder joints or freeing multi-pin IC's, this 195mm long, all metal, high suction desoldering tool has replaceable Teflon tip and enables removal of molten solder from all sizes of pcb pads and track. Primed and released by thumb, it costs only £7.25 including VAT & PP



Snip out and post to David George Sales,  
Unit 7, Higgs Industrial Estate, 2 Herne Hill Road, London SE24 0AU

David George Sales,  
Unit 7, Higgs Ind. Est., 2 Herne Hill Rd., London SE24 0AU.

Please send me:—

- |                       |          |                       |        |
|-----------------------|----------|-----------------------|--------|
| 1 EuroBreadBoard      | @ £ 6.20 | <input type="radio"/> |        |
| or 2 EuroBreadBoards  | @ £11.70 | <input type="radio"/> | Please |
| or 3 EuroSolderBoards | @ £ 2.00 | <input type="radio"/> | Tick   |
| or 1 EuroSolderSucker | @ £ 7.25 | <input type="radio"/> |        |

All prices are applicable from Jan. 1st 1980 and include VAT & PP but add 15% for overseas orders.

Name .....

Company .....

Address .....

ERC/11

Tel. No .....

Please make cheques/P.D. payable to David George Sales and allow 10 days for cheque clearance and order processing

# MAGENTA ELECTRONICS LTD.

## R.E.C. PROJECT KITS

Make us YOUR No. 1 SUPPLIER OF KITS and COMPONENTS for R.E.C. Projects. We supply carefully selected sets of parts to enable you to construct R.E.C. projects. Project kits include ALL THE ELECTRONICS AND HARDWARE NEEDED - we have even included appropriate screws, nuts and I.C. sockets. Each project kit comes complete with its own FREE COMPONENT IDENTIFICATION SHEET. We supply - you construct. PRICES INCLUDE CASES UNLESS OTHERWISE STATED. BATTERIES NOT INCLUDED. IF YOU DO NOT HAVE THE ISSUE OF R.E.C. WHICH CONTAINS THE PROJECT - YOU WILL NEED TO ORDER THE INSTRUCTIONS/REPRINT AS AN EXTRA - 45p. each.

- LIGHT CHANGE ALARM** Dec. 78. £11.84  
In daylight detects someone moving around a room - after dark can be triggered by just torchlight. Units output rs from a relay (included).
- DYNAMIC MIC PRE AMP** Sept. 78 £5.82  
Features the ZN424E - with very low distortion and noise.
- ULTRA SENSITIVE ULTRASONIC REMOTE CONTROL** Feb 79 £12.45 and **DOPPLER SHIFT ADD ON UNIT** Mar 79. extra £5.22  
First part covers the construction of a sensitive remote control switch - an ultrasonic transmitter and receiver. The Doppler Shift add on unit detects movement within the vicinity of the transducers, and so has applications as a burglar alarm.
- RING OF LEDS PRINT TIMER** Jan 80 £11.22.  
Unusual display indicates 8 segments of timing period. A ring of 8 leds light progressively. Switch selectable timing periods of 1, 2, 3, and 4 minutes. Very smartly housed in a Vero Case.
- LOGIC TESTER** Jan 80 £5.89.  
Detects overload, logic state and pulse voltages in TTL circuits. A piece of veroboard is included - but the layout is left to the constructor. Portable. Battery operated. Supplied with test leads.
- TELEPHONE BELL REPEATER** Feb 80 £7.48.  
Includes 2 cases and speakers. Twin fig 8 cable to link units 7p per metre extra. Remote unit warns when the telephone rings. Battery powered.
- INFRA RED INTRUDER ALARM.** Mar 80 £9.98 less cases.  
Invisible infra red beam protects property - when the beam is broken the relay in the receiver is activated. Max. range 3 metres. Kit includes relay. Requires 9V supply.
- STEREO MIXER** Mar. 80 £12.73  
Mixes high impedance dynamic mic and nurse inputs. Based on 4 LF351 ICs. Two dual pots form the controls for mic. and line. Sockets for inputs and outputs.
- CONSTANT CURRENT NI-CAD CHARGER.** Sept 80. £19.98  
Charges up to 10 cells - suitable for all normal ni-cads. Continuously variable output current. Panel meter indicates the output current. Supplied with leads.
- BASIC SHORT WAVE RADIO** June 78 £18.95  
3 band trf design covering 1.2 to 24 MHz. Features five front panel controls - wavechange, bandset, bandspread, reaction, and aerial attenuator. Built on a pcb. The frequency range covers all the HF broadcast and amateur bands.
- 3 BAND SHORT WAVE PRESELECTOR** Feb 79 £15.98  
Uses a dual gate MOSFET. Tunes from 1.6 to 30 MHz in 3 bands. Adjustable rf gain control. Provides additional selectivity and sensitivity when used with a receiver.
- BEGINNERS MEDIUM WAVE RADIO** Aug. 79. £6.98  
Provides crystal earpiece reception of the M.W. band. Crystal earpiece is supplied.
- TOP BAND FERRITE AERIAL UNIT** Sept 79 £8.98  
An active tuned and amplified 160 metre band ferrite rod aerial unit. Provides directional reception facilities when used with a 160 metre receiver. Reduces interference and increases sensitivity.
- SINGLE CHIP M.W. RADIO** Sept 79 £11.37  
Simple sensitive M.W. receiver with loudspeaker. Uses an LM389-IC for rf gain, af gain and power output. Ideal for beginners.
- SHORT WAVE AERIAL TUNING UNIT** Dec 79 £11.98  
Improves receiver performance over 1.6MHz to 30MHz. Provides an increase in signal strength and rejection of strong interfering signals, spurious responses etc.
- SIMPLE SHORT WAVE SUPERHET.** Feb and Mar 80 £27.39  
Covers 180 to 20 metres. No alignment problems. Very low battery current. Plug in coils. Uses a dual gate MOSFET as a mixer. Regenerative RIF stage allows reception of a.m., c.w., and s.b.
- 80 METRE AMATEUR BAND RECEIVER** July 80 £19.98  
Expressly designed for ssb and cw amateur signals. This simple homodyne design provides world wide reception of amateur transmissions. Housed in a smart Vero case.
- PORTABLE SHORT WAVE RADIO** Aug 80. £18.94.  
Suitable for beginners. Covers 25, 31, 41, and 49 metre bands. Fitted with telescopic aerial. Use of TB820M amplifier IC provides loudspeaker output. Regenerative t.r.f. receiver. Smart ABS case.

LATEST KITS: S.A.E. OR 'PHONE FOR PRICES

## MAGENTA ELECTRONICS LTD.

RA1, 98 CALAIS ROAD, BURTON-ON-TRENT, STAFFS., DE13 0UL. 0283-65435. 9-12, 2-5 MON.-FRI. MAIL ORDER ONLY

ADD 35p. P.&P. TO ALL ORDERS. ALL PRICES INCLUDE 15% V.A.T. OFFICIAL ORDERS FROM SCHOOLS ETC. WELCOME. ENQUIRIES MUST INCLUDE S.A.E. OVERSEAS: SEND ORDER WITH 3 INTERNATIONAL POSTAL COUPONS WE WILL QUOTE EXACT PRICE BY AIR MAIL.

EIRE & BFPO ORDERS U.K. PRICES - LESS 10% (COVERS V.A.T. REFUND & EXPORT DOCUMENTS) PAYMENT: STERLING U.K. BANK DRAFT, U.K. POSTAL ORDERS or U.K. CHEQUE. ENQUIRIES: ENCLOSE 2 INTERNATIONAL POSTAL COUPONS.



## ELECTRONICS CATALOGUE

Magenta's Catalogue has been carefully designed for Electronics Constructors. Product data and illustrations make the Magenta Catalogue an indispensable guide for the constructor. Catalogue includes ELECTRONIC COMPONENTS, HARDWARE, TOOLS, CASES, TEST EQUIPMENT. Details of advertised items and CIRCUIT IDEAS for you to build. No minimum order - all products are stock lines. FIRST-CLASS delivery of FIRST-CLASS components. Send for your copy and see how easy our catalogue is to use. WRITE TODAY enclosing 6 x 10p stamps. New. 80/81 edition now out.

## ADVENTURES WITH ELECTRONICS by Tom Dulligan

An easy to follow book suitable for all ages, ideal for beginners. No Soldering. Uses an 'S Dec' breadboard. Gives clear instructions with lots of pictures. 16 projects - Including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-Dec and the components for the projects. Adventures With Electronics. £1.75. Component Pack £16.72 less battery.

## ADVENTURES WITH MICROELECTRONICS

Same style as above book; 11 projects based on integrated circuits - Includes: dice, two-tone doorbell, electronic organ, MW/LW radio, reaction timer, etc. Component pack includes a Bimboard, 1 plug-in breadboard and the components for the projects. Adventures with Microelectronics £2.35. Component pack £29.95 less battery.

## The INSTRUCTOR A FULLY CONSTRUCTIONAL PROJECT INCORPORATING AN INS8060 MICROPROCESSOR CHIP

- A Practical introduction to microprocessor functioning
- Relatively small number of components required
- An instructional

8 part series. Part 1 in Aug. 80 issue. Reprints of previously published part available. 45p each part. The Instructor is a low cost assembly which provides a practical introduction to microprocessors and their functions. It is not a computer, but it is a working circuit which allows microprocessor working to be followed, one program step at a time. Build the Instructor and you will gain microprocessor experience. The series is based on the INS8060 microprocessor IC, also known as the SC/MP Mk.2. Circuits are built on a plug in Eurobreadboard. Kit is available with or without the breadboard. INSTRUCTOR COMPONENT PACK: Including Eurobreadboard £27.85; or less Eurobreadboard £21.65.

**HEADPHONES AND EARPIECES.**  
The short wave radios require a crystal earpiece or high impedance mono headphones.

**MONO HEADPHONES** £2.98.  
High impedance 2k. Sensitive, Lightweight. Adjustable padded earpieces. Fitted with 3.5mm jack plug.

**CRYSTAL EARPIECE** 56p.  
Fitted with lead and 3.5mm jack plug. Top quality.

**STETHOSCOPE.** 69p.  
Optional attachment for use with our earpiece.

## TOWERS INTERNATIONAL TRANSISTOR SELECTOR £10.35

**ANTEX X25 SOLDERING IRON.** 25W. £4.98.  
**SOLDERING IRON STAND.** £2.03.  
**SPARE BITS.** Small, standard, large. 65p each.  
**SOLDER.** Handy size. 95p.  
**EUROBREADBOARD.** £6.20.  
**LOW COST LONG NOSE PLIERS.** £1.68  
**LOW COST CUTTERS.** £1.69.  
**SIREN.** 12V. £5.18  
**P.C.B. ASSEMBLY JIG.** £11.98.  
**P.C.B. ETCHING KIT.** £4.98.  
**MONO HEADPHONES.** 2K Padded, Superior, sensitive. £2.98.  
**STEREO HEADPHONES.** 8 ohm. Padded. £4.35.  
**MAGENTA** gives you **FAST DELIVERY BY FIRST-CLASS POST OF QUALITY COMPONENTS AND KITS.** All products are stock lines and are new and full specification. We give personal service and quality products to all our customers - **HAVE YOU TRIED US?**

**DESOLDERING BRAID.** 69p.  
**HOW TO SOLDER BOOKLET.** 12p.  
**HEAT SINK TWEEZERS.** 15p.  
**SOLDER BOBBIN.** 30p.  
**DESOLDER PUMP.** £5.98.  
**CONNECTING WIRE PACK.** 5 x 5 yd coils. 55p.  
**VERO SPOT FACE CUTTER.** £1.21.  
**VERO PIN INSERTION TOOL.** 0.1". £1.66. 0.15" £1.67.  
**RESISTOR COLOUR CODE CALCULATOR.** 21p.  
**MULTIMETER TYPE 1.** 1,000 o.p.v. with probes. 2" x 3 1/2" x 1". £6.66.  
**MULTIMETER TYPE 2.** 20,000 o.p.v. with probes. 5" x 3 1/2" x 1 1/2". £11.52.

## INTO ELECTRONICS CONSTRUCTION

6 part series in Hobby Electronics Feb 80 - July 80. Reprints available 45p each part, **COVERS THE BASICS OF ELECTRONICS - LOTS OF PRACTICAL WORK.** Circuits are built on a plug in Eurobreadboard. Eurobreadboard and components £15.63. Components only £9.43.

PRICES INCLUDE V.A.T.

# Conquer the chip.




Be it career, hobby or interest, like it or not the Silicon Chip will revolutionise every human activity over the next ten years.

Knowledge of its operation and its use is vital. Knowledge you can attain, through us, in simple, easy to understand stages.

Learn the technology of the future today in your own home.


## MASTER ELECTRONICS

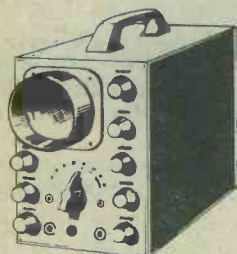

LEARN THE  
PRACTICAL WAY BY  
SEEING AND DOING

- Building an oscilloscope.
- Recognition of components.
- Understanding circuit diagrams.
- Handling all types Solid State 'Chips'.
- Carry out over 40 experiments on basic circuits and on digital electronics.
- Testing and servicing of Radio, T.V., Hi-Fi and all types of modern computerised equipment.

## MASTER COMPUTERS

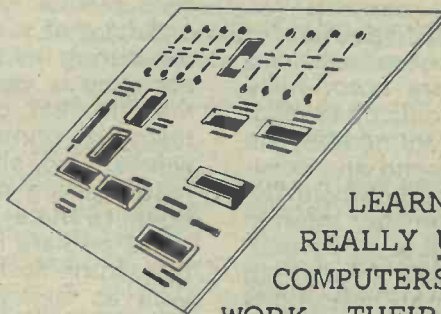

LEARN HOW TO  
REALLY UNDERSTAND  
COMPUTERS, HOW THEY  
WORK – THEIR 'LANGUAGE'  
AND HOW TO DO PROGRAMS.

- Complete Home Study library.
- Special educational Mini-Computer supplied ready for use.
- Self Test program exercise.
- Services of skilled tutor available.

## MASTER THE REST

- Radio Amateurs Licence.
- Logic/Digital techniques.
- Examination courses (City & Guilds etc.) in electronics.
- Semi-conductor technology.
- Kits for Signal Generators – Digital Meters etc.

**FREE**

Please send your **FREE** brochure without obligation to:—

REC/11/811

Name .....

Address .....

BLOCK CAPS PLEASE

I am interested in:—

PRACTICAL ELECTRONICS .....


COMPUTER TECHNOLOGY .....

OTHER SUBJECTS .....

(please state your interest)

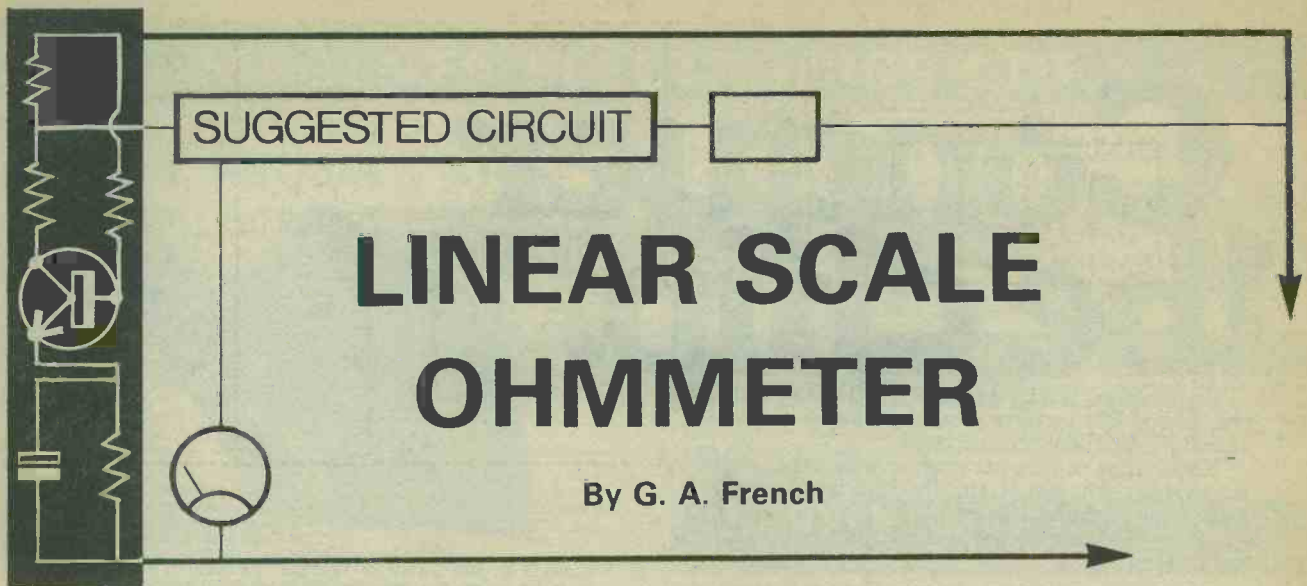**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL**

4 CLEVELAND ROAD, JERSEY, CHANNEL ISLANDS.



# LINEAR SCALE OHMMETER

By G. A. French

The more inexpensive analogue multi-testmeters have resistance ranges and scales which are notoriously inaccurate and difficult to read. The scales are cramped at the high resistance end and accuracy normally worsens with falling voltage in the internal meter battery. It is, in particular, not an easy matter to obtain meaningful indications of resistance when these approach and exceed 1MΩ.

The circuit to be described this month is for a low cost adaptor which can be used with an analogue testmeter when the latter is switched to a suitable voltage range, and it provides linear indications of resistance in five ranges, the lowest range being 0-1kΩ and the highest range being 0-10MΩ. The adaptor does not

give results which have the accuracy of a true laboratory measuring instrument, but the accuracy is very much better than is that given with the testmeter ohms ranges themselves. Also, all the resistance readings are directly proportional to meter voltage indications, and are in consequence free from scale cramping as well as being very easy to evaluate.

## CONSTANT CURRENT SOURCE

The basic mode of operation of the adaptor is shown in Fig.1. Here, a constant current source causes a constant current to be passed through the test resistor whose value is to be ascertained. Since the current is constant the voltage across the resistor is proportional to its resistance value. The voltage at the upper end of the test resistor is applied to an operational amplifier having an extremely high input resistance. The op-amp output is returned to the inverting input and the op-amp thus functions as a voltage follower. The voltage across the resistor, and hence an indication of its value, is then read from the analogue voltmeter connected to the op-amp output.

This method of measuring resistance is not, of course, new but the fairly recent introduction of modern devices to the home constructor component market, including in particular an integrated constant

current source, makes it possible to make up delightfully simple circuits which are capable of measuring resistances up to 10MΩ by the constant current technique.

The integrated constant current source is the LM334Z, and this is available from Maplin Electronic Supplies. It is encapsulated in a 3-pin TO92 package and, for operation at room temperatures, requires only one external resistor to establish the value of the constant current. The device is connected as shown in Fig.2 and the constant current, in amps, is equal to 0.0677 divided by the value of the external resistor. The range of constant currents available extends from 1μA to 10mA. The first current is given when the resistor has a value of 68kΩ and the second current when the resistor has a value of 6.8Ω.


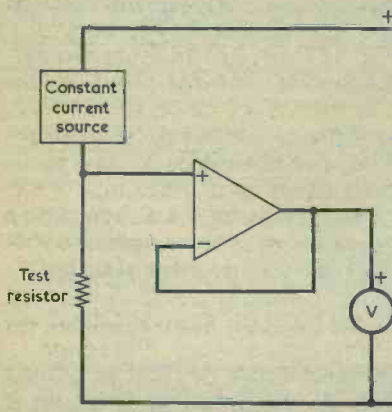



Fig.1. The basic circuit for obtaining linear resistance readings by means of an analogue voltmeter

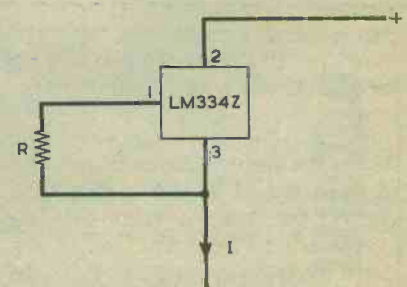

$$I = \frac{0.0677}{R}$$

Fig.2. Obtaining a constant current from the LM334Z



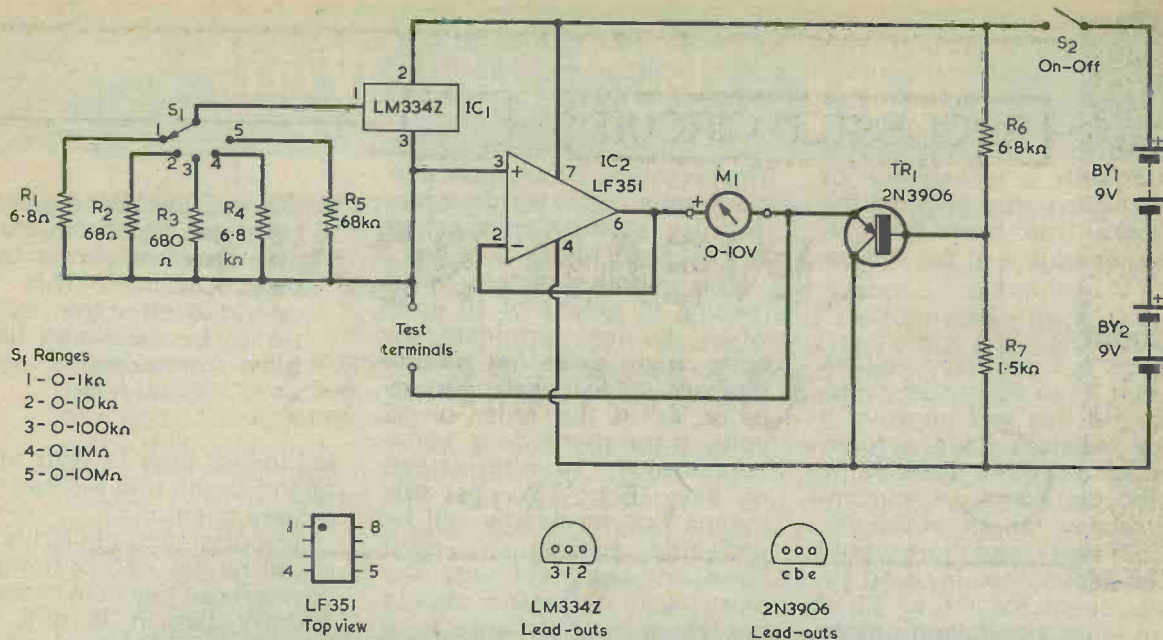

**Fig.3. Full circuit of the linear scale ohmmeter, which offers resistance readings up to 10M $\Omega$ . Meter M1 is a testmeter switched to read 0 - 10 volts. In the insets showing pinning for IC1 and TR1, the lead-outs point towards the reader.**

### ADAPTOR CIRCUIT

The full circuit of the adaptor is given in Fig.3, and it will be seen that the range switch S1 switches in five different values of external current control resistor. On Range 1 the constant current is 10mA, on Range 2 it is 1mA and on Range 3 the current is 100 $\mu$ A. Range 4 gives 10 $\mu$ A and Range 5 allows 1 $\mu$ A to flow. A current of 10mA through a 1k $\Omega$  resistor causes 10 volts to be developed across that resistor, and a current of 1mA through a 10k $\Omega$  resistor similarly produces a voltage of 10 volts. On each of the five ranges the maximum resistance shown for the range causes a voltage of 10 volts to be given. Lower resistances within the range produce proportionately lower voltages.

The resistor being measured is connected to the test terminals and the voltage on the upper terminal is applied to the non-inverting input of the op-amp, IC2, which is connected as a voltage follower. The i.c. chosen for the circuit is an LF351 with an input resistance of 1 tera-ohm, or 1 million megohms. This has J-fet inputs and does not need the

handling precautions that are required with devices having MOS inputs, although it is wise to solder to the input pins with an iron having a reliably earthed bit. The only main precaution needed is to ensure that neither of the LF351 inputs is taken negative of the negative supply pin, as damage to the device can then result.

The LF351 ceases to function as a voltage follower if the input at the non-inverting input passes below about 2 volts positive of the negative supply rail and so it is necessary to raise the voltage follower and meter circuit above the negative rail by a suitable voltage. This is achieved with the aid of the potential divider consisting of R6 and R7, the junction of these two resistors connecting to the base of emitter follower TR1. The voltage at the emitter of TR1 is around 4 volts positive of the negative rail, and falls as battery voltage drops. A precise voltage is not required as the lower test terminal and the negative side of the analogue meter are both returned to the emitter, and the constant current from IC1 is not affected by the voltage at this point. The emitter follower copes comfortably with the varying currents required on

the different resistances ranges. The standing current in the potential divider is about 2.2mA. A 3.9 volt zener diode could have been employed instead of the emitter follower, but it would have required a standing zener current of at least several milliamps to bring it on to the flat part of its characteristic.

As has been already explained, the voltage applied to the non-inverting input of the LF351 is 10 volts maximum on each range. The input voltage varies therefore, from zero to 10 volts. With the 4 volt delay given at the emitter of TR1, the LF351 output voltage swing, relative to the negative rail, is from 4 to 14 volts. Such a swing is comfortably within the capability of an LF351 having an 18 volt supply. In practice, the circuit provides accurate resistance readings even when the supply voltage drops to 14 volts, as the reference voltage at TR1 emitter also falls.

The total current consumed by the circuit is about 4mA on Ranges 5, 4 and 3, this rising to around 5mA on Range 2 and 15mA on Range 1. The two 9 volt batteries may be any type, ranging from PP3 to PP9, as preferred.

The meter, M1, is a testmeter

switched to read 0-10 volts. The circuit will function with quite insensitive meters, and it is only required that the meter resistance should be  $1,000\Omega$  per volt or more. A 0-10 volt meter with a sensitivity of  $1,000\Omega$  per volt will consume an extra 1mA from the batteries when it is at full deflection.

#### ACCURACY

Quite fair accuracy will be given if R1 to R5 are 5% resistors, and this will improve if these resistors have a tolerance of 2%. The LM334Z is quoted as having a current accuracy within 3% of the calculated value, and there would be little advantage in using 1% components for R1 to R5 if these were significantly more expensive than 2% types. If difficulty is experienced in obtaining the  $6.8\Omega$  resistor required for R1 in close tolerance, it may be made up from an  $11\Omega$  and an  $18\Omega$  resistor in parallel. These have a combined calculated value of  $6.83\Omega$ . R6 and R7 can be standard 5%  $\frac{1}{4}$  watt components.

The circuit may be made up in any convenient case with S1 and S2 on the front panel, in company with two terminals for the test resistor and two terminals to which the testmeter

connects. Resistance readings are then proportional to test-meter voltage reading. If, for instance, a reading of 3.4 volts is given on Range 4, the test resistor has a value of  $340k\Omega$ . The prototype circuit gave perfectly satisfactory results when the test resistors approached and reached  $10m\Omega$  in value.

The analogue meter gives a reading in excess of 10 volts when the test terminals are open-circuit and the voltage then applied to it, with new batteries, is of the order of 14 volts. If the meter f.s.d. value happens to be 10 volts (instead of, say, 15 or 20 volts) this means that its needle will be deflected against the right hand end-stop, although the extra current flowing should not cause any damage to a normal meter movement. If this effect is disliked, a press-to-break push button can be added to the circuit, it being connected across the test terminals as shown in Fig.4. The button is pressed, to take a reading, after the test resistor has been connected to the terminals. Incidentally, the fact that the voltmeter gives a reading in excess of 10 volts with the test terminals open-circuit provides an automatic check on battery voltage. If the open-circuit voltage readings

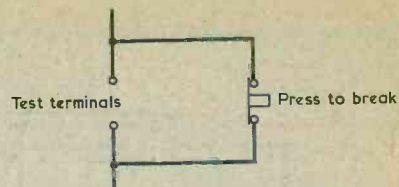


Fig. 4. If desired, a press-to-break push button may be wired across the test terminals. This is operated after the resistor to be measured has been connected to the terminals

fall to less than 11 volts this is an indication that the batteries require changing.

The dissipation in IC1 is low on all ranges except Range 1, where it can rise to in excess of 100mW (which is still well within its maximum rating). There may be a slight drift in readings if the ohmmeter is used for long periods on Range 1 due to the consequent rise in temperature inside the device, but there should be no problems in the short term. The adaptor should not be left switched on with Range 1 selected for excessive times when the push-button of Fig.4 is incorporated, as apart from any other effect there would be an excessive drain on the batteries. ■

## NEW CATALOGUE

Now available from Magenta Electronics is their new 1980-81 catalogue. With 52 large pages and a separate 6 page Price List, this gives details of a very wide range of electronic components, including printed circuit materials, cases, semiconductors, coils, transformers, resistors, capacitors, connectors and testmeters. Detailed illustrations of components are provided. Five pages of the catalogue are devoted to circuit ideas which can be built by the experimenter.

An unusual feature is the inclusion of a large quantity of kits for constructional projects published in this magazine and others. These kits include our current "INSTRUCTOR" series and, in all, there are well over 150 projects listed. Each kit provides, nuts, bolts, and all hardware needed, as well as the purely electronic parts.

The Magenta Electronics 1980-81 catalogue can be obtained from Magenta Electronics Ltd., 98 Calais Road, Burton-on-Trent, Staffs, DE13 0UL by sending payment of six 10p stamps.

## RECENT PUBLICATIONS



**THE PERSONAL COMPUTER BOOK.** By Robin Bradbeer. 226 pages, 210 X 140mm. (8¼ X 5½in.) Published by Input Two-Nine. Price £5.25.

Robin Bradbeer is a free-lance writer on personal computing, as well as being Senior Lecturer in the Department of Electronic and Communications Engineering at the Polytechnic of North London. In this book (which is distributed by MCB Publications Limited, 198/200 Keighley Road, Bradford, BD9 4JQ, Tel. 0274 499821) he sets out to explain what the personal computer can do and how the beginner in the computer world can obtain and take advantage of a suitable machine for his own particular requirements.

The text is concise, pleasant in style and easy to follow. The first five of the seven chapters which make up the body of the book introduce the computer, indicate how the reader can start with computers, and discuss hardware and software. The sixth chapter gives specifications and details for some 50 commercially produced computers and systems which are currently available, as well as for 15 printers and 10 visual display units. Chapter 7 describes the uses to which the computer can be put. There are eight appendices, the first four of which cover binary arithmetic, interface standards, addresses of manufacturers and distributors, and computer clubs and specialist groups in the U.K. The fifth appendix gives an extensive list and evaluation of computer magazines in the U.K., U.S.A. and the Continent, and the sixth a selected bibliography. A glossary of terms appears in the seventh appendix, and advice is given on building kit systems in the final appendix.

This is a comprehensive and carefully prepared publication offering much useful information to the newcomer to computers.

**110 IC TIMER PROJECTS FOR THE HOME CONSTRUCTOR.** By Jules H. Gilder. 125 pages, 230 x 145mm. (9 x 5½in.) Published by Newnes Technical Books. Price £3.10.

The 555 must surely be one of the most widely employed i.c.'s in use today. Basically intended as a monostable or astable multivibrator, it has appeared in very many widely varying applications since its introduction. The book under review gives an excellent idea of the versatility possessed by this unique integrated circuit.

The book commences with a description of the internal circuitry and pin functions of the 555 and then deals with monostable and astable circuits. In both instances, circuits are presented which offer enhanced performance. The section on astable circuits includes, for example, an astable with continuously variable duty cycle and an astable with crystal frequency control.

The following sections cover logic circuits, timer-based instruments, automobile applications, alarm and control circuits, and power supplies and converters. As the title of the book promises, there are 110 different circuits. These are all good and practical and will not only be of considerable interest to the experimenter as well as the constructor but may also, in themselves, spark off further ideas and uses for the 555.

**A GUIDE TO AMATEUR RADIO, 18th Edition.** By Pat Hawker, G3VA. 144 pages, 245 x 180mm. (9½ x 7in.) Published by Radio Society of Great Britain. Price £2.40.

*A Guide To Amateur Radio* first appeared in 1933, and it has now arrived at its 18th edition. Its continuing popularity gives clear evidence that it is a welcome occupant of the bookshelf of anyone having an interest in amateur radio, whether this be for transmitting or simply for listening.

The prime aim of the book is to advise the newcomer to amateur radio, and to assist in the obtaining of a transmitting licence. But in so doing it also provides a great deal of technical information which will help any beginner in electronics in general and in short wave radio in particular. Among the subjects covered are communications receivers, transmitters, aerials, workshop practice and electronic fundamentals. The book also gives specific information on amateur matters, including amateur station operation, the function of the RSGB, international amateur organisations and working to pass the transmitting licence examination.

The book is well set up and laid out, with clear illustrations and diagrams. In cases of difficulty it can be obtained direct from Radio Society of Great Britain, 35 Doughty Street, London WC1N 2AE, for £2.99 post paid.

# NEWS . . . AND

## HANDHELD DMM REDUCED IN PRICE

Fluke's latest low cost handheld DMM, the 3½ digit 8022A Troubleshooter model, has just been reduced in price from £89 to £75, making it even more attractive in design, service and field test work.

The 8022A is a simple yet versatile general purpose DMM providing 6 functions (AC + DC Volts, AC + DC Amps and high and low Ohms) with 24 ranges, including 3 diode test ranges.

A clear 3½ digit LCD display makes it easy to read with the single row of buttons down one side allowing single handed operation when required. Extensive overload protection up to 6 kV for transients and 1000 V or 20 Amps make it practically indestructible in use. The LCD display on the 8022A also provides a battery low, over-range and negative polarity indication. Basic DC accuracy is 0.25%.

The safety leads are especially designed to prevent accidental shock and a full range of accessories are available including probes for high voltage, high current, RF, temperature as well as a battery eliminator for bench work.



## "BROADCASTING TECHNOLOGY FOR THE 1980's"

The IBA has published a 12-page, fully-illustrated, description of current engineering progress and development work being carried out at Crawley Court, Winchester under the title "Broadcasting Technology for the 1980's". This describes the engineering of the "Fourth Channel" under the IBA Act 1979; recent developments for Independent Local Radio; the present state of digital technology in broadcasting, including ORACLE teletext and digital techniques for the application of space satellites.

In a foreword by Tom Robson, IBA's Director of Engineering, he writes:

"The 1980s offer the challenge of the all-digital systems; the new methods of video distribution including optical fibres and satellites; the exploitation of bandwidth at SHF and beyond; the new mobility of lightweight equipment – especially where microwatts of power consumption can match the micro size of the devices. It is a challenge that will call for new skills and new training for a very different world."

Contents: UHF transmitters and the Fourth Channel; RTS award for SABRE; ILR – the new force in sound radio; the ubiquitous digit – digital video processing; IBA digital 'firsts'; the expanding world of teletext; space satellites – questions for the future; IBA – an engineering service.

Copies are available, free of charge, from IBA Engineering Information Service, Crawley Court, Winchester, Hants. SO21 2QA.



The Screwmaster ratchet range, l to r – the 8½" screwdriver, the 3" Chubby, the new bit holder Screwmaster and the new Chubby with their set of bits.

## 'FOUR SCREWDRIVERS IN ONE'

'Four screwdrivers in one' is the latest addition to the Steadfast Screwmaster family of screwdrivers from J. Stead & Co Ltd, of Netherlane, Ecclesfield, Sheffield.

The new screwdriver adaptors incorporate the patented roller ratchet Screwmaster mechanism which was successfully launched earlier this year. There is a sleeve at the end of the driver shaft to hold all types of standard ¼" A/F screwdriver bits.

The bit holder is available in two sizes. The Chubby model is only 3" in length – a size which has already proved its popularity as a ratchet Screwmaster. The larger model is 8¼" in length. Both sizes come with either a magnet or retaining clip at the base of the sleeve to hold the bit in place.

The magnet will also attract a screw – a particular feature if working in tight or awkward conditions. However, in situations where a magnetised blade is not suitable the retaining clip is the alternative.

The adaptor and bits are available separately or in kit form comprising an adaptor, together with No 1 Pozidriv, No 2 Pozidriv, 3/16" and ¼" flat bits.

Retail prices range from £3.35 to £4.90, plus VAT, for the bit holders and £5.95 to £7.50, plus VAT, for the kit form.

## ... COMMENT

As we grow increasingly security conscious, our pockets progressively fill with keys of all shapes and sizes. Apart from the wear and tear these may cause, the danger of loss is always present. An obvious solution is an electronic combination switch, which can be ideal for controlling electrically operated devices such as alarm systems and solenoid releases, etc. To meet this need we are featuring in this issue an article - 'CMOS Combination Switch'.

Since a combination switch involves expenditure in addition to the expense of the device it controls, it is essential to design its circuit such that costs are kept to a minimum. This requirement is achieved in the foregoing design to such an extent that it costs little more than an electrical locking switch!

### SATELLITE DATA BUOY

McMichael has successfully installed a satellite data collection platform (DCP) on a buoy which is moored off the coast of the Isle of Wight.

Data is collected, processed and stored from the on-board sensors and at regular time intervals is transmitted back to the home base in Slough via satellite, satellite receiving station (in W. Germany) and then telex.

Due to the processing capability of the DCP, the transmission time is much reduced and thereby saves battery power during transmission.

A wide beam aerial on the buoy mast ensures that data is still transmitted even during rough weather, which was simulated in this trial by using a buoy with a shortened keel which was kindly supplied by the British Met. Office.

Such data buoys can be moored anywhere in the world whilst the user receives his information at the home base and will gradually replace weather ships which are increasingly expensive to operate, as well as being used on large lakes and other inland water.

There has been interest in this project from many parts of Europe and the Dutch Water Authority have asked for an extension to the trial period whilst they undertake some of their own measurements.

### CASIO ENTERING THE MUSIC BUSINESS

CASIO is a name that most people readily associate with quality calculators and digital watches. Some also recognise Casio as a manufacturer of cash registers and computers.

Casio are breaking new ground by entering the music business with a product called Casiotone. It is a keyboard instrument that can reproduce the sounds of piano, organ, violin, flute, and a couple of dozen other instruments that are normally struck, plucked, bowed or blown. Moreover it is polyphonic - able to play chords of up to eight notes simultaneously.

Technology employed is a development from Casio's earlier electronics expertise. Casiotone's functions are performed by two-chip LSI circuitry. It makes sounds that are pleasing to professional musicians, yet it will sell at a price appealing to amateurs.

### "PATHÉTIQUE" RECORDED USING 3M DIGITAL EQUIPMENT



The first classical recording in England using the 3M Mincom digital multi-track mastering system took place during June at the Kingsway Hall in London.

Carlos Païta conducted the National Philharmonic Orchestra under the leadership of Mr. Sidney Sax for a recording of Tchaikovsky's Symphony No. 6, "The Pathétique". The 3M Mincom 4-track digital recorder was on hire from the Townhouse Recording Studios in Shepherd's Bush. The digital recording was backed up by both 8- and 2-track analogue recorders with Dolby noise reduction equipment on hire from Decca.


The programme was mixed and edited at the Roundhouse Recording Studios on 20th and 21st June using the studio's 3M Mincom 32-track and 4-track digital recorders and electronic editor, as well as new cross fade units also manufactured by 3M. Cutting will shortly take place at The Townhouse, again using the 3M digital preview unit. The Townhouse can probably claim the best cutting facilities in Europe at present since its acquisition of the 3M digital equipment and a new Neuman lathe.

The digital recording of Tchaikovsky's "Pathétique", with Carlos Païta conducting the National Philharmonic Orchestra, is due for release in October.
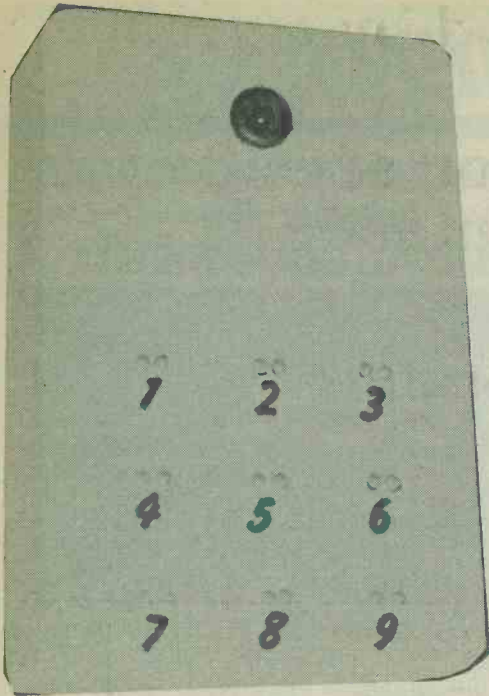
### MICROPROCESSOR APPLICATIONS UNDERWATER

The introduction of microprocessors to the underwater scene represents yet another step forward on the road to extending our knowledge of a range of environmental conditions, and provides yet another precise tool for the better information of designers, engineers and offshore operators. If programmed to recognise and record particular non-typical events and conditions, microprocessors can fill in vital gaps in information which may be missed by instruments performing routine sampling.

The subject is to be dealt with in a one day seminar to be held in November under the auspices of the Society for Underwater Technology of 1 Birdcage Walk, London SW1H 9JJ.



The prototype combination switch is housed in a neat plastic case. Each of the combination numbers is selected by touching the corresponding contact pair with a finger.

As we grow increasingly security conscious, our pockets progressively fill with keys of all shapes and sizes. Apart from the wear and tear these may cause, the danger of loss is always present. An obvious solution is an electronic combination switch, which can be ideal for controlling electrically operated devices such as alarm systems and solenoid releases, etc.

Since a combination switch involves expenditure in addition to the expense of the device it controls, it is essential to design its circuit such that costs are kept to a minimum. This requirement was achieved with the present design to such an extent that it costs little more than an electrical locking switch.

One of the most expensive parts of a combination switch can be the keyboard, press-buttons or other circuit controlling switches which are employed. It was therefore decided to use a "touch contact" system, which may be home produced at almost zero cost. One word of caution, however: touch contacts require clean dry conditions, and are only suitable for indoor applications. CMOS devices can be readily controlled by touch contacts and they incur very low battery current consumption. The design incorporates two CMOS chips, these being a 4081 (quad 2-input AND gate) and a 4001 (quad 2-input NOR gate).


#### OPERATING THE DEVICE

The switch is activated by touching contacts 1, 2, 3, 4 (as numbered in the circuit diagram) in that order. If any other numbered contact is touched the circuit is de-activated and remains in that state for a period of seconds or minutes according to the values chosen for C2 and R9. Thus, the potential thief has to touch the correct contacts in the proper order the *first time* to

# CMOS COMBINATION SWITCH

By

M. P. Horsey

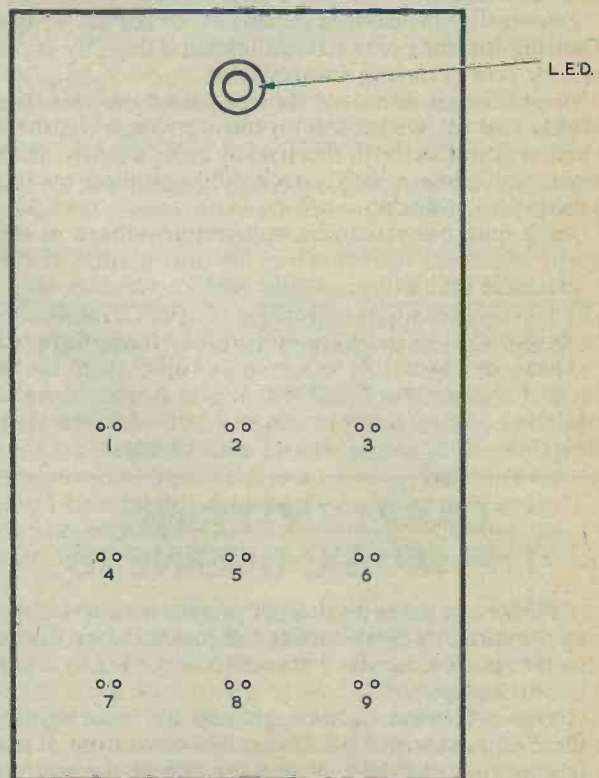

o o - pairs of contacts

Fig.1. Front panel layout of the combination switch. Pairs of contacts are bridged by a finger in the correct sequence to operate the switch. Touching an incorrect contact pair disables the switch for a pre-set period.

•Negligibly low stand-by current.

•Automatic inhibit on selection of incorrect contacts.

•Finger-tip operation

secure operation of the switch. If a wrong contact is touched, even the correct sequence will not operate the switch until the pre-determined delaying period has elapsed.

The layout of the front panel is shown in Fig.1 and the photographs. The pairs of touch contacts are numbered 1 to 9 but these numbers do not correspond with the numbers allocated to the touch contacts in the circuit diagram. The wiring combination to the contacts is carried out as desired by the constructor and it could, for example, produce a correct sequence of 9, 5, 8, 1, with all the other contacts setting up the delay inhibit period.

Most readers will be familiar with the NOR gates in the 4001 chip. The output of each gate will be high, at logic 1, only when both inputs are low, at logic 0. If either input or both inputs are at 1 the gate output goes to 0. In the 4081, each AND gate produces an output 1 only when both inputs are at 1. If either or both inputs are at 0, the output of the gate is also at 0.

#### THE CIRCUIT

The circuit appears in Fig.2. In this diagram, both C2 and C3 are discharged at the instant of applying the 9 volt supply. At this instant, pin 8 of IC2 is held low, because of R7 and R8, and the gate output will be high. This output, coupled via the discharged capacitor C2, keeps pins 12 and 13 high and pin 11 low. The two gates concerned latch into this state. The low output at pin 11 passes to pins 1 and 2 of the third gate of IC2, whereupon pin 3 of that gate goes high, causing C3 to charge via R10 after a very short delay.

However, C3 is discharged at the instant of supply application, thereby biasing the top AND gate of IC1 so that it takes up the state where pin 3 is low, as also is pin 2. These last two pins stay low after C3 has charged. The low output at pin 3 of IC1 is applied to pin 5 of the second AND gate, whose output at pin 4 is consequently low. Following the chain of AND gates, pin 10 is also low as, finally, is pin 11.

When contacts 1 are touched, pin 2 of IC1 goes high, as also does pin 3, and the top AND gate latches into this new state. Pin 5 of the second AND gate is now high so that, if contacts 2 are bridged by the finger, its output goes high also, at pin 4. The progression continues by touching contacts 3 and then contacts 4, whereupon pin 11 of IC1 goes high, turning on transistor TR1 and energising the relay. The relay


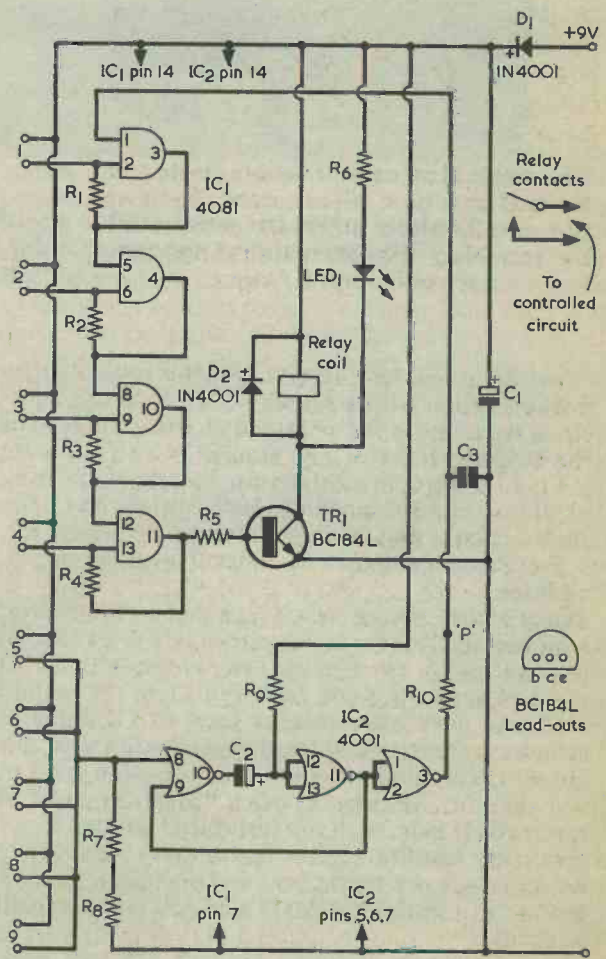


Fig.2. The circuit of the combination switch. Contact sets 1 to 4 have to be touched in numerical order to actuate the switch. Touching any of the other contact sets inhibits the switch for a period dependent upon the values of C2 and R9. Contact set numbering does not, of course, correspond with the numbers on the front panel of the switch.

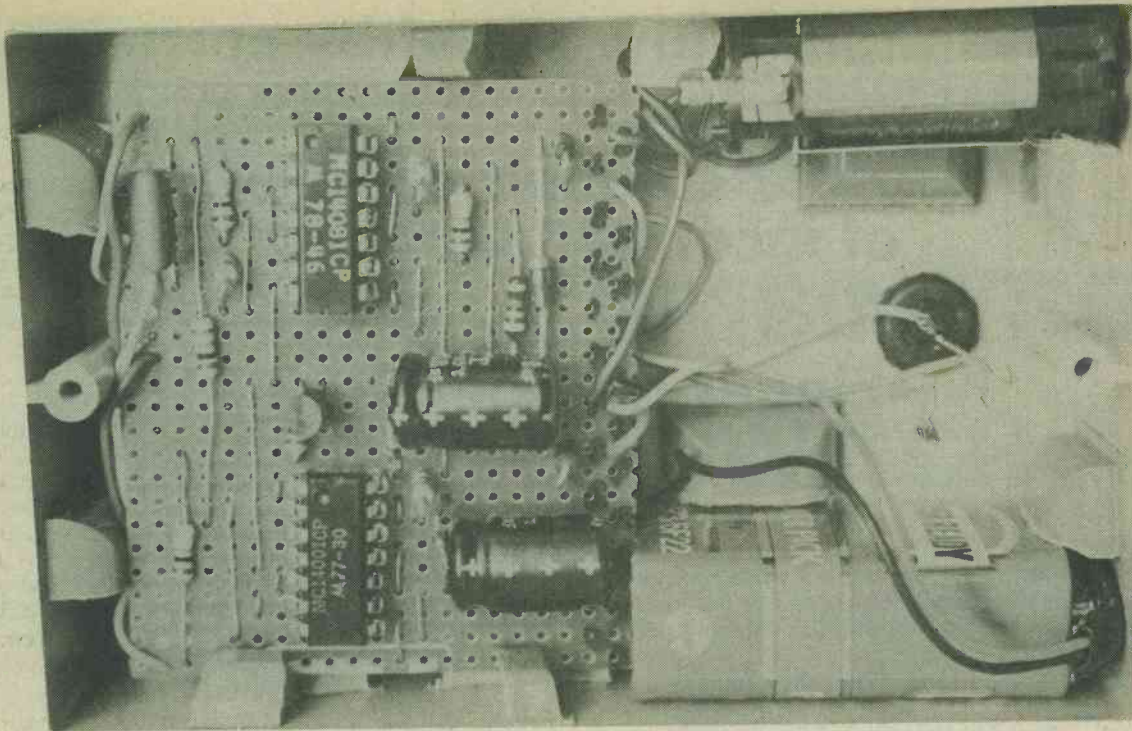

Looking inside the combination switch case. The author's unit is powered by a PP3 battery and incorporates a dry reed relay, which is mounted opposite the battery.

contacts then turn on whatever circuit is controlled by the combination switch. Diode D2 protects the transistor against high inductive voltages when the relay is subsequently released. The transistor also turns on the l.e.d. in its collector circuit, thereby indicating that the correct sequence of touch buttons has been selected. LED1 and its current limiting resistor, R6, are not essential and may be omitted from the circuit, if desired.

If any of the "wrong" contact pairs, 5 to 9 inclusive, is touched, pin 8 of the NOR gate in IC2 is taken high and its output at pin 10 goes low, as also do pins 12 and 13 of the next NOR gate. Pin 11 of the second NOR gate goes high and, as long as C2 remains discharged, these two gates stay latched in this new condition. The high output at pin 11 causes pin 3 of IC2 to go low. This low is passed via R10 to pin 1 of the top AND gate, with the result that contact sets 1 to 4 become inactive. Even if one or more of the AND gate outputs has already been latched high, the low input at pin 1 of the top AND gate will take them all low again.

When, after a "wrong" contact set has been touched, pin 10 of IC2 goes low, capacitor C2 is discharged. It then begins to charge slowly via R9 until, eventually, pins 12 and 13 of IC2 go sufficiently high to cause pin 11 to go low and pin 3 to go high. The first two NOR gates latch back to their initial state and the combination switch may again be operated by touching contacts 1 to 4 in the correct order. The values of C2 and R9 are chosen by the constructor to suit his particular requirements. A very long time delay is not recommended as it would be irritating for the authorised user to have to wait too long if he accidentally touched a wrong contact set. As an example, a value of 1M $\Omega$  for R9, with 4.7 $\mu$ F for

## COMPONENTS

### Resistors

(All  $\frac{1}{4}$  watt 5% unless otherwise stated.)

R1 10M $\Omega$ 10%	R6 1k $\Omega$
R2 10M $\Omega$ 10%	R7 10M $\Omega$ 10%
R3 10M $\Omega$	R8 10M $\Omega$ 10%
R4 10M $\Omega$ 10%	R9 see text
R5 4.7k $\Omega$	R10 1M $\Omega$

### Semiconductors

IC1 4081	D1 1N4001
IC2 4001	D2 1N4001
TR1 BC184L	LED1 red l.e.d.

### Capacitors


C1 100 $\mu$ F electrolytic, 10V. Wkg.
C2 see text
C3 0.01 $\mu$ F polyester, type C280

### Miscellaneous


9-volt battery type PP3 (see text)
Battery connector
Plastic case (see text)
Relay (see text)
18-off touch contacts (see text)
2-off 14-way i.c. holders

C2, will provide a delay of about 3 seconds. Increasing either R9 or C2, or both, will increase the delay. In practice a delay of about 3 $\frac{1}{2}$  minutes is suggested, and this will be obtained with R9 at 4.7M $\Omega$  and C2 at 100 $\mu$ F.



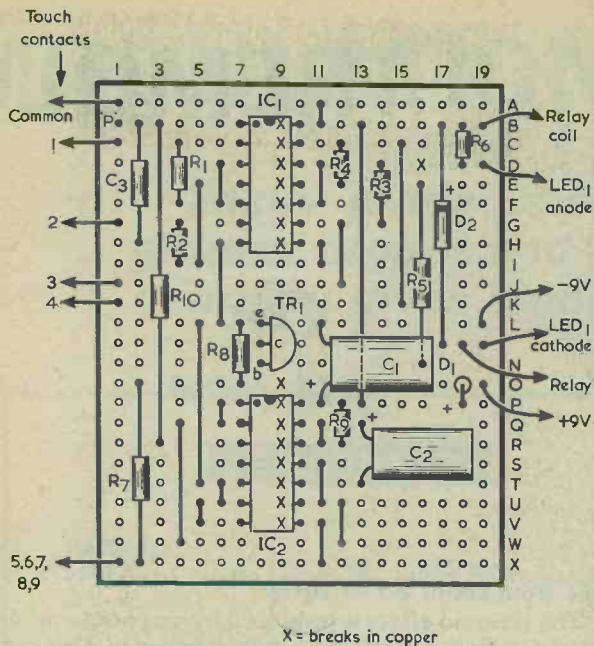

**Fig.3.** Veroboard layout as seen on the component side of the board. The "common" lead from hole A1 connects to one contact of all the contact pairs.

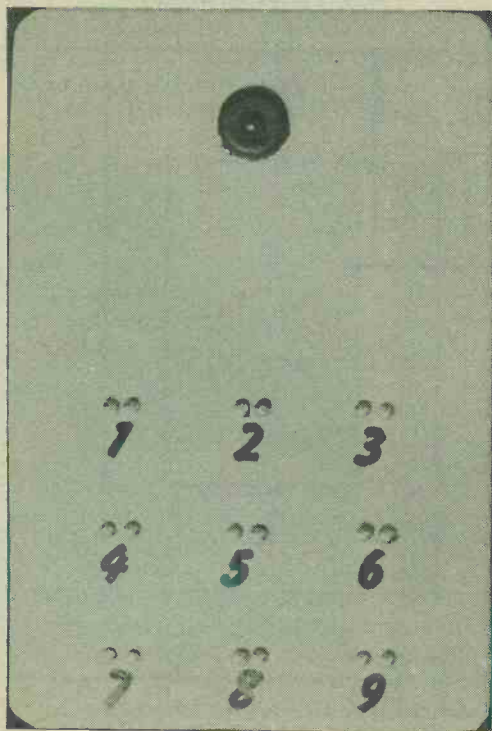

Also mounted on the front panel is a light-emitting diode which lights up when the correct combination has been selected.

Diode D1 is optional, but is included to ensure that no damage is done should the battery be momentarily connected the wrong way round, as can easily happen with a PP3 type connector.

Point "P" is provided to turn off the combination switch once entry has been gained or an alarm switched off, etc. A push-button may be connected between point "P" and the negative rail, and if this is momentarily pressed it will cause all the AND gates to latch low. This switching option was not used with the author's circuit. Touching one of the "wrong" contact pairs will also, of course, cause the AND gates to latch low.

### CONSTRUCTION

The relay can be any type having a coil resistance of 150Ω or more which will energise reliably at some 8 volts. The prototype used a reed relay. The quiescent current consumed by the circuit is negligibly low and the author's unit was powered by a PP3 battery. Once the switch has operated the current drawn is that required by the relay plus some 1 to 2mA in the base circuit of TR1 and about 7mA in LED1. If it is desired that the relay remain energised for relatively long periods, some constructors may prefer to use a 9 volt battery that is larger than PP3 size.

Most of the components are assembled on a 0.1 in. matrix Veroboard having 19 holes by 24 strips. Component layout is shown in Fig.3. Before soldering components in place, make the breaks in the copper strips as indicated. There are 16 of these breaks. To avoid damage to the two CMOS devices it is advisable to solder i.c. holders to the Veroboard and then plug in the two i.c.'s after all wiring has been completed.

The switch may be housed in any plastic case which will take the Veroboard, relay and battery. That employed by the author measured 4½ in. high by 3 in. wide. The contact sets consisted of large stainless steel pins, the diameters of the heads being about 2mm. Each pair is mounted with centres about 4mm. apart, 18 pins being required for the 9 contact pairs. The holes drilled in the front panel of the case allow the pins to be tight push fits. The wires from the Veroboard to the pins are routed to provide the required combination. Avoid overheating the pins when soldering as the plastic may then melt, causing the pins to become loose. Contacts can also be provided by small screws with nuts, the screws having heads with a bright plated finish.

The Veroboard is held in place by pieces of plastic glued to the sides of the case. In the prototype it is at the same end of the case as the contact pins, and its underside is kept well clear of the pin ends. Any other means of mounting the Veroboard which will not interfere with its circuit operation can be used. The l.e.d. is a push fit in a rubber grommet which is also mounted on the front panel.

The completed switch is checked by touching the 4 sequence contact sets in correct order. The l.e.d. should then light up. Next, touch one of the remaining contact sets and the l.e.d. should extinguish. It should not be possible to light it again, by touching the 4 correct sequence contacts, until the time delay imposed by C2 and R9 has elapsed.

The prototype has proved reliable in operation over a long period of time. The touch contacts must be kept clean and dry. Avoid spraying the contacts with ordinary cleaning agents such as are used for dusting, etc., as these can easily produce an insulating film which makes the contacts inoperative. ■



# TREMOLO

By

I. M. Attrill

Although it is one of the easiest forms of electronic musical effect, tremolo is still used very frequently these days. Tremolo units can be simple and inexpensive, and they make an ideal project for the constructor who is interested in electronic music. The design featured in this article produces very low levels of noise and distortion, and is suitable for use with a low level input such as that provided by a guitar pickup. It can handle inputs of up to several hundred millivolts r.m.s. without clipping, and is therefore also suitable for use with many organs and tone generators, etc.

The unit is powered by an internal 9 volt battery and is self-contained. The tremolo frequency is vari-

able from about 2.5 to 10Hz.

The tremolo effect is produced by amplitude modulating the input signal at tremolo frequency. This can be achieved by a unit consisting of two stages: a modulator which has a voltage gain proportional to a voltage fed to its control terminal, and a low frequency oscillator which provides the control voltage. The frequency of the oscillator should be variable to give what is considered the most desirable effect, and it should cause the signal amplitude to be varied smoothly.

Fig.1 shows the complete circuit of the tremolo unit.

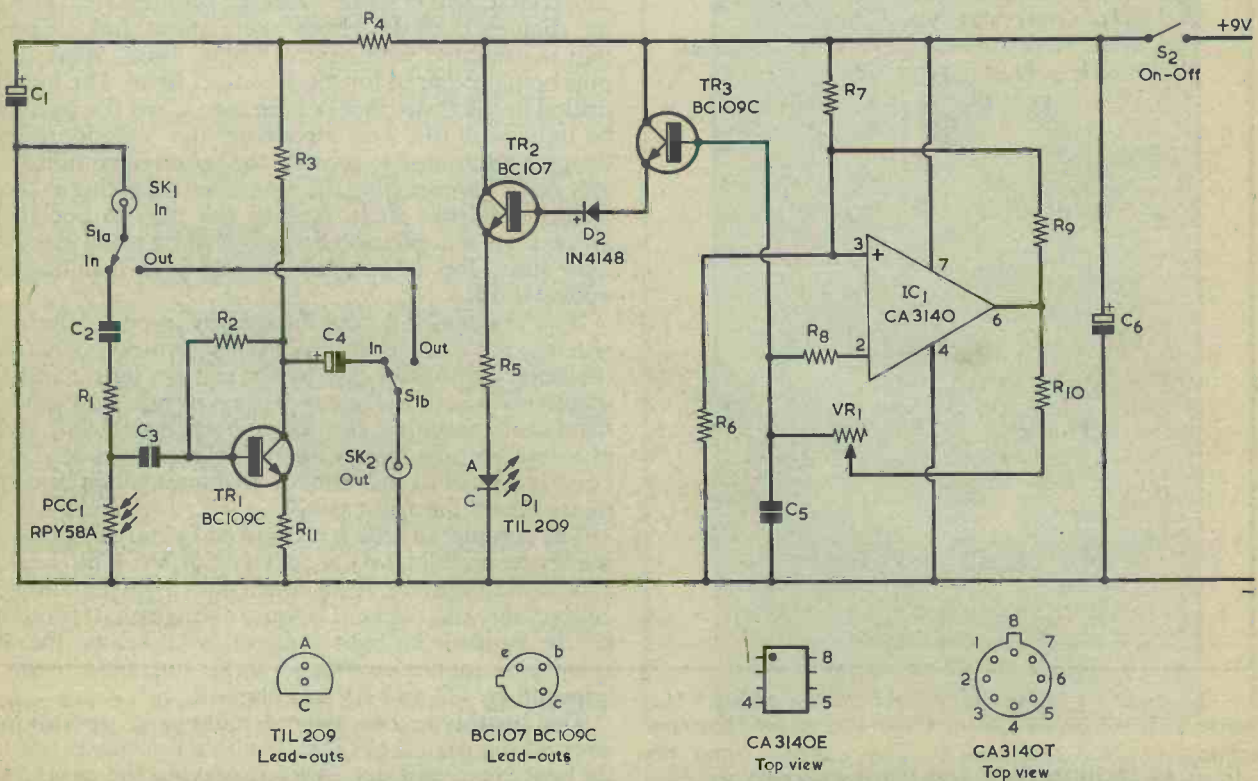


Fig.1. The circuit of the tremolo unit. IC1 appears in an oscillator circuit, the output of which is fed to the TIL209 light-emitting diode. The light from the l.e.d. falls on PCC1 and amplitude modulates the signal applied to TR1.

# MODULATION UNIT

*Easily made circuit adds brilliance to guitars, organs and electronic music. Opto coupling gives smooth modulation.*

## COMPONENTS

### Resistors

(All fixed values  $\frac{1}{4}$  watt 5% unless otherwise stated)

R1 8.2k $\Omega$   
R2 1.8M $\Omega$  10%  
R3 4.7k $\Omega$   
R4 470 $\Omega$   
R5 1.2k $\Omega$   
R6 100k $\Omega$   
R7 100k $\Omega$   
R8 10k $\Omega$   
R9 100k $\Omega$   
R10 33k $\Omega$   
R11 820 $\Omega$   
VR1 100k $\Omega$  potentiometer, linear

### Capacitors

C1 100 $\mu$ F electrolytic, 10V. Wkg.  
C2 1.5 $\mu$ F polyester type C280  
C3 0.1 $\mu$ F polyester type C280  
C4 4.7 $\mu$ F electrolytic, 10V. Wkg.  
C5 1.5 $\mu$ F polyester type C280  
C6 100 $\mu$ F electrolytic, 10V. Wkg.

### Semiconductors

TR1 BC109C  
TR2 BC107  
TR3 BC109C  
IC1 CA3140E or CA3140T  
D1 TIL209  
D2 IN4148

### Photoconductive Cell

PCC1 RPY58A

### Switches

S1 d.p.d.t. (see text)  
S2 s.p.s.t. rotary


### Sockets

SK1 3.5mm. jack socket (see text)  
SK2 3.5mm. jack socket (see text)
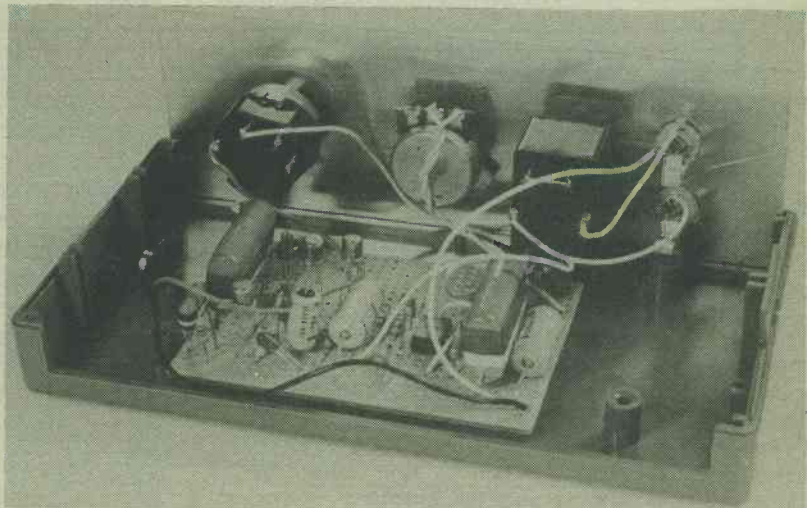
### Miscellaneous

Case (see text)  
9-volt battery type PP3  
Battery connector  
Veroboard, 0.1in. matrix  
2 control knobs  
Nuts, bolts, wire, etc.

Layout inside the case. There is plenty of room available for the 9 volt battery.



The input signal at socket SK1 is applied via S1(a) and d.c. blocking capacitor C2 to the attenuator consisting of R1 and PCC1. The output from the attenuator is fed via C3 to the common emitter amplifier, TR1, and the output signal at TR1 collector passes through C4 and S1 (b) to the output socket, SK2. Due to the unbypassed emitter resistor, R11,

the voltage gain of TR1 is of the order of 6 times only. The transistor has an input impedance at its base of several hundred kilohms.

PCC1 is a cadmium sulphide photo-resistor which has a minimum resistance of 200k $\Omega$  in total darkness. This resistance falls to less than 1k $\Omega$  under reasonably bright conditions. The signal input to TR1 base

can in consequence be varied by varying the light intensity on PCC1, and this effect produces the tremolo amplitude modulation.

The light which falls on PCC1 is provided by the light-emitting diode, D1. The tremolo oscillator employs operational amplifier IC1 in a circuit which has appeared in previous articles in this magazine, and whose functioning will only be briefly described here. The upper plate of C5 couples via the protection resistor, R8, to the inverting input of the i.c., whilst the non-inverting input is connected to the three equal value resistors, R6, R7 and R9. At switch-on, C5 will be discharged, whereupon the i.c. output will

be high and the non-inverting input will be at two-thirds of the supply potential. C5 will then charge via R10 and VR1 until its upper plate takes up the same potential as that at the non-inverting input. The i.c. output then triggers to the low state, causing the non-inverting input to be at about one-third of supply potential, and C5 commences to discharge. When the voltage across C5 falls to that at the non-inverting input the output triggers to the high state and C5 charges once more. The oscillation then continues, with C5 alternately charging and discharging. Oscillator frequency is controlled by VR1.

A roughly triangular waveform is given at the


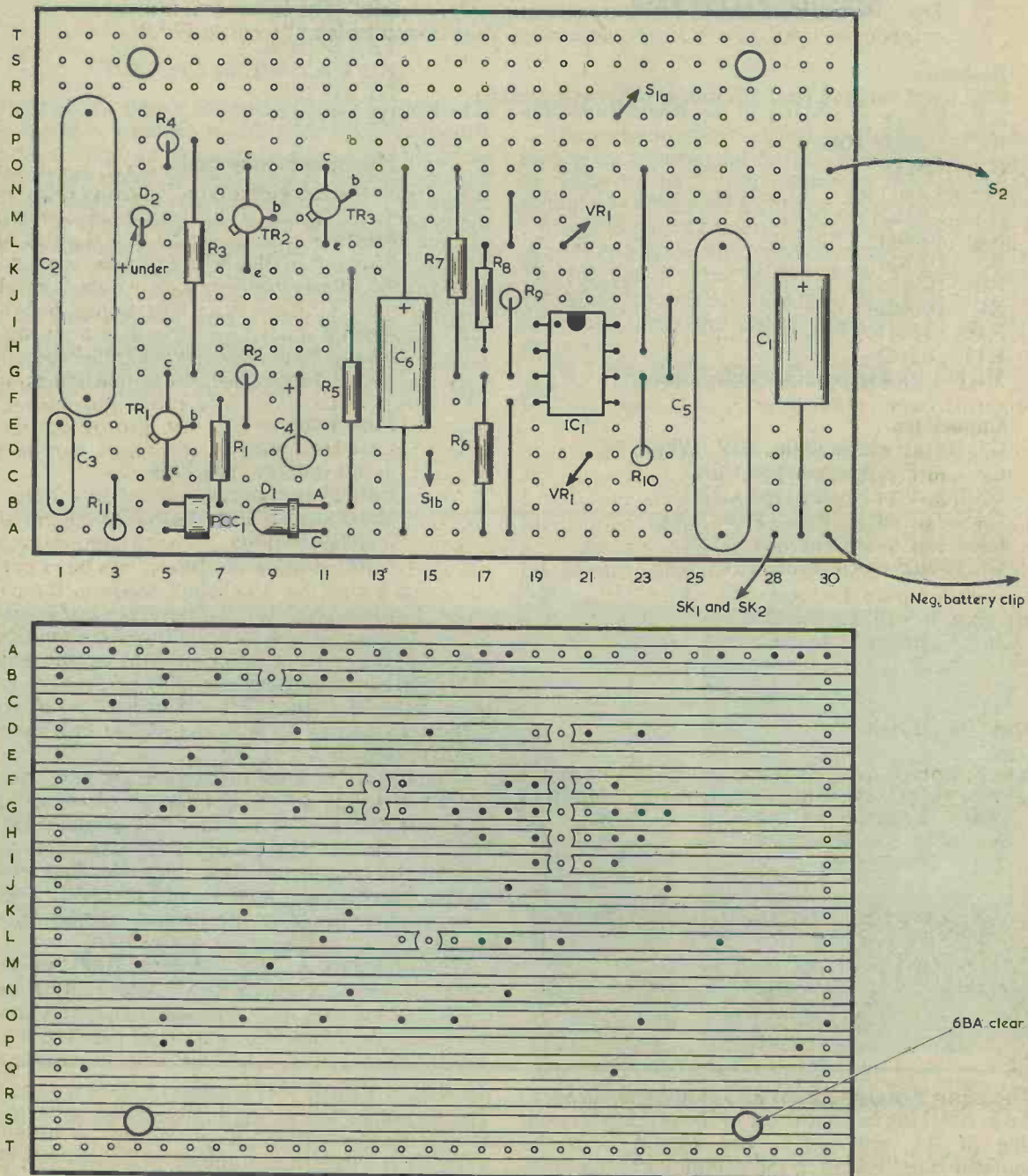


Fig.2. Most of the components are assembled on a Veroboard panel. This diagram shows the component and copper sides of the panel.

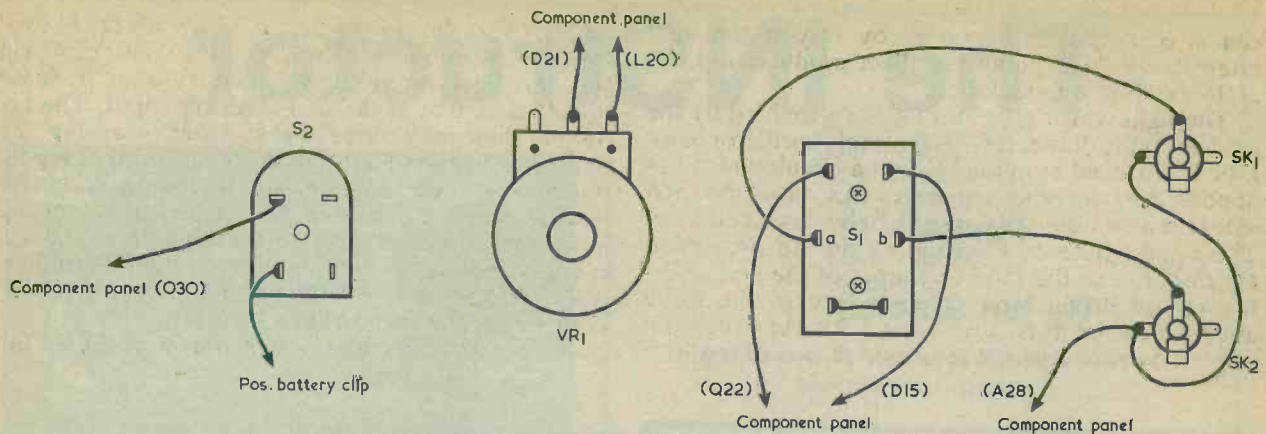

**Fig. 3.** The wiring to the components on the front panel. The letter and number references apply to the corresponding Veroboard holes shown in Fig. 2

upper plate of C5 and this is applied to the base of emitter follower TR3. TR3 couples via D2 to the base of a second emitter follower, TR2, with the result that the input impedance at TR3 base is very high and there is negligible loading on the oscillator. The emitter of TR2 drives the l.e.d., D1, and thereby causes the intensity of the light it emits to vary at oscillation frequency. D2 is interposed between the two transistors to increase the voltage drop from TR3 base to TR2 emitter and to thereby ensure that D1 is fully extinguished when the voltage from the oscillator is at its minimum level.

Switch S1(a)(b) can be used to bypass the unit, so that the tremolo effect can be switched out when it is not required. VR1 controls the tremolo frequency. S2 is the on-off switch for the unit, and current consumption from the 9 volt battery is only 3.5mA. The RPY58A specified for PCC1 is available from Maplin Electronic Supplies. Capacitor C4 is specified as 10V. Wkg., but it will be quite in order to employ a capacitor having a higher working voltage.

## CONSTRUCTION

The prototype tremolo unit is housed in a Verocase type 75-1238D, which has approximate dimensions



On the front panel the input and output sockets are to the left. Switch S1(a)(b) is to the right of these, followed by VR1 and S2.

of 153 by 84 by 59mm. The general layout can be seen from the accompanying photographs, whilst Fig. 3 shows the layout of the front panel components as seen from the rear. S1(a)(b) is a d.p.d.t. toggle switch. However, if the unit is to be used with a guitar, or in other circumstances, where it would be preferable for S1(a)(b) to be a foot operated switch, the components should be housed in a strong case such as a diecast box. S1(a)(b) could then be a heavy duty successive action push button switch mounted on the top of the case. The input and output jack sockets were 3.5mm. with the prototype but any other jack sockets, such as 1/4 in. types, can be employed if these are more convenient.

Most of the circuitry is assembled on a 0.1 in. matrix Veroboard having 30 holes by 20 copper strips. The layout is shown in Fig. 2. The two mounting holes should be drilled after the board has been cut out, following which the breaks are made in the copper strips. IC1 has a MOSFET input stage and is susceptible to damage by high static voltages. It should be the last component to be soldered into circuit, and the soldering iron must have a reliably earthed bit. Either the CA314OE (8 pin d.i.1. version) or the CA314OT (T099 cased) can be employed. The pin layout of both types is shown in Fig. 1.

PCC1 and D1 must be oriented so that the light output of D1 is directed at the sensitive surface of PCC1. If PCC1 is examined it will be found that the lead-out wires can be clearly seen connecting to one side of the component. It is the other side which is light-sensitive and which should face D1. The two components should be positioned so that they are touching each other, or are virtually so.


The wiring from the board to the front panel components is very straightforward and is illustrated in Fig. 3. When this wiring is completed it is merely necessary to mount the component panel to the bottom of the case using 6BA bolts and nuts with spacing washers under the panel. After a final check of the wiring the unit is then ready for testing and use. It will, of course, be necessary to fit the case lid for correct operation, in order that external light cannot fall on PCC1.

# The INSTRUCTOR

## Part 4

By Ian Sinclair
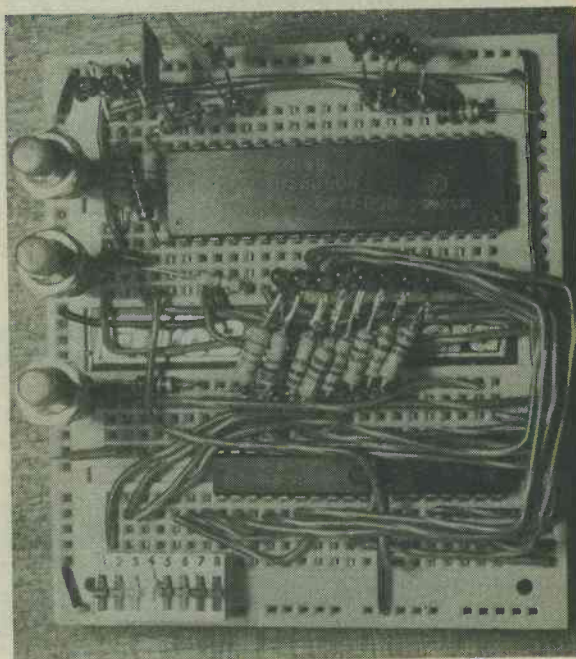
### A PRACTICAL INTRODUCTION TO MICROPROCESSORS



## *Subtraction and the use of negative numbers.*

In Part 3 we saw how the microprocessor deals with addition, and the use of the carry/link bit to "catch" the ninth bit in an addition. We're going to take a further look at this carry/link bit now because it's important in any arithmetical operation. If, for example, you have the carry/link bit set from some previous operation it will, unless you clear it, be automatically added in to a later addition. This may give you the impression that the microprocessor doesn't add very well!

### STATUS TO ACCUMULATOR

Last time, we detected whether the carry/link was set by doing an addition, and checking to see if an extra 1 had been added in. This is a rather roundabout method, so we'll start this month with something easier. It's a single byte instruction, coded as CSA, meaning Copy Status to Accumulator. The effect of this instruction, which is 00000110, is to set all the flip-flops of the accumulator to the same pattern as the flip-flops of the status register. As we've mentioned, the status register is a collection of flip-flops, each of which is used for some different signal. The carry/link bit is bit number 7 of the status register, so that when we carry out the CSA instruction the 7th data bit of the accumulator is set to 1, and we can use the display routine to look at the effect on the data l.e.d.'s. Fig. 1 shows a short routine which gives you a bit of practice in this - it starts, after reset, with the instruction SCL, set carry/link, which sets the carry/link to logic 1. The next step, CSA copies this into the accumulator and

then the two display steps let you see the l.e.d.'s lit. Providing you remembered to reset (so that all registers started at zero), the display will show 10000000, with only D7 lit, indicating that bit 7 of the status register was set. Remember that counting of these flip-flops always starts at 0, so that D7 is what one would normally call the 8th bit.

Just to make certain, the next part of the program in Fig. 1 resets the carry bit. The NOP instruction allows the 8060 to return to normal memory addressing, then CCL clears the carry/link (to zero). Once again, we look at the result by using CSA followed by the display routine. This time, all the data l.e.d.'s are extinguished showing that the carry/link was cleared.

Being able to inspect the carry/link in this way is useful, and it also lets us look at the other bits in the status register. If, by the way, you're wondering why the word "link" is used along with

```
RESET
SCL 0000011
CSA 00000110
Display
NOP 00001000
CCL 00000010
CSA 00000110
Display
```

Fig.1. Reading the status register.

```

RESET
LDI 11000100
196 11000100
ADI 11110100
244 11110100
CSA 00000110
Display

```

Fig.2. Setting the carry/link by a binary addition.

```

RESET
LDI 11000100
128 10000000
ADI 11110100
192 11000000
CSA 00000110
Display

```

Fig.3. A sum which sets another part of the status register.

```

RESET
00101101 complements to
11010010
Then add 1 to get
11010011 which is the 2's complement,
the number in its negative (SIGNED)
form.

```

Fig.4. Forming a 2's complement.

### SUBTRACTION AND NEGATIVE NUMBERS

The arithmetic circuits of microprocessors consist entirely of adders – so how do we subtract one number from another? The answer is that we don't – we add a negative number to a positive number, which comes to the same thing. The obvious next question is – how do we represent a negative in binary? Since we have only the two digits 1 and 0, we have to make use of these, and the answer is that we use a 1 in the most significant place (D7) of the number to show that a negative number is intended. Now this conversion of a positive number to a negative number can be done very easily by a process called 2's complement. The number we're going to subtract must consist of seven bits, because the eighth (D7) is reserved for the "negative sign" bit, and we convert it to negative form by writing all eight bits (Fig.4) and then complementing – swapping each 0 for a 1, and each 1 for a 0. When this has been done, we add 1 to the lowest place (D0) and that's our number in negative form, ready to *add* to the other one. A subtraction of this type, incidentally, involves discarding any carry from D7 so that if we carried out two subtractions in a row we would normally have to clear the carry/link bit. Do we hear an objection? Using seven bits only lets us use numbers up to 01111111, 127 in decimal. It's no problem, really because we can take larger numbers eight bits at a time, and only the highest bit of all needs to be used as a sign bit. Fig.5 shows an example of 15-bit arithmetic, with the 16th bit used as the sign bit. When this is done,

"carry" – be patient, all will be revealed later. Meantime, let's flex our muscles a bit and check if a binary sum has caused the carry/link to be set. The program is shown in Fig.2 – try it, and see if the carry/link is set.

That was straightforward, so now try something for yourself. Question is, does a decimal add cause the carry/link bit to be set? Try adding 10000011 and 10010101 (DCB for decimal 83 and 95), remembering that the add instruction has to be DAI (11101100).

Once you've sorted that out for yourself, it's time for a puzzle. Fig.3 shows the program, which is a simple binary addition of 10000000 and 11000000, followed by a look at the status register. Try it out. You'd expect to find D7 lit, because there's certain to be a carry – but why is D6 lit? The answer briefly is that this is another bit of the status register which has been set by this addition. It's called the overflow, and very shortly we'll see why it has been set.

Number (A) is 01001001 11001011  
 Number (B) is 00110111 11100101 and is to be subtracted from (A).

UPPER LOWER  
 BYTE BYTE

Complement the UPPER BYTE of B to 110010000  
 Then 2's complement the LOWER BYTE of B to  
 00011011  
 Then add:  
 01001001 11001011  
 11001000 00011011

00010001 11100110 and the carry bit is set  
 UPPER LOWER  
 BYTE BYTE of answer.

Fig.5. 15-bit arithmetic.

```

RESET
SCL 00000011
LDI 11000100
5 00000101
CAI 11111100
3 00000011
Display
NOP 00001000
CSA 00000110
Display

```

Fig.6. A simple subtraction program.

```

RESET
SCL 00000011
LDI 11000100
3 00000011
CAI 11111100
5 00000101
Display
NOP 00001000
CSA 00000110
Display

```

Fig.7. A subtraction which gives a negative answer.

only the lower byte of the number which is to be subtracted has 1 added to it, the upper byte is only complemented.

Back to the hardware. The instruction for subtraction is Complement and Add, and we'll use this in its immediate form, CAI, whose binary code is 11111100. This will only complement the number and add it in, it won't add 1. The reason is that 1 only has to be added to the lower byte, when a two byte number is used, so that addition is not part of the instruction. How do we add 1? We could, of course, load in a 1 and add it, but a much simpler method is to set the carry link before the complement and add step. This way, the 1 is automatically added in at the time when the complement is added – simple. Now try this out. A simple binary subtraction program is shown in Fig.6 – we're subtracting 00000011 from 00000101 (decimal 3 from 5) to get the expected answer of 00000010 (decimal 2). The program now goes on to check the status register – which should show the carry which we ignore. Now what happens if we do this the other way round and subtract 5 from 3? Fig. 7 shows the program steps. Try it out and jot down the answer, then find out what's happened to the status register.

No carry in the status register? The answer looks a bit odd too, doesn't it? The reason is that this is a negative answer, and the 1 in the eighth (D7) place indicates this. To make sense of it we have to convert it back to ordinary form by reversing the 2's complement process. This is done by subtracting 1 or by adding 11111111, which is the two's complement of -1, giving the sum 11111101, which is complemented to 00000010, or decimal 2. We can make the microprocessor go

through this routine by using the program in Fig.8. Note that we have started with the result of the subtraction loaded in, because it saves having to start again from scratch. When we copied the status register to the accumulator we lost the data which was in the accumulator.

#### EXTENSION REGISTER

There is a way of preserving that data byte, though, when we want to copy status, and it's shown in the programs of Figs. 8 and 9. The two new instructions are XAE and LDE. XAE means Exchange Accumulator and Extension, and it swaps the byte in the accumulator with the byte in another register called the extension register. If we always start a program with a reset, we can expect that the extension register will be full of zeros when we make this step, so that the result is to tuck away the byte which was in the accumulator and leave a clear accumulator. We can then copy the status register and look at it, knowing that the two sets of bytes are preserved. To look again at the byte which is now in the extension register we use the instruction LDE – Load Accumulator from Extension. This doesn't erase the byte in the extension register, it merely copies it into the accumulator.

Now for some problems. Suppose we use the microprocessor to add two numbers, and one or both of these numbers starts (8th place, D7) with a 1. Does the microprocessor treat this as a negative number, or does it have some magical way of being able to tell the difference between, say 10011010, meaning plus 154, and 10011010, meaning - 102?

```

RESET
LDI 11000100
-2 11111110
ADI 11110100
-1 11111111
CCL 00000010
XAE 00000001
CAE 01111000
Display

```

Fig.8. "Unscrambling" a 2's complement number.

```

RESET
SCL 00000011
LDI 11000100
3 00000011
CAI 11111100
5 00000101
XAE 00000001
CSA 00000110
Display
NOP 00001000
LDE 01000000
Display

```

Fig.9. Using the extension register to store an answer.



10011010 as an unsigned number is  $2 + 8 + 16 + 128 = 154$ .  
 10011010 taken as a signed number is found by subtracting 1 (or ADDING 11111111) to get 10011001, then complementing to get 01100110. This number is 102 in decimal and, because it was a signed number, we must write it as  $-102$ .

**Fig.10. Two identical binary numbers with different meanings.**

See Fig. 10. The answer is simpler than you might think – it can't! The microprocessor simply carries out binary arithmetic and what you make of the numbers is entirely up to you. As a help, though, there's a warning signal which lets you know if you have to be careful about an answer. It's called the overflow bit (OV) and it's bit 6 (counting 0 to 7) on the status register.

To see this in action, try out the four addition programs which are shown in Fig. 11, note the answers and check the OV bit by using the CSA, Display, procedure. The reasons go like this. In example (a) the numbers are positive, no matter how you look at it, and the answer is also positive. There's no carry out of the 7th or 8th place (D6 or D7). The answer is correct, and the OV is not set. In example (b) there are carries out of D6 and D7, and the carry out of D7 causes the carry/link to be set. If we think of this as straightforward unsigned arithmetic, then we're adding decimal 197 to decimal 233, and getting (remembering the 9th bit in the carry/link) the answer decimal 430. Looks all right, but suppose we were thinking of these two as negative numbers? If we were using signed arithmetic, then 11000101 is decimal  $-59$ , and 11101001 is decimal  $-23$ , giving the answer  $-82$ , which is correct. No matter what we make of the figures, then, the arithmetic is correct.

Now for (c). If we take both numbers as unsigned, so that the highest order 1 (in D7) represents decimal 128, then the answer is correct (remembering the carry bit). What if we take the

```
00111101
+ 00011001
```

```
01010110
(a)
```

```
11000101
+ 11101001
```

```
10101110
(b)
```

```
10100010
+ 10011001
```

```
00111011
(c)
```

```
01010110
+ 01110011
```

```
11001001
(d)
```

**Fig.11. Additions which cause different effects on carry and overflow.**

D7 1's as meaning negative sign? 10100010 then means decimal  $-94$ , and 10011001 is decimal  $-103$ , adding to  $-197$ . The biggest number we can handle with seven digits, though, is 128, and the eighth digit has become 0, indicating a positive number! This is an overflow, and the overflow status is set to warn us. If we are using signed numbers, then the 0 at the start is false; the number is really negative. If we reverse the 1's complement on the result, we get the correct answer,  $-197$ .

Next, example (d). Once again, the sum causes no difficulties with unsigned arithmetic, but the answer looks wrong when we think of these as positive numbers, and the answer as negative! Once again, the overflow bit is set as a warning

**RESET**

```
LDI 11000100
    11100111 lower A
SCL 00000011
CAI 11111100
    01011001 lower B
XAE 00000001 stores result in extension
LDE 01000000 brings it back (but leaves a copy in the extension)
Display . . so that you can look at it
LDI 11000100
    00101000 upper A
CAI 11111100
    00011010 upper B
Display
The lower byte of the answer is still in the extension.
```

**Fig.12. The carry used in double-byte subtractions.**

Mnemonic	Code	Operation
LDE	01000000	Load the accumulator from the extension.
XAE	00000001	Exchange accumulator and extension
ANE	01010000	AND extension with accumulator
ORE	01011000	OR extension with accumulator
XRE	01100000	X-OR extension with accumulator
DAE	01101000	Decimal add extension to accumulator
ADE	01110000	Binary add extension to accumulator
CAE	01111000	Complement and add extension to accumulator

Note. In each of these instructions, apart from the exchange instruction, the number stored in the extension register is not cleared nor changed. The accumulator ends up with the result of the instruction.

Fig.13. The extension register instructions summarised.

that two positive numbers don't produce a negative answer. What the overflow flag warns, then, is that we can use the D7 bits as part of the number, but that its sign is wrong. This bit is used as a warning only – it's never added in anywhere. If it has to be checked in a program, the procedure is to copy the status register to the accumulator (carrying any valuable data byte in memory or in the extension register) and then use logical AND to the byte with the pattern 01000000 – we'll explain that later. These status register bits, incidentally, are often called "flags", so that we refer to the carry/link flag and the overflow flag as being set (to 1) or reset (to 0).

Now what does the carry/link bit do when we subtract? Common sense leads to the conclusion that it simply does exactly as it always does – if it's set, it adds in on the next byte. To see what this does we can try a two byte subtraction, as shown in Fig. 12. What we're doing is subtracting (B) 0001101001011001 from (A) 0010100011100111, and it's done in two bytes, as you would expect. We start by loading the lower byte of the number (A), 11100111 and setting the carry/link so that when we complement and add immediate (CAI), we have carried out a 2's complement subtraction.


We can display this byte and also preserve it in the extension register, and then load in the upper byte of number A. Using the complement and add on the upper byte of number B then gives the result of upper byte subtraction, which can be displayed in the usual way. Note that we only need to set the carry/link bit for the lower byte, after that everything is automatic – the carry/link is reset when the first complement and add is put in, then set again by the carry from this stage, to be added in at the next complement and add step.

Now for some homework. Could you write and try out a program so that you could look again at the lower byte of the answer, which was stored in the extension register? Remember that this will be stored only if you haven't reset.

Just one final point. All the arithmetic operations we've looked at so far can also be carried out on numbers in the extension register, using the commands shown in Fig.13. This lets us carry out arithmetic operations on two bytes separately, but the same carry/link is used, so that we need to take great care that a carry from an operation in one register is not taken to the other register unless we want it. Obviously, if we're carrying out double byte arithmetic we'll want the carry, but whatever we're doing we mustn't forget it!

Next month – Logic Operations.

(To be continued)

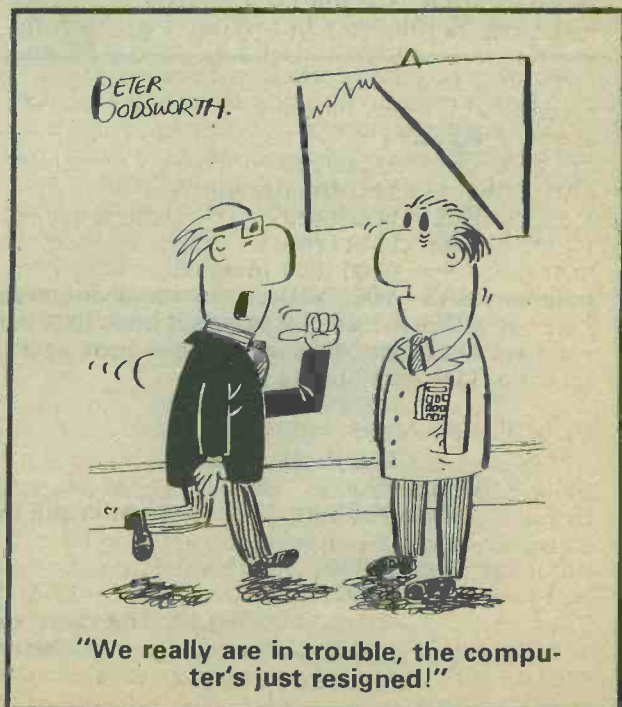

# COIL - COUPLED



## S. W. CONVERTER

By R. A. Penfold

*INDUCTIVE COUPLING TO M.W. radio — no wires.*

*19 to 67 metres.*

*Full superhet selectivity.*

In conjunction with an ordinary medium wave superhet receiver having a ferrite aerial this unit permits reception on the short wave broadcast bands in the range of 4.5 to 16MHz. The range gives full coverage of the 19, 25, 31, 41 and 49 metre bands. The 20 and 40 metre amateur bands are also covered, but the converter is not recommended for amateur bands reception and is really intended as a means of increasing the number of broadcast stations which can be received with an ordinary domestic radio.

There is no need to make any modifications to the receiver with which the converter is used, and there are no direct connections between the converter and the receiver. The converter radiates a strong local signal at a nominal frequency of 1.6MHz, or 188 metres, and this is picked up by the ferrite aerial of the radio. It is merely necessary to place the converter near the receiver and then tune the latter to a quiet point around 1.6MHz. Short wave tuning is then carried out with the converter controls, which alter the received short wave signal frequencies to the 1.6MHz reception frequency of the radio.

### BLOCK DIAGRAM

The stage line-up of the converter is shown in the block diagram of Fig. 1. The aerial signal is selected by the input tuned circuit and is applied to the mixer stage. So also is the output of a tunable oscillator. The difference frequency is then extracted from the mixer by a tuned radiator coil which is resonant at 1.6MHz. The signal and oscillator tuning capacitors are ganged and the two tuned circuits are set up so that the oscillator frequency is always higher than the aerial signal frequency by 1.6MHz. The principle is the

same as that encountered in the first stages of a conventional superhet, and the aerial and oscillator coils specified would produce an intermediate frequency of 1.6MHz in a normal superhet application.

As with the superhet, this line-up can be subject to interference by image signals. If, for instance, it is desired to receive a signal of 10MHz, the oscillator would be set to 11.6MHz to give the difference frequency of 1.6MHz. An image signal at 13.2MHz, which also gives a difference frequency with the oscillator of 1.6MHz, could then break through. It is the

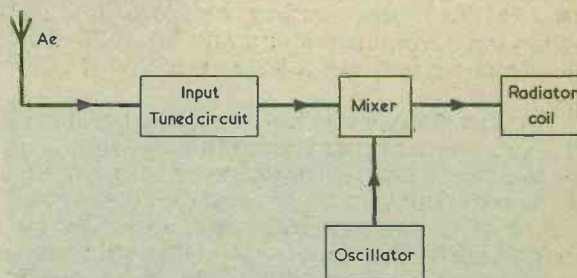


Fig. 1. The stage line-up of the short wave converter. The radiator coil causes an output signal at a nominal frequency of 1.6MHz to be coupled into the ferrite rod aerial of a medium wave receiver. No interconnecting wires are needed between the converter and the receiver.

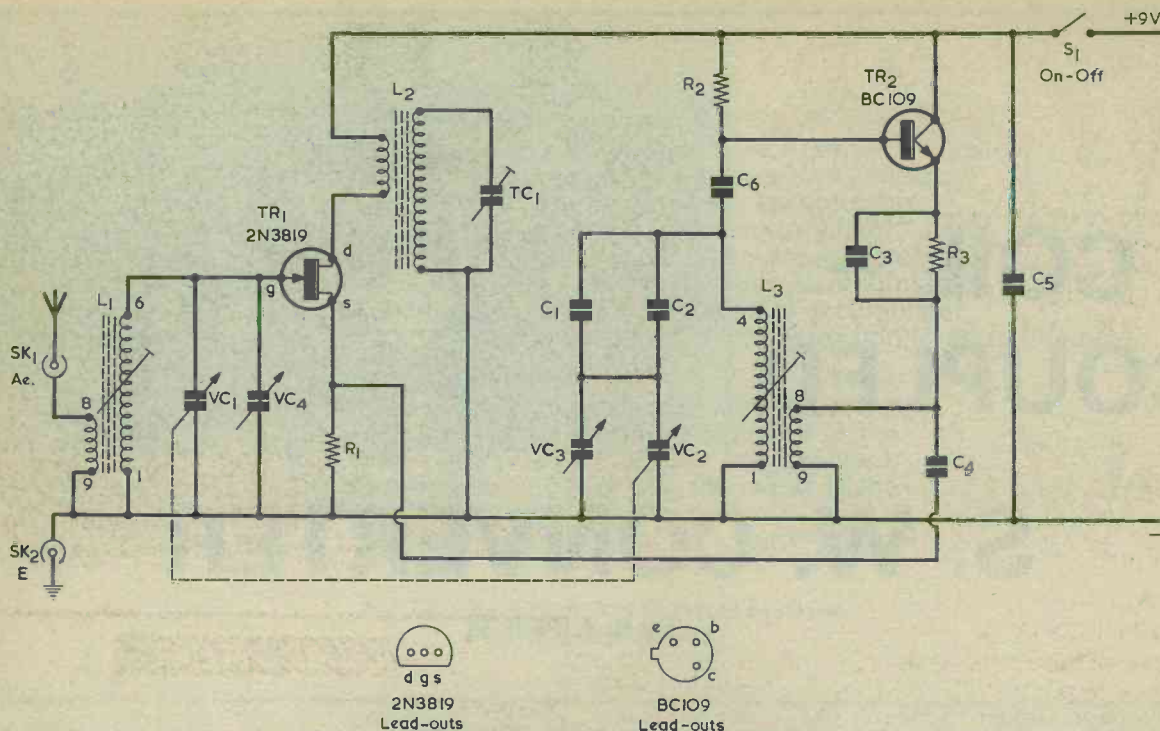


Fig. 2. The circuit of the short wave converter. L1 is the aerial input coil, L3 the oscillator coil and L2 the radiator coil.

function of the aerial tuned circuit to boost the strength of the required aerial signal and to attenuate the unwanted image signal.

The mixer output is coupled to the radiator coil. A tuned coil is used here since, although it makes initial alignment of the converter a little more difficult, it produces a much stronger field strength than does an untuned coil. The coil is, in fact, the coil of a standard medium wave ferrite aerial. The local field strength from the radiator coil is quite high, but it rapidly falls in strength with distance from the coil, and there is no danger of the converter radiating sufficiently strongly to cause interference with other receivers.

#### CIRCUIT OPERATION

The circuit of the converter is shown in Fig. 2. The aerial is coupled to the tuned winding of L1 via the coupling winding, and the tuned winding connects directly to the gate of the mixer, TR1, which has a very high input impedance. The main tuning capacitor is VC1, with VC4 acting as an aerial trim capacitor. There is a third coupling winding on L1 which is not used in the present circuit, and this winding is not shown in the circuit diagram. Source bias for TR1 is provided by R1.

TR2 is the oscillator, and is employed in the emitter follower mode. The tuned winding of L3 couples via C6 to the transistor base, and positive feedback is provided via the coupling winding in the emitter circuit of TR2. Like L1, L3 has a third winding which is not used, and which is not shown in Fig. 2. The main oscillator tuning capacitor is VC2, which is ganged with VC1. VC3 is an oscillator trim capacitor and functions as the bandspread control. Fine tuning is carried out by VC3, which is much easier to adjust than VC2 because of the limited frequency coverage it offers. C1 and C2 in parallel form the oscillator padding capacitor and ensure good tracking over the range covered. The oscillator output couples through C4 to the source of TR1.


The difference frequency present at the drain of TR1 is applied to the coupling winding on the output coil, L2. The large winding is tuned to the output frequency by TC1.

C5 is the supply bypass capacitor and S1 the on-off switch. The total current consumption is only about 2.5mA, which allows many hours of operation from the PP3 battery.



Two sockets, for aerial and earth, are mounted on the rear panel of the case.

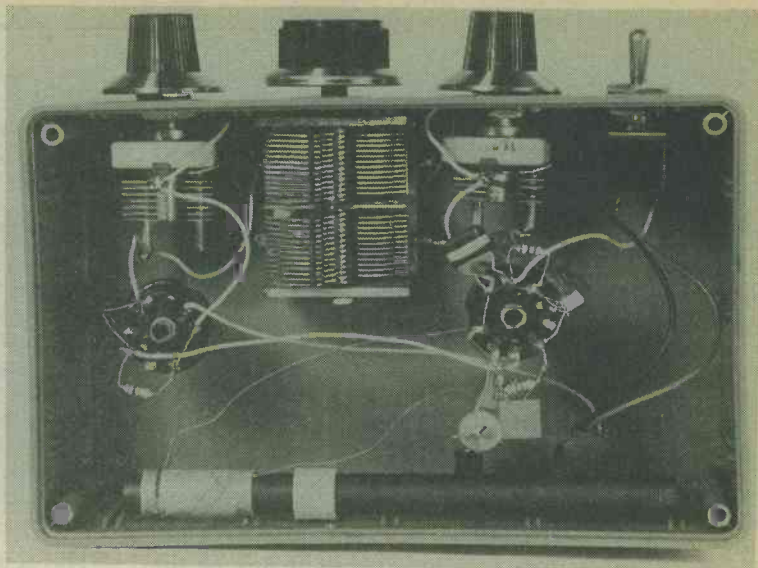Layout of components in the converter. The ferrite rod for the radiating output coil is secured to the rear panel of the case with a plastic clip.



## COMPONENTS

Most of the components are readily available from various suppliers. VC1, 2 is a 2-gang Jackson type 02 component without trimmers. The ferrite rod is secured in position with a plastic clamp, and a nylon "P" cable clip intended for wires of 10mm. diameter was employed in the prototype. This clip is available from Maplin Electronic Supplies. A metal clamp must not be used. In the author's unit, TC1 was a miniature film dielectric trimmer with a maximum capacitance of 65pF. This can also be obtained from Maplin Electronic Supplies. If difficulty is experienced in obtaining any of the Denco items they can be purchased direct from the manufacturer at Denco (Clacton) Ltd., 357/9 Old Road, Clacton-on-Sea, Essex, CO15 3RH.

The converter must be housed in a non-metallic case since a metallic one would shield L2 and prevent it from radiating the output signal. The author employed a plastic case measuring 160 by 100 by 60mm., and any plastic case of about this size, or slightly larger, which will accommodate the components with the same layout can be used. Parts of L1 and L3 project below the bottom of the case, which must be fitted with four cabinet feet at the corners to provide clearance.

## CONSTRUCTION

One of the 160 by 60mm. sides of the author's case forms the front panel. Appearing on this are, from left to right, switch S1, VC3, the 2-gang capacitor VC1,2, and VC4. S1, VC3 and VC4 are secured to the front panel in the normal manner by means of their bush mounting nuts. The hole for VC1,2 takes its ¼in. spindle only. If this component is examined it will be found that there are two 4BA tapped holes in the bottom of its metal frame, and the capacitor is mounted by passing two 4BA bolts through holes in the bottom of the case, passing spacing washers over these bolts inside the case to provide clearance for the ceramic mounts below the capacitor frame and then screwing the bolts into the two 4BA tapped holes. The bolts should be short, so that their upper ends pass only marginally inside the capacitor metal frame. This is an important point to observe because, if the mounting bolts are too long, their upper ends can damage the fixed or moving vanes of the capacitor.

## COMPONENTS

### Resistors

(All ¼ watt 5%)

R1 1kΩ  
R2 1MΩ  
R3 2.7kΩ

### Capacitors

C1 470pF polystyrene  
C2 470pF polystyrene  
C3 180pF ceramic plate  
C4 0.015μF ceramic plate or polyester.  
C5 0.1μF polyester.  
C6 220pF ceramic plate  
VC1,2 365pF + 365pF 2-gang variable, type 02 (Jackson)  
VC3 25pF variable, type C804 (Jackson)  
VC4 50pF variable, type C804 (Jackson)  
TC1 65pF trimmer, film dielectric

### Inductors

L1 Transistor tuning coil, Blue, Range 4T (Denco)  
L2 Ferrite rod aerial type MW5FR (Denco)  
L3 Transistor tuning coil, White, Range 4T (Denco)

### Semiconductors

TR1 2N3819  
TR2 BC109

### Switch

S1 s.p.s.t. toggle

### Sockets

SK1 4mm. insulated socket, red  
SK2 4mm. insulated socket, black

### Miscellaneous

Plastic case (see text)  
9 volt battery type PP3  
Battery connector  
2 B9A valveholders  
3 control knobs  
Plastic clip, 10mm. (see text)  
4 cabinet feet  
Nuts, bolts, wire, etc.

The positions of the holes in the front panel and in the case bottom are measured off from the capacitor itself. With the capacitor employed by the author, the first 4BA bolt was positioned about 15mm. back from the front panel and the second about 34mm. back from the front panel, both being in line with the spindle hole in the panel. However, there is a possibility that the 4BA tapped holes may be positioned differently with some capacitors and so measurements must be taken from the actual component which is to be used. Since the process of marking out and drilling the three holes for the 2-gang capacitor is a little critical, it is recommended that these three holes be drilled first before making the holes for the other three front panel controls.

VC1,2 has a solder tag common with its metal frame on its underside and two p.v.c. covered wires about 6in. long are soldered to this before it is finally mounted. These wires, shortened as necessary, will later be soldered to the moving vane tags of VC3 and VC4. To avoid damage, do not mount any of the variable capacitors until all the remaining holes in the case have been drilled out.

The ferrite rod coil, L2, is mounted near the upper edge of the rear panel, and a hole is required for securing its plastic clamp. SK1 and SK2 are mounted lower down, near the S1 end of the case.

Two mounting holes of about 6.5mm. diameter are required in the bottom of the case for L1 and L3. L1 is positioned behind VC4 and L3 behind VC3, and they should have the tag orientation shown in Fig. 3. Now that all the holes in the case have been drilled the components may be finally mounted. L1 and L3 are secured by the plastic nuts supplied with them. These nuts should be made finger tight only, as the plastic

threads in the nuts or formers can be stripped if they are over-tightened.

### WIRING

The converter is wired up as shown in Fig. 3. It is not advisable to solder directly to the pins of L1 and L3 as the heat of a soldering iron can cause the plastic of the coil formers to melt. In consequence a B9A valveholder is passed over the pins of each coil, and connections are soldered to the valveholder tags. Tags 3 and 4 of L1 are used as dummy anchor tags, as also are tags 2, 3, 6 and 7 of L3. TC1 is mounted by soldering one of its tags to SK2. The front section of the 2-gang capacitor is VC1 and the rear section is VC2. On L2, the tuned winding is the long winding, and the coupling winding is the short winding. All wiring should be kept reasonably short and direct.

The battery fits in the space behind S1.

### AERIAL AND EARTH

The converter is designed for use with an ordinary long wire aerial consisting of some 10 to 40 metres of aerial wire strung up as high as possible and preferably well clear of buildings and other large objects. Where such an aerial is not practicable a short length of ordinary connecting wire, say about 3 metres long, strung around the walls of a room can be used instead. This will give quite acceptable results, but the performance will not of course be as good as is given with a proper outside aerial.

An earth connection is not essential, and it will probably be found to give only a modest increase in signal strengths. The best type of earth is given by a metal pipe buried outside in the soil. A lead, which is as short as possible, connects the pipe to SK2 of the converter.


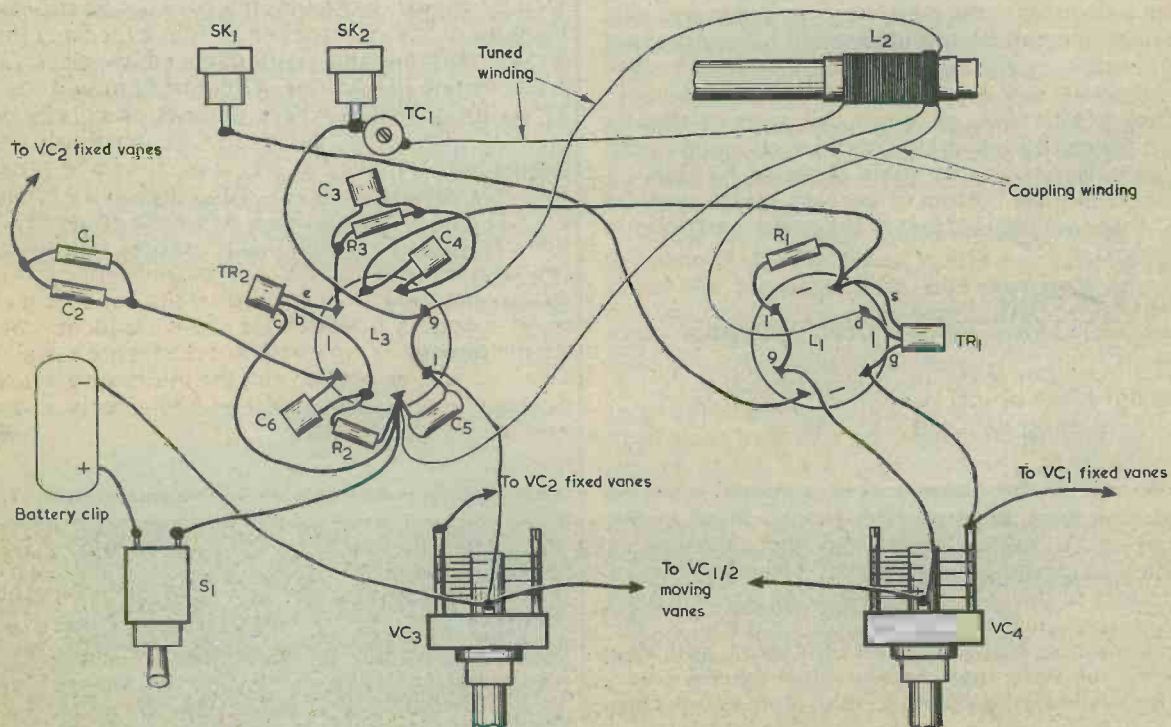


Fig. 3. Wiring up the converter. For ease of presentation, the wiring is shown spread out. In practice, wiring should be kept reasonably short and direct.

Another view  
of the internal wiring.

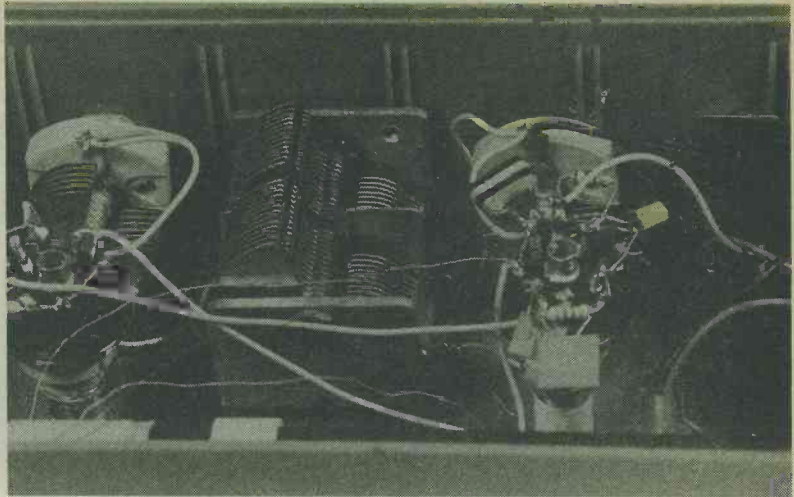

### ADJUSTMENT AND USE

First tune the radio receiver to the high frequency end of the medium wave band as near as possible to 1.6MHz and search for a quiet spot on the band. It is unlikely that it will be possible, after dark, to find a spot which is completely free of any signal, but it should be possible to find a spot where there are only weak background signals which will not significantly interfere with the much stronger output signal from the converter.

L1 and L3 are supplied with their cores fully screwed in, and these should initially be adjusted so that about 2 to 3mm. of metal screw thread protrudes from the plastic of each coil former. The coil former for L2 should be at or near the end of the ferrite rod, although its precise positioning is not very critical. With the medium wave receiver close to the converter, switch on the latter and adjust VC1,2 in search of signals. If none can be found, repeat the operation

with TC1 at various settings. When a station has been found, tune it in as accurately as possible by means of VC3, and then adjust TC1 for optimum results.

After this, many stations should be received at good strength, with VC4 being adjusted to peak the signals. Next, tune in a signal with VC1,2 at about half maximum capacitance and set VC4 for about half its maximum value. Adjust the core of L1 to peak the signal. It should then be possible to peak received signals with VC4, whatever the setting of VC1,2. It may be found that there are two peak settings for VC4, with different stations appearing at each peak. The correct setting is the one with the vanes of VC4 more fully meshed. It is the image response which is being peaked at the other setting.

The positioning of converter and medium wave receiver relative to each other does not seem to be especially critical. However, this may not be the case with some radios, whereupon a little experimenting will soon indicate the positioning which gives the greatest degree of coupling. There will probably be a few relative positions where there is practically no signal transfer, and these should obviously be avoided. Note that the receiver must always be tuned to the same spot on the band when employed with the converter as, otherwise, TC1 will need to be readjusted each time the converter is used. It may sometimes happen that a station appears quite strongly on what was originally a quiet part of the band. It may then be necessary to search for a new frequency, but often the directional properties of the ferrite aerial in the receiver can be used to null the interfering signal. This simply involves rotating the receiver for minimum interference. ■



The front panel components, from left to right, are on-off switch S1, VC3, the 2-gang capacitor and VC4.

### BACK NUMBERS

For the benefit of new readers we would draw attention to our back number service.

We retain past issues for a period of two years and we can, occasionally, supply copies more than two years old. The cost is 73p, inclusive of postage and packing.

Before undertaking any constructional project described in a back issue, it must be borne in mind that components readily available at the time of publication may no longer be so.

# SHORT WAVE NEWS

FOR DX LISTENERS



By Frank A. Baldwin

Times = GMT

Frequencies = kHz

From time to time, the subject of clandestine transmitters is dealt with in this series of articles. Several readers have expressed an interest in these transmissions – an interest shared by the writer – therefore as an opening gambit this month, we again deal with some clandestines recently logged.

“A Voz de Resistencia de Angola” on 4950 at 1820, YL with songs in Portuguese, OM with a harangue in vernacular, YL announcer in a programme of African songs. Carrier abruptly off the air at 1900 without anthem. This is a pro-Unita transmitter which sometimes also identifies as “A Voz de Verdade”.

“Radio Freedom From South Yemen” on 9960 at 1900, OM with a revolutionary song in Arabic – very militant and rousing – then suddenly off the air. All this after a preceding harangue in Arabic. This is an anti-communist and South Yemen government transmitter.

“Radio Homeland” on 15555 at 1747, two OM’s with a discussion in Persian followed by a programme of Persian songs and music in typical style until 1759, at which time there were several announcements by a YL and then sign-off without any anthem. “Radio Homeland” is an anti-Persian government transmitter.

Readers wishing to log any of the above listed transmitters would be well advised to tune to the frequencies shown well in advance of the times quoted, for each logging will be seen to have been made at the signing-off time. Perhaps someone will even succeed in hearing the opening transmissions. If so, let me know.

## AROUND THE DIAL

In which are listed some of the more interesting transmissions logged within recent weeks. Note however that due to publication delay, a few of the time and frequency details may have changed – but not many. To hear the type of programmes stated, all the reader must do is to locate the correct channels at the times quoted here. This article is penned solely for your guidance over the short wave spectrum.

### ● PORTUGAL

Lisbon on 21530 at 1610, OM with a newscast of world events. (OM = Old Man – a male announcer).

Station identification at 1613 “International Service of Radio Portugal”. All in the English programme intended for the Middle East, scheduled from 1600 to 1630.

### ● BELGIUM

Brussels on 6010 at 1605, YL with a local newscast and details of recent events in Belgium in an English programme presumably intended for African consumption. (YL = Young Lady – female announcer).

### ● SPAIN

Madrid on 9765 at 2030, time-check ‘pips’, OM with news of internal affairs and events in the English programme for Europe, scheduled from 2010 to 2110.

### ● WEST GERMANY

Cologne on 17875 at 0626, YL with station identification and announcements at the end of the English programme for West Africa, scheduled from 0600 to 0630.

### ● FINLAND

Helsinki on 15265 at 1940, OM with the English programmed “Northern Report”. The English programme is radiated from 1930 to 2000 to both Europe and Africa.

### ● NORTH KOREA

Radio Pyongyang on 6575 at 2000, OM and YL with station identification and National Anthem various announcements after a preceding interval signal. This was followed by details of English transmissions from Pyongyang. All this in the English programme for Europe, scheduled from 2000 to 2150.

Radio Pyongyang on a measured 9977 at 1642, YL with a talk about communal projects in North Korea. This programme in English is beamed to the Middle East and Africa and is scheduled from 1500 to 1630 according to announcements.

### ● SOUTH KOREA

Seoul on 6480 at 1918, YL announcer, OM song in Korean, in the English programme for Europe, scheduled from 1900 to 2000.

Seoul on 9870 at 1629, OM and YL with an English



programme for the Middle East and North Africa, scheduled from 1600 to 1700. YL with station identification at 1637.

● **CHINA**

Radio Peking on **9530** at 2039, OM with a newscast of world events from the Chinese point of view in an English programme intended for European consumption, scheduled from 2030 to 2230.

● **INDIA**

AIR (All India Radio) Delhi on **5335** at 1344, a programme of local songs and music in an English programme for South East Asia, scheduled from 1330 to 1500. YL with station identification and schedule details at 1500.

● **PAKISTAN**

Radio Pakistan on **15485** at 1742, YL with the "World Service" English programme to the U.K. OM station identification in English then into an Urdu transmission also for the U.K. at 1744.

● **ISRAEL**

Jerusalem on **17685** at 1927, OM with station identification after a newscast of both local and world events in an English programme announced for Africa, Europe and North America from 1900 to 1930. A programme in French followed at 1930.

● **AUSTRALIA**

Melbourne on **21680** at 0659, YL with station identification, details of frequencies, times and target areas. Time-check 'pips' at 0700 followed by a newscast of both local and world events, OM announcer. On this channel the programme is directed both to Asia and the U.K. Also logged on **9570** in parallel to the same target areas and on **15240** directed to the Pacific Area. Other announced channels were **11740**, **15115**, **17725** and **17870** but a rapid survey resulted in either (a) very poor reception or (b) co-channel QRM.

Melbourne on **15240** at 0558, somewhat earlier than the above transmission, OM announcements in English, including frequencies and target areas in an English programme intended for Africa and the Pacific. Time-check 'pips' at 0600 followed by a newscast in English.

● **SOUTH AFRICA**

RSA (Radio South Africa) Johannesburg on **21535** at 0605, OM with station identification, announcement of frequencies and target areas followed by the news in an English programme for West Africa and Europe, scheduled from 0600 to 0700.

● **GRENADA**

Radio Free Grenada on **15105** at 2022, YL with announcements in English, then into a programme of local music and songs. At 2030, OM with a talk about African origins.

● **USSR**

Radio Moscow on **15350** at 1825, OM with a programme in Swahili to Africa (where else?), typical African music and at 1830 news about African affairs from the USSR point of view.

● **AFGHANISTAN**

Kabul on **4740** at 1845, OM announcer in Pashto,

local music and songs. This is the Home Service 1 which is scheduled from 0125 to 0330 and from 1340 to 1940.

● **UGANDA**

Kampala on a measured **5027** at 1903, OM with a newscast in English mainly about local affairs. This is the National Programme which uses English, Swahili and French at various times in the schedule, which is from (weekdays) 1300 to 2100 and from 1400 to 2100. Saturdays and Sundays there is an additional transmission from 0300 to 0545 and on Sundays the afternoon programmes commence at 1430. The power of this recently installed transmitter is 250kW.

● **NICARAGUA**

La Voz de Nicaragua on **5950** at 0155, OM with identification "La Voz de Nicaragua", announcements in Spanish then YL with a folk ballad.

● **COLOMBIA**

Em. Nuevo Mundo, Bogota, on **4755** at 0054, OM with songs in Spanish, local-style music. This one radiates on a 24-hour schedule and the power is 1kW.

La Voz del Cinaruco, Arauca, on **4865** at 0114, OM with announcements in Spanish, local pops on records. The schedule here is from 0900 to a variable 0330 and the power is 1kW.

● **COSTA RICA**

Faro del Caribe (Lighthouse of the Caribbean), San Jose, on **5055** at 0130, OM with station identification in Spanish followed by light orchestral music. The schedule is from 1030 to 0400 (closing time is variable to 0430) and the power is 5kW.

● **VENEZUELA**

Radio Valera, Valera, on **4840** at 0106, OM's with a discussion in Spanish on both local and world sporting events. Radio Valera operates from 0900 to 0400 (variable closing time) and the power is 1kW.

● **BRAZIL**

Radio Ribamar, Maranhao, on **4785** at 0058, OM with a love song in Portuguese. OM with station identification at 0100. The schedule is from 0800 to 0400 and the power is 5kW.

Radio Tabajara, Joao Pessoa, on a measured **4797** at 0103, YL with local pop song, OM announcer. The schedule is from 0730 to 0400 and the power is 2kW. The frequency is liable to vary, nominal is **4795**.

Radio Difusora Taubate, Taubate, on **4925** at 0120, OM announcer in Portuguese, OM with a ballad about the lovelorn. The schedule is from 0830 to 0300 and the power is 1kW.

Radio Cultural do Para, Belem, on **5045** at 0127, OM with local pops in typical style. The schedule is from 0900 to 0300 (variable) and the power is 10kW.

Radio Bare, Manaus, on **4895** at 0117, OM with announcements in Portuguese, local-style dance music on records. The schedule is from 0800 to 0400 (closing time is variable) and the power is 5kW.

Radio Clube do Para, Belem, on **4855** at 0110, local-style pops, OM with lots of commercials. This one operates from 0700 to 0400 and the power is 10kW.

Radio Nacional Brasileira, Brasilia, on **15125** at 2030, OM with identification and a talk about Brazilian postage stamps in an English programme for Europe, scheduled from 2000 to 2100.

# TWO 20dB AMPLIFIERS

**1MΩ Input impedance. Flat response from zero to 1MHz. Switching option for a.c. or d.c. working.**

The second 20dB amplifier, described this month, has a voltage gain of 10 times, is d.c. coupled (with a switched option for a.c. coupling at the input) and has an input impedance of about 1MΩ. Its response is flat from zero to approximately 1MHz. It is primarily intended for use ahead of an oscilloscope when measuring small direct voltages or when investigating waveforms containing relatively low frequencies which are too small in amplitude to provide a useful display with the oscilloscope on its own.

There are other uses for the amplifier and it can be employed to boost the sensitivity of an audio millivoltmeter. It can also be used in conjunction with an ordinary multimeter to provide a sensitive high impedance voltmeter. If, for example, the multimeter is switched to read 0.5 volts, an input of only 500 millivolts to the amplifier will produce full-scale deflection in the meter. The consequent sensitivity is 2MΩ per volt, as compared with the 20kΩ per volt of many standard multimeters. The amplifier can similarly boost the sensitivity of a multimeter switched to a low a.c. volts range. Note, however, that the maximum d.c. output of the amplifier is plus or minus 7 volts, and the maximum a.c. output is approximately 5 volts r.m.s.

## THE CIRCUIT


An operational amplifier is an obvious choice for the unit, and such an amplifier appears in the circuit diagram of Fig.3. The op-amp employed is the CA3130, which has CMOS input and output stages with a bipolar section providing the main voltage gain of the device. With the value specified for the compensation capacitor, C4, the CA3130 gives a unity gain bandwidth in excess of 10MHz and a slew rate of over 20 volts per microsecond.

The op-amp is used in the non-inverting mode with the closed loop gain controlled by the negative feedback resistors, R3 and R2. The gain is equal to the sum of R3 and R2 divided by the value of R2, giving the required figure of 10 times. Both these resistors must be close tolerance types, either 2% or preferably 1%. They are specified as ½ watt because close tolerance resistors are normally available in this rating, rather than in ¼ watt. The calculated level of voltage gain can, of course, only be maintained at frequencies where the op-amp open loop voltage gain is at least 10 times. The frequency at which the gain of an operational amplifier becomes inadequate to maintain the closed loop gain is given roughly by dividing the unity

gain bandwidth by the closed loop gain so that the theoretical closed loop frequency response becomes 1MHz. Tests on the prototype bear this out in practice.

The circuit has dual balanced supply rails with a central earth rail, as is the convention with d.c. coupled operational amplifiers. Two small PP3 batteries provide power, and are connected to the CA3130 via voltage dropping resistors R4 and R6. The resistors are needed because the maximum supply rating for the CA3130 is plus and minus 8 volts. The supply current is a fraction under 1mA, producing a voltage drop of about 2 volts across each resistor and a nominal supply of plus and minus 7 volts.

R1 biases the non-inverting input to earth and causes the input impedance of the amplifier to be 1MΩ. This impedance reduces somewhat at high fre-

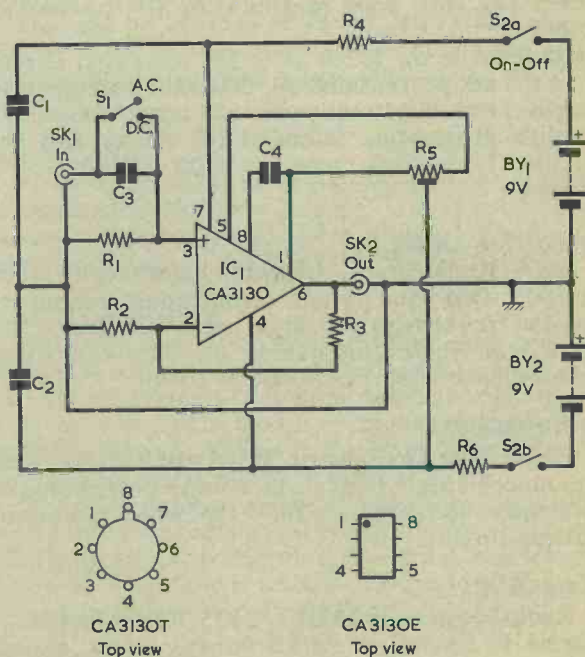

**Fig.3. The d.c. coupled 20dB amplifier. This incorporates an operational amplifier type CA3130.**

## Part 2

By  
M. V. Hastings



The amplifier is housed in an all-metal case which provides screening. This is particularly important with the present design because of its high input impedance.


quencies because of stray capacitances and the input capacitance of the CA3130. There is a d.c. path from input socket SK1 when S1 is closed and the circuit is then direct coupled throughout. Opening S1 causes C3 to be in series with the input to provide d.c. blocking, and the low frequency response has a -3dB point at approximately 10Hz.

An offset null control is required to ensure that the quiescent output voltage is zero. The offset null adjustment is given by R5. S2 (a) (b) is the on-off switch and controls the two outside supply rails. C1 and C2 are supply bypass capacitors.
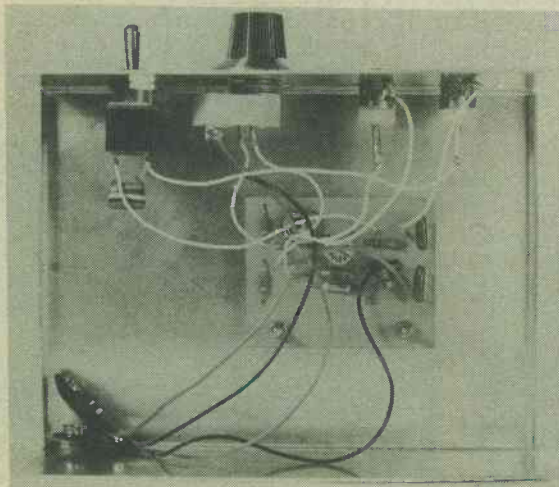
### CONSTRUCTION

The amplifier must be housed in an all-metal case to screen it from mains hum and other sources of interference. The prototype is fitted in a metal instrument case type BC1, which has approximate dimensions of 6 by 4½ by 2in. This case is available from Harrison Bros., P.O. Box 55, Westcliff-on-Sea, Essex, SS0 7LQ.

The front panel layout can be seen in the photographs. From left to right the items mounted on the front panel are SK1, SK2, S2(a)(b) and S1. The two



The printed circuit module is secured to the bottom of the case with two 6BA bolts and nuts, together with spacing washers.

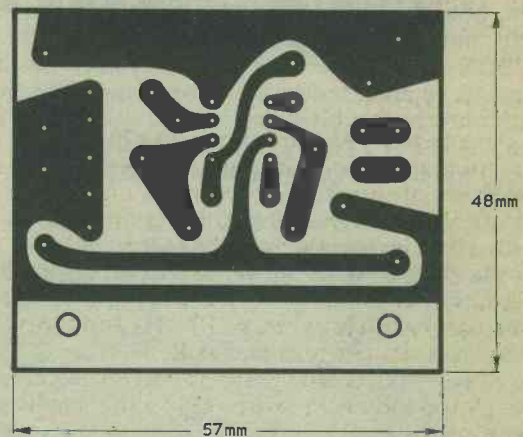
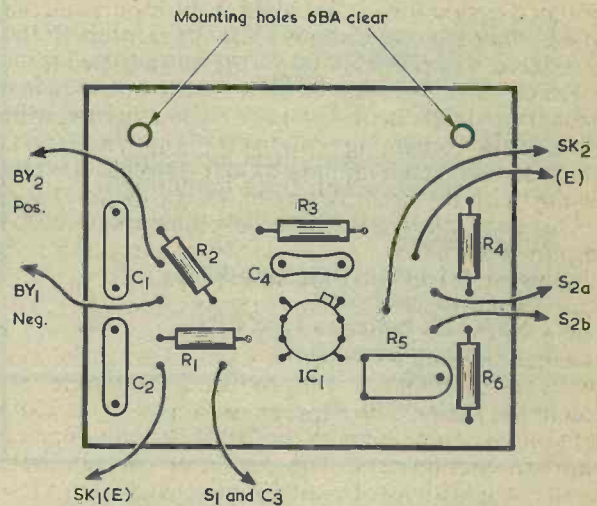


Fig.4. The printed circuit layout pattern. This will take either a CA3130T or a CA3130E.

sockets are flush mounting coaxial types. A solder tag is fitted behind the panel, under the upper securing nut of each socket. C3 is soldered to the tags of S1.

The remaining components are assembled on the printed circuit board, which is shown full size in Fig.4.

## COMPONENTS

### Resistors

- R1 1M $\Omega$  watt 5%
- R2 300 $\Omega$   $\frac{1}{2}$  watt 1% or 2%
- R3 2.7k $\Omega$   $\frac{1}{2}$  watt 1% or 2%
- R4 2.2k $\Omega$   $\frac{1}{4}$  watt 5%
- R5 100k $\Omega$  pre-set potentiometer, 0.1 watt horizontal
- R6 2.2k $\Omega$   $\frac{1}{4}$  watt 5%

### Capacitors

- C1 0.1 $\mu$ F polyester type C280
- C2 0.1 $\mu$ F polyester type C280
- C3 0.1 $\mu$ F polyester type C280
- C4 10pF ceramic or polystyrene

### Semiconductors

- IC1 CA3130T or CA3130E

### Switches

- S1 s.p.s.t. toggle
- S2 (a) (b) d.p.s.t. rotary

### Sockets

- SK1 coaxial socket, flush mounting
- SK2 coaxial socket, flush mounting.

### Miscellaneous

- Metal instrument case (see text)
- Printed circuit board
- 2-off 9-volt batteries type PP3
- 2-off battery connectors
- Control knob
- Nuts, bolts, wire, etc.



On the front panel are the input and output coaxial sockets, the on-off switch and the a.c. - d.c. input selection switch.


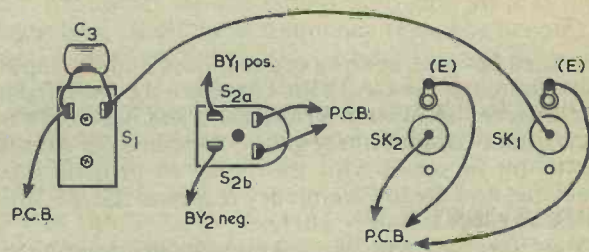


Fig.5. Wiring to the components mounted on the front panel. Use a continuity tester to confirm the appropriate tags of S2(a) (b) before wiring to this switch, as some switches may have a different tag layout

The board is produced and wired up in the normal way, but it should be remembered that the i.c. has CMOS inputs. The i.c. should therefore be the last item to be soldered to the board, and the soldering iron must have a bit which is reliably earthed. Either the CA3130T (TO-99 case) or the CA3130E (8 pin d.i.l.) will fit into the printed circuit layout. The wiring


between the board and the front panel components is illustrated in Fig.5. The board is mounted to the base of the case with two 6BA bolts and nuts, spacing washers being used to keep the board underside clear of the inside of the case.

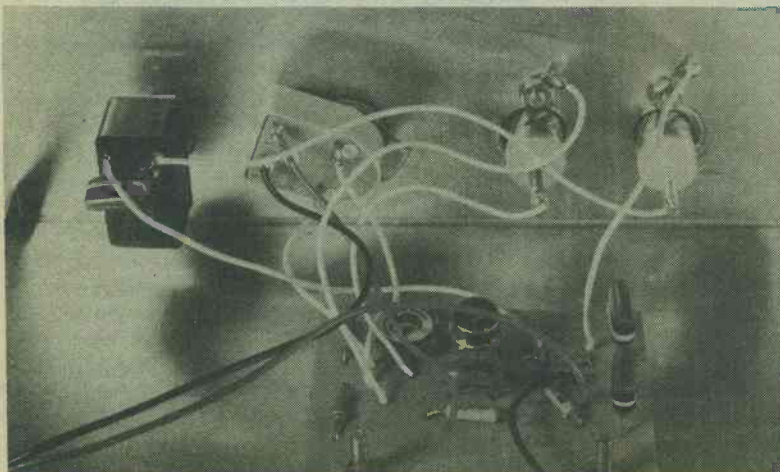Since this amplifier has a lower bandwidth than the unit described last month, there is no need to use



Looking at the wiring to the rear of the front panel

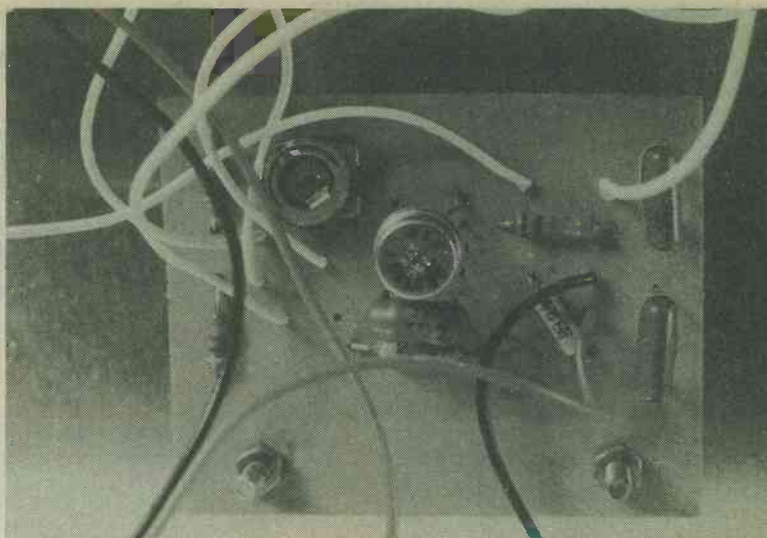A close-up of the printed circuit board assembly.



screened leads inside the case for the connections to SK1 and SK2. External test leads connecting to these two sockets should, however, consist of screened wires.

#### ADJUSTMENT

The only adjustment required to the completed amplifier is the setting up of R5. Connect a multimeter set to read 0-5 volts or more d.c. across the output of the amplifier with negative to chassis. Adjust R5 so

that its slider is about 45 degrees anti-clockwise of its central setting and switch on the amplifier. There will probably be a positive deflection in the meter, or a small negative deflection, and R5 is then adjusted for a zero reading. The multimeter is then switched to its lowest d.c. volts range and R5 finally trimmed for the zero reading.

The amplifier is then ready for use.

(Concluded)

---

## NEW DEFENCE AID

### HELICOPTER NIGHT VISION

Successfully installed on a Sea King helicopter is the new stabilized night vision system pioneered by Marconi Avionics Limited. This gives what is virtually all-round vision and has been developed under contract from the UK Ministry of Defence.

The system, produced by the Marconi Electro-Optical Surveillance Division at Basildon, is for mounting beneath the nose of a helicopter and it consists of a stabilized platform bearing a night vision sensor. In the case of the Sea King installation, the sensor is a Marconi Avionics V325 Intensified Isocon camera, which is


already in production and is in service with the Royal Air Force. It can produce useful television pictures at light levels down to overcast starlight.

A very novel feature of the use of the night vision sensor is that it can be rapidly directed, from side to side and downwards, in synchronism with the pilot's head movement. By projecting an image of the night scene into the pilot's eye via his helmet-mounted display, he can "see" in the dark wherever he happens to be looking, including straight downwards.

The system has an exceptionally fast response (over 100 degrees per second) to direc-

tional commands and is highly stabilized against the effects of helicopter vibration and its movements in pitch and yaw. This exceptional performance means that the system can follow virtually every movement of the pilot's head, whether fast or slow. As a result, pilots soon become used to the new equipment, and very rapidly gain confidence in operating with it.

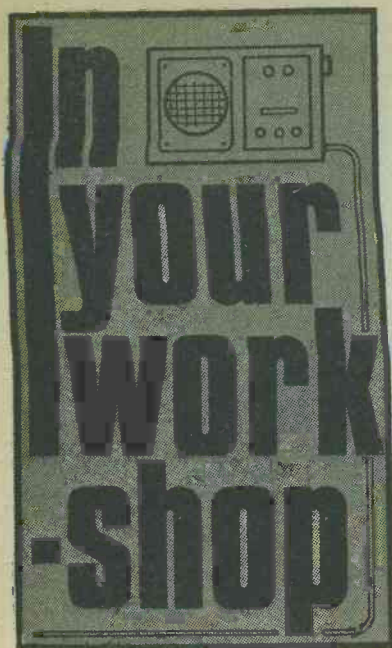The platform has been constructed to the stringent standards already proven with the highly successful "Heli-Tele" daylight viewing system, now in service with the British Army and the security services of several other nations.



# RADIO DISTORTION FAULT

You don't *have* to know  
what's inside an i.c.!

"What," asked Dick cheerfully, "is white on the top and bottom, green in the middle and jumps all round the room?"

Smithy glanced at him malevolently.

"Look," he pronounced sternly, "there's just an hour to go before we shut up the shop for the weekend, and we've only got this single a.m.-f.m. portable to clear up before we leave. Which means that I don't intend to waste time with these ridiculous jokes of yours."

"Shall I give you a clue?"

"I don't even *want* a clue!"

"It could," said Dick unabashed, "alternatively be brown on the top and bottom instead of white. But it would still be green in the middle and it would still jump all round the room."

Smithy put the portable radio on his bench and studiously ignored his assistant.

"Give up?"

"Give up?" repeated Smithy irately. "I'm not going to start!"

"I'll tell you then," said Dick jubilantly. "It's a frog sandwich!"

## I.C. AMPLIFIER

An expression of total incomprehension spread over Smithy's face.

"Is that your joke?"

"That's it," confirmed Dick.

"Good, isn't it?"

"I think it's dreadful. Now,

for goodness' sake let's get on with finding the fault in this radio."

"What is it," asked Dick, "that's white on the top, white on..."

"We will now," interrupted Smithy, "get on with this set. Okay?"

"Well yes, all right then," replied Dick, bringing his thoughts back to the more important matters of the moment. "What's wrong with it?"

Smithy inspected a label attached to the carrying handle of the radio.

"This just says 'Distortion'," he remarked. "Let's hear what it sounds like."

He pressed the medium wave button on the radio and swung its tuning control across the scale. The set was quite lively and picked up a number of signals without any significant second channel whistles. The volume was at a level suitable for listening in a quiet room and there was no noticeable distortion. Smithy tuned in a musical programme and turned up the volume. Distortion at once became evident, increasing in proportion with the loudness of the sound from the speaker.


Smithy pressed the long wave button and tuned to the Radio 4 signal on 1,500 metres. Exactly the same kind of distortion was present here. Finally,

he pulled out the telescopic aerial, pushed the f.m. button and tuned in the local v.h.f. signals. There was no change in the distortion.

"That distortion must be being introduced in the a.f. stages," volunteered Dick.

"I wouldn't argue with that at all," stated Smithy, "unless we've got a really weird fault we wouldn't get distortion in *both* the a.m. and the f.m. sections before the volume control. Besides, the a.f. signal going to the volume control must almost certainly be all right because there's no distortion at low volume levels. Would you like to start getting the back off the set while I get the service manual out? With a fault like distortion it's a good idea to have the circuit of the receiver in front of you, and it will often save a lot of time in looking for the snag. Oh, and check battery voltage on load, of course."

As Smithy walked over to the filing cabinet, Dick removed the battery cover and checked the battery voltage with the receiver switched on. His testmeter indicated a satisfactory voltage slightly in excess of 9 volts. He then started to remove the set back. Whilst he was doing so, Smithy returned with the service manual and opened it out at the circuit diagram. He quickly located the section showing

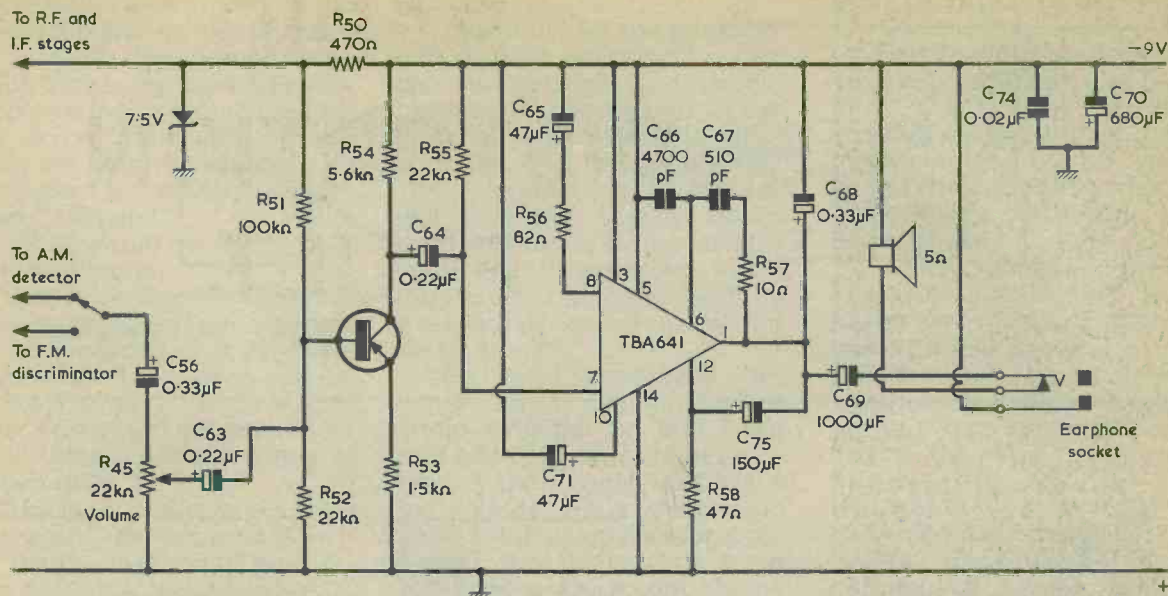

**Fig.1. The a.f. stages of the a.m.-f.m. radio examined by Dick and Smithy. Apart from a slight simplification at the a.m.-f.m. switch section and the volume control, this is taken from the circuit of the Ferguson Model 3182 Mains/Battery Portable Radio and shows the same R and C numbers. The 0.22µF and 0.33µF electrolytic capacitors are tantalum.**

the a.f. stages, and studied it silently. (Fig.1.)

"Oh no," breathed a voice at his right ear.

Startled, Smithy turned his head to see his assistant gazing unhappily over his shoulder at the circuit.

"What are you oh-no-ing about?"

"Those a.f. stages," wailed Dick. "There's an i.c. at the output!"

"Blimey," snorted Smithy. "We've had integrated circuits in domestic equipment for nearly the last ten years. Why should you suddenly start moaning about them now?"

"I've *always* moaned about them," complained Dick. "Just look at the circuit we've got here. We've got a triangle representing the i.c. amplifier, and a whole lot of resistors and capacitors connected to its pins. What we don't know is what exactly is *inside* that triangle!"

#### COMPONENT FUNCTIONS

"That's no problem," said Smithy. "With a fairly simple integrated circuit such as the a.f. amplifier one we've got here it's quite adequate to have just a rough general idea of

what's going on inside the i.c. without bothering about precise circuitry. I'll agree that things tend to get a bit mind-bending when we get on to i.c.'s like microprocessor chips, and with these the likes of you and me have just got to take the manufacturer's word that if we connect the chip up correctly and put in the right inputs we'll get the proper outputs. But, as I say, there's no need to have such an approach so far as the simpler i.c.'s are concerned."

The Serviceman turned the pages of the service manual and examined the Components List for the radio.

"Here's something interesting," he went on. "The maker of this radio has done us a favour by not only listing the components but also stating what their functions are. But before we look at these there are some obvious facts about this audio i.c. which are staring us in the face."

"What are they?"

"That pins 3 and 5 of the i.c. connect to the negative supply rail and that pin 14 is the positive supply input. Also, that pin 1 is the output pin."

"Ah yes," agreed Dick, "there isn't much deduction


needed there! The fact that the negative rail is drawn in this circuit above the positive rail can be a bit confusing at first when you're used to having the two rails the other way round."

"That's true," said Smithy, "but you often meet that sort of thing in these radio circuits. Now let's look at some of the components."


We can start off with C66, C67 and R57. All these are described in the manual as giving stability compensation." (Fig.2(a).)

"That will be like the compensation components which are needed with some op-amps," put in Dick. "The idea is that the capacitors roll off the upper frequencies."


"Exactly," confirmed Smithy. "If the i.c. was allowed to amplify at frequencies which were too high it would be virtually impossible to prevent stray feedback and the whole thing would burst into oscillation. So, when you find relatively low value capacitors, or relatively low value capacitors and resistors in series, connecting to the pins of an unfamiliar audio amplifier i.c. you can be quite certain that they're intended to provide

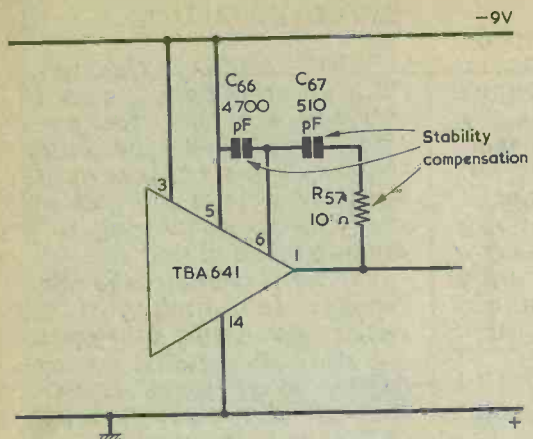


(a)

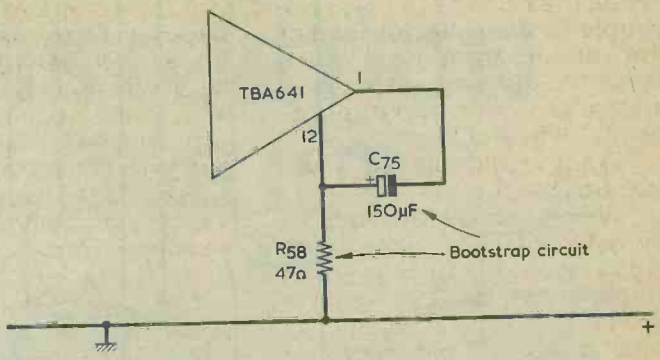


(b)

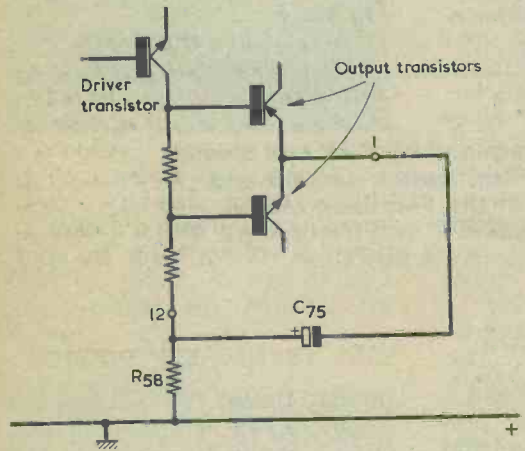

(c)

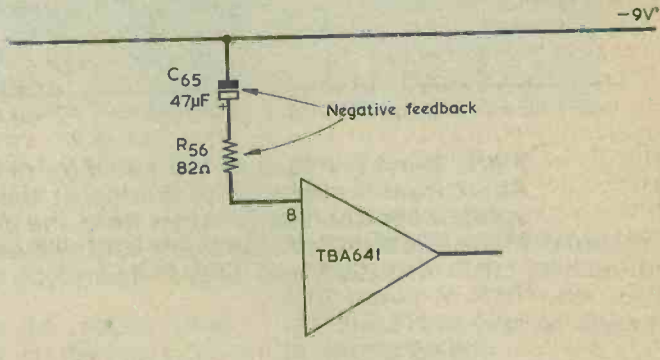

(d)

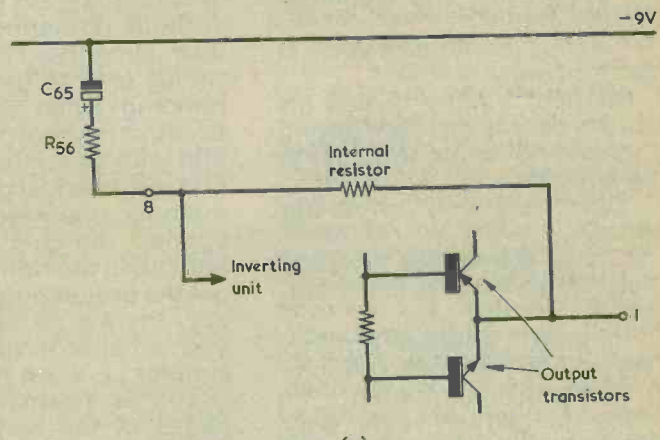

(e)

**Fig.2(a).** Relatively low value capacitors around the audio i.c. provide frequency compensation.

(b). A high value capacitor from the output to another pin, in a circuit such as is shown here, provides bootstrap coupling.

(c). The internal bootstrap circuitry will have the basic form illustrated here.

(d). External negative feedback components. The audio gain of the i.c. is controlled by the value of the resistor.

(e). Inside the i.c. an internal resistor will couple back from the output to an early inverting input.

signal. Whenever you get symptoms like that with an unknown audio i.c. the compensation components and their connections should be amongst the first things you should check."

"There's another capacitor," said Dick, "which connects the output pin to pin 12 of the i.c. But this one's an electrolytic with a value of 150 uF." (Fig.2(b).)

"That one's bound to be a bootstrap coupling capacitor," said Smithy, "and you can recognise it by the fact that it connects to the output and has the

frequency compensation."  
"What would happen if you had a fault there?"

"Well," said Smithy, "the most likely thing is that you'd get an open-circuit in a compensation loop. If this open-circuit caused the i.c. to go into violent oscillation at a supersonic frequency you might get a loud hiss from the speaker, or

you may even hear nothing at all from it. At the same time, the i.c. will quite possibly draw an excessively high current from the power supply. Should the oscillation be of a mild nature the i.c. might work reasonably well on high level a.f. signals but may burble away quietly to itself with low input signals or with no input



sort of high value you'd expect in an a.f. coupling circuit feeding a fairly low impedance. Inside the i.c. the capacitor will couple to the collector load of the driver transistor which feeds the output transistors in a standard bootstrap arrangement." (Fig.2(c).)

"What would happen if you had trouble there?"

"Well," replied Smithy, "if the capacitor went open-circuit the i.c. wouldn't give as much amplification to one set of half-cycles as it does to the other and you'd get distortion when the signal went above a certain level."

"That's what we've got with this radio," commented Dick.

"True," confirmed Smithy, "so we'll check the bootstrap capacitor in a minute. It's more difficult to predict what would happen if the capacitor went short-circuit, but there would most probably be a high loss of output power with distortion at all levels. There would probably be no output at all if the 47Ω resistor coupling pin 12 to the positive rail went open-circuit because there would then be no collector supply voltage for the internal driver transistor."

Dick turned his attention to another part of the circuit.

"There's an 82Ω resistor and a 47μF capacitor going from pin 8 of the i.c. to the negative rail," he announced. "What are they for?" (Fig.2(d).)

"The resistor," said Smithy, looking down at the service manual, "will be for gain control and the capacitor for d.c. blocking. The service manual refers to them as 'negative feedback' and as 'negative feedback and d.c. blocking' respectively."

"How do they work?"

"There'll be an internal resistor inside the i.c. from the output to an inverting point at or near the input of the internal amplifier. This and the external resistor then complete a standard negative feedback loop which allows the i.c. gain to be varied by the external resistor. If that external resistor goes low in value the amplifier gain will increase and if it goes high in value the amplifier gain will reduce." (Fig.2(e).)

"What happens if the resistor or the capacitor go open-

circuit?"

"Theoretically, the amplifier gain drops to unity but in practice the i.c. might go unstable because of the lack of a low impedance between the feedback pin and the supply rail. The manufacturer of the i.c. will normally specify upper and lower limits for the resistor value and the set-maker using the i.c. will, obviously, employ a resistor whose value is within these limits."

"So," said Dick slowly, "if I come across an unfamiliar audio amplifier i.c. and I see that one of its pins connects to one of the supply rails via a fairly large value electrolytic and a small value resistor, can I expect the resistor to be a component which controls the amplifier gain, with the electrolytic giving d.c. blocking?"

"You can," stated Smithy. "Incidentally, the resistor value usually lies between some 50Ω and 200Ω."

## BYPASS CAPACITOR

"Hey," said Dick cheerfully, "this a.f. amplifier i.c. is not so difficult after all. We don't know exactly just what is lurking inside the i.c. but we do know what jobs the external components connecting to it are supposed to do!"

"Which," chimed in Smithy, "makes fault-finding a lot easier when a snag develops in any of those external components. Well now, there's another electrolytic coupling an i.c. pin to the negative rail. That's the 47μF component connecting to pin 10." (Fig.3(a).)

"And what's that for?"

"It's a decoupling or bypass capacitor," stated Smithy, glancing for confirmation at the service manual. "Inside the i.c. there will be a decoupling supply resistor feeding a pre-amplifier stage and the decoupling is completed by the

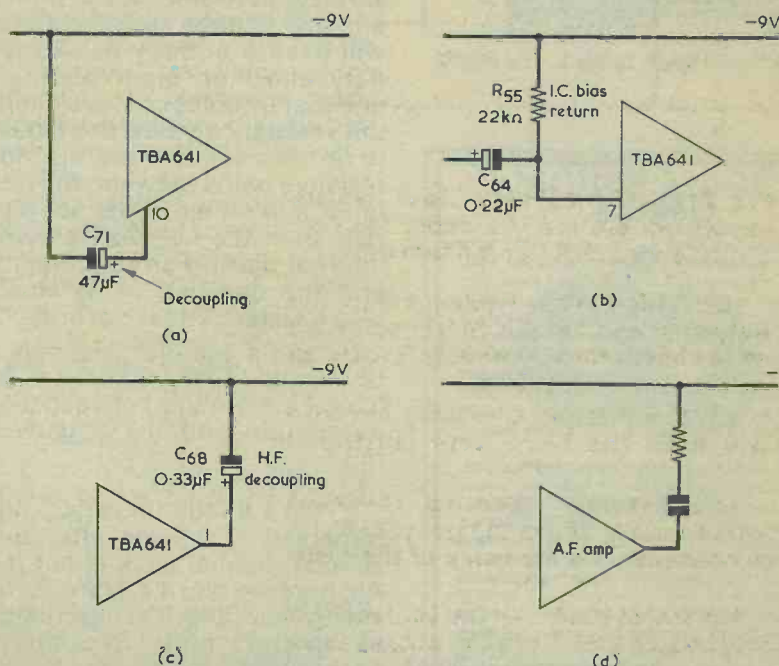


Fig.3(a). In company with an internal supply resistor feeding an internal pre-amplifier, the 47μF external capacitor completes a decoupling circuit.

(b). Audio i.c. input bias arrangements tend to vary between different i.c. types, but a resistor coupling to the negative rail is one of the more common circuits.

(c). The 0.33μF capacitor between the i.c. output and the negative rail maintains a fairly low output load impedance at the higher audio frequencies.

(d). A more common approach is to couple the i.c. output to one of the supply rails via a capacitor and very low value resistor in series.

## ELECTRONIC TUTOR KITS

Learn electronics the effective way by experiments. Each kit contains an illustrated handbook, which takes you step by step through the fundamentals of electronics, plus all the components needed. No soldering. Safe and instructive for even the young enthusiast. Kit 1, £5.85. Kit 2, £5.95. Kit 3, £6.15. SAE for leaflets on this and other RXG products.

**RXG ELECTRONICS LTD.**  
15 Walnut Tree Crescent,  
Sawbridgeworth, Herts, CM21 9EB.

## PEATS for PARTS

### ELECTRONIC COMPONENTS RADIO & TELEVISION

For the convenience of Irish  
enthusiasts we supply:

Radio & Electronics  
Constructor Data Books  
Panel Signs Transfers

Also a postal service

# peats

the world of electronics  
25 Parnell Street, Dublin 1. Tel 749972

## GAREX

V.H.F. Receivers SR-9 for 2-metres F.M., fully tunable 144-146MHz, 2-speed slow-motion dial, also 11 xtal controlled channels. Compact, sensitive, ideal for fixed or mobile listening. Built-in L.S., 12v D.C. operation £47.15 Inc. VAT. Crystals, if required: £2.60 each. All popular 2m. channels in stock. Marine band version (156 162MHz) £47.15 (xtals £2.90). Mains psu for above £11.95. Pocket VHF Receiver 12 channel xtal controlled complete with nicad and charger. 4MHz bandwidth in range 140-175MHz £57.95. Amateur and Marine xtals in stock, prices as SR-9.

Amplifier module new, fully assembled 6W IC unit, 12v D.C. Low impedance (4-8Ω) input and output for extn. speaker amplification, with circuit £2.75.

Neons min wire end 70p/10: £4.50/100

Slide switches min DPDT 20p ea; 5 plus: 16p

Resistor Kits E12 series, 22Ω to 1MΩ 57 values,

5% carbon film, 1/4W or 1/2W Starter pack, 5 each,

value (285) £3.10

Mixed pack, 5 each 1/4W plus 1/2W (570) £5.55

Standard pack, 10 each (570) £5.55

Giant pack, 25 each (1,425) £13.60

BNC Cable mtg socket 50Ω 25p; 5 plus: 20p;

PL259 UHF Plug and Reducer 75p; 5 plus: 67p;

SO239 UHF Socket panel mtd. 60p; 5 plus: 50p;

Nicad rechargeables physically equiv. to zinc-

carbon types: AAA (016) £1.80; AA(U7) £1.30;

CU(11) £3.35; PP3 £5.55. Any 5 plus: less 10%. Any

10 plus less 20%.

We stock V.H.F. & U.H.F. mobile aerials

s.a.e. details.

Access - Barclaycard

PRICES INCLUDE UK POST,  
PACKING & VAT

Mail order only

Sole Address

**GAREX ELECTRONICS**  
7 NORVIC ROAD, MARSWORTH.  
TRING, HERTS HP23 4LS  
Cheddington (STD 0296) 668684

external 47μF capacitor."

"Why do you need decoupling there?"

"Mainly to reduce hum if the i.c. is run from an a.c. mains power supply. If the i.c. is powered by a battery you can often leave out that external decoupling capacitor without running into any difficulties. Now, let's look next at the 22kΩ resistor connecting to the input of the amplifier. The service manual refers to this as an 'i.c. bias return' resistor."

Smithy pointed to the resistor in the circuit. (Fig.3(b).)

"Now, most audio output amplifier i.c.'s," he continued, "require a resistor between the input pin and the negative rail to set up the input bias conditions, and you can expect trouble if the resistor shifts seriously in value. However, you may encounter input bias arrangements which are different from this. The golden rule here is to assume that whatever resistor or resistors connect between the i.c. input and any voltage supply points will have a primary or secondary effect on input biasing, and that troubles could result if the resistance value or values is not correct. If there are no resistive paths between the i.c. input and either of the supply rails then the i.c. has its own internal biasing arrangements and the question of external bias resistance does not arise."

"There's another electrolytic," said Dick. "There's a 0.33μF electrolytic between the output pin and the negative rail."

Smithy frowned.

"That's a little unusual," he remarked. "Let's see what the service manual says about it. Ah, here we are. It's a tantalum electrolytic and it's described as giving 'high frequency decoupling'."

"What's it for?"

"It's to maintain a low impedance at the output as audio frequency increases," pronounced Smithy, "whereupon it counteracts the effect of rising impedance in the speaker and aids stability. Just a minute."

Smithy took a pen out of his pocket, pulled his note-pad towards him and carried out a quick calculation.

"That 0.33μF capacitor," he

stated, "will have a reactance of about 100Ω at 5kHz, and so it doesn't hold the impedance all that low at high audio frequencies. But it will hold it low enough to ensure that there isn't any risk of high frequency instability."

"You said just now," Dick reminded him, "that the 0.33μF capacitor was slightly unusual. Why's that?"

"It's because you usually have a capacitor and resistor in series at the output to reduce high frequency impedance, instead of having a capacitor on its own. The capacitor and resistor form what is called a Zobel network and typical values are around 0.1μF to 0.3μF for the capacitor, with the resistor having quite a low value of around 1Ω. Incidentally, if the i.c. doesn't have a Zobel network or a single capacitor coupling its output to one of the supply rails then you can safely assume that the i.c. is capable of working quite happily without it." (Fig.3(d).)

Smithy looked down at his watch.

"Ye gods," he gasped. "That's twenty minutes gone already, and we haven't even started looking for the fault in this radio!"

"Not to worry, Smithy," Dick consoled him. "At least you've told me how to work my way round an audio amplifier i.c. even when I've got hardly a clue as to what exactly is inside it. And if we do find the fault in this radio before knocking-off time I'll stay on afterwards if necessary to do the actual repair."


## FAULT FINDING

"Very well," said Smithy briskly. "We'll start off with obvious fault-finding checks first. Can you get at the printed board?"

"I can."


"Right then, testmeter ready! Switch on with the volume turned low and check the voltage between chassis and the output pin of the i.c."

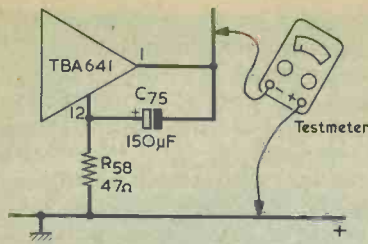Dick selected a voltage range on his testmeter, turned on the radio and checked the voltage between the circuit points referred to by Smithy. (Fig.4(a).)



(a)

Fig.4(a). Dick first measured the voltage at the output of the audio i.c.

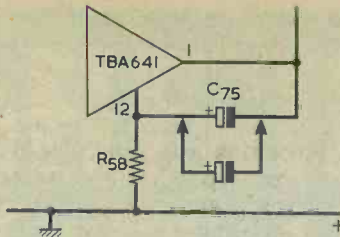

(b)

(b). He next checked the bootstrap capacitor by temporarily bridging it with another capacitor of similar value.

"I'm getting a reading of about 4.4 volts."

"Good," stated Smithy. "That's near enough to central voltage for us to assume, for the time being at any rate, that the input bias circuit for the i.c. is all right. Bootstrap circuit next! You may remember I said that an open-circuit bootstrap capacitor could possibly cause the distortion. So that's the next thing for you to check."

"How do I do that?"

"Turn up the receiver volume to give a distorted output and then bridge the capacitor with another 150µF capacitor."

Dick looked through a box of spare components on Smithy's bench.

"I can't find a 150µF," he stated after a few moments. "Will 100µF do?"

"Yes, of course," said Smithy impatiently. "Come on!"

Dick turned up the volume of the receiver and applied the 100µF capacitor across the 150µF capacitor on the printed board. There was a click in the speaker as he connected the 100µF capacitor into the bootstrap circuit but there was no alteration in the distortion level. (Fig.4(b).)

"Okay," said Smithy. "Well, that seems to eliminate the bootstrap circuit. Turn the volume down and let me think for a moment."

"Perhaps the i.c. is duffy," suggested Dick, as he reduced the volume level of the radio.

"Perhaps it is," agreed Smithy, "but it will still be the last thing we suspect."

"Why's that?"

"First, because i.c.'s are usually nearly as reliable as

discrete silicon transistors, and secondly because changing it is too big a job to contemplate at this stage. There's a third reason, too."

"What's that?"

"We don't have a replacement in stock! Now let's recap. The distortion is appearing after the volume control and, for the moment, we'll say that there's no fault which is blatantly obvious around the i.c. So we'll do some quick checks around the transistor which precedes it. Testmeter ready again! Check the voltage between the transistor base and chassis."

Dick applied the testmeter prods to the printed board once more. (Fig.5(a).)

"There's about 1.2 volts here," he announced.

"That seems reasonable," said Smithy slowly. "Try the voltage between the collector and chassis next."

"Okeydoke."

Dick once more put the meter prods onto the board. (Fig.5(b).)

"I'm getting about 8.9 volts here," he said.

A beatific smile spread across Smithy's lips and he rubbed his hands together.

"Heh, heh," he cackled, taking on the eldritch tones of a witch. "Blood! I smell blood!"

And there was blood, indeed, to smell. The next checks showed that there was only 0.2 volt across the collector load resistor and that this resistor had its true and proper value of 5.6kΩ. Whereupon anyone armed with a pocket calculator and having a glimmering of Ohm's Law will at once tell you that the transistor

## THE MODERN BOOK CO.

Largest selection of English & American radio and technical books in the country.

19-21 PRAED STREET  
LONDON W2 1NP  
Tel: 01-402 9176

## Z TECHNICAL BOOKS

ELECTRONICS - AUDIO - CB RADIO - AMATEUR RADIO - COMPUTERS - PROJECTS.

Guide to CB Radio - Big-D Price £3.00 with Free Leather Bookmark ALSO CB RADIO ACCESSORIES.


Send 12p stamp (not sae) with your name and address for catalogue and prices.

In stock books despatched same day as order received.

### Z. L. COMMUNICATIONS

35, Burnt House Road, Cantley, Nr. Norwich Norfolk, NR13 3RT. Tel: Freethorpe 821.

## MORSE MADE EASY

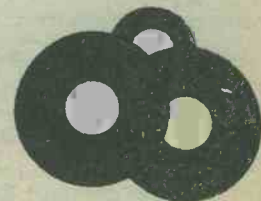

### BY THE G3HSC RHYTHM METHOD!

These courses which have been sold for over 25 years, have been proven many times to be the fastest method of learning Morse. You start right away by learning the sounds of the various letters, numbers, etc., as you will in fact use them. Not a series of dots and dashes which later you will have to translate into letters and words. Using scientifically prepared 3 speed records you automatically learn to recognise the code, RHYTHM without translating. You can't help it. It's as easy as learning a tune. 18 WPM in 4 weeks guaranteed.

The Complete Course consists of three records as well as instruction books. Complete Course £5.50 U.K. p/p 75p. (Overseas postage sufficient for 750gms). Details only s.a.e.

### THE G3HSC MORSE CENTRE

S. Bennett, (Box 8), 45 Green Lane, Purley, Surrey.

Name .....

Address .....

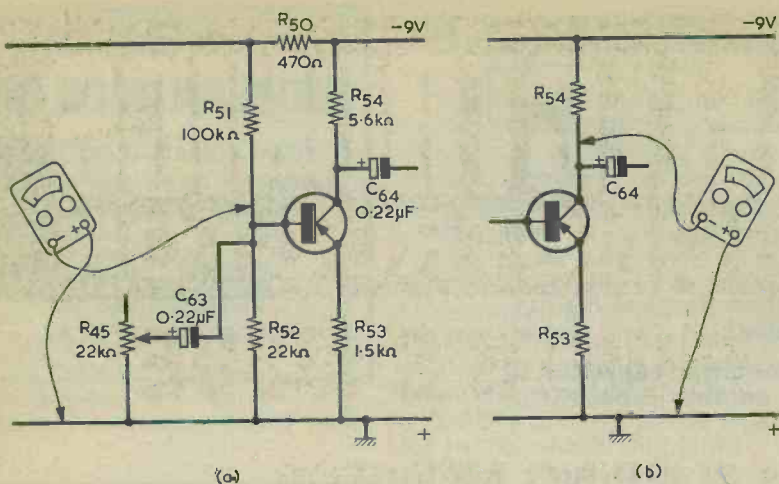


Fig.5(a). A further test consisted of measuring the voltage at the transistor base.

(b). This was followed by a check of the transistor collector voltage.

collector current was equal to 0.2 volt divided by 5.6kΩ or 0.035714mA to 5 significant figures or, if you want even greater accuracy, 35.7143μA to 6 significant figures. The only remaining resistor to check was the 1.5kΩ transistor emitter resistor, and the value of this had risen to some 10 times its nominal value. At the reduced

collector current available to the transistor, it simply had not been able to handle signals above a low level without introducing distortion.

Dick did not even have to remove the board to fit a new 1.5kΩ resistor. He merely had to snip the leads of the faulty resistor close to its body and then quickly solder the new

resistor to these leads. It could be argued that Smithy had devoted all his time to explaining the component functions around the audio amplifier i.e., whereas the fault in *this* particular radio was in a transistor stage that had nothing to do with the integrated circuit. But then who ever said that, in servicing, the fault has to lie in the stage you're devoting all your attention to?

#### LAST WORDS

"That's great," grinned Smithy happily as Dick switched off the radio, which now had a completely acceptable performance so far as distortion was concerned. He consulted his watch. "Blimey, there's still a couple of minutes to go before packing-up time."

"Good," said Dick quickly. "Then you can tell me what's white on the top, white on the bottom and blue in the middle."

"Trust you to spoil everything," sighed Smithy. "All right, what *is* white on the top, white on the bottom and blue in the middle."

"It's a frog sandwich," replied Dick triumphantly. "It's a frog sandwich which has been left too long in the freezer!"

## BOOK REVIEW

**ELECTRONIC MUSIC PROJECTS.** By R. A. Penfold. 110 pages, 180 x 105mm. (7 x 4in.) Published by Bernard Babani (Publishing) Ltd. Price £1.75.

Electronic music effects and sound generators are very popular and it is possible, in many cases, to produce impressive results with the aid of quite simple circuitry. In this book, R. A. Penfold gives details of some 24 music projects which can be readily assembled by the home constructor.

The first chapter covers guitar effects units, and describes two types of tone booster, a fuzz box, a waa-waa unit, an automatic waa-waa unit, and a sustain unit incorporating an opto-isolator. General effects are described in the second chapter, which deals with a tremolo generator, a reverberation unit, an automatic phasor, an audio modulator and an envelope shaper.


The third chapter is devoted to sound generator projects, and includes white and pink noise generators, a glissando tone generator with switched output filters, a vibrato oscillator and a stylus organ. In the fourth and last chapter we find details of an electronic guitar tuning fork, a guitar practice amplifier, a metronome with visible flash, automatic and voice operated faders, a simple sound mixer and a sound-to-light unit with which the apparent speed of a moving light display increases with the volume of the music being played.

This listing shows the wide range of projects dealt with. Each is presented in circuit form with a components list and accompanying text describing circuit operation and giving advice on constructional points. This is another good book from a well-known and prolific author.

# RADIO & ELECTRONICS CONSTRUCTOR

## IN NEXT MONTH'S ISSUE

### ADD-ON CLIPPING MONITOR

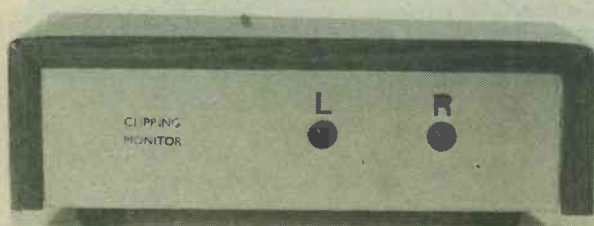

- Monitor circuit powered by amplifier output

- Imposes negligible loading
- Quick turn-on and slow decay

### OPTO-COUPLED VOLUME EXPANDER

- Increases dynamic programme range.
- Switched expansion selects 6dB, 10dB and 12dB.
- Adds realism to orchestral music.



### THE MAGIC HAND

Suggested Circuit

### NOVELTY M.W. RADIO FAULTS

In Your Workshop

## EXPERIMENTAL ELECTRONICS

Tips for the VENTURESOME

PLUS MANY OTHER ARTICLES

# BASIC MEDIUM RADIO

By T. F. Weatherley

## Simple single band loudspeaker radio.

This little radio was originally devised as a practical project in an electronics course to introduce modern components and constructional techniques. The two integrated circuits used have been available for some time but they do serve to illustrate the premise that quite sophisticated equipment can be built with very few discrete components.

The heart of the receiver is the popular ZN414. This integrated circuit contains, to quote the specification, "a ten transistor tuned radio frequency circuit using C.D.I. technology to provide a complete r.f. amplifier, detector and a.g.c. circuit on one chip". The chip is housed in the standard TO18 package and could be mistaken for a BC108. The a.f. amplification in the receiver is provided by an LM380.

### CIRCUIT OPERATION

As can be seen from Fig. 1 the circuit is quite straightforward. It can be thought of as comprising three sections: r.f. amplification and detection, a.f. amplification and a power supply. The last is a 9 volt battery.

The ferrite aerial coil, L1, and VC1 form the inductively tuned circuit, with C1 providing an earth return. R1 and R2 are the ZN414 bias and load resistors respectively. C2 is an r.f. filter capacitor. The ZN414 produces an a.f. output of some 30mV r.m.s. and this is coupled through C3 and R3 to the input of the LM380. A 10MΩ resistor, R5, controls the LM380 gain, and the output is coupled to the speaker through C4.


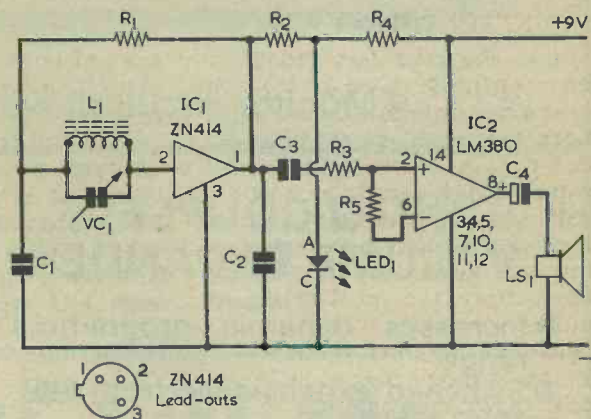



Fig. 1. The circuit of the medium wave radio. The use of two integrated circuits results in a low discrete component count.

The ZN414 requires only 1.5 volts and this is provided by R4 and LED1. The voltage dropped across the l.e.d. is held at a stable value of about 1.5 volts, and the l.e.d. also indicates that the receiver is turned on. The full 9 volts is applied to the LM380.

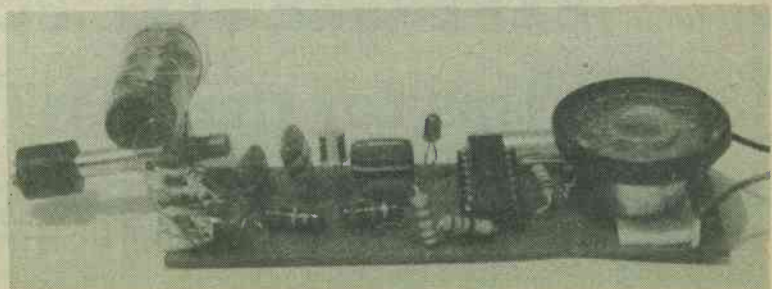A side view of the printed board assembly.



# WAVE

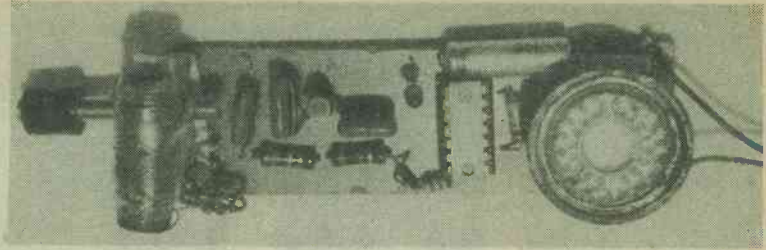

The completed receiver. The prototype employed a very small speaker, but any size speaker may be used.

*Inexpensive design requiring few components.*

## CONSTRUCTION

The radio is built on a printed circuit board measuring 90 by 32mm., or approximately 3½ by 1¼in. This board is shown full size in Fig. 2. After the board has been prepared, the components are fitted and soldered into place as shown. The resistors, and capacitor C4, can be mounted horizontally or vertically as space permits. IC2 can either be soldered to the board directly or mounted in an i.c. holder. In the original, Veropins were used for the connections to the battery, the speaker and to L1 and VC1. The author was lucky enough to obtain a 1in. 8Ω loudspeaker locally and this was positioned on the board as shown in the photographs. A larger 8Ω loudspeaker can, of course, be used and this will need to be mounted away from the board.


## FERRITE AERIAL

The ferrite aerial rod has a diameter of 3/8 in. and is only about 1in. long. This was found by experiment to be the shortest length which still enabled the project to be worth-while. The 1in. length was obtained from a longer rod by the usual method for breaking ferrite rod. First, a groove is filed all around the rod at the point where it is to be broken with a V-edge file, and the body of the rod is then gently tapped against the edge of a wooden bench or table.

The winding consists of 50 turns of 32 s.w.g. enamelled wire close-wound to form a coil about ½in. long at the centre of the rod. The wire gauge is not very critical and slightly thicker or thinner winding wire would also be suitable. It is helpful to fix some Sellotape, sticky side out, on the rod first, since this



Fig. 2. Component and copper sides of the printed board. This is reproduced full size.

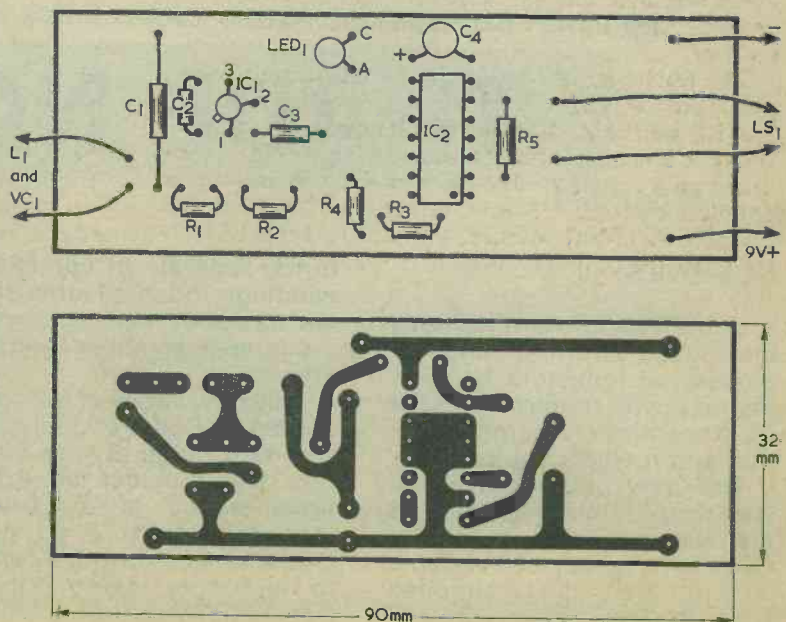

## COMPONENTS

### Resistors

(All  $\frac{1}{4}$  watt 5% unless otherwise stated)

- R1 100k $\Omega$
- R2 1k $\Omega$
- R3 1M $\Omega$
- R4 560 $\Omega$
- R5 10M $\Omega$  10%

### Capacitors

- C1 0.01 $\mu$ F polyester, type C280
- C2 0.1 $\mu$ F polyester, type C280
- C3 0.1 $\mu$ F polyester, type C280
- C4 100 $\mu$ F electrolytic, 10 V. Wkg.
- VC1 60-200pF trimmer (see text)

### Inductor

- L1 see text

### Semiconductors


- IC1 ZN414
- IC2 LM380
- LED1 red l.e.d.

### Speaker

- LS1 8 $\Omega$  speaker (see text)
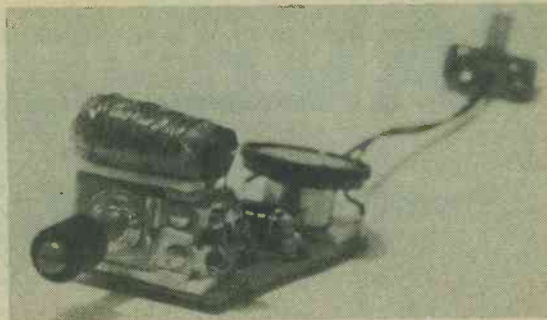
### Miscellaneous

- 9 volt battery
- Printed board materials
- I.C. holder, 14 way d.i.l. (if required)
- Control knob adaptor (see text)



Looking at the trimmer which functions as the tuning control. A home-made adaptor allows this to be adjusted by a control knob.

does not appear to have universal appeal and so a mechanical adaptor which allows a tuning knob to be employed was fabricated. The adjusting screw for the trimmer was 6BA, and this was removed. A length of rod having a diameter of  $\frac{1}{4}$ in. and a central hole capable of taking 6BA studding was located in the spares box. The head was cut from a  $\frac{1}{2}$ in. 6BA bolt, and one end of the threaded section affixed inside the rod. The rod assembly was then screwed into the trimmer in place of the original adjusting screw and an ordinary control knob fitted at the other end of the  $\frac{1}{4}$ in. rod. Similar means of making up an adaptor which allows the trimmer to be adjusted by means of a control knob should suggest themselves to the constructor.

The completed receiver has quite an impressive performance, despite its simplicity. The prototype can pull in a dozen or more stations at the author's home in East Anglia and the a.g.c. provided by the ZN414 makes listening a pleasure.

Current consumption from the 9 volt supply at normal volume levels is around 30mA, and so a fairly large battery is preferable if long listening periods are envisaged. ■

holds the turns in place. The whole winding is finally covered with more tape, and the enamel is scraped away from the two coil ends so that these may be soldered to the tags of VC1.

With the prototype VC1 is a mica compression trimmer having a value of about 60pF minimum and about 200pF maximum. It can be adjusted for station selection by means of a screwdriver. However, this

## TRADE NOTE

### NEW COILS

Codar Telecom Limited have introduced a further range of air spaced inductors to meet higher power requirements for r.f. transmission, communication and medical equipment.

The new coils are wound with copper ribbon or tube and are also available in "Roller Coaster" types of variable inductor. Coils can be supplied with variable pitch spaced



turns, separate or continuous windings, indented turns, taps, and as basic units for complete mounted assemblies ready for fitting.

This new series of inductors augments Codar's widely used standard range of wire inductors and provides an exceptional range of air spaced inductors from  $\frac{3}{4}$  to 15in. diameter, and having 22 s.w.g. to 1in. copper tube conductors. Applications include r.f. oscil-

lators, interstage coupling, pi-net and conventional L-C output.

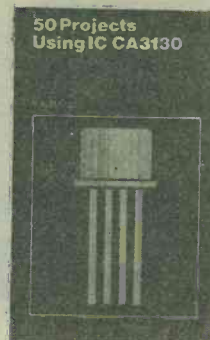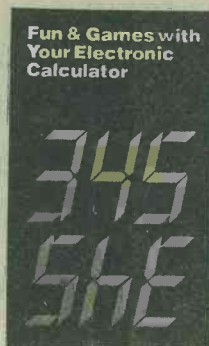In view of the very wide range of applications and differing requirements, coils are made to specification. The service features close co-operation with designers in the early development of new equipment. Further details can be obtained from Codar Telecom Limited, P.O. Box 3, Rottingdean, Brighton, BN2 8AZ.





# DIRECT READER SERVICE RADIO & ELECTRONICS BOOKS

18. 50 Projects Using IC CA3130	£1.25	40. Projects in Opto-Electronics	£1.25
19. 50 CMOS IC Projects	£1.25	41. Radio Circuits Using IC's	£1.35
20. A Practical Introduction to Digital IC's	95p	42. Mobile Discotheque Handbook	£1.35
22. Beginners Guide to Building Electronic Projects	£1.25	43. Electronic Projects for Beginners	£1.35
23. Essential Theory for the Electronics Hobbyist	£1.25	44. Popular Electronic Projects	£1.45
26. 52 Projects Using IC741	95p	45. IC LM3900 Projects	£1.35
28. Two Transistor Electronic Projects	85p	46. Electronic Music and Creative Tape Recording	£1.25
29. How to Build Your Own Metal and Treasure Locators	£1.00	47. Practical Electronic Calculations and Formulae	£2.25
30. Electronic Calculator Users Handbook	95p	48. Radio Stations Guide	£1.45
31. Practical Repair and Renovation of Colour TVs	£1.25	49. Electronic Security Devices	£1.45
32. Handbook of IC Audio Pre-amplifier and Power Amplifier Construction	£1.25	50. How to Build Your Own Solid State Oscilloscope	£1.50
33. 50 Circuits Using Germanium, Silicon and Zener Diodes	75p	51. 50 Circuits Using 7400 Series IC's	£1.45
34. 50 Projects Using Relays, SCR's and TRIACS	£1.25	52. Second Book of CMOS IC Projects	£1.50
35. Fun and Games with your Electronic Calculator	75p	53. Practical Construction of Pre-Amps, Tone Controls, Fitters & Attenuators	£1.45
36. 50 (FET) Field Effect Transistor Projects	£1.25	54. Beginners Guide to Digital Techniques	95p
37. 50 Simple L.E.D. Circuits	75p	55. 28 Tested Transistor Projects	£1.25
38. How to Make Walkie-Talkies	£1.25	56. Digital IC Equivalents and Pin Connections	£2.50
39. IC 555 Projects	£1.75	57. Linear IC Equivalents and Pin Connections	£2.75

POSTAGE: 20p PER BOOK. IF MORE THAN 3 BOOKS ORDERED: 10p PER BOOK

To: Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please send me within 21 days . . . . . copy/copies

Book Nos: . . . . .

I enclose Postal Order/Cheque for £ . . . . .

Name . . . . .

Address . . . . .

(Block Letters Please)

(We regret this offer is only available to readers in the U.K.)

# 'NOTES FOR NEWCOMERS'

## SATISFACTORY SOLDERING

By D. Snaith

### *8 tips to start you soldering successfully.*

Quite a few newcomers to the home-constructor hobby run into difficulties when they attempt to make their first soldered joints. The ability to solder is essential if the hobby is to be truly rewarding and, if you have never soldered before, you *do* need a little practice to get the "feel" of things. About half an hour's experience in soldering together odd wires and tags should be more than adequate, and after this you should be able to tell with some reasonable certainty whether or not you have completed a good joint as soon as the solder has set solid.

#### SOLDERING FACTS

Fig. 1(a) shows a tinned copper wire which is to be soldered to a tag. Although both the wire and the tag may look clean, they will in fact almost certainly be covered with a thin oxide coating. The molten solder has to get past that oxide coating if it is to make a proper joint with the pure metal underneath, and for this reason we apply not only solder to the joint but also *flux*. The flux is a chemical which, when heated, breaks down the oxides. We use cored solders for electronic work, and these consist of solder wires with, typically, five cores containing a suitable flux. So, when we apply the solder we automatically apply the flux as well.

In Fig. 1(b) we apply the soldering iron tip to the work (i.e. the items to be soldered together) so that, preferably, the tip is in contact with both pieces. At the same time we apply the solder to the iron tip and the work. What happens first is that the solder melts at the iron tip and the heated flux at once gets to work on the oxides in the immediate vicinity, allowing the molten solder to "wet" the work pieces. Heat from the iron tip travels quickly through the molten solder to the work pieces, with which the solder is now in

intimate contact. The rate of heat flow is faster than would be given by just placing the iron tip on its own on the work. We apply a little more solder, which now flows over the work pieces and then we remove the solder and the soldering iron. If the solder *flows* over the work pieces we have made a good joint. The completed joint should be smoothly covered with just enough solder to do the job. There will almost certainly have been a little more flux than was needed, and what is left sets hard on the outside of the solder.

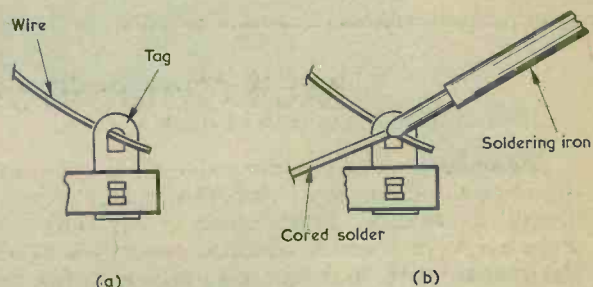


Fig. 1(a). The wire shown here is to be soldered to the tag (b). The tip of the hot soldering iron and the solder are both applied at the same time to the work pieces. The molten solder first speeds the transfer of heat from the iron to the work pieces, and then flows over the pieces to produce the joint.

## SOLDERING SNAGS

Now, here are the things which can go wrong and produce an unreliable solder joint.

1. The soldering iron is applied for too short a time. The solder may run over the work and even cover it but, because the work pieces were not raised to a sufficiently high temperature, has not made a proper joint with them. The result is a rough solder outline, and the joint looks as though you've been trying to solder with sealing wax.

2. The soldering iron has been applied for too long. This may not result in a poor joint but it can cause overheating of components whose lead-out wires form part of the joint. One of the main reasons for initial soldering practice is to find how to arrive at a happy medium between this snag and snag No. 1.

3. There is too little solder in the joint. This will be visually obvious. There should be enough solder to give a sound mechanical joint.

4. Too much solder in the joint. Another conflicting snag, and again visually obvious. A joint with too much solder may in fact be sound, but big blobs of solder look unsightly. What's more, they take too long to cool down after the iron has been removed, with possible overheating of components in consequence. Also, there is a greater risk of snag No. 5 occurring.

5. The work pieces are moved just before or at the instant when the solder sets. Solder does not go direct from the liquid to the solid state as it cools, but passes through a "pasty" condition. If the work pieces are moved when the solder is pasty a poor joint results.

6. The work pieces are too oxidised or dirty. All semiconductor device leads, and those of nearly all modern resistors and capacitors should solder straightaway when using cored solder. But the flux may not be able to break down high levels of oxide. Before attempting a joint with wire which looks dirty or highly oxidised, scrape off the dirt or oxide with a sharp knife and then tin the lead with cored solder. After this it will solder directly.

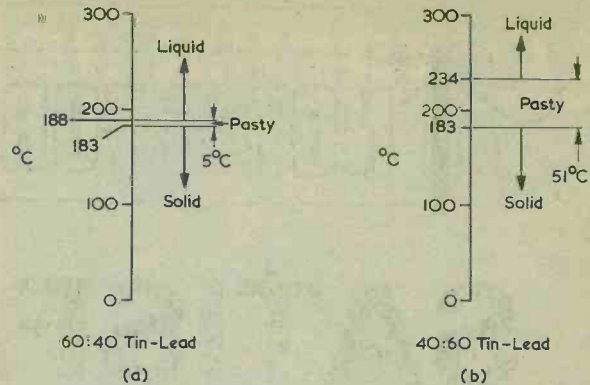


Fig. 2(a). A solder alloy consisting of 60% tin and 40% lead exhibits a very low temperature range in which it is in the pasty state. (b). A 40:60 tin-lead alloy goes from solid to pasty at the same temperature as does 60:40 solder, but the pasty range extends to a very much higher temperature before the solder becomes liquid.

7. Dirty soldering iron bit. Always keep the iron tip nice and shiny with molten solder. This allows heat to travel quickly to the work pieces.

8. Wrong solder. Avoid "electrical grade" or 40:60 solder like a plague. Always use a 60-40 tin-lead alloy or Multicore "Savbit" (which has a little copper added). Fig. 2(a) shows the temperatures at which 60:40 alloy is solid, pasty and liquid, whilst Fig. 2(b) shows the temperatures for the same states in 40:60 alloy. The 60:40 solder is pasty from 183deg. C to 188deg. C, a range of 5deg. C only which in practice is just right. The 40:60 alloy is pasty from 183deg. C to 234deg. C, a range of no less than 51deg. C. The 40:60 solder is hopeless for the small closely spaced solder joints which are encountered in modern electronics. ■

## Mail Order Protection Scheme

The publishers of this magazine have given to the Director General of Fair Trading an undertaking to refund money sent by readers in response to mail order advertisements placed in this magazine by mail order traders who fail to supply goods or refund money and who have become the subject of liquidation or bankruptcy proceedings. These refunds are made voluntarily and are subject to proof that payment was made to the advertiser for goods ordered through an advertisement in this magazine. The arrangement does not apply to any failure to supply goods advertised in a catalogue or direct mail solicitation.

If a mail order trader fails, readers are advised to lodge a claim with the Advertisement Manager of this magazine within 3 months of the appearance of the advertisement.


For the purpose of this scheme mail order advertising is defined as:

"Direct response advertisements, display or postal bargains where cash has to be sent in advance of goods being delivered."

Classified and catalogue mail order advertising are excluded.

# ELECTROVALUE

SUPPLIERS OF COMPONENTS THAT COUNT

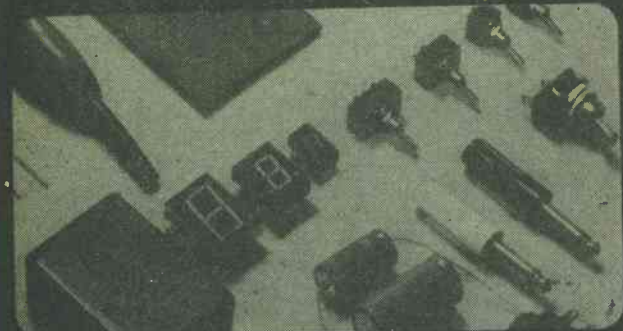

<b>SIEMENS</b> SEMI-CONDUCTOR CAPACITORS FERRITES	<b>NASCOM</b> MICRO COMPUTERS AND ANCILLARIES	<b>VERO</b> BOARDS CASES & KITS
<b>ISKRA</b> RESISTORS	RADIOHM POTENTIOMETERS	BREADBOARDS
	OPTO-ELECTRONICS	SOLDER TOOLS
	SWITCHES	CATALOGUE 10

## OUR MINI-SELECTION POINTS THE WAY!

**EXAMPLE ONE - SOLDERING IRONS**

Aryx 50	£12.08 net	Antex x 25	£4.83 net
Isotip	£25.90 net	Desolder tool SR3A	£7.48 net
Antex C	£4.83 net	500 gm reel solder	£6.61 net

**EXAMPLE TWO - PRINTED CIRCUIT MATERIALS**

PCB's 300 x 150 mm	Etch Resist Pen	£1.14
SRBP S/S £1.38	Breadboards	
F/Glass S/S £1.96	Bimboard	£9.23
Positive resist 75cc	Eurobreadboard	£6.56 net
Ferric Chloride 500 g	T-DeC	£5.18

**EXAMPLE THREE - SWITCHES**

Chrome toggle	13A time switch adaptors	
Std. SPDT 65p	Smiths TS100	£14.43 net
Min. SPDT 66p	Wavechange, Lorlin, 1P12W, 2P6W, 3P4W, 4P3W	46p each

**EXAMPLE FOUR - CAPACITORS BY SIEMENS**

Polyester 7.5mm PCM  
1, 1.5, 2.2, 3.3, 4.7µF, 10, 15, 22, 33, 42µF 8p each, 1µ 12p, .15µ 15p, .22µ 18p, .33µ 21p, .47µ 27p, .68µ 34p, 10mm PCM 1µ 37p.

Electrolytic, axial, (µF/V)  
1/40 24p, 1/100 15p, 2.2/25 24p, 2.2/63 15p, 4.7/16 24p, 4.7/40 15p, 10/25 15p, 10/40 18p, 22/25 18p, 22/40 18p, 22/63 19p, 47/10 18p, 47/25 18p, 47/40 16p, 47/63 20p, up to 1000/16V 36p, then 1000/25V 49p to 47/16 65p.

Also full supporting ranges of other ceramic, plastic and electrolytic caps.

**EXAMPLE FIVE - POTENTIOMETERS BY RADIOHM**

Single gang lin or log	34p	(Twin types stereo matched)
Twin gang lin or log	93p	Slider knobs
Mono slider lin or log	83p	Presets lin, horiz, or vert at
Twin slider lin or log	136p	10p each

**EXAMPLE SIX - RESISTORS**

1/2, 1/4, 1/8W 2.3p 1W 6p  
Wirewound from 21p

**AND AS FOR SEMI CONDUCTORS**

1N914	6p	40673	99p	MU481	£1.70	T1P41A	69p
1N4007	9p	AC128	36p	MJ491	£1.88	T1P41C	74p
1N4148	5p	AC176	67p	MJ2955	97p	T1P42A	69p
1N5402	19p	AD136	£4.25	MJE2955	£1.13	T1P42C	74p
2N1599	£1.01	AD149	£1.01	MJE3055	£1.00	T1P2955	69p
2N2369A	24p	AD161	40p	MPSA12	42p	T1P3055	69p
2N3055	81p	AD162	52p	MPSA63	44p	T1S43	40p
2N3702-11	11p	AF127	43p	OA47	14p	W02	35p
2N4443	£1.78	AL102	£1.84	OA90	8p	2T x 107.9	14p
2N4444	£2.28	BA379	29p	OA91	8p	2T x 300	14p
2N4991	98p	BB103	43p	OA202	16p	62T x 500	16p
2N5457-9	45p	BB104	70p	OC29	£1.23		
40HF40	£2.25	BB105	37p	OC36	£1.18	This list is	
40361	49p	C106D1	52p	T290D	£1.20	but a fraction	
40362	49p	E1110	92p	T1P31A	52p	of what we	
40636	£1.69	E1210	97p	T1P32A	52p	carry.	

**INFORMATION** - To show everything we supply would take about seven pages of closely packed type in this journal - the range is enormous including not only opto devices and very advanced sophisticated items, but all the everyday things you need as well down to nuts and washers! IT'S ALL IN CATALOGUE 10 - OUR 120 PAGE CATALOGUE FREE FOR THE ASKING. PRICES AND V.A.T. - All prices quoted here include V.A.T. for U.K. orders. Overseas buyers deduct 13% when ordering.

**POSTAGE** - For orders up to £5.57 value (U.K.) please add 40p for p/p. If over, orders sent post free in U.K. Overseas orders sent at cost (Min. 40p).

**DISCOUNTS** - 5% allowed on non-net items if order value exceeds £11.50, 10% if order value exceeds £29. Quantity discount prices on most components.

**ELECTROVALUE LTD.** Dept. 28(A), St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB. Phone Egham 33603 Telex 264475.  
Northern Branch (Personal Shoppers only) 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone (061) 432 4945.

# Self-Binder

for "Radio & Electronics Constructor"

The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Rich maroon finish, gold lettering on spine. Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.



**PRICE £2.25** P. & P. 50p  
including V.A.T.

**For your other magazines**  
Plain-backed in Maroon or Green  
(Please state colour choice)

**PRICE £2.25** P. & P. 50p  
including VAT

Available only from:-

**Data Publications Ltd.**  
57 Maida Vale London W9 1SN

RADIO AND ELECTRONICS CONSTRUCTOR

## SMALL ADVERTISEMENTS

Rate: 12p per word. Minimum charge  
£2.00

Box No. 30p extra

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the **bona fides** of Advertisers. Where advertisements offer any equipment of a transmitting nature, readers are reminded that a licence is normally required. Replies to Box Numbers should be addressed to: Box No. —, **Radio and Electronics Constructor**, 57 Maida Vale, London, W9 1SN.

**MODULES.** Mullard LP1164 AM/FM i.f. Unused and guaranteed £1.50. P.P. C.W.O. BA screws, hardware, components, Manufacturers' clearance. S.A.E. lists. Tennex Ltd., Stock Road, Southend-on-Sea, Essex.

**25 MIXED I.C.'S** £1.50. 100 mixed transistors £3.50. Valves. Early radios. Electronic bargains. Interesting lists 15p. Sole Electronics, REC, 37 Stanley Street, Ormskirk, Lancs, L39 2DH.

**BIGGEST RANGE SERVICE SHEETS/MANUALS.** Any published sheet £1. plus s.a.e. Repair data any named TV £5.50 (with circuit set £7). S.A.E. newsletter, quotations, bargains. G.T., 76 Church Street, Larkhall, Lanarkshire.

**BOOKS FOR SALE:** *Experiments with Operational Amplifiers*, by George B. Clayton. £3.75. *Digital I.C. Equivalents & Pin Connections*, by Adrian Michaels, £1.20. *Experimenting with Electronic Music* by Brown & Olsen. £1.20. *Electric Model Car Racing* by Laidlaw-Dickson. 60p. *Understanding & Using Modern Signal Generators* by Charles Gilmore. £1.20. *Electronics Unravelled* by Kyle, £1. *How to Use your VOM VTVM Oscilloscope*, by Clifford, £1. *Modern Radio Repair Techniques*, by Art Margolis, £1. Box No. 394.

**USE OPTICAL FIBRES TO CARRY LIGHT.** Tough, wire-like strands that are excellent for communications, lighting, electrical isolation, etc. Introductory pack totals sixteen feet of four assorted types, plus twenty page illustrated guide. Send £3.55 inclusive to Quantum Jump Ltd., 53 Marlborough Road, Tuebrook, Liverpool L13 8EA.

**THE RADIO AMATEUR INVALID & BLIND CLUB** is a well established Society providing facilities for the physically handicapped to enjoy the hobby of Amateur Radio. Please become a supporter of this worthy cause. Details from the Hon. Secretary, Mrs. F. E. Woolley, 9 Rannoch Court, Adelaide Road, Surbiton, Surrey, KT6 4TE.

(Continued on page 189)

## ELECTRONICS

A NEW AND EXCITING HOBBY!!

BIG, WELL ILLUSTRATED BOOK

Ideal for beginners — gives lots of general information — explains how to build lots of projects:

Intercom, Rain Alarm, Radios, Organ, Parking Light etc. All parts supplied and can be re-used on special deck provided, so **NO SOLDERING** is required. Just needs 4½V battery.



£17.50 inc. VAT & Post

Also

**ADVENTURES WITH MICROELECTRONICS**


— Explore the world of silicon chips —

All components & Deck, £27.95 inc VAT & Post.

Component Catalogue & Bargain List 75p

### GREENWELD

443G Millbrook Road, Southampton SO1 0HX

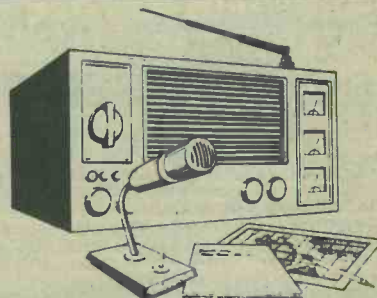

## BECOME A RADIO AMATEUR

Learn how to become a radio amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

No previous knowledge required.

Brochure without obligation to —

**British National Radio & Electronic School**

4 Cleveland Road, Jersey, Channel Islands.

Name .....

Address .....

.....

.....

REC/11/815 BLOCK CAPS PLEASE

# SWITCHVANCE LTD.

49 Wadson Street, London E2 9DP.  
Tel: 01-980 1028/1029

All items brand new and fully guaranteed. Prices inclusive of VAT. Minimum order value £5. Terms: Cash/Cheque/P.O. with order. Please add 40p P&P to all orders except where otherwise marked.

## ELECTROLYTIC CAPACITORS - Wire ended.

Mfd/Volt	Mfd/Volt	Mfd/Volt	Mfd/Volt	Mfd/Volt	Mfd/Volt
0.47/50	4p	10/350	10p	47/50	7p
4.7/50	5p	15/40	6p	68/40	7p
6.8/63	5p	22/16	5p	100/16	7p
10/16	5p	22/63	6p	100/25	7p
10/25	5p	47/16	5p	100/50	9p
10/50	6p	47/25	6p	220/25	8p
				470/16	9p
				470/25	12p
				1000/10	12p
				1000/16	16p
				1000/40	20p
				2200/40	40p
				4700/25	52p
				6800/16	30p

**CANS:** 1500/63 — 35p. 3300/40 — 52p. 4700/40 — 60p. 6800/40 — 80p.

**POLYESTER CAPACITORS - Radial leads.**  
63V: .15, .22, .33, .47, .68 8p. 1.0 12p. 1.5 18p. 250V: .01, .022, .033, .047, .068 5p.  
.1, .22, .47 7p. 1.0 18p. 1.5 23p.

**POTENTIOMETERS.** Rotary. Carbon track. 0.25W log. 0.5W 1in.

Spindle  $\frac{1}{4}$  x  $1\frac{1}{8}$  in.  
Single gang: 1K log, 5K log, 250K log, 1M log. 25p. Single gang D/P switch: 2K5 1in, 5K 1in, 5K log, 10K log, 25K log, 50K 1in, 50K log, 100K 1in, 100K log, 250K 1in, 500K 1in, 500K log. 46p. Dual gang: 1K 1in, 5K 1in, 5K log, 10K 1in, 10K log, 25K 1in, 25K log, 50K log, 100K 1in, 100K log, 250K 1in, 250K log, 500K 1in, 1M log. 60p.

Wirewound 1W (1in). Spindle size  $\frac{1}{4}$  x 2in. 10R, 30R, 220R, 500R, 1K, 3K3, 5K, 50p. Wirewound 3W (1in). Spindle  $\frac{1}{4}$  x 1 or  $1\frac{1}{8}$ in. 10K, 50K. 95p. Presets. 0.1W and 0.15W Vertical or horizontal mtg. 100R — 1M. 6p.

**SWITCHES:** Rotary. 1 pole 12 way, 3 pole 4 way, 4 pole 3 way. 45p. Mains Rockerswitch with built-in neon. DFST. 10A contacts. 80p. 3 gang DP latching pushswitch with knobs. 40p. DIL switches: standard DIL package incorporating 1 — 10 single pole switches. 1 way 35p. 3 way 46p. 5 way 65p. 6 way 70p. 7 way 70p. 8 way 82p. 9 way 82p. 10 way 95p. Also 1 way DP 35p. 2 way DP 46p. 5 way DP 80p. Standard toggleswitch 3A 250V Single pole. Plastic dolly. 32p. Microswitches: All SPDT. Standard V3 size button operated 28p. Subminiature button operated 32p. Subminiature lever operated 35p.

**KNOBBS:** Black pointer type with metal inlay, screw fix. 25mm dia. 20p. Plain brushed aluminium type on black base. Push on for D spindle. 30mm. 14p. Slider control knob. Black with metal inlay. 14p. Button knob for pushbutton switches. Black body metal cap. 14p.

**ANTISURGE FUSES:** 20mm. 160mA 15p. 500mA, 4A, 10A. 12p. 32MM. 200mA, 500mA, 800mA, 1.5A, 2A, 2.5A. 14p.

ALL PRICES ARE INCLUSIVE OF VAT. WE ARE A MAILORDER COMPANY — CALLERS BY APPOINTMENT ONLY PLEASE

**HIGH CAPACITANCE ELECTROLYTICS.** Ideal for P.S.U.'s, Smoothing etc. Voltages 10-25v.d.c. Values 1000-4700uf. Pack of 10 assorted for £2.25. Pack of 25 for £4.25. Sorry no special selections.

**CABLES:** Single stranded connecting wire. Various colours. 4p metre. Figure 8 twin flex 0.5mm for speaker leads, etc. White only. 7p metre. 3 core mains flex 0.5mm (3A) in white. 15p metre. 4 core flex 7/02mm (1.5A) for telephones, alarms, etc. White. 15p metre. 8 core flex 7/02mm (1.5A) overall dia. 10mm. Grey. 30p metre. 10 way ribbon cable. U.S. equiv 7/02mm. Colour coded. 30p metre. U.H.F. Low loss co-axial cable 75 ohm. White only. 20p metre.

**Liquid Crystal Displays.** Field effect, low power requirement. 12.7mm high digits. 7 segment format plus decimal points and colon. 40 pin DIL package. 4-17V operating. Available 3 digit (inc. polarity and overrange) or 4 digit. £7.50. Miniature enclosed relays. 24V 1250 ohm D.P. changeover solder tags. £1.70. 24V (operating range 11-37V) 700 ohm 4 pole changeover. P.C. mounting £1.95. Standard car radio suppressors 1 uf. 150V. Fit on condenser. 30p. Cassette motors 12V. d.c. with variable speed control and pulley. £1.25. Speaker cabinets. Teak effect finish with black front. Dims. 15 x 9  $\frac{1}{2}$  x 6  $\frac{1}{2}$  in. Fitted with 8 x 5 in. 8 ohm speaker. Complete with lead and plug. £16.95 pair. P&P £2.50 pair. Chassis loudspeakers 8in. 8 ohm 15W. Dual-cone Mag. weight 15oz approx. £6.75. 6 x 4 in. 4 or 15 ohm 6W. Mag weight 6oz. approx. £2.60.

## SEMICONDUCTORS:

IN 4001	5p	BC 108C	12p	BF 594	26p
BZY88 4.3	7p	BC 148	7p	BSX 20	20p
BZY88 4.7	7p	BC 177A	15p	BSY 95A	17p
BZY88 6.8	7p	BC 178	14p	BZX61C15	10p
BZY88 12	7p	BC 178A	14p	BZY91C75	11p
BA316 10V	5p	BC 182	11p	TIS 90	18p
BAX 13	7p	BC 183L	11p	2N 2484	21p
BC 107	10p	BC 239C	11p	2N 3707	10p
BC 107A	10p	BC 549	11p	2N 3704	10p
BC 107B	12p	BCY 70	14p	741 (8 pin)	18p
BC 107C	12p	BCY 71	14p	74154	17p
BC 108	10p	BF 180	30p	SN 76023N	175p
BC 108A	10p	BF 195	11p	MC 3401P	46p
BC 108B	12p	BF 451	22p	S01 (2A 100V)	40p

## CONNECTORS:

Professional quality stereo jackplugs  $\frac{1}{2}$ in. Metal body and cable grip. 42p. Stereo jack sockets. Open type 3 contact 20p. Headphone type 8 tag 35p. Chassis DIN sockets. 2 pin 8p. 5 pin 13p. Cannon locking 3 pin DIN plug 65p. Belling Lee 3 pole mains connector 10A 250V. Cable plug and chassis socket 65p pair. Television coax plugs all aluminium body. 17p. BNC free socket 50 ohm 60p. U.H.F. Elbow plugs 150p. U.H.F. 'T' adaptor (2 sockets to 1 plug) 175p. 12 way polythene terminal blocks. 5A 380V. Easily subdivided. 24p.

**MINIATURE BULBS:** M.E.S. 6.5V. 0.3A round and 0.15A tubular. 10p.

L.E.S. 6.5V 1W. and 14V 0.75W 10p.

**PANEL NEON INDICATOR.** Amber lens, chromed body 10mm dia. 250V. 35p.

## THE MODERN BOOK CO

### RADIO & TV SERVICING 1979-1980 Models by R. N. Wainwright £15.50

#### ELECTRONIC FAULT DIAGNOSIS

By I. R. Sinclair Price £3.50

#### ELECTRONIC PROJECTS IN AUDIO

by R. A. Penfold Price £2.50

#### OP-AMPS THEIR PRINCIPLES & APPL.

by J. B. Dance Price £2.50

#### PRINTED CIRCUIT ASSEMBLY

by M. J. Hughes Price £2.10

#### ELECTRONIC SECURITY DEVICES

by R. A. Penfold Price £1.65

#### UNDERSTANDING DIGITAL

ELECTRONICS

by Texas Inst. Price £4.00

#### UNDERSTANDING MICRO-

PROCESSORS

by Motorola Price £4.30

#### THE FIRST BK OF MICROCOMPUTERS

by R. Moody Price £3.35

#### HOW TO BUILD YOUR OWN SOLID

STATE OSCILLOSCOPE

by F. G. Rayer Price £1.70

#### THE OSCILLOSCOPE IN USE

by I. R. Sinclair Price £3.50

#### AUDIO AMPLIFIERS FOR THE HOME

CONSTRUCTOR

by I. R. Sinclair Price £3.50

#### REPAIRING POCKET TRANSISTOR

RADIOS

by I. R. Sinclair Price £2.55

#### MAKING & REPAIRING TRANSISTOR

RADIOS

by W. Oliver Price £2.30

#### WORLD RADIO TV HANDBOOK

by J. M. Frost Price £9.25

#### PROJECTS IN RADIO & ELECTRONICS

by I. R. Sinclair Price £2.50

#### ELECTRONIC PROJECTS IN THE HOME

by O. Bishop Price £2.50

#### SIMPLE CIRCUIT BUILDING

by P. C. Graham Price £2.20

#### 110 SEMICONDUCTOR PROJECTS FOR

THE HOME CONSTRUCTOR

by R. M. Marston Price £3.20

#### HAM RADIO

by K. Ulyett Price £5.00

#### UNDERSTANDING ELECTRONIC

CIRCUITS

by I. R. Sinclair Price £4.50

#### UNDERSTANDING ELECTRONIC

COMPONENTS

by I. R. Sinclair Price £4.50

#### UNDERSTANDING SOLID-STATE

ELECTRONICS

by Texas Inst. Price £3.95

#### A SIMPLE GUIDE TO HOME

COMPUTERS

by S. Ditlea Price £4.00

#### HOW TO BUILD A COMPUTER-

CONTROLLED ROBOT

by T. Loofbourrow Price £5.30

#### THE CATHODE-RAY OSCILLOSCOPE &

ITS USE

by G. N. Patchett Price £4.00

#### A GUIDE TO AMATEUR RADIO

by P. Hawker Price £1.70

#### MAKING TRANSISTOR RADIOS A

BEGINNER'S GUIDE

by R. H. Warring Price £2.90

We have the Finest Selection of English and American Radio Books in the Country  
PRICES INCLUDE POSTAGE

19-21 PRAED STREET (Dept RC) LONDON W2 1NP

Telephone: 01-402 9176

## SMALL ADVERTISEMENTS

(Continued from page 187)

**FOR SALE:** Wide angle 9.5mm cine equipment: camera, projector, screen, etc. Also several other 9.5mm cine cameras. S.A.E. for details Box No. G388.

**WANTED:** Service Manual, circuit diagram of Telequipment Serviscope Type S51A. To buy or borrow copy. Expenses refunded plus small remuneration. 35 Stanhope Road, Swanscombe, Kent, DA10 0AN.

**THE BRITISH AMATEUR ELECTRONICS CLUB** for all interested in electronics. Four Newsletters a year. Library of technical books and magazines. Help for members by experts. U.K. & Eire £4.50. Europe £6. Airmail £7.50:- Sterling per year. Details from Hon. Sec., J. G. Margetts, 3 Bishopstone Close, Golden Valley, Cheltenham, Glos.

**FOR SALE:** Non-working CCTV cameras £25.00. each. J. Fulton, Derrynaseer, Dromore, Co. Tyrone, N. Ireland.

**HEATHKIT DIGITAL DISPLAY** shelf clock with Westminster chimes. Used one month only. £80. (Cost £160). Telephone:- Southend (0702) 711181.

**FOR SALE:** A number of "D & S" three pin, fused, mains plugs and fuses. S.A.E. for details. Box No. G396.

**JOIN THE INTERNATIONAL S.W. LEAGUE.** Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. - both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazines, etc., £6.00 per annum. (U.K. and British Commonwealth), overseas \$12.00. Secretary ISWL, 1 Grove Road, Lydney, Glos., GL15 5JE.

**WANTED:** FAX equipment, manuals, service sheets, etc. G2UK, 21 Romany Road, Oulton Broad, Lowestoft, Suffolk. NR32 3PJ.

**BOOKS FOR SALE:** *Amateur Radio Antennas* by Harry Hooton, £1. *Ham Antenna Construction Projects* by J. A. Stanley, 75p. *All about Cubical Quad Antennas* by W6SAI, £1. *Radio Astronomy for the Amateur* by Dave Heiserman, £2. *HAM-RTTY* by W2NSD, 50p. *Radio Control for Model Yachts* by C. R. Jeffries, £1.00. All plus postage. Box No. G397.

(Continued on page 190)



# Wilmslow Audio

*THE firm for speakers!*

**SEND 50p FOR THE WORLDS BEST CATALOGUE OF SPEAKERS, DRIVE UNITS KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST**

AUDAX ● AUDIOMASTER ● BAKER ● BOWERS &  
WILKINS ● CASTLE ● CELESTION ● CHARTWELL ● COLES ● DALESFORD ● DECCA ● EAGLE ● ELAC ● EMI ● FANE ● GAUSS ● GOODMAN'S ● HARBETH ● ISOPHON ● I.M.F. ● JORDAN ● JORDAN WATTS ● KEF ● LOWTHER ● MCKENZIE ● MISSION ● MONITOR AUDIO ● MOTOROLA ● PEERLESS ● RADFORD ● RAM ● ROGERS ● RICHARD ALLAN ● SEAS ● SHACKMAN ● STAG ● TANNOY ● VIDEOTONE ● WHARFEDALE ●

**WILMSLOW AUDIO** DEPT REC  
SWAN WORKS, BANK SQUARE, WILMSLOW  
CHESHIRE SK9 1HF

Tel: 0625-529599 for Mail Order & Export of Drive Units, Kits, etc.,  
Tel: 0625-526213 (Swift of Wilmslow) for Hi-fi and complete speakers

## A CAREER IN RADIO

Start training *today* and make sure you are qualified to take advantage of the many opportunities open to the trained person. ICS can further your technical knowledge and provide the specialist training so essential to success.

ICS, the world's most experienced home study college, has helped thousands of ambitious men to move up into higher paid jobs - they can do the same for you.

Fill in the coupon below and find out how!

There is a wide range of courses to choose from, including:

### CITY & GUILDS CERTIFICATES

Telecommunications Technicians'  
Radio TV Electronics Technicians'  
Electrical Installations Technicians'  
Electrical Installation Work  
Radio Amateurs'  
MPT Radio Communications Cert

**EXAMINATION STUDENTS -  
GUARANTEED COACHING  
UNTIL SUCCESSFUL**

### TECHNICAL TRAINING

ICS offer a wide choice of non-exam courses designed to equip you for a better job in your particular branch of electronics, including:  
Electronic Engineering & Maintenance  
Computer Engineering/Programming  
Radio, TV & Audio Engineering  
& Servicing  
Electrical Engineering Installations  
& Contracting

### COLOUR TV SERVICING

Technicians trained in TV Servicing are in constant demand. Learn all the techniques you need to service Colour and Mono TV sets through new home study course approved by leading manufacturer.

**POST THIS COUPON OR TELEPHONE FOR FREE PROSPECTUS**

I am interested in .....  
Name ..... Age .....  
Address .....  
Occupation .....

**ICS**

Accredited  
by CACC  
Member of  
ABCC

To  
International Correspondence Schools  
Dept 278A, Intertext House, LONDON  
SW8 4UJ or phone 01-622 9511 (anytime)

## MARCO TRADING

To obtain a free copy of our 35 page list simply send a 20p postage stamp or a large SAE. This advertisement shows only a part of our range. (Our new list includes Tants, Electrolytics, Disc ceramics, etc.)

### 400m/w ZENER DIODES

**Low Price**  
3V6, 3V9, 4V3, 4V7, 5V1, 5V6, 6V2, 6V8, 7V5, 8V2, 9V1, 10V, 11V, 12V, 13V, 13V5, 15V, 16V, 18V, 20V, 22V, 24V, 27V, 30V, 33V  
Price: 8p each 100 any mix £6.00

### RESISTORS

1W at 40°C 5% tol., 2.2- $\Omega$  to 2M $\Omega$ , E12 2p each.  
Resistor Pack - 2.2  $\Omega$  - 2M $\Omega$ , 10 each value (730 resistors) £6.00

### 1 watt ZENER DIODES

3V3 to 200V Full range  
I.C. Sockets  
Price 15p each 100 any mix £12.50  
8 DIL 10p 22 DIL 23p  
14 DIL 13p 24 DIL 24p  
16 DIL 15p 28 DIL 28p  
18 DIL 18p 40 DIL 40p  
20 DIL 22p

### VEROBOARD (Copper Clad)

Size Inch 0-1" 0.15  
2.5 x 1 20p N/A  
2.5 x 5 55p 56p  
2.5 x 3.75 46p 50p  
Speakers 8" x 5" 3 ohm £1.50 each.

### CONNECTING CABLE

Black, Blue, Green, Gray, Orange, Pink, Red, White, Violet, Yellow, Brown.  
Singles 5p per metre  
7/0.2mm 5p per metre  
16/0.2mm 8p per metre

### SPECIAL OFFERS

#### BRAND NEW METAL SLIDER POTENTIOMETERS

60mm TRACK	1+	100+	Mains Rocker	BZY96 ZENERS
500 ohm Lin. Mono	35p	28p	switch with	(2W) - 6vZ
50K Log. Stereo	40p	30p	Neon 10A.	1+ 20p each
100K Lin. Stereo	40p	30p	D.P.S.T.	100+ 12p each
1 Meg Log. Stereo	40p	30p	65p each	

Other values available in 45mm track - send for list.

Send your orders to:

DEPT DP11, MARCO TRADING, THE OLD SCHOOL,  
EDSTASTON, Nr. WEM, SHROPSHIRE SY4 5RJ  
Tel: Whixall (094872) 464/465

Please add 30p postage and packing to each order and add 15% VAT to your total order. Export add NO VAT but add postage. Air/Sea at cost

### TANT. BEAD CAPS

0.1/35v	12p	4.7/35v	12p
0.22/35v	12p	33/6.3v	25p
1.0/35v	12p	47/10v	30p

### SUB. MIN. TOGGLE SWITCHES

SPST-	70p
SPDT-	78p
DPDT-	82p
DPDT-	90p



### BRIDGE RECTIFIERS

2.5 Amp 50V	32p	400V	50p
400V	43p	6.0 Amp 50V	70p
800V	58p	200V	78p
2.0 Amp 50V	35p	400V	85p
100V	42p	25 Amp 100V	
25 Amp 50V	£2.38		£2.41

### 0.1W SUB. MINIATURE PRE-SETS

100  $\Omega$  to 1 Meg Vertical or Horizontal  
Price: 6p each. 100 any mix £4.50

AC128	20p	BC125	10p	BC184	9p
AD149	58p	BC147	8p	ZN3055	48p
BC107	10p	BC153	10p	BY127	12p
BC108	10p	BC172	8p	IN4007	8p
BC109	10p	BC183	9p	IN4148	2p
BYF90	90p	BC212	9p	BC160	37p
BR101	32p	BC214	9p	CMOS	
741	20p	BC140	32p	4011	20p

## SMALL ADVERTISEMENTS

(Continued from page 189)

**FOR SALE:** KW2000 B Transceiver with trapped dipole antenna to match. £150. Prefer buyer collects. George Oxby, G3RRX, 36 Denmark Road, Beccles, Suffolk. Telephone: 0502-715322.

**INTERESTED IN RTTY?** You should find the "RTTY Journal" of interest. Published in California, U.S.A., it gives a wide outlook on the current RTTY scene; RTTY-DX; DXCC Honour Roll; VHF RTTY news; and up to date technical articles are included. Specimen copies 35p from: The Subscription Manager, RTTY Journal, 21 Romany Road, Oulton Broad, Lowestoft, Suffolk, NR32 3PJ.

**WANTED:** Service manual - Ekco car-portable type CP 920. To buy or borrow. Box No. G398.

**FOR SALE:** Photographic enlarging equipment: Vivitar enlarger. Model E.36 with 50mm f. 3.5 and 75mm f.3.5 lenses. Kodak safety light. Kodak contrast filter set. 11 in. x 14 in. printing frame with copying facilities. Measuring flask. Three trays, three tweezers. Three plastic bottles. Clips. Printing paper. Antistatic brush for cleaning negatives. Kodak Photoguide Booklet. Man's protective apron. £75 o.n.o. Pair of Goodman's speakers 8 ohms, 15 watts, £50 o.n.o. R. L. Gee, 3 Longfellow Drive, Hutton, Essex, CM13 2QQ.

**LEARN-KIT OSCILLOSCOPE**, etc. £50. Telephone: Newcastle-Upon-Tyne 862813.

**POSTAL ADVERTISING?** This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list. - The Holborn Direct Mail Company, Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407 6444.

**PEN TYPE SIGNAL INJECTOR** available for £2.50 including air freight. Business Promotion Bureau, 376 Lajpat Rai Market, Delhi 110006, India.

**INTERESTED IN OSCAR?** Then join AMSAT-UK. Newsletters, OSCAR NEWS Journal, prediction charts, etc. Details of membership from: Ron Broadbent, G3AAJ, 94 Herongate Road, Wanstead Park, London, E12 5EQ.

**£5 OSCILLOSCOPE.** Standard junk box components plus approx. another £5 (Total components approx £12). This unit plugs into TV aerial socket and converts TV to oscilloscope. Circuit and plans £3. Kerr, 27 Coles Road, Milton, Cambridge, CB4 4BL.

(Continued on page 191)

## BUILD YOUR OWN

### P.A., GROUP & DISCO SPEAKERS by R. F. C. Stephens

Save money with this practical guide. Plans for 17 different designs, Line source, I.B., Horn and Reflex types, for 8"-18" drive units. £3.95 post free (\$8 overseas).

### THE INFRA-BASS LOUDSPEAKER by G. Holliman

(full constructional details for versions using 15", 12" and 10" (drive units). £2.95 post free (\$6 overseas).

### THE DALESFORD SPEAKER BOOK by R. F. C. Stephens

This book is a must for the keen home constructor. Latest technology DIY designs. Plans for I.B., and Reflex designs for 10-100 watts. Also unusual centre-bass system. £2.20 post free (\$5 overseas).

### VAN KAREN PUBLISHING

5 Swan Street, Wilmslow, Cheshire

### AERIAL SPLITTERS

2-UHF Televisions from one aerial.  
Price £1.70.  
10-Moulded Co-ax Plugs £1.20.  
Low loss Co-ax Cable white 15p per metre.

### 100 MULLARD C280/C281

#### CAPACITORS

Values from .01uf to 1.5uf 250V/W, our choice, good mixed selection. Price £2.00 per 100

**SIGNAL INJECTORS** with (pre-set) variable AF, which emits RF harmonics into the UHF band. Protected up to 300 volts dc. Complete with leads £5.70 each.

All prices include VAT at 15% P&P per order 30p. S.A.E. for leaflets. Access cards.

## ELECTRONIC MAILORDER LTD,

62 Bridge Street, Ramsbottom,  
Via Bury, Lancs. BL0 9AGC. Tel. Ramsbottom 3036

### AERIAL AMPLIFIERS

Aerial amplifiers can produce remarkable improvement on the picture and sound in fringe or difficult areas.

**B45** - for mono or colour this is tunable over complete UHF television band.

**B11** - for stereo or standard VHF/FM radio.

**B11A** - 2 metres Aircraft bands.

All amplifiers are complete and ready to use.

Battery type PP3 or 8v to 18v dc, next to the set type fitting. Prices £6.70 each.



## SMALL ADVERTISEMENTS

(Continued from page 190)

### PERSONAL

**JANE SCOTT FOR GENUINE FRIENDS.** Introductions to opposite sex with sincerity and thoughtfulness. Details free. Stamp to: Jane Scott, 3/Con North St. Quadrant, Brighton, Sussex, BN1 3GJ.

**IF YOU HAVE ENJOYED A HOLIDAY** on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from: - The Hon. Membership Secretary, The Broads Society, "Icknield," Hilly Plantation, Thorpe St. Andrew, Norwich, NR8 8SS.

**SPONSORS** required for exciting scientific project Norwich Astronomical Society are building a 30" telescope to be housed in a 20" dome of novel design. All labour being given by volunteers. Already supported by Industry and Commerce in Norfolk. Recreational. Educational. You can be involved. Write to: NAS Secretary, 195 White Woman Lane, Old Catton, Norwich, Norfolk.

**BROADLANDS RESIDENTIAL CLUB** for elderly people. Are you recently retired and looking for a home? We have a delightful top floor room overlooking Oulton Broad, facing south. Write to: The Warden, Broadlands Residential Club, Borrow Road, Oulton Broad, Lowestoft, Suffolk.

**NORTHAMPTON:** Television and Electrical Goods and Repairs. Old established business in freehold premises retail shop - well known local name. For Sale as a going concern plus s.a.v. Price £22,000 includes Shop, small workroom, private car park. Very busy main road position between public house and car showrooms. Apply:- Jackson-Stops & Staff, 20 Bridge Street, Northampton.

### PRINTED CIRCUIT BOARDS FOR "RADIO & ELECTRONICS CONSTRUCTOR" PROJECTS.

"Two 20dB amplifiers" Board for part 1 68p plus 25p P&P  
Board for part 2 62p plus 25p P&P

All boards ready for use, roller tinned and drilled, glassfibre.


Trade enquiries welcome. Highly competitive prices. Write now for quote To:

#### BRB PRINTED CIRCUITS (REC)

109, Potter Street, Worksop,  
Notts. S80 2HL.
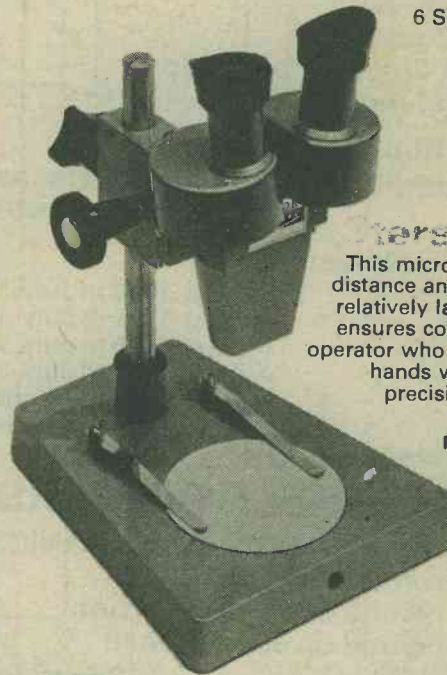
## REVROR OPTICAL & TECHNICAL

6 SICILIAN AVENUE  
LONDON W.C.1  
Tel. 01-836 4536



**PRICED  
FROM  
£148.75**

This microscope's working distance and field of view is relatively large; this feature ensures convenience to the operator who works with both hands while assembling precision mechanisms.

**IDEAL FOR  
PRINTED CIRCUITS  
AND OTHER  
DELICATE WORK.**

**COMES  
COMPLETE WITH**

built-in x 10 Mag.  
Objectives x 20  
Objectives x 35  
At extra cost

We stock one of the largest selections of second hand microscopes and optical magnifiers, on and off stands. Please phone for details.

## RADIO & ELECTRONICS Constructor Projects

CONSTANT CURRENT CHARGER	September	£12.40
9 VOLT 1 AMP POWER SUPPLY	September	£8.80
REMOTE VOLUME ATTENUATOR	August	
(Excludes 3 core cable)		£3.00
CAPACITANCE MEASURING ADAPTOR	July	
(Excludes etched p.c.b.)		£8.75
80M AMATEUR BAND RECEIVER	July	
(Earphone supplied)		£21.75
MODULATED ALARM GENERATOR	June	
(Excludes p.c.b. & speaker)		£4.50
PASSIVE LOGIC PROBE	June	£2.50
DUSK TO DAWN SWITCH	June	£8.50
WIEN BRIDGE A.F. SIGNAL GENERATOR	June	£8.60
DUAL POLARITY VOLTMETER	May	£9.60
LABORATORY POWER SUPPLY	May	£12.80
GENERAL PURPOSE 8W AMPLIFIER	May	
(Excludes p.c.b.)		£12.75
STEREO MIXER UNIT	March	£7.60
INFRA-RED INTRUDER ALARM	March	
(Relay if required £3.20)		£6.10
TELEPHONE BELL REPEATER	February	
(Mic cable 10p/metre)		£5.80
LOGIC TESTER	January (Excludes probe)	£3.05
RING OF LEDS PRINT TIMER	January	£7.80

All kits include parts as specified in the article except where indicated. Postage is 50p per kit. Please allow 10 days for delivery. Remember, we also stock a wide range of components and accessories. Send 30p in stamps for our full lists.

## T & J ELECTRONIC COMPONENTS

98 Burrow Road, Chigwell, Essex. IG7 4HB

# RADIO & ELECTRONICS CONSTRUCTOR

## Single Copies

Price 60p each, p&p 18p

Issue(s) required .....

## Annual Subscription

Price £9.50 inland, £10.50 overseas (including Eire)

post free, commence with ..... issue

## Bound Volumes:

Vol. 27.	August 1973 to July 1974	Price £3.00, post & pkg £1.30
Vol. 28.	August 1974 to July 1975	Price £3.20, post & pkg £1.30
Vol. 29.	August 1975 to July 1976	Price £3.50, post & pkg £1.30
Vol. 30.	August 1976 to July 1977	Price £3.70, post & pkg £1.30
Vol. 31.	August 1977 to August 1978	Price £5.20, post & pkg £1.30
Vol. 32.	September 1978 to August 1979	Price £5.50, post & pkg £1.30

## CORDEX SELF-BINDERS

With title, 'RADIO & ELECTRONICS CONSTRUCTOR' on spine,  
maroon only

Price £2.25, post & pkg 50p

With no title on spine, maroon

Price £2.25, post & pkg 50p

With no title on spine, green

Price £2.25, post & pkg 50p

Prices include V.A.T.

## DATA BOOK SERIES

DB5 TV Fault Finding, 132 pages

Price £1.20, P.&P. 27p

DB6 Radio Amateur Operator's Handbook,

New edition in course of preparation

DB17 Understanding Television, 504 pages

Price £3.95, P. & P. £1.00

DB19 Simple Short Wave Receivers

Price 80p, P. & P. 27p

140 pages

## STRIP-FIX PLASTIC PANEL SIGNS

Set 3: Wording - White

- 6 sheets

Price £1.50, P. & P. 11p

Set 4: Wording - Black

- 6 sheets

Price £1.50, P. & P. 11p

Set 5: Dials

- 6 sheets

Price £1.50, P. & P. 11p

Prices include V.A.T.

I enclose Postal Order/Cheque for ..... in payment for .....

.....

NAME .....

ADDRESS .....

(BLOCK LETTERS PLEASE)

*Postal Orders should be crossed and made payable to Data Publications Ltd.*

*Overseas customers please pay by International Money Order.*

*All publications are obtainable through your local bookseller*

Data Publications Ltd., 57 Maida Vale, London W9 1SN


**PLEASE MENTION THIS MAGAZINE WHEN WRITING TO ADVERTISERS**

# BANDSPREADING

The r.f. amplifier, mixer and oscillator stages of a short wave superhet appear in (a). The r.f. amplifier and mixer input tuned circuits, and the oscillator tuned circuit, are all tuned by a 3-gang variable capacitor. Since tuning at short wave frequencies is sharp the 3-gang capacitor has to be adjusted through a high ratio tuning drive which must have a positive action free of mechanical "backlash".

An alternative approach towards ease of tuning is to connect a small value variable capacitor in parallel with each main tuning capacitor, as in (b). The main tuning capacitor is then the "bandset" capacitor and the small value capacitor the "bandspread" capacitor. The bandset capacitor is set roughly to the frequency desired, final tuning being carried out with the bandspread capacitor. In our example the bandspread capacitor could be a 3-gang component, with its sections in parallel with the sections of the main 3-gang capacitor. Alternatively, a single-gang capacitor having a very low value can be connected across the oscillator tuning capacitor only, since it is the oscillator which effectively selects the signal frequency to be amplified in the receiver i.f. stages.

In (c) the oscillator tuned circuit is tuned by a reverse biased variable capacitance, or varactor, diode, whereupon the potentiometer becomes the receiver tuning control with the voltage at its slider being passed also to similar varactor tuned circuits in the r.f. and mixer stages. If a low value potentiometer is inserted in series with the main tuning potentiometer, as in (d), it will function as a bandspread control and provide fine tuning.

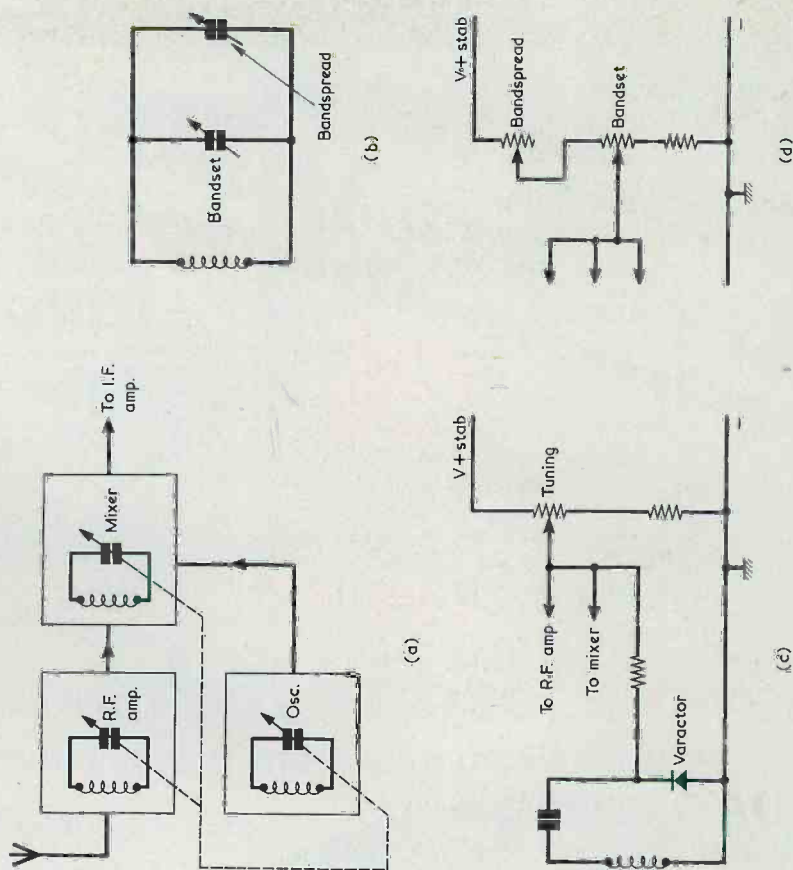


# MAPLIN
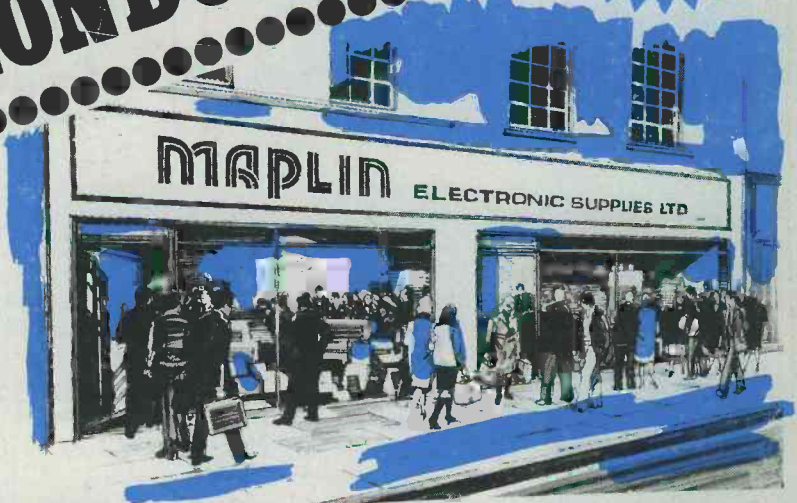
## announce the opening of their new LONDON shop

159-161  
King St.  
Hammersmith  
London W6  
01-748 0926



- \* Excellent metered parking
- \* Close to Hammersmith Underground Station for Piccadilly, District & Metropolitan Lines
- \* Bus no's 260·266·704·27·91 267·290 stop outside



# Opens Tuesday 16th September, 1980


Opening Hours 9.45 am to 5.30 pm Tuesday to Saturday (Closed Monday)

Maplin mail-order –  
Now better than ever!

- \* Up to 8% discount for use with next order
- \* All prices include VAT
- \* Same day service on in-stock lines
- \* Over 95% of our stock lines in stock
- \* Large range of all the most useful components
- \* First class reply paid envelope with every order
- \* Quality components – no rejects – no re-marks
- \* Competitive prices
- \* Your money is safe with a reputable Company

On price, service, stock, quality and security, it makes sense now more than ever to make Maplin – your first choice for components every time!

### Stereo Cassette Tape Deck

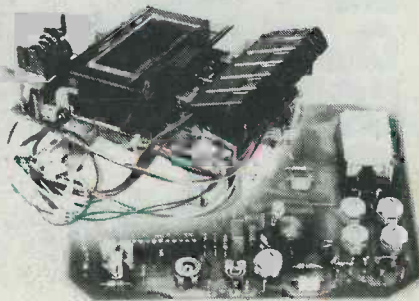

Utilising the superb JVC deck made for Tandberg and a ready-made pre-aligned, tested and guaranteed module, this cassette deck has a superb sound and a high quality specification. We've got everything you need (except cabinet) including full instruction leaflet for only £39.95. Order as XY36P (Cassette Recorder Kit)

### Space Invaders

Fight the space invaders, be a polaris captain or a spaceship commander. Full colour action on your own TV set and over 450 games to play.

Basic console with Combat cartridge (AC00A) £99.50 + £2.50 carriage

All cartridges available including:

Space Invaders (AC26D)	£29.95	Adventure (AC22Y)	£23.95
Indy 500 (AC24B)	£34.50	Skydiver (AC13P)	£16.95
Chess (8levels) (AC28F)	£34.50	Breakout (AC05F)	£16.95
Golf (9holes) (AC18U)	£16.95	Slot Racers (AC19V)	£16.95
Air Sea Battle (AC01B)	£16.95	Programming (AC27E)	£34.50
Space War (AC02C)	£16.95	Olympics (AC04E)	£16.95
Brain Games (AC16S)	£16.95	Street Racer (AC14C)	£16.95
Outlaw (AC03D)	£16.95	Keyboards per pair (AC29G)	£11.95

All prices include VAT and carriage except where shown.

Post this coupon now for your copy of our 1979-80 Catalogue price 70p (plus 46 p&p). Please send me a copy of your 280 page catalogue. I enclose 70p (plus 46 p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.35 or ten International Reply Coupons. I enclose £1.16.

Name \_\_\_\_\_

Address \_\_\_\_\_

REC 11-80

# MAPLIN

Maplin Electronic Supplies Ltd

All mail to:- P.O. Box 3, Rayleigh, Essex SS6 8LR.  
Telephone: Southend (0702) 554155.

Shop: 284 London Road, Westcliff-on-Sea,  
Essex. (Closed on Monday)  
Telephone: Southend (0702) 554000.



Catalogue now available in all branches of WHSMITH Price £1.00