

A NEW HIGH-POWER TELEVISION STATION

Television

and SHORT-WAVE WORLD

MAY, 1938

No. 123. Vol. xi.

**AERIAL FOR
LONG-
DISTANCE
TELEVISION**

**PICTURES ON
A 31-INCH
TUBE**

**20 OTHER
ARTICLES
FULLY ILLUSTRATED**



PICTURES AT 97 MILES!

Actual Untouched Photographs of Pictures Received on

OUR HOME-BUILT LOW-COST TELEVISOR

SEE PAGE 271



**SHORT
WAVES**

**A T-40 TRANSMITTER
THE DOUBLE-DOUBLET AERIAL
AMATEUR ACTIVITIES**

**BERNARD JONES PUBLICATIONS LTD.
CHANSITOR HOUSE, CHANCERY LANE
LONDON W.C.2.**

THE FIRST TELEVISION JOURNAL IN THE WORLD

A BRITISH TRANSMITTING VALVE FOR BRITISH AMATEURS THE EDISWAN E.S.W.20



Believing that the British Amateur Transmitter would prefer to use valves of home origin the Ediswan Co. have produced the first medium power transmitting valve at a price within the reach of all pockets.

The E.S.W.20 is a 20-watt short-wave oscillator fitted with a UX base and will satisfactorily replace similar valves in Class B and Class C circuits with increased efficiency.

CHARACTERISTICS:

Filament Volts - - - -	7.5	Amplification - - - -	22
Filament Current - - -	2.0 amps	Mutual Conductance	1.7 ma/V.
Max. Anode Volts - - -	800	Impedance - - - -	12,500 ohms.
Max. Dissipation - - -	20 watts	Base: 4-pin UX type	

PRICE 17/6

Supplies will shortly be available from Messrs. Webb's Radio, Soho Street, W.C.2. Radiomart (Birmingham) Ltd., and other 'ham' suppliers.

SUPPLIERS OF VALVES TO ALL GOVERNMENT DEPARTMENTS

EDISWAN CATHODE RAY TUBES

EDISWAN CATHODE RAY TUBES are used by leading set makers and home constructors on account of their exceptional efficiency and brilliance.

The full range now includes 9" and 12" tubes electrostatically and magnetically focussed.

Write for full particulars to the Technical Service Department

THE EDISON SWAN ELECTRIC CO. LTD., 155 CHARING CROSS ROAD, LONDON, W.C.2

R.M.336



TELEVISION

and SHORT-WAVE WORLD

Special Features

	PAGE
New Farnsworth Pick-up Tube ...	260
World's Most Powerful Television Station ...	261
Directly-viewed Large Pictures ...	265
The Simplest Televisor ...	267
Television Sound Programmes on Your Broadcast Set ...	275
Marconi E.M.I. System ...	284
10-watt Aero Transmitter ...	294
1938 Valve Designs ...	296
Double-doublet Aerial ...	297
Dual-purpose Communication Receiver ...	301
T-40 Transmitter ...	305
Low-loss T-20 Output Stage ...	314

TELEVISION AND SHORT-WAVE WORLD

Proprietors:
BERNARD JONES PUBLICATIONS, LTD.

Editor-in-Chief:
BERNARD E. JONES.

Editor:
H. CORBISHLEY, F.T.S.

Short-Wave Editor: KENNETH JOWERS

Editorial, Advertising and Publishing Offices:

Chansitor House, 38, Chancery Lane, London, W.C.2.

Telephones: Holborn 6158, 6159.

Telegrams: Beejapee, Holb., London.

Subscription Rates: Post paid to any part of the world—3 months, 3/6; 6 months, 6/9; 12 months, 13/6.

Published Monthly—1/- net. On the first day of the month).

Contributions are invited and will be promptly considered. Correspondence should be addressed according to its nature, to the Editor, the Advertisement Manager, or the Publisher, "Television and Short-wave World," Chansitor House, Chancery Lane, London, W.C.2.

IMPORTANT

"Television and Short-wave World" is registered at the General Post Office, London, for transmission to Canada and Newfoundland by Magazine Post. Entered as Second-class mail matter, Boston, Mass.

COMMENT OF THE MONTH

Small Tubes

WE publish on another page in this issue (p. 292) a letter from a reader giving a brief description of a receiver he has constructed employing a one-inch tube. A picture of such a size may seem absurd and it may be argued that it is theoretically impracticable to obtain a picture comprising 405 lines on such a small area. The fact is, however, as we have been aware for a considerable time, that the definition obtained on miniature screens leaves little to be desired. If it is remembered that the pictures obtained by scanning discs in the old 30-line days were of even smaller area and by means of simple magnification gave a considerable amount of satisfaction to many thousands of experimenters, it will be appreciated that the small tube has its possibilities.

The point we wish to stress is that with the small-tube receiver the experimenter has all the essentials of the modern cathode-ray televisor; at a comparatively small cost it is within his power to obtain valuable constructional and operating experience in addition to a reasonable amount of entertainment. In brief, he can become a viewer. Our correspondent estimates the cost of his receiver as being approximately £10; for rather more than twice this amount it is possible to employ a four-inch tube in the simple type of receiver of which constructional details have been given in recent issues. The small tube is, without doubt, the only solution of the problem of cost and is likely to remain so for a very considerable time.

The Eiffel Tower High-power Station

ALTHOUGH this country is outside the estimated range of the new Eiffel Tower high-power transmitter which is shortly to start working on its full power of 30 kilowatts, there are grounds for believing that it may be receivable in the South of England. Normally expected ranges have constantly been exceeded in the case of the Alexandra Palace transmissions and it seems likely therefore that the distance between Paris and the South of England may be covered in view of the great increase of power and aerial height.

If reception in this country of the French transmissions is found to be possible it will no doubt provide an additional interest. Unfortunately the standards differ, but this is a practical matter in receiver design which owing to the flexibility of the cathode-ray receiver could be overcome.

A NEW FARNSWORTH "PICK-UP" TUBE AMPLIFICATION BEFORE SCANNING

Here are details of a new camera pick-up tube that has been developed in the Farnsworth Laboratories. By reason of the fact that the image is amplified before it is scanned it is claimed that the tube is more sensitive than any of the existing types.

From Our American Correspondent.

PHILO T. FARNSWORTH, of Farnsworth Television Incorporated, has developed a new "pick-up" tube for use in television cameras which experiments have shown to be not only extremely sensitive to out-of-doors daylight under the most difficult conditions, but which also eliminates most—if not all—of the undesirable features that

electrically active material. In front of the image screen toward the window of the tube is placed the anode, or signal screen B. This screen is of a comparatively open mesh of fine wire, so that it is over 95 per cent. transparent.

In operation, the optical image to be transmitted is focused on the image grid A, and the light falling

element than have been available by previous means. Almost all the electrons drawn through the apertures in the image grid are collected by the anode B, although a very small part of them are collected by the photo islands and serve the function analogous to the grid leak. This amplification process results in a tremendous increase in the signal-to-noise ratio.

Increased Sensitivity

Since the image grid is only an inch or so behind the optically clear window, it is not necessary to use a long-focus lens, and a large-aperture optical system is possible. Further, the number of stray electrons picked up by the islands may be controlled (the grid leak is variable). This enables the amount of amplification in elemental amplifiers to be conveniently adjusted to suit varying light conditions and time of response.

This tube, radically different from any other "pick-up" tube, would seem to promise a great increase in the sensitivity of television cameras.

It may be of interest to mention that the same principle has also been applied to the Farnsworth dissector tube. In this case the back of the storage screen is coated with photo-sensitive material which if flooded from a uniform source of light produces photoelectrons. These photoelectrons are subjected to the same triode action as described above. An amplified electron image is thus formed which is scanned across an aperture in the same manner as in the earlier dissector tubes.



A photograph of the new Farnsworth tube.

have troubled television engineers in the design and building of tubes for this purpose.

The principle of the tube briefly is that amplification of the image is accomplished before scanning. The advantage of amplifying before the image is scanned, results from the fact that the amplifier need not respond to very high frequencies and that the effect of the light may be cumulative. The effect is accomplished by effectively embodying within the tube a million or more small triode amplifiers, the control elements of which are sensitive to light.

The new tube consists essentially of an image grid A, a signal screen B, and a cathode-ray gun C, all suitably mounted in the evacuated glass container. The glass tube has a flat window at one end, and a cathode-ray gun is in the neck.

The image grid is made up of a thin sheet of suitable metal, perforated with approximately 160,000 holes to the square inch. On the side towards the window of the tube is deposited an insulating substance, and upon this insulator are deposited numberless small islands of photo-

upon the photo-electrically sensitive islands causes the emission of electrons from individual islands proportional to the amount of light. An electrostatic charge image is thus set up on the image grid. The cathode-ray gun projects a fine high velocity beam of electrons against the metal back of this image grid and secondary electrons are produced at the point of impact of the beam.

These electrons are drawn through the apertures in the screen by the positive potential on the photo islands on the opposite side. This action represents the unique feature of this tube in that a far greater number of electrons are produced per picture

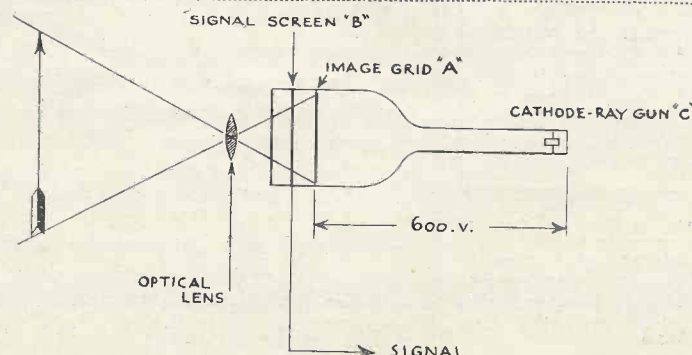


Diagram showing the principle of the tube. The beam is deflected in the usual way by electro-magnetic coils. There is a difference of 22 volts between the signal grid and image grid.

THE WORLD'S MOST POWERFUL TELEVISION STATION

EIFFEL TOWER SHORTLY TO START WITH A POWER OF 30 KILOWATTS

RECENTLY (April 8) the Minister of the French P.T.T. invited members of the Press to inspect the new television transmitter at the Eiffel Tower. This transmitter, soon to be one of the most, if not the most powerful television broadcasting station in the world, was engineered and installed by Le Matériel Téléphonique, French licensee of the International Standard Electric Corporation of New York. The transmitter, which has been regularly operating since September, 1937, with reduced power, has recently been transmitting with a power of 15 kW and will shortly be broadcast-


port the television antenna at the height of 315 metres.

Hopes are entertained that when the Eiffel Tower transmitter comes into operation with its full power of 30 kilowatts it will be possible to receive the programmes in the South of England. This article describes the transmitter and gives details of the transmission standards that will be employed.

The design and construction of the antenna and transmitter have involved not only the solution of new

out without interfering with the elevator service of the Eiffel Tower and with full regard to stresses and strains which could be applied to the structure itself.

The French Posts, Telephones and Telegraphs Department, anxious to ensure that the programmes to be transmitted should be the best that modern technique could provide, have constructed and equipped two studios containing the most up-to-date equipment. These two studios are situated at distances of 5 and 2.5 kilometres from the transmitter to which they are connected by special equipment and cables, the contract

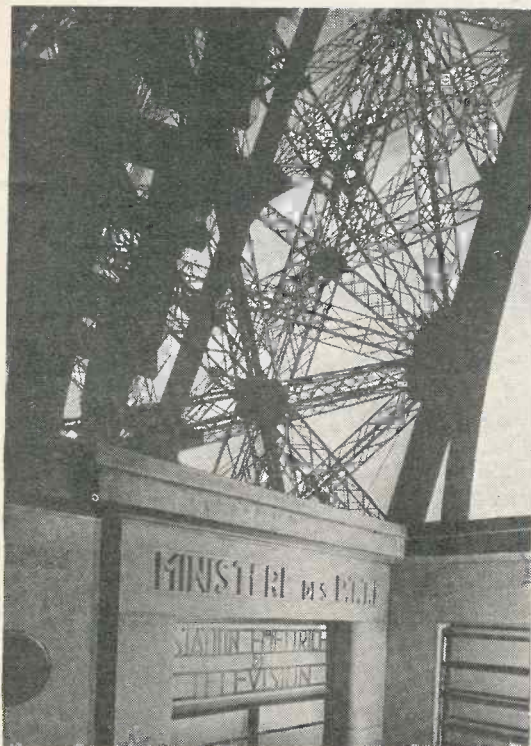

Left. The entrance to the station with the framework of the Eiffel Tower showing in the background.

Right. Installing the feeder cable which runs up the framework of the tower.



ing with a power of 30 kW peak. Already it ranks with the most powerful commercial transmitter of its kind now in operation, awaiting only the utilisation of its full 30 kW power to make it the World's most powerful station.

The transmitter is located at the base of the Eiffel Tower, and use is made of the famous structure to sup-

and difficult technical problems but the solution of many unique difficulties occasioned by the necessity of installing a feeder cable to connect the transmitter and the antenna. This cable has a total length of 380 metres, is over 5 in. in diameter and has a total weight of over 12 tons. It is the longest of its kind in the world. Installation had to be carried

for which was placed with Le Matériel Téléphonique.

The Feeders

The cable is of the coaxial type consisting of a solid inner conductor of copper, supported within a flexible copper outer conductor. This in turn is sheathed in lead after which a fur-

THE AERIAL FEEDER

ther protective covering of impregnated jute and of spirally wound steel wire is applied. The cable has a characteristic impedance of 71 ohms and a maximum attenuation of 4.8 db. per mile at 1 megacycle, 6.6 db. at 3 megacycles and 12.6 db. at 8 megacycles.

Perhaps the biggest problem in the development of a cable of this

carriers for transmission over the cable. For transmission of the image band a carrier frequency of 5.5 Mc. is employed, this giving a total transmitted band of 3 Mc. to 8 mcg.


The Modulator

The equipment for modulating the

and a uniform gain from 3 to 8 megacycles.

Control equipment is provided at both studios and at the radio transmitting station for monitoring the level and form of the signal at the input and output of each unit.

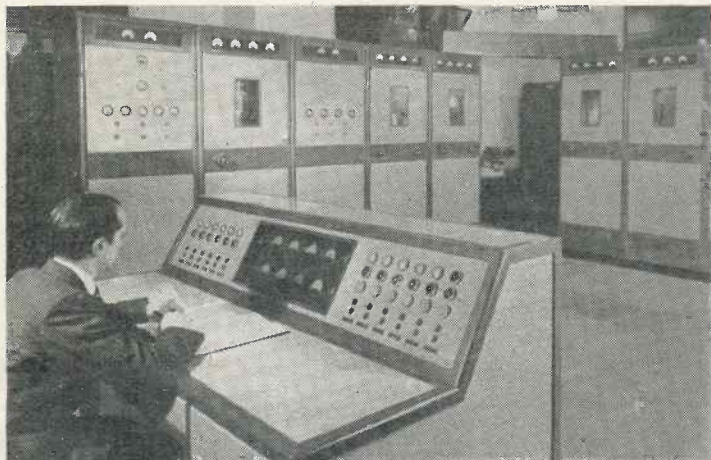The terminal equipment repeaters and control equipment are completely self-contained. All power is supplied



Left. A portion of the transmitter with the control desk in the foreground.

Right. Another picture showing the installation of the feeder which was a task of considerable difficulty.



type is to obtain a perfectly uniform impedance characteristic. This is more and more important as the cable becomes longer. One of the important elements to obtain this result is the outer conductor. This must be flexible, but must not be distorted when bent, and the diameter must be entirely uniform through the length. It must be self-supporting in order that the diameter will not depend on the dielectric between the inner and outer conductors. The problem has been solved by forming the outer tube of a series of interlocking copper strips having a cross section in the form of a letter "Z," as used by the Bell Laboratories in the New York-Philadelphia coaxial cable. These strips are spirally wound and are held in place by a soft steel ribbon which is wound around them. Thus, a completely self-supporting outer tube of constant diameter is obtained.

The dielectric consists of a material having very low dielectric losses at high frequency, and serves simply to centre the inner conductor.

Due to the fact that amplifiers covering wide bands beginning at very low frequencies are difficult to manufacture with satisfactory characteristics, the 5 to 2,500,000-cycle signal is impressed upon high frequency

5.5 Mc. carrier consists of a crystal controlled oscillator, a 5.5 Mc. decoupling amplifier, a balanced oscillator and two push-pull amplifiers. The television signal is supplied directly from the amplifier connected with the scanning device at a level of 50 milliwatts in 70 ohms. This is sufficient to modulate the grid of the modulated amplifier. The complete signal is then amplified in two linear stages and applied to the coaxial cable.

At the receiving end the incoming modulated carrier is amplified and then demodulated in a symmetrical circuit. The 60 milliwatts of television signal produced across the 70-ohm output is applied to the modulating amplifier of the television transmitter. In the case of the longer length of cable, a repeater is necessary to restore the level to its normal value. The repeater consists of a 3-stage amplifier having input and output impedances of 70 ohms

from the 110-volt, 50-cycle supply, the voltage of which is kept constant by means of suitable voltage regulators. In addition the individual plate voltages of the various units are highly stabilised.

The television transmitter itself comprises all the refinements made possible by recent progress in the research laboratories of Le Matériel Téléphonique and its associated companies. Not only is the power the greatest yet attempted, but the definition of the pictures transmitted is higher than that at present employed in any other country.

For several years the laboratories of Le Matériel Téléphonique have been engaged in developing high definition television scanning and transmitting equipment. The first field tests of such equipment were conducted in 1935 when transmission was effected from the laboratories to a demonstration receiver at a distance of several miles. Since then develop-

THE MOST POWERFUL STATION

ment work has been intensified so that when tenders were made on the new Eiffel Tower transmitter it was possible to offer equipment which had, besides the qualities common to all modern transmitters, certain features believed to be unique.

Since there is as yet no definite world-wide standardisation as to the most preferable type of image scanning it was necessary that the transmitter should have sufficiently flexible characteristics to operate regardless of the type of scanning employed, provided that the modulation frequencies remain within the specified band.

30 Kilowatts Power

The transmitter is designed to operate on a frequency between 40 and 50 megacycles (at the moment 46 Mc. is being used) and has a peak continuous power output of 30 kW. The frequency is maintained constant within narrow limits by a quartz crystal oscillator. The quartz is cut to have a low temperature coefficient, and oscillates on the third partial of its fundamental frequency. An oven is provided which maintains the temperature of the crystal constant at $50^{\circ}\text{C.} \pm .5^{\circ}$. The oscillator is followed by two doubler stages which raise the frequency to the final carrier value. The doublers are followed by a single tube amplifier, two air-cooled push-pull amplifiers, and three water-cooled push-pull amplifiers, the output of the final stage being coupled to the 56-ohm transmission line to the antenna.

Modulating Amplifier for Frequencies from 0 to 5 Cycles

Due to difficulties which are normally present in D.C. direct-coupled amplifiers, this modulator effects all the amplification at a carrier frequency on which the 0 to 5-cycle signal is impressed. The 60 mW input to the unit modulates the output of a crystal oscillator-amplifier unit operating on 3 megacycles. The modulated carrier is then amplified in five push-pull air-cooled stages to a level of 2 kW, which is rectified in a symmetrical diode circuit. The load resistance of the rectifier is connected through a low-pass filter in series with the grids of the last H.F. amplifier. The rectified carrier voltage supplies the fixed grid bias for the

H.F. amplifier, and the modulation frequencies modulate the H.F. amplifier grids. The modulation amplifier employs a large reverse feed-back which keeps the linear distortion of the amplifier at a low value.

Modulating Amplifier for Frequencies from 25 to 2,500,000 Cycles

This amplifier receives an input of 3 volts peak in 70 ohms from the coaxial cable terminating equipment and amplifies it to a peak value of about 2,500 volts for modulation of the grid of the final radio-frequency amplifier.

The amplifier consists of four air-cooled stages followed by two water-cooled stages. A modified form of resistance-capacity coupling is used throughout. Due to the extreme limits of the band to be transmitted with small amplitude and phase distortion, care is taken to keep the capacity to ground of the active elements at a minimum. In spite of this it is essential to operate the tubes into a load circuit of comparatively low impedance in order to minimise the loss at the higher end of the amplified band.

The positive terminal of the plate supply to the final stage is earthed, the negative terminal, and hence the entire filament and grid circuit, being at a high negative potential with respect to earth. This is done in order that the plate of the modulator may be connected directly to the grids of the modulated H.F. amplifier, thus avoiding the coupling condenser and high grid resistance which would be necessary if capacity coupling were employed. Thus the D.C. drop in the modulator plate resistor furnishes the negative bias for the H.F. stage, and this bias is varied by the signal output of the modulator.

Monitoring and Test Equipment

The monitoring equipment for a television transmitter is considerably more complicated than that for a sound broadcast station, due to the fact that the modulating wave shapes are neither sinusoidal nor symmetrical, and that in addition to controlling the frequency distortion, harmonic distortion and percentage modulation, the phase distortion must also be maintained at a very low value. At present, the easiest

method for accomplishing this is by means of the cathode-ray oscillograph. Consequently five oscillographs, with their associated equipment, are mounted on the monitoring bays. These give a rapid indication of:

- (1) The envelope of the H.F. output to the antenna.
- (2) The signal components at the input to the modulating amplifier.
- (3) The signal components from a linear rectifier coupled to the output of the transmitter.
- (4) The television image at the input to the transmitter.
- (5) The television image as received from a linear rectifier at the output of the transmitter.

These instruments give an easy and rapid check as to whether the transmitter is operating in the correct manner. For precision measurements they are, of course, supplemented by additional test equipment, which, however, does not form part of the permanent installation.

Power Supply

The transmitter is operated directly from the 500 volt, 50 cycle, 3-phase mains and takes a maximum power of approximately 350 kVA. All direct-current supplies are furnished from either hot-cathode mercury-vapour rectifiers or selenium dry rectifiers, so that no moving machinery is used.

Due to the necessity of avoiding coupling between the various modulator stages and also between the two modulated stages of the H.F. amplifier, five separate power supplies varying from 7,500 volts 2 amperes to 14,000 volts 10 amperes are employed. These are also of the hot-cathode mercury-vapour type and are located in a room adjacent to the transmitter room. The rectifiers employ a type of construction in which the H.T. transformer, filament transformer, and filter choke are mounted in a tank with the rectifier valves mounted directly above the tank and forming an integral part of it.

The control desk is located in the transmitter room facing the equipment and from this desk the transmitter can be set in operation. Separate push buttons, which are so interlocked that they must be operated in

the proper sequence, apply the main power supply, rectifier filaments, transmitter filaments and all H.T. which is located in the transmitter proper, and the external H.T. either together or separately. Indicating lamps show that the various units are operating.

Push buttons are also located on

the various units of the transmitter for individual application of all H.T. and the filament voltages of the water-cooled tubes.

Water cooling Plant

The water cooling system has a flow of 350 litres per minute and is designed to continuously dissipate

200 kW. The system is entirely closed and employs distilled water.

Each water cooled stage of the transmitter is provided with a water flow meter which indicates the flow directly in litres per minute and is provided with a contact for removing filament and H.T. voltage if the flow falls below a predetermined value.

STANDARDS ADOPTED BY THE COMPAGNIE FRANCAISE DETELEVISION

The picture is 450 lines, interlaced, having a frame frequency of 50 per second. The interlacing is accomplished in the following way:

whether "odd" or "even," and the displacement of the lines is produced by a phase shift of the synchronising signal during the

initial lines of the second "even" frame are superimposed on the lines of the preceding frame. The synchronising signal is then retarded by


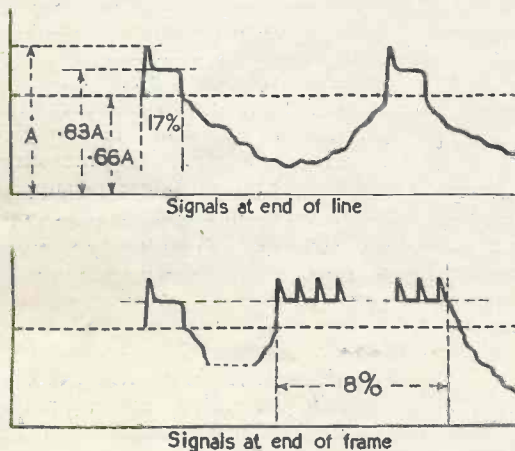


Fig. 1. (left) The synchronising signals correspond to "blacker than black" although the modulation is negative. The line impulse has a short steep front followed by a longer impulse of lower amplitude. The total duration is 17% of the line. The proportion between the amplitude of the pulse and the picture signal is shown in the figure.

The frame synchronising impulse is rectangular, lasting for 8% of the frame. The line impulses are transmitted during the frame pulse, ensuring that the first and last few lines are coincident as explained above.

Fig. 2. (right) The aspect ratio is 4.5 for the visible portion of the figure.

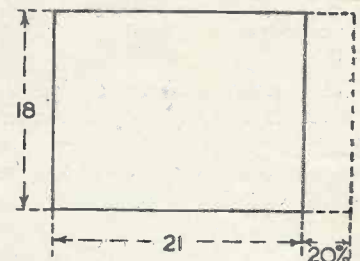

a small amount until the scan has dropped behind by half a line. This has the effect of producing the interlace, which is maintained until a few lines from the end of the frame when the synchronising signal is again advanced to cause the lines to be superimposed. The method is known as "interlacing by internal phasing," and the total time during which the lines are superimposed is equivalent to 30 lines.

The picture synchronising signal coincides with the line synchronising signal at the end of each frame

scanning of the frame. After the completion of one frame (the "odd" one, for example), the

The Philco Television Camera

On page 220 of last month's issue two drawings of camera tubes were shown, the upper, a R.C.A. tube, the power being described as a Farnsworth tube. The latter description was incorrect and the tube shown is one that has been developed by the Philco Radio and Television Corporation of Philadelphia.

The photograph here shows the camera in which this tube is employed. This new Philco television camera is electrically raised and lowered and is designed so that a single control handle rotates, tilts and focuses the camera. It forms a unit of the experimental 441-line television system operating in Philadelphia. The entire transmission sys-



The Philco Camera.

tem, as well as the receivers used in field tests, are capable of transmitting and reproducing frequencies up to 4.2 mc. The sound and vision transmitters operate in the 50-56 mc. channel. Transmitter power is 4 kW peak.

BAIRD TELEVISION LTD. CHANGE OF ADDRESS

Baird Television, Ltd., have now removed their offices and laboratories to new premises at Worsley Bridge Road, Lower Sydenham, S.E.26, telephone Hither Green 4600.

"Television and Short-wave World" circulates in all parts of the world.

DIRECTLY-VIEWED LARGE PICTURES

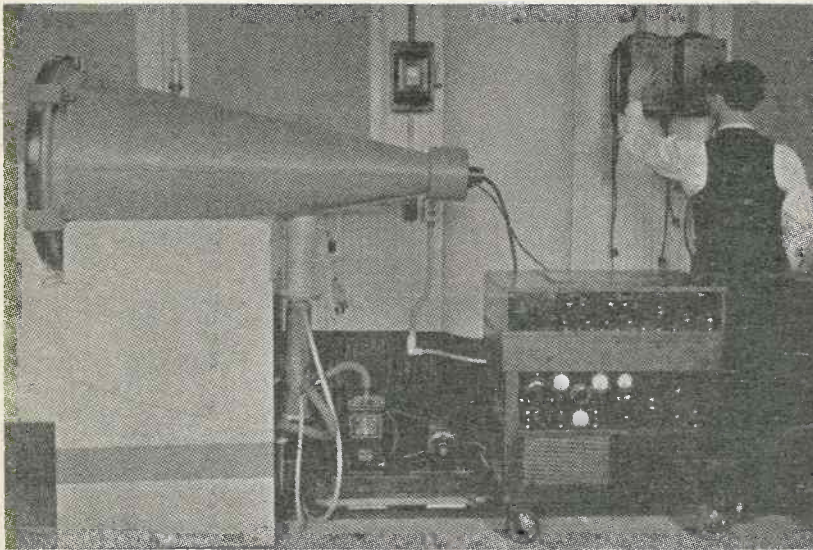


Fig. 2. Side view of tube 4½ ft. long and constructed of steel and plate glass.

MANY solutions to the problem of obtaining large television images have been proposed and several methods have been extensively explored, including projection by cathode-ray tube and also mechanical-optical methods.

An entirely new device for obtaining large bright television images of high contrast and high definition, however, has been developed at the Camden Laboratories of the R.C.A. Manufacturing Company (U.S.A.). It consists of a direct-viewing cathode-ray tube 4½ ft. long and 31 in. in diameter. It is of the continuously evacuated type and gives a picture 18 in. by 24 in. in size. The tube was built with the primary purpose of studying television pictures of large size under conditions where brightness, contrast, and definition were adequate and where the method of reproduction did not limit the performance of the system.

Increase of Light

The most important consideration in favour of the large direct-viewing cathode-ray tube is that the total amount of light obtainable from a luminescent screen is directly proportional to the area of the screen. At present the most widely used luminescent materials for screens in cathode-ray tubes are zinc orthosilicate (willemite) and zinc sulphide. Both materials exhibit the property known as "current saturation." A current-

saturation curve of a yellow willemite screen, bombarded by 10,000-volt electrons in a developmental projection tube, is shown in Fig. 1.

Measurements show that under the conditions of normal television scanning this saturation is a function of the area of the scanning spot and not of the total scanned area. But the area of the scanning spot is necessarily a function of the total area, if

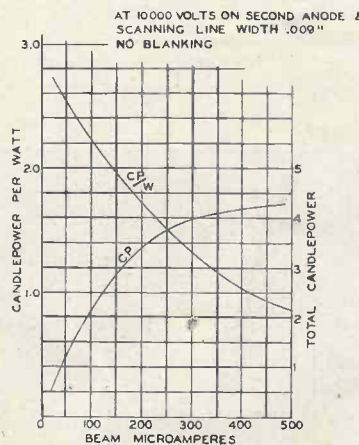


Fig. 1. Current saturation curve of yellow willemite in 3-in. tube.

the detail of the picture is to be preserved; i.e., it cannot be larger than a certain fraction of the total area

Please mention "Television and Short-wave World" when corresponding with advertisers.

DETAILS OF THE WORLD'S LARGEST CATHODE-RAY TUBE

As mentioned last month, a cathode-ray tube has been developed by The R.C.A. Manufacturing Company which has a screen diameter of 31 inches. This article describes its construction.

scanned. In actual practice, since the luminous spot is round, a certain overlap of the scanning lines is permissible. As a limit, after which a serious loss of detail takes place, 50 per cent. overlap may be taken. The present tentative standard calls for 441 lines per frame (American standard), about 10 per cent. of which are blanked out during vertical synchronising time. The observed picture, therefore, consists of 400 horizontal lines. Allowing 50 per cent. overlap, this calls for the line width of one-half of one per cent. of the height of the reproduced picture as the limiting maximum line width.

It may be deduced from the curves of Fig. 1 that at 10,000 volts the maximum useful brightness of this particular type of luminescent screen is 0.7 candle power per sq. ft. The maximum useful beam current (while it is on) is 58 μ a. per sq. in., but when the average power over a period of one complete white frame is considered, it is only 0.80 of the product of volts and amperes (max.).

The factor of 0.80 is introduced because in actual operation the electron beam scans a given picture area for only 80 per cent. of the time since 20 per cent. of the time it is extinguished for the line and frame returns or fly-backs.

Picture Brightness

As to the minimum required brightness of the screen, opinions vary greatly. As a measure, the brightness of a motion-picture screen is often used. A committee of the Society of Motion Picture Engineers concludes that the high-lights of the picture should have at least 11-foot lamberts or 3.5 candles per sq. ft. if

eye fatigue is to be completely avoided. The recommendation, however, is that 0.86 to 1.05 candles per sq. ft. be adopted as a temporary standard. There is very good reason to believe that a television picture should have more light than that.

The reason for low screen brightness being satisfactory for motion-picture theatres is that there is practically no stray light and the size of the image is very large. The theatre hall is devoted to the showing of pictures and everybody there is looking at the picture. The television receiver is placed in a room which is used for other purposes. It may be the living room of a residence, hotel lobby, or a restaurant. To be of maximum usefulness, a television receiver should not interfere with any other functions of the room. The willemite screen by itself at 10,000 volts is capable of giving a surface brightness as high as 100 candles per sq. ft. or 314 foot-lamberts or apparent foot-candles. For a screen 18 in. by 24 in. it would require 25 mA. at 10,000 volts. For the previously mentioned figure of 40 c.p. per sq. ft., only 6 mA. at 10,000 volts are required. The lower the current density of the luminous spot, the higher is the screen efficiency. At 2 mA. and 10,000 volts a directly bombarded luminescent willemite screen of the type described will have a brilliancy of 14.6 c.p. per sq. ft., or 46 ft. lamberts, which is nine times the upper brightness limit of the tentative S.M.P.E. standard.

Air Pressure of 5½ tons

Last year the construction of a direct-viewing tube with screen 18 in. by 24 in. was completed at the Camden Laboratory of the R.C.A. Manufacturing Co., Inc. The tube is of the demountable continuously-evacuated type and has a metal envelope with a Pyrex sight glass. Fig. 2 shows a side view of this tube. The envelope is made of good grade steel ¼ in. thick with arc-welded seams and flanges. It has the shape of a cone, and is 4.5 ft. in length. The outside diameter of the large flange is 31 inches.

A three-stage oil-diffusion pump is directly connected to the tube through a special outlet. For fore-vacuum, a mechanical vacuum pump is connected to the diffusion pump by means of a length of rubber hose. The glass cover is convex outwards, 31 in. in diameter and, 2 in. thick.

This thickness is necessary because the total atmospheric pressure on the glass is approximately 5½ tons. A special machine was constructed for grinding and polishing both surfaces of the glass. The technique used was that of grinding telescope lenses.

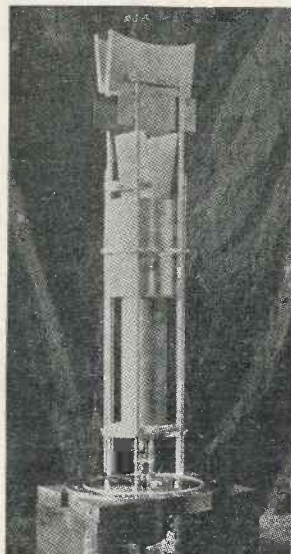


Fig. 3. The electrode assembly of the tube.

For vacuum-tight joints between the glass and metal as well as between metal flanges, pure gum rubber gaskets proved very satisfactory. The performance of the tube is quite satisfactory when vacuum of the order of 10-6 mm. Hg. is reached. Normally such a vacuum is reached after 48 hours of operation. The vacuum measurements are made by means of thermocouple and ionisation gauges attached to the sleeve

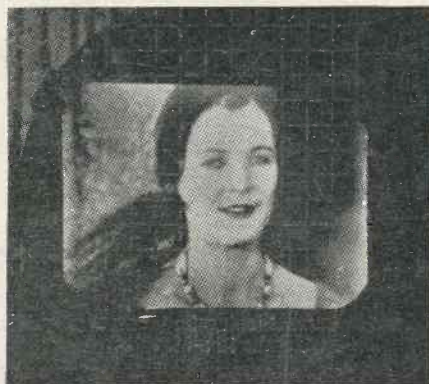


Fig. 4. An untouched photograph of a typical picture obtained on the tube.

connecting the vessel and the diffusion pump.

The tube was designed for 10,000 volts on the second anode. For safety reasons, instead of operating

the metal envelope at 10,000 volts positive, it is grounded and the cathode is raised to the same voltage, but negative. This arrangement greatly facilitates the construction of the electron gun. The electron gun used in this tube is shown by Fig. 3. It gave beam currents as high as 8 mA. at 10,000 volts with corresponding brilliancy of the high-lights. However, the best overall performance was obtained with a gun giving 2 mA. in a narrow beam with negligible focusing and with 150 volts cut-off grid voltage.

The design of the power supply and video amplifier for the demountable tube offered many difficulties. The cathodes in the last stages of the video amplifier had to be operated at minus 10,000 volts, and, of course, had to be capacity-coupled somewhere along the chain to the low-voltage stages. The two coupling condensers during the operation are charged to 10,000 volts and at the same time are required to pass low video frequency currents. All the meters and controls on the last stages of the amplifier had to be insulated for 10,000 volt. A view of the portable outfit containing the video amplifier, synchronising and deflecting circuits, and high and low-voltage supply, is shown on the right-hand side of Fig. 2.

A typical received picture is shown in Fig. 4. The signal was taken from an Iconoscope pick-up of a regular moving picture frame. The photograph has not been retouched. It will be noted from the photograph that the sides of the image are straight and there is no apparent bulging of the image. The reason for this effect is that the 2 in. thick glass disc is used only as a vacuum cover or a sight glass while the luminescent material is deposited on a flat glass sheet ¾ mm. thick, which is fastened to the walls of the tube. The flat appearance of this type of luminescent screen is not its only advantage. The fact that it is flat greatly improves the overall contrast of the reproduced picture. On a concave screen, illuminated parts throw light directly on the blacks of the image, thereby reducing the contrast. The fact that the screen is thin improves the contrast in details by reducing the well-known "halation" or "the spurious ring" effect.

In conclusion, it may be stated that with the tube described, large, bright television images of high detail and of high contrast are obtainable.

THE SIMPLEST HOME-BUILT TELEVISOR

Designed by S. West

PART III. LAYOUT DIAGRAMS OF THE TIME BASE AND CONSTRUCTIONAL DETAILS OF THE POWER PACKS

This article concludes the instructions for building the simplest television receiver yet designed. The two previous instalments dealt with the vision receiver and time base and in the following pages the construction of the power packs are described in detail.

IN the two preceding articles of this series, comprehensive instructions for building the vision and time base units of this simple television receiver were given.

In conclusion of the constructional details it now remains to consider the power pack. This section of the receiver is contained on the bottom deck of the complete television as shown by the photograph below.

The arrangement employed actually consists of two separate power packs. One furnishes some 250 volts for the vision unit and the other approximately 1,200 volts for tube excitation and, by dissipating the excess voltage across a resistance, some 500 volts for the time base.

The circuits are quite conventional and thus will require little description.

Vision Unit

Power Pack

Dealing first with the vision unit power pack, this is comprised by the transformer T₂, the condensers C₃₇, C₃₈ and C₃₉, and the two Varley smoothing chokes.

These are the type DP11 and their terminals are connected, according to the maker's instructions, for the series arrangement. The mains transformer, which is of Sound Sales' manufacture, has a tapped primary.


A Clix voltage selector board with fused bridge permits this primary to be adjusted to suit A.C. mains having voltages from 200-250. No additional fuse is included elsewhere for this power unit and, in view of the desirability of providing some form of safety device, it is important to specify the fused bridge type of selector board when ordering this component.

The reservoir condenser C₃₉ and the smoothing condenser C₃₈ are contained in the same "can." It is immaterial which section is used for either function.

C₃₇ is a cardboard type electrolytic and it is convenient to mount this beneath the

deck. A simple fixing bracket is entirely satisfactory.

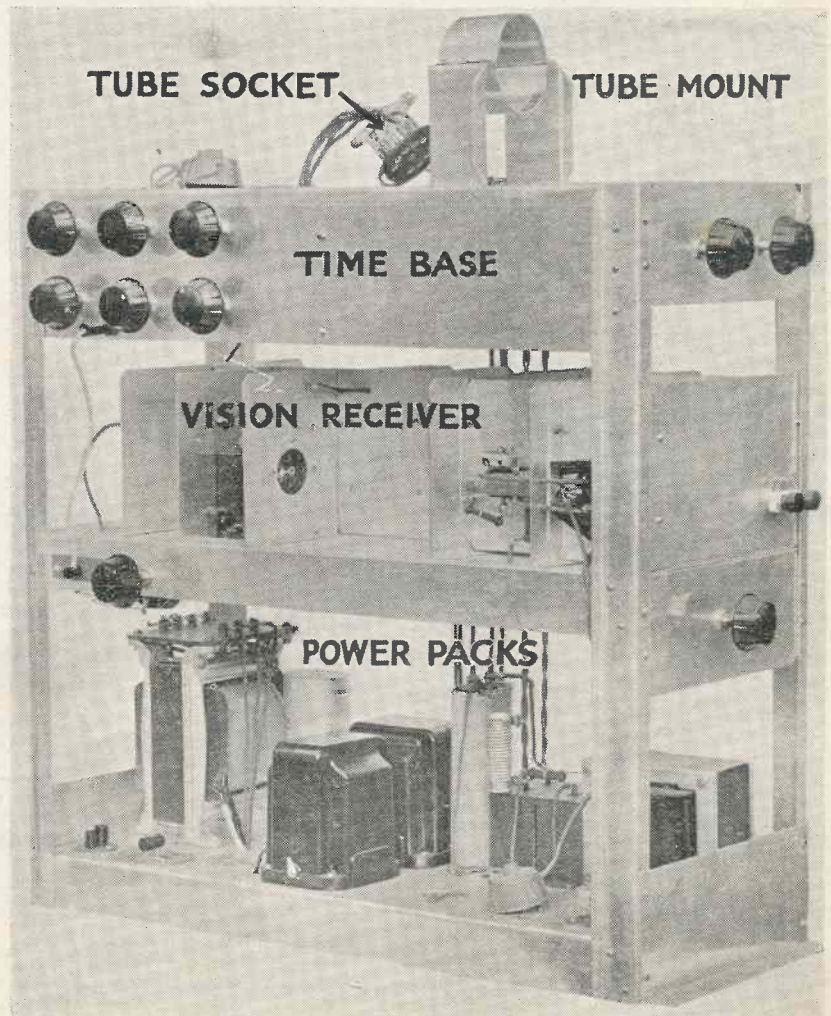An indirectly heated full-wave rectifying valve is employed, for this affords an opportunity for the various valves of the vision unit to acquire their normal operating temperature before application of the maximum high-tension voltage.



Here is a photograph of the complete televisior with the various units indicated.

WIRING DIAGRAM OF TIME BASE

The heater and high tension voltage outputs are taken to a Bryce 10-way connecting block which is mounted at the side of the chassis.

Tube and Time Base Power Pack

For the time base and the C.R. tube exciter voltage a half-wave mercury-vapour type rectifier is employed. The C.R. tube is operated with an earthed cathode; in consequence it is convenient to derive the time base power from the C.R. tube exciter voltage.

A potential between 1,100 and 1,200 volts is provided by the unit. As we require a little over 500 volts only for correct time base operation, the excess 600 volts is dropped across a 50,000-ohm Bulgin type PR17 power resistance.

It is strongly recommended that this type of resistance be employed as the power dissipation is approximately 8 watts.

A Dubilier 50,000-ohm resistance is included in series with the C.R. tube exciter voltage and this fulfils a dual purpose. It provides sufficient smoothing of the


tube voltage and in the event of a breakdown will restrict the rectified current flow to proportions within the rectifying valve rating. Actually this resistance together with its associated condenser is included on the time base deck.

The frame and line bases' supplies are decoupled from each other. The resistance R45, which has a value of 10,000 ohms, in conjunction with the 2 mfd. Dubilier type LEG condenser, satisfying this requirement.

A vacuum type thermal-delay switch, included in the high-voltage secondary, delays application of the high voltage until all the heaters have acquired operating temperature.

The mains transformer is a Keston. A separate voltage selector board is used to permit adjustment of the primary tapings and, as in the case of the vision unit power pack, a fused bridge is specified. Both circuits are then separately safeguarded in the event of a breakdown or short circuit occurring.

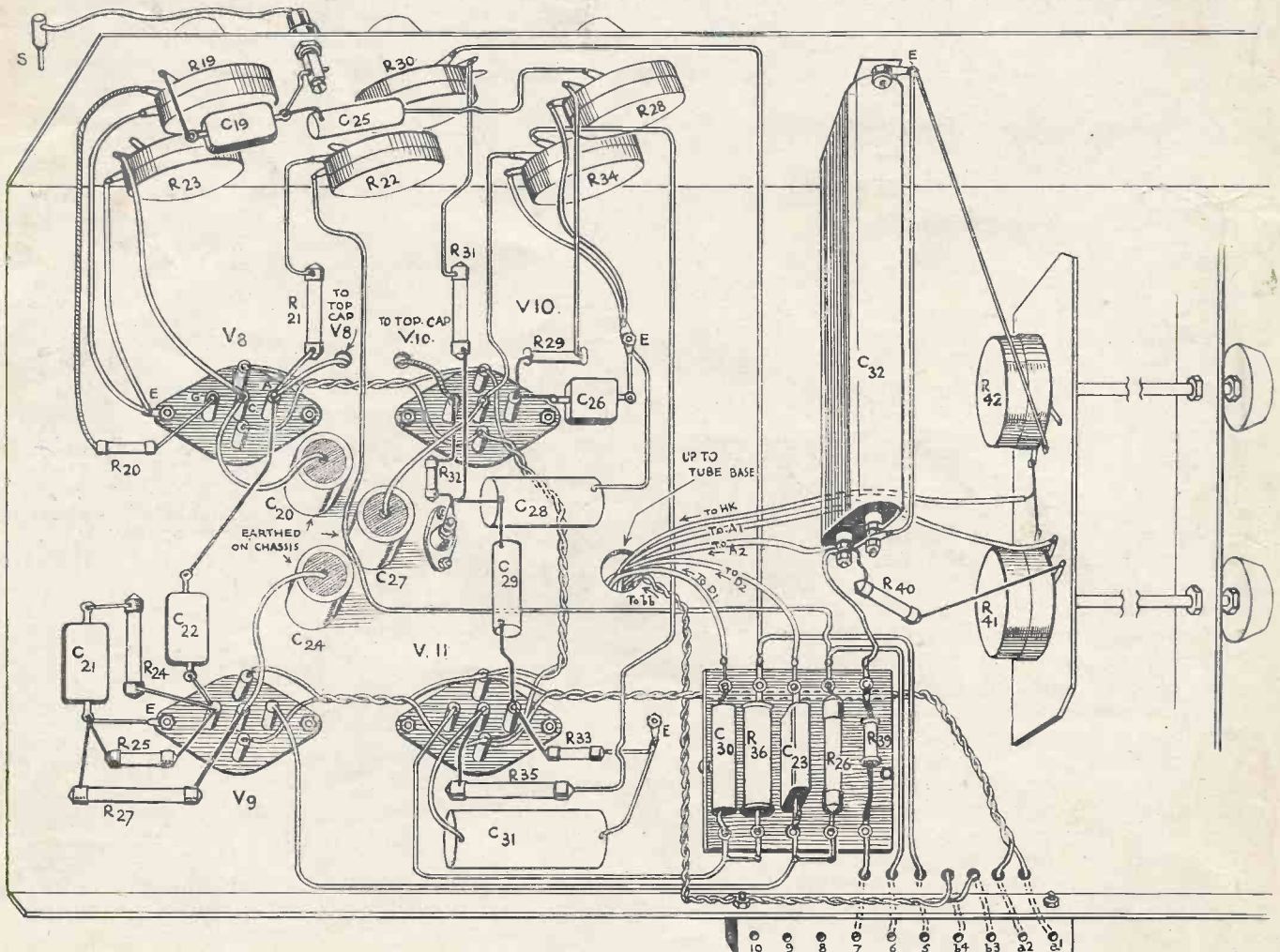The various heater and H.T. voltages furnished by this unit are taken to the Bryce 10-way connecting block. A point concerning this connecting block has



This diagram gives the details of the component assembly and wiring of the underside of the time base. The constructional information was given in last month's issue.


THE POWER PACKS

already been mentioned but it is again repeated here. It is preferable to adhere to the same order of connection as is adopted for the original receiver. The various sockets for the complete assembly will then be correctly juxtaposed, facilitating connection and making for a neat appearance.

It is convenient to carry out the wiring in tinned

already been given. A study of the various illustrations will render the task of construction simple.

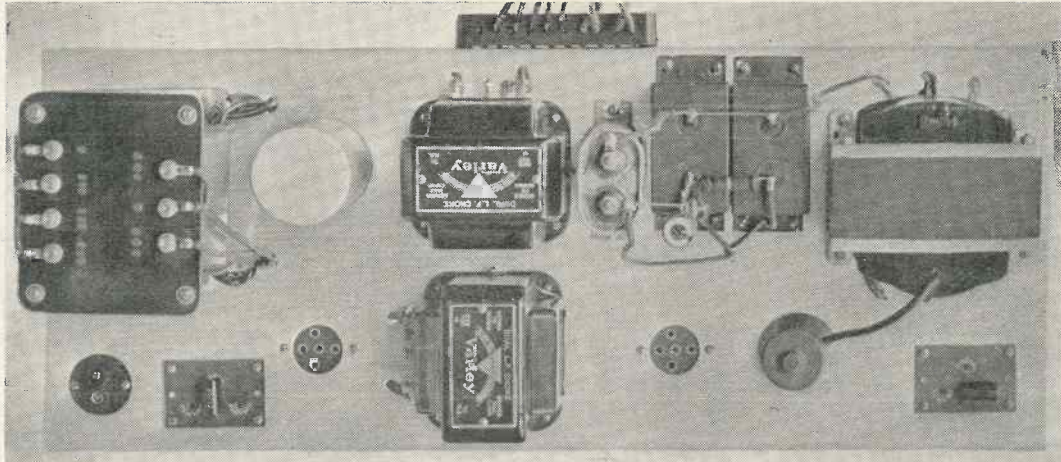It is proposed at this juncture to consider the final assembly of the complete receiver. Unless very special reasons for departing from the original layout exist, it is strongly recommended that this arrangement be adhered to.



A photograph of the upper side of the power packs, from which the component assembly can be clearly seen.


copper, insulated with systoflex; or commercial slide-back wire can be used.

The usual precautions with leads carrying the full H.T. voltage must be observed; also the possibility of heater voltage drop due to employment of insufficiently heavy wire, for these leads requires to be borne in mind.

The external chassis dimensions for the unit have

The whole comprises, when completed, a compact and efficient receiver.

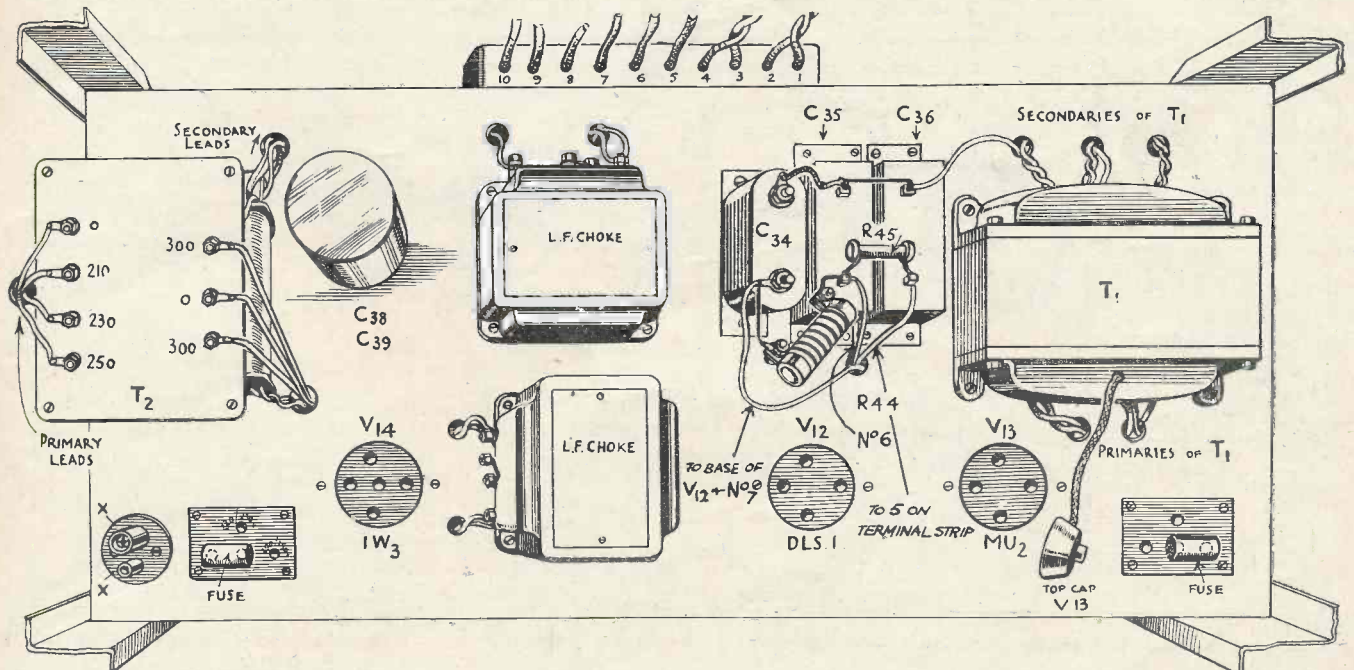It will be seen from the various photographs which have been given, that metal uprights at each corner hold the three units in their correct relative positions. Two 6 B.A. bolts at each corner of the units are sufficient and ensure adequate rigidity.



This diagram, which shows the components and wiring on the upper side of the power packs, should be studied in conjunction with the photograph above.

AN AERIAL FOR LONG-DISTANCE TELEVISION

By S. West.

Here are particulars of a special type of aerial with which excellent vision reception is being consistently obtained at a distance of ninety-seven miles from the Alexandra Palace. Although it is rather more elaborate than the ordinary dipole, its construction is quite as simple.

IT does not appear to be generally appreciated that by reason of the very short wavelengths employed for television transmission quite elaborate aerial arrays are possible even where space is limited.

The writer has observed that even where the receiving station is located at a considerable distance from the transmitter, it is general to find a simple vertical half-wave aerial with reflector comprising, what is, with-


100-mile Reception

During the last three months, the writer has conducted a large number of tests with different aerial arrangements at Worlingham, which is near Beccles in Suffolk, and a distance of about 100 miles from Alexandra Palace. This work is being continued and at a later date it is hoped to give a very full report of the various types

tion, though, is usually a genuine error, and the writer has himself been guilty of it. It arises from the result of confusing road and rail distance to the centre of London with the actual direct distance to Alexandra Palace, which is situated in the north of London.

Below is a fairly accurate indication of the direct distance from Alexandra Palace of several major towns.

- Nottingham, 104 miles.
- Bournemouth, 101.
- Gloucester, 98.
- Birmingham, 98.
- Norwich, 95.
- Beccles, 95.
- Salisbury, 83.
- Kings Lynn, 82.
- Rugby, 74.
- Portsmouth, 70.
- Felixstowe, 68.
- Winchester, 66.
- Ipswich, 65.
- Eastbourne, 61.
- St. Leonards & Hastings, 60.
- Canterbury, 59.
- Frinton & Walton, 62.
- Northampton, 58.
- Clacton, 57.
- Bury St. Edmunds, 57.
- Oxford, 52.
- Colchester, 49.
- Cambridge, 43.
- Brighton, 54.
- Bedford, 41.

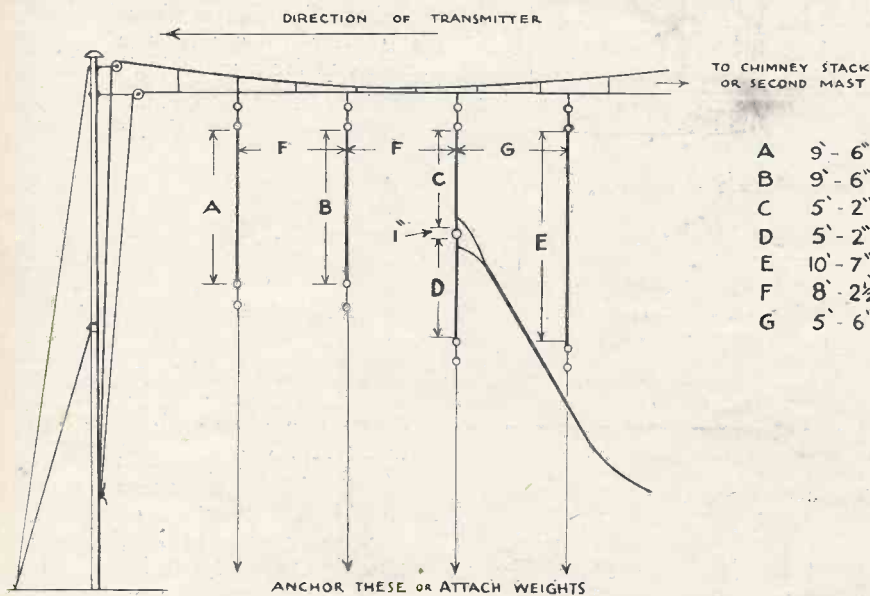

This diagram shows the detailed assembly of the aerial which is provided with reflector and two directors.

out doubt, a most important essential of the receiving outfit.

Whilst it must be admitted there is much to be said for the ease with which these simple aerials may be installed, it is by no means an arduous task to install an arrangement which has a definitely higher efficiency than the conventional arrangement and which, because of this, will mitigate to a large extent the low field strength. Furthermore, there is a considerable improvement in the signal/noise ratio than is accounted for only by the higher gain of the aerial.

of aerial tested, together with measurement data, etc.

In the meantime it is thought that particulars of an aerial which is simple to instal and is capable of providing excellent results at long distances will prove useful.

Elsewhere in this issue, photographs of actual received images are reproduced. Most of these were secured using the simple arrangement here described. (Cover illustration.)

A certain amount of exaggeration is often made in reports of long-distance reception. The exaggera-

AN END-FED ARRANGEMENT

The Aerial Construction

A diagram of the aerial earlier referred to is shown. It consists of a vertical half-wave wire with reflector and two directors. This arrangement is quite directional and it is advisable accurately to determine the correct direction in which it should be oriented. Guess work to determine the correct line is to be deprecated. It is preferable, with the aid of an ordnance survey map, parallel rulers and a good compass, to decide the correct line for the aerial. In this connection observe the correction which is included on the map for the compass bearing.

It will be seen from the diagram that two horizontal rope supports are used to carry the various aerial elements. If this scheme is not adopted it will prove impossible to keep the actual aerial support rope taut and as a consequence considerable trouble will result in arranging the correct relative heights of the aerial elements.


For the halyards and aerial supports tarred ratline should be employed. Ordinary untreated ratline shrinks considerably in wet weather and some part of the arrangement is certain to break under the strain thus caused.

For the aerial elements No. 10 s.w.g. enamelled copper wire can be used.

An End-fed Aerial

An alternative end-fed arrangement of the actual aerial element is given. In many cases this arrangement will prove more satisfactory, especially for cases where the aerial line as related to the point where the lead is to be taken into the dwelling is such as to cause this lead to run adjacent to either the reflector or directors.

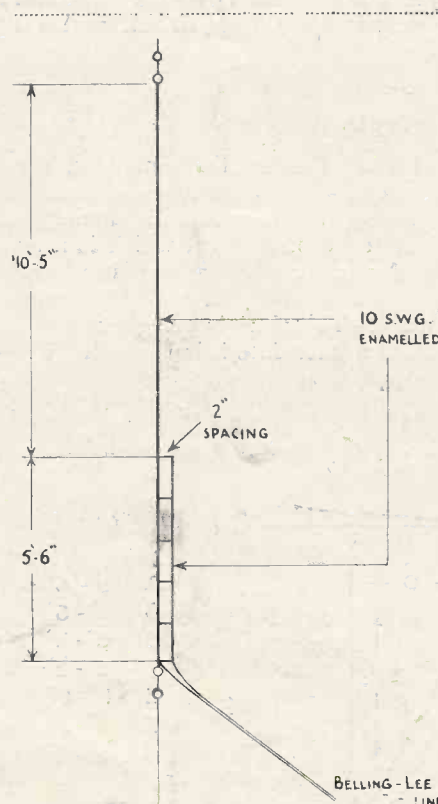The quarter-wave matching section is a conventional arrangement and is comprised of No. 10 s.w.g. copper wire spaced 2 in. Should it prove difficult to secure this gauge



If it is desired to end-feed the aerial C and D (shown in the assembly diagram) may be constructed as above.

of wire a correct match can be obtained using the following formula.

The series impedance required for the matching section is given by the formula $Z = \sqrt{Z_1 \times Z_2}$, where Z is the required matching impedance, Z_1 is the characteristic impedance of the feed line and Z_2 is the aerial impedance.

For a half-wave aerial Z_2 is approximately 2,400 ohms. Using Belling-Lee 75-ohm line $Z = \sqrt{75 \times 2,400} = 425$ ohms approximately. The required wire size and spacing to give this impedance is derived with the following formula:

$$Z = 277 \log_{10} \frac{S}{R}$$

where S = wire spacing and R = radius of the wire.

It is immaterial whether S and R are in inches or m/ms. providing the same unit of measurement is employed for each.

Converting into a form more suitable for our purpose. $S = R$ antilog $\frac{425}{277}$ where S and R are as above.

The following table shows the radius of typical wires. This table and the above formula renders it a simple matter to secure the spacing dimensions for a matching section.

s.w.g.	Radius in ins.
7	.176
8	.160
9	.144
10	.128
12	.104
14	.080
16	.064
18	.048

It is, of course, very desirable to erect the aerial as high as possible and to avoid as far as possible having trees or buildings in line with the transmitter. A little care in choosing the aerial site is amply repaid by the improved performance secured.

The loss occurring in the feeder line is always likely to be less than the improved gain from the aerial where a good position for the installation is located at some distance from the receiver. Therefore, in general, choose the most uninterrupted position for the aerial regardless of feeder length.

B.B.C. Handbook for 1938

THE B.B.C. Handbook for 1938 records the most notable events and developments in the fifteenth year of the British broadcasting service and contains a great deal of standard and up-to-date information about the B.B.C. There are chapters on the Coronation broadcasts, on television, and the new foreign language broadcasts.

The year 1937 was the year of the

new Charter, of thoroughly organised television, of the first broadcasts in foreign languages, of the most extensive experiments yet made in listener research and of substantial increase in the network of Regional transmitters.

There were, it is revealed, over 100,000 hours of broadcasting from the home transmitters, a figure which includes 23,779 hours of Empire broadcasting and 1,619 hours of

television. The aggregate for 1936 was in the region of 87,000 hours.

The handbook contains licence figures and the revenue account and balance sheet for the past year, besides advice on good reception and maintenance of sets. Its price is 1s. 6d. or 1s. 10d. by post, and applications should be addressed to the B.B.C. Publications Department, 35 Marylebone High Street, London, W.1.

A CROWD ALWAYS ASSEMBLES TO WITNESS DEMONSTRATIONS ON BAIRD RECEIVERS.

WHY?

BECAUSE EACH MODEL IN THE RANGE REPRESENTS THE HIGH WATER-MARK OF ACHIEVEMENT.

Among the factors contributing to the first-class performance of all Baird Television receivers are brilliant pictures, freedom from distortion, excellent detail, wide angle of vision, extremely simple operation, high fidelity sound and all-wave radio. Each television receiver incorporates a Baird "Cathovisor" Cathode Ray Tube which has the outstanding advantage of being completely electro-magnetic in operation. These tubes can be supplied separately with the necessary scan-



A small section of the daily crowd which assembled at a recent exhibition to see demonstrations on Baird receivers.

ning equipment where desired. Apart from manufacturing processes, stringent tests are made for electrical emission, tube characteristics, filament rating, and screen quality, and following normal picture reconstitution under service conditions, every Baird Cathode Ray Tube, on completion, is subjected to a very high external pressure test. Baird "Cathovisor" Cathode Ray Tubes are the ideal solution for high quality television pictures. Write for details.



STOP PRESS NEWS

Model T11 Television Receiver complete with All-Wave Radio has been reduced to 55 guineas. Send for full details at once, post free on request. Price includes aerial, installation and one year's free service.

BAIRD TELEVISION LTD.

Lower Sydenham, London, S.E.26

Telephone: HITHER GREEN 4600.


Telegrams: TELEVISOR, FOREST, LONDON.

G.E.C.

CATHODE RAY MONITOR TUBE

TYPE 4051

Made in England

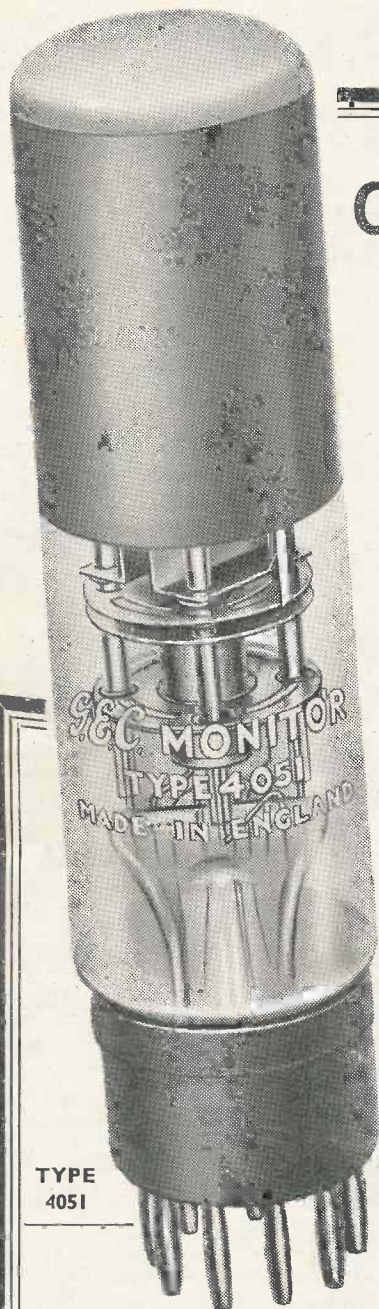

TYPE
4051

This new tube is ideal for all purposes requiring a small, economical low-voltage cathode-ray tube. It offers the following advantages :

1. Small size (overall length about 6 inches only).
2. Low operating voltages. (The tube will operate down to 250 volts.)
3. Separate connections for the four deflector plates (allowing push-pull scan, if desired):
4. Fine focused spot, bright even down to 250 anode volts.

RATING

Heater Voltage	4.0 v.
Heater Current	0.9 amp.
Accelerator Voltage (A ₂)	250-500 max.
Focusing Electrode (A ₁)	50 to 100
Modulating Electrode	0 to -20
British 9-pin base	

LIST PRICE 45/-

For all purposes requiring a rapid test on waveform, frequency measurement, modulation check, determination of amplitude of any variable quantity, etc.

NOTE

New high slope tetrode

OSRAM KTZ41

suitable for oscillograph and Television amplifiers.

CHARACTERISTICS

Heater Voltage	4.0 volts.
Heater Current	1.5 amp.
Anode Voltage	250 max.
Screen Voltage	250 max.
Mutual conductance	7.5 mA/volt
	(measured at Ea-250, Es-250, Eg-2.5).

ALSO


OSRAM Gasfilled Relay GTIC for time base circuit.

This Argon filled relay is ideal for oscillograph time base circuits.

Heater Voltage	4.0 volts minimum
Heater Current	1.3 amp. approx.
Maximum Safe Anode Voltage	500 volts (peak value)
Maximum Safe Anode Current	1.0 amp. (peak value)
	0.5 (R.M.S. value)
	0.3 amp. (average value measured on a moving coil meter).

PRICE 15/- EACH

PRICE £1 5s. 0d. EACH

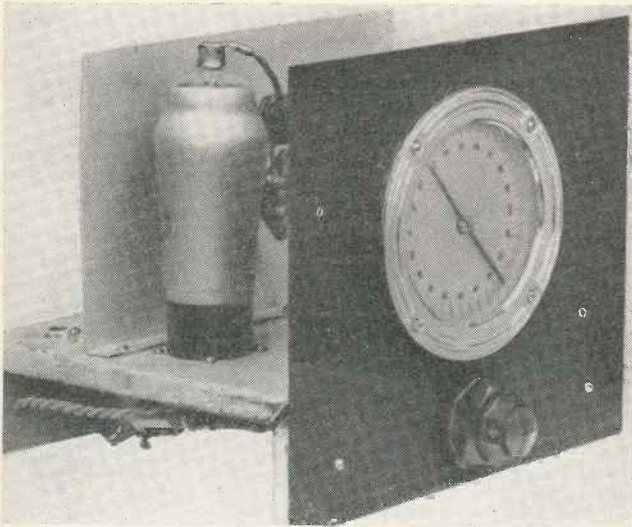

TELEVISION SOUND PROGRAMMES ON YOUR BROADCAST SET

This simple unit can be attached to any broadcast set and will enable the television sound programmes to be heard. It will be found useful in conjunction with vision receivers which have no provision for sound. The cost is very low.

This photograph shows the simple construction of the unit. As will be seen only one valve is employed.

As many of the items included in television broadcasts are of a type that can be appreciated by listeners who cannot obtain the vision side, it is a great advantage to be able in a simple manner to adapt an ordinary broadcast receiver to tune-in these programmes from Alexandra Palace.

In particular programmes such as the transmission of famous dance orchestras and solo artists are of a novel type and quite different from the broadcasts normally obtained on Regional and National wavelengths. Some of the plays are also very interesting, and include famous artists whose names are not always familiar to those who rely solely on the Regional and National programmes for their entertainment.

While many modern all-wave receivers will tune down to 7 metres, the number of people who have purchased such sets is still comparatively small, while it is not to be expected that the average listener will dispense with a perfectly good receiver having only one disadvantage that it does not cover television frequencies.

It is for these listeners that we have produced a very simple super-het convertor for use with any ordinary receiver with a minimum of modification; in fact, no actual wiring alterations have to be made to the receiver.

The circuit of this simple convertor is shown on this page, from which it can be seen that it consists of a multiple valve, one section acting as a hexode detector with the triode portion as a conventional Hartley oscillator. By using this system, the

difficulties which amateurs invariably come up against in convertor design have been overcome, for the oscillator is electronically coupled to the detector by means of the electron stream flowing. Actually, the grid of the triode section is connected directly to the suppressor grid internally.


This system is a most satisfactory one, for it automatically gives the correct amount of coupling, which can never be accurately determined on paper when an inductive coupling

circuit is used with a second coil in the oscillator circuit.

For all intents and purposes, the convertor can be considered as a two-valver with both valves in one common bulb.

Refer to this theoretical circuit. It will be seen that provision has been made for a dipole aerial which is loosely coupled to the grid coil in the detector circuit. This grid coil is centre-tapped so as to reduce the damping effect, so causing greatly

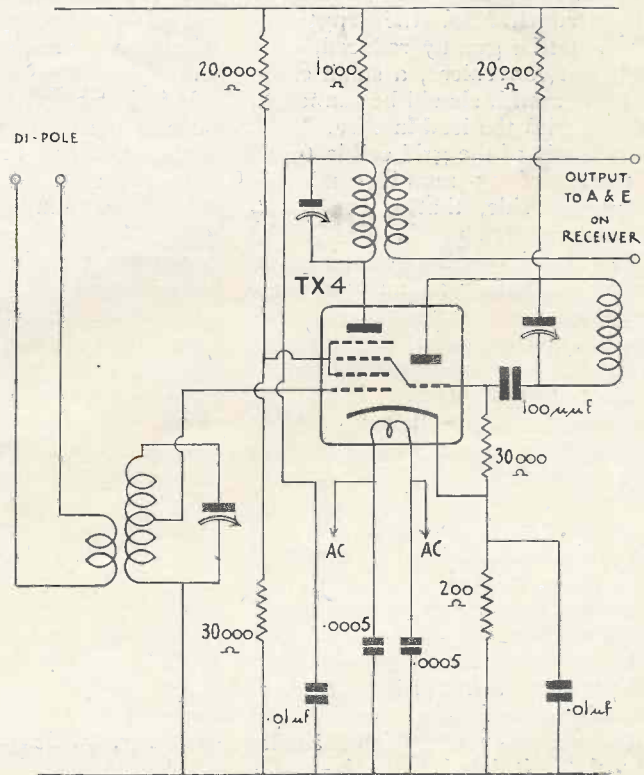Triode hexode is used as a combined detector and oscillator in Hartley circuit. Provision is made for the use of a dipole aerial




decreased amplification, and the possibility of lack of oscillation.

Should an ordinary Marconi aerial with earth connection be used, then the lower side of the aerial coupling coil is connected directly to earth with the aerial connected to the free side. This arrangement, however, causes heavy damping, and even the centre-


dividing screen by means of ebonite bushes. The grid condenser, which has a capacity of .0001 mfd., has one side connected directly to the oscillator condenser, and the other side directly to the grid of the triode section of the TX4.

In the anode of the circuit of the TX4 is the conventional I.F. trans-

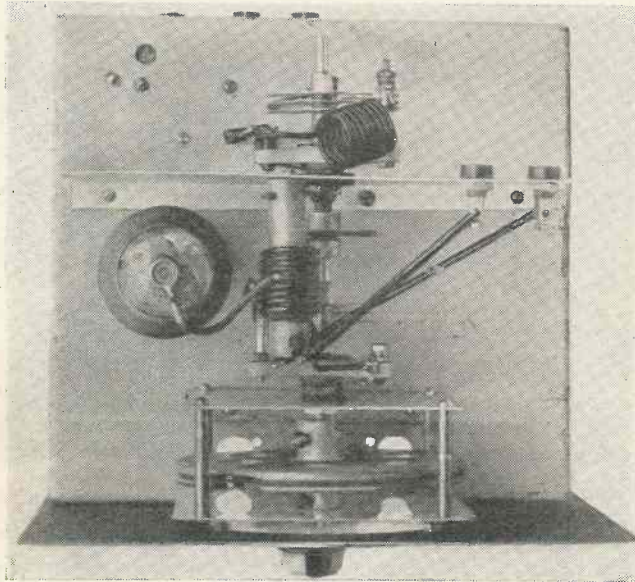Connecting the unit to the parent receiver is quite a simple matter. The di-pole aerial on the main receiver is connected to the di-pole terminals on the convertor, and these can be seen actually mounted on a dividing screen between oscillator and detector sections. The secondary of the output transformer in the con-



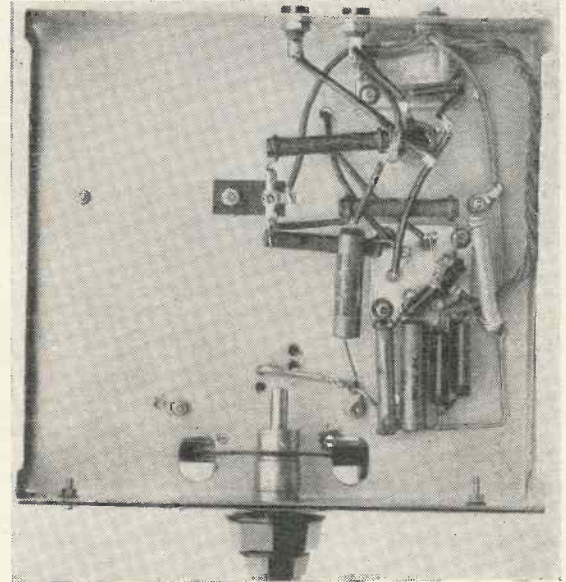This picture shows plan view from which it will be clear that the component assembly is of the simplest



An underside view of the chassis showing the simple wiring.

tapped grid coil may not take care of the additional load, so causing the convertor to go out of oscillation. In such circumstances, the length of aerial must be greatly reduced, or if this is not convenient, a small capacity of 50 mmfd. should be connected in series with the lead-in wire.

The whole of the grid coil is tuned by means of 15 mmfd. condenser having one side, that is the rotor-plates, connected to chassis. The grid coil and coupling winding are mounted in rather an unusual way. It will be seen that the coupling coil is wound on a small half-inch paxolin former which is bolted to the dividing screen. The grid coil is wound around this former, but spaced off it approximately $\frac{1}{4}$ in., and held in place by means of the heavy gauge-connecting wires to the rotor and stator plates of the parallel condenser. This coil consists of 8 complete turns of 1 in. diameter, with the centre tap taken directly to the top of the TX4 valve.

The single oscillator coil, made up of 8 complete turns, 1 in. diameter, is soldered directly across the oscillator condenser which has its rotor plates isolated from the metal

former, having the primary tune by means of a small pre-set condenser. This can be adjusted by means of a screwdriver through the chassis, and should be arranged so that the primary is absolutely balanced.

It is important to notice that both sides of the heaters are by-passed to earth by means of .0005 mfd. condensers. This is to prevent possible modulation hum, which can be very noticeable in a convertor of this kind when used in conjunction with a high-gain receiver.

Assuming that the supply voltage from the main receiver will be approximately 230, the resistances recommended will be of the correct value. The most important resistors are those forming the fixed potential divider in the screen circuit of the TX4. In the high potential side the resistors have a value of 20,000, and in the low potential side, 30,000 ohms.

In the coupling circuit there is a resistor of 1,000 ohms, and in the oscillator anode circuit, a resistor of 20,000 ohms. A very important resistor is in the grid circuit of the oscillator, which has a value of 30,000 ohms.

vertor is then connected to the aerial and earth terminals on the main receiver, and it is immaterial which way round these wires are connected. The only point which might mystify constructors is the method of obtaining the power supply from the receiver.

First, obtain a valve socket to suit any valve in the main receiver, providing it has two external contacts to the heaters. These two terminals are then connected to two leads from the valve heater in the convertor. In that way the main receiver furnishes the heater voltage for the convertor valve.

This leaves two further leads for the high-tension supply. One is negative, the black lead, and is connected to the chassis of the main receiver, or to the earth terminal. The second lead, the red one, is for H.T. positive, and this should be joined to any high-voltage point on the main receiver. For example, the high-voltage side of the loudspeaker transformer will do excellently, and as this transformer is usually accessible, contact can be made by means of a crocodile clip.

(Continued on page 279)

Scannings and Reflections



A LONG-DISTANCE O.B.

AFTER the television broadcast of the Head of the River Race a telegram was received at Alexandra Palace from an Eastbourne viewer announcing reception of the broadcast. The receiver used for this was a standard Baird model, and it is claimed that this is the longest distance over which clear transmission of an outside broadcast has been reported. The B.B.C. felt this of sufficient importance to include it in their Saturday News Bulletin.

VETERAN CARS IN TELEVISION

A gymkhana for old cars, specially staged for television by the Veteran Car Club, will be seen by viewers on May 15, when more than thirty cars, dating from 1896 to 1904, will be drawn up on the Polo Ground at Hurlingham. The television cameras will show such events as Pig Sticking, with balloons as "pigs"; an Obstacle Race, and "Musical Chairs" in which the drivers have to stop and start with a rapidity which sorely tests these ancient vehicles.

Members of the Veteran Car Club own between them more than 145 of these old-timers and it is interesting to note that the term "veteran" is applied to cars made between November 15, 1894, and December 31, 1904. The first date marked the opening of a new era when it was no longer necessary for a car to be preceded by a man carrying a red flag, and the last date marked the end of the 12-miles-an-hour limit. On January 1, 1905, cars were permitted to travel on the roads at twenty miles an hour.

Viewers will see a Benz of 1898 owned by Mr. G. J. Allday, chairman of the Club, and an Arnold motor carriage of 1896 owned by Capt. E. de W. F. Colver. Other models will include a De Dion Bouton of 1900, a Mercedes, Lanchester and Humber, all dating from 1903, and a Clement-Talbot of 1904.

THE BOAT RACE TRANSMISSION

A workman excavating in a Muswell Hill Road almost caused a crisis

on the occasion of the boat-race transmission. Just before the transmission was due to commence he accidentally struck a telephone cable which completely cut-off Alexandra Palace from all outside communication. This meant that there could be no sound commentary accompanying the pictures of the race and it increased the difficulties of the camera operators at Mortlake because all communication had to be made by scribbled messages on paper which were held up before the camera and transmitted in picture form to Alexandra Palace.

TELEVISION AND FILMS

According to the *Era*, the B.B.C. have absolutely denied any intention of using their film unit at Alexandra Palace to make news reel or feature-films.

When asked if it were true that the unit had been formed to make television independent of film co-operation, Gerald Cock said that such a rumour was quite unjustified. "All we expect the unit to do," he added, "is to make short film sequences that we could use as aids to background in studio productions or in outside broadcasts."

Mr. Cock, the *Era* says, further revealed that the B.B.C. had approached the Kinema Renters' Society with a suggestion that a weekly feature should be televised dealing with current or next week's films in the West End cinemas, with illustrative excerpts from the actual films. This idea was turned down by the K.R.S.

"It was intended," Mr. Cock said, "to deal with the best of the films that would be on show at the principal theatres, and we believe that it would have created a new film public."

The opinion of the *Era* is that in declining this offer from the B.B.C. the renters were probably thinking along the same lines as the exhibitors, who are concerned at the competition to the cinemas from free television shows at public houses and clubs.

TELEVISION THE DERBY

The directors of the Epsom Grand Stand Association, Ltd., have decided to withdraw their embargo on the televising of the Derby. Sir Stephen Tallents, speaking on behalf of the B.B.C., when the decision was made known, said that it was most welcome and would, he felt sure, be appreciated by all viewers as warmly as it was by the B.B.C.

The televising of the Derby will open with pictures on the Downs and crowd scenes which should effectively convey the atmosphere of the most famous race meeting in the world.

Three television cameras will be used; one, a super-Emitron equipped with twelve-inch telephoto lens, will, it is hoped, give a view of the start of the race from the far side of the course. Good pictures should be obtained as the horses round Tattenham Corner and come into the finish. It is hoped to show the weighing-in and saddling, and viewers will see close-ups of the owner leading in the winning horse.

Tests already conducted on Epsom Downs have yielded excellent results and it is believed that viewers will see a large part of the race just as if they were watching it through binoculars.

M.P.'s TO VISIT ALEXANDRA PALACE

The Postmaster-General has been requested to arrange for Members of Parliament to visit Alexandra Palace and it is understood that the B.B.C. has agreed to this, but point out that it would only be possible to invite M.P.s in parties of ten owing to limitation of studio space. Invitations are therefore being issued in groups in alphabetical order.

"CHECKMATE"

"Checkmate," the Vic-Wells ballet, which was produced at the Paris Exhibition, will be televised from Alexandra Palace on May 8, with the augmented B.B.C. Television Orchestra. The music is by Arthur Bliss, the choreography by Ninette de Valois, and the costumes and scenery by McKnight Kauffer. More

MORE SCANNINGS

than thirty members of the Vic-Wells Company will be taking part and it is expected that the brilliant costumes of the "chessmen" in red and black will make an attractive picture on the television screen. The ballet will be preceded by a discussion by Arthur Bliss, Ninette de Valois and Mc-Knight Kauffer, who will talk about the construction of the ballet.

TELEVISION NEWS REEL

Officials of the Cinematograph Exhibitors' Association recently held a meeting with the chiefs of the Newsreels companies to discuss the broadcasting of newsreels. Complaints were made by the exhibitors regarding the broadcasting of newsreels, but it is understood that the chief concern was regarding the rediffusion of television programmes in public houses and other places open to the public.

TELEVISION OUTSIDE BROADCASTS

Viewers will be able to watch several important events this summer, for plans have been made for many outside broadcasts to take place which have been made possible mainly by the perfection of the television camera with a 12 in. telephoto lens.

The Chelsea Flower Show is to be televised on May 22, 23 and 24, when Freddie Grisewood and Elizabeth Cowell will be the commentators.

Another good relay will be that of Trooping the Colour on June 9—while the experience gained in televising the Derby will be put to good advantage by the relay of the Northolt Pony Derby on June 13. All viewers will look forward to the televising of test cricket from Lords and the Oval in June and August. In the final Test Match at the Oval, some of the day's play will be televised on four separate occasions.

One of the most successful of the outside broadcasts last year was that of the tennis from Wimbledon. This year, the finals will be televised with the aid of the outside broadcasting van. Those who have not been able to watch polo will have an opportunity during the relay from Hurlingham of the match between India and the rest of the world on July 4. There is also to be a relay from the Wembley Pool of the World Swimming Championships in August.

RADIO INTERFERENCE IN TELEVISION

It has been noticed that amateurs transmitting on the international 20-metre band are causing interference to television programmes. The third harmonic of the 20-metre signals comes in between the sound and vision frequencies, and owing to the flatness of tuning in the average television receiver considerable interference is often caused. This problem is one that will be hard to overcome, so at the present time, amateurs in certain parts of the country, such as Cambridge, have been requested to stop transmitting during the periods when viewers are using their television receivers.

SUN-SPOT EFFECTS

Although short-wave listeners expect unusual conditions this year on the short-waves, the sun-spot effects are causing considerable difficulty to amateurs who wish to maintain consistent communication in various parts of the world. Although it is generally agreed that conditions for reception are generally poor, there are periods when freak results occur. In one instance when it was impossible to maintain communication with local countries such as Norway, stations in Peru and Japan could be received at good strength. It has also been noticed that reception of stations in India, Ceylon and that part of the globe, is now better than it has been for some time, despite the fact that transmissions are rather erratic and are inclined to fade out at a moment's notice.

TELEVISION VALVE FOR AMATEURS

Amateurs will shortly feel the benefit of the design work which is going on with valves for use in television amplifiers. New valves are being produced very frequently, such as the new R.C.A. 1851 which has a slope of 12 mA./B. A similar valve has been produced in this country by the General Electric Company, and amateurs have been quick to realise the advantages of these high-slope valves in ordinary radio receivers. These new valves are ideal for use in radio and intermediate frequency stages, and greatly increased gain can be obtained.

It appears that most of the new components designed primarily for

use in television receivers will be also used in the ordinary short-wave receiver.

AMATEUR TELEVISION IN AMERICA

It is very interesting to notice the different outlook of the manufacturers in America and those in this country. While television, at any rate technically, has been kept rather hush-hush in Europe, the American manufacturers are giving it all the publicity they can. In order still further to increase the interest taken by American amateurs and radio engineers in television, the R.C.A. Company have produced some tubes and necessary components complete with all data that the constructor is likely to need. They are also advertising very extensively despite the fact that there is no television service in America and little likelihood of any return for their money from the ordinary man in the street. They do, however, appreciate that the amateur, if he can obtain supplies and information, will experiment and so increase the interest amongst the ordinary listener.

TRANSMITTING VALVES FOR AMATEURS

For many years British valve makers have refused to produce a valve of the kind suitable for the average amateur transmitter, who has been compelled to buy abroad. Even the few valves that have been produced in recent months have been far too expensive in comparison with the prices asked for valves of American and Dutch origin. However, at the present time there appears to have been a complete reversal of opinion amongst valve makers, and now there are no less than four makers all eager to market valves for the British amateur at prices very similar to that asked for American valves of a similar kind.

SHORT-WAVE RADIO IN TRAINS

While many of the American long-distance trains have included radio communication between driver and guard this system has not taken on very well in Europe. It will be interesting to see how the goods trains on the Norwegian State Railways will find the radio service which has been put into use between engine driver and brakeman. This is quite

AND MORE REFLECTIONS

a new idea for the Norwegian railways and if satisfactory may be included on passenger trains.

INDOOR OR OUTDOOR AERIALS

The Huddersfield Urban Council have prohibited the erection of wireless poles on their new housing estate at Peniston, being of the opinion that indoor aerials are quite satisfactory. While this may or may not be so, they have probably forgotten that the time is not far distant when even the people in Huddersfield will have television receivers, which will certainly require external aerials. These rules and regulations are very often made without any eye to the future.

TELEVISION PLANS FOR SYDNEY

Now that John L. Baird is in Australia and has been able to tell the authorities something about the progress of high-definition television it is expected that television in Australia will be developed in the near future.

In Sydney, however, there are several problems regarding the site for the television station for, if it is erected in the heart of the city, half of the radiation will be wasted over the Pacific Ocean.

Amateurs in Sydney have shown that by picking a high position on the Blue Mountains, it is possible to transmit a good signal into Sydney with quite low power. A station in this position would also be able to cover large towns in the north, east and south, such as Liverpool, Windsor, Penrith, Camden, Newcastle, and Parramatta.

TELEVISION AND THE TELEPHONE

German engineers have been very keen to develop the commercial side of television where applicable to telephone use. A service has been in operation for some time between Berlin and Leipzig, a distance of 90 miles. This has proved so satisfactory that the service is being extended so that thirty telephone calls with vision can be made simultaneously.

TELEVISION A.R.P.

A very successful transmission was that of the Territorial Army A.R.P. group on Easter Monday. The latest

type of anti-aircraft gun, and all the associated equipment was shown and fully explained to viewers. A machine gun was also televised and a gunner explained just how and why a machine gun was needed in addition to the large 3.7 in. anti-aircraft gun. During the evening transmission the searchlight was put into use and the mock air-raid was very satisfactorily televised. Actually the air-raid took the form of an imaginary attack on Alexandra Palace.

LARGE SCREEN PICTURES

It is interesting to draw a comparison between the results obtained in large-screen picture production in this country and Germany. The power required to produce the large picture by Fernseh is of the order of 40 kW. This is controlled power. In the Scopphony picture, the highest controlled power necessary for a picture of this size is only 500 watts. The largest power used is the same as taken by the standard cinema arc.

Price Reduction.

The Baird model T11 television receiver complete with all-wave radio has been reduced in price to 55 gns. This price includes aerial, installation and one year's free service, and represents wonderful value for a really high-class receiver of unique design.

Crystal Bars for Frequency Meters.

One of the requirements of every amateur is a crystal controlled frequency meter, but owing to the cost of the crystal element amateurs are inclined to rely on the less effective absorption type of meter.

Messrs. Radio Clearance, of 63 High Holborn, W.C.1, have a large stock of quartz crystals ground to a frequency of 125 kc. These are priced at the extremely low figure of 4s. 6d. They can also be fitted with 125 kc I.F. transformers for crystal gate superhet work for 7s. 11d. complete.

Amateurs will find quite a lot of components of interest at Radio Clearance, such as three gang midget condensers for 2s. 6d. They also have an excellent stock of new Bryce mains transformers varying from 350 volts for 11s. 6d. up to 500 volts for 17s. 6d. Another excellent line is a 300 volt Mains transformer for 5s. Suitable chokes for use with these transformers are available from 4s. 6d. upwards.

Inexpensive Morse Recorders

Amateurs interested in automatically recording morse signals should make a point of getting in touch with Messrs. Galpins Electrical Stores, of 75 Lee High Road, Lewisham, S.E.13. They have some excellent ex-R.A.F. morse inkers for 30s. which are extremely good value for money.

A visit to Galpins showrooms will not be a waste of time for those who are in the vicinity, for there is a whole host of items suitable for amateurs. Taken at random, there are high-resistance headphones made by B.T.H. and Western Electric for 2s. 6d., 500 mA. filter chokes for 30s. A complete range of Weston moving coil mA. meters, rotary convertors of all kinds, Epoch 20-watt loudspeakers for 45s., Precision wave-meters for as low as 3s. and some really cheap high-capacity condensers. One particularly good item is an electrostatic volt meter of the quadrant type with a 2½ in. scale for 12s. 6d. Please write for the new list of these new components.

"Television Sound Programmes on your Broadcast Set."

(Continued from page 276.)

The main receiver should be tuned to approximately 200 metres, or to a wavelength around that figure where no station is received. If an all-wave receiver is in use, then tune down to approximately 100 metres, as this will provide much more stable operation. If, however, the convertor is being used at a distance from Alexandra Palace, then greater gain can be received if the receiver is tuned to approximately 500 metres.

The following components will be required.

Components.


- 1—Chassis, panel and screen (Peto-Scott).
- 1—Coupling transformer (Peto-Scott).
- 2—15 mmfd. low-loss condenser (Raymart).
- 2—.005 mfd. tubular condenser (Dubilier).
- 2—.01-mfd. tubular condensers (Dubilier).
- 1—.0001-mfd. mica condenser (Dubilier).
- 1—7-pin ceramic valve holder (Clix).
- 1—TX₄ metalized valve (Tungram).
- 2—20,000-ohm 1-watt resistors (Erie).
- 2—30,000-ohm 1-watt resistors (Erie).
- 1—1,000-ohm 1-watt resistor (Erie).
- 1—200-ohm 1-watt resistor (Erie).
- 1—Slow motion tuning drive and scale (B.T.S.).
- 1—.0001-mfd. pre-set condenser (Cydon).
- 1—4-way connecting cable (Bulgin).
- 1—Tapped valve socket (Bulgin).

We have made arrangements with Messrs. Peto-Scott, Limited, to supply readers with a convertor built to this design, which is ready-wired, guaranteed and tested.

TELEVISION IN EASY STAGES

III—HOW THE BEAM IS MADE TO SCAN

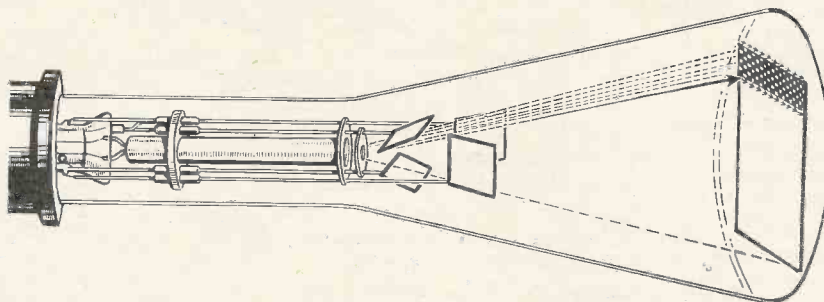The two preceding articles in this short series outlined the principles of television reception and reviewed the type of receiver employed for the reception of the vision signals. The following article ex-



plains in a simple way how the light spot is caused to move across the screen in order to produce the "raster" or unmodulated light scan which is the basis of the picture.

IN the first article of this series (March issue) it was explained that the production of the light spot, from which the picture is built up, and the means to cause this spot to travel across the screen in a predetermined way is entirely a function of one unit of the receiver—that is the time base. The light spot and its movement do not concern the actual transmission except that in order to keep the spot exactly in step with the transmitter a triggering action is provided which at definite intervals has the effect of correcting any inaccuracy.

There is, therefore, the fundamental problem of making the beam move across the screen in such a way that it traces a series of lines at a definite speed and of a definite length.

It will be clear that we have to

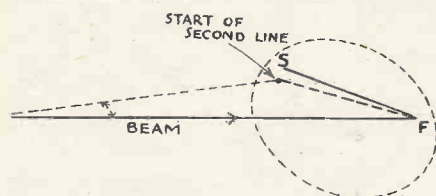


Fig. 1. Diagram showing the movement of the beam to cover the screen.

cause the cathode-ray beam to perform a to-and-fro movement to enable all the scanning lines to be drawn in the same direction in the same way as the eye follows lines of type in a book. This will be clear from Fig. 1, which shows the beam has completed one line in moving from S to F, but before it can draw a second one, it must be returned to a position in line with S and a little below. The drawing of each line is thus followed by a return stroke which places the beam in position for the next one. This return stroke

must, however, be made at such a speed as to be invisible.

For producing a complete line screen on the cathode-ray tube we have, therefore, to deal with three movements:—

The tracing of the line at a certain speed.

The almost instantaneous return of the beam to its original place.

A shift of the beam in a direction at right angles to the line to produce the spacing between them.

How the Movement is Produced

The movement of the beam can be produced either magnetically or electrostatically. If a pair of coils is mounted on either side of the back of the tube and a current, which is caused to gradually increase in value, is passed through them, the beam will move across the screen under the influence of the field produced by the coils.

Similarly, if an increasing voltage is applied to the deflector plates of an electrostatic type of tube, the beam will move correspondingly by reason of electrostatic deflection.

The problem for either system of deflection resolves itself into the production of a varying voltage which will give the required movement of the beam. (This is also the case with magnetic deflection, for the current through the coils will depend upon the applied voltage.)

It is evident that the scanning line

Ensure obtaining "Television and Short-wave World" regularly by placing an order with your newsagent.

must be drawn at a perfectly uniform speed, i.e., the beam must cover equal distances on the screen in equal intervals of time. This means that the voltage applied to the deflector plates, or coils, to move the beam must increase at a uniform rate. After the line has been drawn the beam must be returned to its initial position as quickly as possible in readiness for the next travel, and to cause this the voltage must abruptly drop to zero after it has reached a given value which has resulted in the beam moving the required distance to produce the full line.

These two voltage variations can be represented by a curve to which the name "saw-tooth" has been given because of its appearance. This is shown by Fig. 2 and it indicates the shape of the voltage wave required to draw one line and return the beam to its starting point.

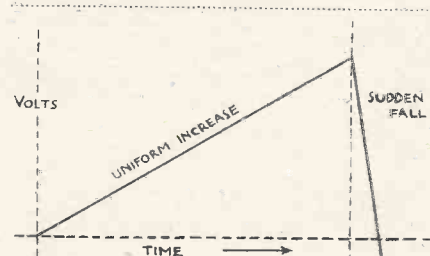


Fig. 2. Curve showing saw-tooth wave and relation of voltage and time.

Up to the present we have seen that the beam must be moved from one side to the other and then fly back practically instantaneously. There is, however, the third condition—the shifting of the beam in a direction at right angles to the line to produce the sequence of lines on the screen. This could be done by a small voltage applied to the other deflector plates at the end of each "out and back" movement of the

HOW SAW-TOOTH WAVES ARE PRODUCED

beam—a sort of ratcheting action which would move the beam by just the right amount to put the second line alongside the first.

It is more simple, however, to apply a similar type of voltage

A very satisfactory arrangement is to use a condenser connected across an H.T. supply in such a way that the voltage across it gradually rises at a rate which can be controlled.

The simplest circuit possible is

distance R —the higher the value of R the longer will the condenser take to charge. The rate of charge can be worked out from a formula which is too complicated to give here, but there is an approximate calculation which can easily be made as follows: The time taken for the condenser voltage to reach 63 per cent. of its final value is called the "time-constant" of the circuit and is given by the product of C the capacity of the condenser in microfarads and R the resistance in megohms. So with a resistance of 5 megohms, and a capacity of 1 mfd. the condenser will take over 5 seconds to reach its final voltage. For scanning requirements, we need $1/25$ th second for one condenser, and this could be given by .01-mfd. and about 3 megohms. For the shorter timing rate of the line scan a much smaller capacity will be required.

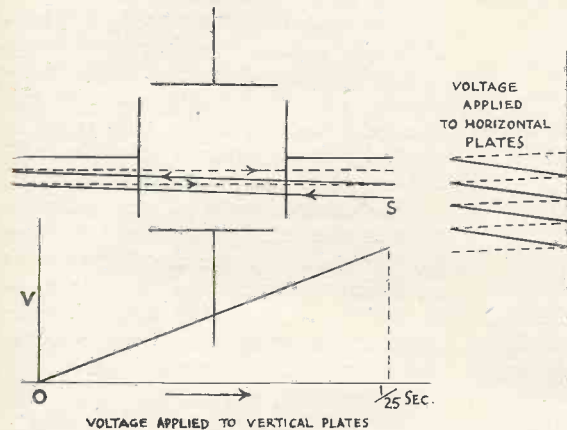


Fig. 3. The zig-zag trace produced when the two deflecting voltages are applied to the deflector plates.

wave to each pair of plates and produce the movement by a combined deflecting effect. If this is done, the beam will be acted on by both voltages during its travel along the line and will slope slightly the whole way, so that at the end of the line it will be sufficiently displaced to start the next line straightaway. The combined deflecting effect is shown in Fig. 3. The path of the beam is shown by the thick and dotted lines in the centre of the drawing and the thin lines below show the curves of voltage change applied to the deflector plates.

To consider a specific example, suppose we require to draw a 405-line screen 25 times per second. The time required to draw one line of the screen will be $1/405 \div 25$ or $1/10,125$ second. The voltage applied to the horizontal deflectors will, therefore, rise to its highest value in this time. If now we arrange that the voltage applied to the vertical deflectors reaches its maximum in $1/25$ second, the beam will move from bottom to top of the screen in this time. It will be understood that the lines drawn by the beam will be slightly sloped, but this is of no consequence since the angle is so slight and the lines are so close together.

There are several ways of producing the voltage curve of Fig. 2, but the most practicable is a purely electrical circuit in which the voltage can be made to vary in the way required.

shown by Fig. 4 and as this is the fundamental circuit on which all scanning systems are based, it is worth while examining it in detail and considering its precise action with the aid of meters.

The condenser C is connected to the H.T. supply through a resistance R which can be varied. At the moment of switching on there is no potential across the condenser, and the voltmeter V will read zero. As the charging current flows into the condenser the voltage gradually rises and the needle of the meter will move across the scale until it reaches the value shown on V_1 , which is connected across the H.T. terminals. The condenser is then fully charged, and the voltage across it is the same as that of the H.T. supply.

The rate at which the condenser voltage rises is controlled by the re-

Immediately the condenser has reached its maximum voltage it must be discharged as rapidly as possible to produce the second part of the voltage wave of Fig. 2. Very many circuit arrangements have been devised for giving a rapid discharge and fall in voltage, but the simplest and easiest method is to employ a gas-filled relay or thyratron.

The Gas-filled Relay

The gas-filled relay is an ordinary triode valve in which a small quantity of inert gas such as neon or helium has been placed. The effect of the gas is as follows:

If the grid of the relay is biased to a negative value, current will only flow if the anode voltage exceeds a certain value, depending on the construction of the valve. To take a typical instance, a bias of 9 volts on the grid would mean that no current would flow from the cathode to the anode until a voltage of 160 was applied. Once the current flows a coloured glow is seen in the bulb, and then the grid has no further control over the discharge. The anode current can only be stopped by reducing the anode voltage to a very low value, and when the glow has ceased it will not start again until the anode voltage is raised to its original value of about 160. From this it will be seen that the relay can be used to discharge the condenser shown in Fig.

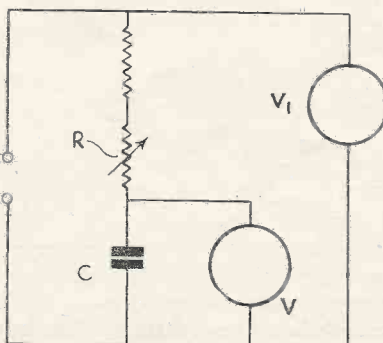


Fig. 4. Diagram showing the fundamentals of a scanning circuit.

THE GAS-FILLED RELAY

4 instantaneously and will be satisfactory.

The valve is connected across the condenser and the grid is given a negative bias. As the voltage rises across the condenser the discharge

at an enormous speed, must, therefore, be operated at some 5,000 volts if they are of the large type and 3,000 if of the smaller type.

The distance moved by the beam on the screen for one volt of poten-

on the anode will be 4×105 or 660. Actually, the calculation will have to be made accurately for the type of tube used and the conditions under which it is run; but the fact remains that an average figure for the deflecting potential to be applied to the beam is 500 volts or more.

Now assume that we apply a potential of 60 volts to the simple scanning circuit already described. The condenser will charge to 500 volts, and the relay will strike at this value if the grid bias is set to a value depending on the characteristics of the relay.

The control ratio of gas relays—that is the relation between the bias on the grid and the anode potential at which the discharge commences—is specified. Assuming it is 20:1 the bias of the relay would have to be set at $500/20$ or 25 volts to ensure striking at the correct value.

The condenser potential, however, when charged through a simple resistance as in Fig. 2 does not follow a linear law, but what is known as an exponential one. This means that the rate of increase of voltage steadily falls off as the condenser charges.

If we plot a curve of charging voltage against time we obtain the curve of Fig. 6, in which the voltage increase is shown for equal intervals of time from the commencement. The increments get less and less as the voltage rises to 600, the full H.T. voltage. The deflection of the beam by this voltage will correspond to the rate of increase, and is shown by the dots under the base line. The beam has certainly been deflected across the screen to the required extent, but the movement is far from uniform and a hopelessly distorted picture would result if this circuit were used without any modifications.

Necessary Modifications

The circuit must be modified, therefore, so that the increase of voltage across the condenser is uniform over the range it is desired to work. This can be done in two ways: by altering the circuit or by increasing the charging H.T., and we can now consider the advantages and disadvantages of each method.

If the resistance in Fig. 2 is replaced with a pentode, the circuit then becomes as Fig. 7. The condenser is connected in series with the anode of the valve and the screen is taken

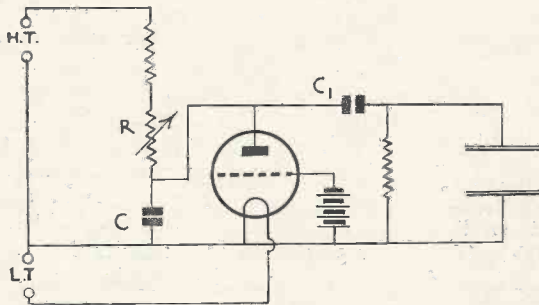


Fig. 5. Scanning circuit employing a gas-filled relay.

suddenly starts at a value determined by the grid bias, and at this point the condenser is short-circuited by the very low resistance of the glowing valve. As soon as the condenser discharges the voltage falls and the discharge ceases when the voltage has fallen to zero. The relay has now become non-conducting and the condenser can be charged again.

A Relay Circuit

The complete arrangement of such a circuit is shown by Fig. 5. The relay is shown connected across the condenser, and the deflector plates of the tube are taken from the anode and cathode connections of the relay, i.e., across the condenser. The voltage variations of the condenser are therefore reproduced across the plates. The condenser C_1 isolates the plates from the H.T. supply. Bias is applied to the grid of the relay as shown.

For several reasons, the simple condenser circuit discharged by a gas-filled relay is not satisfactory in that form for use as a scanning circuit and in order to understand why this is so it will be best to consider the requirements. Obviously the intensity of the spot must be high in order that the image can be seen in dull light. This means that the anode voltage of the tube must be as high as possible, since the intensity is roughly proportional to the anode voltage.

Naturally, the trace on the screen appears fainter as the beam moves faster. Tubes for high-definition reproduction in which the spot travels

tial applied to the deflecting plates, or in other words the sensitivity of the tube, varies inversely as the anode voltage. For a given design of tube there is a formula from which the sensitivity can be found. This is usually given in the form Sensitivity = K/V , where K is a figure given by the makers of the tube and V is the anode voltage at which it is operated. Suppose K is 750, an average figure. Then at 1,500 volts the sensitivity is $750/1,500$ or $\frac{1}{2}$ mm. per volt of deflecting potential. At 3,000 volts the sensitivity will obviously be one-half of this or .25 mm. per volt.

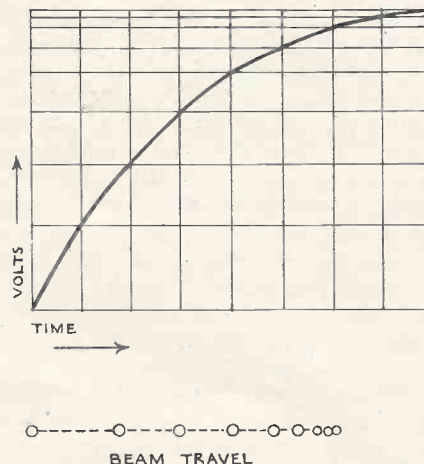


Fig. 6. Diagrams showing the effect of non-linear potential applied to the deflecting plates.

Now for the sake of example let us assume that the picture size is approximately $6\frac{1}{2}$ in. by $4\frac{1}{4}$ in. This means that the travel of the beam will be 165 mm. in the horizontal direction and the voltage required to deflect it this distance at 3,000 volts

HARD-VALVE CIRCUITS


to a potentiometer connected across the H.T. supply. The characteristic of the pentode is such that the anode current remains practically constant over a very wide range of anode voltage.

When the circuit is switched on the condenser will charge at a rate which is determined by the impedance of the pentode, controlled by the screen volts. As the condenser voltage rises, the voltage across the valve falls, the sum of the two being equal to the applied H.T. But as the pentode anode voltage falls the current flowing through it remains substantially constant, enabling the condenser to charge at a constant rate. The voltage across the condenser will rise uniformly with time and the deflecting potential will give a true linear movement to the beam.

This circuit is therefore a method of overcoming the disadvantage of the one previously described and provided that the characteristic of the valve is as straight as possible there is the minimum of distortion in the scan.

An alternative to this rearrangement of circuit is the increasing of the applied H.T. from 600, our estimated figure, to over 2,000! This

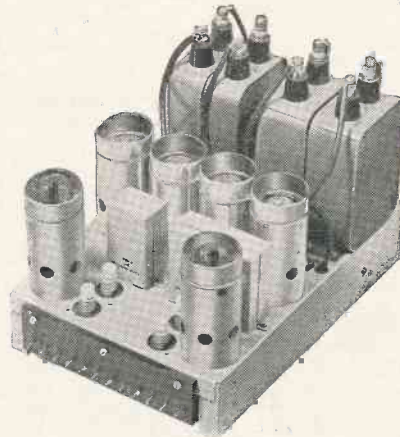The figures, therefore, become 400 and 2,000 and 500 and 2,500, and all that has been done is to magnify the whole voltage scale so that the part we wish to use is sufficiently long to give a full linear travel of the beam without distortion.



A typical time base. This is the construction employed in the G.E.C. receiver.

There are many other types of linear timing circuit. A high-vacuum valve circuit can be made to perform the same job, and be more stable in operation and in general more reliable.

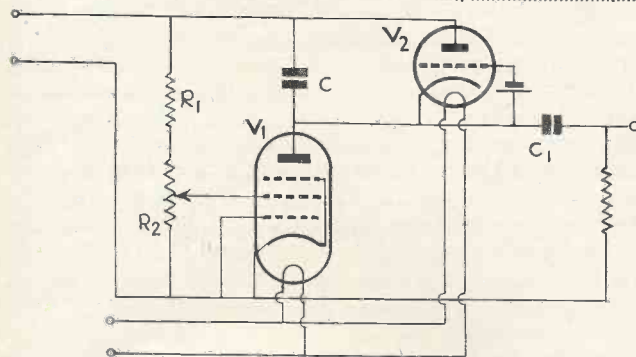


Fig. 7. Scanning circuit employing a pentode in place of the charging resistance.

current rising to a high value. If we imagine a condenser charged and connected across a valve which is normally biased to cut-off point, a sudden pulse of potential applied to the grid and swinging it positive will cause a heavy current to flow through the valve from the condenser and will discharge it in much the same way as the gas relay.

Discharge circuits of this type in which the impulse to the grid is supplied by a separate oscillator have been developed and have the advantage that the frequency of discharge can be kept within very close limits indeed, but they are outside the scope of this article which had the objective of explaining in a simple manner an outline of the means whereby the beam can be caused to travel to cover the screen.

The Technological Institute
of Great Britain

WE have received from The Technological Institute of Great Britain a prospectus entitled "The Engineer's Guide to Success," a very useful guide for those who are considering taking up any branch of engineering as a profession.

The T.I.G.B. was founded in 1917, and has enabled upwards of 25,000 men to embark upon careers in engineering through the medium of correspondence training. The tutorial service embraces the various branches of engineering and allied technology and includes a course on Television which, we understand, is particularly authoritative. These are covered most thoroughly as may be judged from the fact that the T.I.G.B. operates over 200 courses—the widest choice of engineering courses in the world.

Since its inception, the T.I.G.B. has specialised in the training of examination candidates and in order to ensure that a student shall study only for an examination which he is eligible to sit, the regulations governing admission are clearly set out. Training until successful is guaranteed to every student. The prospectus provides a fund of information on the various courses provided by the Institute and copies may be had upon application to Temple Bar House, London, E.C.4, and mention of TELEVISION AND SHORT-WAVE WORLD.


seems curious at first sight but the explanation is not difficult. Referring to the curve of Fig. 6 it is seen that the first 150 volts increase takes place at a uniform rate, i.e., the condenser is charging linearly for the first small portion of its charge. If we magnified this small straight portion of about 150 volts three or four times we should get 500 volts of linear portion, which is what is required. At the same time the overall H.T. must be increased in proportion, so it must be made 4×600 or 2,400 volts.

The principal difficulty in the design of high-vacuum valve circuits is the imitation of the "snap" discharge action of the gas relay. If an ordinary valve is biased back beyond the point at which anode current starts, an increase in anode voltage will cause a gradual rise in anode current instead of the practically instantaneous rise which we require. To accelerate the increase of current in the valve it is possible to swing the grid momentarily positive which will give a rapid flow of

THE MARCONI-E.M.I. TELEVISION SYSTEM

REASONS FOR THE ADOPTION OF THE PRESENT STANDARDS

On April 21st, an important paper was read before the Institution of Electrical Engineers by Messrs. Blumein, Browne, Davis and Green, of E.M.I. Ltd., on the development of the present B.B.C. television system. We gratefully acknowledge the permission of the Institution to publish the following abstract, which will be followed next month by a similar abstract dealing with the London Television Station.

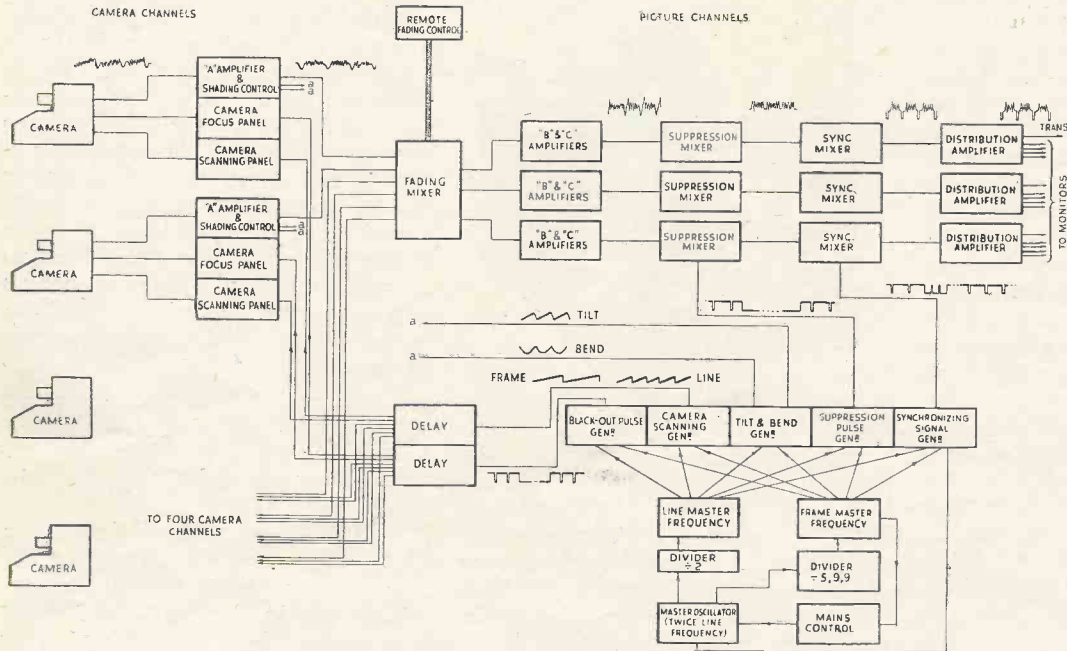

Schematic layout for control equipment of 6-camera and 3-picture channels.

THE vision signals to be transmitted represent from instant to instant the brightness of the picture being scanned, and may have any amplitude between a value representing black and a value representing the brightest part of the picture or "white." The signals may change gradually, as for a gradual shading of the picture, or very rapidly, as for a vertical edge, the ultimate rapidity of change being limited by the size of the transmitting scanning-spot and the frequency-limitations of the transmitting circuits. It should be noted that the vision signals essentially contain all frequencies down to zero and lie one side of the datum level, which is black. The signals in this respect are more akin to telegraph signals than telephone signals.

It has been considered whether better transmission could be obtained by distorting the transmitted waveform from that directly representing brightness, by distorting the frequency characteristic before transmission and correcting at the receiver. A short consideration will show that practically any frequency within the range may be produced at full black-to-white amplitude; so that, if the picture transmitted is not prescribed, any frequency distortion will reduce the transmitted level of some frequencies without enabling the level of any others to be increased. As far as possible, therefore, the vision signals are transmitted with a flat frequency characteristic.

In current cinematograph technique it is usual to increase the contrast by a factor lying between 1.5 and

2.0, presumably to make up for lack of colour. This factor is usually called γ , the original brightness A of any point being related to the reproduced brightness B by the relation $B = kA$. Since the eye is approximately logarithmic, this leads to an increase of contrast of approximately γ . This same effect is required in television. The question naturally arises as to whether this should be applied at the transmitter or the receiver. Now a given small change in light intensity at the picture is more noticeable in dark than in light parts of the picture. With a linear characteristic at the receiver, the dark parts of the picture are liable to suffer severely from quite slight interference.

By applying the correction at the receiver the sensitivity of the receiver is rendered lower for low light-intensities, so that slight interference is not so noticeable. It is advantageous, therefore, to transmit pictures with unity γ and make any correction at the receiver. This is convenient since any unidirectional control, such as the control of beam current in a cathode-ray receiving tube, is likely to be curvilinear in the required sense. Theoretically, assuming a logarithmic sensation law for the eye, a logarithmic transmitting distortion with exponential receiving characteristic is indicated, but such an arrangement is hardly considered practicable, if really desirable; and so far, despite its advantages, has seldom if ever been applied even to sound transmission.

The above arguments lead to the transmission of a signal, as far as possible undistorted in frequency or

THE SYNCHRONISING SIGNALS

amplitude, representative of the brightness of successive elements of the picture scanned with a constant scanning velocity.

As explained above, the vision signals lie within a range limited by black and white (representing the brightest part of the picture). Synchronising signals can therefore be transmitted as signals lying beyond the black or white outside the vision signal range. Such signals may be spoken of as "blacker than black" or "infra-black" if outside the vision signal range in the black direction, or "whiter than white" or "ultra-white" if outside in the white direction. If ultra-white synchronising signals are employed it is necessary to provide special and rather complicated means at the receiver to prevent these synchronising pulses from appearing on the picture. If synchronising signals are employed in the infra-black these signals will not, with the majority of receiver types, appear on the receiver screen, since the majority of light-control devices are unaffected by a signal greater than that necessary to obscure the light. This great advantage of requiring no special synchronising signal-obscuring device at the receiver has led to the adoption of infra-black synchronising signals. In this connection it should be noted that there is a possible workable system employing ultra-white synchronising pulses extending down to zero radiated carrier, with black representing peak carrier.

This system has the merit of providing simple A.V.C. (automatic volume control) and noise suppression at the receiver, but on the other hand a comparatively complex arrangement is necessary for preventing the ultra-white signals from appearing on the screen. The infra-black system adopted can supply A.V.C. and noise suppression with no more, or even less, complex equipment than is required for pulse suppression by the above ultra-white system. Further, for a simple receiver the infra-black receiver is less complex than the ultra-white.

Positive Modulation and 30% Synchronising Pulse

If the synchronising signals are represented by a high carrier ("negative modulation") they will be very prone to interference, which increases the amplitude and so produces at the receiver effective super-strong synchronising pulses. Such strong pulses may greatly disturb the picture-scanning. On the other hand, white being represented by a low carrier value, larger ultra-white signals than those represented by zero carrier cannot be produced, and this reduces the brightness of severe interference.

If, however, "positive modulation" is employed, in which synchronising signals are represented by a low (and, very preferably, practically zero) carrier while white is represented by a high carrier, super-strong interfering synchronising pulses cannot be experienced. This enables comparatively small synchronising signals to be employed while satisfactory synchronisation is still given. With this arrangement strong ultra-white signals can be produced by interference, but these signals are less irritating than the breaking-up of the picture produced by the interference giving super-strong synchronising pulses.

Of course, with negative modulation a carefully designed limiter could be used at the receiver to ensure that the scanning generators could only be affected by signals of the exactly correct amplitude. It is thought that such a limiter would be very difficult to adjust for all reception conditions, and if made self-adjusting would be upset by very severe interference. A similar limiter, not requiring as sensitive an adjustment, may be used for suppressing interference when positive modulation is employed.

Tests were carried out some years ago from Hayes, Middlesex, to St. John's Wood in order to compare positive- and negative-modulation reception in the presence of interference. The initial tests were made using synchronising signals equal in amplitude to the vision signals. With negative modulation the interference gave rise to breaking-up of the whole picture.

A considerable improvement was obtained by changing to positive modulation, the white flashes produced by interference being much less irritating than the breaking-up of the picture. Better results still were obtained by modulating so that the synchronising signal was represented by practically zero carrier. With this condition satisfactory synchronising under interference conditions could be obtained with synchronising signals of only one-fifth the vision amplitude. No interference can possibly produce a field strength, and so detector output, less than zero, so that by modulating down to zero carrier for synchronising signals no super-strong interfering synchronising pulses can be produced, and hence very good interference-free synchronising is obtained at the receiver.

These tests led to a definite decision to adopt a system with substantially zero carrier representing the synchronising signal and with peak carrier representing white. The diminishing return of increased vision signals produced by reducing the synchronising signal down to one-fifth the vision signal led to the adoption of a synchronising signal of three-sevenths of the vision signal.

Intervals between Lines and Frames

The values 50 frames per sec. and 405 lines having been chosen, it was necessary to determine arbitrarily the time-intervals between successive lines and frames to which the receiver must be designed to work. These time-intervals are needed at a cathode-ray receiver for the return stroke, by which the cathode-ray beam is returned from the end of one line of frame to the beginning of the next. Actually the beam is turned off, or "blacked out" during the return stroke, nevertheless the electric or magnetic field controlling beam-deflection must be altered just as though the beam were there to perform the return stroke. Obviously such electric or magnetic fields cannot be altered instantaneously at the end of each line or frame, and thus time-intervals are necessary if some of the picture is not to be missed.

With mechanical receivers using rotating scanning means, successive lines are scanned by different mechanical elements, so that one line may be scanned from the instant the previous line-scan terminates. With such an arrangement absolutely perfect phase synchronisa-

AUTOMATIC VOLUME CONTROL

tion would be necessary to prevent the beginning of a picture being cut off and folded round to the end of the picture. Intervals between lines and frames therefore provide a small black edge round the picture which allows for a small phase-error in the mechanical scanning.

Considering cathode-ray receivers, the total line period for a 405-line system is approximately 100 microsec. (more exactly, 98.8 microsec.), whereas a frame period is 20,000 microsec. It is therefore obvious that it is possible to reverse the scanning field (electrostatic or electromagnetic) in a shorter fraction of the frame period than the line period.

The intervals between frames may therefore be a smaller fraction of the frame period than the intervals between lines are of the line period. On the other hand, the intervals between frames should be longer than the intervals between lines, and this for two reasons. First, the frame frequency is much lower than the line frequency, so that the electrical components of the frame scanning circuit (transformers, and coupling condensers) have longer time-constants and are usually physically bigger, and thus the unwanted strays are greater than for the line-scanning circuit. This makes it more difficult to reverse the frame-scanning field quickly (say, in less than the duration of one line). Secondly, since all synchronising pulses are rectangular and of equal amplitude the frame signals are differentiated from the line signals only by the long duration of the former.

If the frame-scanning signals only are to trip the frame-scanning mechanism, some time must elapse between the end of the picture signals of one frame (which is the earliest moment that the frame-synchronising signals can conveniently be transmitted) and the beginning of the frame return stroke, in order that the long frame-synchronising signal may be transmitted and operate the receiver.

After much consideration the minimum interval between the picture signals of successive lines was fixed at 15 per cent. of the total line period (14.8 microsec.), and the minimum interval between the vision signals of successive frames was fixed at 10 lines (4.94 per cent. of the total frame period). This gives a time efficiency of 80.8 per cent. Any attempt to raise this figure to 90 per cent. would lead to very severe difficulties in connection with scanning cathode-ray receivers. As regards mechanical receivers, it appears also reasonable to give a bigger percentage interval between lines, since the scanning speed is high for lines and the phase accuracy probably more difficult to obtain.

The original specification wave-form was incomplete in one respect. As specified under minimum-interval conditions, and as shown on the drawing, the beginning of line-synchronising signals was coincident with the end of the vision signals of the line. Such coincidence with instantaneous change from white to synchronising is impossible with finite frequency band-widths. Even were such a signal radiated, it would lead to trouble in a receiver of finite band-width, inasmuch as the line synchronising would be affected by the vision signals immediately preceding the line-synchronising signal. The effect of this would be a slight distortion of vertical

edges in dependence on the signal brightness on the right-hand edge of the picture.

The specification should have contained a reference to a minimum additional interval prior to the line-synchronising signal of 0.5 per cent. of a line, making the total minimum interval between the vision signals 15.5 per cent., of which 0.5 per cent. precedes and 15 per cent. follows the beginning of the line-synchronising signal. This additional minimum interval has in fact always been present in all transmissions radiated from Alexandra Palace on the Marconi-E.M.I. system, the apparatus being set to give an interval of between 0.5 per cent. and 1 per cent. between cessation of vision signals and beginning of line synchronising. The existence of some interval between vision and synchronising signals is a practical necessity at the transmitter, so as to give a tolerance which ensures that the vision and synchronising signals do not get mixed.

Automatic Volume Control

Before closing this discussion of the system specification it is well to consider whether the wave-form provides for facilities which may be required in the future. It has often been pointed out that an A.C. transmission system provides automatic volume control (A.V.C.) for television in the same manner as it is available for sound reception.

With an A.C. system, however, the A.V.C. must certainly operate very slowly so as to be unaffected by frame frequency, and therefore it will not be suitable for correcting variations of signal-strengths due to objects moving rapidly near an aerial. Further, the simplification of A.V.C. claimed will hardly justify the increased receiver size necessary to avoid overloads from "wandering" signals, and the reduced signal-strength due to poor use of the transmitter.

Again, it has been pointed out that a D.C. transmission with negative modulation provides simple A.V.C. by observation of the peak synchronising amplitudes. This is admittedly the case, but any simplicity of A.V.C. is, it is thought, outweighed by the complexity of the limiter necessary to suppress false synchronisation.

With the system here described, A.V.C. has not in general been found necessary on the wavelengths at present used. Were an A.V.C. required, however, the necessary control might be obtained by observing the black-level amplitude which always follows a synchronising signal.

The necessary pulse for controlling such a device can, for example, be obtained by differentiating the synchronising pulse and using the trailing edge. There are a number of circuit arrangements available, and the extra equipment involved constitutes a small addition to the multi-valve television set. Furthermore, with synchronising signals extending to zero, the arrangement can be made such that it cannot "lock" in a position of maximum receiver sensitivity, provided this maximum sensitivity is not so great as to overload the receiver completely with surface noise. If desired, a limiter may then be added to suppress interference flashes on the screen, the setting of the limiter being much less critical than in the case of the limiter which is practically a necessity for a negative-modulation system.

“TILT” AND “BEND”

Camera Control Equipment

The camera control equipment may be divided into four main groups, comprising camera channels, picture channels, pulse generators, and supply equipment.

Each camera channel contains a unit for focusing the cathode-ray beam of the Emitron tube, by which the correct potentials may be adjusted for the electrodes. This unit also contains controls for adjusting the beam current for optimum working; a reflecting galvanometer facilitating this operation.

Another unit is included in each camera channel which accepts sawtooth signals from the pulse generator, and drives scanning currents at line and frame frequencies into the deflection coils in the camera. This unit has controls affecting the height and width of the scanned area, and for shifting the scanned area bodily.

Tilt and Bend

Apart from the distortions of the picture signals which are deliberately introduced in the head amplifier, the signals from the camera also contain spurious signals originating in the Emitron tube, of which the character depends largely upon the illumination of the scene being transmitted. These spurious signals occur during both forward and flyback periods at line and frame frequencies.

The effect of the forward-period spurious signals is generally an overall “tilt” of the picture signals in a line or frame scan, or an overall “bend,” or the effect may be a mixture of both “tilt” and “bend.” Further, the “tilt” and “bend” may occur in either sense. The signals photographed are typical of those produced by a scene situated in a field of very poor illumination; Fig. (a) showing the signals received from the camera after magnification in the “A,” “B,” and “C” amplifiers.


Fortunately, under conditions of fair illumination, the “tilt” and “bend” signals conform to a shape which can be balanced by a simple means consisting of artificial shading signals manufactured in the group of pulse generators, of which the “tilt” and “bend” components can be adjusted both in amplitude and in sense by a small number of controls. Fig. (b) shows the picture signals after the introduction of artificial shading signals containing “tilt” and “bend” components.

As the character of the spurious signals is likely to be different in the various camera channels, it is obviously necessary to provide independent shading controls. In each “A” amplifier, to which the picture signals from the appropriate camera are taken, four controls are therefore provided by which the amounts of artificial “tilt” and “bend” signals at both line and frame frequencies may be adjusted.

The spurious signals which occur in the flyback periods are of a more erratic nature, their shapes depending upon a variety of circumstances. Since the scanning currents are synchronised, however, these spurious signals may be suppressed, preparatory to the introduction of the synchronising signals, in the same manner for all camera channels.

The signals from the output of the fading mixer are amplified by a “B” amplifier having adjustable gain,

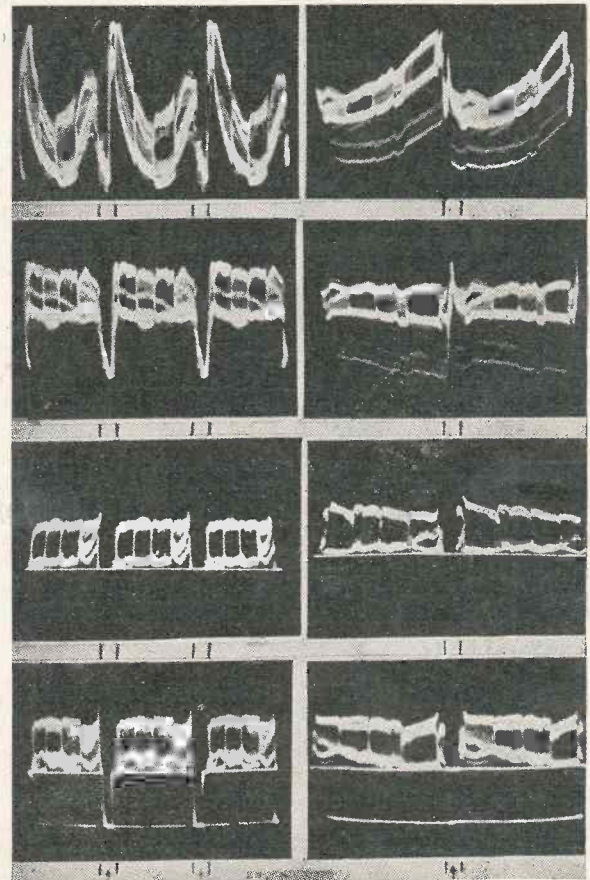with maximum voltage-magnification of 150 times, and a “C” amplifier with fixed magnification of 20 times. Couplings between stages in these amplifiers follow transmission-line practice, in that the capacitance of the anode circuit of one stage is separated from the capacitance of the following grid circuit by a series inductance.



Intervals between lines (line scan) Intervals between frames (frame scan)
Development of television signal wave form.

Following the “C” amplifier, a unit is included in which the intervals between lines and frames are “cleaned up” in readiness for the introduction of the synchronising signals.

The picture signals having been referenced back, the spurious signals are suppressed by adding large positive pulses to the negative picture signals during the intervals between lines and frames. The pulses lift the spurious signals clear of the picture signals in the infra-black direction, and the spurious signals are removed by rectification at a subsequent valve. This valve is provided with a bias control, by which the level at which the suppression pulses are cut off can be adjusted to be the same as that of picture black. Fig. (c) shows picture signals to which this process has been applied.

The picture signals are now free from spurious signals and contain a direct component. In the following unit the synchronising signals are added to the “prepared” intervals between lines and frames, and appear as in Fig. (d). The television signals are now ready for radiation, except for the relative amplitudes of picture and synchronising signals.

RECENT TELEVISION DEVELOPMENTS

A RECORD OF PATENTS AND PROGRESS Specially Compiled for this Journal

Patentees: C. H. F. Muller Akt :: Philco Radio and Television Corporation :: The British Thomson-Houston Co. Ltd. :: M.V. Philips Gloeilampenfabrieken :: E. C. Cork and J. L. Pawsey :: V. Zeitline, A. Zeitline and V. Kliatchko :: Farnsworth Television Inc.


Focusing the Spot

(Patent No. 476,417.)

OWING to slight inaccuracies in the assembly of the electrode system in a cathode-ray tube, it is usually necessary to apply a correcting voltage in order to focus the

oscillation-generator and the input valve for the synchronising signals. The object is to throw back on to the grid of the input valve a negative bias sufficiently strong to paralyse that valve immediately after it has received a synchronising signal. The time-constant of the circuit is also

the scanning action of a stream of electrons. The image so formed is stored up during the interval between successive scanings on the "Lenard phosphor" screen, and the latter is scanned by a ray of infra-red light which is synchronised with the ordinary electron stream from the cathode-ray tube. As a result, the whole of the available photo-electric energy is released and made available for signalling.—The British Thomson-Houston Co., Ltd.

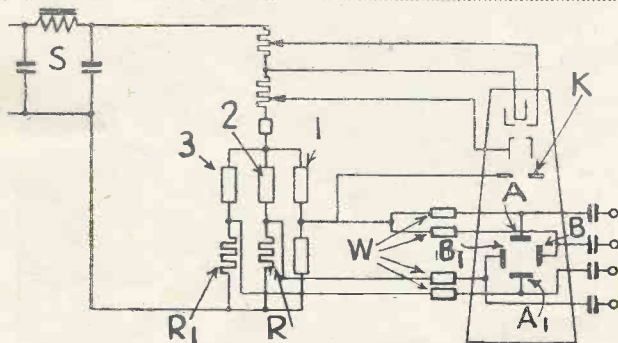

Method of centring the spot.
Patent No. 476,417.

spot dead in the centre of the fluorescent screen. The figure shows a supply potentiometer by means of which the required correction can readily be made.

The potentiometer is shunted across the terminals of the smoothing circuits, and is divided at its lower end into three parallel branches. The first branch has a fixed ratio tapping, and supplies the anode K, and the plates A, B of the usual deflecting system. The branch 2 contains a variable resistance R, which regulates the voltage on the deflecting plate B₁. The voltage on the plate A₁ is adjusted from the branch 3, which similarly includes a variable resistance R₁.

The spot is centred or focused on any desired part of the fluorescent screen by adjusting the variable resistances R and R₁. Fixed resistances are included in each of the supply leads as shown at W.—C. H. F. Muller Akt.

Time-base Circuits

(Patent No. 477,038.)

A feed-back circuit is inserted between the last stage of a saw-toothed

made such that the blocking bias is operative for nearly the whole interval between one synchronising signal and the next, though not quite.

The result is that although the input valve is "released" in time to accept the next synchronising impulse, it does not respond to any static or similar interfering impulses which may arrive during the interval and which may tend to trigger the saw-toothed generator into undesired oscillation.—Philco Radio and Television Corporation.

Photo-sensitive Screens

(Patent No. 477,216.)


The so-called "Lenard phosphors," such as zinc sulphide with a mixture of manganese, have the property, when exposed to light, of storing up the resulting photo-electric effects, and only releasing the accumulated energy when subjected to the action of infra-red rays.

This property is utilised to increase the efficiency of the type of television transmitter in which the picture is first focused on to a "mosaic cell" screen so as to set up an electric image, which is then discharged by

Projection Tubes

(Patent No. 477,612.)

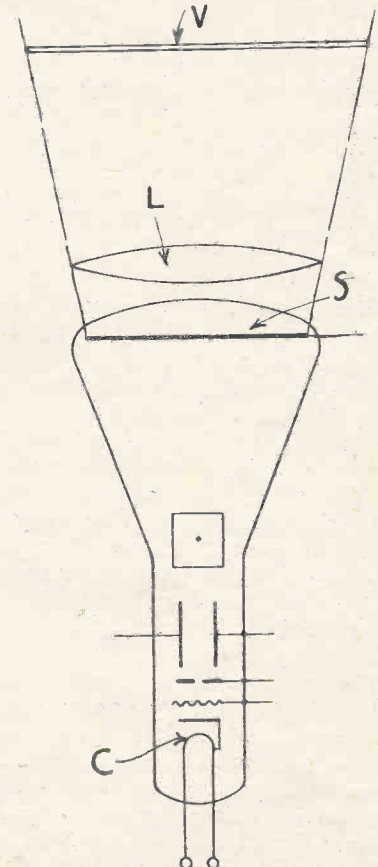Instead of using a fluorescent screen, the picture is formed as an



Projection tube employing a metal screen.
Patent No. 477,612.


incandescent image on a thin metal sheet S by the heat produced by the bombardment of the electron stream from the gun C. The sheet is made of tungsten or molybdenum and should not be more than 20 microns thick. The picture so produced is then projected on to a large viewing screen V through a magnifying lens L.

Unlike ordinary fluorescence, an incandescent picture contains all the primary colours of the original picture, so that it is possible to build up from it a picture in natural colours on the viewing screen. Three separate projection tubes may, for instance, be focused on to the same viewing screen, with a different colour filter for each. Or three different filters can be inserted, in rapid succession, between the sheet electrode S and the screen V, so that the resulting images merge into one coloured picture.—N. V. Philips Gloeilampenfabrieken.

Transmitting Aerials

(Patent No. 477,914.)

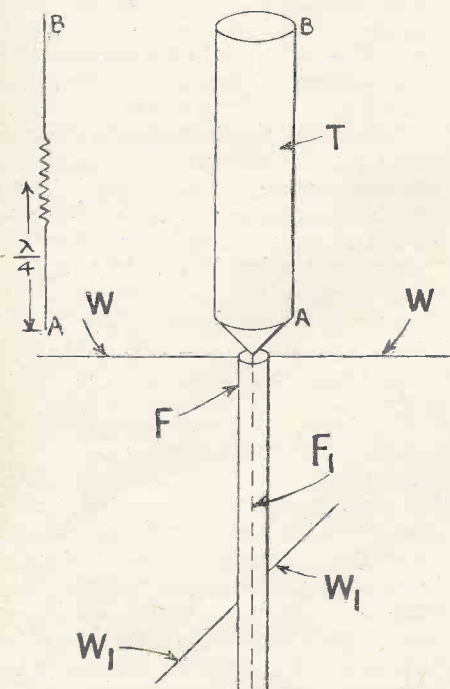As shown in the drawing, the ordinary half-wave wire or rod aerial



Television transmitting aerial.
Patent No. 477,914.

used for transmitting television signals is replaced by a tube T some six or seven inches in diameter, which is directly connected at its lower end to a concentric feed-line F, F₁. A transverse wire W serves to "earth"

the aerial at the working frequency (say, 6.5 metres), and another similar wire W₁ helps to prevent carrier-wave leakage along the outer sheath of the feed line.

The arrangement is designed to "match" the impedance of the feed line to that of the aerial, without the necessity of using a step-up transformer coupling. The latter intro-


—V. Zeitline, A. Zeitline, and V. Kliatchko.

Incandescent Screens

(Patent No. 479,318.)

The usual fluorescent screen of a cathode-ray tube is replaced by a mesh of fine tungsten wire, on which an incandescent image, of high brilliance, is produced by the bombard-

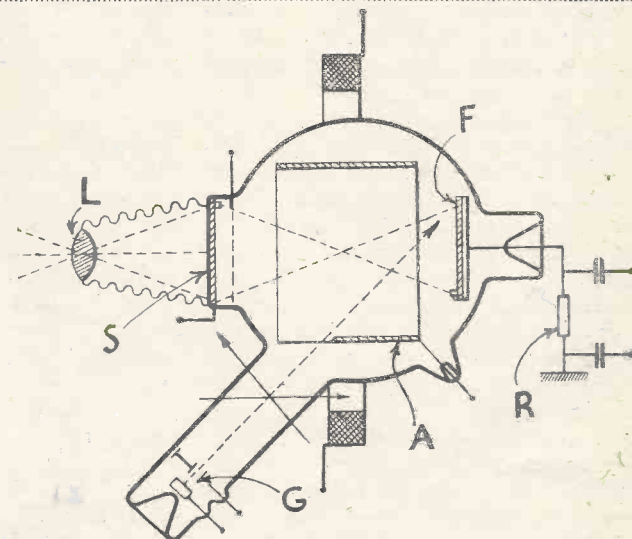Transmitting tube employing fluorescent material on storage electrode.
Patent No. 478,499.



duces a certain amount of selectivity, which is objectionable because, in television, it is necessary for the aerial to radiate a wide band of signals without discriminating between the high and low frequencies.—E. C. Cork and J. L. Pawsey.

Television Transmitters

(Patent No. 478,499.)

It is stated that fluorescent material which emits electrons when scanned by an electron stream is also capable of acting as a "storage electrode," in the same way as the well-known mosaic-cell electrode used in an Iconoscope tube, and therefore forms a simple substitute for the latter.

As shown in the figure, the picture to be televised is projected through a lens L on to a photo-sensitive screen S. The electrons emitted are then focused upon a screen F coated with fluorescent material where, as stated above, an electron image is formed by the charges built up on each elemental area on the coating.

The image charges are swept by a scanning beam from the gun G of the tube, and the resulting currents are taken off through a resistance R and amplified. The action may be varied by causing the scanning beam to produce secondary electrons, which are collected by the anode A.

ment of the electron stream. The metal screen is built up of individual coils of wire, 0.001 in. in diameter wound 1,200 turns to the inch. The ends of the coils are spot-welded to the frame and the assembly is held in one plane by transverse supporting wires.

The screen is first heated to a temperature just below red heat by a local current, or by means of infrared radiation, so as to reduce the amount of work which must be done by the electron stream to produce the required incandescence.—Farnsworth Television Inc.

Summary of Other Patents

(Patent No. 475,928.)

Cathode-ray television transmitter in which the mosaic-cell electrode produces variable secondary emission.—Electric and Musical Industries, Ltd., and H. G. Lubszynski.

(Patent No. 475,999.)

Mechanical scanning system in which a fixed reflector coats with a rotating mirror to cover the image in two (or more) revolutions.—R. G. Wilson and W. D. Silver.

(Patent No. 476,237.)

Cathode-ray tube fitted with a secondary emission electrode and a "storage" electrode, in addition to the usual photo-electric cathode.—W. E. Williams.

Telegossip

A Causerie of Fact, Comment and Criticism

By L. Marsland Gander

EXPANSION of staff is going ahead rapidly at Alexandra Palace and is, in fact, the only visible sign of "Things to Come." During a visit the other day I noticed so many new faces about the studios and corridors that I asked for official figures showing the growth of personnel.

I had a surprise. There are now 280 persons employed on the television staff at the Palace, and approximately 90 are engineers. When the station opened eighteen months ago there were about 150 on the staff.

The chief accession of strength has been in producers. Originally there were exactly five producers who were expected to do everything; the strain was intolerable, the groaning and lamentation awful. Now there are sixteen; yet the hours of transmission have not been greatly increased. The only important extension of programme time since November, 1936, has been the introduction of Sunday transmissions and of outside broadcasts by means of the mobile unit.

I assume, therefore, that with three times as many producers on the job as there were eighteen months ago and only a slight increase in programme time, programmes will improve in quality out of all recognition. Among the new recruits to the producing staff three have had film experience and two stage experience. One, Mr. Fred O'Donovan, formerly manager of the Abbey Theatre, Dublin, has had both stage and film experience and also has the unusual advantage of having acted in television plays already.

Mr. Lanham Titchener, a junior producer, was assistant editor to that French film genius René Clair for two years; Mr. Stephen Harrison, another new junior, worked on such celluloid successes as "Catherine the Great," and "The Private Life of Henry Eighth."

The New Studios

All this is the credit side. But it is now two months since I urged in these columns that the B.B.C. should push on rapidly with the provision of more studio space. Until this is done the producers are hamstrung.

There is yet no sign of a start with the long job of reconstruction and expansion. Why?

This problem is becoming increasingly urgent, the delay increasingly serious. I went into the old No. 2, and I found it was still being used in a lash-up state. Every programme transmitted from No. 2 is virtually an outside broadcast. The thick python-like cables coiled about the floor, a trap for the unwary visitor, are also a symptom of an inexplicable standstill order.

I am told that there is feverish activity behind the scenes, and I can only reply that "the play's the thing." The sands are running out, the three years' guarantee to potential set purchasers is dwindling away. Sixteen British manufacturers are now making sets and producing forty different models between them. No other country has even started to sell to the public. The advantage must not be frittered away because of the national characteristic to build a thing to last for twenty years when its useful life will only be three. Speed up the studio construction, B.B.C.!

"Long-gun" Cameras

By the way, there is a sign of progress in the fact that all the six old Emitron cameras which have seen long service have now been replaced by the new "long gun" type. Have you noticed any difference in the picture? Viewers do not know what a relief to the television engineers that change meant, for some of the older cameras were near the end of their usefulness. Many a time the fate of a transmission has trembled in the balance.

And so, B.B.C., you have got the men, you've got "long guns," you've got the money too! What are you waiting for now?

I saw Sir Noel Ashbridge, newly returned from the Cairo carve-up of wavelengths, inspecting one of the new cameras. Sir Noel is without doubt the chief friend of television in the B.B.C. Cabinet, besides being a member of the Television Advisory Committee. He is a true enthusiast and a significant development is that on the engineering side there is no division between the vision and the

sound staffs. Thus Mr. R. H. Wood is responsible for all outside broadcasts, whether sound or vision, and Mr. R. T. B. Wynn, one of the Broadcasting House seniors, came to the rescue of the mobile unit by having the 100 ft. steel mast formerly used by 5GB transported from Daven-try to Twickenham and to Mortlake.

O.B. Interference

As I have already mentioned in these notes serious interference on the outside transmissions had been caused by interaction between the incoming waves from the mobile unit and the outgoing waves from Alexandra Palace aerial. Use of the little aerial which was specially erected on the summit of the television mast at A.P. to pick up the signals from the van has now been discontinued. Enormous improvement in the quality of reception in the home has been effected by the use of a receiving point at a garage in Swain's Lane, Highgate, about two miles from the Palace. Transmissions from the mobile unit are picked up there on a fifty-foot aerial and piped to the Palace along a balanced television feeder laid for the purpose.

Before this site was chosen B.B.C. engineers scaled the spire of St. Michael's Church, Highgate, which commands a grand view over London, and carried out reception tests in conjunction with the van. These experiments convinced them that it was necessary to establish a receiver somewhere away from the immediate vicinity of the Palace.

Some Bad Luck

What incredible bad luck television has on occasion! A couple of years ago it was a standing joke that at every Press demonstration something went wrong. Now the vision is as reliable as the sound, and on Boat Race day it proved itself more reliable. On the morning of the race a workman put a pneumatic pick through a telephone cable in the Muswell Hill district. Result, the television station was completely cut off from the outside world. The only way Mr. Philip Dorté, in charge of the mobile unit, could communicate with the Palace was by holding up messages scribbled on paper before the camera.

MAY, 1938

HOW THE DERBY WILL BE TELEVISED

Shortly afterwards I was at the Ideal Home Exhibition, Olympia, and Mrs. Neville Chamberlain was inspecting the exhibits. In the television studio specially built there she was to have seen a show televised under conditions identical with those at Alexandra Palace.

At the last moment when all was ready and artists from the ice spectacle at the Coliseum were waiting to begin, all the electric power failed! Mrs. Chamberlain passed through the studio in darkness. Meanwhile on the sets in the adjoining television "parade" all that could be shown was the B.B.C. morning film which daily grows more worn and more tedious. It is all very well to repeat the apology that this film is intended only for trade purposes, but hundreds of people saw it at Olympia and judged television accordingly.

Perhaps the most important fact about the Ideal Home Exhibition was that for the first time in this country television was demonstrated to the public with real showmanship, as it has been for several years both in Paris and Berlin. In some respects the demonstration was superior to any I have seen abroad because not only could the visitor see a studio in action but he could also compare the reception on more than twenty different commercial models seen side by side under anything but ideal working conditions.

There was a lesson for the organisers of the Radio Exhibition which I am glad to hear they have not been slow to learn. I understand that this year's television exhibits will eclipse anything yet attempted. Radiolympia will be the first big occasion for which the B.B.C. will have two mobile units available. The second should be ready by July and is expected to have finished all tests by August.

One unit will probably be stationed at the Zoo, as last year, and the other at Olympia for actual transmissions from a temporary studio there as from the Ideal Home Exhibition.

The Derby

Without a doubt the chief success of the month for television has been the removal of the ban imposed by the Epsom Grand Stand Association on the televising of the Derby. The

secret history of the efforts behind the scenes to bring this about is a story on the one side of magnanimity and on the other of diplomacy.

Sir John Reith, the Director-General, himself first took a hand; but the negotiations were in the main conducted on the B.B.C. side by Sir Stephen Tallents, Controller of Public Relations, and Mr. Gerald Cock, the Television Director. In reversing its previous decision the Grand Stand Association has acted with generosity and foresight and has recognised the wider duty imposed by the fact that the Derby is a national institution. With television at its present stage of development no possible harm could come to the interests of racing—on any argument—by televising the Epsom classic.

At Epsom Mr. Dorté proposes to mount his main camera, a super-Emitron equipped with a 12-in. telephoto lens on the roof of the Royal Stand. With this he will make a gallant attempt to show the distant start. His best pictures should be those of the race from Tattenham Corner to the finish, secured with this same camera. There has already been an anxious conference to decide whether it would be safe to try a switch from this camera to another at the winning post when the horses near the finish.

It has been decided, however, that it would be too risky and the one camera will have to do the whole job. There is a chance that trying a switch-over at such a critical moment might mean that viewers would miss the one thing that matters—the actual finish and the horses flashing past the post.

Coming O.B.'s

Viewers will also see some Derby Eve pictures on May 31 showing pictures of the Downs, the crowds, and the course. Besides the race on Derby Day itself, pictures will be shown of the saddling and weighing-in, and afterwards, of the winning owner leading in his horse. A list of coming events to be covered by the mobile unit makes impressive reading. Here it is:—

- May 14.—Whitney Cup Polo match, from Hurlingham.
- May 15.—Life-saving exhibition, on Judo principles, from Hurlingham pool.

May 22.—Chelsea Flower Show, final preparations.

May 23.—Chelsea Flower Show, private view conducted by C. H. Middleton, Freddie Grisewood, and Elizabeth Cowell.

May 24.—Private view for Fellows of the R.H.S.

June 9.—Trooping the Colours, from Whitehall.

June 24 and 25.—Lord's Test Match.

June 28 to July 2.—Finals Week at Wimbledon.

July 4.—India v. the World, at Hurlingham.

Aug. 6.—World's Swimming Championships, from Wembley.

Aug. 22 onwards.—Whole of the final Test Match.

More Distance Records

More news of long distance reception. Personally, I have been told of good results in North Lancing and Malvern. Delving among B.B.C. correspondence, I found congratulatory letters from Mersea Island, King's Lynn, Eastbourne, Whitstable, Sutton (Ely), Totton (Southampton), Worthing, Rushden (Northants), Harwich, Herne Bay, and Bournemouth. A Bronley listener wrote, with reference to the Wembley International Soccer transmission: "You may be interested to know that two members of the little audience during the match remarked that the ball looked soft; it did not seem to roll properly. We laughed at the time, but read in the paper the next day that both captains complained that the ball was not fully inflated! Was this imagination or is television better than we thought?"

I saw the Head of the River race on a set at home, in Barnes; then went down to the river-bank and watched it in reality; and, finally, entered the B.B.C. television van, at Harrod's Depository, and saw Mr. Dorté wrestling with the task of making the commentary fit the pictures. He was watching two pictures, on the monitor panels, one the picture as actually being seen in the home, the other the view in the next camera waiting to be "mixed in" when the moment arrived.

Our Readers' Views

Correspondence is invited. The Editor does not necessarily agree with views expressed by readers which are published on this page.

Excellent Results on a One-inch Tube!

SIR,

For the past month I have been using a television receiver, designed along lines suggested by recent articles in your journal, employing the R.C.A. 1-in. tube.

I must say that the results are exceeding all expectations, complete programmes being easily followed and enjoyed. The vision receiver employs American type valves and consists of 1 H.F. and 3 I.F. (tuned anode coupling) stages and a single L.F. stage.

Synchronising impulses are separated by means of Mr. Tyers' method employing a diode, and pictures are very steady.

I can definitely advise any readers who do not wish to go to the expense of a full-sized tube, or who have limited voltage at their disposal to make up a set of this nature.

The receiver is being used on D.C. mains and a 250 volts D.C. generator, fed from a 6-volt accumulator, is used to supply the extra voltage for tune base and tube.

The approximate cost of my television receiver is as under:—

	£	s.	d.
Parts for vision set ...	1	18	0
Parts for time base ...	1	10	0
10 American valves ...	2	15	0
2 T ₃₁ Thyratrons ...	2	0	0
913 Tube	1	17	6

£10 0 6

Any readers in the district who would like a demonstration are welcome if they care to make an appointment for an evening session.

R. V. JANSON (Highgate).

Aircraft and Interference

SIR,

Being ideally situated for observing the effect of aircraft on television reception, I was very interested in the paragraph devoted to it in "Scannings and Reflections." But I cannot agree that the interference is due to insufficiently screened ignition systems. In fact, I don't think that the interference has anything to do with the ignition of the aircraft. The interference takes the form of rapid fading of the whole picture—the periodicity of this fading depending

on the position of the aircraft relative to the aerial and Alexandra Palace. If it were ignition interference, it would surely be some kind of white spot effect.

Having observed several hundred instances of this interference, I have noticed that the further the plane is away, the more rapid is the fading (as long as the plane is within a certain angle of A.P. and the aerial) and this fading becomes slower and more marked until the plane has passed over the aerial and out of the angle mentioned before, when the fading ceases altogether, although the craft is nearer the aerial than when the interference was first observed. It is my belief that the whole phenomenon is due to the aircraft absorbing the signal in some way. It would be interesting to hear the opinions of some of your readers interested in this form of interference.

D. S. G. DAVIES (Hendon).

Results with the Low-cost Televisor

SIR,

Many thanks for the trouble which you have taken regarding the valves. I have done as advised. I also take this opportunity of thanking you for the pleasure which has been received by all who have seen the wonderful results of your fine television receiver circuit.

W. BIRKENGER

(North Finchley, N.12).

SIR,

In the hope that they may be of interest to those of your readers who are contemplating building the television receiver described in your issues of October to January last I send you herewith a few comments on the behaviour of the set which I have just completed to that design.

The making of the set progressed without any difficulty and a satisfactory picture was obtained within a few minutes of switching on for the first time. This seems to confirm the claims which were made for its simplicity in operation and suitability for construction by those without previous experience of the building of television apparatus. The lining up of the vision circuits as described in the articles by means of phone signals was quite simple and very little further adjustment was necessary,

while the setting of the time base controls was found to be far less critical than the tuning of any ordinary short-wave receiver.

The set is being operated at a distance of rather more than twenty miles from the Alexandra Palace on a temporary aerial consisting of a plain dipole without reflector, raised only 15 ft. from the ground and badly screened by tall trees. Even with this indifferent aerial a bright and steady picture is obtained on a 12 in. tube, and the need for improving the aerial system arises from the presence of bad car interference from an adjacent main road. Actually this interference provides a good demonstration of the inherent stability of the set, since the picture remains steady without adjustment through an entire programme and even interference so intense as to obliterate the picture practically completely causes no sign of frame shift. With an improved aerial there is no doubt that it will be possible to dispense with one or possibly two of the H.F. stages.

The apparatus was built in the first instance to the original specification, the improvements described in the January issue being deferred until the set was known to be in working order. A D.C. restoring diode has since been added and has resulted in the expected improvement of picture gradation. Fitting of a correcting inductance in the output stage and modification of the H.F. grid bias arrangements are now in hand.

It is perhaps worth while pointing out that the heater winding for the MU2 rectifier required modifying, since that valve as now supplied consumes 2.5 amps. Also the D42 diode requires 0.6 amp. The tube bias resistance R₄₀ had also to be reduced to 25,000 ohms to give the correct bias range for the tube in use.

In conclusion, may I express thanks for this very useful series of articles and satisfaction at the results obtained. The designer is to be congratulated on having produced a set the construction of which can be undertaken with confidence by anyone who is prepared to use reasonable care in following the design and who is capable of carrying out the comparatively simple constructional work involved.

It would be interesting to hear the experiences of others of your readers who have built sets to this design.

L. W. CODD (Addlestone, Surrey).

Trade News of the Month



The Eddystone Frequentite former for high-power transmitters.


IF the British manufacturers continue to produce components for short-wave amateur constructors at the present rate, we in this country will soon have as good a selection as the American amateurs whom we have envied for so many years.

There has been quite a rush of new components of outstanding design introduced just recently, while the recognised American importers are also stocking most of the components which amateurs so badly need.

A Coil Form

A low-loss ceramic coil form is now available from Eddystone which is 5 in. long and 2½ in. in diameter, threaded to take 26 turns of up to 12-gauge wire. This is also provided with 14 holes for leads and tapping connections. The type number of this coil is 1,090, and it is priced at 4s., which is very reasonable considering the size of the form. A suitable sub-base and base are also available.

Practically every amateur at some time or another has used the Eddystone midget condensers for both receiving and transmitting work. A new type of condenser on these lines has now been designed. There are two types, one having a capacity of between three and eighteen-mmfd. and the second with a maximum capacity of 60-mmfd. Both have DL-9 insulation and are suitable for a peak flashover voltage of 3,500. The 18-mmfd. condenser type 1,094 is priced at 3s. 9d., while the 60-mmfd. type 1,093 cost 4s. 6d.

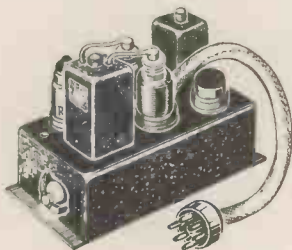

A noise silencing unit can be connected into most types of superhet receivers.

In order to obtain a symmetrical panel layout it is not always possible to lay out the components on the chassis to the best advantage. However, the new Eddystone flexible cable coupling shaft should help very considerably in this respect.

It can be used to drive a condenser switch or resistance, even up to an angle of 90 degrees. The total length of the cable, complete with all fittings, is 5¼ in., and it is priced at 3s. 6d.

Amateurs who have noticed the precision drive made by Eddystone and have found it rather expensive to use many of these on a transmitter, will be interested in a new midget drive of a similar type, priced at 4s. The type number is 1,097, and the dial size is 2½ in. with a fluted knob with a diameter of 1½ in.

A Transmitter Rack


Since the Premier Supply Stores decided to take an active interest in the requirements of British amateurs they



Amateurs contemplating the construction of a modern transmitter will find that this rack produced by Premier Supply Stores is ideal for their purpose. It is built in two sizes, one being 39-in. high and the other 65-ins.

have produced a very interesting range of components and equipment. Their new 19 in. rack is ideal for amateur use, and is at a price which most constructors can afford. The rack only costs 30s., and it will take six 10½ in. panels or a combination of 10½ in., 7 in. and 3½ in. panels. They also supply standard chassis and brackets which fit this rack and all standard relay racks, so that a complete transmitting rack with crackle finished panels and black brackets and chassis costs £4 10s. A smaller model of this rack, which is 39 in. high, is priced at £2 14s.

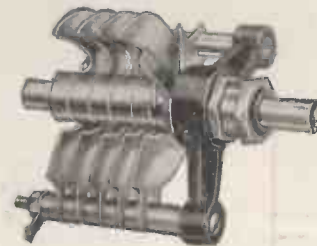It is not always necessary to spend a lot of money in order to obtain a satis-



This is a new design in miniature wide-gap transmitting condensers and is the Eddystone type 1094.


factory microphone, although it is still rather a general impression. Premier have produced a transverse current microphone of the Reisz pattern, complete with the gold-leaf, which is only found in expensive microphones, for 20s. The frequency range is from 45 to 7,500 cycles, while the noise level is extremely low. A table stand, complete with a 9 in. ring, is also available for 7s. 6d.

Noise Silencing


Two interesting items which are very popular amongst American amateurs, are available from Webbs Radio. The first of these is a noise silencing unit which can be attached to any superhet receiver without making modifications to the circuit of the receiver. This unit, which is priced at £3 10s., complete with valves did, on test, filter out car interference, even when the signal strength of the received station was as low as R3. This type of unit should be of particular interest to amateurs who are troubled with local interference from cars.

They also have quite a wide range of Aladdin transformers, which vary in price from 8s. to 18s. 6d., according to type. These transformers provide extreme selectivity and are of the double-tuned type, with the exception of those suitable for crystal filter circuits. In addition to stocking all types of

(Continued on page 317)

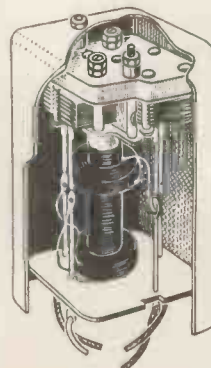

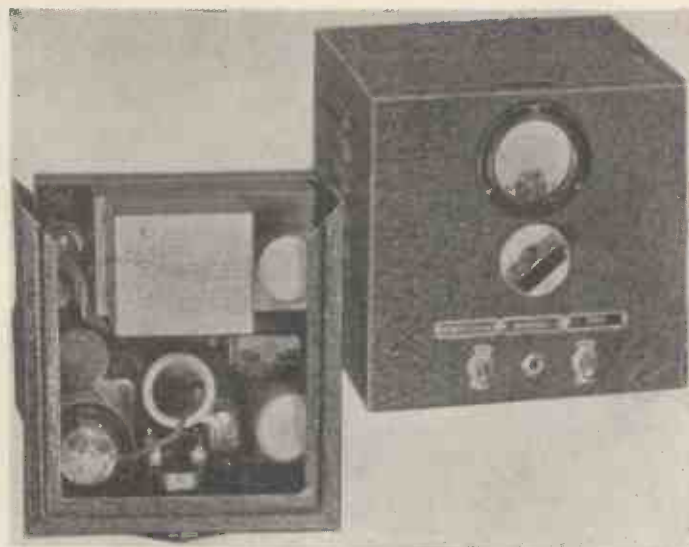These Aladdin transformers are obtainable in all kinds of designs including units for crystal filter circuits.



The lay-out of the components and the symmetrical appearance of the control panel can be judged from this illustration.

MINIATURE transmitters are generally rather unsatisfactory as regards radio frequency output unless they are extremely well designed, but it has been our experience that few amateurs are sufficiently interested to experiment with this type of equipment. There is, however, considerable superficial interest in small transmitting equipment and amateurs would build if a satisfactory design were available.

The transmitter to be described was originally produced in America for aeroplane use and for that reason is extremely small and weighs less than 8 lb.

Amateurs will appreciate that this type of transmitter is not only suitable for use in an aeroplane, but is ideal for temporary use in motor cars, small yachts and for field-days.

The Circuit

The transmitter consists of a single 802 pentode and a tri-tet crystal oscillator and power amplifier operating with an input of approximately 10 watts. It is suitable for operation from a 6-volt or 12-volt accumulator and a vibrator converter or with a battery driven rotary converter whichever is most convenient.

The only dry battery required is for grid bias and this should provide approximately 22.5 volts. It can be seen from the illustration that the transmitter complete with modulator, power pack and smoothing circuit is all contained in a small cabinet measuring $8\frac{1}{2}$ by $9\frac{1}{2}$ by $9\frac{3}{8}$ inches. The only additional accessory is the accumulator which is, of course, a separate unit.

The Transmitter Circuit

The circuit on this page shows how

A 10-watt Aero Transmitter

This interesting two-valve transmitter was originally designed for aeroplane use by THE STANDARD TRANSFORMER CORPORATION of Chicago. It is, however, very suitable for amateur use.

modulator circuit for suppressor grid modulation has been found quite satisfactory in this arrangement.

In the anode circuit of the 802 is the tuned circuit which is not tapped for owing to the perfect screening in the 802 there is no need for neutralising. High-tension voltage is fed into the 802 anode circuit through a normal short-wave choke which is by-passed by .004-mfd. condenser C4.

Constructors should be familiar with the characteristics of the 802 pentode which are as follows:

- Heater voltage, 6.3 volts.
- Heater current, 0.8 amps.
- Anode dissipation, 10 watts.
- Screen dissipation, 6 watts.

When used as a suppressor grid modulated oscillator, the following conditions should be observed:


- D.C. anode voltage, 500 volts.
- D.C. screen voltage, 200 volts.
- Suppressor voltage, 45 volts.
- D.C. grid voltage, 90 volts.
- Peak R.F. grid voltage, 125 volts.

the transmitter section is wired. Between the grid and the cathode of the 802 pentode is connected a crystal of suitable fundamental frequency. Between grid and chassis is the resistance R1 which has a value of 50,000 ohms and automatically provides bias for the valve.

Connected in series with the cathode is the tuned circuit L1C2, C2 being pre-set. The screen voltage is obtained from the mains supply, but dropped down to the correct amount by means of R2 which has a value of 10,000 ohms and is of 2-watts rating.

Modulation

The third grid is connected to the

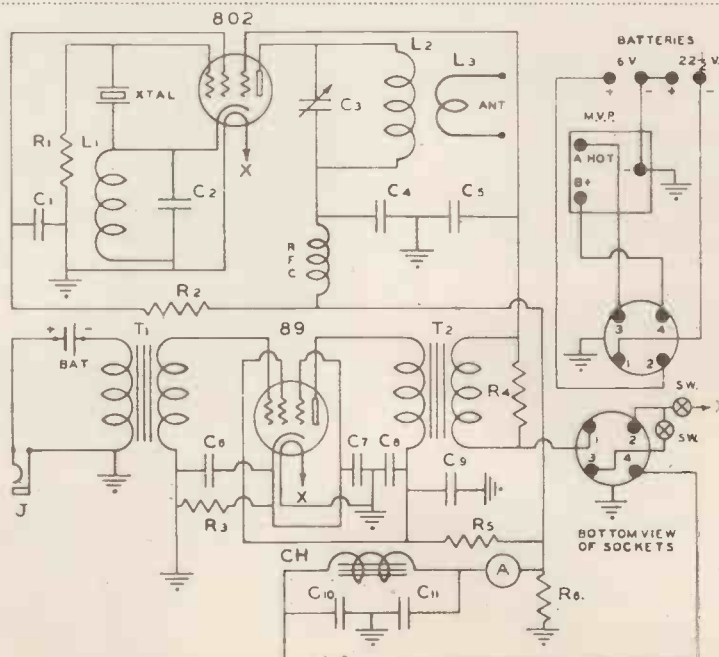

This is the complete circuit of the transmitter plus modulator and smoothing circuit. Only two valves are used.

A 10-watt Aero Transmitter

- D.C. anode current, 22 mA.
- D.C. screen current, 28 mA.
- D.C. grid current, 4.5 mA.
- Grid driving power, .5 watts.
- Grid bias loss, .4 watts.
- Screen resistor, 10,000 ohms.

In the modulator circuit a high-gain carbon microphone is fed directly into the grid circuit of a type 89 pentode via a step-up transformer of 1-70. The energising voltage for the microphone



This close-up view very clearly shows the tuning condenser, microphone transformer and both 802 and 89 valves.

can be obtained from a small bias cell, but in normal circumstances, the low-tension accumulator can be used so as to reduce the total weight of the equipment. This valve has a cathode bias resistance R_3 having a value of 1,000 ohms which is shunted by C_6 , condenser with a capacity of 10 mfd.

The screen of the 89 pentode is connected via R_5 to the main H.T. supply, and this resistor should be of 1 watt rating having a value of 10,000 ohms. It should be noted that the third grid is connected externally to the cathode unlike the normal British type of valve which has the suppressor grid internally connected.

Modulator

Output

When using this circuit the 89 amplifier will provide a maximum output of 2.8 watts, although this can be increased to 3.4 watts by using the same voltage on the screen as on the anode. In normal circumstances the anode current is 25 mA with a screen current of 3 mA.

The components can clearly be seen in the illustration where the 802 is the

semi-screened valve on the left hand side of the chassis. On the right hand side of the chassis is the completely shielded type 89 modulator. Close to the 802 is the anode tuning condenser with the coil L_2 mounted directly behind it. Alongside this condenser and next to the 89 is the optional microphone battery which must be firmly fixed.

A small Bliley crystal is mounted just behind the 802 valve in small insulated sockets. Midget type transformers are required such as those which can be obtained from Messrs. A. F. Bulgin and in front of the 89 valve can be seen the microphone transformer while behind this valve is the midget modulation transformer.

All small components are mounted underneath the chassis while there is space for the Mallory Pack on the chassis if required, but as the accumulator is a separate item, it is quite convenient to mount the Mallory pack with the accumulator.

Battery

Current

It is important that the transmitter be coupled to the power unit and the accumulator by very heavy leads for with a 6-volt battery the current drawn is approximately 7 amperes. This current, of course, is halved if a 12-volt accumulator is employed.

For 70-80

Metres

The original transmitter being designed for aeroplane use has coils suitable for the 70-80 metre bands and in such circumstances L_1 and L_2 have the following dimensions:

L_1 is made up of 24 turns of 18 gauge enamelled covered wire wound to a

total length of 1 in. with a diameter of $\frac{1}{4}$ in. L_2 consists of 31 turns of 18 gauge enamelled wire wound to a length of $1\frac{1}{4}$ in. with a diameter of $\frac{1}{2}$ in. The link coupled coil L_3 consists of 2 turns of insulated wire plugged into the end of the tank coil L_2 .

160 and 40

Metres

For operation on other bands the number of turns required are reasonably proportional so that twice the number of turns would be required on 160 metres or half the number of turns on 40 metres, in either instance a new crystal of the correct frequency must be obtained.

The milliammeter reads the total H.T. supply and with L_3 removed resonance, that is the exact tuning point is indicated, when the meter reading dips downwards as the condenser C_3 is brought into tune. When this point has been reached, the condenser C_2 should be adjusted to give maximum R.F. output.

The presence of radio frequency in the anode circuit L_2 can be checked by means of a small neon bulb or by a 60 milliamp. fuse bulb connected in series with a simple turn loop held close to the coil. Adjustments should be made to obtain maximum light or glow in bulb or neon tube.

With the microphone plug in circuit the amount of glow on a neon tube should increase very violently when the microphone is spoken into. Those who have a radio-frequency meter available will find that maximum modulation is indicated when the R.E. current can be increased by 15 per cent. when the modulator is brought into use. Tone quality is excellent, but care must be taken not to over-modulate the 802 which is quite easily done with the suggested modulator circuit.

Components for A 10-WATT AERO TRANSMITTER.

CABINET AND CHASSIS.

- 1—Steel cabinet type 1033 (Eddystone).
- 1—Steel chassis 8 ins. by gins. turned down 2 ins. (Premier Supply Stores).

COIL FORMS.

- 2—4 Pin threaded type CT₄ (Raymart).

CONDENSERS, FIXED AND VARIABLE.

- 1—.01-mfd type H.V. tubular (C₁) (Dubilier).
- 1—.0001-mfd. type H.V. tubular (C₂) (Dubilier).
- 1—type 900/100 (C₃) (Eddystone).
- 1—.004-mfd 250v. type 620 (C₄) (Dubilier).
- 1—.001-mfd. 250v. type 620 (C₅) (Dubilier).
- 1—type 401 10-mfd. 50 volt (C₆) (Dubilier).
- 1—.01-mfd. type 620 (C₇) (Dubilier).
- 1—.01-mfd. type 620 (C₈) (Dubilier).
- 1—.01-mfd. type 620 (C₉) (Dubilier).
- 1—8-mfd. 500v. type 0281 (C₁₀) (Dubilier).
- 1—8-mfd. 500v. type 0281 (C₁₁) (Dubilier).

CHOKE-HIGH-FREQUENCY.

- 1—2.5 m.h. (Webb's Radio).

CHOKE, LOW-FREQUENCY.

- 1—type LF 2r. S (Bulgin).

DIAL.

- 1—type 1044 with 1012 drive (Eddystone).

HOLDERS, VALVE.

- 5—Ceramic type (Webb's Radio).

MICROPHONE.

- 1—Carbon type TC (Peto-Scott)

METER.

- 1—Flush mounting 0/100 M/A (Bulgin).

PLUGS TERMINALS, ETC.

- 1—Open circuit jack (Bulgin).
- 1—Ceramic terminal strip type 1046 (Eddystone).
- 1—4-pin and plug and socket (Bulgin).

RESISTANCES, FIXED.

- 1—50,000-ohm type 1-watt (R₁) (Erie).
- 1—10,000-ohm type 2-watt (R₂) (Erie).
- 1—1,000-ohm type 1-watt (R₃) (Erie).
- 1—7,000-ohm type 1-watt (R₄) (Erie).
- 1—10,000-ohm type 1-watt (R₅) (Erie).
- 1—60,000-ohm type 1-watt (R₆) (Dubilier).

SUNDRIES.

- 1—Valve screen type VS (Raymart).

SWITCHES.

- 2—type toggle (Bulgin).

TRANSFORMERS.

- 1—type 113 intervalve (Peto-Scott).
- 1—type 111 output (Peto-Scott).

VALVES.

- 1—type 802 (Webb's Radio).
- 1—type 89 (Webb's Radio).

ACCESSORIES.

- 1—Mallory Vibrator H.T. Supply Unit (Webb's Radio).

1938 Valve Designs

Some interesting valve designs have appeared in the last few weeks in types suitable for amateur use. A number of these are described in this article.



This Ediswan triode the ESW-20 is of the low capacity type suitable for high-frequency operation.

HERE appears to be quite an original note in the valve designs produced for amateurs by the British manufacturers. The Ediswan Company are now supplying a valve which is perhaps one of the first of British design to be produced specifically for amateurs at a really competitive price. This valve, the ESW-20, is a small oscillator with a UX base, suitable for a maximum anode dissipation of 20 watts. It has an impedance of 12,500 ohms and an amplification factor of 22. It is, therefore, an ideal doubler or power amplifier.

The ESW-20 also has a 7.5 volt heater, a carbonised anode and tests show that in class-B audio circuits it will provide a speech output of between 65 and 70 watts per pair of valves. This valve is priced at 17s. 6d., and of course has the top cap anode connection as is now usual with modern low-capacity triodes.

Most amateurs know of the internationally famous T-20 valve which has been very popular during the past twelve months. A slightly larger version of this valve has now been produced and appears to be ideally suitable for amateur use. T-40 has a carbon anode Isolantite base and an extremely low inter-electrode capacity. The A.C. resistance of the valve is 8,700 ohms with an amplification factor of 25. As a class-C amplifier it is possible to obtain an efficiency of 75 per cent, giving an R.F. output of 86 watts with a grid driving power of less than 10 watts. The price of this valve is approximately 24s.

A very similar valve to the T-40 is the TZ-40 with a 40 watt anode dissipation has been designed for zero bias class-B amplification or frequency doubler. A pair of these valves in class-B would provide a speech output of 175 watts with 1,000 volts H.T. supply.

A valve which we have used in many of our designs is the old Mullard T-25D.

This, of course, was superseded by the TZ05-20 which is a triode valve suitable for 20 watt anode dissipation. It is now priced at 17s. 6d., and at this figure becomes one of the most economical British valves for transmitting use. It has a 6 volt heater and is suitable for an anode voltage of 400 at 20 metres and is very conservatively rated.

Mullard, incidentally, have now a very complete range of valves suitable for amateur use. There is, for example, the TV05-15, which is very similar to the RK-23 and is priced at 27s. 6d. It has a 12 volt heater and can be used down to 5 metres. Another valve at a similar price is the TZ05-15, which has



The T-40 and TZ-40 both of which have carbon anodes and are suitable for an anode dissipation of 40-watts, are very small in dimensions, being only 2-ins. in diameter: It is, however, possible to obtain an audio output of 170-watts from a pair of TZ-40's and 85-watts carrier power from one T-40.

a 4 volt heater suitable for a minimum wavelength of 15 metres. This pentode valve has a maximum anode dissipation of 15 watts.

The popular RK-20A now has an equivalent in the Mullard range in the TV-135, the price being £4 15s. od. There is also a TZ-135, priced at £4 10s., which is equivalent of the RK-20. It is possible to obtain an efficiency of 78 per cent. with a carrier power of 21 watts when used as a class-C anode modulated radio-frequency amplifier.

We have been conducting some tests on a most interesting Mullard triode valve type TY1-50. This valve has a carbon anode, a 7.5 volt heater, an impedance of 5,250 ohms and a slope of 2 mA./V. The minimum wavelength is .85 metres, while the anode voltage at 2 metres is 1,000 volts. The maximum

anode dissipation is 50 watts. This valve is priced at £3 10s., and as a class-C R.F. amplifier will provide an efficiency of 67 per cent.

We were interested to notice that the Radio Corporation of America had produced a special tetrode valve of extremely high slope for use in television amplifiers.

This valve type 1851 is the first American valve to have more or less typical British characteristics. It is also interesting to note that the General Electric Company have had for some time a valve of this type designated the KTZ41. It has a working slope of 7.5 mA./V measured with a grid voltage of -2.5.

This tetrode has a 7-pin base with the control grid to the top cap and is priced at 15s. Another interesting valve in the Osram range is a rectifier type U52, which is a full-wave vacuum valve with a 5.0 volt heater supplying 250 mA. rectified current with 500 volts R.M.S. on each anode. It is fitted with an octal based so that it is interchangeable with the American valve of similar characteristics.

The KT32 power output tetrode is also available from the General Electric Company, and this is designed for D.C./A.C. operation having a 26.0 volt heater. It requires only 135 volts on both anode and screen, and at this voltage will provide up to 7.5 watts output in class-AB₁ push-pull.

Two absolutely original designs have been produced by Eimac in the KY21 and RX21 valves. KY21 is a mercury vapour grid control rectifier, particularly suitable for use in keying circuits. The RX21 is suitable for a peak anode

(Continued on page 320)



As the maximum grid driving power of this Tungram valve OS12-500 pentode is only 1/10th-watt, it is possible to construct a multi-band transmitter with one of these valves driven by a 6L6 tri-tet oscillator.

AN EFFICIENT AERIAL FOR TRANSMITTING AND RECEIVING

The Double-doublet Aerial

In the December 1936 issue we published the first details of the double-doublet aerial. In view of the advantages and the growing popularity of the aerial we are republishing these details with some additional information supplied by G5ZJ. The designer of the double-doublet aerial is F. R. W. Strafford, G2TD.

A VERY careful study of the elementary half-wave doublet, Fig. 1a with non-radiating feeders preferably of the low-impedance twisted pair, indicates that the best height from the ground for general European and DX working is one half wavelength or approximately 33 feet. If the ground is of the very chalky or stony type the aerial may be as low as one quarter

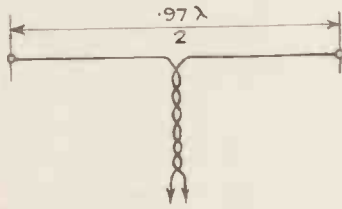


Fig. 1a. Elementary half-wave horizontal doublet.

wavelength or 16 feet on 14 megacycles, since the image patterns due to ground reflections are then much about the same.

The chief disadvantage of the simple half-wave doublet is its directional behaviour, since the polar distribution is as shown in Fig. 1b. An aerial system of this type, which, due to the geography of the writer's garden, is located due east and west, will provide very good contact with Europe, Africa and India, but is extremely erratic and generally poor for America (particularly the U.S.A.). This is quite natural since the theory is fully established in prac-

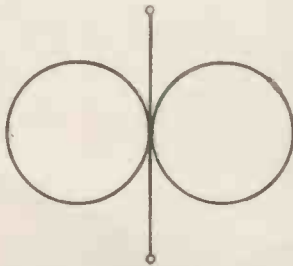


Fig. 1b. Equatorial polar distribution of field strength of elementary half-wave doublet.

tice not only by amateurs, but also by communication companies.

An aerial of this type could be arranged to rotate on some form of mechanical structure so that directional characteristics might be changed at will, purely by a change in the geometry of the aerial system as a whole. While this

method is often favoured abroad it is generally a little too expensive to put into operation in this country, and would probably not be favoured by the vendors of houses in the garden estates of to-day.

The amateur must therefore consider means whereby directional effects may be obtained by simple and economical electrical methods. A vertical aerial is omi-directional, thus distributing its energy uniformly in all directions. This is not economical, particularly for low powered transmitters, since the resultant field strength at points located on a circle of which the aerial is at the centre are relatively weak. Tests over long periods also indicate that simple half-wave vertical aeriels are not very efficient for general low power use even when conditions are good unless the aerial is very well clear of the ground, and this means that a 60 ft. mast is practically essential even at 14 m.c.

The foregoing indicates the reason

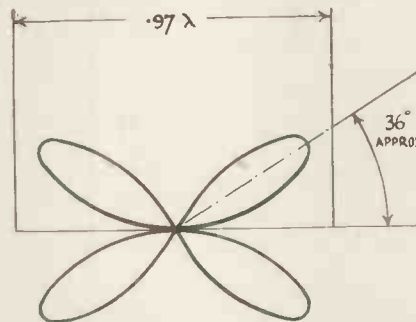


Fig. 2. Equatorial polar field strength distribution for full-wave horizontal aerial.

why a full-wave aerial (66 ft.) on 14 m.c. appears to be so popular. Apart from its useful low-angle radiation components when it is located one half-wavelengths from the ground level, its directivity is modified to that shown in Fig. 2, in which it can be seen that four directive lobes are produced and this arrangement is often used for American DX by those whose gardens runs due east and west, and to whom the half-

wave doublet is practically useless in this direction. (See Fig. 1b).

On the other hand it is also clear that little or no signal is transmitted at right angles to this aerial system. If a full-wave aerial could be arranged in which

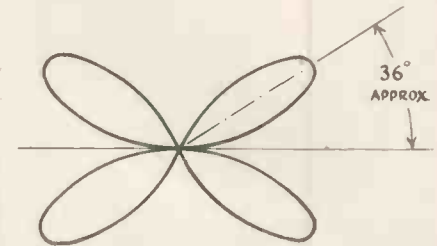


Fig. 3b. Voltage and current distribution of elementary full-wave horizontal aerial and equatorial polar field strength distribution.

the directivity could be changed at will from that shown in Fig. 2 to that in Fig. 1b, a great improvement would have been made. The double-doublet aerial system, not only achieves this result, but actually provides double the field strength of a simple half-wave doublet when it is adjusted to transmit maximum signals at right angles to its own direction. The new system is, therefore (a) as good as a normal full-wave aerial at one setting and (b) twice as good as a half-wave doublet at the other setting.

This change in directivity is achieved by suitably phasing the current distribution in the aerial.

Consider an elementary full-wave aerial as depicted in Fig. 3a. The full line shows the current distribution, while the dotted line represents voltage distribution (the polarity is also shown). This figure shows that the current distribution in each half-wave element of the wire is out of phase. Fig. 3b is the polar distribution of the field strength transmitted (or received) by such a system due to the particular current distribution along its length.

Suppose now the aerial is split into two half waves so that they are end on and without the tops touching, and supposing each half wave is energised in

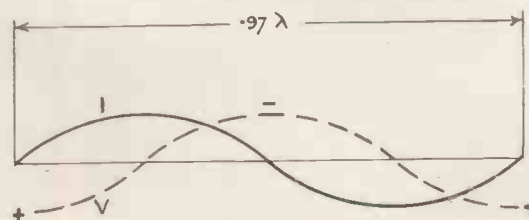


Fig. 3a. Elementary full-wave aerial.

90° Broadside Radiation in Phase

phase. The current and voltage distribution in each half-wave section are shown in Fig. 4a, and are now seen to be in phase with one another. Now study the polar distribution of the field strength (Fig. 4b) and notice how the signal is concentrated in a direction at right angles to the wire. This is even greater than that shown in Fig. 1b for the simple half-wave doublet, and is the means of producing twice the signal

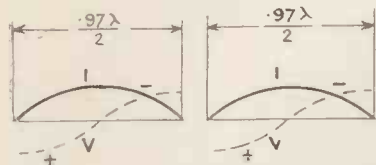


Fig. 4. Two-half waves energised in phase.

strength (for either transmission or reception) along the lines of maximum strength as compared with a simple doublet.

Now this change of the phase of the current in each half wave section of the aerial may be readily achieved by the use of two feeders of the low-impedance twisted type arranged in the centre of each half-wave section. Ordinary lighting flex, cab tyre, v.i.r., etc. for this purpose is known to be used, but is not really suitable for two reasons. Firstly, the surge impedance is of the order of 120 to 150 ohms and does not match the centre impedance (about 80 ohms) of the half-wave section of the aerial. Secondly, the inherent high-frequency losses are quite large and much useful power is absorbed in the feeders and not radiated by the aerial.

A feeder for specific use with half-wave transmitting and receiving aerial has now been produced by Messrs. Belling and Lee, Limited, in which the inherent losses on 14 megacycles are only 1 db. per 100 feet. Furthermore the surge impedance is exactly 80 ohms. With a total feeder length of 100 feet on the experimental aerial at the author's station the losses are quite negligible.

Having erected two simple end-on centre-fed doublets, the twin feeders are brought into the transmitter and connected in series. By reversing one feeder the phase is reversed in one aerial so that the polar pattern is changed as from Fig. 4b, and is thus simply achieved in the transmitting room.

A practical arrangement for operation on 14.3 megacycles is shown in Figs. 5 and 6. The termination of the aerial requires special attention. It is not wise to splay the ends of the feeder for reflection losses may occur and the author also finds that small radio plugs and sockets are better than double-pole double-throw switches since they enable

the minimum splaying of cable connections.

A double-pole double-throw switch is, of course, necessary to change from transmitter to receiver, but here again, the wire of the feeder should be splayed as little as possible and connections should be symmetrical in length. Also the feeder must be used throughout, right to the input circuit of the receiver or coupling coil of the transmitter.

The transmitter coupling coil may consist of three complete hank-wound turns of insulated solid wire the diameter being equal to the final stage tank coil. The coupling coil is then pushed between the two turns of the tank coil nearest the plus H.T. end, and coupled until the stage is normally loaded as with any other type of aerial.

The following details have been compiled by G5ZJ from practical work carried out on the original doublet aerial

When G2TD first showed me the original data on his double-doublet aerial it appeared to be ideal for use in my location. My main aerial must



Fig. 4b. Effect of splitting aerial of Fig. 3a and feeding each half in phase.

always be erected due east and west so that the average aerials which radiate in a broadside manner are of little use except for transmission to South Africa.

The aerial mostly used is a Zepp-fed 138 ft. which has one lobe near enough on North America and another lobe which seems to put a very good signal into South America. I have, however, been in the habit of having a spare aerial handy that would radiate in other directions.

My first tests with the double-doublet showed that it would take the place of my two aerials and that it would perform more or less to the claims of the designer. The aerial was used for many months and was only discontinued

because I gained the impression that despite its good variable directivity the gain in any direction was not up to the 138 ft. aerial.

It was not until I received a considerable amount of conflicting reports about the double-doublet that decided to give it another trial to find if there were any points that had to be noted.

One interesting point that was apparent was that those amateurs who had been using a centre fed aerial found the double-doublet quite satisfactory. This led me to investigate the feeder length.

I found that although the 80-ohm feeder could be of any length if one side was longer than the other, then the aerial worked best in phase and was not at all directional out of phase. This is quite understandable for the different lengths would cause a time lag and effect the correct in and out of phasing.

So this point must be borne in mind, the feeders must be absolutely the same length and symmetrical in every respect. Some interference to local listeners indicated that the feeders were not being fed into a point of exactly 80 ohms impedance, so to overcome this, matching triangles were used. These triangles on 20 metres had to be $4\frac{1}{2}$ in. on either side, after which the aerial worked perfectly.

A further improvement was noticed when the gap between the end of one aerial and the beginning of the other was made the same length as one side of the triangle, that is, $4\frac{1}{2}$ in.

These suggested lengths appear to be influenced by local conditions so that to check these points, it is advisable to erect the doublets quite separately, but in line, of course, terminating each feeder in a single-turn loop.

If the doublets are quite symmetrical they will both draw the same amount of anode current, but if the aerials have been affected by the closeness of the house, for example, the doublet affected will have to be pruned.

I have found without any doubt at all that the full efficiency both in and out of phase will not be obtained until both aerials are tuned up in this manner. Of course, most instances given

(Continued on page 300)

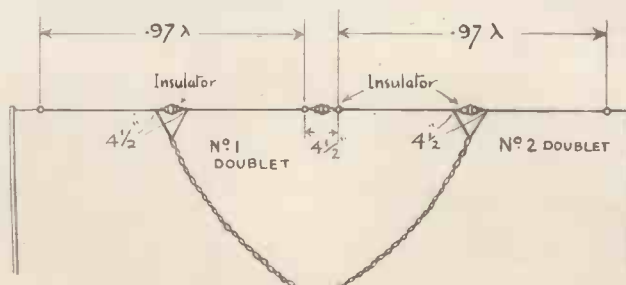


Fig. 5. Typical aerial installation for 14.3 Mc.

Both feeders must be symmetrical even if one has to make one feeder longer than necessary and give it a special "detour" in order to get both feeders the same length. Do not in any circumstances coil the feeder

The Short-wave Radio World

PRESS-BUTTON TUNING

The circuit of the press-button tuning arrangement shown in Fig. 1 is a very interesting one that has been developed by the Howard Corporation of America. The circuit is essentially a super-het converter similar to those used on short-waves. It can, of course, be used with any straight or super-het receiver without making any alterations to the existing set. When used with a straight receiver it converts it into a super-het. When used with a super-het. of any type it converts it into a double-super-het. by virtue of the converter action.

Signals are transferred to the tuned

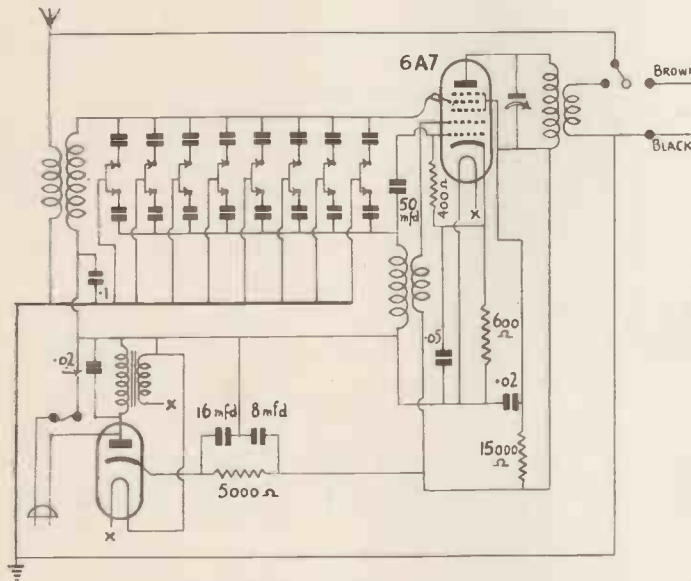


Fig. 1. Remote press-button tuning can be very useful and this circuit developed by the Howard Corporation of America is one that is more than usually effective.

secondary coil which is trimmed by the usual pre-set condenser of average capacity. The control grid of the 6A7 then receives the signal. In addition the oscillator coil then receives the tuned signal in the normal manner.

Both grid and oscillator coils are tuned by means of switched trimmers which are connected to the correct number of push-button switch contacts. The 6A7 then acts as a conventional super-het converter with one exception.

The I.F. frequency generated by the 6A7 must fall within the tuning range of the parent receiver to which the converter is to be coupled.

The two brown and black leads to the right of the diagram are connected to aerial and earth terminals respectively. The I.F. signals generated in the converter are then passed on to the

A Review of the Most Important Features of the World's Short-wave Developments

main receiver. By adjusting the trimmers 8 pre-selected stations can always be obtained by merely pressing the correct button.

REDUCING MAINS NOISE

A rather new idea in filters for insertion in series with the mains lead is shown in the May issue of the American publication *Short-wave and Television*.

The arrangement is shown in Fig. 2 from which it can be seen that the unit is made up of four condensers, two radio-frequency chokes and a small neon tube.

A 500-CYCLE TEST OSCILLATOR

A most useful piece of apparatus has been designed by Don. B. Knock, and published in the *Sydney Bulletin*. It is a test oscillator for the advanced experimenter or transmitting amateur, which has an output relatively free

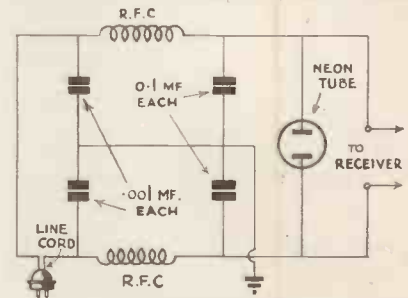


Fig. 2. This type of mains noise filter can be used with any type of receiver.

from harmonics. This simple unit, shown by Fig. 3, has a resistance stabilised circuit giving a good waveform.

The resistance between the anode and the L/C circuit is a great deal larger than the anode resistance of the valve so that the total effective anode resistance becomes nearly a constant value with resultant good frequency stability. If the resistance is high enough just to permit oscillation then the waveform will be exceptionally pure. Attenuation is made possible by means of a potentiometer and the output can be varied from zero to almost three volts peak.

The circuit diagram shows all the values and it is suggested that the oscillator, complete with power supply, should be built in a metal cabinet. The value of the anode resistor depends to a certain extent on the type of choke used, but the average primary of a tapped loudspeaker transformer

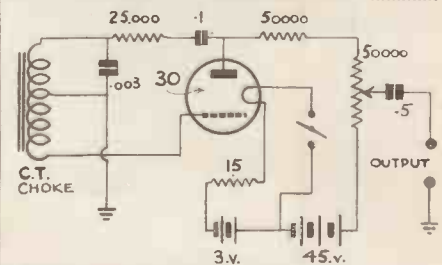


Fig. 3. Service engineers will find this constant tone source of considerable use.

In each side of the mains is connected one of the radio-frequency chokes with a condenser network across each end. The electrical centre of this network is directly earthed.

The two radio-frequency chokes are home made in the following manner. Wind 47 turns of 14-gauge enamel-covered wire on a former 1/2 in. in diameter. The winding length is not important, but the coils should be made in the usual solenoid fashion.

Across the output of the filter, where it is connected to the receiver, is fitted a stabilising neon tube of the 1/2-watt indicator type.

A current of about 15 amperes can safely be passed by these chokes, but should the unit be needed for use with electrical apparatus where a higher current would be required re-wind the chokes with a heavier gauge of wire and double-cotton-covered.

can be used quite well. In such circumstances the resistance value given will be a good average.

Audio frequency output is governed by the value of fixed condenser in the anode circuit and for the frequency

(Continued on page 320)

"The Double-doublet Aerial"

(Continued from page 298)

in the original article will hold good although the feeders will have to be of the same length.

Another point of interest is the method of connecting the feeders to the transmitter. G2TD suggested that one feeder be connected in series with one leg of the other feeder with both feeders taken to the tank coil via a single or two turn link. This works quite well and the system as shown in Fig. 6 is the one I am using at present.

However, the feeders can be terminated in single turn links, both being pushed into the tank coil side by side. To change the phase of the aerial one merely has to reverse one link. The only difficulty with this arrangement, however, is the method to be adopted for connection to the receiver

This double-doublet aerial has been in use for many months with great success at my station, but with the slight alterations suggested.


A test made with ZE1JA indicated just how well the aerial works. With the aerial in phase, that is, giving a 90-degree broadside beam more or less in the direction of South Africa, a field strength of 64 db. was reported. With the link reversed putting the aerial

out of phase, so giving four lobes of 36 degrees, the signal strength in Rhodesia went down to 43 db.

This was most satisfactory and clearly showed that the aerial was working as it should do. The 138 ft.

going on the air with the transmitter.

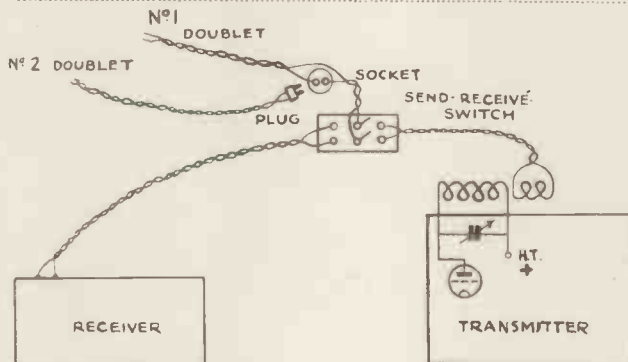On one occasion, during the late evening, ZB1L, in Malta, was worked on a frequency of about 141,250 mc. with the aerial in phase. With the aerial out-of-phase a number of American phone stations were worked all of which were on about the same part of the band. This, of course, would have



A simple arrangement by which the aerials can be used for reception and transmission.

aerial was then tried and the signal strength report was 52 db., so the doublet in phase was much better.

Results were noted on reception and the aerial was found to be very selective indeed. This feature is very useful for it enabled the experimenter to check the aerial without actually

been impossible on the normal type of aerial.

This is particularly noticeable in the morning when working Australian stations for more often than not they cannot be heard on the long-wire aerial whereas they are QSA5 on the double-doublet.

Westinghouse



METAL RECTIFIERS



for unfailing high tension supplies to vision and sound receivers, time bases and cathode ray tubes; distortionless detection; and efficient A.V.C.

Send 3d. to Dept. T. for a copy of "The All Metal Way 1938"

★ Westinghouse Brake & Signal Co., Ltd., 82, York Way, King's Cross, London, N.1.



The Dual-purpose Communication Receiver

This all-wave receiver designed by R.K. BUDGE and KENNETH JOWERS, is already proving very popular among keen all-wave listeners. Some further information on the receiver and also a reliable test report are given in this article.

In this article the A.V.C. and beat-note switch are dealt with. The switch referred to is on the extreme right of this illustration.

RESULTS obtained with the Dual-purpose Communication receiver which was first published in the April issue have exceeded all expectations. While this set was not designed with the object of competing with multi-valve expensive American communication sets, outside unbiased reports indicate that this receiver is about the best value for money that amateurs can obtain at the present time.

Low Noise Level


We have been told that owing to the extremely low noise level and the almost complete lack of valve noise, weak stations can be heard which would very likely be lost on a more sensitive receiver using very many more valves that did have a fairly high noise level.

For this reason, our log book during the past few weeks, showing reception of world-wide stations, indicates a very big percentage of QSA₅ signals, but at low volume level indicating that the receiver is very good for picking up stations from long distances.

As readers will appreciate, during the beginning of April the very severe magnetic storms over Europe, America and Canada caused havoc to short-wave reception, but despite this we were able to contact stations in Burma, India, Malay States and most countries in South America and to maintain consistent two-way communication with the aid of this receiver.

That, in itself, gives a very good idea as to the performance that can be expected from the Dual-purpose receiver.

In order to make quite sure that our good location was not giving us an incorrect impression of this set, we asked Mr. Arthur F. Bear, who is the European and Colonial Representative of the International Short-wave Club, to give the receiver an exhaustive test. He demonstrated it before members of his society at both Brighton and London, and members were in general agreement that the performance was excellent on all wavelengths, and quite easily fulfilled the rather ambitious claims that we made in the last issue. His report is printed herewith, word for word, as it was received from him, and he assures us that the set was tried under perfectly normal conditions, and on aerials that were typical of the average amateur club room.

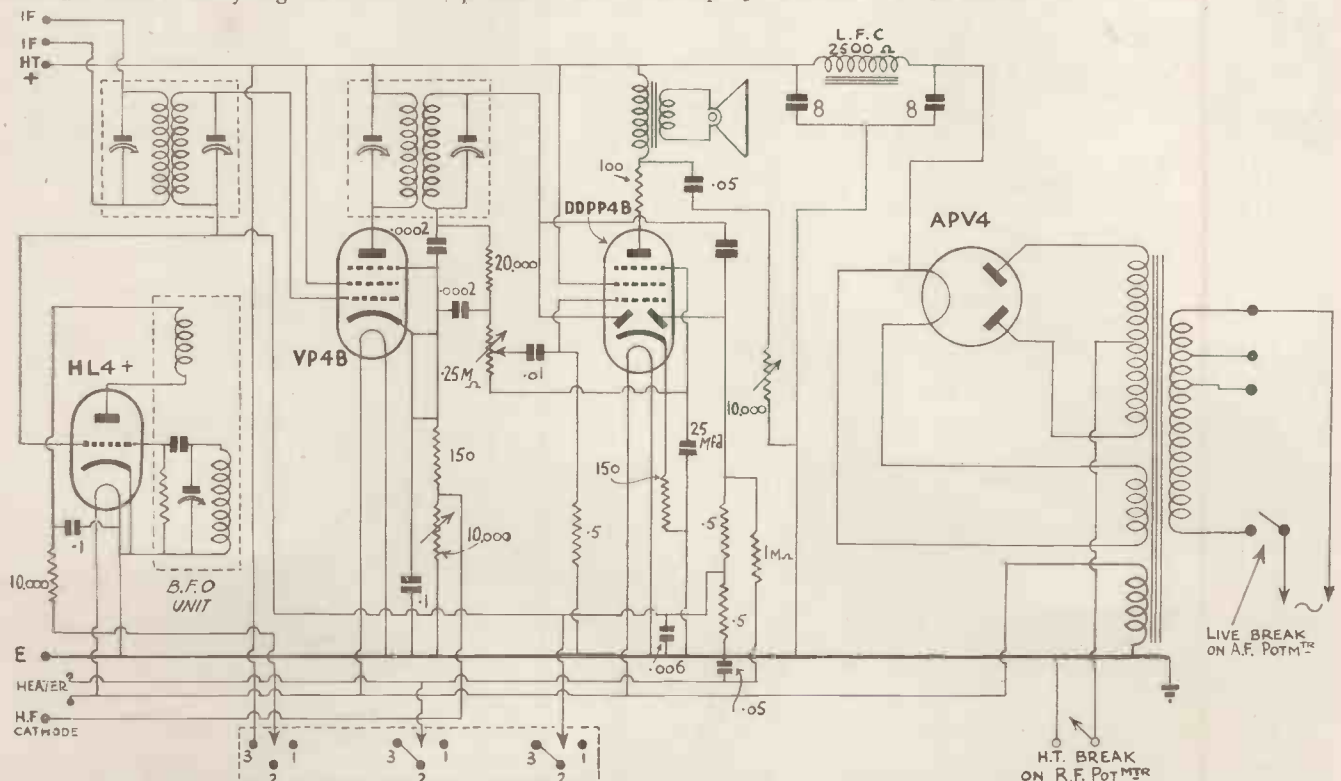

In the last issue we published the complete circuit diagram of the receiver including the ready-wired tuning pack. For the guidance of constructors, however, this is the section of the receiver that has to be wired by them.

Switching

"The receiver has been subjected to rigorous tests at different locations and under varying conditions, and has been found to conform correctly to the published specification. Its performance is most satisfying, especially when one bears in mind the

formance, the receiver was operated off D.C. mains by using a rotary converter.

"On medium and long waves reception left little to be desired, so that the receiver amply lives up to its name of Dual-purpose."



This plan view shows the complete tuner and the layout of the other components. The trimmers in the I.F. transformers are adjusted by the manufacturers and should not need further adjustment.

fact that the cost is extremely low, in fact, the receiver has no comparison in this respect.

"The signal to noise ratio is exceedingly high, and weak signals that were practically unintelligible on a multi-valve commercial receiver, owing to mush and high noise level, could be tuned in with appreciable intelligibility on the Dual-purpose Communication receiver. Both the beat frequency oscillator switch and the method of switching out the A.V.C. action are two very useful refinements for the A.V.C. switch enables one to obtain a true reading of fading, and so afford a correct report.

"Although very quiet conditions prevailed on the higher frequencies during most of the period when the receiver was under test, there were a few days when it was possible to compare results on the 10-metre band with results obtained on other receivers.

"On March 30, some rather good results were obtained, especially during the evening. The 10-metre American amateurs, and the 16- and 19-metre American broadcasters were heard at very useful strength. The following evening results were even better, for several of the American high-fidelity 11-metre stations were heard at around R5 and R6, including stations W9XJL and W9XAZ.

"Excellent results were obtained on most evenings from America on the broadcasting 25- and 31-metre bands, in fact, W1ZAL, W1XK and W2XAS were heard at strengths practically equal to the local medium-wave stations.

"Incidentally, despite this fine per-

Broadcast Reception

This report quite bears out our claims, and for those who are interested in ordinary broadcast reception, we can assure readers that results on broadcast wavelengths are extremely good, with high selectivity and very fine quality, so that the good short-wave performance has not in any way detracted from normal broadcast reception.

One or two readers have raised little problems which are quite easily overcome. The point of the multi-switch in the A.V.C. circuit has apparently not

been fully understood. This switch cuts out the A.V.C. or switches it into circuit as required, while in the third position the A.V.C. action is still out of circuit but the beat-note oscillator is switched into use. On medium waves with the A.V.C. switched out the quality deteriorates on local stations owing to complete overloading of the first stages, so that under no circumstances should the A.V.C. be switched out except when particularly required on short-waves or when receiving CW signals.

Even on short-waves, with most stations the A.V.C. can be left in circuit, but occasionally on very weak transmissions it is possible to increase signal strength by switching out the A.V.C.

R.F. Control

We had purposely arranged for the R.F. and I.F. stages likely to go into oscillation when the I.F. gain control is at maximum. This was done in order to obtain the absolute maximum amount of gain on short-waves. For this reason, on medium and long waves the R.F. volume control should be minutely retarded. If, however, readers wish to prevent this slight oscillation, the cathode-bias resistance in both R.F. and I.F. stages should be increased by 50 ohms each.

Stand-by Switch

Another point of interest is the reason for the H.T. switch which is an integral part of the R.F. volume control. The average amateur transmitter requires some switching system to short-out the receiver without switching off the heater supply. This H.T. switch fulfils that purpose, for when this is in circuit, that is, with the contacts open, no H.T. is applied to the receiver, although the valves remain heated. Immediately the switch is "made" the receiver is ready.

Components for THE DUAL-PURPOSE RECEIVER

CHASSIS AND CABINET.

- 1—Steel chassis finished grey with all holes cut and fitted with terminal strips (Peto-Scott).
- 1—Steel cabinet finished black with all holes cut (Peto-Scott).

CONDENSERS, FIXED.

- 2—.1-mfd. type tubular (Dubilier).
- 3—.0002-mfd. type tubular (Dubilier).
- 1—.01 mfd. type tubular (Dubilier).
- 2—.05-mfd. type tubular (Dubilier).
- 1—.006-mfd. type tubular (Dubilier).
- 2—.8 mfd. type electrolytic 500-volt (Dubilier).
- 1—25-volt 25-mfd. (Dubilier).

COIL UNITS.

- 1—4-band tuner complete with dial (Peto-Scott).
- 1—B.F.O. unit complete type I.F.A. (B.T.S.).

HOLDERS, VALVE

- 2—4-pin VI chassis mounting less terminals (Clix).
- 2—7-pin type VI chassis mounting less terminals (Clix).

HEADPHONES.

- 1—Pair Super Sensitive (Ericsson).

LOUDSPEAKER.

- 1—D.C. type 2,500-ohm field (Rola).

PLUGS, TERMINALS, etc.

- 4—Plug top connectors (Bulgin).
- 1—Jack type P66 (B.T.S.).

RESISTANCES, FIXED.

- 1—50-ohm type ½-watt (Erie).
- 1—100-ohm type 1-watt (Erie).

- 1—150-ohm type 1-watt (Erie).
- 1—10,000-ohm type ½-watt (Erie).
- 1—20,000-ohm type ½-watt (Erie).
- 3—5-meg-ohm type ½-watt (Erie).
- 1—1-meg-ohm type ½-watt (Erie).
- 1—150-ohm type 1-watt (Erie).

RESISTANCES, VARIABLE.

- 1—10,000-ohm potentiometer with switch type J (Dubilier).
- 1—100,000-ohm type potentiometer (Dubilier).
- 1—25 meg-ohm type J with switch (Dubilier).

SWITCH.

- 1—Complete assembly type 143 (B.T.S.)

SUNDRIES.

- 1—Loudspeaker baffle board.
- 1—Mains cord.
- 1—Mains plug type 29 (Clix).

TRANSFORMERS.

- INTERMEDIATE FREQUENCY.
- 2—Type 465 Kc with trimmers (B.F.S.).

TRANSFORMERS, MAINS

- 1—Special type with wire ends model S/1 (New Times Sales, Limited).

VALVES.

- 1—VP4B met (Tungsram).
- 1—DDPP4B (Tungsram).
- 1—HL4 + met (Tungsram).
- 1—APV4 (Tungsram).
- 1—VP4B met (Tungsram).
- 1—TH4A met (Tungsram).

We have made arrangements for a completely wired and tested receiver to be available from Messrs. Peto-Scott, Limited, at a cost of 11½ gns.

With the Amateurs

By G5ZJ

BRITISH amateurs working on telephony do not appear to be making very much headway in the number of zones they have worked and verified. It is the verification, however, that seems to be the difficulty for it is exceedingly hard to obtain a card from some of the out-of-the-way stations. VR6AY is a very good example of this while VO6D is not a great deal better.

G6DT has, I believe, worked 26 zones, while I have just heard from G8MX to the fact that he has worked 26 zones, but what is more important has obtained the required minimum of 20 verifications. Considering that G8MX generally uses about 10 watts and has only just recently obtained his 25 watt permit, his success on short waves shows just what can be done with an efficient low power installation. A photograph of his verifications is shown on this page, and includes some very interesting contacts. Perhaps the best is FR8VX in Reunion Islands followed by the only station in South-West Africa ZS3F. There also appears to be quite a shortage of Burma cards so for that reason XZ2EZ's card is of interest.

These cards do not do justice to the DX that G8MX has worked for during the past few months he has consistently contacted Australia almost every morning even when conditions have been most unfavourable.

In the final stage of his transmitter, G8MX uses a single RK-35 with 500 volts. Modulation is class B with a pair of 46's in a conventional circuit. It appears that the aerial system in use is the main reason for the success obtained by G8MX. Most of his contacts have been made either on a centre-fed W8JK beam or on a conventional two half-waves in phase aerial.

The number of countries contacted on phone using these aerials now exceeds 70 which is very good going considering the generally poor conditions that have prevailed during the year or so that G8MX has been operating.

Many amateurs have asked the simplest way in which they can use a milliammeter in a superhet receiver to act as a tuning indicator. Providing the meter has a scale calibrated from zero to 1 mA. such an instrument will act as a tuning indicator. It should be connected in circuit as indicated by the theoretical circuit shown and adjusted by means of the rheostat until the meter shows a full scale deflection without the aerial connected to the receiver. This rheostat should have a value of between 25 and 50 ohms, but the correct value has to be found by experiment for it will depend on the type of meter used. If the only meter available has a high current reading then similar results can be obtained by connecting the meter in series with the H.T. to all the R.F. and

Some interesting details regarding long distance communication on low power are given in this article while news of the Radio Societies has also been included.

I.F. valves instead of in series with one I.F. valve as shown in the circuit.

I notice that the new Spring Callbook is now available in this country through F. L. Postlethwaite G5KA, price 6s. post free. It is even larger than usual consisting of 284 pages, and includes all stations up to W10XZ, all G3 stations up to G3FB and a complete list of the G8 stations. Most countries of the world are completely up to date, while the map of the United States showing all call districts includes VP7, CM and X regions.

There has been a change in the operating time of the G.E.C. stations, W2ZAD and W2XAF. The following times will be operative until further notice, and have been computed in

owing to the fact that I have been checking some new aerials fed with a new type of low-cost co-axial cable made by Telcon. During this period, I was surprised at the number of countries that could be heard and worked with quite simple equipment. During one week-end, using one of the new transmitters built for amateurs by Premier Supply Stores, I worked no less than 30 different countries on telephony with an operating time which could not have exceeded six hours altogether. This little transmitter consists of a 6L6 tritot oscillator followed by a T-20 in the final stage running with an input of 25 watts. It is modulated by a pair of 6V6 tetrodes in class AB1.

Amongst the countries worked on this transmitter were Albania, Burma, Java, Dominican Republic, Brazil, Phillipine Islands, Chili, Canada, India, Ceylon



These are some of the cards obtained by G8MX, who is now qualified for 20 zone using phone. These cards are all good DX and are but a few of those received to qualify for the WAZ.

British Summer Time. W2XAD operating on 21,500 kilocycles or 13.95 meters will be on the air every day from 11 a.m. until 3 p.m. B.S.T. Operating on 15,330 kilocycles; or 19.56 meters W2XAD can be heard from 3.30 to 10 p.m. B.S.T. Operating on the new channel of 9550 kilocycles, or 31.4 meters, W2XAD will be available to listeners between the hours of 10.30 p.m. and 2 a.m. B.S.T.

W2XAF operating on 9,530 kilocycles, equal to 31.48 meters, is on the air every day from 7 p.m. until 3 a.m. B.S.T. It is hoped that these schedules will remain constant until the 25th September when American Summer Time terminates.

During the past few weeks I have been devoting more time than usual to short-wave transmission and reception

and, of course, almost every European country. This is quite good going when one considers that the transmitter is of commercial design which any amateur can buy over the counter and have on the air in a very few minutes.

There is now a chance of British amateurs picking up ultra short-wave signals from America. The G.E.C. ultra short-wave transmitter in Albany, New York, has been allocated the call-sign W2X01 and is operating on a wavelength of 7.31 metres with a carrier power of 150 watts. It is radiating on Mondays, Wednesdays and Fridays from midnight to 1 a.m. B.S.T. and on Saturday afternoons from 7 p.m. until 9 p.m. B.S.T. The programmes transmitted will be those of W2ZAD.

So far, the most distant report has

Radio Club News

been from Arizona, more than 2,000 miles from Albany, so there is quite a chance that these signals will be heard in Europe.

G2UK, A. C. Gee, has sent me a very good idea for National Field Day for those who are using portable equipment operated from generators driven by an accumulator. Instead of having the starter switch for the generator with the heavy L.T. leads on the operating table which is usually very full up at portable stations, use an old morse key as a



This is the DB-20 pre-amplifier, which can be added to almost any radio receiver and will improve gain by as much as 12 db. A full report on the capabilities of this unit will appear in a later issue.

switch and foot operate it. The South-end group of the R.S.G.B. tried this scheme on last Field Day, and it proved very successful enabling them to make contact with the minimum amount of trouble and delay.

For those interested in programme reception, here are the schedules for Sydney, Melbourne and Perth for the month of May, all times being G.M.T. Sydney, VK2ME operating on a wave length of 31.28 metres will be on the air at the following times:—

Sundays 6 a.m. until 8 a.m.
10 a.m. until 2 p.m.

Mondays 3.30 p.m. until 5.30 p.m.

The second Australian station Melbourne VK3ME uses a wavelength of 31.5 metres and operates Monday to Saturday inclusive from 9 a.m. until 12 mid-day.

VK6ME Perth, operating on 31.28 metres is also on the air Monday to Saturday inclusive, but from 11 a.m. until 1 p.m. As it is always an advantage to have a receiving aerial in the correct location for reception of any particular station, the following details are of interest regarding Schenectady and other stations in a similar area.


For maximum signal at the receiving station from W2XAD or W2XAF the point of maximum signal pick up of the receiving aerial should be directed to a latitude 42 degrees, 47 minutes, 37 seconds north. Longitude 74 degrees, zero minutes, 26 seconds west.

The carrier power on both Schenectady stations is between 20 and 20 kilo-

watts, while the effective carrier power when the Alexanderson panel directive aerials are used is between 200 and 250 kilowatts. The normal carrier power will, however, be increased to 100 kilowatts after June 1st this year.

There are quite a number of Spanish stations operating in or near the amateur bands. These include Tenerife, 40.14 metres; Tetuan, 21.75 metres; Valladolid, 42.82 metres; Vitovia, 42.06 metres; Zaragoza, 42.84 metres; Mallorca, 41.85 metres; Pontevedra, 41.95 metres; San Sebastian, 41.65 metres; and several others which explains just why there seems to be more Spanish stations than ever at the present time. There are also one or two Spanish amateurs who are temporarily commercial, such as EA2BH, EA9A and EA8AE.

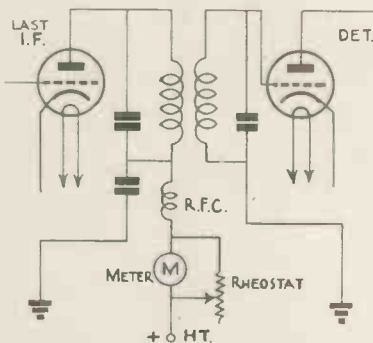I am glad to see that amateurs are being well looked after at the Cairo conference. It appears that the 160 metre band will remain as it stands. There will be a slight readjustment on 80



How to include this tuning meter and its advantages are fully described in the text.

metres, while on 40 metres there will probably be commercial stations between 7,200 and 7,300 K/c, although the amateur allocation will remain as it stands. It also seems quite possible that the 20-metre band will remain untouched, as will be the 10-metre band.

Frequencies between 56 and 58.5 Mc. are to be allotted to television stations, although the authorities concerned can authorise amateurs to use this channel. The frequencies between 58.5 and 60 Mc. are in Europe to be allocated to amateur experimenters.

Similar remarks apply to 112-120 Mc. which is being allocated to the low power stations, although whether amateurs will be able to use these frequencies depends entirely on the administrations concerned.

At the last meeting of the Edgware Short Wave Society, Mr. L. Gregory, G2AI, gave a lecture on the most suitable type of transmitting aerial for long distance work. The new secretary of this society is Mr. F. Bell, and all prospective members are invited to write to him

at 118 Colin Crescent, Colindale, N.W.9.

Two members G3CX and 2AVQ demonstrated transmitting apparatus at the meeting of the Eastbourne and District Radio Society held at the Science Room, Cavendish Senior School, Eastbourne. The Hon. Secretary is J. P. Glickman, of Kersal, Brodrick Road, Hampden Park, Eastbourne, from whom members can obtain full information.

I was glad to hear again from Frank Robb, G16TK, who is the hon. secretary of the City of Belfast Radio Club. He tells me that on 28 Mc. he has worked all continents within a few hours, while the west coast of America has been contacted many times. During the A.R.R.L. contest, he made 100,000 points and worked all W districts on 80 metres, also VEL, VE2 and VE3. He claims that his contacts with XE1A and W6 on 80 metres were the first to be made from G.

The membership of this society has now been increased by over 25 and include 16 full licensed amateurs and 13 with A.A. licences. At their club room they have both A.C. and D.C. mains and are constructing all kinds of apparatus for the benefit of members. Morse construction classes are held every Monday, Wednesday and Thursday evenings and also on Saturday afternoons. The monthly meeting of this society is on the third Wednesday of each month, but all members are supplied with a key to the Club Room. Details of membership can be obtained



Any amplifier giving 7 watts of good quality can be used to drive a pair of these zero-bias type 203Z triodes, which will give an output of no less than 300 watts with only 1,250 volts H.T.

from G16TK, 60 Victoria Avenue, Sydenham, Belfast, N.I.

Our readers are requested to get in touch with H. Turner, at Nunsfield House, Boulton Lane, Alvaston, Derby, for details regarding the Derby Short-wave Radio and Experimental Society.

TRANSMITTING STEP-BY-STEP

By Kenneth Jowers, G5ZJ and
Malcolm Harvey, B.R.S., 1636

A T-40 Transmitter

This is the second in the series of articles on the design of a modern transmitter in easy stages. When the constructor has built the equipment described in this article he will have a transmitter suitable for an input of over 100 watts.

IN our April issue we described the construction of a complete transmitter suitable for use on 40, 20 and 10 metres, with an input of up to 25 watts. The original idea behind this scheme was to enable any interested transmitting amateur to build himself a modern high-power transmitter without

be cleared up regarding the 6L6G and TZ-20 unit.


We have made one modification which we had in mind when originally designing this unit, but thought that it might be rather complicated for the beginner. We refer to the automatic bias in the doubler-stage. We now find this can be

performed by juggling with the grid bias battery. As mentioned on page 256, column three, of our April issue, the off-tune anode current in the C.O. anode circuit should be about 100 mA., which drops to less than 20 mA. when the circuit is tuned to the fundamental or harmonics of the crystal.

In the doubler stage the off-tuned current is over 100 mA., which can be reduced to under 10 mA. when correctly tuned. It will be noticed that when the doubler stage is tuned it will draw the anode current in the crystal circuit from approximately 20 mA. up to the normal working current of 40 to 45 mA.

To check whether the crystal oscillator stage is functioning efficiently, remove the H.T. voltage from the TZ-20, but leave the heaters in circuit. Connect a small milliammeter in series with the 6,000 ohm grid resistor, when it should be possible to obtain a grid current of 20 mA. in this circuit. When H.T. is applied to the TZ-20 anode circuit, then this grid current should drop down to the normal working value of 2 mA.

Connect a single turn loop tightly around the centre of the tank coil L₃ and connect across it a high current flash-lamp bulb. This should light up very brilliantly and, in fact, if the link coil is made larger and tuned to resonance it should be possible to light a 25 watt bulb to full brilliancy, this being obtained with normal input to the TZ-20. By normal input we mean that the TZ-20 is first tuned to minimum anode current, after which the tuned circuit is coupled to L₃ and adjusted so that the TZ-20 draws approximately 25 watts, that is, 50 mA. at 500 volts.

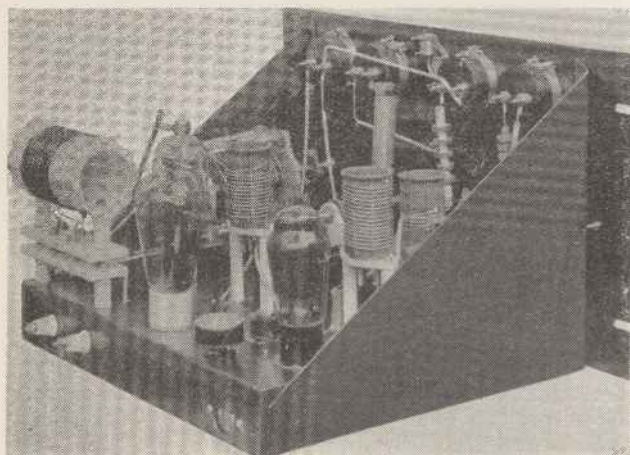

The crystal holder is mounted on two insulated sockets, one of which is connected to cathode. The 6L6 tritode circuit is shown in the foreground.

wasting money on unnecessary components.

For this reason the first section is completely ready for use and in itself is a finished transmitter that is suitable for over half of the amateurs operating in this country. It is also a very suitable circuit for those who contemplate taking up transmission, for it can be operated down to an input of 10 watts, which is generally the maximum permissible wattage allowed to beginners. Without making any alteration to this little transmitter it can be used to drive a third stage which, in turn, is suitable for an input of over 100 watts.


25 Watts Input

Another point in favour of this method of design is that the amateur is on the air immediately he has finished the first section, and can build the second section at his leisure and have it all tested and ready without upsetting the first section. It is then merely a matter of including a link coupled coil between the anode circuit of the TZ-20 valve to convert the transmitter from a 25-watt arrangement up to a 100 watt unit.

However, before going into the construction of the second unit there are still one or two points which remain to

embodied so simply that it is rather a waste of time bothering with dry batteries for grid bias. Consequently, the original circuit for the doubler should be arranged so that the earthy end of the 6,000 ohm grid resistor is actually connected to earth, so cutting out the grid-bias battery. The centre tap from the filament winding should be omitted and in its place must be connected a 400 ohm resistor which has a 20 watt rating.

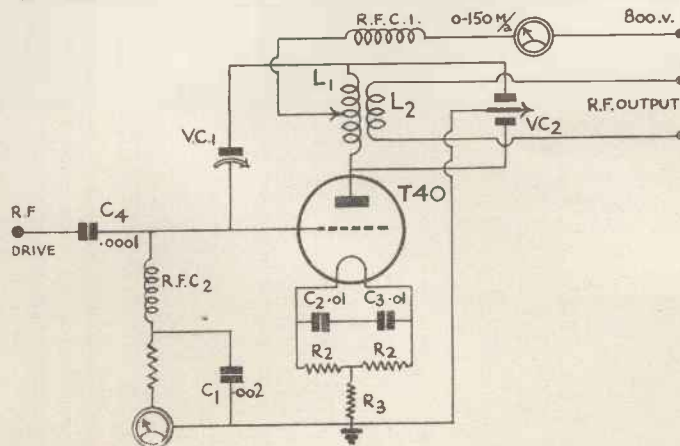This reduces the complications and should enable the constructor to obtain satisfactory results far more quickly and with less trouble than would be ex-



The T-40 triode valve will in this circuit stand an input of at least 100 watts with 800 volts H.T.

3 Wave Bands :: Automatic Bias

After the two stages have been adjusted, and the maximum R.F. output is obtained from the TZ-20 circuit, the transmitter, as it stands, is ready for connection to a conventional type of aerial.

The most suitable point in which to key the transmitter is in the cathode circuit of the 6L6G. Providing a simple filter is connected across the key and a low-value bleeder is in parallel with the CO H.T. supply, then there should be

Coupling


It can be seen that the T-40 unit is connected to the anode circuit of the TZ-20 via a small condenser of .0001-mfd. This condenser, C₄, is shown in both circuits, so as to avoid confusion, but readers will appreciate that only one condenser is used to inter-couple the two units.

The grid circuit is untuned and consists of a radio-frequency choke 5,000 ohm 20 watt grid resistor and a meter


chassis. The buffer condensers and resistors across the heater circuit can be seen in the illustrations of the sub-chassis wiring. The centre point of the resistor R₂ and the conjunction of C₂ and C₃ should, of course, be connected to one side of the bias resistor, R₃.

Neutralising

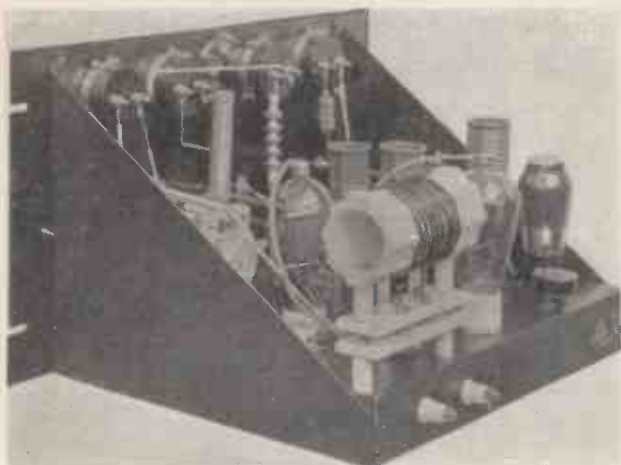Even though the T-40 valve has a very low inter-electrode capacity, it has to be carefully neutralised, so for this



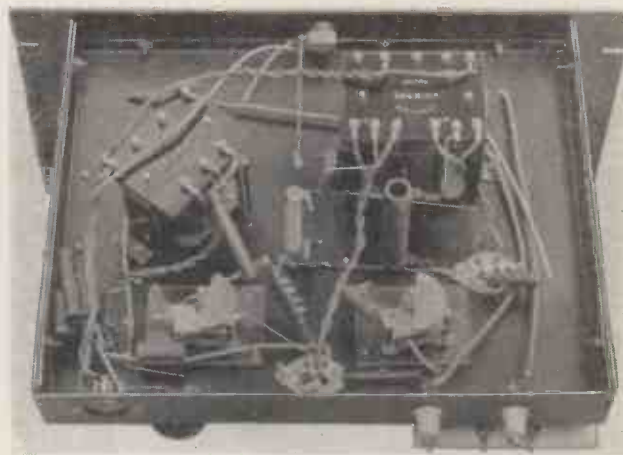The tank coil is wound on one of the new Eddystone low-loss formers which is already threaded. Notice how the tank condenser is mounted on to the side bracket.



Only two filament transformers are needed as one is supplied with two 7.5-volt windings. The auto-bias resistors can be seen in this illustration.

almost complete freedom from key clicks and a chirpy note.

A suitable power pack for this unit and for the T-40 stage will be dealt with in detail in our June issue. Those who require a modulator for phone use can obtain some advance information from this office of a modulator that will be described in the July issue, and will be capable of either modulating the first unit or with a large output valve the second unit.

Now refer to the theoretical circuit and the illustration of the final unit. A T-40 valve is used, as this is, without question, one of the most satisfactory and efficient triodes it is possible to obtain at a reasonable price. It will stand an input of approximately 115 watts, has a carbon anode, is small in size, but is sufficiently robust to withstand severe ill-usage.

The average price for this valve is under 25s., so that the cost is not likely to prohibit amateurs building a modern transmitter capable of world-wide coverage.

The circuit chosen for this T-40 valve is a very simple one of more or less conventional design in view of the fact that it is to be coupled to the previously described drive-stage without having to make any modifications to the existing stage.

reading up to 50 mA. A certain amount of bias is automatically obtained by means of the grid current flowing across this 5,000 ohm resistor, but the rest of the bias required is obtained by means of the current flow across the 400 ohm resistor, R₃. This resistor is actually connected between the centre tap cap of the filament transformer and the chassis, while there is no need to by-pass it to

reason a standard 15-mmfd. low-tuning condenser has been used with all but one of the moving plates removed. This gave approximately triple spacing at a maximum capacity of 5-mmfd. This neutralising condenser, shown in the circuit as VC₁, is connected between the top end of L₁ and the grid of T-40.

The final tank coil, L₁, is wound on one of the new Eddystone low-loss

Components for A T-40 TRANSMITTER

CHASSIS AND PANEL.

- 1—Steel chassis finished black, standard size (Premier Supply Stores).
- 1—Steel panel finished black, 10½ ins. high (Premier Supply Stores).

COIL FORM.

- 1—Ceramic coil form type 1090 with base and socket (Eddystone).

CONDENSERS, FIXED.

- 1—.002-mfd. type H.V. tubular (C₁) (Dubilier).
- 1—.01-mfd. type 691 (C₂) (Dubilier).
- 1—.01-mfd. type 691 (C₃) (Dubilier).
- 1—.0001-mfd. type H.V. tubular (C₄) (Dubilier).

CONDENSERS, VARIABLE.

- 1—Type T15T (VC₁) (Premier Supply Stores).
- 1—Type 1081 50-50-mmfd. (VC₂) Eddystone).

CHOKES, HIGH-FREQUENCY.

- 1—Type 1022 (R.F.C.1.) (Eddystone).
- 1—Type S.W. 69 (R.F.C.2.) (Bulgin).

HOLDERS, VALVE.

- 1—4-pin type ceramic (Amphenol).

KNOBS, ETC.

- 1—Small control handle and scale (Johnson).
- 1—knob type 1044 (Eddystone).

METERS.

- 1—2 in. flush mounting 0-50 mA (Ferranti).
- 1—2 in. flush mounting 0-100 mA (Ferranti).

PLUGS, TERMINALS, ETC.

- 6—Small type fee-through insulators (Johnson).
- 4—1½ in. stand-off insulators (Raymart).

RESISTANCES, FIXED.

- 1—5,000-ohm type 20-watt (R₁) (Premier Supply Stores).
- 1—30-ohm humdinger (R₂) (Premier Supply Stores).
- 1—400-ohm type 20-watt (R₃) (Premier Supply Stores).

SUNDRIES.

- 9—Rubber Grommits ½ in. diameter. (Premier Supply Stores).
- ¼—1b. 10-gauge tinned copper wire (Webb's Radio).
- 36—6 B.A. round head bolts with nuts and washers (Webb's Radio).
- 1—Strip special insulating material 4 ins. by 14 ins. (Premier Supply Stores).
- 1—Strip special insulating material 3 ins. by 6 ins. (Premier Supply Stores).

TRANSFORMERS, FILAMENT.

- 1—6.3 volt 1-A (Premier Supply Stores).
- 1—7.5 volt 2-A and 7.5 volt 3-A (Premier Supply Stores).

VALVE.

- 1—Taylor type T-40 (Webb's Radio).

NOW READY

Premier 1938 New enlarged Illustrated Catalogue, Handbook and Valve Manual! Send 6d. in stamps for 90 pages of Valve Data, Technical Articles, Circuits and Premier 1938 Radio.

PREMIER

SUPPLY STORES

MAKERS OF HIGH GRADE

ALL POST ORDERS

JUBILEE WORKS,
167 LOWER CLAPTON RD.,
LONDON, E.5.
AMHERST 4723

HAM GEAR AT REASONABLE PRICES

CALLERS CAN NOW GET THEIR REQUIREMENTS FROM JUBILEE WORKS AS WELL AS FROM

50 HIGH STREET, CLAPHAM, S.W.4 & 165 & 165a FLEET STREET, E.C.4
Macaulay 2381 Central 2833



THE PREMIER STANDARD RELAY RACK

This piece of amateur equipment is typical of the thoroughness with which we are tackling the needs of the British amateur.

The two racks are constructed of 1 1/2 ins. x 1 1/2 ins. x 3/16ths in. steel angle with panels and chassis cut from 16 gauge steel.

The panels are finished in black crackle, and the chassis and frame in eggshell black finish.

Price:—

67-in. Rack only	30/-
39-in. " "	22/6
10 1/2-in. Panels	4/6
7-in. Panels	3/-
3 1/2-in. Panels	1/6
Chassis and Brackets	5/6

A 10-in. Panel and Chassis and two brackets cost 10/-, and a complete 67-in. rack, with five 10 1/2-in. panels, one 7-in. panel, and one 3-in. meter panel, 6 chassis and 6 pairs of brackets, with all bolts, etc.

Price **£4.10.0** Carriage Forward.

A complete 39-in. rack, with three 10 1/2-in. panels and a 3-in. meter panel, with three chassis, bolts and brackets.

Price **£2.14.0** Carriage Forward.

£5 FOR A NAME!!!

The demand for a reasonably-priced universal modulation transformer suitable for matching any modulator to any R.F. Secondary Load, has prompted us to produce a range of really first-class transformers, which caters for any combination of Primary and Secondary impedances—

But we need a name for them

Send us your suggestion. It may be worth £5 to you, but it must be original, for we cannot use any name now in commercial use.

We make THREE standard sizes. Ratings based on R.F. inputs of up to 50 watts, 150 watts, and 300 watts.

The prices are: 17/6, 32/- and 55/- respectively.

MAINS TRANSFORMERS

Premier Mains Transformers.—Screened primaries 200-250 volts. Guaranteed 1 year. Wire end types.



HT8 + 9 or HT10 with 4 volts 4 amp., C.T. and 4 v. 1 a., C.T. 10/-, 250-250 v. 60 mA. or 300-300 v. 60 mA., with 4 v. 1-2 a., 4 v. 2-3 a., 4 v. 3-4 a., all C.T., 10/- 350-350 v. 150 mA., 4 v. 1 a., 4 v. 2 a., 4 v. 4 a., all C.T., 13/6. 350-350 v. 150 mA., 5 v. 2 a., 6.3 v. 2 a., 6.3 v. 2 a., all C.T., 13/6. Fitted with Panel and Terminals, 1/6 extra. 500-500 volts 150 mA., 4 v. 2-3 a., 4 v. 2-3 a., 4 v. 2-3 a., 4 v. 5 a., all C.T., 21/- 500-500 v. 200 mA., 5 v. 3 a., 6.3 v. 3 a., 2.5 v. 5 a. or 7.5 v. 3 a., all C.T., 25/- 500-500 v. 150 mA., 15/- 1,000-1,000 v. 250 mA., 21/- 1,500-1,500 v. 200 mA., 50/- 2,000-2,000 v. 150 mA., 57/6. Fitted with Panel and Terminals, 2/- extra.

Premier Filament Transformers. Primary 200-250 volts, 1,000 insulation test. 2.5 volt 8 a., C.T., 8/6; 4 v. 5 a., C.T., 9/6; 5 v. 3 a., C.T., 8/6; 6 v. 3 a., C.T., 8/6; 6.3 v. 3 a., C.T., 8/6; 7.5 v. 3 a., C.T., 8/6; 10 v. 3-4 a., C.T., 11/6.

VALVES

AMERICAN VALVES

We hold the largest stocks of U.S.A. tubes in this country and are sole British Distributors for TRIAD High-Grade American Valves. All Conceivable types in stock. Standard types,



5/6 each. All the new Metal-Glass Octal Base tubes at 6/6 each, 210 and 250, 8/6 each. 4-, 5-, 6- and 7-pin U.S.A. chassis mounting valveholders, 6d. each. Octal Bases 9d. each.

EUROPA MAINS VALVES


4 v. A.C. Types, A.C./H.I., A.C./L., A.C./S.G., A.C./V.M.S.G., A.C./H.P., A.C./V.H.P., A.C./P., and 1 watt D.H. Pentodes, all 4/6 each. A.C./Pens, I.H./5/6; A.C./P.X.4, 6/6; Oct. Freq. changers, 8/6; Double Diode Triodes, 7/6; Triode H. ex. Freq. Ch., 8/6; Tri. Grid. Pen., 10/6; 3 1/2 watt I.H. Triode, 7/6.

UNIVERSAL TYPES. 20 v. .18 amps., S.G., Var.-Mu. S.G., Power, H.F. Pen., Var.-Mu. H.F. Pen., 4/6 each.

13 v. 2 amps. gen. Purpose Triodes, 5/6; H. F. Pens. and Var.-Mu. H.F. Pens. Double Diode Triodes, Oct. Freq. Changers, 7/6 each. Full-Wave and Half-Wave Rectifiers, 5/9 each.

BATTERY VALVES, 2 volts, H.F., L.F., 2/3. Power, Super-Power, 2/9. Var.-Mu.-S.G., 4-or 5-Pin Pentodes, H.F. Pens, V-mu.-H.F. Pens, 5/- Class B, 5/- Freq. Changers, 7/6.

SHORT WAVE CONDENSERS

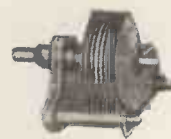

TROLITUL insulation. Certified superior to ceramic. All-brass construction. Easily ganged.

15 m.mfd. 1/6	Double-Spaced
25 m.mfd. 1/9	Transmitting
40 m.mfd. 1/9	Types.
100 m.mfd. 2/-	15 m.mfd. 2/9
160 m.mfd. 2/3	40 m.mfd. 3/6
250 m.mfd. 2/6	160 m.mfd. 4/6

All-brass slow-motion Condensers, 150 m.mfd., Tuning, 4/3; Reaction, 3/9.



10 and 25-WATT TRANSMITTERS

The illustration does not sufficiently convey the merits of this extremely efficient transmitter.

The line up is a 6L6 Tritet, driving a 210 to a very conservative 10 watts on all bands. A complete set of coils and crystal for any one band is supplied.

Anode modulation by a 6J7, driving a 6L6 to 7-8 watts, is more than sufficient for 100 per cent. modulation at first-class quality. Power supply for 200-250 volts A.C. is, of course, included.

Standard Relay rack construction is followed in three 19-in. wide panels and chassis finished black crackle.

Price, with all tubes, crystal and coils (as illustrated).

£15.0.0

The 25-watt rig is a 6L6, driving T20, to extremely high R.F. efficiency, which is anode modulated by a pair of 6V6's in push-pull, class ABL, giving 12 to 15 watts, with negligible harmonic distortion. The construction is similar to the 10-watt TX, being built in our small relay rack, in three 10 1/2 in. x 19 in. units.

Standard black crackle finish.

Price with all tubes, crystal and coils.

£21.0.0

The Exciter Unit

ceramic formers which was introduced only a few days before the transmitter was completed. It is already threaded and supplied with a sub-base and base and will take up to a 12-gauge wire. L₃ in this particular circuit consists of 8 turns of 12-gauge enamelled wire spaced one thread. It is tapped and this tap is

from the four meters are all insulated by means of rubber bushes. These bushes push into a half-inch pole and make quite a tight fit, and are quite capable of standing the 800-volt supply.

Actually, no connection is made to the rotor plates of VC₂, although these should have been grounded to a common

Coil construction is the final item in the design of this transmitter, and it will be noticed that all coils with the exception of the final tank circuit are wound on threaded formers. The first coil is L₁ in the cathode of the 6L6G, and this consists of 5 turns of 14-gauge wire spaced two threads. This will enable the cathode circuit to be tuned with approximately two-thirds of the condenser's capacity. If more turns are used it will be possible for the cathode circuit to be tuned to fundamental frequency, which may have disastrous results to the crystal.


For 40-metre operation the cathode circuit is, of course, short circuited, and L₂ then consists of 14 turns of 16-gauge wire wound to fill the entire former.

For 40-metre operation the tank circuit, L₃, should be 22 turns, wound according to the threading provided.

For 20-metre operation the cathode circuit is brought into use, and L₂ should be wound with 8 turns of 14-gauge wire, spaced the gauge of the wire, while L₃ should be 10 to 12 turns again spaced the gauge of the wire. In the T-20 circuit, L₁ should be 8 turns of 12-gauge enamelled covered wire, centre tapped, while for 40-metre operation this number of turns has to be increased to no less than 26 turns of 14-gauge wire. The link coil, L₂, should be one turn in each case.

With a 40-metre crystal and the cathode circuit unused, the transmitter can be used on either 40 or 20 metres. By making the crystal oscillator a tri-tet arrangement, additional drive is obtained for 20-metre operation, while it also permits quite a high R.F. output on 10 metres. If it is wished to use the lower frequency bands, this will mean modification to the condenser values recommended, for they will be too low in value and, unless precautions are taken, the harmonic output will be high where it is not wanted.

(Continued on page 320)

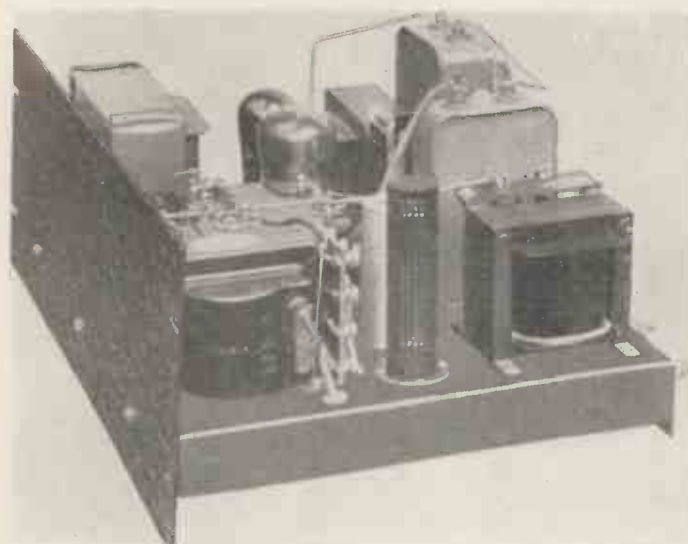

The circuit of the exciter unit which can also be used as a complete transmitter with an input of 25 watts.

taken to 800 volts H.T. via a radio-frequency choke and a meter reading up to 150 mA.

L₂, the link coupling coil, is not shown, for it can either be a single turn loop for coupling on to the following stage, or a tuned circuit suitable for Zepp. feeders. However, we suggest that when L₂ is a single turn loop, that this loop be made of 10-gauge wire, suitably insulated and arranged so that it is spaced off the main coil by approximately $\frac{1}{4}$ in.

Construction

There are several points which may worry constructors when assembling this transmitter. Firstly, notice how the neutralising condensers have been mounted. Two holes, approximately 1 in. in diameter, were cut in the chassis and bolted underneath these holes were two $2\frac{1}{2}$ in. strips of Trolitule. The neutralising condensers are then mounted on the Trolitule so that they come close to their respective valves, but are completely insulated from the chassis. A saw cut should be made in the top of the knob controlling each condenser so that they can be varied by means of a screwdriver.

Coil Leads


It is advisable to connect long leads to the coil holders, which are mounted on Eddystone stand-off insulators before the holders are actually fitted, for it is rather difficult to solder on to the pins with so little space between the end of the pin and the top of the chassis.

The holes that are used to carry leads

point. It was found, however, that the automatic earthing to the chassis was sufficient and did not cause any noticeable difficulty. All leads which pass through the metal chassis should either be bushed or arranged so that they come straight through the centre of a very large pole, so making it quite impossible for a short circuit or a rise in capacity to occur.


Wiring

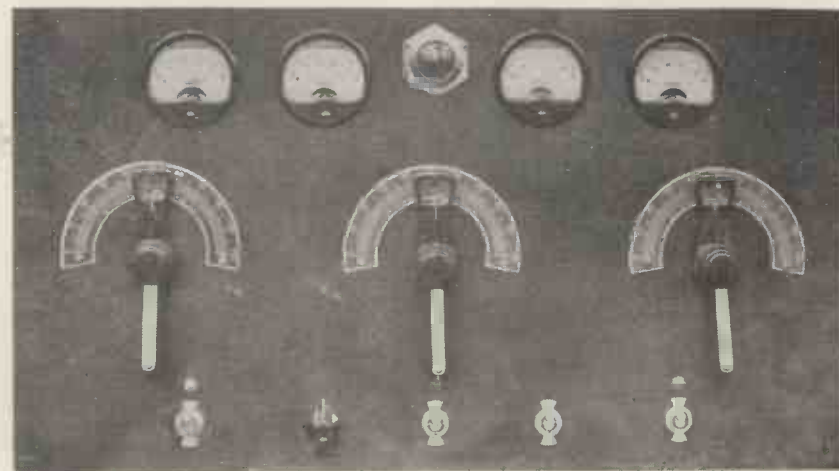Most of the smaller components are mounted in the wiring underneath the chassis, but the larger resistors should be very carefully fixed, so for this reason 12-gauge connecting wire is recommended.



The panel lay-out of the complete 100-watt transmitter with one grid and three anode meters.


For Outstanding Performance

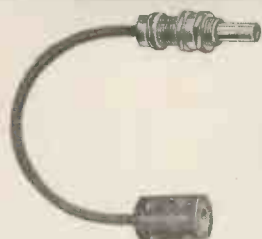


FLEXIBLE COUPLING UNIT.
Cat. No. 1096.
For front panel control of awkwardly plated components. Will drive through 90 deg. perfectly. One hole fixing. For $\frac{1}{4}$ " Spindle. Price 3/6



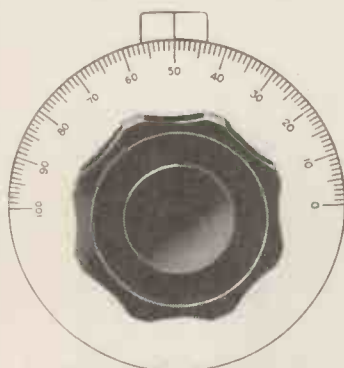FREQUENTITE PILLAR INSULATORS
For transmitting and laboratory work. Ideal for mounting inductances, formers, meters, etc. Tested to breakdown voltage of 30,000 volts. Highly suitable for outdoor insulation. Cat. No. 1049 (wing-nut fitting) Price 1/6
Cat. No. 1095 (2BA Plug and Socket fitting) Price 1/8



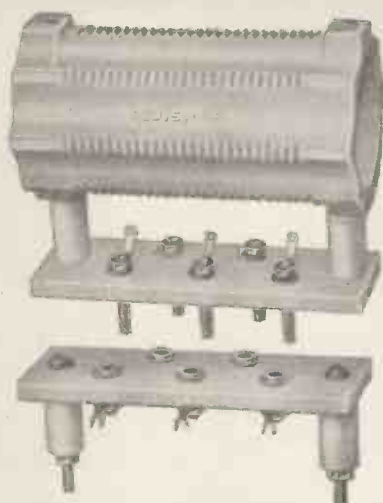PRECISION DIAL. Cat. No. 1077.
For high-grade equipment. White metal 4" scale with machine-cut markings. Instrument type $2\frac{1}{2}$ " control knob. For $\frac{1}{4}$ " spindle. Fitted with single-line indicator. Price 6/9




FREQUENTITE LOW LOSS FORMER
Cat. No. 1090.
Ideal for Amateur transmitters. Former size 5" x 2 $\frac{1}{2}$ ", spiral grooves take 26 turns of wire up to 12 gauge. Winding data supplied with former. Price 4/-

FREQUENTITE SUB-BASE.
Cat. No. 1091.

For mounting former No. 1090. Can be used as base for self-supporting inductances. Power plugs ensure positive contact. Price 3/6

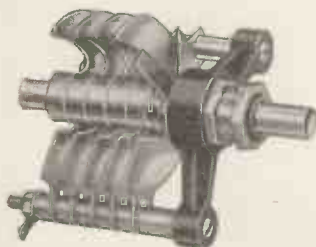FREQUENTITE BASE. Cat. No. 1092.
For mounting former with sub-base. Heavy-duty power sockets for sound electrical connection to former. Price 3/9



HIGH-VOLTAGE MICRODENSER.

Highly efficient. Soldered brass vanes. Constantly maintained capacity; very low minimum 3 mmfd. DL9 insulation. $\frac{1}{4}$ " spindle extended for ganging. Peak flash over voltage 3,500 volts. Easy to gang—capacity matched within 1 per cent. Cat. No. 1094. 18 mmfd. Price 3/9

Cat. No. 1093. 60 mmfd.
For crystal oscillator plate circuit, buffer amplifier, tank tuning up to 100 watts. DL9 insulation. Price 4/6




SLOW MOTION DRIVING HEAD. Cat. No. 1012.
Very useful for Transceivers and Ultra Short Wave Receivers. With 9-1 reduction ratio; pointer moving through 180 deg. Price 3/-



NEUTRALISING CONDENSER
Cat. No. 1088.

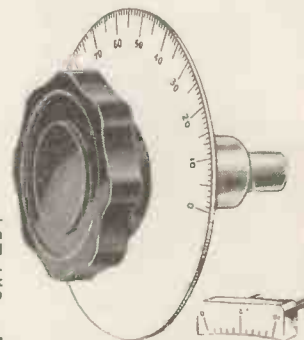For H.F. circuits using low-capacity triodes. Maximum voltage 2,000 volts D.C. Capacity variation 1-8 mmfd. Frequentite pillar insulator mounting, insulated adjusting knob. Price 6/6



PRECISION DRIVE.
Cat. No. 1085.

An instrument type driving movement with slow-motion ratio of 6-1. Vernier indicator allows accurate readings to one-tenth of a division. White metal 4" scale with machine-cut markings. $2\frac{1}{2}$ " instrument control knob. For $\frac{1}{4}$ " M. or F.M. fitting. Price 15/-

SEND FOR 1938 CATALOGUE STRATTON & CO. LTD., EDDYSTONE WORKS, BROMSGROVE STREET, BIRMINGHAM.

EDDYSTONE SHORT WAVE COMPONENTS

London Service : Webbs Radio, 14, Soho St., W.1.



The HRO receiver, an American set produced by National.

Commercial Receivers on Short Waves

Readers interested in all-wave reception will appreciate these notes on some outstanding receivers of different types.

At the present time there are a great number of receivers suitable for communication work on short waves which can be used for normal high quality programme reception as well.

One of the most interesting in this group is the National HRO which is

Selectivity and quality, two features which do not usually go hand in hand, are very good so that on medium waves the receiver gives a good account of itself. The price of this receiver, less power pack, is £49 15s.

British manufacturers have at last realised that there is a very big demand for an all-wave receiver giving a good performance on all bands. A very satisfactory receiver in this class is the H.M.V. 650 which is a 10-valve receiver of unusual qualifications.

In the hands of the ordinary broadcast listener it is capable of picking up stations from all over the world for it tunes from 4.85 to 2,000 metres and what is more important has high sensitivity on these wavelengths.

It is made in two units having the radio section in one and the special output stage and power pack in the other. Two tetrodes in the final stage provide an audio output of 12 watts with real high fidelity. The treble and bass response is controllable by means of variable coil coupling for the top notes and a volume expander for the bass.

On the lowest waveband the cursor travels over a wide arc so that the congested short-wave bands can be combed for stations without any trouble. On amateur wavelengths including 10 and

5 metres it will pick up a large number of stations without any noticeable frequency drift, a feature amateurs will appreciate.

The receiver is very easy to handle and for those who need one receiver for both broadcast and short-wave use with maximum efficiency in both cases this



The lowest wavelength scale is around the edge of this wide tuning scale. The receiver is the H.M.V. 650.

used very extensively by the services in this country. It is a 9-valve instrument covering all frequencies from 1.7 Mc. to 30 Mc. with interchangeable coils. This does not mean, however, changing over a large number of coils for all the units for each band are in one block. In this way the receiver has the advantages of the set with plug-in coils with the advantages of a quick change-over.

The tuning dial is already internationally famous for it embodies the National slow-motion gearing arrangement and a dial calibrated in 500-degrees.


Two stages of pre-selection are built so that image interference simply does not exist. All the I.F. transformers are air tuned and litz wound so giving maximum efficiency. A signal strength meter enables the operator to tell with some degree of accuracy the strength of the carrier of any received signal without having to depend on the ear.



The chassis of the H.M.V. model 650 undergoing bench tests.

H.M.V. instrument can be thoroughly recommended. The price is 24 gns.

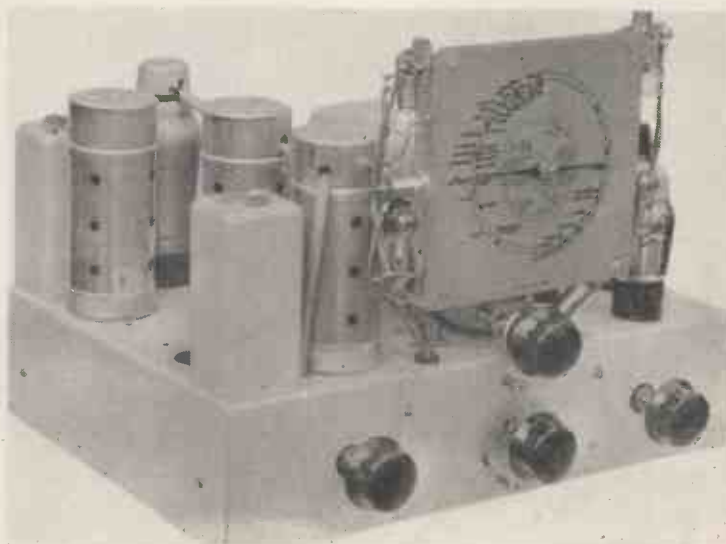
The British Television Supply Co., Ltd., have in recent years been taking



Although this 8-valve B.T.S. chassis only costs 12 guineas it tunes down to 10 metres and has a good performance on that wavelength. A 9-valve model costs £14-14-0

WEBB'S OFFICIALLY APPOINTED DISTRIBUTORS IN
GREAT BRITAIN BY—
HALLICRAFTERS
RME, & HARVEY

NEW SKY BUDDY

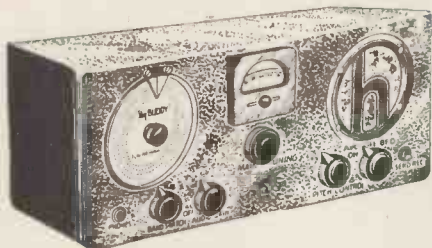

Features.

- 5 Tubes.
- 3 Bands.
- Complete Coverage 18.5 mc. to 545 kc.
- Built-in Speaker.
- Phone Jack.
- A.V.C. Switch.
- Beat Frequency Oscillator.
- Pitch Control.
- Separate Band Spread Dial.

Price £9 0. 0.


NEWRME-501X U.H.F.
Frequency Expander. Frequency coverage 27.8 to 70 megacycles. Built-in Power Pack. Overall sensitivity less than one microvolt. Accurately calibrated.



RADIO AMATEURS' GLOBE, 12 inch diameter, full colour, continental boundaries, produced by Webb's : Post Free

GREAT CIRCLE MAP of the World, 30 inches by 40 inches, full colour, every international prefix plainly marked time zones, continental boundaries.
On heavy paper ... 4/6
On linen, with rollers ... 10/6

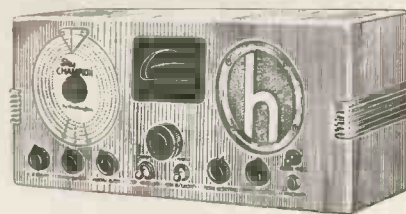NATIONAL 1" C.R.M. OSCILLOSCOPE. Gives graphic picture of operative conditions such as percentage modulation, signal distortion and peak voltage. Unit is self-contained, power supply and controls being built-in. A 50 cycle cycle sweep is provided. Physical dimensions 4½ x 6½ x 8 inches. Price, including all tubes, 230 volt operation, £6 0. 0.



Hallicrafters latest Product.

Features.

- 8 Tubes.
- Complete coverage 7½ to 550 metres.
- 4 Bands.
- Separate Band Spread Dial.
- Individual Coils for each band.
- Inertia Tuning Mechanism.
- Beat Frequency Oscillator.
- AVC Switch.
- Excellent Sensitivity and Selectivity.
- AF Gain Control.
- Band Switch.
- Sensitivity Control.

Price £15 0. 0.

WEBB'S RADIO OFFERS YOU

New Taylor Tubes.
T.40 TZ.40 NOW IN STOCK. First consignment in England came into our depot March 31st. Price 24/- each. Prices now reduced on T.20, TZ.20, now 16/-, 866 Rectifier, 10/-, 866 Junior, 7/-, T.55, 45/-, 203Z, 52/6, 745, 65/-.

Johnson Q Antennae. All types in stock. 5-meter Q, complete, 26/6; 10-metre Q, complete, 25/6; 20-metre Q, complete, 35/6; Johnson Feed-thru Insulators, 1", 8d.; 1½", 10d.

New Johnson Components. Johnson Handles, 4", 3/6; 6", 5/-; John Flexible Shaft, 1/3; Johnson 211 Tube Sockets, 3/6.

Birnback Feed Thru Insulators, 8d. and 10d.

Johnson 6" Feeder Spreaders, 9d. each.

Johnson 10-watt Base-Board Valve Holders, 3/6 (Miniature of the famous 50-watt base.)

Aerovox 75-watt adjustable resistors, wire wound. All Popular Values, 6/6.

Aerovox 200-watt Bleeder Resistance, 11/6.

U.T.C. Varimatch Transformers. VM1, 29/-; VM2, 37/-; VM3, 58/-.

U.T.C. Varimatch Input Transformers. PA.52AX, 23/-; PA53AX, 26/-; PA238AX, 28/-.

Thordarson Transformers. T.2357, S.B. Mike to grid, 8/-; T.5741, 8/-; T.6747, 8/-; T.11M77, 55/-.

Ward Leonard Relays. A.C. operated, D.P., single throw, 30/-.

National Tube Sockets, all types, ceramic, chassis or baseboard, 1/6.

Hammarlund Tube Sockets, all types, Ceramic, 2/6.


Crystal Microphones.
Astatic D.104, hand pattern, 75/-.
Astatic GL5R, with band switch and table stand, £5 10. 6.

Receiving Tubes.
Raytheon First grade Receiving Tubes in glass and metal, all types, from stock, including 6L6, 6L6G, 6V6, 6V6G, 6G5, 25L6, 6J5G, 6E6, 6A6, 6A3, 6A6, 6A3, 6Q7G, 6R7G, all 7/6. Most other types, 6/6.

Special Line.
20 henry 120 milliamp. L.F. Chokes, Ex-Government. Cost approximately £2 each. To clear, 5/6d. Post, add 6d.

New Literature.
RCA Transmitter Tube Handbooks, 1/3.
New Taylor Tube Manual, 6d.
New Thordarson Transmitter circuit manual, 9d.
A.R.R.L. Log Books, 1/8.
A.R.R.L. Hand Books, 1938, 5/6.
Jones Hand Book, 1938, 7/-.
Radio Telephone Hand Book, 3/6.
A.R.R.L. Calculators, all types, 1/-.

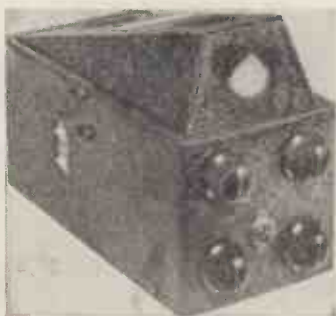ALL McELROY KEYS REDUCED IN PRICE. Famous McElroy Standard "Bug" reduced from 38/- to 27/6. 1938 Model de Luxe Bug, 50/- reduced to 38/-. New Junior Bug, reduced from 22/6 to 17/6. McElroy Straight Key, latest model, heavy cast base, large contact. Reduced from 10/- to 7/6. McElroy Hummer, 1,000 cycle, mechanical oscillator for morse practice, again available from stock, 10/-.



WEBB'S 14, SOHO ST., OXFORD ST., LONDON, W.1
RADIO 41, CARRS LANE, BIRMINGHAM

ALL POST ORDERS TO LONDON.

PHONE: GERRARD 2089.

Cossor :: Hallicrafter

an active interest in the sets needed by amateurs. Having already been manufacturers of high grade radio sets for a number of years they have been able to combine the needs of the amateur and

an output of 7-speech watts into a high-fidelity loudspeaker.

Octal valves are used throughout which can be of either the British or American types. The price of this inter-

works well down to 13 metres is the new Cossor 6864, a six-valve superhet covering four wave-bands. This receiver is again of the rather better class family receiver designed in the first instance for broadcast reception with a wide short-wave coverage in addition.

Our tests on this receiver show that any amateur would be well pleased with the results obtained on the short waves without considering the performance on the broadcast wavelengths.


The 20, 40 and 80 metre amateur bands are covered, while short wave broadcast station down to 13 metres can be received with good reliability. On the broadcast wavelengths tuning is very sharp, while quality is well above the average.

A wide vision tuning scale has been included so that the short-wave listener will not have any difficulty in tuning in the amateur stations on the 20, 40 and 80 metres channels.

This receiver is one of the best so far produced by Cossor and at 16 gns. is good value for money. A point we must stress, however, is that the short-wave performance is very much higher than with the average 6-valve receiver.

A new receiver has just been produced by **The Hallicrafters**, of Chicago. We have been testing this receiver over a long period and have come to the conclusion that it is the best Hallicrafter receiver so far designed. This does not include, of course, the special Hallicrafter model SX-17

The Challenger model SX-18 is a 9-valve instrument designed for amateur communication use from 7.85 metres upwards. It has 5 wavebands up to 550 metres and includes a special method of band-spreading. In addition to the main tuning dial which is carefully calibrated there is a second dial with 1,000 degrees of continuous scale. This enables amateur stations to be logged on the 10 and 20-metre bands for example so that they can be retuned in at any time with-

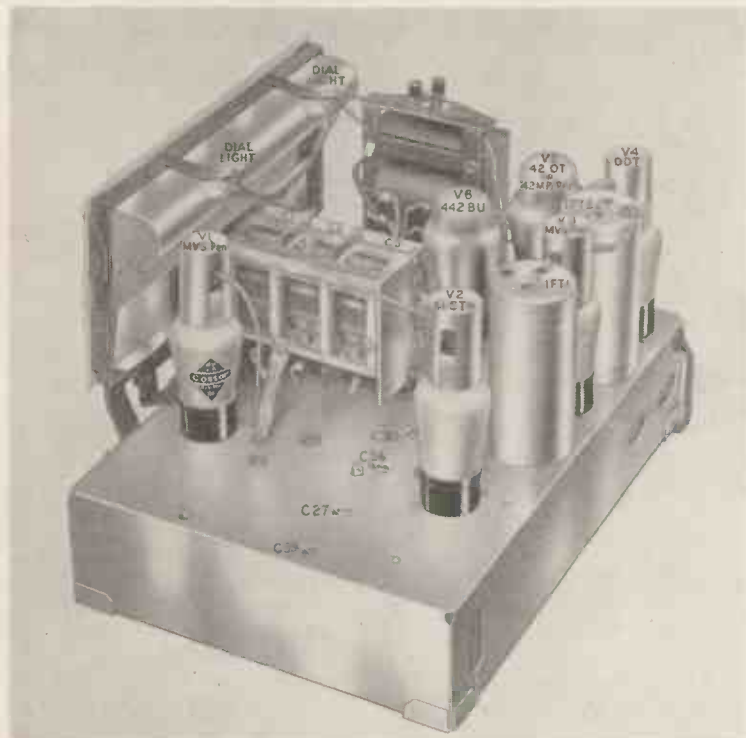

This is the chassis of the new Cossor 6-valve receiver which tunes down to 13 metres.

the broadcast listener and to produce some receivers suitable for both classes of work.

Their 8-valve all-wave receiver embodies many interesting features in a particularly effective circuit having a

esting receiver is 12 gns. less the loudspeaker, so that it is one of the cheapest multi-valve receivers of its kind.

On test the performance was equal to many American communication receivers designed for use on short



A plan view of the new Hallicrafter which includes infinite image rejection.



On the right hand side of the chassis can be seen the 1,000 degree band spread dial. This is another view of the Hallicrafter Challenger model SX-18.

signal-frequency stage on all wavelengths down to 10-metres.

The second detector is, of course, the usual diode followed by a triode amplifier, phase inverter and two 6F6 pentodes in R.C. coupled push-pull giving

waves only, while the medium waves were quite free from image interference.

For those who wish for a cheap multi-valve set at a moderate price this B.T.S. receiver seems to be in a class of its own.

A good family all-wave receiver which

out there being any doubt as to the calibration.

Another fine feature included is infinite image rejection which is the first time we have come across such a scheme

(Continued on page 320.)

SOUND SALES

Special TRANSFORMERS

FOR USE WITH

**CATHODE RAY
EQUIPMENT**

AND

**HIGH VOLTAGE
TRANSMITTING
APPARATUS**


We illustrate our model Tel. EHT., for 200/240 volts at 40/100 cycles. Secondary output 1,750 volts at 20mA.

PRICE
£2-18-6

Our New 56-page Catalogue includes many new products of special interest to readers of this Journal. When sending for your copy, please enclose 6d. P.O. or stamps.

SOUND SALES LIMITED

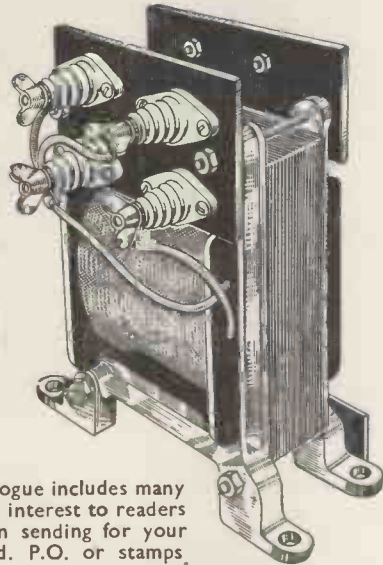Marlborough Road, Upper Holloway, London, N.19
Phone: Archway 1661-2-3 (Contrs. to G.P.O., etc.)



**ELECTRADIX
BARGAINS**


We have the biggest stock of meters, Chargers, Rectifiers, Rotaries and Switch-Gear for special jobs in London, and build to any specification.

INSTRUMENTS FOR ALL PURPOSES. Amps, Milliamps, Micro-amps, Volts, Millivolts, Ohms and Megohms, all accurately measured by the 50-range "Dix-nemeter." A compact moving coil, Precision Fault Locator, 55/-. Type "S" Valve Analysers. Panel has M.C. Meter with rectifier for A.C. All ranges. Adaptor on cable and prods. Fully guaranteed, £5. **MICRO-AMMETERS** for grid current, etc., 0 to 50 micro-amps, full scale, 50 mV. moving coil, 1,000 ohms, flush panel, 2½ in. dial, 40/-. A.C. Rectifier and Chargers for change-overs. Switchgear and autos made to customers' specification.



SELECTOR RELAY SWITCHES.—As illustrated. 8 arms of 25 ways each. Relay solenoid operated for distant control. As used in Tote and Auto 'phone exchange. With Contacts, unused, 10/-. **RELAYS.**—For tiny currents from light cells or for tuned circuit cells. Moving Coil pivoted, work on 50 micro-amps. Half usual price, 60/-. Lightweight type D, 2,000 ohms, 5 m.a., 10/6. C.U. 6-volt Relay, 5/-. 25-way Auto. Heavy current Relays for Transmitters, American, 7/6. Sounder type, 15/-. Creed polarised 2-way Relays, 30/-. Magnetic Key Relay, 15/-. **LIGHT DUTY SWITCHES** for Wave-change and Semi-rotary D.P.C.O., 6d. R.A.F. Switch Boxes for 3 circuits, rocker type, 1/3. Yaxley and Rex Wave-change, D.P., 3-way, roller contact, new, 1/3. Bulgin 3-point Wave-change, 9d. Tunewell

S.P. on-off semi-rotary, 8d. **MAGNETIC SWITCHES.**—Automatic. 2 to 4 amps., 7/6; 6 amps., 10/-. 10 amps., 12/-. 15 amps., 14/-. 20 amps., 16/-. 4½ ozs. 5 m.a. model control. Relays, 8/6. Venner 15-day Time Switches 21/-. **STUD SWITCHES.**—Slate panel 5 in. x 5 in., with 20 studs, two contact arms, ring and knob 5/6. 7-stud on ebonite with plug, 1/9. Yaxley wave change, 2-gang with knob, one hole, 1/2. Revolve Power Plugs, 15 amp., shrouded panel wall, two pairs on iron box, unused, 10/-. **SWITCHES.**—For 50 amps. Charging or arcs. D.P. change over. **STEEL CABINETS.**—Welded angle steel frame, detachable panel sides and back of 16 gauge. Front grid door, hinges and lock. Top panel for three meters. For Transmitters, Amplifiers and high voltage Test gear. Grey enamel, 57/6. Aluminium ply Cabinets, copper lined, front opening for panel, 8½ in. x 8½ in. with side door. Overall size, 18 in. x 18 in. x 11 in., grey enamel, only 30/-. **AERIAL RADIATION METERS.**—Flat panel, 2½ in. dial, hot wire, 0-500 mA., 7/6; 0 to 1 amp., 10/-. 0 to 2 amp., 12/6; 0 to 2½ amp., 12/6. 3 in. dial ditto, 0-4 amps., 21/-. **TURNER MOVING COIL THERMO-JUNCTION R.F. METERS.**—2½ in. dial, flush, 0-½ amp., 30/-. 0-12 amps., 35/-. **TRANSMITTERS, MORSE AND SIGNAL KEYS.** Royal Air Force model, balanced action, solid brass bar, tungsil contacts, indicator lamp. Type KBSL, a guinea key for 7/6. Police Patrol Keys, 21/-. Ship Keys, 25/-. Quad Keys, 30/-. Ask for special illustrated Key List "K.T."

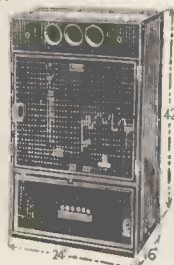

ELECTRADIX RADIOS, Send stamped addressed envelope for our New Sale List "T.S." which includes over 1,000 other bargains.
218, UPPER THAMES ST., LONDON, E.C.4 Telephone: Central 4611

**ELECTRON
OPTICS IN
TELEVISION**

**With Theory and Application
of Television Cathode-ray Tube**

By I. G. MALOFF

Research Division, RCA Manufacturing Co., Inc.,
Camden, N. J.

and D. W. EPSTEIN

Research Division, RCA Manufacturing Co., Inc.,
Camden N. J.

299 pages 9 x 6 Illustrated 21/- net.

THIS important new book develops the theory of electron optics and its most useful application — the television cathode-ray tube, emphasizing those phases of the subject with which the authors have had first-hand experience at the Research Laboratories of the RCA Manufacturing Co., Inc., Camden, N.J. Following a brief description of a complete cathode-ray television system for the purpose of clarifying concepts and terms, the book covers in Part I the theory of electron emission and electron optics and in Part II the problems encountered in designing tubes, practical and economical to construct and capable of producing satisfactory television pictures when used with practical associated apparatus.

Chapter Headings

Preface	Defects of Electron-Focusing System of TCR Tubes
Introduction	Magnetostatic Focusing
Part I. Electron Optics	Part II. Television Cathode-ray Tube
Fundamental Concepts	The Electron Gun
Electron Emission	Deflection of Electron Beams
Analogy between Electron Optics and Light	Luminescent Screens for TCR Tubes
Motion of Electrons in Axially Symmetric Electrostatic Fields	Classifications, Rating and Characteristics of TCR Tubes
Electrostatic Electron Lenses	Accessories
Electrostatic Lenses of Television Cathode-ray Tubes	Vacuum Practice
	Index


McGraw-Hill Publishing Co. Ltd.

Aldwych House,

London, W.C.2.

A Low-loss T20 Output Stage

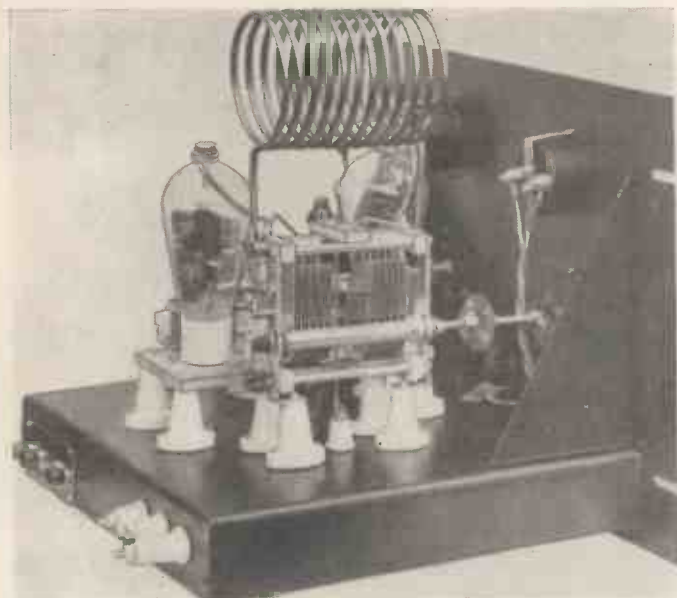In order to obtain the maximum efficiency with modern valves it is well worth completely rebuilding the output stage of the transmitter as is described by G2HK who has built this push-pull T20 arrangement.



The tank circuit and method of mounting the tank condenser can clearly be seen in this illustration.

with high power and exceptional location or good conditions, this rather proves the inaccuracy of the belief, for even during the bad black-out of short-waves during the Easter holiday, I was still able to maintain contact with DX stations such as XZ2EZ, in Burma, and many South American stations.

Construction

Now for a few words on the construction of the input stage. In order to have complete screening between the sub-amplifier and output stage, I have used a heavy gauge steel chassis and panel made for me by Premier. The components are mounted above the chassis on Trolitule insulation; in this way I was able to overcome the difficulty of drilling heavy steel, while at the same time the layout was highly satisfactory.

By mounting the components well off the chassis, leads were kept very short, so further helping to reduce the percentage of loss. The tank condenser, VC2, is mounted on four stand-off insulators, by means of four little brass brackets which have to be home-made. The two T-20's are mounted alongside this condenser on a strip of Trolitule in addition to the by-pass condensers C2 and C3 and the fixed centre-tap resistance, R3.

On the extreme left of the chassis can be seen the plug-in grid coil with a
(Continued on page 318)

WITH modern high-slope low capacity valves, it is well worth while forgetting conventional lay-out and a symmetrical panel appearance in order to obtain the most efficient circuit and component arrangement. It is possible to obtain a very high degree of efficiency without using expensive components and providing care is taken and a little ingenuity is used in the method of construction.

The T20 Triode

Without question, the most popular valve in this country at the present time is the Taylor T-20 which, despite its low cost of 16s., is suitable for 10 watt low power transmitters, while it can be used up to 50 watts if so required.

I have been using a valve of this type for a considerable time, in fact, since they were introduced in America. Even in a normal circuit, without any special precautions, they provide considerably more R.F. output than any similar type of triode, such as the 10, or 801, but it was not until a special circuit and layout was used that the real advantage of this type of valve became apparent.

Despite the low capacity of the T-20, two in push-pull enabled me to obtain just half of the normal capacity, and it was then found possible to increase the inductance of the tank coil, L3, to obtain a highly-efficient circuit. So although I did not particularly require the additional input made possible by the use of two T-20's in push-pull, it was found advisable to use this circuit, for even with a low input the percentage of R.F. output obtained was highly satisfactory.

Balanced Push-pull


The circuit is shown on this page and consists of a balanced push-pull circuit, neutralised, of course, with completely automatic bias. The stage, as it stands,

is complete in itself for a filament transformer is mounted underneath the chassis. By the application of approximately 10 watts drive into the coupling coil L1, the two T-20's can be driven to an input of at least 100 watts.

While this input is too high for the average amateur, I have mentioned this point to indicate just how flexible this stage can be, for the low power amateur with a permit limiting him to 25 watts input will not have any difficulty in working down to this input. As the efficiency of the circuit with this layout is approximately 85 per cent., then I feel that the use of the two valves and slightly added expense is well worth while.

So far, with an input of 25 watts, I have worked over 20 zones on phone, and approximately 70 countries, all within the space of 12 months.


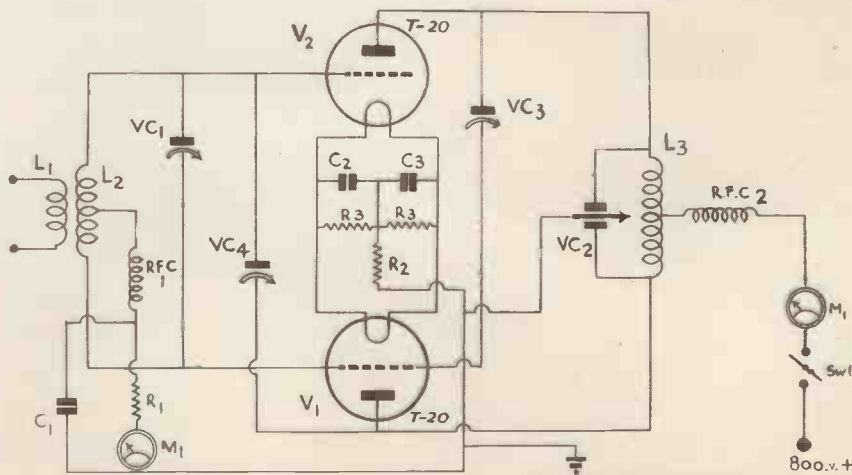
As many of my amateur friends are inclined to believe that successful long distance communication is only possible



This is the circuit used by G2HK, which includes completely automatic bias.

STABILOVOLT

THE SOLUTION
TO UNSTABLE
SUPPLY VOLTAGE

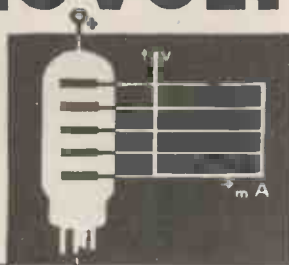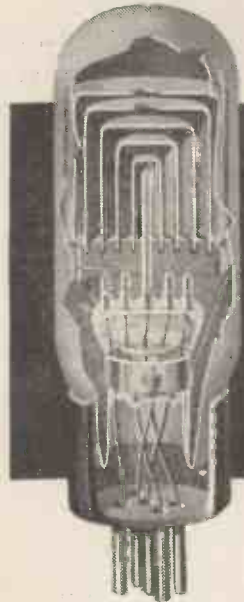


The Stabilovolt tube is a voltage dividing potentiometer and voltage regulator. The voltages tapped are independent to a precision of about .1% from the supply voltage variations, 1-2% from the varying current intensities tapped, .01% from one another. Currents up to 200 mA, voltages of unlimited values subdivided into parts of 70 volts each. Light in weight, small in size, simple and safe in operation.

Prices: Stabilovolt tubes from £1. 16. 0 to £62. Iron Barretters, for use with above, from 16s. to £1. 7. 6. Full particulars from:—

MARCONI'S
WIRELESS TELEGRAPH CO. LTD.
Electra House,
TEMPLE PLACE, W.C.2.

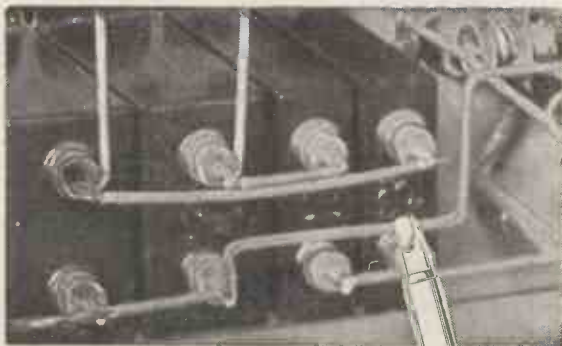100% RELIABLE - IF IT'S ELECTRIC SOLDERING



Every contact a neat, simple and lasting job—that's what Solon electric soldering gives you. Maintains constant heat where you want it—element clamped within the bit concentrates all heat at point.

8/6
DOMESTIC
MODEL
65 watts

Sold with Instruction Book Resin-cored Solder, 6 ft. Flex and Standard Lamp Adaptor.



W. T. Henley's Telegraph Works Co. Ltd., (Dept. Y678a/V.),
Holborn Viaduct, London, E.C.1.

PLENTY TO CHOOSE FROM

We have at least twenty different types of

COMMUNICATION RECEIVERS

in stock and we cannot attempt to describe them all here. Why not send for our free illustrated catalogue giving full technical details or, better still, call on us and see for yourself.

The NATIONAL range includes:—

NC80X, 10-550 m., 10 tubes, speaker, crystal ... £26
NC81X, hambands, 10-160 m., 10 tubes ... £26
NC100, 12 tubes, 10-550 m., speaker ... £35
NC101X, hambands, 10-160 m., crystal, speaker ... £37 10s.

HRO with SPC unit, rack mounted, 10-550 m. ... £68



HALLICRAFTERS receivers are world famous and their range includes:

SKY-BUDDY, 5 tubes, speaker £9

SKY-CHIEF, 7 tubes, speaker £12 10s.

SKY-CHALLENGER II, 9 tubes, crystal model ... £25

SKY-CHAMPION, 8 tubes, 7.5 to 550m. Available soon £15

SUPER SKYRIDER, 11 tubes, crystal, 5-50 m. ... £32

SUPER SKYRIDER, SX17, 13 tubes, noise limiter ... £39 10s.

THE FAMOUS RME series, RME69, crystal, 10-550m. ... £38.


RME69, with LSI noise silencer £41 10s.

DB20 Preselector ... £12 10s.

510X Frequency expander, available soon

A.C.S. RADIO, Technical **G2NK**
Manager.
52-4 Widmore Road, Bromley, Kent
Ravensbourne 0156-7

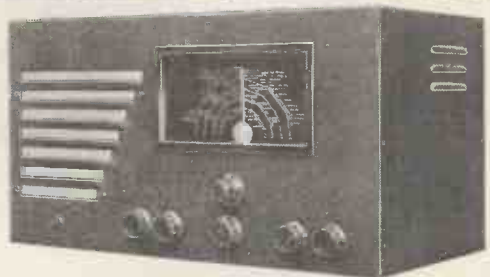Cheap Day Return to Bromley North, 1/6. (20 minutes from Town)
Open until 8 p.m. (except Weds., 1 p.m.)



See Official
TEST
REPORT
in this issue.

NEW Dual Purpose COMMUNICATION RECEIVER — 10-2000 metres

FOR A.C. MAINS 200-250 volts (40-100 cycles).

COMPLETE 6-VALVE RECEIVER with high fidelity speaker incorporated. Housed in Black crackle steel cabinet. Guaranteed, fully tested Cash or C.O.D. or 21/- deposit and 12 monthly payments of 20/3

11 1/2 G N S.

Specified for 10 watt
AEROTRANSMITTER
Peto Scott Microphone (Type T.C.) complete with Transformer. 25/-
Table Model
Telescopic Floor Stand Model See Test Report—Feb. issue £2 2s.

7-METRE CONVERTER

Described in this issue.
FINISHED INSTRUMENT
Assembled and fully tested. Complete with valve, but less Cabinet. Cash or C.O.D. 63/-

Send for complete Lists

PETO-SCOTT CO., LTD.

77 (T.3.), CITY RD., LONDON, E.C.1 Clissold 9875-6-7
62 (T.3.), HIGH HOLBORN, LONDON, W.C.1 Holborn - 3248

DEMONSTRATIONS DAILY

WANTED— THE GREATEST AMPLIFICATION WITH THE LEAST NUMBER OF VALVES

The set—a Dual Purpose Communication Receiver.
Required—as much amplification as possible with
as few valves as possible
And specified by the Television and Short Wave
World were—Tungram Valves. Recommended

because Tungram Valves do all that a good valve
should do, well. The valves specified were VP4B,
DDPP4B, HL4+ and APV4. There is a Tungram
valve for every circuit, and the Tungram range includes
both English and American types (pin and octal bases.)

AND THE CHOICE WAS— TUNGSRAM

The valve with the name behind it!

THE TUNGSRAM ELECTRIC LAMP WORKS (GREAT BRITAIN) LTD., 82, THEOBALDS ROAD, LONDON. TELEPHONE: HOLBORN 3563

COMMUNICATION TYPE RECEIVERS



NEW HALLICRAFTER CHALLENGER, SX-18

Latest American release, possessing many new features, including guaranteed "Infinite Image Rejection," 1,000 degree band spread, "S" meter terminals. Wave range 7.9 to 545 metres, crystal gate, universal A.C. input voltage.

Price complete, £25 0s. 0d.
Six other Hallicrafter models cover every demand. These include the new SKY BUDDY at £9, the new CHAMPION at £15, and the Super Skyrider, £32.

WEBBS CARRY EVERY WORTH-WHILE COMMUNICATION TYPE RECEIVER IN STOCK.

Write for List T.R.

WEBB'S RADIO

(C. WEBB, LTD.)

14, SOHO STREET, OXFORD STREET, LONDON, W.1.
Midland Depot:—
41, CARRS LANE, BIRMINGHAM. All Post Orders to London.

Telephone: GERard 2089

TELEVISION.

A NEW COURSE OF INSTRUCTION,

We have pleasure in announcing that our new "Television" Course has met with remarkable success. The enormous demand for the Course has shown, beyond any shadow of doubt, that it fills that long-felt need which we anticipated when we went to such trouble and expense in its preparation.

We shall be happy to send full details of this special "Television" Course on request. Particulars are also available of other Courses in all branches of Wireless, Television, Talking Picture Engineering, etc., and of the easiest way in which to prepare for the A.M.I.E.E., A.M.I.W.T., A.M.I.R.E., etc., Examinations.

We teach by correspondence, and guarantee "NO PASS—NO FEE." Our Technical Consultant is Professor A. M. Low.

Send for full particulars to-day. Free and without obligation.

THE BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY
337, SHAKESPEARE HOUSE, 17/19, STRATFORD PLACE, LONDON, W.1.



SPECIAL OFFER OF DEMONSTRATION MODEL NATIONAL RECEIVERS

We have for disposal three National Receivers which have been used for demonstration purposes. These receivers are in almost new condition and are open to every inspection and trial.

NATIONAL HRO (serial No. G34) complete with crystal filter, all coils from 9 to 180 metres, band spread and general coverage. Signal strength meter, A.V.C., etc. List price £49 15s. 0d. One model only at £37 10s. 0d.

NATIONAL NC100 for 220/230 volt A.C. input. Automatic coil change covering range from 9 to 500 metres, A.V.C. 10-watt pull output stage, complete with 10-in. speaker chassis. List price £35 0s. 0d. One model only at £30 0s. 0d.

NATIONAL NC101X. As above NC100, but fitted with crystal filter and fitted with coils for complete band spreading of each amateur band from 10 to 160 metres inclusive. 220/230 volt A.C. input complete with 10-in. speaker chassis. List price £37 10s. 0d. One model only at £32 0s. 0d.

Easy payment terms can be arranged.

We hold large stocks of new National receivers, including the HRO, NC100, NC80X and NC81X at standard list prices.

Send 2d. stamp for complete National List.

THE QUARTZ CRYSTAL CO., LTD.,
Kingston Rd., NEW MALDEN, SURREY Telephone: MALden 0334.

RAYMART

CRAFT A CREED

THE SHORT-WAVE SPECIALISTS

We are Authorised Distributors for
BILEY, THORDARSON, TAYLOR TUBES, RME, BASSETT CONCENTRIC CABLE, HOYT METERS, NATIONAL, ETC.
Send us your enquiries. Large stocks carried.

RAYMART SPECIAL OFFERS

W.B. 8-in. Permanent Magnet Speakers at one-third Cost.

Extension Type 7/6 Standard Type (with Transformer) 12/6
GARRARD Senior Automatic Record Changer; standard 12 guinea model, but fitted with high fidelity Brush Plezo Crystal Pick-up. Maker's Cartons.

Limited Number, £4 - 12 - 6
Carriage 2/- extra.

RAYMART LINES SPECIFIED

for apparatus described in this issue

1 Type TC40 Variable Condenser. 40 m.mfd. 3/6
12 Type SM stand-off Insulators, 6d.ea.

G5NI's 66-PAGE MANUAL

Packed full with valuable high frequency information. The greatest value and most comprehensive Manual ever published in this country. 7½d. Post Free.

RAYMART VALVE ANNOUNCEMENT

We are now able to offer a complete range of replace-
ments including those for types PX25, PPS/400-
PP3/250, PX4, AC2Pen., VP4B., TDD4, etc. All
types of Universal Valves including side contact, etc. All
Guaranteed and showing a saving of over 50 per
cent.

Quotations on receipt of types required.

Quantity Discounts to Service Engineers.

RAYMART SHORT-WAVE CATALOGUE

New Edition, enlarged 1½d. Post Free

RADIOMART

G5NI (Birmingham) Ltd.

44, HOLLOWAY HEAD, BIRMINGHAM.

Telephone: MID. 3254.

BULGIN

SHORT-WAVE

experience counts

"Trade News of the Month"

(Continued from page 293)


amateur equipment, Webbs Radio now have most of the better-known American hand-books and catalogues, such as the Radio Telephone hand-book, the Jones Antenna hand-book, and both the R.C.A. receiving and transmitting valve manuals.

A low-loss coil former, type BTX, which is 3½ in. long with a diameter of 1½ in., has been produced by G5NI (Birmingham), Limited. This coil form is threaded to accommodate 32 turns, while provision has been made for a link coil to be wound inside the former. This type of former overcomes the trouble of centre tapping with the upright former in which the tap connection has to pass through the bottom half of the coil. This former, complete with plugs, is priced at 2s. 6d.

The new Bulgin acorn valve holders, VH38 and VH39 are fitted with an entirely new type of contact. The new design gives extra resilience by fold-over design, and eliminates the last possibility of looseness. Both of these holders are priced at 3s.

Amateurs who need fixed condensers for high-voltage working, such as for inter-stage coupling in transmitting circuits should bear in mind that Bulgin have a complete range varying in capacity from .001-mfd. to .1mfd. all suitable for 2,000 volt D.C. working. Condensers of this type are also suitable for peak voltage of 5,000.

A condenser microphone for 25s.,

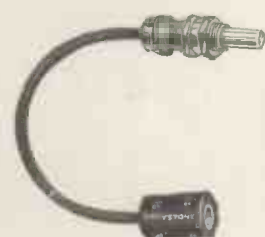

By means of this Eddystone extension coupler condensers and similar components can be operated at an angle of 90-degrees.

which has a sensibly flat response from 50 to 6,000 cycles, is another new design

(Continued on page 319).

RADIO CLEARANCE

63, High Holborn, W.C.1

Phone: Holborn 4631

LARGEST COMPREHENSIVE STOCK OF COMPONENTS IN G.T. BRITAIN

Huge Purchase P.M.M.C. Speakers, by well-known known manufacturer, 7½ cone, latest type magnet, fitted Universal Transformer, with terminals. Suitable for P.P., Class B, Power or Pentode, 9/11 each.

VOLUME CONTROLS. Special offer.

1 Meg. with Switch, 1/6.
500,000, less Switch, 1/3.
100,000 Miniature type, less Switch, 1/4.
5,000 with Switch, 2/-.

RESISTANCES. Special offer.

1 gross assorted ½, 1 and 1 watt Polar N.S.F. Resistances, all good sizes, 4/- gross. Cur selection.
1 Watt Resistances, well-known make, all sizes, 3½d. each, 2/9 dozen.
2 Watt Polar N.S.F. Resistances, following sizes: 100: 160: 400: 600: 2,500: 3,000: 5,000: 40,000: 50,000: 100,000: 120,000: ohms, and 1 meg., 6d. each.

FIXED CONDENSERS.

Electrolytic Can Type, well-known manufacturer.

8 Mfd., 450 volt working, 2/6.
4 Mfd., 450 volt working, 2/6.
8 Mfd., 500 volt working, 3/-.
Cardboard Type, 450 v. working.
8 plus 8 Mfd., 450 volt working, 3/-.
4 plus 4 Mfd., 2/9.
6 plus 4 Mfd., 2/9.
8 plus 4 Mfd., 2/11.

SPECIAL OFFER. PHILLIPS Wet, Can type, Electrolytics.

8 Mfd., 450 volt working, 1/6.
16 plus 8 Mfd., 450 v., 2/-.
16 Mfd., 320 v., 1/6.

25 Mfd., 320 volt working, 1/6.

50 Mfd., 32 volt working, 1/6.

Special offer Cardboard Electrolytic 10 Mfd., 250 volt working, 8d.

TUBULAR CONDENSERS, well-known manufacturer, all sizes up to 0.1, 4½d. each, 4/- dozen.

Special offer. 1 dozen Assorted Polar N.S.F. Tubular Condensers, all good sizes, 1/6 dozen. Cur selection Muirhead 1 Mfd. Tubular Condensers, 350 volt working 10d.

0.1 ditto, 3d. each, 2/9 dozen.

BRYCE MAINS TRANSFORMERS, standard for the season. These Transformers are British made, and are fully guaranteed for 6 months.

350-0-350, 150 m.a., 2-0-2 volts 2.5 amp., 2-0-2 volts 5 amp., 2-0-2 volts, 2 amp., 11/6 each.

500-0-500, 150 m.a., 2-0-2 volts 2.5 amp., 2-0-2 volts 5 amp., 2-0-2 volts 2 amp., 2-0-2 volts 2 amp., 17/6.

All Windings centre tapped.

Special offer Transformers, ex Aerodyne, 300-0-300, 100 m.a., 4-volt 2 amp., 4 volt 4 amp. 5/-.

clunts 1,000 mfd. cardboard ELECTROLYTICS, wire ends, peak voltage, 12 volts, 2/- each.

Dubilier ½ meg. VOLUME CONTROLS, with switch, standard model, very compact, 1/6 each.

H.T.8 Type RECTIFIERS (Skeleton Type), a really splendid job, 4/6 each: 6 bank 4 position Xaley type

SWITCHES, beautifully finished, each bank 5 contact type, plus common, 5/- each.

VISUAL TUNING INDICATOR, m.a. type, complete with mounting bracket, 1/3 each.

3-Gang 0.0005 STRAIGHT CONDENSERS: a precision instrument with ceramic insulation, suitable for all circuits, including all-wave, 3/- each.

DIALS for above, 2-speed type, 9 in. long, 5 in. wide, station marked for 4 wave bands, two short, medium and long, 4/6 each; 465 I.F.'s, iron cored, with trimmers, 2/6 each.

Plessey Can Type CONDENSERS (Electrolytics), complete with fixing clamp, 8 plus 16 mfd., 8 mfd., working voltage 450, 16 mfd., working voltage 350, 2/- each. Plessey 16 mfd., 150 volt working, 1/3 each.

SPECIAL OFFER.

QUARTZ PIEZO CRYSTALS, 125 k.c.

A unique opportunity at a fraction of the original price. Ideal for Wave Meters, Standard Frequency Test or could be re-ground for other frequencies. Unrepeatable price, 4/6 each.

QUARTZ PIEZO CRYSTALS and 125 k.c. I.F. TRANSFORMER as a complete Unit, fully screened

Ideal combination for Single Signal Superhet or Crystal Gate Receivers, 7/11 complete, 14/- per pair.

HUGE PURCHASE—RELAYS, made by well-known manufacturer, Resistance 3,300 ohms, cost 25/- each our price, 5/- each.

Special Offer MAINS TRANSFORMERS, 350-0-350, 120 n.-A. 15 volts C.T. at 4 amp., 4 volts C.T. at 2.5 amp., mains input adjustable 200-250 volts, heavily shrouded, 4/6 each; 20 hy., 100 m.A., 500 ohms choke, unshrouded, 5/11 each; 350-120 indirectly heated rectifier, Cctol base type, well-known make, complete with Cctol base valve-holder, 4/6 each.

Special Offer MAINS TRANSFORMERS, 350-0-350, 120 n.-A. 15 volts C.T. at 4 amp., 4 volts C.T. at 2.5 amp., mains input adjustable 200-250 volts, heavily shrouded, 4/6 each; 20 hy., 100 m.A., 500 ohms choke, unshrouded, 5/11 each; 350-120 indirectly heated rectifier, Cctol base type, well-known make, complete with Cctol base valve-holder, 4/6 each.

SPECIAL OFFER.

QUARTZ PIEZO CRYSTALS, 125 k.c.

A unique opportunity at a fraction of the original price. Ideal for Wave Meters, Standard Frequency Test or could be re-ground for other frequencies. Unrepeatable price, 4/6 each.

QUARTZ PIEZO CRYSTALS and 125 k.c. I.F. TRANSFORMER as a complete Unit, fully screened

Ideal combination for Single Signal Superhet or Crystal Gate Receivers, 7/11 complete, 14/- per pair.

HUGE PURCHASE—RELAYS, made by well-known manufacturer, Resistance 3,300 ohms, cost 25/- each our price, 5/- each.

Special Offer MAINS TRANSFORMERS, 350-0-350, 120 n.-A. 15 volts C.T. at 4 amp., 4 volts C.T. at 2.5 amp., mains input adjustable 200-250 volts, heavily shrouded, 4/6 each; 20 hy., 100 m.A., 500 ohms choke, unshrouded, 5/11 each; 350-120 indirectly heated rectifier, Cctol base type, well-known make, complete with Cctol base valve-holder, 4/6 each.

Special Offer MAINS TRANSFORMERS, 350-0-350, 120 n.-A. 15 volts C.T. at 4 amp., 4 volts C.T. at 2.5 amp., mains input adjustable 200-250 volts, heavily shrouded, 4/6 each; 20 hy., 100 m.A., 500 ohms choke, unshrouded, 5/11 each; 350-120 indirectly heated rectifier, Cctol base type, well-known make, complete with Cctol base valve-holder, 4/6 each.

SPECIAL OFFER.

QUARTZ PIEZO CRYSTALS, 125 k.c.

A unique opportunity at a fraction of the original price. Ideal for Wave Meters, Standard Frequency Test or could be re-ground for other frequencies. Unrepeatable price, 4/6 each.

QUARTZ PIEZO CRYSTALS and 125 k.c. I.F. TRANSFORMER as a complete Unit, fully screened

Ideal combination for Single Signal Superhet or Crystal Gate Receivers, 7/11 complete, 14/- per pair.

HUGE PURCHASE—RELAYS, made by well-known manufacturer, Resistance 3,300 ohms, cost 25/- each our price, 5/- each.

Special Offer MAINS TRANSFORMERS, 350-0-350, 120 n.-A. 15 volts C.T. at 4 amp., 4 volts C.T. at 2.5 amp., mains input adjustable 200-250 volts, heavily shrouded, 4/6 each; 20 hy., 100 m.A., 500 ohms choke, unshrouded, 5/11 each; 350-120 indirectly heated rectifier, Cctol base type, well-known make, complete with Cctol base valve-holder, 4/6 each.

Special Offer MAINS TRANSFORMERS, 350-0-350, 120 n.-A. 15 volts C.T. at 4 amp., 4 volts C.T. at 2.5 amp., mains input adjustable 200-250 volts, heavily shrouded, 4/6 each; 20 hy., 100 m.A., 500 ohms choke, unshrouded, 5/11 each; 350-120 indirectly heated rectifier, Cctol base type, well-known make, complete with Cctol base valve-holder, 4/6 each.

SPECIAL OFFER.

QUARTZ PIEZO CRYSTALS, 125 k.c.

A unique opportunity at a fraction of the original price. Ideal for Wave Meters, Standard Frequency Test or could be re-ground for other frequencies. Unrepeatable price, 4/6 each.

QUARTZ PIEZO CRYSTALS and 125 k.c. I.F. TRANSFORMER as a complete Unit, fully screened

Ideal combination for Single Signal Superhet or Crystal Gate Receivers, 7/11 complete, 14/- per pair.

HUGE PURCHASE—RELAYS, made by well-known manufacturer, Resistance 3,300 ohms, cost 25/- each our price, 5/- each.

Special Offer MAINS TRANSFORMERS, 350-0-350, 120 n.-A. 15 volts C.T. at 4 amp., 4 volts C.T. at 2.5 amp., mains input adjustable 200-250 volts, heavily shrouded, 4/6 each; 20 hy., 100 m.A., 500 ohms choke, unshrouded, 5/11 each; 350-120 indirectly heated rectifier, Cctol base type, well-known make, complete with Cctol base valve-holder, 4/6 each.

Special Offer MAINS TRANSFORMERS, 350-0-350, 120 n.-A. 15 volts C.T. at 4 amp., 4 volts C.T. at 2.5 amp., mains input adjustable 200-250 volts, heavily shrouded, 4/6 each; 20 hy., 100 m.A., 500 ohms choke, unshrouded, 5/11 each; 350-120 indirectly heated rectifier, Cctol base type, well-known make, complete with Cctol base valve-holder, 4/6 each.

SPECIAL OFFER.

QUARTZ PIEZO CRYSTALS, 125 k.c.

LOUDSPEAKER

24-HOUR SERVICE

(BRITISH AND AMERICAN)

TRANSFORMERS DESIGNED AND REPAIRED.

NEW SPEAKERS 3" to 18" P.M. and MAINS ENERGISED.

SPEAKERS OF ALL KINDS FROM 10/6.

SINCLAIR SPEAKERS

ALMA GROVE, COPENHAGEN STREET, TER 4355
LONDON, N.1

"Television and

Short-wave

World" will be

sent post paid

to any part of

the world for

twelve months

for 13/6.

"A T₂₀ Output Stage" (Continued from page 314)

single turn loop attached, again mounted on Trolitule, with the grid condenser, VC₁, mounted next to it.

For a tank coil, twelve turns of 9-gauge wire are used, and spaced so as to bolt directly across the fixed plates of the tank condenser. A centre tap is made on to this coil, and comes down by a heavy flexible conductor to a socket, which in turn goes through the chassis by means of a Johnson feed-through insulator on to a radio-

.002-mfd. can generally be omitted, but as some grid meters are inclined to be inductive it is well worth while including this condenser as a precautionary measure.


It is rather important to use a grid coil, L₂, with a comparatively high inductance, and despite the fact that VC₁ has a capacity of only 40-mmfd., sufficient turns should be used on this coil in order to enable only one-quarter of this capacity to be used.

However, if there is too much drive from the exciter stage, then it will be advisable to make the link coil of 14-gauge wire and to terminate it to soldering lugs bolted to the insulated base on which the grid coil is mounted. The size of this coil can then be adjusted in order to decrease or increase the drive as required.

In normal circumstance, the T-20 valves, with the biasing arrangements provided, will require approximately 35 mA. of grid current to provide maximum R.F. output, and any increase in drive beyond this figure does not appear to be of any appreciable advantage. This is rather lower than the figures quoted by the manufacturers, but has been borne out quite satisfactorily in actual practice.

The maximum permissible input to this stage is 110 watts, at which figure the efficiency is approximately 85 per cent., so that constructors can reckon on this percentage of R.F. being fed into the aerial. It is, however, rather important to feed the final stage in a satisfactory manner, and I suggest that link coupling be employed between tank and aerial coils. Make the wire between link coils of low impedance cable, for this enables the transmitter to be used in any part of the operating room without loss, for the aerial coil can be located and tuned near to the point where the feeders enter the room. This is rather an important point and it has been proved to my complete satisfaction that this method of coupling is undoubtedly the best, while selectivity has been greatly increased.

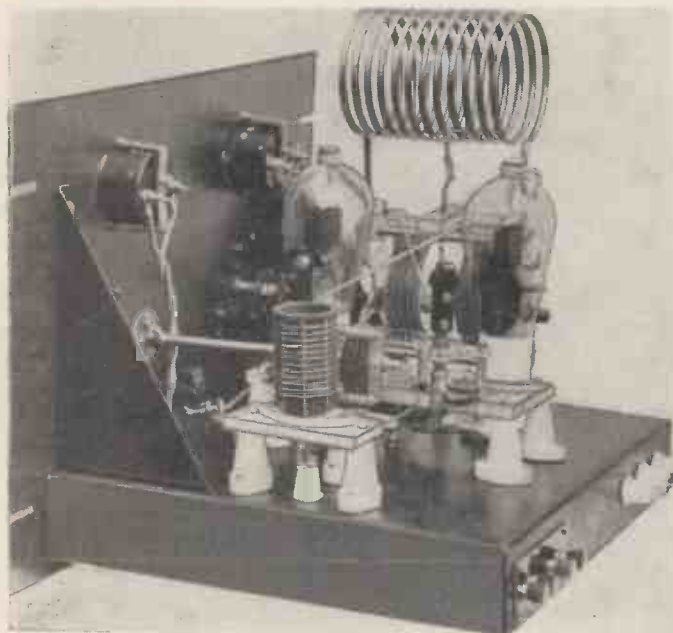The results obtained both in practice and in theory with this high efficiency output stage, more than indicate how well worth while it is to use modern valves in the most efficient manner, and I advise other amateurs who have bought T-20's, T-40's, RK35's, or similar valves, to completely scrap the output stage and rebuild it around the new valve they have chosen.



The grid coil is mounted on an insulating strip, while the photograph shows how the neutralising condensers are mounted on the valve strip. Both anode leads are made of Lewcos braided connected wire which is both ornamental and effective.

frequency choke and ultimately to the 800 volt power supply.

The socket for this tap is mounted on a small insulating strip which is, in turn, fixed to the supporting rods on the tuning condenser. These rods have to be drilled and tapped.

Neutralising condensers are actually 15-mmfd. variables broken down to triple spacing, so as to provide a very low minimum capacity, and mounted directly on to the insulating strip which holds the two valves. Actually, the two rods holding the fixed plates of these neutralising condensers are bolted to the insulating material so that no additional brackets are required.

Underneath the chassis and connected between the filament transformer centre tap and the chassis is R₂, a resistance of 400 ohms with a 20 watt rating. This is the auto-bias resistance for the two T-20's, and accounts for the reason why I am using an 800 volt power pack instead of the 750 volt recommended by the valve maker. The extra 50 volts will be more than consumed by the auto-bias applied to the valves. Additional bias is also obtained by means of the grid current drop across the resistance R₁, which has a value of 4,000 ohms and rating of 20 watts.

The condenser, C₁, having a value of

The grid coil in the original model consists of 12 complete turns on a threaded former with one thread gap between turns. The link coil, L₁, is not shown in the photograph, but it consists of a single turn of heavy gauge rubber-covered wire around the electrical centre of the coil. This is then taken down to the chassis beneath on to a link coil connected around the centre of the sub-amplifier anode coil.

Components for

A LOW-LOSS T₂₀ OUTPUT STAGE

CHASSIS AND PANEL.

1—Standard steel chassis finished black (Premier Supply Stores).

1—Standard panel 10½ ins. high finished grey (Premier Supply Stores).

COIL FORM.

1—4-pin form (Premier Supply Stores).

COIL.

1—Tank coil wound with 3/16 copper tube (Eddy-stone).

CONDENSERS, FIXED.

—0.02-mfd. type H.V. tubular (C₁) (Dubilier).

1—0.1-mfd. type 691 (C₂) (Dubilier).

1—0.1-mfd. type 691 (C₃) (Dubilier).

CONDENSERS, VARIABLE.

1—type TC-40 (VC₁) (Raymart).

1—type 1081 (VC₂) (Eddystone).

1—Tro 15T (VC₃) (Premier Supply Stores).

1—Tro 15T (VC₄) (Premier Supply Stores).

CHOKES, HIGH-FREQUENCY

1—type 1022 (Eddystone).

1—type transmitting (Premier Supply Stores).

HOLDERS, VALVE.

2—type 4-pin ceramic (Amphrenol Webb's Radio).

1—4-pin type ceramic type (V₅) (Clix).

METERS.

1—0/150 mA (M₁) (Howard Butler).

1—0/60 mA (M₂) (Howard Butler).

PLUS, TERMINALS, ETC.

1—Power socket type 10 (Clix).

2—Valve cap connectors (Bulgin).

RESISTANCES, FIXED

1—4,000-ohm type 20-watt (R₁) (Premier Supply Stores).

1—400-ohm type 20-watt (R₂) (Premier Supply Stores).

1—30-ohm humdinger (R₃) (Premier Supply Stores).

SUNDRIES.

2—Strips of transparent insulating material (Premier Supply Stores).

1—10-gauge tinned-copper wire (Webb's Radio).

8—Stand-off insulators type SM Raymart).

TRANSFORMER FILAMENT.

1—7.5 volt 3.5-A (Premier Supply Stores)

VALVES.

2—Taylor T-20 Webb's Radio).

MAY, 1938

"Trade News of the Month."

(Continued from page 317).

by Bulgin which amateurs will find of considerable interest.

A low-loss feeder suitable for high frequency use is always of interest, for it is generally believed that the best feeder for general amateur use is the 600-ohm spaced line. The new Telcon cable type AS5C, which is of the co-axial type with a conductor, has exceptionally low attenuation figures of .04 db. at 7 Mc., .07 at 14 Mc., 1.3 at 28 Mc., 2.4 at 56 Mc. All these figures are for lengths of 65 ft., and we advise readers who consider co-axial cable to be expensive to approach the Telegraph Construction and Maintenance Company for the quotation for the length of cable they require. It will be found that the prices are extremely low.

The Southend and District Radio and Scientific Society.

At the annual dinner and dance of the Southend and District Radio and Scientific Society, Mr. J. W. Burrows, J.P., Chairman of the Board of Management of the Southend General Hospital, congratulated the Society on its past efforts in equipping the local hospitals with radio and in maintaining the installation in good working order, although they had often impoverished themselves in doing so.

The Society's portable call G5QK has had considerable use during the past three years. Direction finding field days have been held on 1.75 Mc. and have been well attended. At the all-night meeting, 43 persons, including 7 ladies, lost their sleep.

The following dates have been fixed for this summer's 1.75 Mc. field days: May 15, June 26, August 21, September 24-25 (all night), October 23.

The winner for the 1937 season of the cup presented by Mr. G. T. Peck for the best all-round performance at field days was Mr. L. G. Pugh, 2BNR.

Further field days are to be held this summer on the ultra-high frequencies. July 3 has been fixed for the first of these events.

All persons who are interested in the activities of the Society are invited to communicate with the hon. secretary, J. M. S. Watson, G6CT, 23 Eastwood Boulevard, Westcliff-on-Sea.

The General Electric Co.'s short-wave station W2XAD can now be received on the higher frequencies. The new wavelength is 13.95 metres when it can be heard from 1 p.m. to 8 p.m., so that during the summer months reception will not be restricted to late evenings. This is a very welcome change and will be appreciated by amateurs who value the 13-metre channel for its reliability.

GALPINS ELECTRICAL STORES

75, LEE HIGH ROAD, LEWISHAM, LONDON, S.E.13

Telephone: LEE GREEN 5240.

Terms: CASH WITH ORDER OR C.O.D.

All goods sent on 3 days' approval against cash.

HEADPHONES, 4,000 ohms, makers, B.T.H. Stirling, Western Electric, etc. Second-hand but in good condition, 2/6 per pair, post free.

TRANSFORMER, 2,500-ohm field, in new condition, 6/9 each.

PHILIPS' MAINS TRANSFORMER, input 200/250 volts, 2,000/0/2,000 volts, 150 m/A., 11½ volts 2½ amps. and 4 volts 8 amps. output, 26/- C/F. 40 henry 250 m/A. Smoothing Choke, 12/6. C/F.

KOLSTER BRANDES MAINS TRANSFORMERS, input 200/250 volts, output 250/0/250 volts; also 4 volts 2 amps. and 4 volts 1 amp., 3/6 each. Philips' 1 mf. 4,000-volt working Condensers, 7/6 each. Muirhead 2 mf. 375 volts working, 1/- each. Dubilier Block Condensers, 350 volt working, 10 mf. tapped, 4 x 4 x 2 mf., 3/-. Ditto, 8 mf. tapped, 4 x 2 x 2 mf., 2/6.

MAINS TRANSFORMERS, 200/250 volt input. Low voltage at approx. 50/75 amps. output, 8/6, C/F. Transformers with unknown windings, 6/6 each; approx. 500 watts.

LARGE MAINS TRANSFORMERS, input 200/250 volts, output 4,000 volt 500 m/A. C.T., also 14 volt 8 amp., 70/- Smoothing Choke, 12 henrys to suit, 30/-

WESTON MOVING COIL MILLIAMMETER, fully guaranteed. 2 in. and 2½ in. dials, 0 to 3, 17/6; 0 to 5, 15/-; 0 to 25, 0 to 50, 14/-; 0 to 150, 0 to 200, 12/6 each. Everett Edgcombe, 0 to 500 m/A., 12/6 each. Moving Coil Meter Movements for recalibrating into multirange meters, approx. 10 m/A., 5/-. Ditto, 4-in. dial, 6/6. Post 9d. A few only, need slight repair, 2/6 each.

ELECTRIC LIGHT CHECK METERS, 200/250 volt 1 ph. 50 cycles, 5 and 10 amp., 6/- each. Post free. G.P.O. Glass Top Relays, approx. 1 m/A., 7/6. Smoothing Chokes, 30 henrys 150 m/A., 5/-. Power Packs, consisting of 2 x 20 henrys 60 m/A. Chokes and 2-2 mf. Condensers at 3/6 each.

EX-G.P.O. RELAY, small type, with platinum contacts, work on small current, various resistances from 300 ohm to 12,000 ohms. Brand new, 3/6 each. Second-hand, but good, 2/- each. Silvertown Highly Sensitive Galvanometers, flat type, reading 800/0/80, 7/6 each.

EX-G.P.O. PEDESTAL TYPE TELEPHONE, with Automatic Dials.—Reading 0 to 9, 8/6. Wall type ditto, 10/6 each. Microphone Transformers, ratio 80 to 1, 2/- Bell Boxes, consisting of A.C. Bell, Mike Transformer, 2 mf. Condenser, 4/- each. G.P.O. Automatic Dials, 0 to 9, 3/6 each. Hand Sets, Earphone and Microphone combined, 4/6 each. Weston Electric Highly Sensitive Microphones, 2/6 each.

SLIDER MAINS RESISTANCES, 2,500 ohms, carry 300 m/A., worm wheel type, 17/6; 1,000 ohms ½ amp., 12/6; 350 ohms 2½ amps., 15/-, etc. Dimmer Resistances, 1 kilowatt, 20/-; 2 kilowatts, 30/-

ROTARY CONVERTORS by well-known maker, D.C. to A.C., all fully guaranteed. 220 volt D.C. to 200 A.C. 150 watts, 50/-; ditto, 100 v. D.C. to 80 v. A.C. 1½ kW, 80/-; ditto, 220 v. D.C. to 200 v. A.C. 400 watt, 70/-; ditto, 100 v. D.C. to 65 v. A.C. 150 watt, 35/-

WESTINGHOUSE RECTIFIERS (second-hand), in guaranteed working order. 500 volts, 250 m/A., in voltage doubler circuit with transformer to suit, 35/- the pair; or Rectifier 22/6; Transformer, 17/6.

LARGE MAINS TRANSFORMERS FOR REWINDING, 1 kW, 15/-; 500 watt, 7/6; 250 watt, 5/-; 150 watt, 3/6 each.

MAINS TRANSFORMERS by well-known makers. Input 200/250 volt 50 cycle 1 phase, 6 and 30 volt out at 15-20 amp., 17/6. Another, 3-5-8 volt at 20-30 amp., 17/6. Another, 10 volt 5 amp., 10/6. Another, with 3-4 volt 3 amp. tappings, all C.T., 7/6.

DOUBLE OUTPUT GENERATOR, shunt wound, ball-bearing, output 2,500 volts 160 m/A., also 16 volts at 14 d.p. C.C. Can also be used as Rotary Converter, 20 to 24 volt input, full H.T. output, 50/-

EPOCH PUBLIC ADDRESS MOVING COIL SPEAKERS, Handle 20 watts 15 ohm and 1,000 ohm. Speech Coils, 15-in. cone, 6-volt field, 45/-

COPPER SCREENED BASE BOARDS, 17½ x 7 in., undrilled, 2/-

STUD SWITCHARMS, with studs, very smooth action, 1/6. Quartz Tubes, 10 x 3/16 in., 5/- per doz.

EX-R.A.F. WAVEMETERS, 200 to 550 metres, visual type, 3/- 300 to 2,500 metres, valve type, 7/6 each, with valves. Post free.

CHARGING DYNAMOS, all shunt wound, fully guaranteed, 15 volt 12 amp., 22/6; 12 volt 8 amp., 17/6. 25 volt 8 amp., 32/6. 50/75 volt 10 amp., 60/- 100 volt 15 amp., 80/- Regulators to suit any of these Dynamos, 12/6 each.

C.A.V. AUTOMATIC CHARGING CUT-OUTS. Any voltage, amps. up to 100 amp. Please state voltage, 7/6 each. Post 6d.

EX-R.A.F. VISUAL WAVEMETER with valve, 1,000 to 9,000 metres, 5/- Ex-naval heterodyne detector unit, 3-valve, 15 to 200 metres, less valves, very useful to the experimenter, 25/- C/F. Enamelled copper instrument wire, 20 gauge, 4 lb. reel, new and unused, 6/-. Ex-G.P.O. Morse tapping keys, three contact type, long brass bar, 6/6 each.

VOLTAGE CHANGING TRANSFORMERS, with 12 months' guarantee. 100/120 volt to 200/240 volts or vice-versa auto wound 100 watt, 10/-; 150 w., 12/6; 200 w., 16/6; 500 w., 25/-; 750 w., 30/-; 1,000 w., 35/-; 1,500 w., 42/6; 2,000 w., 52/6.

DIMMER RESISTANCES, large type, all fully guaranteed. 500 watt, 15/-; 1,000 w., 20/-; 2,000 w., 30/-; with worm-wheel drive, 5/- extra.

TELEGRAPH MORSE INKERS with Sounder, in good condition, 30/-. Ex-R.A.F. 7-valve Receiver Amplifiers, wave-length not known, 7/6. C/F. Radiogoniometers by "Marconi," etc., 15/- "Sullivan" .0005 mfd. Transmitting Variable Condensers, 10/6. Cossor 2-volt general purpose Valves, 3 for 2/6, as new. 2 mfd. 250 volt working Condensers, 9d. each. Single Earphones, 1,000 ohms, 9d. Bobbins, 1,000 ohms, per pair 6d. Microphone Buttons, 9d. ½ mfd. 350 volt working Condensers, 9d. each. Volume Controls, 1,000, 25,000, 100,000 ohms, 1/- each. Ex-R.A.F. Visual Wavemeter with valve. Bulgin Toggle Switches, s.p.c.o., 9d. Resistance Mats wound with Eureka wire, 600 ohms, carry ½ amp., size 24 x 24 in., 4/- each.

MOTOR BLOWERS, fitted ½ h.p. 110 volt motor D.C. Series wound, ball-bearing, 4-in. inlet and outlet, 35/- C/F.

X-RAY SPARK COILS, round type, ebonite covered, 110/230 volt D.C. working, 10-in., 35/-; 8-in., 25/-; 16-in. 55/- Condensers for the primary of Spark Coils, 8 to 14 inch, 7/6. To suit larger coils, 10/- each.

X-RAY TUBES, 7-in., brand new Tungsten Targets, 15/- Packing free, C/F. Platinum Targets, 5-in., 18/6.

ELECTROLYTIC (DRY) CONDENSERS, 8 x 8 x 4 x 4 x 25 x 25 mf. 350 v., 2/6; 8 x 8 x 4 x 4 mf. 350 v., 2/-; 6 x 6 x 6 mf. 500 v., 2/- each. Mains Transformers, 200/250 v. input, 350/0/350 v. 120 m/A. 4 v. 5 a., C.T., 4 v. 2½ a., 20 v. ½ a., C.T., 7/9 each. Mains Chokes, 20 hy. 60 m/A., 2/3; 30 hy. 150 m/A., 5/-

MOVING COIL MOVEMENTS, 7-in., full scale deflection, ½ m/A. gravity action, makers, Evershed, 8/6 each.

X-RAY TRANSFORMER, input 100 v. 50 cy. 1 ph., output 40,000 volts 12 m/A., with Coolidge heater transformer, as new, £5. C/F. Sunray Lamps, floor type, fully adjustable, less burner, D.C. type, 65/-; A.C. type, 95/- C/F. A brand new X-Ray 12-in. Coil complete in polished case with discharge rods, tube holder for 100 or 200-volt supply, 70/- C/F.

ELECTROSTATIC VOLTMETERS, 2½-in. dia., 0 to 250 volt for D.C. only, quadrant type, 12/6 each; ditto, 3½-in. dial for A.C., 25/-

"1938 Valves Designs"

(Continued from page 296)

current of 3,000 mA. with the peak inverse voltage of 11,000.

An indirectly heated half wave rectifier for use in high-voltage power supply units has been produced by Ediswan. This valve, the U21, is very similar in output to the MU2 with the exception that only 15 per cent. of the maximum voltage is developed 35 seconds after the voltage has been applied. This eliminates the use of a delayed switching circuit.

A new pentode with a 20 watt rating and similar to the 837 is now available from Tungstram Valve Company. This valve is designated the OS12/500 and priced at 30s. The main virtue of this valve is that the maximum carrier power is obtained with a grid driving power of only 1/10th watt. Similarly for suppressor modulation only 100 milliwatts are required for maximum percentage modulation.

"A T-40 Transmitter"

(Continued from page 306)

Although no difficulties should be experienced when building the first two stages, in no circumstances should the T-40 stage be operated unless it is connected to a dummy aerial. Otherwise there will be flashover in the condensers, and there is also the possibility of component breakdown. A dummy aerial circuit consists of a coil, condenser, 100

watt lamp, and an 80 ohm non-inductive resistor.

Power Supply

In the next issue, we shall describe two power packs, one giving 500 volts, the other 800 volts suitable for driving the three valves so far described. A complete two-section modulator and power pack is in course of construction, while the final push-pull amplifier, which will be described at a later date, is at the present time undergoing tests. This final stage will be suitable for an input up to 400 watts.

Constructors will clearly understand before even contemplating the construction of this transmitting equipment, they must obtain an official aerial transmitting permit. A full radiating permit must be obtained before transmitting is connected to an elevated aerial.

Full details as to the qualifications needed to obtain these permits can be obtained from the office of the Engineer-in-Chief, Radio Division, General Post Office, Armour House, Aldersgate Street, E.C.

"Commercial Receivers on Short-waves"

(Continued from page 312)

in an amateur receiver. It consists of a sharply tuned circuit in the grid of the input valve which is only used between 14 and 28 M/c. When this control is operated second channel interference

can be completely eliminated leaving the fundamental station in the clear.

It is very useful for cutting out long wave C.W. interference, and also stops interference from broadcast stations from either short or medium waves when the receiver is being used close to a broadcast station.

The performance is as good as any receiver of its type and price we have so far tried, while the sensitivity on 10 metres is outstanding. The receiver is priced at £25 in this country.

"The Short Wave Radio World"

(Continued from page 299)

mentioned should be about .005-mfd. When testing with a pair of headphones across the output circuit there should be sufficient volume to give a strong audio tone into a pair of 2,000-ohm headphones.

Negative bias is provided by means of the one volt drop across the filament resistance, which can be either fixed or variable. When a modulated oscillator is needed to line up a receiver the output is sufficiently stable from this simple unit for that purpose and can be used if required in conjunction with a valve voltmeter.

Amateurs who wish to check the performance of a transmitter when using class-B telephony will be able to use this steady tone source connected into the input of the amplifier.

WHAT IS AMATEUR RADIO?

More and more true radio enthusiasts are joining the ranks of Amateur Radio, and for the benefit of those interested in this excellent movement we have recently published our booklet

"HOW TO BECOME A RADIO AMATEUR"

This booklet is of special interest to readers of "Television and Short-wave World"

The contents include articles and information on:—

WHAT IS AMATEUR RADIO?—MORSE CODE—INTERNATIONAL PREFIXES AND ABBREVIATIONS—THE Q CODE—SIGNAL CODES—THE A.A. LICENCE—THE FULL LICENCE—SELECTED FORMULAE AND DATA—THE PRIVILEGES OF R.S.G.B. MEMBERSHIP.



4d. Send for this interesting booklet . . .

POST FREE

Write to

The Secretary, Radio Society of Gt. Britain,
53, Victoria Street, London, S.W.1

"HOW TO BECOME A RADIO AMATEUR."

TELEVISION DEVELOPMENTS

Are you keeping abreast of modern television developments? Whether amateur or professional you *must* be in touch with the latest trend of research.

The Television Society enables you to meet fellow workers in the field of television, both in this country and abroad.

Founded some 10 years ago The Television Society provides a scientific and non-partisan platform for discussion on all aspects of the subject. Meetings are held monthly during the session (October-June) and are reported in full in the Society's Journal which is sent free to all members.

The Society's activities are shortly being enlarged to meet the growing interest in the subject and members will have a unique opportunity of furthering their knowledge by contact with well-known television engineers.

Full particulars of membership qualifications may be had from the Hon. General Secretary:—J. J. Denton, 25, Lisburne Road, Hampstead, London, N.W.3.

THE TELEVISION SOCIETY


(Founded 1927)

President: Sir AMBROSE FLEMING, M.A., D.Sc., F.R.S.

37 Mullard

Mullard Valves

FOR AMATEUR TRANSMITTERS

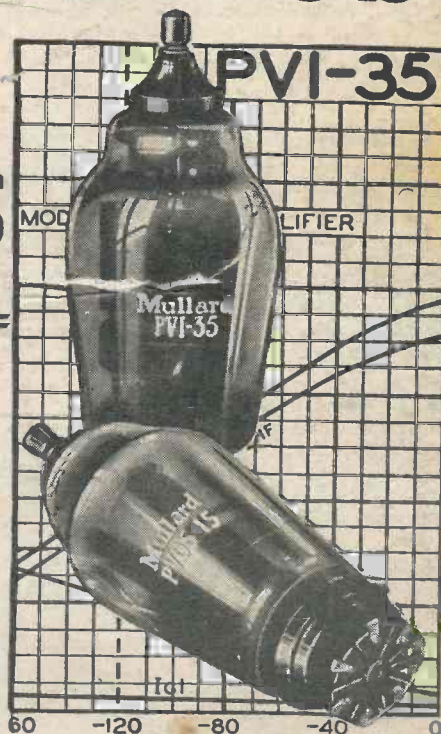

**BRITISH VALVES
NOW AVAILABLE AT
ATTRACTIVE PRICES:**

			s.	d.
TZ05—20	TRIODE	20w	17	6
TYI — 50	TRIODE	50w	£3	10 0
PV05—15*	PENTODE	15w	£1	7 6
PVI — 35*	PENTODE	35w	£4	15 0
PZ05—15	PENTODE	15w	£1	7 6
PZI — 35	PENTODE	35w	£4	10 0

★ INDIRECTLY HEATED CATHODES FITTED

For full data on these types send a postcard to:
TRANSMITTING DIVISION

THE MULLARD WIRELESS SERVICE CO. LTD.
225, TOTTENHAM COURT ROAD, LONDON, W.1.