

# Electronic Engineering

INCORPORATING ELECTRONICS, TELEVISION AND SHORT WAVE WORLD

## PRINCIPAL CONTENTS

**British Electronic Equipment**

*A further review of the Physical Society's Exhibition*

**High Fidelity Bass Compensation**

**Triode Equivalent Circuits**

**A Single Sweep Time Base — Part II**

**2/- FEB. 1946**

# *Keeping* **ELECTRICITY** *in its* **PROPER** *place*

## **MICA**

Raw mica, block and splittings of all grades can be supplied and our factory at Walthamstow is equipped with modern plant for the rapid and economic production of cut, gauged, machined, or made-up mica in the form of condenser films, discs, plates, washers, commutator separators, etc.

## **MICANITE**

Micanite is built-up mica insulation and is manufactured and supplied in every commercial form including Commutator and Moulding Micanite, Flexible Micanite, Mica Tape, Micafolium, Heat-resisting Micanite, Commutator rings and tubes.

## **MICOFLEX-DURATUBE**

Micoflex-Duratube is the registered trade name of our tubes and sleeveings extruded in continuous lengths from Polyvinyl Chloride. There is a wide range of grades, sizes, and colours.

## **PAXOLIN**

Paxolin is our registered trade name for our laminated plastics of the phenolic class. They are manufactured in various grades to suit specific applications and supplied in the form of sheets, tubes, and cylinders. Paxolin insulation is eminently suited for panels, bushings, and insulators, and we are fully equipped to carry out all the necessary machining and fabricating operations.

## **KENUTUF MOULDINGS**

Kenutuf mouldings are available injection-moulded from Polyvinyl Chloride.


## **EMPIRE**

Empire insulation covers a wide range of varnished cloths, silks, woven glass, and papers, both black and yellow, supplied as sheet or as tapes both straight cut and bias. We also supply varnished cotton and silk sleeving.

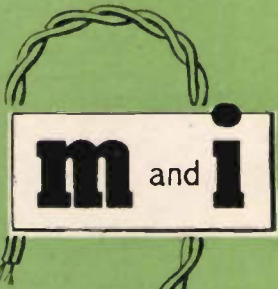
## **The MICANITE & INSULATORS Co Ltd**

EMPIRE WORKS, BLACKHORSE LANE, LONDON, E.17

Makers of MICANITE (Built-up Mica Insulation). Fabricated and Processed MICA, PAXOLIN (Synthetic-resin laminated sheets, rods, tubes and cylinders). High-voltage Bushings and Terminals for indoor and outdoor use. Empire Varnished Insulating Cloths and Tapes and all other forms of Electrical Insulation. Suppliers of Vulcanised Fibre, Leatheroid, Presspahn, etc. Distributors of Micoflex-Duratube Sleeveings, Micoflex-Durasleeve (plastic-covered flexible metal conduit) and Kenutuf Injection Mouldings (P.V.C.)



**m and i**

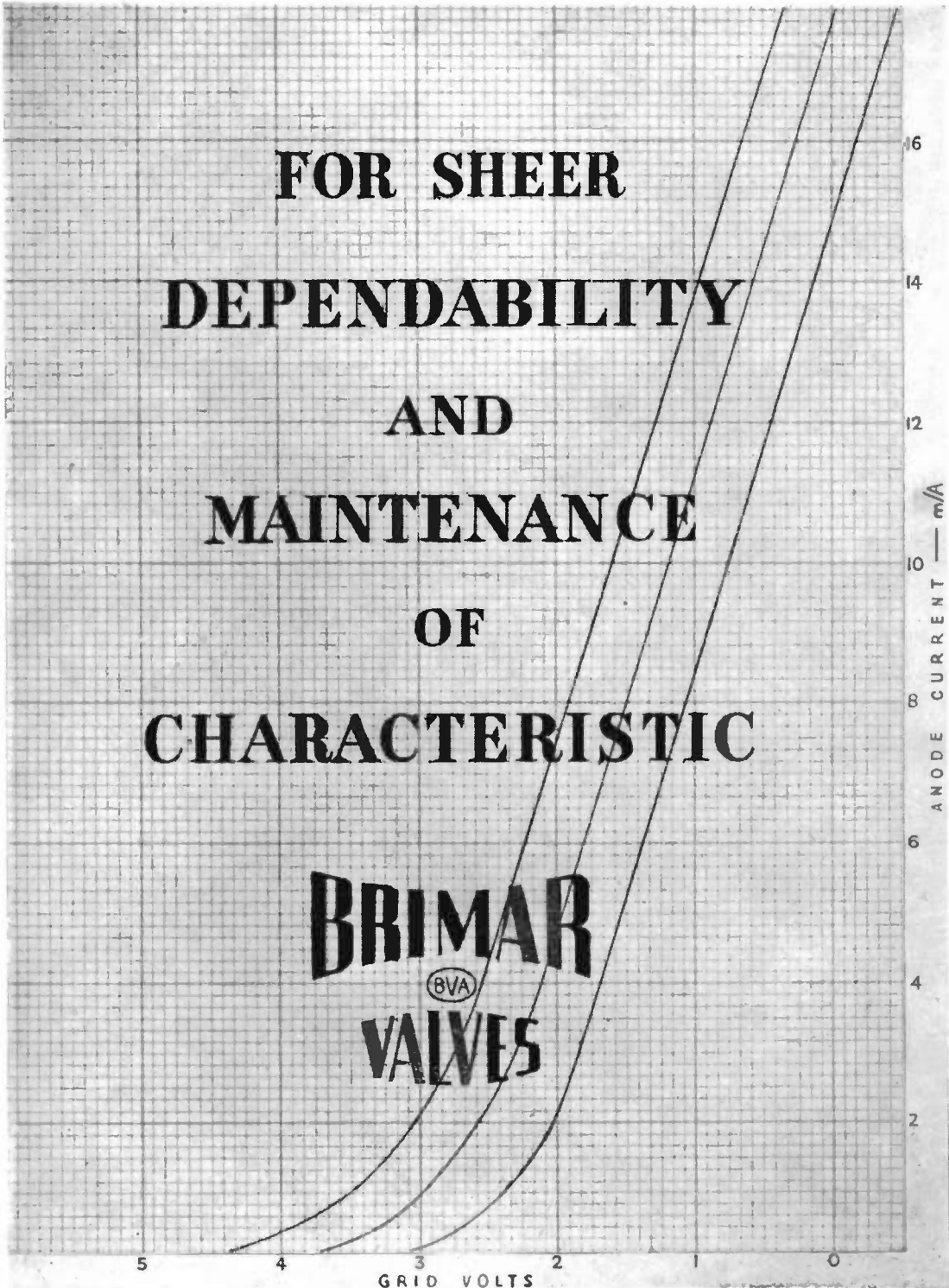


**FOR SHEER  
DEPENDABILITY  
AND  
MAINTENANCE  
OF  
CHARACTERISTIC**

**BRIMAR**  
**(BVA)**  
**VALVES**

ADVERTISEMENT OF STANDARD TELEPHONES AND CABLES LIMITED, FOOTSCRAY, SIDCUP, KENT.

# ELECTRONICS

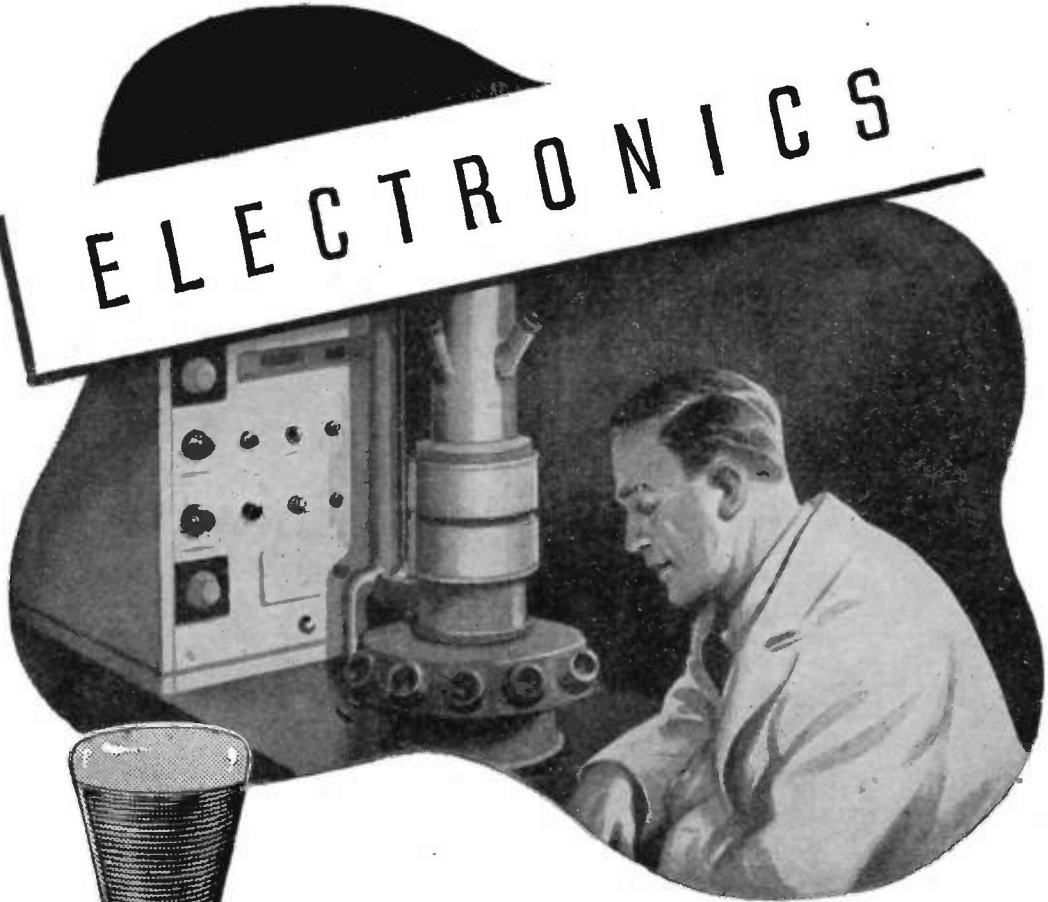

A typical G.E.C. Cathode Ray Tube 4102, with 2 3/4" screen, widely used in industry during the war, and with many peace-time applications.

## made it possible!


On the screen of the Electron Microscope, the scientist examines the characteristics of tiny organisms less than a millionth of an inch long. Electronics have, in fact, brought under scientific examination many germs and bacteria so small that they have never previously been observed in detail by the human eye.

G.E.C. Cathode Ray Tubes and OSRAM Valves cover every electronic application, and will bring to the pursuits of peace many well-tried electronic devices to speed, smooth, and make safer our way of life.

**Osram**  
PHOTO CELLS

**G.E.C.**  
CATHODE RAY TUBES

**Osram**  
Valves

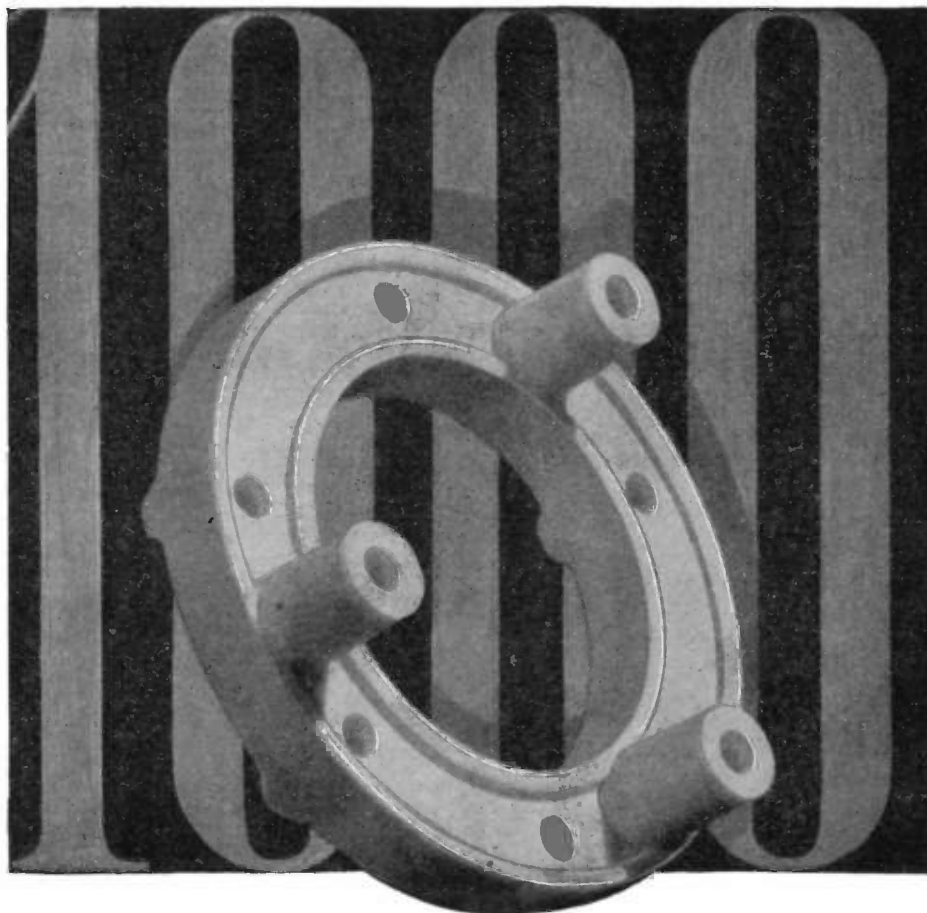

## specify **FREQUENTITE**

The range of Frequentite components covers more than a thousand pieces of every shape and size. Before finalising the design of new components consult



**STEATITE & PORCELAIN PRODUCTS LTD**

Head Office : Stourport-on-Severn, Worcs.

Telephone : Stourport 111

Telegrams : Steatint, Stourport

S.P.17

Now available for  
**LOW VOLTAGES**

12 v. and 24 v.

**SOLON** Industrial Type Electric Soldering Irons rated at 65 watts are now available for use for low voltages. Two models, one fitted with round pencil bit as illustrated, the other with oval tapered bit, they will do the same work as the well-known SOLONS of 65 watt rating for normal voltages.

Design incorporates the many special SOLON features, including fitting of heating element inside the bit. Both models can be supplied fitted with elements for 12 volts or 24 volts as required. Complete with 6 feet of HENLEY twin core flexible.

**SOLON**  
Electric  
SOLDERING IRON FOR INDUSTRIAL USE

Write for details of the complete SOLON range for low and normal voltages

W. T. HENLEY'S TELEGRAPH WORKS CO., LTD.  
(Eng. Dept.) 51-53, HATTON GARDEN, LONDON, E.C.1

## GOOD NEWS FOR RESISTANCE USERS!

BERCO Resistors and Potentiometer-rheostats are again available with moderately quick delivery.


The new 108-page BERCO Technical Catalogue gives detailed specifications, dimensioned drawings and illustrations of the widest range of fixed and adjustable resistances manufactured in this country. Your complimentary copy will be sent in response to your request on your business notepaper. Our engineers will be glad to cooperate with you in the application of resistors in your new equipment.

**THE BRITISH ELECTRIC RESISTANCE COMPANY LIMITED,**  
London Sales Office : 329 High Holborn, W.C.2.  
Phone : HOLborn 2994.

## Technical Reasons Why

# ★ ERSIN MULTICORE SOLDER

Is the Finest Cored Solder in the World

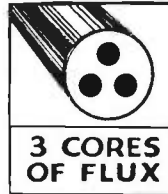


**3 CORES  
OF FLUX**

Three Cores of Flux ensure flux continuity. No lengths without flux are wasted. Consistent high quality joints are obtained with comparatively unskilled labour. Exactly the correct proportions of solder to flux are provided. Separate fluxing operations are obviated and no extra flux is required. The three cores of flux being evenly distributed over the cross section of the solder provide thinner solder walls than otherwise. This gives rapid melting and speeds up soldering. The flux does not tend to run out of the cores; so there is always a supply available for the next joint. The utmost economy of solder and flux is achieved.



Ersin, contained in the three cores of Ersin Multicore Solder, is the fastest non-corrosive flux. Possessing all the non-corrosive advantages of rosin, it enables joints to be speedily made on oxidised or "difficult" surfaces such as nickel. Ersin not only avoids oxidation during soldering but removes surface oxide already present—this is particularly advantageous in respect of materials that have been in stock or apparatus that is being serviced. The use of Ersin Multicore, with correct soldering technique, avoids "HR" or dry joints.

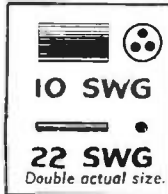

**10 SWG**

**22 SWG**

Double actual size.

Ersin Multicore Solder is made in most gauges between 10 and 22 S.W.G. (-128—028") (3.251—7.109 m/ms). For general radio and electrical production and maintenance 13 and 16 S.W.G. are in most demand.

**Virgin  
Tin & Lead**

Five alloys of Ersin Multicore Solder, made from virgin metals, are available—all antimony free. Under present circumstances 45% tin and 55% lead is the most widely used alloy.

Technically, Ersin Multicore Solder is far superior to any other cored solder. A practical laboratory or production test will demonstrate this and show you that it is the most economical solder to use. The majority of British and overseas manufacturers already enjoy the advantages of Multicore. If you do not, and are engaged upon Government contracts, write for further technical information and free samples.

Single reel rate nominal 1 lb. reels.

**13 SWG - 4/10**

**16 SWG - 5/3**

Above prices subject to usual trade discount.

½ cwt.—ton lots at bulk rate. 6d. cartons for home use, available at most good radio and electrical dealers, ironmongers, etc.

**MULTICORE SOLDERS LTD.** Commonwealth House,  
New Oxford St., London, W.C.1 Tel.: CHAncery 5171-2

PROPRIETORS :

HULTON PRESS, LTD.

# Electronic Engineering

MANAGING EDITOR:

G. PARR.

EDITORIAL, ADVERTISING AND PUBLISHING OFFICES, 43-44, SHOE LANE, LONDON, E.C.4

TELEPHONE  
CENTRAL 7400

Monthly (published last day of preceding month) 2/- net. Subscription Rates: Post Paid to any part of the World—6 months, 13/-; 12 months, 26/-. Registered for Transmission by Canadian Magazine Post.

TELEGRAMS  
HULTONPRES, LUD  
LONDON.

## Success

**W**HAT determines the success of an exhibition? The quality of the exhibits, the way it is talked about, or the number of people who were unable to get near it?

Judged by any of these standards, the recent Physical Society's Exhibition was an undoubted success. So much so that it is hoped it will never be repeated under the conditions which ruled in 1946. The figures of attendance have been variously put at from 10,000 to 70,000. To the unfortunates who were in the exhibition at closing time, the latter figure is more acceptable.

On another page appears a letter from a reader which is a fair sample of the comments which were made during the exhibition and after.

The truth is that the Exhibition even before the war was outgrowing its premises. From a small conversazione at which certain selected instruments were exhibited it has grown to a national scientific event of the year. After a six-year break it might have been foreseen that technical men from all parts would flock to exchange gossip and see what their colleagues had been doing in the interval. But the arrangements were organised as if no break had occurred—the same cramped accommodation, the same limited

time to study the accumulation of new equipment which the manufacturers were just as anxious to show as the visitors to see.

(Incidentally, those who arrived before opening time in many cases walked in and saw the show in comfort!)

However, there is no use in criticising the efforts of the organisers now that the show is over.

The Physical Society has done the greatest service to the community in founding a truly scientific exhibition. Let us hope that it will continue to encourage the electronic and physical industries by holding its exhibition on a limited scale, say by restricting the entries to research items, or by ruling out standard manufactured products.

On the other hand, it is time the industry itself organised a scientific exhibition in a more commodious building, to which invitation would be by ticket only. Such an exhibition, if it embodied the good features of its forerunner, would be an outstanding success. But it must be open for a reasonable period and the stands must be staffed by technical men who are more versed in the details of their equipment than in the latest brand of sales talk. The avoidance of elaborate stand dressing and advertising signs would help to maintain the scientific atmosphere which is such a feature of the Physical Society's Exhibition, and the participators would feel that their efforts were appreciated by visitors well qualified to pass judgment on them.

### Electronic Engineering Monographs

The third Monograph in the series is now ready. It is entitled:

**THE ELECTRON MICROSCOPE**  
BY DR. D. GABOR  
(Research Laboratory, B.T.-H. Co.)

Dr. Gabor is one of the foremost authorities on Electron Optics, and his monograph deals fully with the present developments in electron microscopes and their future possibilities.

Copies will be available through technical booksellers or direct from the Circulation Dept., Hulton Press, 43 Shoe Lane, E.C.4, price 4/9, post free.

Orders should be placed early as the number of copies is limited.

A limited quantity of the Monograph

**PLASTICS IN THE RADIO INDUSTRY**  
by E. G. Couzens, B.Sc., A.R.C.S. and W. G. Wearmouth, Ph.D., F.Inst.P.  
is still available.

This Monograph is obtainable through technical booksellers or direct from the Publishers at 43 Shoe Lane, E.C.4, price 2/6 or 2/8 post free.


## British Electronic Apparatus

Two examples of the many superlative specimens of British electronic equipment which were shown at the recent Physical Society's Exhibition. Over 100 manufacturers were represented in the Trade Section, and the Research Exhibits gave a good cross-section of the variety of projects on which the industry has been engaged during the past five years.

On the left is an instantaneous reading radio compass made by Standard Telephones & Cables, Ltd., incorporating an automatic direction finder using Adcock aerials and a C.R. tube indicator giving instantaneous readings. The readings are free from sense ambiguity.

There is a motor-driven gyro-repeater scale, with three indication speeds for various signals and interference conditions. Frequency range: 67.5-100 Mc/s. or 100-150 Mc/s.

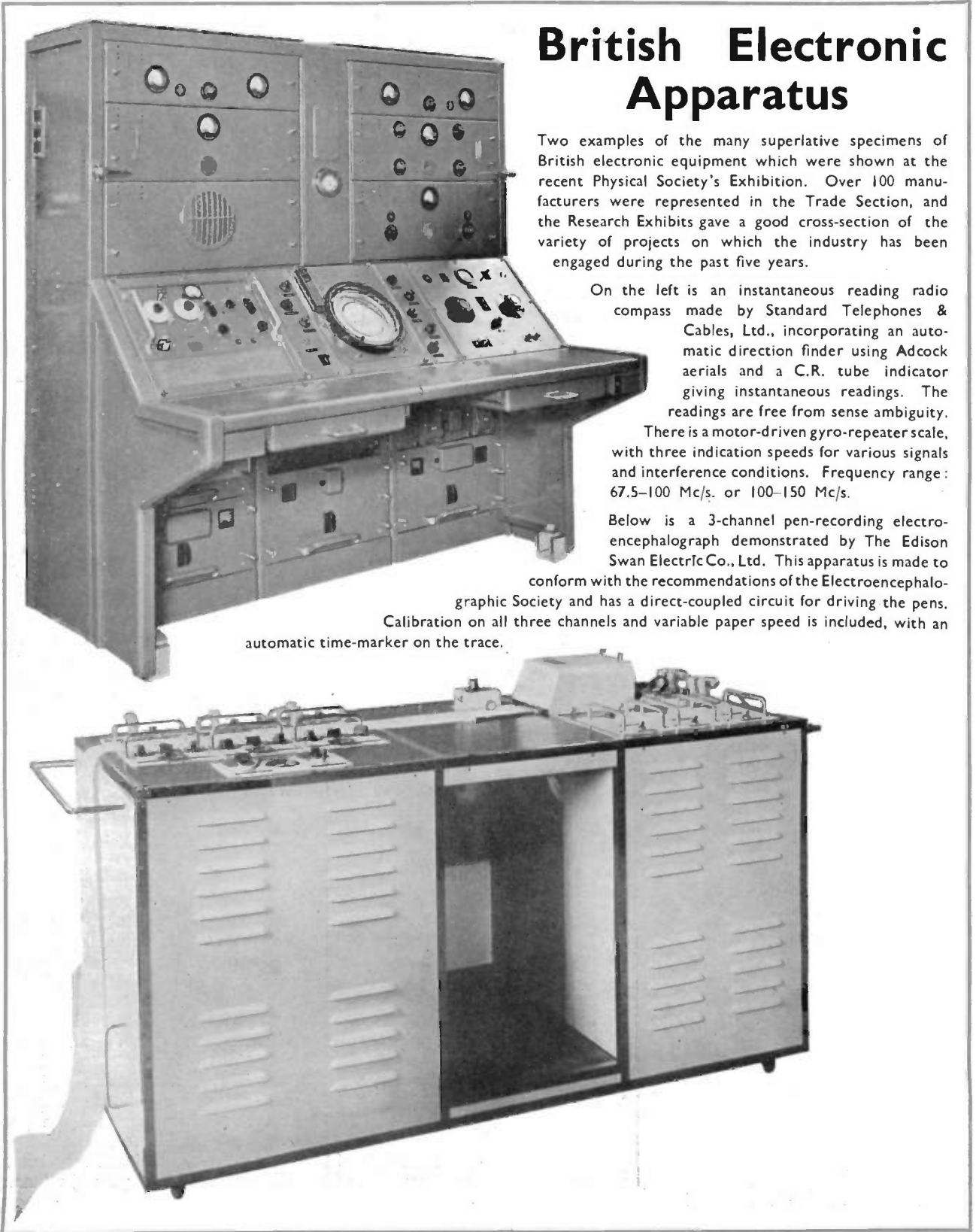Below is a 3-channel pen-recording electroencephalograph demonstrated by The Edison Swan Electric Co., Ltd. This apparatus is made to conform with the recommendations of the Electroencephalographic Society and has a direct-coupled circuit for driving the pens. Calibration on all three channels and variable paper speed is included, with an automatic time-marker on the trace.





## — further Examples of Electronic Equipment shown at the Physical Society's Exhibition

### Ammeter, Thermo-Couple Radio-Frequency

An improved form for use on currents up to 30 amp. at 13.5 metres, incorporating a concentric terminal system.

*Ernest Turner Electrical Instruments, Ltd.*

### Amplifier, D.C.

This amplifier has been developed for use with strain-measurement gauges on aeroplane parts. Its performance is summarised as follows:

**Gain:** A 12-position control is fitted giving gain variations from  $5 \times 10^3$  to  $7.5 \times 10^5$ .

**Input:** The input impedance is  $5 \times 10^8 \Omega$ , and is terminated in a concentric shielded socket.

**Frequency Response:** Linear from zero to 15,000 c/s.

**Output:** This is provided from a quasi-balanced circuit. Voltage output 170 V peak-to-peak; current output  $\pm 3.5$  mA.

**Stability:** The stability for full gain, referred to the equivalent input voltage, is 0.7 mV for the first hour and subsequently less than 0.1 mV per hour.

*Clifton Instruments, Ltd.*

### Audiometer, Dual (McDonald-Poliakoff)

This instrument has been designed by Dr. D. McDonald and Alexander Poliakoff for research work as well as for rapid routine testing of patients. It provides a guide to the patient's hearing aid requirements. The new audiometer consists essentially of two beat-frequency oscillators with independent attenuators, two earphones, two independently adjustable speech channels and a loud-speaker for measurement of masking with a hearing aid.

*Multitone Electric Co., Ltd.*

### Bridge, Resistance and Capacity

This instrument is designed for quick and accurate measurement of resistance and capacitance; provision is also made for testing leakage and power factor of capacitors. The null indicator is a visual electronic device so arranged that an out-of-balance of  $\pm 1$  per cent. is easily discernible; power factor of capacitors on all ranges is measured by an accurately calibrated control marked over a range of 0-60 per cent.

*Measuring Instruments (Pullin), Ltd.*

### Cables, H.F.

A range of high-frequency cables suitable for Radar and general high-frequency use. The dielectric is Telcothene, a mixture of 87½ per cent. polythene and 12½ per cent. polyisobutylene. The electrical properties of Telcothene are: dielectric constant 2.3, power factor between 0.02 per cent. and 0.03 per cent. at frequencies up to 3,000 Mc/s.

*The Telegraph Construction and Maintenance Co., Ltd.*

### Camera, High Speed

This camera permits the taking of 49 pictures on standard 35-mm. cinematograph film at a maximum rate of 10,000 pictures per second, and is designed for photographing of events which are self-luminous, or illuminated artificially or by daylight.

*Scophony, Ltd.*

### Centimetric Waves, Apparatus for the Measurement of

**General purpose test panel.** The unit contains two oscillators of klystron type and their associated power supplies. Each oscillator covers a different band of frequencies and either oscillator may be switched to the common wave-guide system, which includes attenuators, wave-meter and "slotted guide" type or standing wave indicator. Facilities are available for both amplitude and frequency modulation of the oscillators, while the indicating gear includes a mirror galvanometer for use under C.W. conditions and an amplifier and peak voltmeter to be used when the oscillators are amplitude modulated.

**Rotating standing wave detector.** In this apparatus a "slotted guide" is bent to form a semicircle in such a way that a pick-up probe, attached to a rotating drum, travels along the length of the slot. The output of the probe is taken to a crystal detector and hence to an amplifier and cathode-ray unit, the time base of which is synchronised to the rotation of the drum. The picture appearing on the cathode-ray tube is thus a graphical representation of the voltage appearing in the wave-guide and enables simultaneous measurement of both amplitude and phase of standing waves to be accomplished.

*Metropolitan-Vickers Electrical Co., Ltd.*



Wheatstone bridge of new design with built-in A.C. supply and galvanometer. Range, 0.1  $\Omega$ -10 M  $\Omega$ .

—Salford Electrical Instruments Ltd.



Automatic ohmmeter manufactured by the Mervyn Sound & Vision Co., Ltd. This automatically selects the optimum range for the resistance under test to give a reading on the most accurate part of the meter scale. Range, 1  $\Omega$ -10 M  $\Omega$ .

*Leland Instruments Ltd.*

(Below): Sensitive valve voltmeter with feedback amplifier. Range, 0.03-300 V in 9 steps. Frequency response linear from 10 c/s. to 1 Mc/s.

—Dawe Instruments Ltd.






(Left): Frequency spectrometer giving individual components of a complex waveform. 40-16,000 c/s. or 8 kc/s.-3,200 kc/s.

—Standard Telephones and Cables Ltd.

(Above): Photo-electric unit for automatic control of street lighting, signs etc.

—Lo:dex Ltd.

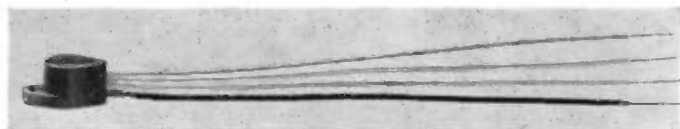

10 mA instrument rectifier moulded in case. Actual size.

—Salford Electrical Instruments Ltd

(Below): Distortion factor meter for measuring total harmonic content of A.F. apparatus.

—Dawe Instruments Ltd.



#### Colorimeter (Prof. E. J. King)

A very convenient instrument for the rapid measurement of colour depth. The readings are taken from the logarithmic scale on the galvanometer. Colour filters are provided to increase the accuracy. It can be operated from the mains supply or from a 2-V accumulator.

*Gambrell Bros. & Co., Ltd.*

#### Condensers, Vacuum

A range of vacuum condensers, in which the electrode system is supported within a glass envelope, developed for use in transmitting and electronic heating equipments. One of the main features of these new condensers is their high current-carrying capacity and high operating voltages.

*Scientific Acoustics, Ltd.*

#### Fault Tracer

This instrument comprises:—

(i) *Signal generator*, giving frequencies of 100 kc/s. to 20 Mc/s., modulated or unmodulated.

(ii) *Audio-frequency oscillator* of 1,000 c/s. fixed frequency with variable output.

(iii) *Signal tracer*, tracing the signal through the radio-frequency, frequency-changer, intermediate-frequency and low-frequency sections of high-frequency and low-frequency equipment.

(iv) *A.C. bridge*, 1,000 c/s., calibrated directly to measure resistance capacity and inductance over a wide range; condenser or insulation leakage test is also included; output indicator and H.T. 6.3 V available for external use.

Dimensions: 12 in. x 9 in. x 7 in. approximately. Finish; battleship grey and nickel-plated fittings.

*Labgear.*

#### Glass-Metal Joints by Centrifuging, Machine for Making

Suitable for making single and "back-to-back" cylindrical seals from about 10-mm. diameter upwards. The centrifuging technique is designed to eliminate tooling and blowing. The machine as shown was evolved to secure a quick method of glassing both ends of copper cylinders to provide anodes for radio valves.

*General Electric Co., Ltd.*

*M.O. Valve Co., Ltd.*

#### Glass-Sealing Alloys—Telcoseal 1, 2, and 3

These are suitable for glass from the borosilicate to the lead types with their wide variety of coefficient of expansion.

*The Telegraph Construction and Maintenance Co., Ltd.*

**Instrument, Suspended Moving-Coil**

A conventional moving-coil instrument in which the normal pivots and jewels are replaced by a special taut suspension of beryllium-copper strip. This gives a shock-proof and frictionless instrument, which can be calibrated to a high degree of accuracy.

*The Record Electrical Company, Ltd.*

**Instruments, Super-Sensitive**

Of the P.M. moving-coil double-pivoted type. Special care has been taken to keep the resistance as low as possible consistent with the maximum degree of reliable service. The Model 23, 3½-in. type, can be supplied with a full-scale deflection as low as 10  $\mu$ A at 2,000  $\Omega$  approximately. The Model 32, 6-in. type, has a sensitivity of 20  $\mu$ A for a resistance of 5,000  $\Omega$ .

*Ernest Turner Electrical Instruments, Ltd.*

**Insulation Resistance Ohmmeter and Insulation Tester**

The principle of operation is that of the impression of a D.C. voltage on an unknown and a standard resistance in series. The voltage drop across the standard is a function of the current through the unknown resistance and is measured by a valve voltmeter.

Test voltages up to 5,000 can be provided, the resistances incorporated in the test circuit limit the current to a safe value on short-circuit.

*Jackson Automatic Controls, Ltd.*

**Lockstrip**

A unit product in tropical insulating material for carriage, housing and protection of small condensers and resistances, etc. A universal connexion device with four basic plates covers almost any requirements. Single- or double-ended tags for connexion fitted to requirements.

*Labgear.*

**Optical Cement**

Used for preparing joints between glass and glass, between "Perspex" and metal, and between metal and metal.

*Imperial Chemical Industries, Ltd.*

**Plastics**

"Perspex" in the forms of sheet, blocks and rods. Examples of shaping, machining and cementing. Applications are cabinets, tanks, photometric equipment, machine casings, drawing instruments and metal-coated reflecting sheets.

*Imperial Chemical Industries, Ltd.*

**Process Timers, Impulse Operated**

(S. J. Smith R. St. G. Terry and the Company's Patents Nos. 566345, 568975.) The single- and dual-hand instruments are examples of impulse-operated timers in their simplest form. The action of setting the hand to the required time for the process has the effect of closing the impulsing circuit, and the time measurement commences. When approaching the end of the run an alarm circuit is set in operation, at the conclusion of which all circuits are automatically opened.

*Telephone Manufacturing Co., Ltd.*

**Radio-Frequency Heating**

A demonstration of rapid continuous concentration of chemical solutions which are sensitive to temperatures above a critical limit. This is achieved by feeding the solution down through two bulbs, which trap any rising foam, into a glass cylinder, on each side of which is an electrode. The liquid boils, energy being furnished by a Redifon R.H.2 generator. The top globe is connected to a pump which maintains a vacuum sufficient to lower the boiling temperature to the required figure—in this case about 10° C.

*Rediffusion, Ltd.*

**R.F. Dielectric-Heating Equipment**

A self-contained generating and heating unit of 4 kW input delivering up to 2 kW at 35 Mc/s. operating on 200-250 V single-phase 50 c/s. supplies. It has been designed primarily for heating plastic moulding materials and general small-scale heating. The high-frequency generator is a push-pull oscillator employing two triode valves, fed from a D.C. unit in the same cubicle at 3,500 V.

*Wild-Barfield Electric Furnaces, Ltd.*

**Relay, Direct Current**


Having a low coil-consumption in the lower voltage range of approximately 1 W and fitted with beryllium-copper contacts capable of handling 10 amp. at 230 V, A.C. or D.C. This relay can be fitted with a mercury switch up to 30 amp., 230 V capacity if desired.

*Hendrey Relays, Ltd.*


**Relay, High Sensitivity, Type H**

A very sensitive high-torque high-speed relay of the moving-coil pattern.

*Elliott Brothers (London), Ltd.*

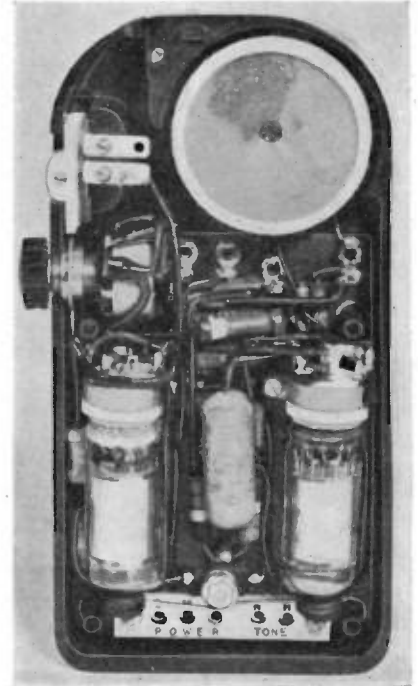

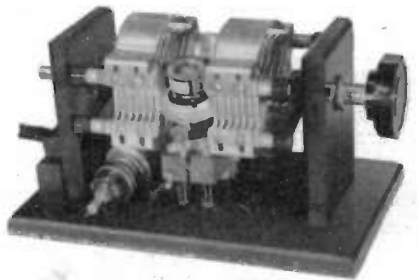Pocket two-valve hearing aid with crystal microphone.  
—Multitone Electric Co., Ltd.



Butterfly oscillator and absorption wave meter covering 250-650 Mc/s. and 250-850 Mc/s.  
—British Thomson-Houston Co., Ltd.

(Below): Highly sensitive multi-range volt-ammeter 100,000  $\Omega$ /V.  
—H. Tinsley & Co., Ltd.



**Relay, High-Sensitivity Snap Action**

With a new type of movement, the action of which is shown by the sketch.

→  
*W. G. Pye & Co., Ltd.*

**Relay, High-Speed Polarised**

(R. E. H. Carpenter's Patents Nos. 315496, 484472 and 559047.) This, the latest form of the Carpenter relay has been designed to combine in one instrument high speed, high sensitivity, and high contact pressure together with a high degree of immunity to external vibration. Two chief types are shown: the standard form, intended for general use, where the greatest robustness and reliability of operation are designed, combined with ample sensitivity for most circuit conditions; and a special model in which considerably higher sensitivity has been achieved.

→  
*Telephone Manufacturing Co., Ltd.*

**Relay, Solenoid Operated**

Incorporating a mechanical escapement mechanism adjustable in three ranges to give any time delay between 5 seconds and 1½ minutes. The coil can be wound for either A.C. or D.C. operation.

*Hendrey Relays, Ltd.*

**Remote Indication, Smith "Desynn" System**

An electrical system for the transmission of indicator movement with accuracy and rapid response. The transmitter, in its simplest form, embodies a circular resistance with three equally spaced tappings and diametrically disposed rotating contacts carrying the 24-V D.C. input.




The "Desynn" indicator has a slotted iron stator with star-connected 3-phase distributed winding to which the tappings of the transmitter resistance are connected. Within the stator is pivoted a permanent magnet, forming a two-pole armature, and carrying the pointer. The position of the contacts of the transmitter resistance influences the strength and direction of the currents in the indicator stator windings, causing the armature to assume a position dependent on that of the transmitter contacts.

*S. Smith & Sons (England), Ltd.*

**Series Plug and Socket**

New model, for inserting ammeters into circuits without interrupting the current when performing experiments.

*The London Instrument Co., Ltd.*

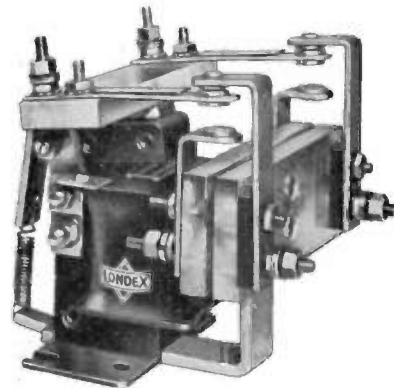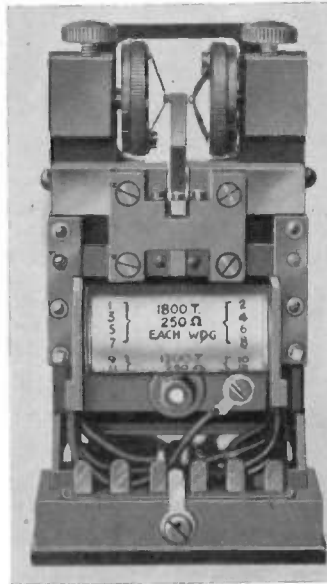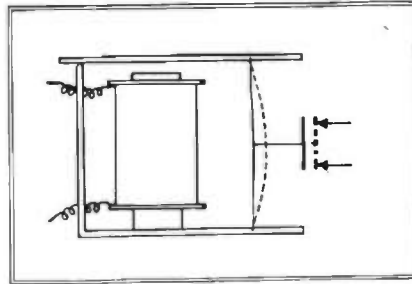

**Heavy-duty relay for automatic starting and stopping of power-driven equipment.**

—Londex Ltd.

**Signal Generator**

Type TF.867, a new design of signal generator for measurements in the range 15 kc/s.-30 Mc/s. mains operated.

*Marconi Instruments, Ltd.*

**Switches, Mercury**

(i) An entirely new range of industrial switches, with exceptionally heavy overload characteristics and ability to interrupt currents far in excess of their rating.

(ii) A new range of switches fitted with platinum contacts giving exceedingly low and constant resistance.

(iii) Novel delay-action switches with new features.

*Mercury Switch Manufacturing Co., Ltd.*

**Switch—****Combined Time-Switch and Time-Checker (E. A. Harvey)**

A portable A.C. mains-operated switch, which can be used to control an external circuit carrying up to 5 amp. at 250 V, or to measure the period during which an external pair of contacts is closed. When it is used for the latter purpose, *i.e.*, as a "time-checker," three ranges are available: 0.02-19.98 sec. in steps of 0.02 sec.; 0.1-99.9 sec., in steps of 0.1 sec.; and 1-999 sec., in steps of 1 sec.

*Ilford, Ltd.*

**Synchronous Induction Motor**

A synchronous motor which, when connected to a 100-V, 50-c/s. A.C. single-phase supply, rotates at 3,000 r.p.m. and consumes 10 W, the power factor of the complete circuit being unity. Reversal of rotation is obtained by connecting the condenser in parallel with either one of the phase windings, which are identical in all respects.

*Scophony, Ltd.*

**Temperature Controller**

Designed for electric on-off control. The duration of on-to-off period is directly proportional to the amount of departure from the control point. If the furnace temperature is well below the control point, the instrument is continuously on and maintains a continuous heat-input. As the control temperature comes within the throttling range of the instrument the ratio of the on to the off period is progressively reduced until control point is reached. This is accomplished by using two opposing galvanometers to actuate the necessary power relay. When the temperature falls away the galvanometers deflect in opposition; one

actuating the power-relay and the other acting as a restoring device in such a way that the duration of on-off is proportional to departure from control point. A further feature of this instrument is the utilisation of a superimposed current to eliminate galvanometer contact resistance; as soon as the galvanometer contacts close, a current of correct polarity is superimposed to deflect the galvanometer further and so break down contact resistance.

*Bristol's Instrument Co., Ltd.*

#### Tester, Valve

Designed for the rapid testing of valves. Tests of mutual conductance, emission of diodes and rectifiers, and heater-cathode insulation are provided for. The instrument is fully mains operated. Switches are fitted for the application of suitable voltages to anode, screens, etc., and heater voltages between 1.4 and 40. Interchangeable valve sockets covering the majority of valves are provided. A high-speed relay fitted in the instrument protects it from damage, should a valve be defective.

*Gambrell Bros. & Co., Ltd.*

#### Testmeter, Multi-Range Electronic

This instrument consists of a highly stable thermionic D.C. millivoltmeter with suitable additional circuit switching to enable D.C. and A.C. voltage, D.C. current, resistance, capacity and power measurements to be made over a very wide range. In all, 47 ranges are provided.

Besides the basic D.C. millivolt, six D.C. voltage ranges are provided having full-scale deflections of 1, 2, 5, 25, 100, 250 and 1,000 V. The input resistance on all these ranges is 11.1 M $\Omega$ , while an external "x 10" multiplier increases the input resistance to 111.1 M $\Omega$  and enables D.C. voltages up to 10,000 V to be measured. Ten D.C. ranges are provided, allowing measurements from 0.25  $\mu$ A to 1 amp., the millivolt drop on all ranges being 150 mV. Three resistance ranges enable measurements to be made from a fraction of 1  $\Omega$  to 10 M $\Omega$ , while an additional insulation range is graduated from a minimum indication of 1 M $\Omega$  to a maximum of 1,000 M $\Omega$ .

*The Automatic Coil Winder & Electrical Equipment Co., Ltd.*

#### Transformers, D.C. Current

The operation of the D.C. current-transformer depends on the fact that the impedance of an iron-cored inductance falls when magnetised by a



Panel-mounting microammeter only 1½ in. in diameter, moving-coil type.

—Nalder Bros. & Thompson Ltd.




Multi-range A.C. D.C. testmeter. 1,000  $\Omega$ /V with safety and overload devices.

—General Electric Co., Ltd.

(Below): Multiple selenium photo-cell with series elements suitable for load resistances of 1 M $\Omega$ . Actual size.

—Evans Electro selenium Ltd.

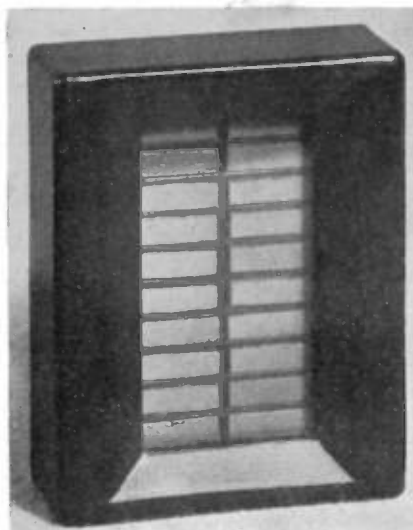

direct current, and, by applying an alternating voltage (not necessarily constant) to a secondary winding, a current proportional to the direct current results. In order to eliminate inductive interference by the A.C. with the D.C. circuits, two cores are employed, so connected that during a given half-cycle the A.C. and D.C. assist one another in one core and oppose one another in the other core. The D.C. current transformer may with equal facility be used for operating, indicating and recording ammeters, relays, wattmeters or watt-hour-meters.

*Everett, Edgcumbe & Co., Ltd.*

#### Valves, Electrometer

The single electrometer valve already developed has similar electrical characteristics to the F.P.54 and can be used in the conventional circuits as described by Du Bridge and Brown (*Rev. Sci. Inst.*, 1933, 4, 533). The design of the double valve exhibited was suggested by Dr. J. C. M. Brentano. This is a double-tetrode tube in which both tetrode sections draw their emission from a single filament and each section resembles the F.P.54 in electrical characteristics.

*Ferranti, Ltd.*

#### Valve, Radio, Demonstration Panel

A number of instruments, with controls for adjusting appropriate voltages to the different electrodes, together with the necessary power supply, is assembled in a convenient form for demonstrating every type of valve used in radio reception. Every important characteristic is clearly and simultaneously indicated, the uses and misuses being instantly apparent. Primarily designed for the instruction of students, it is equally applicable for laboratory use.

*Everett, Edgcumbe & Co., Ltd.*

#### Voltage Selector

Voltage selector designed for laboratory use. It consists of a transformer with windings and tappings so arranged that any voltage from 1 to 599 can be selected by switches arranged in decade.

*Gresham Transformers, Ltd.*

#### Wattmeter, Portable Suspended

A deflectional instrument suitable for frequencies up to 20 kc/s.

*Elliott Brothers (London), Ltd.*

#### Wavemeter, Direct-Reading Oscillating (30 kc/s.-60 Mc/s.)

An improved model of the original Sullivan-Griffiths dynatron wavemeter, but now incorporating a nega-



5-kW silica-seal mercury vapour lamp with 100 amp. tapered strip molybdenum seals.  
—British Thomson-Houston Co., Ltd.


tive resistance valve circuit designed to use modern valves. Accuracy 1 part in 10,000 immediately upon switching on. Short-period stability a few parts in  $10^6$ . Direct-reading frequency scales to an accuracy of 0.01 per cent. Linear frequency law giving negligible interpolation error, the accuracy of simple interpolation being 2 parts in  $10^6$ . Calibration independent of valve replacement. Fitted with crystal-checking circuit. Mains or battery operated.

*H. W. Sullivan, Ltd.*

#### Layer-Type Batteries

These batteries are specially constructed in an exceedingly compact form for use in small radio transmitters and receivers. The normal carbon rod is replaced by a thin conducting layer on the surface of the zinc plate of the adjacent cell, thus eliminating soldered contacts between cells. The elements are completely enclosed in a light plastic container which gives good intercell insulation. The efficiency per unit volume has been increased up to about 70 per cent.

*General Electric Co., Ltd.*

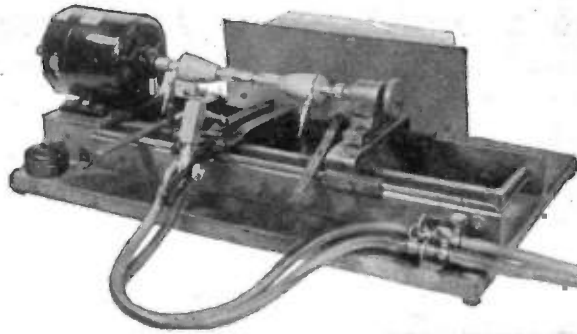


Machine for making glass-to-metal seals by centrifuging.

—G.E. Research Laboratories

(Right): "Cathodray" capacitors specially designed for smoothing circuits of C.R. tube supplies.

—Telegraph Condenser Co., Ltd.

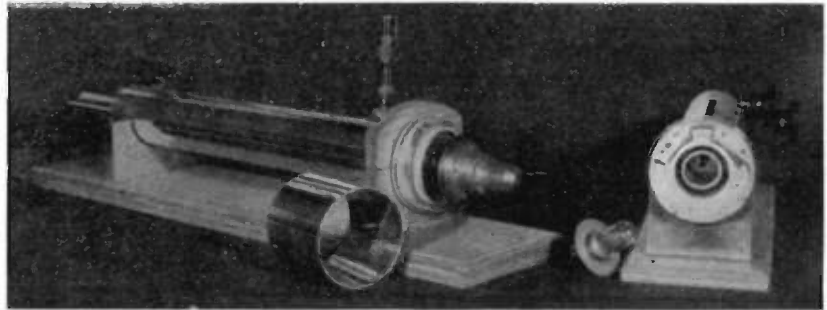

#### Generator, Cathode-Ray Tube Dot-Mosaic

This apparatus is a mechanically switched scanning generator, useful in determining the linearity of the deflectional response of all electrostatic cathode-ray tubes.

*A. C. Cossor, Ltd.*

#### Sensitive Materials for Photographic Recording with the Cathode-Ray Oscillograph

The following materials are specially manufactured for recording: Films, 5R101 (Panchromatic), 5G91 (Orthochromatic), and 5B52 (not colour-sensitised); and Paper, BP1. An exhibit showed one of the special characteristics of 5B52 film, which employs a dyed emulsion on yellow-dyed base, to minimise image-spread, and is thus especially suitable where a wide range of writing-speeds is encountered in a single trace.

*Ilford, Ltd.*

#### Corrections

##### Multi-Range Electronic Tester

In the January issue (p. 15) the manufacturer's name was omitted from a description of this instrument. It is the Automatic Coil Winder and Equipment Co.

##### SenTerCel Rectifiers

Messrs. Standard Telephones & Cables, Ltd., point out that these rectifiers are of the selenium type and not copper oxide as stated in the January issue (p. 18).

#### CV90 Oscillator

CV90 is a triode oscillator valve designed for use with a double coaxial resonator of the type shown. The contacts between the valve electrodes and the circuit are self-locking and permit easy insertion and withdrawal of the valve. (Photograph above.)

One coaxial resonator forms a circuit between the anode and grid of the valve and the other resonator forms a circuit between the grid and cathode. The resonators are independently tuned by means of sliding short-circuiting plungers controlled by rack and pinion mechanisms. "Feedback" is obtained by a built-in capacitance between anode and cathode inside the valve itself. This circuit covers a range of 10 cm. to 100 cm. (300 to 3,000 Mc/s.).

#### CV257 Power Amplifier

This circuit is tunable over the range from 300 Mc/s. to 1,000 Mc/s. The conspicuous feature is that there is no tuning in the grid cathode circuit, the input impedances of the valve matching the characteristic impedances of the R.F. input couple reasonably well.

*—General Electric Co., Ltd.*

# Classified List of Products and Exhibitors

(For addresses of firms mentioned, see Directory, page 44)

## Aircraft Instruments

S. Smith & Sons (England) Ltd.  
Honeywell-Brown Ltd.  
Henry Hughes & Son Ltd.  
George Kent Ltd.  
Cambridge Instrument Co., Ltd.  
Ferranti Ltd.  
Sangamo Weston Ltd.  
De Havilland Aircraft Co., Ltd.

## Amplifiers

Standard Telephones & Cables Ltd.  
Negretti & Zambra Ltd.  
Salford Electrical Instruments Ltd.  
Everett, Edgcombe & Co., Ltd.  
H. Tinsley & Co., Ltd.  
Clifton Instruments Ltd.

## Blooming, Optical Surfaces

Leech Optical Co., Ltd.  
Adam Hilger Ltd.  
Wray (Optical Works) Ltd.  
Barr & Stroud Ltd.

## Bridges, Electrical

Labgear.  
Dawe Instruments Ltd.  
Sunvic Controls Ltd.  
Measuring Instruments (Pullin) Ltd.  
Baldwin Instrument Co., Ltd.  
Salford Electrical Instruments Ltd.  
H. W. Sullivan Ltd.  
H. Tinsley & Co., Ltd.  
Gambrell Bros. & Co., Ltd.  
Muirhead & Co., Ltd.  
British Physical Laboratories Ltd.  
G.E.C. Ltd. (Research Laboratories).  
Leland Instruments Ltd.

## Cables, H.F.

Telegraph Construction & Maintenance Co., Ltd.  
British Insulated Callender's Cables Ltd.

## Calculating Machines

Scientific Computing Service Ltd.

## Cameras

Avlmo Ltd.  
Unicam Instruments Ltd.  
Kodak Ltd.  
W. Vinten Ltd.  
Wray (Optical Works) Ltd.  
Cambridge Instrument Co., Ltd.  
A. C. Cossor Ltd.  
Scophony Ltd.

## Capacitors

E. K. Cole Ltd.  
Scientific Acoustics Ltd.  
Telegraph Condenser Co., Ltd.  
Quickfit & Quartz Ltd.  
Erie Resistor Ltd.  
Labgear.  
Johnson, Matthey & Co., Ltd.  
Dawe Instruments Ltd.  
Standard Telephones & Cables Ltd.  
H. W. Sullivan Ltd.  
H. Tinsley & Co., Ltd.  
Gambrell Bros. & Co., Ltd.  
Muirhead & Co., Ltd.

## Clocks, Master

Telephone Manfg. Co., Ltd.  
Everett, Edgcombe & Co., Ltd.

## Colour and Colorimetry

Evans Electroelenium Ltd.  
Tintometer Ltd.  
Gambrell Bros. & Co., Ltd.  
Automatic Coil Winder & Electrical Equipment Co., Ltd.  
General Electric Co., Ltd.  
British Thomson-Houston Co., Ltd.

## Comparators, Electrical

Dawe Instruments Ltd.  
Standard Telephones & Cables Ltd.  
Elliott Bros. (London) Ltd.  
General Electric Co., Ltd.  
Leland Instruments Ltd.

## Comparators, Mechanical, Optical

Labgear.  
Crescent Gauges Ltd.  
Precision Tool & Instrument Co., Ltd.  
Cambridge Instrument Co., Ltd.  
Salford Electrical Instruments Ltd.

## Converters (Rotary ; Phase)

Standard Telephones & Cables Ltd.  
Westinghouse Brake & Signal Co., Ltd.

## Counters

Phillips Lamps Ltd.  
Ferranti Ltd.

## Crack and Flaw Detectors

Henry Hughes & Son Ltd.  
Metropolitan-Vickers Electrical Co., Ltd.  
Salford Electrical Instruments Ltd.

## Crystals

Marconi's Wireless Telegraph Co., Ltd.  
Salford Electrical Instruments Ltd.  
Marconi Instruments Ltd.  
General Electric Co., Ltd.

## Detonation Meter

D. Napier & Son Ltd.

## Dials and Drives

Telephone Manufacturing Co., Ltd.  
Muirhead & Co., Ltd.

## Diamond Dies

General Electric Co., Ltd.

## Dust Cores

Salford Electrical Instruments Ltd.  
Standard Telephones & Cables Ltd.

## Echo-Sounder

Henry Hughes & Son Ltd.

## Filters (Optical)

Ross Ltd.  
Johnson, Matthey & Co., Ltd.  
Chance Bros. & Austinlite Ltd.  
Standard Telephones & Cables Ltd.

## Flow Measurement

Rotameter Manufacturing Co., Ltd.  
W. Edwards & Co. (London) Ltd.  
George Kent Ltd.  
Elliott Bros. (London) Ltd.

## Fluorimetry

Kodak Ltd.  
Adam Hilger Ltd.  
H. Tinsley & Co., Ltd.  
Automatic Coil Winder & Electrical Equipment Co., Ltd.

## Fluxmeter

Cambridge Instrument Co., Ltd.

## Fork, Valve-Maintained

Muirhead & Co., Ltd.

## Frequency Meters, Controllers and Indicators

Salford Electrical Instruments Ltd.  
Everett, Edgcombe & Co., Ltd.  
Nalder Bros. & Thompson Ltd.  
Marconi Instruments Ltd.  
General Electric Co., Ltd.

## Furnaces

R. M. Catterson-Smith.  
A.E.W. Ltd.  
Johnson, Matthey & Co., Ltd.  
Foster Instrument Co., Ltd.  
Wild-Barfield Ltd.

## Galvanometers

Baldwin Instrument Co., Ltd.  
Cambridge Instrument Co., Ltd.  
H. Tinsley & Co., Ltd.  
Gambrell Bros. & Co., Ltd.  
W. G. Pye & Co., Ltd.  
Marconi Instruments Ltd.

## Gauges (Mechanical)

Taylor, Taylor & Hobson Ltd.  
W. Edwards & Co. (London) Ltd.

## Gauges (Vacuum)

Taylor, Taylor & Hobson Ltd.  
W. Edwards & Co. (London) Ltd.

## Glass Cells (Optical)

Tintometer Ltd.

## Glass Tubing

Chance Bros. & Austinlite Ltd.  
Griffin & Tatlock Ltd.  
Townson & Mercer Ltd.

## Glass-Metal Seals and Joints

Adam Hilger Ltd.  
General Electric Co., Ltd.  
British Thomson-Houston Co., Ltd.  
Telegraph Construction Co., Ltd.

## Graticules

Johnson, Matthey & Co., Ltd.  
Kodak Ltd.

## Heating Apparatus (Electrical and Electronic)

R. M. Catterson-Smith.  
Wild-Barfield Electric Furnaces Ltd.  
Scientific Acoustics Ltd.  
A.E.W. Ltd.  
Quickfit & Quartz Ltd.  
Baird & Tatlock (London) Ltd.  
Johnson, Matthey & Co., Ltd.  
Bristol's Instrument Co., Ltd.  
Rediffusion Ltd.  
Standard Telephones & Cables Ltd.  
Elliott Bros. (London) Ltd.  
Foster Instrument Co., Ltd.

## Impactometer

Salford Electrical Instruments Ltd.

## Impedance Measurement

Dawe Instruments Ltd.  
Standard Telephones & Cables Ltd.  
H. W. Sullivan Ltd.  
General Electric Co., Ltd.  
Leland Instruments Ltd.

## Inductance Standards and Measurement

H. W. Sullivan Ltd.

## Inductance Tuning

Standard Telephones & Cables Ltd.

## Instruments, Indicating

See Meters, Indicating.

## Insulation Measurement

Jackson Automatic Electric Controls Ltd.  
Dawe Instruments Ltd.  
Zenith Electric Co., Ltd.  
Everett, Edgcombe & Co., Ltd.  
H. Tinsley & Co., Ltd.

## Integrators

W. F. Stanley & Co., Ltd.  
W. G. Pye & Co., Ltd.

## Interferometers

Fibreglass Ltd.  
Adam Hilger Ltd.

## Klystrons

E. K. Cole Ltd.  
Ferranti Ltd.  
British Thomson-Houston Co., Ltd.  
The M.O. Valve Co., Ltd.

**Lamps (Special)**

Charles Baker  
Kodak Ltd.  
Adam Hilger Ltd.  
General Electric Co.,  
Ferranti Ltd.

**Lenses**

Ross Ltd.  
Newton & Co., Ltd.  
J. H. Dallmeyer Ltd.  
Taylor, Taylor & Hobson Ltd.  
R. & J. Beck Ltd.  
Leech Optical Co., Ltd.  
Pullin Optical Co., Ltd.  
Wray (Optical Works) Ltd.  
Barr & Stroud Ltd.

**Light and Lighting Controls**

Baldwin Instrument Co., Ltd.  
Record Electrical Co., Ltd.  
General Electric Co., Ltd.

**Lubricant Testing**

D. Napier & Son Ltd.

**Magnetic Field Measurement**

Metropolitan-Vickers Electrical Co., Ltd.  
Cambridge Instrument Co., Ltd.

**Magnetic Materials**

Electro Methods Ltd.  
Standard Telephones & Cables Ltd.  
Permanent Magnet Association.  
Telegraph Construction & Maintenance Co.

**Magnetrons**

Marconi's Wireless Telegraph Co., Ltd.  
General Electric Co., Ltd.  
British Thomson-Houston Co., Ltd.

**Medical Apparatus**

Cambridge Instrument Co., Ltd.  
A. C. Cossor Limited  
Clifton Instruments Ltd.  
Marconi Instruments Ltd.  
Edison Swan Electric Co., Ltd.

**Metal Spraying**

Metallisation Ltd.

**Meters, Indicating**

Dawe Instruments Ltd.  
Baldwin Instrument Co., Ltd.  
Standard Telephones & Cables Ltd.  
Salford Electrical Instruments Ltd.  
Everett, Edgcombe & Co., Ltd.  
Ferranti Ltd.  
Sangamo Weston Ltd.  
Record Electrical Co., Ltd.  
Automatic Coil Winder & Electrical Equipment Co., Ltd.  
Ernest Turner Electrical Instruments Ltd.  
British Physical Laboratories Ltd.  
Elliott Bros. (London) Ltd.

**Metrology**

E. R. Watts & Son Ltd.  
W. Edwards & Co. (London) Ltd.

**Microphones**

Standard Telephones & Cables Ltd.

**Microscopes**

Avimo Ltd.  
Cooke, Troughton & Simms Ltd.  
Taylor, Taylor & Hobson Ltd.  
Charles Baker.  
Precision Tool & Instrument Co., Ltd.  
Metropolitan-Vickers Electrical Co., Ltd.

**Microscopes (Electron)**

Metropolitan-Vickers Electrical Co., Ltd.

**Mirrors**

Ross Ltd.  
Leech Optical Co., Ltd.  
Chance Bros. & Austintite Ltd.

**Moisture Meters**

Dawe Instruments Ltd.  
Baldwin Instrument Co., Ltd.  
Mullard Wireless Service Co., Ltd.  
Marconi Instruments Ltd.  
Record Electrical Co., Ltd.

**Motors (Small)**

Scophony Ltd.  
Drayton Regulator & Instrument Co., Ltd.  
Standard Telephones & Cables Ltd.  
Marconi Instruments Ltd.

**Navigation Aids**

Henry Hughes & Son Ltd.  
Standard Telephones & Cables Ltd.  
Nalder Bros. & Thompson Ltd.  
Decca Navigator Co., Ltd.  
Ferranti Ltd.

**Noise Measurement**

Standard Telephones & Cables Ltd.

**Ohmmeters**

Elliott Bros. (London) Ltd.  
Evershed & Vignoles Ltd.  
Record Electrical Co., Ltd.  
British Physical Laboratories Ltd.  
Leland Instruments Ltd.

**Optical Equipment**

Scophony Ltd.  
R. & J. Beck Ltd.  
Adam Hilger Ltd.  
Pullin Optical Co., Ltd.  
Salford Electrical Instruments Ltd.  
Barr & Stroud Ltd.  
E. R. Watts & Son Ltd.

**Oscillators**

Labgear.  
Dawe Instruments Ltd.  
Mullard Wireless Service Co., Ltd.  
Standard Telephones & Cables Ltd.  
Salford Electrical Instruments Ltd.  
H. W. Sullivan Ltd.  
A. C. Cossor Ltd.  
Muirhead & Co., Ltd.  
Marconi Instruments Ltd.  
Automatic Coil Winder & Electrical Equipment Co., Ltd.  
British Physical Laboratories Ltd.  
British Thomson-Houston Co., Ltd.  
Leland Instruments Ltd.

**Oscillographs, -scopes**

Henry Hughes & Son Ltd.  
Mullard Wireless Service Co., Ltd.  
Salford Electrical Instruments Ltd.  
A. C. Cossor Ltd.

**pH Meters and Recorders**

Griffin & Tatlock Ltd.  
Cambridge Instrument Co., Ltd.  
Muirhead & Co., Ltd.  
Marconi Instruments Ltd.

**Photo-Cells**

Evans Electroelenium Ltd.  
Salford Electrical Instruments Ltd.

**Photographic Material and Equipment**

Townson & Mercer Ltd.  
J. H. Dallmeyer Ltd.  
Leech Optical Co., Ltd.  
Ilford Ltd.  
Wray (Optical Works) Ltd.  
Ferranti Ltd.  
Gambrell Bros. & Co., Ltd.  
Sangamo Weston Ltd.  
Kodak Ltd.

**Photometry**

Adam Hilger Ltd.  
Baldwin Instrument Co., Ltd.  
Salford Electrical Instruments Ltd.  
Everett, Edgcombe & Co., Ltd.

**Pinhole Testers**

Salford Electrical Instruments Ltd.  
British Physical Laboratories Ltd.

**Plastics**

Telegraph Construction & Maintenance Co., Ltd.  
Ebonestos Industries Ltd.  
Bakelite Ltd.  
R. & J. Beck Ltd.  
E. K. Cole Ltd.  
Imperial Chemical Industries Ltd.

**Polarographs**

Cambridge Instrument Co., Ltd.  
H. Tinsley & Co., Ltd.

**Potentiometers**

Erie Resistor Ltd.  
British Electric Resistance Co., Ltd.  
Bristol's Instrument Co., Ltd.  
Negretti & Zambra Ltd.  
Elliott Bros. (London) Ltd.  
H. Tinsley & Co., Ltd.  
Gambrell Bros. & Co., Ltd.  
Foster Instrument Co., Ltd.

**Power Packs**

Leland Instruments Ltd.  
Standard Telephones & Cables Ltd.

**Projection, Optical**

A.E.W. Ltd.  
Ross Ltd.  
Newton & Co. Ltd.  
Avimo Ltd.  
Aldis Bros. Ltd.  
Leech Optical Co., Ltd.  
Charles Baker.  
Adam Hilger Ltd.  
Pullin Optical Co., Ltd.

**Pumps (Vacuum)**

J. W. Towers & Co., Ltd.  
Metropolitan-Vickers Electrical Co., Ltd.  
W. Edwards & Co. (London) Ltd.  
General Electric Co., Ltd.

**Pyrometry**

Wild-Barfield Electric Furnaces Ltd.  
A.E.W. Ltd.  
Honeywell-Brown Ltd.  
Measuring Instruments (Pullin) Ltd.  
George Kent Ltd.  
Foster Instrument Co., Ltd.

**Q Meters**

Dawe Instruments Ltd.  
Standard Telephones & Cables Ltd.  
Automatic Coil Winder & Electrical Equipment Co., Ltd.  
Marconi Instruments Ltd.

**Quartz Crystals**

Marconi's Wireless Telegraph Co., Ltd.  
Standard Telephones & Cables Ltd.  
General Electric Co., Ltd.

**R.F. Spectrum Analyser**

General Electric Co., Ltd.

**Radiometer**

Negretti & Zambra Ltd.

**Recording Equipment**

Thomas Mercer Ltd.  
Avimo Ltd.  
Griffin & Tatlock Ltd.  
George Kent Ltd.  
Cambridge Instrument Co., Ltd.  
Standard Telephones & Cables Ltd.  
Negretti & Zambra Ltd.  
Salford Electrical Instruments Ltd.  
Elliott Bros. (London) Ltd.  
Everett, Edgcombe & Co., Ltd.  
H. Tinsley & Co., Ltd.  
A. C. Cossor Ltd.  
Evershed & Vignoles Ltd.  
Henry Hughes & Son Ltd.

**Rectifiers**

Standard Telephones & Cables Ltd.  
Salford Electrical Instruments Ltd.  
Ferranti Ltd.  
Westinghouse Brake & Signal Co., Ltd.

**Refractometer**

Bellingham & Stanley Ltd.  
Adam Hilger Ltd.

**Relays**

Telephone Manfg. Co., Ltd.  
Hendrey Relays Ltd.  
Electro Methods Ltd.  
Sunvic Controls Ltd.  
Elliott Bros. (London) Ltd.  
Everett, Edgcombe & Co., Ltd.  
Ferranti Ltd.  
Sangamo Weston Ltd.  
Nalder Bros. & Thompson Ltd.  
W. G. Pye & Co., Ltd.  
Londex Ltd.



250 c/s. and the measures so far taken raise all frequencies below 1,000 c/s. to some extent, the response thus modified still leaves the level in the neighbourhood of 250 c/s. slightly too high. This is shown by the discrepancy between curves B and A. The level in this region is now therefore reduced by placing in parallel with the network already described a retractor tuned to 250 c/s. in series with an appropriate resistance.  $L_2$ ,  $C_3$  and  $R_4$  form such a retractor and have the effect of feeding back a slightly greater proportion of these frequencies. Various combinations of values of  $L_2$  and  $C_3$  calculated to resonate at 250 c/s. have been tried out and their overall responses plotted to obtain the desired degree of steepness of the peak, and various values of  $R_4$  have been tried out to obtain the optimal height of peak or amount of compensation. The closest approach to the required curve was found to be obtained with  $L_2 = 4$  H,  $C_3 = 0.1$   $\mu$ F and  $R_4 = 30,000$  ohms. The effect of the combination is shown by curve E. The choke is constructed similarly to

$L_1$  but with a core of 14 mu-metal laminations forming a stack  $\frac{3}{8}$  in.  $\times$   $\frac{7}{32}$  in. and a winding of 1,000 turns of 34 S.W.G. enamelled wire having a D.C. resistance of 23.5 ohms. Increase of the value of  $R_4$  increases the bass-lifting efficiency of the whole system since with higher values the standard amount of feedback which is set by the relation of  $R_4$  to  $R_1$  and  $R_2$  is greater and the reduced feed-back of bass decided by the lower impedance of  $L_1C_1$  to bass is proportionately less. The mean gain of the stage becomes less. Lower values of  $R_4$  somewhat reduce the bass lift relative to the 1,000 c/s. level but improve the smoothing out of the hump at 250 c/s. If a rise of 4 db. be tolerated at 250 c/s. the level at 25 c/s. may be raised above that at 1,000 c/s., but the most satisfactory compromise for music and all general purposes is probably that which leaves a rise of 2.5 db. at 250 c/s. and a 2.5 db. drop at 25 c/s. since neither of these constitutes an at all easily audible discrepancy. It may be mentioned that in fitting  $R_4$  and  $L_2$  it should be remembered

that it is these components which carry the valve current, and moreover that it is  $R_4$  which primarily decides the standard amount of feed-back at 1,000 c/s.

decreased by the decreased impedance of  $C_2$ .  $R_3$  is chosen to make these two effects nearly cancel one another. In the middle register the amount of feed-back tends to be reduced by  $L_1C_1$  and increased by  $L_2C_3$ .  $R_4$  is chosen so that these effects also nearly cancel one another. The data have been obtained throughout by means of H.M.V. constant frequency records and oscillograph measurements of voltages at the L.S. terminals of the amplifier. The amplifier consisted of the first stage described above and in the legend to Fig. 1 (with alternative first stages for other inputs), a second R.C. coupled  $MH_4$ , a phase changer (HL4+) and two  $MH_4$ s driving two  $PP_5/400$ 's in push-pull operating in Class A. With the compensator described and the writer's own energised moving coil pick-up and transformer the overall response is within 2.5 db. of the 1,000 level from 25 c/s. to 8,500 c/s. Transients, moreover, are well preserved and listening tests with three speakers and a dividing network have fully justified expectations based on the response data. A typical overall response curve is shown in Fig. 2, F.

Fig. 3 is appended for comparative purposes and shows the overall response curves obtained on the same amplifier, A, with a high fidelity crystal pick-up; B, with a moving coil pick-up with no tone correction; C, with the same moving coil pick-up with bass lifted by frequency selective potentiometer in grid circuit; D, with moving coil pick-up and frequency-selective negative feedback in cathode circuit as above described. It is anticipated these results will be further improved upon by this method when other stampings become available.

Fig. 2.

- A = Amplifier response required to compensate for falling base of commercial recordings.
- B = Response due to combination  $L_1C_1$  (Fig. 1).
- C = Modification of B due to  $C_2 = 0.001$   $\mu$ F alone in parallel with  $L_1C_1$  (+ a resistance to carry the valve current).
- D = Modification of B due to  $R_3C_2$  with values given under Fig. 1.
- E = Modification of B due to combination  $R_4C_2L_2$  (Fig. 1).
- F = Overall response of pick-up and amplifier with complete bass compensator on commercial disks.


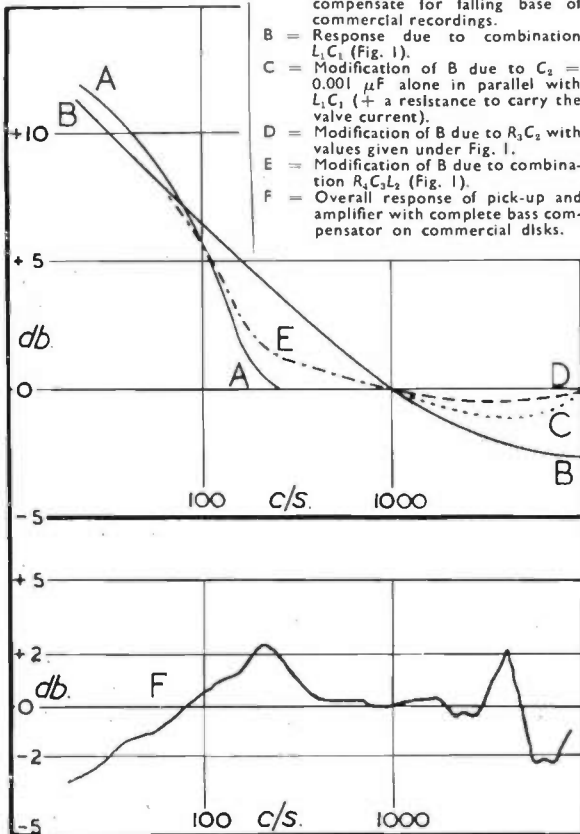


Fig. 3.

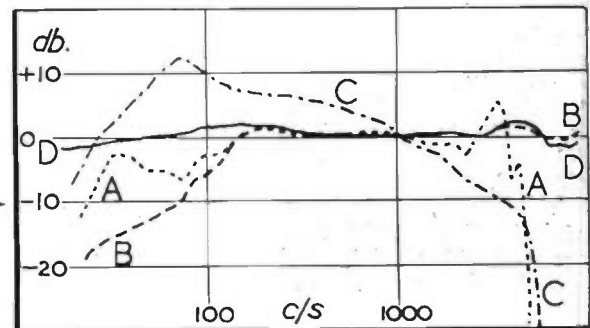

# High Fidelity Bass Compensation

For Moving Coil Pick-Ups

By F. M. HAINES, D.Sc.\*

IT has not been possible up to the present to obtain full advantage of the high fidelity of the moving coil pick-up for want of adequate and sufficiently accurate bass compensation. In the absence of this, its excellent top response leads to a want of balance which is musically most unsatisfactory. Methods of bass compensation in common use involving arrangements of chokes, condensers, tuned acceptors or rejectors, or frequency selective potentiometers in grid or anode circuits, all fail where high fidelity is required, since, as a large number of actual response plots made by the writer have shown, they are not capable of giving even approximately correct compensation at all lower frequencies relative to the 1,000 c/s. level without considerably impairing the top response relative to the same standard. Generally the transients are also impaired.

Response measurements show, however, that a very much closer compensation for the falling level of the bass on commercial disks, and a response curve with no departure over 2.5 db. from the 1,000 c/s. level between 25 c/s. and 8,500 c/s. may be obtained by the use of frequency-selective negative feed-back through an appropriate network placed in the cathode circuit of the first valve of the pick-up pre-amplifier following the input transformer.

The circuit is shown in Fig. 1. Its general effect is that all frequencies above 250 c/s. are about 80 per cent. fed back, incidentally giving improved quality by a smoothing of possible minor irregularities in the upper half of the audible band. Below 250 c/s. where a regularly increasing compensation is required down to 25 c/s. (0.75 db. at 200 c/s., 5.5 db. at 100 c/s., 10 db. at 50 c/s. and 11.1 db. at 25 c/s. as shown by curve A, Fig. 2), there is progressively less feed-back until at 25 c/s. there is practically no feed-back and the full amplification of the stage is obtained.

The main agent is the combination of  $L_1C_1$  (Fig. 1) which forms a tuned acceptor with a minimum impedance at or below 25 c/s. Above 25 c/s. the

impedance rises so that an increasing proportion of the input signal is fed back. The theoretical optimal values for  $L_1$  and  $C_1$  are respectively 10 H and  $4 \mu\text{F}$ , but in practice response curves show that it is better to tune the acceptor well below 25 c/s. (e.g., to about 10 c/s.), the best results being obtained with a  $4 \mu\text{F}$  condenser and a choke passing 0.46 mA on a 50 c/s. 4-volt supply, i.e., of 27.7 H. The core of this choke is of 25 mu-metal laminations, the centre stack being  $\frac{3}{8}$  in.  $\times$   $\frac{3}{8}$  in. and the winding of 900 turns of 36 S.W.G. enamelled wire, the D.C. resistance being 32.5 ohms. The resistance must be as low as possible: at the same time the choke cannot be made unduly large owing to increased capacitive leak. It may be noted that for  $C_1$  an electrolytic condenser may be used if desired, since it is maintained polarised by the drop of potential across  $R_1L_2$  due to the valve current. The effect of the combination  $L_1C_1$  alone is to raise the bass and shift, the originally level response of the amplifier to the curve B shown in Fig. 2. This makes a close approximation to the compensation required by commercial recordings (shown in curve A) up to about 200 c/s. The impedance of  $L_1C_1$ , however, increases indefinitely upwards, and this, if the combination were used alone (with a resistance to carry the valve current), would cause a serious loss of top, as is evident on comparing curves A and B. To counteract this and prevent the falling off above 1,000 c/s. the impedance of the network is kept approximately constant above 1,000 c/s. and the top response fully retained relative to this level by placing in parallel with  $L_1C_1$  the condenser  $C_2$ . The effect of adding  $C_2$  alone is to give an indefinitely rising response above the point at which the impedance of  $C_2$  becomes comparable with that of  $L_1C_1$ . The impedance of  $L_1C_1$  at 1,000 c/s. is 157,000 ohms. For  $C_2$  to equal this,

$\frac{1}{6,280 \times C_2} = 157,000$ , which gives  $C_2 = 0.001 \mu\text{F}$ . Trial shows that this value restores the correct level at 8,500 c/s., but leaves it low at 5,000 c/s. as in curve C. The

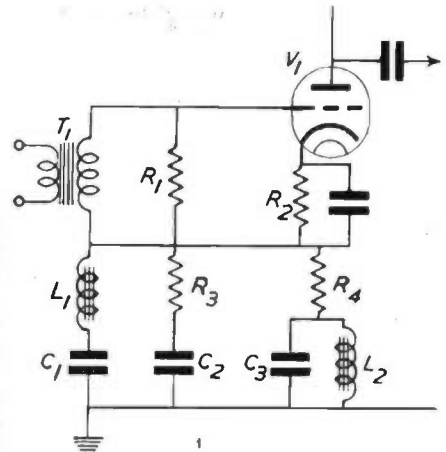


Fig. 1. Circuit for bass compensation by frequency selective negative feedback.

$V_1$ , MH4: load resistance = 50,000 ohms.  
 $T_1$ , Input (matching) transformer. Ratio = 350:1.  
 Primary: 20 t. of 18 g. enam. wire; secondary: 7,000 t. of 44 g. Core: 14 Ni alloy laminations,  $\frac{3}{8}$  in.  $\times$   $\frac{3}{8}$  in. centre stack.  
 $R_1 = 500,000$ ;  $R_2 = 1,000$ ;  $R_3 = 25,000$ ;  
 $R_4 = 30,000 \Omega$   
 $C_1 = 4 \mu\text{F}$ ;  $C_2 = 0.002 \mu\text{F}$ ;  $C_3 \times 0.1 \mu\text{F}$ .  
 $L_1 = 25 \text{ H}$ ;  $L_2 = 4 \text{ H}$ . (For details see text.)

0.001  $\mu\text{F}$  condenser is therefore replaced by a larger condenser (to raise the response earlier) with a resistance in series to limit the lift and give the same total impedance at 8,500 c/s. as a 0.001  $\mu\text{F}$  condenser alone. A 0.001  $\mu\text{F}$  condenser has an impedance at 8,500 c/s. of 18,700 ohms. Thus  $R_3$  must be such that

$$\sqrt{R_3^2 + \left(\frac{1}{\omega C_2}\right)^2} = 18,700 \text{ ohms at}$$

8,500 c/s., which gives  $R_3 = 16,000$  ohms. The effect of  $R_3C_2$  is shown by curve D. Trials show that since minor peaks may tend to appear in this region, 16,000 ohms for  $R_3$  raises the 5,000 c/s. level a little too much, and that in practice 20,000 or 25,000 ohms may allow the minimum departure from the 1,000 c/s. level. The optimal value in any particular case depends upon the properties of the pick-up and matching transformer and the consequent shape of the original response curve in this region. A number of response plots show that with a particular pick-up and transformer used by the writer the most satisfactory values are  $C_2 = 0.002 \mu\text{F}$  and  $R_3 = 25,000$  ohms, with which the deviation of the overall response curve is nowhere more than slightly over 2 db. from the 1,000 c/s. level from 1,000 c/s. to 8,500 c/s.

Since the required compensation (curve A, Fig. 2) begins abruptly at

\* Queen Mary College, University of London.

# Directory of Companies *mentioned on previous pages*

(Compiled from the Physical Society's Exhibition Catalogue)

(See Note on p. 43)

- A.B. Metal Products Ltd.**  
Great South-West Road, Feltham, Mddx.
- A.E.W. Ltd.**  
Imperial Works, High Street, Edgware, Mddx.
- Aldis Bros. Ltd.**  
Sarehole Road, Hall Green, Birmingham.
- Automatic Coil Winder & Electrical Equipment Co., Ltd.**  
Winder House, Douglas Street, London, S.W.1.
- Avlmo Ltd.**  
Taunton, Somerset.
- Baird & Tatlock (London) Ltd.**  
14-17, St. Cross Street, London, E.C.1.
- Bakelite Ltd.**  
18, Grosvenor Gardens, London, S.W.1.
- Baker, Charles**  
244, High Holborn, London, W.C.1.
- Baldwin Instrument Co., Ltd.**  
Grand Buildings, Trafalgar Square, W.C.2.
- Barr & Stroud Ltd.**  
15, Victoria Street, London, S.W.1.
- Beck, R. & J., Ltd.**  
69, Mortimer Street, London, W.1.
- Bellingham & Stanley Ltd.**  
71, Hornsey Rise, London, N.19.
- Bristol's Instrument Co., Ltd.**  
North Circular Road, London, N.W.10.
- British Electric Resistance Co., Ltd.**  
329, High Holborn, London, W.C.2.
- British Insulated Callender's Cables Ltd.**  
Norfolk House, Norfolk Street, London, W.C.2.
- British Physical Laboratories Ltd.**  
Quadrant Works, London, N.W.5.
- British Rototherm Co., Ltd.**  
Merton Abbey, London, S.W.19.
- British Thomson-Houston Co., Ltd.**  
Rugby.
- Cambridge Instrument Co., Ltd.**  
13, Grosvenor Place, London, S.W.1.
- Catterson-Smith, R. M.**  
Adams Bridge Works, Exhibition Grounds, Wembley, Mddx.
- Chance Bros. Ltd. & Austinlite Ltd.**  
Lighthouse Works, Smethwick, Birmingham.
- Clifton Instruments Ltd.**  
80, Newmarket Road, Cambridge.
- Cole, E. K., Ltd.**  
Ecco Works, Southend-on-Sea, Essex.
- Cooke, Troughton & Simms Ltd.**  
Broadway Court, Westminster, S.W.1.
- Cossor, A. C., Ltd.**  
Cossor House, Highbury Grove, London, N.5.
- Crescent Gauges Ltd.**  
River Lane, Leatherhead, Surrey.
- Dallmeyer, J. H., Ltd.**  
Church End Works, High Road, Willesden, London, N.W.10.
- Dawe Instruments Ltd.**  
Woodside Road, Amersham, Bucks.
- Decca Navigator Co., Ltd.**  
1-3, Brixton Road, London, S.W.9.
- De Havilland Aircraft Co., Ltd.**  
(Vibration Department), Stag Lane, Edgware, Mddx.
- Drayton Regulator & Instrument Co., Ltd.**  
West Drayton, Mddx.
- Ebonestos Industries Ltd.**  
Exelsior Works, Rollins Street, London, S.E.15.
- Edison Swan Electric Co., Ltd.**  
155, Charing Cross Road, London, W.C.2.
- Edwards, W., & Co. (London), Ltd.**  
Kangley Bridge Road, London, S.E.26.
- Electro Methods Ltd.**  
112, Brent Street, London, N.W.4.
- Elliott Bros. (London) Ltd.**  
Century Works, Lewisham, S.E.13.
- Erie Resistor Ltd.**  
Carlisle Road, The Hyde, London, N.W.9.
- Evans Electroelenium Ltd.**  
Bishop's Stortford, Herts.
- Everett, Edgcumbe & Co., Ltd.**  
Collindale Works, Collindale Lane, N.W.9.
- Evershed & Vignoles Ltd.**  
Chiswick, London, W.4.
- Ferranti Ltd.**  
Hollinwood, Lancs.
- Fibreglass Ltd.**  
Firhill, Glasgow, N.W.
- Foster Instrument Co., Ltd.**  
Letchworth, Herts.
- Gambrell Bros. & Co., Ltd.**  
307, Merton Road, London, S.W.18.
- General Electric Company, Ltd.**  
Magnet House, Kingsway, W.C.2.
- Gresham Transformers Ltd.**  
Hanworth, Mddx.
- Griffin & Tatlock Ltd.**  
Kemble Street, Kingsway, London, W.C.2.
- Hendrey Relays Ltd.**  
Bourne End, Bucks.
- Hilger, Adam, Ltd.**  
98, St. Pancras Way, Camden Road, London, N.W.1.
- Honeywell-Brown Ltd.**  
Wadsworth Road, Perivale, Greenford, Mddx.
- Hughes, Henry & Son Ltd.**  
Husun Works, New North Road, Barkingside, Essex.
- Ilford Ltd.**  
Ilford, Essex.
- Imperial Chemical Industries Ltd.**  
Nobel House, Buckingham Gate, London, S.W.1.
- Jackson Automatic Controls Ltd.**  
Windsor House, Victoria Street, London, S.W.1.
- Johnson, Matthey & Co., Ltd.**  
73-83, Hatten Garden, London, E.C.1.
- Kent, George, Ltd.**  
Luton, Beds.
- Kodak Ltd.**  
Kingsway, London, W.C.2.
- Labgear**  
Willow Place, Cambridge.
- Leech Optical Co., Ltd.**  
Whetstone, Leics.
- Leland Instruments Ltd.**  
21, John Street, Bedford Row, London, W.C.1.
- Londex Ltd.**  
207, Anerley Road, London, S.E.20.
- London Instrument Co., Ltd., The**  
Newnham Mill, Cambridge.
- Marconi Instruments Ltd.**  
St. Albans, Herts.
- Marconi's Wireless Telegraph Co., Ltd.**  
Electra House, Victoria Embankment, W.C.2.
- Measuring Instruments (Pullin) Ltd.**  
Phoenix Works, Great West Road, Brentford, Mddx.
- Mercer, Thomas, Ltd.**  
Eyewood Road, St. Albans, Herts.
- Mercury Switch Manufacturing Co., Ltd.**  
West Drayton, Mddx.
- Metallisation Ltd.**  
Barclays Bank Chambers, Dudley, Worcs.
- Metropolitan-Vickers Electrical Co., Ltd.**  
Trafford Park, Manchester, 17.
- M.O. Valve Co., Ltd., The**  
Osram Works, Brook Green, Hammersmith, London, W.6.
- Morgan Crucible Co., Ltd., The**  
Battersea Church Road, London, S.W.11.
- Muirhead & Co., Ltd.**  
Elmers End, Beckenham, Kent.
- Mullard Wireless Service Co., Ltd.**  
Century House, Shaftesbury Avenue, London, W.C.
- Multitone Electric Co., Ltd.**  
223-227, St. John Street, Clerkenwell, E.C.1.
- Nalder Bros. & Thompson Ltd.**  
Dalston Lane Works, London, E.8.
- Napier, D., & Son Ltd.**  
Acton, London, W.3.
- Negretti & Zambra Ltd.**  
122, Regent Street, London, W.1.
- Newton & Co., Ltd.**  
72, Wigmore Street, London, W.1.
- Permanent Magnet Association, The**  
301, Glossop Road, Sheffield, 10.
- Philips Lamps Ltd.**  
Century House, Shaftesbury Avenue, London, W.C.
- Precision Tool and Instrument Co., Ltd.**  
353, Bensham Lane, Thornton Heath, Surrey.
- Pullin Optical Co., Ltd.**  
Phoenix Works, Great West Road, Brentford, Mddx.
- Pye, W. G., & Co., Ltd.**  
"Granta" Works, Newmarket Road, Cambridge.
- Quickfit & Quartz Ltd.**  
1, Albemarle Street, Piccadilly, W.1.
- Record Electrical Co., Ltd.**  
Broadheath, Aitricham, Cheshire.
- Rediffusion Ltd.**  
Broomhill Road, Wandsworth, London, S.W.18.
- Ross Ltd.**  
The Optical Works, Clapham Common, London, S.W.4.
- Rotameter Manufacturing Co., Ltd.**  
Vale Road, Portslade, Sussex.
- Salford Electrical Instruments Ltd.**  
Silk Street, Salford, 3, Lancs.
- Sangamo Weston Ltd.**  
Great West Road, Enfield, Mddx.
- Scientific Acoustics Ltd.**  
Truvox House, Exhibition Grounds, Wembley, Mddx.
- Scientific Computing Service Ltd.**  
23, Bedford Square, London, W.C.1.
- Scophony Ltd.**  
Wells, Somerset.
- Smith, S., & Sons (England) Ltd.**  
Cricklewood Works, London, N.W.2.
- Standard Telephones & Cables Ltd.**  
Connaught House, Aldwych, London, W.C.2.
- Stanley, W. F., & Co., Ltd.**  
New Eltham, London, S.E.9.
- Sullivan, H. W., Ltd.**  
Leo Street, London, S.E.15.
- Sunvic Controls Ltd.**  
Stanhope House, Kean Street, Aldwych, London, W.C.2.
- Taylor, Taylor & Hobson Ltd.**  
150, Holborn, London, W.C.1.
- Telegraph Condenser Co., Ltd.**  
Wales Farm Road, North Acton, London, W.3.
- Telegraph Construction & Maintenance Co., Ltd.**  
Telcon Works, Greenwich, London, S.E.10.
- Telephone Manufacturing Co., Ltd.**  
Martell Road, Dulwich, London, S.E.21.
- Tinsley, H., & Co., Ltd.**  
Werndee Hall, London, S.E.25.
- Tintometer Ltd.**  
Salisbury.
- Towers, J. W., & Co., Ltd.**  
Wildnes, Lancs.
- Townson & Mercer Ltd.**  
390, Sydenham Road, Croydon, Surrey.
- Turner, Ernest, Electrical Instruments Ltd**  
Chiltern Works, High Wycombe, Bucks.
- Unicam Instruments Ltd.**  
Arbury Road, Cambridge.
- Vinten, W., Ltd.**  
North Circular Road, London, N.W.2.
- Watson, W., & Sons Ltd.**  
14, Hadley Grove, Barnet, Herts.
- Watts, E. R., & Son Ltd.**  
123, Camberwell Road, London, S.E.5.
- Westinghouse Brake & Signal Co., Ltd.**  
Pew Hill House, Chippenham, Wilts.
- Wild-Barfield Electric Furnaces Ltd.**  
Elecfurn Works, Watford, Herts.
- Wray (Optical Works) Ltd.**  
Bromley, Kent.
- Zenith Electric Co., Ltd.**  
Villiers Road Willesden Green, London, N.W.2.

**Remote Controls and Indicators**

Bristol's Instrument Co., Ltd.  
Standard Telephones & Cables Ltd.  
Negretti & Zambra Ltd.  
Everett, Edgcombe & Co., Ltd.  
Record Electrical Co., Ltd.  
Elliott Bros. (London) Ltd.

**Resistances and Resistors**

A.E.W. Ltd.  
Erie Resistor Ltd.  
British Electric Resistance Co., Ltd.  
Labgear.  
Dawe Instruments Ltd.  
Zenith Electric Co., Ltd.  
Standard Telephones & Cables Ltd.  
H. W. Sullivan Ltd.  
Muirhead & Co., Ltd.

**Sapphires**

Salford Electrical Instruments Ltd.

**Signal Generators**

Labgear.  
Standard Telephones & Cables Ltd.  
Salford Electrical Instruments Ltd.  
Marconi Instruments Ltd.  
British Physical Laboratories Ltd.  
Leland Instruments Ltd.  
Dawe Instruments Ltd.

**Silicones**

British Thomson-Houston Co., Ltd.

**Spectrographs, -meters, -scopes**

Wild-Barfield Electric Furnaces Ltd.  
Unicam Instruments Ltd.  
Adam Hilger Ltd.  
Standard Telephones & Cables Ltd.

**Spectrophotometers**

Adam Hilger Ltd.

**Speed Measurement Instruments**

S. Smith & Sons (England) Ltd.  
Dawe Instruments Ltd.  
Scophony Ltd.

**Spherometers**

R. & J. Beck Ltd.

**Sputtering Apparatus**

W. Edwards & Co. (London) Ltd

**Strain Gauges**

Baldwin Instrument Co., Ltd.  
Salford Electrical Instruments Ltd  
H. Tinsley & Co., Ltd.

**Strain Viewers**

Adam Hilger Ltd.  
Salford Electrical Instruments Ltd.

**Stroboscopes**

Dawe Instruments Ltd.  
Scophony Ltd.  
Henry Hughes & Son Ltd.  
W. G. Pye & Co., Ltd.  
Ferranti Ltd.

**Surge (Absorber, Diverter)**

Metropolitan-Vickers Electrical Co., Ltd.  
Westinghouse Brake & Signal Co., Ltd.

**Switches and Circuit Breakers**

A.E.W. Ltd.  
Thomas Mercer Ltd.  
Hendrey Relays Ltd.  
British Electric Resistance Co., Ltd.  
Chance Bros. & Austinlite Ltd.  
Standard Telephones & Cables Ltd.  
Muirhead & Co., Ltd.

**Switches and Circuit Breakers (Mercury)**

Mercury Switch Manufacturing Co., Ltd.  
Sunvic Controls Ltd.  
Londex Ltd.

**Tachometers**

S. Smith & Sons (England) Ltd.

**Telephone-Circuit Instruments**

Salford Electrical Instruments Ltd.  
Standard Telephones & Cables Ltd.  
Telephone Mfg. Co., Ltd.

**Telescopes**

Ross Ltd.  
E. R. Watts & Son Ltd.  
Charles Baker.

**Temperature (Compensator) Controller, Recorder Indicator, Recorder, Regulator**

Bristol's Instrument Co., Ltd.  
Sunvic Controls Ltd.  
George Kent Ltd.  
Cambridge Instrument Co., Ltd.  
H. W. Sullivan Ltd.  
Everett, Edgcombe & Co., Ltd.  
H. Tinsley & Co., Ltd.  
Sangamo Weston Ltd.  
Foster Instrument Co., Ltd.

**Testing and Measuring, Electrical**

Dawe Instruments Ltd.  
Measuring Instruments (Pullin) Ltd.  
Salford Electrical Instruments Ltd.  
Elliott Bros. (London) Ltd.  
H. W. Sullivan Ltd.  
Everett, Edgcombe & Co., Ltd.  
Gambrell Bros. & Co., Ltd.  
W. G. Pye & Co., Ltd.  
Automatic Coil Winder & Electrical Equipment Co., Ltd.  
Ernest Turner Electrical Instruments Ltd.  
British Physical Laboratories Ltd.

**Thermo-Couples, -Piles**

Adam Hilger Ltd.  
Standard Telephones & Cables Ltd.

**Thermometers**

British Rototherm Co., Ltd.  
Electro Methods Ltd.  
Sunvic Controls Ltd.  
Elliott Bros. (London) Ltd.  
Foster Instrument Co., Ltd.  
British Thomson-Houston Co., Ltd.

**Thickness Testers**

Precision Tool & Instrument Co., Ltd.  
Adam Hilger Ltd.  
Cambridge Instrument Co., Ltd.  
Salford Electrical Instruments Ltd.  
Record Electrical Co., Ltd.

**Thyratrons**

British Thomson-Houston Co., Ltd.  
Standard Telephones & Cables Ltd.  
The M.O. Valve Co., Ltd.

**Time Interval Measurement**

Thomas Mercer Ltd.  
Bristol's Instrument Co., Ltd.  
Telephone Manufacturing Co., Ltd.  
Dawe Instruments Ltd.  
Standard Telephones & Cables Ltd.  
Elliott Bros. (London) Ltd.  
Everett, Edgcombe & Co., Ltd.  
Muirhead & Co., Ltd.  
Marconi Instruments Ltd.  
Ilford Ltd.

**Transformers**

E. K. Cole Ltd.  
Gresham Transformers Ltd.  
Labgear.  
Zenith Electric Co., Ltd.  
Muirhead & Co., Ltd.

**Transformers (Instrument)**

Elliott Bros. (London) Ltd.  
Everett, Edgcombe & Co., Ltd.  
Automatic Cqil Winder & Electrical Equipment Co., Ltd.

**Vacuum Gauges**

W. Edwards & Co. (London) Ltd.  
Cambridge Instrument Co., Ltd.

**Vacuum Seals**

Ferranti Ltd.  
Metropolitan-Vickers Electrical Co., Ltd.  
British Thomson-Houston Co., Ltd.

**Valves, Radio, Demonstrating and Testing**

Standard Telephones & Cables Ltd.  
Salford Electrical Instruments Ltd.  
The M.O. Valve Co., Ltd.  
Everett, Edgcombe & Co. Ltd.  
Ferranti Ltd.  
Gambrell Bros. & Co., Ltd.  
Automatic Coil Winder & Electrical Equipment Co., Ltd.

**Vibration, Mechanical, Measurement**

Thomas Mercer Ltd.  
Hendrey Relays Ltd.  
Salford Electrical Instruments Ltd.  
De Havilland Aircraft Co., Ltd.

**Viscosity, Measurement**

Griffin & Tatlock Ltd.  
Baird & Tatlock (London) Ltd.  
Townson & Mercer Ltd.

**Voltage, Multipliers, Regulators, Selectors, Stabilisers**

Gresham Transformers Ltd.  
British Electric Resistance Co., Ltd.  
Sunvic Controls Ltd.  
Zenith Electric Co., Ltd.  
Westinghouse Brake & Signal Co., Ltd.

**Voltmeters**

See under Instruments, Indicating.

**Wattmeters**

See under Instruments, Indicating.

**Wave, Centimetric Apparatus**

British Thomson-Houston Co., Ltd.  
Metropolitan-Vickers Electrical Co., Ltd.  
Ferranti Ltd.

**Wave-Guide Test Bench**

British Insulated Callender's Cables Ltd. & Nash & Thompson Ltd.  
British Thomson-Houston Co., Ltd.

**Wavemeters**

Standard Telephones & Cables Ltd.  
Salford Electrical Instruments Ltd.  
H. W. Sullivan Ltd.  
Marconi Instruments Ltd.  
British Thomson-Houston Co., Ltd.


**Welding Control Equipment**

Everett, Edgcombe & Co., Ltd.  
Ferranti Ltd.

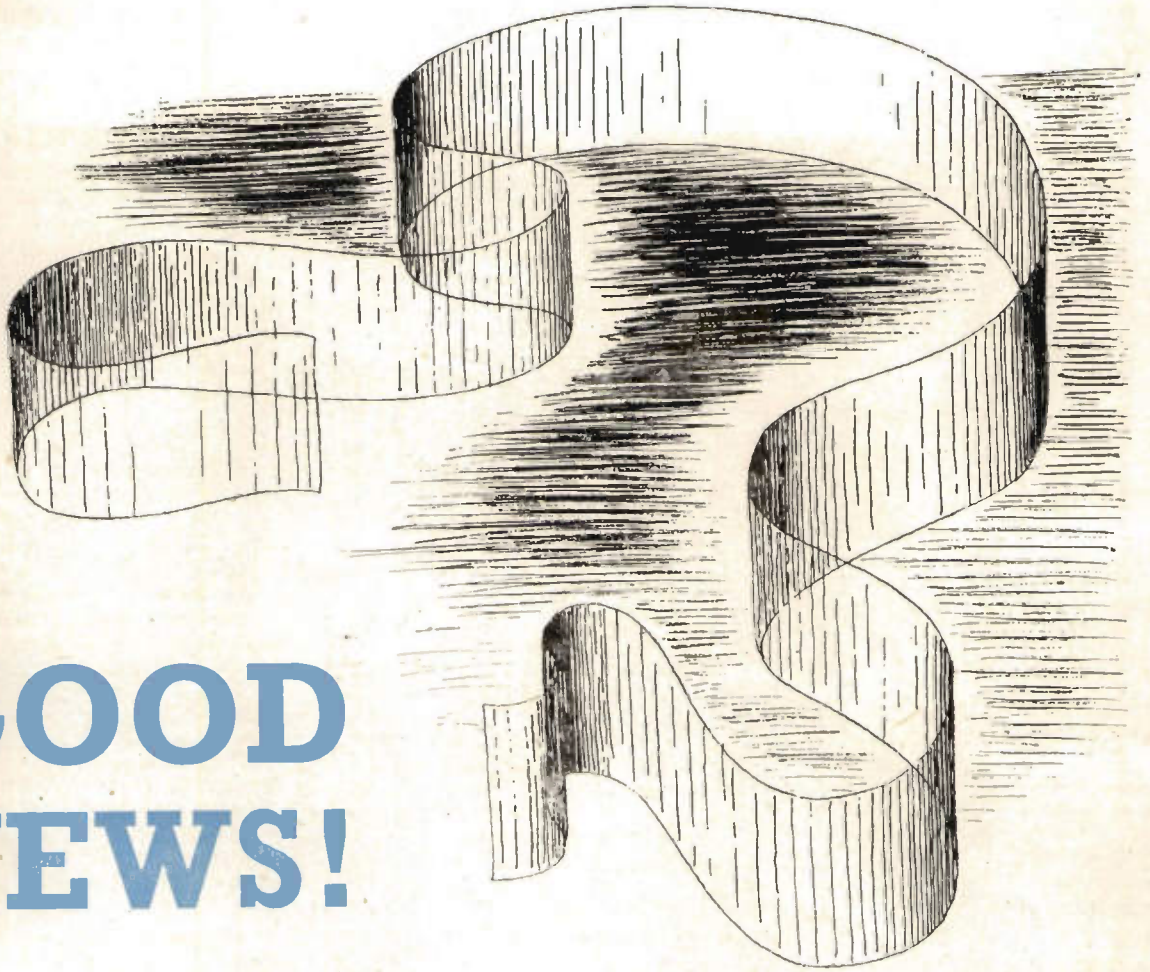**X-Ray Equipment**

Unicam Instruments Ltd.  
Kodak Ltd.  
Adam Hilger Ltd.  
Ilford Ltd.  
Baldwin Instrument Co., Ltd.  
Metropolitan-Vickers Electrical Co., Ltd.  
Philips Lamps Ltd.  
Marconi Instruments Ltd.

Note: This list has been compiled from the official catalogue of the exhibition, from which the names of some well-known electronic manufacturers are missing. The editorial staff of this Journal will be pleased to help inquirers by giving further information on either products or manufacturers not listed here.



# GOOD NEWS!

BX DISTRENE Foil is now available in limited quantities. This foil has all the outstanding electric insulating qualities associated with our "Distrene" brand Polystyrene, among which may be mentioned its high chemical resistance and immunity against water and humidity. There are a dozen jobs or more waiting for Distrene in the electrical industry.

BX DISTRENE Foil is supplied in rolls from  $\frac{1}{8}$  in. to 12 in. in width and in thicknesses from  $\frac{2}{1000}$  in. to  $\frac{8}{1000}$  in.

★ *Send for samples and further information.*

---


**BX PLASTICS LTD., LARKSWOOD WORKS, LONDON, E.4**

# MULLARD

## VALVES



FOR DOMESTIC RECEIVERS

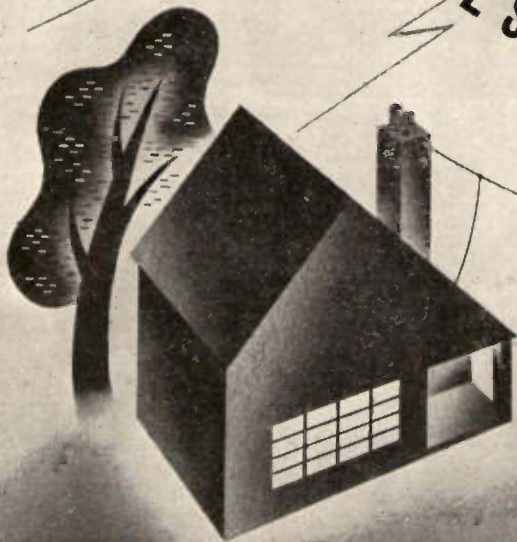

**Recommended Types for  
A.C. Mains Operated Receiver.**

- ECH 35 Frequency changer.
- EF 39 Intermediate Frequency Amplifier.
- EBC 33 Detector L.F. Amplifier.
- EL 33 Output Pentode.
- AZ 31 Rectifier.

*Other recommended types are available for  
A.C./D.C., battery and portable receivers.*

**MULLARD** *THE DOMINANT NAME IN ELECTRONICS*

# A Single Sweep Time Base

## Part II

By D. McMULLAN, B.A.(Cantab), Grad.I.E.E.

IN Part I a description was given of a time base which, although designed primarily for single sweep working, could also be used as a normal free running\* time base as well as providing facilities for sweep expansion in conjunction with an auxiliary time base.

The time base circuit is a combination of the Puckle time base and the Eccles-Jordan trigger circuit, and one of its features is the short time delay between the application of the actuating pulse and the start of the working stroke. When used for sweep expansion, the time base is triggered by an auxiliary time base synchronised with the signal under observation. Any part of a cycle of the signal waveform may be expanded by arranging that the time base is triggered at the appropriate point in the sweep of the auxiliary time base.


In this part some practical details are considered and the circuit of a time base designed on the lines indicated in Part I is given.

### Some Practical Considerations

The circuit of the time base is shown in Fig. 2.1, and its main points will be discussed briefly. The five-pole three-way switch  $S1$  1-5 is used to select the type of operation required: single sweep, sweep expansion or free running. The switch is shown in the single sweep position. The following controls are operative on all three positions:  $VR_1$  and  $S_3$  which vary the velocity of the spot, and  $VR_2$ , which controls the amplitude of the time base output.  $VR_3$  and  $VR_4$  are used in the single sweep and free running conditions only and are the trigger control and pulse input control respectively.  $VR_5$  is the sweep expansion control and  $S_2$  is the auto-manual reset switch for single sweep working.

$V_5$  is used in the sweep expansion circuit (as described in Part I) and also as a phase reversing stage for

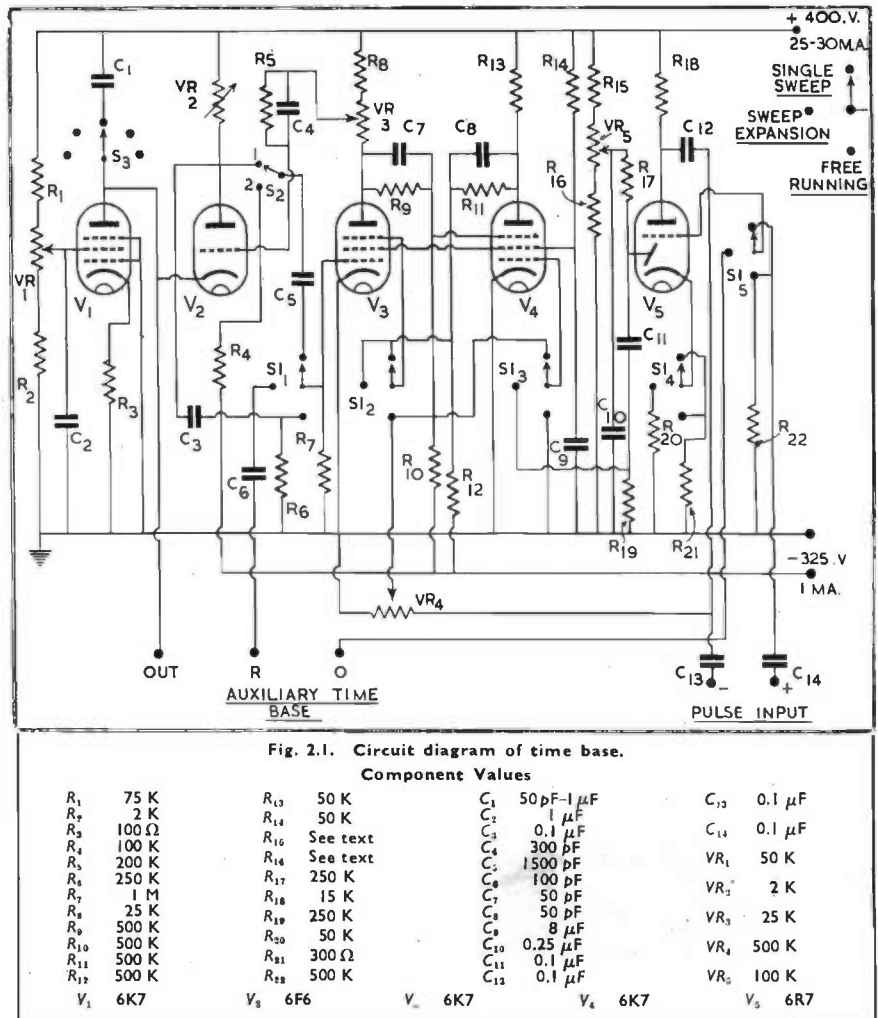\* "Free running" is used in the sense that no external signal is required to actuate the time base although a synchronising signal will probably be used to lock the time base to the waveform under observation.



triggering the single sweep time base on positive pulses as well as a synchronising signal amplifier in the free running condition.

$C_4$  and  $R_5$  are included in the grid circuit of  $V_2$  in order that the circuit shall work satisfactorily in the single sweep condition with low spot velocities. In this case, without  $C_4$  and  $R_5$  the time base will not reset at the end of the working stroke since the condenser  $C_1$  does not discharge fast enough for the cathode of  $V_2$  to follow the grid, with the result that  $V_2$  takes a large grid current interfering with the action of the Eccles-

Jordan circuit  $V_3$ ,  $V_4$ .  $R_5$  reduces this grid current and is shunted by  $C_4$  so that the circuit will operate satisfactorily at high frequencies.

In the free running condition the circuit works as a normal Puckle time base.

A word of explanation is perhaps necessary for the size of the discharge valve  $V_2$ , an output pentode, triode connected. Since a D.C. connexion has to be made between the time base and the cathode-ray tube, when the charging current is varied through  $V_1$  (and hence through  $V_2$  when the time base is in the static condition),

the starting position of the spot is moved across the screen due to the voltage drop across  $V_2$  and  $VR_2$ . Therefore it is advisable to choose a valve with a low D.C. resistance for  $V_2$ , and this, of course, has the additional advantage that the discharge current is increased with a corresponding decrease in the flyback time.

It has been found necessary to supply the screens of  $V_3$  and  $V_4$  through a common resistor and to shunt them with a large condenser to chassis in order that the circuit shall trigger on short pulses and that the changeover time shall be as short as possible. With this arrangement the screen voltages remain practically constant whichever valve happens to be conducting, but if the screens are fed through separate resistors, the screen voltage of the valve that is being cut off immediately rises, interfering with the trigger action (unless the screen is connected to cathode through a condenser). If condensers are connected between screens and cathodes the circuit will take a long time to reach its final condition (the time required depending on the time constant of the screen circuits).

The values of the resistors  $R_{15}$  and  $R_{16}$  in the sweep expansion control ( $VR_5$ ) resistance chain are not given as these depend on the output voltage of the auxiliary time base. It should be noted that the voltage applied to the grid of  $V_5$  should not exceed 300 volts or the valve will not function as a cathode follower. If the peak output volts from the auxiliary time base (measured to ground) do not exceed 300 volts, a D.C. connexion may be made between this time base and the grid of  $V_5$ . Otherwise the connexion must be made through a condenser and the grid of  $V_5$  returned through a high resistance to a point whose positive potential to chassis is equal to half the peak-to-peak output of the

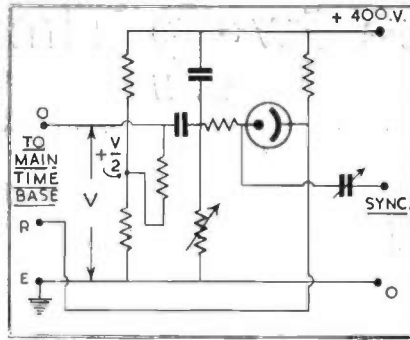


Fig. 2.2. Neon time base for use as auxiliary time base.  $V$  = peak to peak voltage output of time base.

auxiliary time base. If the peak-to-peak output of the auxiliary time base is greater than 300 volts some attenuation must be introduced to limit the peak voltage applied to the grid of  $V_5$ .

The resistors  $R_{15}$  and  $R_{16}$  are so chosen that the potentials at the top and the bottom of the potentiometer  $VR_5$  are equal respectively to the maximum and minimum voltages applied to the grid of  $V_5$ .

An auxiliary time base consisting of a condenser shunted by a neon and fed through a high resistance has been found satisfactory for some work. A suitable circuit is shown in Fig. 2.2. A resistor is included in series with the neon in order to provide the resetting pulse for the main time base. The disadvantages of this arrangement are that the maximum frequency is limited and the voltage output is rather low for working direct into the plates of a cathode-ray tube, although it is large enough for triggering the main time base. However, with an amplifier it is quite adequate for most work.

Care should be taken in the mechanical layout to keep all wires as short as possible. The heaters of  $V_2$  and  $V_3$  should be supplied from separate screened windings on the mains transformer.

**D.C. Supplies**

The H.T. supply to the time base must be well smoothed. The necessity for providing a negative supply to the time base is a disadvantage, but may be fairly easily arranged, since the current drain is only a milliamp or so. One or other of the following methods may be employed. The voltage may be obtained from the cathode-ray tube potentiometer chain or a separate supply may be used. The latter arrangement is probably the best as the modifications necessary to an existing power pack are very simple. A suitable circuit is shown in Fig. 2.3. A metal rectifier is used and is connected to one half of the main H.T. transformer. Resistance smoothing is satisfactory since the current drain is so low. The negative supply voltage is rather critical, and is therefore made adjustable.

**Connexion to C.R.T.**

The connexion of the time base to the cathode-ray tube is rather a problem since isolating condensers cannot be included in the deflector plate circuits. This is because the spot will not start from the same place on the X-axis for each stroke if irregularly spaced transients are being observed.

If it is desired to have the final anode of the cathode-ray tube at earth potential, then the positive H.T. rail of the time base must be earthed.

The author has found that a satisfactory arrangement is to have the final anode of the tube at a potential slightly lower than that of the time base positive H.T. supply rail. A schematic diagram is shown in Fig. 2.4. The valves  $V_6$  and  $V_7$  form a cathode-coupled amplifier for the Y-plates. This circuit removes some of the disadvantages of not having the final anode of the cathode-ray tube earthed, and also has the advantage that the amplifier may be used


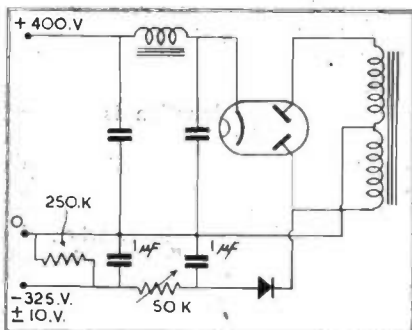


Fig. 2.3 (left). Suggested circuit for obtaining the negative 325-volt supply for the time base from an existing power unit.

Fig. 2.4 (right). Connexion of time base to cathode-ray tube showing the arrangement of the Y-amplifier  $V_6$  and  $V_7$ .

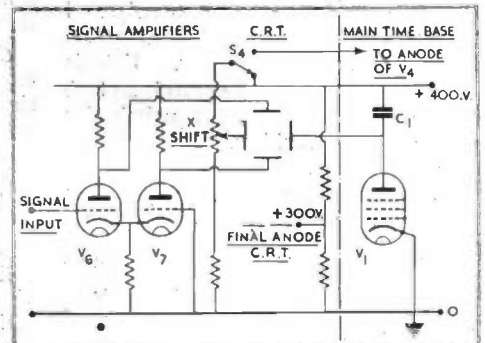



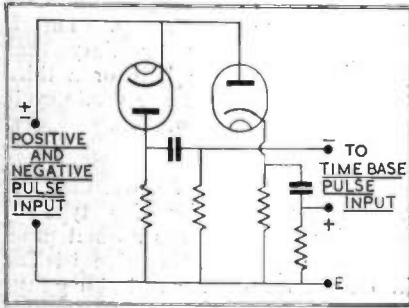


Fig. 2.5. Circuit for separating positive and negative pulses. The condensers and resistors should be selected to suit the duration and repetition frequency of the pulse.

for D.C. voltages. Other advantages are that the deflection is balanced, the amplifier is inherently stable and introduces little distortion. The design of cathode-coupled amplifiers has been fully dealt with previously in this journal and elsewhere.

The switch  $S_1$  connects the X-shift potentiometer either to the +400-volt line or to the anode of  $V_1$  for beam deflection modulation as described in Part I. With the switch in the latter position the spot is deflected off the screen until the main time base starts. The resistance of the potentiometer chain should be about 1 megohm.

**Performance of Time Base**

Some figures on the performance of the time base are given in the table. The figures for time delay and changeover time depend to some extent on stray capacities in the wiring and with special care could probably be improved upon.

**Notes on the Use of the Time Base**

The notes below are an amplification of the methods of using the time base given in Part I. They are not intended to be exhaustive but to act as a guide, since each application of the time base presents its own problems.

**Single Sweep Operation**

The actuating pulse applied to the pulse input terminals may be derived from the external circuits or may be the actual signal being examined. In either case, it may be necessary to shape the pulse before applying it to the time base in order that its duration shall not be too great (causing the time base to make more than one stroke for each pulse). The shaping may be achieved by passing the pulse through a differentiating circuit. The amplitude of the pulse is unimportant as long as it is large enough to trigger the time base. It

may be mentioned here that if the slider of  $V_{R_1}$  is not at its maximum position, a small time delay will be introduced in the start of the time base. This is sometimes useful and if the amplitude of the pulse is sufficient the delay can be varied up to about 10 microseconds. This delay could be increased still further by connecting a small condenser between grid and cathode of  $V_1$ , the input circuit acting as an integrator.

Sometimes it is convenient to be able to trigger the time base on negative and positive pulses from the same source, and this may be achieved by separating the positive and the negative pulses, and applying them to appropriate input terminals. A circuit is shown in Fig. 2.5 and with this arrangement the time base will trigger on the leading edges of the pulses. If it is desired to trigger on the trailing edges, it is only necessary to interchange the connexions to the positive and negative pulse input terminals.

It may be noted in passing that sufficient amplification is provided by  $V_1$  to trigger the time base directly from a photo-cell. This can be very useful when the time base has to be synchronised with a mechanical movement, and in many cases is more convenient than using a switch.

When non-recurrent random transients are being photographed, and the time base is required to make only one stroke, the switch  $S_2$  is turned to position 2. To reset the time base, the switch is switched to position 1 and then back to 2. Of course, when  $S_2$  is at position 1 the time base resets automatically at the end of each stroke.

It is often advantageous (and, when photographing, a necessity) to suppress the beam except during the working stroke. As noted in Part I, there are two simple methods—beam

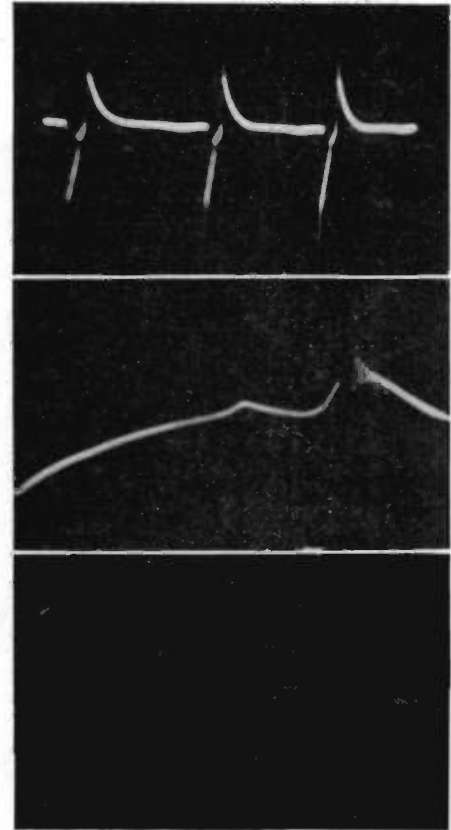


Fig. 2.6 (top). Figs. 2.7 and 2.8. Photographs of traces obtained with the sweep expansion circuit. The bottom photograph is of part of the waveform shown in the top photograph expanded about 500 times.

deflection and beam brightening. In the former, the beam is initially deflected off the screen of the tube until the start of the working stroke. How this is accomplished is indicated in the section above on the connexion of the time base to the tube. Beam deflection modulation will probably be satisfactory for most applications if not more than 5 per cent. of the stroke is lost. As can be seen from Table 1 the changeover time of the valves  $V_1$  and  $V_2$  is about 5 microseconds, so that the shortest sweep time that can be used is 100 microseconds. For sweep times less than 100 microseconds beam brightening may be employed, the beam being suppressed until the start of the time base. One method is to connect the modulating electrode of the cathode-ray tube through a condenser to the anode of  $V_1$ . Very little of the trace will be lost even with high spot velocities, since the voltage change on the anode of  $V_1$  is over 200 volts and only about 10 volts will be required to brighten the spot.

TABLE 1

Performance of Time Base	
Single Sweep Operation	
Sweep time maximum	1 second
minimum	5 microseconds
Time delay	1/2 microsecond
$V_1$ - $V_2$ changeover time	5 microseconds
Minimum amplitude of starting pulse	3 volts negative approx.
	1 volt positive approx.
Time base output	250 volts
Free Running Operation	
Frequency minimum	1 c/s.
maximum	200 kc/s.
Time base output	250 volts (at the lower frequencies)

For many applications it is essential to have the time base sweep calibrated. For this purpose a separate calibrating oscillator may be used and this is especially convenient when a double beam cathode-ray tube is available, as the extra beam can be used to supply the time scale. Alternatively, the X shift potentiometer may be calibrated in time intervals for a specified position of the potentiometer  $VR_1$ , assuming also that the values of the charging condenser  $C_1$  are selected so that the calibration will hold whichever charging condenser is switched in.

#### Sweep Expansion Operation

The procedure for using the sweep expansion circuit is as follows:

A cathode-ray tube is connected across the output of the auxiliary time base which is set so that a stationary two- or three-cycle picture of the signal waveform is visible. An expanded picture of the signal waveform is obtained on a cathode-ray tube connected to the output of the main time base, the degree of expansion being adjusted by

$VR_1$  and  $S_2$  and the part of the waveform expanded being selected by  $VR_2$ . In practice a single tube may be used, the X-plates being switched from one time base to the other.

Some photographs of traces obtained with the sweep expansion circuit are shown in Figs. 2.6, 2.7 and 2.8 and give some idea of its capabilities. Fig. 2.6 shows the waveform of an oscillator with a low frequency "squeg," as seen on a normal oscilloscope. The "squeg" frequency is approximately 75 per second. Fig. 2.7 shows the portion between the negative and positive peaks expanded about 20 times and in Fig. 2.8 the total expansion is about 500 times showing a part of the 60 kc/s. damped oscillation.

It is essential that the output voltage of the auxiliary time base should contain no superimposed A.C. ripple or the expanded trace will be very unsteady with high degrees of expansion. The blurring of the bottom photograph of the expanded trace is due to this cause. It may also be noted here that, due to condenser  $C_n$  discharging, it is possible to ex-

pand only about three-quarters of the auxiliary time base sweep. This is unimportant if the auxiliary time base frequency is a half or a third of the signal, so that one whole cycle is within the range of  $VR_1$ .

#### Free Running Operation

Little need be said about the time base when used for this type of operation, as it follows normal practice. The synchronising signal is fed into the terminal marked "negative pulse," or, if it is weak and requires amplification, into the terminal marked "positive pulse" on Fig. 2.1. The potentiometer  $VR_1$  controls the synchronising input to the suppressor grid of  $V_s$ .

#### Conclusion

It is hoped that the time base described in this article will prove useful as a general-purpose instrument. It is, of course, almost impossible to meet every eventuality, but the circuit is fairly flexible and can be modified for special applications. Little has been said about specific applications, but these will readily occur to the reader.

## Germanium

At the Rochester Fall Meeting of the I.R.E. and American R.M.A., Edward Cornelius (Sylvania Products) described the properties of germanium crystals as contact rectifiers for U.H.F.

Fig. 1 shows the construction of a rectifier unit Type IN.34, in which a square of germanium  $\frac{1}{8}$  in. thick is mounted in a cartridge with a tungsten contact point having a required contour and pressure.

The germanium is reduced from the dioxide by hydrogen and forms, on melting and cooling, crystals of the diamond type with relatively high resistivity at room temperatures.

A small amount of tin added during cooling improves the rectification properties with a slight reduction in resistance.

The characteristics of the crystal are shown in Fig. 2. At values of voltage characteristic of a particular unit (between 75 and 200) the characteristic curve departs from the exponential form and the dynamic resistance becomes zero and then negative as the current is increased,

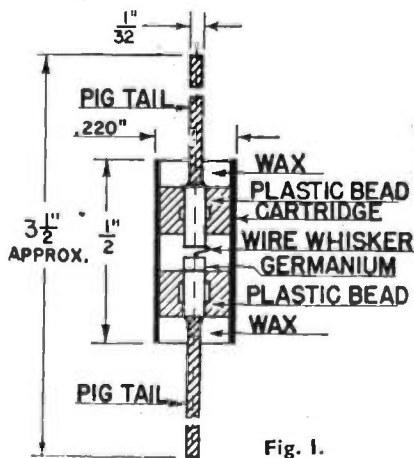


Fig. 1.

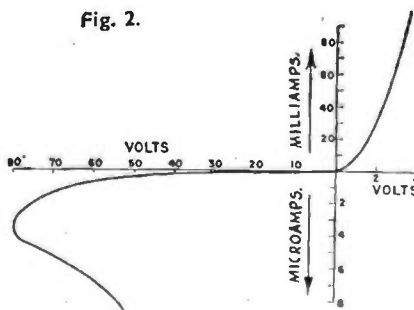


Fig. 2.

## Rectifiers

so that the voltage across the unit decreases. The portion of the curve in which the dynamic resistance becomes negative or zero may be used for voltage regulation, and if necessary a small positive resistance may be added in series to reduce the overall resistance to zero. Normal currents for regulator use are 7-30 mA D.C.

The advantages of this regulator over the gas discharge type are freedom from flicker and absence of high striking voltage, although large changes in ambient temperature or heavy currents may affect the regulation and life of the unit.


Comparison between this rectifier and the 6H6 diode shows that the former has an advantage at low values of load resistance. Very high temperatures may be produced at the contact point if an appreciable current is passed through the unit.

Among the many uses suggested for these crystals are modulators, voltage regulators, L.F. oscillators, D.C. restorers and polarising devices.

—Electronic Industries, Dec., 1945.

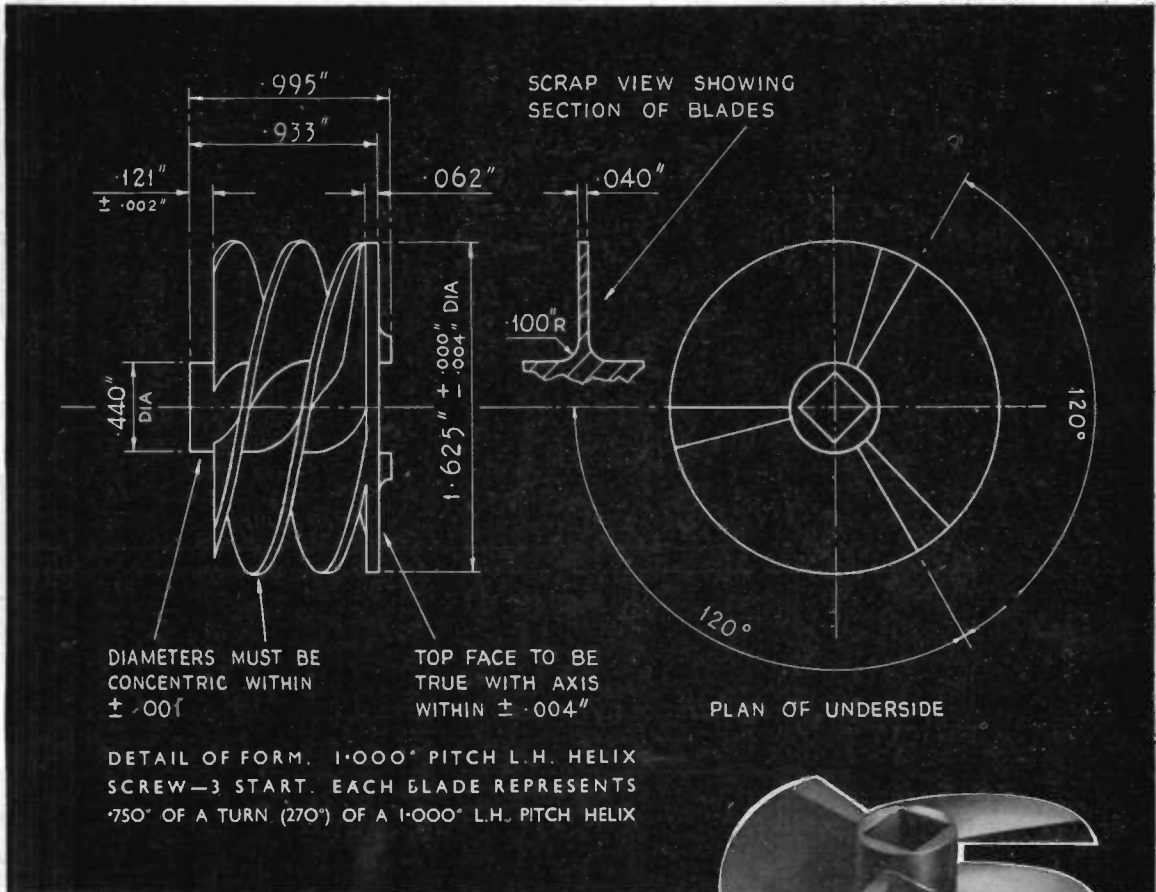
# THIS WAS THE PROBLEM

*It must rotate at 17,000 r.p.m.  
Its flange thickness must be .040". It must  
withstand a pressure of over 10 lb. per sq. in.*


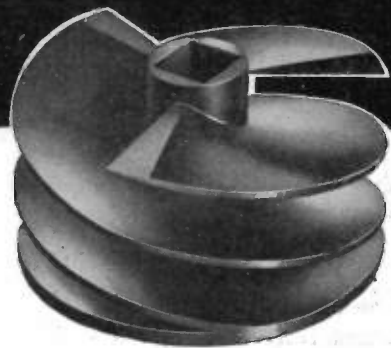
## —solved by moulding in **BAKELITE MATERIAL**

Previously machined from a solid bar of metal on a specially designed machine, this impeller was expensive and took a long time to make. As a Bakelite moulding it is produced in a fraction of the time at a greatly reduced cost. Further, it is more resistant to corrosive liquid.




TEST DATA:  
*At 17,000 r.p.m. pumped 250 galls. an hour—pressure 10 lb. per sq. inch. Later increased to 600 galls. an hour. Stood up to extra revs. perfectly. Material used—Bakelite Moulding Powder X5073. Moulding by Merriott Mouldings Ltd.*

**BAKELITE**  **PLASTICS**

REGD. TRADE MARKS

*Pioneers in the Plastics World*

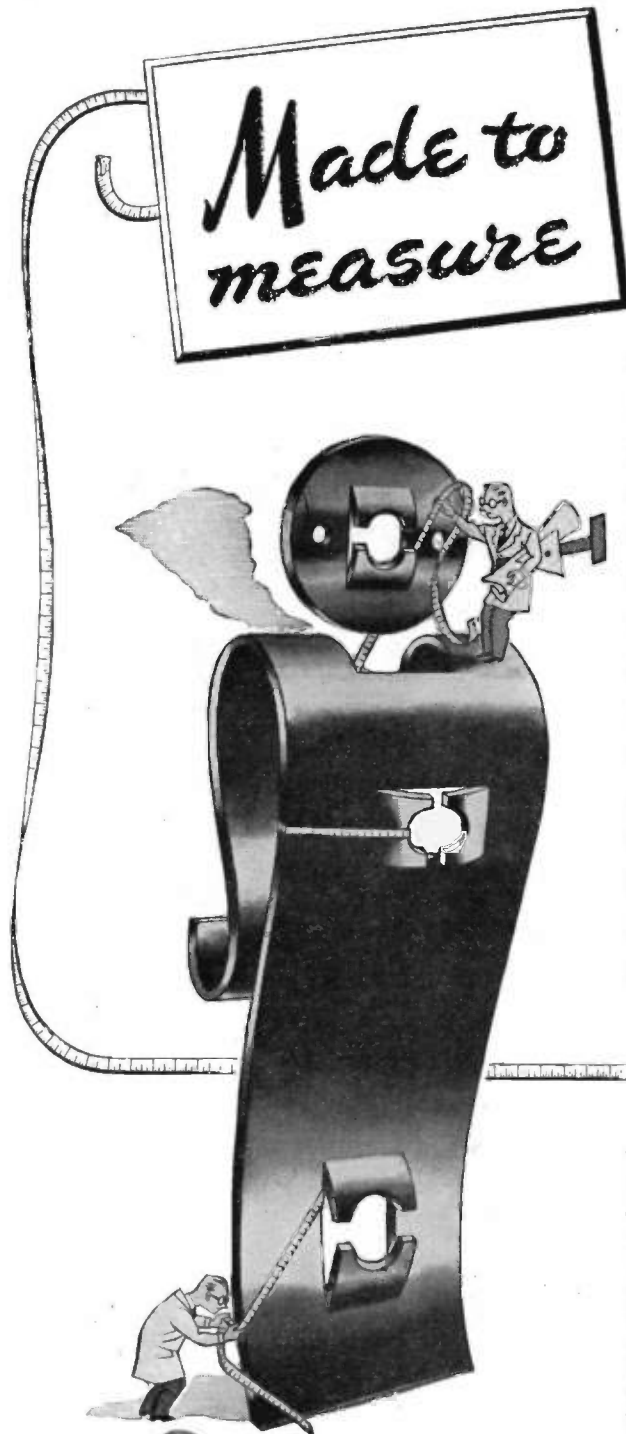
**BAKELITE LIMITED · 18 GROSVENOR GARDENS · LONDON S.W. 1**



The standard Spire nut is only one form, and the most elementary form at that, of fixing by the Spire method. There are already over 300 special Spire designs, each of which has been "made to measure," for some particular job. In most of them no separate nut or washer is needed. The Spire fixing is part of the component itself. It is pretty safe to say that Spire can simplify *most* assembly jobs. Send us along any ordinary assembly-parts or drawings. We'll see if we can't cut out some of the bits and pieces and reduce the operational time by designing a Spire assembly. No charge for this. If it works we'll get your order. If it doesn't we'll tell you so and there's no harm done.

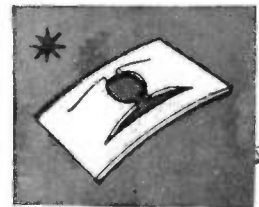**THAT'S Fixed THAT! NP 1506.**

Aircraft manufacturers and coachwork builders employing stressed skin construction are saving time and money and material by the use of this simple Spire fixing. It serves to hold the tack bolts in position until riveting of skin sections has been completed. It is quicker to use than the usual square pressed nut and is easily removed for further use when its 'holding job' is done.



# Spire

\* **A BETTER way of fixing**

# H.F. Band-Pass Filters

## Part II.—Similar Circuits

By H. PAUL WILLIAMS, Ph.D., A.M.I.E.E.

### 2.1 Similar Circuits

#### 2.1.1 General

As was mentioned in the Introduction, it is possible to develop the theory of H.F. band-pass filters quite simply from first principles. Owing to the fact that the circuits involved have Q values of the order of 20 and upwards, it is possible to make an exceedingly useful approximation. This approximation concerns the series impedance of a tuned circuit near resonance and leads to an expression which greatly simplifies the subsequent calculations.

In Fig. 4 the series impedance is given by:—

$$Z = R + j\omega L + \frac{1}{j\omega C}$$

$$= R \left[ 1 + j \left( \frac{\omega L}{R} - \frac{1}{R\omega C} \right) \right]$$

$$= R \left[ 1 + j \left( \frac{\omega^2 LC - 1}{R\omega C} \right) \right]$$

By putting  $\omega = \omega_0 + \delta\omega$  where  $\omega_0$  is the resonant frequency, and by neglecting  $(\delta\omega)^2$  we have:—

$$Z = R \left[ 1 + \frac{2\delta\omega L}{R} \right]$$

$$= R \left[ 1 + j \frac{2\delta\omega}{\omega_0} \frac{\omega_0 L}{R} \right]$$

At this stage we introduce the parameter  $q$  which equals the distance off tune in terms of band-width.  $q$  may be positive or negative according to which side of the on-tune position we go. In this manner the band-pass curves are made applicable to any frequency. It merely becomes a matter of making the appropriate substitution of the number of kc/s. for unit  $q$ .

Now the band-width of a single circuit is given by  $\frac{f_0}{Q}$  where Q has the conventional meaning and equals  $\frac{\omega_0 L}{R}$ .

Therefore  $q = \delta f / \frac{f_0}{Q} = \frac{\delta f}{f_0} \cdot Q = \frac{\delta\omega \cdot Q}{\omega_0}$

$$\therefore q = \frac{\delta\omega}{\omega_0} \frac{\omega_0 L}{R}$$

Hence  $Z = R(1 + jq)$  ..... (1)

$q$  is a dimensionless quantity of the order of  $\pm 1, 2$  or  $3$ . If, for example,

$f_0 = 1,000$  kc/s.

$Q = 100$

then  $f = 985$  kc/s. means  $q = -1.5$

$f = 1,020$  kc/s. means  $q = +2$

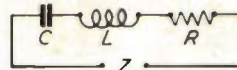


Fig. 4.

#### 2.1.2 Mutual Coupling

The circuit equations for Fig. 5 may be written as follows (N.B.—in practice  $R$  includes the damping due to valves, see Section 3):—

$e = i_1 Z_1 - i_2 j\omega M$  ..... (i)

$0 = i_2 Z_2 - i_1 j\omega M$  ..... (ii)

$$\therefore i_2 = \frac{e j\omega M}{Z_1 Z_2 + \omega^2 M^2}$$

In all practical cases,  $V_2 = i_2 j\omega L$  to a close approximation.

$$\therefore \frac{V_2}{e} = \frac{-\omega^2 M L}{Z_1 Z_2 + \omega^2 M^2}$$

In the present case  $Z_1 = Z_2$  and both are equal to  $R(1 + jq)$ .

$$\therefore \frac{V_2}{e} = \frac{-\omega^2 M L}{R^2(1 - 4q^2 + j4q) + \omega^2 M^2}$$

We now introduce a very convenient parameter  $K$ , which equals the common coupling impedance divided by the series resistance of a single circuit. For the case of unequal damping we use the geometric mean of the two values, i.e.,  $\sqrt{R_1 R_2}$ .

$$\therefore K = \frac{\omega M}{R} = \frac{\omega L}{R} \frac{M}{L}$$

$= Q \times \text{percentage coupling}$

Over the range of frequencies we are interested in,  $K$  may be taken as being a constant and equal to  $\frac{\omega_0 M}{R}$ .

Critical coupling occurs when  $K = 1$ . When  $K > 1$  the circuits are over-coupled and two peaks are formed.

Making this substitution, we have:

$$\frac{V_2}{e} = -Q \frac{K}{(1 + K^2 - 4q^2) + j4q}$$
 ..... (2)

An alternative expression is:

Response off tune  
Response on tune

$$= \frac{1}{1 + K^2} \dots \dots \dots (2a)$$

Graphs of this expression for different values of  $K$  are given in Section 4. The choice of the parameter  $q$  (which involves the band-width) permits these curves to be applied for any value of  $f_0$ .

#### Gain On Tune

From Equation (2) we find that when  $q = 0$ ,

$$\frac{V_2}{e} = -Q \frac{K}{1 + K^2} \dots \dots \dots (2b)$$

This has a maximum value when  $K = 1$  and then

$$\frac{V_2}{e} = -\frac{Q}{2}$$

Therefore the maximum gain on tune is half that given by a single circuit of the same Q.

It must be remembered that  $e$  in the above expressions is the series-injected voltage and not the grid voltage  $e_g$ . In the case of pentode valves we have  $e = k e_g$  where  $k$  is some constant whose values will usually lie somewhere between 4 and 10 (see Section 2.31).

#### Position of Peaks

Equation (2) has its maximum value when  $(1 + K^2 - 4q^2)^2 + (4q)^2$  is a minimum. Calling the latter expression  $y$  we have:—

$$\frac{dy}{dq} = 2(1 + K^2 - 4q^2) \times (-8q) + 32q$$

This is zero when  $z = 1 + K^2 - 4q^2$ . Giving this value for  $q$  the suffix  $m$ , we have:

$$q_m = \pm \sqrt{\frac{K^2 - 1}{4}} \dots (2c)$$

The above equation is only valid when  $K \geq 1$ .

Note that  $q=0$  is also a solution to  $dy/dq = 0$ . This, of course, represents the on-tune point which is a maximum when  $K \leq 1$  and a minimum value when  $K > 1$ . The equation for  $dy/dq$  is really a cubic and has to be solved as such in the case examined in Section 2.23.

**Maximum Response**

Using the value for  $q$  given in Equation (2c) we have:

$$\frac{V_2}{e} = \frac{-QK}{1 + K^2 - 4\left(\frac{K^2 - 1}{4}\right) + j4\sqrt{\frac{K^2 - 1}{4}}}$$

$$\therefore \frac{V_2}{e} = -\frac{Q}{2} \dots (2d)$$

The maximum voltage is therefore independent of  $K$  when  $K > 1$  and always half of that given by a single circuit.

From (2b) and (2d) we find:

$$\frac{\text{Response on tune}}{\text{Maximum response}} = \frac{2K}{1 + K^2} \dots (2e)$$

**Response Equal to that On Tune**

In the case of two peaks, the response becomes equal to that on tune when:

$$(1 + K^2 - 4q^2)^2 + (4q)^2 = (1 + K^2)^2$$

Giving this value for  $q$  the suffix  $s$ , we obtain:

$$q_s = \sqrt{\frac{K^2 - 1}{2}} \dots (2f)$$

Also, by using the value for  $q_m$  given in Equation (2c) we find:

$$q_m = \sqrt{2}q_m$$

**Rough Plot of Response Curve**

Using Equations (2c), (2e) and (2f) we can immediately obtain 5 points on the resonance curve.

Suppose, for instance,  $K = 1.5$ , then from (2e) we find that the response on tune is .923 times that at the peaks. The position of the two

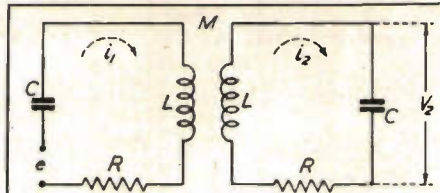


Fig. 5. Mutually coupled circuits.

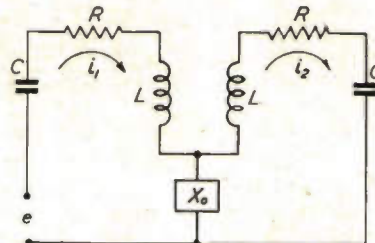


Fig. 6. Circuits with bottom-end coupling.

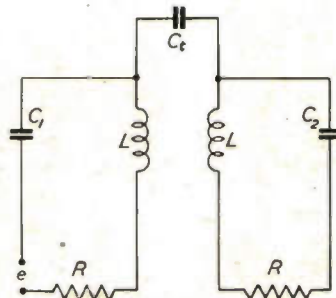


Fig. 7. Circuit with top-end capacity coupling.

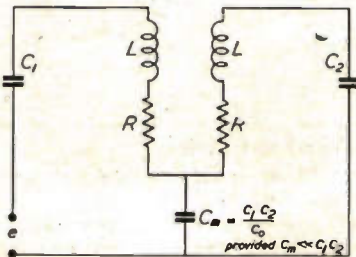


Fig. 8. Circuit of Fig. 7 with top-end capacity replaced by equivalent bottom-end capacity.

peaks is given by  $q_m$ , which equals  $\pm .56$ . Finally, the response again equals .923 when  $q_s = \pm \sqrt{2} \times .56 = \pm .79$ .

**Response well Off Tune**

If  $q > \pm 3K$ , then a good approximation for  $\frac{V_2}{e}$  is  $\frac{QK}{4q^2}$ .

This indicates that well off tune the shape of the response curve is independent of  $K$  and is, in fact, given by:

$$\text{Response} \propto \frac{1}{q^2}$$

**Separation between Peaks**

The separation between the two peaks =  $2q_m$ .  
=  $2q_m$  times the bandwidth (in kc/s.)

$$= 2\sqrt{\frac{K^2 - 1}{4}} \cdot \frac{R}{2\pi L} = \frac{1}{2\pi L} \sqrt{R^2(K^2 - 1)}$$

$$\therefore \text{Separation} \propto (\omega^2 M^2 - R^2)^{1/2} \dots (2g)$$

**Comparison with Single Circuits**

With very loosely coupled circuits  $K \ll 1$  and we may neglect  $K^2$  in Equation (2a).

$$\frac{\text{Response off tune}}{\text{Response on tune}} = \frac{1}{1 - 4q^2 - j4q} = \frac{1}{(1 - j2q)^2}$$

Comparing this with the resonance curve of a single circuit as given by Equation (1), we see that the loosely coupled band-pass has a similar selectivity curve to that given by two single circuits in cascade. For large values of  $q$  (say 3 or more), the response for a single circuit  $\propto \frac{1}{q}$ , while that of any band-pass (whether loosely coupled or not)  $\propto \frac{1}{q^2}$ .

A further comparison with a single circuit is given by examining the relative widths at 3 db. and 20 db. down. Suppose we can tolerate an attenuation of 3 db. down from the maximum, then the optimum band-pass (i.e., minimum width at 20 db. down) is obtained when the circuits are over-coupled as far as possible—in this case until the response on tune has dropped to 3 db. down relative to the peaks.

	Width at 3 db. down	Width at 20 db. down
Single circuit	1.0	10
Best coupled circuit (3db down on tune)	3.12	8.6

In the above table it was assumed that the coupled circuits had the same Q as the single one. If the coupled circuit Q values were increased so that the bandwidth at 3 db. down equalled that of the single circuit (i.e., 1.0q), then the width at 20 db. down becomes  $\frac{8.6 \times 1.0}{3.12} q = 2.75q$ .

Therefore a 3.6:1 improvement is obtained over a single circuit at the 20 db. attenuation level.

If no higher Q circuits are available, then the correct coupling to give a width of 1.0q at 3 db. down is  $K = .67$ . This results in a width of 3.7q at 20 db. down and consequently gives a 2.7:1 improvement over a single circuit.

**2.13 Bottom-End Coupling**

The circuit for this case is shown in Fig. 6.  $X_o$  is the impedance of the coupling reactance at the on-tune frequency. In the equations that follow, the reactance is assumed to have a positive value, i.e., the coupling is a common inductance. If the coupling is a capacity, the sign of  $X_o$  is changed throughout, resulting in a ratio of  $V_2/e$  that is the same as before in magnitude, but has a phase relationship on tune which differs by 180° from the inductive case.

Let  $Z$  = total series impedance, including  $X_o$ .

$$= R + j \left( \omega L - \frac{1}{\omega C} \right) + jX_o$$

$$= R(1 + j2q)$$

The circuit equations are therefore:

$$e = i_1 Z_1 - i_2 j X_o$$

$$0 = i_2 Z_2 - i_1 j X_o$$

Proceeding on the same lines as for Equation (2) we find:


$$\frac{V_2}{e} = -Q \frac{K}{(1 + K^2 - 4q^2) + j4q} \dots (3)$$

where  $K = \frac{X_o}{R}$

Therefore the response is exactly the same as for mutual coupling. But now, since  $Z$  includes the coupling impedance, when we increase the

Fig. 9. Circuit with mixed coupling.

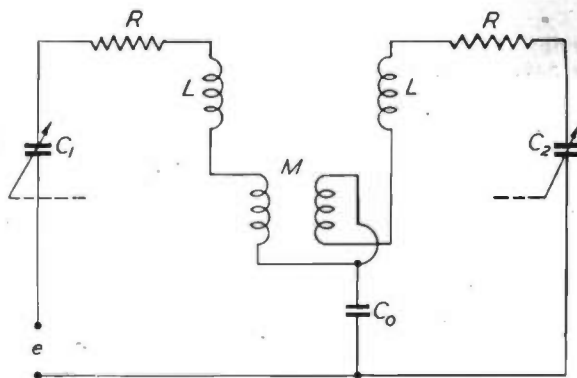Values:  $L_1 - L_2 = 2.310 \mu H$   
 $M = 11.8 \mu H$   
 $C_1 = C_2 = C_o = 0.03 \mu F$



coupling the peaks do not move out symmetrically on either side of the centre frequency.

The difference with mutual coupling, therefore, lies in the fact that trimming cannot be done by first reducing the coupling and then increasing it to the required amount after the circuits have been trimmed.

This feature is brought out if we take  $Z = Z' + X_o$ , where  $Z'$  is the series impedance without  $X_o$ . The expression for the response then becomes:

$$\frac{V_2}{e} = -Q \frac{K}{(1 - 4Kq - 4q^2) + j2(K + 2q)}$$

From an examination of the denominator of the above equation we see that the peaks are no longer symmetrical about  $q = 0$  if the resonant frequency  $f_o$  is taken without  $X_o$  in circuit.

In fact, one peak remains at approximately  $f_o$ , while the other appears above or below  $f_o$  as we increase the coupling. The same is true of top-end coupling and the results may be tabulated as shown below.

Frequency of Second Peak	Bottom-End Coupling	Top-End Coupling
Below $f_o$	$\omega L$	$\frac{1}{\omega C}$
Above $f_o$	$\frac{1}{\omega C}$	$\omega L$

**2.14 Top-End Coupling**

A circuit involving top-end capacity coupling is shown in Fig. 7. The theory of top-end inductive coupling can be developed on similar lines, but since such a circuit involves the use of a high inductance, the case is obviously not used in practice.

The circuit of Fig. 7 can be analysed by using three circulating currents. Such an analysis results in an unsymmetrical expression for positive and negative values of  $q$ . It is therefore easier to replace the top-end capacity by its equivalent bottom-end capacity and use the results of the previous section. To do this we make use of a T arrangement of condensers which is equivalent to the arrangement of top-end coupling.

This procedure reduces the circuit to that shown in Fig. 8. In the latter figure  $C_m = \frac{C^2}{C_t}$  provided  $C_t \ll C$ , which is true in practical cases.

When this substitution has been made, Equation (3) applies.

In this case

$$K = \frac{X_m}{R} = \frac{1}{\omega R C_m} = \frac{C_t}{\omega R C^2}$$

Now  $\frac{1}{\omega R C} = Q \therefore K = Q \frac{C_t}{C}$

The last expression for  $K$  shows that critical coupling occurs when the ratio of the capacities is equal to the Q of the circuits.

Although the approximation given in Fig. 8 leads to the correct shape of curve, erroneous conclusions can be arrived at both with regard to the manner in which the peaks move on increasing coupling and also with regard to the effect of damping one side. For instance, it might be thought that since the resonant frequency of either mesh in Fig. 8 is above that given by excluding the common coupling, the second peak should be above  $f_o$ . The table at the end of the Section 2.13, however, contradicts this deduction.

The explanation lies in the fact

that the equivalent circuit is not sufficiently accurate for this deduction. The true equivalent circuit has tuning condensers of value  $(C + 2C_1)$  and a bottom-end condenser of  $\left(\frac{C^2}{-} + 2C\right)$ .

Thus the value of the two capacities in series (*i.e.*, the total tuning capacity of either mesh) is actually of the order of  $(C + C_1)$  and not  $(C - C_1)$  as would be inferred from Fig. 8. Hence increasing the top-end capacity causes the second peak to move further *down* the frequency scale.

### 2.15 Mixed Coupling

The equations previously developed will also hold for mixed couplings (provided they are purely reactive); for example, we may have

$$X_o = \left( \omega L_o - \frac{1}{\omega C_o} \right) \quad \text{It is obvious}$$

that the value of  $X_o$  will not vary with the tuning frequency in a simple way. So to avoid unnecessary calculations it is useful to examine the change in  $X_o$  with frequency to give either:

- (a) approximately constant peak separation;
- or (b) to pass near, or through, some predetermined points.

(a) Using Equation (2g) we see that the peak separation varies as  $(\omega^2 M^2 - R^2)^{1/2}$ , *i.e.*, in the general case,

$$\text{Peak separation} \propto (X_o^2 - R^2)^{1/2}$$

Therefore the separation is constant if  $(X_o^2 - R^2)$  is constant. To approximate to such a condition we must first plot  $R$  against  $f$  from experimental results. Then values of  $X_o$  are chosen to give the best constant difference with this  $R$  versus  $f$  curve.

Usually the required value for  $X_o$  is of the form  $\left( \omega M_o + \frac{1}{\omega C_o} \right)$

where  $M$  is a negative mutual. This can be made to satisfy two frequencies exactly. A practical example of such a mixed circuit is shown in Fig. 9. In this example the peak separations are correct at 250 and 400 kc/s.

(b) In practice, constant peak separation is usually not of so great importance as the obtaining of certain responses at certain frequencies over the tuning range. A neat method of achieving this as closely as possible has been described by Beatty (*Wireless Engineer*, October, 1932).

The method as applied to mixed mutual and bottom capacity coupling is as follows:

$$X_o = \omega M + \frac{1}{\omega C} \quad (\text{where } M \text{ is a negative mutual}).$$

Then a plot of  $X_o$  against  $\omega$  on log-log graph paper results in the same shaped curves if the product  $MC$  is kept constant (this can be appreciated if we consider the case when  $M$  and  $C$  are replaced by  $kM$  and  $C/k$  on the graph).

As for the position of the curve, this depends on the ratio  $M/C$ .

We now plot  $X/X_o$  against  $f/f_o$  on log-log paper (the suffix  $o$  is here reserved for *some particular value* of the coupling impedance and tuning frequency, and is dropped for the general case).

$$\frac{X/X_o}{\omega M + \frac{1}{\omega C}} = \frac{\omega M + \frac{1}{\omega C}}{\omega_o M + \frac{1}{\omega_o C}} = y, \text{ say.}$$

$$f/f_o = x, \text{ say.}$$

Then  $x$  and  $y$  can be related as follows:

$$\text{Put } \omega_o M = A \left( \omega_o M + \frac{1}{\omega_o C} \right)$$

(where  $A$  is constant)

$$\text{also } \frac{1}{\omega_o C} = (1 - A) \left( \omega_o M + \frac{1}{\omega_o C} \right)$$

$$y = A \frac{\omega}{\omega_o} + (1 - A) \frac{\omega_o}{\omega} \\ = A x \frac{(1 - A)}{x}$$

Curves of  $x$  against  $y$  will be shown plotted for different values of  $A$  in Fig. 33 of Section 4.

$A = 1$  corresponds to pure mutual coupling.

$A = 0$  corresponds to pure capacity coupling.

The curves of Fig. 33 are used in practice by putting the desired curve of  $x$  against  $y$  on tracing paper and moving it about over the figure (keeping the respective  $x$  and  $y$  axes parallel) until the best fit is obtained with some particular value of  $A$ .

The point 1.1 then gives  $f_o$  and  $\left( \omega_o M + \frac{1}{\omega_o C} \right)$ , while the best  $A$  value decides the ratio of  $\omega_o M$  to  $\frac{1}{\omega_o C}$ .

(To be continued.)

## German Tape-Recording Equipment

The U.S. Broadcasting Commission in Europe have recently reported on a German-developed recording and playback equipment, which they consider superior to any used in Europe or America.

The equipment is manufactured by the E.E.G. Magnetophon and uses thin tape of a plastic base, specially made by the I.G. Farben industry. This tape is a form of dry-processed unplasticised polyvinyl chloride 0.035 mm. thick, on which is coated a layer of iron oxide mixture 0.008-0.01 mm. thick.

This mixture consists of black oxide prepared at 230° C. for 6 hours with agitation to give small crystals of magnetic ferric oxide, together with Igelit MP.400 in equal proportions.

The cost is estimated at \$3.00 per roll, which plays for about 20 minutes.

In operation, the tape passes through the gap of a small magnetic armature with the surface bearing the oxide in contact with the armature. Recording and playback is accomplished in the usual way, and there is a wipe-out mechanism enabling the tape to be used again.

At the regular tape speed of 80 cm/sec. it is said that the instrument will record and reproduce frequencies as high as 10,000 c/s. and the normal range is from 20 to 8,000 c/s.

The system was in general use throughout the German Army for fixed station recording and for mobile units, and in 1943-44 the production was approximately 6,000 tapes per month.

The performance of this equipment was apparently known to the B.B.C. engineers, and a demonstration was given to the American mission at Radio Luxembourg, where the equipment has been operating without a fault since 1941. No deterioration in recording has been experienced, surface noise is negligible, and the tape can be easily edited and spliced.



—*Electronic Industries*, Nov., 1945.



# Polyphase from Single Phase

for Valve Supply Circuits

—Communication from E.M.I. Laboratories.

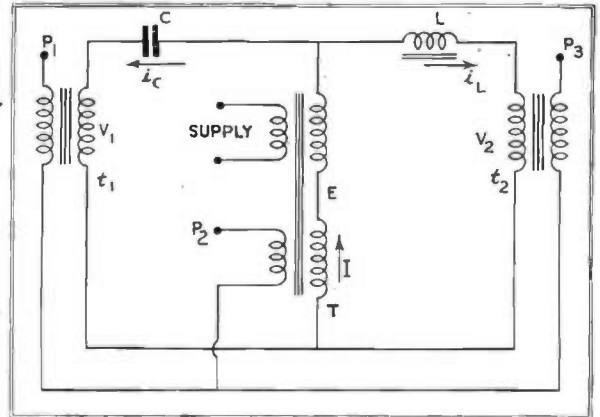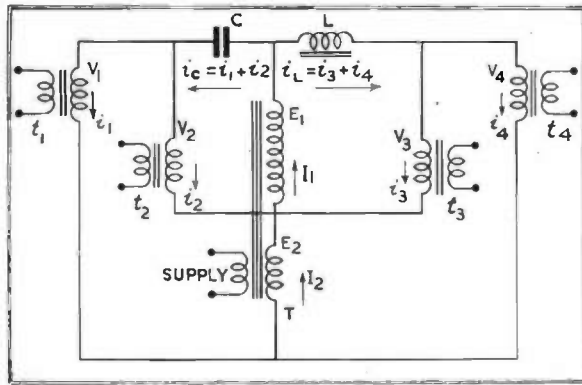

IT happens on occasions in the design of radio apparatus that it is very desirable to employ a polyphase supply circuit rather than a single phase circuit. One instance may be found in the A.C. heating of the filaments of transmitting valves. Often it is observed that the anode current of a transmitting valve is modulated at double the frequency of the heating supply. This is due to the filament heating current setting up a magnetic field within the valve which is able to exert an appreciable controlling influence upon the electron flow to the anode. The effect is known appropriately as the "magnetron effect." When several transmitting valves are operated in parallel it will be clear that the severity of the hum modulation can be reduced by feeding the filaments from a multiple supply so that the magnetron effect in the several valves is out of step. Often, however, the supply available is only single phase.

Again, for supplying direct current to equipment from an A.C. source it is frequently advantageous to use, say, a three-phase rectifier circuit because, for one reason, the smoothing required subsequent to rectification is more simple than with single-phase rectification. Again, however, it may happen that the supply to hand is not the desired polyphase but single phase.

Conversion circuits that are able to provide a polyphase supply when connected to a single-phase source and so overcome in these and like instances the difficulties that may

arise with single-phase supply are shown in Figs. 1 and 2.

Fig. 1 relates to a transmitting circuit in which the filaments of a bank of four transmitting valves are to be fed in different phases so that there is no resultant hum modulation. It can be shown that in the case of a bank of four valves the "magnetron effect" is reduced to a minimum when the phases of currents fed to the filaments of the four valves differ from each other by  $45^\circ$ . Thus, the transformers  $t_1, t_2, t_3, t_4$  have to be arranged to feed the four filaments with currents of equal amplitude in a phase sequence having equal spacings of  $45^\circ$ . This is accomplished by feeding transformers  $t_1$  and  $t_2$  through a capacity  $C$  from the transformer  $T$  and transformers  $t_3$  and  $t_4$  through an inductance  $L$  and properly choosing the tapping points on the transformer  $T$  appropriate to individual transformers, so that the current delivered by the secondary of transformer  $t_1$  leads the supply current in transformer  $T$  by  $22\frac{1}{2}^\circ$  and that delivered by the secondary of  $t_2$  leads by  $67\frac{1}{2}^\circ$ , whereas the currents from the secondaries of  $t_3$  and  $t_4$  are made to lag by  $67\frac{1}{2}^\circ$  and  $22\frac{1}{2}^\circ$  respectively. It should be noted that to this end, namely, the establishment of the required phase relationships, the primary windings are given different values of inductance. These values determine the transformation ratio of each transformer when it is decided, for instance, that each transformer is to feed the same power to its load.

In the case of a bank of three valves the phase difference between the three supplies should be  $60^\circ$  and this may be obtained as shown in Fig. 2. It will be seen that similar principles are employed, but as only three supplies are required, it is sufficient to obtain one supply lagging by  $60^\circ$  by means of a series inductance, one leading by  $60^\circ$  by means of a series capacity and the third in phase with the supply by means of a winding coupled to the supply transformer.

## Electronic Aids to Pig-keeping

The trouble for our designers and engineers is to be able to get to know over all the vast range of industrial processes of this country what are the needs in any particular industry. For example, my colleague has suggested a grand help to farmers—an instrument to measure the thickness of the fat layer on the back of a pig. This thickness apparently determines the price a pig fetches. The farmer of the future won't prod the pig as of yore, but he will carry round a suitable little instrument. This will have a dial that can be set to the latest Fat Stock Prices when the B.B.C. once again broadcasts such information; the instrument will determine the exact thickness of the fat layer, and the worth of the beast will be directly shown on the dial!

—From an address by T. W. Heather (G.E.C.) at the opening of an exhibition of electronic apparatus.

# Triode Equivalent Circuits

By D. A. BELL, M.A., B.Sc.

## I. Introduction

SEVERAL articles on phase conventions in triode circuits have been published recently (References 1, 2, 3), but the net result appears to be to leave confusion worse confounded,\* and probably the main trouble is that different authors have different implicit assumptions and conventions which may not be appreciated by the reader. It therefore seems worth while to show the development of equivalent circuits from first principles, with all assumptions and conventions explicitly stated. The less-known triode equivalent circuit using a fictitious current generator is included, as well as the familiar circuit with fictitious e.m.f. generator.

## 2. The Linearity Approximation and the Omission of D.C.

Consider first the diode circuit of Fig. 1(a), which includes both a battery maintaining a constant potential difference  $E_b$  and an alternator providing an alternating potential  $E_a$  which we will assume to be small compared with the constant potential. (The internal resistances of both battery and alternator are assumed to be negligible.) Then we know that in fact the current through the diode is very nearly:

$$I_a = AV_a^{3/2} = A(E_a + E_b)^{3/2} \dots (1)$$

Since  $E_a$  is assumed small compared with  $E_b$ , a binomial expansion gives:

$$I_a = AE_b^{3/2} \left( 1 + \frac{E_a}{E_b} \right)^{3/2} \approx AE_b^{3/2} \left[ 1 + \frac{3}{2} \frac{E_a}{E_b} + \frac{3}{8} \left( \frac{E_a}{E_b} \right)^2 + \dots \right] \dots (2)$$

and to the first power in  $E_a$ , with a

\* Reference 1 started the trouble, 2 relies upon expressing the output as a cathode-anode potential difference instead of anode-cathode, while 3 endeavours to avoid the difficulty by suggesting that there is no phase relationship at all between anode current and grid voltage.

fixed value of  $E_b$ , this may be recast in the form:

$$I_a = i_o + E_a/R_a \dots (2a)$$

where both  $i_o$  and  $R_a$  are functions of  $E_b$ . For applications in which the steady potentials and currents are not required in the answer, Equation (2a) shows that a circuit equivalent to the real diode arrangement is that shown in Fig. 1(b), the equivalent of the diode being simply a resistance of value  $R_a$ . The two conditions for this equivalence are (a) exclusion of steady components from the problem and (b) the varying components being small enough compared with the (suppressed) steady components to allow the system to be regarded as linear.

As a further step, suppose that a resistance of value  $R$  is connected in series with the diode anode. Clearly the anode voltage will now be:

$$V_a = E_a + E_b - RI_a \dots (3)$$

and the equivalent circuit for A.C. components is that of Fig. 1(c).

## 3. Voltage Generator Equivalent Circuit for the Amplifying Triode

Fig. 2(a) shows a triode having D.C. sources and A.C. generators in both anode and grid circuits, the resultant anode and grid voltages being  $V_a$  and  $V_g$ . Since we now have two circuits, grid and anode, it is necessary to establish some convention to relate the senses of potential differences occurring in them. It is fundamental that the convention relating to some specific item should agree with more general conventions wherever possible, and where an "earth" is available it is a general convention that one may refer to the potential (with respect to earth) of a point, as well as the difference of potential between two points. Applying this to Fig. 2(a), the potentials

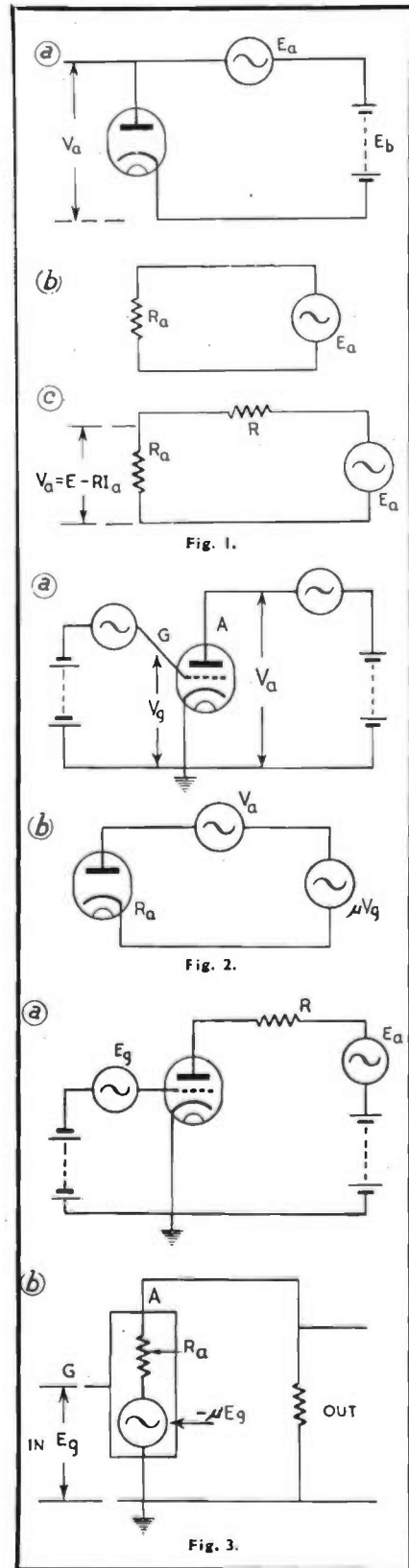


Fig. 1.

Fig. 2.

Fig. 3.

of  $A$  and  $G$  are  $V_a$  and  $V_g$  respectively, and clearly any alternating components of these two potentials are in phase if the two points reach their maximum positive potentials simultaneously. Now it is a well-known property of the triode that the anode current is a function of the factor  $(V_a + \mu V_g)$ , and for changes of potential small enough for the linearity approximation to be valid:

$$I_a = (V_a + \mu V_g)/R_a \dots\dots\dots (4)$$

The circuit equivalent to Fig. 2(a), referred to the anode circuit of the triode, is then as shown in Fig. 2(b). But when we proceed, just as in the diode case, to insert a resistance in series with the triode anode (Fig. 3(a)), we find it impossible to modify Fig. 2(b) in the same way that Fig. 1(b) was turned into 1(c), because  $R$  is in series with  $E_a$  but not in series with  $E_g$ . Resorting, therefore, to algebra, we write for the alternating components of Fig. 3(a):

$$V_g = E_g \dots\dots\dots (5a)$$

$$V_a = E_a - RI_a \dots\dots\dots (5b)$$

In the particular case of an amplifying valve having a signal applied to its grid but no source of alternating e.m.f. in its anode circuit, *i.e.*, if  $E_a = 0$ , Equation (5b) reduces to

$$V_a = -RI_a \dots\dots\dots (6)$$

and  $V_a$  is, of course, the output voltage of the triode amplifier. Eliminating  $I_a$  between (4) and (6):

$$\begin{aligned} -V_a/R &= (V_a + \mu V_g)/R_a \\ V_a &= -\mu V_g R/(R + R_a) \dots\dots\dots (7) \end{aligned}$$

The equivalent circuit which pictorially represents Equation (7) is that shown in Fig. 3(b), in which the valve is replaced by a resistance  $R_a$  in series with a fictitious generator of e.m.f. minus  $\mu E_g$ . But it must be clearly understood that, unlike Fig. 2(b), the circuit shown in Fig. 3(b) *does not contain a valve*; if it is desired to retain the valve in the pic-

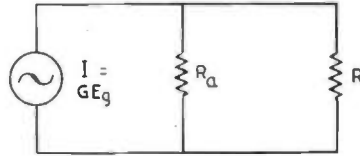


Fig. 4.

ture, we must revert to Fig. 3(a) and Equation (4).\*

**4. Current-Generator Equivalent of the Amplifying Triode**

An alternative circuit which produces the same answer is shown in Fig. 4, where instead of a voltage generator in series with  $R_a$ , we have in parallel with  $R_a$  an infinite-impedance generator delivering a current of magnitude  $GE_g$ , where  $G$  is the mutual conductance and is equal to  $\mu/R_a$ . The external load resistance  $R$  is in parallel with  $R_a$ , so that the current  $I_a$  flows through an impedance  $RR_a/(R + R_a)$ , thereby generating a potential difference:

$$V_a = -GE_g RR_a/(R + R_a) \dots\dots (8)$$

(The negative sign arises because the constant-current generator may be regarded as the limiting case of a generator of large e.m.f. in series with a high resistance, and the potential difference across the external circuit is obviously opposed to the e.m.f. of the generator.) The substitution of  $G = \mu/R_a$  in Equation (8) immediately reproduces Equation (7), and the equivalence of Fig. 4 with Fig. 3(b) is thus demonstrated.

The current-generator equivalent circuit of the amplifying triode has been introduced in the preceding paragraph simply as an algebraic transformation from the voltage-generator circuit; but the current-generator circuit has the advantage of avoiding a reversal of phase between the grid voltage in the real circuit and the fictitious generator in the equivalent circuit. It can further be argued that there is a better physical basis for Fig. 4 than for Fig. 3(b), and the author's approach to this is

\* For example, it would be wrong to insert the fictitious generator voltage  $-\mu E_g$  into the valve equation (4); the grid voltage of the valve is  $+E_g$ .

through shot noise phenomena. The passage of an electron from cathode to anode of a valve is equivalent to a pulse of current which charges the condenser formed by the anode-cathode capacity; and disregarding any effects of space-charge during the flight of the electron, the mean square fluctuation current due to this effect is:

$$\overline{I_{ar}^2} = 2ie \cdot df \dots\dots\dots (9)$$

Now the varying charges placed on the anode are dissipated partly through the external resistance  $R$  and partly by virtue of the fact that they cause changes of anode potential which in turn affect the mean anode current through the valve, *i.e.*, the charges are dissipated partly through the internal anode resistance  $R_a$  of the valve. In effect, therefore, the current flows through resistances  $R$  and  $R_a$  in parallel, and the resultant mean square output voltage (see, for example, Reference 4) is then:

$$\overline{V_{ar}^2} = \overline{I_{ar}^2} \cdot \left( \frac{RR_a}{R + R_a} \right)^2 \dots\dots (10)$$

Equation (10) would be represented by Fig. 4 if the output of the current-generator were changed from  $GE_g$  to  $\sqrt{\overline{I_{ar}^2}}$ .

It may also be argued that the effect of a positive voltage on the grid of a triode is to cause additional electrons to pass to the anode, and that the charge so reaching the anode will be dissipated partly through the external circuit and partly through the anode resistance  $R_a$  of the valve, as described from the shot noise example. This provides some physical basis for Fig. 4 and the concept that  $E_g$  primarily generates a *constant current*, but the presence of a finite  $R_a$  modifies the magnitude of net current flowing through the external circuit. This physical basis provides a case for the more frequent use of the circuit of Fig. 4.

**REFERENCES**

<sup>1</sup> K. R. Sturley, *Wireless World*, May, 1945, p. 140.  
<sup>2</sup> G. V. O. H., *Wireless Engineer*, June, 1945, Vol. 22, p. 261.  
<sup>3</sup> D. H. Parnum, *Wireless World*, July, 1945, p. 209.  
<sup>4</sup> E. B. Moullin and H. D. M. Ellis, *Journ. I.E.E.*, 1934, Vol. 74, p. 323.

# NOTES FROM THE INDUSTRY

## New Year Honours

Many names familiar in scientific and industrial circles are included in the New Year Honours list. SIR EDWARD APPLETON, K.C.B., D.Sc., Ll.D., F.R.S., Secretary, Department of Scientific and Industrial Research, is made K.B.E. SIR ROBERT RENWICK, Bart., lately Controller of Communications, Air Ministry, and Communications Equipment, M.A.P., is also made K.B.E. MR. P. DUNSHEATH, O.B.E., D.Sc., M.I.E.E., chief engineer and director, W. T. Henley's Telegraph Works Co.; MR. A. P. RYAN, of the B.B.C.; MR. C. O. STANLEY, O.B.E., managing director, Pye Limited, and MR. B. C. WESTALL, chairman and managing director of Thomas de la Rue, Ltd., all become C.B.E. DR. ROBERT COCKBURN and MR. J. A. RATCLIFFE, who superintended T.R.E., are made O.B.E., as are MR. E. HARLE, MR. K. C. SINCLAIR, MR. W. F. R. CAMPLING and DR. D. N. TRUSCOTT. MR. C. S. AGATE, of the Gramophone Co., MR. C. A. W. HARMER, of Pye Ltd., MR. J. W. RIDGEWAY, of the Edison Swan Electric Co., and MR. W. H. PETERS, of the G.E.C., Coventry, are also given the O.B.E.

## New Chairman of BREMA

The new executive council of the British Radio Manufacturers' Equipment Association have elected Mr. A. McVie, B.Sc.(Eng.), A.C.G.I., A.M.I.E.E., general manager and director of Kolster-Brandes, Ltd., as the Council's new chairman.

## Dubilier Laboratory Manager

Dubilier Condenser Co. (1925), Ltd., have appointed Wing Commander H. Andrewes, O.B.E., B.Sc., A.M.I.E.E. (late Chief Radar Officer Base Air Forces, South Asia Command), their laboratory manager. He has had a wide experience of radio, Radar, and electronic engineering and will be responsible for all research and development in connexion with the company's products.

## T.C.C.

Mr. C. T. Nuttall has joined the Telegraph Condenser Co., Ltd., as sales engineer. He was formerly component design engineer for the Gramophone Company, and in his new capacity will contact set manufacturers regarding the use of capacitors in radio and television receivers.

## Electronic Developments at B.T.-H.

The British Thomson-Houston Company's Report of Progress in 1945 contains an account of electronic developments in the company's laboratories at Rugby. Many electronic servo mechanisms have been produced for the accurate remote position control for searchlights, guns and Radar aerial systems. Instrument type remote position control servo mechanisms of a few watts output have also been produced during the past year, and induction and D.C. motors driven directly from the electronic circuits have been employed.

In the industrial field thyatron voltage regulators have been developed for controlling the voltage of high frequency alternators used for induction heating. No exciter is used, the whole of the excitation power being obtained from thyatrons. A feature of the control is the high speed of response of the voltage regulator.

An electronic time delay relay has been developed to provide an inexpensive short interval timer. The main features are infinitely variable adjustment over a wide range of the time delay period by knob control, and compactness and high accuracy.

## Met-Vick and Newton & Wright

An agreement has been concluded by which the Metropolitan-Vickers Electrical Co., Ltd., will acquire a substantial interest in Newton & Wright, Ltd., manufacturers of X-ray apparatus and optical equipment. Newton & Wright will remain a separate entity, but there will be the closest co-operation between the organisations of the two companies. The present directors of Newton & Wright will remain on the board; Mr. R. S. Wright is relinquishing his position as managing director, but retains that of chairman; Mr. H. A. Quinton becomes general manager.

## Liverpool University

Dr. J. M. Meek has been appointed to the David Jardine Chair of Electrical Engineering at Liverpool University. Dr. Meek graduated from Liverpool in 1934, and received the degree of Doctor of Engineering at the University in 1942. He was elected to the I.E.E. Council in July last, and will commence his new duties in July of this year.

## Standard Telecommunication Laboratories, Ltd.

Standard Telephones and Cables, Ltd., announce the formation of a central laboratory organisation to undertake long-term research and development in the telecommunication, electronics and allied fields. The new laboratories, to be known as Standard Telecommunication Laboratories, Ltd., will be housed at Progress Way, Gt. Cambridge Road, Enfield, pending the erection of suitable permanent premises. The principal objective will be the intensification of research and development in all aspects of telephony, telegraphy, electronics, cables, radio, television, etc.

## Muirhead and Co., Ltd.

Muirhead and Co., Ltd., have appointed Mr. W. C. Lister, B.Sc., chief sales engineer, to take charge of sales, publicity and customer technical services. Prior to joining Muirhead and Co. in 1930, Mr. Lister was at the G.P.O. Radio Research Station at Dollis Hill. For some years he has been Muirhead's chief development engineer and is, therefore, in a unique position to give technical advice to all users of the company's products.

Mr. P. Cannon, superintendent of the Instrument Making Department, retired at the end of last year after nearly fifty-four years' service.

Mr. J. Bell, M.Sc., M.I.E.E., is relinquishing his appointment with the Admiralty to join Muirhead and Co., Ltd., as chief research engineer on March 1 next.

## Gardners Radio, Ltd.

### Correction

We have been asked to make two corrections in the data which appeared in the Gardners Radio advertisement in our January issue. These are as follows: the price of the mains transformer type R.116 should be 52s. 6d., and the tappings of the R.125 should read: 0-4-6.3 volt 3 amp., 0-4-6.3 volt 4 amp.

## "Pylon" Hearing Aid

An unobtrusive hearing aid has been developed by Park Royal Scientific Instruments, Ltd. Containing a three-valve amplifier and crystal microphone, the complete unit, including batteries, weighs only 10 ounces and measures  $4\frac{1}{2}$  in. by  $3\frac{3}{4}$  in. by  $1\frac{1}{2}$  in.

### New Insulation Co., Ltd.

Mr. A. E. Judge, A.M.I.E.E., has joined the technical sales staff of the New Insulation Company and will be in charge of their London office at Windsor House, 46 Victoria Street, S.W.1.

### B.B.C. Television

The transmission of a still pattern from the London Television Station at Alexandra Palace will start on February 1. Transmissions will thereafter be made on weekdays from 11 a.m. to noon and from 4 p.m. to 5.30 p.m., and will consist of a tuning note and interval signal on the sound channel of 41.5 Mc/s. (7.23 metres) and a still pattern of a black cross on a white background on the vision channel of 45 Mc/s. (6.67 metres).

The choice of the still pattern which can be produced without the use of studio cameras and apparatus will allow the B.B.C. to continue the work of overhauling the studio vision apparatus at Alexandra Palace without interruption from the tests, and will at the same time provide a test signal which is most suitable for the use of the radio trade.

While these transmissions will be of no immediate interest to the general public, the B.B.C. is undertaking them in order to assist the radio trade in the production, testing and servicing of television receivers. The date of the opening of the public television service from Alexandra Palace will be announced later.

### B.I. Callender's Staff

British Insulated Callender's Cables, Ltd., announce the following staff appointments among others:—

Mr. P. V. Hunter, engineer-in-chief.

Mr. D. W. Aldridge, deputy engineer-in-chief and production manager.

Dr. L. G. Brazier, research manager.

Dr. J. L. Miller, chief engineer (equipment and telecommunications).

Mr. J. L. Harvey, general works manager.


Mr. H. J. Allcock, deputy production manager.

### Mr. S. H. Parsonage

Mr. S. H. Parsonage has resigned his appointment as manager at Compound Electro Metals, Ltd., but continues to act as adviser to the company. His new work concerns, among other items, the economic forms of electric heating. Address: 42 Pall Mall, London, S.W.1 (ARN. 6691).
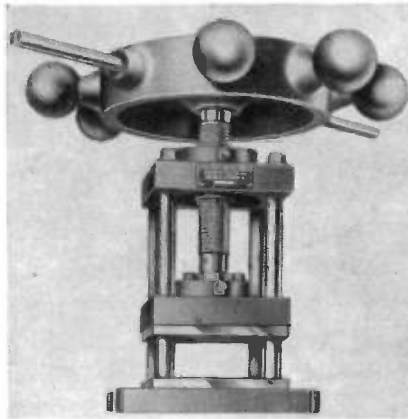
### The "Lab" Press

An experimental laboratory moulding press has been designed by the development department of Wright and Weaire, Limited, High Road, Tottenham, London, N.17. It is small, hand-operated and heated electrically. The manufacture of simple moulding tools, with or without provision for inserts, can be accomplished in very little more time than it takes to produce one or two model pieces in ebonite or other insulating material. Once made, the mould will give 50 or 100 pieces, and even more, according to the material used. Hard brass may be used for short runs or steel for more extended numbers.



### N.E. Coast Exhibition

An Exhibition of Scientific and Engineering Inspection Equipment will be held in Northumberland Road Drill Hall, Newcastle-on-Tyne, from February 12 to 22. Among the exhibits will be the electron microscope, appliances for measuring the thickness of metal coatings, hardness testing apparatus, the magnetic sorting bridge, X-ray industrial units, glass thickness viewers and strainometers. Magnetic, fluorescent and radio-frequency methods of crack detection will be demonstrated. The Exhibition will be opened at 3 p.m. on Tuesday, February 12, and thereafter will be open daily from 11 a.m. to 8 p.m.

### Marconi College

The Marconi Company's training establishment hitherto known as the Marconi School of Wireless Communication will, as from January 1, 1946, be known as Marconi College. Full postal address: Marconi's Wireless Telegraph Co., Ltd., Marconi College, Arbour Lane, Chelmsford, Essex. Tel.: Chelmsford 4401/2.

### Amateur Radio Transmission

Amateur radio transmission is now permitted again in this country. Transmitters are being returned to owners, and the Post Office are to commence the reissue of licences. Two wavebands have been allotted for amateurs' use, 28-29 megacycles and 58.5-60 megacycles.

### Mr. W. H. Stevens

Mr. W. H. Stevens, late of the research laboratories of A. C. Cossor, Ltd., has taken up a position with R.F. Equipment, Ltd., at Amersham, Bucks, where he will be responsible for the design of television receivers.

### Dubilier Agents

The Dubilier Condenser Co. have appointed the following agents in Great Britain:—

Manchester: L. Backhouse, 274 Deansgate.

Durham: A. J. Burke, Leadgate House, Leadgate.

Cardiff: A. E. Luen, 17 Dumfries Place.

Birmingham: A. J. Marc, 18 Newhall Hill.

Bournemouth: F. G. Lawrence, 393 Holdenhurst Road.

### Enemy Radio and Radar Exhibition

There is a possibility that members of the trade will have an opportunity of inspecting captured enemy radio and Radar equipment. The Ministry of Aircraft Production is hoping to secure a suitable hall for an exhibition of this equipment in the very near future. Admission will be restricted to representatives of interested industries, research and experimental staffs and students.

### Startling New Discovery?



Sir Robert Watson-Watt gave the 116th series of lectures for children at the Royal Institution during the Christmas holidays, his subject being "Wireless." The caption supplied with this agency photograph reads: "Sir Robert demonstrates magnetism with an ebonite rod and a piece of paper."

## FEBRUARY MEETINGS

**NOTE.**—In general, visitors are admitted to the meetings of scientific bodies on the invitation of a member, or on application in writing to the Organising Secretary at the address given. In certain cases (marked \*) tickets may also be obtained on application to the Editorial offices of this Journal.

### Institution of Electrical Engineers

All meetings of the London Section will be held at The Institution of Electrical Engineers, Savoy Place, Victoria Embankment, London, W.C.2.

#### Radio Section

Date: February 6. Time: 5.30 p.m.  
Lecture:

"Tendencies in the Design of the Communication Type of Receiver."

By:  
G. L. Grisdale, Ph.D., and R. B. Armstrong, B.Sc.

Date: February 20. Time: 5.30 p.m.  
Lecture:

"New Methods for Locating Cable Faults particularly on High Frequency Cables."

By:  
F. F. Roberts, B.Sc.(Eng.).

Date: February 26. Time: 5.30 p.m.  
Discussion on:

"Comparison of Electrostatic and Magnetic Deflection in Cathode-Ray Tubes."

Opened by:  
V. A. Stanley, B.Sc., and E. W. Bull, B.Sc.(Eng.).

*The Secretary:*  
*The Institution of Electrical Engineers, Savoy Place, Victoria Embankment, London, W.C.2.*

#### London Students' Section

Date: February 18. Time: 7 p.m.  
Lecture:

"The Measurement and Reduction of Noise."

By:  
Dr. A. J. King, M.Sc.(Tech.).

*Hon. Secretary:*  
*R. V. Darton, 27 Church Rise, Forest Hill, London, S.E.23.*

#### Cambridge Radio Group

Date: February 19. Time: 6 p.m.  
Held at:

The University Engineering Laboratory.

Lecture:  
"Some Principles of Ultra Short Wave Aerials."

By:  
Prof. E. B. Moullin, M.A., Sc.D.

*Group Secretary:*  
*D. H. Hughes, c/o Pye Ltd., Radio Works, Cambridge.*

### Institute of Physics

#### Electronics Group

Date: February 20. Time: 5.30 p.m.  
Held at:

The Royal Institution, 21 Albemarle Street, London, W.1.

Discussion:  
"Permanence of Components in Electronic Equipment."

Opened by:  
Dr. W. B. Lewis.

*Group Secretary:*  
*A. J. Maddock, M.Sc., F.Inst.P., Messrs. Standard Telephones and Cables, Ltd., Oakleigh Road, London, N.11.*

#### Manchester and District Branch

Date: February 15. Time: 7 p.m.  
Held at:

Large Physics Theatre, Manchester University.

Lecture:  
"Vision at Low Intensities of Illumination."

By:  
W. S. Stiles, D.Sc.

*Hon. Secretary:*  
*Dr. F. A. Vick, O.B.E., F.Inst.P., Physics Dept., The University, Manchester, 13.*

### Institution of Electronics

#### London Section

Date: February 11. Time: 5.30 p.m.  
Held at:

The Royal Society of Arts, John Adam Street, London, W.C.2.

Lecture:  
"Glass for Electron Tubes."

By:  
Dr. J. H. Partridge.

*Tickets may be obtained from*  
*64 Winifred Road, Coulsdon, Surrey.*

### The Association for Scientific Photography\*

Date: February 22. Time: 6.30 p.m.  
Held at:

The Royal Society of Arts, John Adam Street, London, W.C.2.

Lecture:  
"The Photographic Copying of Documents and Plans."

By:  
F. J. Tritton, B.Sc., F.R.P.S.

*The Secretary:* *A.S.P., 34 Twyford Avenue, Fortis Green, London, N.2.*

### R.S.G.B.

All meetings are held at the Institution of Electrical Engineers, Savoy Place, London, W.C.2.

Date: February 15. Time: 6.30 p.m.  
Lecture:

"The Amateur Bands: Past, Present and Future."

By:  
Arthur O. Milne.

*The General Secretary, R.S.G.B., New Ruskin House, Little Russell Street, London, W.C.1.*

### British Kinematograph Society

Meetings held at the Gaumont British Theatre, Film House, War-dour Street, London, W.1.

Date: February 13. Time: 6 p.m.  
Lecture:

"Current Processes of Colour Kinematography."

By:  
J. Coote, F.R.P.S.

*Secretary:*  
*R. H. Cricks, Dean House, Dean Street, W.1.*

### Brit.I.R.E.

#### North-Eastern Section

Date: February 13. Time: 6 p.m.  
Held at:

The Mining Institute, Neville Hall, Westgate Road, Newcastle.

Lecture:  
"Reproduction from Sound on Film."

By:  
G. Dobson.

*Section Secretary:*  
*H. Armstrong, 69 Osborne Road, Jesmond, Newcastle-on-Tyne.*

### Royal Photographic Society of Great Britain

Date: February 15. Time: 6 p.m.  
Held at:

16 Princes Gate, London, S.W.7.



Lecture:  
"Colour Television."

By:  
L. C. Jesty.

*The Secretary:*  
*Scientific and Technical Group, Research Laboratories, Kodak, Ltd., Harrow, Middlesex.*
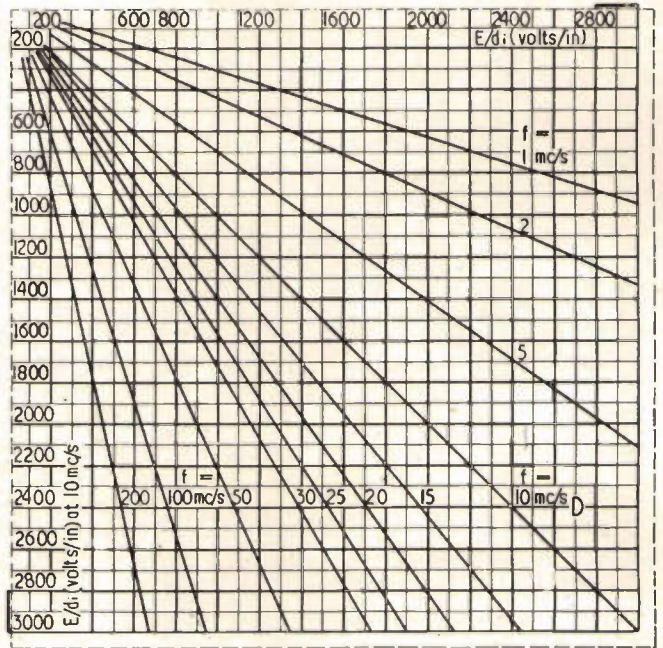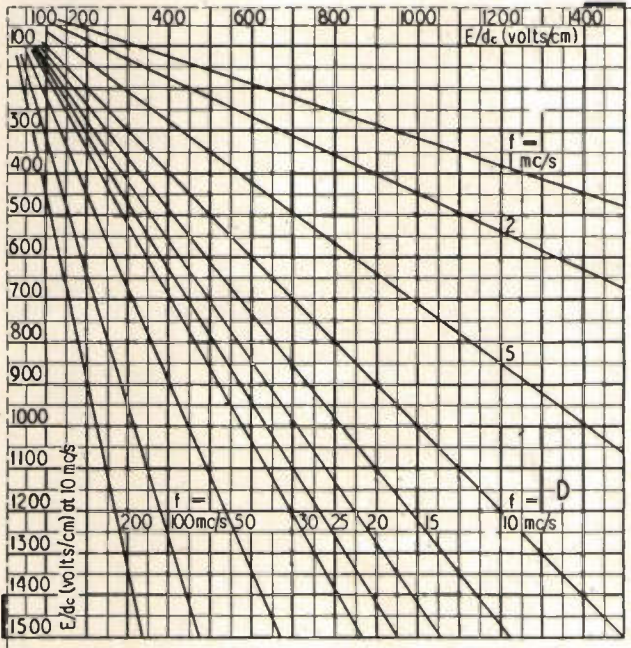
## DIELECTRIC HEATING DESIGN CHART : A CORRECTION

On pages 638 and 639 of the August, 1945, issue appear two Design Charts for Dielectric Heating. It is regretted that an error occurs in the lower right-hand quadrants of each chart, and the corrected curves are reproduced below. Readers are asked to cut out these corrected curves at the dotted lines shown, and superimpose them on the existing curves. Good gum should be used to avoid paper shrinkage.




# SUNVIC CONTROL is as simple as THAT!

The SUNVIC Energy Regulator gives continuously variable control by periodically breaking the heating circuit, with provision for adjustment of the on/off cycle time. For A.C. loads up to 1 Kw. the Energy Regulator has only to be wired up to the heater and power supply. For D.C. and for A.C. loads up to 6 Kw., a SUNVIC Hotwire Vacuum Switch Unit must also be connected, as shown above.

The Energy Regulator will control any load up to its rated capacity without resistance losses. It compensates for line voltage fluctuation and keeps power input constant. As shown, you can instal the Energy Regulator so very easily, too. May we send you detailed technical publication R 12/16 ?



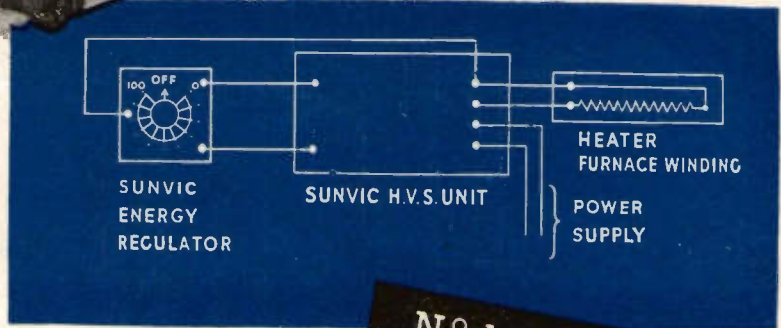SUNVIC CONTROLS LIMITED,  
Stanhope House, Kean Street, London, W.C.2.



**No 1** CONTINUOUSLY  
VARIABLE CONTROL FOR  
ELECTRIC HEATERS, HOT  
PLATES, MUFFLES, ETC.



**STATIC TWO-DIMENSIONAL** visual delineation of any recurrent law.

**RELATIVE TIMING OF EVENTS** and other comparative measurements with extreme accuracy.

**PHOTOGRAPHIC RECORDING** of transient phenomena.

**SIMULTANEOUS INDICATION** of two variables on a common time axis

INDUSTRIAL INDICATING and TESTING afford increasing scope for the Cathode Ray Tube as the only device with the above inherent features, of which the last is unique in the Cossor DOUBLE BEAM Tube.

The Model 339 Cossor Oscillograph thus equipped is invaluable on all problems of research, production or operational testing, when the effect examined is applied as a voltage. When recurrent the traces are studied visually and when transient are recorded photographically, using Model 427 camera.



**A. C. COSSOR Ltd.,**

INSTRUMENT DEPT.

Cossor House, Highbury Grove, London, N.5

\*Phone: CANonbury 1234 (33 lines).

\*Grams: Amplifiers Phone London.

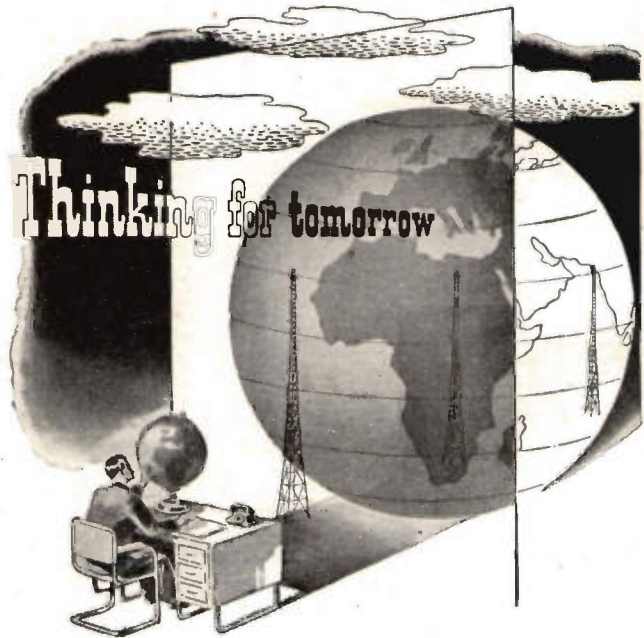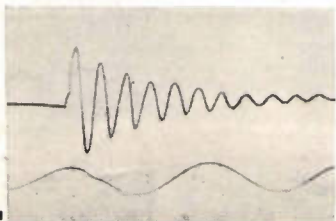

In a world whose tempo is governed by the radio wave, it is necessary to think quickly and to think ahead. Marconi engineers have an advantage in this—the advantage of a technical background that takes in the whole history of wireless communications.

In the reconstitution of old services and the development of new ones, that experience will be vital. On land, on sea and in the air, in the future as in the past, communications will be linked with Marconi—the greatest name in wireless.

**MARCONI**

*the greatest name in wireless*

MARCONI'S WIRELESS TELEGRAPH COMPANY LTD  
THE MARCONI INTERNATIONAL MARINE COMMUNICATION COMPANY LTD  
ELECTRA HOUSE, VICTORIA EMBANKMENT, LONDON, W.C.2




## Frequency Stabilisation of Resonators Influenced by Electron Discharge

*Communication from E.M.I. Laboratories*

IN the generation and amplification of electrical oscillations of ultra-high-frequency it is common to-day to employ resonator devices through which there is arranged to pass an electron beam. The function of the resonator may be, in ways now well known, to modulate the velocity of the beam or to extract energy from a beam which has already been appropriately modulated, for example, by being modulated in velocity and then being allowed to traverse a drift space. In some instances it is desired to vary the average beam current, and when this is so an effect arises that is often inconvenient. The effect is that with the change in mean beam current passing through the resonator the natural frequency of oscillation of the resonator also suffers a change. Thus, if the resonator constitutes the frequency determining circuit of an oscillation generator, the frequency of the generated oscillations is apt to undergo variation as it is attempted to modulate them in amplitude by modulating the mean current of the beam. Or if the resonator is used in an amplifying arrangement and the gain of the amplifier is adjusted by adjusting the beam current, the amplifier may become detuned.

There are several methods, all applications of a common principle, by which difficulties of this kind may be surmounted. The general principle is to utilise a second electron discharge which also influences the resonator and to vary the intensity of the second discharge simultaneously with variation of the first so that the effect of modifying the second opposes the effect of modifying the first. A second electron beam may thus be employed having the essential function of neutralising the undesired changes occurring in association with the first. In general, it may be said, it should have only this function, since if it were employed also for generating oscillations, for example, this secondary function might have a disturbing effect upon the operation of the first beam.

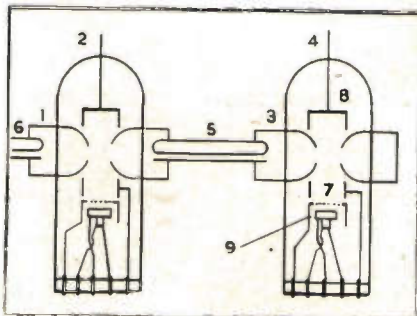The figure shows one application. The tube 2 is a klystron tube of reflexion type for generating ultra-



high-frequency oscillations. The resonator 1 both modulates the velocity of the beam that passes through it and also, after the beam is returned back toward the cathode by a reflector electrode, extracts energy from it and so is maintained in a state of sustained oscillation. The line 6 coupling with the resonator 1 affords an output. The tube 4 is a tube similar to tube 2 but is not arranged to generate oscillations. Its resonator 3 is coupled with the resonator 1 of tube 2 by the coupling line 5, and depending upon the length of this line the beam current of tube 4 is controlled in intensity relative to the control of beam intensity in tube 2, so that the frequency of oscillations set up in the resonator of tube 2 remains constant, or nearly so, as their amplitude is modulated by modulating the beam current in tube 2 by the control grid provided for that purpose. The tube 4 is prevented from itself generating oscillations by applying an appropriate potential to its electrode 8 relative to the potential of its cathode 9. The potential on electrode 8 may be positive with respect to cathode 9, but it may also be negative provided oscillations are not set up in resonator 3, since such oscillations would affect the output from resonator 1. If the line 5 is correctly chosen in length the beam currents of the two tubes may be modulated in antiphase.

It will be clear that instead of employing two tubes and two resonators, but one tube may be employed with a single resonator, this resonator, however, being arranged to have pass through it two electron beams. Instead also of utilising an auxiliary electron beam a controllable gaseous discharge may be used.

## Motor at High Temperature in High Vacuum

During the war Westinghouse motor engineers were asked to build special direct-current armatures that could operate continuously in a temperature of 600° F., and in high vacuum of a few microns pressure. Furthermore, the armatures must give off no gases to contaminate the vacuum system. To add to the rigours of the problem, the armatures had to turn at 1,200 r.p.m. without noticeable vibration and without the addition of any balance weights.

The armatures were wound with glass- and silicone-insulated wire, the coils being wound on both sides of the shaft to maintain weight symmetry. After winding, the armatures were placed in an oven at about 500° F. to burn out any organic material and to drive out all other volatile matter. The entire armature was then subjected for hours to a filling of sodium silicate and mica dust under alternate vacuum and pressure. This was followed by another bake and removal of surplus impregnant.

—*Westinghouse News Service  
Pittsburg.*

## New R.C.A. Beam Power Valve

RCA-2E24 is the designation of a new, quick-heating, transmitting, beam power amplifier designed for mobile and emergency-communications equipment.

Requiring relatively low plate voltage, the 2E24 has a maximum plate input of 30 watts (CCS) or 40 watts (ICAS) in class C telegraph service. In such service, it can deliver 20 watts (CCS) at a plate voltage as low as 400 volts, or 27 watts (ICAS) at 600 volts, with a driving power at the tube of only 0.2 watt.

The 2E24 can be operated at maximum ratings to 125 megacycles and at reduced plate voltage and input to 175 megacycles.

The filament is of the coated type and requires only 0.65 ampere at 6.3 volts.

## BOOK REVIEWS

### Television To-day and To-morrow

Lee de Forest. (Hutchinson's Scientific and Technical Publications, 1945, 16s. net.) 176 pp., 76 figs.

One is often asked at the present time to recommend a book on Television. The book under review, as its name implies, is not a text book, but contains sufficient technical information for a radio man or an intelligent amateur to follow. To the many men and women now leaving the Services with a good grounding in the principles of radio and Radar the book should prove extremely helpful by giving them a correct perspective of the way the things they have learnt fit together into the layout of Television as a whole.

One must remember that Lee de Forest is an American and a very important worker in the radio industry whose opinions are very worthy of consideration. While some of the views he expresses are particularly applicable to Television in the United States, in general his outlook is international. On the technical side the book contains a very fair treatment of the stages of development in which the important steps in both Europe and America are placed in chronological order.

Intermingled with the technical matter of the book in an unorthodox but interesting manner are many notes on the financial, artistic, and other viewpoints on the new Television industry. The chapter on "Suppose Television is your Job" brings to one's notice the fact that the electronic engineers will eventually become a minority in an organised television service. This is a point not generally realised while we are in the development stages of the art, but is obvious when we consider the demands of the programme side of a public service. In fact, the author prophesies that the new industry has the capacity to employ in America more people than any others which have flourished since the railroads were built.

The whole book is infused with a tremendous rising tempo of enthusiasm which it would do well for those in authority in this country to read if

they could be persuaded to spare the time.

The Editor points out that the American text of the book has been Anglicised as much as has seemed necessary to ensure understanding by the English readers.

The only criticisms one can raise here are that the inclusion of photographs of the equipment described would have enhanced the set up of the book, and secondly, the price is high for the class of reader for which it is intended, bearing in mind that this is not a text book.

T. M. C. LANCE.

### "Electrical Engineer" Reference Book

Edited by E. Molloy, assisted by M. G. Say, R. C. Walker, and G. Windred. (Geo. Newnes, Ltd., 42s. net.)

This book is one of the most comprehensive summaries of electrical engineering yet published in this country. It also has the qualification of being thoroughly up to date, each section having been specially written by one or more engineers closely connected with the particular subjects dealt with. In view of prevailing conditions and the fact that the book contains nearly 1,600 pages of actual descriptive matter the price may be considered very reasonable. There are 32 sections, covering the whole of electrical engineering, with the exception of radio and communications generally, but the subject of electronics is well represented both in a special section and incidentally in various places throughout the text.

The first section, on Theory and Calculations, is a prominent feature of the book. It occupies 102 pages, and forms in itself a useful compendium of those basic facts on which the practising engineer so often needs to refresh his memory and almost

equally often fails to find in his books of reference. The treatment here is clear, brief and accurate; in fact, a model of exposition for reference purposes.

Subsequent sections deal with the various branches of power supply, distribution and utilisation, omitting very little and giving on the whole quite adequate treatment to the multitude of subjects. Although a certain amount of overlapping is hardly to be avoided in a work of this kind, the reader may notice this defect rather frequently. Thus the principles of the cathode-ray tube are dealt with in two different sections and types of construction described in at least two other places. Valve voltmeter circuits are given in two different places and the different types of photocells are also described twice, as also are electron lenses; once in connexion with electron optics and again in describing the electron microscope—two subjects which should, of course, have been treated together.

In view of the fact that communications and television are excluded from the book it is rather disconcerting to find descriptions of five types of electron cameras in the section on Electronics. The omission of any treatment of amplifiers or oscillators, apart from a mention of the magnetron, in this section is a serious lapse which calls for attention in future editions.

A feature of the book which will be useful to many engineers is the section on Electrical Literature, representing a bibliography subdivided according to the various sections and giving under each heading a list of books, articles and British Standard Specifications. There is also a section on Progress containing illustrations and descriptions of modern industrial apparatus. Other non-technical sections are on Education for the Electrical Industry and Electricity Rules and Regulations, including the principal points of Home Office and Supply Regulations and Points of Law.

The professional electrical engineer will find this book an indispensable source of reference and information, and it should certainly be available in all works libraries.

**Books reviewed in this  
Journal can be obtained  
from**

**H. K. LEWIS & Co. Ltd.**  
136 Gower Street, W.C.1

*If not in stock, they will be obtained  
from the Publishers when available*

## CORRESPONDENCE

### Phys. Soc. Exhibition

DEAR SIR,—I hope your columns are available to protest at the quite inadequate arrangements made to meet the wide interest aroused by the recent exhibition of the Physical Society. This exhibition is of very great interest to all who are concerned with scientific or engineering matters, but it extends even beyond that because it could have considerable commercial value.

The latter part of this statement may cause some of the exhibition's more academic promoters to raise their eyebrows in horror, but I feel convinced that some reflexion would satisfy them that it is to the considerable advantage of the more abstract aspects of physics that it should be based upon solid commercial foundations.

The exhibition held at South Kensington at the beginning of January was laid out in an extraordinarily unsatisfactory manner; it was widely scattered about a large building although the amount of space was inadequate even had the attendance been a tenth of what it was. In such circumstances it was impossible for any individual to see and absorb more than a small fraction of the intensely interesting exhibits collected there.

Surely the promoters of this exhibition could find means for improvement. It might be that keeping the exhibition open for considerably longer would be sufficient, but it might be desirable to consider charging for admission on one or more days. This would make provision for the less crowded attendance of trade visitors and those having some real and direct interest in the exhibits and, at the same time, it might provide sufficient funds to permit the exhibition to be housed in premises more suitable for its purpose.—Yours faithfully,

J. R. HUGHES.

### Phase Splitter

DEAR SIR,—Your reference chart\* "Methods of Driving Push-Pull Amplifiers" was of particular interest to me because of the circuit depicted in Fig. 4 of a form of the differential phase splitter. This form of


splitter has been used in a simple amplifier which I designed early last year (*R.S.G.B. Bulletin*, March, 1945), and I would point out the greater convenience of using a double-triode for phase splitting, rather than trying to do it in the output stage itself.

An additional A.F. stage is required in any case to drive the output valves fully; consequently the cost of the double-triode and its associated components is outweighed by the saving in the lower H.T. required, and in the simpler smoothing required, since the double-triode is working effectively in push-pull, and needs no decoupling.

The resulting balance of this circuit is very good, and frequency distortion is very low, due to a form of current feed-back inherent in the action of the circuit.

A valuable and interesting property of this circuit is that of being able to reject in-phase signals on the principle used in biological amplifiers (due to Offner).

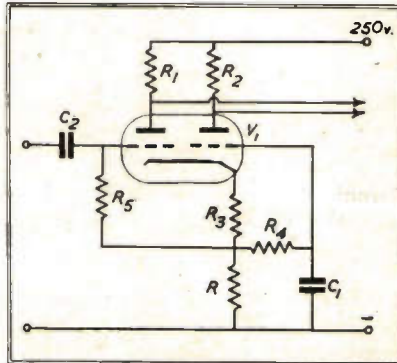As will be seen, this property ensures that phase inversion is complete, and the two driven valves are presented with a push-pull signal automatically balanced.



#### Component Values

V1	...	6N7G, 6C8G, ECC31, etc.	C1	...	0.01 mF		
R1, 2	...	68K	↓	W	C2	...	0.1 mF
R3	...	1K	↓	W			
R4, 5	...	0.75m	↓	W			
"R"	...	10K	↓	W			

A simple circuit of a driving stage is shown; it may be noted that the value of "R" is not critical.

As will be seen, this circuit is very simple, and easy to apply to all types of amplifiers, and gives a gain equal to a normal medium mu triode.—Yours faithfully,

L. A. SAUNDERS.

## PORTABLE FREQUENCY STANDARDS

Two new Furzehill products, for laboratory and test room, for checking the calibration of receivers, oscillators, signal generators, etc., synchronising C.R.O. time bases and similar operations at audio or radio frequencies.

**Type 1703**—Battery operated covering frequencies from 10 kc/s. to 80 Mc/s.

● Immediate delivery.

● **PRICE £25.**

**Type 1744**—Mains operated, covering frequencies from 1 kc/s. to 80 Mc/s. with low-impedance output.

● Available shortly.

Write for detailed particulars :

  
**FURZEHILL**  
**LABORATORIES LTD.**  
**BOREHAM WOOD**  
 HERTS

TELEPHONE ELSTREE 1137

# ABSTRACTS OF ELECTRONIC LITERATURE

## CIRCUITS

### Cathode-Coupled Wide-Band Amplifiers (G. C. Sziklai and A. C. Schroeder)

A general analysis indicates that, in wide-band amplifiers, stable operation is possible with triodes in circuits using the cathode as a signal terminal. The amplification, however, is approximately equal only to the square root of that available with grounded-cathode amplifier, and therefore twice as many tube units are required to obtain the same amplification. In certain applications, however, the utility of such circuits outweighs the loss of gain.

A simple radio-frequency amplifier was designed for television receivers, using a cathode-input circuit. By combining a cathode-output and a cathode-input stage using one single twin-triode tube, a circuit was devised which compares favourably with pentode stages with respect to gain, stability and economy, while it has far superior noise characteristics. The new circuit, called the "cathode-coupled twin-triode" amplifier, provides greater flexibility than conventional amplifier circuits, and can be used for radio-frequency, intermediate-frequency, video, converter, or detector services. Since the same tube type can also be used for synchronising and deflection circuits, the number of tube types can be materially reduced, and greater standardisation with further economical advantages may be obtained. An interesting application of the new circuit is a novel bidirectional amplifier.

—*Proc. I.R.E.*, October, 1945.

### Band-Pass Bridged-T Network for Television Intermediate-Frequency Amplifiers

(G. C. Sziklai and A. C. Schroeder)

Bridged-T networks offer great economy in television intermediate-frequency amplifiers for sharp attenuation of the associated and adjacent sound channels. A simple design method was obtained by the use of the equivalent lattice. By the same method, general formulae were obtained for the phase, attenuation and delay characteristics. Two designs are given to illustrate the convenience of the method.

—*Proc. I.R.E.*, October, 1945.

## MEASUREMENT

### A Method of Measuring the Radio-Frequency Resistance of Wires

(C. Stewart)

A new and relatively simple method of measuring the resistance of wires at frequencies between 200 kc/s. and 40 Mc/s. is described. By this method, the test specimen is strung down the centre of a metal pipe about ten to a hundred feet in length, depending upon the test frequency, to form a transmission line. One end of the line is short-circuited and the other connected to a standard commercial Q-meter. Readings are taken from the Q-meter and applied to curves to obtain the desired resistance. This method of measurement appears to be more reliable than the use of coils, and the results agree closely with calculation by skin-effect formulae.

—*Jour. App. Phys.*, Oct., 1945, p. 608.\*

### The Photoconductivity of Zinc-Cadmium Sulphide as Measured with the Cathode-Ray Oscillograph

(A. E. Hardy)

A new method for the measurement of photoconductivity, involving the cathode-ray oscillograph as a recording instrument, is described. Several interesting aspects of photoconductivity of phosphors, including the quenching effect of red light, are discussed. New evidence in support of the "trapping centre" or metastable-state theory in regard to phosphorescence is presented.

—*Trans. Electrochemical Soc.*, vol. 87 (1945).\*

## TELEVISION

### Problems of Theatre Television Projection Equipment

(A. H. Rosenthal)

Some of the more important problems of theatre television projection technique and equipment are discussed. The importance of the two principles of optical storage and light modulation for overcoming certain limitations is stressed, and some scopphony developments are described in which these principles are utilised.

—*Jour. Soc. Mot. Pic. Eng.*, Sept. 1945, p. 218.

### Capacitors for High-Frequency Induction Heating Circuits

(F. M. Clark and M. E. Scoville)

This paper describes the development of a new type of dielectric liquid called Lectronol. Capacitors containing this liquid are particularly well adapted for use in the tank circuit of electronic heaters used in induction heating. The capacitor is noteworthy because of the absence of cellulose sheet insulation, satisfactory operation being entirely dependent on the superior insulating properties of the Lectronol. Capacitors containing this liquid are characterised by low dielectric loss and high dielectric strength over the frequency range utilised in power oscillators. The capacity per unit volume is approximately twice that obtained with mineral oil. The electrical characteristics of the capacitor are stable under severe conditions of use.

—*Trans. A.I.E.E.*, November, 1945, p. 791.\*

### The Role of Frequency in Industrial Dielectric Heating

(G. W. Scott)

An analysis of the effects of frequency in industrial dielectric heating is given and the expression for the rate of heating is examined in an attempt to determine the practical upper limit of frequency for large-scale industrial heating installations. Graphs are given showing the variation of loss factor with frequency, the maximum tolerable electrode length as a function of frequency and the variation of tuning inductances with frequency for loads of specified capacitance. The advantages of employing high frequencies are pointed out and reference is made to the efficiency of various heating installations.

—*Trans. A.I.E.E.*, Aug., 1945, p. 558.\*

### Electronics Applied to Instrumentation


(H. D. Middel)

This article deals with the contribution of electronics to industrial measurements and control. Recent applications dealt with include measurement of hydrogen-ion concentration, recording spectrophotometers, torque amplifiers, gas analysis and pressure, flow and temperature measurement. Various methods of measurement are described with the aid of circuit diagrams, and their applications outlined.

—*Instruments*, March, 1945, p. 144.\*

\* Abstracts supplied by the courtesy of Metropolitan Vickers Electrical Co. Ltd., Trafford Park, Manchester

# ACCURACY

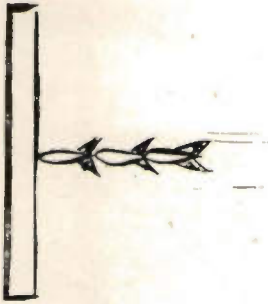

We doubt whether the champ could repeat this feat at will, but you can always rely upon undeviating accuracy in every batch of insulating components machined or moulded from MYCALEX.

Power Factor (at 1 mc/sec. and over).002	Tensile Strength 5,800 (lbs./sq. in.)
Permittivity .... 6.7	Water Absorption .... NIL
Di-Electric Strength (volts/mil) .... 550	Plastic Yield .... 450° C




'Phone : Cirencester 400 or send enquiries to

**MYCALEX COMPANY LIMITED, ASHCROFT ROAD, CIRENCESTER, GLOS.**

MY14

## EQUIPPING A LABORATORY?

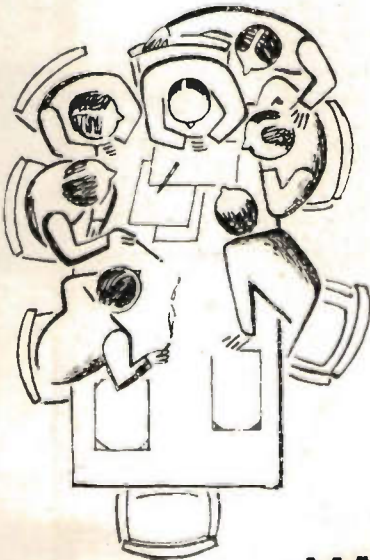

*Let's get our heads together*

Time and time again experience has shown that a considerable saving of time and money could have been made if Marconi Instruments had been called in at the very earliest stages of equipping or re-equipping a scientific laboratory. All too often it is found that vital instruments have to be installed almost as an afterthought when it is too late to site them in the most logical and convenient place. All too often it is found after several measuring instruments have been installed that a single piece of Marconi apparatus could have done the work of them all.

Consult Marconi Instruments from the start—it costs nothing and may save a great deal of time and money.

**MARCONI INSTRUMENTS LTD.**




*The*

# TAYLOR A.C. BRIDGE

## MODEL 110A

These instruments give quick and accurate measurements of Capacity and Resistance. There are six Capacity ranges covering from .00001 to 120 mfd. and the Power factor can also be measured on each range. Six Resistance ranges are available measuring from 1 ohm to 12 megohms. This bridge is A.C. mains operated and a leakage test is also available for detecting leaky paper or mica condensers. Price £14 14s. 0d.

Please write for technical leaflet.

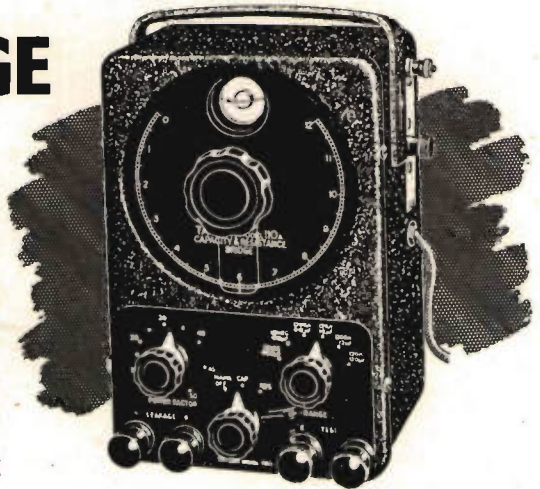

### 6 RANGES OF CAPACITY RANGES OF RESISTANCE

# Taylor

electrical instruments Ltd

Send your enquiries to:—

## TAYLOR ELECTRICAL INSTRUMENTS LTD

419-424 MONTROSE AVE., SLOUGH, BUCKS.  
Tel: Slough 2081 (4 lines) Grams: "Taylins", Slough.

★ SUPREME FOR RADIO COMMUNICATIONS

## TELCON CABLES

with  
**TELCOTHENE**  
INSULATION

This new material produced by TELCON is the latest development in low loss thermoplastic Insulants. A complete range of "TELCOTHENE" insulated cables is now available for use in the Audio, Radio and Ultra High Frequency fields.

Send for H.F. brochure.

TELCON Designed H.F. Cables are the Basis of World Standards.



THE TELEGRAPH CONSTRUCTION & MAINTENANCE CO. LTD.  
Founded 1864  
Head Office: 22 OLD BROAD ST., LONDON, E.C.2. Tel: LONdon Well 3141  
Enquiries to TELCON WORKS, GREENWICH, S.E.10. Tel: Greenwich 1040

## BRAY CERAMIC INSULATORS

for L.F. and H.F. Components; also capacitor dielectrics



made by  
**GEO. BRAY & CO., LTD. LEEDS, 2**  
Established 1863 Phone Leeds 20981

## Dainite MOULDED RUBBER PARTS

The Dainite Service, with 50 years' experience of compounds and mouldings and an up-to-date plant, will quote for your particular requirements in Moulded Rubbers.



THE HARBOROUGH RUBBER CO., LTD.,  
MARKET HARBOROUGH, ENGLAND



**Made in Three Principal Materials**

**FREQUELEX**

An insulating material of Low Dielectric Loss, for Coil Formers, Aerial Insulators, Valve Holders, etc.

**PERMALEX**

A High Permittivity Material. For the construction of Condensers of the smallest possible dimensions.

**TEMPLEX**

A Condenser material of medium permittivity. For the construction of Condensers having a constant capacity at all temperatures.

**Bullers**



**BULLERS LOW LOSS CERAMICS**

BULLERS LTD., 6, LAURENCE POUNTNEY HILL, LONDON, E.C.4  
 Telephone: Mansion House 9971 (3 lines)    Telegrams: "Bullers, Cannon, London"    Manchester Office: 196, Deansgate, Manchester

## CLASSIFIED ANNOUNCEMENTS

The charge on miscellaneous advertisements on this page is 12 words or less, 4/- and 4d. for every additional word. Box numbers count as four words, plus 1/- extra for replies. Remittance should accompany advertisement. Cheques and P.O.'s payable to Hulton Press, Ltd., 43 Shoe Lane, E.C.4. Replies to box numbers should be addressed as above, marked "Elec. Engg." Press date: 15th of month for following issue.

Vacancies advertised in these columns do not relate to men between the ages of 18 and 50 inclusive, or women between the ages of 18 and 40 inclusive, unless they are exempted from the provisions of the Control of Engagements Order, 1945, or the vacancies are for employment excepted from the provisions of that order.

### FOR SALE

**IN STOCK.** Rectifiers, Accumulator Chargers, Rotary Converters, P.A. Amplifiers, Mikes, Mains Transformers, Speakers of most types, Test Meters, etc., Special Transformers quoted for.—University Radio, Ltd., 22, Lisle Street, London, W.C.2. GER. 4447.

### LOUDSPEAKERS

**LOUDSPEAKERS**—We carry on. Sinclair Speakers, 12, Pembroke Street, N.1.

**LOUDSPEAKER** repairs, British, American, any make, moderate prices.—Sinclair Speakers, 12, Pembroke Street, N.1.

### MISCELLANEOUS

**WE WILL BUY** at your price used radios, amplifiers, converters, test meters, motors, pick-ups, speakers, etc., radio and electrical accessories. Write, phone or call, University Radio, Ltd., 22, Lisle Street, London, W.C.2. GER. 4447.

**WEBB'S** Radio Map of the World enables you to locate any station heard. Size 40 in. by 30 in. 2-colour heavy Art Paper, 4/6, post 6d. Limited supply on Linen, 10/6, post 6d.—Webb's Radio, 14, Soho Street, London, W.1. 'Phone: GERrard 2089.

**MORSE** Practice Equipment for Classroom or Individual Tuition. Keys, Audio Oscillators for both battery or main operation. Webb's Radio, 14, Soho Street, London, W.1. 'Phone: GERrard 2089.

**MECHANICAL ENGINEERS** to the Electronic Industry. Precision and Optical Instruments of all types designed and constructed in collaboration with Electronic Engineers. Tecnaphot Ltd., Mile Lane, Coventry.

**CATALOGUE PHOTOGRAPHY** by new process. Behr, 44, Temple Fortune Lane, London, N.W.11. SPeedwell 4298.

**AMATEUR RADIO PRODUCTS**, 50 Glasslyn Road, Crouch End, N.8. Designers and Manufacturers of short-wave radio components and equipment, both for transmitters and receivers. Enquiries invited. Phone: MOUnview 4745.

**"COALS TO NEWCASTLE."**—Our Service on components is now so well known that we are even receiving orders from America.

Our regular customers include many industrial organisations of world-wide repute, who find that for the development of urgently required prototypes, they can get better service and quicker delivery from us—often on components unobtainable elsewhere.

Our suppliers include famous names such as Avo, Pullin and Weston instruments and test equipment; Bulgin, Belling & Lee and Clix components; Buller's ceramics; B. & I., Dubilier, T.C.C. and T.M.C. condensers; Cydon transmitting condensers; Dubilier and Erie resistors; Dubilier and Morganite carbon potentiometers; Colvern wire-wound potentiometers; Cossor, G.E.C. and Mullard cathode-ray tubes; Cossor and Mullard oscilloscopes; Denco Maxi-Q coils and polystyrene products; G.E.C. photo-cells and amplifiers; Muirhead precision drives and dials; Partridge transformers and chokes; Q.C.C. crystals; S.T.C. transmitting valves; S.T.C. and Westinghouse rectifiers; Welwyn precision resistors, etc., etc. Send 2/6 stamp for List. TELE-RADIO (1943), LTD., 177, Edgware Road, London, W.2. Telephone: PADDington 6116.

**VALVES!** 6BG, 6B8G, 6Q7G, 6V6G, 6F6G, 6K7G, 6X5G, 6A7, 5Y3G, 6AC7, 25Y5, 80, 77, 78, 807, 813, EA50, 866A, PEN36C, X42, U04, AC/P2, PENA4, PM11F, 1A5GT, 1Q5GT, L2, or equivalents, at list prices.—M.O.S., BCM Electronic, London, W.C.1.

**1946 AMPLIFIERS.**—De Witt 20-watt high-fidelity model, complete with all valves, ready to use, £7 19s. 6d. Comprises high-mu input stage, twin 6L6 output tetrodes, heavy-duty speaker transformer for 2.5 and 15 ohms, massive A.C. power pack, grey enamelled chassis with volume control, input and output sockets. Carriage extra.—Sole distributors, Kossuth Radio Co., 410, Dudley Road, Edgbaston, Birmingham.

**THERMIONIC VALVES** and discharge tubes. We are now prepared to develop and/or manufacture vacuum or gas-filled devices, special radio valves and cathode-ray tubes to your requirements.—Box 800, "Elec. Engg."

**WE ARE NOW** able to undertake the adjustment of resistors and capacitors over a wide range to within 0.1%. Customers' own apparatus, including audio oscillators and wavemeters, carefully calibrated to any required degree of accuracy. We can supply special precision radio and mechanical components from the small gear or coil to the complete apparatus for the solution of unusual problems. Lydiat Ash Laboratories, Nr. Bromsgrove, Worcs.

**BERRY'S (SHORT WAVE) LTD.** The House for Quality Radio and Electronic products. Send for our 1946 Catalogue; 3d post paid, 25, High Holborn, London, W.C.1.

### SITUATIONS VACANT

**A.M.I.E.E., City and Guilds**, etc., on "NO PASS—NO FEE" terms. Over 95 per cent. Successes. For full details of modern courses in all branches of Electrical Technology send for our 112-page handbook—FREE and post free. B.I.E.T. (Dept. 337B), 17, Stratford Place, London, W.1.

**OPPORTUNITY** for laboratory assistant with knowledge of industrial electronics equipment, power oscillators and central circuits. Must be practical. Write, stating qualifications, age and salary required.—Box 797, "Elec. Engg."

**OPPORTUNITY** for draughtsman with knowledge of radio factory drawing office practice. Write, stating qualifications, age, and salary required.—Box 798, "Elec. Engg."

**DRAUGHTSMEN** and engineers with radio-frequency experience required in the Warrington area for instrument design work.—Replies to G.P.O. Box 20, Warrington, to be marked, "Elec. Engg."

**ELECTRICAL and Mechanical Engineer** for varied and interesting duties in small works. Competence and initiative essential. Knowledge of electronics desirable. Good pay to live man under 40, full or part time.—Box No. 466, c/o Dawsons, 31, Craven Street, London, W.C.2.

**HIVAC, LTD.**, invite applications from young Radio Valve Technicians with experience in all branches of receiving valve production. The post offered will be a staff appointment and will ultimately be pensionable. Write to: The Manager, Hivac, Ltd., Greenhill Crescent, Harrow-on-the-Hill, Middlesex.

**HIVAC, LTD.**, invite applications for the position of Senior Valve Development Engineer. Applicants should have had extensive experience in the design and production of receiving valves and their applications. The possession of academic qualifications will be considered an advantage. The post is pensionable under the company's pension scheme. The salary offered will be commensurate with the applicant's experience and qualifications. Replies will be treated in the strictest confidence and should be addressed to: The Manager, Hivac, Ltd., Greenhill Crescent, Harrow-on-the-Hill, Middlesex.

**LINCOLNSHIRE RADIO THERAPY CENTRE, SCUNTHORPE**, propose to appoint a junior Assistant Physicist for routine and development work in the Physics Department. Hospital experience is not necessary, but electronic engineering would be an advantage. The commencing salary scale is £350-25-400. Applications, quoting qualifications and experience, and accompanied by testimonials, should reach the Director of the Radiotherapy Centre, Memorial Hospital, Scunthorpe, not later than February 14, 1946

**MECHANICAL DESIGNER** required for light electrical appliances, S.E. London district. Good opportunity for a man with original ideas. Write, giving details of experience and qualifications, to Box 801, "Elec. Engg."

**LABORATORY ENGINEER** required for development work in radio firm in North London. Qualifications and ability essential. Salary according to experience. Write Box No. 240, c/o Streets, 110, Old Broad Street, E.C.2.

**DRAUGHTSMEN AND TRACERS** required for development work in radio firm in production of working drawings from data supplied by designers: (1) Mech. draughting, (2) Elect. preferably with experience on radio communication equipment. Workshop experience preferred. Apply in writing, giving full details, to R.T.E., Ltd., 45, Nightingale Lane, London, S.W.12.

**DESIGNER DRAUGHTSMAN** required for South London by Philips Laboratories. Experienced in communications equipment (electrical and mechanical). Apply in writing, with full details, to R.T.E., Ltd., 45, Nightingale Lane, London, S.W.12.

**ASSISTANT DEVELOPMENT ENGINEER** required by established firm of Scientific Instrument Makers, for work on A.C. electrical apparatus. Experience of electronics would be useful. Apply W. G. Pye & Co., Ltd., 80, Newmarket Road, Cambridge, stating salary required and details of experience.

**OLD-ESTABLISHED FIRM** situated in the Midlands specialising in Radio and Telecommunication equipment, require experienced development engineers for their laboratories. Experience in the development for manufacture of one of the following types of equipment is essential. Radio communication, navigational aids, electronic heating, sound reproduction, television or radio receivers. Applicants should quote experience, qualifications, age and salary required. Box 804, "Elec. Engg."

**PHYSICIST** required to undertake research work on cathode-ray tubes and electronic devices of a similar nature. Experience in high vacuum work essential. Salary according to age, qualifications and experience. Apply, in writing, to Cinema-Television, Ltd., Worsley Bridge Road, Lower Sydenham, London, S.E.26.

**DEVELOPMENT DRAUGHTSMAN**, accustomed to work on Radio and Television Transmitters and Receivers. Apply in writing stating age, qualifications and experience to Research Laboratories of the General Electric Co., Ltd., Wembley, Middx.

### SITUATIONS WANTED

**RADIO ENGINEER**, 26, Norwegian, university standard education, with some experience from Britain during war-time, seeks suitable position in the fields of radio or television.—Box 799, "Elec. Engg."

**RADAR OFFICER (R.A.F.)** experienced design, operation, maintenance, desires responsible position with radio or radar firm, preferably Midlands. Release approximately June. Box 802, "Elec. Engg."

**RADAR OFFICER**, 5½ years' experience, requires position in radio or television, preferably research. Extensive knowledge of television, C.R.T. and U.H.F. practice. Demob. July. Box 805, "Elec. Engg."

### WANTED

**WE OFFER** cash for good modern Communication and all-wave Receivers.—A.C.S. Radio, 44, Widmore Road, Bromley.

**CHARTERED ELECTRICAL ENGINEER, Ph.D., M.Sc., etc., and Partner**, having wide experience in electrical measurements, radio and electronic engineering, are prepared to accept work of a consultative nature in these fields. Box 790, "Elec. Engg."

**ONE COPY "ELECTRONIC ENGINEERING,"** August, 1945, required to complete series. Sinclair, 206, Dalry Road, Edinburgh.



**GALPINS**

Electrical Stores

408, High St., Lewisham, London, S.E.13

Phone: Lee Green 0309.

TERMS: CASH WITH ORDER. NO C.O.D.

Closed half-day Thursday. Open all day Saturday.

Electric Light Check Meters, first-class condition, electrically guaranteed, for A.C. mains, 200-250 volts 50 cy. 1 phase 5 amp. load, each 12/6.

Large Paxolin Panel, size 14 in. by 7 in. by 1/2 in., fitted massive switch arm, 12 large studs and contact blade, very smooth action, price 7/6 each.

X-Ray Transformer in oil, input 200 v., output 80,000 volts, rating 5 kVA., with Coolidge winding, £50; ditto, 2 1/2 kVA. at 90,000 volts, £35; ditto, dental type, 45,000 volts, £30.

Fluorescent Screens, 15 by 12, with lead glass, £5.

Large Fan Motors, all direct current, approx 1/2 h.p., 110 v. series wound, in first class condition, 20/- each; D.C. Motors, as above, only for 220 volts, in perfect order, 20/- each.

Rotary Converter, input 230 v. D.C., output 230 v. A.C., 50 cycle, single phase, 1 1/4 kW., constant rating, a high-grade job of very solid construction, £35.

Transformer Core to suit 2 1/2 kW. transformer, complete with clamps and bolts, 25/-.

Large Outdoor Bells, 110 v. D.C. working, 6 in. gong, 17/6.

D.C. Motor, totally enclosed, shunt wound, 220 v. D.C. 1/10 b.h.p., large size, high-grade, 45/-.

Auto Transformers, tapped 0-110-200-220-240 step up or down, 500 watts, £3 10s. od.; 2,000 watts, £9.

Block Condensers, large size, in metal cases, 20 MF, 300 v. A.C. working, 15/-.

Rotary Converter, input 220 v. D.C., at 9 amps., output 68-125 volts, 500 cycles, single phase, 1 1/4 kW., massive construction, price £12.

Fixed Resistances on fireproof mounts, size 12 in. by 1 in., 2 ohms, to carry 10 amps., 2/6.

Pre-Selector Switches, ex-G.P.O., 8-bank, each 25 contacts, complete with actuating relay, 50/-.

Moving Coil Meters, 2 in. dia., flush mounting, 0.5 M.A., 35/-; 0.50 M.A., 32/6; 2 1/2 in. dia., 0.100 M.A., 27/6.

Moving Coil Voltmeters by famous maker, type 301, reading 0-10 volts, 2 1/2 in. dia. panel mounting, as new and unused, nickel-plated finish. Price, 45/-.

Rotary Converter, input 230 v. 1/2 A. direct current; output 80 v. 6 1/2 A. single phase, 2,000 cycles. £7 10s.

Heavy Duty Chokes by famous maker, weight 14 lbs., wound 19 gauge wire, two equal coils, 4 terminals, total resistance 10 ohms. Price 35/-.

Ditto, 12 lbs., single winding, 22 gauge, 15 ohms, 30/-; Ditto, 10 lbs., 20 gauge, two coils, 6 ohms, 25/-.

Ex G.P.O. Relays, multi-leaf, very low current working, 7/6 each.

**— PARTRIDGE —  
TRANSFORMERS  
ARE AGAIN AVAILABLE**

We are now allowed to accept orders from the trade and public for ordinary commercial and domestic needs.

The Partridge organisation is again at your service. Our technical department will be pleased to assist you in your transformer problems.

We look forward to hearing from our old friends and welcome enquiries from newcomers.

May we send you our 1946 catalogue?

Telephone:  Abbey 2244  
**PARTRIDGE**  
**TRANSFORMERS LTD**  
76-B, PETTY FRANCE, LONDON, S.W.1



**RELIANCE  
POTENTIOMETERS**

will be shown on  
Stand No. 21  
at the  
**R.C.M.F. Exhibition**  
to be held at Grosvenor House  
Park Lane, London, W.1  
from February 19-22

**RELIANCE**  
Manufacturing Co. (Southwark) Ltd.  
Sutherland Rd., Higham Hill,  
WALTHAMSTOW - E. 17

Telephone : : Larkswood 3245

**DUAL TESTSCOPE**



This New Dual Model Indicates 2 to 30 volts and 100-750 volts. Send for interesting leaflet L24 on "Testing."

**RUNBAKEN MANCHESTER-1**

**LONDEX for RELAYS**

A.C. and D.C.

The wide range of Londex Relays covers, especially, the Wireless and Electronic fields.



Ask for details and leaflet 205/EO Multiple contact Relay LF

**LONDEX LTD**  
MANUFACTURERS OF RELAYS  
207 ANERLEY ROAD, LONDON S.E.20

**JUST OUT  
THE  
CATHODE-RAY TUBE  
HANDBOOK**

By S. K. LEWER, B.Sc.  
Executive Vice-President of the Incorporated Radio Society of Great Britain

The cathode-ray oscillograph is finding an ever-widening application in numerous branches of science and technology, and the main object of this practical book is to facilitate the use of the cathode-ray tube in its various purposes by setting out the basic principles of its design, construction and operation. The information in this up-to-date book is essential for all radio and electrical engineers and technicians. 6s. net.

**WORKED RADIO  
CALCULATIONS**

By A. T. WITTS, A.M.I.E.E.

This well-known author gives over three hundred worked examples, with answers to typical mathematical problems occurring in examinations for radio mechanics and wireless operators. 6s. 6d. net.

**PITMAN**

Pitman House, Parker St., London, W.C.2

For **RELIABILITY**

Just **TRIX**




Quality Equipment

**THE TRIx ELECTRICAL CO. LTD**  
1-5, MAPLE PLACE, TOTTENHAM CT. RD.  
LONDON W.1.  
TELE: MUSEUM: 5617 "GRAMS & CABLES" TRIXADIO WESDO. LONDON

# The HUB of the "HAM" world
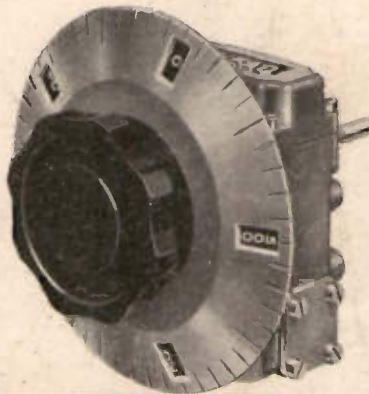
# WEBB'S *Radio*

Keen amateur experimenters know Webb's as the centre where the latest developments can be seen, explained and obtained. Expert technicians test and perfect all classes of radio equipment. A courteous and practical staff is ready to help you at our showrooms. That is why Webb's are recognised as Britain's leading specialists in Radio, Television and Electronics.




### PRECISION CONTROL DIALS

We have a very wide selection of instrument controls by Muirhead, Eddystone, etc., including the National HRO Type, now made by Muirheads. This is a dial giving an equivalent of 10 ft. of calibration scale, 500 degrees, each degree  $\frac{1}{4}$  in. long and is too well known for us to emphasise its superlative qualities.

Muirhead type D206A (National PWO), two driving shafts parallel to panel ... £5 2s. 6d.  
Muirhead type D115A (National NPWO), single drive shaft at right angle to panel. £4 15s. 0d.

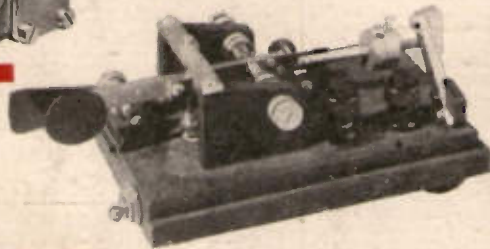
### AUTOMATIC KEY TYPE "RA"

Heavy cast gunmetal base finished fine grey crackle, rubber feet, no desk fixing necessary. Incorporates completely balanced electrical action of improved design. Heavy tungsten contacts, adjustable from 10 to 50 WPM. A key for the really discriminating speed friend. A shorting switch is incorporated in the base for CW/Phone operation. Key type "RA" 47/6


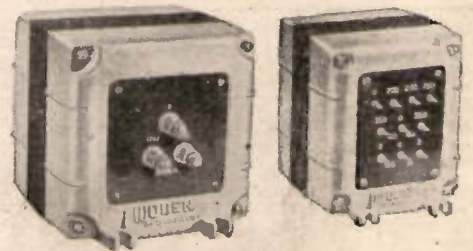
### WODEN TRANSFORMERS

now available in full range from immediate stock, including Filament, all voltages of H.T., Modulation and Driver types. Input and Smoothing Chokes for all current ratings are included. These are the standardised LF Inductors made to match in appearance with grey cast metal end plates, and black laminations. Their use ensures a professional finish to your apparatus. Full list of types and prices available on application.



### TAPPED "BLEEDER" RESISTORS

Vitreous enamel wire wound resistors, power type with adjustable tapping clip.  
50-watt rating:  
25,000 ohms ... 11/3  
50,000 ohms ... 14/9

WRITE, CALL OR TELEPHONE  
**14 SOHO STREET, LONDON, W.1.**

TELEPHONE: GERRARD 2089

OFFICIAL-BUSINESS HOURS: 9 a.m. to 5.30 p.m. SHOP HOURS: 9 a.m. to 5 p.m.  
(SAT. 9 a.m. to 1 p.m.)

Second printing of our INTERIM CATALOGUE is held up through paper control, etc.—Our apologies to many hundreds eagerly waiting for it. As a temporary measure we are sending details of selected items such as are of interest to the home experimenter.