

ELECTRONICS WORLD




APRIL 2004 £3.25

Cellphone access methods

Pseudo-sine wave inverter

USB analogue i/o

The discovery of electron diffraction

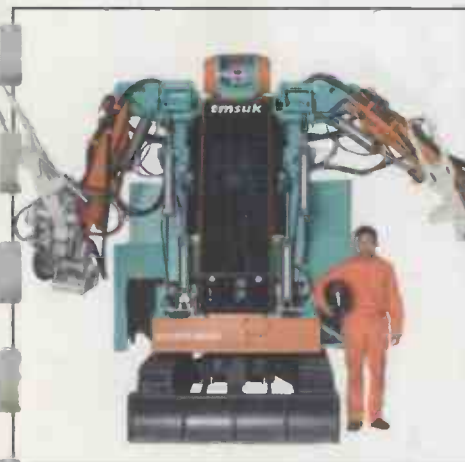

Circuit ideas:

- Leakage current jig
- Digital dice
- Analogue phase shifter

ENI 550L Amplifier (1.5 to 400MHz) 50 Watts	£2500
Hewlett Packard 3314A Function Generator 20MHz	£750
Hewlett Packard 3324A synth. function/sweep gen. (21MHz)	£1950
Hewlett Packard 3325B Synthesised Function Generator	£2500
Hewlett Packard 3326A Two-Channel Synthesiser	£2500
H.P. 4191A R/F Imp. Analyser (1GHz)	£3995
H.P. 4192A L.F. Imp. Analyser (13MHz)	£4000
Hewlett Packard 4193A Vector Impedance Meter (4-110MHz)	£2900
Hewlett Packard 4278A 1kHz/1MHz Capacitance Meter	£3500
H.P. 53310A Mod. Domain Analyser (opt 1/31)	£3950
Hewlett Packard 8349B (2 - 20 GHz) Microwave Amplifier	£2000
Hewlett Packard 8508A (with 85081B plug-in) Vector Voltmeter	£2500
Hewlett Packard 8904A Multifunction Synthesiser (opt 2+4)	£1750
Hewlett Packard 89440A Vector Signal Analyser (1.8GHz) opts AY8, AYA, AYB, AY7, IC2	£9950
Agilent (HP) E4432B (opt 1E5/K03/H03) or (opt 1EM/UK6/UN8) (250kHz - 3GHz)	£6000
Marconi 6310 - Prog'ble Sweep gen. (2 to 20GHz) - new	£2500
Marconi 6311 Prog'ble sig. gen. (10MHz to 20GHz)	£2995
Marconi 6313 Prog'ble sig. gen. (10MHz to 26.5GHz)	£3750
R&S SMG (0.1-1GHz) Sig. Generator (opts B1+2)	£2500
Rhode & Schwarz UPA3 Audio Analyser	£1500
Rhode & Schwarz UPA3 Audio Analyser	£2250
Fluke 5800A Oscilloscope Calibrator	£8995

OSCILLOSCOPES

Agilent (HP) 54600B 100MHz 2 channel digital	£800
Agilent (HP) 54602B 150MHz 4(2+2) channel digital	£1250
Agilent (HP) 54616B 500MHz 2 channel digital	£1750
Agilent (HP) 54616C 500MHz 2 channel colour	£2750
Agilent (HP) 54645D DSO/Logic Analyser 100MHz 2 channel	£2750
Hewlett Packard 54502A - 400MHz - 400 MS/s 2 channel	£1600
Hewlett Packard 54520A 500MHz 2ch	£2750
Hewlett Packard 54600A - 100MHz - 2 channel	£675
Hewlett Packard 54810A 'Infinium' 500MHz 2ch	£2995
Lecroy 9310CM 400MHz - 2 channel	£2250
Lecroy 9314L 300MHz - 4 channels	£2750
Philips 3295A - 400MHz - Dual channel	£1400
Philips PM3392 - 200MHz - 200MS/s - 4 channel	£1750
Philips PM3094 - 200MHz - 4 channel	£1500
Tektronix 2220 - 60MHz - Dual channel D.S.O	£850
Tektronix 2221 - 60MHz - Dual channel D.S.O	£850
Tektronix 2235 - 100MHz - Dual channel	£500
Tektronix 2245A - 100MHz - 4 channel	£700
Tektronix 2430/2430A - Digital storage - 150MHz	from £1250
Tektronix 2445 - 150MHz - 4 channel +DMM	£850
Tektronix 2445/2445B - 150MHz - 4 channel	£800
Tektronix 2465/2465A /2465B - 300MHz/350MHz 4 channel	from £1200
Tektronix TDS 310 50MHz DSO - 2 channel	£750
Tektronix TDS 420 150 MHz 4 channel	£950
Tektronix TDS 520 - 500MHz Digital Oscilloscope	£2500
Tektronix TAS 475 100MHz - 4 channel analogue	£750
Tektronix TDS 340 100MHz - 2 channel digital	£950
Tektronix TDS 360 200MHz - 2 channel digital	£1200
Tektronix TDS 420A 200MHz - 4 channel digital	£1800
Tektronix TDS 540B 500MHz - 4 channel digital	£2500
Tektronix TDS 640A 500MHz - 4 channel digital	£2700
Tektronix TDS 744A 500MHz - 4 channel digital	£4250
Tektronix TDS 754C 500MHz - 4 channel digital	£4500

SPECTRUM ANALYSERS

Advantest 4131 (10kHz - 3.5GHz)	£3000
Agilent (HP) 35665A (opt. 1D1) Dual ch. Dynamic Signal Analyser	£3750
Agilent (HP) 3588A High Performance spec. An. 10Hz - 150MHz	£6250
Agilent (HP) 8560A (opt 002 - Tracking Gen.) 50Hz - 2.9GHz	£5000
Agilent (HP) 8593E (opt 41/105/130/151/160) 9kHz - 22GHz	£12000
Agilent (HP) 8594E (opt 41/101/105/130) 9kHz - 2.9GHz	£4250
Agilent (HP) 8753D Network Analyser (30kHz - 3GHz)	£8500
Agilent (HP) 8590A (opt H18) 10kHz - 1.8GHz	£2500
Agilent (HP) 8596E (opts 41/101/105/130) 9kHz - 12.8 GHz	£8000
Farnell SSA-1000A 9kHz-1GHz Spec. An.	£1250
Hewlett Packard 3582A (0.02Hz - 25.5kHz) dual channel	£1500
Hewlett Packard 3585A 40 MHz Spec Analyser	£3000
Hewlett Packard 3585B 20 Hz - 40 MHz	£4500
Hewlett Packard 3561A Dynamic Signal Analyser	£3500
Hewlett Packard 8568A - 100kHz - 1.5GHz Spectrum Analyser	£3500
Hewlett Packard 8590A (opt 01, 021, 040) 1MHz-1.5MHz	£2500
Hewlett Packard 8713C (opt 1 E1) Network An. 3 GHz	£6000
Hewlett Packard 8713B 300kHz - 3GHz Network Analyser	£5000
Hewlett Packard 8752A - Network Analyser (1.3GHz)	£4995
Hewlett Packard 8753A (3000kHz - 3GHz) Network An.	£3250
Hewlett Packard 8753B+85046A Network An + S Param (3GHz)	£6500
Hewlett Packard 8756A/8757A Scaler Network Analyser	from £900
Hewlett Packard 8757C Scaler Network Analyser	£3500
Hewlett Packard 70001A/70900A/70906A/70902A/70205A - 26.5 GHz Spectrum Analyser	£7000
Tektronix 492P (opt1,2,3) 50kHz - 21GHz	£3500
Tek 496 (9kHz-1.8GHz)	£2500

Radio Communications Test Sets

Agilent (HP) 8924C (opt 601) CDMA Mobile Station T/Set	£8500
Agilent (HP) E8285A CDMA Mobile Station T/Set	£8500
Anritsu MT8802A (opt 7) Radio Comms Analyser (300kHz-3GHz)	£8500
Hewlett Packard 8920B (opts 1,4,7,11,12)	£6750
Hewlett Packard 8922M + 83220E	£2000
Marconi 2955 / 2955A	from £1250
Marconi 2955B/60B	£3500
Marconi 2955R	£1995
Motorola R2600B	£2500
Racal 6103 (opts1, 2)	£5000
Rohde & Schwarz SMFP2	£1500
Rohde & Schwarz CMD 57 (opts B1, 34, 6, 19, 42, 43, 61)	£4995
Rohde & Schwarz CMT 90 (2GHz) DECT	£3995
Rohde & Schwarz CMTA 94 (GSM)	£4500
Schlumberger Stabilock 4015	£3250
Schlumberger Stabilock 4031	£2750
Schlumberger Stabilock 4040	£1300
Wavetek 4103 (GSM 900) Mobile phone tester	£1500
Wavetek 4032 Stabilock Comms Analyser	£4000
Wavetek 4105 PCS 1900 GSM Tester	£1600

MISCELLANEOUS

Agilent (HP) 8656A / 8656B 100kHz-990MHz Synth. Sig. Gen.	from £600
Agilent (HP) 8657A / 8657B 100kHz-1040 or 2060MHz	from £1250
Agilent (HP) 8644A (opt 1) 252kHz - 1030 MHz Sig.Gen.	£4500
Agilent (HP) 8664A (opt 1 + 4) High Perf. Sig. Gen. (0.1-3GHz)	£10500
Agilent (HP) 8902A (opt 2) Measuring Rxr (150kHz-1300MHz)	£7500
Agilent (HP) 8970B (opt 020) Noise Figure Meter	£3950
Agilent (HP) EPM 441A (opt 2) single ch. Power Meter	£1300
Agilent (HP) 6812A AC Power Source 750VA	£2950
Agilent (HP) 6063B DC Electronic Load 250W (0-10A)	£1000
Anritsu MG3670B Digital Modulation Sig. Gen. (300kHz-2250MHz)	£4250
Anritsu/Wiltron 68347B (10MHz-20GHz) Synth. Sweep Sig. Gen.	£9000
EIP 545 Microwave Frequency Counter (18GHz)	£1000
EIP 548A and B 26.5GHz Frequency Counter	from £1500
EIP 575 Source Locking Freq.Counter (18GHz)	£1200
EIP 585 Pulse Freq.Counter (18GHz)	£1200
Fluke 6060A and B Signal Gen. 10kHz - 1050MHz	£950
Genrad 1657/1658/1693 LCR meters	from £500
Gigatronics 8541C Power Meter + 80350A Peak Power Sensor	£1250
Gigatronics 8542C Dual Power Meter + 2 sensors 80401A	£1995
Hewlett Packard 339A Distortion measuring set	£600
Hewlett Packard 436A power meter and sensor (various)	from £750
Hewlett Packard 438A power meter - dual channel	£1750
Hewlett Packard 3335A - synthesiser (200Hz-81MHz)	£1750
Hewlett Packard 3784A - Digital Transmission Analyser	£2950
Hewlett Packard 37900D - Signalling test set	£2500
Hewlett Packard 4274A LCR Meter	£1750
Hewlett Packard 4275A LCR Meter	£2750
Hewlett Packard 4276A LCZ Meter (100MHz-20KHz)	£1400
Hewlett Packard 5342A Microwave Freq.Counter (18GHz)	£850
Hewlett Packard 5385A - 1 GHz Frequency counter	£495
Hewlett Packard 8350B - Sweep Generator Mainframe	£1500
Hewlett Packard 8642A - high performance R/F synthesiser (0.1-1050MHz)	£2500
Hewlett Packard 8901B - Modulation Analyser	£1750
Hewlett Packard 8903A, B and E - Distortion Analyser	from £1000
Hewlett Packard 11729B/C Carrier Noise Test Set	from £2500
Hewlett Packard 85024A High Frequency Probe	£1000
Hewlett Packard 6032A Power Supply (0-60V)-(0-50A)	£2000
Hewlett Packard 5351B Microwave Freq. Counter (26.5GHz)	£2750
Hewlett Packard 5352B Microwave Freq. Counter (40GHz)	£5250
IFR (Marconi) 2051 (opt 1) 10kHz-2.7GHz Sig. Gen.	£5000
Keithley 220 Programmable Current Source	£1750
Keithley 228A Prog'ble Voltage/Current Source IEEE.	£1950
Keithley 238 High Current - Source Measure Unit	£3750
Keithley 486/487 Picoammeter (+volt.source)	£1350/£1850
Keithley 617 Electrometer/source	£1950
Keithley 8006 Component Test Fixture	£1750
Marconi 6950/6960/6960A/6970A Power Meters & Sensors	from £400
Philips 5515 - TN - Colour TV pattern generator	£1400
Philips PM 5193 - 50 MHz Function generator	£1350
Rohde & Schwarz FAM (opts 2,6 and 8) Modulation Analyser	£2500
Rohde & Schwarz NRV/NRVD Power meters with sensors	from £1000
Rohde & Schwarz AMIQ I/Q Modulation Generator 2 channel	£3500
Rohde & Schwarz SMIQ 03B Vector Sig. Gen. 3.3GHz	£7000
Stanford Research DS360 Ultra Low Distortion Function gen. (200kHz)	£1400
Tektronix AM503 - AM503A - AM503B Current Amp's with M/F and probe	from £800
Tektronix AWG 2021 Arbitrary Waveform Gen. (10Hz-250MHz) 2 ch.	£2400
Wayne Kerr 3245 - Precision Inductance Analyser	£1750
Bias unit 3220 and 3225L Cal.Coil available if required.	(P.O.A)
Wayne Kerr 3260A + 3265A Precision Magnetics Analyser with Bias Unit	£5500
W&G PCM-4 PCM Channel measuring set	£3750

All equipment is used - with 30 days guarantee and 90 days in some cases.

Add carriage and VAT to all goods.

1 Stoney Court, Hotchkiss Way, Binley Industrial Estate
Coventry CV3 2RL ENGLAND

Tel: 02476 650 702
Fax: 02476 650 773
Web: www.telnet.uk.com
Email: sales@telnet.uk.com

3 COMMENT

Ghosts – Ian Hickman

4 NEWS

- Diverse technologies cut fuel cell drawback
- Light spreader
- Lithium ion battery gets boost
- Japanese to English speech translation
- Robot to the rescue
- No-melt laser trims cheese
- Patents get re-invented
- Valve goes digital
- Add a bit of colour to your life s
- Chemicals etch holes in PCBs
- Europe gets behind fuels cells
- Flexible displays
- LED headlights hit the road
- Intel claims success with 90nm
- 3D photonic crystals from Oxford
- Sharp gets MBE for violet laser



- LED internal reflector doubles efficiency
- £3.2 billion worth of profit lost every year

10 A PSEUDO-SINE WAVE INVERTER

Ian Hickman has a demonstrator design that can be used as a basis for your own project

14 ANALOGUE AND DIGITAL I/O VIA THE USB PORT

Following on from Colin Attenborough's November 2002 article, this update adds analogue i/o to the basic design

18 ACCESS METHODS OF CELLULAR TELECOMMUNICATIONS SYSTEMS

Things have changed a lot in the 20 years since cellular phones have been around. Ian Poole looks at how the calls get through

22 VOLTAGE OR CURRENT FEEDBACK?

Frantisek Michele investigates the differences between voltage and current feedback and explains how to decide what's best.

26 THE DISCOVERY OF ELECTRON DIFFRACTION

In this slightly 'off topic' article, David Potter looks at electron diffraction



30 NEW PRODUCTS

The month's top new products

38 CIRCUIT IDEAS

- Phase selector for three-phase mains supply
- Intelligent electric fence with burglar alarm
- VHF Pre-amplifier using Max2633
- Leakage current jig
- Instant flicker free turn-on fluorescent lamps
- A novel power good indicator circuit
- Digital dice
- Analogue single span 0-180° phase shifter

46 LETTERS

- War time radio
- Political correctness
- The O or 0 controversy
- EMC
- Airborne lasers
- Wheatstone
- Analogue switching
- The new scholasticism

54 BARE LCD DISPLAY DRIVE IN EMBEDDED APPLICATIONS

Daniel Malik looks at LCD display drives in embedded applications


60 WEB DIRECTIONS

Useful web addresses for electronics engineers



Quasar Electronics Limited
PO Box 6936, Bishops Stortford,
CM23 4WP
Tel: 0870 246 1826
Fax: 0870 460 1046
E-mail: sales@quasarelectronics.com

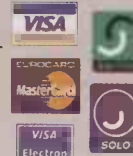Add £2.00 P&P to all UK orders. 1st Class Recorded - £4.
 Next day (insured £250) - £7. Europe - £5. Rest of World - £10.
 We accept all major credit/debit cards. Make cheques/PO's
 payable to Quasar Electronics Limited.
 Prices include 17.5% VAT. MAIL ORDER ONLY.
 Call now for our FREE CATALOGUE containing details of
 over 300 electronic kits, projects and modules.



QUASAR 0871 CREDIT CARD SALES 717 7168 electronics

Motor Drivers/Controllers

Here are just a few of our controller and driver modules for AC, DC, unipolar/bipolar stepper motors and servo motors. See website for full details.

DC Motor Speed Controller (6A/100V)
 Control the speed of almost any common DC motor rated up to 100V/5A. Pulse width modulation output for maximum motor torque at all speeds. Supply: 5-15VDC. Box supplied. Dimensions (mm): 60Wx100Lx60H. Kit Order Code: 3067KT - £12.95
 Assembled Order Code: AS3067 - £19.95

NEW! PC / Standalone Unipolar

Stepper Motor Driver
 Drives any 5, 6 or 8-lead unipolar stepper motor rated up to 6 Amps max. Provides speed and direction control. Operates in stand-alone or PC-controlled mode. Up to six 3179 driver boards can be connected to a single parallel port. Supply: 9V DC. PCB: 80x50mm. Kit Order Code: 3179KT - £9.95
 Assembled Order Code: AS3179 - £16.95



PC Controlled Dual Stepper Motor Driver
 Independently control two unipolar stepper motors (each rated up to 3 Amps max.) using PC parallel port and software interface provided. Four digital inputs available for monitoring external switches and other inputs. Software provides three run modes and will half-step, single-step or manual-step motors. Complete unit neatly housed in an extended D-shell case. All components, case, documentation and software are supplied (stepper motors are NOT provided). Dimensions (mm): 55Wx70Lx15H. Kit Order Code: 3113KT - £16.95
 Assembled Order Code: AS3113 - £24.95



NEW! Bi-Polar Stepper Motor Driver

Drive any bi-polar stepper motor using externally supplied 5V levels for stepping and direction control. These usually come from software running on a computer. Supply: 8-30V DC. PCB: 75x85mm. Kit Order Code: 3158KT - £12.95
 Assembled Order Code: AS3158 - £26.95



Most items are available in kit form (KT suffix) or assembled and ready for use (AS prefix).

Controllers & Loggers

Here are just a few of the controller and data acquisition and control units we have. See website for full details. Suitable PSU for all units: Order Code PSU203 £9.95


Rolling Code 4-Channel UHF Remote
 State-of-the-Art. High security. 4 channels. Momentary or latching relay output. Range up to 40m. Up to 15 Tx's can be learnt by one Rx (kit includes one Tx but more available separately). 4 indicator LED's. Rx: PCB 77x85mm, 12VDC/6mA (standby). Two and Ten channel versions also available. Kit Order Code: 3180KT - £41.95
 Assembled Order Code: AS3180 - £49.95



Computer Temperature Data Logger
 4-channel temperature logger for serial port. °C or °F. Continuously logs up to 4 separate sensors located 200m+ from board. Wide range of free software applications for storing/using data. PCB just 38x38mm. Powered by PC. Includes one DS1820 sensor and four header cables. Kit Order Code: 3145KT - £22.95
 Assembled Order Code: AS3145 - £29.95
 Additional DS1820 Sensors - £3.95 each



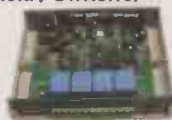
NEW! DTMF Telephone Relay Switcher
 Call your phone number using a DTMF phone from anywhere in the world and remotely turn on/off any of the 4 relays as desired. User settable Security Password, Anti-Tamper, Rings to Answer, Auto Hang-up and Lockout. Includes plastic case. 130x110x30mm. Power: 12VDC. Kit Order Code: 3140KT - £39.95
 Assembled Order Code: AS3140 - £59.95



Serial Isolated I/O Module
 PC controlled 8-Relay Board. 115/250V relay outputs and 4 isolated digital inputs. Useful in a variety of control and sensing applications. Uses PC serial port for programming (using our new Windows interface or batch files). Once programmed unit can operate without PC. Includes plastic case 130x100x30mm. Power: 12VDC/500mA. Kit Order Code: 3108KT - £54.95
 Assembled Order Code: AS3108 - £64.95



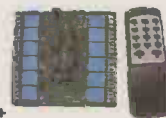Infrared RC Relay Board
 Individually control 12 on-board relays with included infrared remote control unit. Toggle or momentary. 15m+ range. 112x122mm. Supply: 12VDC/0.5A
 Kit Order Code: 3142KT - £41.95
 Assembled Order Code: AS3142 - £59.95



PIC & ATMEL Programmers

We have a wide range of low cost PIC and ATMEL Programmers. Complete range and documentation available from our web site.

Programmer Accessories:
 40-pin Wide ZIF socket (ZIF40W) £16.00
 18V DC Power supply (PSU201) £5.95
 Leads: Parallel (LEAD108) £4.95 / Serial (LEAD76) £4.95 / USB (LEADUAA) £4.95

NEW! USB 'All-Flash' PIC Programmer
 USB PIC programmer for all 'Flash' devices. No external power supply making it truly portable. Supplied complete with 40-pin wide-slot ZIF socket, box and Windows Software. Kit Order Code: 3128KT - £49.95
 Assembled Order Code: AS3128 - £54.95



Enhanced "PICALL" ISP PIC Programmer
 Will program virtually ALL 8 to 40 pin PICs plus a range of ATMEL AVR, SCENIX SX and EEPROM 24C devices. Also supports In-System Programming (ISP) for PIC and ATMEL AVRs. Free software. Blank chip auto detect for super fast bulk programming. Requires a 40-pin wide ZIF socket (not included). Kit Order Code: 3144KT - £64.95
 Assembled Order Code: AS3144 - £69.95



ATMEL 89xxx Programmer
 Uses serial port and any standard terminal comms program. 4 LED's display the status. ZIF sockets not included. Supply: 16-18VDC. Kit Order Code: 3123KT - £29.95
 Assembled Order Code: AS3123 - £34.95



NEW! USB & Serial Port PIC Programmer
 USB/Serial connection. Ideal for field use. Header cable for ICSP. Free Windows software. See website for PICs supported. ZIF socket not incl. Supply: 18VDC. Kit Order Code: 3149KT - £29.95
 Assembled Order Code: AS3149 - £44.95



www.quasarelectronics.com

Secure Online Ordering Facilities • Full Product Listing, Descriptions & Photos • Kit Documentation & Software Downloads

EDITOR**Phil Reed****p.reed@highburybiz.com****CONSULTANT****Ian Hickman****CONTRIBUTING EDITOR****Martin Eccles****PRODUCTION EDITOR/DESIGNER****Jane Massey****J.Massey@highburybiz.com****EDITORIAL E-MAILS****EWeditor@highburybiz.com****EDITORIAL ADMINISTRATION****Caroline Fisher****01322 611274****EWadmin@highburybiz.com****GROUP SALES****Luke Baldock****01322 611292****l.baldock@highburybiz.com****PRODUCTION EXECUTIVE****Dean Turner****d.turner@highburybiz.com****01322 611206****CLASSIFIED FAX****01322 616376****MANAGING EDITOR****Bill Evett****PUBLISHING DIRECTOR****Tony Greville****ISSN 0959-8332****SUBSCRIPTION QUERIES**

Tel (0) 1353 654431

Fax (0) 1353 654400

Disclaimer

We work hard to ensure that the information presented in *Electronics World* is accurate. However, *Electronics World's* publisher - Highbury Business - will not take responsibility for any injury or loss of earnings that may result from applying information presented in the magazine. It is your responsibility to familiarise yourself with the laws relating to dealing with your customers and suppliers, and with safety practices relating to working with electrical/electronic circuitry - particularly as regards electric shock, fire hazards and explosions.

Ghosts

From time to time, ghosts come back to haunt me, arising from articles I have written in the past. For example, the Editor recently forwarded to me an interesting query about "The MOS controlled thyristor", an article which appeared in these pages in the September 1993 issue. Other such ghosts have surfaced from even further back; my first contribution to these pages - a Design Idea entitled "Two for the price of one" - was back in about 1970, a useful circuit although I no longer have a copy of it as published. It's not just from articles either.

Occasional queries arrive, triggered by people reading my books, particularly the one titled "Oscilloscopes"†. This was first published in 1981, is now in its fifth edition, and has never been out of print.

These "ghosts" are always interesting, and originate from readers just about anywhere, France, India, Australia, the USA among other places, all come to mind. They often set me thinking even further back over a career in electronics spanning half a century, to days - for example - spent servicing AI10 units. Airborne Interceptor Mk10 was an airborne radar which saw service during the Second World War, still in service with the RAF's Gloster Meteor NF11 night fighters in the mid fifties, although by then hopelessly out of date. The American "doorknob pentodes" in the IF strip were unobtainable by then,

explaining the pilots' routine complaints of low sensitivity.

A couple of years later found me at The Central Research Laboratories of The G.E.C., in the days when that company's motto was "Everything Electrical". The labs were much later renamed "The Hirst Research Centre", and have now disappeared off the face of the earth, to be replaced by houses, shops and what-have-you. It was, in its heyday, an extraordinary institution, where Ph.D.s were two a penny, and a carefree university-student atmosphere pervaded the buildings. There, at one stage, I had access to a diffusion furnace, and stayed behind one evening to make myself a silicon rectifier. This was for a mains power supply for my home-made battery portable radio, using DK96 series valves with their 25mA filaments. They were happy days, when petrol cost four shillings (20p) a gallon, and - following WWII - things could only get better. Some of the extraordinary activities and characters at the CRL of the GEC in those days would doubtless be of interest to, and probably even strain the credulity of, a later generation, but space dictates that any such reminiscences must await another occasion.

† ISBN 0 7506 4757 4
Newnes/Butterworth-Heinemann

Ian Hickman

All change

Thanks to Ian for the leader - I thought it time that someone else should have a go!

I'd like to let you know of some staff changes here at *EW*.

Firstly, my sincere thanks to Alan Kerr who has been laying out *EW* for years and has now decided to pursue a freelance career. And so we welcome Jane Massey and wish her all the best in her new job. This issue is

her first 'solo' run!

I'd also like to thank Geoff Arnold for all his proofing work over the years; sadly Geoff is retiring from *EW*, even in his retirement! We wish him good luck for the future. And on that note, if anybody thinks that typos in *EW* are too frequent - let me know if you think you could do the (part time) job.

Phil Reed

Electronics World is published monthly by **Highbury Business, Media House, Azalea Drive, Swanley, Kent, BR8 8HU**

Highbury Business is a trading name of Highbury Business Communications Limited, a subsidiary of Highbury House Communications PLC. Registered in England. Registered Number 4189911. Registered Office: The Publishing House, 1-3 Highbury Station Road, Islington, London N1 1SE

Newstrade: Distributed by COMAG, Tavistock Road, West Drayton, Middlesex, UB7 7QE Tel 01895 444055.

Subscriptions: Highbury Fulfillment Services, Link House, 8 Bartholomew's Walk, Ely Cambridge, CB7 4ZD. Telephone 01353 654431. Please notify change of address.

Subscription rates
1 year UK £38.95 O/S £64.50
US\$106.40 Euro 93.52

USA mailing agents: Mercury Airfreight International Ltd Inc, 10(b) Englehard Ave, Avenel NJ 07001. Periodicals Postage Paid at Rahway NJ Postmaster. Send address changes to above.

Printed by Polestar [Colchester] Ltd,

Origination Impress Repro by Design
A1 Parkway, Southgate Way, Orton Southgate, Peterborough, PE2 6YN



HIGHBURY
Business Communications

A SUBSIDIARY OF HIGHBURY HOUSE COMMUNICATIONS PLC

Diverse technologies cut fuel cell drawback


CMR Fuel Cells, a Cambridge-based spin out from Scientific Generics, has a novel fuel cell structure which side-steps cell membrane leakage.

The compact mixed-reactant cell, from which the company gets its name, uses selective electrodes to remove the need for fuel and oxidiser to be separated. In fact, it needs them to be mixed.

Membranes in conventional cells separate fuel and oxidiser and have to be thicker than electrically necessary to cut unwanted fuel leakage into the oxidiser side. "Ours can be much thinner," CMR founder Michael Priestnall told *Electronics World*, "and in principle could be a coating on one catalyst or the other. Just enough to provide electrical insulation."

The CMR design also saves space. In conventional fuel cells, fuel and oxidiser flow across opposite faces of a membrane. This needs flow space, and a baffle to stop the fuel from one cell mixing with the oxidiser from the next. These extra part eat-up volume in cell stacks.

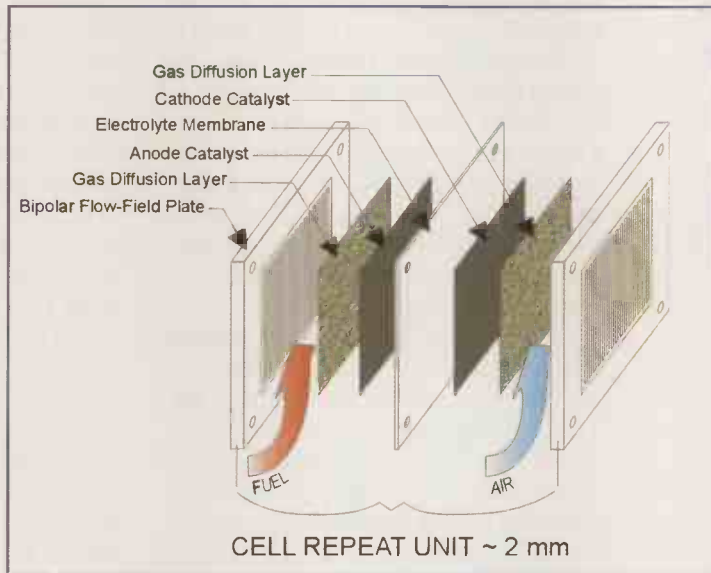In the CMR cell, a mixture of fuel and oxidant flows through a



fully porous anode-electrolyte-cathode assembly, then straight on to the next similar assembly.

Each time, the mixture first meets a fuel-selective catalyst which splits H^+ ions from the fuel. These are absorbed straight into the membrane which conducts ions, while being electrically insulating - preventing electrons flowing back and shorting the cell out, and

porous to the mixture.

When the mixture exits the membrane it meets an oxygen-selective catalyst which combines oxygen and the H^+ ions to make water.


The catalysts are conductive and, as previously mentioned, the membrane is insulating, forcing electrons from the reactions to travel around any external circuit. As it passes each membrane fuel and oxidiser are gradually used up.

By stacking a porous carbon layer between each membrane assembly, the potential from all the cells in a stack can be added for a higher output voltage. Carbon cannot carry H^+ ions and will therefore block any ionic short circuits.

The technology is applicable to most fuel cell chemistries, claims the firm, including the 'direct methanol' types proposed for phones and laptops.

However, it is only applicable to active fuel cells which include oxidiser and fuel pumps, and not passive fuel cells which have a tank of fuel on one side of a membrane and the atmosphere on the other for oxygen - see the box.

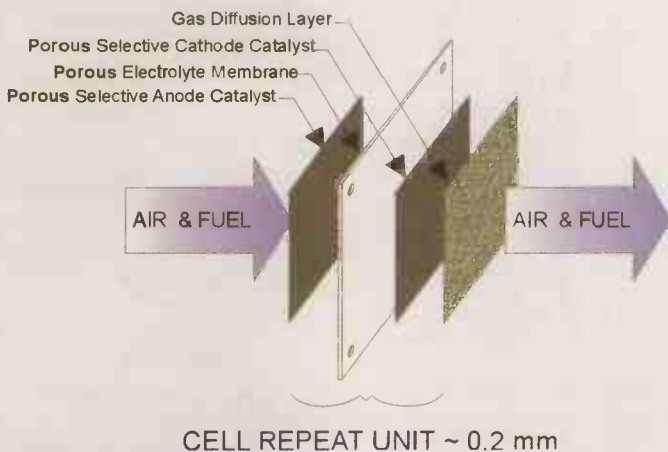Conventional fuel cells (top) have to have sideways flow and therefore need baffles. The flow-through CMR design can be thinner.



Fujitsu Laboratories has developed a material that allows highly concentrated (30 per cent) methanol to be used in passive fuel cells.

"This technology enables much higher power capacities for passive micro fuel cells and realises longer run-times for mobile devices such as notebook PCs, PDAs and mobile phones," said Fujitsu.

Fuel in conventional fuel cells has to be dilute or much of it will leak across the cell membrane and uselessly combines with the oxidiser - for an exception, see the CMR fuel cell article.

Passive systems are simple and lightweight as they have no pumps, but without pumps they cannot self-dilute fuel using waste water, so they have to be fed bulky dilute fuel.

The answer, according to Fujitsu, is a less porous alternative to the standard fluorinated polymer membrane. Its membrane is an aromatic hydrocarbon covered with a high density of platinum-based nano-particle catalyst with methanol blocking properties. "This reduces the total methanol crossover effect to one-tenth that encountered with typical fluorinated polymers," said the firm.

An industry insider told *Electronics World* that the Fujitsu development, unlike many proposed alternative membranes which rapidly self-destruct, looks promising, but would be expensive to produce. The prototype pictured is 15mm thick and delivers 15W.



Japanese to English speech translation

NEC claims to have made a robot capable of bi-directional Japanese-English speech translation.

The translator has been built into the firm's prototype PaPeRo personal robot.

"In order to realise an operable robot capable of conversation with a translation function, small memory and compact translation software are necessary," said NEC. "Through the development of a compact, high-speed speech recognition system NEC succeeded in installing this function in the small robot."

The robot has been programmed with 50,000 Japanese and 25,000 English travel and tourism related words.

At the moment a microphone is necessary. "NEC will continue to work on this system to enable hands-free [microphone-free] voice input."


PaPeRo is at: www.incx.nec.co.jp/robot/robotcenter_e.html

Robot to the rescue

Enryu HyperRescueRobot is a 3.45m tall machine from Japanese firm Tmsuk - better known for personal robot 'friends' and mobile security camera platforms. Weighing 5,000kg, Enryu can span 10m with arms outstretched and move at up to 3km/h. The operator sits inside or can work it remotely. Power comes from a built-in diesel engine. See www.enryu.jp for a video.



Light spreader

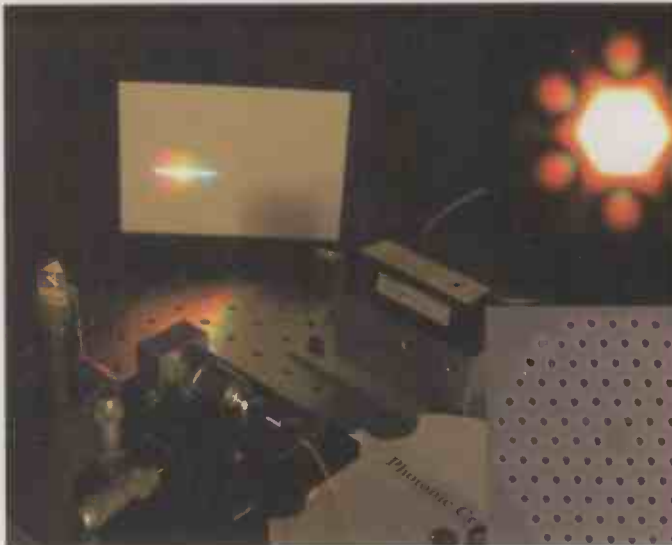

A UK firm has used a photonic crystal fibre to develop a broadband light emitter called an optical supercontinuum.

BlazePhotonics from Bath said the special fibre optic cable takes narrowband light from a solid state laser and outputs light covering an octave or more.

The input at 1,060nm, typically from a Neodymium laser, is turned into light from 550nm (green) to 1,600nm (infra-red). This light could be very useful in applications such as fibre characterisation and testing, optical coherence tomography, microscopy and chemical sensing.

No-melt laser trims cheese

Xiaochun Li, a University of Wisconsin-Madison professor and laser expert, has adapted 'cold laser machining' to cut cheese. "The fast-food industry wants cheese that is still nicely shaped, but is cut very thin," said Li, "But when you cut cheese thinner it tears or sticks to the blade."

Li tried conventional commercial lasers, but they melted or burned the cheese.

However, ultra-violet lasers which cut by photo-ablation had no problems.

Unfortunately for cheese

Existing systems, such as superluminescent LEDs and pumped fibre lasers, are at least twice the price, said the firm.

The converter works due to non-linearity in the fibre and the presence of small sidebands in the input laser. These sidebands are amplified and spread, causing more sidebands which are themselves amplified.

If the fibre is long enough, about 20m, the output is a flat (within about 5dB) spectrum.

A photonic crystal fibre has microscopic air holes throughout the cladding of the fibre. Light can also be guided through a hollow core in some designs.



sculptors, UV lasers are expensive and the computer-driven prototype only cuts at 1mm/s.

Patents get re-invented

The Government has published its Patents Bill, aimed at encouraging innovation with better support for small businesses.

One of the key measures in the bill is the ability for the Patent Office to give an independent opinion on the validity or infringement of patents. This could avoid the need for costly litigation.

"Effective, flexible and up-to-date patent law is essential to help businesses turn bright ideas into successful products and processes," said Lord Sainsbury, Minister for Science and Innovation.

The bill would bring UK patent law into line with the European Patent Convention, making it easier for UK companies to operate across Europe.

It would also deter patent holders from making unreasonable allegations of infringement, said the Patent Office.

Lithium ion battery gets boost

Sanyo Electric is to raise production of its prismatic lithium ion batteries, with an electrode structure said to have better safety than standard Li-ion cells. The prismatic (rectangular) cells use a mixture of lithium cobalt oxide (LiCoO₂) and lithium manganese oxide (LiMn₂O₄) in the positive electrode.

The firm said reducing the cobalt in favour of manganese is good, as it is cheaper and more stable with heat, making it safer. However, LiMn₂O₄ has lower cycle and storage abilities.

Other firms working in this area include PolyStor which bases its cells on lithium nickel cobalt oxide (LiNiCoO₂) cathodes. The polymer construction technology is licensed from Motorola's energy systems group.

Sanyo's latest model, the UF553450L, has an 820mAh capacity, measures 50x34x5.5mm and weighs 19grams. Energy densities are 324Wh/l and 160Wh/kg.

Valve goes digital

A digital valve has been developed for medical applications by Camcon Technology.

The firm's design is bi-stable, and hence does not require power to hold its state. A low power operation would make it ideal for giving patients mobility while on medication.

"Until now, the medical sector has had to rely on big, energy inefficient and fixed installations," said Wladyslaw Wagnanski, inventor of the valve and MD at Camcon. "We hope that our cell battery operated bi-stable pinch valve will break the ground for medical solutions helping patients to be more comfortable and mobile as long as automatic flow controlling device is needed."

Camcon's design is formed from a magnetised armature held in position by permanent magnets. Coils placed around the ends of the armature can be briefly energised to disrupt the magnetic flux, allowing the valve to swing to its alternate position.

Reaction times of the armature are said to be under 100µs, while each switching action uses around 3mJ of energy. Devices have been tested by the firm running to billions of cycles.

Add a bit of colour to your life



The Vos Pad in London is claimed to be the only flat in the world solely lit by LEDs. Lighting company Vos Solutions fitted it out as a showroom. RGB LEDs fittings provide the light and can give almost any colour. www.thevospad.com



Europe gets behind fuel cells

The European Commission has established a hydrogen and fuel cell group to promote the technology. The EC aims to speed the development of fuel cell technology by coordinating international research efforts, both commercial and academic.

The initiative was described as "a milestone for hydrogen and fuel-cell stakeholders in Europe" by Romano Prodi, president of the European Commission.

"I am sure that it will be highly influential in bringing forward a radically new approach to the way we produce and use energy in Europe - and eventually worldwide," said Prodi.

The European programme will run for some ten years, drawing on €2.8bn in public and private money, said the EC.

Unfortunately the UK lags Europe and the US in research and development of fuel cell technology. DTI funding amounts to between £1m to £2m a year.

US spending on fuel cell research dwarfs UK and European efforts. At its height the US put \$3bn into research in one year.

Europe already imports over 50 per cent of its oil, a figure set to rise.

"Current trends are clearly unsustainable. We have to act now in order to change them," said Prodi.

Chemicals etch holes in PCBs

Using chemical etching to make vias in printed circuit boards is a tenth of the cost of existing methods, according to CERN, the European particle physics lab.

CERN developed its chemical etching technique for internal use, but is now hoping to license the idea to PCB makers.

Called ChemicalVia, the process can be used to produce blind and buried vias in multi-layer PCBs.

This capability has, until now, been limited to manufacturers with equipment such as laser drills and plasma etching machines.

CERN, through its UK

representative PPARC, said its licence fee of £15,000 was one tenth of the cost of existing equipment, while running costs are similarly reduced in price.

ChemicalVia can be used on polyimide boards such as Kapton or FR4. A layer of metal is epoxy bonded to the board, and the board is then patterned using photolithography then etched and cleaned using three chemicals.

A final metallisation process fills the vias in exactly the same way as the conventional process.

CERN's approach can produce vias down to 25µm in diameter, more than sufficient for the electronics industry.

Roll-up, roll-up for flexible displays

Philips Research in the Netherlands has produced a quarter-VGA, 320x240 pixel, monochrome display with a bending radius of 20mm.

The five inch panel is based upon an organic active matrix backplane just 25µm thick and containing 80,000 thin film transistors. On top of the backplane is a 200µm thick layer containing reflective electronic ink from US firm E Ink.

Philips said the shift register formed by the organic TFTs are the largest functional circuits ever made using this process.

The firm is spinning off a firm



called Polymer Vision to develop the roll-up displays. The firm claims it is already producing 5,000 displays of this type a year for research purposes.

Intel claims success with 90nm

Perhaps the first mainstream product manufactured using 90 nanometre (90nm) technology has gone on sale - the latest Pentium 4 processor from Intel.

The microprocessor firm described details of the device, codenamed Prescott, which squeezes 125 million transistors into a 112mm² die.

However, moving to such a small process as 90nm does not reduce power consumption in the same way as it reduces area. The firm had to reserve the smallest transistors - those with the highest leakage - for the critical paths in the design. This amounted to just one per cent of the total.

The processor also has double the on-chip cache memory at 1Mbyte. With its extra circuitry, memory and leakage, Prescott actually draws more power than its 0.13µm predecessor, with a maximum power of 115W.

At launch, the Prescott versions of Pentium 4 will clock at up to 3.4GHz, only marginally higher than existing devices. However, the smaller process gives it legroom, and Intel expects to reach 4GHz by the end of this year.

The firm also recently described core circuits for a 90nm processor operating at 10GHz, which would suggest Pentium 4 will scale to a clock rate of 5GHz.

LED headlights hit the road.

LEDs have made it into the headlight of a mainstream vehicle for the first time - as a daytime driving lamp.

Each headlight of the 12 cylinder Audi A8 6.0 uses five Luxeon LEDs from California's Lumileds Lighting.

"Our engineers have evaluated prototypes with many different LEDs," said Dr. Wolfgang Huhn, general manager of lighting for Audi. "Luxeon is the LED we believe is capable of performing in all capacities to the levels required."

All headlamp components, "including low and high beams, fog lamps and newer adaptive front lighting systems that contribute additional light while turning", can be made using LEDs claims Lumileds. And beam patterns which automatically



change for motorway, town and twisty will be possible, it said. This feature requires multiple LEDs programmed to angle and change intensity and has been mooted in concept vehicles


including the Audi Nuvolari and LeMans, and Ford Model U.

Hella develop the Audi headlight, which also includes discharge lamps in what Hella calls a bi-xenon module.

Hella showed a fully LED headlamp at the IAA 2003 show in Frankfurt.

"The implementation of primary lighting functions in headlamps using LEDs is anticipated by the second half of this decade," said the firm.

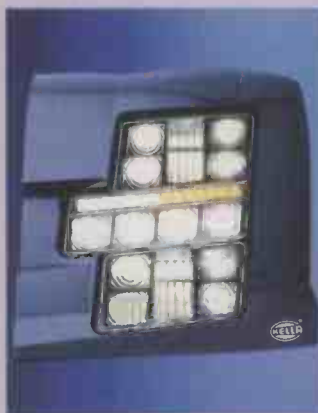In the headlight, dipped beam comes from two five-LED modules split one at the top and one at the bottom. Main beam has four five-LED modules and the daytime running light, which can be dimmed and used as a position light is above, as is the direction indicator.



"An increasing interest is coming from the design departments of automotive manufacturers, now that the light diode offers new potential scope when compared with the conventional headlamp forms and configurations," said Hella. "From a stylistic point of view the LEDs, the preferred and freest of configuration options of many modular lighting systems."

The first LED application in headlamps was in Hella's retrofit LED, xenon and halogen design for the BMW 3 series.

3D photonic crystals from Oxford

Oxford University's physics and chemistry departments have together invented a method of producing 'photonic crystals'.

A photonic crystal is a three dimensional lattice structure with a periodicity similar to that of the wavelength of light. This creates filtering and focussing effects for light of certain wavelengths.


Current technologies for the formation of photonic crystals include the stacking of micron sized polymer balls and deep-etching circles on a surface to

form round rods.

The Oxford technique interferes four laser beams to produce a custom lattice structure in a block of special plastic. Exposure takes only 6ns.

In an extension to the work, "features typical to those expected in working optical devices" have been added.

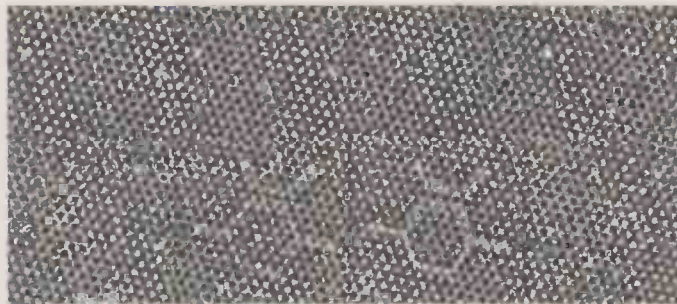Isis Innovation, the intellectual property arm of the university is looking for companies interested in the commercial development of the technology.



Eight photonic crystal layers separated by 0.5µm. Features in the layers relate to four vertical waveguide 'legs' leading to an hexagonal interferometer device where light would pass through and interact with a control signal.

Sharp gets MBE for violet laser

Scientists at Sharp Labs of Europe in Oxford have used molecular beam epitaxy (MBE) to produce a violet laser diode.

This is said to be the first use of MBE to grow such short wavelength - 405nm - devices. It is significant as MBE is a more efficient process than metal organic chemical vapour deposition (MOCVD), which has been the only way of making these devices.


"There is a significant reduction in the consumption of source materials, which can in turn have implications for laser production costs and in reducing the environmental impact of the production method," said Dr Jon Heffernan, head of the project.

"MBE also has advantages in offering more accurate control of the growth than the traditional MOCVD method. Such an advantage may allow the development of new device structures with significantly improved features."

Sharp's first devices are pulsed, but the firm is confident it can move to continuous wave operation, eventually catching up with devices made using MOCVD.

Devices at 405nm are useful as they are specified for Blu-Ray and other standards for high density optical discs. Blue and violet LEDs also form the basis for white LEDs with the addition of a phosphor layer.

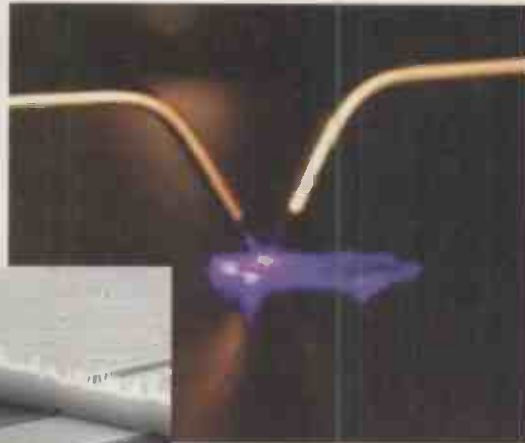Right: Sharp used molecular beam epitaxy to produce 405nm laser diodes.



Left: A photomicrograph showing the violet laser. Light escapes from the dry cleaved face at the end of the laser stripe.

LED internal reflector doubles efficiency



DR-LEDs come in several colours

Omron has introduced an LED package which usefully captures normally-wasted light.

Part of its DR-LED family, the 11mm diameter 2MDR01-11 is aimed at road and rail signaling heads, fixed and variable message signs, large screens in public areas and safety beacons.



Light spilling sideways from the internal chip is captured by two total internal reflections and directed out in the same direction, and with the same divergence, as the main beam.

"Power dissipation is just 123 - 150mW, with up to 20Cd luminous intensity," said Omron.

As well as the 11mm 9 degree version, there is also an 8.5mm 17 degree type.

Typical service is claimed to be 100,000 hours and the package is resilient to moisture, and ultra-violet A and B.

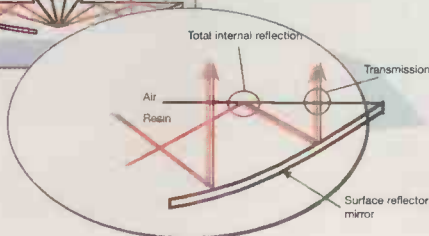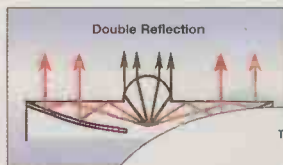Six colours are available with an infrared version planned soon.



Omron's LED captures light that would be wasted

£3.2 billion worth of profit lost every year

The latest Plimsoll Portfolio Analysis - Electronics Manufacturers has revealed that a staggering £3.2 billion of profit is being wasted in the UK Electronics Manufacturers industry every year, due to blatant underperformance and a failure by company leaders to focus on the bottom line.

A quick glance in the latest publication from Plimsoll Publishing Ltd reveals:

- Over a third of companies are making a loss.
- 140 companies are losing money for the 2nd year in row.
- 50% of companies make less than a 3% return on investment.

David Pattison, Senior Analyst at Plimsoll Publishing Ltd, said, "These figures show just how competitive the UK Electronics Manufacturers industry has become. The ability to make a profit is becoming the exception, not the norm."

"Although in the minority, 235 companies delivered a 10% return on investment in 2003, proving that success is

achievable within the industry. This is the level of profitability required to provide a good return to shareholders, pay for investment and help to ensure company longevity."

The latest edition of the Plimsoll Portfolio Analysis - Electronics Manufacturers has given each of the Top 1000 companies in the industry a "Profit Plan" which identifies how each company needs to focus on its bottom line and make more profit. The analysis shows that a staggering £3.2 billion million in extra profit could be created but is currently being unexploited. To succeed in 2004, managers need to learn from the winners by improving company profitability.

The 1150 page analysis examines the last 4 years' profitability, highlighting the winners and losers in this key area of company performance.

Available in paper or electronic format the Plimsoll Portfolio Analysis is available for £305 from www.plimsoll.co.uk or by calling 01642 626400.

2004 PRICE BUSTERS

In line with our policy of producing top quality products at amazing prices we have reduced the price of our best selling items by up to 50%

Don't delay - this is for a limited period only!



**WHEN IT COMES TO POWER
FOR RACKS IT MUST BE**



Olson Electronics Limited
490 Honeypot Lane, Stanmore,
Middlesex HA7 1JX
Fax: 020 8952 1232
e-mail: sales@olson.co.uk
http://www.olson.co.uk

**SEND FOR YOUR
NEW FREE CATALOGUE**

19" Horizontal 2U High

4	Sockets	13A/4/R	@	£22.65 ea. Nett
5	Sockets	13A/5/R	@	£24.99 ea. Nett
6	Sockets	13A/6/R	@	£27.57 ea. Nett
7	Sockets	13A/7/R	@	£30.96 ea. Nett

Vertical

4	Sockets	T13A/4	@	£20.25 ea. Nett
6	Sockets	T13A/6	@	£24.60 ea. Nett
8	Sockets	T13A/8	@	£31.47 ea. Nett
10	Sockets	T13A/10	@	£34.95 ea. Nett
12	Sockets	T13A/12	@	£39.62 ea. Nett

Vertical Left Hand with Switch

4	Sockets	4LH/MS	@	£20.25 ea. Nett
5	Sockets	5LH/MS	@	£23.37 ea. Nett
6	Sockets	6LH/MS	@	£24.60 ea. Nett
8	Sockets	8LH/MS	@	£31.47 ea. Nett
10	Sockets	10LH/MS	@	£34.95 ea. Nett
12	Sockets	12LH/MS	@	£39.62 ea. Nett

Vertical Right Hand with Switch

4	Sockets	4RH/MS	@	£20.25 ea. Nett
5	Sockets	5RH/MS	@	£23.37 ea. Nett
6	Sockets	6RH/MS	@	£24.60 ea. Nett
8	Sockets	8RH/MS	@	£31.47 ea. Nett
10	Sockets	10RH/MS	@	£34.95 ea. Nett
12	Sockets	12RH/MS	@	£39.62 ea. Nett

CALL OUR SALES HOTLINE

020 8905 7273

This promotion cannot be used in association with any other discount or offer. Olson Electronics Ltd reserve the right to change the price without prior notice.

A pseudo-sine wave inverter

Running ac mains powered electronic equipment from an inverter is not always as straightforward as one might think. **Ian Hickman** explains why, and presents a demonstrator design which may be developed to suit any application.

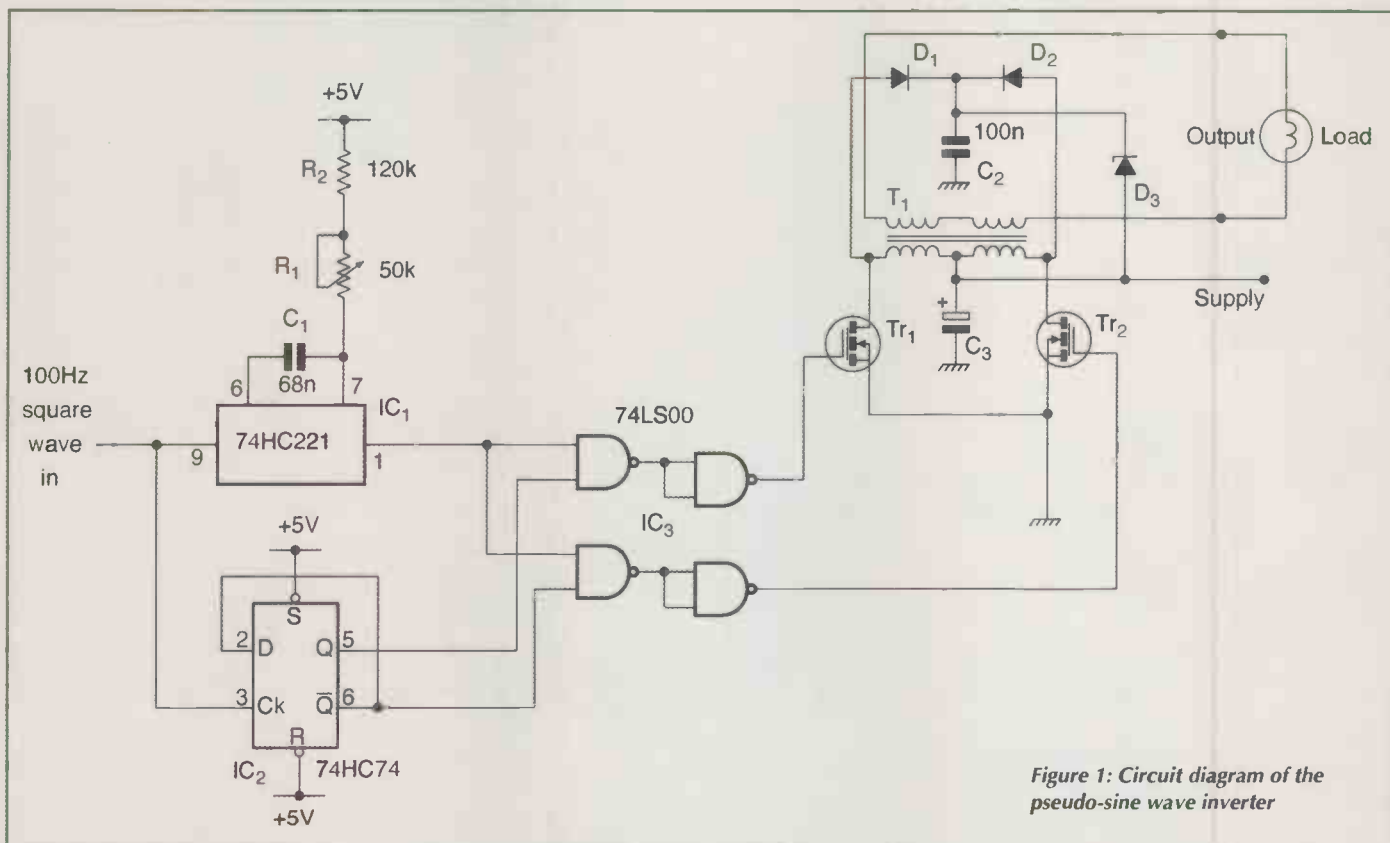


Figure 1: Circuit diagram of the pseudo-sine wave inverter

Back in the 1980s I was conducting some MOD contract tests on direction finding antennas in the middle of Thorney Island, a Class 1 antenna test site on the south coast of England. At one end of the test link, equipment was powered by a small portable diesel generator which seemed to hammer away all day on next to no fuel. At the other end, the equipment was powered by an inverter, run from the battery of the test wagon, or at least that was the plan. Unfortunately, the test signal generator, a Marconi TF2018, kept

falling over, with its software tied up in knots. On investigation, this turned out to be due to the '240V ac' output of the Racal inverter. The output certainly read 240V or thereabouts on the ac range of an AVO and it was only on viewing the inverter output with an oscilloscope that the problem became apparent. The inverter's output waveform was a $\pm 240V$ peak square wave, with just a very modest amount of filtering to file down the sharp edges slightly. With a modern piece of kit, designed to run from any ac voltage in the range 95V to 260V, there would

have been no problem. But the signal generator used a conventional mains transformer, rectifiers, smoothing and regulators. It expected to see a 240V rms sinusoidal mains waveform, with a peak voltage of $\sqrt{2} \times 240 = 339V$ peak. Fed with a 240V square wave, the raw voltage to the regulators, from the rectifier and smoothing capacitor, was inadequate, and the regulator outputs consequently unregulated.

It is an unfortunate fact of life, that for a 240V rms square wave, the peak voltage is $\pm 240V$, not $\pm 339V$; since for a square wave, the rms

voltage simply equals the peak voltage. It is therefore unsuitable for powering the older generation of equipment fitted with a conventional mains transformer and regulated power supplies.

I do not possess a TF2018, but have various other signal generators, oscilloscopes and spectrum analysers of that generation, all perfectly functional. There are plenty of such items advertised in these pages, all at very advantageous prices. However, should you want to operate them away from ac mains, an inverter with a square wave output is unsuitable. It is not practical to design such an inverter with a higher peak output voltage, as a mains transformer run from it might be damaged, for reasons explained in the box. But it is possible to design a 'pseudo sine wave' inverter, along much the same lines as a square wave output inverter, and such an experimental design is described below.

Whilst being quite a low power design, it is readily modified to use other transformers of higher rating.

Pseudo sine waves

As the details in the box show, a square wave is not a very suitable output waveform for an inverter - indeed it could hardly be less like a sine wave. Whilst a stepped approximation, such as the output from a direct digital synthesiser, can come as close as one likes to a sine wave, for an economical design of inverter, a very crude approximation suffices. This is just what the circuit of Figure 1 provides. It is driven from a 100Hz square wave input, which is fed both to a monostable multivibrator, and to a D type flip-flop connected as a divide-by-two circuit. For each of the input pulses, the monostable provides an output pulse whose width is adjustable by means of preset potentiometer R1, connected as a variable resistor.

These output pulses are applied to two NAND gates, which are enabled on alternate half cycles by the Q and /Q outputs of the divide-by-two circuit. Thus Tr₁ and Tr₂ are turned on, on alternate half cycles, energising the low voltage windings of transformer T₁. The transformer used is a 30VA rated toroidal mains transformer with two 120V primary sections and two 15V secondary sections. In this application it is used 'back to front', to provide a 240Vac output from a low voltage dc supply. The rated peak secondary voltage is of course $15\sqrt{2} = 21.2V$, and allowing for a small volt drop in the MOSFETs, I fed the circuit with a

22V dc supply - apart from the logic, which was run from +5V dc. A 15W 240V bayonet cap lamp was used as a convenient load.

Circuit details

During the period when one of the MOSFETs is ON, the magnetising current in the corresponding low voltage section will increase linearly, at a rate proportional to the supply voltage. When the MOSFET is turned off, the resultant stored energy must go somewhere, and D₁ and D₂ are used as 'snubbers', to prevent enormous and potentially damaging peak drain voltages. The positive voltage excursion is limited by a snubber diode, which diverts the 'flyback' energy into the capacitor C₂. This capacitor discharges via the 22V Zener diode D3, back into the supply (which is decoupled by 1000µF capacitor C3), so that half of the flyback energy is recovered and reused.

Figure 2 shows the drain waveform of one of the MOSFETs (upper trace), and the corresponding gate drive waveform. The latter is less than +5V, being LSTTL derived, with limited drive capability, and thus not ideal. Consequently, the drain voltage does not fall immediately to the MOSFET's saturation voltage, an effect clearly visible in the upper trace. The oscilloscope brightness has been deliberately advanced, so that the switch-off spike is clearly visible at 5ms per division, even though it is only around a microsecond wide.

The TEK475A used is an old instrument, but still exhibits a high 'writing speed'.

Figure 3, at a higher timebase speed of 2µs per division, shows (upper trace) the turn-off spike, caught at about +50V by the snubber diode. In this case, the diodes D₁ and D₂ were 1N4148s; these are fast small signal diodes, exhibiting a substantial forward volt drop at the current involved.

Figure 4 shows the same thing but with D₁ and D₂ now type 1N4006. The spike is now limited to +48V due to the lower diode forward volt drop, but the subsequent history of the spike is quite different, presumably due to the longer storage time of the slower diode. The ideal component for the snubber diode would be a fast low forward volt drop type, but the demonstrator circuit was implemented entirely with devices from stock, and a more suitable diode type was not to hand. The same comment applies to the MOSFETs Tr₁ and Tr₂, which were type BUZ10, with a V_{dss} drain voltage rating of only +50V!

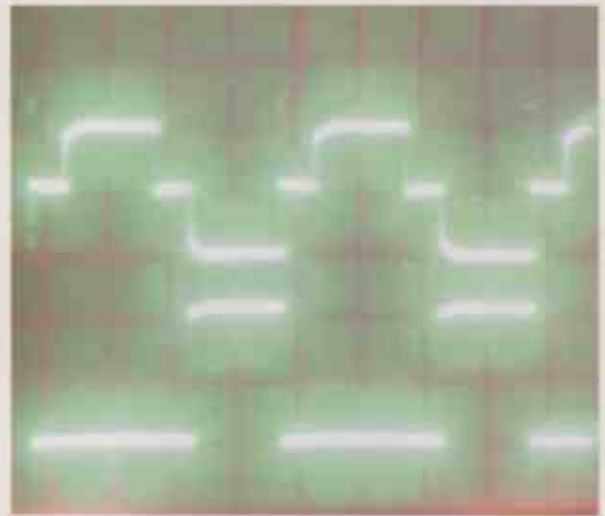


Figure 2 Tr₁ drain waveform (upper trace), 20V/div; Tr₁ gate waveform (lower trace), 2V/div, both at 5ms/div.

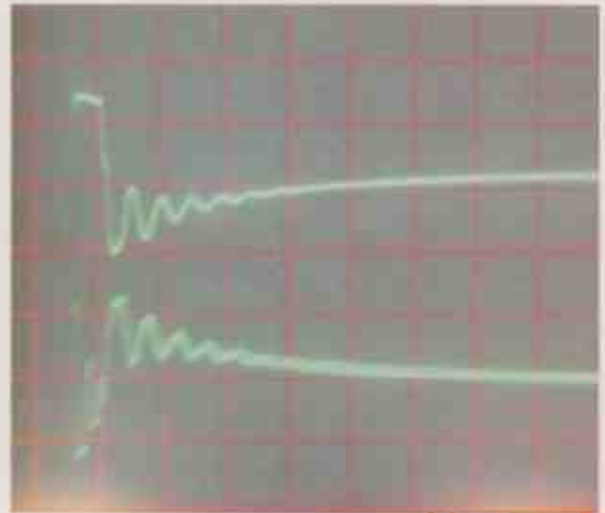


Figure 3: As Figure 2 but 2ms/div. Snubber diodes 1N4148

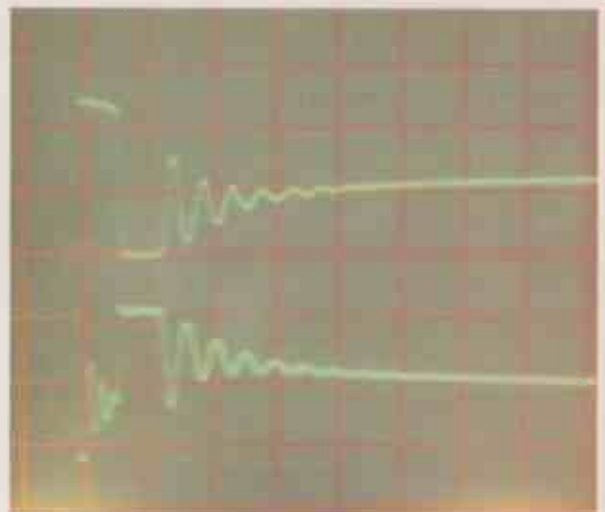


Figure 4 (below) As Figure 2 but 2ms/div. Snubber diodes 1N4006

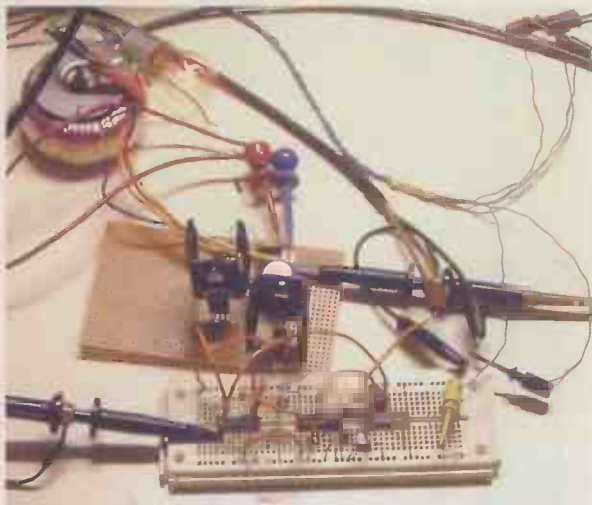


Figure 5: Experimental set-up of the demonstrator circuit.

As a temporary project, most of the circuitry of the demonstrator was put together using plugboard (Experimenter 300™), with just the MOSFETs, snubber diodes, C_2 and the $1000\mu\text{F}$ C_3 supply decoupling capacitor mounted on 0.1 inch matrix copper strip board, as shown in Figure 5.

The lit lamp shows the circuit is running, but the supply voltage was wound down for the photograph, to prevent the lamp “blinding” the camera. In the event, with just a 15W load, the twisted-vane heatsinks on the MOSFETs could have been dispensed with as they showed a negligible temperature rise.

Conclusions

The demonstrator circuit shows that an inverter circuit providing the same peak and rms voltage as 240V ac mains can be built using a very simple design. To a close approximation, the level of losses in a transformer used ‘back to front’ like this, can be expected to be the same as if it were used the usual way round. The additional losses, due to the MOSFETs and snubbers, are small, in view of their high speed switching and the low frequency of operation. Since 22V dc is not a very convenient supply voltage, a custom wound transformer will normally be preferred. MOSFETs with a V_{dd} margin suitable for the particular supply voltage will need to be selected, and a type fully enhanced at $+5\text{V } V_{\text{gs}}$ will be convenient.

The 100Hz drive waveform can simply be a 555 oscillator circuit, running at 200Hz and driving the other half of the 74HC74 flip flop. The pulse width for a 339V peak 240V rms output has been shown to be 5.01ms.

This is so close to 5.00ms that the 74HC221 multivibrator can be omitted and the gate drives produced simply by gating the 100Hz square wave. ●

Mains Transformer

A mains transformer draws a ‘magnetising current’, which is out of phase with the applied primary voltage, lagging it by 90° or a quarter of a cycle. Consequently, over a half cycle, as the mains voltage E increases from zero to a positive maximum and then falls again to zero, the magnetising current I_m rises from its negative peak value $-I_m$, through zero, to its positive peak value $+I_m$. This is illustrated in Figure A, where the blue trace represents both the magnetising current, and the flux. Both are in quadrature with the applied primary voltage, but note that even off load, the total primary current will not be exactly in phase with the flux. This is because there is also a component in phase with the voltage, representing a resistive component, due almost entirely to the core loss.

The flux Φ is in phase with I_m and consequently increases from $-\Phi_m$ through zero to $+\Phi_m$. Thus to support half a cycle of a 50Hz sine wave of 339V peak (10ms duration), a flux change of $2\Phi_m$ is necessary. The mains transformer designer will have designed the transformer so that, off load, at minimum mains frequency and maximum mains voltage tolerance, Φ_m is still safely below saturation of the transformer’s core.

If the mains voltage were twice as much, Φ_m would need to double, or if the frequency were 25Hz rather than 50Hz, then again, Φ_m would need to double. In other words, Φ_m is proportional to the voltage times the half-period, or the ‘ $E \times t$ product’. This is the case, whatever the waveform. In the case of a sine wave, the $E \times t$ product is represented by the coloured area in Figure B. A handy result to remember is that the area under half a cycle of a sine wave is $2/\pi$ times the surrounding rectangle. So from Figure B, the $E \times t$ product for 240V 50Hz mains is $(339 \times 10) \times 2/\pi = 2158\text{V.ms}$ or 2.158 volt.seconds.

Figure B also shows half a cycle of a waveform (red trace) with the same peak voltage and the same $E \times t$ product as 240V ac mains. For this simple flat top pulse waveform, given the peak voltage is 339V, the pulse duration must be $(2158/339)\text{ms} = 6.37\text{ms}$. An inverter with this waveform could safely power an instrument such as the TF2018, providing adequate rectified supply voltage without exceeding the permitted $E \times t$ product of the mains transformer. However, for general use, a rather small pulse width should be used. This is because for general use, a pseudo sine wave inverter should have not only the same peak voltage as ac mains, but also the same rms value. With 6.37ms pulses, the mean square value $339^2 \times 6.37/10 = 732047\text{V}^2$ so the root mean square voltage is $\sqrt{73205} = 270.6\text{V}$, or rather excessive! For a peak voltage of 339V, a pulse width of 5.01ms gives an rms value of 240V. Such a waveform has an $E \times t$ product of only 1.70 volt.seconds, within what a 240V 50Hz transformer can stand, by a large margin. On the other hand, an inverter providing a $\pm 240\text{V}$ square wave output will subject a mains transformer to an $E \times t$ product of 2.4 volt.seconds. This is 11% greater than the figure for which the primary winding of a 240Vac transformer is designed.

Figure A Positive half cycle of 240Vac mains (red, scale -340V to +340V); corresponding magnetising current and flux (blue, scales not shown).


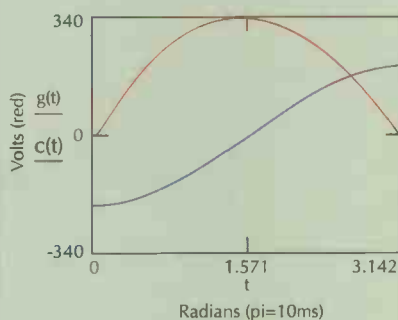


Figure B Indicating the volt.second product of half a cycle of 240Vac mains, and a pulse waveform with the same volt.second product.

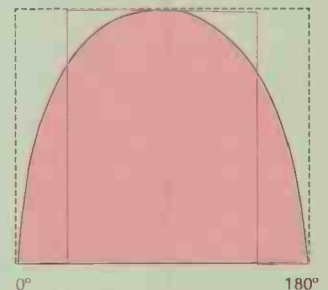


Easy-PC for Windows

World Beating Value in PCB Design Software

from
£97

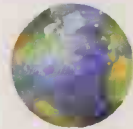High performance Windows based PCB Design Capture, Simulation and Layout software at prices you'd expect from your local computer store!



NEW! in Easy-PC 7

- Library Databook
- Step and repeat plotting
- Swap Connection Mode
- Dimensioning
- Copy to Metafile
- plus much more.....

Stop press... by customer demand, now with Tsien Boardmaker 2 design import...

Number One Systems delivers true 32 bit Windows software applications including features that a few short years ago would only have been available in software tools priced in the thousands!

Test drive Easy-PC and Easy-Spice for yourself and be prepared to be amazed at the super value...

Call for a brochure, price list and demo CD on +44 (0)1684 773662 or email sales@numberone.com



No1 Number One Systems

Number One Systems
Oak Lane, Bredon
Tewkesbury, Glos GL20 7LR
United Kingdom

or download from
www.numberone.com

Complete and fax the coupon to: +44 (0) 1353 654400

I wish to subscribe for one year to Electronics World:

Price UK £38.95 O/S £64.50
 US\$100.62 Euro 102.55

Please tick preferred method of payment

I enclose a cheque payable to Highbury Business Communications Ltd

Please invoice me Purchase No

(NB Purchase order must be included to validate invoice)

Please charge my: Master Card/Visa/Amex/Diners
Club/Switch/Delta (please circle)

Card No _____

Expiry Date _____

(Switch/Delta Only) Valid from / Issue Number

Signature _____

Date _____

Name _____

Job Title _____

Company _____

Address _____

Postcode/Zip _____

Country _____

Telephone/Fax _____

E-mail _____

Please tick here if you do not wish to be contacted by other businesses either by

Mail Telephone Fax E-mail

Please return to: Highbury Subscription Services,

Link House, 8 Bartholomew's Walk, Ely,

Cambridgeshire CB7 4ZD, UK.

Email: wss@wyverncrest.co.uk

(Quote ref: EW1)

ELECTRONICS WORLD


HIGHBURY
Business Communications
A DIVISION OF WYVERN CREST COMMUNICATIONS LTD

The world's leading electronics magazine, **Electronics World** is a technology-transfer magazine for the global electronics industry. It covers research, technology, applications, products and patents in areas such as audio, R.F., components, CAD design, circuit building, PC & Micro based products, tests & measurement, semiconductors, power sources and much, much more....




Make sure you receive your regular monthly copy by subscribing today.....

Analogue and digital i/o via the USB port

Following on from Colin Attenborough's Wide digital i/o from the USB port in EW November 2002, this article adds analogue input and output to the basic design

This article shows how to get 16 bit digital i/o and 12 bit analogue i/o through a computer's USB port. It's an extension of my article printed in the November 2002 edition of Electronics World, which showed how to get digital signals in and out of a PC via the USB port. The complexities of USB were hidden from the user by using a Gigatechnology module which accepts USB signals and provides parallel input/output data. As before, I've provided Visual Basic software to control the hardware (see the picture of the user interface above; this software is available from Electronics World as an email and will be included on the EW 2004 archive disc when released, both as source code so that those with Visual Basic can tinker, and as a compiled version so that those without Visual Basic can still use the hardware. Also as before, I've clocked data in and out of the USB module serially, sacrificing speed for simplicity compared to a parallel design.

Sticking with the serial architecture, I've used the LTC1286 ADC and LTC1451 DAC devices (see Electronics World December 1997). One problem is that while the digital input devices can be clocked at as high a rate as the USB module can handle, the LTC1286 has a maximum clock rate of 200kHz. If I'm to use the same clock source for the digital and analogue input, the clock rate must be reduced. (Yes, it would be possible to use different clock rates for the analogue and digital inputs, but only at the expense of increased complexity.)

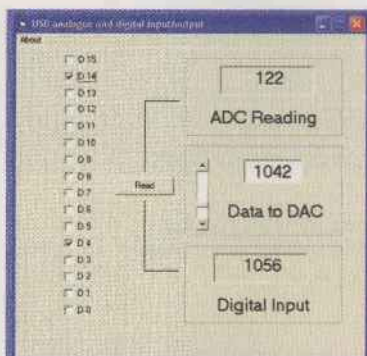

The USB module

The Future Technology Devices International company (<http://www.ftdichip.com>) produces a range of integrated circuits which form the heart of a USB interface.

Two other companies, DLP (<http://www.dlpdesign.com>) and Gigatechnology (<http://www.gigatechnology.com>) make life easier by putting the surface mount FTDI integrated circuits with their associated components in modules with 0.1" pin spacing. This project uses the Gigatechnology USB-02 module; I've used the DLP module with equal success.

The modules take in the USB bus and provide byte wide bidirectional signals. Four other signals control data flow. To take data from the PC, wait until the *RXF output is high and take the *RD input low; data appear on the bidirectional pins. After *RD goes high, the *RXF output goes high. Repeat the process until all the data have been read. Data are sent to the PC on the negative-going edge of the *WR input; the *TXE output goes high in response. When it goes low again, more data can be sent. (In this project, the data rate is low enough for *TXE to be ignored - see the main text.)

Data output...

In outline, to send data to the USB module from the PC:


- Open the device
- Send a string representing the data to be sent from the PC
- Close the device

When sending data to the module from the PC, the Visual Basic program detects changes in the check boxes representing digital data, or changes in the setting of the scroll bar that defines the output of the ADC. The program assembles a string where bit 5 and bit 2 of each character represent the analogue and digital data to be sent. Bit 3 represents a clock signal to clock the data into the 74HC595's input registers and the LTC1451 register. After the data proper have been sent, a further two characters follow. These raise and lower bit 1 to clock the data into the output of the 74HC595s, and to drive the *CS input of the LTC1451.

Although the DAC is a 12 bit device, it receives 16 clock pulses. It still works correctly because the *CS input is appropriately timed. Because it accepts data MSB first, bit 0 must be sent at the same time as bit 16 of the digital output word, with bit 11 being sent at the same time as bit 4 of the digital output word - this is accommodated by the software.

The ADC has an internal 2.048 volt reference, and a times two amplifier - thus the output in millivolts is conveniently equal to the code.

Figure 1: USB module and control circuitry.

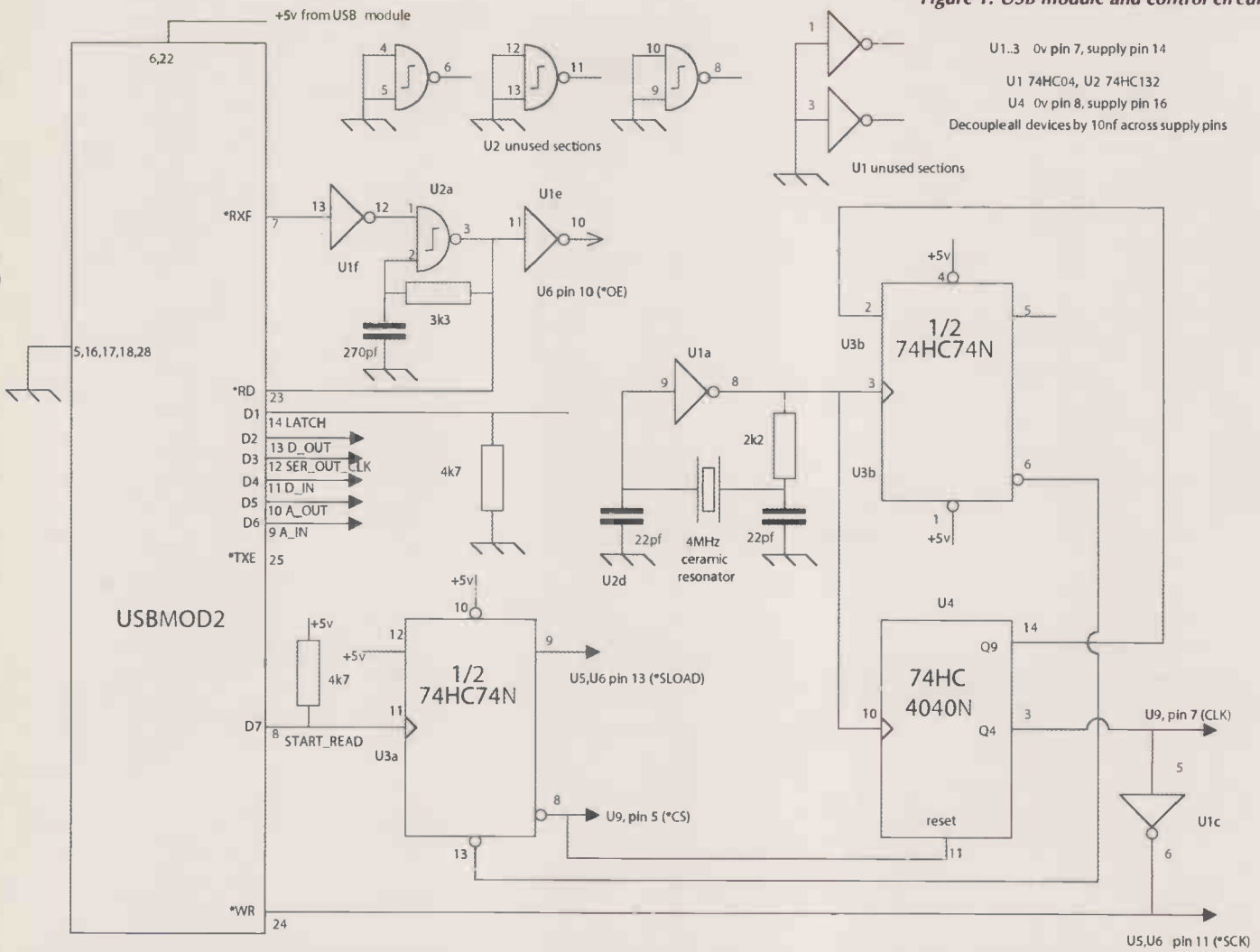

Software

The software comes in three parts and is available by contacting Caroline Fisher at EWadmin@highburybiz.com;

- The Visual Basic code which is specific to this project
- A compiled version of the code so you can use the project even if you don't have Visual Basic
- A .zip file containing a dynamic link library (DLL) which lets the Visual Basic access the functions needed to control the USB module, and also drivers for the module. This can also be downloaded from the Future Technology Devices International website.

Unzip the DLL/driver file. The first time you connect the USB module, you'll be asked where to find the driver. Browse to the directory where you unzipped it, and let the system install it.

(Disconnect your machine from its internet connection temporarily while installing the driver, so the system listens to your choice of what driver to install.)

Figure 2: Digital I/O registers.


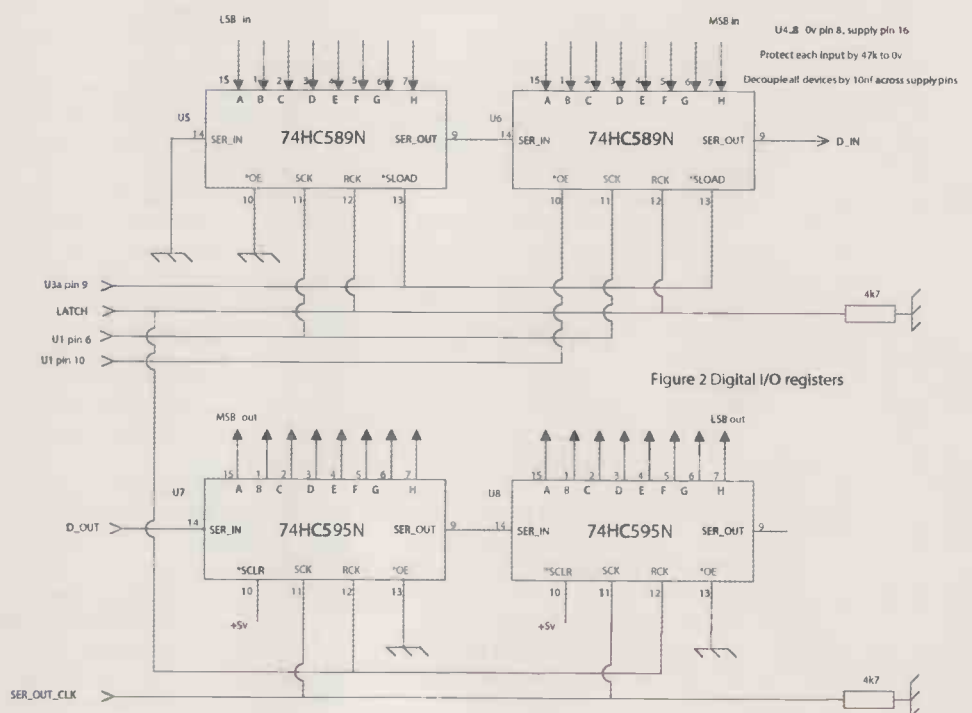


Figure 3: Analogue I/O circuitry

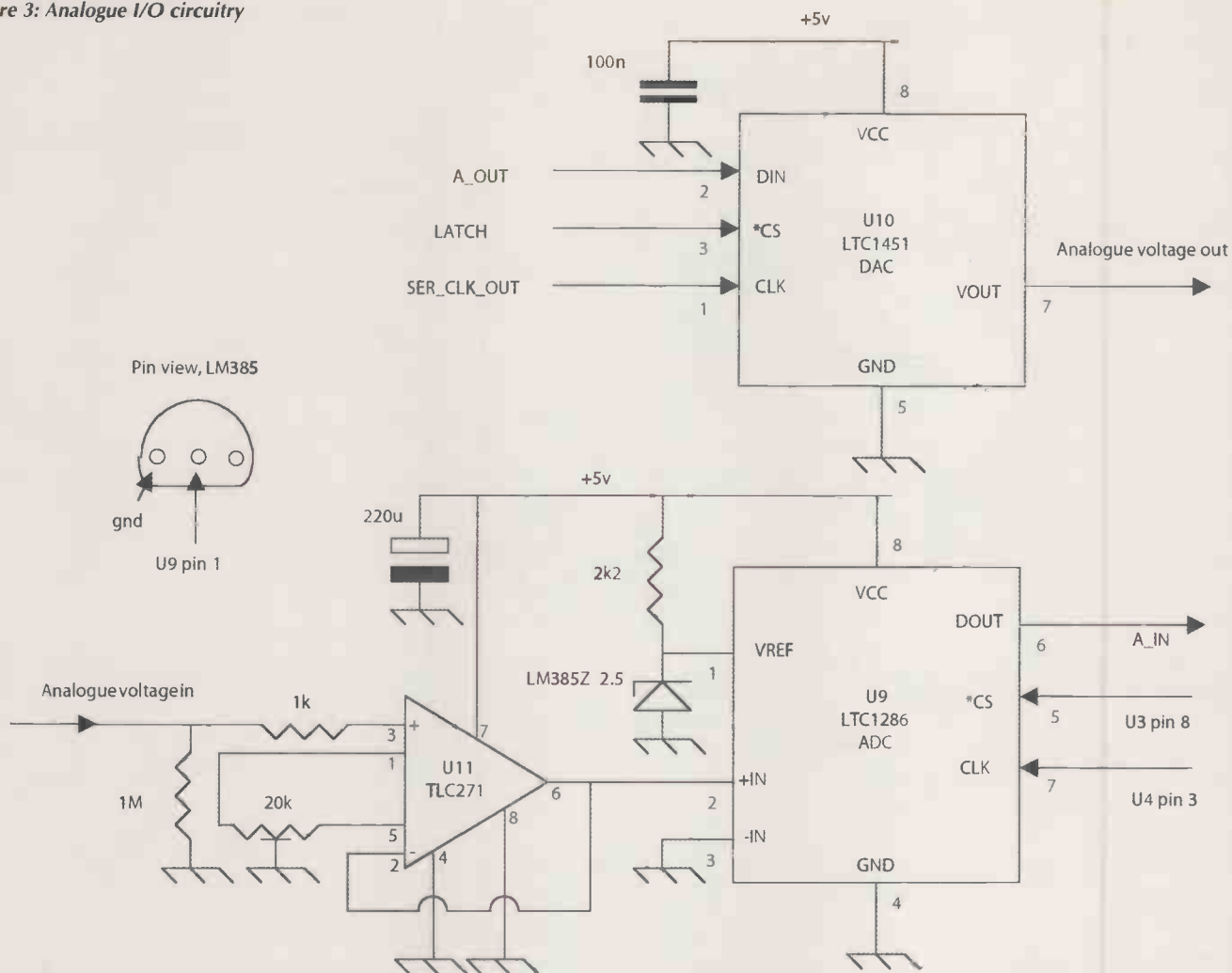

...and input

- Open the device
- Read a string representing the data from the module
- Close the device

To read data into the PC from the module, the program assembles a string which latches data into the input registers of the 74HC589 devices – again using bit 1. Subsequent characters of the string pulse bit 7 low and high again, clocking U3a, and sending its Q output to 1. The signals at the Q and *Q outputs of U3a control the *SLOAD inputs of the 74HC589 devices and the *CS input of the LTC1286. It also removes the reset signal from U4, allowing it to run until its Q9 output goes to logic 1, resetting U3a via U3b. While U4 is running, its Q4 output provides 16 clock edges to clock in data from the LTC1286. The inverse of this signal also clocks the 74HC598 and the USB module's *WR input via an inverter- the 74HC589 and the LTC1286 ADC shift data on different polarities of clock edge, and the

circuit ensures that the USB module accepts data mid-way between active clock edges.

The analogue and digital data from the module are extracted from bits 6 and 4 respectively of the characters in the string returned by the module. The ADC gives the most significant bit (D11) of its output on the fourth clock pulse after the fall of *CS; other bits follow, with the least significant bit (D0) occurring during the fifteenth clock pulse. But we're giving it sixteen clock pulses, for commonality with the digital input; during the sixteenth clock pulse, the ADC outputs D1 again. Therefore software discards the last bit of the conversion received by the USB module, and shifts the remaining bits to the right.

Because the clock rate must be lower than in the digital-only case, there's no need for the *TXE signal from the module - the 200ns 'wait I'm reading in the last byte' pulse will have disappeared long before the next byte is presented, eight microseconds later. It've also attempted a little more elegance by

abandoning the Schmitt-based oscillator and using an oscillator based on a ceramic resonator sustained by a CMOS inverter. There's nothing particularly special about the use of a 4MHz oscillator rate; if you use a different frequency, you may need to choose different outputs of U4 to get a clock rate below 200kHz for the ADC.

The ADC is preceded by a unity-gain op-amp to give high input impedance and to isolate the input from noise generated in the ADC; the potentiometer shown compensates for amplifier offsets, and should be set so that the ADC reads zero for zero input voltage. As the ADC is a 12 bit device, its output code is $4096 * V_{in} / V_{ref}$ V_{ref} is 2.5 volts, provided by the LM385Z- 2.5.

Acknowledgements
I'm grateful to my employers, Cambridge Consultants Limited, for permission to publish this article- and to FTDI for their assistance.

FRUSTRATED!

Looking for ICs TRANSISTORS?

A phone call to us could get a result. We offer an extensive range and with a World-wide database at our fingertips, we are able to source even more. We specialise in devices with the following prefix (to name but a few).



2N 2SA 2SB 2SC 2SD 2P 2SJ 2SK 3N 3SK 4N 6N 17 40 AD
ADC AN AM AY BA BC BD BDT BDV BDW BDX BF
BFR BFS BFT BFW BFX BFY BLY BLX BS BR BRX BRY BS
BSS BSV BSW BSX BT BTA BTB BRW BU BUK BUT BUY
BUW BUX BUY BUZ CA CD DX CXA DAC DG DM DS
DTA DTC GL GM HA HCF HD HEF ICL ICM IRF J KA
KIA L LA LB LC LD LF LM M M5M MA MAB MAX MB
MC MDA J MJE MJF MM MN MPS MP5A MP5H MP5U
MRF NJM NE OM OP PA PAL PIC PN RC S SAA SAB
SAD SAJ SAS SDA SG SI SL SN SO STA STK STR STRD
STRM STRS SV1 T TA TAA TAG TBA TC TCA TDA TDB
TEA TIC TIP TIPL TEA TL TLC TMP TMS TPU U UA
UAA UC UDN ULN UM UPA UPC UPD VN X XR Z ZN
ZTX + many others

Please ask for our Free CD Rom STOCK LIST.

WE STOCK A MASSIVE RANGE OF COMPONENTS!

Mail, phone, Fax, Credit Card orders & callers welcome.



Cricklewood Electronics Ltd

40-42 Cricklewood Broadway, London NW2 3ET

Tel: 020 8452 0161 Fax: 020 8208 1441

www.cricklewoodelectronics.co.uk

E-mail: sales@cricklewoodelectronics.com

WATCH SLIDES ON TV MAKE VIDEOS OF YOUR SLIDES DIGITISE YOUR SLIDES

(using a video capture card)



"Liesgang diat" automatic slide viewer with built in high quality colour TV camera. It has a composite video output to a phono plug (SCART & BNC adaptors are available). They are in very good condition with few signs of use. For further details see www.diatv.co.uk
.....£91.91+ vat = £108.00

Board cameras all with 512x582 pixels 8.5mm 1/3 inch sensor and composite video out. All need to be housed in your own enclosure and have fragile exposed surface mount parts. They all require a power supply of between 10 and 12v DC 150mA.

47MIR size 60x36x27mm with 6 infra red LEDs (gives the same illumination as a small torch but is not visible to the human eye).....£37.00 + vat = £43.48

30MP size 32x32x14mm spy camera with a fixed focus pin hole lens for hiding behind a very small hole.....£35.00 + vat = £41.13

40MC size 39x38x27mm camera for 'C' mount lens these give a much sharper image than with the smaller lenses.....£32.00 + vat = £37.60

Economy C mount lenses all fixed focus & fixed Iris

VSL1220F 12mm F1.6 12x15 degrees viewing angle.....£15.97 + vat = £18.76

VSL4022F 4mm F1.22 63x47 degrees viewing angle.....£17.65 + vat = £20.74

VSL6022F 6mm F1.22 42x32 degrees viewing angle.....£19.05 + vat = £22.38

VSL8020F 8mm F1.22 32x24 degrees viewing angle.....£19.90 + vat = £23.38

Better quality C Mount lenses

VSL1614F 16mm F1.6 30x24 degrees viewing angle.....£26.43 + vat = £31.06

VWL813M 8mm F1.3 with Iris 56x42 degrees viewing angle.....£77.45 + vat = £91.00

1206 surface mount resistors E12 values 10 ohm to 1M ohm 100 of 1 value £1.00 + vat
1000 of 1 value £5.00 + vat

866 battery pack originally intended to be used with an orbitel mobile telephone it contains 10 1.6Ah sub C batteries (42x22dia the size usually used in cordless screwdrivers etc.) the pack is new and unused and can be broken open quite easily.....£7.46+vat = £8.77



Please add 1.66 + vat = £1.95 postage & packing per order

JPG ELECTRONICS

Shaws Row, Old Road, Chesterfield, S40 2RB

Tel 01246 211202 Fax 01246 550959 Mastercard/Visa/Switch

Callers welcome 9:30 a.m. to 5:30 p.m. Monday to Saturday

A QUANTUM LEAP IN EMBEDDED CONTROLLERS

Quick FIRE

SUPERCONTROLLERS

Our range provides:-

- The fastest 68000 based Core up to 66 Mhz.
- Extensive I/O:- Serial, IrDA, SPI, I²C, Analogue, Timers/Counters, RTC, etc.
- Large Memory Capacity:- Flash, SRAM, DRAM.
- Supports:- Mono & Colour LCD's, Touch Panels & Keypads, Very Low Power.

ALSO LOW COST

DEVELOPMENT

- Target easily & quickly.
- Full ANSI 'C' compiler, assembler & linker all Windows32 based.
- Source Level Debug.
- Full Driver Support with Libraries.
- Real Time Multitasking OS with a free run time licence.
- Free Unlimited email support.

www.cms.uk.com

see our web site for full details

CAMBRIDGE MICROPROCESSOR SYSTEMS LTD



Unit 17-18 Zone 'D' Chelmsford Rd. Ind. Est.
Great Dunmow, Essex CM6 1XG

Telephone: 01371 875644

email: sales@cms.uk.com

Access methods of cellular telecommunications systems

It is now over twenty years since the first cellular phone systems were launched. By today's standards the early systems were expensive, coverage was poor and so was their performance. Furthermore when some of the old phones are seen on the movies they see incredibly large, especially when compared to the phones that are in widespread use today. Ian Poole gets connected.

Since the early days of cellular phones there have been many major developments, and more are happening all the time. Nowadays the developments of the cell phone systems are categorised as occurring in three main phases or generations. The first generation (1G) phone systems were the analogue ones that were used in the 1980s and early 1990s. They are still in widespread use in the USA today. These included systems such as TACs (Total Access Communication System) that was used in the UK, AMPS (Advanced Mobile Phone System) in the USA, and NMT (Nordic Mobile Telecommunications) in Scandinavia. They were used in many other countries world wide, but there was also a proliferation of other systems that were also used.

These phone systems were very successful and it soon became necessary to look at ways to utilise the valuable spectrum allocations more efficiently. Accordingly new digital systems were developed. In Europe a system known as GSM was introduced. Initially the letters stood for Group Speciale Mobile, but as its use spread worldwide and the meaning was changed to Global System for Mobile telecommunications. Indeed today the system is by far the most widespread technology with nearly a billion users accounting for 72% of the world market. The system offers many facilities including the use of SIM cards to hold users identities whilst being able to easily swap phones. One of the facilities that has grown astronomically is the use of text



messages with around 24 billion messages sent each month and its use is still growing.

The GSM system adopted a totally different approach to that used by the analogue systems and included a 200kHz channel spacing. In the US a different approach was used when they developed their digital system. The approach they adopted was to make it easier to migrate from the analogue to the digital system. It borrowed many features from GSM, although it did not possess many of the facilities available in GSM such as SIM cards. The system was known under several names including DAMPS (Digital AMPS), USDC (US Digital Cellular), and finally TDMA (Time Division Multiple Access) - as this is the technique that the system uses. In fact

Right: Mobile phone base stations are now small and can be installed very easily in many areas of our towns, cities and countryside (pictures courtesy Nokia)

today it is normally referred to as US TDMA. The system operates on the same 30kHz channels that AMPS uses and this enables it to operate more easily along side the original analogue AMPS system.

In Japan they have a system that is based very closely on the US system, but goes by the name PDC. This can stand for either Personal Digital Cellular and Pacific Digital Cellular - both names as used to refer to this system. Although it has some minor differences from the US-TDMA system, is very similar.

Some time after GSM and TDMA were established, a totally new second-generation system was launched. This was to shape the whole future of cellular telecommunications. It was developed by a then little known California based company named Qualcomm who had been working on spread spectrum techniques for the US Government. The system known as CDMA (Code Division Multiple Access) used a new method of servicing the large number of subscribers to the base station that is discussed later.

The system that went under the trade name cdmaOne underwent its first commercial launch by Hutchison Telecom in Hong Kong in September 1995. Then in March of the following year the first service was launched in the USA and by December 1997 there were over 8 million cdmaOne subscribers.

By the mid 1990s, voice services were well established and new opportunities were seen for developing data services. However to achieve this, significant enhancements were needed. Although this was the main thrust of the third generation networks, these took a long time to develop and interim solutions were introduced, that allowed data services with lower speeds. For GSM networks the GPRS (General Packet Radio Service) was launched. Using what is termed 'packet switching' where individual packets of data can be routed to and from a particular phone instead of circuit switching where a complete circuit is switched all the time for a given user, this enabled much more efficient use to be made of the spectrum and higher data rates to be achieved. A further migration to EDGE (Enhanced Data rates for GSM Evolution) used a new form of modulation to increase the data rates still further.

There are currently two main contenders for third generation systems, both of which use CDMA. The GSM system is migrating to UMTS (Universal Mobile Telecommunications System), which is also known as W-CDMA (Wideband CDMA). Although it requires a

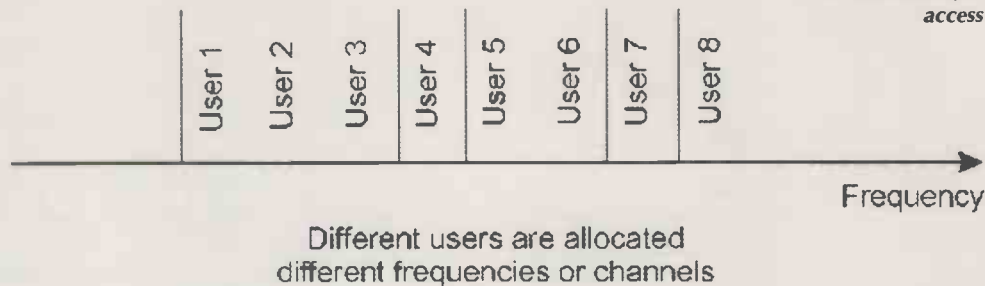


Figure 1 Frequency division multiple access

significant upgrade in infrastructure and W-CDMA phones cannot operate on GSM networks, it is expected to have widespread uptake in the GSM areas. Phones are expected to be dual mode so that they can operate on both networks, handing over between W-CDMA and GSM as required by the coverage although this is causing some problems at the moment.

The cdmaOne system has an evolutionary migration to the full 3G standard. The first step is CDMA2000 1X. This provides data at speeds up to just above 300kbps and is technically termed a 3G system. However there are two alternatives to provide the full 3G data rates. The first is CDMA2000 1xEV-DO. This stands for Evolution Data Only. As the name suggests the idea is that this only provides data services, if voice is required then this is handled on a separate 1X channel. However the full data and voice service is catered for with the CDMA2000 1xEV-DV system which provides full voice capability and data up to 3.1Mbps.

Multiple Access Systems

In order to enable a cellular system to operate, it must allow many users to access the system simultaneously. This is one of the key elements of any cellular system, and as they have migrated through the different

generations different approaches have been used.

The first analogue systems used a technique called FDMA (Frequency Division Multiple Access). Using this scheme different users are allocated different channels, and within any one cell, each channel can only be used once. The system has a control channel that all phones can access and information is passed to the mobile to enable it to move to the required channel.

With channel spacing of typically 25 or 30kHz, the rapidly increasing levels of usage meant that there was a considerable amount of pressure on the available channels.

A TDMA system uses a different approach. As the voice signal is digitised, it is possible to split the voice data into bursts or packets. These can then be interleaved so that several users can share the same frequency channel. Broadly speaking, a GSM signal has frames that are split into eight timeslots. These have a defined data structure into which the data is fitted. The GSM channels are each 200kHz wide allowing for each cell to utilise a number of channels to provide access for the required number of users. This system provides a greater level of spectrum efficiency than the older analogue FDMA systems.

Similarly the North American

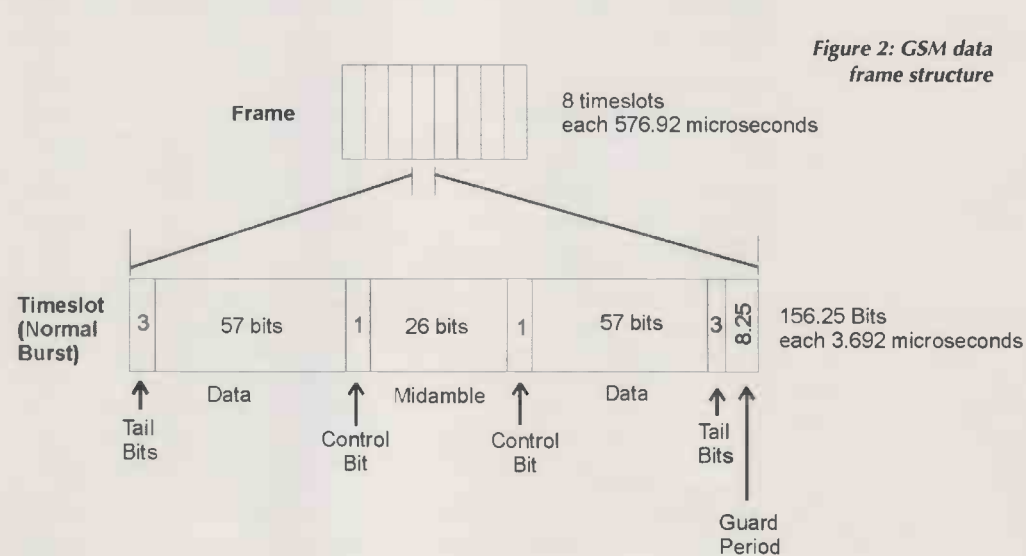


Figure 2: GSM data frame structure

Figure 3: Operation of direct sequence spread spectrum

TDMA system splits the transmission into different time slots for different users although it operates on a 30kHz spacing to retain compatibility with AMPS.

CDMA

The technique being used for the third generation systems is CDMA. This technique came out of the direct sequence spread spectrum work that was being undertaken by Qualcomm. This system involved multiplying the wanted data stream with another code stream to spread it over a wide bandwidth. The signal could then be transmitted and received despite the presence of interference that may have been present on channels within the bandwidth of the spread signal.


Using the CDMA system different codes are assigned to different users rather than different frequencies or time slots. When the receiver and transmitter use the same codes then the signal can be received satisfactorily. In this multiple users can use the same channel, and the different users are separated by the use of a different code.

The operation of CDMA can be likened to being in a large room with many people all speaking together, although in different languages. Although the noise level is high, it is nevertheless still possible to pick out what someone is saying in your own language, despite the fact that they are no louder than others speaking different languages

Operation

To generate a CDMA signal the required data signal is multiplied with what is known as a spreading or chip code data stream. This has a higher data rate than the data itself and it enables the overall signal to be spread over a much wider bandwidth. To decode the signal and receive the original data, the signal is multiplied with the spreading code to regenerate the original data. When this is done, then only the required data is regenerated, all the other data that is generated from different spreading code streams is ignored.

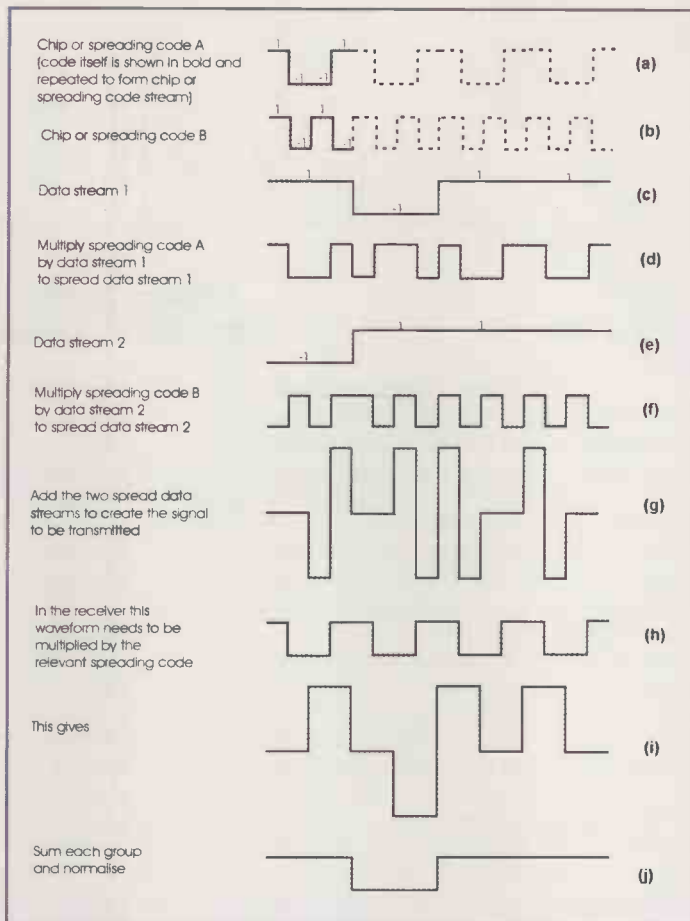The spreading codes can either be a random number (or pseudo random), or more usually what is termed an



orthogonal code. Two codes are said to be orthogonal if when they are multiplied together and the result of the summation over a period of time is zero. For example a codes 1 -1 -1 1 and 1 -1 1 -1 when multiplied together give 1 1 -1 -1. When this is summed it gives zero.

Although pseudo random number codes can be used there is possibility of data errors being introduced into the system.

Example

To see how the system operates it can be seen that the waveforms (a) and (b) in Figure 3 are the spreading codes. The spreading code streams are multiplied with their relevant data. In the diagram spreading code stream (a) is multiplied with the data in (c) to give the spread data stream shown in (d). Similarly spreading code stream (b) is multiplied with the data in (e) to give (f). The two resulting spread data streams are then added together to give the base band signal ready to be modulated onto the carrier and transmitted.

The spreading code stream consists of the spreading code being sent repeatedly so that each data bit is multiplied with each bit of the spreading code. In other words if the spreading code consists of four bits, then each one of these four bits will be multiplied with each data bit. It is also worth noting that the spread rate is the

number of data bits in the spreading code, i.e. the number of bits that each data bit is multiplied by. In this example the spread rate is four because there are four bits in the spreading code. This forms a basic data channel. It is then possible to combine several data channels by simply adding them together, and then modulating the resultant waveform onto the radio frequency carrier.

The signal is transmitted and once a receiver picks it up it undergoes the reverse process. First it is converted down to the base band frequency. The resulting data waveform is then multiplied by a spreading code stream with the relevant spreading or orthogonal code to extract the required data. This process is known as

correlation and it results in the set of data for that code being extracted. By using a different spreading code stream, a different set of data is extracted.

In this case it can be seen that chip stream (a) is repeated in waveform (h). This is multiplied by (g) to give the waveform (i). Each group of four bits (as there are four bits in the chip code used in the example) is summed and from this the data can be reconstituted as shown in waveform (j).

Beyond 3G

Even though the 3G networks are only just starting to be rolled out, early work is already progressing on developing the fourth generation systems. Some trials to assess the best modulation and access techniques have already been undertaken. From this it seems that the systems will be based around COFDM (Coded Orthogonal Frequency Division Multiplex) techniques with data rates rising into tens or hundreds of Megabits per second. So we had better start thinking now what we are going to use this for.

Ian Poole is a freelance consultant and journalist who can be contacted via his website at www.adrio-communications.com

Data Not Easily Accessible?

Radio Data Transfer From XL Systems..... Don't make a mountain out of it!

Your data
is here

remote process control,
telemetry & alarm monitoring ..
.. simple & straight forward
wireless solutions!

WWW.XLS.CO.UK
Tel 01883 622778
Sales@xls.co.uk

XL Systems Ltd

SenSym

SENSORTECHNICS



Honeywell

DATA INSTRUMENTS

Europe's Largest Selection
of Pressure Sensors

Sensortech UK
01788-560426

Are you ready for some extra service?

Contact us today!

Sensortech GmbH
Phone: +49 (0)89 80 08 30
Fax: +49 (0)89 80 08 333
E-mail: info@sensortech.com
Internet: www.sensortech.com

SPECIAL OFFERS

TEKTRONIX 2445A 4 Ch 150MHz Delay, Cursors etc. Supplied with 2 Tektronix probes **ONLY £425**

TEKTRONIX 2232 Digital Storage Scope. Dual Trace 100 MHz, 100ms with probes. £250
H.P. 54501A Digitizing Oscilloscope 100MHz, 4Ch £425
CIRIUS CRL254 Sound Level Meter with Calibrator, 80-120dB, LEO. £95
BECKMAN HD110 Handheld 3 1/2 digit DMM, 28 ranges with battery, leads and carrying case. £30
WAYNE KERR B424 Component Bridge. £50
RACAL 9300 True RMS Voltmeter 5Hz-20MHz usable to 60MHz 10V-316V. £50
RACAL 9300B as above. £75

H.P. 3312A Function Gen 0.1Hz-13MHz AM/FM Sweep/Tri/Gate/Burst etc. £300
FARNELL AMM255 Automatic Mod Meter 1.5MHz-2GHz Unused. £300
FARNELL DSG1 Low Frequency Syn Sig Gen 0.001Hz to 99.99kHz, Low Distortion TTL/Square/Pulse Outputs etc. £95
FLUKE 8060A Handheld True RMS DMM 4 1/2 digit. £95
H.P. 3310A Function Gen 0.1Hz-13MHz AM/FM Sweep/Tri/Ramp/Pulse. £120
FARNELL FLM4 Sine/Sq Oscillator 100MHz low distortion TTL Output, Am. £125
H.P. 545A Logic Probe 3.66A Logic Pulse and 547A Current Tracer. £90
FLUKE 77 Multimeter 3 1/2 digit Handheld. £60
FLUKE 77 SERIES II. £70
HEME 1000 LCD Clamp Meter with Carrying Case. £60

Racal 9008 Automatic Modulation Meter AM/FM 1.5MHz-2GHz **£95**

Datron 1061A High Quality 6 1/2 digit Bench Multimeter True RMS/4 wire/Current Converter **£225**

BLACK STAR ORION PAL/TV Colour Pattern Generator from £75-£125
THURLBYTHANDER TG210 Function Generator, 0.002Hz-2MHz, TTL etc. £80-£95
THURLBYTHANDER P.S.U. PL3200MD, 0V-32V, 0A-2A Twice (late colours). £200

JUST IN

HP. 8640A Signal Generator AM/FM 500kHz-512MHz. £250
KENWOOD CS4025 Oscilloscope Dual Trace 20MHz. £125
LEADER LB0523 Oscilloscope Dual Trace 35MHz. £140
GOULD OS300 Oscilloscope Dual Trace 20MHz. £95
NATIONAL PANASONIC VP7705A Distortion Analyser. £125
KENWOOD UT176 Millivoltmeter 2 Channel. £50
KENWOOD FL140 Wow & Flutter Meter. £50
KENWOOD FL180A Wow & Flutter Meter Used. £75
Elements for the above. £25

BIRD 43 Watt Meter. £75
Elements for the above. £25

MARCONI 893C AF Power Meter, Sinad Measurement. Unused £100 Used £60
MARCONI 2610 True RMS Voltmeter Autorangin 5Hz-25MHz. £195
GOULD J3B Sine/Sq Osc. 10Hz-100kHz. Low distortion. £75-£125
AVO 8 Mk6 in Ever Ready Case, with leads etc. £90
Others Avos. from £50
GOODWILL GVT427 Dual Ch AC Millivoltmeter 10mV in 12 Ranges Freq 10Hz-1MHz. £125
SOLARTRON 7150 DMM 6 1/2 digit True RMS. £125
Elements for the above. £25

SOLARTRON 7150 PLUS £200
UTILITY RACKS
9901A Meters Counter, 50MHz. £75
9902A Counter 12 MHz. £50
9903A Counter, 10Hz-560MHz, 9-digit. £50
RACAL 9943M LCR Databridge. £200
Automeasurements of R, D, L.
HUNTRON TR 99A. £125
MARCONI 2610A Sine/Sq Osc. 10-20MHz. £75

Pipette Illa Tester **£75**
Measuring Instrument **£75**

FARNELL AP60/150 £2000
FARNELL AP100 £2000
H.P. 6012B DC Power Supply 0-50A 100W. £1000
FARNELL AP60/50 1kW Autoranging. £1000
FARNELL H60-150 0-60V 0-50A. £750
FARNELL H60/25 0-60V, 0-25A. £400
Power Supply HPS3010 0-30V, 0-10A. £140
FARNELL Dual PSU XA35-2T 0-35V 0-2A Twice OMD LCD Display. £180
FARNELL L30-2 0-30V, 0-2A. £80
FARNELL L30-1 0-30V, 0-1A. £60
Many other Power Supplies available.
Isolating Transformer 240V In/Out 500VA. £40

FARNELL DTV 12-14 OSCILLOSCOPE

DUAL TRACE 12 MHz TV. COUPLING **ONLY £75**

FARNELL LFI 12-14 Sine/Sq OSCILLATOR

10 MHz - 1 MHz **ONLY £75**

OSCILLOSCOPES

TEKTRONIX TDS350 Dual Trace 200MHz 16/S unused. £1500
TEKTRONIX TDS320 Dual Trace 100MHz 500M/S. £1200
TEKTRONIX TDS310 Dual Trace 50MHz 200M/S. £950
LECHRO 9400A Dual Trace 175MHz SG/S. £750
HITACHI VC6523 Dual Trace 20MHz 20M/S unused. £500
PHILIPS PM3092 2+2Ch 200MHz Delay. £800 As new £950

PHILIPS PM3092 2+2Ch 100MHz Delay. £800 As new £950

TEKTRONIX TDS310 Dual Trace 50MHz 200M/S

TEKTRONIX TDS320 Dual Trace 100MHz 500M/S £1200
TEKTRONIX TDS350 Dual Trace 200MHz 16/S £1500
TEKTRONIX TDS310 Dual Trace 50MHz 200M/S £950
LECHRO 9400A Dual Trace 175MHz SG/S £750
HITACHI VC6523 Dual Trace 20MHz 20M/S £500
PHILIPS PM3092 2+2Ch 200MHz Delay £800 As new £950

OSCILLOSCOPES

TEKTRONIX TDS350 Dual Trace 200MHz 16/S unused. £1500
TEKTRONIX TDS320 Dual Trace 100MHz 500M/S. £1200
TEKTRONIX TDS310 Dual Trace 50MHz 200M/S. £950
LECHRO 9400A Dual Trace 175MHz SG/S. £750
HITACHI VC6523 Dual Trace 20MHz 20M/S unused. £500
PHILIPS PM3092 2+2Ch 200MHz Delay. £800 As new £950

OSCILLOSCOPES

TEKTRONIX TDS350 Dual Trace 200MHz 16/S unused. £1500
TEKTRONIX TDS320 Dual Trace 100MHz 500M/S. £1200
TEKTRONIX TDS310 Dual Trace 50MHz 200M/S. £950
LECHRO 9400A Dual Trace 175MHz SG/S. £750
HITACHI VC6523 Dual Trace 20MHz 20M/S unused. £500
PHILIPS PM3092 2+2Ch 200MHz Delay. £800 As new £950

JUST IN

H.P. 66312A PSU 0 - 20V/0-2A. £400
H.P. 66311B PSU 0 - 15V/0-3A. £400
H.P. 66309D PSU Dual 0 - 15V 0-3A/0-12V 0-1.5A. £750
H.P. 6632B PSU 0 - 20V/0-5A. £500
H.P. 6623A PSU Triple Output ranging from 0-7V 0-5A to 0-20V 0-4A. £850
H.P./Agilent 34401A DMM 6 1/2 digit. £400/£450
H.P. 3478A DMM 5 1/2 digit. £275
FLUKE 45 DMM Dual Display. £400
KEITHLEY 2010 DMM 7 1/2 digit. £950
KEITHLEY 617 Programmable Electrometer. £1250
H.P. 4338A Electrometer. £1500
H.P. 4338A Electrometer 1999 2.6 GHz. £500
H.P. 6623A PSU Triple Output ranging from 0-7V 0-5A to 0-20V 0-4A. £850
H.P. Agilent 34401A DMM 6 1/2 digit. £400/£450
H.P. 3478A DMM 5 1/2 digit. £275
FLUKE 45 DMM Dual Display. £400
KEITHLEY 2010 DMM 7 1/2 digit. £950
KEITHLEY 617 Programmable Electrometer. £1250
H.P. 4338A Electrometer. £1500
H.P. 4338A Electrometer 1999 2.6 GHz. £500
H.P. 6623A PSU Triple Output ranging from 0-7V 0-5A to 0-20V 0-4A. £850
H.P. Agilent 34401A DMM 6 1/2 digit. £400/£450
H.P. 3478A DMM 5 1/2 digit. £275
FLUKE 45 DMM Dual Display. £400
KEITHLEY 2010 DMM 7 1/2 digit. £950
KEITHLEY 617 Programmable Electrometer. £1250
H.P. 4338A Electrometer. £1500
H.P. 4338A Electrometer 1999 2.6 GHz. £500

SPECTRUM ANALYSERS

H.P. 8561B 50Hz - 6.5GHz. £5000
H.P. 8560A 50Hz - 2.9GHz Synthesised. £5000
H.P. 8594E 9KHz - 2.9GHz. £4500
H.P. 8591E 1MHz - 1.8GHz 75 ohm. £2750
H.P. 853A with 8559A 100kHz - 21GHz. £1750
H.P. 8558B with Main Frame 100kHz - 1500MHz. £750
H.P. 3585A 20Hz - 40MHz. £2500
H.P. 3580A 5Hz - 50kHz. £600
ADVANTEST R4131B 10kHz - 3.56GHz. £2750
EATON/Alltech 757.001 - 22GHz. £750
MARCONI 2320 10Hz - 400MHz High Res. £2000
MARCONI 2370 30Hz - 110MHz. from £500
H.P. 182 with 8557 10kHz - 350MHz. £500
H.P. 141T Systems
8553 1KHz - 110MHz. £500
8554 500KHz - 1250MHz. £750
8555 10MHz - 18GHz. £1000
H.P. 8443 Tracking Gen/Counter 110MHz. £250
H.P. 8444 Opt 059. £750
B & K 2033R Signal Analyser. £650
H.P. 8754A Network Analyser 4MHz - 1300MHz. £1250
H.P. 3577A Network Analyser 5Hz - 200MHz. £3000
H.P. 53310A Modulation Domain Analyser Opt 001/003. £5000
ONO SOKKI Portable FT Analyser. £1500
H.P. 8720C Microwave Network Analyser 50MHz-20GHz. £12500

RADD COMMUNICATIONS TEST SETS

MARCONI 2955/2955R from £1000
Rohde & Schwarz CMT 0.1 - 1000MHz. £1500
Schlumberger 4040. £750

STEWART OF READING

110 WYKEHAM ROAD, READING, BERKS RG6 1PL
 Telephone: (0118) 9268041 Fax: (0118) 9351696
 www.stewart-of-reading.co.uk

Callers welcome 9am-5.30pm Monday to Friday (other times by arrangement)

USED EQUIPMENT - GUARANTEED. Manuals supplied.
 This is a VERY SMALL SAMPLE OF STOCK. SAE or telephone for lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to total of goods and carriage.

Voltage or current feedback?

Frantisek Michele investigates the differences between the current-feedback amplifier and the more common voltage-feedback amplifier, and explains how to decide which option best suits a given application.

One question continuously troubles analogue design engineers: "Which amplifier topology is better for my application, voltage feedback or current feedback?" In most applications, the differences between voltage feedback and current feedback are not apparent.

Today's voltage-feedback and current-feedback amplifiers have comparable performance, but there are certain unique advantages associated with each topology. In general, voltage-feedback amplifiers offer lower noise, better DC performance and feedback freedom. Aside from the well-known attribute of current-feedback amplifiers, gain-bandwidth independence, current-feedback amplifiers also tend to offer faster slew rates, lower distortion and feedback restrictions.

With these common attributes known, the design engineer may still ask: "Why?" This article will examine the basics of the current-feedback amplifier in comparison with the voltage-feedback amplifier. The following aspects of each

topology will be examined:

- Closed-loop characteristics
- Open-loop characteristics
- Input-stage differences and advantages

Once these aspects are examined, it will become apparent why voltage-feedback amplifiers have better DC specifications. It will also be clear why current-feedback amplifiers have higher bandwidths for the same power and better linear phase performance over wider bands.

Finally, an internal look at the current-feedback amplifier will explain why distortion and slew rate are enhanced by its topology.

Closed-loop characteristics

The basic amplifier design schematics and their equations hold true for both amplifier topologies. Figure 1 shows the basic circuit topologies and transfer functions for inverting and non-inverting gain configurations. These hold true for both current-feedback and voltage-feedback amplifiers.

One point to remember is that the value of the feedback resistor is limited for current-feedback amplifiers. The current-feedback amplifier data sheet will provide the recommended value for R_f .

These transfer functions assume ideal conditions. Under such conditions, the open-loop gain A of a voltage-feedback amplifier and the open-loop transimpedance gain Z of a current-feedback amplifier are infinite. Therefore, the ideal transfer function, for the non-inverting topology, is generated as follows:

$$\frac{V_{in}}{R_g} = \frac{V_{out} - V_{in}}{R_f}$$

or,

$$\frac{V_{out}}{V_{in}} = \frac{R_f + R_g}{R_g} = G$$

Output voltage is equal to the input voltage multiplied by the gain, G .

Voltage-feedback open-loop characteristics

The fundamental differences between voltage feedback and current-feedback amplifiers begin to show when comparing their open-loop characteristics. Figure 2 illustrates the open-loop characteristics of a voltage-feedback amplifier.

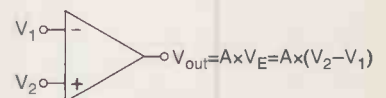


Figure 2: Open-loop characteristic of a voltage-feedback amplifier.

The ideal open-loop terminal characteristics are infinite non-inverting and inverting input impedances and zero output impedance. The output is a voltage source that is controlled by the potential difference between the two input terminals of the amplifier, also called the error voltage: $VE = V2 - V1$

Output is equal to this error voltage multiplied by the open loop gain, A . Once the loop is closed, feedback attempts to drive the error voltage to zero, hence the term voltage feedback.

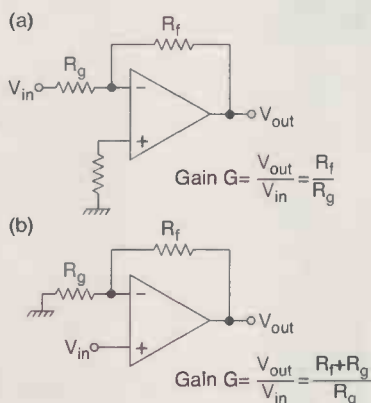


Figure 1: Basic inverting and non-inverting gain topologies hold true for current-feedback and voltage-feedback amplifiers.

Gain bandwidth product

Refer to the non-inverting gain topology of Figure 1. Remember that the open loop gain of a non-ideal amplifier is finite. Re-evaluating, the non-ideal transfer function for a voltage-feedback amplifier becomes:

$$\frac{V_{in} - V_E}{R_g} = \frac{V_{out} - (V_{in} - V_E)}{R_f}$$

Let:

$$V_E = \frac{V_{out}}{A}$$

and,

$$G = \frac{R_f + R_g}{R_g}$$

$$V_{out} = V_{in} \times G \times \frac{1}{1 + \frac{G}{A}}$$

As long as A is much greater than G then the denominator becomes 1 and the amplifier behaves as it did in the ideal case.

The actual open-loop gain is large at DC and rolls off at a rate of 6dB/octave, through most of the frequency range. As the frequency increases, the value of A decreases.

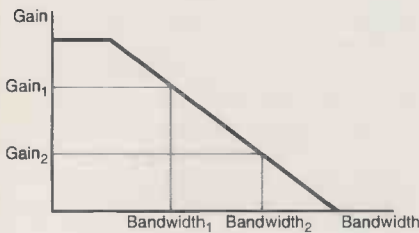


Figure 3: Illustration of the gain-bandwidth product for voltage-feedback amplifiers.

When $A=G$, the overall gain of the circuit will be half its DC value. This is commonly referred to as the -3dB bandwidth of the amplifier.

The rate at which the bandwidth decreases is proportional to $1/G$. For most of the frequency range, the product of gain and bandwidth

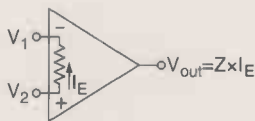


Fig. 4. Current-feedback open-loop characteristics.

becomes constant. This is referred to as the gain bandwidth product.

Gain bandwidth product prevents voltage-feedback amplifiers from obtaining high gain and high bandwidths simultaneously. This is illustrated in Figure 3.

Current-feedback open-loop characteristics

Figure 4 illustrates the open-loop characteristics of a current-feedback amplifier.

There is a unity-gain buffer between the two inputs of the current-feedback amplifier. Ideally, this buffer has infinite input impedance and zero output impedance. Therefore, the ideal open-loop terminal characteristics are infinite non-inverting input impedance, zero inverting input impedance and zero output impedance.

The output is a voltage source controlled by the error current I_E , out of the inverting input. Once the loop is closed, feedback will attempt to drive the error current to zero, hence the term current feedback.

Gain-bandwidth independence

Current-feedback amplifiers are known for their gain-bandwidth independence. The reason for this attribute is explained by calculating the transfer function of a non-ideal current-feedback amplifier.

An evaluation of the transfer function for a non-inverting configuration is shown. The transfer function for an inverting configuration also illustrates the gain-bandwidth independence.

$$I_E = \frac{V_{in} - V_{out}}{R_f} + \frac{V_{in}}{R_g}$$

$$V_{out} = Z \times I_E$$

$$G = \frac{R_f + R_g}{R_g}$$

$$V_{out} = V_{in} \times G \times \frac{1}{1 + \frac{R_f}{Z}}$$

The current-feedback transfer function looks very similar to the voltage-feedback transfer function. As long as Z is much greater than R_f then the amplifier behaves as in the ideal case.

Once Z drops to where it equals R_f , then the gain is lowered to half its DC value. This differs from the voltage-feedback case where gain is determined by both R_f and R_g . For current-feedback amplifiers, if the

gain is increased by lowering R_g , rather than increasing R_f , then the bandwidth is independent of gain.

This expression explains the importance of R_f for current-feedback amplifiers. Current-feedback amplifier data sheets provide the recommended R_f values for various gain settings.

An excessively large or small R_f will compromise stability. Within reason, the feedback resistor can be used to adjust the frequency response. As a rule of thumb, if the value of the recommended R_f is doubled, then the bandwidth will be cut in half.

A look inside voltage-feedback topology

By observing the open-loop characteristics of both amplifier topologies, the differences begin to become apparent. However, a closer look at the input stages will shed more insight onto the issues relating to current feedback versus voltage feedback.

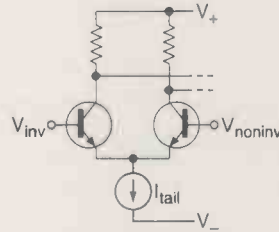


Figure 5: Typical input stage of a voltage-feedback amplifier.

A typical voltage-feedback amplifier input stage is shown in Figure 5. It is a common knowledge that voltage-feedback amplifiers tend to have better DC specifications than current-feedback amplifiers. Most voltage-feedback amplifiers have:

- Low input offset voltage (V_{io})
- Matched input bias currents (I_b)
- High power-supply rejection ratio (PSRR)
- Good common-mode rejection ratio (CMRR)

A close look at the input stages of both topologies will explain why voltage-feedback amplifiers tend to have better DC specifications.

The structure of the voltage-feedback input stage is the reason for better DC specifications. A voltage-feedback input stage is often a simple differential pair – two identical bipolar transistors at the same bias current and voltage. This configuration is often called a balanced circuit because of the symmetry between the two inputs.

Because of this symmetry, there will be no input offset voltage unless the devices do not match. The inputs are the bases of the two transistors. Although the absolute base currents, or input bias currents, may vary considerably due to process variation and temperature, again, unless the devices are not identical, the input bias currents will match.

When either the supply voltage or the common-mode input voltage is altered, the change in the collector-to-emitter voltages is matched for both of the input transistors. Changes in the devices' bias point could effect offset. Again though, due to the balanced topology, the bias currents match and offset voltage is little effected.

The result of this is good CMRR and PSRR.

A look inside current-feedback topology

The input stage of a current-feedback amplifier will also describe a few inherent DC traits of this type of amplifier:

- Non-zero input offset voltage
- Unmatched input bias current

The input stage of a typical current-feedback amplifier is illustrated in Figure 6. It is a voltage buffer. For the offset voltage to be zero, the supply voltage of the n-p-n transistors would have to match the supply voltage of the p-n-p transistors.

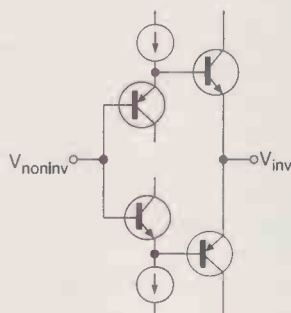


Figure 6: Typical input stage of a current-feedback amplifier.

Since these devices are constructed differently, there is no reason why they would inherently match. Bias currents in current-feedback amplifiers are also fundamentally mismatched.

The non-inverting bias current is the difference between two base currents where the inverting bias current depends on the errors produced in the next stage.

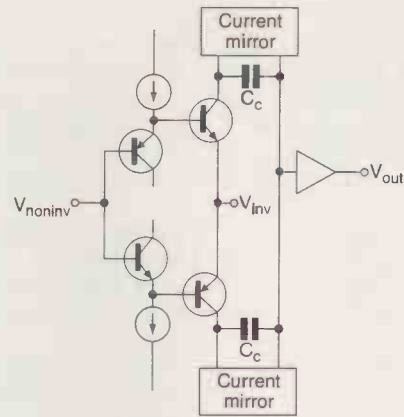


Figure 7: Basic current-feedback amplifier topology.

Advantages of current feedback

One hidden advantage of current-feedback amplifiers is that they usually require fewer internal gain stages than their voltage-feedback counterparts.

Often, a current-feedback amplifier consists of merely an input buffer, one gain stage and an output buffer. Having fewer stages means less delay through the open-loop circuit. This translates into higher bandwidths for the same power.

The basic current-feedback topology in Figure 7 is a single-stage amplifier. The only high-impedance node in the circuit is at the input to the output buffer. voltage-feedback amplifiers usually require two or more stages for sufficient loop-gain. These additional stages add delay and yield lower stable bandwidths.

Distortion

The distortion of an amplifier is impacted by the open-loop distortion of the amplifier and the overall speed of the closed-loop circuit. The amount of open-loop distortion contributed by a current-feedback amplifier is small due to the basic symmetry of the topology.

Figure 7 illustrates a typical current-feedback topology. For every n-p-n transistor, there is a complementary p-n-p transistor. Speed is the other main contributor to distortion.

In many gain configurations, a current-feedback amplifier has a greater bandwidth than its voltage-feedback counterpart. So at a given signal frequency, the faster part has greater loop-gain and therefore lower distortion.

Slew rate

Slew rate performance is also enhanced by the current-feedback

topology. Refer to the typical current-feedback topology of Figure 7.

Slew rate is determined by the rate at which the second two transistors can charge the compensation capacitors C_c . The current that can be sourced by these transistors is dynamic. It is not limited to any fixed value as is often the case in voltage-feedback topologies.

With a step input or overload condition, the current flowing through the transistors is increased and the overdriven condition is quickly removed. To the first order, there is no slew rate limit in this architecture.

Some voltage-feedback amplifiers have input structures similar to current-feedback amplifiers in order to take advantage of the higher slew-rate possibilities. The combination of higher bandwidths and slew rates allows current-feedback devices to have respectable distortion performance while doing so at a lower power.

The basic current-feedback amplifier has no fundamental slew-rate limit. Limits only come about by parasitic transistor capacitances and many strides have been made to reduce even their effects.

In summary

The availability of high-speed operational amplifiers in both current-feedback and voltage-feedback topologies allows design engineers to select the best amplifier to fit his needs.

A current-feedback amplifier complements an application that requires high slew rates, low distortion, or the ability to set gain and bandwidth independently. voltage-feedback amplifiers complement applications where low offset voltage or low noise specifications are required.

OLSON

®

UK's NO.1 IEC CONNECTION

OLSON DISTRIBUTION PANELS WITH IEC 320 SOCKETS INDIVIDUALLY FUSED AND NEON INDICATORS

OLSON PANELS with 10AMP CEE22/IEC SHUTTERED SOCKETS FUSED, DOUBLE FUSED WITH MAINS FILTER AND RCD PROTECTION

OLSON DISTRIBUTION PANELS WITH IEC 320 SOCKETS INDIVIDUALLY FUSED

OLSON DISTRIBUTION PANELS FOR 19" RACK MOUNTING WITH R. F. FILTER AND TRANSIENT SUPPRESSOR

OLSON 'The Rack Range' CEE22/I.E.C. SOCKETS

OLSON POWER DISTRIBUTION UNITS with IEC 320 Sockets

OLSON SEQUENTIAL START POWER DISTRIBUTION PANELS FOR 19" RACK-MOUNT SYSTEMS

OLSON ELECTRONICS LIMITED

OLSON 'THE RACK RANGE' MAINS DISTRIBUTION PANELS FOR 19" RACK MOUNTING HORIZONTAL


OLSON ELECTRONICS LIMITED

OLSON 19" RACK MOUNTING DISTRIBUTION PANELS WITH IEC 320 SOCKETS AND REAR CABLE MANAGEMENT

OLSON ELECTRONICS LIMITED

CALL OUR SALES HOTLINE

020 8905 7273

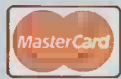


24 HOUR DELIVERY SERVICE

OLSON ELECTRONICS LIMITED
 OLSON HOUSE, 490 HONEYPOT LANE, STANMORE, MIDDX HA7 1JX
 TEL: 020 8905 7273 FAX: 020 8952 1232
 e-mail: sales@olson.co.uk web site: http://www.olson.co.uk



The discovery of electron diffraction

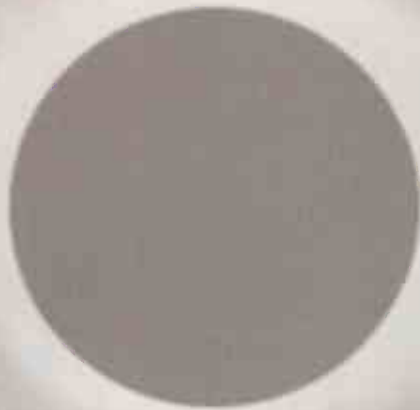

– a somewhat tangled history

Richard Feynman, who contributed a great deal to quantum theory, called the interference of matter waves ‘the great central mystery of quantum physics’ and having no need to pretend to understand, was quite emphatic in saying that no one does. David Potter unravels.

If one can associate a travelling wave with a moving particle, it is natural to look for evidence of that wave. Broglie’s relation $\lambda = h/p$, saying that the wavelength of a travelling particle equals Planck’s constant over the particle’s momentum, tells us immediately that a particle of baseball mass will have a wavelength so short as not to be measurable even in principle. However, electrons of moderate energy will have wavelengths comparable with the spacing of an atomic lattice, so that bouncing electrons off a metal surface might show the sort of diffraction pattern seen with light bouncing off an ordinary diffraction grating. The words ‘diffraction’ and ‘interference’ will be used almost interchangeably here (Feynman once said he could never tell the difference in them)

The equation for diffraction by light waves and by electron waves is $M\lambda = d(\sin \beta' - \sin \beta)$, where β is the angle between the incident beam and the plane of reflectors, β' is the angle of reflection with the plane, M is an integer and d is the distance between reflectors. λ of course is the wavelength. When the two angles have

the same value, the angle of the reflected particles with the incoming beam is twice the incoming angle, giving the more familiar Bragg equation $M\lambda = 2d \sin \alpha$ is used, where $\alpha = 2\beta$.

A web search will give many sites discussing electron diffraction, some with excellent diagrams showing how the patterns come about.

All this begs the question of whether the wave is ‘real’ or just an abstraction, and with what the wave is interacting. Sound waves are periodic variations in the density of the medium and we know how particles, even point particles, can interact with a lattice by momentum transfer. Diffracted electromagnetic waves (again, considering the wave aspect as more than an abstraction) are actually manufactured by the atoms of the lattice (on a higher level, the process is always treated as photon emission). But neither of these mechanisms seems pertinent to how matter waves can be diffracted. There would not be the periodicity if the mechanism were momentum transfer, unless one accepts the early quantum theories of Duane and Lande, and it isn’t plausible that the

atoms of the lattice are emitting matter waves (Broglie’s later pilot wave theory did have the atoms somehow emitting pilot waves to guide the electrons). This later theory was independently worked out by David Bohm in the early 1950s, the beginning of a flood of attempts to bring a sort of reality back into quantum theory.

Meanwhile in Paris...

At the Sorbonne, in 1924, graduate student Louis de Broglie had worked out that for consistency, the new restricted relativity of Albert Einstein must attribute certain wave characteristics to particles. Unless one goes to Broglie’s original papers, one will find the best account of how it all came about in Jammer’s *Conceptual Foundations of Quantum Mechanics*. Though the idea was not well received, either a chance visit of Einstein to the Sorbonne, or a letter written to him by Broglie’s supervisor, kept the thesis from rejection. Both versions are in the literature. According to Jammer, even several years after this, Einstein was somewhat uncertain of the idea when Walter Elsasser’s paper, which actually used Broglie’s idea, was sent to him. It had occurred to several physicists in Germany not long after Broglie published his thesis that perhaps the reflection of electrons from a metal surface might test Broglie’s idea of matter waves. However, perhaps partly due to the economic climate in post WWI Germany, this was not actually pursued in a laboratory.

It is interesting to speculate whether, if Broglie had not developed his thesis, some-

$$m\lambda = d(\sin \beta' - \sin \beta)$$

one else would have in a few years. Seminal ideas often seem to be in the air, with several people more or less thinking of them at about the same time. But the idea of matter waves really seems to have sprung from Broglie's anti-materialist philosophical outlook, which was one somewhat unusual for a physicist of that time. Broglie had been greatly influenced by the philosophy of Henri Bergson in his youth, and during the World War had worked at the military radio transmitter located at the Eiffel Tower. He was influenced at this time by General Gustave Ferrie, who is described in Feuer's book, *Einstein and the Generations of Science*, as a man infatuated by the reality and importance of electromagnetic waves. Thus both from his philosophical leanings and his wartime experience, Broglie was inclined to wave motion as a sort of anti-materialist approach to physics. Jammer describes a different set of influences, his physicist older brother (a specialist on X-rays, who had been involved in the controversy over whether they were particles or electromagnetic waves) and the great theoretical physicist Paul Langevin, who must have also contributed to this mindset.

Another angle

A somewhat different perspective on Broglie is given in Margarita Ryutova-Kemoklidze's book *The Quantum Generation*. It should be noted first that she is a physicist, a graduate of the Landau Institute. She describes Broglie as "an enthusiastic amateur", saying "Whenever he tried to expound his ideas at a seminar, they would cause general merriment". She quotes Einstein as writing to Born about Broglie's work: "Read it! Even though it gives the impression that it was written by a madman, it is a solid piece of work." Rather than read it, Born and friends conducted a satiric seminar, making fun of Broglie's idea. Born later developed a probabilistic interpretation of the wave nature of matter, and received the Nobel Prize for that. He is also famous for the 'Born Approximation', found in every quantum mechanics text.

Ryutova-Kemoklidze describes the influence of Broglie on Schroedinger, in the process describing Broglie as not a professional physicist at all, but an art historian. Einstein had brought Broglie's idea to Schroedinger's attention, and Schroedinger's quick transformation of this into wave mechanics had alarmed his wife. When he told her he had made a discovery that was as important as anything Newton had done, she feared for his sanity. It is worth observing

here that Schroedinger belonged to no group, was as interested (if not more interested) in philosophy and art as in physics, but had done distinguished work in physics already (he was 38). Schroedinger's wave mechanics made a working tool out of Broglie's idea. But the development of quantum mechanics as a probabilistic theory was never accepted by Schroedinger, as it was not by Einstein.

Without wave mechanics, our idea of the world would surely be quite different today, with the philosophical perspective of Dirac and Heisenberg perhaps having a much greater impact. Broglie and Schroedinger, both outsiders, might not have been easily replaced.

In 1919, Clinton Davisson, employed by the AT&T Research Labs, began to experiment with the scattering of electrons from surfaces. He was not unfamiliar with the new ideas coming into physics, and had published a paper on Bohr's atomic theory in 1916.

The latest technology in telephony then was the dialling switcher, a motorised switch having hundreds of contacts, its stepping motors driven by pulses from the new dial telephones just starting to be used. Naturally, with so many surfaces to become oxidised or corroded, the nature of metal surfaces was of interest to AT&T Labs. There was also some interest in the nature of the emitting surface of thermionic vacuum valves, already used as amplifiers in long-distance telephony.

Electron gun

Davisson constructed an apparatus to fire electrons onto copper, nickel and platinum surfaces, hoping to find just what was on the surfaces. A vacuum chamber placed a primitive electron gun close to the surface being investigated, and the charge 'bounced off' the surface was collected by a Faraday cup (just a metal cup connected to an electrometer). He doubtless expected that there would be absorption of the charge, varying in some way to give information about conditions on the surface, perhaps giving evidence of the shell structure of the atom. Davisson and Kunsman published a paper in 1921 with an account of these results. At this time, neither had heard of Broglie's ideas, and there was no attempt to bring in electron interference.

After this point, there is disagreement amongst various accounts. Max Born, or James Franck, or his student Walter Elsasser, seeing Davisson's article, or without seeing the article, considered the idea that electron diffraction from a crystalline surface might confirm Broglie's idea that material particles were associated with a wavelength which

depended on momentum. It does seem established that Elsasser was the first person to analyze in detail Davisson's data.

Jammer states that at first Davisson did not accept the note on this published by Elsasser (which had been published with difficulty). As with so many physicists (even Einstein), waves associated with particles seemed hard to accept. He was introduced to the idea whilst in Europe at a conference, and read Broglie's papers on the homeward voyage.

Davisson resumed his experiments. An accident occurred (vacuum was broken) which required the target in the vacuum chamber to be greatly heated (to bake off the oxide coating resulting from the vacuum break), causing it to re-fuse with much greater regularity. Where there had been many crystals making up the target surface, now there were but a few. Resuming electron scattering, there seemed to be clear maxima at various angles, depending on the voltage used to accelerate the electrons. Davisson was able to relate the scattering angles to electron wavelengths and published a paper on this with Germer in 1927. After this, electron diffraction became an important tool for investigating surface structure, as it still is. Those who want to see the mystery deepen further, can read about the Bohm-Aharoni effect, in which the phase of matter waves, and thus an interference pattern, is affected by passing through a region in which a magnetic or electric potential is not zero, but where there is no electric or magnetic field at all. A good account of this effect is in Mark Silverman's *More Than One Mystery*.

Try this at home

Diffraction can be shown with little expense, using an oscilloscope-type cathode-ray tube and a bit of high voltage. Diffraction rings are seen, easily two, as many as six with more care, with a much brighter central structure, as is seen with photography of a bright star. With proper voltages, a linear diffraction pattern can be seen in the central structure. The rings can be seen over a wide range of voltages, though particular combinations of voltage will sharpen the rings. The central structure requires more care. The eye sees the rings easily, and can see some detail in the central structure at the same time. A video camera or digital camera or film will show either the rings or the central structure, but not at the same time, as the central structure is so much brighter. A better solution would be a CCD camera meant for use with a telescope, since these are more sensitive, exposure time can be varied and



Figure 1: A pair of rings, using a green phosphor 5LP1



Figure 2: The central diffraction pattern, on a green tube



Figure 3: More rings, using a blue phosphor tube

there is processing software to hand. The photographs here do not do justice to the rings as seen by the eye.

The high voltage can be derived from a single supply, as is done in oscilloscopes, using a proper voltage divider. The supply can be arranged to have high impedance outputs for safety. One can buy proportional high-tension supplies cheaply which will give an output two to six kilovolts as the supply voltage is changed from five to fifteen volts. The cathode-ray tube elements do not draw high currents, so that a voltage divider supply can have much more current flowing through the divider proper than is taken by the CRT, thus reducing the interactions of the individual outputs. Many books on oscilloscope circuitry discuss how to make such a divider. These experiments used separate power supplies for the various elements, as such were available.

Older types of cathode-ray tube may be better for this purpose, as they tend to be simpler in construction. Several 5LP1 and 5LP11 tubes were used, a type which has a fairly simple electron gun, and which has post-deflection acceleration. The 5LP1 is a green-phosphor tube and the 5LP11 has a more sensitive blue phosphor which shows more rings. However a newer type with mesh post-acceleration might give diffraction effects at the mesh without a field beyond the mesh to compress the image.

Many books on cathode ray oscilloscopes have a brief discussion of electron optics. One of the best is a manual issued by Tektronix. More detailed books are, for instance, Klemperer's *Electron Optics* (and his *Physics of the Electron*), and Pierce's *Theory and Design of Electron Beams*. Electron guns are usually briefly described in engineering physics texts, as such guns are very commonly found in electronic equipment.

Lensing

The electron gun has a cathode (and heater), a control electrode (often called 'control grid', as the corresponding element in an ordinary valve is a grid) which mainly affects the intensity of the beam, a focus electrode and an accelerator electrode. There is electron lensing by the electric fields between cathode and control electrode,

control electrode and focus ring, and between focus ring and accelerator electrode. The mechanism of electron lensing to some extent mimics that of optical lensing, though some differences make one a little uneasy, an attitude palpable on page 37 of Thompson and Cochrane's 1930's book on electron diffraction. Higher voltage between elements contributes toward sharper focusing, but also makes deflection more difficult. The 5LP1, like many others, has post-deflection acceleration, that being a final electric field after the deflection plates. This allows for a sharper, brighter beam without greatly decreasing the deflection sensitivity, but as it has a lensing effect, compresses the image on the screen (this is discussed on pages 41-43 of the Tektronix manual).

For the 5LP1, a typical set of voltages for the ring pattern would be: final accelerator (2nd anode), 4000V, first accelerator, 2000V, focus 500V, control electrode -25V, all measured with respect to the cathode. For observation of diffraction by the deflection plates (as a linear central pattern), the plates can be tied to the focus electrode rather than to the first accelerator. This will cause more of the beam to hit the deflection plates. Voltages used will vary a great deal for different varieties of cathode-ray tube, and vary noticeably for different tubes of the same type.

To observe the rings, one adjusts voltages to get the smallest, sharpest spot, and turns up the intensity, which will burn the phosphor if left for long. One must get the pattern, observe or photograph, and turn the intensity down. For the central diffraction pattern, the same is true, save that one is not after a small central spot.

Figure 1 shows a pair of rings, using a green phosphor 5LP1. To give a sense of scale, an old burlap Royal Mail bag is draped over the tube.

Figure 2 shows the central diffraction pattern, on a green tube and

Figure 3 shows more rings, using a blue phosphor tube.

For safety's sake, final accelerator may be put at ground potential, with other voltages progressively more negative, as most books on the subject recommend. Doing this requires a filament supply for the CRT heater that is well-insulated.

Image capture

The pictures were made with a monochrome high-resolution video camera, fed into a video capture card. This was done rather than using a digital camera, as suitable lenses are more easily available for video cameras. A macro lens was used for the ring pictures, a shorter focal length macro lens used for the linear central structure. In effect, this was a low power video microscope, though nothing is critical or hard to improvise. However a high-resolution digital camera with a macro lens and manual shutter speeds, or an astronomical CCD camera would have been preferable.

In the usual demonstration of electron diffraction, electrons travel through a thin diffracting crystal, and go to a fluorescent screen. A discussion of this, with the pertinent equations, will be found on many websites. With a post-deflection acceleration cathode ray tube, there will be an electric field after the scattering, which has two effects. The field along the trajectory accelerates the electrons, changing the wavelength as the electron travels.

Also, the lensing action of the field compresses the image. Due to these two factors, the usual equation for image size in diffraction does not quite apply. It should be possible to use a ray-tracing program with a varying index of refraction in the post deflection region to work out electron paths but this was not done.

The central diffraction lines seem to be due to scattering off the vertical deflection plates. Where does the ring-pattern diffraction happen? It seems to be coming from the final aperture on the first accelerator electrode, as diffraction from an earlier source would not make it to the screen. As the aperture is too large for visible diffraction as an aperture, and the metal too thick for the usual transmission diffraction; it would seem that small imperfections on the inside of the aperture, as Thompson discusses on pages 138-140, must be the source. It is not impossible that a layer of gas on the surface may also contribute to the rings. From the usual equation, the electrons accelerated by 2000V would have wavelength about 0.27 Angstrom. This, with the last aperture-to-screen distance of 28cm and a first ring

radius of about 1cm would give spacing between the atomic planes of about 3.8 Angstrom, which is too large for the nickel-copper electrode. However this doesn't take into account the acceleration of electrons after leaving the aperture, which will reduce their wavelength during flight, and the lensing effect of the final field, which will compress the image.

Most magnetically deflected cathode-ray tubes are focused magnetically as well. Lack of deflection plates would mean there is no central pattern. What effect would the magnetic focusing, which operates so differently from electrostatic focusing, have? One hopes someone will find out.

Of the books on electron diffraction listed below, probably the most friendly is Thompson and Cochrane. Pinsker is much more comprehensive. Beeching, probably the first book on the subject to appear, is easy and pleasant to read. Of the books on electron optics, that by Tektronix is the most accessible, with Klemperer close behind. Of the histories, that by Max Jammer is the gold standard.

Bibliography

Books on hardware and electron optics

Cathode Ray Tube Displays, vol 22 of the MIT Radiation Lab series, McGraw-Hill, New York, 1948
Advances in Electronics, vol II, edited by L.Marton, Academic Press, New York, 1950
The Low Voltage Cathode Ray Tube, G.Parr, Chapman and Hall, London, 1937

Cathode Ray Tubes, Tektronix, Beaverton, Oregon
Electron Optics, O. Klemperer, Cambridge Monographs on Physics, Cambridge, 1971
Theory and Design of Electron Beams, J.R.Pierce, Van Nostrand, London, 1954

Books on diffraction:

Electron Diffraction, R.Beeching, Meuthen, London, 1936
The Diffraction of Light, X-Rays, and Material Particles, C Meyer, University of Chicago Press, 1934
Theory and Practice of Electron Diffraction, G.P. Thompson and W.

Cochrane, MacMillan, London, 1939
Electron Physics, O. Klemperer, Butterworths, London, 1959
Electron Diffraction, T. Rymer, Methuen, London, 1970
Electron Diffraction, Z. Pinsker, Butterworths, London, 1953
More Than One Mystery, Mark Silverman, Springer, New York, 1995

Histories

The Quantum Generation, M. Ryutova Kemolkidze, Springer, Berlin, 1995
Einstein and the Generations of Science, L.Feuer, Basic Books, New York, 1974
History of Quantum Theory, F.Hund, Harrap, London, 1974
Conceptual Development of Quantum Theory, M.Jammer, McGraw-Hill, New York, 1966
Paradox Lost, P.R.Wallace, Springer, Hamburg, 1996

Website:

www.nap.adultreadingroom/books/biomems/welsasser.html

THE SPACEPORT MODEM WIRELESS DATALINK



- Digital serial DCE interface with hardware/no flow control
- SpacePort Modem operates on 433.92 MHz and will be available in 151.300-173.250 MHz, 869.85 MHz and 914.5 MHz
- DTE baud rates from 600bps to 115,200bps
- Direct serial connection to microprocessors/microcontroller
- Uses addressable data packets with error checking, packet acknowledgements and re-transmissions to achieve a reliable wireless data link
- Remote configuration enables post installation set up of modem

Now you can test your application with the SpacePort Modem Evaluation Kit:

- Transforms OEM module into complete Radio Modem
- 5V, 1A supply to power-up DTE (e.g. barcode scanner)
- Visual Indications of Operations through LEDs
- On-board RS232 driver for direct Serial Port connection
- Access to internal diagnostic/Test modes using HyperTerminal
- Access to each data/control pins for external interface or testing
- Set-up and Configuration using HyperTerminal

Full technical details are available online at:

www.radiometrix.com

CE Certified by Independent Notified Body

RADIOMETRIX



Radiometrix Ltd
 Hartcran House, Gibbs Couch,
 Watford, WD19 5EZ England
 Tel: +44 20 8428 1220 Fax: +44 20 8428 1221
sales@radiometrix.com

NEW PRODUCTS

Please quote *Electronics World* when seeking further information

Transflective colour STN modules

A 5.7 inch transflective colour STN QVGA module, offering sunlight readability and a temperature range from -20°C to 70°C is now available from Anders Electronics.

The module is one of a range of sizes suitable for a number of applications where performance in outdoor use under high ambient light levels is critical. Applications include data terminals, ticketing and vending machines and portable instruments.

With a long CCFL backlight lifetime, typically 40,000 hours, the 320x240 dot Nan Ya LM639N features built in contrast bias voltage generator, high space efficiency and easy integration into OEM designs. Other sizes available are 3.3in, 3.8in and 3.9in. It has a viewing area of 118.2mm x 89.4mm and operates from a single 5V supply.

Options include a 4-wire resistive touchscreen and a matching CCFL backlight inverter.

Anders Electronics
www.anders.co.uk

Filters represent significant step forward in health and safety in the workplace



Recognising asthma as a serious occupational hazard, Nederman has developed an all-gas filter as an optional extra for its EK pollutional control system. It has four times the absorption capacity of carbon and four times the life, yet does not add to the cost of the EK unit.

Both the EK 1000 and 3000 systems are still available with the original blue filter for dual particle and gas extraction.

Where space is at a premium, and workbenches may not need continuous bench-top extraction, the 2000 and 3000 have trolley mounted options, turning them into fully mobile units.

The adjustable hood on the EK2000 can be shaped to suit various applications, ideal for use in workshops where more than one process is carried out.

Nederman UK
www.nederman.com

Designers free to choose encoders

Four new incremental encoder families which offer designers the freedom to choose the most cost-effective solution to match their specific requirements are available from ITT Industries.

Suitable for a wide range of applications, the encoders make use of electromechanical technology which delivers the best combination of reliability and low cost.

The 10mm NSE10 series hollow shaft devices have 24 indents and offer a rotational life of 100,000 cycles. NSE11 encoders control the 'play' in the shaft to a tight 0.4mm p-p maximum. NSE devices also feature increased functionality; either parameter validation of on/off switching using a 0.5mm travel, 4.5N actuating force SPST contact. NSE12 incremental encoders also offer the above functionality as well as a very distinct actuating force due to the detent torque controlled at 3 – 20mN.m.

Finally the NSE16 features an extended plastic shaft to 31.5mm
ITT Industries, Cannon
www.ittcannon.com

Circuit protection and power switching in a single unit

Featuring a compact, trip free, rocker actuated design, the W51 thermal circuit breakers from Tyco Electronics are available in 5 to 20A ratings. The breakers deliver circuit protection to UL 1077 and power switching in a single unit.

Available with an optional indicator lamp, it can snap into the same 28.5x13.5mm cutout as other common power switches on the market and provides a seamless retrofit or integration into an existing design. The devices may trip between 101% and 134%, but guaranteed to trip at 135% of rating within one hour. At 200% overload trip time is 4 – 40 seconds, while at 600% overload is 0.3 – 1.8 seconds. Typical resistance at 5A current rating at 25°C is 0.050Ω, while for a device rated at 20A it is 0.0125Ω.

Operating temperature is between 0°C – 60°C. Termination options include 6.35mm quick connects or solder terminals.

Tyco Electronics
www.tycoelectronics.com



Ready-to-connect ultrasonic proximity sensors

New from Contrinex is a range of ultrasonic proximity sensors. Available in M18 and M30 sizes these new devices are ideal for applications where distances have to be measured in air to targets that are solid, liquid, granular or in powder form.

The target material may be transparent or coloured, any shape and have either a polished or matt surface.

Available as diffuse or reflex sensors and in switched or analogue versions, sensors are notable for their high excess gain as well as a small blind



zone and can achieve operating distances of up to 6,000mm.

Detection and switch parameters can be programmed to suit individual applications by means of a PC interface device and the accompanying CONPROG software.

Contrinex
www.contrinex.co.uk


Please quote *Electronics World* when seeking further information

High speed laser diode modules enable compact and economical DWDM optical system

NEC Compound Semiconductor Devices Ltd. and NEC Electronics (Europe) GmbH announced its laser diode modules featuring electro-absorption modulator distributed feedback (DFB) laser diode and built-in wavelength monitor enabling compact and economical dense wavelength division multiplexing (DWDM) optical transmission systems design.

The new laser diode modules are designed for use in backbone and metropolitan area networks (MAN) and are available in two device types: the NX8560SJ Series with a transmission rate of 10 gigabits per second (Gbps) and the NX8567SA Series with a transmission rate of 2.5Gbps. The products are designed for DWDM wavelengths from 1530 nanometers (nm) to 1560nm with 50GHz (0.4nm) spacing based on ITU (International Telecommunication Union).

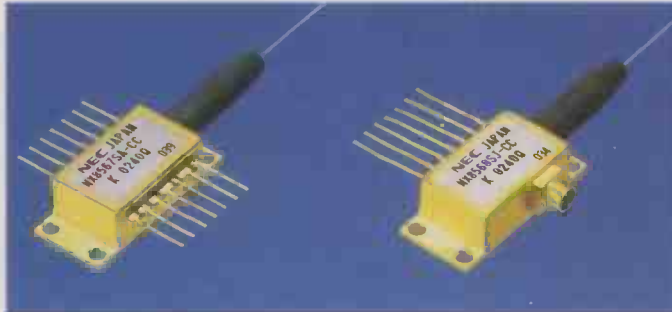The laser diode modules feature a built-in wavelength monitor with an etalon filter, which enables a precision-controlled emitted wavelength required from



DWDM systems. These modules with built in wavelength monitor function reduce cost of an optical transmitter by more than 25% compared with discrete solution where a monitor module is used externally. The size of the unit is reduced by up to two thirds, allowing a compact and economical DWDM system design. To suit individual applications, two device types are offered. Customers can select from the 10Gbps NX8560SJ Series and the 2.5Gbps NX8567SA Series to match their application, allowing flexible system design.

The light source of the modules consists of:

- a DFB laser diode which is

driven by a constant current to reduce the "chirping", i.e., signal transmission distortion caused by wavelength variations

- a monolithically integrated electro-absorption modulator. This enables a transmission distance almost four times longer than that of a directly modulated DFB laser diode with a large amount of chirping.

Mass production of the new laser diode modules is slated to start in April 2004, with annual shipments forecast of 10,000 units in total for all 4 models.

NEC
www.ee.nec.de

Low data rate wireless technology for the medical market

The latest member of the low data rate ASTRIC™ (application specific transmit and receive IC) product family from AMIS is the AMIS-52100. The new chip appeals to sub-5600MHz band wireless applications that require clock and data recovery, and is particularly suited to medical implantable devices. As an alternative to magnetic coupling, the band outlines a specific radio frequency range for two-way communication between medical devices to retrieve important information about a patient's status with improved data transfer rates.

AMIS engineered the 52100 to include its patent-pending Quick Start oscillator with an extremely fast 15µ turn-on time that allows the on-board receiver to quickly power up to check for the presence of a signal in the patented Sniff Mode™. Priced at \$1.95 in quantities of 50 thousand units, assuming a 20-lead SSOP package.

AMI Semiconductor
www.amis.com

Mini contactors in three configurations

Aerco now stocks the miniature industrial control equipment from GE Power Controls. The GE miniature contactors are available in both three and four pole versions. IEC947 standard compliant, the range is supplied as 35mm DIN-rail mounted or screw fixing. All contactors in the range are available in three contact configurations and have terminations for screws, fast-on and PCB configurations. It is possible to mount up to four blocks in tandem and a full range of accessories is available.

Aerco
www.aerco.co.uk

High density modular copper cabling


The AMP Netconnect Division of Tyco Electronics has introduced the Mini RJ21 Connector System, a high-density modular copper cabling system.

This new 24-pair cabling and connector solution provides up to 12 ports with a single cable and accommodates applications including 10/100, POE, VoIP, up to Gigabit Ethernet. The traditional modular 4-pair plug and receptacle are unable to meet high density demands, but the Mini RJ21 solution

combines reduced form factor, cable management, and channel performance to resolve those problems.

This solution is also applicable for any 'plug and play' environment, including data centres and zone-cabled or open office environments. In addition, the Mini RJ21 solution provides an application-independent copper platform for applications today and into the future, while reducing cable bulk in pathways and spaces.

Tyco Electronics
www.tycoelectronics

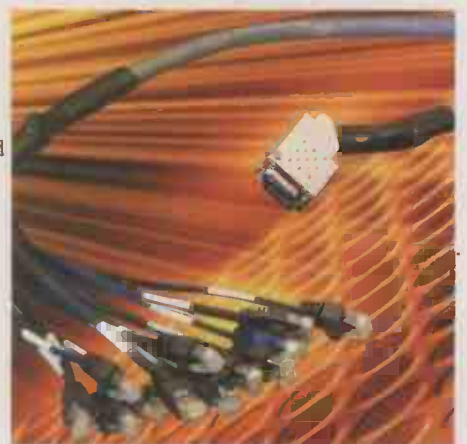

The AMP Netconnect Mini RJ21 connector system

ADVERTISERS INDEX

TELNET.....	IFC, OBC
PC INSTRUMENT MART(UK)....	IBC
QUASAR.....	2
OLSON	9, 25
No1 SYSTEMS	13
CRICKLEWOOD	17
JPG	17
CMS	17
XL SYSTEMS	21
STEWARTS OF READING.....	21
SENSOR TECHNICS	21
RADIOMETRIX.....	29
KOMPASS	35
TEST EQUIPMENT	37
TIE PIE	50
LABCENTER	53
JOHNS RADIO	57
WILMSLOW	57

Low-cost logic analyser operates to 100 MHz

The TA320S from Thurlby Thandar Instruments (TTi) is a self-contained logic analyser that offers 32 data channels and 100MHz acquisition for under £600.

Highly compact, but with a built-in LCD screen capable of displaying high-resolution graphics or 40-column text, control and data entry is by a combination of 'soft' keys and an alphanumeric keypad. An RS-232 interface is incorporated which allows data to be sent to (or loaded from) a personal computer.

The TA320S offers 32 data channels at up to 25MHz in synchronous or asynchronous mode, and eight data channels at 100MHz in asynchronous mode. Glitch capture for events as short as 5 ns is also provided. A choice of data pods is available to suit a wide variety of applications.

The trigger sequencer has up to four steps, with event counting and re-start at each step. Clock delay can also be added, and the trigger can be positioned anywhere within the store. Three external clock inputs are provided, each with

its own qualifier selectable for active edge and active level respectively. This gives highly flexible clocking for synchronous data capture.

State and timing displays can be selected, and data can be grouped as required under

user-defined names. Full search and compare facilities are incorporated. Automatic comparisons between the memories can be performed on a user-specified area of the data, and acquisition can be stopped on an equality or inequality.

Non-volatile storage of both acquisitions and set-ups is also provided, with sufficient memory for ten acquisitions and ten set-ups.

Optional disassembler pods provide support for a range of popular microprocessors. The disassembler software resides within each pod, thus eliminating the need to install special software within the analyser.

The TA320S is highly compact and portable weighing less than 1.5kg. It costs £595 (plus VAT) in the UK.

Thurlby Thandar Instruments Ltd
www.tti-test.com



High performance from small case sized radial electrolytics

NRSZC miniature aluminium electrolytic capacitors from NIC Components Europe Ltd provide low impedance and high stability performance across a wide temperature range. Suitable for use in a wide range of applications including switching power supplies and converters, NRSZC capacitors provide an ideal improved performance update for applications that use NIC's

established NRSZ series.

A capacitance range of 47µF to 18,000µF and rated voltage values of 6.3VDC to 35VDC mean that an NRSZC capacitor can be found to suit most requirements.

They have life expectancy of up to 70,000 hours, and an operating temperature range of -55°C to 105°C.

NIC
www.nicomp.com

Please quote *Electronics World* when seeking further information

Mini ESD diodes ideal for high data rate applications

Featuring very low terminal capacitance ratings, the new miniature ESD protection diodes from Toshiba provide electrostatic discharge and surge protection in high-speed signal applications.

The new DFxA5.6Lxx and DFxA6.2Lxx are suited to portable equipment and other high data rate applications where space is at a premium. Configuration options of two, 2-in-one, or four 4-in-1 integrated diodes help to reduce component count and simplify assemble, while package sizes down to just 1.6x1.6x0.55mm (ESV) ensures optimum space savings.

Toshiba
www.toshiba-europe.com

Bluetooth antenna saves space and weight

EPCOS has begun volume production of an antenna for Bluetooth and WLAN applications with centre frequencies in the range from 2.4 to 2.5GHz.

By using low loss materials and low temperature co-fired ceramic (LTCC) technology. Epcos has kept the antenna's dimensions down to only 10.1x2.6x0.65mm yet the device still features outstanding electrical properties. The antenna radiates up to 70% of the input power even if it is mounted on a conventional mobile phone board. It weighs 0.075g.

EPCOS UK Ltd
www.epcos.com

Test cable kit suitable for all standard portable or bench RF test equipment



Times Microwave Systems has introduced its TM-2230RK/in36 Testmate TM 500hm test cable kit. Designed for operation up to 18GHz, Testmate test cables feature precision stainless steel interchangeable connector heads so expensive adaptors are not necessary. The kit includes the

Testmate 230R three foot test cable, a full range of connector interfaces including two N-males, one N-female, one 716 DIN male, one 716 DIN female and wrenches all in a sturdy foam-fitted carrying case.

Times Microwave Systems
www.timesmicrowave.com

Breaking tradition – low cost SBC processor modules

An ultra-small ARM processor module, able to function as the processing core of a single board computer (SBC), and priced from less than \$50 is now available from Anders Electronics. Based on Intel's Xscale architecture, the module breaks the traditional X86-based relationship of functional content to price and size. With a power requirement of under 1W it offers a viable embedded PC solution for hand-held appliances and consumer electronics where X86 implementations cannot.

Known as the ARM CORE it is part of a range of ultra-small modular SBC building blocks available from Anders, designed to reduce time-to-market and both component and production costs associated with the development of custom embedded PC applications.

Measuring 66x44mm the module offers feature sets comparable to a typical desktop PC and comprises an Intel PXA255 CPU up to 400MHz. Many features are optional according to the application's requirements. The ARM CORE also provides a local bus as well as PCI and LPC buses for interface to off-board expansions. The module is designed for mezzanine attachment to a standard or custom board via two miniature 140-pin connectors.

Prices for an Armbase with Armcore start from \$93.

Anders Electronics
www.anders.co.uk



Linear voltage regulator ICs cover wide current and voltage ranges

The SI-3000 Series of linear voltage regulator integrated circuits is available from Allegro MicroSystems Europe. The series includes devices with voltage ratings from 1.5 to 15V and current outputs from 240mA to 3A.

All the devices feature low dropout voltages between 0.3 and 0.8V and low 'off' and quiescent currents. Overcurrent and thermal protection are included as standard. The range includes single and dual output products with both fixed and adjustable outputs. A variety of surface-mount and through-hole package styles is available including ultra-miniature SOT-89 and SOP-8 types.

Allegro MicroSystems
www.allegromicro.com



Please quote *Electronics World* when seeking further information

Compact electronic load handles 80 A and 80 V


The LD300, new from TTI (Thurlby Thandar Instruments), is a DC electronic load with maximum input levels of 80A and 80V, making it ideally suited for use in investigating the behaviour of many different types of DC power sources such as batteries, solar cells, fuel cells or wind generators, as well as electronic power-supply units.

The new unit has a maximum power dissipation of 300W, and is designed to have very low internal resistance to allow operation at high currents with low voltage drop. Operation down to 500mV is possible at currents up to 10A, rising to 1V at 40A and less than 2V at 80A.

The LD300 provides five different operating modes: constant current, constant voltage, constant power, constant resistance and constant conductance. The value of the

chosen constant parameter is set by 10-turn controls on the front panel. Alternatively, an external control voltage can also be used to set the level of the load. Any desired waveform can be applied, allowing complex load conditions to be simulated.

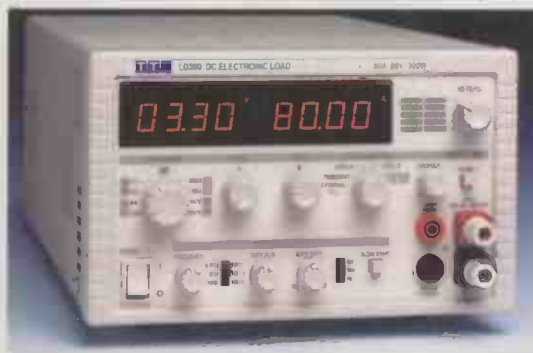An internal transient generator can repeatedly switch the load between two different operating levels set on separate 10-turn controls. The frequency and duty cycle of the transients can be set over a wide range. The transients can also be initiated by an external logic signal. The transitions between the levels have a true linear slewing characteristic in all modes, with



the slew rate adjustable over a wide range.

A low-voltage dropout facility is provided to protect sources such as batteries from damaging levels of discharge by reducing the load current when the source voltage falls below the dropout threshold.

Load conditions are displayed using high-accuracy 4-digit meters. The voltage of the source

can be sensed either internally for convenience or externally for better accuracy. A current monitor output provides a voltage proportional to the current flowing, allowing the behaviour of a source to be viewed on an oscilloscope or external meter.

The LD300 is fully protected against excessive current, power dissipation or internal temperature, and minimises audible noise by automatically controlling the fan speed according to the power dissipation.

The unit is housed in a compact case measuring 130 x 212 x 435 mm (half rack width, 3U height) with a weight of 6 kg.

The LD300 costs £695 (plus VAT) in the UK.

Thurlby Thandar Instruments
www.tti-test.com

Significant benefits offered from new range of 150V tantalum capacitors

A range of 150V wet capacitors featuring an all-tantalum construction is now available from Arcotronics offering cost saving benefits for module configurations, and elimination of the silver-migration problems associated with silver cased capacitors. Available in four standard case sizes, T1, T2, T3, T4, with capacitance values ranging from 2.5µF to 82µF, the new addition to Arcotronic's TH range is rated at 150V at 85°C, able to handle high ripple currents up to 1.86A at 40KHz and has reverse voltage capability.

The 150V version will allow the construction of smaller modules with increased operational voltage as well as reduce the number of

components required to meet high-voltage requirements of series configurations.

With long life reliability, the products are available in leaded and surface-mount versions.

Arcotronics
Tele: +44 (0)1442 877769



New booklet on managing component obsolescence

New guidance on managing the issue of component obsolescence to maximise supply chain efficiency has been issued by the Component Obsolescence Group COG, in the third of its series of information booklets, 'The supply chain minefield – the role of the distributor in managing obsolescence problems'.

The publication aims to provide guidance for end users to help them identify which type of distributor can best provide the service they need and also gives advice on how suppliers and customers can work together to minimise obsolescent problems.

According to COG, if a component within a piece of equipment becomes obsolete,

failure to get suitable replacement parts quickly or at all could incur considerable costs. The booklet costs £5. For further information about component obsolescence contact:

COG
www.cog.org.uk





A click in the right direction

- 23,000 companies
- 21,000 products and services

Call us on 01342 332121

- Any media you choose
- No registration hassle
- FREE to use

ElectronicsWeekly Buyers' Guide
Windsor Court, East Grinstead House
East Grinstead, Sussex RH19 1XA

ElectronicsWeekly
BUYERS' GUIDE

www.ewbuyersguide.com

Please quote *Electronics World* when seeking further information

New fan filters fare bigger and better



Aerco now supplies new large fan filters from ADDA, available to suit the three most popular fan sizes, 120mm², 127mm² and 160 x 172mm. They can be supplied separately or with suitable AC and DC fans.

The most popular filter materials are synthetic fibre or polyurethane foam but other materials of different densities can be supplied to suit virtually every application. All are washable and re-usable and the assemblies are louvered for applications that require regular hosing and washing. When a filter is used in front of a fan the cabinet and fan IP rating can be improved to IP 44 compared with the lower rating of a non-protected fan. The filter frame is manufactured from UL 94 VO material.

Aerco Ltd
www.aerco.co.uk

Double feed detection at top speed

Just announced by Murata is a high frequency ultrasonic transducer, the MA200D1, targeted specifically at printers and scanners used in a range of commercial office and banking equipment. This innovative device has the ability to detect the incidence of double feeding of paper through printers and scanners, even when the paper is very thin, very thick or different thicknesses.

The MA200D1 features a fast response time, short ringing time, wide bandwidth and is less influenced by reflection wave than high sensitivity devices. The transducer is specified with a nominal frequency of 220kHz +/-20kHz, with an overall sensitivity of 1 to 2.5V. Amplification gain is 60dB, directivity of 20° and a capacitance of 2300pF +/-20%.

The device is ideal for equipment such as commercial scanners used for cheques and payment slips, for high speed copy machines and printers for business use, and cash dispensers. Murata has responded to customer demand for a sensor that is

not fazed by the colour, thickness or transparency of the paper, but which can clearly and rapidly detect a double paper feed, without confusion with a single sheet of thicker paper. Machines using this ultrasonic transducer do not need calibration for paper thickness nor do they require mechanical contact with the paper.

The devices provide a faster response than similar transducers in the range, primarily because it uses a shorter drive cycle (typically cycles at 20Vp-p) at 220kHz, and the signal stabilises faster as there is less reflected wave detected.

Murata's MA200D1 transducer measures just 18mm in diameter and has a profile of 9mm.

Murata
www.murata-europe.com



Search engine identifies parts in less than a minute



C&D Technologies has unveiled an online parametric search engine that will help engineers to dramatically reduce the time that they spend in identifying and selecting the most appropriate DC/DC converters and magnetic components for their power applications.

C&D's 'eFAE' (electronic Field Application Engineer) search engine is now available at www.cdpoweronline.com and allows engineers to select the key product parameters in the priority order that is most relevant for a particular application. The engine will then apply a scoring system based on the inputs given and will rapidly identify the most appropriate parts in a maximum of just six steps.

The parameters that engineers can prioritise when searching for DC/DC converters are input voltage, isolation rating, number of outputs, output voltage, package style and power rating. In the case of magnetic components, key parameters are current, inductance and package style. Parameters are entered in their order of importance, and at each step eFAE narrows down the part list available. Users can search for the most closely matching products at any stage of the process.

Unlike previous search facilities, eFAE allows users to specify parameter priorities, meaning that the most appropriate parts for the particular application can be identified in less than a minute.

C & d Technologies (NCL) Ltd
www.cdpoweronline.com

New ScopeMeters with enhanced features for video imaging engineers

The new upgraded Fluke ScopeMeter handheld oscilloscopes, with enhanced sensitivity and a new troubleshooting feature, are now available from TTI (Thurlby Thandar Instruments).

The new range includes four colour and monochrome models for engineers servicing medical imaging and high-resolution video equipment. With the speed, performance and analysis power usually found only on high-end bench oscilloscopes, and with safety certification to

1000V Category II and 600V Category III, the new instruments will help users to solve virtually all electronics measurement problems encountered in the field.

The new models offer double the maximum sensitivity on the y axis, giving 2mV per division for greater measurement accuracy. A new troubleshooting feature offers automatic waveform comparisons, against a reference trace, for 'pass/fail' testing.

All ScopeMeter models now

have a large 320 x 240 pixel display, a fast display update rate, up to 1000V independently floating isolated inputs, 'connect-and-view' automatic triggering, a facility for measurement of effective output voltages of variable speed motor drives and frequency invertors, a 5000-count true-RMS multimeter function, and optional FlukeView software for documenting, archiving and analysis.

Thurlby Thandar Instruments
www.tti-test.com

TEST EQUIPMENT SOLUTIONS

Quality Second User
Test Equipment
With 12 Months Warranty

The Industry's
Most Competitive
Test Equipment Rental Rates

	Sale (GBP)	Rent (GBP)		Sale (GBP)	Rent (GBP)		Sale (GBP)	Rent (GBP)
AMPLIFIERS								
AT/HP 8348A/002 26.5GHz +25dB 25dBm Microwave Amp	9300	395	AT/HP 8510C/010 Microwave Network Ana 45MHz-110GHz	26500	953	AT/HP 3561A 100KHz Dynamic Signal Analyser	2750	99
AT/HP 8349A/001 20GHz 15dB 21dBm Amplifier	2500	99	AT/HP 8712E5 1.3GHz Vector Network Analyser c/w S Param	9500	342	AT/HP 3562A 100KHz Dual Channel Dynamic Signal Analyser	3650	110
AT/HP 8349B 2-20GHz +15dB >50mW Amplifier	2950	89	AT/HP 8714E5 3GHz Network Analyser c/w S Param	13950	503	AT/HP 35660A 102.5KHz Dual Channel Dynamic Signal Ana	3250	98
Amplifier Research 10W1000B 1GHz 10W RF Amplifier	2950	89	AT/HP 8719C/001/010 13GHz Vector Net Ana c/w S Param	19000	684	AT/HP 3585A 40MHz Spectrum Analyser	3950	119
Amplifier Research 1W1000 1GHz 1W RF Amplifier	950	48	AT/HP 8753B/006 6GHz Vector Network Analyser	6500	195	AT/HP 53310A 200MHz Modulation Domain Analyser	3950	119
COMPONENT ANALYSERS								
AT/HP 4155B Semiconductor Parameter Analyser	24000	864	AT/HP 8753E5 3GHz Vector Network Analyser c/w S Param	16950	508	AT/HP 85024A 3GHz Active Probe	1450	43
AT/HP 4194A/001/350 40MHz 50 Ohm Impedance Analyser	15750	788	AT/HP 89440A/Y1/Y8/9/A/B/H/1C2/1F0 DC-1.8GHz Sig Ana	12750	459	AT/HP 8560A 2.9GHz Spectrum Analyser	6750	284
AT/HP 4285A 30MHz Precision LCR Meter	8250	413	AT/HP 89441A-Various option sets available -Call prices from	14000	504	AT/HP 8562A 22GHz Spectrum Analyser	10950	329
DATACOMMS								
AT/HP J3446C LAN Fast Ethernet Internet Advisor	3950	119	OSCILLOSCOPES			AT/HP 8564E 40GHz Spectrum Analyser	23500	846
Fluke DSP4000 Cat 5e/6 LAN Cable Tester	3250	135	AT/HP 54100D 2 Channel 1GHz 40MS/s Digitising Scope	1650	98	AT/HP 8591A/010/021 1.8GHz Spectrum Analyser With TG	3950	119
Microtest 2 W/ INJECTOR+ 2 Way Cat 5 Injector	350	18	AT/HP 54501A 4 Channel 100MHz 20MS/s Digitising Scope	1250	38	AT/HP 8901B 1.3GHz Modulation Analyser	4500	179
Microtest PENTA SCANNER+ Cat 5 Cable Tester	975	50	 <p>Checkout our Latest 2004 Product Guide !! Call Us Now for Your Copy</p>					
Tek 1503C Metallic TDR	2500	107						
ELECTRICAL NOISE								
AT/HP 346B 18GHz APC-3.5(m) Noise Source	1250	65						
AT/HP 8970A 1.5GHz Noise Figure Meter	3450	147						
AT/HP 8970B 1.6GHz Noise Meter	4950	198						
AT/HP 8970B/020 2GHz Noise Meter	6950	209						
ELECTRICAL POWER								
Dranetz PP4300 Power Quality Analyser	4950	179						
Dranetz TR2022 10-1000A Current Clamp For PP4300	595	25						
HT Italia SPEEDTEST Multifunction Electrical Tester	400	24						
Kyoritsu 2017 600V 600A Digital Clamp Meter	300	24						
EMC								
Chase LFR1000 9KHz-150KHz Interference Measuring Receiver	850	43	AT/HP 54600B 2 Channel 100MHz 20MS/s Digitising Scope	1350	62	AT/HP 83732B/1E1/1E5/1E8 0.01-20GHz Synth Signal Gen	22500	675
R&S EB100 20MHz-1GHz EMC Test Receiver	1200	44	AT/HP 54622D 2 + 16 Channel 100MHz 200MS/s Scope	2950	123	AT/HP 8644B/002 2GHz High Performance Synth Signal Gen	7500	225
R&S EP2100 Panoramic Display For EB100	695	28	AT/HP 54645D 2 Channel 100MHz 200MS/s + 16 Ch LA	2850	90	AT/HP 8656B/002 0.01-990MHz Synthesised Signal Generator	950	30
Schaffner NSG1025 Fast Transient/Burst Generator	2950	125	AT/HP 54815A 4 Channel 500MHz 1GS/s Digitising Scope	5250	189	AT/HP 8657A 1GHz Synthesised Signal Generator	1600	48
FREQUENCY COUNTERS								
AT/HP 53131A/010/030 3GHz Universal Counter	1850	67	AT/HP 54825A 4 Channel 500MHz 2GS/s Digitising Scope	6950	255	AT/HP 8664A 3GHz Synthesised Signal Generator	16750	685
AT/HP 53181A 225MHz Frequency Counter	975	50	Lecroy LC584AL 4 Channel 1GHz Digitising Scope	12250	485	AT/HP 84421B 250KHz-3GHz Synthesised Signal Generator	5350	161
Philips PM6670 120MHz Frequency Counter/Timer	350	28	Tek 11801C Digital Sampling Scope (mainframe)	8250	346	AT/HP 84433A/1E5 250KHz-4GHz Synthesised Signal Gen	7950	239
Philips PM6670/011 120MHz Frequency Counter/Timer	350	28	Tek SD20 20GHz Single Channel Loop-through Head	1600	85	Marconi 2032 10KHz-5.4GHz Signal Generator	13250	477
Philips PM6673 120MHz Frequency Counter/Timer	395	20	Tek TDS340A 2 Channel 100MHz 500MS/s Digitising Scope	1700	62	R&S SMOY2 9KHz-2GHz Synthesised Signal Generator	3150	95
Racal 1992 1.3GHz Frequency Counter	1150	35	Tek TDS420A/05 4 Channel 200MHz 100MS/s Digi Scope	3750	146	AT/HP 37717C/UKJ PDH Transmission Analyser	2450	74
Racal 1998 1.3GHz Frequency Counter	695	35	Tek TDS460A/XL 4 Channel 400MHz 100MS/s Digi Scope	3950	143	AT/HP 37721A/004 PDH Transmission Analyser	2750	99
FUNCTION GENERATORS								
AT/HP 33120A 15MHz Function/Arb Waveform Generator	1050	38	Tek TDS520A 2 Channel 500MHz 500MS/s Digitising Scope	2750	117	AT/HP 37732A 50BPS-2MBPS Telecom/Datacom Analyser	2950	135
AT/HP 3325B 21MHz Function Generator	2650	80	Tek TDS644B/4D 4 Channel 500MHz 2.5GS/s Digi Scope	5550	200	Trend AURORA DUET Basic & Primary Rate ISDN Tester	3250	98
AT/HP 8904A 600KHz Function Generator	1350	49	Tek TDS794D 4 Channel 2GHz 4GS/s Digitising Scope	13000	536	Trend AURORA DUET Basic Rate ISDN Tester	995	50
Lecroy 9109/9100-CP Arb Waveform Gen with Controller	1950	59	POWER SUPPLIES			Trend AURORA PLUS Basic Rate ISDN Tester	350	28
Tek AWG2021 125MHz 250MS/s Arb Waveform Generator	4950	149	Many different units available - Call Us -Prices From	250	15	TTC 147 2MBPS Handheld Communications Analyser	3750	113
LOGIC ANALYSERS								
AT/HP 16500A Logic Analyser Mainframe	1250	71	PULSE GENERATORS			TTC Fireberd 6000A Communication Analyser	4250	153
AT/HP 16500C/03 Logic Analyser Mainframe With 32M Mem	2350	85	AT/HP 8012B 50MHz Pulse Generator	1100	65	TTC Fireberd Interfaces - Many diff types avail from stock...	Call	Call
AT/HP 16510A 100MHz Timing 25MHz State 80Ch Card	675	30	AT/HP 8112A 50MHz Pulse Generator	1850	83	W&G PFA-35 2MB/s Digital Transmission Analyser	3850	115
AT/HP 16510B 100MHz Timing 35MHz State 80Ch Card	890	38	AT/HP 8130A/020 300MHz Pulse Generator	5950	245	WIRELESS		
AT/HP 1660A 500MHz Timing 100MHz State 136Ch Log Ana	3650	115	AT/HP 8133A 33-3000MHz Pulse Generator	18500	795	AT/HP 11759C RF Channel Simulator	6950	209
AT/HP 1662A 500MHz Timing 100MHz State 68Ch Logic Ana	2550	89	AT/HP 8160A 50MHz Pulse Generator	2550	92	AT/HP 83220A DCS1800 (1700-1880) Test Set	1750	63
AT/HP 1662AS 500MHz Timing 100MHz State 68Ch with DSO	4500	178	RECORDERS			AT/HP 8902A/002 1.3GHz Measuring Receiver	12650	575
AT/HP 1670A 250MHz Timing 100MHz State 136Ch Log Ana	4950	195	RF SWEEP GENERATORS			AT/HP 8920A/010 1GHz Radio Comms Test Set	4750	143
NETWORK ANALYSERS								
Advantest R3762B 300KHz-3.6GHz Network Analyser	4500	193	AT/HP 8340B 10MHz-26.5GHz Synthesised Sweep Generator	9950	399	AT/HP 8920B/1/4/13/14/51/102 1GHz Rad Comms Test Set	5950	179
AT/HP 3577A 5Hz-200MHz Vector Network Analyser	4750	142	AT/HP 83650A 50GHz Synthesised Sweeper	22550	812	Anritsu ME4510B Digital Microwave System Analyser	10950	329
AT/HP 3589A 150MHz Network/Spectrum Analyser	5950	266	AT/HP 83751A/1E1 2-20GHz Synthesised Sweeper	11650	473	IFR 1600S/16/20/21/22/35 1GHz Radio Comms Test Set	3950	119
AT/HP 8510C Microwave Network Analyser 45MHz-110GHz	22500	975	AT/HP 83752B/1E1/1E5 10MHz-20GHz Synthesised Sweeper	18500	769	Marconi 2945 1GHz Radio Comms Test Set	6500	195
			Anritsu 68147B/2A/18 10MHz-20GHz Synthesised Sweeper	9500	395	Marconi 2955A/2957A 1GHz Rad Comms Test Set with AMPS	2750	99
			Anritsu 68377B/2C 10MHz-50GHz Synthesised Sweeper	22750	819	Marconi 2955R 1GHz Radio Comms Test Set	3150	114
			SIGNAL & SPECTRUM ANALYSERS			R&S CMD55/B1/4/6/9/41/42/43/44/51/61/018/U20 RCTS	6550	236
			Advantest R3261C 9KHz-2.6GHz Spectrum Analyser	5250	235	Racal 6103/001/002 Digital Mobile Radio Test Set	6950	279
			Advantest R3465 9KHz-8GHz Spec Ana With Digital Tx Mode	6950	298	Wavetek 4201S Triband Digital Mobile Radio Test Set	3500	105
			Advantest R9211A 10mHz-100KHz Dual Channel FFT Analyser	2950	89	Wavetek 4202S/AM Triband Digital Mobile Radio Test Set	3500	105
			AT/HP 11848A Phase Noise Interface	12500	492	WaveTek M248330 Antenna Coupler	285	23

If you don't see what you want, please CALL!

See our extensive online catalogue at www.TestEquipmentHQ.com

Flexible commercial solutions available on all products



Prices shown are for guidance in £UK GBP, exclusive of VAT and Ex-Works. All items subject to prior sale. Rental prices are per week for a rental period of 1 month. Free carriage to UK mainland addresses on sale items. Rental or non UK deliveries will be charged at cost. This is just a selection of equipment we have available - if you don't see what you want, please call. All items are supplied fully tested and refurbished. All manuals and accessories required for normal operation included. Certificate of Conformance supplied as standard. Certificate of Calibration available at additional cost. Test Equipment Solutions Ltd Terms and Conditions apply. All E&OE.

01753 596000
Fax: 01753 59 6001

www.TestEquipmentHQ.com
email: info@TestEquipmentHQ.com

CIRCUIT IDEAS

Fact: most circuit ideas sent to *Electronics World* get published

The best circuit ideas are ones that save time or money, or stimulate the thought process.

This includes the odd solution looking for a problem – provided it has a degree of ingenuity.

Your submissions are judged mainly on their originality and usefulness. Interesting modifications to existing circuits are strong contenders too – provided that you clearly acknowledge the circuit you have modified. Never send us anything that you believe has been published before though.

Clear hand-written notes on paper are a minimum requirement: but you will stand a much better chance of early publication if you supply your idea electronically, preferably by email. Any diagrams need to be in a graphic format, not a CAD/CAM or any other obscure file.

Most circuit ideas contributors are paid £35 and good ones attract £50 or even £100! If winners would prefer archive CDs or subscriptions instead of payment please let us know when you send the idea in.

Where software or files are available from us, please email Caroline Fisher with the circuit idea name as the subject.

Send your ideas to: Caroline Fisher, Highbury Business Communications, Nexus House, Azalea Drive, Swanley, Kent, BR8 8HU or email to: ewcircuit@highburybiz.com

Phase-selector for three-phase mains supply


Modern residences are usually three-phase supplied. On the other hand most domestic equipment is single phase. While complete failure of all the three phases are nowadays rare, brown-outs and blackouts on one or two phases are not uncommon. Uninterruptible Power Supplies (UPSs) provide a short-term solution and they do not come cheap, also under most mains conditions 'decorative'. What is needed to improve the availability of single phase mains operated equipment is a device that would detect intolerable brown-out or black-out in the mains phase on which the equipment is operating and effect automatic switching to any one other phase with tolerable line voltage.

The design also provides a measure of protection against brown-out on the operating line by a switch 'search' to a more tolerable line. If no brown-out tolerable line is available, the supply to the appliance is switched off. In

operation, each active line of the A.C. Mains voltage is converted to D.C. control line voltage of approximately 2.5V in the absence of brown-out by the use of the IN4007 rectifier diode. The 22mF capacitor and resistors form an R-C filter network. The IN754 provides voltage stabilisation for a level of deviation of the A.C. Mains from the nominal 220V. The 1k resistor in conjunction with the other resistors form a potential divider with values chosen to provide the needed D.C. control line voltage and a brown-out A.C. cut-in voltage of approximately 110V. The three D.C. control line voltages are fed as inputs to a 'prioritized' line switching logic controller consisting of the combination of 7404 and 7411 logic gates switching in one line of the A.C. mains to the output driver transformer consisting of three separate primary windings each of which has a ratio of 1:1 to the secondary winding, in accordance with the designed

switching logic priority. The line switch priority engages Phase 1 A.C. mains line to the output transformer driver if the Phase 1 A.C. line voltage is above the design brown-out cut-in voltage irrespective of the states of the other two lines that are automatically disengaged from the output driver transformer. Phase 2 line is engaged to the output driver transformer if there is Phase 1 black-out or Phase 1 voltage falls below the design brown-out cut-in level, irrespective of the state of Phase 3 line which in conjunction with Phase 1 line is automatically released from the output driver transformer. Phase 3 line is engaged in operation and Phase 1 and Phase 2 lines automatically released from the output driver transformer if black-out occurs in both Phase 1 and Phase 2 lines or their line voltages fall below the designed brown-out cut-in voltage level.

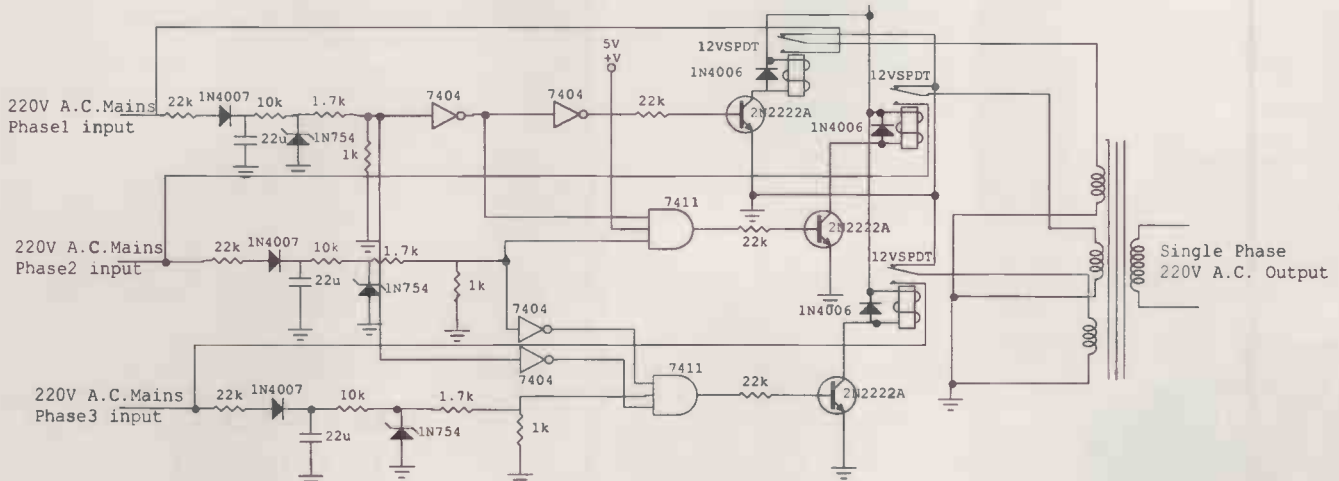Sode-shinni N.J. RUMALA
Minna, Niger State
Nigeria



Intelligent electric fence with burglar alarm

Crude electric fences that are used with a live electric wire around the compound may cause many problems to the locality such as a fence kept for animals like donkeys may affect a dog or smaller animals which are not our target. The circuit presented here differentiates a dog and a donkey or any creatures having somewhat different sizes (taking account of its body resistance). This circuit also works as a burglar alarm. The cost of making this kit is much less £3 pounds excluding the power supply. Normally electric fences cause heavy shocks that may lead to death of the intruding organism. With this circuit there will be a shock for about 22 milliseconds that will be helpful to push the intruder away from the fence. This circuit will be highly useful for farmers, homes and security people.

The working of this circuit is very simple, as every body knows that when a phase and

earth is short-circuited a current will be induced in the wire. This principle is used for making this circuit. The change in electric current is sensed and made to operate a relay via a operational amplifier.

The heart of this circuit is the transformer T1 which can be made easily with parts from a old power supply eliminator transformer from the junk box.

For the construction of transformer T1; take a 6-0-6 PSU transformer of 300 to 500mA capacity, then remove its secondary windings. The primary windings in the transformer is the winding C pointed out in the circuit diagram. A&B are 23 turns of 15SWG bifilar windings with terminals A1, B1, A2 & B2.

As stated above, the main principle is that the induced current is fed to an operational amplifier where it is amplified. A 10k potentiometer is used to adjust the sensitivity


of the relay according to our needs. Diode D1 is used to rectify the output from the op amp and zener diode D2 is used to cancel offset voltage and noise effects. The push to on switch is used to reset the system and transistor Q1 is a npn switching transistor, but any transistor of this type can be substituted. The power supply is an ordinary 10V dc.

This circuit can also used to prevent electric accidents. The same arrangement can be used with the main power supply when any short occurs the main power will be automatically cut off within 15-20 milliseconds. So this circuit is a worthwhile one for any electronics enthusiasts who often get a shock!

P. M. Prabhu
Kerala,
India

Components:

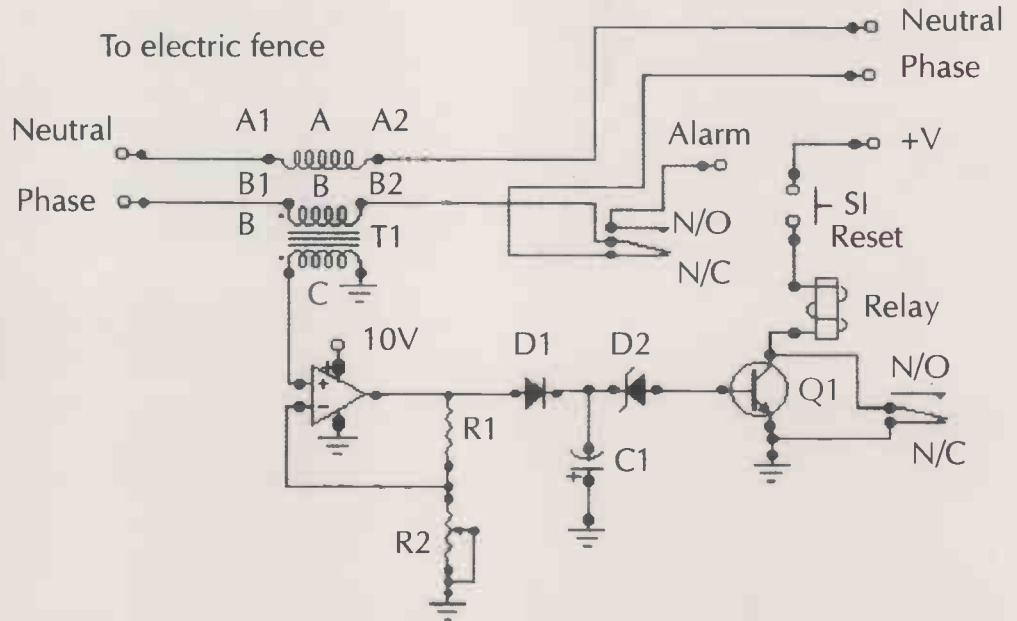
Transformer T1 (see text)
IC MC1458/LM741
Diode D1 IN4001
Diode D2 5.2V Zener
Relay DPDT 12V 200 Ohms 5A
Capacitor C1 4.7mF 25V
Resistor R1 100k
R2 10k potentiometer
Alarm any type
Transistor Q1 SI, 100
Switch on-off switch or push to off switch



VHF Preampifier using Max2633

Here is a high performance RF amplifier for the entire VHF band that can be successfully built without any special test equipment. The grounded-gate configuration is inherently stable without any neutralisation if reasonably good layout techniques are employed. The performance of the amplifier is quite good. The noise figure is below 2dB and the gain is over 13dB. The low noise figure and good gain will help car radios or home stereo receivers pick up those weak distant stations or the lower power 'talk radio' and university stations or distant amateur VHF stations. FM receivers lose signals abruptly, so if your favourite station fades in and out as you drive, this amplifier can have a dramatic effect.

The MAX2633 is a low voltage, low-noise

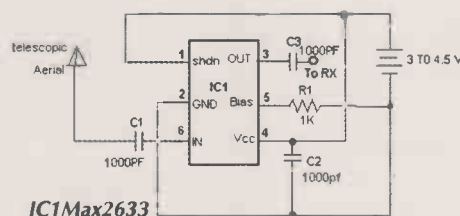

amplifier for use from VHF to microwave frequencies. Operating from a single +2.7V to +5.5V supply, it has a flat gain response to 900MHz. Their low noise figure and low supply current make them ideal for receive, buffer, and transmit IF applications. The MAX2633 is biased internally, has a user-selectable supply current, which can be adjusted by adding a single external resistor

(R1). This circuit draws only 3mA. Aside from a single bias resistor (R1) required for the MAX2633, the only external components needed for this family of amplifiers are input and output blocking capacitors (C1 and C2) and a VCC bypass capacitor (C2). Input and output series capacitors may be necessary to block DC bias voltages generated by the amplifier from interacting with adjacent circuitry. These capacitors must be large enough to contribute negligible reactance in a 50W system at the minimum operating frequency. Use the following equation to calculate their minimum value:

D. Prabakaran
Tamilnadu
India

Leakage current jig

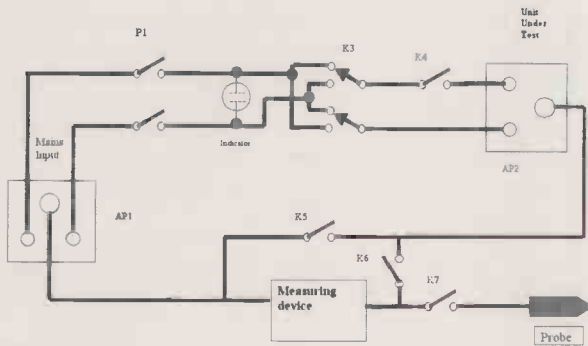


Diagram 1

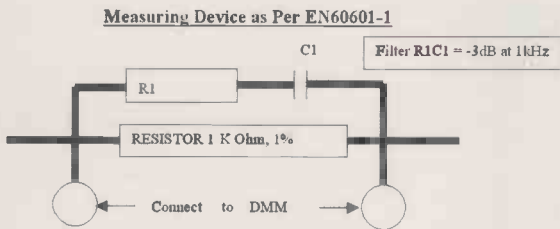


Diagram 2

The following was generated after a request for a simple and relevant leakage current jig required by manufacturers who were manufacturing for a hospital environment and which was not required to be physically touched by a patient but their presence in the hospital is required.

Most of the manufacturers do get their equipment tested for the general electrical requirements as per EN 60601-1, the prime standard for all medical electrical requirement. One of the most important parameters to be investigated in the equipment under test as per the specification is the leakage currents.

The classification of Medical Electrical Equipment standards is as in Table 1. Most of the equipment which does not have the necessity of connecting directly to the patient or act as supporting equipment can be classified as Class I, Type B equipment. This limits the area of the investigation regarding the leakage currents. The types of leakage currents applicable and their limits are as in Table 2. The jig described here makes a simple tool for measurement of the leakage currents.

The block diagram depicts the workings and connection logic for the measurement of the leakage currents. Table 3 details the status of the contacts for the relays for the test number.

The box marked as 'measuring device' is for measuring the leakage current at different conditions. The details of the measuring devices are in Diagram 3. A true RMS digital multimeter in auto range in AC voltage measurement setting is connected across the 'measuring device'. The current is measured as voltage across the Measuring Device (at the highest resolution setting for meters which don't have auto-ranging facility).

The circuit (diagram 2) is the heart of the unit. The micro-controller was used because it will be very handy if you have to modify the same board for some other jig or add some new feature, which would be required by the manufacturer.

The operation of the jig is very easy. On power on via the switch P1 in Diagram 1, the display DP lights and is ready for making measurements.

The next step is to select the test number by pressing the key K1. After the DP lights, every time the K1 is pressed the seven segment display increments by 1 starting from 0. The relation of the displayed number on the display with the test in progress is as given in Table 2. Table 2 gives the maximum limits of current which is allowed as per EN 60601-1 for the Class I, Type B equipment.

Jayant Kathe
Mumbai, India

Editor's note: the code for this project is available by contacting Caroline Fisher (details page 3) quoting reference CI 65.

Parts list:

1 AT89C2051P	IC1
2 4511N	IC2
3 7805T	IC3
4 12MHz	Q1
5 Seven Segment Display (Common Cathode)	D1
6 Transistor PNP TIP42C	T1, T2, T3, T4, T5
7 Transistor PNP BC557	T6
8 Switch	S1, S2
9 Relays (12VDC type)	K3, K4, K5, K6, K7
10 Terminal	X1, X2, X3, X4, X5, X6
11 Appliance Coupler	AP1
12 Socket	AP2
13 Resistor 560Ω	R1, R2, R3, R4, R5, R16, R17, R18
14 Resistor 10KΩ	R19, R6, R7, R8, R9, R10, R20, R21
15 Resistor 24Ω	R11, R12, R13, R14, R15
16 Capacitor C1	10μF
17. Diodes 1N4004	D3, D4, D5, D6

Table 1

Classification/Type of Equipment to be Tested

Class I		There is no Symbol for Class I equipment, however Class I equipment will generally have a protective earth marked with the symbol as indicated
Class II		Test Equipment will be marked with the symbol as indicated, It has double or reinforced insulation as the protection against electric shock
Type B		Test Equipment will be marked with the symbol as indicated. It is defined as having a protective earthed applied part, suitable for internal and external application to the patient, except for direct application to the heart
Type BF		Test Equipment will be marked with the symbol as indicated. It is defined as having an F-type isolation (floating) applied part suitable for internal and external application to the patient, except direct cardiac application.
Type CF		Test Equipment will be marked with the symbol as indicated. It is defined as having F-type isolated (floating) applied part suitable for direct cardiac application.

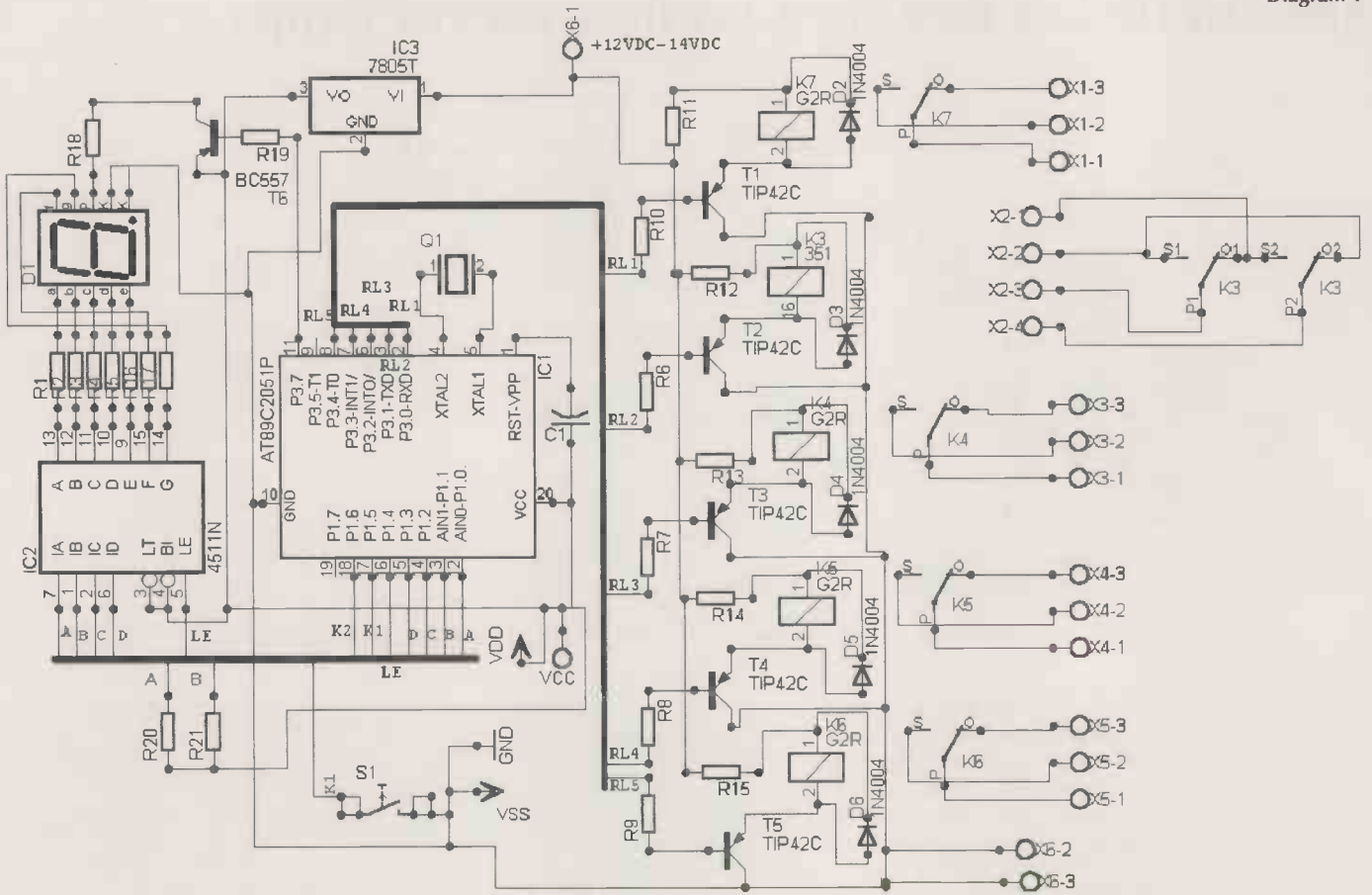



Table 2

Test No.	Limits of Leakage Current as per Spec EN 60601-1	Test Name
0	500µA	Earth leakage Current : Normal Mains Input Condition
1	500µA	Earth leakage Current : Reversed Mains Input Condition
2	1000µA	Earth leakage current : Normal Mains Input: Single Fault condition (Supply Open)
3	1000µA	Earth leakage current : Reversed Mains Input : Single Fault condition (Supply Open)
4	1000µA	Enclosure Leakage Current: Normal Mains Input Condition
5	1000µA	Enclosure Leakage Current: Reversed Mains Input Condition
6	500µA	Enclosure Leakage Current: Normal Mains Input: Single Fault condition (Supply Open)
7	500µA	Enclosure Leakage Current: Reversed Mains Input: Single Fault condition (Input Open)
8	500µA	Enclosure Leakage Current: Normal Mains Input: Single Fault condition (Earth Open)
9	500µA	Enclosure Leakage Current: Reversed Mains Input: Single Fault condition (Earth Open)

Table 3

Test No.	Relay K3	Relay K4	Relay K5	Relay K6	Relay K7	Test Name
0	OFF	ON	OFF	ON	OFF	Earth leakage Current : Normal Mains Input Condition
1	ON	ON	OFF	ON	OFF	Earth leakage Current : Reversed Mains Input Condition
2	OFF	OFF	OFF	ON	OFF	Earth leakage current : Normal Mains Input: Single Fault condition (Supply Open)
3	ON	OFF	OFF	ON	OFF	Earth leakage current : Reversed Mains Input : Single Fault condition (Supply Open)
4	OFF	ON	ON	OFF	ON	Enclosure Leakage Current: Normal Mains Input Condition
5	ON	ON	ON	OFF	ON	Enclosure Leakage Current: Reversed Mains Input Condition
6	OFF	OFF	ON	OFF	ON	Enclosure Leakage Current: Normal Mains Input: Single Fault condition (Supply Open)
7	ON	OFF	ON	OFF	ON	Enclosure Leakage Current: Reversed Mains Input: Single Fault condition (Supply Open)
8	OFF	ON	OFF	OFF	ON	Enclosure Leakage Current: Normal Mains Input: Single Fault condition (Earth Open)
9	ON	ON	OFF	OFF	ON	Enclosure Leakage Current: Reversed Mains Input: Single Fault condition (Earth Open)

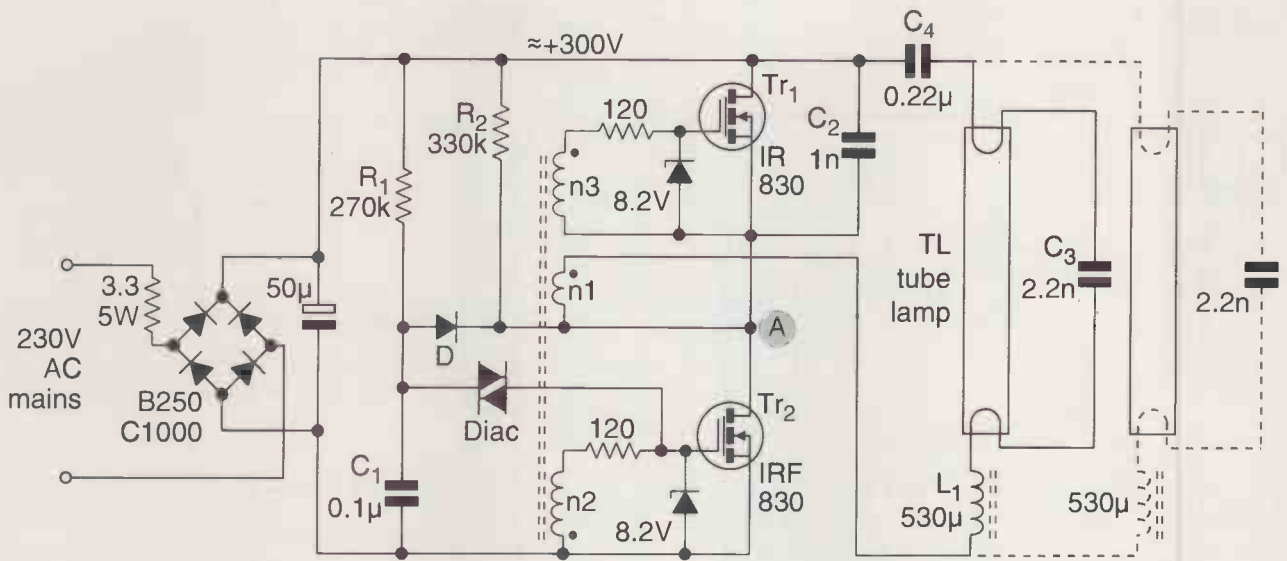Instant flicker free turn-on fluorescent lamps



Electronic power supply devices for lighting purposes are widely used in low-power, so called energy saving lamps. However, in the larger power TL or TLD tube lamps for domestic use, no such solutions are found. This circuit was developed to provide instant, flicker-free turn-on of the popular 1.2/36W and 1.5/50W lamp types by means of a h.f. power oscillator working at about 115kHz. An additional benefit of the h.f. feed is the better light efficiency as compared to the present-day 50/60Hz installations.

After switching-on the mains, resistor R1, capacitor C1 and the Diac form a low-frequency sawtooth oscillator which feeds a series of short pulses into the gate of T2 until the gate capacitance is sufficiently charged and T2 starts to conduct. T2 draws current from the power supply via n1 of transformer TR, inductor L1, capacitor C3 and capacitor C4. The current through n1 induces feedback voltages in n2 and n3, as a result of which the h.f. oscillator starts. Resistor R2 keeps diode D blocked until the start of the main oscillator after which the voltage on C1 is kept low by D and T2.

The frequency of the h.f. oscillator is in the first instance determined by the series-resonance circuit L1 - C3, and is about 145kHz. In resonance, the voltage on C3 exceeds the ignition voltage of the tube (about 1600V) and the tube turns on. After turn-on, the voltage on C3 collapses to the value for normal working conditions, about 320Vp, and the frequency drops to 115kHz due to the heavy loading of C3.

COMPONENTS:

Transformer TR

n1, n2 and n3 wound on ferrite ring core, outer diameter 14mm, me 2000 - 3000
 n1: 4 turns*
 n2: 6 turns
 n3: 6 turns
 All in solid insulated copper wire

*with 2 lamps in parallel: n1 = 2 turns

Inductor L1

Ferrite potcore 26/16mm, me 220, 28 turns of stranded insulated copper wire (litz)
 (The use of 0.7mm solid copper wire is an alternative but may result in a too low Q value to turn the lamp on)

Capacitor C3

A high quality polypropylene type is needed here, again because of circuit Q
 Working voltage 1000Vdc at a minimum.

The signal at point A is a clean square wave with an amplitude equal to the supply voltage, about 300V. Capacitor C2, removes any possible switching spikes, The current through the tube, about 470mA, is controlled by L1; a smaller inductance gives a higher current. The transistors operate in an on/off mode and will need only a little heat sink, if any. The values for frequency and current are valid for one tube connected. However, the circuit is capable of feeding two tubes in parallel (and is in use as such). The only change needed is halving the number of turns for n1.

Fred J. Hofman
 Bellingwolde
 Netherlands

A novel power good indicator circuit for isolated power supplies

In many electronics systems isolated power supplies at various voltage levels are used. Ground isolation of these power supplies is a must to achieve electromagnetic compatibility. A circuit that gives single power good indication maintaining ground isolation among various power supplies is required for such power supplies.


The circuit presented here is a simple and effective solution to a generate power good signal in multiple output power supplies. The circuit is used for a SMPS in which $\pm 18V$, 12V and 5V isolated supplies are generated. It is required to give a power good LED indication on front panel while maintaining ground isolation when the $\pm 18V$ supply voltage level is above $\pm 17V$, and when 12V supply level is between 11.5 and 13V and when the 5V supply voltage level is above 4.7V. To achieve this each power supply voltage level is compared with a respective threshold level. The threshold level is set with combination of zener diode and diode or LED. When supply voltage is higher than the threshold set level, current flows through the photodiode of the respective opto-isolator. The threshold level for the 18V supply is set by a 15V zener diode in series with diode 1N4148. For the 5V supply voltage two green LEDs (D3-D4) are connected in series to set the threshold.

In a case where higher level is also to be sensed, a transistor is added to the basic threshold detection circuit mentioned above that

bypasses the current in the diode of the opto-isolator. In this circuit it is incorporated for the 12V supply. For the 12V supply the lower threshold is set by a 9V zener in series with a green LED (D-5). When the input voltage exceeds 11.5V, the opto-isolator diode conducts. If the supply voltage is higher than the higher level (13V) the transistor (T1) turns on and the current in the photodiode of the opto-isolator is bypassed that turns off the opto-isolator transistor. All the opto-isolator transistors are connected in series. When all the voltage levels are proper all the opto-isolator transistors are on and then only power good indicator LED glows. A suitable supply voltage (5V here) among the various available is selected to power up the power good indicator LED and accordingly the resistor value R2 is calculated. This circuit function can be described as wired AND of optically isolated signals where parallel electrical input signals are logic high when each input voltage level has particular range.

In this circuit four pin opto-isolators (HCPL 817 or equivalent) are used that provide a compact package for this application. The circuit

A novel power good indicator circuit

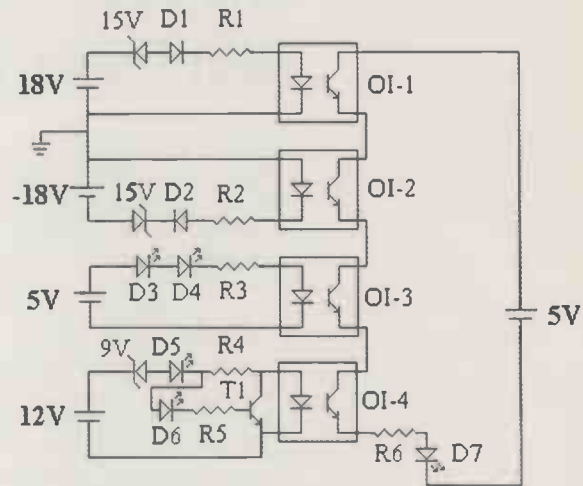

D1-D2 Diode 1N4148, D3-D7 LED, T1 BC547C, OI 1-4, Optoisolator HCPL817 or equivalent, R1-R5 220Ohm, R6 1.8kOhm. (all 1/4W) D7 is Front panel LED.

can be easily adapted for sensing of any other voltage levels (or ranges as done for 12V supply) by properly setting the threshold voltage levels as per specific requirements.

S.V.Nakhe
Indore,
India

Digital Dice

IC1a & IC1b operate as an oscillator at a frequency of about 4kHz. The frequency of oscillation is not critical, it simply needs to be high enough to prevent cheating.


IC2 and IC3 are Binary Counters configured to count in binary from 1 to 6. I found C4 necessary to prevent an oscillation on the transitions. The count sequence is:-

.A 'power on reset' is not required since, if the initial state is outside the correct range, the counters will count into the correct range after a few clock pulses.


Consider IC2 first. When the counter reaches 7 (i.e. 111), the AND gate

formed by R3, D1 & D2 applies a High to PE and this presets the counter to 1 (i.e. 001) thus PE goes Low. The counter then increments in the normal manner until it reaches 7 again. Counter IC3 operates in the same manner except that the clock signal is derived from IC2/Q3.

Count Sequence		
Q3	Q2	Q1
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0

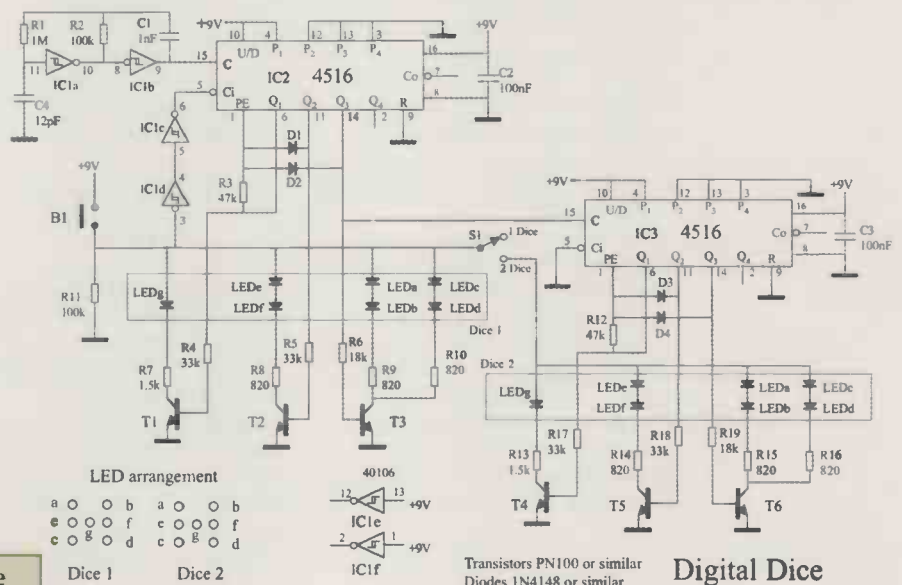

LED arrangement

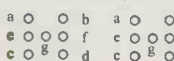

Dice 1 Dice 2

Normally, the counters are incrementing continuously. When button B1 is pressed, IC1d/4 goes Low and IC1c/6 drives the Ci input of IC2 High thus stopping the counters.

B1 also applies +9 Volts to the LEDs to enable them. Transistors T1 to T6 are turned on by Highs on the Q

Transistors PN100 or similar
Diodes 1N4148 or similar

Digital Dice

outputs thus the LEDs indicate the states of the counters. When B1 is released, counting continues.

If two dice are required, S1 is set to the '2 Dice' position thus enabling the second dice.
Len Cox
Forest Hill,
Australia

Analogue single span 0-180° phase shifter with linear phase control

This novel analogue circuit has a variable, single span 0-180° phase shift, virtually linear depending on the setting of a pot. By taking 90° phase shifting and the control function apart, an extremely simple control is possible. The essential part of the circuit consists of a potentiometer loaded with a negative resistor.

Common analogue phase-shifters are hampered by a strong non-linear relationship between control and the resulting phase shift. Another nuisance of many circuits is a voltage gain depending on the selected phase. Analogue circuits that accomplish large variable phase shift like the all-pass filter, never combine a linear single span 0-180° phase shift with only one variable control element. With exception of the all-pass network, all the phase shifters have an absolute gain that varies with the phase setting. Unfortunately the all-pass network exhibits a non-linear relation between control resistor and resulting phase. Furthermore the 0-180° range requires the control resistor to vary from zero to infinity. The presented circuit has a nearly ($\pm 1.05^\circ$) linear relation between potentiometer setting and resulting phase shift. The maximal gain change is a mere $\pm 3.4\%$.

The circuit consists of a potentiometer with known resistance loaded with a negative resistor as indicated in **Figure 1**. The output voltage is taken from the wiper. U_0 is the input voltage, $-U_0$ is its inverse and jmU_0 is a scaled, 90° shifted voltage source. The setting of the pot is given by a ; $0 \leq a \leq 1$. $a=0$ corresponds with 0° phase shift, $a=1$ corresponds with 180° phase shift. At

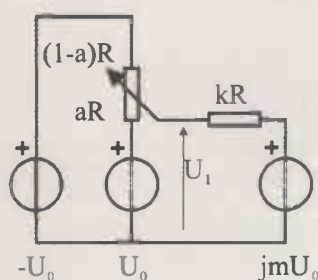


Figure 1

the halfway setting, $a=0.5$, the real components cancel and only the 90° shifted signal stays. These three points are one straight line. k is the ratio of the absolute value of the resistor and the total resistance of the pot. The gain of this circuit as a function of the pot setting is given by

$$\frac{U_1}{U_0} = \frac{k(1-2a) + jm(\alpha - \alpha^2)}{k + \alpha - \alpha^2}$$

The modulus equals

$$\left| \frac{U_1}{U_0} \right| = \frac{\sqrt{k^2(1-2a)^2 + m^2(\alpha - \alpha^2)^2}}{|k + \alpha - \alpha^2|}$$

the argument is given by

$$\varphi = \tan^{-1} \left(\frac{m\alpha - \alpha^2}{k - 1 - 2a} \right)$$

Minimizing the peak error of

$$|\varphi - \pi \cdot \alpha|$$

results in a peak phase error of $\pm 1.054^\circ$ at $m/k = 2.7105$.

Minimizing the gain error,

$$\left| \frac{\sqrt{k^2(1-2a)^2 + m^2(\alpha - \alpha^2)^2}}{|k + \alpha - \alpha^2|} - 1 \right|$$

while using $m/k = 2.7105$, results in $k = -0.7752$. With $m/k = 2.7105$ implies this the value $m = -2.101$. The gain varies only $\pm 3.4\%$ around 0.966, its nominal value.

Figure 2 shows the circuit of the variable-phase oscillator as used in our low-cost low frequency lock-in amplifiers. The essentials are drawn in bold. All resistors are 1% metal film types, the capacitors are 10% polyester foil types. The 10kΩ pot (R), a wire-wound precision 20 turn potentiometer, sets the phase. Conductive plastic potentiometers cannot be used, due to their large tolerances (typical 20%) on the total resistance. The division ratio of an unloaded potentiometer doesn't depend on its resistance. Opamp #IV together with the resistors 10kΩ,

10kΩ and 7752Ω form the negative resistor kR. 7752Ω can be realised by the E24 resistors 8k25 and 121k in parallel. The factor m has been realised in the two-phase oscillator by changing the time-constant of the integrator containing Opamp #II. The circuit with Opamp #I is a positive integrator, allowing for easy implementation of gain control needed for stabilising the amplitude of the oscillations. See ref. 1 for details on the oscillator circuit.


Opamp # III is a sign inverter and the buffer amplifier, Opamp #V, removes any unintended loading of the pot. A not depicted amplitude stabiliser completes the variable phase oscillator. The odd value of 2k265 ($10k \cdot 1/m^2$) can be obtained by the series connection of two standard E24 resistors: 2k21 and 562Ω. By changing the value of this resistor, one can compensate for tolerances in the capacitor values at expense of a frequency change. The frequency of the oscillator depends on the two integrator time-constants and equals

$$f = \frac{m}{2\pi \sqrt{R_1 C_1 R_2 C_2}}$$

$R_1=R_2=10k\Omega$ and $C_1=C_2=100nF$, giving 334Hz. The measured 322Hz deviates because of capacitor tolerances. In our lock-in application the 0° and -90° outputs are fed to voltage-comparators that drive the MOS-switches. The comparators allow $\pm 3.4\%$ amplitude changes. The sine output is made really independent of the phase setting by action of the amplitude stabiliser.

Checking the circuit's actual performance necessitates two minor changes in the diagram shown. The amplitude stabiliser has to be connected to the output of Opamp #II in order to stabilise its voltage. In our case at 2.10Vrms. The second modification is the addition of a switch in the connection of the negative resistor, the + input of Opamp #IV, to the pot's wiper. The small residual voltages at the inputs of Opamp #II and #III, 0.46mV $\angle -90^\circ$ and 0.22mV $\angle -90^\circ$ respectively, make correction of the

Figure 2

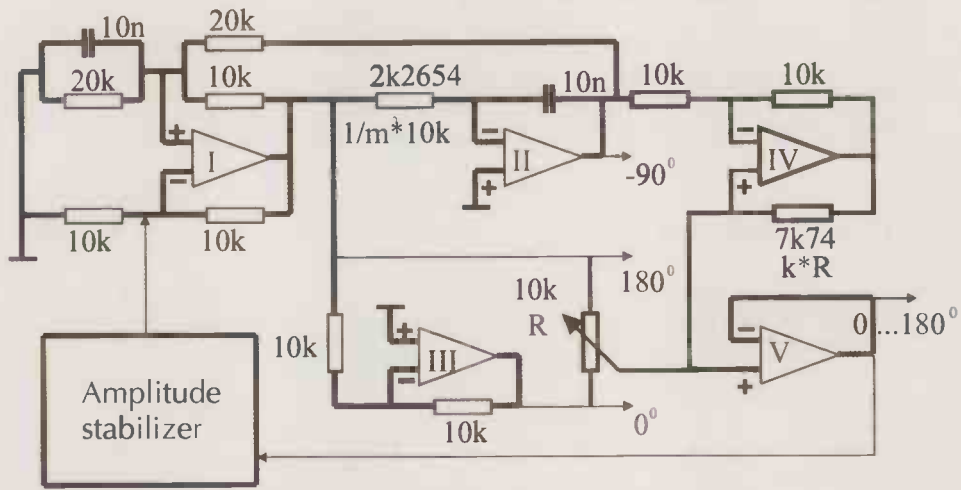

Variable-phase 3 kHz oscillator. OpAmps 741 type

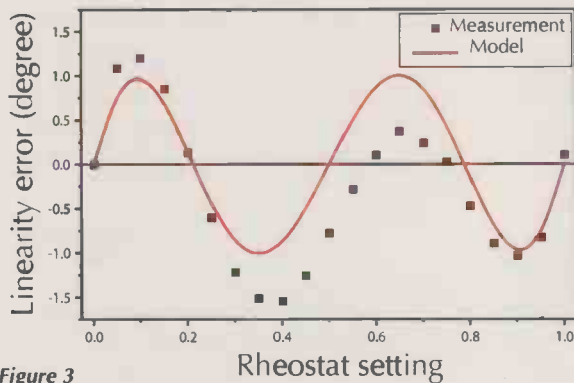


Figure 3

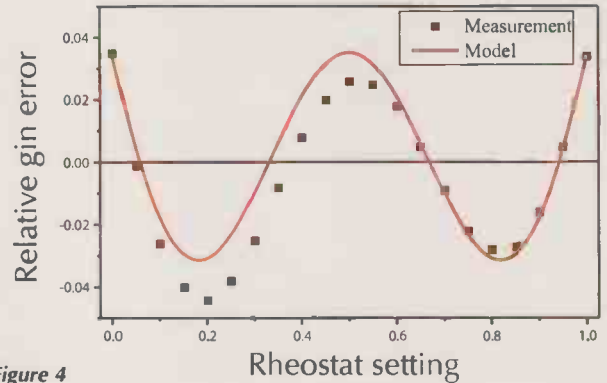


Figure 4

ideal transfer functions unnecessary. The distortion, mainly 2nd harmonic, is 54dB below the fundamental. The 2k26 resistor is tuned to have 1.000Vrms at the 0° output. To do the measurements on the circuit we used a PAR model 128A lock-in amplifier. Its reference input is connected to the 0° output of the circuit. Open the switch between the negative resistor and pot and measure, via a voltage divider if necessary, the In-phase output voltage of Opamp #V at 0° and 180° settings of the pot. These U_{zero} and U_{full} are used in conjunction with $U_{actual\ setting}$ to measure the actual pot setting

$$\alpha = \frac{U_{zero} - U_{actual\ setting}}{U_{zero} - U_{full}}$$

This removes any non-linearity of the pot setting from the measurement. Having determined α , the switch can be closed and the circuit operates as described. Now the In-phase and

Quadrature voltages U_I and U_Q can be measured, giving

$$U_{abs} = \sqrt{U_I^2 + U_Q^2}$$

in the actual circuit about 1.0 V_{RMS} and

$$\varphi = \tan^{-1} \frac{U_Q}{U_I}$$

Figure 3 displays the phase error

$$\left(\frac{\varphi}{\pi} - \alpha \right)$$

* 180 and Figure 4 displays the gain error

$$\frac{2U_{abs}}{U_{zero} - U_{full}} - 0.966$$

as a function of α . The similarity of the simple electrical model and the

actual circuit is for practical applications only limited only by the precision of the components used. The phase shifter circuit can also be used to shift a whole spectrum of frequencies. The necessary 90° shifted spectrum can be acquired by a so-called dome network³. For a broad spectra with large f_{max}/f_{min} ratio a poly phase sequence network⁴ is a more appropriate method for generating the necessary 90° shift.

K. Heeck,
Amsterdam, The Netherlands

References:

- Modern Operational Circuit Design*, John I. Smith, John Wiley & Sons Inc. ISBN 0-471-80194-1, page 161-162
- Aktives Potentiometer mit Tangens-Kennlinie*, Dipl.-Ing. Bernd Lücke, Elektronik pp. 62-64 Heft 11 1980
- Wideband Phase Shifter Networks*, R.B.Dome, Electronics pp. 112-115 December 1946
- A symmetric poly phase network*, M.J.Gingell, British patent 1,174,710 filing 7th June 1968

Letters to the editor

Letters to "Electronics World" Highbury Business Communications, Nexus House, Azalea Drive, Swanley, Kent, BR8 8HU
e-mail EWletters@highburybiz.com using subject heading 'Letters'.

Charging challenge

Charging a capacitor through a resistor is a basic element of electrical theory. The illustration shows the circuit.

The derivation for the voltage across the capacitor seen in at least three text books I have on my shelf goes something like – and here I have not deliberately introduced errors but I have used voltage whereas some use charge.

On closing the switch, the following holds.

The rate of change of voltage on the capacitor


$$\frac{dV}{dt} = \frac{i}{C}$$

The current flow to the capacitor

$$i = \frac{V_0 - V}{R}$$

So the capacitor voltage is given by

$$\frac{dV}{dt} = \frac{V_0 - V}{RC}$$

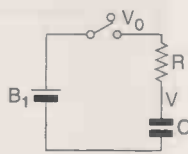

Re-arranging,

$$\frac{dV}{V_0 - V} = \frac{dt}{RC}$$

Integrating,

$$\log(V_0 - V) = \frac{t}{RC} + k$$

where k is the constant of integration. Anti-logging gives

$$V_0 - V = \exp\left(\frac{-t}{RC}\right) \times \exp(k)$$

As k is constant, the term exp(k) is also a constant. At t=0, V=0, making the constant V0. This gives

$$V = V_0\left(1 - \exp\left(\frac{-t}{RC}\right)\right)$$

This expression is correct, but the derivation contains some howlers. I suspect that readers of *Electronics World*, who never knowingly let errors pass them by, may be able to state what is wrong with the above.

John Ellis

Political correctness

Following Phil's request for a more politically correct version of Master Slave, here is my suggestion:

My auntie Ethel has had an idea which might fit the bill.

All devices have equal status, (thus removing the offensive Master, Slave relationship) and they all contend for use of The Medium (a Mrs. Cable at number 12).

A message is passed to Mrs. Cable and she blabs it all round the neighbourhood.

If any house is busy or empty she returns later and tries again.

I think she might be on to something here, we might patent her idea.

Ethelnet would seem a good name.

Just a thought.

Charles Coultas

By email

War time radio


This is a follow-up to letters I have written to you in recent months concerning the Nazi development commercially available Wireless receiver sets. As was pointed out in the original article, these sets lacked sensitivity. But they did not need to be - in the 1940's to avoid Allied Aircraft from using Commercial Radio Stations from using the German Transmitters as homing beacons to bombing raids over their cities, the Germans used a sort of 'Wired-wireless' landlines to carry the RF signal directly to home receiver sets.

In Britain in the 1930's PBX signals were sent directly to homes without any RF transmission at all, just audio signal on an electric current running at 85 Volts. I discovered this in the recent issue of *Practical Electronics* Vol. 32 # 11.

Chad Castagana

Woodland Hills, California, USA

Puzzle

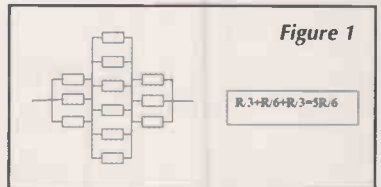

In reply to Raymond G. Lee in *EW* Jan 2004 issue, I was introduced to this problem by either Chris Priest or Dr. Robin Moffet, two colleagues at Plessey Telecoms Research Ltd. in the 70s. I tackled it by remembering a technique taught to me at college - namely simplifying the circuit by shorting out points of equal potential. (Cyril Bateman & Hugh Mirans used the same technique in the December issue). The circuit becomes as per Figure 1).

A technique used by my colleagues was basically based on Kirchoff and inspection. This is much easier and more obvious with a space model rather than an isometric drawing.

Note that upon leaving and entering the circuit the current splits into three and then in between it splits in two again giving:

$$V = IR/3 + IR/6 + IR/3$$

$$V = 5R/6 \dots \dots \dots \text{as before.}$$

Ray D. Smith (Ex PTR, GPT & Marconi)

Appleton
Warrington
UK

Stolen identity

Please keep the history articles coming! The latest, about J. A. Fleming's work on the thermionic triode, covers a particularly important episode. But that photograph of Fleming looked familiar. Then I remembered: it isn't Fleming at all. The very same picture appears on the front cover of Paul Israel's biography of Thomas A. Edison. Perhaps it's a good thing Edison was part of the story as well!

Alan Robinson

By email
Whoops! - Ed.

Not worthy

WOW!! I must have upset Seb. I thought my previous letter would be my last, a more snobbish and arrogant letter I've yet to read.

He seems to be saying that I am not worthy to read *EW* and that I should buy a 'lesser' mag, and that you should not allow someone like me to have a letter printed in *EW*.

I have been buying *EW* & *WW* since 1981 on a permanent basis, I find it provides 'cutting edge' audio circuitry. I realise his 'mentor' is D. Self, although I am on JLH's side of the fence. In my last letter I praised D. Self as someone who deserves 'worldwide acclaim'. I also said I could live with someone who is arrogant and patronising. I should have qualified this by saying I can accept this from people who are worldwide winners in their fields, as is D. Self, Linford Christy and Micheal Shumacker.

Can Seb explain why all power amps which have 100dB distortion can 'sound' different? I.e. reproduce music, with a different tonal basis, even when the frequency responses are identical.

If we were talking about hoovers, TVs or washing machines then I would have no problem with his replies but we are talking about music.

Seb can't reply to me without being subjective ie from his point of view, all life is subjective,

unlike him I can see both points of view and will praise those who deserve it, from both camps.

Cyril Bateman's articles on the capacitor distortion are excellent plus, the very reason I buy *EW*. Somebody wrote into *EW* to say that Cyril's demolition of expensive electrolytes is 'one in the eye' for the 'golden ear', quite true but a bit of tunnel vision, did he not read November 2002 article in which he says that metallised pet capacitors distort the musical reproduction, JHL and the 'Golden ears' have been saying this for 22 years now, therefore should JLH insure his ears as they seem to on a par with the latest 'cutting edge' computer software. How that science has proved JLH right, will we get an apology from his critics?

Justin Underwood writes in critical of Cyril's work as far as need is concerned, Why don't Justin and Seb write to each other as Seb worships science, and, quite rightly, praises D. Self for zero distortion, and Justin seems to say it is not required. I'm audio reproduction. I'm on Cyril's side.

As a last comment on my poweramp, Seb seems to say less is better (number of stances). I'm not D. Self, and have no intention of ripping off D. Self's Power amp circuit. My amp incorporates part circuits from JLH, D. Self, and others and yes it is more

complicated than D. Self's. Do you not know the pleasure I get from a home built amp that isn't an exact copy of anybody else's. My only problem was a 3 millivolts (RMS) of noise, I changed every BJT to low noise, very disappointing, little difference. I then removed the Hitachi T03 Mosfets from the right angled metal strip and sanded down the surface. I then fitted four ceramic washers taken from an industrial power supply; surfaces must be smooth, tightened it all down and bolted back onto the heat sink. I powered up, shorted input and connected an 8 Ohm load and connected my oscilloscope probe to the output as well as my audio millivolt-meter.

I was very pleased to see that the noise was, as I thought, all coming from the output devices, when hot. I measured 170 microvolts a gigantic drop, leaving on for ½ hour it rose to 190 microvolts, not to bad for a 1¼A quiescent current, for +/- 26 VDC voltage rails at 8 Ohms. Distortion is now down to -95dB at 20 Kcs. Still not in D. Self territory buy I'm happy.

I hope you don't ex-communicate me from *EW* and strange as you may think I don't hold any animosity for Seb, only sorrow.

Mr D Lucas
Anstruther,
Fife,
Scotland,
UK

Poor Circuit Ideas

From a brief scan of your magazine Feb 2004, I decided to buy a copy. The article on analogue switching by D. Self is excellent. However the standard of some of the 'circuit ideas' needs some improvement.

The article Electronic water level interlock, Page 45, I expect might work, however there are a few errors. The sponsors have no limiting resistor for the I Base of Q1. The use of 'iron nails' in water would be O.K. for a short-term use only because of corrosion. Also arcing will occur at the N.C. contacts, as the diode I feel ought to be across Relay 2 coil, and not the D.C. supply.

The Alkaline charger article Page 39 has the same oscillogram dis-

played on the left & right hand side of the page. Also there is no explanation of what is happening within the BC337 the base / emitter being reversed biased, presumably goes into reverse breakdown. I wonder about long-term reliability problems? Also a normal type of trickle charge would seem adequate for a 1V battery. So; why is the 4700µF (10V) and BC337 necessary for a single cell? The test refers to a red LED. The diagram shows only green or orange. There is a specific comment that 'only the specified transistors, LED colours, zener voltage and power ratings should be used.' Why?

It would appear that the circuit is difficult to repeat. In what is not

generally a poor quality magazine, might we see some improvement in the future.

P. G. Diestlin
Manchester
UK

You are quite correct about the two identical oscillograms – this was a cock-up on my part. The two figures were in fact two different scans of a paper copy. I forgot to tell the layout dept. that it was an 'either or' situation not both. And I did not spot it whilst proofing. I would also point out that your very own letter had more than a few typos. Pot, kettle and black?

Valve Base Pages Equivalents

O (ZERO)—All entries under “zero” and “O” will be found together under O in the alphabetic section of the index. Where individual manufacturers have indicated either zero or O this has been followed in the tables.

Ooer

The 0 or O debate may be settled for the OC series but may just rumble on a bit longer for the OZ4 gas rectifier. This page from the RCA receiving tube manual clearly shows the OZ4 with an ‘O’ and the OZ4A with an ‘O’.

Paul Bennett
By email

The O or 0 controversy

The following may be a source of the ‘O’, ‘0’ confusion. I’m still not sure what exactly it’s saying.

From Radio Valve Data compiled by the staff of Wireless World 1965 edition, page 124: “O (ZERO)—All entries under zero and O will be found together under O in the alphabetic section of the index. Where individual manufacturers have indicated either zero or O this has been followed in the tables.”

I also attach a photo of an OC 140 and the source material.

Tony Meacock
Norwich,
Norfolk
U.K.



FULL-WAVE GAS RECTIFIER OZ4A

Metal type used as a power rectifier in equipment with vibrator-type power supplies. Outlines section, 2A; requires orbital socket. This tube, like other power-handling tubes, should be adequately ventilated.

MAXIMUM AND MINIMUM RATINGS (Design Center Values)

Peak Inverse Plate Voltage (Per Plate)	500	volt
Peak Starting-Stoppage Voltage (Per Plate)	250	volt
Peak Plate Current (Per Plate)	110	mA
DC Output Current	50	mA

TYPICAL OPERATION WITH VIBRATOR-TYPE POWER SUPPLY AND CAPACITOR INPUT TO FILTER

Peak Plate Supply Voltage (Per Plate)	110	volt
Filtering Capacitor	5000	μF
Total Effective Plate Supply Impedance (Per Plate)	110	ohms
DC Output Current	100	mA

CHARACTERISTICS

Tube Voltage Drop for current of 110 mA (Per Plate)	2.1	volt
-----------------------------------------------------	-----	------

MINIMUM CIRCUIT VALUE

Total Effective Plate-Supply Impedance (Per Plate)	500	ohms
----------------------------------------------------	-----	------

*Absolute value. Under no circumstances should the tube be operated below the value of characteristic values (the portion of transformer voltage wave). Refer to chart at end of section.

OZ4G

EMC

Responding to the Cyril Bateman (always respected) reply in your January issue to my November issue missive, I concur with most of what he says, excepting perhaps that I fail to properly understand EMC filters.

Axiomatically, of course efficacy is down to VSWR with both the filter and the source imparting attenuation. Cyril nicely elucidates the situation, especially specifically for a 50Ω source and load. That’s not a common luxury though. I merely countered by way of extreme examples and reference, that ferrites can confer the resistive component, when Cyril’s letter blanket stated minimal absorption by EMC filters. On first reflection the absorption will generally be minimal but reflections blat back and forth. Something somewhere in the system has to dissipate the undesired, and if ferrites be the determining resistive element then ultimately the EMC filter will be the main agent of attenuation.

Attention to ferrite characteristics can optimise performance. Other times the EMC filter resistive contribution can only be minimal. Ach, Cyril knows all this and one could air the subtleties of disparate systems till the kye come home but EMC is pretty simple stuff really. Dull too.

On a more profound level it is true that I don’t understand – knowledge

unveils avenues of ignorance.

Dunno why Cyril (may I call you Cyril? Andrew to you) infers I don’t use caps and resistors for EMC. One exploits what is appropriate; ferrites, caps, resistors, lead dressing, screening, soggy cabbages if they do the job. Didn’t say the washing machine was out of the box either. Do pay attention in the back row Bateman Major – we shall be asking questions later :-). On one occasion, expedience even led to the use of a multi-band receiver to determine radiation and ameliorate it. The EMC test centre didn’t object.

On the subject of my Norwegian Blue washing machine whose door glass is now happily reincarnated as a salad bowl, do I take it that Cyril is not of the Zen and the Art of Washing Machine Maintenance persuasion? It can be a life changing experience to run a washing machine ‘out of the box’. Never scoped a washing machine and have no burning desire to do so either. Wilful things. The beast was just mega noisy over a wide range of photon energies.

As I said, justifiably anthropomorphising, it snubbed its nose (rather than its spikes) at the statutory regs which Cyril mentioned. The igniter in my central heating system is even worse, though admittedly it is so old

it has flood marks. Sends the cordless phone into paroxysms – on the ‘to do’ list. Another annoyance is TV radiation on my VLF metal detector designs (just a tad more advanced than the recent discussions) but now’t I could do about the submarine and geophysics VLF except shift my frequency.

On a slightly desultory note I would like to thank Cyril for his energetic and assiduous contributions. It’s heartening to have confirmation of component characteristics, known but hitherto somewhat undocumented. Thanks too to *EW* for being the vehicle. My only preference, rather than criticism, is that it would be good to have more of ‘Cyril’ in his writing.

Essence can be drowned in a welter of punctiliousness. Electronics is fun, even hilarious – *Circuit Ideas* sometimes testifies to this. At work, last week’s lab discussions ranged from naked singularities in the canteen, to Pentiums defaulting to 8086 mode, to a simple little triac circuit blowing the server trips, to the influence of J-Lo’s posterior on tectonic subduction.

Tell us your stories Cyril.

Andrew S Robertson
Girvan
Ayrshire
UK

Airborne lasers

I note that Mr. Phelan of Dublin (Letters, EW, March) is amazed at "your sense of wonder as to why CD/MD/DVD players are banned on some flights"

So, yes, it does seem that Fairy Stories are still popular in Ireland! I am not aware of the standards applied to aircraft maintenance in the Republic. But with this possible exception, the rest of the flying public need not be concerned. Passengers are asked not to use electronic equipment during take off and landing as a sensible precaution against RFI. If every passenger tried to use his or her mobile phone, the RF noise level inside the externally screened cabin could be very considerable. Nice try Edward!

Chris Chapman
By email

Airborne lasers II

I was amazed to see the ludicrous suggestion from Edward Phelan (*EW Letters Mar 2004*) that the ban on portable CD players on aircraft had something to do with the laser - even more worrying that a pilot could show such ignorance. There is nothing 'magic' about laser light - it's just light, and infinitely less bright than that from the cabin lights.

The actual reason stems from when portable CD players first appeared, as they were the first common consumer portable devices to use high speed digital clocks (tens of MHz) and switch mode DC-DC converters.

At the time, aircraft were being designed and certified for high immunity to external RF sources (radar, radio transmitters etc.), but internal sources had not been considered, so some airlines restricted them as a precaution.

However the initial concerns about CD players seem to have 'stuck', even as other digital devices came along using far higher clock frequencies. I heard a particularly ridiculous announcement on a plane few years ago: "Laptop computers may be used, but the CD drive must not be accessed." Such technical ignorance is a little worrying to say the least!

Most airlines now seem to have settled down to what most people would agree is a reasonable compromise, by prohibiting the use of any electronic devices during takeoff and landing only.

Mike Harrison
By email

Re: Self

The notion of 'multi-path' reflections at the ionosphere in long distance propagation was used in a recent

article' about interference to short wave reception (from internet transmission through mains electric cables), although the evidence suggested otherwise. Pat Hawker G3VA illustrated³ two alternatives, chordal hops or surface waves, the latter supported by recent sub-ELF data², 0.8Hz ($z=Z_{ed}$) in $c = \lambda f$ gives λ equal to Earth-Moon spacing (3.75×10^6 m), with a spatial node, allowing provision for the stronger 0.4 Hz half-wave fundamental as well as the weak 0.2Hz signal analogous to the closed-pipe fundamental - for longitudinal waves!

Tiller's long-period (26.087 minutes, $f=6.39 \times 10^{-4}$ Hz) data² in $c = \lambda f$ is inconclusive but, in $c = 2\pi Rf$, correlates well with an 'interspatial belt' between Earth and Mars for a limit-cycle involving resonance decoherence, which would explain the 'echo-effect' in 'whispering-galleries', inter alia⁴!!!

1. 'New Scientist', 10th January 2004, page 30; 6th December 2003, page 26
 2. 'EW', January 2003, Letters page 42, ref 1; December 2003, page 58, ref 3
 3. 'Amateur Radio Techniques', RSGB Pub., 4th Edn. 1972, pp.214-5, 207
 4. 'Horizon', BBC TV, Seismic Resonance, Bernard Chouet.
- Mr. A G Callegari BSc., MPHIL. (Lond.)*
Much Hadam, Herts, UK

Wheatstone

As the author of the Wheatstone Bridge article (*EW*, April 2003) which seems to have initiated exchanges on experimental error, I would like to make a couple of points.

I agree with the theory of Mr Bailey's comments in his letter printed in *EW*, February 2004. However, he and earlier correspondents have missed an essential point, which relates both to mine and most practical Wheatstone Bridges. In these, one of the resistance arms is a compound component, being built from four decades of resistors. For this arm, a small value 'units' component which is as much as 100% inaccurate will add little error to the overall value of this resistor arm provided (a) it really is small (e.g. a marked 1 Ohm component is in fact 2 Ohms but not a 9 Ohms resistor being 18) and (b) the thousands decade value is large and as accurate as possible. It would seem from Mr. Bailey's argument that having one low value resistor 100% inaccurate would render all measurements potentially subject to a 100% error. Clearly this is absurd. In fact it is rather difficult to determine a general value for the maximum error when using a compound component.

Secondly, the article described a particular technique to achieve very high accuracy when using my Bridge

design to measure resistors in the range from about 1k to about 10k Ohms. This involved the arithmetic averaging of two experimental results; the first being produced normally and the second by reversing appropriate arms of the Bridge. As I showed algebraically, this technique appears to remove all first order errors in two of the resistance arms.

Analogue switching

Reading the first instalment of D. Self's article on electronic analogue switching (*EW* Jan 2004, pp 11) gave me a feeling of Déjà Vu. Indeed, some 24 years ago I occupied myself with similar research, which led to the design of a Programmable Audio Attenuator, which used electronic analogue switches to produce a gain change range of 60dB in 1dB steps (*WW* May 1980, pp 65). I finally adopted the CD4007 IC as switching elements, as these contain in a single 14 pin DIP a trio of SPDT JFET switches. The need for a combination of series and shunt switches in some cases, as also identified by Mr. Self, is therefore quite easily satisfied. The 4007 has all gates directly accessible, allowing soft switching to be implemented, almost completely suppressing switching transients. I used a combination of 1M ohm resistors and 1.8nF caps for this. It is a pity that this IC is apparently not known to Mr. Self; it solves some identified problems elegantly. A few other refinements that I missed in Mr. Self's articles are the use of asymmetrical supply voltages for the 4000 series. By using +7.6VDC and -8.2VDC, the distortion of the complete unit was further decreased in comparison with the case of +/- 7.9VDC (Using the max allowed voltage of course minimises THD to begin with). The other refinement concerns the switching of small capacitors in simple RC LP filters in combination with high attenuation switching to compensate for the frequency response rise resulting from feed through in off-switches. (On the other hand, the use of the gate bootstrap resistor is a nice touch, one I didn't think about at the time). By using highly optimised circuit topologies and component values, each channel of the attenuator is realised with just 5 inexpensive '4007's.

I realise that it is difficult for an author to know everything published on a subject, but it is slightly disappointing if a publication in our own beloved *EW* (then still *WW*) is missed.

Johannes M Didden
Strassen
Luxembourg

THERE IS INTERESTING NEWS

THE FIRST USB 2.0
100 MS/S, 12-16 bit
MEASURING INSTRUMENT
IN THE WORLD

PC CONTROLLED MEASURING INSTRUMENT COMPLETE PACKAGE STARTING AT £ 435

OSCILLOSCOPE


FFT ANALYSER

VOLTMETER

RECORDER

The Handyscope 3 is a powerful and versatile two channel measuring instrument with an integrated function generator.

- USB 2.0 connection (USB 1.1 compatible)
- sample speed up to 100 MHz per channel
- 8 to 16 bit resolution (6 μ Volt resolution)
- 50 MHz bandwidth
- input sensitivity from 200 mV up to 80 Volt
- large memory up to 131060 samples per channel
- four integrated measuring devices
- spectrum analyser with a dynamic range of 95 dB
- fast transient recorder up to 10 kHz
- several trigger features
- auto start/stop triggering
- auto disk function up to 1000 files
- auto setup for amplitude axis and time base
- auto trigger level and hysteresis setting
- cursor measurements with 21 read-outs
- very extensive function generator (AWG) 0-2 MHz , 0-12 Volt

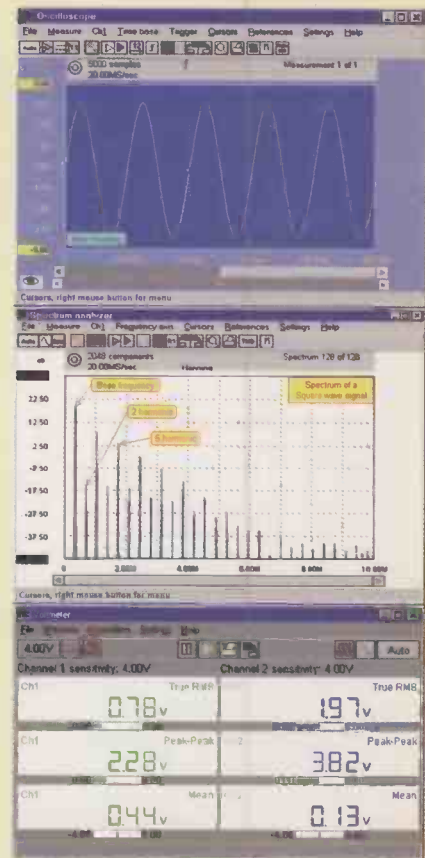

HANDYSCOPE HS3

for more information, demo software, software, source code and DLL's visit our Internet page: <http://www.tiepie.nl>



TiePie engineering (NL)
Koperslagersstraat 37
8601 WL SNEEK
The Netherlands
Tel: +31 515 415 416
Fax: +31 515 418 819

TiePie engineering (UK)
28, Stephenson Road, St. Ives
Cambridgeshire, PE17 3WJ, UK
Tel: 01480-460028
Fax: 01480-460340

The longest project ever?

We all have those projects that we start but never get round to finishing but here is a challenge to your readers. I think that I have completed the longest running project ever – unless, of course, you know otherwise.

I left university in 1979 and completed my electronics apprenticeship at British Aerospace surrounded by sophisticated test equipment. I decided that I wanted a frequency counter and I was going to design it myself. I built the oscillator-display-counter board over the summer of 1979 and drafted some additional circuits for range switching and the input block. I then moved house and changed jobs into IT so had little time for completing it. Then I got married, had kids and the above board languished at the bottom of my junk box. In the mid 1990s I found time to tinker with wires and such and came across this lost, lonely and dusty board and decided to complete the project. I dabbled with high speed

input amplifiers (which always seem to prefer being oscillators) and function switching logic. The dabbling did not come to much other than to prove that I had forgotten all the laws of physics. So, again the board returned to its dust collection role in 1998.

In late 2001 my kids were teenagers, Y2K was no more than an embarrassing memory in IT departments and I had a bit more time. So, I again played around with high speed input circuits that still wanted to oscillate but, after many hours, tamed the beast and proceeded to build the rest of the circuits. By now, the functional requirements of the unit had grown like topsy and I wanted it to do everything. Dozens of spider-web prototype circuits piled up in the corner of the workbench as I converged on a design that did almost everything and discarded the failures. Survival of the fittest, I suppose.

The final test and assembly was completed in January this year and

the project has ended. I even opened a bottle of Spanish Champagne to celebrate. Of course, my wife has no interest in what a frequency counter/period timer/pulse width timer/event counter with continuous or one-shot modes does. Or even cares. She politely humours me and my project perhaps because I started it before I met her.

My tardiness does bring me a particular problem: the older parts of the circuit were built with chips that are now obsolete so don't ask about serviceability! Of course, it would have been much more sensible (and cheaper) to go out and buy a second-hand frequency counter for £50 but we spend too much of life being sensible. Have fun!

So, twenty-four and a half years to successful completion. Any advance on that?

Mike Arnold
Sale
Cheshire
UK

Vibrator replacement

Concerning Jeremy Stevens' circuit idea 'Electronic Half Bridge Replaces Mechanical Vibrator.....' (*EW, Feb04*), I am not convinced that the circuit is a true half bridge, since unlike a normal commutating version; the power mosfets are turned on simultaneously. Furthermore, these two devices are connected in series with opposite ends of the floating transformer primary winding; the switched current is unidirectional and the same through both devices.

This implies that similar results would be achieved using a simple power mosfet, so enabling the majority of the circuit to be eliminated.

I do not understand how the transformer can 'see exactly the same input waveform' as it did when the vibrator was used; the primary drive current is simply switched and no longer reversed.

I do not dispute that the circuit can generate the required 1+T (probably because the transformer's secondary winding is tuned by C1 to resonate at the drive frequency) but I question its mode of operation. It would be interesting to observe the effect of shorting out Q5.

K Cummins
Chale Green
Isle of Wight
UK

Vibrator replacement II

I was impressed with Jeremy Stevens' method of converting an ancient radio to 12V operation without adding an external box (Electronic half-bridge replaces mechanical vibrator in 6V to 12V conversion' (*Circuit Ideas p40 EW Feb04*).

However, and correct me if I am wrong, I think he could save a few components next time. As far as I can see, the circuit is not actually acting at a half-bridge converter, as both Q3 and Q5 conduct at the same time. It is more of a forward/fly-back converter with both ends of the primary inductor switched.

If I am right only Q3 is required. Q5 with all of its associated drive circuitry (Q1, 2, 4 & 5) could be omitted – Q5 being replaced by a short circuit across its drain-source connections. D3, 4 & 5 could also go. And if D6 was replaced with a faster device, R10 could be replaced with a

less power hungry series RC with quite a small C and a lower-power R.

Unfortunately, these changes would remove Mr Stevens' clever way of preventing over-voltage across C1 during warm-up.

So either:

- Add a simple switch-on timer (replace IC1 half a hex inverter and use some of the spare gates as the timer) or
- Short Q3's base drive with a voltage monitor, made with a couple of diodes, a zener and a transistor, connected to T1's outputs or
- Keep Q5 and its drivers, and ditch Q3 instead, making appropriate alterations to the diode bridge.

I hope you can pass this on to Mr Stevens, with my thanks for an inspiring circuit and something to fill the time with on the train home tonight.

Steve Bush
Surbiton, UK

Battery tester

In *Circuit Ideas* January issue, D. Di Mario described a very useful car battery tester. I built a basic version of it, but could not make his exact circuit as I there is a misprint.

Could he please give the correct wiring for the x1/x10 switch? In the text he says that the 100 Ohm pot is marked 2-100Ah. I assume it should say 32-100Ah? Also, what purpose does the 5.1V zener serve? As pin 5 of

a 555 is set at 8V internally (on a 12V supply) there is about 4V across the zener. One final point that confuses me: the ripple across the battery is of the order of tens of mV, so what does the IN4006 in the meter circuit do?

These comments are not meant as criticism: I'm just interested! Thanks.

Jonathan Wellingham
Bristol, UK

The text error was in fact ours – this CI came in on paper and the OCR mis-read some bits. – Ed.

The New Scholasticism

There is widespread refusal to confront alleged problems in the reigning basic theories in science. The science I am most familiar with where this occurs is electromagnetic theory, though I know of other blatant cases, for instance theory of flight.

On the subject of displacement current, our article in December 1978 pointed out that electric charge entering the plate of a capacitor did not immediately desire to traverse the space between the capacitor plates. (Bleaney is wrong when he writes that the field between the plates is uniform.) After entering the capacitor plate from the input wire, the charge first has to spread itself across the plate. Only then can it express a desire to traverse the space between the plates.

This desire led to "Maxwell's leap of genius", Displacement Current. Maxwell himself, and all those who followed him and worshipped him, failed to notice that after entering the capacitor plate from the input wire, the charge had first to spread itself across the plate. This intermediate step has been ignored by all text books and lecturers. Since we pointed it out in 1978, it has been ignored for a further quarter century. All of today's textbooks are written as though this problem, of charge spreading out across the plate, remains unnoticed, like the Emperor's nakedness.

The spreading out of electric charge across the capacitor plate is real electric current, and must cause a real magnetic field, according to Ampere's Rule or the Biot-Savart Law. The alleged genius of Maxwell was that the notional electric current, called by Maxwell "Displacement Current", was invented to produce a magnetic field and so lead to key conclusions. Since the key (and only) purpose of Displacement Current is to cause a magnetic field, it is unacceptable that there continues to be no discussion of the magnetic field which must be caused by the much more real electric current as the electric charge spreads out across the plate from the incoming wire.

So, I pose the question - when a TEM step travels at the speed of light down the vacuum between two parallel plane conductors, a problem was noticed in 1982, now renamed "The Catt Question". The TEM Wave travelling in a coaxial cable with vacuum dielectric is a more easy way to picture the same question. The Catt Question, camouflaged by w for a century, was first noticed in

1982. Prior to that, the only signal discussed was a sine wave, which buried the problem in fancy maths. If the sine wave is replaced by a simple step, the problem becomes obvious for the first time. It is now discussed.

After the step has passed, there appears extra negative electric charge on the surface of the negative conductor to terminate the lateral lines of electric flux between the positive conductor and the negative conductor. Where does this extra charge come from? It took many years of painstaking work to elicit a single reply from each of two luminaries, who totally contradicted each other, and then went silent. All other accredited "experts" also remain silent.

For more than a century, it has been fashionable to drool over Maxwell's Equations, and assume that others have grasped their physical import. For decades, I insisted that I had never doubted Maxwell's Equations. I knew that a hint of such behaviour would lead to ex-communication. Like everyone else, I kept away from them and avoided investigating them. In spite of this, my major advances in electromagnetic theory, and also my computer inventions, were totally suppressed by all journals in the world for some decades.

Some time after Tom Ivall, then editor of *Wireless World*, began to publish my material, I ventured to investigate Maxwell's Equations. I was shocked by what I discovered, and published what I found in *Wireless World*. Since Ivall was my ally, and all other journals in the world still totally boycotted me, I felt I would lose nothing by rocking the Maxwell boat. Ivall had already been threatened for publishing less controversial material by me. There has been more or less no response to my publications on Maxwell's Equations.

In all these three cases, all publication and teaching continues as though what I have said has never been said. The reader is challenged to give reference to any textbook or syllabus that refers in any way whatsoever to my discussions.

We assiduously add more and more bells and whistles onto a brittle structure which has been frozen since about 1920. The structure, which requires avoidance of the above questions, serves no purpose beyond rewarding those who live within its glass home, who live off those they can entice within it. My co-author researched key insights removed from later editions of a standard

textbook. This raises the interesting spectre, that we are not just standing still. We are moving backwards.

I have spent many years trying to understand why there exists so little grasp of the physics of a logic step travelling from one gate to the next. I found that not only students, but also lecturers, have no access to information on the TEM Wave. The TEM Step is the key electromagnetic element in all digital computers, and therefore in 99% of all electronics today. I have found that none of the books in the British Library or in the IEE Library in London discuss the TEM Wave. Heaviside had a complete grasp of the TEM Wave. He had to, because he was sending Morse pulses, or TEM pulses, down a cable from Newcastle to Denmark. A century later, when I arrived in Motorola R&D at the inception of high speed digital electronics (1nsec ECL), I also had to master it. The whole of digital electronics is vulnerable because even today's lecturers have no access to insight into the TEM Wave. They will certainly not learn from Heaviside, whom their textbooks and lectures ignore, or from me. They insist that I do not exist. Ask your lecturer about Catt. He will reply; "Who?"

Ivor Catt

*St. Albans
Hertfordshire
UK*

Further reading:

The material in this letter can be reached via
www.ivorcatt.com/41.htm or
www.electromagnetism.demon.co.uk/41.htm.

Theory of Flight: <http://www.ivorcatt.com/2606.htm>

Displacement Current:
<http://www.electromagnetism.demon.co.uk/z001.htm>

<http://www.ivorcatt.com/2635.htm>

Catt Question:
<http://www.ivorcatt.com/28anom.htm>

<http://www.electromagnetism.demon.co.uk/catanoi.htm>

Maxwell's Equations:
<http://www.ivorcatt.org/ic3804.htm>

<http://www.ivorcatt.com/2804.htm>

Moving Backwards: <http://www.ivorcatt.com/2607.htm>

TEM Wave: <http://www.electromagnetism.demon.co.uk/17136.htm>

<http://www.electromagnetism.demon.co.uk/20136.htm>

The Heaviside Signal:

<http://www.ivorcatt.com/2604.htm>

http://www.ivorcatt.com/1_1.htm
figures 4, 5.

PROTEUS

The Complete Electronics Design System



Schematic & PCB Layout

- Powerful & flexible schematic capture.
- Auto-component placement and rip-up/retry PCB routing.
- Polygonal gridless ground planes.
- Libraries of over 8000 schematic and 1000 PCB parts.
- Bill of materials, DRC reports and much more.

Mixed Mode SPICE Circuit Simulation

- Berkeley SPICE3F5 simulator with custom extensions for true mixed mode and interactive simulation.
- 6 virtual instruments and 14 graph based analysis types.
- 6000 models including TTL, CMOS and PLD digital parts.
- Fully compatible with manufacturers' SPICE models.

Proteus VSM - Co-simulation and debugging for popular Micro-controllers

- Supports PIC, AVR, 8051, HC11 and ARM micro-controllers.
- Co-simulate target firmware with your hardware design.
- Includes interactive peripheral models for LED and LCD displays, switches, keypads, virtual terminal and much, much more.
- Provides source level debugging for popular compilers and assemblers from Crownhill, IAR, Keil, and others.

Virtual System Modelling

New Features in Version 6

- Drag and drop toolbars.
- Visual PCB packaging tool.
- Improved route editing.
- Point and click DRC report.
- Multiple design rules (per net).
- Multiple undo/redo.

Call Now for Upgrade Pricing

Works with
PIC Basic Plus
from Crownhill
Associates

labcenter

Electronics
53-55 Main Street, Grassington. BD23 5AA

Tel: 01756 753440
Fax: 01756 752857

Contact us for
Free Demo CD

www.labcenter.co.uk
info@labcenter.co.uk

Bare LCD display drive in embedded applications

In embedded applications it is often needed to interact with the user by means of displaying numbers or simple texts. LED displays with seven or 14 segments per character are available at low cost and in many different sizes, however they consume a lot of current and this restricts their use in battery powered applications. Daniel Malik explains.

LCD modules driven by HD44780 or compatible controllers have simple interface and low power consumption, however they cost more and their dimensions are often too large to fit into small enclosures.

Bare LCD displays offer both low power consumption and small size, however their drive is usually considered non-trivial. This article aims at explaining the basic principles of Twisted Nematic displays and disclosing one possible method of their drive without a specialised interface circuit or microcontroller peripheral.

Principle of LCD operation

Properties of Liquid crystal materials were discovered in 1888 by an Austrian botanist, F. Renizer. These materials were not suitable for commercial use however. The first nematic crystals which retained their properties even at room temperatures were developed in 1960s, but the real breakthrough came when cyanobiphenyl materials were discovered. These have large positive dielectric anisotropy and a strong birefringence, which makes them almost ideal for the twist cell.

The most common LCD is called the twisted nematic (TN) display. This display consists of a nematic liquid crystal sandwiched between two glass plates. The inner glass surfaces are coated with a transparent metal oxide film which acts as an electrode used to apply voltages across the cells. A polymer alignment layer is placed on top of the electrodes and microscopic

grooves are created in it during the manufacturing process, which force the crystal molecules to align in parallel to the grooves. Layer of polymer spacer beads is eventually applied to one of the glass plates to maintain uniform gap between the two, the plates are placed together and the edge is sealed with epoxy. A small hole is left in the epoxy and the liquid crystals are injected between the plates through this hole under a vacuum. After the hole is sealed, polarizers are applied to top and bottom surfaces of the display. In TN displays the alignment layers and polarizers are created perpendicular to each other, which forces the crystal molecules to twist by 90 degrees under no voltage conditions - see left side of Figure 1.

The light entering the display from the top is polarised by the top polarizer and as it travels through the liquid crystals its polarisation rotates with the molecules. When it emerges, its polarization has been changed by 90 degrees and it passes through the bottom polarizer. However when a voltage is applied to the electrodes, the molecules will arrange vertically - see right side of Figure 1. In this case polarisation of the light passing through the liquid crystals remains unchanged and is blocked by the bottom polarizer.

It is important to minimise DC component of the display drive signal, otherwise electrolysis process will develop and eat-up the electrodes eventually. The optical effect or contrast ratio produced by a segment depends on the applied RMS voltage. An example of TN display optical characteristics can be seen in Figure 2.

TN display drive

When using the LCD display, the goal is obviously to keep voltage below the threshold voltage V_T on those segments we want to appear invisible and above the saturation voltage V_S on those segments we want to appear dark. There is one more parameter used to describe LCD displays and their drives: bias ratio. This is simply the ratio V_S / V_T . It can be seen that bias ratio of the drive (i.e. ratio between the RMS voltage on the dark segments and RMS voltage on the invisible segments) must be bigger than bias

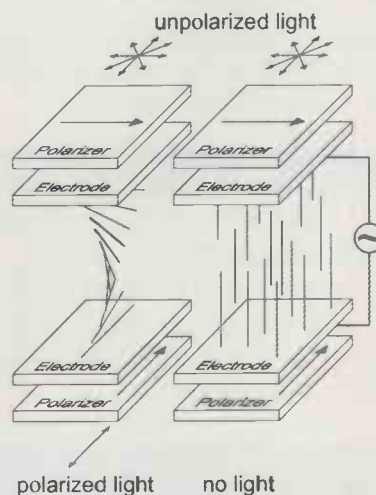


Figure 1: Basic principle of TN display operation

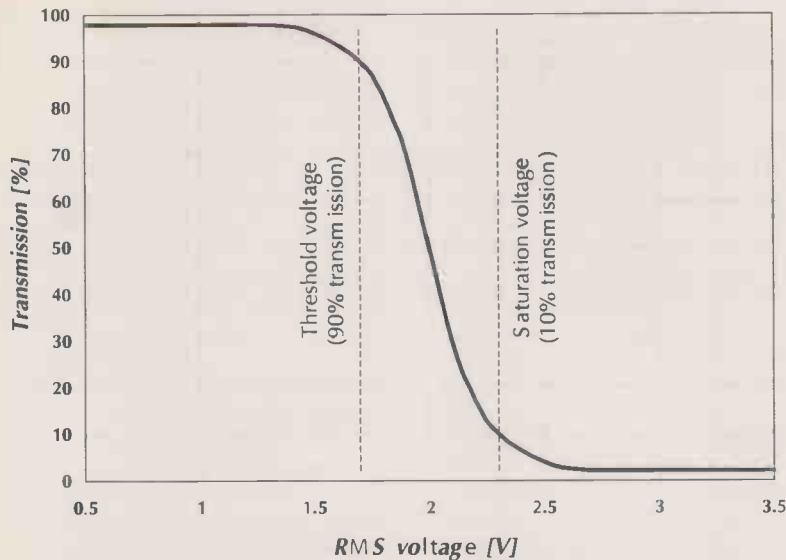


Figure 2: Typical optical response of TN display versus applied voltage

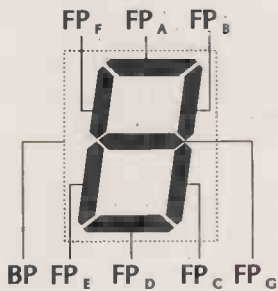


Figure 3: Example of statically driven LCD. There are two basic types of LCDs as far as their drive is concerned: static and dynamic.

Drive of static LCDs

Static LCDs have only one background electrode and one terminal for each segment they can display.

Therefore 7-segment static display capable of displaying one digit will have 8 terminals in total (see Figure



Figure 4: Drive waveforms for static LCDs.

3). Drive waveforms for such display are shown in Figure 4.

Voltage on the invisible segments approaches zero and voltage on the dark segments approaches full supply voltage. The drive bias therefore approaches infinity and no other drive scheme can be better as far as display contrast is concerned. This drive scheme is very simple to implement on general purpose I/Os of a microcontroller and this is why this type of displays is very popular.

Drive of dynamic LCDs

If the driving scheme for static displays is so simple to implement why should we bother with any other type of LCDs? Since the static displays have one terminal for each segment, the number of terminals starts to rise very quickly when we try to add more digits on the same display. In case the LCD has pins (as opposed to rubber strip or thermally bonded flat cable), the added pins increase cost of the display. Another problem is to place all the terminals at the top and bottom edges of the display and it may therefore prove difficult to make the display small enough. Another fact is that we need one GPIO pin for each display segment on the microcontroller side.

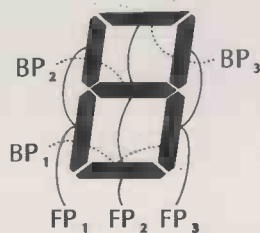


Figure 5: Example of dynamically driven LCD.

The higher the pin count of the microcontroller, the larger the package and cost (number of pins and package size contributes to the microcontroller cost more than one would guess). All these reasons led to attempts to organise the display segments into a matrix (just like buttons in a keyboard).

The dynamic LCDs (also called multiplexed) have multiple backplane electrodes and the frontplane pins are shared by multiple display segments. Example of dynamic LCD is shown in Figure 5. Now the challenge is to

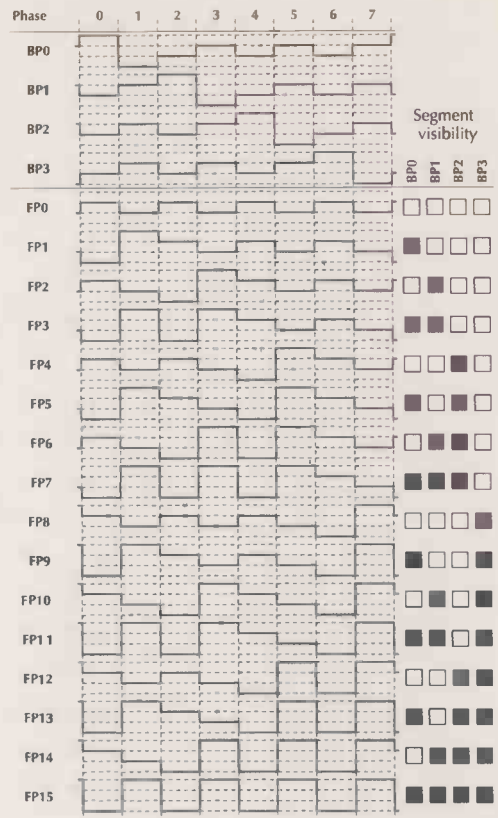


Figure 6: Traditional LCD waveforms.

create waveforms for all the frontplane and backplane pins which would ensure that all the segments we want to appear invisible receive voltage below V_T and all the segments we want to appear dark receive voltage above V_S . How the waveforms should look like is far from obvious. Specialised LCD drive circuits and microcontroller peripherals normally use waveforms outlined in Figure 6 (shown for the case of 4 backplane electrodes).

These waveforms have bias ratio of 1.73 and use 4 discrete voltage levels on all pins. It is easy to see that synthesis of these waveforms without the specialised circuit or peripheral would be quite difficult. Fortunately another driving scheme exists, which can be easily implemented on GPIO pins of a microcontroller. The modified waveforms are shown in Figure 7. These have bias ratio of 1.53 (approx. 12% lower than the original waveforms).

The main advantage is that now we need just 3 discrete voltage levels for the backplane electrodes and only 2 voltage levels for the frontplane electrodes. This is much simpler to implement and circuit similar to the one shown in Figure 8 can be used. The third (middle) voltage level on the backplane electrodes is achieved by configuring the GPIO pin in question as input and allowing the

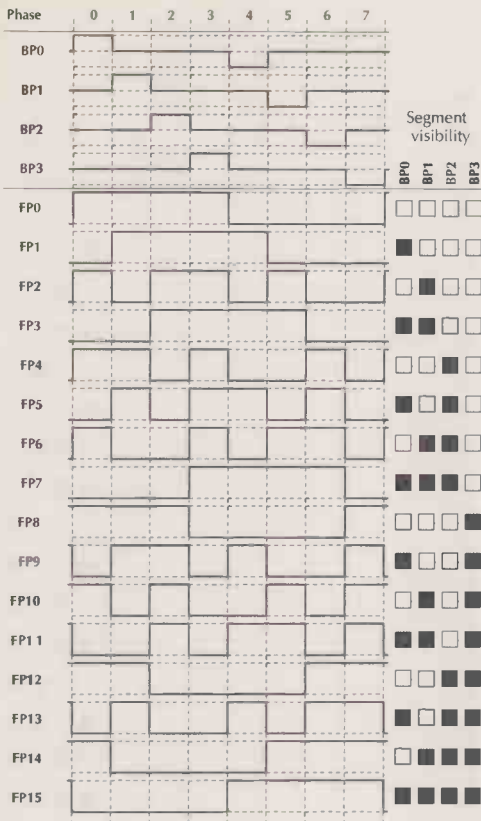


Figure 7: Modified LCD drive waveforms.

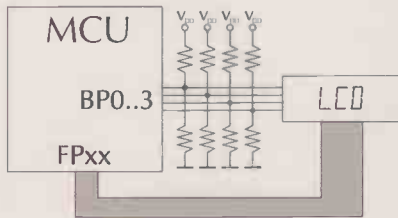


Figure 8: Application circuit.

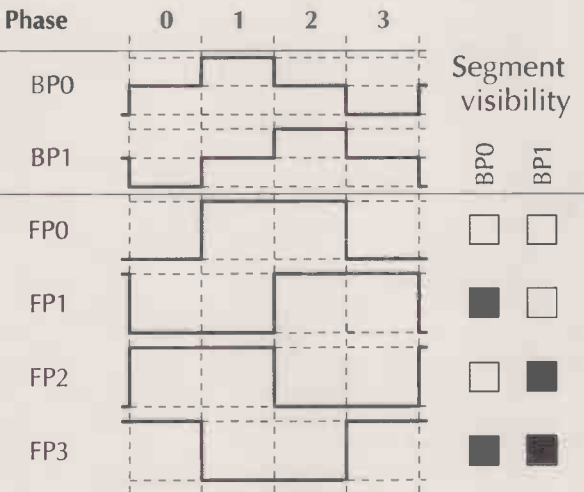


Figure 9: Modified waveforms for two backplane electrodes.

external resistors to define the voltage level. Of course similar waveforms can be devised also for other numbers of backplane electrodes, waveforms for 2 backplane electrodes are shown in Figure 9. It is common property of all the driving schemes, that the bias ratio goes down with the number of backplane electrodes. Therefore higher supply voltage of the microcontroller is needed for displays with higher level of multiplexing. Displays with 2 backplane electrodes can be driven from supply voltage of 3V, however displays with 3 and more backplane electrodes require higher supply voltages of the microcontroller. Since modern microcontrollers run happily from below 3V up to 5V, adjusting the supply voltage is the easiest way of matching the drive voltage requirements of a particular display. In case the supply voltage of the microcontroller is fixed at 5V, dummy cycles can be introduced into the driving scheme to lower the voltages between the display electrodes.

Driving algorithm

An algorithm for driving the display can be devised from the driving waveforms. An example algorithm for display with 4 backplane electrodes is shown below.

This algorithm is relatively easy to implement. Reaction times of TN displays depend on temperature and are usually around 150ms. This allows relatively very slow refresh rates, display manufacturers usually recommend rates around 30Hz. Since the above algorithm has 8 phases, the required interrupt rate to drive the display is 240Hz, which implies very low workload for the MCU. Using higher refresh rate only increases the microcontroller workload and power consumption (since the display is effectively a capacitive load).

Photographs of displays with four and two backplane electrodes driven by general purpose

MC68HC908GP32 microcontroller from Motorola are shown in Figures 10 and 11.

Phase	Action
0	BP0 high, BP1,2&3 middle, FPx receive negation of data for BP0 segments
1	BP1 high, BP0,2&3 middle, FPx receive negation of data for BP1 segments
2	BP2 high, BP0,1&3 middle, FPx receive negation of data for BP2 segments
3	BP3 high, BP0,1&2 middle, FPx receive negation of data for BP3 segments
4	BP0 low, BP1,2&3 middle, FPx receive data for BP0 segments
5	BP1 low, BP0,2&3 middle, FPx receive data for BP1 segments
6	BP2 low, BP0,1&3 middle, FPx receive data for BP2 segments
7	BP3 low, BP0,1&2 middle, FPx receive data for BP3 segments



Figure 10: LCD display with four backplane electrodes.



Figure 11: LCD display with two backplane electrodes.

BACK ISSUES

Back issues of Electronics World are available, priced at £3.50 in the UK and £3.75 elsewhere, including postage.

Please send correct payment to:
Electronics World, Highbury Business Communications, Nexus House, Azalea Drive, Swanley, Kent BR8 8HU

Note that not all issues are available and please allow 21 days for delivery

Electronics World's phenomenal news section starts on page 4

ELECTRONICS WORLD

MARCH 2004 £3.50

Hybrid audio amplifier

The Diode: the first electronic device

Talented USB interface

Capacitance meter


Circuit ideas:

- Programmable temperature controller
- Harsh multi-driver
- Linear diode simulator

Real stars in your eyes


The Electronics World Book Service offers access to our team of specialist publishing experts. We can order any book or CD-ROM currently in print from *War And Peace* to the *Reference Data for Engineers*. All books are delivered free of charge within the UK unless otherwise stated. Order form opposite.


If you are ordering by credit card, need further information, or would like to use our search facilities, call **01737 812727** Fax **01737 813526**
 The order/helpline is open from 9am to 5pm, or leave your order on our out-of-hours answerline or email us at salesteam@boffinbooks.demon.co.uk
 When placing orders please quote
 ● Name ● Address (home & delivery) ● Daytime telephone number ● Debit/Credit card number
 ● Expiry date ● Details of order. Please note prices may change, but are correct at time of going to press.

TCP/IP EMBEDDED INTERNET APPLICATIONS

Edward Insam
 This text highlights an engineer's approach to Internet protocols and applications, reducing R&D time for engineers. The book aims to be the main design guide for the cutting edge of Internet-enabled electronic products and systems.
 Aug 2003 ▲ 384 pages ▲ Index ▲ Appendix
 PB ▲ Published in UK
 Code 0-7506-5735-9 **£32.50**

ELECTRONIC CLASSICS: COLLECTING, RESTORATION AND REPAIR

Andrew Emmerson
 This text encompasses all aspects of buying, collecting, restoring, repairing, sourcing parts, professional services, clubs and societies. The first part covers technical aspects of restoration and details where components can be found. The second part presents useful information for collectors.
 Aug 1998 ▲ 256 pages ▲ Index
 10 half-tones ▲ 50 line illustrations ▲ PB
 Published in UK
 Code 0-7506-3788-9 **£21.99**

NEWNES GUIDE TO TELEVISION & VIDEO TECHNOLOGY

Eugene Trundle
 An exploration of television and video technology. It covers the fundamentals of digital television (satellite, cable and terrestrial) and digital video, as well as providing a grounding in analogue systems.
 3rd edition ▲ Feb 2001 ▲ 432 pages ▲ Index
 PB ▲ Published in UK
 Code 0-7506-4810-4 **£17.99**

NEWNES GUIDE TO DIGITAL TV

Richard Brice
 Covering all aspects of digital television, this text encompasses the electronics of the equipment, data compression, television production, servicing and the different transition methods - terrestrial, satellite and cable. The text has been updated with developments since the 2000 edition.
 2nd edition ▲ Oct 2002 ▲ 304 pages ▲ Index
 45 illustrations ▲ 15 photographs ▲ HB
 Published in UK
 Code 0-7506-5721-9 **£24.99**

RSGB RADIO & ELECTRONICS COOKBOOK


Radio Society of Great Britain
 Only a basic knowledge of electronics is assumed for this collection of electronics projects, and it is ideal for all electronics and DIY enthusiasts and experimenters. Designed by the RSGB, the UK radio amateurs federation, the projects are clearly explained step by step.
 Nov 2000 ▲ 336 pages ▲ PB ▲ Illustrations
 Published in UK
 Code 0-7506-5214-4 **£17.99**

REFERENCE DATA FOR ENGINEERS: RADIO, ELECTRONICS, COMPUTERS AND COMMUNICATIONS

Mac E Van Valkenburg; Edited by Wendy Middleton
 Written by professionals for professionals, this is a complete reference for engineers, covering a broad range of topics. As well as addressing radio technology data, it covers digital electronics, computers and communications.
 9th edition ▲ Aug 2001
 1568 pages & CD-Rom ▲ 1385 line illustrations
 HB ▲ Published in UK
 Code 0-7506-7291-9 **£90.00**

NEWNES GUIDE TO RADIO AND COMMUNICATIONS TECHNOLOGY

Ian Poole
 This is a guide to the technology and applications of modern radio and communications equipment. The author's approach provides a useful foundation for college students and technicians seeking an update on the latest technology.
 Jul 2003 ▲ 352 pages ▲ Index ▲ PB
 Published in UK
 Code 0-7506-5612-3 **£16.99**

DICTIONARY OF VIDEO AND TELEVISION TECHNOLOGY

Jack Tsatsoulin
 This work provides comprehensive and contemporary information on the essential concepts and terms in video and television, including coverage of test and measurement procedures. The CD accompanying the text includes an electronic version of the book.
 Sept 2002 ▲ 365 pages & CD-Rom
 Published in UK
 Code 1-878707-99-X **£29.99**

INTRODUCTION TO DIGITAL SYSTEMS


John Crisp
 This self-study text introduces digital electronics from first principles, before going on to cover all the main areas of knowledge and expertise. It covers the practicalities of designing and building circuits, including fault-finding and the use of test equipment.
 Feb 2000 ▲ 302 pages ▲ Glossary ▲ Index
 PB ▲ Published in UK
 Code 0-7506-4583-0 **£18.99**


NEWNES DICTIONARY OF ELECTRONICS


S W Amos; R S Amos
 Aimed at engineers, technicians and students working in the field of electronics, this dictionary provides clear and concise definitions, including TV, radio and computing terms, with illustrations and circuit diagrams.
 4th edition ▲ Mar 2002 ▲ 394 pages
 100 illustrations ▲ PB ▲ Published in UK
 Code 0-7506-5642-5 **£12.99**


PRACTICAL ELECTRONIC FAULT FINDING AND TROUBLESHOOTING

Robin Pain (Design Engineer, Cotag International Ltd)
 A text using simple circuit examples to illustrate principles and concepts fundamental to the process of analog and digital fault finding. It aims to help the reader tackle any job, from fixing a TV to improving the sound of a hi-fi. A digital multimeter and oscilloscope are needed for these jobs.
 Apr 1996 ▲ 284 pages ▲ Index
 50 line illustrations ▲ PB ▲ Published in UK
 Code 0-7506-2461-2 **£21.99**

PRACTICAL ELECTRONICS HANDBOOK

Ian Sinclair
 A collection of all the key data, facts, practical guidance and circuit design basics needed by a spectrum of students, electronics enthusiasts, technicians and circuit designers. It provides explanations and practical guidance, and includes new sections on SHF techniques and intruder alarms.
 5th edition ▲ Feb 2000 ▲ 571 pages
 Illustrations ▲ PB ▲ Published in UK
 Code 0-7506-4585-7 **£16.99**

FUZZY LOGIC FOR EMBEDDED SYSTEMS APPLICATIONS

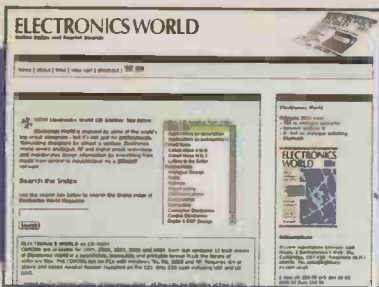Dr Ahmad Ibrahim
 Written by a recognised expert in the field, this covers all the basic theory relevant to electronics design, with particular emphasis on embedded systems. It shows how the techniques can be applied to shorten design cycles and handle logic problems that are tough to solve using conventional linear techniques. All the latest advances in the field are discussed, and practical circuit design examples presented.
 Oct 2003 ▲ 312 pages ▲ PB
 Code 0-7506-7605-1 **£35.00**

ANALOG INTERFACING TO EMBEDDED MICROPROCESSORS

Stuart Ball
 Provides hard-to-find information on interfacing analog devices and technologies to the purely digital world of embedded microprocessors. Gives the reader the insight and perspective of a real embedded systems design engineer, including tips that only a hands-on professional would know. Covers important considerations for both hardware and software systems when linking analog and digital devices.
 March 2001 ▲ 288 pages ▲ PB
 100 line illustrations
 Code 0-7506-7339-7 **£19.99**



WEB DIRECTIONS

Put your web address in front of 18,000 electronic fanatics.

Electronics World acknowledge your company's needs to promote your web site, which is why we are dedicating 2 pages in every issue to WEB ADDRESSES.

Linage only will cost £150 + vat for a full year.

Linage with colour screen shot will cost £350 + vat for a full year, this will include the above plus 3cm shot of your web site which we can produce if required.


To take up this offer or for more information telephone Luke Baldock

Tel 01322 611289

E-mail


l.baldock@highburybiz.com

CHYGWYN
www.chygywn.com

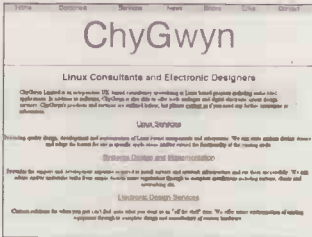


ChyGwyn Limited offers electronic design and embedded software development for remote monitoring, embedded appliances, set-top boxes and similar devices. We are experts in customisation of Linux and write device drivers for custom hardware.

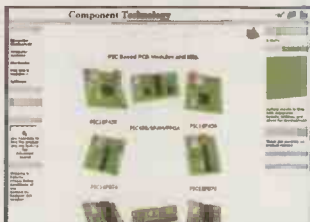COMPONENT TECHNOLOGY
www.componenttechnology.co.uk



- PIC microcontroller kits and modules for students and hobbyist.
- 18F45X, 16F87X Proto-Boards for ease and fast development of project ideas.
- Infrared Illuminators for CCTVs in low ambient light security areas.
- Analogue 8-channel high voltage isolator. Data logging.
- 5% discount code 'elvwdir2004' for Electronics World readers.
- Consultancy
- TIG control systems – REIS interface.
- Real-time X-ray Imaging.

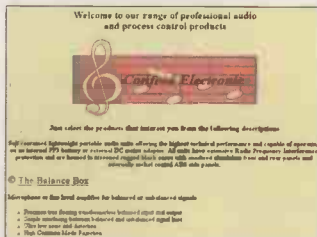CONFORD ELECTRONICS
www.confordelec.co.uk/index.shtml



Lightweight portable battery/mains audio units offering the highest technical performance. Microphone, Phantom Power and Headphone Amplifiers. Balanced/unbalanced signal lines with extensive RFI protection.

CRICKLEWOOD ELECTRONICS
www.cricklewoodelectronics.co.uk



Cricklewood Electronics stock one of the widest ranges of components, especially semiconductors including ICs, transistors, capacitors, all at competitive prices.

DB TECHNOLOGY
www.dbtechnology.co.uk/
EMC Testing and Consultancy.



Anechoic chamber and open area test site.


- Compliance Tests
- Rapid, accurate pre-compliance tests.
- Fixes included. FCC Listed.
- Flexible hourly booking available.

DESIGNER SYSTEMS CO
www.designersystems.co.uk




Electronic product design company with over a decade of experience promoting it's own product range and designing and manufacturing innovative products for client companies/individuals.

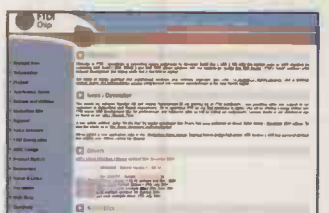FUTURE TECHNOLOGY DEVICES INTL. LTD.
www.ftdichip.com



FTDI designs and sells USB-UART and USB-FIFO interface i.c.'s. Complete with PC drivers these devices simplify the task of designing or upgrading USB peripherals

GREENWELD
www.greenweld.co.uk

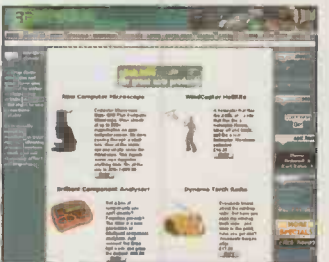

Whether your interest is in electronics, model engineering, audio, computer, robots or home and leisure products (to name just a few) we have a wide range of new and surplus stock available.

To reserve your web site space phone Luke Baldock
Tel: 01322 611289 Fax: 01322 616339

NORCALL Ltd
www.tetra-com.co.uk



Suppliers programmers and repairers of new and refurbished two-way radio equipment. Retuning and recrystallising service available. All types of batteries chargers and aerials supplied. e-mail Norcall@aol.com

QUASAR ELECTRONICS
www.QuasarElectronics.com



Over 300 electronic kits, projects and ready built units for hobby, education and industrial applications including PIC/ATMEL programming solutions. Online ordering facilities. Tel: +44 (0) 870 246 1826 Fax: +44 (0) 870 460 1045 Email: sales@QuasarElectronics.com

SOFTCOPY
www.softcopy.co.uk




As a PC data base or hard copy, SoftCopy can supply a complete index of Electronics World articles over the past ten years. Photo copies of articles from back issues are also available.

TELEVES
www.televes.com




Televes website was launched as an easier way to keep in contact with our World-wide Network of Subsidiaries and Clients. This site is constantly updated with useful information/news plus you can download info on our range: TV Aerials & accessories, Domestic and Distribution amplifiers, Systems Equipment for DTT and Analogue TV, Meters and much more. Tel: 44(0) 1633 875821 email hbotas@televes.com

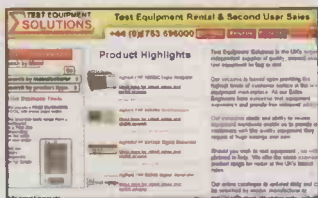TEST EQUIPMENT SOLUTIONS
www.TestEquipmentHQ.com



Test Equipment for rental or second user sale at the industry's lowest prices. All types of equipment from all leading manufacturers including general purpose, communications and industrial test. Items fully refurbished with 1 year warranty. Rental rebate given on purchases.

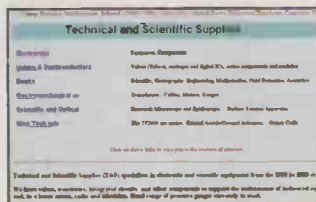TECHNICAL AND SCIENTIFIC SUPPLIES
www.technicalscientific.com



Suppliers of pre-1985 equipment and components.


- Test/Measurement equipment
- Valves and semiconductors
- Transducers and pressure gauges
- Scientific books and catalogues
- Manuals and data sheets

TELONIC
www.telonic.co.uk



Telonic specialists in laboratory AC & DC Power Supplies, Electronic AC & DC Loads, Electrical Safety Testing and complete test systems. Plus RF Filters, Attenuators, Diesel Engine Smoke Measurement, Quartz Crystal Microbalances. Tel +44 (0) 118 9786911

TELNET
www.telnet.uk.com

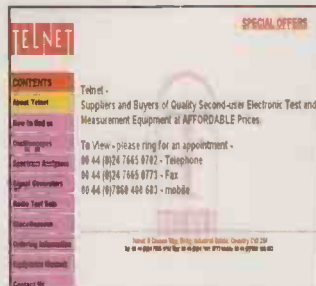

Top quality second-user Test and Measurement Equipment eMail sales@telnet.uk.com

Total Robots
www.totalrobots.co.uk




Robot Kits and Control Technology products, including OOPic the first Object-Oriented Programmable Integrated Circuit. Secure on-line ordering and fast delivery.

ULTRA-CREA OY
www.ultra-crea.fi

Our business idea is to provide our customers complete service, i.e. design from the customer specification to the delivery of finished and tested products. Our offerings are as follows:

- RF transmission line filters from 100MHz to 3GHz
- Special antennas to frequencies as above
- Transmitter and Receiver modules
- RF-subunits such as amplifiers, oscillators, directional couplers etc.

WILMSLOW AUDIO
www.wilmslow-audio.co.uk

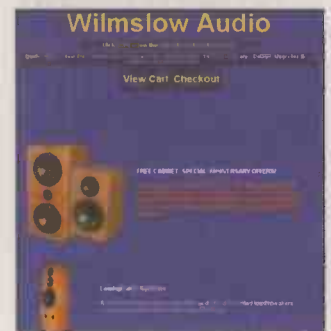

"Uk's largest supplier of high quality loudspeaker kits and drive units. Comprehensive range of components and accessories, including damping products, connectors and grilles materials. Demonstration facilities available.

ELECTRONICS WORLD

On CD-ROM


Electronics World is enjoyed by some of the world's top circuit designers - but it's not just for professionals. Stimulating designers for almost a century. *Electronics World* covers analogue, RF and digital circuit technology and incorporates design information on everything from model train control to input/output via a 10baseT network.. and it's now available all on CD-ROM.

- 12 issues on each CD-ROM
- Full text and diagrams of all articles, circuit ideas, letters etc
- Easy to browse
- Fully searchable by keywords and index
- High-quality print in colour
- Full software listings included
- easy to use

CDROMS are available for 1999, 2000, 2001, 2002 and 2003. Each disk contains 12 back issues of *Electronics World* in a searchable, browsable and printable format PLUS the library of software files. The CDROMS run on PCs with Windows '9x, Me, 2000 and XP. requires IE4 or above and Adobe Acrobat Reader (supplied on the CD).

The CDROMs are only £30 each including VAT and UK post, add £1 extra postage for Europe, £5 extra postage for rest of the world, exclusively available from SoftCopy Limited, address below.

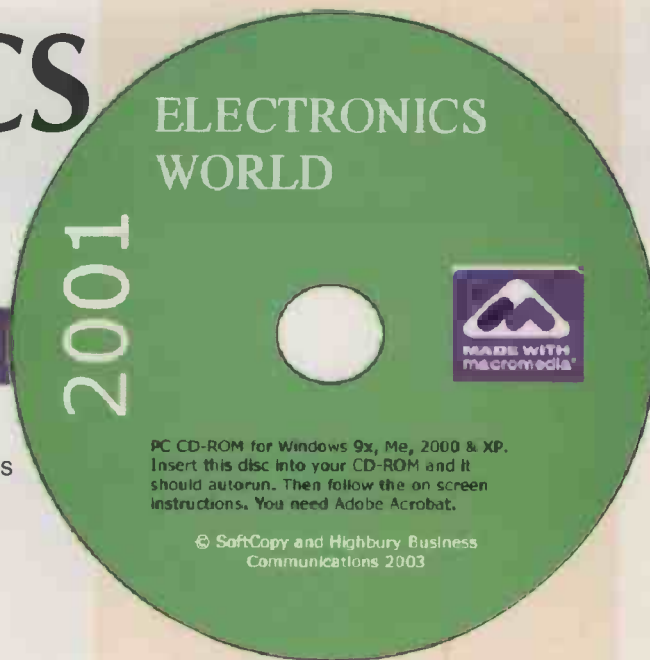Limited special offer for readers of *Electronics World* - all five CDs for the price of four.



1999, 2000, 2001, 2002, and 2003

Please send the following CD-ROMS


_____ qty 1999 NAME _____
_____ qty 2000 Address _____
_____ qty 2001 _____
_____ qty 2002 _____
_____ qty 2003 Card Number _____ Expiry _____

Order now at:

www.ewmag.co.uk

SoftCopy Limited, 1 Vineries Close, Cheltenham GL53 0NU, UK

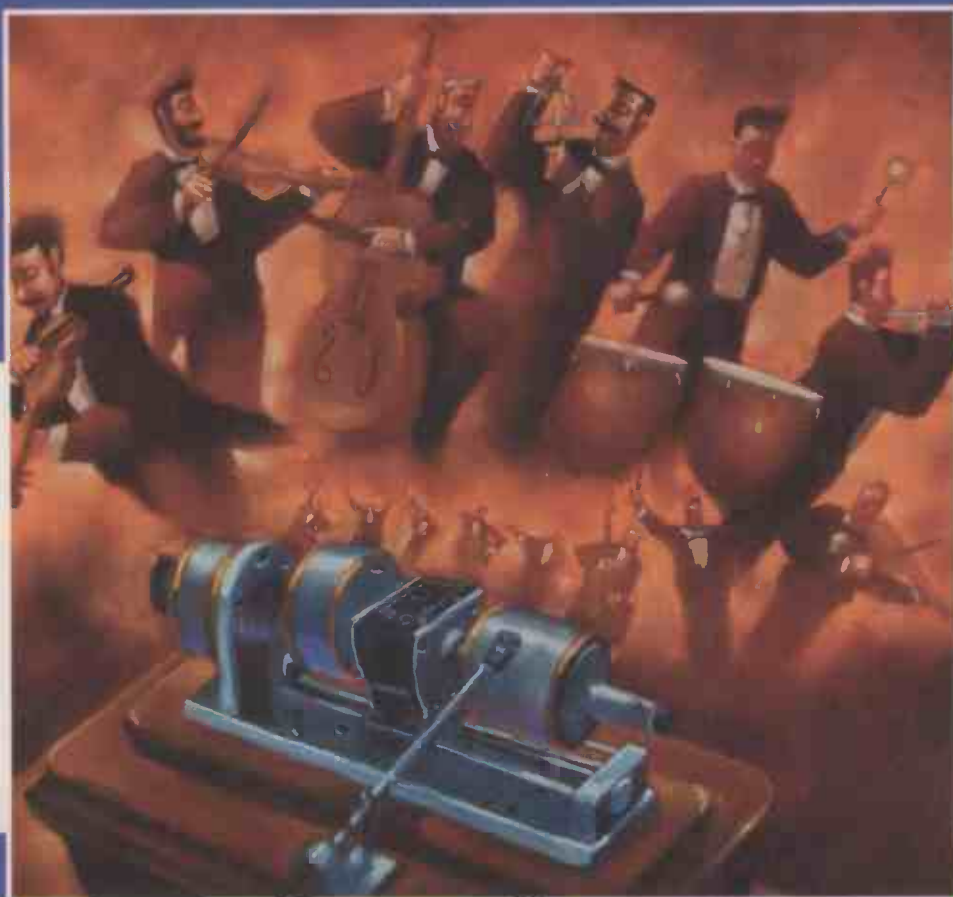62 Tel: +44 (0) 1242 241455 Fax: +44 (0) 1242 241468 sales@softcopy.co.uk



£11.99

**Available from
Electronics World**

All tracks on this CD were recorded on DAT from cylinders produced in the early 1900s. Considering the age of the cylinders, and the recording techniques available at the time, these tracks are of remarkable quality, having been carefully replayed using modern electronic technology by historian Joe Pengelly.

21 tracks – 72 minutes of recordings made between 1900 and 1929. These electronically derived reproductions are no worse than – and in many cases better than – reproductions of early 78rev/min recordings – some are stunning...

Use this coupon to order your copy of Pandora's drums

Please send me CD(s) at £11.99 each including VAT

Cheque

Credit card details tick as appropriate

Name

Address

Phone number

Total amount £.....

Make cheques payable to TELEVISION
Or, please debit my credit card.

Card type (Master/Visa)

Card No

Expiry date

Please mail this coupon to *Electronics World*, together with payment.
Address orders and all correspondence relating to this order to Pandora's drums, *Electronics World*, Highbury Business Communications, Nexus House, Azalea Drive, BR8 8HU

Pandora's drums

Unique and atmospheric music recorded in the early 1900s – the days *before* 78s.

Track

- 1 Washington Post March, Band, 1909
- 2 Good Old Summertime, The American Quartet 1904
- 3 Marriage Bells, Bells & xylophone duet, Burckhardt & Daab with orchestra, 1913
- 4 The Volunteer Organist, Peter Dawson, 1913
- 5 Dialogue For Three, Flute, Oboe and Clarinet, 1913
- 6 The Toymaker's Dream, Foxtrot, vocal, B.A. Rolfe and his orchestra, 1929
- 7 As I Sat Upon My Dear Old Mother's Knee, Will Oakland, 1913
- 8 Light As A Feather, Bells solo, Charles Daab with orchestra, 1912
- 9 On Her Pic-Pic-Piccolo, Billy Williams, 1913
- 10 Polka Des English's, Artist unknown, 1900
- 11 Somebody's Coming To My House, Walter Van Brunt, 1913
- 12 Bonny Scotland Medley, Xylophone solo, Charles Daab with orchestra, 1914
- 13 Doin' the Raccoon, Billy Murray, 1929
- 14 Luce Mia! Francesco Daddi, 1913
- 15 The Olivo Minstrel, 2nd part, 1913
- 16 Peg O' My Heart, Walter Van Brunt, 1913
- 17 Auf Dem Mississippi, Johann Strauss orchestra, 1913
- 18 I'm Looking For A Sweetheart And I Think You'll Do, Ada Jones & Billy Murray, 1913
- 19 Intermezzo, Violin solo, Stroud Haxton, 1910
- 20 A Juanita, Abrego and Picazo, 1913
- 21 All Alone, Ada Jones, 1911

Service Link

ARTICLES WANTED

BEST CASH PRICES PAID

FOR VALVES KT88,
PX4 AND MOST
AUDIO/OTHER
TYPES.

Tel: 01403 784961

Billington Export Ltd.
Sussex RH14 9EZ
Fax: 01403 783519
Email: sales@bel-tubes.co.uk
Visitors by appointment

TOP PRICES PAID

For all your valves,
tubes, semi conductors
and ICs.

Langrex Supplies Limited
1 Mayo Road, Croydon, Surrey CR0 2QP
TEL: 020 8684 1166 FAX: 020 8684 3056

WANTED

VALVES AND VALVE BASES

Valve associated components including
high voltage capacitors, electrolytics etc.
Must be over 250v working, OLD 1 watt
and 1/2 watt resistors (Carbon).
Obsolete semiconductors.

CBS
157 Dickson Road, Blackpool FY1 2EU
Tel: 01253 751858. Fax: 01253 302979

For a **FREE** consultation on how best
to market your products/services to
a professional audience
ring **SCOTT** on 01322 611292

FOR SALE

PRINTED CIRCUIT BOARDS

DESIGNED & MANUFACTURED

- Prototype or production quantities
- Fast turnround available
- PCBs designed from circuit diagrams
- Almost all computer files accepted
- PCB assembly - mechanical assembly
- Full product design-manufacture-test-repair

 Unit 5, East Belfast Enterprise Park
308 Albertbridge Rd, Belfast BT5 4GX
TEL 028 9073 8897 FAX 028 9073 1802
info@agarcircuits.com

SERVICES

POWER SUPPLY DESIGN

Switched Mode PSU
Power Factor Correction
designed to your specification

Tel/Fax: 01243 842520
e-mail: eugen_kus@cix.co.uk

Lomond Electronic Services

WESTDALE ELECTRONICS

We would welcome the opportunity
of quoting for your requirements.

*If you have a problem with your
semiconductors or relays,
give us a call and we will locate
them for you.*

We also have access to inventory
Stateside ie

Current, Obsolete, Mil, Spec

Call: Bryan on -
Tel/Fax:
0115 9402127



SERVICES

From **Concept** To **Production**

**48 HOUR
SERVICE**

Electronic design and manufacturing services for the new millennium:

- Embedded monitoring & control
- PSTN telephones and test equipment
- Datacom interfacing, line driving etc.
- Switch Mode & linear PSU and battery management
- Gas detection systems
- Printed Circuit Board design
- Technical documentation, schematic layout & language translation
- Wireless telemetry systems
- Audio & Video processing
- GSM telemetry via SMS or data (TCP/IP)
- DVD player control systems
- GPS positioning systems
- Specialist cable looms
- Small, medium & large scale manufacturing

Email: sales@designersystems.co.uk
Tel/Fax: +44 (0) 1872 223306




for more information see our web site @
<http://www.designersystems.co.uk>

PCBs Conv/PTH/Multi-Layer/Flexible • UK & Far East production
• CAD Layout • Electronic Design • Assembly (prototype & production)
• SMD m/c assy @ 18,500 cps/hr

Deliveries from

24 Hrs

Prototype
PTH PCBs
from just
£40.00

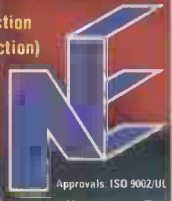

Tel: 01635 40347

Newbury Electronics Ltd
Faraday Road Newbury Berks RG14 2AD
Fax: 01635 36143
e-mail: circuits@newbury.tcom.co.uk
<http://www.newburyelectronics.co.uk>

Visit

www.pcbtrain.com

The low cost source for prototype PCBs
from 1 to 6 layers

WANTED

WANTED Surplus or Obsolete Electronic Components

Turn your excess stock into instant cash!

SEND OR FAX YOUR LIST IN STRICTEST CONFIDENCE

Will collect anywhere in the UK



Mushroom
COMPONENTS


28 College Street, Kempston, Bedfordshire, MK42 8LU

Tel: 01234 363611 Fax: 01234 326611

E-mail: sales@mushroom.co.uk

Internet: www.mushroom.co.uk

Service Link

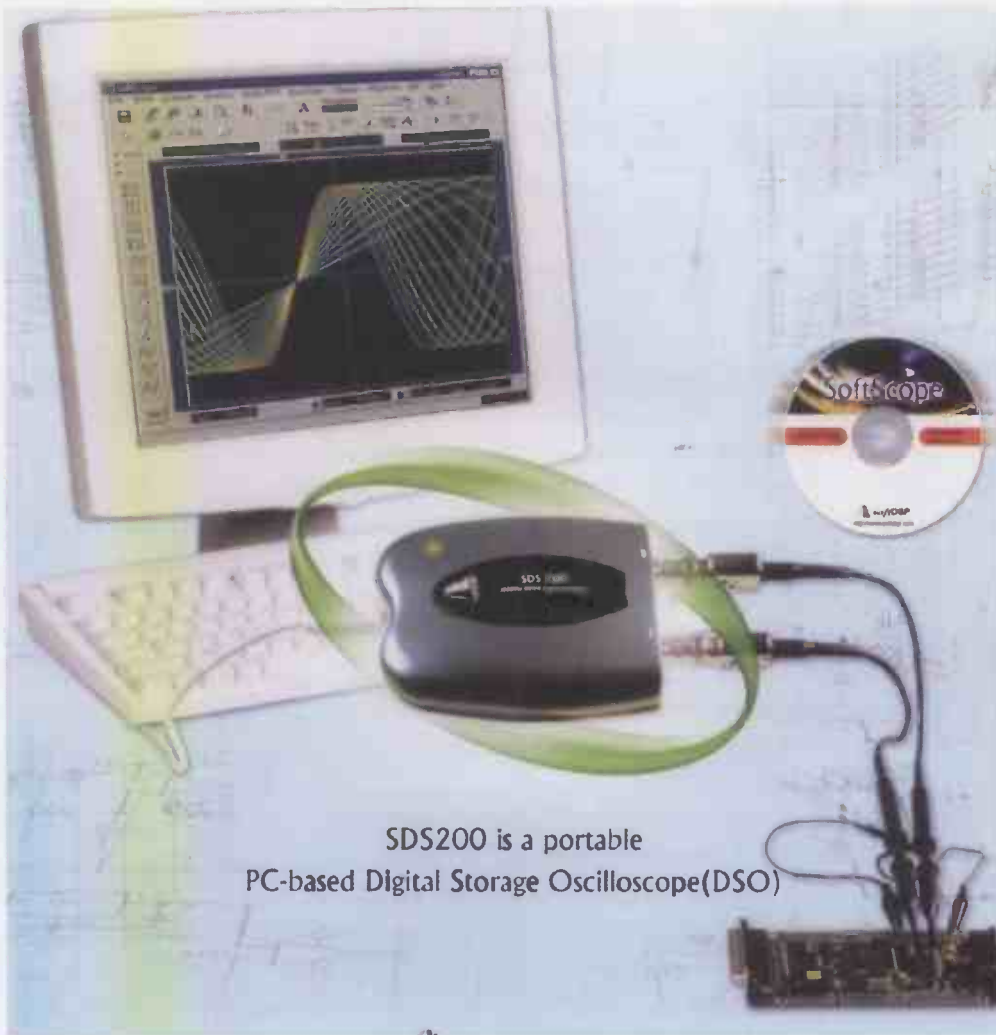

SDS200 is a portable
PC-based Digital Storage Oscilloscope(DSO)

SDS 200, **200MHz** dual-channel digital storage oscilloscope. Small enough to fit in your palm! Powerful enough to perform like a bench scope of a well known brand!

Some of its characteristics

200MHz, 5GS/s equivalent. Vertical resolution: 9 bits/channel, Gain range: from 10mV to 1000v/dv (probe dependent). Timebase: 2ns/div-10s/div. Math measurements (Vp-p, Vmax, Vmin, Vrms, Vamp, Vhigh, Vlow, pos./neg. overshoot, cycle mean, etc). FFT (Rectangular, Hanning, Hamming, Blackman), Advanced trigger (enabling the SDS200 to capture complex signals). Saves files as text, jpg/bmp, Excel or Word. Prints in color or B&W. **USB connection**, not requiring additional power supply.

Simply the best! **And only £565 + VAT**. Order from our online store and save (www.pc-instrumentmart.biz). Call us at +44 1934 514595, attn: Mr. Bourner, for more details.

PC-INSTRUMENTMART (UK) LTD

Telnet

Special Sale of Quality Second-User Test Equipment



Amitsu – MP1552A/B various options ATM/PDH/SDH Analyser	From £1400
Amitsu – MP1560A opt 01/02/03 STM Analyser	£2700
Amitsu – MP1656A opt 02 Portable STM-16 Analyser 1310/1550mm	£4000
Amitsu – MP1570A- SDH/PDH/ATM Tester various	From £2700
Amitsu – MI9001A Optical Power Meter (Various sensors available).....	£650
Amitsu – MN939A/MN939C/MN9605A/MN9610A Optic. Attens.	From £750
Amitsu – ME520A Digital Transmission Test Set.....	£500
Amitsu – ME520B Digital Transmission Test Set.....	£2000
Amitsu – MP1520B Digital Transmission Analyser.....	£1500
Amitsu – ME3520A SDH/SONET Analyser (Tx and Rx)	£6000
Amitsu – ME3620A SDH/SONET Analyser (Tx and Rx)	£7500
Amitsu – MD6430A Network Data Analyser	£9995
Amitsu – Emiscan EMCT Test Solution (Consists: MS2601B/ANT1/4401/MA8611)	£3500
Agilent – J2300E Advisor WAN Protocol Analyser	£5250
Agilent – 8753D (Opt 006) Network Analyser – Colour – 6GHz	£12000
Agilent – 54810A Infinium 500MHz – 2 channel	£3000
Agilent – 54610B 500MHz – 2 channel	£1250
Agilent – 3325B Synthesised Function Gen. (21 MHz).....	£2000
Agilent – 3326A (opt 001) Synth. Function Gen. (13MHz).....	£1500
Agilent – 35665A Dual Channel Dynamic Signal Analyser.....	£4000
Agilent – 71500A – 40GHz Microwave Transition Analyser (Inc 70004A/70820A)	£8000
Agilent – 37717C – Various options available – phone for details.....	from £1000
Agilent – 37718B – Comms. Perf. An. opts 1, 12, 106, 601, 602.....	£9750
Agilent – 8153A Lightwave Multimeter (less I/P Module) Modules available separately.....	£650
Agilent – 8163A Lightweight Multimeter	£500
Agilent – 8156A Dig. Optical Attenuator – various options.....	from £750
Agilent – 8164A Lightwave Measurement Mainframe.....	£2250
Agilent – 86120C Optical Wavelength Meter	from £1500
Agilent – 83480A Sampling Oscilloscope Mainframe (plus ins avail).....	£2950
Burster – 1424 IEEE High Precision Decade Resistor	£1250
IFR 2031 2.7 GHz Signal Generator (opt 05)	£3500
IFR 2850 Digital Transmission Analyser.....	£900
IFR 2853 Digital Transmission Analyser (opts 14, 15, 25).....	£1475
Tektronix CSA 8000 Comms. Sig. An. (ring for plug-ins available).....	from £11000
Tektronix CSA 803C Communications Signal Analyser Mainframe	£3500
Tektronix MTS 100 MPEG Test System	£3000

Lots more equipment available.

Please call for availability and prices.

Tel: 024 7665 0702

Fax: 024 7665 0773

Email: sales@telnet.uk.com

Carriage and VAT added to all goods.
See Inside Front Cover for address.