


IMPROVED BAND-SPREAD SYSTEM

The
**Wireless
World**

MONTHLY
ONE SHILLING

*COVERING
EVERY WIRELESS INTEREST*

FEBRUARY, 1940


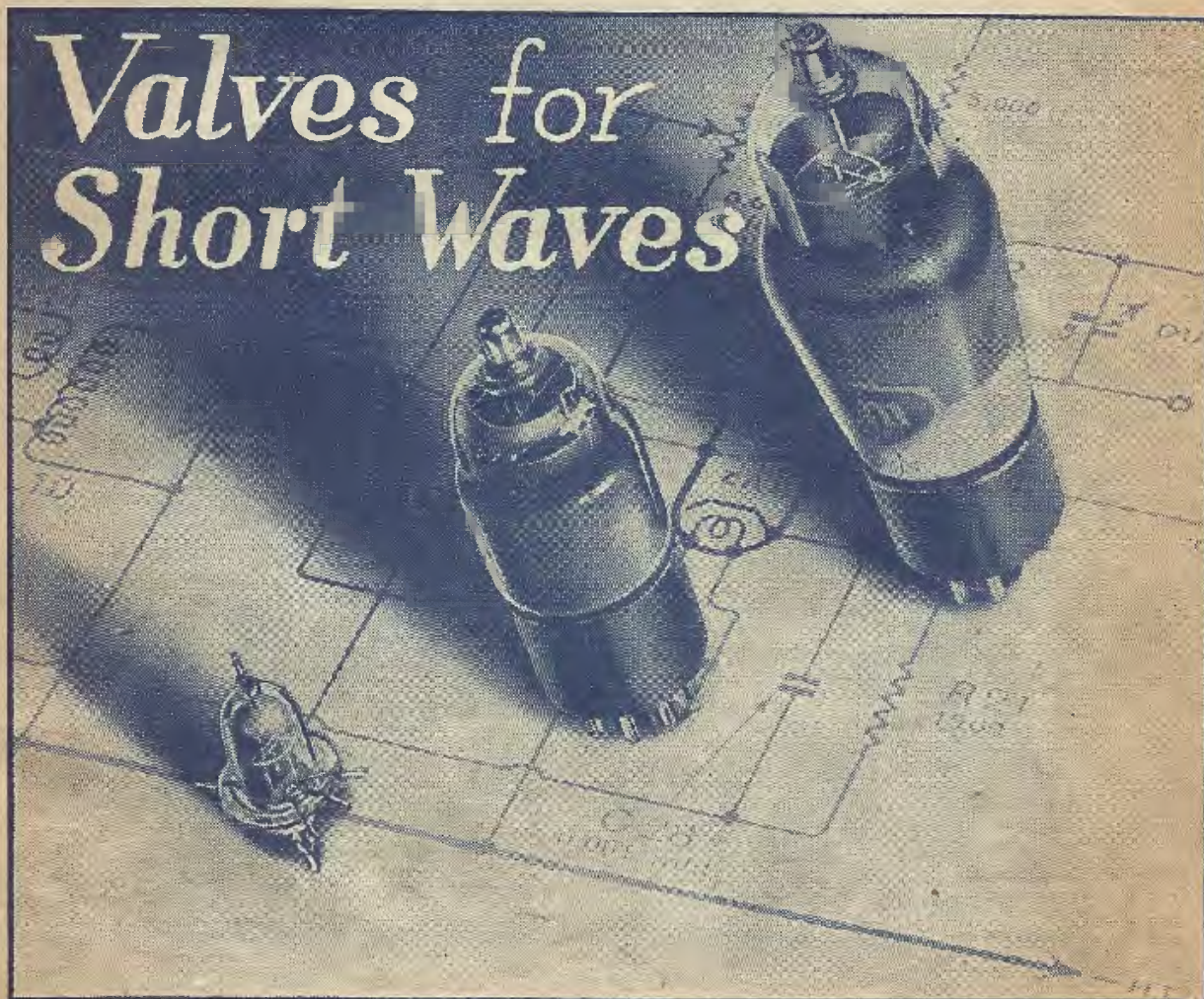


For Battery Sets
THREE NEW
OSRAM
2-VOLT
ECONOMY VALVES

<p>OSRAM X24 An improved Triode Hexode Frequency Changer especially suitable for short wave reception.</p> <p>H.T. ECONOMY—A feature of this type is that it will continue functioning satisfactorily at a lower H.T. voltage than other types, giving a longer life for the H.T. battery.</p> <p>L.T. ECONOMY—Type X24 replaces type X23 with a reduction of 33% in filament current—only 0.2 amp.</p>	<p>CHARACTERISTICS, X24</p> <p>Filament Current ... 0.2 amp.</p> <p>Total Cathode Current 4.5 mA (1.7 mA with 100 volt H.T.)</p> <p>Conversion Conductance 350 micromhos</p> <p>Price 10/6 each.</p>
<p>OSRAM HD24 A Double Diode Triode containing all the features of earlier valves of this type, but with greatly increased L.T. economy.</p> <p>Type HD24 replaces the HD23 with a reduction of 25% in filament current—only 0.10 amp.</p>	<p>CHARACTERISTICS, HD24</p> <p>Filament Current ... 0.1 amp.</p> <p>Amplification Factor } measured at 40 Impedance } at 28,600 ohms Mutual Conductance } 1.4 mA/volt</p> <p>Price 7/6 each.</p>
<p>OSRAM KT24 A High Slope Output Tetrode. This valve is a high sensitivity power tetrode, particularly suitable for small battery sets in which economy of consumption is of greater importance than high power output—type KT24 consumes only 0.2 amp.—a saving of 33% in filament current.</p>	<p>CHARACTERISTICS, KT24</p> <p>Filament Current ... 0.2 amp.</p> <p>Mutual Conductance ... 3.2 mA/volt</p> <p>Price 9/- each.</p>

★ The above valves, together with the OSRAM W21 economy Variable-mu H.F. Pentode, enable a 4-valve battery receiver to be designed with a total filament current of only 0.62 amp. and with no decrease in overall sensitivity over a similar receiver with other valves normally taking 25% to 30% more current from the L.T. accumulator.

**WRITE FOR
TECHNICAL
LEAFLETS**

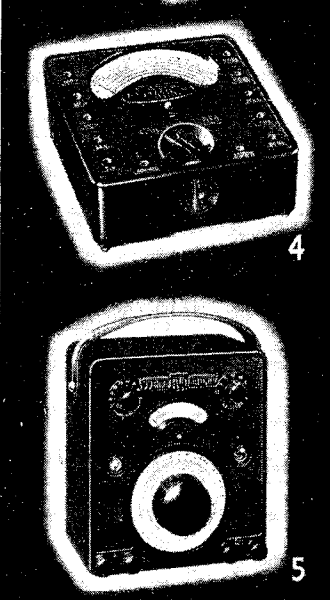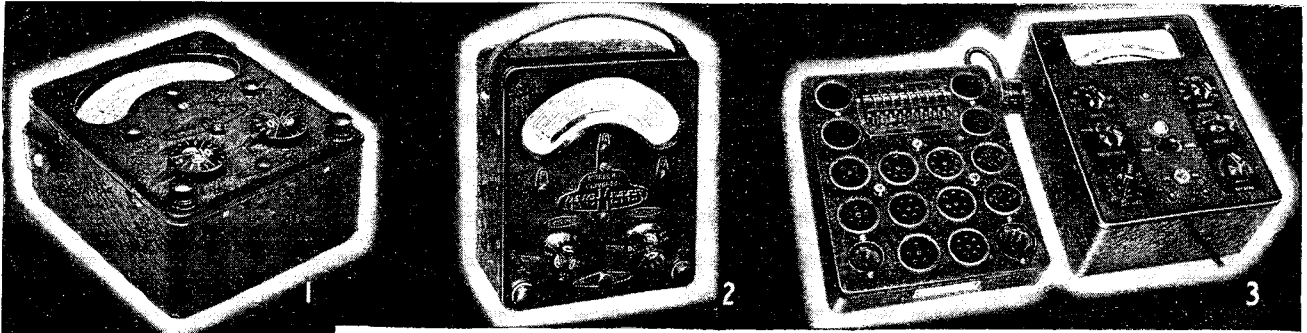

AVO
Regd. Trade Mark


**ELECTRICAL MEASURING
INSTRUMENTS**

BRITISH MADE

In every sphere of electrical test work . . . in the laboratory, the workshop, the service engineer's bench or in the serious experimenter's den . . . the word "AVO" is synonymous with instruments of precision.

The "AVO" range embraces instruments for every essential electrical test. By reason of their reliability and maintained accuracy, even under the most searching of workshop conditions, they are frequently used as a standard by which other Instruments are judged.

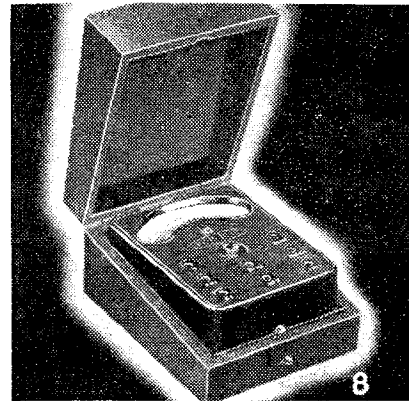Write for fully descriptive literature dealing with any instrument in which you are interested, and for current prices.



1. 46-range Model 7 Universal AvoMeter.
2. 40-range Model 40 Universal AvoMeter.
3. "Avo" Valve Tester.
4. Universal AvoMinor.
5. "Avo" Test Bridge.
6. "Avo" Capacity Meter.
7. All-Wave "Avo" Oscillator.
8. D.C. AvoMinor.


Other "Avo" Instruments :

- 22-range D.C. AvoMeter.
- High Resistance AvoMinor.
- "Avo" Low Resistance Ohmmeter.
- The AvoDapter.
- 9-pin AvoCoupler.

PRECISION METERS
that Master every Testing Problem

Sole Proprietors and Manufacturers:

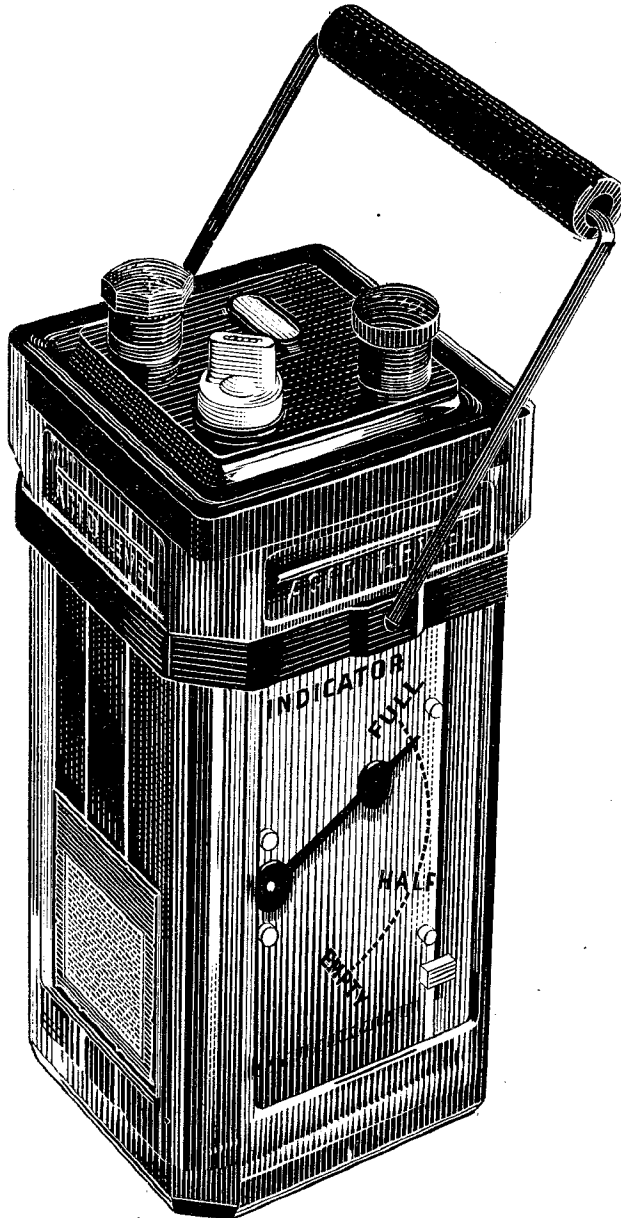THE AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO., LTD., Winder House, Douglas St., London, S.W.1. Telephone: Victoria 3404/7.



Exide

BATTERIES

'Still keep going when the rest have stopped'

The Chloride Electrical Storage Co. Ltd., Exide Works, Clifton Junction, near Manchester. Also at London, Manchester, Birmingham, Bristol, Glasgow, and Belfast.

Why ROGERS- Majestic 'DUPLITONE'

ALL-WAVE RADIO

ensures **Startling Realism**

The new high standard of reproduction set up by the R.M. Duplitone Radio described by critics as "truly startling," is due to an exclusive R.M. principle—the

★BRADBURY CONTRAPHASE

A new method of compensated inverse feed-back, which provides a measure of accentuation of the extreme upper and lower frequencies. The result is *startling realism*.

Immediate delivery of all models

DUPLITONE RADIO provides

★TWO SETS IN ONE

"Duplitone"—a new circuit which, at the turn of a switch, converts a Superhet Receiver to a straight (T.R.F.) Receiver, thereby preserving the normally lost harmonics and overtones.

Illustrated booklet on request

Ask for a demonstration



TABLE MODEL	CONSOLE	RADIOGRAM
14/8T (8 valves)	14/8C (8 valves)	14/8R (8 valves)
13½ Gns.	22 Gns.	28 Gns.

Other Models up to 100 Gns.

R.M. ELECTRIC LTD., Majestic Works, Oaklands Road, London, N.W.2. Telephone: Gladstone 2101

RADIOMART

GENI (B'HAM) LTD.

THE SHORT-WAVE SPECIALISTS

WE CARRY LARGE STOCKS OF ALL TYPES OF SHORT - WAVE AND COMMUNICATION EQUIPMENT, INCLUDING AMERICAN VALVES

RADIOMART SPECIAL OFFERS! Fully shrouded Transformers by America's largest manufacturer. While they last, all 230 v. 50 cy.

T.850 Y—350/350 v. 150 m/A. 4 v. 6 a., 4 v. 2.5 a.	15/-
T.2870S—375/375 v. 150 m/A. 6.3 v. 6 a., 2.5 v. 5 a., 5 v. 3 a.	15/-
T.19610—350/350 v. 150 m/A. 2.5 v. 6 a., 2.5 v. 2 a., 5 v. 3 a.	12/6
T.7286—375/375 v. 120 m/A. 6.3 v. 4 a., 5 v. 3 a.	10/6
T.7000—320/320 v. 80 m/A. 6.3 v. 4 a., 5 v. 3 a.	7/6
T.6925—320/320 v. 80 m/A. 2.5 v. 6 a., 5 v. 3 a.	7/6
T.464919—10 v. 4 a., primary tapped 110-250 v.	5/6
W.372Y—440/440 v. 200 m/A., 6.3 v. 3 a. CT., 5 v. 3 a.	25/-
W.308Y—550/550 v. 200 m/A. 6.3 v. 3 a. CT., 5 v. 3 a.	25/-
T.1113AB—230 to 110 v. 500 watt auto transformer	29/6
T.2311A—230 v. to 110 v. 100 watt auto transformer	12/6
The following chokes are interleaved and impregnated.	
T7007—250 m/A., 135 ohms, 20-8 Hy., cadmium shrouded	12/6
T7007A—150 m/A., 250 ohms, 30-12 Hy., cadmium shrouded	12/6
100 m/A., 20 Hy., 500 ohms, unshrouded	4/11
60 m/A., 15 Hy., 250 ohms.	1/11

FERRANTI Meters at less than half price. 3in. Moving Coil, 10, 25, 50, 100 m/A., 10/6 each. Latest 2in. Flush Moving Coil, 10, 20, 50, 150, 250, 500 m/A., 12/6. 1 m/A. 17/6. Voltmeters 1,000 ohms per volt, 10, 20, 50, 150, 250, 500 volts, 17/6. All as new.

HEAVY DUTY Mains Transformer, worth 45/-, 350/350, 150 m/A., 4 v. 2.5 a. CT. 4 v. 6 a., CT, 12/6; 300/300 v., 80 m/A., 4 v. 3 a., CT, 4 v. 2 a., CT, 6/6. Moving Coil Speaker Transformers power, pentode or push pull, 1/11. 8" Energised Moving Coil Speakers 1,200 ohms with trans. 6/11.

GANG CONDENSERS with Airplane Dial, 8 and 30-1. Cost 35/-. Few only. 4/11. Utility Microdials. List 7/6. Our Price, 3/9. Ideal for Short Waves.

PUSHBACK Wire, 6 vds., 6d., heavy, 9d. Resin-cored Solder, 6ft., 6d.; Screened Flex, single, 6d. yd.; twin, 9d. yd. Assorted Solder Tags, 6d. packet. Humdimmers, 6d. each. Centralab pots, all sizes, 1/9; switched, 2/3; tubular fuses, 2d. Milliammeters, 25 m/A. upwards, 6/9.

VALVES: Reliable replacement: for all types, British and American, showing saving of over 50 per cent.

OUR NEW 66-PAGE MANUAL, packed full of valuable information, Metre-Kilocycle Charts, Shortwave Stations, times of News Bulletins, Shortwave Receivers, constructional articles, etc., 7/6 post free.

THE NEW RAYMART CATALOGUE shows dozens of New Short-Wave Components and is yours for 1/6d. post free.

TRADE ENQUIRIES solicited for all types of communication equipment receivers, etc.

RADIOMART 44, HOLLOWAY HEAD, BIRMINGHAM
GENI (Birmingham) Ltd.

CUT DOWN ASSEMBLY TIME AND COSTS



by using

Simmonds Speed Nuts

(PATENTS APPLIED FOR)

THE MODERN FASTENING SYSTEM THAT IS
REVOLUTIONISING ASSEMBLY IN EVERY INDUSTRY

Simmonds Speed Nuts replace ordinary nuts and lock washers, reduce the number of parts handled by HALF and effect considerable savings in Assembly time and costs.


They absorb bolt stretch and prevent sinking of the bolt head into wood or soft metal surfaces. For bakelite, glass and porcelain, Simmonds Speed Nuts are the perfect fastening.

In knob-to-shaft assemblies they avoid the necessity for either the grub screw or internal spring method of fastening.

There is practically no assembly problem that cannot be solved by the Speed Nut System.

A wide range of standard Speed Nuts is available from stock for all sizes of machine screws, sheet metal screws, rivets and plastic studs. Special types designed to meet individual requirements.

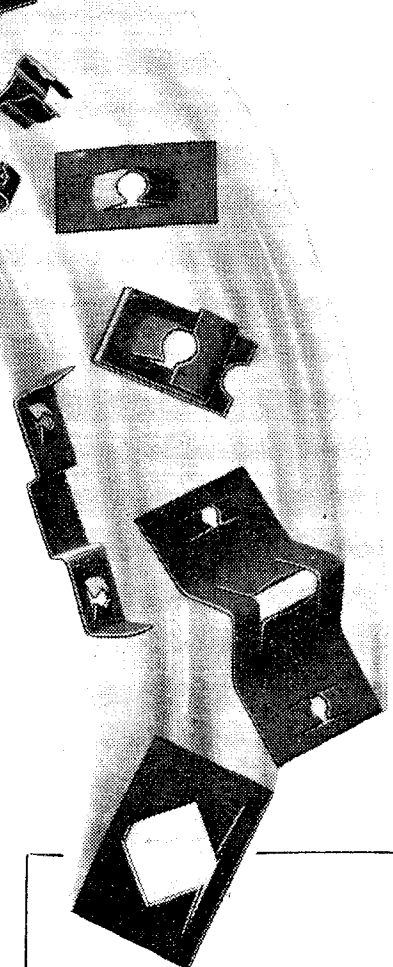MOVE WITH THE TIMES—INVESTIGATE THE SPEED NUT SYSTEM



★ Our Development Department will be pleased to collaborate and put forward the most effective designs to suit your particular needs.



SIMMONDS AEROACCESSORIES LTD
GREAT WEST ROAD, LONDON.



Lensleys

AN APOLOGY which we are proud to make!

So great has been the response to these advertisements for

FEEDER UNITS

that we are afraid customers have experienced delays in delivery.

This is mainly because, rather than spoil the job by using cheap labour, we have adhered to our policy of employing only skilled craftsmen.

In these times, the demands of national service have made, and are still making, heavy demands on such men, necessarily of military age, and our staff has been depleted over and over again.

We are determined to carry on in spite of the war, and we ask our customers to

HELP BRITISH INDUSTRY

in this small way, by supporting us despite the inevitable delays in production. Delivery on most standard models is now about three weeks, and we expect to improve on this very shortly.

ACF5 Type Feeder Unit. A 5-band unit for A.C. operation with 4-volt valves. R.F. stage employing low-noise variable-mu pentode operates on all bands; triode-heptode frequency changer, followed by a single stage of iron-cored I.F. of 465 Kcs, with similar pentode; double-diode triode as detector/AVC/first audio stage. Full vision horizontal scale, calibrated in frequencies and wavelengths; dual-ratio slow motion drive. Magic-eye tuning indicator. Provision for gram. input, if desired. Coverage: 124-35 m., 30-80 m., 73-200 m., 200-550 m., 750-2,000 m. H.T. consumption (max.), 52mA. at 250 volts; L.T. 4½ amps. Chassis size: 11½" x 9" x 3". Price, complete with valves, £9.9.0
Details of other models on application.

JOHN McCLURE LTD.

ERSKINE ROAD, LONDON, N.W.3 PR1mrose
5 435-6

HALLICRAFTERS COMMUNICATIONS RECEIVER 'SX23'

still at its pre-war price!

Embodies all the features of the ideal receiver. New in conception, new in design, and offering a really exceptional performance in sensitivity, selectivity and range. An instrument of extremely advanced design which has solved the problem of FREQUENCY STABILITY by the use of components with compensating temperature coefficients.



Eleven valves; specially tested Bliley 455 kc. Crystal; improved wide range variable selectivity circuit; a brand-new method of stabilising tuned circuits to reduce frequency drift; remarkably high signal-to-noise ratio; 8 Bands—4 covering 10 to 540 metres, 4 for Band Spreading 10-20-40-80 Amateur Bands. It is the only Hallcrafters receiver still available at pre-war price. £33.10s. (Speaker £4). Price is subject to increase on clearance of present stock.

Ask for the special SX23 booklet.

WEBB'S LONDON

14 SOHO ST., Oxford St., W.1

(Open 9 a.m. to 6.0 p.m.)

Telephone: Gerrard 2089.

Emergency Branch: 58, Victoria St., St. Albans, Herts. Phone: 4924

M-R SUPPLIES

offer some more first-class bargains in "much-in-demand" goods. Notwithstanding difficulties of supply we are maintaining our reputation for the right goods at the right price.

Here is the greatest opportunity yet presented in high-fidelity electrical reproducing units. The great advantages of the Piezo-Crystal Pickup, both in output and frequency response, are now universally known, and they have always been very well worth the little extra that they normally cost. However, following a keen cash deal we are able to present this unique opportunity, enabling you to employ a De Luxe Pickup at small expense.

The UNIVERSAL ROTHEMEL-BRUSH PIEZO-CRYSTAL PICKUP HEAD, designed to be fitted to any ordinary tone-arm but easily fixed to any sort of tracking arm, offered only by us at nearly half price, namely 18/6 each nett cash, post paid. These finely constructed heads weigh only 3 ozs. and employ a full-size, waterproofed, rubber mounted crystal element delivering an output of 1.5 volts. Very limited stocks of this model—secure yours now.

Also NEW. The latest Junior model (which has received such fine reports in the technical press). Complete with easy-fix tracking arm and rest, 18/6. Also the DE LUXE model, with ball-bearing tracking arm and rest (World's finest pickup), 45/-. Also HEADS to replace old magnetic types on Collaro or Garrard arms (please state which), 27/6. SYNCHRONOUS ELECTRIC CLOCK MOVEMENTS. Precision made with machine-cut gears. Only 2½in. dia. but will drive up to 1½-inch hands. Fitted spindles for hours, minutes and seconds hands. One-hole fixing. 200/250 v. 50 cycles. Complete with moulded back cover and flex, 18/6.

MINIATURE P.M. M/COIL UNITS. Only 3in. dia. 15 ohms speech coil. Perfect M/coil mikes as they are. Ideal also as extension speakers or for intercommunication, 11/6. LORGNETTE SINGLE PHONES for deaf-aid or individual listening. On 9in. plated handle with ebonite hand-piece, 1,000 ohms res. 4/6. Suitable local volume controls for these, 2/11.

SLIDING RHEOSTATS. Fully enclosed "Safety First" pattern, 7in. long with laminated brush contacts and slate former. Very smooth action, for control of small motors, lights, etc. (Usually 21½-) 400 ohms at 3 amp. Or 600 ohms at 1 amp. Either, 9/6.

AMPLIFIERS: Really good ones at the keenest prices obtainable. GRAMPIAN Type D2. AC/DC 200/250 v. Output 10 watts. Complete portable equipment with speaker, Senior M/Coil Mike, Floor Stand, etc., ready for use, 18 gus. model for £11-15-0 nett cash, carriage paid.

GRAMPIAN, UA12. AC/DC 200/250 v. Output 12 watts. Complete Microphone and Gramophone equipment with built-in electric turntable. Whole outfit in portable form 14in. by 14in. by 11in. With senior 6-gus. M/Coil Mike, Floor Stand, Speaker, etc., ready for use, £25-10-0 model for £15-17-6 nett cash, carriage paid.

G.E.C. 1582. AC 200/250 v. Output 6½ watts. Fine high-fidelity amplifier in closed chassis form with Osram valves. For gram. mike or radio inputs, with switch-over. Multi-matching output for all speech impedances. (List £19-16-0.) Last six at £8-16-6 (plus 2/- part cost). Appropriate portable cabinets for above, polished oak, 15/-.

BATTERY CHARGERS: Now very difficult to obtain! We offer a few brand new Ediswan Tungar Chargers (200/250 v. AC operation), charging 6 or 12 volt accumulators at 3 amps. (or less), £5-17-6.

BRUSH PIEZO-CRYSTAL ELEMENTS, offered at one-half nett cost of importation. 2½in. dia. fitted stylus. For construction of high-grade Microphone, Cardiophone, Tweeter, Pickup, etc. Last few, 6/11 each.

ELECTRIC MOTORS (Fractional). AC 200/250 v. 1/20th H.P. for Cine, Fan, etc. 2,800 r.p.m. with double spindle, 13/6. Also ditto, 1,400 r.p.m., single spindle, 12/6. 1/4th H.P. Motors, DC 200/250 v. "Century," fully enclosed, new (List £6-10-0), a few at 35/-. Large stock of first-class Repulsion Induction AC Motors from 1/6th H.P., please enquire. Also Gramophone Motors, Record Chargers, P.E. Cells, etc.

M-R SUPPLIES

68, NEW OXFORD ST., LONDON, W.C.1. Phone: MUS. 2958

WHARFEDALE EXTENSION SPEAKERS


Prices from 23/-

List on application.

DE LUXE Model with "TRUQUAL" Vol. Control (as illustrated). BRONZE UNIT, Less transformer 66/-

With transformer 74/-

GOLDEN UNIT from... 88/-

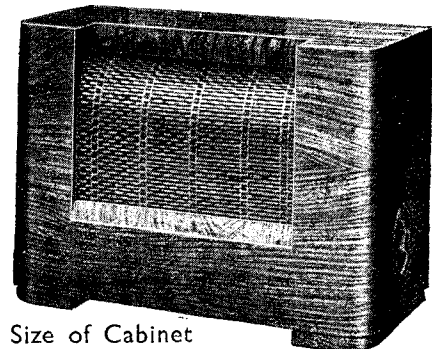

Size of Cabinet 16" x 12" x 8" Walnut. (Mahogany or Oak 2/6 extra.)

ALL WHARFEDALE EXTENSION SPEAKERS are available WITHOUT Transformer in the following types:—

- Type "32" for 1½ to 4 ohms.
- Type "64" for 4 to 6 ohms.
- Type "98" for 7 to 10 ohms.

WHARFEDALE WIRELESS WORKS
Hutchinson Lane, BRIGHOUSE, YORKS.
PHONE: BRIGHOUSE 50

PREMIER RADIO

SPECIAL OFFER

DUAL RANGE SCREENED COILS by well-known manufacturer. Aerial or H.F. transformer. All accurately matched. Suitable for Band Pass, Medium and Long Wave operation. Complete with full diagrams.

2/9 EACH

PREMIER 1940 HIGH FIDELITY AMPLIFIER KITS

Each Kit is complete with ready-drilled chassis, selected components, specially matched valves and full diagrams and instructions.

	Kit of Parts with Valves.	Completely Wired and Tested.
3-watt A.C. Amplifier	£2 6 6	£3 4 0
3-watt A.C./D.C.	£2 6 6	£3 4 0
6-watt A.C.	£6 2 6	£7 0 0
8-10-watt A.C./D.C.	£5 5 0	£6 2 6
15-watt A.C.	£6 14 0	£8 2 6

Black Crackle Steel Cabinet 15/- extra.

NEW PREMIER SELF-POWERED RF TUNING UNIT, incorporating a Var-Mu pentode amplifier followed by a power grid detector. Designed for high-fidelity reception. Wave range 200-560 and 800-2,000 metres. Complete with valves. **£5.5.0**

PREMIER SHORT-WAVE KITS for OVERSEAS NEWS

Incorporating the Premier 3-Band S.W. Coil, 11-86 Metres without coil changing. Each Kit is complete with all components, diagrams and 2-volt valves. 3-Band S.W. 1 Valve Kit, 14/9. 3-Band S.W. 2 valve Kit, 22/6.

DE LUXE S.W. KITS

Complete to the last detail, including all Valves and coils, wiring diagrams and lucid instructions for building and working. Each Kit is supplied with a steel Chassis and Panel and uses plug-in coils to tune from 13 to 170 metres.

1 Valve Short-Wave Receiver or Adaptor Kit	20/-
1 Valve Short-Wave Superhet Converter Kit	23/-
1 Valve Short-Wave A.C. Superhet Converter Kit	26/3
2 Valve Short-Wave Receiver Kit	29/-
3 Valve Short-Wave Screen Grid and Pentode Kit	68/-

ALL-DRY BATTERY PORTABLES

Latest type 1 1/4v. valves and dry batteries. Completely self-contained with M.C. Speaker in handsome leatherette covered case 13 x 9 x 8 1/2. Covers 200-550 metres. Complete with Valves and Batteries **£5.10.0**

U.S.A. 4-VALVE MIDGET RECEIVERS

A.C. or D.C. operation, Medium and Long Waves, M.C. Speaker. Completely self-contained in handsome Walnut cabinet 8" x 6" x 5". Complete **£4.10.0**

U.S.A. MAINS TRANSFORMERS

at less than pre-war prices.

Input 110 v. + 220 v. A.C.
Output 325-325 v. 120 mA. } **7/6 EACH**
5 v. 2 amps. C.T. 6.3 v. 2-3 amps.

Input 230 v. A.C.
Output 325-325 v. 75 mA. } **6/6 EACH**
5 v. 2 amps. C.T. 6.3 v. 2-3 amps.

Input 100-250 v. A.C.
Output 300-300 v. 80 mA. } **6/11 EACH**
4 v. 5 amps. C.T. 4 v. 1 amp.

PREMIER BATTERY CHARGERS for A.C. Mains.

Westinghouse Rectification complete and ready for use.

To Charge :

2 volts at 1/2 amp.	11/9
6 volts at 1/2 amp.	19/-
6 volts at 1 amp.	22/6
12 volts at 1 amp.	24/6
6 volts at 2 amps.	37/6

MOVING COIL SPEAKERS

All complete with transformer. Rola 8 in. P.M.s, 16/6; 10 in. P.M.s, 22/6; G.12 P.M.s, 66/-.

ENERGISED MODELS

Plessy 8 in., 2,500 or 7,500 ohm field, 7/6; G.12 energised, 59/6.

SHORT-WAVE CONDENSERS

Trolitul insulation. Certified superior to ceramic. All - brass construction. Easily ganged.

15 m.mfd.	1/9
25 m.mfd.	2/-
40 m.mfd.	2/-
100 m.mfd.	2/3
160 m.mfd.	2/6
250 m.mfd.	2/11

PREMIER MICROPHONES

Transverse Current Mike. High grade large output unit. Response 45-7,500 cycles. Low hiss level. 23/-.

Moving Coil Mike Permanent magnet model requiring no energising. Response 90-5,200 cycles. Output .25 volt average. Excellent reproduction of speech and music. 48/-.

Microphone Transformers. Suitable for all mikes. Tapped secondaries. A, 20 and 40 : 1; B, 30 and 60 : 1. 6/6 each.

Microphone Stands. Bakelite table stand, 9 in. ring, 7/6 each.

Adjustable Floor Stand. 8 in. ring. Chrome finish. 26/6.

SHORT-WAVE COILS, 4- and 6-pin types, 13-26, 22-47, 41-94, 78-170 metres, 2/- each, with circuit. Premier 3-band S.W. coil, 11-25, 19-43, 38-86 metres. Suitable any type circuit, 2/11.

UTILITY Micro Cursor Dials, Direct and 100 : 1 Ratios, 4/3.

Special Purchase of

"AIR WARDEN"

5-VALVE MIDGET RECEIVERS for 200-250 v. A.C. Mains

Completely self-contained in highly polished wood cabinet 12 x 9 1/2 x 9 in. with built-in Moving Coil Speaker.

Wave range 190-550 metres. Usual Price. £6-6-0.

OUR PRICE 55/-

The Ideal "Stand-by" Receiver.

REPLACEMENT VALVES FOR ALL SETS

EUROPA MAINS VALVES. 4 v. A.C. Types A.C./H.L., A.C./L., A.C./S.G., A.C./V.M.S.G., A.C./H.P., A.C./V.H.P., A.C.P., all 5/3 each. A.C./H.P., A.C./V.H.P., 7 pin, 7/6. A.C./Pens. I.H., 7/6; A.C./P.X4, 7/3; Oct. Freq. Changers, 8/6; Double Diode Triodes, 7/6; 3 1/2-watt D.H. Triode, 9/9. 350 v. F.W. Rect., 5/6; 500 v., 6/6. 13 v. 2 amp. Gen. Purpose Triodes 5/6; H.F. Pens. and Var.-Mu H.F. Pen., Double Diode Triodes, Oct. Freq. Changers, 7/6 each Full and Half-wave Rectifiers, 6/6 each.

TRIAD U.S.A. VALVES

We hold the largest stocks of U.S.A. tubes in this country and are sole British Distributors for TRIAD High-grade American Valves. All types in stock. Standard types, 5/6 each. All the new Octal Base tubes at 6/6 each.

CLEARANCE LINE U.S.A. VALVES

U.S.A. Types, 24, 30, 35I51, 55, 56, 57, 58, 71, 85, 2A5, 2A6, 2A7, 2B7, 6A7, 210, 250, all 2 for 3/-.

YOU MUST HAVE OUR GIANT 1940 ILLUSTRATED CATALOGUE AND VALVE MANUAL ——— OVER 100 PAGES. PRICE 6d.

PREMIER RADIO CO.

ALL POST ORDERS to: JUBILEE WORKS, 167, LOWER CLAPTON ROAD, LONDON, E.5 (Amherst 4723).


CALLERS to: Jubilee Works, or 169, Fleet Street, E.C.4 (Central 2833), or 50, High Street Clapham, S.W.4 (Macaulay 2361).

MARCONIPHONE

885

World's finest gramophone
Mains-controlled constant
speed motor
All-world reception
Hairbreadth selectivity
Real beauty of tone
Low cost

A Marconiphone radiogram, obviously. Appealing alike to the 'ordinary listener' and to the critical technician, with its handy frontal controls for radio and its lid that need be opened only for gramophone playing. Push-button tuning—of course. But with a permeability system by which the listener can instantly pre-select for push-button control programmes of his own choosing. A superhet circuit bristling with worth-while improvements—yet basically a tried and tested arrangement—that has proved its metal in the crucible of an enviably long technical experience. Bringing the world to the fireside with astonishing ease, or reproducing records through a perfected combination of pick-up amplifier and speaker. Inexpensive, yet latent with all that is desirable in modern radio and gramophone engineering. In a word, a thoroughbred!

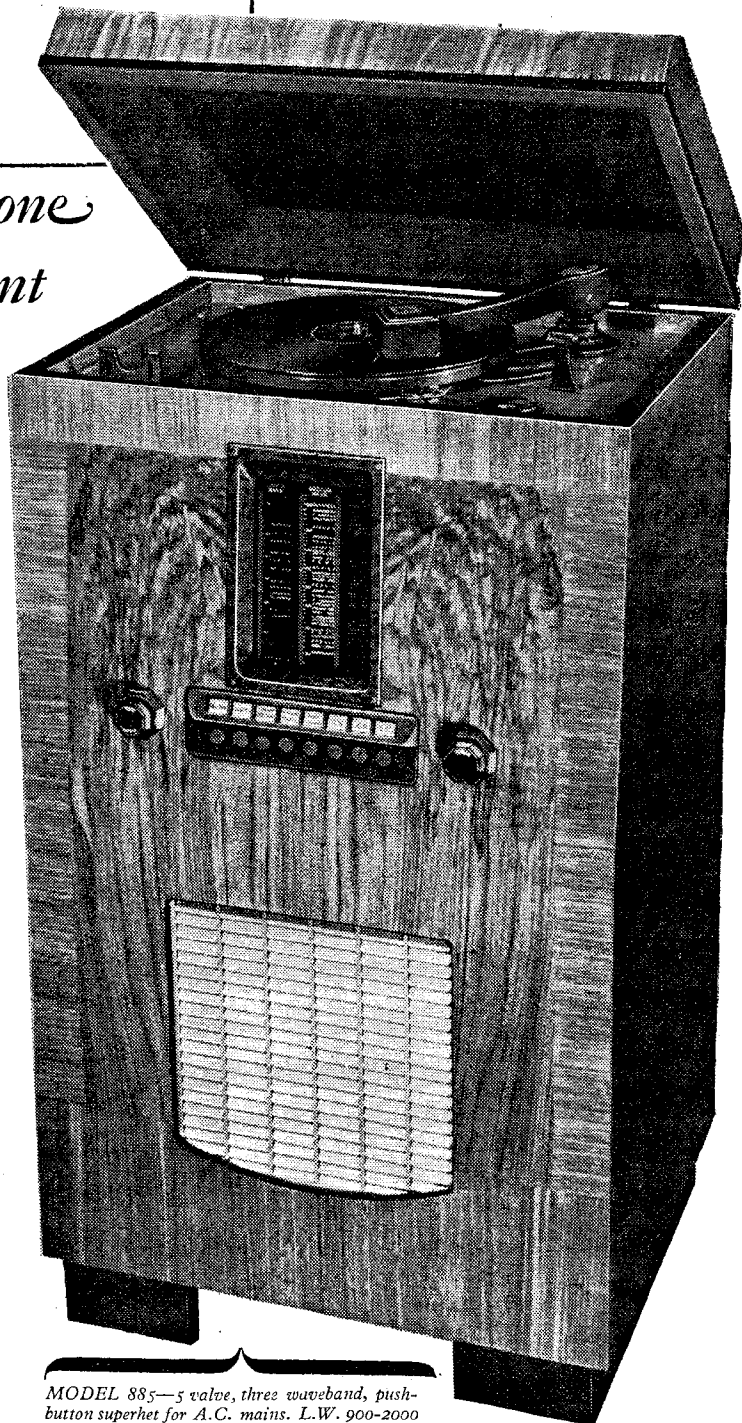

MODEL 885—5 valve, three waveband, push-button superhet for A.C. mains. L.W. 900-2000 metres, M.W. 192-570 metres, S.W. 16-51 metres. Separately lit wavebands. Automatic volume control. Five "easy-change" station-selector push-buttons. Push-button waveband switching. Mains-controlled constant-speed motor with improved switch brake mechanism. External speaker socket-switch device. Rated output 5 watts.

22 gns

THE MARCONIPHONE COMPANY LTD., BOURNES BRIDGE, HAYES, MIDDLESEX

The Wireless World

COVERING EVERY WIRELESS INTEREST

29th Year of Publication

Proprietors : ILIFFE & SONS LTD.

No. 1052

VOL. XLVI No. 4

Editor :
HUGH S. POCOCK.

FEBRUARY 1940

Editorial,
Advertising and Publishing Offices :
DORSET HOUSE, STAMFORD STREET,
LONDON, S.E.1.

Contents

Telephone : Waterloo 3333 (50 lines).
Telegrams : "Ethaworld, Scdlst, London."

EDITORIAL COMMENT	119
SHORT-WAVE VALVES. By F. E. Henderson, A.M.I.E.E. ..	120
PROBLEM CORNER	123
LOUD SPEAKER DESIGN	124
INDUCTIVE DEAF AID. By G. A. V. Sowter, B.Sc.(Eng.)Lond., A.M.I.E.E. ..	126
SINGLE-DIAL BAND SPREAD	129
REACTION REFINEMENTS	133
BUSH MODEL PB63: TEST REPORT	136
CURRENT TOPICS	138
GETTING THE BEST FROM RECORDS: PART I—THE RECORDING CHARACTERISTIC. By P. G. A. H. Voigt, B.Sc., A.M.I.E.E.	141
SHORT-WAVE RECEPTION. By "Ethacomber"	144
PETO SCOTT TROPHY 6: TEST REPORT	146
LETTERS TO THE EDITOR	148
NEWS IN ENGLISH FROM ABROAD	150
CATHODE CIRCUIT PROTECTION	151
RANDOM RADIATIONS. By "Diallist"	152
SHORT-WAVE STATIONS OF THE WORLD	154
RECENT INVENTIONS	155

COVENTRY: 8-10, Corporation Street.
Telegrams : Telephone :
"Autocar, Coventry." 5210 Coventry.

BIRMINGHAM:
Guildhall Buildings, Navigation Street, 2.
Telegrams : Telephone :
"Autopress, Birmingham." 2971 Midland (5 lines).

MANCHESTER: 260, Deansgate, 3.
Telegrams : Telephone :
"Hiffe, Manchester." Blackfriars 4412 (4 lines).

GLASGOW: 26B, Renfield Street, C.2.
Telegrams : Telephone :
"Hiffe, Glasgow." Central 4857.

PUBLISHED MONTHLY.


Price : One Shilling
(Publication date 20th of preceding month.)

Subscription Rates :
Home and Abroad, 14/- per annum.

As many of the circuits and apparatus described in these pages are covered by patents, readers are advised, before making use of them, to satisfy themselves that they would not be infringing patents.

INTEREST and ENTERTAINMENT!

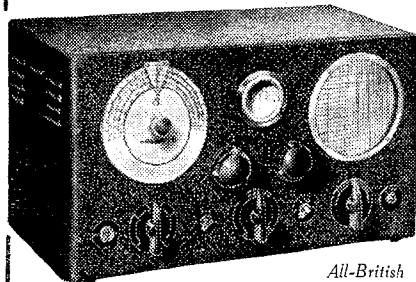The limitations of the so-called all-wave type of receiver is most evident when listening in on the lively ether on 7 to 550 metres



All-British

TROPHY

➔ "6" ➔

Recommended receiver in the junior communications class, 6 valves, electrical bandspreading and other refinements for reliable reception on 6.5 to 545 metres. **£10.19.6**

➔ "8" ➔

Super 8-valve A.C. communications model. R.F. all 5 bands, 7 to 550 metres. Soto-knob bandspreading. Cabinet speaker, 46/3 extra. **£13.17.3**



Installed at RADIO ROYAL
TROPHY models from £6.6.6. Deterred terms. Send now for lists. Demonstrations—note London addresses. Available from all Dealers. Scotland: Clydesdale Supplies. Manchester: Frank Dunderdale Ltd.

Fully Guaranteed.

PETO SCOTT CO. LTD.,

77, (WM4) City Road, London, E.C.1. Tel.: Chisold 9875.
41, High Holborn, W.C.1. Tel.: Holborn 3248.

TWO jobs of work



Two big problems are now facing wireless engineers in this country. First, to meet well and quickly the demands of our Forces—demands which are usually very different from those of domestic radio. Second, to safeguard the standards of domestic radio during a period of many difficulties, of which shortage of material is only one. Of our War work I must not speak. Our plans for domestic radio you will soon know and I believe readers of this paper will approve them. We are going to concentrate on essentials and let all frills and furbelows go hang—a fine large metaphor, I know, but it expresses what I mean.

E. J. POWER, *Managing Director.*

All Murphy Sets, inclusive of valves and batteries, guaranteed for a year

MURPHY RADIO

MURPHY RADIO LIMITED, WELWYN GARDEN CITY, HERTFORDSHIRE

The Wireless World

COVERING EVERY
WIRELESS INTEREST

ESTABLISHED
1911

No. 1052. Vol. XLVI. No. 4

FEBRUARY 1940

Price One Shilling

Editorial Comment

Broadcasting and the Press

DURING the early days of the war it became evident that the Press of this country resented competition from the B.B.C. in the dissemination of news. In commenting on this matter at the time, we expressed the hope that competition would give way to collaboration and, by modifying their methods to suit changed conditions, each party would use its own channel of news presentation to serve the best interests of the public.

Wireless people might be expected to hold the view that an unlimited increase in the power and influence of broadcasting, at the expense of the Press, would be no bad thing. But to do so would be short-sighted; the two services should be complementary, and a strong and virile Press is just as vital as it was before the days of broadcasting. A public that absorbed all its topical information through the ear would lose some of its powers of critical judgment, and would be easily lead along wrong paths by any smooth-tongued demagogue who managed to gain access to the microphone. An important difference between the spoken and the printed word is that one can absorb the meaning of the latter at one's own pace, going back to check facts or to ponder at will over suspected contradictions.

One of the most important tasks that awaits Sir John Reith, the newly appointed Minister of Information, is to smooth away differences that have arisen between the Press and broadcasting, and to help both of them to keep this country—and indeed the whole world—well informed. Veiled suggestions have been put forward that a handicap should be imposed on the B.B.C. by occasionally withholding “scoops” from the Corporation for long enough to allow prior publication

in the newspapers. We do not think that Sir John will for one moment lend an ear to these proposals; such artificial and Canute-like attempts to offset the natural advantages enjoyed by broadcasting in the rapid dissemination of news can only result in failure, and, more important, cause a decline in confidence in our National information service.

Sir John Reith has been associated with broadcasting long enough to be attuned to the speed of modern communication, and, in particular, to have a knowledge of the all-pervading influence of short-wave wireless. We have long felt that the wireless man's outlook, which must in the nature of things be a wide one, has not been sufficiently in evidence at the Ministry of Information, and Sir John's appointment is therefore a matter for satisfaction and congratulation.

So far there are few signs of collaboration between Press and broadcasting, and still fewer indications of those changes in technique on both sides for which we have pleaded. To suggest ways and means is beyond our province; that is a matter for specialists. Some of the possibilities of collaboration are examined in Mr. Wickham Steed's book “The Press.” The author, a former editor of *The Times*, contends that the B.B.C. news service does not necessarily conflict with the function of the newspapers, and that the two channels of news distribution should be supplementary. It is interesting, though perhaps not strictly pertinent to our present subject, to see that Mr. Steed considers the broadcasting of news and views as a “wholesome influence” that may be helpful to the Press.

The world is sorely in need not merely of news but of guidance; it would be a tragedy if the two main channels failed through mutual jealousy or bickering to give of their best.

Short-wave Valves

ADVANTAGES OF SPECIALISED TYPES

By F. E. HENDERSON, A.M.I.E.E. (Osram Valve Dept., The General Electric Co., Ltd.)

THE study of short-wave radio communication goes back very many years, but it is only comparatively recently that ordinary broadcasting sets have been produced for operation over the bands of frequencies corresponding to what are commonly described as "short waves," and generally understood to represent wavelengths below 100 metres. Actually, in commercial practice 100 metres is now considered to be almost "long waves," and the fun really starts when the operating wavelength is extended to below the 15-metre mark. Difficulties in apparatus design and operation go up by leaps and bounds as we descend the wavelength scale still farther, and to obtain a true idea of what we have to deal with it becomes essential to cease talking in wavelengths and become accustomed to think in terms of frequency—millions of cycles, or *megacycles*, per second.

As an example, how many readers realise that the difference between, say, 2 and 2½ metres—only half a metre in terms of wavelength, represents a *frequency*



difference of no fewer than 30 megacycles or 30 million cycles per sec.!

Admittedly, few readers will find it necessary to operate at wavelengths as low as this, but many may have begun to experience the difficulties and unusual precautions associated with ultra-high frequency working when television was launched upon us with all its attendant interests and problems.

To obtain an appreciation of the reasons why short waves bring problems of increasing difficulty in their train, these difficulties going up more and more steeply

Certain effects that are quite innocuous on medium or long wavelengths are liable to give trouble when dealing with short waves. It is shown how these troubles may be minimised by the use of valves specially designed for short-wave working

TABLE 1

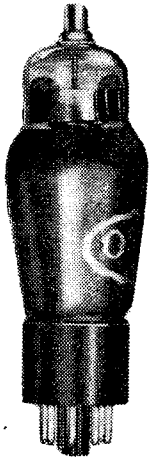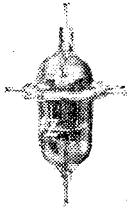	<p>NORMAL RF PENTODE (KTW 63)</p> <p>Mutual conductance 1.5 mA/volt</p> <p>Input capacity 4.5 μF</p> <p>Input impedance at 40 Mc/s ... 13,000 ohms</p>
<p>(To same scale)</p> 	<p>"ACORN" PENTODE (ZA 1)</p> <p>Mutual conductance 1.4 mA/volt</p> <p>Input capacity 3.0 μF</p> <p>Input impedance at 40 Mc/s ... 50,000 ohms</p>

Comparison of input impedance between R.F. pentode of normal design and pentode of comparable mutual conductance but "scaled down" electrodes and short leads.

as the wavelength goes down, some knowledge of the effect of very high frequencies both on circuit values, designs and materials must be available.

There are many aspects from which the complete picture can be viewed, and each component part requires a separate study in itself as to how it is affected by being required to operate at HF voltages, or to carry currents with minimum loss at very high frequencies.

In this article we intend to look at the problem from the point of view of one component—the *Short-wave Valve*. Further, as the average reader's interest in the valve is necessarily restricted at the present time to receiving conditions, the scope can without disadvantage be narrowed down to exclude all the additional problems involved in transmitting conditions, but even so, the demands for reasonable efficiency in the receiving valve and circuit involve no little care in design and application.

Let us ignore for the purpose of this discussion the "ultra-highs" or "micro-waves" as being of small practical interest to the normal reader and consider for our present purpose the realm of short waves lying between, say, 40 metres (7.5 megacycles) and 5 metres (60 megacycles).

What are the principal points to watch in the design of a receiving valve to function satisfactorily at such frequencies, and what are the effects of different designs on the associated circuits?

When a valve is used to amplify a voltage

Short-wave Valves—

developed across a tuned circuit, as in an RF amplifier, the valve itself may introduce several different effects, all of which tend to have an effect on the voltage existing across the tuned circuit in some way or other.

First, there is the purely shunting effect of the valve resistance, which is in parallel with the input circuit and causes damping, with resultant loss in efficiency. The valve characteristic which introduces this damping is called *input impedance*, and becomes of great importance on short waves. This is because the effective value of the shunt resistance decreases in proportion to the square of the frequency.

The input impedance of a valve may be affected by two features:—

(a) The "transit time" of the electrons.

(b) The inductance in the cathode lead.

It would be obviously absurd to spoil a high efficiency tuned circuit by shunting it by a resistance unless a wide band of frequency coverage were required at the expense of selective amplification.

Therefore, two of the aims in design of modern short-wave valves are to reduce the effect of electron transit time and to minimise the cathode lead inductance.

First, then, *transit*

time. This may be taken as the relative time taken for an electron to travel across its controlled path, and for the potentials affecting it in this path to change in magnitude or direction. If this time period of changing potentials is very small, it is conceivable that a given potential may completely reverse in phase while the electron is in transit. It is necessary, therefore, to design a short-wave valve such that the electrons are made to traverse the cathode-to-anode distance in as short a time as possible.

This may be done:—


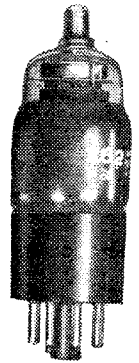
(1) By reduction in the clearances between the electrodes.

(2) By increasing the accelerating voltage; this raises difficult problems of insulation and in the necessary

supply of high voltages in the receiver HT circuits.

A reduction of electrode clearances naturally introduces mechanical difficulties into the manufacture of the valve, but results in an increase in its mutual conductance. Improvements in manufacturing technique have

TABLE 2

 <p>KTZ41</p>	<p>NORMAL RF PENTODE (Low Slope Type) (KTW 63)</p>	<p>NORMAL RF PENTODE (High Slope Type) (KTZ 41)</p>
	<p>Mutual conductance, 1.5 mA/volt... Input impedance, at 40 Mc/s ... 13,000 ohms</p>	<p>... .. 7.5 mA/volt 1,800 ohms</p>
 <p>Z62</p>	<p>RF PENTODE WITH SHORT SEAL (Low Slope Type) (KTW 73)</p>	<p>RF PENTODE WITH SHORT SEAL (High Slope Type) (Z 62)</p>
	<p>Mutual conductance, 1.7 mA/volt... Input impedance, at 40 Mc/s ... 20,000 ohms</p>	<p>... .. 7.5 mA/volt 4,000 ohms</p>

Comparison of input impedance in RF pentodes of comparable mutual conductance, normal and short seal designs. (For the same values of input capacity and lead inductance, the input impedance is inversely proportional to the mutual conductance.)

enabled such reduction in clearances to be achieved, and in short-wave valves this may be utilised by employing a shortened electrode system with the advantages of reduced electrode capacities and, at the same time, entailing no sacrifice of mutual conductance.

The table (No. 1) shows a comparison between two typical RF pentode valves of comparable mutual conductance, and indicates how the "scaled-down" electrode system of the specialised short-wave valve effectively increases the input impedance at high frequencies. It will be noticed that in spite of the reduced clearances the inter-electrode capacity of the "Acorn" is not increased.

Secondly, we come to the effect of the cathode lead. This lead wire has an inductance which, small though

Short-wave Valves—

it may be; represents a very appreciable impedance at high frequencies.

The cathode lead is, therefore, in effect, an inductance common to both grid and anode circuits; thus a component of the anode current produced by the grid

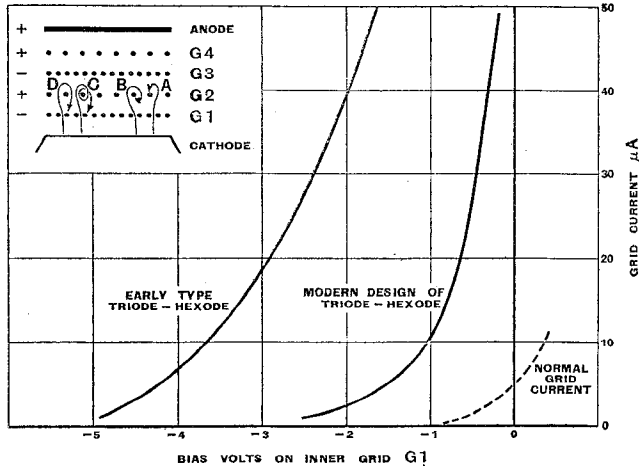


Fig. 1.—“Transit time” grid current in a triode-hexode operating at 20 Mc/s. The majority of the electrons follow paths such as A and B in the inset diagram, but a small proportion follow paths C and D, thus giving rise to a current in the circuit of the grid G₁.

voltage results in a voltage being developed across the cathode lead inductance which is out-of-phase with the grid voltage.

If the impedance of the grid-cathode path were low, such out-of-phase voltage would introduce serious damping across the input tuned circuit, and, unfortunately, it is not possible to ignore such an impedance between the grid and cathode, due to the interelectrode capacity of the valve called the *input capacity*.

Development of short-wave valves, therefore, must also take into account reduction in the grid-cathode capacity if the out-of-phase voltage developed in the cathode circuit is not to be reflected back to the grid circuit with resultant damping. This effect is *in addition* to any effect resulting from the grid-cathode capacity in itself.

The relative effects of the grid-anode and the grid-cathode capacities depend upon the voltages produced; at long waves, or as we approach audio-frequencies, the effect of the cathode impedance normally becomes negligible, and then the grid-anode capacity becomes of prior importance, particularly as the voltage developed across the load circuit can be increased due to higher efficiency tuned circuits, and “feedback” through the grid-anode capacity is a limiting factor.

Table No. 2 shows the relative effects on input impedance by a considerable reduction in cathode lead inductance, resulting from a shortened electrode system. A comparison is given both in the case of the low-slope

and in that of the high-slope classes of RF valve, two well-known types being used as examples.

A type of valve which requires special care in design for efficient short-wave operation is the frequency changer. The type of frequency changer most favoured for this purpose is the triode-hexode multiple valve, or variations of this principle.

In this form of frequency changer the signal is applied to the inner grid in proximity to the cathode, and the oscillator voltage injected by means of a further grid which is joined to that of the local oscillator. It is not, of course, necessary for the oscillator and mixing sections of the valve to be contained in the one envelope, but from the points of view of economy in space and cost, and of facilitating set design, this is commonly done. Sometimes it is desirable for the oscillator to be separate—that is, to operate on a separate cathode system—as will be seen later.

In the triode-hexode class of valve, the coupling between signal and oscillator circuits may be made very small, and “interaction” between them be reduced to a minimum. This effect, often referred to as “pulling,” is well known with certain designs of frequency changers unsuitable for use at short wavelengths.

Having minimised this by suitable design, however, there remains the important effect of electron transit time.

The nature of this transit time effect in short-wave operation is indicated by Fig. 1.

In short-wave frequency changers it is important that the time taken by the electrons in transit between screen and oscillator grid should be as short as possible. This time may be minimised by reducing the oscillator grid-to-screen clearance.

If the oscillator frequency—that is, the time taken for one complete reversal in potential in this space—is comparable with the time taken by an electron in traversing this space, the electron will be driven back to the control grid, the accumulative effect of which is to increase the control grid bias and reduce the effective gain in the valve.

Reduction in oscillator grid-to-screen clearance to

TABLE 3

TRIODE-HEXODE VALVES. HEATER WATTAGE	CHANGE IN OSCILLATOR GRID- EARTH CAPACITY
4.8 (Type X 41)	0.25 $\mu\mu\text{F}$
2.0 (Type X 65)	0.1 $\mu\mu\text{F}$

Effect of heater wattage on “drift.”

overcome this effect naturally increases manufacturing difficulties. With such precautions in design, however, the gain of the valve may be made the same at 30 Mc/s as at 1 Mc/s.

One more aspect of the problem is *frequency drift*. This may become important, and is due to a change in the capacity of the valve due to changes in the mechanical dimensions and in the dielectric constant of the base, both of which are caused by changes in temperature.

Short-wave Valves—

The two ways of counteracting this effect are:—

- (a) Reduction in the inherent electrode capacities.
- (b) Operation at the minimum temperature.

When a receiver is switched on, the cathode of the valve may reach a steady temperature in less than half a minute, but it may take half an hour or more for the whole electrode system to do likewise. This effect becomes more troublesome with an increase in frequency.

Table No. 3 shows a comparison of the change in the oscillator grid-to-earth capacity of typical valves of different heater wattages, so that, in general, the lower the heater voltage the smaller are the capacity changes, and, therefore, the frequency drift of the oscillator with time. This drift may sometimes be reduced by the use of a separate oscillator (referred to above), as in such a case the oscillator grid may be tapped down on the oscillator circuit, and so the effect of drift minimised.

As the development of short-wave valves proceeds apace, the reader will be able to follow from the arguments given in this article the reasons underlying various fundamental features in the design of new-type short-wave valves as they appear.


fault, until I spotted that the meter had been connected to the wrong tag on the valve-holder—I have never been able to remember valve base connections since the octals came in—and when I corrected this matter the reading was fully up; in fact, rather more than usual. But even now the thing won't work properly, although I have been over every connection and component about half-a-dozen times, and am fed up. It is noisy and gives practically no output. Have you any further helpful suggestions to offer? If so, I would be grateful.

Yours sincerely,
Mark Linyer.

What is wrong? Turn to page 132 for Henry Farrad's solution.

CR Tubes and Implosion

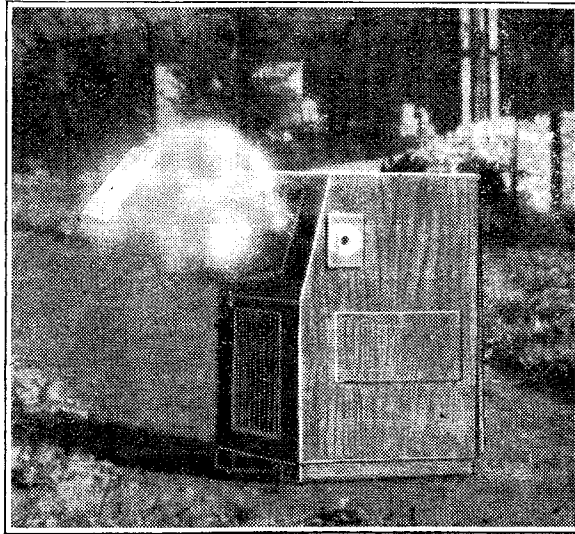IT is generally known that in the case of large cathode-ray tubes such as are used in television sets there is some slight risk of the costly tube shattering, due to an inherent



In the tests, tubes were shattered by a rifle bullet fired through a hole coinciding with the bull's-eye of the target which can be seen on the side of the cabinet. In this case, the glass screen was obviously of inadequate strength.

mechanical defect, or to its receiving a severe blow on the front, which is the weakest part of it. The reason for this is, of course, that the tubes are pumped to a high degree of vacuum, with the result that there is a considerable pressure on the glass walls, more especially the front wall, tending to cause them to collapse inwards, or "implode," as it is usually termed. Great care is taken in the manufacture of the tubes, and there is a sufficient degree of curvature of the front wall to minimise this risk of implosion. It is considered desirable, however, in order to make assurance doubly sure to mount the tube behind a protective glass screen, since if implosion does occur fragments of glass collapsing inwards attain sufficient velocity to overshoot the mark and scatter in all directions.

Experiments in the Kolster-Brandes laboratories have, according to a recent article in *Electrical Communication*, shown that for absolute safety, "armour-plate" glass having a thickness of not less than a quarter of an inch should be used. In the case of experiments in which several tubes were deliberately imploded it was found that ordinary plate glass and other materials afforded insufficient protection.

Henry Farrad's Problem Corner


No. 43.—The Obduracy of an Amplifier

An extract from Henry Farrad's correspondence, published to give readers an opportunity of testing their own powers of deduction:—

100, Quality Street,
Raisley.

Dear Mr. Farrad,

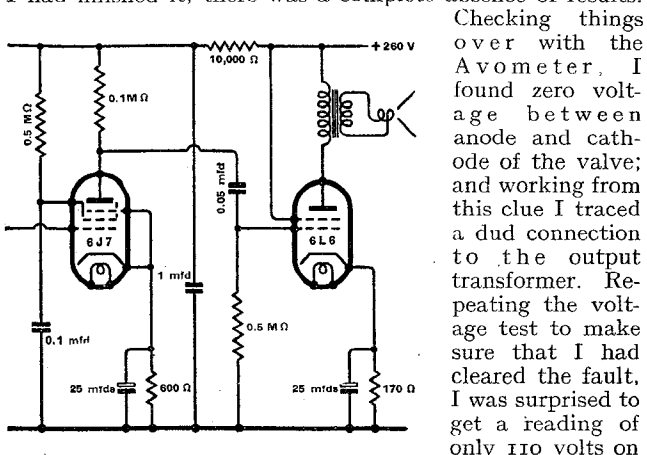Thank you for helping me with the tone corrector in my amplifier.* I have shifted it to an earlier stage, as you suggested, so that there is a high-gain stage between it and the output valve. The latter is now quite conventional, as shown in the diagram herewith. But when I had finished it, there was a complete absence of results.



Checking things over with the Avometer, I found zero voltage between anode and cathode of the valve; and working from this clue I traced a dud connection to the output transformer. Repeating the voltage test to make sure that I had cleared the fault, I was surprised to get a reading of only 110 volts on the 600-volt range. Leaving the meter connected I poked about for some considerable time, but found no further

*The Wireless World, August 3rd, 1939.

Loud Speaker Design

FREQUENCY CHARACTERISTIC TO COUNTERACT ROOM EFFECT

THE sound from a loud speaker working in a small room does not disperse freely into space like the energy from, say, a public-address loud speaker in the open air. Some of it is rapidly absorbed in the walls and furnishings, especially that which is contained in the high-frequency components of the sound. The low frequencies, on the other hand, may be reflected from the walls, floor and ceiling many times before they disappear, and at each reflection will reinforce the direct sound heard by a listener. In fact, the room should be regarded as an essential part of the sound-reproducing system.

It follows that a different type of frequency characteristic will be required for correct tonal balance in a

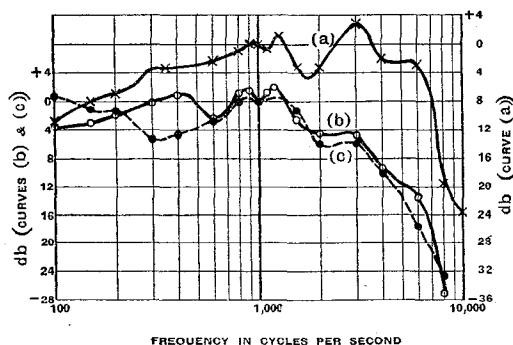


Fig. 1.—Response of typical loud speaker with enclosed back (a) on axis in free space, (b) mean spherical response in free space, (c) average sound pressure in typical furnished living-room measuring 24ft. x 12ft. x 11ft. 6in.

room than for listening at a point on the axis of the loud speaker in the open air. Just what that difference should be will depend not only on the absorption characteristic of the room and its furnishings, but also on the position of the listener and the ratio of direct to reflected sound at that point. The best that can be done is to strike an average for a typical living room and take this as the basis for the specification of the loud speaker characteristic.

Loud Speakers with Enclosed Backs

The formidable task of making a statistical survey of the sound pressure at different points in a room for different positions of the loud speaker has been undertaken by W. West, B.A., and D. McMillan, B.Sc., of the Post Office Engineering Department, and their findings are given in a recent paper.¹

The type of loud speaker selected for study was that in which the back of the cabinet is totally enclosed to suppress radiation from the back of the diaphragm (the

¹ "The Design of a Loud Speaker," allocated for reading before the Wireless Section of the Institution of Electrical Engineers on 6th December, 1939.

A recent paper addressed to the Wireless Section of the Institution of Electrical Engineers makes an important contribution to our knowledge of the acoustics of small living-rooms, and the data given in the following abstract should prove of value to all interested in quality reception in the home

so-called "infinite baffle"). Apart from the improved bass response obtainable with this type of baffle, the investigations were simplified by the elimination of the second source of sound. It was found that for a given size of baffle and diameter of diaphragm a simple relationship existed between the axial response and the mean spherical response in free space.

The latter curve was obtained by calculation from the combined curves taken at 0, 30, 60, 90, 120, 150 and 180 degrees off the axis of the diaphragm.

Average Sound Pressure in Room

Next the loud speaker was set up in a "typical living-room," the acoustical characteristics of which were adjusted so that they were judged to be similar to those commonly found in the rooms of dwelling-houses. The loud speaker was fed with a "warble tone" with a frequency variation of ± 20 c/s, five times per second. Measurements of sound pressure were then made, using a 4ft. wire cube to locate the positions of the calibrated microphone. Readings were taken at the eight corners, and the centre of the cube, and measurements, expressed in decibels, were averaged arithmetically. After lengthy investigations it was found that three different positions of the locating frame for each of two positions of the

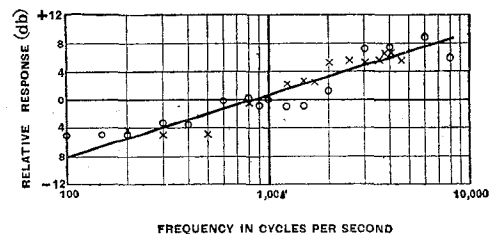


Fig. 2.—Results of analysis of two loud speakers with enclosed backs showing axial response relative to constant mean spherical response. An average rise of output of 2.5 db per octave, measured on the axis, is required to give constant mean spherical response, and hence constant average sound pressure in a typical room.

loud speaker gave a stable average which could be repeated within 2 db at any individual frequency. Each point on the curves of frequency response in the room thus represented at least 54 microphone readings.

Loud Speaker Design—

The group of curves in Fig. 3 represent a complete investigation for one loud speaker. It will be seen that the average sound pressure in the room is related not to the axial sound pressure but to the mean spherical pressure in free space. The same experiment repeated for other loud speakers and rooms produced similar results.

The next step was to establish the relationship between the axial response and the mean spherical response in

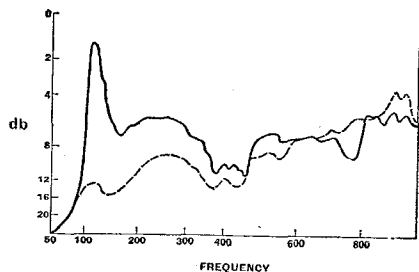


Fig. 3.—Response curves of loud speaker with closed case, full line without damping, dotted line with cotton wool 1 inch thick wrapped round the back of the loud speaker unit.

order that a single curve might be used as a criterion of the performance to be expected in a room. Accordingly, a number of sets of curves were analysed, and a mean curve drawn through the points obtained. These showed (Fig. 2) that for the type of loud speaker under discussion the axial response curve rises approximately 2.5 db per octave relative to the curve of mean spherical sound output, and that a single curve taken in the axis and showing a progressive rise of output with frequency of this amount may be taken as evidence that the loud speaker will produce constant average sound pressure when used in the average living-room.


It is emphasised that this relationship holds only for loud speakers with totally enclosed backs and a diaphragm diameter of about 7 inches, and the design of this type is dealt with in some detail. It is pointed out that the diaphragm resonance will be determined principally by the volume of the air enclosed in the space behind the diaphragm, and a useful formula is given for calculating the resonant frequency on the assumption that the stiffness of the diaphragm centring devices is small relative to that due to the enclosed air. The

formula is:—

$$f_n^2 = \frac{A^2 \rho c^2}{4\pi^2 m v}$$

Where f_n = resonant

Fig. 4.—Section of loud speaker casing suggested as the result of experiments. The lead sheet is used on the back and sides only, while the felt and corrugated packing paper are applied to back, sides, top and base. The outer case is made from 3/8 in. plywood and measures 16 in. high x 14 in. wide, 8 1/2 in. deep, and has an aperture 8 in. in diameter centred 6 in. from the top of the case.

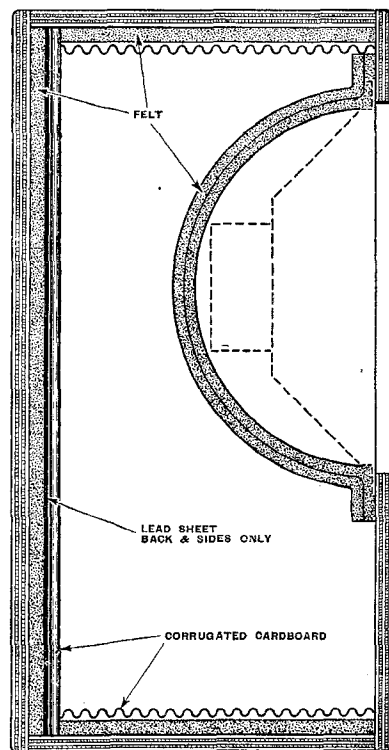


frequency, A = effective area of diaphragm, ρ = density of air, c = velocity of

sound in air, m = mass of diaphragm with coil attached, v = volume of enclosed air.

Without adequate damping the amplitude developed at the main resonance may be considerable. In the specification put forward by the authors (for mass production at reasonable cost) the damping is mechanical and is provided by layers of felt near the back of the diaphragm, where the air displacement is greatest. The curves of Fig. 3 show the effectiveness of this method in practice.

The inside of the case is lined with felt and lead sheet (8oz. per sq. ft.) to ensure complete absorption at low frequencies, and the inner surface is composed of corrugated paper, presumably to scatter and break up internal reflections at high frequencies.

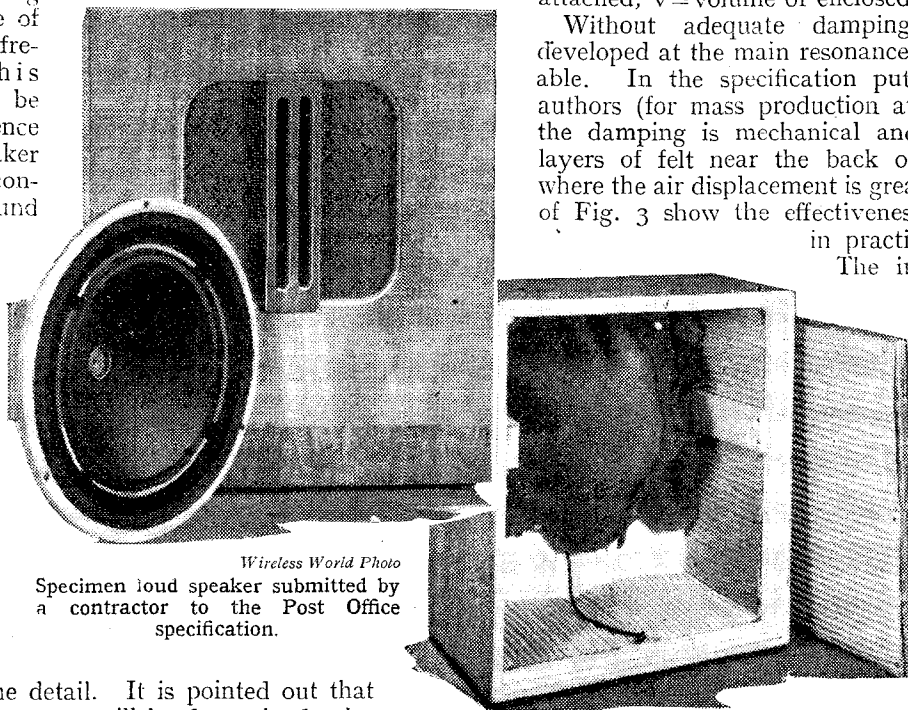Detailed dimensions are given in the original paper but as they relate to a diaphragm, the origin of which is not disclosed, they are not of direct interest to the general reader. It is to be noted, however, that the diaphragm is of the "free-edged" type.



Wireless World Photo
Specimen loud speaker submitted by a contractor to the Post Office specification.

Inductive Deaf Aid

DESIGN OF A PRACTICAL ELECTRO-MAGNETIC SYSTEM

By G. A. V. SOWTER, B.Sc. (Eng.) LOND., A.M.I.E.E.

THE first step towards investigating induction by audio-frequency currents was to run a single loop of wire around the floor of a room as closely as possible to the walls in order to cover the largest area. The ends of the loop were then connected to the radio set output so that the AF currents passed through this loop. The first tests, which can be repeated by any interested reader, were conducted with some early plug-in, long-wave coils extracted from the author's junk box. A pair of telephones were connected to the ends of one of these coils (Fig. 1) in a manner similar to that described in the Willoughby Smith experiments, and it was found that the broadcast programme could be heard comfortably in the 'phones whatever might be the position of the operator in the room. As a variant on the usual microphone tricks at Christmas parties this scheme is to be recommended, although several turns of wire round the room may be necessary with less sensitive telephones.

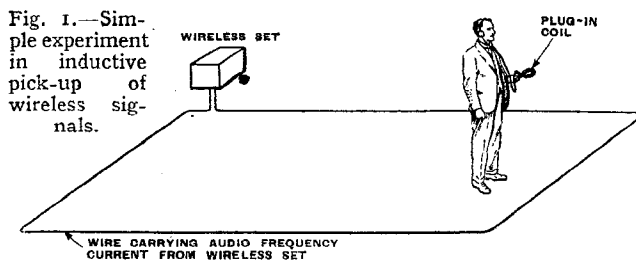


Fig. 1.—Simple experiment in inductive pick-up of wireless signals.

It was noticed that the picked-up programmes varied in strength with different coils, and were susceptible to strength variation with the orientation of the search coil.

Now, bearing in mind the ease with which it is possible to construct transformers which will pick up unwanted hum, it was decided to improve the efficiency of the air-cored pick-up coil in the room experiment by winding a coil with a similar number of turns on a core of soft iron wire. This showed such a distinct improvement over the air-cored coil that an experiment was conducted with the easily magnetised nickel-alloy Mumetal in place of the plain iron.

As is well known, Mumetal has a magnetic permeability of the order of 20,000 for feeble fields, and 80,000 to 100,000 under optimum conditions. When a length of this alloy in the form of an annealed rod is merely placed in the earth's magnetic field, as in Fig. 2, it

The principles of electro-magnetic induction as applied to audio-frequency distribution were described in last month's issue. The author now goes on to show how induction may be used for deaf-aid purposes; the method is particularly suitable for theatres or cinemas, where it has been applied by Multitone

tends to absorb flux, so to speak, but is never magnetically saturated, as was explained in a previous article.¹ The length, and to some extent the diameter, of the

Mumetal rod controls the amount of flux which is picked up, as is indicated by the curve of Fig. 3, which gives the results of a simple experiment.

For this experiment a search coil was placed on a rod 50in. long and $\frac{1}{8}$ in. diameter and the deflections measured on a simple ballistic

galvanometer when the rod was completely reversed in the earth's magnetic field. A few inches were then cut

off the length of the rod and the procedure repeated. Successive reductions in rod length were made, and the galvanometer deflections measured. The results are plotted in the form shown. It is seen that when the rod is a few inches long, the picked-up field is very small, as indicated by the bend at the bottom of the curve. It is very obvious that the longer the rod the greater the pick-up, and this will apply for alternating fields such as those evolved in the room experiment or by the induction deliberately set up on a larger scale, say, in a cinema.

Now, the prospect of assisting the deaf by providing them with long Mumetal rods with search coils and ear-

pieces did not seem very practical, but, in spite of this, a serious suggestion

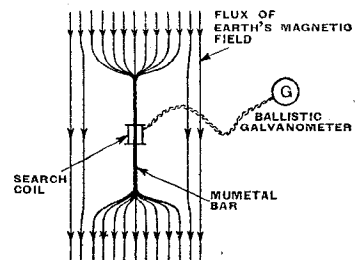


Fig. 2.—Flux distribution of earth's magnetic field in the neighbourhood of a long Mumetal rod. The flux carried by the rod is measured by means of the search coil and ballistic galvanometer, of which the deflection is observed when the rod is reversed.

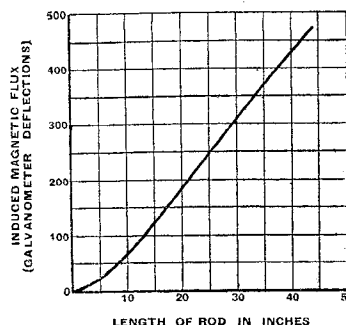


Fig. 3.—Relationship between length of Mumetal rod and induced magnetic flux from earth's field. Rod diameter is 0.125in.

¹ *The Wireless World* August 14th, 1936.

Inductive Deaf Aid—

was made of camouflaging the Mumetal rod for ladies into the form of a lorgnette, and that of the gentlemen into a walking-stick. The idea of a Mumetal walking-stick is by no means new, as the British Society of Dowisers has during recent years employed quite a number of such sticks for the divination of water, and it has been suggested that there is some connection between induction and "dowsing."

To return to the domestic induction experiments, it is assumed that the single loop of wire round the room will compare with the loop that might be installed for deaf-aid purposes in a cinema or theatre except that it is not known accurately what strength of magnetic field is being created therein. If the cinema scheme is to be successful it is assumed that eventually some agreed minimum field will be established such as that created by an RMS speech current of 2, 5 or more amperes passing through a single turn.

A number of transformer bobbins of the dimensions indicated in Fig. 4 were obtained. This was considered a practical size for a portable device, and each bobbin was wound with wire of a different gauge, so that the winding space was completely filled. This meant that there became available a number of pick-up coils having different turns up to 16,000 and with widely divergent resistance values. Two Mumetal rods 18in. long were available for insertion in the coils, and these rods were labelled X and Y respectively. X was approximately $\frac{1}{10}$ in. in diameter, whilst Y had a section of $\frac{3}{16}$ in. \times $\frac{1}{8}$ in.

Since it was anticipated that the performance might depend upon the type of earpiece employed, it was decided to carry out tests with the conventional lightweight deaf-aid earpieces in general use, such as a crystal type of high impedance and a conventional magnetic type of low impedance.

The method of carrying out the tests was not of a precision nature, but gave some very useful information. The loop

round the room was energised from the radio set with its volume control fixed. Any variation in the B.B.C. modulation and character of the programme should not affect results, as a large number of tests were carried out. Listening tests were made with each available search coil, both with and without the Mumetal rods inserted, and the results for both earpieces are best expressed in the form of the curves in Fig. 5. The ordinate scale is of an unusual nature, but is allied to the "R" code of signal strength.

A summary of useful deductions which can be made from these curves is as follows:—

(a) The search coil must be matched in impedance with that of the earpiece being used. This is not unexpected, since the inductor system has the equivalent electrical circuit of Fig. 6, which brings to mind the

well-known fact that "maximum power is obtained when the external resistance is equal to the internal resistance. (b) The low-impedance earpiece is more suitable than the crystal type. (c) Considerable improvement in picked-up energy is effected by utilising a Mumetal rod even as short as 18in. in length. Little difference was noticed whether X or Y rod was used, although longer rods effected an improvement. (d) A

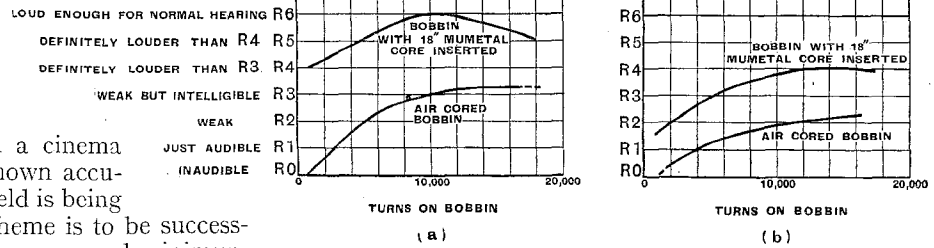


Fig. 5.—Measurements of induced signal strength, made with low-impedance magnetic earpiece (diagram (a)) and with high-impedance crystal earpiece (diagram (b)).

midget air-cored inductor alone of the dimensions specified is not practicable.

To verify this last conclusion, a pancake coil approximately 4in. in diameter and weighing 1 lb. was wound and tried out under the same conditions. The signal obtained was practically inaudible, and it was not considered worth while continuing this experiment to improve the impedance matching.

Interference with Other Services

By increasing the number of inducing turns round the room the received signal was considerably strengthened and led to the conclusion that if the magnetic field strength in a theatre or cinema is adequate, a correctly designed inductor *per se* with limited physical dimensions could give adequate volume for deaf-aid purposes.

The distribution of magnetic field from a single turn of wire carrying current is given in Fig. 7, so that there is a reasonable possibility that a system carrying heavy audio-frequency current may lead to undesired interference with other services. This may limit the permis-

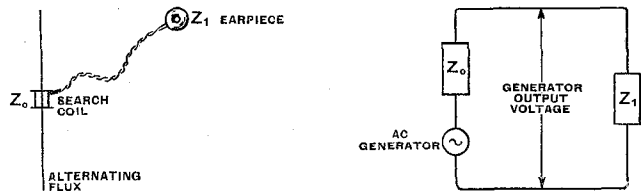


Fig. 6.—Equivalent circuit of inductor connected to earpiece in alternating magnetic field.

sible intensity of the inducing field in the auditorium, and it was therefore decided to carry out further measurements with a weak field, utilising an amplifier which was actually a standard deaf-aid apparatus. In this instance more precise measurements were conducted by the use of a cathode-ray oscillograph for measuring the pick-up and a variable low-frequency

Inductive Deaf Aid—

oscillator for the source of supply to the loop which was placed round the laboratory floor (see Fig. 8).

It was realised that any successful device must eventually be incorporated in the deaf-aid gear, which weighed only $2\frac{1}{2}$ lb., and the increase in weight due to this device must be small. By reason of these limitations various bobbins of the type indicated in Fig. 4 were wound with different gauges of wire to fill completely the winding space available. The number of turns varied between 6,000 and 16,000. A number of rectangular Mumetal laminations of dimensions 2in. by $\frac{3}{8}$ in. by 0.015in. were used to build up cores for these coils.

With the volume control on the deaf-aid amplifier fixed, a suitable resistance was substituted for the ear-piece so that the output voltage due to the induction in

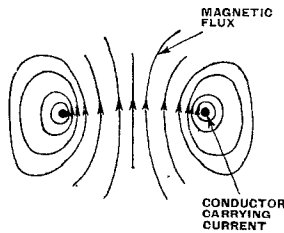


Fig. 7.—Distribution of magnetic field due to a single-turn conductor.

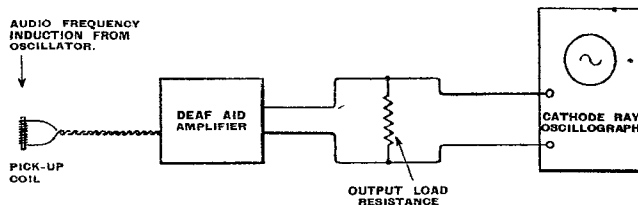


Fig. 8.—Method of testing inductive pick-up devices.

the pick-up coil could be measured by observation on the cathode-ray oscillograph screen. Apart from this, the tests were carried out as before, but readings were taken at different frequencies and with a varying number of Mumetal laminations inserted in the bobbins. The apparatus is shown diagrammatically in Fig. 8.

Summary of Tests

Results of the best coil, which had 10,000 turns, are given in the following table:—

Number of Mumetal laminations inserted as Core	Deflection on C.R.O. in Millimetres		
	500 Cycles	2,000 Cycles	5,000 Cycles
0	3	3.5	5.5
1	9	11	15
2	10	14	16
3	11	15	17
5	13	16	19
Full	14	17	21

It is seen that the insertion of the first lamination has the greatest effect which follows from considerations of the limited flux available, as already discussed. Also, due to the nickel-iron core, the output voltage is increased four to five times, representing a gain of approximately 14 decibels.

Little difference in the output was observable whether the search coil was on the middle or end of the laminations which follows from the fact that most of the flux enters the ends.

A large variety of tests were carried out with the individual bobbins and with bobbins inductively coupled, but the impedance match was a factor, and increasing the turns beyond 10,000 led to reduced output. As a matter of interest it should be noted that a lower permeability nickel iron was not so satisfactory as Mumetal.

Summarising, then, the best design of inductor within the limitations mentioned consists of the following:—

Bobbin: As sketch Fig. 4.

Winding: 10,000 turns of No. 45 SWG wire.

Core: 12 Mumetal laminations 2in. by $\frac{3}{8}$ in. by 0.015in. thick.

Total weight: 2 ounces.

The weight is so small that it can easily be added to an existing deaf-aid equipment without serious effect.

When tried out in a cinema, a deaf-aid amplifier incorporating this design of pick-up was extremely satisfactory and also made it possible for the external magnetic field from an ordinary G.P.O. telephone to be utilised to give greatly enhanced volume, as suggested by certain deaf-aid manufacturers.


New "Raymart" Components

MIDGET MICRO-VARIABLE CONDENSERS AND INSTRUMENT DIALS

IN response to the demand for a high-frequency tuning-condenser occupying the minimum space, a new type has been introduced by Raymart. The spindle is mounted on double-row ball bearings, and both ball races are short-circuited internally by phosphor-bronze brushes. The bearing is very smooth in action and quite free from slackness. A spindle turned from the solid is employed and the insulation is of high-grade ceramic material. Five types are made, with maximum capacities of from 7 to 100 m-mfd., and the prices range from 1s. 7d. to 2s. 3d. each. These condensers are particularly suitable for inclusion in aircraft radio installations where space is limited.

The types TXD and TXJ direct-drive precision-instrument dials are well-finished components, with dull nickel-plated brass scales accurately subdivided in 100 divisions. The knobs are of moulded bakelite, and the metal scale is insulated from the condenser spindle. These dials are British made throughout, and cost 5s. for the 4in., Type TXD, and 3s. 6d. for the 2 $\frac{1}{2}$ in., Type TXJ.

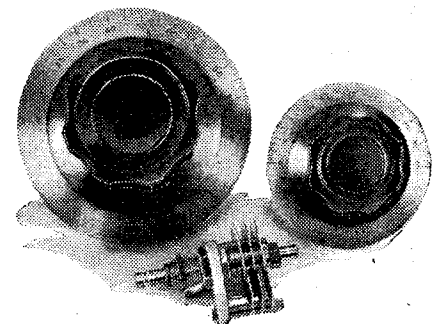The makers are Raymart, G5NI (B'ham), Ltd., 44, Holloway Head, Birmingham, I.



Raymart Types TXD and TXJ instrument dials and Type MC15DX micro-variable condenser.

**SPECIFY
SOUND
SALES**

**WHEN DEPENDABILITY IN AN EMERGENCY
IS A QUALITY THAT CANNOT BE OVERRATED**


Sound Sales Amplifiers are recognised by all established experts to be second to none in compact design, engineering construction, performance and general utility. We have a special department detailed to concentrate on the survey and installation of A.R.P.

Communication Systems under the direction of ex-service men who are able to appreciate the conditions and thus offer specialised technical advice. The illustration shows a typical Sound Sales self-contained Amplifier.

We shall be pleased to send you further details of this model together with a unique but inexpensive multi-channel system which can maintain communications under the most arduous conditions.

May we send you our latest Catalogue and Technical Manual - - - - - Price **6d.**

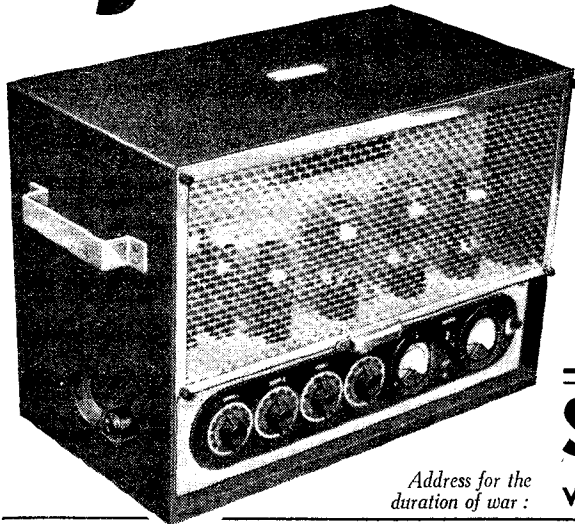All SOUND SALES products can be obtained on DEFERRED TERMS from the LONDON RADIO SUPPLY COMPANY, "Winden," Ardingly Road, Balcombe, Sussex.



Address for the duration of war :

SOUND SALES LTD.
(OF LONDON)
WEST STREET, FARNHAM, SURREY. Farnham 6461-2-3

**POST THIS
COUPON NOW**



The possession of this book is more imperative than ever to discriminating constructors. It describes the world's most reliable rectifier—Westinghouse—in detail; contains many practical circuits; and a wealth of information on H.T. supply, battery charging, detection and A.V.C., etc.

The Westinghouse Metal Rectifier needs no replacement and is very economical and efficient in use.

**WESTINGHOUSE BRAKE & SIGNAL CO. LTD.,
Pew Hill House, Chippenham, Wilts.**


*I enclose 3d. in stamps. Please send me a copy of
"THE ALL-METAL WAY."*

Name.....

Address.....

W.W. 840


**M. MURDO
SILVER
RADIO**

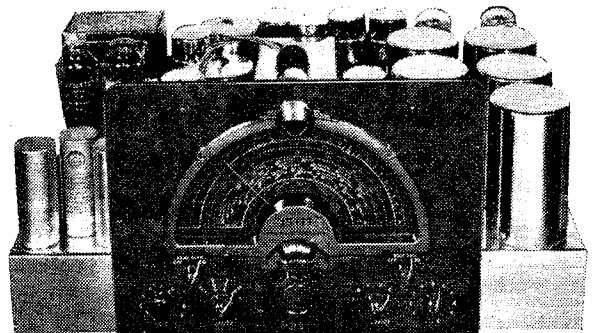

The receiver with a sensitivity of one microvolt absolute

May we send you details

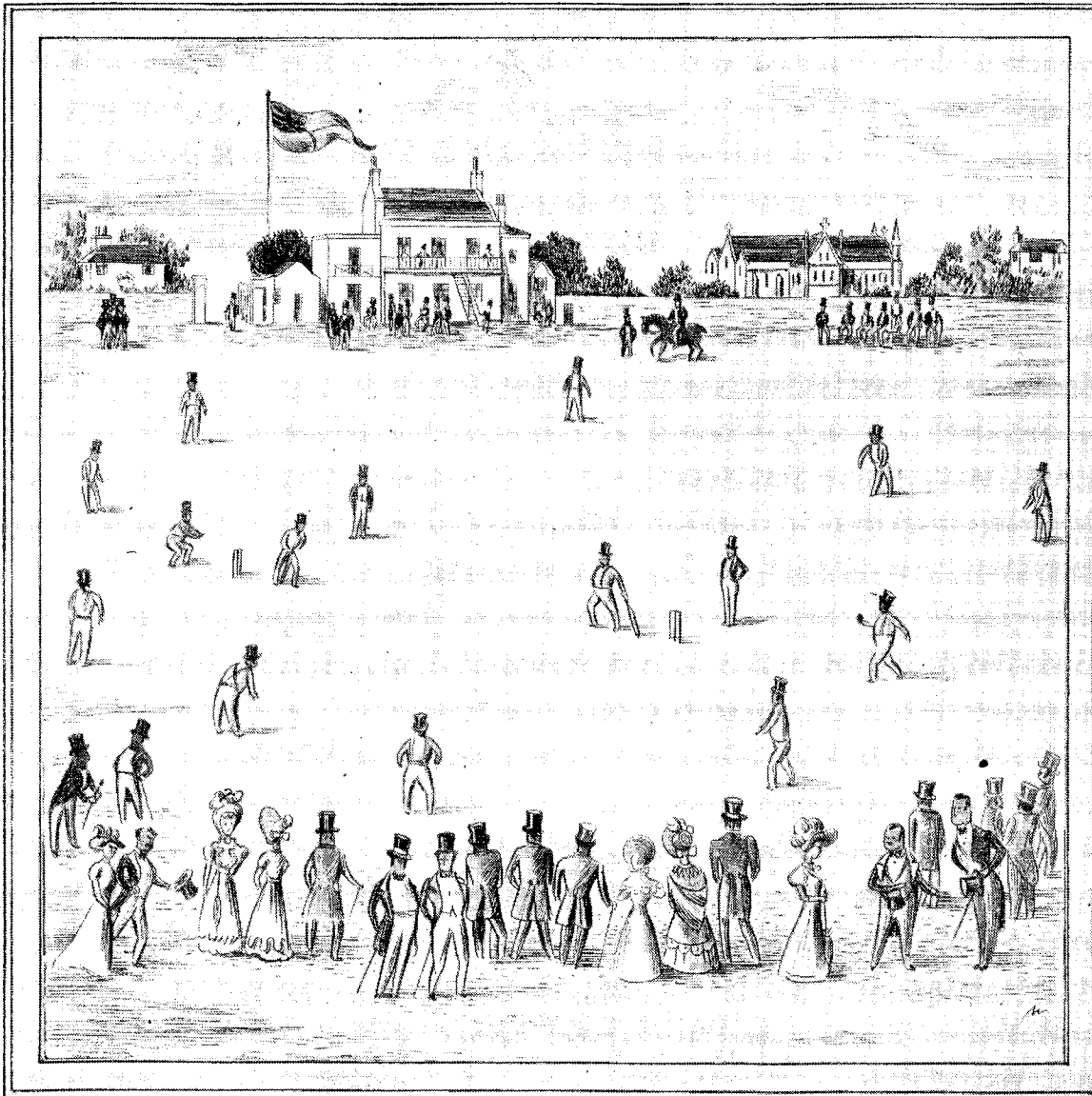**THE ERSKINE
LABORATORIES LTD.**
PROSPECT WORKS NORTH STREET
SCALBY, SCARBOROUGH



THERE WILL ALWAYS BE AN ENGLAND

The cricket match, the rolling countryside, the bustling city streets and a free unfettered life—that is our own immortal England. That is the tradition we have built. That is the tradition we are determined shall remain—forever. And in business?—honest trading, quality above all, a contented team of workers, a promise made and kept—that is the tradition of Dubilier. That is the tradition we are equally determined shall remain through all the trials and troubles we are bound to face.

DUBILIER

DUBILIER CONDENSER CO. (1925) LTD., DUCON WORKS, VICTORIA ROAD, NORTH ACTON, LONDON, W.3

C. R. Casson 156

Single - dial Band Spread

SHORT-WAVE RECEPTION SIMPLIFIED BY NEW SYSTEM OF TUNING

BEFORE describing the system of band spread tuning that forms the subject of this article, it might be advisable to explain what band spread is and why it is sometimes used for short-wave reception. This seems all the more necessary as it does not figure in ordinary broadcast reception, so that newcomers to the short waves may not, therefore, be familiar with it.

Briefly, it is a system for simplifying tuning, and is not used for normal broadcast reception, as on these wavelengths a good slow-motion condenser drive gives all the assistance needed.

Now the medium wave band in an average broadcast receiver has a range of 200 to 550 metres approximately, while a long-wave coverage of 800 to 2,200 metres is not uncommon.

Metres are awkward units in which to deal when explaining matters relating to tuning, especially when we come to band spread and short waves. Their corresponding frequencies in kilocycles or megacycles are much more convenient and lead to a better understanding of the prevailing conditions. In these units the medium wave band becomes 1,500 to 550 kc/s, while the long wave band represents 375 to 135 kc/s. The medium wave band, therefore, covers a range of 950 kc/s, but in the other extends only over a range of 240 kc/s.

As a broadcast station requires between 7,000 and 10,000 cycles (7 to 10 kc/s) in order to transmit speech and music with reasonable fidelity, there is room for 100 stations in the medium band, but space for 27 only in the long. Since the same condenser is used on both wave bands, we might expect to find a station at every gradation of an 0-100 division dial in the one case, but in the other every station spreading over three and a half to four divisions. In-

centally, this explains why tuning on the medium wave band appears to be so much more critical than on the long.

Now let us examine the short waves and, for explanatory purposes, assume that the same size of tuning condenser is used. Actually, this is not a merely hypothetical case, as in many all-wave receivers this condition does obtain. Furthermore, a single short-wave range is not uncommon, and this may cover 19 to 50 metres.

Here, again, metres are deceptive, since the 31 metres in the band represents a coverage in kilocycles of 9,800, giving other space for over a thousand broadcast stations. Actual figures are 15,800 kc/s to 6,000 kc/s. It need hardly be said that tuning on this short-wave band will be ten times more


critical than on the medium wave band.

Let us now examine the case from an angle more favourable to the short-wave receiver or converter, as it was for a short-wave converter that the band-spread system to be discussed here was originally evolved. It is customary to limit the capacity of the tuning condensers to 100 m-mfd. in order to obtain a reasonable coverage on each range, and avoid having to use a multiplicity of coils.

If each short-wave range had the same frequency

coverage as our medium wave band, we should need 17 ranges to tune from 13 to 50 metres, which is, of course, quite impracticable. With a 100-m-mfd. condenser this portion of the short waves can be covered in two steps. This frequency range is essential in order to take in all the short-wave broadcast bands, but coverage in two ranges means that each is over 8,000 kc/s wide. Tuning will still be far more critical than one would like.

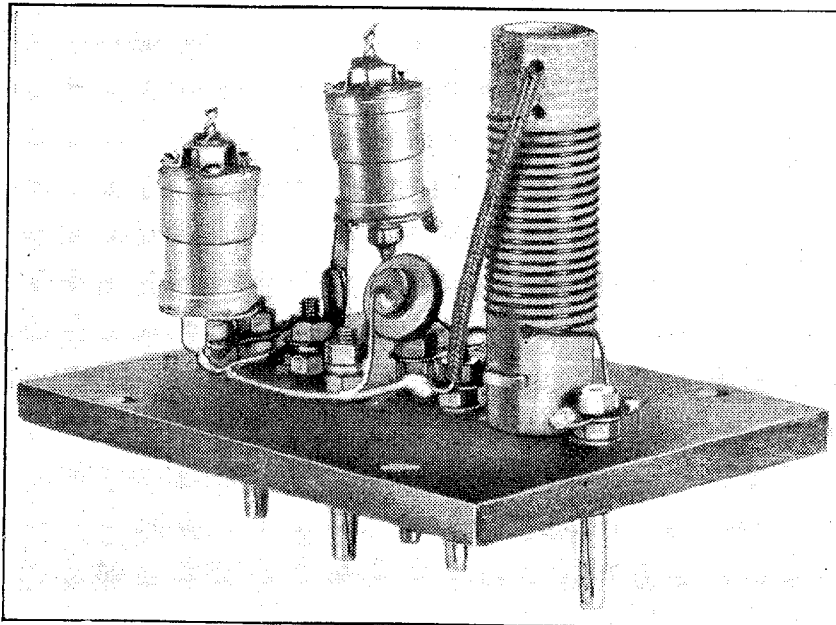Short-wave reception nowadays calls for a tuning system that can be adjusted with certainty to the setting corresponding to the desired stations. Most band spread systems fall short in this respect, but the method described in this article has the advantage of allowing unambiguous "logging" of stations.



Plug-in coil condenser unit (with cover removed) for use with the system of band-spreading described in this article.

Single-dial Band Spread—

What is the alternative to a multiplicity of bands? In the first place, we might ignore everything but the six broadcast bands which are in the vicinity of 13, 16, 19, 25, 31 and 49 metres. We could pair these and build a set with three ranges having a coverage of 13 to 17, 19 to 26, and 31 to 50 metres respectively. The first will have a frequency coverage of 23 to 17.6 Mc/s, the second one of 15.8 to 11.5 Mc/s, and the third will extend from 9.7 to 6 Mc/s. Tuning will be tolerably easy.

The alternative to this scheme is to retain the complete coverage, taking in all and sundry services, but arrange to expand just those portions of the spectrum allocated to broadcasting by using the full range of a small subsidiary tuning condenser. This is the customary system of band spreading. Note that it requires a main tuning condenser of not less than 100 m-mfds., and another variable having about one-tenth this capacity, the smaller being joined, as a rule, in parallel with the larger. A variation of this idea takes the form of connecting the band-spread condenser across a portion and not the whole of the tuning coil.

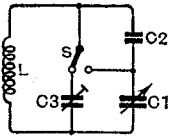


Fig. 1.—Normal tuning or band spread at will is obtained without an additional variable condenser by using this circuit.

The main drawback to either of these schemes is that if one attempts to calibrate the band-spread unit for identification of stations, *precise* accuracy of adjustment of the mains tuning condenser is imperative on all occasions. Rotating the drive to bring the pointer to a mark on the scale will rarely satisfy this condition, and one ought to use a condenser in which is embodied some form of locating device which, of course, must have a number of positions if more than one region of the range is to be expanded.

Desire to obtain the advantages of full coverage on the 13- to 50-metre band, at the same time retaining the ability to "spread" any part of that band with absolute certainty of repetition of tuning settings, led to examination of the possibilities for inclusion in a short-wave converter of the circuit shown in Fig. 1. Its great attractiveness lies in the fact that only one variable condenser is required.

With switch S short-circuiting C₂, the coil L₁ is tuned in the usual way by condenser C₁ and the full coverage is obtained. Now to band-spread any part of this range S is moved to the other position and C₂ placed in series with C₁. As C₂ is a small condenser, the effective maximum capacity of C₁ is thus reduced, for if C₂ is 10 m-mfds., and C₁ is 100 m-mfds., C₁ and C₂ in series gives a maximum of about 9 m-mfds. only. The function of C₃, which is now joined in parallel with the coil, is to pre-tune the circuit to the frequency from which band spread is to commence.

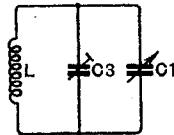


Fig. 2.—Fundamentally, the circuit of Fig. 1 under band-spread conditions of operation reduces to that shown here. C₁ is now a very small variable capacity having a relatively large fixed capacity, C₃, in parallel.

In simplified form, the circuit becomes as shown in Fig. 2, where C₃ is a large capacity in parallel with which is joined a very small variable condenser, here marked C₁.

As C₃ is a pre-set condenser, band spread will always commence at the same frequency, as it is not dependent on adjusting C₃ to what one hopes will be the right capacity every time expansion is required.

This arrangement would be ideal if only one band-spread region per range is used, but as the normal circuit will cover three or four short-wave broadcast bands it hardly serves our purpose. By a simple modification the system can be arranged to make available any number of expansion areas; all that is required is to fit a multi-way switch and include the desired number of band-set condensers. This seems an appropriate description for C₃ of Fig. 1; while we are coining terms, let us call C₂ the band-stop condenser. These modifications produced the circuit shown in Fig. 3.

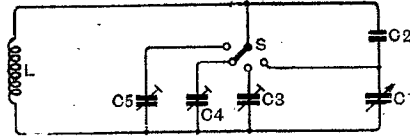


Fig. 3.—An extension of the circuit of Fig. 1 to enable band spread to be employed at three different parts of the range covered by a single coil.

Band-stop Condenser Capacity

Where tried in a converter the system came well up to expectations, and there was only one drawback, incidentally quite a minor one. Calculations of possible coverage with band spread had shown that the amount of expansion would vary at different parts of the short-wave spectrum, and in anticipation of this a double-pole multi-way switch had been fitted so that the band-stop condenser C₂ could also be changed. Not wishing to make the converter too complicated, provision was made for three changes in band-stop capacities, while three band-spread regions per range were considered sufficient for most practical purposes. With these additions the circuit becomes as shown in Fig. 4.

Small ceramic condensers are used in positions C₂, C₃ and C₄, while air-dielectric trimmers are fitted for C₅, C₆ and C₇; these may conveniently be mounted in a plug-in coil unit, the switch and band-stop condensers being embodied in the converter. It will thus be realised that while separate band-set condensers can be used for each expanded region on every range, the three band-stop condensers have to suffice for all the ranges to be covered.

A compromise is necessary, and it is suggested that

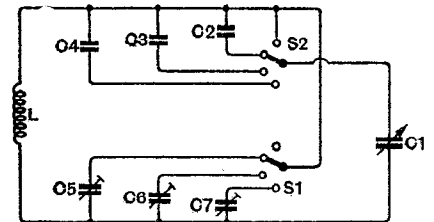


Fig. 4.—By including another switch S₂ and separate series condensers, each having a different capacity, the amount of expansion can be varied for different sub-bands.

Single-dial Band Spread—

capacities be chosen to give the most convenient band spread on the lowest frequency ranges. The coverage will be greater than necessary on the higher frequencies,

cast bands 13-, 16-, 19- and 25-metre ones are included, one of these four will have to do without expansion. All four could be band-spread by fitting six-pin boxes and a five-way switch, but a suitable switch-plate was not available at the time, and in any case spreading is hardly necessary on the lower frequencies.

Space is saved by fitting one of the wafer-type plate switches, sometimes called the Yaxley pattern, that used being a two-pole four-way one.

Band-stop condensers of 5, 10 and 20 m-mfds. were fitted for C8, C9 and C10 respectively. With the 13- to 30-metre coil unit a band width of just over 2 Mc/s is obtained on 13, 16 and 19 metres, which are the three where band spread is used. While admittedly a wider band spread than the needs of broadcast reception dic-

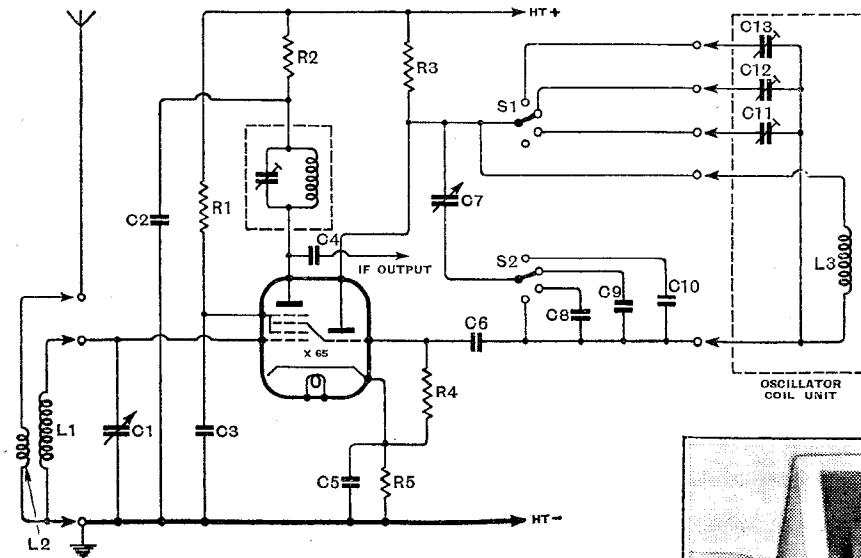


Fig. 5.—Complete circuit of a short-wave converter embodying an oscillator circuit with band spreading on the system described. Plug-in coils are employed. Values of components: C1, 100 m-mfds. variable; C2, 0.1 mfd. tubular; C3, 0.1 mfd. tubular; C4, 5 m-mfds. ceramic; C5, 0.1 mfd. tubular; C6, 100 m-mfds. mica; C7, 100 m-mfds. variable; C8, 5 micro-mfds. ceramic; C9, 10 m-mfds. ceramic; C10, 20 m-mfds. ceramic; C11, 3-30 m-mfds. air trimmer; C12, 3-30 m-mfds. air trimmer; C13, 3-30 m-mfds. air trimmer; R1, 35,000 ohms 1 watt; R2, 1,000 ohms ½ watt; R3, 30,000 ohms 1 watt; R4, 100,000 ohms ½ watt; R5, 300 ohms ½ watt.

but, even so, tuning will be child's play compared with what it would be without this simplification.


Having explained the basic principles of this band-spread system, perhaps a brief description of one way of applying the idea to a practical case might be of some interest.

As already mentioned, the system was first tried out in a converter. This was designed for use with *The Wireless World* 2RF set. Plug-in coils were employed, so that an extensive wave band could be covered if required, although, so far, only the 13- to 60-metre portion has been catered for. Extra coils can easily be constructed whenever required for any waveband. In view of this, ganging was not attempted, signal and oscillator circuits being tuned separately.

Design for a Converter

The theoretical circuit is given in Fig. 5, from which it will be seen that band spread is used in the oscillator only as the relatively flat tuning of signal circuits makes it quite unnecessary to use band spread in these cases.

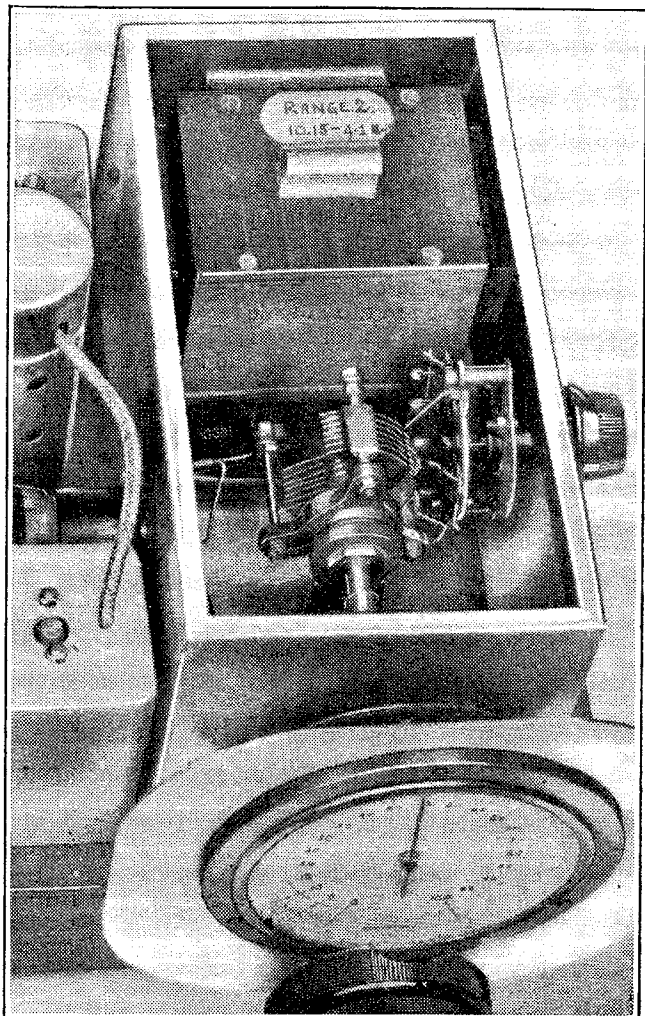The oscillator coil L3, together with three band-set condensers C11, C12 and C13, are assembled in a small coil box to which is fitted five pins. As Range 1 coil box covers 13 to 30 metres, the four short-wave broad-



This photograph shows part of a short-wave converter using the band-spread system described. Constructional details will be published in next month's issue.

Single-dial Band Spread—

tates, it served the writer's purpose, especially as the 20-metre amateur waveband is also covered when band spread is used on 19 metres.

There is no RF stage in this converter, but by using a relatively high intermediate frequency, 1,000 kc/s to be precise, very little trouble has so far been encountered from image-signal interference.

In Fig. 5, only the essential features are shown; for example, it omits the extra IF amplifier that was found desirable in order to improve the sensitivity, and incidentally the selectivity, of the 2RF set on the short waves. With this addition the whole outfit compares very favourably with many far more ambitious sets that have at different times been used for short-wave reception.

Some modifications have had to be made to the original 2RF set, as some trouble was experienced from instability with three amplifying stages tuned to 1,000 kc/s. A reasonable amount of decoupling, however, put an end to this difficulty.

Henry Farrad's Solution

(See Page 123)

MARK LINYER does not mention which valve tag he tapped in error, but assuming anything approaching normal conditions the only connection that would give a voltage of the order mentioned must have been anode (or possibly screen) to control grid. The Avometer, as is well known, takes 6 mA at full scale reading, and therefore on the 600-volt range its resistance is 0.1 megohm. This would virtually connect the control grid to +HT, causing it to take a considerable current and so to drop to a lower voltage because of the resistance of the meter. Even so, it would be positive, and the anode current would be grossly excessive, causing a considerable voltage drop in the output transformer. Altogether, the valve would be very badly treated, and as apparently it was kept in this condition for a considerable time it is not surprising that it was unfit for further use when the error was noticed. In checking the elimination of the first fault, a more serious one had been introduced. The moral is to take care when connecting meters to valve bases.

Taylor Model 45 Valve Tester

A VERSATILE AND UP-TO-DATE INSTRUMENT


THE first essential of a valve tester is that it should be comprehensive, and in this respect the Taylor 45 answers all present and some future requirements. It is fitted with seventeen valve holders suitable for British, Continental and American receiving valves, including Mullard side contact, midget deaf aid valves. American octal, loctal and bantam bases. With an eye no doubt to the future, we find that mutual conductances up to 24 MA/volt have been provided for.

Normally, the range is up to 12 mA/volt and the meter can be used to read the mutual conductance direct or to indicate whether the emission is good or bad compared with the maker's figure.

One of the most attractive features of this instrument is the provision for initial testing of filament continuity, and electrode shorts. These can all be carried out with the valve plugged into its holder before meter readings are taken. Three selector switches are provided for adapting the circuit to the type of valve under test and with these in the zero position a pilot lamp indicates that the filament is continuous when the main selector is set to the appropriate position. With the main selector turned to "Element Shorts" each electrode can be tested in succession, and any short circuit will be indicated by the lighting of the test lamp.

Frequency changers can be tested in each of their sections and diodes and rectifiers checked for emission. There is also a test for heater-cathode insulation with a scale reading up to 10 megohms.

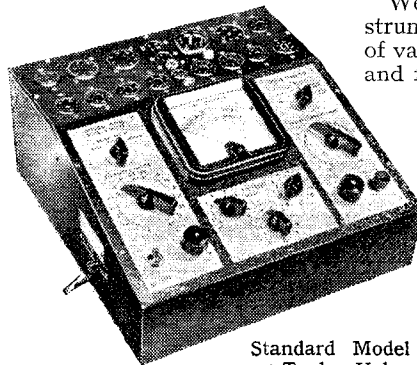A clearly written instruction manual and a list of over a thousand valves with full details for setting the controls and checking mutual conductance or emission is supplied with each instrument.



Standard Model
45 Taylor Valve
Tester.

We have tested the instrument with a number of valves of different types and found the readings in agreement with those taken by other methods. The controls are well arranged and clearly marked, and the switch location is positive. A press-button meter switch is a useful feature which may save the meter in case of errors in the setting of the other controls.

In every way it is a thoroughly up-to-date and practical instrument which can be recommended to servicemen and dealers.

The price of the standard model illustrated is £13 2s. 6d. A portable model fitted in an attaché case measuring 18in. x 13in x 6in. with space for tools costs £13 8s. and a bench model with flush mounting panel is available at £13 13s. The makers are Taylor Electrical Instruments, Ltd., 45, Fouberts Place, London, W.1.

"The Wireless Engineer"

A REGULAR monthly feature of our sister journal, *The Wireless Engineer*, is the Abstracts and References section compiled by the Radio Research Board. In this section are given abstracts of articles on wireless and allied subjects published in the world's technical Press. An index to the year's Abstracts, which in 1939 numbered over 4,800, was included in the December issue. A summary of recently accepted wireless patent specifications is also given each month.

The January issue, published on the first of the month, includes articles on the performance of non-linear circuits, the input capacity of a triode oscillator valve and details of a power oscillator for surface hardening of steel.

The Wireless Engineer is obtainable through newsagents or from the Publishers, Dorset House, Stamford Street, London, S.E.1, price 2s. 8d., post free.

G. E. C. High Tension Batteries

The General Electric Company announce that they are reducing the number of types of high-tension batteries and have decided to concentrate, for the time being, on the "Black Label" and "Blue Label" series.

Reaction Refinements

EFFECTS OF THE AERIAL, RF AMPLIFIER AND AF LOAD

This, the last of a short series of three articles, in which the problems of reaction are examined in the light of modern knowledge, deals with the problem of threshold howl as well as a number of miscellaneous matters which influence the functioning of the detector circuit.

IN last month's issue the effects of the valve and its applied voltages were discussed. It is also found that the circuit constants exercise an effect upon the smoothness of reaction, although it is normally much smaller than the valve conditions. In general, the amount of feed-back used should be small. It is often better to couple the valve loosely to the circuit and to use a normal screen or anode voltage than to couple it tightly and employ a very low voltage.

In the case of the Colpitts circuit of Fig. 3 of last month's article, the initial conditions can be controlled by C_1 , C_2 , C_{gc} , or by a condenser inserted at X. A small value for C_2 or a large one for C_{gc} makes for smooth reaction, but unfortunately reduces signal strength. Excessive capacity for C_1 tends to make regeneration plospy, but is better from the point of view of the signal strength.

What happens can be seen more clearly from Fig. 1, in which C_x represents the condenser referred to above as inserted at X (see Fig. 3 of "Smooth Reaction"). First imagine C_2 and C_x so large that they can be ignored. The incoming signal is developed across C, but the whole of it is not applied to the valve between grid and cathode, but only the fraction $C_1/(C_1 + C_{gc})$. Clearly, the larger C_1 is compared with C_{gc} the more nearly does the voltage applied to the valve equal that across C. The use of a large value for the ratio C_1/C_{gc} , however, does not lead to smooth reaction; the attainment of this desirable result, in fact, demands a small value for the ratio, which is bad for signal strength.

When C_2 and C_x are small, the fraction of the voltage applied to the valve is approximately $1/(1 + C_{gc}/C_1 + C_{gc}/C_2 + C_{gc}/C_x)$. For a given value of C_{gc} , a reduction in the capacity of C_1 , C_2 or C_x reduces the signal on the valve, but improves the smoothness of reaction. It does not matter much which capacity is varied, but as C_1 can rarely be reduced, since it consists of stray and valve capacity, it is better

in practice to reduce C_2 or C_x than to increase C_{gc} . This is because it leads to a lower input capacity.

From the point of view of signal strength both the Colpitts and Hartley circuits are inferior to others, because only a part of the voltage developed across the tuned circuit is applied between grid and cathode of the valve. In spite of this the Colpitts, in particular, has much to recommend it. It has fewer possible modes of oscillation than most other circuits and is, consequently, much freer from parasitic oscillation. It demands a single untapped winding for the tuning coil, which greatly facilitates both design and waveband switching. Finally, the regeneration control can be arranged to exercise unusually little effect upon the tuning.

In all the circuits shown so far the aerial is coupled to the tuned circuit by means of a small coil. There is little doubt that this is the best method of coupling to adopt unless an RF stage is used. In common with all other methods of aerial coupling, however, it is by no means straightforward.

The trouble lies in the aerial itself, for it is not a simple non-resonant structure, but is complex, with many different resonant frequencies. With a plain vertical wire aerial, series resonance occurs at wavelengths corresponding to $4, 4/3, 4/5, 4/7, 4/9, 4/11$, and so on, of the length, and parallel resonance at $2, 1, 2/3, 1/2, 2/5$, and so on, of the length.

A normal length of wire might be 20 metres (rather more than 60ft.) giving series resonance at about 80, 27, 16, 11.4, 9, 7.3 metres and parallel resonance at 40, 20, 13, 10, 8 metres.

If a fixed aerial coupling is used it will be found that around the parallel resonances the set oscillates unusually freely and near the series resonances much less freely than usual. The loading of the aerial on the tuned

circuit depends on the coupling and the aerial impedance. When the impedance decreases near a series resonance point the loading increases and more feed-back has to


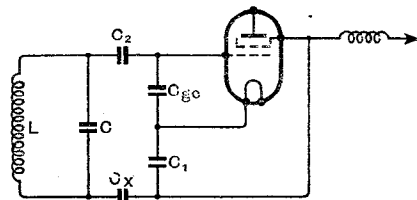


Fig. 1.—This diagram illustrates the effect of the various capacities in the Colpitts circuit.

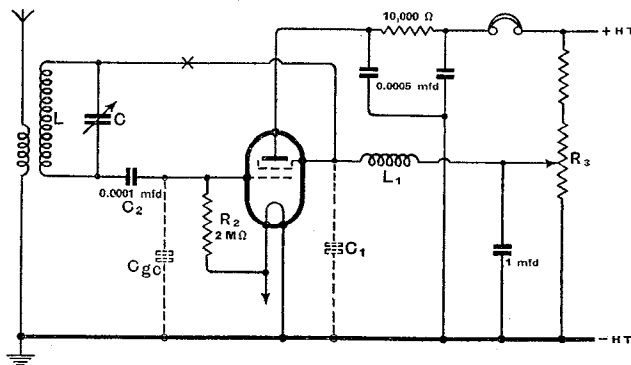

This diagram (Fig. 3 of last month's article on "Smooth Reaction") shows a Colpitts circuit for a battery valve.

Reaction Refinements—

be used to make the valve oscillate. Near parallel resonance the impedance is high and the loading on the tuned circuit low, so that the valve can oscillate readily.

What is needed is variable aerial coupling. This is not always easy to arrange mechanically, and greatly increases the difficulty of operation. Any change in the aerial coupling alters the tuning and reaction, so that the three controls are critically interdependent.

The usual practice is to employ fixed coupling, and arrange it so that it is slightly greater than optimum at the point of series resonance. This gives quite good results on the whole; the regeneration needed varies somewhat throughout the band, but not too badly. The greatest drawback is a loss of signal strength near parallel resonance, where the coupling is less than optimum.

The difficulty is best got over by providing another valve to act as an RF stage. This can have an aperiodic grid circuit, so that it does not complicate the tuning. A tuned grid circuit gives better signal strength, but is more complicated and expensive, and the difficulty of aerial coupling to this new circuit arises. As reaction is not applied to it, however, the difficulty is not nearly as great, but it is still sufficient to make ganging troublesome.

The use of an RF stage has one other advantage, which is so great that it makes its use almost obligatory. It very largely prevents the possibility of radiation from the aerial. With the aerial coupled directly to the tuned circuit of the detector, serious radiation occurs whenever the valve oscillates. A short-wave set is usually used a good deal in the oscillating condition, and so very serious interference with other receivers may be caused.

The RF stage acts as a buffer between the oscillating circuit and the aerial, provided that reasonable screening is adopted, and so removes this trouble. It is probably more efficient in this respect when its grid circuit is aperiodic than when it is tuned, for RF voltages are then much less likely to be picked up on the grid.

Appreciable Gain

The valve is by no means wasted, from the point of view of signal strength, for it can usually be made to give appreciable gain. With an aperiodic grid circuit, however, precautions must be taken against cross-modulation from a powerful medium-wave local station. The arrangement shown in Fig. 2 will usually prevent this trouble. L_1 and L_2 are short-wave RF chokes. L_2 should be a good one, since it comes in parallel with the tuned circuit of the detector. L_1 is much less important, and should not be of too high an inductance. It is particularly important that it should not resonate with the aerial capacity near the medium waveband.

This arrangement may not prove adequate when the local station gives a very strong signal, and it is then

necessary to include a wavetrap in the aerial lead. This will effectively prevent the trouble.

The use of a tuned circuit, however, gives a considerable improvement in sensitivity. The tuning is quite flat, so that only rough ganging to the intervalve circuit will suffice. This is not always easy, however, because with some circuits neither side of the intervalve tuning condenser can be earthed. Actually, the use of a separate tuning control for the aerial circuit complicates the operation very little, and is to be recommended.

It is usually sufficient to tune the aerial circuit to the middle of one of the broadcast bands, and leave it there while the band is explored. For example, if reception is wanted in the 19-metre band, the aerial tuning control can be set for this band and then forgotten.

So far, nothing has been said about the AF output circuit. A load impedance effective at audio-frequency is essential in the anode circuit in order to make use of the output, and it can seriously effect the operation of reaction if it is not correctly arranged. The impedance is normally an inductance or capacity in shunt with a resistance. The former occurs when the load is a pair of phones, a transformer, or a choke, and the latter with resistance coupling. In this latter case the capacitive element comes in through stray and valve capacities; there is also usually an RF by-pass condenser across the coupling resistance.

With an unsuitable load threshold howl is liable to occur. Instead of the valve sliding smoothly and quietly into oscillation, an audio-frequency howl or growl is set up when the valve is just oscillating. It is a very annoying defect, because it manifests itself just at the point of regeneration which is very frequently used, and it is consequently essential to eliminate it.

The first step towards removing it is to understand its cause. Consider a grid detector with an inductive anode circuit load impedance. When the valve begins to oscillate, a large RF voltage is developed on the grid, and through grid rectification the mean grid potential changes in a negative direction. This causes a fall in anode current, and the change in anode current through the anode circuit inductance sets up a back-EMF across it in such a direction as to oppose the change of current. The back-EMF thus acts to increase the anode voltage, and so makes the valve develop a larger amplitude of RF voltage on the grid. This makes the grid potential still more negative, giving rise to a further drop in anode current, and so on.

At length the process slows up and stops; the anode current reaches a minimum, and the back-EMF disappears. The anode voltage is then too low to maintain the RF amplitude, which accordingly falls, making the grid less negative. The anode current rises, and a back-EMF again appears across the anode inductance, but this time in the opposite sense, reducing the effective anode voltage and so still further reducing the RF ampli-

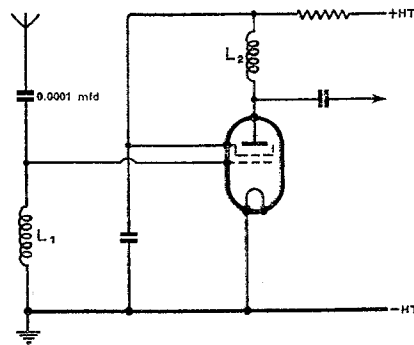


Fig. 2.—The circuit of an RF stage which can be used to precede any of the detectors shown. The aerial circuit is untuned.

Reaction Refinements—

tude. This process continues indefinitely, and the changes of anode current occurring at an audible rate give rise to the howl.

Conditions for howling are worst with efficient detecting action in the grid circuit, a valve of high mutual conductance, and a high value of inductance for the load circuit. The trouble cannot occur with resistance-capacity coupling and grid detection. On the other hand, if the valve functions as an anode bend detector, it occurs with resistance-capacity coupling, but not with an inductive load.

With a triode as grid detector and an inductive load, the only remedy is to shunt the inductance with a resistance. As the resistance is reduced in value, conditions get better and better, and finally threshold howl ceases.

Tetrode or Pentode Valves

In the writer's experience, however, a better remedy is to use a screened tetrode or pentode valve in a suitable circuit. Over a large range of voltages the anode current with such valves is substantially independent of anode voltage. Consequently, the initial rise of anode voltage, due to the back-EMF across the inductance, does not appreciably increase the RF amplitude, and the conditions necessary for provoking threshold howl do not arise.

With a very large inductance of several hundred

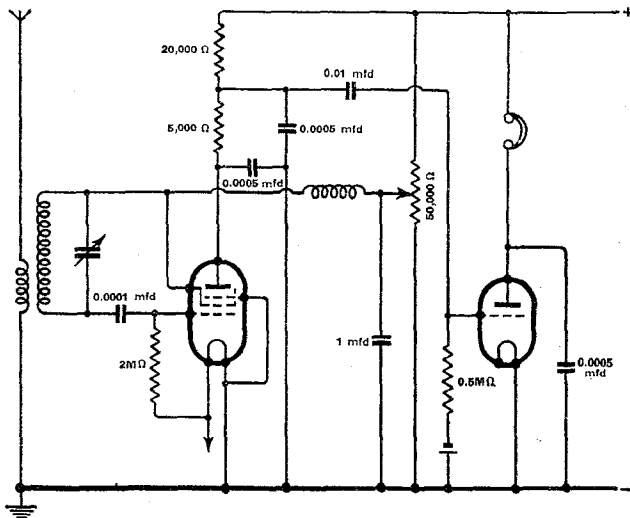


Fig. 3.—This diagram shows an AF stage following the detector and is an arrangement which is very satisfactory in practice.

henrys, such as might be used with choke coupling, trouble may still be experienced, but with phones it is normally completely absent. Even with the comparatively low inductance of phones, threshold howl is liable to occur when a triode is employed.

Resistance-capacity coupling avoids the trouble completely, but is not always easy with a screened tetrode or pentode. A high value of coupling resistance is needed for high gain, and, on account of the voltage drop in it, a low screen voltage is required. The screen voltage is

fairly critical for good AF amplification, with the result that it is often inadvisable to vary it as a regeneration control. Further, with the low screen voltage, the mutual conductance is likely to be below normal, and difficulty may be experienced in obtaining oscillation.

Incidentally, when phones are used immediately after the detector, they can only be inserted directly in the anode circuit when a triode is used. With a screened tetrode or pentode a step-down transformer or auto-transformer is necessary if the full advantage of the valve is to be secured. Even ordinary high-resistance phones are of too low impedance to match a pentode, and a transformer ratio of the order of 5-1 is necessary. It is not critical, however, and a ratio of between 4-1 and 6-1 is normally satisfactory. This naturally leads to a higher value of inductive load on the valve, but in the writer's experience does not cause trouble from threshold howl.

When the detector is followed by an AF amplifier it is usually advisable to employ resistance coupling. Even with a tetrode or pentode detector it is difficult to avoid threshold howl when using a transformer. Two RC stages following the detector give more gain than one with transformer coupling, and are simpler and little more costly. As already pointed out, RC coupling has its difficulties with a pentode, but it will be found very satisfactory if the coupling resistance is kept fairly low in value, say, 20,000 ohms. Of course, if an abnormally high voltage supply is available, it can be made larger.

It is always more difficult to avoid threshold howl when an AF amplifier is used than when the phones are in the detector circuit. This is because the presence of RF currents in the AF circuits greatly accentuates any tendency to such howling. In fact, it can occur when nothing but RC coupling is used. The mechanism involved is then different from that described earlier, but the remedy is to keep RF currents out of the AF circuits as far as possible.

An arrangement which has been found very satisfactory for phones is shown in Fig. 3. For use with a loud speaker a pentode output valve RC coupled to the output of the triode is quite good, although care must be taken to avoid microphony. Among many others, a suitable detector valve is the Mazda SP210, while an HL2 can be used for the AF stage.

New Osram Valves

TWO-VOLT VALVES WITH REDUCED FILAMENT CURRENT

THREE new types have just been introduced in the range of valves designed for use with 2-volt accumulators. They are the X24, HD24 and KT24.

The X24 replaces the earlier X23 and has the same characteristics as the latter with a filament consumption of 0.2 amp. compared with the 0.3 amp. of the X23.

Type HD24 is intended to replace the three double-diode-triodes HD21, HD22 and HD23. Its filament consumption is 0.1 amp. and the triode section has an AC resistance of 28,600 ohms and a mutual conductance of 1.4 mA/volt.

Finally, the KT24 which has been introduced as an alternative to the KT21 has a filament consumption of 0.2 amp. instead of 0.3 amp. and a mutual conductance of 3.2 mA/volt compared with 5.3 mA/volt in the KT21.

Bush Model PB63

AC SUPERHETERODYNE (FIVE-VALVE + RECTIFIER) PERMEABILITY TUNED PUSH-BUTTON CIRCUITS. PRICE 12½ GUINEAS

THIS receiver occupies an intermediate position in the current range of table model receivers, and includes most of the features which characterise this season's Bush sets—a lively short-wave performance, stable push-button tuning circuits and a triode in the output stage for good quality of reproduction.

Circuit.—Three aerial sockets are provided, one for maximum sensitivity, one for maximum selectivity and the third for reception close to a powerful station. The latter brings into circuit a filter to cut down the input to the frequency changer from the local station. An adjustment is provided on the back of the chassis and the range is approximately 255 to 400 metres. A pair of tags at the back of the chassis enable a voltmeter to be connected across the feed resistance to the IF valve in order that this adjustment may be made accurately.

There are ten control buttons, three for waverange on manual tuning, one for gramophone and six for selected stations, two on long waves and four on the medium-wave range. Adjustment of the aerial pre-set circuits is by capacity trimmers, and of the oscillator by variable iron-cored coils connected in parallel with the long-wave tuning inductance. To give the necessary coverage on long waves additional parallel capacity is introduced when the LW waverange switch is "out."

The first valve, a triode-hexode frequency changer, is controlled by AVC on medium and long waves, but not on short waves. The IF transformer in its anode circuit has two degrees of coupling con-


trolled by a single-pole switch. In one position, a common capacity is introduced in the low potential leads from the main tuning condensers on both primary and secondary to increase the coupling and the band width of the response curve. In the other position a capacity equal to that of the coupling condenser is connected in series with the secondary tuning capacity to preserve the symmetry of the circuits. Both IF transformers make use of fixed silvered mica condensers and are permeability tuned. The output secondary is tapped down for both signal and AVC diodes.

A delay voltage is derived from the cathode bias resistance of the double-diode-triode valve and AVC is applied to the IF stage on all wavebands. When using a pick-up, the radio side is silenced by earthing the screen of the IF valve.

As the output valve is a triode, an ad-

ditional stage of AF amplification has been included. Bias for the output stage is derived from a potential divider across the loud speaker field, which is connected in this receiver in the negative HT lead. The external loud speaker is connected to a switch-plug which enables any combination of internal and external loud speaker to be used.

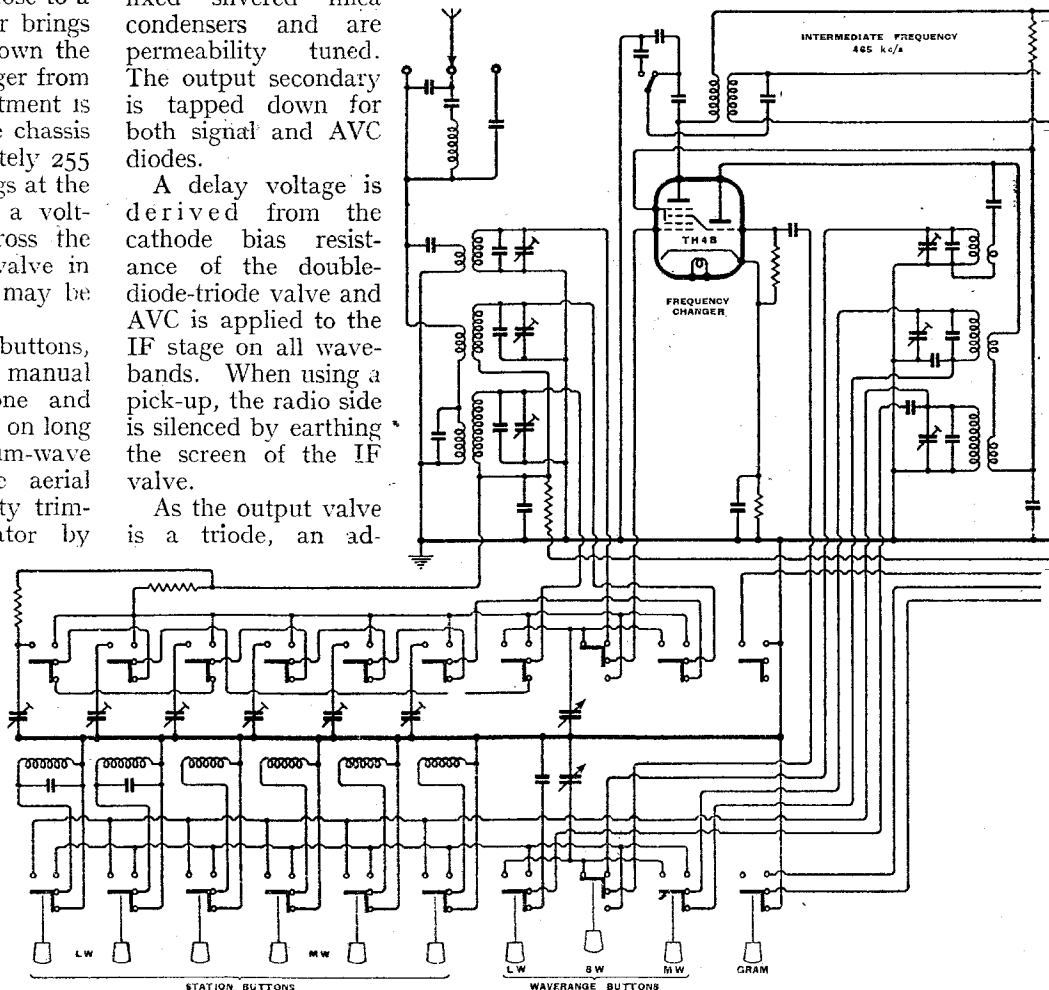Performance.—The maker's decision to return to the much neglected triode for the output stage




is amply rewarded by the quality of reproduction obtained. Not only is the quality at normal volume free from any trace of muzziness due to harmonic distortion, but it is also unspoil by any tendency to over-accentuation of the high frequencies as is often the case with pentodes. That is not to say that top is lacking; quite the contrary, for with the variable selectivity control in the position of normal selectivity the trial balance is just right and does not call for any adjustment of the tune control. The bass response is clean and goes down much farther than the average table model without any resonance which affects in any way the quality of speech. The loud speaker gives excellent transient response and from every point of view this set earns bonus marks for quality of reproduction.

The short-wave performance, too, is outstandingly good, and in spite of

of band spread tuning, the "Telefic" auxiliary dial enables station settings to be repeated with accuracy.

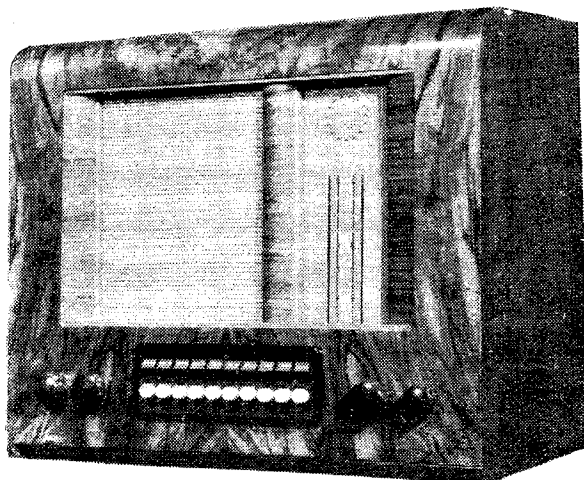On the medium- and long-wave ranges the sensitivity is high enough to bring in any station whose field strength is above the level of prevailing background noise, while the selectivity in the "high" posi-



WAVERANGES


Short 16.5 - 51 metres
 Medium .. 198 - 565 metres
 Long 850 - 2000 metres

slits illuminated generally by a single pilot lamp and circular reflector. Only one pair of slits coincide at a time and as the moving disc makes one sixteenth of a revolution the light appears to travel right round the dial. Thus a 16:1 increase in the ratio of the tuning drive is obtained optically without the complication of extra gearing.

The pre-tuned circuits may be adjusted from the front of the set after removing the moulded escutcheon plate, and a noteworthy refinement here is the provision of miniature wavelength scales alongside the adjusting screws for the cores of the oscillator coils.

From every point of view the PB63 is a well thought out design and both its appearance and performance entitle it to a high place among good quality receivers. The controls are positive and smooth in action and there is no requirement of modern reception—short-wave performance, quality, range and selectivity—which it does not fulfil in ample measure.

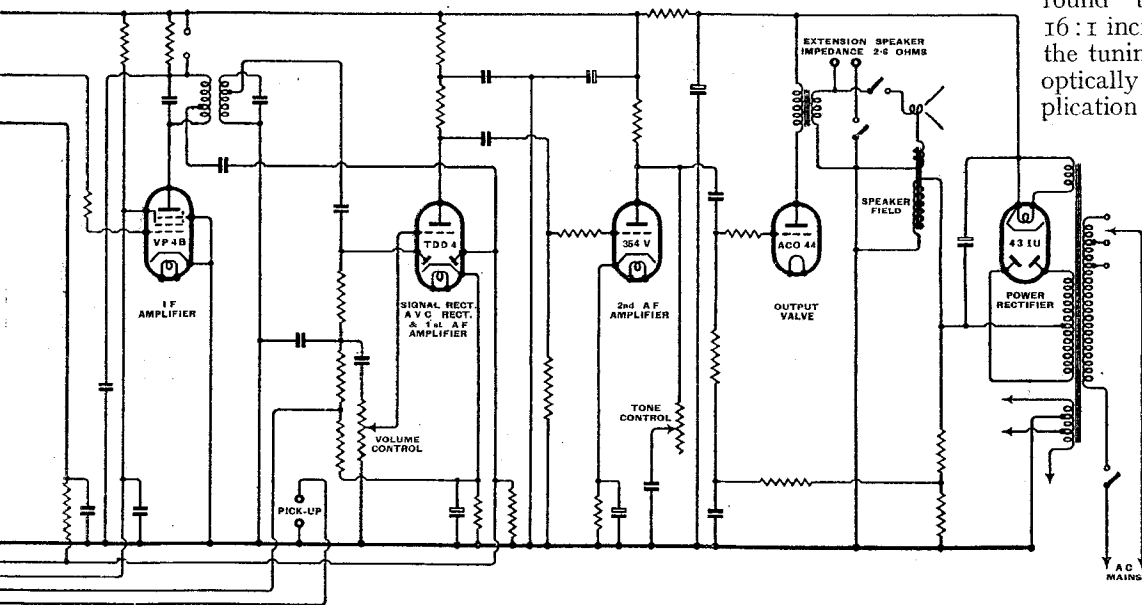Makers.—Bush Radio, Ltd., Power Rd., Chiswick, London, W.4.



Circuit diagram of the Bush PB63. The inductances in the pre-set oscillator circuits and the IF transformers have adjustable iron dust cores. Terminals are provided for a voltmeter in the anode circuit of the IF valve for adjusting the aerial filter.

adverse conditions over the Atlantic, reliable reception was obtained from the principal American stations. The short-wave oscillator circuits are stable and there is no noticeable frequency drift. Microphonic feed-back on strong carriers is absent and second-channel interference negligible. From the mechanical point of view, the tuning is smooth and precise and although there is no form

tion of the control is more than adequate for present reception conditions.

Constructional Features.—The "Telefic" dial is an auxiliary tuning scale for short waves. It consists of fifteen radial slits arranged in a circle and framed to look something like the dial on an automatic telephone. Behind these fixed slits is a revolving disc with sixteen radial

Current Topics

RECENT EVENTS
IN THE WORLD OF WIRELESS

AMERICAN TELEVISION

F.C.C. Report

THE Television Committee of the Federal Communications Commission has recommended that television stations should be permitted to broadcast a limited proportion of commercial programmes. Whilst the Committee hold that television is still highly experimental, the members feel that it has reached a crucial stage, but "extensive developments are yet to be accomplished before television receivers can be bought with the same assurances that go with the sale of an ordinary receiving set." Fewer than 1,000 receivers have been sold since May, 1939, when the N.B.C.'s New York station started regular transmissions.

It is announced in *Broadcasting* that the Committee has recommended the allocation of three channels to metropolitan districts with a population of over 1,000,000; two channels to those with a population between 500,000 and 1,000,000, and one channel to districts with fewer than 500,000 inhabitants. With this assignment of frequencies a maximum power of 10 kW is stipulated.

PLUG IN AND VIEW

Proposed Television Scheme

WHILST television in England is at a standstill, there are signs that it will go ahead with leaps and bounds in the United States. Whereas England had a two-year lead in the television field there is every reason to believe that if the war lasts for two or three years America would gain absolute supremacy both commercially and technically.

As is already known, transmissions from the London television station ceased on September 1st, for reasons of national defence. Mr. Sagall, managing director of Scopphony, Ltd., has submitted a memorandum to the Postmaster-General and the Television Advisory Committee urging them to consider the question of restarting television transmissions. He says: "If the objections of the Defence Authorities to the transmissions of television by radio are incontrovert-

◆ ◆ ◆
FOR THE B.E.F. One of the portable receivers provided by Lord Nuffield's gift of £50,000 from the Nuffield Fund for the Fighting Forces in use in a trench on the Western Front. These battery operated portables, which are made by several well-known manufacturers, are purchased by the N.A.A.F.I.
◆ ◆ ◆



Referring to the cessation of television development abroad, the report states: "An opportunity exists for American industry to construct foundations for a position in the world television market of the future by undertaking active steps at this time to further the technical and operating development of television in this country. This opportunity should not be lost."

FREQUENCY MODULATION

Success of Triple Relay Experiment

HAVING heard a demonstration programme that had been relayed three times by frequency-modulation stations, Mr. K. B. Warner, managing secretary of the American Radio Relay League, and editor of *QST*, said: "I thought it was just technically unbelievable with three relays, yet the programme was still better by far than the present conventional system at its best. In ten years there won't be any orthodox brand of broadcasting remaining except for the lowest grade of local service."

The demonstration programme, which included sounds requiring a high degree of fidelity to reproduce them, was broadcast by W2XCR at Yonkers, New York. It was received and rebroadcast by Major Armstrong's station W2XMN at Alpine, New Jersey. The transmission from W2XMN was received at Meriden, Conn., and again broadcast by W1XPW, which transmission was received in the studio of WDRC, Hartford, Conn., before those invited to hear the demonstration.

It was in order to prove the practicability of a chain of F-M stations that the demonstration was staged, for it is not possible to use cable links between F-M stations as they will not transmit a 15 kc/s band.

About 25 frequency-modulation transmitters, it is stated, will be in use by midsummer.

B.B.C. HOME SERVICE

Criticisms and a Compromise

THE B.B.C. Home Service was severely criticised at a recent meeting of the Radio Industry Luncheon Club, the members of which unanimously passed a resolution that: "While the meeting realises that certain shortcomings in the B.B.C. Home Service are due to measures taken to preserve the national security, it is felt that both the Ministry of Information and the B.B.C. should make clear to the public the fact that poor reception of the English programme is more often due to such emergency measures at the transmitting end than to the fact that listeners' receiving sets have broken down."

Criticisms of the poor and indifferent reception in many areas have also been voiced in the lay Press by dissatisfied listeners. In defence of the B.B.C. engineers, it must be said that it was known before the single-programme Home Service was put into operation that there would be many districts in which reception would be unsatisfactory, but the engineers were powerless to do anything with the system they were called upon to use.

It will be remembered that in November many listeners heard un-

announced musical items on the 342-metre wavelength, which until the war was used by London Regional. These transmissions proved to be from a B.B.C. transmitter, and a few days before Christmas the B.B.C. made the following announcement: "Listeners who find difficulty in receiving the Home programme on either of the two wavelengths, 391 or 449 metres, are advised to try after 6 p.m. any evening the 342-metre wavelength." Since January 7th this wavelength has been used each evening for the special B.E.F. programme.

There are, however, still districts in which reception of B.B.C. programmes is far from satisfactory, and listeners in these areas must have been gratified to hear Sir Adrian Boult say during his recent talk on music: "Our engineers are doing everything possible to devise some means of improvement within the drastic limits of power that are imposed on us by the necessity of wartime. I believe the new wavelength begun a fortnight ago has improved things already, and I want to assure you that tireless efforts are being made to get things better still."

RADIO RELAYS

Conditions of the New Licence

RADIO relay companies have now received the new agreement from the Postmaster-General authorising their operation for a period of ten years from December 31st, 1939. With this is introduced a new scale of fees payable to the Post Office calculated according to the number of subscribers served. Stations with fewer than 300 subscribers will pay £3 annually, those with more than 300 but fewer than 500 £5, while those with over 500 subscribers will pay £10. A separate licence of £1 per annum is still required for each stand-by receiver.

Although the general scheme for the connection of relay exchanges by line to B.B.C. studios, which the Postmaster-General mentioned in the House of Commons last March, has had to be postponed in view of the present heavy demand on Post Office lines, the reception of B.B.C. transmissions by wire is permitted under the terms of the new licence. No provision has been made for the compulsory linking of exchanges to B.B.C. studios, but the P.M.G. reserves the right to impose such a condition.

The distribution of programmes at

carrier frequencies and the use of an earth lead as a part of any circuit for programme transmission are prohibited. To avoid interference with Post Office communication services a minimum clearance of two feet from a Post Office line is specified for the distributing plant.

STANDARD I.F.

WITH a view to facilitating the standardisation of an intermediate frequency for superheterodyne receivers, the Australian Postmaster-General has circularised radio manufacturers in the Commonwealth with a proposal that the frequency of 455 kc/s be adopted. In the memorandum it is stated that unless the majority of manufacturers consider 455 kc/s as unfavourable, it is proposed to protect the band of frequencies between 450 and 460 kc/s by keeping important transmitters out of this band.

In 1937 the Federal Communications Commission of America adopted 455 kc/s as being most suitable for the intermediate frequency.

AUSTRALIA'S WORLD TRANSMISSIONS

Inauguration of International Service

A DAILY short-wave world news service broadcast by the Australian Broadcasting Commission was inaugurated by the Prime Minister of the Commonwealth on December 20th.

Transmission No. 1A, which is directed to central and northern Europe, is radiated from 7 to 9 a.m. (G.M.T.) on 9.615 Mc/s (31.2 metres), the call sign being VLQ. This transmission is at present given in English, French and German, but will later include Dutch, Russian and Norwegian. The principal English transmission is at 8.15 a.m. Transmissions for north and south America and India are radiated on the same frequency at various times between 11.30 a.m. and 4.30 p.m.

The transmission directed to southern Europe and the Balkan States, which at present is given in English and Spanish, but will later include Italian, Arabic and Turkish, is radiated from 7.30 to 8.30 a.m. from VLQ2 on 11.87 Mc/s (25 metres).

A new transmitter, VLW3, at Perth, was used on January 15th for the introduction of transmissions in English and Afrikaans to Africa on 11.83 Mc/s (25.36 metres).

Transmissions to the Dutch East Indies and Japan are radiated from VLR on 9.85 Mc/s (31.3 metres) and VLR3 on 11.88 Mc/s (25.25 metres).

"SENDER BREMEN"

THE German transmitter, working on 395.8 metres, which uses this identification, is situated at Oldenburg, close to the German-Dutch frontier, and about 30 miles from the North Sea. It will be remembered that this station suddenly made its appearance in July, 1939, no mention of it having been made by the German delegation at the Montreux wavelength conference.

In July, our Berlin correspondent reported that there seemed no reason for building this transmitter in a corner of Germany already well served by the local station Bremen unless its transmissions were intended for countries outside Germany. That this was the case has been amply borne out by recent events.

The station's published programmes are very interesting, for they entirely ignore German listeners. They are intended for England and Holland.

Although the power of Bremen has

Current Topics—

not been published, it is thought to be between 100 and 150 kW. Its aerial is directional on Great Britain. The original 2-kW Bremen transmitter continues to transmit on its wavelength of 225.6 metres under the name of Unterweser.

ECHOES OF RADIOLYMPIA

LT.-COL. G. D. OZANNE was given a gold cigarette case together with a piece of jewellery for his wife by members of the Radio Manufacturers' Association as a token of their appreciation of his untiring work in organising Radiolympia, 1939. The presentation was made at a recent luncheon during which the chairman, Mr. W. W. Burnham, revealed that the loss on Radiolympia, which it will be remembered closed prematurely, was between £12,000 and £13,000.

A.I.R.'S FOURTEENTH STATION

THE 5-kW transmitter of All-India Radio at Dacca, which was opened by His Excellency the Governor of Bengal on December 16th, is designed to give a first-rate, direct-ray service to cities within a radius of 50-100 miles of the station, as well as serving Eastern Bengal as a whole.

Working on 257.1 metres, the transmitter, which was erected by Marconi engineers six miles from the studios in Dacca, employs a mast-radiator aerial. Dacca is the ninth centre and the fourteenth transmitter to be erected under the present development scheme of A.I.R. It is proposed to establish a receiving station at Dacca for the purpose of relaying the news broadcast by the central news organisation at Delhi.

I.E.E. MEETINGS RESUMED

THE Council of the Institution of Electrical Engineers having reviewed the position regarding the activities of the Institution in the light of the present conditions, have, in response to the requests of members, announced that its activities will again be resumed. Meetings of the Institution in London will, therefore, be held during the second half of the present session. Activities in the provinces will be resumed when thought advisable by the various committees. All London meetings will be held from 6 to 8 p.m.

GERMANY'S RADIO INDUSTRY

A WELL-KNOWN German radio journal reports that the German radio industry has not only fulfilled its obligations for supplies to the war departments, but has increased its exports to nineteen neutral countries. No fewer than eleven types of AC and AC/DC receivers have been produced for export. The increased demand on the home market for sets at Christmas was also easily met. The previously reported rationalisation of sets, which will come into operation later in the year, will not affect the receivers built for export.

It would appear from the number of sets for home construction recently described in the German technical Press that this side of the industry is also flourishing.



ON THE WESTERN FRONT. A French soldier operating one of the many portable transmitter-receivers which are being used by the allied armies.

FROM ALL QUARTERS

Television Radio Link

GENERAL ELECTRIC engineers are experimenting with a television relay receiver near the Company's television transmitter W2XB on the Helderberg mountain, which is about twelve miles from Schenectady. It is proposed to pick up transmissions from the N.B.C.'s New York transmitter W2XBS, which is approximately 130 miles away, and then to rebroadcast them from W2XB.

Long Distance Broadcasting

SIR NOEL ASHBRIDGE, B.B.C. controller of engineering, will deliver a lecture on "Long Distance Broadcasting" at the Royal Institution, 21, Albemarle Street, London, W.1, on Friday, January 26th, at 5 p.m.

Germany's Jamming Station—Official

It is reported by *The Nottingham Evening Post* that the announcer from Deutschlandsender when reading a list of gifts to German troops recently read "two hundred marks from the jamming station at Stralsund."

American Radio Census

THE introduction of the question "Is there a radio in this dwelling unit?" on the schedule for the United States sixteenth Decennial Population Census, will provide the first accurate survey of receivers in the country.

Little Lawlessness

M. RAYMOND BRAILLARD, director of the U.I.R.'s Control Centre in Brussels, recently stated that with few exceptions countries are keeping to their allocated wavelengths.

Another N.Y. Television Station

APPLICATIONS to operate television transmitters continue to reach the Federal Communications Commission, and one of the most recent is for a 1-kW station in the centre of the Metropolitan area of New York City. It will operate in the 84-90-Mc/s band, a rather higher frequency than those already in use.

Byrd Antarctic Expedition

THREE call signs have been allocated to the Byrd Antarctic Expedition for use in the amateur bands. They are KC4USA, KC4USB and KC4USC.

Captain Plugge

At the last general meeting of the Parliamentary and Scientific Committee at the House of Commons, Captain L. F. Plugge, M.P., was elected chairman.

Belfast Wireless College

THE Caledonian Wireless College is to open a branch college in Belfast which will specialise in the training of marine wireless operators. It will be known as the Belfast Wireless College.

Philco's Chairman

MR. L. D. BENNETT, M.Sc., has been elected chairman of the Philco Radio and Television Corporation of Great Britain in succession to Mr. C. C. Rattey, who has resigned.

Wireless for the Blind

THE National Institute for the Blind has announced that more than £10,000 had been received by the end of the year in response to the Christmas Day broadcast appeal by "an unknown blind man" for the fund which provides and maintains wireless receivers in the homes of needy blind people.

Wireless World Diary

COPIES of *The Wireless World Diary* for 1940 are still available from our publishers, Iliffe and Sons, Dorset House, Stamford Street, London, S.E.1. In addition to the usual features of a diary it contains technical data and reference sections compiled by the staff of this journal. Copies cost 1s. 6d., or, by post, 1s. 7d.

Getting the Best from Records

Part 1.— THE RECORDING CHARACTERISTIC

By P. G. A. H. VOIGT, B.Sc., A.M.I.E.E.

ONLY too often, the feeling of scorn with which radio engineers regard record reproduction is due to the fact that they have never seriously tried to get the best out of records and have therefore never discovered how good modern records can be. No doubt the idea that records cut off at 5,000 c/s is largely responsible, and while this was certainly true of some of the early electric recordings, the commercial recording system which cuts off at such a low frequency is nowadays the exception rather than the rule.

The B.B.C. cannot always satisfy our requirements, so there is much to be said in favour of records, when correctly reproduced. Quite apart from the programme point of view, however, no quality enthusiast should consider his equipment complete until he is able to obtain from the best records a quality of reproduction which is only excelled by the very finest of broadcasts.

This is not merely a matter of connecting up a pick-up and enjoying a record, as most people imagine. The question of pick-up actually introduces several problems which challenge the technical ability of both the quality lover and pick-up designer.

The usual starting point in such matters is the characteristic curve, but, as Mr. Scroggie said in a recent article,* "it is difficult to get authentic information about the characteristics of records." This is a point which must be clarified before we can proceed.

In the days of horn recording, progress was based on laborious hit-and-miss methods, so that all information about the details became the most jealously guarded secrets. This tradition of secrecy is probably responsible for the absence of information deplored by Mr. Scroggie. Readers may therefore be interested to learn the factors which determined the basic characteristics of a recording system upon the development of which I was engaged for several years from about 1923.

When the problem first arose, little was known about electro-acoustics, and the distribution of energy within the audible spectrum was largely a matter of surmise, with a strong bias in favour of the idea that there was

extra energy at low frequencies. No doubt the visible motion of the diaphragm of a big drum contributed to this idea.

However, serious development could not be based on vague beliefs of this kind, no matter how widely held, and so I examined the matter from the only possible standpoint, namely, that of mechanical efficiency. It seemed, since the violin and the double bass are similar except as regards size, that their efficiency, when each is playing in its proper frequency spectrum, is also likely to be similar. The same applies to the piano, namely, if each note is hit with equal force, no great variation in sound output energy could be expected.

This latter was a fairly simple matter to check, providing a few things, particularly microphone characteristic, could be taken on trust. With regard to the microphone employed, this had a calculated response which would be level if the air cushion in it expanded and contracted adiabatically at all audible frequencies. If, however, the air worked isothermally, the response would still be level, but about 3 db higher up. At that time no information was available to show which way the air was working inside the microphone, or whether (as afterwards proved to be the case) the mode of working changed over slowly somewhere in the audible scale. At worst, therefore, unless the microphone calculations were wrong, a 3 db loss in the treble was the maximum error to be expected.

It was obviously impossible to hit the piano keys uniformly by hand, so a mechanical device was made up. This comprised a weight capable of sliding up and down a rod. A cork was attached below to hit the key, and by adjusting the height through which the weight fell the impact could be controlled.

A valve voltmeter giving a reading approximately proportional to the peak value was used, and the results, when plotted out, confirmed the expectation that the general efficiency would be more or less constant throughout the scale.

My original curves seem to have been lost, but Fig. 1 gives a curve taken under the same kind of conditions and redrawn (to conform to modern practice) on a db basis. The local peaks and troughs are familiar to all

This is the first of a series of articles by an acknowledged authority on quality reproduction. The author developed the electrical recording system used by Edison Bell Ltd., and was responsible for the recording of over a thousand titles while he was with that company

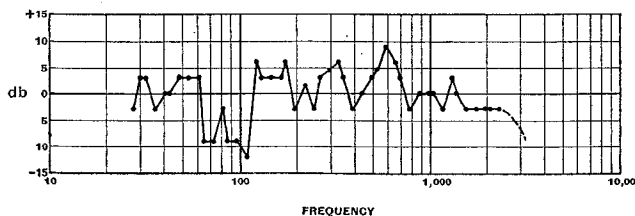


Fig. 1.—Sound output from notes of a piano when struck with equal force.

**Wireless World*, November, 1939.

Getting the Best from Records—

electro-acoustic workers, and are caused by interference effects between the direct and reflected waves which are always present in a room unless it is highly damped. To check up on this, the relative position of piano and microphone was altered, when a new curve completely different in detail would be obtained; even the opening or closing of a near-by door would affect the details of the curve. All the curves, however, had one factor in common, namely, the top octave was weak. This I attributed to the piano itself. With many pianos, the highest notes are so weak as to be lost under the

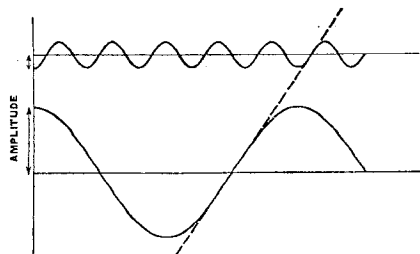


Fig. 2.—In a sine wave the slope in the region of the datum line represents the velocity of the moving point. To maintain a constant slope, the amplitude must be progressively increased as the frequency is decreased.

mechanical noise of the hammers, action, etc. It can, therefore, safely be assumed that the piano builders have some difficulty in maintaining efficiency for those notes in which the strings are very short.

The assumption of a tendency to uniform efficiency over the scale was, therefore, supported by experiment, and in my subsequent experience I have confirmed that (big drums and organs excepted) a high note, particularly the soprano soloist, is just as likely to overload a level chain as a low note.

Sound energy in free air resembles electric energy in many respects. Thus Sound Power (Watts) = Sound Pressure (Volts) \times Sound Velocity (Amps). So that constant output means that both Pressure and Velocity remain constant. If the velocity is kept constant, we find as we go down the scale that amplitude increases. This is quite automatic (see Fig. 2), and I must stress again that increasing amplitude in the bass does not indicate extra power, but is directly due to the fact that, as the period of a low note is long, the excursion is also large.

Constant Velocity v. Constant Amplitude

Basically, the ordinary acoustic gramophone can be considered as a diaphragm driven more or less directly from the record groove and driving into a horn. If the horn were perfect, and big enough to cover the whole musical scale, we should require for constant output that the diaphragm velocity be kept constant. If the coupling between the diaphragm and the groove is rigid, this would call for constant velocity at the needle point.

In other words, given perfect gramophones, constant velocity recording would be ideal.

Unfortunately, constant needle-point velocity introduces two major disadvantages. The one which is generally ignored is that the amplitude of high frequencies becomes so small that they tend to be lost under the accidental surface irregularities. The other disadvan-

tage, to which much publicity has always been given, is that for low frequencies the amplitude would be so great that the grooves might run into one another. Actually in practice this latter is not the real trouble. The real trouble is the commercial one that with some gramophones the soundbox will be thrown out of the groove by a violent excursion, and then keep repeating, while with others, even if they track satisfactorily, the note concerned will soon be worn out. (The same applies with some pick-ups.)

By recording on a basis of constant amplitude, our trouble in the bass would disappear, while in the treble the amplitude of the recorded sound would then exceed the surface irregularities so much as to drown their noise completely. Since under normal conditions constant energy at the mike is a reasonable expectation, constant amplitude recording would seem to be ideal as a means of storing the image of the sound in any medium with an amplitude limitation or a tendency to inherent noise.

With constant velocity, for each octave rise the amplitude drops to half. Constant amplitude, therefore, has, relatively, a top lift of 2:1, i.e., 6 db per octave. It seemed to the writer, therefore, that if something (such as a weak spring) could be included in the stylus bar so as to give a loss of 6 db per octave going upwards, then constant amplitude recordings would prove practical, and the first commercial electric recordings I made (1926) were an attempt at constant amplitude recording.

Unfortunately, these recordings, while better than

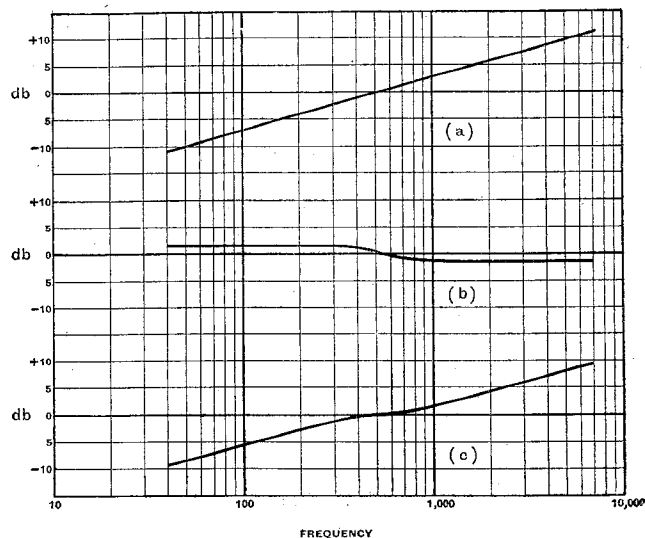


Fig. 3.—Characteristics of the Edison Bell electrical recording system. (a) Cutter characteristic; (b) microphone characteristic; (c) over-all characteristic.

horn recording, were rather "thin" when played on ordinary machines, and it was not possible to wait while the design of gramophones adapted itself to constant amplitude recording. Moreover, electric recordings were also being issued by other companies, and, as they were making no attempt to record on a constant amplitude basis, all possibility of gramophone design adapting itself vanished. Another good reason for abandoning constant amplitude recording was found later, namely, excessive record wear at high frequencies.

Getting the Best from Records—

We have now arrived at the point where we know that constant velocity recording gives us insufficient top, and constant amplitude gives us too much. In the bass,

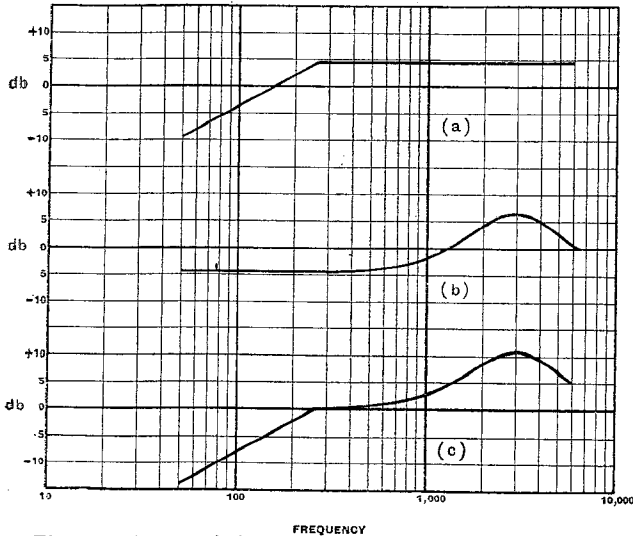


Fig. 4.—Characteristics of another early electrical recording system. The three curves correspond to those of Fig. 3.

things are reversed, and constant velocity gives us too much for the ordinary gramophone, while constant amplitude does not give enough. Obviously, a characteristic somewhere in between the two is required, but just how far in between is a problem not easily settled, especially when it is remembered that the difference between them over the frequency range 32 to 8,000 cycles amounts to 250 to 1, or about 48 db.

The method of solving this problem which would have pleased the managing director best would no doubt have been to measure the characteristics of the gramophone he uses in his office and then make the recording characteristic suit that machine. This, however, did not seem very scientific, especially as I had no guarantee that it was an "average" machine, or even that it might not be altered for some experimental reason soon afterwards. Measurements of several different types of gramophones showed that, except for complete loss of bass, and numerous treble resonances, there was nothing consistent in their output on which a recording characteristic

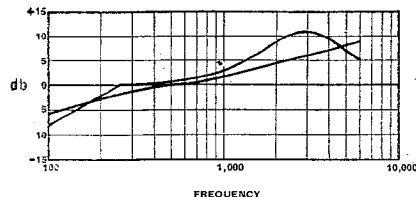


Fig. 5.—Comparison of over-all curves of the systems analysed in Figs. 3 and 4.

could be based. Finally, I decided to strive for a cutter characteristic which would be a scientific compromise and lie exactly in between constant amplitude and constant velocity. Except for the possible 3 db change in the mike, my over-all characteristic would thus be a rising one, rising at the rate of 3 db per octave. The mike change was found to occur slowly in a region about the middle of the scale, and, as this

change was in opposition to the rising cutter characteristic, it would cause a slight flattening of the slope in the region concerned. This is shown in Fig. 3, where the desired cutter curve, the mike curve, and the combination of the two are shown.

It had been published that the recording system used by our competitors had a constant amplitude characteristic below about 250 cycles, and a constant velocity one above. Comparison of one of my records with one of theirs, however, showed that their general balance had much too much top for the published curve to be correct.

Technical confirmation, which showed how a mistake had come to be made, was not published till much later. The mistake was due to the fact that our competitors had assumed their mike curve to be level in the treble. This assumption was based on elaborate pistonphone and thermophone measurements carried out with the microphone at one end of a tube full of hydrogen. When a microphone is used for recording, however, it is situated in free air, where it will reflect high notes but not low ones, and it certainly is not contained together with the artists in a tube full of hydrogen.

The top lift caused by the obstacle effect when a mike is used in free air, and also the added top lift due to cavity resonance, have since been investigated by W. West, of the Post Office Research Dept., and the results were published in the I.E.E. Journal for April, 1930. These showed that microphones of the type used by our competitors when operating in free air, face on to the source of sound, had a top lift amounting, at 3,000 cycles, to as much as 11 db over the rated value. This

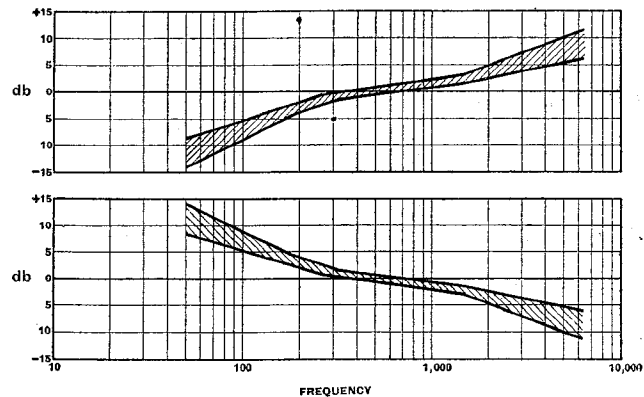


Fig. 6.—Estimated limits of characteristics of modern electrical recordings and the corresponding over-all amplifier and pick-up characteristics required for reproduction.

is shown together with the published recording curve and the combined curve in Fig. 4.

In our competitors' early electric recordings, frequencies above 5,000 were somewhat cut off by the cutters then in use. Since then, however, they have widened the range of recording and effected many other improvements. Comparison of early and recent electric recordings, however, shows that a substantial top lift but rather smoother than the earlier one is retained to this day. In fact, any record recorded on an overall constant velocity basis above 250 cycles, quite apart from surface noise, would sound so dull and heavy as to be unsaleable.

Getting the Best from Records—

In Fig. 5 the important frequency regions between 100 and 6,000 cycles can be compared, the two curves shown superimposed being the relevant parts of the combined curves from Figs. 3 and 4. It will be noticed how remarkably closely they fit.

How does this compare with present-day records? Here, like Mr. Scroggie, I have no official information, but I do know that it is possible to mix in my own recordings with modern records. Although the orchestrations may be antique, and the records show various other signs of old age, there is no impulse to reset treble or bass controls as would be the case if there was any major difference in the over-all characteristic. Moreover, why should there be any change? The basic fundamental laws remain, and the only factor which might influence matters is that surface irregularities are now appreciably reduced. Against this, however, the public has become more critical, and improved reproducing apparatus discloses what little surface there is. These facts tend to balance one another.

All things taken together seem to prove that even if modern records are recorded on a basis which differs from that shown in Fig. 5, then the difference cannot be great, and I would estimate that the curve of the present-day average record lies somewhere between the two lines shown in Fig. 6, which also shows the inverse, i.e., the ideal pick-up characteristic for extracting the music. This last, of course, assumes that the rest of the chain is perfect or corrected for. When this is not so, or when the reverberation curve of the listening room is imperfect, then an appropriate modification can be most helpful.

In connection with this question of pick-up curves, it is most interesting to note the very general tendency to a falling characteristic which modern pick-ups have when used with the circuits recommended by their makers. This would seem to indicate that in their development they have been adapted to the work they have to do, and this may be taken as independent confirmation of the trend shown in the estimated curves of Fig. 6.

Short-wave Reception

NEWS-GATHERING CONDITIONS IN PROSPECT AND RETROSPECT

AFTER having just passed through a period of maximum sunspot activity, we are now undergoing the first winter of an approaching minimum of the solar sunspot cycle. This fact has been brought home to us in a forcible and rather disagreeable manner by the generally poor conditions for night-time short-wave reception that have existed for many weeks. But the story is not one of unrelieved catastrophe, as one might assume from reading the lay Press, which fails to give prominence to anything except the ill effects of the sunspot on wireless. If the editors would consult wireless engineers and not astronomers on the wireless aspects of the matter, they would learn that there is another side to the picture.

As we approach the sunspot minimum, the appearance of single spots or small groups has a marked effect on short-wave conditions. With the appearance of a new spot, after, say, a spotless solar disc of 10 days' duration, the whole waveband upon which good distant reception is obtainable will expand in both directions, but especially downwards (in wavelength). This effect will be noticeable on the very first day that the spot becomes visible (and sometimes even just before) and will persist until the activity disappears, when the conditions will revert to the point where only a narrow band of frequencies are suitable (and then often giving weak signals) at any time of the day.

This good effect, which may persist for about 14 days, the half period of the sun's rotation, may be marred by the usual ionosphere storm lasting about two days and which frequently follows the meridian passage of the spot. On balance, therefore, the appearance of a spot will produce about 12 days of improved reception, not only in signal strength, but also by making available a broader band of working frequencies. This effect will be especially noticeable in the evenings.

Actually, taking the world as a whole, short-wave receiving conditions are not as bad as they seem to be at present in this country, if only because only the northern hemisphere is in winter.

There is another reason for thinking conditions are worse than they actually are. I refer to the failure of the Americans, to whom so many of us turn for alternative programmes and especially news, to provide a short-wave service at all comparable with that provided by the B.B.C. The British overseas service must by now be somewhat ahead of its nearest and only serious competitor, the German "world-sender" at Zeesen.

Let us analyse in more detail the situation as it applies specifically to transmission across the Atlantic.

Best Daylight Frequency

During the hours of daylight throughout most of the year, the best frequencies for transmission from New York to London centre around 20 Mc/s or 15 metres.

It is true that during certain periods in the early afternoons or evenings in winter and spring much higher frequencies than 20 Mc/s can be used with success—witness the performance of the U.S. amateurs on 28 Mc/s (10 metres), but substantially, on a 12 months basis, the correct day frequency is approximately 20 Mc/s (15 metres).

Now, this is a fortunate state of affairs for two reasons, the first reason is the shorter the wavelength, provided it is not too short, the less power is required at the transmitter to produce a workable signal at the receiver.

This is brought about both by the fact that the loss suffered by a wave in traversing the ionised layers increases as the *square* of the wavelength and also by the lower noise level experienced on the shortest waves.

The second reason is that for effective transmission large aerials must be used and that the lowest part of the aerial should be at least one-half of a wavelength in height.

Now on 15 metres a half-wave is only 7½ metres or about 25ft.; so that quite an effective aerial array may be supported on telegraph poles.

But to return to our winter night conditions, here the lowest wavelength, and in fact the only permissible wavelength, is in the region of 50 metres (6 Mc/s if we exclude

Wireless World

Short-wave Reception—

the 9.5 Mc/s (31 metres band), which has a period of usefulness not extending much later than 9 p.m. G.M.T. on most nights.

Now, more power and a much larger aerial system is required to give on 49 metres the same night-time signal/noise ratio in this country that can be obtained on 15 metres in the daytime. For example, the lowest part of the aerial system will have to be at least 80ft. above the ground, and it is interesting to note that for its 49-metre services on GSA and GSL the B.B.C. uses masts many times higher than that.

The American broadcasters, however, have no effective aerial arrays for use on frequencies lower than 15 Mc/s (above about 20 m.) unless the horizontal "V" used by WCBX is considered to be satisfactory in performance up to 25 metres.

As a partial proof of this contention a friend of mine recently drew my attention to the performance of WGEA Schenectady on 9.53 Mc/s (31.48 m.), which generally fades out at about the same time as WNBI on 17.78 Mc/s fails on evenings when both transmitters are audible. If WGEA'S antenna were as efficient as that of WNBI, then this station should, by virtue of its considerably lower frequency, remain a good signal for several hours after WNBI on 17.78 Mc/s (16.87 m.) has faded out.


WNBI's 16-metre European array is a horizontal "V" 100ft. high and with two sides each 570ft. long; a similar aerial for Bound Brook's 49-metre wave would be 340ft. high and have sides nearly 2,000ft. long.

Actually, there is a European "V" at Bound Brook for the 6.10 Mc/s frequency, but it is only 180ft. high and the sides are even shorter than those of the 17.78 Mc/s array.

All international broadcasting services have to make a start somewhere, however, and it must be remembered that 80ft. poles were considered quite suitable by the B.B.C. in 1932 for its short-wave service. Similarly no doubt the seemingly erratic performance of the new Australian transmissions by VLG2 and VLG may be traced to the aerial system at the transmitting end, since the provision of an adequate system for waves about 20 metres is a difficult and costly business.

In the case of Australia, however, we must remember, that the path the signals follow is a very difficult one. They start, perhaps, in the heat of the Australian mid-summer afternoon and travelling by the darkness path over S. America reach us in the early hours of a winter morning. No matter what the period of the year—except possibly during the equinoxes—all the possible combinations of summer light and winter darkness are sampled by the

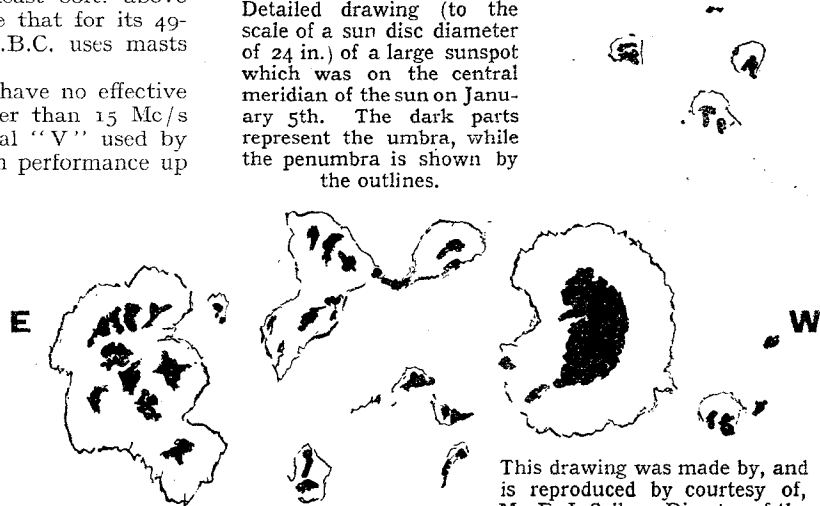Detailed drawing (to the scale of a sun disc diameter of 24 in.) of a large sunspot which was on the central meridian of the sun on January 5th. The dark parts represent the umbra, while the penumbra is shown by the outlines.



This drawing was made by, and is reproduced by courtesy of, Mr. F. J. Sellers, Director of the Solar Section of the British Astronomical Association.

wave on its 12,000 miles journey from Australia. It is for this reason that transmissions from and to Australia are nearly always conducted on waves between 25 and 31 metres (12 and 9.5 Mc/s), although transmissions on 19 and even 16 metres are often very successful for a short period around midday in our winter, when there is daylight practically all the way.


Let us, therefore, remember the special difficulties of wireless transmission from Australia when we don't get the best results on the newly inaugurated broadcasting service. Incidentally, any reports on these transmissions would be especially welcomed by Mr. A. H. Longstaff, London representative of Amalgamated Wireless of Australasia, at Australia House, Strand, London, W.C.2.

"ETHACOMBER."

M.R. Synchronous Clock Movement

AN electric clock adds the finishing touch to receiving installations fitted in special cabinet work, and readers

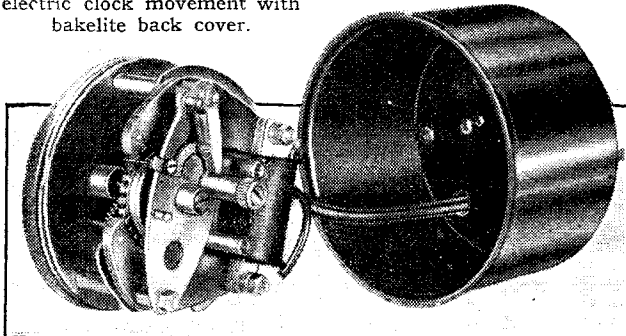Type M.R. 222 synchronous electric clock movement with bakelite back cover.



who make a hobby of designing their own cabinets may be interested to learn that clock movements of English manufacture are still available.

The M.R./222 movement costs 17s. 6d. or 18s. 6d. with bakelite back cover. It is very well made with good bearings and silent running machine-cut gears. The rotor speed is only 187.5 r.p.m. which is much lower than usual, and the life of the movement should be unlimited.

Starting is by means of a spring-loaded trigger which is absolutely certain in action, and does not let one down when starting the clock on a wireless time signal.

A variety of sets of hands and numerals is available and the clock face can be designed to conform with the character of the cabinet work. The diameter of the movement is 2½ in. (3 in. with back cover) and the power consumption is less than 2 watts.

The movements are obtainable from M.R. Supplies, 68, New Oxford Street, London, W.C.1.

Peto Scott Trophy 6

COMMUNICATION TYPE AC SUPERHET. RECEIVER (FOUR VALVES + RECTIFIER AND BEAT FREQUENCY OSCILLATOR)
 PRICE : £10 19s. 6d. (WITH PROVISION FOR VIBRATOR, £12 9s. 6d.)

ALTHOUGH the basic circuit is simple and is without the RF stage which is standard in the Trophy 8, this receiver is nevertheless true to type, and its specification includes many of the features associated with professional communication instruments. Its performance is lively down to the shortest wavelengths, and its calibration is accurate. To the amateur whose interest is not limited to broadcast transmissions only it should make a strong appeal, for its wavelength coverage is continuous, and it is well equipped for morse reception.

Circuit.—A single tuned circuit precedes the triode hexode frequency changer, and is inductively coupled to the aerial. Provision is made for the connection of a doublet aerial system if

strapped and AVC is taken from the common load resistance after suitable filtering. The control voltage, which is delayed, is applied to the frequency changer and IF stage on all wavebands, but may be switched off when searching for weak signals or receiving morse. On the 6.5-20 metre band additional amplification is provided by reducing the bias on the IF valve.


The triode section of the detector stage is resistance coupled to a tet-

rode only for the screens of the frequency changer and IF valves.

In the model tested, a switch and socket were fitted at the back for operating the set from a 6-volt battery. The filaments are fed direct and a vibrator unit delivering 70 mA at 250 volts is required. A suitable unit can be supplied by the makers of the set.

Performance.—As regards range and selectivity, the set is comparable with four-valve broadcast super-

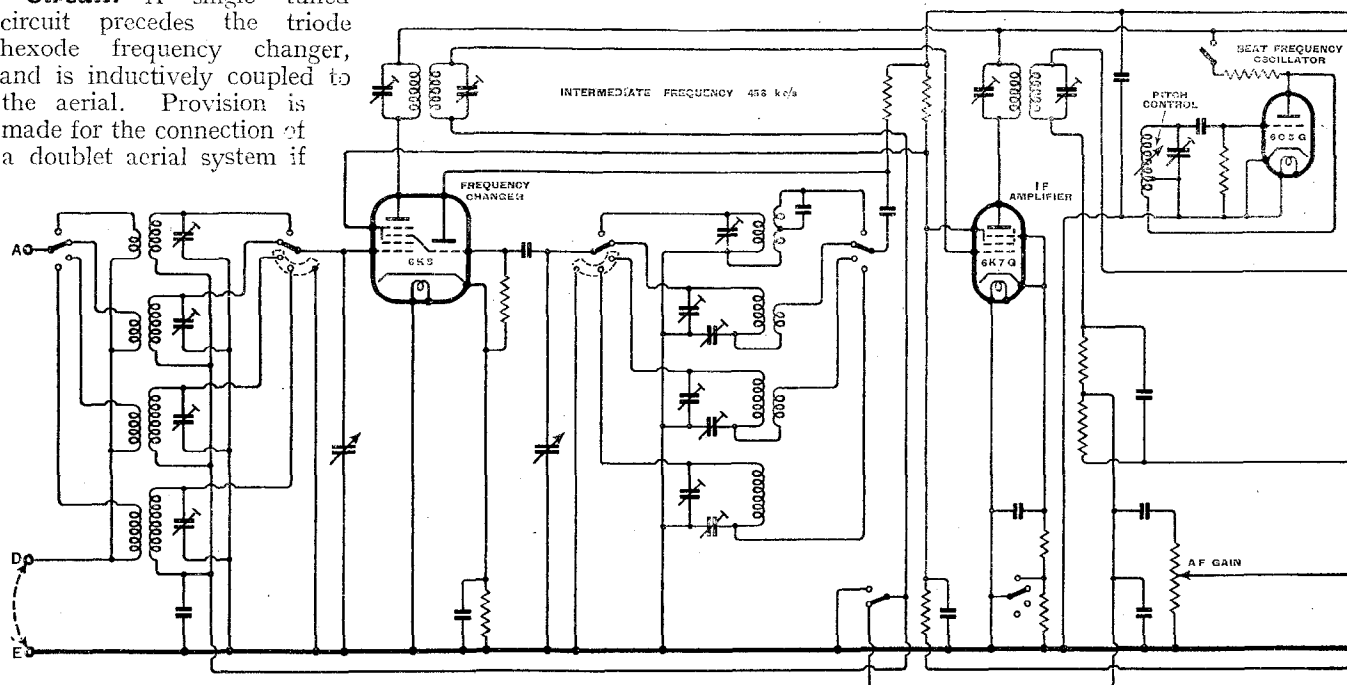Circuit diagram of the Trophy 6. The tuning condensers incorporate ganged band-spread sections in parallel with the main capacities. The connections for an auxiliary filament battery and HT vibrator are supplied as an extra.



maximum efficiency is required for one particular wavelength.

The single IF stage has an iron-cored input transformer, and an air-cored output transformer to the AVC and signal rectifier. This functions as a single diode with the anodes


rode output valve. A switch jack is connected in the output circuit to feed headphones through a condenser, using the primary of the output transformer as a choke. The HT current is smoothed by the loud speaker field, and decoupling is pro-

vided only for the screens of the frequency changer and IF valves. heterodynes in which a single tuned circuit precedes the frequency changer. The sensitivity to weak signals is, however, high, and the feel of the set gives the impression that judicious use of regeneration has been made in the IF stage. With

only one tuned stage at signal frequency some second channel interference is to be expected, and there is a sprinkling of tunable whistles on most wavebands. Repeat tuning points are very weak, however, and can be detected only in the more powerful stations.

The quality of reproduction is rich in high frequencies and is inclined to emphasise background hiss, but its characteristics are admirably suited to speech, which is crisp and clear. There is some tendency to microphonic feedback at full gain on a strong carrier, but it is easily kept under control, since the low frequency response from the 4-inch moving-coil loud speaker is small.

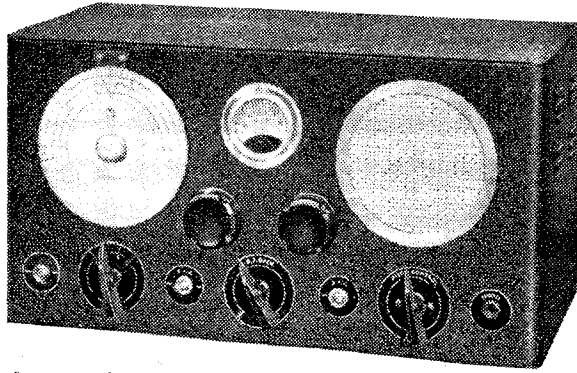Where this receiver scores over the broadcast set is in its performance at very high frequencies. Range



WAVERANGES

- (1) 46-15 Mc/s (6.5-20 metres)
- (2) 17-5.5 Mc/s (17.65-54.5 metres)
- (3) 5.5-1.7 Mc/s (54.5-176.5 metres)
- (4) 1700-550 kc/s (176.5-545 metres)

on the other three waveranges.

The four overlapping waveranges cover 6.5 to 545 metres without a break. The scales corresponding to the first three ranges are calibrated in megacycles, and the fourth (the medium-wave broadcast band) in kilocycles. With the band-spread

condenser at zero, the calibration accuracy was checked at several points on each of the short-wave ranges and found to be well within the reading error of the scale. This is a standard not often reached in communication receivers costing considerably more than this set. The band-spread condenser has an open scale, and the final adjustment of stations on the shortest wave-lengths can be

made with ease and precision.

The provision of an adjustment on the front panel for the local oscillator enables the beat frequency to be adjusted to suit the phones or the listener's particular requirements. This, and the fact that the AVC

circuits can be short-circuited makes the set ideal for morse reception and practice. Incidentally, the receiver may want slight retuning on the band-spread dial when the AVC switch is changed over.

Constructional Features.—The whole of the tuning condenser system including both tuning dials is suspended on rubber. The main tuning condenser is of a standard type and the two-gang band-spread condenser has been added to it. Extensions of the end plates of the main condenser carry the bearings for the moving vanes, of which there are two in each section. A single fixed vane between each pair is soldered direct to the appropriate section of the main condenser.

The controls are well laid out in the front panel of the all-metal cabinet, which is well ventilated and finished with a durable black crystal-line enamel.

Makers.—Peto Scott Electrical Instruments, Ltd., Pilot House, Stoke Newington, Church Street, London, N.16.

BOOKS RECEIVED


The 1940 edition of the famous **Kelly's Directory**—officially known as the Post Office London directory—which has just made its appearance, is particularly noteworthy this year inasmuch as it contains a list of the wartime addresses of the many companies, including wireless firms, who have temporarily evacuated their London offices. The Directory, which embodies all its usual features, also contains the names of no fewer than five hundred London streets which have been renamed during the past twelve months.

The price of the Directory is 60s., and it is published by Kelly's Directories, Ltd., 186, Strand, London, W.C.2.

Freedom Calling. Pp. 64. Published by Frederick Muller, Ltd., 29, Gt. James Street, London, W.C.1. Price 6d.

The story of the secret German "Freedom Station," which has been transmitting on various short wavelengths at intervals since January, 1937, is told by the station's representative in Great Britain, who, of course, remains anonymous.

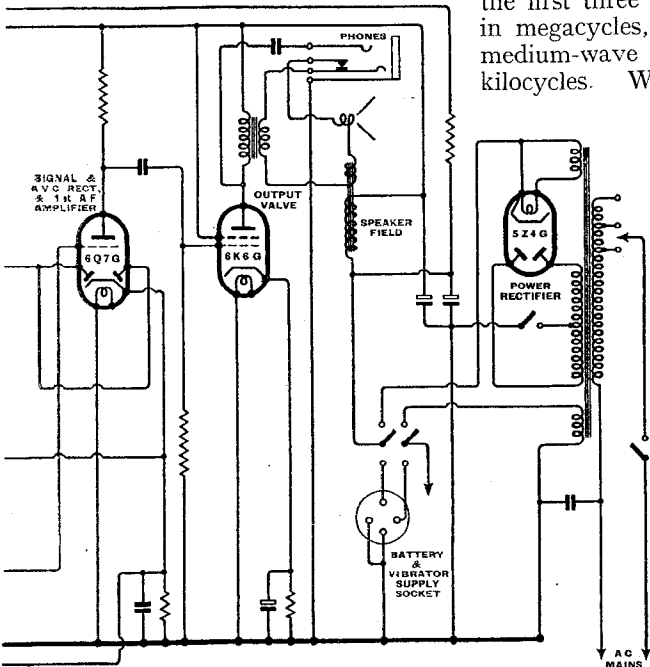The Practical Engineer's Pocket Book, 1940. Published by *Electrical Trading*, 92, Long Acre, London, W.C.2. Price 2s. 10d. post free. A reference book of facts and formulae; there are over 50 sections, and domestic as well as industrial applications of electricity are dealt with. The latest I.E.E. Regulations for the Electrical Equipment of Buildings are summarised.



No. 1 from 20 down to 6.5 metres is remarkably lively and also very uniform in its sensitivity throughout the range. The 13-metre broadcast band stands out, of course, and the beat frequency oscillator is useful in locating distant carriers on this as

Letters to the Editor

THE EDITOR DOES NOT NECESSARILY ENDORSE THE OPINIONS OF HIS CORRESPONDENTS

Reaction Control

I SHOULD like to express my appreciation of the recent article entitled "Smooth Reaction." In my opinion this subject deserves more mention than has been accorded it during the last year or two.

Perhaps something might be said about some of the snags often met with in practice. For instance, it has been my experience that the Colpitts circuit employing a choke in the cathode lead is prone to medium-wave break-through, and this may necessitate rather careful screening of the whole cathode circuit for its complete elimination.

In addition, modulation and tunable hums, and rapid motor-boating when oscillating, are usually found to be more troublesome when the cathode of the detector valve is not directly earthed.

Methods of getting over this that I have found effective in my own receivers are as follows:—

(1) Wiring up the heaters in twin lead-covered electric light cable, and earthing the sheath to the earth point of each stage.

(2) Connecting non-inductive 0.01-mfd. condensers from heater to earth, wired directly to the detector (and sometimes RF and first audio) valveholder.

(3) Adequate filtering of RF currents at the detector anode.

(4) Use of screened cable for power supply leads if a separate power pack is used.

(5) Screening the rectifying valve or complete power pack in perforated zinc.

(6) Connecting mica condensers of 0.001 to 0.01 mfd. across (a) mains leads, (b) mains to earth, (c) HT+ to earth, (d) anodes of rectifying valve to earth or cathode.

Of course, all these precautions are seldom required. Experiment will soon discover the simplest way of curing the trouble.


Another point that requires watching in a TRF receiver is the possibility of the RF stage oscillating before the detector. It usually pays to resort to fairly complete screen-

ing and careful choice of earth returns, etc.

J. C. FIELD.
Redditch.

Miniature Receiver

AS I have received many letters regarding the midget set I described in last month's correspondence columns, I feel that some further details would be of interest. The circuit, as may be seen from the diagram, is a perfectly standard one-valve type. The really important component is the RF choke, which must be reliable if reaction is to be consistent over the whole tuning range, but at the same time it

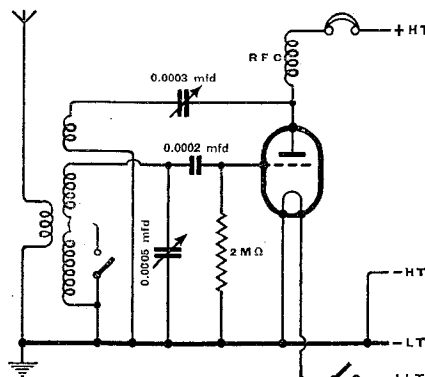

Single valve reaction circuit described by Mr. Taylor.

must be small so that it does not take up too much space. The tuning coil should be small but efficient and I have found that the Telsen 349 midget iron cored dual range type is the most suitable. The valve must be a power or super-power type, and should be of a reliable make; an AF pentode may be used on a lower voltage of HT, but with a reduction in volume.

Normally the HT voltage is 18, although after a little experiment it can often be reduced to 9. The LT is two 1½-volt unit cells in series, which actually give 3 volts, but this soon drops to 2 on load. The set is built into a small wooden cabinet, with midget knobs and a small QMB on/off switch. The tuning and reaction condensers are midget types, and so are the grid

condenser and grid leak. A phone jack is a refinement, and if required this may be the type that will switch off the set as well when the plug is withdrawn.

The aerial should be a good outdoor one if the best results are to be obtained, and an earth is also necessary. I am hoping to experiment with reflex circuits working on low voltages, and also with the new 1.5 volt valves.

G. N. S. TAYLOR.
Newbury, Berks.

Sets for Active Service

THE technical problems of midget receiver design have been fully discussed both in the *Wireless World* and American technical journals. One or two receivers of the "pocket" variety were marketed some time ago but did not come into general use, probably owing to the very small capacity of the accumulator. Now that low-drain 1.4 volt tubes are available the design of small receivers for battery operation should be simplified.

Apart from "pocket" receivers, many men in the Services and Civil Defence organisations would probably welcome an English counterpart of the two-tube AC/DC receivers which provide loud speaker reception in most districts of the United States. The price asked across the Atlantic is about five dollars (25/-).

May I suggest that the radio trade consider the possibility of:

1. Producing three standardised "Service" receivers for mass production—

- a five valve mains super-het. in a strong wooden case;
- a cheap two-tube AC/DC receiver as a second set;
- a pocket receiver using two or three tubes, operating from dry batteries for HT and LT and providing reception on a single head-phone.

2. Requesting the various organisations which provide radios and

Wireless World

other supplies for the Services to undertake the distribution of batteries and spare parts.

3. Making efforts to obtain duty-free admission of any midget valves, etc., which might be required from the United States. This concession, if granted, would roughly compensate for the higher prices of foreign goods consequent on the unfavourable exchange rate.

A. CLARKE.

Rossendale, Lancs.

I AM very interested in the suggestions put forward for suitable radio sets for use with the B.E.F.

As an overseas representative of a British firm my work keeps me travelling abroad for about nine months of the year—when dictators do not stop it.

Before my last trip I made enquiries regarding a suitable radio set for my purpose but had to leave without finding one.

What I wanted was a set with the following points, or most of them, included in its make-up:—

- (1) A case not larger than 6in. x 14in. x 14in.
- (2) Weight not so important but lightness preferred.
- (3) The case able to stand usage, wet and wear.
- (4) The interior and exterior able to endure tropical heat and dampness.
- (5) No projecting knobs.
- (6) Long wave unnecessary.
- (7) Medium and short wave reception very good.
- (8) A loud speaker preferred to earphones.
- (9) Workable on AC, DC, ships' light sockets or dry batteries.
- (10) The batteries standard and purchasable abroad.

I wanted a set that would work

after a bicycle ride in Bermuda or a surf boat drenching on the West Coast; that would receive British news and American opinion from five thousand miles off.

If such a set is available I should be glad to hear of it. If not, I hope the given requirements will help to produce one in the near future. Manufacturers might be surprised at the extent of the market for a Serviceable Portable Radio.

Aberdeen.

L. AULD.

News from the Clubs

Croydon Radio Society

Headquarters: St. Peter's Hut, Ledbury Road, South Croydon, Surrey.

Meetings: 1st Thursday in the month at 8 p.m.

Hon. Sec.: Mr. E. L. Cumbers, 14, Campden Road, South Croydon, Surrey.

At the January meeting the lecturer was Mr. P. G. A. H. Voigt. The large audience, many of whom had come through the black-out from remote parts of London, was an eloquent tribute to the lecturer's popularity, and afforded striking proof of the great interest that is taken in high-quality reproduction.

The next meeting will be on Thursday, February 1st, at 8.0 p.m., and the lecturer will be Mr. H. G. Menage, of R. A. Rothermel, Ltd., who will give a talk entitled, "The Latest Developments in Piezo Crystals."

The Slough and District Short-wave Club

Headquarters: Toe H. Headquarters, William Street, Slough, Bucks.

Meetings: Alternate Thursdays, at 7.30 p.m.

Hon. Sec.: Mr. K. A. Sly, 16, Buckland Avenue, Slough, Bucks.

At the December 21st meeting, Mr. Houchin continued his series of lectures on the "Fundamentals of Radio." The annual general meeting was held on January 4th. It was decided to continue constructional work on the club's receiver at the fortnightly meetings. Morse practice is held at all meetings.

North Manchester Radio and Television Society

Headquarters: 14, Prestwick Road, Prestwick, near Manchester.

Hon. Sec.: Mr. R. Lawton, "Gratton House," Whalley Road, Whalley Range, Manchester.

At the December 14th meeting, a letter from the G.P.O. sectional engineer was read, replying to certain points raised by the society concerning the wartime cancellation of Amateur Transmitting Licences and the confiscation of certain apparatus. It was also announced at the meeting that negotiations had been initiated with the chief postal censor regarding an arrangement whereby short-wave listeners could send reception reports to transmitters in certain countries on the G.P.O. "censored" list.

The next meeting will be held at 7 p.m. on January 23rd.


BOOKS ON WIRELESS

Issued in conjunction with "The Wireless World."

- "FOUNDATIONS OF WIRELESS," by A. L. M. Sowerby. Second Edition. Price 4/6 net. By post, 4/11
- "RADIO LABORATORY HANDBOOK," by M. G. Scroggie. Price 8/6 net. By post, 9/-
- "WIRELESS SERVICING MANUAL," by W. T. Cocking. Fourth Edition. Price 5/- net. By post, 5/5
- "HANDBOOK OF TECHNICAL INSTRUCTION FOR WIRELESS TELEGRAPHISTS," by H. M. Dowsett. Sixth Edition. Price 21/- net. By post, 21/9
- "WIRELESS DIRECTION FINDING," by R. Keen. Third Edition. Price 25/- net. By post, 25/9
- "RADIO DATA CHARTS," by R. T. Beatty. Second Edition. Price 4/6 net. By post, 4/10
- "ELEMENTARY PRINCIPLES OF WIRELESS TELEGRAPHY AND TELEPHONY," by R. D. Bangay. Revised by O. F. Brown. Third Edition. Price 7/6 net. By post, 8/-
- "THE WIRELESS WORLD," DIARY FOR 1940. Price 1/6 net. By post, 1/7
- "LEARNING MORSE." Price 6d. net. By post, 7d.

Obtainable by post (remittance with order) from ILIFFE & SONS, LTD., Dorset House, Stamford Street, London, S.E.1, or from Leading Booksellers and Railway Bookstalls.

INTRODUCING the "FLUXITE" QUINS

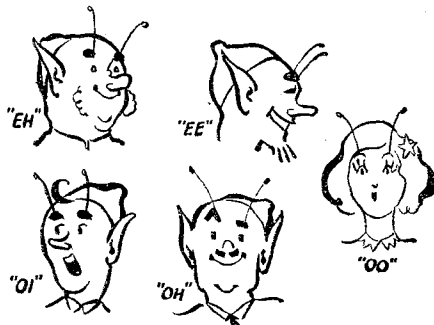

"EH," "EE," "OI," "OH," and "OO"—
We're THE FLUXITE QUINS—calling YOU—
For things you make or mend—
You'll find you can **DEPEND**
On US—when there's soldering to do!"

See that FLUXITE is always by you—
in the house—garage—workshop—
wherever speedy soldering is needed.
Used for 30 years in government
works and by leading engineers and
manufacturers. Of Ironmongers—in
tins, 4d., 8d., 1/4 and 2/8.

Ask to see the FLUXITE SMALL-
SPACE SOLDERING SET—compact
but substantial—complete with full
instructions, 7/6.


Write for Free Book on the art of
"soft" soldering and ask for Leaflet
on CASE-HARDENING STEEL and
TEMPERING TOOLS with FLUXITE.

TO CYCLISTS! Your wheels will
NOT keep round and true unless the
spokes are tied with fine wire at the cross-
ings AND SOLDERED. This makes
a much stronger wheel. It's simple—with
FLUXITE—but IMPORTANT.

THE FLUXITE GUN

is always ready to put Fluxite on the
soldering job instantly. A little
pressure places the right quantity on
the right spot and one charging lasts
for ages. Price
1/6, or filled 2/6.

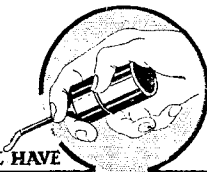FLUXITE LTD.,
(Dept. W.W.),
DRAGON WORKS,
BERMONDSEY
STREET, S.E.1



ALL MECHANICS WILL HAVE

FLUXITE

IT SIMPLIFIES ALL SOLDERING

NEWS IN ENGLISH FROM ABROAD

REGULAR SHORT-WAVE TRANSMISSIONS

Country : Station	Mc/s	Metres	Daily Bulletins (G.M.T.)	Country : Station	Mc/s	Metres	Daily Bulletins (G.M.T.)
America				Ireland			
WNBI (Bound Brook) ..	17.78	16.87	3.0 a.m., 2.0†, 5.0.	Athlone	9.59	31.27	6.45, 10.0 (10.5 Sun.)
WRCA (Bound Brook) ..	9.67	31.02	3.0 a.m.		17.84	16.82	6.45, 10.0 (10.5 Sun.)
WOBX (Wayne) ..	6.12	49.02	6.55 a.m.	Italy			
	9.65	31.09	4.0 a.m.	I2RO3 (Rome) ..	9.63	31.15	12.30 a.m., 6.18, 9.15.
	11.83	25.36	1.55 a.m., 8.30, 10.50§†, 11.30§†, 11.45*.	I2RO4	11.81	25.40	12.30 a.m., 11.0 a.m., 3.55, 6.18.
	15.27	19.65	6.30§†	I2RO6	15.30	19.61	12.30 a.m., 9.45 a.m., 3.55.
	21.56	13.91	1.0, 2.0†, 4.0*†	I2RO8	17.82	16.83	11.0 a.m.
WGEO (Schenectady) ..	9.53	31.48	4.0 a.m.†, 8.30†, 10.15*, 11.25†.	I2RO9	9.67	31.02	11.16.
WGEA (Schenectady) ..	15.33	19.57	1.0, 2.0†, 9.55§†	IRF	9.835	30.52	12.30 a.m.
WPIT (Pittsburg) ..	6.14	48.86	4.0 a.m.†	IQY	11.76	25.70	12.30 a.m.
	11.87	25.26	3.0 a.m.†, 11.45§†	Japan			
	15.21	19.72	2.0†, 4.0†, 5.0.	JVW	7.25	41.34	8.5
	21.53	13.93	1.0†, 2.0.	JZI (Tokio) ..	9.53	31.46	8.5.
WCAB (Philadelphia) ..	6.06	49.50	1.55 a.m., 11.30§†, 12.0 midnight.	JZK	15.16	19.79	1.15 a.m.
	9.59	31.28	1.55 a.m., 4.0 a.m.‡, 6.55 a.m.‡, 8.30§†.	Manchukuo			
	21.52	13.94	8.30§†.	Hsinking	11.77	25.48	2.50, 6.30, 9.0.
WRUL (Boston) ..	6.04	49.67	4.0 a.m.‡, 11.0†.	Newfoundland			
	11.73	25.58	4.0 a.m.†, 8.0.	St. John's	9.48	31.64	10.30.
	11.79	25.45	8.30§†.	Portugal			
WRUW (Boston) ..	15.12	19.83	8.30§†.	—	3.71	80.80	8.0 (Tues., Thurs. and Sat.)
	11.72	25.60	11.0†.	Rumania			
Australia				—	9.28	32.33	9.45†.
VLQ	9.61	31.20	8.15 a.m., 12.30, 4.0.	Russia			
VLQ2	11.87	25.00	8.15 a.m.	RNE (Moscow) ..	12.00	25.00	9.30, 10.30, 12.0 midnight.
VLR	9.58	31.32	9.15 a.m. (9.20 Sun.), 1.20†.	RW96	6.03	49.75	8.0, 10.30, 12.0 midnight.
VLR3	11.88	25.25	2.20 a.m., 8.45‡, 10.0.		9.52	31.51	8.0, 10.30.
					15.18	19.76	8.0 a.m.
					7.51	39.89	9.30, 10.30.
					15.58	19.25	12.0 midnight.
					9.60	31.25	8.0, 9.30, 10.30, 12.0 mid- night.
					7.36	40.76	9.30†, 10.30†.
					8.06	37.22	8.0.
					11.04	25.77	11.0 a.m.
					11.90	25.21	9.30, 10.30†.
				Spain			
				FET1 (Valladolid) ..	7.07	42.43	7.45.
				EAQ1 (Madrid) ..	9.86	30.43	3.25.
				Sweden			
				SBU (Motala) ..	9.53	31.46	9.45
				SBP	11.70	25.63	9.45
				Turkey			
				TAP (Ankara) ..	9.46	31.70	8.15.
				Yugoslavia			
				YUA (Belgrade) ..	6.10	49.18	9.0.
				YUC	9.50	31.56	9.0.

REGULAR LONG- AND MEDIUM-WAVE TRANSMISSIONS

Country : Station	kc/s	Metres	Daily Bulletins (G.M.T.)	Country : Station	kc/s	Metres	Daily Bulletins (G.M.T.)
Finland				Latvia			
Lahti	165	1,807	9.30.	Madona	583	514.6	9.0 (Tues. and Fri.)
France				Kuldiga	1,104	271.7	9.0 (Tues. and Fri.)
Radio-Paris	182	1,648	9.45.	Rumania			
Germany				Radio-Romania ..	160	1,875	9.55†
Hamburg	904	331.9	} 12.15 a.m., 10.15 a.m., 2.15, 5.15, 8.15, 9.15, 11.15.	Bucharest	823	364.5	9.55†
Bremen	758	395.8		Russia			
Hungary				Moscow RVI	172	1,744	9.30, 10.30.
Budapest	546	549.5	10.10	Spain			
Ireland				Burgos	1,258	238.5	10.15.
Radio-Eireann ..	565	531	} 6.45†, 10.0 (10.5 Sun.)	Sweden			
Dublin	1,348	222.6		Motala	216	1,389	} 9.45
Cork	1,235	242.9		Stockholm	704	426.1	
Italy			Falun	1,086	276.2		
Rome	713	429	Horby	1,131	265.3		

All times are p.m. unless otherwise stated. * Saturdays only. † Saturdays excepted. ‡ Sundays only. § Sundays excepted.

Technical Information


SUSPENSION OF INDIVIDUAL SERVICES

THE war has naturally made its call upon the technical personnel of the *Wireless World*, several members having already departed to war service tasks. With a reduced staff we find it necessary to suspend the postal reply service to readers' technical enquiries, which we have hitherto conducted.

We feel that in the present circumstances we should be failing in our duty to our readers as a whole if we continued to allow the time of technical members of the staff to be largely occupied with answering enquiries from individuals when, by relieving them of this work, their whole time can be devoted to the production of the best possible *Wireless World* for the benefit of all readers. Will those, therefore, who have been accustomed to send us their technical problems to solve please accept this intimation that individual requests for technical information must regretfully be declined so long as present conditions prevail?

Cathode Circuit Protection

INDIRECTLY heated cathodes of gasfilled rectifiers and relays require independent switching of the anode and cathode circuits in order that the cathode shall obtain its full working temperature before the anode circuit is closed. Failure to take this precaution results in rapid disintegration of the cathode surface and consequently short life for the valve. Generally, a thermally operated switch of the bimetal strip type is included in the cathode circuit when it is desired to make the circuit operable from a single switch and remove the possibility of the user neglecting to delay the anode switching, or of closing this circuit too soon.

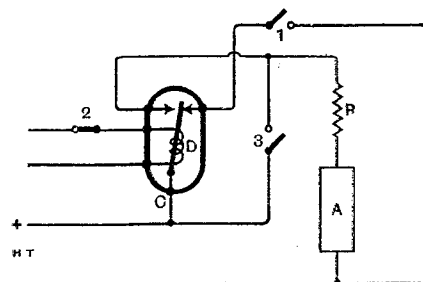

Although the time of closure of the thermal switch is not very accurate, it is sufficiently good to ensure the necessary delay, but it has one disadvantage. The thermal delay on closing is also present on opening circuit and the bimetal contact does not open until an appreciable time after the exciting coil has been switched off. Hence it is possible by accident or otherwise to open the circuit and close it again before the bimetal switch contacts have separated, the time interval being sufficient for the valve

cathode to cool down. The thermal switch may thus be the cause of damage it is designed to avoid.

This may be overcome by the simple addition of a relay of the telephone type with three contacts and an additional contact on the bimetal switch.

Referring to Fig. 1, which shows the position of the contacts when the supply is disconnected, D is the operating coil of the bimetal switch and A a relay with three contacts, 1 and 3 being normally open and 2 normally closed.

When the valve cathode circuit is closed, the coil heats up until the contact arm C makes on the left hand side. This operates relay A, closing contacts 1 and 3 and opening 2. The operation of 3 locks relay A in circuit and the opening of 2 isolates the heater coil D which gradually reverts to its original position. When the contact arm C again makes on the right-hand side, the HT circuit is closed through it and the closed contact 1. If at any time the HT circuit is opened or the supply switched off, relay A will release and its contacts revert to their original positions, so that the whole cycle outlined must be repeated before the HT circuit can be closed again and the cathode of the valve cannot be damaged by switching off for a short time and then closing circuit again.

Moreover, since the HT circuit is closed only after the thermal switch has reverted to its original condition, its operation is more consistent than with a simple thermal switch, since no permanent set in the contact arm is produced by being kept in circuit for a long period, though, of course, its variability due to atmospheric temperature still remains.

R. C. W.

for **VIBRATORS...**
INVESTIGATE THE
BULGIN RANGE

**L.T. to H.T.
Vibrators**




These British-made Vibrators cater for all requirements — Full cycle A.C. at about 100-120 c/s to ultimate D.C. is generated with automatic energisation. The square topped wave form renders smoothing easier and more efficient than that obtained with many rectifying systems. Contacts are of pure end-grain tungsten on special metal springs. All types are complete with instructions. Guaranteed for 1,000 hours approximately. These **BULGIN VIBRATORS** are remarkably quiet in use.

VIBRATOR TRANSFORMERS

All types of Transformers for stepping up voltages are available and give highest efficiency. Windings are fully interleaved, and assembled with massive core, clamped, shrouded; grey finish. Full instructions are supplied.

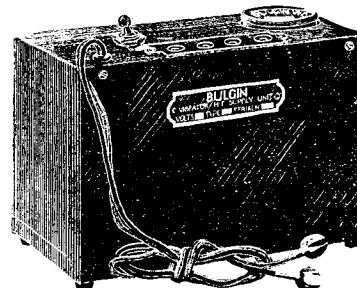From 10/6 each. List No. M.T.2. See Cat. 162, p.93.



**New Type Vibrator Supply
H.T. Unit**

The New Bulgin Vibrator Eliminators employ the latest circuits, and are extremely efficient. Illustrated is new 2v. Model with partially enclosed vibrator. Excellent acoustic and electrical silencing and considerably reduced size. Models are suitable for two, three, four, five valve sets. Complete with Vibrator, on-off, switch and 24 in. L.T. Leads, finished grey cellulose enamel. With full instructions. List No. E.K.125. Price £3-15-0.

★ Please send me the NEW 128 pp. Catalogue No. 162 showing FULL range of Bulgin Products, for which I enclose 3d. stamps. I have not yet had a reference copy. Mention this paper.

ALWAYS DEPEND ON
BULGIN

Advert. of A. F. BULGIN & Co., Ltd., Abbey Road, Barking. Tel.: R1Ppleway 3474 (3 lines).

Random Radiations

By "DIALLIST"

Bargains

LATELY I've come across one or two people who had bought or were on the verge of buying television sets, of all the unlikely things! I could hardly believe my ears when the first of them told me what he'd done; but when he explained the position I agreed that it was no bad thing to do. He had been offered a brand new television-cum-radio receiver at a mere fraction of its original price. And when I say radio receiver, I mean a pretty good "all-wave" set—in a console cabinet, naturally. His argument was: "Television will be going again some day—perhaps sooner than some folk think. Until it does I have a good wireless set to use. When television broadcasts are resumed I shall be ready for them." That seems to be sound common sense and if you come across any of these instruments offered at bargain prices, you might do a lot worse than snap one of them up.

Wired Television

For good and sufficient reasons the broadcasting of television programmes from the Alexandra Palace's aerials has had to be suspended, but Mr. S. Sagall, who has done valuable work in the development of television, recently made an interesting suggestion. Why not, he asks, develop wired television and use it so long as the war lasts? Television transmissions can be made

A.R.P. Black-out Switch

ADVANCE COMPONENTS, LTD., of Back Road, Shernhall Street, Walthamstow, London, E.17, well-known as manufacturers of wireless accessories, have produced an adap-



The Advance "Dorswitch" is easily fitted

tor unit by means of which a lamp is automatically switched off when the door is opened. The "Dorswitch," as it is called, comprises a lamp adaptor, enclosed spring switch, and a stop bracket for attachment to the door. Complete with 12ft. of flex wire and fixing screws, the device costs 4s. 6d.

in this way: the G.P.O. is, or was, engaged in research into the subject long before the war started. If we don't do something of the kind there is a risk that American radio manufacturers, who are going right ahead with television while we are forced to stand still, will capture television, just as Hollywood captured the cinema industry whilst the world was engaged in the Great War. On the other hand, if we develop wired television we can keep public interest alive. Also, those engaged in research and development will see to it that we retain our place at the front of the race instead of lagging behind. There's a lot in that suggestion and I hope that something may come of it.

History Repeats Itself

Talking of television in the United States reminds us of a frank report on the present position there that I saw the other day. When the U.S.A. first became television-conscious the head of a big firm, connected with the radio industry over there, wrote to me to ask for my views on a course that they were considering. They don't make complete receivers of any kind, but they do make component parts of high grade. Television, they said, seemed to offer a new field. Would I let them know what I thought of their prospects, basing my recommendations on knowledge of what had happened in this country. My advice to them was not to rush in, but to await developments. I told them what had happened in one country: immense public interest in television whilst it was still in the laboratory stage; the whole country eagerly awaiting its arrival as a popular hobby; tremendous enthusiasm in the lay papers; then when it did come crowds flocking to demonstrations, exhibitions, and so on; everything apparently all set for something like a boom; BUT for a long time the public would do everything but buy. I said that it would be more interesting to see whether history would repeat itself during television's early days in the States.

A Queer Parallel

It has. Television arrived there, after a long period of keyed-up expectation, heralded by the blaring of all the trumpets and the banging of all the drums at the disposal of a Press second to none in its knowledge of how

to use these instruments for the fullest effect. There was television at the World's Fair; there were television demonstrations galore. Uncle Sam and his wife and family rolled up to see television and to be televised. The whole United States was enthusiastic. Regular programmes began from a number of stations. The ball, in a word, was set rolling. But was it? As matters have turned out, the early history of television on the far side of the Atlantic has so far been very much what it was on this. To quote the report I mentioned in the preceding paragraph, "sales of television receivers have hitherto been negligible." Uncle Sam and his wife and family, in a word, are doing exactly what Mr. and Mrs. John Bull and family did not so long ago. They will read anything that's written about television, they will go a long way to see it, but when it comes to the marketing of receivers, their sales resistance is found to be, as ours was at first, of a singularly high order.

Why Is It?

Curious that things should have panned out on lines almost exactly so similar in the Old World and the New. It was suggested over here that the key reason for unwillingness to purchase was to be found in the poorness of the programmes broadcast. The Americans resolved from the first that that kind of thing would never be said about theirs. Both at the World's Fair and elsewhere, first rate entertainment was put over. We thought that the original television receivers might have been too dear for the purses of most people. They were far cheaper in America. We knew that only some 60 per cent. of our potential "lookers-in" in the London area had suitable supplies of mains-borne electric current. In the States the percentage of those who live in areas served by television transmitters and have the right kind of mains current is probably 90 or more. Lastly, it was suggested by some that our people had been told so often that real television had arrived when it hadn't, that when it did come they had lost interest. Nothing of the kind happened in America. Little was heard of television in the lay Press till it really was on the way. The public was certainly not let down again and again by empty promises. Why did television find it so hard to make its way into homes on both sides of the Atlantic

for some time after it had become a reality? I can't find the answer at the moment. Can you?

A "Lifer for Methuselah!

THE other day I was wondering just how many years in concentration camps my foreign listening would have earned me since the war broke out, had I been a dweller in the Fatherland! So far as I can calculate my combined sentences would have run into four figures. How awful it must be to live in a country where even your sessions at the controls of the wireless set may land you into fearful pains and penalties! It's quite possible that the threat of these very pains and penalties does quite a bit to encourage listening to stations abroad. Stolen fruits are proverbially the sweetest. In your younger days you probably smoked your first cigarette because you were strictly forbidden to do such a thing. I can quite imagine the German household which possesses a set that will bring in foreign stations saying to its collective self, "If these stations are forbidden, they must be sending out exciting things. We must be missing a lot by obediently abstaining from listening to them. Let's have a go at them and see what there is that is so evil for us to hear." I know that if I were in their position the temptation would be far too strong—particularly to a long-distance enthusiast.

The Leaking Accumulator

READER, have you ever had a leaky accumulator in a portable set? I sincerely hope that you haven't, for the results are far from jolly. I have a portable of the suitcase type, which lies on its back with the lid raised when it is in use. The other day I lifted mine off the table—and the bottom fell out of it. The wretched accumulator had somehow sprung a leak and it's surprising how far a little dilute sulphuric acid can go and what damage it can do. It had completely rotted the wood of the case; had soaked through it and ruined a table cover and the table top beneath it. It had penetrated from the battery compartment through the partition into the body of the set. And what a mess there was there! Almost all of the wiring will have to be redone. Some components I have saved by alkaline treatment, but others will, I fear, have to be renewed. All that happened during three or four days when the set was out of use.

I've made a job of the case by repairing it with plywood and leathercloth and I've got most of the rewiring done. The set is working again, but I am sadly afraid that I'll have breakdown after breakdown in the months to come as further now unseen effects of acid corrosion manifest themselves. If you have a celluloid cased accumulator of whose acid-holding qualities you're at all doubtful, take my advice and discard it. It can do many times more damage than it's worth.

Short-wave Black-out

BETTER THINGS TO COME

OUR contributor "Ethacomber," who discusses elsewhere in this issue the effect of present solar activity, forecasts that conditions for night-time short-wave reception will improve progressively during the month of February.

Murphy "78" Series

HIGH-PERFORMANCE CONSOLE AND RADIOGRAM

THESE receivers, the production of which was held up at the outbreak of war, are now to be released in limited numbers.

The A78C is the successor to the A40C, which it resembles in appearance. It is, however, fitted with two loud speakers giving better sound distribution. There are four degrees of selectivity with equivalent audio frequency responses up to 8,500, 7,000, 5,000 and 3,000 cycles. The short-wave side is similar to that of the A76 recently reviewed and includes band spread tuning and a special RF stage. For high quality reception a "side chain" IF stage and rectifier supply AVC, but in the position of maximum selectivity this IF valve is included in main receiving chain.

The A78RG gives even better quality than the console, for it has a larger baffle area and "acoustic tube" control of the radiation from the back of the speakers. A side-by-side arrangement of the radio and gramophone controls has been adopted and separate lids for the two compartments are provided on the top of the cabinet. The record changer takes eight mixed 10in. or 12in. records and is fitted with a crystal pick-up in which either steel or fibre needles may be used.

The price of the A78C is £42, and the A78RG costs £95.

**VORTEXION
MODEL CP20**

15w. AC & 12-VOLT DC AMPLIFIER

A VOLUNTARY APPRECIATION

The Broadway,
Sutcliffe,
Whitstable, Kent.
7th November, 1939.

Dear Sirs,

We duly received the CP20 amplifier. As a Public Address Engineer for the past sixteen years, I should like to convey to you my remarks referring to this equipment. Without a doubt it is the best I have had the pleasure of working with, the quality is superb, both from gram. and mic. and your statement that the amplifier is flat from 30 cycles is modest, in fact I have always built our own amplifiers previously, but this time I must hand it to you, more especially so in view of the price. I could not have built one as good for double the price.

Thanking you for a very good job,
Yours sincerely,

I. F. Pollard (Prop.),
Chestfield Radio.


This small Portable Amplifier, operating either from AC mains or 12-volt battery, was tested by "THE WIRELESS WORLD," October 1st, 1937, and has proved so popular that at Customers' demand it remains unaltered except that the output has been increased to 17.2 watts and the battery consumption lowered to 6 amperes. Read what "The Wireless World" said :-

"During tests an output of 14.7 watts was obtained without any trace of distortion so that the rating of 15 watts is quite justified. The measured response shows an upper limit of 18,000 c/s and a lower of 30 c/s. Its performance is exceptionally good. Another outstanding feature is its exceptionally low hum level when AC operated even without an earth connection. In order to obtain the maximum undistorted output, an input to the microphone jack of 0.037 volt was required. The two independent volume controls enable one to adjust the gain of the amplifier for the same power output from both sources, as well as superimpose one on the other, or fade out one and bring the other up to full volume. The secondary of the output transformer is tapped for loudspeakers or line impedances of 4, 7.5 and 15 ohms.

- AC and 12-volt CHASSIS with valves, etc. £12 12 0
 - Or in Resine Case with Collaro Motor, Piezo P.U. and Mike Transformer £17 17 0
 - AC only CHASSIS with valves, etc. £8 18 6
 - Or in Resine Case with Collaro Motor, Piezo P.U. and Mike Transformer £14 0 0
- Gauze Case for either chassis 12/6 extra.

Many hundreds already in use for
A.R.P. & GOVERNMENT purposes

50w. AMPLIFIER CHASSIS

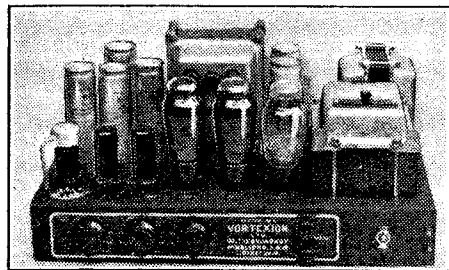

A pair of matched 6L6's with 10 per cent. negative feed-back is fitted in the output stage, and the separate HT supplies to the anode and screen have better than 4 per cent. regulation, while a separate rectifier provides bias. The 6L6's are driven by a 6P6 triode connected through a driver transformer incorporating feedback. This is preceded by a 6N7, electronic mixing for pick-up and microphone. The additional 6F5 operating as first stage on microphone only is suitable for any microphone. A tone control is fitted, and the large eight-section output transformer is available in three types—2-8-15-30 ohms; 4-15-30-60 ohms or 15-60-125-250 ohms. These output lines can be matched using all sections of windings and will deliver the full response (40-18,000 c/s) to the loudspeakers with extremely low overall harmonic distortion.

- CHASSIS with valves and plugs £17 10 0
- Or complete in black leatherette cabinet with Collaro turntable, Piezo P.U. and shielded Mike Transformer £22 10 0
- Goodmans P.A. Speakers in stock.
- Reslo Horns £11 11 0
- Reslo M.C. Microphones £3 15 0
- Amperite Ribbon Microphones from £5 5 0

All P.A. and A.R.P. Warning Gear in stock.
Write for Illustrated Catalogue.
**Vortexion Ltd., 182, The Broadway,
Wimbledon, S.W.19. Phone: LIBerty 2814.**

Short-wave Stations of the World

Arranged in Order of Frequency and Wavelength

Station	Call Sign	Mc's.	Metres	kW	Station	Call Sign	Mc/s.	Metres	kW
Moscow (U.S.S.R.)	RIA	5.85	51.24	15	Huizen (Holland)	PHI	11.73	25.58	20
Moscow (U.S.S.R.)	RNE	6.00	50.00	20	Oslo (Norway)	LKQ	11.73	25.56	5
Zeesen (Germany)	DJC	6.02	49.83	5-40	Boston (U.S.A.)	WRUL	11.73	25.56	20
Moscow (U.S.S.R.)	RW96	6.03	49.75	100	Vatican City	HVJ	11.74	25.55	25
Vatican City	HVJ	6.03	49.75	25	Warsaw (Poland)	SP25	11.74	25.55	5
Boston (U.S.A.)	WRUL	6.04	49.67	20	British Oversea Service	GSD	11.75	25.53	10-50
British Oversea Service	GSA	6.05	49.59	10-50	Rome (Italy)	I2RO15	11.76	25.51	—
Philadelphia (U.S.A.)	WCAB	6.06	49.50	10	Zeesen (Germany)	DJD	11.77	25.49	5-40
Motala (Sweden)	SPO	6.06	49.46	12	Boston (U.S.A.)	WRUL	11.79	25.45	20
Zeesen (Germany)	DJN	6.08	49.35	5-40	Zeesen (Germany)	DJO	11.80	25.42	5-40
Bound Brook (U.S.A.)	WNBI	6.10	49.18	25	Rome (Italy)	I2RO4	11.81	25.40	100
British Oversea Service	GSL	6.11	49.10	10-50	British Oversea Service	GSN	11.82	25.38	10-50
Wayne (U.S.A.)	WCBX	6.12	49.02	10	Wayne (U.S.A.)	WCBX	11.83	25.36	10
Sinkiang (Manchukuo)	WYCY	6.12	49.02	—	Lisbon (Portugal)	CSW5	11.84	25.34	10
Pittsburgh (U.S.A.)	WPIT	6.14	48.86	28	Zeesen (Germany)	DJP	11.85	25.31	5-40
Winnipeg (Canada)	CJRO	6.15	48.78	2	Budapest (Hungary)	HAD	11.85	25.31	—
Wayne (U.S.A.)	WCBX	6.17	48.62	10	British Oversea Service	GSE	11.86	25.29	10-50
Vatican City	HVJ	6.19	48.47	25	Madras (India)	VUM2	11.87	25.28	10
Rome (Italy)	IAC	6.35	47.21	50	Pittsburgh (U.S.A.)	WPIT	11.87	25.26	24
Radio-Nations (Switzerland)	HBQ	6.67	44.94	20	Melbourne (Australia)	VLB3	11.88	25.25	2
Barcelona (Spain)	EAQ1	7.03	42.7	—	Radio-Mondial (France)	TPA11/12	11.88	25.24	12
Valladolid (Spain)	FET1	7.07	42.43	0.25	Chungking (China)	XGOY	11.90	25.21	35
Burgos (Spain)	EAIBO	7.07	42.43	—	Moscow (U.S.S.R.)	RNE	12.00	25.00	20
Lisbon (Portugal)	GSW8	7.26	41.32	10	Warsaw (Poland)	SPW	13.63	22.00	10
Radio-Mondial (France)	TPB7/11	7.28	41.21	25	Radio-Nations (Switzerland)	HPJ	14.54	20.64	20
Moscow (U.S.S.R.)	RWG	7.36	40.76	15	Rome (Italy)	IQA	14.79	20.28	—
Moscow (U.S.S.R.)	RKI	7.51	39.89	25	Moscow (U.S.S.R.)	RKI	15.04	19.95	25
Budapest (Hungary)	HAT4	9.12	32.88	5	Rome (Italy)	I2RO12	15.10	19.87	—
Radio-Nations (Switzerland)	HBL	9.34	32.1	20	Zeesen (Germany)	DJL	15.11	19.85	5-40
Ankara (Turkey)	TAP	9.46	31.70	20	Vatican City	HVJ	15.12	19.84	25
Belgrade (Yugoslavia)	YUC	9.50	31.56	10	Warsaw (Poland)	SP19	15.12	19.84	5
Lahti (Finland)	OED	9.50	31.58	1	Radio-Mondial (France)	TPB6	15.13	19.83	25
Belgrade (Yugoslavia)	YUC	9.50	31.56	—	British Oversea Service	GSF	15.14	19.82	10-50
Melbourne (Australia)	VK3ME	9.51	31.55	5	Motala (Sweden)	SPT	15.15	19.80	12
British Oversea Service	GSB	9.51	31.55	10-50	Tokio (Japan)	JZK	15.16	19.79	50
Moscow (U.S.S.R.)	RW96	9.52	31.51	100	Oslo (Norway)	LKV	15.17	19.78	5
Warsaw (Poland)	SP31	9.52	31.49	5	Moscow (U.S.S.R.)	RW96	15.18	19.76	100
Schenectady (U.S.A.)	WGEO	9.53	31.48	100	British Oversea Service	GSO	15.18	19.76	10-50
Calcutta (India)	VUC2	9.53	31.48	10	Lahti (Finland)	OED	15.19	19.75	1
Tokio (Japan)	JZI	9.53	31.46	50	Zeesen (Germany)	DJB	15.20	19.74	5-40
Motala (Sweden)	SRU	9.53	31.46	12	Ankara (Turkey)	TAQ	15.20	19.74	20
Vatican City	HVJ	9.55	31.41	25	Pittsburgh (U.S.A.)	WPIT	15.21	19.72	18
Schenectady (U.S.A.)	WGEA	9.55	31.41	20-25	Lisbon (Portugal)	CSW4	15.21	19.72	10
Bombay (India)	DUB2	9.55	31.40	10	Huizen (Holland)	PCJ2	15.22	19.71	60
Zeesen (Germany)	DJA	9.56	31.38	5-40	Podebrady (Bohemia)	OLB5A	15.23	19.70	15-30
Millis (U.S.A.)	WBOS	9.57	31.35	10	Rome (Italy)	I2RO14	15.23	19.70	—
British Oversea Service	GSC	9.58	31.32	10-50	Radio-Mondial (France)	TPA2	15.24	19.68	12
Melbourne (Australia)	VLB	9.58	31.32	2	British Oversea Service	GSI	15.26	19.66	10-50
Sydney (Australia)	VK2ME	9.59	31.28	20	Wayne (U.S.A.)	WCBX	15.27	19.65	10
Huizen (Holland)	PCJ	9.59	31.28	60	Philadelphia (U.S.A.)	WCAB	15.27	19.65	10
Philadelphia (U.S.A.)	WCAB	9.59	31.28	10	Schenectady (U.S.A.)	WGEA	15.27	19.65	20-25
Delhi (India)	VUD2	9.59	31.28	10	Zeesen (Germany)	DJQ	15.28	19.63	5-40
Athlone (Ireland)	—	9.59	31.27	—	Delhi (India)	VUD4	15.29	19.62	10
British Oversea Service	GRY	9.60	31.25	10-50	Buenos Aires (Argentina)	LRU	15.29	19.62	7
Moscow (U.S.S.R.)	RAL	9.60	31.25	20	Rome (Italy)	I2RO6	15.30	19.61	50
Cape Town (S. Africa)	ZRL	9.61	31.22	5	British Oversea Service	GSP	15.31	19.60	10-50
Oslo (Norway)	LLG	9.61	31.22	5	Schenectady (U.S.A.)	WGEA	15.33	19.57	20-25
Zeesen (Germany)	DXB	9.61	31.22	5-40	Zeesen (Germany)	DJR	15.34	19.56	5-40
Budapest (Hungary)	HAD	9.62	31.17	—	Budapest (Hungary)	ILAS3	15.37	19.52	5
Rome (Italy)	I2RO3	9.63	31.15	25-100	Moscow (U.S.S.R.)	RAL	15.15	19.35	15
Wayne (U.S.A.)	WCBX	9.65	31.09	10	Oslo (Norway)	LKW	17.75	16.90	5
Lisbon (Portugal)	CS2WA	9.65	31.09	2	Zeesen (Germany)	DJE	17.76	16.89	5-40
Vatican City	HVJ	9.66	31.06	25	Huizen (Holland)	PHI	17.77	16.88	20
Buenos Aires (Argentina)	LRX	9.66	31.06	7	Bound Brook (U.S.A.)	WNBI	17.78	16.87	35
Rome (Italy)	I2RO9	9.67	31.02	25	Tokio (Japan)	JZL	17.78	16.87	50
Zeesen (Germany)	DJX	9.67	31.02	5-40	British Oversea Service	GSG	17.79	16.86	10-50
Bound Brook (U.S.A.)	WRCA	9.67	31.02	35	British Oversea Service	GSV	17.81	16.84	10-50
British Oversea Service	GRX	9.69	30.96	10-50	Rome (Italy)	I2RO8	17.82	16.84	50
Buenos Aires (Argentina)	LRA1	9.69	30.96	7	Wayne (U.S.A.)	WCBX	17.83	16.83	10
Lisbon (Portugal)	CSW7	9.74	30.80	10	Athlone (Ireland)	—	17.84	16.82	—
Rome (Italy)	IRF	9.83	30.52	30	Radio-Mondial (France)	TPB3	17.85	16.81	25
Madrid (Spain)	EAQ	9.86	30.43	10	Radio-Nations (Switzerland)	HHB	18.48	16.23	20
Buenos Aires (Argentina)	LSX	10.35	28.99	12	Zeesen (Germany)	DJS	21.45	13.99	5-40
Lisbon (Portugal)	CSW6	11.04	27.17	10	British Oversea Service	GSH	21.47	13.97	10-50
Radio-Nations (Switzerland)	HBO	11.40	26.31	20	Schenectady (U.S.A.)	WGEA	20.50	13.95	20-25
Warsaw (Poland)	SPD	11.53	26.01	2	Rome (Italy)	I2RO16	21.52	13.94	—
Rome (Italy)	IQY	11.67	25.70	—	Philadelphia (U.S.A.)	WCAB	21.52	13.94	10
Motala (Sweden)	SBP	11.70	25.63	12	British Oversea Service	GSJ	21.53	13.93	10-50
Moscow (U.S.S.R.)	IRA	11.71	25.62	15	Pittsburgh (U.S.A.)	WPIT	21.53	13.93	6
Radio-Mondial (France)	TPA4	11.72	25.60	12	British Oversea Service	GST	21.55	13.92	10-50
Winnipeg (Canada)	CJRX	11.72	25.60	2	Wayne (U.S.A.)	WCBX	21.57	13.91	10

Recent Inventions

Brief descriptions of the more interesting radio devices and developments disclosed in Patent Specifications will be included in these columns.

A NOVEL WIRELESS SET

A SUPERHET is built to resemble a standard reading lamp. The first section, comprising the mixer stage, is located in the base. The IF stage is housed inside the vertical column or stanchion of the lamp, while the AF amplifier, power pack and loud speaker are situated inside the shade. The tuning controls are mounted around the base, which also contains the variable tuning condensers.


D. J. Crowley. Convention date (U.S.A.), December 4th, 1936. No. 512141.

o o o o

THERMIONIC AMPLIFIERS

THE performance of a grid-controlled amplifier can be improved by passing the primary stream through an electron multiplier before it reaches the anode, the secondary current so produced serving to increase the mutual conductance between grid and anode. It is found, however, that there is a tendency for the multiplying action to fall off, as time goes on, this being due, it is thought, to the action of the barium atoms emitted from the coated cathode on the sensitised surface of the target electrodes.

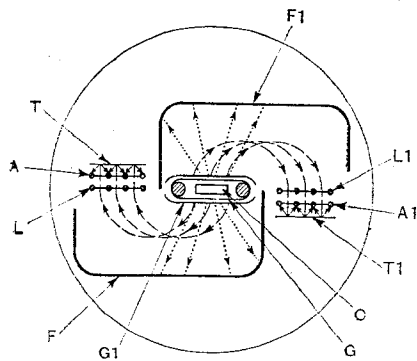The invention seeks to prevent this deterioration by using a valve of the construction shown in cross-section in the accompanying diagram, and by applying to it an external magnetic field which forces the primary stream of electrons to travel from the cathode C and grids G, G1 in the curved path shown in



Electron multiplier construction.

dotted lines. At the end of this path, they pass through "lens" grids L, L1 and open anodes, A, A1 on to "target" electrodes T, T1, the resulting stream, amplified by secondary emission, being finally collected by the anodes. Curved field-plates F, F1 prevent any barium atoms emitted by the cathode C from reaching and so damaging the sensitive target electrodes. Actually the barium

atoms take the straight line paths shown in dotted lines.

Marconi's Wireless Telegraph Co., Ltd. and G. B. Banks. Application dates February 17th and June 21st, 1938. No. 511449.

o o o o

CUTTING OUT ELECTRICAL INTERFERENCE

A KNOWN method of tackling the problem of interference is to throw the receiving circuits out of action, both for signals and interference, so long as the latter is present. Since interference usually takes the form of highly damped impulses which last less than the rooth part of a second, the effect of the interruption is not noticeable to a listener, the signals appearing to come through continuously and without break. According to the invention, the interfering impulses are applied in such a way that they paralyse the local oscillator of a superhet, and so interrupt reception for a fractional part of a second.

The figure shows a local oscillator V, which is coupled to a separate modulating valve M through a resistance R and condenser C, the modulator being coupled to the first IF stage in the usual manner. An interfering impulse, after rectification, applies a paralysing bias to the grid G via the lead L, and so momentarily throws this valve out of action, thus breaking the continuity of the signals fed to the loud speaker for the duration of the disturbing impulse.

Magyar Wolframlamp Co. Convention date (Hungary) September 21st, 1937. No. 511329.

o o o o

INTERFERENCE IN TELEVISION RECEIVERS

ONE effect of interference, especially local disturbances, upon a television receiver is to produce objectionably bright flashes or spots on the picture; another is to upset the proper focusing of the scanning spot, so that it "spreads" and causes distortion.

According to the invention, both sources of trouble can be prevented by inserting a shunt circuit, consisting of a diode rectifier and a condenser, across the load circuit of the first detector.

When a disturbing impulse arrives, the shunt diode becomes conductive, and so by-passes most of the disturbance into the condenser. In other words, it acts as a "limiter" to prevent the interference from creating any undesirably large modulating potential.

Kolster-Brandes, Ltd.; C. N. Smyth; and R. J. Berry. Application date, February 18th, 1938. No. 511519.

o o o o

SOUND-REPRODUCING DIAPHRAGMS

A DIAPHRAGM, suitable for a telephone, microphone, or moving-coil loud-speaker is made of solidified cellulose "foam."

This material may be produced from cellulose by a fermenting process, or by blowing air through it, or by mixing it with any gas-producing substance. The product has a microscopically fine cellular structure, with a density of 0.1 gramme per cubic centimetre, and sufficient rigidity for the purpose in view.


The solidified foam, after being cut out to the required shape is cemented to a thin backing sheet of aluminium foil, the protruding edges of which are first crinkled or corrugated to increase resilience, and are then clamped to a peripheral support.

H. Sell. Convention date (Germany) December 18th, 1937. No. 513289.

o o o o

SMOOTHING IN TRANSMITTER CIRCUITS

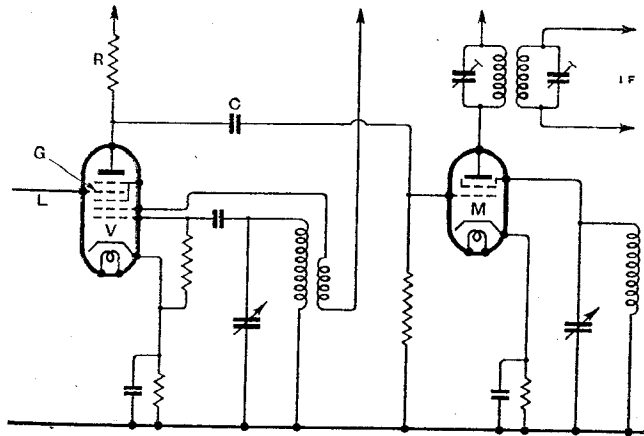IN a high-powered radio transmitter, where power is supplied from a common rectifier or DC source to the final stage of a class B modulator, it is found that at certain low frequencies the smoothing elements in the supply line develop an "anti-resonance" effect



Auto-suppression circuit for electrical interference.

Recent Inventions—

which causes a pronounced distortion of the transmitted signal. The reason is that the power source and filter present a high impedance, of some thousands of ohms at the frequency in question, to the modulator, thus forming, in effect, an unwanted modulation circuit which reacts upon the output fed to the transmitting aerial.


According to the invention, a transformer is included in the DC supply line, the primary winding of which consists of the usual series choke coil, while the secondary winding is short-circuited by a resistance. This prevents large changes of impedance in the smoothing circuit and power source, and so avoids the low-frequency distortion in question.

Marconi's Wireless Telegraph Co., Ltd., and H. Cafferata. Application date March 4th, 1938. No. 513164.

o o o o

VISUAL TUNING INDICATORS

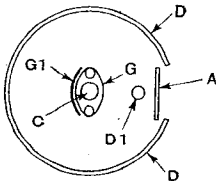RELATES to the type of "glow" indicator in which a long cathode is surrounded by a helical control grid



Increasing brightness of tuning indicator.

type of indicator the anode is usually arranged with the fluorescent surface facing the cathode, so that the glow is to some extent obscured because both the grid and cathode come between it and an observer.

The difficulty is avoided by constructing the glow tube in the way shown in cross section. The cathode C is surrounded by a spiral grid G, of varying pitch, the side farthest from the anode A being blocked by a solid sheet G1. One of the deflecting electrodes D is in the shape of a cylinder, which is gapped, as shown, to enable the fluorescent anode A to be clearly seen. The other deflecting electrode consists of a rod D1 which is placed between the anode and the grid. The arrangement ensures that at least the greater part of the electron stream strikes the anode A on the side turned away from the cathode and facing the observer.

The M-O Valve Co., Ltd. and H. S. Smith. Application date May 20th, 1938. No. 511386.

o o o o

PRESS-BUTTON TUNING

IN some press-button tuning systems, if the listener attempts to use the manual tuning control while one of the selecting buttons is still depressed, he is liable to strain or damage the driving motor; in addition, a disagreeable "chatter" or vibrating movement is imparted to the tuning knob.


Both these defects are avoided by using an arrangement in which, directly the motor has brought the tuning condenser into a position corresponding to the wavelength of the selected station, the motor circuit is automatically opened, and remains so, until another selector button is depressed, irrespective of whether the manual control knob has meanwhile been operated or not. In this way it becomes impossible to start-up the driving motor inadvertently, except in the very unlikely event of the listener operating both selector button and the manual tuning knob simultaneously.

E. K. Cole, Ltd., and A. W. Martin. Application date, February 18th, 1938. No. 511503.

o o o o

THE figure shows an arrangement for increasing the precision of a press-button tuning system in which the variable elements are motor-driven. The spindle S of the tuning condenser C is geared at G to the motor M, and is also connected to the contact-making spindle K1 through gearing G1. The latter is made proof against backlash by using double gear-wheels, which are urged by a spring in opposite directions.

The contact drum D is made in two parts separated by a strip P of insulation. Its spindle K1 carries a worm gear G2, which engages with a fixed nut N, so that the drum D is moved longitudinally as it rotates. This causes the brush B (which is operated by the station-selecting button not shown) to move over the drum D in a spiral path, so that it intersects the insulating strip P at an angle, thereby increasing the effectiveness of the "break" required to arrest the tuning condenser C and the

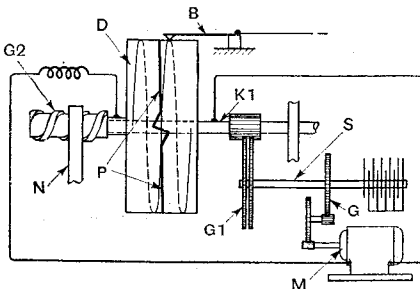

Device for increasing precision of press-button tuning.


driving motor M, at the required tuning point. The ratio of the gearing G1 is such that the brush B makes more than one traverse over the drum for each complete rotation of the tuning condenser.

Murphy Radio, Ltd., J. D. A. Boyd, and L. Fisher. Application date March 16th, 1938. No. 512730.

PHOTO-ELECTRIC AMPLIFIERS

A PHOTO-ELECTRIC cell P is coupled to an amplifying valve V by a circuit which contains no reactive elements, this being particularly desirable when handling television signals. The necessary anode potential for operating the photo-electric cell is de-

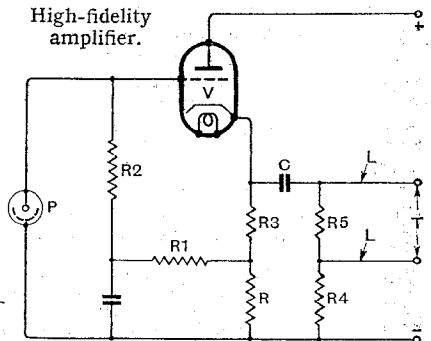veloped across a resistance R in the anode-cathode circuit of the amplifier, and is applied through the series resistances R1, R2, the anode of the cell being directly connected to the grid of the amplifier. Grid bias for the grid of the amplifier is supplied by the resistance



R3, the output being taken from the terminals T through a blocking condenser C.

The resistance R4 is small compared with the resistance R5, and is used to balance out disturbing potentials produced in the line LL, by feeding back to it a corresponding voltage applied in phase opposition.

Baird Television Ltd., and P. E. A. R. Terry. Application date, March 4th, 1938. No. 512327.

o o o o

INTERLACED SCANNING

IT is essential with interlaced scanning to ensure strict timing between the line and frame frequencies, as otherwise successive frames do not fit together accurately. In practice there is a tendency for the line impulses to trigger the frame oscillator prematurely, and the object of the invention is to avoid this.


The mixed signals are applied to an input valve which separates the picture signals from the two sets of synchronising impulses. The line impulses are transferred through a condenser and a transformer coupling to the line oscillator, whilst the slower framing impulses are coupled to their oscillator through a branch circuit which includes a resistance, in series with the coupling coil to the line oscillator and a diode rectifier.

The arrangement is such that any impulses that appear across the resistance and tend to trigger the frame oscillator prematurely are automatically balanced by corresponding impulses from the line oscillator applied to the resistance in opposite phase.

Baird Television, Ltd., and D. V. Ridgway. Application date March 15th, 1938. No. 512795.

The British abstracts published here are prepared with the permission of the Controller of H.M. Stationery Office, from specifications obtainable at the Patent Office, 25, Southampton Buildings, London, W.C.2, price 1/- each.

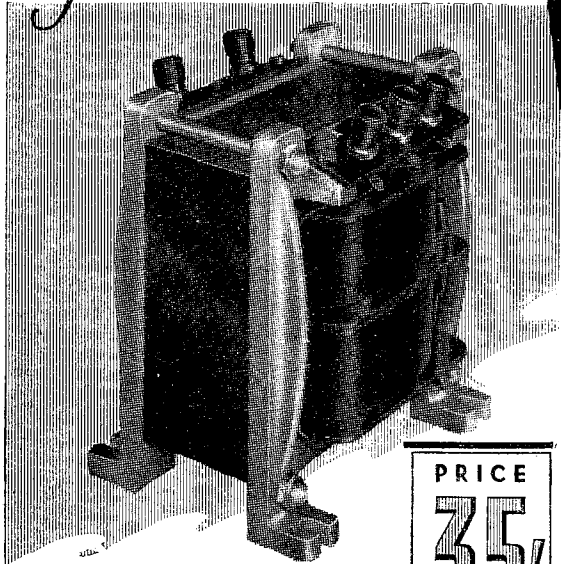...for the **HIGHEST GRADE Loudspeakers**




Size: 3" x 3 1/2" x 4 3/4" high. Net Weight: 5 lbs.
 May we help you with your transformer problems?

(Designed for individual requirements. When ordering, state valves and secondary impedance.)

GOODMANS INDUSTRIES, LTD.
 Lancelot Rd., Wembley, Middx. Phone: WEMbley 4001 (5 lines)

PRICE
35/6

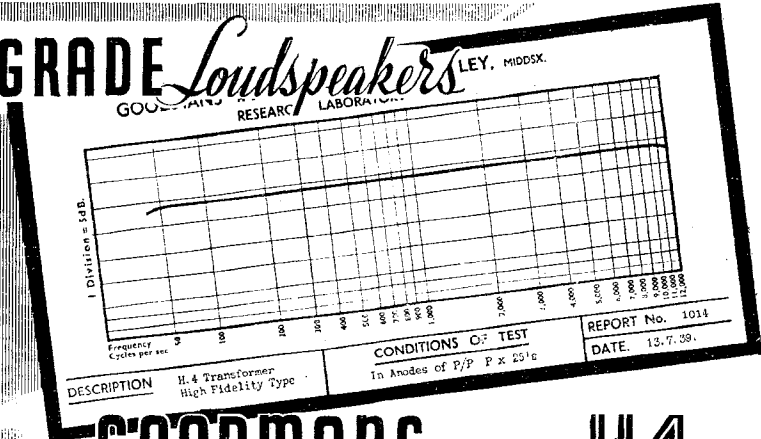

GOODMANS TYPE H4


HIGH-FIDELITY Output Transformer for A.C. powers up to 15 watts

The H.4 Output Transformer has been specially developed for use with High Fidelity equipment. A generous cross section of high grade silicon iron, specially treated to minimize skin losses at the high frequencies, ensures low harmonic distortion at A.C. powers up to 15 watts. The primary and secondary windings are fully sectionalized to reduce self capacity and leakage inductance to a minimum. Although the primary inductance is approximately 50 Henries, the D.C. resistance of each half is only 95 ohms, so that assuming the output valves pass 60 M/A each, the voltage drop will be approximately 6 volts. This transformer can be used with Triodes, Pentodes or Beam Tetrodes, in class A or A.B., push-pull circuits. With anode to anode impedances not exceeding 10,000 ohms, and the secondary to match line or speech coil impedances up to 1,000 ohms, the frequency response will be linear within + or - 1 db. from 40 c.p.s. to 12,000 c.p.s.

The **International**
 for **WORLD WIDE RECEPTION**

For a long time we wondered what was the outstanding thing we could do that would put radio on a different basis. We collated opinion from all over the world and there appeared to be one great want in the minds of the most discerning people—the ability to listen easily and under ideal conditions to practically any station in the world, no matter where you happen to be located.

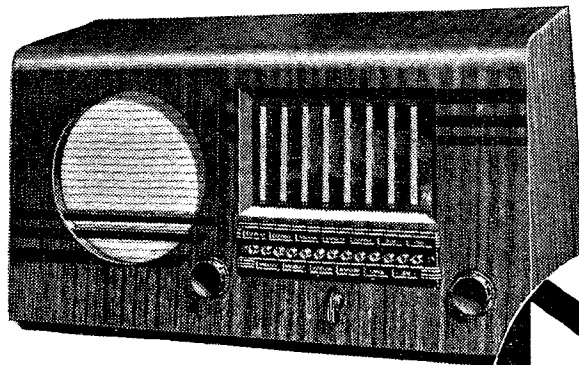For a year, in our laboratories, we sifted this problem as hard as we could, and the outcome of a great technical effort is The International Receiver.



MODEL INTERNATIONAL.—8-waveband A.C. mains Superhet with bandsread tuning, 10" moving coil speaker. 6 watts output. Over 117 short-wave stations tuned by name. Wavelengths: 13.7-14.2, 16.5-17.1, 19.4-20.1, 24.8-25.8, 30.6-31.9, 48-50, 180-560, 850-2,000 metres. Selective inverse feed-back. Sockets for gramophone pick-up and extension speaker. Dimensions of cabinet: 25 x 13 1/2 x 11 1/2 ins. Hire purchase terms available. Price **16 1/2 Gns.**



**Wireless
World**

CLASSIFIED ADVERTISEMENTS

THE CHARGE for advertisements in these columns is 12 words or less 3/-, 3d. for every additional word. Each paragraph is charged separately.

ADVERTISEMENTS, with remittance, should reach Dorset House, Stamford Street, S.E.1, not later than first post Thursday, February 8th, for the March issue, or one day earlier at the Branch Offices, 8-10, Corporation Street, Coventry; Guildhall Buildings, Navigation Street, Birmingham, 2; 280, Deansgate, Manchester, 3; 265, Renfield Street, Glasgow, C.2.

SERIES DISCOUNTS are allowed to trade advertisers on orders for consecutive insertions provided a contract is placed in advance, and in the absence of fresh instructions the entire copy is repeated from the previous issue. 3 insertions, 5 per cent.; 6 ins., 10 per cent.; 12 ins., 15 per cent.

Advertisements received too late for one issue, or crowded out, are published in the first following in which there is space. The Proprietors retain the right to refuse or withdraw advertisements at their discretion.

The Proprietors are not responsible for clerical or printers' errors, although every care is taken to avoid mistakes.

BOX NO. ADVERTISERS should include the words "Box 000 c/o 'The Wireless World'" which must be paid for. An additional 6d. is charged for registration and cost of forwarding replies.

ARMSTRONG


WE, YOU AND THE WAR

Who would have thought when war was declared that we (you and us) would have been carrying on, more or less normally, four months later? There have been many difficulties on our side such as the loss of staff to the Services, shortage of material (as Government demands must, of course, be met first) and this affects you when it comes to delivery. Without your friendly co-operation and consideration our worry would have been doubled and we are indeed grateful for the help you have given us. A tangible proof of our appreciation is that we have increased our prices by only 5 per cent., and this, not until after three months trading at pre-war prices. We would like to assure you that we will not take advantage of conditions to increase our prices above the bare necessary rise in cost of material. Under all circumstances we intend to maintain our fundamental policy of Fair Trading and the hard-won reputation which we enjoy.

If you haven't seen our Illustrated Art Catalogue describing our full range, drop us a card and we will send one along

**MODEL SS10 — 10-V SUPERHET-STRAIGHT!
ALL-WAVE HIGH-FIDELITY R-G CHASSIS**

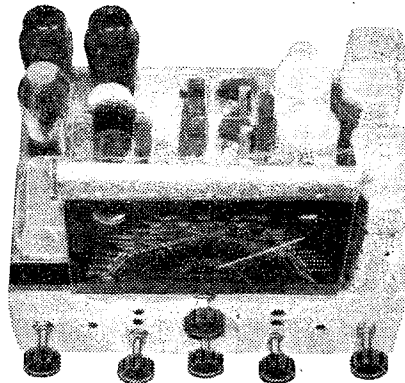Incorporating Two Independent Circuits, Superheterodyne and Straight, having R.F. Pre-amplifier and R.C. Coupled Push-Pull Triode Output capable of handling 8 watts.



The circuit of the SS10 is unique. When used as a STRAIGHT receiver two H.F. stages are in operation with A.V.C. Diode Detector is used for distortionless detection together with Triode Push-Pull output. A turn of only one knob is necessary to switch from "Superhet" to "Straight." The Gramophone **12** gns Amplifier has been specially studied and **12** gns records can be reproduced with excellent quality, plus 5%

MODEL AW38—8-V ALL-WAVE SUPERHET

This radiogram chassis has R.C. Coupled Push-Pull Output capable of handling 6 watts. This being our Quality Year we have carefully studied the design of our more economically priced **8** gns. models and it's now possible to obtain **8** gns. excellent quality with economyplus 5%

MODEL AW125PP—12-V 5-BAND ALL-WAVE R-G CHASSIS (12-550 continuous, 1000-2000 m)

with R.F. Pre-Amplifier, 2 I.F. stages with Variable Selectivity. Manual R.F. gain control and 10 watts R.C. coupled Triode P.P. Output.

Readers need no introduction to this most **17** gns. popular model, so favourably reviewed by *The Wireless World* on Jan. 5th, 1939. plus 5%

**7 DAYS' APPROVAL—12 MONTHS' GUARANTEE
ARMSTRONG MANUFACTURING CO.**

WALTERS ROAD, HOLLOWAY, LONDON, N.7
(Adjoining Holloway Arcade.) Phone: NORTH 3213.

Letters addressed to Box Nos. are simply forwarded to the advertiser. No responsibility is accepted in connection with these advertisements.

DEPOSIT SYSTEM. Readers may deal with advertisers in safety through our Deposit System. Purchase money payable to Hiffe & Sons Ltd. should be deposited with "The Wireless World," when both parties are advised of its receipt.

The time allowed for decision is three days, counting from receipt of goods, after which period, if buyer decides not to retain goods, they must be returned to sender. If a sale is effected, buyer instructs us to remit amount to seller, but if not, seller instructs us to return amount to depositor. Carriage is paid by the buyer, but in the event of no sale, and subject to there being no difference arrangement between buyer and seller, each pays carriage one way. The seller takes the risk of loss or damage in transit, for which we take no responsibility. For transactions up to £10 a deposit fee of 1/- is charged; over £10 and under £50, 2/6; over £50 and under £75, 5/-; over £75 and under £100, 7/6; over £100 one-half per cent. All correspondence must be sent to Dorset House, Stamford Street, London, S.E.1.

Cheques and Postal Orders sent in payment for deposits or advertisements should be made payable to Hiffe & Sons Ltd. and crossed. Notes cannot be traced if lost in transit. They must therefore be regarded as being despatched at sender's risk. Alternatively, they may be sent per registered post.

NEW RECEIVERS AND AMPLIFIERS

A. CHALLENGER RADIO CORPORATION the best firm for reliable, fully guaranteed ultra short-wave radio, have on view in London without exception the finest receivers ever made; for instance, a 5-valve T.R.F. Midget (2 bands) at 75/-; a mains/battery transportable (operating without alteration to A.C., D.C. or batteries), at £8, a 13-valve receiver, 5 bands, 5-2,100 metres, is only £16; any American valve for receivers 1925-40 for 5/6 each, only firsts such as Rathbone Ken-rad, etc., supplied; they have a range like this right up to an 18-valve Challenger Twin Chassis De Luxe, valves and 12in. public address speaker (weight 23lb.), at £29/10; why not call and handle these receivers at your leisure? No obligation to purchase; or handsome, profusely illustrated catalogues forwarded on receipt of 1/2d. stamp; sale list of 1939 receivers also available.

CHALLENGER RADIO CORPORATION, 31, Craven Terrace, London, W.2. Paddington 6492. Nearest point Marble Arch, down Bayswater Rd. turn 5th right. [8787]

A.C.S. RADIO, now at 46, Widmore Rd., Bromley (Ravensbourne 0156), for super all-wave and communication receivers and amateur radio needs; part exchanges; easy payments [8799]

AMBASSADOR Offer 50 only 5 Valve Three-band A.C. Receivers, chassis complete with Mazda valves and 8in. speaker, brand new stock, factory tested before despatch; £6/5 each; cash with order.—R. N. Fitten, Ltd., Hutchinson Lane, Brighouse, Yorks. [8819]

COMMUNICATION RECEIVERS

THE Famous Hallicrafter SX23, released by the makers only in July, 1939, can still be supplied by Webb's Radio at

PRE-WAR Prices.

WE Fortunately Had Good Supplies Delivered in August; no price increase on present stock of this model only £33/10; 11/2 terms available; write for descriptive folder.—W. Webb's Radio, 14, Soho St., London, W.1. Phone: Gerrard 2089. [8818]

RECEIVERS AND AMPLIFIERS CLEARANCE, SURPLUS, ETC.

BANKRUPT Bargains.—Brand new 1938-9 models, makers' sealed cartons, with guarantees, at less 40% below listed prices; also portables and midget radio; send 1/2d. stamp for lists.—Radio Bargains, Dept. A.W., 261-3, Lichfield Rd., Aston, Birmingham. [8735]

USED SETS FOR SALE

MURPHY

A 56V Television Console, as new; offers; Belling-Lee aerial.—33, Byron Rd., Earley, Reading. [8831]

PHILIPS

P PHILIPS 228B Battery Portable, cost 9½ gns., accept 6 gns.; Columbia portable gramophone, 30/-; both new and unused; no longer required owing to change of plan.—Lindsay, 47, Queen's Rd., Bradford. [8797]

PYE

P PYE International, new Dec., 1939, cost 16½ gns.; £14 cash.—Jackson, 54, Prince's St., Stockport. [8822]

S.T.

S.T. 900 Receiver, built from genuine Author kit, 10 coils, little used, lovely condition; best offer.—Lambert, Photographer, Bury St, Edmunds [8807]

MISCELLANEOUS

A.C.S. RADIO, 46, Widmore Rd., Bromley, offer bargains in reconditioned Scott, McMurdo Silver, and various allwave and communication receivers. [8800]

Wanted

WANTED, Ferranti A.F.7c.—Shaull, 74, Valleyfield Rd., S.W.16. Streatham 5326. [8829]

WANTED, McMurdo Guthman U.17 Communication Receiver.—Box 1463, c/o *The Wireless World*. [8826]

COMMUNICATION Receiver, late model, Xtal, perfect.—Hosie, 94, Norway St., Waterlo, Liverpool. [8811]

WANTED, Hallicrafter SX17, complete with speaker, late model.—Box 1441, c/o *The Wireless World*. [8812]

EXCHANGE "W.W." Battery S.W.3 for "Sound" Auditorium P.M. Speaker, Goodmans, or Baker.—Box 1477, c/o *The Wireless World*. [8832]

WANTED for Cash, McMurdo, Scott or equivalent category radiogram, Console or chassis; full particulars to: Box 1462, c/o *The Wireless World*. [8827]

PUBLIC ADDRESS

"PARTRIDGE P.A. Manual," standard handbook on electro-acoustics, amplifiers, and audio circuits; price 2/6 (free to trade).

"PARTRIDGE Amplifier Circuits," describes many modern constructional amplifiers, 2w. to 45w. output, battery, A.C.-D.C., etc.; price 2/- (no free copies).

PARTRIDGE, N., B.Sc., A.M.I.E.E., King's Buildings, Dean Stanley St., London, S.W.1. [0630]

AMPLIFIERS, speakers, microphones, turntables and converters for hire and repairs departments.—Easco, 18, Brixton Rd., S.W.9. Phone: Rel. 1693. [0643]

PUBLIC ADDRESS

Partridge

DISTORTIONLESS OUTPUT TRANSFORMERS


12w. PUSH-PULL TYPE
any single ratio to order

38/6

The recent articles in the "Wireless World" disclosing methods of determining and reducing Harmonic Distortion in Output Transformers have aroused enormous interest amongst sound engineers. For the benefit of those who missed the series and for those who wish to have the articles in bound form for filing purposes, reprints are now available direct from:


N. PARTRIDGE, B.Sc., A.M.I.E.E.,
King's Buildings, Dean Stanley St.,
London, S.W.1.

*Phone: VICTORIA 5035.

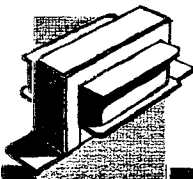

NOTE:—These reprints are costly and limited in number. All genuinely interested are welcome to copies, but please do not send for one out of curiosity alone.

Relax and let yourself go!

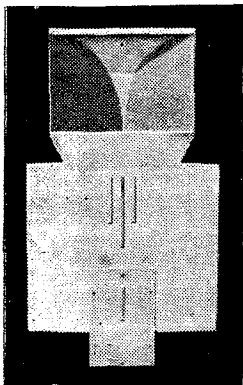

Illustrated is a Home Constructor's Corner Horn with Bass Chamber.

We are now experimenting with special-ised pickups.

THERE'S a world of wisdom at this time in the somewhat slangy words of the popular song.

Have you heard first-class modern records through suitable gear terminating in a "VOIGT" Loud-speaker?

Try it, it's a marvellous mental tonic!

Owing to the high efficiency of the "Voigt" Loudspeaker, 2 watts is enough for the home. For the informal dance, or the Works Canteen, a modest 10 watt amplifier is quite adequate.

Prices from £17-5-0 to £50

VOIGT PATENTS LTD.

THE COURTS SILVERDALE · LONDON · S.E.23
Telephone: SYDenham 6666
Regd. Office: 22, Castle Street, London, E.C.1

VORTEXION P.A. Equipment,

IMITATED, but unequalled.
WE Invite You to a Demonstration.

A.C.-D.C. Dance Band Amplifier, 10 watts output, complete in case, with moving coil microphone, speaker and cables weight 22lb., 12 gns.

A.C.-20 15-20-watt Amplifier, 58-18,000 cycles, independent mike and gram., inputs and controls, 0.037 volts required to full load, output for 4, 7.5, and 15 ohms speakers, or to specification, inaudible hum level, ready for use; 8½ gns. complete.

C.P. 20 12-volt Battery and A.C. Mains Model, as used by R.A.F., output as above; 12 gns.

A.C.-20, in portable case, with Collard motor, Piezo pick-up, etc., £14; C.P.20 ditto, £17/17.

50-WATT Output 6L6s, under 60-watt conditions, with negative feed back, separate rectifiers for anode screen and bias, with better than 4% regulation level response, 20-25,000 cycles, excellent driver, driver transformer, and output transformer matching 2-30 ohms impedance electronic mixing for mike and pick-up, with tone control, complete with valve and plugs; £17/10.

COMPLETE in Case, with turntable, B.T.H., Piezo pick-up and shielded microphone transformer; £22/10.

80-WATT Model, with negative feed back; £25, complete.

120-WATT Model, with negative feed back; £40, complete.

250-VOLT 250 m.a., Full Wave Speaker, field supply unit; 25/-, with valve.

ALL P.A. Accessories in Stock; trade supplied.

SEE Our Display Advertisement on Page 153.

VORTEXION, Ltd., 182, The Broadway, Wimbledon S.W.19. Phone: Lib. 2814. [8241]

NEW MAINS EQUIPMENT

VORTEXION Mains Transformers, chokes, etc., are supplied to G.P.O., B.B.C., L.P.T.B.; why not you?

VORTEXION, Ltd., 182, The Broadway, Wimbledon, London, S.W.19. Telephone: Liberty 2814. [8782]

SHORT-WAVE EQUIPMENT

G5NI for Short Wave Equipment; largest stocks in the country; communication receivers; National agents; American and British Valves, etc. See advertisement on page 2-44, Holloway Head, Birmingham.

"H.A.C." one-valve Short-wave Receiver, famous for over 5 years, now available in kit form; complete kit of precision components, accessories, full instructions, 12/6, post 6d., no soldering necessary; descriptive folder free on request.—A. L. Bacchus, 109, Hartington Rd., S.W.8. [8840]

NEW LOUD-SPEAKERS

BRAND New Speakers.
SAVE Pounds. 1½d. stamp for list of British and American P.A. speakers. Example: P.A. speaker with transformer, weight 21lb., incorporating curved cone; 52/-.

CHALLENGER RADIO CORPORATION, 31, Craven Terrace, London, W.2. Paddington 6492. [8789]

BAKERS' Brand New Surplus Speaker Bargains.

£9 Only.—Usual price £16; brand new corner horn speakers in beautifully finished polished walnut corner horn cabinet, frequency range 30-12,000 cycles, amazingly realistic reproduction.

£3/10—Usual price £6; brand new Baker magnet magnet speakers, as solely specified for the "Wireless World" Quality Four receiver.

45/-—Usual price £5; brand new Bakers super power permanent magnet speakers, ideal for use with Quality receivers, exceptional bargain.

65/-—Usual price £9; brand new Bakers permanent magnet speakers with new type infinite baffle, wide frequency range and exceptional transient response.

BAKERS SELHURST RADIO, The Pioneer Manufacturers, 75, Sussex Rd., South Croydon. [8725]

SECOND-HAND LOUD-SPEAKERS

18 IN. Epoch, 200 v., £3; 12 in. B.T.H. A.C. £2; or exchange P.M.—3rd Floor, 120, Drury Lane, W.C.2. [8830]

VOIGT Unit, twin diaphragm, as new; ½ list.—42, Glasbrydan, Uplands, Swansea. [8836]

EASY L-R-S TERMS

(or Cash as you prefer)

For first-class performance and highly efficient short-wave reception, excellent workmanship, the most reliable components with a super safety-factor margin to ensure years of service

You can't better an

ARMSTRONG QUALITY ALL-WAVE R-G CHASSIS

Thousands are made and sold every year but you never see them offered at reduced prices. There is no need because a good job is always in demand. The prices are reasonable—very reasonable—from 8 to 17 Gns. (plus only 5% war increase).

An outstanding example of Armstrong value is:—
Model 8S10. 10 v. Superhet-Straight R-G Chassis.
Price £13.4.0, or 45/- with order and 10 monthly instalments of 23/-.

Orders are executed in rotation so SEND TO-DAY for illustrated literature of all models with particulars of our convenient terms. (See Armstrong advt., p. 12.)

In addition to the Armstrong range, we shall be glad to quote for all other high-grade equipment, such as Sound Sales Amplifiers, Voigt Speakers, Haynes Radio, Avometers, and PORTABLE A.R.P. RECEIVERS.

ELECTRICAL APPLIANCES

This department—well known to readers—specialises in the supply of Electric Fires, Clocks, Irons, Fans, Vacuum Cleaners, in fact every device for the modern home, operated by electricity.

ALL ON OUR CONVENIENT TERMS

In accordance with our established policy we stock only lines of proved reliability. This is your guarantee of satisfaction backed by our 15 years advertising in the "Wireless World."

HARDSHIP IN THE SERVICES cannot be avoided

but there is one easily overcome. Ever shaved in the open air with no hot water, no cold water—only ice? Try it just once then you will appreciate the joy of a DRY-SHAVE with

VICEROY Non-Electric DRY SHAVER (Made by Rolls Razors Ltd.)

Send one to your friend serving at home or abroad. He will thank you every time he uses it. It's the handiest dry-shaver obtainable. Just press the lever and you get an amazingly smooth and comfortable shave—anywhere, at any time.

Complete in plush-lined case. Cash 2 Gns., or 10/- with order and 5 monthly payments of 7/-.

The New Sunbeam SHAVEMASTER Electric DRY SHAVER (Again available from stock)

Still the best Electric Shaver made The New "475" Comb and hollow-ground Cutter gives a closer and faster shave than ever. Operates on 100/200 v. A.C. or D.C.

Complete with resistor and adaptor in leather case, 4 Gns., or 10/- with order and 8 monthly payments of 10/-.

EITHER SHAVER SENT ON 14 DAYS APPROVAL

against cash, or on first instalment of 10/-. Should Shaver be returned, 7/6 will be refunded.

BRING YOUR SHAVER UP TO DATE

● The new "475" Comb and Cutter fits any old type Shavemaster. We can supply these heads from stock. 7/9 post free.

Write TO-DAY for illustrated particulars of the above

Evacuation address: Est. 1925
THE LONDON RADIO SUPPLY COMPANY
"Winden," Ardingly Road, Balcombe, Sussex

COMPONENTS—SECOND-HAND
CLEARANCE, SURPLUS, ETC.

R.
RADIO CLEARANCE, Ltd.
63 High Holborn, W.C.1. Phone: Holborn 4631.

FILAMENT Transformers, input 200-250 volts, output 4 volts, 4 amps., 4 volts 6 amps.; 4/11 each.

G.E.C. Mains Transformer, American windings, 350-0-350 volts, 65 m.a., 5 volts 2 amps., 6.3 volts 2.5 amp.; suitable for replacement in G.E.C. models; 5/6 each.

24 Mfd. Can Type Electrolytics, 450 volts working; 1/6 each.

T.U.C. 8 mfd. Can Wet Type Electrolytics, 450v. working; 1/3 each.

PRESS Button Units, with 6 press buttons, ready for wiring into set, with circuit; 6/11 each.

GRAMPIAN 10in. Moving Coil Speakers, 10 watt type, 15 ohm speech coil, 2,500 ohm field, 15/-; with Pentode output trans., 17/6.

STRANDED Push Back Wire, 1d. per yard.

CHASSIS Mounting Valve Holders, American, 4-5-6 and 7-pin, 4d. each; Octals, 6d. each; Locals, 10d. each; 7-pin English type, 3d. each.

ROTHERMEL Piezo Crystal Speakers, 7½in. cone. R list 55/-, our price 10/6 each; 10in. cone, 12/6 each.

POGAR N.S.F. 1 Watt Resistances, 4d. each, 3/9 dozen; all sizes up to 2 meg.

WEARITE Mains Transformers.—R.C.B. type, 350-0-350v. 80 m.a., 5 volt 2 amps., 6.3 volts 5 amps., 6/11.

TYPE R.C.4., 500-0-500v., 150 m.a., 4 volts 2 amps., 4 volts 2.5 amps., 4 volts 5.6 amps., 4 volts 2 amps.; 21/-.

PHILCO Mains Transformers, American windings, 350-350 volts, 65 m.a., 6 volts 3 amps., 5 volts 2 amps., 5/- each; ditto but 30 m.a., 6/6 each; ditto but 90 m.a., 7/6 each.

WEARITE 110 K./C. I.F. Transformers; 1/- each.

AMERICAN C.T.S. Volume Controls, finest made, divided spindles, length 2½in. with switch, 2,000, 5,000, 10,000, 25,000, 100,000, 2/6 each; wire wound, 5 watt (less switch), 10,000, 25,000 ohms; 2/- each.

R.K. Senior 12in. Energised Speakers, 20 watt type, 1,000 ohms field, 11 ohms speech coil, 32/6; with tapped transformer, 3,000 and 7,000 ohms, 35/-.

PLESSEY 2-gang Straight Condensers, ceramic insulated, 1/6; Plessey 3-gang straight condensers, ceramic insulated, 2/-.

PLESSEY Dry Electrolytics, can type, 12x16 mfd., 350 volts working, 1/6 each; 6x6 mfd., 500 volts working, 1/6 each; 450 volts working, 1/6 each; 8x8x8 mfd., 500 volts working, 2/11 each; 16x8x4x4 mfd., 500 volts working, 2/11 each; 12x8x8x8 mfd., 500 volts working, 2/11 each; 15 mfd., 450-volt working, 1/3 each.

B.L. Wire-end Type Bias Electrolytics, 50 mfd., 12 volts, 1/3 each; 50 mfd., 50 volts, 1/6 each.

TUBULAR Wire-end Non-inductive Paper, all sizes up to 0.1, 5d. each; 4/9 per dozen.

METAL Case, 1-hole fixing, electrolytic condensers, 550-volt working, 8 mfd.; 2/6 each.

STANDARD Telephone Headphones, resistance 2,000 ohms and 4,000 ohms; 6/11 per pair.

VOLUME Controls, 1,000 ohms, with switch; 1/3 each.

O.0005 3-gang Tuning Condenser Units, with trimmers; 2/11 each.

PLESSEY Energised Speakers, 10in. cone, 2,500 and 1,000 ohm field, with trans., 12/6 each; 6in. cone, 2,500 and 1,500 ohm field, 5/11 each.

RUBBER Grommets; 4d. dozen.

BATTERY Output Pentodes, well-known make; 3/11 each.

BATTERY Double Diode Triode, well-known make; 3/3 each.

RAYTHEON First Grade Valves, largest stockists, all types in stock, including glass series, glass octal series, metal series, bantam series, single-ended metal series, and resistance tubes, all at most competitive prices; send for valve lists.

ALL Orders Must Include Sufficient Postage to Cover.

HOURS of Business: 9 a.m.-6 p.m. week-days, Saturdays 9 a.m.-1 p.m.

RADIO CLEARANCE, Ltd., 63, High Holborn, London, W.C.1. Telephone: Holborn 4631. [8793]

**FOR
A
FIRST
CLASS**

**CHASSIS
RECEIVER**

OR

RADIO - GRAMOPHONE

**RELY
ONLY
ON**

AMBASSADOR

PRICES

FROM **£9 TO £30-10-0**

OBTAINABLE ALL OVER
THE WORLD.

FOR LITERATURE
SEND TO

R. N. FITTON LTD

AMBASSADOR RADIO WORKS

**HUTCHINSON LANE
BRIGHOUSE
YORKS**

'Phone - - - 283

COMPONENTS—SECOND-HAND
CLEARANCE, SURPLUS, ETC.

RYALL'S RADIO, 280, High Holborn, London, W.C.1, offer new goods, post free.

ELLIPTICAL Speakers, Celestion, suitable Ekco replacements, 750 ohms, less transformers, speech 25 ohms, new, handle 8 watts, carry up to 120 m.a.; 3/9 each to clear.

SPEAKERS, pairs, brand new, elliptical cone speakers, made by first class firm, quality of reproduction outstanding, push-pull pentode transformer, fields 325 ohm for smoothing choke, 8,600 as bleeder, circuit available, handle 10-15w.; 10/9 pair.

HEAVERY Duty Mains H.F. Chokes, Goltone, 75w. high inductance type, 1/6; 180w. low inductance type, 1/-.

MAINS Transformers, drop through chassis type, top cover with mains adjustment, input 200-250v., outputs 350-350, 80 m.a. 4v. 2½a., 4v. 4.5 amp., heavy jobs, 6/9 each.

REDUCTION Drives (epicyclic) Polar ex Ferranti, and Plessey, long or medium spindles, ratio 10:1; two for 1/3 or 3/9 dozen.

PLESSEY Fully Screened 2-gang Condensers, short spindles, with top trimmers, 2/9; Plessey mid-gate 2-gangs semi screened, 2/9; both 0005 straight type.

PLESSEY 3-gang Straight Type Condensers, top trimmers, fully screened, brand new, 2/9; Cossor 3-gangs ditto, 1/9, or 12/- dozen.

FERRANTI Air Core Type Tuning Coils, transformer wound, can be used as band pass, tuned grid with reaction, chassis type; three for 2/6, with coil connections.

I.F. Caps, Aii, size 1½x1¼x4in. high, complete with double trimmers, 4/9 dozen; Erie 60 ohm ½-watt resistances, 1/3 dozen; NSF 1 watt ¼ meg., 1/3 dozen; 600 ohm. wire wound 3 watt resistances, four for 1/3; Cornet-Dubilier mica, sizes 001, 002, 003, 1/3 dozen.

THIMBLE Top Caps, 24 for 1/3; clip on bulb holders, 12 for 1/3; volume controls, ½ meg. with switch, Morganic Stackpole, ex K.B., 1/9; Murphy type ½ meg. with D.P. switch, 1/9.

BBRITISH Type Magic Eye Valves, 4v. ¼a. heater, octal base, 3/3; UD2 super power 2v. valves, 2/3 each; similar Triotrons.

AMERICAN Washer Type 4 and 7 Pin Valve Holders, 2/3 dozen; British 5 and 7 pin VII, 2/6 dozen.

MAGNAVOX 7in. Cone Speakers (8in. overall), ribbed pattern, ideal replacement speakers, 2,000 ohms pentode transformers, 7/-, new; also R. & A. 2,500 ohm 7in. type speakers, pentode transformers, 7/9; Plessey 6,500 ohm. 8in. speakers, with pentode transformer, 6/6.

SATOR ½meg. Pots with Switch, 1/3 each, 7/9 dozen; 10,000 ohm broad base tone control type, less switch, 1/3 each, 6/9 dozen.

ELECTROLYTICS, B1, 20x20 mf. at 350v., 25x25v., two for 1/6; size 3in.x2¼in., B1 2x2x2, 400v. peak, 1/3 each, 9/- dozen; 25x25v., two for 1/6; Plessey 30x8x2, 300v. wkg., 1/6 each, 12/- dozen; TCC 8 mf. wet type 802 upright cans, 440v. wkg., 460v. peak, 1/9 each, 15/9 dozen.

U.S.A. Tubes, first grade, in sealed cartons; 80's 4/3, 6A7 4/9, 42 4/9.

SATOR 1,500v. Test Tubular Condensers, assorted, R equal numbers, 0.0002-3-5, 0.001, 0.03, 0.05, 0.002-3, mica; all at 50 for 2/6.

ASSORTED Resistances, 50 for 2/6; 1-watt carbon, U.S.A. make, reasonable assortment given, sizes approx. 450-12,000-17-60-70-90-120 thousand ohms.

SYSTOFLEX ½, mm., ½ gross, 5/-; twin screened 2x14-36, British made, 12 yards, 2/6; minimum quantities.

REX Type Switches, 4B, 2P, 4w., with shorting plate on 5 switches, 2/6 each, length 7in., spindle 2in.; ditto, 3w. 4P. 3B., 1/6; 3w. 3P. 3B., with shorting plate, 1/6; 3w. 2P. 4B., 1/6; any combinations of this item supplied; screens, 3in.-¾in.x3in.-¾in., 5 for 1/3.

TRIMMERS on Porcelain Plessey, double and single, 50-100-200-160 ohm. approx.; 50 for 2/6; special price quantities.

CLIX Valve Holders, 5-pin and 7-pin antimicrophonic type, 3 for 1/6; 7-pin circular, with cover, slotted ends, 3/3 dozen, 24/9 gross.

CLIX Valve Holders, 7-pin, lemon shape, brass, tag ends, 2/3 dozen (1/3 half), 18/9 gross; 4- and 5-pin circular, with cover, slotted ends for soldering, 2/9 dozen, 18/9 gross.

CLIX Valve Holders, 5-pin square and 4-pin long oblong types, 1/3 dozen, 10/9 gross; Clix socket strips, 2-3-4-5-6 sockets, various markings, equal numbers, mixed, 6 for 1/3, 10/9 gross; plugs, 1/3 dozen.

SCREENED Leads, about 4 yards, 3-way, two only screened, 1/3; extra heavy for car sets, with spades, 1/3, 2½ yards.

HAMMERLUND 30mm. Midget Trimmers on Pazo-line, 1/9 dozen; Ultra type brown knobs, octangle, plain arrow, L.S. 1/9 dozen, 8/6 gross assorted, 10/6 gross plain or arrow.

SMALL Iron Core Coils, made by Varley, aerial and oscillator, 465 k/c, 2/6 pair, with coil connections for straight type gang.

WEARITE 110 kc. I.F.'s with Top Trimmers, 1/6 each; sets band pass air core superhet coils, ex Halycon, screened chassis type, 4/9 set five; 110 kc. with coil details. [8796]

Lockwood CABINETS

DETAILS NOW READY of the New AD. 600, a smaller version of the Famous AD. 500

Send 1½d. stamp for details of this and other standard models.

LOCKWOOD & CO.
65, LOWLANDS ROAD, HARROW.
Telephone: BYRon 1818.




V.5 BALANCE TYPE TUNABLE REFLECTOR for Anode Circuit use in H.I.-PI Sets 30/-
Type V.6, similar, but for Grid Circuit use 28/-
Simpler Tuned Types—V.2, with switched cut-off 19/6
"Q.A.S." Tunable 12/-
SCRATCH FILTERS, also TONE CONTROL CHOKES, are still available. **LEAD, CRYSTALS, DETAILERS, FREE. POSTLET-WHITE BROS., "Kinva Works," KINVER, STAFFS.**



Mains Transformers as specified for The Wireless World High Quality Communication Receiver Type WW51—45.

W. BRYAN SAVAGE LTD.
Westmoreland Rd., London, N.W.9. Phone Colindale 7131

THE 70-RANGE, BRITISH MADE TAYLOR METER

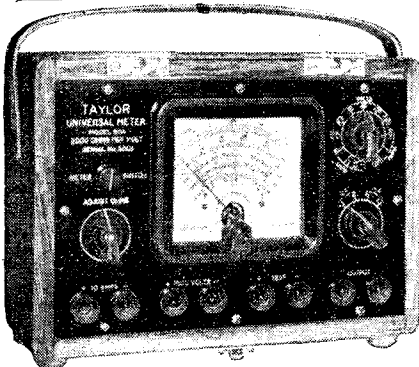

is a fully guaranteed precision-built instrument. Although it is very reasonably priced for such a comprehensive meter, its sensitivity, accuracy and reliability leave nothing to be desired. Fitted with a sturdy 4½ in. moving coil jewelled movement, it covers D.C. volts 0.002-2,000; A.C. output and volts 0.2-2000; D.C. current 10 MA-20 Amps; A.C. current 10 PA-5 Amps; Resistance 0.1 ohm-5 megohms with internal battery. Output, —18 to +60 DB at the touch of two switches, and an adaptor is available to increase the voltage range to 5,000-10,000 A.C. and D.C.

MODEL 80 A
2,000 O.P.V. **11**
A.C. & D.C. GNS.

MODEL 80 B
5,000 O.P.V./D.C.
4,000 O.P.V. **13**
A.C. GNS.

MODEL 80 C
20,000 O.P.V./D.C.
16,700 O.P.V. **15**
A.C. GNS.

To TAYLOR ELECTRICAL INSTRUMENTS Ltd., 45, Fouberts Place, Regent Street, London, W.1 Phone: Gerrard 5255
Please send me particulars/or arrange for me to have a FREE TEST (Strike out whichever is not required) of your Meters, Valve Testers, Signal Generators, Oscilloscopes... Put tick after whichever you are interested in.
Name.....
Address.....

COMPONENTS—SECOND-HAND CLEARANCE, SURPLUS, ETC.

SOUTHERN RADIO'S Bargains.
ALL Guaranteed. Postage extra.
5/-.—Parcel of useful components, comprising condensers, resistances, volume controls, wire circuits, etc., value 25/-; 5/- per parcel.
15/-.—Service man's component kit, electrolytic condensers, volume controls, resistances, tubular, mica, paper condensers, valve holders, etc.; 120 articles contained in strong carrying case, 9in. x 7in. x 7in.; 15/- the kit.
21/-.—Small trader's parcel of components, 150 articles comprising all types condensers, valve holders, resistances, chokes, coils, wire, etc., value 85/-; 21/- the parcel.
5/-.—100 wire-end resistances, assorted capacities, ½ and 1 watt; 5/- per 100.
5/-.—6 volume controls; 5/-.
TELSEN 3-range Meters (volts and milliamps), 4/-; Ormond loud-speaker units, 2/6; crystal sets, 5/6; Westectors, type W2, 2/6; Telsen W349 midgeet iron core coils, 4/6; Step-up transformers, 110-250 volts, 7/-; 8 mid. electrolytic condensers, 500 volts, 1/8; crystal detectors, 2/-; crystals, 6d.; Marconi V24 valves, 5d.
2/-.—10 or instrument carrying cases, ex-Government stock, wood 9in. x 7in. x 7in.; 2/-.
SPECIAL Offer, Limited quantity torch bulbs, 1.5v., 21/- per 100; 2.5v. and 3.5v., 17/6 per 100.
SOUTHERN RADIO, 46, Lisle St., London, W.C. Gerrard 6653. [8904]

LONDON CENTRAL RADIO STORES, 23, Lisle St., W.C.2. Gerrard 2969.
PHILIP'S Step Down Transformers, input 200-240 volts, output 6 volt 3 amp., 2/9 each; B.I. Condensers, 4 mid., 450v. working, resin-oil filled, 3/3; also 0.25 mid., 1,000 volt working, 2/6; 0.1 mid. ditto, 2/3; Townsend buzzers, H.F. type, 4½v.-10v., 3/6, new; all goods advertised in last month's issue still available.

LONDON CENTRAL RADIO STORES, 23, Lisle St., W.C.2. Gerrard 2969. [8841]
PELO SCOTT "Preselector" boxed, as new, 25/-; "Columbia" pick-up, £1.—Barker, 5, High St., Swanscombe, Kent. [8837]

VAUXHALL.—Torch batteries; No. 8, 3-volt, 8d.; Penlite 3-volt, 11d.; flat 4½-volt, 10d.; complete bijou torches with lamp, 3-volt battery, 1/9; bulbs, 2d.; post 2d. extra on each item.
VAUXHALL.—Rola P.M. speakers, 8in. 14/9, 10in. 18/6; Rola energised 1,500 ohm. speakers, 3in. 12/6, 10in. 15/3.

VAUXHALL.—Collaro A.C. gramophone motors, boxed, 29/-; flat sheet aluminium, 12x12in., 3/-; 12x19in., 4/-; 18x18in., 5/6.
VAUXHALL.—Rola G12 P.M. loud speakers, 69/6; G12 energised, 55/-; brand new, with input transformers.

VAUXHALL.—T.C.C. aluminium containers, 8 mid. 600v., 3/-; T.C.C. cardboard containers, 8 mid. 500v., 2/-; 8+8 mid., 3/6; 6+4 mid., 350v., 1/9.
VAUXHALL.—Iron-cored coils on base, with switch, terminals, circuit, 2-gang, 12/6; 3-gang, 19/6.
VAUXHALL.—Three-band 2-gang coils for mains superhet, switch, terminals, 18/-; volume controls, 2/-; with switch, 3/-.

VAUXHALL.—Bar-type condensers, straight 0.0005 mid., trimmers; 2-gang, 6/6; 3-gang, 8/6; full-vision drives, station named, 6/-.
VAUXHALL.—Polar 4-gang straight 0.0005 mid., screened, trimmers, 13/6; Clix chassis valve-holders, 5-pin 5d., 7-pin 6d.; 1-watt resistors, 4d.
VAUXHALL.—Electrolytic condensers; 50 mid. 50v., 1/9; 50 mid., 12v., 1/6; 0.1 mid., 3d.; tubular types.

VAUXHALL UTILITIES, 163a, Strand, London, W.C.2. Write for new free list. [8792]
MAINS RADIO DEVELOPMENT COMPANY'S Super Service. Orders sent immediately, carriage paid or C.O.D. Please note new address, telephone Tudor 4046. Stamp for list 233.

T.C.C. Unused Metal can Wet Electrolytics, 8 mid., 460 volt, 2/6; Hunts card, 50 mid., 12 volt., 1/-; 25 mid., 25 volt, 1/-.
T.C.C. Card Case Electrolytics, 600 volt surge, 8 mid., 2/-; 8x8 mid., 3/6; B.I.C. 50 mid., 50 volt, 1/9.
N.S.F. Unused Wire End Resistors, marked and colour coded, ½, 1 and 2 watt, ten different useful sizes in each parcel of 20 resistors; 1/- the 20, only.

TUBULAR Condensers, unused, wire ends, best make, 400 volt working, 0.0001 to 0.1 mid., 5d.; 0.25, 0.5 mid., 8d.
CLIX Latest Unused Chassis Valve Holders, English 5-pin, 7-pin, 4d.; all American sizes, 6d.; standard sleeving, 1½d. yard.
CENTRALAB Unused Latest Potentiometers, long standard spindle, all sizes, 2/3, with switch 2/6.

DUBILIER Unused Mica Condensers, midgeet tags, 0.00005 to 0.00005 mid., 3d. each, 2/9 dozen.
ERIE Unused One-watt Resistors, all sizes; 4d. each, 3/6 dozen; two-watt, 7d.
MAINS RADIO DEVELOPMENT COMPANY, 52a, Church Crescent, Muswell Hill, London, N.10. [8709]

Masteradio

—MALLORY VIBRAPACKS and MALLORY VIBRATORS

for 11 Portable Power Supply requirements.

Output range from 300 volts at 100 m/a to 120 volts at 25 m/a.

Because Mallory are the World's largest manufacturers of electrical contacts, Mallory Vibrators represent the highest quality obtainable.

Technical data on application from concessionaires for Wholesale and Retail distribution:

MASTERADIO LTD.

VIBRANT WORKS, 193, RICKMANSWORTH ROAD, WATFORD, HERTS.
Telephone Watford 9885

Dits and Dahs!

The Morse Code is the language of the air. Learn it at home.

CANDLER CODE COURSES

not only teach you the right way to send, but the right way to read code sound just as easily as you read print by sight.
Beginners' and Advanced Courses.
Terms: Cash or Monthly payments.
Send for FREE "Book of Facts."

CANDLER SYSTEM CO.,

LONDON OFFICE: (55W), 121, KINGSWAY, W.C.2.

WARD

WE MANUFACTURE:

ROTARY CONVERTERS DC/AC for operating P.A. amplifiers, Radio Receivers, etc.
DC, DC ROTARY TRANSFORMERS, SMALL ALTERNATORS, SMALL D/G MOTORS, H.T. GENERATORS. MAINS TRANSFORMERS up to 10 k.v.a. PETROL ELECTRIC generator sets up to 50 k.v.a.
BATTERY CHARGERS for private and industrial use.

We can also handle general small engineering work.
Full details of any of the above upon request

CHAS. F. WARD

46, FARRINGTON ST., LONDON, E.C.4
Telephone: Holborn 9703.
Works: Bow, E.

THE BEST WAY to LEARN MORSE

"MASTERS" INSTRUCTIONAL RECORDS

Prepared by an ex-R.A.F.V.R. Signal Instructor, these records contain messages at a speed from 2 to 15 words a minute. Details on Request.

Price 3/6 each or Complete Set of Three 9/-

C. E. MASTERS,

Forest Way, Pound Hill, Crawley, Sussex.

SITUATIONS VACANT

WIRELESS Technical Instructors Required in Army Units.

ENROLLMENTS.—Pay 8s. 3d. per day (7 days a week). Clothing, rations and accommodation, or if this cannot be provided, allowances at authorised rates.

CANDIDATES Should Preferably be Under 35 and over 24, and (A) Hold one of the following qualifications:—

GRADUATESHIP of the Institution of Electrical Engineers.

Level (Group III) Certificate of City and Guilds of London Institute Examination in Radio Communication.

Higher National Certificate in Electrical Engineering.

Certificate of City and Guilds of London Institute in Radio Service Work

OR (b) be Able to Pass an Examination on the Following Syllabus:—

CURRENT Electricity.—Properties of an electric current. Ohm's Law and its application. Galvanometers and Measuring Instruments. Electro-magnetism. Magnetic materials. Conductors, Insulators and Dielectrics.

Alternating Currents.—General principles. Effects of Resistance, Inductance and Capacity. Resonance.

Radio.—General character of a radio signal. Knowledge of valves and their simple applications. General knowledge of tuning both transmitters and receivers.

Mathematics.—Knowledge of Algebra and simple Trigonometry.

SUITABLE Candidates will be interviewed at Local Centres, and if successful, will be enlisted and appointed acting Sergeant-Tradesman. For those who are on the Schedule of Reserved Occupations special arrangements will be made to enable them to be enlisted.

APPLICATION Forms, obtainable by postcard from the Under-Secretary of State, War Office (A.G.6.c.), Hobart House, Grosvenor Place, S.W.1, to be lodged by 28th January, 1940.

RADIO Testers and Inspectors; experienced with receivers and/or transmitters and associated equipment.—Write, stating age and experience and rate required, to Box 1282, c/o The Wireless World.

RADIO Service Engineers Required Immediately by Radio Rentals, Ltd., own saloon cars essentials. Vacancies London and Provinces.—Write, stating age and experience, to Service Manager, 11, Mattock Lane, Ealing, W.5.

RADIO Testers Required, applicants must have had technical training and experience of receiver circuit trimming on factory production lines.—Apply Employment Dept., Murphy Radio, Ltd., Welwyn Garden City, or nearest employment exchange.

INSPECTORS Required for Radio Apparatus, produced to Service standards; applicants should have experience of inspection work on broadcast receivers, telephone apparatus, small electrical apparatus or small mechanisms; experience with Government work an advantage; Midland area.—Reply with age, experience and rate expected, to Box 1444, c/o The Wireless World.

ASSISTANT to Inspector in Charge Required for Test Section, handling radio communication transmitting and receiving apparatus of high standard; applicants should preferably have experience with radio laboratory apparatus, control of labour and tests, as applied to radio equipment for Government Services; Midland area.—Write, stating age, experience and salary expected, to Box 1443, c/o The Wireless World.

SITUATIONS VACANT

RADIO.—Wanted, Trouble Shooters for large Radio Factory in Midlands; must have had factory experience. Applicants will be interviewed in London or the Midlands.—Write, stating age, experience and salary required, Box 1479, c/o The Wireless World.

VACANCIES Exist for Civilian Morse and Procedure Instructors at the Electrical and Wireless Schools, Royal Air Force. Candidates must be able to send and receive Morse at not less than 25 w.p.m. and should have had experience of lecturing and teaching, but consideration will be given to others who consider themselves capable. Applications should be addressed to the Under Secretary of State, Air Ministry (S.5.D.), London, W.C.2, giving full particulars as to previous experience, age, etc. Candidates will be required to appear before a selection board at the Schools for interview and test, but may be reimbursed the cost of third class travelling expenses for this purpose.

THE INSTITUTE OF WIRELESS TECHNOLOGY (Founded in 1925, Incorporated) PROFESSIONAL MEMBERSHIP The advantages of professional membership are open to all qualified wireless engineers. Full information, with syllabus, may be obtained from the Assistant Secretary, Institute of Wireless Technology, 25, Firs Drive, Palmers Green, London, N.13

Frank Heaver Ltd. BUSH HOUSE, ALDWYCH, W.C.2 REPRESENTING AMERICA'S LEADING COMPONENT MANUFACTURERS ASTATIC. Microphones—Pick-ups—Cartridges. CROWE. Escutcheons—Pointers—Drives. G.I. Variable Condensers—Tuners. RAYTHEON. Receiving and Transmitting Tubes. MALLORY. Vibrators—Electrolytics—Switches, etc. KURZ-KASCH. Knobs—Mouldings. SICKLES. Coils—I.F. Transformers, etc. HAMMARLUND. Communication Receivers—Transmitting Gear, etc. ALLEN BRADLEY. Resistors. EICOR. Dynamometers—Lighting Sets. STEVENS. Kraft Condenser Tissues. COIL CANS—TUBE SHIELDS—SOCKETS—Etc., Etc. — FROM FACTORY TO USER — Apart from the specialities produced by those manufacturers whose names are listed our associations in the United States are such that we can rapidly secure for you quotations in respect of special material which you may find difficult to obtain at the present time. Telephone: TEMple Bar 2087.

SITUATIONS VACANT

TESTERS Required for Radio Communication Apparatus of Government Service Standards; applicants should have experience of factory testing on broadcast receivers or similar electronic apparatus; positions are in Midland area and hold good prospects for keen applicants.—Write Box 1462, c/o The Wireless World.

IMPERIAL AIRWAYS and British Airways Require Radio Officers, age 25 to 30, of British nationality, for universal service. Applicants must possess P.M.G.'s Air Operator Radio Licences. Preference will be given to those who have had at least two years' marine or air operating experience and to holders of 1st class Marine Certificate and engagement will be subject to applicant being examined and passed fit by company's medical adviser. Emoluments £4/10 to £6/5 per week, according to seniority, plus living pay and allowances according to base. Contributory pension scheme and accident insurance cover. Applications should be addressed to Flying Establishment Officer, Grand Spa Hotel, Bristol, giving full particulars, age, qualifications and experience and commitments in the Reserve Forces (if any).

ELECTRIC LAMPS

5 WATT Electric Lamps, British made, fully guaranteed, 1/6 each, all wattages available; trade enquiries also invited.—Smith, Rugby Lane, Chesham, Surrey.

PATENT AND TRADE MARK AGENTS

GEE and Co. (H. T. P. Gee, Mem. R.S.G.B., etc.), 51-52, Chancery Lane, London, W.C.2. Holborn 4547-8. Handbook free.

PATENTS FOR SALE

THE Owner of British Patent No. 380,876, relating to "Improvements in or relating to Signalling Systems," is desirous of entering into negotiations with one or more firms in Great Britain for the purpose of exploiting the invention either by sale of the Patent Rights or by the grant of Licences on reasonable terms.—Interested parties who desire further particulars should apply to Albert L. Mond and Thiemann, 14 to 18, Holborn, London, E.C.1.

TUITION

RADIO Training, P.M.G. exams and I.E.E. Diploma; premiums free.—Technical College, Hull.

RADIO Officers (Marine), P.M.G. Special Certificate; free prospectus.—Marine School, South Shields.

PRACTICAL Postal Courses, radio television; test equipment design; I.P.R.E. and I.W.T. exams.—Write I.P.E., 3, Shirley Rd., London, W.4.

BUSINESS & PROPERTY FOR SALE, TO BE LET, OR WANTED

FREEHOLD and Unrestricted House, 4 flats, all electric, large garden, very high ground; S.E. district; suitable for wireless and broadcasting operator.—Box 1498, c/o The Wireless World.

CLASSIFIED ADVERTISEMENTS intended for the MARCH ISSUE can be accepted up to Thursday, February 8th.

INDEX TO ADVERTISEMENTS

Table with 3 columns: Advertiser Name, Page Number, Advertiser Name, Page Number. Includes entries like Ambassador Radio Works, Armstrong Manufacturing Co., Automatic Coil Winder Co., etc.

Printed in England for the Publishers, LIFFE AND SONS LTD., Dorset House, Stamford Street, London, S.E.1, by THE CORNWALL PRESS LTD., Paris Garden, Stamford Street, London, S.E.1. "The Wireless World" can be obtained abroad from the following: FRANCE: W. H. Smith & Son, 248, Rue Rivoli, Paris; Hachette et Cie, Rue Raoumure, Paris, and branches; Messageries Dawson, 4, Rue de Faubourg Poissonnerie, Paris. BELGIUM: W. H. Smith & Son, 74-75, Boulevard Adolphe Max, Brussels. AUSTRALIA: Gordon & Gotch, Ltd., Melbourne (Victoria), Sydney (N.S.W.), Brisbane (Queensland), Adelaide (S.A.), Perth (W.A.), and Launceston (Tasmania). NEW ZEALAND: Gordon & Gotch, Ltd., Wellington, Auckland, Christchurch, and Dunedin. INDIA: A. H. Wheeler & Co., Bombay, Allahabad and Calcutta. CANADA: Imperial News Co., Toronto, Winnipeg and Vancouver; Benjamin News Co., Montreal; Gordon & Gotch, Ltd., Toronto. SOUTH AFRICA: Central News Agency, Ltd.; Wm. Dawson & Sons (S.A.), Ltd., Cape Town. UNITED STATES: The International News Co., New York.



PRICE
23/6

1940 ROTHERMEL

JUNIOR MODEL

PIEZO ELECTRIC PICK-UP

HERE is the new 1940 Rothermel Junior Model Piezo Electric Pick-up, utilising a new type of crystal, generating a voltage on the torsion principle, allowing the crystal to be more robust in construction. It is completely enclosed in a die-cast metal housing. The setting is absolutely permanent. This Junior Model employs a crystal element larger than that of the Standard Model and has an output of 1.3 volts r.m.s. The quality of reproduction conforms with the same high standards only secured with a pick-up of the Piezo Electric variety. The weight on the record is only 2½ ounces—an assurance against surface damage. The beautifully finished brown satin arm is specially designed to ensure good tracking and a head rest is supplied with each pick-up.

R.A.R. Rothermel

ROTHERMEL HOUSE, CANTERBURY ROAD,
HIGH ROAD, KILBURN, N.W.6.

Phone: MAIDA VALE 6066.



NCC 495 A.

ROLA

TRANSFORMER
LAMINATIONS

Stamped from High grade Steel, wired and packed in the same consecutive order as they leave the press, ROLA laminations create low transformer costs by their saving on labour.

Eight standard sizes are available from stock, together with associated clamps and covers. Core dimensions .5625" to 1.5".

A comprehensive Bulletin for manufacturers will be sent on request.

BRITISH ROLA LIMITED
MINERVA ROAD, PARK ROYAL, N.W.10
WILLESDEN 4322

B.I.

RADIO MATERIALS

We have had a long experience in the manufacture of all kinds of Cables and Wires, Aluminium Sheets and Strips, Static Condensers, Insulators and Iron Work, Telephone Cords and Copper Earthing Rods, for Radio use.



BRITISH INSULATED CABLES, LTD
CABLE MAKERS AND ELECTRICAL ENGINEERS
PRESCOT, LANCS. Tel. No. PRESCOT 6571

95 Wm

Capacity Tolerances

DOWN TO A NEW LOW LEVEL

1937
 $\pm 15\%$



1940
 $\pm 1\%$

LIGHT, compact, and stable (both electrically and mechanically) T.C.C. Silvered Mica Condensers are being more and more widely used throughout the Radio Industry. The method of construction—the direct deposition of silver on the mica sheets—prevents changes of capacity and ensures a low temperature co-efficient. Further, this method of manufacture makes it possible for us to supply—on a commercial basis—condensers having tolerances as low as $\pm 1\%$. Indeed, three years ago such tolerances in normal quantity production would have been impossible. T.C.C. Research marches forward and keeps pace with the requirements of the Radio Engineer. In the new 1940 Receivers setting still higher levels of efficiency, T.C.C. Silvered Mica Condensers are a vital necessity.

T.C.C.
stabilised
**Silvered Mica
Condensers**

THE TELEGRAPH CONDENSER CO. LTD., WALES FARM ROAD, NORTH ACTON, LONDON, W.3.