

Wireless World

April 1972 20p

Sound pressure level meter

Electronic reading machine



A sample of our scope



Everybody knows Bradley's scope is wide. So is the scope of the 189 sampling oscilloscope. For a start, it's dual channel, and is intended for all sampling applications up to 1GHz. The basic Y sensitivity is 2mV/cm to 1V/cm, which can be increased to 0.8mV/cm. It has signal delay on both channels. And an important feature, you can achieve independent timebase delay on each channel.

Wide timebase ranges cover 10nS/cm to 10 μ S/cm with expansion to 100pS/cm. On the faster timebase ranges expansion is brought in

automatically which means you get direct timebase scaling when the expansion facilities are being used.

What else does the 189 offer? Timebase scanning modes give automatic, manual and external drive facilities, with a choice of channel display giving A or B, A and B alternately, A plus B, or A/B shown as an X/Y function.

Add to this a bright 8 x 10cm CRT display driven at 8kV and you begin to see the scope of the Bradley 189.

If you'd like to sample it, please let us know.

All Bradley instruments can be supplied with a British Calibration Service Certificate from our own B.C.S. approved standards laboratory.

G & E BRADLEY LIMITED
Electral House, Neasden Lane,
London NW10 1RR
Tel: 01-450 7811 Telex: 25583
A Lucas Company


BRADLEY
electronics

Wireless World

Electronics, Television, Radio, Audio

Sixty-second year of publication April 1972

Volume 78 Number 1438

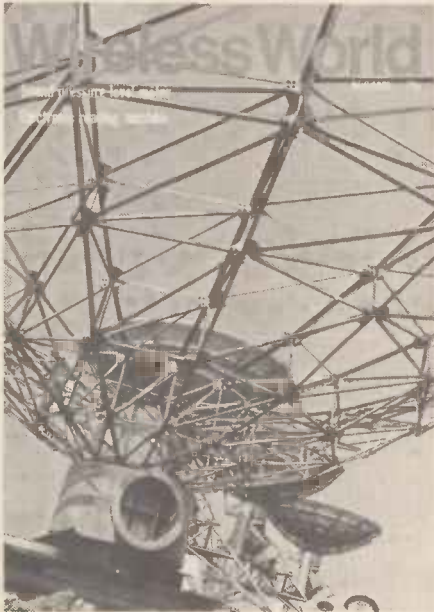

Our cover picture shows some of the eight 42-ft paraboloids being built by Marconi for the new £2M radio telescope at the Mullard Radio Astronomy Observatory at Cambridge University. Spaced over a distance of three miles four of the aerials are fixed and four are mounted on a railway track. *Photographer — Paul Brierley*

Contents

- 153 Exhibitions — general or specialized?
- 154 Hand-portable Transceiver by *D. A Tong*
- 160 H.F. Predictions
- 161 The Electronic Retina by *N. A. Singer*
- 166 Conferences & Exhibitions
- 167 Sound Pressure-level Meter by *J. L. Linsley Hood*
- 168 Announcements
- 169 Recording Level Meter and A.G.C. by *James M. Bryant*
- 170 News of the Month
- 173 How to Simplify Logic Circuits by *N. Darwood*
- 175 Letters to the Editor
- 177 Books Received
- 178 Electronic Building Bricks — 22 by *J. Franklin*
- 179 F.M. Tuner Design — 12 Months Later by *L. Nelson-Jones*
- 184 About People
- 185 Circuit Ideas
- 187 Stereo Cassette Tape Decks: 2 by *B. Crank*
- 192 Sixty Years Ago
- 193 World of Amateur Radio
- 194 Miniature Automatic Telephone Exchange Modifications by *P. F. Gasgoyne*
- 195 April Meetings
- 196 New Products
- 201 Literature Received
- 202 Real & Imaginary by 'Vector'
- A91 APPOINTMENTS VACANT
- A102 INDEX TO ADVERTISERS

IN OUR NEXT ISSUE

The transmission-line loudspeaker enclosure is re-examined and a simpler and better method of construction offered. Suitable drive units and crossover circuits are also specified.

Oscilloscope trace quadrupler. Provides four traces on a single-beam oscilloscope without sacrificing sensitivity or d.c. coupling. Frequency response is from d.c. to 5MHz (3dB down at 8MHz); sensitivity is 50mV/cm when used with a 100mV/cm scope.

ibpa

International Business
Press Associates

I.P.C. Electrical-Electronic Press Ltd

Managing Director: George Fowkes

Publishing & Development Director:
George H. Mansell

Advertisement Director: Roy N. Gibb, M.I.E.E.

© I.P.C. Business Press Ltd, 1972

Brief extracts or comments are allowed provided acknowledgement to the journal is given.

Published monthly on 3rd Monday of preceding month, 20p


Editorial & Advertising offices: Dorset House, Stamford Street, London SE1 9LU. Telephone 01-928 3333. Telegrams/Telex, Wiworld Binespres 25137 London. Cables, "Ethaworld, London S.E.1."

Subscription & Distribution offices: 40 Bowling Green Lane, London EC1R ONE. Telephone 01-837 3636. Subscribers are requested to notify a change of address four weeks in advance and to return envelope bearing previous address.

Subscription rates: *Home*, £4.35 a year. *Overseas*, 1 year £4.35; 3 years £11.10 (U.S.A. & Canada 1 year \$11, 3 years \$27.75).



To each his own.

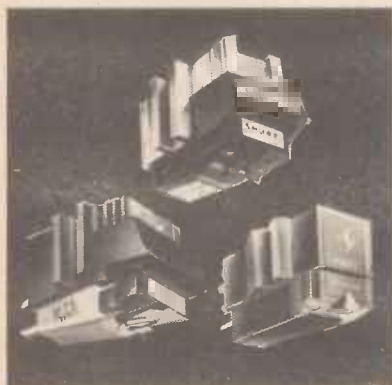

Not everybody needs a concert grand piano, nor does everybody need the Shure V-15 Type II, the most sophisticated cartridge in the world, to enjoy his kind of music in his kind of hi-fi system. For many, the M75 Type 2 Series, widely acclaimed as second only to the V-15, will be more than adequate. Within more circumscribed budgets the M55, M44 Series or M3D, each offering optimum performance in successively lower price ranges, may be an excellent choice. Send us the coupon for our recommendations.

Shure Electronics Limited
84 Blackfriars Road
London SE1, 8HA Telephone (01) 928 3424

- Please send me the full details of Shure cartridges.
- Please recommend the appropriate model for use with my equipment.

Arm or Unit _____

Amplifier _____

Name _____

Address _____



SHURE

Wireless World

Editor:

H. W. BARNARD

Technical Editor:

T. E. IVALL, M.I.E.R.E.

Deputy Editor:

B. S. CRANK

Assistant Editors:
J. GREENBANK, B.A.
G. B. SHORTER, B.Sc.
Drawing Office:

L. DARRAH

Production:

D. R. BRAY

Advertisements:
G. BENTON ROWELL (*Manager*)
G. J. STICHBURY
A. PETERS (*Classified Advertisements*)
Telephone: 01-928 3333 Ext. 533

Exhibitions — general or specialized

During the past 20 years or so, there has been a growing tendency for exhibitions, both in this country and abroad, to get bigger and bigger and more and more diverse in content. Instead of the Components Exhibition, for example, being concerned with components as it was originally in the days of the Grosvenor House show (of happy memory) it has grown into another all-embracing exhibition of components, instruments, electronics and automation. Shows of such size and diversity have, of course, a very useful function in that they provide the would-be buyer with a shop window stretching right across the industry. Many exhibitors and visitors, however, feel that they have become so diverse that they lack the impact of the more specialized exhibition. As an exhibition gains in popularity and grows in stature it almost inevitably attracts exhibitors with peripheral interests and in a few years it has very largely lost its identity as a specialized show. The progress of fragmentation then starts all over again and, as will have been noticed from our news pages and the list of exhibitions we publish each month, there has recently been a swing from generalization to specialization. A note in 'News of the Month' (p.172) gives details of the semiconductor exhibition — SEMINEX — to be held this month in a London hotel. It will be recalled that most, if not all, the semiconductor manufacturers withheld their support from last year's Components Exhibition and are not in the advanced list of exhibitors at this year's I.E.A. show. Other recent or forthcoming specialized exhibitions in the U.K. cover electro-optics, electronic packaging, audio, public address, communications etc. This may well be the future trend in exhibitions, brought about mainly for two reasons. First, the cost of exhibiting at a comparatively small specialized exhibition can be minimal because stands are limited in size and are not elaborate. Secondly, the specialized exhibition can be, and frequently is, linked with a conference, seminar or what have you, including papers dealing with a very limited field of interest.

Having said this about small specialized exhibitions we regret to find that the Physics Exhibition, which has had a character all its own for so many years, is possibly taking the reverse step. The regret is not so much in that it is joining forces with another show — the Labex (laboratory equipment) at Earls Court — but that the particular identity of this non-commercial, research-centred, exhibition may be lost.

It is interesting to note that contrary to the move to specialized exhibitions in this country the well-established gargantuan exhibitions on the Continent continue to grow in size and in popularity.

Despite *Wireless World's* diverse interests we prefer specialized exhibitions; they provide a better opportunity for a 'state of the art' report rather than the 'all things to all men' type of report, which ranges from microcircuits and discrete components through instruments and control equipment to complete systems.

We may be accused of being biased towards small specialized exhibitions because it makes our job of reporting easier. It is not so much the ease with which we can cover an exhibition — even one like SONEX with 60 or 70 exhibitors can take many man hours to cover factually — but we believe our readers prefer a true assessment of a particular field rather than a wide-ranging, disjointed catalogue of exhibits.

Hand-portable Transceiver

A design for 144-6MHz with battery-saving and squelch facilities

by *D. A. Tong, B.Sc., Ph.D. (G8ENN)*

Rather than build fixed station equipment, which could on occasion be taken outside, it was the author's intention to build portable equipment, which would also be suitable for fixed station use. A general view of the two-metre transceiver to be described is shown with its mains power supply and charging unit. Including batteries, loudspeaker and telescopic aerial, the overall size of the unit is 15 × 11 × 6cm and it weighs about 1kg. A highly sensitive receiver is included and the transmitter radiates an a.m. signal of about 1.5W carrier power. In order to go 'on the air', all one has to do is pull out the whip aerial and switch on.

Front panel space is at a high premium in miniature equipment, so wherever possible non-critical circuitry has been used, so that operator adjustment is not required. In order to obtain a reasonable period of operation between battery recharges, some limitation on power output must obviously be accepted. The batteries used by the author are rated at 900mAh and are able to provide a good day's operating at normal transmit-receive ratios. To conserve power, a front panel switch is fitted, which reduces the output

power from 1.5W to 400mW, which is ample for most local contacts. Long periods of monitoring a particular unoccupied receiving channel are also catered for by the inclusion of a sampling device in the receiver, which reduces the battery drain by a factor of ten. The ideal of 'instant operating' can be met only if care is taken in construction. Poor soldered joints and unanchored components can play havoc with reliability, but care is also essential in the design of the outer case.

General circuit design

An overall block diagram of the transceiver is shown in Fig. 1. In the receive mode the unit functions as a dual-conversion superheterodyne in which most of the functions in the so-called 'tunable i.f.' are located in the Mullard i.c. type TAD100. The first intermediate frequency covers 10.7 to 12.7MHz with a first local oscillator on 133.333MHz. The second intermediate frequency is 470MHz. While not ideal, these frequencies were chosen for the following reasons: (a) a miniature block filter is available from Mullard Ltd at a

reasonable price (type LP1175 at 65p); (b) the tunable i.f. needs to be high enough for good first image rejection, but low enough to give good second image rejection and adequate v.f.o. stability.

In the crucial first stages of the receiver a cascode f.e.t. r.f. stage is followed by a f.e.t. mixer. This arrangement gives an excellent weak signal performance and is also relatively free from cross-modulation. The TAD100 includes driver transistors for a complementary pair of audio output transistors. Using the devices specified by Mullard (AC187 and AC188), up to three watts of audio power are available, and the receiver audio stages are therefore also used as a modulator in the transmit mode. Selection of either loudspeaker or modulation transformer as load is accomplished using a transistor gate circuit'. Audio input switching is carried out by a f.e.t. gate which also functions as a squelch gate, as indeed does the loudspeaker gate.

It is not necessary to interrupt any high current path during send-receive switching and this enables small-signal transistors to be used as combined switches and voltage stabilizers, to route stabilized supply voltages to the appropriate, low-level stages in the transceiver. In conjunction with a diode aerial switch, which is r.f. energized, these features reduce the send-receive switch to a single contact closure in the hand-microphone, and no relays are necessary.

In order to be able to operate in the stand-by mode for long periods without draining the battery, the inclusion of squelch (muting in the absence of a received signal) is doubly necessary, since the battery saver circuit requires some definite indication that a signal has been received during its periodic sampling of the monitored channel. When such a signal is received two things happen. First the muting of the receiver is lifted and secondly the sampling ceases and the receiver is continuously energized. Sampling resumes only after a delay of about thirty seconds after the received signal disappears. The sampling process is inhibited if an external power source is used, since it is then unnecessary.

The transmitter is relatively straightforward and uses a crystal controlled oscillator at half the output frequency. Modulation is applied to the driver and



The transceiver and its main power unit and battery charger.

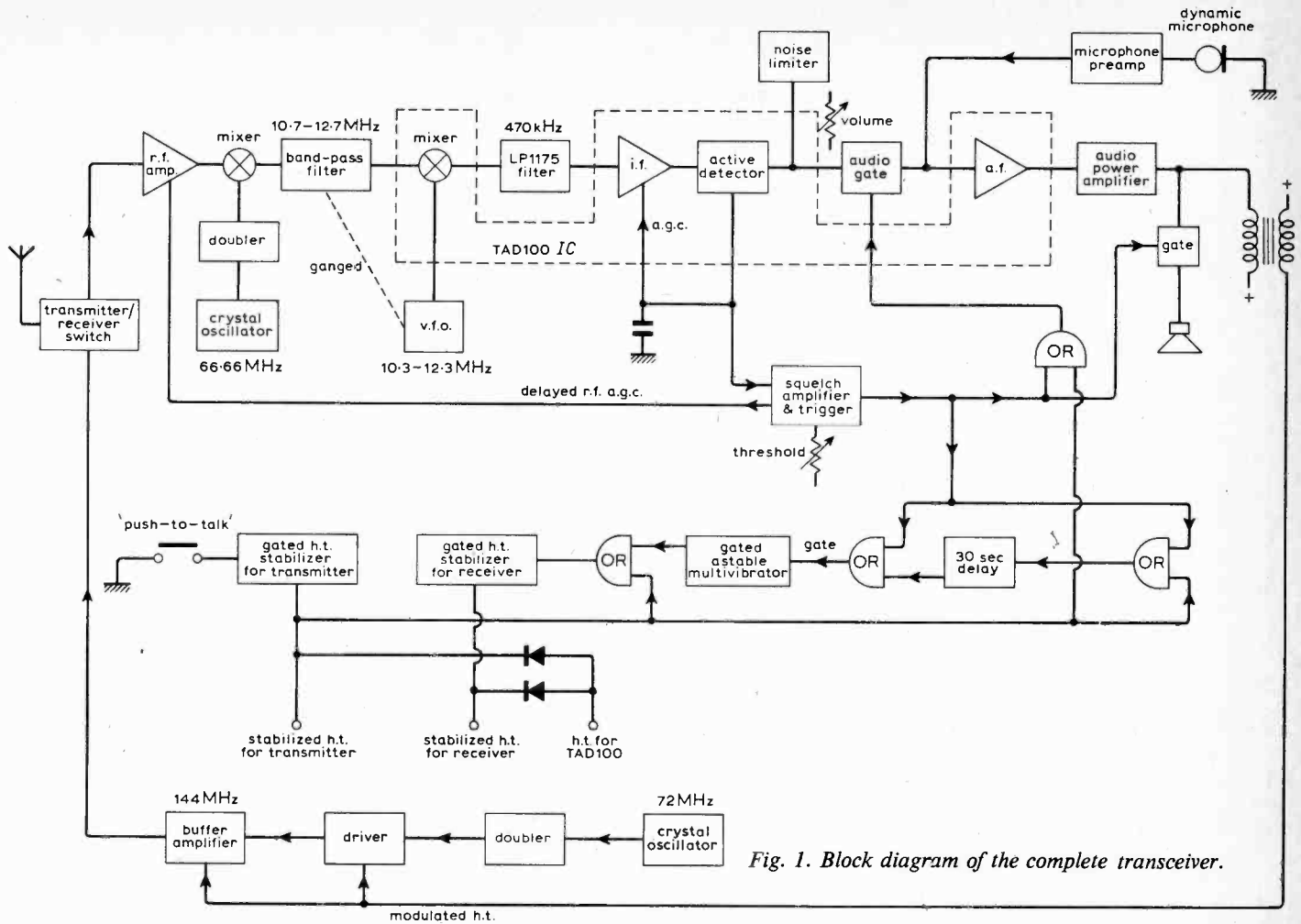


Fig. 1. Block diagram of the complete transceiver.

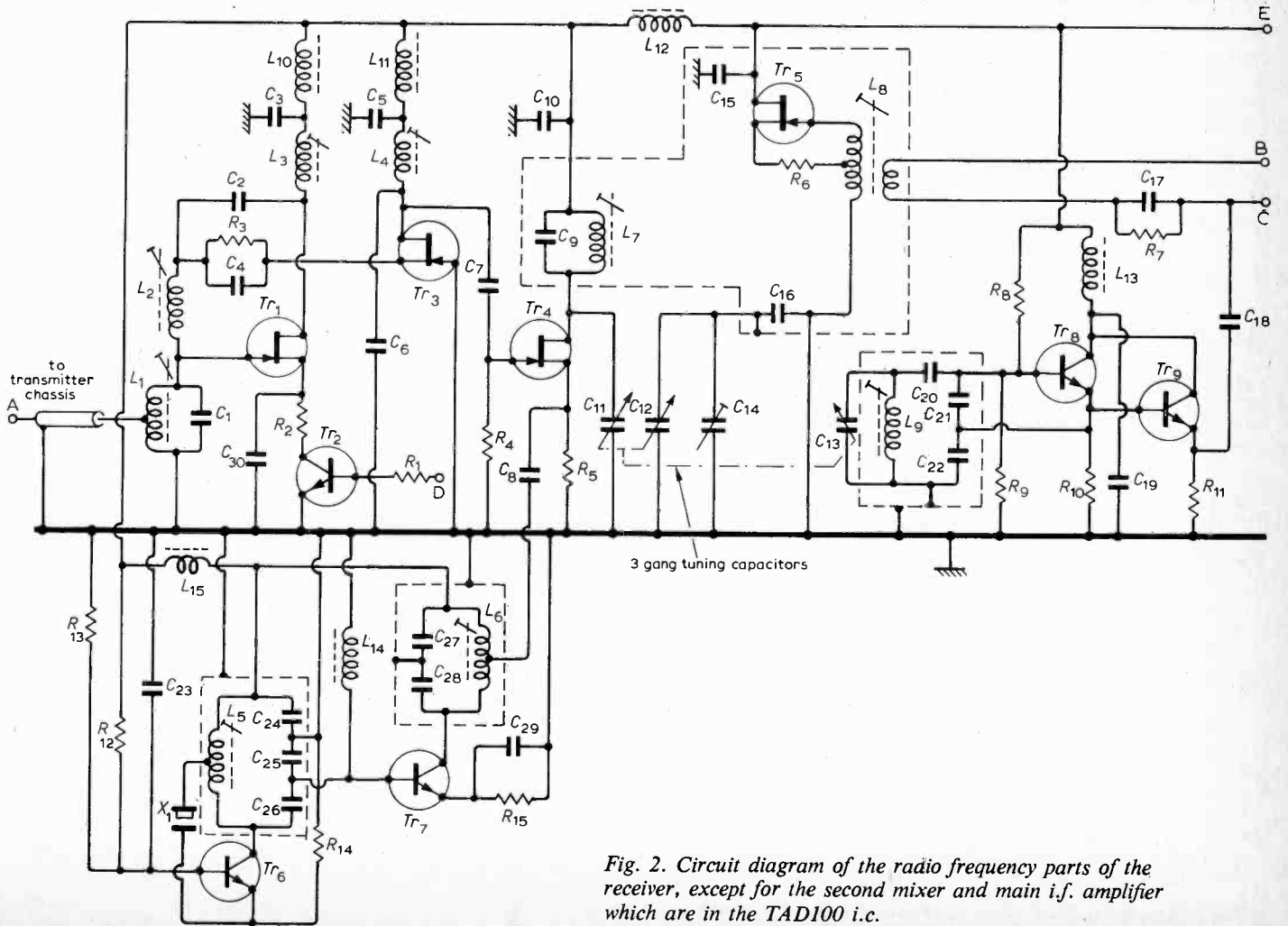


Fig. 2. Circuit diagram of the radio frequency parts of the receiver, except for the second mixer and main i.f. amplifier which are in the TAD100 i.c.

output stages and the receiver audio section is used as the modulator. The power output switch controls the amount of drive supplied by the second stage to the driver stage.

The receiver

The complete circuit diagram of the receiver is given in Figs. 2, 3 and 4, but this also includes most of the send-receive switching components. The cascode r.f. stage (Tr_1, Tr_3) is straightforward to set up and the neutralizing adjustment (L_2) is non-critical. The two transistors are not operated in series with respect to the power supply, because the latter should be larger than the sum of the two pinch-off voltages which could be up to 12V. The basic circuit has previously been used by D. J. Taylor². In the present receiver however the a.g.c. arrangement is a little unconventional and uses a separate transistor, Tr_2 , as a variable source resistance for Tr_1 . At point *D* a positive

voltage decreasing with signal strength is required and this is obtained from the squelch amplifier (Tr_{19} , Fig. 4). The first mixer, Tr_4 , is a conventional f.e.t. mixer with source injection from a frequency doubler, Tr_7 , which is in turn driven by a crystal-controlled overtone oscillator, Tr_6 , at 66.666MHz.

In dual-conversion receivers of this type, the most serious spurious response is at the second image frequency, that is, the frequency spaced by twice the last i.f. (470kHz) from the second local oscillator (10.235 to 12.235MHz). It is particularly serious, because it falls within the two-metre band itself and there is the likelihood therefore of strong signals being in its vicinity. The only cure, given a final i.f. of 470kHz, is to have good selectivity at the first i.f. In this receiver two loosely coupled tuned circuits at this frequency (L_7, L_8) are ganged with the second local oscillator. The coupling is inductive; the two coils being spaced about 13mm

apart inside a double i.f. transformer can. The basic coupling can then be adjusted by fitting a single-turn loop around both coils and phased so as either to aid or oppose the existing coupling. A large increase in selectivity at the first i.f. was obtained in this receiver by adding a *Q*-multiplier (Tr_3) to the second tuned circuit (L_8). The *Q*-multiplication varies inversely with the value of R_6 and the amount used is determined in practice by the accuracy of tracking of this tuned circuit with the v.f.o.

The frequency stability of an a.m. receiver should be such that the total drift under all conditions is small compared with the receiver bandwidth and this is achieved here with the v.f.o. circuit shown (Tr_8, Tr_9). It is basically a Seiler oscillator³ and Tr_9 is used as a buffer stage.

The second mixer is located in the TAD100 i.c. and its output emerges from pin 14 to the input of the block filter at

Fig. 3. Circuit diagram of the part of the receiver which is built around the TAD100 i.c. The squelch and loud-speaker gates are also shown.


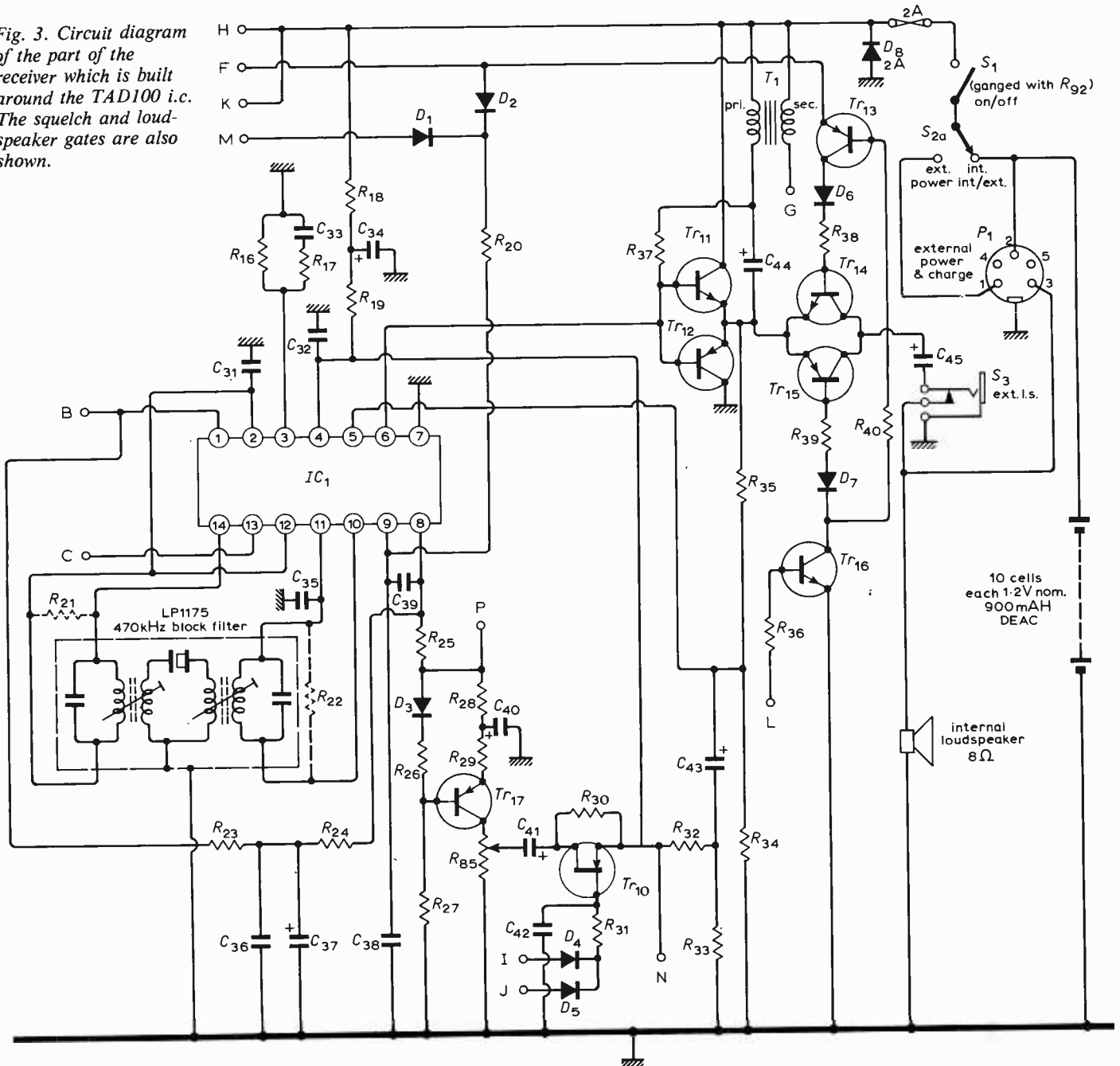


Fig. 4. Circuit diagram of the parts of the receiver involved with squelch, battery saving and send-receive switching of the power supply.

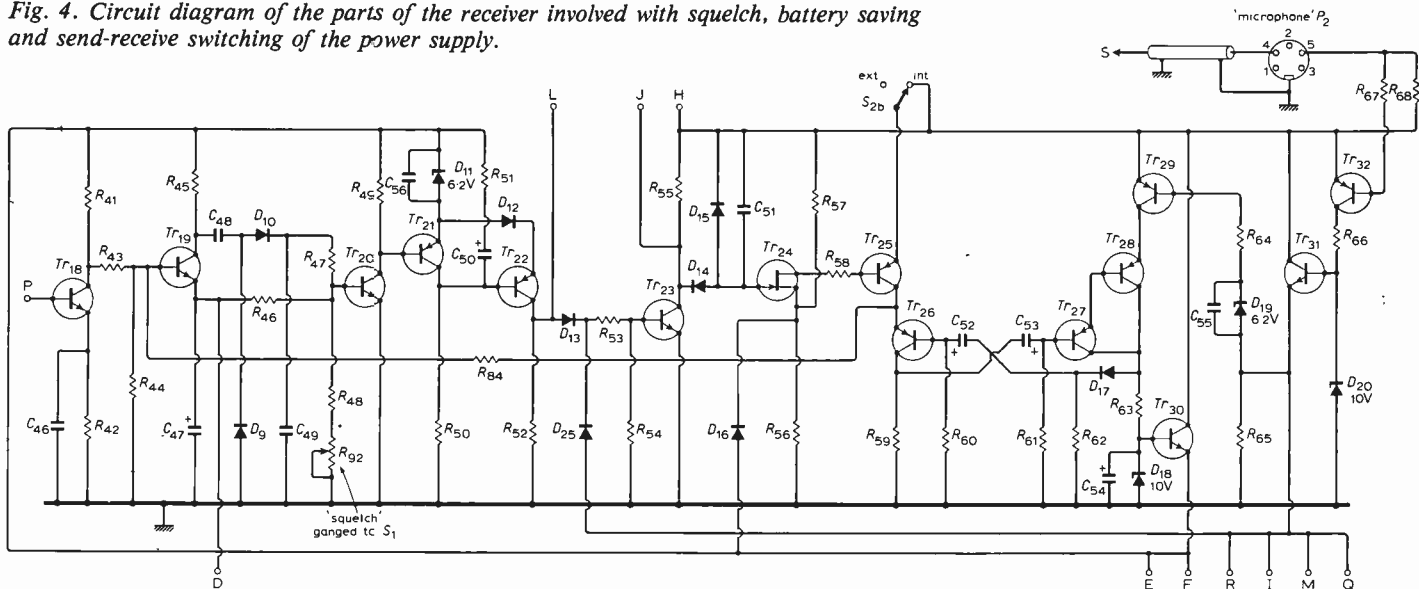

470kHz, which provides the main selectivity in the receiver. In turn, the output from the filter re-enters the i.c. at pins 10 and 11 to be amplified. After amplification the signal is rectified by an active detector within the i.c. and the audio output appears at pin 8 in the form of a positive voltage which goes more positive as the signal level increases. Following smoothing by R_{24} and C_{37} the output is used for the i.f. stage a.g.c. Transistor Tr_{17} limits any noise signal (impulses) on pin 8.

The i.c. contains all of the receiver audio amplifier except for a complementary output pair, Tr_{11} and Tr_{12} , and since the amplifier is also used as the modulator the i.c. needs to be continuously energized. The maximum permissible voltage at pins 2 and 9 is quoted as 9V in the data sheet,


therefore, the transmit and receive h.t. lines, which are stabilized at 9.5V, are used to supply the i.c. This avoids wasting power in a further zener stabilizer. Diodes D_1 and D_2 eliminate mutual interaction of the two supply lines. The first audio stage involves a differential pair and the action of the circuit (as d.c. negative feedback is concerned) is to maintain pins 4 5 at the same average potential. By appropriate choice of the resistor biasing components (R_{18} , 19, 32, 33 and R_{35} , 34) this action ensures that the quiescent voltage at the emitters of Tr_{11} and Tr_{12} remains at one half of the supply voltage. This is why pin 4 is fed from 'raw' h.t. and not from the stabilized line.

The audio output (up to 3W) is connected permanently to the primary of the modulation transformer, T_1 . Isolation

of the loudspeaker when transmitting is carried out by the gate circuit comprising Tr_{13} , 14, 15, 16. Transistors Tr_{14} and Tr_{15} are the gate, the other two transistors being used to control the base currents. The magnitude of this base current determines the peak currents, which can be passed by the complete gate in its on state and this determines the peak audio power passed to the loudspeaker.

Reverse voltage breakdown in the emitter-base junctions of Tr_{14} and Tr_{15} during audio peaks causes a faint sidetone to appear in the loudspeaker, indicating correct functioning to the operator. Diodes D_6 and D_7 stop these breakdown currents from energizing the d.c. control transistors Tr_{16} and Tr_{13} . In addition the loudspeaker gate is used as a squelch gate, with the control

Fig. 5. Circuit of the r.f. section of the transmitter.

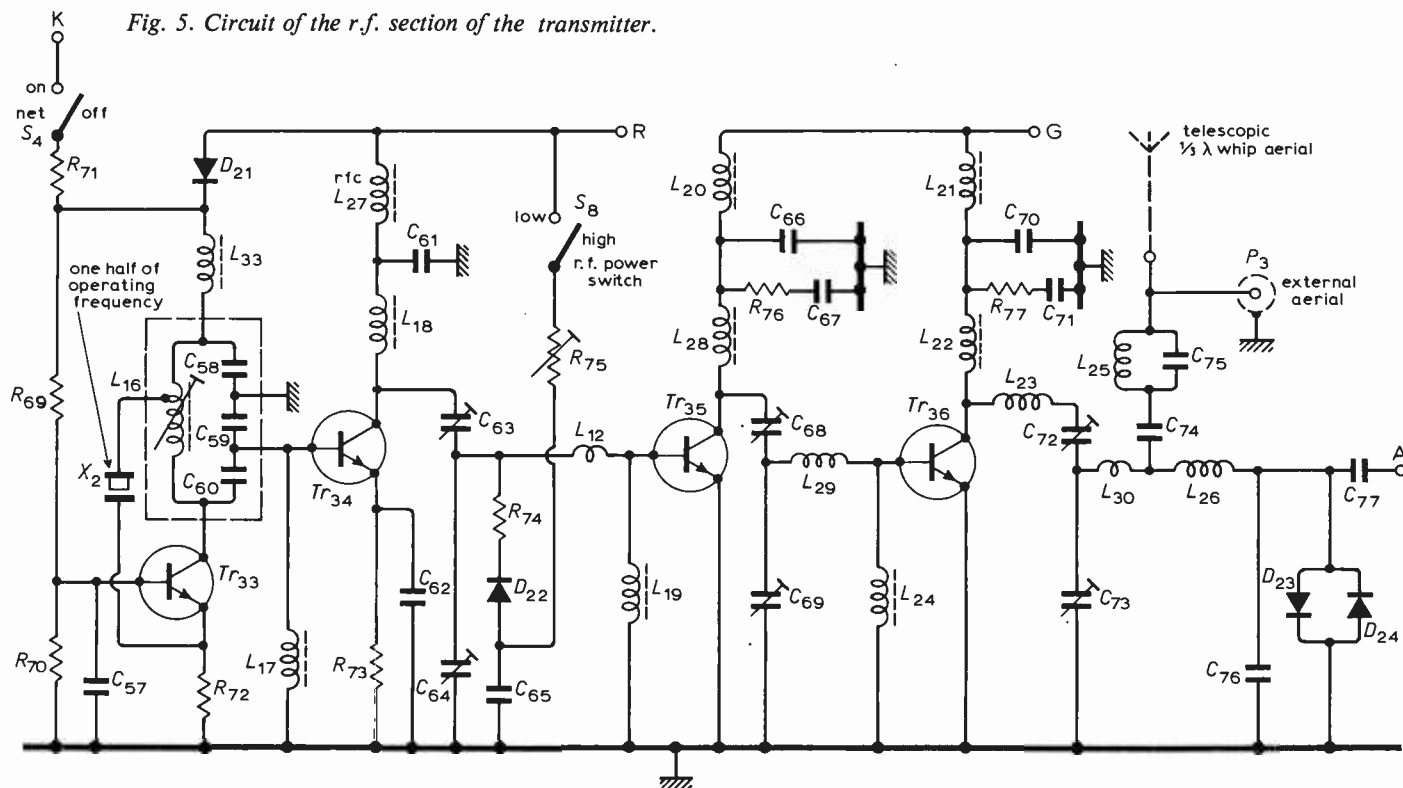


input connected to point *L*, and also it cuts out any clicks in the loud-speaker which might occur during sampling when the whole receiver is being switched on and off repetitively. Details of the power supply arrangements are shown in Fig. 3.

Squelch, battery-saver, send-receive switching

Some of the circuitry in Fig.4 could be omitted and one would still be left with a usable transceiver. The arrangement of *Tr*₁₉, *D*₉, *D*₁₀, *Tr*₂₀ provides noise compensation for the squelch⁴.

In the battery-saving circuit⁷ *Tr*₃₀ and *D*₁₈ act as a voltage stabilizer for the complete receiver, and *Tr*₃₂ and *D*₂₀ do the same for the low-level transmitter circuits. Both of these transistors should have a low saturation voltage, so as not to waste battery voltage. If the current to *D*₁₈ is interrupted, the receiver will be off and there are two reasons why this should happen. The first is if the transmitter is energized. Thus, if the microphone switch is operated (i.e. pin 5 of *P*₂ connected to chassis), *Tr*₃₂ is on, *D*₂₀ passes current, and *Tr*₃₁ applies stabilized h.t. to the transmitter.

This means that *D*₁₉ no longer passes its breakdown current and *Tr*₂₉ switches off, thereby turning off *Tr*₃₀ and the receiver. The second reason is if the receiver is in the sampling mode and this is controlled by the gated multivibrator formed by *Tr*₂₆ and the Darlington pair *Tr*₂₇ and *Tr*₂₈. Transistors *Tr*₂₅ and *Tr*₂₉ form AND gates with *Tr*₂₆ and *Tr*₂₈ respectively. If *Tr*₂₅ is off, *Tr*₂₈ (and hence the receiver) stays on continuously; if *Tr*₂₉ is off, the receiver stays off. Sampling can thus be inhibited if *Tr*₂₅ is off (or indeed if *S*₂ is switched to the 'external power' position). This happens either when a signal is being received, as indicated by the squelch threshold being exceeded and hence by *Tr*₂₂ collector being at about +5V, or when transmitting. In either case *D*₁₃ or *D*₂₅ passes current into *Tr*₂₃ base and in turn *Tr*₂₄ is off and so is *Tr*₂₅. Moreover, *Tr*₂₄ remains off for about thirty seconds after the squelch output ceases because of the time constant of *C*₅₁ with the reverse leakage resistance of *D*₁₅.

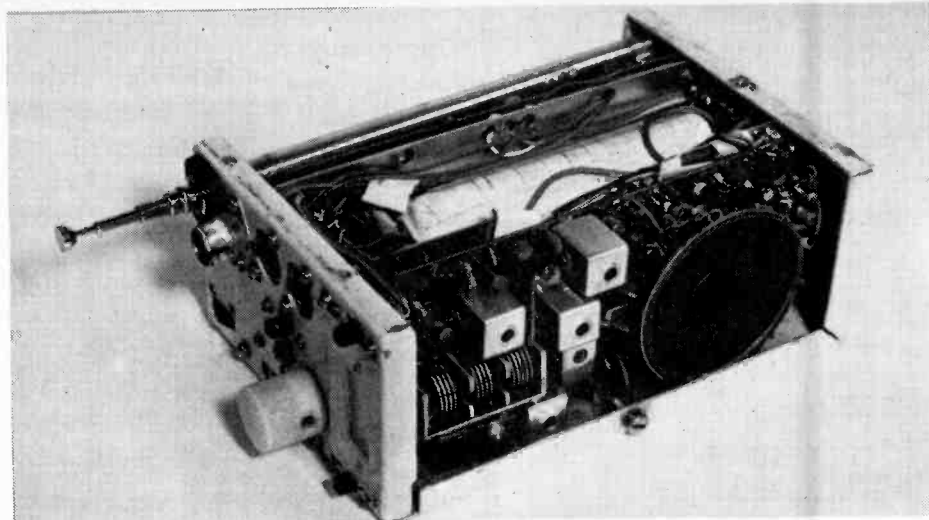

The transceiver with its cover plate removed showing the p.c. board, which carries the complete receiver, loudspeaker and tuning drive.

Fast rise and fall times are required for the receiver switched supply line if spurious effects are to be avoided, and *D*₁₇ ensures this fast fall. The function of the components *R*₅₁ and *C*₅₀ is to make sure that *Tr*₂₂ does not switch on momentarily as the receiver supply voltage falls to zero. If it did, *C*₅₁ would be immediately recharged and sampling would never get under way. When *C*₅₁ has recharged sufficiently to let *Tr*₂₄ conduct slightly, regenerative action via *D*₁₆ ensures a rapid transition by reducing the potential at the source of *Tr*₂₄.

Transmitter

The radio-frequency parts of the transmitter^{5,6} are shown in Fig. 5. Four stages are used beginning with an overtone oscillator, *Tr*₃₃, at one-half the operating frequency (see Fig. 1). The second stage, *Tr*₃₄, is the frequency doubler and this feeds the power output stage *Tr*₃₆, via the driver, *Tr*₃₅.

The 'output switch' is unusual and gives smooth control of the radiated power, without degrading the modulation characteristic. With *S*₈ closed the dynamic impedance of *D*₂₂ depends on the setting of *R*₇₅ and a variable loss is introduced into the drive network for *Tr*₃₅. With *S*₈ open, *D*₂₂ has no effect and full power is obtained. Tuning-up is best carried out with each stage in turn beginning with the

oscillator and with an absorption wavemeter loosely coupled to the coil concerned. A 75Ω dummy load should be connected to the output socket, *P*₃, during this process, with a simple diode rectifier connected across it to give a comparative indication on a meter of the r.f. power output.

It is essential to realise that the tuning adjustments, which give maximum power output^{2,5} will also give severe modulation distortion and hence serious, sideband 'splatter'. If at all possible an oscilloscope should be connected across the monitoring rectifier so as to be able to view the actual modulation waveform. Trimmers *C*₇₂, *C*₇₃, and to a lesser extent, *C*₆₈, *C*₆₉, should then be varied slightly from the settings which give maximum output, until good modulation linearity is achieved. The output carrier level will drop from about 2 to 1.5W, but the recovered audio voltage in a receiver will increase considerably.

The telescopic whip aerial is quoted as being $\frac{1}{4} \lambda$ in length rather than the usual $\frac{1}{2} \lambda$ since this gives a better match to the nominally 75Ω transmitter output impedance. It is assumed that the transmitter is initially tuned up as described above and with the whip aerial retracted.

The parallel tuned circuit formed by *L*₂₅ and *C*₇₅, which is in series with the aerial lead is broadly tuned to 11MHz to help to decrease pick-up of signals at the first intermediate frequency.

The microphone pre-amplifier is shown in Fig. 6 and uses a complementary non-inverting feedback amplifier. In the author's equipment a surplus dynamic microphone (ex-Pye equipment) is used and the overall gain is such that full modulation (about 98%) is obtained when speaking about four inches from the microphone. If necessary the gain may be reduced by connecting a resistor in series with *C*₈₃. Great care is necessary in this type of equipment to avoid rectification of the intense radiated signal in the early audio stages. If this happens, high-frequency oscillations occur in the modulator and the transmitter is useless. The two r.f. chokes, together with *C*₈₀ and

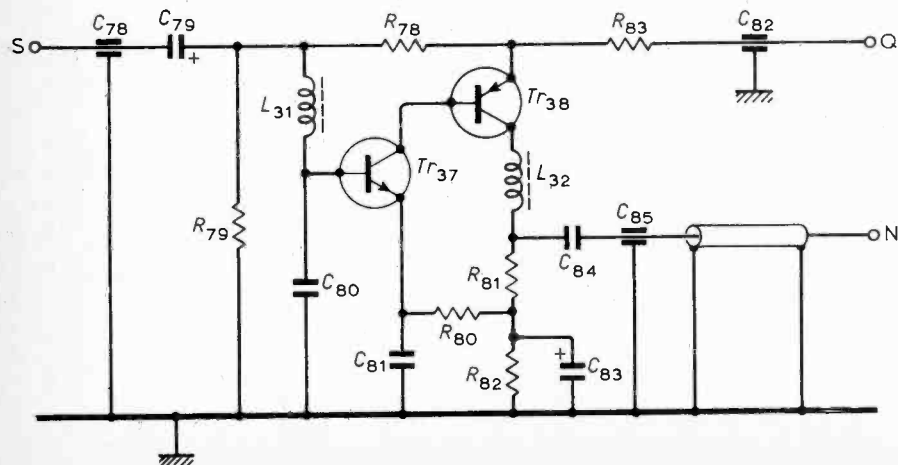


Fig. 6. Circuit of the microphone pre-amplifier.

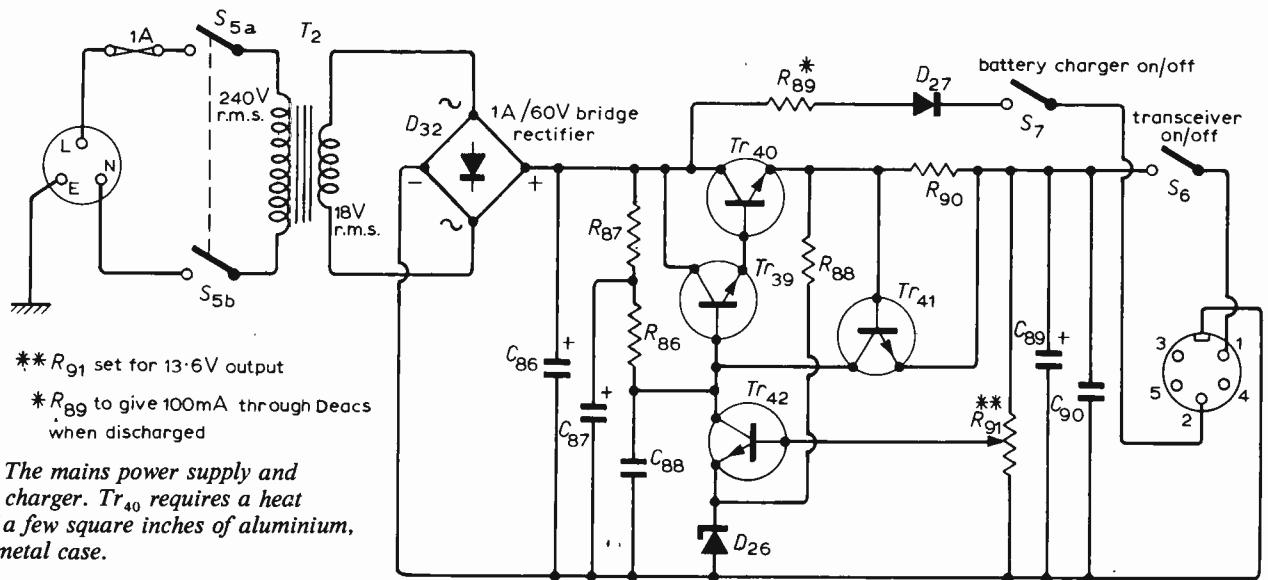


Fig. 7. The mains power supply and battery charger. Tr_{40} requires a heat sink of a few square inches of aluminium, or the metal case.

C_{81} help to avoid this possibility, the choke in the collector lead to Tr_{38} being particularly effective. It is a wise precaution to build this pre-amplifier on a separate subchassis or even into a screened box.

Construction

With equipment of this complexity and compactness, it is considered superfluous and also too difficult, to give highly detailed constructional information. Potential constructors would no doubt have their own ideas on circuit modification and layout and this section therefore deals with the more general points.

The prototype was originally intended to have a variable frequency transmitter and therefore the packing density used in the actual transmitter p.c. board is far less than on the receiver. Two main boards are used, each measuring 14 x 6cm. and the microphone pre-amplifier uses a separate small board. One of the large boards contains all the circuitry in Fig. 5, while the other contains the circuitry of Figs. 2, 3 and 4 together with the receiver tuning dial assembly and loudspeaker. Epoxy-fibre-glass board was used with copper layers on both sides. One surface remains almost intact except for 2mm diameter discs removed around each component hole and is used as an earth plane. All components with one lead going to the negative supply line are soldered directly to this upper copper surface. The advantages over a single-layer board are as follows. (a) Very low inductance earth paths are obtained. (b) The wiring on the reverse side of the board is not too crowded. (c) The wiring is shielded from the components and vice versa. In order to save space, components are mounted with their axis perpendicular to the board and advantage is taken of coil 'cans' and large decoupling capacitors to shield critical components from each other. Plastic encapsulated transistors are more suited to compact forms of construction than the metal cased types and best of all for their small size are the Ferranti E-line devices.

Accessories

In order that the transceiver should live up to its design goal of being 'ever-ready'; two

other pieces of equipment are needed: a mains power supply and charger, and a similar unit for use in a car. Fig. 7 shows the circuit of the mains unit. Overcurrent protection is afforded by R_{90} and Tr_{41} ; with R_{90} equal to 0.5Ω the short-circuit current is limited to about 1A. A fairly high voltage is used for the transformer so that a resistor, R_{89} , can be used to supply a constant current of 100mA to the Deacs (Leclanché primary cells are not suitable) for charging purposes. This does mean however that a heat-sink is required for Tr_{40} . Diode D_{27} is included to avoid discharge of the Deacs if for any reason the mains supply to the charger is switched off with S_7 still in the charge position.

The mobile power supply is shown in Fig. 8 and is used both to filter out noise on the car electrical system and also to limit the supply voltage to the transceiver to 13.6V. If a higher voltage than this is used the audio output pair are liable to be destroyed by thermal runaway; these are the only vulnerable parts of the unit however. If the car battery voltage is less than 13.6V, Tr_{43} is fully on and only about 0.2V is lost. This low voltage drop

is the main reason for specifying a germanium transistor for Tr_{43} . In order to provide charging facilities for the Deacs, Tr_{42} acts as a constant current source supplying 100mA to the Deacs whenever the car battery voltage is above the Deac voltage.

Conclusion

In terms of the initial design goal of a miniature complete two-metre station, the transceiver described in this article has proved very successful. It has given the author and his wife (G8ENO) many enjoyable contacts with stations in most parts of England and some in Europe when operated with a beam aerial on the house. With the whip aerial, ranges are less but distances up to 50 miles have been obtained.

Components list

If diodes or transistors have no type numbers indicated, almost any silicon planar types of appropriate power rating and gain will do. Thus for low power n-p-n transistors, the BC109 or ZTX302 families are appropriate and for p-n-p,

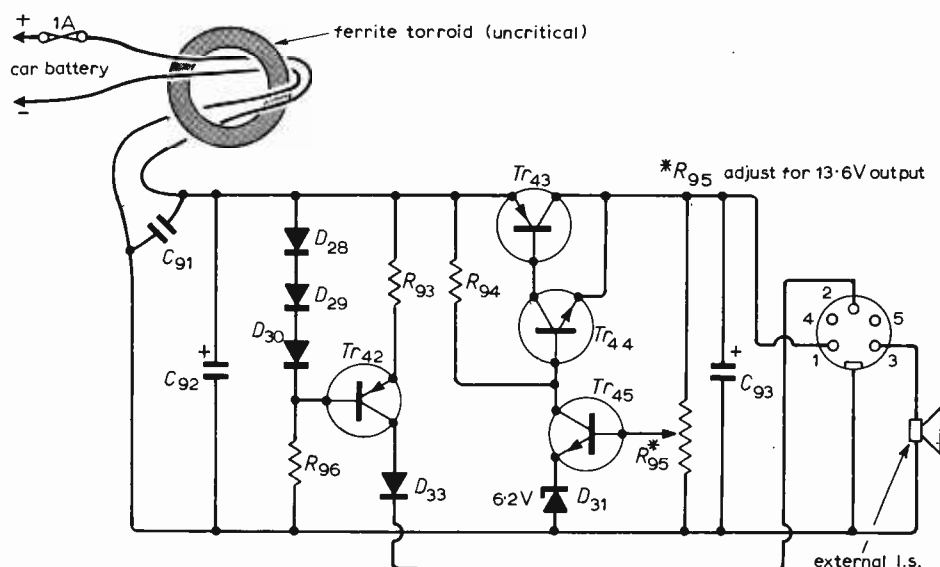


Fig. 8. Power supply and charging circuit for use with a 12V car battery.

the BCY70 or ZTX502 families. Suitable diodes are the OA202 or 1N914 types.

Transistors

1, 3, 4-2N5245	30, 31-2N744
5-E300	33-2N918
6, 7, 8, 9-ME3002	34-BFY90
10-2N3820	35-2N3553
11-AC187	36-BLY33
12-AC188	40-2N3054
24-2N3819	43-AD149

Diodes

23, 24-FD101 32-1A/60V bridge rectifier e.g. REC 41A

Integrated circuit

1-TAD100 (Mullard)

Resistors

1-10k	33-120	65-10k
2-100	34-6.8k	66-1k
3-100	35-18k	67-47k
4-10k	36-10k	68-100k
5-3.3k	37-560	69-5.6k
6-6.8k	38-2.7k	70-1.8k
7-22k	39-680	71-12k
8-10k	40-100k	72-470k
9-5.6k	41-10k	73-100
10-2.2k	42-1.5k	74-560
11-1k	43-15k	75-1k preset
12-5.6k	44-56k	76-10
13-1.5k	45-10k	77-10
14-470	46-22k	78-15k
15-560	47-12k	79-4.7k
16-820	48-4.7k	80-1k
17-150	49-68k	81-4.7k
18-39k	50-39k	82-4.7k
19-27k	51-1k	83-4.7k
20-150	52-22k	84-1.5M
21-220k	53-22k	85-5k 1in
22-150k	54-6.8k	86-750
23-8.2k	55-47k	87-22
24-8.2k	56-22k	88-270
25-390	57-18k	89-See Fig. 7.
26-1.5k	58-39k	90-0.5
27-6.8k	59-39k	91-See Fig. 7.
28-6.8k	60-68k	92-10k 1in
29-820	61-1.5M	93-10
30-180k	62-10k	94-820
31-100k	63-1k	95-See Fig. 8.
32-12k	64-100k	96-82k

Capacitors

1-5μ	48-1μ
2-470μ	49-1μ
3-470μ	50-2.5μ
4-470μ	51-10n
5-470μ	52-6.4μ/10V
6-5μ	53-2.5μ/10V
7-10μ	54-2.5μ
8-2000μ	55-10n
9-22μ (poly)	56-10n
10-1000μ	57-1μ
11, 12, 13-3/CG80-03	58-1000μ
(Wingrove and Rogers)	59-82μ
14-3 to 10μ	60-33μ
15-10n	61-470μ
16-15μ (poly)	62-1000μ
17-50n	63-3 to 15μ
18-47n	64-3 to 15μ
19-10n	65-470μ
20-30μ (poly)	66-470μ
21-470μ (poly)	67-10n
22-470μ (poly)	68-3 to 15μ
23-10n	69-3 to 15μ

24-470μ	70-470μ
25-100μ	71-10n
26-47μ	72-3 to 15μ
27-1000μ	73-3 to 15μ
28-10μ	74-470μ
29-470μ	75-47p
30-470μ	76-10μ
31-0.1μ	77-470μ
32-10n	78-1μ
33-50n	79-1μ/10V
34-4μ/10V	80-470μ
35-0.47μ	81-470μ
36-10n	82-1μ
37-10μ/10V	83-2.5μ/6V
38-50n	84-0.1μ
39-50n	85-1μ
40-3.3μ/10V	86-3000μ/50V
41-1μ/30V	87-200μ/50V
42-0.1μ	88-0.1μ
43-10μ/10V	89-100μ/25V
44-300μ/6V	90-0.1μ
45-300μ/6V	91-0.1μ
	(disc ceramic)
46-10n	92-100μ/25V
47-10μ/10V	93-50μ/25V

Inductors

If no reference numbers are indicated, the inductors are r.f. chokes consisting of two turns of enamelled copper wire (gauge unimportant) wound on a ferrite bead type FX1115 (Mullard). All others are 5mm internal diameter with appropriate ferrite core.

- 5½t, tap 1t from earthy end
- 12t
- 7½t
- 6t
- 5½t, tap 1t from earthy end
- 3½t
- 45.7cm of 38 s.w.g., close wound
- as 7 but centre-tapped and with 4 turn link wound at earthy end
- 25.4cm, 38 s.w.g. close wound

Transformers

- not critical. e.g. laminations 2.5 × 2.5cm of 8mm thickness. Primary 150t, secondary 370t using 32 s.w.g.
- not critical (240V r.m.s. to 18V r.m.s.)

Crystal oscillators


1-66.66MHz overtone type HC-18U

References

- Loudspeaker transmit/receive switch, D.A. Tong, *Wireless World*, October 1970, p.476.
- The G8ARV two-watt, two-metre transistor transmitter, D. J. Taylor, *Radio Communication*, Vol. 45, 1969, pp.840-5. The G8ARV two-metre portable receiver, D. J. Taylor, *Radio Communication*, Vol. 46, 1970, pp.664-669.
- Variable frequency oscillator, E. O. Seiler, *OST*, November 1941.
- Mobile 166MHz a.m. communications receiver, D. Singh, *Mullard Technical Communications*, Vol. 10, 1968, pp.14-29.
- V.h.f. transistor transmitters for a.m. and f.m. operating directly from vehicle batteries, L.M. Cash, *Mullard Technical Communications*, Vol. 10, 1968, pp. 2-13.
- Parasitic oscillations in v.h.f. power amplifiers, G. S. M. Teale, *Mullard Technical Communications*, Vol. 10, 1968, pp.279-284.
- A battery-saving circuit for portable communications receivers, D. A. Tong, *Wireless World*, March 1972, pp.124-125.

H.F. Predictions — April

The charts here are based on an ionospheric index of 46, giving conditions similar to 1966. There are indications the index could be 10-12% higher than this, but with a similar situation last year the measured value was 10% lower than predicted. A higher index would be noticeably beneficial to the North Atlantic route. Seasonal ionospheric changes and longer days in the northern hemisphere flatten the Far East curve considerably. Evening fading is expected to be troublesome on all routes and a period of several subnormal days at the middle of the month looks likely.

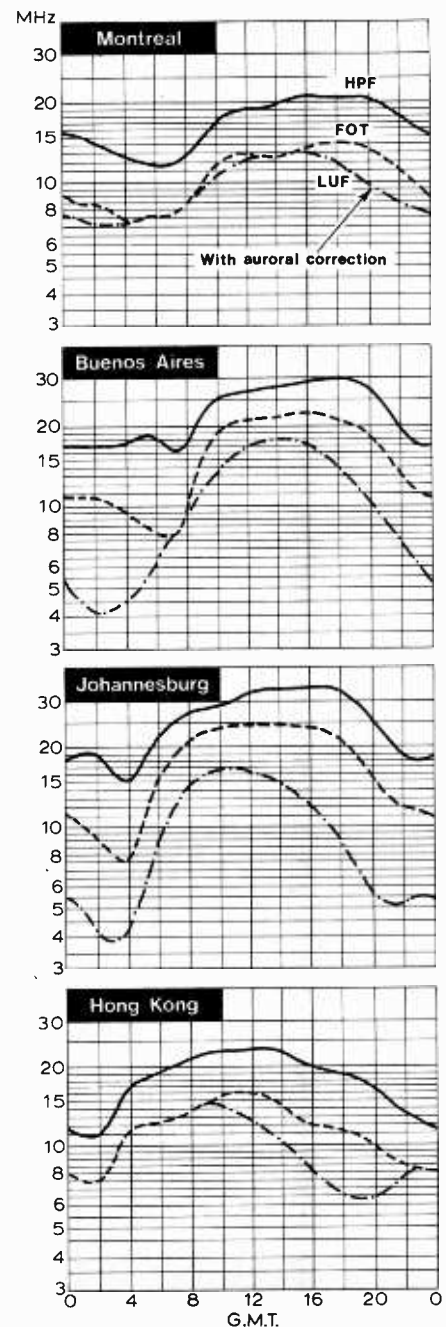

The Electronic Retina

One approach to optical character recognition

by N. A. Singer

With the advent of high speed computers novel methods of data input have been developed. One of these that has been working successfully is optical character recognition (o.c.r.), whereby 'raw' office documents may be used directly as input data. An o.c.r. system which was described in 1967 gave a tenfold improvement in error rate over a punched card system used to feed in a similar volume of data¹. Modern systems have a worst case error rate of one character in 10^3 , for characters well below the E.C.M.A. (European Computer Manufacturers' Association) standard², and of one in 10^6 or higher for characters meeting this standard. Reading speeds of up to 2400 characters per second are possible, and there are systems which can handle multiple printing 'founts' and even hand printed characters.

One of the basic methods of recognizing characters by reading machinery in the field today is called pattern detection. Pattern detection, or 'mask matching', can be thought of as an electronic extension of the mechanical process shown in Fig.1. Image information is compared simultaneously against all sets and values representing the patterns the machine can recognize. These stored sets of values are often called 'masks' because of this analogy.

In the design of o.c.r. systems, there are two main avenues of approach: the flying spot scanner technique; and the 'electronic retina'.* In the flying spot scanner, the character is scanned using a spot of light in order to gather information about the outline of the character (Fig.2). The spot size and number of sweeps per character determine the number of data sampling points. At selected instants in time the reflectance is measured to determine whether the spot is viewing a black or white area. The basis upon which this decision is made varies from the simple to the very sophisticated. An example of the former is found in a simple reading machine, wherein a fixed voltage level is set as a threshold. Any point which is found to indicate less light than is fixed by this threshold is considered to be black. Perhaps the most sophisticated system of

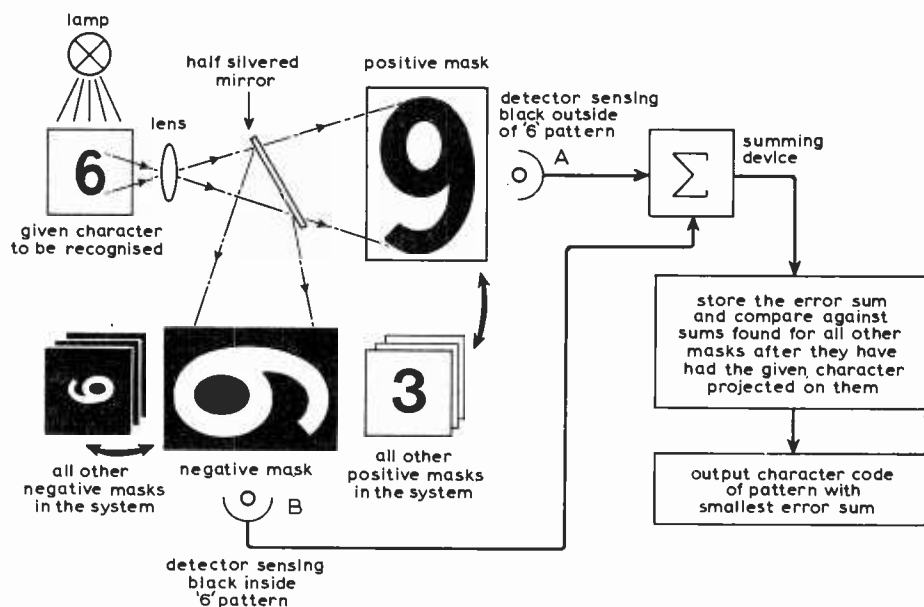


Fig.1. Basic process of pattern detection by 'mask matching'. Information from a scanner or electronic retina is compared simultaneously with all the sets of values representing the patterns the system can recognize. These stored sets of rules are often called masks because of this analogy.

this type to date is one which defocuses the spot and measures the average reflectance near the spot so that this value may be compared with that at the highly focused spot itself and a black-or-white decision made on a localized basis.

As soon as the black/white decision has been made, the scanner continues to the next point to make a similar decision. This process continues, covering an area roughly equivalent in width to that of the characters being read and a height of twice that of the character. (The extra height is made available to allow the character to be misplaced with respect to other characters in the line.) Each of the black/white decisions made is stored in a memory (usually consisting of digital shift register elements). The memory is then periodically examined by some form of recognition circuitry to identify the character.

The most general approach to determine the time at which the examination should be made is to look for a complete vertical column of sampling points that contain

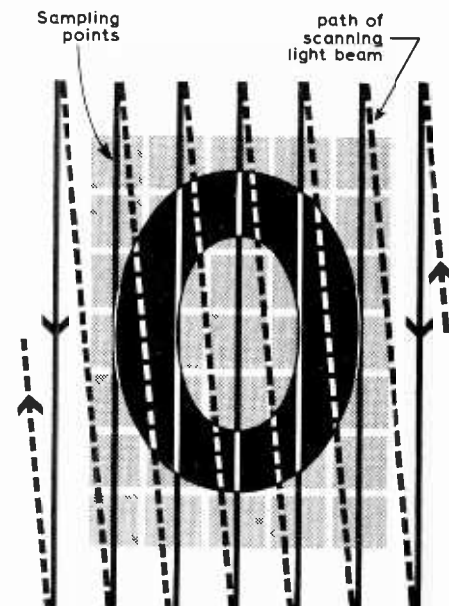


Fig.2. Flying-spot scanner principle. In practice much higher definition is used.

*Electronic Retina is a trademark of Recognition Equipment Incorporated.

no black elements, indicating the white border circumscribing a character. This does, of course, force on the user of the scanner a requirement for high quality printing. For example, many typewriters, printing twelve characters to the inch with a fabric ribbon, cause most of the characters to touch. The scanner manufacturer's philosophy is that this constraint can be overcome by typing or printing only ten characters per inch and using 'one time' ribbons. This form of input usually implies the use of an electric typewriter.

Another approach is to set up a precise timing arrangement relying on the characters being spaced precisely ten to the inch and locating each character as a function of its distance in time from the first one.

Scanning techniques such as those described above will generally result in recognition rates varying from 200 to 2,000 characters per second, depending upon the complication (and thereby cost) of the equipment utilized. Non stylized characters such as those found on the usual office typewriter or high speed line printer are generally read with reject rates approximating to one character in 1,000 and error rates approximating one character in 10,000. These rates can generally be improved upon through the use of highly stylized characters. If one goes to the extreme case of the characters normally used for magnetic ink character recognition, E13B (as employed on British bank cheques) or CMC7 (devised in France by Compagnie Des Machines Bull and sponsored by E.C.M.A.), advanced scanners operating on them may achieve one-tenth of the error and reject rates respectively.

To understand, at least in part, the reasons for the scanner's rather unsatisfactory reading characteristics we must consider a television receiver. In this instance, a high resolution scanning spot is generated that is of constant size and continually forms a picture of unchanging dimensions. Yet, even with such extremely simple circuit requirements, the receiver is rarely able to display a circle as a circle. Extrapolating this to the scanner, usually a low resolution system, the non-stylized letter 'I' is readily distorted to the number '1', the 'O' to 'D', the 'B' to an '8' and so forth. The degree of distortion determines whether the character becomes a reject or a substitution. As a result of the scanner's rather unsatisfactory characteristics it was concluded, by a leading authority in the o.c.r. field in 1961, that the best approach would be to emulate nature and copy the human eye. The rod and cone sensor structure of the retina of the human eye would be analogous to a matrix of photocells, onto which the character could be focused. The cells being held physically constrained, their dimensions with respect to each other would be held constant, thus character distortion could not occur. Until the introduction of solid state devices, the large number of circuits required to build such a machine would have cost far more

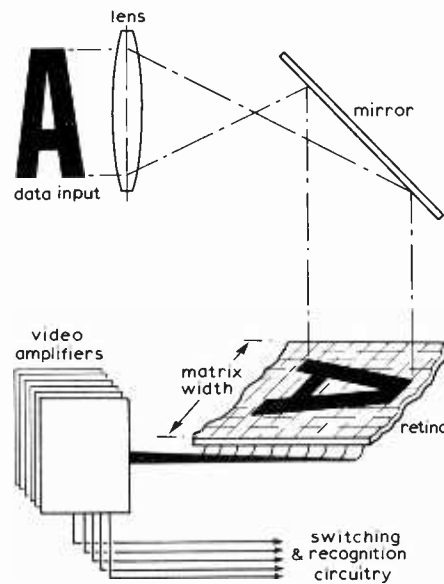


Fig. 3. The retina and associated optical and electronic components.

than the savings it could offer to the user. However in 1963, the first viable machine of this design was delivered on a production line basis to an insurance company in the U.S.A. The device was trade named the Electronic Retina and is generally referred to as the Retina, the entire recognition system of which the retina is but part being named the Electronic Retina Computing Reader.

The basic operation of the retina is simple. Its matrix, like the scanner, is slightly wider than one character width (Fig. 3). However, because it is not subject to distortion its height can be increased virtually at will. Current machines manufactured on this principle have a retina of 576 silicon photo-

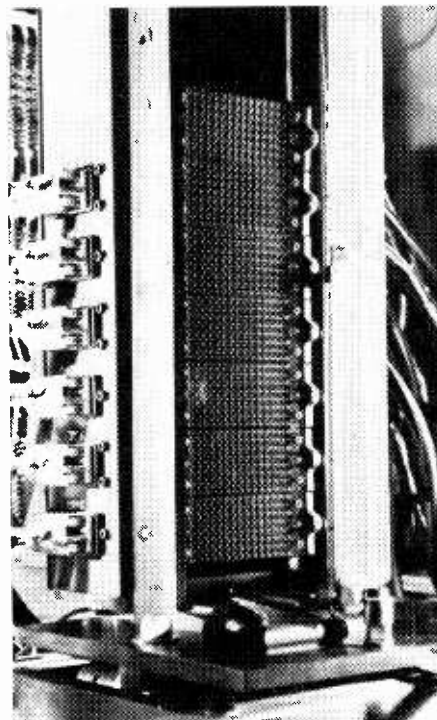


Fig. 4. Electronic retina, showing its construction from seven sections, one containing only two columns of cells forming the 'line finder'.

transistors arranged in a matrix 12 devices wide by 48 devices high. The optically projected and magnified character image is arranged to cover part of the matrix approximately 10 devices wide by 14 devices high. This design allows for vertical misalignment of characters up to one character height up or down.

The retina could use the techniques employed by a scanner making black and white decisions. In a simple case the output of each cell could be compared against the standard voltage and a black-or-white decision made. However, since structural data from the entire character are available simultaneously, the system was designed, without substantial cost increase, such that an absolute black/white decision was unnecessary. In this system the signals from the 576 phototransistors are amplified, each photocell signal by its discrete video amplifier, part of the amplifier's function being to provide a.g.c. and black level reference. The amplifier outputs are of analogue form.

From these outputs four decisions have to be made in the following order:

- 1 Where the character image is on the retina (vertical position).
- 2 If the character image is centred on the retina (horizontal position).
- 3 Which character of the recognition system vocabulary most closely matches the character image on the retina.
- 4 Whether there is sufficient difference between the best match (3) above and the next best match in the system's vocabulary (establish 'confidence level' of correct decision).

A working system

Eight o.c.r. systems based on the electronic retina principle described above have been installed in the U.K. An o.c.r. bureau system has been chosen as the subject for the following description because it gives the greatest insight into both the capabilities and the problems associated with a large system of this type. The equipment was installed in November 1970 and its use now extends over a twelve hour day, reading a vast array of printed or typewritten documents and pages ranging from card stock to airline tickets in thickness.

The recognition circuitry is basically a pattern detection system which looks for black and white in the correct cells of the electronic retina onto which the character under examination is projected. This is compared with stored patterns in its memory (or 'mask' bank). So long as the detected pattern is sufficiently like a stored one and different enough from the remainder a definite decision is reached. Those readers who have printing experience will have found difficulty in differentiating between, say, the character 'O' of one font and the '0' (zero) of another. In a similar fashion the accuracy of an o.c.r. system is improved by using only selected fonts and enabling only those fonts which are required under programme control from the controlling computer. This becomes even more critical when reading lower case or hand printed characters and punctuation as in

publishing work. Indeed it is perhaps the hall mark of an o.c.r. system that it can successfully read data for publication in a non-stylized font because of the reduced difference between (a) lower case characters, for example 'e' and 'a', and (b) punctuation characters, for example full stop and comma.

The system described here has 'masks' for the following fonts:

- IBM 1403
 - IBM 1403 modified
 - OCR B
 - XO4 upper and lower case for publication work
 - E13B (the font on bank cheques)
 - 407E
 - 7B
- } fonts used on credit cards

(A hana-print option is available but is not fitted to this system.)

The first three of the above are non-stylized fonts and common typewriter fonts.

The remainder are special fonts for particular applications. It is a common occurrence for fonts to be intermixed on a particular document. A vertical bar (a black vertical line of particular width) or a code character may be used to switch fonts, again under programme control.

The o.c.r. system includes: a programmed controller (computer working on line) complete with magnetic tape transports, a line printer and other peripherals; a paper transport system; a document carrier for small items being read, and a page carrier for larger items, capable of handling a large range of intermixed sizes and weights of paper; a Retina and associated amplifier circuitry (Fig. 4); and a recognition unit with the 'masks', coding and other circuitry (Fig. 5).

The Electronic Retina, as already mentioned, consists of an array of 567 phototransistors (Fig. 6) arranged in a rec-

tangular pattern 48 units high (rows *a* to *z* and *aa* to *xx*) by 12 units wide. In addition it has a line finding extension of 8 units (rows) high by 2 units wide. The retina is slightly concave to ensure sharp focus of the image across it. Each n-p-n phototransistor is connected in the common emitter configuration, and its leakage is increased by light falling on it. In each of the 576 associated video amplifiers a nominal 526 kHz carrier signal is amplitude modulated by the output of the phototransistor. After passing through the a.g.c. stage the signal is demodulated and fed to video switches and character analysers, as shown in Fig. 5. The video switches (a diode switching matrix), under control of a six-bit 'centre' code received from the 'centre' storage and 'jitter' logic allow only a band of video outputs from the retina (16 high), to be fed to the amplitude correlators. The remaining outputs are unused.

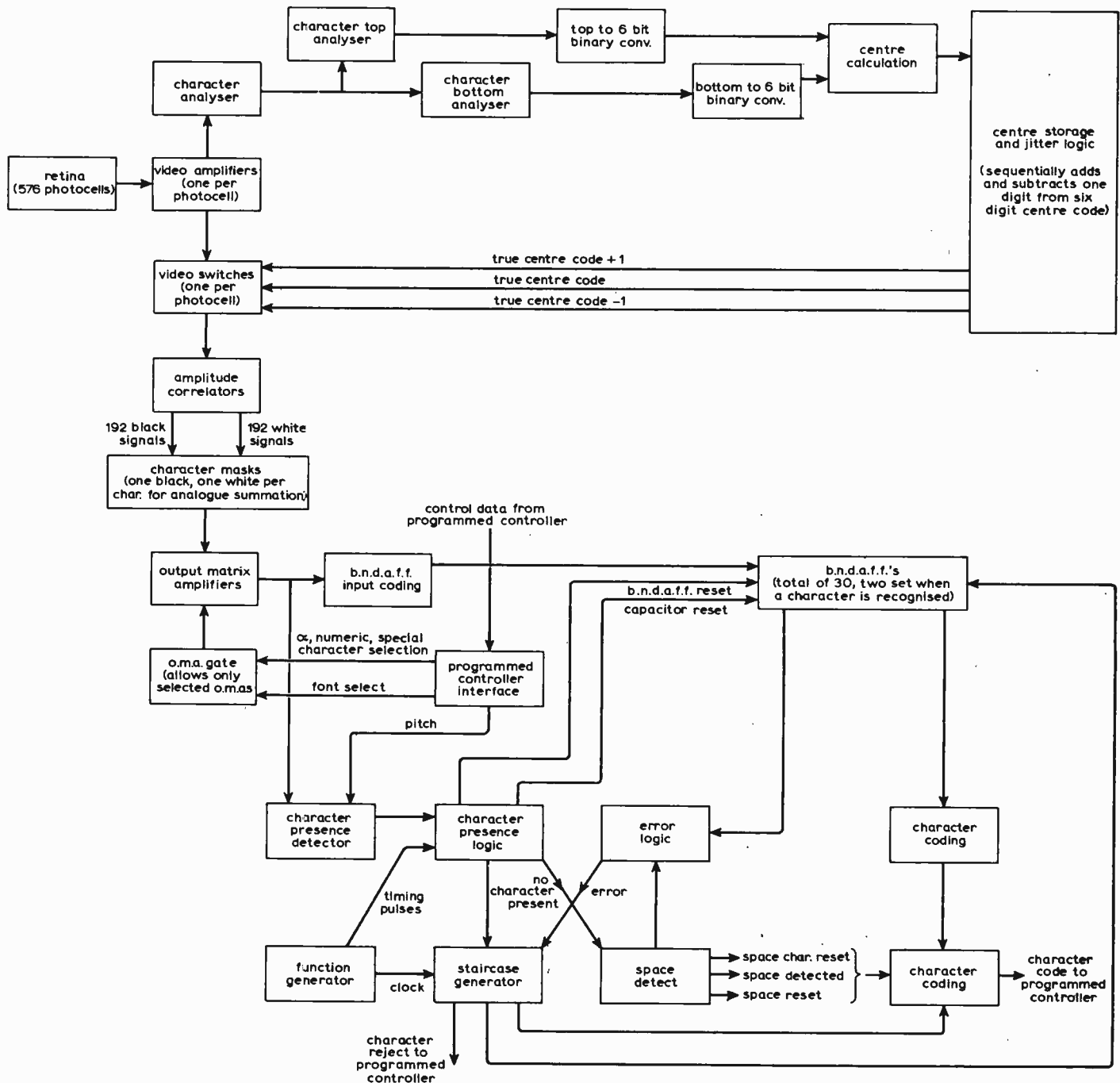


Fig. 5. Block diagram of recognition system based on the electronic retina.

In the character analyser each line of cells in the retina is examined for any black content. As a character passes across the retina (inverted by the lens system), approximately 16 out of 48 rows will have a black level signal present in them. Outputs from all 48 rows of the retina are now examined by the character top and character bottom analysers. The 45 AND gates which constitute top analysers give an output when the row under examination is black, the one below it is also black, and the one above it is white. This indicates that the top of a character is in that particular row of the retina. For instance the gate which analyses a top in row *q* of the retina will give a high output when there is a top in row *q* since all of its inputs will be high at this time, showing that row *p* is white, row *q* is black, and row *r* is black. Hence the criteria for a top of a character are a minimum of two adjacent black rows and at least one white row immediately above, except for row *b* which requires a minimum of three black rows with at least one white row above.

Bottom analysis of a character is provided by 44 AND gates and is similar to top analysis. The criteria for a character bottom are at least one black row and a minimum of three white rows immediately below it on the retina, with the exceptions that a bottom in *vv* only requires two white rows below and a bottom in *ww* only requires one white row below. It should be noted here that only the highest top and the highest bottom are selected within the logic and various conditions such as the character appearing too high or too low on the retina inhibit further processing of the video signals.

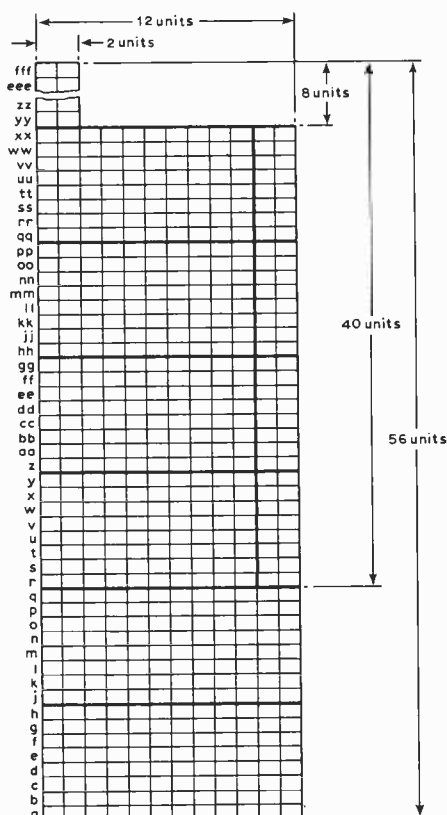


Fig. 6. Physical layout of the electronic retina.

Beloppet för ej gärdas					Anteckningar för ej gärdas i vita fältet nedan	
Hälsotag	Exc.	DIG	Kroner	Öre	Kroner	Öre
460451	4		137	31	137	6255

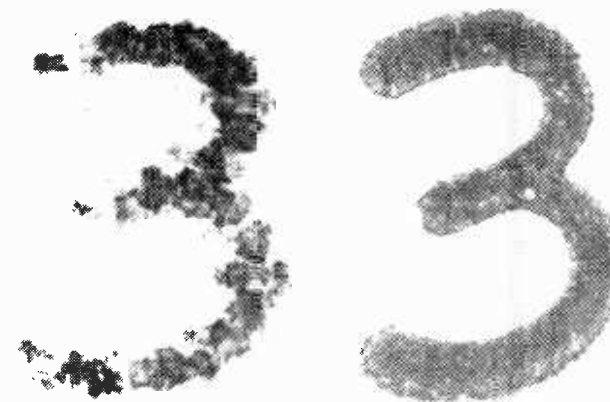


Fig. 7. Part of a Swedish bank giro form (read by an o.c.r. system) showing, enlarged, a comparison of a good and a deteriorated character — demonstrating the need to darken voids and whiten smudges.

The gate output (one of 45) indicating a character top in that row is now converted to a six-bit binary code and fed to the centre calculation circuitry. Similarly the line indicating the character bottom is also converted to a six-bit code and fed to the centre calculation circuitry. Here the two six-bit codes are added and shifted right one place, giving a centre code, corresponding to the centre of the character under examination of the retina. This six-bit code is now applied to the jitter control circuitry where, under normal operation the centre code is modified alternately one line up and one down. This technique gives a higher reading accuracy and will be described more fully later. The centre code is decoded to one energized line (out of 96) and applied to the video switches which gate only the selected area of the retina containing the character under examination to the recognition circuitry.

Recognition circuitry. Now 192 analogue signals (16 by 12 matrix), which correspond to the image of the character on the retina, are fed to the amplitude correlator circuitry, which compares each cell output to the surrounding 20 and modifies the apparent signal from each particular cell depending upon what is occurring in the cells surrounding it. This circuitry helps to whiten smudges on the paper and also to darken any voids contained in the character under examination (Fig. 7).

A complete pattern cannot appear around the cells near the edge of the retina but a phantom line voltage simulates, as required, the total output from the missing cells in these patterns. A total of 192 separate summing matrices obtain algebraic sums of the 20 cell patterns. That is, 192 identical patterns of 20 cells each (some of the cells are phantom) are summed and averaged. All phantom cells are considered

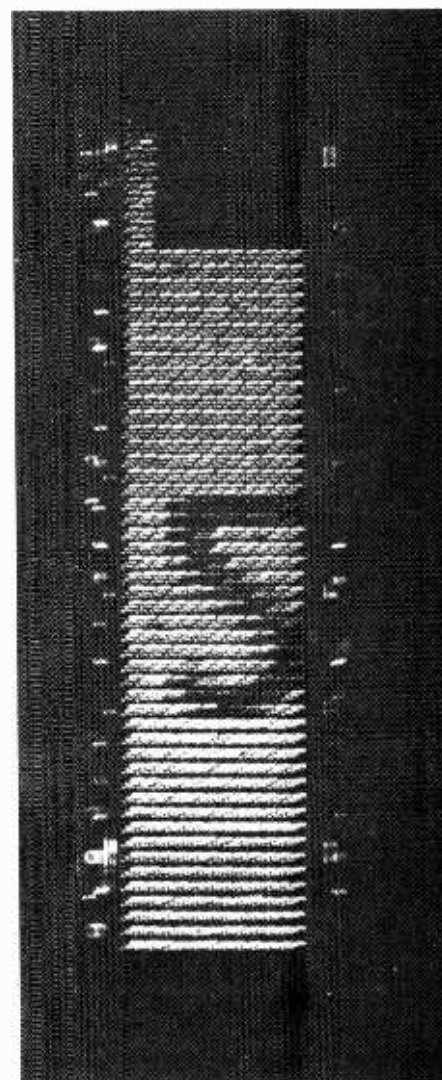


Fig. 8. A character image passing across the retina. The line finder extension can be seen at the top. Note that the character, a '2', is inverted by the lens system.

to be white. Further developments of this technique have been discussed.³ The amplitude correlators give both a black and white d.c. output of approximately complement form for each cell in the selected area of the retina. These 192 black and 192 white d.c. signal lines are connected to the character masks. Two 'masks,' one black and one white, are related to each character. The white 'masks' contain resistors in the expected white areas of the character to which the 'mask' relates. The black 'masks' contain resistors in the expected black areas of the character. White amplitude correlator outputs are connected to black mask inputs and black amplitude correlator outputs to white mask inputs. This corresponds to placing a positive or negative grid of the character over the mask, much as a photographic negative might be matched with a print made from it. The black inputs correspond to a positive, the white inputs to a negative (see Fig 1).

If the character on the retina exactly overlays the mask, the sum of the outputs in that case is such to indicate a zero mis-match for that character mask. Any black detected in the white area of a mask, or any white detected in the black area of a mask results in a decreased d.c. output from the mask. Therefore, if a character does not exactly overlay the mask, a lower output voltage is obtained from the mask. Thus the character mask which least mismatches the character on the retina delivers the highest output voltage. More weight is placed on certain areas of a character by connecting these cell outputs to mask resistors of lower values (for example the tail of the letter Q). Each output line from its associated character mask (up to 360) is now applied to its unique output matrix amplifier (o.m.a.). If very high accuracy in reading is required only certain o.m.as are energized. For example, these may be alphabetical, numerical or a particular font required under control of the programmed controller.

When the output from a particular o.m.a. rises above a threshold level, character presence is detected, and a staircase generator is primed and, after a delay, activated. The circuitry which actually decides which character is present on the retina is termed 'best null detector and flip flop' circuitry (b.n.d.a.f.f.).

A uniquely coded pair of b.n.d.a.f.f.s (out of a total of 30) is set for a particular character, by an o.m.a. peak incremented by the staircase generator. Although the staircase generator may have been primed by a different o.m.a. signal, a larger peak following will be stepped up by the staircase and will set the two associated flip flops indicating the presence of a particular character. After these two flip flops have set, the staircase generator proceeds to count four more steps, in order to check if more flip flops are about to set.

If more than two b.n.d.a.f.f.s set then an error indication is generated, showing that there is insufficient difference between the outputs of two masks to ensure a reliable character decision. The outputs from the 30 flip flops are fed to the character coding

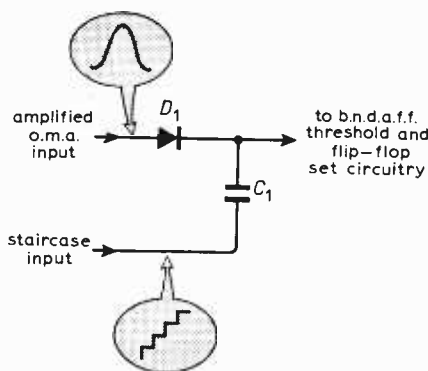


Fig. 9. Method of setting flip flops of 'best null detector and flip flop' unit (b.n.d.a.f.f.).

circuitry which supplies a b.c.d. code to the programmed controller.

A space is detected by allowing a time, equal to 170% of the time taken for a character to transverse the retina, to elapse after the previous character has been detected.

The code representing the character recognized by the recognition circuitry is fed to the programmed controller which stores it and after any required editing of a number of characters, this information is transferred to magnetic tape. Because characters are appearing on the retina at 500 microsecond intervals (for characters at 10 per inch) the computer must be interrupted during any edit routine by a signal indicating that a character has been recognized. This is a real time programming problem and the ways of overcoming this and other difficulties are beyond the scope of this article.

The line finder. The line finder extension of the retina (8 units high by 2 units wide) is employed only when the retina is used to read pages on the page carrier. This extension (seen in Fig. 8) is employed to detect a next line top below the line being read. When an end of line is detected a code

generated by the next line top logic which causes the page to shift to a new position. This ensures that the beginning of the next line will be in the reading area of the retina. Jitter is a technique which basically moves the 'window' on the retina, through which the character is viewed, one row of cells up and one down about the calculated centre. It has the effect of moving the character masks up and down over the unknown character while a decision is being made for the character under examination. The application of jitter in this system has been previously described, but its main advantage is the increase in reading accuracy. On badly formed characters this increase may be as great as 20%.

Setting the b.n.d.a.f.f. Fig. 9 shows the method of setting the b.n.d.a.f.f. flip flop, where the output is the sum of the o.m.a. peak plus the staircase input. Initially C_1 is discharged, hence when the associated o.m.a. output rises, D_1 is forward biased and C_1 begins to charge. When the o.m.a. output has passed its peak and is falling away D_1 is reverse biased, causing the peak value of the associated o.m.a. voltage to be stored on capacitor C_1 . The peak o.m.a. signal primes the staircase generator which is triggered after a delay and this 'pumps up' the staircase input terminal, causing the output to rise in steps.

Referring now to Fig. 10, both the o.m.a. and the staircase input are buffered, before being applied to the summing circuitry previously described. The capacitor C_1 (shown with the asterisk beside) is the capacitor which stores the peak o.m.a. value, and has the staircase input added to it. When the threshold of +6 V together with the forward volt drops of D_2 and the emitter-base junction of Tr_3 are exceeded, a negative pulse is generated as Tr_3 turns on passing through C_2 to turn off transistor Tr_4 , setting the flip flop. The buffered outputs of this flip flop are available to drive associated coding circuitry. As previously stated, two b.n.d.a.f.f. flip flops are set for any particular character. The o.m.a. peak storage capacitor is reset after



Character reading system with electronic retina in tall central cabinet. On the left is a document carrier, and on the right a page carrier. The concertina-like structures shroud the character image from extraneous light.

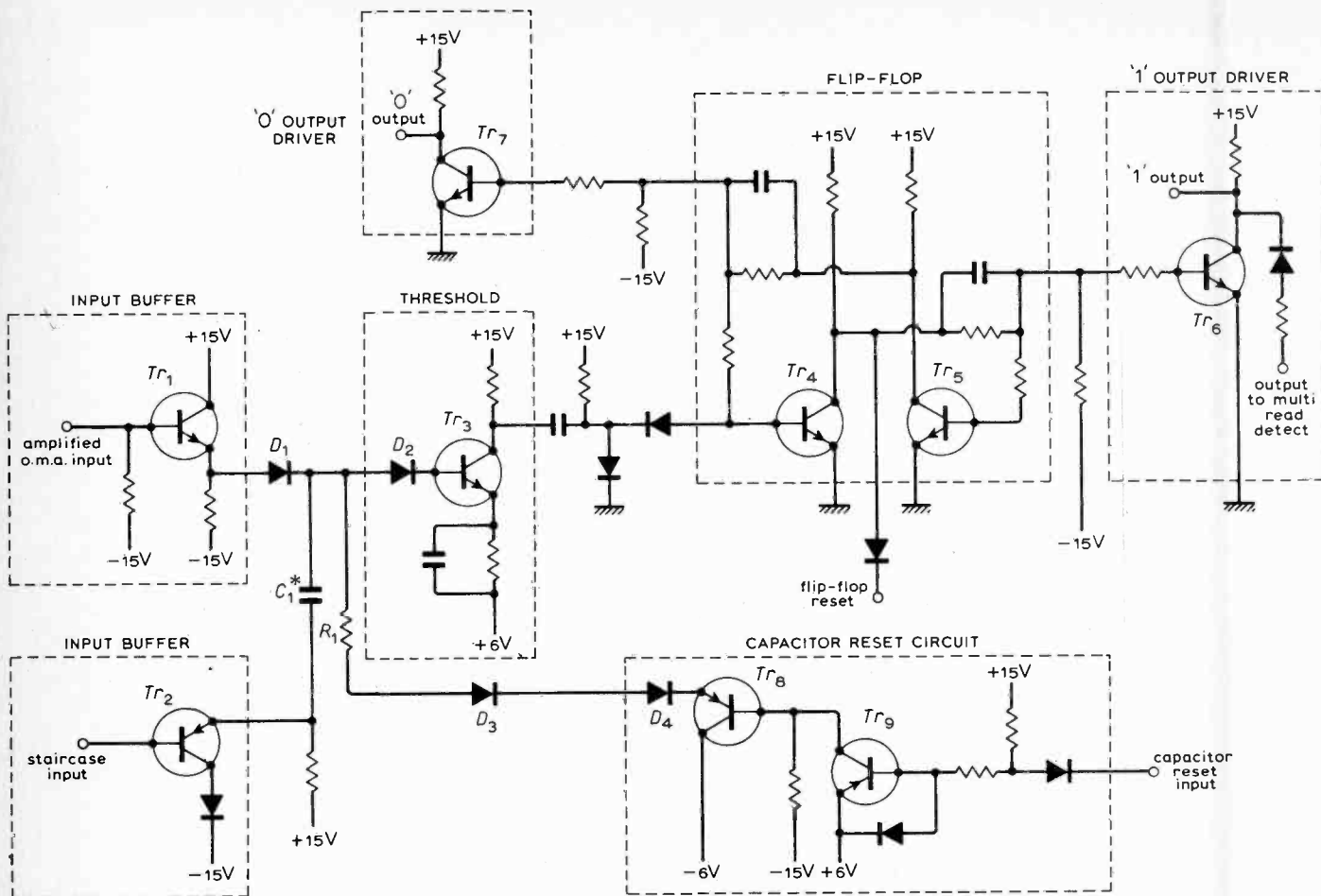


Fig. 10. Circuit diagram of a 'best null detector and flip flop' (b.n.d.a.f.f.).

a delay from the commencement of the staircase generation. This is achieved by applying a positive pulse to the capacitor reset input, which causes transistor Tr_9 to turn off. As transistor Tr_9 turns off Tr_8 is turned on, causing capacitor C_1 to discharge through R_1 , D_3 , D_4 and Tr_8 to approximately 5 volts. The output code to the programmed controller representing the character recognized is left available until another sample is taken. Immediately prior to this the b.n.d.a.f.f. flip flop is reset by applying a negative-going pulse to the flip flop reset input, which causes transistor Tr_4 to conduct and Tr_5 to be cut off, so resetting the flip flop.

Acknowledgement

Photographs are reproduced by kind permission of Optimization Services Ltd., Bromley, Kent.

References

1. "Optical Character Recognition" *Data Processing*, May-June, 1967.
2. E.C.M.A. Standard for Printing Specifications for Optical Character Recognition (May 1968). European Computer Manufacturers' Association, 114 Rue du Rhône, 1204 Geneva, Switzerland.
3. "Simulation of an Alphanumeric Character Recognition System for Unsegmented Low Quality Print" by J. R. Parks, J. Rosemary Elliott and G. Cowing. I.E.E.-N.P.L. Conference on Pattern Recognition, Teddington, 1968. I.E.E. Conference Publication 42.

Conferences & Exhibitions

- LONDON**
 Apr. 11-13 Finnish Embassy
Finnish Electronics Show
 (Commercial Section, Embassy of Finland, 53/54 Haymarket, London S.W.1.)
- Apr. 17-21 The Criterion
SEMINEX — Semiconductors Exhibition and Seminar
 (E. Steadman, 17 Dunganon Dr., Thorpe Bay, Essex)
- GUILDFORD**
 Apr. 11-13 University of Surrey
Industrial Measurement and Control by Radiation Techniques
 (I.E.E., Savoy Pl., London WC2R 0BL)
- LOUGHBOROUGH**
 Apr. 11-13 University of Technology
Digital Processing of Signals in Communications
 (I.E.E.E., 8-9 Bedford Sq., London WC1B 3RG)
- NOTTINGHAM**
 Apr. 20 & 21 The University
Ion Movement in Anodic Films
 (Inst. Physics, 47 Belgrave Sq., London SW1X 8QX)
- SHEFFIELD**
 Apr. 18-20 The University
On-line Computer Control Systems
 (I.E.E., Savoy Pl., London WC2R 0BL)
- SOUTHAMPTON**
 Apr. 18 & 19 The University
Electrostatics Seminar
 (Inst. Physics, 47 Belgrave Sq., London SW1X 8QX)

- Apr. 25-28 The University
Computer Aided Design
 (I.E.E., Savoy Pl., London WC2R 0BL)
- TEDDINGTON**
 Apr. 12-14 N.P.L.
Machine Perception of Patterns and Pictures
 (Inst. Physics, 47 Belgrave Sq., London SW1X 8QX)
- YORK**
 Apr. 10-13 The University
Thin Films Interfacial and Surface Phenomena
 (Inst. Physics, 47 Belgrave Sq., London SW1X 8QX)
- OVERSEAS**
- Apr. 4-6 New York
Computer-communications Networks and Tele-traffic
 (Polytechnic Institute of Brooklyn, 333 Jay Street, Brooklyn, New York 11201)
- Apr. 6-11 Paris
Components Show
 (Société pour la Diffusion des Sciences et des Arts, 14, rue de Presles, 75 — Paris XV^e)
- Apr. 10-12 Santa Barbara
Acoustical Holography
 (I.E.E.E., 345 East 47th St., New York, N.Y. 10017)
- Apr. 10-13 Kyoto
Intermag: Magnetics Conference
 (Intermag 72 Secretariat, KDD Research & Development Lab., 1-23 Nakameguro 2-chome, Meguro-ku, Tokyo)
- Apr. 19-21 San Diego
Microelectronics: Systems and Applications
 (Dr. D. C. Kalbfell, c/o Instruments, Inc., P.O. Box 10764, San Diego, CA 92110)
- Apr. 24-26 Boston
Speech Communications and Processing
 (C. Teacher, Philco-Ford Corp. 3900 Welsh Road, Willow Grove, Penna. 19090)

Sound Pressure-level Meter

A simple battery-operated instrument using a crystal microphone cartridge to obtain flat response in the range 20Hz to 5kHz

by J. L. Linsley Hood

Many readers with an interest in the reproduction of recorded music must have attempted the construction of their own loudspeaker enclosures at some time or other. When this attempt is successful, it can be very gratifying, particularly if the enclosure design contains some elements of novelty, since the constructor can be reasonably certain that nothing quite like it exists anywhere else.

Unfortunately the matching of enclosures to the characteristics of driver units can present considerable difficulties even to the experienced. A complex design of enclosure, and the use of multiple drivers with electrical crossover networks makes the task of obtaining a clean sound even more difficult. While the ear is remarkably tolerant of non-uniformities in frequency response, provided that these are not too large in magnitude or steep in slope, the presence of unwanted large magnitude peaks in the frequency response curve is the undoubted cause of the 'booms', 'honks' and 'squawks' which can make unsuccessful systems so tiring to listen to. If these can be eliminated or lessened by the judicious use of some strategically placed damping material, or some adjustment to the dimensions of the enclosure, a great improvement can often be made to the quality of the sound.

Room acoustics play a very important part in the final performance of most loudspeaker systems, to the extent that an alteration in the position of the reproducer in relation to the walls and other large objects of furniture can sometimes alter the performance significantly.

Use of impedance measurements

If the loudspeaker system is driven from a source which has an impedance higher than that of the loudspeaker, and is fed with a variable frequency signal from an a.f. signal generator or a test record, the frequencies of the cone, enclosure and sometimes even room resonances can often be identified by noting the frequencies at which peaks occur in the a.c. voltage developed across the loudspeaker terminals.

However, from personal observations, audible peaks in the sound output do not always show up as corresponding peaks in the speaker impedance curve, and humps in the impedance curve do not always

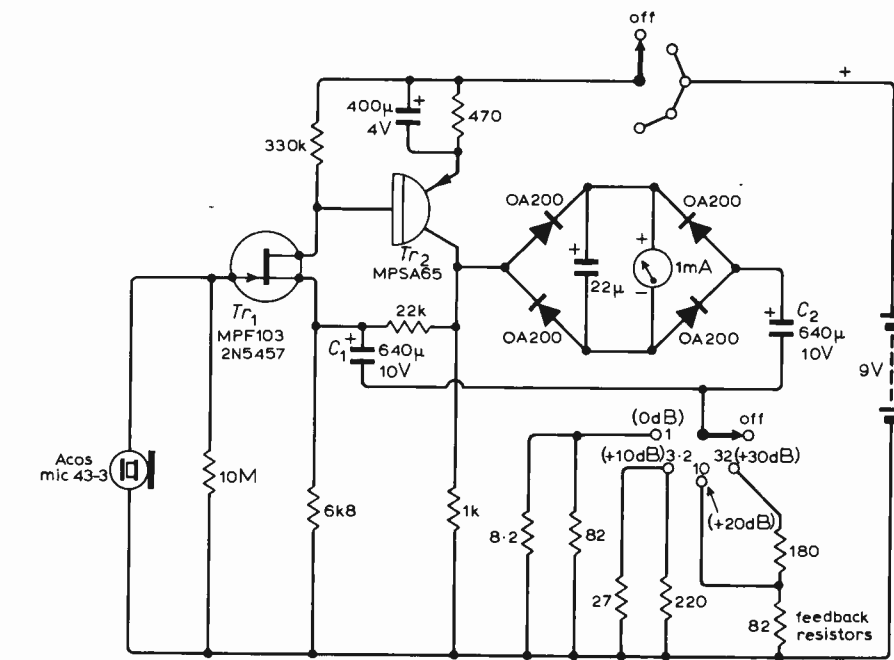


Fig. 1. Circuit of sound pressure-level meter.

result in an increase in sound output level at that frequency, when the loudspeaker is driven from an amplifier having a low output impedance.

For these reasons it is very helpful to the would-be loudspeaker constructor if he has a 'flat-response' sound measuring instrument to check the performance of his designs.

Design of sound pressure-level meter

The measurement of sound levels is a complex task even with elaborate equipment and carefully designed anechoic environments, and any simple instrument used in uncontrolled surroundings is likely

to give imprecise and possibly misleading results. (However, measurement made out of doors with the speaker supported some feet above a lawn may not be too far removed from the anechoic ideal.)

We are concerned to measure the flatness of the speaker's output when it is fed with a constant amplitude sine wave. For this test the measuring instrument should have as flat a response as possible.

Pressure sensitive crystal and ceramic piezo-electric microphone units are relatively cheap and robust, and can provide a flat frequency response coupled with an excellent low-frequency sensitivity. They have a relatively limited high-frequency performance, but a flat response over the range 15Hz-5kHz is considered adequate for sensible test purposes outside the laboratory.

The instrument's circuit is given in Fig. 1. An Acos MIC43-3 crystal microphone unit is used with an f.e.t. amplifier. In order to avoid shunting the drain load-resistor of the f.e.t. a p-n-p Darlington transistor is used as the following amplifier stage. The measuring section is a negative feedback a.c.

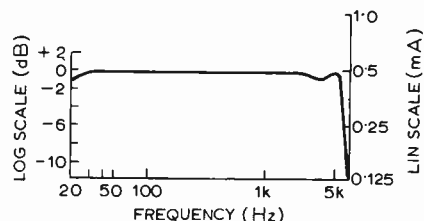


Fig. 2. Response of sound pressure-level meter using Acos MIC 43-3 crystal microphone.

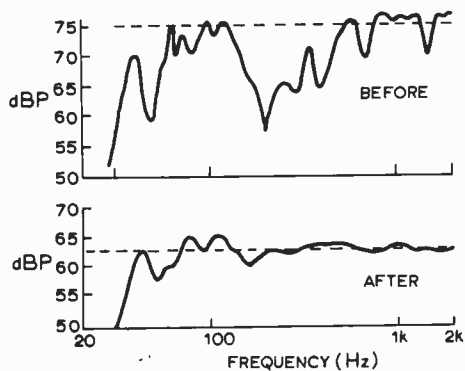


Fig. 3. Response curve, in the range 30Hz-2kHz, of experimental column loaded loudspeaker system before and after modifications.

millivoltmeter circuit. A d.c. feedback path is provided to the positive end of C_1 to ensure stability of the d.c. working point. A five position wafer switch is used to give an 'off' position and four sensitivity ranges. To minimize switch-on meter 'kicks' the least sensitive range is used as the position adjacent to the 'off' position. Sensitivities are arranged in the ratio 1:3.2:10:32, which gives a decibel scale continuity of +30, +20, +10 and 0dB.


A 1mA f.s.d. meter is used for readout and the values of the feedback resistors chosen to give full-scale deflection sensitivities of 10, 32, 100 and 320mV at the gate of the f.e.t.

The '0dB' point was chosen arbitrarily as half-scale deflection on the most sensitive range, and the scale was then marked out with the range +6dB to -20dB (5% deflection). The microphone elements will inevitably vary somewhat in sensitivity, but with two of the three different units of this type tried the half-scale deflection of the meter corresponded on average to normal conversation at about six feet distance. (The third unit was about 50% less sensitive but had a rather better h.f. response.) This sound level is probably of

the order of +55dB with reference to the normal 1kHz '0dB' level of the Fletcher Munson curve, and this gives the instrument a usable range of approximately 35-92dB in sound pressure level.

The frequency response of the instrument was determined by the use of a high-quality headphone element in close proximity to the microphone, but separated from it by a $\frac{1}{4}$ in layer of open-pore polyurethane foam to minimize air column resonances. The curve is shown in Fig. 2. This is in agreement with the response curve for the microphone capsule published by the manufacturers.

Finally, as an example of one of the uses to which such an instrument can be put, the response curve of an experimental column loaded loudspeaker enclosure, using a Wharfedale 'Golden' 10in RS/DD bass driver unit is shown in Fig. 3. The upper curve is the original performance following optimization by input impedance determinations, and the lower curve shows the response of the system after some modification to the column dimensions and the addition of suitable damping material. Although the final frequency response is still not as flat as desired in the two lower octaves, the large and unsuspected trough in the 200-400Hz region has gone, and the series of column resonance absorption slots filled in, with an audible improvement in the system performance. The penalty paid was an approximate 10dB reduction in overall sensitivity.

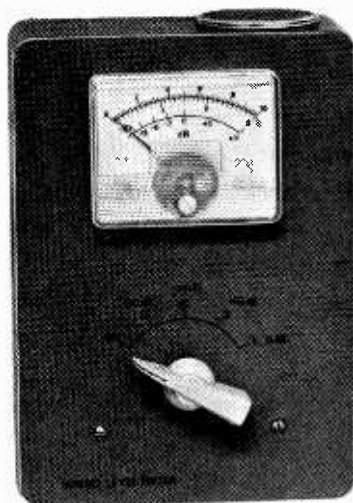

The completed sound pressure-level meter.

Announcements

The Science Research Council has awarded a grant of £59,160 for research into galactic and extra-galactic radioemissions and other problems in radio astronomy under Professor Sir Bernard Lovell at Manchester University.

Two short courses in detection, estimation, and modulation theory will be presented by Professor Harry Van Trees in Brussels, Belgium; Part I, June 26-30; Part II, July 3-7. Further details are available from Dr. Harry L. Van Trees, 27 Grove Hill Avenue, Newtonville, Mass. 02160, U.S.A.

The 1973 German International Radio and TV Exhibition will be held in Berlin from August 31st to September 9th.

Thomson-CSF Electronic Tubes Ltd, Bilton House, Uxbridge Road, London W5 2TT, has been recently formed to promote the sales of Thomson-CSF professional electronic tubes in the United Kingdom. Mr. George W. Bailey is to take charge of sales activities.

GEC-AEI Telecommunications Ltd, P.O. Box 53, Telephone Works, Coventry CV3 1HJ, have changed the name of the company to GEC Telecommunications Ltd.

Airtech Ltd, Haddenham, Bucks, have completed negotiations with Standard Telephones and Cables Ltd, to take over all activities previously carried out by the Avionics Division of S.T.C. in respect of commutated aerial direction finder equipments.

Synergistic Products Inc., Santa Ana, California, manufacturers and distributors of numerically controlled wire wrap, dual in-line package insertion and printed circuit board drilling systems have formed an associate U.K. company, **Cavitron (Europe) Ltd**, 37 Thame Road, Haddenham, Nr. Aylesbury, Bucks, to market Synergistic products in the U.K. and to provide a contract numerically-controlled wire wrapping service. It will also be responsible for the installation (including operator training), and after-sales servicing of Synergistic equipment throughout Europe.

The Industrial Electronic Division of Thorn Bendix Ltd, based at Nottingham, has been merged with Thorn Automation of Rugeley to form a single company under the name of **Thorn Automation Ltd**.

Electrocomponents Associated Ltd, have formed a new company, **Electroplan Ltd**, 13-17 Epworth Street, London E.C.2, to distribute equipment and accessories in the instrumentation, process control and allied fields.

Photo Controls Ltd, Randalls Road, Leatherhead, Surrey, have been appointed U.K. distributors for **photocell lamps** manufactured by Moririca Electronics Ltd, of Japan.

The Electronics and Instruments Division of Bell & Howell Ltd, has acquired the sole U.K. marketing rights for the **Anadex Instruments Inc.** (California) range of industrial analogue and digital measuring, indicating and controlling equipment.

Martron Associates of Marlow, Bucks, has been appointed U.K. and Eire distributor for the **Yokogawa Electric Works (Japan)** range of instruments, including chart, X-Y and photo-recorders, electrical standards, panel meters, and digital and industrial instruments.

Techmation Ltd, 58 Edgware Way, Edgware, Middx. HA8 8JP, have been appointed exclusive agents in the British Isles for the range of **lasers** made by Hughes Aircraft Company and the Santa Barbara Research Centre's range of infra-red detectors.

ITT Components Group, Electromechanical Product Division, West Road, Harlow, Essex, are now responsible for the marketing and servicing of ITT **Metrix** (France) range of instruments in Britain.

British Enkalon announce that they are to acquire Akzo's right to a 60% interest in Brand-Rex Ltd, a company formed to develop, manufacture and sell wire and cable in Western Europe.

Arrangements have been made by Perfection Parts Ltd, of 59 Union Street, London S.E.1 for the marketing of a range of modular etching equipment, which is manufactured by **Transaco** of Stockholm.

J.E. Sugden & Co. Ltd, have moved from Bradford Rd, to Carr Street, Cleckheaton, Yorkshire, BD19 5LA. Tel: Cleckheaton 2501.

Semiconductor Production Equipment Co. Ltd, (Centronic), have moved to premises at 100 High Road, Byfleet, Surrey. Tel: Byfleet 48031.

Hamlin Electronics have moved from London to 14 New Road, Southampton SO2 0AA. Tel: 0703 32832.

The London sales office of **General Instrument Microelectronics Ltd**, is now at 57/61 Mortimer St, London W1N 7TD. Tel: 01-636 2022.

Recording Level Meter and A.G.C.

by James M. Bryant

When developing a signal level meter for a tape recorder it was realized that the circuit could easily be made to function as an automatic level controller as well. Automatic level control is a valuable asset to any tape recorder particularly when recording speech under adverse conditions. When it comes to recording music, automatic level control is a disadvantage because it restricts the dynamic range available. For instance on sustained low-level signals only a small control voltage will be available and the gain of the recording system will increase. The result is that the quiet passages will be louder than they should be. On long, loud, passages the gain of the recording system will be reduced and so will the level of the recorded signal on the tape.

When used as a recording level meter the circuit monitors the audio input voltage to the tape recorder. The a.g.c. voltage is made to vary as the logarithm of the input voltage so that the linear moving-coil meter indicates in dB (VU).

A switch allows the gain controlled amplifier to be put in series with the signal source and the tape recorder, see Fig. 1. The normal recording level control on the tape recorder can now be preset, as described later, and the amplitude of signals reaching the tape recorder will be automatically controlled.

The a.g.c. generator (SL620C) and the amplifier (SL630C) are fully described in data sheets which are available from the manufacturers, Plessey Microelectronics, at Cheney Manor, Swindon, Wiltshire. The amplifier system described will respond quickly (20ms) to an input signal, it will track a rising or fading signal at up to 20dB/s, it will preserve the a.g.c. level during a break in the signal, and will suppress short noise bursts without affecting the overall a.g.c. level. If the pause or break exceeds a preset time the a.g.c. is removed and the system reverts to full gain in about 200ms.

Referring to the circuit, the output of the SL630C is fed to the SL620C which in turn applies sufficient a.g.c. to ensure that the output of the SL630C remains around 80mV r.m.s. The a.g.c. is also applied, via R_3 , to a milliammeter. The negative side of the milliammeter is connected to pin nine of the SL630C, which is a 0.8V reference point for biasing a manual gain control potentiometer. The meter resistance, R_3 , should be $0.7/I$ k Ω , where I is the meter f.s.d. current in mA. The meter

should not have an f.s.d. of more than 2mA, and if its internal resistance is an appreciable part of R_3 , then R_3 should be reduced accordingly. When there is no a.g.c. signal a small reverse current will flow in the meter, but the pointer stops will prevent it moving in response and the current will not be large enough to cause damage. A diode cannot be used to prevent this reverse current flowing as its threshold voltage would affect the meter circuit.

The gain of the tape recorder amplifier should be adjusted so that just over 100mV r.m.s. of input signal is needed to overload it. The pre-amplifier should be adjusted so that it will provide this signal level, and also ensure that the pre-amplifier will drive the 1k Ω input impedance of the unit in parallel with the input impedance of the record amplifier without loss of quality or voltage.

When 100mV r.m.s. is present at the input of the circuit the meter should be at mid-scale. This point should be calibrated 0dB; the positions with inputs of 1V (+20dB) and 10mV (-20dB) should also be marked. Intermediate points may also be calibrated if desired and the meter scale between 0dB and +20dB should be painted red to indicate that overload occurs in this region. Under normal recording conditions the pointer should never enter the red part of the scale.

When a.g.c. is being used the pointer

may be in any position but for optimum a.g.c. range (± 20 dB about nominal) the input to the circuit should be set so that with an average input signal the meter pointer is at 0dB. Input signals between 10mV and 1V r.m.s. will result in an input to the recorder of 80mV \pm 1dB.

Additional notes

Few constructional details are necessary as the circuit is very simple. The following points must, however, be considered. It is assumed in the circuit diagram that both the pre-amplifier which feeds the a.g.c. circuit and the output and the record amplifier input are at earth potential with respect to d.c. levels. If not a 5 μ F capacitor should be connected in series with R_1 , and careful attention paid to the polarity of C_9 .

The upper 3dB frequency of the SL630C is determined by C_1 according to the formula: $(1.3 \times 10^7)/C_1$ (pF).

The signal input and output of the SL630C must be kept apart to prevent h.f. instability.

To preserve l.f. stability and prevent motor-boating C_3 , C_5 and R_4 must not have their values altered by more than 30% from those given in the circuit.

The power supply should be between 6V and 9V and must have either a low source impedance at both h.f. and l.f. or be decoupled by not less than 1,000 μ F in parallel with 0.01 μ F.

Pins six and seven of the SL630C and pin seven of the SL620C are not used, since they have internal connections it is important that they be isolated and this is most easily done by cutting them off as close to the can as possible.

The duration of the pause before the amplifier reverts to full gain after cessation of signal is controlled by C_8 , the value of which, in hundreds of microfarads, should equal the required delay in seconds.

The integrated circuits may be obtained from Farnell Electronic Components Ltd, Canal Road, Leeds, LS12 2TU, or S.D.S. (Portsmouth) Ltd, Hilsa Industrial Estate, Portsmouth, PO3 5JW.

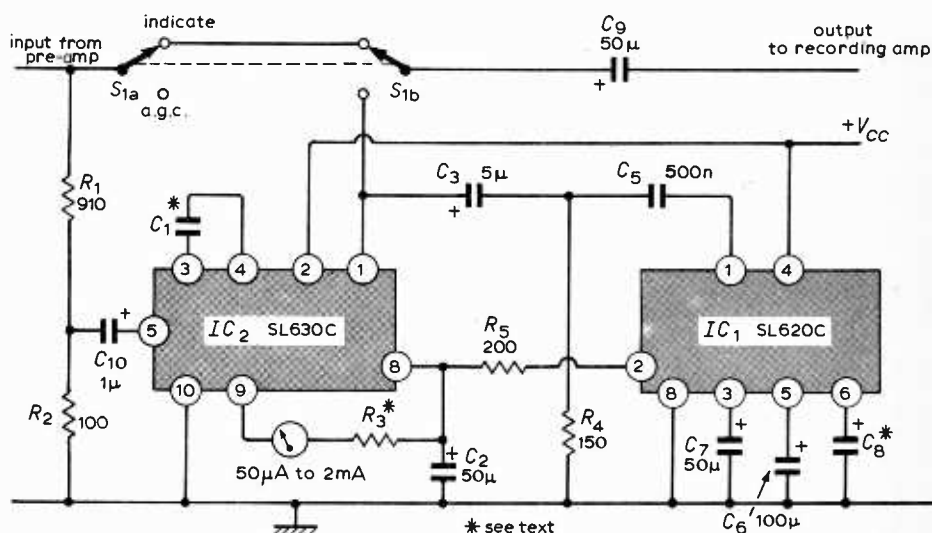


Fig. 1. An input signal of about 100mV is required to drive the circuit so a pre-amplifier would normally be required.

News of the Month

Jupiter fly-by

A spacecraft, Pioneer-F, is undertaking what is probably the most hazardous journey to be conceived by man. It will take the spacecraft close to Jupiter and then out of the solar system altogether, to carry on, as far as we know, for ever. The vehicle escaped from the influence of earth at 51,800km/s (32,000 m.p.h.) and became the fastest travelling object made by man; the orbit of the moon was passed only 11 hours after lift off. Four months after lift off the asteroid belt will be encountered and it has been calculated that the spacecraft has a good chance of getting through unscathed. So far it has been estimated that there might be 50,000 asteroids in the belt ranging from 770km (480 miles) to 1km (0.6 mile) in diameter though the danger presented by these is negligible. More hazardous is the unknown quantity of dust travelling at high velocity. It is thought that an area as large as the U.S.A., if placed in the asteroid belt, would receive impacts by eight particles with a mass of 1g or greater every second or a particle with a mass of $1\mu\text{g}$ would pass through 1m^2 every month. The largest danger is formed by particles

with a mass of between 0.1 and 0.001g of which there are an unknown number. A particle with a mass of 0.01g (which travels at 54,000km/hr (33,600 m.p.h.) can perforate a sheet of aluminium 1cm thick and could therefore seriously damage the spacecraft.

About 300 days after launch Pioneer-F will pass behind the sun and communication difficulties will be experienced due to radio noise generated by the sun.

In just under two years' time Pioneer-F will have travelled about 10^9km (620M miles) and will be in close proximity to Jupiter, the object of the mission, and the period of trajectory will pass at one Jupiter diameter, which is about 140,000km (87,000 miles), distance from Jupiter through a region of intense radiation. High-energy protons (hydrogen nuclei) and electrons in the belts could penetrate the spacecraft and destroy transistors and it is thought that the spacecraft could be crippled or data transmission could be cut off. However, one of the major objects of the mission is to assess the hazard

presented by Jupiter's radiation belts as this is a significant factor in planning future flights, not necessarily to Jupiter.

As the spacecraft is attracted by Jupiter's gravity velocity will increase to 128,000km/hr (78,000 m.p.h.) at periaapsis. During the Jupiter fly-by, if the spacecraft is still operational, an imaging photopolarimeter will alternate between taking polarization and intensity measurements, and taking pictures.

Signals from Pioneer-F during this phase will be received by N.A.S.A.'s deep space tracking network equipped with 64m (210ft) paraboloid aerials. The power of the signal received on earth from Pioneer's 8W transmitter will be about 10^{-17}W and will take 45 minutes to reach earth. This time delay means that spacecraft control signals from earth will have to be sent 45 minutes in advance as Pioneer is controlled by earthbound computers and not on-board control systems.


About 30kg (65lb) of Pioneer's total weight of 260kg (570lb) is taken up with 13 experiments which will measure various aspects of interstellar space and the nature of the Jovian atmosphere; equipment is also included to investigate the asteroid meteoroids, celestial mechanics and S-band occultation.

Pioneer-F is the first spacecraft to be powered by a nuclear (plutonium 238 dioxide) generators. The four generators provided 155W at launch reducing to 140W at Jupiter and 100W in five years time.

The aerial system on the spacecraft employs a high-gain paraboloid, a medium-gain horn and a low-gain helix. Each of the aerials is always connected to at least one of the two receivers and can be switched to either by command from earth or automatically in the event of a receiver failure. It is of interest to note that although the spacecraft's travelling-wave tube transmitters produce only 8W in the S band the 64m (210ft) ground stations can radiate up to 400MW to ensure that the command signals reach the spacecraft at sufficient strength. The huge disparity between these powers is, of course, due to the difference in efficiency between the spacecraft's and the ground station's aerials and receivers and the need to keep the power consumption on board to a minimum.

Communications to Pioneer-F will be on 2,110MHz and from the spacecraft on 2,292MHz. The telemetry system is capable of 2,048 bits per second reducing to half this at Jupiter range.

As Pioneer-F swings by Jupiter (the gravitational pull) velocity will increase to 79,200km/hr (49,320 m.p.h.) reaching the orbit of Saturn in five years' time and Uranus in eight years' time; distance from the sun will then be $2.9 \times 10^9\text{km}$ (1.8×10^9 miles). If Pioneer survives its encounter with Jupiter it will be possible to communicate with it although the transit time required for a signal will lengthen to hours and received signals will become so weak as to be unusable before the spacecraft crosses the orbit of Saturn.

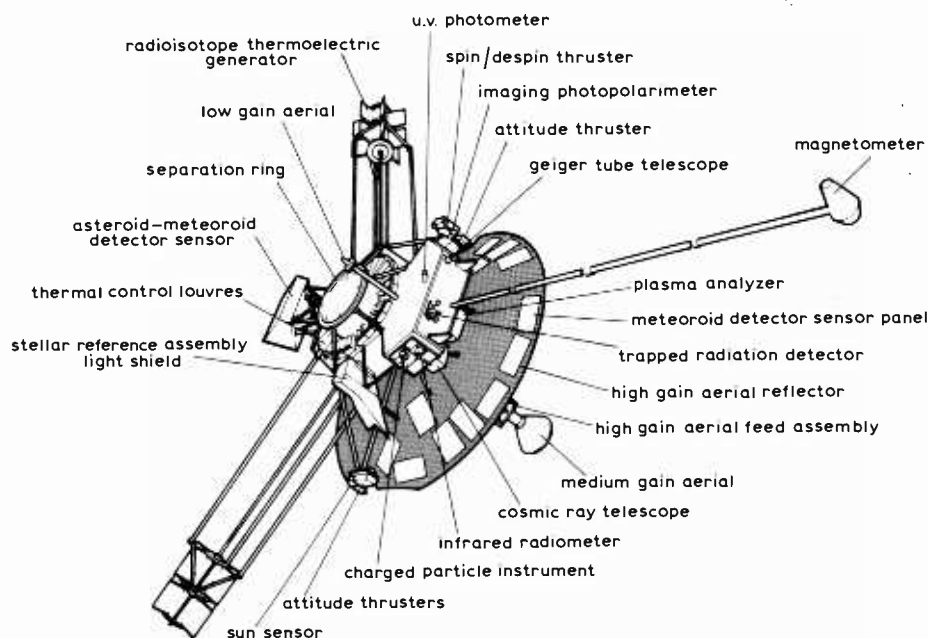

The first spacecraft to employ a nuclear power source, Pioneer-F, is now on its way to Jupiter.

After leaving interplanetary space and far out into interstellar space Pioneer-F should settle on a straight course heading away from the sun at a permanent 41,400km/hr (25,700 m.p.h.).

N.A.S.A. have allowed funds to cover the cost of the spacecraft and monitor and control functions up to three months after the Jupiter fly-by. But this period will be extended if useful information is still being received. The cost of the project is \$100M

No more British i.c.s?

The closing down of the British integrated circuit manufacturing industry, following large losses over the past three years, is now being considered, to judge from a report in the *National Electronics Review* for January-February 1972. At a meeting of the National Electronics Council, attended by John Davies, Secretary of State for Trade and Industry, it was agreed "to invite the leaders of those branches of the electronics industry concerned with the development and production of integrated circuits to set up a Working Party to consider the implications to this country of the continuance or not of an integrated circuit capability . . .". This decision followed statements that Ferranti had lost £400,000 on i.c. production in 1971 and expected to lose £300,000 in 1972, and that the General Electric Company had lost £1M over the past three years. It may be recalled that in 1970 the managing director of Mullard stated that his company was then losing £1M a year on this manufacturing activity (see leader in *W.W.*, Sept. 1970 issue). One speaker at the meeting said that the British i.c. manufacturers ought to have financial support from the Government to enable the industry to survive. If the Government holds to its avowed policy of not helping "lame dog" industries (though this policy is said by some commentators to have collapsed as a result of the Clyde shipbuilding and Rolls-Royce settlements), this support will not be forthcoming and the British i.c. manufacturers may well have to cease production.

Audio video dubbing

Sound facilities of a standard normally associated more with modern recording studios than 'on location' television work were recently used by Thames Television during the production of a series of 13 half-hour shows featuring Tony Bennett at the Talk of the Town, London. One objective was to make sound tapes suitable for issue later as stereo or mono discs.

A special sound mobile control room was used in conjunction with a new sound dubbing system 'Medway' developed at Thames to allow pictures recorded on v.t.r. machines at Teddington studios to be synchronized with sound recorded on location.

The new Thames mobile sound control room has a balancing area 17ft long with acoustic treatment and monitoring to full studio standard. Two Rupert Neve sound consoles provide 36 channels, and a new type of AKG spring-coil artificial reverberation unit provides echo on two channels.

The 'Medway' system allows separate music, effects and dialogue tracks to be recorded on the Scully eight-track machine for later dubbing, balancing and transfer to 2-inch quadruplex v.t.r. tapes. During sound dubbing use is made of a Sony helical scan v.t.r. to maintain atmosphere. The audio machine is interlocked first to the helical-scan machine and later to the quadruplex machine by means of a ten-bit binary address code. Dolby noise-reduction techniques were used during recording and balancing.

Technical controller of the series — which will be shown also in the United States — was John Tasker of Thames Television.

Improving cinema sound

The Dolby noise reduction technique is now being applied to cinema sound. The effect of applying this technique to film is to make the sound quality of optical tracks comparable to that from magnetic tracks. Although background noise in modern films may go largely unnoticed — partly because of the visual 'distraction' from the sound and partly because of tailoring the reproduced sound — it is certainly obvious when you have been made aware of it, especially when the visual content is not so engaging or during 'quiet' passages. Because of the noise inherent in the optical sound track, a rapid reduction in amplitude with increasing frequency is the norm in cinemas, severely limiting realistic sound reproduction.

The noise arises basically from the granular structure of the film and from scratches and dust on the film.

To minimize the perceptibility of this noise the 'Academy' amplitude-frequency reproduction curve, which starts to roll-off at around 3kHz and at 8kHz is 15dB down, is widely used. In practice this attenuation can be as high as 25dB at 9kHz, provided partly by the screen (speakers are invariably mounted behind it), by a filter in the amplifier and, in some cases, by the slit size in the light beam passing through the sound track. Improving sound quality therefore means decreasing the h.f. attenuation as well as adopting a noise reduction technique. So

as well as installing noise reduction 'decoders' in cinemas Rank Film Equipment — who are worldwide distributors (excluding U.S.A.) of the Dolby cinema unit — also survey and improve the cinema equipment, for example removing filters, installing additional h.f. loudspeakers where necessary, and where existing h.f. units are behind the screen bringing them to the front. This last expedient decreases attenuation by 10dB for a screen in good condition and more for treated or nicotine-stained screens. After modifications, amplitude response should extend up to around 9kHz (or at least as far as the optics allow).

The Dolby unit installed, model 364, is an A-type playback unit, specially designed for cinema use. To get best effect, the film sound track must be 'encoded' using conventional Dolby A-type units, models 360 or 361, which increase the recorded level of low-amplitude signals. Although there are no films on release at present using the technique (at least in their entirety), this need not worry the film exhibitor because the cinema unit, which does the converse of the 'encoding' unit, will reduce noise on ordinary films. This is especially useful on old films, the noise level being reduced by 6dB. (Low-level signals are attenuated together with the noise but high-level signals are unaffected.) When operating with 'encoded' film, a reduction of 10dB obtains up to 5kHz, increasing at higher frequencies to a maximum of 15dB. If desired the Academy curve can be switched in on the 364.

Rank are adopting a rental rather than a leasing basis in offering this installation service to U.K. cinemas. Charge for the 364 is £2.74 per week, with an additional rental where extra speakers are used, subject to a minimum rental period of two years.

*Academy of Motion Picture Arts and Sciences

European communications satellite contract

A six-month study contract has been awarded to the Star consortium for a 'configuration definition study' concerned with telephone traffic between European countries and the transmission of television between members of the European Broadcasting Union via the proposed European communications satellite. The British Aircraft Corporation is the prime contractor and Lockheed Missiles and Space Company (California) are consultants to Star for the contract. The contract follows an earlier feasibility study. The Star consortium consists of: B.A.C. (U.K.), Contraves (Switzerland), Dornier (W. Germany), Ericsson (Sweden), CGE Fiat (Italy), Fokker (Netherlands), Montedel (Italy), Sener (Spain) and Thomson CSF (France).

At the same time the Cosmos space

consortium will be carrying out a 'configuration definition study' for the satellite. It is expected that the satellite will weigh about 400kg and will be capable of handling two colour television channels and several thousand telephone conversations. Marconi Space and Defence Systems are the prime contractors.

The Cosmos consortium consists of: GEC-Marconi (U.K.), Etudes Techniques et Constructions Aérospatiales (Belgium), Société Nationale Industrielle Aérospatiale and Société Anonyme de Télécommunications (France), Messerschmitt-Bölkow-Blohm and Siemens (W. Germany) and Selenia (Italy).

Mullard awards to schools

Fourteen pupils from five schools, four of them in the Southampton area, received cash awards on behalf of their schools from Mullard Ltd at a ceremony held at the company's semiconductor plant at Southampton. The awards were made under the auspices of the Southern Science and Technology Forum by Dr Max Smollett, chief development engineer at Mullard Southampton, and were for the planning and content of technical or scientific projects which will be undertaken by the pupils concerned.

The idea of setting up Science and Technology Forums in various areas of the country originally came from Prince Philip in his capacity as chairman of the Schools Science and Technology Committee. The aim of the forums is to help teachers interest their pupils in the application of pure scientific knowledge to technology. The Mullard Awards were for those projects with an electrical or electronic basis.

Details of the first three of the ten awards are as follows: £20 for a logic display board and visual computer. Andrew Hicks (17) and Christopher Mullen (17) Barton Peverill School, Southampton; £20 for 'Poole Grammar School Computer'. Robert Cheatham (16) and Martin Hoyle (17) Poole Grammar School; and £10 for a wind gauge without moving parts. Peter Knight (18) Richard Taunton College, Southampton.

Those pips

Some readers may have been puzzled by the recent change in the six-pip signal transmitted by the B.B.C. which has remained unchanged since it was first broadcast on February 25th 1924. The signal now consists of five short pips (100ms) followed by a longer pip (500ms). The start of the last pip marks the

beginning of an hour to plus or minus 20ms and the whole sequence is controlled by one of the atomic clocks at the Royal Greenwich Observatory.

The change was made on January 1st when Greenwich mean time was brought in step with atomic time. G.M.T. is based on the earth's rotation which is not constant, while atomic time does not vary. It will be necessary to occasionally alter G.M.T. by a positive or a negative leap second to bring it in line with atomic time. For convenience the Greenwich Observatory has decided to insert leap seconds on the last second of the last day in a month (preferably December or June).

In the case of a positive leap second 23h 59m and 60s will be followed one second later by 0h 0m and 0s. When a negative leap second is necessary 23h 59m 58s will be followed one second later by 0h 0m 0s.

Semiconductor plant expands

In phase two of a development programme a further 90,000 sq.ft. has been added to Mullard's power and microwave semiconductor plant at Bramhall Moor Lane near Stockport. The total area now available to Mullard at Stockport plant is 160,000 sq.ft. and as a result a factory a mile away is to be closed. Mullard do not intend to take on more staff in the area at the moment. Of the 700 staff (40% women) more than 20% are qualified to H.N.C. or degree standard.

Time-in-sync clock

The research institute of AEG-Telefunken has developed a clock (called the Telechron) that would seem to render obsolete all present clocks intended for domestic or even professional purposes. It is relatively inexpensive, it is portable, it can have the accuracy of an atomic clock and if switched off for a period and then switched on again will indicate the correct time within two seconds without resetting.

The clock relies on the fact that full information about every second, minute and hour can be transmitted in only 30Hz of bandwidth by existing television and radio transmitters in pulse coded form. No additional filters are needed at either the transmission or the receiving end. A clock would consist of a simple receiver, a shift register, a storage register, a digital display and some logic.

In the case of TV transmitters the time information would be inserted at the end of a frame.

Communication '72

Communication '72, the conference and exhibition to be held in Brighton from the 13th to the 15th June, is to be opened by Earl Mountbatten. The conference, which covers military and civil radio communications (point-to-point, mobile and data) and associated test equipment has been jointly organized by *Electronics Weekly* and *Wireless World*. The conference programme and application forms for tickets for the exhibition (free) and the conference (£25) will be available from the exhibition organizers E. T. V. Cybernetics Ltd., 21 Victoria Road, Surbiton, Surrey, in April.

Seminex

A series of seminars and an exhibition devoted entirely to semiconductors is to be held in London at the Criterion (Piccadilly Circus) between the 17th and 21st of April.

The exhibition will be a simple affair, each company being restricted to a maximum of 30ft of table space on which to display their wares; there will be no large stands.

The seminars have been divided into sessions by subject as follows: 17th a.m. linear i.c.s, p.m. hybrids; 18th m.o.s. all day; 19th memories all day; 20th a.m. digital i.c.s, p.m. opto-electronics; 21st discrete semiconductors. Tickets for the seminars cost £5/day and are available from E. Steadman, Seminex Booking Office, 17 Dungannon Drive, Thorpe Bay, Essex. (Tickets for the exhibition alone cost 40p.)

Companies taking part include: Emihus, Fairchild, Ferranti, General Electric, General Instrument, Intersil, ITT, Lucas, Microwave Associates, Microsystems International, Mullard, Plessey, RCA, Signetics, Texas Instruments, Toshiba, Welwyn Electric, and Westinghouse.

Intercon '72

Nineteen U.K. electronics companies have registered for the I.E.E.E. '72 Intercon Exhibition and Conference to be held at the New York Coliseum from March 20th to 23rd. This will be the fifth year in succession that the Electronic Engineering Association, in co-operation with the Department of Trade and Industry, have organized a U.K. representation at the exhibition. U.K. companies taking part are: Avdel Marketing, Auto Precision, Birch Stolec, Bryans Southern Instruments, Cossor, Dek Printing Machines, Electrolube, EMI, Ferranti, FieldTech, Gordos, Jermyn, London Electrical Manufacturing, Marconi, Plessey, Vickers, Wayne Kerr and SDC Electronics.

How to Simplify Logic Circuits

Introducing the decision-accounts table

by N. Darwood*

The theory of logical circuits is sometimes called switching logic. This is because the function of a combination of switches, such as is shown in Fig. 1(a), is easily described. Whether the components of which it is finally built are NAND, AND or OR gates or switches, the description of a logical circuit is the same. To explain: two switches in series make an AND gate, Fig. 2(a); two switches in parallel make an OR gate, Fig. 2(b). A switch which is short-circuit when 'on' and open-circuit when 'off' makes a logical inverter, Fig. 2(c).

Although the individual switches of a circuit may switch at electronic speeds, the function, i.e. the logic of the circuit, is described as though it is static and such that there is continuity across the circuit; the circuit is then said to be 'on'. For

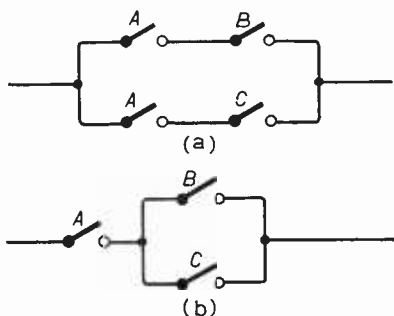


Fig. 1. All the possible switch states in these two (equivalent) combinations are shown in the truth table (first two tables in the text).

example, the logic of Fig. 1(a) is: either (A and B) or (A and C) which is written in shorthand as $AB + AC$. An instance of the usefulness of switching theory is to factorize $AB + AC$ into $A(B + C)$, which is simpler to construct—Fig. 1(b).

In the paper and pencil analysis of a logic circuit, it is sometimes useful to consider all the possible combinations of states of the switches. In the circuit of Fig. 1(b) there are three switches, A, B and C. All the possible states are shown below. Also shown is the condition of the circuit in Figs 1(a) and (b).

A	B	C	$AB + AC$
off	off	off	off
on	off	off	off
off	on	off	off
on	on	off	on
off	off	on	off
on	off	on	on
off	on	on	off
on	on	on	on

Rather than having to write many 'on's and 'off's, it is usual¹ to use 1 for 'on' and 0 for 'off'. Whence the above table becomes

Truth table for circuits of Fig. 1

State	A	B	C	$AB + AC$
0	0	0	0	0
1	1	0	0	0
2	0	1	0	0
3	1	1	0	1
4	0	0	1	0
5	1	0	1	1
6	0	1	1	0
7	1	1	1	1

From the above table we can describe the logic of Fig. 1 as being on when the switches are in state 3 (i.e. 110 in binary form where the least significant bit is on the left), state 5 or state 7. This is the truth-table. One way of designing a logic circuit is to write out the truth-table which shows all the possible states of the switches, then to enter the required 'on' or 'off' circuit condition. Suppose a table as shown below is required.

Truth table 2

State	A	B	C	
0	0	0	0	0
1	1	0	0	1
2	0	1	0	1
3	1	1	0	0
4	0	0	1	1
5	1	0	1	1
6	0	1	1	1
7	1	1	1	0

The first step would be to derive a logical expression by extracting the states of the switches A, B and C that will produce an 'on' condition. From the table the circuit-on conditions are

states: 1 or 2 or 4 or 5 or 6

logical expression: $ABC + \bar{A}BC + \bar{A}BC + ABC + \bar{A}BC$

Armed with this expression we can draw the logic diagram. There are five terms in the expression, hence five AND gates which feed into a five input OR gate are needed. The logic diagram is shown in Fig. 3. The logic diagram may now be converted into some other type of logic using, say, NAND

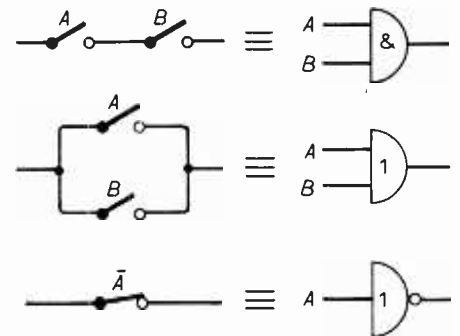


Fig. 2. In writing the logic diagram equivalent of switch diagrams, the notation shown is used.

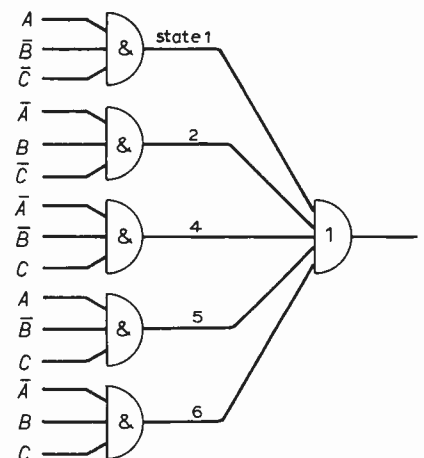


Fig. 3. To draw a logic circuit, the 'on' condition is normally written from the desired truth table. Truth table 2 gives an expression with five 'on' terms, realised by the logic gates shown.

gates. The conversion technique is a separate branch of logic circuit theory.

Returning to the logic diagram of Fig. 3, the circuit uses six logical elements. Using the truth-table or the rules of Boolean algebra (for example $AB + AC = A(B + C)$; $A + \bar{A} = 1$, $A + A = A$) the full expression can be simplified, for example, to $A\bar{B} + \bar{A}C + \bar{A}BC + \bar{B}C$. The logic diagram of this expression, logically equivalent to Fig. 3, is shown in Fig. 4. Thus we can have two different, but logically equivalent, expressions one of which is simpler to construct than the other.

The question can be asked—are there other different ways a logical circuit can be built? Many methods exist for finding if a

*Decca Navigator Co. Ltd.

simpler logical expression is possible, e.g. the Harvard method²; but they require a knowledge and a skill of Boolean algebra which usually only professional logic designers, or logicians, attain through constant practice.

Decision-accounts table

However, a new approach to the problem is being made, whereby not only are simpler expressions derived but also all the other equivalent expressions can be listed. This gives a complete analysis of the circuit. A table lists all the states to which a particular logic term, such as $\bar{A}C$, applies—in this instance states 4 and 6. (See logic tables opposite for three factors.) The table does not contain the states to which expressions apply, found by looking up the states for each term. To illustrate: the expression derived for Fig. 4 is

$$A\bar{B} + \bar{A}C + \bar{A}BC + \bar{B}C$$

Enter the tables at the section for three factors A, B and C, with each term, and extract the corresponding state, thus

- $A\bar{B} = 1,5$
- $\bar{A}C = 4,6$
- $\bar{A}BC = 2$
- $\bar{B}C = 4,5$

Therefore the expression, when implemented in hardware, will be on for states 1, 2, 4, 5 or 6, see Fig. 3.

Having found the states that apply to the circuit, to find logically equivalent expressions reverse the procedure by entering the tables with the states 1, 2, 4, 5 and 6, and extract all the terms that apply, as shown below.

Decision-accounts table 1

State no.						term found
1	2	4	5	6		
✓			✓			$\bar{A}B$
	✓			✓		$\bar{A}B$
		✓	✓			$\bar{B}C$
		✓		✓		$\bar{A}C$

Now as long as we take a combination of these terms that account for all the required states, then that combination will suffice. For example, the three terms $\bar{A}B$, $\bar{A}B$ and $\bar{B}C$ suffice. The circuit, Fig. 5, uses less hardware than Fig. 4.

The above table is called a decision-

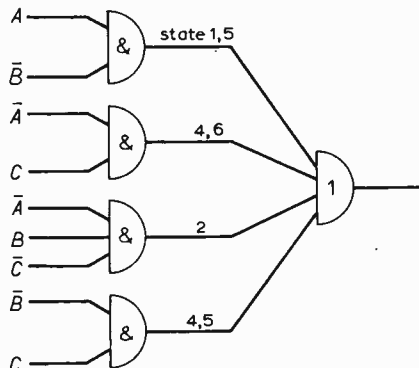


Fig. 4. The logic circuit of Fig. 3 could be simplified by using the rules of Boolean algebra on the logic expression of truth table 2, resulting in five instead of six gates.

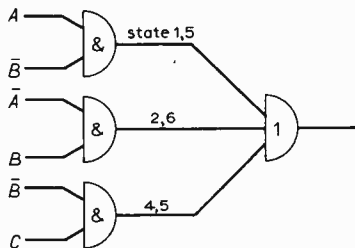


Fig. 5. To find other equivalent expressions or logic circuits of Fig. 3, a 'decision-accounts' table is compiled using logic tables which show all the terms that account for the required states. This allows the simpler circuit shown to be drawn.

accounts-table. In conjunction with the logic table, they form a Boolean expression simplification method³. The tables are easily derived⁴. This same decision procedure is useful also to programmers and systems analysts who have to formulate and programme complex logical decisions.

By extending the method we look for other expressions, perhaps simpler or perhaps just as simple but different, that will produce the same output for the same combinations of switch states. Because this is a new procedure it may be a little difficult to grasp. One logical law need be used to perform the manipulation. The law is $X + XY = X$, which allows us to eliminate a term if it is ORed with a factor of itself. The logic diagram of this law is shown in Fig. 6, in terms of switches and gates. If, for clarity, we label the rows of the decision-accounts table P, Q, R and S, then a more complex instance of the absorption law, as it is called, could be

$$PQS + PQ = PQ$$

Having drawn up the accounts table, we can now calculate the different ways of constructing the logic of Fig. 3. (The example is purposely obvious to show the reasoning). The accounts table, re-labelled, is

Row	State				
	1	2	4	5	6
P	✓			✓	
Q		✓			✓
R			✓	✓	
S			✓		✓

The first column is accounted for by row P, the second by Q, the third by R or S (= R + S) and the fourth by P + R and the fifth by Q + S.

Also we have to account for the first column and the second and the third, and so on. Hence an expression for this particular decision-accounts table could be

$$P \cdot Q \cdot (R + S)(P + R)(Q + S)$$

which can be expanded to $(PQR + PQS)(PQ + PS + RQ + RS) = PQR + PQRS + PQR + PQRS + PQS + PQS + PQRS + PQRS = PQR + PQS$ (by application of the absorption law, $X + XY = X$). The final expression $PQR + PQS$ shows that either rows P, Q and R or rows P, Q and S may be used to construct the initial logic expression.

Because $P = A\bar{B}$, $Q = \bar{A}B$ and $R = \bar{B}C$, then one expression that could be used is

$$A\bar{B} + \bar{A}B + \bar{B}C$$

or, alternatively, because $S = \bar{A}C$, the following expression could be used

$$A\bar{B} + \bar{A}B + \bar{A}C$$

That the alternatives are equivalent to the original may be proved by the truth table,

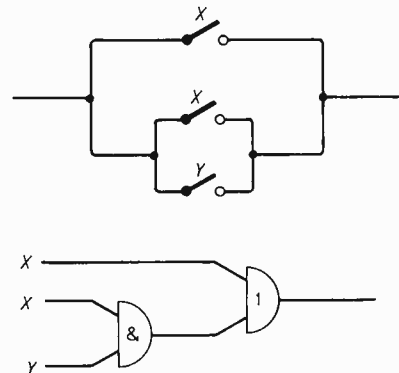


Fig. 6. In extending the decision-accounts technique the basic Boolean absorptive law $X + XY = X$ is used, which allows elimination of a term which is ORed with a factor of itself.

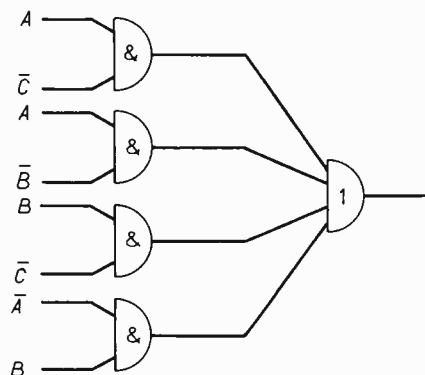


Fig. 7. In finding equivalent expressions for this circuit, the decision-accounts table 2 shows it can be achieved in either of two ways with one gate less.

or by showing via the logic tables that the three expressions produce the same states, which is the same thing.

Further example

Suppose the example is the circuit shown in Fig. 7; the Boolean expression is derived from the circuit as

$$A\bar{C} + \bar{A}B + \bar{B}C + \bar{A}B$$

Enter the logic tables at the section for three factors A, B and C to extract the states to which each term applies

- $A\bar{C} = 1,3$
- $\bar{A}B = 1,5$
- $\bar{B}C = 2,3$
- $\bar{A}B = 2,6$

Therefore the expression is ON for states 1, 2, 3, 5 or 6. Next draw up an accounts table. To ease the working the rows are labelled P, Q, R and S.

Logic tables

two factors	
0 = $\bar{A}\bar{B}$	0, 1 = \bar{B}
1 = $A\bar{B}$	0, 2 = \bar{A}
2 = $\bar{A}B$	1, 3 = A
3 = AB	2, 3 = B
three factors	
0, 1 = $\bar{B}\bar{C}$	2, 6 = $\bar{A}\bar{B}$
0, 2 = $\bar{A}\bar{C}$	3, 7 = AB
0, 4 = $\bar{A}\bar{B}$	4, 5 = $\bar{B}\bar{C}$
1, 3 = AC	4, 6 = $\bar{A}\bar{C}$
1, 5 = AB	5, 7 = AC
2, 3 = $\bar{B}\bar{C}$	6, 7 = BC
0 = $\bar{A}\bar{B}\bar{C}$	0, 1, 2, 3 = \bar{C}
1 = ABC	0, 1, 4, 5 = \bar{B}
2 = $\bar{A}\bar{B}\bar{C}$	0, 2, 4, 6 = \bar{A}
3 = ABC	1, 3, 5, 7 = A
4 = $\bar{A}\bar{B}\bar{C}$	2, 3, 6, 7 = B
5 = $\bar{A}\bar{B}\bar{C}$	4, 5, 6, 7 = C
6 = $\bar{A}\bar{B}\bar{C}$	
7 = ABC	

Decision-accounts table 2

Row	State					Term
	1	2	3	5	6	
P		✓		✓		AC
Q	✓				✓	AB
R		✓	✓			BC
S			✓		✓	AB

The accounts table expression is

$$(P+Q)(R+S)(P+R)QS$$

$$= (R+S)QS(P+QR)$$

$$= QS(P+QR) = QSP+QRS$$

The final expressions show we can construct the circuit by either rows Q, R or S, i.e.

$$A\bar{B} + B\bar{C} + \bar{A}B$$

or, alternatively, from rows Q, S and P, i.e.

$$A\bar{B} + A\bar{C} + \bar{A}B$$

On looking back at the accounts table, it is intuitive that to account for each column ('on' state of the switches) at least once, then rows Q and S are essential (called prime-implicants in the literature). Rows Q and S account for states (columns) 1, 5, 2 and 6, leaving state 3 outstanding. With the prime implicants we may choose either row P or row R. Hence Q & S & (P or S) is the choice of decisions.

Readers may like to simplify and/or find alternative expressions for the following

$$AB + \bar{A}\bar{C} + BC$$

$$A\bar{B} + B\bar{C} + \bar{B}\bar{C} + \bar{A}B$$

$$A + \bar{B}\bar{C} + \bar{A}B$$

$$\bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + ABC$$

References

- Boole, G. *Mathematical Analysis of Logic* (1847). Blackwell, 1965.
- Bowran, A. P., *Boolean Algebra*, Macmillan 1965.
- Hohn, F. E. *Applied Boolean Algebra*, Macmillan, 1966.
- Darwood, N., *Representation of Logic Tables*, *Electronic Engineering*, Jan. 1971.
- Darwood, N., *Simplification of Decision Tables*, *Computer Weekly*, 29 July 1971.

Letters to the Editor


The Editor does not necessarily endorse opinions expressed by his correspondents

Universal meter amplifier

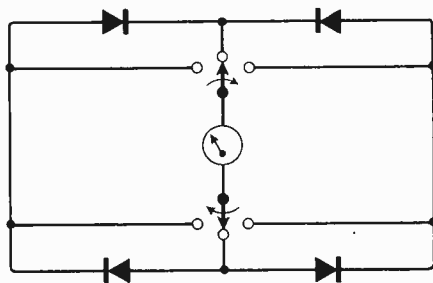A. J. Ewins's universal meter amplifier (February page 61) seems to be one of the more attractive of such designs. However, there are one or two points which worry me.

I am puzzled by his use of a half-rectifier/half-resistor bridge, instead of a full rectifier bridge, for the meter movement circuit. He has certainly reduced to a half the pedestal voltage to be overcome in the diodes, but to achieve this he has reduced the effective sensitivity of the movement to nearly a third. Thus, to achieve the same degree of accuracy at the lower end of the scale the open loop gain has to be half as much again as with a full bridge. This amounts to almost 5dB. (And to clinch the argument, suitable diodes, when bought in quantity, are much cheaper than resistors!)

It is true that his development of this part of the circuit in Fig. 4 (i.e. the insertion of 1kΩ between the two diodes) gains him more with a hybrid bridge than it would with a full bridge, but with the values given he is in fact only just regaining that 5dB anyway!



The full bridge circuit has other useful advantages. One of the weaknesses of the overall design is that the circuit cannot isolate a.c. from d.c. (a feature which is occasionally of great value). A two-pole three-way, switch inserted as shown at the centre of a full rectifier bridge circuit overcomes this difficulty together with that of polarity indication. Its positions represent d.c.+, a.c., d.c.-, and the need for a further diode, normally short-circuited, is obviated. The same switch assembly can cope with the switching for d.c. isolation shown in the

author's Fig. 5. The net result is very much more versatile for very little extra.

A further thought occurs to me. Surely what Mr Ewins is doing is simply to design, around a basic i.c., a high quality op-amp. Is it not possible that a standard package i.c. op-amp, with a couple of source followers tacked on the front, would do the job as well at considerable saving of money, space, and circuitry? If one were prepared to accept a minimum viable reading of 50mV at 100kHz (and 5mV at 10kHz) a simple 741 could be used as the centre of the circuits of Figs 4 and 6. Other i.c.s might, however, be more satisfactory.

Giles Hibbert,
Oxford.

The author replies:

I am glad of the opportunity Mr Hibbert's letter gives me to comment on one or two further points of possible interest in connection with my universal meter amplifier design.

First, let me explain my thinking behind the use of the half-diode/half-resistor bridge. The amplifier was specifically designed around the Avo Model 9 meter movement which needs a 10kΩ shunt in order to achieve the required damping and sensitivity of 50μA. Tapping the 10kΩ resistor at the centre only reduces the current sensitivity of the meter by half to 100μA. Admittedly, in terms of the meter's basic sensitivity of 37.5μA, the sensitivity of the circuit is decreased by a factor of 100/37.5, i.e. 2.67, and if any other meter movement were used the circuit arrangement would not be as attractive. However, there is another point worth considering. Mr Hibbert says that by decreasing the sensitivity of the meter circuit the open loop gain of the amplifier has to be half as much again to achieve the same degree of accuracy at the lower end of the scale. In this he is not altogether correct since in this case it is *voltage* gain that is important and not current gain. By replacing two diodes with two resistors I have admittedly reduced the current sensitivity of the meter circuit, but I have effectively increased the voltage sensitivity, which is more important. (I am aware that the basic meter movement shunted by the 10kΩ resistor, tapped in the centre, has a decreased voltage sensitivity of 37.5 μA

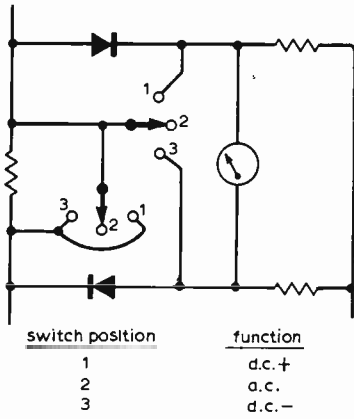


Fig. 1.

× 8333 ohms, which is approximately equal to 312mV, as opposed to its basic voltage sensitivity of 125mV. However, the removal of a diode and its associated, approximate, 600mV drop has the greater effect.) I am able further to effectively increase the voltage sensitivity of the circuit by forward biasing the two diodes in the circuit. It would not be possible to forward bias all four diodes in a full-bridge rectifier.

Mr Hibbert's suggestion for making the circuit give indications of d.c. -, a.c. and d.c. + is a good one. The use of the half-diode/half-resistor bridge does not preclude this possibility, see Fig. 1.

Mr Hibbert is quite correct in his assumption that the circuit is basically a high-quality operational amplifier, but the substitution of a standard package i.c. op-amp is not so straightforward. Apart from the fact that at the time of designing the circuit I had not had occasion to use a standard op-amp there is the point that they are awkward to balance for open- and short-circuit conditions, which is the requirement of the circuit of Fig. 3 of my article. A further, most important, point is that their output impedances are normally low and it is a requirement of both my final circuits that, for good linearity, the output impedances should be as high as possible before the application of negative feedback. However, since designing my original circuits I have given some thought to the possible use of standard op-amps.

Provided source-followers are used in front of the op-amp, giving high input impedances and eliminating the zero balancing problem, the appended circuits of Figs. 2 to 4 can be used for increasing the output impedance of the standard op-amp.

The circuit of Fig. 4 is the simplest because the TAA861 op-amp requires an external load resistor and it is a simple matter to make this a constant-current source. All three output stages will considerably increase the open loop voltage gain of the final circuits and it should be possible to increase the basic sensitivity of the amplifiers as Mr Hibbert suggests. I have recently constructed a millivoltmeter of 50mV sensitivity using the high output impedance circuit of Fig. 2 and a 709 op-amp. With a 1mA meter and a full-diode bridge the frequency response was from d.c. to 20kHz and the linearity excellent. Zero drift was no problem at all.

A. J. Ewens

Imported equipment

Recent years have witnessed a large influx of foreign electronic equipment into this country especially in the audio field. While most of this equipment functions well most of the time, occasionally one comes across rather woebegone individuals who, in good faith, have purchased imported equipment which has, through no fault of their own, deteriorated and in many cases ceased to function.

Out of sympathy and understanding one offers to help find the cause of the trouble in the malfunctioning equipment, or to suggest that a recommended electronic repair firm would surely put the item back into good working order. This latter idea is usually greeted with varying degrees of derision, several attempts having been made in this direction. One learns that the estimates have been prohibitive to the extent that it would be cheaper to buy another unit or that the firm contacted have no knowledge of the brand concerned and hence will not undertake the repairs needed.

One returns to the former offer of help,

and is immediately confronted with a piece of equipment which certainly has an accompanying basic circuit diagram, but strangely no testing information or data. Closer examination reveals individual component brand names which are not unknown but on the other hand not easily obtained even via foreign component distributors.

What is one to do then? The first task is to discover working tolerances, especially with regard to the transistors used. Many foreign transistor manufacturers have agencies from where it might be reasonably expected to acquire information. One writes or telephones and discovers that only the types of transistor (which are limited) used in their own equipment are obtainable and information about even those types is far from complete. No, the types that one mentioned are not marketed in this country and no information is available other than from the parent company. How long must one wait before an answer of some description is received? Perhaps three months one is told. Net result, return to square one.

Substitution manuals are consulted next and the characteristics of the proposed substitution component carefully studied. All may be well but there is always the underlying feeling that this procedure is quite unsatisfactory.

Finally, through the good offices of the embassy or trade delegation one obtains the address of the company which manufactures the equipment. A letter is posted indicating what information is required and also mentioning that reasonable cost incurred by the company for a reply will be borne. One waits, and waits. A fortnight, a month goes by, two months, three months and yet four months and still no reply!

Is it that the exporters have so many very closely guarded secrets or that the foreign exporters could not care less about their equipment once it has left their shores?

S. Braidford,
Wotton-under-Edge,
Gloucester.

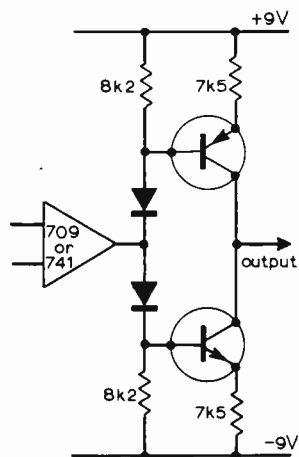


Fig. 2

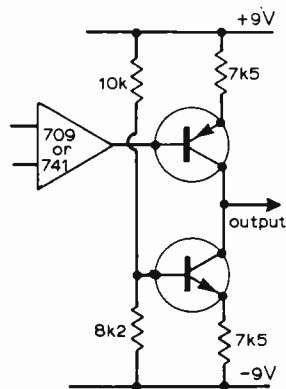


Fig. 3

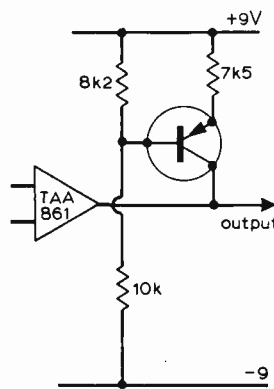


Fig. 4

Figs. 2-4 are possible high-impedance output stages using a standard op-amp at the front

TV standards abroad

I would like to bring to the notice of your English readers who are contemplating emigrating to New Zealand the matter of television receivers. I have had quite a number of sets brought to me for conversion to N.Z. standards which have been sold, as suitable for our conditions, by English firms. Unfortunately this is often not easy or cheap and the owner generally has a set which is as dear as one on the market here and no spares available.

So for the information of your readers I'd like to pass on the details of our standards. We use 625 lines but only on v.h.f. Channel 1 (44 to 51 MHz), Channel 2 (54 to 61 MHz) and Channel 3 (61 to 68 MHz). Channels 4 to 9 are between 174 and 216 MHz so that a BBC2 u.h.f.

set is useless here. There are some European models which are usable and need minor adjustments to the three lower channels (for Channels 2, 3 and 4 European) but in our Channels 4 to 9 the channel switch only has to be set to the next highest channel to get satisfactory reception, e.g. EU7 is NZ6. Our sound i.f. is 5.5 MHz.

I am surprised that so little is known of the New Zealand situation in the U.K. and I have as mentioned come across people who have been told because the set operates on 625 lines in the U.K. it will work on 625 lines in N.Z. A similar situation would prevail for anyone going to Australia as they have the 625-line and 5.5 MHz system but have 13 channels some of these being in the v.h.f. f.m. band. Many of their channels are close to the N.Z. ones and sometimes cause interference even over 1200 miles. I have a very well known English TV in my 'junk box' which was bought in London for £50 and the only thing 625 on it is the label on the systems change knob. The 625 adaptor was not even in the receiver! Unfortunately when this was pointed out to the firm they just said they didn't accept responsibility as the 'salesman had left'!!
B. E. Graham Goodger,
Lower Hutt,
New Zealand.

Automatic telephone exchange

In the February issue I read with great interest the article on the design of a 'Miniature automatic telephone exchange' by G. F. Goddard, and was most impressed with its simplicity.

However, as all relays in use are P.O. type 3000, with open springsets, I would suggest that the method of switching on the mains power unit is changed as the existing arrangement is potentially dangerous.

Across the springsets of relays RLA and RLB both 245 V a.c. and 50V d.c. are to be found. In addition to the life of these contacts, RLA/1 and RLB/1 (live side 245V) being reduced unless heavy-duty

material is used, there is a very real danger of intending constructors receiving a nasty shock at mains voltage when working on the exchange, or alternatively shorting the 245V a.c. with the 50V d.c., due to the close proximity of this type of springset.

Although my suggested circuit modification requires the use of two additional relays (MSA and MSB) I feel the additional cost is more than offset by the improved safety factor as it is possible to mount these relays remote from the telephone switching relays. The type of relays used could be either heavy duty octal types, or mercury wetted contact relays, both having protective covers over their contacts, and a coil resistance of 3.3kΩ or more.

Also, the circuit diagram in Fig. 3 shows contact RLJ/3 as a normally open type. This would have to be normally closed otherwise on lifting the handset of any of the telephones, unselector U1 would continually drive as the coil of relay RLC has no path to -50V to operate on finding the calling extension.

N. Monk,
Kettering,
Northants.

Incremental computer

The object of designing a hybrid computer is to improve the methods of processing information.

Accurate processing presupposes accurate input data — may we therefore point out that the development for which a grant has been given by S.R.C., to which you refer on p.112 of the March issue, is being carried out jointly by the University of Surrey (not Sussex as you stated) and Cranfield Institute of Technology.

W. F. Lovering & R. E. H. Bywater,
University of Surrey,
Guildford.

Stereo decoder

Readers who have built the phase locked stereo decoder (Sept. 1970) may have noticed the decoder will 'blink' while the

receiver is being tuned. This is annoying when making fine tuning adjustments: e.g. during mono reception the decoding process is allowed with deterioration in s/n ratio; and during stereo reception, if tuned, the decoder momentarily resorts to mono operation.

The fault is caused by large d.c. changes (generated at the f.m. detector during tuning) being differentiated by C₅ and thus 'fooling' the in-phase lock detector IC₃.

Fortunately the cure is simple: a 47,000pF capacitor should be added in series with R₃₅.


P. Lacey,
Crediton,
Devon.

Books Received

Radio Data Reference Book (3rd edition) by G. R. Jessop contains data presented in the form of graphs, tables and charts with only sufficient text to permit its effective use. The aim is to provide as wide a range of material as possible, which if sought by the normal means would involve a lengthy search through many volumes. It has been assumed that the reader will have sufficient fundamental knowledge for the direct application of data and where theoretical information on any subject is required the reader is referred to the appropriate reference books. A section contains a comprehensive list of frequencies allocated to radio and TV broadcasting stations in the United Kingdom, channel information on world television systems and amateur frequency allocations in the U.K. Pp.150. Price £1. Radio Society of Great Britain, 35 Doughty Street, London WC1N 2AE.

Radio, Television and Audio Test Instruments (2nd edition) by Gordon J. King is essentially a practical guide and is written with the emphasis on application and testing methods. In some cases it has also been necessary to consider various design and circuit features, so that the reader may fully appreciate the scope and diversity of application of the instrument. Chapter subjects include d.c., a.c. and electronic meters, signal generators, oscilloscopes, and component testing. There is also a comprehensive section on instruments for colour television and audio measurements (new to this edition). Most chapters have been modified from the first edition and some have been rewritten. Pp.199. Price £3.80. The Butterworth Group, 88 Kingsway, London WC2B 6AB.

The Arlington Dictionary of Electronics takes a middle line between oversimplified definitions and definitions which, while complete are highly technical. The terms included cover a wide range of electronic systems and networks (active and passive networks, control and telemetry systems, analogue and digital computers and communication systems) and also touch on applications in fields such as data processing, acoustics and medicine. Mathematical descriptions are provided where helpful and there are numerous pictorial representations and circuit diagrams. Pp. 171. Price £3. Arlington Books (Publishers) Ltd., 38 Bury Street, St. James's, London, S.W.1.

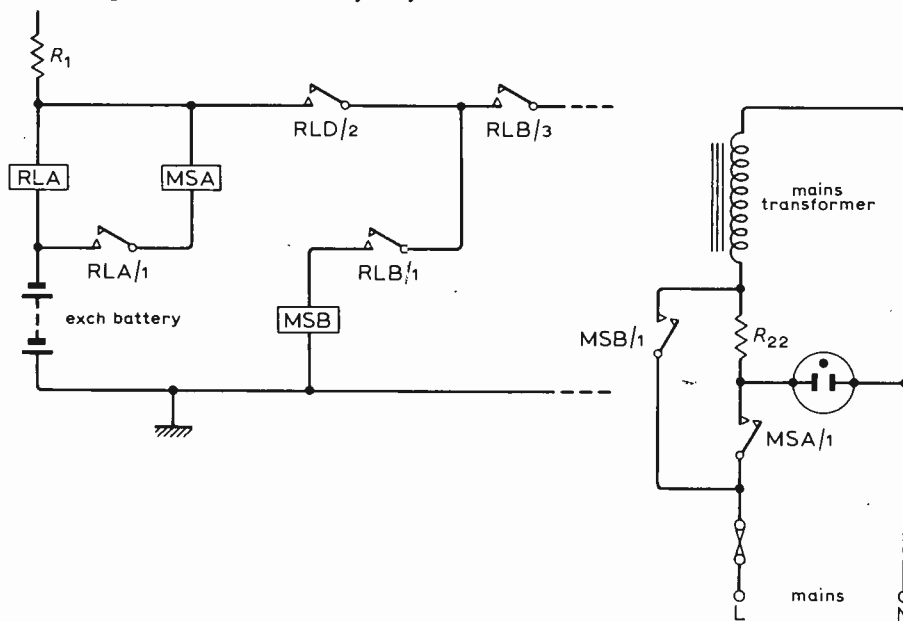

Electronic Building Bricks

21. The closed-loop follower

by James Franklin

In industrial and domestic equipment we sometimes wish to make an output variable automatically 'follow' an input variable — to go through the same pattern of change with time in strict proportionality (i.e. with a constant ratio of output value to input value). To illustrate the idea some examples of followers* are shown in Fig. 1. In a servomechanism (a), the output variable could be mechanical displacement providing high power (e.g. moving a large load), which is following an input displacement of low power, such as a manually-operated lever. At (b) is an

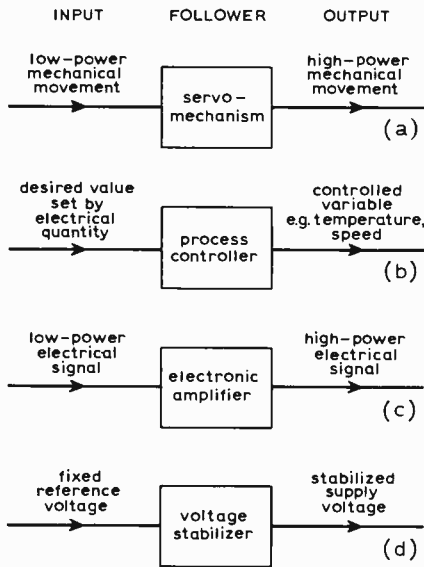


Fig. 1. Examples of followers.

electronic controller as used in industrial process control. Here the output variable 'follows' the input variable in that it stays fixed in a constant ratio to the adjustable electrical input value. If the input variable is re-set, usually by hand, to some new desired value the output variable changes correspondingly and remains constant at the new value. At (c) is an electronic amplifier as used in radio and television: the high power output signal must accurately follow the low power input signal, otherwise distortion of the signal waveshape will occur. Finally at (d) is a

*Not to be confused with certain electronic circuits with this name, e.g. emitter follower, cathode follower, source follower.

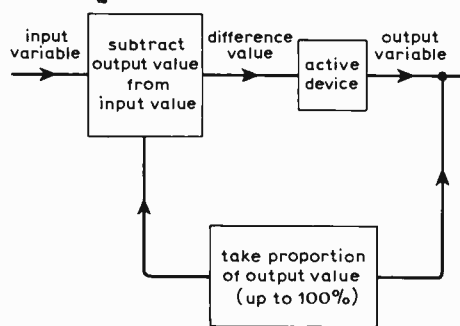


Fig. 2. Basic principle of the closed-loop follower.

voltage stabilizer for the power supply of electronic equipment. This is similar to (b) in that its output variable 'follows' the input variable, a fixed reference voltage, by staying constant at a voltage proportional to that reference voltage.

How can the engineer be certain that the output variable is indeed accurately following the input variable? For example, in an electronic amplifier, as described in Part 9, if there is a non-linear relationship between the power changes in the high-power circuit and the power changes in the low-power circuit the output variable will certainly not follow the input variable — the amplifier will introduce distortion. A basic method adopted to ensure accurate following is shown in Fig. 2. This is to compare continuously the output variable, or a proportion of it, with the input variable, subtract the output value from the input value (see Part 14) and use the difference value as the input to the active device. (By active device we mean a motor, linear actuator, flow valve, electronic amplifier etc. according to the nature of the

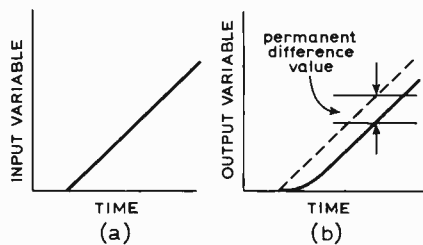


Fig. 3. The permanent difference value required in a closed-loop follower: (a) the input variable and (b) the output variable.

follower.) Consider now what happens if the output variable does not follow the input variable. If for a given increase of the input variable, the output variable increases disproportionately, the magnitude of the fraction sent back to the subtractor is also increased and so the difference value is reduced in magnitude. Since the active device is controlled by the difference value, the magnitude of the output variable is reduced. Thus an automatic correction has taken place. Conversely if the output variable decreases disproportionately for a given input variable decrease, the fraction sent back to the subtractor will also be decreased, the difference value will be increased and the magnitude of the output variable will be increased — again an automatic correction.

It might be thought that the system should operate to make the difference value become zero, since this would show that the output was exactly the same as the input. In fact this cannot be, first because permanent zero input to the active device would mean permanent zero output, which would be useless. Hence a small difference value must always be maintained, and this is illustrated in Fig. 3. The smaller the difference value the more accurate the follower, so to permit an extremely small difference with the required output value the active device must be designed to magnify its input as much as possible. Another reason for the presence of a difference value is that in a practical system, such as an electro-mechanical positioner, information takes

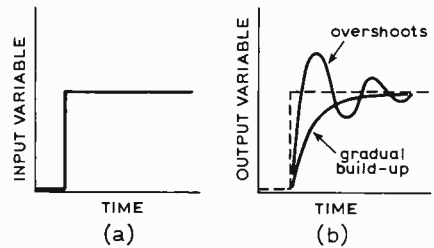


Fig. 4. Two possible transient errors (b) when a closed-loop follower responds to a sudden change in the input variable (a).

time to travel through the active device and back to the subtracting device. Some of this delay could be caused by components which have electrical or mechanical reactance (see Part 7) and this causes a transient error when the follower is responding to a sudden change in the input variable. Two possible examples of this are shown in Fig. 4 (b), one being a gradual build-up of the output variable and the other a series of overshoots.

Because in Fig. 2 information flows from the output back to the input a loop is formed, and the method is known as closed-loop control. It goes under various names in particular apparatus (sometimes depending on what the input and output variables are), such as error-correcting, null-seeking, self-balancing, servomechanism, automatic regulator, phase-locked loop, automatic gain control, automatic frequency control, and negative feedback (the word 'negative' being derived from the subtraction process mentioned above).

F.M. Tuner Design -- 12 Months Later

by L. Nelson-Jones, F.I.E.R.E.

The author of the articles on the stereo f.m. tuner design (April, May 1971) looks back on the 12 months since the design was published and gives some hints on getting the best from the design. Cures are listed for the small number of troubles – out of nearly 2,000 tuners for which parts have been sold – experienced by readers. Test voltages are also given as well as dial mechanism and stereo decoder mounting details. A solid-state tuning indicator is described separately on pages 182 and 183.

This tuner has been made by many of the readers of *Wireless World* and, inevitably, a few of these tuners have given trouble. Most of these troubles have been traced to component faults, or errors in construction, but two faults in particular have recurred in a number of cases. One of these is concerned with oscillator tracking, and the other an instability, apparently in the r.f. section, but which is very difficult to track down.

Oscillator tracking

In many cases it has not been possible to get the oscillator to quite reach 108-MHz

coverage while at the same time covering down to 87.5MHz, because the oscillator coil could not be closed up enough without shorting. The first attempt to increase the inductance of the oscillator coil was to reverse the direction of winding thus giving about an extra half turn. This proved to be too big an increase resulting in the coil not being able to be reduced in inductance sufficiently even with the turns highly extended. The next move was to increase the diameter of the coil some 15%, but this too proved non-effective due to the close proximity of the tuning capacitor body, and in

fact an appreciable drop in inductance was noted. Finally it was found that the very small increase in inductance needed could easily be obtained by standing the coil further away from the printed circuit board. Instead of mounting the coil so that the turns are 2.5mm clear of the board, as described in the original article, it should be mounted with 5 to 6-mm clearance. The coil should now track easily with the turns spaced from one another by about half a wire diameter. The r.f. coils both track normally with the turns spaced by approximately one wire diameter. In each case this is about the 'natural' length of the coils.

In existing tuners it will be necessary to remove the oscillator coil and fit a new one to effect this cure as it is unlikely that the existing coil will have sufficient surplus lead length. Take great care when removing the leads from the board. The simplest way in my experience is to cut the coil off leaving a reasonable lead length, and then to remove each lead separately, being very careful to pull the lead through the board from the component side (never from the copper circuit side). This minimizes the risk of 'pad lifting'. The holes are then cleared of solder, being careful not to increase the hole diameters, and a new coil fitted in the normal manner but with the increased clearance. Fig. 1 shows the amended mounting details for the coil.

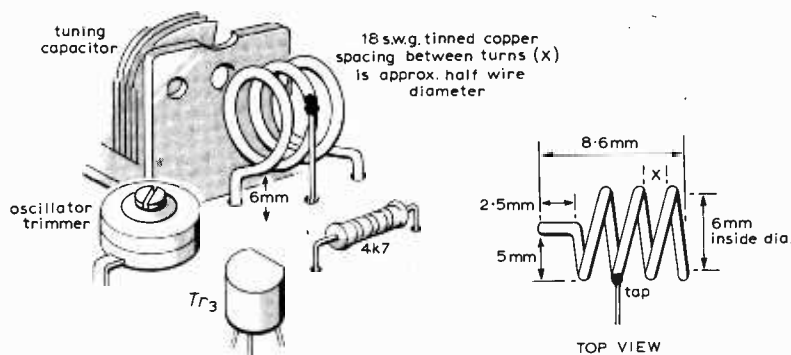


Fig. 1. For those who cannot tune to 108MHz, inductance of oscillator coil can be increased by moving it further away from the printed board.

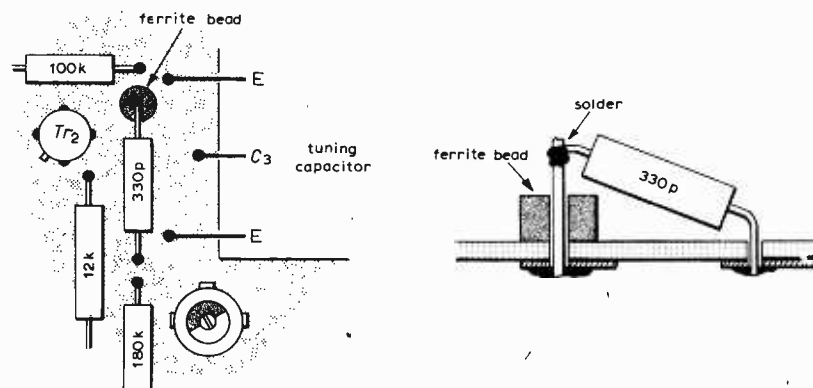


Fig. 2. In some cases unwanted oscillation at around 500MHz has caused odd effects, and has been cured by adding a ferrite bead as shown (see also photograph).

Instability

This fault has proved a very elusive one which nearly always shows up only at the upper end of the frequency coverage. It can also show up as an excessive noise level, with more than a reasonable number of spurious responses, but with the tuner working quite normally on strong signals. Most readers deduced that the mixer was unstable, others that it was the r.f. stage, and some that the oscillator was squegging, which can give a similar effect. In fact it seems likely that all three stages are involved, as the oscillation is almost certainly not at the normal carrier frequencies for which the receiver was designed but around 500MHz.

It is extremely hard to track down the exact mechanism, but it appears that it is usually associated with f.e.t.s having higher than average gain in this u.h.f. region. An f.e.t. differs from a bipolar device in that the drop off in gain with frequency is much

more sudden. A device such as those used in the tuner r.f. and mixer stages can have barely reduced gain up to say 450MHz, above which the gain rapidly reduces so that little gain exists at say 600MHz. For this reason I believe that only a few tuners have this trouble, and this is confirmed by the fact that of those with the trouble that I have examined, all had f.e.t.s in the r.f. stage with higher than usual I_{dss} currents, and with these devices one would usually expect a higher gain at u.h.f.

The path for the feedback appears to be via the g_2-g_1 capacitance of the mixer, via the oscillator layout to the r.f. stage input, through this stage back to g_1 of the mixer and thus full circle. This view of the mode of oscillation is backed by a number of facts, such as the fact that the oscillation frequency is unaffected by the receiver tuning, but is affected by the voltage applied to the 'varicap' diode, and that a ferrite bead in series with the oscillator feed to g_2 of the mixer effectively suppresses the oscillation. I suspect that the inductor forming the u.h.f. resonant circuit is formed by the earth plane of the printed board.

The cure for this problem is thus a very simple one and the location of the ferrite bead is shown in Fig. 2. It is mounted on the lead of the 330-pF oscillator feed capacitor. It may be mounted on either end of the capacitor, but is more easily mounted on the end shown. To mount the ferrite bead (Mullard FX1115 or Radiospares anti-parasitic beads) on a tuner already constructed, the end of the capacitor is unsoldered from the board, a tinned copper wire is soldered in place of the capacitor lead in the board, and the ferrite bead placed on this lead. The capacitor is then soldered to the wire above the bead (Fig. 2).

Oscillator temperature coefficient

A small number of readers have complained of excessive drift of the tuner, even with the a.f.c. switched on. It is suspected that the oscillator may have had a faulty component in these cases, but a tuner subjected to a

Unwanted oscillation at u.h.f. may be cured with a ferrite bead over the lead of the oscillator output capacitor.

large change in temperature on warming-up (for instance a tuner in use in the same cabinet as a valve amplifier) may give rise to some problems. The main component causing the drift is the oscillator trimmer capacitor which has a temperature coefficient of up to -1000 p.p.m./deg C. Most of the oscillator components have measurable temperature coefficients, but the trimmer is much the highest.

It must not be forgotten that the tuner must be operated from a stable supply as the tuner has quite a high voltage-versus-frequency coefficient— 330 kHz/V without a.f.c., and 60 kHz/V with.

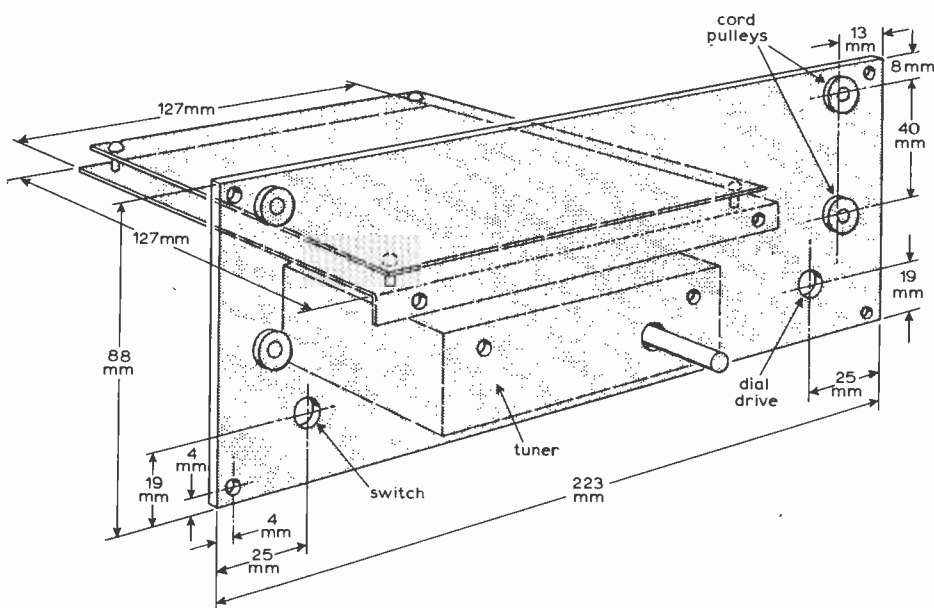
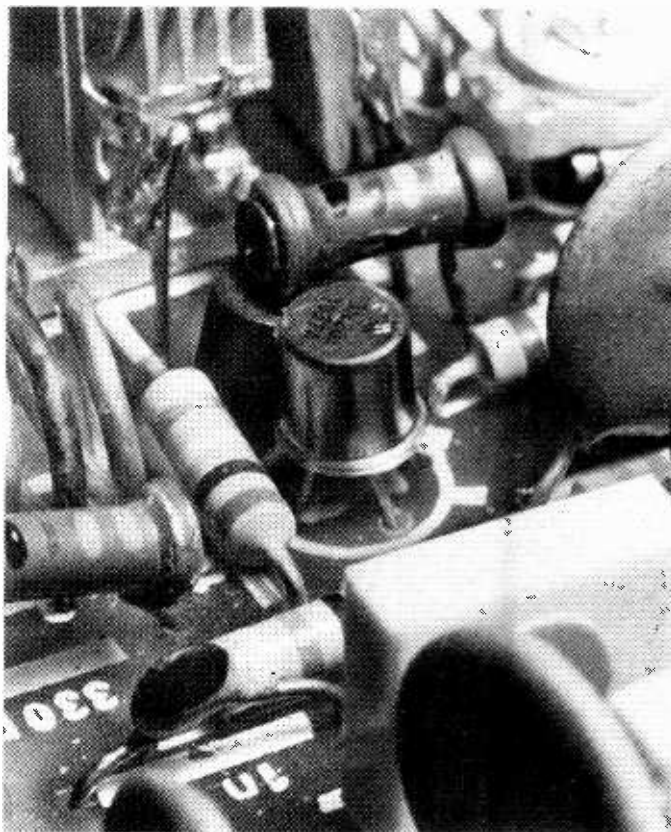


Fig. 3. New dial mounting system applicable when using stereo decoder (a) and front panel cut-outs for tuning meters (b).

Measurements have been made on a tuner fitted with a trimmer having a lower temperature coefficient of N470 (i.e. -470 p.p.m./deg C). This trimmer gives rather better drift figures: -6 kHz/deg C with a.f.c. and -16 kHz/deg C without a.f.c. These figures are quite acceptable in normal circumstances.

Thus for readers having trouble with drift the change to the N470 device, which is of the same type as that used at present but of 3.5 to 13pF range, will make a considerable improvement.

For those requiring a still greater freedom from drift the use of an air dielectric or p.t.f.e. trimmer will give an improvement. Jackson type 5440/PC/PT/14.0 should be adaptable to the task although its pins will need spreading slightly, and the stator and rotor connections will be reversed so that on tuning with a screwdriver the placing of the screwdriver in the slot will pull the oscillator off tune and the screwdriver must be removed before re-checking the alignment.

My advice is therefore to leave well alone unless drift is a problem, in which case an investigation should be made to ascertain the component responsible in case there is a faulty item. Should the trimmer be the cause as indicated then a change to a type having a better temperature coefficient may be the cure. The most useful tool to ascertain approximately the relative temperature coefficients of the various components is a miniature soldering iron, which may be held close to components to heat them up, in conjunction with a tuning meter of approximately 2–0–2V f.s.d. The drift of the tuner is easily seen on such a meter which has a deflection constant of approximately 100kHz/V. A 'freezer' aerosol is not

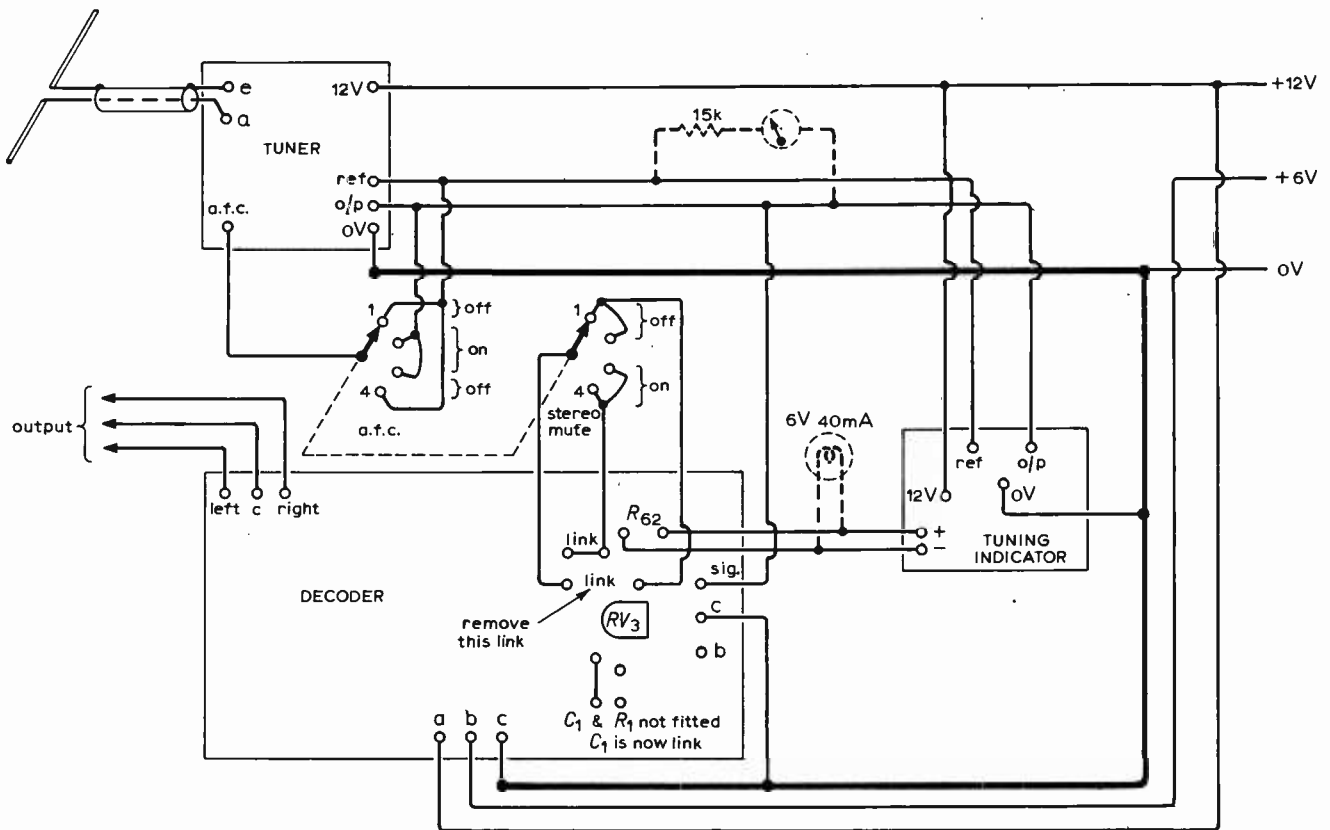


Fig. 4. Wiring diagram for connecting decoder and tuning indicators.

satisfactory as the large amount of condensation produced causes erroneous results due to the effect of the moisture on the stray capacitances.

Mounting the tuner and decoder

In the original article I suggested a method of mounting the tuner which is quite satisfactory. However, many readers will want to take advantage of the increasing amount of stereo broadcasting now available, and to receive these transmissions a decoder is needed. The design by Portus and Haywood (September 1970 issue) works well with the tuner, and I have therefore designed a new dial mounting system for use with this decoder and either a moving-coil meter or solid-state tuning meter. This chassis system is shown in Fig. 3.

The interconnection of the tuner and decoder is a simple matter provided the decoder has been assembled for single polarity supplies. Using supplies of +6V and -6V would mean having three separate supplies for tuner and decoder together. The connections are shown in Fig. 4. This also shows the connections needed to mute the decoder in the event of excessive noise on stereo transmissions, thus gaining the 20dB or so extra signal-to-noise ratio of a mono signal. There are two possibilities for muting the decoder, (a) the decoded outputs may be shorted together or (b) the decoder may be disabled by reconnecting the junction of R_{46} and R_{48} of the Portus and Haywood decoder to 0V (connection C) instead of to the collector of Tr_{13} . This point of the circuit is easily accessible and the resistor junction is disconnected from Tr_{13} by removing a link on the board adjacent to RV_3 , replacing it with two leads

to each end of the previous link. A third lead is connected to the short link adjacent to the positive end of D_4 , and next to the link removed. These connections are shown in Fig. 4.

Either a three- or four-way switch may be used for a.f.c. and decoder muting, depending whether muting is required with or

Test voltages for f.m. tuner

test point	voltage relative to 0-V line (V)	comments
Tr_1 gate 1	0	
gate 2	4	
source	1	approx. 0.7 to 1.5V spread
drain	11.5	
Tr_2 gate 1	0	
gate 2	1.7	approx. 1.0 to 2.0V spread
source	1	approx. 0.7 to 1.5V spread
drain	11.7	
Tr_3 emitter	5.4	
base	6	
collector	12	
Tr_4 emitter	6.6	
base	6	
collector	0.75	
IC_1 pin 1	no connection	
2	3.6	
3	0	
4	2.9	
5	7	
6	9.7	
7	11.5	
8	no connection	
IC_2 pin 1	5.8	depends on tuning (4 to 7.5V)
(nominal)		
2	3.5	
3 & 4	0	
5, 6 & 7	1.35	
8	0.13	
9, 10 & 11	0	
12	3.5	
13	11.5	
14	5.2	depends on tuning (3 to 7.5V)
(nominal)		
a.f.c. reference	5.2	

Measurements assume a meter of 20k Ω /V and a +12-V supply.

without a.f.c. This is the last position of the four-way switch, and is not strictly necessary. However, for completeness the four-way switch is shown.

All parts for this dial system and the stereo decoder mounting are available from Integrex Ltd, P.O. Box 45, Derby, TE1 1TW, including a set of printed scales. The ferrite bead is also available.

Finally, a list of alterations and corrections to the original article, some of which have already been published.

- A capacitance of 15pF is now recommended for the oscillator base capacitor, not 47pF.
- Decoupling of r.f. stage is 1nF, not 47nF (top of L_2).
- Fig. 2 caption last line should, of course, read '4.7nF at pin 1 of IC_2 ', not pin 2.
- In Fig. 2, the 2.2k Ω resistor at pin 5 of IC_1 should go directly to the +12V supply, and not via the 100- Ω resistor.
- In Fig. 6(c) the coil (L_5) should have 10 turns.
- The components list should have listed 1nF, nine off, and 47nF, nine off, disc ceramic capacitors.
- Type 3N201 m.o.s.f.e.t. can be used in place of the 40673.
- Texas types TI409 or TIS64 can be used in place of the 40244 transistor, now obsolete.
- Ferranti transistor type ZTX500 can be used in place of BC213L.
- ITT diode type BA110 can be used in place of TIV307.

Turn over for notes on tuning indicators.

Fitting a moving-coil or solid-state tuning indicator

Fitting a tuning indicator to the f.m. tuner is a simple matter using a centre-zero meter of 100-0-100µA sensitivity (Fig. 1). With a correctly-aligned tuner the d.c. output level and a.f.c. reference voltages are equal when the tuner is on tune, and differ when it is off tune. Thus as a station is tuned in the meter first deflects to one side as the station is reached, then deflects back through zero as the station's frequency is passed, finally falling back close to zero when well off tune again. If a.f.c. is switched on the above effect is modified. On tuning towards a station the meter suddenly snaps to a reading as the a.f.c. captures the carrier. This reading may be either side of zero depending on how fast one tunes to the station. It is then only necessary to set the meter to zero for correct tuning, as the tuning cannot remain on any section of the S-shaped demodulator characteristic except the correct central portion, due to a.f.c. action. On tuning off the station with a.f.c. connected, the meter will deflect to a maximum in the appropriate direction and then snap near to zero as the a.f.c. 'loses' the station.

In designing the tuner I deliberately did not use a very strong a.f.c. control loop so that tuning could be done with or without a.f.c. In normal use it is often easiest to leave the a.f.c. permanently on, as tuning with moderate a.f.c. is so simple, especially for the less-skilled members of the family.

The cut-out for the dial panel is shown in Fig. 2.

Solid-state indicator

The recent improvement in the availability of light-emitting diodes at acceptable prices makes their use for indicators in electronic equipment very attractive. Fig. 3 shows a simple circuit using these diodes. Correct tuning (i.e. equality of output and a.f.c. reference voltages), is indicated by equality of the light output from the diodes D_1 and D_2 . The diode D_3 and its associated resistors are for use as a stereo indicator lamp. The values chosen produce the approximate equivalent of a 6-V 40-mA lamp, and were chosen to match the requirements of the stereo decoder by Portus and Haywood (September 1970 issue).

The action of the circuit of Fig. 3 needs little explanation. It is a long-tailed pair which with equal voltages at the two bases will pass equal currents through the two diodes. When the base voltages differ the current through the long-tail resistor divides unequally between the two transistors, so that when the input to Tr_1 is approximately 1V below the input to Tr_2 then most of the current flows through Tr_2 and D_2 . When the input to Tr_1 is approximately 1V above the input to Tr_2 then most of the current flows through Tr_1 and D_1 .

Fig. 4 shows the relationship between the potential difference of the bases of Tr_1 and Tr_2 and the current through the two diodes as measured in the circuit of Fig. 3. The difference in peak currents off tune is of no practical importance as the visual difference

is not great, and in any case there is no basis for comparison as either one light is on, or the other. In use the correct tuning point is easily found. Because the input impedance loads the output of the tuner, it is important to ensure that the input impedance of this tuning indicator is sufficiently high and linear, over a range of

approximately $\pm 1V$ about the centre. Full $\pm 75\text{-kHz}$ deviation is equivalent at the tuner output to $\pm 0.7V$. This requirement for reasonable input impedance linearity has been achieved in this circuit by degeneration in the emitters of Tr_1 and Tr_2 , the resistor values being chosen to obtain the correct sensitivity.

The input resistance of the circuit is

$$\beta_1 \left[r_{e1} + R_2 + \frac{(R_4 + r_{e2} + R_5/\beta_2)R_3}{R_4 + r_{e2} + R_5/\beta_2 + R_3} \right] + R_1$$

Assuming minimum current gain for the

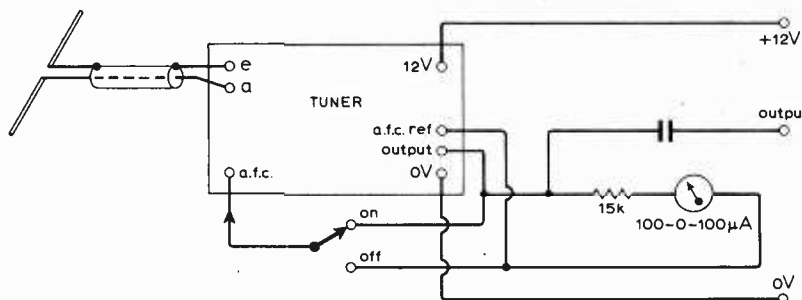


Fig. 1. Adding a moving-coil indicator is simple. With a.f.c. on and with a station tuned in, one merely sets the meter for zero indication.

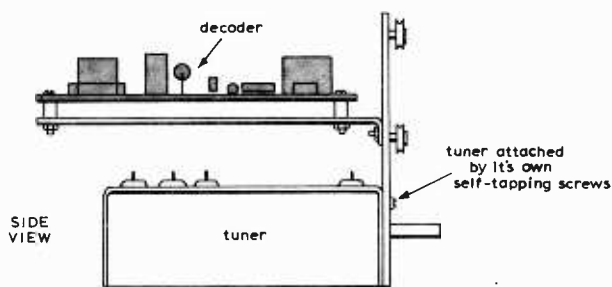
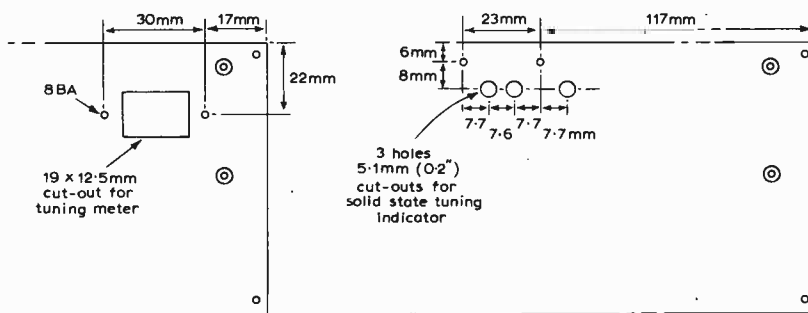


Fig. 2. Cut-outs for the two alternative tuning indicators.


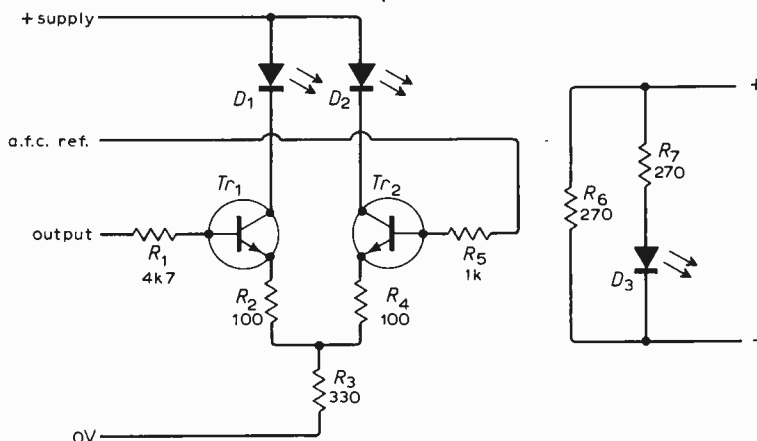
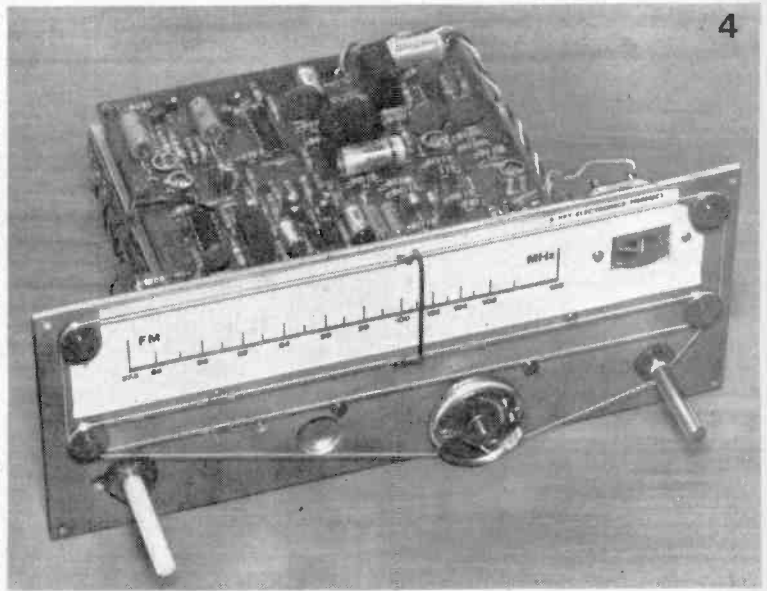
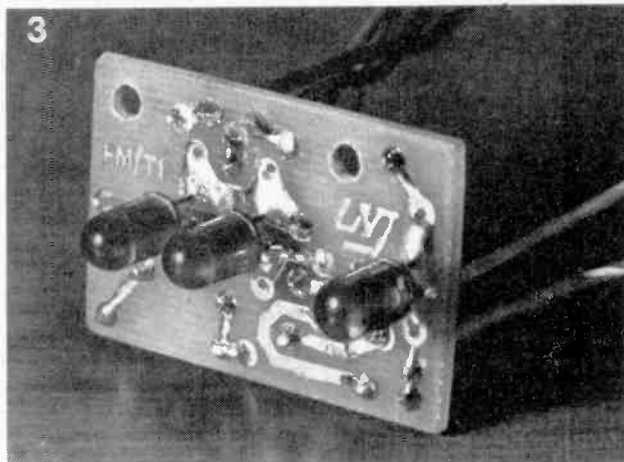
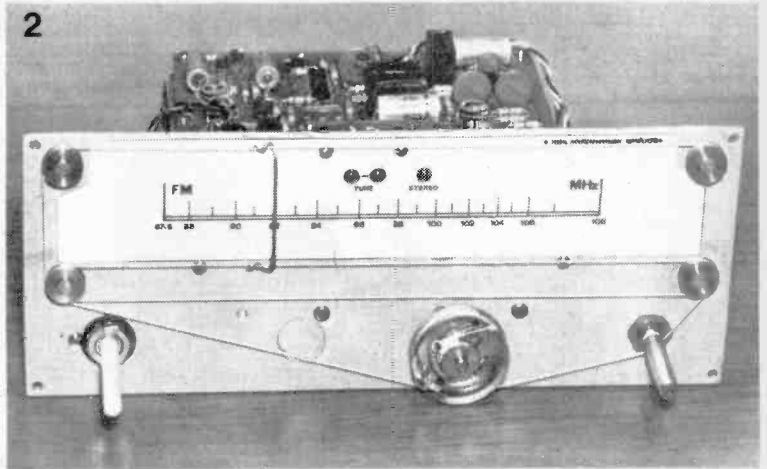


Fig. 3. Author's suggested circuit for solid-state indicator gives both tuning and stereo indication. Diode cathode is identified by the short lead and orange spot.

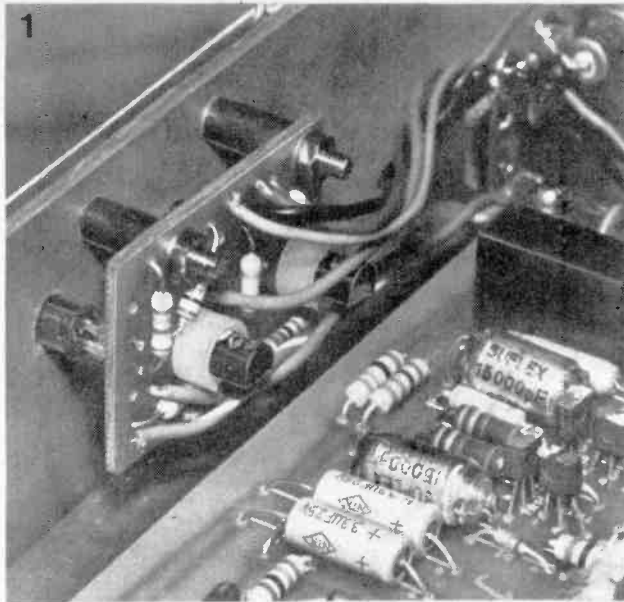

1 and 2: Mounting of solid-state indicator p.c. board. 3: Diodes mounted on p.c. board. 4: Front panel with moving-coil indicator.

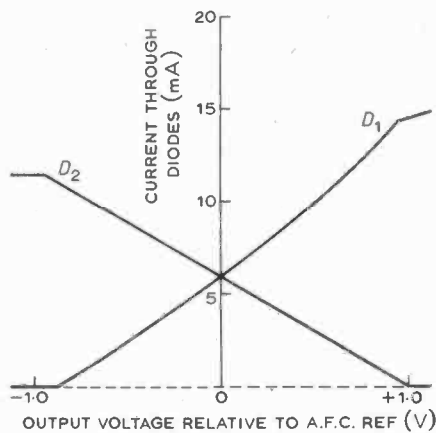


Fig. 4. Difference in off-tune current between the two diodes is not important as the lamps are never both fully on.

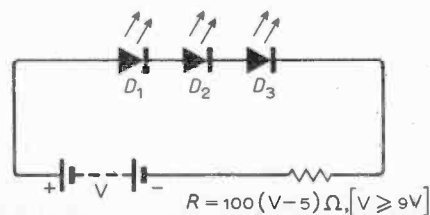


Fig. 5. The two diodes with most nearly equal brilliance can be selected for the tuning indicator when operated in series.

transistors of 220 and the values of Fig. 3 we get values of $47.35k\Omega$ for V_{in} 0.7V above a.f.c. reference, and $46.50k\Omega$ for V_{in} 0.7V below. The attenuation ratio formed by the output impedance of the tuner ($2.2k\Omega$) and the tuning indicator circuit therefore varies by less than 0.08% over this span. Even if it were not for the need to linearize and raise the input impedance of the tuning indicator, R_2 and R_4 would still be needed, because with these two resistors effectively removed (by connecting together the two emitters of Tr_1 and Tr_2), the complete span from D_1 full on to D_2 full on is only $\pm 0.2V$. This sensitivity is too high for easy tuning and considerable flicker of the diodes is caused by the modulation of the carrier.

The resistors R_1 and R_5 are chosen to equalize the resistance seen by the two transistors, to minimize offset due to base current. These base resistors also ensure that the circuit does not become a resonant line oscillator when long leads are connected to the circuit. With modern planar transistors it is all too easy to get such effects if precautions are not taken.

Construction

The prototype tuning indicator is shown above, with the board mounted behind the tuning dial of a tuner. (A photograph shows the unit removed from the dial to show the

mounting of the diodes.) The board is designed to take the type of diode having two pins on 2.5mm (0.1in) centres, and these are mounted on the circuit side. If desired, the board can be mounted remote from the diodes with leads from the board to the diodes.

Lamp matching. As there is some variation of brilliance of the diodes with identical currents from one lamp to another, it is desirable that the two lamps D_1 and D_2 be approximately matched for brilliance. This is easily done by temporarily connecting the lamps in series and passing a current through all three lamps at once (Fig. 5). The two lamps having most nearly equal brilliance are used for D_1 and D_2 .

Avoid excessive heat or mechanical force on the leads of these lamps as they are easily damaged by heat, by the nature of the materials used and of their small size.

Components. Resistors should be $\frac{1}{8}$ -watt, 5% tolerance and of the carbon film type. Transistors should have a $V_{cb} \geq 20V$ and an $h_{FE} \geq 220$ at I_C of 5mA, e.g. BC109, BC169, BC184L. Diodes are Hewlett Packard 5082-4440. All parts for the tuner, decoder, and indicator are available from Integrex Ltd, P.O. Box 45, Derby, DE1 1TW.

About People

'For his outstanding contributions to electronic engineering, particularly in the development of microwave radar, and for his contributions to engineering education and training', the I.E.E. has elected **G. S. C. Lucas, O.B.E., Hon.D.Tech., F.C.G.I.**, an honorary fellow. Mr. Lucas retired from A.E.I. Electronics, of which he was director and group general manager, in 1966. He started his career with the British Thomson-Houston Company in 1915 and after serving his apprenticeship studied at the City and Guilds (Engineering) College, London. In 1925 he went into the B.T.-H. research laboratory where he became responsible for developments in the audio engineering field. For his contribution to the development during the war of centimetric fire-control radar Mr. Lucas was awarded an O.B.E. When, in 1945, the B.T.-H. Electronics Engineering Dept. was set up he became manager and in 1952 chief engineer.

The fiftieth award by the I.E.E. of the Faraday Medal has been made to **Professor F. C. Williams, C.B.E., D.Sc., D.Phil., F.R.S.** for his outstanding contributions to the theory and design of electronic circuits; his leadership of the team which developed the best computers to be sold commercially; his contributions to the theory of alternating-current motors; and his leadership of the team which made important contributions to the design of electric motors and generators'. Professor Williams, who is 60, was a member of Watson-Watt's radar research team at Bawdsey from 1939. In recognition of his work on the development of I.F.F. (identification, friend or foe) he received the American John Scott award. In 1947 Dr Williams joined the staff of Manchester University where he is professor of electrical engineering.

Douglas Stevenson, aged 45, assistant general manager of ITT Components Group Europe for the past two years, has been appointed general manager of the Group.

Educated in Edinburgh, Mr. Stevenson joined Standard Telephones and Cables Ltd, a subsidiary of ITT, in 1955, later becoming manager of ITT's Capacitor Division at Paignton. In 1961 he moved to Brussels as manager of the Components Division of ITT Standard. Returning to the U.K. in 1963, he became manager of the then Components Marketing Division of S.T.C. at Footscray, Kent. At the beginning of 1970 he became assistant general manager of the Brussels-based ITT Components Group Europe with factories in Germany, the U.K., France, Portugal, Switzerland, Italy and Spain.

R. B. Coulson, B.E., B.Sc., M.I.E.E., has been elected to the board of the English Electric Valve Co. and appointed general manager. Born in Australia, and a graduate of the University of Sydney, Mr Coulson came to England in 1949, and joined E.E.V. in 1950 taking charge of the development and production of travelling-wave tubes. In 1958 he was promoted sales manager. E.E.V. has also announced the appointment of **F. C. Thompson, B.Sc., Ph.D., F.I.E.E.**, as deputy general manager. Dr. Thompson graduated from Liverpool University, and served with A.A. Command before becoming a senior scientific officer at the Telecommunications Research Establishment, Malvern, in 1942. He joined E.E.V. in 1945 as engineer in charge of microwave tubes, and was made manager of the Radar Tube Division in 1956. He was appointed assistant general manager in 1962, and elected to the board in 1969.

Ivan J. P. James, B.Sc., F.I.E.E., F.I.E.R.E., who has been with EMI since 1937, has been appointed scientific adviser to the company's Central Research Laboratories while still retaining his present position of technical director of EMI's Sound and Vision Equipment Division. Mr. James led the team which designed the 2001 colour television camera.

EMI have also announced the appointment of two assistant directors in the Central Research Laboratories. They are **J. A. Lodge**, who has become assistant director, audio and television research, and **R. J. Froggatt**, assistant director, systems research. Mr. Lodge assumes responsibility for work in audio frequency techniques, mechanics and optics, sound recording and reproduction, and television. Mr. Froggatt takes charge of research on all other systems including cognitive, display and microwave systems, and automation.

Michael Moore, M.I.E.R.E., is appointed technical manager responsible for design and development and the manufacturing activity of the electronics division of Benney-Geartech Ltd., of Chandler's Ford, Hants. Mr. Moore has spent the last six years as a senior engineer with C.E.R.N., the European organization for nuclear research.

Bert Horlock, M.I.E.E., M.I.E.R.E., chief engineer of Granada TV Rental has been appointed to the board of the company. He joined the Granada organization in 1961 at the Manchester TV Centre and in 1965 transferred to the television rental company as chief engineer responsible for research and development and also technical training and standards.

Cyril G. T. Withers, chief experimental radio officer at the Aeroplane and Armament Research Establishment, Boscombe Down, retires on the 31st March, after nearly 26 years service in the Navigation and Radio Division. Mr. Withers joined the Air Ministry Research Establishment (later T.R.E.) in 1940 and worked on the development and the operation of the C.H.L. and G.C.I. radar systems. For part of this period he was attached to R.A.F. 60 Group, Leighton Buzzard. In 1943 he was granted an honorary commission in the R.A.F. for special ground and airborne radar duties overseas. At the end of the war he was attached to 'T' Force in Germany which was formed to investigate the activities and progress of German scientists. He was later transferred to A. & A.E.E. to take over the Airborne Radar Trials Section. In 1960 he was appointed head of the radio side of the Division from which he is now retiring.

Richard J. Constantine has joined Farnell Instruments Ltd. as internal sales engineer at the Wetherby Office of the company. He was formerly a radio and electronics officer with I.T.T. Marine Radio Co. Ltd. He was radio officer on the last commercial trip of the *Queen*

Elizabeth and spent some time on the Royal Research Ship *Discovery* where he also started transmitting as one of the few Maritime Mobile amateurs (call sign G3UGF/MM). Farnell Instruments Ltd have their own amateur radio society which uses the call sign G4ADQ.

M. J. Tattam has joined GEC-Elliott Process Automation Ltd as sales manager of its Telemetry Systems Division at New Parks, Leicester. He was export manager of the Industrial Instrument Division of Smith's Industries Ltd from 1969 having previously been sales manager, telemetry and data acquisition systems of the instrument division.


Roger Appleton, who was named chief engineer (designate) of London Weekend Television last September, when **Brian Pover**, controller of engineering, left the company, has been appointed chief engineer. Mr. Appleton, who was London Weekend Television's head of production engineering prior to his new appointment, began his career in television in 1954, when he joined the B.B.C. In 1958, after a spell at Granada Television, he went to Rediffusion. When London Weekend took over Wembley Studios from Rediffusion in 1968, Mr. Appleton became supervisory engineer. In February 1970 he was appointed head of production engineering responsible for the technical staff and facilities at Wembley Studios. As L.W.T.'s chief engineer, Mr. Appleton is responsible for the installation of technical facilities at its new South Bank Television Centre, which is expected to come into service in April. Mr. Pover, who is being retained by L.W.T. as a consultant, has joined Prowest Ltd, manufacturers of television monitors and other professional equipment, as managing director.

Plessey Telecommunications has appointed **T. H. Pritchard** as manufacturing executive. Major Systems Division; **R. C. Lawson** as general manufacturing manager; and **A. E. Brothers** as manufacturing manager. Mr. Pritchard, who will be at the company's headquarters in Liverpool, joined the Plessey Company at Swindon in 1952 as a quality manager, later becoming divisional manager. Since 1962 he has been responsible for the Garrard manufacturing operation. Mr. Lawson, general manufacturing manager, Strowger Major Systems Division, who is 51, was educated at the Royal Naval College, Dartmouth, joining the Plessey Company in 1946 as a production operator. Mr. Brothers, manufacturing manager at the Company's Edge Lane, Liverpool, factory is also 51, and was previously manufacturing manager at the Plessey installation in Brazil.

Circuit Ideas

Active zener with slow run up

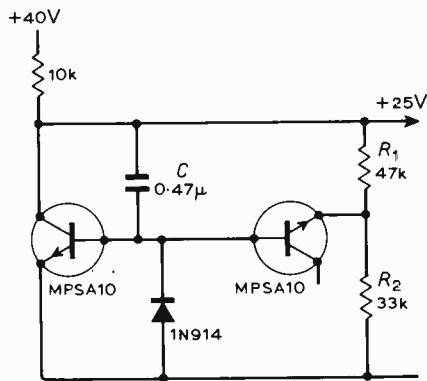The active zener circuit ('High-performance Low-cost "Active Zener" Regulators', Joachim Preis, Oct, 1969) can be combined with the slow run up circuit of P. Lacey (*Circuit Ideas* May 1971) with one transistor doing both functions.



The active zener can operate with very low current, provided that R_1 and R_2 are large and the load current is low. This makes it possible to use a low, non-electrolytic capacitor as the timing capacitor C.
J. Skjelstad,
Norway.

Low distortion f.m. demodulator

A t.t.l. one-shot monostable may be used as a high-linearity f.m. demodulator by connecting it in the circuit shown. Due to

the constant width of the output pulse the duty cycle, and hence the voltage at the output of the integrator network R_1C_1 , are directly proportional to the i.f. Capacitor C_2 is chosen to give a pulse width of 47ns, (the period of one half-cycle at 10.7MHz), this value giving optimum linearity, and as the i.c. includes a Schmitt trigger on the input the circuit need not be driven from a limiter. A demodulator of this type produces high-level noise output in the absence of a proper signal due to random triggering of the one-shot by noise and thus a mute circuit is mandatory. Muting is achieved here by feeding the inhibit terminals of the Schmitt trigger from the collector of the half-wave rectifier Tr_1 . R_1 and C_1 also serve as de-emphasis components and therefore the load impedance should be kept as large as possible in order to avoid degradation of the frequency response. Harmonic distortion at ± 75 kHz deviation is less than 0.5%.

P. Keenan,
Dunstable,
Beds.

Zero marking of a.c. waveforms

It was found that in certain conditions the current of a simple experimental d.c. motor could be negative for part of a revolution. It was easy to show this using a c.r.o. which had a d.c. amplifier — if a double-beam c.r.o. is available, one trace

can be used to indicate zero level. However, when conditions for negative current were being investigated, it was more convenient to mark the waveform of armature current to show the points at which it passed through zero. This could be done by using two diodes as shown in Fig. 1. Current through R_1 , a low-value resistor, develops a voltage proportional to the armature current. Because of the voltage drop across a conducting diode, the relation between the voltage applied to Y_1 and that applied to Y_2 is as shown in Fig. 2. If the voltage under examination becomes very large in relation to the voltage drop across a conducting diode, the 'flats' tend to disappear. If the voltage is less, at positive or negative maxima,

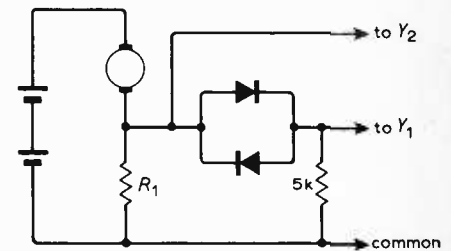


Fig. 1.

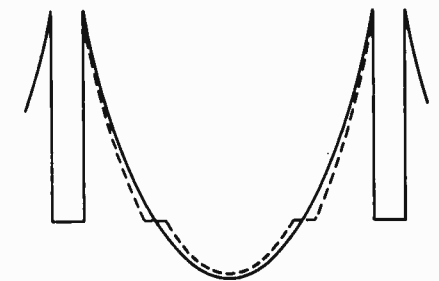


Fig. 2.


than the forward diode voltage drop, the output is zero for the respective period. It should be possible to choose R_1 so that it lies between the two limits corresponding to these conditions.


T. Palmer,
Kew.

Constant-current battery charger

The circuit consists of a rectified and smoothed d.c. supply of about 20V, which is applied in series with a constant-current regulator to the battery. The current is derived from switched resistors, R_1 to R_5 , held at a constant voltage by the zener diode and transistors Tr_1 and Tr_2 which form a Darlington pair. Germanium power transistors such as OC28, OC35, OC36, 2N1021, or similar types are used.

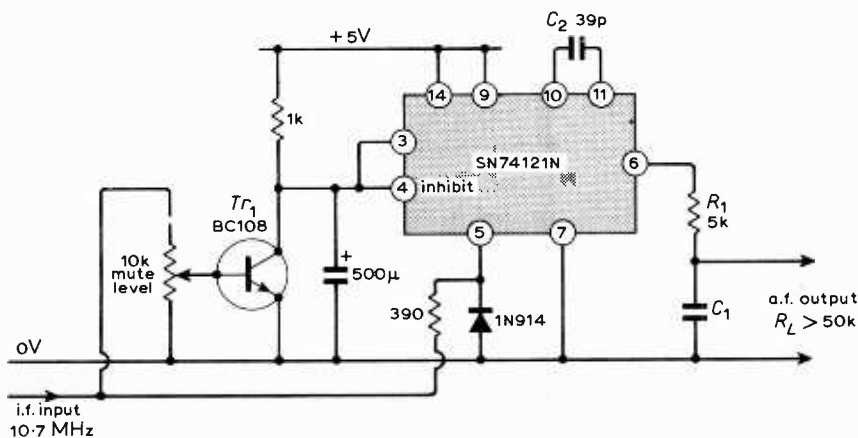The unit which is used for charging batteries up to 12V has several advantages over conventional battery chargers in that the output terminals may be accidentally short-circuited without damage to components. Also, an ammeter is not necessary, since the current is determined by the selection of switched resistors,



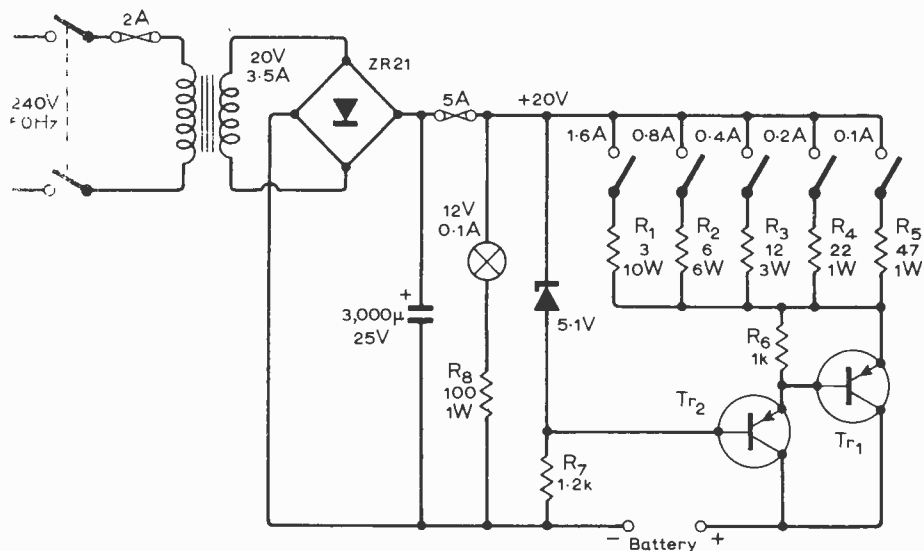

... calibrated current which does not alter during charging. Currents from 0.1 to 3.1A may be selected by closing the appropriate switches and the value of current supplied is approximately given, by $4.8/R$, where R is the appropriate switched resistor. The charging current may be increased to 10A by uprating the components and selecting different values of R .
David Allen,
Manchester.

Now refer to the table below and calculate C_1 , C_2 and C_3 by multiplying the appropriate factor by C_0 :

For	C_1	C_2	C_3
Multiply C_0 by	2.06	0.29	1.03

The capacitors are chosen to be within 1% of these calculated values.


This circuit allows the possibility of using several stages in cascade without emitter following: a 7th order circuit works very well at about 70dB/octave, but different multiplying factors must be considered.

A high-pass filter of the same order can be designed by inverting the elements R and C in each stage.

S. J. Morris,
University Hospital of Wales,
Cardiff.

Low-pass active filter

This circuit utilizes a unity gain amplifier configuration, which is stable using a minimum number of components. A wide range of transistors can be used for this amplifier, but low-noise devices are preferable (e.g. 2N2926 for the n-p-n and 2N5354 for the p-n-p). A gain of unity is obtained by choosing R_1 so that $R_1 = h_{ie} \beta_2$. Resistor R_E was chosen to be $2.7k\Omega$. $V_S(+)$ was 10V and $V_S(-)$ was 15V for the correct d.c. conditions for the transistors.

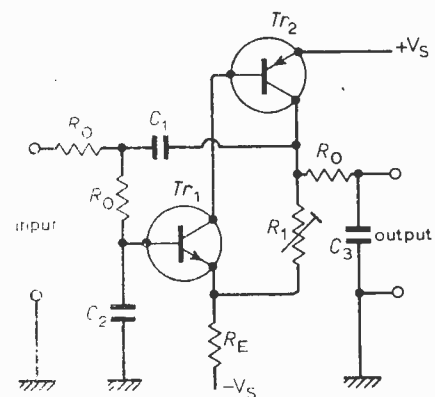


For a ripple of 0.1dB in the pass band and a fall off of 20dB/octave after cut-off frequency f_0 , choose a convenient value of R and calculate.

$$C_0 = \frac{1}{2\pi f_0 R_0}$$

Variable-gain volume control

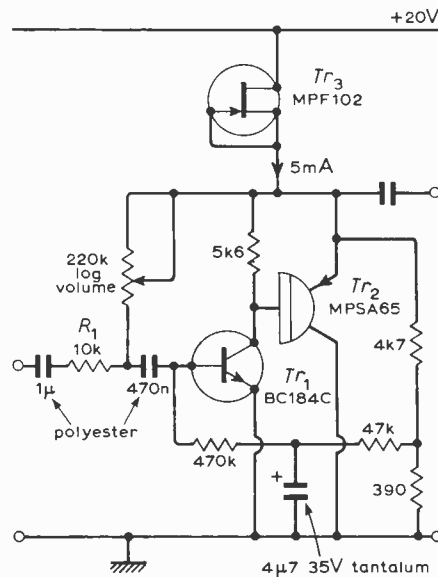Large overload capability is not often provided by commercial amplifiers, but can easily be obtained by using a variable-gain volume-control stage at the input of the pre-amplifier. Inverting




amplifier circuits can easily be designed which will give overload factors of greater than 40dB at normal listening levels. The circuit shown has a maximum voltage gain of $\times 22$ but this is reduced to nearly zero at the minimum setting of the potentiometer. Sensitivity may be altered by increasing the value of R_1 — e.g. $22k\Omega$ gives a gain of $\times 10$. The inverting amplifier basically has one stage which provides a high open-loop gain ($\approx \times 2000$) by employing a d.c. bootstrap circuit, and applied negative feedback reduces stage distortion to a very low level. Signal-to-noise ratio for the circuit shown is greater than 73dB on a 10mV input. For low noise and distortion the BC184C should be selected to have a current gain of greater than 400, and the field effect transistor (MPF102) should have an $IDSS$ of 5mA or greater. The circuit is tolerant of hum and noise on the supply line and so may be run from a poorly stabilized supply. Total harmonic distortion at a gain of $\times 22$ and 1V r.m.s. output measured 0.025% at 1kHz and 0.05% at 10kHz. Equivalent input noise is less than $2\mu V$, in the bandwidth 20kHz with input shorted to earth; and upper break frequency ($-3dB$) above 100kHz, with gain $\times 22$.

A. Jenkins,
Taunton.

(The symbol shown for Tr_2 —the Motorola Darlington transistor type MPSA65 — was originally suggested by J. L. Linsley Hood in his article 'The Liniac', published in *Wireless World* in September 1971. Ed.)

Overtone oscillator

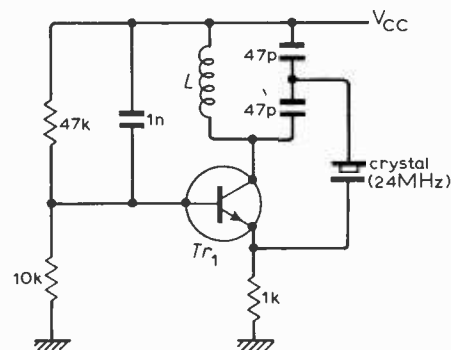The circuit works well with low activity crystals and is suited to either overtone or fundamental operation. The ratio of the series capacitors controls the amount



of feedback and the inductor, L , resonates with the series capacitors at the desired output frequency, giving an output which may be taken directly from the emitter resistor or by means of link coupling. The transistor Tr_1 is a 2N706 (or similar type) and the circuit operates from a 12V supply.
L. V. Gibbs,
Wellington,
New Zealand.

A survey of Stereo Cassette Tape Decks

2: More test reports, a listening test and advice on getting the best from a cassette

by Brian Crank*

Last month, in part one of this article, we described in detail how the various measurements were carried out and the reader is advised to read this account before interpreting the test results given here. Briefly, we made a set of curves using standard (ferrous oxide) tape on each recorder and, if the machine was equipped with a chromium dioxide tape equalization switch, we repeated the measurements using chromium dioxide tape.

In every case the top amplitude/frequency curve is the left channel at OVU (full recording level). The next two curves below this are the left and right channels at -10VU (for assessing channel, balance etc.) and the lowest curve is crosstalk relative to the top OVU curve.

A constant 3kHz signal was recorded on the tape and played back through a spectrum analyser. The results are given in the curves mounted below the amplitude/frequency curves. The major peak is the 3kHz fundamental. The spectrum analyser automatically switched ranges at 6.3kHz so the gap in the response at this point occurs just before the second harmonic. The major harmonic distortion occurs at the third harmonic (9kHz) and is the peak on the right of each trace.


All the measurements given in the test reports are as measured by us. The harmonic distortion figure is high because it includes everything (hum, tape noise etc.) outside a narrow band centred on 1kHz.

National R-275-U



Total harmonic distortion 2%: Signal-to-noise ratio, NFD out 44dB, NFD in 50dB: Wow and flutter 0.22%: Bias oscillator frequency 106kHz: Input for OVU, phono L-27mV R-28mV, DIN L-1.6mV R-1.65mV, microphone (not measured): Output DIN and phono L-740mV R-860mV: Rewind 1m 42s: Dimensions 440 × 300 × 120mm. Price £139.95.

Six oblong push buttons switching internal solenoids are used to control the tape transport mechanism in this machine. This method is convenient, easy to operate and the best we have tested. It is a pity that the wow and flutter is so high. There is a small red light which lights up when the tape is travelling at $1\frac{7}{8}$ i.p.s. during play and record. In addition when the white record button is pressed the button lights up but the tape does not move until the play button is pressed to give the user a chance to set the recording level. If at the start of a recording, even in the middle of the tape, the tape position counter is set to zero and a switch marked memory is set to on, then at the end of the recording if the rewind button is pressed, the tape will rewind to the start of the recording and switch off automatically.

The machine has twin rotary type recording level controls which make fading a stereo signal a difficult task. The top control panel of the machine is unnecessarily cluttered with a pair of rotary output level controls. When it is considered that the machine will be used in conjunction with a high-quality amplifier incorporating a volume control it makes sense to use preset output level controls on the recorder tucked away at the back of the machine out of sight and out of the way.

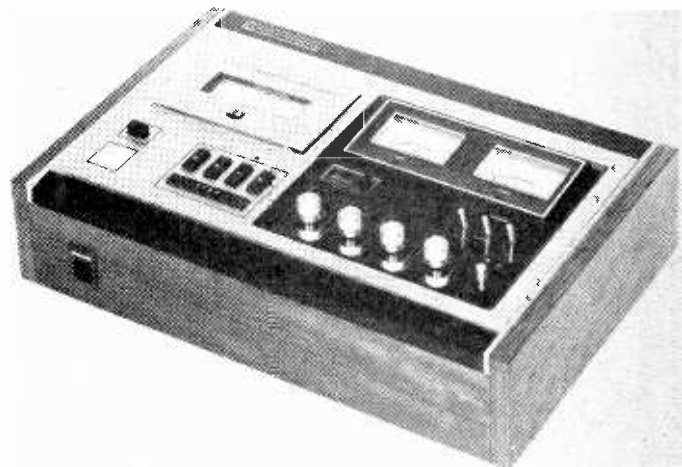

National R-275-U

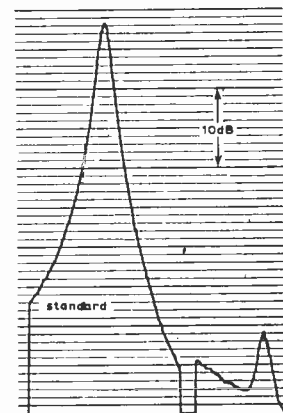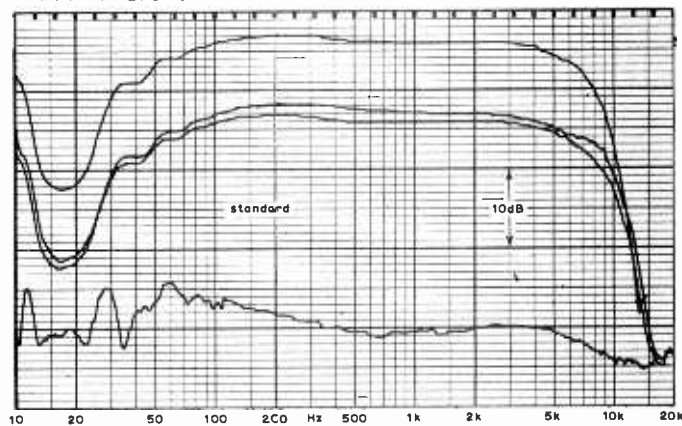

* Deputy Editor, *Wireless World*

Three toggle switches are used to switch on the memory system, to alter the equalization between 'SG' (special grade?) and normal, and to switch the NFD (noise free device) in and out. We are not sure what is meant by special grade and normal tape but gather that SG out to be used when recording on low noise tape. The machine we tested was not built for the British market and we understand that this switch will be used for conventional chrome/standard equalization switching when the machine is introduced into this country. The NFD was discussed in part 1 in the section on noise reduction systems but it does not compare favourably with the Dolby system. The control panel is completed by an on/off switch and a cassette eject button. A headphone output socket is fitted to the front of the machine.

On the rear of the machine, set in a recess, are the DIN and phono input/output sockets, twin miniature microphone input jacks and a socket for controlling the machine remotely.

We cannot comment on the instruction book, it was written in Japanese! (not being intended for this country).

The sample of the National R-275-U we tested, judged on our measurements, did not compare well with the other machines.

Sansui SC-700



Total harmonic distortion 1.6%: Signal-to-noise ratio, Dolby out 47dB, Dolby in 52dB: Wow and flutter 0.14%: Bias oscillator frequency 106.7kHz: CrO₂ erase 52dB: Input for OVU, phono L-66mV, DIN L-14mV, microphone L-0.5mV, centre -0.5mV: Output, phono high L-0.95V, phono low L-300mV, DIN L-0.95V: Rewind 2m: Dimensions 385 × 255 × 103mm: Price £191.65.

This is another product of Nakamichi Research (look at the frequency response); however, it is somewhat different from the other Nakamichi machines tested in styling and in the facilities it offers. The tape transport is standard and the usual indicator lamp is provided for record. Unfortunately an output level control (dual concentric) is provided on the top control panel. This should have been banished to the back of the machine and the space occupied by a mono/stereo switch which the machine lacks. The recording level controls are also of the rotary dual-concentric type and the friction between the two knobs is such that, once the balance has been set both knobs turn together. This system is quite acceptable. A third rotary level control is used for the centre microphone. This machine is the only one tested which can be used with three microphones simultaneously. The effect of using three microphones, according to the instruction manual, is to 'prevent the shortage of centre sound when recording in a large room with the normal left and right microphones widely separated and to enhance the sound effect in vocal recordings'. The three microphone jacks share the front of the machine with a headphone output jack. Three push-buttons on the top of the machine are used for switching in the Dolby system (with an associated indicator light), chrome/standard tape equalization and a power switch.



The two VU meters are situated on top of the machine to the



Sansui SC-700

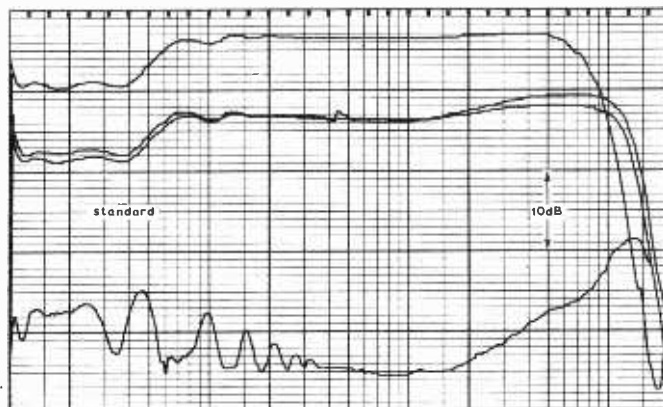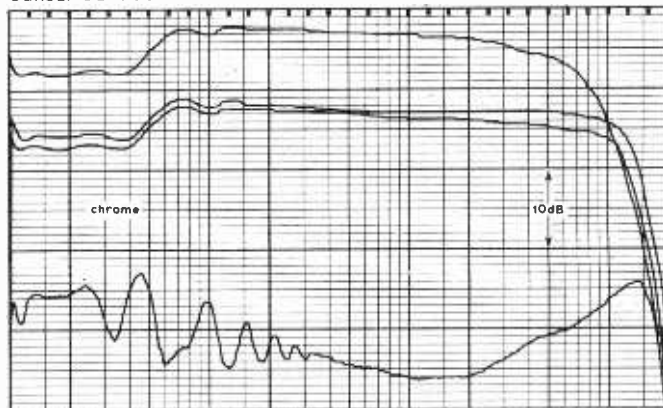

10 20 50 100 200 Hz 500 1k 2k 5k 10k 20k

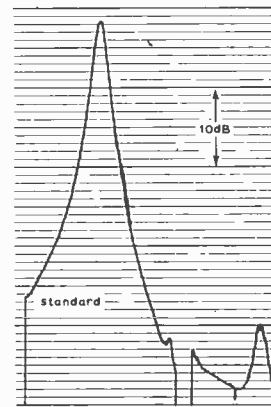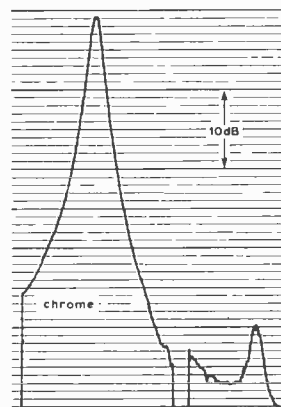

rear on a sloping panel. They are very large (68mm) and light up like Christmas trees in green, red and white; each meter is lit by two 6.5V 0.25A lamps run at 5.4V. The meters are easy to read at a distance which is a better solution to the problem of accidental overload than the flashing lights used on some other machines. Unfortunately the right-hand meter on the test machine did not work (so most of our measurements were made only in the left channel); however, it is only fair to mention that the machine had been flown specially from Japan for our tests and had also undergone two road journeys without having a pre-delivery check. It was the first machine of its type in the country.

On the rear of the machine there is a voltage selection panel (100 to 240V, 50 or 60Hz), a fuse, high- and low-level phono input sockets, phono output sockets and a DIN input/output socket. The machine incorporates 48 transistors (including two f.e.t.s), 16 diodes and two thermistors.

The instruction book is excellent and is well illustrated. The machine comes complete with a full circuit diagram, a cleaning cloth and an angled head 'felt tipped pen' for cleaning the record and replay heads.

Apart from the few shortcomings discussed this is a good machine which can be recommended from the performance point of view but one has to pay highly for the few extra facilities it offers over other Nakamichi machines.

Teac A-350

Total harmonic distortion 2.3%: Signal-to-noise ratio, Dolby out 50dB, Dolby in 53dB: Wow and flutter 0.15%: Cr₂ erase 50dB: Input for OVU; DIN L-0.2mV R-0.2mV, phono L-85mV R-85mV: Output DIN and phono L-550mV R-550mV: Rewind 1m 46s: dimensions 430 × 247 × 200mm: Price £144.

This machine was lent to us by an independent laboratory who had been evaluating it. If this laboratory found something out of adjustment they put it right. The machine is, therefore, not necessarily representative of production items which will be sold in this country.

The six tape transport control keys have a not-very-pleasant 'loose then stiff' feel although the mechanism itself seems to perform well enough and returns a fairly respectable wow and flutter figure. A long narrow amber lens is illuminated by a spot of light which travels down the length of the lens when the tape is moving in either the record or playback modes. Below the lens is a Perspex light guide and a small lamp. The light path between the lamp and guide is interrupted by a slotted disc. The idea is a good one in that one can see from a distance if a cassette has jammed. The top control panel has two long slider type record level controls and two slider output level controls which are a waste of panel space as discussed earlier. Three toggle switches are used for chrome/standard tape equalization, microphone and DIN or line



input selection, and Dolby in/out with the usual associated Dolby warning light. Between the reasonably sized and fairly well illuminated VU meters is an unnecessary peak level warning lamp. One would have thought the only reason for an indicator of this sort was to be able to see, from a distance, if overload was occurring. As the lamp on the Teac is set at the bottom of a tube one would need to hang from the ceiling to see it from any distance. On the front of the machine are jack sockets for two microphones and a pair of headphones. The DIN and phono input and output sockets are set in a recess at the back of the machine. A fuse is fitted underneath.

The frequency response is 'Nakamichi-like' and the matching between channels is very good indeed. The machine has a good, average, all-round performance. We cannot comment on the instruction book as an English version is not yet available.

Uher compact report stereo 124





Total harmonic distortion 3%: signal-to-noise ratio 50dB: Wow and flutter 0.18%: Bias oscillator frequency 100.8kHz: Input for OVU (all DIN), radio L-3.7mV R-4mV, line (phono) L-150mV R-161mV, car radio (d.c. isolated) L-56mV R-56mV, external microphone L-0.2mV R-0.2mV: outputs, radio L-0.8V R-0.8V, car radio L-45mV R-45mV, speaker 2V across 4Ω: Rewind (mains power) 2m: Dimensions 185 × 180 × 57mm. Price £185.

The Uher 124 differs considerably from the other machines tested and is designed to function both as a portable recorder and as an adjunct to a high-quality audio system. It is the smallest machine we tested (by a long way) it is the only one to contain an internal loudspeaker and the only one capable of operating from a variety of power sources.

The 124 can be powered by six small pen-cells, a lead acid accumulator, a nickel cadmium battery, a 12V car battery or from the mains (100-130V, 200-240V, 50 or 60Hz) using a mains power unit. An accumulator or the batteries slip into a compartment at the rear of the machine and, if desired, the mains power unit can be plugged in as well. The machine will then run from the mains and the accumulator will be recharged. The mains power unit is the same size as the accumulators and can be slid into the battery compartment for continuous mains operation if required. We noticed a fairly high level of hum when the mains power supply was fitted inside the machine.

The cassette is loaded into a slot in the front of the machine 'thin end first'. The tape transport mechanism has two main controls, a three-position (forward, reverse and neutral) fast wind lever and a five position 'joy stick' type switch. With this switch up the machine is switched off. When the lever is moved to the central position the machine is switched on provided that a cassette is in position. Moving the lever to the left or right selects play in the forward or reverse direction (the machine has a four element head so there is no need to turn the cassette over to play the other 'side'). Moving the switch down puts the machine in the pause condition. A small moving-coil indicator shows which 'side' of the cassette is selected. When playing back, on reaching the end of the tape the machine automatically reverses and plays back the other 'side'. One can record only in one direction.

Teac A-350

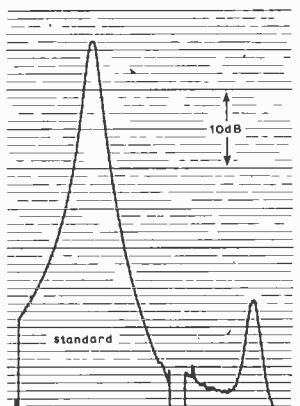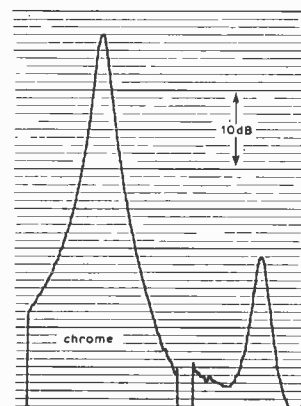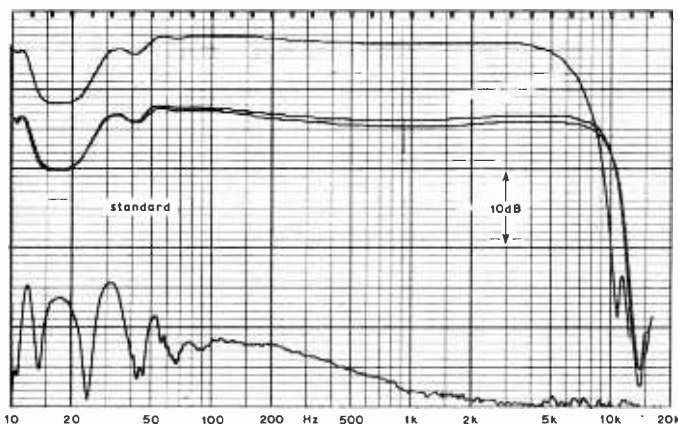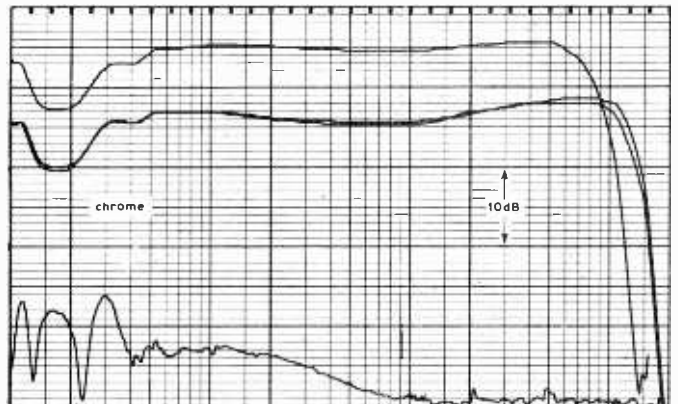





Other front panel controls include four push-buttons which switch the internal speaker off, select internal or external microphone, automatic level control on/off and select record. The internal microphone is fitted to the front panel and is a low-voltage capacitor type. When automatic level control is selected the time constant in use is determined by which input socket is being employed. A manual rotary record/playback level control and a single VU/battery-level meter completes the front panel. No means is provided for adjusting the stereo balance and a mono/stereo switch is not included.

On the rear of the machine are two sockets, one for connection to a car radio and the other for connection to the mains power supply unit when it is being used separated from the machine.

Three sockets on the side allow the connection of headphones or loudspeakers, line in and line out, and a variety of accessories including remote control units. Access is provided to the unused record sections of the record/playback head and another pin allows the motor speed to be varied remotely.

Uher compact stereo 124

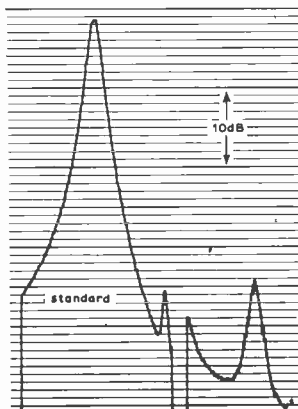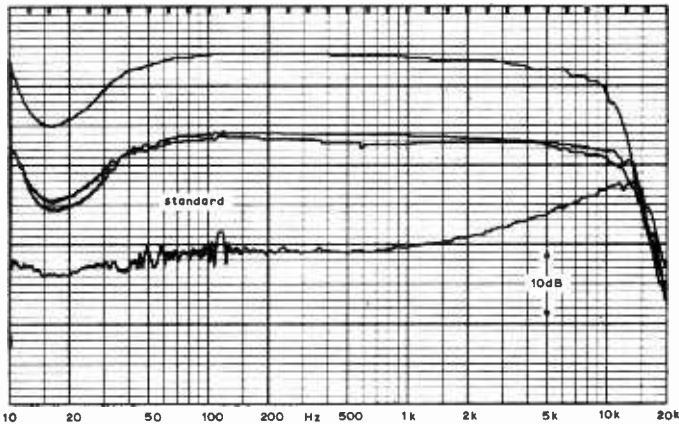

Considering that it has not a noise reduction system the signal-to-noise ratio is very good indeed and has been achieved by using specially designed high-inductance heads. Unfortunately the price which has been paid for this noise reduction is a fairly poor crosstalk performance. All other aspects of the performance are good and Uher are to be congratulated for packing so much into such a small space.

The tape transport mechanism seems to be very choosy when it comes to cassettes, and cassettes which run smoothly on other machines will not necessarily be accepted by the 124.





As soon as the equalization standard for chromium dioxide tape is decided Uher intend to fit a chrome equalization circuit which will be selected automatically when a chrome cassette is put into the machine.

Wharfedale DC9

Total harmonic distortion 2.2%: Signal-to-noise ratio, Dolby out 49dB, Dolby in 54dB: Wow and flutter 0.18%: Bias oscillator frequency 102.2kHz: CrO₂ erase 50dB: Input for 0VU, DIN and phono L-39mV R-39mV, microphone L-0.2mV R-0.2mV: Output DIN and phono L-1V R-1.1V: Rewind 2m 11s: Dimensions 279 x 216 x 89mm: Price £110.

Taking into account normal production and adjustment tolerances the machine is identical to the Bell & Howell DES 1700 as far as

Wharfedale DC9

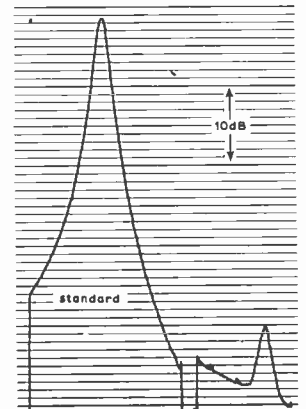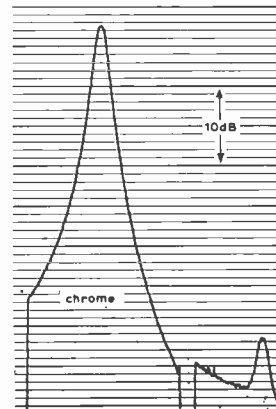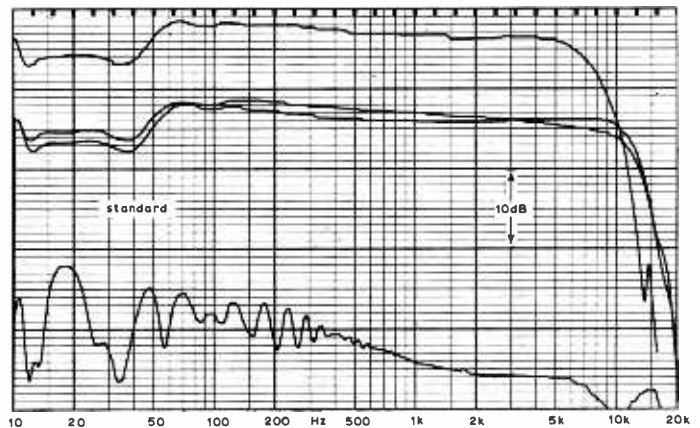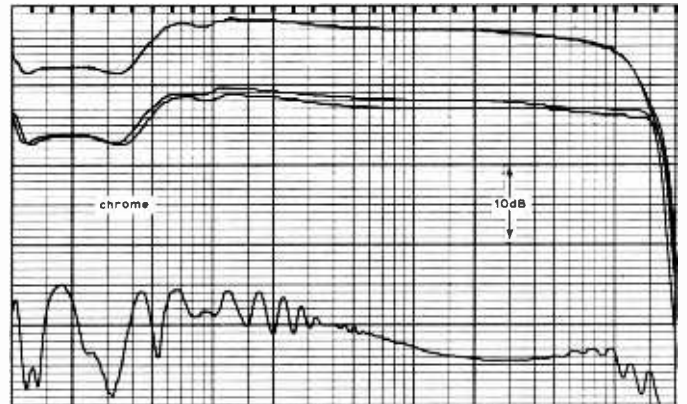



performance is concerned and is in fact another product of Nakamichi Research. The DC9 is smaller than the 1700 and its top mounted controls are perhaps more convenient to use with the exception of the two rotary recording level controls. To properly fade a stereo signal one has to use two hands, not a good point. Three push-button switches are employed for Dolby in/out, chrome/standard tape equalization and power on/off; there is not a mono/stereo switch. Like the Bell & Howell there are three indicator lamps (power, record, Dolby). Microphone input is by front panel jack sockets and DIN and phono output/input sockets are provided on the rear of the machine. There is also an output level control on the rear of the machine.

The instruction book is fairly good but it can be a little difficult to follow because it is written in three languages badly laid out.

The choice between Wharfedale and Bell & Howell must be made purely on small points which are a matter of personal preference; styling, size, rotary or slider recording level controls, mono/stereo switching, and input/output socket arrangements. The frequency response of the machine is good.

Listening test

Last month we mentioned that we had carried out a listening test in which we compared an open-reel tape recorder with one of the cassette recorders we had tested. The object was to assess what one lost in performance, if anything, if one bought a cassette recorder. To do this we assembled two listening panels. The first panel was made up from both males and females who had no special technical or musical knowledge. The second panel, all male, was chosen for either technical or musical ability (in some cases both) and comprised members of the editorial staffs of our associated publications: *Electrical and Electronic Trader*, *Electrical and Radio Trading*, *Electrical Review and Electronics Weekly* together with the technical staff of *Wireless World* and two music critics.

Acoustically the room used for the tests did not differ widely from conditions one would find in a large living room. The equipment, with the exception of the loudspeakers, was situated in an adjacent room so that the listeners did not know which machine they were hearing.

Material from disc records was used as a standard against which the recorders were compared. For disc reproduction we employed a Garrard Zero 100s turntable fitted with a Shure V15 Mk 2 cartridge, a Bang and Olufsen 3000 tuner amplifier and a pair of the folded horn loudspeakers designed by John Greenbank and described in the January 1972 issue of *Wireless World*.

The cassette tape deck was the Bell & Howell DES 1700 (reviewed last month) and the open-reel tape deck was a Tandberg 3000X. Both these machines cost about the same (within a few pence).

We then had a difficult problem to resolve. The Tandberg was a three-speed machine (1 7/8, 3 3/4 and 7 1/2 i.p.s.). At what speed should we run it for the comparison tests? A good argument could be put forward for using each of these speeds. In the end it was decided

to use the Tandberg at its best at 7 1/2 i.p.s. It should be pointed out that at this speed the Tandberg is much more expensive to run in terms of tape cost than the cassette machine.

As we were using the open-reel machine at its best we did the same for the cassette recorder and operated it with the Dolby noise reduction system switched in and with a chromium dioxide tape cassette. The open-reel machine was used with the reel of low-noise Tandberg ferrous oxide tape that came with it.

To the user, although both machines cost the same, they have different advantages and disadvantages. The cassette machine was the easiest to operate, it had a noise reduction system and had all the advantages one normally associates with cassettes from the handling point of view. The Tandberg did not have a noise reduction system, it had three speeds and offered such facilities as sound-on-sound, sound-with-sound, off tape monitoring (because of the three heads) etc.

In the listening tests the Tandberg came out slightly better than the Bell & Howell on signal-to-noise ratio. We feel, however, that this may not have been the case if the machines had been in the same room as the listeners because the mechanical noise from the Tandberg was much higher than that from the Bell & Howell. In a smallish room this could have swayed the listeners in favour of the Bell & Howell on this point.

We chose extracts from four discs and these were recorded on the cassette and open-reel machines.

The inexperienced panel listened first to the disc and then to the two recorders and were asked to say how good the recordings were when compared to the disc. They were given four choices: the same as, slightly worse than, much worse than and very much worse than. They were asked to make their judgment after assessing background noise, 'tonal quality' and 'clarity'.

When analysing the results, if a person thought the cassette recorder was slightly worse than the disc and the open-reel recorder was much worse than the disc one point was scored in favour of the cassette machine. If a listener thought that the machines both sounded slightly worse than the disc or both sounded much worse than the disc a zero was scored. In other words, one point was scored for each category difference between the two machines. The results are summarized in Fig. 11(a). It can be seen that seven listeners thought that the cassette machine sounded one category better than the open-reel machine, one thought the open-reel machine sounded better and one said that both machines sounded the same. One must conclude that as far as our inexperienced panel was concerned the cassette tape recorder was to be preferred.

(a)

	Cassette recorder	Open reel recorder
overall	1 1 1 1 1 1 1	1 0

(b)

	Cassette recorder	Open reel recorder	
bass response	1 1 1 2 1 6	1 2 2 1 1 7	0 0 0 0 0 0 6
treble response	1 1 1 1 4	1 2 1 2 1 2 1 1 1 1 1 14	0 1
noise	1 1 1 3	1 1 1 1 1 1 1 1 8	0 0 0 0 4
distortion	1 1 2 1 2 1 1 2 1 2 1 15	1 1 1 1 1 1 5	
wow & flutter	1 1	1 1 1 3	0 0 0 0 0 0 0 7
overall	1 1 1 1 1 5	1 1 1 1 1 1 1 1 1 9	0 0 0 2

Fig. 11 (a) Inexperienced listeners thought the cassette best while, (b), the panel of experts preferred the reel-to-reel machine.

The experienced panel was asked to compare the recorders with the disc on the following points: bass response, treble response, signal-to-noise ratio, distortion, and wow and flutter. They were also asked to give an overall assessment of performance. For most of these points they were asked to place a recorder into one of six categories on a scale similar to that already detailed for the inexperienced listeners. Again a recorder scored one point for each category it was judged better than the other machine in relation to the disc. If both machines were given the same rating a zero was scored. The results are summarized in Fig. 11(b). The total score is given in the bottom right-hand corner of each 'block'.

The bass response of both machines was judged to be very similar with 6 points for the cassette, 7 for the open-reel and 6 listeners saying there was no difference. All the listeners thought the recorders were not as good as the disc on this point by a fairly large amount.

The open-reel machine was judged to have a much better treble response than the cassette by 14 points to 4, with one listener saying there was no difference. In general the reel-to-reel machine was thought to be only slightly worse than the disc.

The open-reel machine had the edge on signal-to-noise ratio but, as already stated, was mechanically noisier.

The sample of the Tandberg we used suffered from high-frequency distortion, which is reflected in the results. The cassette machine was rated much better than the open-reel by 15 points to 5 and slightly worse than the disc.

Both machines were rated the same for wow and flutter and no different from the disc. Two of the listeners complained that the material we used was unsuitable for this test.

Overall the experienced listeners preferred the Tandberg by 9 points to 5, a ratio of about 2:1. If one takes the difference between the scores for each aspect of performance and adds them up, this 2:1 ratio appears again. It is probably fair to assume that the distortion of the high frequencies on the Tandberg was an isolated case and does not occur on all machines of this type. If this was indeed so then the open-reel machine must be classed as being much better than the cassette recorder.

One possible explanation for the differing views of the two panels is that some members of the inexperienced panel may have grown accustomed to listening to small radio sets and medium-priced radiograms and had come to prefer this kind of sound.

It would appear that when one buys a cassette recorder one trades performance and versatility for convenience in use. However the cassette recorder we tested, while not performing as well as its reel-to-reel counterpart, put up a creditable performance and many people would think that the trade-off was worthwhile.

Caring for, and using, a cassette recorder

If you buy a cassette recorder there are two other essential purchases you must make besides a supply of blank cassettes. These are a small bottle of isopropyl alcohol and some 'cotton wool buds' (small balls of cotton wool attached to short wooden sticks often used in baby care). Both items cost only a few pence from a chemist.

Cassette recorders employ heads with an extremely narrow gap that soon becomes clogged with oxide from the tape which lifts the tape away from the heads causing poor erase and useless recordings. The oxide also builds up on other parts which come into contact with the tape; in particular the pinch wheel. The wow and flutter figure of one of the recorders tested dropped by 50% after the pinch wheel and tape path had been cleaned.

The rule is to clean the heads and the tape path after five or ten cassettes of playback time and *before every recording is made*. This is no great hardship as the task takes only a few seconds.

The average machine has a very large number of internal preset adjustments which will probably require periodic attention, and mechanical parts will require cleaning and lubricating at intervals. These are jobs for the manufacturer and we feel that it would be reasonable to return the machine every six months to a year for overhaul. Some manufacturers in fact recommend this.

Cassettes should be stored in a cool place and the surface of the tape should not be touched with the fingers. It is a good practice after playing back a recording not to wind back the tape if the cassette is to be stored. This is because fast wind spooling is not

as even as spooling during record or playback so there will not be as much stress stored in the tape and, consequently, there will be less tendency for the coils of tape to adhere to one another during storage.

It is false economy to buy cheap cassettes as these could contain abrasive tape that will soon wear out expensive heads. There may also be a tendency for such cassettes to stick or jam.

When recording it is usually better to err on the side of under-recording rather than the converse.

All of the machines had some means of switching the drive motor off automatically should the tape stop moving for any reason. In addition some machines had a solenoid which operated under these conditions to disconnect the complete drive system, having the same effect as pressing the stop button.

If a recorder is not fitted with the automatic drive disconnect mechanism it is essential not to leave the machine with the play button pressed and the motor not running. If you do, a flat on the pinch wheel will develop which will cause wow and flutter.

The ideal machine?

We are of the opinion that not one of the machines tested was ideal, either from user or performance point of view. If features of the different machines were to be combined to produce an ideal machine we would choose:

The National tape transport controls with the Advent or the Nakamichi mechanism. The frequency response of the Akai. The versatility of the Uher. The Sansui VU meters. The machine would also have slider type recording level controls (or perhaps the Advent level system), a mono/stereo switch, a choice between chrome and standard tape equalization, a Dolby noise reduction system with a calibration oscillator, a preset output level control, a choice of phono or DIN input/output sockets, a headphone monitoring jack, and twin microphone jacks. Such a machine would probably be very expensive. In the reports we have already stated our opinion regarding output level controls. Another point which we found very annoying was the absence on some machines of a mono/stereo switch. This switch is usually only a single-pole on/off type that parallels the two channels at the input for mono operation. Without it, when recording from a mono source, all the information is in one channel only and half of one's audio system is being wasted. Apart from all the sound coming from one corner of the room one loses the impression of spaciousness normally associated with playing a mono signal through a stereo system. A stereo/mono switch can easily be added externally but this is not very convenient.

Finally, a number of the machines came equipped with a non-standard mains plug (Japanese) which we think is bad practice.

Sixty Years Ago

April 1912. *The Marconigraph* contained an article by H. Riall Sankey 'Mechanical Analogies Applied to Wireless' which describes the action of a tuned circuit in a manner that would probably be welcomed by many newcomers to the art today. "If a weight is dropped into still water concentric wavelets will be formed. If the weight is too large or the height from which it is dropped is too great, not only will waves be formed, but there will be splashing, and this splashing corresponds to the brush discharge already referred to. If the weight be fixed to a horizontal spring, and a force is momentarily applied to the weight, it will oscillate in a well-known manner. It will hit the water, and each time it does so will produce waves in the manner already pointed out, and if the energy is too great there will be splashing as well as waves. A smaller weight placed underneath the big one held up by a horizontal spring, will also form an oscillatory system, and will be put into motion by the large weight first hitting the small weight, which, in its turn, will hit the water and produce the waves. Matters can be so arranged that the energy imparted to the small weight at each impact is sufficient to produce the maximum amount of wave without any splashing . . .

"It is obvious that a necessary condition to carry out this effect is that the small weight shall always be just at the top of its path as the big weight comes down to hit it — that is to say, both oscillatory systems must have the same time-period, or, in other words, they must be tuned."

This analogy explained the action of a transmitter of the time which consisted of a tuned transformer (large weight) to set the frequency of the spark and provide a means of feeding energy into the system. The small weight represents the aerial coupling transformer.

World of Amateur Radio

"Top band" season

The latest 160-m bulletin issued by Stew Perry, W1BB, confirms impressions that the band is opening earlier and closing later this year, in line with lower sunspot activity, producing DX that would have been unthinkable a few years ago on this m.f. band. Scotland to West Australia, Eire to Hong Kong, Alaska to Hong Kong, Europe to South America are among the many contacts reported. ZP8AY, Ascension Island, made several hundred contacts with Europe, United States, West Indies, Brazil, etc before closing towards the end of 1971. There is hope that another station on the island, ZD8CS, may open on the band soon. The Czech top-band station, OK1ATP, has made more than 200 contacts with the United States since 1968. Stew Perry himself made 12 transatlantic contacts during the tests of January 9th. He rates long-wire Beverage aerials as 'No 1 for receiving only' listing other effective top-band aerials as verticals (quarter-wave, or less with top loading) providing they are used with multiple ground radials, inverted-vee sloping dipoles, inverted-vee dipoles, dipoles and long-wire types. One American station, W4BRB, is reported to be using 300 sq ft of aluminium foil in thin strips to increase ground capacity.

New look at mechanical TV

In a recent letter to Michael Hallett, manager of the I.T.A.'s Television Gallery, Chris Long, of East Hawthorn, Victoria, Australia, reported that a new low-definition television system which he has developed is being used by a fast-growing group of Australian amateurs on 1.8 MHz, as a 'moving image' alternative to slow-scan TV. The system, with a standard of 48 lines, 4 fields, uses mechanical scanning with a Nipkow disc but with direct scanning rather than flying-spot techniques to allow scenes illuminated in natural light to be transmitted. A member of the Australian group has developed means of adapting almost any oscilloscope to provide a suitable monitor. The restricted bandwidth permits transmission on h.f. and the Australians are hoping that the idea will

spread internationally. Chris Long has also built a 30-line scanning unit as part of a demonstration he is giving of mechanical television systems and has acquired a tape of video signals taken from the I.T.A.'s 'Phonovision' 30-line video disc.

In the U.K. amateur TV licences have risen to 214, and there are also numbers of enthusiasts who confine their activity to closed-circuit operation. The British Amateur Television Club's next convention is to be held on Saturday, September 16 at I.T.A. headquarters in Knightsbridge, London. *CQ-TV*, the bulletin of the club, has started a series of articles on 625-line PAL colour.

One of Europe's keenest exponents of slow-scan TV, Professor Franco Fanti, IILCF of Bologna, Italy, has just published two new booklets 'Slow scan TV monitor' (Italian text) and 'Slow scan flying spot scanner' (Italian text plus English summary) giving full construction details of these two essential items of slow-scan equipment.

John Tanner, G6NDT/T, is now active from Andover with 100 watts vision in the 70-cm band.

Local activities

Probably nobody knows just how many active local societies, clubs and groups devoted to amateur radio exist in the U.K. There are over 330 (including a number overseas) affiliated to the R.S.G.B. but almost certainly there are many less formally constituted groups. Some have permanent club rooms, some meet in members' homes weekly or monthly. Some wax and wane in a short space of time, some maintain successful activity over many years, others vanish almost without trace. Popular activities include junk sales, morse classes, club 'project' evenings, and 'natter nites' (*sic*). But the mainstay is the informal lecture, and these reflect current interests to a remarkable degree. The current crop of lectures includes such topics as slow-scan TV, crystal-controlled clocks, s.h.f. and v.h.f. equipment, problems of r.t.t.y., ham radio in the South Pacific, aerial circus, early days of amateur radio, video tape methods, converting business radio

equipment for v.h.f. use, test equipment and even nuclear physics — with such variety clearly the spell of local meetings has by no means vanished!

Two popular annual events covering a wider area loom up. The 18th annual v.h.f./u.h.f. convention at the Winning Post Hotel, Whitton, near Twickenham, Middlesex, is on Saturday, April 22nd. The Northern Radio Societies Association convention/exhibition is at Belle Vue, Manchester, on Sunday, May 7th.

The 1972 Affiliated Societies Contest was won by G3SSO, the station of the Government Communications Headquarters' amateur radio society at Cheltenham. Runner-up was G3BEA, club station of British European Airways. More than 50 societies entered.

U.S.S.R. "50" stations

Since February 23rd, the Radio Sport Federation of the U.S.S.R. has been operating five special stations as part of a 'radio expedition' to commemorate the 50th anniversary of the founding of the Union of Soviet Socialist Republics in 1922. In the first week, the stations used the call signs UA50 (UA fifty) A to E, with the second letter of the prefix changing each week until June 7th. To judge by the strong signal and snappy procedure of UA50B when I worked the station on 3.5 MHz, this group of stations intends to register many thousands of contacts.

In brief

To encourage more s.s.b./c.w. activity on v.h.f. bands, Tom Douglas, G3BA, suggests that between the hours of 19.00 and 23.00 local time, stations should send CQ calls every hour on the hour. . . . The Australian Ionospheric Prediction Service (whose interest in transequatorial propagation was noted in the February 'W.o.A.R.') has invited co-operation from amateurs in studies of transequatorial openings and v.h.f. propagation between Australia and the Antarctic. . . . The 21st anniversary of the University of Keele will include special operation of its amateur radio society's station G3UOK on April 22 on 3.5, 14 and 144 MHz. . . . Violent ionospheric storms were reported in the third and fourth weeks of February. . . . The White Rose Mobile Rally on Easter Sunday, April 2, will be at Lawnswood High School, Leeds 6 (details, R. Short, G3YEE, Bradford 664220). . . . North Midlands mobile rally is on April 16 at Drayton Manor Park, near Tamworth. . . . Dr John Saxton, who was R.S.G.B. president in 1970, is being invited to be president in the Society's Diamond Jubilee year of 1973. . . . Royal Signals Amateur Radio Society is to operate GB3RCS, from May 14 to 22 to mark the 75th anniversary of Marconi's experiments over distances of up to eight miles in May 1897 when the Royal Engineers (from which Royal Signals was formed) assisted.

Pat Hawker, G3VA

Miniature Automatic Telephone Exchange Modifications

The writer built a telephone exchange similar to the one described by G. F. Goddard and suggests some modifications

by P. F. Gascoyne

I was pleased to read the article 'Miniature Automatic Telephone Exchange' by G. F. Goddard in the February issue if only to find out that I am not the only reader of *Wireless World* who has his own telephone exchange at home. I was surprised that his did not contain more electronics, although I must confess that mine, now about 12 years old, has none. There are many points of similarity between the two systems. U1, U2 and relays RLC, D, E and J all have their counterparts. Perhaps the comments below may be of use to readers.

Relays

Post Office 3000 relays with slugs are not so common as those without, so other methods of slugging relays could be useful. For instance, for RLB one could use a freewheel diode across the coil (connect the anode to the negative side of the coil). For RLE try using a $1k\Omega$ coil shunted by a 820Ω 3W resistor (this is used in my system). Relays RLD, F, G and H can be slugged with either a freewheel diode or, if longer delays are required, an electrolytic capacitor (with a 470Ω series current-limiting resistor) across the coil. The slug on RLJ is, I believe, to stop the relay chattering to the 50Hz ring current. In this case a freewheel diode would not work. Some possibilities are: an electrolytic straight across the B coil (include some current-limiting resistance in the lead from RLJ/1); use a frequency much higher than 50Hz for the calling signal (see below) so that slugging is unnecessary; take a leaf out of the G.P.O.'s book and provide the slugging action by using a contact of RLJ to short circuit the holding (B) coil until it operated (Figs 1(a) and (b) illustrate possible methods using this idea). In Fig. 1(a) the 47Ω resistor saves damage occurring if RLJ/1 should make before RLJ/4 breaks. In Fig. 1(b) an extra contact is saved.

Of course, relays RLF, G and H would ideally be replaced by one relay and a transistor multivibrator.

Normally in an exchange, the dial pulses are received by a fairly standard 3000 type relay. However, exchanges also have two relays associated with each line, a 'line' relay to detect when the hand-set is lifted to make a call, and a 'cut off' relay to disconnect the line relay once the

equivalent of U1 has found the calling line. Thus the calling line is then connected directly to the 'impulsing' relay with nothing in shunt. Mr. Goddard's circuit saves the use of the 'line' and 'cut off' relays but at the expense of having $5.6k\Omega$ in shunt with the impulsing relay. This could slug a 3000 type relay so that it would not respond correctly to the dial pulses. This effect is negligible with a high speed relay because of its much smaller inductance. However, double pole high speed relays are not as common as single pole types. A possible alternative is to use a P.O. type 23 (this is a modern miniature plug-in relay about 25mm high with a transparent

cover), or one of its commercial equivalents. Typically one with a coil resistance of $2.5k\Omega$ has an inductance of around 24H when operated. If this were used, when the dial contacts broke during an impulse, the relay current would decay with a time constant of about 3ms. Since the release current is around 30% of the normal current, the release will be delayed by a similar time giving a total release time of the order of 14ms, i.e. about the same as an un-slugged 3000 type. (A dial returning at normal speed gives 10 impulses per sec. with a 66% break ratio, i.e. each pulse is 66ms break, 34ms make.) For RLC's other function, that of stopping U1, there should be no problems.

Ringing

To provide a better sound when operating the bells on 50Hz I would advise the following adjustments. Slacken the screw holding the central magnet and adjust so that the armature is just touching one pole piece and there is an 0.008in gap at the other. Set the clapper so that when it is moved slowly from side-to-side it just fails to reach the bell gongs.

High frequency ring current

Some years before the G.P.O. brought out their 'Trimphone' some of the telephones on my exchange were smaller than a 'Trimphone', and emitted a squawking noise to signal a call. How? By scrapping the bell and feeding a high-frequency ring current (produced by a buzzing high speed relay) to the earphone of the handset, via a $0.1\mu F$ capacitor connected across the cradle switch. The relay produces a 600Hz sawtooth waveform of 40V peak-to-peak (a square wave from a multivibrator would probably be just as effective and certainly more reliable). In my exchange the ring tone is produced, from the ring current, by bridging a small capacitor across the equivalent of the break section of contact RLH/3. The circuit of G.P.O. telephones includes a transformer with three windings (some non-G.P.O. telephones of similar external appearance do not) and some other components which match the microphone and earphone to the line. These components form a semi-balanced bridge circuit which prevents the speaker hearing

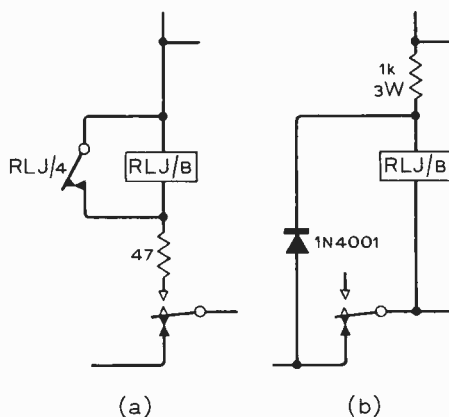


Fig. 1. Alternative ways of slugging relay RLJ/B

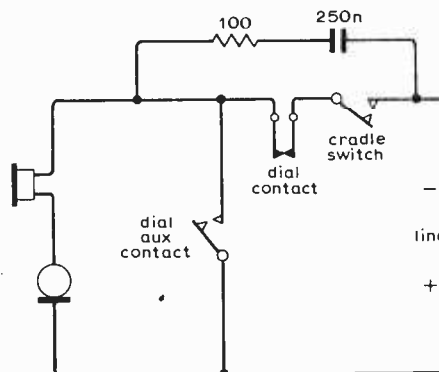


Fig. 2. Ringing circuit used by the writer which does away with the bell. The calling note is produced by the earpiece.

himself too loudly. These complications improve efficiency, but are not essential if all the lines are short in length; thus, for my telephones, I used the circuit in Fig 2. The 100nF capacitor has been increased to 250nF and forms part of a spark quench circuit for the dial as well. It is supposed to be bad to put d.c. through the

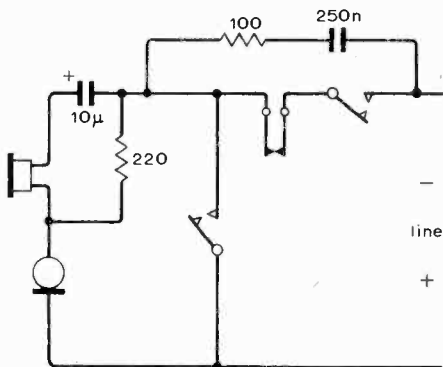


Fig. 3. Similar to Fig. 2 but for use with modern balanced armature earpieces.

earpiece. I have had no trouble with moving-iron type earpieces, but for the modern balanced armature types, it could cause the armature to be driven up against one pole. For these types, therefore, I would suggest a circuit like Fig. 3. The electrolytic need be only a few volts working but watch the line polarity. The auxiliary dial contact short circuits the dial during pulsing, to avoid unpleasant clicks in the earpiece. There are actually two sets of auxiliary contacts; one set is permanently connected to the pulsing contacts and the other, being spare, is bent clear and used as the cradle switch contact.

Power supply

Although there is something to be said for switching a series resistor into the main supply, since otherwise, on no load, the reservoir capacitor will charge up to the peak transformer voltage, I am not sure that the use of an auxiliary battery supply is worth while. If the mains supply is left 'on' permanently the extra power consumed in the idle condition is small, while turning it 'off' does not really increase the safety, since at any time a telephone can be lifted turning it 'on' again. Talking of safety, though, it would be advisable to adopt the recommendations given in Mr N. Monk's letter in this issue. I would also advise connecting a 0.25A thermal cutout in place of, or in series with, FS2. This will protect the uniselector coils from overheating if any fault should cause them to be permanently energized (when their current will rise to 0.75A as opposed to an average of 125mA when stepping).

Finally there is a couple of mistakes on the original circuit diagram. RLJ/3 should be a normally closed contact, and the zener diode, D_s, should be reversed.

April Meetings

Tickets are required for some meetings: readers are advised, therefore, to communicate with the society concerned

LONDON

6th. IERE — "Visual telecommunication systems: a review of some technical problems" by I. Macdiarmid at 18.00 at the Engineering Lecture Theatre, University College, Torrington Pl., W.C.1.

10th. IEE — "B.B.C.'s television management information systems" by C. Lashmar and G. D. Cook at 17.30 at Savoy Pl., W.C.2.

11th. IEE — Discussion on "Magnetic bubbles" at 17.30 at Savoy Pl., W.C.2.

11th. IEE Grads — "Minicomputers and automation" by J. Woodcock at 18.30 at Savoy Pl., W.C.2.

11th. AES — "The control of acoustic feedback by room equalization — some recent investigations" by J. H. Kogen at 19.15 at the Mechanical Engineering Dept., Imperial College, Exhibition Rd., S.W.7.

12th. IEE — "Computer programming as an engineering discipline" by Professor C. A. R. Hoare at 17.30 at Savoy Pl., W.C.2.

12th. SERT — "The Philips video cassette recorder" by R. Smith at 19.00 at I.T.A., 70 Brompton Rd., S.W.3.

13th. IEE — Discussion on "The electrical and electronic systems in Concorde" at 18.00 at Savoy Pl., W.C.2.

13th. RTS — Fleming memorial lecture "A television service fit for artists" by Dr. G. B. Townsend at 19.00 at the Royal Institution, Albemarle St., W.1.

17th. IEETE — Panel meeting on "Electronics" at 18.00 at IEE Lecture Theatre, Savoy Pl., W.C.2.

18th. IERE — "Modern dynamic measurement techniques" by J. D. Lamb and P. A. Payne at 18.00 at the Engineering Lecture Theatre, University College London, Torrington Pl., W.C.1.

19th. Inst. Nav. — "Long haul airlines and satellite communications" by J. O. Clark at 17.00 at the Royal Aeronautical Society, 4 Hamilton Pl., W.1.

19th. IERE — "The consequences of innovation on society" by R. Loveridge at 18.00 at the Engineering Lecture Theatre, University College, Torrington Pl., W.C.1.

20th. IEE — Colloquium on "Microwave mixers and mixer diodes" at 14.00 at Savoy Pl., W.C.2.

24th. IEE — Discussion on "Aesthetic aspects of aerial design and siting" at 17.30 at Savoy Pl., W.C.2.

25th. IEE — Colloquium on "Developments in oscilloscopes" at 10.00 at Savoy Pl., W.C.2.

25th. IERE/Inst. Nav. — Colloquium on "Flight deck displays and instrumentation for future civil short-field aircraft" at 10.30 at Mullard House, Torrington Pl., W.C.1.

26th. IEE — Discussion on "Coaxial digital transmission at 120M bits" at 17.30 at Savoy Pl., W.C.2.

27th. IEE — Kelvin lecture on "Crystals" by Prof. F. C. Frank, at 17.30 at Savoy Pl., W.C.2.

BIRMINGHAM

6th. SERT — Colour television forum — demonstrations and lectures by British television manufacturers at 19.30 at The Byng Kendrick Suite, University of Aston, Gosta Green.

20th. IEE Grads — "Electronic organs" by J. D. Ward at 19.30 at the MEB Offices, Summer Lane.

BRISTOL

20th. SERT — "Thorn 8000 colour television receiver" by A. E. Cullum at 19.30 at Cabot House, Bristol Polytechnic, Ashley Down Road.

CAMBRIDGE

6th. SERT — "Pulse code modulation" by C. G. Williams at 19.30 at Cambridge College of Technology, Collier Road.

CARDIFF

25th. IEE Grads — "Communications; tomorrow's world" by T. Rowbotham at 19.00 at U.W.I.S.T.

CARLISLE

12th. IEETE — "Colour television" by A. D. Campion at 19.30 at the Technical College, Victoria Place.

CARMARTHEN

19th. IEETE — "Communication by satellite" by V. C. Meller at 19.30 at the Carmarthen Technical and Agricultural College.

CHELMSFORD

25th. IERE/IEE — "History of the television camera tube" by W. Turk at 18.30 at the Civic Centre.

DUNDEE

18th. IEE Grads — "The planning and development of v.h.f. networks for television" by T. Sykes at 19.30 at Fulton Bldg., Dundee University.

EVESHAM

18th. IEE Grads — "From cylinder to stereo" by G. Garside at 19.30 at BBC Club.

IPSWICH

19th. IEE — "Electronics in medicine" by M. F. Docker at 18.30 at Civic College.

LIVERPOOL

26th. IERE — "The engineer doctor relationship" by H. S. Wolff at 19.00 at the Department of Electrical Engineering and Electronics, the University.

LYNEHAM

11th. IEETE — "Micro-electronics" at 19.30 at Royal Air Force Station.

MALVERN

13th. IERE — "Development of television relay stations" by B. C. Taylor at 19.00 at The Abbey Hotel.

MANCHESTER

20th. IERE — "U.H.F. mobile radio telephones" by W. H. Wheel at 18.15 at Renold Building, U.M.I.S.T.

20th. SERT — "Disc recording" at 19.30 at Renold Building, U.M.I.S.T.

NEWCASTLE-UPON-TYNE

5th. IEE — "Satellite television broadcast reception" by K. G. Freeman at 18.30 at the Polytechnic.

12th. IERE — "Recent developments in colour television cameras" by K. G. Johnson at 18.00 at Ellison Building, Polytechnic, Ellison Pl.

READING

12th. IERE — "Thick film hybrid circuits" by G. Brooke and W. E. B. Baldwin at 19.30 at the J. J. Thomson Laboratory, University of Reading, Whiteknights Park.

SWANSEA

13th. IERE/IEE — "Measurement of oceanographic variables" by Dr. W. R. Parker at 18.15 at the Department of Applied Science, University College.

WOLVERHAMPTON

12th. IERE — "An outline of loudspeaker design" by R. H. Fisher at 19.15 at the Polytechnic.

26th. IERE — "The Industrial Relations Act and the chartered engineer" at 19.15 at the Polytechnic.

New Products

Polycarbonate capacitors

Housed in flame-proof nylon cases, type CSK polycarbonate capacitors from Seatronics (UK) are designed for high density packaging on printed-circuit boards. Capacitance range is 0.01 to 10 μ F with $\pm 10\%$ and $\pm 5\%$ tolerance over the working voltage range of 63 to 400V d.c. Tan delta is less than 0.003 at 1kHz and the capacitors will withstand a 50% increase in the working voltage for 30 seconds. The normal operating temperature range is -55° to $+85^\circ$ C. Seatronics (UK) Ltd, 22-25 Finsbury Square, London EC2A 1DT.

WW305 for further details

250MHz timer/counter

A resolution of 1Hz is achievable at maximum frequency on the nine-digit timer/counter by Advance Electronics. Known as the TC14/15, it uses Motorola MECL3 emitter-coupled logic. Input sensitivity is 10mV at an input impedance of 1m Ω in parallel with 18pF, reducing to 12pF for a sensitivity of 100 or 500mV. The full track version, TC15, will accept plug-in units, one extending the range to 500MHz with a new Plessey i.c. divider and especially useful in mobile communications. (This unit has an input impedance of 50 Ω .) A fast warm-up 10MHz crystal oscillator

gives a stability of ± 1 in 10^7 from 0 to 50 $^\circ$ C, and an alternate oscillator is available with a stability of ± 5 in 10^8 (after 45 min warm up). Accurate triggering is claimed with 'difficult' waveforms. Trigger level is continuously variable over a range ± 10 times the sensitivity. Advance Electronics Ltd, Raynham Road, Bishop's Stortford, Herts.

WW331 for further details

Analogue multimeter


A linear resistance measurement scale and overload protection permitting a.c. mains voltage to be applied to any input range, or any combination of inputs without damaging the instrument, are features of the Philips PM 2404 analogue multimeter introduced in the U.K. by Pye Unicam. The instrument covers both a.c. and d.c. voltages from 100mV to 1000V f.s.d., with an input impedance of 10M Ω , in nine ranges with a 1:3:10 switching sequence plus currents of from 1mA to 10A f.s.d. in a similar range switching sequence. On resistance measurements a constant current circuit is employed to obtain the linear resistance ranges. With both current and voltage parameters, polarity is indicated automatically by a small moving-coil meter built into the main unit. The overload protection facility permits a.c. or d.c. voltages up to 250V to be connected

to its inputs on any range setting without damage. Overload on resistance or voltage measurements results in full scale deflection of the meter. If it happens on current measurements, then the shunt circuit is protected by a voltage-limiting diode until the fuse blows. Although normally available as a mains operated unit, the PM 2404 can also be supplied with a rechargeable battery pack. Other accessories for the instrument include a high-voltage probe (up to 30kV), a v.h.f. probe (up to 700MHz), and current range accessories for both a.c. and d.c. Pye Unicam Ltd, York Street, Cambridge.

WW316 for further details

Low-cost sine/square oscillator

Lyons Instruments are producing a new series of low-cost instruments. First in the new 'Interlab' series is the SQ10, a signal source with low sine-wave distortion and fast square-wave rise time together with 50 Ω source impedance and high output amplitude. Frequency range is 10Hz-1MHz, and signal amplitude 10V p-p (3.5V r.m.s. sine) into 250 Ω or greater, 5V p-p into 100 Ω , and 2.5V p-p into 50 Ω . The

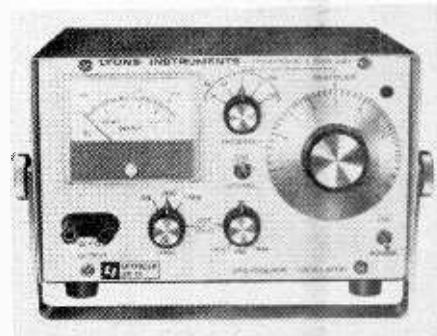


attenuator gives 0-40dB in 20dB steps and vernier. Sine-wave distortion is typically 0.05%, 50Hz-100kHz, less than 0.15% at 10Hz, and 0.5% at 1MHz. Rise time is typically 50ns. Price £57. Lyons Instruments Ltd, Hoddesdon, Herts.

WW318 for further details

Digital voltmeters

A complete range of 12 digital voltmeters, all of the same size, appearance and panel layout but with different specifications and prices, has been introduced by Solartron. Called the Master Series, they do not offer any advance on present-day specifications but, rather, a wide range of user options within the same basic package. Between the 12 models the measurement options available are d.c. voltage (0-10mV to 1.2kV); a.c. voltage mean sensing (0-100mV to 0-1.2kV); a.c. voltage r.m.s. (0-1V to 0-1.2kV); d.c. ratio; 2/4 terminal resistance; normal speed (10/s) or high speed operation (100/s); isolated outputs and programming; and mains locked integration. Maximum voltage sensitivities are either 1 μ V (ten models) or 10 μ V, and

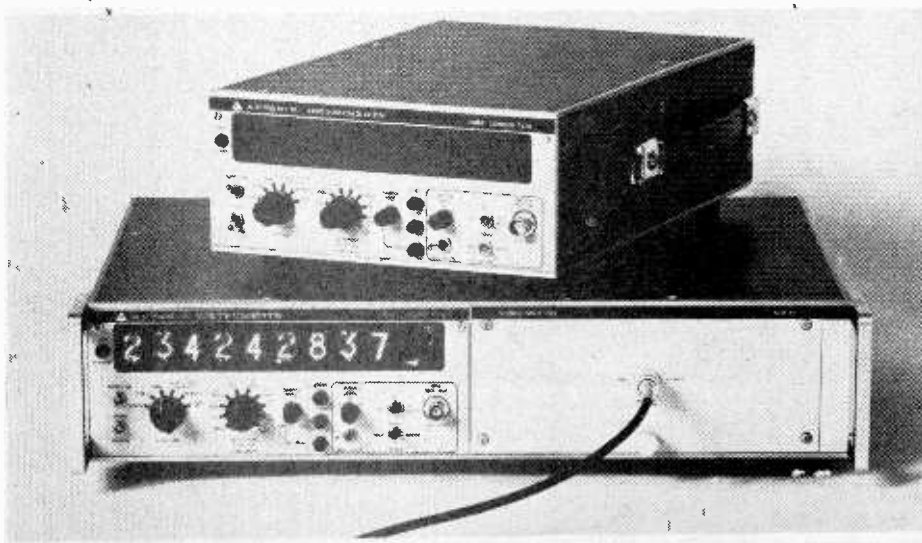

maximum current sensitivity 100pA. Eight models have 6-digit and four models 5-digit displays. Protection against wrong range selection is included, and all inputs are floating. Auxiliary modules available are for a.c. and d.c. current measurement; off-limit detection; pre-selected programming of measurements; linearization, a.c./a.c. ratio, Ω/Ω ratio; and output encoding for paper tape punches, teleprinters etc. Prices for ten models range from £495 to £1,190 with those for two models to be announced. The Solartron Electronic Group Ltd, Farnborough, Hants.

WW333 for further details

Digital multimeter

Digitest 501 from Dynamco is a small, general-purpose multimeter employing a simple grid selection of function and range. It measures from 100 μ V to 1kV d.c., 100 μ V



to 420V a.c., 100m Ω to 1.5M Ω , and 100nA to 1.5A (with shunt option) a.c. and d.c. It has a scale accuracy of 0.3% to 1.5% according to the function selected. Price £89. Dynamco, The Street, Shalford, Guildford, Surrey.

WW308 for further details


Audio modules

A range of printed-circuit plug-in modules intended for use in studios, public address and discotheque sound systems is made by Chadacre Electronics. The range includes a tone control/equalizer, line output amplifier (600 ohm), disc input and microphone pre-amplifiers, VU meter driver, mixing amplifier, headphone amplifier, line-up oscillator, ring modulator, v.c.o., envelope shaper, noise generator, 'phasing' circuit and four-channel pan pot. As well, there is a compressor module, six-channel mixer, a band-pass filter with variable Q, noise generator and spring reverberation unit. all available in cases, but without power supplies. Most units require a 24V power supply. Chadacre Electronics Ltd, 43 Chadacre Avenue, Clayhall, Ilford, Essex.

WW334 for further details

Wafer switch kits

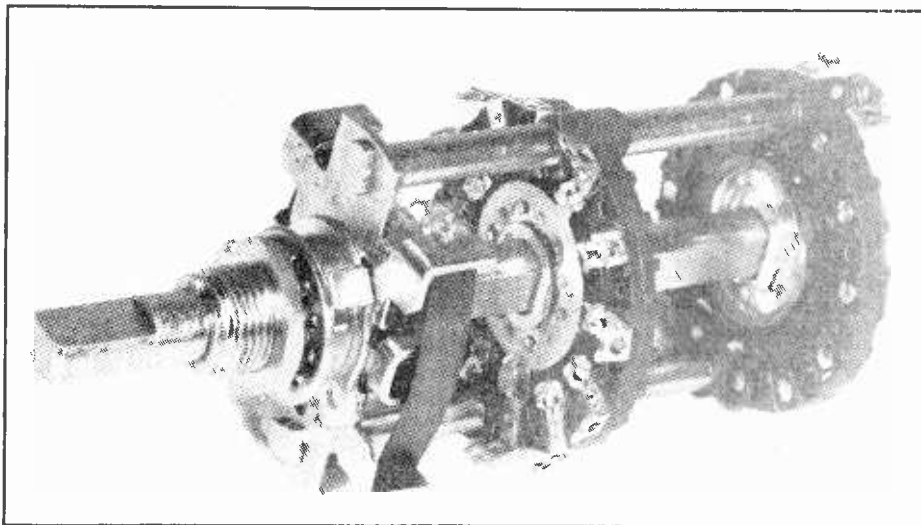The N.S.F. model MK rotary wafer switch is now available from Celdis in kit form. The switches have 1½in diameter moulded wafers with up to 12 switching positions



with one, two or four poles per wafer. Contact rating is 5A continuous at 300V a.c./d.c. Switching capability is 60mA at 250V d.c., 150mA at 250V a.c. (r.m.s.). Shaft assemblies have a standard index mechanism with an operating torque of 25oz. in and are available in 1, 2 and 3in lengths. Celdis Ltd, 37/39 Loverock Road, Reading, Berks. RG3 1ED.

WW322 for further details


High-voltage pulse generator

A kilovolt pulse generator providing pulse widths between 3 and 100ns with rise and fall times of 1ns has been announced by Instrument Technology. The amplitude of the pulses is continuously variable between 1kV and 9kV, and a pulse repetition rate of up to 100Hz is possible. The unit has a delay trigger circuit giving 20ns delay with 1ns jitter. Switch selection of either signal shot (push button) or repetitive shot is provided, with the repetitive application requiring a 5V positive external trigger. Instrument Technology Ltd, 67 Lower Road, Kenley, Surrey.

WW309 for further details

Null balance voltage calibrator

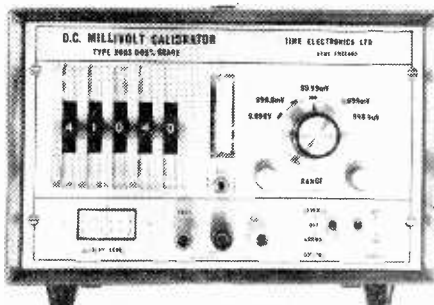A portable battery-powered d.c. voltage calibrator which incorporates a null balance indicator, is available from Time Electronics. Sensitivity is better than 2 μ V per division allowing voltages down to 1mV to be measured to better than 0.1% accuracy




with the convenience of direct digital readout. The basic accuracy of the instrument is $\pm 0.05\%$ of reading with the option of a $\pm 0.02\%$ version. Voltages from 1 μ V to 10V can be measured on five ranges. The circuit uses a Muirhead standard cell as the basic reference source. A chopper stabilized amplifier provides voltage accuracy better than 25p.p.m./ $^{\circ}$ C and 100p.p.m. per annum. When used for calibration purposes the instrument can supply up to 25mA without loss of accuracy. Time Electronics Ltd, Elliott Road, Bromley, Kent BR2 9PA.

WW303 for further details

Push-button tuner

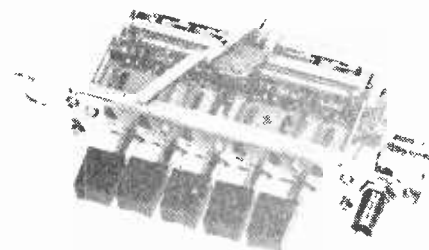Sydney S. Bird & Sons have introduced a new push-button tuner for car radio receivers with the special advantage of enabling manufacturers to design sets down to 42mm high while still being suitable for receivers up to 51mm high and with U.K. and Continental spindle centres, of



130mm and 138mm. The AW160 series tuner can be supplied with 2, 3, 4, 5 or 6 coils giving a.m. and f.m. operations, and the five buttons may be sequenced in any combination of medium-wave, long-wave, or f.m. Sydney S. Bird & Sons Ltd, Cyldon Works, Fleets Lane, Poole, Dorset.

WW319 for further details

Microwave IMPATT diodes

New diodes from Hewlett-Packard are claimed to be the first silicon IMPATTs to achieve microwave power levels higher than 1W.

Characteristics

	5082-0424	5082-0425	5082-0426	
Frequency range	5.3-8	8-10	10-13.5	GHz
C.W. output power (minimum)	1.5	1.25	1.0	W
Maximum junction temp. rise at rated power	175	175	175	°C
Operating voltage (typical)	125	100	80	V
Operating current (typical)	220	210	200	mA
Efficiency (typical)	6.5	7.0	7.0	%
Thermal resistance (typical)	5.0	7.0	9.0	°C/W
Junction capacitance at breakdown (typical)	1.7	1.4	1.5	pF


The larger junction area needed is achieved by paralleling four diodes on a single chip. Hewlett-Packard Ltd, 224 Bath Road, Slough Bucks. SL1 4DS.
WW321 for further details

Low-noise professional tape

A matt-backed a.f. tape for professional use and with the high-performance properties of untreated tape has been developed and introduced by EMI. The tape (type 816) is claimed to be superior to other matt-backed tapes in terms of both modulation noise and print through. (The advantage of matt-backed tapes is the higher 'spooling' speed and uniform wind.) A recently developed method of measuring modulation noise, which gives better agreement between noise and its subjective effect, is used in assessing the new tape. Ratio of 1-kHz maximum replay level to a.m. noise is -38.5dB, to d.c. noise is -49dB and to bias noise is -74dB (6.55mm track width, 38cm/s). The tape is available in the four standard widths and is intended for operation at 38 or 19cm/s. EMI Tape Ltd, Hayes, Middx.
WW301 for further details

Fault locator for long cables

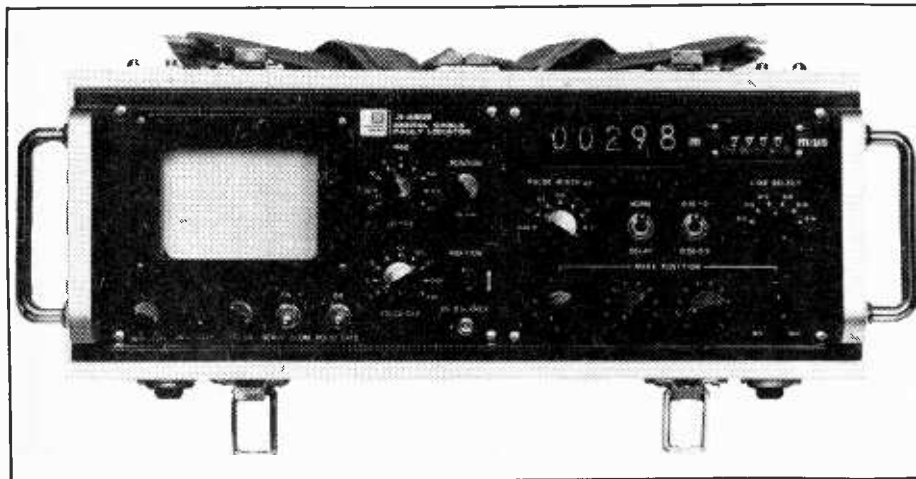
The Takeda TR-4902 digital cable-fault locator from Euro Electronic Instruments, gives a direct reading of fault position or cable length for submarine, underground, communications, or aerial cables. Using an electronic counter to measure the interval



between transmitted and reflected pulses, which are displayed on a built-in monitor oscilloscope, the system achieves an accuracy of 0.1%, with a resolution of 1 metre over its distance measuring range of 20 to 19,999 metres. Front panel controls are provided for setting the propagation constant of the cable under test and for varying the pulse width when required. The distance to the fault or to the end of the cable is given in metres as a direct-reading 5-digit display. Euro Electronic Instruments Ltd, Shirley House, 27 Camden Road, London N.W.1.
WW306 for further details

TV camera for low light levels

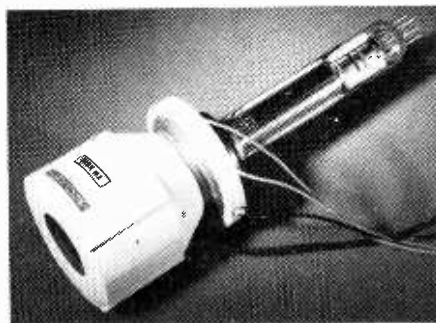The Esicon (TX538), a sensitive pick-up tube from Thomson-CSF, uses 1in vidicon-type hardware. The principle of operation is that within an image section electrons emitted by the photocathode are accel-



ated, focused, and then strike one side of an electron multiplier target, where they are then multiplied while penetrating the target material. On the readout side, the 'charge

pattern' is analyzed by means of a low velocity vidicon-type electron beam. The purely dielectric nature of the target permits long lasting charge accumulation: faint images can be extracted out of the photon noise and enhanced through integration. Lag is very low, allowing non-smear pictures with fast moving objects. As the Esicon photocathode is deposited on a fibre optic faceplate, an image intensifier stage can easily be coupled in front of the pick-up tube. As such the Super-Esicon (TX540) is capable of live pick-up for example in the low light level conditions of an overcast, moonless night (10^{-4} to 10^{-5} lux). If an appropriate scintillator crystal is attached in front of the photocathode of the Esicon (or of the image intensifier stage) the device becomes sensitive to X, gamma or neutron radiation. Thomson-CSF Electronic Tubes Ltd, Bilton House, Uxbridge Road, Ealing, London W5 2TT.

WW327 for further details

Mains input filters

Waycom Semiconductors are marketing the Schaffner FN series of encapsulated mains input filters handling up to 15A. The series provides high attenuation of frequencies up to 300MHz, and units are available in either plastic or metal cases. Waycom Semiconductors Ltd, Wokingham Road, Bracknell, Berks.

WW326 for further details

High-current silicon transistors

Two TO3 encapsulated transistors, types 2N3771 and 2N3772, with a maximum dissipation rating of 150W and a current rating of 30A are available from Mullard. Both are n-p-n devices. Characteristics:


	2N3771	2N3772	
Max. V_{CBO}	50	100	V
Max. V_{CEO}	40	60	V
Max. I_{CM}	30	30	A
Max. dissipation, P_{tot}	150	150	W
Max. junction temperature	200	200	°C
h_{FE}			
$V_{CE}=4V,$ $I_C=10A$	—	15 to 60	
$V_{CE}=4V,$ $I_C=15A$	15 to 60	—	

Mullard Ltd, Mullard House, Torrington Place, London WC1E 7HD.
WW310 for further details

Logic-card range

A new type of logic card has been introduced by Viking Industries (UK) to accept 14- and 16-pin i.c. sockets and wire-wrap posts for discrete components in any

Continued on p. 199

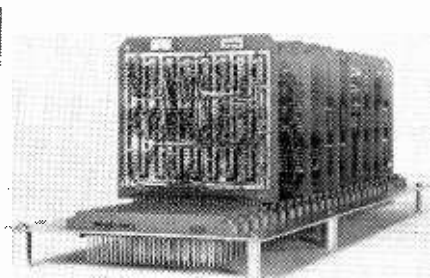


combination. Two card sizes are available (4.5×4.5 in and 9.25×4.5 in) giving an almost unlimited number of configurations. Both sizes have 35-way double-sided gold-plated contacts for standard p.c. connectors. Cards with pins already inserted to customer requirements can be supplied. Viking Industries (UK) Ltd, Barton Industrial Estate, Faldo Road, Barton-le-Clay, Beds.

WW311 for further details

Insulating washers

Insulating washers for semiconductors in TO-3, TO-66 (2 and 9pin), SO-55, DO-4, DO-5 and 'thermatab' packages are now available from Jermyn. Manufactured from I.C.I. 'Melinex' polyester film the washers

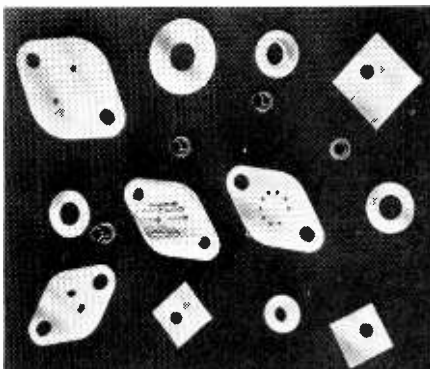

are 0.002in thick, tough, and flexible. The thermal performance is good.— for the TO-3 washer it is typically 0.8°C/W including the two interfaces. Jermyn Industries, Vestry Estate, Sevenoaks, Kent.

WW315 for further details

Low cost diacs


Hutson Industries type D-30 diac, from Claude Lyons, is suitable for use as a trigger for triacs and s.c.r.s. The breakover voltage is $32\text{V} \pm 4\text{V}$, and breakover symmetry $\pm 3\text{V}$. The diode is DO-7 encapsulated. Prices start at 22p for 1-24. Claude Lyons Ltd, Hoddesdon, Herts.

WW320 for further details

40MHz oscilloscope

A dual-beam, 40MHz oscilloscope made by Advance Electronics has a deflection factor of 5mV/cm at full bandwidth. The solid-state oscilloscope, type OS3000, has an alternate deflection factor of 1mV/cm

up to 10MHz. A dual timebase with calibrated delay gives a choice of timebase A only, A bright-up by B, B delayed by A, or A and B mixed, this last a feature new to oscilloscopes of the same cost. (Ranges extend from 2s/cm to 200ns/cm , and down to 20ns/cm with 8×10 expansion.) It is designed for easy customer repair — the timebase, power supply and e.h.t. units for instance are easily removed and extension leads allow oscilloscope operation with the units removed. A useful feature is

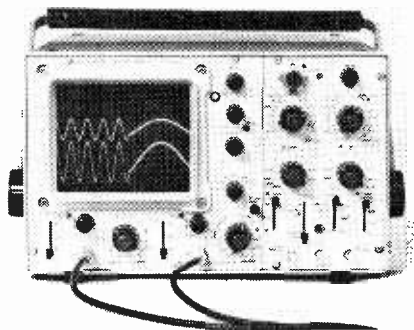

a Y-amplifier output which permits cascade operation of the two Y-amplifiers to give a deflection factor of $200\mu\text{V/cm}$. The Y-amplifier output can also of course be used to feed the X-input. Rise time of the Y amplifiers is less than 9ns. Overshoot is constant with varying attenuation. Display area is $10 \times 8\text{cm}$. Price £360. Advance Electronics Ltd, Raynham Road, Bishop's Stortford, Herts.

WW329 for further details

D.C. millivoltmeter

A wide-range millivoltmeter from Noronix, type NVM 1, has 11 voltage ranges from 100V full-scale down to a maximum sensitivity of 1mV full-scale, giving $10\mu\text{V}$ resolution. Input resistance is $1\text{M}\Omega/\text{V}$. For transducer applications a full-scale reading may be obtained with a signal anywhere in the range $300\mu\text{V}$ to 100V. The case is nylon-coated steel with recessed plastic-fronted meter. The meter will with-



stand high electrical overloads. The battery power supply is stabilized, and the 'sampling-chopper' d.c. amplifier gives good rejection of interfering a.c. signals. Price £36. Noronix Ltd, Love Lane, Woolwich, London SE18 6HL.

WW328 for further details

Electrolytic capacitors

Single or multiple section electrolytic capacitors, type 35D from Sprague, are available in the range 6.3-450V. The largest capacitance available for standard units is $2 \times 23,500\mu\text{F}$ at 6.3V d.c. The capacitors can be operated over a temperature range of -40 to $+85^\circ\text{C}$, and can tolerate high ripple current. A pressure-type safety vent is standard. Sprague Electric (UK) Ltd, 159 High Street, Yiewsley, West Drayton, Middx.

WW323 for further details

Miniature light-emitters

Light-emitting diodes types 183CQY and 185CQY from Mullard, are miniature gallium arsenide phosphide devices that emit bright red light through a wide angle. The 183CQY is intended to replace conventional indicator lamps in systems that use solidstate circuits. It operates with a power supply of 2V at 20mA to produce a radiation with an intensity of 170cd/m^2 , and has an impedance of about 100Ω . The 185CQY can display the numbers 0 to 9 and the decimal point. It operates with a power supply of 2V at 5mA and emits radiation with an intensity of 684cd/m^2 . The numbers, which measure only $2 \times 3\text{mm}$, are formed as a standard 7-segment display. Mullard Ltd, Mullard House, Torrington Place, London WC1E 7HD.

WW314 for further details

High-voltage pulse transformer

A 30kV pulse transformer model 355-30, manufactured by Hartley Measurements, is designed to trigger spark gaps, flash tubes, etc. It can be operated by a low-cost thyristor circuit or, for high-speed applications by a thyratron. It measures $96 \times 25 \times 25\text{mm}$ approx. and is suitable for printed-circuit board mounting. Output is 30kV for a 300V input pulse; rise time less than $1\mu\text{s}$. Hartley Measurements Ltd, Kent House, High Street, Hartley Wintney, Hants.

WW307 for further details

High-resolution digital voltmeter

Model 701 digital voltmeter from Fenlow has a resolution of 1 part in 20,000, sensitivity of $10\mu\text{V}$, input resistance of $20,000\text{M}\Omega$ and accuracy of 0.01%. A new




conversion technique employed avoids switching at low levels. Series mode rejection is 80dB. The instrument measures $210 \times 75 \times 140\text{mm}$ approx. Price £198. Fenlow Electronics Ltd, Whittet's Eyot, Jessamy Road, Weybridge, Surrey. **WW313 for further details**

Low-power audio amplifier i.c.

An integrated circuit audio amplifier, type TBA915, from Mullard, is intended for use in portable receivers and miniature transmitter-receivers where small battery size is important. Under typical operating conditions, the circuit normally takes a current of 2.5mA when quiescent, but a squelch facility can reduce this to $400\mu\text{A}$. Output is up to 500mW. The high-frequency response of the TBA915 can be adjusted by means of capacitance in the feedback path. An input of 10mV will produce full output; signal-to-noise ratio at this power level is 75dB. Encapsulation is TO-74. Mullard Ltd., Mullard House, Torrington Place, London WC1E 7HD. **WW330 for further details**

Quadraphonic pan pot

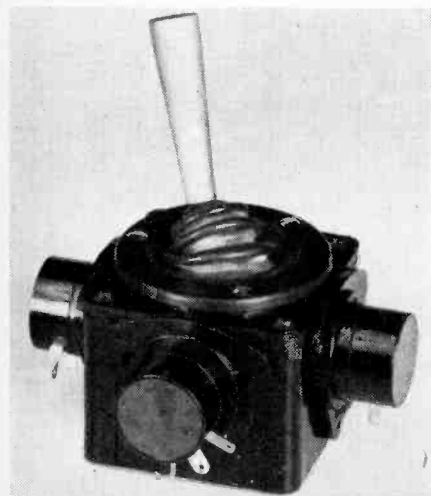
Intended for studio use, the quadraphonic panoramic potentiometer made by Sigma Products claims to be cheaper than its competitors. Movement of a single control knob gives proportional control of four potentiometers. The potentiometers are high-resolution, low-noise wirewound types



with a value of $3.9\text{k}\Omega$ and a linear law (The law can be modified with external resistors.) Unit price is £15.75. Sigma Products Ltd, 72 St. Andrews Road, Northampton. **WW302 for further details**

Bistable relay

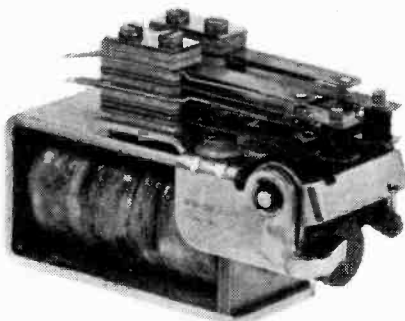Magnetic Devices have announced a bistable relay with coils for d.c. working. With each successive operation the solenoid actuates a cam into either high or low positions. Thus the contacts are operated every alternate time the relay is energized. Contact arrangements are built



up as required from single pole to a maximum of four poles. Provision is made for alternative contacts which can be operated direct from the solenoid if required. Coils can be wound for up to 230V d.c. Magnetic Devices Ltd, Exning Road, Newmarket, Suffolk. **WW312 for further details**

Solid-state microwave signal source

Microwave signal source, type 6070 from Marconi Instruments covers the frequencies 400 to 1200MHz in a single range. It has mechanical/digital readout. The instrument contains an i.c. power supply, square-wave generator and modulator drive circuit assembled on to a single printed-circuit board fitted with an edge connector. Frequency stability is typically 0.001%. A transistor cavity-controlled oscillator gives a minimum power output over the whole frequency band in excess of 50mW with a typical maximum power of 250mW. The r.f. output line incorporates a p-i-n

diode modulator and low-pass filter. External amplitude and modulation can be applied through a front panel B.N.C. socket. Optional accessories include a levelling amplifier and a wideband detector. Marconi Instruments Ltd, St. Albans, Herts.

WW324 for further details

Encapsulated bridge rectifiers

Two silicon single-phase bridge rectifier assemblies from Westinghouse, types SxPF3 and SxPF4, have voltage ratings of $80\text{-}1000\text{V}_{RRM}$. Current ratings are 9A (225A overload) and 13A (300A overload) for the SxPF3 and SxPF4 respectively. Prices are £108 per 100 for the S1PF3 (100V) and £127 per 100 for S1PF4 (100V). Westinghouse Brake and Signal Co. Ltd, 82 York Way, King's Cross, London N1 9AJ.


WW325 for further details

Pulse generator

Model TT100 the first of a new range of pulse generators from K.S.M. Electronics provides a p.r.f. of 1Hz-7MHz, delay of 50ns-1s, pulse width of 50ns-1s, and a positive and negative pulse obtained from separate sockets, each pulse being variable from zero to 10V into 50Ω . The instrument measures $89 \times 140 \times 324\text{mm}$. K.S.M. Electronics Ltd, Bradmore Works, Brookmans Park, Hatfield, Herts. **WW317 for further details**

Versatile multimeter

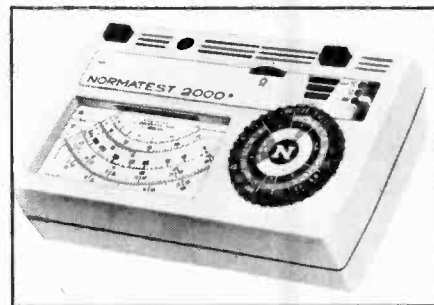The Normatest 2000, made by Norma of Vienna and available in the U.K. from Croydon Precision Instrument Co, has 41 ranges with facilities for the measurement of a.c. and d.c. voltage and current, resistance, temperature and gain. It has an internal resistance of $20,000\Omega/\text{V}$ d.c. and $4,000\Omega/\text{V}$ a.c. The moving-coil system is



a taut-band suspension with a short-term overload capacity of 1,000 to 1 and a built-in fuse to ensure maximum overload protection. The instrument is contained in a plastic case and accessories such as temperature feelers, range multipliers and clip-on transformers are available. Price complete with carrying case and test leads is £17.50. Croydon Precision Instrument Co., Hampton Road, Croydon CR9 2RU. **WW304 for further details**

Literature Received

For further information on any item include the appropriate WW number on the reader reply card

ACTIVE DEVICES

The 1972 catalogue from Chromasonic Electronics, 56 Fortis Green Road, London N10 3HN, gives prices and specifications of all their components (active and passive)WW401

A data sheet is available on the MM1101, 11011, MM1101A1 and 1101A2 256-bit fully decoded static random access memory i.c.s and an application note on the use of MM5260. National Semiconductor (U.K.) Ltd, Larkfield Industrial Estate, Greenock, ScotlandWW402

Specifications of a 30A (Io) power thyristor 31RCS. are given in a data sheet from International Rectifier, Hurst Green, Oxted, SurreyWW403

James Millen Manufacturing Co. Inc, 150 Exchange Street, Malden, Massachusetts 02148, have sent us a booklet containing details of their components, grid dip meters, amateur radio equipment, module oscilloscopes, magnetic shields and delay linesWW443

We have a booklet describing Signetics range of linear and operational amplifiers, comparators, phase locked loops and m.o.s. products. Quarndon Electronics Ltd, Slack Lane, DerbyWW444

PASSIVE COMPONENTS

Celdis Ltd, Loverock Road, Reading — distributor for London Electrical Manufacturing Co. Ltd — have produced a wall chart for comparison of dielectricsWW404

A brochure 'Aerials and Accessories' gives technical details of equipment from J. Beam Aerials Ltd, Rothersthorpe Crescent, NorthamptonWW405

A catalogue contains details of the range of quartz crystal filters manufactured by Salford Electrical Instruments Ltd. Peel Works. Eccles. Manchester M30 0HLWW406

Two publications about Cambion Electronic Products Ltd, Cambion Works, Castleton, Nr. Sheffield, S30 2WR are:

Multilanguage Catalogue 102A on terminals, r.f. chokes and connectorsWW407
'Product News'WW408

A data sheet is available covering all switches from Birch-Steele Ltd, Ponswood Industrial Estate, Windmill Road, Hastings, SussexWW411

APPLICATIONS

Technical Publication No. 4 from Waycom Semiconductors Ltd, Wokingham Road, Bracknell, Berks, is called 'Mains Filters for Equipment using Digital Integrated Circuits'WW412

'Detecting Sources of Vibration and Noise using H.P. Fourier Analyzers' is note 140-1 from Hewlett-Packard Ltd, 224 Bath Road, Slough, BucksWW413

EQUIPMENT

A leaflet is available on modular 35MHz oscilloscope 3100. Cossor Electronics Ltd, The Pinnacles, Elizabeth Way, Harlow, EssexWW414

'Abridged catalogue of process instrumentations' is a booklet giving general information on products from Honeywell Ltd, Charles Square, Bracknell, BerkshireWW415

We have received two publications from Foxboro-Yoxall Ltd, Redhill, Surrey.
'Process Control Information: with explanatory notes'WW416
Details of the extended process computer range, FOX2WW417

Data sheets on recent Rhode & Schwarz instruments are available. Aveley Electric Ltd, Arisdale Avenue, South Ockendon, Essex RM15 5SRWW418

Aero Electronics (AEL) Ltd, Gatwick House, Horley, Surrey, have several data sheets describing a range of radio communications equipment, which includes the h.f. s.s.b. transceiver AEL 3015AWW419

Catalogue No. 8172 ('Electronics Catalogue 1972') from Eagle International, Precision Centre, Heather Park Drive, Wembley, Middx, describes their range of audio equipment, electronic components and accessoriesWW420

Digital measuring instruments from Farnell Instruments Ltd, Sandbeck Way, Wetherby, Yorkshire LS22 4DH, are described in Publication T1WW421

We have a leaflet describing a range of audible circuit and voltage testers produced by Coventry Controls Ltd, Godiva House, 49 Allesley Old Road, Coventry CV5 8BUWW422

Specification sheets of the range of Audix products are contained in a booklet. Audio Sound Systems and Electronics, Stansted, EssexWW423

A booklet on sound control consoles gives general facilities and performance specifications. Cadac (London) Ltd, Stansted, EssexWW424

Data sheets on the products of At Yu Electronics cover oscilloscopes, phase meters and power supplies. B. Hepworth & Co. Ltd, P.O. Box 10, Bank Buildings, Kidderminster, Worcs.WW425

Tally Corporation, 8301 South 180th Street, Kent, Washington 98031, have sent us a leaflet describing their on- and off-line print stationWW426

The Soundcraftsmen RP10-12 professional recording/playback equalizer is described in a news sheet. The unit is for tape, disc and p.a. use. Soundcraftsmen: 1310 E. Wakenham Avenue, Santa Ana, California 92705WW427

We have a leaflet describing the Series IT7000 ignition tachometer. The meter is for use with capacitor electronic ignition systems. Dynalco Corporation, 4107 N.E. 6th Avenue, Ft. Lauderdale, Florida 33308WW428

'LI Newsletter' contains product news from Lyons Instruments Ltd, Hoddesdon, HertsWW429

Computer Automation Incorporated Ltd, 95a High Street, Rickmansworth, Herts, have sent us a leaflet on CAPABLE — a minicomputer-based logic circuit testing systemWW430

A news sheet describes model 3720A spectrum display, which provides frequency and time analysis of electrical signals when combined with digital correlator 3721A. Hewlett-Packard Ltd, 224 Bath Road, Slough, Bucks, SL1 4DSWW431

A series of electronic units from Ortofon for disc recording studios includes a cutting head amplifier (GO 701), which can transfer a sine wave power of 500W. The amplifier and its power supply (GE 701) are described in a leaflet. Ortofon A/S, 5 Trommesalen, DK-1614 Copenhagen V, DenmarkWW445

GENERAL INFORMATION

'General Conditions of Contract 1972: Parts I & II' is a revised version applicable from 1st March 1972. Crown Agents (for overseas governments and administrations), CS Department, 4 Millbank, London SW1P 3JDWW433

Portescap (U.K.) Ltd, 204 Elgar Road, Reading, RG2 0DD, have produced the ESCAP 26P series of high-performance d.c. micromotors, which are described in a leafletWW435

We have received details of the new electronic maintenance and calibration service for test and measuring equipment offered by EMI Service, The Installation and Maintenance Division of EMI Electronics Ltd, Blyth Road, Hayes, Middx.WW436

Five publications from the British Standards Institution, 2 Park Street, London W1A 2BS are:

BS9027: 1972 'Rules for the preparation of detail specifications for forward travelling — wave power tubes of assessed quality'Price £1
BS9610:1972 'Quartz crystal units of assessed quality for oscillator applications: Generic data and methods of test'Price £2
BS9000 'General requirements for electronic components of assessed quality Part 2:1972 Data on generic and detail specifications'Price £1.10
BS800 Part 1:1972 'Radio interference limits and measurements. Equipment embodying small motors'Price 90p
BS800 Part 3:1972 'Radio interference limits and measurements. Semiconductor control devices'Price 70p

We have received two leaflets from the British Broadcasting Corporation, Engineering Information Department, Broadcasting House, London W1A 1AA.

'How to receive B.B.C. T.V. 625 lines and colour'
'V.H.F. radio transmitting stations'

Studio 99 Video Ltd, 81 Fairfax Road, Swiss Cottage, London N.W.6, have sent us a new list of video tape prices and 'Fact Sheet No. 2' containing information on new products and using microphones and TV cameras in poor lightWW439

'Multirange' units for use with Interscale educational instruments are described in a leaflet. White Electrical Instrument Co. Ltd, Spring Lane North, Malvern Link, Worcs, WR14 1BLWW440

'Special Metals' is a leaflet (German or English versions), which summarizes available metals and applications. There is also a sheet on rhodium and iridium crucibles for the production of monocrystals. Degussa Public Relations Department, D6000 Frankfurt am Main 1, Postfach 3993WW441

Butterworths, 88 Kingsway, London WC2B 6AB, have produced two leaflets describing books available on radio and televisionWW442

Information on educational literature from Mullard Ltd, New Road, Mitcham, Surrey CR4 4XY is contained in the 'Educational Service Bulletin'WW409

Details and prices of new films (On to Mach-2, Learning Metric, Intrumi, Insight, Momentum of Electrons, Looking at Ourselves) are given in a leaflet from the Central Film Library, Government Building, Bromyard Avenue, Acton, London W3 7JBWW410

Real and Imaginary

by "Vector"

'It will not last the night —'

Burning the candle at both ends, although an expressive metaphor, is something I find difficult to do literally; as a consequence this is being written with the aid of the conventional single-ended guttering flame — at the time of putting pen to paper we are still in the power-cut era.

During the past few years we have had more than a basinful of national strikes; the postmen, the power-station engineers and now the miners have all made their respective points. The two last-mentioned have given those of us who live in all-electric homes, or rely upon electrically-operated fuel pumps, a sharp taste of what it must have been like to winter in the Flintstone era. Come to think about it though, the Flintstones had the edge over us with a crackling wood fire at the cave mouth.

But our shivering won't have been in vain if it has made us reflect upon where our boasted technologies have got us. This is the age of the specialist, in which the individual is quite helpless to provide at first hand the fundamentals of life for his family. More diabolical still, he can't even provide them at second hand unless he has the tacit approval of a handful of key men. In short, neither our own electronics industry nor any other is the discrete watertight compartment which in less troubled times we imagine it to be. We are inextricably linked one to the other, with main arteries feeding us with raw materials. A blockage of one of those sources and the country suffers a thrombosis.

Don't misunderstand me; I'm not knocking the miners. My own personal views about them (for what the thoughts are worth) are governed by the amount of money I would want for risking death by crushing, explosion, fire, gas or silicosis. No, it's the insane principle whereby 56 million people can be hi-jacked by a handful — however just their cause might be — which is the point at issue.

The basic trouble lies in that incredible computer which is the human brain; it's so fearfully adept at devising new technologies but so woefully inept at providing the wisdom with which to apply them properly. While lip-service is paid to easing the lot of the community the prime mover in technological innovation is profit; as a consequence we are exhausting world supplies of raw materials at a lunatic rate, destroying the balance of nature and

spreading pollution over the earth and the waters that cover the face of the earth. The last man on this planet will die alongside a huge pile of gold and diamonds and empty food and water pots.

When I first read Samuel Butler's 'Erewhon', well, frankly, I thought poor old Samuel wasn't in full possession of his marbles. You know the bit I'm referring to — where his hero finds that the Erewhonians had virtually no machinery in their country. At some stage in their history they had realised where the cult of technology was taking them and they had called a halt, relegating the machines to museums where they provided an admonitory lesson to the young. At the time of first reading I thought this concept incredibly stupid; only much later did I realise that the stupidity lay in me.

An old timer's lament

You'll have seen in the March issue (page 113) that broadcasting in this country celebrates its fiftieth anniversary this year. The first station was 2MT, Writtle, and the second, 2LO, London.

The following lines were discovered on the body of an old-time radio engineer who died from an overdose of pop music: —

'I remember, I remember . . .'
(With apologies to Thomas Hood)

I remember, I remember,
The, callsign 2MT
And 'Wr-r-r-rattle calling!' through the night
And P. P. Eckersley.
That half an hour just once a week
Passed all too soon away
So we demanded then to have
A half an hour each day.

I remember, I remember,
The callsign 2LO
One hour per day we now received
We moaned 'That ration's low!' —
Today our punishment fits our crime
By greed we are undone —
We're lumbered now by day and night
With squawking Radio One!

Mention of P. P. Eckersley, who was the first chief engineer of the B.B.C., reminds me that if you're interested in the beginning of things, try and get hold of a copy of his book 'The Power behind the Microphone' published in 1941 (Jonathan Cape) which gives an eminently readable

account of the start of broadcasting in this country. Writing of 2MT Writtle he tells how (after dining at the 'local') he began that irreverent approach to the microphone which was to endear him to his audience. He continues:—

"We signed off with a theme song. I sang it in a high tenor voice to the tune of Tosti's 'Goodbye'"

Dearest, the concert's ended, sad wails the heterodyne,

You must soon switch off your valves, I must soon switch off mine,

Write back and say you heard me, your 'hook-up' and where and how,

Quick! for the engine's failing; goodbye you old low-brow!"

His account in his book of how he applied for his first job is something which every young reader of *W.W.*, keen to make electronics a career, would do well to remember. Eckersley says:—

"My simple dream on leaving Bedales [school] in 1911 was to figure as a leading man of science, a great wireless inventor. . . . It is a thousand pities that everyone, keen as I was, . . . cannot have the advice given me by the genial Mr. Andrew Gray, so many years Chief Engineer of Marconi's Wireless Telegraph Company. When Mr. Gray interviewed me he asked questions about wireless . . . to all of which he got intelligent and correct answers. He then switched to questions on electrical engineering. . . . It soon became clear that I knew little or nothing about electrical engineering. Mr. Gray delivered a little lecture, the gist of which was 'Wireless is only a branch of electrical engineering and electrical engineering is founded upon the principles of electricity and magnetism. First learn about these so that you will readily understand electrical engineering and then take up wireless, when you can rise, if you have ability, to the top of the profession. Otherwise you will be bound to stick somewhere short.'"


*Actually I think the tune was 'Parted'.

Snap, crackle and pop

Most readers have heard of shot noise, flicker noise, current (or i/f) noise and those noises which carry the familiar names of Johnson and Barkhausen, but who has heard of popcorn noise? Not many, I dare say. Nevertheless I came across this description, somewhat unexpectedly, in a Japanese technical journal. It turns out there is no distinguished Japanese researcher called Popcorn, nor is popcorn noise one of the unfortunate side effects of making transistors out of maize, but just a new name for what has previously been called burst or pulse noise — because it occurs as peaks of energy (typically several milliseconds apart) of much greater amplitude than the general noise waveform. I understand that one of the first people to study this type of noise, actually in 1956 in point contact germanium diodes, was Rex G. Pay for his M.Sc. thesis at Birmingham University.

the choice is yours

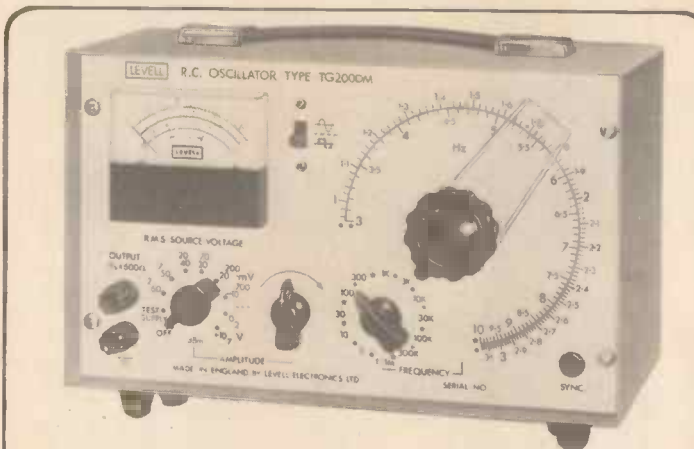ANALOGUE or DIGITAL 1Hz to 1MHz R.C. OSCILLATORS



FREQUENCY 1Hz to 1MHz in 12 ranges. Acc. $\pm 2\%$ $\pm 0.03\text{Hz}$.

SINE OUTPUT 7V r.m.s. down to $<200\mu\text{V}$ with $R_s = 600\Omega$

DISTORTION $<0.1\%$ to 5V, $<0.2\%$ at 7V from 10Hz to 100kHz.

SQUARE OUTPUT 7V peak down to $<200\mu\text{V}$. Rise time $<150\text{nS}$.


SYNC. OUTPUT $>1\text{V}$ r.m.s. sine in phase with output.

SYNC. INPUT $\pm 1\%$ freq. lock range per volt r.m.s. input.

METER SCALES 0/2V, 0/7V & $-14/+6\text{dBm}$. on TG200M & DM only.

SIZE & WEIGHT 7" high x $10\frac{1}{2}$ " wide x $5\frac{1}{2}$ " deep. 10 lbs.

TG200	TG200D	TG200M	TG200DM
£42	£45	£52	£55
Sine O/P	Sine & Sq. O/P.	Sine O/P	Sine & Sq. O/P
		+meter.	+meter.

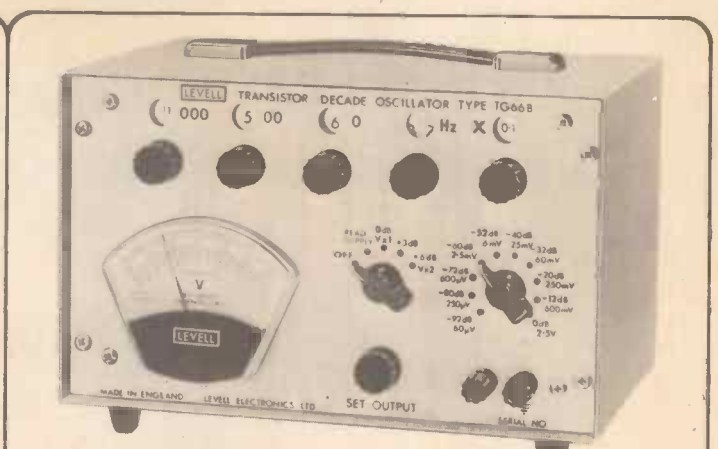

FREQUENCY 0.2Hz to 1.22MHz on four decade controls.

ACCURACY $\pm 0.02\text{Hz}$ below 6Hz, $\pm 0.3\%$ from 6Hz to 100kHz, $\pm 1\%$ from 100 kHz to 300 kHz, $\pm 3\%$ above 300 kHz.

SINE OUTPUT 5V r.m.s. down to $30\mu\text{V}$ with $R_s = 600\Omega$

DISTORTION $<0.15\%$ from 15Hz to 15 kHz.

METER SCALES 2 Expanded voltage & $-2/+4\text{dBm}$.

SIZE & WEIGHT 7" high x $10\frac{1}{2}$ " wide x 7" deep. 12 lbs.

TG66B	TG66A
£120	£150
Batteries only,	Mains unit & batteries incl.

Prices include batteries with 400 hour life.
Mains power units £10 extra. Leather cases £6 extra.



LEVELL
PORTABLE INSTRUMENTS

R.C. OSCILLATORS

Levell Electronics Ltd., Park Road, High Barnet, Herts. Tel: 01-449 5028

Send for literature covering our full range of portable instruments.

WW-003 FOR FURTHER DETAILS



COMMUNICATION
SPEAKER
SP-50

BUILT IN MECHANICAL FILTER 8 TUBES COMMUNICATION RECEIVER 9R-59DS

Shortwave Success Always With TRIO's 9R-59DS

TRIO have the complete communications receiver in the 9R-59DS. A true example of the best in professional test equipment, the intrepid amateur can confidently operate this instrument with a 1.5 watt power output. With 8 vacuum tubes and 7 diodes, the 9R-59DS has a power consumption of 45 watts. Rely on full speaker range with the 9R-59DS with its $2\mu\text{V}$ sensitivity and optimum selectivity of -50dB . The most modern communications refinements are incorporated in every feature. Total reliability.



SSB COMMUNICATIONS RECEIVER JR-310

SPECIFICATIONS:

• Frequency Ranges: Band A 550-1600KHz, B 1.6-4.8MHz, C 4.8-14.5MHz, D 10.5-30MHz • Sensitivity: $2\mu\text{V}$ for 10dB S/N Ratio (at 10MHz) • Selectivity $\pm 5\text{KHz}$ at -50dB • Power Consumption: 45 watts • Audio Power Output: 1.5 watts • Tube & Diode Complement: 6BA6 \times 3, 6BE6 \times 2, 6AQ8 \times 2, 6AQ5, SW-05S \times 2, SW-05 \times 2, IN60 \times 2 • Dimensions: Width 15", Height 7", Depth 10".



TRIO ELECTRONICS, INC. 6-5, 1-chome, Shibuya, Shibuya-ku, Tokyo, Japan
Sole Agent for the U.K. B.H. MORRIS & CO., (RADIO) LTD. 84/88, Nelson Street, Tower Hamlets, London E1. Phone: 01-790 4824

News of the Decade

Capacitance boxes available from
20pf.-140uf. Accuracies up to 0.05%

Inductance

Air space 1mH-1H
Accuracy 5%

Resistance Boxes

from 0.1-10 MΩ
Average accuracy 0.1%

Resistance Elements
suitable for use up
to 1MHz.

High Dissipation Resistance Boxes

Five Decade		
HD1	0 to 1,111,100 ohms by 10 ohm steps 1% Tolerance	£45.00
HD5	0 to 1,111,100 ohms by 10 ohm steps 5% Tolerance	£35.00
HD1/L	0 to 111,110 ohms by 0.1 ohm increments 1% Tolerance	£47.00

Jay-Jay Inductance Boxes

Cat. Ref.		
L1	3 Decade 1 mH to 1 Henry	£37.00
L2	2 Decade 1 mH to 100 mH	£26.00
L3	2 Decade 10 mH to 1 Henry	£29.45

Jay-Jay "Point One" Resistance Boxes

Average Accuracy 0.1%		
Four Decade		
R5	0 to 111,100 ohms by 10 ohm steps	£24.00
R4	0 to 11,110 ohms by 1 ohm steps	£24.50
R3	0 to 1,111 ohms by 1/10 ohm steps	£25.00
Five Decade		
R11	0 to 10 meg ohms by 100 ohm steps	£34.50
R7	0 to 1,111,100 ohms by 10 ohm steps	£29.25
R9	0 to 111,110 ohms by 1 ohm steps	£29.75
R10	0 to 11,111 ohms by 1/10 steps	£30.25
Six Decade		
R20	0 to 1,111,110 by 1 ohm steps	£36.00
R21	0 to 111,111 by 0.1 ohm steps	£36.50
R22	0 to 11,111.1 by 0.01 ohm steps	£37.00

Jay-Jay Junior Decade Resistance Boxes

Average Accuracy 0.4%		
Six Decade		
J60	Range 0 to 1,111,100 ohm by 1 ohm steps	£18.90
Five Decade		
J1	Range 0 to 1,111,100 by 10 ohm steps	£15.60
J2	Range 0 to 111,110 by 1 ohm steps	£15.40
Four Decade		
J3	Range 0 to 111,100 by 10 ohm steps	£12.40
J4	Range 0 to 11,110 by 1 ohm steps	£12.20
Three Decade		
J5	Range 0 to 11,100 by 10 ohm steps	£9.95
J6	Range 0 to 1,110 by 1 ohm steps	£9.90

Jay-Jay Capacitance Boxes

Cat. Ref.			
Three Decade Model			
C3	100 pf. to 0.111 mfd.	1% Tolerance	£22.00
PC3	100 pf. to 0.111 mfd.	½% Tolerance	£31.50
Four Decade Model			
C4	100 pf. to 1.111 mfd.	1% Tolerance	£35.00
PC4	100 pf. to 1.111 mfd.	½% Tolerance	£48.00
Switched Capacitance Boxes			
C100	1 mfd. to 100 mfd.	5% Tolerance	£65.00
C140	1 mfd. to 140 mfd.	5% Tolerance	£75.00
C60	0.1 mfd. to 61 mfd.	5% Tolerance	£59.00
C60P	0.1 mfd. to 61 mfd.	1% Tolerance	£110.00
Air Spaced Capacitors			
VC1	10 to 160 pf.	1% Tolerance	£12.00
Variable Capacitors			
VC2	20 to 1130 pf.	1% Tolerance	£22.00
VC4	50 pf. to 0.1114 mfd.	1% Tolerance	£28.75
VC5	50 pf. to 1.1114 mfd.	1% Tolerance	£43.00
Precision Air Spaced Capacitors			
PVC1	5 to 200 pf.	½% Tolerance	£36.00
PVC2	Precision Variable Capacitor 15 to 100 pf.	½% Tolerance	£44.00
PVC4	Precision Incremental Capacity ±0.5 pf. and ±5 pf.	1% Tolerance	£36.00
SVC5	Precision Variable Capacitor 50 pf. to 1.1114 mfd. ±0.05% tolerance—major decade		£230.00

Jay-Jay Junior Decade Capacitance Boxes


Cat. Ref.	Accuracy 1%	
JC1	3 Decade 100 pf. to 0.111 mfd.	£12.90
JC2	3 Decade 30 pf. to 10,140 pf.	£13.70




Most ranges available from stock.
Write for descriptive leaflet or demonstration.

J.J. Lloyd
Instruments Limited
Brook Avenue, Warsash, Southampton SO3 6HP.
Tel: Locks Heath 4221

WW-005 FOR FURTHER DETAILS

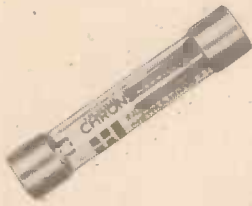

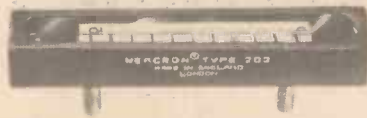Do you use equipment requiring
MAINTENANCE SCHEDULES
MAINTENANCE REPLACEMENTS
GUARANTEE RECORDS



Do you know the cost per running hour for
DEPRECIATION



How do you record these vital running times?
 By the old fashioned pen and paper method?

SURELY NOT!



Get up to date with the modern
 electro-chemical elapsed time indicator
 method using

MERCRON

or

CHRONSISTOR

SMALL, LIGHT AND INEXPENSIVE

Manufactured by:—



**INDUSTRIAL
 INSTRUMENTS
 LIMITED**

TRANSIPACK®

Laboratories and sales:
 STANLEY ROAD, BROMLEY, KENT, ENGLAND.
 Postal Code: BR2 9JF.
 Telephone: 01-460 9212/3
 01-464 5812

Telegraphic address:
 TRANSIPACK BROMLEY.
 Telex No. 896071 (TRANSIPACK LDN.).

Factory:
 THEAKLEN DRIVE, PONSWOOD INDUSTRIAL
 ESTATE, HASTINGS, SUSSEX, ENGLAND.
 Telephone: Hastings 7344/6/8.



3009 + 150

We receive many enquiries about the use of our precision pick-up arms with the Thorens TD 150 turntable.

The SME Model 2000 Plinth System includes pre-cut pick-up mounting boards and motor boards which make this a simple matter.

Alternatively, existing items can usually be adapted.


Full details are given in information sheet No. 7, a copy of which we will send you on request.

SME

The best pick-up arm in the world

SME Limited · Steyning · Sussex · England
Telephone Steyning (0903) 814321

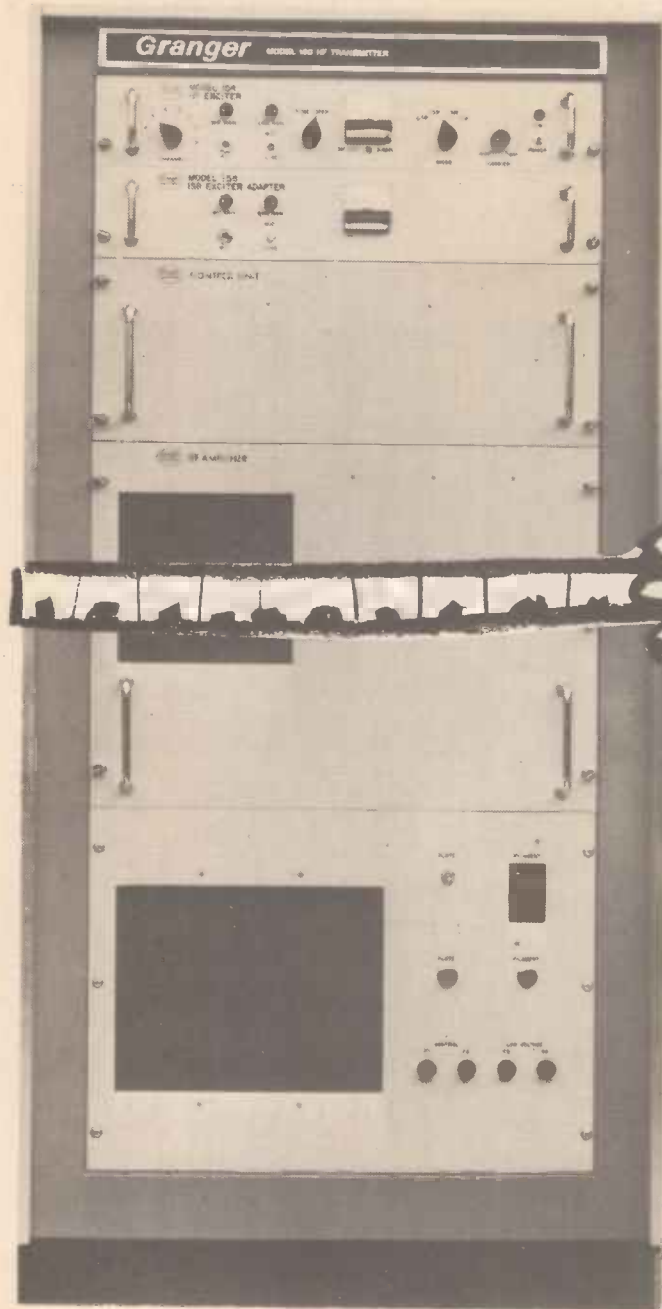SSB Transmitters tailor-made to suit your needs.



A range of modern HF SSB transmitters
with manual or automatic control
and various frequency band options.
Full technical details on request

Granger
Associates


1, Brooklands Road, Weybridge, Surrey
Telephone: BYFLEET 44261-4, Telex: 261780
Cables: Ansound, Weybridge

WW—008 FOR FURTHER DETAILS



Give us just 2 minutes

and we'll
show you what
our new clip-on
can do!

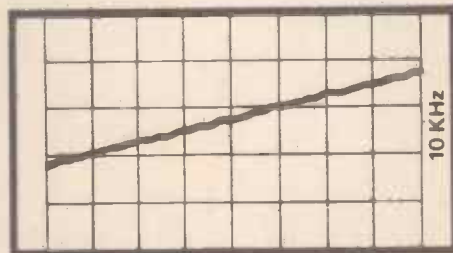*Before you
even begin making
comparisons - note that
the scale below is
100-times up on the
one above!*



1 HOUR

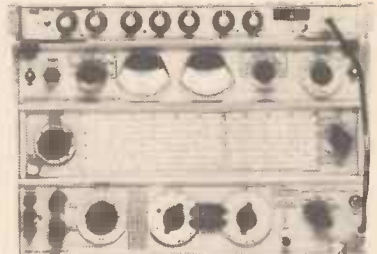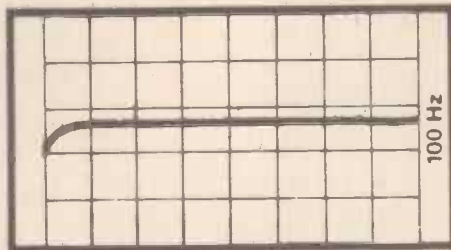

The TF2002 Series HF Signal Generators go digital with a new clip-on synchroniser that cuts the warm-up time taken to reach frequency stability from 2-3 hours to 2-3 minutes. Flat!

And don't confuse it with a lock box. In function it couldn't be less like one. The required frequency is simply set up on the decade dials (within 10Hz). The signal generator then only needs to be tuned *approximately* to this frequency until the synchroniser indicates that it is 'locked-in'. And locked-in it stays. The frequency

stability is 1×10^{-6} which will hold from 10° to 35°C. Indefinitely. And simply by switching the synchroniser decade dials, bandwidth measurement can be made within 1% of the working frequency.

Attached to the TF2002AS, the TF2170 offers a stability performance comparable to a frequency synthesiser at a saving of about £1,000. And this with no risk of generating spurious outputs at low levels. The TF2170 can be supplied separately or complete with the TF2002AS which still retains its existing features including frequency

coverage from 10kHz to 72MHz a.m./f.m.

Have you got 2 minutes?
Contact us at St. Albans for a working demonstration. At our place or yours. Just 2 minutes—3 at the outside. Promise.



**See us on Stands
A21, A22, A23,
in the entrance foyer**

MARCONI INSTRUMENTS LIMITED
A GEC-Marconi Electronics Company.
Longacres, St. Albans, Herts, England.
Tel: St. Albans 59292. Telex: 23350.

**Most
manufacturers
call these extras**

21 active columns plus
19 floating decimal points
Serial or parallel entry options
Automatic column suppression
Multiple space printing
Roll or fan-fold paper
Red or black print-out

**We
call them
standard**



£345

Buying a digital printer without these extras is like buying a car without a heater and screen washers. So we put extras in our new DP21 as standard. It works out cheaper and we pass the savings on to you.

But the basic spec. is far from standard. The DP21 prints 21 columns (19 data plus 2 symbol) with 15 characters per column at 3 line/s.

The floating decimal point can be commanded to print together with a numerical character to save column space. DP21 accepts true or complimentary parallel-entry t.t.l./d.t.l.


VENTURE
MEASUREMENT FOR INDUSTRY

binary coded logic. If required, the printer can be supplied in kit form for custom building.

Make a straight comparison with with any other machine. By adding extras you might end up with a printer nearly as good. But not at the same low price.


Write or 'phone Ian Byatt
(Extension 3188) for information.

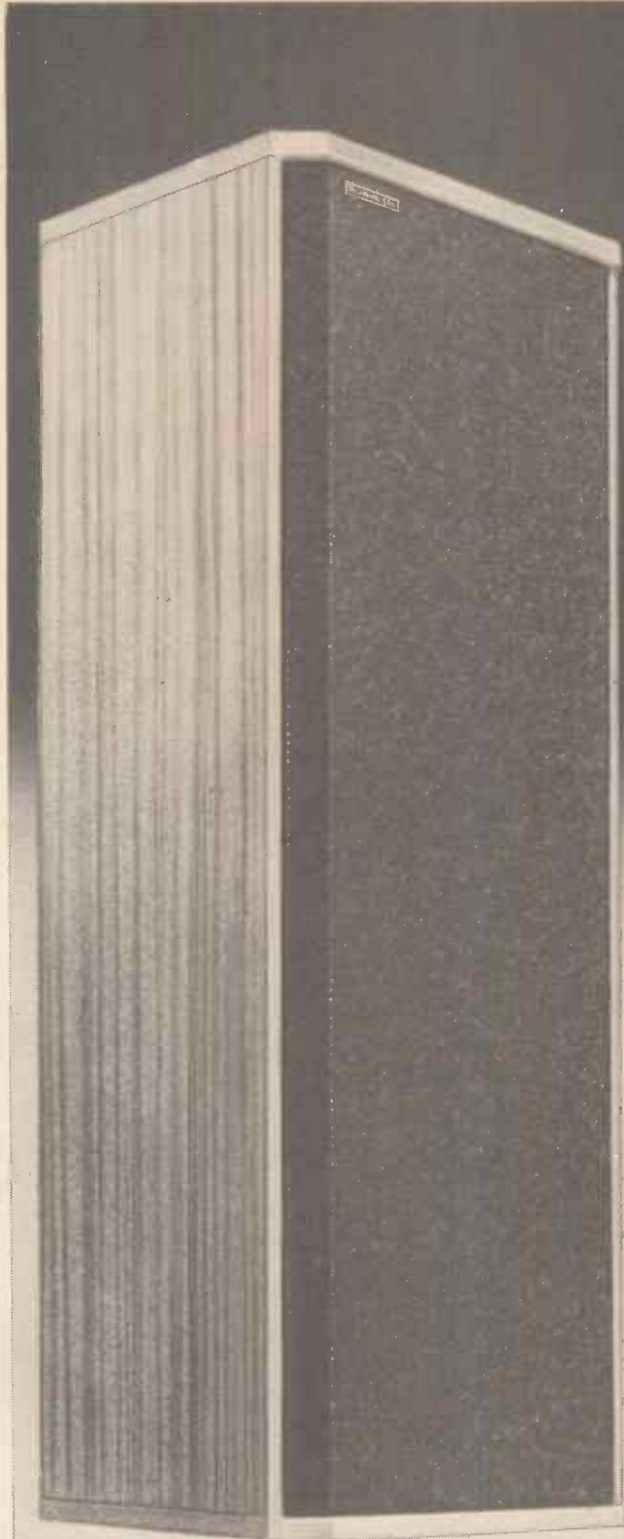SMITHS INDUSTRIES LIMITED INDUSTRIAL INSTRUMENT DIVISION
Kelvin House, Wembley Park Drive, Wembley, Middlesex, HA9 0NU.
Tel: 01-452 3333. Telex: 25366.



Celestion Loudspeaker Engineering advances the state of the art to a new plateau.

Ditton 66 Studio Monitor

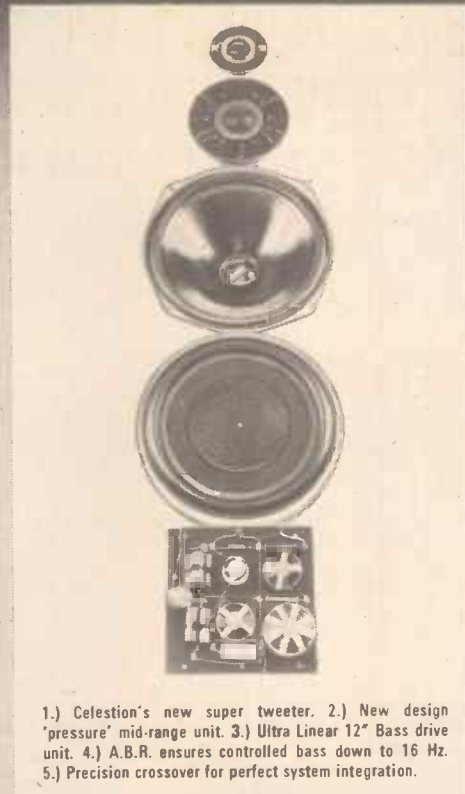

1.) Celestion's new super tweeter. 2.) New design "pressure" mid-range unit. 3.) Ultra Linear 12" Bass drive unit. 4.) A.B.R. ensures controlled bass down to 16 Hz. 5.) Precision crossover for perfect system integration.

Illustrated above is the Ditton 66 showing the beautiful appearance of the acoustic enclosure.

Celestion Ditton Series

Loudspeakers for the Perfectionist

ROLA CELESTION LIMITED DITTON WORKS, FOXHALL ROAD, IPSWICH, SUFFOLK



Section of the new Celestion mid-range unit giving superb power handling and detail.

In just 30 minutes from now, Racal will be on the air.



Easy to set up. Simple to commission. And just as easy to dismantle. Racal transportable radio stations make it possible to provide reliable sophisticated communications facilities, at any time, anywhere.

Compact, self-contained and extremely robust, these stations are designed for transportation by land, sea or air. Racal transportables are comprehensively equipped and may be fully engineered to a customer's individual requirements. The company's extensive experience and proven expertise in

communication systems planning is available to advise on the most effective installation for any particular application including the associated antenna systems.

Racal transportables can be supplied to meet such diverse applications as HF/VHF communication centres, radio beacons, mobile signalling centres, radio monitoring and mobile military command posts.


Find out more about some of the world's finest transportable communications systems. Communicate with Racal - today.

RACAL COMMUNICATIONS LTD.
Western Road, Bracknell,
Berks, England.
Tel: Bracknell 3244,
Telex: 84166,
Cables, Racal Bracknell.



Racal...the communications people.


RACAL
The Electronics Group

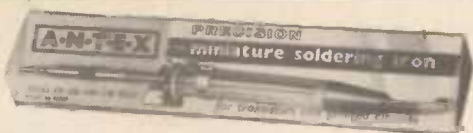

CN.240/2 Miniature soldering iron 15 watt 240 volts, fitted with nickel plated 3/32" bit and packed in transparent display box. Also available for 220 volts. Price £1.70

CN.240 Miniature soldering iron 15 watt 240 volts, fitted with iron coated 3/32" bit. Up to 18 interchangeable spare bits obtainable. This iron can also be supplied for 220, 110, 50 or 24 volts. Price £1.70 (Supplied in standard pack)

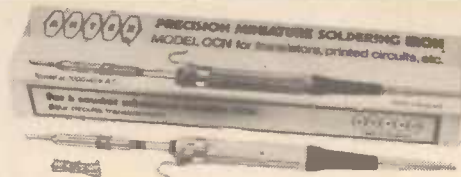G.240 Miniature soldering iron 18 watt 240 volts extensively used by H.M. Forces. Suitable for high speed soldering and fitted with iron coated 3/32" bit. Also available for 220 volts. Spare bits 1/8", 3/16" and 1/4" are obtainable. Price £1.83 (Supplied in standard pack)



CCN.240 New model 15 watt 240 volts miniature soldering iron with ceramic shaft to ensure perfect insulation (4,000 v A.C.). Will solder live transistors in perfect safety, fitted with 3/32" iron coated bit. Spare bits 1/8", 3/16" and 1/4" available. Can also be supplied for 220 volts. Price £1.80

CCN.240/7 The same soldering iron fitted with our new 7-star high efficiency bit for very high speed soldering. The bits are iron coated, nickel and chromium plated. Price £1.95



E.240 20 watt 240 volts soldering iron fitted with 1/4" iron coated bit. Spare bits 3/32", 1/8" and 3/16" available. Can also be supplied for 220 and 110 volts. Price £1.80.

ES.240 25 watt 240 volts soldering iron fitted with 1/8" iron coated bit. Spare bits 3/32", 3/16" and 1/4" available. Can also be supplied for 220 and 110 volts. Price £1.83



MES. 12


A battery operated 12 volts 25 watt soldering iron complete with 15' lead, two crocodile clips for connection to car battery and a booklet "How to Solder" packed in a strong plastic wallet. Price £1.95



SK. 1 SOLDERING KIT

The kit contains a 15 watt 240 volts soldering iron fitted with a 3/16" bit, nickel plated spare bits of 5/32" and 3/32", a reel of solder, heat sink, cleaning pad, stand and booklet "How to Solder." Also available for 220 volts

Price £2.75

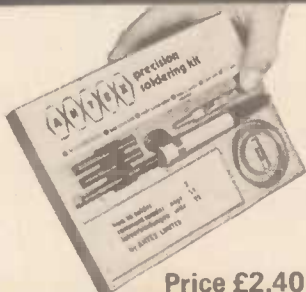

SK. 2 SOLDERING KIT

This kit contains a 15 watt 240 volts soldering iron fitted with a 3/16" bit, nickel plated spare bits of 5/32" and 3/32", a reel of solder, Heat Sink, 1 amp fuse and booklet "How to Solder"

Price £2.40.

GSS Desoldering Tool

Model GSS with 1/2" tip diameter. Model ESS with 5/32" tip diameter

£4-67

ESS Desoldering Tool

£4-67



De-soldering tool working on compressed air for industrial use with an air line or occasional use with foot pump. Efficient, self-cleaning operation on Venturi principle. Split-second action. Press valve control.



Model ESS or GSS complete with foot pump
£5-65

sign here

to answer all your soldering problems

I enclose cheque
P.O./Cash
(Giro No. 2581000)


Name _____

Address _____

ww 4

Please send the Antex colour catalogue.


Please send the following

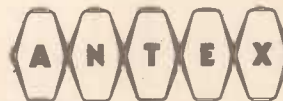

from electrical and radio shops or from
Antex Ltd. FREEPOST (no stamp required) **Plymouth, PL1 1BR.**
Telephone 0752 67377/8

Farnell frequency measurement

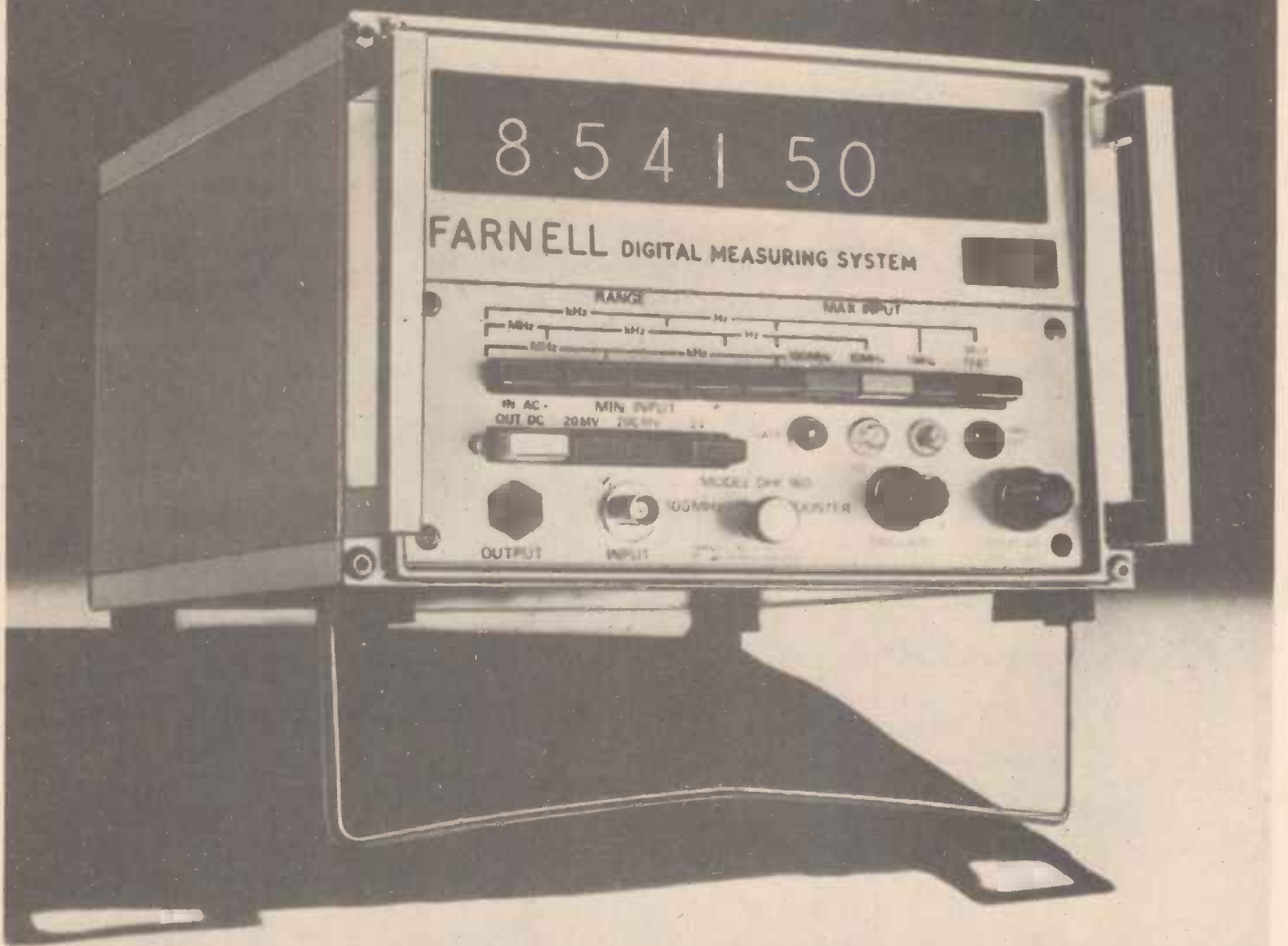■ 100MHz ■ 6 Digit Display ■ Good Sensitivity ■ £340



The Farnell 100MHz counter type DMF 600P/DHF 160 is direct counting and provides 6 digit display of frequencies from 0.1Hz to 100MHz. Accuracy is 5 PPM, sensitivity typically 10mV and drift less than 3.5 parts in 10^6 per week. At £340, it's very good value for money.

and a bonus too!

It's based on a modular design - the main frame accepts any one of nine plug-in modules so the instrument can measure d.c. volts down to $1\mu\text{V}$, a.c. volts, frequency, time, resistance 0.001Ω to $1000\text{M}\Omega$, capacitance 1pF to $10,000\mu\text{F}$ and so on. All these additional functions are available at a fraction of the cost of

separate instruments — you only purchase the display section and power supplies once, when you buy the main frame. Even if you only need a good counter at the moment, it is worth remembering this bonus. It could save you an awful lot of money.

Full Details From

Farnell

Farnell Instruments Ltd.
Sandbeck Way, Wetherby, LS22 4DH
Tel: 0937 3541. Telex: 557294.
London Tel: 01-802 5359

In just 2 minutes, find out how you can qualify for promotion or a better job in Engineering ...

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast - makes learning easier and something you look forward to. If you'd like to know how just a few hours a week of your spare time, doing something constructive and enjoyable, could put you out in front, post the coupon today. No obligation.

THEY DID IT— SO COULD YOU

"My income has almost trebled... my life is fuller and happier."—Case History G/321.

"In addition to having my salary doubled, my future is assured."—Case History H/493.

"Completing your Course meant going from a job I detested to a job I love."—Case History B/461.

FIND OUT FOR YOURSELF

These letters—and there are many more on file at Aldermaston Court—speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you.

WHICH SUBJECT WOULD INTEREST YOU?

Mechanical
A.M.S.E. (Mech.)
Inst. of Engineers
Mechanical Eng.
Maintenance Eng.
Welding
General Diesel Eng.
Sheet Metal Work
Eng. Inspection
Eng. Metallurgy
C. & G. Eng. Crafts
C. & G. Fabrication

Auto & Aero
A.M.I.M.I.
MAA/IMI Diploma
C. & G. Auto Eng.
General Auto Eng.
Motor Mechanics
A.R.B. Certs.
Gen. Aero Eng.

Management & Production
Computer Programming
Inst. of Marketing
A.C.W.A.
Works Management
Work Study
Production Eng.
Storekeeping
Estimating
Personnel Management
Quality Control
Electronic Data Processing
Numerical Control
Planning Engineering
Materials Handling
Operational Research
Metrication

Constructional
A.M.S.E. (Civ.)
C. & G. Structural
Road Engineering
Civil Engineering
Building
Air Conditioning
Heating & Ventilating
Carpentry & Joinery
Clerk of Works
Building Drawing
Surveying
Painting and Decorating
Architecture
Builders' Quantities

General
C.E.I.
Petroleum Tech.
Practical Maths.
Refrigerator Servicing.
Rubber Technology
Sales Engineer
Timber Trade
Farm Science
Agricultural Eng.
General Plastics

General Certificate of Education
Choose from 42 'O' and 'A' Level subjects including:
English
Chemistry
General Science
Geology
Physics
Mathematics
Technical Drawing
French
German
Russian
Spanish
Biology
B.I.E.T. and its associated schools have recorded well over 10,000 G.C.E. successes at 'O' and 'A' level.

WE COVER A WIDE RANGE OF TECHNICAL AND PROFESSIONAL EXAMINATIONS.

Over 3,000 of our Students have obtained City & Guilds Certificates. Thousands of other exam successes.

Draughtsmanship
A.M.I.E.D.
Gen. Draughtsmanship
Die & Press Tools
Elec. Draughtsmanship
Jig & Tool Design
Design of Elec. Machines
Technical Drawing
Building

Electrical & Electronic
A.M.S.E. (Elec.)
C. & G. Elec. Eng.
General Elec. Eng.
Installations & Wiring
Electrical Maths.
Electrical Science
Computer Electronics
Electronic Eng.

Radio & Telecomms.
C. & G. Telecomms.
C. & G. Radio Servicing
Radio Amateurs' Exam.
Radio Operators' Cert.
Radio & TV Engineering
Radio Servicing
Practical Television
TV Servicing
Colour TV
Practical Radio & Electronics (with kit)

Free!

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). We'll send you full details and a FREE illustrated book. No obligation and nobody will call on you... but it could be the best thing you ever did.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept B7, Aldermaston Court, Reading RG7 4PF.

POST THIS COUPON TODAY

Accredited by the Council for the Accreditation of Correspondence Colleges.



(Write if you prefer not to cut this page)

To: B.I.E.T., Dept B7, Aldermaston Court, Reading RG7 4PF
Please send me book and details of your Courses in

Name

Address

Subject of Interest Age

B.I.E.T. - IN ASSOCIATION WITH THE SCHOOL OF CAREERS - ALDERMASTON COURT, BERKSHIRE



10Hz - 80kHz

Gardners

-0.5dB

How much bandwidth do you need?

Whatever your requirement you can make an economical choice from the five Gardners Ranges of Top Performance Line Matching Transformers

SUPER FIDELITY

The Super Fidelity Series, with a frequency response of 10Hz to 80kHz - 0.5dB, gives the widest possible bandwidth. For high accuracy instrumentation and recording applications.

WIDE & EXTRA WIDE-BAND

The Wide and Extra Wide-band, too, are outstanding performers with a frequency range 30Hz - 20kHz or more - for the 0.5dB points. Used extensively by Broadcasting and Recording companies throughout the World.

MINIATURE & STANDARD

Even the smallest units provide excellent bandwidth for most purposes, 30Hz - 22kHz for the 1.0dB points.

All Gardners Line Matching Transformers (excepting the very smallest in the range) are fully magnetically shielded, giving very high hum rejection ratios. Some of the available types are so well balanced that they can be employed in two wire to four wire hybrids with rejection ratios better than 55dB.

Prices start from £2.61 (*recommended retail price*) and all types are usually available from Stock. Complete technical information is given in brochure GT.5 'Audio Frequency Transformers' which we will gladly send you on request.

Gardners

GARDNERS TRANSFORMERS LIMITED
Christchurch Hampshire BH23 3PN Tel: Christchurch 2284
(STD 0201 5 2284) Telex 41276 GARDNERS XCH




**SUB-STANDARD MULTI-RANGE VOLTAMMETER
TYPE U4311**

Sensitivity 333Ω/V on AC and DC ranges
Accuracy 0.5% DC and 1% AC
13 DC Voltage ranges 75mV to 750V.
14 DC Current ranges 300μA to 7.5A.
10 AC Voltage ranges 750mV to 750V.
11 AC Current ranges 3mA to 7.5A.
Overload protection by transistorized relay cut-out.
Scale length 165mm.

PRICE £49.00

FULL INFORMATION ON REQUEST

STRIP CHART RECORDERS

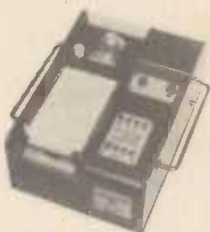

HIGH SPEED RECORDERS TYPE H320
Moving coil mechanism with natural frequency of oscillation of 5Hz and sensitivity of 8mA FSD. Syphon ink-pen with large reservoir capacity. Paper footage indicator. 8 chart speeds from 1.2 to 3000mm per hour selected by push buttons. Width of recording channel 80mm.
SINGLE CHANNEL RECORDER H320-1 £55
THREE CHANNEL RECORDER H320-3 £90



**MULTI-RANGE UNIVERSAL
PORTABLE AC/DC VOLTAMMETER
TYPE H350**
8 AC/DC current ranges 5mA to 5 Amps
8 AC/DC voltage ranges 5-500V.
8 Chart speeds 20 to 5400mm per hour.
Chart width 100mm
PRICE £78



**PORTABLE RECORDING MILLIAMMETER
H352**
Sensitivity 1mA DC. D.C. resistance of the movement 10670 ohms. Chart width 100mm. Six chart speeds 20 to 5400mm per hour.
PRICE £52



**SWITCHBOARD TYPE TEN CHANNEL
EVENT RECORDER TYPE H30**
Instruments provides permanent record of duration and sequence of up to ten operation. Syphon pens with large ink reservoirs are mounted on rotary relays energized from a 12V D.C. source. Six chart speeds 20 to 5400mm per hour.
PRICE £52



FOR IMMEDIATE DELIVERY

OSCILLOSCOPES



SYNCHROSCOPE C1-5
3-in. tube. Built-in time base calibrator. Voltage measurement scale. 10mc/s pass-band. Sensitivity 10mV per mm. Nine pre-set triggered sweep rates from 1 to 3000μsec. Free-running time base 20Hz to 200 kHz. Input attenuator 1-10-100 times.
PRICE £38

SINGLE BEAM D.C. OSCILLOSCOPE C1-19



5½-in. tube giving display size of 80 x 50mm.
Passband DC to 1MHz.
Sensitivity 5mm/mV.
Sweep range 100μsec to 10sec per stroke.
Internal time-base and amplitude calibrators.
Long afterglow screen.
Input attenuator 1-10-100-1000 times

PRICE £98.



DOUBLE BEAM OSCILLOSCOPE C1-16
Double gun rectangular tube giving display size of 40 x 100mm. Passband 5mc/s for 3db down. Sensitivity 20mV per cm. 18 pre-set calibrated sweep durations from 0.2 μ sec/cm to 100m sec per cm. Free running time base 50Hz to 1mc. Built-in amplitude calibrator. Crystal time base marker.
PRICE £87

ALL THESE INSTRUMENTS ARE SHOWN, AND CAN BE DEMONSTRATED, IN OUR SHOWROOM, AT 46 WESTBOURNE GROVE, LONDON, W.2, FROM 9.30 TO 5.30, MONDAY TO FRIDAY.

FULL SERVICING FACILITIES

Z & I AERO SERVICES LTD.
44A WESTBOURNE GROVE, LONDON W.2

Tel: 727-5641


Telex 261306

NOTE: THE ABOVE EQUIPMENT IS OF USSR MANUFACTURE

Build with LEKTROKIT the simple as A·B·C construction system for electronic engineers

With imagination and a box of bricks you can build anything: bridges: towers: castles.

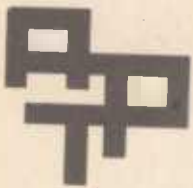With LEKTROKIT and a screwdriver you can build anything you need: chassis; racks; trolleys; panels; shelves; consoles; etc. Keep LEKTROKIT in stock for ECONOMY and SPEED—ready for instant action.



A.P.T. ELECTRONIC INDUSTRIES LTD.
CHERTSEY ROAD BYFLEET · SURREY
TEL: BYFLEET 41131 · TELEX 262525
A member of the Bonochord Group of Companies

WW—018 FOR FURTHER DETAILS

NEW FROM

LINEAR

Representing really exceptional value

TWO STEREO
AMPLIFIERS

IN ELEGANT TEAK FINISH CASES!



LINEAR 606 6+6 WATTS

0-200-230-250v. 50 Hz A.C. mains operation.
Inputs for magnetic or Ceramic Pickup.
Tape or Radio Tuner

Recommended
Retail Price

£22.50

FANE HIGH FIDELITY LOUDSPEAKERS. We are the sole U.K. distributors to the wholesale and retail trades and would suggest the very reasonably priced 808T or 807T Bin 10,000 Gauss 10 watt dual cone models for use with our 505 or 606 amplifiers.

TECHNICAL DETAILS

Bass Control ± 12 d.b. at 40 Hz.
Treble Control ± 12 d.b. at 14 KHz.
Sensitivities Mag P.U. 3.5 m.v. into 47K ohm R.I.A.A. Ceramic P.U. 35m.v. into 100K ohm. Tape Amp. 100 m.v. into 100K. Radio Tuner 400 m.v. into 400K ohm.
Crosstalk 53 d.b.
Hum and Noise - 75 d.b. min. vol - 85 d.b. max. vol.
Total Harmonic Distortion 0.1% at 1w into 15 ohms.
Output (per channel) 6.5 watts I.H.F.M.

- ★ Individual Bass and Treble Controls.
- ★ Frequency Response $\pm 1\frac{1}{2}$ d.b. 20 Hz to 65 KHz.
- ★ Outputs for Speaker impedances between 3 and 15 ohms. ★ Stereo/Mono Switch.
- ★ Input Selector Switch. ★ Solid State Circuitry.
- ★ Attractive silver finished metal facia and matching control knobs.

A modestly priced solid state unit.
The Silver Facia with black lettering enhanced by matching control knobs, provides a high standard of appearance. Suitable for crystal or ceramic Gram. Pickup cartridges and Radio input.
A wide range of tone variation is provided by the separate Bass and Treble 'lift' and 'cut' controls.
A selector switch permits instantaneous selection of Gram. or Radio.
Speaker impedances between 3 and 15 ohms are suitable.

TECHNICAL DETAILS

Frequency Range
20Hz to 20KHz
Output (per channel)
5 watts I.H.F.M.
Bass Control
 ± 12 d.b. at 60 Hz
Treble Control
 ± 14 d.b. at 14 KHz



LINEAR 505 5+5 WATTS

Recommended
Retail Price

£17.50

0-200-250v. 50 Hz A.C. mains operation

PRINTED CIRCUIT CONSTRUCTION
EMPLOYING 10 TRANSISTORS

ALL LINEAR AMPLIFIERS GUARANTEED FOR 12 MONTHS

Wholesale and Retail enquiries to the Manufacturers

LINEAR PRODUCTS LTD., Electron Works, Armley, Leeds. LS12 3SA Tel.630126

WW—019 FOR FURTHER DETAILS

Hear how, see how, know-how



Communications are a vital element in the management and administration of people in every field of activity. Audio and visual communications systems – to educate, warn, entertain, inform, locate – demand the application of specialist skills and the availability of reliable, purpose-designed equipment. EMI has the skills

and the equipment to meet any requirement for audio or visual communications with a cost-effective, proven system – whether public address, sound reinforcement, CCTV – or any combination. EMI has the know-how in audio and visual communications. Please ask for full details of our comprehensive range of products.

A member of the
EMI Group of Companies.
International leaders in Electronics,
Records and Entertainment.




Sound
and Vision
Systems

EMI Electronics Ltd., Television Equipment Division, Blyth Road, Hayes, Middlesex, England.
Telephone: 01-573 3888, Ext. 2011

WW-020 FOR FURTHER DETAILS

Magnetic shielding problems?

TELCON OFFER THREE SIMPLE ANSWERS

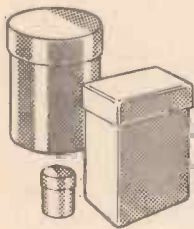


Standard shields

Telcon Metals offer an extensive standard range of high efficiency Mumetal shields, which fit most cathode ray, photo multiplier and radar tubes, together with a selection of boxes and cans for microphones, pick-ups, transistors and transformers. These are normally supplied stove enamelled in hammer grey externally and matt black internally. Other finishes can be supplied by arrangement.



Fabricated shields

Telcon Metals offer complete facilities for fabricating special shields in Mumetal and composite shields in Mumetal/Radiometal to customers' individual requirements. All Telcon shields are made to close tolerances and have excellent finish and appearance. For the highest efficiency and extra close fitting tolerances, the 'Telform' technique is recommended. These shields can be produced in complex shapes with a minimum of welded seams and very close uniformity throughout batches. A comprehensive design/advice service is available to assist all customers.

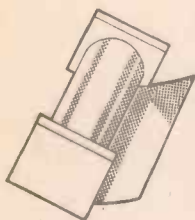

'Telshield' wrap-around foil

'Telshield' is an easy to use, ferromagnetic shielding foil, which can be cut with scissors, wound into cylinders, cones, etc., and fixed with adhesive tape, clips or spot welds, to provide a permanent efficient shield. It is economical to use, especially for research, development and short-run applications which do not merit the tooling involved in the production of fully fabricated shields. 'Telshield' is supplied in a standard thickness of 0.05 mm, in widths of 150, 50 and 25 mm in convenient packs costing approximately £5. Other thicknesses and widths are available by arrangement.

Please send for further information to

TELCON

Telcon Metals Ltd.,
Manor Royal, Crawley, Sussex.
(Crawley 28800)

WW—021 FOR FURTHER DETAILS

We'll pot your 'babies' for you



When you've got components that call for encapsulation—bring them along to Whiteley. With efficient potting, your components will be totally insulated and environmentally protected—and Whiteley experience in developing this advanced plastics technique will ensure that it is applied to full advantage.

We can encapsulate in epoxy resin or polyurethane—hot setting or cold setting as required. Where fillers offer advantages, we can apply them, expertly. We are ready to handle small quantities or volume production for you. It's one more way in which you can capitalise on our production resources. For electrical and electronic work—right through from design to final assembly—you can safely follow the example of many famous names—and call in Whiteley.

Whiteley

versatility...

ELECTRONIC & ELECTRICAL DESIGN

PRODUCTION CAPABILITY

CABINET MAKING

SHEET METAL FORMING/FINISHING

PLASTICS MOULDING

ENCAPSULATION

WHITELEY ELECTRICAL RADIO CO. LTD.
Mansfield, Notts, England. Tel. Mansfield 24762
London Office: 109 Kingsway, W.C.2. Tel. 01-405 3074

WW—022 FOR FURTHER DETAILS



If you can use a soldering iron and follow simple instructions, you can assemble any of these high performance products in a few hours. And save a lot of money.

Heathkit have the world's widest range of top quality electronic products designed specifically for home assembly.

Of which we show just 4 above.


The AD110 is our new stereo cassette recorder. It gives

you cassette convenience, reel performance and Heathkit

quality. Designed to complement various other Heathkit Hi Fi products, it costs only £74.80 + £8.45 for twin matched stereo mikes.

Another new product, the Tiger transistor radio kit

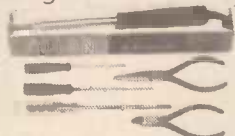costs £10.90. It gives long life from every large PP9 battery, weighs just 3 lbs, and gives really good reception on Long & Medium wavebands.



And, as you can see, it looks pretty good too.


Costing just £18.45 complete with speaker and aerial, the CR1 car radio gives unsurpassed reception. A 6 transistor, 2 diode circuit gives 4 watts output, pre-assembled and aligned tuning unit makes assembly easy, and push-button controls give instant selection.

The AA14 30 watt stereo amplifier is an established

product, proven in use by thousands of satisfied customers. Featuring a 17 transistor, 6 diode circuit, it costs £30.00 less cabinet.

These products and all the others in the Heathkit range are easily assembled by anyone who can use a soldering iron and follow our superbly clear, step-by-step instructions. Furthermore, in the unlikely event that you get stuck, we guarantee to help you out.

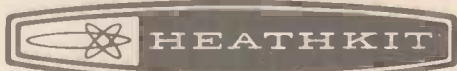Find out more. Send for our free 1972 catalogue. Now.




You can make it if you try.

Please send me the FREE New 1972 Heathkit catalogue. WW 04/72

Name

Address

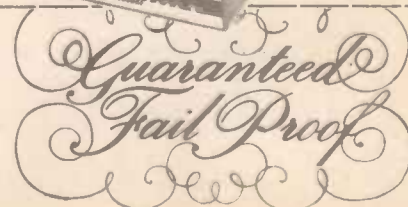
HEATH (Gloucester) Ltd., Gloucester GL2 6EE





Eddystone

DIECAST BOXES

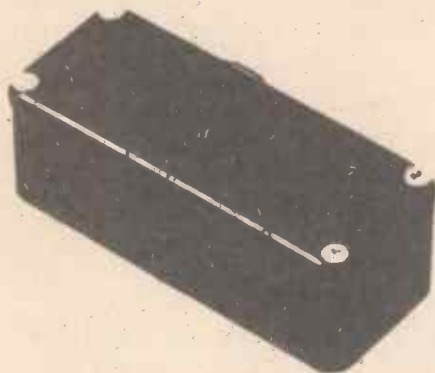

WORLD-WIDE AVAILABILITY

Diecast in aluminium alloy, BS 1490 LM2

SIX SIZES

- Cat. No. 7969P— $3\frac{9}{16} \times 1\frac{1}{2} \times 1\frac{17}{32}$ in
(Illustrated) 92.1 x 38.1 x 31 mm
- Cat. No. 7134P— $4\frac{3}{8} \times 2\frac{3}{8} \times 1\frac{17}{32}$ in
111.1 x 60.3 x 31 mm
- Cat. No. 6908P— $4\frac{11}{16} \times 3\frac{11}{16} \times 2\frac{27}{32}$ in
119.1 x 93.6 x 56.4 mm
- Cat. No. 6827P— $7\frac{25}{64} \times 4\frac{45}{64} \times 2\frac{27}{32}$ in
187.3 x 119.1 x 56.4 mm
- Cat. No. 6357P— $7\frac{25}{64} \times 4\frac{45}{64} \times 3\frac{27}{32}$ in
187.3 x 119.1 x 81.8 mm
- Cat. No. 7970P— $7\frac{3}{8} \times 7\frac{3}{8} \times 2\frac{21}{32}$ in
187.3 x 187.3 x 67.5 mm

(Nominal outside dimensions)

Rugged. Corrosion resistant.

Self adhesive plastic strip available for mounting PCB's internally.

Easily Machined. Good Surface Finish.

Illustrated brochure and information on your local Distributor from:

Eddystone Radio Limited


Alvechurch Road, Birmingham B31 3PP, England
Telephone: 021-475 2231. Telèx: 337081

A Member of Marconi Communication Systems Limited

LTD/ED 93

WW—024 FOR FURTHER DETAILS

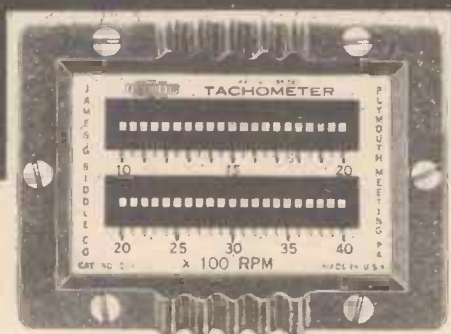Accurate and direct measurement of speed without coupling to moving parts



FRAHM resonant reed TACHOMETERS

for hand use or permanent mounting

Ranges and combinations of ranges from 900 to 100,000 r.p.m.

Descriptive Literature on Frahm Resonant Reed Tachometers and Frequency Meters available from the sole U.K. Distributors. Manufacture and Distribution of Electrical Measuring Instruments and Electronic Equipment. The largest stocks in the U.K. for off-the-shelf delivery.


Anders means meters

ANDERS ELECTRONICS LIMITED

48/56 Bayham Place, Bayham Street,
London NW1. Tel: 01-387 9092

WW—025 FOR FURTHER DETAILS

nombrex

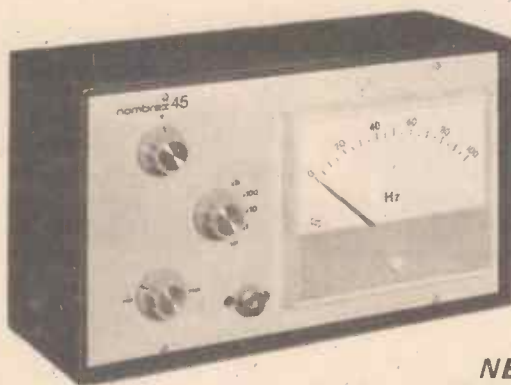

NEW
MODEL 45

DIRECT READING FREQUENCY METER

PRICE £27.50

- MEASURES FREQUENCY FROM 10 Hz TO 100 kHz.
- MEASUREMENT INDEPENDENT OF SIGNAL WAVE FORM.
- ACCEPTS INPUT LEVELS FROM 10mV TO 5V.
- FOUR DECADE SWITCH RANGES.
- SENSITIVITY CONTROL.
- CALIBRATION CONTROL.
- POWERED BY 9 VOLT BATTERY.

Trade and Export enquiries welcome.


Send for full technical leaflets.

Post and Packing 35p. extra.

NOMBREX (1969) LTD., EXMOUTH, DEVON

Tel: 03-952 3515


WW—026 FOR FURTHER DETAILS

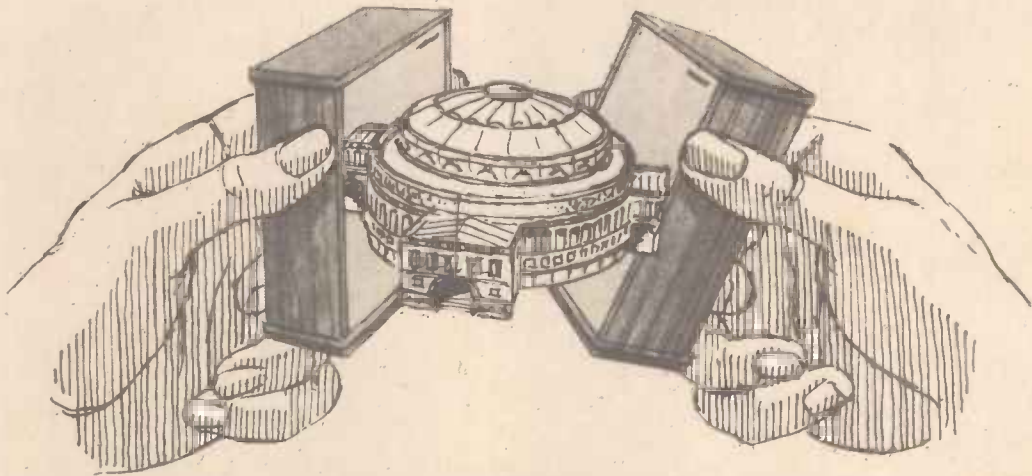

it's all a **great illusion . . .**

Stereosound is one of the best technical tricks of the century, and Tannoy Monitor Gold loudspeakers help the illusion along. The piano won't seem eighteen feet wide, you won't hear the violins left, right and centre, in fact the illusion will be as good as the recording engineer can make it. (He probably used Tannoy monitors in the studio.)

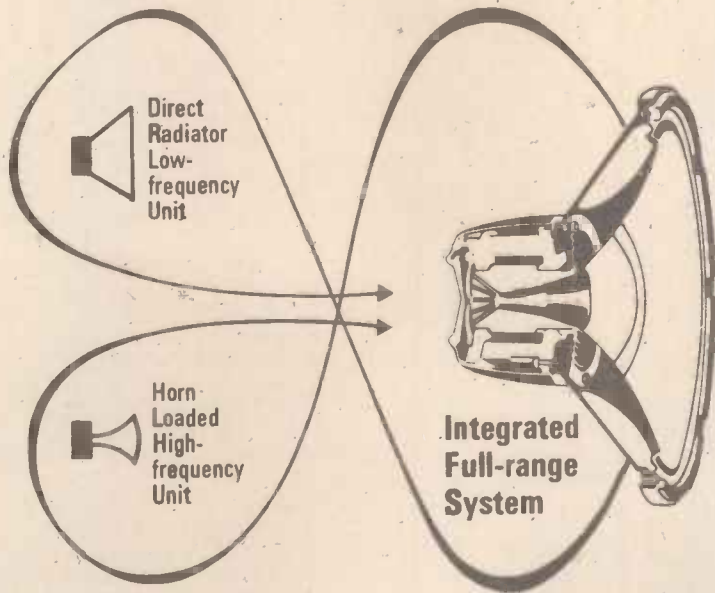our own contribution to the magic—
two into one will go!



THE *Monitor*
GOLD*
DUAL CONCENTRIC

Frequency Response: 30-20,000 Hz. Power Handling Capacity: 15" 50 watts, 12" 35 watts, 11 1/2" 25 watts. Impedance: 8Ω nominal, 5Ω minimum.

Available from the best dealers in a wide range of enclosures including the **NEW CHATSWORTH**



TANNOY PRODUCTS · NORWOOD RD · WEST NORWOOD SE27 9AB TEL: 01-670 1131

Sitesold**ETC/1 ELECTRONICALLY CONTROLLED****SOLDERING SYSTEM**

This equipment has been designed to provide the most outstanding thermal performance and control yet achieved with a Soldering Iron, combined with the total avoidance of electrical interference.

At the same time, it overcomes the problems of repair costs and complications associated with common temperature controlled Irons, and offers a standard of reliability unattainable with other designs.



Please write or ring for leaflets 5/1017/9

LIGHT SOLDERING DEVELOPMENTS LTD.

28 Sydenham Road, Croydon CR9 2LL.

Tel: 01-688 8589/4559

WW—028 FOR FURTHER DETAILS

Another tremendous bargain from Jermyn

**Better spark at all revs.
Easier cold starting.
Longer battery life.
Less wear on points.
Smoother running.
Lower petrol consumption.
Longer plug life.**

Set of parts to enable the electronics hobbyist to build the Electronic Ignition as described in P.W. June '71. Inverter transistors, Diodes, Zeners, Resistors, Capacitors, Transformer, robust die cast box 2 x 3½ x 4½", circuit diagram and **Free Car Sticker.**

State + or -ve earth and send cheque or P.O. £7.75 including p. and p. to: -

JERMYN
Jermyn Industries, Vestry Estate, Sevenoaks, Kent.

(Not suitable for beginners)
Prompt despatch by post.

£7.75 complete

WW—029 FOR FURTHER DETAILS


Vortexion

50/70 WATT ALL SILICON AMPLIFIER

WITH BUILT-IN 5-WAY MIXER USING F.E.T.s.

This is a high fidelity amplifier with bass cut controls on each of the three low impedance balanced line microphone stages and a high impedance (1.5 meg.) gram stage with bass and treble controls, plus the usual line or tape input. All the input stages are protected against overload by back to back low self capacity diodes and all use F.E.T.s for low noise, low intermodulation distortion and freedom from radio breakthrough.

A voltage stabilised supply is used for the pre-amplifiers making it independent of mains supply fluctuations and another stabilised supply for the driver stages is arranged to cut off when the output is overloaded or over temperature. The output is 75% efficient and 100V balanced line or 8-16 ohms output are selected by means of a rear panel switch which has a locking plate indicating the output impedance selected. The mixer section has an additional emitter follower output for driving a slave amplifier, phones or tape recorder, output .3V out on 600 ohms upwards.

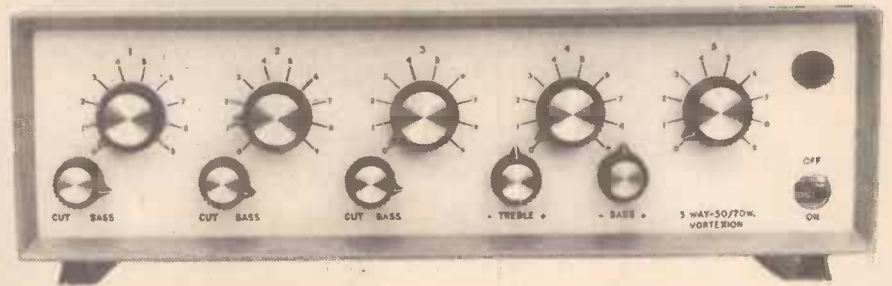

50/70 WATT ALL SILICON AMPLIFIER WITH BUILT-IN 4-WAY MIXER (0.3% intermodulation distortion) using the circuit of our 100% reliable 100 Watt Amplifier with its elaborate protection against short and overload, etc. To this is allied our latest development of F.E.T. Mixer Amplifier, again fully protected against overload and completely free from radio breakthrough. The mixer is arranged for 2-30/60Ω balanced line microphones, 1-HiZ gram input and 1-auxiliary input followed by bass and treble controls. 100 volt balanced line output or 5/15Ω and 100 volt line.

100 WATT ALL SILICON AMPLIFIER. A high quality amplifier with 8 ohms-15 ohms or 100 volt line output for A.C. Mains. Protection is given for short and open circuit output over driving and over temperature. Input 0.4 V on 100K ohms.

THE 100 WATT MIXER AMPLIFIER with specification as above is here combined with a 4 channel F.E.T. mixer, 2-30/60Ω balanced microphone inputs, 1-HiZ gram input and 1-auxiliary input with tone controls and mounted in a standard robust stove enamelled steel case. A stabilised voltage supply feeds the tone controls and pre amps, compensating for a mains voltage drop of over 25% and the output transistor biasing compensates for a wide range of voltage and temperature. Also available in rack panel form.

CP50 AMPLIFIER. An all silicon transistor 50 watt amplifier for mains and 12 volt battery operation, charging its own battery and automatically going to battery if mains fail. Protected inputs, and overload and short circuit protected outputs for 8 ohms-15 ohms and 100 volt line. Bass and treble controls fitted. Models available with 1 gram and 2 low mic. inputs, 1 gram and 3 low mic. inputs or 4 low mic. inputs.

20/30 WATT MIXER AMPLIFIER. High fidelity all silicon model with F.E.T. input stages to reduce intermodulation distortion to a fraction of normal transistor input circuits. The response is level 20 to 20,000 cps within 2dB and over 30 times damping factor. At 20 watts output there is less than 0.2% intermodulation even over the microphone stage at full gain with the treble and bass controls set level. Standard model 1-low mic. balanced input and HiZ gram. Outputs available 8/15 ohms OR 100 volt line.

200 WATT AMPLIFIER. Can deliver its full audio power at any frequency in the range of 30 c/s-20 Kc/s ± 1 dB. Less than 0.2% distortion at 1 Kc/s. Can be used to drive mechanical devices for which power is over 120 watt on continuous sine wave. Input 1 mW 600 ohms. Output 100-120 V or 200-240 V. Additional matching transformers for other impedances are available.

F.E.T. MIXERS and PPMs. Various types of mixers available. 3, 4, 6 and 8 channel with Peak Programme Meter. 4, 6, 8 and 10 Way Mixers. Twin 3, 4, and 5 channel Stereo, also twin 4 and 5 channel Stereo with 2 PPMs.

VORTEXION LIMITED, 257-263 The Broadway, Wimbledon, S.W.19 1SF

Telephone: 01-542 2814 and 01-542 6242/3/4

Telegrams: "Vortexion, London S.W.19"

Another reason why Enthoven is No.1 in solder



Superspeed solder wire

Enthoven's Superspeed soldering wire features an activated-rosin flux core and is ideal for those applications where a wide variety of different jobs must be handled with a single solder.

But don't forget the rest of the Enthoven range. It gives you a wide choice of high-quality products developed for use with modern techniques. It includes Flux Cored Solder Wires, Solder Pre-forms, Solid Solders, Selective Fluxes, solder specialities, materials for printed circuitry and for soldering aluminium.

And behind every Enthoven product stands a comprehensive advisory service that can solve your knottiest soldering problems.

Enthoven Solders Limited
 Dominion Buildings, South Place
 London EC2M 2RE.
 Tel: 01-628 8030 Telex: 885737
 Cables: ENTHOVENLONDON EC2M2RE



WW-031 FOR FURTHER DETAILS



STOCKISTS



MULTIMINOR MK. IV

REPAIR SERVICE
7-14 DAYS

We specialise in repair, calibration and conversion of all types of instruments, industrial and precision grade to BSS.89.

Release notes and certificates of accuracy on request.



MODEL 8 MK. III

Suppliers of Elliott, Cambridge and Pye instruments

LEDON INSTRUMENTS LTD

76-78 DEPTFORD HIGH STREET, LONDON, S.E.8

Tel.: 01-692 2689

G.P.O. APPROVED

CONTRACTOR TO H.M. GOVT.

WW-032 FOR FURTHER DETAILS

Make contact with Teonex

For electronic valves (a really comprehensive range), neon indicator tubes, semi-conductors (a wide variety), integrated circuits.

Teonex offers more than 3,000 devices. They are competitively priced and they are superlative in performance, because the company imposes strict quality control. Teonex concentrates entirely on export and now operates in more than sixty countries, on Government or private contract. All popular types in the Teonex range are nearly always available for immediate delivery. Write now for technical specifications and prices to Teonex Limited, 2a Westbourne Grove Mews, London W11, England. Cables: Tosupply London W11. Telex 262256.

Electronic valves, neon indicator tubes, semi-conductors and integrated circuits for export




sounds international

WW-033 FOR FURTHER DETAILS



THE WORLD OF ROHDE & SCHWARZ

is full of TV Test Equipment

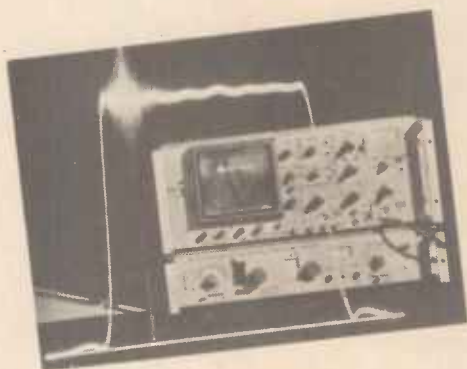

CATALOGUE CONTENTS

Rohde & Schwarz have a world wide reputation as manufacturers of electronic measuring instruments for use in research, development, and production. A major area of involvement is Television measurements.

It is the purpose of TV measurements to ensure the stability of required transmission quality between the TV camera and the home receiver through continuous monitoring. To this end, camera monitors, test equipment at the central distribution points and test assemblies for TV transmitters are employed, in addition, propagation measurements for transmitter network plans must be made.

1. Transmission network measurements (active)
2. Transmission network measurements (passive)
3. In-service testing
4. TV equipment
5. Test assemblies for use in production
6. Peripheral equipment (e.g. field-strength meters).



for
YOUR
FREE
COPY
of the
Catalogue
APPLY TO


VIDEOSKOP SWOF III

A fully transistorized combination unit of video sweep generator, selective receiver and display unit (a sweep and analysis system). **THE VIDEOSKOP III TYPE SWOF** operates in the 10 kHz to 20 MHz frequency range. Shown here with the sideband adapter it is possible to carry out measurements on TV transmitters to a range extending up to 1000 MHz.



AMF

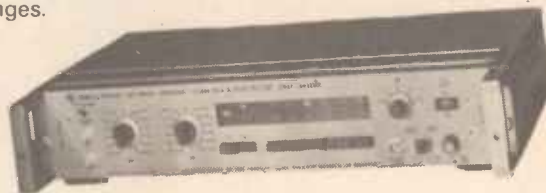The new fully transistorized **TV DEMODULATOR TYPE AMF** is a vestigial-sideband receiver with Nyquist slope, used for the demodulation of monochrome & colour signals (NTSC, PAL, SECAM) and of TV sound signals. It is equally suitable for measurements and monitoring in the RF and IF ranges.



SPAF

The **COLOUR GAIN AND DELAY TEST TYPE SPAF** is a combination unit which may be used with the SPIF Pulse and Bar Signal Generator.



SPEF

A **V.I.T. INSERTER** with up to eight independent insertion channels, can be used with SWOF for investigation of passband and vestigial sideband characteristics during transmission.

aveley electric LTD

Arisdale Ave
South Ockendon, Essex

Tel: Sth. Ockendon 3444
Telex: 24120 Avel Ockendon

Check our check list

Meters available in over 100 case sizes, Edgewise, Rectangular, Round and Square, Bakelite, Clear plastic and Metal cases.

- Clip-on Volt/Ammeters.
- Contact Meters, Moving Coil Relays, Solid State.
- Desk Stands.
- Digital Panel Meters.
- Edgewise Meters.
- Educational Instruments.
- Electrostatic Voltmeters.
- Frequency Meters—Deflectional
- Frequency Meters—with Contact Arms Solid State.
- Frequency Meters—Vibrating Reed.
- Galvanometers.
- Hour Meters, Elapsed Time Indicators A.C. & D.C.
- Hermetically Sealed Meters.
- Instrument Rectifiers.
- Long Scale, 180° and 240° Meters.
- Maximum Demand Indicators.
- Motammeters Moving Iron with overload scale.
- Moving Coil Meters.
- Moving Iron Meters.
- Multi-range Meters.
- Pedestal Pattern Meters.
- Phase Switches.
- Portable Instruments.
- Portable Instrument Cases.
- P.P.M. Meters.
- Resistors or Multipliers.
- Shunts.
- Sub-Standard Instruments.
- Switchboard Meters.
- Tachometer-Indicators.
- Tachometer-Generators.
- Tachometer-Resonant Reed.
- Test Equipment.
- Test Sets, A.C./D.C. (Precision).
- Thermocouple Meters.
- Thermo Junctions
- Transducers—Wattmeter
- Transducers—Frequency
- Transformers—Current.
- Transformers—Split Core
- Transformers-Potential.
- V.U. Meters
- Wattmeters—Panel Mounting.
- Wattmeters—Portable (Precision).
- Waterproof Pattern Meters.

... interested? Give us a ring.


it's the longest



K.M. SERIES with clear front Shadowless Dials. Available in most ranges of Moving Coil and Moving Iron. Eight case sizes. Scale lengths from 0.75" — 6.25".



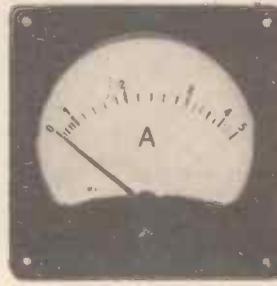Circular Scale 240° Meters, Models CS60 and CS80. Nominal scale lengths 4", 5.5". Available in sensitivities from 200 microamps Moving Coil.



Vulcan Short Scale Meters Models V1, V2, V3 and V4. Nominal scale lengths 1.625", 2", 2.85", 3.5". Available in all ranges of Moving Iron normal or overload scale.



Models KE1 and KE2 Miniature Edgewise Meters. Nominal scale lengths 1.2" and 2". Available in sensitivities from 50 microamps Moving Coil.

ANDERS ELECTRONICS LIMITED

48/56 Bayham Place, Bayham Street, London, N.W.1.
Telephone 01-387 9092.

Manufacturers and distributors of Electrical Measuring Instruments. Sole U.K. distributors of FRAHM Resonant Reed Frequency Meters and Tachometers. Manufacturers of purpose built electrical and electronic equipment to customers' requirements.

Anders means meters

Now it's longer!

We've made these four new additions to our already large range of meters. They are well designed and pleasing to look at. And they are competitively priced.

We also offer a fast delivery of non-standard instruments. In small or large quantities. And many requirements can be supplied off the shelf. Ask for details of our special dial drawing and metric conversion service to customers individual specifications.


NEW temperature controlled soldering iron.




THE ORYX 50

- *Screw adjustment range 200°C to 400°C.
- *Heat settings accurate to $\pm 2\%$.
- *One tip for all temperatures.
- *Temperature adjustable whilst iron is on.
- *Cool, comfortable handle.
- *Standard tip — long life iron coated.
- *Choice of 11 tip sizes.
- *Built-in indicator lamp — thermostat controlled.
- *Rated at 50 watts.
- *12, 24, 50, 115 or 210/250v. models.

TYPICAL CURVE OF THE ORYX 50

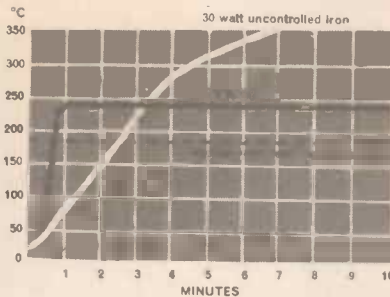

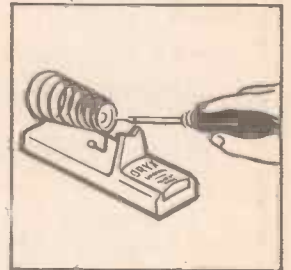
Price
with long life tip.
£5.20
STAND:
£1.95



Send for Technical Literature to

W. GREENWOOD ELECTRONIC LIMITED
21 Germain St, Chesham, Bucks, England. Tel: Chesham 4808/9. Telex 83647. Cables: Greenelec, Chesham.

WW—036 FOR FURTHER DETAILS

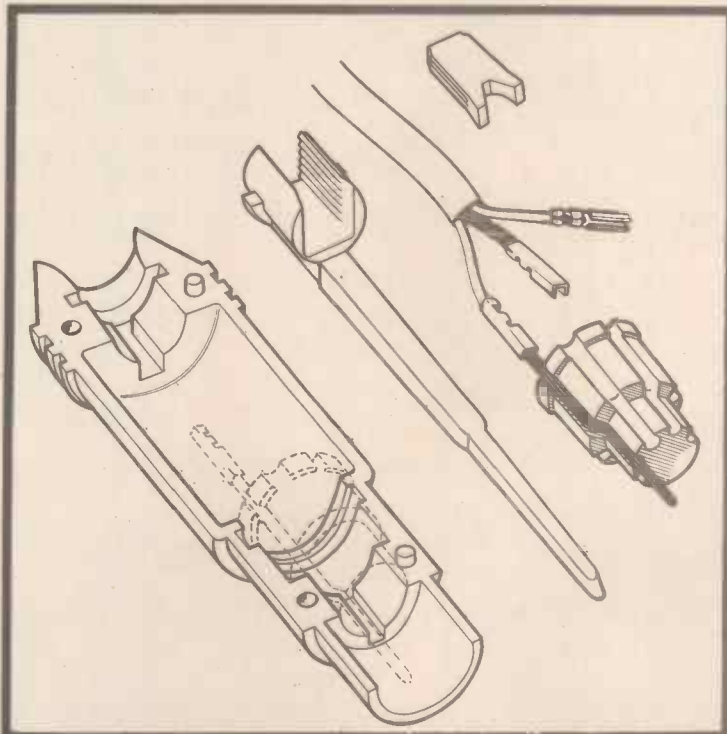

PD Connectors

NO SOLDERING
NO SCREWS
NO MESSING
INTERCHANGEABLE PINS
MATCH ANY CONFIGURATION
2·3·5 PIN STEREO
PRICE 28p

Please forward PD Connector DIN Series Type 235A.

I enclose a P.O. / M.O. / Cheque / Cash for
Price per plug 31p includes postage & packing. Money back guarantee —
Goods must be returned within 14 days.

Colours: Brown Green Blue Red Tick colour req'd.

Name

Address

WW4

PE Parry Electronic Developments Ltd
Assay House 28, Greville Street London EC1N 8SU Telephone 01-242 1100

WW—037 FOR FURTHER DETAILS.

Jack Plugs, 201, 310, 316, 309, 404
 Jack Strips 310, 320, 510, 520, 810
 Line Transformers
 Resistor Lamps and Holders
 Jack sockets 300, 500, 800
 Resistor Bobbins, coils and spools
 Bells and Bell Transformers 6V or 12V
 Low Pass Filters
 U Links and Sockets
 Fuse mountings 4028 and Mounting H.15B.
 Mountings Protector Strip H.40
 Patching and switchboard Cords
 Patch Panels
 Terminal Blocks and Strips
 Uniselectors and Miniature Uniselectors
 Ringing Generators



Large stock of GPO Type Components available for prompt delivery
COMMUNICATION ACCESSORIES and EQUIPMENT LIMITED

77, AKEMAN STREET, TRING, HERTS.

TELEPHONE: TRING 3476.

TELEX: 82362.

WW-038 FOR FURTHER DETAILS

TESTING-TESTING-TESTING

Valves and CRT's

Apart from the larger transmitter types the Model 45D Valve Tester is ready to test just about every electronic valve. Add an adapter and you've got yourself a CRT tester, too. Rapidly detects any normal fault. All told the 45D is invaluable.



Radio and TV Receivers

The Model 68AM Signal Generator covers the frequency range 100kHz to 240MHz entirely on fundamentals and includes a variable level 400Hz signal. Robust and simple to use. Specially designed for radio and TV engineers.



Sweep Alignment of F.M. Receivers

The 62A AM/FM Signal Generator offers swift, accurate and complete facilities for the sweep alignment of r.f., i.f. and discriminator or ratio detector stages of a.m. and f.m. receivers. And that's just one of the many uses of this highly versatile, inexpensive instrument.



YOU AND
Taylor
MAKE A GREAT TEAM

Post to: Taylor Electrical Instruments Limited, Archcliffe Road, Dover, Kent.
 I know Taylor has the name for quality and reliability but I don't know all the facts. Please send me a data sheet on the 45D 68AM 62A-AM/FM (Please tick as applicable)

Name _____

Company _____

Address _____


WW/4

THORN Thorn Measurement Control and Automation Division

WW-039 FOR FURTHER DETAILS

RECORDER AMPLIFIERS

AND INSTRUMENTATION SYSTEMS

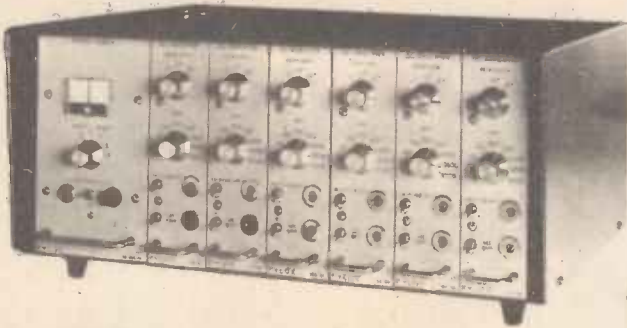

150 series DIFFERENTIAL DC AMPLIFIERS

Wide dynamic range—
high common mode rejection
Low noise, low drift performance
Modular or cased presentation

also

MINI-AMP FE-251-GA differential dc pre-amplifier

Compatible modules and cards ensure ease of application and great flexibility.

FYLDE ELECTRONIC LABORATORIES LIMITED
16 OAKHAM COURT, PRESTON (0772) 57560

WW-040 FOR FURTHER DETAILS

RESISTANCE BOXES

TYPE RBB



A range of robust resistance decades for use in AC or DC networks and measuring systems. They all incorporate the "CROPICO" type SP1 low contact resistance switch and the coils are wound in "Manganin". Standard models are available from stock with 1, 4, 5 or 6 dials.

ACCURACY

±0.1% at the full rated current

Temperature Co-efficient

20 p p m per Degree C

Range


0.0001 ohm to 10 Megohms.

Request full details from:

CROYDON PRECISION INSTRUMENT COMPANY
Hampton Road, CROYDON (Postal Code: CR9 2RU)
Telephone: 01-684 4025 and 4094

WW-041 FOR FURTHER DETAILS

The magnificent seven.

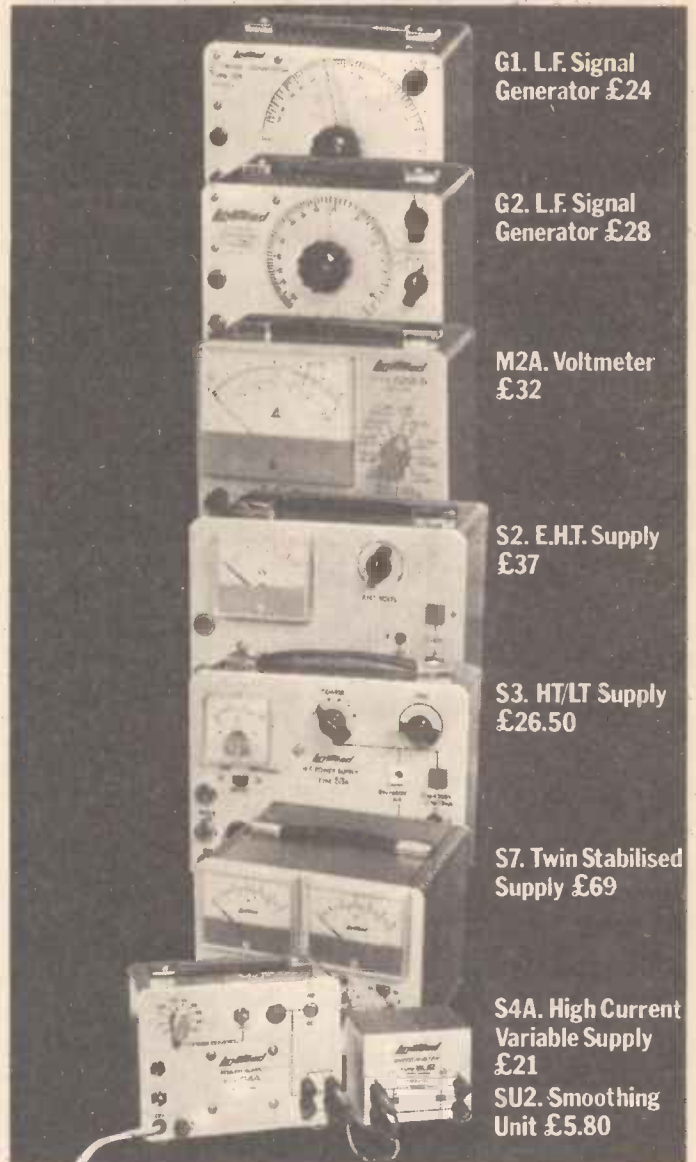

G1. L.F. Signal Generator £24

G2. L.F. Signal Generator £28

M2A. Voltmeter £32

S2. E.H.T. Supply £37

S3. HT/LT Supply £26.50

S7. Twin Stabilised Supply £69

S4A. High Current Variable Supply £21

SU2. Smoothing Unit £5.80

Linstead are the best British made electronic instruments at their price on the market today.

G1. Nuffield Ref. 181. 10Hz to 100kHz. 0-6v. r.m.s. Sine wave. 0-9v. peak to peak Square wave. 0-1 watt into 3 ohms.

G2. Nuffield Ref. 181. 10Hz to 100kHz. Sine Wave 0-6v and 1 watt into low impedance. Square wave 1/2 microsecond rise time. Step attenuator
M2A. 12 A.C. ranges 100 microvolts to 400 volts. Frequency 10Hz-1MHz. 8 D.C. ranges 0 to 400v. Impedance 10 megohms.

S2. Nuffield Ref. 14. 0-6kv. 1 mA at 5kv. Metered. 6.3v at 3A. insulated for operation at E.H.T.

S3. Nuffield Ref. 15. 0 to +300v. to -25v. at 0 to 60mA. 2 insulated outputs at 6.3v. 2A.

S7. 0-30V. 0-1A. per section. Fully protected against overload and short circuit. Outputs floating and can be series or parallel connected.

S4A. Nuffield Ref. 59. 0 to 25v. A.C. and D.C. 0 to 8A 1v. steps. Thermal-magnetic cut-out.

SU2. For use with S4A. Pi-filter 0-4A.


Send me Catalogue about the Magnificent Seven.
Linstead Electronics,
Roslyn Works, Roslyn Road, London N15 5JB.
Telephone: 01-802 5144

NAME
COMPANY
ADDRESS

Linstead
The best for less

WW-042 FOR FURTHER DETAILS


Telford range of Oscilloscope Cameras

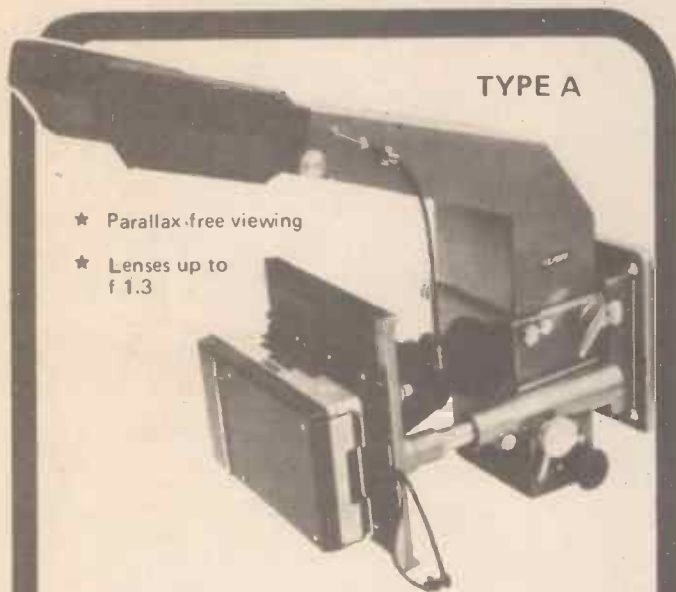

TYPE A

- ★ Parallax-free viewing
- ★ Lenses up to f 1.3

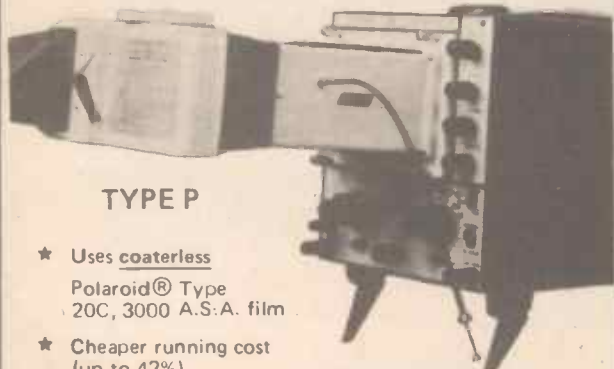Modular system with range of film backs, lenses, viewing systems and adaptors to meet virtually all requirements



TYPE P

- ★ Uses coaterless Polaroid® Type 20C, 3000 A.S.A. film
- ★ Cheaper running cost (up to 42%)
- ★ Lowest purchase price for comparable specification
- ★ Precision Dallmeyer f 4.5 lens
- ★ Inexpensive interchangeable adaptor for most popular scopes

More complete details available on request from:

**Telford
PRODUCTS LTD.**
WADSWORTH ROAD
PERIVALE GREENFORD
MIDDX. ENGLAND
Telephone: 01-998 1011
Telex: 935524

® Reg. Trade Mark.

DAVALL A MEMBER COMPANY OF BENTIMA INDUSTRIES LIMITED

WW-043 FOR FURTHER DETAILS

- PRODUCTION TESTING
- DEVELOPMENT
- SERVICING
- EDUCATION

POWER UNITS

NOW AVAILABLE WITH **3**
VARIABLE OUTPUTS



Type VRU/30/25 — £144.35

Input 200-250V. 50Hz
or 110-120V. 60Hz to order
Output 1: 0-30V. 25A. D.C.
Output 2: 0-80V. 10a. A.C.
Output 3: 0-260V. 4A. A.C.

Other units also available
with outputs of:
0-60V 12A.
0-125V 6A.
0-250V 3A.


ALL CONTINUOUSLY
VARIABLE

SEND FOR FURTHER DETAILS
OF THESE VERSATILE UNITS TO

Valradio LIMITED, BROWELLS LANE,
FELTHAM, TW13 7EN, MIDDLESEX.
TELEPHONE 01 890 4242

WW-044 FOR FURTHER DETAILS

METER PROBLEMS?

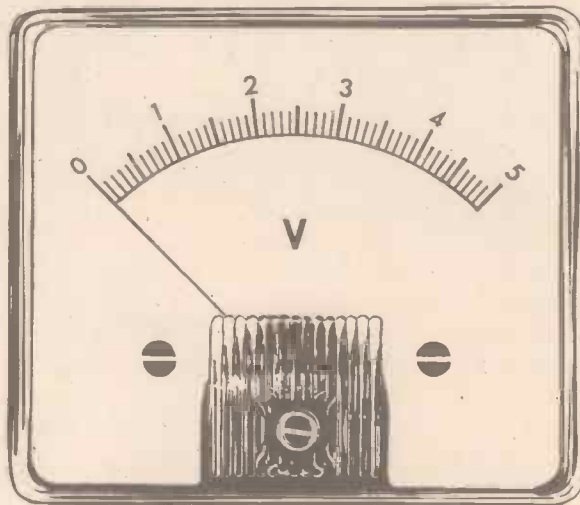

A very wide range of modern design instruments is available for 10/14 days' delivery.

Full Information from:

HARRIS ELECTRONICS (London)
138 GRAYS INN ROAD, W.C.1 Phone: 01/837/7937

WW-045 FOR FURTHER DETAILS

The unequalled amplifiers!

Every lab has at least one amplifier need that only Brookdeal performance *really* measures up to. Which is yours? The '72 lineup is no ordinary family, but a unique array of amplifier talent — exceptional in linearity, low in noise. Two new models extend the frontiers of circuit design even further. Together, the

Brookdeal lineup provides the ideal match to a vast range of signal sources. Tell us the signal *you* need to amplify — we'll send performance details.

Brookdeal Electronics Ltd., Market Street, Bracknell, Berks, England. Telephone 0344 23931 Telex 847164.

Brookdeal



Your special amplifier need?

801A is a special project — a low noise amplifier with 96dB gain in a very small package indeed, for line communications. A customer problem successfully met. Tell us yours. If it's technically feasible, Brookdeal expertise can make it.

432 For high impedance sources

Differential, or single-ended inputs, in an amplifier designed for minimum loading effect on high impedance sources — input impedance 100M Ω and approx. 0.1 pF. Noise figure at 1kHz is < 2dB from 100k Ω source, < 0.5dB from 1M Ω source. Frequency range 1Hz to 1MHz, gain switchable to 20, 40 or 60dB.

450 Versatile low-noise lab amplifier

Really flexible, with switch selected high and low pass filters plus external filter facility. Noise figure very low over wide range of source resistances and frequencies (typ. 4nVrms/ $\sqrt{\text{Hz}}$ at 1kHz). Frequency range 1Hz to 300kHz, gain 18dB to 100dB. Dual input impedance 100k Ω and 50M Ω .

452 Even higher performance, lower noise

Extreme versatility for almost any lab job. Non-linearity typically 0.001%, and lower noise especially at flicker frequencies — typically 13nVrms/ $\sqrt{\text{Hz}}$ at 10Hz. Variable high and low pass filters to 1% accuracy, and instant overload recovery. Frequency range 1Hz to 1MHz, gain 19dB to 100dB, 100M Ω input impedance.

453 High performance lab preamplifier

With intermodulation products typically 0.001%, 453 is the perfect instrument for extending the sensitivity of wave and spectrum analysers, tracking filters and oscilloscopes. Set the gain and forget about it! Extremely low noise typically 19nVrms/ $\sqrt{\text{Hz}}$ at 10Hz. Frequency range 1Hz to 1MHz, gain 19dB to 80dB, 100M Ω input impedance.

431 Preamplifies nanovolt signals

Designed to noise-match very low source resistances — 10 Ω to 1k Ω . Two input modes, frequency range of 1Hz to 100kHz, and 60dB gain. 431 amplifier is battery powered.

Brookdeal worldwide agencies: America Keithley Instruments Inc. Ohio (216) 248 0400. Australia H. Rowe & Co. Pty. Ltd. Melbourne 42/0481. Austria Ing. Wilhelm Thilo, Klagenfurt, 0 42 22 70549. Canada R-O-R Associates Ltd., Ontario 4162917121. Denmark Tage Olsen A/S, Copenhagen 01 294800. Finland Into O/Y, Helsinki 11 123. France Radio Equipments-Antares, Division Electronique, Paris 737 54 80. Germany Keithley GmbH., Munchen 0811 745321. Greece H. Johanides, Athens 818 624. Holland and Belgium Intechmij N.V., The Hague 25 12 12. Israel R.D.T. Electronics Engineering Ltd., Tel-Aviv 266181-2. Italy Vianello S.P.A., Milan 563 081. Japan Toyo Trading Co., Tokyo 279 0771. New Zealand Sample Electronics (NZ) Ltd., Auckland 667-356. Norway Norsk Marcopikompani A/S, Oslo 67 04 86. South Africa Radiokom (1969) Pty. Ltd., Braamfontein 48 5712. Spain Payma S/L, Madrid 2153941. Sweden T&I Inter A.B., Stockholm 0864 18 00. Switzerland Fritz Weber, Zurich 051 85 4444.




MAKE BIG REDUCTIONS WITH JACKSON



CATALOGUE NO. 5870

The Jackson Friction Ball Drive Reduction Unit is unique. Simply because it's the only one of its type and size available in the United Kingdom. It has sealed lubrication, with a hardened steel shaft and bearings to give it extra long life. And it's low in price. The unit has a 10:1 reduction ratio, with an output torque of 8 oz. ins. minimum.

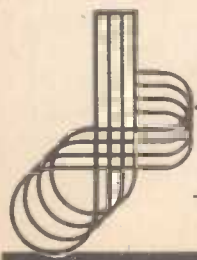Our skilled personnel can produce custom made components to suit your individual needs. And with 45 years of experience your guarantee is our reliability.



Write for fully illustrated catalogue:


JACKSON BROTHERS (LONDON) LIMITED

KINGSWAY, WADDON, CROYDON, CR9 4DG.
TEL: 01-681 2754/7 U.S. OFFICE: M. SWEDGAL,
258 BROADWAY, NEW YORK, N.Y. 10007.

WW-047 FOR FURTHER DETAILS

BULGIN

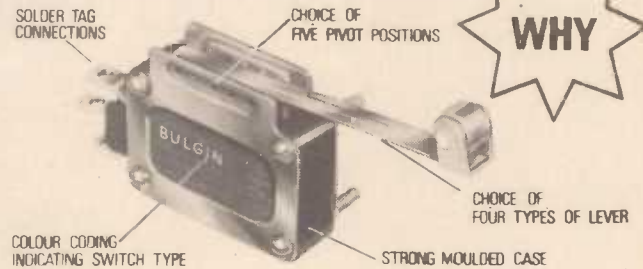Precision Micro-Switches
Repeat Orders Follow
Year After Year



BRITISH PATENT No. 738422. USA PATENT No. 2828372

A CHOICE OF OVER 75 TYPES



List Number S.502/Reset

List Number S.506/RB



List Number S.720

List Number S.520—S.528

SUB MINIATURE TYPES



List Number S.800

List Number S.800/L

List Number S.801/Z

OPEN BLADE TYPE



List Number S.690—S.691

List Number S.735—S.739

WE have undeniable evidence from two famous manufacturers that Bulgin Micro Switches incorporating the original "Rolling Spring Action" were selected for use in their equipment after life tests had been made on all other makes. Reliability was of utmost importance.

WE are constantly receiving repeat orders from certain firms who standardised our switches over 20 years ago.


THE use of just one component which fails at a critical moment can cost a lot of money in servicing and have most serious consequences.

WE do take every care by most exacting tests of every individual switch so that the chances of failure are reduced to a minimum.

OUR components might cost a little more, but realistic companies know from experience the constant quality control we keep on all components made by the House of Bulgin.

CUSTOMERS CAN ALWAYS RELY ON
'THE HOUSE OF BULGIN' FOR SERVICE, QUICK DESPATCH
AND GUARANTEED SUPPLIES FOR YEARS TO COME

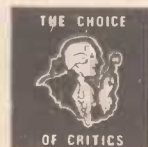TECHNICAL LITERATURE AVAILABLE ON REQUEST. QUOTE WW/4/72




A. F. BULGIN & CO LTD

ELECTRONIC COMPONENT MANUFACTURERS
BYE-PASS ROAD · BARKING · ESSEX
TEL.: 01-594 5588 (12 lines) TELEX 897255

WW-048 FOR FURTHER DETAILS

OMRONS MIGHTY MIDGETS

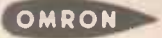

Process Control



STPYMH
Panel Mounting Timer
Exclusive plug-in connection. Times up to 24 hours.



STPNH
Plug-in Timer
Smallest electromechanical type available. Times up to 24 hours.



TDA
Automatic Recycling Timer
Fully solid state. Variable ON/OFF. Times to 60 secs.



61FGP
Plug-in Floatless Switch
Fully solid state with relay output. Lowest cost unit available in United Kingdom.



WL-10-FNJ
Limit switch
Sealed coil spring. Full range available.



VAQ4
Pushbutton Switch
Attractive button and reliable switch. New low prices.



C5G3
Rotary Microswitch for coin-op mechanisms.




S1A
One of the smallest microswitches available.

EX-STOCK DELIVERY ALWAYS

PRICES

Average prices for reasonable quantities are shown	STPYMH	£7.00	WL-10-FNJ	£3.50
	STPNH	£6.50	VAQ4	27p
	TDA	£19.00	C5G3	40p
	61FGP	£4.50	S1A	17p

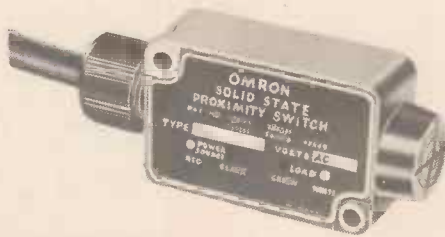VARIABLE TRANSFORMERS ARE ALWAYS AVAILABLE FROM STOCK AT THE LOWEST PRICES




SOLID STATE PROXIMITY SWITCH
low cost : high performance
ex-stock delivery : DC operation
OMRON proximity switch type TL-2-GPA senses all ferrous and non-ferrous metals and provides output of .4A.
Detects presence of metals up to 5.5mm from the protruding head. Works direct from 24VDC supply to switch AC or DC loads. No ancillary components are necessary for metal sensing
PRICE EACH £9.50 FROM STOCK



Fully shrouded variable transformers — input 240VAC output 0-260VAC
1 amp £7.00 10 amp £22.50
2.5 amp £8.05 12 amp £23.60
5 amp £11.75 20 amp £49.00
8 amp £15.90
Supplied complete with mounting brackets for bench and panel mounting.



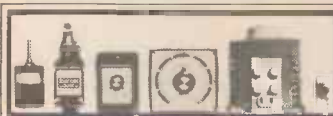New solid state variable voltage control
input 240VAC output 25-240VAC
5 amp £9.50
10 amp £15.20
Substantial quantity discounts available



IMO. PRECISION CONTROLS LTD.

**313 Edgware Rd., London W.2
Telephone 01-723 2231**

Three New Faces from DYNAMCO




- NEW 7060**
Precision T.V. waveform monitor.
- Combined waveform and picture monitor.
 - All line standards (including CCTV).
 - Odd & Even field selection.
 - Pulse & Bar overlay (same field).
 - 75 Ω and 1 M Ω switched attenuators.
 - Post Office TV test set Type 13B



- NEW 72 SERIES**
The On-Site commissioning/servicing scope.
- Light/Rugged/Compact.
 - High Brightness for Low Occupance Signals.
 - Dual Channel 15 MHz/Signal delay.
 - Full delayed sweep/delay gate timebase with two trigger inputs.
 - Post Office Oscilloscope Type 14A.



- NEW 7130**
Wideband extension of 71 Series Oscilloscopes.
- 50 MHz Dual Channel plug-on amplifier.
 - 100 MHz High writing speed display unit.
 - Full delayed sweep/Gate timebase module.
 - True dual trigger inputs/Unrestricted trigger source selection.
 - Complete compatability with all 71 Series modules.


 East Mains Industrial Estate,
Broxburn, West Lothian, Scotland
DYNAMCO Telephone: Broxburn 2631 Telex: 72174

WW—050 FOR FURTHER DETAILS

ENCAPSULATION —

low tool cost method for cylindrical coils and potting. Enquiries also for—

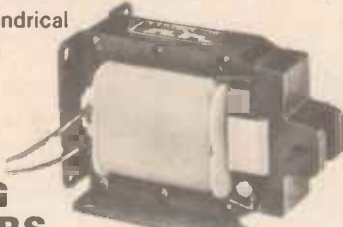**REED RELAYS
SOLENOIDS
COIL WINDING
TRANSFORMERS
to 10 k.V.A.**



Solenoid SRM.
7 lbs to 14 lbs at 1½"

R. A. WEBBER LTD.
Knapps Lane, Bristol 5. 0272 657228

WW—051 FOR FURTHER DETAILS

PARKER SHEET METAL FOLDING MACHINES



Forms channels and angles down to 45 degrees which can be flattened to give safe edge. Depth of fold according to height of bench.

BENCH MODEL

36" × 18 gauge capacity.....	£35.00
24" × 16 gauge capacity.....	£32.00
Carriage Free	

One year's guarantee.
Money back if not satisfied.

Send for details:

A. B. PARKER

FOLDING MACHINE WORKS,
UPPER GEORGE STREET,
HECKMONDVIKE, YORKS.

Telephone 3997

Also the well-known vice models of

36" × 18 gauge capacity.....	£15.00
24" × 18 gauge capacity.....	£12.00
18" × 16 gauge capacity.....	£12.00
Carriage Free	

WW—52 FOR FURTHER DETAILS

cut contact wear and tear with

ELECTROLUBE
REGD
contact lubricants



the trouble shooter range

The life of all types and sizes of electrical contacts is greatly extended with Electrolube lubricants—specially developed to loosen tarnish, inhibit arcing and maintain reliable contact performance. In aerosols, bulk containers, and other convenient packaging.

Also Contact Cleaning Strips, Freezer, Silicone Grease, Printed Circuit Lacquer, Preclène.
Write for technical data sheet.


Electrolube Ltd,
Slough, Bucks, England. Tel: Slough 25574

WW—053 FOR FURTHER DETAILS

E55 CONNECTORS



For the want of a nail . . .

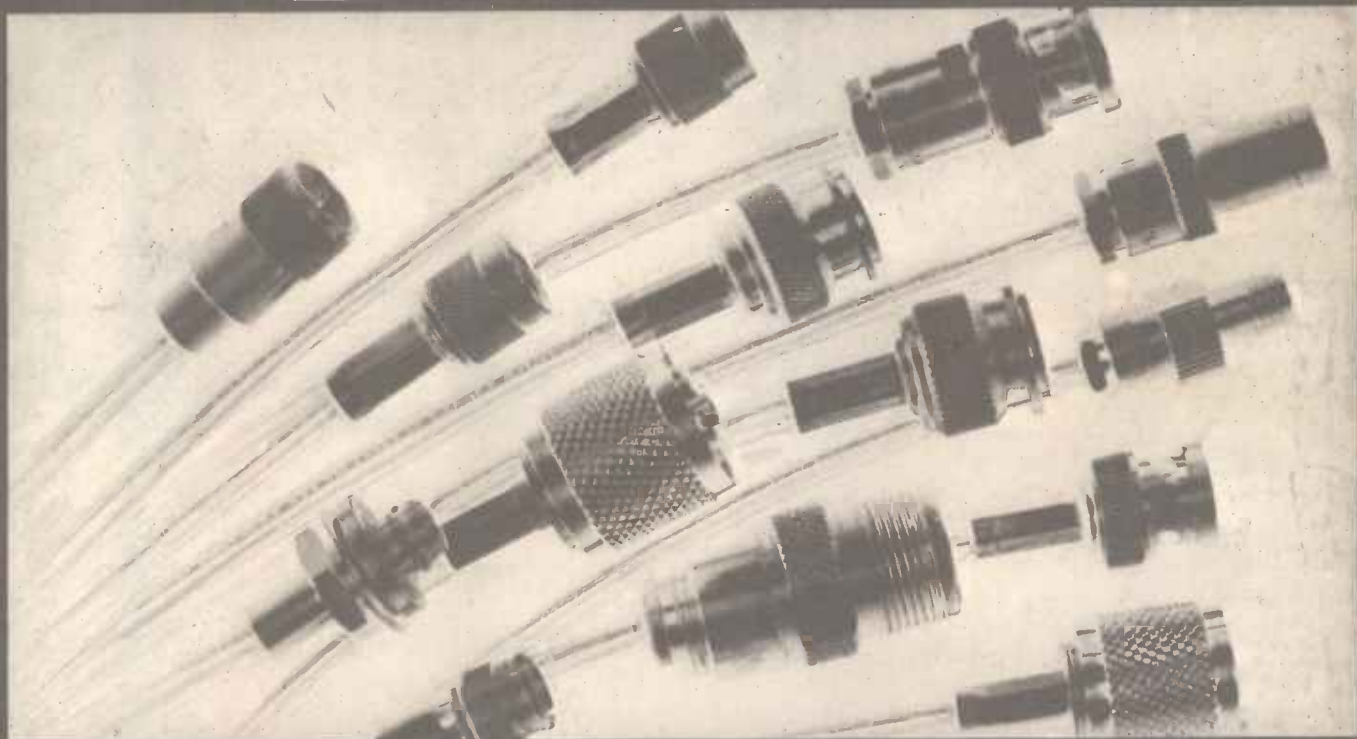

. . . for the want of a connector
... a contract was lost!

Transradio care about delivery

We can supply ex-stock from a large variety of R.F. connectors and cables.

Quality

We regard quality as our No. 1 aim, our quality control is second to none.

Problems

We have a design team that can deal with your special requirements, from mini lines to large connectors of up to 2 MW.

Prices

We have just reduced our R.F. cable prices considerably and are constantly reviewing connector prices. Quantity prices can be negotiated.

You can rely on Transradio

We have been 30 years in the business and know a thing or two.

A wide range of connectors is always available.

When your need is for precision connectors you cannot do better than come to us.

If you haven't yet received our catalogues drop us a line and we will put one in the post.

Suppliers to all the important people.

Aren't you important too?

Just pick up the phone — we're waiting to help you . . .

Contractors to the Industry, the Post Office, Armed Services, Broadcasting & Television Authorities.



RF Connectors, Cables and Cable Assemblies

Transradio Ltd. 183 Park Avenue London NW10 · Phone: 01-965 6281 Telex: 923004

Subsidiary of Felten & Guillaume Kabelwerke A. G. KOLN-MULHEIM

THE GUARANTEED

Canterbury Audio

VALUE FOR MONEY PRODUCTS

FOR PROMPT DELIVERY

HIGH EFFICIENCY

HIGH DAMPING

HIGH FIDELITY

SPEAKER ENCLOSURES

- FREQUENCY RESPONSE 29-21000HZ
- POWER HANDLING UP TO 25 WATTS

**SONEX 72
SPECIAL
OFFER**

FROM MARCH 22
TO MAY 1 ONLY

25% DISCOUNT

on complete set as
advertised with either
pair of speakers

31" x 11½" x 13¼"

£39.60 EACH

31" x 13½" x 13¼"

£39.60 EACH

21" x 11½" x 13¼"

£19.60 EACH

21" x 13½" x 13¼"

£19.60 EACH

PURCHASE TAX INCLUDED
IF APPLICABLE

**FINISH IN TEAK
OR WHITE**

CARRIAGE, PACKING & INSURANCE £1.50 LARGE, £1.00 SMALL

CANTERBURY AUDIO, 4 Station Rd., West Canterbury, Kent, England
Telephone: Canterbury 60431


FOR PROMPT DELIVERY

Canterbury Audio

PROFESSIONAL MODULAR CONSTRUCTION STEREO AMPLIFIER

ASSEMBLY

CA STEREO 80

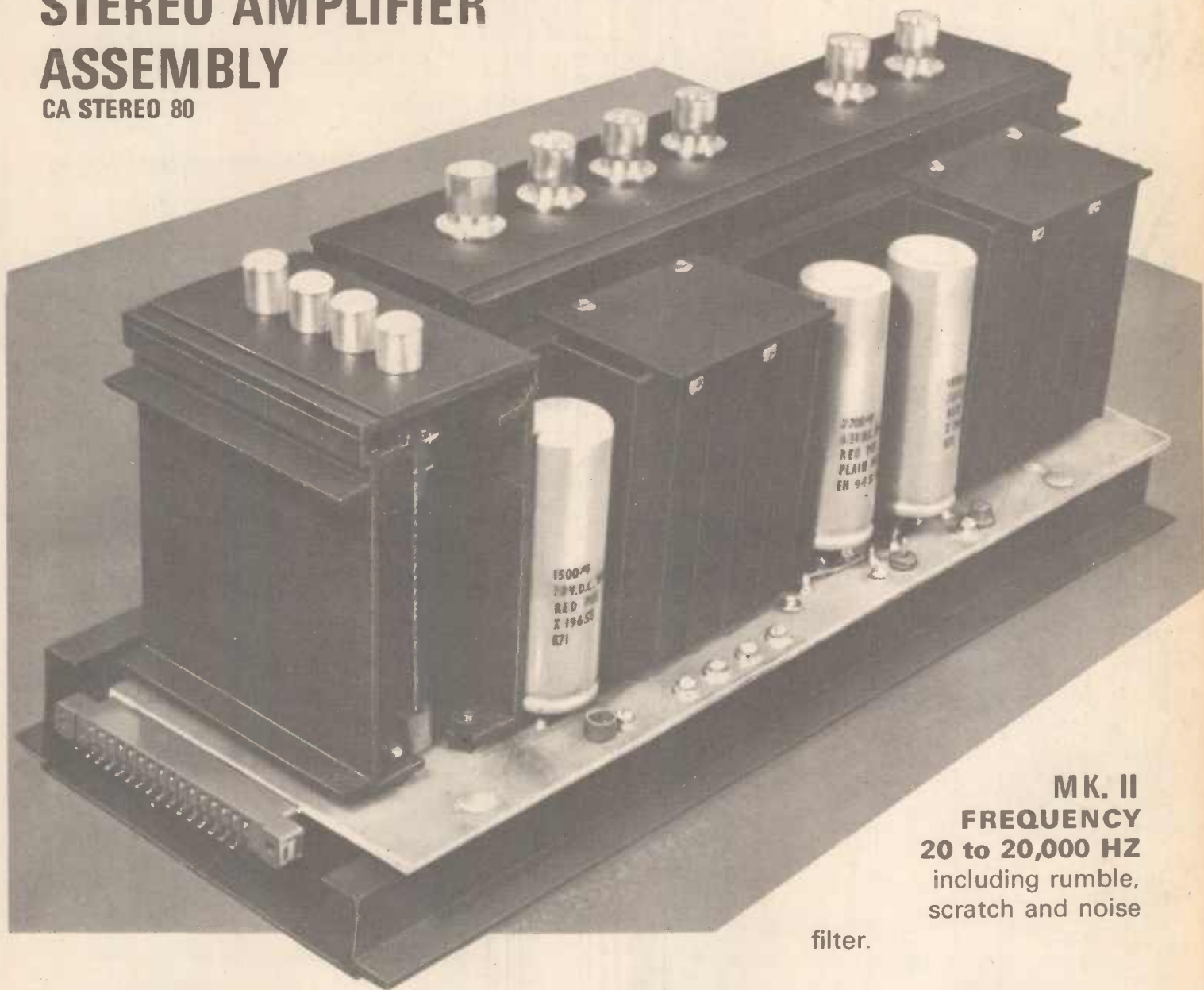

**MK. II
FREQUENCY**
20 to 20,000 HZ
including rumble,
scratch and noise

filter.

● EXCEPTIONALLY

low background noises, and hum. Power output up to 40 watts per channel into 4Ω load.

Stabilised power supplies
£6.95
10 watts per channel.

● READY FOR USE

Mk. I — same as above, but with input selector on pre-amplifier board with the power supply — £38.90. Mk. II with the power supply — £40.40.

BASIC PRICES, WITHOUT POWER SUPPLY — Mk. I £31.95 — Mk. II £33.45

**AMPLIFIER UNIT IN CABINET WITH POWER SUPPLY AND TURNTABLE ALSO AVAILABLE
CARRIAGE, PACKING AND INSURANCE: POWER SUPPLY 50p. AMPLIFIER 75p. BOTH £1.25**

CANTERBURY AUDIO, 4 STATION ROAD, WEST CANTERBURY, KENT, ENGLAND. Telephone: CANTERBURY 60431

WW—055 FOR FURTHER DETAILS

CAN YOU READ THIS AD WITHOUT TURNING THE PAGE?



If you spend any time servicing or testing logic using a scope, you'll be used to neck twisting like this. Why not take a look at our solution to the problem? Our P50 series Logipen weighs a few ounces, is six inches long, and is now in use through-out industry and government departments;

TWIN SOLID STATE LAMPS display logic levels, open circuits, pulse trains, clocks and single pulses of either polarity down to 30ns.

TWO PRECISION THRESHOLD DETECTORS monitor the input signal ensuring only valid logic levels are displayed as such. Standard settings for TTL are:—

0 - 0.4 volt; LO lamp on. 0.4 - 2.4 volt; neither lamp on. 2.4 - 5 volt; HI lamp on.

PUSHBUTTON enables capture and display of brief pulses down to 30nanoseconds

POWER REQUIREMENT less than 30mA, at 5 volts; power leads terminated in crocodile clips or sockets to fit a chip clip.


CIRCUIT LOADING less than 50uA, at thresholds. Screw-in replaceable probe tip and tip adaptor are gold plated.

NO SERVICING OR SETTING UP - NO LAMP CHANGING - INSTANT READOUT

And the price? - just £20 - Sale or return. Also 10V, 12V & 15V versions and specials made to order. Use the reader reply card NOW for full data sheet.

pe CONSULTANTS

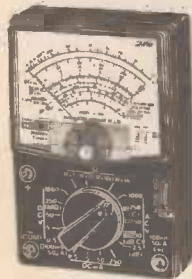8 Trafalgar Court, Trafalgar road
Southampton, Hants; SO1 3RY
(0703) 32874



MODEL U-50DX

SANWA MULTI TESTERS

USED THROUGHOUT THE WORLD, SANWA'S EXPERIENCE OF 30 YEARS ENSURES ACCURACY, RELIABILITY, VERSATILITY, UNSURPASSED TESTER PERFORMANCE COMES WITH EVERY SANWA 6 Months' Guarantee Excellent Repair Service

Model P-2-B	£5.25	Model AT-45	£16.95
Model JP-5D	£6.30	Model 380-CE	£17.20
Model 360-YTR	£8.90	Model N-101	£20.00
Model U-60DX	£9.00	Model 460-ED	£23.40
Model A-303TRD	£11.85	Model EM-700	£45.96
Model K-30THD	£13.55	Model R.1000CB	£59.25
Model E-80TRD	£14.75		

Cases available with most meters

Please write for illustrated leaflet of these and other specialised Sanwa meters

SOLE IMPORTERS IN U.K. QUALITY ELECTRONICS LTD.

47-49 HIGH STREET, KINGSTON-UPON-THAMES, SURREY. KT1 1LP
Tel: 01-546 4585

WW-057 FOR FURTHER DETAILS

TRIANGLE DIGITAL SERVICES 13, PARK ROAD, LONDON N.W.4.



£69

COUNTER-TIMER-FREQUENCY METER

TRIPLE POWER SUPPLY, +12V +5V -12V (1 AMP) £49
MILLIVOLTMETER £19
ELECTRONIC THERMOMETER £21

Customised instruments and test systems will be quoted without any implied obligation.

WW-058 FOR FURTHER DETAILS



Si451 Millivoltmeter

★ 20 ranges also with variable control permitting easy reading of relative frequency response

£35.00

JES AUDIO INSTRUMENTATION

Illustrated the Si453 Audio Oscillator

SPECIAL FEATURES:

- ★ very low distortion content—less than .05%
- ★ an output conforming to RIAA recording characteristic
- ★ battery operation for no ripple or hum loop
- ★ square wave output of fast rise time

£40.00

also available

Si452 Distortion Measuring Unit

★ low cost distortion measurement down to .01% with comprehensive facilities including L.F. cut switch, etc.

£30.00

J. E. SUGDEN & CO. LTD., CARR STREET, CLECKHEATON, YORKS. BD19 5LA. Tel: 09762-2501

WW-059 FOR FURTHER DETAILS

CONSTRUCT YOUR OWN COLOUR TV RECEIVER



Starting in the April
issue of *Television*
this outstanding series

gives full constructional details of a
modern single-standard full PAL specification
colour receiver.


In addition to complete constructional details, arrangements have been made for easy supply of all components required, including printed circuit boards. Special features of this 22in. set include: Strong simply-made cabinet. Printed circuit board construction. Front pull-out draw containing all convergence controls for easy adjustment. Optional built-in crosshatch generator. Choice of varactor or conventional tuner. Automatic frequency control. RGB tube drive. Latest 22 in. Mazda flat-face square-corner tube. Delay-line PAL decoder. Fully integrated sound channel (using two i.c.s.), intercarrier amplifier and audio output.

MAKE SURE YOU DON'T MISS IT . . .
IT'S THE FIRST CONSTRUCTIONAL SINGLE-STANDARD
COLOUR TELEVISION RECEIVER USING RGB DRIVE
TO BE PUBLISHED IN A MAGAZINE

TELEVISION

APRIL ISSUE (on sale March 20) 20p
Order from your newsagent TODAY!

THE POINT FIVE-TWO C STUDIO CONSOLETTA

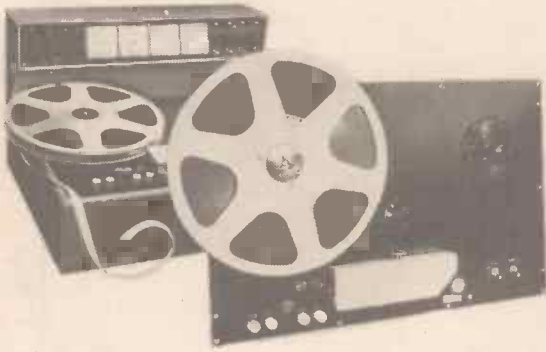

THE COMPLETE, FOUR CHANNEL, HALF INCH TAPE RECORDER

Table-top mounting, fully remoteable, solenoid actuation. Balanced inputs, 600 ohm, 0 dbm. Balanced or unbalanced outputs, 600 ohm, 0 dbm with reserve to +19 db. Cannon connectors throughout. 20 to 18,000 cps, NAB equalisation (DIN or CCIR on special order). Sel-sync with switch patching. Full A-B monitoring. Plug-in circuitry, heads, relays, solid state controls, motors. Employs the JSR .52 Tape Transport with reel diameters to 11.5 inches. Available for $\frac{1}{4}$ inch tape, for monaural and stereo broadcast and for master tapes.

Prices and literature from:—

JOHN STEED RESEARCH LTD.,

220 Edgware Road,
London, W.2, England.

Phone: 01-723 5066

WW—060 FOR FURTHER DETAILS

TELEPRINTERS · PERFORATORS REPERFORATORS · TAPEREADERS DATA PROCESSING EQUIPMENT

SALE OR HIRE



**2-5-6-7-8 TRACK AND
MULTIWIRE EQUIPMENT**

Special Codes Prepared



**TELEGRAPH AUTOMATION AND COMPUTER PERIPHERAL ACCESSORIES
DATEL MODEM TERMINALS, TELEPRINTER SWITCHBOARDS**

Picture Telegraph, Desk-Fax, Morse Equipment; Converters and Stabilised Rectifiers; Line Transformers and Noise Suppressors; Tape Holders, Pullers and Fast Winders; Governed, Synchronous and Phonic Motors; Teleprinter Tables and Cabinets; Silence Covers; Distortion and Relay Testers; Send/Receive Low and High Pass Filters; Teleprinter, Morse,

Teledelts Paper, Tape and Ribbons; Polarised and specialised Relays and Bases; Terminals V.F. and F.M. Equipment; Telephone Carriers and Repeaters; Diversity; Frequency Shift, Keying Equipment;

Racks and Consoles; Plugs, Sockets, Key, Push, Miniature and other Switches; Cords, Connectors, Wires, Cables, Jack and Lamp strips, and Switchboard Accessories; Teleprinter Tools; Stroboscopes and Electronic Forks; Cold Cathode Matrices; Test Equipment; Miscellaneous Accessories, Teleprinter and Teletype Spares.



TELEPRINTER EQUIPMENT LTD.

Gaiety Works, Akeman Street, Tring, Herts

Tel: Tring 3476 (STD 0442 82)

Cables: RAHNO TRING

Telex: 82362, A/B BATEY TRING

WW—062 FOR FURTHER DETAILS

A match made by Hatfield



An extensive range of High Power impedance matching transformers is available on quick delivery from Hatfield Instruments. The range of H.F. Transformers covers P.E.P. ratings of 400W, 1.5KW, 3KW and 5KW.

The 6000 Series offers the most efficient means of coupling transmission systems of dissimilar characteristic impedances operating within the H.F. communications band. They are suitable for exterior mounting or in a transmission hall. All types are waterproof, can be pressurised, and are completely corrosion-resistant.

Send for full details of Hatfield High Power Transformers and a copy of our Short Form Catalogue.

HATFIELD

forward thinking
in electronics

HATFIELD INSTRUMENTS LIMITED

Burrington Way, Plymouth PL5 3LZ, Devon.

Tel. Plymouth (0752) 72773/4 Grams: Sigjen, Plymouth. Telex: 45592

South-East Asia: for prompt service and deliveries, contact:

Hatfield Instruments (NZ) Ltd., P.O. Box 561, Napier, New Zealand.

WW—061 FOR FURTHER DETAILS

240° of shadowless readings. That's the Taylor Fyneline 'Wide Angle' range.



Meet Taylor's new range of 'Wide Angle' panel meters. The 240° circular scale offers scale lengths of approximately twice that of similar 90° movements.

Model 38, illustrated here, is the smallest in the range with the scale length of $4\frac{3}{8}$ in. and a panel width of little more than $2\frac{1}{2}$ in. Find out more about the complete Fyneline range including our 'Standard' and 'Picture Frame' models. Write for data sheet now.

Taylor


Taylor Electrical Instruments Ltd.,
Archcliffe Road, Dover, Kent.
Telephone: Dover 2634 Telex: 96283

Thorn Measurement Control and Automation Division.

THORN

WW—063 FOR FURTHER DETAILS

COLBERT WORK POSITIONERS - 300 SERIES

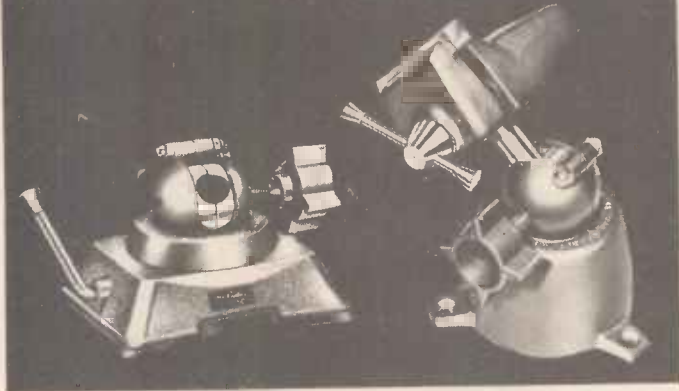

Colbert Pana-Vise WORK POSITIONERS are specially designed to quickly and easily achieve the most CONVENIENT, COMFORTABLE and TIME-SAVING work position. Available with vacuum clamp or screw-on base. They can be ROTATED, TIPPED, TILTED.

ANGLED, ELEVATED, LOWERED. The required work position is firmly secured with a patented ONE KNOB CONTROL, a unique feature of COLBERT POSITIONERS. A series of special holders is available for various types of work. Full details available on request.

Distributors:

Special Products Distributors Limited

81 Piccadilly, London, W.1. Tel: 01-629 9556

Cables: Specipro London
(made in U.S.A.)

WW-064 FOR FURTHER DETAILS



If you think closed circuit television is complicated, come to Dixons

As distributors of every famous name in TV equipment, Dixons can offer you totally unbiased advice on every problem connected with CCTV. The service we offer is complete: consultation, quotation, supply and installation. Come to our showrooms and we'll show you the very latest equipment in this field. From ITC mini-CCTV at £99.95 for a camera and monitor to a comprehensive system selling at £50,000.

When you've chosen the system best suited to your requirements, we can offer you a choice between outright purchase, contract hire, hire purchase and short term rental. Our full-time staff technicians will check the equipment you buy before installation and give you unbeatable after sales service. So don't make a move in CCTV without us. Call in or send us the coupon for more information or a particular quotation. Or phone us at 01-437 8811.

TO: Dixons CCTV Ltd., 3 Soho Square, London W.1.

I am interested in CCTV.
Please send me details by return of post.

NAME

ADDRESS

Main agents
for Memorex
video tape



WW-065 FOR FURTHER DETAILS

JAMES SCOTT

SALE OF SURPLUS ELECTRONIC EQUIPMENT
The following items are available for immediate delivery at very competitive prices—
A more comprehensive list is available on application

NEWMARKET PACKAGED AUDIO AMPLIFIERS IN MANUFACTURER'S BOXES.

PC9 Supply voltage 9 Volts D.C. Output power 1 Watt
8Ω Price £2.00 each




PC9 High to Low Impedance Matching Pre-amplifier.
Supply Voltage 9 Volts D.C. Input Impedance 1MΩ
Output Impedance 2KΩ
Frequency response 20HZ-20KHZ Distortion (Typical) 1%
Price £0.50



NEWMARKET MODULAR POWER SUPPLIES BRAND NEW IN MANUFACTURER'S BOXES

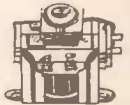PC101 Supply Voltage 220-250V A.C. Output Voltage
9 Volts D.C. at 100MA Price £1.15 each



PC102 Supply Voltage 220-250V A.C. Output Voltages:
21 Volts D.C. at 330MA
21 Volts A.C. at 540MA
Price £2.00




NEWMARKET TRANSISTORS

NKT 351	73p	NKT 12329	27p	2N 2222	18p	NKT 218	23p
NKT 352	25p	NKT 12429	27p	NKT 12	30p	NKT 221	30p
NKT 406	60p	NKT 13329	27p	NKT 72	25p	NKT 222	18p
NKT 420	£1.80	NKT 13429	27p	NKT 73	22p	NKT 223	25p
NKT 450	30p	NKT 16229	27p	NKT 121	21p	NKT 224	22p
NKT 603	22p	NKT 20329	29p	NKT 124	28p	NKT 227	25p
NKT 613F	28p	NKT 80111	65p	NKT 125	38p	NKT 237	29p
NKT 674	30p	NKT 80113	98p	NKT 128	35p	NKT 238	16p
NKT 677	18p	NKT 80125	80p	NKT 127	23p	NKT 249	29p
NKT 713	27p	BC 107	8p	NKT 128	18p	NKT 261	19p
NKT 734	24p	BC 108	8p	NKT 129	22p	NKT 270	18p
NKT 736	30p	BCY 70	13p	NKT 135	24p	NKT 271	16p
NKT 773	23p	BFY 51	17p	NKT 137	30p	NKT 272	15p
NKT 0216	20p	BSY 95A	10p	NKT 142	48p	NKT 273	18p
NKT 3055	23p	2N 697	13p	NKT 143	48p	NKT 274	16p
NKT 6917	27p	2N 706	8p	NKT 212	23p	NKT 275	21p
NKT 10339	23p	2N 914	15p	NKT 213	23p	NKT 278	18p
NKT 10419	17p	2N 918	28p	NKT 214	21p	NKT 301	70p
NKT 10439	25p	2N 930	22p	NKT 215	19p	NKT 302	85p
NKT 10519	20p	2N 1990	22p	NKT 217	48p	NKT 303	70p
						NKT 304	76p

S. T. C. RELAYS — BRAND NEW



TYPE	CONTACT FORM	NOMINAL COIL VOLTAGE	COIL RESISTANCE (OHMS)	PRICE EACH
250 ARO	4 CHANGEOVER	6V D.C.	52	£0.68
250 AMO	4 CHANGEOVER	12V D.C.	185	£0.68
250 ABO	4 CHANGEOVER	48V D.C.	2,500	£0.68
250 GJO	2 CHANGEOVER H.D.	12V D.C.	185	£0.68
250 GEO	2 CHANGEOVER H.D.	48V D.C.	2,500	£0.68

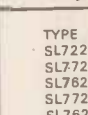

TYPE	CONTACT FORM	COIL VOLTAGE	SWITCHING CURRENT	PRICE EACH
SL7222212	3 Pole On/Off	12V A.C.	10A @ 440V AC	£1.00
SL721215	3 Pole C/O	12V D.C.	10A @ 440V AC	£1.00
SL7822715	2 Pole C/O	220V A.C.	10A @ 440V AC	£0.87
SL722715	3 Pole C/O	220V A.C.	10A @ 440V AC	£1.00
SL7621215	2 Pole C/O	12V D.C.	10A @ 440V AC	£0.87




TYPE	CONTACT FORM	COIL VOLTAGE	COIL RESISTANCE	PRICE EACH
SP 13372	Single Pole C/O	6V D.C.	140Ω	£0.40
SP 13366	Single Pole C/O	12V D.C.	350Ω	£0.40
11301D.	Single Pole C/O	8V D.C.	875Ω	£0.40

UNISELECTOR SWITCHES

6 Bank 25' Way. 75 Coil 50V D.C. Operation. Mounted on Modular Type Chassis with front panel containing 20 Illuminated Push Button Switches. Completely wired for operation.

Price £15
P&P £0.55

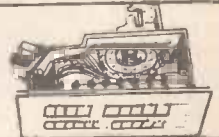

AUTOMATIC CYCLER UNIT

This unit generates stepping pulses (50 Volts D.C.) at intervals of 6 pulses per min. to 120 pulses per Min — continuously variable. Can be used for Automatic Stepping of one or more uniselector switches shown above.

Price £12.50
P&P £0.45

NEWMARKET PACKAGED AUDIO AMPLIFIER

PC10 Magnetic replay head amplifier supply voltage 9 volts D.C.
Input Impedance 150

Price £1.20 each
P&P £0.10

WE HAVE A LARGE RANGE OF CAPACITORS & RESISTORS. PLEASE SEND A STAMPED AND ADDRESSED FOOLSCAP ENVELOPE FOR YOUR CATALOGUE

POST & PACKING OVER £2 — FREE, OVER £1 & UNDER £2 — 15p, UNDER £1 — 10p UNLESS SPECIFICALLY MENTIONED

JAMES SCOTT (ELECTRONIC ENGINEERING) LIMITED
CARNTYNE INDUSTRIAL ESTATE, GLASGOW E.2.
TEL: 041-778 4206

WW-066 FOR FURTHER DETAILS

Enhancing our image

In 1969 Telequipment introduced the D53S which was universally acclaimed as the world's first realistically-priced true dual-beam storage oscilloscope. Now Telequipment announce the DM53A - with all the features of the D53S and the added advantages of variable enhancement and the remote control of Erase and single shot time base Reset.

The tube circuitry provides five alternative conditions of operation:

- (a) Normal: P31 characteristics as in a conventional non-storage oscilloscope.
- (b) Variable Persistence: Provides continuous control from 0.2 second to more than 1 minute.
- (c) Storage (without enhancement): As a storage oscilloscope, it is capable of storing traces for periods of up to 10 minutes.
- (d) Store (with variable enhancement): The writing speed may be increased up to about ten times.
- (e) Hold: Retention time of image written in the store condition is prolonged up to one hour.


A choice of differential, ultra high gain, or wide band with Signal Delay plug-in Y amplifiers, makes the DM53A capable of meeting almost any measurement requirement.

Send for full details now and see just how great is the value offered in the Telequipment DM53A. U.K. Prices: £490-£556, depending on choice of amplifiers.

TEKTRONIX U.K. Ltd. Telequipment Sales,
Beaverton House P.O. Box 69 Harpenden, Herts.
Tel: Harpenden 61251 Telex: 25559



WW-067 FOR FURTHER DETAILS

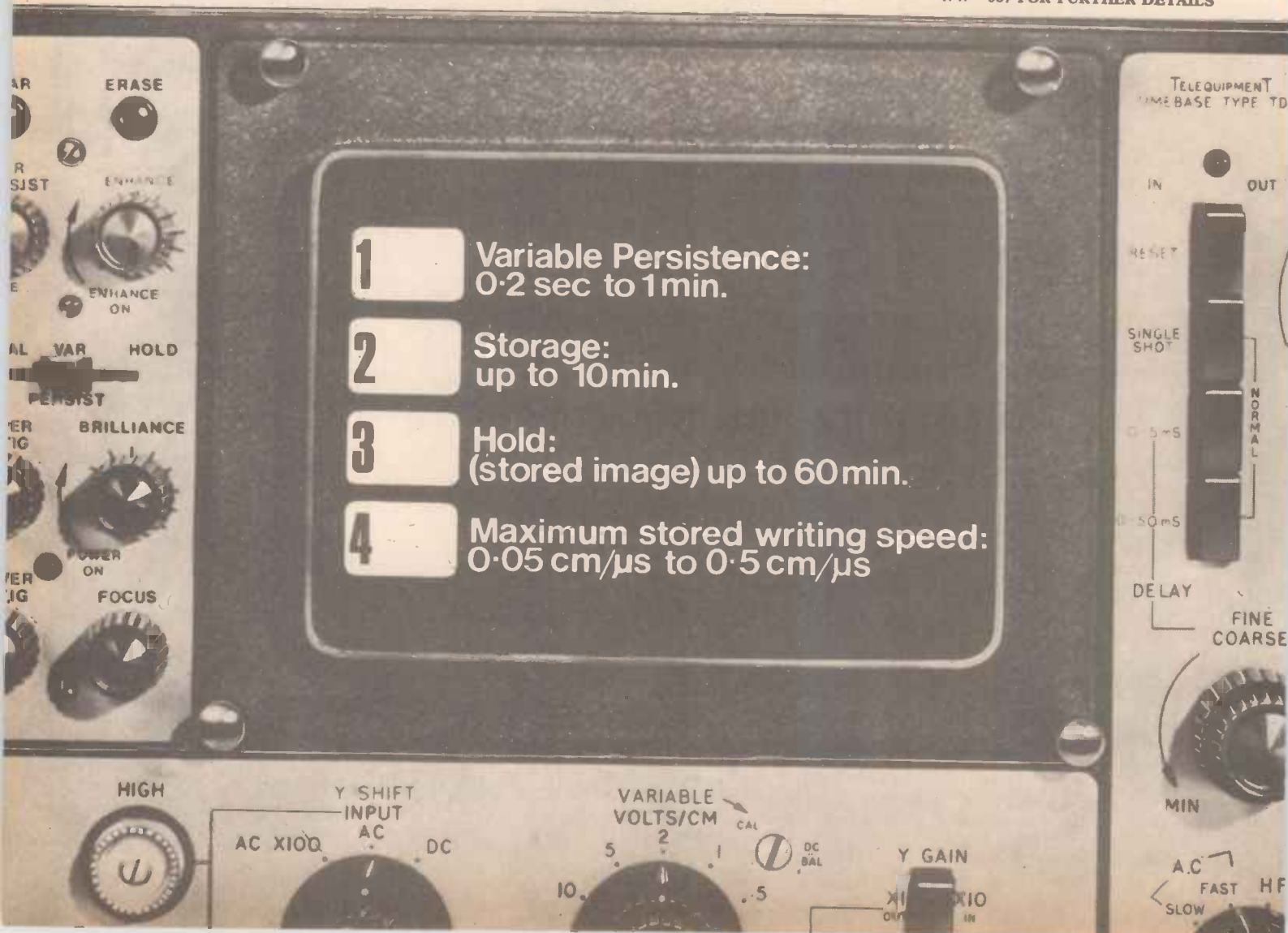


Wireless World

Electronics, Television, Radio, Audio

Sixty-second year of publication April 1972

Volume 78 Number 1438

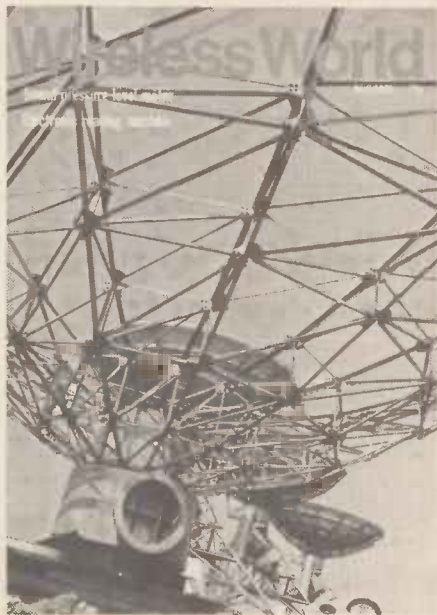

Our cover picture shows some of the eight 42-ft paraboloids being built by Marconi for the new £2M radio telescope at the Mullard Radio Astronomy Observatory at Cambridge University. Spaced over a distance of three miles four of the aerials are fixed and four are mounted on a railway track. *Photographer — Paul Brierley*

Contents

- 153 Exhibitions — general or specialized?
- 154 Hand-portable Transceiver *by D. A Tong*
- 160 H.F. Predictions
- 161 The Electronic Retina *by N. A. Singer*
- 166 Conferences & Exhibitions
- 167 Sound Pressure-level Meter *by J. L. Linsley Hood*
- 168 Announcements
- 169 Recording Level Meter and A.G.C. *by James M. Bryant*
- 170 News of the Month
- 173 How to Simplify Logic Circuits *by N. Darwood*
- 175 Letters to the Editor
- 177 Books Received
- 178 Electronic Building Bricks — 22 *by J. Franklin*
- 179 F.M. Tuner Design — 12 Months Later *by L. Nelson-Jones*
- 184 About People
- 185 Circuit Ideas
- 187 Stereo Cassette Tape Decks: 2 *by B. Crank*
- 192 Sixty Years Ago
- 193 World of Amateur Radio
- 194 Miniature Automatic Telephone Exchange Modifications *by P. F. Gasgoyne*
- 195 April Meetings
- 196 New Products
- 201 Literature Received
- 202 Real & Imaginary *by 'Vector'*
- A91 APPOINTMENTS VACANT
- A102 INDEX TO ADVERTISERS

IN OUR NEXT ISSUE

The transmission-line loudspeaker enclosure is re-examined and a simpler and better method of construction offered. Suitable drive units and crossover circuits are also specified.

Oscilloscope trace quadrupier. Provides four traces on a single-beam oscilloscope without sacrificing sensitivity or d.c. coupling. Frequency response is from d.c. to 5MHz (3dB down at 8MHz); sensitivity is 50mV/cm when used with a 100mV/cm 'scope.



I.P.C. Electrical-Electronic Press Ltd
Managing Director: George Fowkes
Publishing & Development Director:
George H. Mansell
Advertisement Director: Roy N. Gibb, M.I.E.E.

© I.P.C. Business Press Ltd, 1972


Brief extracts or comments are allowed provided acknowledgement to the journal is given.

Published monthly on 3rd Monday of preceding month, 20p


Editorial & Advertising offices: Dorset House, Stamford Street, London SE1 9LU. Telephone 01-928 3333. Telegrams/Telex, Wivorld Bisnespres 25137 London. Cables, "Ethaworld, London S.E.1."

Subscription & Distribution offices: 40 Bowling Green Lane, London EC1R ONE. Telephone 01-837 3636. Subscribers are requested to notify a change of address four weeks in advance and to return envelope bearing previous address.

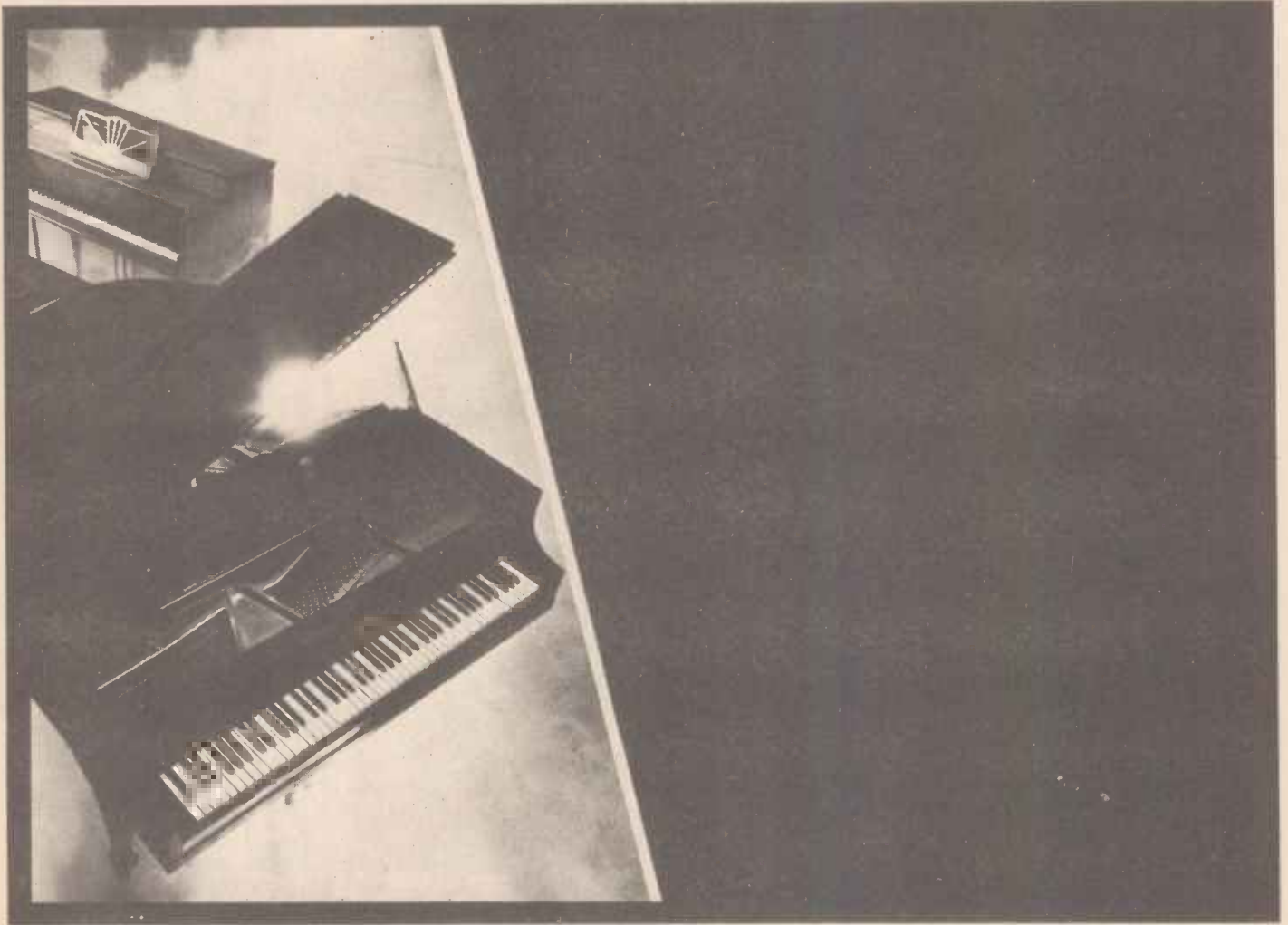Subscription rates: *Home*, £4.35 a year. *Overseas*, 1 year £4.35; 3 years £11.10 (U.S.A. & Canada 1 year \$11, 3 years \$27.75).



To each his own.

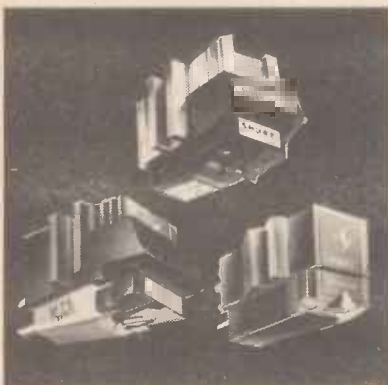

Not everybody needs a concert grand piano, nor does everybody need the Shure V-15 Type II, the most sophisticated cartridge in the world, to enjoy his kind of music in his kind of hi-fi system. For many, the M75 Type 2 Series, widely acclaimed as second only to the V-15, will be more than adequate. Within more circumscribed budgets the M55, M44 Series or M3D, each offering optimum performance in successively lower price ranges, may be an excellent choice. Send us the coupon for our recommendations.

Shure Electronics Limited
84 Blackfriars Road
London SE1, 8HA Telephone (01) 928 3424

WW-068 FOR FURTHER DETAILS

- Please send me the full details of Shure cartridges.
- Please recommend the appropriate model for use with my equipment.

Arm or Unit _____

Amplifier _____

Name _____

Address _____



Super stars

HIGH-PERFORMANCE MF/HF RECEIVERS

- * P & T Stations
- * Civil Aviation Networks
- * Naval & Military Forces
- * Maritime Mobile Service



Three high-grade receiver designs with a choice of tuning wide enough to span the whole world of MF/HF communications.

Here is simply unbeatable performance. Outstanding frequency stability. Unyielding front-end protection. Unrivalled AGC. Plus exceptional dynamic range and blocking characteristics. From this great threesome :

R550 Selection of continuously variable or full frequency synthesis tuning 100kHz – 30MHz. Adopted by the Royal Navy for use in British warships.

R499 10 switched channels, 255 – 525kHz, 1.5 – 30MHz. Optional filters, BFO and carrier reinsertion to provide any or all of CW, MCW, USB, LSB, ISB and DSB services with choice of bandwidths.

R551 Mercantile Marine version of R550, 15kHz – 30MHz. Type approved by British Ministry of P & T and overseas administrations and in use by leading shipowners.



REDIFON
A Member Company of the Redifusion Organisation.

Redifon Telecommunications Limited,
Broomhill Road, London SW18 4JQ
Telephone: 01-874 7281

All you need for Hi-fi. An amplifier, two speakers, and a



BSR make more turntables than everyone else in the world put together.

Our range includes high-quality sensibly priced models, both single play and automatic.

The MP60 player, already immensely popular, costs only £15.20, complete with low mass, fully counterbalanced square section pick up arm, slide in cartridge holder, bias compensator, viscous cueing, 3½lb die cast turntable, 4-pole motor and immaculate BSR styling.

For a few pounds more, you can buy the HT70, boasting the same super features but with three more refinements. A deep-rim die cast turntable, which is one pound heavier than the MP60. A rotating stub spindle to reduce record friction and a dynamically balanced synchronous motor, which compensates for normal fluctuation in mains voltage.

With these models, and our range of automatics, you get the flexibility of price you need to build your whole Hi-fi set up.

You can choose your own speakers and your own amplifier, to suit your pocket, from

the many excellent examples on the market.

And if you're not too sure about the ins and outs of Hi-fi, your dealer will be only too pleased to help and advise you. But make sure you ask him to show you the range of BSR turntables. For a preview, just return the coupon below, and we'll send you our illustrated brochures.

BSR Ltd., McDonald Division, Monarch Works, Cradley Heath, Warley, Worcs. Telephone: Cradley Heath 69272.

Please send me your illustrated brochures of the complete BSR McDonald range of turntables.

Name _____

Address _____

BSR McDONALD

It's a sound start

w/2

New from Ferrograph

For the maintenance of professional recording equipment.

Now, for the first time, all the major parameters of a magnetic recording system can be measured on a single, inexpensive instrument. The Ferrograph RTS1 Recorder Test Set.

Consisting of 4 basic sections—variable frequency audio generator, millivoltmeter with associated attenuator, peak-to-peak wow and flutter meter, and distortion measuring network—this instrument will measure frequency response, distortion, crosstalk, erasure, input sensitivity, output power and signal/noise ratio.

Completely solid state and lightweight, it may be used in the field as well as the laboratory,


operating on voltages of 100-120, 200-250 volts at 50 or 60 hz.

It is developed specially for those people who have to operate, maintain or service all types of tape recorders, sound-on-film equipment and audio apparatus.

The Ferrograph RTS1.
Made to stand the test.
Why not write for further details ?

FERROGRAPH

SOUNDS GOOD

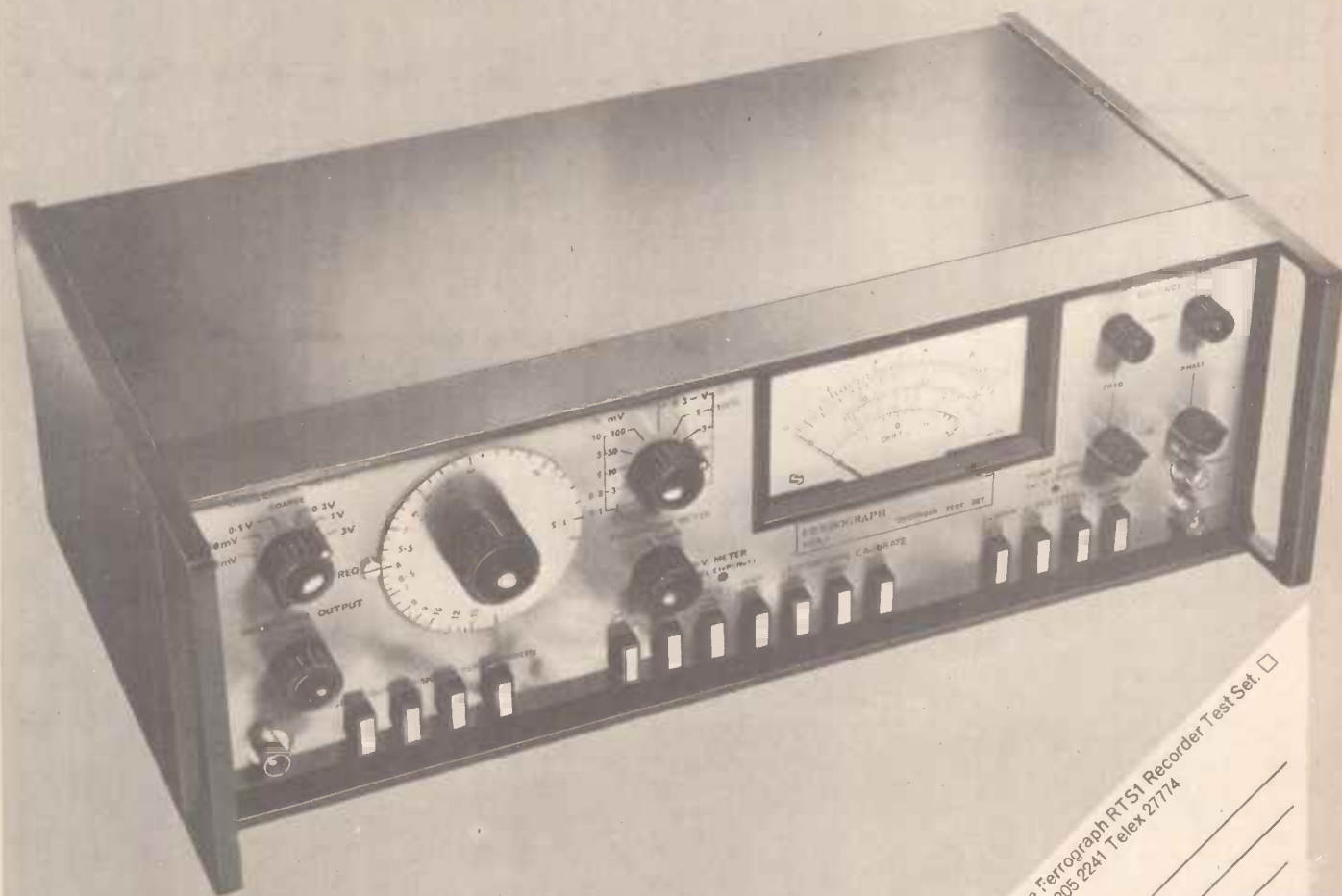

Please send me full details on the Ferrograph RTS1 Recorder Test Set.

NAME _____
ADDRESS _____

The Ferrograph Company
Limited, The Hyde,
Edgware Road,
Colindale,
London
NW9. WWW

DYMAR

- for Radiotelephone testing

Dymar one of Britain's largest producers of VHF radiotelephones manufacture a range of very economically priced instruments specifically designed for use in the design, production and servicing of Radio Telephone Equipments. The type 785 Modulation Meter for example, is a solid state instrument for the measurement of depth of modulation in amplitude transmitters or the frequency deviation in the case of F.M. transmitters. It is specifically designed for narrow deviation transmitters in today's mobile and portable VHF radiotelephones, the most sensitive deviation range being 3kHz f.s.d.



Type 785
A.M./F.M. Modulation Meter

OTHER DYMAR INSTRUMENTS

585 Portable A.F. Power Meter	745 Two-Tone Signal Generator
701 Wideband Millivoltmeter	761 Noise Factor Meter
705 A.F. Microvoltmeter	765A Distortion Factor Meter
711 VHF Millivoltmeter	771A A.F. Wave Analyser


Carrier Frequency Range 30MHz-480MHz
F.M. Deviation 3kHz f.s.d.-100kHz
A.M. Modulation Depth 3% f.s.d.-100%
Sensitivity Better than 2 millivolts over the whole frequency range

DYMAR

Full details from :-
DYMAR ELECTRONICS LIMITED
Colonial Way, Radlett Road, Watford, Herts.
Telephone: Watford 21297

WW-072 FOR FURTHER DETAILS

Meeting amplification needs

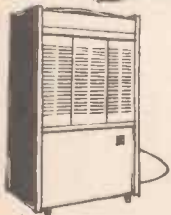

'Toa' PA-III Meeting Amplifier
A modern, compact, portable unit that brings clarity and 'life' to meetings, lectures, demonstrations, and other gatherings—where a voice must carry effectively. Ideal for conferences, exhibitions, schools and stores.

Complete with built-in speaker and neck-slung/hand mike. Operates off Mains or Batt. (No need to waste time searching for an electric socket!) Unit takes extra mike, and has input for record-player or tape.

Goldring 

Goldring Manufacturing Company (Great Britain) Ltd.
10 Bayford Street, Hackney, London E8 3SE. Phone: 01-985 1152

WW-073 FOR FURTHER DETAILS





Mrs Soulsby of Satchwell takes 20 seconds to run the test *twice* - to make sure the board is properly bedded down on the test panel.

'Our Testmatic TM60 gave us a 70% saving in year one Next year it will be more.'

David Evans, Satchwells Controls Systems Ltd., Slough

Wayne Kerr's Testmatic TM60 is designed to do routine fault-finding on circuit boards, sub-assemblies, and cableforms. But its real end product is money: immediate definable, measurable savings far above the cost of its purchase.

Satchwells' experience is a case in point. When they saw the prototype TM60 they were so impressed with its potential for them that they put in an order and took the first production model that Wayne Kerr ever made.

They immediately applied it to the unit that represented their largest production batch - a circuit board that goes into a control for central heating systems.

By rapid fault finding and correction, they could afford to make fewer boards. They reduced rejects at final test from 25% to less than 10% of production.

They not only saved money in production, they saved the time of a skilled man. With the

Testmatic doing in 20 seconds what used to take 20 minutes, the chief troubleshooter was much less burdened with merely routine work.

Then, too, they saved the capital represented by boards waiting to be tested and repaired.

And all this has been only a beginning. Next year their TM60 will be put to work testing other types of boards in addition to the one it now tests. The more it works, and the more diversely it works, the more it will save.

Stop Press! Satchwells' have now taken delivery of another TM60.

For the full story of the Testmatic TM60 please fill in:

For the attention of Mr.

Company Name

and Address.....

W.W.4

Post to Wayne Kerr (TM60) Tolworth Close, Tolworth, Surbiton, Surrey, KT6 7ER or call 01-399-6751.

Wayne Kerr is a member of the Wilmot Breeden Group.

Exhibiting at the Kensington Close Hotel. May 8th - 12th


50 MHz for £975*

with Tektronix 7403N

One mainframe — and up to 25 plug-in options for outstanding versatility and performance. Up to 65 MHz bandwidth; sensitivity to 10 μ V/div. Large 6½ in. screen, versatile trigger source selection, mode switching, push button controls, colour-keyed panels. Standard package* includes 7403N mainframe, 7A18 Opt 1 50 MHz (5mV/div) amplifier and 7B53N 5ns/div timebase.



committed to technical excellence

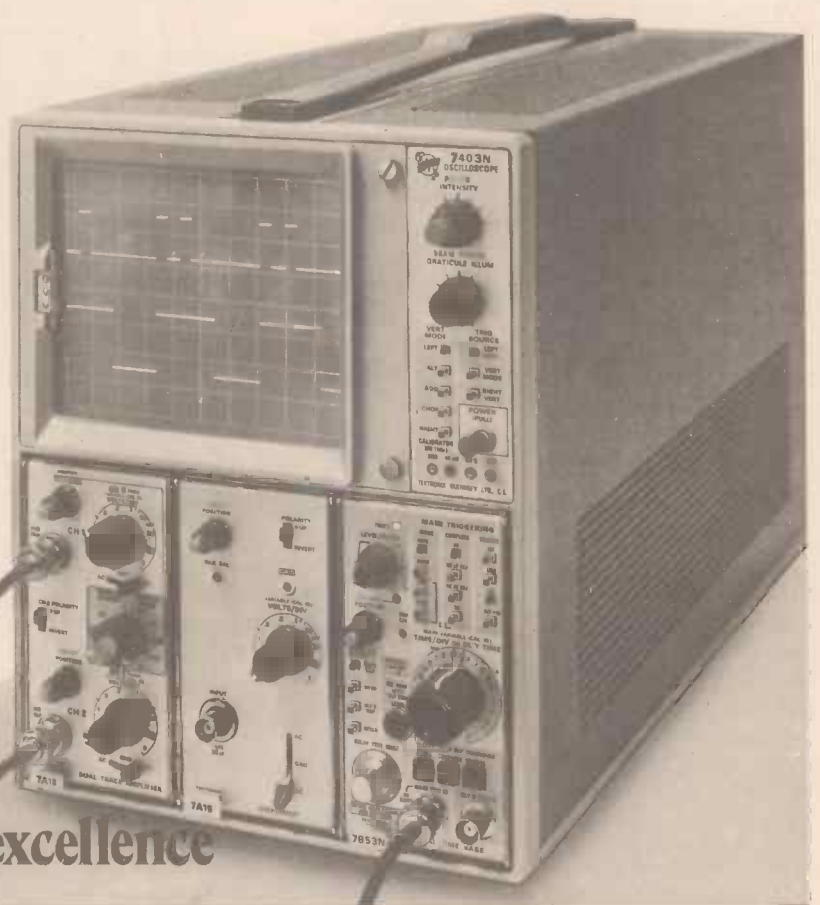

Tektronix U.K. Ltd.,
Beaverton House, P.O. Box 69,
Harpenden, Herts.
Tel: Harpenden 61251 Telex: 25559

Northern Region:
Beaverton House, 181A Mauldeth Rd,
Manchester 19
Tel: 061-224 0446 Telex: 668409

Scottish Region:
7 Shiel House, Craigshill, Livingston,
West Lothian, Scotland.
Tel: Livingston 32766/7

WW—075 FOR FURTHER DETAILS



**The Garrard Zero-100:
no other deck can do so much
for your Hi-Fi system**

Don't take our word for it, take a look over...

Read the experts' verdict on the Garrard Zero-100

'Now and again, in the world of audio, there comes a piece of equipment that is not only different enough to catch public imagination but also technically sound enough to allay the suspicions of the ultra-conservative. Such a device is the Garrard Zero-100.'


Records and Recording (UK), September 1971 (H W Hellyer)

'A simple list of all the Zero-100 features should serve to spotlight the changes that have been incorporated in this model. . .

- *15-deg. vertical tracking angle adjustment.
- Sliding-weight stylus-force adjustment – easy to adjust as little as one-tenth of a gramme.
- Magnetic anti-skating control.
- Spring-loaded tonearm safety restrictor (lock).
- Long-taper variable speed control.
- Illuminated stroboscope, with two bands of lines, one for each speed.
- Rotating manual spindle.
- Proven Synchro-Lab motor – combination of induction and synchronous types.
- Full-diameter platter.
- *Safe 2-point record support.
- Handsome combination of chrome, brass and plexiglas for tonearm mounting.'

Audio (USA), July 1971

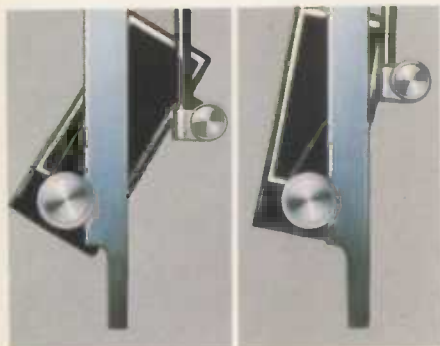'The most striking feature of the pickup arm, of course, is the auxiliary rod to the right of the straight, rectangular cross-section aluminium arm. This is pivoted at both ends and its effect is to rotate the cartridge



The pivoting head at the start and end of a playing cycle.

housing directly above the stylus tip so that at all points, as the pickup tracks across the record, the plane of stylus motion remains truly at right angles to the groove. This causes the reproducing stylus to imitate the motion of the cutting stylus very accurately in tracking the recorded waveform, and is in contrast to the normal pivoted arm which tracks in an arc across the record. The angular error is a small, but important, source of harmonic distortion.'

The Gramophone (UK), August 1971 (John Borwick)

Base shown available July 1972



'The anti-skating control involves no mechanical linkage to the arm. A simple slide on the fixed arm mounting serves to place a shield between a fixed magnet and one mounted on the movable gimbal which supports the arm. Separate calibrations are provided for conical and elliptical styli.'

Audio (USA), July 1971

'Garrard supply a small clear plastic device which slides over the cartridge carrier and is marked with a small cross for aligning the stylus to give correct cartridge positioning relative to the headshell. This was a delight to use.'

Popular Hi-Fi (UK), June 1971 (David Line)

'Setting the playing weight is quite straightforward and accurate. The main counterbalance weight is a substantial brass cylinder with a ribbed plastic core to provide the decoupling which avoids low frequency resonant vibrations being set up as the pickup tracks record warps etc.'

The pickup arm housing and assembly, showing the magnetic bias compensator calibrated for spherical and elliptical styli.



Publication No. 4469

The required playing weight is applied by means of a stylus force weight which slides along the underside of the pickup arm. The scale, from 0 to 3 grammes, is about 3 3/8 inches long so that very precise setting of the weight is possible.'

The Gramophone (UK) August 1971 (John Borwick)

'Wow and flutter are good. To measure less than 0.08% on a turntable of this type and cost is phenomenal – I may have had a particularly good one. A colleague widely

separated from me reports W&F as low as 0.05%, so I can only applaud Garrard for having made the best of the Synchro-Lab motor, now proven on several recent models.'

Records and Recording (UK), September 1971 (H W Hellyer)

'Garrard's Zero-100, in basic performance, easily ranks with the finest *automatic turntables on the market. Its novel arm – which really works as claimed – and its other unique design features suggest that a great deal of development time, plus sheer imagination, went into its creation. In our view, the results were well worth the effort.'

Stereo Review (USA), July 1971 (Hirsch-Houck Laboratories)

*The references to the automatic Zero-100 occur because, at the time of the reviews, only the automatic version was available. The Zero-100 is now available in single-play form, with facility for 'fluid damped' autoplay of single records.

- 1 Brass counterbalance weight
- 2 Magnetic bias compensation
- 3 Rigid acrylic pickup arm housing
- 4 Gimballed pivots
- 5 Stylus force adjustment (under arm)
- 6 Low resonance pickup arm
- 7 Control arm
- 8 Control link pivot
- 9 Pickup head pivot
- 10 Vertical cartridge angle adjustment (on auto player only)

If you'd like to read our full facts on the Zero-100 write now for colour brochure.


Garrard 

A PLESSEY QUALITY PRODUCT

Garrard, Newcastle Street, Swindon, Wiltshire, England.


ZF 380/238K/2-72K

Printed in England

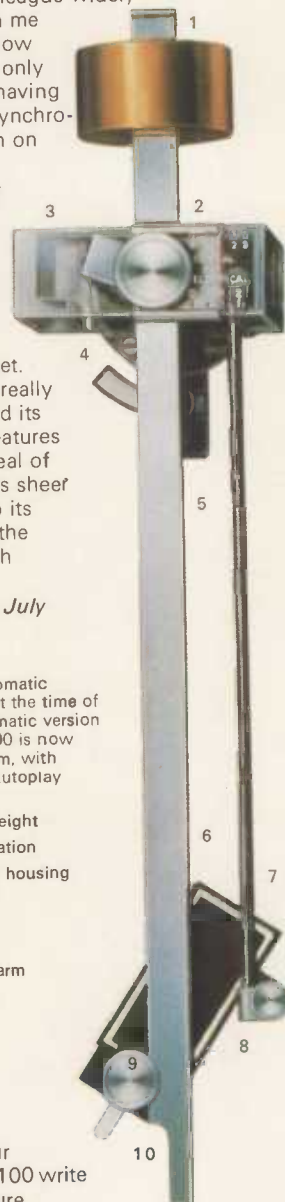

new

Super IC-12

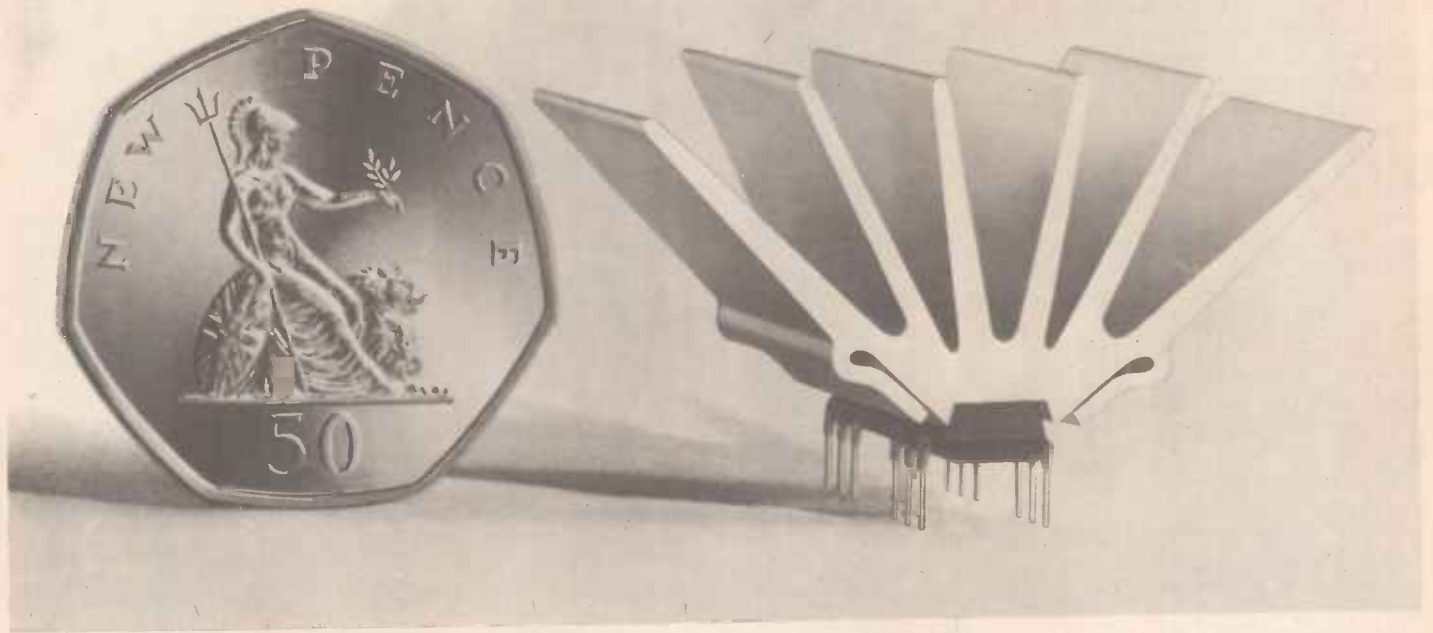

High fidelity Monolithic Integrated Circuit Amplifier

Two years ago Sinclair Radionics announced the World's first monolithic integrated circuit Hi-Fi amplifier, the IC.10. Now we are delighted to be able to introduce its successor, the Super IC.12. This 22 transistor unit has all the virtues of the original IC.10 plus the following advantages:

1. Higher power.
2. Fewer external components.
3. Lower quiescent consumption.
4. Compatible with Project 60 modules.
5. Specially designed built-in heat sink. No other heat sink needed.
6. Full output into 3, 4, 5 or 8 ohms.
7. Works on any voltage from 6 to 28 volts without adjustment.
8. NEW 22 transistor circuit.

Output power 6 watts RMS continuous (12 watts peak).

Frequency Response 5 Hz to 100KHz \pm 1 dB.

Total Harmonic Distortion Less than 1%. (Typical 0.1%) at all output powers and all frequencies in the audio band.

Load Impedance 3 to 15 ohms.

Input Impedance 250 Kohms nominal.

Power Gain 90dB (1,000,000,000 times) after feedback.

Supply Voltage 6 to 28 volts (Sinclair PZ-5 or PZ-6 power supplies ideal).

Quiescent current 8mA at 28 volts; low enough to make the IC.12 ideal also for battery operation.

Size 22 x 45 x 28 mm including pins and heat sink.

With the addition of only a very few external resistors and capacitors the Super IC.12 makes a complete high fidelity audio amplifier suitable for use with pick-up, F.M. tuner etc. Alternatively, for more elaborate systems, modules in the Project-60 range such as the Stereo 60 and A.F.U. may be added.



FREE 44 page instruction manual now included with all units. Available free on request to present IC.12 users. Gives full circuit and wiring diagrams for many applications including car-radios, oscillators, etc.



Price, inc. **FREE** printed circuit board for mounting and manual.

£2.98 Post free

SINCLAIR GENERAL GUARANTEE

Should you not be completely satisfied with your purchase when you receive it from us, return the goods without delay and your money will be refunded in full, including cost of return postage, at once and without question. Full service facilities are available to all Sinclair customers.

Sinclair Radionics Ltd, London Rd, St. Ives
Huntingdonshire PE17 4HJ
Telephone St. Ives (048 06) 4311

sinclair

Sinclair Project 60



Project 605

The easy way
to buy and
build
Project 60



Project 605 is one pack containing: one PZ5, two Z30's, one Stereo 60 and one Masterlink. This new module contains all the input sockets and output components needed together with all necessary leads cut to length and fitted with neat little clips to plug straight on to the modules. Thus all soldering and hunting for the odd part is eliminated. You will be able to add further Project 60 modules as they become available adapted to the Project 605 method of connecting.

Complete Project 605 pack with comprehensive manual, post free **£29.95**

All you need for a superb 30 watt high fidelity stereo amplifier.

Project 60 offers more advantage to the constructor and user of high fidelity equipment than any other system in the world.

Performance characteristics are so good they hold their own with any other available system irrespective of price or size.

Project 60 modules are more versatile – using them you can have anything from a simple record player or car radio amplifier to a sophisticated and powerful stereo tuner-amplifier. Either power amplifier can be used in a wide variety of applications as well as high fidelity. The Stereo 60 pre-amplifier control unit may also be used with any other power amplifier system as can the AFU filter unit. The stereo FM tuner operates on the unique phase lock loop principle to provide the best ever standards of audio quality. Project 60 modules are very easily connected together by following the 48 page manual supplied free with Project 60 equipment. The modules are great space savers too and are sold individually boxed in distinctive white and black cartons. With all these wonderful advantages, there remains the most attractive of all – price. When you choose Project 60 you know you are going to get the best high fidelity in the world, yet thanks to Sinclair's vast manufacturing resources (the largest in Europe) prices are fantastically low and everything you buy is covered by the famous Sinclair guarantee of reliability and satisfaction.

Typical Project 60 applications

System	The Units to use	together with	Units cost
Simple battery record player	Z.30	Crystal P.U., 12V battery volume control, etc.	£4.48
Mains powered record player	Z.30, PZ.5	Crystal or ceramic P.U. volume control etc.	£9.45
12 W. RMS continuous sine wave stereo amp. for average needs	2 x Z.30s, Stereo 60, PZ.5	Crystal, ceramic or mag. P.U., F.M. Tuner, etc.	£23.90
25 W. RMS continuous sine wave stereo amp. using low efficiency (high performance) speakers	2 x Z.30s, Stereo 60, PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	£26.90
80 W. (3 ohms) RMS continuous sine wave deluxe stereo amplifier. (60 W. RMS into 8 ohms)	2 x Z.50s, Stereo 60 PZ.8, mains transformer	As above	£34.88
Indoor P.A.	Z.50, PZ.8, mains transformer	Mic., guitar, speakers, etc., controls	£19.43

F.M. Stereo Tuner (**£25**) & A.F.U. Filter Unit (**£5.98**) may be added as required.

Sinclair Radionics Ltd, London Road, St. Ives,
Huntingdonshire PE17 4HJ. Tel: St. Ives 64311

sinclair

Project 60 Stereo F.M. Tuner

Built and tested. Post free. **£25**



The phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio. Now, Sinclair have applied the principle to an F.M. tuner with fantastically good results. Other original features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and squelch circuit for silent tuning between stations. In terms of a high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically as the tuning control is rotated, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with most other high fidelity systems.

SPECIFICATIONS—Number of transistors: 16 plus 20 in I.C. **Tuning range:** 87.5 to 108 MHz. **Capture ratio:** 1.5dB. **Sensitivity:** 7µV for lock-in over full deviation. **Squelch level:** 20µV. **Signal to noise ratio:** > 65dB. **Audio frequency response:** 10 Hz – 15 KHz (±1dB). **Total harmonic distortion:** 0.15% for 30% modulation. **Stereo decoder operating level:** 2µV. **Cross talk:** 40dB. **Output voltage:** 2 x 150mV R.M.S. **Operating voltage:** 25-30VDC. **Indicators:** Stereo on; tuning. **Size:** 93 x 40 x 207mm.

Stereo 60 Pre-amp/control unit

Built, tested and guaranteed. **£9.98**




Designed for Project 60 range but suitable for use with any high quality power amplifier. Again silicon epitaxial planar transistors are used throughout, achieving a really high signal-to-noise ratio and excellent tracking between channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs.

SPECIFICATIONS—**Input sensitivities:** Radio – up to 3mV. Mag. p.u. 3mV: correct to R.I.A.A curve ±1dB:20 to 25,000 Hz. Ceramic p.u. – up to 3mV: Aux – up to 3mV. **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE + 12 to -12dB at 10 KHz: BASS + 12 to -12dB at 100Hz. **Front panel:** brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207mm.

A.F.U. High & Low Pass Filter Unit

Built tested and guaranteed. **£5.98**

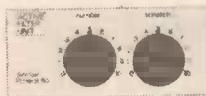

For use between Stereo 60 unit and two Z.30s or Z.50s, and is easily mounted. It is unique in that the cut-off frequencies are continuously variable, and as attenuation in the rejected band is rapid (12dB/octave), there is less loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The A.F.U. is suitable for use with any other amplifier system. Two filter stages – rumble (high pass) and scratch (low pass). **Supply voltage** – 15 to 35V. **Current** – 3mA. **H.F. cut-off** (-3dB) variable from 28KHz to 5KHz. **L.F. cut-off** (-3dB) variable from 25Hz to 100Hz. **Distortion** at 1 KHz (35V. supply) 0.02% at rated output. **Size:** 66 x 40 x 90mm.

Z.30 & Z.50 power amplifiers

Built, tested and guaranteed with circuits and instructions manual. **Z.30 £4.48** **Z.50 £5.48**



The Z.30 and Z.50 are of advanced design using silicon epitaxial planar transistors to achieve unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at 15w (8Ω) and all lower outputs. Whether you

use Z.30 or Z.50 amplifiers in your Project 60 system will depend on personal preference, but they are the same size and may be used with other units in the Project 60 range equally well.

SPECIFICATIONS (Z.50 units are interchangeable with Z.30s in all applications).

Power Outputs

Z.30 15 watts R.M.S. into 8 ohms using 35 volts:

20 watts R.M.S. into 3 ohms using 30 volts.

Z.50 40 watts R.M.S. into 3 ohms using 40 volts:

30 watts R.M.S. into 8 ohms using 50 volts.

Frequency response: 30 to 300,000Hz ± 1dB.

Distortion: 0.02% into 8 ohms.

Signal to noise ratio: better than 70dB unweighted.

Input sensitivity: 250mV into 100 Kohms (for 15w into 8Ω)

For speakers from 3 to 15 ohms impedance.

Size: 14 x 80 x 57 mm.

Power Supply Units



Designed special for use with the Project 60 system of your choice. Use PZ.5 for normal Z.30 assemblies and PZ.6 where a stabilised supply is essential.

PZ.5 30 volts unstabilised £4.98

PZ.6 35 volts stabilised £7.98

PZ.8 45 volts stabilised

(less mains transformer) £7.98

PZ.8 mains transformer £5.98

Guarantee

If within 3 months of purchasing Project 60 modules directly from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail. Air-mail charged at cost.

sinclair

To: SINCLAIR RADIONICS LTD LONDON ROAD ST. IVES HUNTINGDONSHIRE PE17 4HJ

Please send

Name

Address

I enclose cash/cheque/money order.

WW4



Opportunities Unlimited in RADIO, TELEVISION, ELECTRONICS

**City & Guilds Telecommunication
Technicians' Certificate
Ministry of Post & Telegraphs
Certificate**

*Which one would qualify you
for higher pay?*

International Correspondence Schools provide specialized training courses for all these certificates (tuition for individual subjects also provided) and with the help of the Schools' experienced tutors you can be sure of early success. You will have the advantage of building on your practical experience and ensuring that you have the technical knowledge so essential for success in electronics.

And the result? You'll soon be qualified in your field of electronics, and in a position to choose your opportunity.

Find out how ICS can help you. Send for our *free* prospectus right away.

**ALL EXAMINATION STUDENTS ARE
COACHED UNTIL SUCCESSFUL**

NOW—COLOUR TV SERVICING COURSES

As the demand for colour TV increases, so does today's demand for trained servicing engineers. You can learn the techniques of servicing colour and monochrome TV sets through new home study courses specially prepared for the practical TV engineer.

SELF-BUILD RADIO COURSES

We'll teach you both the theory and practice of valve and transistor circuits, as well as how to service them, while you build your own 5 valve receiver, transistor portable and high grade test instruments. You build equipment of real practical use!

Accredited by the Council for the Accreditation of Correspondence Colleges
Member of the Association of British Correspondence Colleges

**POST TODAY FOR FULL DETAILS OF ICS COURSES IN
RADIO, TV AND ELECTRONICS**

International Correspondence Schools, Dept. HA64, Intertext House,
Stewarts Road, London, SW8 4UJ

Please send me *free* and *without any obligation* the ICS Prospectus

(State subject or Exam)

Name Age

(BLOCK CAPITALS PLEASE)

Address

Occupation



INTERNATIONAL CORRESPONDENCE SCHOOLS


**UNBEATABLE UNREPEATABLE
OFFER
SHIBADEN SV700E
625 & 405 LINE
1/2" VIDEO TAPEREORDER
at under HALF PRICE**



**SAVE £200 ON
EX-DISTRIBUTORS'
REDUNDANT STOCK
ONLY £198 each**

GUARANTEED FULL WORKING ORDER AND
COMPATIBLE WITH LATEST MACHINES.
ORDER NOW WHILE LIMITED STOCKS LAST.
(TRADE ENQUIRIES WELCOME)
AUDIO ADVERTISING (DEPT IVS)
43 MALDEN WAY, NEW MALDEN, SURREY
01-942 9635/6

WW-078 FOR FURTHER DETAILS

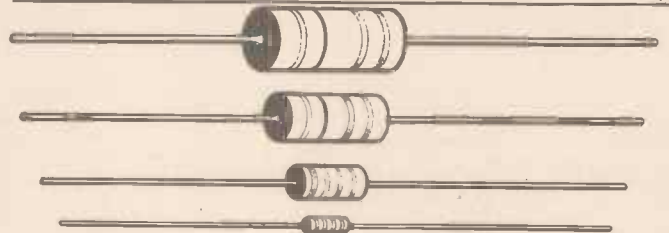

OHMIC


Hot moulded carbon resistors and
potentiometers. Modular op amps
Send for literature



Bourns (Trimpot) Ltd.,
Hodford House, 17/27 High Street,
Hounslow, Middlesex.
Telephone: 01-572-0111 Telex: 264485.

KWP/B49

WW-079 FOR FURTHER DETAILS

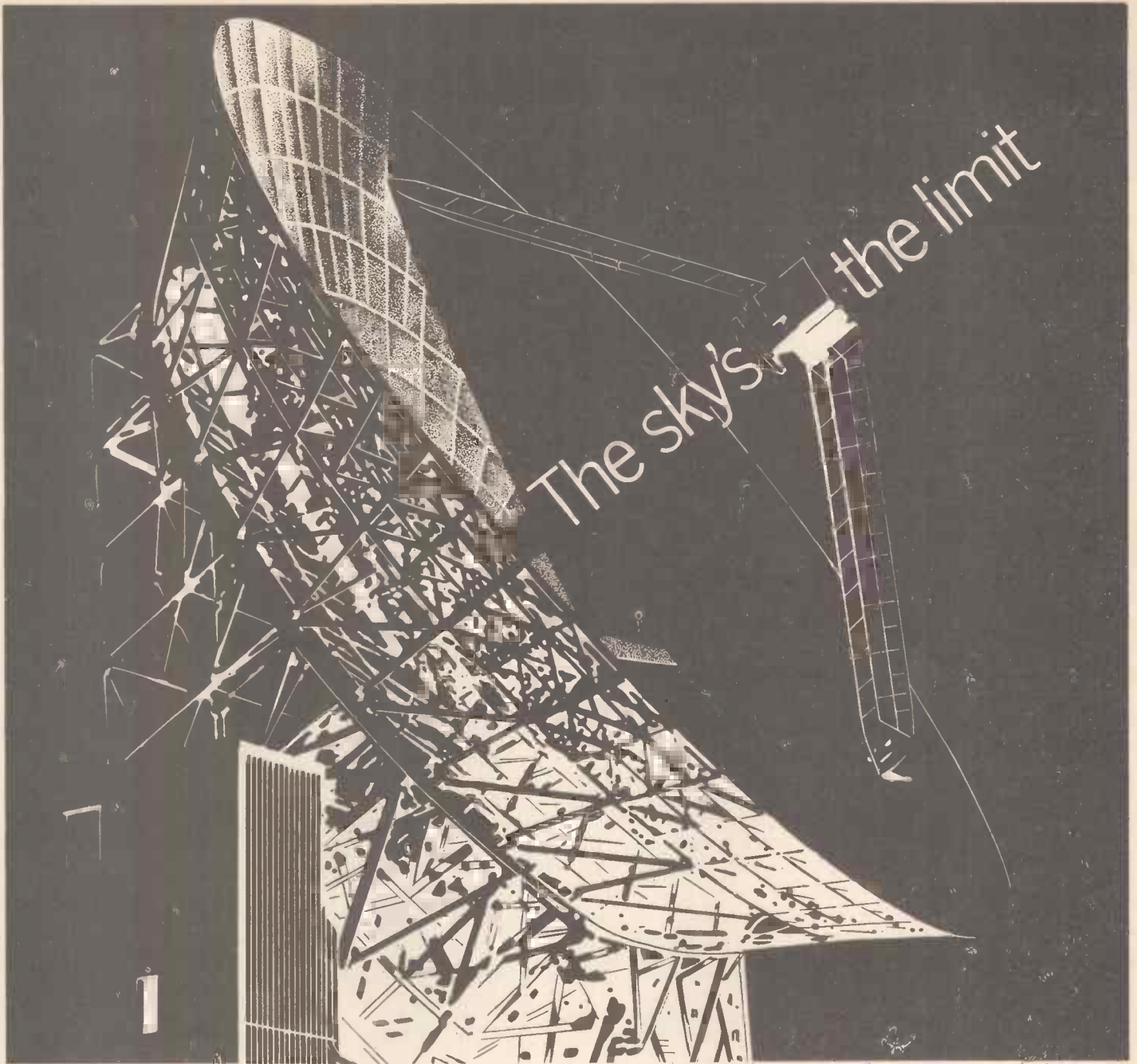

International Instruments, Electronics, Automation Exhibition Olympia London 8-12 May 1972

Keeping up with developments in this fast moving industry can be difficult. That's why the IEA Exhibition was born and why you should seize this opportunity to visit the only international show this year to cover the field.

25% of the exhibitors come from 18 overseas countries and for the first time there will be special sections: one for process control instrumentation and one for electronic components.

Equipment and techniques need to be examined carefully, especially when they change radically and relentlessly.

The Intelsat project is a classic

example. This project is big business — it costs \$30,000,000 per match to blue touchpaper. 82 countries are involved and U.K. is the second largest contributor. The IEA Exhibition means business.

See you there.

The IEA Exhibition is sponsored by the 5 trade associations of the industry. Tickets available only from exhibitors or at 30p at the door.

Open: 10.00-18.00 daily (except Wed. and Thurs. open until 20.00)

For further information please return this coupon to: Industrial Exhibitions Limited, 9 Argyll Street, London, W1V 2HA.

Please send me _____ catalogues 50p. each including p & p (published 3 weeks before opening day).



Travel and Accommodation Arrangements

Official exhibition travel agents have been appointed. They can provide a complete travel service from the London office or through their representatives around the world: inclusive or individual rates for booking air, rail and sea journeys, vehicle hire, guides, accommodation and other services from their comprehensive range.

Please indicate the number of persons in your party and whether you wish to deal with London office or a local agent.

Number of persons _____
London office/local agent.

Name _____


Company _____

Address _____



"COMPUTERFLASH"

Send for your
FREE copy now!

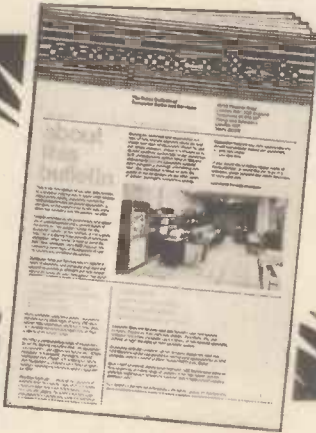

Computer Sales and Services listing of
equipment and systems from stock.

Or visit our showrooms at
49-53 Pancras Road, London N.W.1.

COMPUTER SALES & SERVICES (Equipment) LIMITED
49-53 PANCRAS ROAD, LONDON N.W.1. TEL: 01-278 5571

WW-080 FOR FURTHER DETAILS

TRANSFORMERS

COILS

CHOKES

TRADE ENQUIRIES WELCOMED

SPECIALISTS IN

FINE WIRE WINDINGS

MINIATURE TRANSFORMERS
RELAY AND INSTRUMENT COILS
VACUUM IMPREGNATION TO APPROVED STANDARDS

ELECTRO-WINDS LTD.

CONTRACTORS TO G.P.O., L.E.B., B.B.C.

123 PARCHMORE ROAD, THORNTON HEATH, SURREY
01-653 2261 CR4 8L Z EST. 1933

WW-082 FOR FURTHER DETAILS

QUASI-DIFFERENTIAL

CHOPPER AMPLIFIER

BRITISH MADE



IMMEDIATE DELIVERY

This amplifier can be used for differential applications where the common mode voltage is limited to $\pm 1v$ d.c. There is no 50 Hz c.m.r.r. and an external capacitor allows for optimisation of the frequency response versus chopper ripple:

TYPICAL CHARACTERISTICS

offset voltage	0.15 μ V/°C
noise voltage	1 μ Vp-p
bandwidth	dc-100Hz (adjustable)
slew rate	adjustable
metal case	1.5" square x 0.62" deep

ancom limited devonshire street cheltenham 53861

WW-081 FOR FURTHER DETAILS



VITAVOX HIGH QUALITY

MICROPHONES LOUDSPEAKERS
PRESSURE UNITS H.F. HORNS
And a wide range of associated eqpt.


Further information from

VITAVOX LTD

Westmoreland Road, London NW9 9RJ
Telephone: 01-204 4234

WW-083 FOR FURTHER DETAILS

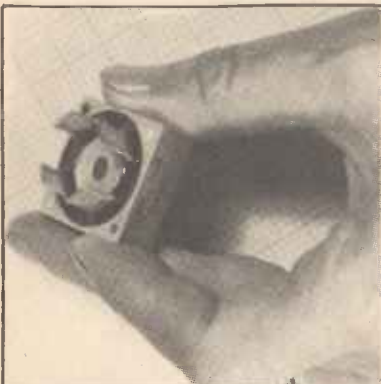BRIDGE RECTIFIER FROM SSDI (MACHINED ALUMINIUM CASE)



Type	PIV per leg	Sine Wave RMS input Voltage Max.	Average DC Output Amps TC=(case temp.)			Average DC Output Amps TA = Ambient Temp. (No heat Sink)			Peak 1 Cycle Forward Surge	Peak Recurrent Forward	VF Max. per leg. @3ADC	Reverse Current (I _R Max. per leg. @ PIV)		
			55°C	100°C	125°C	25°C	55°C	100°C				25°C	25°C	100°C
	Volts	Volts	Amps	Amps	Amps	Amps	Amps	Amps	Amps	Amps	Volts	UA	UA	
SDA 129	600	420	25	18.5	12.5	6.0	5.0	3.0	200	100	1.0	5	100	

Maximum thermal impedance junction to mounting surface 1.5°C/Watt!
Maximum operating and storage temperature -55°C to +150°C
SIZE (excluding Soldering Tags)
1.125" x 1.125" x 0.437"

PRICES
1-24 £2.12
25-99 £1.95
100-999 £1.72

CIC


CONCORDE INSTRUMENT COMPANY
28 CRICKLEWOOD BROADWAY, LONDON NW2.

TEL: 01-452 0161/2/3
TELEX: 21492

WW-084 FOR FURTHER DETAILS

TUNE IN TO OXLEY

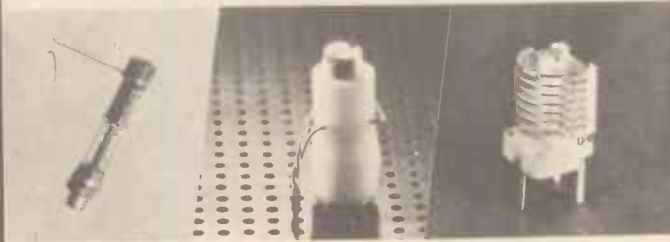WITH OUR ESTABLISHED AND MOST RECENTLY DEVELOPED TRIMMER CAPACITORS



- ★ P.T.F.E. tubular trimmers.
- ★ Quartz tubular trimmers.
- ★ Plastic base P.T.F.E. and air dielectric trimmers.
- ★ Ceramic trimmers.
- ★ Temperature compensating trimmers.
- ★ Ceramic base P.T.F.E. and air dielectric trimmers.
- ★ Maximum capacitance values from 2pF to 100pF.

We feel sure we can meet your most exacting requirements for precision trimmer capacitors.

For further details please contact the manufacturers:

OXLEY DEVELOPMENTS CO. LTD
 PRIORY PARK, ULVERSTON, N. LANCS.
 TEL: ULVERSTON 262 1, TELEX 6541.
 CABLES: OXLEY ULVERSTON



WW—085 FOR FURTHER DETAILS

For a Professional Finish To your Quality Kit



CURRENT RANGE

Universal Metalwork — Wooden Case — Stereo Bailey 30w Front Plate — Bailey 30w kits with fibreglass PCB's and edge connector mtg. Bailey 20w kits, Bailey Pre amp, Linsley Hood Class A, Sugden Class A (Reprint now available.) Stuart tape circuits, full set of fibreglass PCB's and all parts for primary design. Ready-wound inductors and Bogen heads for 1/2" tape and cassettes in stock.

NEW FOR THIS MONTH — Large heavy duty Mains transformer for Linsley Hood Class A designs Secondary tapped at 25, 30, 35 and 40v 2.5A to suit the different versions of this amplifier. Size 3 3/4 x 3 3/4 x 4 1/2 high. Tagboard terminations. Fully impregnated and built for continuous use. Our type No. 750 £4.20 post free. Replaces parts 750a, 750b and 750c.

P.S. Anybody want fully wound mains transformers for the bench, Power Supply in February W.W.?

For free list, please send foolscap (9 x 4") s.a.e.

ALL U.K. ORDERS ARE POST FREE.

Overseas at cost.

HART ELECTRONICS

PENYLAN MILL, MORDA, OSWESTRY, SALOP.

Personal callers are always welcome, but please note we are closed all day Saturday.

TRANSFORMERS

MAINS ISOLATING SERIES
 Primary 200-250 Volts Secondary 240 Volts Centre Tapped (120V) and Earth Shielded
 ALSO AVAILABLE WITH 115/120V SECONDARY WINDING

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	P & P £ p
100	20	1 11	7.0 x 6.0 x 6.5	1.61 30
61	100	3 8	8.9 x 8.0 x 7.7	2.39 36
30	200	5 12	10.2 x 8.9 x 8.3	2.62 52
62	250	9 8	12.0 x 10.3 x 10.0	4.39 52
62	250	12 4	9.5 x 12.7 x 11.4	5.80 67
55	350	15 0	14.0 x 10.8 x 12.4	7.77 82
63	500	27 0	17.1 x 11.4 x 15.9	11.20
92	1000	40 0	17.8 x 17.1 x 21.6	20.63
128	2000	63 0	24.1 x 21.6 x 15.2	34.10
129	3000	84 0	21.6 x 21.6 x 20.3	53.34
190	6000	178 0	31.1 x 35.6 x 17.1	87.52



440V 300VA ISOLATOR, Primary 440V Secondary 240V, Centre Tapped Screened and Shrouded, £9.43. P & P 67p.

AUTO SERIES (NOT ISOLATED)

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	P & P £ p
113	20	1 11	7.3 x 4.3 x 4.4	0-115-210-240	0.85 22
64	75	1 14	7.0 x 6.4 x 6.0	0-115-210-240	1.66 30
4	150	3 0	8.9 x 6.4 x 7.6	0-115-200-220-240	2.00 36
66	300	6 0	10.2 x 10.2 x 9.5	" "	3.89 52
67	500	12 8	14.0 x 10.2 x 11.4	" "	5.78 67
84	1000	16 0	11.4 x 14.0 x 14.0	" "	10.49 82
93	1500	28 9	13.5 x 14.9 x 16.5	" "	15.20
95	2000	40 0	17.8 x 16.5 x 21.6	" "	19.84
73	3000	45 8	17.4 x 18.1 x 21.3	" "	26.99

TOTALLY ENCLOSED 115V AUTO TRANSFORMERS

115V 500 Watt totally enclosed auto transformer, complete with mains lead and two 115V outlet sockets, £7.85. P & P 67p. Also available a 20 Watt version, £1.67, P & P 22p.

LOW VOLTAGE SERIES (ISOLATED)

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Windings	P & P £ p
111	0.5	0.25	12	0-12V at 0.25A x 2	0.85 22
213	1.0	0.5	1	0-12V at 0.5A x 2	1.01 22
71	2	1	1	0-12V at 1A x 2	1.33 22
18	4	2	2	0-12V at 2A x 2	1.86 36
70	6	3	3	0-12V at 3A x 2	2.24 42
108	8	4	4	0-12V at 4A x 2	2.48 52
72	10	5	5	0-12V at 5A x 2	2.94 52
17	16	8	7	0-12V at 8A x 2	4.54 52
115	20	11	13	0-12V at 10A x 2	5.78 67
187	30	15	16	0-12V at 15A x 2	10.67 82
226	60	30	34	0-12V at 30A x 2	19.61

30 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
112	0.5	1 4	8.3 x 3.7 x 4.9	0-12-15-20-24-30V	1.01 32
79	1.0	2 0	7.0 x 6.4 x 6.0	" "	1.35 36
3	2.0	4 6	8.9 x 7.0 x 7.6	" "	2.01 36
20	3.0	6 0	10.2 x 8.9 x 8.6	" "	2.48 42
21	4.0	8 0	10.2 x 10.0 x 8.6	" "	2.94 52
51	5.0	6 8	12.1 x 10.0 x 8.6	" "	3.66 52
117	6.0	7 8	12.1 x 10.0 x 10.2	" "	4.36 52
88	8.0	10 0	14.0 x 11.7 x 10.0	" "	5.64 67
89	10.0	12 2	14.0 x 10.2 x 11.4	" "	7.14 67

50 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
102	0.5	1 11	7.0 x 7.0 x 5.7	0-19-25-33-40-50V	1.33 30
103	1.0	2 10	8.3 x 7.3 x 7.0	" "	1.94 36
104	2.0	5 0	10.2 x 8.9 x 8.6	" "	2.69 42
105	3.0	6 0	10.2 x 10.2 x 8.3	" "	2.94 52
106	4.0	9 4	12.1 x 11.4 x 10.2	" "	4.83 52
107	6.0	12 4	12.1 x 11.1 x 13.3	" "	7.14 67
118	8.0	18 9	13.3 x 13.3 x 12.1	" "	9.32 97
119	10.0	19 12	16.5 x 11.4 x 15.9	" "	11.68 97

60 VOLT RANGE

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
124	0.5	2 4	8.3 x 9.5 x 6.7	0-24-30-40-48-60V	1.35 36
126	1.0	3 0	8.9 x 7.6 x 7.6	" "	1.88 36
127	2.0	5 6	10.2 x 8.9 x 8.6	" "	2.94 42
125	3.0	8 8	11.9 x 9.5 x 10.0	" "	3.65 52
123	4.0	10 6	11.4 x 9.5 x 11.4	" "	5.78 67
120	6.0	16 12	13.3 x 12.1 x 12.1	" "	8.37 82
122	10.0	23 2	16.5 x 12.7 x 16.5	" "	13.85

LEAD ACID BATTERY CHARGER TYPES

Ref. No.	Amps.	Weight lb oz	Size cm.	Primary 200-250 Volt	For Charging 6 or 12 Volt Batteries	P & P £ p
45	1.5	1 9	7.0 x 6.0 x 6.0			1.34 30
5	4.0	3 11	10.2 x 7.0 x 8.3			2.03 42
86	6.0	5 12	10.2 x 8.9 x 8.3			3.07 52
146	8.0	6 4	8.9 x 10.2 x 10.2			3.69 52
50	12.5	11 14	13.3 x 10.8 x 12.1			5.20 67

Please note, these units do not include rectifiers

All ratings are continuous. Standard construction: open with solder tags and wax impregnation. Enclosed styles to order.

TRANSISTORS

TO MANUFACTURERS' FULL SPECIFICATIONS

BC107/108/109 9-0p each	2N 3055 68p each with mica and bushes	AD 161/162 60p pair with mica and bushes
25 + 7.5p	25 + 55p	25 + 55p
100 + 6.5p	100 + 45p	100 + 50p
500 + 6.0p	500 + 40p	500 + 45p
Minimum order 10 pieces this range.		1000 + 40p

★ Quantity prices on application

Also stocked: SEMICONDUCTORS • VALVES

MULTIMETERS • MAINS KEYNECTOR

ELECTROSIL METAL OXIDE RESISTORS

*Carriage via B.R.S.

BARRIE electronics

11 MOSCOW ROAD, QUEENSWAY

LONDON W2 4AH Tel: 01-229 6681/2

NEAREST TUBE STATIONS: BAYSWATER, QUEENSWAY

WW—086 FOR FURTHER DETAILS

Great new OFFER from DIOTRAN TRANSISTORS

AC107	15p	AD 149	45p	BC108	10p	BC177	17p	BF119	70p	BFX84	20p	EC431	15p	OC201	27p	2N524	55p	2N294	27p	2N3403	22p	2S323	50p
AC113	20p	AD 161	35p	BC109	11p	BC178	17p	BF152	35p	BFX85	27p	EC403	15p	OC202	27p	2N527	60p	2N2217	20p	2N3404	32p	2S324	£1.20
AC115	23p	AD 162	35p	BC113	25p	BC179	17p	BF153	35p	BFX86	22p	GET 880	27p	OC203	25p	2N696	12p	2N2218	25p	2N3405	45p	2S325	£1.20
AC125	17p	AD 163	50p	BC114	30p	BC182	20p	BF154	35p	BFX87	25p	MAT 100	15p	OC204	25p	2N697	15p	2N2219	27p	2N3414	20p	2S326	£1.20
AC128	17p	AD 164	50p	BC115	30p	BC181	22p	BF157	45p	BFX88	22p	MAT 101	17p	OC205	35p	2N698	24p	2N2220	22p	2N3415	20p	2S327	£1.20
AC129	17p	AD 171	£2.00	BC116	35p	BC182	20p	BF158	25p	BFY50	20p	MAT 120	15p	OC309	35p	2N699	55p	2N2221	22p	2N3417	37p	DIODES & RECTIFIERS	
AC128	17p	AD 171	£2.00	BC117	35p	BC182L	10p	BF159	30p	BFY51	20p	MAT 121	17p	P 346A	17p	2N706	7p	2N2222	27p	2N3525	75p	AA119	5p
AC144	17p	AD 172	£2.10	BC118	25p	BC183	15p	BF160	30p	BFY52	20p	MPE 102	43p	P 387	45p	2N706A	9p	2N2368	17p	2N3702	12p	AA120	5p
AC147K	17p	AF 114	17p	BC119	45p	BC183L	10p	BF162	30p	BFY53	17p	MPE 105	43p	OC271	43p	2N708	12p	2N2369	15p	2N3703	12p	BA116	27p
AC151	17p	AF 115	17p	BC125	35p	BC184	10p	BF163	35p	BSX19	15p	OC19	30p	ORP12	43p	2N709	45p	2N2359A	50p	2N3704	15p	BA125	22p
AC154	15p	AF 116	17p	BC126	35p	BC184L	13p	BF164	35p	BSX20	15p	OC20	50p	ORP60	40p	2N711	40p	2N2411	50p	2N3705	12p	BY100	15p
AC155	17p	AF 117	17p	BC132	25p	BC186	27p	BF165	35p	BSY25	15p	OC22	30p	ORP61	40p	2N717	42p	2N2412	50p	2N3706	12p	BY101	15p
AC156	17p	AF 118	30p	BC134	30p	BC187	27p	BF167	22p	BSY26	15p	OC23	33p	ST140	12p	2N718	24p	2N2646	55p	2N3707	13p	BY105	15p
AC157	17p	AF 124	27p	BC135	30p	BC207	17p	BF173	22p	BSY27	15p	OC24	45p	ST141	17p	2N718A	50p	2N2711	27p	2N3708	8p	BY114	12p
AC195	17p	AF 125	20p	BC136	30p	BC208	17p	BF176	35p	BSY28	15p	OC25	25p	TIS43	40p	2N726	27p	2N2712	22p	2N3709	8p	BY126	15p
AC196	17p	AF 126	20p	BC137	35p	BC209	17p	BF177	35p	BSY29	15p	OC26	25p	UT46	27p	2N727	27p	2N2714	25p	2N3710	10p	BY127	15p
AC197	20p	AF 127	20p	BC139	45p	BC212L	17p	BF178	45p	BSY38	15p	OC28	40p	V405A	25p	2N743	17p	2N2904	25p	2N3711	10p	BY130	15p
AC198	14p	AF139	33p	BC140	35p	BC231L	17p	BF179	50p	BSY39	15p	OC29	40p	V406A	25p	2N744	17p	2N2904A	30p	2N3819	40p	BY210	15p
AC199	14p	AF178	50p	BC141	35p	BC241	12p	BF180	30p	BSY40	30p	OC35	30p	ZG301	15p	2N914	17p	2N2905	25p	2N3820	£1.00	BY211	32p
AC176	23p	AF179	50p	BC142	45p	BC225	25p	BF181	30p	BSY41	35p	OC36	40p	ZG302	15p	2N918	30p	2N2905A	27p	2N3903	25p	BY212	30p
AC177	20p	AF180	50p	BC143	40p	BC226	35p	BF182	30p	BSY95	12p	OC41	20p	ZG303	15p	2N929	22p	2N2906	25p	2N3904	27p	BY213	35p
AC181	30p	AF181	50p	BC145	45p	BC317	12p	BF183	30p	BSY95A	12p	OC42	22p	ZG304	20p	2N930	25p	2N2906A	27p	2N3905	25p	BY216	35p
AC188	30p	AF186	45p	BC147	17p	BC318	12p	BF184	25p	bs105	£3.90	OC44	15p	ZG306	35p	2N131	20p	2N2907	25p	2N3906	27p	BY217	35p
AC117	25p	AF239	37p	BC148	12p	BC319	12p	BF185	30p	C1M1	60p	OC45	12p	ZG308	35p	2N132	22p	2N2907A	30p	2N4058	15p	BY218	30p
ACT18	10p	AF211	37p	BC149	17p	BC320	20p	BF188	30p	C400	30p	OC70	15p	ZG309	35p	2N1302	17p	2N2923	13p	2N4059	10p	BY219	25p
ACT19	22p	AF212	45p	BC150	17p	BC321	22p	BF194	23p	C407	25p	OC71	9p	ZG313	17p	2N1303	17p	2N2924	13p	2N4060	12p	DA5	17p
ACT20	20p	AL102	85p	BC151	20p	BC322	22p	BF196	24p	C424	17p	OC72	12p	ZG338A	15p	2N1304	20p	2N2925	13p	2N4061	12p	DA10	22p
ACT21	20p	AL103	85p	BC152	17p	BC323	17p	BF196	30p	C425	40p	OC74	12p	ZG334	15p	2N1305	20p	2N2926(G)	12p	2N4062	12p	DA17	7p
ACT22	15p	ASY26	25p	BC153	27p	BC324	20p	BF197	35p	C426	30p	OC75	15p	ZG345	15p	2N1306	22p	2N2926(V)	17p	2N5172	12p	DA70	7p
ACT27	15p	ASY27	30p	BC154	30p	BC325	17p	BF199	20p	C428	20p	OC76	15p	ZG371	13p	2N1307	22p	2N2926(O)	10p	2N5458	43p	DA79	8p
ACT28	15p	ASY28	25p	BC157	20p	BC326	17p	BF200	45p	C441	27p	OC77	25p	ZG378	10p	2N1308	27p	2N3010	80p	2S1034	75p	DA81	7p
ACT30	25p	ASY29	25p	BC158	17p	BC327	15p	BF222	80p	C442	35p	OC81	9p	ZG374	17p	2N1309	27p	2N3011	20p	2S1031	50p	DA85	7p
ACT32	25p	ASY30	25p	BC159	20p	BC328	17p	BF210	25p	C444	37p	OC80	9p	ZG377	27p	2N1613	20p	2N3053	20p	2S1024	45p	DA90	5p
ACT34	15p	ASY31	25p	BC161	13p	BC329	15p	BF211	17p	C450	17p	OC82	12p	ZG382	15p	2N1889	35p	2N3054	50p	2S1025	45p	DA91	7p
ACT35	15p	ASY32	25p	BC168	13p	BC330	15p	BF212	80p	C720	12p	OC83	25p	ZG382	15p	2N1890	45p	2N3055	60p	2S1030	50p	DA95	7p
ACT36	30p	ASY33	25p	BC169	13p	BC331	15p	BF213	30p	C722	25p	OC84	20p	ZG414	30p	2N1893	37p	2N3391	20p	2S1035	£1.00	DA202	7p
ACT37	15p	ASY34	25p	BC170	12p	BC332	10p	BF214	30p	C740	25p	OC139	15p	ZG417	25p	2N2160	60p	2N3392	17p	2S1036	£1.00	SD10	4p
ACT40	15p	ASY35	25p	BC171	13p	BC333	10p	BF216	30p	C742	25p	OC140	17p	ZG418	30p	2N2167	75p	2N3393	15p	2S1037	£1.00	SD19	4p
ACT41	15p	ASY36	25p	BC172	13p	BC334	10p	BF217	30p	C744	17p	OC170	15p	ZG419	30p	2N2448	60p	2N3394	15p	2S1038	60p	IN914	4p
ACT44	35p	ASY37	25p	BC173	13p	BC335	10p	BF218	30p	C746	17p	OC171	15p	ZG420	22p	2N2492	30p	2N3395	20p	2S1039	50p	IN916	5p
AD140	40p	AS21	40p	BC174	13p	BC336	10p	BF219	30p	C762	17p	OC200	25p	ZG444	30p	2N2993	30p	2N3402	22p	2S1040	45p	IN4148	6p
AD142	40p	BC107	10p	BC175	22p	BC337	10p	BF220	27p	C764	17p												

**10 MILLION DIODES
SILICON OR GERMANIUM**
—state which when ordering

250	50p.	10,000	£10.00
1000	£2.00	50,000	£30.00
5000	£7.00	100,000	£50.00

**2,000,000 SILICON
PLANAR TRANSISTORS**
TO18 P.N.P. & N.P.N TYPES

state which when ordering

100	£1.50	10,000	£90.00
500	£6.00	50,000	£400.00
1,000	£10.00	100,000	£825.00

**LINEAR INTEGRATED CIRCUIT
709/PC S.G.S.**

TO-5 can 8 lead. Full specification high gain Operational Amplifier data supplied. Lowest ever price.

QUANTITY	1-9	10-24	25-99	100-999
PRICE EACH	37p.	34p.	30p.	25p.

**BRAND NEW
UNI-JUNCTION TRANSISTORS**

BRAND NEW FULLY TESTED EPOXY CASE UNI-JUNCTION TRANSISTORS: Type TIS43 and BEN 3000 and replacement for 2N2846. Full data available. LOWEST PRICE AVAILABLE ANYWHERE. 100 off 20p each = £20; 500 off 17p each = £87.50; 1,000 off 15p each = £150. Sample devices 35p each on request.

SILICON PLANAR DIODES

HIGH QUALITY SILICON PLANAR DIODES. SUB-MINIATURE DO-7 Glass Type, suitable replacements for OA200, GA202, BAY38, IS130, IS940, 200,000 to clear at £4 per 1,000 pieces. GUARANTEED 80% GOOD. DA90 GERM. DIODES 30PW 45MA DO-7 GLASS. 30,000 Available New and Coded. Price £3 per 100, £11 per 500, £17 per 1,000 pieces. Once sold cannot be repeated.

DIOTRAN SALES
P.O. BOX 5, WARE, HERTS.
Full money-back guarantee
POSTAGE & PACKING 7p

THE WORLD'S FINEST

POWER AMPLIFIER! DC300



DC-coupled throughout, the DC300 offers unequalled reproduction of frequencies from DC to 20,000Hz. Users in the U.K. include The Post Office, CEBG, CERL, National Physical Lab., Road Research Lab., Queen Mary College, Universities at Bath, Salford, Manchester, and Southampton, and the Institute of Sound & Vibration. Laboratory uses include driving Vibrators, Stimulators and Motors, Servo loops, and many more. Full data available on request.

Frequency Response ±0.1 db Zero-20 KHz at 1 watt into 8 ohms. +0.6 db Zero-100 KHz. Less than 5° 0-10KHz.
Phase Response
Power Response ±1db Zero-20KHz at 150 watts RMS into 8 ohms.
Power at Clip Point Typically 190 watts RMS into 8 ohms, 340 watts RMS into 4 ohms per channel.
Total Output (IHF) Typically 420 watts RMS into 8 ohms, 800 watts RMS into 4 ohms.
T.M.D. Better than 0.03% at 1KHz at 190 watts level.
I.M. Distortion (60-7KHz 4:1) Less than 0.1% from 0.01 watt to 150 watts RMS into 8 ohms, typically below 0.05% (max. 0.08%).
Damping Factor Greater than 200 (Zero to 1KHz into 8 ohms at 150 watts RMS).
Hum and Noise (20-20KHz) 100db below 150 watts RMS output (unweighted, typical 110db).
Slew Rate 8 volts per micro-second. S-R is the maximum value of the first derivative of the output signal.
Dimensions 19in. standard rack mount (W.E. hole spacing), 7in height, 9 3/4in. deep (from mounting surface).
Weight 40 pounds net weight.
Finish Bright-anodized brushed-aluminum front-panel with black-anodized front extrusion, access door, and chassis.

PRICE £360

Sole Agents: MACINNES LABORATORIES LTD.
71 Oakley Rd., Chinnor, Oxon. Tel. Kingston Blount (0844) 52061

WW—087 FOR FURTHER DETAILS

DABAR AUDIO MIXER MODULES



A RECENT ADDITION TO OUR VERY POPULAR RANGE OF MIXER MODULES FOR STUDIO, P.A. & DISCOTHEQUE USE IS OUR SERIES UMF MODULES. THE MODULES, CONSTRUCTED ON GLASS-FIBRE PRINTED CIRCUIT MATERIAL ARE COMPLETE WITH A BLACK ANODISED FACIA PLATE WHICH CARRIES THE PRE-AMP CARD WITH THE FOUR CONTROLS: L.F., H.F., ECHO SEND & P.F.L. TOGETHER WITH A SLIDER FADER AS THE MAIN CHANNEL OUTPUT LEVEL CONTROL.

A TEN CHANNEL MIXER/LINE AMPLIFIER WITH VU METER IS AVAILABLE ON A MATCHING FACIA PLATE AND HAS AN EXPANDER INPUT AND PRESET ADJUSTMENT FACILITIES FOR VU ADJUSTMENT. THE LINE AMPLIFIER WILL DELIVER UP TO +20dBm.

INPUT MODULES UMF SERIES

- UMF1 200-600 ohm Mic (unbalanced)
- UMF2 50k Mic (unbalanced)
- UMF3 1.5mV Mag P/U R.I.A.A.
- UMF4 5mV Mag P/U R.I.A.A.
- UMF5 Crystal P/U 500mV
- UMF6 High level Tape/Tuner 5mV

MIXER/LINE AMPLIFIER MODULES

- MX/LNTA-F-VU mixer/line amp with VU meter
- MX/LNTA-F-S mixer/line amp less VU meter
- BPF1 Blanking Plate. PU11/30 30v Power unit for above modules

FACIA DIMENSIONS: 11.2" x 2.75"

PRICES: UMF1 -6 £15.00 each. MX/LNTA-F-VU £18.00 each. MX/LNTA-F-S £16.00 each. BPF1 £2.00 each. PU11/30 £8.00 each.

**BRAND NEW
TOP QUALITY COMPONENTS**

POWERTRAN ELECTRONICS

**FAST
SERVICE**

COMPONENTS FOR W.W. AMPLIFIER DESIGNS

30W BLOMLEY (New approach to class B)	
Semiconductor set	5-70
Resistors, capacitors, pots	1-85
F/Glass PCB	0-70
30W BAILEY (Single power rail)	
Transistor set	5-10
Resistors, capacitors, pots	1-45
F/Glass PCB	0-65
LINSLEY-HOOD CLASS A (Dec., 1970, circuit)	
2N3055 pair, BC212L, 2N1711	1-45
Resistors, capacitors, pot	1-80
F/Glass PCB	0-60
LINSLEY-HOOD 20W CLASS AB	
MJ481/491, MJE521, BC182L, BC212L, zener	3-35
Resistors, capacitors, pots	2-20
F/Glass PCB	0-70

Please state 8Ω or 15Ω
REGULATED 60V POWER SUPPLY
 A 5 transistor series stabiliser, suitable for a pair of Bailey or Blomley amplifiers, featuring very effective S/C protection. All components, including mech. parts, heat sink, fuses, etc.

Power supplies for other amplifiers also available
100W AMPLIFIER (Oct., 1970, Hardcastle & Lane)
 Designer, Texas Instruments approved kit has now undergone various improvements including facilities to up-rate power to 200W. Details in list LI21DI.
 Amplifier kit

23 mm. CARBON POTENTIOMETERS	
Single: Linear values: 100, 220, 470, 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2	0-11
Log values: 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2	0-11
Dual: Linear values: 10K, 22K, 47K, 100K	0-35
Log. values: 4K7, 10K, 22K, 47K, 100K, 2M2	0-35
Balance: Purpose designed; better than Log./A Log. No attenuation at mid point. 10K only	0-45



BAILEY/BURROWS STEREO PRE-AMP FRONT PANEL
 Part of metal work system. 13 in. by 4 1/2 in. silk screen printed, brushed 16 g. aluminium. Hole spacing is compatible with Linsley-Hood and Bailey/Burrows pre-amp PCBs on which the pots are directly mounted.

PRE-AMPS
 Each component set comprises of all specified resistors, capacitors, transistors, pots, including special balance control for stereo sets.
BAILEY/BURROWS (Aug., 1971)
 Stereo F/Glass PCB

SEMICONDUCTORS

2N699	0-30	BFY50	0-20
2N1613	0-20	MJ481	1-20
2N1711	0-25	MJ491	1-30
2N3053	0-20	MJE521	0-70
2N3055	0-55	MPSA05	0-30
2N3702	0-11	MPSA12	0-55
2N3703	0-10	MPSA14	0-35
2N3704	0-11	MPSA55	0-35
2N3705	0-10	MPSA66	0-40
2N3706	0-09	MPSH05	0-20
2N3707	0-11	MPSU05	0-60
2N3708	0-07	MPSU55	0-70
2N3709	0-09	TIP29A	0-50
2N3710	0-09	TIP30A	0-60
2N3711	0-09	TIP31A	0-60
2N3819	0-23	TIP32A	0-70
2N3904	0-25	TIP33A	1-00
2N3906	0-25	TIP34A	1-50
2N4058	0-12	TIP3055	0-60
2N4062	0-12	1B08T20	0-50
2N4302	0-60	1B40K20	1-40
40361	0-47	IN916	0-07
40362	0-57	IS44	0-05
BC107	0-10	IS920	0-10
BC109	0-10	IS2047	0-15
BC125	0-15	IS2056	0-15
BC126	0-22	IS2062	0-15
BC182K	0-10	IS2082	0-15
BC212K	0-12	IS2100	0-15
BC182L	0-10	IS2150	0-15
BC184L	0-11	IS2200	0-15
BC212L	0-12	IS3062	0-25
BF259	0-60	OA47	0-07

MATCHING & MICA WASHERS AT NO CHARGE

For further details please write for free list

**22 THE PANTILES,
BEXLEYHEATH, KENT**


U.K. POST FREE OVERSEAS AT COST MAIL ORDER ONLY

NEW SLIDER POTENTIOMETERS

As used on only the most exclusive of Audio Amplifiers and Mixers.
 European made, high quality moulded construction, suitable for both panel and PCB mounting.



	DIMENSIONS (SINGLE AND DUAL)		
LENGTH	87mm.	10K LOG SINGLE	0-40
WIDTH	10mm.	10K LOG DUAL	0-60
TRAVEL	55mm.	BLACK/CHROME KNOB	0-12

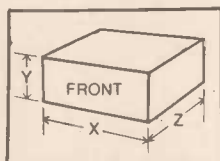

Contil Mod-2 instrument cases are ideal for development and cheaper for production. Made with PVC coated materials there is no paint to scratch, the surface is scuff resistant and easy to clean. Coated aluminium front and back panels gives easy cutting with rigidity and coated steel top, bottom and sides gives strength and ease of assembly. Three heights of cases, four widths and two depths give 48 different cases. Mod-2 means modern design, low cost, off the shelf delivery.

	X	Y	Z	1 off	P&P		X	Y	Z	1 off	P&P
A	4.5	3	8.5	2.20	18p	N	4.5	7	13	3.40	28p
B	4.5	7	8.5	2.50	28p	O	4.5	10	13	4.40	35p
C	4.5	10	8.5	3.05	28p	P	9	3	13	3.40	28p
D	9	3	8.5	3.05	28p	Q	9	7	13	4.40	35p
E	9	7	8.5	3.40	28p	R	9	10	13	5.40	35p
F	9	10	8.5	4.00	28p	S	13	3	13	4.40	35p
G	13	3	8.5	3.40	28p	T	13	7	13	5.40	35p
H	13	7	8.5	4.00	28p	U	13	10	13	6.60	45p
I	13	10	8.5	4.40	35p	V	18	3	13	5.40	35p
J	18	3	8.5	4.00	28p	W	18	7	13	6.60	45p
K	18	7	8.5	5.40	35p	X	18	10	13	8.00	45p
L	18	10	8.5	6.60	45p	G	Woodgrain			4.00	28p
M	4.5	3	13	2.50	28p						

Kit of Sinclair hardware inc. capacitors, plugs, sockets, screws, wire heat sink, fuse, fuse holder, etc. £3.40 P & P 22p.
 Sinclair punched case and chassis, Mod 2 type G in wood grain, £4.25 P & P 28p.

Type G is now available in simulated teak in wood grain finish and ideally suited for domestic equipment. Also available ready punched for Sinclair Project 80, with or without A.F.U. It is available with a set of fitting plugs, sockets, fuses, etc.



WEST HYDE DEVELOPMENTS LIMITED, RYEFIELD CRESCENT, NORTHWOOD HILLS, NORTHWOOD, MIDD., HA6 1NN. Telephone: Northwood 24941/26732. Telex: 923231
WW-089 FOR FURTHER DETAILS



'Brightcase'
INSTRUMENT CASE

"Brightcase" as an ideal housing for the new Rhodes Batch Flowmeter


NEW GOOD LOOKS

A drastically reduced number of parts and the smart look of anodised aluminium and black P.V.C. coated steel, combine to create a beautiful new case with a marked reduction in cost. Of standard 19" rack size, the Brightcase can be used freestanding, or one on top of another, or racked, using separate mounting brackets.

- (1) The Brightcase improves the appearance of any equipment.
- (2) The Brightcase is stable on any face. The front handle protrusion protects knobs, meters, etc. Protrusion at the rear protects connectors, cables, etc.
- (3) The Brightcase can be stacked vertically.
- (4) The Brightcase top and bottom panels are of textured black PVC coated steel.
- (5) The Brightcase is ideal for modular systems.
- (6) The Brightcase arrives completely assembled, in its special pack.

WEST HYDE

New simple construction

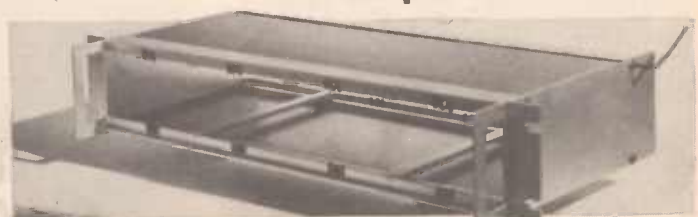

Send for literature and prices
 WEST HYDE DEVELOPMENTS LTD., RYEFIELD CRESCENT, NORTHWOOD HILLS, NORTHWOOD, MIDD., HA6 1NN. Telephone: Northwood 24941/26732

TEST EQUIPMENT

1. Marconi Carrier Deviation Meter TF.791B £55
Freq. Range: 4-250 MHz in 4 ranges
Dev. Range: 5-75 KHz in 3 ranges
2. Pye Wheatstone Bridge, 7435. Immaculate condition £55
3. Marconi Universal L.C. R. Bridge TF.868/1 £60
Measures Inductance $1\mu\text{H}-10\text{H}$ at 1KHz and
Capacitance $1\mu\text{F}-100\mu\text{F}$ 10 KHz
Resistance $1\Omega-10\text{M}\Omega$
4. Tinsley AC Stabiliser Type 5105B. Output: 2 amps max. £60
5. Marconi Sensitive Valve Voltmeter TF.1100 £48
Measures AC volts: 1mV-300V in 12 ranges
6. Marconi Distortion Factor Meter TF.142F £85
Freq. Range: 100-8,000 Hz in 4 ranges
7. Marconi Distortion Factor Meter TF.142E £45
Freq. Range: 100-8,000 Hz in 4 ranges
8. Solartron Pulse Generator Type CT395. Mint condition £70
9. Dawe Stroboscope Type I214B. 300-6,000 flashes/min. £22
10. Ediswan L.F. Oscillator R.666. £30
11. Solartron Oscillator OS.101 £30
Freq. Range: 25 Hz-250 KHz in 4 ranges
Output: 0-10V in 1 dB steps. 600 Ω
12. Solartron Oscillator Co.546 £35
Freq. Range: 25 Hz-500KHz in 5 ranges
Output: 0-10V in 1 dB steps. 75 Ω and 600 Ω
13. Solartron Digital Voltmeter LM902.2 £80
14. Muirhead Phasemeter Type D-729-AM plus Supply Unit D-729-AS. Complete. £120
15. Advance Transistorised Measuring Counter T.C.I. £30
16. Philips V.T.V.M. GM6017. 0-300V in 10 ranges. Freq. 2-200 KHz. £26
17. Pye Scalamp Galvanometer £22
18. Loxor Variable Delay Line. 417 μs . 680 Ω £20
19. Cambridge Instruments Versatile Galvanometer £15
20. British Physical Labs. Megohmmeter RM.175-CZ £18
21. Elliott Bros. Precision Portable Wattmeter. 0-750W £15
22. Sangamo-Weston AC Voltmeter Model S.82. £10
To B.S. 89 standard. Two ranges: 10V, 200V
23. Marconi Modulation Meter 3-72 MHz. TF.546 £20
24. Tinsley Vernier Potentiometer Model 4363A. £75
25. Marconi 'G' Magnification Meter TF.329G £45
26. Solartron Voltmeter LM903. £55
27. Marconi Pulse Generator TF675E. Freq. range 100-50KHz. Pulse length 0-15 μs -50 μs in 5 ranges. £38
28. Tinsley Universal Shunt Type 3000. £5
29. Solartron Laboratory Amplifier AWS. 51A. Range 15Hz-350KHz. £20
30. Ernest Turner Precision Voltmeter. £12
AC volts in 5 ranges. 5/10/25/50/250V F.S.D.
31. Dawe Wide Range L.F. Oscillator. 400C. 0-1Hz-1KHz in 4 ranges. £28
32. General Radio. U.H.F. Signal Generator. 804B. 8-330MHz in 5 ranges. O.P. 1 μV -20 μV . £18
33. Avo Testmeter. CT 38 £18
34. Marconi Valve Millivoltmeter TF 899. £10
35. Avo Valve Voltmeter CT. 208 £12
36. Hunts Capacitor Analyser and Resistance Bridge CRB. 3 £15
37. Advance R.F. Signal Generator G.1 £35
Freq. 13-250 MHz in 5 ranges
O.P. 1 μV -100mV. Mod. 1 KHz Sine/Sq.
38. Advance R.F. Signal Generator E.2. Model 2 £35
Freq. 100 KHz-100 MHz in 6 ranges
O/P 1 μV -100mV. A/F Mod.
39. Advance R.F. Signal Generator P.1 £28
Freq. 100 KHz-100 MHz in 6 ranges
O.P. 1 μV -100mV. A/F Mod.
40. Solartron L.F. Phase Sense Voltmeter VP.253 p.o.A.
41. Taylor R.F. Signal Generators
Freq. range 100 KHz-240 MHz in 8 ranges
Models 68 and 68 A/M £35
Model 67A £30
42. Advance Timer Counter TC 1A £55
43. Airmec Modulation Meter Type 210. P.o.A.
44. Cossor Model 1428 Oscilloscope Camera complete with Drive Unit Model 1429. £45
Film speeds 4/12/36 inches/sec.
45. Advance P.P.3 Power Supply. 2 x 30V. 1A d.c. £50
Variable.
46. Tektronix Plug-in Unit 53/54E £30
Low level Differential Calibrated AC Pre-amp. -05-10 Mv/cm.
47. E.M.I. Plug-in Modules Set of 3. Brand new. £60
882 Spike Generator
884 Black-White Generator
885 Window Generator
48. D.M.A.C. X-Y Plotter GDE 2243. P.o.A.
49. Electronic Associates Ltd. Veriplotter P.o.A.
50. Cambridge Pen Recorder. P.o.A.
51. Airmec Oscillator Type 858. £48
30 kHz-30 MHz.
52. Kelvin Hughes Chart Recorder. P.o.A.
53. Pye Portable Wheatstone Bridge 7384. £42
54. Muirhead Phase Meter D729AM. P.o.A.
55. Consolidated Electric Recording Oscillograph P.o.A.

56. Solartron T.F.A. Converter JX541A. P.o.A.
57. Pye Galvo Modulator SLE103. P.o.A.
58. Elliott Recorder CT93. P.o.A.
59. Dead Weight Tester 0-1000 P.S.I. P.o.A.
60. Turner Voltmeter 102S. P.o.A.

OSCILLOSCOPES

- E.M.I. WM16. Complete with Dual Trace Plug-in Amp./Differential Plug-in Amp./Trolley. £175
Solartron CD.1220. With Wide Band unit. £190
Solartron CD.1220. With Dual Trace unit. £220
Solartron CD.1220. With Differential Amp unit. £240
Cawkell Remscope SO.1. Storage Oscilloscope. £130
E.M.I. WM2. Complete with Amp Type 5. £30
E.M.I. WM8. £48
Solartron CD.643S. £55
Solartron CD.711S2. £75
Mullard L101 DB. £45
Solartron CD.643-2. £52
Mullard L.203 D.B. £55
Solartron CD.513. £45
Marconi TF.1330. £75
Solartron CD.1014.2. £70

MINIATURE GEARED MOTORS

- 240V AC. 1 rpm, 1/5 rpm, 240V AC Haydon 6 digit minutes counter. £2-40 P.P. 10p
240V AC. 12 rpm. £1-00 P.P. 10p
24V DC. 1 rpm. 80p P.P. 10p

SOLENOIDS

12V DC Operation. 2 1/2" x 1 1/2" dia. 50p each. P.P. 10p

T.V. CAMERA LENSES

- Rank Taylor Habson Vidital Lenses £25 each
Focal length 8 cm. Brand New
E.M.I. T.V. Camera Focus Coil Assemblies £10 each

WIRE-WOUND POTENTIOMETERS

- Colvern, Reliance. All values from 1 Ω -100K Ω . 1p each. P.P. 5p
360° wire-wound pots. Colvern
CLR/6605/418 10K Ω . £1-50 each
10-turn pots. Bourns. 10K Ω \pm 5% Lin. 0-25% £1-00 each
360° Precision Servo Potentiometers. Ether type 4004/17. 500 Ω . 3" dia. 1/4" spindle; 1/8" spindle £4-00 each

MULTITURN TRIMPOTS

Mec, Bourne, Painton, Reliance
10, 50, 100, 250, 500, 1K, 2K, 2K5, 5K, 10K, 20K, 25K ohms. 60p each. P.P. 5p

RELAYS

- 12V d.c. 2p make contacts. 15A. Magnetic devices G8-55564. 70p. P.P. 15p
G.P.O. Relays. 2000 Ω 2p c/o. H/D contacts 50p. P.P. 8p
Latching Relays. B. & R. Type H02/T.498 2p c/o. 380 Ω 98p. each P.P. 8p

PHOTOMULTIPLIERS

EMI Type 9524H. £15 each

D.C. TACHOGENERATOR

Sperry Type 4. 14V. 1000 RPM. £10 each

30 MIN. PROCESS TIMER

SAIA Type Kod 1 el. £8-50 each
Motor 220V. 50Hz.
Switch contacts. 10A. 380V. a.c.

SEMICONDUCTOR BARGAINS

(For a limited period only)

- | | | | |
|------------------------------|--|-----------------------|-----|
| Diodes and Rectifiers | | OA210 5A 400V | 30p |
| | | OA211 4A 800V | 40p |
| | | OA202 | 8p |
| | | BYX 36-300 1A 300V 5p | |
| | | BYX 36-600 1A 600V 6p | |
| | | BA112 | 10p |
| | | IN659 | 4p |
| | | IS100 750mA 600V | 6p |
| | | IS115 750mA 600V | 6p |
| | | IS103 750mA 400V | 5p |
| | | ZIB22 | 10p |
| | | BZY88C 6-2V | 10p |
| | | VR625-F-6-2V 2-25W | 15p |
| | | IN5256B | 10p |
| | | 2N3055 | 55p |
| Transistors | | BFY53 | 15p |
| | | 2N3053 | 20p |
| | | NKT222 | 20p |
| | | (AC128 Equivt) | 18p |
| | | NKT135 | 20p |
| | | (2N1305 Equivt) | 20p |
| | | 2N2398 | 75p |
| | | BC239B | 75p |
| | | (BC109 Equivt) | 8p |
| | | OC28 | 45p |

Quantity discounts: 25+ 10%, 100+ 20%
P.P. 5p under £1, over £1 free.

Dublilar Nitrogol Paper Capacitors. B.1096
4 μF . 20% 750V d.c. 60p. P.P. 12p

VIBRATORS

- Plessey Type 12 I.A.S.D.
12V. sep. drive, non-synchronous. 30p P.P. 10p
Plessey Type 614
6V. Non-synchronous. 30p P.P. 10p
24V. Type XC 354. 75p P.P. 10p

PAINTON METAL FILM RESISTORS

Type PMF60 1/4W. 1% Tol. 50 p.p.m.
94 Ω , 140 Ω , 150 Ω , 180 Ω , 200 Ω , 240 Ω , 300 Ω , 330 Ω , 360 Ω , 470 Ω , 560 Ω , 620 Ω , 720 Ω , 820 Ω , 1K, 1K2, 1K3, 2K, 2K4, 2K5, 2K7, 3K3, 5K6, 7K2, 24K, 39K, 40K, 50K, 100K, 200K, 240K, 300K, 430K, Type PMF.65 1/4W. 1% Tol. 50 p.p.m., 1K, 500K, 750K, 1M.
Price 1 off 6p each. 25 off 3p each. P.P. 5p under £1, over £1 free.

MINIATURE EPOXY ENCAPSULATED PHOTORESISTOR AND LAMP ASSEMBLY

Size: 1" x 1/4" x 1/4"
Max. Lamp Voltage: 20V d.c.
Cadmium sulphide photoconductive device
Mullard Type RPY.58
Max. power dissipation: 200mW
Max. cell voltage (d.c. and repetitive pk.): 50V
Initial dark resistance: 200K Ω (min.)
Initial illuminated resistance (IV applied voltage, 50 lux illumination): 0-35K Ω min.-1-4K Ω max.
Dozens of applications including: a.g.c. circuits, autofocus, tremelos, compressor limiters, etc., etc.
Available in either clear epoxy encapsulation 75p or black light-tight encapsulation. 85p P.P. 10p

VEROBOARD

Size	Drilled Printed Circuit with Copper Strips	Plain Drilled Uncovered
	0-1" matrix	0-15" matrix
2 1/2" x 5"	30p	18p
2 1/2" x 3 1/2"	25p	15p
3 1/2" x 5"	35p	—
3 1/2" x 3 1/2"	30p	—
17" x 2 1/2"	82p	50p
17" x 3 1/2"	97p	72p
17" x 5"	—	85p

VEROBOARD ACCESSORIES

- Vero Spot Face Cutter. 52p
Vero Pin Insertion Tool. 64p
Vero Pins
0-1" mat. 28p p. pack 36; £2-85 p. pack 1000
0-15" mat. 28p p. pack 36; £2-98 p. pack 1000

EDGE CONNECTORS

	0-1" Pitch	0-15" Pitch
24 way.	32p	8 way. 20p
36 way.	42p	16 way. 24p
		24 way. 32p

P.P. Under £1-00 10p; over £1-00 free

AUDIO PLUGS AND SOCKETS

- Din Continental Connectors
2 way 3 way 5 way 5 way
180° 240°
- | | | | | |
|----------------------------|-----|-----|-----|-----|
| Plug. | 12p | 15p | 17p | 17p |
| Chassis Mounting Skt. | 10p | 12p | 15p | 15p |
| In-line Socket. | 13p | 12p | 17p | 17p |
- Phono Connectors
Plug Plastic (red, blue, green, black, white). 6p
Plug Shielded (SPPS). 11p
Chassis Mounting Socket:
Single. 6p
2 way. 8p
3 way. 13p
4 way. 20p
Dual Phono Socket—In-line Connector (DJ1). 15p
Shielded In-line Photo Sockets (SPS1). 14p
- Jack Plugs and Sockets
2.5mm Sub-miniature
Plug Plastic (P25). 6p
Plug Shielded (CH204). 10p
Chassis Mounting Socket (S35P). 7p
In-line Socket (OC25). 6p
- 3.5mm Miniature
Plug Plastic (P35). 9p
Plug Plastic Long Barrel (H304). 10p
Plug Shielded (CH304). 11p
Chassis Mounting Socket (S35P). 7p
In-line Socket (OC35). 10p
- | Standard Size | Mono | Stereo |
|--|------|-------------|
| Plug Plastic. (P31) | 12p | 22p (P232) |
| Plug Shielded. (SP31) | 18p | 28p (SP32) |
| In-line Socket. (OC30) | 25p | 30p (OC64) |
| Chassis Mounting Socket (OC34) | 14p | 20p (SS34) |
| Chassis Mounting Socket Insulated. (SISS) | 22p | 28p (SSBBB) |

T.V. AERIAL CO-AXIAL PLUGS AND SOCKETS—BELLING-LEE

- Co-axial Plug (L734P). 10p
Co-axial Free Socket (L734J/AL). 20p
Co-axial Socket—Chassis Mounting Flush (L734/S). 10p
Line Connector—double-ended for above plugs (L616). 16p
Co-axial Socket—Surface Chassis Mounting Moulded (L603). 12p

CAR RADIO ACCESSORIES

- Car Radio Aerial Plug (NCP2). 15p
Line Coupling for above plug (NCC). 15p
Fuse-holder Auto In-line (NFH). 10p
P.P. Under £1-00 10p; over £1-00 Free

C. T. ELECTRONICS

267 ACTON LANE, LONDON, W.4 01-994 6275

Nearest Underground—Chiswick Park (District Line); Acton Town (Piccadilly Line). Bus Routes: E3, 88, 207, 15, 7, 260.

Please Note: As yet we do not have a catalogue available. Any queries please phone or call at the above address

Business Hours: MONDAY to SATURDAY 9.30 a.m. to 6 p.m. WEDNESDAY 9.30 a.m. to 1 p.m.

WANTED. SURPLUS OR REDUNDANT COMPONENTS AND TEST EQUIPMENT

FM TUNER

NELSON-JONES

Approved parts for this outstanding design (W.W. April 1971).
Featuring 0.75 μ V sensitivity. Mosfet front end.
Ceramic I.F. strip. Triple gang tuning, $\frac{1}{2}$ V r.m.s.
output level, suitable for phase locked decoder,
as below. Designer's own P.C.B.

All parts including P.C.B. S.A.E. please lists.

PHASE LOCKED STEREO DECODER PORTUS AND HAYWOOD

Approved kit for this superb decoder (W.W. Sept. 1970).
Featuring 40dB separation up to 10kHz. NO COILS.
Negligible spurious tones (birdies). Simple setting up.
Suitable for wide variety of tuners including the
NELSON-JONES TUNER as above

Complete decoder kit **£8.97**, p.p. & ins. 16p

New IC: Stabilised PSU. S/C, overload protected, low
ripple. **£3.55**, p.p. 19p

LIGHT EMITTING DIODES (Red)

Hewlett Packard panel or PCB mounting with free mounting
clip—clear or black. Order LED1.

Monsanto miniature PCB mounting with radial leads.
Order LED2. Please add postage.

NOW ONLY 39p each with connection data
RESISTORS. $\frac{1}{4}$ W 5% Low Noise Carbon Film. 10 ohms-4.7M E12
1-9 1p., 10-99 0-9p. each. Please add postage.

INTEGREX LIMITED
P.O. BOX 45 DERBY DE1 1TW

Train for television

Course commences 6th September, 1972

This is your opportunity to train as a
television and radio engineer on our full-time
Two-Year College Diploma Course specially
designed to cover the examinations of the
City and Guilds Radio, Television and
Electronics Technicians' Certificate.
Full theoretical and practical instruction on
all types of modern receivers — including
the latest colour sets.

Minimum entrance requirements are Senior
Cambridge or 'O' Level, or equivalent in
Mathematics and English.

Please send free prospectus to:

Name _____

Address _____

THE PEMBRIDGE COLLEGE OF ELECTRONICS
(Dept. ww5) 34a Hereford Rd., London W2 5AJ

MULTI-RANGE PORTABLE AC/DC RECORDING VOLTMETER TYPE H390



Specification:

Measurement ranges:
AC and DC 5-15-50-150-250-
500mA—1.5—5 amps.
5-15-50-150-250-500V
DC only 150mV
Accuracy 1-5% DC. 2-5% AC
Frequency Range 45 to 1,000c/s
Damping Time 2 second maximum
Chart width 100 mm.
Chart Speeds 20-60-180-600-1,800-
5,400 mm/hr.
Chart Drive 220-250V. AC 5c/s
Overall Dimensions 170 x 265 x 305 mm.
Weight 22 lb.
Supplied brand new complete with instruction
manual, chart paper, spare pen,
one bottle of ink, pen filler, 2 sets change gears, scale and connecting leads.
£78.00

TEN CHANNEL EVENT RECORDER TYPE H30

A robust instrument designed for panel
mounting or portable use. Each channel con-
sists of a 12-volt rotary relay to which a
siphon pen large ink reservoir is fitted. Current
consumption is approx. 120mA per pen.



Chart Speeds 20-60-180-600-1,800-
5,400 mm/hour
Chart Width 100 mm.
Chart Drive 220-250V
Overall Dimensions 160 x 160 x 255 mm.

Supplied brand new with instruction manual, chart paper,
two bottles of ink, pen blower, pen filler, two spare move-
ments with pens and two sets of change gears.
£52.00



MULTIMETER TYPE C.1085

Specification:

DC volts 6—1.2—3—12—60—120—300—
1.2KV
AC volts 3—12—60—300—600—1.2KV
DC Current .30 μ A—6—60—300mA—12 amps
Resistance .1—100—1K—10K ohms
Sensitivity .DC 100,000 ohms per volt
AC 10,000 ohms per volt

Price **£14.00**



NUMICATOR PRICE LIST

End Reading	Quantity	GR10M/U (Clear)	Price each (less base)
1-3			£1.40
4-10			£1.35
11-25			£1.30
26-100			£1.20

Price Base. Bases 20p each.

Side Reading	38m/m Lead	(Amber)
XX3/FA	38m/m Lead	(Red)
XX3/F	6m/m Lead	(Red)
XX3A/F	6m/m Lead	(Clear)
XX3A	38m/m Lead	(Red)
XX11/F	38m/m Lead	(Amber)
XX23/FA	38m/m Lead	
1-3	£1.15 each	
4-10	£1.10 each	
11-25	£1.05 each	
26-100	95p each	

All Post Free

750 WATT LIGHT DIMMER

A solid state thyristor controlled light dimmer
designed for simply fitting into a standard plaster
depth box in place of the switch. Use for dimming
the light for watching television, in children's bed-
rooms or can be built into a box and used as a
variable speed device for electric drills.

**SMALL QUANTITY ONLY
CANNOT BE REPEATED**
£4.95 each, p. & p. included.

AC/DC MULTIMETER & TRANSISTOR TESTER TYPE U4341

Specification:

DC Voltage 0-3-1.5-6-30-60-150-300-900V
AC Voltage 1.5-7.5-30-150-300-750V
DC Current 0-08-0.6-6-60-600mA
AC Current 0-3-3-30-300mA
Resistance 0-3-5-50-500K ohms. Range
may be extended to 5
megohms with the use of an
external power supply 35-40V
Transistor Collector cut off current 60 μ A
Parameters. DC current gain hFE 10-350
Accuracy DC ranges 2-5%
AC ranges 4-0%
hFE 5-0%
Sensitivity DC 16,700 ohms per volt
AC 3,300 ohms per volt
Voltage drop at the terminal. DC Current 0-80V
AC Current 1-5V

Supplied brand new complete with operator's
manual, probes, leads, and carrying case.
£10.50

UNIVERSAL METERS

Type U4312 Type U4313
DC Current, mA 300 50-120
DC/AC Current mA. 1.5-6-15-60-
150-500 0.6-3-15-
60-300
DC/AC current A 1.5-6 15
DC Millivolts 75 75
DC/AC Volts 0-3-1.5-7.5- 1.5-3-7.5-
30-60-150- 15-30-60-
300-600-900 150-300-
600
DC Resistance, Kiloohms 0-2-3-30 0-5-5-50-
500
DC Resistance, Additional Ranges 300 K ohms. 5 megs
3 megs
using external source
12-5V 140V 41V
Capacity using external source
of 220V 0-5 μ F
Transmission Level 10 to
+12dB
Accuracy Ranges AC 1-5% AC 2-5%
DC 1% DC 1-5%
Sensitivity ohms DC 667 DC 20,000
per volt AC 667 DC 2,000

PRICE £9.75 £10.50

Both instruments are supplied with carrying
case, test leads and operating instructions.
All units are BRAND NEW and are
guaranteed for twelve months, subject to
our conditions.

ELECTRONIC BROKERS LIMITED
49-53 Pancras Road, London NW1 2QB
Tel. 01-837 7781 Telex 267307
SEE ALSO PAGE 78

CROUZET GEARED MOTORS (Self Start)
 T832T, 12v, 50Hz, 15 r.p.m. $\frac{1}{2}$ " x $\frac{1}{2}$ " dia. shaft £1-00
 T832, 24v, 50Hz, $\frac{1}{2}$ " r.p.m. $\frac{1}{2}$ " x $\frac{1}{2}$ " dia. shaft £1-00
HORMAN GEARED MOTORS (Self start)
 MK1, 60v, 50Hz, $\frac{1}{2}$ " r.p.m. $\frac{1}{2}$ " x $\frac{1}{2}$ " dia. shaft £1-00
 MK6, 230v, 50Hz, $\frac{1}{2}$ " r.p.m. $\frac{1}{2}$ " x $\frac{1}{2}$ " dia. shaft £1-75
 MK6, 110v, 60Hz, $\frac{1}{2}$ " r.p.m. $\frac{1}{2}$ " x $\frac{1}{2}$ " dia. shaft £1-15
 MK7, 60v, 50Hz, $\frac{1}{2}$ " r.p.m. $\frac{1}{2}$ " x $\frac{1}{2}$ " dia. shaft £1-00
 MK8, 125v, 50Hz, $\frac{1}{2}$ " r.p.m. $\frac{1}{2}$ " x $\frac{1}{2}$ " dia. shaft £1-35

MULLARD MULTIPLE GEARED MOTORS (Self Start)
 AU5020, 24v, 50Hz, 0.5W, 250 r.p.m. $\frac{1}{2}$ " x $\frac{1}{2}$ " dia shaft 50p
 AU 5005/02, 220 V., 50Hz., 1.5W, 250 r.p.m. 10T Pinion 75p
 AU5050/02, 110/220V., 50Hz., 2W., 250 r.p.m. 10T Pinion £1-25
 AU5050/94, 24/48v., 50Hz., 2W., 250 r.p.m. 10T Pinion £1-00
 AUS100/04, 117v., 60Hz., 7W., 300 r.p.m. $\frac{1}{2}$ " x $\frac{1}{2}$ " dia shaft £1-60
 AU5300/80EE, Gearbox only, Ratio 1250:1 For use with 5050/02 and 5050/94 Motors Above £1-50
 Some items equipment all checked before despatch (prices are Post and packing paid in U.K.)
Klaxon Geared Motor Square body, 2 $\frac{1}{2}$ " x 2 $\frac{1}{2}$ " x 2", one r.p.m., torque—2 lb. in. 240v. A.C., 50Hz. £5.25 (Post paid.)

DESSYN POSITION TRANSMITTERS AND RECEIVERS
 For 24V D.C. operation. We have available various types of Transmitters and Blank Dial Receivers. Please advise us of your approximate requirements and we will be pleased to quote.

3 WATT FLUORESCENT FITTINGS (complete with lamps)
 These industrial fittings are extremely attractive and comprise a cast main housing together with an opal perspex diffuser. Overall dimensions: 14" long, 4" wide and 3 $\frac{1}{2}$ " deep. These fittings are for 240v 50Hz operation. The front reflector is maintained in position by two triangular-headed locking bolts. £2-95 (inc. p. & p.).

TRANSFORMER/RECTIFIER UNIT
 Comprising a 380-440v 3 phase, 50Hz input transformer and stud mounted silicon rectifiers. Output is 220v D.C. 18 amps. Ideal for operation of D.C. motors etc. £27-50 (including carriage U.K. Mainland).

CRT DEFLECTION YOKES
 These are designed to provide a radial time base in synchronism with a Magalip Transmitter. Price on application.

ETHER ELECTROMETHODS LOW INERTIA INTEGRATING MOTORS
 Available ex-stock at extremely low prices. For 1-5, 6, 12 and 24V operation in stock.


Mike Headset Assembly No. 10 with moving coil headphones and microphone. Brand new condition in original manufacturers' boxes. £1-50 (Post paid).

Current Transformers, 100-5 amps. £1-75 (Post paid).
R.F. Connectors. A selection of R.F. plugs and sockets at a give away price, including N, BNC, UHF, Burnedpt, etc. Cut off leads and thus not suitable for sale as new items. 6 for £1 (Post paid), 40 for £5 (Post paid).

AERIAL DIRECTION INDICATING KIT
 This set comprises a pair of Magslips to provide remote indication of aerial azimuth and comprises a transmitter and receiver. The transmitter is directly coupled to the remote aerial and the receiver can be mounted at the control point, to provide immediate and continuous indication of aerial position. Supply voltage required is 50v 50Hz and the price £5.75 (P.D.) including a pointer for the receiver. The suggested use of these items would include a mains operated, geared motor to drive the aerial, controlled from the position to which is fed back position information by the magslip link. Transformers to provide 50v 50Hz from 240v A.C. £1-95 each. (P.Pd.)

SPECIAL CABLE OFFER
 1 core DEF 12c-45 (1X 14/0076" screened) 85p per 100 yds.
 1 core DEF 12 1/2" 45 colours, our choice 65p per 100 yds.
 1 core Uniprennet 6 £1-25 per 100 yds.
 1 core Unitorsilmet 14 £2-25 per 100 yds.
 1 core Unitorsilmet 12 £2-00 per 100 yds.
 1 core Uniprennet 24 (1X 110/0076") £2-75 per 100 yds.
 1 core Unipren 4 £1-25 per 100 yds.
 6 core Sextocorvinmet small No. 1 (6X 14/0076") £12-00 per 100 yds., 16p p. yd.
 6 core Sextocorvinmet No. 2 £7-00 per 50 yds., 18p p. yd.
 8 core Octocorvet No. 1 or No. 2 £8-50 per 50 yds., 21p p. yd.
 10 core Decorvinmet No. 3 £10-00 per 50 yds.
 18 core 18 Corvinmet No. 3 £17-50 per 50 yds., 45p p. yd.
 25 core 18LD £23-50 per 50 yds., 60p p. yd.
 Conductors and Screened 25 core 25 Corvinmet No. 2 (18 x 23/0076") + 7 x 14/0076" £25-00 per 50 yds., 62p p. yd.
 25 core 25 Corvinmet small £26-50 per 50 yds., 65p p. yd.
 (N.B. 'Met' is screened overall). Post paid U.K.
 All carriage paid U.K. Mainland. Complete list of cables on request.

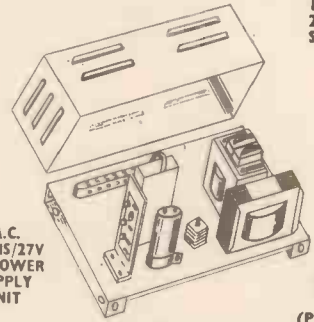FLOODLAMPS
 For use with back reflectors by internationally famous company. 200w, 250v G.E.S.—£1-50 per 4. £7-50 per pack of 25 (post paid). Also 300w, 240v G.E.S.—£1-50 per 3. £4-50 per pack of 12 (post paid). These lamps are fitted with front silvered bulbs to enhance reflection from the fitting.



MAINS TO 27V 500mA STABILISED

£3-65 EACH (P.Pd.U.K.)

A.C. MAINS TO 27V D.C. POWER SUPPLY UNITS.
 These interesting 27V 0-5A units (will happily provide 700mA indefinitely) are built into an attractive grey-finished instrument case, provision being made for base or side mounting. Cable entry grommets are mounted in the base of the unit. The choke capacity smoothed output is solid state stabilised against variation in input voltage and output current, and input and output fuses with spares are fitted. The output operates a built-in S.P.C.C.O. relay to switch for instance an alarm circuit. Input voltage is 200-250V, A.C. in 10V steps, while the transformer secondary carries two taps. All terminations to a Grelco block. There is adequate room for other equipment within the ventilated case, which is 12" x 10" x 6" deep. Our price, brand new in carton with circuit, only £3.65.

DRY REED INSERTS

Overall length 1.85" (Body length 1.1")
 Diameter 0.14" to switch up to 500 mA at up to 250v D.C. Gold clad contacts. 62 $\frac{1}{2}$ p per doz. £3-75 per 100; £27-50 per 1,000; £250 per 10,000. All carriage paid.
 Heavy duty type (body length 2") diameter 0.22" to switch up to 1A. at up to 250V, A.C. Gold clad contacts, £1-25 per doz., £6-25 per 100; £47-50 per 1000; £450 per 10,000. All carriage paid.

SPECIALIST STOCKISTS OF SERVOMOTORS, SYNCHROS, MAGSLIPS AND PLUGS AND SOCKETS

Servo and Electronic Sales Ltd

Electrical and Servo Control Engineers - Electrical Suppliers - Engineering Stockists - Aeronautical Suppliers
 Redg. Office: 45a HIGH STREET, ORPINGTON, KENT. Phone: Orpington 31066
 Postal orders and Technical enquiries to 19 MILL ROAD, LYDD, KENT (Works). Phone: Lydd 20252 (STD 0679) or 67 LONDON ROAD, CROYDON, SURREY (Retail Branch and Instrument Repairs).
 Phone: 01-488-1512 (Croydon)

MARSHALL'S INTEGRATED CIRCUITS

NEW LOW PRICES • LARGEST RANGE • BRAND NEW • FULLY GUARANTEED

SEE OPPOSITE PAGE FOR OPTOELECTRONICS AND SPECIAL OFFER ON NIXIE TUBES

BCA LINEAR ICS				MOTOROLA				PLESSEY				MULLARD TTL				MULLARD & SIEMENS LINEAR									
Type	1-24	25-99	£	Type	1-24	25-99	£	Type	1-24	25-99	£	1-11	12-24	£	1-11	12-24	£	1-11	12-24	£					
CA3000	1-80	1-40	£	CA3049	1-60	1-43	£	CA3059	1-65	1-46	£	SN7420	0-20	0-18	£	SN74107	0-82	0-49	£	FJH101	0-87	£	TAA241	1-30	£
CA3001	2-89	2-40	£	CA3050	1-84	1-64	£	CA3060	4-91	4-37	£	SN7423	0-51	0-47	£	SN74110	0-80	0-75	£	FJH121	0-87	£	TA230	4-00	£
CA3002	1-80	1-30	£	CA3051	1-34	1-20	£	CA3062	2-55	2-27	£	SN7405	0-48	0-45	£	SN74111	1-57	1-45	£	FJH141	0-87	£	TA243	1-50	£
CA3004	1-80	1-00	£	CA3052	1-85	1-47	£	CA3064	1-20	1-07	£	SN7427	0-48	0-45	£	SN74118	1-30	1-25	£	FJH161	0-87	£	TA263	0-70	£
CA3005	1-17	1-05	£	CA3053	0-46	0-41	£	CA3065	1-20	1-07	£	SN7430	0-80	0-75	£	SN74119	1-92	1-80	£	FJH171	0-91	£	TA283	0-80	£
CA3006	2-80	2-40	£	CA3054	1-09	0-97	£	CA3075	1-13	1-00	£	SN7432	0-48	0-45	£	SN74122	0-50	0-47	£	FJH221	0-87	£	TA300	2-00	£
CA3007	2-83	2-34	£	CA3055	2-40	2-13	£	CA3076	1-13	1-00	£	SN7433	0-80	0-75	£	SN74123	2-85	2-70	£	FJH231	0-87	£	TA320	0-65	£
CA3008	1-80	1-40	£					CA3090Q	3-46	3-09	£	SN7434	0-80	0-75	£	SN74124	2-85	2-70	£	FJH241	0-87	£	TA340	2-10	£
CA3008A	2-86	2-64	£									SN7437	0-64	0-60	£	SN74125	1-40	1-35	£	FJH251	3-12	£	TA360	0-50	£
CA3010	1-37	1-23	£									SN7438	0-64	0-60	£	SN74126	3-52	3-40	£	FJH261	0-87	£	TA380	1-30	£
CA3010A	2-53	2-25	£									SN7439	0-80	0-75	£	SN74127	1-40	1-35	£	FJH271	0-87	£	TA400	0-65	£
CA3011	0-74	0-65	£									SN7440	0-23	0-21	£	SN74128	2-20	2-10	£	FJH281	0-87	£	TA420	0-70	£
CA3012	0-69	0-79	£									SN7441A	0-87	0-83	£	SN74129	1-40	1-35	£	FJH291	0-87	£	TA440	0-50	£
CA3013	1-05	0-94	£									SN7442	0-85	0-81	£	SN74133	1-40	1-35	£	FJH301	0-87	£	TA460	0-50	£
CA3014	1-24	1-10	£									SN7443	2-86	2-70	£	SN74134	2-20	2-10	£	FJH311	0-87	£	TA480	0-50	£
CA3015	2-09	1-86	£									SN7444	2-86	2-70	£	SN74135	1-68	1-60	£	FJH321	0-87	£	TA500	0-50	£
CA3015A	3-40	3-03	£									SN7445	2-86	2-70	£	SN74136	1-68	1-60	£	FJH331	0-87	£	TA520	0-50	£
CA3016	2-46	2-18	£									SN7446	1-00	0-95	£	SN74137	1-92	1-82	£	FJH341	0-87	£	TA540	0-50	£
CA3016A	3-73	3-38	£									SN7447	1-00	0-95	£	SN74138	1-80	1-75	£	FJH351	0-87	£	TA560	0-50	£
CA3018	0-84	0-75	£									SN7448	1-00	0-95	£	SN74139	2-60	2-55	£	FJH361	0-87	£	TA580	0-50	£
CA3018A	1-10	0-99	£									SN7449	1-00	0-95	£	SN74142	4-26	4-10	£	FJH371	0-87	£	TA600	0-50	£
CA3019	0-84	0-75	£									SN7450	0-20	0-18	£	SN74143	2-20	2-10	£	FJH381	0-87	£	TA620	0-50	£
CA3020	1-26	1-13	£									SN7451	0-20	0-18	£	SN74144	2-20	2-10	£	FJH391	0-87	£	TA640	0-50	£
CA3020A	1-80	1-43	£									SN7452	0-43	0-41	£	SN74145	4-45	4-20	£	FJH401	0-87	£	TA660	0-50	£
CA3021	1-56	1-39	£									SN7453	0-20	0-18	£	SN74146	6-40	6-10	£	FJH411	0-87	£	TA680	0-50	£
CA3022	1-30	1-18	£									SN7454	0-20	0-18	£	SN74147	6-40	6-10	£	FJH421	0-87	£	TA700	0-50	£
CA3023	1-26	1-13	£									SN7455	0-20	0-18	£	SN74148	4-38	4-18	£	FJH431	0-87	£	TA720	0-50	£
CA3026	1-00	0-80	£									SN7456	0-40	0-38	£	SN74149	2-40	2-30	£	FJH441	0-87	£	TA740	0-50	£
CA3028A	0-74	0-65	£									SN7472	0-32	0-30	£	SN74150	2-64	2-55	£	FJH451	0-87	£	TA760	0-50	£
CA3028B	1-05	0-94	£									SN7473	0-43	0-41	£	SN74151	2-64	2-55	£	FJH461	0-87	£	TA780	0-50	£
CA3029	0-97	0-77	£									SN7474	0-43	0-41	£	SN74152	2-12	2-05	£	FJH471	0-87	£	TA800	0-50	£
CA3029A	1-65	1-47	£									SN7475	0-45	0-44	£	SN74153	1-80	1-70	£	FJH481	0-87	£	TA820	0-50	£
CA3030	1-37	1-23	£									SN7476	0-45	0-44	£	SN74154	1-80	1-70	£	FJH491	0-87	£	TA840	0-50	£
CA3030A	2-53	2-25	£									SN7477	0-70	0-65	£	SN74155	4-80	4-80	£	FJH501	0-87	£	TA860	0-50	£
CA3033	2-53	2-25	£									SN7478	1-40	1-35	£	SN74156	4-80	4-80	£	FJH511	0-87	£	TA880	0-50	£
CA3033A	4-26	3-90	£									SN7479	0-87	0-82	£	SN74157	1-80	1-70	£	FJH521	0-87	£	TA900	0-50	£
CA3035	1-25	1-10	£									SN7480	0-70	0-65	£	SN74158	4-80	4-80	£	FJH531	0-87	£	TA920	0-50	£
CA3036	0-73	0-65	£									SN7481	1-40	1-35	£	SN74159	4-80	4-80	£	FJH541	0-87	£	TA940	0-50	£
CA3037	1-65	1-47	£									SN7482	0-87	0-82	£	SN74160	1-80	1-70	£	FJH551	0-87	£	TA960	0-50	£
CA3037A	2-53	2-25	£									SN7483													

LARGEST STOCK

WIDEST SELECTION

LOW PRICES AND RETURN OF POST SERVICE

TRANSISTORS Brand new and fully guaranteed. PLEASE NOTE:—Matching charge (Audio Transistors only) 15p extra per pair. Many more semi-conductors in stock. Please enquire for types not listed.

Table listing various electronic components such as transistors, diodes, and resistors with their respective part numbers and prices.

SILICON RECTIFIERS table listing PIV ratings (50, 100, 200, 400, 600, 800, 1000, 1200, 1400) and prices for different types.

DIODES AND RECTIFIERS table listing various diode models like IN914, IN916, IN4007, etc., and their prices.

MAINS TRANSFORMERS table listing transformer models like 1 amp Charger, 2 amp Charger, etc., and their prices.

TRIACS table listing triac models like SC35D, SC36D, etc., and their prices.

INTEGRATED CIRCUITS SEE OUR ADVERTISEMENT ON OPPOSITE PAGE. SHOWING NEW I.C.s AT NEW LOW PRICES.

THYRISTORS table listing thyristor models like PIV 50, 100, 200, 300, 400 and their prices.

VEROBOARD table listing board sizes and prices for different matrix configurations.

RESISTORS table listing resistor values and prices for different series.

Wire Wound table listing wire-wound resistor values and prices.

"SCORPIO" Capacitor discharge ignition system. (as published in Practical Electronics, Nov. 1971).

COMPLETE KIT £10.00 P. & P. 50p.

OPTOELECTRONICS

Table listing optoelectronic components like MINITRON 7 SEGMENT INDICATOR, DRIVER FOR ABOVE, etc., and their prices.

NEWS! NEWS! NEWS!

Our associate company CONCORDE INSTRUMENT Co. is now a franchised distributor for SIEMENS, JERMYN IND., SSDI and THOMSON C.S.F.

THERMISTORS (MULLARD) table listing thermistor models like R53 (STC), K151 (Siemens), etc., and their prices.

PANEL METERS table listing meter models like 38 Series—FACE SIZE 42 x 42 mm, etc., and their prices.

MULLARD C280 M/FOIL CAPACITORS table listing capacitor models and their prices.

PRESETS Carbon Miniature and Sub miniature. Vertical and Horizontal. 0.1 watt, 0.2 watt, all at 0.06 each. 0.3 watt 0.075.

CARBON POTENTIOMETERS table listing potentiometer models and their prices.

Log. or Lin. With switch, Wire-wound Pots (3 wats), Twin-Ganged Stereo Pots. (Log. and Lin.) Less Switch 0.40

HEAT SINKS table listing heat sink models and their prices.

ZENER DIODES table listing zener diode models and their prices.

Antex ISW. Soldering Iron table listing soldering iron models and their prices.

POSTAGE AND PACKING CHARGES table listing postage and packing charges for different regions.

ALL PRICES SUBJECT TO ALTERATION WITHOUT PRIOR NOTICE

Telex 21492 A. MARSHALL & SON LTD 28 CRICKLEWOOD BROADWAY, LONDON, N.W.2

Send 15p FOR NEW COMPREHENSIVE PRICE LISTS CALLERS WELCOME Hours: 9-5.30 pm Mon-Fri 9-5 pm Sat

BI-PRE-PAK



TELEPHONE DIALS
Standard Post Office type
Guaranteed in working order

ONLY 50p

COMPLETE TELEPHONES



NORMAL HOUSEHOLD TYPE
AS SUPPLIED TO THE POST OFFICE
EX. G.P.O.

NOW at only 95p
P & P 35P EACH

NEW TESTED AND GUARANTEED PAKS

B2	4	Phot Cells, Sun Batteries, 0.3 to 0.5V, 0.5 to 2mA	50p
B79	4	IN4007 Sil. Rec. diodes, 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B89	200	Mixed Capacitors. Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors. Approx. quantity, counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values	50p
H8	4	BY 127 Sil. Recs. 1000 PIV 1 amp, plastic	50p
H9	2	OC71 Light Sensitive Photo Transistor	50p
H12	50	NKT 155/259 Germ. diodes, brand new stock clearance	50p
H18	10	OC71/75 uncodded black glass type PNP Germ.	50p
H19	10	OC81/81D uncodded white glass type PNP Germ.	50p
H28	20	OC200/1/23 PNP Silicon uncodded TO 5 can	50p
H29	20	OA47 gold bonded diodes codded MCS2	50p

NEW UNMARKED UNTESTED PAKS

B66	150	Germanium Diodes Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	50	Sil. Diodes sub. min. IN914 and IN916 types	50p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1, 2N706A, BSY95A, etc.	50p
B1	50	Germanium Transistors PNP, AF, and RF.	50p
H6	40	250mW Zener Diodes DO-7 Min. Glass Type	50p
H10	25	Mixed volts, 1 1/2 watt Zeners. Top hat type	50p
H17	20	3 Amp. Silicon Stud Rectifiers. Mixed volts	50p
H15	30	Top Hat Silicon Rectifiers, 750mA Mixed volts	50p
H16	8	Experimenters' Pak of Integrated Circuits. Data supplied	50p
H20	20	BY126/7 Type Silicon Rectifiers, 1 amp plastic Mixed volts	50p

MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1 each



OUR VERY POPULAR 3p TRANSISTORS

FULLY TESTED & GUARANTEED

TYPE "A" PNP Silicon alloy, TO-5 can.
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" NPN Silicon plastic encapsulation.

FULLY TESTED AND MARKED SEMI-CONDUCTORS


	£ p		£ p
AC107	0.15	OC170	0.23
AC126	0.15	OC171	0.23
AC127	0.17	OC200	0.25
AC128	0.15	OC201	0.25
AC176	0.20	2G301	0.13
ACY17	0.20	2G303	0.13
AF239	0.30	2N711	0.50
AF186	0.20	2N1302-3	0.15
AF139	0.30	2N1304-5	0.17
BC154	0.20	2N1306-7	0.20
BC107	0.10	2N1308-9	0.22
BC108	0.10	2N3819FET	0.45
BC109	0.10		
BF194	0.15		
BF274	0.20	Transistors	
BFY50	0.15	OC20	0.50
BSY26	0.13	OC23	0.30
BSY28	0.13	OC25	0.25
BSY27	0.13	OC26	0.25
BSY28	0.13	OC28	0.30
BSY29	0.13	OC35	0.25
BSY95A	0.10	OC36	0.37
OC41	0.15	AD149	0.30
OC44	0.13	AUY10	1.25
OC45	0.10	2S034	0.25
OC71	0.10	2N3055	0.50
OC72	0.10	Diodes	
OC81	0.13	AA42	0.10
OC81D	0.13	OA95	0.09
OC83	0.18	OA79	0.09
OC139	0.13	OA81	0.09
OC140	0.15	1N8114	0.07

F.E.T. PRICE BREAKTHROUGH !!

This field effect transistor is the 2N3823 in a plastic encapsulation, coded as 3823D. It is also an excellent replacement for the 2N3819.

Data sheet supplied with device.

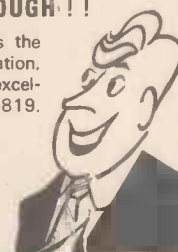1-10 **30p** each, 10-50 **25p** each, 50+ **20p** each.



BULK BUYING CORNER

NPN/PNP Silicon Planar Transistors, mixed, untested, similar to 2N706/6A/B, BSY26-29, BSY95A, BCY70, etc. £4.25 per 500; £8 per 1,000.

Silicon Planar NPN Plastic Transistors, untested, similar to 2N3707-11, etc., £4.25 per 500; £8 per 1,000.

Silicon Planar Diodes, DO-7 Glass, similar to OA200/202, BAY31-36, £4.50 per 1,000.

NPN/PNP Silicon Planar Transistors, Plastic TO-18, similar to BC113/4, BC153/4, BF153/160, etc., £4.25 per 500; £8 per 1,000.

OC44, OC55 Transistors fully marked and tested, 500+ at 8p each; 1,000+ at 6p each.

OC71 Transistors, fully marked and tested, 500+ at 6p each; 1,000+ at 5p each.

3823E Field effect Transistors. This is the 2N3823 in Plastic Case, 500+ **13p** each; 1,000+ **10p** each.

1 amp Miniature Plastic Diodes:
1N4001, 500+ at 4p each, 1,000+ at 3p each.
1N4004, 500+ at 5p each, 1,000+ at 4p each.
1N4006, 500+ at 6p each, 1,000+ at 5p each.
1N4007, 500+ at 8p each, 1,000+ at 7p each.

FREE CATALOGUE

for TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS AND FULL PRE-PAK LISTS



8 RELAYS FOR £1

Various Contacts and Coil Resistances. No individual selection Post & Packing 25p.

COLOUR T.V. LINE OUTPUT TRANSFORMERS

Designed to give 25kV when used with PL509 and PY500 valves. As removed from colour receivers at the factory. **NOW ONLY 50p** each post and packing 23p.

Quantity	1-10	10-50	50+
BB105 Varicap Diodes	10p	8p	6p
OC71 or 72 Fully Tested Unmarked	5p	5p	4p
Matched Sets 1-OC44 and 2-OC45's Per Set.	25p	20p	15p
Matched Sets of OC45's 1st and 2nd 1F	15p	12p	10p
OA47 Gold-Bonded Diodes, Marked and Tested	3p	3p	2p
1-watt Zener Diodes 7.5, 24, 27, 30, 36, 43 Volts	5p	4p	3p
10-watt Zener Diodes 5.1, B.2, 11, 13, 16, 24, 30, 100 Volts	20p	17p	15p
Micro Switches, S/P, Q/O	25p	20p	15p
1-amp Bridge Rec's, 25-volt	25p	22p	20p

INTEGRATED CIRCUITS

SL403D Audio Amp., 3-Watts	2.00	1.95	1.80
709C Linear Opp. Amp.	25p	20p	15p
Gates, Factory Marked and Tested by A.E.I.	25p	22p	20p
J. K. Flip-Flops Factory, Marked and Tested by A.E.I.	40p	35p	30p
SN7490 Decade Counter	50p	45p	40p
UL914 Dual 2 1/2 V Gate	40p	35p	30p

LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 15p each.
16 pin type at 16p each.

BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines:

B.P.1. Transistors Equivalents and Substitutes 40p, this includes many thousands of British, U.S.A., European and C.V. equivalents.

The Iltffe Radio Valve and Transistor Data Book, 9th Edition 75p.

Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits. Send for lists of these English publications.

BUMPER BUNDLES

These parcels contain all types of surplus electronic components, printed panels, switches, potentiometers, transistors and diodes, etc.

2 LBS IN WEIGHT FOR £1

Post and packing 25p.

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME
ADDRESS

MINIMUM ORDER 50p CASH WITH ORDER PLEASE. Add 10p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE.

BI-PRE-PAK LTD

DEPT. B, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344

SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.
● LOW COST ● QUICK DELIVERY ● OVER 200 RANGES IN STOCK ● OTHER RANGES TO ORDER

NEW "SEW" DESIGNS! CLEAR PLASTIC METERS BAKELITE PANEL METERS

TYPE SW. 100
100 x 80 mm.

50μA	£3-60
50-0-50μA	£3-45
100μA	£3-20
100-0-100μA	£3-45
500μA	£3-35
1mA	£3-10
20V. D.C.	£3-10
50V. D.C.	£3-10
300V. D.C.	£3-10
1 amp. D.C.	£3-10
5 amp. D.C.	£3-10
300V. A.C.	£3-10
VU Meter	£3-75

TYPE S-80
80 mm. square fronts

50μA	£3-20
50-0-50μA	£3-10
100μA	£2-75
100-0-100μA	£3-10
500μA	£3-00
1mA	£2-60
20V. D.C.	£2-60
50V. D.C.	£2-60
300V. D.C.	£2-60
1 amp. D.C.	£2-60
5 amp. D.C.	£2-60
300V. A.C.	£2-60
VU Meter	£3-37

"SEW" CLEAR PLASTIC METERS

Type MR.85P. 4 1/4 in. x 4 1/4 in. fronts.

10mA	£2-80
50mA	£2-60
100mA	£2-80
500mA	£2-80
1 amp.	£2-80
5 amp.	£2-80
15 amp.	£2-80
30 amp.	£2-80
20V. D.C.	£2-80
50V. D.C.	£2-80
150V. D.C.	£2-80
300V. D.C.	£2-80
15V. A.C.	£2-80
300V. A.C.	£2-80
S Meter 1mA	£2-87
VU Meter	£3-60
1 amp. A.C.*	£2-80
5 amp. A.C.*	£2-80
10 amp. A.C.*	£2-80
20 amp. A.C.*	£2-80
30 amp. A.C.*	£2-80

Type MR.38P. 1 21/32 in. square fronts.

200mA	£1-60
300mA	£1-60
500mA	£1-60
750mA	£1-60
1 amp.	£1-60
2 amp.	£1-60
5 amp.	£1-60
10 amp.	£1-60
15V. D.C.	£1-60
18V. D.C.	£1-60
15V. D.C.	£1-60
20V. D.C.	£1-60
100V. D.C.	£1-60
150V. D.C.	£1-60
300V. D.C.	£1-60
500V. D.C.	£1-60
750V. D.C.	£1-60
15V. A.C.	£1-70
50V. A.C.	£1-70
150V. A.C.	£1-70
300V. A.C.	£1-70
500V. A.C.	£1-70
S Meter 1mA	£2-10
VU Meter	£2-70

Type MR.55P. 2 1/2 in. square fronts.

50μA	£3-10
50-0-50μA	£2-60
100μA	£2-60
100-0-100μA	£2-60
500μA	£2-30
1mA	£2-00
5mA	£2-00
10mA	£2-00
50mA	£2-00
100mA	£2-00
500mA	£2-00
1 amp.	£2-00
5 amp.	£2-00
10V. D.C.	£2-00
20V. D.C.	£2-00
50V. D.C.	£2-00
300V. D.C.	£2-00
15V. A.C.	£2-10
300V. A.C.	£2-10
S Meter 1mA	£2-10
VU Meter	£3-20
1 amp. A.C.*	£2-00
5 amp. A.C.*	£2-00
10 amp. A.C.*	£2-00
20 amp. A.C.*	£2-00
30 amp. A.C.*	£2-00

Type MR.45P. 2 in. square fronts.

50μA	£2-25
50-0-50μA	£2-10
100μA	£2-10
100-0-100μA	£1-87
500μA	£1-87
1mA	£1-75
500-0-500μA	£1-75
1mA	£1-70
5mA	£1-70
10mA	£1-70
50mA	£1-70
100mA	£1-70
500mA	£1-70
1 amp.	£1-70
5 amp.	£1-70
10V. D.C.	£1-50
20V. D.C.	£1-50
50V. D.C.	£1-50
300V. D.C.	£1-50
15V. A.C.	£1-80
300V. A.C.	£1-80
S Meter 1mA	£2-85
VU Meter	£2-25
1 amp. A.C.*	£1-70
5 amp. A.C.*	£1-70
10 amp. A.C.*	£1-70
20 amp. A.C.*	£1-70
30 amp. A.C.*	£1-70


"SEW" BAKELITE PANEL METERS

Type MR.65. 3 1/4 in. square fronts.

500mA	£1-95
1 amp.	£1-95
2 amp.	£1-95
5 amp.	£1-95
15 amp.	£1-95
30 amp.	£1-95
50 amp.	£1-95
5V. D.C.	£1-95
10V. D.C.	£1-95
20V. D.C.	£1-95
50V. D.C.	£1-95
150V. D.C.	£1-95
500V. D.C.	£1-95
30V. A.C.	£1-95
50V. A.C.	£1-95
150V. A.C.	£1-95
300V. A.C.	£1-95
500V. A.C.	£1-95
1 amp. A.C.*	£1-85
5 amp. A.C.*	£1-85
10 amp. A.C.*	£1-85
20 amp. A.C.*	£1-85
30 amp. A.C.*	£1-85
50 amp. A.C.*	£1-85
VU Meter	£3-10

*** MOVING IRON — ALL OTHERS MOVING COIL**
Please add postage

SEW EDUCATIONAL METERS

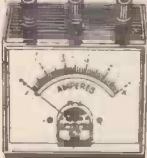

Type ED 107
Size overall 100mm x 90mm x 108mm

A new range of high quality moving coil instruments ideal for school experiments and other bench applications. 3 1/2 in. mirror scale. The meter movement is easily accessible to demonstrate internal working.

Available in the following ranges—	
50μA	£5-00
100μA	£4-65
1mA	£4-40
50-0-50μA	£4-65
1-0-1mA	£4-40
1A d.c.	£4-40
5A d.c.	£4-40
10V d.c.	£4-40
20V d.c.	£4-40
50V d.c.	£4-40
300V d.c.	£4-40
Dual range	
500mA/5A d.c.	£4-85
5V/50V d.c.	£4-85

EDGWISE METERS

Type P.E.70. 3 17/32 in. x 1 11/32 in. x 2 1/4 in. deep.

50μA	£3-10
50-0-50μA	£3-00
100μA	£3-00
100-0-100μA	£2-90
200μA	£2-90
500μA	£2-75
1mA	£2-45
300V. A.C.	£2-45
VU Meter	£3-40

Send for illustrated brochure and further details on all Sew Panel Meters—Discounts for quantities

MULTIMETERS for EVERY purpose!

ROUND SCALE TYPE PENCIL TESTER MODEL TS.68



Completely portable, simple to use pocket sized tester. Ranges: 0/3/30/300V A.C. and D.C. at 2,000 o.p.v. Resistance 0-20K ohms. Only £1-97. P. & P. 13p.

MODEL 1092 Testmeter.
5,000 O.P.V.
0/3/15/150/300/1200 V. D.C.
0/6/30/300/600 V. A.C.
0/300μA/300 mA
0/10K/1 meg Ω
Decibels —10 to +16 db
£2-75 each + 15p P. & P.



HIOKI MODEL 730X
30,000 O.P.V. Overload protection. 6/30/60/300/600/1200 VDC. 12/60/120/600/1200 VAC. 60 μA/30 mA/300 mA. 2K/200K/2 megohm. —10 to +63 db. £6-50. P. & P. 15p.



HIOKI MODEL 700X
100,000 O.P.V. Overload protection. Mirror scale. 3/6/12/15/3/6/12/30/60/120/300/600/1200 VDC. 1.5/3/6/12/30/60/150/300/600/1200 VAC. 15/300μA/3/6/150/300 mA. 6/12 AMP DC. 2K/200 K/2 Meg/20 megohm. —20 to +63 db. £13-50. P. & P. 20p



SKYWOOD SW-500
50 K Ω/Volt. Mirror scale DC. volts: 0.8/3/12/30/300/600. A.C. volts: 2/30/300/600. D.C. current: 20μA/6/60/600mA. Resistance: 10K/100K/1 Meg. Decibels: —20 to +57 db. £7-50. P. & P. 18p.



Model S-100TR MULTI-METER/TRANSISTOR TESTER 100,000 o.p.v. MIRROR SCALE/OVERLOAD PROTECTION 0/12 —6/3/12/30/120/600 V D.C. 0/6/50/120/600 V. A.C. 0/12/600μA/12/300MA/12 Amp. DC. 0/10K/1 MEG/100 MEG. —20 to +60 db. 0-01 — 2 mfd. Transistor tester measures Alpha, beta and Ico. Complete with batteries, instructions and leads. £13-50. P/P 25p.



370 WTR MULTI TESTER
Features A.C. current ranges. 20,000 o.p.v. 0/5-2-5/10/50/250/500/1000 V DC. 0/2-5/10/50/250/500/1000 V AC. 0/50μA/1/10/100MA/1/10 Amp DC. 0/100MA/1/10 Amp AC. 0/5K/50K/500K/5MEG/50MEG. —20 + 62 db. £15. P. & P. 25p.



TMK Model TW-50K 46 ranges, mirror scale, 50K/Vol. D.C. 5K Volt A.C. D.C.: Volts 125, 25, 1-25, 2-5, 5, 10, 25, 50, 125, 250, 500, 1000V. A.C. Volts: 1-5, 3, 5, 10, 25, 50, 125, 250, 500, 1000V. D.C. Current: 25, 50μA, 2-5, 5, 25, 50, 250, 500mA, 5, 10 amp. Resistance: 10K, 100K, 1 MEG. 10 MEG Ω. Decibels: —20 to +81-5 dB. £8-50. P. & P. 17p.



TE22 SINE SQUARE WAVE AUDIO GENERATORS

Sine: 20 cps to 200 kc/s. on 4 bands. Square 20 cps to 30 kc/s. Output impedance 5,000 ohms, 200/250 v. A.C. operation. Supplied brand new and guaranteed with instruction manual and leads, £17-50. Carr. 37p.

TE-20 D RF SIGNAL GENERATOR
Accurate wide range signal generator covering 120 Kc/s-500 Mc/s on 6 bands. Directly calibrated. Variable R.F. attenuator, audio output. Xtal socket for calibration. 220/240V. A.C. Brand new with instructions. £15. Carr. 37p. Size 140 x 215 x 170 mm.



BELCO DA-20 SOLID STATE DECADE AUDIO OSCILLATOR

New high-quality portable instrument. Sine 1 Hz to 100 KHz. Square 20 Hz to 20 KHz. Output max. +10 db (10 K ohms). Operation 220/240 v. A.C. Size 215 mm x 150 mm x 120 mm.
Price £27-50
Carr. 25p.

240° WIDE ANGLE 1mA METERS
MW1-6 60mm. square £3-97
MW1-8 80mm. square £4-97
P. & P. extra




TRANSISTORISED L.C.R. A.C MEASURING BRIDGE

A new portable bridge offering excellent range and accuracy at low cost. Ranges: R 10 — 11.1 MEG Ω 6 Ranges ± 1%. L 1μH — 111 HENRY. RIES. 6 Ranges — 2%. C 10PF — 1110MPD. 6 Ranges ± 2%. TURNS RATIO 1:1/1000 — 1:11100. 6 Ranges ± 1%. Bridge voltage at 1,000 CPS. Operated from 9 volts. 100mA. Meter indication. Attractive 2 tone metal case. Size 7 1/4" x 5" x 2" £20. P. & P. 25p.



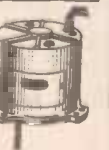230V/240V SMITHS SYNCHRONOUS GEARED MOTORS
Built-in gearbox. All brand new and boxed. 60 RPM CW; 30 RPM CW; 2R/HR ACW; 2R/HR CW; 8R/DAY CW; 10 RPM CW; 20R/HR ACW. 50p each. Post 12p.



HT100B4 MULTIMETER
Features A.C. current ranges. 100,000 o.p.v. Mirror Scale. Overload protection. 0/5-2-5/10/50/250/500/1000 V DC. 0/2-5/10/50/250/500 V A.C. 0/10/250μA/2-5/25/250 mA/10 Amp DC. 10 Amp AC. 0/20K/200K/2MEG/20MEG. — 20 + 62 db. £12-50. P. & P. 25p.




RUSSIAN 22 RANGE MULTIMETER

Model U487 10,000 o.p.v. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2-5/10/50/250/500/1000V D.C. 2-5/10/50/250/500/1000V A.C. D.C. Current 10 mA/100/1000 mA/1A. Resistance 300 ohms/3/30/300K/3M Ω. Complete with batteries, test leads, instructions and sturdy steel carrying case.
Our Price £5-97. P. & P. 25p.



TO-3 PORTABLE OSCILLOSCOPE, 3" TUBE

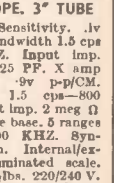Y amp. Sensitivity. 1v p-p/CM. Bandwidth 1.5 cps — 1.5 MHz. Input Imp. 2 meg Ω. 25 PF. X amp sensitivity. 9v p-p/CM. bandwidth 1.5 cps — 800 KHz. Input Imp. 2 meg Ω. 20 PF. Tube base. 5 ranges 10 cps — 300 KHz. Synchronization. Internal/external. Illuminated scale. 140 x 215 x 850 mm. Weight 15 1/2 lbs. 220/240 V. A.C. Supplied brand new with handbook £37-50. Carr. 50p.



HONEYWELL DIGITAL VOLTMETER VT.100

Can be panel or bench mounted. Basic meter measures 1 volt DC, but can be used to measure a wide range of AC and DC volt, current and ohms with optional plug in cards. Specifications: Accuracy: . . . 0.2 . . . 1 digit. Resolution: 1 mV. Number of digits: 3 plus fourth overrange digit. Overage: 100 + (up to 1999). Input impedance: 1000 Meg ohm. Measuring cycle: 1 per second. Adjustment: Automatic zeroing, full scale adjustment against an internal reference voltage. Overload: to 100V. D.C. Input: Fully floating (3 poles). Input power: 110-230V. A.C. 50/60 cycles. Overall size: 5 1/2 in. x 2 1/8 in. x 8 3/16 in. AVAILABLE BRAND NEW AND FULLY GUARANTEED AT APPROX. HALF PRICE £49-97 Carr. 50p.



G. W. SMITH & Co. (Radio) Ltd.
ALSO SEE NEXT TWO PAGES

SEMICONDUCTOR VALVES

ALL DEVICES BRAND NEW AND FULLY GUARANTEED

TRANSISTORS

2G301	20p	2N3606	27p	40310	45p	BC172	15p	BSX19	17p	NKT281	27p
2G302	20p	2N3607	22p	40311	35p	BC175	20p	BSX20	15p	NKT401	87p
2G303	20p	2N3638	18p	40312	47p	BC178	20p	BSX21	80p	NKT402	90p
2G306	42p	2N3638A	20p	49314	20p	BC179	20p	BSX26	45p	NKT403	75p
2G309	30p	2N3642	18p	40315	37p	BC182	10p	BSX27	47p	NKT404	55p
2G371	15p	2N3643	20p	40316	47p	BC182L	10p	BSX28	32p	NKT405	75p
2G374	20p	2N3644	25p	40317	57p	BC183	9p	BSX29	82p	NKT406	62p
2G381	22p	2N3645	25p	40318	47p	BC183L	9p	BSX30	15p	NKT451	62p
2N3884	42p	2N3691	15p	40323	32p	BC184	11p	BSX36	20p	NKT452	62p
2N404	20p	2N3692	15p	40324	47p	BC184L	11p	BSX78	25p	NKT453	62p
2N696	15p	2N3693	15p	40326	37p	BC186	25p	BSY24	15p	NKT454	62p
2N697	15p	2N3694	18p	40329	30p	BC187	20p	BSY25	15p	NKT455	62p
2N698	25p	2N3702	10p	40344	27p	BC212L	10p	BSY26	17p	NKT456	62p
2N699	30p	2N3703	10p	40347	57p	BC213L	12p	BSY27	17p	NKT457	62p
2N706	10p	2N3704	11p	40348	58p	BC214L	15p	BSY28	17p	NKT458	62p
2N706A	12p	2N3705	10p	40380	40p	BCY10	27p	BSY29	17p	NKT459	62p
2N708	15p	2N3706	9p	40381	40p	BCY30	27p	BSY32	25p	NKT460	62p
2N709	62p	2N3707	11p	40382	60p	BCY31	30p	BSY36	25p	NKT461	62p
2N718	25p	2N3708	7p	40370	32p	BCY32	30p	BSY37	25p	NKT462	62p
2N718A	30p	2N3709	9p	40406	67p	BCY33	30p	BSY38	25p	NKT463	62p
2N726	30p	2N3710	9p	40407	40p	BCY34	30p	BSY39	22p	NKT464	62p
2N727	30p	2N3711	12p	40408	30p	BCY35	30p	BSY43	50p	NKT465	62p
2N814	17p	2N3712	12p	40409	55p	BCY39	60p	BSY51	32p	NKT466	62p
2N816	17p	2N3714	22-00	40410	62p	BCY40	60p	BSY52	32p	NKT467	62p
2N818	30p	2N3715	21-23	40412	60p	BCY41	15p	BSY53	37p	NKT468	62p
2N829	22p	2N3716	21-30	40467A	67p	BCY42	15p	BSY54	37p	NKT469	62p
2N830	20p	2N3717	22-40	40468A	35p	BCY43	15p	BSY56	90p	NKT470	62p
2N997	40p	2N3791	22-06	40469	74p	BCY44	32p	BSY78	45p	NKT471	62p
2N1090	20p	2N3819	44p	40600	57p	BCY58	22p	BSY90	57p	NKT472	62p
2N1091	25p	2N3820	55p	40603	50p	BCY59	22p	BSY96A	15p	NKT473	62p
2N1131	25p	2N3823	50p	40603	50p	BCY60	22p	C424	15p	NKT474	62p
2N1132	25p	2N3824	27p	40603	50p	BCY70	15p	C450	15p	NKT475	62p
2N1302	17p	2N3854A	27p	40617	24p	BCY71	20p	C451	15p	NKT476	62p
2N1303	17p	2N3855	27p	40618	24p	BCY72	15p	C452	15p	NKT477	62p
2N1304	25p	2N3856	30p	40619	24p	BCY73	15p	C453	15p	NKT478	62p
2N1305	25p	2N3857	30p	40620	24p	BCY74	15p	C454	15p	NKT479	62p
2N1306	25p	2N3858A	35p	40621	24p	BCY75	15p	C455	15p	NKT480	62p
2N1307	25p	2N3859	27p	40622	24p	BCY76	15p	C456	15p	NKT481	62p
2N1308	25p	2N3860	30p	40623	24p	BCY77	15p	C457	15p	NKT482	62p
2N1309	25p	2N3861	30p	40624	24p	BCY78	15p	C458	15p	NKT483	62p
2N1310	25p	2N3862	30p	40625	24p	BCY79	15p	C459	15p	NKT484	62p
2N1311	25p	2N3863	30p	40626	24p	BCY80	15p	C460	15p	NKT485	62p
2N1312	25p	2N3864	30p	40627	24p	BCY81	15p	C461	15p	NKT486	62p
2N1313	25p	2N3865	30p	40628	24p	BCY82	15p	C462	15p	NKT487	62p
2N1314	25p	2N3866	30p	40629	24p	BCY83	15p	C463	15p	NKT488	62p
2N1315	25p	2N3867	30p	40630	24p	BCY84	15p	C464	15p	NKT489	62p
2N1316	25p	2N3868	30p	40631	24p	BCY85	15p	C465	15p	NKT490	62p
2N1317	25p	2N3869	30p	40632	24p	BCY86	15p	C466	15p	NKT491	62p
2N1318	25p	2N3870	30p	40633	24p	BCY87	15p	C467	15p	NKT492	62p
2N1319	25p	2N3871	30p	40634	24p	BCY88	15p	C468	15p	NKT493	62p
2N1320	25p	2N3872	30p	40635	24p	BCY89	15p	C469	15p	NKT494	62p
2N1321	25p	2N3873	30p	40636	24p	BCY90	15p	C470	15p	NKT495	62p
2N1322	25p	2N3874	30p	40637	24p	BCY91	15p	C471	15p	NKT496	62p
2N1323	25p	2N3875	30p	40638	24p	BCY92	15p	C472	15p	NKT497	62p
2N1324	25p	2N3876	30p	40639	24p	BCY93	15p	C473	15p	NKT498	62p
2N1325	25p	2N3877	30p	40640	24p	BCY94	15p	C474	15p	NKT499	62p
2N1326	25p	2N3878	30p	40641	24p	BCY95	15p	C475	15p	NKT500	62p
2N1327	25p	2N3879	30p	40642	24p	BCY96	15p	C476	15p	NKT501	62p
2N1328	25p	2N3880	30p	40643	24p	BCY97	15p	C477	15p	NKT502	62p
2N1329	25p	2N3881	30p	40644	24p	BCY98	15p	C478	15p	NKT503	62p
2N1330	25p	2N3882	30p	40645	24p	BCY99	15p	C479	15p	NKT504	62p
2N1331	25p	2N3883	30p	40646	24p	BCY00	15p	C480	15p	NKT505	62p
2N1332	25p	2N3884	30p	40647	24p	BCY01	15p	C481	15p	NKT506	62p
2N1333	25p	2N3885	30p	40648	24p	BCY02	15p	C482	15p	NKT507	62p
2N1334	25p	2N3886	30p	40649	24p	BCY03	15p	C483	15p	NKT508	62p
2N1335	25p	2N3887	30p	40650	24p	BCY04	15p	C484	15p	NKT509	62p
2N1336	25p	2N3888	30p	40651	24p	BCY05	15p	C485	15p	NKT510	62p
2N1337	25p	2N3889	30p	40652	24p	BCY06	15p	C486	15p	NKT511	62p
2N1338	25p	2N3890	30p	40653	24p	BCY07	15p	C487	15p	NKT512	62p
2N1339	25p	2N3891	30p	40654	24p	BCY08	15p	C488	15p	NKT513	62p
2N1340	25p	2N3892	30p	40655	24p	BCY09	15p	C489	15p	NKT514	62p
2N1341	25p	2N3893	30p	40656	24p	BCY10	15p	C490	15p	NKT515	62p
2N1342	25p	2N3894	30p	40657	24p	BCY11	15p	C491	15p	NKT516	62p
2N1343	25p	2N3895	30p	40658	24p	BCY12	15p	C492	15p	NKT517	62p
2N1344	25p	2N3896	30p	40659	24p	BCY13	15p	C493	15p	NKT518	62p
2N1345	25p	2N3897	30p	40660	24p	BCY14	15p	C494	15p	NKT519	62p
2N1346	25p	2N3898	30p	40661	24p	BCY15	15p	C495	15p	NKT520	62p
2N1347	25p	2N3899	30p	40662	24p	BCY16	15p	C496	15p	NKT521	62p
2N1348	25p	2N3900	30p	40663	24p	BCY17	15p	C497	15p	NKT522	62p
2N1349	25p	2N3901	30p	40664	24p	BCY18	15p	C498	15p	NKT523	62p
2N1350	25p	2N3902	30p	40665	24p	BCY19	15p	C499	15p	NKT524	62p
2N1351	25p	2N3903	30p	40666	24p	BCY20	15p	C500	15p	NKT525	62p
2N1352	25p	2N3904	30p	40667	24p	BCY21	15p	C501	15p	NKT526	62p
2N1353	25p	2N3905	30p	40668	24p	BCY22	15p	C502	15p	NKT527	62p
2N1354	25p	2N3906	30p	40669	24p	BCY23	15p	C503	15p	NKT528	62p
2N1355	25p	2N3907	30p	40670	24p	BCY24	15p	C504	15p	NKT529	62p
2N1356	25p	2N3908	30p	40671	24p	BCY25	15p	C505	15p	NKT530	62p
2N1357	25p	2N3909	30p	40672	24p	BCY26	15p	C506	15p	NKT531	62p
2N1358	25p	2N3910	30p	40673	24p	BCY27	15p	C507	15p	NKT532	62p
2N1359	25p	2N3911	30p	40674	24p	BCY28	15p	C508	15p	NKT533	62p
2N1360	25p	2N3912	30p	40675	24p	BCY29	15p	C509	15p	NKT534	62p
2N1361	25p	2N3913	30p	40676	24p	BCY30	15p	C510	15p	NKT535	62p
2N1362	25p	2N3914	30p	40677	24p	BCY31	15p	C511	15p	NKT536	62p
2N1363	25p	2N3915	30p	40678	24p	BCY32	15p	C512	15p	NKT537	62p
2N1364	25p	2N3916	30p	40679	24p	BCY33	15p	C513	15p	NKT538	62p
2N1365	25p	2N3917	30p	40680	24p	BCY34	15p	C514	15p	NKT539	62p
2N1366	25p	2N3918	30p	40681	24p	BCY35	15p	C515	15p	NKT540	62p
2N1367	25p	2N3919	30p	40682	24p	BCY36	15p	C516	15p	NKT541	62p
2N1368	25p	2N3920	30p	40683	24p	BCY37	15p	C517	15p	NKT542	62p
2N1369	25p	2N3921	30p	40684	24p	BCY38	15p	C518	15p	NKT543	62p
2N1370	25p	2N3922	30p	40685	24p	BCY39	15p	C519	15p	NKT544	62p
2N1371	25p	2N3923	30p	40686	24p	BCY40	15p	C520	15p	NKT545	62p
2N1372	25p	2N3924	30p	40687	24p	BCY41	15p	C521	15p	NKT546	62p
2N1373	25p	2N3925	30p	40688	24p	BCY42	15p	C522	15p	NKT547	62p
2N1374	25p	2N3926	30p	40689	24p	BCY43	15p	C523	15p	NKT548	62p
2N1375	25p	2N3927	30p	40690	24p	BCY44	15p	C524	15p	NKT549	62p
2N1376	25p	2N3928	30p	40691	24p	BCY45	15p	C525	15p	NKT550	62p
2N1377	25p	2N3929	30p	40692	24p	BCY46	15p	C526	15p	NKT551	62p
2N1378	25p	2N3930	30p	40693	24p	BCY47	15p	C527	15p	NKT552	62p
2N1379	25p	2N3931	30p	40694							

HI-FI EQUIPMENT

SAVE UP TO 33% OR MORE
SEND S.A.E. FOR DISCOUNT PRICE LISTS AND PACKAGE OFFERS!

RECORD DECKS

B.S.R.

Mini Mono: £4.97
 CI29: £6.70
 MP60: £10.75
 510: £11.85
 510: £9.85
 510: £34.47
 MP60 TPD1: £17.65
 MP60 TPD2: £15.85
 610 T.P.D.1: £20.97
 510 T.P.D.1: £15.75
 610 Package: £9.85
 H.T.70: £15.55
 H.T.70 Package: £22.50

THORENS

TD125: £59.85
 TD125AB: £94.85
 TX25: £6.70
 TD150: £29.20
 TD150A II: £34.50
 TD150AB II: £40.25
 TX11: £3.77

GARRARD

2025 T/C: £25.50
 3000: £7.50
 3500: £9.75



SP25 III: £10.50
 SL58B: £13.45
 AP76: £18.90
 SL72B: £23.95
 SL75B: £26.50
 SL95B: £23.95
 401: £29.95
 Zero 100A: £45.85
 Zero 100S: £42.75

GOLDRING

GL69/2: £18.97
 GL69/2P: £24.95
 GL72: £22.95
 GL72P: £29.95
 GL75: £28.95
 GL75P: £35.95
 LID72: £3.75
 LID75: £3.95
 GL85: £47.95
 GL85P: £55.95
 LID85: £4.85
 G101: £23.95
 G89: £19.85

PIONEER


PL12AC: £36.50

TELETON SAQ-206B STEREO AMPLIFIER



Latest exciting release. Brand new model, beautifully styled with walnut case. 6 + 6 watts rms. Switched inputs for mag. xtal. aux. tape. Incorporates volume, bass, treble and sliding balance control, scratch filter and loudness control. Rec. List £32.50. Our Price £19.95. Carr. 17p. Suggested system. SAQ 206B amplifier, SP25 III, plinth and cover, G890 cart, pair of Apollo speakers. Total Rec. List £81. Our Price £52.50. Carr. £1.50.

TELETON SPECIAL OFFER!

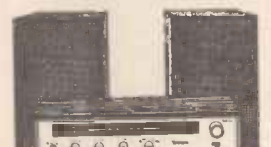

CRIOI AM/FM STEREO TUNER AMPLIFIER WITH MATCHING PAIR OF SPEAKER SYSTEMS Output 4 watts per channel. Excellent reception AFC, built-in MPX. Cer/XTAL Input. Total List £50.25. OUR PRICE £22.75. Carr. 62p.


Also available with Garrard 2025T/C, Record Changer, Plinth, cover and stereo cartridge. Ready wired. £36.50. Carr. £1.

TELETON F.2000 AM/FM STEREO TUNER/AMPLIFIER



Probably the most popular budget Tuner/Amp. and now offered at a ridiculous low price. 5 watts rms. per channel. Tape/Cer. phono inputs. AFC/Built-in MPX. List £51. Our Price £28.75. Carr. 50p.

LAFAYETTE LA. 324 STEREO AMPLIFIER

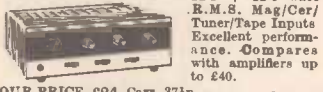

12.5 + 12.5 watt input. 26 ranges. Large R.M.S. Mag/Cer/Tuner/Tape Inputs. Excellent performance. Compares with amplifiers up to £40.

OUR PRICE £24. Carr. 37p.

TAPE CASSETTES

Top quality in plastic library boxes
 C90 60 min 30p, 3 for £2p
 C60 90 min 42p, 3 for £1.10
 CI20 120 min 52p, 3 for £1.35
 Cassette Head Cleaner 30p. Post Extra.

TMK MODEL I17 ELECTRONIC VOLT METER

Battery operated, 11 meg input. 26 ranges. Large 4 1/2" mirror scale. Size 5 1/2 x 4 1/2 x 2 1/2 in. DC Volts 0-3-1200V. AC Volts 3-300V RMS. 8-0-800V; P-P. DC Current 12-12MA. Resistance up to 2000M ohm. Decibels -20 to +51 db. Complete with leads/instructions. £17.50. P. & P. 20p.

E.H.T. TESTER -30KV.

Completely self-contained with built-in voltmeter. Easy to read, very accurate, reliable construction. An essential for colour television servicing, etc. Size 360mm. long. 50mm. dia. £8.95. P. & P. 25p.

230 VOLT A.C. 50 CYCLES RELAYS

Brand new. Sets of change-over contacts at 5 amp rating. 50p each P. & P. 10p (100 lots £40). Quantities available.



HOMER INTERCOMS
 Ideal for home, office, stores, factories, etc. Supplied complete with batteries, cable and free instructions.

2 Station £2.97. P. & P. 15p.
 3 Station £5.25. P. & P. 15p.
 4 Station £6.62. P. & P. 17p.



EMI LOUDSPEAKERS
 Model 350. 13" x 8" with single tweeter/crossover. 20-20,000 Hz. 15 watt RMS. Available 8 or 15 ohms. £27.50 each. P. & P. 37p.
 Model 450. 13" x 8" with twin tweeters/crossover. 55-13,000 Hz. 8 watt RMS. Available 8 or 15 ohms. £3.50 each. P. & P. 25p.

TE 1018 DE-LUXE MONO HIGH IMPEDANCE HEADSET

Sensitive, soft earpads, adjustable headband. Magnetic, impedance 2,600 ohms. £1.97. P. & P. 15p.

MP7 MIXER PREAMPLIFIER

5 microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. 9 1/2" x 5" x 3". Inputs Mics: 3 x 3mV 50K; 2 x 3mV 600 ohm. Phono meg. 4 mV 50K. Phono ceramic 100mV 1 meg. Output 250mV 100K. £8.97. P. & P. 20p.

HOSIDEN DH-02S STEREO HEADPHONES

Wonderful value and excellent performance combined. Adjustable headband. 8 ohm impedance. 20-12,000 cps. Complete with lead and stereo jack plug. ONLY £2.37. P. & P. 12p.

CI-5 PULSE OSCILLOSCOPE

For display of pulsed and periodic waveforms in electronic circuits. VERT. AMP. Bandwidth 10MHz. Sensitivity at 100 KHz 2 V RMS/mm. 1-25; HOB. A.M.P. Bandwidth 500KHz. Sensitivity at 100KHz. V. RMS. 3-25; Preset triggered sweep 1-3,000 usec.; free running 20-200,000Hz in nine ranges. Calibrator pipe. 220 x 360 x 430mm. 115-230V. AC operation. £39.00 Carr. paid.

MCA. 220 AUTOMATIC VOLTAGE STABILISER

Input 88-125 VAC or 178-250VAC. Output 120VAC or 240VAC. 200VA rating. £11.97. Carr. 50p.

TRANSISTOR FM TUNER

6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6in. x 4in. x 2 1/2in. 3 I.F. stages. Double tuned discriminator, ample output to feed most amplifiers. Operates on 9 volt battery. Coverage 88-108 Mc/s. Ready built ready for use. Fantastic value for money. £6.37. P. & P. 12p. STEREO MULTIPLEX ADAPTOES, £4.97.

WS62 TRANSCEIVERS

Large quantity available for EXPORT! Excellent condition. Enquiries invited.

SPECIAL OFFER! SINCLAIR PROJECT 60 STEREO FM TUNER



The first tuner in the world to use the phase lock loop principle—as used for receiving signals from space craft because of its vastly improved signal to noise ratio. Provides fantastic results even in difficult areas. Tuning range 87.5 to 108MHz. Automatic stereo indicator. Sensitivity: 2uV. AFC range ± 200KHz. Signal to noise ratio: 65dB. Output voltage 2 x 150mV. Operating voltage 25-30V DC. Size 93 x 40 x 207 mm. REC. LIST PRICE £25.

OUR PRICE ONLY £16.95 P. & P. 25p.
 Unrepeatable offer—buy now and save over £8.

FR-2 PHOTO ELECTRIC RELAY SYSTEM

Inexpensive warning or counting system consisting of an enciter and relay unit. Relay unit has variable sensitivity control and switch for intermittent alarm operation. Enciter unit has removable infra red filter and A.C. outlet socket to operate bells, counters, etc. 240V AC. Complete with cables and instructions. £9.97. P. & P. 25p.



UR-1A SOLID STATE COMMUNICATION RECEIVER

4 Bands covering 550kc/s - 30mc/s. FET, 8 Meter. Variable BFO for SSB, Built in Speaker. Bandspread, Sensitivity Control. 220/240V AC or 12v DC. 12 1/2" x 4 1/2" x 7". Brand new with instructions. £25. Carr. 37p.

LAFAYETTE HA-600 RECEIVER

General coverage 150-400 kc/s, 550kc/s-30 mc/s. FET front end, 2 mech. filters, product detector, variable B.F.O., noise limiter, 8 Meter. Bandspread. RF Gain. 15" x 9 1/2" x 8 1/2". 18 lb. 220/240V AC or 12v DC. Brand new with instructions. £45 Carrage 50p.

TE-16A TRANSISTORISED SIGNAL GENERATOR

5 Ranges 400 kHz-30 MHz. An inexpensive instrument for the handyman. Operates on 9 v. battery. Wide easy to read scale. 800 kHz modulation. 5 1/2 in. x 4 in. x 3 1/2 in. Complete with instructions and leads. £7.97 P. & P. 20p.

RUSSIAN CI-16 DOUBLE BEAM OSCILLOSCOPE

5 mc/s Pass Band. Separate Y1 and Y2 amplifiers. Rectangular 5 in. x 4 in. C.B.T. Calibrated triggered sweep from .2 usec. to 100 mill-sec. per cm. Free running time base 50 or 1 mc/s. Built-in time base calibrator and amplitude calibrator. Supplied complete with all accessories and instruction manual. £97 Carr. paid.

RECORD DECK PACKAGES

Decks supplied ready wired in teak veneered plinth and cover fitted with cartridge.

Garrard 2025 T/C with Sonolone STACRD. £13.95
 Garrard SP25 III/Type GTAHCD £18.95
 Garrard SP25 III with Goldring G900 £19.95
 Garrard SP2511/Shure M75-6. £28.95
 Garrard AP76/Shure M75-6. £30.95
 Garrard AP76 with Goldring G800. £29.95
 BSR MP60 with Audio Technica AT.55 £21.00
 Goldring GL72 with Goldring G800. £37.50
 Goldring GL75 with Goldring G800. £37.50
 Goldring GL75 with Goldring G800E £46.85
 Carriage 50p extra any model.

1021 STEREO LISTENING STATION

For balancing and gain selection of loud-speakers with additional facility for stereo headphone switching. 2 gain controls, speaker on-off slide switch, stereo headphone sockets. 6" x 4" x 2 1/4". £2.25. P. & P. 15p.

SINCLAIR EQUIPMENT Project 60. Package Offers



2 x Z30 amplifier, stereo 60 pre-amp, P26 power supply. £16.75. Carr. 37p. Or with P26 power supply. £18.85. Carr. 37p. 2 x Z50 amplifier stereo 60 pre-amp, P28 power supply. £20.25. Carr. 37p. Transformer 4 £23. 92-97 extra. Add to any of the above £4.97 for active filter unit and £16 for a pair of Q16 speakers. PROJECT 60 FM TUNER £18.95. Carr. 37p. All other Sinclair products in stock. IC12 £2-50. 2,000 amplifier £23.75. Carr. 37p. 30 Amp. 50 Amp. £31.50. Carr. 37p. Neoteric amplifier £43.95. Carr. 37p. PROJECT 60S £20.97. Carr. 37p.

NS-1600W STEREO AMPLIFIER

Exceptional budget price amplifier. All silicon transistor. Handsome Walnut case. Switched input selector, separate balance, volume, treble, bass controls. Output 2 x 6W RMS. Inputs Mag, Tape, Xtal, Tuner, Tape Out. £14.75. Carr. 37p.

LATEST CATALOGUE

New 6th edition giving full details of a comprehensive range of HI-FI EQUIPMENT COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. FREE DISCOUNT COUPONS VALUE 50p. 272 pages, fully illustrated and detailing thousands of items at bargain prices.

SEND NOW! STILL ONLY 37 1/2p p+p 10p

POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range available ex-stock. Single hole fixing. 1/2 in. dia. shafts. Bulk quantities available.
 25 WATT. 10/25/50/100/250/500/1000/1500/2500 or 5000 ohms. £1.7p. P. & P. 7p
 50 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. £1.05. P. & P. 7p
 100 WATT. 15/10/25/50/100/250/500/1000 or 2500 ohms. £1.37p. P. & P. 7p.

"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality • Low price • Immediate delivery

MODEL 8-260
 General Purpose
 Bench Mounting
 1 Amp .. £7.00
 2.5 Amp .. £7.05
 5 Amp .. £11.75
 8 Amp .. £15.90
 10 Amp .. £22.50
 12 Amp .. £23.60
 20 Amp .. £49.00

MODEL 8-260 B Panel Mounting
 1 Amp .. £7.00
 2.5 Amp .. £8.05

Please add postage
 ALL MODELS
 INPUT 230 VOLTS, 50/60 CYCLES
 OUTPUT VARIABLE 0-260 VOLTS
 Special discounts for quantity

G.W.SMITH & CO. (RADIO) LTD

27 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-636 3715
 3 LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204
 34 LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155
 311 EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387

OPEN 9-6 MONDAY TO SATURDAY

All Mail Orders to—
 11-12, Paddington Green,
 London, W.2
 Tel: 01-262 6562
 (Trade supplied)

MODERN TELEPHONES type 706. Two tone grey £3.50 ea. The same but black £2.75 ea. P. & P. 25p ea.
BRAND NEW, two tone grey £6 ea. P. & P. 25p ea.
PHOTOMULTIPLIERS. EMI 6097X at £8.50 ea. 6097B & 6097C—£5 ea. Type 931A—2.25 ea.
TRANSISTOR OSCILLATOR. Variable frequency 40 c/s to 5 kc/s. 5 volt square wave o/p, for 6 to 12V DC input. Size 1½ x 1½ x 1½in. Not encapsulated. Brand new. 57p ea.

RELAYS

G.E.C. Sealed Relays High Speed 24V. 2m 2b—23p ea.
S.T.C. Sealed 2 pole c/o 700 ohms (24V). 15p ea. 12v 35p ea. 2,500 ohm (okay 24v)—13p ea.

CARPENTERS polarised Single pole c/o 20 and 65 ohm coil as new, complete with base 37p ea.
 Single pole c/o 14 ohm coil 33p ea; Single pole c/o 45 ohm coil 33p ea.
 Varley VP4 Plastic covers 4 pole c/o 5K—30p ea. 15K—33p ea.

POLARISED Relay 2 pole c/o 250 ohm and 250 ohm coils—25p ea.

POTENTIOMETERS

COLVERN 3 watt. Brand new. 5; 10; 25; 100; 250; 500 ohms; 1; 2.5; 5; 10; 25; 50k all at 13p ea.
MORGANITE Special Brand new. 2.5; 10; 100; 250; 500K; 2.5 meg. 1 in. sealed. 17p ea.

BERCO 2½ Watt. Brand new. 5; 10; 50; 250; 500 ohms; 1; 2.5; 5; 10; 25; 50K at 20p ea.

STANDARD 2 meg. log pots. Current type 15p ea.
INSTRUMENT 3 in. Colvern 5 ohm 35p ea; 50k and 100K 50p ea.

BOURNE TRIM POTS. 10; 20; 50; 100; 200; 500 ohms; 1; 2; 2.5; 5; 10; 25K at 35p ea.

ALMA precision resistors 100K; 400K; 497K; 998K; 1 meg—0.1% 27p ea.; 3.25k, 13K—0.1% 20p ea.

ERIE feed through ceramic coils 1000 pf—4p ea.

Sub-min. **TRIMMER** ½ square. 8. 5pf. Brand new 13p ea.

VISCONOL EHT CAPACITORS

Size 1 x 2½ ins. Size 1½ x 5½ ins.
 0.05mfd 2.5kV 50p ea. 0.01mfd 10kV 50p ea.
 0.001mfd 5kV 40p ea. 0.002mfd 18kV 65p ea.
 0.001mfd 10kV 50p ea. 0.01mfd 15kV 80p ea.
 0.05 mfd 5kV 60p ea. 0.0005mfd 20kV 60p ea.
 Size 2½ x 6½ ins. 0.1mfd 7kV 40p ea.
 0.05mfd 8kV 50p ea. 0.1mfd 5kV 35p ea.
 Brand new 0.25mfd 5 KV. Dubilier 50p ea. P. & P. 15p.
E.H.T. 2mfd. 5kV. Brand new £1.50 ea.

E.H.T. POWER UNITS type 1033, 0-3kV. £15 ea. Carr. £1.50.

E.H.T. TRANSFORMERS (Standard Mains) 2,850V 750MA. £25 ea. 3,440V 660MA. £25 ea.

Carriage at cost. Chokes and Capacitors for above available.

DECADE DIAL UP SWITCHES. Finger-tip. Engraved 0/9. Gold plated contacts. Size 2½" high, 2½" deep, ½" wide. 75p ea. Bank of 4 with escutcheon plates, etc., 2½" high, 2½" deep, 2½" wide. £2.50.

LIGHT EMITTING DIODES (RED)
 from Hewlett-Packard
 Brand new 38p each
 Holder—1p ea. Information—5p

PHOTOCELL equivalent OCP 71 13p ea.
 Photo-resist type Clare 703. (TO5 Case). Two for 50p.
BURGESS Micro Switches V3 5930. Brand new 13p ea.

4 DIGIT RESETTABLE COUNTERS. 1000 ohm coil. Size 1½ x ½ x 4½ in. As new, by Sodeco of Geneva. £2.50 ea.
 As above but 350 ohm. £3.50 ea.

TRANSFORMERS. All standard inputs.
STEP DOWN ISOLATING trans. Standard 240V AC to 55-0-55V 300W. £3 ea. P. & P. 35p.
 Neptune series 460-435-0 etc. 230 MA and 600-570-540-0 etc. 250 MA. £3.50 incl. post.
 Multi 6-3 Volts to give 48V 3-5 Amps etc. £3.50 incl. post.
 Gard/Param/Part. 450-400-0-400-450. 180 MA. 2 x 6-3v. £3 ea.
 Transformer 250-80MA; 13V-1.2A and 6-3V 5A. £1.50. P. & P. 25p.
 Neptune series, multi. 6-3V to give 38V at 6 amps. £2.50 ea. Carr. £1.
 Neptune series 350-0-350V at 55 MA, separate winding 500-0-500V at 250 MA. £2.00 ea. Carr. £1 extra.
 Transformer, size 2½ x 2½ x 3", 3 x 6-3V at 1 amp. 75p ea. P. & P. 25p.

CHOKES. 5H; 10H; 15H; up to 120mA. 42p ea. P. & P. 17p. Up to 250mA 63p. P. & P. 35p.
 Large quantity LT, HT, EHT transformers.

**HARTLEY TYPE 13A
 DOUBLE BEAM OSCILLOSCOPE**

TB 2 c/s-750 kc/s. Band width 5.5 Mc/s. Sensitivity 33 Mv/cm. Calibration markers-100 kc/s and 1 Mc/s. Cathode follower probe for H.F. testing. A completely reliable general purpose oscilloscope complete with all accessories, probe etc. £25.00 ea. Carr. £1.50.

As above. No accessories BUT CIRCUIT DIAGRAM Only £18.00. Carr. £1.50.

OSCILLOSCOPES

SOLARTRON 7118.2 D.B: DC—9 mc/s. In fine condition £50.

SOLARTRON 643 DC—15 mc/s. Good condition £50.

SOLARTRON DC—10 mc/s. CD513—£40.

SOLARTRON CD513.2—£42.50. CD5238—£45.

SOLARTRON CT316 (D800 range) DC—6 megs. £20.

COSSOR 1049 Mk. 3. DB. £25

All carefully checked and tested. Carriage £1.50 extra.

MARCONI

Noise Gen. TF1106. £40. Carr. £1.50.

Vacuum tube Voltmeter TF1041A. £35; 1041B. £45.

Wide Range Oscillator TF 1370 and TF 1370A. 10 c/s-10 mc/s from £140.

Deviation Meter TF934/2. £50 ea. Carr. £1.50.

Deviation type 719. £30 ea. Carr. 75p.

TF 1026 Frequency Meter £12.50. Carr. 75p.

TF 329 Magnification Meter. As new condition £60.

TF 195 Audio Generator £10. Carr. £1.50.

TF 801A Signal generator £35. Carr. £1.50.

Better grade £55 ea. Carr. £1.50.

TF 286 Magnification Meter £45. Carr. £1.

TF 269 N. 5 Impedance Bridge from £50 ea. Carr. £1.50.

TF 144G Signal Generator. Serviceable. Clean £15. In exceptional condition £25. Carr. £1.50.

TF 885 Video Oscillator Sine/Square £35 Carr. £1.50.

TF 885/1 £55. Carr. £1.54.

SOLARTRON

Stabilised P.U. SRS 151A. £15. Carr. £1.50.

Stabilised P.U. SRS 152. £10. Carr. £1.50.

Precision Millivoltmeter VP252. £25. Carr. £1.

Oscillator type OS 101. £30. Carr. £1.50.

AVO

Electronic Testmeter CT 38. Complete £20 Carr. £1

CINTEL

Square and Pulse gen. PW 0-05 to 0-3 micro secs. 15mV to 50V; rep rate 5 hz to 250 kz £20. Carr. £1.

AIRMEC

Signal Generator type 701. £25. Carr. £1.50.

AIRMEC Generator type 210 £120. Carr. £1.50.

E.M.I. Oscilloscope type WM16. Main frame £125. Choice of Plug in 7/2 DC—24 mc/s x 2 £35; 7/1 DC—40 megs £25. Differential unit available from £40.
E.M.I. WMB. DC to 15 mc/s. Complete with plug in pre-amp, from £40.

BECKMAN MODEL A. Ten turn pot complete with dial. 100k 3% Tol 0-25%—only £2.13 ea.

E.H.T. Base B9A in Polystyrene holder with cover. Brand new. 13p ea.

FIBRE GLASS PRINTED CIRCUIT BOARD. Brand new. Single sided up to 2½" wide x 15" ½p per sq. in. Larger pieces 1p per sq. in. Double sided. Any size 1p per sq. in. Postage 10p per order.

PANEL mounting lamp holders. Red or green. 9p ea.
 Miniature **PANEL** mounting lamp holders—10V 15MA—5p ea.

Standard 240V **MOTORS** by CITENCO reduction gearbox to 19 r.p.m. reversible. £5 ea.
 Also 57rpm and 114rpm.

GYROS Large clear plastic topped. Type A £4 ea. P. & P. 75p.

Single pole 3-way 250 V AC 15 amp switch. 8p ea. P. & P. 5p. Large discount for quantity.

Squirrel cage **BLOWER ASSEMBLY** complete with standard mains input motor. Size 7" x 2½" dia. only 80p ea. P. & P. 25p ea.

CLAUDE LYONS Main Stabilizer. Type TS-1L-580. Input 119-135 volts 47/65 cs. Output 127+/-0.25% 16 amps. £30. Carr. £2.

MAGNETRONS TYPE CV370. Brand new. Boxed. £8 ea.

KELVIN & HUGHES 4-channel multi-speed recorders complete with amplifiers. £45.

EVERSHED & VIGNOLES Recording paper. Brand new boxed. L618H4 7" wide, 1½" dia. 17p roll; JL900H4 7" wide, 1½" dia. 25p roll.

19in. Rack Mounting **CABINETS** 6ft. high. Double Bay complete with doors. Fine condition. £25. Carriage at cost.

SPECIAL OFFER

SELECTED B.C. 221 Recalibrated to Ministry Specification in brand new condition, complete with circuit, only £27.50. Carr. £1.50.

WAYNE Kerr Universal Bridge type CT375. £40 ea. Carr. £1.50.

MULLARD ELECTROLYTICS
 2200MFD 100v
 10A (50°C)
 75p each
 BRAND NEW BOXED
 LARGE REDUCTION FOR QUANTITY

SANGO 50 micro amp rectangular meter. Size 2½ x 3 with 4 separate scales, lever operated, 0/6 white, 0/60 blue, 0/600 red and set zero. £1.00 ea. P. & P. 17p.

SEEING IS BELIEVING!

GOOD CONDITION. BC221 complete with correct charts, circuit diagrams. ONLY £16.00. Carr. £1.00.

C.R.T.'s 5" type CV1385/ACR13. Brand new with spec. sheet. 63p ea. P. & P. 35p.

MARCONI Valve Voltmeter 428B/1 £5 ea. Carr. £1.

RESISTORS by PIHER. Carbon Film. 1 and 2 watt. All 5%. Brand new Perfect. Mixed values. Only 50p per 1-lb. weight. P. & P. 12p.

COSSOR D.B. Scopes—some models from £15.

Genuine **MULLARD** Transistors/Diodes. Tested and guaranteed. OC41, 42, 76, 77, 83; OAS. 10. All at 3p ea. OC23—10p ea.

CAPACITOR PACK—50 Brand new components only 50p. P. & P. 17p.

POTS—10 different values. Brand new.—50p. P. & P. 17p.

COMPONENT PACK consisting of 2-2 pole 2 amp push on/off switches; 4 pots 1 double; 1-small double pole vol control; 250 resistors ½ and ¼ watt many high stabs. Fine value at 50p per pack. P. & P. 17p.

COMPLETE Printed Circuit TRANSISTOR I.F. strip 470 kc/s, audio out Size 1½ x 4 ½ x 1½ in. ONLY 75p. P. & P. 10p.

3000 Series relays—15 mixed values (new and as new, no rubbish) £1.00. P. & P. 37p.

MUST GO! Solartron Storage oscilloscope QD910. Tested, working. ONLY £100. Carr. extra.

STUART TURNER No. 12 Water pump GPH720/10FT.HD or GPH150/45FT.HD. Complete with standard mains input isolating transformer. Ideal fountains, waterfalls, etc. ONLY £5 ea. P. & P. £1.25.

SUNVIC D.C. Amplifier. Standard Mains, 0-1mv. to 100mv. input. Fantastic value at £6 ea. Carr. £1.50.

DELIVERED TO YOUR DOOR 1 cwt. of Electronic Scrap chassis, boards, etc. No Rubbish. FOR ONLY £3.50. N. Ireland 50p extra.

SPECIAL OFFER—Five useful Moving Coil Meters ONLY £1.50. P. & P. 50p.

LOOSE LEAF BINDERS. Blue plastic cover. 4 ring. Standard size. 4 for £1. P. & P. 35p. 25 for £5. Carr. £1.

Panel switches DPDT 6x eq. 10p ea.; DPST Brand new, 17p ea.; DPST twice, brand new 25p ea.

HEAVY DUTY 6 amp. 2 pole c/o—20p ea.

GRATICULES. 12 cm. by 14 cm. in High Quality plastic. 30p ea. P. & P. 5p.

Official Orders Welcomed, Gov./Educational Depts., Authorities, etc., otherwise Cash with Order
FOR CALLERS. Always a large quantity of components, transformers, chokes, valves, capacitors, odd units, etc., at 'Chiltmead' prices. Callers welcome 9 a.m. to 10 p.m. any day.

CHILTMHEAD LTD

7/9 ARTHUR ROAD, READING, BERKS. (rear Tech. College) Tel.: Reading 582605/65916

HENRY'S FOR LOW COST FIRST GRADE BRAND BRANDED

GERMANIUM and SILICON TRANSISTORS, DIODES, RECTIFIERS TRIACS, FETS, ZENERS, BRIDGES and INTEGRATED CIRCUITS

BY ATES · EMIHUS · FAIRCHILD · FERRANTI · I.T.T. · MULLARD · NEWMARKET · PHILIPS · R.C.A. · TEXAS · TRANSITRON

TRANSISTORS A SELECTION FROM OUR LIST SEND FOR YOUR FREE COPY TODAY!

Table of transistor specifications including part numbers, descriptions, and prices. Columns include part numbers (e.g., AAY30, AAZ13), descriptions (e.g., BF115, BF154), and prices (e.g., 25p, 10p).

HENRY'S LOW COST INTEGRATED CIRCUITS

BRAND NEW, FULL SPECIFICATION, TTL 74 SERIES BRANDED FAIRCHILD, I.T.T. AND TEXAS

Table of integrated circuit specifications including part numbers, descriptions, and prices. Columns include part numbers (e.g., 7400, 7401), descriptions (e.g., Quadruple 2-input NAND gates), and prices (e.g., 20p, 18p).

FROM STOCK QUANTITY OFFERS!

Table of quantity offers for various components. Columns include part numbers (e.g., AF117, 2N2646), descriptions, and prices for different quantities (e.g., 25 + 17p, 100 + 15p).

INTEGRATED CIRCUITS

Table of integrated circuit specifications including part numbers, descriptions, and prices. Columns include part numbers (e.g., MFC4000P, MFC4010P), descriptions, and prices.

TRIACS

Table of triac specifications including part numbers, descriptions, and prices. Columns include part numbers (e.g., MFC4000P, MFC4010P), descriptions, and prices.

PLESSEY INTEGRATED CIRCUIT 3 Watt Amplifier SL403D

Complete with 8-page booklet, circuits and data. £1.50 ea. LIMITED SPECIAL OFFER

ZENER DIODES

Table of zener diode specifications including part numbers, descriptions, and prices. Columns include part numbers (e.g., 400m/w BZY 88), descriptions, and prices.


SILICON RECTIFIERS ALL TUBULAR

Table of silicon rectifier specifications including part numbers, descriptions, and prices. Columns include part numbers (e.g., IN4001, IN4002), descriptions, and prices.

BRIDGE RECTIFIERS SILICON POTTED

Table of bridge rectifier specifications including part numbers, descriptions, and prices. Columns include part numbers (e.g., Type P.I.V. Amps), descriptions, and prices.

COMPLETELY NEW 10th EDITION CATALOGUE

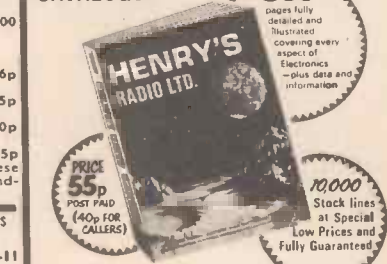

PLUS! FIVE 10p VOUCHERS FOR USE WITH PURCHASES A NEW HENRY'S CATALOGUE IS A MUST FOR ELECTRONICS TODAY!

OUR RANGE IS ALWAYS EXPANDING—Enquiries invited for new types arriving daily ADDITIONAL DISCOUNTS—10% 12+; 15% 25+; 20% 100+—DELIVERY IS FROM STOCK

HENRY'S SEMI-CONDUCTOR DEPARTMENT 303 EDGWARE RD., LONDON, W2. TEL: 01-723 1008/9 RADIO LTD. CALLERS 356 EDGWARE ROAD W2.

NEW LIST - NEW PRICES 1971 TRANSISTOR LIST 1500+ SEND FOR YOUR FREE COPY TODAY...

DISCOUNTS 10% 12+ 15% 25+ 20% 100+ POSTAGE 7p. ALL ORDERS

We respectfully ask customers to include a minimum £1.00 per order, it helps to plan ahead & saves postage as well.

BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1 THE VALVE SPECIALISTS Telephone 01-722-9090 GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX, Littlehampton 6743

Please forward all mail orders to Littlehampton

Table of electronic components with columns for part numbers (e.g., 0A2, 0B2, 1A3) and their corresponding descriptions or values.

ELECTRONIC ORGAN DIVIDER BOARDS built to high industrial/computer spec. 5 octave set £15. COPPER LAMINATE P.C. BOARD 8 1/2 x 5 1/2 x 1/16 in. 12 1/2 sheet, 5 for 50p

HIGH-SPEED MAGNETIC COUNTERS. 4 digit (non reset) 24 or 48v. (state which) 4 x 1 x 1 in. 35p. P.P. 5p. 5 digit (non reset) 6v. d.c. (2 1/2 x 1 1/2 in.) 75p. P.P. 5p.

COMPUTER TAPES. 2400 ft. 1/2 in. On N.A.B. Hubs complete with transparent cassette case. £2 ea. P.P. 50p. LIQUID LEVEL SWITCH. Detects even mildly conductive liquids

PRECISION A.C. MILLIVOLTMETER (Solartron) 1.5m.v. to 15v.: 60db to 20db. 9 ranges. Excellent condition. £22.50. P.P. £1.50. WAVE ANALYSER Type 853 (AIRMEC). 30Kc/s.—30Mc/s. Excellent condition. £25. Carr. £2.

MICROAMMETERS (4 in. sq. Weston) 25-0-25 microamps. New/boxed. £2.25 ea. P.P. 25p. PRECISION CAPACITANCE JIGS. Beautifully made with Moore & Wright Micrometer Gauge. Type 1, 18.5p to 1220pf. £10 ea. Type 2, 9.5p to 11.5pf. £6 ea.

TELEPHONE DIALS (New) £1 ea. RELAYS (G.P.O. '3000'). All types. Brand new from 37 1/2p ea. 10 up quotations only. TELEPHONE EXTENSION CABLE 3 core/cream p.v.c. 100 yd. coil £2 200 yd. coil £3.75. P.P. 25p.

LIGHT DIMMERS (2000 watt) Triac Controlled. 3 1/2 x 2 x 1 1/2 in. £5.75 ea. P.P. 25p. TRANSFORMERS L.T. TRANSFORMER. (Shrouded) Prim. 200/250v. Sec. 20/40/60v. 2 amp. £2 ea. P.P. 40p.

BLOWER FANS (Snail type) Type 1: Housing dia. 3 1/2 in. Air outlet 1 1/2 x 1 in. £2.25. P.P. 25p. Type 2: Housing dia. 6 in. Air outlet 2 1/2 x 2 1/2 in. £4. P.P. 50p. Both types 115/240v. A.C. (brand new). RELAYS SIEMENS/VARLEY PLUG-IN. Complete with transparent dust covers and bases. 2 pole c/o contacts 35p ea; 6 make contacts 40p ea; 4 pole c/o contacts 50p ea.

PATRICK & KINNIE 191 LONDON ROAD • ROMFORD • ESSEX ROMFORD 44473 RM79DD

SIGNAL GENERATOR TS-403B/U (or URM-61A): (Hewlett Packard). A portable, self-contained, general-purpose test equipment designed for use with radio and radar receivers and for other applications requiring small amounts of RF power such as measuring standing-wave ratios, antenna and transmission line characteristics, conversion gain, etc. Both the output freq. and power are indicated on direct-reading dials. 115V, AC, 50 c/s. Freq.—1800-4000 Mc/s. CW, FM, Modulated Pulse—40-4000 pulses per sec. Pulse Width—0.5-10 microseconds. Timing—Undelayed or delayed from 3-300 microseconds from external or internal pulse. O/pout—1 milliwatt max., 0 to -127 db variable. O/pout Impedance—50 Ω. Price: £120 each + £2 carr.

SIGNAL GENERATOR TYPE 902: (P.R.D.). A portable, general-purpose, broadband, microwave signal generator designed for testing and maintenance of aircraft radio and radar receivers in the SHF band. The RF output level is regulated by a variable attenuator calibrated in dbm. The frequency dial is calibrated in Mc/s. Provision is made for external modulation. Power Supply—115V, ±10% A.C., 50 c/s. Freq.—3650-7300 Mc/s. Internal Transmission—CW, Pulse, FM, External Transmission—Square Wave, Pulse. Power O/pout—0.2 milliwatts. O/pout Attenuator: -7 to -127 dbm. Load—50 Ω. Price: £135 each + £2 carr.

TEST SET TS-147C: Combined signal generator, frequency meter and power meter for 8500-9600 Mc/s. CW or FM signals of known freq. and power or measurement of same. Signal Generator: O/pout -7 to -85 dbm. Transmission—FM, PM, CW. Sweep Rate—0-6 Mc/s per microsec. Deviation—0-40 Mc/s per sec. Phase Range—3-50 microsec. Pulse Repetition Rate—to 4000 pulses per sec. RF Trigger for Sawtooth Sweep—5-500 watts peak. 0.2-6 microsec. duration, 0.5 microsec pulse rise time. Video Trigger for Sawtooth Sweep—Positive polarity, 10-50V peak. 0.5-20 microsec duration at 10% max. amplitude, less than 0.5 microsec rise time between 90% and 10% max. amplitude points. Frequency Meter: Freq. 8470-9360 Mc/s. Accuracy—+2.5 Mc/s per sec. absolute, +1.0 Mc/s per sec. for freq. increments of less than 60 Mc/s relative, ±1.0 Mc/s per sec. at 9310 Mc/s per sec. calibration point. Accuracy measured at 25° C and 60 humidity. Power Meter: Input: +7 to +30 dbm. Output -7 to -85 dbm. Price: £75 each + £1 carr.

MICROLINE IMPEDANCE METER MODEL 201: 5300-8100Mc/s. £75 each, £1 carr.

MICROLINE DIRECTIONAL COUPLER MODEL 209: 5260-8100Mc/s. 24DB. £12.50 each, post 35p.

COAXIAL TEST EQUIPMENT: COAXSWITCH—Mnfrs. Bird Electronic Corp. Model 72RS; two-circuit reversing switch. 50 ohms, type "N" female connectors fitted to receive UG-21/U series plugs. New in cnts., £6.50 each, post 37p.

POLARAD MSG-1 MICROWAVE SIGNAL GENERATOR: 95-2GHz, 0 to -127dbm output. Freq. accurate to within ±1%. Internal FM, pulse and squarewave modulation. £165 each, carr. £1.50.

POLARAD MSG-3 MICROWAVE SIGNAL GENERATOR: 4.5-8GHz. Internal pulse and squarewave modulation. £185 each, carr. £1.50.

POLARAD MSG MICROWAVE SIGNAL GENERATOR: 12.4-17.5GHz. £225 each, carr. £1.50.

TS-45/APM3 "X" BAND SIGNAL GENERATOR (and transmitter output power and frequency meter): 8.7-9.5GHz. Accuracy ±2MHz. 115V a.c. £25 each, carr. £1.

PRD FREQUENCY METER 5810: 9-1.5GHz. £55 each, post 60p.

USM-24C OSCILLOSCOPE: 3 in. oscilloscope with 2c/s to 10Mc/s vertical response, and 8c/s to 800Kc/s horizontal response. Sensitivity 50 mv. rms/inch. Triggered sweep, built-in trigger pulses and markers. Mains input 115V, 50c/s. Complete with all leads, probes and circuit diagram. £42.50 each, carr. £2.

SIGNAL GENERATOR TS-497B/URR: (Boonton). Freq. 2-400 Mc/s in 6 bands. Internal Mod. 400 or 1000 c/s per sec. External Mod. 50 to 10,000 c/s per sec. External PM, Percent Mod. 0-30 for sine wave, Am or Pulse Carrier. O/pout Voltage 0.1-100,000 microvolts cont. variable. Impedance 50 Ω. Price: £85 each + £1.50 carr.

FREQUENCY METER TS-74 (same TS-174): Heterodyne crystal controlled. Freq. 20-280 Mc/s. Accuracy .05%. Sensitivity 20 mV. Internal Mod. at 1000 c/s. Power Supply—batteries 6V and 13.5V. Complete with calibration book. (Manufactured for M.O.D. by Telex. "As new" in cartons.) £75 each. Fully stabilised Power Supply available at extra cost £7.50 each. Carr £1.50.

CT.54 VALVE VOLTMETER: Portable battery operated. In strong metal case with full operating instructions. 2.4V-480V. A.C. or D.C. in 6 Ranges, 1Ω to 10MegΩ in 5 Ranges. Indicated on 4in. scale meter. Complete with probe, excellent condition. £12.50, carr. 75p.

CT.381 FREQUENCY SWEEP SIGNAL GENERATOR: 85Kc/s-30Mc/s and response curve indicator with 6in. CRT tube and separate power supply. Fully stabilised. Price and further details on request.

DIGITAL VOLTMETER & RATIO METER Model BIE. 2116, £65, carr. £2.

DIGITAL VOLTMETER Model BIE. 2114, £55, carr. £2. (Mnfrs. Blackburn Instruments).

MARKA SWEEP GENERATOR MODEL VIDEO (Kay Electric, USA) £65, carr. £2.

MARCONI VARIABLE ATTENUATOR Type 386C: £15 ea. Carr. 60p.

MODULATOR UNIT: complete with transformer and 2x807 valves mounted in 19 in. chassis x 8 in. high x 8 in. deep. £4.50 secondhand cond., or £6.50 new cond. Carriage £1.

RF UNIT: suitable for use with the above unit. Complete with 2x3E29 valves. Ideal for conversion to 4 metres. £5 secondhand cond., or £7.50 new cond. Carriage £1.

POWER UNITS AVAILABLE FOR FOLLOWING SETS: 52 set—mains input, 150V @ 60mA and 12V @ 3 amps, new cond. £3.50. Receiver type 88 (1475)—mains input, 250V @ 80mA and 6.3V @ 4 amps, new cond. £3.50. No. 19 set £2.50. C12 set £4.00. 88 set £2.50. Carriage all types £1 extra.

STABILISED BENCH POWER SUPPLY: fully smooth, dual output, positive or negative, 2-6V; 6-9V; 9-12V and 12-16V all at 2 amps d.c. from mains input. £25 + £2 carr.

LONDEX AERIAL CHANGEOVER RELAY: 24V D.C. £1.50 ea. + 25p post

ROTARY CONVERTERS: Type 8a, 24 v D.C., 115 v A.C. @ 1.8 amps, 400 c/s 3 phase, £6.50 each, post 50p. 24 v D.C. input, 175 v D.C. @ 40mA. output, £1.25 each, post 20p.

CONDENSERS: 30 mfd 600 v wkg. d.c., £3.50 each, post 50p. 15 mfd 330 v a.c., wkg., 75p each, post 25p. 10 mfd 600 v. 43p each, 25p post. 8 mfd 2500 v. £5 each, carr. 63p. 8 mfd 600 v. 43p each, post 15p. 8 mfd. 1% 300 v. D.C. £1.25, post 25p. 4 mfd 3000 v. wkg. £3 each, post 37p. 4 mfd 2000 v. £2 each, post 25p. 4 mfd 600 v., 2 for £1. 0.25 mfd, 2Kv, 20p each, post 10p. 0.01 mfd MICA 2.5Kv, £1 for 5, post 10p. Capacitor 0.125 mfd, 27,000 v. wkg. £3.75 each, 50p post. 2.25 mfd 25 Kv. wkg. £20 each, £3 carr.

TCs MODULATION TRANSFORMERS, 20 watts, pr. 6,000 C.T., sec. 6,000 ohms. Price £1.25, post 25p.

SOLENOID UNIT: 230 v. A.C. input, 2 pole, 15 amp contacts, £2.50 each. post 30p.

CONTROL PANEL: 230 v. A.C., 24 v. D.C. @ 2 amps, £2.50 each, carr. 75p.

OHMITE VARIABLE RESISTOR: 5 ohms, 5½ amps; or 40 ohms at 2.6 amps; 500 ohms, 0.55 amps: Price (either type) £2 each, 25p post each.

TX DRIVER UNIT: Freq. 100-156 Mc/s. Valves 3 x 3C24's; complete with filament transformer 230 v. A.C. Mounted in 19in. panel, £4.50 each, carr. 75p.

POWER SUPPLY UNIT PN-12A: 230V a.c. input 50-60 c/s. 513V and 1025V @ 420 mA output. With 2 smoothing chokes 9H, 2 Capacitors, 10Mfd 1500V and 10Mfd 600V. Filament Transformer 230V a.c. input. 4 Rectifying Valves type 5Z3. 2 x 5V windings @ 3 Amps each, and 5V @ 6 Amp and 4V @ 0.25 Amp. Mounted on steel base 19"Wx11"Hx14"D. (All connections at the rear.) Excellent condition £6.50 each, carr. £1.

AUTO TRANSFORMER: 230-115V, 50-60c/s; 1000 watts. mounted in a strong steel case 5" x 6½" x 7". Bitumen impregnated. £6 each, Carr. 63p. 230-115V, 50-60c/s, 500 watts. 7" x 5" x 5". Mounted in steel ventilated case. £3.50 each, Carr. 50p.

LT TRANSFORMER: PRI 230V. Output 3 x 6.3 at 3 amps each winding, 3½" x 4" x 5". Fully shrouded £1.50 post 50p.

VARIABLE VOLTAGE REGULATOR TRANSFORMER: Input 230V A.C.; Output 57-5V-230V in 16 equal steps @ 21 Amps. £22.50 each, carr. £1.50.

TRANSFORMER: 230V A.C. input. 17.75V @ 35 Amps output. £9.50 each, carr. £1.

TRANSFORMER: 'C' Core. 230V A.C. input. 1000-0-1000V or 750-0-750V @ 250mA. £6.50 each, carr. 75p.

MODULATOR UNIT: 50 watt. part of BC-640, complete with 2 x 811 valves, microphone and modulator transformers etc. £7.50 each, 75p carr.

CATHODE RAY TUBE UNIT: With 3in. tube, Type 3EG1 526(CV1 colour) green, medium persistence complete with nu-metal screen, £3.50 each, post 37p.

APNI ALTIMETER TRANS./REC., suitable for conversion 420 Mc/s., complete with all valves 28 v. D.C. 3 relays, 11 valves, price £3 each, carr. 50p.

ANTENNA WIRE: 100 ft. long. 75p + 25p post.

APN-1 INDICATOR METER, 270° Movement. Ideal for making rev. counter. £1.25, post 25p.

VARIABLE POWER UNIT: Complete with Zenith variac 0-230V., 9 amps.; 2½ in. scale meter reading 0-250V. Unit is mounted in 19 in. rack. £15 each, £1.50p carr.

AIRCRAFT SOLENOID UNIT D.P.S.T.: 24V, 200 Amps, £2 each, 25p post.

RADAR SCANNER ASSEMBLY TYPE 122A: Complete with parabolic reflector (24 in. diameter), motors, suppressors, etc. £35 each, £2 carr.

DECADE RESISTOR SWITCH: 0.1 ohm per step. 10 positions. 3 Gang, each 0-9 ohms. Tolerance ±1% £3 each, 25p post. 90 ohms per step. 10 positions, total value 900 ohms. 3 Gang. Tolerance ±1% £3.50 each, post 25p.

CRYSTAL TEST SET TYPE 193: Used for checking crystals in freq. range 3000-10,000Kc/s. Mains 230V, 50c/s. Measures crystal current under oscillatory conditions and the equivalent parallel resistance. Crystal freq. can be tested in conjunction with a freq. meter. £12.50 each, £1 carr.

LEDEX SWITCHING UNIT: 2 ledex switches, 6 Bank and 3 Bank respectively 6 Pos.; 1 Manual switch, 16 Bank 2 Pos. £4 each, 50p post.

VARIAC TRANSFORMERS: Input 115V, output 0-135V at 2 Amps. £3 each 50p post. Input 115V, output 135V at 5 Amps. £5 each, 50p post.

RACK CABINETS: (totally enclosed) for Std. 19 in. Panels. Size 6 ft. high x 21 in. wide x 16 in. deep, with rear door. £12 each, £2.50 Carr. OR 4 ft. high x 23 in. wide x 19 in. deep, with rear door. £8.50 each, £2 Carr.

FUEL INDICATOR Type 113R: 24V complete with 2 magnetic counters 0-9999, with locking and reset controls mounted in 3in. diameter case. Price £2 each, 25p post.

GEARED MOTOR: 24c. D.C., current 150mA, output 1 rpm, £1.50 each, 25p post. **ASSEMBLY UNIT** with Letcherbar Tuning Mechanism and potentiometer, 3 rpm, £2 each 25p post. **SYNCHROS:** and other special purpose motors available. List 3p.

ACTUATOR UNIT: With 115V d.c. geared motor; o/pout 12.5 rpm; torque 16 ins. oz; reversible; micrositches and potentiometer. £3.50 ea. + 40p post.

DALMOTORS: 24-28V d.c. at 45 Amps, 750 watts (approx. 1hp) 12,000rpm. £5 each, 50p post.

GEARED MOTOR: 28V d.c. 150 rpm (suitable for opening garage doors). £4 each, 50p post.

MOTOR: 240V single phase, 2,400 rpm. 1/40 H.P. approx. Price £1.75 each, 25p post.

CALLERS BY TELEPHONE
APPOINTMENT ONLY

W. MILLS

3-B TRULOCK ROAD, LONDON, N17 0PG

Phone: 01-808 9213 and
WILSTEAD 605

H.T. TRANSFORMERS

AT A FRACTION OF MAKER'S PRICE

PARMEKO POTTED TYPES: Pri taps 200-240v. Sec. 1875v. 60m/a. 4.2kV. Pk. wkg. and 500v. Sec. 130v. 450m/a. 4.5v. 2a. £3.00. Carr. 45p. REDCLIFFE POTTED TYPE E.H.T.: Pri. taps 200-240v. Sec. 1600v. 50m/a. and 250v. 50m/a. 6.3v. 0.6a. 6.3v. 0.5a. 4.5v. 1.5a. £4.50. Carr. 50p. WODEN OPEN-FRAME TYPES TABLE-TOP CONNECTIONS, TROPICALISED: Pri. 230v. Sec. 890-710-0710-890v. 120m/a. £2.50. P.P. 40p. Pri. taps 200-240v. Sec. 130v. 450m/a. three times. "C" core. £4.50. P.P. 45p. TIBBLES OPEN-FRAME TYPE TABLE-TOP CONNECTION, TROPICALISED: Pri. taps 200-240v. Sec. taps 150, 165v. 4a. £4.50. Carr. 50p. L.T.P. Pri. 200-240v. Sec. tapped 300-325v. 0.4a. 6.4v. 1.8a. OPEN FRAME TABLE-TOP CONNECTIONS £3.50. Carr. 50p.

L.T. TRANSFORMERS PARMEKO POTTED TYPE

All Primaries 220-230v. Type 1: Sec. T.9-10v. 0.05a-10v. 0.5a. 6.3v. 3.5a. 6.3v. 1.2a. £1.50. P.P. 25p. Type 2: Sec. 24/30/32v. 2a. £1.50. P.P. 25p. Type 3: Sec. 12v. 6a. £1.50. P.P. 25p. Type 4: Sec. 4.2v. 1a. 75p. P.P. 20p. Type 5: Sec. 6.3v. C.T. 5a. 6.3v. 1.2a. 6.3v. 1.2a. £1.25. P.P. 25p. Type 6: 6.3v. C.T. 2.5a. 75p. P.P. 20p. Type 7: 7v. 5a. 6.3v. 4a. 6.4v. 2a. 6.4v. 2a. 5.2v. 8a. £1.75. P.P. 25p. WODEN: Pri. 220-240v. Sec. 10.5v. 2a. Fully shrouded. £1.50. P.P. 25p. Pri. 240v. Sec. 10v. 7a. and 3v.a. £2.50. P.P. 35p.

HEAVY DUTY HT CHOKES

Parmeko 10H 655 m/a. Res. 80Ω. Size 7 x 7 x 7 ins. Open type. £4.50. Carr. £1. Gresham 9H 500 m/a. 5KV wkg. Res. 40Ω. Potted type. 9 x 8 x 8 ins. £6.00. Carr. £1.25. 15H 300 m/a 50 ohm. "C" core potted type. £3.12. P.P. 50p. 10H 300 m/a 60 ohm. "C" core potted type. £2.75. P.P. 50p. 15H 180m/a.200ohm. "C" core potted type. £2.25. P.P. 45p. 20H 350m/a.200ohm. "C" core potted type. £3.50. P.P. 50p. 1H 1A. 15 ohm £3.50. P.P. 75p.

GARDNERS LT TRANSFORMERS

Pri. 200-220-240v. Sec. 2.0-2v. 11a. Twice 8Kv. D.C. wkg. £3. P.P. 50p. Pri. 200-220-240v. Sec. 6.6v. 7a. Four times 4Kv. D.C. wkg. £3.50. P.P. 50p. Pri. 230-250v. Sec. 2.0-2v. 11a. 25Kv. D.C. wkg. £5.50. Carr. 75p.

HEAVY DUTY LT TRANSFORMERS

By famous maker. Fully Tropicalised. Pri. tapped 100, 110, 120, 200, 220, 240v. E.S. Three Separate Secondaries 27v. 9a., 9v. 9a., 3v. 9a. Plus 17.0-17v. 0.25a. and 17v. 0.25a. Table-top connections. £4.50. Carr. 50p.

T.E.C. 240-110v. ISOLATION TRANSFORMERS

Pri Tapped 10. 0. 200. 220. 240v. sec. Tapped 110-112.5-115v. Conservatively rated at 9 amps. Tropicalised open frame type. Terminal Board connections. Size 9 x 9 x 7 ins. Weight 60 lbs. £15.00. Carr. 90p.

L.T.P. LT TRANSFORMERS

Pri. 220-240v. sec. 6.3v 8 amp. Four times. Fully tropicalised. Table top connections. £3.90. Carr. 60p.

Samson's (ELECTRONICS) LTD. 9 & 10 CHAPEL ST., LONDON, N.W.1 01-723-7851 01-262-5125

CURRENT RANGE OF BRAND NEW L.T. TRANSFORMERS, FULLY SHROUDED (*excepted) TERMINAL BLOCK CONNECTIONS. ALL PRIMARIES 220/240v

Table with columns: No., Sec. Taps, Amps, Price, Carr. It lists various transformer models like 1A, 1B, 1C, 1D, 2A, 2B, 2C, 2D, 3B*, 3C, 3D, 3E, 4A*, 4B, 4C, 4D, 5A, 5B, 5C, 5D, 6A, 6B, 7A*, 7B, 7C, 7D, 8A, 8B, 8A, 9A, 10A*, 11A, 12A, 13A with their respective specifications and prices.

Note: By using the intermediate taps many other voltages can be obtained. Example: No. 1 .. 7-8-10-15-17-25-33-40-50v. No. 2 .. 4-8-12-16-20-24-32v. No. 5 .. 3-6-9-12-15-18v.

STEP DOWN 240/110v. AUTO TRANSFORMERS FOR AMERICAN EQUIPMENT.

Fitted with 2 or 3 pin American sockets. All sizes from 80 to 24kva. available. Send s.a.e. for list. American sockets, plugs, adaptors also available.

GARDNERS AUTO TRANSFORMERS

Tapped 0, 200, 210, 220, 230, 240, 250v. 600 watts. Open frame type, table top connections £2. P.P. 35p.

EX G.P.O. TRANSFORMERS

Pri 180, 200, 220, 240v. Sec. 100-0-100v. 65 M/A and 61 64-67v. 150 M/A and 6v. 1A open type T-block connections. £1.25. P.P. 25p.


CHLORIDE HEAVY DUTY LEAD-ACID BATTERIES in glass containers. Set of 24, giving 50v. D.C. 85a.h. Filled, in perfect condition, with connectors and mains charger. £120 ex-warehouse.



EXCID LEAD-ACID BATTERIES in glass containers. Size 7 x 5 x 2 1/2 ins. 10v. 5a.h. Supplied brand new with charging instructions. Ideal for lighting, alarm systems, etc. Two packed in original maker's cartons. £1.75. Carr. 50p. One £1.00. Carr. 25p.

G.P.O. 20-WAY JACK STRIPS

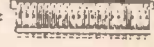Type 320 BN. Ex-equipment. Perfect condition. 75p. P.P. 10p.



6-DIGIT COUNTERS


By Counting Instruments Ltd. 48v. D.C. resettable. Size 3 1/2 x 2 1/2 x 2 1/2 ins. £2.00. P.P. 15p.

VEEDER-ROOT COUNTERS

6-digit resettable. 230v. A.C. Size 3 1/2 x 2 1/2 x 1 1/2 ins. £2.00. P.P. 20p. Counting Instruments Ltd. 48v. D.C. 6 digits resettable. 3 1/2 x 2 1/2 x 1 1/2 ins. £2.00. P.P. 20p.

BERCO RHEOSTATS

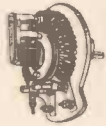0.2Ω 75 watts 3 ins. dia. 75p. P.P. 20p. Other types available: 50Ω 1a. 2 1/2 ins. dia. 50p. P.P. 20p. 100Ω 0.75a. 3 ins. dia. 60p. P.P. 20p. 12Ω 3a. 3 1/2 ins. dia. 75p. P.P. 20p. Inst. Pos. 110Ω 3 1/2 ins. dia. 20 watts. 50p. P.P. 20p.



OMRON SUB-MINIATURE RELAYS

Type 105IN, 12v. D.C. 1 C.O. 5 amp contact overall. Size 1 x 1 x 1 in. New and boxed with mounting screws. 45p. P.P. 5p.



T.C.C. CAPACITORS


0.5 mfd. 10,000v. D.C. wkg. £2.50. S.I.C. 25,000 mfd. 12v. D.C. wkg. 40p. P.P. 10p. 10,000 mfd. 16v. D.C. wkg. 8,000 mfd. 10v. D.C. wkg. 3,150 mfd. 40v. D.C. wkg. 40p. P.P. 10p.

HIGH-CAPACITY ELECTROLYTICS

Tubular type Sprague 40,000 mfd. 10v. D.C. wkg. 50p. P.P. 15p. S.I.C. 25,000 mfd. 12v. D.C. wkg. 40p. P.P. 10p. 10,000 mfd. 16v. D.C. wkg. 8,000 mfd. 10v. D.C. wkg. 3,150 mfd. 40v. D.C. wkg. 40p. P.P. 10p.

PLESSEY COUNTERS

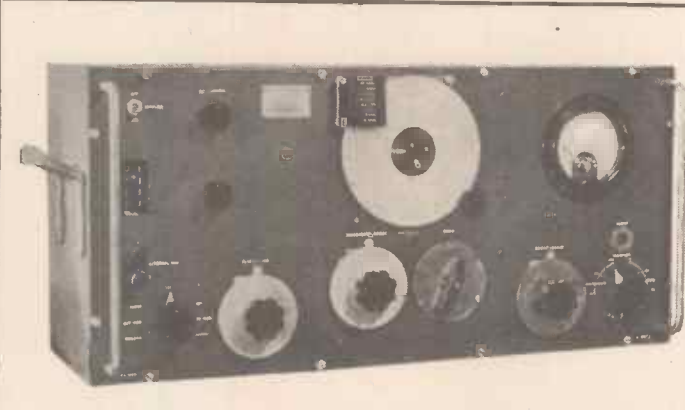A.C. 240v. Five Digits. Overall size 2 1/2 x 1 1/2 x 1 1/2 ins., 95p. P.P. 15p.



MARCONI SIGNAL GENERATOR TYPE TF-144G: Freq. 85 Kc/s-25Mc/s in 8 ranges. Incremental: ± 1% at 1Mc/s. Output: continuously variable 1 microvolt to 1 volt. Output Impedance: 1 microvolt to 100 millivolts, 10 ohms 100mV - 1 volt - 52.5 ohms. Internal Modulation: 400c/s sinewave 75% depth. External Modulation: Direct or via internal amplifier. A.C. mains 200/250V, 40-100c/s. Consumption approx. 40 watts. Measurements 29 x 12 1/2 x 10 in. Second hand condition. £27.50 each, Carr. £1.50.

MARCONI SIGNAL GENERATOR TYPE TF-144H/S: Frequency Range 10Kc/s-72Mc/s. RF Output 2µV-2V at 50Ω. Int. Mod. 400 and 1000c/s. Excellent condition with Manuals. £200.00 each. Carr. £2.

FREQUENCY METER BC-221: 125-20,000 Kc/s, complete with original calibration charts. Checked out, working order £18.50 + £1 carr.; OR BC-221 (as received from Ministry), good condition, less charts, £8.50 + £1 Carr.

MARCONI DEVIATION TEST SET TF-934: 2.5-100Mc/s (can be extended up to 500Mc/s on Harmonics). Dev. Range 0-75Kc/s in modulation range 50c/s-15Kc/s. 100/250V a.c. £45 each, £1.50 carr.

TELEPRINTER CREED TYPE 7B: Page-printer, 24V d.c. power supply, "as new" condition, in original packing case, £25.00 each. Second-hand condition (excellent order), no parts broken, £15.00 each. Carriage both types £2. CREED TELEPRINTER TYPE 7B: Page-printer (GPO Model) with 110/250V d.c. motor £20 each. Secondhand condition. Carr. £1. CREED TELEPRINTER 54/N4: This type of teleprinter has 4 keyboards with letters and figures, £75 each: Carr. £1. CREED TELEPRINTER MODEL 75: Receiver only. Page. £35 each. Carr. £1. CREED TELEPRINTER MODEL 75: Receiver and transmitter. £45 each. Carr. £1. CREED REPERFORATOR TYPE 7P/N4: £35 each. Second-hand condition. Carr. £1. CREED REPERFORATOR TYPE 7P/N3: £25 each. Second-hand condition. Carr. £1. CREED TELEPRINTER RECEIVING REPERFORATOR 7TR/3: Provides a means for storing in the form of perforations in a paper tape, messages received in Start-Stop code at stations where traffic has to be transferred from one circuit to another. Will interpret signals correctly from either 7-unit or 7 1/2-unit transmitters; standard operating speed is 50 bauds. Punching mechanism designed to punch one or two tapes simultaneously. Can accommodate 1 or 2 tape rolls. Automatic starter which enables unit to be left unattended. Brand new in cases complete with tuning fork, rolls of tape, and miscellaneous operating spares. Power supply 24v £30 each; or second hand cond. (no spares) £18.50 each. Carr. either type £1.50. CREED REPERFORATOR MODEL 85: secondhand, excellent cond. £18.50 each. CREED REPERFORATOR MODEL 86R: (similar to above) new cond. £30.00 each. Carr. either type £1.50. CREED AUTO TRANSMITTER 6S/4: secondhand cond. £10.00 each. Carr. £1. CREED AUTO TRANSMITTER 6S/4M: Secondhand condition. £12 each. Carr. £1. CREED AUTO TRANSMITTER 6S/6: new cond. £15.00 each. Carr. £1. CREED AUTO TRANSMITTER 6S/6M: Secondhand condition. £17 each. Carr. £1.

OSCILLOSCOPE PROBE TM8119

High impedance 100/1 resistive attenuated probe for accurate display of HF waveforms or short rise time pulse signals, offered brand new with all accessories and instruction manual. List price £17. Our price £17.50 including earth bayonet TM8119A. A MARCONI PRODUCT

MARCONI TF 1020A RF POWER METER. Range: 0-100 watts 75 ohms. £50 P. & P. 75p.
We have in stock wattmeters and RF loads up to 1,000 watts.

MUIRHEAD DECADE RESISTANCE BOXES

Type A-25-P. In 5 decades total resistance 111, 110 ohms. Accuracy 0.1%. Price £23. P. & P. 50p.

MUIRHEAD SCREENED ATTENUATOR TYPE A 304B
Impedance 600 ohms. 111db in steps of 10db. (H-section.) Price £50.

PHILIPS MODEL GM 6010. DC low level electronic voltmeter measurements from 1mV for full scale deflection to 300Vdc in twelve ranges. Indication on 5 inch mirror scale. A first-class instrument at an economical price. Only £40 plus battery. P. & P. 75p.

WAVE ANALYSERS

AIRMEC model 248 5MHz to 300MHz film scale frequency setting. Price £85
AIRMEC model 853 30kHz to 30MHz film scale frequency setting. Price £80
MULLARD FERROXUBES Type LA4. Brand new boxed. Price 95p P. & P. inc.

OSCILLOSCOPES

TEKTRONIX Type 551 with L&G plug in or CA type.
TEKTRONIX Type 545B with CA plug in, hand book.
TEKTRONIX Type 561A with types 3B3 and 3A6 plug in as new.
TEKTRONIX Type 661 sampling scope, with 452 and 5T1A plug-ins.
TEKTRONIX Type 531A DC to 15MHz. All the above oscilloscopes have been carefully tested and calibrated and carry a six months guarantee, large savings up to 50% can be made on the manufacturers list price. Or if you are considering upgrading your equipment we can offer you a fair price for any used Tektronix scope, or plug-ins.

MUIRHEAD PRECISION DECADE OSCILLATOR TYPE 890A

Frequency range = 1Hz to 111.11 KHz incorporates precision 5MHz crystal with miniature scope display any frequency within the range may be selected and repeated with absolute accuracy. Perfect condition. Price £135
MUIRHEAD Modulator Type D-978-A Price £125
MUIRHEAD PHASE METER Type 729-AM Enables user to read direct indication of phase angle and the difference in level between two sinusoidal voltages, both voltages may also be measured. Supplied in as new condition. Price £275

SOLARTRON PHASE ANGLE MEASURING EQUIPMENT
Comprising: Low frequency decade oscillator 4 phase type OS-103.
TFA Carrier Converter type JX-641 and Phase Sensitive Volt Meter type VP250.

LOW FREQUENCY SPECTRUM ANALYSER TYPE FENLOW
Range 0.3Hz to 1KHz excellent condition Price £100

AIRMEC ELECTRONIC OHM-METER 861
Resistance may be read directly on large six inch scale meter from 0.3 ohm to 10M ohms in six ranges in good serviceable condition for 240vac operation £33

SCHOMANDL PRECISION FREQUENCY METER TYPE FDI WITH FDMI ADAPTOR
GPO approved equipment for Radio Telephone Marine servicing etc., offered in as new condition with calibration certificate.

5 MULLARD OC36 TRANSISTORS
Mounted on plug in P.C. Board. Absolutely brand new unused. Size 6x5 ins. Our price only £1.25 p. & p. inclusive.

10 MULLARD GET I13 TRANSISTORS+10 diodes resistors etc. Size 6x5 ins. Brand new boards. Only 55p p. & p. inclusive.

AERIAL CHANGE/OVER RELAYS
of current manufacture designed especially for mobile equipments, coil voltage 12v., frequency up to 250 MHz at 50 watts. Small size only, 2 in. x 1/2 in. Offered brand new, boxed. Price £1.50, inc. P.&P.

MINIATURE AEI UNISELECTORS
12 position x 3 bank 250 ohm coils, 1 bridging and 2 non-bridging wipers available now—Types 2200A and 2302A complete with bases. Price £4 p.p. 50p

ETHER TRANSITROL TEMPERATURE CONTROLLERS. MODEL 990
Range 0-1,000°C and 0-800°C. Auto cold junction compensated, the easy way to regulate ovens, furnaces, etc. Offered brand new boxed £28. Little used type £22 each. P.P. 50p.

**CIRSACLE METERS**

The Servomex controllers are high quality units designed to keep your mains voltage constant regardless of deviations on line voltage, the units are not frequency conscious and very suitable for photographic uses and test equipment etc.

Types available:
AC2/Mk2B max. rating—9 amps .. £45
AC7 max. rating—30 amps .. £75

White scale, black numerals

TELEMAX HIGH VOLTAGE INSULATION TEST SET. Model E.115.
1kv. to 15kv. Used for the detection and measurement of leakage current and the operation of high voltage apparatus, the output voltage used is measured on a large 3 1/2 in. meter, any leakage which flows in the test circuit is indicated on the same calibrated meter. The instrument is non-lethal and may be short circuited without damage, small portable mains operated supplied in first class condition. Price £30.

TINSLEY VERNIER POTENTIAL-METER 4363D

DORAN VERNIER POTENTIAL-METER, portable type with potential divider and galvanometer.

DORAN pH Meter Portable type £18.
DORAN WHEATSTONE BRIDGE. Portable. £20.

MAGNIFICATION METERS
Marconi Q Meter Model TF329G perfect condition .. £50
Marconi HF Q Meter TF886A perfect condition .. £40

WESTERN ELECTRIC. Frequency Standards incorporates precision 200Hz value maintained fork. This small module has many applications. Only £7.50.

CANNON XLR AUDIO SERIES PLUGS & SOCKETS

XL 3-11. 3 pole plug
XL 3-32. 3 pole socket 125p The pair
XL 6-11. 6 pole plug
XL 6-32. 6 pole socket 150p The pair
XL 3-32. 3 pole socket fixed .. 75p
XL 3-31. 3 pole socket fixed .. 75p
Offered brand new sealed packs at a little over half price.

LUCAS CAR RELAYS. 12 v. Heavy duty make. Suitable for spotlights, horns, overdrives, etc. Brand new. Only 37 1/2p. Special price for quantities.

LUCAS POWER DIODES
Type DD 716
P.I.V. 400 max. 35 amp (gold plated) stud mounting. In sets of four. Only £2. P. & p. 10p.

AM/FM SIGNAL GENERATOR
TF948
Variable output 1µV-100 MV in one db steps continuously variable AM Mod to 80%. FM Mod Variable 600 KHz max frequency range in 2 bands 20-80MHz. Price £85.

ROBAND STABILISED P.S.U.
V50/50
4 decade voltage selection from 0-500 at 0.5 amp output adjustable in 5000 steps. Voltage and current clearly indicated on quality meters. Fuse/Protected late equipment. Price £85.

MAGNETIC AB (SWEDEN) NOISE FIGURE METERS
Type 113
As new. With Plug-in Amplifiers.

ROHDE & SCHWARZ POLYSCOP SWOB I
c/w accessories for sale or hire.

SIX Level A.E.I. Uniselectors miniature plug in type 2216A coil 125 ohms. non-bridging wipers with index. 12 position 6 bank. Absolutely brand new in makers cartons sold complete with base. £6.50

IMHOFS FRILEC INSTRUMENT FANS
Dimensions 1.5 ins. deep x 4.5 x 4.5. Very silent running precision fan specially designed for cooling electronic equipment, amplifiers, etc. for 110V a.c. current practice is to run fan from split primary of mains transformer or use suitable mains dropper. Available brand new, boxed, list price over £10. Our price £2.75. P.P. 20p.

SERVOMEX MAINS VOLTAGE CONTROLLERS

The Servomex controllers are high quality units designed to keep your mains voltage constant regardless of deviations on line voltage, the units are not frequency conscious and very suitable for photographic uses and test equipment etc.

Types available:
AC2/Mk2B max. rating—9 amps .. £45
AC7 max. rating—30 amps .. £75

BARGAIN OFFER—LOW VOLTAGE STABILISED POWER SUPPLIES
*Voltage Range 16-24V.
*Current Range to 6 Amps.
*Full over-voltage and Current protection.
*AC Ripple content better than 5mV. These PSUs are constructed to exacting standards and incorporate the very best of components and circuit design for long life and reliability. Employs Silicon transistors, thyristors, C-Core transformer etc. Offered in perfect condition, carefully checked before despatch. List price over £125. Our price only £26.50. Carriage £1. 9 Amp model .. £30

UNISELECTOR SWITCHES
Standard BPO Type, 3 bank, 25 positions (+ 4 position auxiliary bank), bridging wipers, fitted spark suppression. Brand new and boxed, famous manufacturer. Price only £2.75. P. & P. 25p.
BPO Type, 16 banks, 50 positions, full wipe non-bridging contacts. 100 ohms. Coil operating voltage 48V. Offered in good used condition at only £5 each. P. & P. 50p.
BPO Type, 8 banks, 25 positions, 48V. operation. Offered in good used condition for £2 each. P. & P. 25p.

POLARAD SPECTRUM ANALYSER
Model 2992A
Frequency coverage 0.01 GHz-91 GHz. Latest type solid state. Price and details on request.

MULLARD VALVE TESTERS HI-SPEED
A few of the following available. Mks. II and III with 300 cards. Fully overhauled and electrically perfect. £47.50. Mk. IV with 1,000 cards. £65. All supplied with instructions, etc.

R.F. SIGNAL GENERATORS
MARCONI TF801D/I range 10 to 485 MHz P.U.R. £42
MARCONI TF801A range 10 to 300 MHz £42

MARCONI TF867 range 15kHz to 30MHz £175
MARCONI TF762C range 300 to 600 MHz £65

HEWLETT PACKARD 612A 400 to 1200 MHz P.U.R.
HEWLETT PACKARD 616a 1780 to 4,000 MHz £125
AIRMEC Model 201 range 30kHz to 30 MHz £75
AIRMEC Model 701 range 30kHz to 30 MHz £65
AIRMEC Model 257 range .003 to 30Hz £55

SAUNDERS/MARCONI CT480 range 7 to 12 GHz £105
SAUNDERS/MARCONI CT478 range 1.3 to 4.5 GHz £85

AUDIO OSCILLATORS SQUARE WAVE GENERATORS

DONNER (USA) Model 1200 sine wave range—1Hz to 1MHz in six ranges variable amplitude. Price £40
MARCONI TF895A 25Hz to 5 MHz sine/square. Price £35

TEKTRONIX Model 105 square wave 1Hz to 1MHz. Price £60
PRECISION APPARATUS INC. sine wave 5Hz to 600kHz. Price £40
SOLARTRON Model CO-546 25Hz to 500kHz Price .. £35

COLLINS MECHANICAL FILTERS
Type F455 J31
B9A fitting new price £7.50.

Cossor Electronic Invertors type CRA 200. A high quality device for producing a 115v 400HZ single phase output. Incorporating the following features: Input 23-28V D.C.
* Full overload protection.
* Sine wave output.
* Remote control facilities.
* Completely Solid State (Silicon transistors).
* Built to Aircraft specifications.
* 180VA of output continuous.
May be run in series operation for 3 phase requirements. Offered brand new boxed units. Price £17.50 Carriage 50p

Constant Voltage DC Power Supplies Model DC8

A stabilised unit supplying 48Vdc at 4 amps input 200-245vac stabilised to within +1% at full load. Supplied new .. £12

DISTORTION FACTOR METER RADIOMETER TYPE BKFS

As New with Manual. Price £85.

COAXIAL SWITCHES
American Manufacture
Suitable for aerial changeover and high frequency switching up to 1,000 MHz miniature Vacuum drawn type 110 v dc operation connections BNC and N types. Offered brand new, boxed. Price £3.25.

LEAD-ACID EQUIPMENT BATTERIES 10v 5AH.
Transparent casing. Size 2 1/2 x 5 x 7 in. Offered brand new and boxed, 2 batteries per box, complete with links and full instructions. Can supply voltages in the range from 2-20v. Price £2.25, inc. P. & P.

OSCILLOSCOPE
Solartron Type 523/S.2. DC-10 MC/S Bandwidth. Sensitivity max. 1 MV/CM. Fully overhauled and calibrated. Ready for use. Guaranteed 3 months. Price £52.50. P. & p. £2.

MARCONI TF96 IMPEDANCE BRIDGE
Inductance range: 1µH to 100 Henrys.
Capacitance range: 1pF to 100 µF.
Resistance range: 0.1 ohm to 100 MΩ.
Components may be measured at 80Hz, 1kHz and 10kHz. Accuracy nominally 1%. Power supply 100-250V a.c. Offered in as little used condition. Price £65.

We will overhaul, service and calibrate any type of oscilloscope quickly and efficiently. We also purchase Solartron, Tektronix, Tequipment, EMF, Cossor, etc.

MUIRHEAD PRECISION 50 Hz ELECTRONIC TUNING FORK

Type D418D
Output variable. Amplitude 300V max. Applications suitable for time standard driving, etc. New condition. Price £55.

LORAN RECEIVER TYPE 262A.
Marine Set. Use: for long-range navigation to enable operator to determine his position when weather conditions or distance prevent the use of standard methods. Range 750 miles (day), 1400 miles (night). Dimensions 18 x 17 x 26 in. The above units are offered in good used condition, complete with technical manual. Price £50.

VARIACS (DURATRAC)
3 amp type motorised version. 240 AC. As new. Only £8.50. P. & p. 50p.
Variac Zenith 15 amp model. As new condition. Price £17.50.
Also motorised version of above, with Drayton RQ motors. £23.50.

HELICAL POTENTIOMETERS
STC Relcon, 10-turn, Type No. HEL/07-10/1001/A. Following values supplied ex-stock.

Res. 500 ohm ±1%
1K ohm
5K ohm
20K ohm

All above Helicals are brand new stock. Quantities available. Price £1.25 each. P. & P. 5p for one.

Beckman Type A Helical pots. 5 Watt, 10 turn. Resistances available. 30Kohms and 50Kohms. Brand new and boxed. Price £1.75 each.

Bournes Helical pots. Miniature type. Resistance 10Kohms. Brand new. Price £1.50.

We have available from stock many other types and values, please telephone for quotation.

OMRON POWER RELAYS. Type Mk2PL. 230 V. A.C. coil. Two heavy duty c/o contacts. Complete with perspex cover and actal base. New and boxes. Price 80p. Carriage each 5p.

"INTERCOM TELEPHONES"
We have a large quantity of modern desk telephones and associated 10 watt amplifiers available together with telephone dials, and standard B.P.O. components preferably to be sold as one lot.

P.F. RALFE 10 CHAPEL ST. LONDON N.W.1
Phone 01-723 8753



**HEWLETT PACKARD TYPE 185B
VERSATILE SAMPLING SCOPE**

This instrument brings the convenience of the low frequency scope to high frequency measurements in the micro-nano and picosecond ranges.

Full specification and price available on request.

BRAND NEW ONE ONLY



**SMITHS SERVOSCRIBE TYPE
RES11.20 FLAT BED RECORDER**

A multi-range, multi-speed desk type potentiometric recorder designed for general laboratory use where the record is required to be expressed linearly with respect to time. Records may be made on either roll charts or graph sheets in either ink or ball pen.

Input range: 2mV to 20V in 11 ranges or continuously variable.


Recording width: 8 ins. (200 mm).

Response: 1 sec for f.s.d. (nominal).

Chart drive: 8 speeds 600/mm/min to 30 mm/hr synchronous.

Supply: 230V 50Hz.

Manufacturer's Price.....£300.00
Electronic Brokers' Price.....£195.00




**AIRMEC 853 H.F. WAVE
ANALYSER**

Frequency range: 30KHz-30MHz in 7 bands.

A very popular instrument which has been refurbished to manufacturer's specification.

£45.00

**SALES BULLETIN
SEND FOR
YOUR FREE COPY**



**ROHDE & SCHWARZ Zg
DIAGRAMS HF
IMPEDANCE PLOTTER**

These instruments will rapidly plot the loci of the impedance or admittance of any item such as antennas, transformers, absorbers, filters and other networks. Impedance measurements are possible from 0.02Z₀ to 50Z₀, where Z₀ = 50, 60 or 75 ohm.

Type ZDU 30-420MHz.....£550
Type ZDD 300-2400MHz.....£650

ELECTRONIC BROKERS



PORTABLE TRANSISTOR TESTERS

TYPE R2446
Self-contained battery powered for checking leakage, current and gain of PNP and NPN transistors. Meter and audio indication. Gain range 10-150 continuously variable. PRICE: £7.50

TYPE R2285
Self-contained battery powered for checking leakage, current and gain of PNP transistors only. Meter and audio indication. Gain range 10-150 continuously variable. PRICE: £4.85

BRAND NEW MINIATURIZED AUTOMATIC STRIP CHART RECORDER

by RUSTRAK of America. This recorder indicates the magnitude of applied currents or voltages by a continuous distortion-free line on pressure sensitive paper. Chart width 2 1/2 in. Chart speed 1/2 in. per min. Moving coil movement, scale calibrated 0-100 microamps. Int. resistance 4,600 ohms. Chart drive motor 12V DC. Supplied less case. C/W handbook. Price £40. P. & F. 50p.

MEMORY PLANES

Ferrite core memory planes with wired ferrite cores. Used for building your own computer or as an interesting exhibit in the demonstration of a computer. Mounted on plastic material, frame 5x8 in. Consisting of matrices 40x25x4 cores each one individually addressable and divided into 2 halves with independent sense and inhibit wires. £6.65. P. & F. inclusive.

TEN TURN 360° ROTATION POTENTIOMETERS

Res. Ohms	Linearity Per cent	Manufacturers	Model	Price
100/100/100	0-5	Beckman	A.S.	£8.00
200	0-5	Beckman	A.	£3.00
500	0-1	Colvern	2501	£2.25
500	0-1	Colvern	2610	£2.50
500	0-1	Colvern	28/1009/11	£3.00
500	1-0	Relcon	HEL107-10	£2.25
1K	0-5	Beckman	SA1101	£3.00
2K	0-25	Beckman	7216	£3.00
2K	0-25	Reliance	GPM15	£2.00
2K	0-1	General Controls	GPA15/4	£2.00
5K	0-5	Relcon	07-10	£2.50
5K	0-5	Colvern	CLR2503	£3.00
10K	0-5	Beckman	A.	£3.00
10K	0-1	Colvern	CLR25/1001	£3.50
15K	0-1	Colvern	CLR2402	£3.00
18K	0-5	Beckman	A.	£3.00
25K	0-5	Hellpot	8AJ337	£3.00
29K	0-05	Beckman	SA1244	£4.50
30K	0-1	Colvern	2409	£1.50
30K	0-1	Beckman	8A95C	£3.00
30K	0-1	Beckman	A.88	£3.50
30K	0-5	Beckman	8A1692	£3.00
30K	0-25	Beckman	8A1679	£3.25
30K	1-0	Colvern	2492/1	£1.50
50K	0-1	Reliance	07-10	£2.25
50K	0-1	Colvern	07-5	£2.25
50K	0-1	Colvern	2503	£2.25
50K	X	Foxes	PX4	£2.25

Res. Ohms	Per cent Linearity	Manufacturers	Model	Price
50K	0-5	Beckman	A.	£3.00
50K	0-1	Beckman	A.	£3.50
100K/100K	0-5	Ford	A.	£3.50
100K	0-1	Beckman	A.	£3.00
100K	0-5	Beckman	A.	£3.50
100K	0-5	Colvern	2501	£2.25
100K	0-1	Colvern	2610	£2.50
298K	0-1	Beckman	SA3902	£3.50
300K	0-1	Beckman	A.	£3.50

THREE TURN 780° ROTATION

Res. Ohms	Per cent Linearity	Manufacturers	Model	Price
100/100	0-5	Beckman	C.	£3.00
100/100	0-5	Beckman	Type C	£3.00
300	0-5	Beckman	9303	£2.25
1K	0-5	Fox	PX2/H3	£2.25
10K	0-5	Beckman	C.S.	£2.25
20K/20K	0-1	Beckman	C.S.	£3.00
10K/10K	0-1	Beckman	C.	£3.00
50K	0-5	Beckman	C.	£1.75

FIFTEEN TURN 5400° ROTATION

Res. Ohms	Per cent Linearity	Manufacturers	Model	Price
25K/25K	0-5	Beckman B.	10 watts	£8.50
46K/46K	0-5	Beckman B.	10 watts	£8.50

TWENTY TURN 7200° ROTATION

Res. Ohms	Per cent Linearity	Manufacturers	Model	Price
1 Meg.	0-5	General Controls	PXM130	£4.00
50K	0-5	Reliance		£2.00

156 TURN 56760° ROTATION

Res. Ohms	Per cent Linearity	Manufacturers	Model	Price
490	0-5	Kevin Hughes	KTP0701	£9.50

FIVE TURN 1800° ROTATION

Res. Ohms	Per cent Linearity	Manufacturers	Model	Price
200	0-5	Relcon	HEL07-05	£2.25
500	0-5	Colvern	CLR2505	£2.00
U1-5K	0-5	Colvern	CLR2505	£2.00

FIVE-AND-A-HALF TURN

Res. Ohms	Per cent Linearity	Manufacturers	Model	Price
500	0-5	Colvern	2405	£2.00

OUR STOCKS ARE CONSTANTLY CHANGING—PLEASE LET US KNOW YOUR EXACT REQUIREMENTS

DYNAMCO 2010 DIGITAL VOLTMETER

Fully overhauled. Calibrated (certified) and Guaranteed.

Specification: Scale 109999. DC. Accuracy: 0.001% f.s.d. Range: 10 microV-1 kV; I/P Z greater than 25,000 M ohm; C.M.B. DC. 160 dB. 50Hz. 130 dB O/P. Parallel E.C.D. Inductive potentiometric system for excellent stability. Price: £850 (new price over £2,000).

HEWLETT PACKARD TYPE 8551B SPECTRUM ANALYSER

A highly versatile analyser which covers the range from 10-1MHz to 400Hz. The accuracy and flexibility of the instrument make it suitable for many applications beyond the capability of other spectrum analysers. These include wideband but rapid RFI measurements, spectrum surveillance, and spectrum signature work, and semiconductor evaluations embracing such tests as fast pulsing viewed in the frequency domain. Full specification and price on application.

ELECTRONIC BROKERS LIMITED (Dept. WW/4)
49/53 Pancras Road London NW1 2QB
Telephone 837 7781 Telex 267307

SPECIAL OFFER!

SINGLE PEN RECORDER—ELLIOTT TYPE 230

A most versatile pen recorder producing a trace on a curvilinear 3 in. strip chart. Two synchronous speeds: 1 in. and 6 in. per hour.

Fitted with high and low alarm contacts operated by the moving coil. Basic movement 0-1mA DC coil resistance 400 ohms. Fitted with rectifier to allow operation on AC effective coil impedance at 50Hz 1800 ohms.

Power supply required: 230V 50Hz

Applications: Ideal for recording relatively slow changing phenomena such as:
Temperature: Gas or liquid Flow Rates, Sound Levels, Speed variations, Power Demand, Rainfall, humidity, etc.

PRICE £25.00
Clockwork version also available **PRICE £29.50**

MARCONI TF867 STANDARD SIGNAL GENERATOR

Carrier Frequency:
Range: 15Kc/s-30Mc/s in 11 bands.

Calibration Accuracy: ±1%.

Stability: After warm up the drift in a 10-minute period is, typically, less than 0.005% for carrier frequencies up to 3-2Mc/s and less than 0.01% from 3-2-2-30Mc/s.

Output Voltage: 0.4µV-4V.

Impedance: 75 ohms nominal for outputs from 2-4V. 75 ohms for outputs from 4µV-2V. 13 ohms for outputs from 0.4µV-0.4V.

Accuracy: below 3Mc/s ±0.25dB or ±0.1µV. 3-10Mc/s ±0.5dB or ±0.2µV. 10-30 Mc/s ± 1.0dB or ±0.5µV.

Power Supply: 100-125V. 200-250V 40-100c/s.

Dimensions: 18 in. high x 21 in. wide x 14 in. deep.

Price: £185.00

MARCONI TF995A/2 FM/AM SIGNAL GENERATOR

A compact instrument suitable for broadcasting and testing in I.T.U. bands 6, 7 and 8.

Frequency range: 1.5-220MHz.

Output Volts: 0.1µV to 200mV.

£175.00

SERVO COMPONENTS

We have a large stock of servo components including motors, tachogenerators, gearheads, etc. Please let us know your requirements or ask for our current stock list.

MODEL 1706 VISICORDER U/V RECORDER

In almost new condition. This direct reading U/V Recorder can record up to 6 channels simultaneously from DC 5000Hz at writing speed of 30,000 ohms/sec. Recording range: DC-5000Hz. Paper width: 4 1/2 ins. wide. Optical Arm: 19 cm. Paper Speeds: Eight speeds from 0.25-32 in./sec. and 6-800 mm/sec.

Dimensions: H. 10 1/2 in., W. 12 in., Depth 14 in.

Complete with 4 3KHz Galvos. £350

GENERAL PURPOSE MULTI-RANGE ELECTROMETER

Electronic Instruments Model 6610

Accuracy: On the voltage ranges the accuracy of the meter is better than 1% and the amplifier better than 1/2% on all ranges.

Amps: 0 to 10⁻¹⁴ amps f.s.d. to 0 to 3 x 10⁵ amps f.s.d.

Coulombs: 0 to 10⁻¹² coulombs f.s.d. to 0 to 3 x 10⁻³ coulombs f.s.d.

Volts: 0 to 0.1V f.s.d. to 0 to 30V f.s.d.

I/P Resistance: 10⁵ ohms.

I/P Capacitance: approx. 3pF.

Zero drift typically better than 2% in 24 hours.

Brand new and guaranteed for 3 months..... £95.00

A BARGAIN IN NEW POWER SUPPLIES. AT LESS THAN HALF MANUFACTURER'S PRICES

O/P Voltage 7.5V-9V. Max. load current 10 Amps. Max. ripple on full load approx. 60mV. p-p. Threshold current. 10-5A. Overvoltage protection. OUR PRICE £19.50

Join BBC's Saturday People with the CT80!



© Radio Times

One of BBC radio's most exciting stars! Rosko is a high spot on Radio 1's non-stop pop programme with his action packed show.

Along with the other Saturday D.J's, Rosko uses the versatile CT80 to drive his show along

with a remarkable combination of hard rock and noise.


With every desirable feature and proven performance Plessey CT80 Cartridge Recorders are used by major broadcasters around the world. Contact us for complete details of the CT80 range.

PLESSEY



SALES Hayden Laboratories Limited Hayden House
17 Chesham Road Amersham Bucks
SERVICE 12-13 Poland Street London W1V 3DE
Telephone 01 7343748-9
or the manufacturer Plessey Electronics Pty. Limited
91 Murphy Street Richmond Australia 3121 Telex 30383
Cables PLESSELEC Melbourne

LINDAIR (ELECTRO-TECH) LTD

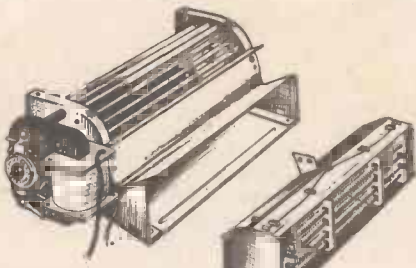

TANGENTIAL HEATER

Silently driven by a shaded pole Mycalex motor. Compact, powerful and quiet running with aluminium impeller (outlet $5\frac{1}{2} \times 1\frac{1}{2}$). Mains voltage. PLUS matching heater unit with spiral element. May be switched for 500 or 1,000 watts.

PRICE ONLY £1-60
P. & P. 40p.

PROGRAMME TIMER BY HONEYWELL
A bank of 15 micro-switches are each independently operated by 15 pairs of cams which in turn are individually adjustable to give switching periods of zero to 12 seconds with infinitely variable combinations. A mains synchronous motor drives the cam shaft at 1 rev. per 12 seconds (5 R.P.M.). Designed originally for vending machines at a cost of £15-00 plus. Many applications where continuous sequence programmes are required, such as lighting effects etc. New in original makers cartons. First class value at £5-75 plus 25p P. & P.



"GOYEN" PRESSURE SWITCH—Incorporating differential adjustment between 2" and 12" water gauge (a max. of approx. $\frac{1}{2}$ p.s.i.). A single pole change-over switch rated 15 amps. 250v. is actuated. Air inlet tube $\frac{1}{2}$ " dia. Projection $\frac{1}{2}$ ". Overall size, dia. $3\frac{1}{2}$ ", depth 2" plus $\frac{1}{8}$ " (air tube). £1-25.

"TEDDINGTON" CONTROLS THERMOSTAT—Adjustable between 75° and 100°C. A further internal adjuster takes the maximum up to 120°C. Circuit cuts in again at 3° below cut-out setting. 42" capillary and sensor probe. The thermostat actuates a 15 amp. 250v. c/o switch. A second single pole on/off switch is incorporated in the adjustment mechanism. 88p.

VINKOR POT CORE ASS. TYPE LA.2103 (core LA.2100). Normal price £1-48. Our price 75p each. Special quote for quantity.

UNISELECTORS. 8 Bank 25-way 24v. Double sweep. Brand new in maker's boxes. £5-25. P. & P. 25p.

AMPEX 7-5v. D.C. MOTOR. This is an ultra-precision tape motor designed for use in the AMPEX model AG20 portable recorder. Torque 450MG/CM. Stall load at 500ma. Draws 60ma on run. 600 rpm $\pm 5\%$ speed adjustment, internal AF/RF suppression, $\frac{1}{4}$ " dia. x 1" spindle, motor $3\frac{1}{2}$ " dia. x $1\frac{1}{2}$ ". Original cost £16-50. Our price £4-25. P. & P. 25p. Large quantity available (special quotations). Mu-metal enclosure available 75p each.

"WINGCHESTER" (U.S.A.) TRACK STEREO RECORD/REPLAY HEAD. 200mH. £2-50 Carr. Paid.

"CROUZET" TYPE 96S. 115/240v. 50Hz. 47/48 watts. 50 rpm. Scoutly constructed. Size: $2\frac{1}{2}$ " dia. x $3\frac{1}{2}$ " long, plus spindle $1\frac{1}{2}$ " x $\frac{1}{4}$ " dia. Anticlock. £2-75. P. & P. 25p. TYPE 95S. Same as above, but 3 rpm. £3-00. P. & P. 25p.

Unless otherwise stated—all items are NEW and UNUSED. Postal or carriage charges are for Great Britain only. We welcome orders from established companies, educational establishments, etc. All orders under £2-50, cash with order please.

MICRO-LITES

Wonderful engineering—micro miniature incandescent lamp small enough to pass through the eye of a needle! 1,000's of uses. Will operate from the output of a transistor. Rating: 1.5v, 10-15ma. Size 4.4 x 1.4mm. dia. Leads 22mm. These fantastic lamps have a life expectancy of 1,000 hrs.

OUR PRICE £3-25
per doz.
Free p. & p.



"PRECISION FAN CO." (Smiths Industries) DOUBLE ENTRY CENTRIFUGAL FAN/BLOWER—This is a beautifully balanced, particularly quiet running unit giving approx. 90 cubic ft./min. The motor is a 2 pole shaded pole 240v. Mycalex, drawing only 240ma on run. Weight 2 1/2 lb. Sizes: Case dia. 3-1", width (case only) 3-12 1/2 in., width overall (inc. motor) 5-25 in., aperture 3-12 1/2 in., by 1-8 1/2 in. Offered well below makers price at £2-95 P. & P. 25p.

"SORENG" MAINS SOLENOID. 1" travel, 18 lb. pull (approx.). Size: $2\frac{1}{2}$ " long x $2\frac{1}{4}$ " x $2\frac{1}{2}$ " high. Powerful-£1-75. P. & P. 25p.

NEW "ISKRA" 240v. A.C. RELAY—3 x 6 amp Change-over contacts. 63p.

S I E M E N S HIGH SPEED RELAY. Type 89L. 1,700 μ + 1,700 μ coil. New 63p each.

"DAVENSET" MAINS SOLENOID. 1" travel. 8 lb. pull (approx.). Size: $2\frac{1}{2}$ " long x $2\frac{1}{2}$ " x $2\frac{1}{2}$ " high. Similar in appearance to "SORENG" £1-25. P. & P. 25p.

6 DIGIT NON-RESET COUNTER by E. N. M. Ltd. 240v. A.C. Size $2\frac{1}{2}$ " high x $1\frac{1}{2}$ " x $1\frac{1}{2}$ ". £1-75.
5 DIGIT NON-RESET COUNTER 240v. A.C. £1-20.

SEEN THIS? THIS IS THE ONLY WAY WE COULD ILLUSTRATE THIS FABULOUS ITEM!

NORPLEX the famous American fibre-glass copper-clad laminate. Finest quality with Woven Glass base of Epoxy-resin. Excellent mech. and elec. conductive properties. Heat Resistant. Ideal for P.C.s, etc. THIS IS A SPECIAL PURCHASE AND ONLY AVAILABLE WHILE STOCKS LAST. Sizes: $12" \times 12"$; $24" \times 12"$; $24" \times 24"$; FULL SHEET $43" \times 37"$ (11 sq. ft.). Single sided copper with thicknesses of $\frac{1}{16}$ ", $\frac{1}{8}$ ", $\frac{3}{16}$ ", $\frac{1}{4}$ ", also Double sided $\frac{1}{16}$ ", $\frac{1}{8}$ ", $\frac{3}{16}$ ", $\frac{1}{4}$ ". PRICE ONLY £1 per sq. ft. £8 per full sheet. P. & P. 25p up to 4 sq. ft. Over 4 sq. ft. (cut sizes only) Post FREE. Full sheets post by rail G.B. only £1 one or more sheets.


FURTHER BULK PURCHASE SILVANIA MAGNETIC SWITCH NOW COMPLETE WITH REFERENCE MAGNET!
A magnetically activated switch. Vacuum sealed in a glass envelope. Silver contacts normally closed, rated 3 amp at 120v, 1 1/2 amp at 240v. Size (approx.) $1\frac{1}{2}$ " long x $\frac{1}{2}$ " dia. Ideal for Burglar Alarms, Security systems, etc., and wherever non-mechanical switching is required. New Lower Price. Only £2-10 for 12. £8 for 50 or £15 for 100 complete with magnet.

ATLAS SUB-MINIATURE LAMPS type LI12 and LI123—a high efficient light source with excellent light output and low power demand. Ratings 5v. 60ma. $75 \pm 25\%$ lumens. Life expectancy 60,000 hours or at 6v. 70ma. $75 \pm 25\%$ lumens 5,000 hours. Dimensions: Uncapped 6.3×3.1 mm. leads 12.7 mm.; capped 9.1×3.1 mm. Ideal for instrument lighting normally sold in excess of 60p each, our price £1-50 per dozen or boxes 50 at £5 per box.

ATLAS MIDGET PANEL LAMPS unrivalled for indication purposes requiring a brilliant but tiny light source. Available with flange cap or wire ended in the following ratings: Capped: 6v. 1A and 12-14v. 0.8A. Uncapped: 4v. .25A, 6v. 1A, 6v. 2A. £1.20 per dozen or boxes of 50 at £4 per box.

LT. TRANSFORMERS. Prim. 220/240v. Sec. 0-5 10-15-20v. at 2 amps. £1-25 P. & P. 15p.
Prim. 200/240v. Sec. 0-1-56-58-60 at 3-5 amps plus 0-90 at 100 ma. Wax impregnated with screw term. blocks. Weight 10 lbs. £3-60 plus 40p P. & P.
Prim. 220/240v. Sec. 0-13 at 1-5 amp. 63p. P. & P. 15p.

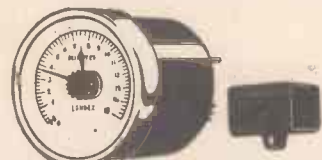"HONEYWELL" V3 Series. Flush micro-switch 10 amp. c/o. The side panel is insulated. End plate size: $2" \times 8"$. £1-50 per doz. Carr. Paid.



SYNCHRONOUS AUTO-RESET PROCESS TIMER BY LONDEX LTD.

Type 1MP Mk. 2.
Brand New and Boxed

These well known timers are already in world-wide use and are perfect for Industrial Electronic Timing, Research and for all machine control timing problems. Repetitive accuracy better than 0.5% of full scale setting. Two or more can be interconnected to give control of a series of processes. 230/250v. 50Hz, also available 60Hz. 15 minutes full scale, 15 secs. per division. Driven by self-starting sync. motor. Contact rating 5 amp at 250v. a.c. Incorporates solenoid operated clutch. Also, lever actuated micro switches.

Normal price probably in excess of £16. Complete with multi-pin connector as illustrated. **OUR PRICE ONLY £6-50**

"FINDER" 240v. A.C. Octal Relay 2c/o 6 amp contacts, Perspex enclosed, 75p.

"OMRON" Type 1050 Micro-switch action relay 12v. D.C. 1c/o 65p.

S.T.C. Midget Sealed Relay type 4109EC. 12v. 40 mA 170 μ , single H.D. make. 53p each.

"B. & R." 3 c/o. 10 amp. contacts (silver) operates n 2 volts D.C. Draws approx. 1 amp. Size: $2" \times 1\frac{1}{2}" \times 1\frac{1}{2}"$. £1-00.

MAGNETIC DEVICES. 12v. 3xH.D. c/o Contacts size $1\frac{1}{2}" \times 1" \times 1\frac{1}{2}"$. 63p each.

SANGAMO WESTON. Moving coil relay 315 Ω 310 μ a, complete with base, 75p each.

"MALLORY" LONG LIFE BATTERIES. Type A. RM12 cell 1.35v. 3,600 ma/H. CAP. 250/300 ma cont. current. Size: $2\frac{1}{2}" \times 1\frac{1}{2}" \times 1\frac{1}{2}"$. 5 for £1-00 or £2-00 per doz. Carr. Paid.
Type B. Comprises 8 x RM625 cells. (1.35v. per cell), giving 10.5v. in all 350 ma/H. CAP. 20/25 ma cont. current. Size: $2\frac{1}{2}" \times 1\frac{1}{2}" \times 1\frac{1}{2}"$. 3 for £1-00 or £3-00 per doz. Carr. Paid.

GEARED MOTORS "Parvulus" Reversible 100 RPM G geared Motor. Type S.D.14. 230/250v. A.C. 22 lb./in. $\frac{1}{2}$ " spindle. 1st class condition. £7-50 each. P. & P. 50p. Also limited number only as above. Brand New. £12-50 each. P. & P. 50p.

"HONEYWELL" MICROSWITCHES
Two and three bank, manual push. Ideal for vending machines, etc. Each bank comprises a change-over rated at 15 amps 240v. A.C. The through-panel mounting assembly is in heavy polythene surmounted by black knob. Neck dia. $\frac{1}{4}"$. 2 bank 40p. 3 bank 55p.

CURRENT FLOW INDICATOR
Ideal for all types of battery operated equipment (portable machines, tape recorders, etc.). Four white segments appear when current flows. Coil is 600 Ω 6/12v. Drawing only 8 ma on function. Neat in appearance. Size: dia. $1\frac{1}{2}" \times 1\frac{1}{2}"$ deep. Fixing centres $1\frac{1}{2}"$. £1-50 each. Carr. Paid.

ERNEST TURNER 800 μ A METER
160 μ movement, 2" case, elliptical plastic front. Green-Red-Green uncalibrated scale. £1-50 each. Carriage Paid.

MYCALEX. Open frame shaded pole motors. 240v. 50Hz 7 rpm. 28 lb./in. 80 rpm. 12 lb./in. £2-25 each. P. & P. 25p.

BRAND NEW "GRYPHON" BROOK REVERSIBLE MOTORS. Type TE 230/250v. 50Hz. 1 Ph. .083 h.p. 1,380 rpm. 0-96 amp at full load, $\frac{1}{2}"$ spindle. This is a superbly constructed, standard-foot mounted unit, with the extra facility of reversal by remote switching. Weight 16 lb. 10 oz. Offered in original maker's packing at approx. half price. £7-50. Carr. 75p.

BRAND NEW "SMITHS" SYNCHRONOUS GEARED MOTORS. Revs per min. 2-3-6-10-30-60. Revs per hour. 15-20-40. Revs per day 4-8. 75p each. Carr. paid.

SYNCHRONOUS MOTORS. 220/380v. 50/60Hz. 250-300 rpm. 75p each.

MAINS INDUCTION MOTOR. Open frame, $\frac{1}{2}"$ spindle, weight $\frac{1}{2}$ lb. Powerful. 88p each. P. & P. 12p.

We would like to announce that **ELECTRO-TECH SALES** have now become members of the **LINDAIR GROUP** which will mean an expansion programme giving a comprehensive and streamlined service. Whatever your electronic or electro-mechanical requirements—contact us first, maybe we can help. We also welcome trade enquiries. Visit our new component shop **JUST OPENING** at 315 Edgware Road.

NATION WIDE SERVICE + ATTRACTIVE DISCOUNTS ELECTROVALUE - an independent company since its establishment in 1965

ELECTROVALUE Electronic Component Specialists

RIVLIN PRECISION RESISTORS

0.1% TO 0.01% TOLERANCE £1-£2 for values 100K and under Prices and delivery on request

RESISTORS - 10%, 5%, 2%

Table with columns: Code, Power, Tolerance, Range, Values 1 to 9, 10 to 99, 100 up available. Includes values for carbon film, metal oxide, and wire wound resistors.

Codes: C = carbon film, high stability, low noise. MO = metal oxide, Electrosl TR5, ultra low noise. WW = wire wound, Epressil. Values: E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. E24 denotes series: at E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions on total value of resistor order.)

CAPACITORS

SIEMENS 5% POLYCARBONATES

250V up to 0.1mF; 100V 0.1mF and above. 0.01, 0.012, 0.015, 0.018, 0.022, 0.027, 0.033, 0.039, 0.045, 0.056, 0.068, 0.082, 0.1, 0.12, 0.15, 0.18, 0.22, 0.27, 7p; 0.33, 0.39, 9p; 0.47, 10p; 0.56, 13p; 0.68, 15p; 1.00 30p.

MULLARD polyester C280 series

250V 20%; 0.01, 0.022, 0.033, 0.047 3p each; 0.068, 0.1, 4p each; 0.15, 4p; 0.22, 5p. 10%; 0.33, 7p; 0.47, 8p; 0.68, 11p; 1uF, 14p; 1.5uF, 21p; 2.2uF, 24p.

MULLARD SUB-MIN ELECTROLYTICS C424 range, axial lead

Values (uF/V): 0.6/4; 1/40; 1.6/25; 2.5/16; 2.5/64; 4/10; 4/40; 5/64; 6.4/6.4; 6.4/25; 8/4; 8/40; 10/2.5; 10/16; 10/64; 12.5/25; 16/10; 16/40; 20/16; 20/64; 25/6.4; 25/25; 32/4; 32/10; 32/40; 32/64; 40/16; 40/2.5; 50/6.4; 50/25; 50/40; 64/4; 64/10; 80/2.5; 80/16; 80/25; 100/6.4; 125/4; 125/10; 125/16; 160/2.5; 200/6.4; 200/10; 250/4; 320/2.5; 320/6.4; 400/4; 500/2.5.

LARGE CAPACITORS

High ripple current types: 1000/25, 28p; 1000/50, 41p; 1000/100, 82p; 2000/25, 37p; 2000/50, 57p; 2000/100, £1.44; 2500/64, 77p; 2500/70, 92p; 5000/25, 62p; 5000/50, £1.10; 5000/100, £2.91.

SIEMENS POT CORES

In a range of types having air gaps from 1.0 mm. to zero at prices from 19p for cores and 14p for adjusting screw. Full details, see our latest catalogue, post free 10p.

10W/150 BAXANDALL SPEAKER

As originally designed by P. J. Baxandall and described in Wireless World. 10 watt/150 ohm loudspeaker with equaliser network speaker unit and specially designed cabinet in kit form. Size when built approx. 18" x 12" x 10". Price, inc. carriage paid in U.K. £13.90

CARBON TRACK POTENTIOMETERS, long spindles. Double wipers

SINGLE GANG linear 100 to 2.2M Ohm, 12p; Dual gang log, 4.7k Ohm to 2.2M Ohm, 12p; Dual gang linear 4.7k Ohm to 2.2M Ohm, 42p; Dual gang log, 4.7k Ohm to 2.2M Ohm, 42p; Log/antilog, 10k, 47k, 1M Ohm only 42p; Dual antilog, 10k Ohm only, 42p. Any type with 2A D.P. mains switch, 12p extra. Only decades of 10, 22 & 47 available in ranges quoted. DUAL CONCENTRIC in any combination of above values, 60p; with switch, 72p.

CARBON SKELETON PRE-SETS

Small high quality, type PR linear only: 100 Ohm, 220 Ohm, 470 Ohm, 1k, 2k, 4k, 10k, 22k, 47k, 100k, 220k, 470k, 1M, 2M, 5M, 10M Ohm. Vertical or horizontal mounting, 5p each.

ZENER DIODES 5% full range E24 values: 400mW: 2.7V to 36V, 15p each; 1W: 6.8V to 82V, 27p each; 1.5W: 4.7V to 75V, 60p each. Clip to increase 1.5W rating to 3 watts. (type 266F) 4p.

SIEMENS 3N 3055 POWER TRANSISTOR

Made to Siemens superb standards of specification and dependability. With free insulating set. NOW ONLY 50p.



ELREMCO SOLDERSTAT SOLDER IRONS

A popular and beautifully made example from a wide and versatile range of soldering irons of exceptional quality. Type HMS for 16 or 24 watts. A.C. mains.



£1-70

Minitron DIGITAL INDICATOR

TYPE 3015F Seven segment indicator compatible with standard logic modules and power supplies. Figs. 0.9 from well illuminated filament segments to give character of 9mm height plus decimal point. Power requirement 8mA from 5V D.C. per segment. A limited number of alphabetical symbols also available. In 16 lead die case £2-00

Suitable BCD decoder driver type FLL12IT £1-35. Die Socket: 16 lead 30p. No. 3015G showing + or - and fig. 1 and decimal point £2.00.

MISCELLANEOUS ITEMS FROM STOCK

- 30W BAILEY AMP. PARTS: Transistors and PCB for one channel, £6.46. Rs and Cs for one channel. £1.95. Power Supply (Reg.) £4.75. MAIN LINE AMPLIFIER KITS: 70 watt power amp. module kit, £12.60 nett. Power supply kit, £6.00 nett. Matching pre-amp kit, £3.30 nett. (Above prices for mono.) Stereo Kit. 2 power amps. pre-amp kit, power supply kit and matched controls for building into your own cabinet, £38.40 nett. S-DeC, £1.44; Four pack, £5.10. DeCSTOR pack, £2.88. T Dec, may be temperature cycled (208 points), £2.88. uDecA, £3.18. uDecB, £5.84. Also integrated circuit carriers. THERMISTORS: VA1039, VA1040, VA1055, VA1066, VA1077, CZ-6, K151-1K, VA1100, 15p. R24, R53, R54, £1.35. R154. HANDBOOK OF TRANSISTOR EQUIVALENTS, 40p. HANDBOOK OF TESTED TRANSISTOR CIRCUITS (H. Mass), 40p. RADIO & ELECTRONICS. Colour codes & data wall chart, 15p. ENGINEERS REFERENCE HANDBOOK & TABLES, 20p. (Add 3p. for postage on each of above if bought separately.) INSULATED SCREW TERMINALS in range of seven colours, each 12p. Matching plugs: 2mm, each 5p; 4mm, each 7p. Plugs, sockets, hardware, Veroboard, edge connectors, switches, etc., in stock at keen prices.

SIEMENS TTL INTEGRATED CIRCUITS

Table listing Siemens TTL integrated circuits with columns: Part Number, Description, Price. Includes items like FLH101 (7400) Quad 2-input NAND, FLH201 (7401) Quad 2-input NAND, O/C collector, FLH191 (7402) Quad 2-input NOR, FLH291 (7403) Quad 2-input NAND, O/C collector, FLH211 (7404) Hex inverter, FLH271 (7405) Hex inverter, O/C collector, FLH161 (7408) Quad 4-input NAND, O/C collector, FLH391 (7409) Quad 2-input NAND, O/C collector, FLH111 (7410) Triple 3-input NAND, FLH351 (7413) Dual 4-input NAND Schmitt, FLH121 (7420) Dual 4-input NAND, FLH131 (7430) 8-input NAND, FLH141 (7440) Dual 4-input NAND power, FLH101 (7414) BCD-decimal decoder, nixie driver (16) £1.22, FLH281 (7442) BCD-decimal decoder (16) £1.16, FLH361 (7443) Excess 3-decimal decoder (16) £1.45, FLH371 (7444) Excess 3-Gray-decimal decoder (16) £1.45, FLH151 (7450) Expandable dual 2 wide 2-input (20p), FLH161 (7451) Dual 2 wide 2-input (20p), FLH171 (7453) Expandable 4 wide 2-input (20p), FLH181 (7454) 4 wide 2-input (20p), FLY101 (7466) Dual 4-input expander (20p), FLH101 (7470) JK flip flop (45p), FLH111 (7472) JK master slave flip flop (32p), FLH121 (7473) Dual JK master slave flip flop (45p), FLH141 (7474) Dual d-type edge triggered flip flop (45p), FLH151 (7475) Quad bi-stable latch (16) 45p, FLH131 (7476) Dual JK master slave flip flop (16) 45p, FLH221 (7480) Gated full adder (60p), FLH231 (7482) 2 bit binary full adder (87p), FLH241 (7483) 4 bit binary full adder (16) £1.32, FLH341 (7486) Half adder (33p), FLH161 (7490) Decade counter (80p), FLH221 (7491) (AN) 8 bit shift register £1.28, FLH171 (7492) Divide by 12 counter 85p, FLH181 (7493) 4 bit binary counter 80p, FLH231 (7494) 4 bit shift register, parallel I/P, series O/P (16) £1.13, FLH191 (7495) 4 bit left shift right shift register (87p), FLH261 (7496) 5 bit shift register (16) £1.48, FLH301 (74100) Dual quad bi-stable latch (24) £1.64, FLH281 (74104) JK master slave flip flop with JK input 43p, FLH271 (74107) Dual JK master slave flip flop 52p, FLK101 (74121) Monostable flip flop 48p, FLH201 (74190) Up down decade counter (16) £1.80, FLH211 (74191) Up down binary counter (16) £1.80, FLH241 (74192) Up down decade counter with clear (16) £1.74, FLH251 (74193) Up down binary counter with clear (16) £1.74. All packages 14 leads unless stated otherwise before prices.

SEMI-CONDUCTORS Brand new, guaranteed to spec. No seconds or surplus.

Large table listing semiconductor components with columns: Part Number, Description, Price. Includes diodes, transistors, and integrated circuits.

COMPONENT DISCOUNTS Not allowed on nett price items 10% on orders for components for £5 or more, 15% on orders for components for £15 or more. Prices subject to alteration without prior notice.


POSTAGE AND PACKING FREE on orders over £2. Please add 10p if under. Overseas orders welcome: carriage and insurance charged at cost. U.S.A. CUSTOMERS are recommended to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore PA 19081.

Laskys

TM.1 TEST METER 1000 ohms/volt. 1,000's IN USE
 Lasky's new look top value TM.1 is a really tiny pocket multimeter providing "big" meter accuracy and performance. Precision movement calibrated to +3% of full scale. Click stop range selection switch. Beautifully designed and made impact resistant black case with white and metallic red/green figuring. Ohms zero adjustment. Size only 2 1/4 x 3 1/4 x 1 1/4 in. ● DC/V: 0-10-50-250-1,000 at 1K/ohms/V. ● AC/V: 0-10-50-250-1,000 at 1K/ohms/V. ● DC Current: 0-1mA, 100mA, ● resistance: 0-150K ohms. ● Decibels: -10 +22dB. ● Complete with test leads.
LASKY'S PRICE £1.85 C & P 15p.




DIGITAL CLOCK COMPLETE WITH KNOBS
 This unique digital clock is available exclusively from Lasky's in chassis form for you to mount in any housing that you choose. All settings are achieved by two dual-concentric controls at the front including: On/off and auto alarm "sleep" switch. 10 minute division "click" set alarm (up to 12 hour delay), time adjustment. Ultra simple mechanism and high quality manufacture guarantee reliable operation and long life. The sleep switch will automatically turn off any appliance — radio, TV, light, etc., at any pre-set time up to 60 min and in conjunction with the Auto setting will switch on the appliance again next morning. The clock measures 4 1/2 in (W) x 1 1/2 in (H) x 3 1/4 in. (D) (overall from front of drum to back of switch). SPEC: 210/240 V AC. 50Hz operation; switch rating 250V 3A. Complete with instructions ● Auto sleep switch ● 12 hour alarm ● Mains operation ● Shock and vibration proof ● Made especially for Lasky's by famous maker ● Built-in alarm buzzer ● Hours, minutes, seconds read-off ● Forward and backward adjustment ● Silent synchronous motor.
SPECIAL QUOTES FOR QUANTITIES LASKY'S PRICE £6.50 C & P 25p.

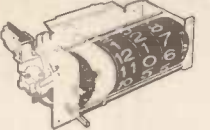


BSR TD8S 8 TRACK STEREO CARTRIDGE PLAYER
 An entirely new development from BSR — An 8 track stereo tape cartridge player for home use that everyone can afford. The TD8S will play all standard pre-recorded 8 track cartridges (there are thousands of top titles available) changing from track to track absolutely automatically and repeating continuously if required. Operation is simplicity itself — the unit is switched on and off by the insertion of the cartridge; the only external control being a channel selector with illuminated channel indicator. Adjustment is provided for tape head height. The TD8S is suitable for use with most modern stereo amplifiers and delivers a pre-amp output of 125mW. Power requirements: 210/250 V AC 50Hz. Frequency response: 50 Hz 10KHz, 4 pole dynamically balanced synchronous motor maintains unwavering speed accuracy — independent of mains fluctuations. Compact in size the TD8S is housed in black and woodgrain plastic cabinet. Size: 8 1/2 (W) x 3 1/4 (H) x 19 1/2 (D) in.
LIST PRICE £24.20 LASKY'S PRICE £19.95 C & P 35p.



BELTEK 8 TRACK CARTRIDGE PLAYER
 The Beltek C5700 8 track Stereo car player brings a new standard of design and performance to your motoring pleasure. A truly remarkable feature of this unit is its size — 4 1/2 (W) x 1 1/2 (H) x 8 1/4 in. (D) — only just bigger than the 8 track cartridge which it plays! The ultra compact dimensions of the C5700 are made possible by the use of 2 monolithic IC's in place of the usual circuit arrangement. Accepts all standard pre-recorded 8 track stereo cartridges and has unique "fine tune" control for adjustment of the tape head alignment which eliminates the chance of track overlap (cross talk). Other features include automatic head cleaner, channel select and channel repeat push buttons, slider type volume and tone controls, channel balance control. Tech spec: max output 10W (5 watts per channel) frequency response 50Hz 10KHz. Output imp. 4 ohms. Operates on 12V DC negative earth systems. Beautifully styled with black, ivory and chrome trim finish.
BELTEK C5700 complete with mounting brackets and 8 track pre-recorded demonstration cartridge. £23.50
BELTEK C5700 with pair SP24 speakers £29.00 C & P 25p each on C5700 and SP24 speakers.
 Beltek SP24 speakers are available perfectly matching the C5700 in performance and finish — specially designed for optimum performance in heavily damped car interior. Size: 7 1/4 in (W) x 6 in. (D) x 4 1/4 in. rear. 2 1/4 in. front (H) Comp. with connecting leads.

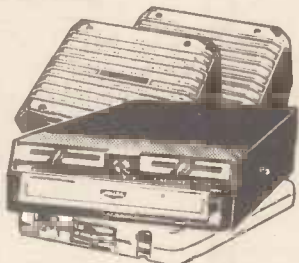

PYE SHORT WAVE CONVERTER
 High quality transistorised ultra compact Shortwave Converter for use with any suitable MW (AM) car radio. Suitable for use on 12V positive or negative earth systems. The Pye model 2649 is simply connected to the radio via a 1/2 in socket and provides shortwave coverage in 9 push-button selected band spread ranges (13, 16, 19, 25, 31, 41, 49, 60 and 90M) combined with the normal radio tuning to give full cover from 3.12MHz 21.75MHz. On/off switch and by-pass switch for normal MW radio use. Complete with mounting bracket fitting and alignment instructions. Black hammer crackle finished case. Size: 6 in. (W) x 1 1/4 in. (H) x 3 1/4 in. (D). (Can be used with any AM radio.)
LASKY'S PRICE £8.75 C & P 20p.

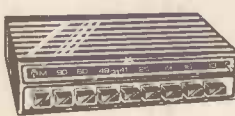

TAPE SCOOP
 EMI 2,400ft Professional Tape on 10 1/2 in metal NAB spools. Fully guaranteed brand new. Today's value over £5.00 each
£1.25 each 5 for £5.00 C & P 20p 5 for 50p

OUT NOW! 1972 AUDIO-TRONICS
NEW REVISED EDITION
 The great new 1972 revised edition of Lasky's famous Audio-Tronics catalogue is now available — FREE on request. The 44 newspaper size pages — many in full colour — are packed with 1,000's of items from the largest stocks in Great Britain of everything from the Radio and Hi-Fi enthusiast. Electronics hobbyist, Serviceman and Communications Ham. Over half the pages are devoted exclusively to every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals). Tape recording and Audio accessories. Don't miss LASKY'S AUDIO-TRONICS CREDIT CARD SCHEME offering holders one month's interest free credit up to £50. Send your name and address and 15p for post and inclusion on our regular mailing list.

207 EDGWARE ROAD, LONDON, W.2.
 33 TOTTENHAM CT. RD, LONDON, W1P 9RB.
 109 FLEET STREET, LONDON, E.C.4.
 152/3 FLEET STREET, LONDON, E.C.4.
HIGH FIDELITY AUDIO CENTRE
 42-45 TOTTENHAM CT. RD, LONDON, W1P 9RD.
MAIL ORDERS AND CORRESPONDENCE TO
 3-15 CAVELL STREET, LONDON, E1 2BN



Wilkinsons

EST. 1921



RELAYS P.O. TYPE 3000 AND 600
BUILT TO YOUR SPECIFICATION
 Contacts up to 8 changeover
 ★ DUST COVERS
 ★ QUICK DELIVERY
 ★ KEEN PRICES
 ★ QUOTATIONS BY RETURN HOME & OVERSEAS

NEW P.O. TYPE UNISELECTORS FROM STOCK, 50V. 11 LEVEL, 1 BRIDGING, 10 NON-BRIDGING, 3, 4 AND 5 LEVEL ALSO AVAILABLE

RELAYS, As used in automatic machines. Operating from 24v. D.C. with 4 Make and 4 Break heavy-duty contacts and dust cover. Small or large quantities supplied, packed in original case, 63p each. Lots of 200 50p each.
IMHOFF BLOWER UNITS in a standard 19 in. rack mounting assembly with Glass Fibre Air Filter and directional Duct. Capacitor Fan Motor 1/50th H.P. 200/250 Volts or 100/125 Volts 2,800 R.P.M. £17-50, carriage £1-50.
AXIAL fans as used in above units 6 in. blades reversible type size 7 in. by 7 in. with open flange each end £15 each carr. 75p, as above but with 1/15th H.P. motor also £15 each carr. 75p.
AXIAL fans 8 in. blades 1/10th H.P. 200/250 Volts 2,800 R.P.M. 8 1/2 in. long by 9 in. reversible type with open flange each end £16 each; carr. 75p.

MINIATURE DIGITAL INDICATOR, size of digits 1 in., illuminated by 28-volt lamps, reading 0 to 9 with left and right hand decimal points, quick disconnect at rear of unit for easy lamp replacement. When one of the twelve lamps is lighted, at the rear of the unit the lamp projects the corresponding digit on to the condensing lens through a projection lens on to the viewing screen at the front of the unit. £2-50 ea., send s.a.e. for illustration and full details.

PORTABLE VOLTMETERS 160 volts AC/DC moving iron 8 in. Mirror scale in polished wood case with hinged flap 9 1/2 in. by 8 1/2 in., only £5 each, post 75p. resistance supplied to extend range to 320 volts (scale reading x 2) 50p extra.
VOLTMETERS 2 in. flush round AC/DC with fixing clip 0-20 or 0-40 volts £2-50 each. 2 in. flush round 0-5 amp same price, post paid.

MINIATURE BUZZERS, 12 volts, with tone adjuster 40p each as illustrated.
LEDEX ROTARY SOLENOIDS AND CIRCUIT SELECTORS, size 5S 4 pole 1 1/2 way and off £8-50, 24 pole 1 1/2 way and off £13-50, 54 pole On/Off £10-50.
BRIDGE MEGGERS, SERIES 1, 1,000 volts, range 0/100 M ohms-infinity, with resistance Box 0/9999 ohms. Brand new, £65-00 ea.
VEEDER-ROOT COUNTERS with zero reset 800 counts per minute. 6 figures. 110 v. A.C. £5 ea.

HIGH SPEED COUNTERS
 3 1/2 in. x 1 in. 10 counts per second, with 4 figures. The following D.C. voltages are available, 6 v., 12 v., 24 v., 50 v., or 100 v. Also supplied with auxiliary contacts. normally open 40p extra.



L. WILKINSON (CROYDON) LTD.
 LONGLEY HOUSE LONGLEY RD. CROYDON SURREY
 Phone: 01-684 0236 Grams: WILCO CROYDON

VERY LIMITED QUANTITY FERROGRAPH (SERIES 5) STEREO TAPE RECORDERS

A few of these first class machines have been professionally adapted to make them into complete STEREO RECORDERS/REPRODUCERS.
 A lower track record/playback head has been fitted into the third head position on the standard WEARITE deck, in addition to the normal upper track head. A second identical electronic chassis and P.S.U. complete the modification.
 The specification is as for the original mono machine, plus stereo i.e. 3 1/2 and 7 1/2 i.p.s.: superimposition; variable erasure (fading in or out) on already recorded material; peak-reading meter for recording; separate bass, treble, gain controls aux. sockets on front panel and on P.S.U.; pause control; clock-type counter. STEREO: separate heads, electronics and P.S.U. provide — a higher than normal cross-talk ratio; completely independent recording and playback control of either channel (in addition each channel has its own mains switch); simultaneous recording/mixing of different sources on each channel etc.
 The unit, and an additional monitor panel, is mounted on a common frame and housed in a metal cabinet. The Complete frame may be removed as a whole (or dismantled into sub-sections) and installed or built-in to personal requirements. Price £99.00 plus carriage.

MI-19467-A MASTER OSCILLATORS

These R.C.A. units which are used in the ET 4336 transmitter and which were supplied as a separate item, each in its own slide-in metal case, are ideal as the heart of any high-power transmitter, unmodified as a low-power (approx. 20w) transmitter, or as a basis for modification to suit individual requirements. They incorporate a 6-position oscillator switch (covering 1 to 5 MHz); a 3-position Multiplier switch (covering 2 to 10 MHz); a D.C. current meter, and oscillator and multiplier coils with "turns counting" mechanisms for precise tuning. Power requirements are H.T. and L.T. for the 807 valve plug in the unit, and are brought in by an 8-pin Jones plug on the rear of the chassis. The basic frequency coverage of the oscillator is 1 to 10 MHz, which can be extended to 20 MHz when used as the oscillator section of a higher power transmitter or when used on its own. All these and many more details are covered in full in the extremely comprehensive instruction/service manual (supplied with each unit) containing wiring and circuit diagrams, adjustments, photographs, etc. BRAND NEW. Price per unit is £8.50 including 2 807 valves. Carriage 75p.



COLOMOR ELECTRONICS LTD.
 170 GOLDHAWK ROAD,
 LONDON, W.12. 01-743 0899 01-748 8006

SERVICE TRADING CO

Postage and Carriage shown below are inland only. For Overseas please ask for quotation. We do not issue a catalogue or list.

MATSUNAGA VARIABLE VOLTAGE TRANSFORMERS

INPUT 230 v. A.C. 50/60
OUTPUT VARIABLE 0/260 v. A.C.

Carriage Paid
BRAND NEW. All types.

0-260 v. at 1 amp	£7-00
0-260 v. at 2-5 amps	£8-05
0-260 v. at 5 amps	£11-75
0-260 v. at 10 amps	£22-50
0-260 v. at 15 amps	£25-00
0-260 v. at 20 amps	£49-00
0-260 v. at 25 amps	£58-00
0-260 v. at 37-5 amps	£82-00
0-260 v. at 50 amps	£98-00

Special discount for quantity
OPEN TYPE (Panel Mounting)

1 amp	£4-75
1 amp	£7-00
2 1/2 amp	£8-05

L.T. TRANSFORMERS

All primaries 220-240 volts.

Type No.	Sec. Taps	Price	Carr.
1 30, 32, 34, 36 v. at 5 amps		£4-68	30p
2 30, 40, 50 v. at 5 amps		£6-88	33p
3 10, 17, 18 v. at 10 amps		£4-95	22p
4 6, 12 v. at 20 amps		£6-43	33p
5 17, 18, 20 v. at 20 amps		£7-28	33p
6 6, 12, 20 v. at 20 amps		£6-88	38p
7 24 v. at 10 amps		£5-23	28p
8 4, 6, 24, 32 v. at 12 amps		£7-15	33p
9 6 and 12 v. at 10 amps		£3-75	35p

RING TRANSFORMERS

Functional Versatile Educational

These multi-purpose Auto Transformers, with large centre aperture, can be used as a Double wound current Transformer, Auto Transformer, H.T. or L.T. Transformer, by simply hand winding the required number of turns through the centre opening. E.g. Using the RT.100VA Model the output could be wound to give 5V @ 12Amps, 4V @ 25Amps, or 2V @ 50Amps, etc.

Prices: RT.100VA 3.18 turns per volt, £2-25 + 17p p. and p.
RT.300VA 2.27 turns per volt, £4-20 + 28p p. and p.
RT.1KVA 1.82 turns per volt, £6-50 + 33p p. and p.
RT.2KVA 1.5 turns per volt, £10-50 + 48p p. and p.
RT.3KVA 1.5 turns per volt, £14-00 + 50p p. and p.

DOUBLE WOUND VARIABLE TRANSFORMERS

Fully isolated, low tension Secondary winding. Input 230 v. A.C. Output continuously VARIABLE 0-36 v. A.C. 0-36 v. @ 5 amp, £10-59 P. & P. 43p.
0-36 v. @ 20 amp, £23-10 P. & P. 75p.
Ideally suited for Educational, Industrial and Laboratory use.

36 volt 30 amp. A.C. or D.C. Variable L.T. Supply Unit

Input 220/240 v. A.C. Output Continuously variable 0-36 v. A.C./D.C. Fully isolated. Fitted in robust metal case with Voltmeter, Ammeter, Panel Indicator and chrome handles. Input and Ideally suited for Lab. or Industrial use. £68 plus £2 p. & c.

230 VOLT AC SOLENOID

EXTREMELY POWERFUL SOLENOID with approximately 14lb. pull, lynch travel. Fitted with mounting feet. Size 4 inches long, 2 1/2 inches wide and 3 inches high. Price £2-00 including post & pkg.

230-250 VOLT A.C. SOLENOID

(Similar in appearance to above illustration.) Approx. 1 1/2 lb. pull. Size of feet 1 1/2 x 1 1/2. Price 85p incl. post. Manufactured by Westool Ltd.

18-24 VOLT D.C. SOLENOID

Size: O.A.L. 3 1/2 in. x 1 1/2 in. x 1 in. Maximum push 1 at approx. 1 lb. PRICE: 75p incl. P. & P.

50 in. 1 ELECTRONIC PROJECT KIT

50 easy to build Projects. No soldering, no special tools required. The Kit includes Speaker, meter, Relay, Transformer, plus a host of other components and a 56-page instruction leaflet. Some examples of the 50 possible Projects are: Sound level Meter, 2 Transistor Radio, Amplifier etc., etc. Price £7-75. P. & P. 30p.

MICRO SWITCH

5 amp. c/o contacts. Fitted with removable push button assembly. Ex. P.O. 20 for £1-00 incl. post (min. order 20).

'HONEYWELL' LEVER OPERATED MICRO SWITCH

15 amps 250 volt A.C. c/o contacts. NEW in maker's carton. Price 10 for £1-90 incl. P. & P.

'HONEYWELL' PUSH BUTTON, PANEL MOUNTING MICRO SWITCH ASSEMBLY

Each bank comprises of a change-over, rated at 10 amps 240 volt A.C. Black knob 1 in. dia. Fixing hole 8 in. Prices: 1-bank 30p, 2-bank 40p, 3-bank 55p. (Illustrated). Inc. P. & P.

POWER RHEOSTATS

(NEW) Ceramic construction, winding embedded in Vitreous Enamel, heavy duty brush assembly designed for continuous duty. AVAILABLE FROM STOCK IN THE FOLLOWING VALUES:

100 WATT 1 ohm 10a., 5 ohm 4.7a., 10 ohm 3a., 25 ohm 2a., 50 ohm 1.4a., 100 ohm 1a., 250 ohm .7a., 500 ohm .45a., 1k ohm 280mA., 1.5k ohm 230mA., 2.5k ohm .2a., 5k ohm 140mA., Diameter 3 1/2 in. Shaft length 3 in. dia. 3/8 in. £1-50. P. & P. 15p.
50 WATT 1-12/10/25/50/100/250/500/1K/1.5K/2.5K/5K ohm. All at £1-12. P. & P. 11p.
25 WATT 10/25/50/100/250/500/1K/1.5K/2.5K/3-5K ohm. All at 78p. P. & P. 5p.

Black Silver Skirted knob calibrated in Nos. 1-9. 1 1/2 in. dia brass bush. Ideal for above Rheostats, 18p ea.

PROGRAMME TIMERS

(Mfg. by 'Magnetic Devices Ltd')
240v. A.C. 5 r.p.m. 'Crouzet' motor. Drives 15 cams, each operating a 10 amp c/o micro switch. Cams are individually variable, allowing innumerable combinations. Ideally suited for machinery control, automation etc. Also in the field of entertainment, for chaser lights, animated displays etc. NEW £5-75. P. & P. 25p.

STROBE! STROBE! STROBE!

FOUR EASY TO BUILD KITS USING XENON WHITE LIGHT FLASH TUBES. SOLID STATE TIMING + TRIGGERING CIRCUITS. PROVISION FOR EXTERNAL TRIGGERING. 230-250v. A.C. OPERATION.

EXPERIMENTERS 'ECONOMY' KIT
Adjustable 1 to 36 Flash per sec. All electronic components including Veroboard S.C.R. Unijunction Xenon Tube-instructions £6-30 plus 25p P. & P.

NEW INDUSTRIAL KIT
Ideally suitable for schools, laboratories etc. Roller tin printed circuit. New trigger coil, plastic thyristor Adjustable 1-80 f.p.s. Price £10-50. 50p P. & P.

HY-LIGHT STROBE
This strobe has been designed for use in large rooms, halls and the photographic field, and utilizes a silica tube for longer life expectancy, printed circuit for easy assembly, also a special trigger coil and output capacitor. Speed adjustable 1-30 f.p.s. Light output approx. 4 ioules. Price £12-00. P. & P. 50p.

SPECIALLY DESIGNED FULLY VENTILATED METAL CASE incl. reflector, £4-00. P. & P. 45p. Post paid with kit.

'SUPER' HY-LIGHT KIT
Approx. 4 times the light output of our well-proven Hy-Light strobe.
Incorporating Heavy duty power supply.
Variable speed from 1-23 flash per sec.
Reactor control circuit producing an intense white light.
Never before a Strobe Kit with so HIGH an output at so LOW a price. ONLY £20-00 plus 75p P. & P.

ATTRACTIVE, ROBUST, FULLY VENTILATED METAL CASE specially designed for the Super Hy-Light Kit including reflector, £7-00. P. & P. 45p.

7-INCH POLISHED REFLECTOR. Ideally suited for above Strobe Kits. Price 53p and 13p P. & P. or post paid with kits.

CONSTANT SPEED, PRECISION MADE 6 VOLT D.C. GOVERNED MOTOR

Seven pole armature, ballrace bearing. 2.750 r.p.m. Length 2 11/16. Dia. 13/16. Shaft length 5/16. Shaft dia. 5/64. No load 40 ma. Normal load 35 ma. Ideal for portable recorders etc., etc. Price £1-25, p. & p. 10p.

240 V A.C. SOLENOID OPERATED FLUID VALVE

Will handle liquids or gases up to 7 p.s.i. Forged brass body, stainless steel core and spring. 1/2 in. b.s.p. inlet/outlet. Precision made, British mfg. PRICE: £1-75 P. & P. 20p. Special quotation for quantity. NEW in original packing.

D.C. AMMETERS

Available in 1 amp., 5 amp., 15 amp., 20 amp. Size 2 1/2 in. dia. 1 1/2 in. deep. £1-75 incl. P. & P. 0-300 volts A.C. £1-90 incl. P. & P.

MOTOROLA MAC11/6 PLASTIC TRIAC 400 PIV 10 AMP

Now available EX STOCK supplied complete with full data and applications sheet. Price £1-05 plus 7p P.&P. Suitable Diac 30p (RCA40583).

SIX FIGURE RESETABLE COUNTER

48 Volt D.C. operation. Packed in maker's carton. Price: £3-50 P. & P. 20p.

INSULATED TERMINALS

Available in black, red, white, yellow, blue and green. New 10p each. Post paid 'Minimum order 6.

G.E.C. 12-WAY 15 AMP CONNECTORS

NEW in maker's carton
BAKELITE £1-25 per doz.
FLEXIBLE £1-50 per doz. Post paid. (Minimum 1 doz.)

HIGH FREQUENCY TRANSISTORISED MORSE OSCILLATOR

Adjustable tone control. Fitted with moving coil speaker, also earpiece for personal monitoring. Complete with morse key. £2-25 plus 18p p. & p.

RELAYS NEW SIEMENS PLESSEY, etc. MINIATURE RELAYS AT COMPETITIVE PRICES.

1	2	3	4	1	2	3	4
45 6-9 2HD M	50p	700 15-35	2 c/o HD	73p*			
185 12-18 4 c/o	73p*	700 16-24	6 M	63p*			
280 9-12 2 c/o	73p*	1250 24-36	4 c/o	63p*			
700 16-24 4 M2B	63p*	2500 36-45	6 M	63p*			
700 16-24 4 c/o	78p*	2400 30-48	4 c/o	50p*			
700 12-24 2 c/o	63p*	9000 40-70	2 c/o	50p*			
40 10-18 4 c/o	73p*	15k 85-110	6 M	50p*			

12 VOLT D.C. RELAY

140 ohm coil, three sets c/o contacts rated at 5 amps. 78p incl. P. & P. (Similar to illustration below.)

'DIAMOND H' 230 VOLT A.C. RELAYS (Unused)

Three sets c/o contacts rated at 5 amps. Price 30p. P. & P. 10p. (100 lots £40-00 incl. P. & P.)

'KEYSWITCH' 230 VOLT A.C. RELAYS

One set c/o contacts rated at 7.5 amps. Boxed. Price 40p. P. & P. 5p. (100 lots £32-00 incl. P. & P.)

MINIATURE RELAYS

9-12 volt D.C. operation. 2 c/o 500 M.A. contacts. Size only 1 in. x 1/2 x 1/2 in. Price 58p post paid. 30-36 v. D.C. operation. 2 c/o 500 M.A. contacts. 3,200 ohm coil. Size only 1 x 1/2 x 1/2 in. 43p post paid.

LIGHT SOURCE AND PHOTO CELL MOUNTING

Precision engineered light source with adjustable lens assembly and ventilated lamp housing to take MBC bulb. Separate photo cell mounting assembly for ORP.12 or similar cell with optic window. Both units are single hole fixing. Price per pair £2-75 p. & p 18p.

200-250 v. A.C. NEON INDICATOR

Available in RED or AMBER at 20p each, or in GREEN at 32p. Min. order 3 units. P. & P. 5p.

VENNER ELECTRIC TIME SWITCH

200/250 volt. Ex-GPO. Tested, perfect condition. Two ON, two OFF, every 24 hrs. at any manually pre-set time. Price: 10 amp, £2-75. 15 amp, £3-25. 20 amp, £3-75. P. & P. 20p. Also available with Solar Dial ON at dusk, OFF at dawn, Prices as above.

UNISELECTOR SWITCHES—NEW

4 BANK 25 WAY FULL WIPER
25 ohm coil, 24 v. D.C. operation £5-88, plus 22p P. & P.
6 BANK 25 WAY FULL WIPER
25 ohm coil, 24 v. D.C. operation. £6-50, plus 22p P. & P.
8 BANK 25 WAY FULL WIPER
24 v. D.C. operation. £7-63, plus 22p P. & P.

230V/240V COMPACT SYNCHRONOUS GEARED MOTORS

Manufactured by either Sangamo, Haydon or Smith. Built-in gearbox.

1 RPM cw	1 RPH A/cw	10 RPH A/cw
2 RPM cw	2 RPH A/cw	15 RPH A/cw
60 RPM cw	3 RPH A/cw	20 RPH cw
	6 RPH cw	30 RPH cw

cw = Clockwise, A/cw = Anti-clockwise rotation.

Fraction of makers' price. All at 75p incl. P. & P.

12 VOLT DC MOTOR

Powerful 12 volt 1 amp REVERSIBLE motor. Speed 3,750 rpm. Complete with external gear train (removable) giving approx. final speed of either 240 r.p.m. or 125 r.p.m. Size 4 1/2 in. x 2 1/2 in. dia. Price inc. post either type 95p.

BODINE TYPE N.C.I. GEARED MOTOR

(Type 1) 71 r.p.m. torque 10 lb. in. Reversible 1/70th h.p. cycle .38 amp. (Type 2) 28 r.p.m. torque 20 lb. in. Reversible 1/80th h.p. 50 cycle .28 amp. The above two complete U.S.A. motors are offered in 'as new' condition. Input voltage of motor 115v A.C. Supplied complete with transformer for 230/240v A.C. input. Price, either type £3-15 plus 35p P. & P. or less transformer £2-13 plus 27p P. & P. These motors are ideal for rotating aeriels, drawing curtains, display stands, vending machines, etc. etc.

ALL MAIL ORDERS, ALSO CALLERS AT:
57 BRIDGMAN ROAD,
LONDON, W4 5BB. Phone: 01-995 1560
Closed Saturdays.

SERVICE TRADING CO.

SHOWROOMS NOW OPEN
AMPLE PARKING

PERSONAL CALLERS ONLY
9 LITTLE NEWPORT STREET,
LONDON, WC2H 7JJ.
Tel.: 01-437 0576

THE BEST BUY IN FREQUENCY COUNTERS

THE YAESU YC-305 £97.50!

- Free delivery by Securair in 24 hours normally
- * Counts to 30 MHz
- * Operates on AC or 12 VDC
- * Read-out to 1 Hz
- * 8 digit capability
- * Superbly engineered



SPECIFICATION
 Frequency Range: 5 Hz to 30 MHz
 Accuracy: ± time base stability +1 count
 Gate Times: 1 milli-second or 1 second
 Frequency Unit: MHz and KHz
 Input Impedance: high 1M ohms, low 56 ohms
 Input Capacity: less than 20 pF
 Maximum Input: 60V p-p less than 10 sec. 20V p-p continuous
 Time Base Frequency: 1,000 KHz crystal controlled
 Stability: 0.0005% at 25°C
 Power Requirement: 100/110/117/200/234V AC 18VA or 12-14.5 VDC 1A
 Dimensions: 8-3/4W x 3-1/4 x 10-1/2 inches
 Weight: approx. 8 lb.
 Tube and Semiconductors: integrated circuit 25; silicon transistor 8; FET 1; silicon diode 11; display tube 5
 We are Yaesu Musen Co. DISTRIBUTORS in the U.K. All equipment carries a one year Manufacturer's Guarantee for which we carry full spares and service facilities.

* Your 'ONE-STOP' single source of all YAESU equipment plus MASTS, TOWERS, ROTATORS, ANTENNAS.
WESTERN ELECTRONICS (U.K.) LIMITED
 OSBORNE ROAD, TOTTON, SOUTHAMPTON, SO4 4DQ
 Tel: TOTTON 4930 or 2785 Cables: AERIAL, SOUTHAMPTON

WW—094 FOR FURTHER DETAILS

RADIO MAST & ANTENNAS

DIPOLE JUNCTION UNITS



MANUFACTURERS OF:

- Aerial Systems for M.F. & H.F. range including: Centre Fed Half Wave Dipoles.
- Delta Matched Dipoles.
- Folded Dipoles.
- Broad Bank Cage Monopoles.
- Rhombic Systems.
- Quadrant Dipoles.
- Inverted "V" Arrays.
- Terminated Folded Dipoles.
- M.F. "T" & "L" Aerials.
- Vertical Radiators.
- Radio Masts:
- Portable Tubular.
- Permanent Tubular.
- Permanent Lattice.
- Dipole Centre Connectors.
- Transmission Line Equipment.
- Lead-in-Insulator Panels.
- Coaxial and Wire Feeder.
- Routes.

Shown CCJ/2
 Lightweight 4 oz.
 Mobile or Portable
 NATO Coded
£2.95

Type CCJ/1
 Heavy duty. Weight 12 oz. Up to 2 KW
 For permanent installations flexible end connections **£4.90**

Both the above units supplied with all necessary fittings including 1/p plugs. They can also be used as junction for long wire aërials to coaxial cable for feed into buildings.

SUPPLIERS TO:

Government Ministries, Crown Agents, principal manufacturer's of Telecommunications equipment and overseas governments and administrations.

INSULATORS:

We maintain large stocks of antenna strain, mast stay, egg, and line insulators. Only 20,000 in stock. Commercial and Export enquiries. Please send for preferred stock list. Many others available in small quantities.

SOUTH MIDLANDS CONSTRUCTION LIMITED
 S.M. House, Osborne Road, Totton, Hants. England
 Telephone: Totton 2785/4930 Cables: Aerial, Southampton

WW—095 FOR FURTHER DETAILS

EX COMPUTER PRINTED CIRCUIT PANELS 2" x 4" packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price, 10 boards, 50p. P. & P. 7p. With a guaranteed minimum of 35 transistors. Transistor Data included.

SPECIAL BARGAIN PACK. 25 boards for £1. P. & P. 18p. With a guaranteed minimum of 85 transistors. Transistor Data included.

PANELS with 2 power transistors sim. to OC28 on each board plus components. 2 boards (4 x OC28) 50p. P. & P. 5p.

9 OA5, 3 OA10, 3 Pot Cores, 26 Resistors, 14 Capacitors, 3 GET872, 3 GET872B, 1 GET875. All long leaded on panels 13" x 4". 4 for £1. P. & P. 25p.

12V 4A POWER SUPPLY

Extremely well made by FRAKO GmbH in W. Germany, with constant voltage mains transformer, tapped input from 115V to 240V. Full wave rectification and capacitor smoothing. Size 9" x 6" x 5", weight 11 lb. These units are brand new, unused and fully guaranteed. Maker's price believed to be around £80. Our Price £9.50. Carr. 50p

250 MIXED RESISTORS
 1/4 and 1/2 Watt 62p

DIODES 1 AMP 1,000 PIV
 4 for 50p P. & P. 5p
 709C Operational Amplifier
 TOS 8 lead I.C.
 1 off 50p; 50 off 35p;
 100 off 20p; 250 off 15p

QUARTZ HALOGEN BULBS
 12V 55W for car spotlights and projectors etc. 50p

RELAY OFFER
 Single Pole Changeover Silver Contacts
 2" x 7" x 6". 2.5KΩ Coil operates on 25 to 50V. 8 for 50p. P. & P. 8p.

BUMPER BARGAIN PARCEL

We guarantee that this parcel contains at least 1,750 components. Short-leaded on panels, including a minimum of 350 transistors (mainly NPN and PNP germanium, audio and switching types—data supplied). The rest of the parcel is made up with: Resistors 5% or better (including some 1%) mainly metal oxide, carbon film, and composition types. Mainly 1/4 and 1/2 watt. . . diodes, miniature silicon types OA90, OA91, OA95, IS130, etc. . . capacitors including tantalum, electrolytics, ceramics and polyester. . . inductors, a selection of values. . . also the odd transformer, trimpot, etc., etc. . . These are all miniature, up to date, professional, top quality components. Don't miss this, one of our best offers yet! Price £3.25. P. & P. 33p—U.K. New Zealand £1 P. & P.

EX-COMPUTER POWER SUPPLIES

Reconditioned, fully tested and guaranteed. These very compact units are fully smoothed with a ripple better than 10mv. and regulation better than 1%. Over voltage protection on all except 24v. units. 120v-130v. a.c. 50c/s input. Mains transformer to suit £3 extra if required.

We offer the following types:

6v. 8a. £10	20v. 15a. £15
6v. 15a. £14	30v. 7a. £12
12v. 20a. £16	24v. 4a. £14

Carrage 75p per unit.

150 High Stabs 1/4, 1/2 and 1 Watt, 5% and Better 62p

LARGE CAPACITY ELECTROLYTICS
 41" x 2" dia. 18,800 mfd 30V 40p each
 16,000 mfd 12V P. & P. 6p each
 25,000 mfd 25V
 41" x 3" dia. 8,000 mfd 55V 50p each P. & P. 12p each

EXTENSION TELEPHONES
 99p ea. P. & P. 25p
£1.75 for 2 P. & P. 50p
 These phones are extensions and do not contain bells.



STANLEY QUALITY KITS

Here at last are some truly superbly designed Hi Fi kits. Out kits are already causing enormous interest. A well-designed kit is one that is sought after, and a well presented kit (with no missing parts) is easy to construct.

30 Watt R.M.S. Hi-Fi Transistor Power Amplifier Kit.
 Specification: 30 watts R.M.S. into 8 ohms.
 Frequency Response: —3dB at 16Hz-62,000 Hz.
 Total Harmonic Distortion: Less than 0.22% for any power up to 30 watts.
 Total Harmonic Distortion at 1kHz at 20 watts into 8 ohms is less than 0.03%.
 Kit comprises: P.C. board, low noise 5% carbon film resistors, good quality electrolytic and polystyrene capacitors, 8 top quality transistors, large heat sink, etc. etc.
 Price of Module Kit, £8.00 p.p. 20p; 2 for £16.00 post free.
 Built and Tested, £9.00 p.p. 20p; 2 for £18.00 post free.

HI-FI STEREO PRE-AMPLIFIER KIT
 This first-class kit has inputs for magnetic or ceramic cartridges, tape, radio, auxiliary 1, auxiliary 2.
 Brief Specification: Tone Controls: ± 10dB at 100 Hz; ± 10dB at 10kHz.
 Filters: Low pass turnover at 5kHz, 10kHz, 20kHz and 40kHz.
 Overload Factor: 34 dB all inputs.
 Total Harmonic Distortion: 0.03% at normal output; 0.3% at 20 dB overload.
 Price £24.00 post free.

NEW RELEASE—60 WATT TRANSISTOR POWER AMPLIFIER KIT
 Specification: 60 watts R.M.S. into 8 ohms.
 Frequency Response: 10 Hz-30,000 Hz.
 Total Harmonic Distortion at Full output into 8 ohms is less than 0.15%.
 Input 1V into 10K for 60 Watts.
 This kit has short circuit proof protection. Price £11.50 p.p. 20p.
 Details of power supplies and pre-amps available, please state your exact requirements.


MAIL ORDER ONLY
STANLEY ELECTRONICS
 SUITE ONE, 8 FOSTER LANE, LONDON E.C.2. Tel.: 01-606-0352

Transistor TELEPHONE AMPLIFIER



Increase efficiency of Office, Shop and Workshop with this **DELUXE TELEPHONE AMPLIFIER** which enables you to take down long telephone messages or converse without holding the handset. Just moisten the suction pad and stick it to one side of the telephone. A useful office aid. On/Off switch. Volume control. Operates on one 9v battery. Size 3in. x 4 in. Ready to operate. Add 14p extra for battery. P & P 22p.

4-STATION INTERCOM

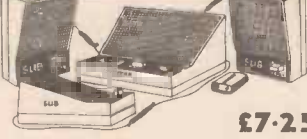

This NEW, versatile De Luxe 4-Station Transistorised Intercom (1 Master and 3 Subs) for desk or wall mounting can solve your communication problems instantly. Effective range 300ft. Call/talk/listen from Master to Subs and Subs to Master. With Selector switch. Ideally suitable for office, shop, home or surgery. Adaptable for Mains. Complete with three 66ft. connecting wires and accessories. On/Off switch, volume control. P. & P. 40p.

WEST LONDON DIRECT SUPPLIES
 169 KENSINGTON HIGH STREET, LONDON W8 6SN

KEYTRONICS MAILING ADDRESS
 44 EARLS COURT ROAD, LONDON W.8
 WAREHOUSE AND DISPATCH
 01-478 8499

THE SOUND

OF QUALITY



A COMPLETELY NEW DESIGN FURTHER IMPROVED IN APPEARANCE AND IN PERFORMANCE

SUPER 30 Mk III

Only high grade components by leading manufacturers.

COMPLETE KIT OF PARTS Carr. 65p

Or FACTORY BUILT with 12 months guarantee. Dep. £5-75 and 9 mthly payments £3-50 (Total £37-25)

Or FACTORY BUILT in cabinet as illustrated. Dep. £7 and 9 monthly payments £3-99 (Total £42.91).

PRINTED CIRCUITRY, TWENTY SILICON TRANSISTORS, FOUR DIODES, FOUR RECTIFIERS.

TECHNICAL DETAILS (applying to each channel where appropriate).

CONTROLS: PUSH-BUTTON SELECTOR (1) Disc (2) Radio (3) Tape (4) Mono L (5) Mono R (6) SPEAKER DIS. (7) Mains on/off. Bass, Treble, and Balance Plus Ceramic Mag. P.U. Switch.

£25

£33-75

£38-75



SEND S.A.E. FOR FREE COLOUR BROCHURE OF MONEY SAVING FULL SYSTEM PACKAGE OFFERS

REPRESENTING VALUE FAR HIGHER THAN THE PRICES SUGGEST!

HIGH FIDELITY STEREO AMPLIFIER

- ★ SATIN SILVER METAL FACIA with black lettering. Black edged knobs with bright silver finish centres.
- ★ PUSH-BUTTON SELECTOR SWITCHING
- ★ NEON INDICATOR
- ★ JACK SOCKET FOR HEADPHONES
- ★ CABINETED MODEL VENEERED IN SATIN TEAK. SUITABLE FOR ANY MODERN PICK-UP CARTRIDGE CERAMIC or MAGNETIC, REGARDLESS OF PRICE. WE RECOMMEND USE WITH THE BEST ANCILLARY EQUIPMENT THAT CAN BE AFFORDED.

OUTPUT: 15 watts R.M.S. (Continuous) into 8 ohms.
10 watts R.M.S. (Continuous) into 15 ohms.
HUM & NOISE -75dB Min. Vol. -55dB Full Vol.
HARMONIC DISTORTION 0.1% at 1000 Hz 10 Watts
FREQUENCY RESPONSE: -3dB 7Hz to 70KHz
TREBLE CONTROL: +16dB to -12dB at 14KHz.
BASS CONTROL: +17dB to -16dB at 40Hz
SENSITIVITIES: Disc Mag. 2.5mV. Ceramic 35mV. Radio 120mV. Tape 120mV.
REAR PANEL SOCKETS ARE FOR 3 PAIRS OF INPUTS (1) P.U. (2) Radio (3) Tape Amp. Plus pair for tape recorder signal take off and 2 pairs for speaker connections.



R.S.C. TA12 Mk III 6.5 + 6.5 WATT STEREO AMPLIFIER

FULLY TRANSISTORISED, SOLID STATE CONSTRUCTION HIGH FIDELITY OUTPUT OF 6.5 WATTS PER CHANNEL

Designed for optimum performance with any crystal or ceramic Gram. P.U. cartridge, Radio tuner, Tape recorder, etc. ★ 3

separate switched input sockets on each channel ★ Separate Bass and Treble controls ★ Slide Switch for mono use ★ Speaker Output 3-15 ohms ★ For 200-250v. A.C. mains ★ Frequency Response 20-20,000 c.p.s. -2dB ★ Harmonic Distortion 0.3% at 1,000 c.p.s. Hum and Noise -70dB ★ Sensitivities: (1) 50mV; (2) 400mV; (3) 100mV. Output rating I.H.F.M. ★ Handsome finish Fascia plate and Knobs.

COMPLETE KIT OF PARTS WITH FULL WIRING DIAGRAMS & INSTRUCTIONS £15-50 Carr. 40p S.A.E. for Leaflet
FACTORY BUILT WITH 12 MTHS GUARANTEE £19.50 Dep. £3 & 9 monthly pymts VENEERED £23 IN TEAK Dep: £3 & 9 monthly pymts HOUSING £2-55 (Total £22-35) HOUSING £2-55 (Total £25-95)

THE YORK HIGH FIDELITY 3'SPEAKER SYSTEM

Performance comparable with units costing considerably more. KIT COMPLETE Moderate size (approx. 25 x 14 x 10in.). Range 30-20,000 c.p.s. Impedance 15 ohms. Consists of (1) 12in. 15 watt Bass unit with cast chassis. Roll rubber cone surround for ultra low resonance, and ceramic magnet. (2) 3-way quarter section series cross-over system. (3) 8 x 5in. high flux middle range speaker. (4) High efficiency tweeter. (5) Appropriate quantity acoustic damping material. (6) Peak veneered cabinet. (7) Circuit and full instructions. REMARKABLE VALUE HEAR IT AT ANY BRANCH



R.S.C. A10 30 WATT ULTRA LINEAR HI-FI AMPLIFIER

Highly sensitive. Push-Pull high output, with Pre-amp/Tone Control Stages. Hum level -70dB. Frequency response ±3dB 30-20,000 c.p.s. All high grade components and Valves 2E86, 2E80, 6CX83, 807, 807, GZ34. Separate Bass and Treble Controls. Sensitivity 30 millivolts. Suitable for High Impedance mic. or pick-ups. Designed for Clubs, Schools, Theatres, Dance Halls or Outdoor Functions, etc. For use with Electronic Organ, Guitar, String Bass, etc. Gram, Radio or Tape. Reserve L.T. and H.T. for Radio Tuner. Two inputs with associated volume controls so that two separate inputs such as Gram and "Mixer" can be mixed 200-250 v. A.C. For 8 & 16 Ω speakers. COMPLETE KIT PARTS, WIRING DIAGRAMS, INSTRUCTIONS. £15-75 Twin-handled perforated cover £1-90. Or factory built with EL34 output valves and 12 months' guarantee for £19-75. Tech. sigs. apply to factory built units. Carr. 65p. TERMS: Deposit £4 and 9 monthly payments of £2-10 (Total £22-90). Send S.A.E. for leaflet.



FANE LOUDSPEAKERS 'POP' 25/2

Dual cone 15 Ω (for uses other than Bass Guitar or Electronic Organ). 12in. 25 watt CARR. PAID £6-75 Terms: DEPOSIT £1 and 9 monthly payments 75p (Total £7-75).

HI-FI LOUDSPEAKER ENCLOSURES

Teak or Afrormosia veneer finish. Modern design. Acoustically lined. All sizes approx. Carr. 30p extra. JES Size 16x11x9in. Pressurised. Gives pleasing results with any 8in. HI-FI speaker. £5-35 SES For optimum performance with any 8in. HI-FI speaker. 22x15x9in. Ported SE10 For outstanding results with HI-FI 10in. speaker. 24x15x10in. Ported. £6-47 SE12 For high performance with 12in. HI-FI speaker and Tweeter. Size 25x16x10in. Pressurised. £7-87

FANE 807 HIGH FIDELITY LOUDSPEAKER

A full range 8in. 10 watt unit for excellent sound quality in suitable enclosure. Roll P.V.C. cone surround and long throw voice coil to achieve very low fundamental resonance at 30 c.p.s. Tweeter cone is fitted to extend high note response. Frequency range 25 Hz to 15 KHz. Impedance 3 Ω or 8-15 Ω. State requirements. Cast Chassis. £3-85 REMARKABLE VALUE AT ONLY

FANE ULTRA HIGH POWER LOUDSPEAKERS

All power ratings are R.M.S. continuous. 2 years' guarantee. High flux ceramic magnets. ALL CARRIAGE FREE.

18" 'POP' 100 RATING 100 WATTS 14,000 GAUSS 8/15 OHMS

Dep: £6 and 9 monthly payments £22-95 £2-20 (Total £25-80)

15" 'POP' 60 RATING 60 WATTS 14,000 GAUSS 8/15 OHMS

Dep: £3-30 and 9 monthly payments £11-30 (Total £15). FOR BASS GUITAR OR ELECTRONIC ORGAN, ETC.

12" 'POP' 50 RATING 50 WATTS 13,000 GAUSS 15 OHMS

Dep: £2 and 9 monthly payments £1-20 (Total £12-80). PAIR SUITABLE ALL PURPOSES.



R.S.C. MAINS TRANSFORMERS

FULLY GUARANTEED. Interleaved and Impregnated where necessary. Primaries 200-250v. 50c/s. Screened.
MIDGET CLAMPED TYPE 2 1/2 x 2 1/2 in.
250v., 60mA, 6.3v. 2a. £1-05
250-250v., 60mA, 6.3v. 2a. £1-05
FULLY SHROUDED UPRIGHT MOUNTING
250-250v., 60mA, 6.3v. 2a., 0-5-6.3v. 2a. £1-40
250-250v., 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-20
300-300v., 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-20
300-300v., 130mA, 6.3v. 4a., c.t., 6.3v. 1a. £2-20
For Mullard 510 Amplifier. £2-65
350-350v., 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-60
350-350v., 150mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-65
425-425v., 200mA, 6.3v. 4a., c.t., 5v. 3a. £2-95
425-425v., 200mA, 6.3v. 4a., 0-5-6.3v. 3a. £5-10
450-450v., 250mA, 6.3v. 4a., c.t., 5v. 3a. £2-50
TOP SHROUDED DROP-THROUGH TYPE
250-250v., 70mA, 6.3v. 2a., 0-5-6.3v. 2a. £1-35
250-250v., 100mA, 6.3v. 3.5a. £1-55
250-250v., 100mA, 6.3v. 2a., 6.3v. 1a. £1-60
300-300v., 80mA, 6.3v. 4a., 0-5-6.3v. 3a. £1-65
250-250v., 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-20
300-300v., 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-20
300-300v., 130mA, 6.3v. 4a., c.t., 6.3v. 1a. £2-60
Suitable for Mullard 510 Amplifier
350-350v., 100mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-20
350-350v., 150mA, 6.3v. 4a., 0-5-6.3v. 3a. £2-60
FILAMENT or TRANSISTOR POWER PACK TYPES
6.3v. 1.5a. 45p; 6.3v. 2a. 54p; 6.3v. 3a. 76p; 6.3v. 6a. £1-30; 12v. 1a. 55p; 0-9-18v. 1a. £1-10; 0-12-20-42v. 2a. £1-76; 12v. 3a. or 24v. 1.5a. £1-35; CHARGER TRANSFORMERS 0-9-15v. 11a. 99p; 21a. £1-10; 3a. £1-25; 5a. £1-45; 6a. £1-65; 8a. £2-00.
AUTO (Step Up/Step Down) Transformers
0-110/220v., 200-230-250v. 50-80 watts. £1-10
150 watts, £1-90; 250 watts, £2-75; 500 watts, £5-75.
OUTPUT TRANSFORMERS
Standard Pentode 5,000 Ω to 7,000 Ω to 3 Ω 50p
Push-Pull 8 watts EL84 to 3 Ω or 16 Ω 83p
Push-Pull 10 watts 6V6 ECL86 to 3, 5, 8 or 15 Ω £1-37
Push-Pull EL84 to 3 or 15 Ω, 15-12 watts. £1-35
Push-Pull Ultra Linear for Mullard 510, etc. £2-20
Push-Pull 15-18 watts, sectionally wound 6L6 KT66, etc. for 3 or 15 Ω £1-99
Push-Pull 20 watt high quality sectionally wound 6L6, 6L6, KT66, etc. to 3 or 15 Ω £2-30

AUDIOTRINE HIGH FIDELITY LOUDSPEAKERS

Heavy construction. Latest high efficiency ceramic magnets. Treated Cone surround. "D" indicates Tweeter Cone providing extended frequency range up to 15,000 c.p.s. exceptional performance at low cost. Impedance 3 or 8-15 ohms.

WHEN ORDERING PLEASE STATE IMPEDANCE
HF 808T 8" 10W £2-88 HF 120D 12" 15W £4-75
HF 102D 10" 10W £3-40 HF 126 12" 15W £5-50
HF 120 12" 15W £4-25 HF 128D 12" 15W £5-90

AUDIOTRINE HI-FI SPEAKER SYSTEMS

Consisting of matched 12in. 11,000 line 15 watt 15 ohm high quality speaker, cross-over unit and tweeter. Smooth response and extended frequency range ensure surprisingly realistic reproduction. Carr. 30p.
Or SENIOR 15 WATT inc. HF120 £5-95
15,000 line Speaker £6-85. Carr. 30p.

NOTTINGHAM NEW BRANCH NOW OPEN 19/19a Market Street

HIGH QUALITY LOUDSPEAKERS

In teak or afrormosia veneered cabinets. L13 8-10 Watt Model. 3 or 15 ohms, 13 x 8in. Gauss 10,000 lines. Carr. 40p L12 12 in. 20 Watt Gauss 10,000 lines 15 Ω. Size approx' 16 x 18 x 10 in. Or dep. £3 and 9 mthly pymts £1-20 (Total £13.80) £5-25 Model. £11-95 Carr. 50p mthly pymts £1-20 (Total £13.80)

R.S.C. COLUMN SPEAKERS

Covered in Roxine and Vynair, ideal for vocalists and Public Address. 15 ohm matching. TYPE C48S 30, watts. Fitted four 8in. high flux 8v. speakers. £17-75 Or dep. £3 and 9 mthly pymts £2 (Total £21). Carr. 50p. TYPE C412S, 50 watts. Fitted four 12in. 11,000 lines 15 watt Speakers. £31 Or deposit £4 and 9 monthly payments of £3-37 (Total £34-33). Carr. 75p.

R.S.C. BATTERY/MAINS CONVERSION UNIT

Type BM1. An all-dry battery eliminator. Size 5 1/2 x 4 1/2 x 2in. approx. Completely replaces batteries supplying 1.5v. and 90v. to battery radio where A.C. mains 200/250v. 50 c/s is available. Complete Kit with Diagram £3-25 Ready for use £3-75

INTEREST CHARGES REFUNDED on Credit Sales, settled in 3 months

SMOOTHING CHOKES

150mA, 7-10H. 250 Ω 70p; 100mA. 10H. 200 Ω 60p; 80mA. 10H. 350 Ω 50p; 60mA. 10H. 400 Ω 25p.

SELENIUM RECTIFIERS

F.W. Bridged 6/12v. D.C. Output. Input Max. 18v. A.C. 1a., 25p; 2a., 35p; 3a., 50p; 4a., 65p; 6a., 80p.

- BRADFORD 10 North Parade (Half-day Wed.) Tel. 25349
- BLACKPOOL (Agent) O & C Electronics 227 Church St.
- BIRMINGHAM 30/31 Gt. Western Arcade (Half-day Wed.) Tel. 021-236 1279.
- DERBY 26 Osmaston Rd. The Spot (Half-day Wed.) Tel. 41361
- DARLINGTON 18 Priestgate (Half-day Wed.) Tel. 68043
- EDINBURGH 133 Leith St. (Half-day Wed.) Tel. 556 5766
- GLASGOW 326 Argyle St. (Half-day Tues.) Tel. 248 4158
- HULL 91 Paragon Street Half-day Thurs.) Tel. 20505



HI-FI CENTRES LTD.

MAIL ORDERS to: 106 HENCONNER LANE, LEEDS 13. Terms C.W.O. or C.O.D. Postage 25p extra under £2. 30p extra over £2, or as stated. Trade supplied. S.A.E. with enquiries. EXPORT ENQUIRIES WELCOMED. BRANCHES OPEN ALL DAY SATURDAYS. MAIL ORDERS MUST NOT BE SENT TO SHOPS.

- LEICESTER 32 High Street (Half-day Thurs.) Tel. 56420
- LEEDS 5-7 County (Mecca) Arcade, Briggate (Half-day Wed.) Tel. 28252
- LIVERPOOL 73 Dale Street (Half-day Wed.) Tel. 236 3573
- LONDON 238 Edgware Road, W.2 (Half-day Thurs.) Tel. 723 1629
- MANCHESTER 60A Oldham Street (Half-day Wed.) Tel. 236 2778
- MIDDLESBROUGH 106 Newport Rd. (Half-day Wed.) Tel. 47096
- NEWCASTLE UPON TYNE 41 Blacket Street (opp. Fenwick's Store) (Half-day Wed.) Tel. 21469
- NOTTINGHAM 19/19A Market Street (Half-day Thurs.) Tel. 48068
- SHEFFIELD 13 Exchange Street (Castle Market Buildings) (Half-day Thurs.) Tel. 20716

G. F. MILWARD

Mail Orders: **DRAYTON BASSETT, TAMWORTH, STAFFS**

ELECTRONIC COMPONENTS

Wholesale/Retail: **369 Alum Rock Road, Birmingham B8 3DR. Tel. 021-327 2339**

NEW LINES !!!!!

E.M.I. Speakers with twin tweeters	£3.75
8 watt amplifiers complete	£2.80
Cassette Tapes: C60, 57p; C90, 75p; C120, 90p.	
GOLDRING MAGNETIC CARTRIDGES (G850)	£4.75
Cardioid Ball type Mikes (usually £6-60)	£3.75
Intercom with Battery & Lead	£2.50
Neons, with resistor and 2 ft lead	5p
Speakers, 8 ohm, 2 1/2 in.	45p
MULLARD DATA BOOK FOR 1972	30p
TRANSISTOR EQUIVALENT BOOK. LATEST EDITION.	
Mikes, Low impedance, dynamic stick type with on/off switch	£1.00
.. Crystal, hand	50p
.. Crystal, Inserts with bracket	20p
Lockable car aerials	£1.25
Dee-Gee 25 watt pencil bit soldering irons	98p
Speakers, 2 1/2 in, 8 ohms	50p
Insulating Tape, 1/2 in wide, 10 yard rolls	5p
Miniature Output Transformers	12p
Rotary Switches, 4 pole 3 way or 2 pole 6 way	15p
Switch cleaner, aerosol cans	50p

RECTIFIERS 1N4007 1200 peak volts, 30 amps peak current, 1 amp mean current. 100 for £7-50, 1,000 £50

Electrolytic Capacitors	Miniature type. Both wires same and.		
2,000 µf 25 volt Rev.	25p	} 3p each.	
1,000 µf 70 volt	35p		
10,000 µf 35 volt	50p		
10,000 µf 25 volt	35p		
2,000 µf 18 volt	20p		
60µf + 200µf 300 volt	30p	Axial leads.	
400 µf 275 volt	25p	250 µf 25 volt	10p
10 µf 6 volt	2p	500 µf 25 volt	13p
10 µf 25 volt	4p	1,000 µf 25 volt	16p
16 µf 250 volt	8p	2,000 µf 25 volt	25p
32 µf 275 volt	8p	400 µf 40 volt	20p

UNBEATABLE PRICE !!!!!

LINEAR INTEGRATED CIRCUITS. Direct from manufacturer, all 100% to specification.
 709C 35p 100 up 24p
 741C 50p 100 up 35p

VEROBOARD

2 1/2 in x 1 in x 0.15 in	4p	5 in x 3 1/2 in x 0.15 in	28p	3 1/2 in x 3 1/2 in x 0.1 in	24p
3 1/2 in x 2 1/2 in x 0.15 in	16p	17 in x 2 1/2 in x 0.15 in	55p	5 in x 2 1/2 in x 0.1 in	23p
3 1/2 in x 3 1/2 in x 0.15 in	20p	17 in x 3 1/2 in x 0.15 in	74p	5 in x 3 1/2 in x 0.1 in	28p
5 in x 2 1/2 in x 0.15 in	20p	3 1/2 in x 2 1/2 in x 0.1 in	21p		

Spot Face Cutter 38p. Pin Insert Tool 48p. Terminal Pins (0.1 or 0.15) 36 for 18p. Special Offer Pack consisting of 5 2 1/2 in x 1 in boards and a Spot Face Cutter—30p.

RECORD PLAYER CARTRIDGES. Well below normal prices!
 G90 Magnetic Stereo Cartridges, Diamond Needle, 6mV output, £2.75. ACOS GP 67/2 (Mono, Crystal) 75p. ACOS GP 91/3 (Compatible, Crystal) £1. ACOS GP 93/1 (Stereo, Crystal, Sapphire) £1.25. ACOS GP 93/1D (Stereo, Crystal, Diamond) £1.63. ACOS GP 94/1 (Stereo, Ceramic, Sapphire) £1.50. ACOS GP 94/1D (Stereo, Ceramic, Diamond) £1.88. ACOS GP 95/1 (Stereo, Crystal with two L.P./Stereo needles) £1.25.

TRANSISTORISED FLUORESCENT LIGHTS, 12 volt. All with reverse polarity protection. 8 watt type with reflector, suitable for tents, etc., £3. Postage/Packing 25p. 15 watt type, batten fitting for caravans £4. Postage/Packing 25p. 13 watt type, batten with switch. 2 1/2 in x 2 in x 1 in £5. Postage/Packing 25p. THESE CAN BE SENT ON APPROVAL AGAINST FULL PAYMENT.

MULLARD POLYESTER CONDENSERS
 1,000pf, 1,200pf, 1,500pf, 1,800pf, 2,200pf, 15p per dozen (all 400V working).
 0.15µf, 0.22µf, 0.27µf, 30p per dozen (all 160V working). 25% discount for lots of 100 of any one type.

RESISTORS
 1/2 and 1 watt. Most values in stock. 75p per 100. 10p per dozen of any one value.
WIRE WOUND MAINS DROPPERS. Hundreds of values from 0.7 ohm upwards. 1 watt to 50 watts. A large percentage of these are multi-tapped droppers for radio/television. Owing to the huge variety these can only be offered "assorted" at 50p per dozen.

SILVER MICA/CERAMIC/POLYSTYRENE CONDENSERS
 Large range in stock, 75p per 100 of any one value. 15p per dozen.

RECORDING TAPE BARGAIN! The very best British Made low-noise high-quality Tapel 5in Standard 38p. Long-play 45p. 5 1/2 in Standard 45p. Long-play 60p. 7in Standard 60p. Long-play 82p. We are getting a fantastic number of repeat orders for this tape. Might we suggest that you order now whilst we still have a good stock at these low prices?

STOCKTAKING CLEARANCE! IMPOSSIBLE TO REPEAT!

We have huge numbers of components in quantities too small to advertise individually. In order to "clear the decks" we have made up parcels containing a mixture of carbon and wire-wound resistors, electrolytic and paper condensers, controls, transistors, diodes etc., for a tiny fraction of normal price. It is emphasised that these are mixed parcels only—contents cannot be stipulated! Sold only by weight.
 Gross weight 2 lb. £1 (postage 20p)
 Gross weight 5 lb. £2 (postage 30p)

FANTASTIC OFFER! 4,000,000 DIODES TO CLEAR!

Germanium (OA 91 type)
 Gold Bonded Silicon (BA 144 type)
 Zener (400 mw. BZY 88 type)

300	50p	1,000	£1
10,000	£9	OF ANY ONE TYPE	

TANTALUM CAPACITORS. COMPARE THE PRICE—ONLY 10p EACH !!!!!

Sub-miniature types	Miniature types	5-6 µf 35 volts
-047µf 50 volts	-022µf 20 volts	8-2 µf 10 volts
-056µf 50 volts	-033µf 20 volts	8-2 µf 35 volts
-07 µf 20 volts	-047µf 20 volts	15 µf 35 volts
-1 µf 20 volts	-068µf 35 volts	18 µf 35 volts
-1 µf 50 volts	-12 µf 35 volts	22 µf 15 volts
-18 µf 20 volts	-15 µf 35 volts	27 µf 20 volts
-33 µf 35 volts	-22 µf 50 volts	56 µf 15 volts
-47 µf 35 volts	-47 µf 50 volts	56 µf 20 volts
-68 µf 20 volts	-68 µf 35 volts	150 µf 6 volts
1-0 µf 15 volts	-68 µf 50 volts	
2-2 µf 3 volts	1-0 µf 35 volts	Standard
2-7 µf 15 volts	1-0 µf 75 volts	6-8 µf 50 volts
2-7 µf 35 volts	1-8 µf 20 volts	7-5 µf 20 volts
3-0 µf 12 volts	2-2 µf 20 volts	8-2 µf 150 volts
10-0 µf 1.5 volts	2-7 µf 50 volts	12 µf 35 volts
	3 µf 12 volts	12 µf 50 volts
	3-3 µf 15 volts	39 µf 20 volts
	4 µf 20 volts	82 µf 20 volts
	4-7 µf 35 volts	150 µf 15 volts
	5-6 µf 6 volts	270 µf 6 volts

NEW! NEW! NEW! NEW!


An aerosol spray providing a convenient means of producing any number of copies of a printed circuit both simply and quickly.

Method: Spray copper laminate board with light sensitive spray. Cover with transparent film upon which circuit has been drawn. Expose to light. (No need to use ultra-violet.) Spray with developer, rinse and etch in normal manner. Light sensitive aerosol spray £1.00 plus postage
 Developer spray 50p

SPECIAL 50p PACKS. ORDER 10 PACKS AND WE WILL INCLUDE AN EXTRA ONE FREE !!!!!

RESISTORS, 1/2 watt	100 50p	TRANSISTORS	
assorted	20 50p	P.N.P. Untested but mainly O.K.	50 50p
Wire-wound 1 to 3 watt	15 50p	N.P.N. Untested but mainly O.K.	50 50p
5 to 7 watt	10 50p	OCF 71 equivalent	5 50p
10 watts	12 50p	Light-sensitive Diodes	10 50p
Multi-tapped		(These produce up to 1ma from light)	
PAPER CONDENSERS	50 50p	OC44 Mullard 1st grade	4 50p
Tv types	100 50p	OC45 Mullard Boxed	5 50p
Miniature		2G378 Output, Marked	5 50p
ELECTROLYTIC CONDENSERS		2G371 Driver, Marked	5 50p
Suitable for Mains	10 50p	ASY 22, Marked	5 50p
Radio/Tv	20 50p	BY 127 Rectifiers	4 50p
Transistor types	15 50p	IN4007 Rectifiers (1200V peak)	4 50p
Mixed (both types)		STC 3/4 Rectifiers	6 50p
POLYSTYRENE CONDENSERS	100 50p	DIODES (OA 81 & OA 91)	40 50p
MULLARD POLYESTER COND.	50 50p	WIRE	
SILVER MICA WIRE-WOUND 3-Watt SLIDERS	15 50p	Solid Core. Insulated	100yds. 50p
VOLUME CONTROLS	5 50p	Stranded ditto	50yds. 50p
Assorted		SOLAR CELLS	
NUTS AND BOLTS. Mixed length/type		Large Selenium	2 50p
8 B.A.	100 50p	Small	3 50p
6 B.A.	100 50p	(6 cells will power a Micromatic radio)	
4 B.A.	100 50p	CO-AXIAL CABLE	
2 B.A.	100 50p	Semi Air-spaced	15yds. 50p
METAL SPEAKER GRILLES	6 50p	CRYSTAL TAPE RECORDER MIKES	
7 1/2 in. x 3 1/2 in.		CRYSTAL EARPIECES	
EARPIECES, MAGNETIC		3-5mm Plug	1 50p
No Plug	6 50p	TRANSISTORISED Signal Injector Kit	1 50p
2-5mm Plug	4 50p	TRANSISTORISED Signal Tracer Kit	1 50p
3-5mm Plug	4 50p	TRANSISTORISED CAR REV. COUNTER KIT (Needs 1 ma. meter as indicator)	1 50p
500 MICRO-AMP LEVEL METERS	1 50p		
VEROBOARD. TRIAL PACK 5 BOARDS + CUTTER	50p		

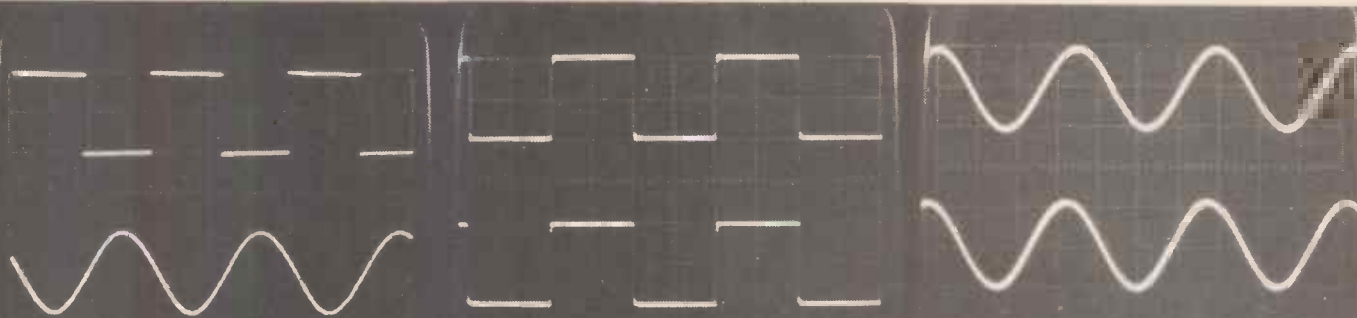2 HZ TO 20 MHz SOLID STATE BEAM SWITCH FOR ONLY £9.25. P.P. 25p.



20 HZ

100 KHZ

30 MHZ

We supply a completely assembled ready to connect and use Glass Fibre printed circuit board (size $4\frac{3}{4}$ " x $3\frac{1}{4}$ "") with 47 high quality components consisting of 6 silicon epitaxial transistors, 10 silicon diodes, 21 carbon film resistors, 8 capacitors, a chop selector switch and shift control (these both on flying leads). British Manufacture—Sole Distributors.

Freq. Response
Chop rate
Input Impedance
(both channels)

Input range

(attenuators available at extra cost)

Power requirements

System loss

Completely encased with attenuators and BNC Connectors. £25 each.

2 HZ — 20 MHz
50 and 100 KHz
1 meg ohm 25pf.

100 mV to 1V

(attenuators available at extra cost)

9 to 15 volts

less than 10%

IKEGAMI 625 CAMERA with standard lens. £65.

ROHDE & SCHWARZ—UHF RECEIVER, 280-940 MHz (4600 MHz) Type USVD-(BN 1523). ONLY £450.

ROHDE & SCHWARZ Z-g-DIAGRAPH, 300-2400 MHz Type ZDD (BN 3562) 50 ohms. In FINE CONDITION. ONLY £275.

REMSCOPE Storage Oscilloscope type S01. Fine Condition complete with manual. £125 ea. Carr £1.50.

TRANSISTOR INVERTOR. 12V to 1.5 KV 2 MA AC. Size $1\frac{1}{2}$ " x $2\frac{1}{2}$ " x 4". ONLY £2.95 P & P 25p.

SOLARTRON Precision Millivoltmeter type VF252. Max. sensitivity 1.5mV full scale. £30 ea. Carr £1.50.

SOLARTRON LABORATORY AMPLIFIER AWS 51A. 15cs to 350KHz 60db attenuator in 1db steps. Balance output, meter scaled in db's and volts. £12 ea. Carr £1.50.

SOLARTRON TFA CARRIER CONVERTER JX641. £50. Carr £1.50. Associated equipment available.

47000 mfd 25V
28A
60p ea. P & P 10p.

MULLARD
CAPACITORS
2200 mfd 100V
10A (50°C)
75p ea.
(500 off-50p ea.)

3150 mfd 40V
70°C
60p ea.

TEKTRONIX Time mark unit type 181 £75.
TEKTRONIX CA Plug-in £75.
TEKTRONIX Current probe type P6402 £240.

ELECTRON MICROSCOPE BY TESIA
completely self-contained including optics on table size 5ft 9in x 2ft 5in x 2ft 9in high. Full information and price, etc., on request.

THERMAL MICROPLOTTER BY PHILCO
complete with calibrator and optics with BRYANS auto plotter type 2100. P.U.R.

POLARD SPECTRUM ANALYSER
complete with 5 plug-in units covering 10-44,000MHz. Price £425.

MARCONI U.H.F. SIGNAL GENERATOR TF 1060
450 MHz to 1200 MHz. £220. Carr £1.50.

MARCONI FM/AM SIGNAL GENERATOR TF 1066/1
10 MHz to 470 MHz. £385. Carr £1.50.

MARCONI VTVM TF 1300
As new. £50 ea. Carr £1.

MARCONI WIDE BAND MILLIVOLTMETER TF 1371
£65. Carr £1.50.

FREQUENCY METER by J.A.C; ELECTRONICS LTD. MODEL 331
—AS NEW. ONLY £475.

STABILIZED POWER UNIT for BC221 Freq. Meter, Slide-in and connect. ONLY £3.75p P & P 75p.

MARCONI L.C.R. Bridge type 868 £65. Carr £1.50.

VALVE VOLTMETER type 202. 1.5V full scale to 150V AC and 1V full scale to 100V DC. Large mirror scaled meter. Standard mains input, supplied complete with probe, leads, etc. £15 ea. Carr £1.

RACAL VOLTAGE to FREQUENCY CONVERTOR SA503. 0.5V to 500V. £25 ea. Carr £1


E.H.T. POWER UNIT. 0-40KV Variac controlled, metered. As new condition, £150. Carriage at cost.

CHILTMEAD LTD

7/9 ARTHUR ROAD, READING, BERKS. (rear Tech. College) Tel.: Reading 582605/65916

KEEPING IN TUNE

through BRIMAR

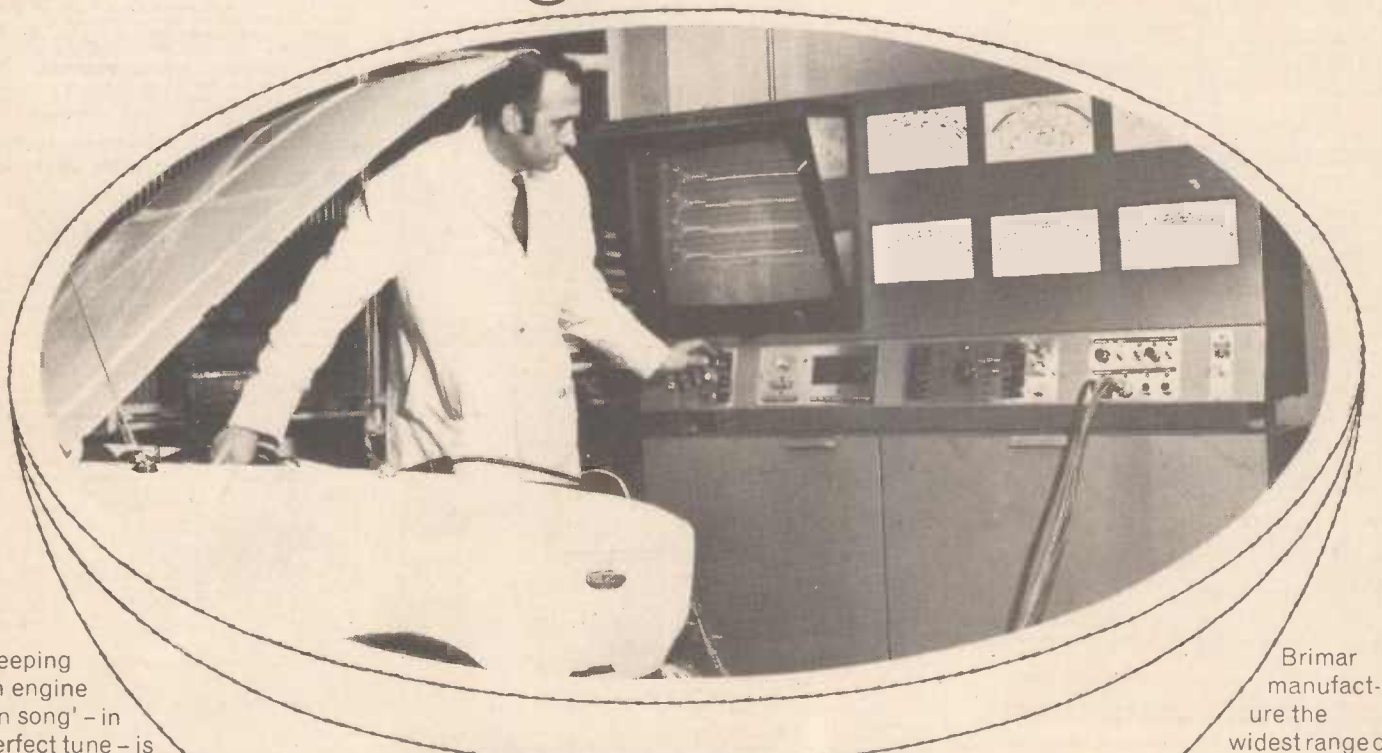

Keeping an engine 'on song' - in perfect tune - is as important to the average motorist interested in economy as to the sporting motorist concerned mainly with performance. Crypton Tuning is becoming available in more and more garages throughout the country. The main feature of Crypton-Triangle's latest engine analyser, the Dynascope 24 Model BD140 is the ultra-wide-screen oscilloscope, which not only makes diagnosis easier, but allows for far easier instruction in classes, even in bright sunlight. The tube used, is, of course, a Data Display Tube from Brimar.

Brimar manufacture the widest range of cathode ray tubes for industry. Research continually increases the range to meet newer, more complex developments. Brimar look ahead to stay in front.

CRT reliability

BRIMAR

**Thorn Radio Valves
and Tubes Limited,**
Mollison Avenue, Brimsdown,
Enfield, Greater London.
Tel: 01-804 1201

THORN
BPT. 7

Thermostat with Probe. Made by the famous Ranco Thermostat Co. Covers the range from approx. 0°-200°C, variable by a control spindle, handles currents up to 16 amps. Length of capillary and sensor tube approx. 3 ft. 6 in. These are ideal for ovens and as a general purpose thermostat. Price 50p each or 10 for £4.50.

Small Tuning Condensers fitted to many imported Japanese and Hong Kong radios. 2-gang about 200pF per gang. Size approx. 1 in. by 1 in. with a 1/4 in. diameter spindle with dust cover. 25p each or 10 for £2.25.

Heat Sink. Small type as used with 0081 etc. Price 5p each or 10 for 45p.

High Voltage Condenser. 0.265 mfd. 1500V RMS which means that these have a D.C. rating of over 4000V. 75p each or 10 for £6.75.

125w Starter. For 8 ft. fluorescent tubes. Mazda 1 1/2 in. canister, 4-pin base. Price 20p each or 10 for £1.80.

IF Transformers. 465 K.C. double tuned and made for transistor circuits. 35p per set of 3. 10 sets for £3.15.

Spectacle Frames (cases). With built-in hearing aids. The amplifier and battery being housed in the arms. Although these are complete hearing aids we are selling them purely for the sub-miniature components they contain. We give no guarantee that they are in working order also these may be second hand. Price £2.50 each.

Giant Rev Counter. This is an 8-in. diameter moving coil meter with extra long (260 deg.) pointer movement. 1mA full scale deflection. New and guaranteed perfect. Probably costing anything up to £20. Limited number only, our price £5.50 each plus 40p post and insurance.

Foot Switch. Twin levers each of which operates a 10-amp QRM change-over switch. Price 60p each.

9V Gram Unit. On unit plate with 33-45 change lever, complete with turntable price £2.25 each plus 20p post and insurance.

18-Way Plug and Socket. 15p per pair. 10 pairs for £1.35.

1 Hour Minute Timer. Made by Smiths complete with control knob and calibration dial. This month's special bargain at 50p. Useful in the Kitchen, Office and Dark-room etc.

Programmers. 5 revs per minute. Made by Magnetic Devices Ltd. The contacts may be set to trigger anywhere around the shaft, ideal for motivated lighting displays, sequential switching etc. Drive motors are 200-240V 50Hz. Model A has 5 change-over contacts. Price £1.50. Model B has 11 change-over contacts. Price £3.

Programmers. 6 revs per minute. Similar to previous items but having 8 sets of change-over contacts. Motor 200-240V 50Hz. Price £3.50 each.

Black Heat Element. Copper clad 1/4 in. tubular construction replacements in Triclity and many other cookers also suitable if connected in series to heat airing cupboards and for other low temperature applications. The following types are available.

90W Model. 14 in. long by 1 1/2 in. wide. Made by Backer. Price 75p or 10 for £6.75. 2200W Model. W shaped. 14 1/2 in. by 9 in. wide. 85p each or 10 for £7.85.

Radiant Cooker Rings. As fitted to Triclity and many other popular cookers. We have two types. These are copper clad 1/4 in. tubular construction. Both models have an external diameter of 6 1/2 in. and the elements have been slightly flattened to increase radiation.

Backer Type 7D1. 2000 watts has a metal cover, size approx. 3 in. by 1 1/2 in. in. over the element connections. So in addition to being a replacement this could also quickly be made into a boiling ring as it only needs mounting on a simple iron frame. This element is rated 200-210V but it is perfectly safe on 240V and as there are usually 5mm controlled the lower voltage rating is not all that important. Price 75p each or 10 for £6.75.

Backer Model 7D1 Mk II. again 2000 watts rated but has no cover over element ends. Price 65p each or 10 for £6.85.

Tricity Cooker Elements. We have quite an assortment of these and will describe them in future issues—but if in the meantime you are needing these then please let us have a sketch, we may have the exact one in stock.

Slide Switch. 2-pole change-over panel mounting by two 5BA screws. Size approx. 1 in. by 1 in. rated 250V lamp. 5p each. 10 for 50p. Protective cover 50p. 75p each.

Sub Miniature Slide Switch. DPDT 18mm (3/4 in. approx.) between firing centres. 12p each or 10 for £1.08.

Small Crp. Clips. Suitable for instruments, etc. 5p each or 10 for 45p.

Bell Transformer. Normal mains input 4, 6, 8V, output, normal bakelite case with protective cover. 75p each.

Mains Transformer. Primary 240V tapped 230V. Secondary 20V 1 amp. Price 60p each or 10 for £5.40.

Transformer. Primary 230-240V. Secondary 6.5-0-6.5V 1 amp. With fitted primary screen. 85p each or 10 for £4.85.

Dial Thermometer. Reading from 200-525°F. used on Triclity and other cookers. This has a fancy case, one of which would be a 1 1/2 in. hole or alternatively it can just be rested on the object whose temperature it is required to measure. Size 2 x 3/4 in. overall diameter. Depth 1/2 in. below and 1/2 in. above mounting panel. Price 80p each or 10 for £7.20.

THERMOSTATS

Type "A" 15 amp. for controlling room heaters, green-houses, airing cupboard. Has spindle for pointer knobs. Quickly adjustable from 30-38 deg. F. 47p plus 5p post.

Suitable box for wall mounting. 25p. F. & P. 5p.

Type "B" 10 amp. This is a 17 in. long rod type made by the famous Sunvic Co. Spindle adjusts this from 50-550 deg. F.

Internal screw alters the setting so this could be adjustable over 30 deg. to 1000 deg. F.

Suitable for controlling furnace, oven, kiln, immersion heater or to make flame-steady or fire alarm. 42p plus 12p post and insurance.

Type "D". We call this the Ice-ast as it cuts in and out at around freezing point, 2/3 amps. Has many uses, one of which would be to keep the loft pipes from freezing, if a length of our blanket wire (16 yd.) 50p is wound round the pipes. 37p. P. & P. 5p.

Type "E". This is standard refrigerator thermostat. Spindle adjustments cover normal refrigerator temperature. 47p. plus 5p post.

Type "F". Glass encased for controlling the temperature of liquid—particularly those in glass tanks, vats or sinks—thermostat is held (half submerged) by rubber sucker or wire clip—ideal for fish tanks—developers and chemical baths of all types. Adjustable over range 50 deg. to 150 deg. F. Price 90p plus 10p post and insurance.

HIGH ACCURACY THERMOSTAT

Uses differential comparator I.C. with thermistor as probe. Designer claims temperature control to within 1/7th of a degree. Complete kit with power pack £5.50.

Recorded Tapes. Not cassettes but normal 5 in. spools. 33 in. speed, suit most tape recorders. Mainly World Record Club. Popular and Classical. We have over 150 titles now in stock. Price 85p each or 5 for £2.50. Send for list of titles interested.

TREASURE TRACER

Complete Kit (except wooden battens) to make the metal detector as the circuit in Practical Wireless August issue. £2.95 plus 20p post and insurance.




SMITHS 24-HOUR 2 ON/2 OFF TIME SWITCH

This is the popular model, as used in the Autosee and Morphy Richards time switches. Once programmed, this will repeat until reprogrammed. For window lighting, house protection, etc. Only needs a case and an output socket. 230v. 50 cycles. Contacts switch up to 14 amps. Price £2.75 + p&p 25p.

FIRE ALARM BELL

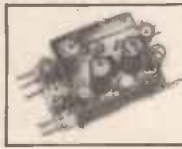Mains operated. Really loud ring 6" gong. Size approx. 12" x 6" x 4 1/2". Suitable outside or inside. Heavy cast with 1 1/2" conduit entry. Made by A.F.A. Operates off 200-240V AC. £3.75 plus 60p.



MULLARD AUDIO AMPLIFIER MODULE

Uses 4 transistors, and has an output of 750mW into 8 ohms speakers. Input suitable for crystal mic, or pick-up. 9 volt battery operated. Size 2" long x 1 1/2" wide x 1" high. SPECIAL SNIP PRICE 60p each. 10 for £5.40.

INSTRUMENT SWITCHES

Miniature precision switches with 1" dia. moulded wafers. Silver plated 5 amp contacts, standard 1" spindle.

No. of Poles	2 way	3 way	4 way	5 way	6 way	8 way	9 way	10 way	12 way
1 pole	60p	60p	60p	60p	60p	60p	60p	60p	60p
2 poles	80p	80p	80p	80p	80p	80p	80p	80p	80p
3 poles	60p	60p	60p	60p	60p	60p	60p	60p	60p
4 poles	60p	60p	60p	60p	60p	60p	60p	60p	60p
5 poles	60p	60p	60p	60p	60p	60p	60p	60p	60p
6 poles	60p	60p	60p	60p	60p	60p	60p	60p	60p
7 poles	60p	60p	60p	60p	60p	60p	60p	60p	60p
8 poles	60p	60p	60p	60p	60p	60p	60p	60p	60p
9 poles	60p	60p	60p	60p	60p	60p	60p	60p	60p
10 poles	60p	60p	60p	60p	60p	60p	60p	60p	60p
11 poles	60p	60p	60p	60p	60p	60p	60p	60p	60p
12 poles	60p	60p	60p	60p	60p	60p	60p	60p	60p

2 AMP VARIAC

Variacs without a doubt are a most useful device and no workshop should be without two or three of them. Special purchase enables us to offer ex-equipment but mechanically and electrically sound. 2 amp. Variac's at the very low price of £3 each, plus 50p post, etc.

THIS MONTH'S SNIP

FLUORESCENT TUBES 15p EACH

Here is a golden opportunity to light up those murals and pelmetis and to put lights where you have often planned to have them or if plant growing is your hobby why not install a bank over your f ring bench—remember we can supply the control gear at very low prices too, (£1 per set). This is a *Special Spring Offer*. First grade tubes all of best makers and all at the low price of 15p each in boxed lots of 24 of similar type or 20p each for less than 24. All the tubes are perfectly standard having normal bi-pin ends and all are white (coloured tubes available if required). Following types available: 18", 15 watt; 24", 40 watt; 36", 40 watt; 39", 40 watt. All at the same low price and even lower prices if you buy a large quantity. Sorry but we cannot despatch less than a box of 24 as the cost of carriage and packing would be prohibitive, however you may mix the 24 to your requirement and the special price for a mixed 24 would be £4. If not collecting please add 50p per box per 200 miles.

BATTERY CONDITION TESTER

Made by Malory but suitable for all batteries used by Ever Ready and others, most of which are zinc carbon types but also mercury manganese—lead—silver oxide and alkaline batteries may be tested. The tester puts a dummy load on the battery and the meter scale indicates the condition depending upon which section the pointer rests. The section reads "replace", "weak" or "good". The tester is complete in its case, size 3 1/2" x 6 1/2" x 2" with leads and prods. Price £1.75 plus 20p postage.

DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plug and on/off switch with neon warning light. Supplied complete with 7 feet of heavy cable. Wired up ready to work, £2.25 less plug; £2.50 with fitted 13 amp plug; £2.65 with fitted 15 amp plug, plus 25p P. & P.

HONEYWELL PROGRAMMER

This is a drum type timing device, the drum being calibrated in equal divisions for switch purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro switches each of 10 amp type operated by the trips thus 15 circuits may be changed per revolution. Drive motor is mains operated 5 revs. per min. Some of the many uses of this timer are Machinery control, Boiler firing, Dispensing and Vending machines, Display lighting animated signs, Signalling etc. Price from Makers probably over £10 each. Special snip price £5.75 plus 25p post and ins. Don't miss this terrific bargain.

COMPUTER TAPE

2,400ft. of the Best Magnetic Tape money can buy—users claim good results with Video and sound. 1 in. wide £1.00 plus 33p post and insurance, with cassette. 1/2 in. wide £1.00 plus 30p post and insurance with cassette. 1 in. wide 85p plus 25p post and insurance with cassette. Spare spools and cassettes—1 in. 75p. 1/2 in. 75p each plus 20p post and insurance.

CAPACITOR DISCHARGE CAR IGNITION

This system which has proved to be amazingly efficient and reliable was first described in the *Wireless World* about a year ago. We can supply kit of parts based on circuit (*Practical Wireless*). Price £4.95. When ordering please state whether for positive or negative systems. De-luxe model £6.95. De-luxe and made-up ready £8.95. All plus 30p post and packing.

SMITHS 20 AMP CLOCK SWITCH

This is a famous Smiths Clock with 20 amp on/off switch. (Switch on/off time is continuously variable). A beautiful unit. Offered at less than the cost of the clock alone. £2 with application notes and circuits. Glass front and bezel 75p extra. Post and insurance 20p.

SOLDER GUN

A must for every busy man, gives almost instant heat also illuminates Job. Dual heat 100/140 watt £3.75 plus post & ins. 20p. BIG JOB 250 watt model. £4.75 plus post & ins. 40p.

Where postage is not stated then orders over £5 are post free. Below £5-add 20p. S.A.E. with enquiries please.



DRILL CONTROLLER

New 1kW model. Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions £1.60, plus 13p post and insurance. Made up model also available £2.25 plus 13p P. & P.

MAINS OPERATED CONTACTOR

220/240V. 50 cycle solenoid with laminated core so very silent in operation. Closes 4 circuits each rated at 10 amps. Extremely well made by a German Electrical Company. Overall size 2 1/2 x 2 in. £1 each.



DOUBLE LEAF CONTACT

Very slight pressure closes both contacts. 6p each. 60p doz. Plastic push-rod suitable for operating 5p each, 45p doz.

AUTO-ELECTRIC CAR AERIAL

with dashboard control switch—fully extendable to 40in. or fully retractable. Suitable for 12v positive or negative earth. Supplied complete with fitting instructions and ready wired dashboard switch. £5.75 plus 25p post and ins.

TOGGLE SWITCH

3 amp 250v. with fixing ring. 75p each 75p doz.

MICRO SWITCH

5 amp. changeover contacts, 6p each, £1.00 doz. 10 amp. on/off 10p each or £1.05 doz. 15 amp. changeover 15p, 10 for £1.35.

MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—2 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole, 6 way—1 pole, 12 way. All at 18p each, £1.80 dozen, your assortment.

WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. 60p post free.

BLANKET SWITCH

Double pole with neon light into side so luminous in dark. Ideal for dark room light or for use with waterproof element—new plastic case. 25p; 10 for £2.25 3 heat model 38p; 10 for £3.42.

HEARING AID AMPLIFIERS

(Ex behind ear deaf aids) 3 transistors on tiny P.C. board with volume control—whole thing only about half as big as Oxco type. £1.75 or with sub-miniature microphone and L.S. attached £3.50.

ELECTRIC CLOCK WITH 20AMP. SWITCH

Made by Smith's these units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set—also on the left is another time or alarm—this may be set in minutes up to 1 hour. At the end of the period a bell will sound. Offered at only a fraction of the regular price—£2.50, less than the value of the clock alone—post and ins. 15p.

LIGHT CELL

Almost zero resistant in sunlight increases to 10 K. Ohms in dark or dull light, epoxy resin sealed. Size approx. 1 in. dia. by 1/2 in. thick. Rated at 800 MW. wire ended. 3ip. Suit most circuits

CAR ELECTRIC PLUG

Fits in place of cigarette lighter. Useful method for making a quick connection into the car electrical system. 38p each or 10 for £3.42.

QUICK CUPPA

Mini Immersion Heater. 350W. 200/240V. Boils full cup in about two minutes. Use any socket or lamp holder. Have at bedside for tea, baby's food, etc. £1.25, post and insurance 14p. 12V car model also available. Same price. Jug model also available £1.50 plus P. & P. 14p.

SNAP ACTION SLIDE SWITCH

Rated 5a. 240v. Made by Arrow. Type fitted in the handles of electric drills, vacuums, etc. 5p each, 10 for 45p.

NUMICATOR TUBES

For digital instruments, counters, timers clocks, etc. Hi-vac XN. 3. Price 99p each 10 for £9.

POCKET CIRCUIT TESTER

Test continuity for any low resistance circuit, house wiring, car electrics. Tests polarity of diodes and rectifiers. Also ideal size for conversion to signal injector (circuit supplied), 30p or 2 for 50p. Post paid.

12 WAY SUB-MINIATURE MULTI-CORE CABLE

7-0076 copper core each core P.V.C. insulated and of different colour. P.V.C. covered overall and approx. 3/16in. thick. Price 20p per yard.

AERO SERVICES LTD




A.C./D.C. MULTIMETERS with taut suspension movements



U4312 LOW SENSITIVITY (667 o.p.v. AC/DC). 35 ranges covering 75mV, 300mV to 900V DC, 300µA to 6A DC, 300mA to 900V AC, 1.5mA-6A AC. £9.75.

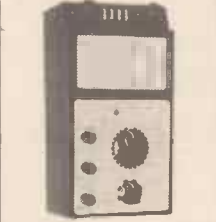
U4313 HIGH SENSITIVITY (20,000 o.p.v. DC, 2000 o.p.v. AC). 39 ranges covering 75mV DC, 1-10-1000-1000 kilohms, capacitance and output level. £10.50.



U4341 MULTIMETER/TRANSISTOR TESTER. Sensitivity 16700 o.p.v. DC, 3300 o.p.v. AC. 27 ranges covering 0.3-900V and 0.06-300mA AC, 1.5V-750V and 0.3-300mA AC, 4 resistance ranges up to 2 Megohms, two ranges of transistor current gain. £10.50.



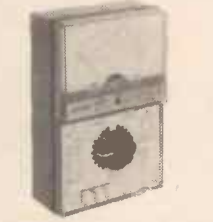U4355. 2000 o.p.v. DC, 2000 o.p.v. AC. 30 ranges covering 50µA, 1.5mA-2.5A DC, 5mA-2.5A AC, 75mV, 2.5V-1000V DC, 2.5V-1000V AC, 3 resistance ranges up to 300 kilohms. £8.75.



U4324. 29000 o.p.v. DC, 4000 o.p.v. AC. 33 ranges covering 60µA-3A DC, 300µA-3A AC, 0.6-1200V DC, 3-900V AC, 4 resistance ranges and output level. £8.00.

WHEN ORDERING BY POST PLEASE ADD £0-12½ (2/6) IN £-FOR HANDLING AND POSTAGE. NO C.O.D. ORDERS ACCEPTED

PARTICULARS AVAILABLE ON REQUEST

TRANSISTORS		ACI188 0-30		ASZ17 0-75		BF184 0-25	
2N404 0-17	2N3054 0-55	ACI17	ASZ18 0-75	BF185 0-20			
2N444A 0-25	2N3055 0-75	0-275	ASZ20 0-25	BF186 0-15			
2N696 0-17	2N3133 0-30	ACY18 0-20	ASZ21 0-30	BF195 0-18			
2N697 0-17	2N3134 0-30	ACY19 0-20	ASZ22 0-30	BF196 0-25			
2N698 0-30	2N3391 0-20	ACY20 0-20	ASZ23 0-30	BF187 0-20			
2N705 0-70	2N3391 0-15	ACY21 0-20	ASZ24 0-30	BF200 0-35			
2N706 0-10	2N3393 0-15	ACY22 0-15	ASZ25 0-30	BF200 0-20			
2N708 0-15	2N3394 0-15	AD140 0-50	ASZ26 0-30	BF208 0-23			
2N916 0-40	2N3395 0-20	AD149 0-50	ASZ27 0-30	BF208 0-20			
2N929 0-22	2N3402 0-15	AD161 0-35	ASZ28 0-30	BF208 0-20			
2N930 0-25	2N3403 0-15	AD162 0-35	ASZ29 0-30	BF208 0-25			
2N987 0-30	2N3404 0-15	ADZ11 1-25	ASZ30 0-30	BF210 0-50			
2N1131 0-25	2N3414 0-20	ADZ12 1-25	ASZ31 0-30	BFY11 0-50			
2N1132 0-25	2N3415 0-15	AF114 0-20	ASZ32 0-30	BFY17 0-40			
2N1184 1-25	2N3416 0-25	AF115 0-20	ASZ33 0-30	BFY18 0-55			
2N1301 0-40	2N3417 0-25	AF116 0-20	ASZ34 0-30	BFY19 0-50			
2N1302 2N3646 0-40	AF117 0-20	BF178 0-20	ASZ35 0-30	BFY50 0-25			
0-175	2N3702 0-12	BF179 0-20	ASZ36 0-30	BFY51 0-20			
2N1303 0-25	2N3703 0-12	BF180 0-20	ASZ37 0-30	BFY52 0-25			
2N1304 0-25	2N3704 0-12	BF181 0-20	ASZ38 0-30	BKX190-175			
2N1305 0-25	2N3707 0-15	BF182 0-20	ASZ39 0-30	BKX26 0-20			
2N1306 0-25	2N3709 0-12	BF183 0-20	ASZ40 0-30	BKX26 0-20			
2N1307 0-20	2N3710 0-12	BF184 0-20	ASZ41 0-30	BKX26 0-20			
2N1308 0-25	2N3711 0-15	BF185 0-20	ASZ42 0-30	BKX26 0-20			
2N1309 0-30	2N3819 0-35	BF186 0-20	ASZ43 0-30	BKX26 0-20			
2N1613 0-22	2N3904 0-35	BF187 0-20	ASZ44 0-30	BKX26 0-20			
2N1711 0-25	2N3905 0-20	BF188 0-20	ASZ45 0-30	BKX26 0-20			
2N1924 0-15	2N3906 0-40	BF189 0-20	ASZ46 0-30	BKX26 0-20			
2N1905 2-10	2N4107 0-50	BF190 0-20	ASZ47 0-30	BKX26 0-20			
2N2147 0-75	AC113 0-15	BF191 0-20	ASZ48 0-30	BKX26 0-20			
2N2160 0-65	AC125 0-30	BF192 0-20	ASZ49 0-30	BKX26 0-20			
2N2217 0-30	AC126 0-20	BF193 0-20	ASZ50 0-30	BKX26 0-20			
2N2218 0-30	AC127 0-20	BF194 0-20	ASZ51 0-30	BKX26 0-20			
2N2219 0-35	AC128 0-15	BF195 0-20	ASZ52 0-30	BKX26 0-20			
2N2359A 0-20	AC132 0-35	BF196 0-20	ASZ53 0-30	BKX26 0-20			
0-20	AC151 0-25	BF197 0-20	ASZ54 0-30	BKX26 0-20			
2N2646 0-60	AC153 0-20	BF198 0-20	ASZ55 0-30	BKX26 0-20			
2N2906 0-35	AC154 0-15	BF199 0-20	ASZ56 0-30	BKX26 0-20			
2N2923 0-16	AC157 0-20	BF200 0-20	ASZ57 0-30	BKX26 0-20			
2N2924 0-15	AC169 0-10	BF201 0-20	ASZ58 0-30	BKX26 0-20			
2N2926 0-15	AC176 0-25	BF202 0-20	ASZ59 0-30	BKX26 0-20			
2N3053 0-25	AC187 0-30	BF203 0-20	ASZ60 0-30	BKX26 0-20			

0A2 0-38	5X8 0-60	6B97 1-30			
0A3 0-45	5Y3GT 0-40	6B98 0-85			
0A4G 1-00	5Z3 0-60	6B99 0-85			
0B2 0-35	5Z4G 0-60	6B9E 0-25			
0B3 0-70	6/30L2 0-80	6B9T 0-25			
0C2 1-00	6A8G 0-40	0-85			
0C3 0-38	6A84 0-25	6B26 0-40			
0D3 0-85	6A7 0-40	6C4 0-33			
1A3 0-35	6A4A 0-55	6C85A 1-50			
1A5GT 0-35	6A5 0-22	6C86 0-35			
1A5 0-40	6A7 0-40	6C16GA			
1B3GT 0-40	6AG6 0-50	1-25	6B97 0-40	12A7U 0-30	30C18 0-80
1C5GT 0-40	6A8 0-30	6C07 0-55	6B9T 0-40	12A7V 0-40	30F8 0-95
1G4GT 0-50	6AK5 0-35	6CH6 0-60	6B9T 0-40	12A7W 0-45	728A 16-00
1G6GT 0-50	6AK5W	6CL6 0-55	6B9T 0-40	12A7X 0-85	30FL1 0-75
1H5GT 0-50	6AC6 0-45	6C08 0-75	6B9T 0-40	12A7Y 0-35	807 0-50
1L4 0-20	6AK6 0-60	6C16 0-55	6B9T 0-40	12A7Z 0-35	811A 1-60
1N5GT 0-55	6AL3 0-43	6C16 0-55	6B9T 0-40	12A7Z 0-35	812A 3-50
1Q5GT 0-60	6AL5 0-20	6C16 0-55	6B9T 0-40	12A7Z 0-35	813 3-75
1R4 0-45	6AM5 0-35	6D3 0-50	6B9T 0-40	12A7Z 0-35	829B 3-50
1R5 0-40	6AM6 0-38	6D6 0-60	6B9T 0-40	12A7Z 0-35	831A 4-00
1R8 0-30	6AN8 0-55	6D6 0-60	6B9T 0-40	12A7Z 0-35	833A 17-00
1R5 0-30	6AQ5 0-38	6D6 0-60	6B9T 0-40	12A7Z 0-35	833A 17-00
1T4 0-30	6AQ6 0-45	6E5 0-60	6B9T 0-40	12A7Z 0-35	833A 17-00
1Y5GT 0-50	6AR5 0-45	6E5 0-60	6B9T 0-40	12A7Z 0-35	833A 17-00
1U4 0-30	6AR6 0-55	6E7 0-30	6B9T 0-40	12A7Z 0-35	833A 17-00
1U5 0-60	6AR11 1-25	6E7 0-30	6B9T 0-40	12A7Z 0-35	833A 17-00
1V2 0-50	6AS5 0-45	6F5 0-75	6B9T 0-40	12A7Z 0-35	833A 17-00
1X2B 0-50	6AS6 0-40	6F6 0-25	6B9T 0-40	12A7Z 0-35	833A 17-00
2A3 0-50	6AS7 0-85	6F7 0-40	6B9T 0-40	12A7Z 0-35	833A 17-00
2AF1 2-75	6AT6 0-35	6F7 0-40	6B9T 0-40	12A7Z 0-35	833A 17-00
2C2BA 0-60	6AUGTA	6F7 0-40	6B9T 0-40	12A7Z 0-35	833A 17-00
2C40 4-00	6AU2 1-25	6F7 0-40	6B9T 0-40	12A7Z 0-35	833A 17-00
2C51 0-45	6AU6 0-25	6F7 0-40	6B9T 0-40	12A7Z 0-35	833A 17-00
2CWA 0-70	6AV5GT	6F7 0-40	6B9T 0-40	12A7Z 0-35	833A 17-00
2E2 0-30	6AV6 0-30	6F7 0-40	6B9T 0-40	12A7Z 0-35	833A 17-00
2K25 0-30	6AWA 0-60	6F7 0-40	6B9T 0-40	12A7Z 0-35	833A 17-00
2X2 0-40	6AX4GTB	6F7 0-40	6B9T 0-40	12A7Z 0-35	833A 17-00
3A4 0-40	0-80	6F7 0-40	6B9T 0-40	12A7Z 0-35	833A 17-00
3A5 0-75	6AX5GT	6F7 0-40	6B9T 0-40	12A7Z 0-35	833A 17-00
3BP1 3-00	6J4	6F7 0-40	6B9T 0-40	12A7Z 0-35	833A 17-00
3D6 0-25	6B4G 1-00	6J5GT 0-30	6B9T 0-40	12A7Z 0-35	833A 17-00
3D21A 3-00	6B7 0-40	6J6 0-20	6B9T 0-40	12A7Z 0-35	833A 17-00
3Q4 0-50	6B8G 0-25	6J7 0-45	6B9T 0-40	12A7Z 0-35	833A 17-00
3Q5GT 0-50	6B8 0-25	6K8GT 0-80	6B9T 0-40	12A7Z 0-35	833A 17-00
3E4 0-35	6B8 0-25	6K7 0-25	6B9T 0-40	12A7Z 0-35	833A 17-00
4-250A 13-50	6B8 0-25	6K8 0-40	6B9T 0-40	12A7Z 0-35	833A 17-00
4-400A 16-00	6B8 0-25	6K8 0-40	6B9T 0-40	12A7Z 0-35	833A 17-00
4B92 4-50	6B9 0-50	6L7 0-40	6B9T 0-40	12A7Z 0-35	833A 17-00
4HA5 0-48	6BK4B 1-25	6L8 0-45	6B9T 0-40	12A7Z 0-35	833A 17-00
4THA 0-50	6BK7A 0-40	6LD20 0-50	6B9T 0-40	12A7Z 0-35	833A 17-00
5A84 0-60	6BL7GTA	6N7GT 0-45	6B9T 0-40	12A7Z 0-35	833A 17-00
5B/254M 2-50	6B8 0-80	6N7GT 0-45	6B9T 0-40	12A7Z 0-35	833A 17-00
5CPL 5-00	6B9 0-25	6Q 0-40	6B9T 0-40	12A7Z 0-35	833A 17-00
5D21 6-00	6BQGTB	6R7G 0-45	6B9T 0-40	12A7Z 0-35	833A 17-00
5R4G 0-75	6B7 0-85	6S2 0-40	6B9T 0-40	12A7Z 0-35	833A 17-00
5T4 0-35	6BQ7A 0-45	6S4 0-45	6B9T 0-40	12A7Z 0-35	833A 17-00
5V4G 0-45	6BR7 0-90	6S4 0-45	6B9T 0-40	12A7Z 0-35	833A 17-00
5W40T 0-50	6BR8 0-70	6S7 0-45	6B9T 0-40	12A7Z 0-35	833A 17-00

FULLY GUARANTEED



FIRST QUALITY VALVES

30C18 0-80	723A/B 7-00	CBL31 1-00	EAS0 0-20	ECL83 0-70	EL821 0-60	HBC91 0-40	PCF87 0-90	PY800 0-40	UBF80 0-40
30F8 0-95	728A 16-00	CL4 0-75	EA52 4-50	ECL84 0-55	EL822 1-30	HP93 0-40	PCF200 0-75	PY801 0-50	UBF89 0-35
30FL1 0-75	807 0-50	CL33 1-30	EABC80	ECL85 0-55	EL823 1-30	HP94 0-45	PCF201 0-75	PZ30 0-35	UBL1 0-60
30FL12 1-20	811A 1-60	CL31 0-35	0-35	ECL86 0-40	EM34 1-00	HK90 0-40	PCF800 0-80	QQV02-6	UBL21 0-65
30FL14 0-85	812A 3-50	DAP1 0-50	EAP42 0-55	ECLL800	EM71 0-80	HL23 0-50	PCF801 0-50	QQV03-10	UC28 0-40
30L1 0-40	813 3-75	DAP91 0-30	EAP801	2-00	EM80 0-45	HL23DD	PCF802 0-50	QQV03-125	UF41 0-60
30L15 0-85	829B 3-50	DAPF92 0-60	EP9 0-75	EM81 0-60	EM82 0-40	HL23DD	PCF803 0-50	QY4-250A	UF43 0-60
30L17 0-90	833A 17-00	DAPF93 0-45	EB34 0-20	EM83 0-60	EM84 0-35	HL42DD	PCF804 0-50	QY4-400A	UF85 0-40
30P19 0-85	837 1-00	DB3/91 7-00	EB91 0-20	EM85 1-00	EL92 0-50	HL92 0-50	PCF805 0-50	R18 0-60	UL1 0-85
30PL1 0-75	866A 0-75	DC90 0-50	EB93 0-50	EM87 0-70	EL94 0-50	HL94 0-50	PCF806 0-70	R18-250A	UL4 0-80
30PL13 0-93	872A 3-50	DF91 0-30	EB94 0-65	EM87 0-70	EL94 0-50	HL94 0-50	PCF807 0-50	RL8 0-80	UM4 0-50
30PL14 0-90	884 0-75	DF92 0-20	EB95 0-30	EM87 0-70	EL94 0-50	HL94 0-50	PCF808 0-55	S130 1-75	U11 0-75
30L15 0-85	892B 3-50	DF96 0-45	EB96 0-30	EM87 0-70	EL94 0-50	HL94 0-50	PCF809 0-55	S130F 1-75	UY1 0-50
30L17 0-90	893A 17-00	DF96 0-45	EB97 0-30	EM87 0-70	EL94 0-50	HL94 0-50	PCF810 0-50	S2 0-75	UY11 0-60
30P19 0-85	837 1-00	DF96 0-45	EB98 0-40	EM87 0-70	EL94 0-50	HL94 0-50	PCF811 0-50	S2 0-75	UY11 0-60
30PL1 0-75	866A 0-75	DF96 0-45	EB99 0-30	EM87 0-70	EL94 0-50	HL94 0-50	PCF812 0-50	S2 0-75	UY11 0-60
30PL13 0-93	872A 3-50	DF96 0-							

APPOINTMENTS VACANT

DISPLAYED SITUATIONS VACANT AND WANTED: £9 per single col. inch.

LINE advertisements (run-on): 50p per line (approx. 7 words), minimum two lines. Where an advertisement includes a box number (count as 2 words) there is an additional charge of 25p.

SERIES DISCOUNT: 15% is allowed on orders for twelve monthly insertions provided a contract is placed in advance.

BOX NUMBERS: Replies should be addressed to the Box number in the advertisement, c/o Wireless World, Dorset House, Stamford Street, London, S.E.1.
No responsibility accepted for errors.

Advertisements accepted up to
**WEDNESDAY, 12 p.m., 5th
APRIL** for the **MAY** issue,
subject to space being available.

INSTRUMENT TECHNICIANS

We have vacancies in our Instrumentation Laboratory for Staff Technicians with experience of the installation and operation of test measurement systems, incorporating mainly electrical/electronic instruments. Candidates should have practical ability, and a minimum educational standard of ONC or equivalent and should preferably have served an apprenticeship in electronics or as instrument mechanic.

The Company operate an excellent Pension Scheme and assistance will be given with removal expenses to Barrow.

This is not only an opportunity to work in one of the most technically advanced Shipyards in the U.K. but also to enjoy the amenities offered by the neighbouring Lake District National Park.

Applicants should write, stating qualifications, experience to date, age and present salary to:-

C. H. Purkiss, Staff Personnel Manager,
(Ref. S.149/IT/DQ), VICKERS LIMITED,
Barrow Shipbuilding Works, P.O. Box 6,
Barrow-in-Furness, Lancashire.

VICKERS leaders in marine technology
SHIPBUILDING GROUP

SURREY EDUCATION COMMITTEE GIPSY HILL COLLEGE

Kenry House, Kingston Hill, Kingston upon Thames

TECHNICIAN

required for the Educational Aids Department. Salary on Technical Scale 2/3, from £1,038 to £1,395 plus £105 London allowance. Qualification and experience in electronics are expected. An interest in photography or graphics would be welcome.

For further details apply to the Senior Administrative Officer at the College, telephone 01-549 1141.

1732

CHARLES AIREY ASSOCIATES LTD.

of 155 Knightsbridge, S.W.1.

Have an ever changing register of vacancies within the Electronics Industry.

Current vacancies include:

1. Development Engineers for Radio Paging Systems.
2. Design Engineer for Colour TV to £2,500.
3. Post Design Services Engineer HF, SSB Equipment to £1,800.
4. Installation/Maintenance Engineers for communal aerial systems or wired systems in Hotels.
5. Installation or commissioning Engineers for PABX crossbar strouger or TXE2 exchanges.

Whatever your skills or experience, write or telephone:

David Hilton or Judy Hortin
01-581 0286

1734

Electronic Test Engineers

Pye Telecommunications of Cambridge has immediate vacancies for Production Test Engineers.

The work entails checking to an exacting specification VHF/UHF radio-telephone equipment before customer delivery; applicants must therefore have experience of fault finding and testing electronic equipment, preferably communications equipment. Formal qualifications while desirable, are not as important as practical proficiency. Armed service experience of such work would be perfectly acceptable.

Pye Telecommunications is the world's largest exporter of radio-telephone equipment and is engaged in a major expansion programme designed to double present turnover during the next five years. There are therefore excellent opportunities for promotion within the company. Pye also encourages its staff to take higher technical and professional qualifications.

These are genuine career opportunities in an expansionist company, so write or telephone without delay for an application form to:

Mrs. A. E. Darkin,
Pye Telecommunications Limited,
Cambridge Works, Haig Road, Cambridge.
Telephone: Cambridge 51351 Ext. 355

 Pye Telecommunications Ltd

Shore jobs for Radio Officers.

If you'd like a job ashore, at a United Kingdom Coast Station, the Post Office will start you off on £1,252.13 – £1,576.60, depending on age, with annual rises up to £2,145.75 (compulsory pension contributions are included in these amounts). In addition you would receive payments that can be as much as £300 or more a year for attendances during evenings, nights, Saturday afternoons and Sundays. Opportunities also exist for overtime.

There are good prospects for promotion to higher posts.

You will need to be 21 or over, with a 1st Class Certificate of Competence in Radiotelegraphy issued by the Postmaster General, or the Ministry of Posts and Telecommunications, or a

Radiocommunication Operator's General Certificate issued by the Ministry of Posts and Telecommunications, or an equivalent certificate issued by a Commonwealth administration or the Irish Republic.

Find out more by writing to:
The Inspector of Wireless Telegraphy,
IMTR, Wireless Telegraph Section (WW),
Union House, St. Martins-le-Grand,
London, EC1A 1AR.

Post Office
Telecommunications

Electronics Service Engineer for work on digital/analogue data recording systems

EMI Electronics Limited has a vacancy in its Installation and Maintenance Division for an Engineer to be responsible for the installation, commissioning and maintenance of digital/analogue data recording systems. He will be based at Hayes, Middlesex, but the position will involve work in the field in the U.K. as well as occasional overseas visits.

Applicants, aged 25-45, should have reached H.N.C. Electronics standard, and should be conversant with tape transport mechanisms.

Starting salary will be up to £2000.00 per annum, assistance will be given with removal expenses. Company benefits include free Life Assurance and a contributory Pension Scheme. Please apply in writing, stating brief career details, or ring :-

EMI

R.C. Dwyer, Personnel Department,
EMI Limited, Hayes, Middlesex.
Tel. No. 01-573 3888 Ext. 2887.

1651

International leaders in Electronics, Records and Entertainment

UNIVERSITY of KENT AT CANTERBURY

Applications are invited for the posts of **EXPERIMENTAL OFFICER** and **TECHNICIAN** in **PHYSICS** for work on the development, construction and maintenance of equipment associated with research projects. Experience in electronics would be an advantage. A degree would be desirable but not essential for the post of Experimental Officer and a national diploma qualification desirable but not essential for the post of Technician. Appointments initially for one year with the possibility of renewal, on scale £990-£1902 for the post of Experimental Officer and £1041-£1410 for the post of Technician.

Application forms and particulars from the Assistant Registrar, Faculty of Natural Sciences, Chemistry Building, The University, Canterbury, Kent, quoting Ref. A.5/72 for the post of Experimental Officer and T.72/1 for the post of Technician. Closing date 31st March.

1715

GRANADA TELEVISION TRAINEE SOUND ENGINEERS

We are looking for bright young men to train as Assistant Engineers (Sound) in our Manchester Studios. The people we appoint will be electronics engineers in the age range 20 to 25 years, possessing at least a physics 'A' level or an ONC in physics or electrical engineering. Although short on practical experience at a professional level, they will be knowledgeable about the theory of sound studio techniques and equipment. They will also be able to demonstrate an informed interest in some field of music.

Appointments will be at a salary of £1,670 per annum, increasing to £2,117 upon satisfactory completion of a nine month training period.

We offer excellent working conditions, including four weeks paid holiday and generous Granada Group pension and life assurance benefits.

Write with full details to:

Robert Connell
Granada Television
MANCHESTER M60 9EA
1708

ROYAL HOLLOWAY COLLEGE (University of London) Englefield Green, Surrey.

SENIOR INSTRUMENT TECHNICIAN

for operation, maintenance and repair of scientific instruments. Salary on the scale £1,398 — £1,707.

Applications together with the names and addresses of two referees should be sent to the Personnel Officer. 1721

NEVE

require an

Electronic Design Engineer

to work on advanced circuits for professional audio systems of which previous experience is essential. A thorough background in the design of linear systems is necessary, and a familiarity with analogue/digital data processing techniques desirable. A good ear and an appreciation of music would be an advantage. The successful applicant must be able to act on his own initiative. Good salary—negotiable at interview.

THE SOUND OF NEVE IS WORLD WIDE

Apply to:

Personnel Manager,
NEVE ELECTRONIC LABORATORIES
LIMITED

Melbourn, Royston, Herts.

Telephone: Royston 60776

1742

Benefit from the TV Cassette Revolution

In the fields of entertainment, education and industrial training, the future for the Electronic Video Recording System is unlimited. The EVR Partnership, consisting of ICI and CIBA/GEIGY, has established up-to-date facilities for cassette production at Basildon and the people who join us now will benefit from our growth and share in our success.

SENIOR MAINTENANCE ENGINEER

£2,420-£2,900 p.a. + shift pay.

To be responsible for the maintenance of a wide range of highly sophisticated electronic equipment with the assistance of a team of maintenance engineering staff. A minimum qualification of an HNC or its equivalent, together with several years experience of the maintenance of television equipment is essential. Knowledge of Quadruplex Video Tape Recorders and Flying Spot Telecine equipment would be advantageous.

ELECTRON BEAM RECORDER ENGINEER

£2,000-£2,400 p.a. + shift pay.

To be responsible for the maintenance of Electron Beam Recorders used to produce master film from television signals. Applicants must be qualified to at least HNC level and have experience in the design or maintenance of video equipment using modern semiconductor circuit techniques. Some experience of, or recent training in television engineering, electron physics, vacuum engineering, photography and servo systems would be an advantage. Detailed training will be given to well qualified engineers having a very good knowledge of the principles, but lacking in practical experience of some of the techniques mentioned above.

Video Recorders and Telecine Equipment Staff

ENGINEER

£2,000-£2,400 p.a. + shift pay.

To be responsible for the setting up, first line maintenance and operation, including some editing of video tape recorders and telecine equipment. Experience of the operation or maintenance of similar equipment and the good understanding of colour television principles is essential. An HNC or its equivalent is desirable.

ASSISTANT ENGINEER

£1,600-£1,960 p.a. + shift pay.

To work with the Engineer on the same operational tasks. A minimum qualification of ONC or its equivalent, together with a good understanding of colour television principles is essential. Some previous experience of the operation or maintenance of television studio equipment is desirable.

All these posts involve shift work at our new Processing Station at the new town of Basildon. Salaries, working conditions and opportunities for promotion are excellent and for most of the people who join us, there are houses available to rent.

Suitably experienced people are invited to write, quoting Ref: MM4/WW, giving details of their qualifications and experience, to:



The Personnel Manager,
EVR Processing Station,
Christopher Martin Road,
Basildon, Essex.

An ICI and CIBA/GEIGY Partnership

Opportunities with Redifon in Radio Communications

Experienced Test Engineers are invited to write to Redifon with regard to vacancies in our Test Department at Wandsworth.

The salary range for these positions is £1,287-£1,749 plus. The Company is engaged in the design and manufacture of a wide range of radio communications and allied equipment from military pack-set to broadcast transmitter, including communications receivers, M.F. beacons, teleprinter terminals, complete radio office installations for the Merchant Marine and mobile H.F. S.S.B. stations. Our Test Engineers have sound technical knowledge coupled with good practical experience in the alignment and test of H.F. and V.H.F. Communications equipment.

The work is varied and interesting and offers excellent opportunity to broaden experience in semiconductors S.S.B. and Frequency Synthesis.

Please write to: **G. F. Rice, Quality Manager (Dept. P) Redifon Telecommunications Ltd., Broomhill Road, Wandsworth SW18 4JQ or telephone The Recruitment Officer 01-874 7281**

REDIFON

A Member Company of the Redifusion Organisation



1970

TEST ENGINEERS

The leading U.K. Manufacturers of high grade T.V. monitors and ancillary T.V. studio equipment require Test Engineers for their rapidly expanding test department.

Situated in the Berkshire town of MAIDENHEAD the company offers pleasant working conditions, good salaries, and a friendly environment.

Duties will cover the testing of our complete range of equipment.

Previous experience on television equipment is not essential but candidates must have a thorough knowledge of electronics and testing procedures.

Reply to:

PROWEST ELECTRONICS LTD.,

Boyn Valley Road, Maidenhead, Berks.

Telephone: Maidenhead 29612

1740

H.M. GOVERNMENT COMMUNICATIONS CENTRE

has vacancies at Hanslope Park for

TELECOMMUNICATION SCIENTISTS/ENGINEERS

Posts are available in teams engaged in the development and trials of communication equipments. Experience in Audio, RF, VHF, UHF or Digital techniques is required. **Age:** 25-35 years.

Qualifications: A Degree in Telecommunications or Electronics is preferred, HND or C & G Full Technological Certificate acceptable. **Experience:** 3-5 years work in communication or electronic design. **Salary:** Depends on qualifications and experience. Normally in the range of £1,810-£2,350 p.a. but a few Senior posts are available for exceptional candidates. **Applications:** with personal details, qualifications and experience to:

Personnel Officer, HMGCC, Hanslope Park, Wolverton, Bucks.

1704

FOREMOST IN THE UNITED KINGDOM

IN CONSTANT TOUCH WITH EVERY EMPLOYER OF EXPERIENCED ELECTRONICS ENGINEERS

Our professional placement service is specialised, confidential and completely free

Phone us at any time or write quoting EW 103



ELECTRONICS APPOINTMENTS LTD

NORMAN HOUSE
105, 109 STRAND, LONDON WC2
TEL: 01-836 5557

HI-FI FANATIC NEEDED

We need a Readers' Queries Manager who can deal with a wide variety of readers' problems concerned with hi-fi. The applicant must have a detailed knowledge of current audio and radio products both from the technical and buying viewpoint. He will work in conjunction with two of Britain's leading hi-fi magazines.

The ideal candidate will be under 30 and will have had experience of the hi-fi industry from either the retailing or the production sides. He must be capable of putting his ideas on to paper in a brief and concise fashion and must also be able to show that he is an enthusiast for high quality sound reproduction.

Salary is negotiable. Write to Box No. 1713.

BUSINESS OPPORTUNITY

Earn a substantial extra income through a fascinating part-time business of your own that you could share with your wife and operate from your own home. This is an outstanding business opportunity with rewards exceeding £5000 per annum at the higher levels. We are looking for organisational and managerial ability. Telephone for an appointment

VISTA MARKETING MAIDENHEAD 28754 1728

Small specialist electronic manufacturing company requires

TEST ENGINEER

with good basic understanding of transistor pulse circuitry. Interesting and varied work. Commencing salary around £1,500.

Hounslow 01-570 4065 1730

University of Newcastle upon Tyne Department of Photography and Teaching Aids Laboratory Film and Television Section

ENGINEERING MANAGER—TV and FILM

Required, as soon as possible, to assume overall responsibility for the operational availability of black and white studios and mobile unit, advise on setting up, maintaining and operating additional small scale facilities in a number of separate teaching departments, and to organise the training of academic and technical staff within the University, and occasionally from elsewhere, in the operation of CCTV equipment. A degree or HNC with endorsement or similar qualifications are desirable, with studio and O.B. experience with the BBC or ITV or a large CCTV studio operation in a responsible operational engineering role in both sound and vision. The ability to undertake practical CCTV and helical scan VTR engineering work personally during programme recording and editing is essential. Salary on the scale £2,040 to £3,003 (to be revised under recent salary award). Membership of F.S.S.U. required.

Applications (3 copies) giving full details of qualifications and job experience with the names of three referees should be sent not later than 29th March, 1972 to The Registrar, The University, Newcastle-upon-Tyne NE1 7RU, from whom further particulars may be obtained. Please quote reference W.W. 1718

SITUATIONS VACANT

REDIFON TELECOMMUNICATIONS LTD., require fully experienced TELECOMMUNICATIONS TEST ENGINEERS and ELECTRONICS INSPECTORS. Good commencing salaries. We would particularly welcome enquiries from ex-Service personnel or personnel about to leave the Services. Please write, giving full details to—The Recruitment Officer, Redifon Telecommunications Ltd., Broomhill Road, Wandsworth, S.W.18. [21

TECHNICIAN with some experience of electronic engineering required for postgraduate department concerned with experimental media. Interest in development of light and sound visual media an advantage. Starting salary between £1,200-£1,250pa according to qualifications and experience. Please send full details of age, training and previous experience to the Assistant Registrar (Administration), Royal College of Art, Kensington Gore, London, SW7 2EU. [1706

SITUATIONS WANTED

ENGLISH Radio Technician, ex-R.E.M.E., and Danish Electronic Technician interested in spare-time service department, based in Denmark, for an electronic firm exporting to Europe. Box No. 1732.

ARTICLES FOR SALE

BRAND NEW TO FULL SPECIFICATIONS ALL DEVICES GUARANTEED

10p each: OC71, OC45. 15p each: ME1001, ME1002, ME2001, ME2002, ME4001, ME4101, ME4103, ME4104, ME9003. 17p each: ME4002, ME4102, ME6003. 20p each: ME0404, ME0404-1, ME0413, ME0414, ME4003, ME6001, ME6002, ME6101, ME9001, ME9002, ME9021, ME9022. 22p each: ME0404-2, ME9001. 23p each: ME0483, ME1100, ME1120, ME3001, ME3011, ME3102, ME6002, ME9003. 24p each: ME0411, MT0414, MT4104. 25p each: ME0401, ME0402, ME0412, ME0463, ME0491, ME0492, MT0413, MT4103. 27p each: ME501, ME3002, MT0404, MT6003. 30p each: ME0461, ME0462, MT0404-1, MT6001, MT9003. 34p each: ME502, MT0404-2, MT3011, MT6002. 35p each: ME503, ME511, MT8121, MT0411, MT0403, MT4101, MT9002. Quantity Price List available for industrial and trade users. CASH WITH ORDER. ELECTRONIC SUPPLIES, P.O. BOX 218, LONDON NW.

ARVAK ELECTRONICS. 3-channel sound-light converters, £17. Strobes, £16. Rainbow Strobes, £132.—74 Bedford Avenue, Barnet, Herts. 01-449 1268. [19

A QUANTITY of new EMI Vidicons type 9677C and 9677M, 35% off list price, also a number of Grundig CCTV Cameras, Pan & Tilt unit, various lenses, GPO approved line transmission amplifiers for CCTV along standard GPO lines. Also two broadcast standard 14in. Monitors. Tel. 794 7350 during office hours. [1701

AUDIO MIXER UNITS AND KITS. Partridge Electronics, Dept. WW12, 21-25 Hart Road, Thundersley, Benfleet, Essex. Tel. South Benfleet (STD 037-45-3256). For more details see W.W. March issue. [22

ARMATURE winding machine. Automatic winding by electrical and hydraulic programme, fitted with electronic digital counter. To clear £30. Also "QUICK-WAY" armature winding machine with manual switching. To clear £25.—102 Parrswood Road, Withington, Manchester 20. Tel. 061-224 3553. [1872

BATTERY CHARGERS. Heavy-duty 15amp model 240 volt A.C. will charge 6 volt, 12 volt, 24 volt batteries at 5 variable charging rates. Fitted 0-20amp meter, fuse, variable control on/off switch, all leads. Completely ready for use. Guaranteed "MALDEN" Unit sent by return B.P.S. £16-50.—Malden Transformers, 134 London Road, Kingston-on-Thames. Tel. 546-7634. [1723

COLOUR TV Camera (Studio), complete with lenses, tubes and cables. In perfect working order. Bargain £1,000. 01-229 0898 day or 01-907 0548 evening. [25

COLOUR, UHF and TV SERVICE SPARES. SPECIAL OFFER VARICAP Electronic tuned transist. UHF tuners ELC 1043 incl. connection data £4-50 P/P 25p. Chrominance Delay Line DLI £1-95 P/P 25p. Luminance Delay Line £1-30 P/P 25p. Colour Monitor Decoder Panels designed to BBC standards incl. circuit data, Pal Filter and Delay £6. Chrominance £6, Luminance £4-50. Encoded video input £2-50, P/P 25p (or set of 4 £17-50 P/P 35p). Also quantity Colour TV Camera panels and astute manufacturers' surplus. Colour receiver panels. Plessey Colour scan coils £6-75 P/P 35p. Convergence coils £3-80 P/P 25p. Blue lateral £1-25 P/P 10p (or complete set £10 P/P 50p). Mullard type colour Scan coils £3-50 P/P 35p. Latest convergence coils for electronic control of static convergence £1-75 P/P 25p. Leading Brit. maker Colour LOPT assy. incl. EHT output and focus control £3-50 P/P 35p. Integrated transist. decoder unit incl. circuits £1-25 P/P 10p. Convergence board coils AT4040 25, 55, 79, 25p P/P 10p. B9D valve bases for colour valves and PL500 series 12p P/P 5p UHF tuners transist. incl. slow motion drive, indicator £3-95. CHF transist. push button £5-25. Knobs 40p. UHF/VHF basic integrated tuner £3-95. Cydon UHF valve tuners £1-50. all tuners P/P 25p. UHF list available on request. Transist. UHF/VHF IF panels £4-75 (or salvaged £2-50) P/P 25p. MURPHY 600/700 series complete UHF conversion kits incl. tuner, drive assy., 625 IF amplifier, 7 valves, accessories housed in cabinet plinth assembly £7-50 P/P 50p. SOBELL/GEC 405/625 Dual standard switchable IF amplifier and output chassis incl. cct. £1-50 P/P 30p. PHILIPS 625 IF amplifier panel incl. cct. £1-00 P/P 25p. VHF turret tuners AT7650 incl. valves for KB Featherlight, Philips 19TG170, GEC 2010 etc. £2-50, PYE miniature incremental for 110 to 830, Pam and Invicta £1-95. A.B. miniature with UHF injection suitable KB, Baird, Ferguson, 75p, Ekco, Ferranti, Plessey push button with UHF injection £1-00, all tuners P/P 25p. New fireball tuners Ferguson, HMV, Marconi £1-90 P/P 25p. Large selection LOPTs, Scan coils, FOPTs available for most popular makes. PYE/LARGEAR transist. Masthead UHF Booster £5-25. Power unit with Lagbear "Triest" 3 unit UHF/VHF distributor amplifier, mains operated £6-50 P/P 25p. MANOR SUPPLIES, 172 WEST END LANE, LONDON, N.W.6 (No. 28, 59, 159 Buses or W. Hampstead Tube Station). MAIL ORDER: 64 GOLDERS MANOR DRIVE, LONDON, N.W.11. Tel. 01-794 8751. [60

RADIO OPERATORS

DO YOU HAVE
PMG I, PMG II, MPT, 2 YEARS OPERATING EXPERIENCE?

POSSESSION OF ONE OF THESE QUALIFIES YOU FOR CONSIDERATION FOR A RADIO OPERATOR POST WITH THE COMPOSITE SIGNALS ORGANISATION

On satisfactory completion of a 7 month specialist training course, successful applicants are paid on scale rising to £2000 pa; commencing salary according to age—25 years and over £1453 pa. During training salary also by age, 25 and over £1152 pa with free accommodation.

The future holds good opportunities for established (ie pensionable) status, service overseas and promotion.

Training courses commence every January, April and September. Earliest possible application advised.

Applications only from British-born UK residents up to 35 years of age (40 years if exceptionally well qualified) will be considered.

Full details from:

Recruitment Officer
Government Communications Headquarters
Room A/1105
Oakley Priors Road
CHELTENHAM Glos GL52 5AJ
Telephone: Cheltenham 21491 Ext 2270

92

BRENTFORD ELECTRIC LIMITED

require the following personnel:—

AN ELECTRONICS DESIGN ENGINEER

to augment an enthusiastic team engaged on a variety of projects in power regulation. Applicants should be Graduate Electronic Engineers with several years industrial experience and preferably some familiarity with closed loop controls, logic circuits, Thyristor circuits or operational amplifiers.

Hours: 9.00 a.m. to 5.10 p.m. Mondays to Thursdays, and
9.00 a.m. to 4.40 p.m. Fridays. (37-hour week)

Apply: Personnel Services,
Brentford Electric Limited,
Manor Royal, Crawley, Sussex. Tel: Crawley 27755 1703

★ **ARTICLES FOR SALE** ★

RADIO TELEPHONES

50 STORNO CQM33C FM 12v 68-88MHz .. £16	25 PYE RANGER 2202 AM 12v 68-88MHz £20
10 COSSOR I03BE FM 12v 88-108MHz .. £16	10 PYE VANGUARD AM25B 12v 68-88MHz £40
4 COSSOR 144AE-AM 12v 68-88MHz .. £16	10 PLESSEY PTR61E AM 12v 116-132MHz £16
2 COSSOR 104E2 AM 12v 2-8 mHz .. £100	6 STC STR9Z AM 24v 115-145MHz .. £100
2 COLLINS 185-4C AM 24v 2-18MHz .. £200	10 STC STR12D AM 24v 118-131MHz .. £100

TI154-R1155 & SPARES. LARGE QUANTITY EXPECTED IN DURING MARCH.

CRYSTALS

Over 20,000 in stock between 2 & 19MHz, most styles available; from £1 each. Terms. Cash with order. Retail shop counter sales & mail order (carr. inc. above). S.A.E. all enquiries.

BAGINTON ELECTRONICS

MARKET CORNER, BAGINTON, COVENTRY, WARKS.
Also at Coventry Airport. Phone Coventry (0203) 302668
1745

WITWORTH TRANSFORMERS

Line output transformers

Manufacturers of the largest range in the country. All makes supplied. Free catalogue.

Modern BAIRD, BUSH, GEC, PHILIPS Replacement types ex-stock.

For "By-return" service, contact your nearest Depot: Phone: 01-948 3702

TIDMAN MAIL ORDER LTD.

Dept. W.W., 236 Sandycombe Road, Richmond, Surrey
VALVES, TUBES, CONDENSERS, RESISTORS, RECTIFIERS and FRAME OUTPUT TRANSFORMERS also stocked.

CALLERS WELCOME. 90

GUARANTEED COMPONENT BARGAIN

C90 COMPACT CASSETTE British manufacturer, 1 at 54p, 3 off 50p each, 10 off 46p each.

BC107/8/9 9p; BC147/8/9 10p; BC157/8/9 10p; BC142/3 30p; 40361 38p; 40362 42p; 2N3055 50p; BYZ13 21p.

Tantalum capacitors—wide range—quantity inquiries invited

Free UP p. & p. above 50p min. order. Send or telephone 01-556 0340 for lists.

GOLDTECH ASSOCIATES (Main Order), 27 Hoop Lane · London · NW11 8JN 1747

EX-RENTAL TVs (UNTESTED)

Complete with 13 channel tuners. Good cabinets. Carriage £1-50 extra.

- 19" 21" slimline (110" tube) .. £5-00
- 23" allinline .. £7-50
- 19" BBC 2 sets .. £14-50

Tubes Ex-Equipment Tested

SINGLE PANEL

- 19"/21" any type .. £3-00
- 23" any type .. £4-00

TWIN PANEL (BONDED)

- 19" bonded .. £5-00
- All tubes add £1 carriage.

VALVES EX EQUIPMENT

EB91	5p	30L15	12½p	PL36	22½p
EBF89	12½p	30P4	12½p	PL81	17½p
ECC82	12½p	PC97	17½p	PY81	15p
ECL80	7½p	PCF86	17½p	PY800	15p
EF80	12½p	PC84	7½p	PY82	7½p
EF85	12½p	PCF80	7½p	PY83	22½p
EF183	12½p	PCC89	12½p	U191	17½p
EF184	12½p	PCL85	22½p	6F23	17½p
EY86	17½p	PCL82	17½p	30PL1	22½p
30PL13	20p	PCL86	17½p	30P12	20p
630LZ	12½p	PCL83	12½p	30F5	10p

Add 2½p per valve p. and p. Orders over £1 p. and p. free

UHF TUNERS

For Ferguson 850, 900 chassis, adaptable for most U.H.F. chassis £2-50, p. & p. 50p.

SLOT METERS

Smiths reconditioned switchmaster MKIII. Decimalized. Perfect working order. 12 for £25 delivered. For sample send £2-50 c.w.o.

TRADE DISPOSALS (Dept. T.S./W.W.),
Thornbury Roundabout, Leeds Road, Bradford, Yorks. (Tel. 0274/665670) 91

PLAYBACK MACHINES £3

These machines made by Clarke & Smith were formerly used as "Talking books for the blind" and contain a sensitive (20µV) amplifier with tone and volume controls using 2x ECC83, EL84, E280, also incorporating a tone detector. Output is 2 watts into 7 x 4" 3 ohm speaker, with jack socket for extension. Original deck with solenoid operation uses single 4-pole AC motor, and the unit is enclosed in a polished wood cabinet 13 1/4 x 14 1/4 x 9", ONLY £3+£1 carr. Ferrograph simultaneous double channel tape recorder in cabinet or can be rack mounted £50. Dowe 1201B stroboscope £35 (£1). Marconi TF144G Sig. gen. 85kHz-25MHz £12 (£2). Doran DC potentiometer 10µV-1.8V £15 (£1). Power unit 100-136V in 3V steps at 1A, standard mains i/p £2 (80p). Wavemonitor G302, scope needing PSU, £6 (£2). TF517F £12 (£1). TF885, immaculate £30 (£2). NEW COMPONENTS: 12x BC108 £1; 4x 2N3055 £2; 7x BFY51 £1; 5x 1000µV/50V £1; 10x 470µF/25V £1; 7x 1000µF/25V £1; 8µF/2500V, boxed £2 (40p). Ferric Chloride crystals in sealed 1 lb. packs, 30p (15p), 10 lbs. £2-50 (40p). Resistors: 1% 3p; 2% 2p; 5% 1p. (Postage in brackets). SURPLUS COMPONENTS AND EQUIPMENT PURCHASED. LIST FREE. Hotline to GREENWELD: 01-777 2001.

GREENWELD ELECTRONICS (WV),
24 Goodhart Way, West Wickham, Kent

CALLERS WELCOME,
PLEASE PHONE FIRST

1738

CUT THE COST OF SERVICING WITH LONG LIFE

TOSHIBA VALVES

LOOK AT THESE PRICES AND MAKE YOURSELF POUNDS MORE PROFIT

Type	Goods	P. Tax	Total
EB.91	14½p	5p	19½p
ECC.82	22½p	7½p	30p
EF.80	20½p	7p	27½p
EF.183	28p	9½p	37½p
EF.184	28p	9½p	37½p
EH.90	25½p	8½p	34p
PCC.189	31½p	11p	42½p
PCF.80	25½p	8½p	34p
PCF.86	30p	10½p	40½p
PCF.801	32½p	11p	43½p
PCF.802	31½p	11p	42½p
PCL.82	25½p	8½p	34p
PCL.84	25½p	8½p	34p
PCL.85	28p	9½p	37½p
PCL.86	28½p	10p	38½p
PFL.200	39½p	13½p	53p
PL.36	40½p	14p	54½p
PL.84	21p	7p	28p
PL.504	42p	14½p	56½p
PL.508	47½p	16p	63½p
PL.509	72p	24½p	96½p
PY.500A	47½p	16p	63½p
PY.800	22p	7½p	29½p

Subject to settlement discount 5 per cent of Goods content 7 days and 2 per cent monthly Toshiba valves are being used extensively by major national companies. Here is your opportunity to take advantage of the savings to be made.

Write or 'Phone

COMBINED PRECISION COMPONENTS (PRESTON) LTD.
3 Moor Park Avenue, Preston, PRI 6AS, Lancashire. Tel. Home Sales Division, Preston 0772 56347. Export Division, Preston 0772 54157

New Price List from 20th August 82

G.W.M. RADIO LTD.

D11/13. Approx. 10 tons of ancillary equipment including Aerial Matching Units, Operators Control Units, etc. HM100/150 a quantity of units and spares. High Voltage variable vacuum capacitors by Jennings, types UXCF and VMHC in various capacities. All in good unused condition. Enquiries invited.

Mr. L. C. Grout, 40/42 Portland Road,
Worthing, Sussex. Tel.: 0903 34897 1739

PRECISION

POLYCARBONATE CAPACITORS

Fresh stock — Fully tested

Close tolerance capacitors by well-known manufacturer. Good stability and very low leakage. All 63V d.c.

0.47µF:	±5% 30p;	±2% 40p;	±1% 50p
1.0µF:	±5% 40p;	±2% 50p;	±1% 60p
2.2µF:	±5% 50p;	±2% 60p;	±1% 75p
4.7µF:	±5% 70p;	±2% 90p;	±1% 115p
10µF:	±5% 110p;	±2% 140p;	±1% 180p
15µF:	±5% 160p;	±2% 210p;	±1% 270p

P.E. SCORPIO IGNITION SYSTEM

Special 1µF 400V a.c. capacitor for use in place of two existing 0.47µF 1000V d.c. units (C6 and C7). Does the job of both. Size 2" x 2". Price 45p each. Post and packing 5p on all orders.

V. ATTWOOD

P.O. Box 8, ALRESFORD, HANTS. 1726

ELECTRONIC EQUIPMENT

- Hewlett Packard 400D Valve Voltmeter .. £50
- Hewlett Packard 200D Wide Range Oscilloscope 5Hz-600KHz .. Each £45
- Hewlett Packard 130C Oscilloscope 200uV/cm Sensitivity .. £100
- Hewlett Packard 203A Variable Phase Function Generator 0-00005Hz-60KHz. Sine and Square Wave .. £250
- Hewlett Packard 3734A 5MHz 5 digit Multi-function Counters .. Each £80
- Hewlett Packard 211A Square Wave Generator 1Hz-1MHz .. £50
- General Radio 1554A Sound and Vibration Analyser .. £150
- General Radio 1564 Sound and Vibration Analyser .. £250
- General Radio 1562 Sound level Calibrator .. £85
- General Radio 1350-A Generator-Recorder Assembly .. P.o.A.
- General Radio 1142-A Freq Meter and Discriminator 5Hz-15MHz .. £65
- Solartron 546 Oscillator 25Hz-500KHz .. £30
- Solartron D9095 Stabilised amplitude Generator .. £50
- Solartron CD1015 Oscilloscope .. £50
- Solartron CD1012 Oscilloscope B.W. 25MHz .. £65
- Solartron CD1400 Oscilloscope D/B B.W. 15MHz £170
- Thorn WJ12 Off Air Television Receiver .. £45
- Advance 78B A.C. Millivoltmeter .. £25
- Advance 77B A.C. Millivoltmeter .. £25
- Gresham Lion Wave Form 625 Line Pulse and Bar C. Lyons PG33 Pulse Generator .. £200
- Radiometer MS27de FM-AM Standard Signal Generator 0.3 to 240MHz. Virtually new .. £325
- Airmec 859 Auto continuity tester .. £75
- Wayne Kerr A321 Wave Analyser 20Hz-20KHz .. £125
- Tektronix Plug-in CA : L : K : B : D : 3A1 : 3B3, etc. .. from £25
- Hewlett Packard Plug-in 1732A .. £25
- Epsilon MRI200 Brand New Magnetic Data Recording Systems. (Send for descriptive leaflet) .. P.o.A.

Other equipment available includes Vibration Equipment, Tape Decks, P.S.Us., Printers, etc.

GOOD QUALITY INSTRUMENTS ALWAYS NEEDED ALSO ENVIRONMENTAL EQUIPMENT. CONSULT US BEFORE YOU DISPOSE OF YOUR SURPLUS EQUIPMENT.

Equipment for hire at Competitive Prices. Export Buying Agents of Instrumentation and Research Equipment for Overseas Customers.

MARTIN ASSOCIATES

Myrorian, Greensward Lane, Nr. Reading, Berks. Tel: ARBORFIELD CROSS 610 or WEST FOREST 4896 1746

NEW BRANDED LOW COST FULL SPEC

FOR IMMEDIATE DELIVERY

1-24	25-99		1-24	25-99
P.	P.		P.	P.
7400	16 14		7473	36 34
7403	16 14		7474	36 34
7410	16 14		7475	41 39
7413	26 24		7476	36 33
7420	16 14		7490	69 64
7430	16 14		7492	69 64
7440	16 14		74121	53 48
7450	16 14		74141	90 85

ELEKTRON SUPPLIES

259 CARDINGTON RD., BEDFORD

TERMS C.W.O. FREE POSTAGE OVER £5

FOR SMALLER ORDERS ADD 7P

QUOTES GIVEN : MONEY REFUND GUARANTEE

Trampus electronic

- Numerical indicator 3015F 0.9DP, 5v 8mA bar £1-89.
- Socket 35p. 7447 Driver £1-29. Nixie 180v 0.9 DP £1-25.
- Light Emit Diodes. Visible red 2v 67p. Infra-red £1-49.
- IC Photo Detector/amp 44p. SCR 400v 4a 67p.
- 709 31p. 741 34p. 3.5W AF IC amp £1-49. TTL Gates 15p.
- 74N Full range available. DIL Sockets 14/16 Pin 12p.
- BC 107/8/9 8p. BC177 12p. ME 0404-2 18p. 2N3055 49p.
- Zeners 400mW 12p. 1a Rects. 50v 5p. 400v 9p. Data 7p.
- FREE Lists a.e. All brand new, money back guarantee. C.W.O. P.P. U.K. 7p. P.O. Box 29, Bracknell, Berks. 1727

TRIACS-ISOLATED CASE


- No. 410 10A, 400V, TO-220 plastic £1-15
- No. 1415 15A, 400V, TO-220 plastic £1-95
- No. 430 30A, 400V, TO-3 surface mtg. £4-30
- No. 406 6A, 400V, TO-5 non-isolated £0-87
- No. 425 25A, 400V, Stud non-isolated £3-00
- No. 031 ±30V trig. diode. Pk. of 5 £1-00
- Discount: 10-29 10%; 30-99 15%.
- Bulk prices (100-100K) on request.
- P. & P. 7p under £5. C.W.O. only. 48 hr. service.

OPTTECH ELECTRONICS
Stammore, Middx. HA7 4JP 1722

WW-098 FOR FURTHER DETAILS

A UNIQUE CONVERTIBLE TROLLEY

FROM THIS TO THIS IN SECONDS

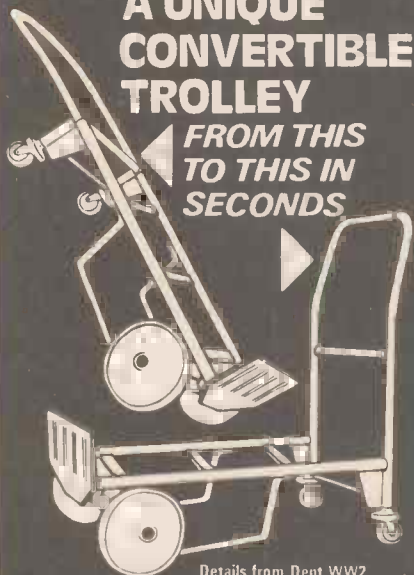

Details from Dept WW2

Sheffield Steel Products Ltd.
Sheffield S9 1RU. Tel: (0742)41235

FOR SALE

- 1—Fernseh 16 mm Telecine machine including Bauer projector, spares and film winder.
- 1—Intertherm R.F. Generator, type 1P60/14/30M serial No. 1158, 30KW, 350/550 KHz.
- 1—Plating through hole equipment ref. 286/1 with 400 amp rectifier system, one tank No. 6 and No. 8 tank.
- 1—Liquid Helium plant.
- 1—300Line board telephone exchange. Various surplus stores items. Price—subject to negotiation.

Contact: **J. J. Seymour,**
Horley 5544 1712

BEAT THIS FOR VALUE. Guaranteed tested and individually boxed ex-equipment PL504's at 17p each. PL36, PCL82, PCL83, PCL84 at 10p each. P&P 4p per valve, 12 or over 24p per valve, orders over £3 free. Other types available, S.A.E. list. SAME DAY SERVICE. L. & D. Components Ltd., 71 Westbury Ave., London, N22 6SA. 01-888 2701. [1709]

BUILD IT in a DEWBOX quality plastics cabinet 2 in. X 2 1/2 in. X any length. D.E.W. Ltd. (W.), Ringwood Rd., Ferndown, Dorset. S.A.E. for leaflet. Write now—R'ght now. [76]

COLOUR TV I.C.'s, full range. Countless bargains, i.e. AD161/162 pair 60p. F.M. modules as before. Set MPX Coils 75p. Set AM Coils plus ferrite aerial and oscillator £1. Set F.M. I.F.'s (6) £1. P&P 6p. Full details in our new illustrated 1972 Catalogue 20p post free. M.P. Dept., Chromasonic Electronics, 56 Fortis Green Road, N10 3HN. [20]

EX. BBC outside broadcast equipment consisting of a line transmission amplifier, mixer and power supply £95 one, 2 new Grundig light beam telephones, £180. Tel. 794 7350 during office hours. [1702]

LADDERS, 20ft., £7-80. carr. 80p. Leaflet, Callers welcome.—(Dept. W.W.W.), Home Sales, Baldwin Road, Stourport, Worcs. Tel. 02-993 5222 order C.O.D. Answer phone installed. [26]

M. G. SCROGGIE (Cathode Ray) disposing of lab. Brenell Mk. 5M recorder, Leak Sandwich speaker, GR Precision variable capacitor, Precision 3/30/300 voltmeter, Elliott precision 0-44 wattmeter, stabilized power unit—95 to +500 V, bridge detector-amplifier, Campbell frequency bridge, insulation meter, low ohmmeter, GR audio power meter, R1155A receiver, components, etc. Tel. 01-460 6360. [1717]

PRINTED Circuit Board in 6 standard widths. 2 in., 2 1/2 in., 3 in., 3 1/2 in., 4 in and 5 in. X any length. 1/16 in. Fibreglass 2p per 3 sq. in. Paxolin 1p per 2 sq. in. P. & P. 5p per order. S.a.e. quotations for other sizes and quantity discounts.—J. Knopp, 11 Connaught Gardens, Braintree, Essex, CM7 6LY. Tel. Braintree 25254. [1725]

PYE V.H.F. Radio Telephone comprising Type AM27F base station and 14 Cambridge mobiles. Further particulars from the Water Engineer, Plastirion, Russell Road, Rhyll. Tel. Rhyll 2254. [1724]

SERVICE Sheets (1925-1971) for TV's, Radios, Transistors, Tape Recorders, Record Players, etc.; over 8,000 models available. S.A.E. enquiries Hamilton Radio, 54 London Road, Bexhill-on-Sea, Sussex. Tel. Bexhill 7097. [18]

SONY CV2000B Video recorder and CVM306BP monitor complete with manual and spare tape plus two Murphy monitors, £315 o.n.o. Brighton 778191 or Rustington 3137 (evenings). [1731]

SPECIAL RESISTOR offer due to the enormous response to our last offer. Here is another bargain, 250 for £1 E24 series 4-7 ohms to 10M Ω and ΩW 5 per cent and 10 per cent mixed. Your selection, but subject to a maximum of 20 different values, and no more than 50 of any one value. If any value is out of stock the nearest will be sent. Note no quantity discount allowed. All goods as previously advertised in March issue Wireless World. COMPONENT FACTORS, P.O. Box 18, Luton, Beds. [1724]

SURPLUS Electric Cable. 3 core rubber covered 28/0076 (100 yd coils) £4-00 per roll. 50p postage. 3 core rubber covered 28/0076 (500 yard coils) £15-50 per roll. Free. 3 core PVC Black 14/0076. (100 yd coils) £3-50 per roll. 25p. Single core PVC clat. 14/0076. (100 yd coils) £0-60 per roll. 10p. 3 core PVC Black flat 28/0076. (100 yd coils) £3-50 per roll. 25p. Single core PVC black. 14/36. (100 yd coils) £0-50 per roll. 10p. Instrument Case Strap. 5/16in. wide nylon black. (100 yd coils) £0-50 per roll. 10p. Broxbourne Eng. Co., Salisbury Road, Hoddesdon, Herts. Telephone Hoddesdon 63666. [1689]

SURPLUS to requirements, HT rectifiers, diodes. Mullard by 127 1200 PIV lamp, 1/49, 12p; 50/99 10p; 100/1,000 Sp. Mullard OC 45, 1-99 10p; 100-500 7p, 500 up 5p. Cash with order, P&P 10p. J.D.A., 219 Gloucester Road, Croydon, CRO 2DW. [1733]

TELETYPE PUNCH £40, disk memory £20, also odd cores stores, connectors and ICs. 01-282 6058 evenings. [1737]

TWIN POWER SUPPLY PANELS, semi-stabilised, 1 contains 2 X Texas IB10J10 Silicon Bridge Rectifiers, 100 P.I.V. at 1A; 1 X Mullard OAZ225 Zener Diode, 7-5V, 10W, 1 X I.T.T. Zener Diode, 5-1V, 1W; 5 X Texas IS121 Silicon Diodes, 150 P.I.V. at 200mA. Electrolytic Capacitors, 2 X Plessey 1,000 microF, 25V; 2 X 50 microF, 50V; 2 X Mullard 250 microF, 25V; 2 X Mullard 640 microF, 25V. Circuit details supplied. A very definite bargain £1, post 10p.—Elekon Enterprises, 12A Tottenham Street, London, W1P 9PQ. Tel. 01-580 7391. [1719]

VACUUM is our speciality. New and second-hand rotary pumps, diffusion outfits, accessories, coaters, etc. Silicone rubber or varnish outgassing equipment from £40. V. N. Barrett (Sales) Ltd., 1 Mayo Road, Croydon, 01-684 9917. [29]

VHF KIT 80-180 MHz receiver, tuner, convertor. Transistorised, remarkable performance. £4 or s.a.e. for literature. Johnsons (Radio), St. Martins Gate, Worcester, WR1 2DT. [99]

WIRELESS WORLD twenty-one bound volumes 1950/71, excellent condition. £50 O.N.O. Box W.W. 1711 Wireless World.

4 COSSOR CC 303 A.M. High Band 20watt Mobile V.H.F. Radio Telephones 121 Kc/s channelling, £65 each. 15 Cossor CC 15 A.M. High Band 15watt Mobile V.H.F. Radio Telephones 25 Kc/s channelling (suitable for conversion to 121 Kc/s, £35 each. 1 Cossor CC 109 A.M. Base Station High Band 15watt V.H.F. Radio Telephone 25 Kc/s channelling (suitable for conversion to 121 Kc/s), £65. Apply: Lincs Radio Systems Ltd., Cosalt Buildings, Fish Dock Road, Grimsby, Tel. Grimsby 57381. [1705]

9V MINI MAINS PACK KIT. Components for compact 9V d.c., 120mA battery eliminator, buildable to size of PPT etc. battery safe double wound transformer, runs coil. With leaflet, £0-90 only, UK post 5p. AMATRONIX LTD., 396 Seladm Road, S. Croydon, Surrey CR2 0DE. [103]

INDIVIDUAL POCKET DOSIMETERS, LATEST GOVERNMENT RELEASE. Type 2A & 3, 11,000 available individually wrapped in boxes of 50. Also 300 Charging Units No. 1 for the above Dosimeters individually boxed, both are absolutely Brand New, supplied one box of 50 Dosimeters with one Charger £14, Post/Packing £1, 25 and one Charger £9, Post/Packing £1. Singly 50p, Post/Packing 10p; Chargers £2-50, Post/Packing 25p. Probable cost of one Dosimeter £10. Larger quantities by quotation. TRANS-RECEIVERS due to Warehouse clearance, old stock, we have for disposal, few only Trans-Receiver (approx. 40) No. 62 MK2, made by Pye for the Navy and Army. Using a total of 11 Valves, 1 RF and 2 IF stages, A.V.C., BFO, covering 1-5 mc/s to 10 mc/s (approx. 200 to 30 meters) in two switched bands. Can be used on RT or CW F.O. or Crystal. A very good internal ATU made of a rotating Silver wire coil, Tunable over the complete range, suitable for aerials 4ft. to 100ft., Internal P.U. for 12 volt DC. A meter is fitted for checking voltages A.V.C. etc. Housed in a Metal Waterproof Case approx. size 18 X 10 1/2 X 1 1/2 ins. Supplied in very good used condition with Headphones & Mike, two spare Valves, Circuit boxed, few only at £12-50, Carr. £1. Air-tested £1 extra. Also 20 only V.H.F. TX—RX B44 MK3 made by Murphy Radio for the army, using 12 Valves (B77 Bases) covering 60-95 mc/s in three preset channels, Crystal controlled. Tuning Condenser is simply tuned to one of three adjustable preset positions, RX & TX switched independent. Internal large Speaker and Power Unit for 12 volts DC. Panel Test Meter, housed in Alloy Waterproof Case size 14 1/2 X 12 1/2 X 7 ins. approx. Supplied in New or as New condition with all six Crystals £8-50, Carr. £1-50 or slightly used no Crystals £6, Carr. £1-50. CRYSTAL CALIBRATOR NO. 10. Range 500 Kc/s to 10 mc/s, up to 30 mc/s on Harmonics. Size 7 1/2 X 7 1/2 X 4", Power 300 volts HT, 12 volts LT. The Calibrator can plug into a Power Socket on the 62 Trans-Receiver which it was normally used with. Supplied in good used condition with circuit £3-75. Post 50p. Or Brand New in Carton with operating manual and Circuit connectors to cost £5-75. Post 50p. JOHNS RADIO Dept. F, 424 Bradford Rd., Batley, Yorks. 83

BUSINESS OPPORTUNITIES

INVEST £1,100 in Stock with International, exciting growth organisation. Reap £500 monthly income with prospects of £1,100 monthly. Requirements: Honesty, Hard work and Determination.—Write fully to: SCANOCO, Down Ampney, Private Road, Chelmsford, Essex. (Distributors of Golden Chemical Products.) [1748]

TEST EQUIPMENT SURPLUS AND SECONDHAND

SIGNAL generators, oscilloscopes, output meters, wave voltmeters, frequency meters, multi-range meters, etc., etc., in stock.—R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley. 4986. [64]

RECEIVERS AND AMPLIFIERS SURPLUS AND SECONDHAND

COMMUNICATIONS RECEIVER AR-88D including handbook but no speaker £40 o.n.o. Reading 477376. [1749]

HRO RXSs, etc., AR88, CR100, BRT400, G209, £640, etc., etc., in stock.—R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley. 4986. [65]

NEW GRAM AND SOUND EQUIPMENT

GLASGOW.—Recorders bought, sold, exchanged; cameras, etc., exchanged for recorders or vice-versa.—Victor Morris, 343 Argyle St., Glasgow, C.2. [11]

TAPE RECORDING ETC.

YOUR TAPES TO DISC.—£2,000 Lathe. From £1-50. Studio/Location Unit. S.A.E. Leaflet. Deroy Studios, High Bank, Hawk St., Carnforth, Lancs. [70]

ARTICLES WANTED

TEST EQUIPMENT

We wish to buy Test Equipment, ancillary spares and devices; Components, plugs and sockets, meters, relays, motors, valves, semi-conductors, microphones, head sets, C.C.T.V. equipment; Receivers, Transmitters, Microscopes, Theodolites, Levels, cameras, Computers and ancillary equipment, lenses (professional and amateur) for motion picture and still work; film in bulk. Immediate decisions and immediate payment.

CONNECTORS & ELECTRONICS LTD 20 College Drive, Ruislip, Middlesex Telephone: Ruislip (713) 5953 66

AVO 8 WANTED. Any condition. Any quantity. Send for packing INS. Huggett's Ltd., 2 Pawsons Road, W. Croydon, SY. [28] HIGHEST possible cash prices for Akai, B. & O., Brenell, Ferragroup, Revox, Sanyo, Sony, Tandberg, Uher, Vortexion, etc. 9.30-5. 01-242 7401. [102] WANTED, all types of communications receivers and test equipment.—Details to R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley. 4986. [63]

WANTED by collector, Burndept Grecian Vase Floor Speaker. Box W.W. 1714 Wireless World.

WANTED, surplus transistors, semiconductors, resistors, and radio and TV parts. Please state price.—Velco Electronics, Bridge Street, Ramsbottom, Bury, Lancs. Tel. 070-682 3036. [17]

WANTED, televisions, tape recorders, radiograms, new valves, transistors, etc.—Stan Willetts, 37 High St., West Bromwich, Staffs. Tel. Wes. 0166. [72]

VALVES WANTED

WE buy new valves, transistors and clean new components, large or small quantities, all details, quotation by return.—Walton's Wireless Stores, 55 Worcester St., Wolverhampton. [62]

SERVICE & REPAIRS

SCRATCHED TUBES. Our experienced polishing service can make your colour or monochrome tubes as new again for only £2-75. With absolute confidence send to Retube Ltd., North Somercote, Louth, Lincs, or phone 0507-85 300. [24]

TENDERS

CITY OF LONDON POLICE—Communications equipment for disposal. Tenders are invited for an assortment of Low-band V.H.F. A.M. Base-station and Mobile Equipment (over five years old). List available from: The Commissioner of Police for the City of London "A" Department, 37 Wood Street, London, E.C.2. [1710]

CAPACITY AVAILABLE

A DESIGN Service for audio amplifiers, tape recorders, FM tuners, etc. Full production engineering support. All designs guaranteed specification and valve engineered. For prompt quote Box No. WW 1751 Wireless World.

AIRTRONICS LTD., for Coil Winding—large or small production runs. Also PC Boards Assemblies. Suppliers to P.O. M.O.D., etc. Export enquiries welcomed. 3a Waterand Road, London, S.E.13. Tel. 01-852 1706 [61]

COIL winding capacity. Transformers, chokes, R.F. coils, etc., to your specification. Sweetnam & Bradley Ltd., Bristol Road, Malmesbury, Wilts., or Tel. Malmesbury 3491. [12]

DESIGN, development, repair, test, and small production of electronic equipment. Specialist in production of printed circuit assemblies. YOUNG ELECTRONICS, 54 Lawford Rd., London, N.W.5. 01-267 0201. [1601]

ELECTRONIC and electrical assembly, panel wiring etc. Prototype and short runs a speciality. J.M.L. Electronic 061-643 4741. [1736]

ELECTRONIC Manufacturing Contractors, customers spec.—Deane Electrics. 01-992 8976. [1475]

TECHNICAL WRITING—Service Manuals—P.C. Layouts—Instruction books prepared to spec. Rapid Service. J. W. Taylor, 2 Stonor Road, W.14. Tel. 01-603 5405. [1750]

WE undertake the manufacture of transformers singly or in quantities to any specification. All work guaranteed for 12 months.—Ladbroke Transformer Co. Ltd., 820a Harrow Road, Kensal Rise, N.W.10. Tel. 01-969 9314. [23]

TECHNICAL TRAINING

C.I.E. A.M.S.E. City & Guilds, etc. Thousands of exam successes. Postal courses in all branches of Engineering. Prospectus FREE.—State subject of interest. B.I.E.T. (Dept. H.18), Aldermaston Court, Reading RG7 4PF. Accredited by C.A.C.C. [13]

ENGINEERS—get a technical certificate. Postal courses in Engineering, Electronics, Radio, TV, Computers, Draughtsmanship, Building, etc.—FREE book from: B.I.E.T. (Dept. H.17), Aldermaston Court, Reading, RG7 4PF. Accredited by C.A.C.C. [16]

COURSES

FULL TIME COURSES IN ELECTRONICS and TELEVISION. These are nine month courses, starting next September, which lead to City and Guilds certificates. Extensive laboratory work is included, and there are, in most cases, no fees for those under 18 at enrolment. Full details from: Section 434, Electrical and Electronic Engineering Department, Southall College of Technology, Beaconsfield Road, Southall, Middx.

TUITION

BECOME "technically qualified" in your spare time. Home study courses in Radio, TV, Servicing and Maintenance, R.T.E.B., City & Guilds, etc.—Informative FREE guide: Chambers College (Dept. R.107), Aldermaston Court, Reading, RG7 4PF. [14]

BOOKS

GOVERNMENT SURPLUS WIRELESS EQUIPMENT HANDBOOK. Contains circuits, data, illustrations for British/USA receivers, transmitters, trans/receivers and a wide range of equipment. Modifications to sets and test equipment included. Price £2-85 pp. 15p.—Myers (W.W.), 112 Stamburn Crescent, Leeds 17, Yorks.

OPTICS. How to use lenses and mirrors. 112p, 100 illustrations. Hardback. Best book on the market for the newcomer to optics. £1 each on 14 days approval against cash. New and Ex Gov. optical equipment of all types. 48 page illustrated catalogue free for 3p stamp. H. W. ENGLISH, 496 Rayleigh Road, Hutton, Brentwood, Essex. Dept. W.W. [1716]

WORLD RADIO TV HANDBOOK £2-80 post paid worldwide. All users are invited to write for a free copy of the fortnightly World Radio Bulletin and my Price List. (Mail only) D. McGarva, 16 Chambers Street, Edinburgh EH1 1HS. [27]

POWER UNITS

400c/s I/P contain 8 N.P.N. Sil transis Texas type 2S012A, these are power type Vc 70v Ic 2 amps, also 18 200 P.I.V. 8 amp and 18 200 P.I.V. 1 amp diodes plus misc parts. New boxed.

£4.50 plus 75p carr.

270° METERS

F.S.D. 1 Ma Scale marked 0, 2, 4, 6, 8 x Deg Cent, size 2" O.S.D. 3½" long, high grade Aircraft inst., supplied new and boxed.

£1.25 plus 15p post.

400c/s INVERTORS

I/P 24/28v D.C. O/P 115v 400c/s 180Va sine wave all transistor, by A.C. Cossor for M.O.D. supplied new with connecting data.

£12 plus 50p carr.

MAINS VOLT STABILISERS

I/P 200/240v 50c/s O/P 240 at 200 watts, regulation + or -25% for 10% I/P change, distortion less than 3%, all transistor supplied new with circ.

£15 plus £1 carr.

SERVO INTEGRATORS

Part of bombing computer all transistor: contains two separate integrator units with 2x tacho gen., 4xsyncro con Tx, 2x motor units, 400c/s supply, supplied in good condition by Smiths.

£8 plus 75p carr.

EXTRACTOR FANS

8" dia fan unit motor 115v 50c/s 3,300 RPM with front grill, full enc. bushless motor conds supplied, ex American equip.

£2.50 plus 50p carr.

POWER FILTERS

Made by Filtron U.S.A. type SP278, rated 250v A.C. or 600v D.C. at 30 amps, size 6" long 2½" dia, single nut fixing, ex American equip.

£1.50 per pair plus 30p carr.

TIMER UNITS

Intended to give time periods up to 1,000 secs. in 10 sec. steps as Dekatron display with int 10 Kc crystal OSC., 6 tubes are used in the display section, requires etc. P.U., supplied in new cond.

£12 plus £1 carr.

SCOPE TROLRIES

Made by Cossor, supplied in used cond.

£5 plus 75p carr.

DYNAMOTOR UNITS

These are new spares for T.C.S. Tx/Rx 12v I/P O/Ps 220v 100 Ma £1 and 440v 200 Ma £1.50. Both plus 25p carr.

CIRCUIT DIAGRAMS

1035 Mk2 and 3 1049 Mk3a, 13a CD518 (CT316), OS-8 all 50p each. CD513-2 and CD1014-2 £1.50 each. CT38 50p, TF801A 75p, R1155B & L, 1392, 1475, ARR-2, APN-9 all 30p each. TF144G. B40 75p each.

WIRING STRIPS

These are solder type wiring strips 24 way, supplied new £1.25 per 100 or sample 10p.

MISC. ODDMENTS TO CLEAR

T.V. monitor E.M.I. type 301 14" £37. T.V. waveform mon E.M.I. type 302 £26. E.M.I. Cam Con unit transistor £18. Digital Printer H.P. 11 line, motor 115v 60 c/s printer only no electronics £15. Inverter 24/28v D.C. to 115v 400c/s 3 phase 150 Va by Echo transistor, new cond. £18. Airmec type 761 Freq. standard with book £26. Power units 115v A.C. to 150v D.C. at 500 Ma stab with meters £6.75. Scopes American type USM-50 response 3c/s to 15 Mc/s 115v I/P £39.50, also USM-24 115v I/P at £33. Sig. gen TF801A 10/300 mc/s with book, good £26. Rustrack recorder 240v motor tape speed 6"/Hr coil 1 Ma £14.

The above prices include carr. Goods are ex equip unless stated otherwise. Callers by appointment only. Phone Sheffield 369882, evenings only.

A. H. SUPPLIES
57 MAIN ROAD, SHEFFIELD S9 5HL

TRANSFORMERS

DOUGLAS GUARANTEED
12 or 24 Volts

Output V. & Amps.	Ref. No.	Price	P. & P.
12V x 2 250 mA x 2	MT111 CB*†	£0.89	8p
12V x 2 500 mA x 2	MT213 CT*†	£0.97	13p
12V x 2 1A x 2	MT 71 AT†	£1.48	24p
12V x 2 2A x 2	MT 18 AT	£2.04	30p
12V x 2 3A x 2	MT 70 AT	£2.59	32p
12V x 2 4A x 2	MT 108 AT	£2.92	35p
12V x 2 5A x 2	MT 72 AT	£3.33	34p

Output Amps	Ref. No.	Price	P.P.	Output Ref. No.	Price	P.P.
500 mA	MT 112 CT†	1.12	15p	4A	MT 21 AT	3.10 40p
1A	MT 79 AT†	1.55	29p	5A	MT 51 AT	4.31 42p
2A	MT 3 AT	2.23	30p	8A	MT 88 AT	6.32 50p
3A	MT 20 AT	2.64	32p	10A	MT 89 AT	7.19 50p

Output Amps	Ref. No.	Price	P.P.	Output Ref. No.	Price	P.P.
500 mA	MT 102 AT†	1.45	24p	3A	MT 105 AT	3.91 41p
1A	MT 103 AT	2.00	32p	4A	MT 106 AT	5.06 41p
2A	MT 104 AT	3.10	32p	6A	MT 107 AT	7.47 50p

Output Amps	Ref. No.	Price	P.P.	Output Ref. No.	Price	P.P.
500 mA	MT 124 AT†	1.46	30p	2A	MT 127 AT	3.16 41p
1A	MT 126 AT	2.24	32p	3A	MT 125 AT	4.59 41p

Power output	Winding tapped at	Ref. No.	Price	P. & P.
20 VA	0-115-210-240	MT 113 CT	£0.89	15p
75 VA	" "	MT 64 AT	£1.72	30p
150 VA	0-115-200-220-240	MT 4 AT	£2.15	31p
200 VA	" "	MT 65 AT	£2.00	32p
300 VA	" "	MT 66 AT	£2.00	32p
500 VA	" "	MT 67 AT	£2.04	49p

VA	Ref. No.	Price	P.P.	VA	Ref. No.	Price	P.P.
60	MT 191 AT* †	2.24	32p	250	MT 194 AT*	6.91	50p
100	MT 192 AT* †	2.73	32p	350	MT 195 AT*	8.17	53p
200	MT 193 AT* †	5.02	50p	500	MT 196 AT*	12.00	67p

400 V. Output at 50-Hz. Ref. IT3 AT Price P. & P.
C-D Ignition system by E. M. Marston Esq. £2.30 29p

EQUIPMENT RANGE

Sec. Output (r.m.s.)	Ref. No.	Price	P. & P.
3-0-3 V.	200 mA MT 209 CB*†	£0.89	8p
9-0-9 V.	100 mA MT 13 CB*†	£0.91	8p
12-0-12	50 mA MT 210 CB*†	£0.91	8p
20-0-20	30 mA MT 211 CB*†	£0.91	8p
0-20 x 2	300 x 2 MT 214 CT*†	£1.21	14p
0-8-9 x 2	500 mA x 2 MT 207 CT*†	£1.48	20p
0-15-20 x 2	500 mA x 2 MT 205 AT*†	£2.12	29p
0-15-27 x 2	500 mA x 2 MT 203 AT*	£2.45	29p
0-15-27 x 2	1A x 2 MT 204 AT*	£3.42	30p
20-12-0-12-20	700 mA (d.c.) MT 221 AT*	£1.11	35p

AT indicates open universal fixing with tags; CT is open U-cliparm fixing with tags; CB is open U-cliparm fixing with P.C. spalls; * with interwinding screen; † tapped 240V Primary; ‡ Primary tapped at 210-240V; other Primaries tapped at 200-220-240V. Over 200 types in stock through agents or direct. Send for list. DOUGLAS ELECTRONICS INDUSTRIES LTD., Dept. No. 19, Thames Street, LOUTH, Lincs.

ELECTRONIC CIRCUITS MANUAL

Over 3,100 modern electronic circuits, complete with values of all parts, organized in 99 logical chapters for quick reference and convenient browsing.

by John Markus

£9.50 Part Postage 25p

OPERATIONAL AMPLIFIERS

by Burr-Brown £7.20 Postage 25p

RADIO AMATEUR HANDBOOK

1972 by A.R.R.L. £2.70 Postage 25p

RADIO TECHNICIAN'S BENCH MANUAL

by Hellyer £3 Postage 10p

AUDIO TECHNICIAN'S BENCH MANUAL

by John Earl £3 Postage 10p

RADIO & ELECTRONIC LABORATORY HANDBOOK

by M. G. Scroggie £4.75 Postage 20p

1972 WORLD RADIO-TV HANDBOOK

£2.80 Postage 10p

110 INTEGRATED CIRCUIT PROJECTS FOR THE HOME CONSTRUCTOR

by R. M. Marston £1.20 Postage 7p


THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST
of British and American Technical Books

19-21 PRAED STREET,
LONDON, W 2 1NP

Phone 723 4185
Closed Sat. 1 p.m.


BETTER GET 'SET'

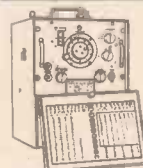

Famous BC.221 Frequency Meter 125 KHZ-20 MHz. Complete with valves, crystal and charts. £19.50. Carr. £1.50. No. 22 TM/RC 2.8 Mc/s. Complete with 12V. D.C. P.S.U., headphones, mike and all cables. £22.50. Carr. £2.50.

Marconi 801A Signal Generator. 10-310 MHz. In original transit case. £45. Carr. £2.50.

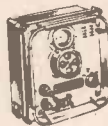Crystal Calibrator No. 10. Crystal controlled heterodyne wavemeter covering 50 KHz-10 MHz (Harmonics up to 300 KHz). Power required 300V. D.C. 15mA. 12V. 0-3A D.C. Test equipment for 62TM/RC. Special Offer £2.50. P. & P. 50p. Few only—No. 62 TM/RC 1-5-10 MHz. £17.50. Carr. £2.



AERIAL MAST EQUIPMENT

20' Telescopic Masts. £3.75. Carr. £1.

5' 2" extension sections to fit bottom of above mast to increase height. £1.25 each (any number supplied)

15' Mast. (7-5' 2" interlocking sections) with base plate and 12 nylon gusset with semi-auto tensioner. £19.50. Carr. £1.50.

70' Mast. Ditto. 16 gusset, black and tackle. £37.50. Carr. £2.50.

AERIAL RODS. 3 ft. screw-in 1" dia. sections. Brand new, green finish. Suitable for many other uses. 10 for £2. Carr. 50p. 25 for £3. Carr. Paid.

R.F. ANTENNA TUNER (A.T.U.) Cylinder design 10" x 4½". Precision calibrated scale. Suitable for tuning most aerials for increased signal strength. A must for serious operators for RC or TM. Full instructions. Only £11.75. P. & P. 25p.

R.F. ANTENNA TUNER (A.T.U.) OPEN TYPE Mounted on ceramic former and feet. "Roller Coaster" design 16G silver or silver plated wheel traveling on wire on ceramic former. Will handle considerable R.F. in original packing. As used with No. 53 Transmitter. Only £2.50. P. & P. 50p.

R.209 Mk II Communication receivers. 11 valve. Covers 1-20 Mc/s. 4 bands. AM/FM. CW, BFO. 12V D.C. Internal Power Supply, as new tested. £18.50 Carr. £1.50.

No. 19 Set Transceiver. Rebuilt. Complete station with PSU, Cables, Mic., Aerial, etc. £21.50 Carr. £3.

No. 19 SET 500uA Meters. Scaled 0-600 and 0-15v. Brand New. Boxed. £1.25. Post paid. (Quantity prices on request.)

R.F. Amplifier. To increase output of No. 19 set. Only £3.75. Carr. £1.25. Instruction book for RF Amp. 37p. Post paid.

All No. 19 spares in stock. Complete instruction book with circuits for No. 19 equipment. 37p. Post paid. Heavy Duty Batteries. New in metal cases with carrying handles. 6v 100/125 AH. 15" x 11" x 7". £3.50. Carr. £1.25. 6v 170AH. 15" x 13" x 7". £6.50. Carr. £1.25. Liquid Prismatic Compases. 2" dia. £7.50. P. & P. 25p.

Famous Tele 'F' Field Telephones. Suitable for Farms, Building Sites, etc. Communication up to 5 miles or more. Rugged construction, will last a lifetime. Only £6.15 pair. Carr. £1.25. (Twin telephone wire for above available—ask for price.)

Ex RAF Periscopes. Made by Kelvin Hughes containing a precision made optics system providing crystal clear wide range vision (2 prisms and 8 lenses). Built in 24v heating circuit to prevent misting and frosting. Approx. 24" long with folding handles and rubber eyepiece. Weight 4lbs. Complete, as new, in instrument case. Only £5.75. Carr. 75p.

Many other Ex-Govt. Surplus Equipment items in stock: Receivers etc. in small quantities too numerous to mention. Enquiries invited. List 25p. Post paid. (Refundable against purchases over £3.)

C.W.O. Carriage charges apply to Mainland only. Minimum Export Order £50.

Surplus Electronic Trading

Drivers End Lane, Codicote, Hitchin, Herts, SG4 8TP
Hours of Business: 8-5 Mon-Fri.; 8-12 Sat.
Telephone: Codicote 242 for appointment.

MULLARD AUDIO CIRCUITS

Components inc. P.C. boards now available for these excellent designs

S.A.E. for lists

ANDOR ELECTRONICS LTD.
45 Lower Hillgate, Stockport.
Tel: 061-480 9791



Quartz Crystal Units
ACCURATE RELIABLE

Private enquiries, send 5p in stamps for brochure

THE QUARTZ CRYSTAL CO. LTD.
Q.C.C. WORKS, WELLINGTON CRESCENT,
NEW MALDEN, SURREY. 01-942-0334 & 2988



YUKAN SELF-SPRAY SO PROFESSIONAL THE YUKAN AEROSOL WAY—
Get these NOW! OR **BLACK WRINKLE (CRACKLE)** finishes

Yukan Aerosol sprays contain 45% fine quality durable easy instant spray. No stove baking required. Hammers available in grey and blue. 90c car. pd. Modern Eggshell Black Wrinkle (Crackle) producing a 3D textured finish. 90c car. pd. all at 85p per push-button self-spray can at our counter. Also durable, heat and water resistant Black Matt finish (339g self-spray cans only) 75c car. pd.

SPECIAL OFFER: One can plus optional transferable wrap on trigger handle (value 25p) for 90c car. pd.

Choice of 13 self-spray plain colours and primer (motor car quality) also available.

Please enclose cheque or crossed P.O. for total amount direct to:
307a EDGWARE ROAD,
Dept: Q 4 YUKAN, LONDON, W2 18N

We supply the Finest Government Departments, Municipalities, Authorities, Institutes and Leading Industrial Organisations—We can supply you too.

Thanks to a bulk purchase we can offer **BRAND NEW P.V.C. POLYESTER AND MYLAR RECORDING TAPES**

Manufactured by the world-famous reputable British tape firm, our tapes are boxed in polythene and have fitted leaders, etc. Their quality is as good as any other on the market, in no way are the tapes faulty and are not to be confused with imported, used or sub-standard tapes. 24-hour despatch service.

Should goods not meet with full approval, purchase price and postage will be refunded.

S.P.	3in. 160ft.	10p	5in. 600ft.	30p
	5 1/2in. 900ft.	40p	7in. 1,200ft.	45p
	3in. 225ft.	12 1/2p	5in. 500ft.	42 1/2p
L.P.	5 1/2in. 1,200ft.	50p	7in. 1,800ft.	65p
	3in. 350ft.	22 1/2p	5in. 1,200ft.	60p
D.P.	5 1/2in. 1,800ft.	80p	7in. 2,400ft.	£1-00

Postage on all orders 7 1/2p

COMPACT TAPE CASSETTES AT HALF PRICE

60, 90, and 120 minutes playing time, in original plastic library boxes.
MC 60 45p each. MC90 62 1/2p each. MC 120 92p each

STARMAN TAPES
28 LINKSCROFT AVENUE, ASHFORD, MIDD. Ashford 52136

WW-096 FOR FURTHER DETAILS

OSMABET LTD.

We make transformers amongst other things.

AUTO TRANSFORMERS. 0-110-200-220-240v a.c. up or down, fully shrouded fitted insulated terminals, 30 watt £1-35; 50w £1-80; 75w £2-10; 100w £2-55; 150w £3-15; 200w £3-90; 300w £5-25; 400w £6-30; 500w £7-50; 600w £8-25; 750w £9-75; 1000w £12-75; 1500w £18; 2000w £24-75; 3000w £33; 4000w £45; etc.

MAINS TRANSFORMERS. Prim 200/240v a.c. TX2 250-0-250v 150 Ma, 6-3v 4A CT, 0-6-6-3v 3A, £4-05; TX3 300-0-300v 120 Ma, 6-3v 2A CT, 0-6-3v 2A, 6-3v 1A, £4-05; TX8 250-0-250v 65 Ma, 6-3v 1-5A, £2-10; MT1 200v 30 Ma, 6-3v 1A, £1-20; MT2 230v 45 Ma, 6-3v 1-5A, £1-50; MT2A 250v 60 Ma, 6-3v 2A, £1-95; MT3 Prim 110/240v, Sec 250v 100 Ma, 6-3v 2A, £2-25.

MULTIVOLT TRANSFORMERS. Prim 200/240v a.c. OMT4/1, tapped sec 0-60v 1A, £2-25; OMT4/2, ditto 2A, £3-45; OMT5/1, tapped sec 0-110v 1A, £3-45; Duo secs 12v 4A—12v 4A, £3-60; Duo sec 0-10-20-25v 2A 10-20-25v 2A, £3-60.

24v AUTO TRANSFORMERS. Input 200/240v a.c., output 24v 150w £4-50; 250w £6-75; for quartz Halogen lamps.

LOW VOLTAGE TRANSFORMERS. Prim 200/240v a.c. 6-3v 1-5A £3p; 3A £1-13; 6A CT £1-80; 12v 1-5A, £1-13; 3A CT £1-80; 6A CT £2-70; 18v 1-5A CT £1-80; 24v 1-5A CT £1-80; 3A CT £2-70; 6A £3-75; 8A £6; 12A £9; 40v 3A CT £3-45; 50v 6A CT £9-75.

MIDGET RECTIFIER TRANSFORMERS. Prim 200/240v a.c. size 1 1/2 x 2 x 1 1/2 in. PPT1 9-0-9v 0.3A; PPT2 12-0-12v 0-25A; PPT3 20-0-20v 0-15A £1-20 each; size 2 x 2 1/2 x 1 1/2 in. MT9v 9-0-9v 1A 98p; MT12v 12-0-12v 1A; MT20 20-0-20v 0-75A £1-13 each.

O/P TRANSFORMERS FOR POWER AMPLIFIERS. 30 watt, A-A load 6-6K, sec 3-7-5-15 ohms, £4-05; 50 watt, A-A load 3K, £6-75; 100 watt A-A load 3K, £11-40; up to 400 watt to order to your specification.

MAINS TRANSFORMERS FOR POWER AMPLIFIERS. TX 6 Prim 200/240v a.c. Sec. 425-0-425v 500 Ma, 6-3v 6A CT, 6-3v 6A CT; 0-6-6-3v 3A, £12-75; TX1 Sec 425-0-425v 250 Ma, 6-3v 4A CT, 6-3v 4A CT, 0-6-6-3v 3A £7-50.

LOUDSPEAKERS FOR POWER AMPLIFIERS. New famous makes for public address systems, bass guitar, electronic organs, Hi-Fi, etc. 12in. 15W/Tweeter £4-99; 12in. 25W £5-60; 12in. 35W £7-20; 12in. 50W £10-50; 60W £11-50; 15in. 60W £12-90; 18in. 100W £22-50; E.M.I. 13 1/2 x 8in. 10W 3, 8 and 15 ohms £2-25 each; 13 1/2 x 8in. Hi-Fi 10W fitted twin tweeters with crossover network, 3-8 and 15 ohms, £4 each. Hi-Fi 8 x 5in. 8 ohm, £1-85; Horn tweeters 2-16 Khz, 8, 16 ohms, £1-50 each.

MANUAL OF POWER AMPLIFIERS. Issued by G.E.C. Valve circuits 30 to 400 watts, with price list, 25p.

LOUDSPEAKERS. 2in. 35a, 2 1/2in. 80a, 2 1/2in. 25n, 3in. 8 or 30n, 60p; 3 1/2in. 3 or 15a, 4in. 8 or 15a, 5in. 3, 15 or 25n, 5 x 3in. 3, 8, 15 or 25n, 90p; 6 x 4in. 25n, 7 x 4in. 3 or 15n, 6in. 3n, £1-05; 8 x 5in. 3, 8, 15 or 25n, £1-50; 8in. 3n, £1-85; 10 x 6in. 3, 8 or 15n, £2-10.

BULK TAPE ERASERS. 200/250v, a.c. immediate erasure of any size spool of magnetic tape, cassettes, £2-40, + 24p.

TAPE RECORDER MOTORS. A variety of uses, blowers, fans etc. New, 230/250v a.c. 50p each.

BECKMAN HELIPOT 10 TURN PRECISION POTS. 10K 5%, 10n. Tol 0-25%, £1-25 each.

MINIATURE RELAYS, with transparent cover only 1/2 oz. for models etc. 2 C.O. in 9; 15; 20 or 30v d.c. 50p each.

PRINTED CIRCUIT ETCHING KITS. Solutions and equipment to make your own P.C. boards, instructions £1-40, + 15p p. & p. extra. P.C. boards 8 x 6in. 15p each.

S.A.E. ENQUIRIES—LISTS, MAIL ORDER ONLY
46 KENILWORTH ROAD, EDGWARE, MIDD., HA8 8YG
Carriage extra on all orders Tel: 01-858 8314

EXCLUSIVE OFFERS

AMPEX

Precision Instrumentation and Data TAPE RECORDER-REPRODUCERS

TYPE FR 100A: 8x speeds, 15/16", 1", 3", 7", 15", and 30" per second, 5 tracks, 1" tape (easily changed to 1/2" or 1" by changing rollers and heads), 104" reel capacity. Push button control. Precision servo control to 0.75 μ sec, track timing 5 μ sec. Drift free within 1 per cent. Accuracy 10⁴ per week. Power input 165/125v 48 to 400 cycles. PRICE £150.
FR 100B: Speeds and specification as above but 14 tracks and 1" tape. PRICE £150.
TYPE FR 1100: as above but 1/2" and 4 speeds, 3", 7", 15" and 30" per second, and 4 track, easily changed to 1/2" or 1" and of lighter and more modern construction than TYPE FR 100B. PRICE £125. The above comprise complete units with electronics in 6 ft. cabinets.

COMMERCIAL TYPE LATTICE STEEL AERIAL MASTS

All masts are sectional and have mating ends for joining to make up to 250 feet for the smaller sizes and 750 feet for the larger sizes. Details and prices below are for 10 foot sections. All are galvanised finish. Top and base fittings are extra.
Type A Lightweight 6" sides triangular £9
Type B Mediumweight 12" sides triangular £17-50
Type C Mediumweight 18" sides triangular £22
Type D Heavyweight 22" sides triangular £24
Type E Heavyweight 31" sides triangular £29

HIGHEST QUALITY 19" RACK MOUNTING CABINETS Totally Enclosed

TYPE F: North Eastern Engineering Co., U.S.A. 80" high x 22 1/2" wide x 24" deep. Standard rack mounting totally enclosed cabinets with rear door fitted espagnolette bolts and open front. Rack panel mounts recessed 1" from front edges, drilled and tapped all the way down every alternate 1" and 2 1/2" with 2 cutouts of 2", 2" from top and 3" from bottom in rack mounting strips, flat bottom to floor. Actual rack panel mounting space is 7 1/2".
PRICE £12-50 (Carriage extra)
TYPE G: 80" high x 22 1/2" wide x 24" deep. As above Type F but slightly shorter and deeper, 4" dia. circular vent in top and no gaps in rack mounting strips. Usable rack mounting space is 7 1/4". Bottom panel is raised 2" from floor.
PRICE £12-50 (Carriage extra)

ALSO OTHER TYPES 80" TO 88" HIGH AVAILABLE
Full details of all above available on request.

FREE
40-page list of over 1,000 different items in stock available—keep one by you.

- ★ Avo Model 160 Valve Tester..... £24-00
 - ★ 500 Watt Auto Transformers..... £4-00
 - ★ Beckman Eput Meters 7 Decade..... £50-00
 - ★ Westinghouse Rectifiers 220V 2A D.C..... £12-50
 - ★ Racal S452 Counter Timers..... £65-00
 - ★ Cossor 1428 Motorised Oscilloscope Camera..... £26-00
 - ★ Advance C.V. Transformers 1500 watts..... £27-00
 - ★ Super large Co-ax Cable 1 1/2 in. dia..... per length
 - ★ BC-1031 Panoramic Adaptors..... £33-00
 - ★ H.M.V. Model 3000 Cabinet Speakers cost £100 each, per pair..... £45
 - ★ Stabilised Power Supplies 25v, and 40v, 30A..... £35
 - ★ Multhead Laboratory Air Condensers 0-001 m/l..... £12
 - ★ Marconi TF-340 Output Power Meters..... £22
 - ★ Avo Electronic Multimeters CT-471A..... £50
 - ★ Ferranti High Speed Tape Readers 5/7 Track..... £25
 - ★ Marconi TF-567 Standard Signal Generators 15 Hz/30 m/cs..... £155
 - ★ Rhoads and Schwarz E.S.M. 300 85/300 m/cs V.H.F. Receivers..... £280
 - ★ Factory R.F. Interference Unit, 50 amps, 600V, A.C. new..... £45
 - ★ Labrec Stabilised Power Units D4140, 320v 7 m/s..... £35
 - ★ C.C.T.V. Marconi 625 line BD-671 Camera, Control Unit, 14 in., Monitor with Cables complete channel working order..... £195
 - ★ Flann Microwave Attenuators 4/12 G/m..... £50
 - ★ E.H.T. 40KV Transformers and associated Equipment up to 6KW available..... P.U.R.
 - ★ 10 foot long 6" sides Triangular Lattice Steel Mast Sections with mating lugs for joining up to 200 feet. New condition..... £9
 - ★ Collins B-390 Communications Receivers 0.5/30.0 m/cs..... £275
 - ★ Weston 2 1/2-D.B. Meters—10/+8..... £2
 - ★ Advance TT-1A Transistor Testers..... £9-50
 - ★ Solartron Oscilloscopes CD 611..... £55
 - ★ Facsimile Machines 90 R.P.M..... £75
 - ★ 5 1/2 inch. dia. Meteorological Balloons..... £1-50
 - ★ New Magnetic Recording Tape made by E.M.I. (USA) 3600 ft on N.A.B. Spools..... £5-50
 - ★ Uniselectors 10 bank 25 way full wipe ex. new..... £3
 - ★ Precision Mains Filter Units new..... £1-50
 - ★ Avo Geiger Counters new..... £5
- Carriage extra at cost on all above.
All goods are ex-Government stores.

We have a large quantity of "bits and pieces" we cannot list—please send us your requirements we can probably help—all enquiries answered.

P. HARRIS ORGANFORD — DORSET
BH16 6ER
BOURNEMOUTH 65051

Dimmit

range of light dimmers

Standard wall mounting rotary and slider control models


Rotary: 400W £3-10, 1KW £3-90
module only: 400W £2-80, 1KW £3-30

Slider: 400W £3-95, 1KW £4-65
module only: 400W £3-40, 1KW £3-90

Send 10p for complete catalogue of Dimmits & Dimmit components.

Trade enquiries invited.
Discount for quantities.

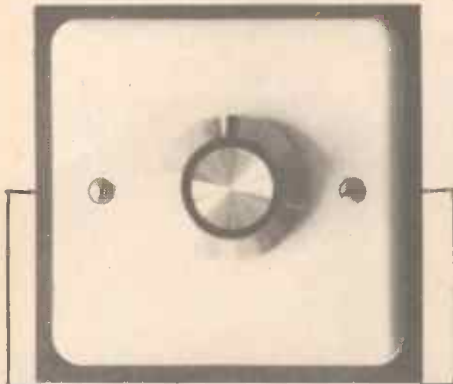YOUNG ELECTRONICS
54 Lawford Rd., London NW5 2LN. 01-267 0201



DIMMERSWITCH £2.70

High quality 400 watt dimmer switch made by expanding manufacturer. Ideal for T.V. lounges, children's bedrooms, projector rooms, etc.
As supplied to Schools, Hospitals, Government departments, etc.
Normally fitted in a matter of minutes—simply replaces your light switch.
Free MK Mounting Frame supplied on request.
CWO to:—

Dept. WW **SOLID STATE LIGHTING**
The Firs, Smallworth Lane, Garboldisham, Diss, Norfolk

PRINTED CIRCUITS & ELECTRONIC EQUIPMENT

- LARGE & SMALL QUANTITIES
 - FULL DESIGN & P.T.H. PROTOTYPE SERVICE
 - ASSEMBLIES AT REASONABLE PRICES
- for full details contact



K.J. BENTLEY & PARTNERS
18 GREENACRES ROAD, OLDHAM
Tel 061 624 0939

Grampian

'SERIES 7 AMPLIFIERS'
for ultimate reliability and coolest running



GRAMPIAN REPRODUCERS LIMITED
Hanworth Trading Estate, Feltham, Middlesex.
Telephone: 01-894 9141.

18.04.72

CASH IMMEDIATELY AVAILABLE for redundant and surplus stocks of radio, television, telephone and electronic equipment, or in component form such as meters, plugs and sockets, valves, transistors, semi conductors, capacitors, resistors, cables, copper wire, screws and nuts, speakers, etc.
The larger the quantity the better we like it.

BROADFIELDS & MAYCO DISPOSALS
21 Lodge Lane, London, N12.
Telephone: 01 445 2713 01 445 0749
Evenings: 01 958 7624

WANTED ELECTRICAL AND ELECTRONIC SURPLUS EQUIPMENT
BEST PRICES PAID
FIELD ELECTRIC LTD
3 SHENLEY ROAD, BOREHAMWOOD
Telephone ELSTREE 6009



THE ONLY COMPREHENSIVE RANGE OF RECORD MAINTENANCE EQUIPMENT IN THE WORLD!



Send P.O. 15p for 48 page booklet providing all necessary information on Record Care.

CECIL E. WATTS LIMITED
Darby House
Sunbury-on-Thames, Middx.

WE PURCHASE ALL FORMS OF ELECTRONIC EQUIPMENT AND COMPONENTS, ETC.

CHILTMead LTD.
7, 9, 11 Arthur Road, Reading, Berks.
Tel: 582 605

BRAND NEW—FULL SPEC. DEVICES

709, 33p; 723, 75p; 741, 36p; 2N2926 Grn., 8p; 2N3055, 48p; BFY 50-1-2, 10p. I.C. pin sockets in strip 0-7p per pin
Dalo PC Marker, 80p; 3 amp. 200 V. Rect. 11p.
Discounts start at 10 off.

JEF ELECTRONICS (W.W.4)

York House, 12 York Drive, Grappenhall, Warrington, WA4 2EJ. Mail Order only. C.W.O. P. & P. 7p per order. O/Seas 65p. List free on application. Money back if not satisfied.

DIGITAL NIXIE-READ-OUT CLOCK — 12 OR 24 HOUR. HOURS, MINUTES AND SECONDS



LINKED TO MAINS FOR ACCURACY. SIZE 8 1/2" x 5" x 3 1/2".
OPTIONAL HOLD AND RESET FACILITY.
PRICE, 12 hour £39.50. (Kit price £29.50)

TELERADIO SPECIAL PRODUCTS,
325-7 Fore St., Edmonton, London, N.9. 01-807 3719
Send also for data on LINSLEY HOOD, BAILEY and TEXAS HI-FI AMPLIFIERS

We can now supply:
WW Designs Built and Tested
ex. Nelson Jones FM tuner, decoder, etc. (also alignment service)


All Electronic Components
ex. 1N914-6p, BC107-10p, Log/Lin pots-16p, etc.
Send 10p for our catalogue of components, units, equipment, etc. Mail order only.

YOUNG ELECTRONICS
54 Lawford Rd., London NW5 2LN. 01-267 0201

QUARTZ CRYSTAL UNITS from

- 1.0-60.0 MHZ
- FAST DELIVERY
- HIGH STABILITY
- TO DEF 5271-A

STOP PRESS! NOTE NEW RANGE

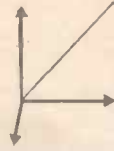

TEL. HYTHE 8961

WRITE FOR LEAFLET AT-1
McKNIGHT CRYSTAL Co.
SHIPYARD ESTATE
HYTHE, SOUTHAMPTON

OVERNIGHT

Prototype Printed Circuits
Fastest in London Area
48 hour and Overnight Services
Electronic & Mechanical Sub-Assembly Co. Ltd.
Highfield House, West Kingsdown, Nr. Sevenoaks, Kent.
Tel: West Kingsdown 2344

LONDON CENTRAL RADIO STORES

TELEPHONE CABLE. Plastic covered grey 4-core coloured coded. 71p per yd. Special quote for quantity.

RECORD STORAGE UNITS. Brand new, Anti-warp. 'Compact 200' stores 200 records. £11.96. P.P. £1.20. 'Compact 100' stores 100 records. £5.57. P.P. 58p. Leaflets available. S.A.E.

ELECTRICITY SLOT METERS (5p in slot) for A.C. mains. Fixed tariff to your requirements. Suitable for hotels, etc. 200/250v. 10 A. £4.50, 15 A. £5.00, 20 A. £5.50. P.P. 60p. Other amperages available. Reconditioned as new 2 years guarantee.

MODERN DESK PHONES, red, green, blue or topaz, 2 tone grey or black, with internal bell and handset with 0-1 dial £4.50. P.P. 37p.

5-WAY PRESS BUTTON INTER-COM TELEPHONES in Bakelite case with junction box handset. Thoroughly overhauled, guaranteed. Price £5.25. Wiring diagram on request, send s.a.e.

10-WAY PRESS-BUTTON INTER-COM TELEPHONES in Bakelite case with junction box handset. Thoroughly overhauled. Guaranteed. £6.75 per unit. Wiring diagram on request, send s.a.e.

20-WAY PRESS-BUTTON INTER-COM TELEPHONES in Bakelite case with junction box. Thoroughly overhauled. Guaranteed. £7.75 per unit. Wiring diagram on request, send s.a.e.

QUARTERLY ELECTRIC CHECK METERS. Reconditioned as new. 200/250 v. 10 A. £2.12; 15 A. £2.62; 20 A. £2.87. Other amperages available. 2 years' guarantee. P.P. 25p.

23 LISLE ST. (GER. 2969) LONDON W.C.2
Closed Thursday 1 p.m. Open all day Saturday

Build a PROJECT "X" SYNTHESISER using Dewtron* PROFESSIONAL MODULES

(*Regd. Trademark)

VOLTAGE CONTROL amplifiers, oscillators, filters and P-H-A-S-E.

MAN-SIZED PATCHBOARD, no cables.

CASH SAVINGS by buying sets of modules and components.

ALL MODULES available separately.

Send S.A.E. for details or 15p for full musical catalogue.
D.E.W. Ltd., 254 Ringwood Rd., Ferndown, Dorset

TRANSFORMER LAMINATIONS enormous range in Radiometal, Mumetal and H.C.R., also "C" & "E" cores. Case and Frame assemblies.


MULTICORE CABLE IN STOCK CONNECTING WIRES

Large quantities of miniature potentiometers (trim pots) 20 ohm to 25K. Various makes. Wholesale and Export only.

J. Black

OFFICE: 44 GREEN LANE, HENDON, N.W.4. 2AH
Tel: 01-203 1855. 01-203 3033
STORE: LESWIN ROAD, N.16
Tel: 01-249 2260

SOMMERKAMP

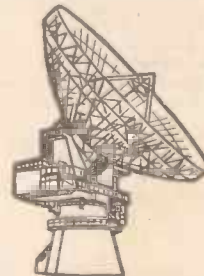

Biggest stock in Europe for Japanese Wireless Intercoms, 2m FM and Amateur SSB Transceivers. For 3 postal IRC's we send our new colour catalogue.


SOKA SRL, Box 176, CH-6903 Lugano, Switzerland
TX: 79314, Tel: 91-88543

WW-097 FOR FURTHER DETAILS

WE PURCHASE

COMPUTERS, TAPE READERS AND ANY SCIENTIFIC TEST EQUIPMENT. PLUGS AND SOCKETS, MOTORS, TRANSISTORS, RESISTORS, CAPACITORS, POTENTIOMETERS, RELAYS TRANSFORMERS ETC.

ELECTRONIC BROKERS LTD.
49 Pancras Road, London, N.W.1. 01-837 7781

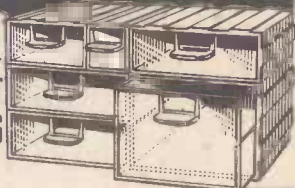**INTER-LOCKING
PLASTIC STORAGE DRAWERS****NEW!
HANDY!
TIDY!**
**DISCOUNT
PRICES****5 SIZES
ALL INTERLOCK**

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots/handles on front. Build up any size cabinet for wall, bench or table top.

BUY AT TRADE PRICES!

Single units (1D) £1.35 per dozen size approx (2 1/4" high 2 1/4" wide 5" deep)
 2D £2.25 per dozen. 3D £2.35 for 8 units.
 6D £3.65 for 8 units (2 3D's in 1 outer)
 6D1 £3.30 for 8 units. Postage/Carriage 35p for orders under £5. Carriage paid for orders over £5.

PLUS QUANTITY DISCOUNTS!

Orders £5 and over DEDUCT 5% in the £
 Orders £10 and over DEDUCT 7 1/2% in the £
 Orders £20 and over DEDUCT 10% in the £

QUOTATIONS FOR LARGER QUANTITIES**IVORYET
LIMITED**

(Dept. WW4) 124 CRICKLEWOOD
 BROADWAY LONDON, N.W.2
 TEL. 01-450 4844

**DESIGNER-APPROVED
"W.W." HI-FI KITS****★ LINSLEY HOOD MODULAR PRE-AMP**

July 1969 design with Dec. 1970 mods. Versatile system built on Lektrokit with layout details.

★ LINSLEY HOOD 15-20W AMPLIFIER

July 1970 latest and ultimate design. O/P capacitor PCB (SRBP/Fibreglass), Tr3, 4 & 5 mount compactly onto heat-sink. Our kit personally tested and approved by the designer. O/P Tr's matched for spec'd performance. Metalwork now available ensures simple construction of amps. and power supply.

★ BAILEY 30W AMPLIFIER (Nov. '68)

Mk. IV PCB (SRBP/Fibreglass) has extra pre-set for quiescent current. Output capacitor and PCB mount directly and compactly on specially designed generous heat-sink.

★ NEW!!! BAILEY PRE-AMP (AUG. 1971)

Superbly engineered kit of this established amp. Uses RH & LH fibreglass PCBs enabling a stereo version to be built in 8 x 2 1/4 x 2 1/4 in. or 8 x 1 1/4 x 5 1/4 in. Basic metalwork ex-stock; fascia plate and cabinet soon. Especially recommended to drive 15-20W AB amp.

AFTER-SALES SERVICE at reasonable cost.


REPRINTS of any one article at 30p } Inc'g p.p.
 DETAILED PRICE LISTS at 5p } (Stamps accepted)

★ PERSONAL CALLERS WELCOME—BY
 ★ APPOINTMENT. DESPATCH BY RETURN
 ★ REFUND GUARANTEED ON ALL PARTS

A.1 FACTORS

72 Blake Road, Stapleford,
 Nottingham

Tel. Nottingham 46051 Giro No. 487 6008
 (10 a.m.—12 Midnight 7 days/week)

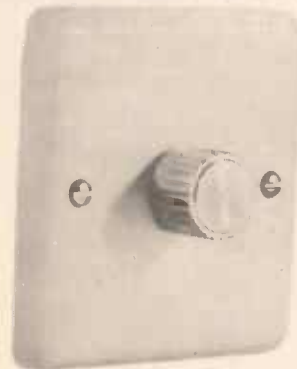**Vary the strength
of your lighting with a
DIMMASWITCH**

The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The ivory mounting plate of the DIMMASWITCH matches modern electric fittings. Two models are available, with the bright chrome knob controlling up to 300w or 600w of all lights except fluorescents at mains voltages from 200-250V, 50Hz. The DIMMASWITCH has built-in radio interference suppression.

Price: 600w—£3.20. Kit form—£2.70.
 300w—£2.70. Kit form—£2.20.

All plus 10p post and packing.

Please send C.V.O. to:—

DEXTER AND COMPANY
 4, ULVER HOUSE, 19 KING STREET,
 CHESTER CH1 2AH TEL: 0244-25883

As supplied to H.M. Government Departments,
 Hospitals, Local Authorities, etc.

**CUT YOUR LEVEL PROBLEMS DOWN TO SIZE;
WITH A CHADACRE ELECTRONICS AUDIO COMPRESSOR TYPE 9521**

Almost every audio source can benefit from a degree of compression, that is to "ame" the dynamic range of the programme.

Compression will tend to increase the density of the sound, this is due to the fact that the low and medium levels are increased, relative to the maximum levels.

"The Ratio" of the compressor will determine the density, i.e., the rate at which the gain increases: e.g., a ratio of 6 : 1 simply means that for a 6 dB increase of input signal the resulting output will only rise 1 dB.

The speed at which the compressor reduces the level, is termed attack "time," and the optimum attack time for a compressor lies between 1 and 10 Ms.

The rate at which the compressor takes to restore its gain back to normal is termed the "release time."

Both of the above time characteristics are adjustable on the 9521 compressor. They are fast attack/fast release, medium attack/medium release, special attack/slow release. Specially designed for automatic level control of a tape recorder. These "time constants" are selected via a 3-position switch. Also adjustable: input gain control, compression control, compressor in/out* for comparing the uncompressed signal, and on/off control* to disconnect the supply.

The uses the 9521 compressor may be put to are very comprehensive. Below are listed just a few.

In a mixing console, where it may be inserted in individual channels, between the microphone amplifier and line amplifier. Used in this sphere it will prevent overload distortion of the following stages, and may also be used to create special effects, which may suit the artistic requirements of the programme.

In conjunction with a discotheque system, to give a constant level, with the peak level; the compressor will make the R.M.S. value appear as a constant peak level, thereby packing the maximum "punch" for this type of application.

It may also be used in public address work, where it will compensate for poor microphone technique. Intelligibility may be improved and enable the amplifier to be used at a lower gain setting, with the consequential risk of acoustic feed-back howls greatly reduced.

The world of radio communication may also reap the advantages of the compressor. By applying the 9521 in this field, the "talk power" or intelligibility over a noisy channel is greatly improved, it is preferable to speech clipping, as it does not introduce harmonic distortion.

Finally, it can be effective to the hard of hearing, who may need to listen to the radio or television at an uncomfortably high volume (to others) in order to hear everything. If, however, the dynamic range of the material is compressed, the annoyance factor caused to others by the peak sound levels is reduced.

The 9521 compressor is available either as a Module, mounted on a Painton 15-way plug; order: 9521/M. Or built in an attractive robust case. The input and output connections are terminated on a Din socket.

The power requirements may be either satisfied from internal batteries† (ample space provided) or an external power supply may be fed into the two banana sockets provided. Order: 9521/C.

* Available on cased units only.

† Two Type PP9.

9521—SPECIFICATION

Power requirements: 18v/4.5mA—30v/6mA.

Input impedance: 50kΩ. Output impedance: 600Ω. Ratio: continuously variable, 1 : 1 through 6 : 1. Unweighted noise level: 90 dB. Fast attack/fast release: may be pre-set anywhere between 1Ms and 10Ms, normally set for 10Ms at factory. Medium attack/medium release: 0.5 secs Fast attack/slow release: attack approx. 3Ms, release approx. 7 secs.*

* Longer release times available on request.

PRICES

9521/C—1-4 £28-50. 5-10 £26-50. 11-25 £24.

9521/M—1-4 £19-50. 5-10 £15-50. 11-25 £13-50.

CHADACRE ELECTRONICS LIMITED**(AUDIO DIVISION)****43 CHADACRE AVENUE, CLAYHALL, ILFORD, ESSEX****TELEPHONE: 01-550 7119**

Need a counter-fast?

Labhire 71
pick of the world's best instruments

phone today - use tomorrow

We hold the pick of the world's digital counters, on 24-hour standby. Oh yes, and oscilloscopes, voltmeters, signal generators, meters, test sets, recorders, power units.

You name it, we rent it out... fast... on very reasonable terms.

Try us, or start by sending for the Labhire brochure.

SOUTH Cores End Road,
Bourne End, Bucks.
06-285 23106

NORTH Shearer House,
Dunham Rd, Altrincham, Cheshire.
061-928 0080

INDEX TO ADVERTISERS

Appointments Vacant Advertisements appear on pages 91-97

	PAGE		PAGE		PAGE
A1 Factors.....	101	Gardners Transformers Ltd.....	14	Quality Electronics Ltd.....	38
Adcola Products Ltd.....	Cover iii	Goldring Mfg. Co., Ltd.....	48	Quartz Crystal Co., Ltd.....	99
A. H. Supplies.....	98	Grampian Reproducers Ltd.....	100		
Ancom Ltd.....	56	Granger Associates Ltd.....	6	Racal Communications Ltd.....	10
Anders Electronics Ltd.....	20, 26	Greenwood, W., Electronic Ltd.....	27	Ralfe, P. F.....	77
Andor Electronics Ltd.....	99			Redifon Ltd.....	45
A.N.T.E.X. Ltd.....	11	Harris Electronics (London) Ltd.....	30	Rola Celestion Ltd.....	9
A.P.T. Electronic Industries Ltd.....	16	Harris, P.....	99	R.S.C. Hi-Fi Centres Ltd.....	85
Audio Advertising.....	54	Hart Electronics.....	57	R.S.T. Valves Ltd.....	60
Aveley Electronic Ltd.....	25	Hatfield Instruments Ltd.....	40		
		Heath (Gloucester) Ltd.....	19	Samson (Electronics) Ltd.....	74
Barrie Electronics.....	57	Henry's Radio Ltd.....	73	Scott, James (Electronic Eng.) Ltd.....	41
Bentley, K. J., & Partners.....	100	Henson, R., Ltd.....	100	Service Trading Co.....	83
Bentley Acoustic Corporation Ltd.....	72			Servo & Electronic Sales Ltd.....	64
B.I.E.T.....	13	I.C.S. Ltd.....	54	Shure Electronics Ltd.....	44
Bi-Pak Semiconductors.....	76	I.E.A. Exhibitions.....	55	Sinclair Radionics Ltd.....	51, 52, 53
Bi-Pre-Pak Ltd.....	66	I.M.O. Precision Controls Ltd.....	33	S.M.E. Ltd.....	5
Black, J.....	100	Industrial Instruments Ltd.....	4	Smiths Industries Ltd.....	8
Bourns (Trimpot) Ltd.....	54	Integrex Ltd.....	63	Smith, G. W. (Radio), Ltd.....	67, 68, 69
Bradley, G. & E., Ltd.....	Cover ii	Ivoryet Ltd.....	101	Soka S. R. L.....	100
Brookdeal Electronics Ltd.....	31			Solid State Lighting.....	100
B. S. R. McDonald.....	46	J.E.F. Electronics.....	100	South Midlands Construction Ltd.....	84
Bulgoin, A. F., & Co., Ltd.....	32	Jackson Bros. (London) Ltd.....	32	Special Product Distributors Ltd.....	41
Bull, J. (Electrical), Ltd.....	89	Jermyn Industries.....	22	Stanley Electronics.....	84
		Keytronics.....	84	Starman Tapes.....	99
Canterbury Audio.....	36, 37	Labhire Ltd.....	102	Steed, John, Research Ltd.....	40
Cesar Products Ltd. (Yukan).....	99	Lasky's Radio Ltd.....	82	Sugden, J. E., Ltd.....	38
Chadacre Electronics Ltd.....	101	Ledon Instruments Ltd.....	24	Surplus Electronic Trading.....	98
Chiltmead Ltd.....	71, 87, 100	Levell Electronics Ltd.....	1		
Colomor (Electronics) Ltd.....	70, 82	Light Soldering Developments Ltd.....	22	Tannoy Products.....	21
Communication Accessories & Equip. Ltd.....	28	Linear Products Ltd.....	16	Taylor Electrical Insts. Ltd.....	28, 40
Computer Sales and Service Ltd.....	56	Lindair (Electro-Tech) Ltd.....	80	Tektronix (U.K.) Ltd.....	50
Concorde Instrument Co.....	56	Linstead Electronics.....	29	Telcon Metals Ltd.....	18
Consumers Association.....	Loose Insert	Lloyd, J. J., Insts. Ltd.....	31	Teleprinter Equipment.....	40
Croydon Precision Inst. Co.....	29	London Central Radio Stores.....	100	Teleguipment Sales.....	42
C.T. Electronics Ltd.....	62	LST Electronic Components Ltd.....	61	Teleradio, The (Edmonton) Ltd.....	100
				"Television".....	39
Dabar Electronic Products.....	58	MacInnes Laboratories Ltd.....	58	Telford Products Ltd.....	30
D.E.W. Ltd.....	100	Marconi Instruments.....	7	Teonex Ltd.....	24
Dexter & Co.....	101	Marshall, A., & Sons (London) Ltd.....	64, 65	Thorn Radio Valves & Tubes Ltd.....	88
Diotran Ltd.....	58	McKnight Crystal Co.....	100	Transradio Ltd.....	35
Dixons Technical (CCTV) Ltd.....	41	Mills, W.....	74, 75	Triangle Digital Services.....	38
Douglas Electronic Industries Ltd.....	98	Milward, G. F.....	86	Trio Corporation Ltd.....	2
Dymar Electronics Ltd.....	48	Modern Book Co.....	98		
Dynamco Ltd.....	34	Multicore Solders Ltd.....	Cover iv	Valradio Ltd.....	30
		Nombrex Ltd.....	20	Vitavox Ltd.....	56
Eddystone Radio Ltd.....	20	Osmabet Ltd.....	99	Vortexion Ltd.....	23
Electrolube Ltd.....	34	Oxley Developments Co., Ltd.....	57		
Electronic Brokers.....	63, 78, 100	Parker, A. B.....	34	Watts, Cecil E., Ltd.....	100
Electronic & Mechanical Sub-Assembly Co., Ltd.....	100	Parry Electronic Developments Ltd.....	27	Wayne Kerr, The, Co., Ltd.....	49
Electronic Design Associates.....	60	Patrick & Kinnie.....	72	Webber, R. A., Ltd.....	34
Electrovalve.....	81	P E Consultants.....	38	Western Electronics (U.K.) Ltd.....	84
Electro-Winds Ltd.....	56	Pembridge, The, College of Electronics.....	63	West Hyde Developments Ltd.....	59
E.M.I. Electronics Ltd.....	17	Plessey Co. Ltd. (Garrard).....	Bound-in Insert	West London Direct Supplies.....	84
Enthoven Solders Ltd.....	24	Plessey Electronic Pty. Ltd.....	79	Whiteley Electrical Radio Co., Ltd.....	18
		Powertran Electronics.....	59	Wilkinson, L. (Croydon) Ltd.....	82
Farnell Instruments Ltd.....	12			Young Electronics.....	99, 100
Ferroglyph, The, Co., Ltd.....	47			Z. & I. Aero Services Ltd.....	15, 90
Field Electric.....	100				
Future Film Developments.....	60				
Fylde Electronic Laboratories Ltd.....	29				

with

ADCOLA

you're on the right wave-length



*

FEATURING THE NEW INVADER MODEL (L 646)



ADCOLA PRECISION SOLDERING EQUIPMENT

offers you the right quality at the right cost for every requirement from home output to full scale industry.

- Extensive range to choose from.
- Precision quality for increased efficiency.
- Speedy after-sales service.
- Interchangeable bits—ex stock.
- Special temperatures available at no extra cost.
- Designed and developed to lower your production costs.

Always choose ADCOLA for sound soldering!

ADCOLA

(Regd Trade Mark)

ADCOLA PRODUCTS LTD.

Adcola House, Gauden Rd. London S.W.4

Tel: 01-622 0291/3

Grams: Soljoint, London

Telex: Adcola London 21851

POST COUPON NOW FOR DETAILS OF OUR EXTENSIVE RANGE

To ADCOLA PRODUCTS LTD. (Dept. H), Adcola House, Gauden Road, London, S.W.4.

Please send me a copy of your latest catalogue by return.

NAME.....

ADDRESS

W.W.1

Other important manufacturers using automatic soldering machines for printed circuits have also found that the advantages of using **EXTRUSOL** include:

1. **Less dross on initial melting**
2. **More soldered joints per pound of solder purchased**
3. **Less reject joints**
4. **Improved wetting of electronic components and printed circuit boards**
5. **More uniform results**

ALL EXTRUSOL is completely protected by plastic film from the moments of manufacture until it is used. **EXTRUSOL** can be released under AID authority and supplied to U.S.A. Spec. QQ-S-571d.

EXTRUSOL is supplied in 1-lb. and 2-lb. Trapezium Bars and Pellets in different alloys with strictly controlled tin contents to suit the appropriate soldering machines, baths and pots. Bars are available for automatic solder feed. Many overseas manufacturers, including those in the U.S.A., are now using **EXTRUSOL** in conjunction with the wide range of Multicore Soldering Chemicals and Liquid Fluxes. Write on your Company's note paper for comprehensive technical information about **EXTRUSOL** & Multicore Soldering Chemicals.



Multicore Solders Limited,
Maylands Avenue,
Hemel Hempstead, Herts.
Tel: Hemel Hempstead 3636. Telex: 82363.

Yet another manufacturer specifies

EXTRUSOL

EXTRUSOL is used exclusively in the automatic soldering equipment at the Plessey factory at Upminster and the illustration shows computer printed circuit boards being soldered.

