

wireless world

MARCH 1979 40p

Australia \$A1.25
Canada \$1.75
Denmark Kr. 11.00
Germany Dm. 4.00
Greece Dr. 47.00
Holland Dfl. 4.50
Italy L. 1100
New Zealand \$NZ 1.50
Norway Kr. 11.00 incl. moms
Singapore M \$3.25
Spain Ptas. 80.00
U.S.A. \$1.65

Novatext tutorials

Logic analyser

H.f. synthesizer





A Synthesized Signal Generator from **mi**

£8,000? £6,000? £4,000? under £2,000?

Somehow some of our customers have been persuaded that our prices are as big as we are. Sometimes the biggest brains are the most cost-conscious brains. For example, our illustration shows a synthesized signal generator which costs £1,900*: the new 520MHz TF2015/1 Signal Generator with its associated Synchronizer. With this combination, synthesizer operation is obtainable without any degradation of generator signal purity, performance and versatility.

Leakage specification is lower than any other available VHF/UHF source and output accuracy at low levels beats all others in the price range.

Building on the enviable reputation of the TF2015 for performance, reliability and value, we have now introduced two new a.m./f.m. versions: the TF2015/1 for narrow band mobile radio testing and TF2015/2 for telemetry and other wideband applications. The U.K. price for TF2015/2 with Synchronizer is £2,150*. All have a frequency coverage of 10 to 520MHz with calibrated a.m. and f.m.

Tuning in 100Hz steps whilst under locked conditions provides a valuable facility for bandwidth measurements and channel stepping. Digital setting of frequency with direct readout means no waiting for counter gate times when you want high resolution, and no r.f. leakage from display holes.

*Special U.K. price

One in four

Only one in four of our customers tells us he needs the stability of a synthesizer. So the other three can save almost half the cost of the synthesizer combination by buying the analogue part alone. So, whether you require a synthesizer or a signal generator you can now obtain quality at ordinary prices.

Optional accessories include Pulse Modulator TF2169, i.f. probes for 'squelch killing', multiple calibration plates for units of output level, matching pads, attenuators, reverse power protection and carrying case.

Write or 'phone for full details:

mi MARCONI INSTRUMENTS

Marconi Instruments Limited · Longacres · St. Albans · Hertfordshire · England AL4 0JN · Tel: (0727) 59292 · Telex: 23350

Marconi Electronics Inc · 100 Stonehurst Court · Northvale · New Jersey 07647 USA · Tel: (201) 767-7250 · Twx: 710-991-9752

Marconi Instruments · 32 avenue des Ecoles · 91600 Savigny-Sur-Orge · France · Tél: 996.03.86 · Télex: 600541.F

Marconi Messtechnik GmbH · 8000 München 21 Jörgstrasse 74 · West Germany · Tel: (089) 58 20 41 · Telex: 5 212642

A GEC-Marconi Electronics Company

WW-001 FOR FURTHER DETAILS



Front cover shows aerial of Niederhorn television transmitter operated by Swiss PTT on v.h.f. and u.h.f. colour. Photo: The Hamer-Smith Swiss collection.

IN OUR NEXT ISSUE

Home computer. The start of a series on the construction and use of a microcomputer, which uses a novel language and which is designed for mathematical problem solving.

Teletext remote control is a further unit designed to extend the usefulness of the *Wireless World* teletext decoder.

Digital data recording without f.s.k. A simple interface for audio recorders using differentiation.

Current issue price 40p, back issue (if available) 50p, at Retail and Trade Counter, Paris Garden, London SE1. Available on microfilm please contact editor.

By post, current issue 55p, back issues (if available) 50p, order and payments to Room CP34, Dorset House, London SE1 9LU.

Editorial & Advertising offices: Dorset House, Stamford Street, London SE1 9LU.

Telephones: Editorial 01-261 8620, Advertising 01-261 8339.

Telegrams/Telex: Wiworld Bispres 25137 BISPRS G
Cables: Ethaworld, London SE1.

Subscription rates: 1 year: £7.00 UK and \$23.40 overseas (\$24 USA and Canada).

Student rate: 1 year, £3.50 UK and £4.50 overseas (\$11.70 USA and Canada).

Distribution: 40 Bowling Green Lane, London EC1R 0NE. Telephone 01-837 3636.

Subscriptions: Oakfield House, Perrymount Road, Haywards Heath, Sussex. RH16 3DH. Telephone 0444 59188. Please notify a change of address.

USA mailing agents: Expeditors of the Printed Word Ltd, 527 Madison Avenue, Suite 1217, New York, NY 10022, 2nd-class postage paid at New York.

© IPC Business Press Ltd, 1979
ISSN 0043 6062

wireless world

ELECTRONICS/TELEVISION/RADIO/AUDIO

MARCH 1979 Vol 85 No 1519

43 Performing blights

44 Low-cost logic analyser — 1

by B. C. Adams

49 Novatexts

by P. Williams

53 Electronic organ tone system — 5

by A. D. Ryder

58 Circuit ideas

Thyristor touch tuning Audio switching unit
Continuous d-to-a converter

60 Computer buses — 2

by I. Witten

65 Antennas and propagation — 2

by R. Ashmore

67 The history of displacement current

by I. Catt, M. F. Davidson, D. S. Walton

69 H.f. amateur band frequency synthesizer — 1

by M. Small

73 News of the month

Audience response to wavelength changes GEC and Hitachi join forces

77 Communications in tunnels

by K. F. Treen

52 World of amateur radio / 78 Books received / 85 Sixty years ago

91 Literature received

79 Letters to the editor

Mobile c.b. dangers Displacement current Military electronics

83 Frequency synthesizers — 4

by R. Thompson

86 Magnetic gyration

by J. B. Williams

89 Antenna aiming calculations

by R. M. Stephenson

92 New Products

94 Sidebands


ibpa

International Business Press Associates

ABC

MEMBER OF THE ADVERTISING BUREAU OF CIRCULATIONS

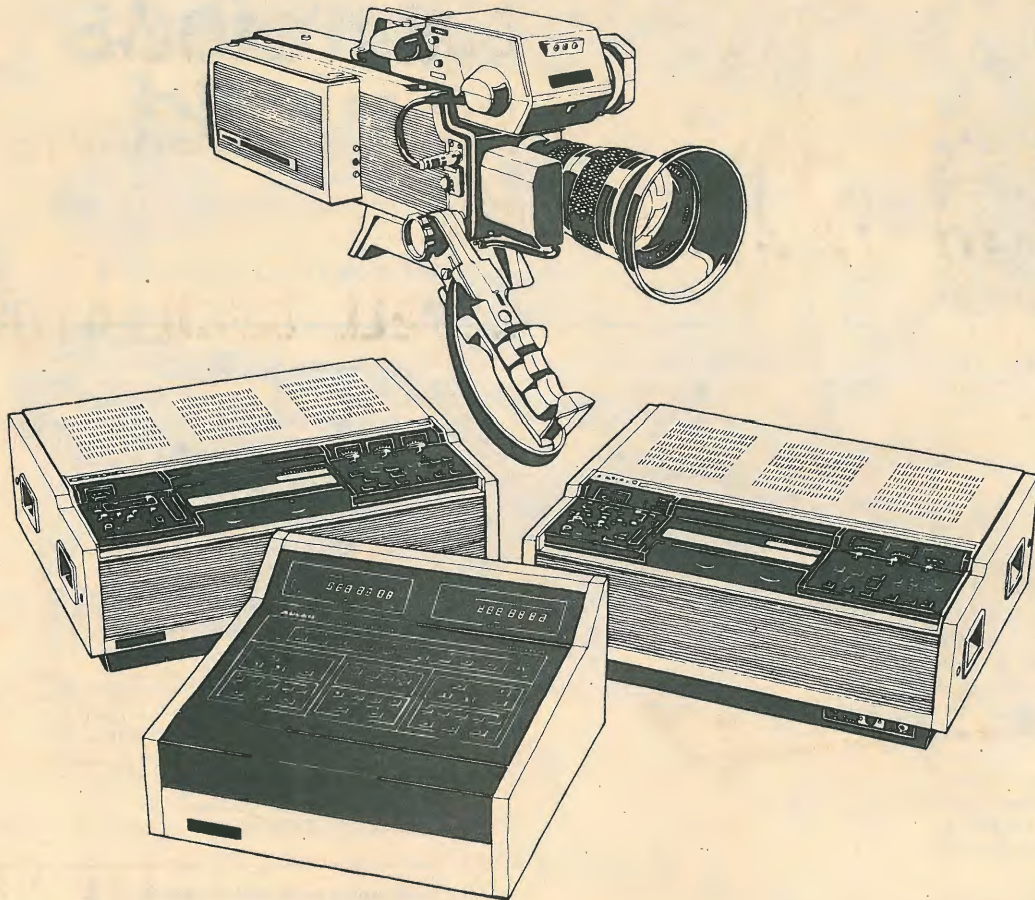From Bell & Howell, exclusive distributors of JVC video products to the educational, industrial and institutional markets in the UK and Eire.



JVC. BELL & HOWELL. SUPERSHIELD.

Choose video equipment with all these names in mind.

Above: a new, complete and outstanding video system from JVC. One three-tube colour camera, of studio quality but portable. Two *editing* U-format video cassette recorders. One automatic editing control unit. Designed to meet broadcast requirements, and therefore excellent in any other application, they should be seen in action before deciding how to re-equip a video production centre which aims at the highest standards (though by no means at the highest current price).

At the other end of the comprehensive JVC range is low-cost equipment for surveillance and similar tasks. Between the extremes: a wide choice of b/w and colour cameras and recorders (reel-to-reel and U-format). And now, of course, VHS - VHS made by the people who invented and developed it, JVC.

For leaflets about JVC video products or, still better, a demonstration, use the coupon. We'll also send you a leaflet on Fuji video tapes, worth reading about because their exclusive Beridox coating is so good for the picture.

We'll also tell you about the third name in our headline, Supershield. This is a new and, we believe, unique guarantee, covering all video and audio-visual products made or distributed by Bell & Howell (excluding only camera tubes, tapes and projector lamps). For two years after purchase, Supershield gives free

technical advice, free parts *with no labour charges*, and (in mainland Great Britain) free collection from your premises to one of our Supershield workshops and free delivery back to you when the job is done. JVC plus Bell & Howell was already a strong combination. JVC plus Bell & Howell plus Supershield, plus a national network of first-class dealers, should be unbeatable.

Please tick squares, fill in your name, clip coupon to your letterhead and mail in an unstamped envelope to Bell & Howell A-V Ltd, Freepost, Wembley, HA0 1BR. Leaflets, please, on:

JVC video products generally JVC VHS Demonstration arrangements

Name _____



BELL & HOWELL

Information systems. For work, education and entertainment.

WW 3 79



DON'T GAMBLE WITH PERFORMANCE BUY LEVELL OSCILLATORS



FREQUENCY 1Hz to 1MHz in 12 ranges.
0 to 1% fine control on TG200DMP.

ACCURACY $\pm 1.5\% \pm 0.01\text{Hz}$ up to 100kHz.
 $\pm 2\%$ up to 1MHz.

SINE OUTPUT 7V r.m.s. down to $< 200\mu\text{V}$ with $R_s = 600\Omega$.

DISTORTION $< 0.05\%$ from 50Hz to 15kHz,
 $< 0.1\%$ from 10Hz to 50kHz, $< 0.2\%$
from 5Hz to 150kHz, $< 1\%$ at 1Hz and
1MHz.

SQUARE OUTPUT TG200D, DM & DMP only, 7V peak
down to $< 200\mu\text{V}$. Rise time
 $< 150\text{nS}$.


SYNC OUTPUT $< 1\text{V}$ r.m.s. sine in phase with output

SYNC INPUT $\pm 1\%$ freq. lock range per volt r.m.s.

METER SCALES TG200M, DM & DMP only. 0/2V,
0/7V & $-14/+6\text{dBm}$.

SIZE & WEIGHT 260 x 130 x 180mm. 4.3kg with
batteries.

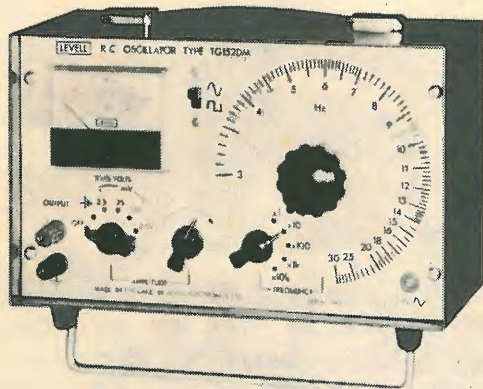TG200 TG200D TG200M TG200DM TG200DMP
£85 £90 £105 £110 £115



FREQUENCY 3Hz to 300kHz in 5 decade ranges.

ACCURACY $\pm 2\% \pm 0.1\text{Hz}$ to 100kHz.
Increasing to $\pm 3\%$ at 300kHz.

SINE OUTPUT 2.5V r.m.s. down to $< 200\mu\text{V}$

DISTORTION $< 0.2\%$ from 50Hz to 50kHz.
 $< 1\%$ from 10Hz to 200kHz.

SQUARE OUTPUT 2.5V peak down to $< 200\mu\text{V}$.

SYNC. OUTPUT 2.5V r.m.s. sine.

METER SCALES 0/2.5V & $-10/+10\text{dB}$ on
TG152DM.

SIZE & WEIGHT 260 x 130 x 180mm. 3.4kg with
batteries.

TG152D

TG152DM

Without meter **£68**

With meter **£85**

FREQUENCY 0.2Hz to 1.22MHz on four decade
controls.

ACCURACY $\pm 0.02\text{Hz}$ below 6Hz.
 $\pm 0.3\%$ from 6Hz to 100kHz.
 $\pm 1\%$ from 100kHz to 300kHz.
 $\pm 3\%$ above, 300kHz.

SINE OUTPUT 5V r.m.s. down to $30\mu\text{V}$ with $R_s = 600\Omega$.

DISTORTION $< 0.15\%$ from 15Hz to 15kHz.
 $< 0.5\%$ at 1.5Hz and 150kHz.

METER SCALES 2 Expanded voltage and $-2/+4\text{dBm}$


SIZE & WEIGHT 260 x 180 x 180mm. 5.4kg.

TG66B

TG66A

Battery model **£225**


Mains & battery model **£240**

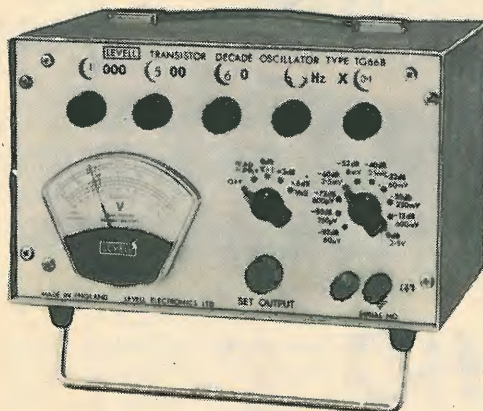

Prices are ex works with batteries. Carriage, packing and VAT extra.
Optional extras are leather cases and mains power units.
Send for data covering our range of portable instruments.

LEVELL ELECTRONICS LTD.

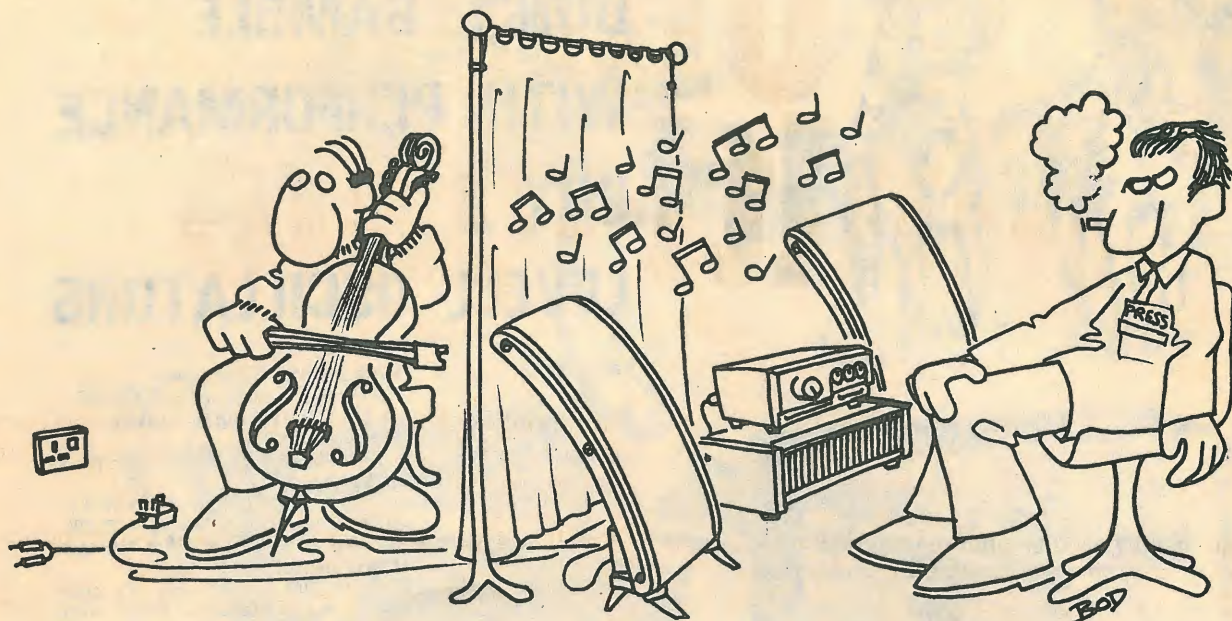MOXON STREET, BARNET, HERTS., EN5 5SD.
TEL: 01-449 5028/440 8686



Artistic licence?

We at QUAD go to a very great deal of trouble to ensure that with a QUAD 33 in the Cancel position, the voltage delivered to your loudspeakers is a virtually exact RIAA transfer of the voltage the pickup will produce into a stated passive load. Nothing added – nothing taken away.

A visiting journalist recently suggested that we should not do this. Final adjustment should be done by ear, he said.

What an opportunity!

After all we know that if we add a little warmth with a subtle boost in the lower middle and balance this with an ever so gentle hump in the quack region (2-3kHz), we can make most programmes sound superficially more impressive. Come to that, why not change the $3180\mu\text{S}$ to $5000\mu\text{S}$ adding a little more 'heft' that most people will fall for. We could even make a special model for the boom and tizz brigade.

Been to any live concerts recently ?

For further details on the full range of QUAD products write to:
The Acoustical Manufacturing Co. Ltd.,
Huntingdon, Cambs. PE18 7DB
Telephone: (0480) 52561

QUAD



for the closest approach to the original sound

QUAD is a Registered Trade Mark

The Ultimate Multi-mate

It's easy to see why Philips new PM 2517 digital multimeter is called The Ultimate Multi-mate. No other DMM comes anywhere near its

combination of laboratory performance and handy form - for such a handy price. Take a look at some of the features it packs in.

Full 4-digit display giving higher resolution than 3½ digits for 80% of measurements. Parameter readout, too.

Small and sturdy construction makes this DMM ideal for bench or field work.

Choice of LED or LCD display - choose the one that suits you, the price is the same. Mains unit supplied free with LED version.

Ergonomic design allows it to work in any position without fuss or fumble.

Autoranging with manual override. Average auto response time less than two seconds.

True RMS rather than "average" detection. The Ultimate Multi-mate measures non-sinewave AC signals more accurately.

High accuracy - necessary to make full use of those four digits. An impressive 0.2% of reading $\pm 0.05\%$ of scale on d.c. volts.


Current to 10A via a separate input is standard, not optional, on the PM 2517.

Overload protection that is so comprehensive you have to try very hard to do any damage, even with mains and TV booster voltages.

Low-cost temperature option makes possible measurement from -60 to $+200^{\circ}\text{C}$.

Data hold option means that in tricky situations you can "freeze" measurements for increased operator safety and convenience.

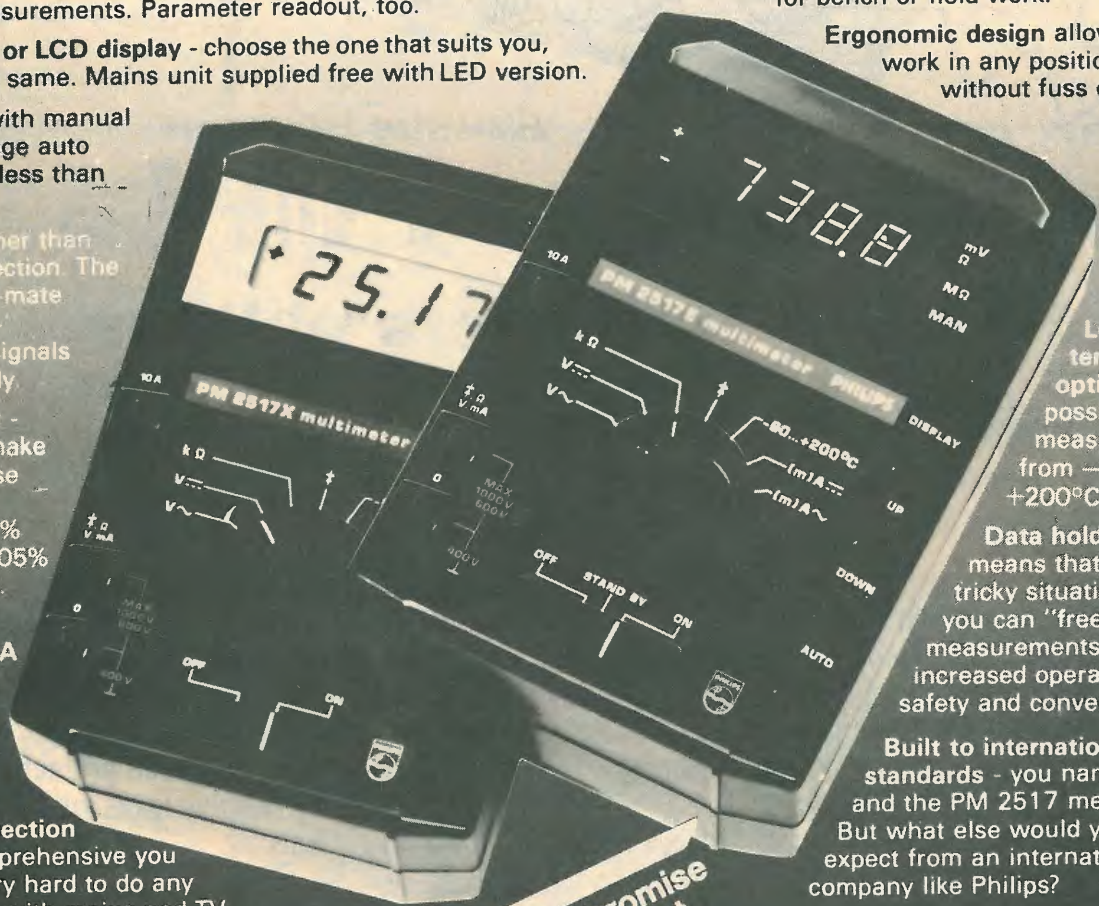Built to international standards - you name them and the PM 2517 meets them. But what else would you expect from an international company like Philips?



The no-compromise 4-digit instrument

The Ultimate Multi-mate is available from Wessex Electronics Ltd., 114 - 116 North Street, Downend, Bristol BS16 5SE. Tel: (0272) 571404; Rank Radio International, Watton Road, Ware, Herts. (Tel: Ware 3966); and Philips Service Centres (phone 01-686-0505 for the address of your nearest branch).

It can also be purchased from the U.K. marketing organisation



Pye Unicam Ltd

Philips Electronic Instruments Dept
York Street, Cambridge, England CB1 2PX
Tel: Cambridge (0223) 58866 Telex: 817331



Test & Measuring Instruments

PHILIPS

THINK OF A SHAPE



S 500D — dual channel
up to 500W/RMS per
channel DC-20 KHZ

Whatever it is, the **HH** 'S' range of power amplifiers will handle it

The **HH** 'S' range is designed to handle heavy industrial usage in the fields of vibrator driving, variable frequency power supplies and servo motor systems.

S 500D

Dual Channel

19" rack mount 3½" high
500w r.m.s. into 2.5 ohms per channel
900w r.m.s. in bridge mode
DC-20 KHZ at full power
0.005% harmonic distortion (typical) at
300w r.m.s. into 4 ohms at 1 KHZ
3KW dissipation from in-built force cooled
dissipators

S 250D

Single Channel

19" rack mount 3½" high
500w r.m.s. into 2.5 ohms
Retro-convertible to dual channel
DC-20 KHZ at full power
Full short and open circuit protection
Drives totally reactive loads with no
adverse effects

A complete range of matching transformers and peripheral equipment for closed loop, constant current and voltage use are available.

Alternative input and output termination to order. Rack case for bench use built to specifications. For complete data write or call.



Kirkham Electronics

MILL HALL, MILL LANE, PULHAM MARKET, DISS, NORFOLK IP21 4XL
DIVISION OF K.R.S. LIMITED
TELEPHONE (037 976) 639/594

FRANCHISED COMMERCIAL AND INDUSTRIAL AGENTS FOR **HH** ELECTRONIC


WW — 065 FOR FURTHER DETAILS




A quality range of British made electrical accessories plus a How to book. Do your own home electrical work with complete confidence. See Cat. pages 129 to 134



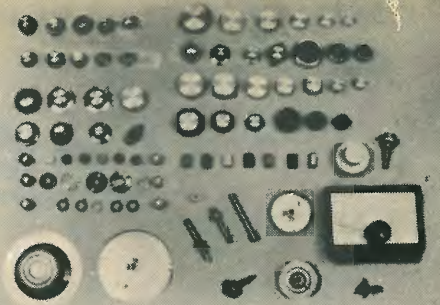This superb organ — build the first working section for just over £100. Full specification in our catalogue



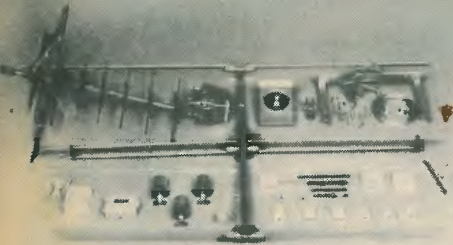A range of highly attractive knobs is described in our catalogue. Our prices are very attractive too!



Mobile amateur radio, TV and FM aerials plus lots of accessories are described in our catalogue



A pulse width train controller for smooth slow running plus inertia braking and acceleration. Full construction details in our catalogue



A wide range of disco accessories at marvellous prices. Our catalogue has all the details



Add on bass pedal unit for organs. Has excellent bass guitar style for guitarists accompaniment. Specification in our catalogue



The 3800 synthesiser — build it yourself at a fraction of the cost of one ready made with this specification. Full details in our catalogue



Touch operated rhythm generator 'The Drumsette'. Construction details 25p (Leaflet MES49). Specification in our catalogue.

MAPLIN

ELECTRONIC SUPPLIES LTD

All mail to:-
 P.O. Box 3, Rayleigh, Essex SS6 8LR.
 Telephone: Southend (0702) 554155.
 Shop: 284 London Road,
 Westcliff-on-Sea, Essex.
 (Closed on Monday).
 Telephone: Southend (0702) 554155.



A superb technical bookshop in your home! All you need is our catalogue. Post the coupon now!



An attractive mains alarm clock with alarm, snooze, and battery back-up. Complete kit with case only £7.30 incl. VAT & P&P. MA1023 module only £3.42 incl. VAT.



A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without. Over 280 pages — some in full colour — it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.

Our bi-monthly newsletter contains guaranteed prices, special offers and all the latest news from Maplin.



A 63-key ASCII keyboard with 625 line TV interface. 4-page memory and microprocessor interface. Details in our

Post this coupon now for your copy of our 1979-80 catalogue price 75p.

Please send me a copy of your 280 page catalogue as soon as it is published (8th Jan. 1979). I enclose 75p but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 75p refunded immediately. If you live outside U.K. send £1 or ten International Reply Coupons.


NAME _____

ADDRESS _____

Our early involvement from becoming a



can save a good idea flash in the pan.

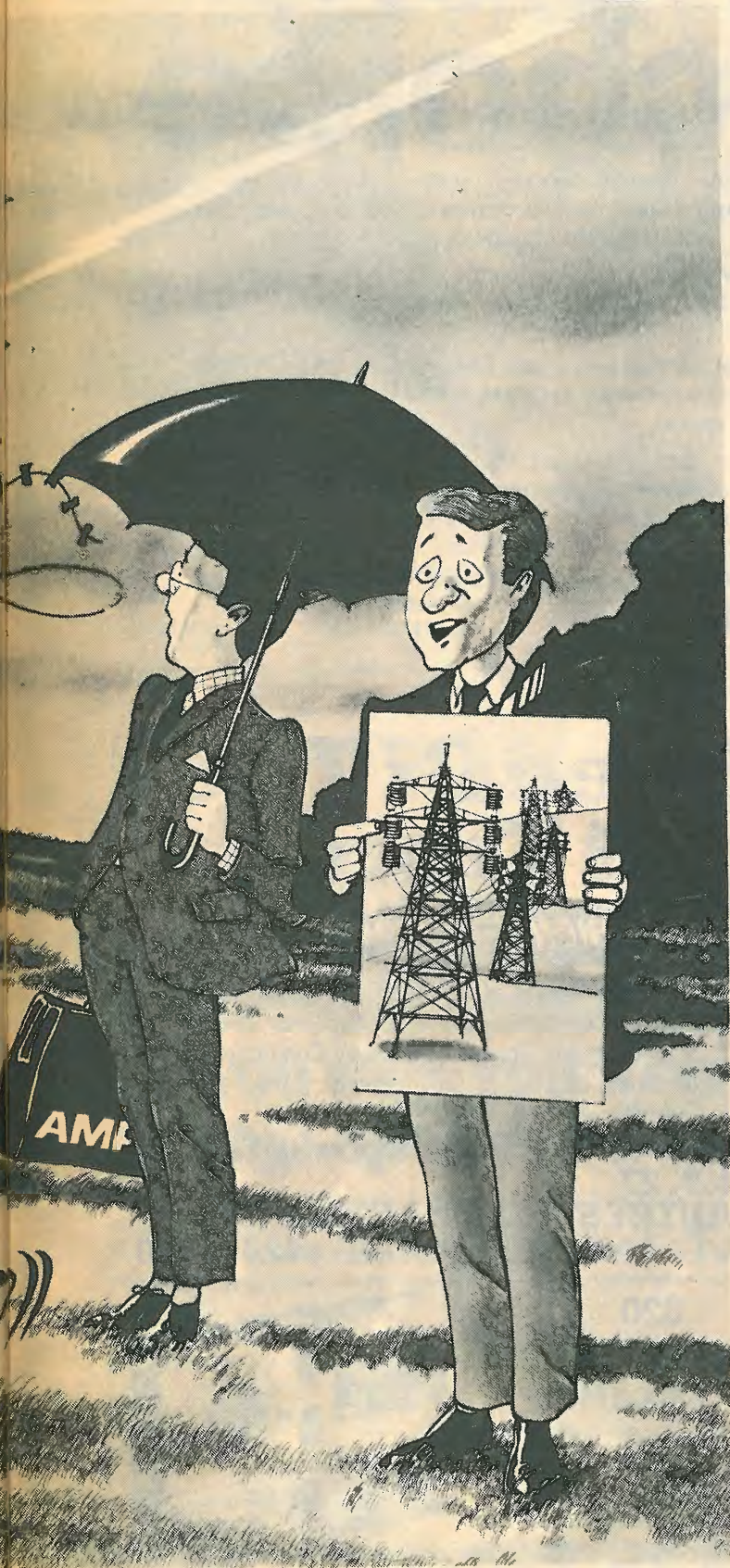

In the development of a project, the design engineer cannot afford to become involved too deeply in every associated technology.

He often needs the help of specialists in solving particular problems. Especially where electrical connection is concerned.

AMP Sales Engineers offer such a specialist service. Working in close co-operation with the design team while the ideas are still very flexible can often prove invaluable.

And the results of involving AMP at the earliest stage of design can be dramatic to say the least—more reliable circuitry, improved performance with greater output and economy in production.

In fact, when the capabilities of AMP are coupled to the design team's engineer's flair and inventiveness you have a unique combination. A combination for success.

Call in AMP on your next design job, telephone 01-954 2356.

You'll certainly find our early involvement a great help.

AMP
Our connections fit in
with your ideas.

AMP OF GREAT BRITAIN LTD., TERMINAL HOUSE, STANMORE, MIDDX.

KGM TV MONITORS

the big choice

Type 224 — the ruggedized monitor for those really demanding situations — extremes of weather, temperature, vibration and frequent change of site.

Standard KGM monitors range from 12" — 24". Our long experience of CCTV enables us to meet almost any special requirement.


VDU's — visual display units have also been supplied in large numbers to suit customers' requirements. Tell us your needs and we will gladly quote.

Send for your data sheets on the full range of CCTV monitors and cameras designed and manufactured by KGM. KGM also supply an extensive range of ancillaries and distribution units.

KGM ELECTRONICS
LIMITED

Clock Tower Road, Isleworth,
Middlesex TW7 6DU
Tel: 01-568 0151. Telex: 934120


WW — 043 FOR FURTHER DETAILS

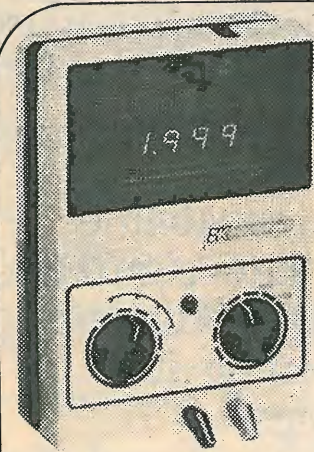

2810 3-1/2 Digit Portable DMM with 5% Accuracy

FEATURES: 3½ digit easy to read LED display · 0.5% typical DC accuracy · Autozeroing · 100µV, .01Ω, 1mA resolution · 10 ohm range and control to zero lead resistance · Selectable High-/Low-power ohms on four ranges · Fully overload protected.

2830 New 3-1/2 Digit Lab DMM

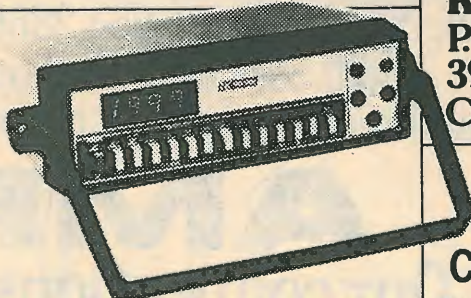

FEATURES: Bright 3½ digit LED display · 0.5% DC accuracy · 100µV, 100nA, .01Ω resolution · 100mV AC and DC ranges · Selectable high-/low-power ohms · Autozeroing · Autopolarity · Completely overload protected · AC operation standard, DC power pack optional · Protected against RF interference · Built-in 10 amp current range.

Three Of The Best From.....

BK PRECISION DYNASCAN CORPORATION


For details of the full range of Electronic Test Equipment: including Capacitance Meters DMM'S Frequency Counters Scopes Power Supplies and Semi-Conductor Testers

Contact - Sole UK Distributors

RADIO SUPPLIES(Components)LTD.
P.O.BOX 27
39 WHITBY STREET, HARTLEPOOL
CLEVELAND. TELEPHONE: 0429-75750

820 New Portable Digital Capacitance Meter

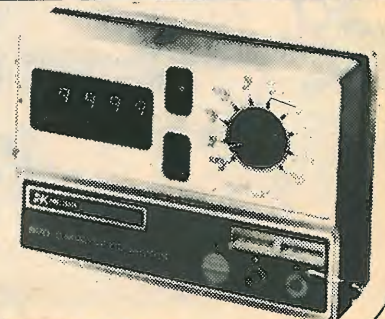FEATURES: Measures capacitance to 1 Farad in 10 ranges · Resolves to 0.1pF on lowest range · 4 digit easy-to-read LED display · 0.5% accuracy · Special lead insertion jacks and banana jacks · Fuse protected · Uses either rechargeable or disposable batteries · Overrange indication.



WW—019 FOR FURTHER DETAILS



If you want your connectors to have a good innings specify Ferranti.

Ferranti circuit board edge connectors are known for their staying power. They're designed for a far higher number of insertions and withdrawals than you're likely to make. They need to be, so that you can rely on them throughout their working life.

You'll like our other design features too. Low force spring contacts. Gold flash or full gold plating on the contacts as you wish. Terminals for wire wrapping or soldering. Many options; pitches of .100" (2.54mm)—modular connector, .150" (3.81mm), .156" (3.96mm) and .200" (5.08mm).

Contact: Connector Sales, Ferranti Limited,
Professional Components Department, Dunsinane Avenue,
Dundee DD2 3PN, Scotland.

Telephone: 0382 89321 Telex: 76166

Distributors: Giltech Components Ltd., 22 Portman Road,
Battle Farm Industrial Estate, Reading, Berks RG3 1ES


Telephone: 0734 582131

FERRANTI
Connector Capability

WW — 012 FOR FURTHER DETAILS

New from AMCRON


Real Time Analyser RTA2

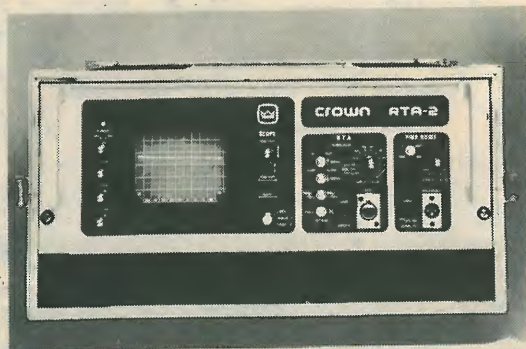

The Amcron RTA2 Real Time Analyser is designed as much for use as a production tool as it is for on-site audio analysis of theatres, and recording studios. A flight case is available.

- ★ 5" CRT Display
- ★ Internal Pink Noise Source
- ★ 1/3 or 1 octave Display
- ★ Frequency range 20 - 20kHz
- ★ Outputs for X-Y Recorders
- ★ Compatible with any microphone
- ★ Price £1,960 ex. VAT

POWER AMPLIFIER D75

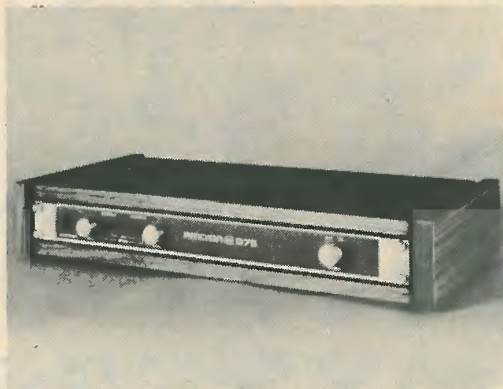

The AMCRON D75 power amplifier replaces the previous model D60. Employing completely new type circuitry it offers also many new features but without any increase in the price.

- ★ New Amcron IOC comparator.
- ★ Balanced XLR input connectors.
- ★ Signal Presence indicators.
- ★ Separate Signal/chassis earth.
- ★ 45 watts into 8 ohms per channel.
- ★ Price £230 ex. VAT.

Other AMCRON products include:


DC300A amplifier 500 watts/chan.	£550
D150A amplifier 200 watts/chan.	£350
VFX2A Electronic Variable Filter	£270
EQ2 Equaliser	£599
IC150A Pre-amplifier	£260
IMA Intermodulation Distortion Analyser unit	£610

MACINNES LABORATORIES LTD.
 Carlton Park Industrial Estate
 Saxmundham, Suffolk, IP17 2NL
 Tel. Saxmundham (0728) 2262/2615

WW — 031 FOR FURTHER DETAILS

OLSON

MINICASES

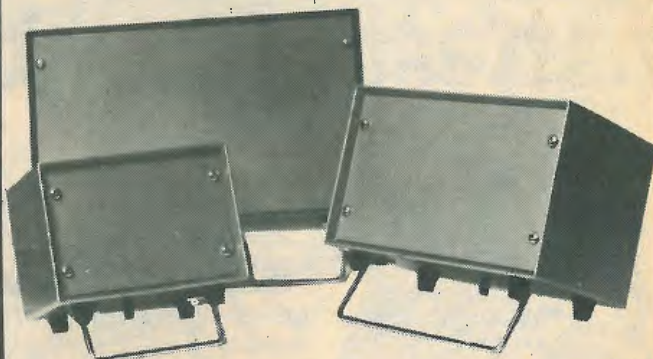

Type	Overall Dimension			Case no vents	Case with vents	Chrome leg
	Width	Height	Depth			
21	6 1/2"	4 1/2"	4 1/2"	—	5.88	1.15
22	8 1/2"	5 1/2"	5 1/2"	—	6.50	1.15
23	10 1/2"	6 1/2"	6 1/2"	—	7.70	1.30
24	12 1/2"	7 1/2"	7 1/2"	—	8.45	1.30
25A	6 1/2"	4 1/2"	4 1/2"	5.60	6.20	1.30
25B	6 1/2"	4 1/2"	6 1/4"	6.00	6.60	1.30
26A	8 3/4"	5 3/4"	6 1/4"	7.90	8.50	1.30
26B	8 3/4"	5 3/4"	8 1/4"	8.25	8.85	1.30
27A	12 1/4"	7 1/2"	5 1/2"	8.65	9.35	1.30
27B	12 1/4"	7 1/2"	8"	9.35	10.05	1.30
28A	14"	10 1/2"	6 1/2"	10.20	10.90	—
28B	14"	10 1/2"	8 1/2"	11.15	11.85	—
29A	10"	4"	6"	7.15	7.75	1.30
29B	10"	4"	8"	7.53	8.13	1.30
30A	12"	5"	6"	7.80	8.50	1.30
30B	12"	5"	8"	8.15	8.85	1.30
31A	14"	6"	6"	8.50	9.20	1.30
31B	14"	6"	8"	8.93	9.63	1.30
61	15 1/2"	7 1/2"	9 1/2"	—	13.00	—
62	17 1/2"	8 1/2"	9 1/2"	—	15.00	—
63	16 1/2"	9 1/2"	9 1/2"	—	15.00	—
64	15 1/2"	7 1/2"	12 1/2"	—	15.00	—
65	17 1/2"	8 1/2"	12 1/2"	—	17.15	—
66	16 1/2"	9 1/2"	12 1/2"	—	17.15	—

Postage & VAT extra

INSTANT TRUNKING SYSTEM!




Ready to use. Internal wiring suitable for 30 amp

TR6 — 6 sockets switched	£21.50
TR9 — 9 sockets switched	£25.50
P&P £1.85	+VAT

PORTABLE POWER DISTRIBUTION FOR INSTANT MAINS!

NEW! 10 sockets switched in sloping box

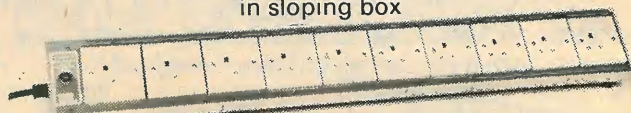

Type 13A/10SW **£27.50. P&P £1.85 + VAT**



COMPLETE WITH 6FT. CABLE AND 13 AMP-FUSED PLUG

4 sockets 13A	£12.15
6 sockets 13A	£14.30
4 sockets 13A switched	£13.75
6 sockets 13A switched	£15.95

ALL DISTRIBUTION PANELS ARE FITTED WITH MK SOCKETS & PLUG
 Send for details of complete range + postage 85p each + 8% V.A.T.
OLSON ELECTRONICS LTD., FACTORY NO. 8, 5-7 LONG ST., LONDON E2 8JH
 TEL: 01-739 2343


WW—017 FOR FURTHER DETAILS

The professionals' colour pattern generator



Over 20 patterns to CCIR or RTMA standards

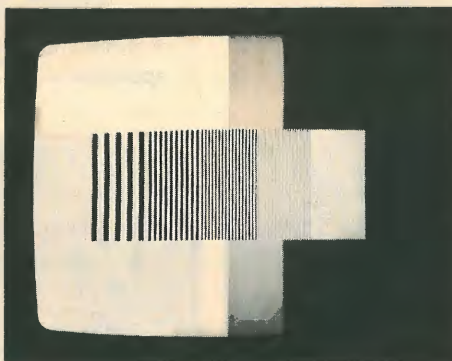- Full RF coverage: TV IF, Band I-III-IV and V.
- Electronic tuning and choice of six preset channels.
- Synchronisation according to TV standard, also obtainable as composite and frame sync.
- Adjustable Video, calibrated chroma/burst and variable RF amplitude.
- Internal/external video and sound modulation.



Linearstaircase signal with 8 identical steps combined with definition pattern of 5 vertical bars at 0.8 - 1.8 - 2.8 - 3.8 and 4.8 MHz.

This pattern generator is the finest available for precise measurement and alignment work on video equipment including domestic TV receivers, VCR's, VTR's, VLP's, closed circuit and cable TV installations. Service technicians, video development engineers, TV broadcast staff and lecturers will all appreciate the quality and ease of use of this compact but very versatile pattern generator. More than 20 patterns are available on six channels frequencies using instant touch-button selection. The RF, video and trigger outputs are superior to many other portable generators and closely resemble those transmitted from your local TV station.

Find out more about the PM 5519 and the rest of the Philips audio and video service equipment range by requesting our new Service Brochure.



Pye Unicam Ltd

Philips Electronic Instruments Dept
York Street, Cambridge, England CB1 2PX
Tel: Cambridge (0223) 58866 Telex: 817331



**Test & Measuring
Instruments**

PHILIPS

□ OSCILLOSCOPES 10 - 150 MHz □ DIGITAL & ANALOGUE MULTIMETERS □ CONVERSATIONAL DATA LOGGERS □ RECORDERS CHART & X - Y □ LF & RF OSCILLATORS □ MICROWAVE EQUIPMENT
□ DC POWER SUPPLIES & AC STABILIZERS □ FREQUENCY COUNTERS & TIMERS □ TV STUDIO & TRANSMISSION INSTRUMENTATION □ PULSE GENERATORS □ AUDIO & VIDEO SERVICE EQUIPMENT


WW — 083 FOR FURTHER DETAILS

Buying video equipment?

Then talk to someone who picks horses for courses better than most.



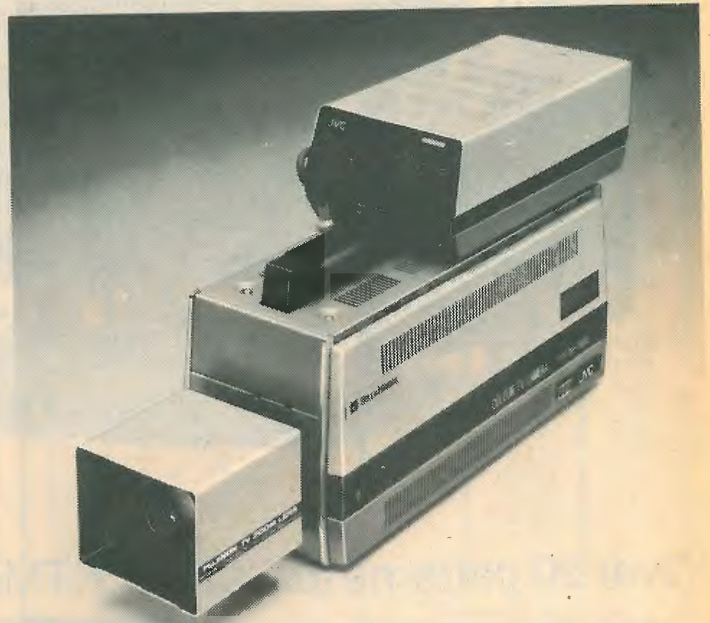
The JVC VHS recorder and GC3300 camera form an economical colour system for duties like rôle playing and product demonstrations.



A three-tube colour camera with a wide range of applications: JVC's NUI800.



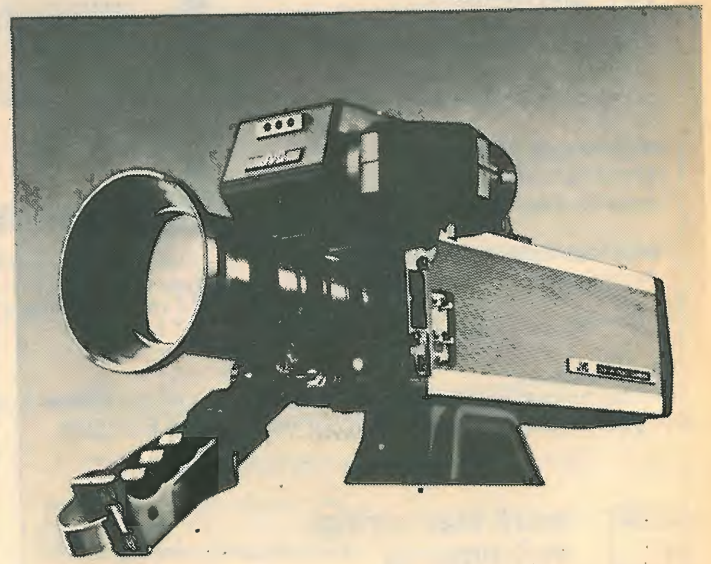Fuji video tapes—among the world's finest—are a comprehensive range extending from VHS to broadcasting.



The outstanding new JVC CY8800, truly portable but with a 'studio' standard of performance.

Before making a purchasing decision, talk to one of Bell & Howell's specialist video dealers. You'll find he's a specialist with some special qualities. He knows everything worth knowing about the JVC and other video products distributed by Bell & Howell, as you'd expect. He also knows which of these products, or which combination of them, is likely to be best for whatever video job you have in mind.

Indeed, he'll even resist the temptation to sell you any kind of video equipment if your message can be conveyed just as well by a tray of slides plus a cassette of audio tape. Conversely, he'll have the courage to start talking in four figures, or maybe five, if a substantial investment is what you've got to make.

And, when the decision has been made and the order placed, you have a guarantee of highly skilled free advice on anything to do with the equipment you buy. That's part of the exclusive new Bell & Howell Supershield warranty, which also

guarantees free replacements or repairs, with no labour charges, for two years from the date of purchase.*

First-class video equipment. First-class advice. The support of a first-class (and, we believe, unique) guarantee. For all of these, just contact one of the Bell & Howell specialist video dealers whose names and addresses you can obtain by using the inquiry service or writing in an unstamped envelope to Bell & Howell A-V Ltd, Freepost, Wembley, Middlesex, HA0 1BR (01-903 5411).

*This two-year warranty even includes video heads and excludes only video tapes and camera tubes. In mainland Britain, too, we collect and deliver free when guarantee service is required.



BELL & HOWELL


Information systems. For work, education and entertainment.



CR8500LE, JVC's new U-format recorder, designed for assemble and insert editing and with important special features.



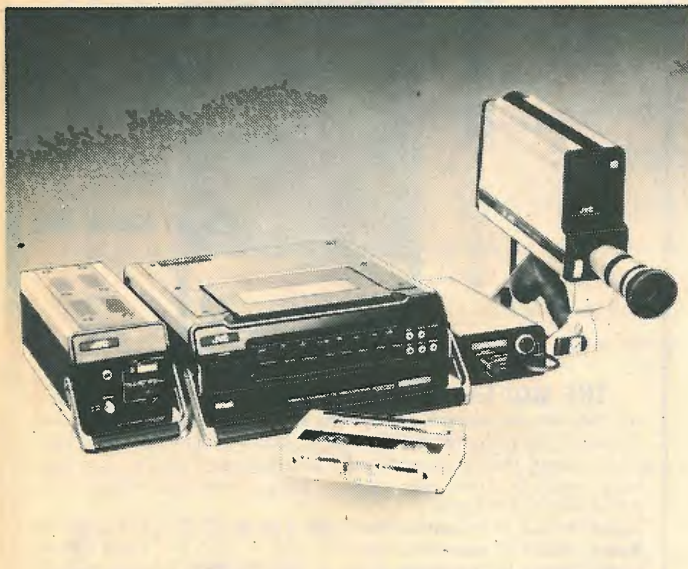One of the current JVC range of 3/4 in. U-format video cassette recorders, with full remote control.




A JVC configuration for U-format recording on location, based on the CR4400 portable recorder and two-tube GC4800 colour camera.



The JVC accessory range extends from simple vision switches to effects and mixing units—and beyond.

100,000,000,000,000 Ohms

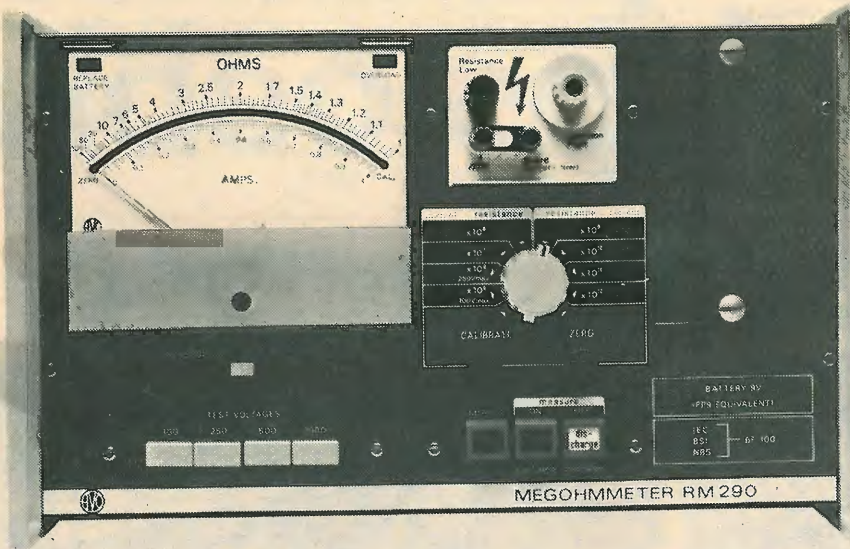

The AVO RM290 is a bench type megohmmeter with a resistance range that goes up to $10^{14} \Omega$ making it ideal for those applications where there is a need to measure the electrical resistance of non-conducting materials...accurately!

You can use the RM290 for tests on insulating components in electronic assemblies or on capacitor dielectrics. Resistance measurements can be made at test voltages of 100, 250, 500 or 1000 V. Readout from the single resistance scale on the meter is direct, irrespective of the test voltage selected.

You'll find the AVO RM290 a great asset. Get in touch with us today and we'll let you have the full facts.



AVO Limited, Archcliffe Road, Dover, Kent, CT17 9EN
Tel: 0304 202620 Telex: 96283

Thorn Measurement & Components Division

You'll never meet a better meter

WW — 039 FOR FURTHER DETAILS



Only Valves are good enough for this customer.

As the demand for high quality sound increases, so does the need for M-OV valves.


Valves, and only valves, can provide the level of performance many listeners now demand.

M-OV Beam Tetrode KT77 and KT88 valves meet all audio market requirements from 30-200 watts.

KT77 is especially rugged and ultra linear.

KT88 is a proven long-life valve that is at home in your quality equipment.

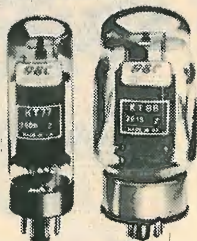Get in touch with us now for technical data and details of worldwide distribution.



M-OV
A MEMBER OF THE GEC GROUP


S&C

S 666

THE M-O VALVE CO LTD, HAMMERSMITH, LONDON, ENGLAND W6 7PE.
TELEPHONE 01-603 3431. TELEX 23435. GRAMS THERMIONIC LONDON

WW — 028 FOR FURTHER DETAILS

ELECTRONIC INDUSTRIAL THERMOMETER

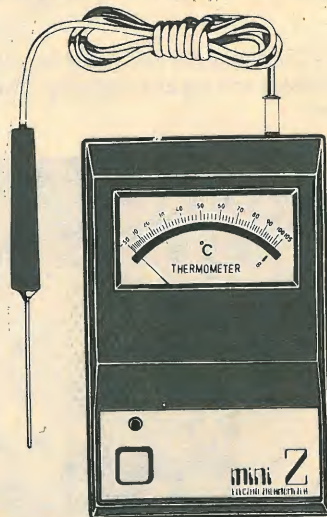

THE MODERN WAY TO MEASURE TEMPERATURE

A Thermometer designed to operate as an Electronic Test Meter. Will measure temperature of Air, Metals, Liquids, Machinery, etc., etc. Just plug-in the Probe, and read the temperature on the large open scale meter. Supplied with carrying case, Probe and internal 1 1/2 volt standard size battery.

- Model "Mini-Z 1" measures from -40°C to $+70^{\circ} \text{C}$. Price £30.00
- Model "Mini-Z 2" measures from -5°C to $+105^{\circ} \text{C}$. Price £30.00
- Model "Mini-Z Hi" measures from $+100^{\circ} \text{C}$ to 500°C . Price £33.00 (VAT 8% EXTRA)

Write for further details to

HARRIS ELECTRONICS (LONDON)
138 GRAY'S INN ROAD, LONDON, WC1X 8AX
(Phone 01-837 7937)

WW—015 FOR FURTHER DETAILS

15 - 240 Watts!

HY5 Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc.) are catered for internally, the desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

FEATURES: Complete pre-amplifier in single pack — Multi-function equalization — Low noise — Low distortion — High overload — two simply combined for stereo.

APPLICATIONS: Hi-Fi — Mixers — Disco — Guitar and Organ — Public address.

SPECIFICATIONS:

INPUTS: Magnetic Pick-up, 3mV; Ceramic Pick-up 30mV; Tuner 100mV; Microphone 10mV;

Auxiliary 3-100mV; input impedance 47k Ω at 1kHz.

OUTPUTS: Tape 100mV; Main output 500mV R.M.S.


ACTIVE TONE CONTROLS: Treble \pm 12dB at 10kHz; Bass \pm at 100Hz.

DISTORTION: 0.1% at 1kHz; Signal/Noise Ratio 68dB.

OVERLOAD: 38dB on Magnetic Pick-up; SUPPLY VOLTAGE \pm 16.50V

Price £6.27 + 78p VAT. P&P free.

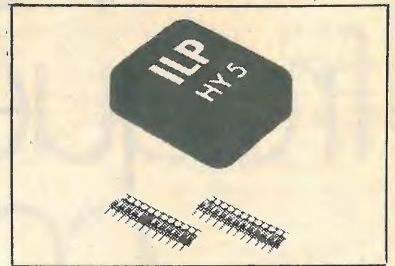HY5 mounting board B1 48p + 6p VAT P&P free.



HY30 15 Watts into 8 Ω

The HY30 is an exciting New kit from I.L.P., it features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

FEATURES: Complete kit — Low Distortion — Short, Open and Thermal Protection — Easy to Build.

APPLICATIONS: Updating audio equipment — Guitar practice amplifier — Test amplifier — Audio oscillator.


SPECIFICATIONS:

OUTPUT POWER 15W R.M.S. into 8 Ω . DISTORTION 0.1% at 15W.

INPUT SENSITIVITY 500mV. FREQUENCY RESPONSE 10Hz-16kHz — 3dB.

SUPPLY VOLTAGE \pm 18V.

Price £6.27 + 78p VAT. P&P free.

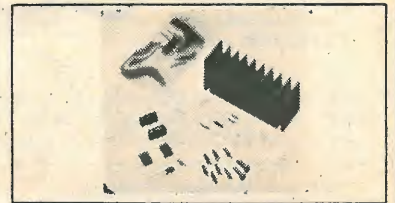

HY50 25 Watts into 8 Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

FEATURES: Low Distortion — Integral Heatsink — Only five connections — 7 Amp output transistors — No external components.

APPLICATIONS: Medium Power Hi-Fi systems — Low power disco — Guitar amplifier

SPECIFICATIONS: INPUT SENSITIVITY 500mV.

OUTPUT POWER 25W RMS into 8 Ω LOAD IMPEDANCE 4-16 Ω . DISTORTION 0.04% at 25W at 1kHz.

SIGNAL/NOISE RATIO 75dB. FREQUENCY RESPONSE 10Hz-45kHz — 3dB.

SUPPLY VOLTAGE \pm 25V. SIZE 105.50 x 25mm.

Price £8.18 + £1.02 VAT. P&P free.



HY120 60 Watts into 8 Ω

The HY120 is the baby of I.L.P.'s new high power range, designed to meet the most exacting requirements including load line and thermal protection, this amplifier sets a new standard in modular design.

FEATURES: Very low distortion — Integral Heatsink — Load line protection — Thermal protection — Five connections — No external components.

APPLICATIONS: Hi-Fi — High quality disco — Public address — Monitor amplifier — Guitar and organ

SPECIFICATIONS:


INPUT SENSITIVITY 500mV

OUTPUT POWER 60W RMS into 8 Ω LOAD IMPEDANCE 4-16 Ω . DISTORTION 0.04% at 60W at 1kHz.

SIGNAL/NOISE RATIO 90dB. FREQUENCY RESPONSE 10Hz-45kHz — 3dB. SUPPLY VOLTAGE \pm 35V.

Size: 114 x 50 x 85mm.

Price £19.01 + £1.52 VAT. P&P free.

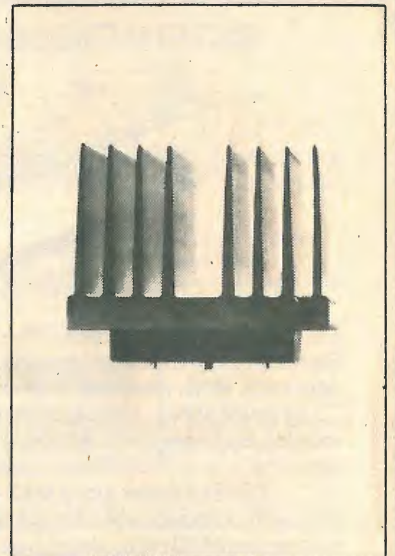

HY200 120 Watts into 8 Ω

The HY200, now improved to give an output of 120 Watts, has been designed to stand the most rugged conditions, such as disco or group while still retaining true Hi-Fi performance.

FEATURES: Thermal shutdown — Very low distortion — Load line protection — Integral Heatsink — No external components.

APPLICATIONS: Hi-Fi — Disco — Monitor — Power Slave — Industrial — Public address.

SPECIFICATIONS:


INPUT SENSITIVITY 500mV.

OUTPUT POWER 120W RMS into 8 Ω LOAD IMPEDANCE 4-16 Ω . DISTORTION 0.05% at 100W at 1kHz.

SIGNAL/NOISE RATIO 96dB. FREQUENCY RESPONSE 10Hz-45kHz — 3dB. SUPPLY VOLTAGE \pm 45V.

SIZE 114 x 100 x 85mm

Price £27.99 + £2.24 VAT. P&P free.

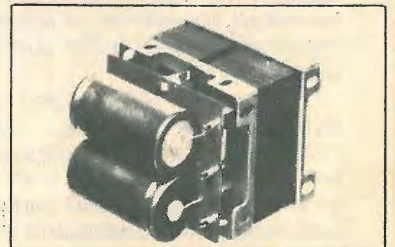

HY400 240 Watts into 4 Ω

The HY400 is I.L.P.'s 'Big Daddy' of the range producing 240W into 4 Ω ! It has been designed for high power disco or public address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

FEATURES: Thermal shutdown — Very low distortion — Load line protection — No external components.

APPLICATIONS: Public address — Disco — Power slave — Industrial.

SPECIFICATIONS:

OUTPUT POWER 240W RMS into 4 Ω LOAD IMPEDANCE 4-16 Ω . DISTORTION 0.1% at 240W at 1kHz.

SIGNAL/NOISE RATIO 94dB. FREQUENCY RESPONSE 10Hz-45kHz — 3dB. SUPPLY VOLTAGE \pm 45V.

INPUT SENSITIVITY 500mV. SIZE 114 x 100 x 85mm.

Price £38.61 + £3.09 VAT. P&P free.

POWER SUPPLIES

PSU36 suitable for two HY30's **£6.44 + 81p VAT**

PSU50 suitable for two HY50's **£8.18 + £1.02 VAT**

PSU70 suitable for two HY120's **£14.58 + £1.17 VAT**

PSU90 suitable for one HY200 **£15.19 + £1.21 VAT**

PSU180 suitable for two HY2000's or one HY400 **£25.42 + £2.03 VAT**

TWO YEARS' GUARANTEE ON ALL OF OUR PRODUCTS

I.L.P. Electronics Ltd.

Graham Bell House

Roper Close

Canterbury

Kent CT2 7EP

Tel (0227) 54778

Please Supply _____

Total Purchase Price _____

I Enclose Cheque Postal Orders Money Order

Please debit my Access account Barclaycard account

Account number _____

Name & Address _____

Signature _____

For value in frequency counters, count on us.



You won't be disappointed. Because CSC offers more range, more accuracy, more versatility than anyone else . . . at lower prices. Choose from three portable, easy-reading counters and a compact, range-extending pre-scaler!

Our calculator-sized MAX-550 is the top of the line, with continuous readings from 1000 Hz up to a *guaranteed 550 MHz* and above. Measures AM, FM digital or video signals with this 6-digit, audio-to-UHF know-it-all. No switching or adjusting of polarity, slope, trigger or input level, either. Just turn it on and feed in signal. Only £102.06*

Our MAX-100 looks and performs like an expensive instrument. But it's not . . . even though it measures continuously from 20 Hz past a guaranteed 100 MHz, with 8-digit accuracy and 1 Hz resolution. With its high sensitivity, and big .6" LED display, MAX-100 is ideal for a wide range of audio, ultrasonic, RF, video and digital applications. Especially at a modest £85.37*

Price includes Post, Packing and VAT for 1-off. Prices are for UK only. For Europe and 10%. Outside Europe add 12½%.

Our MAX-50 may be mini in size, but it offers maximum value. Bringing down measurement costs for hams, computer enthusiasts and audiophiles. Completely automatic, MAX-50 accurately measures signals from 100 Hz to above a *guaranteed 50 MHz*. An outstanding value at only £59.94*

Our compact PS-500 Prescaler extends the capabilities of any 50/100 MHz counter from 50 to 500 MHz and beyond. The perfect companion to MAX-50 and MAX-100, it has a 400 mV output, to drive less sensitive counters. Modestly priced at £39.42*

When it comes to frequency measurement, we've got you covered. In range. Accuracy. And versatility — with a broad family of accessories from antennas and input connectors to AC and car-battery adaptors.

CSC. Capability you can count on . . . at a price you can afford.

We are manufacturers of breadboarding and testing devices, function generators, digital logical analysis and testing instruments, test clips and power boards. Send for a free catalogue.

Prices, specifications subject to change without notice. *Manufacturer's suggested list.

HOW TO ORDER: Tel: 0799 21682 and give us your Access, American Express or Barclaycard number, and your order will be in the post that night. Or send your order, enclosing cheque, postal order, or credit card number and expiry date. OR send for our latest FREE catalogue.

CONTINENTAL SPECIALTIES CORPORATION



Europe, Africa, Mid-East: CSC UK LTD.
Shire Hill Industrial Estate, Units 1 and 2
Saffron Walden, Essex CB 11 3AQ
Telephone Number: SAFFRON WALDEN 21682
TLX 817477 DEPT 15/L

AGENTS REQUIRED AT HOME AND ABROAD. PLEASE CONTACT MRS TINA KNIGHT DIRECT.

WW — 101 FOR FURTHER DETAILS

BIMENCLOSURES

ALL METAL BIMCASES

Red, Grey or Orange 14swg Aluminium removable top and bottom covers. 18 swg black mild steel chassis with fixing support brackets.

BIM 3000
(250x167.5x68.5mm)
£14.58




MINI DESK BIMCONSOLES

Orange, Blue, Black or Grey ABS body incorporates 1.8mm pcb guides, stand-off bosses in base with 4 BIMFEET supplied. 1mm Grey Aluminium panel sits recessed with fixing screws into integral brass bushes.

BIM 1005 (161 x 96 x 58mm) £2.18
BIM 1006 (215 x 130 x 75mm) £3.05

MULTI PURPOSE BIMBOXES

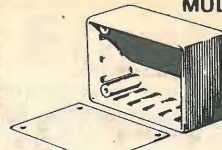

Orange, Blue, Black or Grey ABS with 1mm Grey Aluminium recessed front cover held by screws into integral brass bushes.

1.8mm pcb guides incorporated and 4 BIMFEET supplied.

BIM 4003 (85x56x28.5mm) £1.18
BIM 4004 (111x71x41.5mm) £1.62
BIM 4005 (161x96x52.5mm) £2.19

ALL METAL BIMCONSOLES

All aluminium, 2 piece desk consoles with either 15° or 30° sloping fronts, sit on 4 self-adhesive non-slip rubber feet. Ventilation slots in base and rear panel for excellent cooling. See latest catalogue for new styles and sizes

15° Sloping Panel


BIM7151 (102x140x51[28] mm) £10.67
BIM7152 (165x140x51[28] mm) £11.44
BIM7153 (165x216x51[28] mm) £12.61
BIM7154 (165x211x76[33] mm) £13.82
BIM7155 (254x211x76[33] mm) £15.36
BIM7156 (254x287x76[33] mm) £16.67
BIM7157 (356x211x76[33] mm) £17.58
BIM7158 (356x287x76[33] mm) £18.55

30° Sloping Panel

BIM7301 (102x140x76[28] mm) £10.67
BIM7302 (165x140x76[28] mm) £11.44
BIM7303 (165x183x102[28] mm) £12.61
BIM7304 (254x140x76[28] mm) £13.82
BIM7305 (254x183x102[28] mm) £15.36
BIM7306 (254x259x102[28] mm) £16.67
BIM7307 (356x183x102[28] mm) £17.58
BIM7308 (356x259x102[28] mm) £18.55

ABS & DIECAST BIMBOXES

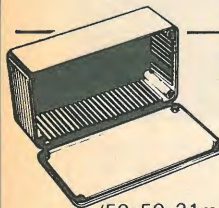
6 sizes in ABS or Diecast Aluminium. ABS moulded in Orange, Blue, Black or Grey. Diecast Aluminium in Grey Hammetone or Natural. All boxes incorporate 1.8mm pcb guides, stand-off supports in base and have close fitting flanged lids held by screws into integral brass bushes (ABS) or tapped holes (Diecast).



	ABS		Diecast		Hammetone		Natural	
(50x50x31mm)	N/A		BIM5001/11	TBA	£1.02			
(100x50x25mm)	BIM2002/12	£0.96	BIM5002/12	£1.46	£1.19			
(112x62x31mm)	BIM2003/13	£1.13	BIM5003/13	£1.78	£1.46			
(120x65x40mm)	BIM2004/14	£1.35	BIM5004/14	£2.24	£1.82			
(150x80x50mm)	BIM2005/15	£1.52	BIM5005/15	£2.84	£2.28			
(190x110x60mm)	BIM2006/16	£2.37	BIM5006/16	£3.94	£3.33			

Also available in Grey Polystyrene with no slots and self-tapping screws
BIM 2007/17 (112x61x31mm) £1.00

LOW PROFILE BIMCONSOLES

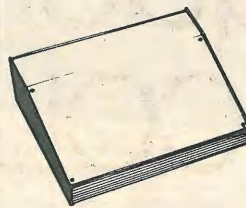

Orange, Blue, Black or Grey ABS body has ventilation slots as well as 1.8mm pcb guides and stand-off bosses in base. Double angle recessed front panel with 4 fixing screws into integral brass bushes. 4 BIMFEET supplied.

BIM 6005 (143 x 105 x 55.5 [31.5] mm) £2.37
BIM 6006 (143 x 170 x 55.5 [31.5] mm) £3.08
BIM 6007 (214 x 170 x 82.0 [31.5] mm) £4.12

EUROCARD BIMCONSOLES

Orange, Blue, Black or Grey ABS body accepts full or 1/2 size Eurocards, with bosses in the base for direct fixing. 1.8mm wide pcb guides incorporated and 4 BIMFEET supplied. 1mm Grey aluminium lid sits flush with body top and held by 4 screws into integral brass bushes.



BIM 8005 (169x127x70[45] mm) £4.12
BIM 8007 (243x187x103[66] mm) £6.10


BIMTOOLS + BIMACCESSORIES

MAINS BIMDRILLS

Small, powerful 240V hand drill complete with 2 metres of cable and 2 pin DIN plug. Accepts all tools with 1mm, 2mm or .125" dia. shanks Drills brass, steel, aluminium and pcb's. Under 250g, oil load speed 7500 rpm. Orange ABS, high impact, fully insulated body with integral on/off switch £10.53


Mains Accessory Kit 1 includes 1mm, 2mm, .125" twist drills, 5 burrs and 2.4mm collet £2.48

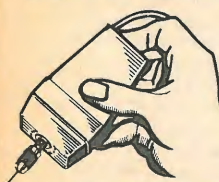Mains Kit 2 includes Mains BIMDRILL as above, 20 assorted drills, mops, burrs, grinding wheels and mounted points, 1mm, 2mm, 2.4mm and .125" collets. Complete in transparent case measuring 230x130x58mm £22.14



BIMDAPTORS

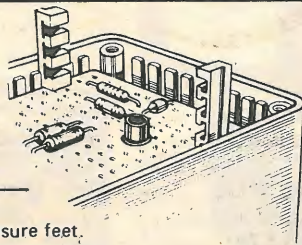Allows pcb's to be flat mounted sandwich fashion in BIMBOXES, BIMCONSOLES, and all other enclosures having 1.5mm wide vertical guide slots. One plastic BIMDAPTOR on each corner of pcb(s) enables assembly to be simply slid into place. 54mm long, 10 slots on 5mm spacing and can be simply snapped off to length. £1.08 per pack of 25.



BIMFEET

11mm dia. 3mm high, grey rubber self-adhesive enclosure feet. £0.77 per pack of 24



12 VOLT BIMDRILLS

2 small, powerful drills easily hand held or used with lathe/stand adaptor. Integral on/off switch and 1 metre cable.

Mini BIMDRILL with 3 collets up to 2.4mm dia. £ 8.10
Major BIMDRILL with 4 collets up to 3mm dia. £13.60

Accessory Kits 1 have appropriate drills and collets as above plus 20 assorted tools. Mini Kit 1 - £15.12, Major Kit 1 - £19.44. Accessory Kits 2 have appropriate drills, collets plus 40 tools and mains-12V dc adaptor. Mini Kit 2 - £34.02, Major Kit 2 - £39.42. Accessory Kits 3 as appropriate Kits 2 plus stand/lathe unit. Mini Kit 3 - £45.36, Major Kit 3 - £50.76.



BIMPUMPS


2 all metal desoldering tools provide high suction power and have easily replaceable screw in Teflon tips. Primed and released by thumb operation with in-built safety guard and anti-recoil system.

BIMPUMP Major (180mm long) £7.99
BIMPUMP Minor (150mm long) £6.80



BIMIRONS

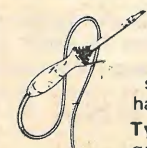Type 30 General Purpose 27 watt iron with long life, rapid change element, screw on tip, stainless steel shaft and clip on hook. Styled handle with neon. £4.05




Type M3 Precision 17 watt iron, quick change tip, long life element, styled handle with clip on hook. £4.43

BIMBOARDS



DIL COMPATIBLE BIMBOARDS

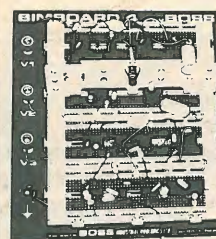

Accept all sizes (4-50 pin) of DIL IC packages as well as resistors, diodes, capacitors and LEDs. Integral Bus Strips up each side for power lines and Component Support Bracket for holding lamps, switches and fuses etc. Available as single or multiple

units, the latter mounted on 1.5mm thick black aluminium back plate which stand on non slip rubber feet and have 4 screw terminals for incoming power.

BIMBOARD 1 has 550 sockets, multiple units utilising 2, 3 and 4 BIMBOARDS incorporate 1100, 1650 and 2200 sockets, all on 2.5mm (0.1") matrix.

BIMBOARD 1 £ 8.83
BIMBOARD 2 £21.01
BIMBOARD 3 £29.84
BIMBOARD 4 £38.79

DESIGNER PROTOTYPING SYSTEM

1, 2, or 3 BIMBOARDS mounted on BIM 6007 BIMCONSOLE with Integral Power Supply (±5 to ±15Vdc @ 100mA and fixed +5Vdc @ 1A) All O/P's fully isolated. Short circuit and fast fold back protection. Power rails brought out to cable clamps that accept stripped wire or 4mm plug.

DESIGNER 1 £55.62
DESIGNER 2 £61.02
DESIGNER 3 £66.42

NEC

RADIO AMATEUR COMMUNICATION EQUIPMENT
NIPPON ELECTRIC

CQ-P-2200E 2 meter FM 12 channel portable/mobile 1/3 watt transceiver
137-150 Mhz



Features: battery cartridge system, all 12 channels X-tal fitted, 1750 Hz tone-call system, AXC or RIT switchable, highly efficient squelch, high (3 watts) low (1 watt) output power switchable, lambda 1/4 or 5/8 telescopic antenna selectable. Provisions for: external power 13.5 V DC, external antenna, earphone, external speaker. NEW: Professional plug-in moduls construction, with all units shielded, selected high quality parts secure long life. Range: up to 50 KM. direct, up to several hundreds of kilometers over repeaters. Universality: mobile or portable (with the snip of a finger). High sensitivity: 0.2 uV for 20 db S/N.

CQ-R-700 6 band general coverage receiver with ultra high sensitivity (0.1 uV for 170 KHz-30.0 Mhz 15 db S/N on 30 Mhz)



Features: VFO patent allows perfect frequency read-off and tune-in with ease. Selectivity selectable wide/narrow. Modes: SSB (USB/LSB), CW or AM. Noise-blanker incorporated, large, illuminated two colour S-meter, 500 KHz and 50 Hz calibration facility. Modern electrical layout. A true solution for all searching a reliable mean for short range or continuous long haul reception.

CQ-LINE 300 - 3000 watts HF-LINE. Modes: USB/LSB, CW, AM, RTTY (FSK), FAX in 1.6 - 30.0 Mhz full digital readout.




In many thousands of applications the CQ-LINE has proven their reliability and sturdiness. Its versatility and high power make the CQ-LINE a true partner for long distance communication. Even with simple antenna from home or car, world-wide contacts are no problem.

UK: please contact our distributor Messrs. William Munro, Invergordon, High Street 100, telef.: 349-852351-4 - Telex: 75265.

CEC SOLE DISTRIBUTOR EUROPE OF **NEC**
RADIO AMATEUR AND CB EQUIPMENT
VIA VALDANI, 1, CH 6830 CHIASSO/SWITZERLAND,
TELEF. 091/446464, TELEX 64077 CEC CH
WW-046 FOR FURTHER DETAILS

THE NEW MOST IMPORTANT LINK

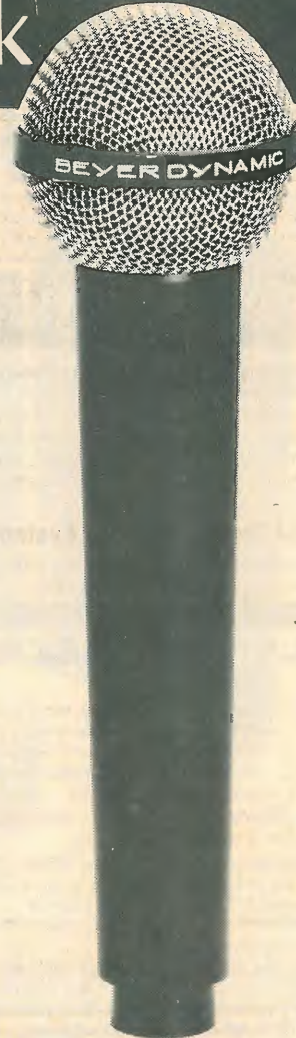

IN THE P.A. CHAIN . . .
M 260 NS

DYNAMIC RIBBON MICROPHONE

Specifications:

Frequency Response:	50 — 18 000 Hz
Polar Pattern:	Hypercardioid
Output Level:	0,9mV/PA ± -60 dbm
EIA Sensitivity Rating:	- 153 dbm
Electrical Impedance:	200 ohms
Load Impedance:	> 1000 ohms

Excellent anti-feedback characteristic over the whole frequency range.

Send now for Brochure to:
BEYER DYNAMIC (GB) LTD.
1 Clair Rd., Haywards Heath, Sussex


NAME

ADDRESS

WW-048 FOR FURTHER DETAILS

Understanding Digital Electronics

New teach-yourself courses

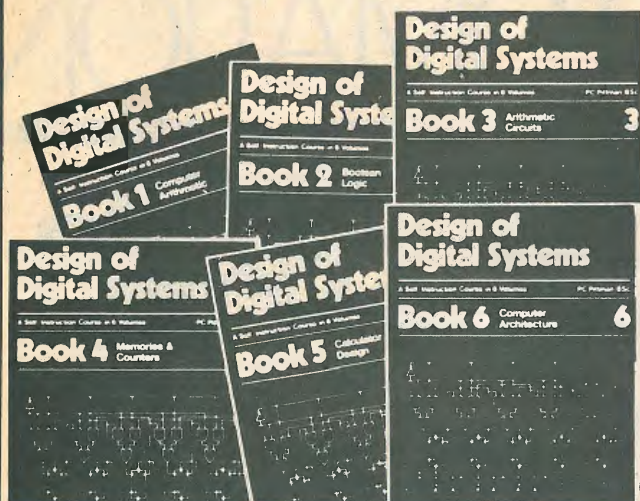

In the years ahead the products of digital electronics technology will play an important part in your life. Calculators and digital watches are already commonplace. Tomorrow a digital display could show your vehicle speed and petrol consumption; you could be calling people by entering their name into a telephone which would automatically look up their number and dial it for you.

These courses were written by experts in electronics and learning systems so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being faster and more thorough than classroom learning. You work at your own pace and must respond by answering questions on each new piece of information before proceeding.

After completing these courses you will have broadened your career prospects and increased your fundamental understanding of the rapidly changing technological world around you.

The six volumes of Design of Digital Systems cost only: £8.10
And the four volumes of Digital Computer Logic and Electronics cost only: £4.60
But if you buy both courses, the total cost is only: £12.00


+ 90p post & packing
 + £1 post & packing

Price includes surface mail anywhere in the world — Airmail extra.

Design of Digital Systems is written for the engineer seeking to learn more about digital electronics. Its six volumes — each A4 size — are packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra to memories, counters and simple arithmetic circuits, and finally to a complete understanding of the design and operation of calculators and computers.

The contents of Design of Digital Systems include:

- Book 1** Octal, hexadecimal and binary number systems; conversion between number systems; representation of negative numbers; complementary systems; binary multiplication and division.
- Book 2** OR and AND functions; logic gates. NOT, exclusive OR, NAND, NOR and exclusive-NOR functions; multiple input gates; truth tables; De Morgans Laws; canonical forms; logic conventions; Karnaugh mapping; three-state and wired logic.
- Book 3** Half adders and full adders; subtractors; serial and parallel adders; processors and arithmetic logic units (ALUs); multiplication and division systems.
- Book 4** Flip flops; shift registers; asynchronous and synchronous counters; ring, Johnson and exclusive-OR feedback counters; random access memories (RAMs) and read only memories (ROMs).
- Book 5** Structure of calculators; keyboard encoding; decoding display data; register systems; control unit; program ROM; address decoding; instruction sets; instruction decoding; control program structure.
- Book 6** Central processing unit (CPU); memory organisation; character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming; assemblers; computers; executive programs; operating systems and time sharing.

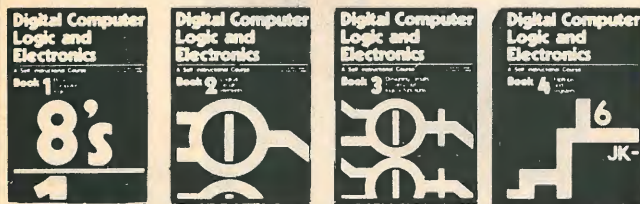

Digital Computer Logic and Electronics is designed for the beginner. No mathematical knowledge other than simple arithmetic is assumed, though the student should have an aptitude for logical thought. It consists of four volumes — each A4 size — and serves as an introduction to the subject of digital electronics. Everyone can learn from it — designer, executive, scientist, student, engineer.

Contents include: Binary, octal and decimal number systems; conversion between number systems; AND, OR, NOR and NAND gates and inverters; Boolean algebra and truth tables; De Morgans Laws; design of logic circuits using NOR gates; R-S and J-K flip flops, binary counters, shift registers and half adders.

CAMBRIDGE LEARNING ENTERPRISES, UNIT 35, RIVERMILL SITE, FREEPOST, ST. IVES, HUNTINGDON, CAMBS. PE17 4BR, ENGLAND
TELEPHONE: ST. IVES (0480) 67446

PROPRIETORS: DAYHIDGE LTD. REG. OFFICE: RIVERMILL LODGE, ST. IVES
 REGD. IN ENGLAND No. 1328762

Flow Charts & Algorithms

HELP YOU PRESENT

safety procedures, government legislation, office procedures, teaching materials and computer programs by means of YES and NO answers to questions.

THE ALGORITHM WRITER'S GUIDE explains how to define the questions, put them in the best order and draw the flow chart, with numerous examples shown. All that students require is an aptitude for logical thought. Size A5, 130 pages. This book is a MUST for those with things to say.

£2.95 + 45p post & packing by surface mail anywhere in the world. Airmail extra.

GUARANTEE

If you are not entirely satisfied your money will be refunded.
 Please allow 21 days for delivery

Cambridge Learning Enterprises, Unit 36, Rivermill Site
 Freepost, St. Ives, Huntingdon, Cambs. PE17 4BR
 England

Please send me the following books

-sets Digital Computer Logic & Electronics @ £5.50, p&p included
-sets Design of Digital Systems @ £9.00, p&p included
-Combined sets @ £13.00, p&p included
-The Algorithm Writer's Guide @ £3.40, p&p included

Name

Address

I enclose a cheque/PO payable to Cambridge Learning Enterprises for £.....
 Please charge my Access/Barclaycard/Visa/Eurocard/Mastercharge/Interbank account number

Signature deleted as appropriate
 Telephone orders from credit card holders accepted on 0480-67446 (ansafone). Overseas customers should send a bank draft in sterling drawn on a London Bank. ww36

programme, plug in and switch on to BULGIN AUTOMATION

Building an industrial control system has never been simpler. Wherever there is a need to automate production machinery or process plant the new Bulgin System is the answer.

Sequences, times and other quantities required for a programme are simply set up on each module with a screwdriver. Then each module is plugged into the mother board and switched on. It's as easy as that!

Result — a great deal of time and money saved, plus a really reliable and robust control system that *you* have matched precisely to your machine or process.

Send for our brochure today.



BULGIN

MODULAR CONTROL SYSTEM

Bulgin Electronics



One of the Bulgin Group of Companies **Soundex Ltd**
Park Lane, Broxbourne, Herts. Tel: Hoddesdon 64455

WW — 086 FOR FURTHER DETAILS

NEW! Cassette copiers from PENTAGON

Simple operation — fully automatic 16 times speed.
Choice of one or three copies. C32/34 —
outproduces all other makes — 75 C60 per hour.
Budget Price from £587 + VAT

Model
C32S —
Mono
C34S —
Stereo

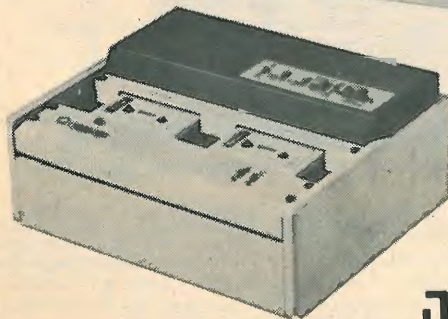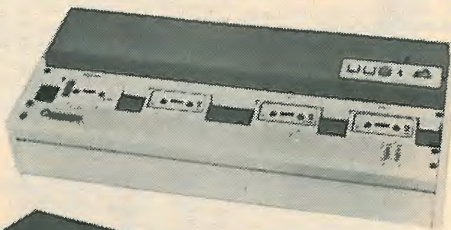

Model
C-1 —
Mono
C-4 —
Stereo


PENTAGON from ITA

1-7 Harewood Avenue, Marylebone Road
London NW1. Tel. 01-724 2497. Telex: 21879

WW — 088 FOR FURTHER DETAILS

FYLDE

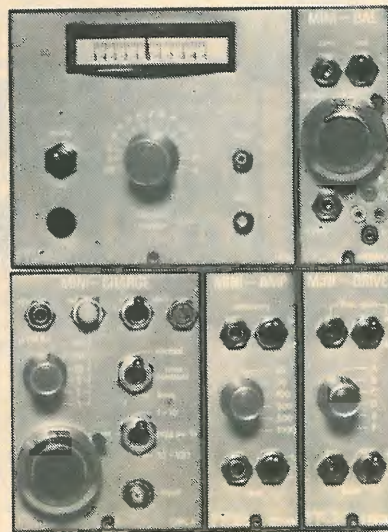TRANSDUCER and RECORDER AMPLIFIERS and SYSTEMS



reliable high performance & practical controls. individually powered modules—mains or dc option single cases and up to 17 modules in standard 19" crates small size—low weight—realistic prices.

FYLDE

49/51 Fylde Road Preston
PR1 2XQ
Telephone 0772 57560

Fylde
Electronic
Laboratories
Limited.

WW — 059 FOR FURTHER DETAILS

Amid the confusion . . .

So much is stated, contradicted and re-stated, but in the end it is not a matter of opinion.

Other things being equal, 'goodness' can be expressed in simple terms. A pick-up arm should have the lowest possible effective mass, coupled with the highest possible rigidity.

A cartridge should have the lowest possible effective tip mass, coupled with a correctly related compliance and tare (cartridge weight).

These are the rules of physics and engineering. They can be denied for various reasons but the penalty is then paid each time you play a record.

Immediately available.


In case of difficulty write to Dept 0650, SME Limited Steyning, Sussex, BN4 3GY

SME

The best pick-up arm in the world

The Series III precision pick-up arm and Shure V15 Type IV cartridge. Designed and built by the rules for faithful, uncoloured musical reproduction.


**Design Council
Award 1978**

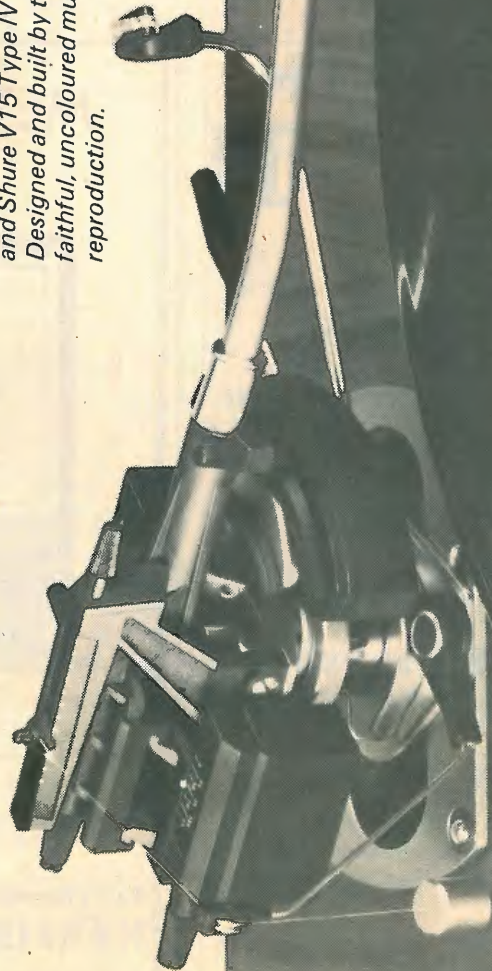

"Stereo Sound is Japan's principal hi-fi magazine. The Summer '78 issue carries an article compiled by seven leading critics. Of forty-three arms they recommend the SME Series III as the best and the Series II Improved as good".



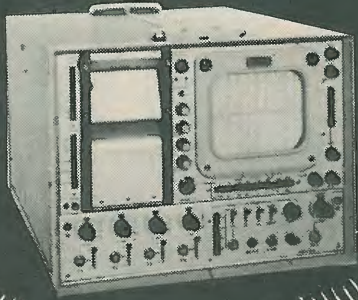A NEW INSTRUMENT FOR WIDENING INDUSTRIAL APPLICATIONS



The FOR-4 Mark 2

The new Medelec FOR-4-2 fibre optic recording oscilloscope is the result of a constant research and development policy. It incorporates many refinements which have been made to customers' special requirements.

The FOR-4-2 provides industrial and research users with high quality recording facilities at really low cost. X-Y Plot, Transient and Raster mode are all available in a single instrument.

Special features of the Medelec FOR-4-2 include:

- 10 times gain X and Y (1mV/cm on 4 Y channels)
- Fully automatic triggering (with higher sensitivity)
- Improved recording facilities (for greater flexibility)
- Light control filter (for excellent contrast)
- Wide speed range (from 0.1 to 1000 mm/sec - in 3 models)
- Internal loudspeaker (for audio monitoring)

For further information on the new FOR-4-2 or instruments in the range, contact:

MEDELEC LIMITED
Manor Way, Woking
Tel: Woking (048 62) 70331
Telegrams: Medelec, Woking


medelec



Leaders in Fibre Optic Recording

HARMSWORTH


FASTENERS FOR ELECTRONICS
FASTEX

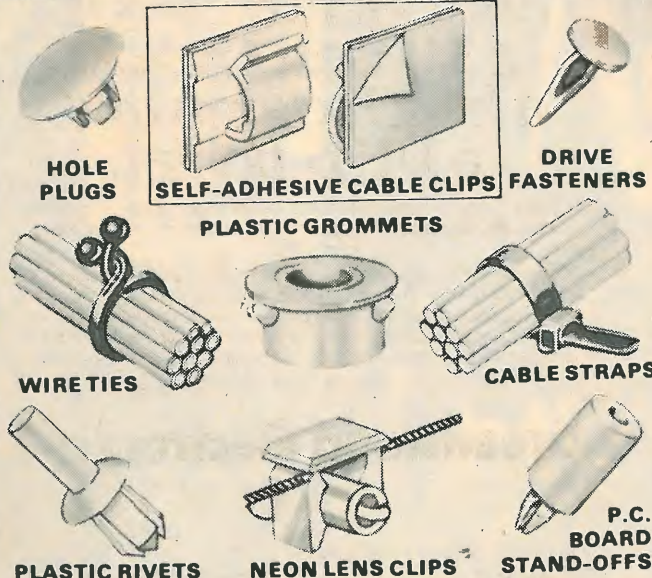

One piece mouldings made from thermoplastic materials for mechanical strength, high electrical and vibration resistance. Fast to install. Reduced in-place costs. Leaflets on request.

HARMSWORTH, TOWNLEY & CO. LTD.
HAREHILL TODMORDEN LANCS OL14 5JY
Phone TODMORDEN 2601 (STD 070-681 2601)

METER PROBLEMS?

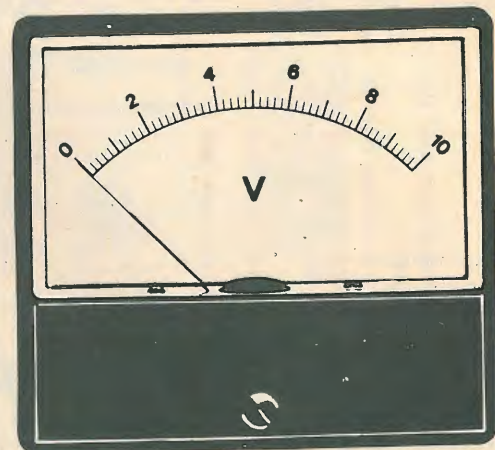

137 Standard Ranges in a variety of sizes and stylings available for 10-14 days delivery. Other Ranges and special scales can be made to order.

Full Information from:

HARRIS ELECTRONICS (London)

138 GRAYS INN ROAD, W.C.1 Phone: 01/837/7937


WW - 077 FOR FURTHER DETAILS

WATFORD ELECTRONICS

33 CARDIFF ROAD, WATFORD, HERTS, ENGLAND

Tel. Watford 40588/9.

DM 900

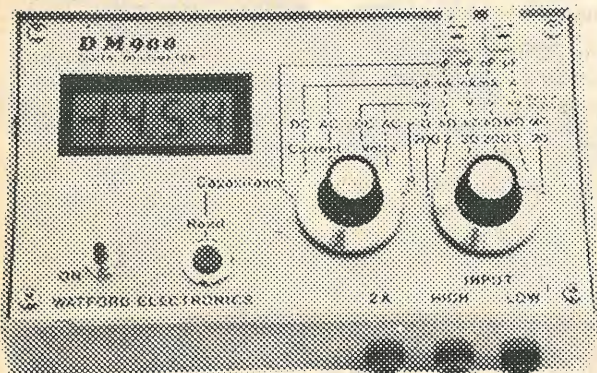

THERE ARE 900 REASONS FOR BUYING THIS MULTIMETER (with direct reading capacitance range)

Its 900 cubic centimetres are packed with up to the minute technology offering a low cost yet accurate method of measuring voltage, current, resistance and capacitance too, on a total of 30 RANGES. The WATFORD ELECTRONICS DM900 uses latest MOS Integrated Circuits which drive a 3½ digit Liquid Crystal Display for extremely low power consumption.

Specifications:

- | | |
|-----------------------------------------|---------------------------------------------------|
| ● DC VOLTS 5 ranges 200mV to 1KV | } $Z_{in} > 10M\Omega$ |
| ● AC VOLTS 5 ranges 200mV to 1KV | |
| ● DC CURRENT 5 ranges 200µA to 2A | |
| ● AC CURRENT 5 ranges 200µA to 2A | |
| ● RESISTANCE 6 ranges 200Ω to 20MΩ | |
| ● DIODE Voltage Drop 100nA to 10mA | |
| ● CAPACITANCE 4 ranges 2nF to 2µF | |
| ● Accuracy on all ranges better than 1% | ● Isolated Floating Ground |
| ● 0.5" 3½ digit LCD Display | ● Dual Slope A/D Conversion |
| ● Single 9V (PP3) Power Supply | ● Critical Input Protection |
| ● Sampling Rate > 2 per second | ● Overrange Indication |
| ● Display Test Facility | ● Polarity Indication |
| ● Battery Test Facility | ● True Auto Zero |
| ● Movable Decimal Point | ● 30 Ranges |
| | ● Overall size: 160 x 95 x 60mm |
| | ● Colour: Grey (standard) Black Orange (optional) |

The DM900 incorporates dual slope A/D conversion; true auto zero; polarity and overrange indication; battery and display test facilities. Its input impedance of over 10MΩ allows voltage measurements in high impedance circuits without distorting circuit operation.

The DM900 is small and robust. It measures only 160 x 95 x 60mm and is housed in an ABS case which will fit in your coat pocket or briefcase.


The DM900 has been specially designed for Watford Electronics and is available in kit form or ready built.

Special Offer: £78.50 plus VAT (p&p insured add 80p)

Also available in Kit form for the Enthusiast at **£54.50 plus VAT plus 80p** (probes and carrying case £3.00 extra).

WW—026 FOR FURTHER DETAILS

New from GREENWOOD

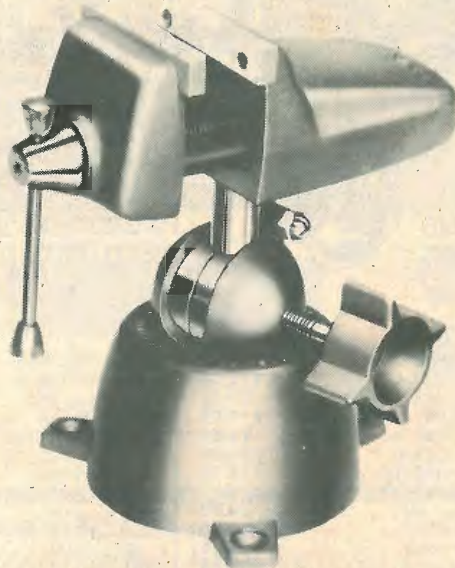

PANAVISE®

a precision vice
that rotates a full
360 degrees-tilts
180 degrees from
vertical to horizontal,
and offers a choice
of 3 bases, 3 heads,
a bench clamp and
a PCB holder.

We think it's like no other vice you've ever used. Its head rotates a full 360 degrees - and tilts 180 degrees from vertical to horizontal.

One conventional knob locks work in any desired position, firmly yet gently. You can choose a standard, low profile or vacuum base - a standard, low profile or wide opening head - a bench clamp mounting base - a printed circuit board holder and of course replacement jaws and pads if ever you need them.

Panavise is more than just a vice - it's a system.

Greenwood Electronics

Greenwood Electronics, Portman Road, Reading RG6 1NE
Telephone 0734-599844 Telex 74598

Obtainable also from our distributors:

Electroplan Ltd
P.O. Box 19, Orchard Road,
Royston, Herts SG8 5HH.

West Hyde Developments Ltd
Unit 9, Park Street Industrial Estate,
Aylesbury, Bucks HP20 1ET.

Toolrange Ltd
Upton Road, Reading RG3 4JA.
Special Products Distributors Ltd
81, Piccadilly, London, W1.
ITT Electronic Services
Edinburgh Way, Harlow,
Essex CM20 2DF.

WW — 071 FOR FURTHER DETAILS

WILMSLOW AUDIO

The firm for Speakers

HI-FI DRIVE UNITS



PA GROUP & DISCO UNITS



WILMSLOW AUDIO

KITS FOR MAGAZINE DESIGNS etc.



SPEAKER KITS



HD12 9D25	£6.00
HD13 D34H	£12.00
HD20 BZ5J4	£9.45
HD20 B25H4	£11.98
HD11 P25EBC	£5.56
Baker Superb	£22.50
Castle 8RS/DD	£12.35
Chartwell CE205 8" bass, matched pairs only	£59.90
Coles 4001	£6.25
Coles 3000	£6.25
Celestion HF1300 II	£8.25
Celestion HF2000	£9.95
Dalesford D10 tweeter	£8.25
Dalesford D20/105 4"	£10.95
Dalesford D30/110 5"	£10.95
Dalesford D50/153 6 1/2"	£11.95
Dalesford D50/200 8"	£11.95
Dalesford D70/250 10"	£24.95
Dalesford D100/310 12"	£34.95
Decca London	£41.25
Decca CO/1000/8	£8.95
Decca DK30	£27.50
E.M.I. type 350 4 ohm	£9.25
E.M.I. 14A/770 14" x 9"	£16.95
E.M.I. 8" x 5" d/c 10 watt	£3.95
Isophon KK10/8	£8.25
Isophon KK8/8	£7.50
Jordan Watts Module	£17.95
Jordan 50mm Unit	£22.50
Jordan CB Crossover	£22.50
KEF T27	£8.50
KEF B110	£10.95
KEF B200	£11.95
KEF B139	£24.95
KEF DN13	£4.95
KEF DN12	£7.25
KEF DN22 pair	£36.00
Lowther PM6	£49.95
Lowther PM6 MKI	£52.00
Lowther PM7	£86.50
Peerless DT10HFC	£9.75
Peerless K010DT	£8.95
Peerless K040MRF	£11.75
Radford BD25 II	£26.95
Radford MD9	£14.50
Radford MD6	£17.95
Radford FN8/FN831	£19.95
Richard Allan CG8T	£9.95
Richard Allan CG12T Super	£22.45
Richard Allan HP8B	£15.50
Richard Allan LP8B	£10.35
Richard Allan HP12B	£25.25
Richard Allan DT20	£7.25
Richard Allan DT30	£7.45
Seas HO86	£8.75
Shackman Electrostatic C/W polar network & X/O pair	£112.00
Tannoy HPD 295A	£78.00

Tannoy HPD 315A	£87.00
Tannoy HPD 385A	£105.00
Baker Group 25	£13.00
Baker Group 35	£14.50
Baker Group 50/12	£21.00
Baker Group 50/15	£33.00
Celestion G12M	£13.50
Celestion G12H	£17.95
Celestion G18C	£41.95
Celestion G12/75 (alum. dome)	£22.50
Celestion G12/75 (d/cone)	£24.50
Celestion G12M/50 (cambric edge)	£16.95
Celestion G15/100 (alum dome)	£32.50
Celestion MH1000	£13.50
Celestion Powercell 12"/100	£45.95
Celestion Powercell 15"/100	£48.95
Celestion Powercell 15"/125	£51.95
Fane Pop 40	£10.95
Fane Pop 50H	£12.50
Fane Pop 75	£16.95
Fane Pop 65	£19.95
Fane Pop 80	£21.95
Fane Pop 100	£35.95
Fane J44 horn	£6.50
Fane J104 horn	£13.75
Fane J73 horn	£9.75
Fane Guitar 80L	£19.75
Fane Guitar 80B	£19.95
Fane Disco 80	£21.50
Fane PA80	£19.50
Fane Bass 85	£29.95
Fane Crescendo 12A	£42.95
Fane Crescendo 12B	£44.95
Fane Crescendo 15/100	£54.95
Fane Crescendo 15/125	£64.95
Fane Crescendo 18	£75.95
Fane 920 II Horn	£45.95
Fane HPX1/HPX2	£2.50
Goodmans 8PA	£4.25
Goodmans 12P	£19.75
Goodmans 12PD	£22.50
Goodmans 12PG	£21.25
Goodmans 18P	£45.50
Goodmans 50HX	£20.50
McKenzie C1280	£22.95
McKenzie GP15	£32.95
McKenzie TC15	£32.95
McKenzie CG15 Bass	£55.95
Motorola Piezo Horn	£8.50
Richard Allan HD8T	£14.50
Richard Allan HD10T	£15.75
Richard Allan HD12T	£20.95
Richard Allan HD15	£36.95
Richard Allan HD15T	£37.95

Kits include drive units, crossovers, BAF/Long fibre wool, etc. for pair of speakers. Carriage £3.50

Practical HiFi & Audio PRO9-TL (Rogers) £118.00

Felt panels for PRO9-TL £5.50 + £1.50 p&p

HiFi Answers Monitor (Rogers) £129.00

HiFi News State of the Art (Atkinson) £161.00

Popular HiFi Mini Monitor (Colloms) £63.00

Popular HiFi Round Sound (Stephens) including complete cabinet kit £68.00

Popular HiFi (Jordan) £91.00

Practical HiFi & Audio Monitor (Giles) £119.00

Practical HiFi & Audio Triangle (Giles) £86.00

Practical HiFi & Audio BSC3 (Rogers) £60.00

Practical HiFi Mini Triangle (Giles) £99.00

HiFi News Tabor (Jones) £59.75

HiFi News Tabor (with H4 bass units) £65.00

Wireless World T.L./KEF (Bailey) £112.00

Wireless World T.L./Radford (Bailey) £154.00

HiFi News Minilink (Atkinson) £43.00

SMART BADGES FREE WITH ALL ABOVE KITS (TO GIVE THAT PROFESSIONAL TOUCH TO DIY SPEAKERS!)

Send 3 x 7p stamps for reprints/construction details of any of above designs.

CARRIAGE & INSURANCE

Tweeters/Crossovers	40p each
Speakers up to 10"	75p each
Speakers 12"	£1.50 each
Speakers 15"	£2.50 each
Speakers 18"	£3.50 each
Speaker Kits	£2.50 pair
Mag. design kits	£3.50 pair

Prices per pair. Carriage £2.50.

Dalesford System 1	£52.90
Dalesford System 2	£55.75
Dalesford System 3	£101.75
Dalesford System 4	£108.00
Dalesford System 5	£139.00
Dalesford System 6	£93.00
Eagle SK210	£15.00
Eagle SK215	£29.00
Eagle SK320	£37.00
Eagle SK325	£67.00
Eagle SK335	£91.00
Goodmans DIN20	£31.50
Goodmans Mezzo Twinkit	£51.95
Kef Kit I	£59.50
Kef Kit III	£119.95 (carr. £5)
Lowther PM6 Kit	£103.00
Lowther PM6 MKI Kit	£108.00
Peerless 1060	£71.95
Peerless 1070	£122.00
Peerless 1120	£139.00
Peerless 2050	£49.95
Peerless 2060	£65.95
Radford Studio 90	£154.00
Radford Monitor 270	£208.00
Radford Studio 270	£275.00
Radford Studio 360	£390.00
RamKit 50 (makes Ram 100)	£69.95
Richard Allan Tango Twin Assembly	£43.50

Richard Allan Maramba T.R.8 £61.50

Richard Allan Charisma T.R.12 £90.00

Richard Allan Super Triple £73.00

Richard Allan RA8 £46.50

Richard Allan RA82 £74.00

Richard Allan RA82L £79.95

Seas Mini £17.90

Seas 203 £35.50

Seas 302 £43.90

Seas 303 £73.90

Seas 503 £119.90

Wharfedale Denton 2XP £26.95

Wharfedale Linton 3XP £41.95

Wharfedale Glendale 3XP £56.95

Everything in stock for the speaker constructor! BAF, long fibre wool, foam, crossovers, felt panels, components, etc. Large selection of grille fabrics. (Send 15p in stamps for fabric samples) (Prices correct at 1/1/79).

SWIFT OF WILMSLOW
The firm for Hi-Fi
5 Swan Street,
Wilmslow, Cheshire.

Send 15p stamp for free 38 page catalogue 'Choosing a Speaker'

Telephone: Speakers, Mail Order and Export: 0625 529599. Hi-Fi: 0625 526213

Lightning service on telephoned credit card orders!

WILMSLOW AUDIO
The firm for Speakers

Swan Works, Bank Square,
Wilmslow, Cheshire.



OUR RANGE OF PRODUCTS ARE NOW INDIVIDUALLY AND ATTRACTIVELY PACKAGED

Our new catalogue lists circuit boards for all your projects, from good old Veroboard through to specialised boards for ICs. And we've got accessories, module systems, cases and boxes — everything you need to give your equipment the quality you demand. Send 25p to cover post and packing, and the catalogue's yours.

VERO ELECTRONICS LTD. RETAIL DEPT.
Industrial Estate, Chandlers Ford, Hants. SO5 3ZR
Telephone Chandlers Ford (04215) 2956


WW — 009 FOR FURTHER DETAILS

745 COUNTER TIMER

DC-32 MHz

FREQUENCY, PERIOD, TIME & TOTALISE

± 5ppm STABILITY @ 25°C

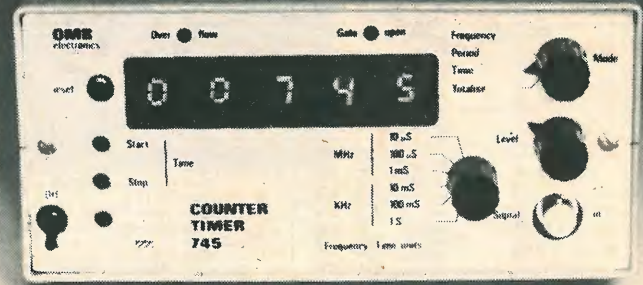

745 COUNTER TIMER £97 + £2.50 P&P

WW 094

Other products include:


- | | |
|-----------------------------------------|--------|
| 643 Function Generator £105 | WW 095 |
| 643A Function Generator £89 | WW 096 |
| 631 Filter Oscillator £112 | WW 097 |
| 746 Autoranging Frequency Meter £75 | WW 098 |
| 615 Off Air Standard £81 | WW 099 |
| 35 Series Digital Panel Meters from £26 | WW 100 |

Delivery is normally ex-stock — telephone for confirmation
Prices correct at time of going to press, subject to change without notice


OMB electronics, Riverside, Eynsford, Kent. Tel: 0322 863567

LOWE ELECTRONICS LTD.

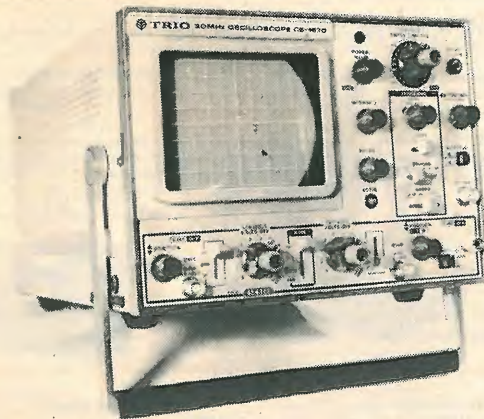119 CAVENDISH ROAD, MATLOCK, DERBYSHIRE
TEL. 0629 2430 OR 2817. TELEX 377482 LOWLEC G



New Model

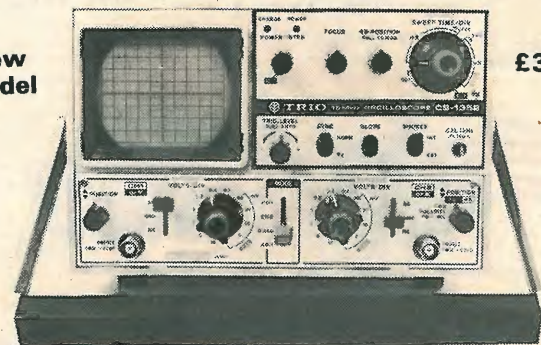

£389

CS1352 DC—15MHz and 2mV/CM AND portable AC/DC/Internal battery

TRIO OSCILLOSCOPES


The Trio range of oscilloscopes offer top quality at moderate cost. The brief specifications show the performance features which have made these oscilloscopes firm favourites in all parts of the world, with bandwidths to 30 MHz and sensitivities down to 1mV/cm on 130 mm screens. Prices are very realistic and we try to ensure that delivery is ex-stock at all times — quite a change these days.

CS-1570 130mm DUAL TRACE TRIGGERED SWEEP OSCILLOSCOPE

£512 + 8% VAT
including two X10
Full Bandwidth Probes

- 130mm mesh PDA
- DC-30MHz/5mV
- Delay line
- Auto level triggering
- Display modes (CH1 CH2 DUAL ADD)
- Trigger modes (AC LF Rej HF Rej DC)

- SPECIFICATION**
- Bandwidth: DC to 30MHz (—3dB)
 - Deflection factor: 5mV/div to 5V/div
 - Input R.C. 1MΩ 24pF
 - Risetime: 11.7nsec
 - Overshoot: Better than 3%
 - Signal delay: 160nsec
 - Polarity: CH2 can be inverted
 - Sweep time: 0.2μs/div to 0.5s/div
 - Magnifier: x 5
 - Linearity: Better than 3%
 - Calibrator: 0.5Vpp (1kHz square wave)
 - Intensity modulation: More than 5Vpp
 - Phosphor: P31
 - Power: AC 100/120/220/240V 50/60Hz, 25W
 - Dimensions: W260 x H190 x D375 (mm)
 - Weight:

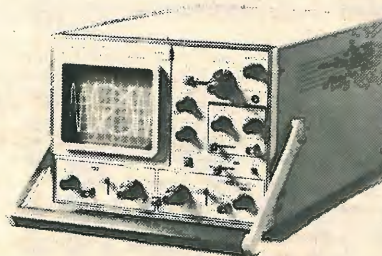

CS 1575
Unique 4 function audio analysis scope. Shows not only two channels but also phase relationship between them. DC—5MHz 1mV/CM A must for the audio engineer/repairman

£288

Also available
CS1560A 15MHz £352
CS1562 10MHz £290
And many more items of Trio Equipment
55p for full catalogue and price list

FOR FULL DETAILS ON THESE AND OTHER MODELS, CONTACT THE SOLE AGENTS, LOWE ELECTRONICS

WW—034 FOR FURTHER DETAILS

MHz electronics

2111 WEST CAMELBACK SUITE B PHOENIX, ARIZONA USA

(602) 242-3037

R F Transistors

Type	Price	Type	Price	Type	Price
2N1561	\$15.00	2N5637	\$20.70	HEPS3006	\$19.90
2N1562	15.00	2N5641	4.60	HEPS3007	24.95
2N1692	15.00	2N5643	20.70	HEPS3010	11.34
2N1693	15.00	2N5764	27.00	HEPS5026	2.56
2N2857JAN	2.45	2N5862	50.00	MMCM918	1.00
2N2876	12.35	2N5913	3.25	MMT72	.61
2N2880	25.00	2N5922	10.00	MMT74	.94
2N2927	7.00	2N5942	49.50	MMT2857	1.43
2N2947	17.25	2N5943	1.75	MMT3960A	6.25
2N2948	15.50	2N5944	7.50	PT4186B	3.00
2N2949	3.90	2N5945	10.90	PT4571A	1.50
2N2950	5.00	2N5946	13.20	PT8659	10.72
2N3287	4.30	2N6080	5.45	PT9784	24.30
2N3300	1.05	2N6081	8.60	PT9790	41.70
2N3302	1.05	2N6082	9.90	PT9847	26.40
2N3307	10.50	2N6083	11.80	JO4030	15.60
2N3309	3.90	2N6084	13.20	40281	10.90
2N3375	7.00	2N6094	5.75	40282	11.90
2N3553	1.80	2N6095	10.35	40290	2.48
2N3818	6.00	2N6096	19.35	TA7994	50.00
2N3824	3.20	2N6097	28.00		
2N3866	1.09	2N6136	18.70	FET's	
2N3866JAN	4.14	2N6166	36.80	40673	1.39 or 10/10.00
2N3866JANTX	4.85	2N6439	43.45	3M128	1.35 or 10/10.00
2N3924	4.00	MM1500	32.20	2N5248	.60 or 10/ 4.50
2N3925	6.00	MM1550	10.00	MPP102	.45 or 10/ 3.50
2N3927	11.50	MM1552	50.00	MEM631	.63 or 10/ 5.30
2N3950	26.25	MM1553	56.50		
2N3961	6.60	MM1601	5.50	TERMS :	
2N4072	1.70	MM1602	7.50	All CHECKS and MONEY ORDERS ARE	
2N4073	2.00	MM1607	8.65	IN US FUNDS !!!	
2N4135	2.00	MM1620	17.50	ALL ORDERS SENT AIRMAIL DAY	
2N4427	1.24	MM1661	15.00	Please include \$2.50 Minimum for	
2N4430	20.00	MM1669	17.50	postage.	
2N4440	8.60	MM1943	3.00	ALL PRICES IN US DOLLARS.	
2N4957	4.00	MM2605	3.00	ALL PARTS PRIME/GUARANTEED.	
2N4958	6.30	MM2608	5.00		
2N4959	2.12	MM8002	2.05	BANK AMERICARD/VISA/MASTERCARD	
2N4976	19.00	MM8006	2.12	Your Number;	
2N5070	13.80	MRF245	31.05		
2N5090	6.90	MRF304	43.45	Exp. Date	
2N5108	3.90	MRF501	.49	Your Signature	
2N5109	1.55	MRF504	6.95		
2N5160	3.34	MRF509	4.90	IC's	
2N5177	20.00	MRF511	8.60	MCI530C	1.50
2N5179	.68	MRF646	20.70	MCI590C	6.50
2N5184	2.00	MRF5177	20.70	MC4024F	3.27
2N5216	47.50	MRP8004	1.90	TMS4024	10.00
2N5589	4.60	HEP76/S3014	4.95		
2N5590	6.30	HEPS3002	11.30		
2N5591	10.35	HEPS3003	29.88		
		HEPS3005	9.55		

MHZ Electronics Kits :

Kit # 1
 Motorola MC14410CP CMOS Tone Generator.
 CMOS Tone Generator uses 1 MHz crystal to produce standard dual frequency dialing signal. Directly compatible with 12 key Chomeric Touch Tone Pads. Kit includes the following:
 1 Motorola MC14410CP Chip
 1 1 MHz Crystal
 1 PC Board
 And all other parts for assembly. **NOW ONLY \$15.70**

Kit # 2
 Fairchild 95H90DC Prescaler 350MHZ.
 95H90DC Prescaler divides by 10 to 350 MHZ. This kit will take any 35MHZ Counter to 350 MHZ. Kit includes the following:
 1 Fairchild 95H90DC Chip
 1 2N5179 Transistor
 2 UC-88/U BNC Connectors
 1 PC Board
 And all other parts for assembly. **Now Only \$19.95**

Kit # 3
 Fairchild 11C90DC Prescaler 650MHZ.
 11C90DC Prescaler divides by 10/100 to 650 MHZ. This counter will take any 65 MHZ Counter to 650MHZ. or with a 82890 it will take a 6.5 MHZ Counter to 650MHZ. Kit includes the following:
 1 Fairchild 11C90DC Chip
 1 2N5179 Transistor
 2 UC-88/U BNC Connectors
 1 LM7805 Voltage Regulator
 1 50volt 1amp Bridge
 1 LED Indicator
 1 PC Board
 And all other parts for assembly. **Now Only \$29.95**

FAIRCHILD VHF and UHF Prescaler Chips

95H90DC	350MHZ Prescaler Divide by 10/11	\$ 8.95
95H91DC	350MHZ Prescaler Divide By 5/6	8.95
11C90DC	650MHZ Prescaler Divide By 10/11	15.95
11C91DC	650MHZ Prescaler Divide By 5/6	15.95
11C93DC	1GHz Divide by 248/256 Prescaler	29.90
11C70DC	600MHZ Flip/Flop with reset	12.30
11C58DC	ECL VCM	4.53
11C64DC	Phase Frequency Detector (MC4044F/L)	3.82
11C24DC	Dual TTL VCM (MC4024P/L)	3.82
11C06DC	UHF Prescaler 750MHZ D Type Flip/Flop	12.30
11C05DC	1GHz Counter Divide by 4	74.35
11C01FC	High Speed Dual 5-4 Input NO/NOR Gate	15.40

Crystal Filters. Tyco 001-19880 same as 2194F
 10.7MHZ Narrow Band Crystal Filter
 3 db bandwidth 15khz minimum, 20 db bandwidth 60khz minimum 40 db bandwidth 150khz minimum
 Ultimate 50 db : Insertion loss 1.0db Max. Ripple 1.0db Max. Ct. 0+ - 5pf. Rt. 3600 Ohms.
 Now Only \$ 5.95


WW - 030 FOR FURTHER DETAILS

TOTAL AMPLIFICATION FROM CRIMSON ELEKTRIK

WE NOW OFFER THE WIDEST RANGE OF SOUND PRODUCTS -

STEREO PRE-AMPLIFIERS

MC 1

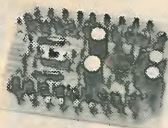

CPR 1



CPR 1 - THE ADVANCED PRE-AMPLIFIER. The best pre-amplifier in the U.K. The superiority of the CPR 1 is probably the disc stage. The overload margin is a superb 40dB, this together with the high slewing rate ensures clean top, even with high output cartridges tracking heavily modulated records. Common-mode distortion is eliminated by an unusual design. R.I.A.A. is accurate to 1dB; signal to noise ratio is 70dB relative to 3.5mV, distortion < .005% at 30dB overload 20KHz.

Following this stage is the flat gain/balance stage to bring tape, tuner, etc. up to power amp. signal levels. Signal to noise ratio 86dB; slew-rate 3V/uS; T.H.D. 20Hz-20KHz < .008% at any level.

F.E.T. muting. No controls are fitted. There is no provision for tone controls. CPR 1 size is 138x80x20mm. Supply to be ± 15 volts.


MC 1 - PRE-AMPLIFIER. Suitable for nearly all moving-coil cartridges. Sensitivity 70/170uV switchable on the p.c.b. This module brings signals from the now popular low output moving-coil cartridges up to 3.5mV (typical signal required by most pre-amp disc inputs). Can be powered from a 9V battery or from our REG 1 regulator board.

REG 1 - POWER SUPPLY. The regulator module, REG 1 provides 15.0-15v to power the CPR 1 and MC 1. It can be used with any of our power amp supplies or our small transformer TR 6. The power amp kit will accommodate it.

POWER AMPLIFIERS. It would be pointless to list in so small a space the number of recording studios, educational and government establishments, etc. who have been using CRIMSON amps satisfactorily for quite some time. We have a reputation for the highest quality at the lowest prices. The power amp is available in five types, they all have the same specification. T.H.D. typically .01% any power 1kHz 8 ohms; T.I.D. insignificant; slew rate limit 25V/uS; signal to noise ratio 110dB; frequency response 10Hz-35kHz, -3dB; stability unconditional; protection drives any load safely; sensitivity 775mV (250mV or 100mV on request), size 120x80-25mm.

POWER SUPPLIES. We produce suitable power supplied which use our superb TOROIDAL transformers only 50mm high with a 120-240 primary and single bolt fixing (includes capacitors/bridge rectifier).

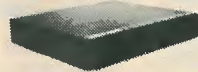POWER AMPLIFIER KIT. The kit includes all metalwork, heatsinks and hardware to house any two of our power amp modules plus a power supply. It is contemporarily styled and its quality is consistent with that of our other products. Comprehensive instructions and full back-up services enables a novice to build it with confidence in a few hours.



POWER AMPLIFIER MODULES	
CE 608 60W/8 ohms 35-0-35v	£16.30
CE 1004 100W/4 ohms 35-0-35v	£19.22
CE 1008 100W/8 ohms 45-0-45v	£23.22
CE 1704 170W/4 ohms 45-0-45v	£29.12
CE 1708 170W/8 ohms 60-0-60v	£31.90

TOROIDAL POWER SUPPLIES	
CPS 1 for 2xCE 608 or 1xCE 1004	£14.47
CPS 2 for 2xCE 1004 or 2/4xCE 608	£18.82
CPS 3 for 2xCE 1008 or 1xCE 1704	£17.66
CPS 4 for 1xCE 1008	£15.31
CPS 5 for 1xCE 1708	£22.68
CPS 6 for 2xCE 1704 or 2xCE 1708	£23.98

HEATSINKS	
Light duty, 50mm, 2 C/W	£1.30
Medium power, 100mm, 1-4 C/W	£2.20
Disco/group, 150mm, 1-1 C/W	£2.85
Fan, 80mm, state 120 or 240v	£18.50
Fan mounted on two drilled 100mm heatsinks	
2x4 C/W, 65 C max. with two 170W modules	£29.16
THERMAL CUT-OUT, 70 C	£1.90

POWER AMP KIT £32.40

PRE-AMPS:
 These are available in two versions - one uses standard components, and the other (the S) uses MO resistors where necessary and tantalum capacitors.

CPR1	£29.49
MC1	£18.50
CPRIS	£39.98
MC1S	£29.49

POWER SUPPLY: TR6 £1.75

BRIDGE DRIVER, BDI
 Obtain up to 340W using 2x170W amps and this module.
 BDI £5.40

CRIMSON ELEKTRIK

1A STAMFORD STREET, LEICESTER LE1 6NL. Tel. (0533) 537722

All prices shown are UK only and include VAT and post. COD 90p extra, £100 limit. Export is no problem, please write for specific quote. Send large SAE or 3 International Reply Coupons for detailed information. Distributor: Micnic Teleprodukt, Box 12035, S-750 12 Uppsala 12, Sweden.

WW-045 FOR FURTHER DETAILS

More second user bargains from Carston

Top Quality Test Equipment at the keenest of prices

Acoustic
BRUEL & KJAER
 2203 Precision sound level meter 400
 2204 Precision sound level meter 475
 1613 Octave filter set couples directly to 2203 & 2204 250
CEL
 112 LEQ meter-digital readout 575
Bridges
CAMBRIDGE
 43379 Decade resistance bridge 75
MUIRHEAD
 D30A Wheatstone bridge test set 175
SULLIVAN
 T1098 Decade resistance bridge 190
WAYNE KERR
 B221 Universal bridge 180
 B601Z RF bridge to 5 MHz }
 SR26B Source for B601Z } 475
Cable Test Equipment
MARCONI
 TF2091A/TF2092A White noise generator/receiver 300 channel system complete 550
SIEMENS
 3W518/3D335 Cable test oscillator and voltmeter 10 kHz-17 MHz 310
STC
 74226B Telephone cable test set 350
WANDEL AND GOLTERMAN
 TFFM43 Cable test voltmeter 10 kHz-14 MHz 90
Counter Timers
HEWLETT PACKARD
 5253B Converter plug-in to 512 MHz 380
 5263A Time interval plug-in 60
MARCONI
 TF2414A DC-40 MHz 7 digits 170
 TF2422 Frequency divider to 300 MHz 50
RACAL
 9024 10 Hz-600 MHz 7 + 1 digits 325
 9059 DC-560 MHz with battery pack 300
 9835 DC-15 MHz 6 digits 175
 9837 DC-80 MHz 6 digits 245
Function Generators
HEWLETT PACKARD
 3300A 0.01 Hz-100 kHz sine, square triangular }
 3301 Auxiliary plug-in } 150
Insulation Testers
EDGCUMBE
 Metrohm Hi resistance test set 50
Logic Analysers
HEWLETT PACKARD
 1601L Logic state analyser 12 channel display 1050
SPECTRUM DYNAMICS
 550 Universal programmer/verifier for ROMs 1550
Mains Monitors
AMPROBE
 LAV2X Mains voltage recorder 45
 LAV3X Mains voltage recorder 45
 LAV4X As LAV3X with suppressed zero 50
GEC
 FB31A Surge monitor records mains spikes + filter 85
RUSTRAK
 288 + CT Clamp-on AC recording ammeter 110
Microwave
HEWLETT PACKARD
 423A Crystal detector 65
 X382A Attenuator 'X' band 220
 788C Directional detector 145

Modulation Meters
RADIOMETERS
 AFM1 AM/FM modulation meter 205
Oscilloscopes
ADVANCE
 OS1000 DC-15 MHz dual trace 265
HEWLETT PACKARD
 184A + 1801A + 1822A DC-50 MHz system, T.B. and amplifier included, storage facility (storage de-rated please ask for details) 650
LANSCOPE
 419A Display oscilloscope 4 trace 200
PHILIPS
 PM3232 DC-10 MHz dual trace 375
TEKTRONIX
 3A74 4 channel amplifier for 560 series 285
 453A DC-60 MHz dual trace 750
 454B + CA DC-24 MHz dual trace system 350
 5103/D11 + 5A18 + 5L4 Spectrum analyser and storage system 1950
 20 Hz-100 kHz
 5103N/D13 + 5A18N + 5B12N Storage system 20 div/ms DC-2 MHz 675
 5103N/D15 + 5A18N + 5B12N Storage system 800 div/ms DC-2 MHz 595
 5A21N DC-1 MHz differential 95
 7A13 DC-100 MHz differential comparator 350
 7B70 Dual time base with 7B71 delayed sweep (for 7000 series) } 275
TELEQUIPMENT
 D54 DC-10 MHz dual trace 275
Oscilloscope Probes - Current
TEKTRONIX
 P6021 AC current probe to 20 MHz 220
 P6022 AC current probe to 150 MHz 240
Oscilloscope Probes - Voltage
HEWLETT PACKARD
 1121A 500 MHz 90
TEKTRONIX
 P6032 Sampling probe kit 15
 P6046 Differential probe DC-100 MHz 250
Oscilloscope Cameras
HEWLETT PACKARD
 195A Pack film polaroid 285
 198A Pack film polaroid 145
TEKTRONIX
 C30AR Roll film polaroid 130
 C31A Roll film polaroid 135
Power Meters
HEWLETT PACKARD
 432A/478A 10 MHz-1.2 GHz wideband with bolometer 350
Power Supplies
DANA
 Battery Pack for use with 3800 series 5
FARNELL
 TSV70 DC stab. variable 70 V/5 A 140
HEWLETT PACKARD
 6265B DC stab. variable 40 V/3 A 195
 6267B DC stab. variable 40 V/10 A 215
 6269B DC stab. variable 40 V/50 A 350
SYSTRON DONNER
 LNG 16-10 16 V/10 A variable 95
Pressure & Displacement Transducers
ELECTRO MECHANISMS
 LVDT DC linear variable ±0.50 inches 25
SCHAEVITZ
 P700 Pressure sensor 250 psi 30

Pulse Generators
E. H. RESEARCH
 G710 5 V/50 Ω 30 Hz-50 MHz RT 5 ns 100
 132AL 50 V/50 Ω 5 Hz-3 MHz RT 12 ns 175
LYONS INSTRUMENTS
 PG2E 10 V/50 Ω 1 Hz-16 MHz RT 10 ns 130
 PG23 10 V/50 Ω 1 Hz-10 MHz RT 5 ns 135
SYSTRON DONNER
 101 10 V/50 Ω 10 Hz-10 MHz RT 5 ns 95
 110B 10 V/50 Ω 5 Hz-50 MHz RT 4 ns 195
Recorders & Signal Conditioning Equipment
BRUNO WOELKE
 ME102B Wow and flutter meter 120
 ME102C Wow and flutter meter 150
BRUSH
 260 Six channel 80 Hz response, ink writing 2400
BRUEL & KJAER
 2305B Stylus Recorder includes 50 db pot 650
HEWLETT PACKARD
 7035B 8 1/2" x 11" 0.4 mV-4 V/cm 500
 17502A Plug-in for 7100 series recorder temperature module 75
METRAWATT
 RA6 6 channel UV with conditioning amplifiers 695
NAGRA
 IVD Portable tape recorder 950
SE LABS
 3006DLT 12 channels UV 6 inch chart 450
 A1000 Galvo 600 Hz 0.34 mA/cm 30
MICROMOVEMENTS
 M100 Galvo 60 Hz 2.5 μA/cm 25
 M400 Galvo 300 Hz 50 μA/cm 25
 M1000 Galvo 600 Hz 0.34 mA/cm 25
 M1600 Galvo 1000 Hz 0.4 mA/cm 25
 M8000 Galvo 5 kHz 15.5 mA/cm 25
SMITHS
 RE520.20 2 pen potentiometric roll chart 385
 RE551.20 X-Y1 Y2 plotter A3 time base fitted 575
SIEMENS
 Oscillostore 4 channel digital storage system with UV recorder 3300
 KOMP III 2 pen potentiometric roll chart 575
Signal Sources & Generators
HEWLETT PACKARD
 200CD 5 Hz-600 kHz O/P 10 V RMS 75
 608E 10 MHz-480 MHz AM 410
 0.1 μV-1 V O/P 8693/100 3.7-8.3 GHz 5 mW, sweeper plug-in 525
LEVELL
 TG150DM 1.5 Hz-150 kHz 2.5 V 45
MARCONI
 TF1370A 10 Hz-10 MHz 3 mV-3 V O/P 160
TEXSCAN
 VS40 1-300 MHz sweeper 450
 VS80A 1-1000 MHz sweeper 650

T.V. Test Equipment Prices from £
MARCONI
 TF2909 Gray scale generator 350
Temperature & Humidity
AMPROBE
 T8650 Recording thermometer 12"/hr chart speed 50
COMARK
 1604BLU Analogue thermometer 0-100 °C 55
DARTRON
 82 Thermohygrograph 45
LEE-DICKENS
 HP5 Humidity probe 130
 HUMIGUN Temp/humidity probe with meter 215
RAYTEK
 T1000 Infra-red thermoprobe 275
Voltmeters - Analogue
AVO
 9 AC/DC/Ω 50
BRADLEY
 CT471C AC/DC/Ω/current multimeter 350
HEWLETT PACKARD
 427A AC/DC/Ω multimeter 295
 3406A 10 kHz-1.2 GHz 395
KEITHLEY
 610B Electrometer recorder O/P 330
LINSTEAD
 M2B DC/AC 10 Hz-500 kHz 50
MARCONI
 TF2603 AC voltmeter to 1.5 GHz 375
NORMA
 U-Function Dual channel, peak/RMS meter 495
PHILIPS
 PM2454B AC voltmeter to 12 MHz 300
PYE
 11320 Scalamp galvo 10 mV-300 V 10
Voltmeters - Digital
ADVANCE
 DMM3 1999 FSD AC/DC/Ω/current 85
DANA
 5230 11999 FSD AC/DC 175
BOONTON
 93A 20 Hz-20 MHz true RMS 285
FLUKE
 8300A 11999 FSD DC only 150
 8300A OP1 11999 AC/DC/Ω 185
HEWLETT PACKARD
 3474/2 9999 FSD AC/DC/Ω 215
SOLARTRON
 A200 19999 FSD DC only 200
 A205 19999 FSD AC/DC/Ω 300
 A215 199999 FSD AC/DC/Ω 475
 LM1867 101999 FSD DC only 175
Wave Analysers
HEWLETT PACKARD
 302A 20 Hz-50 kHz 75 db range 550

Redundant Test Equipment
 Why not turn your under-utilized test equipment into cash? Ring us and we'll make you an offer.

JUST AVAILABLE

Acoustic
BRUEL & KJAER
 1614 Third octave, filter
 2Hz - 160 kHz
 1 ONLY **£1000**

Oscilloscopes
TELEQUIPMENT
 D83/V4/52A DC-50 MHz
 with amplifier
 and timebase
 5 ONLY **£450**



Contact David Kennedy or Kathy Goodman
01-267 4257
 Carston Electronics,
 Shirley House, 27 Camden Road,
 London NW1 9NR. Telex: 23920

sales hire repair



**You'll do better at Martin Associates
we guarantee it!**

BRIDGES	
Wayne Kerr B.521 Universal Bridge 1%	£85.00
Wayne Kerr B.601 R.F. Bridge 15KHz-5MHz Plus Adaptors	£195.00
Wayne Kerr B.221 Universal Bridge 0.1% Plus Adaptor	£225.00
COUNTERS	
Advance TC4 + TCD100 4 digit 10Hz-100MHz	£135.00
Marconi TF.2401A 8 digit DC-110MHz. 300MHz-2.5GHz	£500.00
Racal 835 6 Digit Counter/Timer DC-15MHz	£135.00
Systron Donner 6053 7 Digit 20Hz-3GHz	£550.00
Systron Donner 1037 8 Digit DC-500MHz	£300.00
DIGITAL VOLTMETERS	
H-P 3439A 4 digit AC/DC 10V-1000V 100KHz	£200.00
METERS	
Advance VM.78 Millivoltmeter 1Hz-1MHz 1mV-300V	£60.00
Avo Precision Avometer DC 0.3%: A.C. 0.75%	£160.00
H-P 430C + 477B Power Meter 0.01-10mW: 10MHz-10GHz	£115.00
Kamoden HMG-500 500V Megohm Meter. Battery operated	£60.00
Level TM6B Valve Voltmeter	£100.00
Marconi 6593 MkIII VSWR + Amplifier	£275.00
Marconi TF.2604 Electronic Voltmeter	£225.00



MARTIN ASSOCIATES
34 Crown Street
Reading
Berks. RG1 2SE
Tel. Reading (0734) 51074

North Atlantic 202BR Phase Angle Voltmeter	£120.00
Telonic 9011A Frequency Meter 1-18GHz	£400.00
OSCILLOSCOPES	
Tektronix 567 Sampling 1GHz. Digital Readout	£750.00
Tektronix 535A DC-15MHz Dual Beam Oscilloscope	£215.00
Tektronix 541A DC-30MHz Dual Beam. Main Frame Only	£130.00
Tektronix 585A + 82 P.1. DC-80MHz Dual Beam	£550.00
Tele Equipment S.43 DC-15MHz Single Beam	£95.00
Tektronix C27R Oscilloscope Camera Polaroid Roll	£350.00
Tektronix Plug Ins. B:D:K:H:L:CA:M:1A1 1A2:1A6 From Telford Type A Oscilloscope Camera. Polaroid Roll	£75.00
SIGNAL SOURCES	
General-Radio 1362 UHF Oscillator + 1267 P.S.U.	£600.00
General Radio 1209C 250MHz-960MHz Oscillator	£150.00
General Radio 1215C 50MHz-250MHz Oscillator	£150.00
General Radio 1215C 50MHz-250MHz Oscillator	£350.00
Hewlett-Packard 608D 10MHz-420MHz 0.1µV-0.5V 50 ohms	£500.00
Hewlett-Packard 608F 10MHz-455MHz Signal Generator	£200.00
Hewlett-Packard 200CD 5Hz-600KHz 10V into 600 Ohms	£400.00
Marconi TF.995A AM/FM Signal Generator 1.5-220MHz From Malden Electronics 738 1Hz-10MHz Pulse Generator	£195.00
Marconi 801D/1 10MHz-470MHz 0.1µV-1V into 50 ohms	£285.00
Marconi 2003 PhM/MA 0.4-12.5MHz Transistorised	£200.00
Marconi 1099 Sweep Generator up to 24MHz 0.3-3V NEW	£200.00

RECORDERS	
Advance HR-100 X-Y Recorder	£125.00
Bryans 1806 X-Y Recorder	£225.00
Bryans 22020 Auto Plotter X-Y	£450.00
Hewlett-Packard 7700 Recorder System 6 Pen Thermal + Amplifier & Transducers	£700.00
Oxford 3000 Potentiometric Flat Bed 2 Pen	£450.00
Bell & Howell 5-124 17 Channel U/V Recorder	£800.00
Southern Inst. M.1300 10 Channel U/V Recorder	£600.00

*Hundreds
more items
in stock!*

MISCELLANEOUS	
Linberg Diffusion Furnace Triple Zone	£3000.00
L.E.C. Climatic Oven -80°C to +110°C	£1000.00
Hearson Oven Amb -50°C	£125.00

WW-024 FOR FURTHER DETAILS

MPU XTALS

OVER SEVENTY
STANDARD FREQUENCIES

TENS OF
THOUSANDS STOCKED

DELIVERY FREE
WORLD-WIDE



INTERFACE QUARTZ DEVICES LTD
29 Market Street, Crewkerne, Somerset TA18 7JU
Crewkerne (0460) 74433 Telex 46283 inface g
WW - 057 FOR FURTHER DETAILS

1/2 watt **ATTENUATORS
TERMINATIONS
IMPEDANCE
TRANSFORMERS**
MANUFACTURED BY ELCOM SYSTEMS INC.




LOW COST FAST DELIVERIES
FROM

Aspen Electronics Limited

Communications Equipment and Components
2 KILDARE CLOSE, EASTCOTE, RUISLIP, MIDDLESEX HA4 9UR
Telephone: 01-868 1188. Telex: 8812727

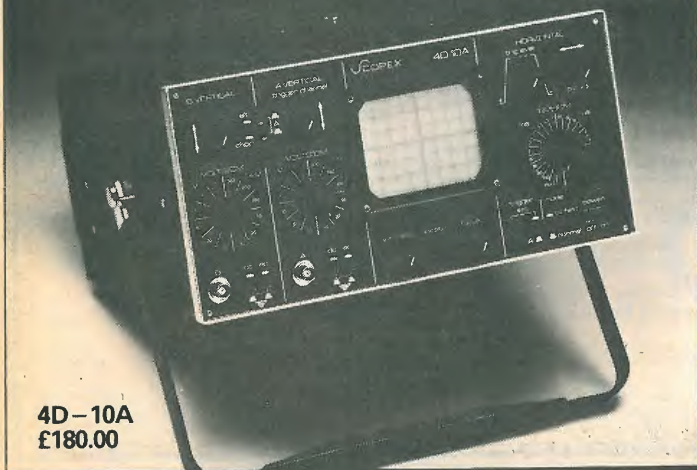
Scopex vital statistics: 2% more in accuracy, around 20% less in price.



4D-10A
£180.00



4D-25
£285.00

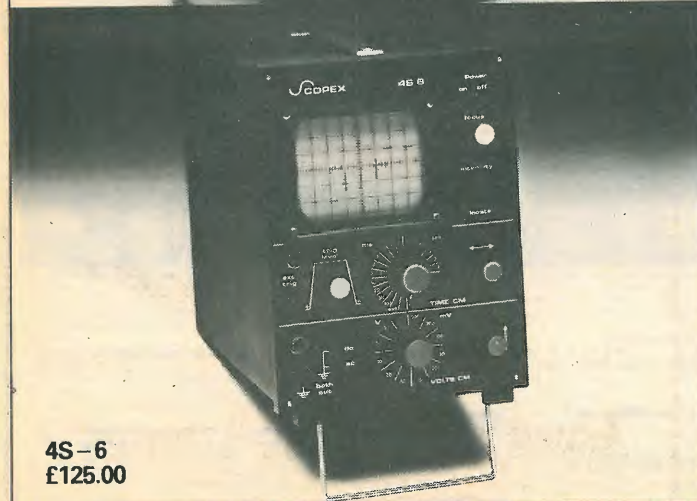

4S-6
£125.00

Greater accuracy, lower cost plus something more – a wide range covering dual trace, 10 and 25MHz, long persistence, rack mounted – single trace 6MHz, long persistence and battery portable models, plus a wide variety of accessories and probes.

The figure of 3% accuracy compares very favourably with the 5% claimed by our competitors. As does the Scopex reputation for producing reliable, easy to use oscilloscopes for just about every application.

Take the 4D – 10A dual trace model. Guaranteed 3% accuracy achieved by a stabilised power supply including the EHT. 10mV – 50V/cm sensitivity, TV field trigger and trace locate. £180.00*

Or the 4D – 25. Dual trace model with DC – 25MHz bandwidth and 10mV/cm sensitivity. Signal delay allows you to trigger from and see the leading edge of any signal. Trigger level and slope are selected on one dual function control. £285.00*

For more details of these and the full Scopex range simply return the coupon. Remember what you gain in accuracy, you lose in price.

* U.K. list price excluding VAT. (Correct at time of going to press)

SCOPEX

Scopex Sales
Pixmore Avenue, Letchworth, Herts. SG6 1JJ.
Tel: (04626) 72771

Please send me full details of the Scopex range of oscilloscopes.

Name _____

Company _____

Address _____

Tel.: _____



WW3/79

Scopex GmbH Hasselfelder Weg 36 1000 Berlin 45

WW-052 FOR FURTHER DETAILS

SYNERTEK* SYM-1 MICROCOMPUTER

Features Include:

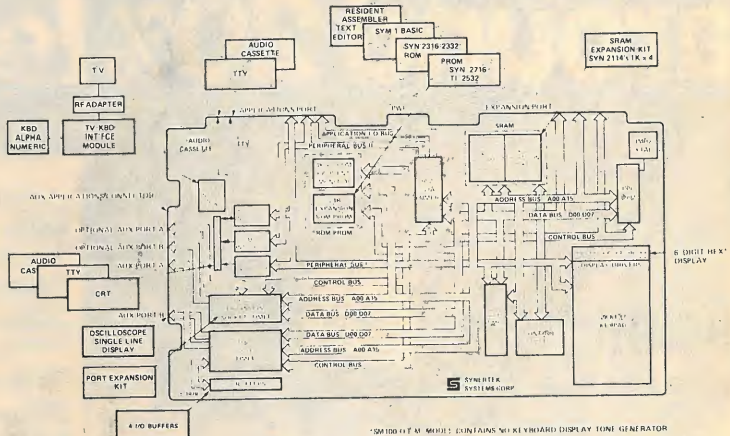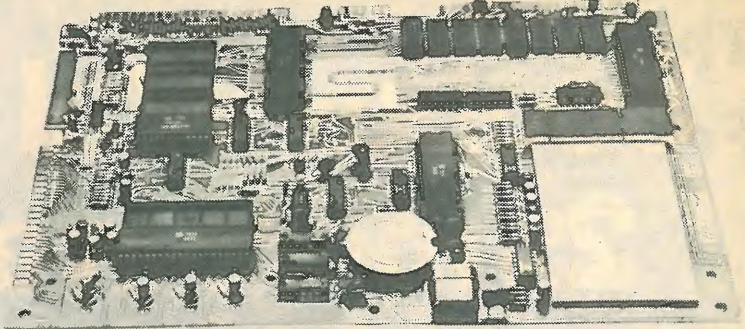

- Ready to use because it's fully assembled, tested and completely integrated as soon as you open the shipping container.
- 51 total I/O lines, expandable to 71.
- The powerful SY6502 8-bit microprocessor with advanced architectural features which make it one of the largest selling "micros" on the market today.
- Five on-board programmable interval timers available to the user for timing loops, watchdog functions, and real-time communications protocols.
- 4K-byte ROM SUPER-MON resident monitor and user expandable.
- Single 5-volt power capability is all that is required.
- 1K-bytes of static RAM on-board with sockets provided for immediate expansion to 4K bytes on-board, with total memory addressability to 65,536 bytes.
- User PROM/ROM — the system is equipped with 4 PROM/ROM expansion sockets for SY2316/SY2332 ROMs or 2716/2732 EPROMs, up to 28K bytes.
- Standard interfaces: digital audio cassette recorder interface with remote control; full duplex 20mA teletype interface; system expansion bus interface; TV/KB controller board interface; RS 232 compatible interface; four strappable relay drivers or input buffers; and a 32-character single line oscilloscope display interface.
- Application port — 15 bidirectional TTL lines for user applications with expansion capability for added lines.
- Expansion port for add-on modules (51 I/O lines in basic system).
- Separate power supply connector for easy disconnect of the DC power.
- Uses same hardware interface busses as KIM-1 (MOS Technology).

Sym-1 Microcomputer Board £192 (+8% VAT)
Sym-1 Reference Manual £7 (no VAT)

Ex-stock from:—

CITADEL PRODUCTS LTD.

50 High Street, Edgware, Middx. HA8 7EP. Tel: 01-951 1848

*Synertek Inc.
is a Honeywell Company

**QUARTZ
CRYSTALS
—FAST!**



AEL

AEL CRYSTALS LIMITED
Gatwick House, Horley, Surrey, England RH6 9SU
Telephone: Horley (02934) 5353 Telex: 87116 (Aerocon Horley)
Cables: Aerocon Telex Horley

WW — 040 FOR FURTHER DETAILS

JES AUDIO INSTRUMENTATION



Illustrated the Si452
Distortion Measuring
Unit—low cost distortion
measurement down to
.01% £56.00

Si451 £70.00 Si453 £70.00
Comprehensive Millivoltmeter Low distortion Oscillator
350µ Volts 20 ranges sine — square — RIAA

prices plus VAT

J. E. SUGDEN & CO. LTD. Tel. Cleckheaton (0274) 872501
CARR STREET, CLECKHEATON, W. YORKSHIRE B19 5LA

WW — 053 FOR FURTHER DETAILS

Design,
manufacture &
installation

Audix Limited
Station Road, Wenden
Saffron Walden
Essex CB11 4LG

Tel: Saffron Walden
(0799) 40888
Telex: 817444

audix

Sound & Communications systems


Please send me details

- Sound reinforcement/
public address equipment
- Theatre sound equipment
- Hospital distribution
and nurse call systems
- Intercom systems,
commercial & industrial
- Hotel entertainment systems
- Simultaneous interpretation
and conference systems

Name _____

Address _____

This Is The Famous

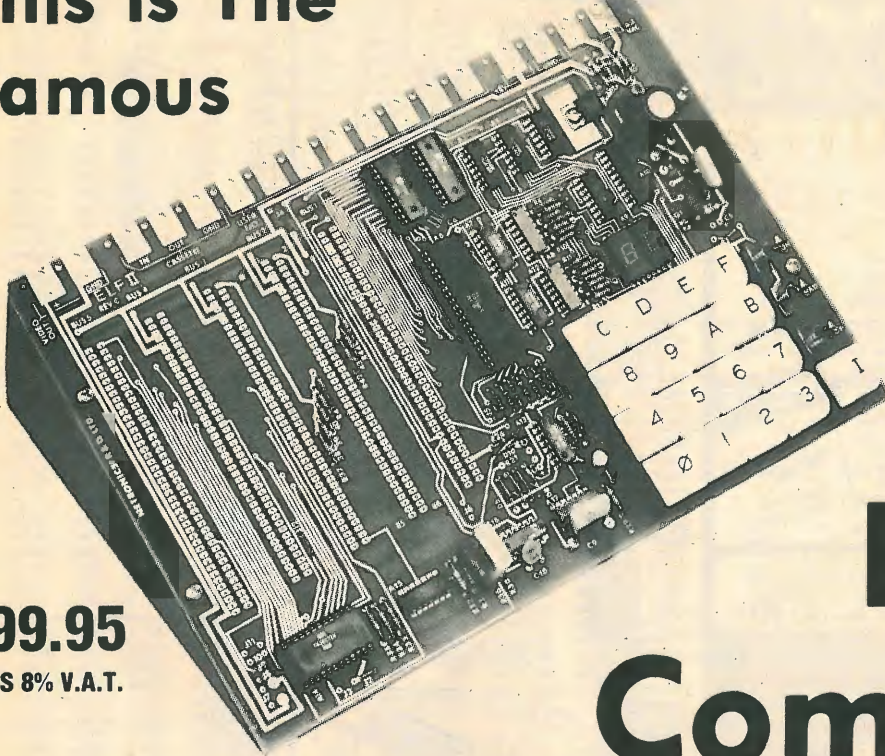

£99.95
PLUS 8% V.A.T.

ELF II Computer

SPECIFICATIONS

The £99.95 ELF II computer features an RCA COSMAC COS/MOS 1802 8-bit microprocessor addressable to 64K bytes with DMA, interrupt, 16 registers, ALU, 256 byte RAM expandable to 64K bytes, professional hex keyboard fully decoded so there's no need to waste memory with keyboard scanning circuits, built-in power regulator, 5 slot plug-in expansion bus (less connectors), stable crystal clock for timing purposes and a double-sided, plated-through pc board plus RCA 1861 video IC to display any segment of memory on a video monitor or TV screen along with all the logic and support circuitry you need to learn every one of the RCA 1802's capabilities

Stop reading about computers and get your hands on one! With ELF II and our new *Short Course* by Tom Pittman, you can master computers in no time at all! ELF II demonstrates all 91 commands an RCA 1802 can execute and the *Short Course* quickly teaches you how to use each of the 1802's capabilities.

ELF II's video output lets you display an alphanumeric readout or graphics on any TV screen or video monitor and enjoy the latest video games.

But that's not all. Once you've mastered computer fundamentals, ELF II can give you POWER with add-ons that are among the most advanced found anywhere. American IEEE chapters plus hundreds of universities and major corporations have chosen the ELF II to introduce their students and personnel to microprocessor computing!

Learn The Skill That May Soon Be Far More Important Than Your College Degree!

The ability to use the computer may soon be more important to your earning power than a college degree. Without a knowledge of computers, you are always at the mercy of others when it comes to solving highly complex business, engineering, industrial and scientific problems. People who understand computers can command MONEY and to get in on the action, you must learn computers. Otherwise you'll be left behind.

ELF II is The F-A-S-T Way to Learn Computer Fundamentals!

Regardless of how minimal your computer background is now, you can learn to programme a computer in almost no time at all. That's because Netronics has developed a special *Short Course on Microprocessor And Computer Programming* in non-technical language that leads you through every one of the RCA COSMAC 1802's capabilities so you'll understand everything ELF II can do... and how to get ELF II to do it!

All 91 commands that a 1802 can execute are explained to you step-by-step. The text, written for Netronics by Tom Pittman, is a tremendous advance over every other programming book in print.

Keyed specifically to the ELF II, it's loaded with "hands on" illustrations. When you're finished, ELF II and the 1802 will no longer hold any mystery for you.

In fact, not only will you be able to use a personal computer creatively, you'll also be able to understand computing articles in the technical press.

If you work with large computers, ELF II and our *Short Course* will help you to understand what makes them tick.

A Dynamite Package For Just £99.95 Plus 8% V.A.T.!

With ELF II, you learn to use machine language — the fundamental language of all computers. Higher level languages such as FORTRAN and BASIC must be translated into machine language before a computer can understand them. With ELF II you build a solid foundation in computers so you'll really know what you're doing, no matter how complicated things get.

Video output also makes ELF II unique among computers selling such a low price. Attached to your TV set, ELF II becomes a fabulous home entertainment centre. It's capable of providing endless hours of fun for both adults and children all ages! ELF II can create graphics, alphanumeric displays and fantastic video games.

Only a low cost RF modulator is required to connect ELF II to your TV's aerial socket! (To order see below.)

ELF II's 5-card expansion bus (connectors not included) allows you to expand ELF II as your needs for power grows. If you're an engineer, or hobbyist, you can also use ELF II as a counter, alarm, lock, thermostat, timer, or for countless other applications.

ELF II Explodes into a Giant!

Thanks to ongoing work by RCA and Netronics, ELF II add-ons are among the most advanced anywhere. Plug in the GIANT BOARD and you can record and play back programmes, edit and debug programmes, communicate with remote devices and make things happen in the outside world. Add Kluge Board to get ELF II to solve special problems such as operating a more complex alarm system or controlling a printing press. Add 4k RAM board and you can write longer programmes, store more information and solve more sophisticated problems.

Expanded, ELF II is perfect for engineering, business, industrial, scientific and personal finance and tax applications. No other small computer anywhere near ELF II's low price is backed by such an extensive research and development programme.

The ELF-BUG Monitor is an extremely recent breakthrough that lets you debug programmes with lightning speed because the key to debugging is to know what's inside the registers of the microprocessor and, instead of single stepping through your programme, the ELF-BUG Monitor, utilising break points, lets you display the entire contents of the registers on your TV screen at any point in your programme. You find out immediately what's going on and can make any necessary changes. Programming is further simplified by displaying 24 bytes of RAM with full address, blinking cursor and auto scrolling. A must for serious programmers!

Netronics will soon be introducing the ELF II Colour Graphics & Music System — more breakthroughs that ELF II owners will be the first to enjoy!

Now BASIC Makes Programming ELF II Even Easier!

Like all computers, ELF II understands only "machine language" — the language computers use to talk to each other. But, to make life easier for you, we've developed an ELF II Tiny BASIC. It talks to ELF II in machine language for you so that you can programme ELF II with simple words that can be typed out on a keyboard such as PRINT, RUN and LOAD.

"Ask Not What Your Computer Can Do... But What Can It Do For YOU!"

Don't be trapped into buying a dinosaur simply because you can afford it and it's big. ELF II is more useful and more fun than "big name" computers that cost a lot more money.

With ELF II, you learn to write and run your own programmes. You're never reduced to being a mere keypunch operator, working blindly with someone else's predeveloped software.

No matter what your speciality is, owning a computer which you really know how to use is sure to make you a leader. ELF II is the fastest way there is to get into computers. Order from the coupon below!

H. L. AUDIO, 138 KINGSLAND ROAD, LONDON E2 8BY

SEND TODAY FOR DETAILS OR ORDER

NOW AVAILABLE FOR ELF II —

- Tom Pittman's *Short Course On Microprocessor & Computer Programming* teaches you just about everything there is to know about ELF II or any RCA 1802 computer. Written in non-technical language, it's a learning breakthrough for engineers and laymen alike. **£5.00** post paid!
- Deluxe metal cabinet with plexiglas dust cover for ELF II. **£29.95** plus £1.50 p&p.
- RF Modulator for use with TV set. **£3.00** post paid.
- GIANT BOARD kit with cassette I/O, RS 232-C/TTY I/O, 8-bit P. I/O decoders for 14 separate I/O instructions and a system monitor/editor. **£39.95** plus £1.00 p&p.
- Kluge (Prototype) Board accepts up to 36 IC's. **£17.00** plus 50p. p&p.
- 4k Static RAM kit. Addressable to any 4k page to 64k. **£89.95** plus 50p. p&p.
- Gold plated 95-pin connectors (one required for each plug-in board). **£5.70** post paid.
- Professional ASCII Keyboard kit with 128 ASCII upper/lower case set, 96 printable characters, on board regulator, parity, logic selection and choice of 4 handshaking signals to mate with almost any computer **£64.95** post paid.
- Deluxe metal cabinet for ASCII Keyboard. **£19.95** plus £1.50 p&p.
- ELF II Tiny BASIC on cassette tape. Commands include SAVE, LOAD, + x, 0, 26 variables A-Z, LET IF/THEN, INPUT, PRINT, GO TO, GO SUB, RETURN, END, REM, CLEAR, LIST, RUN, PLOT, PEEK, POLE. Comes fully documented and includes alphanumeric generator required to display

alphanumeric characters directly on your TV screen without additional hardware. Also plays tick-tack-toe plus a drawing game that uses ELF II's hex keyboard as a joystick, 4k memory required. **£14.95** post paid.

Tom Pittman's *Short Course on Tiny BASIC* for ELF II. **£5.00** post paid.

Expansion Power Supply (required when adding 4k RAM). **£19.95** plus £2.00 p&p.

ELF-BUG Deluxe System Monitor on cassette tape. Allows displaying the contents of all registers on your TV at any point in your programme. Also displays 24 bytes of memory with full addresses, blinking cursor and auto scrolling. A must for the serious programmer! **£14.95** post paid.

Coming Soon: A-D D-A Converter, Light Pen, Controller Board, Colour Graphics & Music System... and more!

Call or write for wired prices!

H. L. AUDIO LTD., Dept. W.W.
138 Kingsland Road, London E2 8BY
Tel: 01-739 1582

Sole European Distributors for Netronics R & D Ltd., U.S.A.

Yes! I want to run programmes at home and have enclosed: £109.56 including postage and V.A.T. for RCA COSMAC ELF II kit, £5.94 including postage and V.A.T. for power supply (required), £5.95 for RCA 1802 User's Manual, £5.95 including postage and V.A.T. for *Short Course on Microprocessor Computer Programming*.

I want mine wired and tested with power supply. RCA 1802 User's Manual and *Short Course* included for just **£184.10** including postage and V.A.T.

I am also enclosing payment (including postage and V.A.T.) for the items checked at the left.

Total Enclosed £.....

USE YOUR ACCESS BARCLAYCARD

Account No.....

Signature..... Exp. Date.....

PHONE ORDERS ACCEPTED 01-739 1582

Print Name.....

Address.....

DEALER ENQUIRIES INVITED

WW—020 FOR FURTHER DETAILS

STEVENSON

Electronic Components

RESISTORS

Carbon film resistors. High stability. Low noise 5%.

E12 series. 4.7ohms to 10M. Any mix:
each 100+ 1000+
0.25W 1p 0.9p 0.8p
0.5W 1.5p 1.2p 1p

Special development packs consisting of 10 of each value from 4.7ohms to 1 Meg-ohm (650 res.) 0.5W £7.50. 0.25W £5.70.

METAL FILM RESISTORS

A range of high precision, very high stability, low noise resistors. Rated at 1/4W. 1% tolerance. Available from 51ohms to 330K in E24 series. Any mix:

each 100+ 1000+
1/4W 1% 4p 3.5p 3.2p

Special development pack consisting of 10 of each value from 51ohms to 330K in E24 series. Any mix: (a total of 930 resistors) £23.75

OPTO

LEDs 0.125in. 0.2in.
Red TIL209 TIL220 9p
Green TIL211 TIL221 13p
Yellow TIL213 TIL223 13p
Clips 3p 3p

DISPLAYS
DL704 0.3 in CC 130p
DL707 0.3 in CA 130p
FND500 0.5 in CC 100p



OUR NEW ILLUSTRATED 40 PAGE CATALOGUE CONTAINS A WIDE RANGE OF COMPONENTS INCLUDING:

BOOKS, HARDWARE AND AN EXTENSIVE SELECTION OF PASSIVE COMPONENTS



Send large S.A.E.

TRANSISTORS

AC127 17p
AC128 16p
AC176 18p
AD161 38p
AD162 38p
BC107 8p
BC108 8p
BC109 8p
BC147 7p
BC148 7p
BC149 8p
BC158 9p
BC177 14p
BC178 14p
BC179 14p
BC182 10p
BC182L 10p
BC184 10p
BC184L 10p
BC212 10p
BC212L 10p
BC214 10p
BC214L 10p
BC477 19p
BC478 19p
BC479 19p
BC548 10p
BCY70 14p

BCY71 14p
BCY72 14p
BD131 35p
BD132 35p
BD135 38p
BD139 35p
BD140 35p
BF244B 36p
BFY50 15p
BFY51 15p
BFY52 15p
MJ2955 98p
MPSA06 20p
MPSA56 20p
TIP29C 60p
TIP30C 70p
TIP31C 65p
TIP32C 80p
ZTX107 14p
ZTX108 14p

ZTX109 14p
ZTX300 16p
2N697 12p
3N1302 38p
2N2905 22p
2N2907 22p
2N3053 18p
2N3055 50p
2N3442 135p
2N3702 8p
2N3704 8p
2N3705 9p
2N3706 9p
2N3707 9p
2N3708 8p
2N3819 22p
2N3904 8p
2N3905 8p
2N3906 8p
2N4058 12p
2N5457 32p
2N5458 30p
2N5459 32p
2N5777 50p

DIODES

1N914 4p
1N4001 4p
1N4002 4p
1N4004 5p
1N4006 6p
1N4148 3p
1N5401 13p
1N5402 15p
1N5404 16p
1N5406 18p
BZY88series 2V7 to 33V 8p ea.

LINEAR

709 25p
741 22p
747 50p
748 30p
CA3046 55p
CA3080 70p
CA3130 90p
CA3140 70p

LM301AN 28p
LM318N 125p
LM324 50p
LM339 50p
LM380 75p
LM382 120p
LM1830 150p
LM3900 50p
LM3909 60p
MC1496 60p
MC1458 35p


NE555 25p
NE556 60p
NE565 120p
NE567 170p
SN76003 200p
SN76013 140p
SN76023 140p
SN76033 200p
TBA800 70p
TDA1022 650p
ZN414 75p

SKTS

Low profile by Texas.

8 pin 10p
14 pin 12p
16 pin 13p

24 pin 24p
28 pin 28p
40 pin 40p

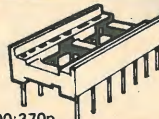

Soldercon pins: 100:50p. 1000:370p

74LS

LS00 16p
LS01 16p
LS02 16p
LS03 16p
LS04 16p
LS08 16p
LS10 16p
LS13 30p
LS14 70p
LS20 16p
LS30 16p
LS32 24p
LS37 26p
LS40 22p
LS42 53p
LS47 70p
LS48 48p
LS54 16p

LS73 29p
LS74 29p
LS75 44p
LS76 35p
LS78 35p
LS83 60p
LS85 70p
LS86 33p
LS90 45p
LS93 45p
LS95 65p
LS123 56p
LS125 40p
LS126 40p
LS132 60p
LS136 36p
LS138 54p
LS159 50p
LS151 50p
LS153 50p
LS155 80p

LS156 80p
LS157 45p
LS164 90p
LS174 60p
LS175 60p
LS190 80p
LS192 70p
LS193 70p
LS196 80p
LS251 60p
LS257 55p
LS258 55p
LS266 40p
LS283 60p
LS290 55p
LS365 45p
LS366 45p
LS367 45p
LS368 45p
LS386 35p
LS670 180p

TTL

7400 12p
7401 12p
7402 12p
7404 12p
7408 14p
7410 12p
7413 25p
7414 48p
7420 12p
7427 24p
7430 12p
7442 43p
7447 55p
7448 58p

7454 14p
7473 25p
7474 25p
7475 32p
7476 28p
7485 70p
7489 145p
7490 32p
7492 35p
7493 34p
7494 52p
7495 52p
7496 50p
74121 25p
74122 33p
74123 40p
74125 35p
74126 35p

74132 50p
74141 56p
74148 90p
74150 70p
74151 50p
74156 52p
74157 52p
74164 70p
74165 70p
74170 125p
74174 68p
74177 58p
74190 72p
74191 72p
74192 64p
74193 64p
74196 55p
74197 55p

CMOS

4001 15p
4002 15p
4007 15p
4011 15p
4013 35p
4015 60p
4016 35p
4017 55p

4018 65p
4023 15p
4024 45p
4026 95p
4027 35p
4028 52p
4029 60p
4040 68p
4042 54p
4046 100p
4049 28p

4050 28p
4066 40p
4068 20p
4069 16p
4071 16p
4075 16p
4093 48p
4510 70p
4511 70p
4518 70p
4520 65p

FULL DETAILS IN CATALOGUE!

We now have an express telephone order service. We guarantee that all orders received before 5pm. are shipped first class on that day. Contact our Sales Office now! Tel: 01-464 2951/5770.



Quantity discounts on any mix TTL, CMOS, 74LS & Linear circuits. 25+ 10%, 100+ 15%. Prices VAT inc. Please add 30p for carriage. All prices valid to 30th April. Official orders welcome.

BARCLAYCARD & ACCESS WELCOME.



Mail orders to: STEVENSON (Dept WW)

236 High St, Bromley, Kent, BR1 1PQ, England

Keep your tools handy in case...



With JENSEN

special quality industrial tool kits and cases

Send now for details of the superb Jensen range of tools, meters and accessory equipment, all in the most handy and robust cases - also available separately. Jensen products are specifically designed for industrial use, perfect for all engineers, technicians, electricians, instrument repairmen etc. Choice of more than twenty kits and cases.

Write for free Jensen catalogue to:

SPECIAL PRODUCTS DISTRIBUTORS LTD,

81 Piccadilly, London W1V 0HL. Tel: 01-629 9556. Cables: Specprod London W1.

WW-090 FOR FURTHER DETAILS

REGULATED POWER SUPPLIES

Protection:

All models internal foldback, overload, thermal and short circuit protected. Fully fused.



2-YEAR GUARANTEE

Type AD12 - AD24 (Illustrated)

TYPES AVAILABLE	AD12	AD24	AD2412	ADV030
MODEL NO.	AD12	AD24	AD2412	ADV030
OUTPUT CURRENT:	8 amp	8 amp	16 amp	5 amp
NOMINAL OUTPUT VOLTS	12	24	12	0 to 30 Fully variable and metered
INPUT VOLTS	115-230-250 50 cycles a/c	115-230-250 50 cycles a/c	24 DC	115-230-250 50 cycles a/c
TOLERATED MAINS VARIATION	15%	15%		15%

PRICES

1 off - AD 12-AD24 £62.50
1 off - AD 2412 £52.00
1 off - ADV030 £118.00
All subject to VAT @ 8%

SOUTHERN ELECTRONICS

6 WESTCLIFF ARCADE, RAMSGATE, KENT
TEL. THANET (0843) 57888

WW - 056 FOR FURTHER DETAILS

carbon film RESISTORS

ON BANDOLIERS OR PREFORMED 12.5mm
AT NO EXTRA COST



AERO SERVICES LTD.

42-44A-46 Westbourne Grove
London W2 5SF
Tel. 01-727 5641 Telex 261306

WW-066 FOR FURTHER DETAILS

RECHARGEABLE BATTERIES

TRADE ENQUIRIES WELCOME

Full range available to replace 1.5 volt dry cells and 9 volt PP type batteries, SAE for lists and prices. £1.25 for booklet. "Nickel Cadmium Power," plus catalogue.

Write or call at:

SANDWELL PLANT LTD.

2 Union Drive, Boldmere
Sutton Coldfield, West Midlands 021-354 9764

See full range at TLC, 32 Craven street, Charing Cross, London WC2.

WW-010 FOR FOR FURTHER DETAILS

VIEWDATA... TELETEXT... VIDEO RECORDERS... TV GAMES...

The new world of TV using is expanding at the speed of light. To help you get the maximum profits from it. IPC Electrical - Electronic Press has launched a brand-new quarterly: **Viewdata and TV User**.


Issue No. 1 explained in clear, non-technical terms how Viewdata works and how it differs from Teletext. It covered Prestel (the Post Office Viewdata System) in detail. It also reviewed a wide range of news and products. Subsequent issues are

If you are interested in the development of Viewdata

covering the developing story of Viewdata, Teletext, home video cassette recording, TV screen games, home computers and every other aspect of TV using, and how it can benefit you. Each issue of Viewdata and TV

User will contain the current Prestel directory, and will be available to all Prestel users free of charge. To others, the annual subscription is £2.00. Not much for a journal which could be your passport to a whole new world of interest. Post this coupon, with your cheque, today!

...you could use a new journal!

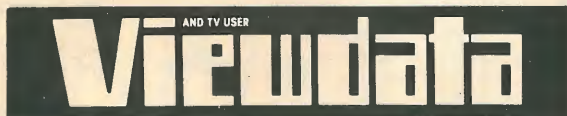

Quarterly

Editorial enquiries: Owen Ascroft (editor)

Advertisement enquiries: Stewart Goodwin

at Dorset House, Stamford Street, London SE1 9LU. Tel: 01-261 8000

TO TAKE IT REGULARLY, POST THIS COUPON NOW.

To: Subscriptions Dept.
IPC Business Press (S. & D.) Ltd.
Oakfield House, Perry Mount Rd.
Haywards Heath, Sussex

Please send me Viewdata and TV User quarterly for a year. I enclose cheque/P.O. for £2.00 (inc. post and package) made payable to IPC Business Press Limited.

Name

Address




88-108MHz in : AF out

VHF FM TUNERSET

The long experience of Larsholt Electronics is reflected in this superbly engineered VHF Band II varicap FM tuner module. (As used in the Signalmaster Mk8).

The four stage frontend employs dual gate MOSFET transistors for both RF and Mixer stages, providing the 7252 with a 1uV sensitivity for 30dB S/N (m). The IF uses a dual ceramic IF filter, and provides all usual HiFi functions, of tuning meter drives, muting, AFC and AGC. THD is only 0.1%

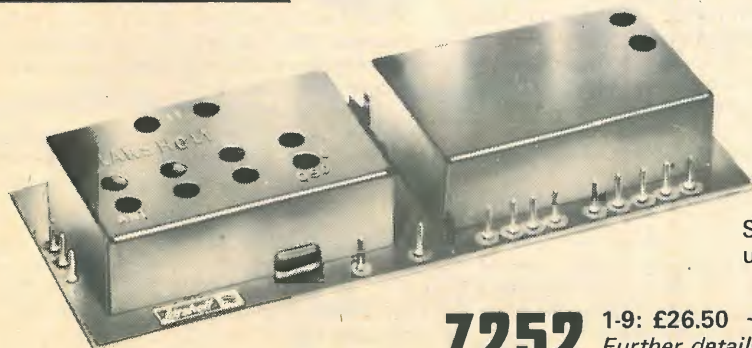Special frequency options are available for OEM use, where the high standard of Larsholt construction is frequently employed in sound distribution systems



7252 1-9: £26.50 + 12.5% VAT (£29.81) PP 25p

Further details of this and other Larsholt products in Catalogue (40p)

ex-stock, from: **Ambit international**, 2 Gresham Road, Brentwood, Essex. tel(0277) 216029

WW-022 FOR FURTHER DETAILS

MODEL 756 FULL ASCII KEYBOARD

LOW COST!
Fully Assembled



756 KEYBOARD

- * Intended for professional micro-processor applications.
- * This one Keyboard will meet most present and future requirements.
- * Full 128-character ASCII 8-bit code
- * Tri-mode MOS encoding.
- * Applications notes for auto repeat, numeric pad, serial output.
- * Upper and lower case characters generated by keyboard with latching shift-lock.
- * Selectable polarity.
- * Size 305 X 140 X 32mm (12 1/4 X 5 1/2 X 1 1/4 in)
- * MOS/DTL/TTL compatible outputs.
- * New guaranteed OEM grade components.
- * Needs +5 and -12V supply
- * Board has space for small low cost DC/DC converter so that entire unit operates off single 5V rail.

NUMERIC KEYPAD


£49.90 + VAT

Also available
 Numeric keypad — interfaces with 756 £7.50
 DC to DC converter to give -12V £5.00
 (Mounts direct on 756 P.C.)
 Plastic enclosure type 701 £10.75
 Gold plated edge connector type 756/con £1.95


Generous Quantity Discounts Available
 U.K. orders add 8% VAT on order total.
 All U.K. enquiries to
CITADEL PRODUCTS LTD.
 50 High St., Edgware, Middx. HA8 7EP
 Tel.: 01-951 1848

- * Alpha lock.
- * Extra loose keys available.
- * Supplied complete with full technical data.
- * Rugged mil. spec. G-10 PCB with plated through holes.
- * 2-key roll-over
- * DC level and pulse strobe signal for easy interface to any 8-bit input port microprocessor system, video display or terminal board. Strobe pulse width 1 ms.
- * User selection of positive or negative logic data and strobe output.

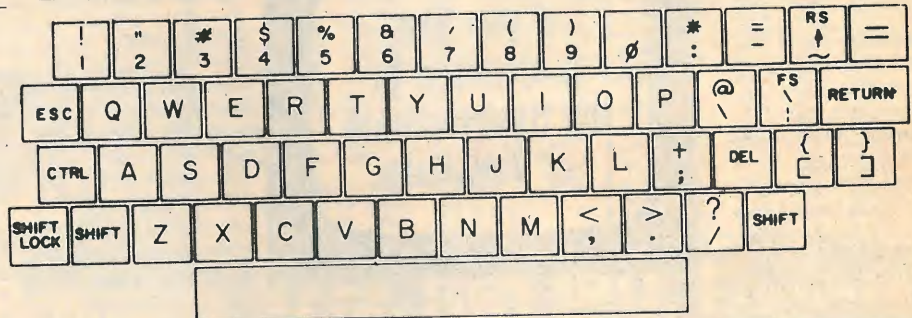Carter Associates
 P.O. Box 11262 VLAEBERG
 South Africa postal code 8018



WW-008 FOR FURTHER DETAILS

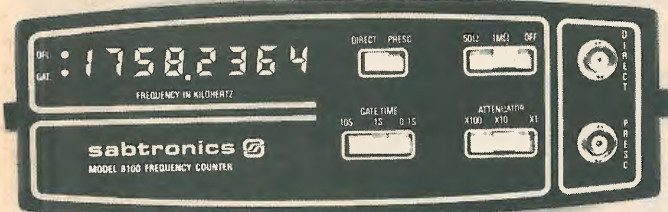

Model 8100 Frequency counter,
 Kit £ 69.95
 assembled tested: £ 84.95
 (plus p.p. £ 3.50 and VAT at 8%)



Model 2000 3 1/2 Digit DMM
 Kit £ 49.95
 assembled: £ 69.95
 (plus p.p. £ 3.00 and VAT at 8%)

The Winners

These two products are our best sellers!

The two products shown above from Sabtronics are our best selling products. Both these products compare with similar equipment selling for at least £ 150.00. Is there more to these products than value? Let's take a closer look.

The Frequency Counter Model 8100

It employs LSI Technology, has the performance and characteristics you demand, guaranteed frequency range of 20 Hz to 100 MHz; selectable hi/lo impedance; superior sensitivity; selectable resolution and selectable attenuation. Plus an accurate time base with excellent stability. An 8 digit LED Display features floating decimal point, leading zero suppression and overflow indicator.

Brief specifications:

Frequency Range: 20 Hz to 100 MHz guaranteed, (10 Hz to 130 MHz typical) — Sensitivity: 10 mV RMS,


20 Hz to 50 MHz (5 mV typical); 15 mV RMS, 50 MHz to 100 MHz (10 mV typical) — Selectable impedance: 1 MΩ/25 pF or 50Ω — Attenuation: X1, X10 or X100 — Accuracy: ± 1 Hz plus time base accuracy — Aging Rate: ± 5 ppm/yr — Temperature Stability: ± 10 ppm, 0° to 50° C — Resolution: 0.1 Hz, 1 Hz, 10 Hz selectable — Display: 8-digit LED, floating DP, overflow indicator — Overload Protection — Power Requirement: 9-15 VDC.
 Optional prescaler will be available from around March 1979.

The DMM Model 2000

The model 2000 is all solid-state, incorporating a single LSI circuit and high quality components. It has five functions and a total of 28 ranges. Input overload protection, auto polarity and auto zero are provided on all ranges and a basic DCV accuracy of 0.1% ± 1 digit.

Brief specifications:

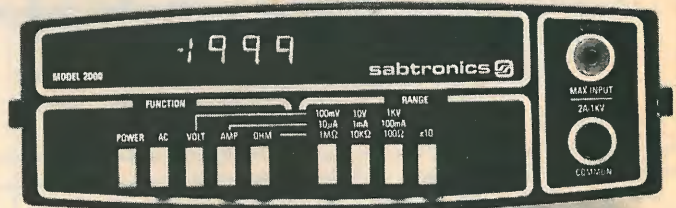DC volts in 5 ranges: 100 μV to 1 kV — AC volts in 5 ranges: 100 μV to 1 kV — DC current in 6 ranges: 100 nA to 2A — AC current in 6 ranges: 100 nA to 2A — Resistance: 0.1Ω to 20 MΩ in 6 ranges — AC frequency response: 40 Hz to 50 kHz — Display: 0.36" (9.1 mm) 7-segment LED — Input impedance: 10 MΩ — Size: 8" W x 6.5" D x 3" H (203 x 165 x 76 mm) — Power requirement: 4 "C" cells (not included).



Order yours now! Write to:

Timwood Ltd.
 Prospect Road, Cowes,
 Isle of Wight, England Telex 86892.
 Send payment with your order.

WW - 078 FOR FURTHER DETAILS

NEW PRODUCTS BULLETIN

ITA



ORBAN from USA

Dual channel multispring reverb unit. Each channel features four springs — far smoother than single spring systems. "Twang" and "boing" are virtually eliminated by incorporating a floating threshold limiter. Bass, mid-range EQ and bandwidth controls. The best compact reverb unit available.

ITAM 882

New Stereo Mixer, built to a specification not a price! Ultra low noise, -128dB. 8 inputs+8 direct outputs, 2 outputs with VU meters. 2 limiters. XLR mic inputs (balanced). 3 band EQ + mid sweep.
£395 + VAT



ITAM Graphic Equalizer

A fully professional graphic equalizer at a reasonable price. Stereo, with 10 bands per channel, 19 inch rack mounting.
£280 + VAT.


OTARI DP4050 OCF IN CASSETTE DUPLICATOR

Now with 3% + 7% master capability and Ferrite heads. Duplicates 6 cassettes each run at 8 times speed. Over 80 stereo C60 per hour. Unquestionably the finest in cassette copier available from the world's largest duplicator manufacturer.



AMPEX ATR-700

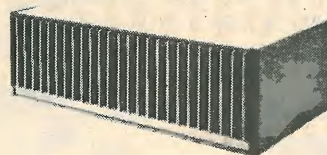Now every studio can afford legendary Ampex performance and reliability. Fully professional specification including balanced inputs/outputs, Cannon connectors, variable tape speed, sel sync. The price will fit this year's budget, not next year's! Sole distribution by ITA.



QUAD

The new 405 power amplifier is now in stock. 100 watts per channel — simply the best, for £££'s less! Immediate Delivery!



1-7 Harewood Avenue, Marylebone Road, London NW1.
Tel: 01-724 2497 Telex: 21879

FRANCE: Son Professionnel, 2 Rue des Tennerolles,
92210 Saint Cloud (Paris). Tel 602 6815.

The Teleprinter Plus... Transtel 315



The Transtel 315 word processing communications terminal includes all the best developments and refinements that have been introduced in a decade of teleprinter technology.

This high performance teleprinter has many plus features, including:—

- Microprocessor control
- High quality dot matrix printout
- KSR or ASR with up to 8k memory
- Speeds of up to 30 cps
- Telex or private wire operation
- Full word editing capability

The Transtel 315 gives you high performance at a moderate price, and with thousands of machines installed worldwide, you need not worry about reliability and after sales service.

Contact us today for further information or to arrange a convincing demonstration.

TRANSTEL®

Transtel Communications Limited
Mill Street, Slough, Berkshire SL2 5DD, England
Telephone: Slough (0753) 26955 Telex: 849384
WW — 084 FOR FURTHER DETAILS

**EXPORT
ENQUIRIES
INVITED!**

pocket-sized 500 MHz FREQUENCY COUNTER

(CM7044)

for UHF/VHF or CB
mobile radio


- * ± 2 ppm accuracy (0.0002%)
- * Overload protected
- * Built-in Ni-Cad battery pack
- * Exceptional value

Frequency Ranges
(Switched)
(a) 10MHz – 50MHz
(b) 40 MHz – 500 MHz

Sensitivity
50 MHz range, 30 mV
500 MHz range, 50 mV

Display
7 digit, 7 segment LED display

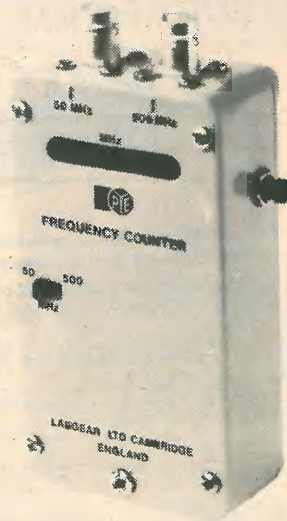Dimensions
4.75" x 2.6" x 1.25"
(121 x 67 x 32mm)



Labgear

Labgear Limited Abbey Walk
Cambridge CB1 2RQ England
Telephone: 0223 66521 (7 lines) Telex: 81105 LAB
Telegrams: Labgear, Cambridge

WW—033 FOR FURTHER DETAILS

PRODUCTION TESTING

DEVELOPMENT

SERVICING

POWER UNITS

Now available with
3 OUTPUTS



Type 250VRU/30/25

OUTPUT 1: 0-30v, 25A DC
OUTPUT 2: 0-70v, 10A AC
OUTPUT 3: 0-250v, 4A AC

ALL
Continuously
Variable

Valradio

VALRADIO LIMITED, BROWELLS LANE, FELTHAM
MIDDLESEX TW13 7EN
Telephone: 01-890 4242/4837

WW — 055 FOR FURTHER DETAILS

YOUR GUIDE TO GOOD LISTENING

HIFI YEAR BOOK 1979

Pickups/Motors/Tuners/Amplifiers/Microphones
Recorders/Speakers/Cabinets/Audio Systems

OUR NEW TRIO.



Hi-Fi Year Book is firmly established as the annual reference to just about everything the quality hi-fi market has to offer. The 1979 edition is better than ever: over 450 pages of products and photographs — separated into the major categories of equipment — giving you descriptions, prices, specifications, who makes it, where to buy it . . . everything you need to know. And this information is backed by authoritative articles on the latest hi-fi developments and their application. So if you want a reliable guide to the latest and best hi-fi products available, order your copy today because it sells out pretty quickly.

HI-FI YEAR BOOK 1979

Available direct from the publishers @ £3.50 inclusive or from leading booksellers and newsagents price £3.00.


ORDER FORM To: General Sales Manager, Room CP34, IPC Business Press Ltd., Dorset House, Stamford Street, London SE1 9LU.

Please send me _____ copy/copies of Hi-Fi Year Book 1979 @ £3.50 a copy inclusive, remittance enclosed. Cheque/p.o. should be made payable to IPC Business Press Ltd.

NAME _____
(please print)
ADDRESS _____

Registered in England No. 677128.
Registered Office: Dorset House, Stamford Street, London SE1 9LU.

NEW TESTER

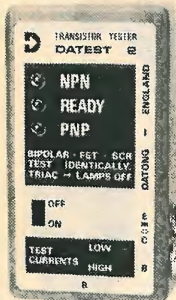

Designed for fast **in-circuit** testing, new **DATEST 2** tests transistors, FETs, SCRs and Triacs even when shunted by resistors as low as 20 ohms.

It will usually test every device in even a DC coupled AF power amp. or in a colour TV (except line o/p) **while still in circuit.**

Automatic NPN/PNP indication, foolproof three-LED display, and unique test-probes allow a very high rate of testing even by unskilled users.


Other features include long battery life, low battery warning, rugged die-cast case, reliable six-IC circuit. Best news of all DATEST 2 is affordable and available from stock.

Full data sheet free on request.

ONLY £39.50
+ VAT (8%)
WITH PROBES

DATONG ELECTRONICS LIMITED
Spence Mills, Mill Lane, Bramley, Leeds LS13 3HE
Telephone: Pudsey (0532) 552461

WW-044 FOR FURTHER DETAILS.

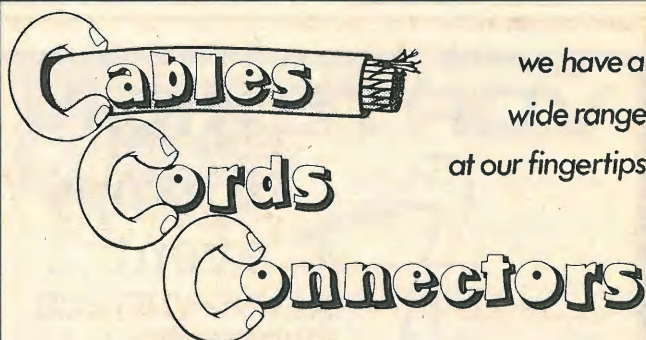

we have a wide range at our fingertips

FUTURE FILM DEVELOPMENTS
36/38 Lexington Street, London W1R 3HR
Telephone 01-437 1892/3 • Telex 21624 ALOFFD G

WW-036 FOR FURTHER DETAILS

we wondered why....

The B.B.C., British Rail, B.A.C., Decca Acoustics, Institute of Sound and Vibration Research, I.C.L., Post Office Telecommunications, Philips Research, U.K. Atomic Energy Authority, and many Universities were among our customers.

Maybe they liked the competitive prices of our modules, or the fact that all modules have a frequency response from 20Hz to 22kHz, 0.2dB, a slew rate of 8 volts per microsecond, input sensitivity of 0dB (0.775V), a damping factor greater than 400 to 1kHz and a total harmonic distortion less than 0.055% at 1kHz.

Or could it be that they want for the reliability and the comprehensive protection circuitry. Then there's the full 2 year guarantee which accompanies our range of modules.

OR PERHAPS THEY JUST LIKED THE SOUND OF US!

J.P.S. ASSOCIATES
(ASTONKILN LTD.)
BELMONT HOUSE
STEELE ROAD
PARK ROYAL
LONDON NW10 7AR
Tel: 01-961 1274/5



DENMARK

T.S. RADIO
Bakkegardsvj. 36
3300 Frederiksvaerk.
Denmark
Tel. (03) 12 07 39
Mr. Ole Juul-Moller.

BELGIUM

IATA
Studelek Elektronika
Tennestraat 260
1000 Leuven Belgium
Tel. (016) 234554
Contact Mr Leo Savannen

ENGLAND Midlands

CROXFORD CUSTOM EQUIP.
64 London Road,
Leicester
Tel. 0533 538465
Mr. Phil Croxford.

ENGLAND West

SEVERNSIDE AUDIO & LTD
29 The Promenade
Gloucester Road,
Bristol BS7 8TZ.
Tel. 0272 41666
Mr. Peter Hannay.

ENGLAND South

R.E.W. AUDIO VISUAL
126 Charing Cross Road,
London,
W.C.2
Tel. 01 836 2372
Mr. John Cowan.


SCOTLAND

ATMOSPHERE LTG. & SOUND
57 Nelson Street,
Aberdeen
Scotland
Tel. 0224 572005
Mr. Keith Main.

J.P.S. 60 : 60 Watt.
J.P.S. 100 : 100 Watt.
J.P.S. 150 : 150 Watt.



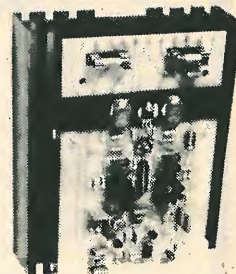Power supplies available to suit all modules. Send for further information on our range of pre-amplifier modules. JPS products are now stocked at the distributors shown below. Further information on all products available direct from JPS Associates or via reader reply service.
All modules are made in the United Kingdom.



WW-035 FOR FURTHER DETAILS

ambit international [®]

The PW Sandbanks Metal Locator: a kit based on this recently published design for this uniquely effective type of metal locator is available for only £35.00 + 8% VAT. The kit closely resembles the appearance as published, except that a close fitting injection molded housing replaces the vacuum molded electronics box - to improve the environmental suitability of the construction. Carriage for complete kits £1.

The New Catalogue - "Tecknowledgey Part 2"
Part 2 of the catalogue: by the time this advert reaches the press, part 2 should be on sale. Sorry it's late, but it contains so many new and interesting things that we felt we had to hold up production to include them. Part three by the autumn - and already there are many new items to go in! Part one 45p, part 2 50p. (inc PP etc).

Radio ICs			
TDA1062	HF/VHF tunerhead 1.95		
TDA1083	One chip AM/FM rx 1.95		
TDA1090	One chip HiFi am/fm 3.95		
TDA1220	One chip am/fm rx 1.75		
HA1197W	HiFi AM tuner IC 1.40		
CA3123E	AM tuner IC 1.40		
TBA651	AM tuner IC 1.81		
CA3089E	Famous FM IF system 1.94		
CA3189E	As 3089+ deviation mute 2.75		
HA1137W	AF preamp, adj, agc 2.20		
TBA120	Improved S/N 3089 limiting amp+detector 0.75		
TBA120S	high gain 1.00		
MC1350P	agc'd IF preamp 1.20		
MC1330P	synch AM/video detector 1.35		
KB4406	Cascade IF preamp 0.65		
uA753	limiting FM preamp 1.95		
Communications circuits			
SD6000	DMOS RF/Mixer pair 3.75		
KB4412	Bal mixers, 1F+agc 2.55		
KB4413	AM/SSB det. squelch, agc 2.75		
KB4417	mic processor 2.55		
MC3357	best thing in NBFM yet 3.12		
MC1496P	popular double bal mixer 1.25		
Multiplex decoders + noise blanker			
MC1310P	popular PLL decoder 2.20		
uA758	buffered 1310 2.20		
CA3090AQ	RCA PLL decoder 3.25		
HA1196	improved PLL decoder with stereo preamps 3.95		
HA11223	19kHz pilot cancel, low distortion, high S/N with stereo preamps 4.35		
KB4437	as HA11223 with remote VCO kill facility 4.55		
KB4438	stereo MUTEING preamp for post decoder mute 2.22		
KB4423	impulse noise blanker 2.53		
Discrete devices: more than ever:			
BF960	800MHz/2.8dB nf mosfet 1.60*		
BF961	200MHz/2.0dB nf ... 0.80*		
40822	FM RF amp ... 0.43*		
40823	FM mixer 0.51*		
40673	Famous MOSFET 0.55*		
2S149/2sK133	120V/100W MOSPOWER output devices 10.50*		
LEDs: the best value today			
3mm	5mm	2.5x5mm	
Red	0.14	0.14	0.17
Green	0.18	0.16	0.20
Yellow	0.18	0.15	0.20
Orange	0.22	0.29	0.24
100 off mix, 25% discount. All are AEG first grade types - absolutely no junk. 5mm clips for panel mounting 0.03 each			
Misc. ICs for radio/audio applications			
U237B	5 LED bargraph driver 0.80*		
SAS6610	4 station touch tune IC 1.48*		
SAS6710	adds 4 stations to 6610 1.48		
MSM5523/4	LW, MW, SW and FM digital frequency readout plus clock, timers, stopwatch £14*		
MSM5526	LW/MW/FM DFM with direct drive for LCD £11*		
TCA730	DC volume control 3.50		
TCA740	DC tone control 3.50		
TDA1028	DC input switch 3.50		
TDA1029	DC mode switch 3.50		
Radio and Tuner modules			
We cannot really list all the details we would like to here - but with advent of the new mark 3 tuner system, the Dorchester and matching AF units, Ambit offers you the widest choice ever, plus hardware and styling that matches the very high standards we have set in this new range.			

TERMS etc: CWO please. VAT on Ambit items is generally 12½%, except where marked (*). Catalogue part 1:45p, part 2 50p all inclusive. Postage 25p per order, carriage on tuner kits £3. Phone Brentwood (0277) 216029/227050 9am-7pm. Callers welcome inc. Saturdays.

At last, DIY Hi Fi which looks as if it isn't.

That's not to say it doesn't look like HiFi - just that it doesn't look like the usual sort of thing you have come to associate with DIY HiFi. The Mk3 outstrips and outperforms all British made HiFi tuners, and most imported ones too. Certainly at the price, there isn't one near it. But more than that, it looks superb. A small pic here would be an insult, so send an SAE for details on the kit that looks as if it isn't. It's something else.....


- ★ Exceptionally high performance - exceptionally straightforward assembly
- ★ Baseboard and plug-in construction. Future circuit developments will readily plug in, to keep the MkIII at the forefront of technical achievement
- ★ Various options and module line-ups possible to enable an installment approach to the system

and now previewing the matching 60W/channel VMOS amplifier:

- ★ Matching both the style and design concepts of the MkIII HiFi FM tuner
- ★ Hitachi VMOS power fets - characterized especially for HiFi applications
- ★ Power output readily multiplied by the addition of further MOSFETs
- ★ VU meters on the preamp - not simply dancing according to vol level
- ★ Backed with the usual Ambit expertise and technical capacity in audio

The PW Dorchester-LW, MW, SW, & FM stereo tuner

THE DIGITAL DORCHESTER ALL BAND TUNER

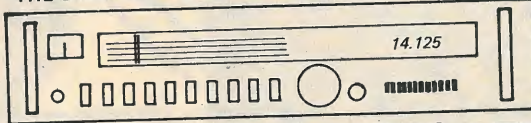

With styling and dimensions to fit in with the rest of AMBIT's new range of tuner & audio equipment.

When the new range of OKI digital frequency display ICs was announced, the original prototype of the Dorchester had been made - but since so many of you wanted to use the OKI frequency counterdisplay system with the Dorchester, we quickly designed a unit to incorporate the necessary facilities. The Digital Dorchester is designed in 19 inch form, and forms a perfect match for the other units in the range. If you don't want to go to the expense of the full Ambit DFM1 module, with AM/FM/Time/Timers, then the MA1023 clock module can be used instead.

The Dorchester has been described in PW Dec., Jan. and Feb. issues - but for those of you who may have missed it - it is an All Band broadcast tuner, covering LW/MW/SW and FM stereo in 6 switched ranges. Construction is very straightforward, with all the switching being PCB mounted - and the revolutionary TDA1090 IC used for AM/FM.

The electronics for the radio section of the Dorchester remain unchanged at £33.00, with 12.5% VAT. The hardware package, of case, meter, PSU now costs £33.00 + 8% with the MA1023 available for an extra £5 only. For the fully digital version, with Ambit DFM1, the price is £56.50 + 8% VAT.

2 Gresham Road, Brentwood, Essex.

WW-050 FOR FURTHER DETAILS

VORTEXION



a happy event...

... a new addition to our family of amplifiers. The VTN 30. The new baby weighs in at 30 watts, and has a maximum of 3 inputs.

The other members of the Vortexion family are the system 2000, 50/70 watt and CP50 mains/battery amplifiers. Contact Jennifer Hall - VORTEXION DIVISION.

Clarke & Smith Manufacturing Co. Ltd., Melbourne Works, Melbourne Road, Wallington, Surrey. Tel. 01-669 4411 Ext. 38.

Telex Casint G 22574; Telegrams: Electronic Wallington.

WW - 054 FOR FURTHER DETAILS

Audio Modules

Build your system or make add-ons with SESCOM audio modules.



MIC-4
Low Impedance
Microphone Pre-amp



LA-3
Line Amplifier Transformer
Balanced 600 ohm output



PS-1
Power Supply
24 volts DC
regulated 120/240
VAC input

Pre-amps
Balanced low impedance for microphone, high impedance general purpose, RIAA Phono, NAB tape (1%, 3%, 7%, 15 ips).

Equalizers
Active (bass, mid-range, treble) high pass filter, low pass filter.

Other Modules
Line amp, power amp, compressor, sine wave oscillator, plug-in power supply.

Accessories
Sheet metal, sockets, slide pots.
Low distortion < 1%, low noise, bi-fet op-amps, high slew rate, single supply (9-36 volts DC), plug-in.



"Quality
Engineered
Sound
Products"

SESCOM, INC.
P.O. Box 590,
12931 Budlong Ave.,
Gardena, CA 90247 U.S.A.
(213) 770-3510, (800) 421-1828,
TWX (910) 346-7023

SEND FOR YOUR FREE COPY
OF OUR NEW CATALOG

We also manufacture
audio transformers,
snakes, direct boxes
and mic-splitters

WW-011 FOR FURTHER DETAILS

OSTS

CD4000 CMOS

Since AMBIT introduced the "One Stop Technology Shop" to our service, we have been pleased to see just how many users of electronic components appreciate our guarantee to supply goods only from BS9000 approved sources. More than ever, professional and amateur electronics engineers cannot afford to waste time on anything less than perfect pedigree products.

SEE THE AMBIT AD TOO!

4000	17p	4059	563p	4522	149p
4001	17p	4060	115p	4527	157p
4002	17p	4063	109p	4528	102p
4006	109p	4066	53p	4529	141p
4007	15p	4067	400p	4530	90p
4008	80p	4068	25p	4531	141p
4009	58p	4069	20p	4532	125p
4010	58p	4070	20p	4534	614p
4011	17p	4071	20p	4536	380p
4012	17p	4072	20p	4538	150p
4013	55p	4073	20p	4539	110p
4016	52p	4075	20p	4541	141p
4017	80p	4076	90p	4543	174p
4018	80p	4077	20p	4549	399p
4019	60p	4078	20p	4553	440p
4020	93p	4081	20p	4554	153p
4021	82p	4082	20p	4556	77p
4022	90p	4085	82p	4557	386p
4023	17p	4086	82p	4558	117p
4024	76p	4089	150p	4559	389p
4025	17p	4093	50p	4560	218p
4026	180p	4094	190p	4561	65p
4027	55p	4096	105p	4562	530p
4028	72p	4097	372p	4566	159p
4029	100p	4098	110p	4568	281p
4030	58p	4099	122p	4569	303p
4031	250p	4160	90p	4572	25p
4032	100p	4161	90p	4580	600p
4033	145p	4162	90p	4581	319p
4034	200p	4163	90p	4582	164p
4035	120p	4174	104p	4583	84p
4036	250p	4175	95p	4584	63p
4037	100p	4194	95p	4585	100p
4038	105p	4501	23p		
4039	250p	4502	91p		
4040	83p	4503	69p		
4041	90p	4506	51p		
4042	85p	4507	59p		
4043	85p	4508	248p		
4044	89p	4510	99p		
4045	150p	4511	149p		
4046	130p	4512	98p		
4047	99p	4513	206p		
4048	60p	4514	260p		
4049	55p	4515	300p		
4050	55p	4516	125p		
4051	65p	4517	382p		
4052	65p	4518	103p		
4053	65p	4519	57p		
4054	120p	4520	109p		
4055	135p	4521	236p		

Micromarket

PRICES SLASHED

8216	1.95	2114	£10
8224	3.50	2708	£10.55
8228	4.78		
8220P	£6		
8250P	2.75		
8255	5.40		
8212	2.30		

Development
MEK6800 £220
TK80 £306

MEMORIES
AMI, Signetics,
TI, Intersil,
Harris etc. OA

TTL: Standard AND LP Schottky

N'	LSN'	N'	LSN'	N'	LSN'	N'	LSN'	N'	LSN'	
7400	13	20	7455	35	24	74126	57	44	74185	134
7401	13	20	7460	17		74128	74		74188	275
7402	14	20	7463			74132	73		74190	115
7403	14	20	7470	28		74133		28	74191	
7404	14	24	7472	28		74136		40	74192	105
7405	18	26	7473	32		74138		60	74193	105
7406	38		7474	27	38	74139		60	74194	105
7407	38		7475	38	40	74141		56	74195	95
7408	17	24	7476	37		74142	265		74196	99
7409	17	24	7478			74143	312		74197	85
7410	15	24	7480	48		74144	312		74198	150
7411	20	24	7481	86		74145	65		74199	160
7412	17	24	7482	69		74147	175		74248	
7413	30	52	7483A			74148	109		74249	
7414	51	130	7484	97		74150	99		74251	
7415	24	7485	104			74151	64	84	74253	105
7416	30	7486				74153	64	54	74257	108
7417	30	7489	205			74154	96		74258	153
7420	16	24	7490	33	90	74155	54	110	74259	420
7421	29	24	7491	76	110	74156	80	110	74260	153
7422	24	24	7492	38	78	74157	67	55	74261	353
7423	27	7493	32	99	74158			60	74266	40
7426	36	27	7494	78		74159	210		74273	124
7427	27	27	7495A	65	99	74160	82	130	74275	312
7428	35	27	7496	58	120	74161	92	78	74279	52
7429	35	32	7497	185		74162	92	130	74283	120
7430	17	24	74100	119		74163	92	78	74290	90
7432	25	24	74104	63		74164	104		74293	95
7433	40	32	74105	62		74165	105		74295	120
7437	40	24	74107	32	38	74166			74298	107
7438	33	24	74109	63	38	74167	20		74324	150
7440	17	24	74110	54		74168			74325	242
7441	74		74111	68		74169		200	74326	247
7442	70	99	74112	88		74170	230	200	74327	237
7443	115		74113		38	74172	625		74352	100
7444	112		74114		38	74173	170	120	74353	100
7445	94		74116	198		74174	87	120	74362	715
7446	94		74118	83		74175	87	110	74365	49
7447	82		74119	119		74176	75		74366	49
7448	56	99	74120	115		74177	75		74367	43
7449		99	74121	25		74178			74368	49
7450	17	24	74122	46		74180	85		74373	77
7451	17	24	74123	48		74181	165	350	74374	77
7453	17	24	74124			74182	160		74375	60
7454	17	24	74125	38	44	74184	135			450p

Voltage Regs

NEW LOW PRICES

7800 series UC TO220 package 1A	all 95p
7900 series UC TO220 package 1A	all £1
78MUC series TO220 package 1/2A	all 90p
78LCP series TO92 100mA	all 35p

L200 up to 3A/adjustable V&A 195p

78MGT2C 1/2amp adjustable volts 175p

79MGT2C 1/2amp adjustable volts 175p

723C precision controller 65p

MAINS FILTERS FOR NOISE/RFI etc

1 amp in IEC connector £4.83

5 amp in 'wire in' case £3.87

NE550A 73p

LINEARS non-consumer

LM339N	66p
LM348N	186p
LM3900N	60p
709HC to5	64p
709PC dil	36p
710HC to5	65p
710PC dil	59p
723CN	65p
741CH to5	66p
741CN 8dil	27p
747CN	70p
748CN	36p
NE531T	120p
NE531N	105p

OPTO 7 seg displays

0.43" High Efficiency HP:

5082 7650 red CA] 233p
5082 7653 red CC	
5082 7660 yellow CA	
5082 7663 yellow CC	
5082 7670 green CA	
5082 7673 green CC	

0.3" Standard HP

5082 7730 red CA] 147p
5082 7740 red CC	

0.5" Fairchild

FND500 red CC	150p
FND507 red CA	150p

The ICL7216BPI is still the cheapest way to make a full 8 digit/ 10MHz frequency counter/timer, and with 10 external components + display - it is also one of the simplest. For £19.82, it takes a lot of beating. The mains filters have been extended now to include a 6amp IEC version at £5.10, and with the amount of electronic noise on the average supply (next door's fridge, for instance) it is a really worthwhile addition to any sensitive equipment. LPSN TTL now includes many more of latest types, all - of course - are absolutely prime first quality types. And don't forget our range of OPTO displays includes Hewlett Package high efficiency 0.43" types in all colours - renowned as the finest quality in the market. For other types of component - discrete LEDs, radio and audio devices, tuner modules, kits etc., see our other advertisement for more details - or send for the AMBIT catalogue system. Part one (45p) includes details of our background 'standard' items, and the new part two includes all the latest introductions and developments, plus a rundown on OSTs.

TERMS: CWO pse., VAT to be added at 8% (inland), pp 25p per order. When ordering from the OSTs and Ambit - a single combined remittance and pp charge is sufficient. Account details OA.

2 Gresham Road, Brentwood, Essex.

WW-049 FOR FURTHER DETAILS

PRECISION POLYCARBONATE CAPACITORS

All high stability-extremely low leakage

440V ac range (+-10%)	63V DC RANGE (€)						
µF	L (mm)	D	£/each	µF	(Tol. +-1%)	+2%	+5%
0.1	27	12.7	1.34	0.01-0.2	1.80	1.22	0.88
0.22	33	16	1.66	0.22-0.47	1.82	1.24	0.90
0.25	33	16	1.78	1.0	2.26	1.52	1.08
0.47	33	19	2.08	2.2	2.80	1.94	1.42
0.5	33	19	2.24	4.7	4.00	2.72	2.24
0.68	50.8	19	2.48	6.8	4.88	3.36	2.66
1.0	50.8	19	2.64	10.0	6.94	4.68	3.56
2.0	50.8	25.4	3.74	22.0	13.32	9.98	6.80

TRANSISTORS, DIODES, I.C.s, Bridge, Rectifiers, Capacitors, Plugs & Sockets, Vero, etc.

RESISTORS: High stability, low noise, carbon film +-5% tol. 1/2W @40 C. 1/2W @70 C. E12 series only - from 2.2 ohm to 4.7M. All 2p each 15p/10 of any one value 95p/100 of any one value. £4.35/500 (may be mixed in 100's) £8/1000 (may be mixed in 100's).

SPECIAL DEVELOPMENT PACK: 10 off each value 2.2 ohm to 2.2M (730 resistors) - £6.50 each. (1W c/f 5%-5p ea; 2w c/f 5%-8p ea.)

PRESETS: 0.1W submin. skeleton presets - vertical or horizontal. 100 ohm to 1M 7p each. £3/50 £5/100 £22/500 £40/1000. Values may be mixed.

ZENER DIODES: 400mW ± 5% 3V-33V - 10p; 1W 3V3-200V - 18p.

TANT. BEAD CAPS: µF/0.1, 0.2, 0.22, 0.33, 0.47, 1/35 - 10p; 2/25 - 11p; 2.2/35 - 12p; 4.7/35 - 15p; 6.8/35, 10/25 - 17p; 10/35, 15/20, 22/15, 33/10, 47/6.3 - 21p; 68/3 - 17p; 100/3 - 21p.

Please add 25p P&P and 8% VAT to all items except those marked * which are 12 1/2%.

MARCO TRADING (Dept. W12) The Old School, Edstaston, WEM, Shropshire

Tel: WHIXALL 464 (STD 094872) (Props Mincast Trading Ltd.)

WW - 029 FOR FURTHER DETAILS



Model 146
VERY LOW DISTORTION (.0015%)
AUDIO SIG. GENERATOR

Based on
J. Linsley Hood Design (W.W.)
£36
(Kit. £31) + tax 8%

Low cost version, A0113 (02p dist), **£27.50 (Kit £23)**. Other instruments include: Millivoltmeter, Tachometer, Noise level meter, Distortion Analyser, F.M. Sig. Gen. Crystal Frequency Standard, KEF Speaker Units. Send S.A.E. for lists. VAT extra 8%. Post/Pkg. £1.50.

TELERRADIO ELECTRONICS
325 Fore Street, Edmonton, N.9. 01-807 3719
Closed all day Thursday

WW - 069 FOR FURTHER DETAILS

Ferranti Semiconductor Distributors Nationwide.



Semicomps Northern Ltd.,
Keighley
Tel: 0535 65191



Woolley Components Ltd.,
Altrincham
Tel: 061-941 1911



Intel Electronics Ltd.,
Henlow
Tel: 0462 812505



Comway Electronics,
Bracknell
Tel: 0344 24765





Semicomps Ltd.,
St. Albans
Tel: 0727 24522



Semicomps Ltd.,
Kenilworth
Tel: 0926 59411



S.D.S. Components Ltd.,
Portsmouth
Tel: 0705 65311



ITT Electronic Services,
Harlow
Tel: 0279 26777



Swift Hardman,
Rochdale
Tel: 0706 47411



FERRANTI Semiconductors

WW-038 FOR FURTHER DETAILS

At the end of the test session the communications engineer sang the praises of our filters.

"What performance" he said, referring to the capability of the Barr & Stroud EF3 Filter System in satisfying his signal conditioning needs. He and other engineers in many fields are equally complimentary about our supporting range of Active Filter Modules and our Custom-Built Filter Service.

We have fully descriptive literature which will generate similar enthusiasm in yourself. Use the journal reply system or call us, Barr & Stroud Limited, (Detp. WW6), Melrose House, 4-6 Savile Row, London W1X 1AF. Telephone: 01-437 9652. Telex: 261877.

EF3 Variable Filter System

Designed on a modular basis to give flexibility in use and to match your budget. A plug-in system developed for use in labs., test departments, anywhere where signal conditioning is required.

Filter units can be used separately or combined to give a wide variety of functions from low-pass to band-separate.

The current pass-band capacity is from d.c. to 10 MHz.

Active Filter Modules

The ready-to-use convenience of small, encapsulated filter units, each with a basic function. No filter knowledge required to set up for specific characteristic or cut-off frequency. These filters are equally suited to the one-off lab. application and the large quantity production requirement.

Available in low-pass, high-pass, universal and notch designs with a range of cut-off frequencies and attenuation rates.

Custom-Built Filters

The basis of our filter activity, this service has for 20 years provided solutions to customers specific requirements. Based on in-house computer facilities and an extensive programme library we can design and manufacture the filters not provided in our standard range.

Designs can be passive or active with cut-off rates up to several hundred dB per octave in a frequency range up to around 70 MHz.



Barr & Stroud

adds to your resources

ELECTRONIC FILTERS. OPTICAL FILTERS. FIBRE OPTICS.
LASERS. SCIENTIFIC AND MEDICAL INSTRUMENTATION.

wireless world

Performing blights

Editor:

TOM IVALL, M.I.E.R.E.

Deputy Editor:

 PHILIP DARRINGTON
 Phone 01-261 8435

Technical Editor:

 GEOFFREY SHORTER, B.Sc.
 Phone 01-261 8443

Projects Editor:

 MIKE SAGIN
 Phone: 01-261 8429

Communications Editor:

 RAY ASHMORE, B.Sc., G8KYY
 Phone 01-261 8043

Drawing Office Manager:

ROGER GOODMAN

Production:

ALAN KERR

Advertisement Controller:

G. BENTON ROWELL

Advertisement Manager:

 BOB NIBBS
 Phone 01-261 8622

DAVID DISLEY

Phone 01-261 8037

Classified Manager:

 BRIAN DURRANT
 Phone 01-261 8508 or 01-261 8423

 BARRY LEARY (*Classified Advertisements*)

Phone 01-261 8508

 JOHN GIBBON (*Make-up and copy*)

Phone 01-261 8353

Publishing Director:

GORDON HENDERSON

It is not open to question that goods sold by retailers should be capable of fulfilling the purpose for which they are meant — they should be of “merchantable quality”. Most people need no urging to insist that this law should be observed; a faulty pair of shoes or a watch that gains or a tape recorder that doesn’t are quickly returned whence they came and instant action demanded.

Usually, the fault is obvious: if a pair of shoes lets the water in, one can be reasonably sure there is a hole in them; a book with pages missing is an affront to the eye and a bag of crisps containing nothing but little blue packets brooks no argument.

Times are changing rapidly, more so than ever before, and the words “high technology” are bandied about and taken to mean, in our own industry, “clever electronics”. Domestic tape recorders, amplifiers and tuners are not in the same class as industrial equipment, computers and the like when judged by the height of their technology, but on the domestic scene they are clever enough to be the least-understood kind of hardware ever found in the average person’s home.

Of course, radios and record players have been around for many years, but all they have been expected to do (by this mythical “average person”) is to produce a large enough amount of “mellow” music. Now, the possession of an array of satin chrome and teak, high-quality equipment comes a good second to the bed and dining table when setting up house.

The choice of the equipment, when not made on appearance alone, is often prompted by the scanning of reviews in the magazines devoted to high-fidelity sound — and very thorough some of them are. But an ominous note is sounded in many reviews seen in these magazines to the effect that

adjustments have not been properly carried out by the makers, drastically reducing the quality of reproduction — and this is on equipment lent by makers, not bought in shops. On tape recorders, for example, head alignment is frequently a cause for complaint, as are the amount of bias current and Dolby level adjustment.

It does not seem possible for most users to investigate the finer points of performance themselves, which means they are totally in the hands of the maker/retailer organization. Since it would be unrealistic to suppose that, when sold, every single piece of equipment is at the peak of its potential, it must be assumed that there are instruments in service which are not performing as well as they might, the reasons for which the user is at a loss to explain, even supposing he can detect the shortcomings.

It would probably increase the price of equipment to an unacceptable level to expect that each instrument be subjected to a stringent examination of every facet of its specification, and since it seems probable that many purchasers would not be greatly upset by a signal-to-noise ratio of 57dB instead of 58dB, it would be unwarranted. But is there, perhaps, scope for specialist organizations to “breathe on” equipment, at a price, to make sure it is performing up to its capabilities? In an ideal world, this sort of thing would not be needed, but it seems to be an increasingly rare experience to buy a complicated object — a car, music-centre, house — and be completely happy with its performance. Exhortations from public to manufacturers appear to have negligible effect. It might be better and cheaper, of course, for the maker to do no testing at all, the specialist taking over completely: the maker couldn’t then charge for work which hasn’t been done.

Low-cost logic analyser

Simple, yet flexible design with discrete I.e.d. display

by B. C. Adams

As digital i.c.s and systems get larger and more complex, so the problems of testing and de-bugging also become more difficult. To keep pace with these problems, costly commercial analysers have been designed to maintain the systems. This design offers several useful features and enables the constructor to build a versatile, yet economical logic analyser.

THE PROBLEMS INVOLVED in testing and function checking digital equipment are exactly the same for the amateur constructor as they are for industry except that the cost of a commercial logic analyser is prohibitive to the constructor. Faced with this

problem, I designed a reasonably simple analyser which can provide almost any information that may be required from a logic system. With a little experience and ingenuity the user can overcome most diagnostic problems.


Introduction

A block diagram of the analyser is shown in Fig. 1. The instrument is a self-contained unit which comprises four main sections, a 16-bit parallel data input latch, a sample channel and display matrix, a hexadecimal comparator, and a trigger input with control logic.

In operation, the analyser monitors a number of different signal points and displays their state. If a particular section is triggered, the data is stored. All

inputs are interfaced to the internal logic via comparators which provide a high input impedance, compatibility with high level or t.t.l. logic, and permit the threshold transition level to be controlled. The 16-bit parallel latch outputs are taken to a row of I.e.d.s which indicate the 0 to 1 state of each input. The latch can be used, for example, to sample a data bus at a predetermined time or in the event of a fault, which can be especially useful when debugging

Fig. 1. Block diagram of the analyser which comprises four basic sections. All external inputs are interfaced to the logic by comparators.

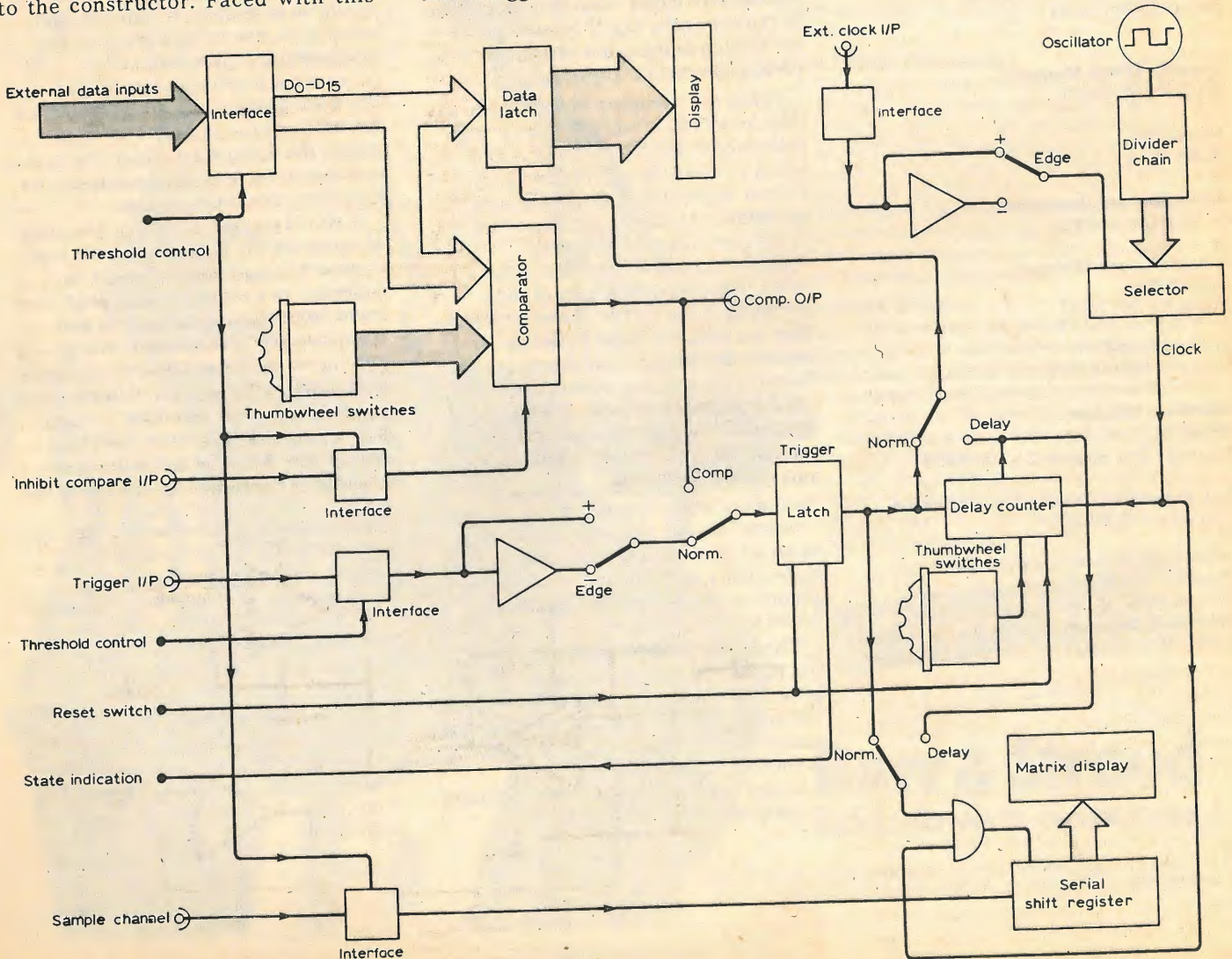

microprocessor machine-code programs.

The sample channel can be used to store and display any sequential input signal by loading it into a 32-bit serial shift register at a preselected clock rate. The contents of the register can then be continuously displayed on an l.e.d. matrix. When a trigger signal occurs, the sample clock is inhibited and the display matrix indicates the states of the 32 previous input pulses. By using the external sample clock input, a data-domain rather than time-domain display can be generated which is necessary when monitoring synchronous logic.

A 16-bit hexadecimal comparator continuously compares the data-latch inputs with a hexadecimal code set on thumbwheel switches. A true output is generated when the latch input code equals the hexadecimal code, and this can be used either as an external control signal, or switched internally to the trigger input. Many microprocessors use hexadecimal coding for their machine code instructions, so the analyser can be triggered by a particular machine instruction and store data from, for example, a peripheral at a time related to that instruction. An input is provided which can inhibit the compare output, during a change in state of the parallel data inputs, until they have settled.

The data latch and sample channel can be individually controlled by the external trigger input which has a separate logic threshold control, and provision for positive or negative-edge triggering. The trigger signal is detected by a latch, and the state of the latch is displayed by an l.e.d. which flashes when a correct trigger signal has been received. In addition to signals from the trigger latch, control may also be derived from a delay counter which generates a signal a preselected time after the trigger latch has changed state. This delay mode is useful because it allows any combination of pre-trigger and post-trigger information to be stored by the data latch and sample channel. The delay is set by a 0 to 99 thumbwheel switch, and is the thumbwheel setting multiplied by the sample rate selection.

Circuit description

The main requirements for the input interface are that it should be high impedance, fast, and should allow control of the 0 to 1 to 0 transition threshold. The external sample-clock input is similar, but with a preset transition threshold. It is also necessary for the interface to accept both t.t.l. and high level logic inputs. The circuit in Fig. 2 shows the SN2710 comparator which was chosen for its speed and its ability to drive t.t.l. This device does, however, have a relatively high input current requirement which restricts the input impedance. To overcome the in-

Specification	
Data inputs, sample channel and compare /inhibit input	
Propagation delay for low to high	70ns
Propagation delay for high to low	95ns
Input resistance	90kΩ
Transition threshold	1.5 to 10V
Transition hysteresis	0.175V
Maximum input	+12V
Minimum input	-2V
Trigger input as above except for	
Propagation delay from trigger signal to disable signal	70ns
Transition threshold	1.5 to 10V
Delay mode	Selectable from 0 to 99 times the selected clock period or external input period
Clock	
Source	Internal oscillator or external input
Clock period selection	20ns to 20ms
External input	The same as data input except for threshold which is fixed at 2.2V.

herently low hysteresis of the comparator, about 175mV of feedback hysteresis is added by R₃.

A combination of input resistance and intrinsic shunt capacitance of the comparator tends to increase the propagation delay, but this has been partly overcome by the addition of a speed-up capacitor C₁, which provides some input overdrive for each edge of the input waveform. The reference voltage for each comparator is derived from a common op-amp via separate source-impedance matching resistors. It is essential that a well-stabilized voltage is used for the variable threshold levels, because power supply ripple can cause incorrect transition switching.


Low power Schottky t.t.l. is used to limit the load on each comparator, and

to keep the total propagation delay to a minimum.

Trigger and delay

The trigger and delay circuit is shown in Fig. 3. The trigger channel is interfaced with its own threshold control, and the signal is used to clock a D type flip-flop connected as a latch. The output of the latch is used to gate a low-frequency oscillator which drives the trigger indicator lamp and delay counter. As shown, the latch can be reset using the clear input, and positive or negative-edge triggering is achieved via two inverters. Once the latch has been triggered, the CTL output goes high and enables the two synchronous decade counters. The count is compared with the thumbwheel switch setting by exclusive-OR gates, and the gated outputs are decoded when the counter value reaches the required number. The counters are then disabled by taking their inputs low. The delay and the CTL signals can both be used for switch selection to the sample channel and the

Fig. 2. Interface comparator and threshold level controls. Resistor R₃ provides about 175mV of feedback to increase the hysteresis.

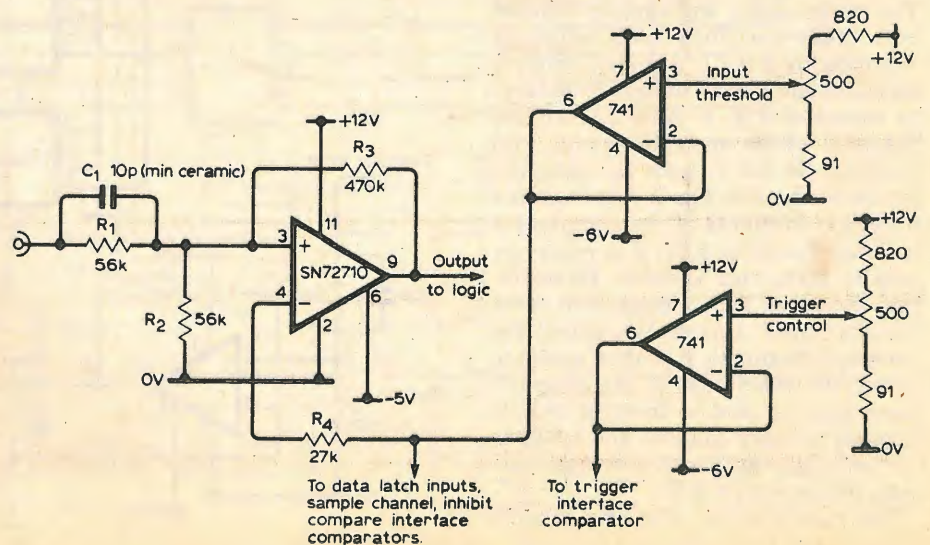

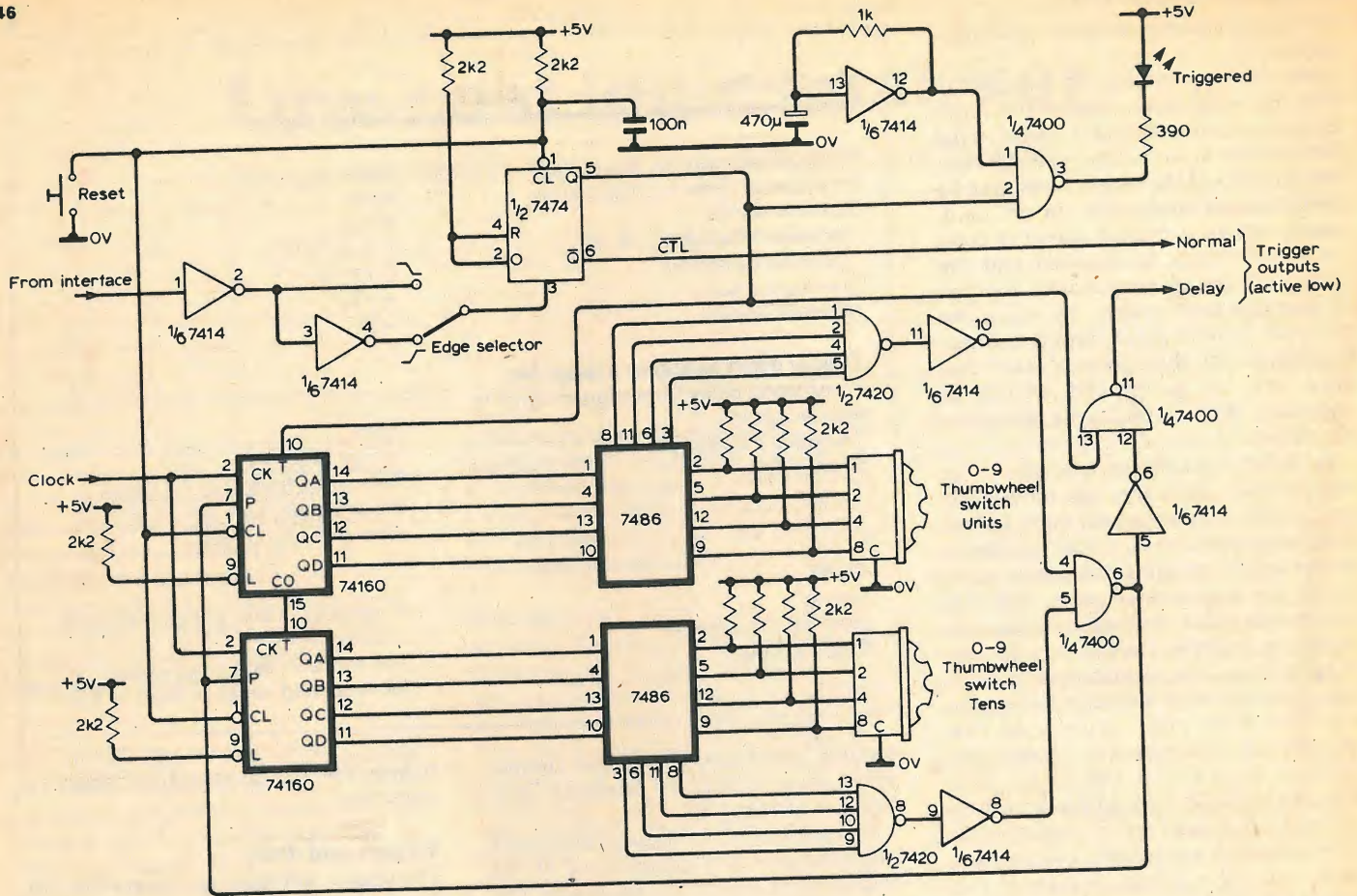


Fig. 3. Trigger and delay circuit. The counter clock may be fed from the clock and divider chain in Fig. 4, or from the external input.


Fig. 4. Clock generator and external input.

data latch disable inputs. The counter clock period may either be derived from the internally generated clock and divider chain in Fig. 4, or from the external input, in which case the delay counter can be used to trigger a data section after a pre-determined number of pulses at the trigger input.

Internal clock generator and external input

The trigger-delay and sample-channel both require a clock train which is supplied by a t.t.l. Schmitt trigger oscillator and a chain of decade dividers as shown in Fig. 4. Alternatively an external clock may be used, and provision for this is made by using the interface circuit in Fig. 2. Although the transition threshold of the comparator is shown preset at 2.2V, it is relatively easy to make this variable. However, this should be kept independent from the data-input threshold control for maximum flexibility. It is often useful to determine which edge of the external-input signal is used to drive the sample channel or delay counter, and a switch for selecting the positive or negative-edge has been included.

The total number of clock outputs

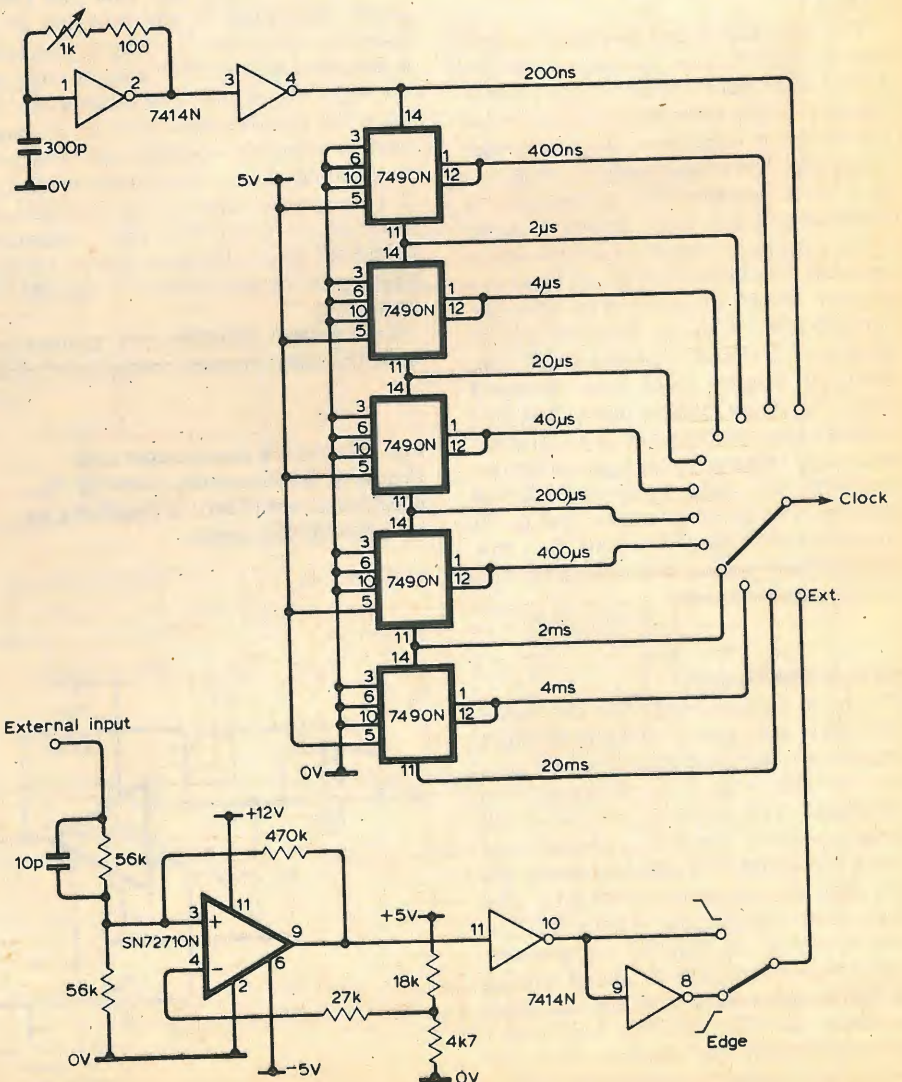

available, including the external source, is twelve and on the prototype these are selected by a 1-pole 12-way rotary switch connected to the clock inputs of the sample-channel and delay-counter which are linked. It is just as easy, however, to allow both clock inputs to independently select a clock line by using two rotary switches.

Data latch inputs and hexadecimal comparator

The data-latch and l.e.d. display circuitry is shown in Fig. 5. The interface comparator outputs in Fig. 1 directly drive the hexadecimal comparator and the bistable latches. The latch outputs each control an individual l.e.d. which is positioned on the front panel directly above the corresponding data input socket.

While the enable input is at logic 1, the latch output will follow the data input condition, and when the enable is taken to a logic 0, the latch output will hold the logic state which was present

Fig. 5. Data latch and display. Because the 74LS latches have a low output current capability, a reduced l.e.d. current of about 5.5mA is used.


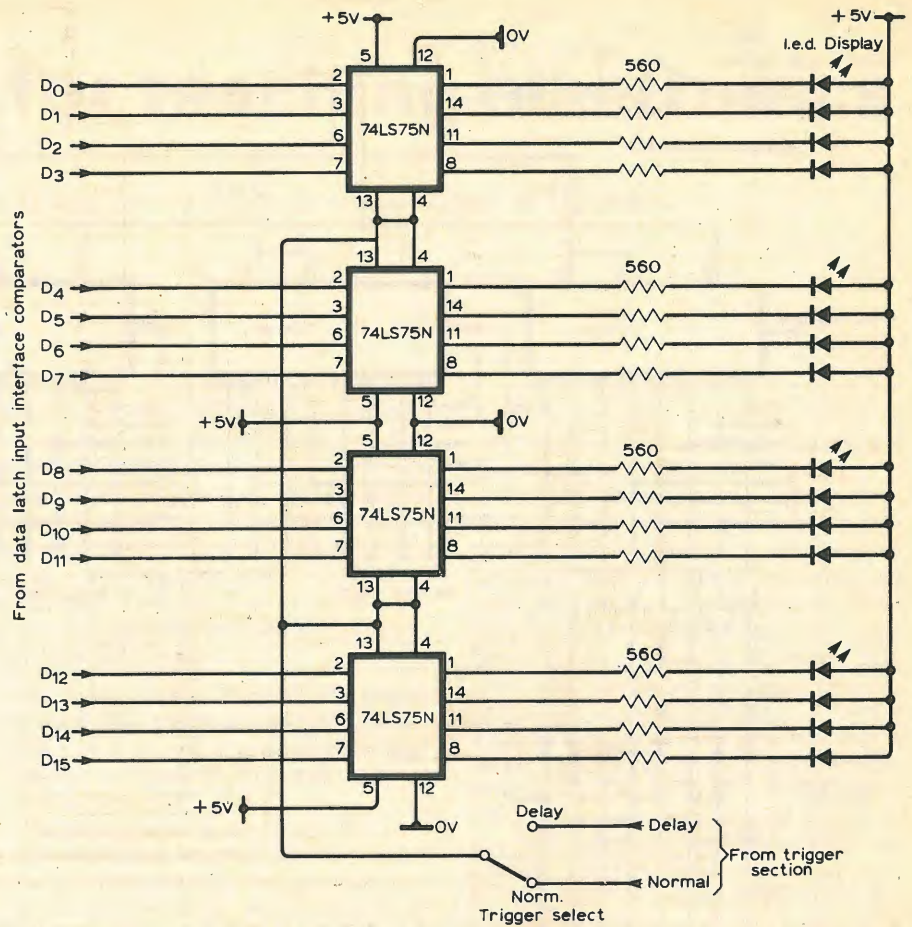


Fig. 6. Hexadecimal comparator.

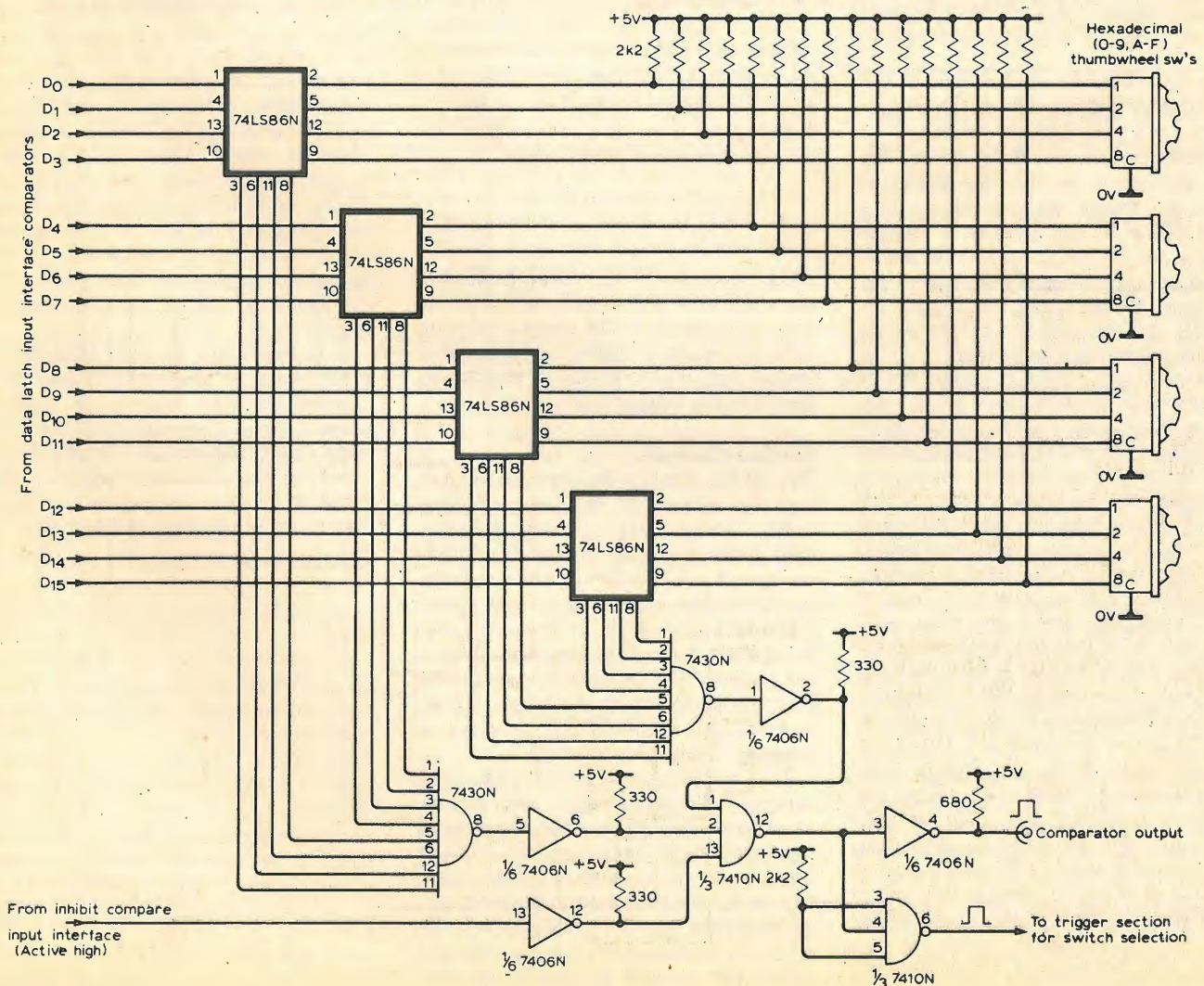

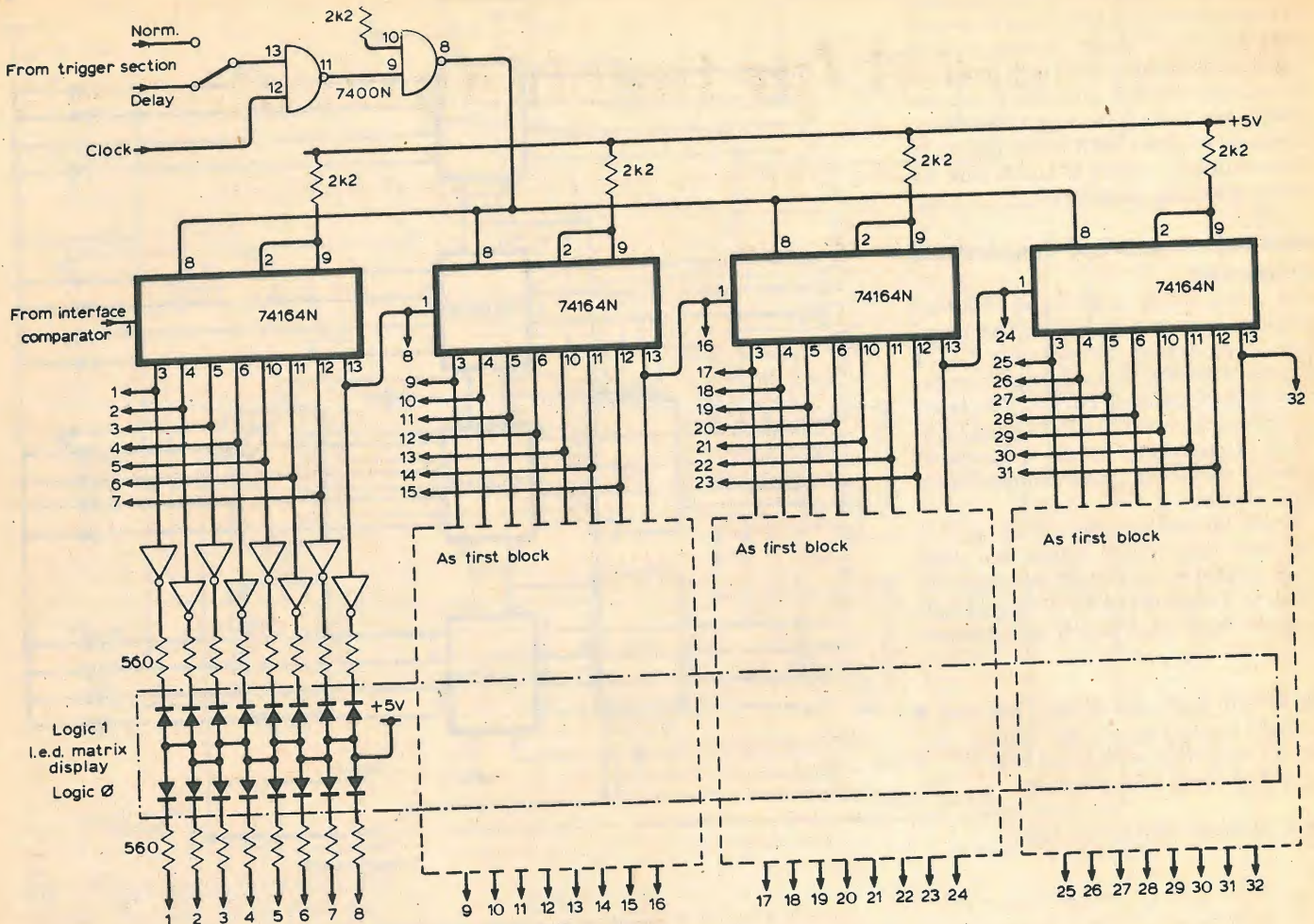


Fig. 7. Sample channel and display matrix. In the prototype, two spare NAND gates were used as inverters. All other inverters are 7400N types.

at the time of the transition. The latch-
enable signal is derived from the trigger
section and a switch is provided to
select either normal or delay mode. The
data-latch therefore has the ability to
sample and freeze the state of the data
inputs either at the time of a trigger
signal occurring, or at a pre-determined
time or operational point after the trig-
ger signal. By disabling the trigger in-
put, the i.e.d. display can be used as a
16-bit real time logic indicator.

The low output current capability of
the 74LS series necessitates a lower i.e.d.
current than would normally be used,
and in this case it is about 5.5mA. How-
ever, this has proved to be quite
acceptable. By using the Q latch output,
an i.e.d. that is illuminated indicates a
logic 1 and vice versa. The circuit has
been designed to show 16 bits of data,
although this can easily be expanded or
reduced in blocks of four bits depending
on the user's requirements. It should be
noted that extra control signal buffering
will be required if further bits are added.

The hexadecimal comparator section
is shown in Fig. 6. The comparator
continuously compares the logic state
of the data inputs with a hexadecimal-
coded binary value set on the thumb-
wheel switches. This signal can be used
as a control for either external use or as
a trigger command, and also as a signal
to be displayed on the sample channel.
The compare/inhibit input, which uses
the standard interface, disables the

compare-output when taken high, and
thus inhibits unwanted comparisons
from the exclusive-OR gates. An open
collector output is taken to a front panel
socket and also to a switch which can
feed it to the trigger input.

Sample channel

The 32-bit sample-channel store uses
four 8-bit series shift-registers as shown
in Fig. 7. Input data is presented to the
shift register via an interface compar-
ator, and clocked through the register
on the positive edge of each clock cycle.
Therefore, the register contains the
input logic states that appeared during
the previous 32 clock periods. By dis-
abling the clock when a trigger signal
occurs, the register will store the
previous 32 bits of input data.

The register contents are con-
tinuously displayed on an i.e.d. matrix
as shown. The top row of the matrix
represents logic 1 register bits, and the
bottom row represents logic 0. By using
the external clock input, the combina-
tion of shift register and display forms
a time or data domain storage channel
which can be used for displaying one-

shot pulses or pulse trains. Use of the
trigger-delay mode enables the channel
to store and display events occurring
after the trigger signal. By delaying 16
sample clock periods, the first half of the
display will show the state of the sample
channel input for the 16 clock periods
before the trigger signal, and the second
half of the display will show the state of
the input for the 16 periods after the
trigger signal.

It is important to note that for an
input pulse or change of state to be
clocked into the register, it must be
present for at least one positive clock
edge. For this reason, it is always advis-
able to have a clock sampling frequency
of at least five times the expected
frequency of the input waveform. □

to be continued

New format for teaching electronics

"Novatexts" are a breakaway from conventional textbooks

by Peter Williams Ph.D., Paisley College of Technology

TEXTBOOKS HAVE NOT CHANGED their format in our generation — nor in the last. There are good reasons for this: the format has been successful for so long that there have to be. Conventionally the work is divided into chapters of roughly equal length, each chapter dealing with a single subject. Within each chapter there is a variety of information. In engineering and science at least four types are distinguishable: diagrams, figures and graphs; text, often describing the diagrams and linking them to the analysis; mathematical material developing the theoretical background; examples either practical or numerical. The last category can be extended to include data on particular devices or systems, references to related topics and so on. It is possible without diminishing its importance to describe this section as "house-keeping", a collection of useful functions that vary from occasion to occasion, e.g. some chapters lend themselves to worked examples, while others benefit from reference to manufacturers' data.

On each subject the reader is presented with this range of information, that, fully absorbed, leads to a balanced judgement. It is at this point that the approach can be challenged. It assumes implicitly that each reader is in need of all the information all the time. In some cases certain sections are indicated as being of advanced level, or of being subsidiary to the main theme, but that all the types of information are necessary does not appear to be questioned.

Consider the order in which the material is presented: the text introduces a topic, followed by a circuit diagram, a graph or a scale drawing. Some aspect of the material is then analysed, perhaps with a worked example and the text resumes. The pattern, or sometimes the lack of it, is repeated throughout each chapter, the aim being to provide a logical and coherent development of the whole subject at a level appropriate to the readers. The material is presented sequentially, and the reader is constrained to follow that sequence if he or she is to benefit most from the efforts of the author.

★ ★ ★

The proposition underlying the new approach is simple: that at any given

time the information needed by a reader is less than that presented by the author. (This does not conflict with the truism that the need is always more than any author can provide.) The proposition is that different types of information are appropriate to different users, and to the same users at various times. The following illustrations may help to make the case:

- a technician asked to produce a piece of test equipment would find a diagram of a circuit or a scale-drawing helpful, particularly if backed up by a worked example.
- a student meeting a subject for the first time would need a description of the principles well before the rigours of the mathematical analysis became important.
- during a second-level course the general principles should have been absorbed leaving the analysis as the key section though with reference to explanatory material to fill gaps in the memory.
- a working engineer coming on an unfamiliar topic would welcome a visual summary of the subject in diagrammatic or graphical form; this would show the degree of relevance of the material and whether the text and analysis merited further study.

This is the case for the separation of a subject into separate types of information. It is not argued that this should always be done, but that it is an alternative of say diagrams, text analysis, examples. The weakness is that the physical separation onto different pages makes it almost as difficult to find the explanation of a diagram or the equations referred to in the text. There appears to be no way of juggling the information in a book to meet these requirements. This is because there is the hidden and apparently reasonable assumption that each sub-division of the book needs a number of pages. To a reader of this journal it will be clear that the format allows a far greater amount of material on the page. As a rough guide a WW page of text has 1200 to 1600 words depending on the type-size. By comparison, a novel has about 220 to 300 words per page with comparable figures for many text books. This shows the intensive nature of the information available in an A4 journal format — a 300-page text book can be accommo-

dated in less than 60 pages, which is comparable to the editorial matter in a single issue of the journal.

The importance lies not in the value-for-money aspect but in the fact that a double-page spread is equivalent to perhaps a dozen pages of conventional text books. This represents a short chapter, and readily encompasses single topics within a longer chapter. The topic can now be presented at one sitting as it were and the format chosen is shown on page 50. The presentation is series-parallel rather than purely serial in that each of the four types of information appears sequentially but with the four streams of information in parallel. The first-time reader can scan the left-hand column and perceive the nature and scope of the topic at a glance. Even before the details are gleaned from the text, the development of the ideas should be clear and the

"Different types of information are appropriate to different users, and to the same users at various times."


reader should know whether the text analysis or examples are most likely to meet his needs. Thus students, engineers, teachers and technicians can select the types of information they need in the most convenient order.

Because the data streams are parallel, it is easy to cross-refer from diagram to text, to relate the analysis to the diagrams and so on without having to turn pages. To facilitate this a further constraint has been accepted: the text has generally been broken down into paragraphs of 150 to 250 words, with each paragraph related to the adjacent diagram. The diagrams, figures and graphs have been selected to assist this division. It is not thereby implied that all diagrams are of equal importance but the attempt has been made to partition the left-hand page into units of comparable length. This is neither possible nor desirable for the analysis, since certain equations apply to more than one diagram, while some diagrams may require several equations.


continued on page 88

Capacitor charging and discharging


Linear Ramp: Constant Current

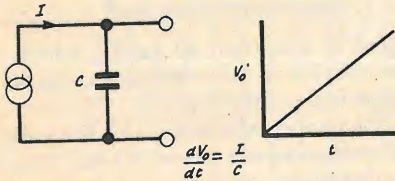


Capacitor Discharge

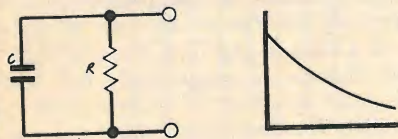


Sawtooth Generation

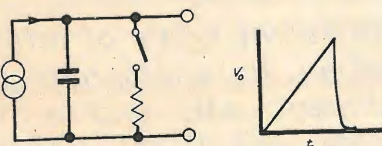

Ramp Non-Linearities

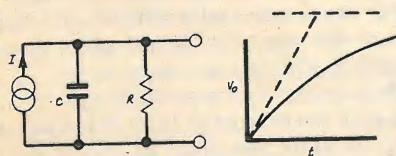

Op Amp Sawtooth Generator

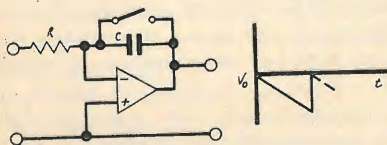

Ramp, sawtooth and triangular wave generators, astables, monostables and pulse generators all depend on one simple fact: when a capacitor accumulates charge from some source of current its voltage changes. Further, the rate at which the voltage changes is directly proportional to the magnitude of the current. The variety of these circuits and their applications tends to obliterate this common property. It is very helpful to return to the behaviour of a single capacitor connected to a current source, a resistor, or both. In this way both the ideal behaviour and the departures from the ideal can be identified before considering the many versions that have been proposed for the above functions. A perfect current generator sustains a defined current into any load including that of a capacitor regardless of the terminal voltage. (Because most practical generators approximate to voltage sources, the behaviour, of current sources may appear less obvious, and a formal restatement of this basic property helps to avoid confusion.) The capacitor has the property that charge and voltage are proportional, $Q = CV$, provided that the capacitance C remains constant. Observing that current is the rate of flow of charge then the relationship between current and rate-of-change of voltage follows.

If a capacitor is charged to a given voltage and then has a resistor placed in parallel with it, that charge is dissipated. The higher the terminal voltage the greater the initial current flow and hence the rate at which the charge is lost. Hence the slope of the voltage waveform is steep at first, progressively diminishing as the voltage falls. The voltage is asymptotic to zero and the point at which the capacitor is said to be 'discharged' is thus arbitrary — for practical purposes, a final voltage of 1-10% of the initial value might be used. (In some cases the presence of a constant-current term in the model of the active devices used results in the capacitor voltage genuinely passing through zero). The property that the rate-of-change of voltage is proportional to the voltage itself leads to an exponential relationship between voltage and time. In this the resistor and capacitor always appear in the relationship as a product and it is convenient to write $\tau = CR$ where τ is referred to as the time constant of that portion of the circuit. A complex circuit has many time constants but it is often possible to evaluate the effects of each separately.

The two previous voltage waveforms can now be joined together to provide a pattern that if repeated continuously is described as a saw tooth waveform. It consists of a linear slope or ramp followed by a rapid, but not necessarily linear, return to zero or some very low value. A single cycle of this waveform can be obtained by switching the capacitor from the current generator to the resistor. This would leave the current generator open-circuit for part of the time, and by analogy with a short-circuited voltage generator this state of affairs can be seen as undesirable. As the discharge is required to be very rapid the current flow in the resistor is much greater than that from the source and it is more usual to leave the current generator connected. This raises the minimum value of the final output to IR , but provided $IR \ll V_{C(\text{max})}$ this is no great disadvantage. The switching is simple in this form, consisting only of a single-pole switch. If the switch is operated at pre-determined instants the generator is said to be triggered and such a ramp-generator is the basis of oscilloscope time-bases. Alternatively, a level-sensing circuit can be used to activate the switch when the ramp reaches some particular voltage (free-running mode).

No perfect current generator exists, and the imperfection is most often that of a constant parallel resistance. This includes any leakage resistance of the capacitor and the input resistance of the following stage, as well as the finite output resistance of the generator. The current in the resistor is still much less than that from the generator if the circuit is to have any pretence of being a ramp generator, but the gap progressively closes as the output voltage increases. Hence the output departs from the ideal linear ramp. The error can be calculated either in terms of the difference between the actual and ideal voltages at any instant or in terms of the difference in the slopes. As the purpose of such a calculation is often to compare the relative merits of different arrangements it matters little which is used; the slope error is easier to calculate and is used in the following section. The actual error is usually obtained by expanding the exponential equation and taking account of the low-order terms in the expansion. In circuits involving active devices, the effect of finite voltage and current gains are shown to be equivalent to additional resistive losses.

A practical and widely-used form of sawtooth generator uses an operational amplifier. The configuration is that of an inverting integrator, and with a constant input voltage, the current in R is constant, assuming a true virtual earth corresponding to infinite voltage gain. Departures from this assumed condition are discussed later. The input current of an operational amplifier is finite, small and almost independent of the signal condition. It may be either positive or negative depending on whether npn or pnp transistors form the input stages. This current either increases or decreases the capacitor current by a small but constant fraction, leaving the ramp linear but with a slightly modified slope. Any voltage offset of the input devices modifies the voltage across R , providing a similar slope error. The inverting nature of the stage results in a negative-going output ramp for a positive input voltage. It is the virtual earth behaviour resulting from the very large voltage gain that allows the constant input voltage to produce a proportional and constant charging current. It also allows the output voltage to be nearly equal to the capacitor voltage while the output can be loaded without any significant change in the capacitor current.

Capacitor charging: constant-current

THEORY

The voltage built up across a capacitor when charged from a constant-current source follows from the basic relations

$$Q = CV$$

$$I = dQ/dt$$

$$\frac{dV}{dt} = \frac{1}{C} \frac{dQ}{dt} = \frac{I}{C}$$

$$\text{and } V = \int_{t_1}^{t_2} \frac{I}{C} dt$$

For I constant, and V_1 the initial value of V

$$V = \frac{I}{C}(t_2 - t_1) + V_1$$

In many practical circuits the initial voltage across the capacitor is zero giving

$$V = It$$

The discharge cycle would be similar, with a constant current discharge; in most cases the discharge is through a resistor. Let the initial voltage be V_1 , with the current flowing *into* the capacitor still I

$$\frac{dV}{dt} = \frac{I}{C} = \frac{V}{CR}$$

For convenience write $CR = \tau$ the *time-constant* of the CR network

$$\frac{dV}{dt} = \frac{V}{\tau}$$

Hence $V = V_1 \exp -t/\tau$

with $V \rightarrow V_1$ for $t \rightarrow 0$

and $V \rightarrow 0$ for $t \rightarrow \infty$

There are two conditions of interest in which both resistive and constant current terms are present. In the first, the resistor switched into the circuit to discharge the capacitor is normally so low that the constant current has a negligible effect on the duration of the discharge. It limits the absolute lowest output to IR.

The second condition considers the effect of stray leakage or load resistances that disturb the linearity of the charging cycle.

$$\text{Then } \frac{dV}{dt} = \frac{V}{\tau} + \frac{I}{C} = \frac{1}{C}(I - V/R)$$

The slope departs from the original value of I/C more and more as V increases, with a fractional error of $(V/R)/I$ corresponding to V/V_{max} where V_{max} is the theoretical maximum voltage output if all the current were flowing in the leakage resistance R. The analysis can also be carried out by converting into the corresponding voltage generator form and treating it as a standard RC timing circuit with a corresponding large drive voltage (IR), with the output as only a small portion at the bottom of the experimental charging cycle.

The information can be applied to the op.amp sawtooth generator shown. To a first order for high-gain op.amps, the capacitor current depends on V/R and the input bias current. The latter is independent of the output voltage to a first order i.e. modifies the output slope to be proportional to $(V/R - I_{bias})$ without disturbing the linearity.

EXAMPLES

1. An operational amplifier has a compensating capacitor of 30pF into which its first stage can deliver a maximum current of $\pm 20\mu A$. Calculate the slew rate i.e. the maximum rate-of-change of voltage across the capacitor


$$\frac{dV_C}{dt} = \frac{d(Q/C)}{dt} = \frac{1}{C} \frac{dQ}{dt} = \frac{I}{C}$$

$$\frac{dV_C}{dt_{max}} = \frac{I_{max}}{C} = \frac{20 \cdot 10^{-6}}{30 \cdot 10^{-12}} \text{ V/s}$$

$$= 0.67 \times 10^6 \text{ V/s}$$

$$= 0.67 \text{ V}/\mu\text{s}$$

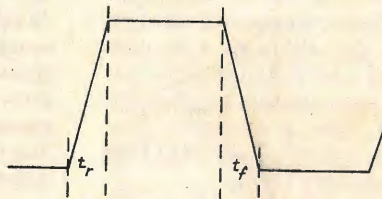2. An amplifier is loaded by a stray capacitance of 10pF and is to reproduce 10V peak-peak square-waves at a 10MHz clock-rate. What should the peak current-capability of the amplifier be, if the rising and falling edges are to occupy less than 10% of the total time?



$$t_r + t_f < \frac{100\text{ns}}{10}$$

$$\text{i.e. } t_r = t_f < 5\text{ns}$$

$$\text{As before } \frac{dV}{dt_{max}} = \frac{I_{max}}{C}$$


$$\frac{10\text{V}}{5\text{ns}} = \frac{I}{10\text{pF}}$$

$$I_{max} = \frac{10 \times 10 \times 10^{-12}}{5 \times 10^{-9}} = 20 \times 10^{-3} \text{ A}$$

Hence the amplifier output current must be at least 20mA.

3. A 1mF capacitor in a full-wave rectifier power supply is charged to a peak voltage of 18V. If the voltage is to decay by $< 1\text{V}$ between successive peaks, estimate the minimum value of load resistance that can be used (i) using the exponential decay equations; (ii) by the approximate method of assuming the discharge current is constant at its peak value. Assume mains frequency 50Hz.

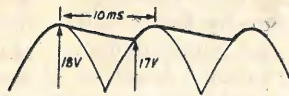(a) Capacitor discharges almost for a half cycle i.e. $\approx 10\text{ms}$



$$17 = 18 \exp(-10^{-2}/R \times 10^{-3})$$

$$\frac{10}{R} = \ln\left(\frac{18}{17}\right)$$

$$R = 175\Omega$$

(b) For linear decay $1 \approx 18/R$

$$\Delta V = 1\text{V}$$

$$\Delta t = 10\text{ms}$$

$$\frac{\Delta V}{\Delta t} = \frac{I}{C}$$

$$\frac{1}{10^{-2}} = \frac{18}{R \cdot 10^{-3}}$$

$$R \approx 180\Omega$$

Sun-spots, sweepers and buried clocks

Although the approaching sun-spot peak is clearly going to be a high one, it now seems that it may not reach the bumper figures (over 200) predicted a few months ago: the sudden "recession" last summer seems to have had a lasting effect. Nevertheless, prospects for 50MHz and similarly high frequencies producing long-distance contacts are good. A series of s.s.b./c.w. contacts between KH6EQI in Hawaii and a number of Australian stations took place last Autumn, for the first time in 20 years.

Martin Harrison, G3USF, recently appealed for co-operation from British amateurs in collating more information on "sweepers and creepers," the unexplained natural emissions that sweep across finite bands of frequencies (often in the region 20 to 30MHz but sometimes much lower). Ted Cook, ZS6BT in Johannesburg, South Africa has recently forwarded to me a tape cassette providing many excellent examples of these curious and distinctive signals. So far, although a number of theories have been tentatively put forward, there is no entirely satisfactory explanation of these phenomena, first observed by Gerson and Gossard in 1958 (see WoAR, February 1978).

R. H. Dicke of Princeton University has recently put forward the idea that despite the apparently large and random variations in the periodicity of the sunspot cycles (cycles varying from 7.3 to 17.1 years have been recorded) the Sun appears to have the ability to "remember" and re-adjust to the correct spacing between maxima — almost as though there were an accurate chronometer buried deep in the Sun. His explanation for the apparent variations is that the transport of the magnetic field from the deep interior to the surface requires a long time and is subject to irregularities.

Band plan problems

The system of voluntary band-planning, introduced into Europe by the RSGB some 30 years ago and subsequently endorsed by the International Amateur Radio Union, has long been recognised as a highly desirable, if not essential, means of separating non-compatible transmission modes. However the increasing number of modes and specialised communication techniques (virtually unknown when the system was set up) is making it difficult to modify and extend band planning so that it satisfies everybody. One finds, for example, grumbles with the present situation on the popular 144MHz band. Some users are seeking specifically a.m. as well as n.b.f.m. "channels" and there have been problems with overlapping "satellite" and "emergency" alloca-



tions. A major problem is that frequent modifications to a v.h.f. band-plan can prove costly for stations not using frequency-synthesizer techniques, owing to the cost of new crystals.

Then again, on h.f. most r.t.t.y. operation is within the "telegraphy" sections of the various bands, though this does not seem to have been recognised by the writers (G3VYV, G8IAT and G4GQO) of the "Letter to the Editor" in the January issue who were apparently "stunned" by my suggestion that this mode can (and does) have high interference-potential. They did not seem to grasp that this referred to those using manual telegraphy, where one would find it extremely difficult to "notch out" an r.t.t.y. transmission, whatever may be the case with 'phone transmissions.

From all quarters

One of the less desirable aspects of amateur radio is that it seems to make its adherents more likely to receive unwanted "chain letters" promising to bring in thousands of dollars to those foolish enough to send money to the name at the top of the list and then forward copies of the letter to about 20 other people. A reader sent me (for inspection I hasten to say) a recent copy of one of these pests with their appeals or warnings against "breaking the chain." Pulling the chain on them is more appropriate.

Special event call signs in the series GB2, GB3 or GB8 plus two or three letters are available through the RSGB provided that application is made at least one month before the event. However, once a particular call sign has been allotted to a group, the same call will not be issued to another group for a different event. The special prefix "GT" is being authorised during the Isle of Man Millennium for use between June 30 and July 8 (inclusive). Normal prefix for the Isle of Man is "GD."

The Japanese scientists — M. Morimoto, H. Hirabayashi and J. Jugaku — have pointed out that if in-

telligent civilisations are common throughout the Galaxy, they must have formed a community using communication and must be sending radio beacon signals. They suggest it is possible to specify not only the most likely frequency on which to listen (4829.659MHz, the spectral line of formaldehyde) but also the directions to be searched.

The Swedish farmer-amateur Lars Erik Johansson, SM4AQL keeps his station on the air (and his farm running) from an ambitious cow-powered methane digester cum electric generator. The reactor, at any one time, contains some 22,000 gallons of slurry formed from the output of 50 cows and 40 heifers, providing 4,000 litres of fresh slurry daily and producing some 70 cubic metres of methane gas each day.

While a number of amateurs have been puzzled at why some Japanese-made amateur radio equipment seems to sell at relatively much lower prices in the U.S.A. than in the UK, rather fewer (Rev G. C. Dobbs, G3RJV of the G-QRP-Club is an exception) have remarked on the extraordinary difference between what the Post Office now charges for International Reply Coupons (25p each) and what it is prepared to give for them.

The BARTG newsletter has pointed out that amateurs using s.s.b. rigs for r.t.t.y. often have power amplifiers working at well under 50 per cent efficiency and that even the old and often discarded a.m./c.w. rigs have uses other than as boat anchors: their Class C power amplifiers and large power units designed for high duty cycles can provide potent r.t.t.y. signals.

In brief

Application has been made for the operation of the first two 24GHz beacon stations on the Isle of Wight and Alderney... National events announced for 1979 include: March 10, National VHF Convention at The Winning Post, Twickenham, Middlex; May 11-12, RSGB Amateur Radio Exhibition, Alexandra Palace, London; August 5, National Mobile Rally, Woburn Park; September 15, RSGB H.F. Convention, Birmingham; and September 22, Scottish V.H.F. Convention, Dundee... Bert Mathews, G6QM of Cheltenham has died — he was a sub-manager of the RSGB QSL Bureau for over 30 years... Denis Campbell, G13TAC, a radio and electronics officer aboard the cable ship "Mercury" has been keeping a daily schedule from the Bermuda area with his father, G130LJ... North Midlands Mobile Rally, organised jointly by The Midland Amateur Radio Society and Stoke-on-Trent Amateur Radio Society will take place on Sunday, April 29 at Drayton Manor Park, near Tamworth.

PAT HAWKER, G3VA

Electronic organ tone system — 5

Vibrato, noise, expression pedals and stop control

by A. D. Ryder, M.A., Ph.D., F.I.E.E.

This article completes the section on tonal variations, and concludes the electronic organ tone system by describing further optional additions together with some general notes.

MODIFIED FILTERING may also be useful with cross-keyed ranks (see below), otherwise only octave harmonics are available.

For use with modified filtering, the harmonic content of the SQB signal may be increased by combining octavely-related divider outputs to produce an unequal mark-to-space ratio signal for gating. It is preferably to use OR or NAND functions rather than their inversions to minimise the d.c. component. For example, the NAND of 65.4, 131 and 262Hz provides a 1:7 pulse with a fundamental of 65.4Hz for which the first 16 harmonics are listed in table 12 with a saw-tooth for comparison.

Because the third harmonic of F1, for example, is nearly equal in frequency to C₃ with accurate equal temperament, an out-of-tune rank may be built up using 3/4 F1, for C1, 3/4 F'1 for C'1 and so on, which contrasts usefully with in-tune stops. This requires keying signals KB in Fig. 14 to be cross-linked (or separately generated). For example, the KB signal from manual C1, normally at 65.40Hz, must drive a gate on the F card supplied from the 1.5f₀ divider output at 65.48Hz, and so on with these gates feeding a separate set of buses. A similar scheme is possible using the fifth harmonic where the much larger frequency difference produces noticeable beats similar to a celeste. The lowest note of a celeste rank is usually tenor C, and the appropriate frequency is available at 2.5f₀ on the G' card. Table 13 shows the linking pattern for both arrangements. The same principle could be applied using the 7th and 9th harmonics to create larger frequency-differences. To provide the necessary frequencies, the reference input in Fig. 47 would be 12f₀ or 24f₀ with p.l.l. circuit components modified accordingly.

As the ear is insensitive to pitch at

Table 13 Third and fifth harmonic cross-keying. The table shows manual frequencies for the first octave of each cross-keyed rank.

Played	CK1	C'K1	DK1	D'K1	EK1	FK1	F'K1	GK1	G'K1	AK1	A'K1	BK1
Keyed	F1.5	F'1.5	G1.5	G'1.5	A1.5	A'1.5	B1.5	C03	C'03	D08	D'03	E03
Hz	65.48	69.38	73.50	77.87	82.50	87.40	92.60	98.11	103.9	110.1	116.7	123.6
Played	CK2	C'K2	DK2	D'K2	EK2	FK2	F'K2	GK2	G'K2	AK2	A'K2	BK2
Keyed	G'2.5	A2.5	A'2.5	B2.5	C05	C'05	D05	D'05	E05	F05	F'05	G05
Hz	129.8	137.5	145.7	154.3	163.5	173.2	183.6	194.5	206.0	218.3	231.3	245.0

high frequencies, the 8th harmonic signal may be extended beyond EK5 by using 6th harmonic frequencies and so on. This is equivalent to the breaking back of a mixture. The transistor gate in Fig. 13 can function as a mixer because of the low input resistance at the base, but its usefulness is limited to octave combinations due to transient effects during keying. To build up a mixture rank, separate gates are preferable although they may use a common SQB set and filter. For comprehensive mixtures, it is necessary to expand to two sets of cards,

Vibrato

The term vibrato is used here for frequency modulation at 4 to 8Hz with a pk-to-pk amplitude of up to one semitone, 100 cents, though much smaller amplitudes, down to five cents or less, are useful. Sinusoidal modulation is preferable for large amplitudes. As noted in part 2, f.m. may be applied directly to the gate-card generators and, if a common signal is used, normal vibrato is produced. A 100 cent swing requires about 0.7V r.m.s. at the vibrato inputs. The use of independent signals is considered in the next section. Fig. 48 shows a low impedance sinewave source suitable for normal vibrato. In the trigger circuit, R₁ or R₂ may be trimmed for an equal mark-to-space ratio at A, i.e., for minimum second harmonic. Resistor R₃ or C₁ sets the

Fig. 48. Low impedance sinewave source for vibrato. The potentiometer may be remotely mounted and connected with twisted wire.

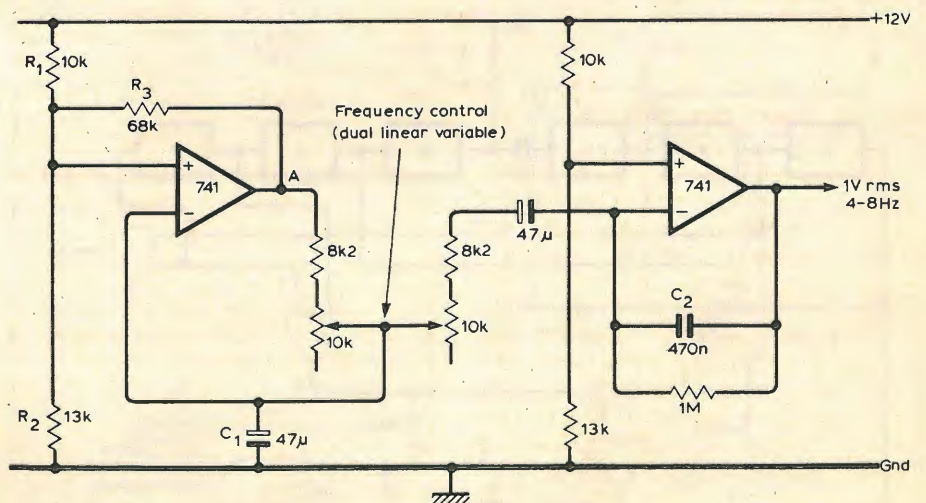


Table 12 Harmonic components as a percentage of the fundamental.

Harmonic No	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16
1:7 pulse	100	92	81	65	48	31	14	0	11	19	22	22	19	13	7	0
Sawtooth	100	50	33	25	20	17	15	13	11	10	9	8	7	7	7	6

frequency range of the control, which may be remotely mounted using twisted wire. The output level may be increased up to about 2.5V r.m.s. by reducing C_2 .

Vibrato applied at the generators will affect all three departments and all frequencies. Vibrato to an individual department offers more flexibility, and helps a solo stop, for example, to stand out distinctively. It is sufficient to consider the h.f. channels only, because a pipe organ vibrato or tremulant has little effect on the bass pipes. Frequency modulation can be achieved by passing the signal through a bucket-brigade delay device, such as the Mullard TDA 1022 or Reticon SAD 1024, and modulating the clock frequency. The phase ϕ of the output, relative to the input, depends on the line delay D , and because the frequency corresponds to $d\phi/dt$, the output frequency varies as dD/dt . For sinusoidal modulation, the peak frequency deviations occur at the zeros of the modulating signal, where

its slope is a maximum, and so have an amplitude proportional to both the frequency and amplitude of the modulation. Also, because D is a number of clock periods, e.g. 256 periods, it is the clock period rather than its frequency which should be linearly related to the modulating signal.

The circuit in Fig. 49 shows a period-modulated oscillator based on Circard 15-16, with a current mirror for constant-current charging of the 470p timing capacitor. The modulation amplifier provides the necessary low-impedance drive to pin 5, and has a gain inversely proportional to frequency so that the peak dD/dt , and thus the signal frequency deviation, is independent of the modulation input frequency. The clock excursions are greatest at low modulating frequencies, and the working point of pin 5 is set by the 7k5/8k2 divider to maximise the linear range. The adjustment can be trimmed by using a p.l.l. with a suitably short loop

time-constant to derive the effective modulation waveform, and with a signal of say 8kHz as a carrier. The oscillator frequency is controlled by the voltage at pin 5 and R_1, C_1 . The 6k8 resistor reduces the charging time of the input blocking capacitor at switch-on.

Bucket-brigade devices need two-phase clock signals, and manufacturers' data sheets show suitable circuits for deriving these from an input of twice the required clock frequency. The circuit values in Fig. 49 are for a 100 kHz clock, which requires the oscillator to run, unmodulated, at 200 kHz. Using a delay of 256 clock periods, the required modulation input is then about 1 V r.m.s. for 50 cents pk-to-pk f.m. Deeper modulation up to about 100 cents can be used, but the low-frequency limit is 4 to 5 Hz at this level. Although it entails correspondingly wide excursions, a relatively high clock frequency minimises a.f. noise from the device, and raises the frequencies of spurious output signals, so that a second-order output filter with a corner frequency of 12kHz is satisfactory. Care should be taken to set the signal input bias to the centre of the linear range, and r.f. bypassing at the input may also help to reduce noise.

In general, organ pipe harmonics fluctuate in phase with respect to the fundamental, and this effect can be simulated using a modulated and an un-modulated channel with a passive 6 dB/octave crossover at say 1 kHz, so that the modulated channel predominates at h.f. Separate speakers allow reflected sound to smooth out the comb-like frequency response which is produced if a delayed and undelayed channel are mixed electronically. Various other effects are possible by cyclic variation of channel gain, etc.

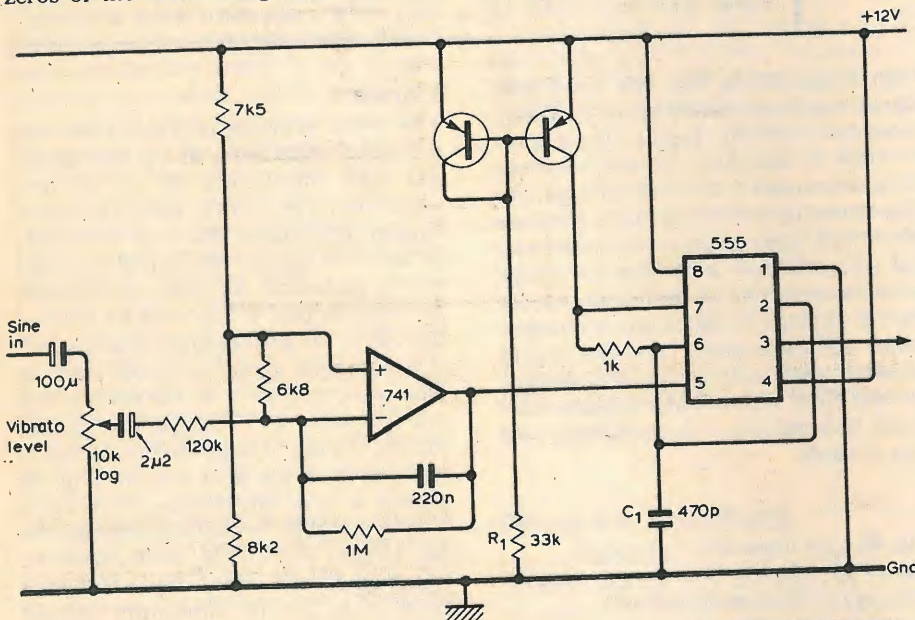


Fig. 49. Period-modulated oscillator. The oscillator frequency is controlled by the voltage at pin 5 and R_1, C_1 .

Noise: quasi-chorus

A pseudo-random binary sequence (p.r.b.s.) noise generator with a cycle length of $2^{18}-1$, approximately 262,000 is shown in Fig. 50. Using a clock frequency of about 30 kHz, the signal at any output is substantially uniform over the a.f. range, and the periodicity of about $8\frac{1}{2}$ s is unnoticeable. The clock may be derived from the 1 MHz crystal by using a division of 32, or from pin 3 of the 240 divider in Fig. 37, about 29 kHz. A noise-jitter chorus effect can be produced by applying band-limited noise signals to the gate-card vibrato inputs, and the circuit in Fig. 50 provides four time-shifted versions of the p.r.b.s., each of which may be used to modulate three adjacent semitones. The network shown at D has a 3 dB frequency of about 100 Hz, and also sets the mean level at E to +2V, which avoids transient frequency shifts when the switch is operated.

For use as a noise bus for mixing into stop combinations, the p.r.b.s. signal needs to be gated, by key operation, with an amplitude following roughly an

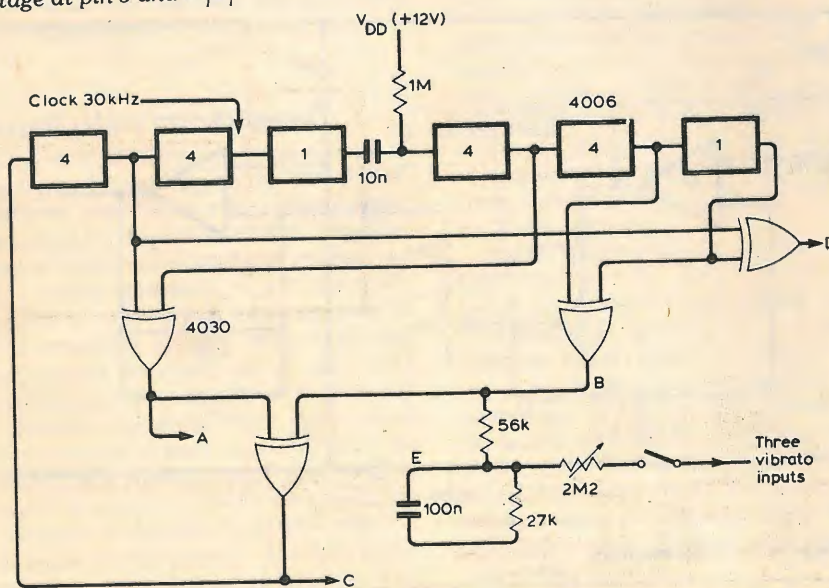


Fig. 50. P.r.b.s. generator with additional output. The capacitance coupling avoids persistence of the all-zeros condition. The output network shown at B is repeated for outputs A, C and D.

r.m.s. characteristic. Fig. 51 shows a basic circuit where Tr_2 corresponds to the p-n-p transistor in Fig. 33, and the noise gate is an inverted form of those in Fig. 13. Again, the time-shifted outputs of Fig. 50 can provide substantially uncorrelated signals for different stops or departments.

Expression pedals and amplitude modulation

The usual pipe organ expression pedal, which controls the swell department only, allows a greater variety of effects than if the whole organ were enclosed in a swell-box, and this arrangement can be adopted with the present design, with pedals for the other departments if required. A wide-range pedal is hard to control musically, and 15 or 20 dB is about right. The MC3340P electronic attenuator can provide a simple noise-free control, and although it introduces some low-order distortion at higher attenuations, this is not a serious drawback. The main difficulty is in the scaling, and each device needs individual calibration. Fig. 52 shows the basic connections. The gain depends on the pin 2 voltage, and is controllable by an external resistance R_c . The gain reaches a maximum of about $\times 4$ when R_c is zero. If this is defined as 0 dB, the gain varies more or less linearly with R_c between about -6 dB, ($R_c = R_{6_0}$) and -26 dB, ($R_c = R_{26}$). These two values must be found by trial, and also the open-circuit voltage E at pin 2, and R_{e_0} , the value of R_c which pulls down the pin 2 voltage to $E/2$. Typical values are $R_{6_0} = 7k\Omega$, $R_{26} = 12k\Omega$, $E = 5.3$ V, $R_{e_0} = 4.7k\Omega$. Resistance R_c can consist of a fixed $7k\Omega$ resistor in series with a $5k\Omega$ variable which is controlled by the pedal. In practice, however, the choice of pedal resistor is restricted. Fig. 53 shows a simple pedal linkage with an approximately linear action over an arc of 90° . This operates a wire-wound variable resistor which gives, for example, a swing R_v of $3.3k\Omega$ with a $10k\Omega$ variable resistor. In general, it is necessary to scale down the effective value of R_{e_0} and hence R_{6_0} and R_{26} to suit the available R_v , by a factor s , which in this case is $3.3/5.0$ or 0.66 . Fig. 54 shows two additional resistors R_a and R_b , which are used for this purpose. Assuming a 12V supply, the values are

$$s = \frac{R_v}{R_{6_0} - R_{26}}, R_f = s \cdot R_{6_0}$$

$$R_a = \frac{12 \cdot s \cdot R_{e_0}}{E(1-s)}, R_b = \frac{E \cdot R_a}{(12-E)}$$

For a 15dB range, R_{21} is measured and used in place of R_{26} .

The MC3340P may also be used for amplitude modulation tremulant by applying the modulation to pin 2. However, if an expression pedal is used as well, the modulation sensitivity necessarily varies with the pedal setting. To compensate for this, C_1 is increased to say $47\mu F$ to have a dominantly low reactance. The modulation is applied to

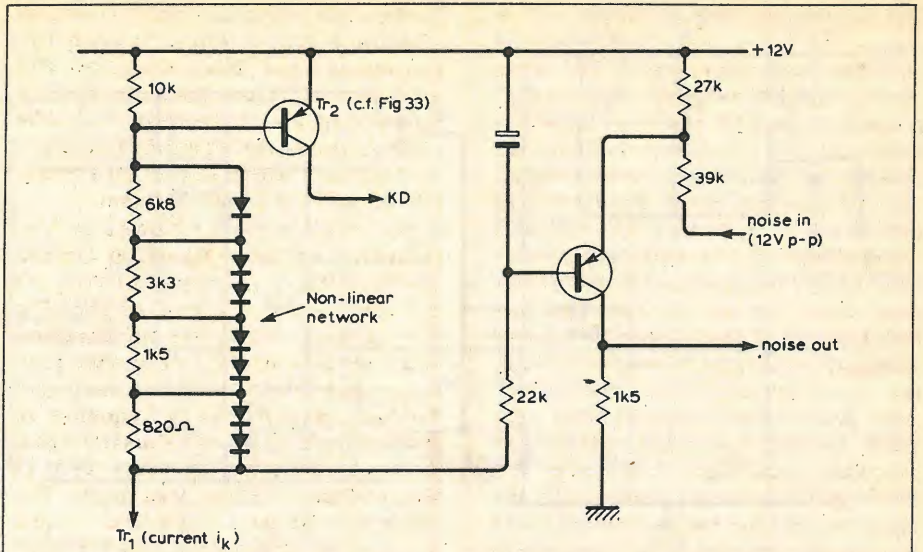


Fig. 51. Basic noise gating. The current i_k is proportional to the number of keys operated, and the noise output amplitude is required to vary as $\sqrt{i_k}$.

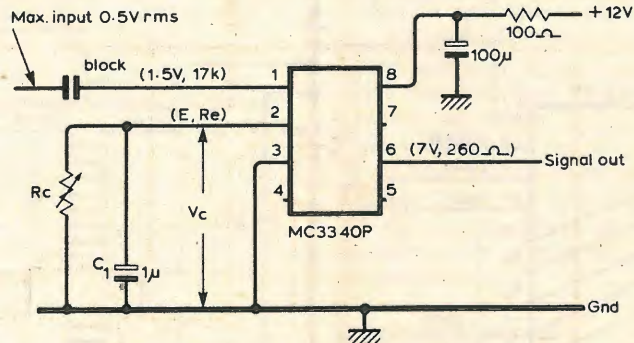


Fig. 52. Basic electronic attenuator. The figures in brackets show open-circuit d.c. voltages and internal resistances.

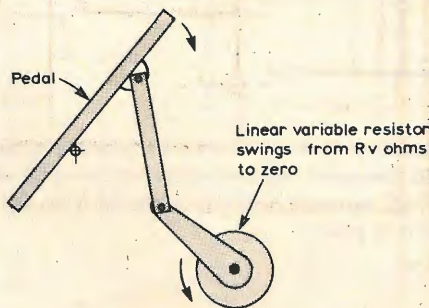


Fig. 53. Expression-pedal linkage. This arrangement provides an approximately linear action over an arc of 90° .

Fig. 54. Modified control network.

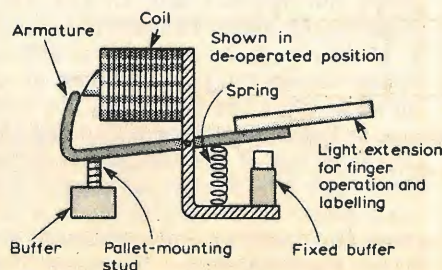
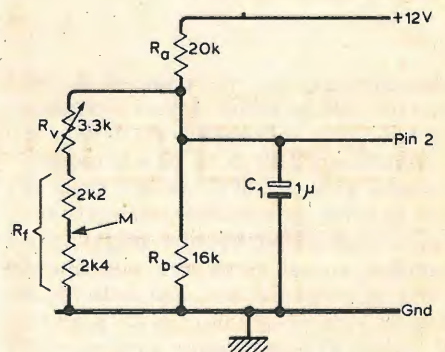


Fig. 55. Pallet-magnet with tab extension.

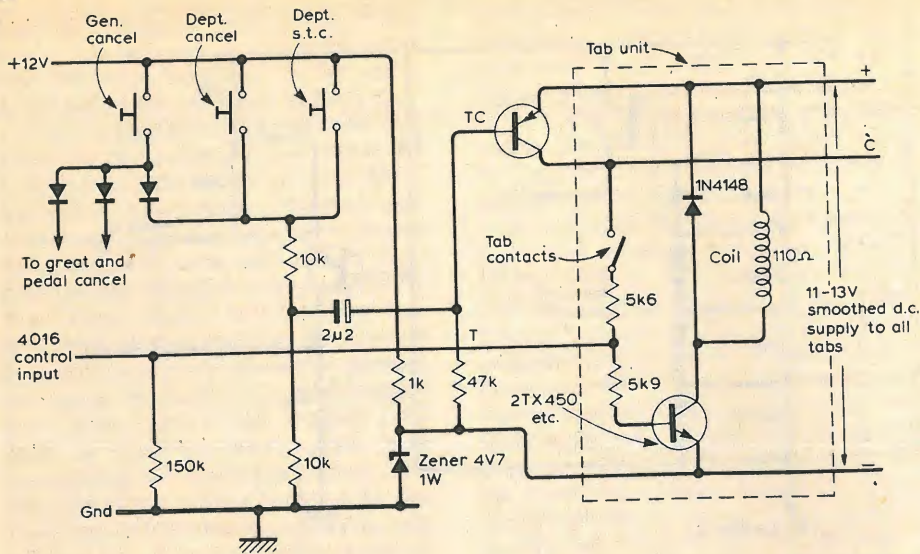


Fig. 56. Stop tab circuit and swell department cancelling.

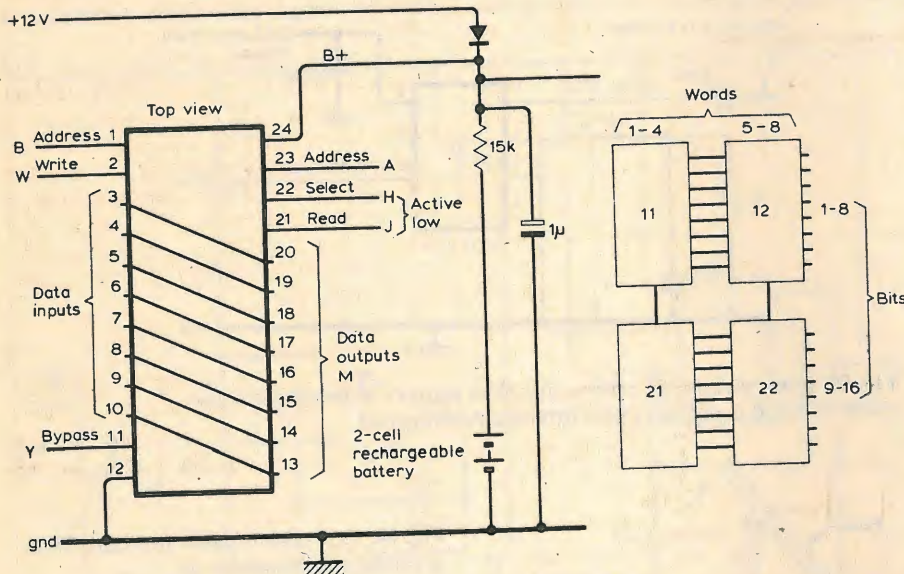


Fig. 57. Pin connections for the 4036 and battery. The insert shows a block diagram of the four packages for one department, and these are wired as follows, B+, gnd, A, B, J, W and Y - common to all four. 11-12, 21-22, outputs and inputs, (pins 13 to 20) - common in pairs. 11-21, 12-22, H, - common in pairs.

approximately the mid-point of R_f , so that the voltage swing at pin 2 increases as the gain increases. At 6 Hz, a modulation of 2 dB pk-to-pk will require an input at M of 100 to 150 mV r.m.s. If two or three independent channels are to be controlled by one pedal, the simplest course is to link additional variable resistors, because individual devices vary widely in gain for a given V_c value. The calibration process will then allow reasonable tracking.

Stop control

The use of 4016 devices, as previously mentioned, allows switching of stops and couplers via unscreened leads from the console stop-tabs. Each 4016 control input should have a pull-down resistor, to ground, of 150kΩ. The form of stop-tab described is an adaptation of the widely used pipe-organ pallet-magnet, shown in Fig. 55, which requires about

0.11 A at 12V. Although inefficient magnetically, it is designed for silent operation, and the shape allows parts to be attached, in particular a finger tab and light wire contacts to close in the operated position. Also, the fixed buffer may be replaced by one mounted on a stiff spring which can be depressed by extra finger pressure to operate further contacts for second-touch cancelling, s.t.c. This is only necessary for speaking stops, not couplers, and all s.t.c. contacts for one department are in parallel.

In the circuit of Fig. 56 the switching action causes the tab to remain up or down as moved by the finger. The voltage at T with the tab on is 9 to 10V, the negative rail of the tab supply being nominally 4.7V positive to ground. For s.t.c. purposes, the cancel signal is differentiated, and t.c. only interrupts the C line for about 40 ms. The t.c. circuit is repeated for the other departments, and

the general-cancel piston activates all three.

The main purpose of magnetically operated or motorised tabs is to permit them to be controlled in combination by pistons (buttons) arranged for thumb or foot operation, and the automatic movement of the tabs keeps the player informed. The circuit in Fig. 56 permits the same T line to be used for both stop and tab control because a momentary connection of T to + 12V will operate the tab, and a momentary ground will release it.

The 4036 memory can be used in a simple parallel configuration to store and execute combinations, and a small battery allows them to be retained with the mains power off. The 4036 stores four words of 8-bits, and this description assumes that 16-bits (stops, couplers, etc.) are used per department, and that it is required to store eight combinations or words. Four are selectable by departmental pistons, c.p., and four by general pistons, g.p., which control all departments at once, using 12 packages in all. Couplers are included because of their tonal importance in the present design, although this is not universal practice.

Each combination is stored, or changed, by capture. It is set up manually on the tabs, and then allocated to a particular c.p. or g.p. by holding in that piston while simultaneously operating a separate capture button. This results in a write operation at the corresponding memory address. Fig. 57 shows one 4036 package, and the interconnection of four to produce 16 output lines. These are connected to the T lines of the department tabs, and two select lines, H1-4 (packages 11, 21) and H5-8 (packages 12, 22) which are in effect address lines together with the common address lines A and B. As Fig. 58 shows, the addresses are allocated to the c.p., B high, and g.p., B low, in two groups of four.

The memory control is shown in Fig. 59. With no piston operated, lines J, high, W and Y, low, are inactive and the M outputs take the potential of their T lines. Operation of a piston generates a memory address/select, and simultaneously a low at J via the two left-hand 4093 sections, which cause the address contents to be read onto the T lines, and drive them high or low to set the tabs accordingly. Holding in a capture button sets Y high, and prevents a subsequent J low from causing a read-out. Instead, operation of a piston then switches all four 4093 sections, and the high or low states of the T lines are written into the address from the inputs. The c.r. couplings and trigger action delay the write pulse until the address lines are stable, and ensure that it terminates before the piston is released. The 4093 devices are supplied from the battery so that the memory outputs float, J high, with power off, and the T lines do not draw current. Battery drain

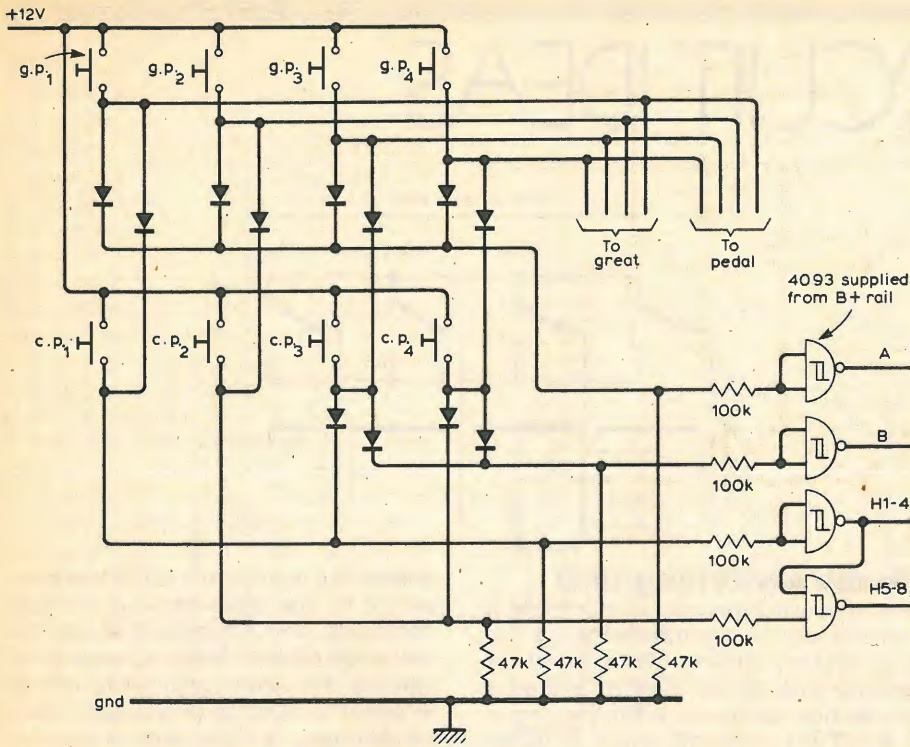


Fig. 58. Addressing for swell department. The other departments are similar, with common connections to the general pistons.

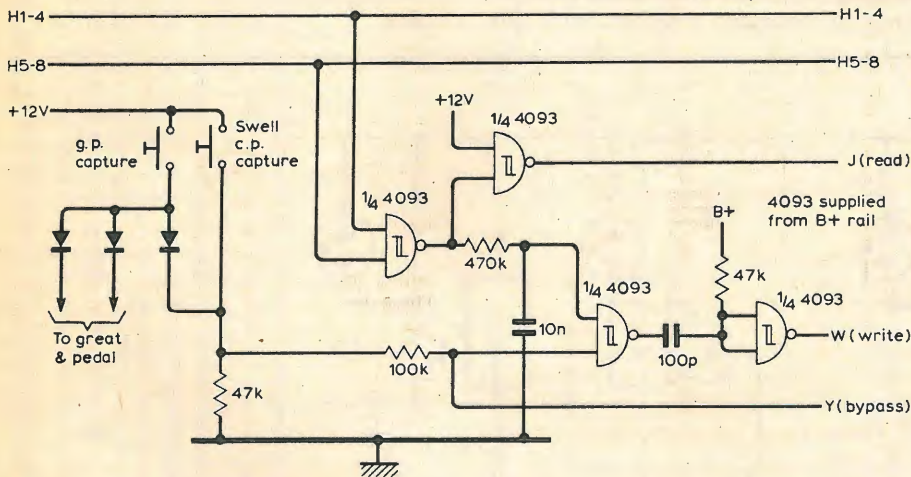


Fig. 59. Memory control for the swell department.

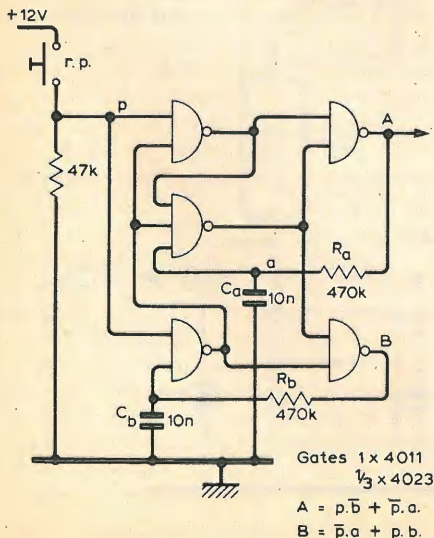


Fig. 60. Toggle circuit. Components Ra and Ca are omitted from Fig. 60.

Fig. 60. Toggle circuit.

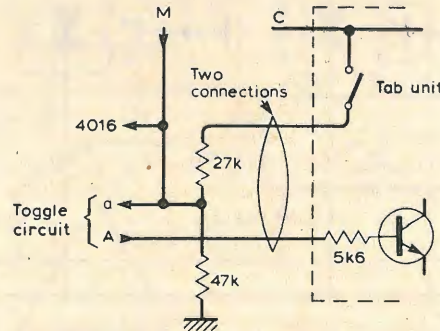


Fig. 61. Tab control by the toggle circuit. Components Ra and Ca are omitted from Fig. 60.

is only nanoamps, and the smallest cell size is suitable.

The two or three most used couplers, such as great-to-pedal, are often found also from reversible pistons, r.p., push-on, push-off. This function requires some form of toggle or divide-by-two circuit. For example, a flip-flop preceded by a trigger circuit to produce a clean signal from the piston contacts. The circuit in Fig. 60, however, is more economical. A counter cell must have four distinct states, which requires two memories, A and B, and if p is the signal to be counted, the basic logic is,

$$A = p.B + p.A \quad B = \bar{p}.A + p.B$$

In package counters, switching races are controlled by additional gates. In Fig. 60, which is a manipulation of the basic logic to minimise the package count, they are avoided by the RC delays. These delays also permit the latching action to be slowed sufficiently to immunise the toggle from contact bounce and interference. This allows direct connection to the r.p.

To use this circuit with a tab, the feedback path from A to a is arranged via the tab itself, which provides a delay, as shown in Fig. 61, and two connections are brought back from the tab unit. Manual tab operation, or a pulse from the memory, leaves the toggle appropriately set so that a subsequent r.p. actuation produces the expected result. □

Acknowledgement

The advice on tonal variations given by Mr E. L. Jones of Hiykon Ltd is gratefully acknowledged, and the p.r.b.s configuration of Fig. 50 is also due to him.

A 30 min cassette recording of the prototype is available for £2.00 c.w.o. A set of 15 special printed circuit boards (12 x E01, 3 x E02) is also available for £117.32 c.w.o. Both items are post free in the UK, and delivery is about 2 weeks and 4 weeks respectively.


Purchasers of these will also receive supplementary component and procurement details. Hiykon Ltd, Woodside Croft, Ladybridge Lane, Heaton, Bolton, BL1 5ED.

CIRCUIT IDEAS

Thyristor touch tuning

The use of thyristors as the switching elements in a touch-tune unit simplifies the circuit and gives improved reliability over conventional designs. Initially the s.c.r. in channel 1 is on due to the 10nF capacitor, and tuning potentiometer R_1 is activated. If the s.c.r. in channel 2 is triggered, 30V is dropped across R_2 and R_1 momentarily has a voltage drop of $VC_1C_2 + VR_2$, i.e. 60V. As the cathode of SCR₁ is now more positive than the anode, the holding current is zero and the thyristor is therefore turned off, which leaves R_2 as the active potentiometer. Triggering any other s.c.r. will repeat this process. The circuit includes neon channel indicators which were chosen for their low current consumption. The high voltage supply was obtained by tripling the 30V supply. Alternatively, i.e.d. indicators can be used as shown.


R. P. Beales
Kempsey
Worcester

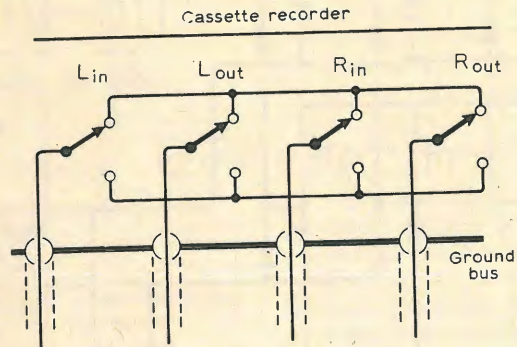

Audio switching unit

A simple switching unit suitable for hi-fi systems can be constructed using the bus system shown. Each input or output, such as the cassette recorder connections in the diagram, requires a 1-pole 2-way centre off switch. Switches for the inputs and outputs of each piece of equipment should be grouped together and labelled. Any switches in the up position are connected together, similarly, switches in the down position are also connected together. With this

system any input or output can be connected to any other input or output. Obviously, some connections should not be attempted, such as tape-in to tape-out. For some applications it may be useful to label the two switch buses left and right, or input and output. It is also useful to supplement the buses with jack sockets so that temporary leads can be patched into the unit.
F. A. B. Smith
Washington D.C.
U.S.A.

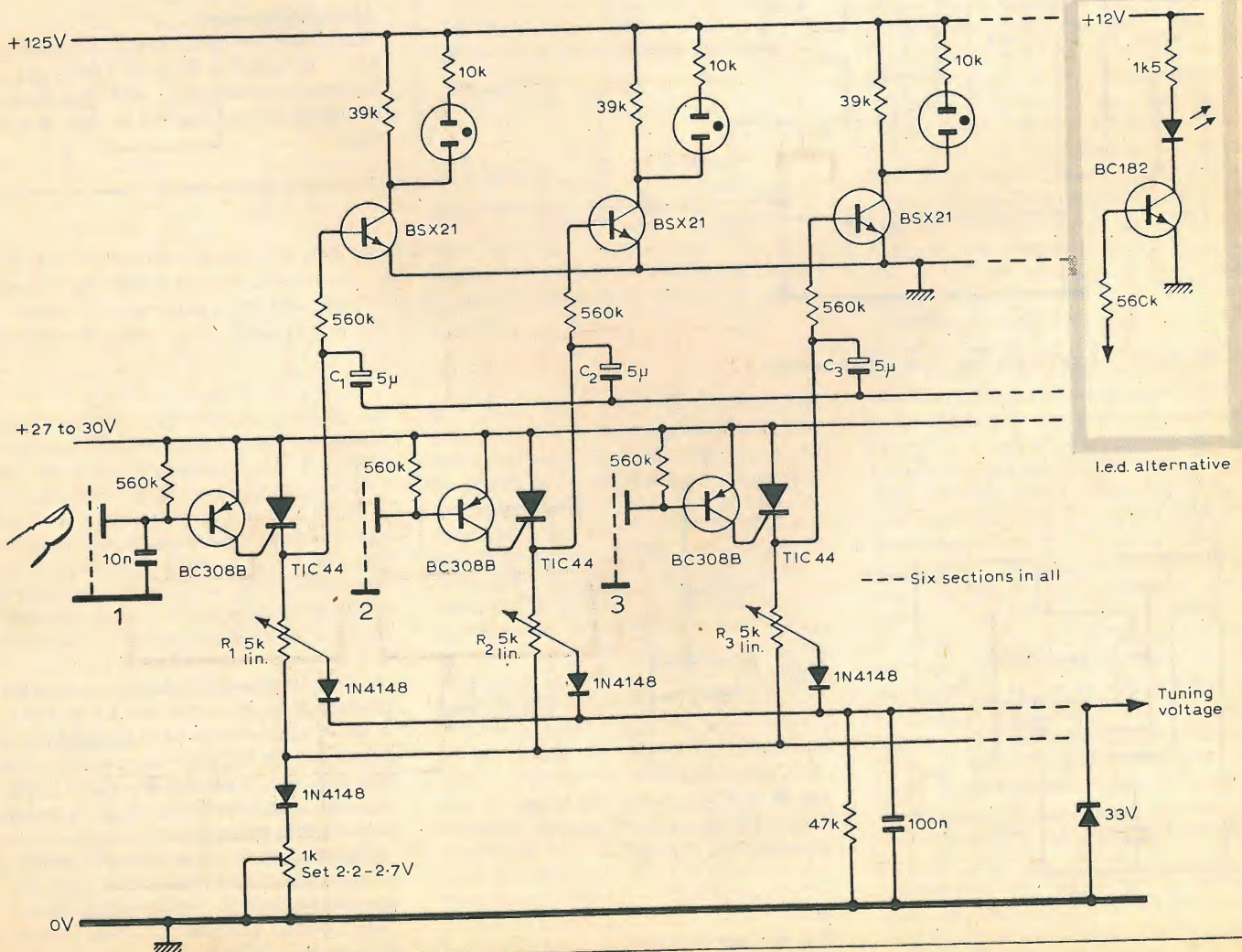


Continuous d-to-a converter

In Motorola's data library a d-to-a converter is shown where an up-down counter output is converted to an analogue current by an MC1408L, and compared with the input signal. A comparator in a MC1407L switches a clock from up to down-counting and vice-versa, to equalize the input signal and analogue current. The conversion is

low. The counter output is also used to switch off the counter just before it runs off-scale. The design now gives a satisfactory monitor output up to around 40kHz with a system delay of 1µs irrespective of input amplitude and frequency.

J. E. Dahl
 J. D. Whitehead
 University of Queensland
 Australia

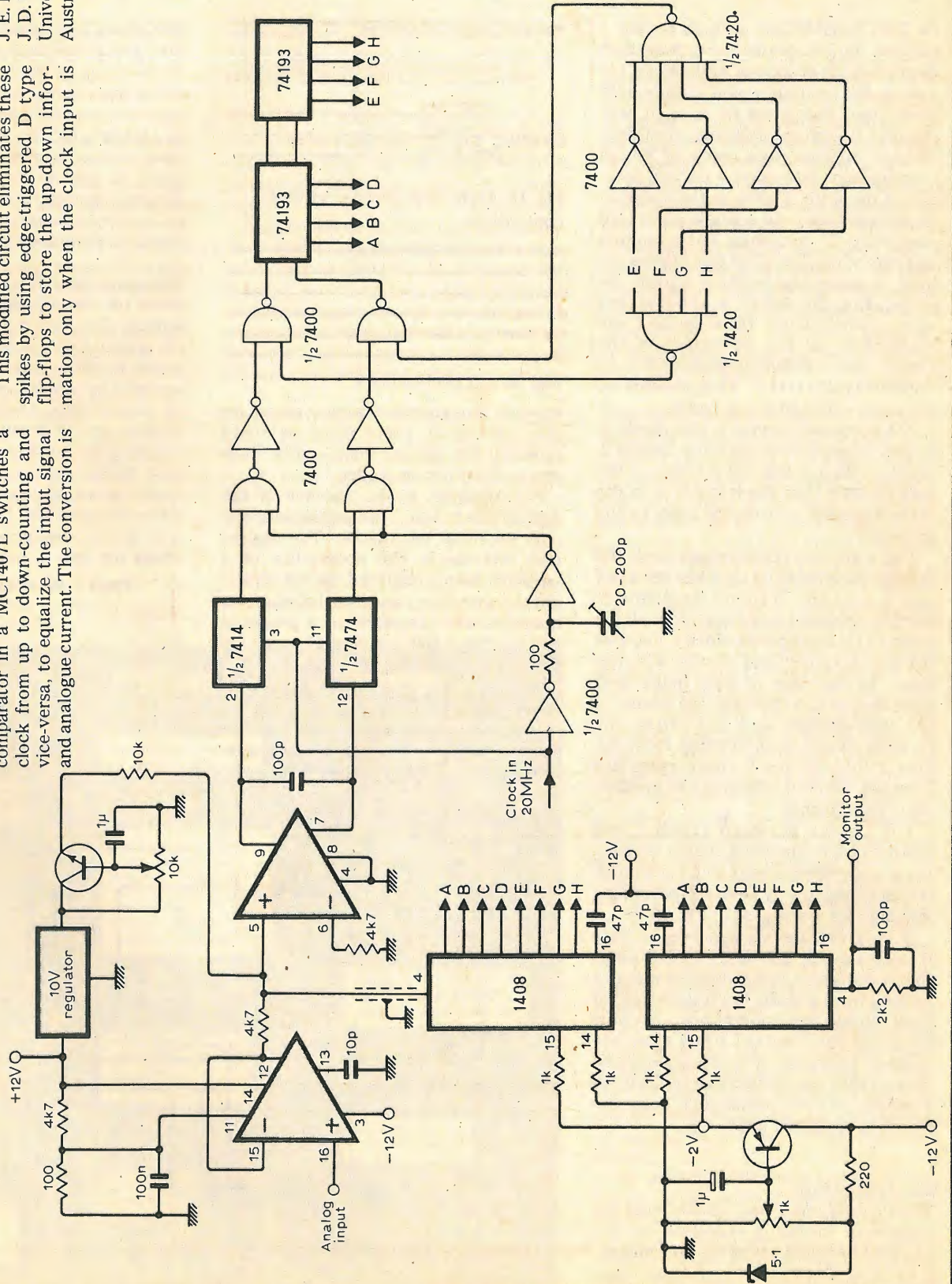This modified circuit eliminates these spikes by using edge-triggered D type flip-flops to store the up-down information only when the clock input is



Computer buses — 2

Read/write control and contention for possession of the bus

by Ian H. Witten, M.A., M.Sc., Ph.D., M.I.E.E.

Department of Electrical Engineering Science, University of Essex.

IN THE EXAMPLES quoted, device 1 has sent data to device 2. Suppose that device 2 is the processor and device 1 is a store. Since the store will usually hold more than one word of data, it will respond to several different combinations of address lines, each of which combinations addresses a certain location of the store. Typically, there will be 16 address lines, and a single store unit may have 2^{12} locations, each holding one byte of data. So 12 of the 16 lines are used to select the location within the store, and the other 4 address the storage device itself. Thus, device 2 will respond to all the addresses in the range, say $\langle 0010000000000000 \rangle$ to $\langle 0010111111111111 \rangle$. This presents no problems with address decoding.

The processor, device 1, also needs to be able to read from the store, device 2. In this case, it is still the initiator of the data transfer, but the transfer is in the other direction — from the store to the processor.

There are two relationships here: the master/slave relation between devices 1 and 2, and the receiver/transmitter relation. Device 1 is the master in all the cases so far considered, since it initiates the bus activity; and device 2 is the slave. In the case of data being sent from device 1 to device 2, the former is the transmitter and the latter the receiver, whereas in reading from device 2 into device 1 these roles are reversed, without affecting the master/slave relationship.

The choice between reading and writing is accomplished simply by adding a read/write control line to the bus, which is held low by device 1 for reading and high for writing, as in Fig. 19.

If only one device can ever initiate transfers along the bus — in the sense that a processor can initiate reading or writing from a store, but a store cannot itself initiate these operations — we now have all the control lines that are needed. However, if there are several devices that can initiate bus activity, for example, several processors, some interesting problems arise.

Bus contention

At any time, only one device must be capable of initiating transfers on the bus. This device is called the bus master. If several devices are potential bus

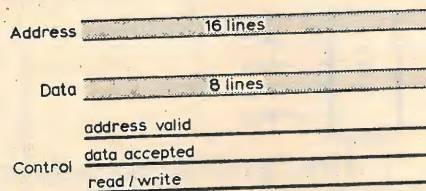


Fig. 19. Asynchronous bus, without contention.

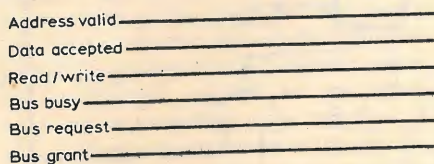


Fig. 20. Bus control lines.

masters (imagine several processors on the same bus), there must be some protocol for passing mastership from one to the other as needed.

For example, in the absence of the dashed line in Fig. 1, the processor is the only potential bus master. The dashed line introduces the possibility of a transfer being initiated by an input/output interface, and the interface in question will therefore be a potential bus master. Table 1 summarizes which devices are potential masters.

The ideal bus structure is one where every potential master uses the same protocol to communicate with other devices, and none is in overall charge. This increases the reliability of the sys-

tem, since any device can fail without disrupting bus activity that does not involve it. If, on the other hand, just one of the devices had responsibility for the organisation of the bus, its failure could be catastrophic. We will stray from this ideal in the following two sections in order to see how existing computer systems operate their buses, but return to it later to examine more unconventional "distributed" bus protocols.


Bus controller. "Bus contention" occurs when two devices both desire bus mastership. The best cure for contention is prevention! A "bus busy" control line is added to show when the bus is active, asserted by the bus master throughout its mastership. There is normally no mechanism to prevent a device from hogging the bus for ever: it is assumed that device designers understand the importance of leaving the bus free whenever possible.

A device requests mastership only when the bus is not busy. Suppose it

Table 1. Potential bus masters

	Potential bus master	
Processor	yes	
Store	no	
i/o interface	Slow device (e.g. teletype)	no
	Fast device (e.g. disk)	yes

Fig. 21. Daisy-chaining of the "bus grant" line.

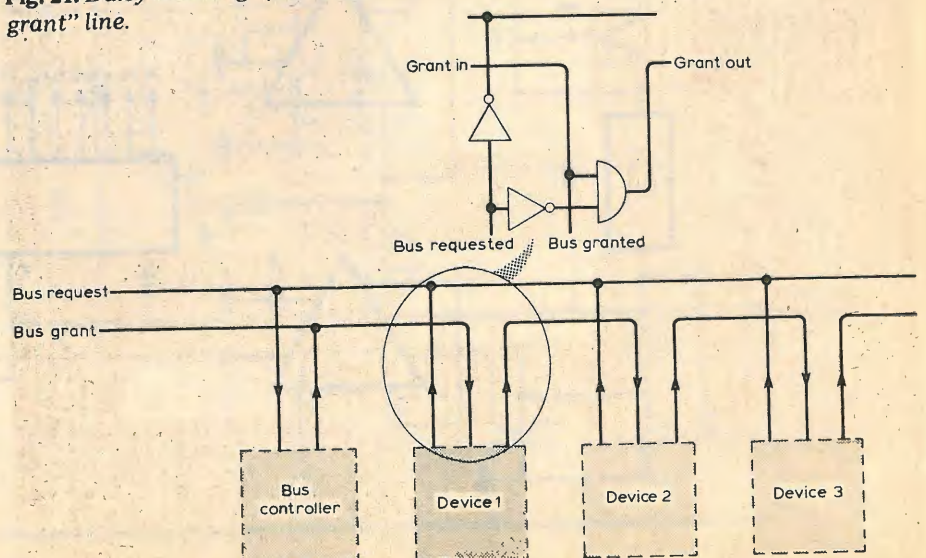

does so by asserting "bus busy". This by itself may seem an adequate protocol for transferring mastership but, unfortunately, it is not. If two devices simultaneously assert "bus busy", they will each think they have the bus to themselves, resulting in collisions. Hence there must be a protocol for requesting bus mastership, and having it granted by a central authority — the bus controller. A "bus request" and a "bus grant" line are introduced for this purpose. The controller monitors "bus busy" and "bus request", and issues grants when appropriate. Fig. 20 shows the control lines so far.

However, the "bus grant" line as described does not completely solve the problem. Each device requesting the bus will see the grant line being asserted, and each will think that it is now bus master. One way out is to "daisy-chain" the "bus grant" line through the devices, as in Fig. 21. A device, seeing "bus grant", will only pass the signal on to the next device if it itself does not want the bus. Hence a device has priority over all other devices which are further away from the controller than it, when contention occurs.

Fig. 21 also shows the circuitry which controls the daisy-chaining. When a device wants mastership, it takes the "bus requested" signal high, signalling a request on the "bus request" line. Note that this line cannot be tri-state, since there is no way of preventing simultaneous bus requests, and more than one tri-state gate cannot actively drive the same line at the same time. It is the only bus line we have introduced that must be wired-AND, and an open-collector gate is shown driving at low to signal a request. If the "grant in" line is

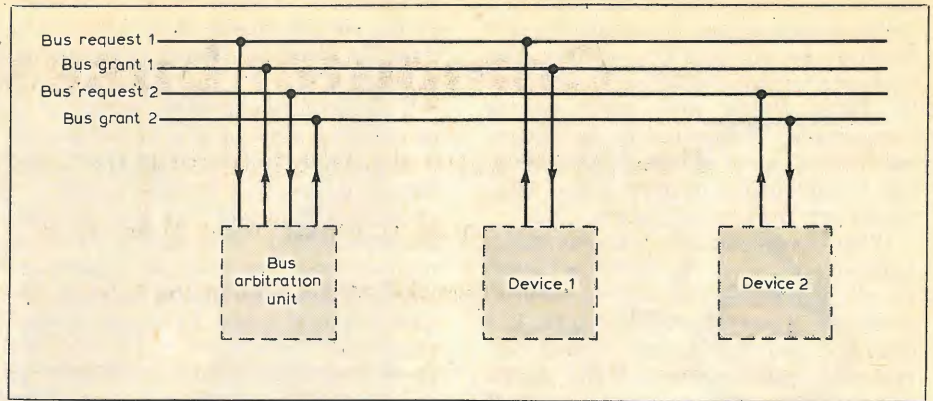


Fig. 23. Bus control with an arbitration unit.

asserted, it is routed through the "grant out" line provided the bus has not been requested. If it has, the grant chain is broken and the device achieves mastership.

A summary of the protocol necessary for a device to gain and relinquish bus mastership is given in Fig. 22, in which the bus is used for a single "send" operation during mastership. Although the protocol is quite complicated, we have seen how each step is necessary if the bus is to perform its job correctly.

Bus arbitration. An alternative to daisy-chaining the "bus grant" signal is to have separate "bus request" and "bus grant" lines for each device, as shown in Fig. 23. When contention occurs, the bus controller can select one of the

contending devices and give it alone mastership by asserting its grant line. In this case, the controller is in a position to impose a priority structure on devices using programmed priority levels, and is often called a bus arbitration unit.


The disadvantage of bus arbitration is that the number of lines increases by two for each device added. However, the delays inevitably associated with a long daisy-chain are avoided. In practice a compromise solution is sometimes adopted, with say 8 priority levels, 8 "bus request" and "bus grant" lines, and several devices daisy-chained within each priority level.

Distributed buses. In general, if several identical autonomous devices are connected to a single bus, in a system with no protocol, bus controller or arbitration unit, there is no way of guaranteeing that two or more of them do not try to use it at the same time. However, if such "collisions" can be detected, it is possible to devise protocols for re-transmission which ensure that the information gets through eventually.

Although it should be possible to detect collisions by looking for the neither-high-nor-low logic level that occurs when two tri-state gates, both enabled, are fighting for the bus, in practice distributed buses usually use serial transmission. So far, the bus has been considered as a parallel collection of wires, where the address, data and control information is presented in parallel, one wire for each bit of the information. However, if the bus wires are expensive, it is more attractive to use one line only for the information, and transmit the bits one after another on this one wire. This is the case, for example, when radio is used as the bus medium: to transmit 32 bits in parallel requires 32 different radio frequencies to be reserved for the bus, and radio bandwidth is a scarce resource. (The cost of duplicating the radio receiver and transmitter 32 times for each device connected to the bus is not negligible either!)

To detect collisions using serial transmission, some error-checking information is sent with the data. For example, one might send each transmission twice, and the receiver could check that they were the same. It is

Fig. 22. Protocol for gaining bus mastership and sending data.

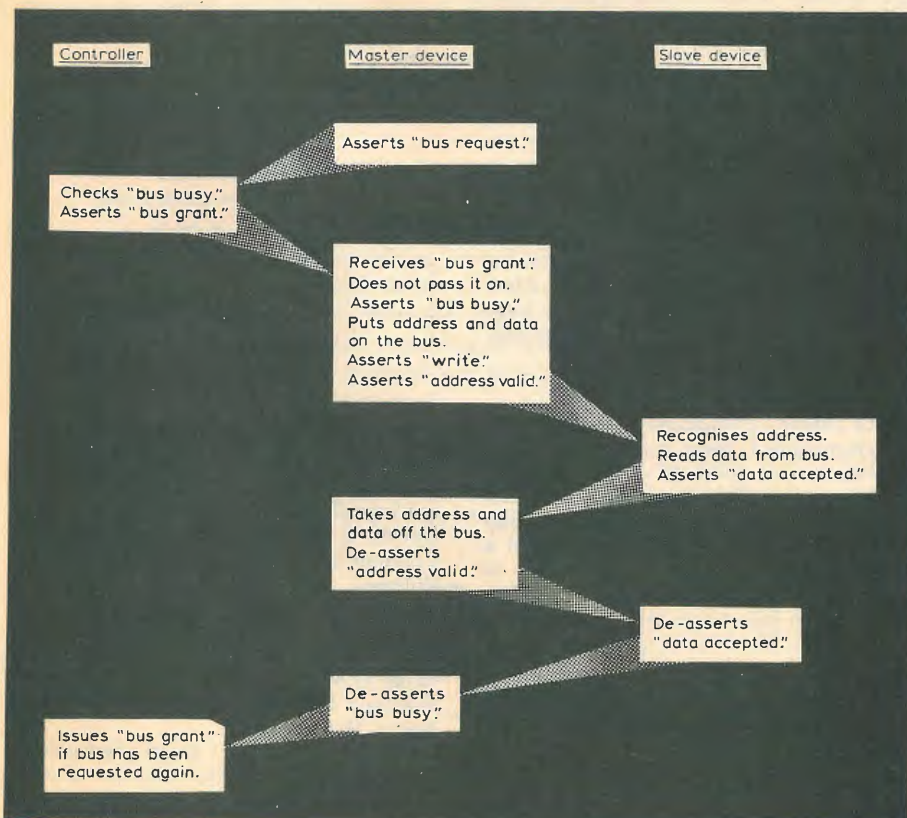

extremely unlikely that in the event of a collision when two transmitters are driving the bus simultaneously, the duplicate versions will check correctly. In fact, there are much more economical collision-detection mechanisms than double transmission, but we need not be concerned with them here: the principle is enough.

When a receiver sees a transmission addressed to it, it sends a "data accepted" or "acknowledgement" message. However, if a collision has occurred and the transmission is corrupted, it remains silent. If the sender has not received acknowledgement of his transmission after a reasonable time, he should assume that it has collided, and re-transmit it. However, if two senders collide on a transmission, it is important that they should not time out after exactly the same interval and collide when sending again, and so on



The author

Ian H. Witten graduated with a B.A. in mathematics from the University of Cambridge, England, an M.Sc. in computing science from the University of Calgary, Canada, and a Ph.D. in electrical engineering science from the University of Essex, England. He was a Commonwealth Scholar at Calgary during 1969-1970 and has been a lecturer in the Department of Electrical Engineering Science at Essex University since then.

His research interests span the field of man-machine systems; he has specialized in the fundamental problems of machine learning, and in computational phonetics — the science of speech synthesis by computer. He is the author and co-author of about 35 technical publications, including several on speech synthesis.

During a sabbatical year in 1977, he worked at the University of Canterbury, New Zealand, on learning machines, at the University of Calgary on speech synthesis by computer, and at Bell-Northern Research, Montreal, on speech analysis.

Dr. Witten is on the Editorial Board of the International Journal of Man-Machine Studies, and recently, as a consultant to the Open University, participated in the development of a new course entitled "The Digital Computer."

ad infinitum! This situation is avoided by the simple expedient of making the time-out interval random (within suitable bounds).

If an acknowledgement is corrupted by colliding with another transmission, it will simply fail to be received. The device which was expecting the acknowledgement will then time-out and transmit again. This means that the receiver will see the same message twice, and care should be taken to ensure that this does not have any harmful effects. For example, each message could be numbered, so that the receiver can simply discard the second message after acknowledging it.

The scheme described is used in the Aloha network of computers in the Hawaiian islands. Note that no attempt is made to detect if the bus is busy before sending: this means that collisions can be expected fairly often and much of the bus's bandwidth will be used for re-transmissions. (One way of calculating just how much — under very simple assumptions — is given as an Appendix.) A more sophisticated mechanism is for the sender to listen to the bus before transmitting, to see if it will cause a collision by interfering with another transmission. This is analogous to the "bus busy" information described earlier. While this can be expected to reduce substantially the frequency of collisions, it will not eliminate them altogether since two devices may still decide to send at exactly the same time. A further refinement is for the sender to monitor its transmission itself and check that the bits it "hears" are the same as those it sends. If there is a discrepancy, this indicates a collision and it should cease transmitting at once. However, this is not feasible in the case of radio, since locally transmitted signals tend to swamp the local receiver and so collisions are not detected locally.

Appendix

Suppose d devices are attached to a distributed bus, each of which sends m messages (excluding re-transmissions) per second. All messages take T seconds to transmit. A synchronous or interlocked bus could handle the traffic provided the total time for dm messages was less than 1 second, i.e. provided $dmT < 1$.

Now let the re-transmission rate be r re-transmissions/sec. In 100 seconds, there will be $100d(m+r)$ messages sent (including re-transmissions). These will occupy a total of $100d(m+r)T$ seconds which must, of course, be less than 100, and during the remaining $100 - 100d(m+r)T$ seconds the bus will be unused. Hence the probability of a message requiring re-transmission is $100d(m+r)T/100$. Now since there are r re-transmission for m real messages, the re-transmission rate can also be expressed as r/m .

Hence $r/m = 100d(m+r)T/100$,
from which

$$r = \frac{dm^2T}{1-dmT}$$

We observed above that $100d(m+r)T$ must be less than 100 seconds, since the bus cannot be used more than full-time. Hence

$$d \left(m + \frac{dm^2T}{1-dmT} \right) < 1,$$

$$\text{or } \frac{dmT}{1-dmT} < 1,$$

$$dmT < 1/2$$

This shows that the maximum number of messages that can be originated under the distributed bus organization is only half that which the bus could handle if control were centralized.

Actually, these calculations are rather simplified. In real life, even a bus with centralized control cannot necessarily handle the traffic if dmT is close to 1, because this is the average load — the peak load will be higher. If messages are generated stochastically, then the performance of a centralized bus will depend on whether messages can be queued by the devices that originate them. For example, suppose a device wants to send a message, but the (centralized) bus is busy. It must wait for the bus to become free. If, while it is waiting, another message appears which must be sent as well, the device needs to be able to queue the two messages. If it can't, then a message will be lost and so the bus must be overloaded. If it can, how many message can be queued? Two? Two hundred? This is one of the parameters that will affect the performance of a bus with centralized control. In the most optimistic case, where an unlimited number of messages can be queued by each device if necessary, the centralized bus will be able to operate provided $dmT < 1$. Statistical calculations show that the Aloha distributed bus becomes saturated if dmT grows as big as $1/2e$ (Abramson, 1970). Thus the distributed bus can handle about 20% of the traffic that a centralized bus can.

Further reading

- Abramson, N. (1970) "The ALOHA system — another alternative for computer communications." *AFIPS Conference Proceedings* 37: 281-285; November.
- Davies, D. W. and Barber, D. L. A. (1973) *Communication networks for computers*. Wiley.
- Metcalfe, R. M. and Boggs, D. R. (1976) "Ethernet: distributed packet switching for local computer networks." *Communications of the ACM* 19: 395-404; July.
- Peatman, J. B. (1977) *Microcomputer-based design*. McGraw Hill.
- Williams, G. E. (1977) *Digital technology: principles and practices*. Chicago: Science Research Associates. □



AVO. You'll never meet a better meter

Nobody makes a more impressive range of analogue meters for the professional than Avo.

And within this impressive range is a series of smaller meters which can be picked up with a thumb and forefinger and slipped into a pocket for those applications where simple portability is a crucial factor.

These are the Models 71 and 73 Multimeters, the electronic EM272, the electrician's "Multiminor" MM5, the 300 and 1200 Clampmeters and the LM4 Lightmeter.

These instruments may be smaller than the rest, but they're equally big in quality, accuracy and reliability.

Otherwise we'd never call them Avo.

Get in touch today and we'll let you have the full facts.



AVO LIMITED
Archcliffe Road, Dover, Kent, CT17 9EN.
Telephone: 0304 202620 Telex: 96283



Thorn Measurement & Components Division

Antennas and propagation — 2

Further developments in antenna technology

by R. Ashmore

Part one gave extracts based on some of the papers presented at the Antennas and Propagation Conference, held at the Institution of Electrical Engineers in London recently. Topics covered included a systems engineering approach to antenna design, satellite communications and the amateur radio service. This second part continues where Part one left off, with the discussion on amateur antennas, based on the paper⁴ by Les Moxon, G6XN.

A RECENT analysis showed that at least 80% of the h.f. stations contacted used relatively small antennas on rotary beams. These had closely-spaced half-wave elements providing about 6dB gain (relative to a dipole). This kind of antenna, on the popular DX bands, gives considerable directivity because of the narrow bandwidths. Even smaller beams are needed, but methods of size reduction so far employed have used lossy devices such as loading coils or resonant feed lines. Les Moxon therefore gives consideration to design optimization on the smaller antennas with a view to achieving increased efficiency.

Large beam antennas commonly used in commercial installations operate on an additive principle in that the gain and the volume of space occupied by the array are proportional to the number of elements. In contrast, the smaller amateur beams use a subtractive process where energy is concentrated in the wanted direction by arranging that cancellation is less complete in that direction than in the unwanted directions.

Mr Moxon gives an example of a beam antenna comprising two parallel, closed-spaced dipoles fed in antiphase to give a figure-of-eight directional pattern. This pattern is readily converted into a cardioid by introducing a phase shift corresponding to the spacing. Provided all the available power is radiated, the gain, 4.2dB for both of the above cases, will be independent of size. The practical realization of obtaining higher gains using more than two elements is extremely difficult because of the low radiation resistances, narrow bandwidths and close tolerances inherent in the subtractive method of beam formation, but the two-element design above allows

considerable reduction in size without loss of effective gain.

The useful bandwidth of the smallest beam tried was found to be less than 100kHz but the required coverage of 350kHz was achieved by separately feeding each element through appropriate networks located at the transmitter.

In developing the small antenna it was found that to tune shortened elements to resonance without introducing losses, it was necessary to use as much capacitive loading as possible. The resulting concentrations of metal at the ends of the elements produced very severe capacitance overcoupling of the elements, effectively preventing the beam from operating. This difficulty was overcome by neutralizing the excess coupling using two additional wires to provide antiphase capacitance coupling between the ends of the elements.

Restricted space often goes hand-in-hand with height limitations, so it may not be enough just to reduce the size of the antenna. Where ranges are short the need can usually be met by vertical polarization for ground-wave communication or horizontal polarization for high-angle, sky-wave working. However, where longer ranges are required the use of steep ground slopes, if available, is the simplest solution, otherwise vertical polarization may provide the

only answer. In the latter case, cancellation of the direct wave by the ground-reflected wave is incomplete so that a modest DX communication capability, almost independent of height, can be achieved.

The paper then discusses the use of beam antennas for multiband DX operation. Beam antennas for amateur DX communications are normally required to cover bands about 3% in width centred near 14, 21 and 28MHz. To achieve this, beam antennas used by amateurs have traps to effectively shorten the elements at the higher frequencies. This, says Mr Moxon, is a wasteful process because the half-wave element for 14MHz can be used as two half-waves in phase at 28MHz to obtain 2dB of extra gain by the additive process.

The traps, which are liable to deteriorate, also add losses, restrict bandwidth and increase top weight. Alternatives include resonant feeders and tuning and matching networks located in the centre of the elements. However, the author of the paper recently adapted a linear resonator, as shown in Fig. 2 (a), to provide operation with full aperture at the higher frequencies, without significant effect on operation at the lowest frequency. The inductance L of the conductor AB is tuned by C to act as an insulator at 28MHz. For 21MHz the capacitor is increased to achieve resonance with the inductance of the outer portions of the dipole. (Further analysis is given in Ref. 4).

The capacitance may be switched, or resonance may be achieved simultaneously at 21 and 28MHz by providing two capacitors as shown in Fig. 2 (b). This works on the principle that higher frequency resonances have little effect on the lower frequencies, while the high value of k (k being the coupling factor between the current paths and X_L/X_C) brings the parallel and series resonances so close together that the 21MHz path via C_1 is inductive at 28MHz. The main effect of the extra capacitances in Fig. 2 (b) is that the effective value of L is modified. The two capacitors, C_2 and C_3 , are added to increase the shunt inductance of 28MHz (having little effect at 21MHz) to avoid narrowing of the bandwidth.

Mr Moxon points out that this type of resonator may also be used to tune a

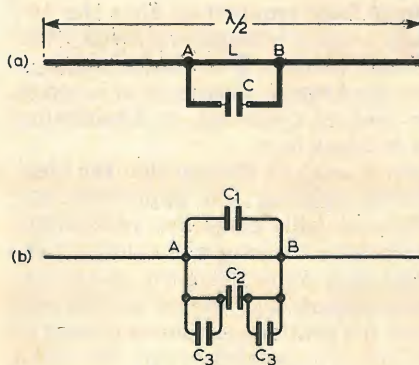


Fig. 2. (a) A linear resonator for a $\lambda/2$ dipole. This will enable simultaneous operation at the design frequency and also at a higher frequency. (b) A linear resonator arrangement showing additional capacitors for three-frequency operation.

conductor to or away from any specific resonant frequency, or, for example, to allow masts or rigging to be used as antennas at a small number of discrete frequencies. It may also be used to overcome nulls in the polar diagram of an antenna caused by the near presence of resonant metal structures.

Broadcasting

The Independent Broadcasting Authority (IBA) expect that by completion of the u.h.f. transmitter network they will be operating about 650 transmitters in Bands IV and V. This means that when the fourth channel comes into operation, the total number of transmitters will be about 2600 within the 44 channels of the u.h.f. band. While careful planning avoids serious interferences arising within the appropriate service areas, broadcasters who need to receive signals outside these areas, for rebroadcast, find that irregular propagation can cause them considerable interference problems. Consider for example the u.h.f. link across the English Channel from Stockland Hill to Alderney, part of the colour-tv feed to the Channel Islands. This is an over-the-horizon sea path of 135km length and, characteristically, the received signal is very variable in strength with a range of about 60dB and generally very weak. For this reason, the signal is very susceptible to co-channel interference (c.c.i.) from several sources both within and outside the UK. Crystal Palace in London, Wrekin in Shropshire and Kippure in Ireland (the latter being at an angle of only 7° off the wanted signal) are particularly powerful sources of c.c.i. at the receiving end of this link.

To obtain a broadcast quality signal the reception pattern of an antenna needs on occasions to have null depths of the order of 45dB in the directions of interfering sources. Since this was not possible with conventional arrays, the IBA decided to investigate the properties of adaptive arrays. Details of this investigation are given in a paper⁵ by M. D. Windram from the Authority's Winchester establishment.

The paper lists the main advantages of the adaptive array. When operating the adaptive array automatically adjusts the antenna pattern to give minimum interference, and it will handle these interferences whether they are from single or multiple sources. The antenna can also track the changing apparent direction of interference resulting from propagation effects, and because of its adaptability does not present a severe mounting and tolerance problem, as does a fixed array.

After considerable theoretical study and investigations into the behaviour of a simple four-element adaptive array, the IBA built a prototype half-size (eight element) array. The results of tests on this array confirmed the theory and an operational antenna was instal-

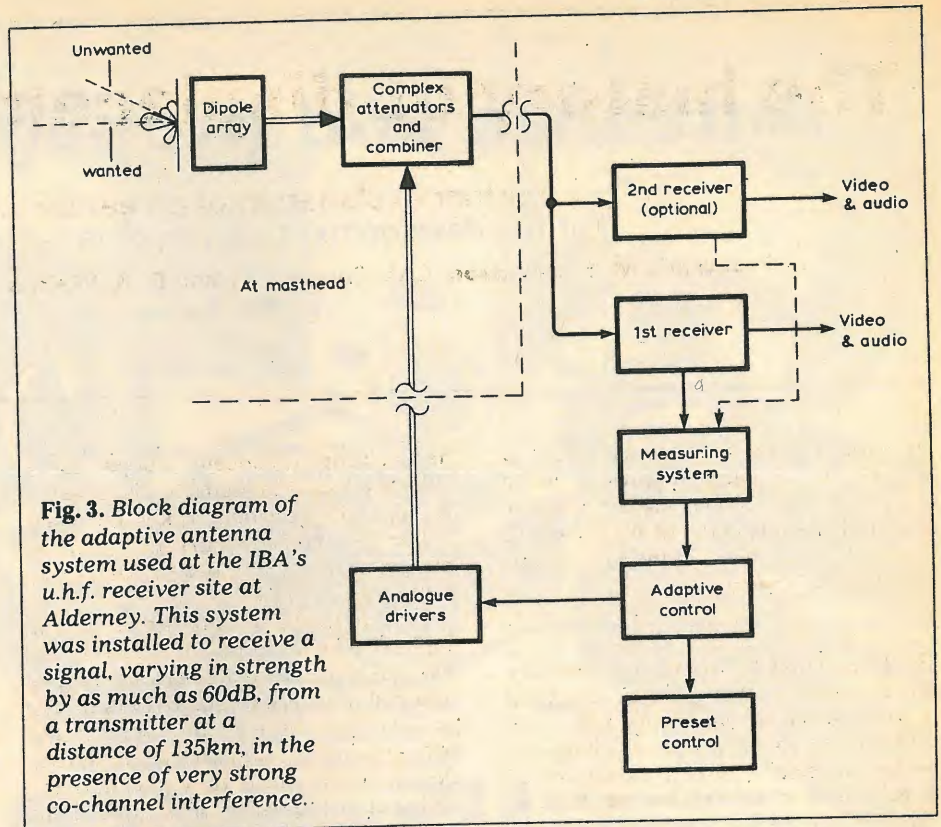


Fig. 3. Block diagram of the adaptive antenna system used at the IBA's u.h.f. receiver site at Alderney. This system was installed to receive a signal, varying in strength by as much as 60dB, from a transmitter at a distance of 135km, in the presence of very strong co-channel interference.

led at Alderney in March 1977. The final operational antenna system used at Alderney is shown in Fig. 3. This is a 16×4 dipole array constructed as a 2×2 array of 8×2 dipoles.

A similar system, having a linear array of 16 elements, is described in the IEE paper. The output of each element is connected to a network which effectively controls the amplitude and phase of that output. These output signals are then combined to create a voltage-controlled antenna, the pattern of which is a function of the control voltages. This combined output is fed to the system's receiver or receivers which provide the video and audio outputs and also the signals required for the system's measuring circuitry. Up to four receivers may be used within the control loop. The output from the measuring system is then passed to the adaptor control unit which provides the control logic required to alter the antenna control voltages to modify the antenna pattern. The control logic is converted into analogue form to drive the element combiner, so completing the feedback loop.

Initial analysis showed that the ideal element spacing was approximately $2/3\lambda$ since this combined reasonable directivity with easy null control. Cartesian ($X + jY$) type control of the antenna outputs was chosen as this provided the continuous control needed in the adaptive process, where for small changes in control, discontinuities could cause instability. Pure phase shifters have finite phase ranges and would therefore present serious problems.

For u.h.f. arrays of a size similar to that used at Alderney, it is necessary because of the expense, stability and

maintainability to use control algorithms which take measurements by making step changes in the control voltages to the array, thus stepping the antenna pattern and measuring the result in terms of c.c.i. on the output signal. The use of correlation methods or similar techniques are too expensive, although in principle capable of giving more accurate measurements of error. The theory of the adaptive array and the theoretical conclusions made by the IBA are described in much greater detail in Mr Windram's paper.

The operational system used at Alderney has helped the IBA to maintain a virtually continuous colour service without drop-out due to excessive co-channel interference. Based on results so far Mr Windram says, "we can now state with confidence that propagative mechanisms such as sea scatter and tropospheric scatter do not degrade the performance of the adaptive aerial, and in fact the adaptive aerial has considerable advantages over a fixed array in that it can track the changes in apparent c.c.i. direction caused by scattering processes".

The IBA is now investigating the design of a simpler four-element system for use on links having perhaps two or at the most three sources of interference requiring rejection of about 45 to 50dB. This system will use the same principles but the amount of equipment will be considerably reduced, and this combined with rapidly improving technology makes possible the use of a microprocessor to control the array. In conclusion Mr Windram says that it has been shown from theory and confirmed in practice that an adaptive array pre-

The history of displacement current

Further explanation of an earlier article

by I. Catt and M. F. Davidson (CAM Consultants) and D. S. Walton (Icthus Instruments Ltd)

As a result of correspondence following their article "Displacement current" in the December 1978 issue, the authors feel that further explanation of their views is required. They offer it in the form of this brief historical survey.

IN THE EARLY nineteenth century electromagnetic theory made advances, a cornerstone of the theory being the doctrine of conservation of charge q , which developed into the doctrine of continuity of electric current flow, $dq/dt = i$.

In the middle of that century Maxwell struggled with the paradox of the capacitor, where charge entered one plate and then flowed out of the other plate apparently without traversing the space between the plates (Fig. 1). It seemed that electric charge was being destroyed on the upper plate and being re-created when it reappeared on the lower plate. Maxwell "cut the Gordian knot" as Heaviside put it (Heaviside 1893) by postulating a new type of current, called "displacement current", as flowing across the gap BC in Fig. 1 so as to save the principle of continuity of electric current.

"Displacement current" was a result of his postulation of "electric displacement". Maxwell said that the total outward displacement across any closed surface is equal to the total charge inside the closed surface (Maxwell 1873).

It is not surprising that objections were raised. Notice, in Fig. 2, that if in any circuit there should be a break, BC, in the current path, we are bound by the principle of conservation of charge to say that the current i , that is the flow of charge, entering B from A accumulates as charge $\int idt$ at B, and the current reappearing at C "accumulates" as equal negative charge $-\int idt$. By definition, electric displacement outward from B equals the total charge trapped at B; $D = \int idt$ and $i = dD/dt$. It is not a coincidence that "displacement current" saves the idea of continuity of electric current; it does so by definition. With the postulation of displacement current, it would never in future be possible to devise an experiment which might refute the principle of continuity of electric current. Popper would therefore say that "displacement current" is

an unscientific concept (Popper 1963). Whenever charge seems to disappear at a point, displacement takes its place. Whenever electric current seems to disappear at a point, displacement current takes its place.

It is important that Maxwell and Heaviside believed that the current entering a capacitor plate became trapped and had nowhere to go. Writers on the subject must be glad that some route between B and C for real current did not declare itself, since they say that the brilliant postulation of displacement current led to the postulation by Maxwell of waves in space.

Meanwhile, even as Maxwell was contemplating the ethereal displacement current, practical electricians were inventing and building wired telegraph systems. The distortion of signals travelling long distances was bad, and was thought to be due to the fact that the capacitance of the telegraph wires had to be charged up through the resistance of the wires, resulting in an RC time constant which attenuated different frequencies dif-

ferently. As late as 1910 virtually all electricians (including Lord Kelvin) did not accept Oliver Heaviside's claim that a telegraph wire had distributed inductance as well as capacitance, and that if only this inductance were increased by the addition of periodic loading coils, distortion-free transmission over long distances could be achieved (Heaviside 1893).

It was important for Heaviside to encourage a sensible approach to the characteristic impedance of telegraph lines, because the practical pay-off in telegraphy and telephony would be immense. (This misunderstanding delayed the introduction of telephones for twenty years.) This practical pay-off would be best achieved by arguing that signals travelling down (between) telegraph lines were undistorted TEM and similar to the waves in space discovered by Hertz in 1887, twenty years before, and previously postulated by Maxwell as one implication of his proposed displacement current.

It was important for Heaviside not to criticise the theory he was trying to argue from, Maxwell's electromagnetic theory. So it would have been injudicious for Heaviside to question the concept of displacement current, and he never did.

The essence of the concept of a transverse electromagnetic wave, TEM, is that nothing — field, flux, or current — flows laterally across the surface of the wave front. The analogy is the Severn Bore, where we see a single step of water rushing up the River Severn. Everything ahead of the step is steady, and everything behind the step is steady. There is no lateral, sideways flow. In the electromagnetic case (Fig. 3), the idea of a lateral flow of current across the face of a TEM step is absurd, and would result in a longitudinal magnetic field; the step would "get ahead of itself". Further, since the step travels forward at the speed of light, $1/\sqrt{\mu\epsilon}$, any lateral flow would cause embarrassment by travelling even faster, in the same way that when you walk across inside a moving train by Pythagoras' Theorem you are travelling faster than the train.

Now although in the case of a capacitor, displacement current needed to be regarded as just like a real current, for instance causing a magnetic field; in

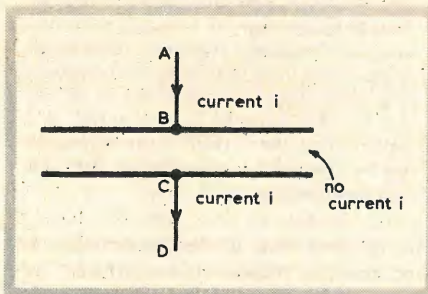


Fig. 1. Charge flowing into one plate of a capacitor, as current i , and flowing out of the other plate.

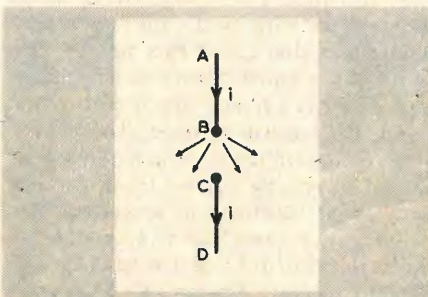


Fig. 2. Electrical circuit AD with a break in the current path at BC. Charges accumulate at B and C.

the case of the D flux at the front of a step of TEM ($E \times H$) energy current travelling down a telegraph line, the displacement clearly must not behave like a real current – for instance by creating a magnetic field which would reach out ahead of the wave front and ruin its TEM nature.

Maxwell and later Heaviside did not notice the discrepancy in the requirements of displacement current; that in a capacitor it must act like a real current but in a transmission line it must not; because neither of them knew that a capacitor is no more nor less than a transmission line (*Wireless World*, Dec. 1978, p. 51). This is even today known by very few scientists. Maxwell, along with today's text-book writers (e.g. Fewkes 1956, Bleaney 1957), believed that the displacement current dD/dt travelling across between the plates of a capacitor BC was uniformly distributed, and it is only very recently that it has been pointed out that the flow of current and field in a capacitor is identical with that in a transmission line; that the field moves out from the capacitor's leads as if they were links to one end of a transmission line. So the discrepancy could not become apparent.

A serious difficulty for displacement current arises when we realize that the two plates, BB', CC' in Fig. 4, are a transmission line. We know that the current i travelling down to B from A then flows out sideways from B along the capacitor plates, failed to declare itself to Maxwell, and everyone has followed his lead.

In a transmission line (Fig. 4), everyone agrees that the current i entering the line at B leaves B by flowing along the line BB'. No displacement current dD/dt between the lines is needed for us to retain the doctrine of conservation of charge and conservation of current. In fact, if this dD/dt were regarded as a current, far from saving the doctrine, it would destroy it, because now more current ($i + dD/dt$) would be leaving the first section of the plate BB' than was entering it. The last sentence is difficult to grasp; no matter, because it is easy to see, and sufficient to see, that if i enters B from A and i leaves B along BB', continuity of current is preserved without our having to postulate displacement current.

"But surely we cannot just drop displacement current when for a century every expert (e.g. Solymar 1976, Winch 1963) has been protesting that it is the foundation of our craft; that 'Maxwell's leap of genius' in proposing displacement current was what got the subject going – leading to Hertz's discovery of waves in space, for instance?"

The answer lies hidden in Heaviside's magnificent, regal statement, "We reverse this." In his "Electrical Papers", Vol. 1, 1892, page 438, Heaviside wrote;

Now, in Maxwell's theory there is the potential energy of the displacement

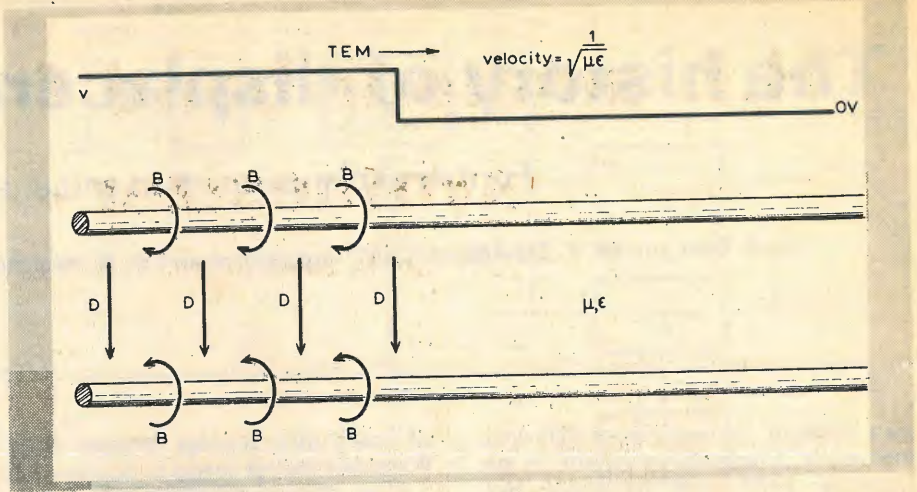


Fig. 3. A TEM step (top) travelling at the speed of light and guided by two wires (below). The B arrows represent magnetic flux lines and the D arrows electric strain between the wires.

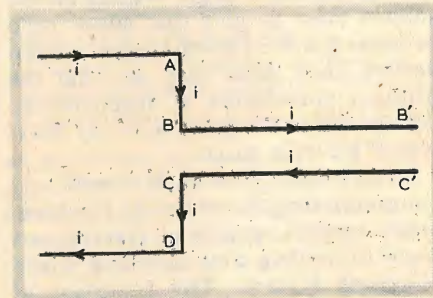


Fig. 4. Current flowing into and out of capacitor plates BB' and CC'. These two plates together constitute a transmission line.

produced in the dielectric parts by the electric force, and there is the kinetic or magnetic energy of the magnetic induction due to the magnetic force in all parts of the field, including the conducting parts. They are supposed to be set up by the current in the wire. We reverse this; the current in the wire is set up by the energy transmitted through the medium around it...

The discrediting of displacement current merely makes Heaviside's "We reverse this" mandatory. It means that the field must be the cause and electric current an effect, rather than (as Maxwell thought) the other way round.

If we keep to "Theory H", the theory that the field $E \times H$, travelling along between the wires at the speed of light – what Heaviside called the "energy current", is the cause, then electric charge and electric current are merely what define the edge of an energy current. If electric current is that which defines the side of an energy current, then we may with equal justification postulate "displacement current" as that which defines the front face of a step of energy current. Under "Theory H", Maxwell's 'leap of genius' (in postulating displacement current and thence waves in space) becomes tautological; "Because a wave in space if it existed would have

to have a front face (displacement current), then I propose such a front face and therefore I propose waves in space."

Maxwell would have saved us a century of confusion if he had had enough insight to say, "Since circuits containing capacitors, that is, open circuits, work, it follows that the essence of electromagnetics cannot be electric current in closed circuits of conductors; it must be something else. What about waves in space?" Heaviside, seventy years ago, missed the key point by a whisker. He failed, but he failed gloriously. He never discovered the flaw in the structure, displacement current.

References

- Bleaney, B. I. and Bleaney 1965, *Electricity and Magnetism*, 2nd Edn (Oxford: Clarendon) p. 258.
- Fewkes, J. H., and Yarwood 1956, *Electricity and Magnetism*, Vol. 1 (London: University Tutorial Press) p. 505.
- Heaviside, O., 1893, *Electromagnetic Theory*, (London. Reprinted New York: Chelsea Publishing, 1971) p. 28 section 30; p. 441 section 218.
- Maxwell, J. C., 1873, *A Treatise on Electricity and Magnetism*, (Oxford: Clarendon) p. 253.
- Popper, K. R., 1963, *Conjectures and Refutations*, (London: RKP) p. 37.
- Solymar, L., 1976, *Lectures on Electromagnetic Theory*, (Oxford: OUP) p. 6.
- Winch, R. P., 1963, *Electricity and Magnetism*, (Englewood Cliffs: Prentice-Hall) p. 387.

Further reading

- Catt, I., Walton and Davidson 1979, *Electromagnetic Theory*, (St. Albans: CAM Publishing, 17 King Harry Lane).
- Catt, I., Walton and Davidson 1979, *Digital Hardware Design* (London: Macmillan).
- Catt, I., "The rise and fall of bodies of knowledge", *The Information Scientist*, 12 (4), December 1978, pp. 137-144. □

The next seminar by the authors on digital electronics design will be held at St Albans on May 3-4. For information, contact C.A.M. Publishing, 17 King Harry Lane, St Albans, Herts.

H.f. amateur band frequency synthesizer — 1

by M. Small, B.Tech. (G4DVI)

This article describes a frequency synthesizer which is capable of covering most of the h.f. band, and which has been used as the local oscillator of an h.f. amateur-band transceiver by the author for five months. The synthesizer contains three basic components: a digital phase-locked loop, a variable frequency interpolation oscillator and a heterodyne mixer.

WISHING to build a transceiver to cover the amateur bands from 10-160m, and to avoid the expense of buying a large number of crystals, the author was prompted to investigate synthesizers using phase-locked loops. A costing showed that, with the availability of cheap t.t.l. m.s.i., a phase-lock loop which would provide the equivalent of 32 crystals could be built for the component cost of between 5 and 8 crystals.

There are many different ways of making frequency synthesizers. (a survey of synthesizers appeared in the Sept., Oct. and Nov., 1978 issues and on p.83 of this issue — Ed.)

The system sketched in Fig. 1 comprises a phase-locked loop which provides frequencies, in 500kHz steps, between 7 and 23MHz. The output of this is combined with a variable frequency from 5 to 5.5MHz, the products of mixing covering a band from 1.5 to 28.5MHz.

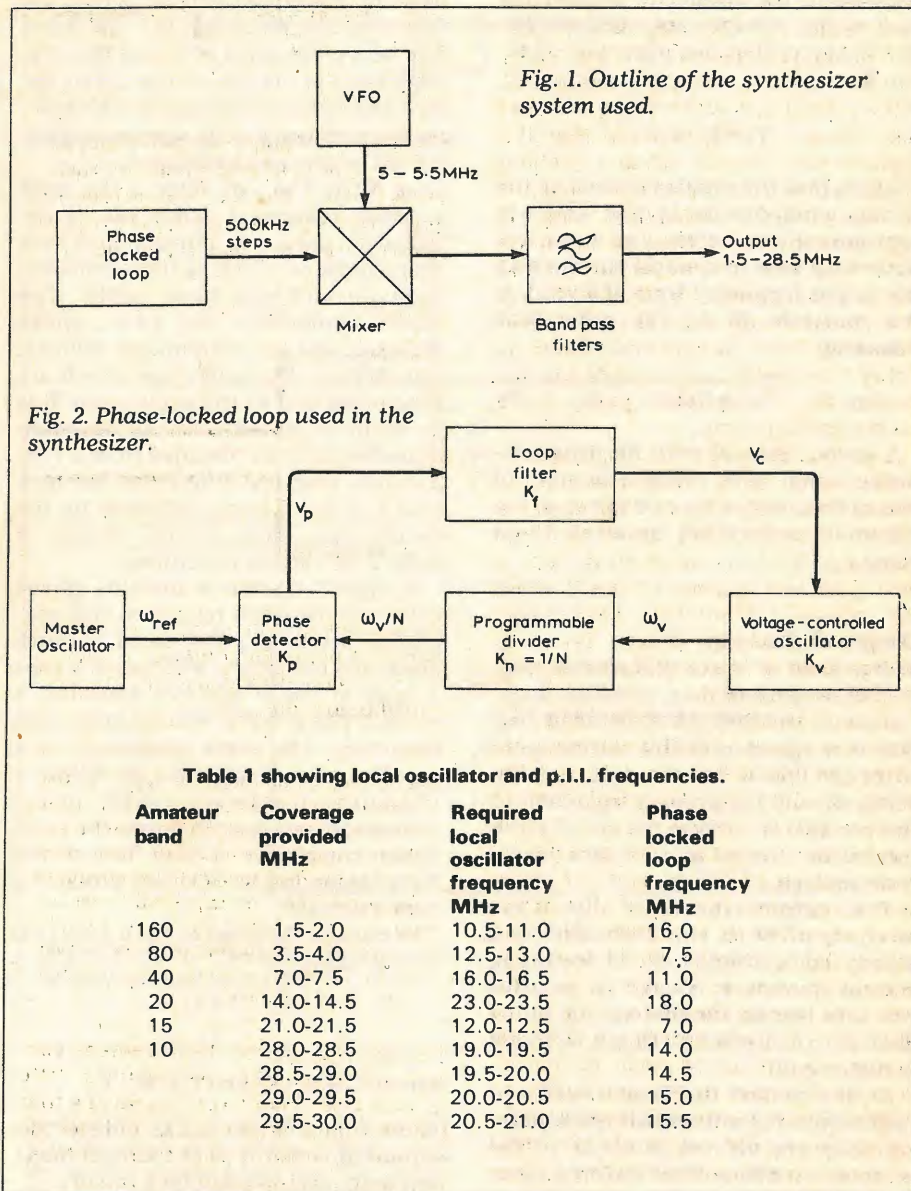


Fig. 2. Phase-locked loop used in the synthesizer.

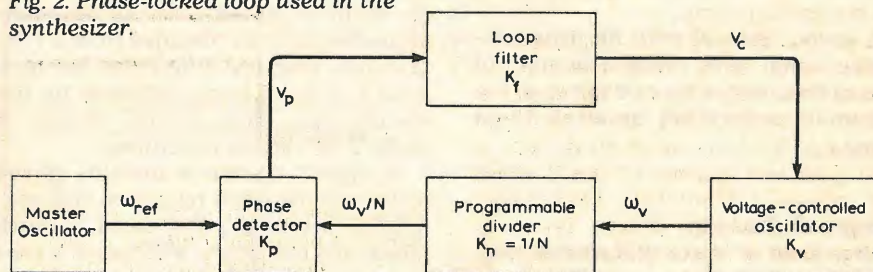


Table 1 showing local oscillator and p.l.l. frequencies.

Amateur band	Coverage provided MHz	Required local oscillator frequency MHz	Phase locked loop frequency MHz
160	1.5-2.0	10.5-11.0	16.0
80	3.5-4.0	12.5-13.0	7.5
40	7.0-7.5	16.0-16.5	11.0
20	14.0-14.5	23.0-23.5	18.0
15	21.0-21.5	12.0-12.5	7.0
10	28.0-28.5	19.0-19.5	14.0
	28.5-29.0	19.5-20.0	14.5
	29.0-29.5	20.0-20.5	15.0
	29.5-30.0	20.5-21.0	15.5

Two sets of local oscillator frequencies would give coverage of the amateur bands for a given intermediate frequency. For a given v.f.o. frequency, there are also two sets of frequencies from the phase-locked loop which could be used to obtain the required local-oscillator frequencies. Tables of all these possibilities were drawn up but only the final one used, Table 1, is shown. This was chosen because direct coverage of the normal h.f. band is also obtained, extending the potential use of the device.

Principle of phase-locked loop

The operation of a phase-locked loop system can be seen from Fig. 2. The loop contains a voltage-controlled oscillator whose output frequency (ω_v) is a function (K_v) of the control voltage V_c .

$$\omega_v = K_v \cdot V_c \text{ rads/sec}$$

The output from this oscillator is buffered and fed into the programmable divider which divides the input frequency by some integer N , so that its output has a frequency equal ω_v/N and

	Performance
range	1.5 to 28.5MHz, in 500kHz bands.
output	70mV r.m.s. into 500 ohms.
stability	Digital phase-locked loop: 10 ppm/degree Centigrade Interpolation oscillator: 50Hz per 15 minutes after 10 minute warm up.
purity of output	In-band spurious outputs typically 90dB below carrier. Out-of-band products from mixer more than 30dB below carrier.
lock up time of phase-locked loop	Small signal: 5ms to within 10% of change. Large change: approx. 8ms per MHz change.

its transfer function $K_n = 1/N$.

The output from the divider is taken to a phase detector where it is compared with a reference frequency ω_{ref} , derived from a master oscillator. The phase detector produces an error voltage V_p , whose magnitude is a function K_p of the phase error between the two signals.

$$V_p = K_p \cdot \phi_e$$

This error voltage is smoothed by the loop filter, to remove residual traces of the reference frequency and to tailor the response of the system. It is then fed back to the voltage-controlled oscillator. The loop filter has a transfer function K_f

$$V_c = K_f \cdot V_e$$

Given that the characteristics of the various components in the loop are appropriately matched, the loop will settle with time to a stable state where the output frequency from the v.c.o. is the multiple N of the reference frequency.

$$\omega_v = N\omega_{ref}$$

Clearly, since N may be programmable within some range, a number of output frequencies may be selected, the minimum separation between them being ω_{ref} .

Design of the loop

Design aims of a p.l.l. will specify such factors as settling time, stability, spectral purity and drift. More detailed analysis is required to enable the designer to predict how these aims can be achieved, and the primary approach to this problem is through the use of servo mechanism theory and Laplace transform analysis.

The Laplace transform allows the analysis of both the transient and steady state conditions in feedback control systems. It is valid for positive real time, linear parameters. An introduction to its use for p.l.l.s can be found in reference 1.

In this method the feedforward and feedback transfer functions of the control loop are defined in terms of the complex variable s . The resulting equations may be tested using largely algebraic techniques to determine the stability of the system. In addition, their type and order can be used to indicate the transient response characteristics to be expected under various conditions of input.

In the p.l.l. system of Fig. 1, the feedforward transfer characteristic of the loop,

$$G(s) = K_p \cdot K_f \cdot K_v \dots \dots \dots (1)$$

and the feedback transfer function,

$$H(s) = K_n = 1/N \dots \dots \dots (2)$$

The characteristic equation of the loop CE is defined to be

$$1 + G(s) \cdot H(s) = \phi$$

which, in the case of this loop, is

$$1 + K_p \cdot K_f \cdot K_v \cdot K_n = \phi$$

When the loop is closed its transfer function is

$$\frac{1}{1 + G(s) \cdot H(s)}$$

Substituting from (1) and (2), this becomes for our system

$$\frac{1}{1 + K_p \cdot K_f \cdot K_v / N} \dots \dots \dots (3)$$

Now some of the functions K_p, K_v, K_f have a complex nature; that is they are functions of s . Equation (3) will therefore be a polynomial of s , and the characteristics of the polynomial define the type and order of the system. The practical consequence of its type in particular will be discussed shortly.

Loop filter. The loop filter is the main variable component which can be designed to tailor the fundamental loop characteristics — lock up time, transient response and loop band width. The other components, the v.c.o., phase detector and programmable divider, usually have characteristics which are fixed or defined by the application. It is generally accepted that the optimum characteristics are obtained from a type 2 system, practical differences between type 1, 2 and 3 being indicated by the steady-state phase errors, shown in Table 2 for various conditions.

A type 2 system maintains phase coherence between reference and controlled oscillators for steps in both phase and frequency, whereas in a type 1 system there always remains a residual phase error which varies with frequency. The extra advantage of a type 3 system being able to follow a changing frequency with phase coherence is not usually worth the extra design complexity. A loop filter of the form shown in Fig. 3(a) will produce a type 2 system.²

The transfer function of such a filter is (if A is large)

$$K_f = \frac{1 + T_2}{T_1}$$


where $T_1 = R_1 \cdot C_1$ and $T_2 = R_2 \cdot C_1$

These time constants can further be expressed in terms of the loop natural frequency (ω_n) and damping factors (ζ)


$$T_1 = \frac{K_p \cdot K_v}{N\omega_n^2} \quad T_2 = \frac{2\zeta}{\omega_n}$$

hence
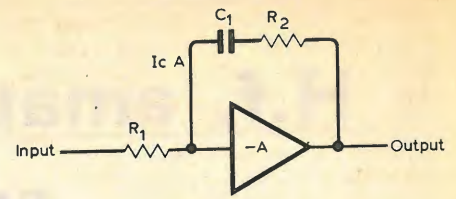
$$R_1 = \frac{K_p \cdot K_v}{N\omega_n^2 C_1} \quad R_2 = \frac{2\zeta}{\omega_n C_1}$$



(a)

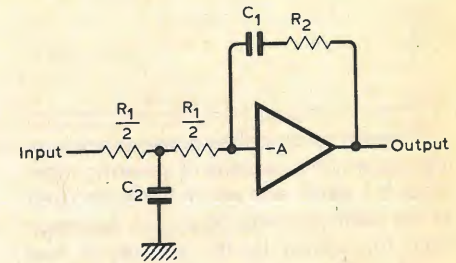

(b)

Fig. 3. Loop filter to obtain a Type 2 form of phase characteristic is at (a), modified as at (b) to contain additional filter R_1, C_2 for the reduction of error pulses.

The values required for ω_n and ζ must be chosen by the designer to obtain the required settling characteristics (transient response) or frequency response (peaking and roll off). The values for ω_n and ζ can be chosen using the normalized transient response curves shown in Fig. 4, which plot the response to a step in frequency. The effect of varying the damping factor is shown and the normalized time axis is a function of ω_n . From these it can be seen that for reasonable values of damping factor $2 > \zeta > 0.5$ a system will lock to within 10% of the step within the time, $t = 5/\omega_n$. Thus, the required settling time can be used to determine ω_n and the shape of the response.

Limiting conditions

For the phase-lock loop system to possess the characteristics predicted by the solution of these equations, it is necessary that none of the components are driven beyond the range over which their transfer functions are as described, that is to say, into limiting. This is normally avoided by allowing sufficient tolerance between the boundary design conditions and the known physical limits on the components.

The limits on components to be considered are

- maximum and minimum output voltages obtainable from the operational amplifier.
- limit of the linear voltage/frequency characteristic of the varicap diode.
- maximum output from the phase detector.

STEADY STATE PHASE ERROR

Type	step phase	step frequency	step rate of change of frequency
1	zero	constant	continuously increasing
2	zero	zero	constant
3	zero	zero	zero

These limits must be allowed for under the worst case design value of overshoot as found from the normalized time-domain response curves. This is the case most likely to drive the operational amplifier or the varicap diode out of the linear region. The combined effect of maximum overshoot at the edge of the band covered together with error pulses from the phase detector should also be catered for. The problem of error pulses is most readily reduced by inserting a simple, low-pass filter between the phase detector and the integrator. This can be obtained by dividing the resistor R_1 in the integrator circuit into two parts and inserting a capacitor C_2 , as in Fig. 3(b).

The turnover frequency of this filter should be chosen to be 10 times the natural frequency of the loop, ω_n , so as not to reduce the phase margin of the system. The filter has the additional advantage that it reduces the feed through of the reference frequency and so contributes to the spectral purity, which may be expected from the output of the voltage-controlled oscillator. The turnover frequency can be shown to be

$$f_c = \frac{4}{2\pi \cdot R_1 \cdot C_2}$$

Response to large changes in N

The response of the system to a large change in the division ratio N can be much slower than that predicted by the Laplace method. This occurs when the maximum cumulative phase error that the phase detector can handle is exceeded during lock up. However, it is possible to estimate the maximum frequency step which will remain within this limit and the response time when it is exceeded.

The maximum phase error that the phase detector used here can handle is $\pm 2\pi$ radians. If this is exceeded, the output remains of the correct polarity, because the device contains a frequency detector, but its magnitude is a sawtooth function of increasing phase error, as in Fig. 5. This sawtooth has a repetition frequency equal to the instantaneous difference between the two input frequencies. The sawtooth modulates the control voltage, causing the system to settle in what appears to be an oscillatory manner. Since the loop contains what is effectively a low-pass filter, the oscillations appear to increase in amplitude as the v.c.o. approaches its target frequency.

It is possible to predict the maximum frequency step which can be achieved with a phase error of less than $\pm 2\pi$ radians. If the loop is initially in a locked condition, both the reference frequency and the output from the programmable divider have the same frequency and phase, illustrated in Fig. 6 by the portion of the graph A-B. At point B, the modulus of the divider is instantaneously changed by some step. The

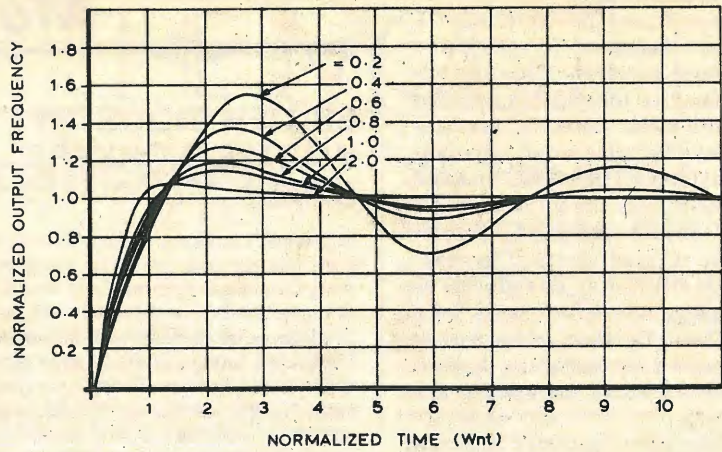


Fig. 4. Normalized response curves in the time domain of Type 2 system to a step in frequency.

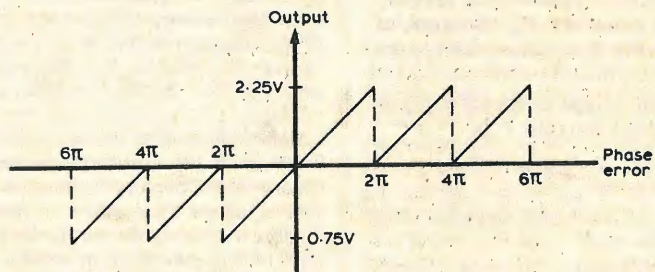


Fig. 5. Sawtooth output of phase detector for wide capture band.

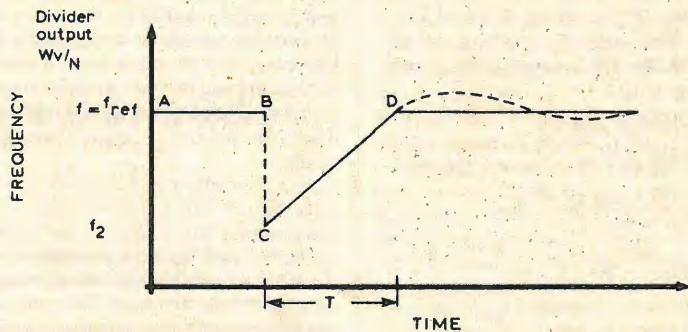


Fig. 6. Effect of changing division ratio of programmable divider.

v.c.o. frequency is initially unchanged and the result is that the output from the divider changes to a new frequency f_2 , shown by BC in Fig. 6. The loop now starts to respond to correct the increasing phase and frequency coherence will again be achieved after time T .

The magnitude of the phase error is

$$\phi_{CD} = \pi (f_{ref} \pm f_2) T \text{ rads.}$$

If the original division ratio was N_1 and the new ratio is N_2 then

$$f_2 = \frac{N_1}{N_2} \cdot f_{ref}.$$

So the original equation can be re-written

$$\phi_{CD} = \pi \cdot f_{ref} \cdot \left(1 \pm \frac{N_1}{N_2}\right) \cdot T.$$

Given that the maximum phase error is

$$\begin{aligned} -2\pi < \phi_{max} < 2\pi, \\ -2\pi < \pi \cdot f_{ref} \cdot \left(1 \pm \frac{N_1}{N_2}\right) \cdot T < +2\pi \\ = \left(1 - \frac{2}{f_{ref} \cdot T}\right) < \pm \frac{N_1}{N_2} < \left(1 + \frac{2}{f_{ref} \cdot T}\right) \end{aligned}$$

For example, if the term $f_{ref} \cdot T$ has a value of 50, which is reasonable to ensure minimum feed through of f_{ref} , then N_1/N_2 must be within the range.

$$\frac{48}{50} < \frac{N_1}{N_2} < \frac{52}{50}$$

So the maximum step in N corresponds to about $\pm 4\%$, if phase coherence is to be maintained.

Reference feedthrough

The most significant problem with a digital phase detector is reference frequency feed through. This occurs when the loop is locked because of leakage in the phase detector, integrator or any other similar small unbalancing conditions. The feedthrough frequency modulates the v.c.o. and this modulation can be detected as sidebands on the wanted signal. The magnitude of this effect may be reduced by the loop integrator which acts as a low-pass filter. Further suppression may be obtained by including further low-pass filters or by balancing the leakage effects.

The MC4044 phase detector contains a charge pump with a small reverse leakage current, which may, at extremes of temperature, be $5\mu\text{A}$, but is typically less than $0.1\mu\text{A}$. If it is assumed that the reference frequency is greater than the time constant T_2 , the gain of the filter at this frequency tends to R_2/R_1 .

The apparent phase detector output due to the leakage current I_L is

$$V_{p(\text{leakage})} = R_1 I_L$$

Thus the error voltage due to this leakage is

$$V_{E(\text{leakage})} = \frac{R_1 \cdot I_L \cdot R_2}{R_1} = R_2 \cdot I_L$$

It is possible to compute the magnitude of the sidebands produced for small leakage effects using normal f.m. theory. For f.m. signals with a small modulation index the magnitude of the first sideband is

$$J_1 = \frac{1}{2} (\text{modulation index})$$

In the case here this is

$$J_{1(\text{leakage})} = \frac{1}{2} \cdot \frac{V_{e(\text{leakage})} \cdot K_v}{\omega_{\text{ref}}}$$

$$\text{i.e. } \frac{\text{sidebands}}{\text{carrier}} = \frac{1}{2} \cdot \frac{R_2 \cdot I_L \cdot K_v}{\omega_{\text{ref}}}$$

$$= 20 \log_{10} \frac{1}{2} \cdot \left(\frac{R_2 \cdot I_L \cdot K_v}{\omega_{\text{ref}}} \right) \text{dB}$$

To be continued □

References

1. Garth Nash. Phase-locked loop design fundamentals. Motorola application note AN535.
2. P. Atkinson and A. J. Allen. Design of Type 2 digital phase-locked loops. *Radio and Electronic Engineer*, Nov. 1975, p.657.

More letters

BRITISH INDUSTRY WASTES WORKERS' SKILLS

Mr Pepper's advice (January letters) to those with engineering skills to emigrate to a seller's market is economically sound and his example testifies to the reality of our social freedom, i.e. to the existence of international free-trade. Intra-nationally of course, constraints other than those of commodity market-value are recognised by executives and other workers, e.g. *Der Spiegel* recently reported that British workers are "treated like dirt" (classwise) and of course they too sometimes find their skills better paid elsewhere.

The recovery of "British" industry has long been sought in the same direction. Most large firms find it more profitable not to export but to manufacture within their market region, i.e. not the produce but the production is exported. The "British" problem is therefore twofold:

1. Dependence upon supra-national firms.
2. The working structure chosen by most firms wherein personnel placement in "division of labour" categories is made a class attribute with rigidly controlled contributions to and rewards from society.

As a socially constructive approach to the problem I recently suggested to my employer (a major international industry) via the suggestions box that an "innovators' workshop" be incorporated as a subsidiary of the group, administered by the innovators with spare time access to the group's employed expertise, and to some capital plant during normal unused periods, in order to develop to prototype stage potentially commercial products for separate exploitation with joint equity.

Being socially revolutionary the idea was rejected (cf. the Lucas Combine plan). To demonstrate the scope of the project I described in outline to the management a novel 3D system enabling transmission and recording of "look around" 3D motion colour images, with "zoom" and projection facilities.

It is not, therefore, the technocrat's current differentials alone, but the hierarchy's increasing failure to employ creatively skills of all kinds which defines our socio-economic problem.

C. H. Dierks
Nether Stowey
Somerset

3D TELEVISION

Being away at the time your November issue was published I only recently saw the article "What future for television?" with its discussion on three-dimensional viewing. It certainly revived memories of a quarter of a century ago for we could have had such then, compatible and in colour.

My father, the late Granville Bradshaw, whose inventions spanned many fields but who was better known for his advanced designs of automobile, motorcycle and aero engines, some of which are to be found in the Science and other museums worldwide, developed in the 1930s a system for the three-dimensional display of pictures where an

object in the foreground, say, was angularly displaced in relation to the background as the viewer moved across the screen of the display, thus giving a very realistic 3-D impression. In fact it was as if one could 'look around the back' of the object as in real life.

With this in mind when, in the early 1950s television concerns were becoming somewhat apprehensive of losing their new-found audiences which flocked back to the cinemas with their wide screen and stereoscopic systems now all the rage, he conceived the idea that the principle of his 3-D picture display, which was wholly mechanical, could be adapted for television viewing and asked me to design an appropriate electronic 3-D system based on this, which I did.

Both the BBC and the then ITA were approached and were greatly interested but had to admit they had no mandate to move into this field, let alone any finance with which to carry out experiments, so, as it has so often been said, yet another British invention being too far ahead of its time was stifled at birth.

Readers of that eminent journal of the day *Picture Post* may remember the publication of an article headed "We can have 3-D Television" on this very project. The date, July 1953.


Geoffrey Bradshaw
Leatherhead
Surrey

May I correct Professor Bell for a minor inaccuracy in his article "What future for television" (November issue)? I remember as a boy seeing in London the feature/musical film "Kiss Me Kate" at the Empire Leicester Square and "House of Wax" at the Warner Leicester Square in 3D using 45°/45° polarised glasses. I also refer him to the *British Kinematograph Society Journal* for reports on 3D films, especially in the USSR. His comment "... but does not appear to have produced any normal film in 3D, neither feature or documentary" is consequently in serious error.

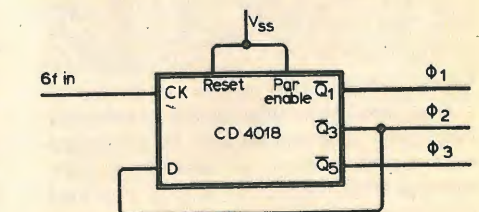H. L. Yentis
Edgware
Middlesex

GENERATING THREE PHASES

Three phases may be generated more simply than the method suggested in "Circuit Ideas" in the August 1978 issue p.60, by substituting



a CD4018 variable divider for the CD4017, since this gives square wave outputs, displaced in phase from one another (see the accompanying diagram).

D. Austin
Birmingham

NEWS OF THE MONTH

White paper on broadcasting strongly criticized

The Government's White Paper on broadcasting was likened to a haystack stuffed with weapons in the November 78 issue of *Independent Broadcasting*, the IBA's quarterly journal. This was a personal reaction by the IBA's director of television, Mr Colin Shaw, a former chief secretary to the BBC.

In the article, Mr Shaw said that the White Paper proposed Government intervention on a scale previously unknown in Britain. This, he said, far exceeded anything that would be considered tolerable if it were applied to the press or book publishing. He recalled that the broadcasters had always acknowledged that the Government's responsibility for the allocation of frequencies secured by international agreement gave politicians a greater right and opportunity to intervene in the conduct of broadcasting, and that, until now, they had exercised this right with caution. Very early in the history of broadcasting in Britain, ministers had evolved the formula, in dealing with parliamentary questions, that the day-to-day responsibility for the broadcasting services rested with the broadcasting authorities. By these means, British broadcasting had enjoyed a degree of independence in editorial

control as great as any to be found in the world and out of them had grown a reputation for the range and quality of programming which was widely envied. However, according to Mr Shaw, there were indications that both of these might be in danger. "Well intentioned as it may be, and innocent-seeming, in some of the proposals it contains, the White Paper stands like a haystack stuffed with weapons against some future need," he said.

Mr Shaw also discussed the threats posed to the independence of broadcasting by some of the proposals for ministerial appointments to the IBA and BBC advisory bodies and to service management boards in the BBC. He asked whether the members of the OBA would have the trustee role traditionally given to the Governors of the BBC and members of the IBA, who act both as trustees of the national interest and as a buffer between the Government and programme makers. "In a television interview not long ago after the White Paper appeared, the Home Secretary seemed to be saying that they would not", he said, "... The OBA would be highly vulnerable to Government pressure in the absence of such a buffer".

GEC and Hitachi join forces to make tv sets

Following the example set by Rank and Toshiba, who in August last year said that they were to operate jointly, two more companies, GEC and the Japanese company Hitachi, have announced that they are to work together in the manufacture of television sets at Hirwaun in South Wales. This union has been welcomed by Alan Williams, Minister of State for Industry, whose own policy is to encourage co-operative ventures between Japanese and British companies.

Mr Williams said when the announcement was made that this venture, like the one taken by Rank and Toshiba, would make it clear in Japan that we (the British) really do want Japanese companies in our country. He welcomed the project for a number of reasons. Apart from saving a large number of jobs which were very seriously threatened in an area of high unemployment, it would enable Japanese technology to be applied to British industry. It would also increase efficiency and exports and save time on imports, and it would show that yet another major country had chosen the UK as a base for its manufacture for the whole of Western Europe. GEC already sourced over half of their non-tube components and materials from within the UK, and the new joint venture would make the maximum use of UK tubes, components and materials, subject to commercial considerations. There would also

be extra investments to improve the quality of the components and this in turn would add to the capability of the British component industry and help to improve the quality and reliability of British-made consumer electronics.

Mr Williams suggested that the venture would be a great encouragement to Japanese and other foreign investors. Repeatedly these investors had shown that small and medium-sized, well-managed enterprises in this country could operate well, could be highly efficient and have high productivity, resulting in the country having the best-profitability in Europe.

Discussions between Hitachi and the Department of Industry, about Hitachi's proposal to establish a colour-tv manufacturing facility in the UK, initially took place during 1977 and early 1978, but as a result of opposition from certain sections of the British tv industry the company eventually withdrew its proposals. However, during his visit to Japan in April 1978, Mr Williams stressed his, and the British Government's, disappointment at Hitachi's decision, and he indicated that it was in sensitive sections such as tv manufacture that co-operation between Japanese and British companies would bring mutual benefits, and might prove the best way forward.

RCA to enter videodisc market

Following the lead of Philips and MCA (see News, p.39, Feb. 79 issue) RCA has decided to launch its "Selecta Vision" videodisc system in the United States of America. RCA's president, E. H. Griffiths, said that they would proceed with "maximum speed" to get the product ready for introduction in the US, and a schedule for the product's introduction, and marketing concept aimed ultimately at full national distribution, would be announced later this year.

The company is giving the videodisc system top priority because their market research indicates that it will become a multi-million-dollar business in the 1980's. Before RCA would consider going ahead with the project two years ago the company's chief executive set certain goals which had to be met. They planned to develop a videodisc player that could be sold at a retail price of \$400 (about £200) or less, and an uncoated disc that would contain one hour of programming per side, or a total of two hours per disc. There also had to be available adequate software, or programming, to support the introduction of the system and to sustain it in the market. RCA say that they have now met these goals.

The RCA system is very different to the Philips/MCA system in that it uses a grooved disc that is played with a diamond stylus (the latter uses an optical system so that no stylus or needle ever touches the disc). RCA's disc revolves at 450 rev/min, contains one hour of programming on each side, and is expected to sell for about \$10 to \$17 (about £5 to £8.50).

The disc comes in a plastic sleeve, similar to a record album cover, which, when inserted into a slot on the front of the videodisc player, deposits the disc on the turntable. To remove the disc, the empty sleeve is simply re-inserted into the slot.

RCA's initial catalogue of programmes will contain 250 titles including feature motion pictures, musical sports, cultural, education and children's programmes.

New electronics teaching programmes available in UK

A series of electronic training systems for subjects ranging from elementary principles to modern communications and computers, is now available in the UK. These systems, which are supplied by Dagem Systems Ltd, are modular programmes containing all the equipment and manuals needed to perform a series of laboratory experiments in the subjects they cover. The elementary, basic and intermediate laboratory systems, for example, consist of a set of experimental circuit boards and plug-in components. Each circuit is permanently wired underneath its board and the plug-in components, which complete the circuit, are used only for the parameters which are changed during the experiment. Each electronic training system is supplied with its appropriate theoretical and experimental manuals.

First transatlantic video link using optical fibres

On December 12 a two-way sound and video system, originated and terminated with optical fibre equipment, linked the Post Office's Contravision studio in London with a Bell Canada studio in Toronto, Canada. This was the first ever transatlantic link of its kind and also the first time that colour television had been used for Contravision, which is the Post Office's conference-by-tv system. The two-way link enabled the participants to hold 'across the table' discussions with their colleagues on the other side of the Atlantic.

The transatlantic discussions demonstrated the capabilities of optical fibre transmission systems in sending sound and vision signals over long distances and also marked the start of a two-year household trial of an optical fibre system — initially serving 35 residential telephone customers in Yorkville, Toronto — which Bell Canada is carrying out.

The main link in the communications chain was the Intelsat satellite positioned 22,300 miles above the Atlantic Ocean. This carried the signals between Britain and Canada. Underground optical fibre cable systems in London and Toronto were used to carry the signals to and from the two studios. In London, outgoing signals were transmitted over a 1.7km optical fibre link, supplied by British Insulated Callenders Cables Ltd (BICC) and Plessey Telecommunications Ltd, to the Post Office Tower. This system has been in public service for the past two years as part of the Post Office's public

Contravision network.

According to the Post Office, together with British industry they have developed optical fibre systems to the extent that they could be installed and working in the UK telephone network by 1980. Their aim initially is to introduce optical fibres into key inter-city networks and between telephone exchanges within main city centres. Already telephone calls are being carried by two experimental optical fibre links in the UK — a 13km link in Suffolk and a 9km link in Hertfordshire. Two further trial links are nearing completion. These are between Maidenhead and Slough, supplied by Plessey and BICC, and between Uxbridge and Ruislip, supplied by GEC and TCL. On the Suffolk link, at Martlesham, Post Office researchers are studying more advanced systems for inter-city and undersea operations, as well as cost-reduced systems.

The optical fibre cables at the Canadian end of the transatlantic link were made by Northern Telecom Ltd and were linked to a laboratory where research for the two-year trial is being carried out. Bell Canada's research company, Bell Northern Research Ltd, started work on practical fibre-optic transmission systems in 1972. Then, in 1977, following work for the Department of National Defence, they installed a 1.42km optical fibre link between two switching centres in Montreal to test optical fibres under field conditions. Each pair of fibres in this trial are used to transmit and receive 96 simultaneous telephone conversations.

News in brief

Post Office trials on an **inductive coupler to help people using hearing aids** fitted with pick-up coils to make better use of the telephone have been completed. The coupler replaces the standard telephone inset. Eighty per cent of the trial 'guinea pigs' reported a substantial improvement in reception when using the new device. Some minor modifications were made as a result of this trial, and a first contract for 100,000 units has now been placed. First deliveries of these devices are expected early this year.

The University of Essex will be holding its annual **electronics summer school for teachers** during the week July 9-13, 1979. This year, as well as courses in linear circuit design and digital circuit design, a **third course in electronic systems** is available which is closely related to the A.E.B. electronics systems A-level course. The **linear design course** covers the use of transistors and operational amplifiers in analogue applications, particular emphasis being placed upon design philosophy related to the basic circuits in a hi-fi amplifier. The **digital design course** concentrates on the use of the transistor as a switch and develops design using integrated logic circuits. A programme of laboratory experiments is included on each course so that the lecture material is fully supported. Further information on the summer school may be obtained from Dr M. J. Hawksford or Mrs J. L. Mead at the Department of Electrical Engineering Science, University of Essex, Wivenhoe Park, Colchester CO4 3SQ (Tel. 0206 862286, ext. 2262/2299).

Third Marisat shore station commissioned

Japan's maritime-communications shore station, for use with the Marisat (Maritime satellite Communications) satellite above the Indian Ocean, was officially commissioned on November 18. The station, which is located at Yamaguchi in the western-most part of the main island, was completed in September by the Nippon Electric Co. Ltd (NEC) for Kokusai Denshin Denwa Co. Ltd (KDD), Japan's international communications company. KDD's Intelsat standard A earth station is also located on the same site.

The new station can provide, via the Marisat satellite, 22 high-grade telegraph lines and two telephone lines between land subscribers and ships in the Indian Ocean and the water off Japan and Southeast Asian countries. It is the third station of its kind in the world and the first to be capable of accessing the Marisat satellite over the Indian Ocean. The other two stations, which have access to Marisat above the Pacific and the Atlantic oceans, are located in the USA, one at Santa Paula in California, and the other at Southbury in Connecticut. Since the Marisat system can now cover almost all the waters of the world it not only ensures a high standard of world-wide maritime communications services and efficient operation of ships, but also provides better safety and distress services.

The Marisat station has a duplex configuration and a 13m-diameter Cassegrain antenna, which is commonly used for the C and L bands. A network control processor assigns the channel and controls the line connection between ships (both at sea and in ports) and

land subscribers or shore stations, performs telegraph and telephone signal conversion, and supervises the status of lines.

In addition, the Marisat system, which is jointly owned and operated by several US communications companies, also provides services for facsimile and data transmission. All of these services are, of course, only available to ships equipped with a Marisat ship terminal. A typical ship terminal consists of an r.f. and antenna assembly mounted in a water-proof radome above deck and a communications console installed below deck. NEC, together with Anritsu Electric Co. Ltd of Tokyo also manufacture such a terminal.

Picture shows a Jetstream T. Mk 2 aircraft, the first of sixteen being delivered to the Royal Navy. On-board equipment includes a static inverter, Model 060-05, made by Brandenburg Ltd. The Model 060-05 is a three-phase unit delivering 115V at 400Hz for the aircraft's electronic equipment. It operates from 28V d.c. and can provide a total output power of 1500VA. Output frequency and voltage are maintained constant over a wide range of input voltages and load variations.

The sixteen aircraft, which will replace Sea Princes currently in service in an observer training role, are manufactured by the Scottish Division of British Aerospace's Aircraft Group.



Post Office meets Government's financial targets

According to a statement by Sir William Barlow, the Chairman of the Post Office, continued stable prices and a vigorous drive for increased business has enabled the Post Office to achieve results which show that the Corporation is still meeting the financial targets set by the Government.

Interim unaudited results show that in Telecommunications, the Post Office had an income of £1549.1 million and a profit after interest of £144.7 million over the half year to September 29, 1978. Figures for the full year to March 31, 1978, show a £2924 million income and £326.6 million profit. In Posts, results for the full year showed an income of £1325.1 million and profit of £40.4 million and for Girobank and Remittance Services, £77.9 million and £0.7 million respectively. Corporation figures, again for the full year, give an income of £4183.2 million with a

profit before dividend and taxation of £367.7 million.

The financial results for the current half year, for each of the three main businesses, are consistent with their full year targets set by the Government. For Telecommunications this represents 6% return on mean net assets at replacement costs. Mr Barlow suggested that the half year results reflected the increased use which was being made of the Post Office services. This, he said, was partly due to the fact that telephone rentals and call charges had not increased for more than three years and postal charges had been frozen for 18 months. Telephone traffic had continued to increase and determined efforts were being made to improve the quality of the international telephone operator service, which Mr Barlow considered had fallen short of the standard required.

Product liability conference

A special one-day conference on product liability is to be held at the Europa Hotel, London, on Friday, March 2. It is hoped that the conference will enable delegates to study in-depth not only the UK's liability law today, and its likely changes tomorrow, but also its practical effects through insurance and through hazard reduction.

Greville Janner, Q.C., Member of Parliament for Leicester West, said when the conference was announced that every executive and manager concerned with the manufacture or marketing of products should have been following developments in our law with grave concern and in preparation for change. He referred to the Law Commissions, the Royal Commission on Civil Liability (the Pearson Commission) and to the EEC Draft Directive, as well as to changes which have already been made in the USA and in many of the EEC countries (see News, p.47, Jan 79 issue).

Speakers at the conference will present the

practical aspects of product liability law, as it affects all those concerned with the manufacture, distribution, purchase or sale of industrial products. Mr Janner will also explain how to use documentation in order to cope with product liability problems — actual and likely — with special regard to the new anxieties created by "The Supply of Goods (Implied Terms) Act" and "The Unfair Contract Terms Act". The other speakers will be: Lord Pearson, who was chairman of the Royal Commission on Civil Liability and Compensation for Personal Injuries (the Pearson Committee Report, 1978); Professor Anthony Jolowicz of Trinity College, Cambridge, an expert in EEC and USA product liability law; Oliver Prior, a product liability insurance specialist and Brian Mair, who is the MD of Plessey Assessment Services Ltd, a product liability consultancy.

The conference is to be held by Industrial & Commercial Technical Ltd (In Com Tec), Park House, Park Street, Camberley, Surrey.

Government enters mobile radio business

The British Government has now gone into mobile radio after its acquisitions a few years ago with Ferranti and the more recent investment in Inmos Ltd. The National Enterprise Board (NEB) and Berc Group Ltd (formerly Ever Ready Company (Holdings) Ltd) have reached agreement in principle to form a joint company to acquire the business of Burndept Electronics (ER) Ltd, a wholly-owned subsidiary of the Berc Group. It is planned that the NEB will invest £510,000 in Burndept in exchange for 51% of the equity, with Berc retaining a 49% holding. This investment will enable the company to expand in existing markets and also to develop additional products.

Burndept Electronics, who manufacture a wide range of two-way radio communications equipment, employ about 400 people and are located in Erith, Kent, and Biggleswade, Bedfordshire. They supply personal radios to the majority of UK police forces and also to a variety of industries. The company also manufactures a full range of vehicle-mounted radio equipment, base stations, complex radio control schemes and emergency rescue systems.

In the last six years Burndept has made

about a £1 million loss, mainly due to the cutbacks in police spending and to inflation eating away the profit on their fixed price contracts. Berc, who were unable to give the financial and technical support needed, plan to concentrate on their portable power business.

News in brief

The Post Office is anxious to do the right thing in relation to **microwave radiation exposure** and are, within their own powers, seeking to allay the fears currently being expressed by the media. They are providing attenuators for new inland microwave radio contracts to reduce the power fed to antennas by an order of 20dB, when necessary, thus reducing the radiation from the antenna. Instructions are also being given to people working in front of antennas to ensure that the power inputs to the antennas are either removed, reduced sufficiently or measured to confirm that the radiation level is permissible.

Audience response to wavelength changes

A document issued by BBC Radio says that, on balance, reception for all four BBC radio channels on their new wavelengths, is better than it was before the introduction on the 23rd November, 1978. The majority of listeners questioned four days after the changes said that reception had improved or remained the same and only a small proportion reported that their reception had deteriorated. The BBC is examining those areas where it is known that people are experiencing poor reception.

Figures from the normal BBC Daily Audience Research Survey were as follows: percentage of listeners reporting that reception was now better on Radios 1, 2, 3 and 4 was 45%, 35%, 24% and 35% respectively; those reporting that reception had deteriorated were 6%, 10%, 14% and 12% respectively. Listeners reporting that reception was about the same on Radios 1, 2, 3 and 4 were 49%, 55%, 62% and 53% respectively.

A preliminary examination of listening figures for the first three days on the new wavelengths show a slight increase in audiences for Radios 1 and 2 and no change in the size of audiences for Radios 2 and 4.

Maritime radar to be fitted to Nimrod

Searchwater, perhaps the world's most advanced maritime radar, will soon be fitted in the RAF's Nimrod aircraft. The radar and equipment division of EMI Electronics at Hayes, Middlesex, delivered the first production model of Searchwater to the Ministry of Defence on November 7 last year.

Searchwater is the result of more than six years of research and development work by the staff of EMI Electronics and engineers from the Royal Signals and Radar Establishment at Malvern, Worcestershire. The radar uses its own computer to detect, measure, track and classify its targets and its power and versatility have already been demonstrated during extensive flight trials. At very long ranges Searchwater can even detect targets as small as the periscope of a submerged submarine, say EMI. During the six years of its development, designers continually modified Searchwater to accommodate the latest electronic technology despite the rapid changes taking place.

Tandberg ends Norwegian operations

At a special meeting in Oslo, the Norwegian Government recommended to the management of Tandberg Radiofabrikk A/S that the company close down their trading operations with effect from the next day (Dec. 14). Despite this, the government has pledged to continue to support the company with a view to restructuring the special product divisions of the Group that have a continuing commercial future. In addition, a sum of 50 million Nkr which had been offered to the company two days before would still stand and would be employed for an orderly wind-down of the operations in Norway and to investigate the remaining operations.

Tandberg have eleven overseas subsidiary companies and other representatives worldwide, including the Leeds company Tandberg (UK) Ltd, the most successful of the daughter companies with a turnover of over £6½ million.

V.d.u. health hazards warning

TASS, The Technical, Administrative and Supervisory Section of the Amalgamated Union of Engineering Workers, is warning its committees of representatives of the potential health hazards associated with the use of visual display units. This warning comes in a document, from the general secretary of TASS, Ken Gill, which says a sizeable body of evidence shows that unless a v.d.u. or terminal is used correctly there can be potential health hazards to the operator. The document is concerned specifically with the introduction of these units in areas of clerical work and gives, as a guidance to the representatives, the conditions in which v.d.u.s should be used.

According to the document, clerical work ideally requires brightly lit work areas, preferably near daylight, whereas v.d.u.s are best used in shady conditions. This contradiction means that the v.d.u.s are seldom used under the correct lighting and, in some cases, reflections on the screen can be brighter than the projected image. The document suggests that offices in which v.d.us are used should be kept gloomy and local lighting provided where necessary for work areas.

The health hazards associated with v.d.us include visual fatigue, stress, posture ailments and radiation exposure. TASS attempts to give the causes of these afflic-

tions and describes in quite considerable detail the symptoms experienced by the sufferers. Visual fatigue they say is caused by glare, reflections and lack of contrast on the screen. Stress results among other things from slow computer response times, poor environmental conditions and 'the information load'. Posture ailments such as back-ache, headache and aching muscles are blamed on the bad standard v.d.u. layout, the fact that the screen is usually above the keyboard. This, says TASS, imposes an immobility which leads to the aches/pains described.

Radiation exposure is the cause of major concern to TASS because they say that the health hazard has not yet been determined. However, to minimise risk they suggest that v.d.u.s should be frequently serviced by qualified engineers and the front of the tube covered by a glass panel. They also suggest that the set be enclosed in a metal case to give maximum protection in case of explosion.

As a guide to office committees who may negotiate agreements on the introduction of v.d.u.s, TASS gives a total of 14 recommendations. In addition to regular maintenance of the units, they suggest that the screens be tested for glare and reflections and that ambient lighting be reduced to below 300 lux,

with additional local lights being fitted where necessary for ordinary clerical work. One recommendation suggests that each piece of v.d.u. equipment should have a plaque attached stating how it should be operated and specifying the health hazards which can occur if the safeguards are not followed.

News in brief

Strathearn Audio Limited, the Belfast high-fidelity equipment manufacturer, established by the Government five years ago, is to close. The reason for the closure is that the Treasury is unwilling to consider providing additional funding until the autumn of 1979, by which time their proposed association with Aiwa would have been in effect and the company's viability would have been assured, because of heavy debts. Despite the company chairman's faith in the company — those on the inside claim to be able to see the light at the end of the tunnel and a very real future ahead — the Treasury feels unable to provide them with the necessary funds to pay for the development of new products and to pay off the debtors.

continued from page 66

sents a successful solution to the problems of c.c.i in the u.h.f. band. With advancing technology, he says, costs may be expected to fall to the point at which adaptive antennas will be used increasingly by the broadcasters, especially when the fourth channel is brought into use.

Antenna work in ESA

Three years ago at the last IEE antenna conference, the European Space Agency's activities, mainly concerning their then new payload antennas, were described. Since then, several of these activities have been completed and new developments have started. A paper⁶ by J. Aasted from ESA reviews the present antenna and propagation activities at ESA.

A major part of ESA's work in payload antennas has been in the development of dual-polarized reflector antennas. This has led to a better understanding of the depolarization mechanism and has also resulted in the development of new antenna types having much improved cross-polarization performance. One example is the off-set reflector antenna which, though previously rejected for dual polarized systems due to its asymmetry, is now a prime contender because of improved feed designs.

In the lower-frequency S and L bands,

reflector antennas become impractical for small beamwidths and array antennas may be preferred. These also allow the use of multiple simultaneous beams. ESA have developed and are now testing an L-band 19-beam antenna system which is to be used for earth coverage from a geostationary satellite. As one moves to the higher frequency bands (11/14 and 20/30GHz) and narrow beam widths ($\frac{1}{2}^\circ$ to $\frac{3}{4}^\circ$) the need arises for improved test ranges because the standard ranges are likely to be increasingly affected by multipath effects. ESA is therefore investigating the near-field measurement technique. Of the three scanning methods the Agency has chosen to develop the spherical technique and an experimental facility is now being set up at the Technical University of Denmark.

ESA is presently developing a standard cardioid type radiator for S-band and are anticipating moving all telemetry and telecommand into this band, or even higher. The antenna is designed to be boom-mounted on top of a payload. They are also planning to develop reflector-type, multiple beam antennas with contoured coverage for the higher 20 and 30GHz bands. The realisation of these antennas will require tight tolerance reflectors and a new class of feed systems. Work on this has already been started and that will be

intensified in the next two years.

So far, ESA's work in propagation has concentrated on the 11/14GHz bands. Data from ten radiometers stationed across Europe have been analysed and have formed the basis for the European propagation model which will be verified with direct measurements from OTS. The Agency is also developing radiometers for the 20 and 30GHz bands. At the higher frequencies, however, says the ESA paper, deep fades may occur which radiometers are unable to record. Because of this a propagation experiment is planned using H-SAT, which will carry a beacon for the purpose. In addition, ESA will be carrying out diversity experiments to try to solve the fading problem.

To be continued

References

4. Moxon, L. A., Radio Society of Great Britain, High-frequency antennae and propagation modes in relation to the amateur service, pp 83-86, Part 1.
 5. Windram, M. D., Independent Broadcasting Authority, Crawley Court, Winchester, Adaptive antennas for u.h.f. broadcast reception, pp 30-35, Part 1.
 6. Aasted, J., European Space Agency, Netherlands, Antenna and propagation work in ESA, pp 230-231, Part 1.
- All IEE Conference Publication Number 169, Antennas and Propagation, from International Conference on 28-30th November, 1978.

Radio communication in tunnels

A note on the "split-path" paradox.

by K. F. Treen

From time to time, suggestions are made that radio propagation, (particularly with reference to the private mobile radio-frequency spectrum) throughout the length of tunnels in which bends introduce excessive losses, could be achieved by receiving the signal with a suitable antenna at the end of a straight portion and then connecting this antenna to a second antenna which would re-radiate the signal in the required direction. In terms of propagation losses, conventional available powers and antenna gains, this is not a very practicable arrangement.

PASSIVE COMMUNICATION in tunnels is not comparable to the passive reflector systems used in some microwave links, either as the main reflectors in a line of sight link, where they are used as means of avoiding feeder losses, or en route to avoid obstacles present in the shortest path. In these cases the wavelengths are small and reflector sizes are very large in terms of wavelength.

For the purposes of this note, propagation loss is calculated as a free-space attenuation which, between isotropic antennas, is $(4\pi r)^2/\lambda$ where r is the range and λ the wavelength in the same units.

This expression is optimistic for most tunnel conditions and available wavelengths; in practice, signal strengths would be much less than calculated.

Consider a tunnel of length r with a transmitter at one end and a receiver at the other. If the transmitter effective radiated power (e.r.p.) into the tunnel is W_t watts and the receiver antenna gain is G_r , the tunnel end to end attenuation considered as free space, is given by $(4\pi r)^2/\lambda$. With a transmitter e.r.p. of W_t watts and a receiver antenna gain of G_r , the r.f. power fed to the receiver is given by

$$W_t \times \left(\frac{\lambda}{4\pi r} \right)^2 \times G_r \text{ watts} \dots (1)$$

Assume a bend in the tunnel at a point distant l from the source and around which significant propagation will not take place. At this point insert two auxiliary antennas, one directed normally to the transmitter and the other to

the receiver. Let the two antennas be connected together with a lossless feeder cable and let their respective gains be G_1 and G_2 .

The r.f. power at the output of the auxiliary receiving antenna is

$$W_t \times \left(\frac{\lambda}{4\pi l} \right)^2 \times G_1 \text{ watts.}$$

This power is fed without loss to the auxiliary re-transmitting antenna, giving an effective re-radiated power of

$$W_t \times \left(\frac{\lambda}{4\pi l} \right)^2 \times G_1 \cdot G_2 \text{ watts.}$$

The distance to the final receiver is $(r-l)$, and the power fed to the input of the receiver is given by:

$$W_t \times \left(\frac{\lambda}{4\pi l} \right)^2 \times G_1 \cdot G_2 \times \left(\frac{\lambda}{4\pi(r-l)} \right)^2 \times G_r \text{ watts} \dots (2)$$

Equations (1) and (2) represent the 'direct' (i.e. directly through a straight tunnel) and the 'indirect' signal strengths respectively. It is clear that equation (1) represents a power greater than equation (2). Dividing (1) by (2) we get:

$$\frac{16\pi^2 l^2 (r-l)^2}{G_1 G_2 \lambda^2 r^2} \dots (3)$$

Applying practical values to a system in which the receiver is mobile and is situated at the end of the tunnel distant r from the transmitter.

Let frequency = 450 MHz; hence wavelength $(\lambda) = 0.67\text{m}$.

Let length of tunnel $(r) = 2000\text{m}$.

Let bend be at 1000m $(l = r/2)$.

Let transmitter e.r.p. = 7dBW. (5W)

Let receiver antenna gain $(G_r) = 3\text{dB}$. (2:1)

Let back to back antenna gains each equal 8dB. (6.31:1)

Then from equation (1), for the direct case, the r.f. power input to the receiver is equal to:

$$5 \times \left(\frac{0.67}{4\pi \times 2000} \right)^2 \times 2 \text{ watts.}$$

= 7.1×10^{-9} watts, or -81.5dBW, a very adequate signal strength.

Equation (2) gives the result for the indirect case as:

$$5 + \left(\frac{0.67}{4\pi \times 1000} \right)^2 \times 6.31 \times 6.31 \times$$

$$\left(\frac{0.67}{4\pi \times 1000} \right)^2 \times 2 \text{ watts.}$$

= 3.21×10^{-15} watts or -145dBW, too weak for reliable operation.

The difference of 63.5 dB is given directly by equation (3). It is also apparent, by inspection of that equation that the difference value is maximum when $l = r/2$. As the point at which the intermediate antennas move from the centre $(l = r/2)$ point in either direction, the r.f. input power to receiver increases, at first fairly slowly but as either end is approached the increase is asymptotic to 6dB as the distance to the ends is halved. In order to restore the 'direct' condition it would be necessary to interpose an amplifier with a gain given by equation (3) between the pick-up and re-radiating antennas (and of course, effectively decouple them from each other), or alternatively increase the gain of these antennas such that the total sum gain is:

$$2 \times \left(\frac{G_1 G_2}{2} \times \frac{16\pi^2 l^2 (r-l)^2}{G_1 G_2 \lambda^2 r^2} \right),$$

which reduces to:

$$\frac{16\pi^2 l^2 (r-l)^2}{\lambda^2 r^2} \dots (4)$$

Applying the values for r , l and λ given above, we get the sum gain as

$$\frac{16\pi^2 \times 1000^2 \times 1000^2}{0.67^2 \times 2000^2} = 8.79 \times 10^7 = 79.4\text{dB.}$$

Thus each antenna would need to have a gain of approximately 40 dB, generally an impracticably difficult task in most tunnels. As the frequency is raised (hence generally falling outside the band allocated for private mobile radio purposes) the production of high gain antennas becomes easier; on the other hand, the free space attenuation increases. In some rare cases losses may be decreased by the generation of waveguide modes of propagation but these could not normally be relied upon.

Wireless World — a decade of growth

If we consider raising the frequency by ten times to 4500 MHz. ($\lambda = 0.067\text{m}$) and maintaining the same received power as in the direct case, (7.1×10^{-9} watts or -81.5 dBW) with the same transmitter e.r.p. of 5W (7dBW) we would need a receiver antenna gain of 23dB instead of 3dB, an almost impossible value to achieve for an omnidirectional mobile antenna. Alternatively, the e.r.p. of the transmitter could be increased by 20 dB to 27dBW (500W) by using say, a 1 watt transmitter and a parabolic antenna of 0.67 metres diameter which, at 50% efficiency, would provide a gain of 27 dB. For the indirect case at 4500 MHz, we can again apply equation (4) to ascertain the sum gain of the intermediate antennas. Substituting the values as before we get

$$\frac{16\pi^2 \times 1000^2 \times 1000^2}{0.067^2 \times 2000^2}$$

$$= 8.79 \times 10^9$$

$$= 99.4\text{dB.}$$

Thus each of the two antennas would need a gain of about 50dB which at 50% efficiency would entail a paraboloid of 9.54 metres diameter, a somewhat impracticable value.

In conclusion, what is shown above is not that radio communication through tunnels is impossible, (adequate systems either as separate entities or in association with external mobile radio schemes have been achieved) but that sufficient illumination by the radio wave cannot be provided simply by passive means. In many cases, radiating cables would provide the most satisfactory solution with a minimum of design problems and, when used with repeaters, would cater for almost any configuration.

A short curriculum vitae of Mr Treen appeared in the issue for August, 1978, in which he was the author of an article on a proposed radiating cable system.

More and more people are reading *Wireless World*. This is clear from our latest circulation figure, which has just topped the 70,000 mark. According to the Audit Bureau of Circulations the average number of copies distributed in the twelve months ending 31st December, 1978 was 70,125 per issue. This was an increase of 1,608 copies per month on the corresponding 1977 circulation of 68,517.

And here we are not merely noting an isolated increase for one particular year. If you look back over the past decade, this increase proves to be in fact one more step in a continuing process of growth. In 1968 we had a circulation of 48,401 copies per month. The graph then shows a steady overall climb with fluctuations of only about a thousand from the ideal smooth curve — giving an average increase over the whole decade of 2,172 copies per month each year. And remember the journal is paid for by its readers, it's not a "give-away" as many are. People who buy it really need it.

These figures can only mean that *Wireless World*, now in its 68th year of publication but unwithered by age, is still doing its job. It is not only keeping

its long-standing professional and general readers, some of whom have taken the journal for thirty years or more, but continuously attracting new readers in the highly competitive and increasingly specialized field of electronics publishing. On average more than one person reads each copy, and the total readership now amounts to 215,000.

An important aspect of this growth is the continuing increase in *Wireless World's* overseas circulation, which is now over 23,000 per month — a figure greater than the total circulation of some of our contemporaries in professional electronics publishing. Apart from the major groups of readers — in all countries of Western and Eastern Europe, all states of the USA, in the USSR and China, in most countries of the African and South American continents, not forgetting Australasia, Scandinavia, the Indian sub-continent and South-East Asia — you will find them in unexpected places from Afghanistan to Haiti, from Ethiopia to Iceland, from Alaska to Sri Lanka and on small islands like the Faroes, the Azores and those in the Pacific and Indian Oceans. The "World" in our title really does mean what it says!

BOOKS RECEIVED

BSO Directory '79, edited by Linda Holland, is compiled by the people who produce the journal *Broadcasting Systems and Operation*, and is a comprehensive guide to broadcasters, equipment and services. The book is in four parts; the first being a list of the world's radio and television authorities and stations, with addresses. Part 2 contains the names, company executives, agents and activities of companies supplying equipment and services. The third part is a listing of equipment and services, classified by type, with the names of relevant companies in each field, and the final section contains brief descriptions of the equipment produced by the world's manufacturers. Each section is indexed.

The 208-page book is extremely comprehensive, being the first such compilation to

appear, according to the publisher, who expresses the intention to expand the listings in forthcoming editions. The publishers are B.S.O. Publications Ltd, P.O. Box 1, 41 High Street, Wivenhoe, Colchester CO7 9EA, and the price is £25.

Elements of Computer Science, by Glyn Emery, with assistance from David Bale, is designed to accompany a first-year course in computer science. The treatment is such that no knowledge of computing is necessary to take full advantage of the text: the very basics of logic and a logical view of problem solving are treated in three chapters, as are the various number systems. Programming is built up from a discussion of the structure of data and its control, through programming and operating systems, to a section on the structure of languages. Although the main part of the book is concerned with digital computing, a section on the analogue variety takes up the final chapter. Exercises are

provided after each chapter. Glyn Emery is Professor of Computer Science at the University College of Wales, Aberystwyth. The book is published in paperback by Pitman Publishing Ltd, 39 Parker Street, London WC2B 5PB, at £2.95.

Man-made Radio Noise, by Edward N. Skomal, analyses and characterises virtually all the sources of man-made interference, found in industrial society. Each type of noise source is given a chapter (automotive, power lines, etc) and is then related to other sources in an analysis of composite noise in metropolitan areas, at the surface. This exercise is then repeated to give a picture of composite noise at specific altitudes over large cities. The book is extremely comprehensive in coverage and the treatment is thorough and mathematical. Copious references are provided. Costing £16.15 in hard back, this 342-page book is published by Van Nostrand Reinhold Company Ltd, Molly Millars Lane, Wokingham, Berks.

MOBILE CB DANGERS

If Mr Riley is trying to argue a case against mobile c.b. based on danger to human life (January letters), he should produce more convincing evidence than the results of artificial tests conducted by a university research group. I have no statistics to prove it, but I doubt if radio-controlled mini-cabs, which have both inexperienced drivers as well as mobile radio operators, show an excessively high accident rate due to use of the radio in heavy traffic.

Surely only the silliest driver will attempt to operate a radio while negotiating a hazard, which requires both hands to be on the steering wheel? The tests referred to by Mr Riley, would, I am sure, produce even more alarming results if the drivers concerned were told to light a cigarette or change a tape cassette, while negotiating the obstacle course set for them by the university.

The point which should be made about mobile c.b. radio is how many lives could be saved by intelligent use of it on the roads. I am at present in correspondence with the Home Minister over this aspect of c.b. radio, in connection with the recent tragic pile-ups on the M1 and M5. I firmly believe that prior warning could have been given in time to those drivers involved if some had been equipped with mobile c.b. The time factor is vital in fog and, under these circumstances, any driver, especially truck drivers, would have the c.b. open all the time; therefore, they would be prepared for advance warning of an accident from any c.b. equipped vehicle a mile or so ahead. This would allow time to take evasive action and also warn other drivers in the vicinity, visually and on the radio, of the situation.

Mr Riley states that police "frown on" the use of mobile c.b. If this is the case, what then is their reaction to the carnage of a motorway pile-up, which often includes their own men and vehicles? Police patrol cars on the motorway are just as vulnerable as other vehicles in fog, and are equally helpless in either warning or being warned by other drivers, or of summoning assistance if their vehicles are immobilised in the accident area.

In my opinion, the time has now come for Chief Constables to stop frowning on c.b. and to start listening instead to the conclusions of their own motorway patrolmen; and then make public their views of the benefits that mobile c.b. radio could bring to motorway safety and the saving of human life.

Tanlaw
House of Lords
Westminster

Whilst Mr Riley makes some valid points with the help of the OU (January letters) he also makes some presumptions, e.g. that a driver using a "c.b." would continue to discuss the evening's menu with his wife, etc., and simultaneously attempt almost impossible trials of judgement on the road. Also Mr Riley feels that accident statistics would suddenly rise "if dozens of inexperienced c.b. users suddenly [took] to the road." This assumes that inexperienced c.b. users would also be inexperienced drivers. Tell that to new taxi drivers.

May I state that, notwithstanding my name, I am English, white and a road user, also I value my life and others. Furthermore, I have had several years' experience on US roads, notably, with about a "dozen" truck drivers who drive the road crew and p.a. equipment belonging to the rock-and-roll group that I work for between every major



USA city (many, many thousands of miles). Invariably, if they suspected danger ahead (or behind) they immediately dropped the 'mic' in their laps and coped with the situation, if any, then recontacted. Most importantly the same reaction was seen by myself in the many 17-21-year-olds that I have as friends in Los Angeles and Miami. Incidentally my own (hired) car had everything but c.b. and I didn't miss it.

Mike Januszkiewicz
Ipswich
Suffolk

TELETEXT CHARACTER ROUNDING

My November 1978 article on the character rounding board IV for the *Wireless World* decoder mentioned that the power unit originally supplied with decoder kits could not provide the additional 530mA needed for the new board. (Current and very recent kits have an uprated power supply which can provide the extra, as long as the regulator heat sinking is sufficient.)

Since the board was originally designed, low power Schottky t.t.l. has become available at prices only marginally higher than the standard type. With the same or only slightly lower speeds, and a fanout of five into standard t.t.l., the low power Schottky (L.S.) can in most cases replace it directly with an appreciable saving in current consumption.

Board IV built with L.S. i.c.s apart from IC₂₀₈ (74121), draws 230mA against 530mA for the standard (the r.o.m. accounting for 50mA in both cases), the only change necessary being an increase in C₂₀₂ from 1n to 1n5.

On board III the current fell from 570 to 270mA with four i.c.s having to stay as standard — IC₁₀₄ (74150) not available as L.S., IC₁₂₅ (7473) where the L.S. version has different logic, and IC₁₀₅ (74157) and IC₁₂₅ (7408) which drive the television set and video interface.

This means that the two L.S. boards together draw less than the standard board III, and can therefore be fed from the original power unit, saving the cost and inconvenience of renewing or adding to it, while with the new larger one 600mA at least is left available for possible future extensions, such as ultrasonic remote control. It is understood that the kit supplier intends to offer L.S. i.c. sets as an option for these two boards.

On board IV the timing component values for the odd/even field detector monostable IC₂₀₈ were derived from T.I. data for the

74121 and it has been found that with other manufacturers' products the value of R₂₀₂ may have to be changed if the character rounding jitters or does not work.

Owing to a typographical error the reference "Broadcast Teletext Specification — BBC, IBA, BREMA — September 1976" was omitted from the list of references at the end of the article, and some of the reference numbers in the text are therefore wrong. Also the source resistance of a t.t.l. output in the high state is printed as 190 ohms instead of 130, and the phrase "two r.a.ms in parallel" in the centre of p.49, should read "two r.o.ms ...".

J. H. Hinton
Cambridge

DISPLACEMENT CURRENT

I am slightly alarmed by some of the statements in the article "Displacement current — and how to get rid of it" (December 1978). I suggest that there would justifiably be an outcry if the authors were to have written paragraph 5 as follows ...

Since the inductance has now become a transmission line, it is no more necessary to postulate 'magnetic flux' in an inductor than it is necessary to do so for a transmission line. The excision of 'magnetic flux' from electromagnetic theory has been based on arguments independent of the classical dispute ... (an apparent negation of Faraday's law of Induction).

Displacement current (without the inverted commas) is as real and justifiable a concept as conduction, or convection, current in charge transport — it is directly analogous to the time differential of magnetic flux in magnetic theory ($\partial \vec{D} / \partial t$ instead of $\partial \vec{B} / \partial t$ if you want to be precise). Displacement current is neither a mathematical convenience nor an artefact of a faulty model for a capacitor, it is a fundamental part of Maxwell's equations.

To those who have designed high frequency networks, interchanging between a capacitor or inductor and a transmission line is common practice: the inductors and capacitors used actually look like short transmission lines. Such circuits can be analysed using either of two methods; the discrete approach in which case each line has an equivalent inductance and capacitance or the distributed approach in which case characteristic and terminating impedances are important. Paragraph 4 could be misleading because it confuses the lumped and distributed techniques: a transmission line used as a capacitor, or a capacitor appearing as a transmission line, must have some inductance which is inherent in the component construction. This will become clear in the next paragraph.

Consider an ideal transmission line. For analysis this has a few useful parameters; L — the series inductance per unit length, C — the shunt capacitance per unit length, Z_0 — the characteristic impedance ($= \sqrt{L/C}$), and v — the characteristic velocity ($1/\sqrt{LC}$). (And where do we get these parameters from? Why, of course, from electromagnetic theory using $\vec{B}, \vec{H}, \vec{E}, \vec{J}$, and naturally enough \vec{D} the electric flux or displacement vector.) The impedance measured at the end of an open circuited transmission line of length d is simply $Z_{in} = Z_0 / j \tan(\omega d/v)$. But if $(\omega d/v)$ is small, a condition of lumped circuit analysis, we can expand the tan term to obtain

$Z_{in} = Z_0(j\omega d/v) + \frac{1}{2}Z_0(j\omega d/v)$. Using the transmission line parameters this gives $Z_{in} = 1/j\omega(dC) + j\omega(dL/3)$ which can be interpreted quite easily as a capacitor and inductor in series. To me that would seem a very plausible mechanism for an internal series inductor in a capacitor.

At 'low frequencies' a capacitor may well be a good equivalent circuit for a particular form of transmission line, but at increased frequencies the series inductance must be considered: eventually we must switch to a distributed analysis, otherwise we are going to be barking up the wrong tree in the wrong ball park. For digital systems where harmonics extend into the GHz region very careful consideration must be given to distributed effects in what are nominally lumped components.

P. I. Day
Maidstone
Kent

The authors reply:

We would like to make three points which we hope will clear up any misunderstanding that Mr Day has over the statements we made.

1. He wrongly assumes that we say inductance does not exist. Series inductance does not exist as a separate entity, but distributed inductance does, linked to distributed capacitance as a measured property of a transmission line defined as characteristic impedance.

2. We are considering an ideal step response of a component and the inclusion of frequency in the discussion is making an unnecessary complication.¹

3. If Mr Day believes that you can swap "magnetic flux" with the displacement vector (current) then where does this exist when a step is propagating down a transmission line?

I. Catt, M. F. Davidson and D. S. Walton

Reference

1. Interconnection of logic elements, *Wireless World* June 1978, p. 61.

FERRITE ROD AERIALS

In his article in the December 1978 issue Professor Sutcliffe refers to the ferrite rod as "... collecting and concentrating the radiated magnetic field and channelling it through a coil wound round the middle of the rod". He states that this approach is strangely unrewarding although it has provided a challenging exercise in field theory and mathematics.

I am still looking for a lucid explanation as to the manner in which ferrite rod receiving aerials and, for that matter, dielectric receiving aerials can achieve gain. It is easy to get a physical picture of say a parabolic dish several wavelengths in diameter and placed normal to the direction of the transmitter acting as a collector whose aperture is effectively that derived from its geometry and concentrating the field at the focus. Nothing utterly complicated is done to the electromagnetic wave except possibly some shadowing for a distance behind the dish. Even a half-wave dipole or a Yagi array have a physical aperture of which one can conceive reasonably easily but when one considers the ferrite rod aerial used in many receivers today it is difficult to grasp the means by which an oncoming wave becomes aware that it is to be intercepted by some-

thing that is physically small in relation to its alleged effective aperture.

Does the wave, once it finds itself in the presence of permeable or dielectric material, somehow signal back to those adjacent portions of the oncoming wave that they have to 'concentrate' and, should this take a finite time, could one consider that a signal comprising a series of very short pulses with complete gaps in between the pulses would be received by the ferrite rod aerial with no aerial gain being achieved?

Perhaps I have got it all wrong and the answer is associated with the ratio of wavelength to the comparatively small physical size of the ferrite rod aerials.

The concept of a ferrite rod or dielectric aerial as a transmitter conjures up a somewhat different picture; the 'concentration' is there at the beginning. Perhaps the reciprocity theorem is not quite right after all.

K. F. Treen
Totteridge
London N20

MILITARY ELECTRONICS

Your admirable editorial in the January issue glosses over the real dilemmas which face the practitioner of electronic engineering. The first is that military and civil developments are tightly enmeshed — or optimistically, there has been a good deal of beating of swords into plough-shares. An obvious example is radar: this was originally a military development but now forms the essence of air traffic control, maritime navigation and checking the speed of road traffic. The Loran navigation system grew out of devices to aid bombing missions and Omega has obvious military potential for the USA. There is little difference between a 'spy-in-the-sky satellite' and a 'weather satellite'. The initial war-time urge to develop powerful electronic computers was based on various military needs; but the EMI brain (or body) scanner would not be possible without computer technology. The progressive miniaturisation of computers has made it easier to put adequate navigational computers in aircraft, rockets and space vessels, whether civil or military; and at the present time microprocessors are finding industrial use so that our government says that the future of British industry depends on its learning to use microprocessors.

So long as all the large electronics firms are substantially involved in military work, the ordinary citizen is expected to acquiesce in it. Society has always tolerated a very small minority of drop-outs, whether monks in the mediaeval past or hippies in the present day, but it cannot continue to function unless most of its members accept its norms. (Of course it may be argued that it should not continue to function.) A few can take refuge in university work, but even here one suspects that the funding of research may sometimes be influenced by anticipation of military advantage. Very few of those who have developed expertise in electronics will be prepared to scrap the lot because they regard some of the applications as evil. As the physicist Max Born wrote*: "Science has undoubtedly two aspects: it can be regarded from the social standpoint as a practical collective endeavour for the improvement of human conditions, but it can also be regarded from the individualistic standpoint, as a pursuit of mental desires, the hunger for

knowledge and understanding, a sister of art, philosophy, and religion."

So should electronic engineers feel a special responsibility about armaments, in the same way that some eminent American physicists felt that the original development of the atom bomb had placed a special responsibility upon them, or should moral and political arguments be left to moral and political organisations? If the latter, is it reasonable for electronic engineers who are probably depending on the armaments trade for half their income (on average) to support organisations such as International Voluntary Service whose long-term aim is to eliminate the need for armaments? What about the short-term effect on employment of any significant reduction in the armaments business? There are no easy answers, but we all need to arrive at some sort of answer.

D. A. Bell (Professor)
Walkington, Beverley,

Yorks

**Natural Philosophy of Cause and Chance*, reprinted by Dover Publications, 1964

Your leader "The death delivery business" in the January issue is most timely. How can one pretend that the world expenditure on armaments is necessary for the defence of democracy when the records of the two super-powers are of expansionism, cruelty and corruption, and when armaments are used in so many countries not for defence but for internal suppression?

When hundreds of millions of people exist on such incomes as £50 per annum can one justify such squandering of the earth's resources?

The military-industrial complexes of the two super-powers have more in common with each other than they have with their respective populations, and one of today's greatest dangers is that if the populations object to these unnecessary expenditures, these complexes may be tempted to indulge in offensive acts in order to justify their own existence and continuation in being.

The left and right wings of society are equally to blame. It is unfortunate that many people delude themselves that they have no responsibilities in this matter because they do not see the results of their handiwork. Responsibility lies not only with those who pull triggers but also with those who drive lorries, type letters and clean offices. Can they not be made to realise that those who would live by the sword must expect to die by the sword? Unfortunately the rest of us also are likely to die by it.

Roy C. Whitehead
Sutton
Surrey

INTELLIGENT MACHINERY

Recently I have been likening a microprocessor to a paralysed person in a wheel-chair, because it cannot itself perform any actions. I now realise that I should have said "a deaf and blind person in a wheel-chair" because a microprocessor cannot itself gather information: it can only manipulate information which is fed to it in machine-readable form. In other words, intelligent machinery (November 1978 editorial) requires sensors and actuators as well as the information processor. It is for this reason that the Electronic Engineering Department of the University of Hull, for example, offers a

degree course in "Instrumentation and Control" as well as the course in Electronic Engineering (which includes a computer option). There is more to automation than silicon chips!

D. A. Bell (Professor)
Walkington, Beverley,
Yorks.

Until his retirement in 1978, Professor D. A. Bell was Professor of Electronic Engineering at the University of Hull. - Ed.

"DID YOU KNOW?"

Epsilon spoils his otherwise interesting article in the December 1978 issue by incorporating several errors.


The inductance formula used to derive his expression for X (p. 67) is the well known formula for a length of straight wire,

$$L = 10.2 \log_e(2l/r) \mu H \text{ from which}$$

$$X = 2\pi f 0.2 \log_e(2l/r - 1) \Omega$$

(f in MHz, all other dimensions in metres. I have used r here for radius - I think D for a radius is highly confusing!)

Fig. 5 contained several important errors. I think the diagram should look like this:

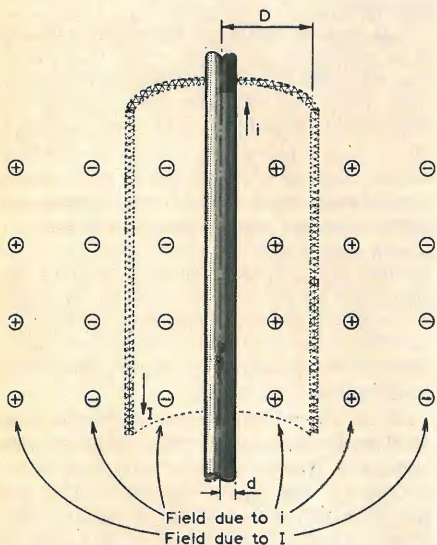

Because of the incorrect drawing, the sentence including "... (but note that this expression is not applicable when x is less than d) ..." became misleading. It is true, however, for the drawing as shown above.


The reason is, of course, that for high frequency currents, skin effect keeps the current to the surface of the centre conductor and hence both i and H are zero within. Likewise, in the outer conductor, skin effect keeps the currents to the inside surface of it.

The author explains the zero ground plane current in terms of magnetic effect and mutual inductances. However, a valuable alternative approach is to regard it in terms of field boundaries. The outer conductor forms one boundary (and the inner conductor the other) for both the electric and magnetic fields as in a waveguide. Thus the current on both the conductors forms the field boundary and all of the current flows in these boundaries. Since skin effect keeps the current to a thin inside layer of the outer conductor there can be no field and no current elsewhere. Thus at very low frequencies where the skin depth is thick compared with the outer conductor wall thickness a resistive volt drop will occur along it and current will flow in parallel paths like the "infinite" ground plane.

In the high frequency case, perhaps Epsilon would like to comment on the current route if one end of the braid is open circuit?

One final point concerning ground planes. Even an infinite ground plane has resistance and inductance. The "spreading" resistance around the two connecting points gives it resistance and the flux produced by a current between connecting points gives it inductance.

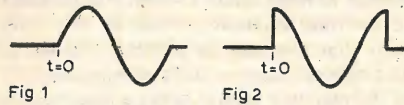Regarding the discussion on audibility of phase errors (Letters, December issue and earlier), a sine wave chopped into short bursts with varied start and stop times cannot be used for audibility tests. If we consider the two extreme cases of Figs. 1 and 2 where the sinewave is switched at zero or at peak,



the spectra of these two pulses is totally different. Fig. 1 has a fall-off as $1/\omega^2$ at high frequencies, whereas Fig. 2 has a fall-off as $1/\omega$ at high frequencies. These are equivalent to 12dB/octave and 6dB/octave.

Any distinction the ear makes between them will probably be the result of the energy rich h.f. spectrum associated with the abrupt level change in Fig. 2 at $t = 0+$. I think this point is the same as Mr Coleman's.

B. J. C. Burrows
Ewelme
Oxford

Epsilon replies:

As expected from previous discussions with colleagues, my article "Did you know?" in the December 1978 issue aroused many comments. Some readers wrote to me concerning the capacitor problem (I shall deal with their comments at a later point in this reply) and others, while not disagreeing with my explanation concerning the screening of the coaxial cable, had clearly had many unfortunate experiences to the contrary.

Regrettably, one or two minor errors did appear as follows. In the second equation on page 67 the r.h.s. should be divided by two, and a 2π should appear in the third equation. d in Fig.3 refers to the inner conductor rather than the outer as originally shown, and on balance I find Mr Burrows's version of Fig.5 more satisfactory. It is hoped that the minor errors did not interfere with readers' enjoyment.

Mr Burrows's letter is concerned mainly with the explanation of coaxial cable screening in terms of field boundaries and skin effects. I have no objection to treating a cable as a TEM waveguide (except that this leaves the original question unanswered), but do raise a protest at the invoking of skin effect as the reason that screening exists. To begin with, skin effect does not cause all the current to flow in the inside of the cable, and for many of the frequency ranges of commercial interest appreciable currents flow on the outside of the braiding. Furthermore, even if currents were limited to the inside of the braiding, the problem as formulated in the article would remain unchanged.

If the outer braid of the cable is broken, the solution to the current flow is clearly geometry and frequency dependent. However, certain observations can be made. The cable is no longer screened, a forward current will flow in the braiding, which will have a potential above ground, and return currents

will flow in the earth plane. Their path (or rather, that of the elementary current filaments) will follow a route which gives the lowest loop inductance, i.e. the current will be concentrated under the projection of the cable onto the ground plane.

Turning now to the capacitor problem, some readers expressed doubt about the given solution, preferring instead to seek comfort in their own explanations. These mainly relied on the presence of losses, caused by resistance or arcing (solutions which I excluded by the reasoning given in the article), or by radiation, which some claimed was always present. Other readers ignored the statement that inductance was intrinsic.

One reader raised the interesting problem of what happens when the capacitance is altered slowly by separation of the plates or by changing the dielectric constant. In such cases the same inconsistency between the answers obtained by the conservation of charge or of energy appears. The explanation lies in the mechanical strain between the plates, which is caused by electrostatic attraction and which changes to account for the energy difference.

Further insight into the original problem can be obtained by allowing the capacitors to have distributed constants and using a configuration which precludes the escape of radiative energy. Consider the circuit shown in Fig.1, which consists of two capacitors made in the form of coaxial cylinders. The cylinders are really coaxial lines, closed at one end but open circuited, and are a good substitution for the familiar tubular capacitors.

One capacitor is charged to a voltage V and is connected to the other to form a completely closed system from which energy cannot escape. The capacitors can operate at superconducting temperatures, so that there are no resistance losses. Sketch the voltage along the capacitors as a function of time.

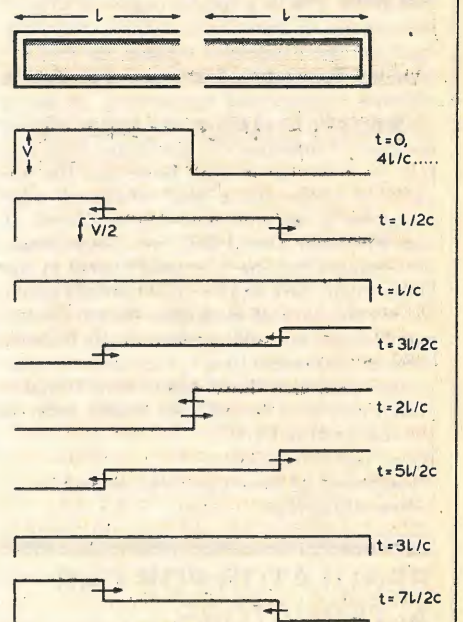


Fig. 1

The answer is given in Fig.1, and to forestall further questions, note that:
(a) Energy and charge are conserved.
(b) The current flow also has the form shown in the figure, with a peak amplitude given by V/Z_0 , (Z_0 is the characteristic impedance of the coaxial structure).
(c) Since current is finite, and in any case can

be made small by making V small, it can always be below the critical level at which superconductivity is suppressed.

(d) By a similar reasoning, arcing need not occur.

(e) There is no escape of radiation.

(f) There is no such thing as a perfect, open circuit, and end effects will modify the square wave shown. However, this does not invalidate the above arguments.

(g) No matter how short the capacitor length, the oscillating nature of the discharge remains.

Point (g) is really the whole crux of the matter, since it guarantees an oscillation which can temporarily store the "missing" energy in inductive fields.

I hope that the more refined model will assist readers in their further understanding of the subject.

FOUR YEAR DEGREE COURSE

I have noted your article entitled "New four year degree course in electronics" which was published in the December issue of *Wireless World*. As you well know, there is considerable interest in the establishment of a variety of four year courses in this country prompted by the UGC's initiative in 'management enriched' courses. Many other universities in the United Kingdom are following a similar route on a free-lance basis and, as you correctly report, Southampton is one of these establishments.

It is, of course, appropriate that any initiative of this kind should be given its place in the technical and academic press but it should not escape the notice of editors of these journals that courses of four years duration have been operated for many years in the United Kingdom. I am not thinking of four year sandwich courses but of genuine four year academic courses such as the one which Hull has made available since the mid-1960s. This is a special degree course in electronic engineering which not only qualifies the successful student for the degree of Bachelor of Science but also a diploma in electronic engineering for those students who have achieved a high academic standard. Consequently, graduates from the four year course in Hull have had the experience of the extra year which we now recognise as an enhanced degree course. It was Professor David Bell, my predecessor, who established the four year course in the Department here and he must take the credit for his remarkable foresight. Relatively minor changes are taking place in the Department at the present time to incorporate in the course structure those component subjects which now find favour with bodies such as the IEE and the UGC.

Alan Pugh (Professor),
Department of Electronic Engineering,
University of Hull.

REGULATOR FOR CAR ALTERNATORS

We would like to draw your attention to the article "Regulator circuit for car alternators" in your August 1978 edition. As electronic design engineers we would like to express our dissatisfaction with the article, and feel very displeased that such a poor design should appear in *Wireless World*. An example of the design deficiencies involves Tr_3 , whose maximum base drive is 140mA,

assuming a 14.4V line. This device (MJE3055) has a specified minimum h_{FE} of 20 at $I_c = 4A$ and $V_{CE} = 4V$, which would produce a collector current of 2.8A minimum. Assuming a nominal 3.5R rotor resistance the device would then try to dissipate 13W. If the machine has a nominal 30A output, the regulator may limit this to about 20A due to the lack of available field current. Neither of these are desirable features although the former will assist R_1 in driving out moisture from the unit!

The maximum collector current of Tr_1 will be 6.3mA, of which 2.7mA will flow in R_2 , leaving a base current of 3.6mA in Tr_2 when it is desired to turn off Tr_3 . The device specified for Tr_2 (2N3053) has a minimum gain of 25 with $I_c = 150mA$ and $V_{CE} = 2.5V$ so the collector current could be 90mA with 50mA still flowing as base current in Tr_3 . This means that a minimum collector current of 1.0A could still flow, with Tr_3 dissipating 11W and the machine output being a minimum of 7A. Assuming a higher gain for Tr_3 to help saturation merely worsens the minimum output figure. This cannot be regarded as satisfactory.

It should be noted also that the worst case specified saturation voltage of a 2N3053 is 1.4V with $I_c = 150mA$, $I_b = 15mA$, so increasing the available base drive to Tr_2 could not guarantee to turn Tr_3 off even with its existing inadequate base drive.

The selection of a nominal zero temperature coefficient is not satisfactory in view of the negative temperature coefficient of the terminal voltage of a lead acid battery. If a part charged battery is being charged from a relatively high output machine, the battery temperature will rise, terminal voltage fall and charging current increase.

The battery temperature will then rise further and so on. This can rapidly damage a battery and possibly cause it to explode, yielding hot concentrated sulphuric acid. This tendency may be exacerbated by the high value of the recommended setting voltage.

Other perhaps more minor problems are also apparent. It is unlikely that the range of setting provided by R_9 will cope with reasonable variations in R_4 , R_5 , R_6 , D_1 , Tr_1 and Tr_2 . The wiper of R_9 may possibly lift off due to vibration and put the machine on to nearly full field and maximum output. Sensing the machine voltage on the ignition switch is prone to trouble arising mainly from voltage drops across the switch, connections wiring and fuses if fitted. No useful indication of the method of selection of C_1 is given. A better design would include circuitry to induce switching. The circuitry to drive the warning light would be unnecessary if a nine-diode machine was used. The extra three diodes provide an additional isolated positive supply, and can be easily fitted to older machines.

We feel that a design which has so many major and minor faults in philosophy, design and component selection should not be published in any magazine, and particularly not in a semi-professional magazine such as *Wireless World*. We wonder how many other designs would prove to have similar shortcomings, if subjected to a similar analysis.

M. J. Newsome and S. A. White,
London, NW10.

Mr Watkinson replies:

The gain of transistors follows a distribution curve where the peak is at the typical gain. The percentage of units having worst case gain is very small, as these units are at the tail

of the distribution. When dealing with the alleged inability of Tr_2 to turn off Tr_3 , statistics tells us that the chances of having two devices which are simultaneously worst case are negligible, being the product of the two probabilities.

On my own unit Tr_3 saturates at 0.3volts. I have not wasted my time measuring the minimum collector current.

I am aware of the temperature coefficient of accumulator voltage, but I cannot see why it is valid to assume that the temperature of the regulator tracks the temperature of the battery as the two are usually found in different places on the vehicle. In my own vehicle the battery is not in the engine compartment, but the regulator is. Having accepted that the two components differ in temperature, adopting a zero coefficient is simple good design practice.

No figures accompany the allegation about the range of adjustment of the pot, but the fail-safe mode is deliberate. The inductive current limiting of the alternator prevents damage on full field. This is better than having no generator at all, particularly at night. A friend drove his van around with full field current for several weeks until he tired of topping up the battery and replaced the regulator.

It is no easy matter to install extra diodes in an alternator. Not only would this render the unit a one-off; impossible to replace away from home, but the extra parts, wiring and connections required would consume more effort than making the trivial but effective circuit I have offered. I had nine-diode machines in mind when I wrote about the tortuous means used to drive a light bulb.

The article clearly shows how to avoid trouble with voltage drops and if the instructions are followed no trouble will result.

The prototype unit was constructed in 1973 and has given no trouble. The battery dates from before this and only requires occasional topping up.

Whilst heralding *Wireless World* as a semi-professional publication Messrs Newsome and White descend to the sensational verbiage of the crusading tabloid in their attack, which does nothing to support their shaky technical criticisms. In closing I should point out that the acid in batteries is dilute only; perhaps this will save me when mine explodes!

J. R. Watkinson.

MICROCOMPUTER BUSES

I would like to take up Mr Aylward's points about the amateur bus standard E-78 (December letters).

I am endeavouring, with the support of the microprocessor manufacturers and a great many professional microprocessor users, to define a microprocessor bus standard for use with the new generation of 16-bit microprocessors. I do not believe that E78 is suitable as a professional standard, for it suffers too many deficiencies to support the devices Mr Aylward mentions. I would like to invite anyone who is interested in this topic to write to me for further information.

Paul L. Borrill
Mullard Space Science Laboratory
University College London
Holmbury St Mary
Dorking
Surrey

Frequency synthesizer — 4

Examples of design using techniques already described

by R. Thompson, M.I.E.E.

Single frequency

Having looked generally at types of synthesizing circuit, three applications have been chosen to illustrate specific designs. The first example is a synthesizer for an atomic standard. The problem is simplified here by approximating the hydrogen maser frequency to 1420.405 MHz, ignoring the last five significant digits. The requirement is to produce a reference frequency at 5 MHz, locked to the accuracy of the maser. This represents the type of synthesizer required for special purpose, single-frequency use. Figure 21 shows a possible arrangement.

Because of the high frequency of the maser the synthesis is organised in two loops. One loop generates 1400 MHz and subtracts this from the maser signal; the other loop synthesizes the residue, or intermediate frequency. An i.f. of 20.405 MHz is suitable to provide the high gain necessary to amplify the maser signal. The 1400 MHz is generated by a $140 \times$ p.l.l. multiplier, followed by a $2 \times$ harmonic multiplier. A single-stage p.l.l. multiplication by 240 is not used because the output frequency would be too high for the divider. The synthesis of 20.405 MHz can be carried out with a simple divider and p.l.l. multiplier.

Variable frequency

The next example has a very different requirement, the provision of a frequency which can be easily varied over a range of many decades, while retaining reference frequency stability. This requirement cannot be met simply by putting several decades of variable dividers in a p.l.l. Apart from the problem of designing a v.c.o. capable of operating over several decades of frequency, there could be severe tuning time problems. The reference frequency would equal the lowest frequency increment, which may be required to be a fraction of one Hertz. The loop bandwidth would have to be at least an order narrower than this so that the tuning time could be very long. There would be wide changes in loop gain as the frequency was changed which would have to be compensated for if a reasonably constant damping factor is to be maintained.

Because of these difficulties the normal design approach to this type of

synthesizer is to cascade synthesizing stages, each stage providing one decade of frequency control. Figure 22(a) shows the basic arrangement.

Selector switch D selects a harmonic of Δf between 0 and $9\Delta f$. This is divided by 10 and added to the harmonic selected by switch C. This combined frequency is divided by 10 and added to the Δf harmonic selected by B; and so on. The final output frequency is therefore a decimal number of times Δf , the digits being readily and independently variable.

The disadvantage of this simple scheme is that the interface between stages is at widely varying frequency. This can be avoided by the arrangement shown in Fig. 22(b). The cascading of stages incorporating 10 times dividers and mixers is similar to the previous scheme. However the frequency added in each stage is the sum of the selected harmonic plus $0.9 f_1$. This means that the output of each stage consists of the variable frequency plus a fixed offset. This offset can be removed at the output of the final stage.


Figure 23 illustrates a typical decade module suitable for cascading in a

manner similar to that shown in Fig. 22(b). The harmonic multiplier and $0.9 f_1$ mixer/generator are combined in the one p.l.l. The fixed portion of the divider ensures that f_1 is generated by the v.c.o. when the selected value of C and D are zero. With the example frequencies shown N_0 is 180. Stepping switch C by one increases the p.l.l. multiplication by one, therefore adding 10 kHz to the output frequency. The output frequency never varies by more than $\frac{1}{2}\%$ and modules can be cascaded at will allowing smaller increments of frequency. An advantage of the divide and cascade system is that loops can all be operated at high comparison frequencies giving low noise and fast tuning time, but the tuning time increment can be made arbitrarily small by cascading more stages and/or increasing the division ratio.

V.h.f. variable

As a final example; a typical v.h.f. communications synthesizer has been chosen. The requirement is for a carrier frequency selectable in 25kHz channels over the range 150-170 MHz. Here the frequency range to be covered is comparatively restricted, allowing the use of a single p.l.l. with a variable divider. Figure 24 (a) illustrates a suitable arrangement

Fig. 21. Arrangement of synthesis to obtain a 5MHz signal locked to an atomic standard of 1420.405 MHz.

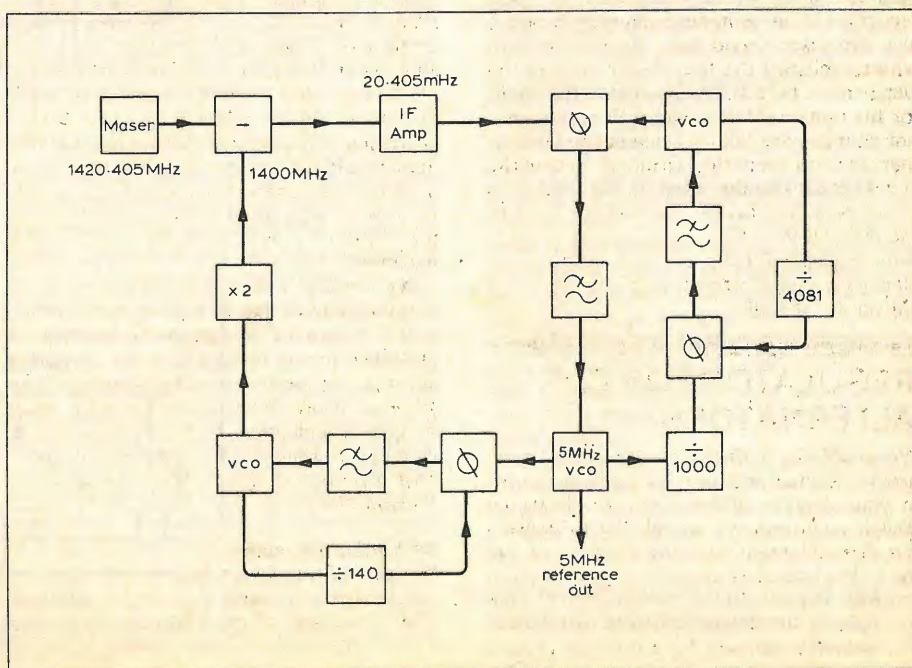

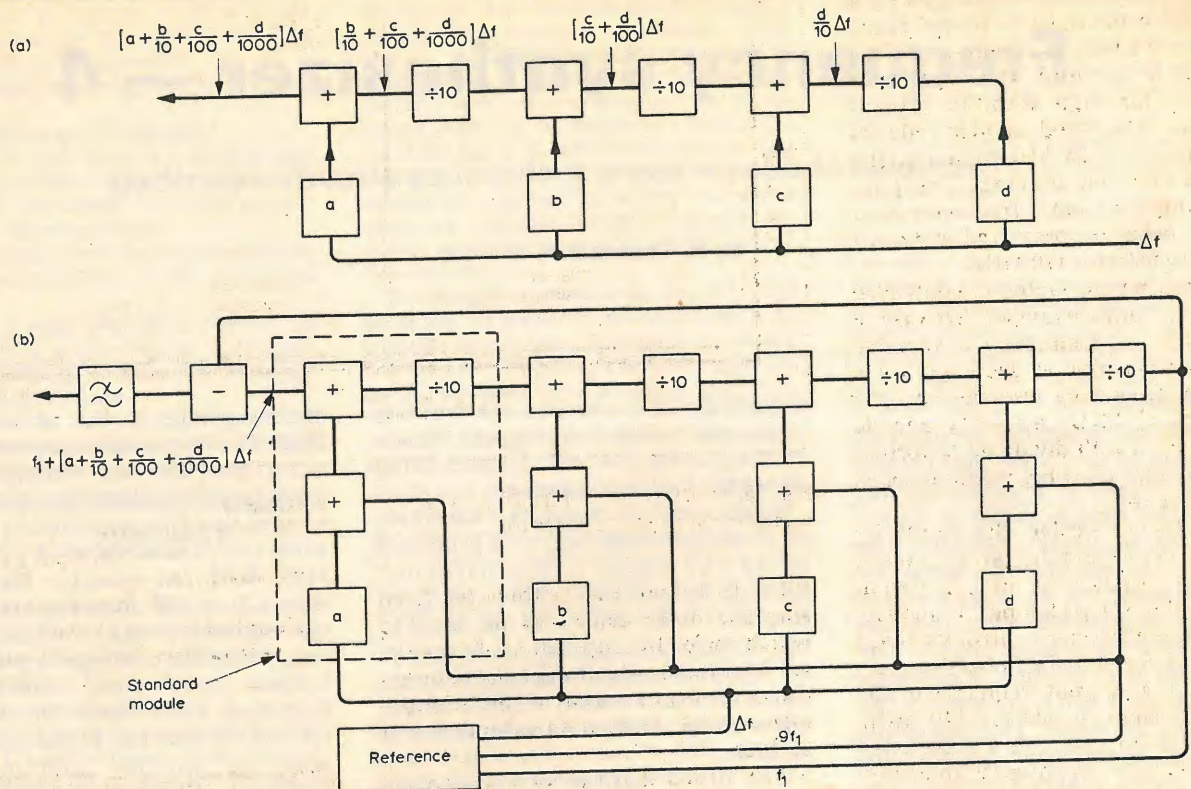


Fig. 22. Cascade of synthesizers to provide a variable-frequency output at (a). Circuit at (b) avoids wide frequency difference between stages.

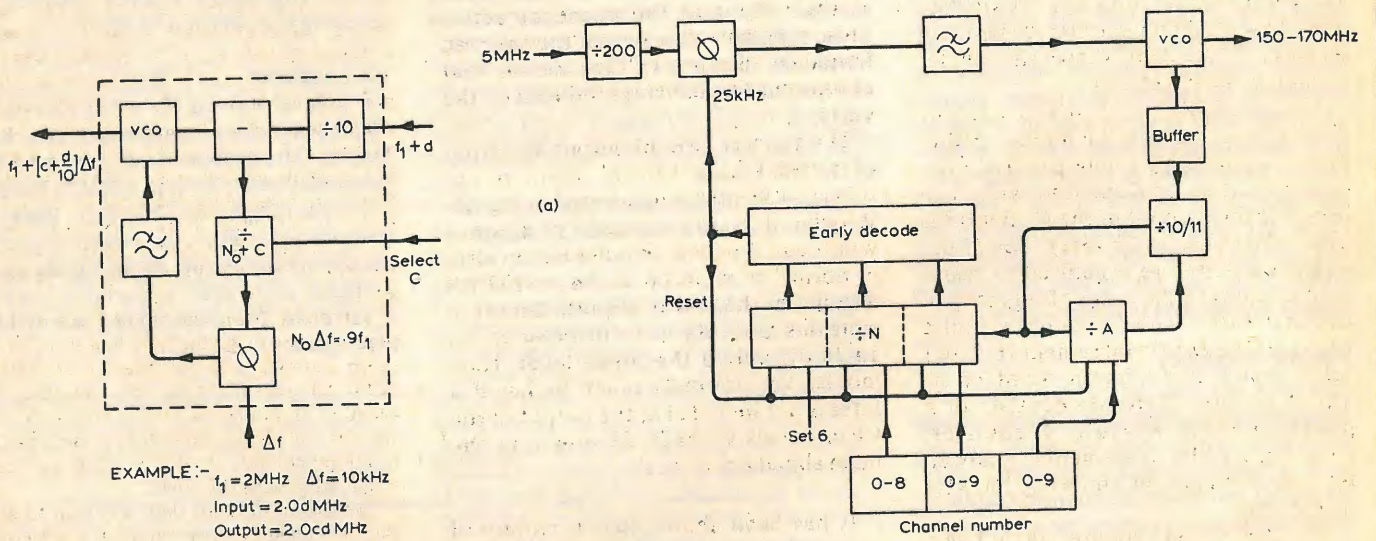


Fig. 23. Divider used in Fig. 22.

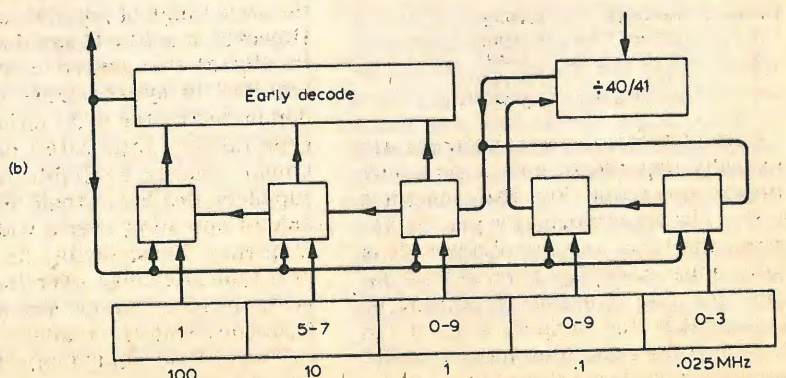


Fig. 24. Variable-frequency synthesizer for v.h.f. communications. Divider is shown at (b).

This is a two-stage synthesizer consisting of a fixed divider followed by a p.l.l. variable multiplier. The reference frequency of 5 MHz is a common choice since it is around the optimum frequency for high stability crystal oscillators. The fixed divider reduces the reference to 25 kHz which is the required channel spacing. The p.l.l. must multiply its input frequency by a factor of 6000 to obtain 150 MHz, increasing to 6800 for 170 MHz.

The multiplying factor is controlled by the p.l.l. variable divider. Because of the high v.c.o. frequency a variable modulus prescaler is used, giving a maximum frequency into the variable divider of 17 MHz. An early decode circuit is used with divide by N portion of the counter, allowing medium-speed logic to be used.

As explained earlier, the divide by 10/11 variable-modulus arrangement allows the output to be incremented in steps equal to the p.l.l. input frequency. The three synthesizer control switches are marked in channel numbers starting with 000 for an output frequency of 150 MHz and rising to 800 for 170 MHz. Each switch programmes a presettable decade divider to the number indicated on the switch, the final decade stage having a fixed programming of 6. All zeros on the switches therefore gives the required division of 6000 for 150 MHz, while 800 will give a division of 6800 for 170 MHz. If the setting switches are required to indicate frequency directly a modified counter design can be used. Figure 24(b) shows the divider portion of such a circuit.

The variable modulus prescaler divides by 40/41 and the higher scaling ratio may possibly allow the early decode circuit to be dispensed with. The least significant digit of the N counter is now 1 MHz (40×25 kHz). The N decades are therefore organised to relate their settings to the output frequency in decimal form. The 'A' counter must count off the 25 kHz increments below 1 MHz; that is a maximum count of 40. The A counter therefore consists of a programmable modulo 4 counter, counting 25 kHz increments, followed by a decade counter counting 100 kHz increments.

The final decade counter again has a fixed preset, this time 1, and the four setting switches will be marked as follows:

switch	markings	scaling
1	5, 6 or 7	$\times 10$ MHz
2	0 to 9	$\times 1$ MHz
3	0 to 9	$\times 0.1$ MHz
4	25, 50 or 75	$\times 0.001$ MHz

Communications synthesizers are normally required to give a very pure output spectrum. For this reason a buffer circuit is normally placed between the v.c.o. and the dividers. This buffer must have high reverse attenuation so that spurious frequencies generated in the dividers are not fed back into the v.c.o. In practice a buffer would also be placed at the output of the

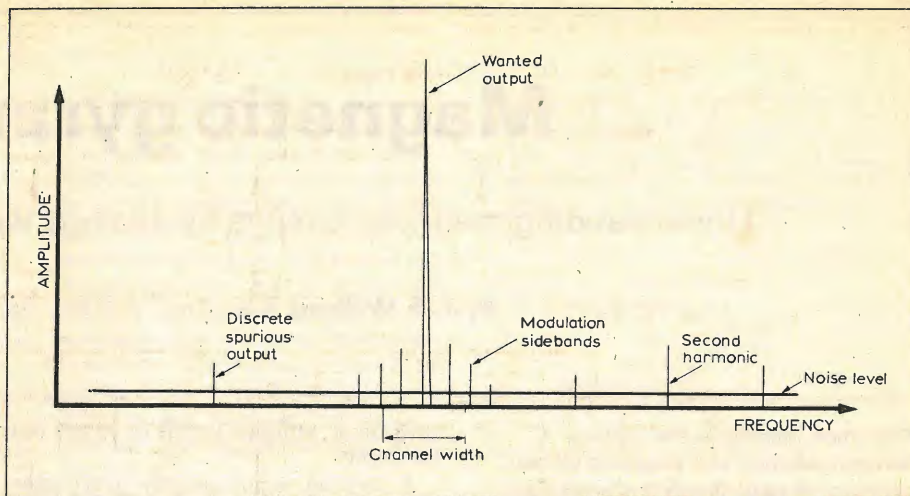


Fig. 25. Synthesizer in Fig. 24 provides this general type of spectrum.

v.c.o. to isolate the synthesizer from spurious noise generated in the load which could effect operation of the loop. Another factor which will help maintain a clean output signal is the comparatively high 'comparison' frequency of 25 kHz. This allows a fairly fast loop which means that the loop will cancel much of the low frequency phase noise generated in the v.c.o.

The loop design will probably be a high-gain, second-order type with a lead lag filter. The high gain will minimise the comparison frequency component at the output of the phase detector. This, supplemented by additional high frequency filtering, will reduce the level of spurious frequencies produced by the v.c.o.

The general form of output spectrum obtained with a typical communications synthesiser is illustrated in Fig. 25. Wideband noise measured in a bandwidth equal to the channel bandwidth, is normally required to be 80-100 dB down on the main signal. Discrete spurious outputs are normally to be 10-20 dB above the noise level. Harmonics are normally much higher if a filter is not included at the output of the v.c.o. Levels of 20-30 dB down on the main signal are typical.

It has been shown that a variety of approaches can be adopted in meeting the requirements of generating one frequency from another. The choice of design approach will vary depending on the wide range of possible applications. However, it is true to say that advances in digital integrated circuits have resulted in synthesizers now being dominated by the p.l.l./variable divider type design. Integrated circuits are cheap, readily available from many suppliers, flexible in their use and capable of operating over a wide range of frequency. These factors have resulted in a radical change over the past five years in the accuracy, size and cast of frequency sources available for application in field equipments and in the laboratory.

References

1. Frequency Synthesis
— V. F. Kropua (Griffin 1972)
2. Phaselock Techniques
— F. M. Gardner (Wiley 1966)
3. Phase-locked Loop Systems
— Data Book. Motorola Semiconductor Products Inc.

SIXTY YEARS AGO

The March 1919 issue was much concerned with getting the amateurs back on the air after their enforced silence during the 1914-18 war. We feared that the government, having taken complete control of wireless communication, would "relinquish their hold very reluctantly, and in their future activities may totally prohibit the erection and the maintenance of a wireless installation by the amateur." A campaigning article in support of the amateurs contained backing up statements by Guglielmo Marconi himself, Professor J. A. ("diode") Fleming and Professor W. H. Eccles, and ended with a call for readers' views. Obviously the amateurs did get back.

But apart from the immediate and the practical, the magazine still had time for the more esoteric and speculative aspects of radio science. Marconi, for example, was asked in an interview for his views on what we now call SETI (search for extra-terrestrial intelligence) but then described as "communication with the stars".

"Senatore Marconi then went on to state that he hoped for communication with intelligence on other stars. Dealing with the question of the language difficulty, he said that although it was an obstacle he did not think it was insurmountable. 'You see, one might get through some such message as 2 plus 2 equals 4, and go on repeating it until an answer came back signifying yes — which would be one word. Mathematics must be the same throughout the physical universe. By sticking to mathematics over a number of years, one might come to speech; it's certainly possible.'

"Certainly communication with the stars, if at all possible, must be effected by wireless telegraphy; and the more recent discovery of a means of magnifying signals to almost any degree places within our hands an instrument of almost infinite delicacy. When so great a scientist as Senatore Marconi talks seriously of these possibilities it behoves the sceptic to consider his position."

Magnetic gyration

Understanding magnetic circuits by analogy with electrical circuits

by J. B. Williams B.Sc.(Eng), A.C.G.I., M.I.E.E.

This article introduces the analogy between electrical and magnetic circuits, covering the basic theory and workings. The analogy is a consistent one and does not fail the modern test of energy which has changed many concepts in recent years. The difference can perhaps best be imagined as if we had for years been treating all our electric circuits in terms of charge, not current, and often electric field strength and charge densities. We abandoned these concepts for circuit work many years ago.

A LARGE PROPORTION of practising electrical and electronic engineers have only a hazy understanding of magnetic circuit theory while being quite familiar with electric circuit theory. So widespread is this among many with very different backgrounds that one is forced to ask whether the fault lies in the presentation of the subject rather than in the people concerned.

Many engineers are used to tackling problems outside their own field, such as those in heat transfer, by analogy with electrical circuits. The subject of magnetism, closely related to the familiar electrical area, has however not been very satisfactorily treated by this method. A confusing system of units has for many years disguised the fact that electrical and magnetic quantities are dimensionally amenable to manipulation by the same mathematics. As explained by "Cathode Ray" in the January 1973 issue, the introduction of SI has removed this first barrier by making the electrical and magnetic quantities relate directly without the use of strange conversion factors.

Most electrical circuit theory is based on the concept of impedances, both resistive and reactive, i.e. those capable of energy dissipation and energy storage. An attempt was made to overcome the lack of a suitable magnetic "impedance" by using the concept of reluctance, which was supposed to be analogous to resistance in an electrical circuit. However resistance is a dissipative component and reluctance, which is related to inductance, is a storage component. This makes for a very poor analogy.

Perhaps the biggest blockage to understanding was the link between the electrical and magnetic circuits. The electrical current links directly into the magnetic circuit but the more useful

parameter, voltage, seems to be left out on a limb.

A method which largely overcomes these problems and opens the way to an easier understanding is due to work by Buntentbach* and others in the U.S.A. but does not appear to have had a wide circulation in this country. It is the aim of this article to introduce this system to a wider readership.

It is necessary to go back to the basic formulae of electromagnetism to see the dimensional similarities.

The first relationship is between magnetomotive force F , the magnetic "voltage", and electrical current

$$F = NI \quad (1)$$

where N is the number of times I that is producing F , or more normally the number of turns. The second relationship is between voltage and rate of cutting of flux ϕ . This is the rate of flux change $\dot{\phi}$ multiplied by the number of times it is linked, i.e.

$$V = N\dot{\phi} \quad (2)$$

The important magnetic property permeability μ is linked to inductance that the magnetic circuit produces

$$L = N^2\mu A/l \quad (3)$$

The term $\mu A/l$ could be called the specific permeability as it is the modified value for that particular shape of magnetic circuit, it is known as permeance, P i.e.

$$L = N^2P \quad (4)$$

As N is a dimensionless number F has the dimension of amps, $\dot{\phi}$ the dimension volts, and P the dimension inductance. The previous reluctance-resistance analogy was based on the similarity of the equations

$$V = IR \quad \text{and} \quad F = \phi S = \frac{\phi}{P} \quad (5)$$

where S is reluctance. However there is another electrical equation of similar form

$$V = \frac{Q}{C} \quad (6)$$

Inductance is a storage not a dissipative parameter and hence so is permanence (equation 4). Thus attempting to use resistance as the analogous property for reluctance, S (the reciprocal of permanence) is not a happy state of affairs. There is a much better analogy in equations 5 & 6, capacitance also being a storage parameter.

Thus the "current" in the magnetic circuit is not ϕ but rate of change of flux $\dot{\phi}$. This means that we now have a looking-glass circuit in which the "voltage" has the dimension amps and the "current" the dimension volts. The main component in this circuit P behaves like a capacitor but has the dimension of inductance. Flux ϕ is seen to be analogous to charge Q .

Another way of checking this is to consider the energy stored in a magnetic circuit.

$$E = \frac{1}{2}LI^2 = \frac{1}{2}PN^2I^2 \quad (7)$$

$$E = \frac{1}{2}PF^2$$

This can be seen to be analogous to the capacitive energy equation

$$E = \frac{1}{2}CV^2$$

Magnetic-electric circuit link

Having explored the magnetic circuit and found it to behave in an analogous fashion to the electric circuit, although it is a looking-glass similarity, now look at the link or mirror itself. The basic equations 1 & 2 link the "voltages" and "currents" on the two circuits. In addition, the magnetic circuit should have a magnetic impedance Z_m ($= F/\dot{\phi}$) and this should be related to the electrical impedance Z

$$Z = V/I = \frac{N\dot{\phi} N^2\phi}{F/N} = \frac{F}{N}$$

$$Z = \frac{N^2}{Z_m}$$

Equations 1 & 2 can be seen to be the defining relations of a Tellegen gyrator with a gyration constant N . This gyrator gyrates a voltage to a current times N , which is the required relationship. An impedance in one circuit gyrates to admittance times N^2 in the other circuit as in equation 8. The gyrator thus fulfills the requirements of the electrical-magnetic circuit link.





*Analogies between magnetic and electrical circuits, by Rudolph Buntentbach. *Electronic Products*, October 1969.

It is worth investigating the simplest magnetic arrangement to gain some understanding of the working of the analogy.

Air-cored inductor

In Fig. 1 if V is a step function, the classic result is obtained in the electrical circuit:

$$V_1 = V \exp -tR/L \quad (8)$$

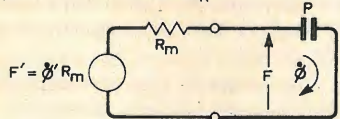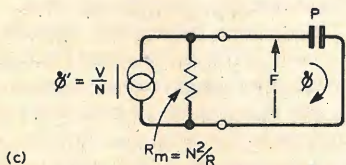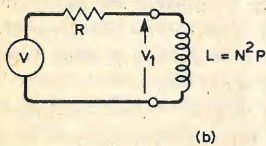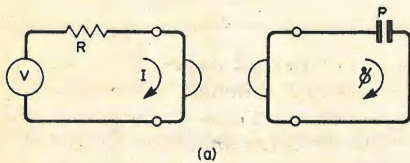

In the magnetic circuit ϕ is also a step function, from equation 2, and hence a similar equation can be derived. This can be calculated directly but a shortcut can be used by using the current-to-voltage source transformation in Fig. 1 (c) and (d). The voltage source and its resistor have the same properties as the current source and its resistor. This can be checked by considering the open and short-circuit conditions for the two sources.

The circuit in Fig. 1 (d) is now familiar and we can write down the expression for when F is a step function:

$$F = F'(1 - \exp -t/PR_m)$$

by analogy to the standard capacitor charging equation. Hence

$$\phi = \frac{F' - F}{R_m}$$

$$\phi = F' \exp -t/PR_m$$

$$\phi = \phi \exp -t/PR_m$$



Converting each term in this equation to its electrical counterpart yields equation 8.

It can also be seen that if a fixed voltage is applied to the inductor (i.e. R is small and R_m large) ϕ is constant and hence the F across P increases linearly.

If V is an alternating source the electrical impedance is $j\omega L$ and hence the

Tellegen gyrator

The gyrator is a theoretical circuit component like a resistor, capacitor or perfect transformer, but unlike these others a simple practical realisation does not exist. It is similar to a transformer in that it links two circuits, but the link is between the voltage in one circuit and the current in the other. For this reason it is useful as the theoretical link between the electrical and magnetic circuits. It is denoted with two semicircles facing each other.

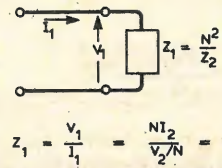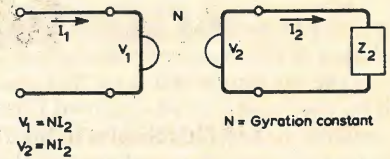

Rules of gyrator behaviour in either direction:

- Voltages gyrate to current sources multiplied by N
- Resistances gyrate to conductances multiplied by N^2
- Inductances gyrate to capacitances multiplied by N^2
- Short circuits gyrate to open circuits
- Components in series gyrate to components in parallel

magnetic impedance is $1/j\omega P$. F and ϕ are seen to be at 90° to each other as are V and I in the electrical circuit.

Nowhere in this discussion of the inductor have we mentioned the flux ϕ . This is the integral of $\dot{\phi}$ and is given by $\phi = PF$

which is analogous to equation 5. In the a.c. case this becomes sinusoidal like the other quantities and is apparently in phase, thus leading to much traditional confusion.

Magnetic cores

At first sight substituting a core of a magnetic material merely gives a much larger value to P (large μ hence large P from equation 3) but iron and ferrite cores are also conductive. Much ingenuity has gone into minimizing the conductive paths, but they still exist, producing as it were small single-turn secondaries distributed a round the core. These can be approximated by one limped component as in Fig. 2.

The conductive path, being an electric circuit, is linked into the magnetic circuit via another gyrator where $N_2 = 1$. This reflects into the magnetic circuit as a series resistance and hence into the

electrical circuit as a resistance in parallel with the inductance.

Transformers

A transformer has another electrical circuit gyrate into the magnetic circuit with constant N_2 as in Fig. 2. More secondaries can easily be added by putting in more gyrators in series in the magnetic circuit. The primary voltage V_1 causes $N_1 \phi$ in the magnetic circuit which in turn causes V_2 .

$$V_2 = \dot{\phi} / N_2$$

$$\therefore V_2 = V_1 N_1 / N_2$$

which is the normal transformer voltage equation.


If V_1 is a fixed alternating voltage then ϕ is a fixed sinusoid and there will be a drop of F_p i.e. $V_1 = N\dot{\phi}$. But at this frequency P has an impedance $Z = 1/2\pi fP$ i.e.

$$\text{i.e. } \dot{\phi} = 2\pi fPF_p$$

$$\therefore V_1 = N2\pi fPF_p \quad (10)$$

But $\phi = PF$
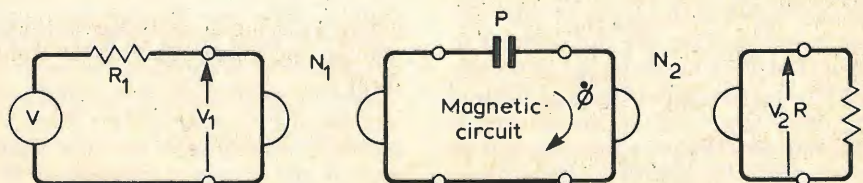
$$\therefore \dot{V}_1 = N2\pi f\dot{\phi}$$



$$\text{i.e. } V_1 = \frac{2\pi N f \phi_{\max}}{\sqrt{2}} = 4.44 N f \phi_{\max} \quad (11)$$


This is the transformer equation and is important in the design of transformers. ϕ_{\max} is the maximum working flux that is to be used and can be obtained from the usually-quoted flux density B , multiplied by the cross-sectional area of the core. However equation 10 can be rewritten

$$V_1 = \frac{2\pi N f P F_{\text{pmax}}}{\sqrt{2}}$$

$$V_1 = 4.44 N f \mu A \dot{H} l = 4.44 N f \mu A \dot{H} l$$

\dot{H} being mmf per unit length. This would be the useful form if the basic magnetic information on the material was presented as a graph of μ against H , or a value of μ was given up to a certain value of H where it starts to fall as saturation begins. This is more in line with standard capacitor practice where the maximum voltage, not charge, is stated.

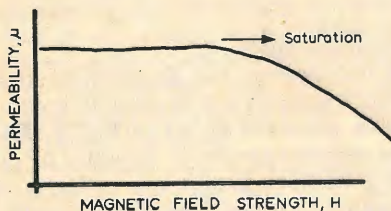Presenting the information in this form means that P can be calculated directly



and hence so can the open-circuit primary current, as $F_p = NI_1$.

Consider now the effect of a load on the secondary.

The load on the secondary can be reflected back into the magnetic circuit, a heavy load being a small resistor. This becomes a large "resistor" in the magnetic circuit. As ϕ is fixed the "drop" F_L must become large and hence F_{total} . The current in the primary must rise in the same way as F_{total} . Thus F is the variable in the magnetic circuit.

Energy

The amount of energy stored in a core is an important factor in d.c. to d.c. converters and in some forms of filter design. It is also important to understand the effect of air gaps introduced into the core.

When a voltage is connected to the terminals of an inductor ϕ flows in the magnetic core. The mmf F developed across P can be determined from

$$\phi t = PF$$

where t is time, which is a restatement of equation 9 for a fixed ϕ . In other words, F (and hence I) rises linearly with time. The energy stored is $\frac{1}{2}PF^2$ from equation 7. If the primary is suddenly open circuited, the energy is left stored in the form of mmf F on a "capacitance" P . An open circuit of the primary converts to a short circuit on the other side of the gyrator. A very large ϕ will thus flow causing a very large primary voltage. This can be coupled to some arrangement that only removes the energy at a high voltage, such as a

breakdown device, and a voltage converter such as the ignition coil of a car has been produced. A high ϕ , corresponding to the high voltage, will flow until the energy stored in the core has been dissipated.

If an air gap is added in the magnetic path it would appear that another component should be added in series in a magnetic circuit is normally shown as total reluctance

$$= \frac{l_1}{\mu_1 a_1} + \frac{l_2}{\mu_2 a_2}$$

$$\text{i.e. } \frac{1}{P_{\text{total}}} = \frac{1}{P_1} + \frac{1}{P_2}$$

which is two "capacitors" P_1 and P_2 in series.

As magnetic materials have a very much larger μ than air it can be seen from equation 3 that only a very short length of air gap is required to make P_1 and P_2 equal. For example a gap of around 0.025mm (1 thou) is required in small commercial ferrite cores.

If we now have two "capacitors" of value P with ϕ flowing through them, twice the energy can be stored in them in the same time. In practice a piece of magnetic material can only be worked to a certain value of F before saturating and hence more energy can be stored in the system.

The value of F across each P will be the same and hence the total F will be twice as large. The current ramp will thus be twice as fast. The two "capacitors" can be gyrated out into the electrical circuit as two inductors in parallel. \square

continued from page 51

The central feature of the approach is partitioning: the material is partitioned into topics that fit within a page-pair with successive pairs grouped together into themes as appropriate; each page is partitioned into smaller units based on the diagram or graph. This feature has been found to be particularly helpful when the work has to be edited or up-dated. It also allows particular pages or sections to be included in other courses, e.g. an appropriate section of one course can be simply transferred to another as revision material.

There remain objections to this new format: it is artificial and constrains the material to fit a particular pattern; it is inappropriate to some topics; the balance between the types of information is wrong. They are not difficult to rebut. The work has to be put into some pattern and the tighter the organisation the more the mind of the author is concentrated. Where a topic cannot be comfortably fitted into a single page-pair it can be extended to two or more. The structure is formalized, as an aid to clarity in writing and understanding,

not as a rigid set of rules. These can be bent as required, to make more room for analysis at the expense of examples or vice versa. After such changes it is important to return to the original structure as the starting point for the next section, so that the benefits of a formal and systematic approach are retained.

Finally, no matter how enticing ideas may be, they must be shown to be practical. The subject area chosen is that of oscillation in the broadest sense, encompassing ramp sawtooth, and triangular wave generators; astables, monostables and diode-pump circuits; RC and LC sinusoidal oscillators; the techniques of frequency and amplitude control. Wherever possible the opportunity has been taken to find unifying concepts, simple equations to cover the largest range of applications and novel and useful applications of the ideas. The merits or otherwise of the new format and of the material presented in it should perhaps be considered separately. There are cases where consciously and unconsciously the

writing has been shaped by the format, but on re-reading this series of articles in their draft form I have no doubt that the format is much more widely applicable. Conversely, the particular viewpoint embodied in these articles could have been expressed in a conventional layout with little change in the detailed material.

No new format is going to replace the standard text book, nor is this one intended to. What it does is to present the reader with an alternative. In writing this series the organization of the work has been a considerable stimulus to new ideas and to the re-arrangement of the old. I hope you will find the results as helpful.

I would like to record my thanks to many colleagues who have helped through discussion and argument to evolve this approach; to those students who have patiently suffered earlier experimental versions of this format; to the editor and staff of Wireless World for their willingness to consider new ideas and their skill in making them work in print. \square

Antenna aiming calculations

Method using a pocket programmable calculator

by Andrew M. Stephenson

TERRESTRIALLY BASED antennas may be aimed by reference to any of several co-ordinate systems, but the one chosen will have to accommodate local operational constraints. If we forget for the moment those fixed and special-purpose antennas such as in permanent microwave relays and large satellite ground stations, which can be established in a relatively leisurely fashion or have the advantage of convenient reference points, the only co-ordinate system that is of real use is that known as the horizon system, whose two co-ordinates are azimuth (a) and altitude (h).

Azimuth, often colloquially referred to as "compass bearing", is taken here as the eastward angle from due north, to the target antenna (0° to 360° , or 0° to $\pm 180^\circ$). Altitude is the angle between the horizontal and the target (0° to $\pm 90^\circ$). See Figs 1 and 2, in which station A is aiming for station B.

The purpose of this article is to describe a set of mathematical formulae with which it is possible to derive a and h , given the latitude (L) and longitude (λ) of stations A and B. The prevalence of excellent scientific calculators now makes their evaluation straightforward. Indeed, the advent of the pocket programmable machine has almost rendered this task trivial, and has permitted additional calculations to be made which formerly were best performed graphically or by means of approximations. An appendix includes a pair of programmes for the Hewlett-Packard HP-25. Owners of the HP-65 and other calculators may also find them useful as inspiration.

The shortest path between two points on a sphere lies along a "great circle", as shown in Fig. 1. The azimuth of B from A is the angle between their great circle and the one that passes through A and the poles.

To avoid wrestling with the generalised mathematics of solid elliptical geometry, it is usual to regard the Earth as a sphere. This is a good enough approximation since the practical discrepancies will usually be swamped by other (e.g., atmospheric) effects. Even so, the derivation of useful formulae for the azimuth is not to be undertaken lightly. There are many versions, all descending by one tortuous route or another from standard spherical geometry formulae, and the ones given

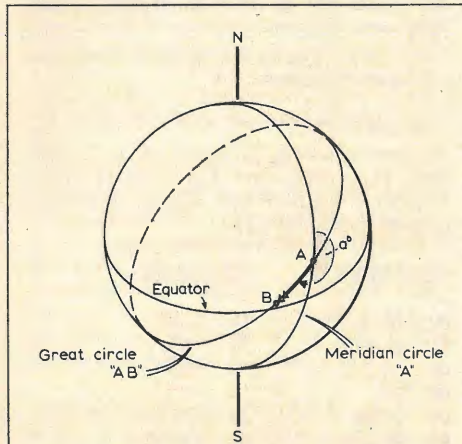


Fig. 1. Illustrating the azimuth part of the horizon system of co-ordinates. The azimuth of point B from point A is the angle a° between their great circle and the great circle that passes through A and the poles.

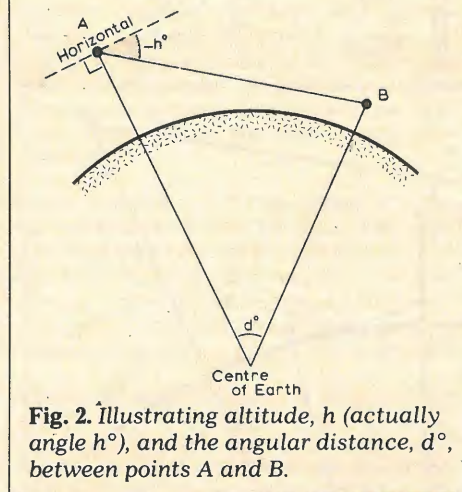


Fig. 2. Illustrating altitude, h (actually angle h°), and the angular distance, d° , between points A and B.

here therefore should not be regarded as definitive. It may be that the reader's calculator possesses a special function that renders them obsolescent; he is encouraged to discover refinements of his own.

The usual approach is first to determine the angular distance between A and B, which is shown as angle d° at the centre of the Earth in Fig. 2, then use it to find a , while saving it for the evaluation of h .

Thus:

$$d = \cos^{-1} \{ \sin(L_A) \cdot \sin(L_B) + \cos(L_A) \cdot \cos(L_B) \cdot \cos(\lambda_B - \lambda_A) \}$$

From this, without further ado or preliminary explanations:

a = Argument (X,Y) where

$$Y = \sin(\lambda_B - \lambda_A) \cdot \cos(L_A) \cdot \cos(L_B)$$

$$X = \sin(L_B) - \cos(d) \cdot \sin(L_A)$$

Stop a moment. Many calculators now have polar/rectangular co-ordinate conversion keys. These can save many programming headaches, such as when X becomes very small compared with Y. Use the function if it is there; otherwise, take care.

One should also beware of two special cases that can arise. The commoner of them is when A is at either of the poles. As a general rule it is safer not to attempt the derivation of meaningless figures, so if this condition arises, reconsider what the "compass bearing" would be. Likewise, if A and B are directly opposite each other on the Earth, one great circle is as good as another, and d can only be 180° . Of these two cases, it is only worth testing for $L_A = \pm 90^\circ$ (or $\cos(L_A) = 0$), when d will probably still be needed and will still mean something.

Having set the azimuth, we still have the altitude to find. This much simpler problem masks a whole set of dependent ones. B may be below the horizon for one reason or another, either because the sea is in the way, or because some mountain happens to be taller than was thought before arrival at the station site. Such details can be checked as follows.

Fig. 3 summarises the situation. Each station has its antenna situated at some height (H_A and H_B) above the nominal surface of the Earth, taken as sea level here. The Earth's radius is R . The altitude of B may easily be shown to be:

$$-h = \tan^{-1} \frac{Y}{X} \text{ where}$$

$$Y = \frac{(H_A + R)}{(H_B + R)} - \cos(d)$$

$$X = \sin(d)$$

Again, use should be made of the rectangular-to-polar function if it is available, lest the calculator be confronted with the awkward problem of one antenna directly above the other (which can happen).

Next, it may be useful to know if B lies below the horizon. As shown earlier, "horizon" can mean two things, either of which can be acutely embarrassing to those users who had not intended to rely on atmospheric refraction to complete the signal path for them.

In the case of the sea level horizon:

$$-h_H = \cos^{-1} \left[\frac{R}{(H_A + R)} \right]$$

(Note that the angular surface distance of the horizon is also h_H .)

In the case of spurious obstructions, we are (or should be) more interested in what clearance (ΔH) exists between them and the line-of-sight signal path. Since these obstructions are usually close enough to appear on the same medium-scale map as A (and possibly B, too), the input values are conveniently expressed as plane measures: surface distance (D_S) and height (H_S).

$$\Delta H = \left[\frac{(H_A + R)}{\tan(h) \cdot \sin(\sigma) + \cos(\sigma)} - (H_S + R) \right]$$

where $\sigma = \frac{180 \cdot D_S}{\pi R}$

If stations A and B are close enough, it may be better to use as d in the altitude formula a value derived from the map surface distance, D_S :

$$d = \frac{180 \cdot D_S}{\pi R}$$

This reduces the effects of errors arising from the original measurement of λ and L , and may obviate the need for

azimuth calculations if the bearing can be taken from the map too. The course adopted will depend on local circumstances, naturally.

Appendix A contains two HP-25 programmes: Azimuth, which generates a and d ; and Altitude, which covers the calculations relating to h , h_H , and ΔH . Appendix B gives some examples of the use of these programmes, and suggests a use for the formulae that may not at first be obvious.

Appendix A: HP-25 antenna aiming programmes

All angles are in decimal degrees unless otherwise shown (D.MS). "(w)" means "write as a value"; other symbols have their keyboard meanings.

Azimuth

Accepts: own long. (λ_A); own lat. (L_A); other long. (λ_B); other lat. (L_B) - all in D.MS. Computes: azimuth (a); angular separation of stations A and B (d).

STEP KEYS

- 00 (R/S)
- 01 g→H
- 02 STO 3
- 03 R/↓
- 04 g→H
- 05 RCL 0
- 06 -
- 07 STO 2
- 08 f COS
- 09 RCL 3
- 10 f COS
- 11 ×
- 12 RCL 1
- 13 f COS
- 14 ×
- 15 RCL 3

STEP KEYS

- 16 f SIN
- 17 RCL 1
- 18 f SIN
- 19 ×
- 20 +
- 21 g COS⁻¹
- 22 STO 7
- 23 RCL 2
- 24 f SIN
- 25 RCL 3
- 26 f COS
- 27 ×
- 28 RCL 1
- 29 f COS
- 30 g x=0
- 31 f FIX 0

- 32 ×
- 33 RCL 3
- 34 f SIN
- 35 RCL 7
- 36 f COS
- 37 RCL 1
- 38 f SIN
- 39 ×
- 40 -
- 41 g→P
- 42 x↔y
- 43 g x≥0
- 44 GTO 47
- 45 RCL 4
- 46 +
- 47 RCL 7
- 48 x↔y
- 49 GTO 00

USE OF PROGRAMME

- #1 (w) 360
STO 4
 - #2 (w) λ_A
g→H
STO 0
(w) L_A
g→H
STO 1
f PRGM
 - #3 (w) λ_B
ENTER ↑
(w) L_B
R/S
display shows a ; y-register and R_7 contain d . If $L_A = \pm 90^\circ$, display switches to integer format.
 - #4 For new 'other station', repeat from #3.
 - #5 For new 'own station', repeat from #2.
- Notes: 1. If $L_A = 90^\circ$, a is returned as 0° . 2. If A and B diametrically opposite each other, an error condition may arise owing to calculator imprecision. 3. Stores R_5 and R_6 are unused.

Altitude

Accepts: angular separation of A and B (d); radius of Earth (R); height of own antenna (H_A); height of other antenna (H_B); obstruction height (H_S) and surface distance (D_S). Computes: altitude of other antenna ($-h$) and of the sea level horizon ($-h_H$); clearance between obstruction and signal line-of-sight path (ΔH).

STEP KEYS

- 00 (R/S)
- 01 RCL 4
- 02 STO 2
- 03 +
- 04 STO +2
- 05 STO 0
- 06 x↔y
- 07 RCL 4
- 08 +
- 09 +
- 10 RCL 7
- 11 f COS
- 12 -
- 13 RCL 7
- 14 f SIN
- 15 g→P
- 16 x↔y
- 17 STO 3
- 18 RCL 2
- 19 g COS⁻¹
- 20 x↔y
- 21 f x<y
- 22 GTO 25
- 23 f PAUSE
- 24 GTO 23

STEP KEYS

- 25 R/S
- 26 STO 1
- 27 R/↓
- 28 RCL 4
- 29 STO +1
- 30 +
- 31 gπ
- 32 +
- 33 1
- 34 8
- 35 0
- 36 ×
- 37 f COS
- 38 f LASTx
- 39 f SIN
- 40 RCL 3
- 41 f TAN
- 42 ×
- 43 +
- 44 RCL 0
- 45 x↔y
- 46 +
- 47 RCL 1
- 48 -
- 49 GTO 25

USE OF PROGRAMME

- #1 (w) radius of Earth
STO 4
- #2 (w) angular sep., d
STO 7
- #3 f PRGM
(w) H_B
ENTER ↑
(w) H_A
R/S

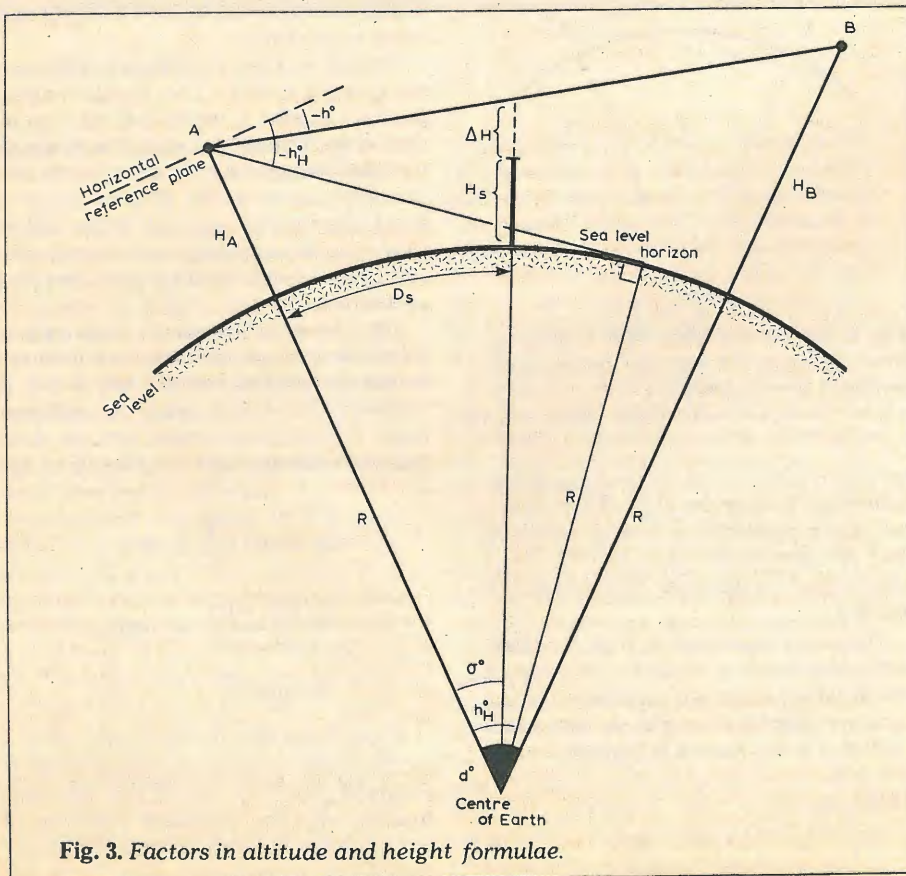


Fig. 3. Factors in altitude and height formulae.

LITERATURE RECEIVED

displays altitude of other antenna, $-h$. If this is below the sea level horizon it will blink; this may be halted by pressing any key. In any case, the "horizon value, $-h_H$, will be in the y-register.

#4 If $-h$ displayed is acceptable, GTO 26 (if not blinking, ignore this GTO operation); if not, then restart at #3 with new heights.

#5 For clearances, continue:

(w)D_s
ENTER ↑
(w)H_s
R/S

displays clearance, ΔH , in same units as H and R.

#6 To repeat for other obstructions, go to #5.

#7 For new station heights, go to #3.

#8 For new d , go to #2.

Notes: 1. R, H_A, H_B, H_S (and ΔH) must all be in the same linear units. 2. Altitudes computed are negative if above the horizontal. 3. Heights are all a.s.l. if positive; negative are below sea level. 4. Radius of Earth used may be local value. 5. Stores R₅ and R₆ are unused.

Appendix B: Examples

An ambitious radio amateur plans to establish a station (at $\lambda_A = -4^\circ 18' 30''$; $L_A = 50^\circ 31' 05''$; and 333.5m above sea level) from which he hopes to contact three other stations as follows:

1. By h.f. to a friend in Melbourne, Australia ($\lambda_B = \text{approx } 145^\circ$; $L_B = \text{approx } -37^\circ 50'$). 2. By u.h.f. to another friend on a nearby hill ($\lambda_B = -3^\circ 59' 08''$; $L_B = 50^\circ 31' 13.7''$; and $H_B = 12\text{m mast} + 445\text{m a.s.l.}$).

3. By S-band microwave link to a geostationary satellite over the Atlantic Ocean ($\lambda_B = -30^\circ$; $L_B = 0^\circ$; and $H_B = 35796660.91\text{m a.s.l.}$).

The radius of the Earth he takes as 6367467.5m, this being the arithmetic mean of the equatorial and polar values. Note that H_B of the satellite is its orbital radius minus this value.

Procedure

(a) He determines the various bearings and d values using the Azimuth programme.

$a_1 = 71.588^\circ \text{true}$ $d_1 = 154.8570868^\circ$
 $a_2 = 89.201^\circ$ $d_2 = 0.2052409307^\circ$
 $a_3 = 211.936^\circ$ $d_3 = 55.04195678^\circ$

(b) Retaining the d values for those applications in which obstructions could be a hazard or where he will want an altitude figure, he uses the Altitude programme to determine $-h$, assuming the extra height provided by his masts as 5m (i.e., $H_A = 5 + 333.5 = 338.5\text{m a.s.l.}$).

$-h_1 = 77.429^\circ$ blinking. (i.e.: approx 77° below the horizontal.)

$-h_2 = -0.195^\circ$. (i.e.: approx 0.2° above the horizontal.)

$-h_3 = -27.241^\circ$.

(c) He estimates that only the u.h.f. link is liable to be obstructed, so he checks the map and sees two possibly troublesome hills. Re-use of Altitude programme checks the clearances:

$D_{S1} = 3442\text{m}$ $H_{S1} = 250\text{m}$ $\Delta H_1 = 101.15\text{m}$
 $D_{S2} = 18741\text{m}$ $H_{S2} = 381\text{m}$ $\Delta H_2 = 48.88\text{m}$

Theoretically, therefore, he has a clear view of Station 2, and knows this before reaching the site. Unhappily, no amount of programming will ensure that the owners will allow him to camp there (at Kit Hill, Cornwall, west of Dartmoor).

Advantages of automatic testing equipment are set out in a booklet from Teradyne, who feel that fables and cartoons are a help in disseminating their message. Teradyne Ltd, Clive House, 12 Queens Road, Weybridge, Surrey WW 401

Replacement guide for semiconductors of all types, using Philips devices, is now available. Salient performance data is provided for transistors, thyristors and triacs, but replacements only for other devices. Mullard Ltd, Mullard House, Torrington Place, London W.C.1.

To provide a basic insight into the preparation and production of printed circuits, Isola of Duren have published a 32-page booklet, in which the Isola material is described and manufacturing methods illustrated. Information is offered on recommended ways of preparing artwork. Isola Werke A.G., D-5160 Duren, Postfach 236, West Germany WW 402

Analytical instruments for chemists is briefly described in a short catalogue from Hewlett-Packard. Instruments listed include gas chromatographs and accessories, liquid chromatographs, mass spectrometer systems and ancillary equipment. Hewlett-Packard, Winnersh, Wokingham, Berks RG11 5AR WW 403

Assistance with the design of radar circuitry is provided by Plessey's Radar Applications Handbook. Design details, with p.c. layouts, are given for preamplifiers, a 120MHz log. strip and swept-gain i.f. strip and detector. Analogue-to-digital converters are also covered. Copies can be had from Plessey Distributors.

120W, 300W and 600W amplifiers are the subject of a leaflet from Derritron. The units are intended as drivers for vibrators or p.a. amplifiers, giving 1% t.h.d., from 5Hz to 20kHz, at rated output. Derritron Electronics Ltd, Sedlescombe Road North, Hastings, East Sussex TN34 1XB WW 404

Electronic timer Series E is described by Tempatron in a new leaflet. This is a c.m.o.s. timer offering a variety of operational modes. Timing ranges between 0-100ms and 0-30h are available. Tempatron Ltd, 6 Portman Road, Reading, Berks WW 405

Components catalogue from Rank lists a variety of general electronic parts and spares for Rank Radio equipment. There is also a section on servicing instruments, tools and materials. Rank Radio International Ltd, RSVP Service, Walton Road, Ware, Herts SG12 0DY WW 406

Development, design and use of KEF Calinda and Cantata loudspeakers is subject of Kef-tops, Vol.3, No.2. Eight-page paper, covering background and performance details of speakers. Accompanying note points out that lower curve in Fig.8 (b) should be reactance, not resistance. KEF Electronics Ltd, Tovil, Maidstone, ME15 6QP. WW407

Linear circuit applications is a 20 page booklet containing over 40 applications of RCA i.c.s. Obtainable from Distronic Ltd, 50-51 Burnt Mill, Elizabeth Way, Harlow, Essex WW 408

Phase Angle Voltmeters is title of note from North Atlantic, Techn. Bulletin 120, describing theory of these instruments. It can be obtained from Bill Cullum, Applications Engineer, North Atlantic Industries Inc., 60 Plant Avenue, Hauppauge, N.Y. 11787, USA WW 409

Magnetic Perception Heads: Principles and Practice, describes heads used for detection of moving objects. Application note is produced by Orbit Controls Ltd, Lansdown Industrial Estate, Gloucester Road, Cheltenham, Glos GL51 8PL WW 410

Dry reed relays fully described in 32 page catalogue from Associated Automation. General background information followed by specific data on devices made by AA. Catalogue is available from 70 Dudden Hill Lane, London NW10 1DJ WW 411

GaAs power oscillators, described in Application Note TE-213 from Microwave Semiconductor Corporation. Devices used cover frequency range 3-18GHz. Useful list of references. Can be had from Pascall Electronics Ltd, Hawke House, Green Street, Sunbury-on-Thames, Middx TW16 6RA WW 412

Voltage regulators for microprocessors listed and characterized in 15 page booklet from Lambda Electronics Co., Abbey Barn Road, High Wycombe, Bucks WW 413

Multiplying d-a converters in c.m.o.s. is subject of 40 page guide published by Analog Devices. Section on theory is followed by 25 applications, including gain adjustment, panners, function generator, phase shifter and power series generator. Analog Devices, Central Avenue, East Molesey, Surrey WW 414

Optoelectronic devices from Monsanto described in new short-form catalogue, available from Swift Hardman, P.O. Box 23, Baillie Street, Rochdale, OL16 1JE WW 415

Portable Data terminal and v.d.u., Tele-ZIP, allowing communication between telephone and computer, using television set as v.d.u., and ZIP-64 low-cost v.d.u. both described in leaflets from Data Dynamics, Data House, Springfield Road, Hayes, Middx WW 416

High-voltage and r.f. connectors from Suhner described in two catalogues, available from Suhner Electronics Ltd, Telford Road, Bicester, Oxfordshire OX6 0LA WW 417


NEW PRODUCTS

Professional readers are invited to enter codes on the reply-paid card bound in at pages 112/3

Measuring systems

A range of modules (amplifiers, signal conditioners, etc.) enable a complete industrial measuring system to be assembled to individual requirements. A typical system for a weighing application is shown in the photograph and is built up using a power supply, amplifier, peak value store, auto-tare and limit switch, all contained in a cast metal housing which is secure against dirt and the direct jet from a hose. Reference-signal generators are included, providing 225Hz, 5kHz or direct-voltage outputs. The equipment is made by Hottinger Baldwin Messtechnik and is marketed here by Carl Schenck (UK) Ltd, Stonefield Way, Ruislip, Middx HA4 0JT.

WW301

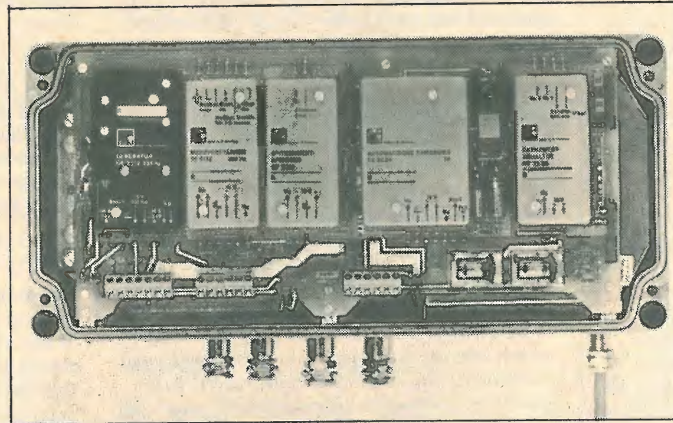

WW301

Digital multimeters

Two new meters by Sinclair, the DM350 and DM450, are 3½ and 4½-digit instruments respectively, offering a similar set of ranges and facilities, the DM450 at greater accuracy and resolution. Basic accuracy is 0.1% ± 1 digit and 0.05% ± 1 digit and each type will measure from 100µV d.c. and a.c., 1nA d.c., 1µA a.c. and from 100mΩ to 20MΩ. Each has a diode test facility. The instruments are in very slim plastic cases with tilt stands, similar in form to that of the older DM235, and can be provided with a carrying case and neck strap for 'hands-off' use. Four C cells provide the power, or an a.c. adaptor can be used. Rechargeable batteries and a high-voltage probe are accessories. Sinclair Radionics, London Road, St. Ives, Huntingdon, Cambs PE17 4HJ.

WW302



WW302

tronic components for overheating.

The meter used with the probe must have an impedance of over 10kΩ on the 0-3V range. Maximum error of the combination is quoted as ±1.7°C ± the error of the meter. Power to the probe unit is 9V, a small radio battery lasting around 120 hours of continuous use, and the end of battery life is indicated. B and K Precision, 6460 W. Cartland Street, Chicago, Illinois 60635, U.S.A.

WW303



Temperature probe

Effectively a temperature-to-voltage transducer, the Model TP-28 from B and K Precision enables temperature in the range -50° to +150°Celsius to be measured by means of an ordinary analogue or digital voltmeter. Liquids, gases or solids can be examined and in the case of a liquid the short settling time after a 100° change of 10s is achieved. A suggested way of using the probe is to examine small elec-

audio input/output point for tone controls and v.c.r. audio pre-amplifier and power amplifier. The power amplifier can operate in either a class B or a constant current consumption mode. The power output at $V_s = 24V$ is up to 4.5W into 16 ohms (class B) or 3.5W into 16 ohms (c.c.c. mode). The device is mounted in a power d.i.l. package incorporating a copper slug for up to 15W power dissipation. SGS-ATES (UK) Ltd, Planar House, Walton Street, Aylesbury, Bucks.

WW305

Remote controlled transmitters

A range of 1.0kW frequency synthesized h.f. solid-state transmitters, designated the T1005 series, offers full remote control over any distance. Up to 10 transmitters can be controlled from a single unit. The makers say a country's complete h.f. transmitting network could be controlled from one point in this way. Frequency, type of service and other operational facilities, including optional antenna selection, are all under the control of the remote operator. Frequency and service information can be stored on up to 15 channels for recall purposes. Commands are made on a 20-button keyboard, and a digital readout is provided of transmitter, channel and frequency selected. The series of transmitters covers a frequency range of 1 to 29.9999 MHz, with 290,000 channels in 100Hz steps. Transmission modes are s.s.b., c.w., m.c.w., d.s.b. and optional i.s.b. A control system gives protection from mismatch of an antenna circuit ranging from short-circuit to open-circuit output. Redifon Telecommunication Ltd, Broomhill Road, Wandsworth, London SW18 4JQ.

WW306

Power resistors

The Erg range of miniature, wirewound power resistors, with new closer tolerance, are said to fill the gap left by metal oxide power resistors in the lower values of resistance. The range is from 30 milliohms up to 18kΩ in the higher voltage applications, at an initial tolerance of 1% to 5% - any value in the range. Instability is claimed to be reduced by the use of crimped leadouts, and temperature variations are normally specified as +60 p.p.m./°C. Alternative specifications for specialized work are available. Erg Components, Luton Road, Dunstable, Beds LU5 4LJ.

WW304

Buzzers

Small buzzers, for use in portable, battery-operated equipment, are now available in a new range, Type GA100/K, from Highland. The 400Hz tone is produced electronically, at between 70 and 83dBa at 22cm. Supplies of 2.5, 6,

Television sound i.c.

The TDA2190 integrated circuit, contains an i.f. limiter amplifier with output low pass filter, f.m. detector, d.c. volume control,

12 or 24V d.c. are needed, depending on the version ordered, each type being contained in 22 x 15 x 10mm plastic case, which is colour coded to indicate voltage. The units can be mounted by a clip, by double-sided adhesive strip or by adhesive. Weight is 7g. Highland Electronics Ltd, Highland House, 8 Old Steine, Brighton, East Sussex BN1 1EJ. WW307

Printer interface



A driver for the Roxburgh SF-30 print mechanism accepts ASCII, bit-parallel character-serial inputs from c.m.o.s. voltage levels. The type 3001 operates the seven-electrode head of the SF-30 to print 64 alphanumeric characters on a 7 x 5 matrix of dots, accommodating 18 characters per line at two lines per second. Voltage supplies needed by the driver board are 12V, -12V, 24V and 35V, provided by a separate power supply, also obtainable from Roxburgh, who are at 22 Winchelsea Road, Rye, East Sussex TN31 7BR.

WW308


Interchangeable-scale meters

A range of analogue panel meters, comprising ammeters, voltmeters (both moving-coil and moving-iron), varimeters and frequency meters, have removable, interchangeable scale plates. These can be put in or taken out without opening or tampering with the rest of the instrument, so the user can add his own markings. Available in three DIN sizes, 72, 96 and 144 mm square with quadratic scales, all the meters are to specifications CEI 13.6, IEC Publication 51, BS89, VDE 0410, DIN 43700, 43701 and 43802. The total range of scales available goes from mA to MV. The meters have 90° sweep, compressed scales for overload and employ damped, jewelled movements. Long scale instruments (240°) are also available. IMO Precision Controls Ltd, 349 Edgware Road, London W2 1BS.

WW309

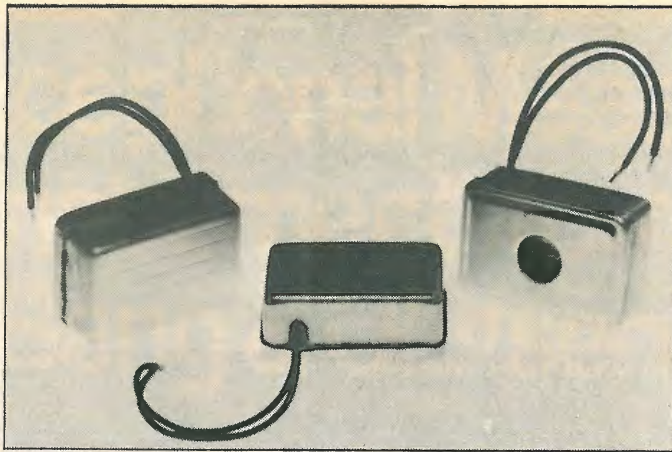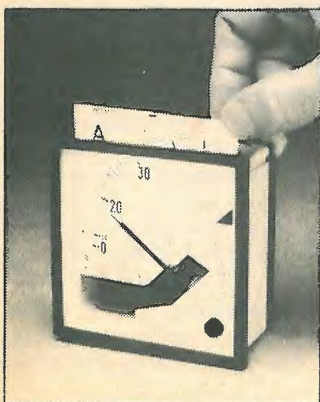

WW307

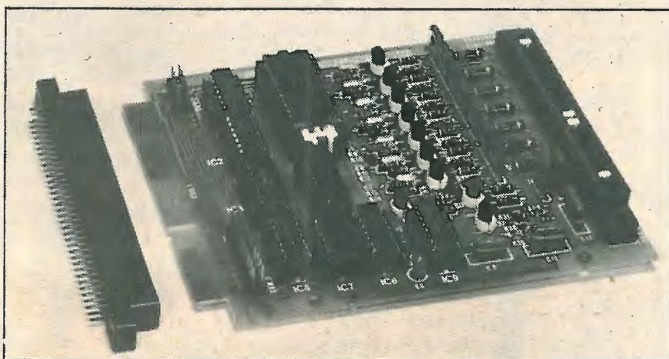

WW308


Taut-band VU meters

Sifam's new volume level meter has a performance "virtually indistinguishable from that of a true VU meter under most conditions" according to their marketing director. The new meters meet the requirements of the American Standard C16.5 1954, the company say, except the clause relating to dynamics. They are more heavily damped and have a rise time of about 0.1 second greater than traditional VU meters. They quote time from 0 to -3VU as 0.21 to 0.26 seconds, which compares with 0.13 to 0.15 for their conventional meters. Makers say the price is less than £5. Sifam Ltd, Woodland Road, Torquay TQ2 7AY.

WW310

Signal-processing xy recorder

Sounding more like a new British Standard, BS8000 is a microprocessor-based xy plotter than can digitize, record and process up to eight channels of analogue information. Either raw or processed data are plotted in real time or stored on a flexible disc, equivalent to about 100 metres of chart paper. You can record on pre-set triggering or on event triggering modes at up to 20,000 points per second, or at regular intervals with as few as 86 points per day. Information can be pro-

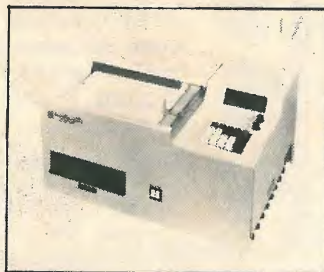

cessed before plotting, of course, in a variety of ways that includes averaging, smoothing, differentiation, integration.

Last year the same company introduced the first chart recorder with built-in memory enabling the Transcribe 10 to perform as a transient recorder. Bryans Southern Instruments Ltd, Willow Lane, Mitcham, Surrey CR4 4UL.

WW311

Large-numeral multimeter

We first saw the Metrix digital multimeter at the recent opening of Precision Instrument Laboratories new showroom. It is notable in that two PP3 batteries will give 1000 hours operation. And the number of hours service left in the battery can be displayed once the expected life drops below 200 hours. What's more, manganese alkaline batteries double this time to give three years "autonomy" at eight

hours a day. This long battery life for a digital multimeter, and its 18mm numerals, single-function switch and price of £109 make it unique among such meters. The c.m.o.s. microprocessor and liquid crystal display consume 250µA. Accuracy on most range is ±1% reading ±0.25% f.s.d. (better on direct voltage) and best resolution 1mV, 10A and 1Ω. Many other performance details of the instrument, made by Metrix of Chemin de la Croix Rouge, Anney are available from their U.K. agents Precision Instrument Laboratories Ltd, 727 Old Kent Road, London SE15.

WW312

Power regulator

The Domino power regulator has a group of parallel slave units controlled by a voltage or current master amplifier. By connecting an appropriate number of 20A. slaves in parallel, any required current can be regulated. The units are encapsulated circuits enclosed in a metal case, which has an electrically isolated flat aluminium surface for mounting on convection or force-cooled heat sinks. Each slave can dissipate up to 250W at 20A, and the voltage master provides voltages between 0 and 55V. The constant current system can provide accuracies and linearities claimed to be better than 0.01%. A redundancy system enables full output to be maintained if one of the slaves becomes faulty. Roband Electronics Ltd, Charlwood Works, Charlwood, Surrey RH6 0BU.

WW313

Router for p.c.bs

A router has been designed specifically for development of prototype p.c. boards. The removable guide pin, adjustable fence and end/depth stop, fitted as standard, allow a variety of work to be done. Profiles can be cut from a master using the guide pin; cut-outs for edge connector keys, relays and other components can be made using the fence and end stop, and unwanted tracks removed using the cutter heights adjustment. Also, boards can also be chamfered to remove rough edges. Construction is of steel and aluminium and the key type chuck has a 4mm maximum capacity. The work area is lit by a lamp and the 100-watt motor drives the cutter at 16000 to 18000 r.p.m. A vacuum cleaner adaptor is available for removing swarf. Price is £245 plus v.a.t. Circuitape Ltd, 33 New Street, Aylesbury, Bucks.

WW314

Silicone geraniums

In the interval between the fall of the despotic valve and the beginning of integration, the majority of semiconductor devices were carved out of germanium. It wasn't a name commonly used by non-technical people and, as often as not when they did come across it, it came out as *geranium*. It even crept into *Wireless World* on one or two occasions, but we kept quiet about it and everyone was too kind to refer to the mistake. The BBC, of course, maintained such a high standard that they never, ever committed such a gaffe.

It's all changed now, though. We don't have much geranium now, but we do seem to have much the same trouble with silicone. I recently had a letter from F. L. Devereux who, as most readers will know, was Editor of *W.W.* for many years. He writes a very entertaining letter, does Dev., and although he appears cheerful on the surface, one can sense the raw, naked aggression under the surface. His *bête noir* is the now widespread use of the word silicone, when silicon is meant, as in silicon chip. And the surprising thing is that the BBC are as much to blame as anyone, this time. He has this fantasy, he says, of microprocessors being made of a kind of elastomer and moulded into the form required by the designer.

It's a bit sad about the Beeb, I feel. The Pronunciation Unit used to be concerned mainly with words like Brno, Szechwan and axolotl, but must now be kept fairly busy explaining how to speak plain English. Since the gabblers, mutterers and mid-Atlantic snarlers took over, one can't depend on broadcasters for a lead any more. It's as though the Coldstream Guards had started to slop around like a bunch of old lags in the exercise yard.

Production wine

It's been a good year for apples. We have two trees, both a bit peculiar but laden down to the ground with the rummest-looking fruit I've ever come across. One is a crab-apple, which is fair enough, I suppose, although a bit limited in application, and the other produces gigantic red apples. Not just red skins, you understand, but red all the way through. The first year we moved into the house, I kept waiting for them to turn into ordinary apples, but they never did.

Well, anyway, in our family, we draw the line at red apple pie and after a while we got fed up with apple jelly, so I thought I'd get into wine making. Two years ago, I made a tentative gallon of wine in a most unscientific way and it was beautiful. It went through the malo-lactic fermentation (pure luck,



nothing to do with intent) and it tasted like nectar. So, this last October, I went gently mad and made seven gallons, only this time I got hold of all the technical-looking glassware and yeast, and tablets and stuff and did the job properly and it's awful. Actually, it's only just now clearing, but I've been having a furtive taste every now and then and the effect is grotesque. It feels as though it's making hair grow on the inside of your head.

As I've mentioned before, electronics is into practically everything now, so there has to be a way of testing the brew before it goes beyond recall. You can't tell by looking at it that it's going to be either poisonous or liquid gold, and there is definitely a need for some kind of gizmo or dip into it, with a meter scaled from, say, 'Uk' to 'Wow', or 'sink' to 'cellar'. Warned in time, my seven gallons could possibly have been upgraded from Uk to So-So, but now there are going to be lots of very drunk sewer-rats stumbling around. Maybe a pH meter would help, if I knew what to look for, but I haven't come across anything, so far, which will warn me to take remedial action. It could be I've identified a hole in the market here.

Freudian chip

I always seem to be going on about computers. It isn't that I have anything against them — not much, anyway — but I do become noticeably agitated when someone suggests that computers could take over from the Almighty in their spare time and spend the rest of the week playing each other at three-dimensional chess. In a recent communication from a firm of program (see? I haven't forgotten!) suppliers for a home computer, the spectacular suggestion is made that if one is experiencing a pain in the brain, all one has to do is post a floppy disc into the machine, which promptly turns into a psychiatrist. Honestly! Cross my heart, that's what it says. The sample of operator/computer conversation in the handout

seems to be concerned with this chap who can't stand the sight of his mother and I would dearly like to know how it finishes. Also, what effect a fault in programming would have. The first case of matricide committed on advice from a computer would definitely be in the 'man bites dog' class of news item, and could conceivably cause a good deal of head scratching in the legal profession. The program is actually very relevant since anyone who thinks a computer is going to help in circumstances of that kind is almost certainly in need of a psychiatrist.


Sight and sound

A letter from John Corner, of Whiteley Electrical Radio, informs me that the public address system at London Bridge was not, when I wrote the piece in the October issue, new. It was the old equipment I heard, the new one still being in their factory. So much for British Rail's accuracy in replying to a request for information. I've heard the new system now, and the concourse coverage is much improved, but there does seem to be a certain amount of trouble in the station itself. I'm now convinced that the problem lies more in the way it is used than in the system — some announcements are clear as a bell, others convey no information at all. Not to me, at any rate. The ones I can make out are spoken slowly, with expression; the others are read in a flat monotone, at a speed which allows the main echo to coincide with the next syllable, rendering both useless.

The recommended drill now adopted by experienced commuters is to hang about unconcernedly in the concourse until the train one wants is signalled on the big new visual-display board and then to race like a stag to get to the train before all the fierce ladies with their enormous bags beat you to it. The p.a. is of great help here, because as soon as you see the destination come up, you can start running and listen for the platform number on the wing, so to speak. I've gained nearly five seconds, several times, in this way. If you stop to pick up the people you've knocked down there is, of course, a danger of losing the advantage.

I still think v.d.us on the platforms would be a good idea, since those whose business it is to make life difficult sometimes change the destination of a train when everyone is comfortably settled with the crossword, and if you can't hear the platform p.a. you are left wandering about asking complete strangers what in the world is happening. I am usually reduced to chasing after the mob, and I am certain I shall finish up in Eastbourne one of these days. Not that I have anything against Eastbourne, but I happen to live near Croydon.

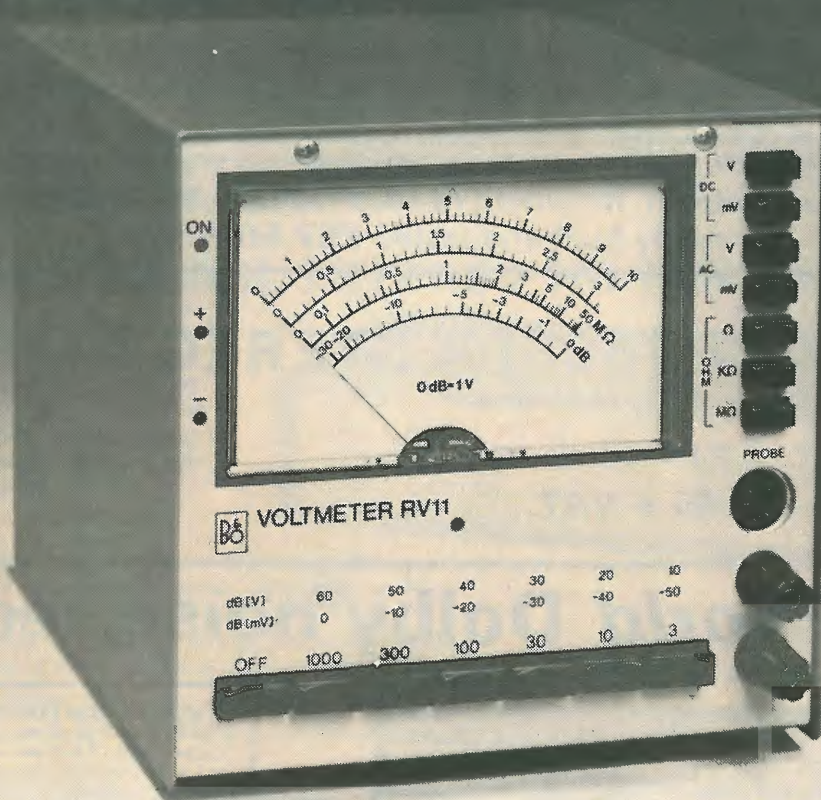An Exceptional Measuring Instrument from Bang & Olufsen



B&O Voltmeter RV11 is the result of 11 years research.

B&O has been working on the construction and development of test instruments since 1959. The expertise gained during these two decades has resulted in a range of measuring instruments with a particular relevance to design/development and service fields.

B&O Voltmeter RV11 is a multimeter for the measurement of AC and DC volts and ohms. The pushbutton function and range selectors are quick and easy to use and are positioned to form an instant read-out of settings during use.

Ranges:

Volts	3mV – 1000 V AC/DC
Resistance	0.2Ω – 50 MΩ
Frequency range	10 Hz – 1 MHz
Input impedance	10 MΩDC/1 MΩAC

Options:

Probes are available at extra cost allowing direct measurement of temperature, frequency, high voltage DC and R.F. signal voltage.

Send in reply card for our brochure giving detailed information about RV11 and other instruments in the B&O range.

Bang & Olufsen
A solid investment



NRDC-AMBISONIC UHJ



SURROUND SOUND DECODER

The **first ever** kit specially produced by Integrex for this British NRDC backed surround sound system which is the result of 7 years' research by the Ambisonic team. W.W. July, Aug., '77.
 The unit is designed to decode not only UHJ but virtually all other 'quadrophonic' systems (Not CD4), including the new BBC HJ 10 input selections
 The decoder is linear throughout and does not rely on listener fatiguing logic enhancement techniques. Both 2 or 3 input signals and 4 or 6 output signals are provided in this most versatile unit. Complete with mains power supply, wooden cabinet, panel, knobs, etc.

Complete kit, including licence fee **£49.50 + VAT**
 or ready built and tested **£67.50 + VAT**

NEW S5050A STEREO AMP

50 watts rms-channel. 0.015% THD. S/N 90 dB, Mags/n 80 dB.

Tone cancel switch. 2 tape monitor switches.
 Complete kit only **£63.90 + VAT.**

Wireless World DolbyTM noise reducer

Trademark of Dolby Laboratories Inc.



Featuring:

- switching for both encoding (low-level h.f. compression) and decoding
- a switchable f.m. stereo multiplex and bias filter.
- provision for decoding Dolby f.m. radio transmissions (as in USA).
- no equipment needed for alignment.
- suitability for both open-reel and cassette tape machines.
- check tape switch for encoded monitoring in three-head machines.

Typical performance

Noise reduction better than 9dB weighted.
 Clipping level 16.5dB above Dolby level (measured at 1% third harmonic content)

Harmonic distortion 0.1% at Dolby level typically 0.05% over most of band, rising to a maximum of 0.12%

Signal-to-noise ratio: 75dB (20Hz to 20kHz, signal at Dolby level) at Monitor output

Dynamic Range >90db

30mV sensitivity.

Complete Kit **PRICE: £43.90 + VAT**

Also available ready built and tested **Price £59.40 + VAT**

Calibration tapes are available for open-reel use and for cassette (specify which) **Price £2.40 VAT**

Single channel plug-in DolbyTM PROCESSOR BOARDS (92 x 87mm) with gold plated contacts are available with all components **Price £9.00 + VAT**

Single channel board with selected fet **Price £2.75 + VAT***

Gold Plated edge connector **Price £1.75 + VAT***

Selected FETs **65p** each + VAT, **110p** + VAT for two, **£2.10** + VAT for four.

Please add VAT @ 12½% unless marked thus*, when 8% applies (or current rates)

We guarantee full after-sales technical and servicing facilities on all our kits, have you checked that these services are available from other suppliers?



INTEGREX LTD.


Please send SAE for complete lists and specifications
**Portwood Industrial Estate, Church Gresley,
 Burton-on-Trent, Staffs DE11 9PT
 Burton-on-Trent (0283) 215432 Telex 377106**

INTEGREX

S-2020TA STEREO TUNER/AMPLIFIER KIT

SOLID MAHOGANY CABINET

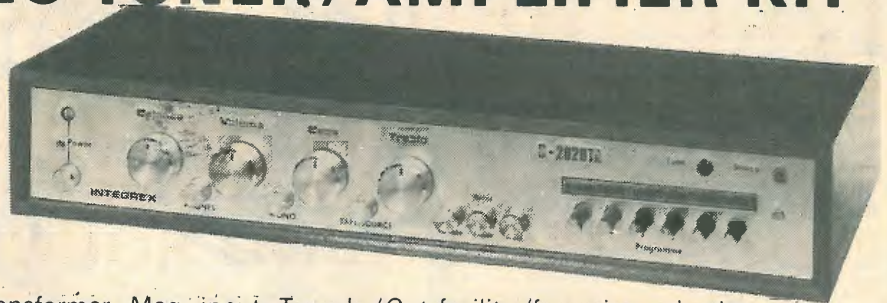
A high-quality push-button FM Varicap Stereo Tuner combined with a 24W r.m.s. per channel Stereo Amplifier.



Brief Spec. Amplifier Low field Toroidal transformer, Mag. input, Tape In/Out facility (for noise reduction unit, etc.), THD less than 0.1% at 20W into 8 ohms. Power on/off FET transient protection. All sockets, fuses, etc., are mounted for ease of assembly. Tuner section uses 3302 FET module requiring no RF alignment, ceramic IF, INTERSTATION MUTE, and phase-locked IC stereo decoder. LED tuning and stereo indicators. Tuning range 88—104MHz. 30dB mono S/N @ 1.2 μ V. THD 0.3%. Pre-decoder 'birdy' filter. **PRICE: £59.95 + VAT**
Nelson-Jones Mk. 2 Stereo FM Tuner Kit. Price: **£69.95 + VAT.**

NELSON-JONES MK. I STEREO FM TUNER KIT

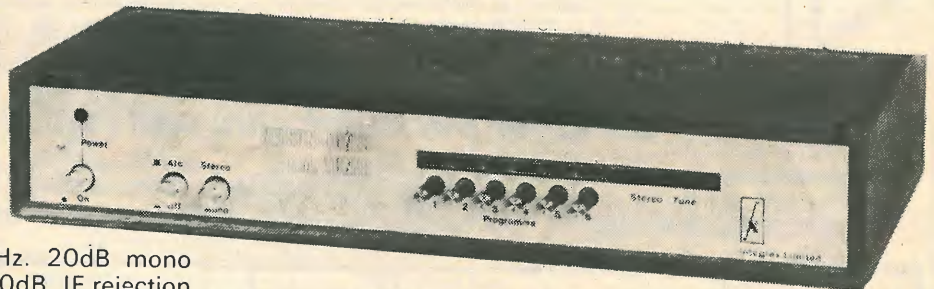A very high performance tuner with dual gate MOSFET RF and Mixer front end, triple gang varicap tuning, and dual ceramic filter/dual IC IF amp.



Brief Spec. Tuning range 88—104MHz. 20dB mono quieting @ 0.75 μ V. Image rejection — 70dB. IF rejection — 85dB. THD typically 0.4%. IC stabilized PSU and LED tuning indicators. Push-button tuning and AFC unit. Choice of either mono or stereo with a choice of stereo decoders.

Compare this spec. with tuners costing twice the price.

Mono £36.40 + VAT
With ICPL Decoder £40.67 + VAT
With Portus-Haywood Decoder
£44.20 + VAT



Sens. 30dB S/N mono @ 1.2 μ V
THD typically 0.3%
Tuning range 88—104MHz
LED sig. strength and stereo indicator

STEREO MODULE TUNER KIT

A low-cost Stereo Tuner based on the 3302 FET RF module requiring no alignment. The IF comprises a ceramic filter and high-performance IC Variable INTERSTATION MUTE. PLL stereo decoder IC. Pre-decoder 'birdy' filter Push-button tuning

PRICE: Stereo £33.95 + VAT

S-2020A AMPLIFIER KIT

Developed in our laboratories from the highly successful "TEXAN" design. PC mounting potentiometers, switches, sockets and fuses are used for ease of assembly and to minimize wiring Power 'on/off' FET transient protection.



Typ Spec. 24+24W r.m.s. into 8-ohm load at less than 0.1% THD. Mag. PU input S/N 60dB. Radio input S/N 72dB. Headphone output. Tape In/Out facility (for noise reduction unit, etc.). Toroidal mains transformer.

PRICE: £35.95 + VAT



BASIC NELSON-JONES TUNER KIT	£15.70 + VAT	PHASE-LOCKED IC DECODER KIT	£4.47 + VAT
BASIC MODULE TUNER KIT (stereo)	£18.50 + VAT	PUSH-BUTTON UNIT	£6.00 + VAT
PORTUS-HAYWOOD PHASE-LOCKED STEREO DECODER KIT			£8.80 + VAT

NEW The West Hyde MOD-1 Range


Swiss craftsmanship comes to instrument cases!



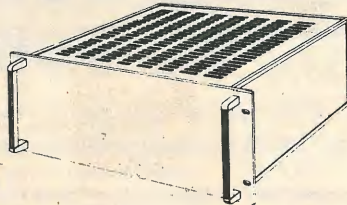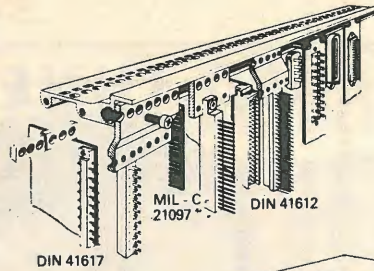
The "Type C" series (above) are finished in aluminium and blue and come complete with handles and feet. 19" rack mounting brackets are available for all sizes, together with a wide variety of card guides and connector profiles. Prices from **£23.17**.



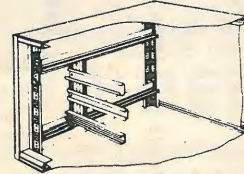The "Type A" series racks (left) are available in two depths and heights of 2 to 6 U. The front panel is 4mm thick natural anodised aluminium, and the sturdy framework will carry up to 50 kg. Accessories include chassis plates, blue cover plates and mounting extrusions. Prices from **£14.96**.



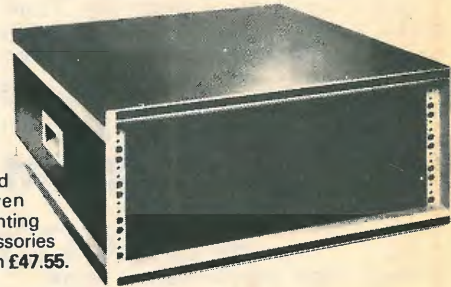The "Type E" series 19" housings (right) are made to take the Type A racks, or our 19" front panels. Attractively finished in blue and light grey, the cabinets may be supplied in two depths and seven heights. Slide rails, mounting rails and many other accessories are kept in stock. Price from **£47.55**.



Send for our catalogue and price list!

All West Hyde cases are available with substantial discounts for quantities. The Mod-1 Range have price breaks at 5, 10, 25, 50 and 100 off. (20% discount at 100 off). Prices include post and packing and are correct at press date. 10% discount is given on first two price breaks if cases are collected.

WEST HYDE DEVELOPMENTS LIMITED, Unit 9, Park Street Industrial Estate, AYLESBURY, BUCKS. HP20 1ET. Phone: Aylesbury (0296) 20441. Telex: 83570

WW — 070 FOR FURTHER DETAILS

10 OUTLET DISTRIBUTION AMPLIFIER 2

One floating input 10 independent floating outputs at 600 ohms for general studio work or feeding multiple slave pa amplifiers. Electronic input circuit which withstands mains or static voltages on the signal lines.

Total Harmonic Distortion, all outputs loaded, at -16dBV /

1kHz	0.01%
100Hz-20kHz	-76dB, 0.015%

Static Intermodulation Distortion, 50Hz + 7 kHz Output +12dBV /

50Hz	0.01%
7 kHz	-86dB, 0.005%

This unit meets the IBA "signal path" specifications and is available as a complete unit or as a set of all parts excluding the case and XLR connectors.

STEREO DISC AMPLIFIER 2
SUPERLATIVE PERFORMANCE FOR BROADCASTING DISC MONITORING AND TRANSFER. Magnetic cartridge to balanced lines with HF and LF filtering. Mains powered. Meets IBA specification. Specifications December advertisement.

PEAK PROGRAMME METERS
Meet IEC268-10A, BS5428. PPM2 Standard performance drive circuit under licence from the BBC. Reviewed Studio Sound, September 1976. Ernest Turner meter movements 642, 643 and TWIN stocked.

STABILIZER FOR HOWL REDUCTION, BALANCED AND UNBALANCED VERSIONS BOXED OR RACK MOUNTING

PUBLIC ADDRESS: SOUND REINFORCEMENT



+5Hz Fixed Shift Circuit Boards as WW July 1973 article but improved noise level.

Small enough to be built inside the cabinets of many amplifiers.

Complete kit and manual **£30**
Board built and engraved **£38**
including **PSU & mains transformer** DESIGNER APPROVED
SURREY ELECTRONICS
The Forge, Lucks Green, Cranleigh
Surrey GU6 7BG Tel: 04866 5997
CASH WITH ORDER less 5%
UK POST FREE ADD VAT at 8%

SINCLAIR PRODUCTS

Microvision TV UK model **£89.95**. PDM35 **£27.25**. Mains adaptor **£3.24**. Case **£3.25**. DM350 **£67.80**. DM450 **£96.50**, DM235 **£49.45**. Rechargeable bats. **£7.50**. Mains adaptor **£3.70**. Enterprise prog calculator **£21.95**. Cambridge prog calculator **£13.13**. Prog library **£3.45**. Mains adaptor **£3.20**.

COMPONENTS

Send see for full list. 1 1/2 FtC1 **£1.05**. Dalo pen 73p. 60 zinc pcb 55p. Laminate cutter 75p. Small drill 20p. zn414 **£1.05**, pcb and extra parts for radio **£3.85**. Case **£1**. 1N4148 14.1p. 1N4002 2.9p. 723 29p. 741 15p. NE555 23p. bc128b. bc183b. bc184b. bc212b. bc213b. bc214c 4.5p. Plastic equivs bc107, bc109 4.8p. 1/2W 5% E12 resistors 10R to 10M 1p. 0.8p for 50% of one value. Electrolytics 16v 5/12/25/10/22mf 5p, 100mf 6p, 1000mf 10p, 1500mf (PC) 3.4p. 10v 2mf 1.7p, 1000mf 5.1p, 2200mf 6p. Polyesters 250v 0.15, .068, .1mf 1 1/2p. Ceramics 50V E6 22pf to 47n 2p. Polystyrenes 63v E12 10pf to 10n 3p. Zeners 400mW E24 2v7 to 33v 7p.

TV GAMES

Send see for data. AY-38500 + kit **£8.95**. Rifle kit **£4.95**. AY-38600 + kit **£12.50**. Stunt cycle chip + kit **£10.90**. Racing cars chip + kit **£17.90**.

TRANSFORMERS

6.0-6v 100ma 74p, 1 1/2a. **£2.35**. 6.3v 1 1/2a **£1.89**. 9.0-9v 75ma 74p, 1a **£2**, 2a **£2.60**. 12.0-12v 100ma 90p, 1a **£2.49**.

IC AUDIO AMPS

With pcb J12 6w **£1.60**. JC20 10W **£2.95**. Send see for data.

BATTERY ELIMINATORS

3-way tupe 6 7/8 / 9v 300 ma **£2.95**. 100ma radio type with press-studs 9v **£3.35**, 9+9v **£4.50**. Stabilized tupe 3/6 / 7 1/2 / 9v 400ma **£5.30**. 12v car converters 3/4 1/2 / 6 7/8 / 9v 800ma **£2.50**.

BATTERY ELIMINATOR KITS

Send see for data. 100ma radio types with press studs 4 1/2v **£1.40**, 6v **£1.40**, 9v **£1.40**, 4 1/2+4 1/2 **£1.80**, 6+6v **£1.80**, 9+9v **£1.80**. Stabilised 8-way types 3/4 1/2 / 6 7/8 / 9 / 12 / 15 / 18v 100ma **£2.80**, 1Amp **£6.40**. Stabilised power kits 2.18v 100ma **£3.60**. 2.30v 1A **£6.95**. 2.30v 2A **£10.95**. 12v car converter, 6 7/8 / 9v 1a **£1.35**.

T-DEC AND CSC BREADBOARDS

Send see for data. 15 di adaptor **£2.14**, exp300 **£6.21**, exp350 **£3.40**, exp650 **£3.89**, exp4b **£2.48**.

BI-PAK AUDIO MODULES

S450 **£23.51**, AL60 **£4.86**, pa100 **£15.58**, spm80 **£4.47**, bmt80 **£5.95**, stereo 30 **£20.12**.

SWANLEY ELECTRONICS

(Dept. WW)
32 Golsel Road, Swanley, Kent
post 30p extra. Prices include VAT

THE MOST COST EFFECTIVE FREQUENCY COUNTERS



OFF / AIR FREQUENCY STANDARD TYPE 103
10MHz, 1MHz
Stability 1 part 10⁸ **£108**
TYPE 102 CRYSTAL FREQUENCY
Standard 10MHz, 1MHz, 100kHz
Stability 5 parts 10¹⁰ **£135**



FREQUENCY COUNTER TYPE 801B
401A 50MHz 6 Digit **£150**
701A 80MHz 8 Digit **£210**
901M 520MHz 8 Digit **£395**
1001M 1.2GHz 8 Digit **£670**
Start / Stop versions Plus **£18**

501 50MHz 8 Digit **£192**
801B/M 250MHz 8 Digit **£280**
Memory versions available if not suffixed M **£30 extra**



LED COUNTERS
302 50MHz. 5 digit **£108**
All standard counters in centre column now available as the .02 Series with LEDs.

SUPPLIERS TO: Ministry of Defence, G.P.O., B.B.C., Government Depts., Crystal Manufacturers and Electronic Laboratories world-wide for 18 years.



ELECTRONICS, 6 WOLSEY ROAD, ASHFORD, MIDDX. ASHFORD 53661

WW — 076 FOR FURTHER DETAILS

MAINS TRANSFORMERS (TM)

All these have 230/240V 50Hz Primary

Voltage	Our Ref	Price	Post
1v	2 amp TM 1	£1.94	40p
2.4v	5 amp TM 2	£1.82	45p
4v	7 amp TM 32	£2.70	60p
6v	¼ amp TM 37	85p	40p
6.5v	¼ amp TM 37	85p	40p
6.5v	200 mA TM 21	£1.62	40p
6.5v-0-6.5v	100 mA TM 21	£1.62	40p
6.5v-0-6.5v	750 mA TM 7	£2.16	45p
6.5v-0-6.5v	100 mA TM 33	£1.62	40p
6.3v	2 amp TM 12	£1.89	40p
8.5v	1 amp TM 12	£1.62	40p
8.5v + 8.5v sep. winding	½ amp TM 12	£1.62	40p
9v	1 amp TM 5	£1.62	45p
1 amp c core	1 amp TM 11	£1.89	40
3½ amp	TM 11	£2.70	60p
5 amp	TM 38	£2.24	60p
10v	25 amp TM 15	£4.86	£1.25
10v-0-10v	4 amp TM 50	£3.78	£1.25
10v-0-10v	12½ amp TM 15	£4.86	£1.25
12v	½ amp TM 9	£1.05	50p
13v	100 mA TM 21	£1.52	40p
13v	¼ amp TM 7	£2.16	50p
12v	1 amp TM 10	£1.89	50p
12v-0-12v	50 mA TM 19	£1.62	40p
12v-0-12v	1 amp TM 41	£3.24	50p
15v tapped 9v	2 amp TM 11	£2.70	50p
17v	½ amp TM 12	£1.62	50p
18v	¼ amp TM 13	£1.80	50p
20v	½ amp TM 14	£1.62	50p
20v (with 6v ½ amp)	2 amp TM 50	£3.78	£1.25
20v	6 amp TM 46	£4.32	£1.25
20v	12½ amp TM 15	£4.86	£1.25
20v-0-20v	6 amp TM 15	£4.86	£1.25
24v	1½ amp TM 16	£2.12	60p
24v	2 amp TM 17	£2.17	60p
24v + 2v 7 amp	2 amp TM 39	£2.97	70p
24v	4 amp TM 40	£3.78	80p
25v	1 amp TM 18	£2.43	60p
25v	2 amp TM 38	£2.96	60p
30v	8 amp TM 15	£4.86	£1.25
37v	37 amp TM 34	£31.86	enquire
40v	3 amp TM 46	£4.32	£1.25
40v	5 amp TM 48	£5.02	£1.25
40v tapped 30v, 20v & 10v	2 amp TM 15	£4.86	£1.25
40v-0-40v	2½ amp TM 48	£5.02	£1.25
50v-2 amp with 6.3v shrouded	2 amp TM 22	£4.86	£1.25
50v	8 amp TM 29	£11.65	£1.75
60v tapped 40v & 20v	2 amp TM 46	£4.32	£1.25
70v	4½ amp TM 24	£7.02	£2.50
75v-3 amp with 6.3v shrouded	TM 23	£6.10	£2.00
75v	4½ amp TM 24	£7.02	£2.50
80v tapped 70v & 75v	4 amp TM 24	£7.02	£2.50
80v centre tapped	2½ amp TM 48	£5.02	£1.25
100v	1 amp TM 25	£7.02	£1.75
100v-0-100v	½ amp TM 25	£7.02	£1.75
200v	½ amp TM 25	£7.02	£1.75
250v-0-250v & 6.3v 2a	50 mA TM 36	£3.78	£1.00
250v	100 mA TM 36	£3.78	£1.00
500v	50 mA TM 36	£3.78	£1.00
260v (and over secs)	60 mA TM 26	£3.24	£1.00
4 kv	5 mA TM 49	£4.05	70p
4 kv	5 mA TM 30	£7.02	£1.00
8 kv	5 mA TM 45	£4.05	£1.00
8.5 kv	10 mA TM 31	£10.26	£2.00

Full RANGE OF Mains to 120v Auto transformers available.

MULLARD UNILEX

A mains operated 4 + 4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost anyone, in easy to assemble modular form and complete with a pair of Plessey speakers this should sell at about £30 but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only **£15** including VAT and postage.



UNISELECTORS

These are pulse operated switches as used in automatic telephone switchboards, etc. The pulse moves the switch arm through one position. Except where indicated the selectors are 25 position types and 50v coil is standard. 24v or 12v operation extra at £2 per switch.



3 pole	£5.90
4 pole	£6.98
5 pole	£8.20
6 pole	£9.20
8 pole	£11.40
10 pole	£13.60

12 pole £15.88
2 pole 50 way £8.60
3 pole 50 way £11.40

INDUCTION MOTORS

One illustrated is our reference MM11 made for ITT ¼" stack 1½" spindle £2.25. Other size ½" stack model £1.75. 1" stack £2.75. 1½" stack £3.25.




RELAYS

12 volt two 10 amp changeover plug in 95p. 12v three 10 amp changeover plug in £1.28. 12v two changeover miniature wire ended 95p. 12 volt open single screw fixing two 10 amp changeovers 85p. 12v open three 10 amp changeovers £1.25. Latching relay mains operated 2 c/o contacts £2.11. Mains operated three 10 amp changeovers open type one screw fixing £1.25. Many other types with different coil voltages and contact arrangements are in stock, enquires invited.




EXTRACTOR FAN

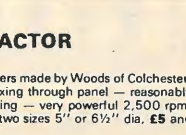Ex computers made by Woods of Colchester, ideal for fixing through panel — reasonably quiet running — very powerful 2,500 rpm. Choice of two sizes 5" or 6½" dia, £5 and £6.



FLUORESCENT INVERTOR

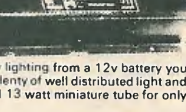For camping — car repairing — emergency lighting from a 12v battery you can't beat fluorescent lighting. It will offer plenty of well distributed light and is economical. We offer invertor for 21 and 13 watt miniature tube for only £3.95 with tube and tube holders as well



This Month's Snip

Hartley CT 436 double beam oscilloscope DC6M hz. Beautiful condition may have slight faults. Manuals available. Snip price **£75.00**, carriage **£5.00**. Tektronix, Marconi, Philips and other make scopes in stock.


PP3/PP9 REPLACEMENT MAINS UNIT

Japanese made in plastic container with leads size 2 x 1½ x 1½ this is ideal to power a calculator or radio. It has a full wave rectified and smoothed output of 9 volts suitable for a loading of up to 100mA **£2.53**.



TANGENTIAL HEATER UNIT

A most efficient and quiet running blower heater by Solatron — same type as is fitted to many famous name heaters — Comprises mains induction motor — long turbo fan — split 2 kw heating element and thermostatic safety trip — simply connect to the mains for immediate heat — mount in a simple wooden or metal case or mount direct onto base of say kitchen unit — price **£4.95** post **£1.50** control switch to give 2kw, 1kw cold blower or off available 60p extra

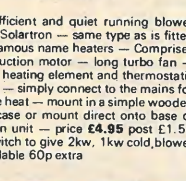

MOTORISED DISCO SWITCH

With 10 amp changeover switches, multi adjustable. Switches are fitted at 10 amps each so a total of 200w can be controlled and this would provide a magnificent display. The motors are 50V but they can be driven by a resistor or condenser, voltage dropper, 8 switch model **£5.25**, 10 Switch model **£5.75**, 12 Switch model **£6.75**.



TERMS
Prices include Post & VAT but orders under £6.00 please add 50p to offset packing etc. Bulk enquires please phone for generous discount 01-688 1833 Access and Barclaycard accepted.

J. BULL (ELECTRICAL) LTD
(Dept. WW)
103 TAMWORTH ROAD
CROYDON CR9 1SG

IT'S FREE!

Our monthly Advance Advertising Bargains List gives details of bargains arriving or just arrived — often bargains which sell out before our advertisement can appear — It's an interesting list and it's free — just send S.A.E. Below are a few of the Bargains still available from previous lists.

Telephone Ringing Mains Unit. Rather novel unit as it not only reduces mains to 50 volts but also reduces the mains frequency to 25Hz. This frequency gives correct ringing tone for GPO bells. These units were made for the GPO so obviously are first class. Completely enclosed and safe to mount on the wall or stand on a shelf. Price **£3.20**.

Telephone Extension Bells in bakelite wall box. These will save your missing calls when you are out in the garden or shed, etc. Price **£3.16**.

Variable Mains Supply. A bench mounting unit which contains an isolation transformer for safety and a 2 amp variac for adaptability. With this you will be able to get continuously variable mains supply from zero to full voltage at 2 amps. A real time saving device. Only Price **£20.75**.

Answering Machines still available as last month's newsletter but supplies are going down rapidly and this may well be your last chance to acquire one of these. A very large purchase this month enables us to offer a range of radio items. You will find the prices well below average.

Cassette Recorder/Player. Japanese or Hong Kong made, these have all the normal facilities record, playback, fast rewind etc., also sockets for stop/start, microphone, earphone and lead for mains as these operate from mains or HP 1 batteries. **£12.50**.

Six Transistor Pocket Radio. Medium wave only but with Radio 2 and Radio 4 changing places. Medium wave is all the average listener will want in the future. These little radios would make a lovely gift for a child. Modern design and in popular colours. Please state preferred colour and give an alternative price only **£1.50**.

AM/FM Radios. There's no doubt that FM does give better reproduction in good areas so a more adult member of the family will be pleased with one of these. The ones we have are in leatherette cases and are battery / mains radios having the mains unit built in and are complete with mains plug. These cover medium wave and VHF with optional AFC. Price **£6.75**.

8 Track to Cassette Adaptors. Cartridges are going out of popularity. Cassettes on the other hand are being made in increasing numbers and cover practically every field of sound entertainment. Cassettes can be played in 8 tracks if you have an adaptor. We offer these adaptors complete in carrying case and the price is only **£8.50**.

Soft Toy Radios. Not necessarily only for the younger members of the family as these are soft and cute and have universal appeal. Dolls, Poodles, elephants and rabbits each with zip compartment at the bottom where the radio fits. Medium wave only, working from PP3 batteries. When ordering please state preference and if possible give an alternative. **£4.50**

5 Band Portable. A very impressive radio in black imitation crocodile case. Size approx. 12 ins. wide, 7 ins. high and 4 ins. deep. This has metal embossed carrying handle and a pullout chrome plated FM aerial, covers the following bands AM 535 to 1605 KHz FM 88 to 108 MHz weather band and 162.5 MHz and it has a logging scale. This battery / mains radio has the built in mains unit also serves as a charger if you use rechargeable batteries. The mains lead with plug tucks away in its own compartment, another feature is a dial indicator which shows state of batteries. A real snip at **£10.50**.

Upright Multi Band Radio. 5 Bands and again a most desirable radio, all other details similar to the one above. Only real difference being slightly smaller case, again in imitation crocodile, but with soft handle and shoulder strap. Interesting point about both receivers is that if used with rechargeable batteries the built in mains unit serves as a charger. Price **£11.50**.

Extension Speaker Cabinets. A new delivery of these enables us to bring down the price quite a lot. We can now supply the smaller ones (11 x 8 x 4 1/2 approx) at **£1.95**. Post £1.00 and we have a larger one with a silver finish size approximately 12½" x 9" x 5½". Price of this is **£1.69**, post £1.50. If you can call and collect these cabinets you can save yourself the quite considerable postage and you only have to buy a few to get a discount as well. The quantity discount for these is a special rate of 25% if you buy four or more. Note these cabinets are very good quality (made for Rail Audio Systems) the grill material is Dacron.

Slide Switch Bargain. Double pole changeover standard size with good length of connecting wire soldered to each tag — 10 for **£1.38**.

Motor Start Relay. The current through the motor start winding is passed through a coil which gives a slight time delay before connecting the motor winding. This has heavy duty contacts and can be used for many other projects. Price **54p**.

Six Digit Counter. Mains operated, 1 pulse moves counter throughout digit, not resettable but all you have to do is to make note of the number before the start of each count. Real bargain at **80p**.

Be Prepared for possible blackouts and interruptions in electricity supplies. We have a range of emergency lighting nearby. We still have the fluorescent outfits for operating 12" tubes from 12v car battery, and the price is still the same **£3.95**, plus 50p post complete with a 21" tube.

Sleepers. 6/12 volt battery or transformer operated, ideal for using in many alarm circuits but particularly for car and motor-cycle alarms. These give a loud shrill note. American made by Delta Alarms. Price **£1.08** + 8p. Large quantities available.

Most Useful Timer. Up to 12 on/off's per 24 hours is what you can get from the Verner time switch if you fit our adaptor. The shortest on/off time is one hour but you can use any combinations of on/off to make up the 24 hours. An obvious use for this is to control immersion heaters. These are real current consumers and even though the thermostats are working properly, economies can be quite considerable if a time switch is used. Our Venners are all capable of 20 amp switching. There is of course many other applications for the time switch, which you will remember in its basic form follows the sun switching on at dusk and off at dawn. Price **£3.24** plus 50p post for switch with adaptor, extra for plastic case **£1.08** or metal case **£2.16** + 16p.

Safe Solists. For growers who use soil heating on benches, economies can be made by using a thermostat but if mains voltage equipment is used then the thermostat must be enclosed in a waterproof and earthable container. We can now supply this price **£3.78** + 28p. This container will accept the normal immersion heater type thermostat but for soil heating you want one which covers 50 deg Fahrenheit and upwards, we can supply these at **£3.20**.

Motorised Light Flasher. We can offer two motorised units both capable of 2,000 watts of light. Our ½ second flasher changes every ½ second and the 2 second flasher changes every 2 seconds. Either type **£8.40**.

Frightening Fuel Bills could loose some of their sting if you fit double glazing but even if the fuel bill does not come down much you will have a more comfortable home less draughts etc. Double glazing frames movable in the spring, can be easily made using rigid PVC sheetings. We have this, it is as clear as glass and virtually as everlasting. It is easy to fit as you can cut it bend it, nail it, etc. A recent purchase enables us to offer this at well below current price. It is 600 mm (23½" wide) and available in any length (it rolls up like lino). Price **5p** per sq ft. Minimum order 20 sq ft for **£1.06** post 50p. Orders over £5.00 post free. Longer lengths price negotiable.

Car Battery Power Unit made for Rank Radio. This unit has been designed to operate 6 volt battery powered equipment from a 12v car battery it provides a reliable source of stabilized voltage and gives protection to your equipment in case of accidental reversal connections also again excessive current. We can now supply this at a special price. The unit is very robust and virtually everlasting if used sensibly. It uses a negative earth car battery but will operate in a positive earth car providing the instrument being played is not connected to the car chassis. A real bargain at **£2.20**.

Project Boxes. All those offered in a recent newsletter are still available have now had a much larger one size 8½ x 5½ x 3½. Price **£1.85**.

Car Starter Charger Kit. New version, two 10 amp rectifiers, 250W transformer and the start charge switch with instructions. Price **£9.75**. This is probably one of the most useful pieces of equipment you can have in your garage. Sooner or later you or someone will leave something on and you will have a flat battery. This starter will get you away usually in less than five minutes.

Interested in Tape Control. American made tape punches, really beautiful units and the start charge switch with instructions. Price **£9.75**. This is probably one of the most useful pieces of equipment you can have in your garage. Sooner or later you or someone will leave something on and you will have a flat battery. This starter will get you away usually in less than five minutes.

Interested in Topo Control. American made tape punches, really beautiful units and the start charge switch with instructions. Price **£9.75**. This is probably one of the most useful pieces of equipment you can have in your garage. Sooner or later you or someone will leave something on and you will have a flat battery. This starter will get you away usually in less than five minutes.

25 Watt Audio Systems in Cabinets. Comparing 8 woofer and 3 tweeter with crossover and terminal connection panel mounted in simulated teal finish cabinet with fabric front. These are extremely good quality units comparable with those selling at twice the price. Cabinet size approx. 20" high, 10 3/4" wide and 8 1/2" deep, heavy cabinet made of thick blockboard. Price **£25.00** the pair, well worth you coming to collect them but if you cannot collect them then still worth adding **£5.00** the pair for carriage.

Tilt Switch 15 amp. Meant to switch off heater should it be knocked over, this pendulum-operated switch is on only when it is in the upright position. It could be incorporated in burglar alarm, car alarms etc. Contacts look quite able to cope with 15 amp loads at mains voltage. Price **54p**.

Heating Pads. These measure 11" long x 8 3/4" wide and are flat. Look rather like pieces of thick blotting paper. Wire ended 250 watt or joined in series they would be approx. 60 watt each. Dozens of uses. Price **80p** or two for **£1.50**.

Load Ringing Bell, industrial type with 6" going, 24v FC operated. Price **£7.50**.

Switch Trigger Mat, size 24" x 18" for going under carpet, etc. Price **£2.50**.

24v Relay with latching contacts. Price **95p**. **Secret Switch** with key. Price **85p**. **24v amp D.C. Power Supply.** Price **£5.50**.

Circuit Diagrams. No charge, just request.
Mouth Operated switch. Probably not made with this use in mind, more likely made for washing machines to control water level, etc., this is a sensitive low pressure device which operated three 1 pole changeover switches at different levels of pressure but all within a normal person's blowing capacity — blow gently into it and No. 1 switch operates, blow a little stronger and No. 2 operates, blow harder still and No. 3 operates. The switch is airtight so weight of water or other fluid substance could operate it. Undoubtedly a switch with very many applications. Osc type construction, this is approx. 3 1/4" dia x 1 3/4" thick — the air entry is a pipe approx. 3/16" dia. — electrical contacts we estimate at 10 amp c/o a 230v coil connection by push on tags. Order Ref. PS. 4. Price **£1.95**. Large quantity available.
Powerful Induction Motor. 1 1/2" stack, 2 amp, 100 mA would drive a small lathe, drill or grinder or would power a blowing or extracting fan. Fit suitable pulleys and it would drive a pebble polisher or similar, being double ended it will drive in either direction. Can also be fixed from either end, fixing bolts are fitted and these are 1 1/4" apart. Spindles 1/2" in diameter extend 1 3/4" beyond each end plate. A motor like this would cost at least £3 from 10 makers but we have a large quantity to offer at **£2.50**. Order Ref. MM. 10.
Vu Meter. Edgewise mounting through hole size 1 1/2" x 1/2" approx., these are 100 micro amp fsd and fitted with internal 6v bulb for scale illumination, also have zero reset. The scale is not calibrated but has very modern appearance. Price **£1.85**.

DELAY SWITCH
Mains operated — delay can be accurately set with pointers knob for periods of up to 2 1/2 hrs. 2 contacts suitable to switch 10 amps — second contact opens few minutes after 1st contact 95p.

SOUND TO LIGHT KIT. Based on the Everyday Electronics circuit, this is a very efficient little unit and when made up is in every way equal to professional models costing many times the price. This unit is not tuned to any particular frequency, it is simply dependent upon volume. This is no disadvantage, in fact the effect is very pleasing. It will control up to 750w of lighting and it works well with amplifiers with outputs of 1.50 watts. The kit complete with leads and plastic case is **£4.00** only, or 10 for **£36.00**, post and VAT paid.

Z & I AERO SERVICES LTD.

Head Office: 44a WESTBOURNE GROVE, LONDON W2 5SF
Tel. 727 5641 Telex 261306

RETAIL SHOP
85 TOTTENHAM COURT ROAD, W.1
Tel. 580-8403


SPECIAL OFFER OF BRAND NEW USSR MADE MULTIMETERS



TYPE	U4313	U4315
Sensitivity D.C.	20,000 o.p.v.	20,000 o.p.v.
Sensitivity A.C.	2,000 o.p.v.	2,000 o.p.v.
D.C. Current	60µA-1.5A	50µA-2.5A
A.C. Current	0.6mA-1.5A	0.5mA-2.5A
D.C. Volts	75mV-600V	75mV-1000V
A.C. Volts	15V-600V	1V-1000V
Resistance	1K-1M	300Ω-500kΩ
Capacity	0.5µF	0.5µF
Accuracy	1.5% D.C. 2.5% A.C.	2.5% D.C. 4% A.C.

Price complete with pressed steel carrying case and test leads
Packing and postage

£10.50
£1.50

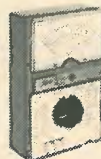


TYPE U4324

D.C. Current	0.06-0.6-60-600mA-3A
A.C. Current	0.3-3-30-300mA-3A
D.C. Voltage	0.6-1.2-3-12-30-60-120-600-1200V
A.C. Voltage	3-6-15-60-150-300-600-900V
Resistance	500Ω-5-50-500kΩ
Accuracy	D.C. 2.5% A.C. 4% (of F.S.D.)

PRICE complete with test leads and fibreboard storage case £9.50
Packing and postage £1.20

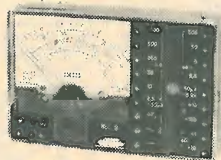TYPE U4323 COMBINED WITH SPOT FREQUENCY OSCILLATOR



Sensitivity	20,000Ω/V
Voltage ranges	2.5-1000V A.C./D.C.
Current ranges	0.05-500mA D.C. only
Resistance	5Ω-1MΩ
Accuracy	5% F.S.D.
Oscillator output	1kHz 50/50 squarewave 465KHz sinewave modulated by 1KHz squarewave

PRICE, in carrying case, complete with leads and manual
£8.00
Packing and postage £1.00



TYPE U4341 COMBINED MULTIMETER AND TRANSISTOR TESTER

Sensitivity	16,700Ω/V D.C., 3,300Ω/V A.C.
Current	0.06-0.6-6-60-600mA D.C., 0.3-3-0-30-300mA A.C.
Voltage	0.3-1.5-6-30-60-150-300-900V D.C. 1.5-7.5-30-150-300-750V A.C.
Resistance	2-20-200kΩ-2MΩ
Transistors	Collector cut-off current 60µA max D.C. current gain 10.350 in two ranges

PRICE, complete with steel carrying case, test lead, battery and instruction manual £9.50
Packing and Postage £1.50

THIS OFFER IS VALID ONLY FOR ORDERS ACCOMPANIED BY REMITTANCE WHICH SHOULD INCLUDE DELIVERY CHARGES AS INDICATED AND 8% V.A.T. ON THE TOTAL.

OUR 1978 CATALOGUE/PRICE LIST OF VALVES, SEMICONDUCTORS, PASSIVE COMPONENTS AND TEST EQUIPMENT IS AVAILABLE. PLEASE SEND P.O. for £0.30 FOR YOUR COPY

WW - 079 FOR FURTHER DETAILS

NEW! AMERICAN STYLE CRADLE TELEPHONE AMPLIFIER




ONLY
£16.95
+ VAT £1.36

Latest transistorised Telephone Amplifier is completely automatic with detachable plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the hand-set. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for 'conference' calls: leaves the user's hands free to make notes, consult files. No long waiting. On/Off switch, volume control. Model with tape-recording facility £19.95 + VAT £1.60. P.&P. 89p. C.W.O. 10-day price refund guarantee.

WEST LONDON DIRECT SUPPLIES (W/W)
169 Kensington High Street, London W.8

NEW IMPROVED MAINS INTERCOM

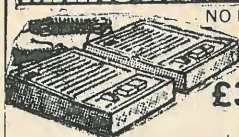

NO BATTERIES
NO WIRES
ONLY

£32.99
per pair
+ VAT £4.12

Made to High Safety and Telecommunications Standards. The modern way of instant 2-way communications. Supplied with 3-core wire. Just plug into power socket. Ready for use. Crystal clear communications from office to office. Operates over ½-mile range on the same mains phase. On-off switch, volume control. Useful as office intercom, surgery and homes, between office and warehouse. Full price refund if returned in 10 days. Six months' service guarantee. P.&P. 99p.

CONNECTORS
CANNON
PAINTON
BELLING LEE
PLESSEY
GREENPAR
AMPHENOL



1,000s in stock from:

Servo and Electronic Sales

SERVO AND ELECTRONIC SALES LTD.
24 HIGH STREET, LYDD, KENT TN29 9AJ
TELEPHONE: LYDD (0679) 20252 TELEX: 965265 AB SERVOE G

Sanwa from: Quality Electronics Limited

At above address

Transformers

Efficient design and manufacture ensures that all our transformers have a low heat-rise at full load, making a more reliable and safer product. Safety is also the reason behind our clip-on terminal insulators, which can make our transformers 'touch-proof' in use.

Lascar Components
Billericay (02774) 3394
P.O. Box 12 Second Avenue Billericay Essex



●3VA to 50VA miniature mains Transformers, Clamp and Printed Circuit mounting.

●Large Standard Range stocked in depth.

●'Blue Riband' service gives 7-14 day delivery on custom wound transformers.

●'Blue Star' service for OEM's, top quality transformers custom-wound at really competitive prices (from 89p at 500 up).

WW - 032 FOR FURTHER DETAILS

Which Microcomputer System offers you a choice of CPU?



OURS DOES!

It has long been established that for a particular application there is an optimum microprocessor, but the purchase of a new Microprocessor Development System for each application is prohibitively expensive. With the Quarndon Microcomputer System only the cpu board has to be changed. Each high-performance microcomputer board, using an 8080A, Z80, 2650, or 8085A as cpu can be used with an extensive common range of memory and interface boards, including our new high-performance fixed/floating point Arithmetic Processing Board.

The Quarndon QMS System provides true economy, allowing a change of cpu with a minimum of expenditure on new hardware.

QUARNDON ELECTRONICS LTD

SLACK LANE—DERBY DE3 3ED

Telephone: DERBY 32651 Telex: 37163 (Quarndon Derby)

WW — 105 FOR FURTHER DETAILS

It's W-W-WINTER S-S

74 SERIES TTL ICs

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
7400	£0.07	7427	£0.21	7472	£0.19	74105	£0.35	74163	£0.60
7401	£0.09	7428	£0.25	7473	£0.22	74107	£0.22	74164	£0.65
7402	£0.09	7430	£0.08	7474	£0.22	74110	£0.35	74165	£0.65
7403	£0.09	7432	£0.20	7475	£0.27	74111	£0.55	74166	£0.75
7404	£0.09	7433	£0.28	7476	£0.22	74118	£0.75	74167	£2.00
7405	£0.09	7437	£0.20	7480	£0.40	74119	£1.10	74174	£0.60
7406	£0.22	7438	£0.20	7481	£0.80	74121	£0.22	74175	£0.60
7407	£0.22	7440	£0.10	7482	£0.65	74122	£0.35	74176	£0.55
7408	£0.12	7441	£0.45	7483	£0.55	74123	£0.38	74177	£0.55
7409	£0.12	7442	£0.38	7484	£0.82	74136	£0.50	74180	£0.80
7410	£0.09	7443	£0.68	7485	£0.65	74141	£0.50	74181	£1.25
7411	£0.15	7444	£0.68	7486	£0.22	74145	£0.54	74182	£0.55
7412	£0.14	7445	£0.64	7489	£1.60	74150	£0.65	74184	£1.00
7413	£0.22	7446	£0.60	7490	£0.30	74151	£0.45	74190	£0.68
7414	£0.45	7447	£0.45	7491	£0.60	74153	£0.45	74191	£0.68
7416	£0.22	7448	£0.52	7492	£0.32	74154	£0.80	74192	£0.65
7417	£0.22	7450	£0.09	7493	£0.28	74155	£0.48	74193	£0.60
7420	£0.09	7451	£0.09	7494	£0.70	74156	£0.48	74195	£0.55
7421	£0.19	7452	£0.09	7495	£0.45	74157	£0.48	74195	£0.55
7422	£0.15	7453	£0.09	7496	£0.48	74160	£0.55	74196	£0.60
7423	£0.20	7454	£0.09	74100	£0.80	74161	£0.60	74197	£0.58
7425	£0.18	7460	£0.09	74104	£0.35	74162	£0.60	74198	£1.00
7426	£0.21	7470	£0.24					74199	£1.00
								74279	£1.00

CMOS ICs

Type	Price	Type	Price	Type	Price	Type	Price
CD4000	£0.12	CD4017	£0.65	CD4031	£1.60	CD4055	£1.00
CD4001	£0.13	CD4018	£0.70	CD4035	£0.90	CD4056	£1.15
CD4002	£0.13	CD4019	£0.35	CD4037	£0.78	CD4069	£0.15
CD4006	£0.80	CD4020	£0.80	CD4040	£0.78	CD4070	£0.15
CD4007	£0.14	CD4021	£0.75	CD4041	£0.68	CD4071	£0.15
CD4008	£0.80	CD4022	£0.75	CD4042	£0.68	CD4072	£0.15
CD4009	£0.40	CD4023	£0.13	CD4043	£0.78	CD4081	£0.15
CD4010	£0.42	CD4024	£0.55	CD4044	£0.78	CD4082	£0.15
CD4011	£0.13	CD4025	£0.13	CD4045	£1.15	CD4510	£0.80
CD4012	£0.14	CD4026	£1.00	CD4046	£0.95	CD4511	£0.80
CD4013	£0.35	CD4027	£0.45	CD4047	£0.75	CD4516	£0.85
CD4014	£0.70	CD4028	£0.60	CD4049	£0.35	CD4518	£0.85
CD4015	£0.70	CD4029	£0.75	CD4050	£0.35	CD4520	£0.85
CD4016	£0.35	CD4030	£0.40	CD4054	£0.95		

BOOKS BY BABANI

The following books are offered at 10% off their normal price

	Normal Price	Sale Price
BP6	£0.40	£0.36
BP14	£1.10	£0.99
BP22	£0.75	£0.68
BP24	£0.75	£0.68
BP26	£0.85	£0.77
BP27	£0.60	£0.54
BP32	£0.85	£0.77
BP34	£0.95	£0.86
BP35	£0.95	£0.86
BP36	£0.75	£0.68
BP37	£1.10	£0.99
BP39	£1.25	£1.13
BP40	£2.50	£2.25
BP41	£2.75	£2.48
BP42	£0.75	£0.68
BP43	£1.25	£1.13
BP44	£1.45	£1.31
BP45	£1.25	£1.13
BP46	£1.35	£1.22
BP47	£1.35	£1.22
BP48	£1.35	£1.22
BP49	£1.45	£1.31
BP50	£1.35	£1.22
BP55	£1.45	£1.31
BP160	£0.75	£0.68
BP202	£0.75	£0.68
BP205	£0.75	£0.68
BP213	£0.85	£0.77
BP215	£0.85	£0.77
BP216	£0.85	£0.77
BP217	£0.85	£0.77
BP221	£0.95	£0.86
BP222	£0.95	£0.86
BP223	£0.95	£0.86
BP224	£0.95	£0.86
BP225	£0.95	£0.86
BP226	£1.20	£1.08
BP227	£1.25	£1.13
BP228	£1.25	£1.13

VPS30 Variable Regulated Stabilised Power Supply Module

Incorporating a short circuit protection and current limiting:

Voltage Regulation	2-30v
Regulated Current	0-2A
AC Input Maximum	25v

Eliminates the use of batteries and thus saves +s — can be used time and time again. **ONLY £7.60 + V.A.T.**

BRAND NEW
ITT 923 Silicon
Diodes 200mA 200v.

100 off	£2.00
500 off	£9.00
1,000 off	£15.00
10,000 off	£130.00

P.C. BOARD

Single-sided Fibre-glass Board
12" x 3 1/2" approx 2 pcs **£143 £0.60**

THYRISTORS

No. THY1A/50	1 Amp.	50 volt	T05	18p
No. THY1A/400	1 Amp.	400 volt	T05	32p
No. THY3A/50	3 amp.	50 volt	T064	25p
No. THY3A/200	3 Amp.	200 volt	T064	32p
No. THY3A/400	3 Amp.	400 volt	T064	40p
No. THY5A/50	5 Amp.	50 volt	T066	25p
No. THY5A/400	5 amp.	400 volt	T066	40p
No. THY5A/600	5 Amp.	600 volt	T066	50p
No. C106/4	6 Amp.	400 volt	TO220	42p

TRIAC

S84	8 Amp.	400 volt	TO220	80p
-----	--------	----------	-------	-----

DIACS

ITT	V413	equit	12p
BR100	D32	each	12p

CAPACITOR PAKS

16201	18 Electrolytics	4.7µF — 10µF
16202	18 Electrolytics	10µF — 100µF
16203	18 Electrolytics	100µF — 680µF

All 3 at SPECIAL PRICE of £1.20*

16160	24 Ceramic Caps	22pF — 82pF
16161	24 Ceramic Caps	100pF — 390pF
16162	24 Ceramic Caps	470pF — 3300
16168	21 Ceramic Caps	4700pF — 0.047µF

All 4 at SPECIAL PRICE of £1.60*

RESISTOR PAKS

Order No.	60%W.	100 ohm — 820 ohm
16213	60%W.	1K — 8.2K
16215	60%W.	10K — 82K
16216	60%W.	100K — 820K

All 4 at SPECIAL PRICE of £1.60*

16217	40%W.	100 ohm — 820 ohm
16218	40%W.	1W — 8.2K
16219	40%W.	1K — 8.2K
16220	40%W.	100K — 820K

All 4 at SPECIAL PRICE of £1.60*

VOLTAGE REGULATORS

Positive			
No. MVR7805	µA/805	TO220	55p
No. MVR7812	µA7812	TO220	55p
No. MVR7815	µA7815	TO220	55p
No. MVR7818	µA7818	TO220	55p
No. MVR7824	µA7824	TO220	55p

Negative			
No. MVR7905	µA7905	TO220	75p
No. MVR7912	µA7912	TO220	75p
No. MVR7915	µA7915	TO220	75p
No. MVR7918	µA7918	TO220	75p
No. MVR7924	µA7924	TO220	75p

µA723C	TO99	38p	72723	14 pin Dil	38p
LM309K	TO3	£1.20			

SWITCHES

No. 1617R	5 x Mainz Slide Switches	40p
No. S17	5 x Miniature Slide Switches	40p
No. S18	4 x Standard Slide Switches	40p
No. S19	4 x Miniature Push to Make single hole mounting	40p
No. S20	3 x Miniature Push to Break single hole mounting	40p
No. S21	Push button Switch Pak 4 x Assorted types multi bank and singles Latching and non-Latching	£1.00*

AUDIO LEADS

Order No.	127	Audio lead 5 pin DIN plug to 4 phono plugs	90p
	129	Audio lead 5 pin plug to 5 pin DIN plug — Mirror Image	70p
	130	5-metre lead 2 pin DIN plug to 2 pin DIN inline socket	45p

AUDIO PLUG AND SOCKET PAKS

Order No.	S1	5 x 3.5 mm Plastic Jack Plugs	40p
	S2	5 x 2.5 mm Plastic Jack Plugs	40p
	S3	4 x Strt Plastic Jack Plugs	50p
	S4	2 x Stereo Jack Plugs	30p
	S5	5 x 5 Pin 180° DIN Plugs	50p
	S6	8 x 2 Pin Loudspeaker Plugs	50p
	S7	6 x Phono Plugs Plastic	50p
	SR	5 x 3.5 mm Chassis Sockets (Switched)	25p
	S9	5 x 2.5 mm Chassis Sockets (Switched)	25p
	S11	2 x Stereo Jack Sockets with instruction leaflet for Hi-Phone connection	50p
	S12	5 x 5 Pin 180° DIN Chassis Sockets	40p
	S13	8 x 2 Pin DIN Chassis Sockets	50p
	S14	6 x Single Phono Sockets	40p

P.C. BOARD

S110	Mixed Bundle P.C.B. Fibre-glass paper single and double-sided. Fantastic value	75p
------	--------------------------------------------------------------------------------	-----

SPECIAL OFFER!

UNTESTED SEMICONDUCTOR PAKS

Code Nos shown below are given as a guide to type of device. The devices themselves are norm unmarked.

No. 16130	100 Germ. Gold bonded diodes like OA47	40
No. 16131	150 Germ. Point contact diodes like OA70/81	40
No. 16132	100 200mA Sil. diodes like OA200	40
No. 16133	150 75mA Sil. Fast switching diodes like IN4148	40
No. 16134	50 750mA Sil. top hat Rects.	40
No. 16135	20 3 amp Sil. stud Rect.	40
No. 16136	50 400mw Zeners D.O.7 case	40
No. 16137	30 NPN Plastic trans. like BC107/8	40
No. 16138	30 PNP Plastic trans. like BC177/8	40
No. 16139	25 NPN trans. like 2N697/2N1711 TO39	40
No. 16140	25 PNP trans. like 2N2905 TO39	40
No. 16141	30 NPN trans. like 2N706 TO18	40
No. 16143	30 NPN Plastic trans. like 2N3904	40
No. 16144	30 PNP plastic trans. like 2N3906	40
No. 16145	30 PNP Germ. trans. like OC71	40
No. 16147	10 NPN TO3 Power trans. like 2N3055	40

I.C. SOCKET PAKS

No. S66	11 x 8 pin DIL Sockets	£1.10
No. S67	10 x 14 pin DIL Sockets	£1.10
No. S68	9 x 16 pin DIL Sockets	£1.10
No. S69	4 x 24 pin DIL Sockets	£1.10
No. S70	3 x 28 pin DIL Sockets	£1.10

MAMMOTH I.C. PAK

Approx. 200 Pieces. Assorted fall-out integrated circuits, including: Logic, 74 series, Linear, Audio and D.T.L. Many coded devices, but some unmarked — you to identify.

*Order No. 16223 £1.00

MATCHED PAIRS OF PNP GERMANIUM MED. POWER TANS

2 amp	750mW	
VCE	VCB	HFE
NKT301	40 60	30-100 35p per pair
NKT302	40 60	50-100 35p per pair
NKT303	20 30	30-100 25p per pair
NKT304	20 30	50-150 25p per pair

From U.S.A. by

DINDY SCREW CASED LOW NOISE CASSETTES

Order No. S53 10 for £3.50*

HEAD-CLEANING CASSETTE 45p each

AUDIO AMPLIFIER RETURN OF THE AL20A

By popular demand — this useful 5 watt Power Amplifier is offered at the re-introduction price of **£2.75***. Hook-up data supplied.

ETCH RESIST PENS

Order No. 1609	50p each
----------------	----------

UNIUNCTION TRANSISTORS

UT46	TIS43	20p
FETs		
2N3819	15p	2N5458

2 AMP. BRIDGE RECTIFIERS

Metal Stud Mounting	
No. S45	50V (K

SALE T-T-TIME again!

SPECIAL OFFER!

COMPONENT PAKS

5 pieces Assorted Ferrite rods	40p
2 pieces Tuning gangs MW LW	40p
50 metres Single strand wire	40p
assorted wire	40p
10 Reed switches	40p
3 Micro switches	40p
20 Assorted electronics	40p
Trans types	40p
1 pack Assorted Hardware nuts bolts etc	40p
20 Assorted tag strips and panels	40p
15 Assorted control knobs	40p
15 Assorted Fuses 100mA 5 amp	40p
60W resistors mixed values	40p
30 metres stranded wire	40p
assorted colours	40p
120 1/2 watt resistors Pre-formed	40p
1978 Prod Our mix	60p
120 1/2 watt resistors Pre-formed	60p
1978 Prod Mixed values	60p
250 1/2 watt resistors	60p
Range 100 ohms-1 8 meg	£2.00
220 1/2 watt resistors	£2.00
Range 100 ohms-10 meg	£2.00
60 Low ohms 1/2 watt resistors	60p
10-100 ohms	60p
40 Low ohms 1/2 watt resistors	60p
10-100 ohms	60p
25 Mixed wirewound resistors	60p
20 Tantalum bead caps	£1.00
0 22-100mF Our mix	£1.00
High-quality electrolytics 10mF-500mF	£1.00
voltage range 15 50V	£1.00
Our mix 40 for	£1.00
C280 Pak Contains 50 metal foil caps	£1.00

Crystal EAR Pieces S126 Less plug	£0.20
Plugs for above	£0.09
No 16106 2 5 plastic	£0.11
No 1697 3 5 plastic	
Mono Crystal Cartridge S127 GP91-1SC Special Offer	£1.00
Nickel Cadmium Rechargeable Batteries 1.25v	£2.50
S128 3500D Cell size=U2	£0.90
S129 900C Cell size=U11	
S130 Complete kit of parts to build nickel cadmium charger	£3.50
Super Save Pak S124 6 x 741P	£1.00
S125 5 x 555	£1.00
S138 Surplus End of Manufacturers Line Pre-amp with Bass Treble Volume Control & circuit diagram supplied	ONCE ONLY OFFER, £1.25
S137 20 Assorted Slider Knobs - Chrome Black	£1.00
S131 2 x 12v Relays plastic case	£0.70
S132 2 x 24v Relays plastic case	£0.60
S133 1 Switch bank 5-way incl silver knob	£0.75
S134 4 x Magnets suitable for reed switches	£0.10
S135 1 Veroboard pak 2 pcs 45sq. ins approx	£0.80
S136 15 Veroboard pak 2 pcs 60sq. ins approx	£1.10
16199 1 Veroboard pak pcs 30sq. ins approx	£0.50
16200 15 Veroboard pak pcs 30sq. ins approx	£0.50

TRANSISTORS BRAND NEW - FULLY GUARANTEED

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
AC107	25p	BC177	12p	BF194	9p	TIP32A	34p	2N1613	15p
AC126	14p	BC178	12p	BF195	9p	TIP32B	35p	2N1711	15p
AC127	16p	BC179	12p	BF196	9p	TIP32C	36p	2N1893	28p
AC128	16p	BC182	9p	BF197	12p	TIP41A	34p	2N2218	15p
AC128K	24p	BC182L	9p	BF200	25p	TIP41B	35p	2N2218A	18p
AC176	16p	BC183	9p	BF209	22p	TIP41C	36p	2N2219A	18p
AC176K	24p	BC183L	9p	BFX84	18p	TIP42A	37p	2N2219	15p
AC187	16p	BC184	9p	BFY50	12p	TIP42B	37p	2N2221	15p
AC187K	26p	BC184L	9p	BFY51	12p	TIP42C	38p	2N2221A	16p
AC188	16p	BC212	10p	BFY52	12p	TIP2955	65p	2N2222	15p
AC188K	26p	BC212L	10p	MPSA05	22p	TIP3055	42p	2N2222A	16p
AD161/1	162 MP	BC213	10p	MPSA06	22p	ZTX107	7p	2N2369	10p
AF139	30p	BC213L	10p	MPSA06	22p	ZTX108	6p	2N2904	14p
AF239	30p	BC214	10p	MPSA55	22p	ZTX109	7p	2N2904A	15p
BC107	6p	BC214L	10p	MPSA56	22p	ZTX300	7p	2N2905	14p
BC108	6p	BC251	10p	OC44	12p	ZTX301	7p	2N2905A	15p
BC109	6p	BCY70	12p	OC45	12p	ZTX302	9p	2N2906	12p
BC118	10p	BCY71	12p	OC71	12p	ZTX500	8p	2N2906A	14p
BC147	8p	BD115	40p	OC72	9p	ZTX501	10p	2N2907	12p
BC148	8p	BD131	35p	OC75	12p	ZTX502	12p	2N2907A	13p
BC149	8p	BD132	37p	OC81	14p	2N696	10p	2N2926G	8p
BC154	16p	BF115	17p	TIP29A	35p	2N697	10p	2N2926Y	7p
BC157	9p	BF167	19p	TIP29B	36p	2N706	7p	2N3053	12p
BC158	9p	BF173	20p	TIP29C	36p	2N706A	8p	2N3055	35p
BC159	9p	BF180	25p	TIP29C	38p	2N708	8p	2N3702	7p
BC169	10p	BF181	25p	TIP30A	38p	2N1302	12p	2N3703	7p
BC170	6p	BF182	25p	TIP30B	36p	2N1303	15p	2N3704	6p
BC171	6p	BF183	25p	TIP30C	37p	2N1304	15p	2N3903	11p
BC172	6p	BF184	25p	TIP31A	38p	2N1307	18p	2N3904	11p
BC173	7p	BF185	25p	TIP31B	38p	2N1308	22p	2N3905	11p
				TIP31C	34p	2N1309	22p	2N3906	11p

POTENTIOMETERS

Under 40mm TRAVEL	
6 x 470 Ohm LIN Single	40p
6 x 1K LIN Single	40p
6 x 5 K LIN Single	40p
6 x 22 K LIN Single	40p
6 x 47 K LOG Single	40p
6 x 47 K LIN Single	40p
6 x 100 K LIN Single	40p
6 x 100 K LOG Single	40p
6 x 500 K LOG Single	40p
6 x 50 K LIN Single	40p

POTENTIOMETERS

Under 60mm TRAVEL	
6 x 2 5 K LOG Single	40p
4 x 100 K LOG Dual	40p
4 x 1 3 MEG LOG Dual	40p
6 x 220 K LIN Single	40p
6 x 100 K LOG Single	40p
6 x 500 K LIN Single	40p

WIREWOUND

Wirewound Pots Linear 1 Watt	
20mm Mixed - useful values 5 for	£1.00

CARBON TYPES

Car Radio type Dual Switched Pot	
20mm mounting	
10K Lin switched	
25 K Lin	each 60p

DUAL POTS P.C. MOUNTING

4 x 100 K Lin	£1.00
4 x 100 K Log	£1.00
15 Rotary Pot Assorted	40p
25 Pre-sets Assorted Values	40p

ZENER PAKS

20 mixed values 400mW Zener diodes 3-10V	£1.00
20 mixed values 400mW Zener diodes 11-33V	£1.00
10 mixed values 1W Zener diodes 3-10V	£1.00
10 mixed values 1W Zener diodes 11-33V	£1.00

CON POWER TRANS. N.P.N.

BD371 2 Amp 1 2w 60Vceo	
Hfe 40-400 Case T092	
with heat tab - 5 for	60p
2N5293 P.C.A. 36w 4 Arms	
75Vceo Hfe 30-120 - 5 for	£1.00

ORDERING

Minimum postage and packing for Sale Orders £0.50 PLUS any further postage as stated as per this Sale Advertisement. Overseas Orders - ADD extra for Air-mail. V.A.T. Please ADD V.A.T. as follows: 12 1/2% to items marked *, 8% to unmarked items. NO V.A.T. on Books. SEND FOR YOUR BI-PAK CATALOGUE. 65p POST FREE.

RESISTORS

40 MIXED VALUES, 1 watt & 2 watt	
RESISTORS No. S143	£0.60

PROGRAMMABLE UNIJUNCTIONS

2N6027 with data	£0.24
------------------	-------

DIODES

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
AA119	5p	BAX16/	5p	BYZ16	30p	OA85	7p	IS44	3p
AA213	4p	OA202	5p	BYZ17	28p	OA90	6p		
BA100	6p			BYZ18	28p	OA91	7p	IN5400	10p
BA115	5p	BY100	15p	BYZ19	28p	OA95	7p	IN5401	11p
BA144	5p	BY127	10p	OA47	5p			IN5402	12p
BA148	10p	BY210	32p	OA70	5p	IN34	5p	IN5404	13p
BA173	10p	BY211	32p	OA79	7p	IN60	6p	IN5406	16p
BAX13/		BY212	32p	OA81	7p	IN914	4p	IN5407	17p
OA200	5p	BY213	30p			IN148	4p	IN5408	19p

LINEAR I.C.s

TBA800	£0.75	UA709	£0.20	748P	£0.28
TBA810	£0.85	UA711	£0.25	UA748	£0.28
TBA820	£0.65	UA703	£0.20	72558	£0.45
LM380	£0.80	741P	£0.18	MC1310P	£1.25
LM381	£1.25	72741	£0.20	76115	£1.25
72709	£0.20	UA741C	£0.20	NE555	£0.22
		72747	£0.55	SL414A	£1.80

ZN414 RADIO CHIP 75

OPTOELECTRONICS

DISPLAYS	Price
No. 1510. 707 LED Display	£0.70
No. 1511. 747 LED Display	£1.50
No. 1512. 727 Dual LED Display	£1.55

LEDs

No. S120. 125 Bright Red	£0.09
No. S121. 2 Bright Red	£0.09
No. 1502. 125 Green	£0.12
No. 1505. 2 Green	£0.12
No. 1503. 125 Yellow	£0.12
No. 1506. 2 Yellow	£0.12
No. S82. Clear 2 Illuminating Red	£0.10

P.O. RELAYS

S85 - 2 Off Post Office relays	40p
--------------------------------	-----

BATTERY HOLDERS

to take 6 x HP7s	
Order No. 202	10p each

EX-G.P.O. MICROSWITCHES

Order No. S51	4 for 50p
---------------	-----------

CABLE CLIPS

S65-50 2.5mm round single pin fixing	30p
--------------------------------------	-----

2nd QUALITY LED PAKS

No. 1507. 10 Assorted Colours & Sizes	£0.75
No. S122. 10x. 125 Red	£0.60
No. S123. 10x. 2 Red	£0.60

LED CLIPS

No. 1508/1. 125 125	5 for £0.12
No. 1508/2. 2	5 for £0.15
No. S139. Infra-red Emitter, Fairchild FPE100	£0.50

SPECIAL REDUCTIONS

No. 1514 NORP 12	45p each
No. S76 OCP71	5 for £1.00
No. S83 5 NIXIE Tubes ITT 5870 ST	£2.00
No. S77 (including Data)	
Neon Indicator Lamps 230V AC State Colour (Red, Amber and Green)	25p each

POWER SUPPLY STABILIZER BOARD

Unused ex-equipment stabilizer board. Input 30V. D.C. Output 20V. Complete with circuit diagram	
Order No. S81	£1.25

I.C. INSERTION EXTRACTION TOOLS O/N 2015 30p each

BI-PAK
DEPT. W.W.3, P.O. Box 6, Ware, Herts.
COMPONENTS SHOP: 18 BALDOCK STREET WARE, HERTS.

Marshall's Electronics



A. Marshall (London) Ltd., Dept: WW. Head Office mail order: Kingsgate House, Kingsgate Place, NW6 4TA. Tel: 01-624 0805
 Retail Sales London; 40-42 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/2. Telex: 21492. London: 325 Edgware Road, W2. Tel: 01-723 4242.
 Glasgow: 85 West Regent Street, G2 2QD. Tel: 041-332 4133. Bristol: 1 Straits Parade, Fishponds Road, B516 2LX. Tel: 0272 654201.

POPULAR INTEGRATED CIRCUITS. (A very small selection from our vast stocks, please enquire about devices not listed.)

CA3018 0.75	LM341P5 0.80	LM1303N 1.15	SAS570 2.70	TBA550Q 3.80	7405N 0.22
CA3018A 1.10	LM341P7 2.10	LM1304N 1.52	SAJ110 2.10	TBA5600Q 3.80	7406N 0.56
CA3020 2.20	LM341P15 0.80	LM1305N 1.52	SO41P 1.35	3.00	7407N 0.55
CA3020A 2.50	LM341P15 0.80	LM1307N 1.22	SO42P 1.35	TBA570 2.10	7408N 0.22
CA3028A 0.80	LM341P24 0.80	LM1310N 2.10	SN76001N 1.30	TBA570Q 2.20	7409N 0.22
CA3028B 1.25	LM348N 0.80	LM1351N 1.30	SN76003N 2.38	TBA700Q 2.20	7410N 0.26
CA3030 1.50	LM348N 0.95	LM1458N 0.45	SN76013N 1.50	TBA720AQ 2.20	7411N 0.26
CA3030A 2.20	LM358N 0.60	LM1498N 0.97	SN76023N 1.50	2.06	7412N 0.26
CA3038 2.90	LM360N 3.00	LM1808N 2.10	SN76033N 2.50	TBA750 2.36	7413N 0.30
CA3038A 1.40	LM370N 3.30	LM1812N 6.20	SN76033N 2.50	TBA750Q 2.45	7414N 0.80
CA3045 1.55	LM370N 3.30	LM1820N 1.10	SN76033N 2.50	TBA800 1.30	7416N 0.38
CA3046 0.77	LM371T 2.35	LM1828N 1.90	SN76033N 2.50	TBA810S 1.30	7417N 0.36
CA3048 2.45	LM350K 6.45	LM1830N 1.90	SN76033N 2.50	TBA820 0.80	7420N 0.22
CA3052 1.78	LM373N 3.35	LM1841N 1.90	SN76033N 2.50	TAA300 3.70	7423N 0.32
CA3080 0.85	LM374N 3.36	LM1845N 1.50	SN76033N 2.50	TAA263 1.35	7425N 0.32
CA3080A 2.10	LM377N 1.80	LM1848N 1.98	SN76033N 2.50	TCA160C 2.36	7427N 0.32
CA3086 0.50	LM378N 2.40	LM1850N 1.90	SN76033N 2.50	TCA160B 2.55	7427N 0.32
CA3088B 1.87	LM379S 4.25	LM1889N 4.90	SN76033N 2.50	TCA270 2.99	7430N 0.22
CA3089 2.90	LM380N 0.96	LM1931N 1.10	SN76033N 2.50	TAA350A 1.15	7432N 0.30
CA3090 4.40	LM380N14 1.08	LM3301N 0.60	SN76033N 2.50	TAA521 1.10	7437N 0.35
CA3130 1.06	LM381AN 2.70	LM3302N 0.55	SN76033N 2.50	TAA522 2.10	7438N 0.32
CA3140 1.04	LM381AN 2.70	LM3401N 0.55	SN76033N 2.50	TAA550 0.48	7440N 0.20
LM301 0.30	LM381N 1.69	LM3900N 0.68	SN76033N 2.50	TAA560 2.10	7441AN 0.84
LM307N 0.50	LM382N 1.32	LM3905N 1.15	SN76033N 2.50	TAA570 2.20	7442N 0.76
LM308N 0.95	LM384N 1.55	LM3909N 0.78	SN76033N 2.50	TAA370A 5.45	7445N 1.40
LM309K 1.95	LM386N 0.88	LM3911N 1.10	SN76033N 2.50	TAA630 2.40	7446AN 0.90
LM317K 3.35	LM387N 1.10	LM3920N 1.75	SN76033N 2.50	TAA960 3.90	7447AN 0.80
LM318N 2.45	LM388N 1.00	LM3921N 1.75	SN76033N 2.50	TAA970 4.20	7448N 0.80
LM320TS 2.15	LM389N 1.00	LM3922N 1.75	SN76033N 2.50	TAA611B 2.50	7450N 0.22
LM320T1 2.15	LM702C 0.81	LM3923N 1.75	SN76033N 2.50	TAA621 2.50	7451N 0.22
LM320T15 2.15	LM709 0.70	LM3924N 1.75	SN76033N 2.50	TAA661B 1.45	7453N 0.22
LM320T15 2.15	LM709 0.70	LM3925N 1.75	SN76033N 2.50	TAA700 4.50	7459N 0.22
LM320T24 2.15	LM710 0.67	LM3926N 1.75	SN76033N 2.50	TAA930A 1.45	7470N 0.46
LM320P5 1.15	LM710 0.67	LM3927N 1.75	SN76033N 2.50	TAA930B 1.45	7472N 0.30
LM320P12 1.15	LM710 0.67	LM3928N 1.75	SN76033N 2.50	TAD100 2.00	7473N 0.44
LM320P15 1.15	LM710 0.67	LM3929N 1.75	SN76033N 2.50	TAA611A 1.85	7474N 0.32
LM320P24 1.15	LM710 0.67	LM3930N 1.75	SN76033N 2.50	TAA661B 1.45	7474N 0.32
LM323K 6.95	LM710 0.67	LM3931N 1.75	SN76033N 2.50	TAA661B 1.45	7474N 0.32
LM339N 0.60	LM710 0.67	LM3932N 1.75	SN76033N 2.50	TAA661B 1.45	7474N 0.32
LM340TS 0.88	LM710 0.67	LM3933N 1.75	SN76033N 2.50	TAA661B 1.45	7474N 0.32
LM340T15 0.88	LM710 0.67	LM3934N 1.75	SN76033N 2.50	TAA661B 1.45	7474N 0.32
LM340T24 0.88	LM710 0.67	LM3935N 1.75	SN76033N 2.50	TAA661B 1.45	7474N 0.32

ALL PRICES NOW INCLUDE VAT CORRECT AT 12.11.78

Our range covers over 8,000 items. The largest selection in Britain. Top 200 ICs, TTL, CMOS & LINEARS

MICROPROCESSOR SUPPORT CHIPS

RAM	ROM	TRISTATE BUFFER	8080 SUPPORT
2101-2 £3.63	1702AQ £8.10	DM81L595 £1.36	8224 £4.58
2102-2 £1.94	5204Q £11.00	DM81L596 £1.36	8228 £5.85
2111-2 £3.63	2708Q £13.00	DM81L597 £1.36	8212 £3.10
2112-2 £3.63	2716 £40.00	DM81L598 £1.36	8216 £2.60
2107 £8.47			8226 £2.60
2116 £36.55			8253 £11.38

VAT INCLUSIVE PRICES
 8154 RAM 1/0 chip £8.83

MICRO CHIP

SC7MPT £12.96	MM5303 £6.85
SC7MP11 £10.80	MM5307 £13.69
6800P £16.99	DM8678 £15.40
8080A £7.42	AY313 £8.75
57109 £12.75	
57180 £10.25	
57161 £10.25	

CONVERT TV SET TO VDU

The new CRT control chip from Thomson CSF SFF96384. Convert your TV set into an electronic VDU - 16 lines x 64 characters - requires RAM, character generator and little else for a basic VDU. Available as chip or full display card. Full cursor control, 5 volts TTL compatible, line erase, full card includes UART, Modem, Char. gen. etc. Comp video out from encoded keyboard.

NEW CHIP £17.20 FULL CARD £151

LEDs + OPTO

Displays 7 seg Com anode or cath Red 8mm HT £1.50 10mm HT £1.55 14mm HT £1.57 18mm HT £1.85

LEDs Red Gr Yell Small 3mm

Red	Gr	Yell
.18	.19	.19

Large 5mm

Red	Gr	Yell
.20	.20	.20

Extra

1 red LD271	IR receiver	Opto coupler
.40	.40	.40
.05	.15	.15

TRIACS plastic pack 400V T0220

4 amp	7.2p	16 amp	9.3p
6 amp	7.7p	20 amp	£1.87
8 amp	8.2p	25 amp	£2.20
12 amp	9.3p		

THYRISTORS plastic power

4 amps	8 amps	12 amps
100v x 38	100v x 47	100v x 63
200v x 44	200v x 54	200v x 70
400v x 54	400v x 68	400v x 90

Branded Texas quality product

NEW 1979 CATALOGUE

40 page catalogue - new enlarged micro section - largest range of quality components from franchised suppliers available in UK. All VAT inclusive prices. Over 8,000 line items plus lots more 50p post paid or 40p to callers at any of our four branches.

MARCONI TEST EQUIPMENT

TF791D Deviation meter
 TF455E Wave analyser. New. £135
 TF1101 RC oscillators. £65
 TF1099 20MHz Sweep generators
 TF1041 B & C. VT Voltmeters
 TF1102 Amplitude modulator. 500MHz
 TF1020A Power meter. 100W. 250MHz. £85
 TF1152A/1 Power meter. 25W. 500MHz. £75
 TF890A/1 RF test set. £425
 TF801B/3S Signal generator. £175
 TF1064B/5 VHF. FM Signal generator
 TF1400 Pulse generator
 TF675F Pulse generator
 TF1370 Wide-range RC oscillator. £125
 TF2162. MF Attenuator
 TF1058 UHF/SHF signal generator
 TF995A/4. AM/FM signal generator
 TF1066 AM/FM signal generator
 TF340 Power meters.

ADVANCE CONSTANT VOLTAGE TRANSFORMERS

Input 190-260V AC. Output constant 220 Volts. 250W. £25 (£2 carriage)

POLARAD type TSA. SPECTRUM ANALYSER.

C/w type STU/2M plug-in unit covering from 950 to 4500 MHz.

NICKEL CADMIUM BATTERIES

Size 'D' (HP2) 4 A.H. £2 (pp. 20p)
 Size 'F' 6.00 A.H. £2.75 (pp. 25p)

POWER SUPPLIES

ADVANCE PMA47. 0-15V @ 3 Amps. £30
 ADVANCE RMA20. 0-7V @ 20 Amps. £39
 Both brand new, boxed, with book.
 APT10459/11. 10-15V @ 7.5A £25
 APT10459/13. 24V (var) 5A £25
 (All items + £1 carr.)

BECKMAN TURNS COUNTER DIALS

Miniature type (22mm diam.). Counting up to 15 turn "Helipot". Brand new with mounting instructions. Only £2.50 each.
Wandel & Gottman Equipment
 Level Meter 0.2-1600KHz
 Level Oscillator 0.2-1600KHz
 Level Transmitter 0.3-1350KHz
 Carrier Frequency Level Meter

P. F. RALFE ELECTRONICS

10 CHAPEL STREET, LONDON, NW1
 TEL: 01-723 8753

TEST EQUIPMENT

LEADER TV FM Sweep and marker generator
 AIRMEC 210 Deviation meter
 HEWLETT-PACKARD 302A Wave-Analyser
 RACAL type 801R. 100MHz digital frequency meter
 TEXSCAN X-Y oscilloscope. 9-inch CRT
 TELETYPE ASR33 now in stock
 SOLARTRON 1420. 2 digital voltmeter. 6 ranges to 1KV
 BOONTON 80 Signal generator. 2-400MHz £105
 BOONTON 230A RF Power Amplifier £325
 BPL Capacitance decade (5) CD133. 100pF-1uF £45
 GERTSCH Frequency meter and deviation meter 20-1000MHz
 HEWLETT-PACKARD 695A Sweep oscillator £350
 HEWLETT-PACKARD Sweep oscillator £110
 DERRITRON. Digital Wheatstone Bridge
 MUIRHEAD K-134-A Battery op. wave analyser
 WEINSHEL Power Supply Modulator MO3



BRUEL & KJOER Vibration equipment 1018
 BRUEL & KJOER Frequency analyser 2105
 BRUEL & KJOER Microphone amplifier 2603
 BRUEL & KJOER Type 3301 Automatic frequency response recorder 200Hz-20KHz
 MUIRHEAD-PAMETRADA D489EM Wave Analyser
 TEKTRONIX 555 scope with plug-ins types CA (2 off), 21, 22
 TEKTRONIX 515A Oscilloscope
 TEKTRONIX 545 main frames. £210. Choice of plug-in units extra
 TEKTRONIX 585A oscilloscope with '82' P.I. DC-80MHz
 TEKTRONIX type 180A Time-marker generator £110
 TELEQUIPMENT DM53A Storage oscilloscope
 TEKTRONIX 556. 50MHz oscilloscope
NOTICE. All the pre-owned equipment shown has been carefully tested in our workshop and reconditioned where necessary. It is sold in first-class operational condition and most items carry our three months' guarantee. Calibration and certificates can be arranged at cost. Overseas enquiries welcome. Prices quoted are subject to an additional 8% VAT.

ROHDE & SCHWARZ EQUIPMENT

HUZ Field Strength Meter. 47-225MHz.
 AMF TV. Demodulator 55-90MHz.
 Selective UHF v/meter, bands 4&5 USVF.
 Selectomat. RF Voltmeter. USWW. BN 15221

Standard attenuator. 0-100dB. 0-300MHz. DPR.	£450
UHF Sig. gen. type SDR 0.3-1 GHz	£750
UHF Signal generator type SCH.	£175
UHF Test receiver type USVD	£325
POLYSKOP SWOB 1.	

PYE-LING VIBRATORS

3 ohm coil. Overall dimensions 9 x 6 1/2 x 6 1/2 cms. Each £5.25 (25p P&P).

SOLARTRON Type CD1400 OSCILLOSCOPES

Double-beam, DC-15MHz (-3dB). Complete with types CX1441 (2 off) plug-in Y-Amp units, 100mV/cm (10mV to 750KHz) and type CX1444 Sweep delay time-base unit. Sold in first class operational condition with guarantee. £175 + 8% VAT.

'CENTAUR' INSTRUMENT COOLING FANS

Made by Rotron Holland. These are very high quality, quiet running fans, specially designed for the cooling of all types of electronic equipment. Measures 4.5 x 4.5 x 1.5in. 115V AC. 11 Watts. The list price of these is over £10 each. Also 230V. AC available. Either voltage £4.50 each (postage 25p).

TEKTRONIX TYPE 556

OSCILLOSCOPE WITH TYPES 1A1 and 1A2 PLUG-IN UNITS. First class condition throughout.

TELEVISION MONITORS

Philips studio quality precision colour monitors and Pye monochrome 405/525/625 lines.
PACE ELECTRONICS VARI PLOTTER
 Type 1100E £175

MUIRHEAD DECADE OSCILLATORS Type 890A.

1Hz-110KHz in four decade ranges. Scope monitored output for high accuracy of frequency. Excellent generator.

...and now No. 3!

This third book in Wireless World's popular series will be welcomed by all concerned with designing, using and understanding electronic circuits. It comprises information previously included in the third ten sets of Wireless World's highly successful Circards — regularly published cards giving selected and tested circuits, descriptions of circuit operation, component values and ranges, circuit limitations, modifications, performance data and graphs. The book follows on from Circuit Designs Nos. 1 and 2. It is magazine size in hard cover and contains ten sets of Circards plus additional information and an explanatory introduction. Like its predecessors, it may soon be difficult to obtain, so you are advised to order your copy without delay.


Voltage to frequency converters.
Amplitude modulators.
Reference Circuits.
Voltage regulators.
RC oscillators — part 1.
RC oscillators — part 2.
C.M.O.S. — part 1.
C.M.O.S. — part 2.
Analogue multipliers.
R.m.s./log./power law circuits.

circuit designs

3

Collected Circards

PWilliams/JCarruthers/JHEvans/JKinsler

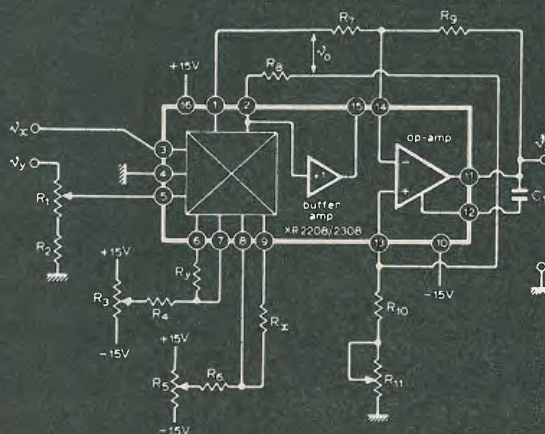

A WIRELESS WORLD PUBLICATION

A book from

wireless world

General Sales Department, IPC Business Press Ltd.,
 Room CP34, Dorset House, Stamford Street, London SE1 9LU.

ORDER FORM

To: General Sales Department,
 IPC Business Press Limited, Room CP34, Dorset House,
 Stamford Street, London SE1 9LU.

Please send me.....copy s of
 Circuit Designs — Number 3 at £14.50 each
 inclusive. I enclose remittance value £.....
 (cheques payable to IPC Business Press Ltd.)

NAME.....
 (please print)
 ADDRESS.....


Company registered in England and a subsidiary of Reed International Ltd.
 Registered No. 677128. Regd. office: Dorset House, Stamford Street,
 London SE1 9LU.

ASCENSION ISLAND YUGOSLAVIA UNITED STATES OF AMERICA JORDAN GREECE INDIA GUYANA PORTUGAL FALKLAND ISLANDS UNITED ARAB EMIRATES JAMAICA HOLLAND KENYA

EIRE GRENADA SAUDI ARABIA NEW ZEALAND NORWAY SINGAPORE ICELAND SWEDEN MALAYA INDONESIA BRAZIL SWITZERLAND ZAMBIA GIBRALTAR CHILE SPAIN

ELECTRONIC KITS OF DISTINCTION FROM POWERTRAN

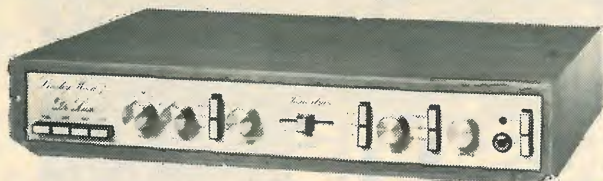DE LUXE EASY TO BUILD LINSLEY-HOOD 75W AMPLIFIER



AVAILABLE AS SEPARATE PACKS
PRICES IN OUR FREE CATALOGUE

SPECIAL PRICE FOR COMPLETE KIT £99.30


The standard model of our kit for Mr. Linsley-Hood's 75 watt design has for a long time offered exceptional performance at a very modest cost with high quality high power ready-built units of comparable quality generally being over three times the price.

Features of the amplifier include very low distortion (less than 0.01%), 75W rms per channel power output, rumble filter, variable slope scratch filter, variable transition frequency tone controls, tape monitoring facilities and individually adjustable inputs. This model is based on 5 circuit boards which not having the controls mounted on them can, if desired, be effectively used separately in high performance audio systems not based on our metalwork.

Our new De Luxe model uses 14 boards which interconnect with gold plated contacts and are designed to have the potentiometers and switches mounted upon them. This system almost eliminates internal wiring, making installation, after their assembly, delightfully straightforward, and as each board can be easily removed in seconds from the chassis, checking and maintenance is so simple that even newcomers to electronics will be able to cope competently with the kit. Additional features of our new model are inclusion of the latest circuit improvements, generously sized heat sinks for heavy duty use, even in tropical climates, and metal oxide resistors throughout for long-term stability and reliability.

Pack	Price	Pack	Price
1. Fibreglass printed circuit board for power amp	£1.15	11. Fibreglass printed-circuit board for power supply	£0.85
2. Set of resistors, capacitors, pre-sets for power amp	£2.50	12. Set of resistors, capacitors, secondary fuses, semiconductors for power supply	£5.40
3. Set of semiconductors for power amp	£6.50	13. Set of miscellaneous parts including DIN skts., mains input skt., fuse holder, interconnecting cable, control knobs	£6.20
4. Pair of 2 drilled, finned heat sinks	£1.10	14. Set of metalwork parts including silk screen printed fascia panel and all brackets, fixing parts, etc.	£8.20
5. Fibreglass printed-circuit board for pre-amp	£1.90	15. Handbook	£0.30
6. Set of low noise resistors, capacitors, pre-sets for pre-amp	£4.10	16. High Quality Teak Veneer cabinet 18.3" x 12.7" x 3.1"	£10.70
7. Set of low noise, high gain semiconductors for pre-amp	£2.40		
8. Set of potentiometers (including mains switch)	£3.50	2 each of packs 1-7, 1 each of packs 8-16 inclusive are required for complete stereo amplifier. Total cost of individually purchased packs	£92.80
9. Set of 4 push-button switches, rotary mode switch	£5.40		
10. Toroidal transformer complete with magnetic screen/ housing primary: 0 117-234 V; secondaries: 33-0-33 V, 25-0-25 V	£12.95		


STANDARD LINSLEY-HOOD 75W AMPLIFIER

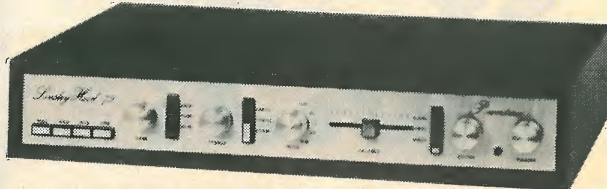

SPECIAL PRICE FOR COMPLETE KIT

£79.80

WIRELESS WORLD FM TUNER

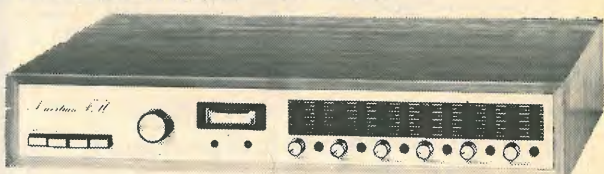

SPECIAL PRICE FOR COMPLETE KIT

£70.20


Pack	Price	Pack	Price
1. Stereo PCB (accommodates 2 rep. amps, 2 meter, amps, bias/erase osc. relay)	£3.35	10. Set of capacitors, rectifiers, L.C. voltage regulator P.C.B. for power supply (Powertran design)	£2.80
2. Stereo set of capacitors, M.D. resistors, potentiometers for above	£7.95	11. Set of miscellaneous parts, including sockets, fuse holder, fuses, interconnecting wire, etc.	£3.40
3. Stereo set of semiconductors for above	£8.50	12. Set of metalwork including silk screened fascia panel, internal screen, fixing parts, etc.	£7.10
4. Miniature relay with socket	£2.90	13. Construction notes	£0.25
5. PCB, all components for solenoid, speed control circuits	£3.80	14. High Quality Teak Veneer cabinet 18.3" x 12.7" x 3.1"	£10.70
6. Goldring-Lenco mechanism as specified	£18.50		
7. Function switch, knobs	£1.90	One each of packs 1-14 inclusive are required for complete stereo cassette deck. Total cost of individually purchased packs	£83.00
8. Dual VU meter with illuminating lamp	£6.95		
9. Toroidal transformer with E.S. screen prim. 0-117V, 234V, Sec. 15V	£4.90		

Matsushita WY 436 AZ head (optional extra) . £4.50 (free with complete kit)

Designed in response to demand for a tuner to complement the world-wide acclaimed Linsley-Hood 75W Amplifier, this kit provides the perfect match. The Wireless World (Skingley and Thompson) published original circuit has been developed further for inclusion into this outstanding slimline unit and features a pre-aligned front end module, excellent a.m. rejection and temperature compensated varicap tuning, which may be controlled either continuously or by push-button pre-selection. Frequencies are indicated by a frequency meter and sliding LED indicators, attached to each channel selector pre-set. The PLL stereo decoder incorporates active filters for "birdy" suppression and power is supplied via a toroidal transformer and integrated regulator. For long term stability metal oxide resistors are used throughout.

AVAILABLE AS SEPARATE PACKS — PRICES IN OUR FREE CATALOGUE

LINSLEY-HOOD CASSETTE DECK

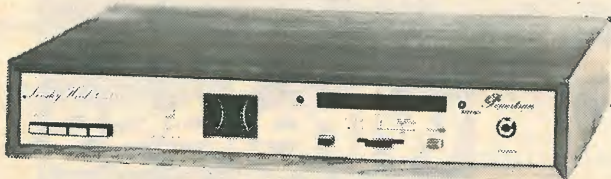


SPECIAL PRICE FOR COMPLETE KIT


£79.60

Published in Wireless World (May, June, August 1976) by Mr. Linsley-Hood, this design, although straightforward and relatively low cost, nevertheless provides a very high standard of performance. To permit circuit optimization separate record and replay amplifiers are used, the latter using a discrete component front-end designed such that the noise level is below that of the tape background. Pushbutton switches are used to provide a choice of equalization time constants, a choice of bias levels and also an option of using an additional pre-amplifier for microphone use. The mechanism used is the Goldring-Lenco CRV, a unit distinguished in its robustness and ease of operation. Speed control and automatic cassette ejection are both implemented by electronic circuitry. This unit which is powered by a toroidal transformer and uses metal oxide resistors throughout offers an excellent match for the Wireless World Tuner and the Linsley-Hood 75 Watt Amplifier. Circuit changes as published in February, 1978, follow-up article are included in the kit AT NO EXTRA COST! A higher performance head (Matsushita WY 436 AZ head as recommended in the follow-up article) is offered as an optional extra but this will be automatically supplied FREE OF CHARGE with all orders for complete kits!

T20+20 AND T30+30 20W, 30W AMPLIFIERS

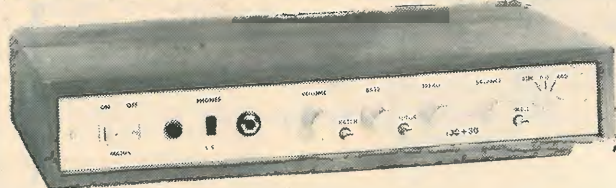

WWII TUNER

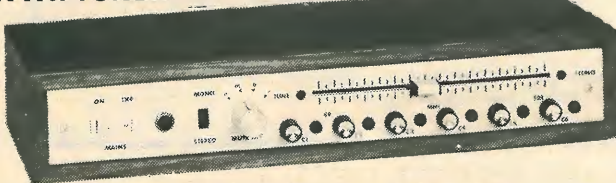

SPECIAL PRICE FOR COMPLETE KIT £47.70

AVAILABLE AS SEPARATE PACKS — PRICES IN OUR FREE CATALOGUE

Following the success of our **Wireless World FM Tuner Kit** this cost reduced model was designed to complement the **T20+20** and **T30+30** amplifiers and the cabinet size, front panel format and electrical characteristics make this tuner compatible with either.

Designed by Texas engineers and described in Practical Wireless, the Texan was an immediate success. Now developed further in our laboratories to include a Toroidal transformer and additional improvements, the slimline T20+20 delivers 20W rms per channel of true Hi-Fi at exceptionally low cost. The **easy to build** design is based on a single F/Glass PCB and features all the normal facilities found on quality amplifiers including scratch and rumble filters, adaptable input selector and headphones socket. In a follow-up article in Practical Wireless further modifications were suggested and these have been incorporated into the T30+30. These include RF interference filters and a tape monitor facility. Power output of this model is 30W rms per channel.


SPECIAL PRICES FOR COMPLETE KITS

T20+20 KIT PRICE £33.10

T30+30 KIT PRICE £38.40

AVAILABLE AS SEPARATE PACKS — PRICES IN OUR FREE CATALOGUE

POWERTRAN SFMT TUNER

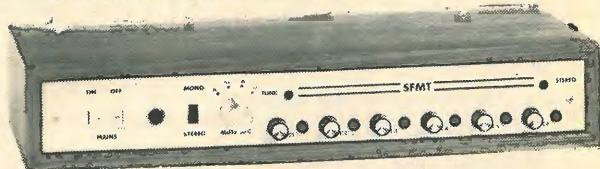

PRICE FOR COMPLETE KIT £35.90

AVAILABLE AS COMPLETE KIT ONLY

This is a simple, low cost design which can be constructed easily without special alignment equipment but which still gives a first-class output suitable for feeding any of our very popular amplifiers or any other high quality audio equipment. A phase-locked-loop is used for stereo decoding and controls include switchable afc, switchable muting and push-button channel selection (adjustable by controls on the front panel). This unit matches well with the **T20+20** and **T30+30** amplifiers.


200 + 200 watt AMPLIFIER

As featured in *Electronics Today International*

**400W rms continuous — 800W peak!
0.03% THD at FULL power!
PLUS all the following features too!**

- * Each channel totally independent with its own stabilised power supply driven by custom designed TOROIDAL transformers!
- * Inherent reliability — monster heat sinks for cool running at the hottest venues — electronic open and short circuit protection!
- * Ultra low feedback (an incredible low 14dB overall!), super high slewing rate (20V/μs), 200W rms continuous to 4 ohm from EACH channel, input sensitivity 0.775V (0dB).
- * Professional quality components, sturdy 19 rack mounting chassis complete with sleeve and feet for free standing work too.
- * Easy to build — plenty of working space with ready access to all components, minimal wiring, extensive instruction suitable for both experienced constructors and newcomers to electronics.
- * Value for money — quality and performance comparable with ready-built amplifiers costing over £600!

PSI 4002 STUDIO MODEL

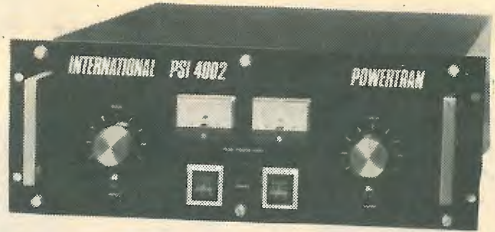

Cabinet size 17.2" x 6.7"

COMPLETE KIT ONLY £196.90 + VAT

**READ THE REVIEW
IN SOUND INTERNATIONAL DEC 78!**

TRANSCENDENT 2000 SINGLE BOARD SYNTHESIZER

As featured in *Electronics Today International*



The kit includes fully finished metalwork, fully assembled solid teak cabinet, filter sweep pedal, professional quality components (all resistors either 2% metal oxide or 1/2% metal film!) and it really is complete — right down to the last nut and bolt and last piece of wire! There is even a 13A plug in the kit — you need buy absolutely no more parts before plugging in and making great music! Virtually all the components are on the one professional quality fibre glass PCB printed with component locations. All the controls mount directly on the main board, all connections to the board are made with connector plugs and construction is so simple it can be built easily in a few evenings by almost anyone capable of neat soldering! When finished you will possess a synthesizer comparable in performance and quality with ready built units selling for between £500 and £700!

**COMPLETE KIT
ONLY
£172.00 + VAT!**

Comprehensive handbook supplied with all complete kits! This fully describes construction and tells you how to set up your synthesizer with nothing more than a multi-meter and a pair of ears!

CHROMATHEQUE 5000 5-CHANNEL LIGHTING EFFECTS SYSTEM

This versatile system featured as a constructional article in *ELECTRONICS TODAY INTERNATIONAL* has 5 frequency channels with individual level controls on each channel. Control of the lights is comprehensive to say the least. You can run the unit as a straightforward sound-to-light or have it strobe all the lights at a speed dependent upon music level or front panel control setting or use the internal digital circuitry which produces some superb random and sequencing effects. Each channel handles up to 500W and as the kit is a single board design wiring is minimal and construction very straightforward.

Kit includes fully finished metalwork, fibreglass PCB, controls, wire, etc. — Complete right down to the last nut and bolt!

**COMPLETE KIT ONLY
£49.50 + VAT**



MPA200 100W MIXER/ AMPLIFIER

**COMPLETE KIT
£49.90
+ VAT**



Wireless World Designs: Full kits are not available for the projects below but PCBs and component sets are stocked. Further details of these and other packs are in our Free Catalogue.

30W Bailey Amplifier	Linsley-Hood Low Distortion Oscillator.	E. F. Taylor Pre-Amplifier
BAIL Pk 1 F/Glass PCB £1.00	LDO Pk 1 Fibreglass PCB £1.65	EFTP Pk 1 Fibreglass PCB (stereo) £1.45
BAIL Pk 2 Resistors, Capacitors £2.35	LDO Pk 2 MO Resistors, capacitors £2.60	EFTP Pk 2 MO Res, caps (stereo) £3.20
BAIL Pk 3 Semiconductors £4.70	LDO Pk 3 Semiconductors £3.90	EFTP Pk 3 Semiconductors (stereo) £4.20

Details of Stuart Tape Recorder and SQ Quadraphonic Decoders are in FREE CATALOGUE

All kits also available as separate packs (eg PCB component sets, hardware sets, etc). Prices in our FREE CATALOGUE.

EXPORT A SPECIALITY!

Our Export Department can readily despatch orders of any size to any country in the world. Some of the countries to which we sent kits last year are shown in this advertisement. To assist in estimating postal costs our catalogue gives the weights of all packs and kits. This will be sent free on request, by airmail, together with our "Export Postal Guide" which gives current postage prices. There is no minimum order charge. Prices same as for U.K. customers but no Value Added Tax charged. Postage charged at actual cost plus 50p documentation and handling. Please send payment with order by Bank Draft, Postal Order, International Money Order or cheque drawn on an account in the U.K. Alternatively for orders over £500 we will accept Irrevocable Letter of Credit payable at sight in London.

**Value Added Tax not included in prices
UK Carriage FREE**

PRICE STABILITY. Order with confidence! Irrespective of any price changes we will honour all prices in this advertisement until March 31st, 1979, if this month's advertisement is mentioned with your order. Errors and VAT rate changes excluded.

U.K. ORDERS: Subject to 12 1/2% surcharge for VAT (i.e. add 1/6 to the price). No charge is made for carriage. *Or current rate if charged.

SECURICounter DELIVERY: For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit.

SALES COUNTER: If you prefer to collect your kit from the factory, call at Sales Counter (at rear of factory). Open 9 a.m.-4.30 p.m. Monday-Thursday.

QUALITY: All components are brand new first grade full specification guaranteed devices. All resistors (except where stated as metal oxide) are low noise carbon film types. All printed circuit boards are fibreglass, drilled roller tinned and supplied with circuit diagrams and construction layouts.

**FOR FURTHER INFORMATION PLEASE WRITE OR
TELEPHONE FOR OUR FREE CATALOGUE**

POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE ANDOVER
ANDOVER HANTS SP10 3NN (0264) 64455

MUSCAT & OMAN
FRANCE
DENMARK
GAMBIA
AUSTRALIA
HONG KONG
NAURU
GERMANY
TUNISIA
LUXEMBOURG
NIGERIA
FINLAND
SOUTH AFRICA
CZECHOSLOVAKIA
AUSTRIA

NEW GUINEA
ISRAEL
GUERNSEY
CYPRUS
BELGIUM
UGANDA
BRUNEI
TRINIDAD
SOUTH WEST AFRICA
ITALY
JAVA
SIERRA LEONE
WINNWARD ISLANDS
CANADA
MALTA


J. L. Linsley-Hood High Quality Cassette Recorder



We are the Designer Approved suppliers of kits for this excellent design. The Author's reputation tells all you need to know about the circuitry and Hart expertise and experience guarantees the engineering design of the kit. Advanced features include: High quality separate VU meters with excellent ballistics. Controls, switches and sockets mounted on PCB to eliminate difficult wiring. Proper moulded escutcheon for cassette aperture improves appearance and removes the need for the cassette transport to be set back behind a narrow finger trapping slot. Easy to use, robust Lenco mechanism. Switched bias and equalisation for different tape formulations. All wiring is terminated with plugs and sockets for easy assembly and test. Sophisticated modular PCB system gives a spacious, easily built and tested layout. All these features added to the high quality metalwork make this a most satisfying kit to build. Also included at no extra cost is our new HS15 Sendust Alloy record/play head, available separately at **£7.60** plus VAT, but included FREE as part of the complete kit at **£81.50** plus VAT. REPRINTS of the 3 articles describing this design **45p** No VAT. REPRINT of Postscript article **30p** No VAT.

TEST CASSETTE TC1

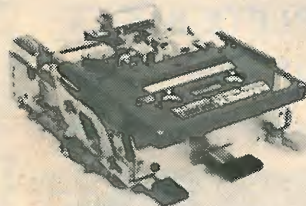Special Hart Copyright test tape makes it easy to set up VU level, head azimuth and tape speed, without test instruments. Suitable for any cassette recorder. Complete with instructions **£2.50** inc VAT.



SCOOP PURCHASE

Everybody thought they had all gone but we found them! Brand New Garrard CT4 cassette mechanisms as used by J. L. Linsley-Hood in the prototype cassette recorder. These come complete with the motor and solenoid boards fitted, wired and tested. Record/play head is a Matsushita WY435z. Equivalent Lenco value **£22**. Our price only **£11.99** plus **£1.50** VAT.

PLASTIC ESCUTCHEON

Suitable for CRV and CT4 mechanisms. As used on our cassette recorder, complete with mounting screws **£1.99** plus VAT.

CASSETTE HEADS

A large range of cassette heads for domestic, industrial and audio visual purposes is available from us. The very best stereo head that we can find is our HS15 Sendust Alloy Super Head. This has an even better high frequency response than our HS14 which it replaces. Unlike cheaper and ferrite types this excellent high frequency performance is combined with a high output, thus maintaining the best possible signal to noise ratio. **Price £7.60** plus VAT.

4-TRACK Record/play head. Scans all 4 tracks on cassette tape. Suitable for auto-reverse mechanisms, film sync, quadrophonics and many other purposes. Standard impedance **£7.40** plus VAT. Full details of these and other heads are in our lists.

LENCO CASSETTE MECHANISMS

We hold stocks of a range of Lenco tape transports for all uses, we can also supply spare parts. For example: CRV Motors complete **£4.00** plus VAT. CRV Drive Belts **90p** plus VAT.

CASSETTES

Our laboratory tests on recorders made us realise how important the choice of cassette is. Wow and flutter is obviously affected by the quality of the housing but the performance differences caused by the tape are enormous. It is possible to record a signal at the same level on two different cassettes one of which will replay at a VU level 10db higher than the other. Poor tape can also lose all signals above 8KHz! These tests enable us to offer what we think is the best value available. The tape is a Super Ferric High Energy Low Noise formulation.

- C90 **80p** } Complete with library case and index card
- C60 **60p** }
- C10 **35p** } Complete in library case. Suitable for Micro Programming.

ALL UK ORDERS ARE POST FREE
Please send 9x4 SAE for lists giving fuller details and price breakdowns.

HART ELECTRONICS

Penylan Mill, Oswestry, Salop

Personal callers are always welcome
but please note we are closed all day Saturday

LINEAR	LM380	60p	SN76013ND	TBA700	180p
AY38500	LM381N	90p	SN76023N	TBA720Q	225p
CA3039	LM382	90p	SN76023ND	TBA750Q	200p
CA3046	LM391	180p	SN76033N	TBA800	80p
CA3060	LM555	25p	SN76033ND	TBA810	100p
CA3065	LM709C	40p	SN76227N	TBA820	100p
CA3076	LM710T05	60p	SN76228N	TBA920Q	280p
CA3080	LM710DIL	65p	SN76660N	TCA270Q	220p
CA3084	LM723T05	40p	TAA300	TCA270S	220p
CA3085	LM723DIL	40p	TAA350	TCA760	300p
CA3086	LM733	120p	TAA550	TCA4500A	450p
CA3088	LM741	20p	TAA570	TD1008	350p
CA3089	LM748	40p	TAA661B	TD1034	450p
CA3090AQ	LM1303N	100p	TAA700	TD2002	300p
CA3123E	LM1458	100p	TAA790	TD2020	300p
CA3130	LM3080	75p	TAD100	TL084	120p
CA3140	LM3900	55p	TAD110	XR320	250p
LF356	LM3909N	65p	TBA120S	XR2206	450p
LF357	MC1310P	140p	TBA120T	XR2207	450p
LM211H	MC1312P	150p	TBA480Q	XR2208	600p
LM300TRS	MC1314P	190p	TBA520Q	XR2216	650p
LM301AN	MC1315P	230p	TBA530Q	XR2567	250p
LM304	MK50398	650p	TBA540	XR4136	150p
LM307N	MM5314	380p	TBA550Q	XR4202	150p
LM308T05	MM5316	480p	TBA560C	XR4212	150p
LM308DIL	NE529K	150p	TBA641A12	YN414	100p
LM309K	NE555	25p		95H90	700p
LM310T05	NE556	90p			
LM311T05	NE562B	400p			
LM317K	SAD1024	1500p			
LM324	SL917B	650p			
LM339	SN76003N	150p			
LM348N	SN76013N	110p			

In 4148 diodes by I.T.T./Texas 100 for £1.50
Static RAM 2102 1024x1 bit 450 nano sec £1.00 each
2112 256x4 bit 450 nano sec £2.50
Murata ultrasonic transducers 40kHz £2.00 each or £3.50 pair
ALL PRICES INCLUDE POST AND VAT

7400	10p	7432	20p	7482	75p	74126	35p	74155	45p	74181	130p
7401	10p	7433	28p	7483	75p	74128	60p	74156	45p	74182	50p
7402	10p	7437	20p	7484	70p	74130	120p	74157	45p	74184	120p
7403	10p	7438	20p	7485	60p	74131	90p	74160	55p	74185	100p
7404	12p	7440	12p	7486	25p	74132	45p	74161	55p	74188	320p
7405	12p	7441	45p	7489	130p	74135	90p	74162	55p	74190	70p
7406	25p	7442	40p	7490	25p	74136	80p	74163	55p	74191	70p
7407	25p	7443	60p	7491	40p	74137	90p	74164	60p	74192	60p
7408	12p	7444	60p	7492	35p	74138	100p	74165	60p	74193	60p
7409	12p	7445	65p	7493	30p	74141	50p	74166	75p	74194	55p
7410	12p	7446	50p	7494	70p	74142	180p	74167	160p	74195	50p
7411	15p	7447	50p	7495	45p	74143	270p	74170	100p	74196	50p
7412	15p	7448	50p	7496	45p	74144	270p	74173	80p	74197	50p
7413	25p	7450	12p	7497	120p	74145	55p	74174	60p	74198	100p
7414	45p	7451	12p	74100	80p	74147	100p	74175	60p	74199	100p
7416	25p	7453	12p	74104	40p	74148	90p	74176	50p	74293	90p
7417	25p	7454	12p	74105	40p	74150	65p	74177	50p	741500	18p
7420	12p	7460	12p	74107	25p	74151	45p	74178	75p	745112	80p
7421	20p	7470	25p	74108	100p	74153	45p	74179	120p		
7422	15p	7472	20p	74109	25p	74154	70p	74180	90p		
7423	20p	7473	25p	74118	75p						
7425	20p	7474	25p	74120	80p						
7426	22p	7475	25p	74121	25p						
7427	22p	7476	25p	74122	35p						
7428	25p	7480	40p	74123	40p						
7430	12p	7481	85p	74125	35p						

T. POWELL
306 St Paul's Road London N1
Telephone 01-226 1489
Barclay / Access credit cards accepted
Shop closed from 21st December to 2nd January

RADFORD

AUDIO MEASURING INSTRUMENTS

- Oscillators**
LDO3. Low Distortion Oscillator **£300.00**
LDO3B. Low Distortion Oscillator, balanced output
..... **£400.00**
- Distortion Measuring Sets**
DMS3. Distortion Measuring Set, manual nulling **£250.00**
DMS4. Distortion Measuring Set, auto-nulling . **£350.00**
- Voltmeters**
HSV1. Audio Microvoltmeter, average responding
..... **£175.00**
HSV2. Audio Microvoltmeter, true r.m.s. reading **£225.00**
- Noisemeters (psophometers)**
ANM1. Audio Noisemeter and Microvoltmeter,
average responding **£200.00**
ANM2. Audio Noisemeter and Microvoltmeter,
true r.m.s. reading **£250.00**
ANM3. Audio Noisemeter and Microvoltmeter,
true r.m.s. and quasi-peak responding **£300.00**

Descriptive leaflets available on request.
RADFORD LABORATORY INSTRUMENTS LTD.
4 High Street, Nailsea, Bristol BS19 1BW
Tel. 02755-6637

"THE PROFESSIONALS"

NEW MODEL CTR-2A 500 MHz & 1 GHz COUNTERS

NEW
Period Measurement

1 us to 1 sec.



10 mv @ 150 MHz

NEW
Built-in Pre-Amp

The New Model CTR-2A Series Counters are designed and built to the highest standards to fulfill the needs of commercial communications, engineering labs and serious experimentors. With an accuracy of +.00005%, the CTR-2A can handle the most critical measurements and is about half the cost of other commercial counters.

If you need a reliable counter at an affordable price, the CTR-2A is the answer.

- Built-in Pre-Amp 10 mv @ 150 MHz
- Period Measurement (Optional)
- 8 Digit 3 LED Display
- Input Diode Protected
- High Stability TCXO Time Base
- 12V-DC Operation (Optional)
- Built-in VHF-UHF Prescaler
- Oven Controlled Crystal ± .5 ppm
- Automatic Dp Placement
- Selectable Gate Times—1 & 1 sec.
- TCXO Std. ± 2 ppm

TRADE & EXPORT ENQUIRIES WELCOME

SOTA COMMUNICATION SYSTEMS LTD.

26 CHILDWALL LANE, BOWRING PARK, LIVERPOOL L14 6TX. Tel: 051-480 5770

NEW! 600 MHz Mini Counter

£145 + 8% VAT



General Purpose Low Cost Counter Without the Sacrifice of Basic Performance

"Check the features we have that some other low-cost counters don't have"

- All Metal Cabinet
- Sensitivity 10 MV at 60 MHz
- Completely Auto Decimal Point
- 8 Digit 4 LED Display
- 240V or 12V Operation
- Selectable Gate Times (1 sec & .1 sec)
- Input Cable Included
- Push Button Controls
- Built-in Preamp
- 12V Input Jack
- Gate Light
- Crystal Time Base 1 ppm

Prices CTR-2A-500 £280 & VAT 8% CTR-2A-1000 £420 & VAT 8%

We are exclusive UK Distributors for **DAVIS ELECTRONICS**, NY, U.S.A. and European Distributors for **LUNAR ELECTRONICS**, San Diego California, U.S.A. (Linear Amplifiers & Receive Preamplifiers)

WW — 027 FOR FURTHER DETAILS

RADIO SHACK LTD for DRAKE



TR-7 Transceiver

Ham Bands with 1.5-30 MHz receive with built-in 150 MHz frequency counter plus option of 0-1.5 MHz receive and /or any transceiving application 1.8-30 MHz.

RADIO SHACK LTD

For Communications equipment including Trio products and Trio testgear.

We are situated just around the corner from West Hampstead Underground Station (Bakerloo line). A few minutes' walk away is West Hampstead Midland Region station and West End Lane on the Broad Street Line. We are on the following Bus routes: 28, 59, 159. Hours of opening are 9-5 Monday to Friday. Closed for Lunch 1-2. Saturday we are open 9-12.30 only. World wide exports.

DRAKE ★ SALES ★ SERVICE

RADIO SHACK LTD

188 BROADHURST GARDENS, LONDON NW6 3AY

Giro Account No. 588 7151. Telephone: 01-624 7174

Cables: Radio Shack, London, NW6. Telex: 23718



The only thing to match our Sales Service is our After-Sales Service

When you get your test equipment serviced or maintained by the London Instrument Repair Centre, you get the same top quality work that made the instrument in the first place—and backed by a full year's warranty too.

Contact the address below for your nearest centre.



LONDON INSTRUMENT REPAIR CENTRE

The service organisation of:





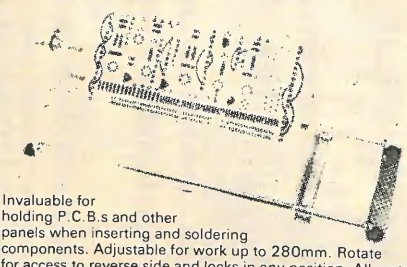

Archcliffe Road, Dover, Kent. Telephone: 0304-202620

Thorn Measurement & Components Division

WW — 062 FOR FURTHER DETAILS

NEW for electronic design engineers!

FIX-PRINT JIG for printed circuits



Invaluable for holding P.C.B.s and other panels when inserting and soldering components. Adjustable for work up to 280mm. Rotate for access to reverse side and locks in any position. All metal.

Write or phone for full details. Price **£10.50** inc. VAT. P&P £1.

PRECISION PETITE LTD

S2 Drill Stand

Robust, all metal with ample throat dimensions. Adjustable height cantilever with lever actuated feed. Spring return. Will accept both drills.

£18.50 inc. VAT P&P 106p


P2 Mk. 2 Drill £19.50 inc. VAT. P&P 86p

S1 Drill Stand

Constructed to take the popular P1 drill and ensure a high degree of accuracy in all types of electrical precision work.

£6.50 inc. VAT. P&P 38p.

P1 Drill £10.00 inc. VAT. P&P 38p



HAVE YOU TRIED SPADE DRILLS for printed circuit boards and other soft materials? No clogging — cooler — cleaner holes — there's a range of sizes. 0.1 to 2.5mm.

119a HIGH STREET TEDDINGTON MIDDLESEX TW11 8HG
TEL: 01-977 0878 Sole UK Distributors

WW — 073 FOR FURTHER DETAILS

TTLS by TEXAS 74175 85p 74176 90p 74177 90p 74178 160p 74179 4000 15p 74180 93p 74181 200p 74182 90p 74183 150p 74184 150p 74185 400p 74186 500p 74187 100p 74188 100p 74189 100p 74190 100p 74191 100p 74192 100p 74193 100p 74194 100p 74195 95p 74196 95p 74197 80p 74198 150p 74199 150p 74200 150p 74201 150p 74202 22p 74203 22p 74204 22p 74999 22p 75000 22p 		93 SERIES 9301 160p 9302 175p 9308 316p 9310 275p 9311 275p 9312 160p 9314 165p 9316 225p 9321 225p 9322 160p 9324 160p 9328 200p 9329 200p 9370 200p 9374 200p LINEAR I.C.s 'AY1-0212 600p 'AY1-1313 688p 'AY1-1320 320p 'AY1-5050 211p 'AY5-1315 600p 'AY5-1317 636p 'CA3019 75p 'CA3048 22p 'CA3048 22p 'CA3060E 220p 'CA3080E 175p 'CA3089E 175p 'CA3090AQ 375p CA3130E 100p CA3160E 100p CA3161E 130p CA3162E 140p FX209 450p ICL7106 750p ICL8038 340p LF358P 95p LF358P 45p LM301An 40p LM311 120p LM318 200p LM324 70p LM339 75p LM348 95p LM377 175p LM380 175p LM381AN 160p LM389N 140p LM709 36p LM710 35p LM725 50p LM733 100p LM741 22p LM747 22p LM748 35p LM3900 400p LM3911 130p LM4136 120p MC1310P 180p MC1458 200p MC1495L 200p MC1496 100p MC3340P 100p VOLTAGE REGULATORS Fixed Plastic TO-220 1A 1ve 1ve 5V 7805 75p 12V 7812 75p 15V 7815 75p 18V 7818 90p 24V 7824 90p 100mA TO-92 5V 7805 35p 12V 7812 35p 15V 7815 35p 18V 7818 35p 19L15 80p OTHER REGULATORS LM309K 135p LM317T 200p LM323K 625p LM723 37p TBA625B 120p TL430 65p 78H05KC 675p 78MGT-C 135p OPTO-ELECTRONICS 2N5777 45p OC171 10p ORP12 80p LEDS O 2 TIL32 IR 75p TIL209 Red 13p TIL211 Gr 25p TIL212 Y 25p TIL216 Red 3p DISPLAYS 3015F 200p DL704 140p DL707 Red 140p 707 Gr 140p DL747 Red 225p 747 Gr 225p FND357 120p FND500 120p FND507 120p MAN3640 175p TIL311 600p TIL312 3 110p TIL321 2 130p TIL330 140p 7750 60 200p 		RESISTORS Carbon film 5% High Stab Min TO BS9110 1/4w 100-1MΩ E12 7p per pack of 5 (one value) £1.20 per 100 (one value) 1/2w 100-10MΩ E12 5p per pack of 3 (one value) £1.50 per pack of 100 (one value) TRANSISTORS AC126 25p AC127/8 25p AC176 25p AC187/8 25p AF116/7 30p AC149 70p AD161/2 45p BC107/8 11p BC109 11p 'BC117 20p 'BC147/8 9p BC158 10p 'BC157 8 10p 'BC159 11p 'BC169C 12p 'BC172 12p 'BC177 8 17p BC179 17p BC182 3 10p BC184 11p BC187 30p BC212 3 11p BC241 12p BC461 36p BC477 8 30p BC516 7 50p BC547/8 16p BC548C 16p BC549C 16p BC557/8 16p BC559C 18p BCY70 18p BCY71/2 22p BD131 12p BD135 56p OC29 13p OC35 130p RD208 200p R2010B 200p RF200 32p RF244B 35p RF256 70p RF257/8 32p RF259 36p RF339 30p RF340 30p RF341 30p RF342 30p RF343 30p RF344 30p RF345 30p RF346 30p RF347 30p RF348 30p RF349 30p RF350 30p RF351 30p RF	
-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	--	--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	--	------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	--

SERVICE TRADING CO

WHY PAY MORE?!

MULTI RANGE METERS Type MF15A.
A.C./D.C. volts 10, 50, 250, 500, 1000 Ma.
0.5, 0.10, 0.100, Sensitivity 2000V, 24 ranges.
Dimensions 133 x 92 x 45mm. Price **£7.00**
plus 50p P&P (**£8.10** inc. VAT & P).



TRIAC.

Raytheon tag symmetrical Triac. Type Tag 250/500v. 10 amp 500 piv.
Glass passivated plastic triac. Swiss precision product for long term
reliability **£1.25** P&P 10p (**£1.46** inc. VAT & P) (inclusive of date and
application sheet). Suitable Diac **22p**.

0 to 60 MINUTES CLOCKWORK TIMER.

Double pole 15 amp 230AC. Contacts (no dial) **£1.50**, P&P 30p (**£1.94**
inc. VAT & P). N.M.S.

MERCURY SWITCH

Size 27m x 5mm, 10 for **£5.00**, P&P 30p, total
including VAT **£5.72**. Min. quantity 10. N.M.S.



230 VOLT AC FAN ASSEMBLY

Powerful continuously rated AC motor complete
with 5 blade 6 1/2" aluminium fan. New reduced
price **£3.00** P&P 65p (**£3.94** inc. VAT & P).
N.M.S.



21-WAY SELECTOR SWITCH with reset coil

The ingenious electro mechanical device can be
switched up to 21 positions and can be reset from
any position by energising the reset coil.
230/240v. A.C. operation. Unit is mounted on
strong chassis. Complete with cover. Price **£5.50**
P&P 75p (**£6.75** inc. VAT & P). N.M.S.



VORTEX BLOWER AND VACUUM UNIT

Dynamically balanced totally enclosed 9"
rotor with max. air delivery of 1.5 cubic
metres per min. Max. static pressure
600mm W.G. Suction or blow from 2
side-by-side 37mm I.D. circular apertures
fitted to base of unit. Powerful continuously
rated 115v. a.c. motor mounted on alloy base
with fixing facilities. Dimensions: Length
22cm x width 25cm x height 25cm.
These units are ex-equipment but have had minimum use. Fully tested
prior to despatch. Price **£12** + **£1.50** P&P (**£14.50** inc. VAT & P).
Suitable transformer for 230/240v a.c. **£6** + **£1 P&P** (**£7.56** inc. VAT & P).




CENTRIFUGAL BLOWER

Smith type FF8 1606 022 220/240V A.C.
Aperture 10x4 1/2cm overall size 16x14cm. Price
£3.75 P&P 75p (incl. VAT **£4.86**). Other types
available. S.A.E. for details. N.M.S.



24V DC BLOWER UNIT

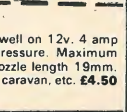USA made. 24V D.C. 8 amp blower that operates well on 12v. 4 amp
D.C. producing 30 cu. ft. min. at normal air pressure. Maximum
housing dia. 110mm. Depth inc. motor 75mm. Nozzle length 19mm.
dia. 22mm. Ideal for cooling mobile equipment, car, caravan, etc. **£4.50**
P&P 75p. (**£5.67** inc. VAT & P). N.M.S.




MINIATURE UNISELECTOR

12V. 11 way 4 bank (3 non-bridging, 1 homing) **£2.50** P&P 35p.
(**£3.08** inc. VAT & P).


MICRO SWITCHES

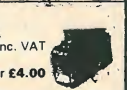Sub min lever m/switch type MML46, 10 for **£2.50**.
Type 3 115M 906T 10 for **£2.50** post paid (**£2.70** inc. VAT
& P).
18F lever operated 20a. c/o. mf. Unimax USA. 10 for **£4.00**.
plus 50p P&P (min. order 10) (**£4.86** inc. VAT & P).
D.P. C/O lever m/switch, mfg. by Cherry Co. USA. Precious metal, low
resistance contacts. 10 for **£2.50**, P&P 30p. Total inc. VAT **£3.02** (min
10). N.M.S.



NEW HEAVY DUTY SOLENOID

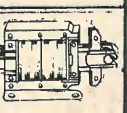Mfg. by Magnetic Devices. 240v A.C.
Operation approx. 10lb. pull at 1/4in.
Rating intermittent. Price **£4.00** P&P 60p.
(**£4.96** inc. VAT) N.M.S.



PYE EYETHER

240v A.C. Solenoid. Approx. 1 lb. pull. 1/4in
travel. intermittent rating. Price **£1.00** P&P
20p (**£1.30** inc. VAT & P). N.M.S.

WESTOOL TYPE MMS MODEL 2

240V AC. Approx. 1 1/2 lb pull at 1/2 in. Rating 1. Price **£1.50** P&P 20p
(**£1.94** inc. VAT & P). N.M.S.

240 A.C. SOLENOID OPERATED FLUID VALVE

Rated 1 p.s.i. will handle up to 7 p.s.i. Forged brass
body, stainless steel cone and spring 1/2 in. b.s.p. inlet
outlet. Precision made. British mfg.
PRICE **£3.50** Post 50p (**£4.32** inc. VAT & P). N.M.S.



INSULATION TESTERS (NEW)

Test to I.E.E. spec. Rugged metal construction,
suitable for bench or field work, constant speed
clock. Size L. 8 in., W. 4 in. H. 6 in., weight 6 lb.
500 VOLTS 500 megohms **£48.00**, Post 80p (**£53.78** inc. VAT & P)
1000 VOLTS 1000 megohms **£55.00**, Post 80p (**£60.26** inc. VAT & P)
SAE for leaflet.



YET ANOTHER OUTSTANDING OFFER

New IMFD 600V Duffler wire ended capacitors, 10 for **£1.50** P&P 50p.
(**£2.16** inc. VAT + P&P). (Min 10).
N.M.S.

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230 v. A.C. 50/60
OUTPUT VARIABLE 0/260V A.C.



BRAND NEW. All types.
200W (1 Amp) fitted A/C

volt meter	£14.50
0.5 KVA (Max. 2 1/2 Amp)	£17.00
1 KVA (Max. 5 Amp)	£22.50
2 KVA (Max. 10 Amp)	£37.00
3 KVA (Max. 15 Amp)	£45.50
5 KVA (Max. 25 Amp)	£74.00
10 KVA (Max. 50 Amp)	£168.00
17 KVA (Max. 75 Amp)	£260.00

Carriage extra

LT TRANSFORMERS

0-10v-15v at 3 amp. (ex new equip) **£2.50** P&P 50p (**£3.24** inc. VAT)
13-0-13v at 1 amp **£2.50** P&P 50p (**£3.24** inc. VAT)
25-0-25v at 2 1/2 amp **£4.50** P&P 75p (**£5.67** inc. VAT & P)
0-4v/8v/24v/32v at 12 amp. **£18.50** P&P **£1.90** (**£22.03** inc. VAT & P)
0-6v/12v at 20 amp **£14.70** P&P **£1.50** (incl. VAT **£17.70**)
0-12v at 20 amp. or 0-24v at 10 amp. **£12.00** P&P **£1.50** (**£14.58** inc. VAT & P)
0-6v/12v at 10 amp. **£8.25** P&P **£1.25** (incl. VAT **£10.26**)
0-6v/12v/17v/18v/20v at 20 amp. **£18.00** P&P **£1.50** (**£22.10** inc. VAT & P)
0-10v/17v/18v at 10 amp. **£10.50** P&P **£1.50** (incl. VAT **£12.98**)
Other types in stock; phone for enquiries or send see for leaflet.

ROTARY VACUUM AIR COMPRESSOR & PUMP

Carbon vane oil-less. 100/115v a.c. 1/12 h.p.
motor 50/60 cycle 2875/3450 rpm. 20"
vacuum 1.25 c.f.m. 10 p.s.i. (approx. figures).
Mfr. by Gast Co. Fraction of maker's price **£14.00**
P&P **£1.00** (Total: **£15.20** inc. VAT). Suitable
transformer **£3.50** P&P 50p. (Total: **£3.78** inc.
VAT). N.M.S.



BLOWER/VACUUM PUMP

3 phase A.C. motor. 220/250v or 380/440v. 1.425 rpm 1/4 hg cont.
Direct coupled to William Allday Alcosa carbon vane blower/vacuum
pump. 0.9 cfm 8 hg. Price **£22.00** P&P **£2.00**. (**£25.92** inc. vat + p).
N.M.S.

STROBE! STROBE! STROBE!

HY-LIGHT STROBE KIT Mk. IV

Latest type Xenon white light tube. Solid state timing and triggering
circuit. 230/240 volt A.C. operation. Speed adjustable 1-20 f.p.s.
Designed for large rooms, halls, etc. Light output greater than many
(so called 4 Joule) strobes. Price **£18.00** post **£1** (**£21.60** inc. VAT
& P). Specially designed case and reflector for Hy-Light **£8.80** Post
£1.00 (**£10.58** inc. VAT & P).

ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

4ft. 40 watt **£8.70** (callers only). 2ft. 20 watt **£8.20**. Post 75p.
(**£7.51** inc. VAT & P). (For use in stan bin fittings). Mini 12in. 8
watt **£2.80**. Post 35p (**£3.40** inc. VAT & P). 9in. 6 watt **£2.25**
Post 35p (**£2.81** inc. VAT & P). 6in. 4 watt **£2.25** Post 35p (**£2.81**
inc. VAT & P).

Complete ballast unit. Either 6", 9" or 12" tube 230V. A.C. op.
£3.50 plus P&P 45p (**£4.27** inc. VAT & P). Also available for 12V.
D.C. op. **£3.50** plus P&P 45p (**£4.27** inc. VAT & P).

400w UV lamp and ballast complete **£31.50**. Post **£3**. (**£37.26**
inc. VAT & P) 400w UV lamp only **£11.25** Post **£1.20** (**£13.45**
inc. VAT & P).

SQUAD LIGHT

A new conception in light
control. Four channels each
capable of handling 750 watts
of spotlights or dozens of small mains lamps. Seven programs all speed
controlled plus flash modulation; effectively giving 14 different displays.
Makes sound-to-light obsolete. Completely electrically and mechanically
noise free. Price only **£80.00** (**£85.61** inc. vat + p)
S.A.E. (Footscap) for further details. Post 75p



WIDE RANGE OF DISCO LIGHTING EQUIPMENT

S.A.E. (Footscap) for details

XENON FLASH GUN TUBES

Range of Xenon tubes available from
stock. S.A.E. for full details.



RELAYS

Wide range of AC and DC relays available
from stock. Phone or write in your en-
quiries.

230/240V A.C. Relays: Arrow, 2 c/o. 15 amp **£1.50** (**£1.84** inc. VAT
& P).
T.E.S. open type 3 c/o. 10 amp **£1.10** (**£1.40** inc. VAT & P). Omron or
Keyswitch 1 c/o. 7 amp **£1.00** (**£1.30** inc. VAT & P).

D.C. Relays: Open type 8/12V 3 c/o 7 amp **£1.00** (**£1.30** inc. VAT & P).
Sealed 12V 1 c/o 7 amp octal base. **£1.00** (**£1.30** inc. VAT & P). Sealed
12V 2 c/o 7 amp octal base. **£1.25** (**£1.56** inc. VAT & P). Sealed
12V 3 c/o 7 amp 11-pin. **£1.35** (**£1.67** inc. VAT & P). 24V. Sealed 3
c/o 7 amp 11-pin. **£1.35** (**£1.67** inc. VAT & P) (amps = contact rating).
P&P on any Relay 20p.
Other types available - phone for details. N.M.S.


Diamond H heavy duty A.C. relay 230/240v a.c., two c/o contacts 25
amps res at 250V a.c. **£2.50** P&P 50p. (**£3.24** inc. VAT + P&P). Special
base 50p.

VAT AT CURRENT RATE
MUST BE ADDED
TO ALL ORDERS
FOR THE TOTAL VALUE OF GOODS INCLUDING
POSTAGE UNLESS OTHERWISE STATED

GEARED MOTORS

100 R.P.M. 115 lbs. ins.!!

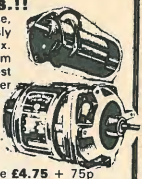115 lbs. ins., 110 volt, 50Hz, 2.8 amp, single phase,
split capacitor motor. Immense power. Continuously
rated. Totally enclosed. Fan cooled. In-line gearbox.
Length 250mm. Dia. 135mm. Spindle Dia. 15.5mm
Length 115mm. ex-equipment tested **£12.00** Post
£1.50 (**£14.58** inc. VAT & P). Suitable transformer
230/240 volt **£8.00** Post 75p (**£8.45** inc. VAT & P).
R&T



GEARED MOTORS

28 r.p.m., 20lb. inch 115v a.c. Reversible motor.
71 r.p.m., 10 lb. inch. 115v a.c. Reversible motor.
Both types similar to above drawing. Price either type **£4.75** + 75p
P&P. (**£5.94** inc. VAT + P&P)
Supplied with transformer for 240v a.c. operation **£7.25** + P&P **£1**.
(**£8.91** inc. VAT + P&P).
N.M.S.

FRACMO MOTOR

56rpm 50lbs inch 240vAC reversible, 0.7 amp.
sharplength 35mm, dia. 16mm, weight 6 kilos
600 grams. Price **£15.00** P&P **£1.50** (**£17.82**).
N.M.S.



PARVALUX MOTOR TYPE S.D.2

12v D.C. shunt 1/30th ph motor. Continuously rated 4000 rpm. Price
£10.00 P&P 75p (**£11.61** inc. VAT & P). N.M.S.

PARVALUX 230/250V A.C. MOTOR

Type SD18 240V AC reversible 30 rpm 50lbs inch.
Price **£15.00** P&P **£1.50** (**£17.82** inc. VAT). N.M.S.



CITENCO

FHP motor type C 7333/15 220/240v A.C. 19
rpm reversible motor, torque 14.5 kg. Gear ratio
144:1. Brand new incl. capacitor, our price
£14.25 + **£1.25** P&P (**£16.74** inc. VAT & P).
N.M.S.



CRUZET - 230/240V AC 2 rpm synchronous geared motor £2.90


P&P 30p (Total: **£3.48** inc. VAT). N.M.S.
HAYDON - 230/240V AC 1 rpm synchronous geared motor **£2.90**
P&P 30p (Total: **£3.46** inc. VAT). N.M.S.

REVERSIBLE MOTOR 230V A.C.

General Electric 230V A.C. 1,600 r.p.m. 0.25 amp. Complete with
anti-vibration mounting bracket and capacitor. O/A size 110mm x
90mm. Spindle 5/16 dia. reversing. Ex-equipment tested **£3.00**. Post
50p (**£3.78** inc. VAT & P).


RODENE UNISEIT TYPE 71 TIMER

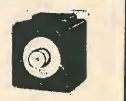0-60 sec. 230V AC operation. Incorporating a lapsed
time indicator and repeat facilities. A precision
motorised timer ideal for process timing, photography,
welding, mixing etc. Price **£6** P&P 60p
VAT & P. N.M.S.



METERS (New) - 90mm DIAMETER

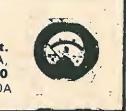AC Amp. Type 62T2. 0-1A, 0-5A, 0-20A. AC Volt.
0-15V, 0-300V. DC Amp. Type 65C5. 0-2A, 0-10A,
0-20A, 0-50A DC Volt. 0-15V, 0-30V. All types **£3.50**
ea + P&P 50p (**£4.32** incl. VAT) 0.5A DC 0-100A
D.C. Price **£5.00** + 50p P&P **£5.94** incl. VAT



'VENNER TYPE' ERD TIME SWITCH

200/250V AC 30 amp. 2 on/2 off every 24 hrs. at any
manually pre-set time. 36-hour spring reserve and day
omitting device. Built to highest Electrical Board
specification. Price **£7.75** P&P 75p (**£9.18**). R & T.



SANGAMO WESTON TIME SWITCH

Type S251 200/250V AC 2 on/2 off every 24 hours. 20 amps contacts
with override switch, diameter 4" x 3". price **£6.00** P&P 50p (**£7.02**
inc. VAT & P). Also available with Solar. R & T.

AEG TIMESWITCH

200/250V AC 1 on/1 off every 24 hours. 80 amp contact (ideal storage
heaters). Spring reserve **£10.00** P&P 50p (Total: **£11.34** inc. VAT).
N.M.S.

AC MAINS TIMER UNIT

Based on an electric clock, with 25 amp, single-
pole switch, which can be preset for any period up
to 12 hrs. ahead to switch on for any length of
time, from 10 mins. to 6 hrs. then switch off. An
additional 60 min. audible timer is also incorporated.
Ideal for Tape Recorders, Lights, Electric
Blankets etc. Attractive satin copper finish. Size
135 mm x 130 mm x 60 mm. Price **£2.25**. Post
40p. (Total inc. VAT & Post **£2.87**). N.M.S.



POWER RHEOSTATS

New ceramic construction, vitreous enamel
embedded winding, heavy duty brush assembly,
continuously rated.

25 WATT 10, 25, 100, 150, 250, 500, 1k, 1.5k ohm **£2.40** Post
20p (**£2.81** inc. VAT & P). **50 WATT** 100, 250 ohm **£2.90** Post 25p
(**£3.40** inc. VAT & P). **100 WATT** 1 / 5 / 10 / 25 / 50 / 100 / 250
/ 500 / 1k / 1.5k / 2.5k / 5k ohm. **£5.90** Post 35p (**£6.75** inc. VAT
& P).

Black Silver Skirted Knob calibrated in Nos. 1-9, 1 1/2 in dia brass
bush. Ideal for above Rheostats. **24p** ea.

SPECIAL OFFER

BERCO type L RHEOSTAT
85 ohm 300 watt 1.86 amp **£7.50** P&P 50p (Total: **£8.64** inc. VAT).
N.M.S.

FRACMO MOTOR

1400 rpm. HP 1/30 continuously rated 115V AC fitted with
anti-vibration cradle mounting. Supplied complete with transformer for
230/240V AC op. **£10.00** P&P **£1.00** (Total: **£11.88** inc. VAT). N.M.S.


N.M.S. - New Manufacturers' Surplus
R & T - Reconditioned and Tested

ACCOUNT CUSTOMERS MIN. ORDER £10.00

ALL MAIL ORDERS. ALSO CALLERS AT:
**57 BRIDGMAN ROAD, CHISWICK,
LONDON, W4 5BB. Phone: 01-995 1560**
Closed Saturdays

SERVICE TRADING CO.
SHOWROOMS NOW OPEN
AMPLE PARKING

PERSONAL CALLERS ONLY
9 LITTLE NEWPORT STREET,

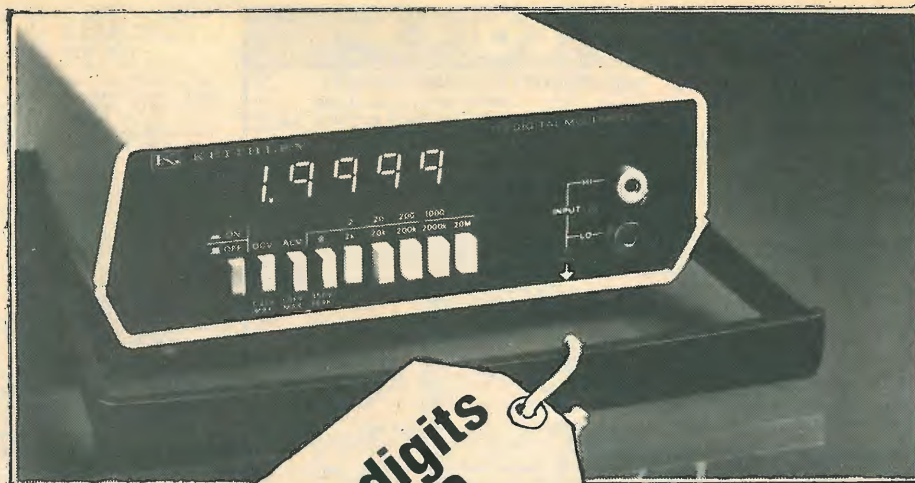

Model 178

**Now ...
the next
generation of
bench DMMs!**

Two New Keithley Models offer uncompromising performance and outstanding value!

- Accuracy 3 1/2's can't match 0.04% + 1 digit on dc volts and ohms
- Large, bright, 20,000-count LED display that's quick and easy to read.
- Convenient bench size that won't get "lost" yet doesn't crowd.
- Exceptional reliability.

Model 178 offers functions and ranges for most measurement needs 100 μ V to 1200V dc, 100 μ V to 1000V ac, 0.1 Ω to 20M Ω .

Model 179 is a full-function, multi-feature model offering the same advantages as the 178. Plus

TRMS AC; 10 μ V Sensitivity; Hi and Lo Ohms; AC and DC Current Yet it's still half the price you'd expect. Only £199.


Both models feature designed-in reliability Rugged circuits use a minimum of parts — high quality, off-the-shelf parts — carefully assembled and tested by Keithley. Outstanding overload protection and rugged mechanical design keep both units going even after severe abuse. One-year accuracy specifications minimise recalibration costs. A battery option, user installable, gets you off "line" for critical measurements or for field use.

For complete specifications on the 178 and 179, call Keithley Instruments, 1 Boulton Road, Reading. Phone 0734 861287

KEITHLEY
The measurement engineers.

WW-029 FOR FURTHER DETAILS

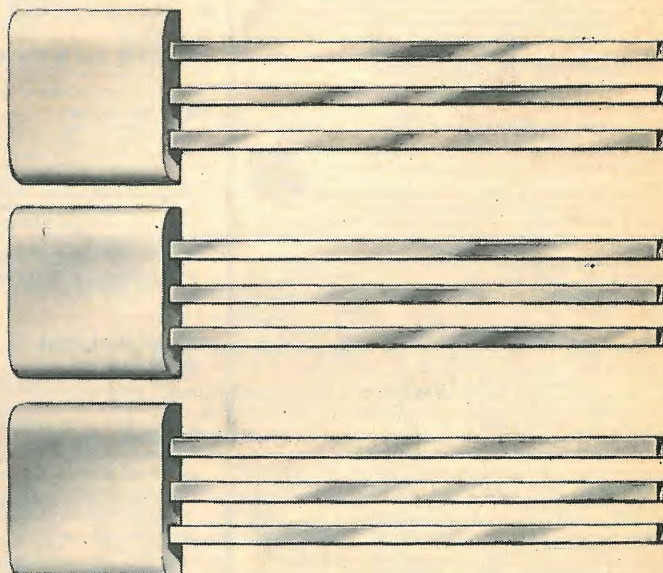**Double your diodes
with Ferranti
and save
on system costs.**



If you're using glass diodes, here's a gentle warning. Pre-forming and insertion costs can make them more expensive than you think on the assembly line.

Ferranti ZDX double diodes save you all that. Each package contains two connected diodes so you save both on insertion cost and component counts.

The ZDX range includes both switching and general purpose diodes.

Common anode, common cathode or series pair.

Ready to plug into your PCB—another saving.

And they're competitively priced. Saving again.


Data and samples? Contact:

Discrete Components Marketing, Ferranti Electronics Limited, Fields New Road, Chadderton, Oldham CL9 8NP. Call—061-624 0515.

FERRANTI
Semiconductors

WW-037 FOR FURTHER DETAILS


Introducing Acorn

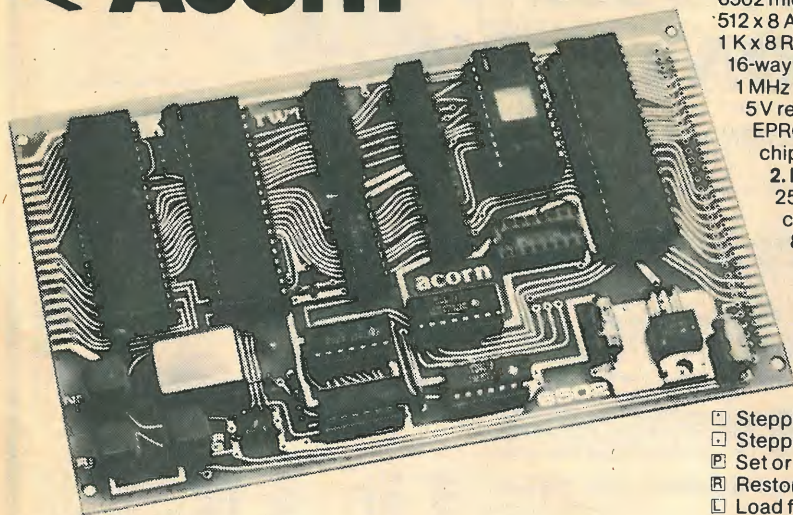

A professional MPU card

Designed as a general purpose industrial controller based on the 6502 MPU, this card is complemented by a matching Eurocard hex keyboard and CUTS standard cassette interface, to create the new...

Acorn Microcomputer

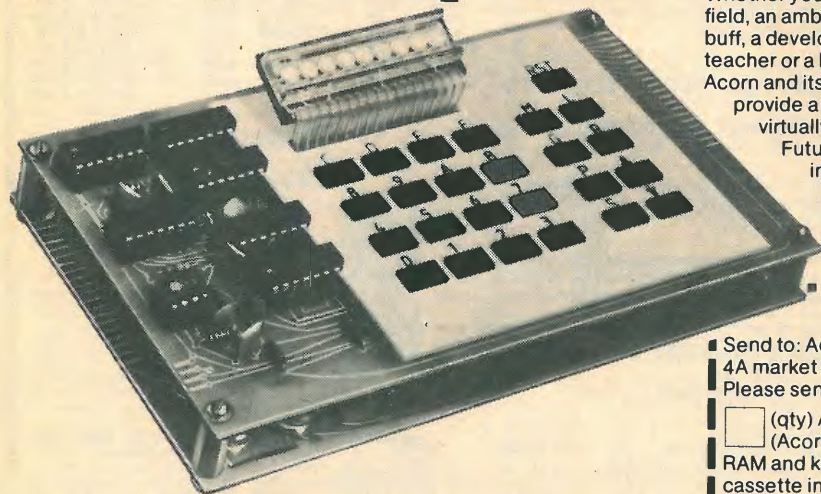

This compact stand-alone micro-computer is based on standard Eurocard modules, and employs the highly popular 6502 MPU (as used in APPLE, PET, KIM, etc). Throughout, the design philosophy has been to provide full expandability, versatility and economy. Take a look at the full specification, and see how Acorn meets your requirements

Acorn technical specification

The Acorn consists of two single Eurocards:

- 1. MPU card**
6502 microprocessor
512 x 8 ACORN monitor
1 K x 8 RAM
16-way I/O with 128 bytes of RAM
1 MHz crystal
5 V regulator, sockets for 2 K EPROM and second RAM I/O chip.

- 2. Keyboard card**
25 click-keys (16 hex, 9 control)
8 digit, 7 segment display
CUTS standard crystal controlled tape interface circuitry

Keyboard Instructions:

M Memory Inspect/
Change (remembers last address used)

- Stepping up through memory
- Stepping down through memory
- Set or clear break point
- Restore from break
- Load from tape
- Store on tape
- Go (recalls last address used)
- RST Reset

Compact, easy to use Acorn Monitor includes the following features:

- System program
- Set of sub-routines for use in programming
- Powerful de-bugging facility displays all internal registers
- Tape load and store routines

Acorn - with real expandability!

The standard Acorn is fully expandable to 65 K of memory, and the Acorn bus is available on the 64-way edge-connector. Whether you're a beginner in the field, an ambitious home computer buff, a development engineer, a teacher or a businessman, the Acorn and its family of modules will provide a practical solution in virtually every situation.

Future expansion for Acorn includes the following software and hardware.

Software

Basic interpreter, assembler, dis-assembler, editor, TTY and disk operating system.

Hardware

Memory-mapped VDU system (with upper and lower case ascii graphics and hardware scroll) floppy disk controller for 5 1/4 in and 7 in disks, a memory card with 8 K bytes of static RAM (2716) and 4 K bytes of EPROM (2114), a PROM programmer (for all types of PROM usable on ACORN a full ascii keyboard, a backboard for the ACORN bus, and a Eurocard racking system.

Acorn Operating Manual

With Acorn, you'll receive an operating manual that covers computing in full, from first principles of binary arithmetic, to efficient hex programming with the 6502 instruction set. The manual also includes a listing of the monitor programs and the instruction set, and other useful tabulations; plus a selection of 12 interesting and educative program samples.

Acorn, as a kit or fully assembled, the choice is yours with this coupon!

With such flexibility at such a price, the ACORN package is one you'll want to make the most of, soon. Whether you're a hobbyist, computer technician, R&D engineer or a computer user, Acorn provides you with a highly cost-effective basis for a computer or an industrial development system.

To get your Acorn, just complete this coupon, enclose a cheque (or an official company order) and send it to us. If Acorn doesn't meet your highest expectations, return it to us as received within 14 days, for a full cash refund.

Acorn comes with a comprehensive guarantee covering replacement of any faulty components, plus an expert service facility.

Take another look at Acorn's spec, check the price again, then send your order today!

**Acorn Computers Ltd,
4A Market Hill, Cambridge, Cambs.
Cambridge (0223) 312772.**

Order form

Send to: Acorn Computers Ltd, 4A market Hill, Cambridge, Cambs. Please send me the following:

(qty) Acorn Microcomputer(s) (Acorn MPU card with 1 K RAM and keyboard card with cassette interface, in kit form, with assembly instructions) at £65.00 plus £5.20 VAT

(qty) Acorn Microcomputer(s), as above, assembled and tested at £75.00 plus £6.00 VAT

(qty) Acorn controller(s) (minimum configuration MPU board with 6502, RAM I/O, TTL logic and capacitor-controlled clock at £35.00 plus £2.80 VAT (Post and packing free on all orders) Please allow 28 days for delivery. I enclose a cheque for £..... (indicate total amount) made out to Acorn Computers Ltd.

I enclose an official company order

Please send me further details of this and other Acorn options

Name _____

Address _____


**ACORN
COMPUTER**
Regd. No. 1403810.

C. T. ELECTRONICS (ACTON) LTD.

267 & 270 ACTON LANE, LONDON W4 5DG. Telephone: 01-994 6275

Registered in England 1179820

CMOS

4000UB	0.17	4027B	0.44	4075B	0.20
4001UB/B	0.17	4028B	0.77	4076B	1.17
4002UB/B	0.17	4029B	1.03	4077B	0.39
4006B	1.04	4032B	0.89	4078B	0.20
4007UB	0.18	4034B	1.71	4081B	0.20
4008B	0.87	4040B	0.97	4082B	0.20
4011UB/B	0.18	4043B	0.88	4093B	0.80
4012UB/B	0.20	4044B	0.84	40160B	1.19
4013B	0.43	4049UB	0.50	40161B	1.19
4014B	0.83	4050B	0.43	40162B	1.19
4015B	0.83	4051B	0.82	40163B	1.19
4016B	0.48	4052B	0.82	40174B	0.85
4017B	0.79	4053B	0.82	40175B	0.86
4018B	0.83	4066B	0.55	40194B	1.19
4020B	1.11	4068B	0.20	4510B	1.01
4021B	0.90	4069UB	0.20	4511B	1.25
4022B	0.82	4070B	0.46	4512B	0.91
4023UB/B	0.18	4071B	0.20	4516B	1.01
4024B	0.70	4072B	0.20	4518B	0.97
4025UB/B	0.20	4073B	0.20	4528B	0.80

6" IMHOFF 19" Racks. Brand new. **£25.00 each** +8% VAT.

We have at time of press over 2 million Electrofil & Welwyn Metal Oxide Resistors well below manufacturer's price. Phone for details.

This advertisement is a fraction of stock held by us. Phone for details:

No mail order accepted unless over £5.00. Hours of business 9.30am-6pm, Mon-Sat continuous. Carriage & packing charge extra. Government, colleges and export welcome.

We have considerable stock of PT10 & PT15 Presets. Special price for PT15 of the following value: 100Ω, 1k5, 2k2, 4k7, 10k, 22k, 47k, 100k. All the above values @**£25/1,000**. @12½% VAT. Retail prices all values 10p either PT10 size or PT15. Open or enclosed.

2200µF 100V computer grade electrolytic Mullard **£1.00** +VAT. 12½%.

PL259 Plugs with Reducers **50p each** retail. SO239 to suit Plug (259) Bulkhead Socket **45p each** +8% VAT.

BNC Plugs. Brand new. **30p** +8% VAT. Either 50Ω or 75Ω.

N Connectors available at a fraction of list price. Phone for details.

Sealectro Plugs (miniature) Conhex for VHF & UHF applications

75p straight entry type 51-130-3187-91, **90p** right-angled gold plated type 055-014-3196.

All the above RF Connectors are held in depth and are brand new.

Cassette Monotape Heads ¼" **£1.00 each**. Brand new.

Cassette Erase Tape Heads ¼" **£1.00 each**. Brand new. +12½% VAT.

Potentiometers W. Wound 1Ω-100v by A. B. or Colvern Ltd, 1½ watt **40p**, 3 watt **60p**, 5 watt **80p**.

ROTARY SWITCHES available in 30 different types, prices range from **45p-£1.20** +8%. PREH Television Push-button Tuner Units. 4 and 6 button, brand new in original boxes. **75p each** +12½% VAT. Large quantity available.

SPECIAL OFFER 100k LIN Mono Slider Potentiometer by Noble (metal body). 63mm length, **price 20p each** +12½% VAT. All boxed as original. **Discount on quantity.**

SPECIAL OFFER 2k 2 LIN single gang Potentiometer by Egen. ¼" shaft, ⅝" bush plastic spindle. **Price 10p each** +12½% VAT. **Discount on quantity.**

Miniature Moulded Track Presets by Plessey. Screwdriver operation. 0.25W dissipation. PCB fixing. **15p each** +8%.

Open Cermet Presets. Most values in stock. **15p each** +8% VAT.

Trimpots 100-500kΩ 10 turn and 20 turn **50p each** +8% VAT. By MEC, Paignton, Bournes Mini Square, ¾" rectangular or 1½" rectangular Cermet or W. Wound.

Convergence Pots. Most television values. **20p each** +12½% VAT.

MOTORS (+8% VAT)

PAPST Motor HSZ 20-25-2-425 EEM. 42V 50C/S 10µf cap across size: < 6cm Diam 3.4cm. Shaft: < 1.7cm Diam 4mm. **£1.00 each.**

Smiths Motor 240V 50 C/S 3-hole fixing. Spaced 4.75cm 3rpm. Shaft 1.5cm 3mm diam. **£1.50 each.**

Cassette-deck Motor by Fujiya. 6V DC. <3.25cm. Diam. 3.5cm. Shaft diam 2mm <.9mm. 3-hole fixing 4cm to centres. **£1.25 each.**

General Time Motors with clutch. 240V 1/5rpm. 2-hole fixing. 4.75cm, 3cm depth. Body diam. 4.85cm. Shaft length 1cm, diam. 3mm. **£1.50 each.**

Crouzet Motors. Speeds 6rpm and 10rpm. 2-hole fixing. 4.75cm, 3.9cm depth. Body diam. 4.5cm. Shaft <0.9cm. Diam. 4mm. **£1.50 each.**

Miniature DC Motor 4-15V operation. High torque. <3.5cm. Body diam. 2cm, 2-hole front fixing, shaft diam. 1.75mm. **£1.00 each.**

Plus large stocks General Time Motors in the following speeds: 1/180, ½ rph 12V DC; 1/5rpm 240V; 1rpm 240V.

Miniature Motor Clutches by General Time (USA) 24V operation. Body diam. 2.2cm, 6mm shaft centre. **£1.30 each.**

PUSHBUTTON SWITCH UNITS

4-way 2P/CO. **50p each**. 7-way 5.2P/CO 2.4P/CO. **80p each**. By A. B. Electronics. 8% VAT.

Mullard Pot Core FX2241 **30p each** 8% VAT. Mullard Ex-computer Electrolytic 20,000µF/45V. **40p each.**

Toko FM, AM, IF Coils etc. Stockholding now in excess of ½ million PCS. Any style available to callers only. **10p each** or 50 PCS for **£1.00** +VAT 12½%.

EDGE CONNECTORS

(8% VAT)

Single-sided 0.1 pitch. 40-way fixing holes 118mm — RS type **£1.20**. 24-way fixing holes 73mm — UCL **70p**.

Single-sided 0.15 pitch. 15-way fixing holes 75mm — gold plated — EB **60p**. 18-way fixing holes 85mm including locating pin. **75p**. 32-way fixing holes 136mm — gold plated — EB. **£1.50**. 27-way fixing-holes 122mm **£1.30**.

Double-sided 0.1 pitch. 2 x 40-way fixing-centres 117mm gold-plated — Viking **£2.00**.

Double-sided 0.15 pitch. 2 x 40-way fixing-centres 165mm gold-plated **£2.00**.

TRANSFORMERS

6-0.6 500mA (240V Pri) (63x35x43)	£1.40
0-11 2A 0-22 1A (240V Pri) (76x64x60)	£2.40
12V 130mA (240V Pri) (36x45x40)	£0.75
18V 140mA (240V Pri) (38.4x31x32)	£0.80
18V 2A (240V Pri) (80x55x70)	£2.80
18V 2½A (240V Pri) (115x65x62)	£2.50
28V 2A (240V Pri) (63x45x37)	£1.00
32V 250mA (240V Pri) (46x37x31)	£1.20
Auto 110, 115, 120, 220, 230, 240, 250V 150VA	£1.50
0-2.4-6-8-10-12V 0-1.2V 5A (RMS) 240V Pri (98x67x80)	£6.00

TTL

7400	0.14	7449	1.00	74125	0.50
7401	0.14	7450	0.20	74132	0.70
7402	0.14	7451	0.20	74141	0.75
7403	0.14	7453	0.20	74150	1.00
7404	0.14	7454	0.20	74151	0.70
7405	0.18	7460	0.20	74153	0.70
7406	0.32	7470	0.35	74154	1.00
7407	0.32	7472	0.30	74155	0.70
7408	0.20	7473	0.30	74156	0.85
7409	0.20	7474	0.30	74157	0.70
7410	0.18	7475	0.45	74160	0.95
7411	0.20	7476	0.35	74161	0.50
7412	0.20	7480	0.60	74162	1.00
7413	0.30	7481	1.00	74163	1.00
7414	0.70	7482	0.90	74164	1.00
7416	0.30	7483	0.80	74165	1.00
7417	0.30	7484	1.10	74166	1.00
7419	0.20	7485	0.90	74167	2.50
7420	0.18	7486	0.30	74170	2.00
7421	0.20	7489	1.60	74174	0.95
7422	0.35	7490	0.35	74175	0.80
7423	0.32	7491	0.50	74176	0.80
7425	0.30	7492	0.45	74177	0.80
7426	0.30	7493	0.40	74180	0.80
7427	0.30	7494	0.90	74181	1.85
7428	0.40	7495	0.65	74182	0.95
7430	0.18	7496	0.65	74184	1.50
7432	0.26	7497	1.90	74185	1.50
7433	0.50	74100	1.40	74188	2.50
7437	0.30	74104	0.70	74190	1.00
7438	0.30	74105	1.70	74191	1.00
7440	0.18	74107	0.30	74192	1.00
7441	0.70	74109	0.55	74193	1.00
7442	0.50	74110	0.55	74194	1.00
7443	1.30	74118	0.95	74195	0.95
7445	1.00	74119	1.30	74196	0.95
7446	1.00	74121	0.28	74197	0.80
7447	0.75	74122	0.55	74198	1.60
7448	0.75	74123	0.55	74199	1.60
				74283	1.60

VEROBOARDS

0.1" Pitch Copper Clad		0.15" Pitch Copper Clad	
2.5" x 5"	0.59	2.5" x 5"	0.53
2.5" x 3.75"	0.50	2.5" x 3.75"	0.44
2.5" x 1.7"	1.77	3.75" x 5"	1.98
3.75" x 5"	0.66	3.75" x 5"	0.74
3.75" x 3.75"	0.59		
3.75" x 1.7"	2.28		
4.7" x 1.7.9"	2.99	0.15" Pitch Plain Board	
2.5" x 1" (Sold in 5s)	0.70	5" x 3.75"	0.47
		2.5" x 5"	0.30
0.1" Pitch Plain Board			
3.75" x 1.7.9"	1.49	New V-Q DIP Board	1.11
3.75" x 2.5"	0.36		
3.75" x 5"	0.56		

ALUMINIUM BOXES, PLAIN

Type	L	W	H	Retail	Price
AB 7 (ins 5)	4	2 ½	1	0.70	
AB 8 (ins 4)	4	1	1	0.70	
AB 9 (ins 4)	2 ½	1	1	0.70	
AB 10 (ins 4)	5 ½	1	1	0.70	
AB 11 (ins 4)	2 ½	2	1	0.85	
AB 12 (ins 3)	2	1	1	0.70	
AB 13 (ins 6)	4	2	1	1.00	
AB 14 (ins 7)	5	2	1	1.20	
AB 15 (ins 8)	6	3	1	1.55	
AB 16 (ins 10)	7	3	1	1.75	
AB 17 (ins 10)	4 ½	3	1	1.45	
AB 18 (ins 12)	5	3	1	1.75	
AB 19 (ins 12)	8	3	1	2.40	

ALUMINIUM BOXES, BLACK REXINE COVERED

Type	L	W	H	Retail	Price
RB 1 (ins 6)	4 ½	2 ½	1 ½	1.30	
RB 2 (ins 8)	5	2	1	1.55	
RB 3 (ins 9)	5	2 ½	1	1.85	
RB 4 (ins 11)	6	3	1	2.10	
RB 5 (ins 11)	7 ½	3 ½	1	2.55	


ALUMINIUM BOXES, BLUE REXINE COVERED

Type	L	W	H	Retail	Price
RB 1 (ins 6)	4 ½	2 ½	1 ½	1.45	
RB 2 (ins 8)	5	3	1	1.70	
RB 3 (ins 9)	5	3 ½	1	1.80	
RB 4 (ins 11)	6	4	1	2.30	
RB 5 (ins 11)	7 ½	4 ½	1	2.70	

The above advertisement is a fraction of our stock holding. Trade & Export welcome. No Mail Order other than trade. VAT extra 8% or 12%. P&P dependent on article, etc.

U.K. RETURN OF POST MAIL ORDER SERVICE, ALSO WORLDWIDE EXPORT SERVICE

BSR DE LUXE AUTOCHANGER £17.50 Post £1
Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability. Stereo Ceramic Cartridge. AC 200/250V. Size 13 1/2 x 11 1/4 in. 3 speeds. Above motor board 3 3/4 in. Below motor board 2 1/2 in. with Ceramic Stereo/Mono cartridge.




BSR Budget Autochanger £14.95 Post £1
with stereo cartridge, plays all size records

HEAVY METAL PLINTHS ONLY Post £1.00
Cut out for most BSR or Garrard decks. Silver grey finish. Model "A" Size 14 1/2 x 12 x 3 in. £3.50
Model "B" Size 16 x 13 3/4 x 3 in. £4.50

TINTED PLASTIC COVERS ONLY
SIZES: 14 1/2 x 12 1/2 x 4 1/4 in. £3.17 1/2 x 14 x 4 in. £4.50. 15 1/4 x 13 3/4 x 4 in. £3.75. 15 x 13 x 3 in. £3.50. 17 1/4 x 9 1/2 x 3 1/2 in. £3. Post £1. 14 1/2 x 14 x 2 1/2 in. Rosewood sides £4. Ideal for record decks, tape decks, etc.


BSR SINGLE PLAYER
Ideal replacement or disco deck with cueing device and stereo ceramic cartridge. 3 speeds. Large turntable, modern design. £19.50 Post £1
BSR P182 3 speeds flared aluminium turntable "S" shape arm, cueing device, ceramic cartridge £22.50.
BSR MP60/P128 Stereo Ceramic, balanced arm, cueing device. Bias compensator £24.50. Magnetic £5 extra.



GARRARD HI-FI AUTO CHANGER £14.95 Post £1
Model 5-300 3-speed stereo cartridge. Cueing devices



SMITH'S CLOCKWORK 15A TIME SWITCH £3.30 Post 35p
0-6 hours Single pole two-way. Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Brand new.



ELAC HI-FI SPEAKER £5.95 Post 35p
8in. TWIN CONE Large ceramic magnet. 50-16,000 c/s. Bass resonance 40 c/s. 8 ohm impedance. 10 watts. RMS. 20 watt model £8.95 Post 45p



LOW VOLTAGE POWER PACK FOR MODELS £2.50 Post 50p
Ready made. Famous make. Will supply 10 volts D.C. at 400mA. With terminals and mains lead.


VOLUME CONTROLS £1.00 Post 35p
5kΩ to 2MΩ LOG or LIN L/S 35p. D.P. 60p. Stereo L/S 85p. D.P. £1. Edge S.K. S.P. Transistor 45p.

80 Ohm Coax 15p yd.
FRINGE LOW LOSS 15p yd.
PLUGS 10p. SOCKETS 10p.
LINE SOCKETS 25p
OUTLET BOXES 80p
300 ohm FEEDER 5p yd.

EMI 13 1/2 x 8in. LOUDSPEAKERS £8.95 Post 45p
With tweeter and crossover. 10 watt. 3 or 8 ohm. £10.50 Post 65p
With tweeter and crossover. 15 watts. 8 ohm.



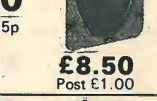Suitable Bookshelf Cabinet £8.50 Post £1.00
Teak finish. For EMI 13 x 8 speakers. Size 16 x 11 x 8 inches approximately.



THE "INSTANT" BULK TAPE ERASER £5.50 Post 50p
Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/250V. Leaflet S.A.E. Will also demagnetise small tools. Head Demagnetiser only £4.75.



RELAWS. 12V DC 95p. 6V DC 85p. 240V AC 95p.
BLANK ALUMINIUM CHASSIS. 6 x 4—95p; 8 x 6—£1.40; 10 x 7—£1.55; 12 x 8—£1.70; 14 x 9—£1.90; 16 x 6—£1.85; 16 x 10—£2.20. **ANGLE ALI.** 6 x 3/4 x 3/4 in—15p.
ALUMINIUM PANELS. 6 x 4—24p; 8 x 6—38p; 14 x 3—40p; 10 x 7—54p; 12 x 8—70p; 12 x 5—44p; 16 x 6—70p; 14 x 9—94p; 12 x 12—£1; 16 x 10—£1.16.
PLASTIC AND ALI BOXES IN STOCK. MANY SIZES
VARICAP FM TUNER HEAD with circuit & connections. Some technical knowledge required £4.95.
TAG STRIP 28-watt 12p.
TAPE OSCILLATOR COIL. Valve type. 35p.
BRIDGE RECTIFIER 200V PIV 1/2 amp 50p. 8 amp £2.50.
TOGGLE SWITCHES SP 30p. DPST 40p. DPDT 50p.
MANY OTHER TOGGLES IN STOCK. Please enquire.
PICK-UP CARTRIDGES ACOS. GP91 £2.00. GP94 £2.50.
SONOTONE stereo £2.00.
WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt 15p.
CASSETTE MOTOR. 6 volt £1.00.

RCS SOUND TO LIGHT KIT Mk. 2 £17 Post 35p
Kit of parts to build a 3 channel sound to light unit 1,000 watts per channel. Suitable for home use. Easy to build. Full instructions supplied. Cabinet £4 extra. Will operate from 200MV to 100 watt signal.

R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS £2.95 Post 45p
All parts and instructions with Zener diode, printed circuit rectifiers and double wound mains transformer. Input 200/240V a.c. Output voltages available, 6 or 7.5 or 9 or 12V d.c. up to 100mA or less. Size 3 x 2 1/2 x 1 1/2 in. Please state voltage required.

R.C.S. POWER PACK KIT £3.35 Post 30p
12 VOLT, 750mA. Complete with printed circuit board and assembly instructions. 12 VOLT 300mA Kit, £3.15.

R.C.S. "MINOR" 10 watt AMPLIFIER KIT £2.95 Post 35p
This kit is suitable for record players, guitars, tape playback, electronic instruments or small P.A. systems. Two versions available. Mono, £12.50; Stereo, £20. Post 45p. Specification 10W per channel; input 100mV; size 9 1/2 x 3 x 2 in. approx. S.A.E. details. Full instructions supplied. A.C. mains powered.

R.C.S. DRILL SPEED CONTROLLER/LIGHT DIMMER KIT. £3.25 Post 35p
Easy to build kit. Printed circuit Will control up to 480 watts AC mains

R.C.S. STEREO PRE-AMP KIT. £2.95 Post 35p
All parts to build this pre-amp. Inputs for high, medium or low imp per channel, with volume control and P.C. Board Can be ganged to make multi-way stereo mixers

MAINS TRANSFORMERS ALL POST 75p.

250-0-250V 70mA, 6.5V, 2A	£3.45
250-0-250V 80mA, 6.3V, 3.5A, 6.3V 1A	£4.60
350-0-350V 80mA, 6.3V, 3.5A, 6.3V 1A	£5.80
300-0-300V 120mA, 2x6.3V 2A C.T., 5V 2A	£5.50
220V 45mA, 6.3V 2A	£1.75
HEATER TRANSFORMER, 6.3V 1/2 amp £1.50 3 amp £1.75	

GENERAL PURPOSE LOW VOLTAGE, Tapped outputs


2 amp, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V	£5.30
1 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£5.30
2 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£8.50
3 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£11.00
5 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£14.50

12V, 100mA £1.00 **20V, 40V, 60V, 1 amp** £3.50
12V, 750mA £1.30 **12V, 3 amp** £2.95
10-0-10V 2amp £2.45 **10V, 30V, 40V, 2 amp** £2.75
30V, 5 amp and 17V-0-17V, 40V, 2 amp £2.95
2 amp £3.45 **20V, 1 amp** £2.20
0.5, 8, 10, 16V, 1/2 amp £1.95 **20V-0-20V, 1 amp** £2.85
9V, 3 amp £2.75 **30V-0-30V, 2 amp** £7.00
25-0-25V 2 amp £3.50 **2 of 18V, 6 amp, each** £9.00
30V, 2 amp £3.00 **12-0-12V, 2 amp** £2.95
30V, 1 1/2 amp £2.75 **9V, 1/4 amp** £1.30

AUTO TRANSFORMERS, 115V to 230V or 230V to 115V 150W £5.00
250W £6.00 **400W** £7.00 **500W** £8.00

FULL WAVE BRIDGE CHARGER RECTIFIERS
6 or 12V outputs, 2 amp £7.50 4 amp £11.25
CHARGER TRANSFORMERS: 1 1/2 amp £3.50, 4 amp £6.50, 12V, 1 1/2 amp Half Wave Selenium Rectifier 25p

COMPACT SPEAKERS £16 pair Post £1.30
Teak or White 13 x 10 x 6in. approx. 50 to 14,000 cps. 10 watts. 4 or 8 ohms.



EXTENSION SPEAKERS £3.95 ea.
Globe shaped cases in high gloss mouldings of red or green, are finished with chrome frontal trim and provided with screw-on rubber inset protective bases. In addition, 2 1/2 metres of strong lead already fitted with phono plug is supplied. Full Range Quality Frequency Response Impedance: 8 ohms Power Peak: 5 watts




LOW VOLTAGE ELECTROLYTICS
1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.
500mF 12V 15p; 25V 20p; 50V 30p;
1000mF 10V 25p; 25V 35p; 50V 47p; 100V 70p.
2000mF 6V 25p; 25V 42p; 420mF / 500V £1.30.
2500mF 50V 62p; 3000mF 25V 47p; 50V 65p.
3900mF 100V £1.80, 4700mF 63V £1.20, 2700mF / 76V £1.
5000mF 6V 25p; 12V 42p; 35V 85p; 5600mF / 76V £1.75

HIGH VOLTAGE ELECTROLYTICS
8/350V 22p 8+8/450V 50p 50+50/300V 50p
16/350V 30p 8+16/450V 50p 32+32/450V 75p
32/500V 75p 16+16/450V 50p 100+100/275V 65p
50/350V 50p 32+32/350V 50p 150+200/275V 70p

MANY OTHER ELECTROLYTICS IN STOCK
SHORT WAVE 100pF air spaced gangable tuner, 95p.
TRIMMERS 10pF, 30pF, 50pF, 5p, 100pF, 150pF, 15p.
CERAMIC, 1pF to 0.101mF, 5p. Silver Mica 2 to 5000pF, 5p.
PAPER 350V-0-17p; 0.5 13p; 1mF 150V 20p; 2mF 150V 20p; 500V-0.001 to 0.05 12p; 0.1 15p; 0.25 25p; 0.47 35p.
MICRO SWITCH SINGLE POLE CHANGE-OVER 20p.
SUB-MIN MICRO SWITCH, 25p. Single pole change over.
TWIN GANG, 385 + 385pF 50p; 500pF standard 75p.
365 + 365 + 25 + 25pF, Slow motion drive 65p.
120pF TWIN GANG, 50p; 365pF TWIN GANG, 50p.
NEON PANEL INDICATORS 250V, Amber or red 30p.
RESISTORS: 1Ω to 10MΩ, 1/4W, 1/2W, 1W, 20% 2p; 2W, 10p.
HIGH STABILITY. 1/4W 2% 10 ohms to 1 meg., 12p.
Ditto 5%. Preferred values 10 ohms to 10 meg., 5p.

ELECTRO MAGNETIC PENDULUM MECHANISM 95p Post 30p.
1.5V DC operation over 300 hours continuous on SP2 battery, fully adjustable swing and speed. Ideal displays, teaching electro magnetism or metronome, strobe, etc.

BAKER MAJOR 12" £15 Post £1.00
30-14,500 c/s, 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s. Rated 25W. NOTE: 4 or 8 or 16 ohms must be stated.



Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. Post £1.60 each Please state 4 or 8 or 16 ohms. £20

"SALE" BAKER "BIG-SOUND" SPEAKERS. Post £1
'Group 25' 12 inch 30 watt £12
'Group 35' 12 inch 40 watt £14
'Group 50/15' 15 inch 75 watt £33
4 or 8 or 16 ohm 4 or 8 or 16 ohm 8 or 16 ohm

BAKER LOUDSPEAKER, 12 INCH, 60 WATT, GROUP 50/12, 4 OR 8 OR 16 OHM HIGH POWER. FULL RANGE PROFESSIONAL QUALITY. RESPONSE 30-16,000 CPS MASSIVE CERAMIC MAGNET WITH ALUMINIUM PRESENCE CENTRE DOME. Post £1.60


TEAK VENEERED HI-FI SPEAKER CABINETS £8.50 Post £1
For 13x8in. or 8in. speaker £5.95 Post 75p
For 6 1/2in. speaker and tweeter Many other cabinets in stock. Phone your requirements. **SPEAKER COVERING MATERIALS.** Samples Large S.A.E. **LOUDSPEAKER CABINET WADDING** 18in wide 20p ft.

R.C.S. 100 watt VALVE AMPLIFIER CHASSIS £99 carr. £6.00
Four inputs. Four way mixing, master volume, treble and bass control. Suits all speakers. This professional quality amplifier chassis is suitable for all groups, disco, P.A., where high quality power is required. 5 speaker outputs. A/C mains operated. Slave output socket. Produced by demand for a quality valve amplifier. 100V line output to order £10 extra. Send for leaflet. Suitable carrying cab £16.50 Price £99 carr. £6.00



Horn tweeters 2-16kc/s. 10W 8 ohm or 16 ohm £3.60.
Audax Tweeters 3-18kc/s. 50W 8 ohm £7.50.
CROSSOVERS. TWO-WAY 3000 c/s 3 or 8 or 15 ohm £1.90, 3-way 950 cps/3000 cps. £2.20.
LOUDSPEAKERS P.M. 3 OHM 7x4in. £1.50; 6 1/2in., £1.95; 8x5in., £1.90; 8in., £2.50.
SPECIAL OFFER: 80 ohm, 2 1/4in., 2 3/4in., 35 ohm, 3in., 25 ohm, 2 1/2in., 3in., 5x3in., 7x4in., 8 ohm, 2 1/2in., 3in., 3 1/2in., 5in., 15 ohm, 3 1/2in., 4in., 6x4in., 7x4in., 5x3in., 3 ohm, 2 1/2in., 2 3/4in., 3 1/2in., 5in. dia. £1.50 each.
PHILIPS LOUDSPEAKER, 8in., 4 ohms, 4 watts, £1.95
RICHARD ALLAN TWIN CONE LOUDSPEAKERS
8in. diameter 4W £2.50. 10in. diameter 5W £2.95; 12in. diameter 6W £3.50. 3/8/15 ohms, please state.
MOTOROLA PIEZO ELECTRIC HORN TWEETER. £7.95
Handles up to 100 watts. No crossover required.
BLACK PLASTIC CONSTRUCTION BOX with brushed aluminium fascia. Sturdy job. Size 6 1/4 x 4 3/4 x 2in. £1.50

BAKER 150 WATT PROFESSIONAL MIXER AMPLIFIER £79 £1.50 carr.
All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 4 8/16 ohms. A.C. Mains. Separate treble and bass controls. Master volume control. 100 volt line model £99



BAKER 50 WATT AMPLIFIER £59 Post £1
Superior quality ideal for Halls, PA systems, Discos and Groups. Two inputs with Mixer Volume Controls, Master Bass, Treble and Gain Controls. 50 watts RMS. Three loudspeaker outlets 4, 8, 16 ohm. AC 240V (120V available). Blue wording on black cabinet


GOODMANS COMPACT 12-INCH BASS WOOFER. £9.95 each Post £1
Standard 12in. diameter fixing with cut sides 12 x 10. 14,000 Gauss magnet. 20 watts R.M.S. 4 ohm imp. Bass resonance = 30 c.p.s. Frequency response 30-8000 c.p.s.



ALUMINIUM HEAT SINKS. FINNED TYPE. Sizes 5" x 4" x 1" 95p. 6 1/2" x 2" x 2 1/4" 65p.
JACK PLUGS. Plastic 25p; Metal 30p.
JACK PLUGS Stereo Plastic 30p; Metal 35p.
JACK SOCKETS. Open 20p; Closed 25p.
JACK SOCKETS Stereo Open 25p; Closed 30p.
FREE SOCKETS - Cable end 30p.
2.5mm and 3.5mm JACK SOCKETS 15p.
2.5mm and 3.5mm JACK PLUGS 15p.

DIN TYPE CONNECTORS
Sockets 3-pin, 5-pin 10p. Free Sockets 3-pin, 5-pin 25p.
Plugs 3-pin 20p; 5-pin 25p.
PHONO PLUGS and SOCKETS ea. 10p.
Free Socket for cable end ea. 15p.
Screened Phono Plugs ea. 15p.
TV CONVERGENCE POTS 15p each
Values = 5, 7, 10, 20, 50, 100, 200, 250, 470, 2000 ohms.

MONO PRE-AMPLIFIER. Mains operated solid state pre-amplifier unit designed to complement amplifiers without low level phono and tape input stages. This free-standing cabinet incorporates circuitry for automatic R.I.A.A. equalisation on magnetic phono input and N.A.B. equalisation for tape heads. £4.50 Post 50p



LCR TESTING with the B424

C L R

push

. . . . connect

17.95 nF


read!

As fast and as simple as that, for batch testing, laboratory use or instrument servicing.

Accuracy 0.25% over a wide measurement range.

With its companion CA4 jig unit, the B424 Meter forms an easy-to-use L, C and R Component Test Station . . . and all for less than £600.

Write or ring today for details

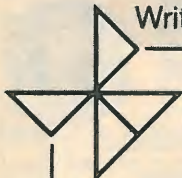

Wayne Kerr

WILMOT BREEDEN ELECTRONICS LIMITED

DURBAN ROAD BOGNOR REGIS WEST SUSSEX
PO22 9RL ENGLAND
TELEPHONE BOGNOR (02433) 25811
TELEX 86120

AUSTRIA - Peerless & Handels-GmbH	Tel: 0222 83 22 24
BELGIUM - Regulation-Mesure SPRL	Tel: (010 32 2) 771.20.20
FINLAND - Finnmetric OY	Tel: 460844
FRANCE - Tekelec-Airtronic	Tel: (Paris) 027.75.35
GERMANY - Keithley Instruments GmbH	Tel: (089) 7144065
ITALY - Ing. S. & Dr. G. Belotti SRL	Tel: (Milan) 54.20.51
NETHERLANDS - C. N. Rood BV	Tel: (070) 99.63.60
NORWAY - Metric AS	Tel: (02) 28-26-24
SPAIN - Unirtronic SA	Tel: (Madrid) 242.5204
SWEDEN - Scandia Metric AB	Tel: (Stockholm) 82.04.10
SWITZERLAND - G & P Electronics AG	Tel: (01) 64.32.31
U.S.A. - Mechanical Technology Inc, Latham, NY.	Tel: (518) 785-2211

WW - 111 FOR FURTHER DETAILS

PRECISION DIAL GAUGES John Bull No. 6 series 1, .01mm. £6 P.P. 50p

COAXIAL CRYSTAL DETECTORS. (Marconi-Saunders), 200 MHz-12 GHZ. £7.50

FIBREGLASS COPPER-CLAD BOARD
9x4 1/2x1 1/16in. 40p P&P 10p
9x6x1 1/16in. 50p P&P 15p
9x4 1/2x1 1/16in. (double sided) 50p P&P 10p
9x6x1 1/16in. (double sided) 65p P&P 10p
15x15x1 1/16in. (double sided) £2.50 P&P 50p

OFF-CUT PACKS. 150 sq. ins. £1 P.P. 25p.

LOW PROFILE RELAYS (ZETTLER) P.C.
Mounting. 6v or 12v. D.C.
1 P. c/o 50p. P&P 10p.
2 P. c/o. 75p. P&P 10p.
4 P. c/o. £1. P&P 10p.
1 P. c/o (Latching) 50p. P&P 10p
2 P.c/o (Latching) 50p. P&P 10p

PLUG-IN (CRADLE) RELAYS 6/12/24/48V.W.
2 P. c/o. 65p. P&P 10p
4 P.c/o. 85p. P&P 10p.
BASES 10p each

P.A.R. BI-STABLE RELAYS. 24v d.c. 4 c/o £1 P.P. 15p.

PLUG-IN RELAYS 240v a.c. 10 amp contacts
3 pole c/o (11 pin) £1 P.P. 15p
2 pole c/o (8 pin) 85p P.P. 15p

U.H.F. COAXIAL CABLE (white) Double screened.
Lab. quality 100m. drum £10 p.p. £1.50.

MULTICORE CABLES
4 CORE RIBBON (RAINBOW) CABLE 4 - 10/.2m.m.
Forming 1/4in. wide strip. 10m-75p-£3; 100m-£6. P&P 1p per metre.

10 CORE CABLE 10 x 7/76 (10 colours) P.V.C.
O.D. 7m.m. 10m-£2.50m-£8.50. 100m-£16. P&P 2p per metre

16 PAIR RIBBON CABLE 16x2 core P.V.C.
Double sheathed forming 2in wide strip
10m-£3; 50m-£13.50; 100m-£25. P&P 2p per metre.

E.H.T. MODULES (resin encapsulated, in metal box)
i/p 240x.50hz. o/p 13.7 kv. @ 7 watts (150x95x72m.m.) £10 P.P. £1.

P.C. EDGE CONNECTORS
32 way (.1 pitch) finished end 49p P&P 10p
56 way (.1 pitch) cuttable 65p P&P 15p
64 way (.1 pitch) cuttable 75p P&P 15p
64 way gold plated pins 90p P&P 15p
Mounting pillars for 56/64 way 15p per pair.

'DRYFIT' RE-CHARGEABLE BATTERIES (Lead / Acid)
Ex. Equip. Good condition. tested.
6v @ .9 A.H. £1.25 P&P 35p
6v @ 2.6 A.H. £2.50 P&P 50p
6v @ 6 A.H. £3.50 P&P 75p
6v @ 7.5 A.H. £5.00 P&P 75p

J. B. PATTRICK

191/193 London Road
Romford, Essex RM7 9DJ
Romford 44473

JAYEN

BUILD THESE ADVANCED DESIGN INSTRUMENTS

DM-2



DIGITAL MULTIMETER

- DC Volts1mV to 1000V
- AC Volts1V to 500V
- DC Current ...0.1mA to 0.2A
- Resistance1Ω to 20MΩ
- Battery Test Point
- Auto Polarity & Zero
- Total cost less than £30 (incl. case)

FG-1a



FUNCTION GENERATOR

- 30mV to 10V pk-pk
- 1Hz to 100kHz
- DC coupled amplifier
- Sine, Square & Triangle
- Separate TTL output
- Total cost less than £20 (case extra)

To: JAYEN Developments, 21 Gladeside, Bar Hill, Cambridge CB3 8DY
Tel: (0954) 80285

Please send a JAYEN

- DM-2 @ £4.85
- FG-1a @ £4.50

Name _____

(Incl. VAT and P&P) Address _____

Each kit comprising a PC board, punched and lettered Front Panel, Instructions and Component Shopping List.

Money to be refunded if the kit is returned within 10 days.

ww3

WW-073 FOR FURTHER DETAILS

Catronics NEW

WW TELETEXT DECODER

components and PCB for new Character Rounding "Board 4" available now. PCB £14.60. Kit (inc. PCB) £25.75

"Board 3" is also available as an additional unit to update the "Wireless World" Teletext Decoder to give double height characters, colour background, conceal/reveal, etc., as described in December 1977 and January 1978 issues of *Wireless World*

The Kit includes plated-through hole P.C.B. all components and installation instructions. Price £33.88 + VAT (£3.47) + P&P (30p) = £37.45 total. P.C.B. available separately at £19.30.



Set of 5 PCBs £23.95 + 30p p&p
 Components Kit (inc. PCBs) £139.25 + £1.50 p&p
 Cabinet £18.00 + £1.00 p&p

Also PLATED THROUGH hole PCBs at additional cost of £26
FULL FAULT-FINDING AND REPAIR SERVICE AVAILABLE

COMPONENTS ALSO AVAILABLE SEPARATELY — SAE for price list
 READY BUILT AND TESTED DECODERS — £241.87 + £5 Carr.
 DE LUXE VERSION WITH NEW FACILITIES — £292.50 + £5 Carr.

FULL SPEC. PROFESSIONAL TELETEXT DECODER

We are now agents for V.G. Electronics Ltd., and can offer their model VGE1022 (as supplied to broadcasting authorities, etc.) at the **SPECIALY REDUCED PRICE OF £248 + VAT = £279**

FREQUENCY COUNTER CHIPS

The following counter i.c.s. are now available

74C926 **£5.30**; MK50395 **£7.55**; ICM7208 **£15.70**; ICM7216C **£22.70**;
 ICM7216D **£19.65**; ICM7226 **£27.20**. Application information also available
 Try us for 7 segment displays, display drivers and prescaler I.C.s

All prices include VAT but please add min. 30p p&p

CATRONICS LTD. (Dept. 923)

Communications House,
 20 WALLINGTON SQUARE,
 WALLINGTON, SURREY.
 Tel. 01-669 6700

WW-923 FOR FURTHER DETAILS

SEND FOR S I N T E L FREE CATALOGUE

S I N T E L

CD4015	0.83	CD4032	0.89	CD4049	0.50	CD4072	0.20	CD4099	1.65
CD4016	0.48	CD4033	1.25	CD4050	0.43	CD4073	0.20	CD4502	0.81
CD4017	0.79	CD4034	1.71	CD4051	0.82	CD4075	0.20	CD4510	1.01
CD4018	0.85	CD4035	1.06	CD4052	0.82	CD4076	1.17	CD4511	1.25
CD4019	0.50	CD4036	2.86	CD4053	0.82	CD4077	0.39	CD4514	2.47
CD4020	0.15	CD4020	1.11	CD4037	0.85	CD4054	1.04	CD4078	2.82
CD4021	0.17	CD4021	0.90	CD4038	0.96	CD4051	1.18	CD4081	2.01
CD4022	0.82	CD4039	2.78	CD4056	1.18	CD4082	0.20	CD4518	0.97
CD4026	1.04	CD4023	0.18	CD4040	0.97	CD4059	4.29	CD4085	0.64
CD4027	0.18	CD4024	0.70	CD4041	0.75	CD4060	1.00	CD4086	0.64
CD4028	0.87	CD4025	0.20	CD4042	0.69	CD4063	0.98	CD4089	1.39
CD4029	0.50	CD4026	1.55	CD4043	0.88	CD4066	0.55	CD4093	0.80
CD4030	0.50	CD4027	0.44	CD4044	0.84	CD4067	3.35	CD4094	1.69
CD4031	0.18	CD4028	0.77	CD4045	1.26	CD4068	0.20	CD4095	0.94
CD4032	0.20	CD4029	1.03	CD4046	1.20	CD4069	0.20	CD4096	0.94
CD4033	0.43	CD4030	0.50	CD4047	0.89	CD4070	0.46	CD4097	3.35
CD4034	0.83	CD4031	2.00	CD4048	0.50	CD4071	0.20	CD4098	0.98

COMPONENTS

SOLDERCON	CLOCK CHIPS	DISPLAYS	CRYSTALS	MEK6800D2	190.00
PINS	AY51202	3.10 TYPE FN0500 C.C.	1.30 32.768 KHz	2.95 MC6800	13.88
100	0.50 AY51224	3.45 TYPE TRL 32.1 C.A.	1.30	MC6820	6.94
1000	4.00 MK50253	5.40 SLT01	4.90 MEMORIES/μps	780-CPU	16.80
3000	10.50		2102A-B	1.85 280A-CPU	22.40
			7112A-4	2.90 280-CTC	10.15
				280-P/D	10.15

Free data is available on some of these items. SEND FOR FREE CATALOGUE

**SOME 74LSTTL
 NOW AVAILABLE
 PLEASE SEND
 FOR LIST**

Our offices are at Chapel Street, Oxford, but please do not use this as a postal address

FAST SERVICE. We guarantee that Telephone Orders for goods in stock, received by 4.15 p.m. (Mon-Fri) will be dispatched on the same day by 1st Class Post (some heavy items by parcel post) and our stocking is good. Private customers should telephone and pay by giving their Access or Barclaycard number with a minimum value of £5. Official orders no minimum. Official orders, Companies, Govt., Nats. Inds., and Univa.
ORDERS: C.W.O. add VAT at 8% + 35p p&p. TELEPHONE and CREDIT invoiced ORDERS add VAT at 8% + 60p p&p minimum charge (the balance will be charged at cost). Please send FAST SERVICE. EXPORT ORDERS welcome, no VAT but add 10% (Europe), 15% (Overseas) for Air Mail p&p. For export postage rates on heavy items—contact us first.

SEND YOUR ORDER TO **SINTEL**
 PO BOX 75C OXFORD
 Tel: 0865 49791

TRANSFORMERS

SAME-DAY DESPATCH

MAINS ISOLATOR			VAT 8% 12 or 24-VOLT		
PRI 120 or 240V Sec 120 or 240V			Separate 12V windings Pri 220-240V		
Centre Tapped and Screened					
Ref. VA (Watts)	£	P&P	Ref	12v	24v
07* 20	4.40	.79	111	0.5	0.25
149 60	6.70	.96	213	1.0	0.5
150 100	7.61	1.14	71	2	1
151 200	11.16	1.14	18	4	2
152 250	13.28	1.50	85	5	2.5
153 350	16.43	1.84	70	6	3
154 500	20.47	2.15	108	8	4
155 750	29.06	OA	72	10	5
156 1000	37.20	OA	116	12	6
157 1500	51.38	OA	17	16	8
158 2000	81.81	OA	115	20	10
159 3000	86.66	OA	187	30	15
			226	60	30

50 VOLT RANGE
 Pri 220-240V. Sec. 0-20-25-33-40-50V.
 Voltages available 5, 7, 8, 10, 13, 15, 17, 20, 25, 30, 33, 40 or 20V-0-20V and 25V-0-25V Screened

Ref.	Amps	£	P&P
102	0.5	3.41	.78
103	1.0	4.57	.96
104	2.0	7.16	1.14
105	3.0	8.56	1.32
106	4.0	15.06	1.50
107	6.0	14.62	1.64
118	8.0	20.26	2.08
119	10.0	24.98	OA

30 VOLT RANGE
 Pri 220-240V
 Sec. 0-12-15-20-24-30V
 Voltages available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V or 12V-0-12V and 15V-0-15V.

Ref.	Amps	£	P&P
112	0.5	2.64	.78
79	1.0	3.57	.96
3	2.0	5.77	.96
20	3.0	6.20	1.14
21	4.0	7.99	1.14
51	5.0	9.87	1.32
117	6.0	11.17	1.45
88	8.0	14.95	1.64
89	10.0	17.25	1.84

60 VOLT RANGE
 Pri 220-240V
 Sec. 0-24-30-40-48-60V. Voltages available 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60V, or 24V-0-24V and 30V-0-30V

Ref.	Amps	£	P&P
124	0.5	3.88	.96
126	1.0	5.91	.96
127	2.0	7.60	1.14
125	3.0	11.00	1.32
123	4.0	12.52	1.84
40	5.0	15.84	1.64
120	6.0	18.06	1.84
121	8.0	25.56	OA
122	10.0	29.55	OA
189	12.0	34.06	OA

SCREENED MINIATURES Primary 240V

Ref.	mA	Volts	£	P&P
238	200	3-0-3	2.57	.55
212	1A, 1A	0-6, 0-6	2.85	.78
13	100	0-9-9	1.99	.38
235	330, 330	0-9, 0-9	1.99	.38
207	500, 500	0-8-9, 0-8-9	2.77	.71
208	1A, 1A	0-8-9, 0-8-9	3.53	.78
236	200, 200	0-15, 0-15	1.99	.38
239	50mA	12-0-12	2.57	.38
214	300, 300	0-2, 2-20	2.80	.78
221	700 (DC)	20-12-0-12-20	3.41	.78
206	1A, 1A	0-15-20, 0-15-20	4.63	.96
203	500, 500	0-15-27, 0-15-27	3.99	.96
204	-1A, 1A	0-15-27, 0-15-27	6.04	.96

HIGH VOLTAGE

MAINS ISOLATING
 Pri 200/220 or 400/440
 Sec 100/120 or 200/240

VA	Ref.	£	P&P
60	243	6.70	1.32
350	247	16.43	1.84
1000	250	37.10	OA
2000	252	61.81	OA

BRIDGE RECTIFIERS

100v	25A	£2.10
200v	2A	45p
400v	2A	55p
200v	4A	65p
400v	4A	80p
400v	6A	£1.40
500v	12A	£2.35

TEST METERS

AV08 Mk. 5	£81.70
AV071	£33.50
AV073	£45.20
AV0MM5 MINOR	£28.66
WEE MEGGER	£66.90
TT169 (tests transistors in circuit)	£34.75
U4315 budget meter (42 ranges)	20kΩ V/DC 1000V
AC/DC (9 ranges)	2.5A AC/DC
500K resistance, in robust steel case with leads, full instructions.	£15.85

EM272 316KΩ	£53.70
DA116 Digital	£102.00
Megger BM7 (Battery)	£44.15
MM5 Multiminor	£27.56

MINIATURE TRANSFORMER

Ref.	Amps	Price	P&P
171	500MA	2.09	.45
172	1A	2.96	.78
173	2A	3.59	.78
174	3A	3.75	.86
175	4A	5.73	.96

ABS PLASTIC BOXES

Inset brass nuts, slots to take PC cards (boards) flush fitting lid.	
PB1 80mm x 62 x 40	.65p
PB2 100mm x 75 x 40	.73p
PB3 120mm x 100 x 45	.87p
PB4 215mm x 130 x 85	£2.54

ANTEX SOLDERING IRONS

15W	£3.75
25W	£3.95

AUTO TRANSFORMERS

Ref. VA (Watts)	TAPS	£	P&P
113	15 0-115-210-240V	2.48	.71
64	75 0-115-210-240V	4.01	.96
4	150 0-115-200-220-240V	5.35	.96
66	300	7.75	1.14
67	500	10.99	1.64
84	1000	18.76	2.08
93	1500	23.28	OA
95	2000	34.82	OA
73	3000	59.21	OA
80s	4000 0-10-115-200-220-240	76.86	OA
57s	5000	89.50	OA

CASED AUTO TRANSFORMERS

MINI-MULTIMETER	£	P&P
DC1000V, AC1000V	75V £7.73	1.14
AC/DC1000Ω/V	150V £10.01	1.14
DC-100mA. Res—150K	250V £9.92	1.45
Bargain at £7.20	500V £19.17	1.64
VAT 8% P&P 62p	750V £23.41	1.76
	1000V £27.88	2.30
	1500V £26.02	OA
	2000V £49.97	OA

PANEL METERS

43mm x 43mm	82mm x 78mm
0-50μA	£6.20
0-500μA	£5.95
0-1mA	£5.95
0-30V	£5.95
VU Indicator Panel 90mm 250μA	£3.36
VU Indicator Edge 54mm x 14mm μA FSD	£2.60

NEW RANGE TRANSFORMERS

Pri	0-120;	0-100-120;	120v or 220-240v	Sec.
0-36-48	twice to give 72v or 92v.			
2A	12.14	PP	£1.40	4A 18.17 PP</

K9

COMPONENTS

GRAPHIC HOUSE
PANGBOURNE
BERKSHIRE

PROFESSIONAL SUPPLIES TO THE AMATEUR

LINEAR SELECTION			DIODE/TRANSISTOR SELECTION						
CA3130T	1.06	uA709	0.65	8AX13	0.05	BC209C	0.15	0A91	0.17
LM301-B	0.30	uA710	0.66	8AX16	0.05	BC212	0.11	ZT107B	0.09
LM308-B	0.95	uA723-14	0.45	8C107	0.10	BC214B	0.15	1N4001	0.05
LM3300K	1.95	uA741-B	0.27	8C108	0.10	BCY70	0.15	1N4004	0.06
LM3900M	0.68	uA747-14	0.57	8C109	0.10	BCY71	0.20	1N4148	0.04
NE555-B	0.32	uA748-B	0.47	8C207	0.10	BCY72	0.15	1N5401	0.11
NE556-14	0.62	7805-UC	0.81	8C207B	0.11	BFX85	0.30	2K3053	0.19
TBA810	1.30	7812-UC	0.81	8C207B	0.10	BFY50	0.20	2K3055	0.49
TBA820	0.80	7905-UC	1.30	8C208A	0.10	DA47	0.11	2K3702	0.10
ZK414	1.40	7912-1C	1.30	8C209	0.10	DA90	0.14	2K3703	0.09
ZT202	0.79								
	0.65								

BZY88 ZENER DIODES 2V7-33V 0.05

CMOS SELECTION			TANTALUM CAPS						
4000	0.14	4023	0.15	4093	0.64	0.1mfd 35v	0.087	6.8mfd 35v	0.122
4001	0.15	4026	1.28	4507	0.49	0.15mfd 35v	0.087	5mfd 35v	0.208
4002	0.16	4027	0.48	4508	2.21	0.22mfd 35v	0.087	22mfd 35v	0.211
4009	0.30	4030	0.46	4510	1.02	0.33mfd 35v	0.087	33mfd 25v	0.211
4010	0.46	4051	0.83	4511	0.98	0.47mfd 35v	0.087	10mfd 25v	0.122
4011	0.15	4053	0.83	4518	0.98	0.68mfd 35v	0.087	6.8mfd 25v	0.109
4012	0.16	4060	0.98	4520	1.05	1mfd 35v	0.087	47mfd 16v	0.211
4013	0.41	4066	0.48	4528	0.90	1.5mfd 35v	0.087	33mfd 16v	0.208
4016	0.39	4069	0.17	4556	0.85	2.2mfd 35v	0.087	22mfd 16v	0.122
4017	0.76	4075	0.17			3.3mfd 35v	0.093	10mfd 16v	0.109
4020	0.89	4081	0.17			4.7mfd 35v	0.109	100mfd 6.3v	0.208
4022	0.81	4082	0.17						

TTL SELECTION			OPTOELECTRONICS						
7400	0.12	7496	0.57	74186	7.15	Red 3mm	0.12	10mm Comm Anode	1.55
7401	0.12	74110	0.45	74190	0.99	Red 5mm	0.12	14mm Comm Anode	1.57
7402	0.12	74120	0.80	74193	0.97	Green 3mm	0.16	18mm Comm Anode	1.85
7404	0.13	74121	0.25	7446A	0.67	Green 5mm	0.16	Height:	
7405	0.13	74122	0.38	7447A	0.64	Yellow 3mm	0.19	8mm Comm Cathode	1.50
7407	0.26	74123	0.53	7448	0.59	Yellow 5mm	0.19	10mm Comm Cathode	1.55
7410	0.12	74126	0.44	7470	0.28	FN500	1.41	14mm Comm Cathode	1.57
7411	0.18	74132	0.57	7473	0.25	FN501	1.41	18mm Comm Cathode	1.85
7413	0.25	74136	0.72	7474	0.25	FN507	1.41		
7420	0.12	74141	0.58	7480	0.45				
7421	0.27	74142	1.96	7484	0.88				
7422	0.17	74160	0.78	74147	1.25				
7427	0.24	74181	0.78	74148	1.15				
7428	0.32	74182	0.78	74150	0.96				
7430	0.13	74183	0.78	74151A	0.60				
7440	0.13	74184	0.87	74153	0.60				
7422A	0.52	74185	0.87	74154	1.03				
7485	0.83	74173	1.16	74157	0.63				
7480	0.33	74174	0.87	74159	1.85				
7483	0.37	74175	0.58	74197	0.87				
7494	0.75	74180	0.87	74198	1.45				
7495	0.51	74184A	1.18	74393	1.94				

ORDERS:
C.W.O. P.O., Cheque
All price include VAT

DISCOUNT:
Orders over £10 less 5%
Over £20 less 10%
Over £50 less 15%
Over £100 less 20%
Add 30p for P&P (Export Extra)
Send SAE for our complete stock list

WW — 085 FOR FURTHER DETAILS

Nevenco mixing consoles — sophisticated performance from the pioneers



The Corinthian

The new Nevenco range of mixing consoles is low on cost and high on quality and performance. It is designed exclusively for non-profit organisations; the Christian communicator, broadcaster, music or programme producer; and for universities, colleges and training studios with specialised needs and the ever-growing demand for sophisticated production.

The Philippiian Portable: 8 mono or stereo inputs, 2 programme and 2 auxiliary outputs.

The Phippian Studio: Desk-mounted version with studio interface.

The Ephesian Console: 16 input, 4 bus full production console for the programme and small music studio.

The Corinthian Console: 16 to 24 input, 8 bus for stereo and simultaneous mono multi-purpose recording and TV Sound.


All feature wide band low distortion, low noise and high reliability together with detailed attention to facilities and layout to your needs — the sort of equipment you would expect from Rupert and Evelyn Neve, Geoff Watts and Alan Foster, pioneers of the world's most advanced audio consoles.

Nevenco Ltd

2 Hills Road
Cambridge CB2 1JP England
Tel. Cambridge 62392
(STD 0223)

WW—023 FOR FURTHER DETAILS

Try our boots on for size

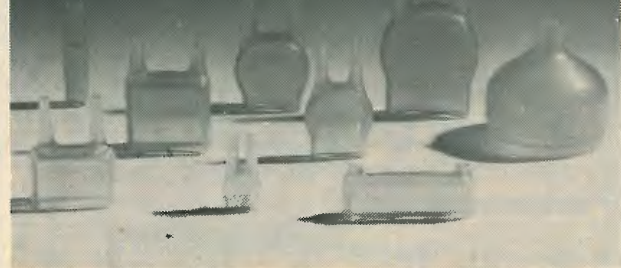

Highvoltage capacitor boots give complete insulation of the terminal. Slip-on assembly — no mess, no heat. 30 sizes ensure a snug fit, yet the terminal remains easily accessible. 3 types for Tantalum, Aluminium and Ceramic capacitors, all conforming to UL safety and flammability ratings. FREE samples and catalogue showing our full range of insulator covers on request.



HIGHVOLT CONNECTORS LTD.
Uddens Trading Estate,
Nr. Wimborne, Dorset BH21 7NL.
Tel: Ferndown (STD 0202) 871411/2/3/4
Telex: 41408

WW — 081 FOR FURTHER DETAILS

ELECTROVALUE

for a good deal better than most

YOUR LEADING DIRECT SUPPLIERS FOR

- ▶ Transistors
- ▶ Opto-electronics
- ▶ Associated items of all kinds
- ▶ I.C.s
- ▶ Rs and Cs

ALL IN OUR 120-PAGE CATALOGUE NO. 9 — FREE FOR THE ASKING

WE PAY POSTAGE
on U.K. orders with cash over £5 list value. If under, add 27p handling charge.

WE GIVE DISCOUNTS
on C.W.O. orders in U.K. — 5% on list value over £10; 10% on list value over £25 except net items.

WE STABILIZE PRICES
by keeping to our quarterly price lists.

WE GUARANTEE
all goods brand new, clean and to spec. No seconds or surplus.

WE ARE NATIONAL DISTRIBUTORS FOR



NASCOM MICROCOMPUTERS

For delivery from stock
Nascom 1 — **£165 (net) + V.A.T.**
Also full supporting Nascom programme, club details, etc. Brochure on request.

MOTOROLA Evaluation Kit (for M680 Microprocessor) £175.67 (net) + V.A.T.

TRADE ENQUIRIES INVITED

ELECTROVALUE LTD

Dept. WW3, 24 St. Judes Road, Englefield Green, Egham, Surrey, TW20 0HB.
Phone Egham 3603. Telex 264475.
Northern Branch (Personal shoppers only), 680 Burnage Lane, Burnage, Manchester, M19 1NA. Phone (061) 432 4945.

ALL INVOICES, ENQUIRIES, ETC. TO
OUR TEMPORARY ADDRESS OF

CHILTMHEAD LTD

NORWOOD ROAD
READING

Telephone No.: READING 65916

POCKET TERMINAL

Midget duplex unit with man-sized facilities

Until you've tried it, you won't believe how much capability we've packed into the Pocket Terminal. We've gone all-out to make it the most practical and useful hand-held data communications device available.



Here's just a few of the facilities:

- Transmits 128 ASCII codes.
- Displays full 64 character ASCII set clearly.
- 30 character memory accessible through display.
- Single 5V supply required at 400mA max.
- 110 or 300 baud transmission, selectable.
- 20mA loop or V24/RS232 level versions available.
- Parity codes and stop bits settable to your standard.
- Reacts to bell, cursor and formatting control codes.

Pocket Terminal is a convenient, versatile, totally portable tool for anyone who needs to communicate with computers or their peripherals. Send for details now from:



GR ELECTRONICS LTD.

Fairoak House, Church Road, Newport, Gwent NPT7EJ. UK
Telephone: Newport (0633) 67426 Telex: 28604 Ref.1796

WW-103 FOR FURTHER DETAILS

MAIL ORDER PROTECTION SCHEME (Limited Liability)

If you order from mail order advertisers in this magazine, except for classified advertisements, and pay by post in advance of delivery, Wireless World will consider you for compensation if the advertiser should become insolvent or bankrupt, provided

1. You have not received the goods or had your money returned; and
2. You write to the publisher of Wireless World explaining the position not earlier than 28 days from the day you sent your order and not later than 2 months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the advertiser has been declared bankrupt or insolvent up to a limit of £3,550 per annum for any one advertiser so affected and up to £10,000 per annum in respect of all insolvent advertisers. Claims may be paid for higher amounts, or when the above procedure has not been complied with, at the discretion of Wireless World; but we do not guarantee to do so in view of the need to set some limit to this commitment and to learn quickly of readers' difficulties.

This guarantee covers only advance payments sent in direct response to an advertisement in this magazine (not, for example, payments made in response to catalogues, etc., received as a result of answering such advertisements. Personal advertisements are excluded.

PROFESSIONAL STYLE AUDIO LEVEL METERS



These British made audio level meters are based on the Sifam taut band movement, and are suitable for use in portable equipment for stage or location. They are calibrated for use with 3K6 resistor 4VU above the scale marking so that reference deflection (OVU) is produced by a signal 4VU above 1mW in 600 R (1.228V).

Prices: AL22 £7.00 each or £13.50 pair
AL22F £8.50 each or £16.50 pair

All prices inclusive of VAT. Add 75p P&P. Access Welcome.

For full details of this product and the complete Sifam meter range from our stock, contact:

BRENSAL ELECTRONICS LIMITED

24 Park Row
Bristol BS1 5LJ
Telephone Bristol (0272) 294188

ASTRA-PAK

92 GODSTONE ROAD, WHYTELEAFE, SURREY CR3 0EB

GRAND SALE

All prices include VAT. Add 25p for P.&P (Extra for overseas). Send SAE for complete Special Offers list. Where more than one price appears, overall quantity prices apply to groups of devices of the same type (74 and 74LS) cannot be mixed).

7400 SERIES			74LS00 SERIES			7400 SERIES			74LS00 SERIES			7400 SERIES			74LS00 SERIES			CMOS			1+ 25+ 100+			1+ 25+ 100+			1+ 25+ 100+			LINEARS																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
1+	25+	100+	1+	25+	100+	1+	25+	100+	1+	25+	100+	1+	25+	100+	1+	25+	100+	1+	25+	100+	1+	25+	100+	1+	25+	100+	1+	25+	100+																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
7400	.08	.075	.07	7401	.11	.105	.10	7402	.11	.105	.10	7403	.11	.105	.10	7404	.11	.105	.10	7405	.12	.115	.11	7406	.22	.21	.20	7407	.22	.21	.20	7408	.13	.125	.12	7409	.11	.105	.10	7410	.11	.105	.10	7411	.17	.16	.15	7412	.14	.135	.13	7413	.23	.21	.20	7414	.46	.43	.40	7415				7416	.22	.20	.18	7417	.22	.20	.18	7420	.11	.105	.10	7421	.22	.21	.20	7422	.17	.165	.16	7423	.20	.19	.18	7425	.20	.19	.18	7426	.21	.20	.19	7427	.21	.20	.19	7428				7430	.11	.105	.10	7432	.21	.20	.19	7433	.30	.27	.26	7437	.20	.19	.18	7438	.20	.19	.18	7440	.12	.115	.11	7441	.48	.45	.43	7442	.40	.38	.34	7443	.65	.60	.57	7444	.64	.59	.56	7445	.53	.50	.48	7446	.55	.52	.50	7447	.50	.44	.40	7448	.55	.50	.48	7449				7450	.12	.115	.11	7451	.12	.115	.11	7453	.12	.115	.11	7454	.12	.115	.11	7455				7456	.12	.115	.11	7470	.25	.23	.21	7472	.22	.20	.18	7473	.23	.21	.20	7474	.23	.21	.20	7475	.30	.28	.28	7476	.26	.24	.23	7478				7480	.40	.36	.34	7483	.52	.45	.46	7484	.84	.80	.77	7485	.62	.68	.55	7486	.22	.20	.19	7489	1.35	1.25	1.18	7490	.30	.28	.26	7491	.60	.55	.52	7492	.33	.30	.28	7493	.25	.23	.23	7494	.50	.45	.42	7495	.50	.45	.42	7496	.48	.42	.38	7497	1.80	1.70	1.65	74100	.80	.72	.68	74101	.40	.36	.34	74105	.37	.34	.32	74107	.22	.20	.18	74109	.28	.26	.24	74110	.36	.34	.32	74111	.55	.52	.50	74112				74113	.28	.26	.24	74114				74116	1.10	1.00	.95	74118	.78	.75	.72	74119	1.10	1.00	.95	74120	.80	.78	.74	74121	.24	.22	.20	74122	.32	.29	.27	74123	.38	.35	.32	74124	1.80	1.50	1.42	74125	.32	.30	.28	74126	.32	.30	.28	74128	.60	.55	.52	74130	.40	.36	.32	74132	.47	.44	.42	74134	.82	.80	.78	74135	.82	.80	.78	74136	.52	.48	.46	74137	.74	.68	.66	74138				74141	.52	.48	.46	74142	1.95	1.75	1.68	74143	2.30	2.10	2.00	74144	2.30	2.10	2.00	74145	.55	.50	.48	74147	1.00	.92	.88	74148	.84	.78	.75	74150	.60	.55	.50	74151	.48	.41	.38	74152	.48	.41	.38	74153	.48	.41	.38	74154	.78	.68	.60	74155	.50	.44	.40	74156	.82	.75	.68	74157	.65	.60	.58	74158	.55	.52	.48	74159	1.95	1.80	1.70	74160	.57	.52	.48	74161	.50	.44	.40	74162	.57	.52	.48	74163	.57	.52	.48	74164	.57	.52	.48	74165	.57	.52	.48	74166	.70	.64	.59	74167				74168				74169				74170	1.20	1.10	1.00	74172	3.80	3.65	3.40	74173	.90	.84	.80	74174	.64	.60	.56	74175	.58	.54	.51	74176	.58	.54	.51	74177	.56	.52	.49	74178	.90	.80	.75	74179	1.08	1.00	.95	74180	.80	.70	.62	74181	1.15	.95	.80	74182	.52	.47	.44	74183	1.25	1.00	1.00	74185A	1.00	.90	.86	74186	7.20	6.90	6.70	74188	2.60	2.40	2.25	74189				74190	.68	.60	.55	74191	.68	.60	.55	74192	.62	.55	.48	74193	.60	.50	.46	74194	.58	.50	.46	74195	.58	.50	.46	74196	.56	.50	.46	74197	.50	.44	.40	74198	.98	.85	.78	74199	.98	.90	.85	74221	1.20	1.00	.88	74247				74248				74249				74251	1.00	.82	.74	74257				74258				74266				74279	1.90	1.70	1.55	74279	1.10	.90	.82	74283	1.50	1.30	1.20	74284	3.50	3.20	3.00	74289				74290				74293	1.20	1.00	.80	74298	1.80	1.55	1.40	74352				74353				74365				74367				74368	1.10	.85	.70	74386				74390	1.70	1.40	1.25	74393	1.75	1.45	1.25	74670	1.60	1.40	1.30	74189	.68	.60	.55	74190	.68	.60	.55	74191	.68	.60	.55	74192	.62	.55	.48	74193	.60	.50	.46	74194	.58	.50	.46	74195	.58	.50	.46	74196	.56	.50	.46	74197	.50	.44	.40	74198	.98	.85	.78	74199	.98	.90	.85	74221	1.20	1.00	.88	74247				74248				74249				74251	1.00	.82	.74	74257				74258				74266				74279	1.90	1.70	1.55	74279	1.10	.90	.82	74283	1.50	1.30	1.20	74284	3.50	3.20	3.00	74289				74290				74293	1.20	1.00	.80	74298	1.80	1.55	1.40	74352				74353				74365				74367				74368	1.10	.85	.70	74386				74390	1.70	1.40	1.25	74393	1.75	1.45	1.25	74670	1.60	1.40	1.30

Mixed prices apply for quantity discount

WW-087 FOR FURTHER DETAILS

OPERATIONAL AMPLIFIERS

Second Edition

G. B. Clayton, BSc

The first edition has been extensively rewritten and enlarged, to provide an introduction for the newcomer to the subject and a comprehensive coverage of the known modes of operational amplifier action. The enormous expansion in operational amplifier use has been taken into account and many useful circuits are presented. The text will prove equally valuable to both students and the practising engineer in the measurement sciences.

1979 0 408 70202 8 £9.50 US \$ 21.50

PROGRAMMING FOR MICROPROCESSORS

Andrew Colin, MA, FBCS, CEng, FIEE

This book will enable electronic engineers, and amateurs with a knowledge of digital electronics, to learn microprocessor programming in the quickest and most efficient way. It covers the level of detail essential to the successful design of microprocessor systems and warns of common pitfalls. The Motorola 6800 is the main example used, but the techniques described can easily be transferred to other devices.

1979 0 408 00320 0 £7.95 US \$ 18.00



NEWNES - BUTTERWORTHS

Borough Green, Sevenoaks, Kent TN15 8PH

ADLEY
8000-10000
7000-8000
6000-7000
5000-6000
4000-5000
3000-4000
2000-3000
1000-2000
0-1000

1000-2000
2000-3000
3000-4000
4000-5000
5000-6000
6000-7000
7000-8000
8000-9000
9000-10000

1000-2000
2000-3000
3000-4000
4000-5000
5000-6000
6000-7000
7000-8000
8000-9000
9000-10000

1000-2000
2000-3000
3000-4000
4000-5000
5000-6000
6000-7000
7000-8000
8000-9000
9000-10000

1000-2000
2000-3000
3000-4000
4000-5000
5000-6000
6000-7000
7000-8000
8000-9000
9000-10000

Electronic Brokers Ltd

The Test Equipment People

Calibrated & Guaranteed 12 Months

Sound Level Meters

GENERAL RADIO
1933 Sound Level Meter with 1935 Cassette Data Recorder. 10dB-130dB. A, B & C weighting. Supplied with 1/2 microphone. Fast and slow response. Built in Octave band analyser with 10 centre frequencies from 31.5Hz to 16kHz, uses normal high quality C60 cassettes. Both Units are battery operated **£2,600.00**
1565B Portable Sound Level Meter 40-140dB. A, B & C weighting. Fast and slow response **£225.00**
1981 Portable Sound Level Meter 70-120dB. A weighting. Digital and analogue reading. Maximum hold facility on digital readout **£575.00**
1983 Portable Sound Level Meter 70-120dB. A weighting **£190.00**

AC Voltmeters & Electronic Multimeters

ADVANCE
VM77E Transistorised Voltmeter 10Hz-6Mz. 1mV-300V I/P Z 10M Ohms **£130.00**

BOONTON
91H RF Valve Voltmeter 20KHz-1200MHz. 100µV-300V **£415.00**

BRADLEY
112RF Millivoltmeter 3mV-300mV. 1-300MHz. Battery operated **£375.00**

BRUEL & KJAER
2409 Electronic Voltmeter 2Hz-200KHz. 10mV-1000V True RMS **£245.00**

HEWLETT PACKARD
400F AC Voltmeter 20Hz-4MHz 100µV-300V **£235.00**
411A RF Millivoltmeter 500KHz-1GHz. 10mV-10V **£395.00**

PHILIPS
PM.2503 Electronic Multimeter AC/DC Voltage and Current **£90.00**

ROHDE & SCHWARZ
U.R.V. RF Voltmeter 1KHz-240MHz with 50 Ohms insertion unit 20mV-10V **£235.00**

SIGN
AM324 AC Voltmeter 15Hz-500KHz 1mV-300V **£60.00**

Analogue Multimeters

AVO
 Model 7 **£40.00**
 Model 8 **£55.00**
 Test Set No. 1 **£65.00**
 Precision Avo **£45.00**
 Leads, Prods, clips for Avo's **£4.95**

PHILIPS
PM 2412 AC/DC Volts & amps 40K Ohms/V **£60.00**

Analysers

GENERAL RADIO
1911A Recording Sound Vibration Analyser 2.5Hz-25kHz. 1/3 and 1/10 octave bandwidth. Recorder spec: 7Hz-200kHz, 1mVac sensitivity 20-40 or 80dB range. **£2,100.00**

HEWLETT PACKARD
310A Wave Analyser 1KHz-2.5MHz. 10µV-100V voltage range. > 76dB dynamic range. B.F.O. and recorder O/P. Has built in AM, LSB and USB detector. **A SUPERB UNIT OF THE HIGHEST QUALITY** **£1200.00**
333A Distortion Analyser 5Hz-600KHz 0.1%-100% also Auto Null **£515.00**

RACAL
409 Modulation Meter 3-1500MHz. AM & FM **£345.00**

ROGERS/SIGN
DM.344 Distortion Meter 20Hz-20KHz **£230.00**

TEKTRONIX
1L30 Spectrum Analyser Plug In 925MHz-10.5GHz **£1200.00**
1L40 Spectrum Analyser Plug In 1.5-12.4GHz **£1275.00**

T.E.S.
D.566B Distortion Meter 10Hz-1MHz. 0.03 to 100% **£305.00**

MARCONI INSTRUMENTS
T.F. 791D Deviation Meter 4-1024MHz. Dev. 10Hz 125KHz **£195.00**

UREI
Sonipulse 100A Acoustical Analyser 40-16KHz. 27 x 1/3 octave bandpass filters. Microphone not included **£675.00**

Attenuators

MARCONI INSTRUMENTS
TF.1073A Series Step Attenuator DC-100MHz 0-100dB 50 or 75 Ohms **£75.00**
TF.2162 Step Attenuator DC-1MHz. 0-111dB 600 Ohms **£120.00**

ROHDE & SCHWARZ
RBD Attenuator BN 33662/60 DC-600MHz 20dB 60 Ohms **£40.00**
DPR Step Attenuator BN 18042/60 DC-300MHz 0-100dB 60 Ohms **£90.00**

ROHDE & SCHWARZ
RBD UHF Attenuator BN33661/50 DC-2.4GHz. 10dB. 50 Ohms **£55.00**

SEND FOR NEW 86 PAGE CATALOGUE

Containing latest information on our stocks of test equipment, minicomputers, computer peripherals, stroboscopes and tachometers.
 Airmail to overseas addresses, £2.

Bridges

GENERAL RADIO
1608A Impedance Bridge C. 0.05pF-1100µF L. 0.05µH-1000H R. 0.05MOhms-1.1MOhms **£1450**


MARCONI INSTRUMENTS
TF.2701 In Situ Universal Bridge **£395.00**
TF.1245 'Q' Meter Supplied with TF.1246 Oscillator 40KHz-50MHz **£625.00**

WAYNE KERR
B.221 (CT.530) Univ. Bridge 0.1% accuracy **£275.00**
Q.221 Low Impedance Adaptor for use with B.221 **£75.00**
B.521 (CT.375) Univ. Bridge 1% accuracy **£120.00**


Calibration Equipment

HEWLETT PACKARD
740B DC Voltage Source & Differential Voltmeter **£850.00**
741B DC Voltage Source & AC/DC Differential Voltmeter **£975.00**

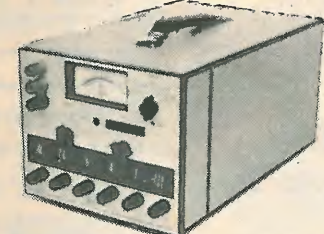FLUKE
332A DC Voltage Calibrator 0-1111.1110V in 3 ranges. 1ppm resolution. 0.003% calibration accuracy. O/P current 0-50mA **£1350.00**
931B True RMS Differential Voltmeter 10Hz-1MHz. 0.01V-1100V **£1,050.00**
883AB. AC/DC Differential Voltmeter 1mV-1100V **£975.00**
80E High Voltage Divider. Division Ratios 1,000:1 and 10,000:1. Max I/P 10kV. 0.01% Accuracy **£225.00**



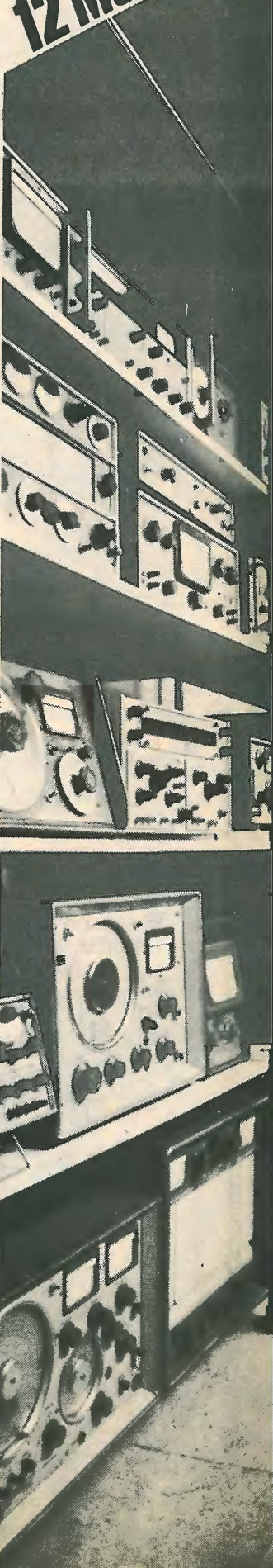TEKTRONIX
184 Time Mark Generator **£275.00**
2901 Time Mark Generator **£400.00**
2101 5nS Pulse Generator **£525.00**
109 Pulse Generator. Repetition rate 550-720Hz 250 ps risetime. Output 0-55V into 50 ohms **£320.00**



A copy of our trading conditions is available on request

ELECTRONIC BROKERS LIMITED
49-53 Pancras Road, London NW1 2QB **ADD 8% VAT TO ALL PRICES**
Tel. 01-837 7781. Telex: 298694
Hours of Business: 9 a.m.-5 p.m. Carriage and Packing charge extra on all Mon.-Fri.: closed lunch 1-2 p.m. items unless otherwise stated.

Calibrated & Guaranteed 12 Months

Electronics

49-53 Pancras Road, London NW12

Tel: 01-837 7781



Digital Counters

ADVANCE

- TC.15 + TC.15P1 Counter & Plug In** DC-500MHz. 9 digit. 10mV sensitivity **£495.00**
- TC.17 or TC.17A Time Counter** Freq. period. Period Average. Pulse width count DC-80MHz **£195.00**
- TC.21 Time Counter** Freq. Time, Period, Count Pulse width 2Hz-10MHz **£195.00**



TC.22 Time Counter DC-100MHz **£275.00**

FLUKE

- 1900A opt. 01** 5Hz-80MHz. 25mV Sensitivity with battery option **£215.00**
- 1900A Multifunction Counter.** 6 digit LED display. Autoranging. 5Hz-80MHz. 25mV sensitivity **£175.00**
- 1910A-01 Multifunction Counter.** 7 digit LED display, autoranging. 5Hz-125MHz. 15mV sensitivity. Battery/Mains operated **£285.00**
- 1910A** as 01 model but no battery opt **£199.00**
- 1911A-01 Multifunction Counter.** 7 Digit LED Display. Auto ranging. 5Hz-250MHz. 15-30mV sensitivity. Battery/mains operated **£380.00**
- 1920A-06 Communications Counter** 9 digit LED display. 5Hz-520MHz 15-25mV Sensitivity. Burst facility. A.F. resolution multiplier **£490.00**
- 1920A-13 Communications Counter** As 1920A-06 but 5Hz-1GHz, and no A.F. resolution multiplier **£525.00**
- 1925A Multifunction Counter** 9 digit LED display. 5Hz-125MHz. 15-25mV sensitivity. Adjustable trigger level. EMI Proof case **£405.00**
- 1953A-07 Universal Timer Counter** 9 digit LED display DC-520MHz. 30mV sensitivity variable trigger level **£675.00**
- 1953A-15-16 Universal Timer Counter** 9 digit LED display. DC-125MHz. 30mV sensitivity. Variable trigger level IEEE interface, rear inputs **£850.00**
- 1953A-15** as with opt. 16 but no rear input **£825.00**

PHILIPS

- PM.6612 Timer Counter** 10Hz-80MHz 9 digit display **£405.00**
- PM.6615 Timer Counter** 10Hz-1GHz. 10mV sensitivity **£795.00**
- PM.6620 Timer Counter** DC-45MHz. 50mV sensitivity **£395.00**
- PM.6661 Frequency Counter** 10Hz-80MHz. 20mV sensitivity. 8 digit **£185.00**
- PM.6630A Timer Counter** DC-160MHz. 8 digit Display **£600.00**
- PM.6645 Frequency Counter** 30Hz-512MHz. 5mV sensitivity **£710.00**

Digital Voltmeters & Multimeters

Carriage and packing charge extra on all items unless otherwise stated

Hours of business: 9a.m.-5p.m. Mon.-Fri. Closed lunch 1-2p.m.

ADVANCE

DRM6 True R.M.S. DVM 4 1/2 digit, scale 1999. 10mV-1KV 10µV resolution. Frequency range DC-1MHz **£295.00**

FLUKE

- 8020A DMM.** 3 1/2 digit LED Display. DC volts and current. Resistance and diode test. Battery operated **£99.00**
- 8030A-01 DMM.** 3 1/2 digit LED Display. DC Voltage and current. True rms AC Voltage and current. Resistance and diode test. Rechargeable battery supply **£135.00**
- 8600A-01 DMM** 4 1/2 digit LED display DC-AC voltage and current. Resistance. Mains or battery operated **£335.00**
- 8600A** as 01 model but no battery opt. **£290.00**

HEWLETT PACKARD

- 3490A DM** 5 1/2 digit, scale length 120000. AC Volts 1V-1KV 10µV resolution. DC Volts 100mV-1kV. 1µV resolution. Resistance 100 Ohms-10M Ohms. 1M Ohms resolution. Full auto-ranging and variable sample rate. Self check facility **£595.00**
- 34702A DMM C/W 34740A Display** 4 1/2 digit. AC/DC & Ohms **£295.00**

PHILIPS

- PM2424 DMM** 4 digit **£300.00**
- PM.2443 DC DVM** 4 1/2 digit, scale length 19999 **£430.00**
- PM2513 D.M.M.** 3 1/2 digit **£90.00**
- PM.2513A DMM** 3 1/2 digit, scale length 1999 **£95.00**

S.E. LABORATORIES

- SM210 DC DVM** 4 digit, scale length 9999. 100mV-1kV, 10µV resolution **£250.00**
- SM214 AC-DC DVM** 5 1/2 digit, scale length 10999. SC-DC Volts 1.1V-1.1kV, 10µV resolution **£300.00**

SCHLUMBERGER

A243 Digital Voltmeter 5 1/2 digit. 1µV resolution Autoranging DC & AC (mean) & Ohms **£675.00**

WESTON

4449 3 1/2 digit D.M.M. AC-DC volts and current, resistance **£79.50**

Miscellaneous

E.N.I.
500L R.F. Amplifier 2-500MHz. 20Db gain. 300mW o/p **£315.00**

FLUKE

412B H.V. Power Supply 0-2100V. Resolution 5mV o/p current 5-40mA **£365.00**

BRUEL & KJAER

2607 Measuring Amplifier 2Hz-200kHz. 10µV-300V range. Average times 0.1S-300S. A, B, C and D weighting. Output signal 10V rms for F.S.D. on meter **£1,200.00**

Oscilloscopes

COSSOR

- CDU 150 Dual Trace Oscilloscope** DC-35MHz. 5mV/20V/div. Full delayed sweep. Long persistence CRT **£450.00**
- 4000 Dual Trace Oscilloscope** DC-50MHz. 5mV-10V/div. Full delayed sweep. Unused **£495.00**

DYNAMCO

- 7100 Dual Trace Portable Oscilloscope** with 1Y2 and 1X2 modules DC-30MHz. 10mV-20V/div. Full delayed sweep **£350.00**
- 7500 Dual Trace Portable Oscilloscope** DC-40MHz. 10mV-20V/div. Full delayed sweep. Unused **£485.00**

HEWLETT PACKARD

- 184B Storage Scope** Rack style, vertical persistence, c/w 1808A Dual Channel Vertical Amp, DC-75MHz. 1825 base and Delay Generator, UNCONDITION — BARGAIN **£1,600.00**
- 1707B Dual Trace Portable Oscilloscope** DC-75MHz. 10mV/div. Full delayed sweep **£850.00**

PHILIPS

- PM.3240 Dual Trace Portable Oscilloscope** DC-50MHz. 5mV-20V/div. Full delayed sweep. From **£500.00**
- PM3010 Miniature Scope** DC-50MHz Trace. Battery/Mains operation. weight 1.8 Kg **£300.00**

SOLARTRON

CD 1400 Dual Trace Oscilloscope off CX 1441 and 1 off CX 1448 mod DC-15MHz **£1,000.00**

TEKTRONIX

- 531A Bench Oscilloscope** with Diagonal Plug-In unit CA. DC-13. Sensitivity 50mV-20V/div. **£2,000.00**
- 647A Bench Oscilloscope** with Diagonal Plug-in unit 10A2A and constant time base plug-in unit 11B2A DC-13. Sensitivity 10mV-20V/div. **£1,200.00**
- 585A Bench Oscilloscope** with Diagonal Plug-in unit 82 DC-80MHz. sensitivity 10mV-50V/div. **£700.00**
- 547 Bench Oscilloscope** with Diagonal Plug-in unit 1A1 DC-50MHz. sensitivity 5mV-20V/div. **£700.00**
- 545B Bench Oscilloscope** with Diagonal Plug-in unit CA DC-24MHz. sensitivity 50mV to 20V/div. **£400.00**

432 Portable Scope Dual Channel DC 25MHz. 1mV/Div. SUPERB CONDITION. QUANTITIES AVAILABLE **£400.00**



661 Sampling Scope c/w 5T3 and Dual Trace and accs. **£500.00**

CA Plug In for 530, 540 and 580 series **£100.00**


T832 Dual Trace Portable oscilloscope DC-35MHz. 2mV-10V/div. Sweep 0.5S-10nS/div. With trigger hold off **£500.00**

- 7313 Split Screen Bistable Storage scope** c/w 7A18 and 7B53A modules DC-25MHz. 5mV-5V/div. Full deflection sweep. Auto erase can be converted trace unit with addition of another module. EXCELLENTLY PRICED AT **£240.00**
- 7A26 Dual Trace Plug In Unit.** DC-200MHz. 5mV-5V/div **£60.00**
- 7D11 Digital Delay Plug In Unit.** De time or events. Digital delay readout digits. 100nS-1S delay time. 1nS resolution. Delay internal CRT display **£80.00**
- 543B Bench Oscilloscopes** with Diagonal Plug-in unit CA **£300.00**
- 555 Dual Beam Scope (Mainframe)** 33MHz wide choice of Plug-ins **£300.00**
- 422 Dual Trace Battery Portable Oscilloscope** DC-15MHz. 10mV-20V/div **£70.00**

A copy of our trading conditions is available upon request

Please note: All instruments offered are secondhand and tested and guaranteed 12 months unless otherwise stated

Calibrated & Guaranteed 12 Months

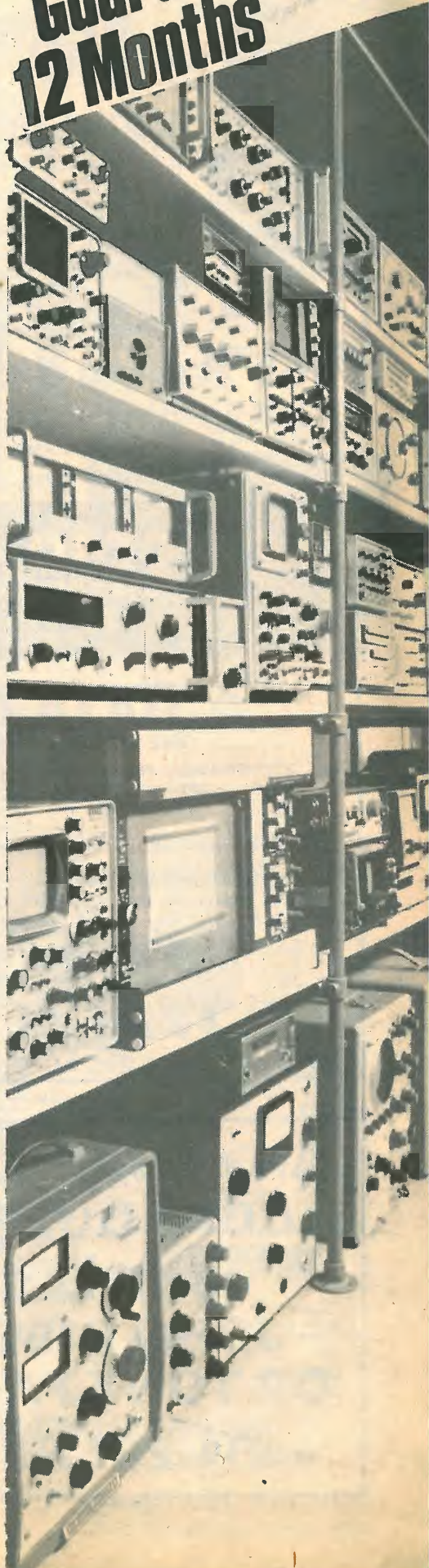

Brokers Ltd

The Test Equipment People

Oscilloscope Probes

PROBES
EB90 X1 Probe Kit DC-20MHz, 1.5 mtr cable 40pF I/P cap. 500V DC max. working. BRAND NEW **£9.00**
EB91 X10 Probe Kit DC-80MHz, 1.2 mtr. cable I/P Z 10M Ohms paralleled by 10.8pF. Compensation 15-50pF. BRAND NEW **£11.00**
EB95 X1 and X10 Switched Probe Kit. DC-15MHz in X1. DC-80MHz in X10. I/P Z 10M Ohms paralleled by 10.8pF in X10. 1.2 mtr. cable. BRAND NEW **£15.00**

GREENPAR
GE81500/2 X1, X10 Probe Kit. DC-200MHz. 10M Ohms I/P resistance. Compensation 15-50pF. UNUSED **£27.00**

Power Meters

HEWLETT PACKARD
430C RF Power Meter with 477B Thermistor Mount 10MHz-10GHz. 100mW **£225.00**

MARCONI INSTRUMENTS

TF 893A AF Power Meter 20Hz-35KHz. 1mW-10W I/P Z 2.5 Ohms-20K Ohms **£185.00**
TF 1020A Series RF Power Meter DC-250MHz. 50-100W FS or 150-300W FS. I/P Z 75 Ohms on 50-100W model. 50 Ohms on 150-300W model. From **£105.00**

T.E.S.
MU964 AF Power Meter 20Hz-50KHz. 1mW-10W I/P Z 2.5 Ohms-20K Ohms **£175.00**

Pulse Generators

ADVANCE
PG.52B Modular Pulse Generator 0.1Hz-30MHz/z w 2 x P3, 3 x P2, P4, P5, P1 **£700.00**
PG59 Dual Output Pulse Generator (CT600) 1Hz-10MHz **£595.00**

PHILIPS
PM5715 Pulse Generator Similar spec. to PM5712 but with variable rise and fall times **£875.00**
PM5775 Pulse Generator 1Hz-100MHz. Variable delay, width, rise and fall time. Single or double pulse, base line offset **£800.00**
PM5776 Pulse Generator Same spec. as PM5775 but dual O/P **£900.00**

Recorders

ADVANCE
Omniscribe 5000 Strip Chart Recorder 1 and 2 pen models available. Please contact us for full details on modules and main frames. From **£200.00**

PHILIPS
PM8110 Mini Single Channel Chart Recorder Sensitivity 10mV-10V full span. Chart width 12cm. Chart speed 5 and 20mm/min **£250.00**

RECORD
3" Paper Width Recorder with 500 μ A sensitivity FS. Left-hand zero. 1 and 6 per hour chart speed **£75.00**

Radio Receivers

EDDYSTONE
730/1A Communication Receiver 480KHz-30MHz in 5 ranges, BFO, noise limiting, AF filter, AVC, RF/gain, S Meter **£175.00**

730/4 Communications Receiver 480KHz-30MHz, 5 Bands, BFO, noise limiting, AVC, RF gain, AF filter. UNUSED CONDITION **£275.00**

880 Communications Receiver 500KHz-30.5MHz in 1MHz wavebands. BFO, AGC, RF/IF gain, noise limiting, AF filter, S Meter **£325.00**

RACAL
RA117E Communications Receiver 1-30MHz MHz and KHz tuned separately. Selectivity 100Hz-13kHz in 6 ranges. BFO, AVC, Noise limiter, RF/IF gain, S meter **£375.00**

Signal Sources

ADVANCE
H1E LF Sine/Square Oscillator 15Hz-50KHz. Sine Square **£75.00**
J2E L.F. Oscillator 15Hz-50KHz **£90.00**
J4 L.F. Oscillator 10Hz-100KHz **£135.00**
SG67A Wide Range Oscillator 1Hz-1MHz sine or square wave **£95.00**
SG68A Low Distortion Oscillator 1.5Hz-150kHz. Battery operated. Distortion less than 0.01% **£150.00**

FLUKE
6160A/DX Synthesised Signal Generator 4-30MHz. 1Hz resolution **£675.00**

HEWLETT PACKARD
202H AM/FM Signal Generator 54-216MHz. From **£495.00**
608D VHF Signal Generator 10-420MHz. From **£495.00**
612A U.H.F. Signal Generator 54.0-1230MHz. From **£950.00**
616A U.H.F. Signal Generator 1.8-4.2GHz. **£550.00**
626A S.H.F. Signal Generator 10-15.5GHz **£500.00**
AM Generator 608E, 10-480MHz. AM 0-95% **£675.00**

MARCONI INSTRUMENTS
TF 801D/1 AM Signal Generator 10kHz-470MHz **£400.00**
TF.995A/5 AM/FM Signal Generator 1.5MHz-220MHz **£380.00**
TF995B/2 AM/FM Signal Generator 200KHz-220MHz **£675.00**
TF1060 AM Signal Generator 450-1250MHz. From **£400.00**
TF1101 R-C Oscillator 20Hz-200KHz. 1mV-20V into 600 Ohms. Metered O/P **£125.00**
TF2015/1 AM/FM Generator, 10-520MHz. Narrow Deviation model for mobile radio testing. **Pristine condition** **£1100.00**
TF2006 AM/FM Generator, 10-220 MHz **£875.00**

TF.2005R Two Tone AF Signal Source **£350.00**
TF2100 AF Oscillator 20Hz-20KHz **£150.00**

MUIRHEAD
D890A L.F. Decade Oscillator 1Hz-111.1kHz **£260.00**

PHILIPS
PM5125 Sine/Square Oscillator 10Hz-1MHz **£145.00**
PM5167 Function Generator 1MHz-10MHz. Sine, square, + pulse, ramp, triangle, single shot with variable phase **£875**
PM5105 LF Oscillator 10Hz-100KHz **£156.00**
PM5324 AM/FM Signal Generator 100KHz-110MHz **£450.00**
PM5326 AM/FM Signal Generator 100KHz-125MHz Digital Readout **£695.00**



TELECOMMUNICATIONS

SG5U Battery Operated F.M. Signal Generator 400-480MHz **£390.00**

SIGN ELECTRONICS
S324 Low Distortion Oscillator 6Hz-60kHz Battery operated **£90.00**

Sweep Generators

KAY
154C Sweeper Main Frame with PM7650B Plug-in Unit 50KHz-110MHz **£450.00**

MARCONI INSTRUMENTS
TF1099 MF Sweep Generator 100KHz-20MHz **£175.00**

ROHDE & SCHWARZ
Polyscop SWOB I Wideband Sweeper and Display 0.5-400MHz **£1,000.00**
SWH LF Sweep Generator 50MHz **£250.00**

Test Sets

MARCONI INSTRUMENTS
TF.2332 AF Transmission Test Set 20Hz-20kHz **£425.00**
TF.2333 MF Transmission Test Set 30Hz-560kHz **£600.00**
TF.2343 Quantization Distortion Tester **£400.00**

A copy of our trading conditions is available upon request

49-53 Pancras Road
London NW1 2QB
Tel: 01-837 7781. Telex: 298694

ADD 8% VAT TO ALL PRICES

OPTOELECTRONICS

RED £0.10
GREEN £0.19
YELLOW £0.18

RED £0.14
GREEN £0.19
YELLOW £0.18

DISPLAYS

HP5082-7730 **£1.15**
DL704 **£1.15**
FNDS07 **£1.05**
DL704 Economy **£0.75**
DL707 Economy **£0.75**

74 Series TTL

7400	0.12	7473	0.27	74153	0.65
7401	0.12	7474	0.27	74154	1.05
7402	0.15	7475	0.33	74155	0.70
7403	0.12	7476	0.25	74156	0.70
7404	0.15	7480	0.50	74157	0.65
7406	0.25	7482	0.73	74160	0.70
7407	0.25	7483	0.60	74161	0.75
7408	0.14	7485	1.05	74162	0.75
7409	0.18	7486	0.30	74163	0.75
7410	0.12	7489	2.45	74164	0.85
7411	0.18	7490	0.34	74165	0.85
7412	0.20	7491	0.75	74166	1.25
7413	0.36	7492	0.45	74167	2.95
7420	0.12	7493	0.45	74173	1.45
7425	0.25	7494	0.90	74174	1.05
7427	0.25	7495	0.55	74175	0.90
7430	0.12	7496	0.55	74176	1.05
7432	0.27	74100	1.35	74177	0.85
7437	0.27	74104	0.45	74180	1.10
7438	0.27	74105	0.45	74181	2.10
7440	0.12	74107	0.35	74182	1.20
7441	0.48	74121	0.30	74185	2.10
7442	0.50	74122	0.40	74190	1.05
7445	0.80	74123	0.52	74191	1.05
7446	0.80	74125	0.45	74192	0.95
7447	0.85	74126	0.55	74193	0.95
7448	0.50	74132	0.65	74194	0.95
7450	0.12	74136	0.75	74195	0.95
7451	0.15	74141	0.80	74198	0.95
7453	0.15	74145	0.70	74197	0.95
7460	0.15	74150	0.90	74198	1.95
7472	0.27	74151	0.55	74199	1.95

C-MOS

4016	0.40	4046	1.35
4017	0.90	4047	0.95
4018	0.90	4049	0.50
4022	0.90	4050	0.50
4023	0.20	4060	1.15
4024	0.80	4066	0.70
4025	0.20	4069	0.25
4027	0.55	4070	0.25
4010	0.45	4076	0.20
4011	0.15	4928	0.75
4012	0.15	4029	1.00
4013	0.36	4033	1.25
4014	0.90	4040	1.00
4015	0.90	4042	1.75

C7205EN MULTITESTER

20,000 OPV
£9.75
P&P 75p

AC volts: 0 to 10, 50, 250, 1000
DC volts: 0 to 5, 25, 125, 500, 1000
DC current: 0 to 50 μ a, 250 ma
Resistance: 0 to 300 ohms, 6K, 30K
6 meg ohms
— 20 to + 22 db
115 x 78 x 33mm

Decibels:
Size: 115 x 78 x 33mm



LB1 TRANSISTOR/DIODE TESTER

£19.95
P&P 75p

Tests 1CO, Alpha and Beta. Measures parameters of transistors so that readings can be checked against manufacturers specification. Quick Test socket mounted on front panel. Full view meter for accuracy and easy reading.
Dims.: 178 x 108 x 83mm



IT 1/2 20,000 OPV

£11.95
P&P 75p

AC volts: 0 to 10, 50, 100, 500, 1000
DC volts: 0 to 5, 25, 50, 250, 500, 2500
CD current: 0 to 50 μ a, 2.5 ma, 250 ma
Resistance: 0 to 6K ohms, 6 meg ohms
— 20 to + 22 db
Decibels: 10 pt, 0.01 μ f, 0.1 μ f
Capacitance: 4 1/2 x 3 1/4 x 1 inch



TE20D R.F. SIGNAL GENERATOR

£57.00
P&P £1.25

Accurately covers 120 KCS. To 500 MCS in 6 bands. Directly calibrated. Variable R.F. Attenuator. 240V AC.
Dims: 140 x 215 x 170mm



TMK600 MULTITESTER

30,000 OPV
£20.95
P&P 75p

A sturdy and reliable instrument. Has internal buzzer.

AC volts: 0 to 2.5, 10, 25, 100, 250, 500, 1000
DC volts: 0 to 0.25, 1, 2.5, 10, 25, 100, 250, 1000
DC current: 0 to 50 μ a, 5 ma, 50 ma, 12 amp.
Resistance: 0 to 6K, 60K, 6 meg, 60 meg.
Decibels: — 20 to + 56 db
Short test: Internal buzzer
Size: 160 x 110 x 55mm



LT101, 1,000 OPV

£6.95
P&P 75p

AC volts: 0 to 10, 50, 250, 1000
DC volts: 0 to 10, 50, 250, 1000
DC current: 0 to 1 ma, 100 ma
Resistance: 0 to 3K ohms
0 to 150K ohms
Size: 2 x 3 1/2 x 1 inch



Linear

380	14 Pin DIL	£1.05
381	14 Pin DIL	£0.00
387	8 Pin DIL	£0.75
555	8 Pin DIL	£0.30
565	14 Pin DIL	£1.10
567	8 Pin DIL	£1.40
741	8 Pin DIL	£0.20
741	TO5	£0.25
748	8 Pin DIL	£0.35
3046	14 Pin DIL	£0.75
3130	8 Pin DIL	£0.85
3140	8 Pin DIL	£0.85
3140	TO5	£0.80
3900	14 Pin DIL	£0.80

RAM
2102 450 nSec. **£1.40**

ELECTRO-TECH COMPONENTS LTD.

364 EDGWARE ROAD, LONDON, W.2. TEL: 01-723 5667
CALLERS WELCOME

DATA GENERAL COMPUTERS

WE HAVE SEVEN COMPLETE SYSTEMS. EACH COMPRISING:

Cabinet with power supplies. Fans, mains filter units, 240V 50HZ. Nova 820 mainframe 240V 50HZ, Nova 820 expansion chassis 240V 50HZ. CPU1 (8206) power mon and restart. CPU2 (8207) mult/div. I/O int (4007/4010) for TTY. 8192K 16-bit memory board (8269/8274) word word. Disc pack controller board (4046). Gen. purpose int. bd. with data channel (4040/4042). 2.5m byte disc storage system (Diablo) Series 30 (4047A) moving head. Disc power supply (240V 50HZ) with adaptor and logic board (4047). Computer Control Panel.

OFFERS AROUND £5000

C.T. ELECTRONICS (ACTON) LTD.

267 & 270 ACTON LANE, LONDON, W4 5DG Telephone: 01-994 6275

ANY MAKE-UP OR COPY QUERIES CONTACT JOHN GIBBON OR TONY FAYERS 01-261 8353

IS YOUR POWER SUPPLY OUTGROWING SYSTEM SIZE? THEN SWITCH TO ASTEC SWITCH MODE POWER SUPPLIES



Reliable, Compact, Efficient
50W Range 4" x 8.5" x 2", 2lb. 5V 10A and other voltages available.
100W Range 6.5" x 8.5" x 2", 3.3lb. 5V 20A and other voltages available.

GET MORE WATT PER £ WITH ASTEC

VIDEOTIME PRODUCTS
56 Queens Road, Basingstoke, Hants, RG21 1REB
Tel: (0256) 56417 Telex 858747

Electronic Brokers The Computer People

STOP PRESS — LATEST SPECIAL PURCHASES

SEALCTRO PATCH BOARDS

Programme boards for switching and interconnecting input/output circuits. 11 x 20 XY matrix. Interconnection is by means of shorting, skip and component holding pins (not included). Dimensions: 7½" x 5¾" x 1"

PRICE: £12.50
(mail order total £14.58)

NEW KEYTOP/KEYSWITCH KITS — ASCII CHARACTER SET BRAND NEW SURPLUS

Pack of 58 keytops and keyswitches comprising:—49 "Qwerty" set, TTY format + 9 Edit/Function keys

PRICE: £15.00
(mail order total £17.28)

SURPLUS ASCII KEYBOARDS

KB3 ROM-encoded ASCII keyboard with 63-push-button key stations. Selectable mode — either full ASCII or TTY. Selectable parity. TTL-compatible. Power requirements, +5V-12V. Constructed on rugged PCB with metal mounting plate. Supplied with full technical data.

Manufacturers surplus.

ONLY £35.00 + p.&p.
VAT (mail order total £39.42)



SCOOP!

Now available — further limited stocks of Hazeltine H 1200 24 x 80 format, remaining spec. as for H 1000

PRICE: £425



H1000 ONLY £350
HAZELTINE H1000 SPECIFICATION
SCREEN SIZE — 12" diagonal.

MASSIVE BULK PURCHASE BRINGS YOU HAZELTINE VDUs AT LOWEST EVER PRICES

SCREEN CAPACITY — 960 characters 80 per line x 12 lines.
CURSOR — underline.
CHARACTER GENERATION — 5 x 7 dot matrix 625 line raster.
CHARACTER SET — 64 ASCII alphanumeric and symbols.
CHARACTER SIZE — 1/8 inch (.32cm) nominal height. 3/32 inch (.24cm) nominal width.
TUBE PHOSPHOR — P4 (white on black)
REFRESH RATE — 50 fields per second.
KEYBOARDS — TTY format attached.
INDICATORS — Power On. Parity Error. Dataset ready.
PARITY — Parity error indicated by Parity light and question mark (?) displayed in character position.
TRANSMISSION — Asynchronous. Switch-selectable for any two standard rates up to 9600 baud.
OPERATING MODES — Full/half Duplex.
MEMORY — High speed MOS refresh.
STANDARD INTERFACE — CC ITT V-24. (EIA RS-232 B/C).
REMOTE COMMANDS — Home Cursor, Clear Screen, Carriage Return, Line Feed.

HAZELTINE H2000 SPECIFICATION

SCREEN SIZE — 12" diagonal. 1998 characters; 74 per line x 27 lines.
CHARACTER GENERATION — 5 x 7 dot matrix 625 line raster.
CHARACTER SET — 64 alphanumeric and symbols. 32 ASCII control codes.
KEYBOARD — Detachable, solid state, teletypewriter design. 10-key numeric cluster plus editing and cursor control keys.
TRANSMISSION — Asynchronous. Switch-selectable for combinations of 5 standard rates, 75 to 9600 baud.
OPERATING MODES — Switch-selectable, full duplex, half duplex or batch (buffered).
MEMORY TYPE — 2048 x 8 RAM.
EDITING FEATURES — Full Cursor controls plus Insert/Delete Character, Insert/Delete Line, Clear Screen, Clear Foreground Data Only, Tab.
STANDARD INTERFACE — CC ITT V-24 (EIA RS-232 B/C) or 202C Compatible.
REMOTE COMMANDS — Insert/Delete Line, Clear Screen, Clear Foreground Data Only, Home Cursor, Address Cursor, Set Background Intensity, Set Foreground Intensity, Carriage Return, Backspace, Ring Bell, Transmit, Print.



H-2000A ONLY £495
Also available:
H-2000B £595

AUXILIARY OUTPUT — Standard printer interfaces; standard cassette interface; remote monitor interface.
TUBE PHOSPHOR — P39 (green on black).

Mini-Computer Exchange

DEC BIG SAVINGS ON OUR LARGE STOCK OF PROCESSORS, PERIPHERALS AND ADD-ON MEMORY

PDP8A Add-on RAM Read/Write Memory:—
MSBAA 1K £225.00
MSBAA 2K £375.00
MSBAD 4K £550.00

PDP11-04/11-34 Add-on MOS Memory:—
MS11FP 8K £550.00
MS11JP 16K £1,200.00

PDP11-05/11-40/11-45 Add-on Parity Core Memory:—

MM11LP 8K £1,000.00
MM11UP 16K £1,250.00
MF11UP 16K complete with backplane £1,500.00
PCB1 High Speed Reader/Punch & Control for PDP81 £895.00
..... £195.00

DD11A 4 SPC-slot backplane £195.00
DR11B DMA Interface complete with backplane £750.00

VT8E Alphanumeric & graphic Display terminal complete with PDP8E interface £875.00
KW11P Programmable Clock £345.00

PR11 High-speed paper tape reader and control £1,450.00
RT01AB Numeric single-line data entry terminal £150.00

TC11 TU56 DEctape drive and control £1,395.00

Printers and Terminals

LARGE STOCKS OF ASR33 AND KSR33 TELETYPE TERMINALS


- * ASCII Keyboard
 - * Hard-copy unit (friction or sprocket paperfeed)
 - * Paper tape punch and reader (ASR33 only)
 - * Line unit (20mA/6V/80V)
- Prices from **£425 (KSR)** and **£650 (ASR)**.

CENTRONICS MODEL 101 MATRIX PRINTERS

- * 64 ASCII (uppercase) character set
 - * 132 Column
 - * 165 Characters per second
 - * 5 x 7 dot matrix
 - * Parallel Input
- PRICE: £750.00**

ANOTHER SCOOP PURCHASE — SCOPE DATA 240 CPS MATRIX PRINTER

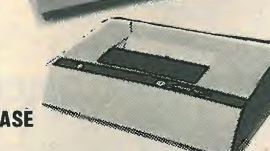- * 80 Column Receive-Only Printer with full upper & lower case ASCII character set.
 - * Standard RS232 interface
 - * Electro-Sensitive printing ensuring quiet operation
 - * BRAND NEW SURPLUS.
- Dimensions: 17½" x 13½" x 5½"
- PRICE: ONLY £695**



WANG THERMAL PRINTERS

- * 64 ASCII (uppercase) character set
 - * 80 Columns
 - * Silent Operation
 - * 30 characters per second
 - * RS232 Input
- PRICE: £495.00**

Keyboards

NEW TOP QUALITY ASCII KEYBOARDS AT LOW, LOW PRICES



- * Full 128 ASCII character set with ROM encoding
- * Standard TTL logic — power requirements + 5V-12V
- * Range of spares and accessories.

KB756 56 key-stations, mounted on PCB **ONLY £49.50**
(mail order total £55.08)

KB756MF As above, fitted with metal mounting frame for extra rigidity **ONLY £55.00**
(mail order total £61.02)

Optional Extras:		Mail Order Total
KB15P Edge connector	£ 3.35	£ 4.05
KB701 Plastic Enclosure	£12.50	£14.31
KB702 Steel Enclosure	£25.00	£28.62
KB710 Numeric Pad	£ 8.00	£ 9.18
KB2376 Spare ROM Encoder	£12.50	£14.04

LATEST ADDITION TO THE RANGE



KB771 71 Station keyboard incorporating separate numeric/cursor control pad and installed in custom-built steel enclosure with textured enamel finish. Case Dimensions: 17¼" x 7½" x 3¾"

Total weight: 4kg. **PRICE £95.00**
(mail order total £108.00)

Quantity Discounts available

ELECTRONIC BROKERS LIMITED (COMPUTER DIVISION)

49-53 Pancras Road, London NW1 2QB. Tel. 01-837 7781. Telex: 298694

A copy of our trading conditions can be supplied on request

Hours of business:
9 a.m.-5 p.m. Mon.-Fri. Closed lunch 1-2 p.m.

ADD 8% VAT
TO ALL PRICES

Carriage & Packing charge extra
on all items unless otherwise stated

WW — 110 FOR FURTHER DETAILS

SOUTHEAST ENGLAND'S ELECTRONICS CENTRE

PHILIPS GM 6001
20 HZ - 1000 MHZ

VVM

We are now able to offer this superb compact VVM at even lower prices. Original specifications
1v-300v AC
300mv-1000v DC
1Ω-1000MΩ resistance
Input Z
0.3v range 10MΩ
1v range 30MΩ
All others 100MΩ

Features include:
Large readable meter, switchable centre zero, lightweight, supplied complete with manual and mains plug, believed in good condition but untested.

NEW LOW PRICES
*Grade 1 damaged A.C. probe £25.00 + p.p.
*Grade 2 less A.C. probe £20.00 + p.p.
*Probe circuit shown in manual.

Post and Packing £1.75.



OPEN MONDAY-SATURDAY 9am-5.30pm

OPTO SMASH!

TIL 302/MAN 7 7 segment LED readout common anode direct drive (via resistors) from 7447 £1-10 each
TIL 119/OC72 Darlington opto isolator 3 for £1-00.

SAVE THAT SPACE! THICK FILM RESISTOR NETWORK 7x100Ω resistor in DIL pack. Ideal for use with 7 seg. displays etc. 4 for £1-00.

TIL305 0.3" x 5 matrix LED alphanumeric readouts £4.75 each.

PHOTO TRANSISTOR
Fairchild FPT-100 NPN silicon 30v, 25ma. 4 for £1-00.

In stock now test equipment, microprocessors, teletypes, transformers, power supplies, scopes, sig. gen's, motors, peripheral equipment, I.C.'s, tools, components, variacs, keyboards, transistors, microswitches, V.D.U.'s sub-assemblies + thousands of other stock lines. Just a mere fraction of our vast range, is displayed below: 100's of bargains for callers.

SUPER VALUE PCB Special

This superb P.C.B. consists of 59 digital I.C.'s including 7442, 7475, 7404 etc. etc. All I.C.'s are plugged in on 14 and 16 pin D.I.L. top quality gold plated sockets. The board also includes 77 long lead 2N3704 NPN transistors, 1 TIP 33, 77 IN4148 silicon diodes, res. caps. connectors etc. All components easily removable. Original cost well over £100.00.

59 digital I.C.'s
78 silicon transistors
59 D.I.L. I.C. sockets

Unbeatable value at **£4.75** + p.p. 75p.

HOW TO GET HERE
Victoria or London Bridge to East or West Croydon. 1 minute from West Croydon Bus and Rail Stations. 25 minutes Gatwick Airport.

THIS MONTH'S SNIP

HARTLEY CT436 DC-6 MHZ DOUBLE BEAM OSCILLOSCOPES

A new Ministry release enables us to offer this much coveted mains portable scope, featuring a real double beam C.R.T. with independent brightness controls, and sensitivity of 10mv/cm. Dimensions of only 10" x 10" x 15" make this ideal for portable work, T.V. servicing etc. etc.

Supplied in good external condition complete with mains lead, but untested Full service manual £5.00 purchased with scope, £10.00 purchased separately.

£75.00 + p.p. £4.50.

DISPLAY I.C. AND TRANSISTOR BARGAINS NEVER CHEAPER

All I.C.'s and Transistors by well known manufacturers and fully guaranteed. No fall outs. Comprehensive data on I.C.'s 12p per type.

2N4351 N channel MOS FET,
2N4352 P channel MOS FET,
95p each £1.50 per pair.

HIGH VOLTAGE NPN POWER SWITCHING transistors BVcbo 600v BVceo 500v 8Vbe 5v 1c 5 amps Pz 125 watts HFE 60 typ ft 2.5 mhz ideal invertors, etc. TO3 £1.50 each 4 for £5.00.

BF258 NPN 250v @ 200 ma 40p each 3 for £1-00.

A.E.I. power TRIACS 10 amp 400v ready mounted on 2 1/2" x 2 1/2" heatsink 95p each 4 for £3-50.

I.R. BS801 2.5 amp 100v bridge rec. P.C. mount long leads. 30p each 4 for £1-00.

IN4998 4 amp 100v P.C. mount diodes Long leads 12p each 10 for £1-00.

I.R. 25G60 60 amp 600v silicon stud diodes £1-80 each 8 for £1-00.

E.C.C. 1.6 amp 400v triacs 35p each 4 for £1-00.

2N1671B unijunction 450mw 30v 45p each 3 for £1-00.

IN4004-SD4 1 amp 400v diodes 6p each 20 for £1-00.

I.R. 10 AMP BRIDGE RECS. 200 volt working. £1-00 each.

ULTRA 39 WAY 0.1" DOUBLE SIDED EDGE CONNECTORS. Open ended, ideal veroboard, easily cut 75p each.

PLESSEY EDGE STACKABLE DECADE SWITCHES Gold plated contacts, dimensions 2 x 2 x 3/8 80p each 8 for £5.00.

LM309K +5v 1.2 amp regulator £1.00 each 6 for £5.00

AMPHENOL 50! BNC chassis socket single hole fixing 45p each

C90 Audio Cassettes screw type construction 40p each 3 for £1-00.

Scotch 215 Long Play Tape Brand new "4" low noise on 1200 5 1/4" spools £1-50 each 4 for £5-00 + P.P. 45p.

1000 Watt fully shrouded auto transformers term. block connections £13.75 + P.P. £2-25.

Bulbs 24v 14 watt white frosted S.B.C. 8 for £1-00.

S.B.C. Bulb Holders All steel cad. plated panel mount easily fixed via nut and round hole. Ideal disco displays, scoreboards etc. 4 for £1-00.

Xtal filters S.E.1. OC1121/B miniature low insertion loss P.C. mount C.F. 10.7 mhz with B.W. of 7.5 khz. 2000 Ω imp. in-out Brand new at £7.50

Heavy Duty Flat Insulated Earth Braid 80-100 amp braided tinned copper in heavy clear P.V.C. sheath 40p per metre £5-00 for 15 metres P.P. 8p per metre.

BULGIN miniature 6 way male chassis mount socket and matching shrouded free plug. 60p each 2 for £1-00.

Red L.E.D.'s full spec. 0.2" 12p each 10 for £1-00.

Dynamic Stick Mics 600 Ω with built in on/off switch complete with lead and min. jack plug £1-00 each.

TO5 HEATSINKS "Thermaloy" black anodised press on aluminium finned type. 15p each 10 for £1-00.

HARDWARE PACK Don't be stuck for the right nut and bolt for the job. Pack contains B.A. Metric, Unified, Self Tap. etc. nuts, bolts, screws, washers, etc. in brass bronze and steel. All steel items plated. Average contents 400-600 pieces. **£2.50** sold by weight, 2-lb bag

M.P.U. CORNER

SAVE £120 TANDY TRS 80 MEMORY UPDATE

Update your new or existing TRS 80 from 4K to 16K of RAM. Install your own chips and save £120.00. Kit includes full instructions and 8 x 16K full spec. devices. Simple plug-in and jumper. **£108** change no soldering.

TRS 80 software now in stock. Programs include: Micro Chess, Space Fighter, Startrek 3, etc. Phone for details.

RACAL SUPERGRADE C10 CASSETTES screw fixing, complete with library cases, 2 for £1.00, 10 for £4.50, p+p 70p.

Self-adhesive die cut Cassette labels 20 for £1.00.

POWER SUPPLY UNITS

5 VOLT 2.5 AMP T.T.L. P.S.U.

Made for T.T.L. this compact ex computer systems unit features a 10 amp transformer with D.C. outputs of 5 volts @ 2.5 amps and 7.5 volts @ 5 amps. The 5 volt output is fully regulated and smoothed and has electronic current limiting. May be easily moded for 5 volts @ 7.8 amps, believed working but untested.

Complete with circuit **£7.25** p.p. £1-50

EQUIPMENT CASES

Superb professional fully enclosed, made for the G.P.O. to the highest standard, offered at a fraction of their original cost they feature aluminium sides, hinged removable front panel, which can be secured by 2 screws to prevent prying fingers. All are finished in two tone G.P.O. grey and although believed brand new may have minor scuff marks/scratches due to bad storage. Dimensions:

SMALL 16" D x 6 1/2" H x 8 1/4" W **£5.25** + P+P £1.00

MEDIUM 16" D x 6 1/2" H x 14 1/4" W **£7.25** + P+P £1.15

LARGE 16" D x 12 1/2" H x 17 1/4" W **£10.75** + carr £1.75

MUFFIN FANS

Ideal equipment cooling etc. tested, ex-equipment.

240v 50-60 HZ **£5.75** + p.p. 40p

110v 50-60 HZ **£4.75** + p.p. 40p

MOS ROM CHARACTER GENERATORS

Purchased from a major V.D.U. manufacturer, this end of line Motorola 3 chip R.O.M. set is pre-programmed to give a full 96 upper and lower case character font on a 10x7 matrix for the upper case and a 14x5 matrix for the lower descenders "g j p q y" thus resulting in a superb and extremely legible display. Full ASCII input, TTL compatible in and out. Supplied with 9 page data and instruction pack, brand new at only **£7.25** P+P 30p.

This item cannot be repeated. Hurry while stocks last.

ELECTRONIC COMPONENTS & EQUIPMENT

66% DISCOUNT

Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of I.C.'s Transistors, Relays, Cap's., P.C.B.'s, Sub-assemblies, Switches, etc. etc. surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads., we are packing all these items into the "BARGAIN PARCEL OF A LIFETIME" Thousands of components at giveaway prices! Guaranteed to be worth at least 3 times what you pay plus we always include something from our ads. for unbeatable value!! Sold by weight

71b £ 4-75 141b £ 7-50
281b £12-75 561b £21-00
1121b £34-00 P.P. £1-00

MANY HUNDREDS OF TRANSFORMERS IN STOCK - SEND SAE FOR LIST

DIODES · DIODES

1N4148-1N914-types etc. mixed and untested 1000+ bag £1-50 P.P. 40p. Buy some for a friend!

Where cost of post and packing not indicated please add 25p per order. Collection saves cost of postage but if collecting please telephone to check availability.

We are always interested in buying P.C.B.'s surplus components, test equipment, valves, etc. Phone for details

KEYBOARD

A special bulk purchase enables us to offer the above Keyboard at a lowest ever price. 49 coded keys encoded into a direct TTL compatible 7 bit output. Features such as delayed strobe, 5 volt D.C. single rail operation and rollover protection make this an absolute must for the MPU constructor! Supplied complete with connection diagram and edge connector, at a secondhand "no time to test" price of only **£18.50** P.P. £1-50

SEMICONDUCTOR 'GRAB BAGS'

Amazing value mixed semiconductors, include transistors, digital, linear I.C.'s, triacs, diodes, bridge recs. etc. etc. All devices guaranteed brand new, full spec. with manufacturers markings, fully guaranteed.

50 + BAG **£2.75** 100 + BAG **£4.95**

MULLARD + PLESSEY HY-GRADE SMOOTHING CAPS

1500 mF 100v Screw Term	50p*
3300 mF 63v Screw Term	60p*
4500 mF 25v Screw Term	60p*

*ex equipment but tested

HIGH EFFICIENCY SMITHS RADIAL BLOWERS

Are your hot parts sweltering? Then keep them cool with our high efficiency radial snail type blowers. Made by Smiths, designed for continuous use in expensive electronic equipment very powerful and quiet, gives massive air flow to prolong component life and reliability. Easily mounted, air aperture 2 1/2" x 3" supplied complete with fixing bolts. Ideal liners etc. Please state 240v or 110v operation. 50hz only.

BRAND NEW
£4.25 P.P. £1-10

MINIATURE SNAIL BLOWER

This superb "little" blower, imagined as a cube measures only 3 1/4" x 3 1/4" x 3 1/4" with a 1 1/4" x 1 1/4" air output aperture. Almost silent running, ideal for miniature projectors, computers, P.S.U.'s etc. Brand new at only Please state 110v or 240v operation.

£3.99 + p.p. 55p.

ONE INCH NUMERIC DISPLAYS

This fine example of modern miniature optical engineering consists of a 12 lamp and lens system constructed to project numerals between "0" and "9" and a "." and "-" sign onto an opaque screen to give extremely legible, rounded characters of up to 1" in height. Features easily replaceable 6 volt bulbs, changeable "negative for different character fonts. Dimensions 1 1/2" x 1 1/2" supplied complete with bulbs and plug in carrier. Ex. equipment

£1.75 p.p. 30p.

ELECTRONICS

103 Tamworth Road Croydon CR9 1SG 01 688 1833

MAIL ORDER INFORMATION:
All prices inclusive of VAT. Cash with order. Minimum order value £1-00. Postage quoted for UK only. Bona Fide account orders minimum £10-00. Export and trade enquiries welcome. Orders despatched same day where possible. Access and Barclaycard welcome.

VALVES		Minimum Order £1.00	VALVES VAT PLEASE ADD 12 1/2 %								
A1065	1.25	EL41	0.80	PL509	3.25	3A4	0.80	6J6	0.50	20L1	1.00
ARB	0.50	EL81	1.05	PL802	2.80	3D6	0.40	6J7	0.75	20P1	0.40
ARP3	0.60	EL82	0.60	PLL80	1.80	3D21	20.00	6J7G	0.50	20P3	0.60
ATP4	0.50	EL84	0.60	PY33	0.60	3E29	5.50	6K7	0.70	20P4	1.10
B12H	3.00	EL86	0.95	PY80	0.60	3S4	0.50	6K7G	0.35	20P5	1.00
CY31	0.50	EL90	1.30	PY81/8000.55	3V4		0.85	6K8GT	0.55	25L6GT	0.80
DAF96	0.60	EL91	1.60	PY82	0.45	5B/254M	6.50	6L6M	1.90	25Z4G	0.70
DET22	19.50	EL95	0.70	PY83	0.50	5B/255M	6.50	6L6GT	0.90	30C15	1.00
DF96	0.60	EL504	0.80	PY88	0.85	5B/258M	6.50	6L7G	0.65	30C17	1.10
DK96	0.80	EL802	1.50	PY500	1.35	5R4GY	1.10	6L18	0.60	30C18	
DH76	0.40	EL822	3.00	PY859	5.75	5U4G	0.95	6L20	0.50	see PCF805	
DL92	0.50	EM31	0.75	PY801	0.60	5V4G	0.65	6Q7G	0.80	30F5	1.00
DY86/87	0.55	EM80	0.60	QV03	102.50	5Y3GT	0.55	6A7	0.55	30F12	1.20
DY802	0.85	EM81	0.60	QV03-12.50	5Z3		1.00	6SG7	0.75	30FL12	1.20
E55L	7.50	EM84	0.40	WQV06-40A	5Z4G		0.70	6S17	0.70	30FL14	1.80
E88 CC/01		EM87	1.00		14.00	5Z4GT	0.75	6S17GT	0.50	30L15	1.00
	1.30	EY51	0.45	QV03-12	2.50	6AB7	0.60	6SK7	0.60	30L17	1.00
E180CC	1.30	EY81	0.45	SCI/400	4.00	6AC7	0.60	6SL7GT	0.75	30P12	1.00
E180E	8.00	EY86/87	0.55	SCI/600	4.00	6AH6	0.50	6S24	0.75	30PL1	1.00
E182CC	3.50	EY38	0.55	SP61	0.85	6AK5	0.55	6S07	0.75	30PL13	1.10
EA76	2.00	EX80	0.45	TT21	7.50	6AK8	0.40	6V6GT	0.80	30PL14	1.10
EABC80	0.50	EZ81	0.60	U25	1.00	6AL5	0.40	6X4	0.60	35L6GT	1.00
EB91	0.40	GY501	0.90	U26	0.85	6AL5W	0.85	6X5GT	0.55	35V4	0.80
ECC33	1.00	GZ32	0.65	U27	1.00	6AM5	1.60	6Y6G	0.95	35Z4GT	0.70
EBF80	0.50	GZ33	0.50	U191	0.75	6AM6	0.55	6Z4	0.65	50C5	0.70
EBF83	0.50	GZ34	2.00	U281	0.50	6AN8	0.85	6-30L2	0.90	50C6DG	1.20
EBF89	0.50	GZ37	2.50	U301	0.50	6A05	1.30	7B7	0.80	75	1.00
EC52	0.40	KT66	4.00	U801	0.80	6A05W	0.85	7V4	0.80	75C1	0.80
ECC81	0.55	KT88	5.75	UABC80	0.60	6AS6	0.80	9D2	0.60	76	0.80
ECC82	0.50	MH4	1.00	UAF42	0.75	6AT6	0.75	9D6	0.75	78	0.75
ECC83	1.15	ML6	1.00	UBF80	0.55	6AU8	0.40	10C2	0.80	80	0.75
ECC84	0.45	OA2	0.55	UBF89	0.50	6AV6	0.50	10F18	0.60	85A2	2.20
ECC85	0.50	OB2	0.60	UBL1	1.00	6AX4GT	0.80	10P13	0.60	723A/B	11.00
ECC86	1.25	PABC80	0.40	UBL21	0.75	6AX5GT	1.00	11E2	11.00	803	6.00
ECC88	0.60	PC85	0.50	UCC84	0.60	6B7	0.75	12A6	0.60	805	18.00
ECC189	0.80	PC86	0.85	UCC85	0.60	6BA6	0.40	12AT6	0.45	807	1.00
ECC90	0.50	PC88	0.75	UCF80	0.30	6BE6	0.50	12AT7	0.55	813	10.50
ECC92	0.45	PC90	1.25	UCH81	0.60	6BG6G	1.00	12AU7	0.50	829B	11.00
ECCF801	0.75	PC884	0.45	UCL82	0.75	6B16	1.10	12AV6	0.70	832A	4.50
ECH34	0.95	PC89	0.55	UF41	0.80	6BQ7A	0.80	12AX7	0.50	866A	2.80
ECH35	1.50	PCC189	0.85	UF80	0.45	6BR7	2.30	12BA6	0.50	931A	6.00
ECH42	0.85	PCF80	0.80	UF85	0.50	6BW6	2.80	12BC6	0.60	954	0.50
ECH81	0.40	PCF82	0.40	UL41	0.75	6BW7	1.00	12BE6	0.60	955	0.55
ECH84	0.95	PCF84	0.65	UL84	0.75	6C4	0.40	12C8	0.55	956	0.50
ECL80	0.60	PCF86	0.85	UM80	0.60	6C6	0.55	12E1	4.25	957	0.90
ECL82	0.55	PCF200	0.90	UM84	0.40	6CH6	3.00	12J5GT	0.40	1625	1.00
ECL83	1.20	PCF201	0.90	UY82	0.55	6CL6	0.75	12K7GT	0.60	1629	0.70
ECL85	0.65	PCF801	0.90	UY85	0.50	6CY5	0.90	12K8GT	0.70	2051	1.00
ECL86	0.55	PCF802	0.85	VR105/30	1.80	6D5	0.50	12Q7GT	0.50	5783	2.50
EF37A	1.85	PCF805	1.80			6EA8	0.80	12SC7	0.55	5842	6.50
EF39	2.90	PCF806	0.85			6F6GB	0.90	12SH7	0.70	5933	3.00
EF40	0.70	PCF808	1.80		1.25	6F8G	0.75	12S17	0.55	6057	0.85
EF41	0.75	PCG200	0.80	Z66	0.60	6F12	0.85	12S07	0.55	6080	0.85
EF80	0.40	PCL81	0.60	X61M	1.50	6F14	0.80	12Y4	0.40	6064	0.85
EF83	1.50	PCL82	0.65	Z800U	3.00	6F15	0.60	13D6	0.60	6065	1.20
EF85	0.45	PCL84	0.70	Z801U	3.50	6F17	1.00	14S7	1.00	6067	1.00
EF86	0.55	PCL86	0.70	Z900T	1.50	6F24	0.90	19A05	0.75	6080	3.50
EF91	0.65	PCL805/85		1A3	0.60	6F33	4.20	19G3	10.00	6146	3.80
EF92	0.75		0.75	1L4	0.30	6H6	0.95	19G6	6.00	6146B	4.20
EF95	0.55	PD500	3.25	1R5	0.55	6J4WA	1.75	19H5	17.00	6360	2.00
EF183	0.65	PFL200	1.35	1S4	0.40	6J5	0.75	20D1	0.60	8020	5.50
EF184	1.60	PL36	0.80	1S5	0.40	6J5GT	0.55	20F2	0.60		
EF804	2.00	PL81	0.75	1T4	0.40						
EFL200	0.75	PL82	0.50	1U4	0.60						
EH90	0.80	PL83	0.50	1X2B	1.10						
EL32	0.90	PL84	0.95	2D21	0.55						
EL34	2.20	PL504	1.40	2K25	11.00						
EL37	3.00	PL508	1.30	2X2	0.80						

POSTAGE: £1-£2 20p; £2-£3 30p; £3-£5 40p; £5-£10 60p; over £10 free.

VIDECON TUBE TYPE P863B
English Electric - £20

MARCONI SIGNAL GENERATORS

TF 2400/1 Frequency Converter up to 510MHz.
MODULATION METER 210A. 2.5-300MHz. AM 0-100% FMD+100KHz in 4 ranges. **AIRMEC**
VHF WAVE ANALYSER 248 Freq from 5MHz to 300MHz.

TF 801 D/1/S SIGNAL GENERATOR. Range 10-485MHz in 5 ranges. R.F. output 0.1V-1V. Source C.M. 500 output impedance. Internal modulation at 1KHz at up to 90%.

TF 995 A/1 or A/2 or A/2M or A5 SIGNAL GENERATORS. Very high class AM/FM 1.5MHz to 220MHz. Detailed spec. and price on application.

TF 995 S/S with additional amplifier to give extra high output between 1.5 and 5 Mc/s.

HIGH FREQUENCY SPECTRUM ANALYSER. MARCONI TYPE 1094A/S. Basic Freq. range 3 to 30 Mc/s and with LF unit from 100Hz to 3 MHz. Measures relative amplitudes up to 60dB.

TF1041 S VALVE MULTIMETER. DC voltage from 300mV to 1.000V. AC voltage from 300mV to 300V at up to 1.000MHz.

WHITE NOISE TEST SET. The instrument consists of two units: a Marconi Noise Generator Type TF 2091 and Noise Receiver Type TF 2092. Measures noise and intermodulation on wide band multichannel telephone systems. Suitable for 12 channel to 2,700 channel system.

MARCONI TF 867 SIGNAL GENERATOR
Range 15KHz to 30MHz. Output 0.4µV to 4V to 13 or 75 ohms. Impedance with termination (supplied). Built in crystal check facility with handbook. CT 478; CT 479; QT480 Signal Generators frequency from 1.3kMS up to 11kHz output up to 1mV CW and imp. mod.

LEVEL OSCILLATOR TYPE REL 3W29.
Frequency from 0.3 to 1200Kc/s. Mod. ext. output from +16dB to -60dB. Impedance output 75, 140, 600 ohms.

36' AERIAL MASTS consisting of 6 sections 6" 8" X 2 1/4" dia. Complete with all accessories to erect and instal.

RHODE & SCHWARZ
Z-g DIAGRAM TYPE 20U 30-420MHz-500. Model type ZDD. Frequency 300-2400MHz. Directly measures multiterminal networks, phase shift, phase angle with complementary POWER SIGNAL GENERATOR TYPE SMLM high freq. resolution, internal external mod. up to 3v out.

LOW RESISTANCE HEADPHONES TYPE CLB
£1.50. 40p postage. VAT 12 1/2 %.

VALVES AND TRANSISTORS
Telephone enquiries for valves, transistors, etc.; retail 749 3934; trade and export 743 0899.

OUR ANNUAL OF SALE TEST EQUIPMENT STARTS FEBRUARY 1st

OSCILLOSCOPES (NEW PRODUCTION)
SCOPEX 4S-6, 6MHz. Single Beam. 10mV sensitivity. Display — 6cm x 8cm. Weight: 4.5kg.
SCOPEX 4B-10A, 10MHz. Dual Trace. 10mV sensitivity. Display — 6cm x 8cm. Weight: 6kg.
DARTON D12, 15MHz. Dual Trace. 1mV sensitivity. Display — 8cm x 10cm. Weight: 7.8kg.

SIGNAL GENERATOR H.P. MODEL 680C. High power, stable and high accuracy. Frequency 10 to 480MHz. Modulation level 0 to 95% at carrier levels 0.5V output level continuously from 0.1µV into a 50 ohm. Maximum output 1V.

FOR EXPORT ONLY
Mulard C11. High power installation, 1000W. Technical details and prices available on request.

TEKTRONIX OSCILLOSCOPES
645A. Bandwidth DC to 30MHz.
570 CHARACTERISTIC CURVE TRACE
CABLE LAYING APPARATUS No. 11. New production P.O.A.
FURZEHILL SENSITIVE VALVE VOLTMETER
TYPE V200A full scale from 10mV to 1000V in 6 steps without amplifier.
EDDYSTONE COMMUNICATIONS RECEIVER
MODEL 730/1A 730/4. Frequency from 500kc/s to 28Mc/s.
HIGH VACUUM VARIABLE CAPACITORS — ceramic variables — UC 1000A/20/150=VMMHC 1000 60-1000µF, 20kv-150A RF max=27MHz.
TEST SET FT2 for testing Transceivers A40, A41, A42 and CPCR26.
UNIVERSAL WIRELESS TRAINING SET No 1 Mk 2 YA 8316 to train 32 operators simultaneously on key and phone. Complete installation consists of 3 kits packed in 3 special transit cases.
HARNESSES "A" & "B" CONTROL UNITS "A", "R", "31", "J2", "Microphones No 5, 6, 7 connectors, frames, carrier sets etc.

VAT FOR TEST EQUIPMENT PLEASE ADD 8%

COLOMOR (ELECTRONICS LTD.)
170 Goldhawk Rd., London W.12
Tel. 01-743 0899
Open Monday to Friday 9-12.30, 1.30-5.30 p.m.

The Polar capacity

Wingrove & Rogers have now expanded their operations to include four distinct divisions within the Company. Write or phone for further detailed information and samples.

Wingrove & Rogers Ltd.
Domville Road
Liverpool L13 4AT
Tel: 051-220 4641
Telex: Chacom Liverpool 627110 for Winrog



LAIN GREX SUPPLIES LTD

Climax House, Fallsbrook Rd., Streatham, London SW16 6ED

RST Tel: 01-677 2424 Telex: 946708 RST

SEMICONDUCTORS

AA119 0.16	AA230 0.27	AA313 0.42	AAZ13 0.18	AAZ15 0.34	AAZ17 0.27	AC107 0.60	AC125 0.20	AC126 0.20	AC127 0.20	AC128 0.20	AC141 0.25	AC141K 0.35	AC142 0.20	AC142K 0.30	AC176 0.20	AC187 0.20	AC188 0.20	AC189 0.20	AC191 0.85	AC192 0.85	AC193 0.85	AD149 0.70	AD161 0.45	AD162 0.45	AD166 0.45	AF114 0.35	AF115 0.35	AF116 0.35	AF117 0.35	AF139 0.40	AF186 1.20	AF239 0.75	AFZ11 2.75	AFZ12 2.75	AS226 0.40	AS227 0.40				
AS215 1.25	AS216 1.25	AS217 1.25	AS220 1.50	AS221 2.00	AU113 1.70*	AU110 1.70*	AV110 1.70*	BA145 0.13*	BA148 0.13*	BA155 0.10*	BA156 0.09	BA156 0.09	BA156 0.09	BAX13 0.06	BAX16 0.06	BC107 0.12*	BC108 0.12	BC109 0.12	BC113 0.12*	BC114 0.12*	BC115 0.12*	BC116 0.12*	BC118 0.10*	BC125 0.16*	BC126 0.20*	BC135 0.14*	BC136 0.15*	BC137 0.15*	BC147 0.08*	BC148 0.08*	BC149 0.08*	BC157 0.08*	BC158 0.08*	BC159 0.10*	BC167 0.11*	BC170 0.12*	BC171 0.10*			
BC172 0.10*	BC173 0.12*	BC177 0.15	BC178 0.14	BC179 0.16	BC182 0.11*	BC183 0.10*	BC184 0.11*	BC212 0.13*	BC213 0.12*	BC214 0.15*	BC237 0.09*	BC238 0.12*	BC301 0.25	BC303 0.24	BC308 0.10*	BC308 0.10*	BC327 0.20*	BC328 0.18*	BC337 0.18*	BC338 0.17*	BC340 1.00	BCY31 1.00	BCY32 1.00	BCY33 0.90	BCY34 0.90	BCY39 3.00	BCY40 1.00	BCY42 0.25	BCY43 0.25	BCY58 0.16	BCY70 0.17	BCY71 0.15	BCY72 0.15	BCZ11 1.50	BD115 0.45	BD121 1.20	BD123 1.20	BD124 1.30		
BD131 0.35	BD132 0.38	BD135 0.34*	BD136 0.34*	BD137 0.35*	BD138 0.40*	BD139 0.43*	BD144 2.00*	BD181 1.10	BD182 1.18	BD237 0.40	BD238 0.55	BDX10 0.91	BDX32 2.00	BDY20 1.25	BDY60 1.50	BF115 0.25	BF152 1.18	BF153 0.20	BF154 0.17	BF159 0.23	BF180 0.16	BF182 0.20	BF173 0.20	BF177 0.24	BF178 0.24	BF179 0.25	BF180 0.30	BF181 1.00	BF182 0.30	BF183 0.25	BF184 0.25	BF185 0.25	BF194 0.09*	BF195 0.09*	BF196 0.10*	BF197 0.12*	BF200 0.27	BF224 0.20*	BF244 0.28*	
BF257 0.24	BF258 0.26	BF259 0.32	BF336 0.30*	BF337 0.30*	BF338 0.31*	BFS21 3.06	BFS28 2.23	BFS29 2.23	BFS30 2.23	BFS31 2.23	BFS32 2.23	BFS33 2.23	BFS34 2.23	BFS35 2.23	BFS36 2.23	BFS37 2.23	BFS38 2.23	BFS39 2.23	BFS40 2.23	BFS41 2.23	BFS42 2.23	BFS43 2.23	BFS44 2.23	BFS45 2.23	BFS46 2.23	BFS47 2.23	BFS48 2.23	BFS49 2.23	BFS50 2.23	BFS51 2.23	BFS52 2.23	BFS53 2.23	BFS54 2.23	BFS55 2.23	BFS56 2.23	BFS57 2.23	BFS58 2.23	BFS59 2.23	BFS60 2.23	
CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90	CRS3/60 0.90

VALVES

A1834 9.00	A2084 11.81	A2137 8.75	A2426 11.19	A2521 10.11	A2900 7.50	A3343 22.23	AZ14 1.15*	BK448 62.70	BS90 84.75	BTS10 27.75	BS15 34.50	BT17 61.85	BT19 21.15	BT29 188.90	BT69 183.25	BT75 79.65	BT86 74.35	CB131 1.50*	CL33 2.00*	CY31 1.00*	CIK 10.00	C3A 10.00	DA16 20.20	DA41 18.70	DA42 10.70	DA100 46.00	DAF91 0.40*	DAF96 1.00*	DET22 21.00	DET24 46.00	DF91 4.00*	DF96 1.00*	DK91 1.05*	DK92 1.25*	DK93 1.00*	DL92 0.75*	DL94 1.20*	DL96 1.10*	DL510 8.25	DL515 10.76	DL516 10.76	DL519 10.76	DM70 10.76	DM71 1.50	DM76/7 0.55*	DY802 0.80*	E5L 21.89	E800C 5.00	E800F 7.20	E801 6.32	E802 5.33	E811 6.12	E822C 6.20	E833C 6.23	E838 5.43	E841 1.20	E842 2.00	E843 1.00	E844 5.16	E845 4.65	E846 4.96	E847 0.50*	E848 0.50*	E849 0.50*	E999 0.50*	E1000 0.50*
------------	-------------	------------	-------------	-------------	------------	-------------	------------	-------------	------------	-------------	------------	------------	------------	-------------	-------------	------------	------------	-------------	------------	------------	-----------	-----------	------------	------------	------------	-------------	-------------	-------------	-------------	-------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	-------------	-------------	-------------	------------	-----------	--------------	-------------	-----------	------------	------------	-----------	-----------	-----------	------------	------------	-----------	-----------	-----------	-----------	-----------	-----------	-----------	------------	------------	------------	------------	-------------

BASES

B7G unskirted 0.15	B7G skirted 0.30	B9A unskirted 0.30	B9A skirted 0.30	Int Octal 0.20	Local 0.55	Nuvistor base 0.55	8 pin DIL 0.15	14 pin DIL 0.17	16 pin DIL 0.17	Valve screening cans all sizes 0.30																																											
2API* 8.50	5ADPI 35.00	5BP1* 10.00	5CPI* 5.00	5CPIA 40.00	5DPI 7.00	5DPIA 15.00	5DPIB 15.00	5DPIC 25.00	5DPIE 36.00	5DPIF 36.00	5DPIG 36.00	5DPIH 36.00	5DPII 36.00	5DPIJ 36.00	5DPIK 36.00	5DPL 36.00	5DPM 36.00	5DPN 36.00	5DPO 36.00	5DPP 36.00	5DPT 36.00	5DPU 36.00	5DQ 36.00	5DR 36.00	5DS 36.00	5DT 36.00	5DU 36.00	5DV 36.00	5DW 36.00	5DX 36.00	5DY 36.00	5DZ 36.00	5E 36.00	5F 36.00	5G 36.00	5H 36.00	5I 36.00	5J 36.00	5K 36.00	5L 36.00	5M 36.00	5N 36.00	5P 36.00	5Q 36.00	5R 36.00	5S 36.00	5T 36.00	5U 36.00	5V 36.00	5W 36.00	5X 36.00	5Y 36.00	5Z 36.00

CRTS

5ADPI 35.00	5BP1* 10.00	5CPI* 5.00	5CPIA 40.00	5DPI 7.00	5DPIA 15.00	5DPIB 15.00	5DPIC 25.00	5DPIE 36.00	5DPIF 36.00	5DPIG 36.00	5DPIH 36.00	5DPII 36.00	5DPIJ 36.00	5DPIK 36.00	5DPL 36.00	5DPM 36.00	5DPN 36.00	5DPO 36.00	5DPP 36.00	5DPT 36.00	5DPU 36.00	5DQ 36.00	5DR 36.00	5DS 36.00	5DT 36.00	5DU 36.00	5DV 36.00	5DW 36.00	5DX 36.00	5DY 36.00	5DZ 36.00	5E 36.00	5F 36.00	5G 36.00	5H 36.00	5I 36.00	5J 36.00	5K 36.00	5L 36.00	5M 36.00	5N 36.00	5P 36.00	5Q 36.00	5R 36.00	5S 36.00	5T 36.00	5U 36.00	5V 36.00	5W 36.00	5X 36.00	5Y 36.00	5Z 36.00
-------------	-------------	------------	-------------	-----------	-------------	-------------	-------------	-------------	-------------	-------------	-------------	-------------	-------------	-------------	------------	------------	------------	------------	------------	------------	------------	-----------	-----------	-----------	-----------	-----------	-----------	-----------	-----------	-----------	-----------	----------	----------	----------	----------	----------	----------	----------	----------	----------	----------	----------	----------	----------	----------	----------	----------	----------	----------	----------	----------	----------

INTEGRATED CIRCUITS

7400 0.16	7401 0.16	7402 0.16	7403 0.16	7404 0.16	7405 0.16	7406 0.16	7407 0.16	7408 0.20	7409 0.20	7410 0.16	7411 0.16	7412 0.26	7413 0.26	7414 0.26	7415 0.26	7416 0.26	7417 0.26	7418 0.26	7419 0.26	7420 0.17	7421 0.17	7422 0.17	7423 0.32	7424 0.32	7425 0.32	7499 0.32	7500 0.32
-----------	-----------	-----------	-----------	-----------

Terms of business: CWO. Postage and packing valves and semiconductors 25p per order. CRTs 75p. Items marked * add 12 1/2% VAT. Others 8%. P & P at 8%.

† Indicates cheap quality version or surplus, but also available by leading UK and USA manufacturers. Price ruling at time of despatch.

Account facilities available to approved companies with minimum order charge £10. Carriage and packing £1 on credit orders.

Over 10,000 types of valves, tubes and semiconductors in stock. Quotations for any types not listed. S.A.E.

Telephone 01-677 2424/7
Telex 946708
E & O.

Appointments

Advertisements accepted up to 12 noon Friday, February 23 for April issue, subject to space being available.

DISPLAYED APPOINTMENTS VACANT: £8.50 per single col. centimetre (min. 3cm)
LINE advertisements (run on): £1.20 per line, minimum three lines.
BOX NUMBERS: 60p extra. (Replies should be addressed to the Box Number in the advertisement, c/o Wireless World, Dorset House, Stamford Street, London SE1 9LU.)
PHONE: Barry Leary on 01-261 8508
Classified Advertisement Rates are currently zero rated for the purpose of V.A.T.

It's the nearest nature could have got to our Adaptive Antennas



If nature had the research and development facilities that STL take for granted, the Bat would have adaptive antennas, as well as a precise navigation system.

The one thing we don't take for granted are our R & D people. Because when you're working on projects like satellite navigation systems, adaptive microwave antennas and novel radar concepts the future's very much in your hands.

And that means you. High-calibre graduate and post-grad men and women with R & D experience in any of the following: radar system design and modelling; antenna systems, particularly arrays; VHF-UHF receiver circuits; high-speed digital circuit design; signal processing for radar and spread spectrum signals; microprocessor integration with radio and radar systems.

As ITT's principal European Research Centre, we can naturally offer you excellent salaries and benefits

together with generous relocation expenses to this essentially rural area on the Herts/Essex border.

If you're ready for the future now, please send the coupon or contact Vaughan Hartridge, Personnel Department, Standard Telecommunication Laboratories Ltd., London Road, Harlow, Essex CM17 9NA, or telephone him on: Harlow 29531 ext. 361.

Please send an application form to: 146/78 WW1/79


Name _____

Address _____

Where the future's happening now **STL**

(8985)

Professional Careers in Electronics

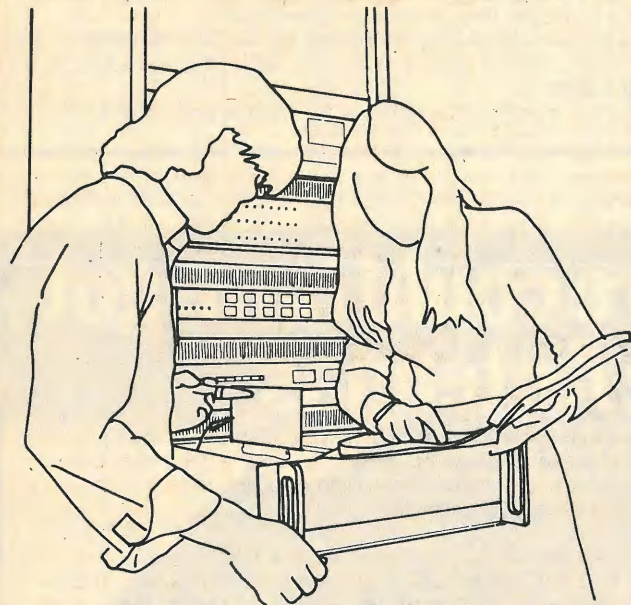

All the others are measured by us...

At Marconi Instruments we ensure that the very best of innovative design is used on our range of communications test instruments and A.T.E. We have a number of interesting opportunities in our Design, Production and Service Departments and we can offer attractive salaries, productivity bonus, pension and sick pay schemes together with help over relocation. If you are interested to hear more, please fill in the following details:-

Name _____ Age _____

Address _____

Telephone Work/Home (if convenient) _____

Years of experience 0-1 1-3 3-6 Over 6

Present salary £2,500- £3,500- £4,500- over
 3,500 4,500 5,500 £5,500

Qualifications None C & G HNC Degree

Present job _____

Return this coupon to John Prodger, Marconi Instruments Limited, FREEPOST, St. Albans, Herts, AL4 0BR. Tel: St Albans 59292

**Marconi
Instruments**

A GEC MARCONI ELECTRONICS COMPANY

(9002)

OFFSHORE OPPORTUNITIES

COMMUNICATION ENGINEERS £8,500 + p.a. Repair and Maintenance of VHF, UHF, Troposcatter and Multiplex equipment. HNC qualification or Forces experience (Foreman of Signals) preferred and experience essential. Engineers work 2 weeks on/offshore schedule.

COMMUNICATION TECHNICIANS £7,000 p.a. ONC or City & Guilds Communications with 2 years practical experience.

ELECTRONIC ENGINEERS c. £8/9,000 p.a. Experienced on following equipment: CCTV Systems, Process Instrumentation, Acoustic Equipment, Micro-processors. HNC or BSc qualification preferred.

ELECTRONIC TECHNICIANS c. £7,000 p.a. + Technicians with some computer, digital and analogue instrumentation experience. Aberdeen based with periodic offshore work. Relocation assistance will be given.

COMPUTER ENGINEER/PROGRAMMER c. £8,000 p.a.

Qualified to BSc. or HNC level with indepth experience of computer and peripheral equipment. Reasonable knowledge of programming in Cobol/Fortran languages.

ELECTRONIC/INSTRUMENT TECHNICIANS c. £8,000 p.a.

To work offshore on 2 week on/off schedule. Petrochemical or heavy industrial experience required.

For further information and application forms please contact Margaret Duthie.

GTS

Gramplan Technical Services Ltd.

27 York Place, Aberdeen. Tel: (0224) 28921

Licence No. SC 14

MAINTENANCE TECHNICIAN

Experience in audio/visual electronic installation and a knowledge of light engineering/fabrication techniques would be an advantage.

You should have at least seven years' experience and be qualified to ONC level.

Salary within the scale £3,675-£4,212.

Application form from the Staffing Officer, Polytechnic of the South Bank, Borough Road, London SE1 0AA. (01-928 8989) quoting ref. ETS5.

Polytechnic
of the
South Bank

(8972)

Keeping in touch...


We are Europe's leading exporters of two way radio communications systems and as such can offer you the chance to work on exciting new development projects in some of the best equipped laboratories in the country.

Join us in Cambridge and you will be benefiting from a plan of growth and development that has seen £7 million recently invested in a new laboratory, production and headquarters complex on the banks of the Cam.

Electronic Development Engineers (RF or Digital)

RF Engineers to join teams working on the development of fixed, portable and link products or sub-units. Must have radio communications development experience and be familiar with design of VHF/UHF communications equipment or low medium

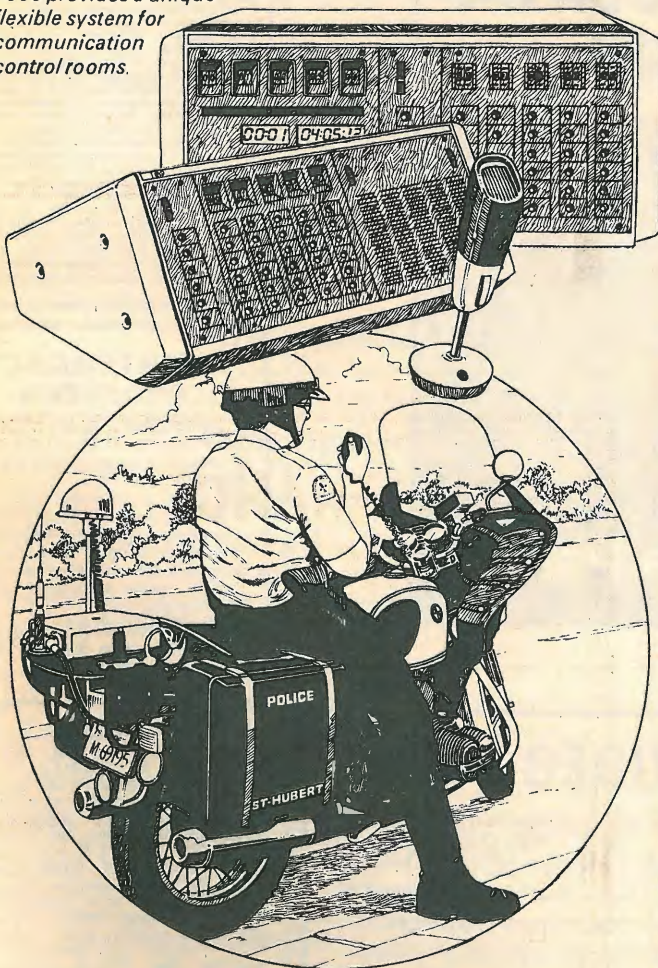The most advanced control system in the world, the Pye MASCOT 1000 provides a unique flexible system for communication control rooms.



capacity multiplex radio links. We also require engineers with hand portable development experience.

Digital engineers to work on computer-based interactive systems including digital signalling, encoders/decoders, speech synthesis and data display. Must have experience of either machine code and assembler language programming or the design of digital and analogue circuits. We're looking for men and women qualified to B.Sc. or HND level, with at least 2 years' experience.

Systems Development Engineer

To evaluate technical feasibility of new enquiries and to propose cost-effective engineering solutions. This entails provision of technical documentation and liaison with production, installation and field service departments.

Applicants should be qualified to Degree, HND or HNC level and have experience of Systems Engineering, Commissioning, Design/Development or Field Work. Knowledge of two or more of the following is essential: HF/VHF/UHF equipment; data and line transmission; control; logic and processors; telegraphy, line printers or exchange practice.

Electronic Designers

To make a major contribution to a project team developing low capacity FDM/PCM radio links. Applicants should hold a degree/HND or equivalent qualification in Electronics and have had at least 10 years' relevant design experience.

Mechanical Designers

To participate in the total design of new products. You should have acquired experience of product design for medium to large quantity production runs, and have extensive knowledge of design in sheet-metal, plastics and diecast metal. An HNC or equivalent qualification is desirable.

PCB Draughtsmen

To join small teams of product engineers. You should have sound knowledge of the latest PCB design layout techniques and high quantity PCB production methods. Experience of computer aided design and precision plotting is a major asset. A relevant ONC or equivalent qualification is preferred.

We're offering good salaries to applicants of either sex with generous relocation expenses and good career prospects plus an extremely attractive working environment, including sports ground, pavilion and social facilities within the complex. Living in Cambridge has its own benefits too, not only is it an attractive city, but it offers excellent sporting, recreational and cultural facilities and a wide choice of reasonably priced housing. Added to which, London is quite close to hand, with the new M11 opening in Autumn and a rail journey soon to be brought down to under 1 hour. So, apply now quoting job title to Alan Depauw, Personnel Officer, Pye Telecommunications Ltd., St. Andrews Road, Cambridge, CB4 1DW. Telephone Cambridge 61222 Ext. 305.



Pye Telecommunications Ltd

St Andrews Road, Cambridge, England, CB4 1DW
Tel: Cambridge (0223) 61222 Telex: 81166 PYE TEL COM CAMB

If you've seen our distinctive product advertising in the national press, you'll be aware of our new range of Direct Entry computer controlled typesetting systems that are making such an impact on the printing and publishing industry worldwide. Isn't that the kind of field you should be working in — a new technology that is really going places?

Naturally we're looking for rather special field service engineers and to join us you have to be the type of man or woman who can think logically, look for the unexpected, and can diagnose and repair faults single handed — even when you're miles from base.

And because you'll have a lot of customer contact, often at high level, you'll have to be

diplomatic and tactful. Technically, you should be qualified to ONC or HNC level and have had several years relevant field experience. A knowledge of optical physics and a general mechanical aptitude would also be useful. You can expect to travel widely initially about 2 days per week. We're offering up to £5000, a Cortina 1600 Estate, generous expenses and benefits. And with our policy of continual development bringing new equipment onto the market every year, your prospects could not be better.

So, don't you think it's time you responded to this challenge? If you do, contact David Hilton, Personnel Manager, Linotype-Paul Ltd., Kingsbury Road, London NW9 8UT.

ISN'T IT TIME YOUR SERVICE ENGINEERING SKILLS TOOK ON A NEW CHALLENGE?



QUEEN MARY COLLEGE (University of London)

TECHNICIAN (Grade 5)

required to join the Molecular Astronomy Group in the Physics Department at Queen Mary College. The post is tenable to the 31st December, 1981 and the successful applicant will be expected to assist in the development, construction and testing of Electronic/Optical systems and equipment, including Microwave Components. He will assist the group in preparing and carrying out observing campaigns at observatories in both Northern and Southern Hemispheres. HNC equivalent qualification is desirable, but more important is practical ability in Electronics and General Workshop practice. Salary scale £3,186 to £3,394 per annum (under review), plus £465 per annum London Weighting, 5 day week, 4 weeks' annual leave, plus a week at Christmas and Easter, which includes the public holidays. Further information may be obtained from Mr. D. A. Young, telephone 980 4811, ext. 349. (8973)

AUDIO + VIDEO LTD.

We are acknowledged as being the largest video tape duplicators in Europe with 5 Quad machines, 3 colour T/Cs, our own digital Standards Converter and countless duplication machines of all standards, providing unsurpassed quality. We are obviously looking for Engineers to match and will pay up to £7,000 for the right persons. If you have the desired experience contact Cliff Carroll on 01-580 7161. (8993)

THE ROYAL FREE HOSPITAL HAMPSTEAD

Medical Physics Technicians (Electronics) Grades III and IV

Two electronics technicians are required for the Electronics Workshop of this major teaching hospital to assist with the development and maintenance of electronic circuits and equipment.

Applicants (male or female) for the Grade III post should hold the City and Guilds Full Technological Certificate in appropriate subjects or an equivalent qualification and have good practical experience in the design of electronic circuits using state-of-the-art techniques.

Similar qualifications are required for the Grade IV post. A working knowledge of analogue and digital circuit techniques and an ability to service electronic equipment would be an advantage.

Salaries for these posts are on scales: £4,098-£5,142 p.a. (Grade III) and £3,432-£4,488 p.a. (Grade IV), including all allowances. The Grade and starting salary will depend on qualifications and experience.

Application forms (to be returned by 15th March, 1979) and Job Description available from the Personnel Department, The Royal Free Hospital, Pond Street, Hampstead, London NW3 2QG. Tel. 01-794 0500 Ext. 4286. Please quote ref. Grade III 0758 and Grade IV 0761.

Camden and Islington Area Health Authority. (T). (8929)

UNIVERSITY OF WARWICK ELECTRONICS TECHNICIAN

Applications are invited for the post of Electronics Technician Grade 7 in the Department of Chemistry and Molecular Sciences to take charge of a well-equipped electronics workshop. The duties include responsibility for maintenance of both electrical and electronic equipment in the Department, design and construction of specialised electronic equipment, modifications to existing equipment, and the supervision of a Grade 4 Technician employed primarily on repair and maintenance work. The Department is equipped with a wide range of scientific instrumentation including mass spectrometers, magnetic resonance instruments, spectrophotometers and chromatographic equipment, and the successful candidate (male/female) will probably hold an HNC or equivalent in the field of electronics and have wide experience in the design and maintenance of complex electronic equipment. The University is situated in pleasant rural surroundings within easy commuting distance of Coventry, Kenilworth and Leamington Spa. Starting salary is on an incremental scale £4,254-£4,782 p.a. (under review with effect from 1 October, 1978) and will depend on experience and qualifications. Applications giving full details including the names of two referees should be sent to the Personnel Office, University of Warwick, Coventry, CV4 7AL as soon as possible. Please quote reference number 22/20/78. (8935)

MAINTENANCE ENGINEER

A Maintenance Engineer is required for the repair and testing of a range of professional audio and lighting control equipment.

Applicants should have sound knowledge of modern analogue and digital techniques and, ideally, possess a current driving licence. Salary will be negotiable around £4,000 p.a.

Apply with full details of qualifications to Box No. 8956 (London area). (8956)

CHIEF TECHNICIAN (Grade 7) required in School of Education, University of Reading, to head team of 4 technicians providing service for teaching and research. Facilities include general labs., photographic lab., language lab., TV studio and A/V aids lab. and other specialised workrooms and labs. HNC or equivalent qualification desirable with substantial appropriate experience. Salary in scale £4254-4782 p.a. (under review). Apply for further details, quoting Ref. TW07A, to Assistant Bursar (Personnel), University of Reading, Whiteknights, Reading, Berks, RG6 2AH. (8940)

RADIO TELEPHONE SERVICE ENGINEER required in Croydon. Proven ability to repair equipment more important than formal qualifications. Salary commiserate with ability. Contact LONDON CAR TELEPHONES on 01-680 1010. (8822)



Technician Engineers

The Plessey Development Laboratory at Havant, Hampshire, is sub-contractor for the most advanced VHF communications system ever to be developed for the British Army. This system – known as “Single Channel Radio Access” – allows mobile subscribers to use the Ptarmigan trunk telephone network for both voice and data messages.

We are now proceeding with the second phase of development, creating new career opportunities for Technician Engineers who wish to advance their knowledge.

What jobs are on offer?

We are looking for Technician Engineers with experience in industry or H.M. Services to work in the following fields.

VHF Radio Equipment Development and Evaluation

Successful candidates will be involved in the development of transmitters and receivers and in the evaluation of their electrical and environmental performance under a variety of conditions.

Development and Evaluation of Digital Equipment

Candidates with a special interest in digital circuits and systems will find opportunities to work under the guidance of experienced senior engineers on the most up-to-date techniques, including microprocessors.

What qualifications?

The type of work we do needs people with practical experience of transistorised equipment, a common sense approach and a willingness to work with others towards a common goal. Ideally, you will possess a City & Guilds Full Tech. Cert., ONC or HNC.

Salaries and career prospects?

We operate a separate structure for Technician Engineers which offers scope for career development. You could become a Principal Technician Engineer in charge of a small section, while the exceptional younger person would be encouraged to qualify to transfer into the Professional Engineering grades. Because our plans for business expansion are soundly based on a full order book for a wide range of both government sponsored and private venture products, we can offer you both job stability and the up-to-date experience which is essential to our future growth.

Technician Engineers are recognised as important members of our teams and are rewarded accordingly. Situated in a semi-rural environment near Portsmouth, Chichester, the South Downs and several seaside resorts, we are well placed for housing, educational and recreational amenities. Generous relocation assistance will be given as appropriate and there is a comprehensive range of large company benefits.

Please write with brief career details or telephone for an application form. L. Wise, Recruitment Manager, The Plessey Company Limited, Martin Road, West Leigh, Havant, Hants. Tel: (0705) 486391. Applications are invited from either sex.

 **PLESSEY**

Electronics Engineers on the move

WALLINGTON, SURREY**REF. WW95**

AUDIO TAPE ENGINEER

For design and development of magnetic tape copying machines, tape play-back machines. Experienced H.N.C. level.

Attractive salary offered

BERKSHIRE**REF. WW96**

DIGITAL/LOGIC DESIGNERS

Self-motivating engineers experienced in MSI and LSI techniques required by R&D group of a major British defence contractor engaged in development of new equipment.

Salaries up to £7,000 p.a.

Capital Appointments Ltd. 29/30, Windmill St. London, W.1. ☎ 01-637 5551

30 MILES S.W. OF LONDON**REF. WW97**

POWER CONVERSION SPECIALIST

Engineer experienced in design of static invertors and power supplies (in a range up to 1KVA) to lead a team developing equipment for military applications.

Salary negotiable up to £7,000 p.a.

ENFIELD**REF. WW98**

CIRCUIT DESIGN ENGINEER

An electronics company seeks a young circuit design engineer to join the existing small dynamic development team. Good prospects. Formal qualifications preferred.

Salary c. £5,000 p.a. initially

Capital Appointments Ltd. 29/30, Windmill St. London, W.1. ☎ 01-637 5551

WATFORD**REF. WW99**

STANDARDS/SPECIFICATION ENGINEER

An interesting opening for a mature engineer with previous design experience to join a dynamic team working on sophisticated medical equipment using latest state of art devices including microprocessors.

Salary c. £7,500 p.a.

ALL UK AREAS**REF. WW100**

SALES ENGINEERS

Are urgently required for client companies selling electronic components, computers and peripherals communications, industrial control equipment and scientific instruments.

Salaries to £10,000 p.a.

Capital Appointments Ltd. 29/30, Windmill St. London, W.1. ☎ 01-637 5551

REF. WW101

PERSONNEL MANAGERS COULD YOU USE THIS SPACE? TELEPHONE BRIAN CORNWELL FOR DETAILS

ILFORD**REF. WW102**

TEST ENGINEERS

Technician engineers to test and trouble shoot mod transmitter, receivers. Minimum 4 years' experience. H.N.C. Electronic Engineering or C.&G. Full Tech. Cert. preferred.

Salary to £4,950 p.a.

Capital Appointments Ltd. 29/30, Windmill St. London, W.1. ☎ 01-637 5551

ENFIELD**REF. WW103**

TEST EQUIPMENT ENGINEERS

We need your skills! A new department has been formed to design test gear and ATE for in house use. Several appointments will be made.

Salary £5,000-£7,000 p.a.

SOUTH-EAST LONDON**REF. WW104**

PROJECT ENGINEER

Design and development of special purpose machines. Experience of AC and DC rotating machines and the associated electronic control equipment.

Salary to £6,000 p.a.

Capital Appointments Ltd. 29/30, Windmill St. London, W.1. ☎ 01-637 5551

OVERSEAS**REF. WW105**

TECHNICAL REPRESENTATIVE

Well-qualified engineer to represent major communications company throughout Middle East. Good knowledge of UHF/VHF equipment essential.

Salary negotiable

SOUTH COAST**REF. WW106**

SYSTEM DESIGN ENGINEER

To be responsible for the analysis and design of avionic systems including software design and customer acceptance.

Salary range £4-6,000 p.a.

Capital Appointments Ltd. 29/30, Windmill St. London, W.1. ☎ 01-637 5551

Electronics Engineers on the move

DESIGN, TEST, Q.A: FIELD SERVICE, SALES, MANAGEMENT, ETC.

**INVEST
5 MINUTES
IN YOUR
FUTURE**

Improve your chances of obtaining the best Electronics job available by registering with us NOW. We are recruiting for over 3,000 Companies throughout the U.K. whose products range from computers to communications. Salary levels for experienced Engineers are highly competitive. The specific jobs advertised on the facing page are all urgent positions to be filled. Phone us if you wish to discuss any specific vacancies.

By returning the application form below, your job requirements will be matched against our clients' numerous vacancies, many of which are not advertised. Your application will be treated in strict confidence and no approaches will be made to existing employers or to any other companies you care to specify. Please remember, our service is completely FREE to applicants. If you wish to discuss any aspect of the Electronics job market, you are welcome to phone any time. Please ask for Brian Cornwell.

Capital Appointments Ltd. 29/30, Windmill St. London, W.1. ☎ 01-637 5551

PLEASE WRITE IN BLACK INK.

NAME: _____ ADDRESS: _____

Tel: (Home): _____ (Office): _____

Date of Birth: _____ Place of Birth: _____ Nationality now: _____ If not British, is a Work Permit req'd? _____

Marital Status: _____ Car Driver: _____ Car Owner: _____

Type of Position required: _____ Approx. Salary level: _____

Please indicate areas in which you are prepared to work:				Are you a houseowner?	Are you willing to relocate?
Cent. London	S. Coast	E. Midlands		Are you prepared to travel — In U.K?	Overseas?
S.E. London	West Country	W. Midlands		State of health:	
S.W. London	N.W. Engl.	E. Anglia		Notice Period required:	
N.E. London	N.W. Engl.	Wales		Availability for Interview:	
N.W. London	Scotland	Overseas			
Home Counties: N.W.		N.E.	S.W.	S.E.	

EDUCATION:

Secondary School Qualifications:

College or University Qualns:

Any Professional Membership:

INDUSTRIAL EXPERIENCE:		Products	Job Title	Responsibilities	Reason for leaving	Final Salary
Period of Employment	Company & Location					

ELECTRONICS PROFILE: Indicate extent of experience— A—Extensive; B—Moderate; C—Limited; If Nil experience, leave blank.

<input type="checkbox"/> Telephone Eqpt.	<input type="checkbox"/> Data Commns.	<input type="checkbox"/> Radio/Hi-Fi/T.V.	<input type="checkbox"/> Broadcast Eqpt.
<input type="checkbox"/> Digital/Logic	<input type="checkbox"/> Analogue Eqpt.	<input type="checkbox"/> Software/Programming	<input type="checkbox"/> Minis/Microprocessors
<input type="checkbox"/> Computers/Periphs.	<input type="checkbox"/> Test Gear/ATE.	<input type="checkbox"/> Process Control	<input type="checkbox"/> Power Supplies
<input type="checkbox"/> UHF/VHF. Comms.	<input type="checkbox"/> Microwave	<input type="checkbox"/> Radar/Nav aids.	<input type="checkbox"/> Medical Electronics
<input type="checkbox"/> Signalling Systems	<input type="checkbox"/> Security Eqpt.	<input type="checkbox"/> Avionics	<input type="checkbox"/> Simulators
<input type="checkbox"/> Weapons	<input type="checkbox"/> Scientific Eqpt.	<input type="checkbox"/> Data Recorders	<input type="checkbox"/> Photocopiers
<input type="checkbox"/> Phototypesetting	<input type="checkbox"/> Servo-mechs.	<input type="checkbox"/> Components-Active	<input type="checkbox"/> Components—Passive
<input type="checkbox"/> Product Eng.	<input type="checkbox"/> Electrical Eng.		

Others — Please state.

Please indicate any Companies you do not wish us to contact.

Ref. Nos. of specific vacancies in which you are interested:

If you wish to detail further aspects of your experience or job requirements, please enclose on a separate sheet.

SENIOR RADIO TECHNICIANS

Starting Salary £8,500 - £10,800 pa tax free

Saudia, flag carrier of the Kingdom of Saudi Arabia requires Senior Radio Technicians for its Communication Division based in Jeddah and Riyadh. Duties will include general maintenance and repair of ground radio equipment as well as the upkeep of technical manuals, service records and spare part logs. Some travel will be involved visiting various locations served by the Airline within Saudi Arabia.

Applicants should have had at least 3 years recognised technical training and 5 years related experience. City and Guilds certificate or equivalent would be an advantage. Current driving licence is essential.

Commencing point on the salary scale related to qualifications and experience. These posts which are open to men aged between 25-45, are offered on a two-year renewable contract together with free accommodation, free and reduced rate air tickets for you and your family, 40 calendar days vacation per annum plus relocation allowance.

Please write with full personal and career details quoting job title and department number to:-

**Area Personnel Manager - Europe,
Saudi Arabian Airlines,
Department 153/1,
508/510 Chiswick High Road,
London W4 5SQ.**

Closing Date: February 28th, 1979.



APPOINTMENTS IN ELECTRONICS £5 - £10,000

Take your pick of the permanent posts in:

- MISSILES — MEDICAL COMPUTERS
- RADAR — COMMS MICROPROCESSOR
- HARDWARE — SOFTWARE

For free expert advice and immediate action on salary and career improvement, phone or write to, Mike Gernat BSc.

Technomark
Electronics and Computer Recruitment

11 Westbourne Grove
London W2. 01-229 9239

ELECTRONICS TECHNICIAN (Grade 5) required in Department of Psychology, University of Reading, to take charge of the electronic workshop. The work involves both design and construction, and advice to staff and students on electronic problems, with considerable freedom of choice in methods used. The departmental programme already depends heavily on advanced analogue and digital techniques. Minimum qualifications would be a recognised membership; at least 7 years varied experience desirable. Salary in scale £3186-£3720 p.a. (under review). Apply with full details and names of 2 referees, quoting Ref. T06A, to Assistant Bursar (Personnel), University of Reading, Whiteknights, Reading, Berks, RG6 2AH. (8939)

CAPITAL APPTS.

FREE LISTS

101 Design/Development and Test Jobs
Permanent and Contract
To £6,000

(8782)

29 Windmill St.

London, W.1.
637 5551 day, 636 9659 eve.

SEISMIC ENGINEERS

We are looking for two young electronics engineers with degree or equivalent qualifications, to join our marine seismic acquisition company.

This is a field position, with the successful applicants joining the technical crew of our exploration vessel M/V GOEL EGEDE for on-board training in seismic techniques. They will start as Assistant Technicians with a salary of £6,000+ per annum, and one month's leave after each two months on the crew.

The seismic industry offers an interesting career with world-wide travel, and rapid promotion for the right person.

Geophysical Offshore Exploration is a member of the Sefel Group, which has seismic processing centres in Houston, Denver, Calgary and London.

Please write with full curriculum vitae to:



General Manager
Geophysical Offshore Exploration
Turriff Building
Great West Road
Brentford
Middlesex TW8 9HY

(9008)

ELECTRONIC SERVICE ENGINEERS

LONDON - BRISTOL - MANCHESTER - GLASGOW

Our Company specialises in both sales and servicing of Discotheque Sound and Lighting Equipment.

We are the UK's leading Company in this specialised field and due to continued expansion, we have vacancies in London, Bristol, Manchester and Glasgow.

Applications are invited from Electronic Service Engineers who have had at least 5 years' experience working with either Hi-Fi, Studio, PA or similar equipment.

We offer excellent salaries (depending on age and experience) generous staff discount scheme, a bonus paid 4 times per year, plus the opportunity to progress with a young, go-ahead company.

In the first instance, ring or write to: Mrs. L. Cooper, Personnel Officer for further details. (Reverse charges if you wish).

Roger Squire's Barnet Trading Estate,
Park Road, Barnet,
Herts. EN5 5SA.
Telephone: 01-441 1919

SERVICE SPECIALIST

Kontron Intertechnique
are looking for a
PRODUCT SPECIALIST

for their range of computer based instruments. The position involves field service in Laboratories mainly in the South of England. Knowledge of state-of-the-art digital systems is required.

This is a very demanding job but the company is prepared to reward a successful engineer with attractive remuneration and work satisfaction.

Apply to:

John Clapham
(Technical Director)
Kontron Intertechnique
P.O. Box 88
St. Albans
Herts.
AL1 5JG

(9010)

MARINE ELECTRONICS

We need an engineer familiar with Radar, MF/HF synthesised SSB/VHF Autopilots, etc. to service and install anywhere, but must be based in London.

If you are able to be your own boss apply giving details of experience salary required.

We are also prepared to offer an engineering partnership arrangement, if you are the right man.

TELESONIC MARINE LTD.
243 Euston Road
London N.W.1.

(8959)

DEVELOPMENT ENGINEERS

WHO ARE ALL AT SEA.
Radar or Transmitter Design

Marconi Communication Systems Ltd., is amongst the world leaders in the design, development and manufacture of a wide range of advanced communication systems for industrial and commercial use.

Right now we are currently working on several exciting projects concerning communication and radar equipment for the Merchant Navy.

As a result we now need to recruit additional engineers (men/women) who will be immediately involved in the design and development phase with the extended responsibility of overseeing the designs through to production.

If you have a degree or equivalent coupled with practical experience of communications or radar displays and techniques, then we would like to talk to you about a position at our headquarters in Chelmsford.

The prospects for the future are bright and in addition to an attractive negotiable salary, we offer good conditions and benefits including removal expenses in appropriate cases.

Why not find out more by telephoning Gordon Short on Chelmsford (0245) 53221 or write to him at Marconi Communication Systems Ltd., New Street, Chelmsford, Essex, for an application form.

A GEC-Marconi Electronics Company



(8946)

The pass card to 3000 potential employers

Here is a unique and efficient way of placing your name and abilities before many potential employers without leaving your armchair.

It won't involve you in inconvenient meetings or undercover 'phone calls. You won't be pestered by us. You won't be asked for any money.

Over 3,000 good employers, of all sizes in all industries, send us details of their personnel requirements. When you post the coupon below, we will send you an application form to be completed and returned with relevant details about yourself and those companies you don't want to join (which we guarantee to treat as confidential).

We match your skills and ambitions with our clients' needs. Only when we find one of them is looking for someone like you - only when we have checked again that you have not included them on your list of employers not to be contacted - will we tell them about you. Then the invitation to talk comes directly from that employer.

If you think of all the different types of jobs offered by those 3,000 companies - and we've been doing this for seven years - you can see that we've helped thousands of people to better opportunities and higher earnings.

Post this coupon today.

Lansdowne
Appointments Register,
Design House,
The Mall, London
W5 5LS.
Tel: 01-579 2282
(24 hour
answering
service).

Our clients are keen to meet men and women, aged 20 to 40 years, with potential earnings of between £4000 and £7000 p.a.

Name: _____
Address: _____

Lansdowne Appointments Register,
Design House, The Mall,
W5 5LS. Tel: 01-579 2282
(24 hour answering service).

ww15/2



For those too busy doing a good job to find a better one.

Development Engineer—

Electronics Measurements

The person selected for this position will be a member of a team which provides an electrical measurement service for Motor Car chassis and engine development.

Some of the more specific duties include:-

The application of strain-gauges and the installation of lead, pressure, displacement, noise and vibration transducers in motor car chassis and engines and the calibration and operation of these devices, together with the appropriate signal conditioning and recording apparatus.

Other areas of responsibility include the preparation of engineering reports, data analysis and the servicing and calibration of apparatus.

Candidates should possess Degrees or Higher National Certificates in electronic engineering and preferably have been employed for a number of years in the field of electronic measurements.

Our expansion in the field of modern technology offers good prospects for the successful applicant.

Persons selected from outside areas will be offered generous assistance with re-location costs.

Holidays commence at 28 days per annum, good social and welfare facilities and a subsidised employee canteen are available.

Male/female candidates should write, or better still phone, for further information to:

**John Williams or Edward Owen,
Rolls-Royce Motors Limited,
Car Division,
Pym's Lane,
Crewe CW1 3PL.
0270 55155 Ext. 3339.**



(8971)

**UNIVERSITY OF LEEDS
DEPARTMENT OF PHYSIOLOGY**
Applications are invited for the post of:—
**ELECTRONICS
TECHNICIAN
GRADE 5**

The successful applicant will be responsible to the Chief Electronics Technician for the development, construction and maintenance of a wide variety of electronic equipment associated with research and teaching of biological studies.

Candidates should hold ONC or equivalent qualifications in relevant subjects and have at least 7 years' appropriate experience, including any training period. Salary on the scale £3186-£3720 a year.

Applications stating age, qualifications and full experience together with the names and addresses of two referees should be addressed to Mr. E. French, Departmental Superintendent, Department of Physiology, Medical and Dental Building, The University, Leeds LS2 9JT.

(8942)

**CA CAPITAL
APPOINTMENTS LTD.**

FREE JOBS LIST
for
FIELD SERVICE ENGINEERS
BASIC SALARIES TO
£7,000 + CAR

(8781)

**30 Windmill Street, London, W1
01-637 5551**

**APPLIED MICROSYSTEMS
LTD.**

There are vacancies for a

LOGIC DESIGNER

with some 6800 microprocessor experience and also for a person to undertake printed circuit assembly in a small and growing company.

**Ring or write to Steve Brown at 17
Baker Street, Weybridge, Surrey.
Weybridge 48177.**

(8943)

RADIO TECHNICIANS Keep police lines open

Police depend on communications equipment every hour of the day — so if this equipment suddenly acts up, the police are seriously handicapped. That's where you can make a difference. As a Police Radio Technician in Central or South London, you'll help make sure our wide range of equipment is in top working condition.

Qualifications: two years' experience together with either C & G Telecommunications Technicians Intermediate Certificate; ONC or equivalent.

Salary: from £3092 - £4165 p.a. according to age at entry, rising to £4717 p.a. including Inner London Weighting Allowance. There are substantial extra allowances for those employed on shiftwork at New Scotland Yard. Benefits include day-time release to study for higher qualifications, assistance with course fees and 4 weeks' holiday a year. Good prospects of promotion.

For details and an application form, contact:

The Secretary, Room 213/WW/RT, 105 Regency Street, London SW1P 4AN. Telephone 01-230 3122 (24 hour answering service).

(8948)

**NEWCASTLE AREA HEALTH AUTHORITY (TEACHING)
ELECTRONICS & MEDICAL ENGINEERING SECTION
NEWCASTLE GENERAL HOSPITAL**

CHIEF ELECTRONICS TECHNICIAN (GRADE 2)

Applications are invited for the above position. The Chief Electronics Technician will assist the Senior Area Electronics Engineer in the maintenance of electronic and medical engineering equipment.

The position offers a unique opportunity to lead a specialist team of Technicians covering all applications of electronics in medicine, including brain scanning equipment and communications.

Salary Scale: £4,470 rising to £5,610 by 8 annual increments.

Candidates must have a broad experience of electronics, experience of medical electronics an advantage. Minimum academic qualifications — H.N.C. Electronic Engineering or equivalent.

Job description and application forms available from Area Engineer's Office, Newcastle Area Health Authority (T), Area Headquarters, Scottish Life House, 2-10 Archbold Terrace, Newcastle-upon-Tyne NE2 1EF. Closing date for completed application forms: 7th March, 1979.

(8928)

ELECTRONICS TESTER

A vacancy exists in our Instrument Shop for an Electronics Tester, must have previous experience of testing electronic equipment including logic circuits.

Good working conditions, canteen facilities.

Apply: **Mr. M. Leigh, Manager Instrument Workshop, PO Box 290, Technico House, Christopher Street, London EC2P 2ER.**

(9004)

Radio Officers Sea Sick?

If you've seen quite enough of the sea, and are thinking now of a shore-based job that suits your qualifications, the Post Office Maritime Service can offer you interesting work, job security, good pay, plus the pleasure of enjoying all the comforts of home where you appreciate them most - at home!

Vacancies exist at several coast stations for qualified Radio Officers to carry out a variety of duties that range from Morse and teleprinter operating to traffic circulation and radio telephone operating. And for those with ambition, the prospects of promotion to senior management are excellent.

You must have a United Kingdom Maritime Radio Communication Operator's General Certificate or First Class Certificate of proficiency in Radio-telegraphy or an

equivalent certificate issued by a Commonwealth Administration or the Irish Republic. Preferably you should have some sea-going experience.

The starting pay at 25 or over will be about £4450; after 3 years service this figure rises to around £5750. (If you are between 19 and 24 your pay on entry will vary between approximately £3500 and £4050). Overtime is additional, and there is a good pension scheme, sick-pay benefits and at least 4 weeks' holiday a year.

For further information, please telephone Andree Trionfi on Freefone 2281 or write to her at the following address: ETE Maritime Radio Services Division (WW), ETE17.1.1.2, Room 643, Union House, St. Martins-le-Grand, London EC1A 1AR.



(7141)

**UNIVERSITY OF LIVERPOOL
DEPARTMENT OF PHYSICS**

**EXPERIMENTAL or SENIOR
EXPERIMENTAL OFFICER**

To collaborate with academic staff in the design and development of systems for collecting and processing experimental data. Work involves exploitation of microcomputers with links to PDP11's and large S.R.C. computers. Candidates must have some knowledge of digital circuits and computers and hold degree or equivalent qualification. Good opportunity for young graduate to gain experience. Salary according to age and experience, on the scale for Experimental Officers - up to £5604 p.a. - or Senior Experimental Officers - up to £6555 p.a. - (under review). Applications forms may be obtained from The Registrar, The University, P.O. Box 147, Liverpool, L69 3BX.

Quote Ref: RV/474/WW

(8998)

SERVICE ENGINEER

Kontron Intertechnique have installation of Beta countries. We are seeking a Field Service Engineer to work in the area South of the Thames. The engineer would be responsible for field service within his own area.

This is a very demanding job but the company is prepared to award a successful engineer with attractive remuneration and work satisfaction.

Apply to:
John Clapham
(Technical Director)
Kontron Intertechnique
P.O. Box 88
St. Albans
Herts.
AL1 5JG

(9011)

Electronic Engineers - What you want, where you want!

TJB Electrotechnical Personnel Services is a specialised appointments service for electrical and electronic engineers. We have clients throughout the UK who urgently need technical staff at all levels from Junior Technician to Senior Management. Vacancies exist in all branches of electronics and allied disciplines - right through from design to marketing - at salary levels from around £4000 to £8000 p.a.

If you wish to make the most of your qualifications and experience and move another rung or two up the ladder we will be pleased to help you. All applications are treated in strict confidence and there is no danger of your present employer (or other companies you specify) being made aware of your application.

**TJB ELECTROTECHNICAL
PERSONNEL SERVICES,**
12 Mount Ephraim,
Tunbridge Wells,
Kent. TN4 8AS.

Tel: 0892 39388



Please send me a TJB Appointments Registration form:

Name

Address

(9005)

Instrumentation Engineer (Electronics)

The Development Instrumentation Department, at the Rolls-Royce East Kilbride Engine Test Facility, has a vacancy for a Section Leader to head a small group which is responsible for maintenance and manufacture of signal processing and recording equipment.

Work includes development and construction of specialised instruments as well as maintenance, fault diagnosis and repair of existing equipment.

Applicants should have appropriate experience and hold an H.N.C. or equivalent qualification. Salary will be in the range £4482 - £5082 and the usual excellent conditions of employment will apply.

Please apply in writing quoting experience to:
Personnel Manager, Rolls-Royce Limited,
Aero Division - Scotland, East Kilbride, Glasgow G74 4PY.



AERO DIVISION

8992

ROYAL POSTGRADUATE MEDICAL SCHOOL

Department of Medicine

TECHNICIAN

required to assist in electronic equipment development work in the Respiratory Division of the Department of Medicine.

Experience in analogue, digital and software techniques desirable, together with an interest in instrumentation development.

Salary on scale £3646 to £5086, initial placing dependent on qualifications and experience.

Application forms and further particulars may be obtained from the Personnel Office, Royal Postgraduate Medical School, 150 Du Cane Road, London W12 0HS, quoting reference number 2/120/WW.

(8934)

UNIVERSITY OF LIVERPOOL DEPARTMENT OF PHYSICS

ELECTRONICS TECHNICIAN

To assist in developing and commissioning digital and analogue electronics equipment.

Applicants must possess recognised qualification and have previous experience. Salary on a scale up to £4365 p.a. according to qualifications and experience (under review).

Application forms may be obtained from The Registrar, The University, P.O. Box 147, Liverpool. L69 3BX.
Quote Ref: 473/WW

(8997)

ENGINEER TECHNICIAN

required to be responsible for expanding the electronic research and development laboratory for a small professional firm of consulting engineers. Salary by negotiation.

Please apply, quoting qualifications and experience, to Dr. Bruce Smith, Smith Associates Consulting System Engineers Limited, 20 Queens Road, Weybridge, Surrey.

(8944)

ELECTRONICS SERVICE ENGINEER

required for P.A. and Lighting hire company.

This position is for a qualified senior person of proven technical ability capable of managing a small busy workshop.

Apply in writing to:
John Denby
ENTEC
Shepperton Studio Centre,
Shepperton, Middlesex.

(8933)

AUDIO SERVICE ENGINEERS

We require additional staff to join our small team in our Service Department based in London NW1 (near Marylebone Station).

The work involves the maintaining, servicing and overhauling of top quality audio equipment for the film and T.V. industry.

Ideally, you should have previous experience in this field, although product training will be given. On some occasions you would also be required to visit other locations in the U.K.

In return, we are offering very attractive salaries plus non-contributory pension scheme and four weeks' annual holiday.

For further information, in strict confidence, please contact Maureen Sleight on Gerrards Cross (STD 02813) 88447 or write giving full C.V. to Mr. J. Rudling

HAYDEN LABORATORIES LIMITED
6 Bendall Mews, Bell Street, LONDON NW1

(8933)

HAYDEN

TELEVISION PROJECT ENGINEER

Pro-Bel Ltd manufactures custom built vision and audio switching systems for the professional broadcast industry, and markets the CapGen character generator and Elcon tape cleaner.

Due to expansion we require additional junior and intermediate engineers to be responsible for customer liaison, design and test of switching systems.

The position offers a chance to join a small expanding company and to be involved in all stages of contracts from initial planning to customer acceptance. A certain amount of U.K. and overseas travel will be involved.

In addition to a good salary we offer BUPA membership, a friendly environment and excellent career prospects.

For more details contact David Steel at:

pro-bel
LIMITED

TERRACE ROAD, BINFIELD, BRACKNELL
BERKSHIRE RG12 5DN ENGLAND
Telephone BRACKNELL (0344) 56969/56960

(8930)

We've always looked for Test Engineers who weren't afraid of New Ideas

Pye Telecommunications have made many original contributions to the technology of mobile radio; for instance, we were the first manufacturer to use printed circuit boards. But whatever we have achieved, we have always backed it with the specialist skills and abilities of our test engineers – the men and women who put the final seal of approval onto all our equipment.

If you welcome the challenges offered by a wide variety of products, many incorporating up-to-the-minute technology, then you'll fit in at Pye. To join us you should have had sound experience of fault diagnosis, alignment, and testing at PCB level, preferably on communication equipment. Forces experience would be particularly suitable. As the leading manufacturer of two-way UHF/VHF radio

systems in Europe, we can offer you excellent working conditions, well-equipped workshops with a broad range of modern test gear, good career prospects and a stable company structure where you will find security and job satisfaction. Starting salaries are between £3800 and £4300 depending on technical ability.

The positions are based at Haverhill in Suffolk, where key-worker housing may be available for those moving from other parts of the country.

**For further details please write or phone, reversing the charges where necessary, to Mrs. Catherine Dawe, Senior Personnel Officer,
Colne Valley Road, Haverhill, Suffolk.
Tel: Haverhill 4422.**




Pye Telecommunications Ltd

Colne Valley Road, Haverhill, Suffolk.
Tel: Haverhill 4422.


A member of the Pye of Cambridge Group

(8932)

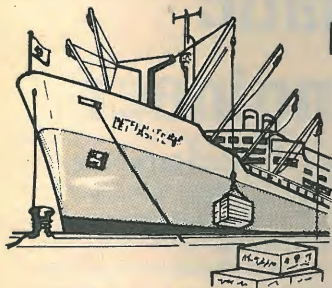

Exporting Colour TV sets is never easy

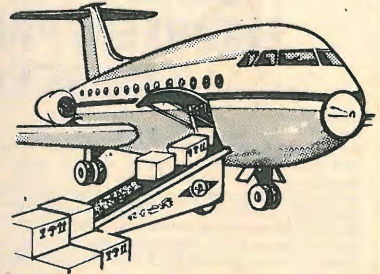Every market requires something different and whether it's a change to the circuitry for differing TV standards or systems, or an alternative styling or finish, it invariably requires engineering involvement in ensuring our customers get what they want.



WE ARE SEEKING A PROJECT LEADER TO LOOK AFTER THE TECHNICAL NEEDS OF OUR DORIC CUSTOMERS AT HOME AND ABROAD.

Ideally you will be a qualified, professional, self motivated TV engineer who can apply your skills to organizing a small but enthusiastic team to solve a wide variety of problems associated with the design, production and operation of a sophisticated range of colour TV receivers. You will be experienced in project management, development of colour TV and customer service, with particular emphasis on export markets. Some knowledge of safety performance of domestic electronics, test house approvals and quality assurance assessment in a modern factory environment will also be useful.

The team also checks out audio products from world-wide sources, prior to purchase, and hence some experience of the performance and constructional requirements of this type of equipment will be an asset.

You will be based at our engineering centre at Chessington, Surrey, but occasional visits to our factories in the North East and to our customers, both at home and overseas, will be required.

You will be paid an attractive salary and generous assistance with relocation expenses will be offered, where appropriate.

If this sort of challenge is of interest and you feel you can make a real contribution to the success of our operation, please write or telephone to:-

Mr. H. Brearley,
Rediffusion Consumer Electronics Limited,
Fullers Way Sth., Chessington, Surrey. KT9 1HJ
Telephone: 01 397 5411



REDIFFUSION

We've variety and interest to offer you as a service and test engineer in Stanmore

It's the variety that comes with working on a wide range of equipment. And the interest of knowing that your skills and experience are playing a vital role in maintaining the critical standards demanded by major airlines and Air Forces for their highly sophisticated avionics equipment.

Working either in aircraft or in our well equipped and pleasantly situated workshops in Stanmore, Middlesex, you will be involved in the repair, maintenance and overhaul of a variety of advanced airborne electronics equipment, both British and American.

It's work for which you'll need

to have sound practical experience of radio and electronics theory, ranging from audio to microwave. You should also have experience of using advanced test equipment for fault diagnosis, although training can be given where necessary.

We can offer you an excellent salary and benefits together with really first-class working conditions and subsidised staff restaurant, so if it's variety and interest you're looking for write now with details of your experience to: Mrs. E. Wagg, Marconi Avionics Limited, 22-26 Dalston Gardens, Stanmore, Middlesex HA7 1BZ. Telephone: 01-204 3322.

MARCONI AVIONICS

A GEC-Marconi Electronics Company

(8763)

SOUND ENGINEER

The Royal Opera House requires an **Assistant Sound Engineer**. The position would suit someone with Studio or Broadcasting experience who is prepared to work long and unsocial hours. The work is very varied and requires an engineering background and some musical knowledge.

Apply to **Eric Pressley, Royal Opera House, Floral Street, London WC2E 7QA.** (8978)

TOP JOBS IN ELECTRONICS

Posts in Computers, Medical, Comms, etc. ONC to Ph.D. Free service.

Phone or write: **BUREAUTECH AGY, 46 SELVAGE LANE, LONDON, NW7. 01-959 3517.**

(8994)

Engineers

- DESIGN / DEV
- TEST
- FIELD SERVICE

High Salaries - Most Areas

Phone 01 - 731 4353

(8995)

Apex Personnel

EMI

SENIOR DESIGN ENGINEER/PROJECT ENGINEER

Pantak (EMI) Ltd., based in Windsor, Berkshire, are one of the world leaders in Industrial, Security and Medical X-ray equipment. We require one Senior Design/Project Engineer in our Development/Design Dept. who will be principally concerned with the design of our new range of specialist electronic products which are based around inverter and switch mode circuits. The successful applicant will also be in control of a small team. Minimum qualifications would be an HND with experience in the specified technologies, with approximately 10 years' previous experience. A B.Sc in Electronic Engineering would be a distinct advantage. Benefits for the position are those you would expect from the EMI Group, and include:

- ★ An attractive salary around £7,000 p.a.
- ★ Career opportunities.
- ★ A 35-hour working week.
- ★ Four weeks' holiday.
- ★ First-class pension scheme with free life assurance.
- ★ Excellent subsidised canteen
- ★ Generous relocation expenses where applicable.

We also require

ONE ELECTRONIC TEST ENGINEER

who will be responsible for testing and fault-finding analogue and digital control circuits. For this position we offer a salary around £4,000 p.a. with all other benefits as above.

To find out more, telephone **DAVID DRAKE, Personnel Officer, now on Windsor 55611**, or write to him at: **PANTAK (EMI) LTD., VALE ROAD, WINDSOR, BERKS.**

Pantak

A member of the EMI Group of companies
International leaders in music, electronics and leisure

(8962)



Automatic Test Engineer North West London

Radiomobile, the leading manufacturer of in-car entertainment equipment is looking for a young Electronics Engineer who is willing to take a key role in a new and important development at their main production unit.

Your responsibilities will be:-

- ★ to take an active part in the implementation and running of Automatic Test Equipment.
- ★ To produce jigs and programmes for this equipment and to run self-check programmes when required.
- ★ To monitor the information from the A.T.E. and feedback details of component failures to the production area.

Applicants should be qualified to HNC (Electronics), C & G FTC (Electronic) or equivalent.

If you have a keen and demonstrable interest in radio and looking for an appointment with an attractive salary, plus bonus, plus benefit package.

PER
Professional & Executive Recruitment

Contact: **Jane Brooks on (01) 235 7030 Ext. 246**
(answering service out of hours
(01) 235 6938)

Applications are welcome from both men and women

(8955)

RADIO TECHNICIANS

299858 PO WD G
0299992 PO TS G
FB69 1224 LONDON T 43

JOHN J SMITH BRIDGE ST YORKS

REFERENCE TO TWO YEAR CONTRACT -
GROUND RADIO - SAUDI ARABIA STOP

PLEASED TO TELL YOU THAT YOUR APPLICATION FOR TECHNICIAN
POST IS ACCEPTED STOP WE WOULD LIKE TO FINALIZE VIZA /
PASSPORT ARRANGEMENTS ETC PLEASE
01-574 5000 SOONEST TODAY STOP

COL 20 W1 01-574 5000

299992 PO TS G
299858 PO WD G

POST OFFICE TELEGRAM
NO CHARGE FOR DELIVERY

TSO FB69

JOHN J SMITH
BRIDGE STREET
YORKS

Here's a communication that's worth £16,350 tax free

Lockheed Aircraft International in Saudi Arabia are now offering two year contracts worth £16,350 tax free to Ground Radio Technicians who can install, maintain and repair SHF, UHF, VHF, and HF(SSB) radio equipment and systems and who preferably have knowledge of systems engineering and microwave systems. Lockheed's operations cover the installation, repair and maintenance of a wide range of highly complex electronic equipment in the fields of communications and aviation services.

So a two year contract with them will not only see a sizeable increase to your bank balance - it will also see you developing your specialist experience in an operational environment.

The minimum total earnings we have mentioned include bonus and cost of living allowance.

Then there's a substantial benefits package which includes:

- * Three paid leave periods annually with three free flights home to the UK
- * Free food, laundry and bachelor accommodation
- * Free medical care and life insurance
- * Good recreational facilities
- * Excellent prospects for employment beyond the contract period.

If you are interested in hearing more about these excellent opportunities, write or phone, quoting ref: 017L, to
Recruitment Officer,
IAL, Aeradio House,
Hayes Road, Southall,
Middlesex. Tel: 01-574 5000.



**HAMPSHIRE
FARNBOROUGH COLLEGE OF TECHNOLOGY**
Ref. 79/1/A22

LECTURER

Grade 1 in Electrical Engineering

Able to teach up to at least T.E.C. Certificate level. Appropriate qualifications required, with practical experience in Electronics. Further particulars from:

The Staffing Officer
Farnborough College of Technology
Boundary Road, Farnborough, Hants, GU14 6SB
S.A.E. please.

Closing date: 9th March, 1979.

(8975)

CANCER RESEARCH CAMPAIGN
4 MV Van de Graaff
ELECTRICAL ENGINEER / PHYSICIST
(Scientist or S.R.O.)
PHYSICS OR ELECTRONICS TECHNICIAN

for operation application and development of this unique multi-purpose machine for non-clinical research into biological and biochemical effects of radiation to improve cancer therapy. Neutron and pulsed and continuous beams of electrons produced.

Lecturer or S.R.O. to manage accelerator and its technical staff, should have degree (or equivalent) or high degree and experience of particle accelerators, ionizing radiations, electronics, vacuum technology mechanical design starting salary to £6,530 (CMRC Grade 2) according to experience, qualifications and age.

TECHNICIAN Candidates, preferably with HNC or degree and some experience as above. Starting salary to £5,034 (MCR Tech) according to experience, qualifications and age.

Apply: Deputy Director CRC Gray Laboratory, Mount Vernon Hospital, Northwood, Middlesex HA6 2RN.

(9001)



**Major DME
developments for
2900 and a new
small system**

Our work in progress could mean real career progression for you!

**Bracknell, Berks;
Kidsgrove, Staffs
£4,000-£8,500**

Join the company where exciting things are happening on brand new hardware! Right now we are working on major new Small System developments at Bracknell and Kidsgrove.

This could be your opportunity for real personal career progression. There will be considerable scope for your skills in one of our *integrated* development teams where both hardware and software people have the opportunity to work profitably together or you could find a rewarding future specialising in your chosen field.

Wherever you work you will find every opportunity for fast personal development and this, coupled with our unrivalled reputation for training, adds up to an offer not to be missed.

The successful application of your skills is vital to our total systems development.

That is why we need:

Programmers

with assembler, operating systems development or microcode experience.

Engineers

with a background in state-of-the-art technology.

In both cases we expect you will be in your 20's with at least 2 years experience behind you.

Naturally relocation expenses and full large company benefits are available.

Interested?

Call John Milner on Bracknell (0344) 24842 Ext: 2373 or Peter Mills Ext: 2169 or write to ICL, Lovelace Road, Bracknell, Berks, RG12 4SN quoting reference WW 1173

International Computers

think computers - think ICL



(8958)

ELECTRONICS TECHNICIAN

c.£4,000 p.a. Southampton

STRUCTURAL DYNAMICS LIMITED

is a specialist, high technology company with a team of over 30 offering consultancy services in the vibration analysis of large steel structures and associated rotating machinery. The company's services include monitoring systems for machinery and structures and vibration / acoustic troubleshooting.

To support continued expansion an **ELECTRONICS TECHNICIAN** is required to assist on a number of electronic projects associated with analogue/digital instrumentation.

Candidates should preferably have an education to ONC standard, although a demonstration of practical ability in constructing and testing prototypes would be considered satisfactory. A knowledge of Linear I.Cs and CMOS devices would be advantageous.

Salary in accordance with experience, BUPA contributory pension scheme and four weeks' annual holiday.

Telephone J. G. Sindall on Southampton (0703) 35611 for an application form, or apply directly in writing to Structural Dynamics Limited, 18 Carlton Crescent, Southampton SO1 2ET.

ST. BARTHOLOMEW'S HOSPITAL RADIATION PHYSICS DEPARTMENT MEDICAL PHYSICS/ ELECTRONICS TECHNICIAN GRADE III (or IV)

To assist in the servicing of a new 20 MeV Linear Accelerator, a 4 MeV Linear Accelerator, E.M.I. Body and Head CT scanners and other radiotherapy equipment. To assist in the manufacture of dosimetry equipment and devices required for development and research.

Experience in Radiation Physics or computers would be advantageous but not essential as training will be given where necessary.

There will be opportunities to obtain higher qualifications.

Applicants should possess ONC/HNC (Electronics) or other appropriate qualifications and for Grade III, at least 3 years' relevant experience as a Grade IV technician or equivalent.

Salary Scale £3423-£5142 p.a. inclusive.

Application forms from Personnel Department, St. Bartholomew's Hospital, London, EC1A 7BE, in writing, or phone 01-600 9000, ext. 3186. Please quote ref. no. PTB/203.

Closing date 10 days to 2 weeks from date of appearance.

(8982)

Opportunities in Broadcast Technology

Pye TVT now have openings for Development Engineers. Based in Cambridge, you will be working in our studio and transmitter development laboratories on a wide variety of projects.

TRANSMITTER DEVELOPMENT

You will be involved on a number of aspects of design in television f.m. sound and a.m. sound broadcast transmitters and transposers. Broadcast experience is an asset, but first essentials are interest and enthusiasm.

STUDIO ENGINEERING

Openings exist in aspects of the design of digital equipment for broadcast T.V. application and in the design and development of analogue and digital video processing systems for broadcast T.V. pick-up devices. Experience of high speed digital signal and/or data processing equipment is essential.

Opportunities exist at all levels and salary will depend on previous experience and background. Applicants should be qualified to degree/H.N.D. level. Pye TVT offer generous relocation expenses, competitive salaries, good holidays, plus the opportunity for career advancement within the broadcast industry.

For an application form, contact:

Alison Millar, Personnel Officer,
Pye TVT Limited, Coldhams Lane, Cambridge CB1 3JU.
Telephone Cambridge (0223) 45115



A member of the Pye of Cambridge Group

Pye TVT Limited

The Broadcast Company of Philips

8991

RADIO TECHNICIANS

At the Government Communications Headquarters we carry out research and development in radio communications and their security, including related computer applications. Practically every type of system is under investigation, including long-range radio, satellite, microwave and telephony.

Your job as a Radio Technician will concern you in developing, constructing, installing, commissioning, testing, and maintaining our equipment. In performing these tasks you will become familiar with a wide range of processing equipment in the audio to microwave range, involving modern logic techniques, microprocessors, and computer systems. Such work will take you to the frontiers of technology on a broad front and widen your area of expertise — positive career assets whatever the future brings.

Training is comprehensive special courses, both in-house and with manufacturers, will develop particular aspects of your knowledge and you will be encouraged to take advantage of appropriate day release facilities.

You could travel — we are based in Cheltenham but we have other centres in the UK, most of which, like Cheltenham are situated in environmentally attractive locations. All our centres require resident Radio Technicians and can call for others to make working visits. There will also be some opportunities for short trips abroad, or for longer periods of service overseas.



WORK IN COMMUNICATIONS R&D AND ADD TO YOUR SKILLS

You should be at least 19 years of age, hold, or expect to obtain shortly, the City and Guilds Telecommunications Technician Certificate Part 1 (Intermediate), or its equivalent, and have a sound knowledge of the principles of telecommunications and radio, together with experience of maintenance and the use of test equipment. If you are or have been in HM Forces your Service trade may allow us to dispense with the need for formal qualifications.

You start on £2927 at 19, up to £3700 if you are 25 or over, rising to £4252, and promotion will put you on the road to posts carrying substantially more. There are also opportunities for overtime and on-call work paying good rates.

Get full details from our **Recruitment Officer, Robby Robinson, on Cheltenham (0242) 21491, Ext. 2269, or write to him at GCHQ, Oakley, Priors Road, Cheltenham, Glos. GL52 5AJ.** If you seem suitable, we'll invite you to interview in Cheltenham — at our expense, of course.

(8508)

Skilled in Electronics? You could become a Systems Engineer

- Are you at least 20 years of age?
- Have you 2 years' practical electronics experience plus any one of the following?
 - City & Guild's full electronic certificate
 - HNC in electronics
 - A completed electronics apprenticeship
 - An H.M. Forces electronics training
- Will you accept the challenge of maintenance and diagnosis on ICL's complex computer systems?

YES? Then we are interested in training you to join our skilled teams of Systems Engineers in maintaining our customers' computers. After a thorough initial training you will be based on one of our customer sites in the U.K. Within 18 months you should be a fully trained Systems Engineer with a career rich in opportunity ahead of you. You will have the satisfaction of using all your technical expertise, tact and personality as a representative of ICL. If you are interested in one of these jobs, with excellent salaries and

conditions even during training, then return this coupon or phone David Reeves on Stevenage (0438) 68347 or 68334 for an application form.

TO: David Reeves, CED Recruitment, ICL, Cavendish Road, Stevenage, Herts SG1 2DY.

I would like to find out more about being a Systems Engineer.

Name _____

Address _____

International Computers



think computers - think ICL

Ref. WW1197 (8969)

PAY PEANUTS GET MONKEYS

The firms for whom we are recruiting want Electronic Engineers not monkeys. The salaries we obtain for our clients reflects this.

New graduate £4,500 p.a.

28 Year old project leader £8,000 + car.

25 year old graduate £6,000.

24 year old £4 an hour (contract).

CURRENT VACANCIES INCLUDE

1. **Design Development Engineers** for a telecommunications command control project involving P.C.M.; Time division multiplexing, A/D conversion, active filters and circuits for speech compression. To £8,000. Middlesex, Berks. border.
2. **Project Engineers, Systems Engineers** for industrially sponsored research association with particular emphasis on automation and computerisation for the process industries. To £7,500. Surrey.
3. **Young Hardware/Software Systems Engineer** for design and development associated with mini computer/microprocessor, controlled A.T.E. Exp. assembler programming preferred. To £5,500. South Coast.
4. **Logic Designers** all levels for state of the art equipment used in the printing industry. Microprocessor/minicomputer based systems. To £6,500. West Country.
5. **Computer Field Engineers** — Vacancies throughout U.K. including Home Counties. Southern England, Nottingham, Newcastle, Northampton, Leeds, Coventry, Bristol, Swansea. Salaries negotiable.

FOR PERMANENT STAFF

LITERALLY thousands of vacancies including **Contract Test Engineers and Contract Prototype Wiremen.** Home Counties and on the South Coast.

Excellent rates. For further details please contact:

Charles Airey Associates

"PROBABLY THE BEST KNOWN SUPPLIER OF ELECTRONICS ENGINEERS IN THE COUNTRY" — FINANCIAL TIMES

155 KNIGHTSBRIDGE, LONDON, SW1. TEL: 01-581 0286

(9009)

Radio Technology — London

TELECOMMUNICATIONS OFFICER

The work includes the study of radio propagation matters over the whole of the radio spectrum (10kHz-27.5GHz); forward planning and regulation of frequency bands allocated to broadcasting, maritime and land mobile services; type-approval of equipment for mobile services; development of equipment for the location and suppression of radio interference.

Candidates (aged at least 23) must have ONC in Engineering (with a pass in Electrical Engineering 'A') or in Applied Physics, or an equivalent qualification. In addition, they should have had experience in the operation of radio receiving equipment and have a knowledge of current operational systems of radio communications.

Salary starting between £4080 and £4820 (according to age) and rising to £5170. Promotion prospects. Non-contributory pension scheme.

For further details and an application form (to be returned by March 14, 1979) write to Civil Service Commission, Alencon Link, Basingstoke, Hants, RG21 1JB, or telephone Basingstoke (0256) 68551 (answering service operates outside office hours). **Please quote T/5025.**

HOME OFFICE

(8984)

SITUATIONS VACANT

Telecommunications

We require staff, male or female, to prepare and maintain the latest in communications equipment used by the Police and Fire Brigades in England and Wales.

You will need to be qualified at least to City and Guilds Intermediate Telecommunications standard and be able to demonstrate practical skills in locating and diagnosing faults in a wide range of equipment from computer based data transmission to FM and AM radio systems. You would live near to and work from one of our service centres located throughout England and Wales or our Headquarters in the London area. Specialist courses of training are run to assist staff to keep up to date with developments and new equipment, and there are opportunities for day release to gain higher qualifications. Applications from registered disabled persons will be considered.

Promotion prospects are good and the

work represents a secure future with generous leave allowances and a non-contributory pension scheme.

Possession of a driving licence is essential since some travelling will normally be involved.

The salary is £2627 (at 17), £3176 (at 21) and £3700 (at 25), rising to a maximum of £4252.

If you are interested in working with us, then write for further details and an application form stating where you are interested in working, to:

Mr C B Constable Directorate of Telecommunications Horseferry House Dean Ryle Street LONDON SW1P 2AW Telephone: 01-211 6420



HOME OFFICE

8894

Electronic Test Engineers

We manufacture and market audio noise reduction equipment which is used by major recording companies, recording studios and broadcasting authorities throughout the world and have enjoyed successful growth since incorporation in 1968.

The success of such films as "Star Wars" and "Close Encounters of the Third Kind" has led to an increased demand for our cinema equipment and contributed to our need for experienced test engineers for all our professional products.

If you have practical knowledge and experience of electronic testing, think you can test, calibrate and trouble-shoot our sophisticated equipment, enjoy the challenge of quality and delivery pressures and want to hear about the excellent pay and conditions, telephone Tony Hill, 01-720 1111.



Dolby Laboratories Inc
346 Clapham Road
London SW9 9AP
Telephone 01-720 1111

8931

Medical Sales Engineers

Kontron Instruments Limited develop, manufacture and market a comprehensive range of medical and analytical equipment throughout the world. Planned expansion creates the following opportunities:

Patient Monitoring

A vacancy exists covering the northern home counties. Candidates should preferably be aged 23 to 35 with an HNC Degree or equivalent in bio medical engineering, electronics or life sciences. Relevant selling experience or a hospital background in physiological measurement or medical electronics would be equally acceptable.

Salary + commission £7-8,000 p.a. Company car, pension and other attractive fringe benefits.

Cardiology

Our fast expanding cardiology division has vacancies in various parts of the country. Applications are invited from candidates aged 23 to 35 having the qualifications and/or experience outlined above.

Salary + commission £7-8,000 p.a. Company car, pension and other attractive fringe benefits.

These positions would suit ambitious sales engineers or senior hospital technicians, with a keen desire to enter marketing.

Contact or submit curriculum vitae to

Personnel Manager,
Kontron Instruments Ltd.,
Campfield Road, St. Albans, Herts.
Tel: St. Albans (0727) 33221



KONTRON

Serving hospitals throughout the world



(8980)

ARTICLES FOR SALE

EXCLUSIVE OFFER

RACK MOUNTING CABINETS HIGHEST QUALITY 19"

Ref	HI"	Width"	Depth"	Price
PE	10	21	13	£10.00
LL10	54	21	18	£20.00
TT	64	25	26	£45.00
SL	71	25	26	£50.00
PT	72	20	21	£20.00
TK	75	22	21	£20.00
ST	85	22	24	£70.00

Racal cabinets for RA-17/117 **£30.00**

Over 60 types available from 12" to 90" high. Also twins, triples and consoles. Above are only a few types. Please send for full list.

AUDIO AND INSTRUMENTATION-TAPE RECORDER-REPRODUCERS

- * Plessey 1033 Digital Units, 7 track 1/2"
- * Plessey M5500 Digital Unit, 7 tracks 1/2"
- * Ampex FR-100, 6 speeds, stereo 1/2"
- * Ampex FR600, 4 speeds, 7 track 1/2"
- * D.R.I. RMI, 4 speeds, 4 tracks 1/4"
- * Minicom CMP-100, 6 speeds, 7 tracks 1/4, 1/2, 1"
- * Ampex 351 2 speed 2 tracks 1/4"
- * SM. N. 4 speeds 14 track 1"

Prices of above £70 to £500

Also Transport Docks only available

We have a large quantity of "bits and pieces" we cannot list - please send us your requirements, we can probably help - all enquiries answered.

All our aerial equipment is professional MOD quality

- * Tektronix 543A Oscilloscopes CA £290.00
- * Tektronix 545A Oscilloscopes D £275.00
- * Tektronix 561A Oscilloscopes 80 £360
- * Marconi TF 2200A Oscilloscopes £375.00
- * Solafron CD 1014 Oscilloscopes £110.00
- * Solafron 1016 Oscilloscopes £90.00
- * Rhode & Schwarz QVH Q meters 50Kc/30 MCS £160.00
- * Rhode & Schwarz Z00 Diagraph 300/2400 MCS £425.00
- * Rhode & Schwarz SWLM Signal Generators 30/300 MCS £180.00
- * Rhode & Schwarz SMAF AM/FM Oscillators 10/230 £220.00
- * Rhode & Schwarz SDR VHF Signal Generators 300/1000M £300.00
- * Rhode & Schwarz SWH Sweep Generators 50K/12M £160.00
- * Rhode & Schwarz SWOB-1 Polyscopes at 5/400M £400.00
- * Rhode & Schwarz SBR Signal Generators 1.6/2.4B £200.00
- * Rhode & Schwarz ESM-300 VHF Receivers 180/300M £275.00
- * Racal RA-17 P Receivers (New) £950.00
- * R.C.A. AR-88 Receivers £80.00
- * Eddystone 770U VHF Receivers (no turret coils) £90.00
- * Nems Clarke 1306 VHF Receivers £190.00
- * Collins KWT B Transmitter Receivers SSB P.U.R.
- * Phico HC-150 HF Point-to-point receivers P.U.R.
- * Rohand RD 50A Oscilloscopes £160.00
- * B & K 2407 Electronic Voltmeters £230.00
- * Advance Advac Electronic Voltmeters £90.00
- * CT 82 Noise Generators £45.00
- * Wayne Kerr B 801 R.F. Bridge £170.00
- * Winslow "S" Band Spectrum Analyzers P.U.R.
- * M.E.S.L. Sweep Generators 4/8 SWS £260.00
- * Airmec 352 Sweep Generators 200 cyc/200Kcs £130.00
- * Advance Transistor Testers TT-1S £45.00
- * Advance Digital Voltmeters DVM-1 £80.00
- * Marconi TF 329 Magnification Meters £140.00
- * Marconi TF 1065B FM Signal Generators £425.00
- * Marconi TF 801/0/1 AM Signal Generators £290.00
- * Ferranti 7.5Kv Auto Voltage Regulators £150.00
- * Thermionic Airport Time Injection Units £70.00
- * Manson TFM-101 Multipliers £240.00
- * Bradley CT 471B Electronic Multimeters £90.00
- * Sarvomec 25w Auto regulators £130.00
- * 125N Lattice Masts, 25" sides P.U.R.
- * 30N Lattice Masts, 14" sides £35.00
- * 10N Light Lattice Sections, 6" sides £18.00
- * Rohand Oscilloscopes 50A and plug-ins £190.00
- * EM 1/2" Audio Tape 3600 FT Mab £4.50
- * SE4/2B C.R.T.s £18.00
- * SES/2A C.R.T.s £19.00
- * 3AZP/Z (DMM-9) C.R.T.s £18.00
- * Plessey 3 & 6KCS S.S.B. Filters £14.00
- * AVO CT 471A Electronic Multimeters £75.00
- * EMI R 301 Tape Recorders £50.00
- * Smeetho L Tape Recorders £29.00
- * DG-7.5 C.R.T.s £4.00
- * Unselectors, 10 Bank 25-way £3.50
- * 40T. Sectional Aluminium Masts, complete £95.00
- * Narda 504 Freq. meters 200-500 M/cs £45.00
- * Multi-purpose Trolleys with Jacks 19 x 17 £16.00
- * E.M.I. Documents CCTV Output £45.00
- * Advance SKVA CV Transformer £250.00
- * Metal V.D.U. Tables 30" x 36" x 30" £24.00

MANUALS

We have a quantity of Technical Manuals of Electronic Equipment, not photostats, 1940 to 1960. British and American. No lists. Enquiries invited.

- * Data Efficiency Responders 240v £28.00
- * Belling Lee 100 Amp Interference Filters £76.00
- * Oscilloscope Trolleys from £18.00
- * Racal MA1978 pre-Selectors £65.00
- * Rack Mounting Operator Tables £10.00
- * Gammont K Alee 1740 Flutter Meters £75.00
- * 75T Aluminium Lattice Masts, 20" sides £400.00
- * 5.5 8 track Punches £48.00
- * Racal MA-175 I.S.B. Modulators (new) £45.00
- * Tally 5 8 Track Tape Readers 60 sps £48.00
- * Tally 5 8 Track Tape Readers Track Spooling £65.00

We have a quantity of Power Transformers 250 watts to 15KVA at voltage up to 40KV. Best quality at low prices. Lists available.

- * Racal RA-63 SSB Adaptors, new £70.00
- * Racal RA 298 L.S.B. Transistorised Converters (new) £120.00

We have a varied assortment of industrial and professional Cathode Ray Tubes available. List on request.

PLEASE ADD CARRIAGE AND V.A.T.
P. HARRIS
ORGANFORD, DORSET, BH16 6BR
BOURNEMOUTH (0202) 765051(8981)

SITUATIONS VACANT

Medical equipment for Hospitals

A VITAL ROLE FOR ELECTRICAL/ELECTRONIC ENGINEERS

These opportunities are in the Scientific and Technical Branch which provides the scientific, engineering and other professional services essential to the provision of medical apparatus, instrumentation and supplies to hospitals.

The successful candidates will join a team working on the specification, laboratory testing, inspection and quality control of a wide range of medical electrical and electronic equipment used in the National Health Service. Some UK travel required.



Candidates must have a degree or an equivalent qualification in electronics or electrical engineering and at least 2 years' experience in the design of electronic equipment covering analogue and digital circuits. Experience of medical electrical equipment advantageous.

Starting salary between £4,790 and £6,200 depending on qualifications and experience. Non-contributory pension scheme. Promotion prospects.

For further details and an application form (to be returned by 15 March, 1979) write to Civil Service Commission, Alencon Link, Basingstoke, Hants, RG21 1JB, or telephone Basingstoke (0256) 68551 (answering service operates outside office hours). Please quote T(40)85/2.

(8996)

Field Technicians and Technician Engineers

for Installation/Commissioning/Maintenance work on to Telecommunications/Radio systems currently being commissioned

Instrumentation/Telemetry

At least 3 years experience in electronic instrumentation or digital telemetry is required for work on this unique computer controlled telemetry system.

subject to experience and qualifications SALARY SCALE RISES TO £5493 per annum (inclusive)

For an application form and further details without commitment, telephone READING 593331 or write to the DIVISIONAL MANAGER, Thames Water, Conservancy Division, Nugent House, Vastern Road, Reading RG1 8DB.

Thames Water

(9006)

ARTICLES FOR SALE

LAB CLEARANCE: Signal Generators; Bridges; Waveform, transistor analysers; calibrators; standards; millivoltmeters; dynamometers; KW meters; oscilloscopes; recorders; Thermal, sweep, low distortion true RMS, audio FR, deviation. Tel. 040-376236. (8250)

G.W.M. RADIO LTD., 40/42 Portland Road, Worthing, Sussex. Tel. 34897. Pneumatic masts 40ft. By Scam Clark. 300 watt radar calorimeters, noise generators, type CT410, Eddy-stone communication receivers 730/4, v.g.c. £185.00 inc. Many bargains for callers, surplus always wanted. (8832)

INVERTERS

High quality DC-AC. Also "no break" (2ms) static switch, 19" rack. Auto Charger.



COMPUTER POWER SYSTEMS
Interport Mains-Store Ltd.
POB 51, London W11 3BZ
Tel: 01-727 7042 or 0225 310916

(8783)

TECHNOLOGICS CPG6RF colour bar and pattern generator. UHF Ae 1/P, new colour power battery design, 8 descending PAL colour bars crosshatch, dots, etc., full kit incl. case, etc., £36. Built £54. PG6RF kit £21.50, built £28. Add-on colour bar unit C6 in kit £15.50, built £22 plus £1 p&p, 8% V.A.T. Mail order from Technologics, Dept WW, 8 Egerton St., Liverpool L8 7LY. (8951)

SOLAR CELLS: bits, books and bargains. Send stamp for list or 95p for Solar Cell booklet and Data sheets. Edencombe Ltd 34 Nathans Road, North Wembley, Middlesex HA0 3RX. (8061)

ARTICLES FOR SALE

COLOUR, UHF AND TV SPARES. CEEFAX, ORACLE IN COLOUR. MANOR SUPPLIES "EASY TO ASSEMBLE" TELETEXT KIT. Including TEXAS Decoder. Aerial Input, completely external unit, no further connections to set. Full facilities, mixed TV programme and Teletext, Newsflash. Update, and many special features not found in other units. Demonstration model in operation at 172 West End Lane, NW6. Phone or write for further information.

TEXAS TIFAX XM11 Decoder module, new, £130, p/p £1.00.
NEW COMBINED COLOUR BAR GENERATOR PLUS CROSS HATCH KIT (Mk4) UHF Aerial input type. Eight vertical colour bars plus R-Y, B-Y, Luminance combinations, Grey scale etc. Pushbutton controls. Battery operated £35, De Luxe case £4.80, aluminium case £2.40, battery holders £1.50, mains supply kit £5.78, p/p £1.00. Built and tested (battery) £58, p/p £1.20.
CROSS HATCH KIT, UHF Aerial input type, also gives peak white and black levels. Battery operated, £11, p/p 45p. Add-on Grey Scale kit £2.90, p/p 35p. Aluminium case £2, p/p 85p. Cross Hatch Unit, complete and tested in De Luxe case £20.80, p/p £1.

"WIRELESS WORLD" TV Tuner and FM Tuner Projects by D. C. Read. Kits of parts available, CRT test and reactor kit for colour and mono £19.80 p/p £1.20. UHF Signal Strength Meter kit £18, p/p 90p. 625 TV IF Unit for Hi-fi amps or tape recording £6.80 p/p 70p. Decca Colour TV Thyristor Power Supply Unit, incl. H.T., L.T., etc. Incl. circuit £3.80, p/p £1.20. Bush A823 (A807) decoder panel £7.50, p/p £1. Bush 161 T-B panel A634 £3.80, IF panel A583 £3.80 p/p 90p. Bush Portable TV 11V stab power supply unit £4.80 p/p £1. Bush CTV 25 Convergence Panel plus yoke, blue lateral £3.60 p/p 90p. Philips Single Standard Convergence Units complete, incl. 16 controls £3.75 p/p 85p. Colour Scan Coils, Mullard or Plessey, £8 p/p 90p. Mullard AT 1023/05 Converg. Yoke £2.50 p/p 75p. Mullard or Plessey Blue Laterals 75p p/p 35p. BRC 3000 type Scan Coils £2 p/p 90p. Delay Lines: DL20 £3.50, DL50 £3.50. DLIE, DLI 85p p/p 45p. Lum delay lines 50p p/p 40p. G8 Tripler £6. BRC 300 Tripler £6.60 p/p 75p. Others available. Philips G8 Decoder part-complete £2.50 p/p 75p. GEC 2040 Ex-Rental Panels. Decoder £5.00. Time Base £5.00, p/p 90p. VARICAP TUNERS UHF: Gen. instr. £3.50. ELC 1043 £4.50, ELC 1043/05 £5.50. VHF: ELC 1042 £4.80, Philips VHF £3.80. Salvaged UHF & VHF Vari-caps £1.50 p/p 35p. VARICAP CONTROL UNITS, 3 position, £1.20. 4 PSN £1.50, 5 PSN £1.80, 7 PSN £2.80. Special offer 6 position £1. p/p 35p. UHF Transd. Tuners incl. slow motion drive £2.80, 4 position push button £2.50. 6 psn. £4.20, p/p 90p. Helical Pots 100K, 4 for £1.20 p/p 30p. Thorn 850 Dual Std. Time Base panels 50p. Philips 625 IF panel incl. oct. 50p p/p 70p. Mullard Mono Scan Coils for Philips Stella, Pye, Ekco, Ferranti, Invicta £2.00 p/p 85p. Large selection LOPTS, FOPTs available for most popular makes. MANOR SUPPLIES 172 WEST END LANE, LONDON, N.W.6. Shop Premises. Callers welcome. Thousands of additional items available not normally advertised. (Nos. 28, 159 buses or West Hampstead-Bakerloo Line and British Rail). Mail Order: 64 Golders Manor Drive, London, N.W.11. Tel: 01-794 8751. V.A.T. Please Add 12% TO ALL PRICES (EXCEPT WHERE MARKED. V.A.T. 8%). (60)

TRANSFORMER PROBLEMS?

1VA-1KVA Prototypes in 7-10 days. Phone Vince Sellar on 06076-66716.

TRENT TRANSFORMERS LTD
Chapel Street
Long Eaton, Nottm.

(8363)

SITUATIONS VACANT

Development Engineers for sub-hunting and train spotting

Ultra Electronic Communications, part of the international Dowty Group are world leaders in sonar buoy design and manufacture, advanced railway and train location networks, sophisticated aircraft communication systems and search and rescue beacons.

Development Engineers are highly regarded at Ultra and enjoy considerable autonomy and opportunities for travel and customer liaison worldwide, and the chance to contribute and influence projects in a sophisticated technological environment.

To join us you should be qualified to degree level Electronics or Mechanical Engineering and have upwards of 4 years experience of development work in an electromechanical/electronics environment.

Salaries will be negotiable and accompanied by a wide range of attractive large company benefits, including a very generous relocation package.

Men and women, for further information and an application form, please phone or write to **Mr. Gavin Rendall, Personnel Manager, Ultra Electronic Communications Limited, 419 Bridport Road, Greenford, Middlesex, UB6 8AU.**
Tel: 01-578 0081.



U.E.C.

Electronic Communications Ltd

The Polytechnic of North London

TECHNICIAN (Grade IV)

Applications are invited for the appointment of a Grade IV Technician in the Department of Electronic and Communications Engineering.

This interesting post involves the operation and maintenance of high grade test equipment, together with the general responsibility for students' day-to-day requirements with experiments and projects in the laboratory. Participation in R and D work in the audio engineering field in liaison with the audio team is encouraged.

Educational level: ONC/OND, City and Guilds, approved apprenticeship or equivalent qualifications.

Experience: at least 7 years (including training period).

Salary Scale: £3441-£3891 inclusive of London Weighting.

Application form obtainable from the Establishment Officer, The Polytechnic of North London, Holloway Road, N7 8DB. Further details from the Departmental Laboratory Superintendent (Telephone: 607 2789, Extn. 2176).

(8977)

ARTICLES FOR SALE

NOSTALGIA COLLECTING

THE VINTAGE WIRELESS COMPANY 1920 to 1950

Receivers, valves, components, service data, historical research, books, magazines, repairs and restorations. A complete service for the collector and enthusiast of vintage radio.

THE VINTAGE WIRELESS COMPANY
64 Broad Street, Staple Hill, Bristol BS16 5NL
Tel: Bristol 565472 (8966)

TIRRO's new mail order price list of electronic components now available on receipt of SAE. Tirro Electronics, Grenfell Place, Maidenhead, Berks. (8965)

CONSTRUCTOR PLANS — Hundreds sold! Pulse Induction Metal Locator, advanced economical switched CMOS design, Mk II £1.50, Mk III with stabiliser, 5 ICs £1.75, Radio Telescope 5-Metre £2, Solar Energy Furnace £1.80, Digital Multi-tested/frequency counter 22 ranges £1.50, R & E Publications, Highlands, Needham Market, Suffolk. (8976)

ROYAL BOROUGH OF KINGSTON-UPON-THAMES

DISPOSAL OF SURPLUS STORES

Offers are invited for the following item

1 Pye base radio station type F27 with five radio control units and five microphones, all in serviceable condition.

Goods may be viewed between 0730 and 1130 or 1300 and 1600 on Mondays to Fridays at the Villiers Road Depot by arrangement with the chief storekeeper, Mr. P. Beckinsale, Tel: 01-549 1257. (8947)

SURPLUS CAPACITORS: C280 250v. Price per hundred including postage — 0.068 £1.50; 0.33 £2.00; 0.1 £1.00 (1,000 £8; 5,000 £30). B. Malloy, 66 Woodvale Avenue, Belfast BT13 3EX, N. Ireland. (8964)

EX BBC VIDEO AND SOUND MODULES — mainly unissued. Lot includes two waveform monitors, quantity of colour distribution amps., and sound mixer modules S.A.E. for list to Geen, 8 Millgate, Delph, Nr. Oldham. (8957)

ARTICLES FOR SALE

SOWTER TRANSFORMERS

WITH 37 YEARS' EXPERIENCE we have the expertise to design and manufacture ANY TYPE OF AUDIO TRANSFORMER AT THE RIGHT PRICE

Whilst we specialise in every kind of transformer for audio control decks and mixers, demands are increasing for **LOUDSPEAKER TRANSFORMERS** and **100 VOLT LINE AUDIO OUTPUT TRANSFORMERS** for most kind of amplifier from 30 watts to 500 watts output. We have standard designs for AMCRON and BOSE amplifiers and can also supply **Multi-output transformers for COLUMN LOUDSPEAKERS** in a wide variety of powers. A recent tendency is the demand for **OUTPUT TRANSFORMERS FOR ULTRA LINEAR VALVE AMPLIFIERS** using KT88 and KT66 BEAM TETRODES and for these we have standard designs with exceptional performance. Many of our output transformers for loudspeakers have been installed in Theatres, Television Studios, Lecture and Concert Halls, Churches and Outdoor Arenas whilst others are in constant use for high quality portable Public Address Systems. We will supply single transformers, or any quantity, with short delivery times and, without obligation on your part, will quote price and exact dispatch on receipt of your requirements.

KINDLY NOTE OUR NEW ADDRESS AND TELEPHONE NUMBER: E. A. SOWTER LTD., Transformer manufacturers and designers, P.O. BOX No. 36, IPSWICH IP1 2EL, ENGLAND. Tel: Ipswich (0473) 52794-219390.

(8289)

SYSTEM DESIGN WITH MICRO PROCESSORS

by D. Zissos Price £7.00

SOFTWARE DESIGN FOR MICRO-COMPUTERS

by C. A. Ogdin Price: £7.00

BASIC FOR HOME COMPUTERS: A SELF-TEACHING GUIDE

by B. Albrecht Price £4.55

BEGINNER'S GUIDE TO HOME COMPUTERS

by M. Grosswirth Price: £3.20

BASIC COMPUTER GAMES

by D. H. Ahl Price: £6.00

DIGITAL INTEGRATED CIRCUITS & COMPUTERS

by B. Woollard Price: £3.55

THE OPTOELECTRONICS DATA BK FOR DESIGN ENGINEERS

by Texas Inst. Price: £4.15

USING DIGITAL & ANALOG INTEGRATED CIRCUITS

by L. W. Shacklette

Price: £8.50

VIDEO YEARBOOK 1979

Price: £13.00

INTEL THE SEMICONDUCTOR MEMORY BOOK

Price: £11.00

★ Prices includes postage ★

THE MODERN BOOK CO.
SPECIALISTS IN SCIENTIFIC & TECHNICAL BOOKS
19-21 PRAED STREET
LONDON W2 1NP

Phone 723 4185
Closed Sat. 1 p.m.

(8974)

HUGE BARGAIN PACK OF ELECTRONIC AND RADIO GOODIES. Too many items to list. All brand new and useful. No junk. Valve at least £25. Only £9 including post and packing. C.W.O. (U.K. only). Refund if not delighted. A. Philpott, 171 Great Brays, Marlow, Essex CM18 6DT.

Z80 MOSTEK DEVELOPMENT BOARD SDB80 plus power supply all neatly mounted as one unit. Includes circuits and all handbooks, ready to go. £700 new. £300 o.n.o. to R. Tuthill, Golden River Co. (08692) 44551. (8937)

WAVEFORM GENERATOR feedback TWG501, £55; dual variable power supply, 18v, £25. Phone 0305 852 136. (8952)

CHESS CHALLENGER 10 level version, ultra low prices including V.A.T. and postage and packing only £160. Gammonmaster 2 with doubling cube £115. Atari home video computer £127, extra cartridges only £12. Mail order only to Jagberry Limited, 95 Ardwell Avenue, Barkingside, Ilford, Essex. 01-588 7352. (8938)

THE FABULOUS D2 MICROPROCESSOR EVALUATION KIT FROM MOTOROLA

Featuring 24 key keyboard, Seven segment display, Cassette interface, Errom & Ram Expandable Interface Capability. Full Documentation, 5 Volt power supply required. One year's FREE membership of The Amateur Computer Club with every purchase. £176 + £1.50 P&P + 8% VAT.

ENAMELLED COPPER WIRE

SWG	1 lb	8 oz	4 oz	2 oz
14-19	2.60	1.40	66	55
20-29	2.80	1.60	85	65
30-34	3.00	1.70	95	70
35-40	3.35	1.90	110	79
40-43	4.50	2.50	1.90	1.25
44-46	5.00	3.00	2.10	1.65
47	8.00	5.00	3.00	1.76
48	15.00	9.00	6.00	3.30

Tinned Copper, Even Gauges 14-30 £3 per lb. Multicore 60/40 Solder 18SWG £3.24 per lb. Prices include P&P and VAT.

SAE brings list of copper and resistance Wires.

THE SCIENTIFIC WIRE COMPANY
PO Box 30 London E4 (7771)



Private enquiries, send 13p in stamps for brochure

THE QUARTZ CRYSTAL CO. LTD.

Q.C.C. WORKS, WELLINGTON CRESCENT
NEW MALDEN, SURREY 01-942 0334 & 2988

8493

PYE SPEECH SCRAMBLERS. Price per: Creed 75 teleprinter £40; Creed syn motor 3,000 rpm £5; Advance PP3 twin stab DC supply £30; Advance double pulse gen PG 5002C £35; H.P. ratio meter mod 416B £30; H.P. Audio sig gen 205AA £33; Cossor RMS meter 1453 £27; Marconi valve volt meter TF 1100 £15; Mufax 18in recorder type D-649 £120; Teleprinter tape and paper, 1' and 1/2 mag tape Dyn-amco 2001 MKZ DRM £75; Airmec oscillator-amplifier type 254 £55 plus V.A.T. Skipton Electronic Suppliers, 29 Keighley Road, Skipton, North Yorkshire. Tel: 0756 4397. (8949)

CLEARANCE SALE: Linsley-Hood 75 Watt Power Amp Modules. Fit Powertran standard chassis. Basic Module £10.50, module with BDY56 power transistors £13.50. Linsley-Hood amplifiers constructed and repaired. Prices inclusive, details free. I. G. Bowman (Dept WW), 59 Fowey Avenue, Torquay, S. Devon. (8999)

60KHz MSF Rugby Receiver, BCD TIME OF DAY OUTPUT. High performance, phase locked loop radio receiver, 5V operation with 1 second LED indication. Kit complete with tuned ferrite rod aerial £14.08 (including postage and VAT). Assembled circuit and cased-up version also available. Send for details, Toolex, Sherborne (4359), Dorset. (8252)

T.V. TUBE REBUILDING. Complete plant, equipment, supplies and training. If you can afford the best contact Western-Whybrow Engineering. Tel. 073 676 2265. (8048)

BIG SALE OF TEST EQUIPMENT

2,000 plus items to go

Sale starts Saturday, 10th March through to the 17th Sunday inclusive

Open from 9 o'clock till 6

EXAMPLE

Polyscope SWOB 1 £220.00.
Tetscope from £60.00 to £120.00 for a mainframe.
Some other makes cheaper.
Signal generators from £20.00 and many other bargains.
Sold as seen.

P & R TEST EQUIPMENT

Salcott Mill, Goldhanger Road, Heybridge
Near Maldon, Essex
Tel: Maldon (0621) 57446

(9015)

REVOX B77 TAPE RECORDERS. limited number, used approx. 50 hours 3 1/2 track, guaranteed for twelve months. £515 inc. V.A.T. EMI AND RACAL ZONAL, professional tape on 7in and NAB spools. Keen prices. Send for list. NEVENCO C90 cassettes £6.50 for 10 inc. V.A.T. Audio equipment for professional users, e.g. Uher, AKG, Beyer, Sennheiser etc. New range of NEVENCO mixing consoles especially for churches, charities and missions. NEVENCO LIMITED, 2 Hills Road, Cambridge CB2 1JP. Tel: (0223) 62392. (8950)

HI-FIDELITY DESIGNS No. 1 (a Wireless World publication). We had announced that this publication was out of print but we now discover that we have 350 copies in stock. Due to our announcement, many readers were disappointed, but we are now pleased to inform them that copies are available from The General Sales Manager, Room CP34, Dorset House, Stamford Street, London SE1 9LU. Please forward your order together with your remittance of £1.50 (including P&P) made payable to IPC Business Press Ltd. (8652)

ARTICLES WANTED

SPOT CASH

paid for all forms of electronics equipment and components.

F.R.G. General Supplies
550 Kingston Road, London
Tel: 01-404 5011
Telex: 24224 Quote Ref 3165

(8742)

WE PURCHASE ALL FORMS OF ELECTRONIC EQUIPMENT AND COMPONENTS, ETC.

SPOT CASH
CHILTMead LTD.
7, 9, 11 Arthur Road
Reading, Berks.
Tel. (0734) 582 605

TURN YOUR SURPLUS Capacitors, transistors, etc., into cash. Contact COLES-HARDING & Co., 103 South Brink, Wisbech, Cambs. 0945-4188. Immediate settlement. We also welcome the opportunity to quote for complete factory clearance. (7439)

ELECTRONIC SCRAP. Components, etc., Receivers, Transmitters Test Equipment wanted. Ferrographs from £15 in stock. Contact M & B Radio, 86 Bishopgate Street, Leeds 1. Tel. Leeds 35649. (8011)

STORAGE SPACE is expensive, why store redundant and obsolete equipment? For fast and efficient clearance of all test gear, power supplies, PC boards, components, etc., regardless of condition or quantities. Call 01-771 9413. (8209)

SPOT CASH for all types test equipment, receivers, transmitters, valves, components, cable and surplus electronic scrap. M & B Radio, 86 Bishopgate Street, Leeds LS1 4BB. 0532 35649. (8789)

MINICOMPUTERS PERIPHERALS INSTRUMENTATION

For fastest, better CASH offer
Phone:

CHILTMead LTD.
Reading (0734) 586419

EQUIPMENT WANTED

TO ALL MANUFACTURERS AND WHOLESALERS IN THE ELECTRONIC RADIO AND TV FIELD

BROADFIELDS & MAYCO DISPOSALS

will pay you top prices for any large stocks of surplus or redundant components which you may wish to clear. We will call anywhere in the United Kingdom.

21 LODGE LANE
NORTH FINCHLEY, LONDON N12 8JG
Telephone Nos. 01-445 0749/445 2713
After office hours 958 7824

A.R. Sinclair

Electronic Stockholders
Stevenage 812193

We purchase all types of Mechanical and Electronic Equipment and Surplus stocks.

(8189)

BOOKS

THE STORY OF RADIO by W. M. Dalton, M.I.E.R.E. Authentic, nostalgic, readable. Volume I. How Radio Began. From electrics to radio 1914. Volume II. Every One An Amateur 1920/26, constructors & BBC. Volume III. The World Starts to Listen 1926/30. Receivers, transmitters, talkies, television. Each volume £4.50 p&p 50p. Adam Hilger Ltd., Techno House, Redcliffe Way, Bristol BS1 6NX. (9014)

COURSES

SERVICES

Don't keep it to yourself

We need your knowledge and experience

With sound practical experience and the necessary qualifications - degree, diploma, professional qualifications, HND, HNC, FTC, etc., depending on your specialisation - you can train as a lecturer in Further and Higher Education. A one-year grant-aided course will prepare you to teach in one of the following areas:

- Agriculture & Horticulture ● Business Studies ● Catering & Allied Subjects ● Clothing & Fashion ● Construction ● Education for the Disadvantaged ● Engineering ● English ● Languages ● Liberal Studies ● Nautical Studies ● Nursing & Health Studies ● Management ● Mathematics ● Painting and Decorating ● Printing & Graphic Arts ● Sciences ● Social Work

For further details, either phone or send the coupon to any of the following colleges:-
Bolton College of Education (Technical), Chadwick Street, Bolton BL2 1JW.
Tel: Bolton 22132.

Garnett College, Downshire House, Roehampton Lane, London SW15 4HR.
Tel: 01-789 6533.

The Polytechnic, Huddersfield, Holly Bank Road, Lindley, Huddersfield HD3 3BP.
Tel: Huddersfield 25611.

Wolverhampton Polytechnic, Faculty of Education, Compton Road West, Wolverhampton, WV3 9DX. Tel: Wolverhampton 24286.

Please send further details and an application form for a one-year course to train as a lecturer or apply by letter quoting the reference number as shown below.

NAME _____

ADDRESS _____

(8941)

REF. WW2

CAPACITY AVAILABLE

I.H.S. SYSTEMS

Due to expansion of our manufacturing facilities we are able to undertake assembly and testing of circuit boards or complete units in addition to contract development.

We can produce, test and calibrate to a high standard digital analogue and RF equipment in batches of tens to thousands.

Telephone to arrange for one of our engineers to call and discuss your requirements, or send full details for a prompt quotation.

TEL. 01-253 4562

or reply to Box No. WW 8237
(8237)

COIL WINDING

Large or small
PRODUCTION RUNS

AIRTRONICS LTD

GARDNER INDUSTRIAL ESTATE
KENT HOUSE LANE
BECKENHAM KENT BR3 1UG
01-659 1147

8936

Wind your own coils

**Short runs,
Long runs,
One type,
Many types,
Simple,
Complex.**

You name it



**will help you
wind it**

**AVO LIMITED Archcliffe Road,
Dover, Kent, CT 17 9EN.
Tel: 0304 202620 Telex: 96283**

8915

SKILLED HAND assembly, one-offs and small batch runs. — I. G. Bowman, 59 Fowey Avenue, Torquay, S. Devon. (9000)

Specialised PCB Service

- Layouts · Photography · Drilling
- Roller Tinning · Gold Plating
- Legend Printing · Profiling
- Special quick prototype service

Crofton Electronics Limited
35 Grosvenor Road, Twickenham
Middlesex - Tel. 01-891 1923

8210

HIGHWAY ELECTRONICS. Logic design, PCB artwork, assembly, testing, custom built electronics, Unit 112, Springvale Ind. Estate, Cwmbran, Gwent NP44 5BG. Telephone Cwmbran (06333) 68042.

(8347)

PCB ARTWORK DESIGN SERVICE with component notation masters and assembly drawings. PADS Electrical Ltd, 01-850 6516, 45 Southwood Road, New Eltham SE9. (7905)

EDUCATIONAL

C AND G EXAM

Make sure you succeed with an ICS home study course for C and G Electrical Installation Work and Technicians. Radio/TV/Electronics Technicians. Telecomms Technicians and Radio Amateurs.

COLOUR TV SERVICING

Make the most of the current boom! Learn the techniques of servicing Colour and Mono TV sets through new home study courses, approved by leading manufacturers.

TECHNICAL TRAINING

Home study courses in Electronics and Electrical Engineering, Maintenance, Radio, TV, Audio, Computer Engineering and Programming. Also self-build radio kits. Get the qualifications you need to succeed. Free details from:

International Correspondence Schools, Dept. 280P, Intertex House, London SW8 4UJ. Or phone 01-822 9911.

(8970)

TEST EQUIPMENT

We are disposing of a considerable amount of good quality test gear including Tektronic scopes at silly prices.

* Ring Derek Pattinson now and discuss your requirements.

Crofton Electronics Ltd.
35 Grosvenor Road,
Twickenham, Middlesex.
Tel. 01-891 1923 (8211)

PRECISION SHEET METAL work. chassis, panels, etc., steel, stainless or aluminium, long/short runs, good deliveries. EES Ltd., Clifford Rd Monk's Road, Exeter 56280 36489. (8060)

DESIGN AND DEVELOPMENT, competent engineering effort available for all aspects of electronic design. Single circuits or complete systems, prototype to production run. E.I.A., 80 Wheatland Lane, Wallasey, Merseyside, 051-639 9122. (8615)

DESIGN SERVICE. Electronic Design Development and Production Service available in Digital and Analogue Instruments, RF Transmitters and Receivers for control of any function at any range. Telemetry, Video Transmitters and Monitors, Motorised Pan and Tilt Heads etc. Suppliers to the Industry for 16 years. Phone or write Mr. Falkner, R.C.S. Electronics, 6 Wolsey Road, Ashford, Middlesex. Phone Ashford 53661. (8341)

W.K.F. ELECTRONICS
(R.P.C.B.S. Ltd.)
THE CIRCUIT BOARD SPECIALISTS - UNIVERSAL SUPPLIERS

Contractors for: P.C.B. Production, Contract Drilling, Electroplating, Laminate Cutting.
Services for: Master Artwork Preparation, Process Photography, Circuit Diagrams, Layouts & Legends.
Consultants for: Instrument Engineering, Automatic Control & Applications.

Do-it-Yourself Won't Do: Today's assemblies demand close tolerances.
Goodbye to the Long Wait: 3 to 7 Day Prototype P.C.B. Production Service.
Quotations: By Return. **Guaranteed Quality** on every process.
Short or Long Term Production now acceptable from 1 to 10,000 units.

We Universally Distribute: Laminate, Carbide Drill Bits & Routers, Process Chemicals (any), Pre-sensitized Laminate, Drilling Machines (Manual, Multi-spindle, N.C./C.N.C. Control), Graphic Art Drafting materials & aids.

We Manufacture to Specification: Quality Circuit Boards (Single or Double Sided with any finish). Due to expansion we now have space available for prototype or long term production.

For Quotations: Submit Copy Masters, Roughs, Circuit or Sample units for costing.


To:
W.K.F. ELECTRONICS
FLEET HOUSE, WELBECK STREET
WHITWELL, WORKSOP, NOTTS.
TEL. WORKSOP (0909) 720695
TELEX: 547616
Telephone Quotations: Ask for pricing.

NOTICE TO OTHER MANUFACTURERS

IS YOUR DRILLING / ROUTING DEPARTMENT A BOTTLENECK?
IF SO TRY OUR SERVICE FOR DRILLING AND ROUTING

THE RATES ARE VERY REASONABLE AND THE FAST SERVICE WILL ENSURE THAT YOUR CUSTOMERS' DELIVERIES ARE MET

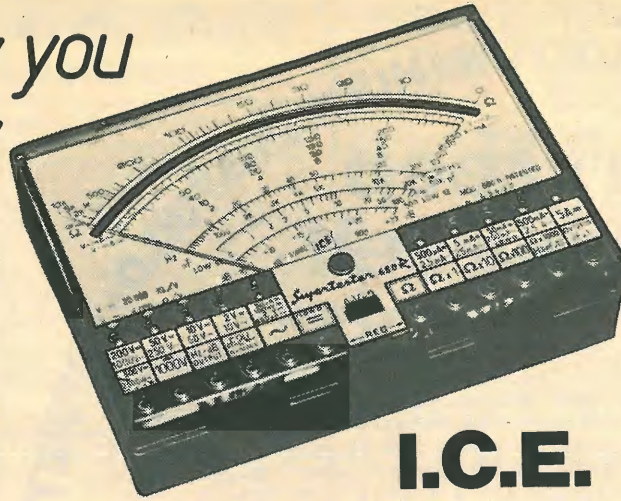Here's why you should buy an I.C.E. instead of just any multimeter



I.C.E.

WW-106 FOR FURTHER DETAILS

- * Best Value for money.
- * Used by professional engineers, D.I.Y. enthusiasts, hobbyists, service engineers.
- * World-wide proven reliability.
- * Low servicing costs.
- * 20K/volt sensitivity and high accuracy.
- * Large mirror scale meter.
- * Fully protected against overload.
- * Large range of inexpensive accessories.
- * 12 month warranty, backed by a full after sales service at E.B.Sole U.K. Distributors.

Prices from £16.60 — £32.00 + VAT
Send for full colour leaflet and prices on whole range including accessories.

ELECTRONIC BROKERS LIMITED

49-53 Pancras Road, London NW1 2QB.
Tel: 01-837 7781. Telex: 298694.

INDEX TO ADVERTISERS

Appointments Vacant Advertisements appear on pages 129-151

PAGE	PAGE	PAGE
Acorn Computer 113	Ferranti 11, 41, 112	Patrick, J. B. 116
Acoustical Mfg. Co. Ltd. 4	Future Film Developments 39	Powell, T. 108
AEL Crystals 32	Fylde Electronic Labs Ltd. 22	Powertran Electronics 106, 107
AMP of Great Britain 8, 9	GEC M-O Valve 16	Precision Petite Ltd. 109
Ambit International 35, 40, 41	G.R. Electronics 119	Pye Unicam 5, 13
Antex 63	Greenwood Electronics Ltd. 25	Quarndon Electronics (Semiconductors) Ltd. 101
Aspen Electronics Ltd 30	Harmsworth Townley & Co. Ltd. 24	Radford Lab. Insts. Ltd. 108
Astra-Pak 120	Harris Electronics (London) Ltd. 16, 24	Radio Components Specialists 115
Audix Ltd 32	Hart Electronics 108	Radio Shack 109
Avo Ltd 16, 64	Hi-Fi Y/Book 39	Radio Supplies Comps 10
Bang & Ollufson 95	Hivol Connectors 118	Ralfe, P. 104
Barr & Stroud Ltd. 42	H. L. Audio 33	R.C.S. Electronics 98
Barrie Electronics Ltd 117	I.L.P. Electronics Ltd. 17	R.S.T. Valves 128
Bell & Howell 2, 14, 15	Industrial Tape Applications 22, 37	Sabtronic (UK) Ltd. 36
Beyer Dynamics (GB) Ltd 20	Integrex Ltd. 96, 97	Sandwell Plant Ltd. 35
Bib Hi-Fi Accessories Cover iv	Interface Quartz Devices Ltd. 30	Scopex Instruments Ltd. 31
Bi-Pak Semiconductors Ltd. 102, 103	Jayen Developments 116	Sescom 40
Boss Industrial Mouldings Ltd. 19	JPS Associates 39	Service Trading Co. 111
Brensal Electronics Ltd. 119	K. & A. Distributors 110	Servo & Electronics Sales Ltd. 100
Bulgin Electronics Soundex Ltd. 22	Keithley Instruments Ltd. 112	Shure Electronics Ltd. Cover ii
Bull, J. 99	KGM Electronics Ltd. 10	Sintel 117
Butterworth & Co. (Pub.) 120	Kirkham Amplifier 6	SME Ltd. 23
Cambridge Learning 21	Labgear Ltd. 38	Southern Electronics 34
Carston Electronics Ltd. 29	Langrex 128	Sota Communication System 109
Carter Associates 36	Lascar Electronics 100	Special Products Ltd. 34
Catronics 117	Levell Electronics Ltd. 3	Sugden, J. E. & Co. Ltd. 32
CEC Corporation 20	London Instrument Repair Centre 109	Surrey Electronics Ltd. 98
Chiltmead Ltd. 119	Low Electronics Ltd. 27	Swanley Electronics Ltd. 98
Circards No. 3 105	MacInnes Laboratories Ltd. 12	Technomatic Ltd. 110
Citadel Products Ltd. 32	Maplin Electronic Supplies 7	Teleradio Hi-Fi 41
C. N. Stevenson 34	Marco Trading 41	Transtel Communications 38
Colomor (Electronics) Ltd. 127	Marconi Instruments Ltd. Cover ii	Valradio Ltd. 38
Clarke Smith (Vortexion) 40	Marshall, A. & Sons (London) Ltd. 104	Vero Electronics Ltd. 27
Continental Specialities 18	Martin Associates 30	Videotime Products 124
Crimson Elektrik 28	Medelec 24	Viewdata 35
CT Electronics 114, 124	Milward, G. F. 110	Watford Electronics 25
Datong 39	Multicore Solders Ltd. Cover iv	West Hyde Developments Ltd. 98
Display Electronics 126	MHZ Electronics 28	West London Direct Supplies 100
ECM (K9 Comps) 118	Nevenco 118	Wilmot Breeden Elec. Ltd. 116
Electro-Tech 124	Olson Electronics Ltd. 12	Wingrove & Rogers Ltd. 127
Electronic Brokers Ltd. 121, 122, 123, 152	OMB Electronics 27	Wilmslow Audio 26
Electronic Brokers Ltd. (Second User Computer Div.) 125		Z. & I. Aero Services Ltd. 35, 100
Electrovalue 119		

OVERSEAS ADVERTISEMENT AGENTS:

France: M. D. Soubeyran, Compagnie Francaise D'Editions, Division Internationale, 40 Rue du Colisee, Paris 8e Telephone 225-77-50 — Telex 280274.

Hungary: Mrs. Edit Bajusz, Hungexpo Advertising Agency, Budapest XIV, Varosliget Telephone: 225 008 — Telex: Budapest 22-4525 INTFOIRE.

Italy: Sig. C. Epis, Etas-Kompass, S.p.a. — Servizio Estero, Via Mantegna 6, 20154 Milan. Telephone: 347051 — Telex: 37342 Kompass.


Japan: Mr. Inatsuki, Trade Media — IBPA (Japan), B.212, Azabu Heights, 1-5-10 Roppongi, Minato-ku, Tokyo 106. Telephone: (03) 585-0581.

UNITED States of America: Ray Barnes, IPC Business Press, 205 East 42nd Street, New York, NY 10017 — Telephone: (212) 689 5961 — Telex: 421710. Mr. Jack Farley Jnr., The Farley Co., Suite 1584, 35 East Wacker Drive, Chicago, Illinois 60601 — Telephone: (312) 6 3074.

Mr. Victor A. Jauch, Elmatex International, P.O. Box 34607, Los Angeles, Calif. 90034, USA — Telephone (213) 821-8581 — Telex 18-1059.

Mr. Jack Mentel, The Farley Co., Suite 650, Ranna Building, Cleveland, Ohio 44115 — Telephone: (216) 621 1919. Mr. Ray Rickles, Ray Rickles & Co., P.O. Box 2008, Miami Beach, Florida 33140 — Telephone: (305) 532 7301. Mr. Tim Parks, Ray Rickles & Co., 3116 Maple Drive N.E. Atlanta, Georgia 30305 Telephone: (404) 237 7432. Mike Loughlin, IPC Business Press, 15055 Memorial, Ste 119, Houston, Texas 77079 — Telephone (713) 783 8673.

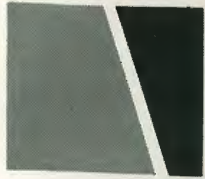Canada: Mr. Colin H. MacCulloch, International Advertising Consultants Ltd., 915 Carlton Tower, 2 Carlton Street, Toronto 2 — Telephone: (416) 364 2269. *Also subscription agents.




fact: you can choose your microphone to enhance your sound system.

Shure makes microphones for every imaginable use. Like musical instruments, each different type of Shure microphone has a distinctive "sound," or physical characteristic that optimizes it for particular applications, voices, or effects. Take, for example, the Shure SM58 and SM59 microphones:

SM59

**Mellow, smooth,
silent...**


The SM59 is a relatively new, dynamic cardioid microphone. Yet it is already widely accepted for critical studio productions. In fact, you'll see it most often where accurate, natural sound quality is a major consideration. This revolutionary cardioid microphone has an exceptionally flat frequency response and neutral sound that reproduces exactly what it hears. It's designed to give good bass response when miking at a distance. Remarkably rugged—it's built to shrug off rough handling. And, it is superb in rejecting mechanical stand noise such as floor and desk vibrations because of a unique, patented built-in shock mount. It also features a special hum-bucking coil for superior noise reduction!

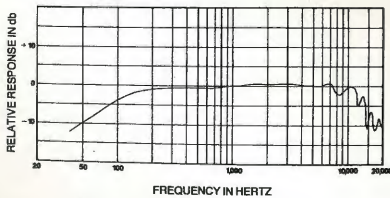

SM58

**Crisp, bright
"abuse proof"**

Probably the most widely used on-stage, hand-held cardioid dynamic microphone. The SM58 dynamic microphone is preferred for its punch in live vocal applications... especially where close-up miking is important. It is THE world-standard professional stage microphone with the distinctive Shure upper mid-range presence peak for an intelligible, lively sound. World-renowned for its ability to withstand the kind of abuse that would destroy many other microphones. Designed to minimize the boominess you'd expect from close miking. Rugged, efficient spherical windscreen eliminates pops. The first choice among rock, pop, R & B, country, gospel, and jazz vocalists.

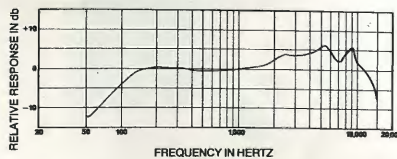

professional microphones...by



Shure Electronics Limited, Eccleston Road, Maidstone ME 15 6AU—Telephone: Maidstone (0622) 59881



gets it together...

Toolbox Reels

Three solders that cover all your electrical applications.

40/60 Tin/Lead **Size 3** £2.16 each
 60/40 Tin/Lead **Size 10** £2.38 each
 Savbit Alloy/ **Size 12** £2.29 each



Soldering Flux Paste 'Ersin'

A fast non-corrosive, rosin flux for general and electrical soldering.

Use in conjunction with 'Ersin' Multicore solders.

Size RF10 48p inc. VAT

'Arax' Use in conjunction with 'Arax' Multicore solder for general metal fabrication.

Size AF14 48p inc. VAT

Multicore Desoldering Wick

For desoldering component leads from PCB's or removing solder from virtually any joints.

Size AB10 97p inc. VAT



Wire Strippers and Cutters

Easily adjustable for most sizes of flex and cable.

Fitted with extra strong spring for automatic opening. Easy grip handles and handle locking device.

Ref 9
£1.15 inc. VAT



Handy Dispensers (All prices inc. V.A.T.)

- Size 19A** All electrical work 63p
- Size PC115** For small components 69p
- Size SV130** Use with copper bits and wires £1.08
- Size AR140** Metal repairs 86p
- Size AL150** Aluminium 76p
- Size SS160** Stainless Steel £1.08

Savbit Dispenser

For radio, TV and similar work. Reduces copper erosion.

Size 5 58p inc. VAT



Emergency Solder

Self fluxing, tin/lead solder tape that melts with a match. For electrical and non-electrical applications. **Size ES36** 39p inc. VAT

Econopak

A reel of 1.2mm 'Ersin' Multicore solder for general electrical use. **Size 13A** £2.59 inc. VAT

A reel of 3mm 'Arax' Multicore solder for general non-electrical use. **Size 16A** £2.59 inc. VAT



Solder Cream

Tacky mixture of solder powder and correct percentage of flux for difficult to reach areas.

Electrical/Electronic ('Ersin' Flux) **Size BCR10** £1.08
 Metal joining ('Arax' flux) **Size BCA14** £1.08

Stainless Steel & Jewellery ('Arax Flux) **Size BCA16** £1.38
 (All prices inc. V.A.T.)



... Bib® keeps it playing

Cassette Editing Kit

Make editing simple with the Bib splicer, tape cutter and splicing tape. Standard pack with 6.3mm adaptor. **Ref 56** £1.99 inc. VAT

In permanent storage case with tape piercer and winder remover. **Ref 98** £2.70 inc. VAT

USA Pat. No. 4067563 (splicer)
 Brit. Pat. No. 1507583 (splicer)
 Brit. Pat. No. 1258280 (method of splicing)



Groov-Kleen

Parallel tracking, it cleans whilst disc plays. Engineered in chromed steel and with two bases to suit all decks. Pat. Pending

Ref 101A Brit. Reg. Des. No. 982790
 £3.97 inc. VAT U.S.A. Reg. Des. No. 247622



Stylus Cleaning Kit

Unique cleaner in chromed steel with brush tip, cover and built in magnifying inspection mirror. Complete with anti-static fluid in permanent storage box. **Ref 112** £3.97 inc. VAT.

Groov-Stat Electronic 3000

This improved static reducer, powered by one small battery, neutralises record surface static in seconds. Comes in permanent storage box with FREE static tester.


Ref 3000 £9.98 inc. VAT
 (Pat. pending)



Record Valet

Soft bristles on leading edge remove dust and humid velvet pad collects particles. This advanced cleaner is engineered in chromed steel and is supplied with dust cover in permanent storage box.

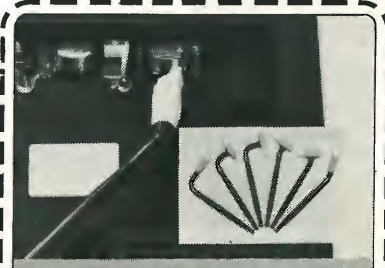Ref 110 Pat. Pending
 £5.49 inc. VAT Reg. Des. No. 981808



Tape Head Maintenance Kit

Everything necessary for cleaning heads, capstan and pinch wheel on all types of recorders.

Cleaning and polishing pads, cleaning liquid and brush inspection mirror included. **Standard Pack Ref 25** £1.99 inc. VAT
Permanent Storage Box with cleaning cloth
 Brit. Pat. No. 1485069 **Ref 99** £2.70 inc. VAT



In difficulty send direct, plus 20p P & P. Send S.A.E. for free copy of colour catalogue detailing complete range. **Bib Hi-Fi Accessories Limited, Kelsey House, Wood Lane End, Hemel Hempstead, Herts., HP2 4RQ.**