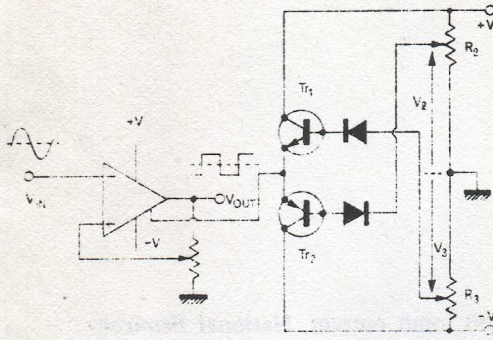


### Op-amp comparator/Schmitt (bipolar clamping)



#### Circuit description

Operational amplifiers used as comparators (or as level-sensing circuits when positive feedback is used for hysteresis) have output swings which vary with temperature and from unit to unit. Some amplifiers have access to the drive point of the output stage and this point may be clamped at selected positive and negative potentials by zener diodes or suitably biased transistors as shown. Clipping is at much lower current levels than if attempted directly at the output. Variable resistors  $R_2$  and  $R_3$  set the positive and negative clamping levels,  $R_1$  determines hysteresis at the clamping levels. Diodes provide base-emitter breakdown protection.

For  $0 < V_2 < 3V$   
 $V_{out}^+ = V_2 + 3V_{be}$   
 $V_{clamp}^+ = V_{out}^+ - V_{be}$   
 For  $-3V < V_3 < 0$   
 $V_{out}^- = V_3 - 3V_{be}$   
 $V_{clamp}^- = V_{out}^- + V_{be}$

**Typical performance**  
 Supplies:  $\pm 5V$ ; IC: 748  
 Tr<sub>1</sub>: BC125; Tr<sub>2</sub>: BC126  
 Diodes: 1N914  
 $R_1, R_2, R_3$ : 10k $\Omega$   
 With  $V_{in} = 1V$  pk-pk  
 at 10kHz,  $V_{out}^{\pm}$  adjustable  
 $\pm 1.6$  to  $\pm 4.4V$ .  
 Rise and fall times  
 $\approx 700ns$ .  
 Supply currents  
 $\pm 2.5mA$   
 Max  $V_{in} = \pm V$ .


#### Component changes

Useful range of supplies:  $\pm 5$  to  $\pm 18V$ .  
 Transistors: general-purpose silicon types.  
 Useful range of  $R_1$ : 1 to 100k $\Omega$ .  
 Useful range of  $R_2, R_3$ : 1k $\Omega$  (increases supply current drawn) to 100k $\Omega$  (produces error in  $V_2$  and  $V_3$  unless base current loading is reduced by use of higher-gain transistors).  
 Useful frequency range: d.c. to approx. 160kHz. If a higher-speed operational amplifier is used, transistors may limit the frequency response unless high-speed versions are used.  
 Diodes may be omitted for low supply voltages and/or high reverse base-emitter breakdown transistors. Base-emitter junctions may receive supply voltage at extreme settings of  $R_2$  and  $R_3$ .

# Wireless World Circard

## Series 2: Comparators & Schmitts-2

### Basic Schmitt circuit

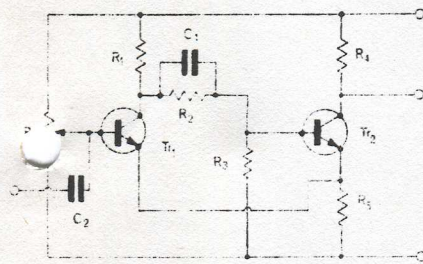


#### Circuit description

Emitter coupling between Tr<sub>1</sub> and Tr<sub>2</sub> introduces positive feedback causing a regenerative switching action into one of two states. When  $V_{in}$  is below threshold level  $V_1$ , Tr<sub>1</sub> is non-conducting and Tr<sub>2</sub> conducts, the base voltage being determined by  $R_1, R_2$  and  $R_3$ . The emitter potential is then well-defined. As input voltage exceeds  $V_1$ , Tr<sub>1</sub> begins to conduct, reducing its collector potential, and hence that of the base and emitter of Tr<sub>2</sub>. This drop in potential is fed back to the emitter of Tr<sub>1</sub>, thus further increasing the conduction of Tr<sub>1</sub> until Tr<sub>1</sub> is on and Tr<sub>2</sub> is off. A similar regenerative action occurs when the input voltage is reduced below the threshold level  $V_2$ , returning the circuit to its original condition. A typical input-output voltage characteristic is shown above, where  $V_1 - V_2$  is termed the hysteresis or backlash of the circuit.

#### Component data


Transistors: BC125  
 Supply: +5V  
 $R_1, R_4$ : 4.7k $\Omega$   
 $R_2, R_3$ : 2.2k $\Omega$   
 $R_5$ : 1k $\Omega \pm 5\%$   
 $R_6$ : 4.7k $\Omega$  pot.  
 $C_1$ : 100pF (speed-up)  
 $C_2$ : 2.2 $\mu F$   
 Signal level from 500- $\Omega$   
 source: 2V pk-pk.  
 Output swing: 1.5 to 5V  
 up to 100kHz.

#### Transfer characteristic

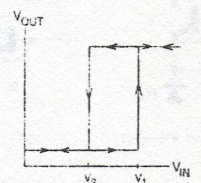
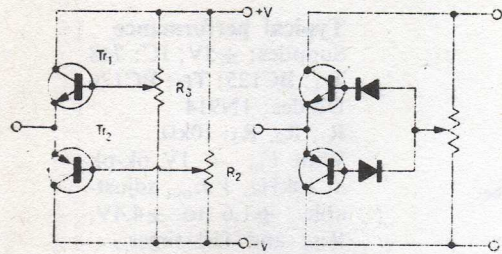
#### Component changes

Resistor  $R_6$  permits adjustment of threshold level  $V_1$ . Useful ratio  $R_2/R_3$  is in the range 0.5 to 2.0, giving control of trip level and hysteresis range of 0.2 to 0.8V.  
 Useful  $C_1$  range: 1nF to 100pF. Optimum 100pF at a source frequency of 1MHz.  
 Rise time: 150 to 100ns using oscilloscope probe.  
 For  $R_4 = 1k\Omega, R_1 = 100\Omega, R_2/R_3 = 0.5$ , output swing at 1MHz is 3 to 5V, for load capacitance up to 33pF.



### Circuit modifications

- Diodes can be placed in series with the emitters of the transistors. This still provides base-emitter breakdown protection but the diodes then carry the larger emitter currents producing larger diode p.d.s.

- $R_2$  and  $R_3$  could be connected as shown on left allowing the base potentials of both  $Tr_1$  and  $Tr_2$  to be set positive or negative independently. It would then be possible for  $Tr_1$  base to be positive and  $Tr_2$  base to be negative, which would allow excessive conduction in  $Tr_1$ ,  $Tr_2$ .

- Fig. on right shows a modification which allows the mean level of  $V_{out}$  to be set positive or negative by the potentiometer with its peak-to-peak value still determined by  $\pm 3V_{be}$ .

### Further reading

IC op.amp beats fets on input current, National Semiconductor application note AN-29, 1969, p.15.


Clayton, G. B., Operational Amplifiers, Butterworth 1971, pp.145-9.

Applications Manual for Operational Amplifiers Philbrick/Nexus Research, 1968, pp.59 & 101.

### Cross references

Series 2, cards 4 & 6.

© 1972 IPC Business Press Ltd.

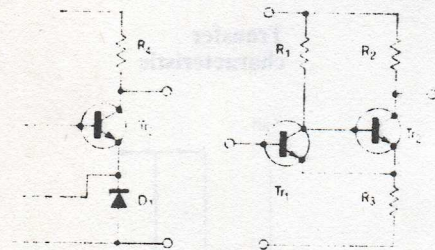

### Circuit modifications

The emitter resistor may be replaced by a zener diode (left). This means the emitter potential variation is less dependent on current flow through each transistor. Typical performance:

$V_{CC} = 10V$ , D: 5.1V zener diode.  $R_1: 680\Omega$ ,  $R_2, R_4: 1.5k\Omega$ ,  $R_3: 3.3k\Omega$ . Drive signal: 2V pk-pk: output swing: 5.2 to 10V. Hysteresis: 110mV.

On right, useful range of  $R_3$ : 10 to 500 $\Omega$ . Useful range of  $R_2$  1 to 2k $\Omega$ .  $R_1: 1k\Omega$ . Typical performance:

$V_{CC} = 5V$ ,  $R_E = 10\Omega$ ,  $R_1 = R_2 = 1k\Omega$ . Minimum sinusoidal drive signal at 100kHz: 2V pk-pk. Output swing: 0.8 to 5V.

Frequency may be increased to 300kHz if drive voltage is increased to 4V pk-pk.

### Reference

1. Zero-hysteresis Schmitt trigger, in Electronic Circuit Design Handbook, 4th edition. 1971 p.108.

### Further reading

Crump, A. E., Design of Schmitt trigger circuits, *Wireless World*, vol. 73, 1967, pp.122-7 and 175-7.


Circuit Consultant's Casebook, Hemingway, T. K., Business Books, 1970, pp.129-37.

### Cross references

Series 2, cards 3, 7 & 8.

© 1972 IPC Business Press Ltd.

### Complementary m.o.s. Schmitt

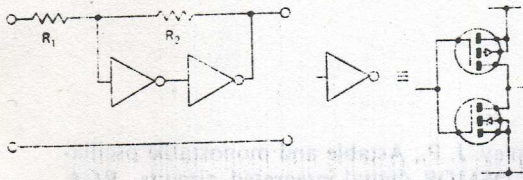

#### Circuit description

Two c.m.o.s. inverters are cascaded with positive feedback defined by ratio  $R_2/R_1$ . Provided this ratio is less than the forward gain in the inverters' linear region, switching follows the appropriate input changes. Output swing approaches supply lines and current from source is small as very high output resistance of inverter allows  $R_1, R_2$  to be large. With small hysteresis switching levels are near supply mid-point.

IC: CD4007AE (connected as triple inverter)  
 Supply: 10V  
 $R_1$ : 1M $\Omega$   
 $R_2$ : 10M $\Omega$   
 $V_1$ : 5.9V  
 $V_2$ : 5.1V  
 Output swing: 10V  
 Input current:  $\pm 0.5\mu\text{A}$


#### Component changes

- Any combination of inverters, gates or buffers giving voltage gain  $> +1$  may be used. Examples: RCA CD4001AE, Motorola MC14001 quad 2-input NOR gates; CD4009AE hex buffer inverters.
- Supply voltage +3 to +15V (special versions down to 1.5V).
- $R_2/R_1$  may be varied between 1 and 100. At upper end of range positive feedback may be too little to guarantee switching. At lower end hysteresis is comparable to supply voltage.
- To minimize capacitive effects/hum pickup reduce  $R_1, R_2$  to  $\sim 10\text{k}\Omega$ . Lower values reduce output swing and accuracy of hysteresis, while increasing current from source.

# Wireless World Circard

## Series 2: Comparators & Schmitts-4

### High-power comparator/Schmitt

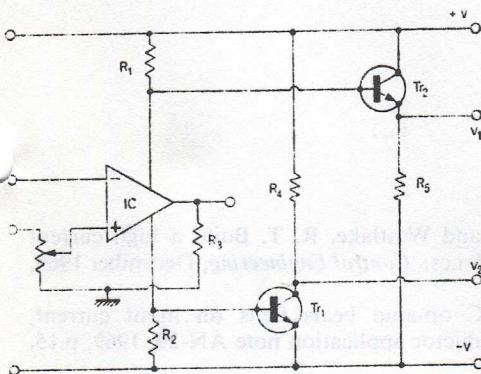

#### Circuit description

The output swing of standard op-amps is significantly less than the supply voltage, particularly when the latter is low. The current available is also low. With some op-amps the current in the positive supply lead is large when the output voltage is positive and the output current is large but is small when the output voltage is negative. The negative supply current behaves similarly. The change in supply current as the input signal varies can be used to drive following transistors which may supply currents of several hundred milliamperes at a voltage very close to the supply voltage.


#### Performance data

IC: 741; Supplies  $\pm 5\text{V}$   
 $\text{Tr}_1$ : BFR41,  $\text{Tr}_2$ : BFR81  
 $R_1, R_2$ : 220 $\Omega$ ,  $R_3$ : 270 $\Omega$   
 $R_4, R_5$ : 68 $\Omega$ , 3W  
 Minimum  $V_{in} = 800\text{mV}$  pk-pk.  
 Max.  $\pm V = \pm 7\text{V}$ , limited by  $R_4$  and  $R_5$ .

With maximum permissible sinusoidal input of 8V pk-pk,  $V_1$  and  $V_2$  are both square waves swinging between -5 and +4.8V, and -5 and +5V respectively.  $V_1$  and  $V_2$  are in-phase while the currents in  $R_4$  and  $R_5$  are in anti-phase. Max. frequency 1kHz—waveform squareness is lost at higher frequencies.
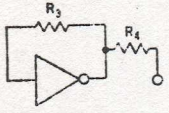
#### Component changes

- To maximize output voltage swings  $\text{Tr}_1$  and  $\text{Tr}_2$  must be driven into saturation i.e. base currents of 5 to 10% of load current are required. Reducing  $R_3$  will increase base current.
- Resistors  $R_1$  and  $R_2$  may need to be reduced for some op-amps having larger off-load currents (180 $\Omega$  was found satisfactory for a 748).



IC: CD4077AF (complementary m.o.s. Schmitt)  
 Supply: 10V  
 R1: 1MΩ  
 R2: 10MΩ  
 R3: 20V  
 R4: 21V  
 Output swing: 10V

**Circuit modifications**

- Buffer input with third inverter/gate increasing input resistance (typical input current ~ 10pA). Resistor R<sub>1</sub> may be dispensed with, the output resistance of buffer taking its place, with R<sub>2</sub> reduced to range 1 to 30kΩ. Resulting hysteresis in range 2.5 to 0.2V.
- Use spare inverter self-biased by large resistor (~ 10MΩ) (see Fig.) to bias input terminal of first inverter via second resistor (~ 10MΩ). This sets mean potential near to centre of linear region, assuming well-matched inverters. Signals may now be a.c. coupled and 200mV pk-pk typically triggers circuit over a range of supply voltage and temperature with no adjustment of bias level.

**Further reading**


Dean, J. A. & Rupley, J. P., Astable and monostable oscillators using RCA COSMOS digital integrated circuits, RCA application note ICAN-6267.  
 Schmidt, B., Schmitt trigger design uses CMOS logic, *Electronic Design*, Vol. 20, 27 April 1972, p.72.

**Cross reference**

Series 2, cards 1, 2 & 8.

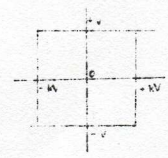**Circuit modifications**

The circuit can be altered to give a Schmitt characteristic with controllable hysteresis by connecting either  $V_1$  or  $V_2$  via the pot. shown to the non-inverting input of the op-amp. Using  $V_2$  we obtain the characteristic shown right in which  $k$  is the pot tapping and  $V$  the supply voltage (5V). This hysteresis is not dependent on the saturation level of the amplifier as it would be if the amplifier output were fed back. Hysteresis width is controllable up to about 0.1V of the pk-pk value of the input provided the input is kept below about 5V pk-pk.




**Further reading**

Campbell, D. L. and Westlake, R. T. Build a high current servoamplifier with i.c.s. *Control Engineering*, December 1969, p.91.  
 Widlar, R. J., IC op-amp beats f.e.t.s on input current, National Semiconductor application note AN-29, 1969, p.15.

**Cross references**

Series 2, card 9.

### Unijunction-equivalent Schmitt

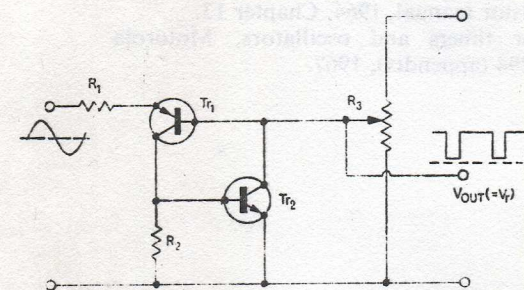

$$V_{in}(\text{on}) = V_r + (n+1)V_{be}(\text{on})$$

where  $n = R_1/R_2$

#### Typical performance

Supply: +5V  
 Tr<sub>1</sub>: BC126 Tr<sub>2</sub>: BC125  
 R<sub>1</sub>, R<sub>2</sub>: 1kΩ R<sub>3</sub>: 4.7kΩ  
 $V_{out}(\text{on}) = 0.04\text{V}$   
 $V_{out}(\text{off}) = V_r = 2.5\text{V}$   
 $V_{in}(\text{on}) = 3.8\text{V}$   
 $V_{in}(\text{off}) = 3.0\text{V}$   
 Supply current: 8mA (on), 1mA (off)

#### Circuit description

The transistors together have properties similar to those of a unijunction transistor. When  $V_{in}$  is low Tr<sub>1</sub> and Tr<sub>2</sub> do not conduct and  $V_r$  is defined by R<sub>3</sub>. For  $V_{in} \approx V_r + 1.3\text{V}$ , Tr<sub>1</sub> and Tr<sub>2</sub> begin to conduct, regenerative switching via Tr<sub>2</sub> clamping  $V_{out}$  close to 0V. Reversal of switching occurs when  $V_{in}$  falls. Significant current is drawn from the source unless a limiting resistor (R<sub>1</sub>) is included.


#### Component changes

Tr<sub>1</sub>: any general purpose p-n-p silicon transistor.  
 Tr<sub>2</sub>: any general purpose n-p-n silicon transistor.  
 Maximum useful frequency  $\approx 100\text{kHz}$ .  
 Range of  $V_r$  source resistance (seen by Tr<sub>1</sub> base): about 2.2kΩ to 33kΩ.  
 $R_1$  (max)  $\approx 3.3\text{k}\Omega$ . For large R<sub>1</sub> values  $V_r$  source resistance must be increased for rapid switching action. The output can only be lightly loaded with large  $V_r$  source resistance.

# Wireless World Circard

## Series 2: Comparators & Schmitts-6

### Variable hysteresis level detector

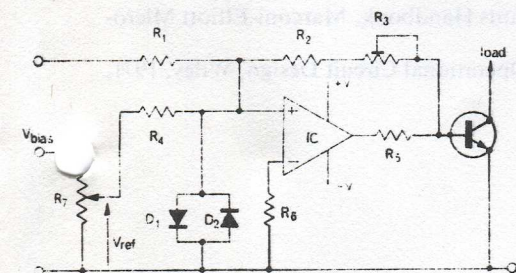

#### Circuit description

$V_{ref}$  adjusts the level at which the output switches without affecting hysteresis. Positive feedback path R<sub>2</sub> and R<sub>3</sub> provides hysteresis controllable by R<sub>3</sub>. Sensitivity can be modified by changing input resistance R<sub>1</sub>. Positive output swing is determined by the base-emitter voltage of the transistor and the negative output by the particular operational amplifier used. Diodes on the input provide breakdown protection of the op-amp against excessive input voltages.

#### Component data

Supplies:  $\pm 15\text{V}$   
 R<sub>1</sub>, R<sub>4</sub>: 2.2kΩ  
 R<sub>2</sub>: 100kΩ  
 R<sub>3</sub>: 100MΩ  
 R<sub>5</sub>: 3.3kΩ  
 R<sub>6</sub>: 1kΩ  
 R<sub>7</sub>: 1kΩ

D<sub>1</sub>, D<sub>2</sub>: general-purpose diodes.  
 IC: 741  
 Tr: ME4103 (in general determined by driving circuit)  
 All resistors  $\pm 5\%$ .

#### Component changes

IC: 748 or LM301A.  
 For  $V_{ref}$  of -1V to -14V, R<sub>3</sub> = 0, supplies:  $\pm 15\text{V}$ ;  
 hysteresis: 180mV  $\pm 2\%$ ;  
 trip level:  $V_{ref} + 200\text{mV}$ .  
 For  $V_{ref}$  of -1V to -4V, R<sub>3</sub> = 0, supplies:  $\pm 5\text{V}$ ;  
 hysteresis: 700mV  $\pm 5\%$ ;  
 trip level:  $V_{ref} + 100\text{mV}$ ;  
 Hysteresis: 10mV, R<sub>3</sub> = 1MΩ, supplies:  $\pm 10 \rightarrow \pm 15\text{V}$ ; trip level:  $V_{ref} + 100\text{mV}$ .  
 In general, hysteresis may be further increased by reducing R<sub>2</sub> + R<sub>3</sub>.

### Circuit modifications

If the input voltage is fed directly to  $T_1$  emitter the circuit may be used to clamp it to a low level (about 0.7V with a 5V supply) when it exceeds some maximum permissible level. For example,  $V_r$  could be the output from a voltage regulator and  $V_{in}$  its input voltage. If  $V_{in}$  (regulator input) rises excessively the circuit will rapidly clamp the regulator input to a low value protecting the regulator and the circuitry it supplies during the time taken for the supply fuse to blow. The transistors require a current rating greater than the supply peak current on s.c. loading.  $R_2$  and  $R_3$  may then need to be reduced.

### Further reading

General Electric transistor manual, 1964, Chapter 13.  
Unijunction transistor timers and oscillators, Motorola application note AN-294 (appendix), 1967.

### Cross references

Series 2, cards 2 & 12.

© 1972 IPC Business Press Ltd.

### Circuit modifications

- If output voltage swing required at lower currents,  $T_1$  may be omitted and  $R_5$  reduced to zero. Hysteresis is then controlled by op-amp output swing.
- Alternative methods of defining output swing and hence hysteresis include series back-to-back zener diode or diode limiting circuits.
- For higher speed operation, IC may be any comparator.
- For higher output currents,  $T_1$  may be replaced by a Darlington pair. If only an indication of output state is required, most op-amps can deliver sufficient current to drive small light-emitting diodes.

### Further reading


Linear Integrated Circuits Handbook, Marconi-Elliott Microelectronics, pp.167/8.  
Smith, J. I., Modern Operational Circuit Design, Wiley, 1971, pp.186/7.

### Cross references

Series 2, cards 9-11.

© 1972 IPC Business Press Ltd.

### High-speed Schmitt circuit

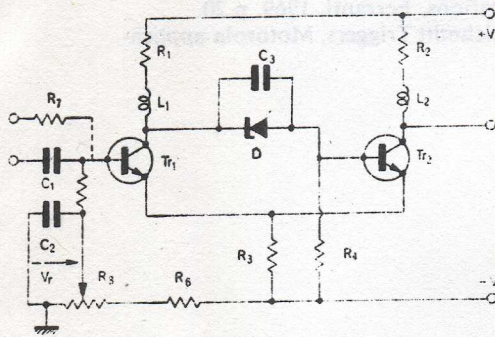

#### Circuit description

For maximum speed, Schmitt trigger circuits should operate with the transistors out of saturation at all times. A zener diode in the bias network can assist this. In this circuit, current levels are higher than in the basic Schmitt to maximize gain-bandwidth product. The inductors compensate for capacitive loading to optimize rise time. The upper and lower thresholds are negative and the hysteresis is variable but is not independent of the threshold levels.

#### Typical performance


Supplies:  $\pm 5V$   
 Tr<sub>1</sub>, Tr<sub>2</sub>: BSX20  
 D<sub>1</sub> = BZX55, C3V9  
 R<sub>1</sub>, R<sub>2</sub>, R<sub>3</sub>, R<sub>5</sub>, R<sub>7</sub>: 100 $\Omega$   
 R<sub>4</sub> 10k $\Omega$ .  
 R<sub>6</sub>: 3.3k $\Omega$ ; R<sub>8</sub>: 1k $\Omega$   
 C<sub>1</sub>, C<sub>2</sub>: 0.1 $\mu F$ ; C<sub>3</sub>: 27pF  
 L<sub>1</sub>, L<sub>2</sub>: 0

$V_T = -1.0V$ ;  $V_{in}(Tr_{2on}) = -2.02V$ ;  $V_{in}(Tr_{2off}) = -0.31V$   
 Hysteresis: 1.71V  
 $V_{out(on)} = 0.2V$   
 Supply current  
 +40mA, -50mA Tr<sub>2off</sub>  
 +43mA, -51.5mA Tr<sub>2on</sub>

#### Component changes

Useful range of  $V_T$ : 0 to -1.47V  
 Corresponding hysteresis range: 2.9 to 1.64V.  
 L<sub>1</sub> and L<sub>2</sub> can be adjusted to produce a required rise time with a defined overshoot for given capacitive loading. The same principle applies to the complementary Schmitt. With L<sub>1</sub> = L<sub>2</sub> = 0.11 $\mu H$ , rise time < 8ns with 5% overshoot at low switching rates.  
 The circuit functions to at least 40MHz with defined output levels although the waveform is rounded at high frequencies. Careful printed circuit layout is necessary for good high-frequency operation.


### TTL Schmitt circuit

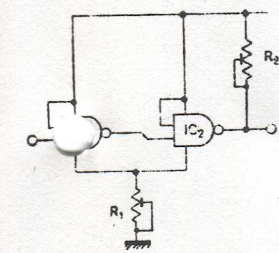
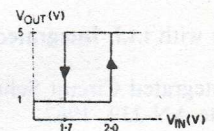
#### Performance data

Graph obtained with R<sub>2</sub>: 250 $\Omega$ , R<sub>1</sub>: 30 $\Omega$   
 Supply: 5V  
 ICs: 7400  
 Frequency 0 to 1MHz.  
 Threshold values and hence hysteresis may be changed slightly by varying R<sub>1</sub> and R<sub>2</sub>.

Lower limit (1V as shown) is affected by R<sub>1</sub> and R<sub>2</sub>.  
 With R<sub>1</sub> = 0 there is no positive feedback and switching is not clean.  
 With R<sub>2</sub> =  $\infty$  upper limit is reduced from 5V.



#### Circuit description


Each NAND gate with one input gate disabled behaves as an inverter. The circuit with positive feedback via R<sub>1</sub> is very similar to the basic Schmitt trigger as each gate is essentially identical. This results in the potential across R<sub>1</sub> being constant and independent of which inverter is enabled. This results in an offset voltage compensated by R<sub>2</sub>.

#### Component changes

Any t.t.l. inverter may be used.
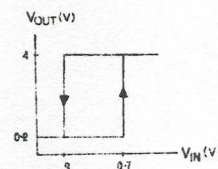
#### Circuit modifications

An alternative t.t.l. Schmitt is SN7413, produced by Texas, and has two in a single package. Typical characteristics are shown below. Frequencies up to several MHz can be handled, but ringing may occur beyond 100kHz if the circuit layout is poor.



### Circuit modifications

Precise adjustment of the negative rail voltage allows the output to be made truly t.t.l.-compatible with levels of 0V and +5V. The output from  $Tr_2$  may be used to feed a high-speed t.t.l. gate or an e.c.l. gate to "square up" the waveform at high frequencies. Circuits of this type may be useful in conjunction with t.t.l. or e.c.l. circuitry as they provide alternative options of switching levels and hysteresis. To assist supply decoupling at high frequencies, ferrite beads can be added to the supply line wiring.

### Further reading

E-Line Transistors Applications, Ferranti, 1969. p.20.  
MECL Integrated Circuit Schmitt Triggers, Motorola application note AN-239.

### Cross references

Series 2, card 2 & 8.

© 1972 IPC Business Press Ltd.

### Further reading

Electronic Circuit Design Handbook, Tab Books, 4th edition, p.129.  
Designing with t.t.l. Integrated Circuits, McGraw-Hill, 1971. pp.53-7.  
MECL Integrated Circuit Schmitt Triggers, Motorola application note AN-239, 1967.


### Cross references

Series 2, cards 2, 3 & 7.

© 1972 IPC Business Press Ltd.



### Low-voltage level sensor

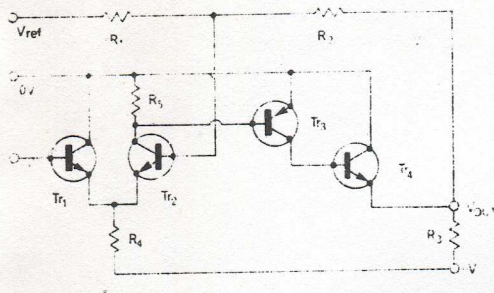

Supply: -12V  
 $V_{ref}$ : -1V  
 Tr<sub>1</sub>, Tr<sub>2</sub>, Tr<sub>4</sub>: BC125  
 Tr<sub>3</sub>: BC126  
 Switching levels  
 on: -1.35V  
 off: -1.03V

R<sub>1</sub>: 3.3kΩ  
 R<sub>2</sub>: 100kΩ  
 R<sub>3</sub>: 470Ω  
 R<sub>4</sub>: 82kΩ  
 R<sub>5</sub>: 10kΩ



#### Circuit description

Operation from single-ended supplies makes level-sensing of low voltages difficult (lower limit usually set by transistor  $V_{be}$ ). Taking signal and reference voltages with respect to opposite side of supply as shown allows much reduced triggering voltages. A long-tailed pair drives an inverting stage with positive feedback from the output to the non-inverting input. Input current is small, reducing to zero after switching. For positive-going signals, a complementary version using a positive supply voltage gives comparable results.

#### Component changes

- Supply voltage -5 to -25V, upper value depending on transistor breakdown. At lower voltages, switching levels become more supply sensitive. Reduce  $R_4$  at lower supply voltages to keep current in it to  $\sim 120\mu A$ .
- Reference voltage -200mV to -5V.
- Load currents up to 100mA possible with no change in circuit. Replacing  $Tr_4$  by higher rating transistor, and scaling all resistors down by factor of 5 allows load currents of up to 0.5A (BFR41, BFY50 etc).
- $Tr_1-Tr_4$  replaced by any general-purpose silicon planar transistors results in comparable performance: matched pair at input reduces drift.
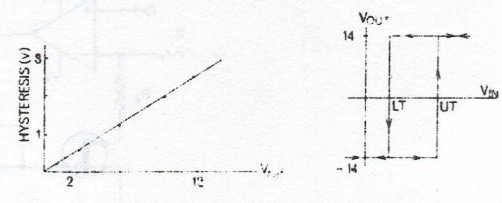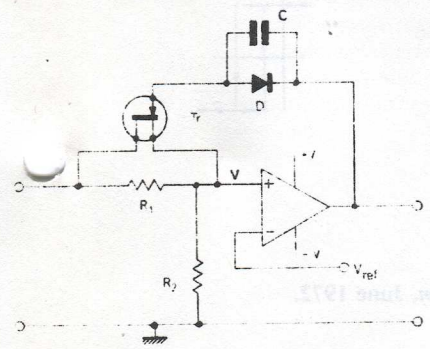
### Reference-controlled hysteresis circuit



#### Performance data


Graphs obtained with Supplies:  $\pm 15V$   
 Tr: Motorola 2N4092  
 D: 1N914, IC: 741  
 $R_1$ :  $5.6k\Omega \pm 5\%$   
 $R_2$ :  $27k\Omega \pm 5\%$   
 C: 100pF  
 Lower threshold (l.t.):  $V_{ref}$   
 Upper (u.t.):  $V_{ref} \cdot (R_1 + R_2) / R_2$   
 Hysteresis:  $V_{ref} R_1 / R_2$   
 Max. frequency: 300Hz  
 $V_{ref}$  must remain positive.

#### Circuit description

With a low  $V_{in}$ ,  $V_{out}$  is initially negative and the f.e.t. switch is off.  $V'$  is then given by  $V_{in} R_2 / (R_1 + R_2)$ . Increasing  $V_{in}$  until  $V'$  is just greater than  $V_{ref}$  causes  $V_{out}$  to change sign, the f.e.t. then conducts and shorts out  $R_1$  making  $V'$  equal to  $V_{in}$  and forcing  $V_{out}$  to become even more positive.  $V_{out}$  will only become negative again when  $V_{in}$  is reduced below  $V_{ref}$ . The positive feedback does not come into action immediately  $V_{out}$  starts to leave its saturated condition, so the output may lie between the saturated levels.
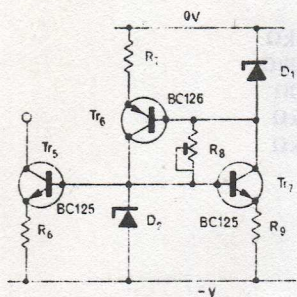
#### Component changes

Using a 748 op-amp the maximum frequency can be extended to 4kHz. National Semiconductor f.e.t. 2N3819/7127 may be used.  $R_1$  is chosen such that the f.e.t. on-resistance is much lower than  $R_1$  and the off-resistance is much higher than  $R_1$ . Varying  $R_1$  and  $R_2$  hysteresis of  $0.1V_{ref}$  and  $10V_{ref}$  can easily be obtained. Choice of diode and capacitor is not critical.



### Circuit modifications

- Reference and signal inputs may be interchanged if minimum current drain from reference is required.
- Replacing  $R_4$  by constant-current circuit minimizes shift of switching levels with varying supply voltage. Fig. shows a ring-of-two reference circuit biasing constant-current stage, and providing stable voltage across  $R_7$  to act as switching-level reference. Replaced by potentiometer for variable reference.
- Tapping  $R_2$  with a zener diode to 0-V line stabilizes hysteresis without limiting output voltage swing.
- For light loading  $Tr_4$  may be omitted.


### Further reading

- Williams, P., Low-voltage level-sensing circuit, *Electronic Engineering*, 1968, pp.517-9.  
 Callahan, M. J., Integrated level detector, *IEEE Journal of Solid-State Circuits*, vol. SC-7, 1972, pp.185-8.

### Cross reference



Series 2, cards 6, 10 & 11.

© 1972 IPC Business Press Ltd.

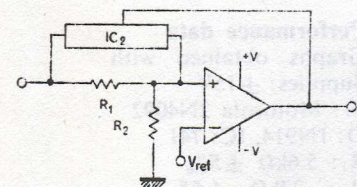
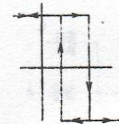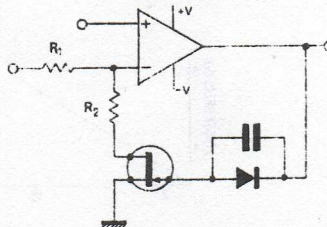
### Circuit modifications

- With a negative  $V_{ref}$ ,  $V'$  should be connected to the inverting input and  $V_{ref}$  to the non-inverting input to obtain the positive feedback switching action.
- With a low reference voltage and low supply voltage (e.g.  $<1V$  with  $\pm 5V$  supply), f.e.t. pinch-off voltage causes unsatisfactory switching. The f.e.t. and its associated diode and capacitor may be replaced by a c.m.o.s. switch, left. The switch used was CD4016AE, the minimum  $R_1$  in this case being about  $10k\Omega$ .
- For applications where  $V_0$  is required to be positive, for positive  $V_{ref}$  and small  $V_{in}$ , one may use the circuit on right, the resulting characteristic being as shown on right. The formulae for the upper and lower thresholds and the hysteresis are the same as those for the original circuit.



### Further reading


G. S. Oshiro, *Electronic Design*, June 1972.

### Cross reference

Series 2, cards 4 & 6.


© 1972 IPC Business Press Ltd.

### 'Window' detector

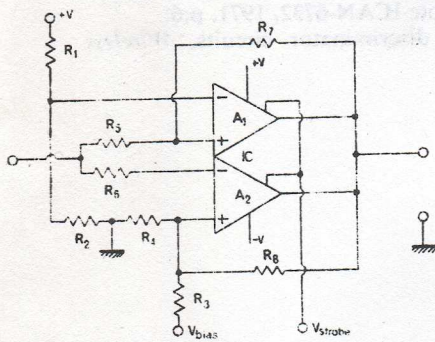

**Typical performance**  
 IC: 711  
 Supplies +12V, -6V  
 $V_{\text{strobe}} = +5\text{V}; V_{\text{bias}} = -12\text{V}$   
 $R_1, R_3: 5.6\text{k}\Omega$   
 $R_2, R_4, R_5, R_6: 470\Omega$   
 $R_7, R_8: 22\text{k}\Omega$   
 $V_{\text{OU}} = 953\text{mV}; V_{\text{OL}} = 886\text{mV}$  (i.e.  $V_{\text{OU}}$  hysteresis = 67mV)  
 $V_{\text{U}} = -946\text{mV}; V_{\text{L}} = -879\text{mV}$  (i.e.  $V_{\text{OL}}$  hysteresis = 67mV)

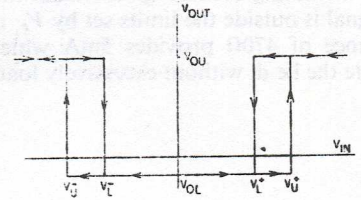$V_{\text{OU}} = +4.4\text{V}; V_{\text{OL}} = -0.4\text{V}$  (inputs commoned)  
 Supply current: +11.5mA, -5mA  
 Strobe current: 76μA  
 Bias current: 2.2mA




#### Circuit description

A<sub>1</sub> is a non-inverting comparator having a positive reference level ( $V_r$ ) set by  $R_1$  and  $R_2$ . Amplifier A<sub>2</sub> is an inverting comparator having a negative reference ( $V_r$ ) set by  $R_3$  and  $R_4$ .  $V_{\text{out}}$  remains at a low level when  $V_r < V_{\text{in}} < V_r$ , and A<sub>2</sub> is capable of switching its output to  $+V_{\text{OU}}$  when  $V_{\text{in}} < V_r$ . As the outputs of A<sub>1</sub> and A<sub>2</sub> are common,  $V_{\text{out}} = +V_{\text{OU}}$  when  $V_{\text{in}} < V_r$ , or when  $V_{\text{in}} > V_r$ . Hysteresis is introduced by the positive feedback on A<sub>1</sub> (by  $R_7$  and  $R_5$ ) and A<sub>2</sub> (by  $R_8$  and  $R_4$ ). See transfer characteristic above. From an output level viewpoint the circuit is t.t.l. compatible.

#### Component changes

Maximum useful frequency  $\approx 1\text{MHz}$ .  
 $V_{\text{OU}}$  may be varied over the range +0.4 to 4.4V by setting  $V_{\text{strobe}}$  in the range +1 to +5V.  $V_{\text{OL}}$  remains fixed at -0.4V. Variation of  $R_1$  and/or  $R_3$  provides independent control of the positive and negative threshold levels. Minimum useful value of  $R_1$  and/or  $R_3 \approx 700\Omega$ .  
 Minimum load resistance (for 10% reduction of  $V_{\text{OU}}$ )  $\approx 680\Omega$ .

### Complementary Schmitt

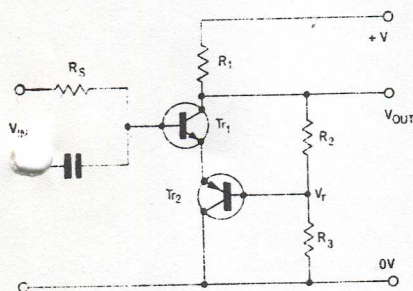

#### Circuit description

This is a complementary form of circuit using emitter coupling, as in the classic Schmitt. Neither transistor conducts for low input voltages. When  $V_{\text{in}}$  exceeds  $V_r + 2V_{\text{be}}$ , both transistors conduct causing the output voltage to fall regeneratively. With suitable resistance values, the supply current in the off state can be made much less than in the on state.

#### Typical data

$V_{\text{in}}(\text{on}) = V_r + 2V_{\text{be}}$   
 Supply: +12V  
 $\text{Tr}_1: \text{BC125}; \text{Tr}_2: \text{BC126}$   
 $R_1, R_3: 1\text{k}\Omega; R_2: 10\text{k}\Omega$   
 $R_5: 100\Omega; C_1: 0.1\mu\text{F}$   
 $V_{\text{in}}(\text{on}) = 2.16\text{V}$

$V_{\text{in}}(\text{off}) = 1.59\text{V}$   
 hysteresis = 0.57V  
 $V_{\text{O}}(\text{on}) = 1.0\text{V}$   
 $V_{\text{O}}(\text{off}) = 11\text{V}$   
 Supply current:  
 10.5mA (on), 1mA (off)

#### Component changes

- Varying  $R_2$  in the range 5 to 20kΩ allows the hysteresis to be adjusted within the range 1.16 to 0.21V, without significantly changing  $V_{\text{in}}(\text{off})$ .  $V_{\text{in}}(\text{on})$  correspondingly varies in the range 2.81 to 1.74V.
- If Tr<sub>2</sub> is a high-current-gain transistor  $V_{\text{in}}(\text{off}) \approx 2V_{\text{be}}$ ; with a lower gain transistor  $V_{\text{in}}(\text{off})$  will be increased due to the significant p.d. across  $R_3$  produced by Tr<sub>2</sub> base current.
- A speed-up capacitor of about 27pF across  $R_2$  improves the turn-on time from about 90ns to 30ns. Turn-off time is typically 90ns. Maximum useful frequency is typically 2MHz.

### Circuit modifications

- Where hysteresis is not required the positive feedback resistors may be omitted.
- A visible-light-emitting diode connected to output terminal through a limiting resistor gives visual indication when the input signal is outside the limits set by  $V_{r1}$  and  $V_{r2}$ . Typically a resistance of  $470\Omega$  provides  $5\text{mA}$  which is sufficient to illuminate the l.e.d. without excessively loading the IC.

### Further reading

- Application of linear microcircuits. SGS, 1969. pp.105-6.  
Op-amp circuit collection, National Semiconductor application note AN-31, 1970, p.3.  
Measurement of burst ("popcorn") noise in linear integrated circuits, RCA application note ICAN-6732, 1971. p.6.  
Cole, H. A., Differential discriminator circuits, *Wireless World*, 1971, pp.603-4.

### Cross references

Series 2, card 6.

© 1972 IPC Business Press Ltd.

### Circuit modifications

A  $47\text{-}\Omega$  resistor included in series with the 'free collector' of  $\text{Tr}_2$  provides a complementary pulse output. These pulses typically have an amplitude of  $0.6\text{V}$  (with a  $12\text{-V}$  supply) i.e. sufficient to drive a following transistor or thyristor.  $\text{Tr}_1$  will still saturate and  $\text{Tr}_2$  will remain unsaturated. The value of this resistor may be considerably increased if it is returned to a separate negative supply. With a value  $\leq R_1$  a second output is then available without significantly changing the circuit action.

### Further reading

- Hemingway, T. K., *Electronic Designer's Handbook*, Business Books, 1970, 2nd edition, pp.177-181.  
Feinberg, R., *Handbook of Electronic Circuits*, Chapman and Hall, 1966, p.52.

### Cross references

Series 2, cards 2 & 5.

© 1972 IPC Business Press Ltd.